

JUNE 1976 \$1.00\*  
NZ \$1.15

# electronics

## TODAY

INTERNATIONAL



**Train controller**  
**5 watt stereo**  
**Novice transmitter**

*Registered for posting as a periodical - Category C*

# HOW TO CHOOSE MICROPHONES





# A turntable with features you'd expect only on a more expensive unit

One feature you'll notice is the price; in fact we believe it to be 'the best buy' turntable available today.

With features only expected on more expensive units, such as wow and flutter of 0.5 WRMS thanks to the DC motor with FG (frequency generator) servo-controlled circuits.

How's this for a list of features. Practical, purposeful features like

- illuminated stroboscope
- elliptical stylus

- completely automatic tone arm return
  - viscous-damped cueing lever
  - anti-skating dial scale control
  - CD4 ready
  - audio insulated legs
- and the list just goes on.

Any way you want to look at it, you'll agree the Technics SL23 is a sound buy, with appearance and performance to match.



For a National Technics Catalogue please write to:  
National Technics Advisory Service, P.O. Box 49, Kensington, N.S.W. 2033.



# Technics

by National

WT GD 105 T



# electronics TODAY

INTERNATIONAL




A MODERN MAGAZINES PUBLICATION

JUNE 1976, VOL. 6 No. 6



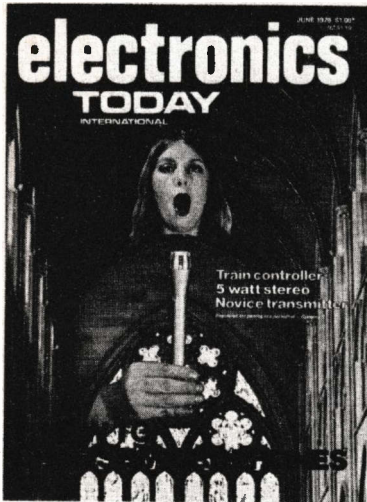Editorial Director Collyn Rivers  
Assistant Editor Steve Braidwood



\*Recommended retail price only

COVER: Microphone survey on page 16. Photo composition by George Hofsteters.

## PROJECTS

- FIVE WATT STEREO** .....44  
*Good hi-fi with just two ICs and a few bits & pieces*
- MODEL TRAIN CONTROLLER** .....51  
*Speed control, inertia stop/start, emergency stop, etc.*
- NOVICE TRANSMITTER** .....71  
*Full constructional details for an 80m rig*

## FEATURES

- HOW TO CHOOSE A MICROPHONE** .....16  
*The different types and their uses*
- ANTENNAS** .....29  
*Final half of Roger Harrison's practical guide*
- COMPONENT CODES** .....34  
*The logic behind the system*
- ELECTRONICS IT'S EASY!** .....84  
*From computer to microprocessor*

## DATA SHEETS


- LM382 low-noise stereo preamplifier IC** .....58
- BD266 & BD267 high power Darlington transistors** .....60
- LM379 six-watt plus six-watt audio IC** .....64

## NEWS & INFORMATION

- |                              |         |                         |          |
|------------------------------|---------|-------------------------|----------|
| News                         | .....5  | Ideas for experimenters | .....99  |
| Calculator contest           | .....14 | Audio facts             | .....109 |
| Special offer: calculator    | .....67 | Reader services         | .....118 |
| Special offer: clock/watches | .....96 | Advertisers' index      | .....118 |

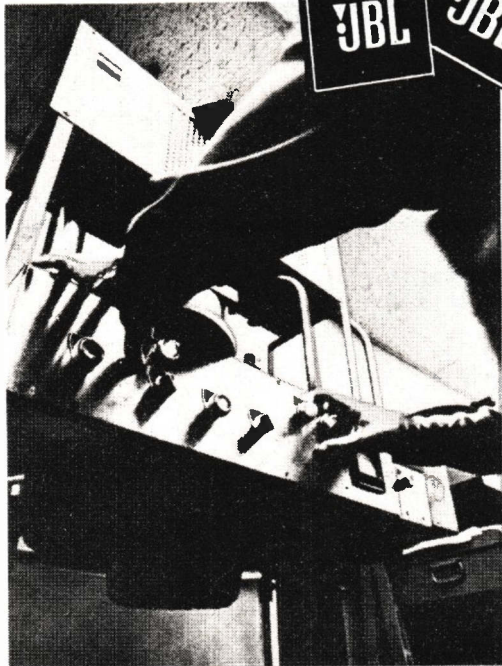
# Hand made sound.

With JBL you know you're not just paying for the name. You're paying for a quality of sound that is impossible to mass produce.



JBL's require equipment so specialised we had to design and build our own.

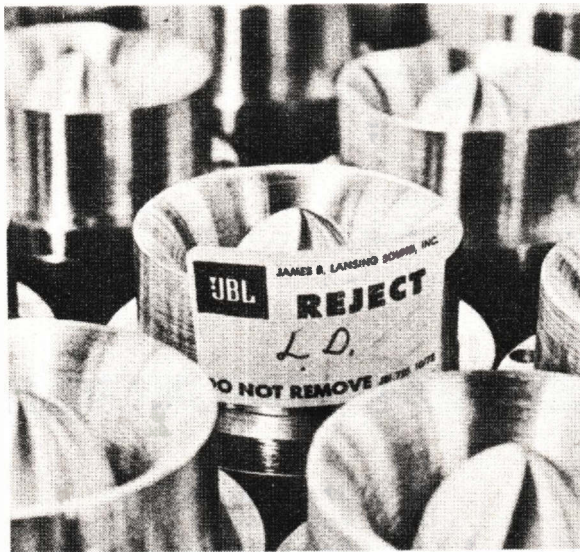If we cut out all the things we do by hand, and the checking double checking and rejecting, we could probably produce a speaker for about 25% less. But then it wouldn't really be a JBL. Our reputation is based on an unchanging commitment to quality. We make no compromises. Never have, never will. The same applies to all the JBL range. Like the JBL Decades.




Near enough is just not good enough.



Cabinet tolerances are typically held to 1/64th of an inch.

Until we developed them just recently, most JBL's were out of the normal person's reach. Now you can own a pair of JBL's for around \$500.

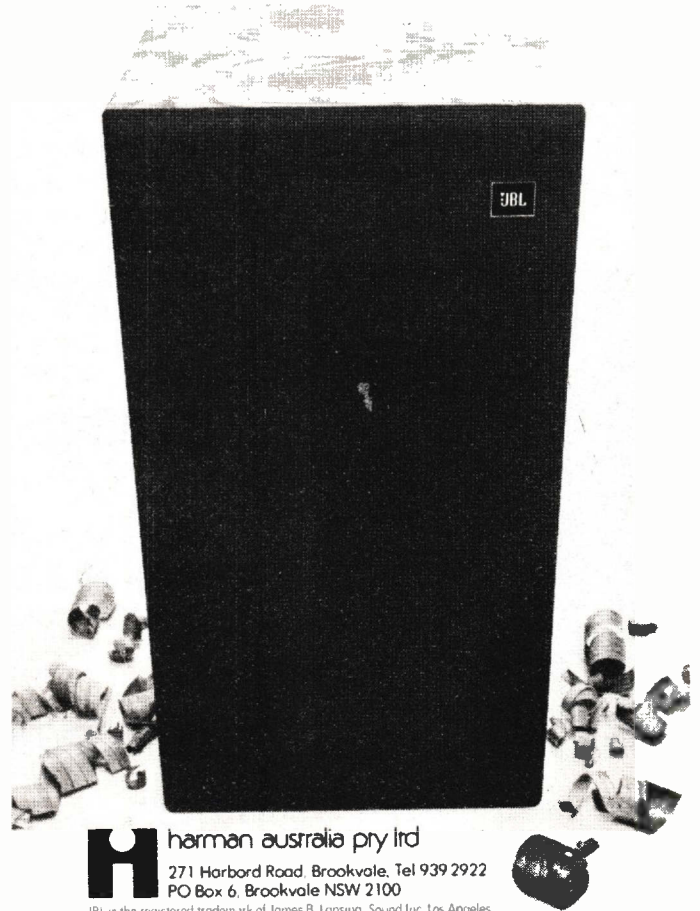They're still more expensive than ordinary speakers, but then they're JBL's aren't they.



**h**armon australia pry ltd  
271 Harbord Road, Brookvale, Tel 939 2922  
PO Box 6, Brookvale NSW 2100

JBL is the registered trademark of James B. Lansing Sound Inc. Los Angeles





## IR FOR THE HARD OF HEARING

A wireless infrared communication system for use in classrooms for the hard-of-hearing has been developed by Siemens. Being free of cables and leads, the pupils can move about unhindered and yet be in constant touch with the teacher, via their headphones. The system is superior to the induction systems previously used in that the transmission

is contained within the walls of one classroom.

In the classroom there are four infrared radiators, which are either fixed on mobile stands and placed around the room or mounted on the walls or ceiling. Each radiator has twelve LEDs; the 48 diodes are sufficient to ensure that a classroom measuring about 80 sq metres is evenly "illuminated". The total power of the radiation is only 0.5 watts.

## MICROSURGERY CAMERA

The potential of TV as a teaching aid was demonstrated recently at an International Microsurgery Workshop in Sydney, attended by about 30 surgeons from abroad and Australia. By means of a Hitachi compact colour TV camera linked to a high power microscope, microsurgical techniques were shown on colour TV monitors, and the surgeons were then able to copy the methods shown on the screens.

The demonstrators used a Zeiss microscope with a Hitachi 9015 camera mounted integrally to the viewing optics. This was the first demonstration in Australia of this camera from AWA Rediffusion, recently appointed a distributor of Hitachi closed circuit television products in Australia. The Hitachi 9015 is about 100 mm square and 220 mm long. More details from AWA Rediffusion Pty. Ltd.



## ELECTRONICS SHOW

Australia's first consumer Electronics Show is to open in Sydney this August. The show, to be held in the Sydney Hilton, is sponsored by the High Fidelity Association and supported by Hi-Fi Review. It will include seminars and the first conference of Australia retailers. The show will be open to the public for limited periods.

## 30 MINS OF TV ON A CARD!

A photosensitive plate, 127 x 178 mm, costing about 25c to make, can store a digitised TV programme. The Digital Recording Company of New York already has a prototype and plans to make pre-production units available in about a year. The company estimates that playback equipment could cost as little as US\$300.

The system uses microscopic dots and spaces, at a density of 300 000 000 bits per square inch, to record the data.

## TIME DELAY PROBLEMS

We apologise to readers who had to wait longer than usual for their May issue. The delay was a result of production problems we were facing at that time and for the next few issues ETI will not appear in the shops until the beginning of the month on the cover.



## SINGLE MASK BUBBLE MEMORY

In magnetic bubble memories that are controlled by current pulses and a rotating magnetic drive field, three or more masks are needed for processing one chip. The Philips Research Laboratories in Eindhoven have made an experimental bubble memory requiring only one mask per chip. Writing, reading and erasure are achieved by temporary changes of the sense of rotation of the drive field.

## ONE WATCH, TWO DISPLAYS

Now available in the US is the new Pulsar men's watch from Time Computer. This watch uses separate LED displays for time and day of the week. By not adapting seven-segment displays for alpha characters the letters are given a more readable shape.

## KODAK INSTANT ELECTRONICS

Kodak's new instant cameras are using a four-function bipolar linear IC to control aperture selection, shutter speed, and indicators for flash required and low battery. The eight pin transparent plastic DIP also includes a silicon photo diode.

## ELECTRONIC ALARM WATCH

The Japanese manufacturer, Citizen Watch, are marketing (overseas at the moment) an LCD watch which displays hour, minutes and seconds, and in addition has an alarm facility.

## VOICE CONTROLLED COMPUTER FOR NAVY

EMI Threshold Ltd has delivered its third voice-operated computer system to the UK Ministry of Defence. This system, which is operated and controlled solely by human speech, is to be used by the office of the Hydrographer of the Navy for digitising feature information of navigational charts.

## CB SELF-LICENSING

The FCC has introduced a temporary system to cope with the flood of applications for CB licences. The applicant simply fills in a form and makes a call-sign by taking the letter K, adding his initials, and then his zip code.

## HP27

A new pocket calculator combining the most frequently used scientific, statistical and financial functions has been introduced by Hewlett-Packard. The HP-27, priced at \$217.00 including tax, (\$195.00 excluding tax), contains more preprogrammed functions and operations than any other HP pocket calculator.

The HP-27 is the first pocket calculator to incorporate tools to perform most scientific calculations as well as financial capability. For the business person, the calculator provides a combination of compound interest and statistical capabilities.

The HP-27 provides several new functions: in statistics — variance, correlation coefficient and normal distribution; in finance — net present value and internal rate of return for up to 10 uneven cash flows. Ten addressable memories for data storage, five financial memories, the last-x memory and the



four operational stack memories allow the user to make complex, lengthy calculations without having to record intermediate answers or re-enter constant data. Six selectable clearing options increase the flexibility of use of the calculator's memories.

Customer deliveries will begin within four weeks from Hewlett-Packard Australia Pty. Ltd., 31-41 Joseph St. Blackburn, Vic 3130.

## GILLETTE WATCHES

Gillette, the razor company, has ordered digital watch modules for LED watches they plan to market later this year in the US.



## NEW TEKTRONIX TERMINAL

The lowest priced computer graphics terminal from Tektronix, the 4006-1, has been announced recently. The 4006-1 is compatible with most main-frame computers and it will be supported by the same graphic software available for Tektronix' complete family of graphic terminals, plus a new Interactive Graphing Package.

Hard copy compatibility is included using the Tektronix 4631 hard copy unit. Off-line storage can be provided by the Tektronix 4923 Digital Cartridge Tape Recorder.

The crisp, clear (800,000 point) graphics and the low price is expected to invite both OEM accounts and end users.

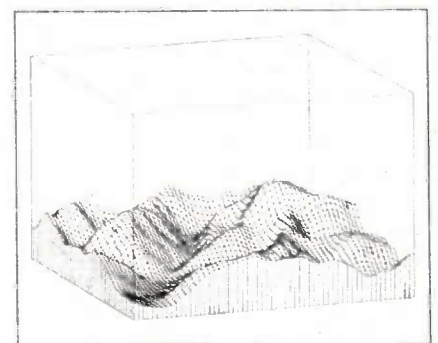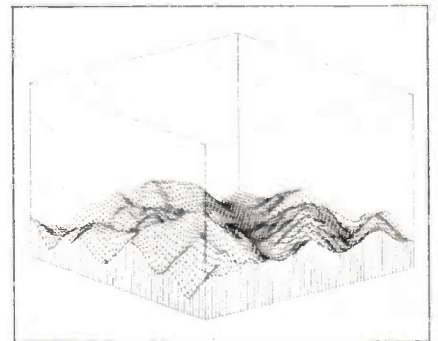The newly-developed Interactive Graphing Package enables the non-programmer to generate on-screen single and multiple line graphs, bar charts, log plots and calendar plots. Additional features of this package include automatic sealing and interactive labelling.



*These two plots show a digitised perspective of a landscape constructed from a contour map. The two views are of the same area: one from the southeast and one northwest. The user can rotate the plot for any view.*

*(Continued on page 11)*



# The **CONVOY** BIG 'C' Story



New premises, 4 Dowling Street Sydney. Free Parking Opposite

In the space of three months a remarkable change has been made to an old building at the wharf end of Dowling Street, Woolloomooloo, where Convoy has moved from their smaller premises nearby. It has been completely renovated and transformed into a complex of showrooms to demonstrate and supply high quality High Fidelity equipment and Colour T.V., in three separate acoustically treated rooms, Audio Visual Programming studios, an A.V. Theatrette, Administration, and well equipped Service facilities. Ample space is available for Convoy's activities in the Wholesale distribution of TDK Tape and top line Hi-Fi equipment.



Entrance Foyer to Convoy Sound

**Convoy**  
New Premises  
with the  
**BIG 'C' Motif**  
at  
Woolloomooloo



# The Convoy Sound Story

**CONVOY SOUND** – This is the new trading name by which retail activities will be known in future – previously The Technocentre. For Hi-Fi enthusiasts considering the purchase of quality equipment, a visit to Convoy Sound provides the opportunity to hear a wide range of famous brands, listen in comfort without the intrusion of traffic noise or other equipment and talk with experienced sales staff. Clients may park at the Shell Service Station opposite without charge. The three acoustically treated demonstration rooms enable clients to hear equipment as it would sound in their home environment.



**THE B & O ROOM** – As you enter the new showrooms on your left is a demonstration suite entirely devoted to Bang & Olufsen equipment, attractively designed in a Scandinavian decor and natural Pine. Convoy are the B & O specialists in the Sydney area for the Danish Bang & Olufsen (B & O) equipment. A company that enjoys the highest reputation for design orientated High Fidelity equipment and what are regarded by many as the finest colour T.V. sets in the world.

**THE SWINGER'S ROOM** – Ahead of you the "Swinger's Room" is a complete contrast with its bright and exciting decor. This suite has been set aside for the more popular medium and upper quality equipment from selected and famous brands which include B & W, Harman Kardon, J.B.L., Marantz, Nakamichi, Peerless, Pioneer, Sonab, Teac, Technics etc. A room designed for the young enthusiasts and those interested in the modern trends of music.



**CONNOISSEUR'S ROOM** – A few steps to the right and you walk into the "Connoisseur's Room", quietly elegant in its decor, this suite has been established for the sound perfectionist, who may sit in a quiet relaxing atmosphere and experience the subtle differences that are to be heard in the world's best amplifiers, tape decks and loudspeakers.

No one who is considering a really top quality system, or who wants to measure their own system against the best, should miss visiting this unique sound demonstration.



# Convoy

## Products & Services

**TDK** Magnetic Tapes



Nakamichi  
Spoken  
Here

Cassette Recorders

**B&W Loudspeakers**

*Accuphase* Amplifiers

**ELECTROSONIC**

### TDK Magnetic Tapes and Cassettes

Convoy are the exclusive distributors in Australia for TDK Electronics Co. Limited, one of the world's leading manufacturers of magnetic tape. Founded in 1932, today TDK is renowned the world over for its magnetic tape technology and its complete lines of Audio, Video and Computer grade tapes of unsurpassed quality.



Audio Visual Demonstration Theatre



Nakamichi Research Inc. is now generally accepted as the world leader in design and manufacture of cassette recorders with a quality equalling the best reel-to-reel tape recorders.

### Bowers & Wilkins (B & W) Monitor Loudspeakers

John Bowers who founded B & W just over 10 years ago has been a pure sound fad for many years. All B & W speakers are designed to produce clean natural uncoloured sound without distortion. The latest product from B & W, the DM6, has been described as the finest domestic loudspeaker yet produced.

Convoy Service Division

### Accuphase Amplifiers and Tuner Amplifiers

Accuphase design philosophy greatly reflects the origin of its brand name. It is derived from the two words, "ACCURATE" and "PHASE". Accuphase equipment can even be likened to a rare "Stradivarius". At least, that is how much stress is attached in manufacturing policy to originality and handcraftsmanship.

### Electrosonic

Electrosonic Limited London, England, are one of the leading designers and manufacturers of electronic control equipment for synchronised slide/sound Audio Visual presentations.

Audio Visual Encoding Studio





# THE CONVOY STORY

## Company Growth Built on Quality

Convoy was founded in March 1965 by its Chairman Malcolm Goldfinch in Kent Street, Sydney. He maintains a close interest in the business and makes frequent trips overseas to keep in touch with new product development and the manufacturers Convoy represents in Australia. The Company achieved steady growth during its early years which first made necessary its move to Maclean Street, Woolloomooloo. Progress accelerated over the past three years requiring much larger premises.

The firm's Managing Director, Dennis Gowing who joined Convoy in January 1973, attributes the Company's growth largely to the careful selection of outstanding products to represent — all are market leaders in their respective fields, yet complimentary to each other. Dennis Gowing says, "By specialising in top quality equipment, the reputation of Convoy can only stand or fall on the excellence and performance of the equipment and services the Company presents to its clients". "For this reason irrespective of the manufacturer's Warranty, our technicians carefully test all items of equipment sold prior to sale and in many instances we offer our own Warranty which exceeds the manufacturer's Warranty. For example, Convoy offers a 5 Year Warranty on some top quality amplifiers".

## Why Woolloomooloo?

Convoy requires considerable space and parking for its various activities. In a City location the noise of traffic impairs the effective use of demonstration rooms, city parking is difficult and costly for clients and staff, and high city rents would make it difficult to hold down prices.

Convoy's management decided to remain in the area where they had become so well known over the last six years, as Woolloomooloo is conveniently located only eight minutes away from the production, advertising and promotional world in North Sydney, City Professional Investment and Commercial areas, Macquarie Street Doctors and still within easy reach of Kings Cross and the Eastern Suburbs.

Clients contemplating the purchase of top quality Hi-Fi equipment, or involved in the encoding of an Audio Visual programme or planning a Multi-Screen presentation, will find Convoy easy to identify with its attractive and very distinctive "Big C" exterior building decoration.

## Company Organisation

Convoy is organised into autonomous yet complimentary Divisions.

**Convoy Sound** handles the Retail activities of the Company

**Convoy TDK Division** is responsible for the Australia wide distribution of TDK tape.

**Convoy Wholesale Division** handles the exclusive distribution of top quality Hi-Fi equipment.

**Convoy Electrosonic** handles the sale and hire of Electrosonic equipment for Audio Visual presentations.

**Convoy Service** provides technical service back-up to all Convoy Divisions also Warranty and other service to clients.

## Convoy Sound

is the new trading name by which the retail activities will in future be identified. The main showrooms and demonstration rooms are located on the Ground Floor at 4 Dowling Street, Woolloomooloo, Sydney. A smaller City showroom devoted exclusively to Bang & Olufsen equipment, was recently opened at 387 George Street at the rear of Dukes Records.

In the Dowling Street premises all the demonstration rooms are acoustically treated to resemble the acoustics in your own home. Although they are just a few paces from each other, they enclose you completely in their own special and separate worlds of sound. Being free of ambient noise from traffic one can listen undisturbed and at peace and judge the quality of sound at low volume as you would use in your own home. Dennis Gowing says, "You cannot demonstrate top quality Hi-Fi equipment against a background of traffic noise or with other equipment operating in the same showroom".

## TDK Tape Division

Convoy are the exclusive distributors in Australia for TDK ELECTRONICS CO. LTD 'one of the world's leading manufacturers of top quality magnetic tape. TDK are credited with bringing about a "revolution" in tape technology which turned the cassette into a true high fidelity medium. TDK's latest breakthrough in tape technology is Super Avilyn — SA. An entirely new magnetic particle completely interchangeable with Chromium Dioxide, but with superior sensitivity in low and middle frequencies and much reduced headwear. Authoritative commentators have said that Super Avilyn tape looks like being one of the most important advances in tape formulations in the mid-seventies.

## Wholesale Division

Executive offices and wholesale trade displays are located on the First Floor. This Division handles the Australia wide distribution of top quality Hi-Fi equipment including world renowned brands such as Bowers & Wilkins Loudspeakers, Nakamichi Tape Decks and Accuphase Amplifiers.

## Convoy Electrosonic

A major portion of the First Floor is given over to Convoy's Electrosonic Division. If you plan a marketing seminar, an exhibition or permanent Audio Visual installation, here you will find experts to advise you, a theatre to demonstrate and discuss your requirements, and a fully equipped A.V. encoding studio. A wide range of equipment for single or multiscreen synchronised Slide/Sound Audio Visual presentations is available, either on outright sale or rental. Convoy Electrosonic equipment is in use at ● Hunter Douglas Domus ● Regatta Point Exhibition Canberra ● O.T.C. Theatre Broadway Sydney ● L.J. Hooker auction rooms Sydney ● C.S.I.R.O. Observatory Parkes etc. etc.

Clients for whom Convoy have handled touring A.V. presentations includes A.N.Z. Bank ● Ford Motor Company ● Liptons Tea ● G.E. ● S.C. Johnson ● National Bank ● Hoover ● V.W. etc. etc.

## Convoy Service

Convoy's technicians have the service capability and experience to handle the most complex electronic audio and audio visual equipment. A large well equipped Service Department is located on the Top Floor of the new building.

Convoy is made up of a young enthusiastic team of competent executives, all specialists in their respective areas. They have, at their disposal probably the best facilities for demonstrating top quality sound and Audio Visual equipment in Australia, if not the Southern hemisphere. The products they represent are world leaders in their respective areas.

## CONVOY INTERNATIONAL PTY LIMITED,

*A complete service for quality high fidelity, colour T.V. and audio visual equipment.*

**MAIN SHOWROOMS**  
4 Dowling St., Woolloomooloo  
Sydney 2011.

**Tel: 357 2444 358 2088.**  
**Telex AA23111**

**B&O  
CITY SHOWROOM**  
387 George St., City  
(in Dukes Records)  
**Tel: 29 1364**



## NEW GENERAL COVERAGE RECEIVER FROM YAESU MUSEN

A new general coverage receiver has appeared from Yaesu Musen. It is the FRG-7, based on the design of the Wadley Loop drift cancellation circuit. It covers the range 0.5 – 30 MHz continuously in 1 MHz bands, with dial readout of better than 5 kHz.

The FRG-7 accepts any of three power sources: 230 V ac, external 12 V dc and internal 8 dry cells. The FRG-7's Wadley loop system, coupled with its triple conversion superhet circuit provides an extremely high sensitivity and excellent stability.

The Australian agents for Yaesu Musen are Bail Electronic Services, 60 Shannon Street, Box Hill North, Vic 3129.

## DIGITAL WATCH WITH HANDS!

A Swiss company, Zenith Time, have a digital watch which looks like a conventional 'analogue' watch: it displays the time on ordinary watch hands. Below and to the right of the dial there is a small LED display which can show seconds, date, or am/pm. Setting of either section is by push-button.

## ALI'S THE LOUDEST


High volume speakers of the future are likely to be made from aluminium. The moving elements (the cone and voice coil) of speakers used by rock bands frequently overheat and fail. A division of US's Keene Corporation has recently developed an adhesive-coated aluminium foil for use in these sensitive components.

## RF SWEEP GENERATORS

Two new RF sweep generators have been announced by Tektronix: SW 503 (50Ω) and the SW 503 Option 1 (75Ω). Both generators cover a frequency range of 1 to 400 MHz. They have variable sweep rate, step attenuator, 20 dB vernier attenuator, and a crystal controlled marker generator which provides comb type markers at 1, 10, and 50 MHz.

A unique feature when used in conjunction with a DC 502 Digital Counter (with option 7 installed) is their ability to provide a variable marker covering the entire 1 to 400 MHz frequency range with the marker frequency read directly on the digital counter.

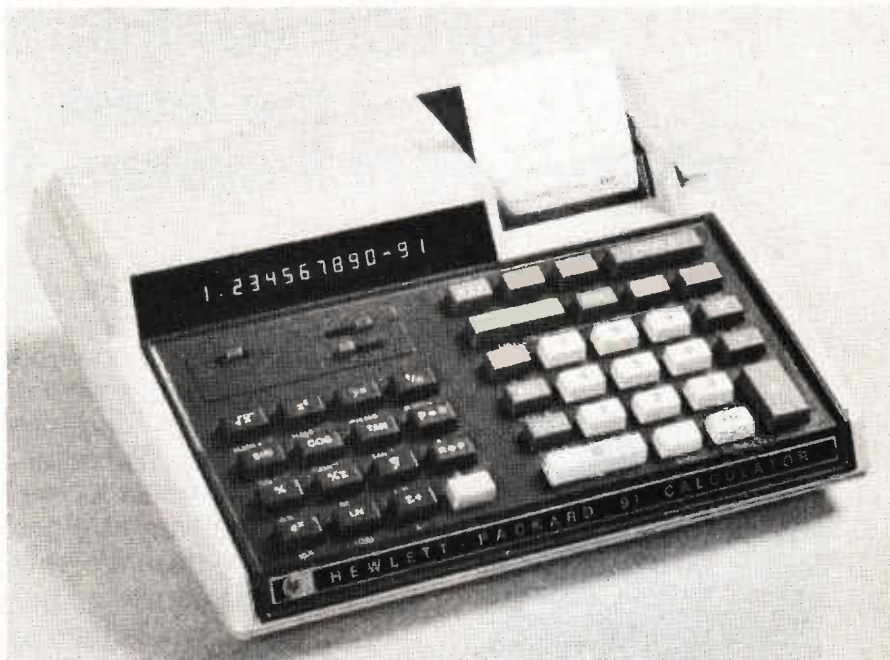The picture shows the SW503 (Option 1) in the TM 515 power module with DC502 (Option 7) counter, DM502 Digital Multimeter and SC502 scope. Tektronix Australia, 80 Waterloo Road, North Ryde, NSW 2113.



## PORTABLE PRINTING CALCULATOR


The first of a new generation of small, portable printing calculators operating on rechargeable batteries or line current was introduced by the Hewlett-Packard recently. The HP-91, priced at \$487 (\$541.79 including sales tax, if applicable) is an advanced scientific calculator with a large display and a buffered keyboard (so data may be keyed in at high speed).

The 1.2 kg calculator is small enough (229 x 203 x 64 mm) to fit into a briefcase for travel or a desk drawer for security. The HP-91 is a more powerful version of the HP-45 pocket calculator, with the added capability of creating a printed log of all calculations. It has all of the preprogrammed functions

of the HP-45, plus 16 addressable memory registers instead of 9; engineering notation; performs regression and linear estimates; three percent functions instead of two; and keyboard buffering seven keystrokes deep.

A 220-page owner's handbook is included with the calculator. It contains user instructions and a comprehensive application section that gives the most efficient keystroke sequences for solving problems in the fields of mathematics, statistics, finance, navigation and surveying. An AC adapter/recharger and a carrying case also come with the new calculator.

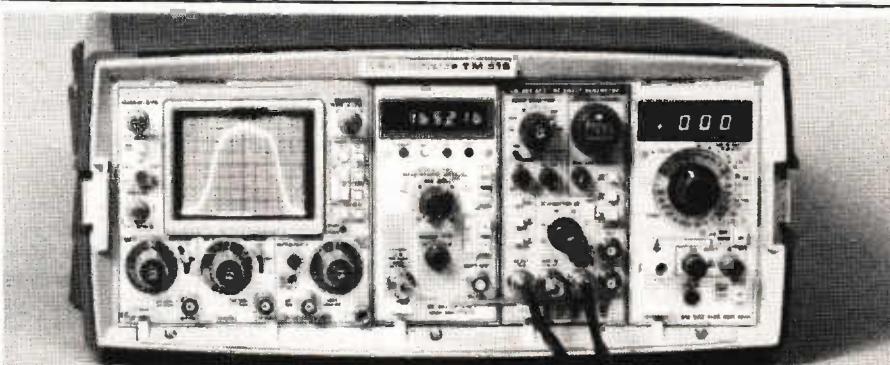The HP-91 is available approximately four weeks after receipt of order from Hewlett-Packard Australia Pty Ltd., 31 Joseph St., Blackburn, Vic 3130.





---

# New Rondo 3000X

From Convoy International-  
the latest  
'silver-look' hi fi system from Pioneer.

It must be the last word in stereo systems.  
A rare marriage of design purity and sound excellence.

In the Rondo 3000X, the imposing receiver-amplifier hits a new peak in functional elegance. The turntable is precise in profile. While the 3-way, 3 speaker system has a clean-cut brilliance. In this new Rondo, 'X' marks the difference between today and the exciting sounds of tomorrow.



Covered by exclusive  
Pioneer 1-2-3 warranty.

**\$489**

See it now...hear it now at  
**Convoy International** PTY.  
LTD.

4 Dowling Street, Woolloomooloo. 2011  
Telephone 358-2088.

 **PIONEER®**  
leads the world in sound

PN101




## ADD YOUR OWN COLOURS

A video colourising device is now available from Fairlight Instruments. The Fairlight Colour Synthesiser, Model 108, generates a six colour image from a standard black and white video source. Each selected colour is allocated to one of six grey-scale ranges, between black and white.

Video production units can use this equipment to add any desired colours to B/W or colour film, or videotape. The 108 is especially useful for graphics and animation. Startling effects can be achieved by selecting unusual or complementary colours.

An interesting feature of the 108 is that the colour turnover points (the grey level at which one colour changes to another) are variable. Setting up is facilitated by a switchable reference band test pattern. The colours and turnover points are displayed in order of grey-scale value across the top of the output picture.

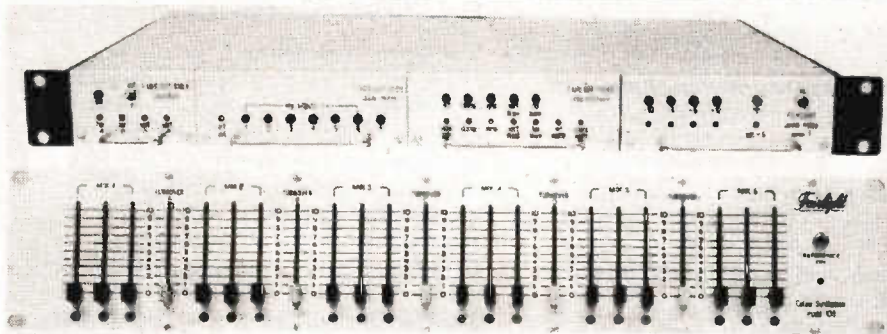The unit can generate its own sync and blanking, if required, allowing a



complete colourising system to comprise a black and white camera, a colour monitor and the 108. For studio situations sync and blanking can be accepted externally.

For further information contact Fairlight Instruments Pty Ltd., 15 Boundary Street, Rushcutters Bay, NSW 2011. Telephone 31-3606.

## RAIL FORCE TRANSDUCER

British Rail scientists have developed a simple method of measuring the internal rail force of a long length of rail in service. Until now there has been no reliable means for determining the force



other than by cutting the rail and measuring the resultant change in length. This method does not require cutting the rail.

The transducer is a cylinder 29 mm in diameter (the standard fishbolt hole size on BR). The transducers operate on the vibrating wire principle and each device has two sensing elements built into it to cover a stress measuring range of 700 kN compressive to 300 kN tensile load. Readings from the transducers are taken using the portable strain measuring instrument (type GT1169). Temperature readings are made at the same time to monitor changes in stress free temperature. A rail force value is then determined using a calibration curve.

The Australian agents are Richard Foot (Australia) Pty. Ltd., 63 Hume Street, Crows Nest, NSW 2065.

## FOR THE URBAN SPACEMAN

A new organisation has been formed in the US to give non-NASA people a say in the future of the space programme. The National Space Institute is open to people from all walks of life and it will present their views to NASA and Congress. Membership fees (in US\$) are: \$9 (under 18), \$15 (annual, adult), \$100 (life) and \$1000 (corporate). Members will get advice on technical queries, and a magazine is planned. NSI is designing a 'Space Product' logo for manufacturers to use on products based on space technology.

## MPU ON TV

MACE are able to supply Matrox products MTX1632 and MTX816. These modules will display alphanumeric data on a standard TV monitor when connected to the address and data buses of a microprocessor system. The 816 gives 8 lines of 16 characters and the 1632 gives 16 lines of 32 characters. The one-off prices are \$194 and \$285, plus sales tax and duty (if applicable). Delivery time is 6 to 8 weeks. From Measuring and Control Equipment Co. Pty. Ltd., 9 Mobbs Lane, Carlingford, NSW 2118.

# news digest

## LEADLESS PACK

General Instrument's Microelectronics division are to offer some of their ICs in leadless packages. The Mini-Pak is much smaller than its DIP equivalent: 13 x 13 x 3 mm versus 38 x 13 x 5 mm for a 28-connection chip. GIM will offer its TV game and several calculator chips in the new format. The connections are made to an array of solder bumps on the underside of the square substrate.

# FOR SALE

Used laboratory equipment in good condition. Most with original handbook.

1. Schlumberger strip chart recorder Model No. EU 205-11.
2. Weston Model 4444 Auto ranging digital multimeter.
3. AVO. meter No. 8 MK II.
4. Hewlett-Packard Model 4260 A universal bridge.
5. Schlumberger digital voltmeter Model No. LM1604.
6. Hewlett-Packard oscilloscope. Model 182A main frame with type 1801A — 50 MHz dual vertical amplifiers and delayed time base type 1822A with P 6021 current probe.
7. Climatic cabinet temperature adjustable from 25°C to 110°C  $\pm 1^\circ\text{C}$  with 2ft x 2ft x 2ft working space.

Contact Mr Max Palmer  
**LUKE ELECTRICS,**  
Cook Street, Mitcham, Victoria,  
Telephone 874-7444.



## MICROPROCESSOR WATCHES

Intel will soon be producing chips that answer the varying market (as far as features are concerned) problems of the watch-chip manufacturer. It is possible to mask-program the chips for 4-, 6-, or 8-digit displays, up to 8 timing functions, and a choice of segment styles and alphanumeric.

## MS MOVE

MS Components have moved to new premises in Redfern. The shop, at 164-166 Redfern Road gives increased display area for the company's hi-fi products: KEF, Ultralinear, Lenco, Sherwood, etc.

The company also sells components from the shop — direct or by mail order. The new phone number is 69 5922.

## ELECTRONIC OLYMPICS

The Olympic Radio and Television Organisation will employ a trained staff of 1680 for the two weeks July 17th to August 1st. TV services will be provided for 70 countries and radio for all 110 countries represented. Provision will be made for 700 commentators and there will be at least 19 mobile units, 87 VTRs, 103 CTV cameras, 17 slow-motion VTRs and 4500 audio circuits! Australia's programmes, like those from other major broadcasters, will come from augmented productions, using some ORTO feed but supplementing this with our own cameras and production.

## ETI KITS IN NEW ZEALAND

Good news for our readers on the other side of the Tasman. We have, from time to time, received letters from our New Zealand readers enquiring after the availability of kits of components for several ETI projects. Often the smaller New Zealand market has discouraged local suppliers from assembling kits and with the import restrictions it has been virtually impossible for New Zealand hobbyists to build a number of popular projects.

Applied Technology Pty. Ltd., a leading supplier of kits to the Australian market, has now made arrangements to have a range of the more popular ETI kits available directly to New Zealand readers, and has established a small warehouse facility in Auckland. The local operation is to be staffed by Kiwi enthusiasts. Negotiations are currently proceeding to establish the necessary licences, and from our initial investigations most kits will be available. There is also a strong possibility that most components, particularly semi-conductors, will also be offered.

Further enquiries may be directed to Applied Technology (N.Z.) Pty. Ltd., The Electronic Mailbox, P.O. Box 4289, Auckland, New Zealand.

## NIPPON MPUs

Nippon are hoping to win a large proportion of the Japanese microcomputer market with a range of new products that will completely match the range of 8-bit devices presently produced by Intel.

## PROJECTION TV

After the introduction of the Advent (Video Beam) projection TV in 1974, other models are being developed by Advent and other US companies. GE have demonstrated a rear-projection type offering perfect registration and high brightness. A single beam source eliminates convergence problems and the colour image is formed by deformation of a thin oil film. The screen is then illuminated with a xenon arc source giving an image seven times brighter than models projecting a conventional picture tube image.

## ERRATUM P. 65 MAY 1976

The special offer with Dick Smith Electronics had a typing error on the coupon: the text correctly stated that 25 EM402 diodes were available for \$1.

# WIN A CALCULATOR!

Each month we are offering an electronic calculator as a prize in this regular competition. This time it is the Unitrex 901MR mini slide-rule electronic calculator. All you have to do is complete the crossword below and get it back to us by the 16th of July. Then we will draw coupons from a barrel until we find a correct entry. The winner will be announced in ETI soon afterwards.

## THIS MONTH'S PRIZE

The Unitrex 901MR is a mini slide-rule calculator with full memory. Using algebraic logic it can handle chain and mixed calculations, displaying the results on its 8-digit display. Squares, square-roots and reciprocals are automatic and a true 4-key memory selectively stores and accumulates in a separate register. The percentage key enables add-on and discount capability. There is automatic constant on all four main functions. The calculator indicates credit balance and overflow. Case and batteries are included.

## CLUES

### ACROSS

1. *Alter me oar (electrically)*
9. *One problem on the TV in Hanover*

### DOWN

1. *Jostle*
3. *The man who invented the telephone*
5. *Modulator-demodulator*

## RESULT OF APRIL CONTEST

What are the chances of 2 or more people out of a group of 26 having the same birthday? Surprisingly it is odds on ... almost 60%! The nearest answer on the entry coupon was 63% and the winner is Mr Y Young of Applecross, WA.


Send to:  
Calculator Contest (June)  
Electronics Today International  
15 Boundary St  
Rushcutters Bay NSW 2011

### \*Win a Calculator Contest\*

NAME .....

ADDRESS .....

..... P/code ..  
Permit No TC 7578

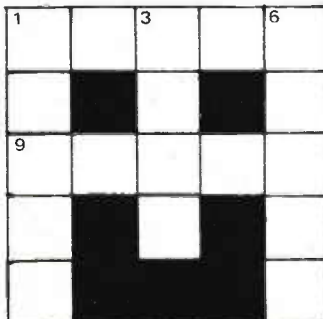




 **SENNHEISER**
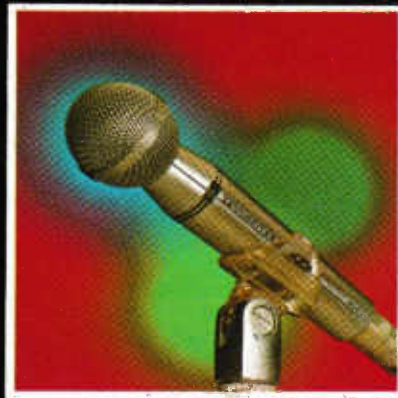
## MICROPHONES

Sennheiser offers the widest choice of studio quality microphones. Used by the TV and prominent commercial broadcasting stations, Sennheiser microphones will satisfy every application and requirement.



Sennheiser's significant design features give you low sensitivity to noise and vibration, with maximum brilliance of reproduction and perfect directional characteristics.

If you would like to know more about the huge range of Sennheiser microphones, now is the time to talk to Cunninghams.

**R.H. Cunningham**  
Pty. Ltd.

VIC: 493-499 Victoria St.,  
West Melbourne. 3003  
Phone: 3299633



N.S.W.: 4-8 Waters Rd., Neutral Bay.  
2089. Ph. 9092388  
W.A.: 65 Balcombe Way, Balga. 6061.  
Ph. 494919  
QLD: L. E. BOUGHEN & CO.,  
30 Grimes St., Auchenflower. 4066.  
Ph. 3708097

S.A.: Werner Electronic Industries Pty. Ltd.,  
Unit 25, 6-8 Gray Street,  
Kilkenny. 5009. Ph. 2682801

TELEX: Melbourne 31447.  
Sydney 21707, Brisbane 41500.



# Choosing your microphone

A microphone simply converts sounds to audio signals, or does it? There are many types of microphone and they all perform in different ways. So don't just pick the first one that comes to hand; this article will help you decide which mike is best for the job.




*The Shure PE5EQ E-Qualidyne microphone.*

MICROPHONE SPECIFICATIONS tend to be masterpieces of obscurity. The beginner faced with buying a microphone has to reconcile conflicting requirements between the equipment he already has, the recordings he wants to make, and the amount of money he can afford to pay. The literature he gets from manufacturers may or may not be very helpful.

Microphones react differently to sounds coming from different directions. The most important direction, of course, is from the front. The directional response can be considered as a comparison between this front or 'on-axis' response and all other directions.

A polar plot or polar diagram, three of which are shown in Fig. 1, is a line joining all those points around the microphone which give the same output for a given sound level. In



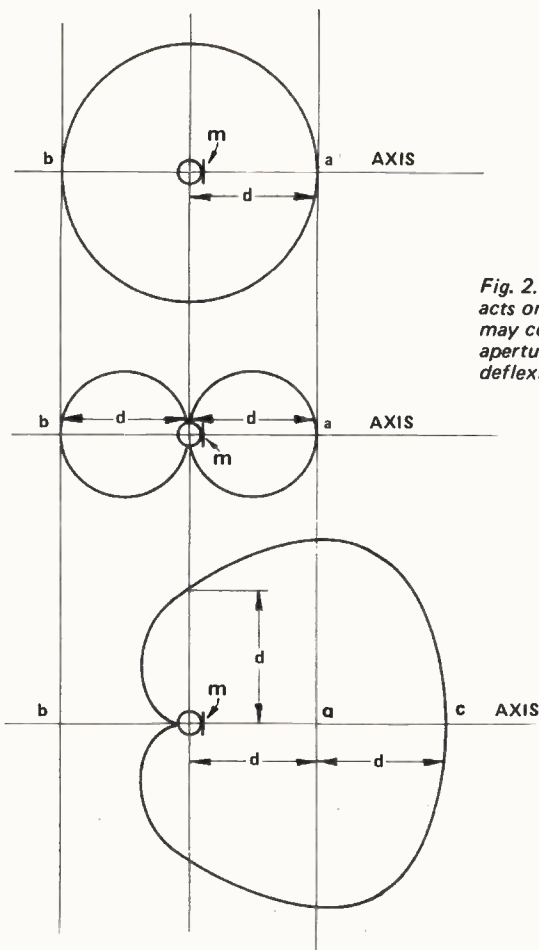


**Fig. 1. Polar Diagrams.**  
 Top: Omnidirectional response.  
 Centre: Bidirectional or figure of eight.  
 Bottom: Cardioid, the sum of the top and the middle responses.  
 Response at *c* in the bottom diagram is the same as that at *a* on the other two diagrams, where  $a \text{ to } m = a \text{ to } c$ .


other words, if you were to move a sound all around the omnidirectional microphone shown at the top of Fig. 1 you would get the same output from the microphone without having to move closer to it. On the other hand, if you were to move a sound round the figure of eight microphone there would be no response from the microphone at the sides at right angles to its axis but the response would increase again towards the back.

### PRESSURE TRANSDUCER

The directional characteristics of the microphone depend on its construction. If, as in Fig. 2, the rear of the diaphragm is totally enclosed apart from an atmospheric pressure equalisation tube, then the diaphragm will react only to rapid changes in air pressure. If the diaphragm is not so big as to interfere with the sound waves it will respond to sound from any

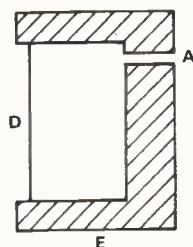


**Fig. 2. Pressure operation.** Diaphragm *D* reacts only to rapid pressure changes, which may come from any direction. *A* is a small aperture to avoid permanent diaphragm deflexions, *E* is the enclosure.

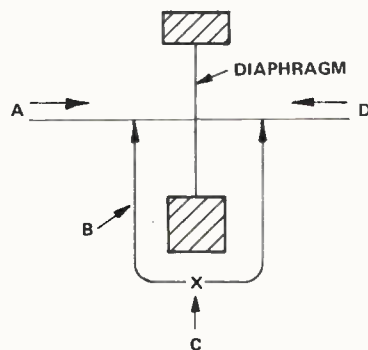

**Fig. 3. Pressure gradient operation.** Distance *x* is the path difference between the front and the back of the diaphragm.

direction since these changes in pressure can approach from any direction. Thus it is a pressure transducer.

Another kind of operation is pressure gradient operation. The diaphragm (Fig. 3) is exposed on both sides. A sound wave coming from direction *A* strikes the front of the diaphragm first and then travels round to the back. In doing so it will have to move distance *x*, the path difference between front and back. In this time the pressure at the front of the diaphragm will have altered according to the pressure pattern of the incoming wave. If the wavelength of the sound is long compared with *x* (Fig. 4) the pressure change which occurs while the wave travels distance *x* will not be great. In the limit, when the sound pressure is constant, there will be no difference along the path length *x* at all. At low frequencies *x* will be small compared

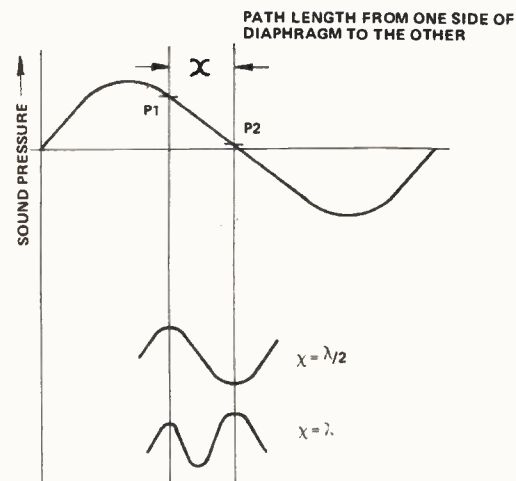

**Fig. 4. Pressure gradient and frequency.** As the wave travels distance *x* its amplitude (i.e. the pressure) changes and the diaphragm senses this differential.

with the wavelength and it can be assumed that  $P_1$  to  $P_2$  is a linear portion of the pressure curve, so that  $P_1 - P_2$  genuinely represents the pressure gradient. Here the force on the diaphragm is proportional to frequency, and this is roughly true until the distance is a quarter of the wavelength of the sound.

### CARDIOID PATTERNS

The pressure gradient microphone will only respond to sounds from the front. Sounds from position *C* in Fig. 3 will have no effect on the diaphragm since pressures on either side of it are equal. Sounds from *D* will have the same effect as those from *A* but will be phase reversed since they move the diaphragm in the opposite sense, so that although the microphone would give the same voltage output at *B* as at *A*, the output at *A* would be  $+V$  and the voltage at *B* would be  $-V$ . It is for this reason that if the omnidirectional and figure of eight characteristics are combined — as they can be by connecting an omnidirectional microphone element to a figure of eight element — then the responses of the two characteristics add at the front and subtract at the back, giving the cardioid characteristic shown in the third part of diagram 1.

### PHASE SHIFT

The cardioid characteristic can also be obtained as follows. Figure 5 shows a phase shift operated microphone, in which the amount by which the phase of the incident wave is shifted between the front and the rear of the microphone is related to the angle of incidence of the sound wave. In the diaphragm shown, the path difference



# Choosing your microphone

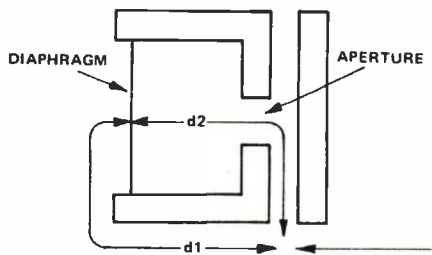


Fig. 5. Phase shift operated microphone.

for sound behind the microphone is zero because  $d_1 = d_2$ . This means that there will be no response to sounds coming from the back. If the sound comes from the front there will be a phase shift which will reinforce the motion of the wave impinging on the front of the diaphragm. For the arrangement shown, the reinforcement will be maximum when  $d_1 + d_2 = \lambda/2$  making the pattern frequency dependent, and in a practical microphone ports are provided for the high, medium and low frequencies to give a uniform response, as shown in Fig. 6. Here  $d_1$  is the distance to the low frequency port,  $d_2$  that to the mid frequency port and  $d_3$  is that to the high frequency port. The three ports can be replaced by a long slot.

As the size of the ports or slot tends to zero the microphone will tend to become pressure operated, giving an omnidirectional pattern. As the size of the ports tends towards infinity, where

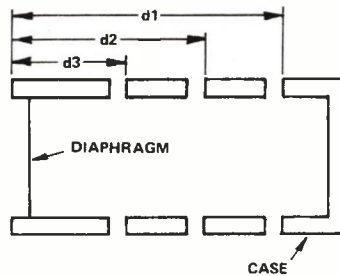


Fig. 6. Ported phase shift microphone.

the back of the diaphragm is open, the microphone will tend toward pressure gradient operation, giving a bidirectional or figure of eight pattern. When the apertures are between these sizes the microphone will act in a combination of pressure and pressure gradient operation, giving various forms of cardioid pattern.

## HAND MICROPHONES

The omnidirectional microphone is best for use as a hand microphone. There is less handling noise and the user need not be on axis for the microphone to give full output. The omnidirectional microphone, is also less prone to a phenomenon known as 'proximity effect', which means that as the microphone gets nearer to the source of a sound it exaggerates the bass response. On the other hand an omnidirectional microphone is not easily used in public address work

because it may pick up the sound from an audience loudspeaker and re-amplify it, causing howl-round or feedback. This is best eliminated by using a cardioid, which does not respond to sounds coming from behind it and will not be so affected by auditorium loudspeakers. Often auditorium loudspeakers are placed in front of the performers and have their own directional pattern which prevents their output reaching the stage microphones.


## POPPING

Another problem is breath popping, which occurs when a performer sends a puff of hot steamy air into the internal organs of a microphone. Omnidirectional microphones are less sensitive to this kind of thing and cardioids can be protected from it by windshields. A ribbon might not recover. If a windshield is used on a cardioid with a port or aperture in the body of the microphone, as in the AKG series, the ports should be windshilded too.

The figure of eight combination overcomes disadvantages inherent in the omnidirectional and cardioid designs. The omnidirectional, while it has many advantages, responds to echoes and reverberations in a room as well as the direct sound. The cardioid responds, in general, to the direct sound, which is why it tends to be used in situations where an audience is present and it can therefore reduce the coughs, chair scrapes and, if you're unlucky, snoring that may occur on such occasions. On the other hand the cardioid tends to produce a very dry sound, particularly if used too close, and recordings made this way can often be said to need some reverberation. The figure of eight is a perfect compromise, on many occasions, introducing just the right amount of reverberation and keeping off unwanted noise.

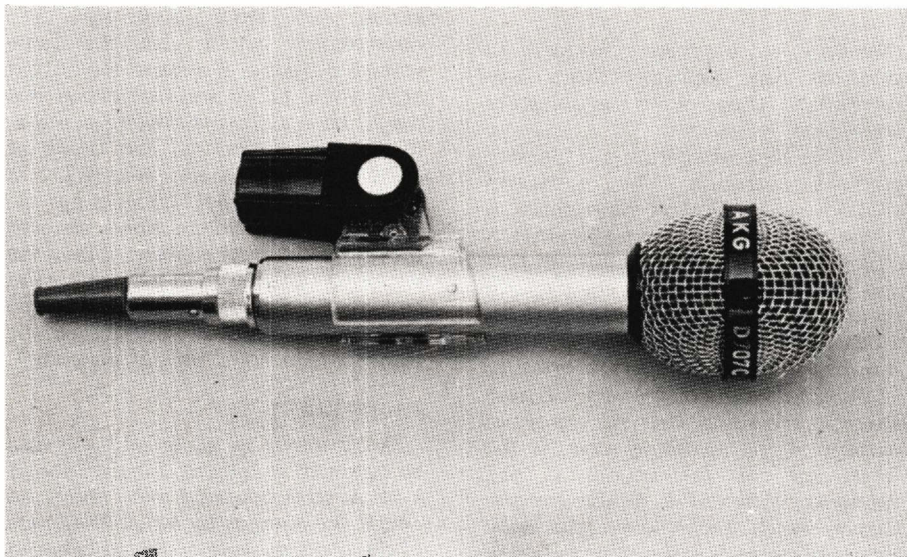
## REFLECTIONS

Figures 7 and 8 show the common situation when recording. In Figure 7 the microphone receives a direct sound from the instrument as well as numerous indirect sounds reflected from walls, floor and ceiling. For a variety of reasons in a concert hall these tend to be predominantly sounds reflected from the side of the hall. The cardioid will tend to diminish its response to sounds as they come from a direction nearer the back of the



The AKG D707C microphone.



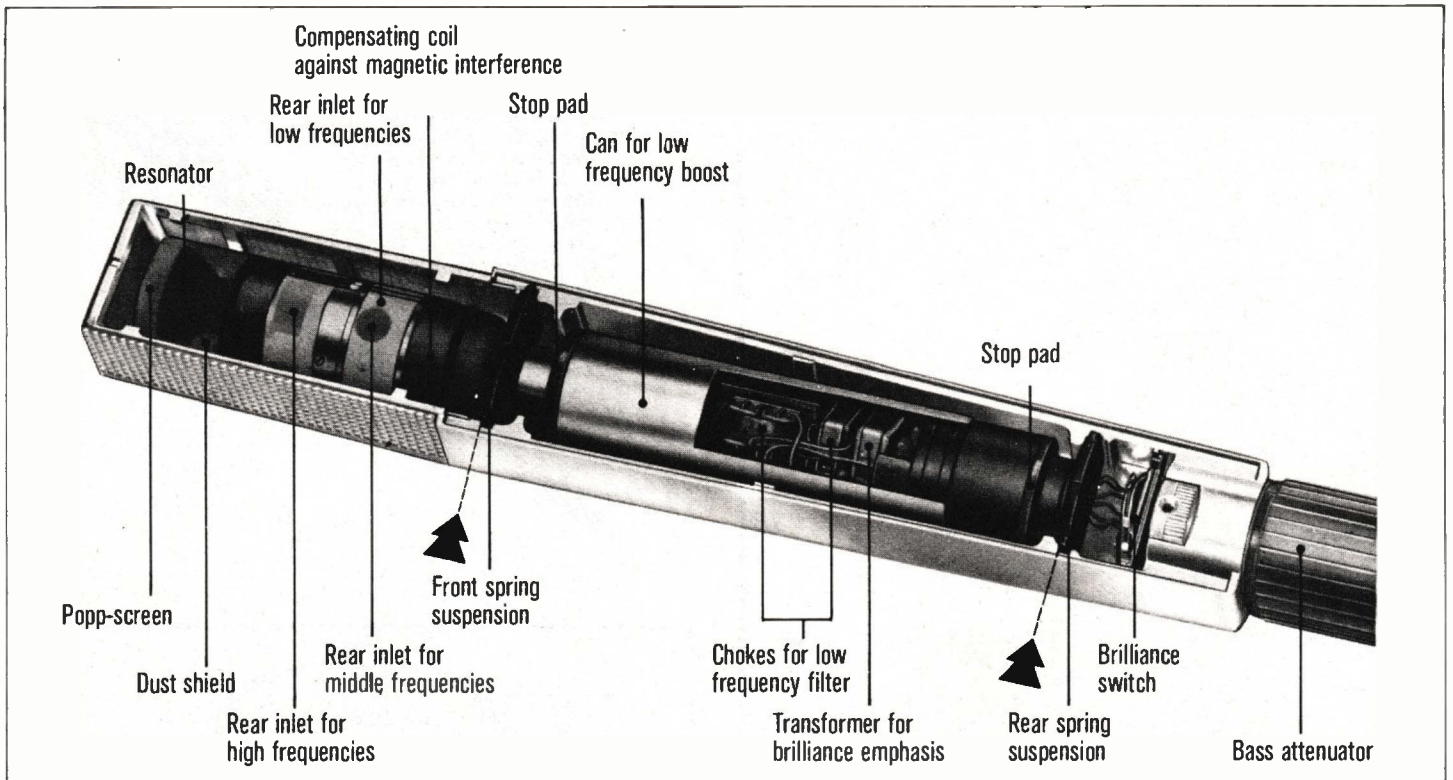

Inside the elaborate Sennheiser MD411 studio microphone. The transducer is isolated against the vibrations of the outer housing by the suspension springs.

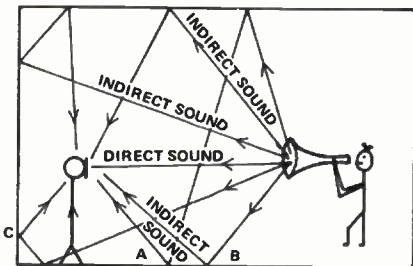


Fig. 7. If the mike is too far away the indirect sounds (echoes) drown the direct sounds.


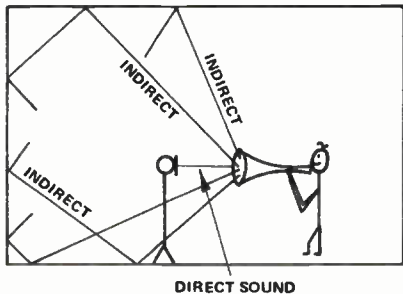



Fig. 8. Moving the mike closer in alters the direct/indirect sound ratio.

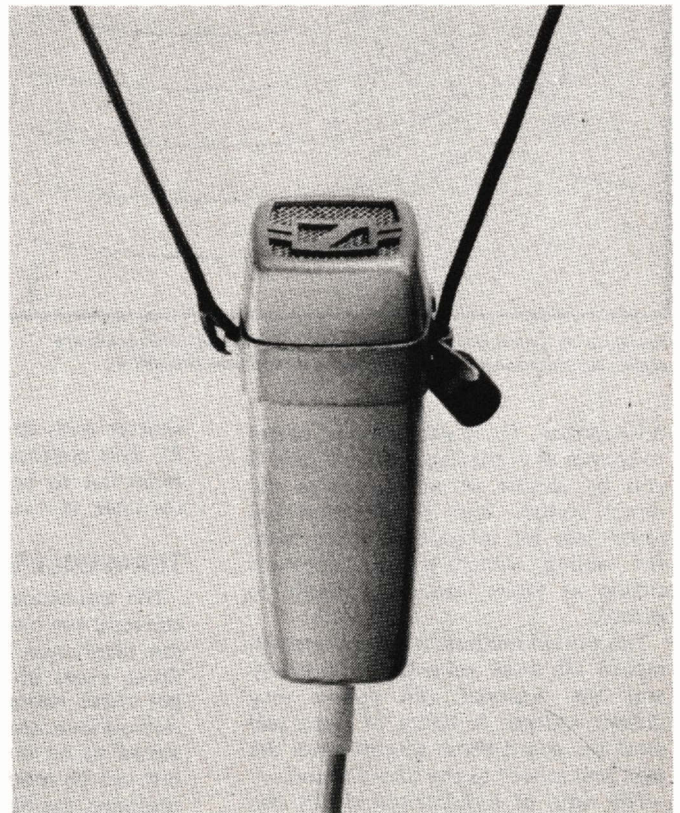The Sennheiser Lavalier microphone MD214. The response of this microphone is designed to give a natural voice reproduction when it is worn on the chest. It is designed to reduce rustling noise as the wearer's clothes rub against it.





# Choosing your microphone

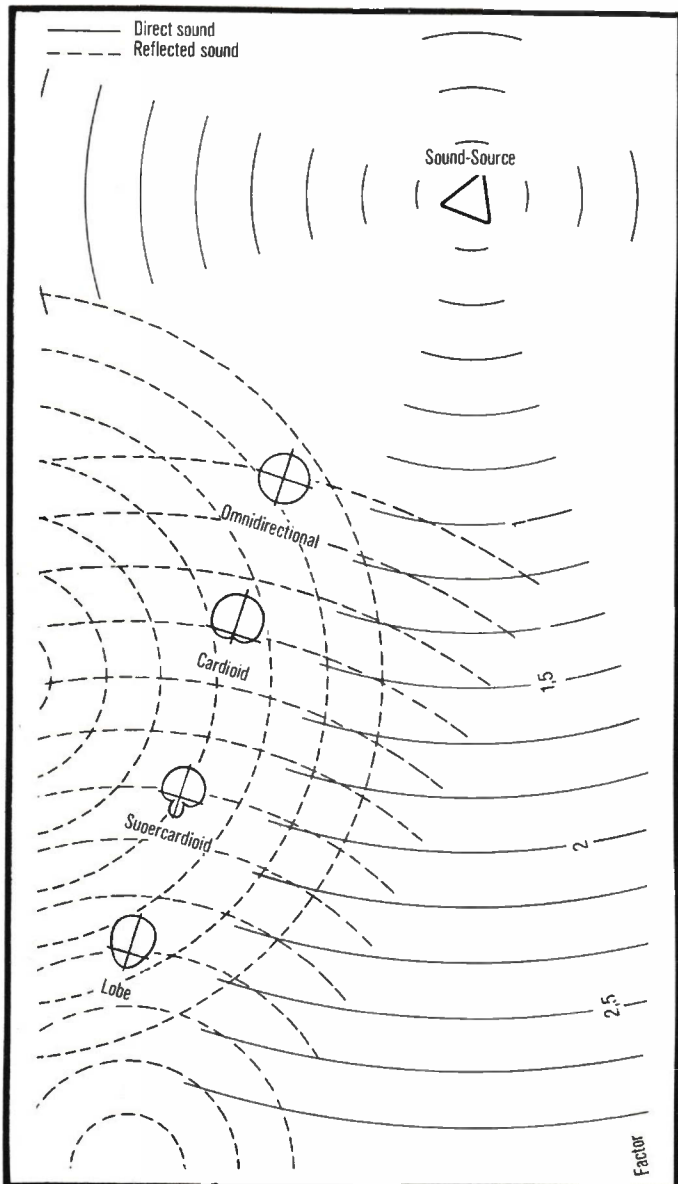

Positions at which the intensities of direct and radiated sound are equal, for microphones with differing directional properties.

microphone. So it will respond better to sounds at A than sounds at C, and B will be almost as well heard as the direct sound. The B reflection has much less far to go than those from the ceiling, which is why speakers sitting at tables can be difficult to record.

The omnidirectional microphone will record all these reflections faithfully and the trumpet will sound very distant indeed. A figure of eight will tend to record those sounds from the rear wall as well as the direct sound.


The ratio of indirect sound can also be varied by giving the direct sound a

shorter path to the microphone (Fig. 8). This approach should be used if an omni has to be used, but as we shall see later, it is not suitable for ribbons.
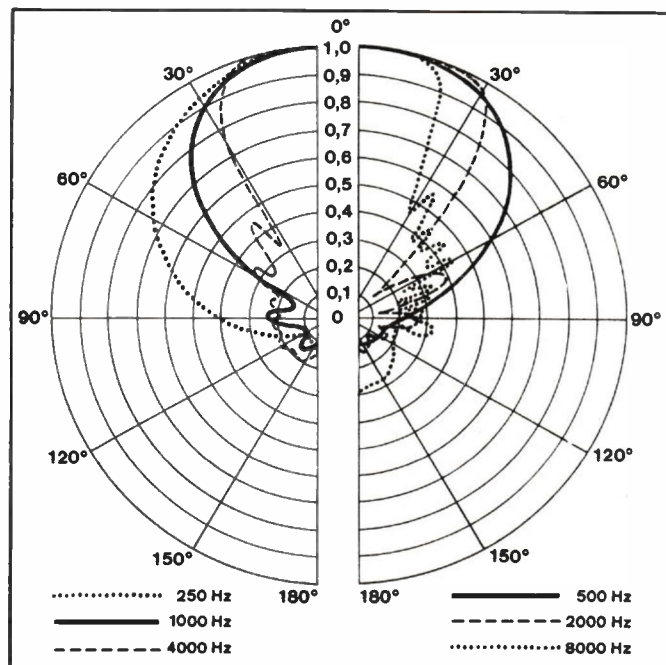
## TRANSDUCERS

The transducer is the element which converts the mechanical movements of the diaphragm into electrical signals. Three types of transducer are used to get these various response in quality microphone: the **moving coil**, which is suited to an omnidirectional response but can be modified to give a cardioid response, the **ribbon**, which is far more suited to figure of eight operation than

The Sennheiser MKH 815 condenser microphone. This device combines the interference and pressure gradient principles to give smooth frequency response and high directionality. The length is 550 mm but the performance makes it ideal for out-of-shot use in film and TV. The graph shows the polar response at six frequencies.



other responses, and the **capacitor**, condenser or electrostatic microphone.

Both moving coil and ribbon microphones work on the same principle — that when a conductor moves in a magnetic field an electrical signal is induced in the conductor. The size of the signal depends on the rate at which the conductor moves across the field.

## CHEAP MICROPHONES

Before looking at the three high quality transducers, there are two other types to consider — the carbon microphone and the crystal



microphone. The carbon microphone is seldom used these days.

It operates by monitoring the resistance of a capsule of carbon granules as it changes under pressure from a diaphragm. The quality is poor but the high output (the change in a small dc bias voltage) was an attractive feature back in valve days.

The crystal microphone is common today where a cheap microphone is needed. The quality is adequate for speech work and the high impedance output easily drives simple transistor amplifiers. Two Rochelle Salt elements with metal electrode coverings form a square bimorph. Three corners are fixed to pillars in the housing of the transducer and the fourth corner is connected to the centre of the diaphragm.

Another type used, especially in mobile communication, is the rocking armature type. The frequency response of these microphones coincides with the valuable section of the speech frequencies and avoids a lot of background noise.

## MOVING COIL

In Fig. 9 the moving coil is attached to a diaphragm, and when sound waves hit the diaphragm the coil moves and gives a signal across its ends. The same happens in the ribbon microphone.


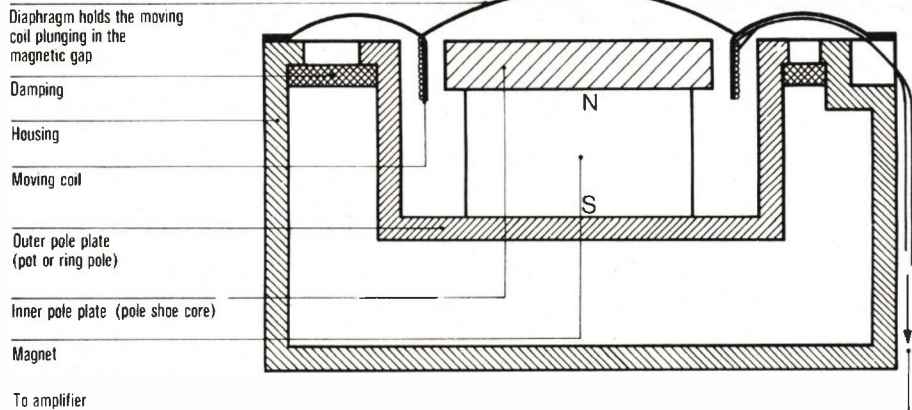


Fig. 9. Transducer principle of the moving-coil microphone.

The moving coil is more widely used in studios and on stage than any other. It is robust, gives a good output level, has a good transient response and frequency response, and is reliable and inexpensive. It is best suited to omnidirectional work and can become rather complicated if used as a cardioid. Even as an omni the response becomes less omnidirectional at high frequencies because the case interferes and this has to be compensated for by making the microphone smaller — though as it gets smaller the output decreases.

The impedance of the moving coil microphone is low, between 20 and 30 ohms. Also, compared with the output of the lower quality crystal and ceramic types of microphones, the output is low, so a transformer may be needed to step up both impedance and output voltage for the input of the tape recorder, amplifier or mixer. Often the transformer is built into the case of the microphone and can be fitted with a number of secondary windings, so that the microphone can be matched into a variety of impedances.

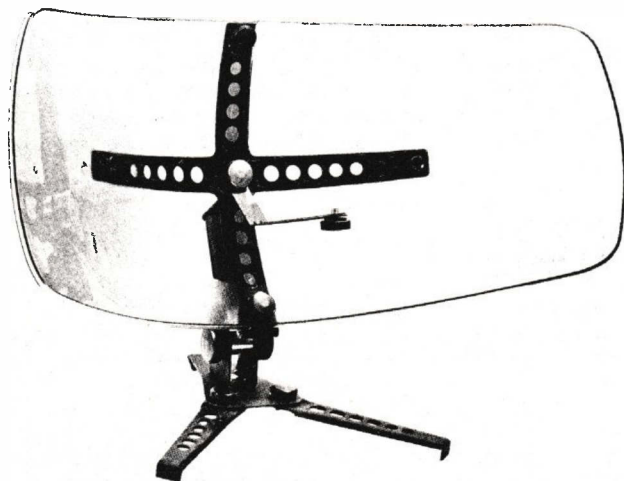

Another way to get a highly directional response: the parabolic reflector. The reflector on the JVC TL-E71 gives a 15 dB gain at 5 kHz. The picture shows only the reflector, the microphone has to be attached to the arm. This is a useful accessory for the amateur recordist who wants to make wildlife tapes.

The Sony ECM-99 "one-point" stereo microphone. This makes stereo recording easy for the novice; both microphones are in one housing with built-in wind screen.



The Shure SM5A is a boom microphone with a built-in 100 Hz hi-pass filter to cut out subsonic transients (caused by rapid boom movement or wind). These transients can overload the recorder's input.



# Choosing your microphone

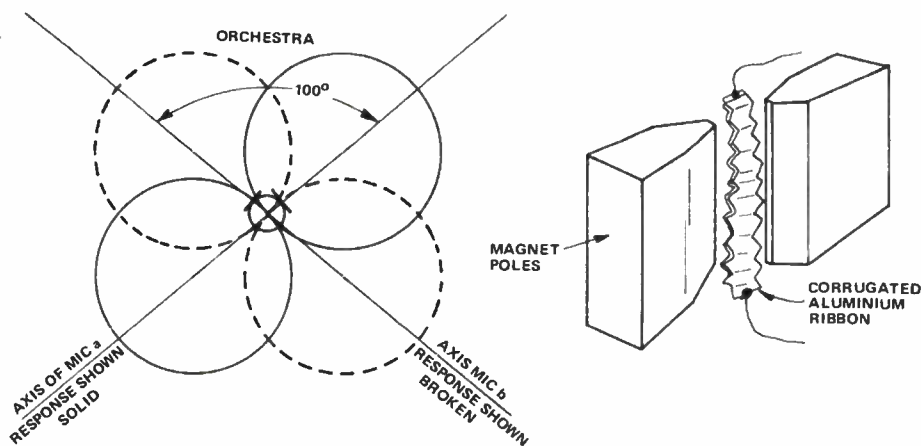


Fig. 12. Use of two ribbon mics for orchestral recording.

Ribbon microphone.

ribbon microphone should be used at mouth level in such circumstances.

## CAPACITOR

The capacitor microphone can be arranged to have any of the three polar patterns and even any in between. It works on the principle that if the charge on a parallel plate capacitor is kept constant the voltage across the plates is proportional to the distance between the plates. One plate is kept fixed and the other is flexible and responds to sound, so that the sound varies the voltage across the plates, and gives an audio output signal. The charge on the plates is kept constant by polarising the plates via a large resistor, see Fig. 11, and the audio voltage is extracted via an isolating capacitor. The microphone has a flexible plate on either side of the fixed plate so that two outputs are obtained which can be added, subtracted or mixed in varying degrees to obtain various polar patterns.

Capacitor microphones undoubtedly exhibit the best frequency response, and can be flat up to 15 kHz or so, with a -3 dB point as high as 18 kHz or higher. In addition they have very high output level, can be very high and, as we have seen, can give various polar patterns.

The problem with a capacitor microphone is that its source is a small capacitance, which gives a very high value of source impedance at audio frequencies. Any signal source with a high source impedance may suffer from stray fields picked up by the cable connecting it to its amplifier and from a deterioration in frequency response along the cable. Thus a buffer amplifier has to be built close to the microphone cable. This means that the


## RIBBON

Figure of eight operation is usually achieved with a ribbon microphone. Much of the foregoing remarks about the need for a transformer apply here as they do with the moving coil microphone, except that the ribbon microphone has a far lower impedance and output than the moving coil microphone. The impedance might be as low as an ohm and a transformer is always needed, particularly since a ribbon microphone with a wide frequency response is likely to give a very low output. The ribbon microphone is an excellent choice for stereo, where two arranged as shown in Fig. 12 may give excellent results for recording an orchestra.

Note that if two microphones are to be used for recording stereo the off-axis response is very important. Since they will not be pointed directly at the orchestra they need to reproduce high frequencies at an angle to the front of the microphone. Most manufacturers of repute give some idea of the off-axis response of a microphone by publishing a polar diagram plotted at various frequencies.


Orchestral recording is ideal for the ribbon microphone, since it is very prone to 'proximity effect', and should never be used near to loud bassy instruments. It is also very delicate and cannot be used outside, where a gust of wind may damage it permanently. It should never be used held in the hand, since it is more prone to handling noise than any other microphone. It may have a large stray magnetic field, so a ribbon microphone should be kept away from recording tapes.

Ribbon microphones can also be used to make small studios less dead without including reflections, particularly those from tables. A bi-directional microphone can be used for two persons speaking, one either side, and for drama it is very useful for an actor to be able to step 90° round the microphone to 'disappear' from the scene. For more speakers, as in a discussion, it is better to use an upward facing cardioid, which will, again, cut out those unwanted table reflections and paper shuffling sounds without making the discussion sound as though it is being held in a room lined with cotton wool or at night in the centre of the Simpson desert. Broadcasting studios often have a well in the middle of the table for placing such a microphone in and another advantage of this is that it tends to lower the microphone's prominence in the minds of those having to speak into it, particularly if they are not experienced broadcasters. Note that a

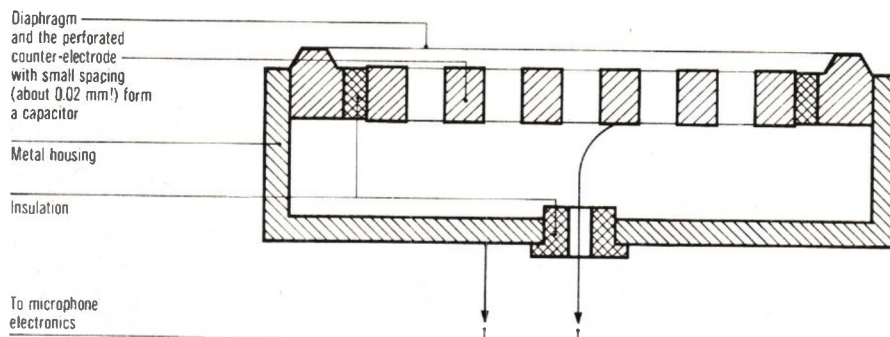

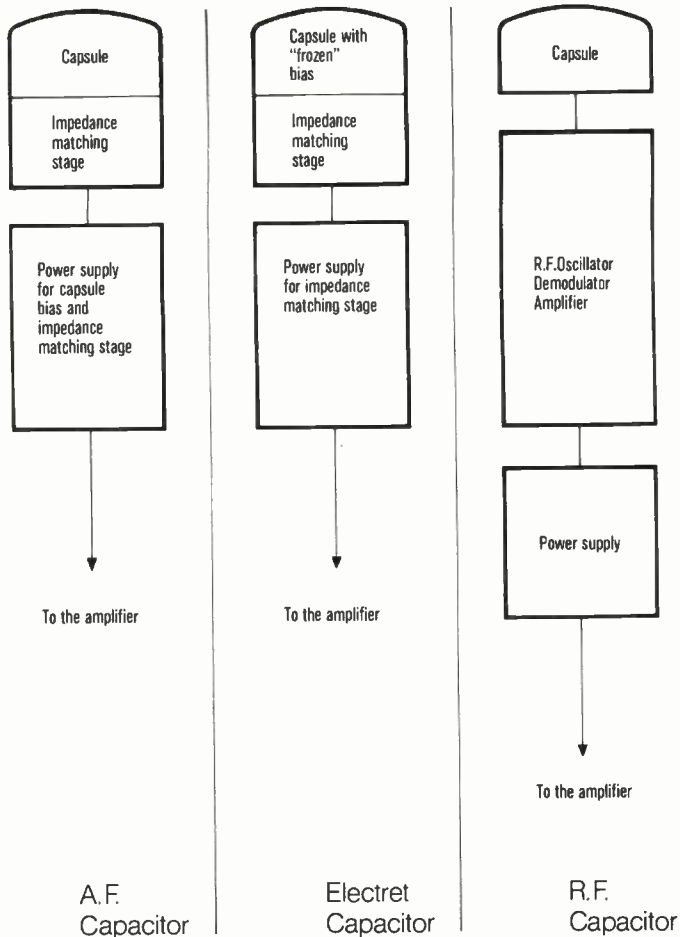Transducer principle of the capacitor microphone.





This is a special microphone for use in ambisonic systems. It contains four transducers.

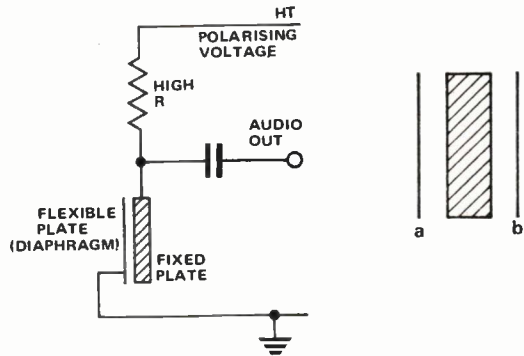


Fig. 11. Some capacitor microphones have a flexible plate either side of a fixed plate. Each single diaphragm gives a cardioid response so that if the two outputs are added, the results is omnidirectional, and if subtracted is bi-directional or each cardioid can be used alone.

**Three types of capacitor microphone system: AF, Electret and RF.**

**AF** The capacitor is charged at a constant rate via a very high resistance. The variations in capacitance produce variations in charge voltage which need to be transformed to lower impedances before they are fed to the pre-amplifier.

**Electret** In this type there is no need for an external polarising voltage: special foils are used which are permanently charged (a special process in their manufacture provides a charge which will never die away). However the acoustic properties of the foils are inferior to those of the AF capacitor mike.

**RF** These mikes give low noise figures. The capacitance is used in a discrimination tuned circuit to which RF (usually 8 MHz) is applied. The discriminator gives an AF output to match the capacitance changes in the microphone. These types are for studio use.

amplifier has to be powered but, on the other hand, the output can be as high as the amplifier designer requires.

All this means that for a capacitor microphone you may need an external power supply and an internal impedance convertor. Sometimes the diaphragm is made of metal-flashed plastic, which can distend in heat, such as found under television lighting. Even if the capacitor polarising voltage is supplied by an electret — a permanently polarised crystal — a battery is still needed to power the buffer amplifier because the electret cannot supply any current. The electret may be an uncertain proposition and perhaps susceptible to heat and moisture. Even an externally powered capacitor microphone is susceptible to an increase in noise in humid conditions.


**SPECIFICATIONS**

The moving coil microphone can respond to frequencies up to about 12 kHz or so and, when the

microphone has two elements and a crossover, just as in a loudspeaker, the response can go up to 14 or 15 kHz, although the off-axis response may not be quite as good as that because of the separation between the capsules. The ribbon microphone has a response up to 10 kHz but its off-axis response is equally good 50° either side of the axis.

The sensitivity of the microphone is a measure of the voltage it delivers for a given sound input. It is one of the most confusing of microphone specifications since it can be defined in

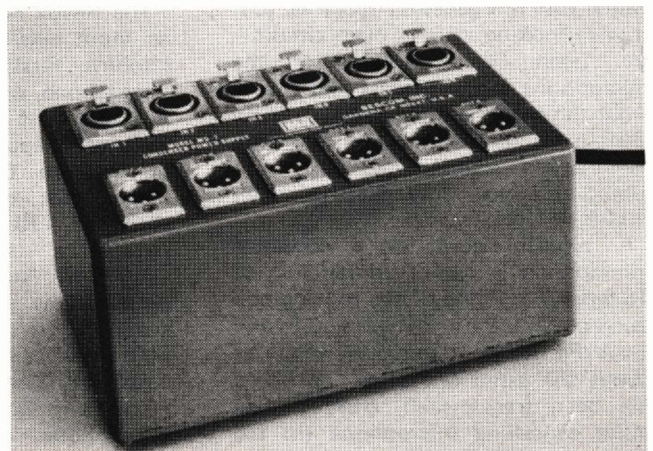Users of capacitor microphones often need to change batteries, but with this supply they can run up to six mikes from the mains. A constant 48 V is supplied at up to 14 mA. From Sascom.



# Choosing your microphone

## COMPANIES REFERRED TO IN THIS ARTICLE

ATRAM (Uher),  
5 McLaren Street,  
North Sydney,  
NSW 2060.

Audio Engineers (Shure),  
342 Kent Street,  
Sydney,  
NSW 2000.

AWA (AKG, Revox),  
554 Parramatta Road,  
Ashfield,  
NSW 2131.

RH Cunningham (Sennheiser),  
PO Box 4533,  
Melbourne,  
Vic. 3001.

Hagemeyer BV (JVC),  
59 Anzac Parade,  
Kensington,  
NSW 2033.

Sony Kemtron Pty Ltd,  
453-463 Kent Street,  
Sydney  
NSW 2000

Klarion Enterprises (Sescom),  
Regent House,  
63 Kingsway,  
South Melbourne,  
Vic. 3205.

Radio Parts (Zephyr, etc),  
562 Spencer Street,  
West Melbourne,  
Vic. 3003.

so many ways. Typical definitions are  $\text{mW}/10 \text{ dynes}/\text{cm}^2$ ,  $\text{mV}/\text{dyne}/\text{cm}^2$ ,  $\text{mV}/\text{N}/\text{m}^2$ ,  $\text{mV}/\text{microbar}$ , and  $\text{MV}/\text{Pa}$ . Alternatively the quantity can be expressed in  $-\text{dB}$ .

$\text{Dynes}/\text{cm}^2$ ,  $\text{n}/\text{m}^2$ , microbars and Pa are all ways of expressing pressure, so that the preceding figure is a measure of the output for a given pressure on the diaphragm of the microphone.

1 microbar =

1 dyne/cm<sup>2</sup>, and 1 N/m<sup>2</sup> = 1 Pa.

10 microbars or dynes/cm<sup>2</sup> =

1 N/m<sup>2</sup> or 1 Pa.

One microbar is the peak level of a normal voice 1 metre from the microphone. A singing voice is likely to be much louder and a trumpet or trombone even more so.

We have already seen that the output of the microphone varies according to the output impedance. The output may be defined in mW into a given load, usually 600 ohms, or it may, more often, be defined as a voltage, in which case it is generally specified as if it were looking into an open circuit — the open circuit voltage of the microphone is the highest and that is what the manufacturer wants to show you in his specification! (a 600 ohm microphone feeding into 600 ohms would produce only half its open circuit voltage.

A typical figure for a capacitor microphone is  $1.5 \text{ mV}/\text{dyne}/\text{cm}^2$ , or  $15.0 \text{ mV}/\text{Pa}$ . Some of the moving coil microphones vary between 0.5 and  $1 \text{ mV}/\text{Pa}$ . A ribbon microphone can be about the same once the impedance has been transformed, although one noise cancelling microphone (in the

STC range) has an output in the region of less than  $0.1 \text{ mV}/\text{Pa}$ .

The sensitivity may be defined in negative dB, where the dB reference should be stated and can be any of the quantities previously mentioned, such as  $1 \text{ V}/\text{Pa}$  or  $1 \text{ mW}/\text{dyne}/\text{cm}^2$ .

## IMPEDANCE AND MATCHING

The next problem is that you have to match the microphone output to your amp or tape recorder input. There are two rules here: the output impedance should be a half or a third the input impedance of the device into which it is feeding, and the sensitivity of the microphone should be two to four times the maximum input sensitivity of the device into which it is feeding. This gives enough input from the microphone to avoid too low a signal, which would increase noise, and it also means that there will not be so much output from the microphone that the input to the recorder is overloaded.

The Revox A77, for instance, quotes an input sensitivity of  $0.15 \text{ mV}$  at 6 kilohms. First, you're looking for a microphone with a maximum output impedance of around 2 k. Next you want an output from the microphone of between 0.3 and  $0.6 \text{ mV}$ . This means that the sensitivity will be between  $-70 \text{ dB}$  and  $-64 \text{ dB}$ . The reference is  $1 \text{ V}/\text{microbar}$ , or  $10 \text{ V}/\text{N}/\text{m}^2$ . Note that if the voltage is doubled the sensitivity increases by 6 dB. If the reference is  $1 \text{ mW}$  into 600 ohms the reference is  $0.776 \text{ V}$  and  $1 \text{ mW}$  into 1 kohm gives  $1 \text{ V}$ .

The self generated noise in the microphone varies with its source

impedance, and the lower this is the better from the noise point of view. At any rate the noise should be between 20 and 30 dB measured to DIN standard 45405, or defined as between 0.2 and  $0.3 \text{ Veff}$ .

The dynamic range of a microphone is a measure of its ability to record the softest and the loudest sounds equally well. At the top end it will begin to distort once the sound reaches a certain loudness and the level at which the microphone distorts by, say, one per cent can be taken as the reference level. At the quiet end the microphone may give an output which is barely above its own noise level. The dynamic range should be between 120 and 130 dB. It should be noted that this quantity isn't all that significant since the limitations of the input amplifier are more likely to be dominant — if the microphone gives out more than  $1 \text{ mV}/\text{dyne}/\text{cm}^2$  the output will be  $0.1 \text{ V}$  at a sound level of 114 dB or so, which can occur, and the amplifier is likely to distort.

Finally, the front to back ratio for a cardioid should be between 15 and 25 dB, the higher the better, depending on the application. ●





# AKG

## Microphones & Headphones

**D109** — Weight only 35g. Attractively styled and miniaturised, cable length 10m, Omni-directional characteristics.

**Technical Data:** Type: Dynamic pressure receiver; Frequency response: 50... 15000 Hz; Tolerance within: max.  $\pm 3.5$  dB; Sensitivity at 1000 Hz: 0.1 mV/ $\mu$  bar (-80 dbv); Impedance at 1000 Hz: 200 ohms  $\pm 15\%$ ; Min. Actual Load Impedance: 400 ohms; Directional Polar Response: spheric; Weighted Noise Level: 0.26 $\mu$  veff (filter CCITT-C/DIN 45 405); Unweighted Noise Level: 0.2 $\mu$  veff; Max. Sound Pressure level at a distortion factor of a 0.5% at 1000 Hz: 500 $\mu$  bar (128 dB SPL); Diaphragm: MAKROFOL



**D190** — Wind and pop-shield, pronounced directional characteristics, removable grille cap for easy servicing.  
**Technical Data:** Type: Dynamic pressure gradient receiver; Frequency Range: 30... 16,000 Hz; Sensitivity at 1000 Hz: 0.23 mV/ $\mu$  bar (-73 dbv); Impedance at 1000 Hz: 280 ohms  $\pm 20\%$ ; Min. Actual Load Impedance: 500 ohms; Directional Characteristics: Cardioid; weighted noise level: 0.25 $\mu$  veff (Filter CCITT-C/DIN 45 405); Unweighted Noise Level: 0.2 $\mu$  veff; Max. Sound Pressure Level at a distortion of 0.5% at 1000 Hz: 500 $\mu$  bar (128 dB SPL).



**D707** — Microphone system elastically suspended preventing mechanical shocks from reaching the transducer. Available with DIN and Cannon connectors.

**Technical Data:** Type: Dynamic pressure gradient receiver; Frequency Response: 60... 16,000 Hz with a tolerance of max.  $\pm 3.5$  dB; Sensitivity at 1000 Hz: 0.15 mV/ $\mu$  bar (-76.5 dbv); Impedance at 1000 Hz: 230 ohms  $\pm 20\%$ ; Min. Actual Load Impedance: 400 ohms; Directional Polar Response: Cardioid; Weighted Noise Level: 0.26 $\mu$  veff (filter CCITT-C/DIN 45 405); Unweighted Noise Level: 0.2 $\mu$  veff; Max. Sound Pressure Level at a distortion of 1% at 1000 Hz: 500 $\mu$  bar (128 dB SPL); Diaphragm: MAKROFOL.



**D2000** — Functional design and robust construction, heavy diecast housing with matt finish. Available with DIN and Cannon connectors.

**Technical Data:** Type: Dynamic pressure gradient receiver; Frequency Response: "bass" position, 25... 15,000 Hz; "medium" position, 50... 15,000 Hz; Tolerance within: max.  $\pm 2.5$  dB; Sensitivity at 1000 Hz: 0.23 mV/ $\mu$  bar; Impedance at 1000 Hz: 220 ohms  $\pm 20\%$ ; Min. Actual Load Impedance: 500 ohms; Directional polar response: Cardioid; Weighted Noise Level: 0.26 $\mu$  veff; Unweighted Noise Level: 0.2 $\mu$  veff; Max Sound Pressure Level for a non-linear distortion factor of 1%: 500 $\mu$  bar (128 dB SPL).

**K140** — "Cardan" — ultra light weight yet robust construction. One cable only for both earpieces, wiring completely integrated inside headband.

**Technical Data:** Frequency Range: 20... 20,000 Hz; Normal Power Requirement: 50 mw per channel, for a sound pressure level of 112 dB (80 $\mu$  bar) at 1000 Hz; Max. Undistorted Continuous Power Level: 119 dB SPL per system equivalent to 250 mw or 12v per system, at less than 1% thd; Sensitivity at 1000 Hz: 15 $\mu$  bar/v  $< 1.5$  Pa/v  $< 97.5$  dB SPL; Impedance: 600 ohms  $\pm 20\%$  per channel over the entire frequency range.



**K160** — Flexible double headband offers additional comfort, has detachable earpieces.

**Technical Data:** Frequency Range: 16... 20,000 Hz; Normal Power Requirement: 1 mw per channel, for a sound pressure level of 112 dB (80 $\mu$  bar) at 1000 Hz equivalent to 775 mw per system; Max. Undistorted Continuous Power Level: 125 dB SPL per system equivalent to 20 mw, or 3.5v per system, at less than 1% thd; Sensitivity at 1000 Hz: 100  $\mu$ bar/v  $< 114$  dB SPL; Impedance: 600 ohms  $\pm 20\%$  per channel over the entire frequency range.

For further details of these fine products contact:



**AMALGAMATED WIRELESS (AUSTRALASIA) LTD.**

**NEW SOUTH WALES**  
554 Parramatta Road, Ashfield, 2131.  
Phone 797-5757.  
King & Darby Streets, Newcastle, 2300.  
Phone 2-5166.

**HOBART**  
4 Lefroy Street,  
North Hobart.  
Phone 34-5266 34-5412

**LAUNCESTON**  
44-46 Garfield Street,  
Phone 44-5155

**TOWNSVILLE**  
213 The Market,  
Keane Street, Currajong.  
Phone 79-6155

**QUEENSLAND**  
73-75 Jane Street,  
West End, Brisbane, 4101  
Phone 44-1631.

**WESTERN AUSTRALIA**  
33 Railway Parade,  
Mount Lawley, 6050.  
Phone 71-0888

**VICTORIA**  
Miles Street, Mulgrave, 3170.  
Phone 560-4533

**SOUTH AUSTRALIA**  
48 King William Road,  
Goodwood, 5034.  
Phone 272-2366

**CANBERRA A.C.T.**  
Suite 3, TNT Bldg,  
23 Barrier Street, Fyshwick,  
2609. Phone 95-3431.

# EDGE ELECTRIX



31 BURWOOD ROAD, BURWOOD, NSW 2134,  
PO BOX 1003 BURWOOD NORTH TELEPHONE 747 2931

## Country Customers Please Note

We are mail order specialists and would like to supply your requirements. For free quotation write or phone.

**We now stock KEF for the person who wants the very best in speaker kits.**

**SK3 Concerto Kit**  
B139 50w RMS Woofer  
B110 Midrange  
T27 Tweeter  
2-B139  
2-B110  
2-T27  
2-DN12 Crossover Networks  
\$279 Pr.



B110



B139



T27

Pre-cut boxes to suit \$55 ea.  
Transmission Line Boxes \$89 ea.  
Full Kef range available, write or phone for information and quote on any Kef speaker.  
5 year warranty

P & P freight on

... Conclusion from stereo buyers guide speakers No. 4 on product report on Kef concerto speaker ...

"Among the finest speakers available today, obviously well designed, well made and giving excellent reproduction. They are not cheap but one must expect to pay for quality."

## HITACHI CASSETTES

PRICED LOWER THAN EVER

	Qty.	1 to 12 to 24		
		11	23	plus
C60 Low Noise	1.50	1.35	1.25	
C90 Low Noise	1.85	1.75	1.65	
C120 Low Noise	2.45	2.30	2.20	
C46 Ultra Dynamic	1.85	1.75	1.65	
C60 Ultra Dynamic	2.05	1.95	1.85	
C90 Ultra Dynamic	2.40	2.30	2.20	
C120 Ultra Dynamic	3.20	3.10	2.90	
C60 Ultra Dynamic Royal	2.40	2.30	2.20	
C90 Ultra Dynamic Royal	3.00	2.85	2.70	
C90SM BASF	2.40	2.20	2.00	
P & P 1-12 \$2.00	12-24 \$3.00	24+ \$3.50		

Parts for ETI 740 FM Tuner available now

**EDGE ELECTRIX SPECIAL PLAYMASTER 146 AM/FM TUNER KIT \$135.00**

Including Front Panel but no Metal Work.

P & P \$3.00

## MAGNAVOX MV 50

The fabulous Magnavox MV 50 speaker kit now available.

This system uses  
2-10/40 40W RMS Woofer  
2-625 6" midrange  
4-XJ3 dome tweeter  
2-MV 50 crossover networks

Speakers available separate

10/40... \$21.50 ea.

625... \$15.95 ea.


XJ3... \$8.95 ea.

MV50... Crossover \$19.95 ea.

Save on the complete kit.

Only \$145 Pr.

Boxes Available.

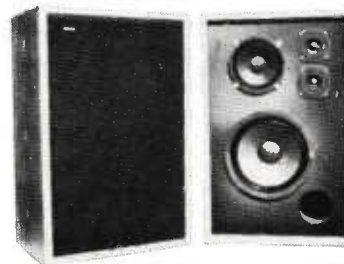

P & P FREIGHT ON

## MAGNAVOX

8/30... \$13.95 8" Woofer 30W

6J... \$7.50 6" midrange

8WR... \$11.50 8" twincone

6WR... \$10.50 6" twincone

## PHILIPS

AD0160/T8-1" dometweeter \$12.00 ea.

AD5060/Sq8-5" squawker \$22.50 ea.

AD0210/Sq8-2" dome squawker \$38.00 ea.

AD8066/W8-8" 40W Woofer \$18.50 ea.

AD12100/W8-12" 40W Woofer \$49.00 ea.

ADF500/4500/8-3 way crossover \$14.50 ea.

ADF 600/4000/8-3 way crossover \$29.00 ea.

## PHILIPS

7A System... 2-AD12100/W8

2-AD5060/Sq 8

2-AD0160/T8

2-ADF 500/4500/8...

\$185 Pr.

P & P freight on

## PHILIPS

14 System 2-AD12100/W8

2-AD0210/Sq 8

2-AD0160/T8


2-ADF600/4000/8... \$245 Pr.

P & P freight on

PLEASE ADD SUFFICIENT PACK & POST



# COMPARE THE SOUND. COMPARE THE PRICE.

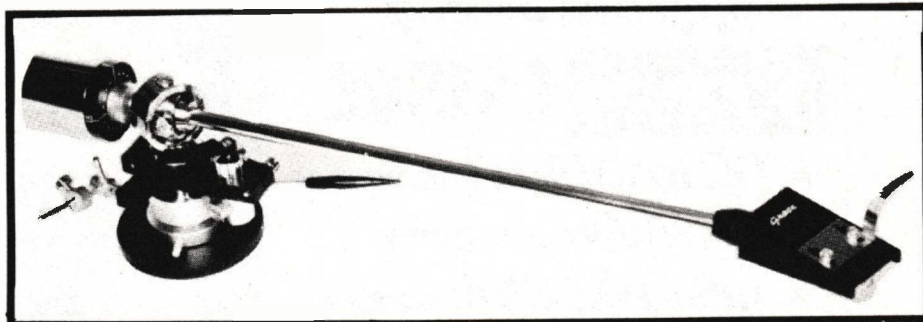

## CARTRIDGES:

With cartridges, with tone arms, with whatever, there will always be some who claim to be the best there is. Probably, they'll be seen around exhibitions a lot, on equipment being demonstrated, and so on. But we believe it's well worthwhile taking a little time to consider what "the best" really means; in terms of quality *and* in terms of price.

About the Grace F9E/Extended Range 4 Cartridge (just one of the F9 Series) Hi-Fi Review had this to say: "The F9-E is one of the sweetest sounding cartridges we've heard, providing a very full sound with virtually no audible distortion. It would be suitable for use with top quality systems where it's capabilities could be fully realised."

Based on the renowned F8 series, (including Gold Medal winning, best selling F8L elliptical cartridge, and F8C Custom with luminal trace elliptical stylus), the new F9 range may very well cause the discerning purchaser to ask just where all that extra money is going in what some would allege to be "the best".

## TONE ARMS

Typifying the range of Grace Tone Arms is the Grace G707 low mass arm. In order not to distort the mid frequencies, because of dead mass, the G707 is provided with a non interchangeable acrylic head shell. This is an integral part of the entire arm. However, changing cartridges can still be easily achieved. Model G840F has the Universal type interchangeable head shell.

A high precision double gimbal pivot refined after over 10 years of manufacturing experience is used on this arm. The gimbals now use aircraft instrument micro pivot bearings to reduce friction resistance to less than 20 milligrams.

### Available from...

- N.S.W.: M & G Hoskins Pty. Ltd., (Showroom) 400 Kent St., Sydney 2000, Telephone: 559-4545 & 559-3693.
- QLD.: Stereo Supplies, 95 Turbot St., Brisbane 4000, Telephone: 21-3623.
- S.A.: Challenge Hi-Fi, 96 Pirie St., Adelaide 5000, Telephone: 223-3599.
- TAS.: Audio Wholesalers Pty. Ltd., 9 Wilson St., Burnie 7320, Telephone: 31-4111.
- VIC.: Encel Electronics Pty. Ltd., 431 Bridge Road, Richmond, 3121, Telephone: 42-3761.
- W.A.: Albert TV & Hi Fi, 282 Hay St., Perth 6000, Telephone: 25-2699.
- A.C.T.: Duratone Hi Fi, Cnr. Botany St., & Aitree Crt., Phillip 2606, Telephone: 82-1388.

*Sole Australian Distributors*

**INTERNATIONAL DYNAMICS (AGENCIES) PTY. LTD.,**  
23 Elma Rd., North Cheltenham, 3192, Melbourne 95-1280.



## YOU DON'T HAVE TO BE THE MOST EXPENSIVE TO BE "THE BEST."

# NEW Dual Trace, Triggered Sweep

**TRIO CS1562**

- ★ DC to 10MHz BANDWIDTH
- ★ 10mV/div SENSITIVITY
- ★ 1μS to 0.5S/Div SWEEP

**ONLY \$379.00**

(ex Tax or \$435.85 inc. tax)

Ideal for T.V., Education, Research etc., etc.

- TV-V and TV-H sync + 5x magnified sweep
- X-Y operation plus Z-mod
- CHOP/ALT automatically selected
- Dual FET vertical amp
- Stabilised EHT DC-DC converter
- Die-cast front panel.

Call in for a demonstration at leading electronics stores or at the sole Australian agents - Parameters Pty. Ltd.  
 SYDNEY: 68 Alexander St., Crows Nest 2065  
 Tel: 439 3288  
 MELBOURNE: 53 Governor Rd., Mordialloc 3195  
 Tel: 90 7444  
 Take advantage of your Bankcard.



Have you seen the new Trio CO1303D, 5MHz single trace and CS1560, 15MHz dual trace scopes? Check all your instrument requirements for a better buy from Trio.



**PARAMETERS PTY LTD**

# Enjoy great Hi-Fi Sound While on the Move...

## Fit a DOMINION Car Stereo

**DOMINION Model 4100 \*\$61.20**




Mini under-dash cassette stereo player, 5 watts per channel, fast forward, rewind, auto stop, with slider volume and tone and balance controls.  
 Dimensions: 5 1/4" wide x 6 1/2" deep x 2" high.

**SPECIAL OFFER**

With each DOMINION car stereo purchased: One pair 5" 5 Watt car wedge speakers or One pair 7" x 5" speakers with black metal grilles at NO EXTRA CHARGE.

\*Quantity discounts on application.

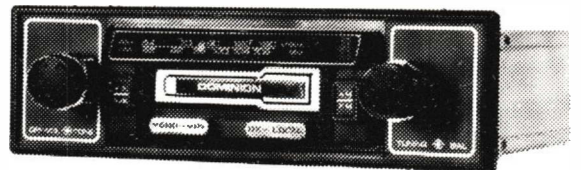**DOMINION Model 4511 \*\$99.45**  
 With stereo FM radio



High quality, in-dash mounting stereo cassette player. With a sensitive AM/FM stereo radio. A DX local-long distance reception switch, fast forward control, 5 watts output per channel. Dimensions: 7 wide x 5" deep x 2" high.

Distributed throughout Australia by:

**radioparts** GROUP

562 Spencer Street, North Melbourne. Phone 329-7888  
 1097 Dandenong Rd., East Malvern. Vic. Phone: 211 8122



# Antennas - Part 2

Last month Roger Harrison, VK2ZTB, looked at the basic concepts of antennas and showed you how to build simple dipoles and baluns. In this final part he describes other popular antennas and their construction.

ANOTHER ARRANGEMENT OF the basic dipole is the 'folded dipole' or 'two-wire' dipole. The advantage of this is that it transforms the impedance of the feedpoint by a factor of four. This allows the use of higher impedance two-wire balanced feedlines such as the 300 ohm flat TV ribbon type. This has the advantage of being cheaper. It is also possible to construct your own two-wire feedline. The folded dipole also has the advantage of increasing the bandwidth of a dipole which is generally in the vicinity of only 2%-5% of the resonant frequency of the antenna. However, the bandwidth of an ordinary single-wire dipole is quite adequate to cover the novice bands.

Nevertheless, if you have plenty of 300 ohm TV ribbon on hand, or only wish to spend a limited amount on the antenna and feedline, particularly where there is a long run of feedline involved, the folded dipole is a good alternative.

The basic construction is shown in Fig.13. The lengths are obtainable from Fig.6. The centre insulator can be made in a similar manner to the one illustrated in Fig.9 or the feedpoint joint can be sandwiched between two blocks of plastic screwed together. The antenna itself can be made from TV ribbon as illustrated. One wire is cut at the centre to make the feedpoint to which the 300 ohm feedline is connected. Each wire is soldered together at the ends. Alternatively, two wires of about 14 gauge to 18 gauge (or 10/010 hookup wire) are run parallel to each other, using wooden or plastic spacers. The wires can be spaced anywhere between 100 mm and 200 mm apart. Use wider spacing, say 200 mm, on 3.5 MHz and narrower spacing on the 21 MHz and 27 MHz bands.

The feedline is ordinary 300 ohm TV ribbon which is a very inexpensive feedline. As most transmitters are

arranged to have a low impedance unbalanced output, generally 50 or 70 ohms, a balun will be necessary. The transformation from 300 ohm to 70 ohms is about four-to-one (4:1). Consequently a suitable balun must not only convert from balanced to unbalanced but also transform the impedance by the appropriate ratio. This may be purchased or you can make one.

There are two simple methods that can be used to make this sort of balun. As for the 1:1 balun, you can make a wideband 4:1 transformer, or construct a balun from coax.

**Wideband 4:1 Balun Construction.** This is constructed in exactly the same manner as the 1:1 transformer using three, 180 mm lengths of enamelled copper wire twisted together at about two twists per 10 mm. Wind three turns through the two holes of the balun core previously recommended. (Neosid type 1050-1-F14). Find and identify the

three starts and finishes, and then connect them as shown in Fig.14.

It does not matter a great deal in this application if the transmitter output and receiver input is intended to match into 50 ohms, as the mismatch is quite small and most circuits will cope with this with little or no degradation in performance.

### Coaxial Cable 4:1 Balun Construction.

This type of balun is sometimes referred to as a 'trombone' balun as its form, illustrated in Fig.15, is reminiscent of that instrument. A loop of coax is added, in series with the feedpoint end of the coax feedline as shown. This results in a 4:1 impedance transformation as well as a balanced-to-unbalanced transformation.

The three ends of the coax lines may be taped together and the inner and outer conductors connected as in Fig.15. Alternatively, three coax plugs may be used to terminate the ends of

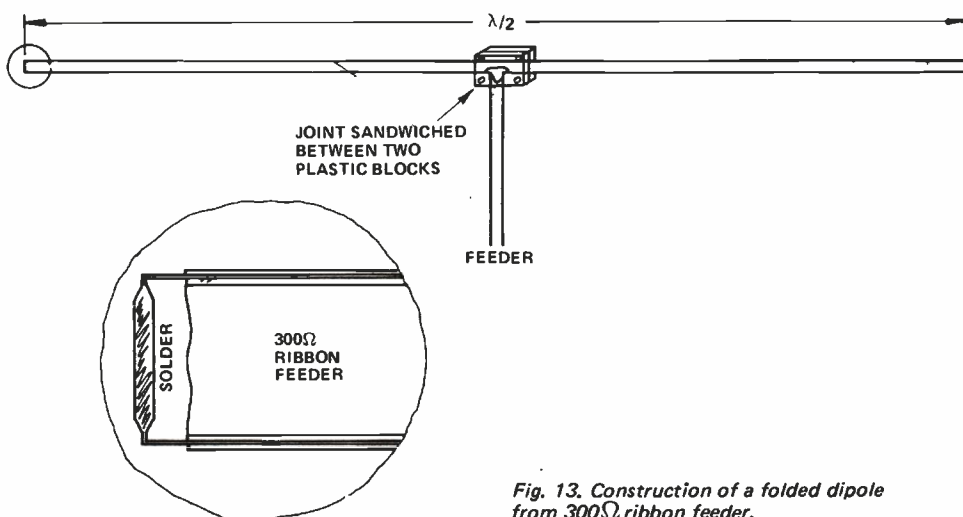


Fig. 13. Construction of a folded dipole from 300Ω ribbon feeder.

# Antennas

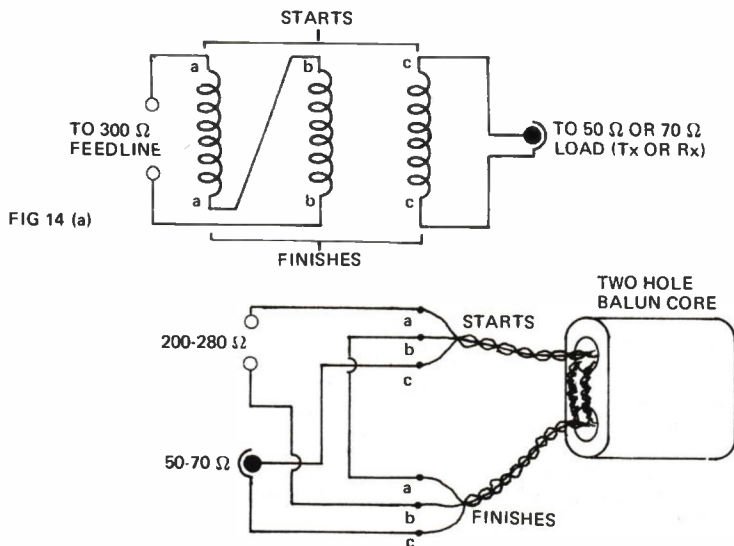


Fig. 14. Construction and connections for a 4:1 wideband balun transformer.

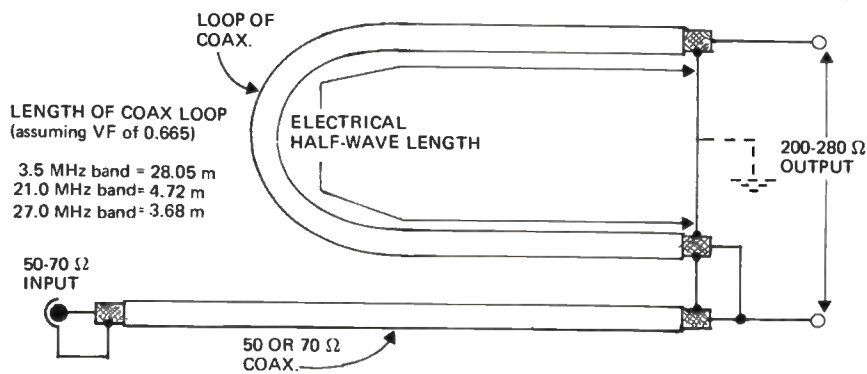


Fig. 15. Coax balun giving 4:1 impedance transformation.

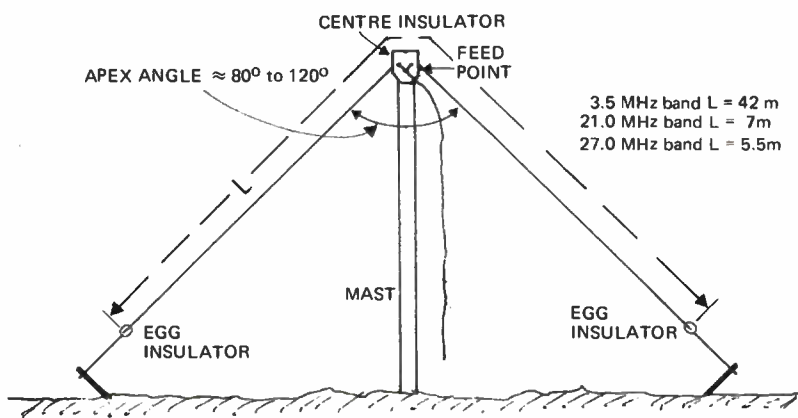


Fig. 16. The "Inverted Vee" dipole.

the feedline and the loop, and these plugged into suitably mounted sockets – whatever takes your fancy.

The length of the loop is an electrical half-wavelength, taking into account the velocity factor of the cable. The lengths given in Fig.15 are for polyethylene insulated coax, having a velocity factor of 0.665. The trombone loop may be suitably coiled and taped for convenience. This sort of balun is too heavy to suspend from the feedpoint of a folded dipole and it is probably easier to mount the balun somewhere near the transmitter and receiver.

## THE INVERTED-VEE DIPOLE

To erect any of the dipoles just discussed, two supports are needed, one for each end. This is not always convenient. A dipole may be supported at the centre and the elements taken down at an angle as illustrated in Fig.16. However, this changes the resonant frequency of the antenna and it needs to be somewhat longer than a plain dipole cut for the same frequency. The angle between the elements may be between 80° and 120°.

The lengths given in Fig.16 are a compromise as the actual length for resonance of the antenna on the desired frequencies will vary depending on the apex angle and the height of the ends above the ground. The apex angle should not be less than 80° as the currents in the elements tend to cancel and the antenna efficiency suffers.

Coax may be connected directly to the feedpoint if necessary, but the use of a 1:1 balun is recommended. The inverted-vee may be constructed like the folded dipole if the use of 300 ohm TV ribbon feedline is contemplated.

As the actual resonant frequency of an inverted-vee varies depending on its construction, trimming the lengths may be a desirable procedure to obtain maximum efficiency. For this operation, one needs a suitable SWR indicator, or better still, an impedance bridge and lots of patience. The ends are trimmed equally a little at a time, for minimum SWR or for best null on the impedance bridge, at the centre frequency of the band of interest.

The ends may be only a metre or so off the ground for the 3.5 MHz antenna.

The inverted-vee antenna has a largely omnidirectional radiation pattern in the horizontal plane. It also has the advantage of being able to receive and radiate vertical as well as horizontally polarized signals and it also exhibits a

In my article in the MAY issue on ANTENNAS, a vile canard has been perpetrated in Fig. 10 on page 26. There is NO SUCH THING as a ferrite balun core made by Phillips, type 4322-020-3150. It is also mentioned in the text on the same page. Sorry 'bout that folks. Apologies all round.



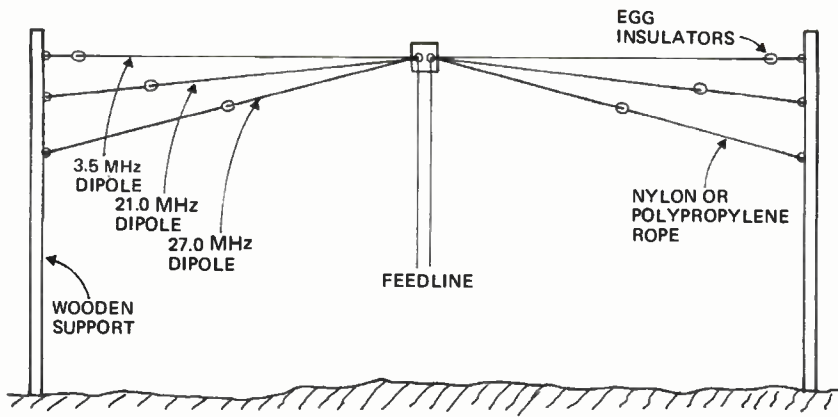


Fig. 17. The multiband dipole.

low radiation angle making it a good antenna for DX working.

### THE MULTIBAND DIPOLE

The multiband dipole is illustrated in Fig.17. In essence, it is simply a number of dipoles constructed for different bands, paralleled at the feedpoints.

It can be fed directly with coax, although this is not really recommended. It is better practice to use an appropriate balun (1:1) as previously described. Only the wideband balun can be used as the coaxial baluns are single frequency devices.

The lengths can be obtained from Fig.6. Each dipole need not be attached to the same support so that they all lie in the same plane as illustrated, but they may be run at angles to one another. In fact, this is a good idea if you can physically arrange it.

### THE SINGLE-LOOP ANTENNA

This antenna consists of a single square loop of wire, approximately one wavelength long, mounted vertically, appearing as a diamond, and fed in one corner. Owing to its size, it is rather too large to be practical on the 80 metre band. The antenna, and dimensions for 21 MHz and 27 MHz, is illustrated in Fig.18. It presents a good match to 50 ohms at the feedpoint and either of the 1:1 baluns is recommended for feeding a coax cable.

The wire used should be a heavy gauge (14g to 18g B & S) single strand wire (enamelled or tinned copper wire). Alternatively, 10/010 or heavier hookup wire could be used. Install egg insulators at the corners B and D, to take the two guy ropes. Insulate corner C also if a metal mast is used. Instead of using two guy wires to hold out the two corners B and D, a wooden cross-arm could be used.

The single-loop antenna has a bi-directional radiation pattern,

broadside to the plane of the loop. Because of this, it is preferable to orient the loop broadside to the main direction you wish to work. This antenna can be rotated if you wish, in which case it should be constructed with the cross-arm supporting corners B and D. It is a very effective and yet simple antenna for DX working on 21 MHz and 27 MHz. Mount it as high as possible to gain the most effectiveness from it. It has some gain over a dipole which is an advantage, and a low radiation angle which is, naturally, helpful for DX working.

### A NOTE ABOUT FEEDLINES

As far as possible, the feedline should always be run away from dipoles at right angles to the antenna in order not to disturb the radiation.

If you do not wish to use a folded dipole, and yet need to use the inexpensive 300 ohm TV ribbon for a feedline, 4:1 baluns can be mounted at each end of the feedline as shown in Fig.19.

When terminating coax where it is mounted outside, seal the end of the cable with waterproof insulation tape or with a proprietary sealing compound (such as Selleys sealing compound). Always solder joints.

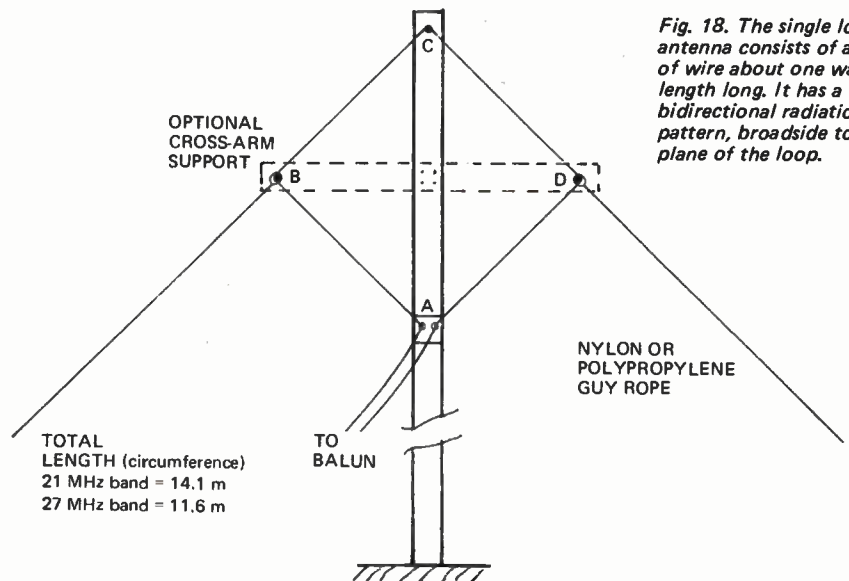


Fig. 18. The single loop antenna consists of a length of wire about one wavelength long. It has a bidirectional radiation pattern, broadside to the plane of the loop.

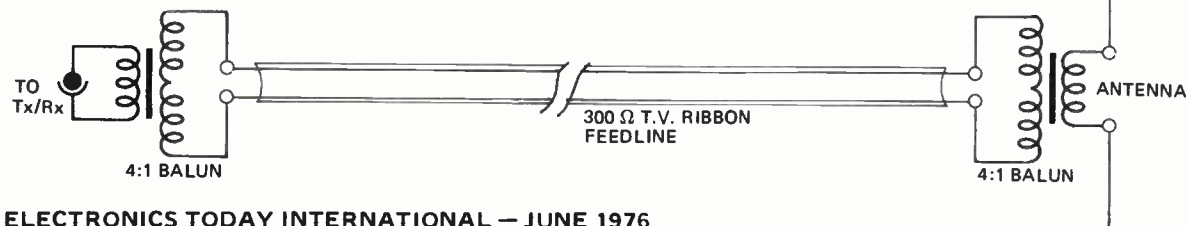


Fig. 19. Using inexpensive 300 ohm TV ribbon to feed an antenna with a low impedance feedpoint, instead of using coax.





## Does your system hunger for one?

Hi fi systems also need the right kind of nourishment. One of the most effective ways of providing it is featured above: the AKAI AA-1020 AM/FM Tuner Amplifier.

It puts out 20 effortless watts RMS per channel (both channels driven, from 20 to 20,000 hz, no more than 0.4% THD into 8 ohms load). It comes with the kind of facilities that produce the best kind of sound. And at \$340†, the price isn't likely to turn you off.

But maybe your system hungers for a lot more power, in which case

you should see our more powerful models.

Of course, like all AKAI hi fi equipment distributed by AKAI Australia, it comes with our Complete Protection Plan\*. Which simply means 12 months full parts and labour warranty on all Tape Equipment, 2 years full parts and labour warranty on all Amplifiers, Turntables and Speakers and a lifetime warranty on all GX Tape Heads.

So, if your amplifier isn't all it should be, see your AKAI dealer. He'll put your mind at ease.


The AKAI Hi-Fi Professionals are: **NEW SOUTH WALES — SYDNEY CITY AND METROPOLITAN**, Sydney: Douglas Hi-Fi, 338 George Street; Duty Free Travellers Supplies, 400 Kent Street; European Electronics, 187 Clarence Street; Instrol Hi-Fi, Cnr. Pitt & King Streets; Magnetic Sound Industries, 32 York Street; Jack Stein Audio, 275 Clarence Street. **Bankstown**: Selsound Hi-Fi, Cnr. North Terrace & Apian Way, Burwood: Electronic Enterprises, 11 Burwood Road; Edge Electrix, 31 Burwood Road. **Concord**: Sonarta Music Services, 24 Cabarita Road. **Cremorne**: Photo Art & Sound, 287 Military Road, Crows Nest: Allied Hi-Fi, 330 Pacific Highway. **Hurstville**: Hi-Fi House, 127 Forest Road. **Liverpool**: Miranda Stereo & Hi-Fi Centre, 166 Macquarie Street. **Miranda Fair**: Miranda Hi-Fi & Stereo Centre, Shop 67, Top Level, Mona Vale: Warringah Hi-Fi, Shop 5, Mona Vale Court, Parramatta: Gramophone Shop, Shop 151, Westfield Shoppingtown; Selsound Hi-Fi, 27 Darcy Street. **Roselands**: Roselands Hi-Fi, Gallery Level, South Hurstville: Selsound Hi-Fi, 803 King George's Road, Summer Hill: Fidelia Sound Centre, 93B Liverpool Street, Sutherland: Sutherland Hi-Fi, 5 Boyle Street. **Waitara**: Hornsby Hi-Fi, 71 Pacific Highway, Westleigh: Sound Incorporated, 16 Westleigh Shopping Centre. **NEW SOUTH WALES COUNTRY**, Albury: Haberecht's Radio & TV, 610 Dean Street. **Bega**: Easdowns, 187-191 Carp Street. **Bowral**: Fred Hayes, 293 Bong Bong Street. **Broken Hill**: Pee Jay Sound Centre, 364 Argent Street, Gosford: Gosford Hi-Fi, 163 Mann Street; Miranda Stereo & Hi-Fi Centre, Cnr. Donnison & Baker Streets, Moss Vale: Bourne's Merchandising, 1 White Street. **Newcastle**: Ron Chapman Hi-Fi, 880 Hunter Street; Eastern Hi-Fi, 519 Hunter Street. **Nowra**: Nowra Hi-Fi, Shoalhaven Arcade, Taree: Taree Photographics, Graphic House, 105 Victoria Street. **Wagga Wagga**: Haberecht's Radio & TV, 128 Bavis Street. **Wollongong**: Hi-Fi House, 268 Keira Street; Selsound Hi-Fi, 2-6 Crown Lane, A.C.T., Civic: Allied Hi-Fi, 122 Bunda Street, Fyshwick: Allied Hi-Fi, 4 Paragon Mall, Gladstone Street. **QUEENSLAND**, Brisbane: Chandler's, 120 Edward Street; Chandler's, 399 Montague Road, West End: Stereo Supplies, 95 Turbot Street; Tel Air Electronics, 187 George Street, Nambour: Custom Sound, Currie Street, Mt. Isa: The Sound Centre, West Street. **Rockhampton**: Chandler's, 144 Alma Street, Southport: Stokes Electronics, Scarborough Street. **SOUTH AUSTRALIA**, Adelaide: Ernsmiths, 48-50 King William Street; Flinders Trading Co., 55 Flinders Street; J.B. Electronics, 115 Gouger Street, Blackwood: Blackwood Sound Centre, 4 Coromandel Parade. **Glenside**: Steiner Electronics, Conyngam Street. **Moana**: Bob Carmen, 185 Commercial Road. **VICTORIA**, Melbourne: Douglas Hi-Fi, 191 Bourke Street. **Warrnambool**: A. G. Smith, 159 Liebig Street. **WESTERN AUSTRALIA**, Perth: The Audio Centre, 883 Wellington Street, Calista: Hub Hi-Fi, Kwinana Hub, Gilmore Avenue, East Victoria Park: Japan Hi-Fi, 889 Albany Highway, Nedlands: Audio Distributors, Broadway Shopping Centre, Broadway, Midland: Midland Audio, 16B Great Northern Highway, Mosman Park: Audio Distributors, 14 Glyde Street. **W.A. COUNTRY**, Bunbury: Aabel Music, 130 Victoria Street, Kalgoorlie: Hambley's Hi-Fi, Shop 13, Central Arcade, Hannan Street. **TASMANIA**, Burnie: James Loughran & Sons, 29-31 Wilpot Street, Hobart: Quantum Electronics, 181 Collins Street, Launceston: Wuls & Co., 7 Quadrant. **NORTHERN TERRITORY**, Darwin: Pfitzners Music House, Smith Street.

\*The Complete Protection Plan does not cover equipment purchased outside Australia. †Recommended retail price only.


70613R

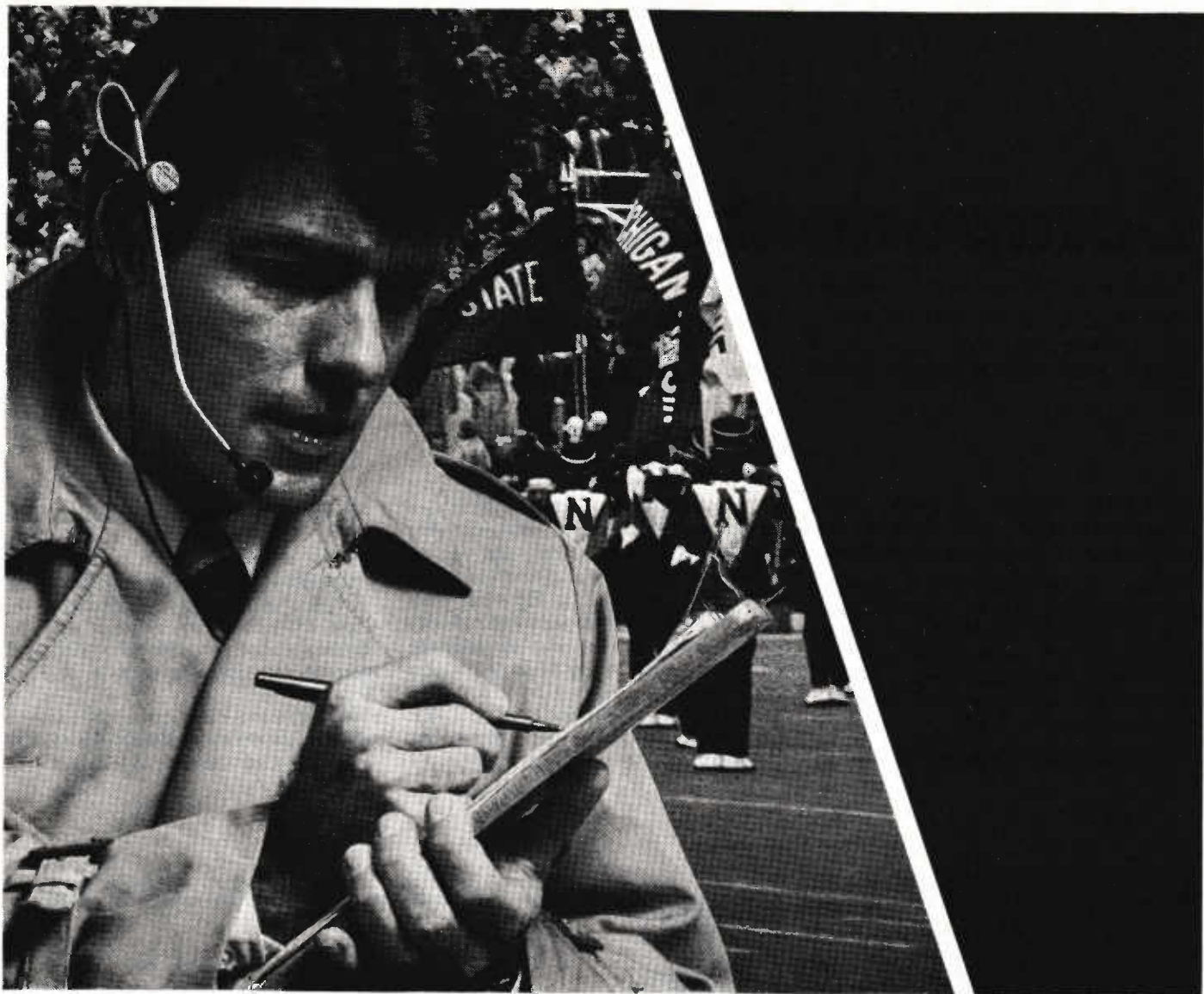**AKAI**  
The name you don't have to  
justify to your friends.





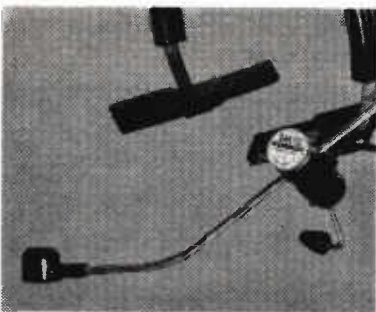**Next best thing  
to a sound proof booth.**



Shure's new headset microphones are coming through loud and clear. With their unique miniature dynamic element placed right at the end of the boom, Shure's broadcast team eliminates the harsh "telephone" sound and standing waves generated by hollow-tube microphones. The SM10 microphone and the SM12 microphone/receiver have a unidirectional pickup pattern that rejects unwanted background noise, too. In fact, this is the first practical headset microphone that offers a high quality frequency response, effective noise rejection, unobstructed vision design, and unobtrusive size.

Distributed in Australia by  
**AUDIO ENGINEERS PTY. LTD.**  
342 Kent Street, Sydney. Write for catalogue.



**AUDIO ENGINEERS (Vic.)**  
2A Hill Street  
THORNBURY. 3071. Vic.

**RON JONES PTY. LTD.**  
57 Castlemaine Street,  
MILTON. 4064. Qld.

**ATHOL M. HILL PTY. LTD.**  
1000 Hay Street,  
PERTH 6000 W.A.

# Component codes and values

This issue carries the third part of our series on electronic components, which so far has dealt only with capacitors. This article looks more generally at the codes used to mark passive components and the ranges of values available.

MODERN FIXED RESISTORS, capacitors and RF chokes are encapsulated in a variety of packages.


For resistors, the most common package is a cylindrical casing having axial leads (Fig 1). Cylindrical body types having radial leads and single-ended types are also manufactured. Some power resistors are rectangular with a square cross-section — Fig. 1. (d).

Fixed capacitor encapsulations take a


wider variety of shapes, which are largely dictated by the manufacturing process. Plastic film and paper capacitors are often cylindrical with axial leads — as shown in Fig 2 (a). They are also moulded into rectangular shapes having leads coming out at opposite ends — as shown in Fig 2 (b), or through one side for convenient printed circuit mounting — as shown in Fig 2 (c). Ceramic capacitors are commonly disc-shaped or square (plate-types) — see

Fig 2 (d) and (e) respectively. Older type ceramic capacitors were usually tubular with radial leads as in Fig 2 (f) although at least one manufacturer still makes and markets capacitors in this style. Moulded mica capacitors are usually square or rectangular with leads coming out opposite ends as in Fig 2 (b).

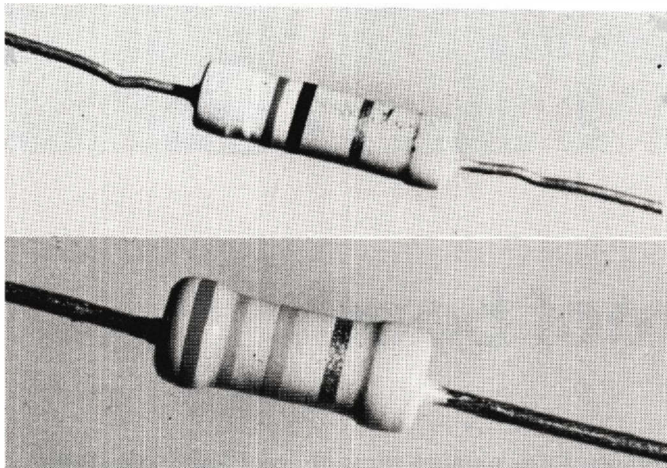Moulded inductors, principally used as RF chokes are generally cylindrical with axial leads, very similar to resistors.




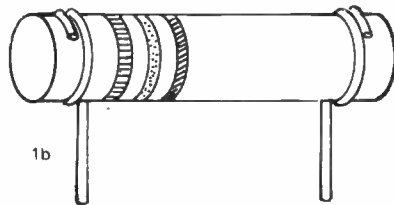1(a) Cylindrical body type with axial leads




1(b) Cylindrical body type with radial leads

Figure 1. Common body shapes of small, modern fixed resistors. RF chokes and some capacitors are similarly encapsulated.

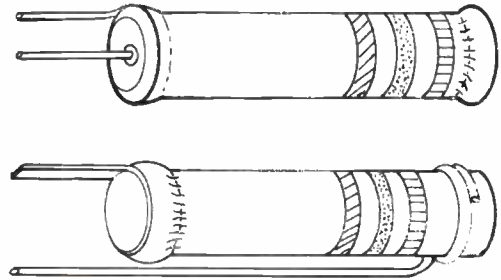

1(c) Single-ended cylindrical body types

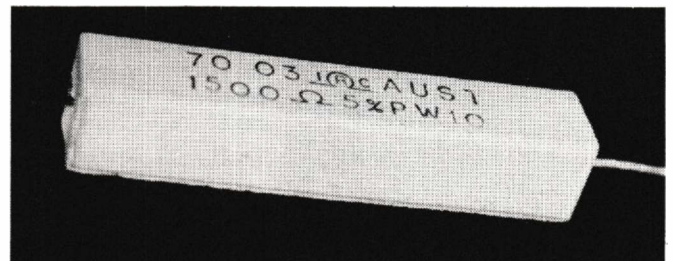


1(d) Rectangular-shaped power resistor






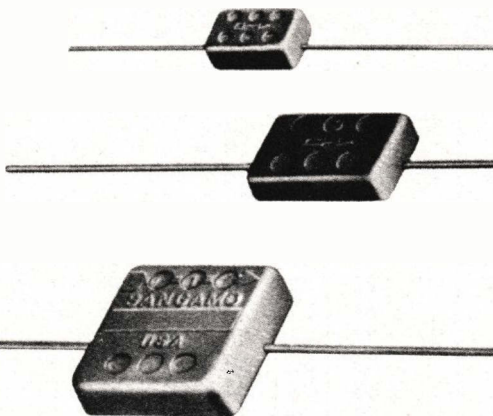2(a) Cylindrical body capacitor with axial leads




2(b) Flat moulded capacitors

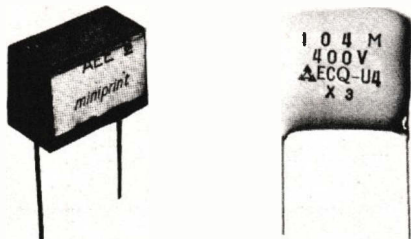

2(c) Flat-moulded capacitors suitable for printed circuit mounting.


Figure 2. Common body shapes for various capacitor styles.

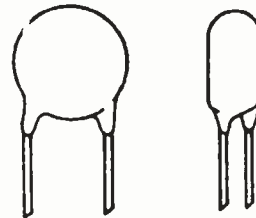

2(d) Disc-shaped ceramic



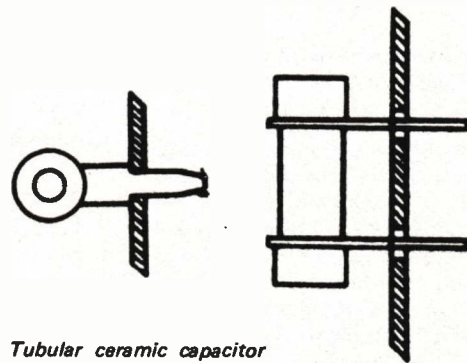2(e) Square- or plate-shaped ceramic capacitor



2(f) Tubular ceramic capacitor

### Component Markings

The value, tolerance and other characteristics are marked on the body of fixed components using one of three basic systems:—

- (d) directly on the body
- (b) a series of coloured bands or dots according to a standard code.
- (c) a series of numbers and letters according to a standard code — known as a typographic code.

The basic colour code is given in Table 1. Its use on typical cylindrical-shaped components is illustrated in Fig 3. The first and second digits represent the significant figures of the component value. The decimal multiplier determines the position of the decimal point and the order of the value of the component — i.e., ohms, megohms etc, or  $\mu F$ , pF etc. The tolerance indicates the tolerance range either side of the nominal value of the component. This means that the actual component value


THE STANDARD COLOUR CODE

TABLE 1

colour	significant figure	decimal multiplier	tolerance $\pm\%$
BLACK	0	1	20 *
BROWN	1	10	1
RED	2	$10^2$ or 100	2
ORANGE	3	$10^3$ or 1000	
YELLOW	4	$10^4$ or 10,000	
GREEN	5	$10^5$ or 100,000	
BLUE	6	$10^6$ or 1,000,000	
VIOLET	7	$10^7$ or 10,000,000	
GREY	8	$10^8$ or 100,000,000	
WHITE	9	$10^9$ or 1,000,000,000	
GOLD	—	$0.1$ or $10^{-1}$	5
SILVER	—	$0.01$ or $10^{-2}$	10
none	—		20

\* used with capacitors

# Component codes and values

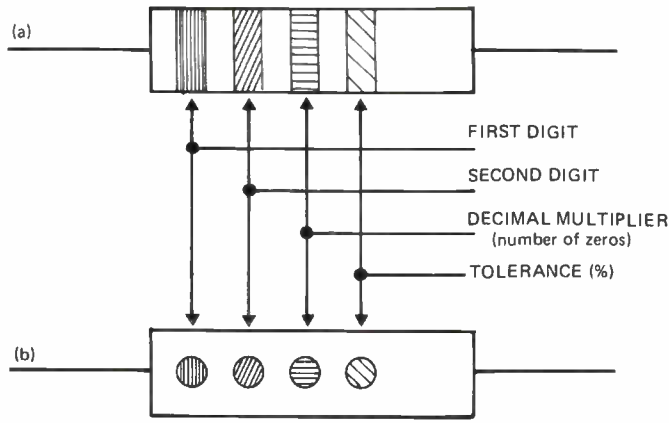

EXAMPLE: — BROWN, BLACK, RED, GOLD.  
 1 0 10<sup>2</sup> ±5%  
 = 1000 (ohm, μF, μH) ±5% tolerance

Fig. 3. How the colour code values on a resistor are used to calculate the value and tolerance.

may lie anywhere between the tolerance extremes. Tolerance is usually quoted as a percentage.

The way in which the standard colour code is applied on a component and how other characteristics, such as voltage rating or temperature coefficient, are indicated is explained in detail in the sections of this series dealing with component marking codes.

Typographic marking codes take a variety of forms. They generally involve a group of numbers indicating the value of the component, and prefix or suffix letters (or both) indicating other characteristics such as voltage rating,

tolerance etc. The letters are deciphered by reference to tables showing the characteristic accorded to a particular letter. These tables are drawn up according to a standard international convention. The different typographic codes used and how to interpret them

are also explained in the sections on component marking codes.

### Preferred Values

If you examine the values of fixed components, you will notice that the values appear 'odd', and further more,

TABLE 2

Preferred numbers in a decade for the E6, E12, E24 & E96 series						
E6 20%	E12 10%	E24 5%	E96 1% and 2%			
10	10	10	10.0	10.2	10.5	10.7
		11	11.0	11.3	11.5	11.8
	12	12	12.1	12.4	12.7	
		13	13.0	13.3	13.7	14.0 14.3 14.7
15	15	15	15.0	15.4	15.8	
		16	16.2	16.5	16.9	17.4 17.8
	18	18	18.2	18.7	19.1	19.6
		20	20.0	20.5	21.0	21.5
22	22	22	22.1	22.6	23.2	23.7
		24	24.3	24.9	25.5	26.1 26.7
	27	27	27.4	28.0	28.7	29.4
		30	30.1	30.9	31.6	32.4
33	33	33	33.2	34.0	34.8	35.7
		36	36.5	37.4	38.3	
	39	39	39.2	40.2	41.2	42.2
		43	43.2	44.2	45.3	46.4
47	47	47	47.5	48.7	49.9	
		51	51.1	52.3	53.6	54.9
	56	56	56.2	57.6	59.0	60.4
		62	61.9	63.4	64.9	66.5
68	68	68	68.1	69.8	71.5	73.2
		75	75.0	76.8	78.7	80.6
	82	82	82.5	84.5	86.6	88.7
		91	90.9	93.1	95.3	97.6

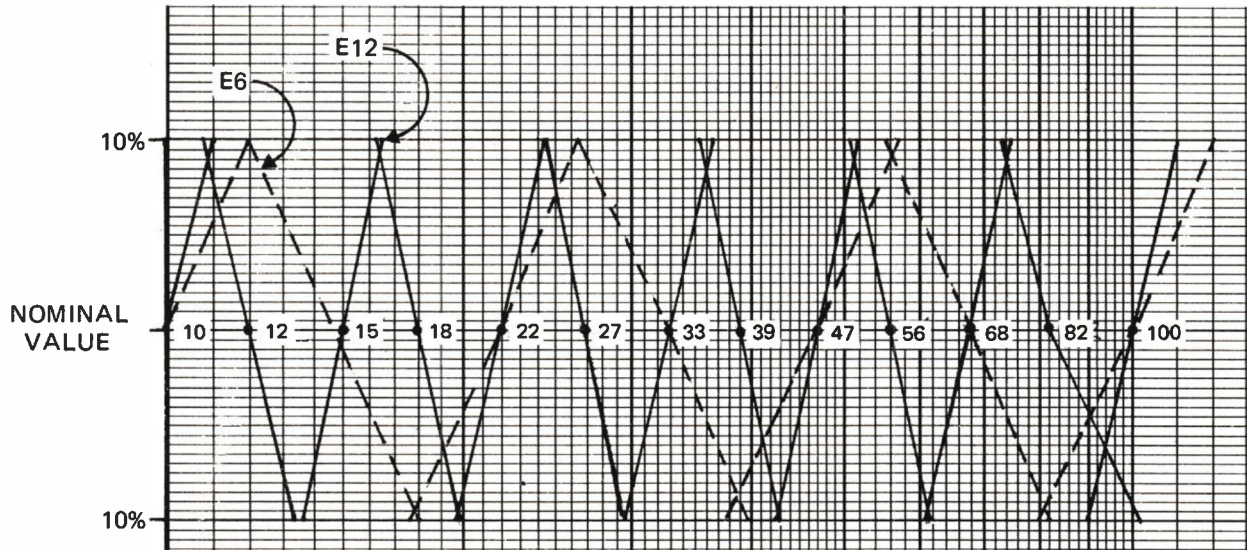


Figure 4: Tolerance extremes of the E6 and E12 preferred series of values.



that the same significant figures repeat in each decade — i.e., 47, 470, 4700; .0068, .068, 0.68 etc. This is because a system of what is called 'preferred numbers' or 'preferred values' is used. The basic system of preferred numbers spans the decade from 10 to 100. Higher and lower decades simply have the decimal place shifted right or left accordingly.

There are several preferred number series, the three most common ones have six, twelve and twenty four numbers per decade and are known as the E6, E12 and E24 series respectively. The numbers in a decade of each of these series are given in Table 2. Each number is derived from a constant difference between numbers (or steps) of  $10^{1/6}$  for the E6 series,  $10^{1/12}$  for the E12 series and  $10^{1/24}$  for the E24 series. The numbers are rounded off to two significant figures for convenience. These numbers provide a convenient tolerance range for component values in the different series. The E6 series is used for  $\pm 20\%$  tolerance components, the E12 series for  $\pm 10\%$ , and the E24 series for  $\pm 5\%$  components.

For close tolerance, high stability components, the E96 series is used. This provides a series of 96 numbers per decade, each being approximately 2% higher than the preceding value. Thus, this series is used for components having specified tolerances of 1% and 2%. The tolerance extremes of 1% components overlap. As the values need to be quoted to three figures, the component markings will, accordingly, be different from those components having values

TABLE 3

Tolerance extremities for the E6, E12 and E24 preferred value series						
-20%	-10%	-5%	nominal value	+5%	+10%	+20%
8	9	9.5	10	10.5	11	12
		10.5	11	11.6		
	10.8	11.4	12	12.6	13.2	
		12.4	13	13.7		
12	13.5	14.3	15	15.8	16.5	18
		15.2	16	16.8		
	16.2	17.1	18	18.9	19.8	
		19.0	20	21.0		
17.6	19.8	20.9	22	23.1	24.2	26.4
		22.8	24	25.2		
	24.3	25.7	27	28.4	29.7	
		28.5	30	31.5		
26.4	29.7	31.4	33	34.7	36.3	39.6
		34.2	36	37.8		
	35.1	37.1	39	41.0	42.9	
		40.9	43	45.2		
37.6	42.3	44.7	47	49.4	51.7	56.4
		48.5	51	53.6		
	50.4	53.2	56	58.8	61.6	
		58.9	62	65.1		
54.4	61.2	64.6	68	71.4	74.8	81.6
		71.3	75	78.8		
	73.8	77.9	82	86.1	90.2	
		86.5	91	95.6		
E6	E12	E24		E24	E12	E6

← lower extremities
upper extremities →

New Low Price  
**\$269**  
 FOR/FOA Sydney



# KENWOOD QR666

**High performance Communications Receiver**  
 For the short wave listener or amateur radio operator.




This high performance, solid state receiver covers the frequencies 170 KHz-30 MHz with 6 bands, receiving in the AM, SSB and CW modes. Three way power supply operates from 110/240V AC, internal or external 12V DC. The unit includes a 500 KHz marker oscillator.

**Available from your radio dealer or your Kenwood Amateur Radio Equipment dealer:**

- MITCHELL RADIO COMPANY, Albion, QLD
- DICK SMITH ELECTRONICS, Gore Hill, NSW
- VICOM, Artarmon, NSW
- DIGITRONICS, Newcastle West, NSW
- VICOM INTERNATIONAL, Auburn, VIC
- HAM RADIO SUPPLIERS, Melbourne, VIC
- FARMERS RADIO, Adelaide, SA
- INTERNATIONAL COMM. SYSTEM, Pt Adelaide, SA
- WILLIS TRADING COMPANY, Perth, WA WE502

\*Recommended retail price

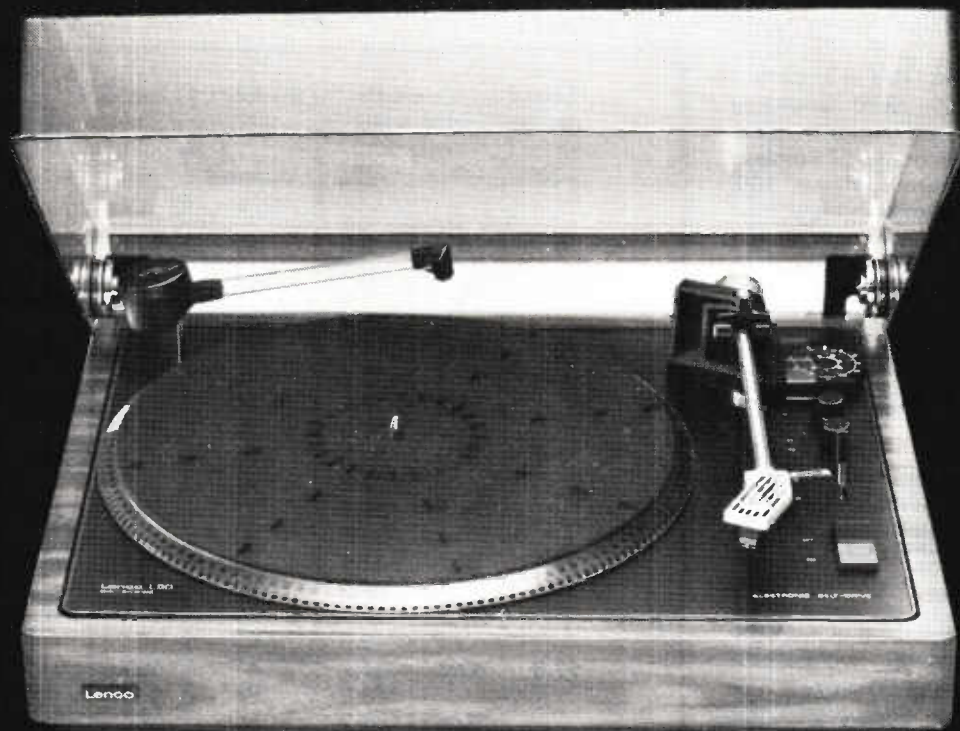Kenwood Amateur Radio Equipment is marketed in Australia by Weston Electronics Company, P.O. Box 71, KINGSGROVE, NSW 2208.



# Lenco.

## A masterpiece of Swiss precision.

Photimport proudly present the precision-engineered Lenco range of Hi-Fi turntables. In Australia, test results have shown that wow and flutter are almost impossible to measure in Lenco equipment. For those who seek near-perfection in sound reproduction at a reasonable price, Photimport highly recommend Lenco.

## Engineered for incomparable sound.

### L90

The L90 Lenco Electronic Hi-Fi—a new top-ranking belt-driven transcription turntable. 16-pole synchronous motor, illuminated strobe, dampened spring suspension, and anti-skating device. As precise as a Swiss watch—to give superb quality sound.

### L65

The L65 Lenco Automatic belt-driven Hi-Fi turntable. Light aluminium tone arm. After selection of record diameter, tone arm lowers itself automatically onto the record. After playing, it returns itself to tone arm rest. Viscously dampened suspension. A high-quality instrument for excellent reproduction of sound.

### L60

The L60 turntable, precision engineered for superb quality sound reproduction. Manual operation, but with all other advanced features of the L65. An opportunity for music lovers to obtain Lenco's renowned sound transcription at a moderate price.

# PHOTIMPOR

MELBOURNE ADELAIDE BRISBANE PERTH SYDNEY

Head Office: 69 Nicholson Street, East Brunswick, Vic. 3057  
Australia. Telephone: 38 6922

For descriptive literature and specifications send a 30 cent stamp to  
**Qualitron Industries Division** of Photimport at the above address.



# Component codes and values

in the E6, E12 or E24 series. The values in the E96 series are also shown in Table 2.

The tolerance specification indicates that a component may have a value, differing from the nominal value, anywhere between the limits specified. For example, a 1000 ohm resistor with a tolerance specification of  $\pm 10\%$  may have a value anywhere between 900 ohms and 1100 ohms.

The tolerance extremities for the E6, E12 and E24 series are indicated in Table 3 and the way in which the tolerance extremes overlap are illustrated, for the E6 and E12 series, in Fig. 4.

A batch of components of the same nominal value may not have actual values spread throughout the tolerance range, centred on the nominal value. For example, a batch of  $\pm 20\%$  tolerance components may have actual values between +10% and +17% of the nominal value. More usually, actual values may be spread between say, -18% and +11% with a few outside this range. Those components falling within the tolerance extremities of the closer tolerance series are usually selected from the batch prior to marking. Thus, a batch of  $\pm 20\%$  tolerance (E6 series) components of a particular nominal value, may not contain any values within  $\pm 5\%$  of the nominal value. However, there may be many in the batch within  $\pm 5\%$  (or closer) of a value 10% higher than the nominal value. As an example, a batch of 1000 ohm resistors may have most of the actual values spread between 1045 ohms and 1155 ohms, with the rest scattered across the tolerance range.

Apart from resistors, capacitors and RF chokes, zener diodes are manufactured according to the preferred values system also, having nominal zener voltages according to the E24 series and voltage tolerances of  $\pm 2\%$  and  $\pm 5\%$ .

The temperature coefficient characteristic of capacitors may also be specified with values in the preferred series, usually from the E24 series, although for convenience, and by convention, only selected numbers through several decades are used. This is discussed in the section on capacitors.

## Selecting and Substituting

In many applications in electronic circuits, the component values, unless otherwise specified, may be varied substantially without markedly affecting the performance of a circuit. This applies particularly to decoupling and bypass components where components having tolerances of -20%, +80% are commonly used. Apart from this, tolerance limits of component values in a particular circuit or portion of a circuit, of  $\pm 20\%$  are common, otherwise the E6 series of values would not be used. This wide latitude in tolerance limits rarely has much effect on the performance of a circuit. If close tolerance components are necessary then they will be specified on the circuit or in any description of the circuit.

(It should be noted however that 5% tolerance resistors are now almost universally available and cost little more - if anything at all - than 10% or 20% resistors. For this reason, 5% resistors are generally specified for Electronics Today's projects).

E24 5%	E12 10%	E6 20%
7.5		
8.2	8.2	
9.1		
10	10	10
11		
12	12	
13		
15	15	15
16		
18	18	
20		
22	22	22
24		
27	27	
30		
33	33	33
36		
39	39	
43		
47	47	47
51		
56	56	
62		
68	68	68
75		
82	82	
91		
100	100	100
110		
120	120	
130		

TABLE 4


## CHOOSING THE RIGHT VALUE

- (1) **SUBSTITUTION:** If a component cannot be replaced by a substitute of the same nominal value and tolerance rating, it can be replaced by a closer tolerance component of any of the 3 values shown in the next column on the left.
- (2) **DESIGN:** Find the nearest value (to the calculated value) in the left-hand column. If high tolerance is not important an appropriate value from the column on the right may then be selected.

**ETI**  
by **jaycar**  
PTY LTD.


PROFESSIONAL SOUND  
EQUIPMENT FOR THEATRE  
AND ROCK BANDS

AUDIO EXPANDER  
COMPRESSOR

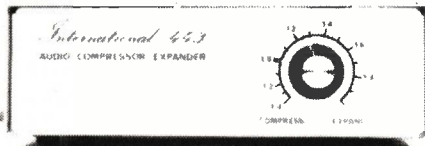


Complete Kits Now  
Available at \$80.00.


ETI 3600 and 4600  
MUSIC SYNTHESISERS

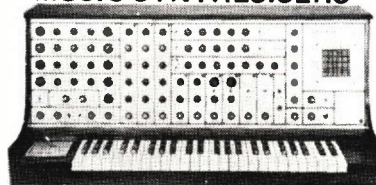

STAGE MIXER

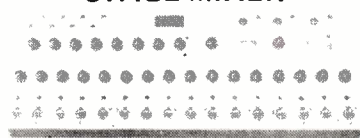

414 MASTER MIXER

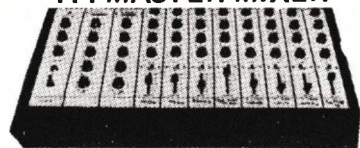

For audio engineers we have a wide range of electronic components at wholesale prices, cannon plugs and sockets, microphone cable etc., also available:- electronic cross-overs 100 watt power slaves  
Send stamped addressed envelope for price lists.

**jaycar**  
PTY. LTD

Telephone 211-5077  
P.O. BOX K39, HAYMARKET  
N.S.W. AUSTRALIA 2000  
405 Sussex St, Sydney  
ENTRANCE OFF LITTLE HAY ST.

# The problem with buying a receiver today is that someone, somewhere has one better.



## Here it is.

The RX 802 AM/FM Stereo Receiver by Rotel. It's the top of our line and probably the best receiver your dollars could buy.

What makes it the best? Engineering precision. 2x50 watts RMS continuous power, both channels driven into 8 Ohms with less than 0.5% THD from 20 to 20,000 Hz. Ceramics filters, integrated circuits and an AM/FM tuner section with 1.5  $\mu$ V sensitivity, that independent lab reports could only describe as 'outstanding'.

There are also a couple of other points you'll find interesting. Like input jacks for two turntables and input/output jacks for two tape decks.

Which means that you can now dub from one tape deck to another without the inconvenience of having to switch leads.

Or tape, one program while listening to another tape play back. With a flip of a switch and two extra speakers you can even simulate four channel sound.

If you would like to discover more about the RX 802 — or the rest of our line — RX 602, RX402, RX202, please write to the address below and we'll send you the specifications and lab reports to back up our statement that model for model, you won't find better power and performance for the price.

Distributed in Australia by:

# INTERDYN


INTERNATIONAL DYNAMICS  
(AGENCIES) PTY. LTD.  
23 Elma Rd., North Cheltenham,  
Melbourne, Victoria 3192

Available from:  
N.S.W.: M & G Hoskins Pty. Ltd., (Showroom) 400 Kent St., Sydney 2000,  
Telephone 559-4545 & 559-3693. Qld: Stereo Supplies, 99 Turbot St., Brisbane  
4000, Telephone: 21-3623. S.A.: Challenge Hi-Fi, 96 Pirie St., Adelaide 5000,  
Telephone: 223-3599. Tas.: Audio Wholesalers Pty. Ltd., 9 Wilson St., Burnie  
7320, Telephone: 31-4111. Vic.: Enzel Electronics Pty. Ltd., 431 Bridge Road,  
Richmond, 3121, Telephone: 42-3761. W.A.: Albert TV & Hi Fi, 282 Hay St.,  
Perth 6000, Telephone: 25-2699. A.C.T.: Duratone Hi Fi, Cnr. Botany St., &  
Aitree Cr., Phillip 2606, Telephone: 82-1388.





# Scope Cordless 60w Soldering Tool

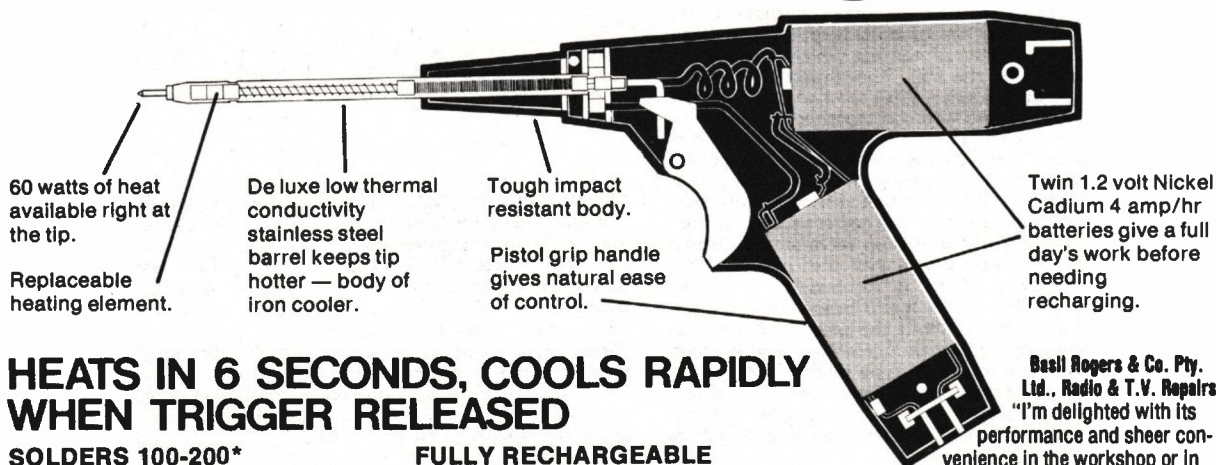

60 watts of heat available right at the tip.

Replaceable heating element.

De luxe low thermal conductivity stainless steel barrel keeps tip hotter — body of iron cooler.

Tough impact resistant body.

Pistol grip handle gives natural ease of control.

Twin 1.2 volt Nickel Cadmium 4 amp/hr batteries give a full day's work before needing recharging.

## HEATS IN 6 SECONDS, COOLS RAPIDLY WHEN TRIGGER RELEASED

### SOLDERS 100-200\* TYPICAL JOINTS BEFORE RECHARGING

\*Light electrical connections. Capacity will vary for lighter or heavier joints.

**PISTOL GRIP DESIGN** balances weight of cells for comfort and tip control.

**FULLY RECHARGEABLE OVERNIGHT**, from car, power-point or Scope Transformer.

**ABSOLUTE SAFETY** No earth leakage currents. Solder anywhere with total personal and component protection.

### Kevin Ball, T.V. Technician.

"In my job I work mainly on circuit boards and I'm rapt with Scope Cordless. I've never reached a point where the gun can't handle a day's soldering. I like the feel of it; tremendous balance."

### Basil Rogers & Co. Pty. Ltd., Radio & T.V. Repairs.

"I'm delighted with its performance and sheer convenience in the workshop or in the field. It's light, fits easily in your hand and you can solder even with the set on."

# SCOPE

Distributors to the Electrical Trade:

**NATRONICS PTY. LTD.** The Crescent, Kingsgrove, N.S.W. 2208

Manufactured by: **SCOPE LABORATORIES, MELBOURNE.**

# 6 TV GAMES ON ONE IC

WHK will distribute one of the most advanced TV Games MOS Circuit in Australia. This 24 Pin device has been designed to provide 6 different games using a standard television receiver. The MOS Circuit is intended to be battery powered and a minimum number of external components are required to complete the system.

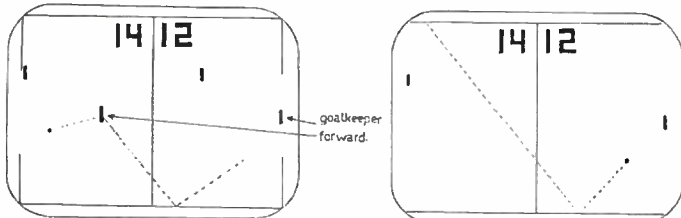


Fig. 2. Football Game

Fig. 1. Tennis Game

**FEATURES:** 6 selectable Games — Tennis, Football, Squash, Pelota or Rifle Shooting — two games; Automatic Scoring; Score display on TV Screen, 0 — 15; Selectable Bat Size; Selectable Angles; Selectable Ball Speed; Automatic or Manual Ball Service; Realism Sounds; Shooting Forwards in Football Game; Visually defined area for all Ball Games.

**OPERATING CHARACTERISTICS: TENNIS & FOOTBALL:** With the Tennis game the picture on the television screen would be similar to Fig. 1 with one 'bat' per side, a top and bottom boundary and a centre net, the individual scores are counted and displayed automatically in the position shown. The detail of the game will depend upon the selection of the options. Considering the situation where small bats are used and all angles, after reset has been applied, the scores will be 0, 0 and the ball will serve arbitrarily to one side at one of the angles. If the ball hits the top or bottom boundary it will assume the angle of reflection and continue in play. The player being served must control his bat to intersect the path of the ball. When a 'hit' is detected by the logic, the section of the bat which made the hit is used to determine the new angle of the ball. To expand on this, all 'bats' or 'players' are divided logically into four adjacent sections of equal length. When using the four angle option it is the quarter of the bat which actually hits which defines the new direction for the ball. The direction does not depend upon the previous angle of incidence. With the two angle option the top and bottom pairs of the bats are summed together and only the two shallower angles are used to programme the new direction of the ball. The ball will then traverse towards the other player, reflecting from the top as necessary until the other player makes his 'hit'. This action is repeated until one player misses the ball. The circuitry then detects a 'score' and automatically increments the correct score counter and updates the score display. The ball will then serve automatically from the centre line towards the side which had just missed. This sequence is repeated until a score of 15 is reached by one side, whereupon the game is stopped. The ball will still bounce around but no further 'hits' or 'scores' can be made. While the game is in progress, three audio tones are output by the circuit to indicate top and bottom reflections, bat hits and scores. The 'football' type is shown in Fig. 2, and with this game each participant has a 'goalkeeper' and a 'forward'. The layout is such that the 'goalkeeper' is in his normal position and the 'forward' is positioned in the opponent's half of playing area. When


the game starts, the ball will appear travelling from one goal line towards the other side. If the opponent's forward can intercept the ball, he can 'shoot' it back towards the goal. If the ball is missed it will travel to the other half of the playing area and the first team's forward will have the opportunity of intercepting the ball and redirecting it forward at a new angle according to the 'player' section which is used. If the ball is 'saved' by the 'goalkeeper' or it reflects back from the end boundary, the same forward will have the opportunity to intercept the outcoming ball and divert it back towards the 'goals'. A 'score' is made in the 'football' game by 'shooting' the ball through the defined goal area. The scoring and game control is done automatically as for the tennis game. The same audio signals are used to add atmosphere to the game.

**SQUASH:** In this game (not illustrated) there are two players who alternately hit the ball into the court. The right hand player is the one that hits first, it is then the left hand player's turn. Each player is enabled alternately to insure that the proper sequence of play is followed.

**PELOTA:** This game is similar to squash except that there is only one player.

**RIFLE SHOOTING:** This game (not illustrated) has a large target which bounces randomly about the screen, a photocell in the rifle is aimed at the target. When the trigger is pulled the shot counter is incremented, if the rifle is on target the hit counter is incremented, a hit noise is generated and the target is blanked for a while. After 15 shots the score appears but the game can still continue.

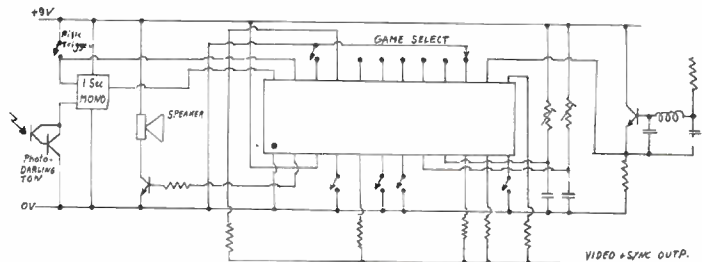**RIFLE GAME NO. 2:** In this game the ball traverses the screen from the right under control of the manual serve button. Otherwise the game is as above.



**PRICE & DELIVERY:** The manufacturer of this "6 in 1 TV Game IC" has received huge orders from Europe. The proposed delivery of our large order is scheduled for October 76. Due to the great demand for this outstanding IC we suggest you place your order now. Price each \$28.00. Prepaid Orders received before August 15th \$25.20 each. Discount: 1 — 4 nett, 5 — 9 less 5% 10 — 24 less 10%, 25 onwards less 15%. Post, Pack & Insurance \$2.00 per Order. With your Order Acknowledgement you receive full Circuit diagrams. We intend to manufacture a PC Board to suit at extra cost. To Companies who wish to manufacture complete units on a commercial basis, we offer this "6 in 1 TV Game IC" at a very special price. (Minimum quantity 500 off).



**W.H.K. ELECTRONIC & SCIENTIFIC INSTRUMENTATION**

MANUFACTURING, IMPORT, EXPORT, WHOLESALE & RETAIL

2 GUM ROAD, ST. ALBANS, 3021. VICTORIA, AUSTRALIA. PHONE: 396-3742 (STD area code 03)

POSTAL ADDRESS: P.O. BOX 147, ST. ALBANS, VICTORIA, AUSTRALIA 3021.



# We've found a tape deck with the beauty of Hasselblad, the clarity of Minolta, and the precision of Bolex.

We searched high and low, reel to reel and deck to deck. For sound recording equipment that has the same high standard of manufacture as our leading camera brands. Top of our list came a brand named Dokorder. Dokorder's reel to reel tape decks are available in two and four channel stereo featuring three-motor and three-head facilities. Dokorder machines range in price from less than \$285 to around \$915. Advanced design features include electronic operation of tape transport, speed change and multi-sync facilities on the more expensive models. Cassette decks are available with amplifier options, the celebrated Dolby noise reduction system and many other special features.

Telephone or drop us a line. We'd be pleased to send you full specification and price details.

## The name is Dokorder.



Second reel (illustrated) extra.

## PHOTIMPORT

Melbourne Adelaide Brisbane Perth Sydney

For descriptive literature and specifications, send a 30 cent stamp to Qualitron Industries Division of Photimport (Australia) Pty. Ltd.

Head Office: 69 Nicholson Street, East Brunswick, Vic. 3057  
Australia, Telephone 386922

PA3/D

# Five watt stereo

This simply-constructed amplifier gives high quality reproduction for surprisingly low cost. The five watts per channel output is sufficient for the average listening room even when inefficient loudspeakers are used.

**THIS PROJECT UTILISES A NEW** advance by IC manufacturers. A few years ago no-one would have believed a complete stereo hi-fi amplifier could be made from just two ICs plus a few passive components. Today more and more components are contained within the IC so a power amplifier is as easy to use as an op-amp.

**Easy to build** — Readers who were previously apprehensive about building audio power amplifiers should have no trouble with this design — there is little to go wrong.

**Adequate Power** — The output is unlikely to be found lacking unless the loudspeakers are very inefficient. Speakers of this type usually belong to the hifi enthusiast who spends lots of money on his system; the inefficiency of the speakers is compensated for in the amplifier. In an average set-up it is unlikely that you would, under normal listening conditions, be able to tell the difference between the ET1444 and a twenty watt amplifier.

## FIVE WATT HI-FI AMPLIFIER

**LM379** — National Semiconductor recently supplied ETI with samples of their new dual five-watt audio amplifier IC — the LM379. The circuitry around the IC is very simple in comparison to most of those previously available. The gain is set in a similar way to that for an operational amplifier: by the ratio of two resistors in the feedback network. In addition the IC features internal stabilization, current limiting and thermal protection.

**Preamp** — We decided to try the IC in conjunction with the dual low-noise preamplifier IC also from National Semiconductor — the LM382. The combination results in a simple stereo amplifier which works very well indeed.

Whilst tone control could be achieved very simply it was decided that the performance of the amplifier deserved good treatment. So we use more effective tone controls.

The result is a five-watt stereo amplifier, ETI 444, simple and inexpensive to build, and with a surprisingly high performance.

## CONSTRUCTION

As with most straightforward projects the use of a printed circuit board is not only desirable from an ease of construction point of view, but it also helps to ensure identical results to those of our prototype.


The components may be assembled to the board in any order but we find it preferable to assemble the low-height components first, ie, resistors, diodes. Before installing IC2 make sure that a hole of about 6 mm diameter is drilled in the board at the end where the heatsink is to be mounted (after the IC is installed). Take care that all polarized components, such as diodes, ICs, electrolytic capacitors and integrated circuits, are mounted with the correct orientation.

Solder 25 to 50 mm lengths of tinned copper to each of the lugs on the potentiometers and then mount the potentiometers in the appropriate

## MEASURED PERFORMANCE OF PROTOTYPE ETI 444

<b>POWER OUTPUT</b>	
Into 8 ohms	5 watts per channel
<b>DISTORTION</b>	
At 3 watts out	0.15%
At 4 watts out	0.5%
At 5 watts out	3.0%
<b>FREQUENCY RESPONSE</b>	
High-level input	+10 dB, 4 Hz to 200 kHz -3 dB
<b>SENSITIVITY</b>	
Magnetic input	1.5 mV
High level input	190 mV
<b>LOAD IMPEDANCE</b>	8 ohms or higher
<b>INPUT IMPEDANCE</b>	
Magnetic input	approx. 100 k
High level input	approx. 10 k
<b>SIGNAL TO NOISE RATIO</b>	
High level input	67 dB
Phono input (ref 10 mV in)	64 dB unweighted



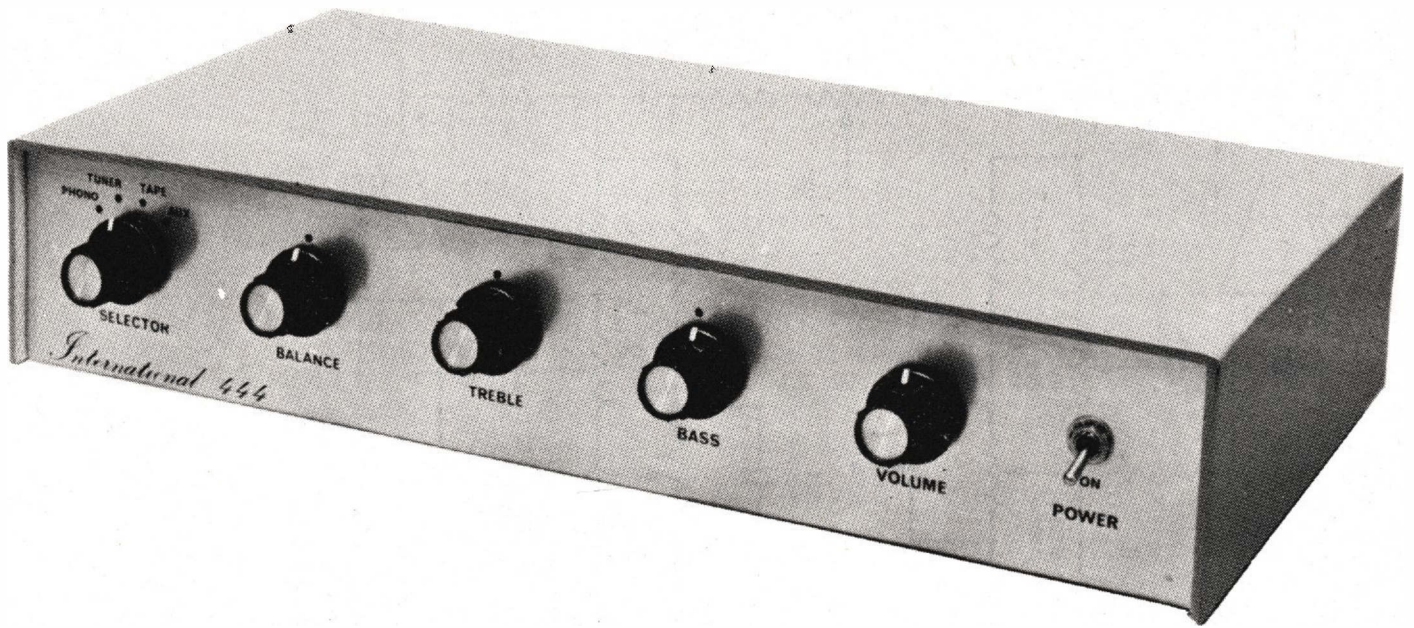

position by threading the tinned copper wires through the holes provided in the printed-circuit board. Pull the wires down so that the lugs are almost flush with the board and the potentiometers are all in line. Then solder the wires.


The heatsink may now be mounted

onto IC2 using a single nut and bolt. Care must be taken to ensure that the heatsink does not touch any of the potentiometers as it is at a potential of  $-12$  volts.

The unit may now be mechanically assembled by securing it to the front

panel by means of the potentiometer shafts and nuts, and by fitting two 6.4 mm spacers between the rear of the board and the chassis.

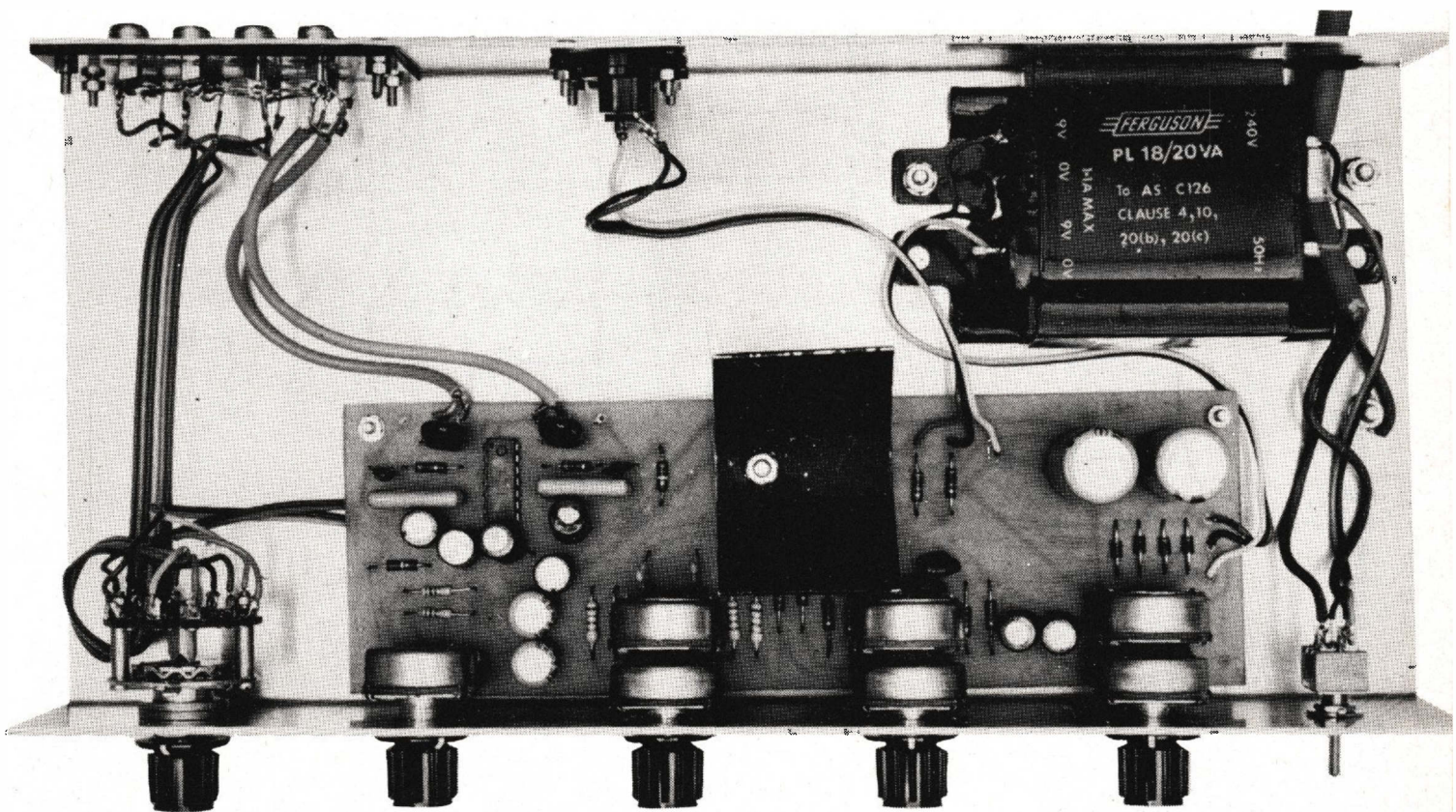Finally wire the unit as shown in the component overlay diagram.



# Five watt stereo

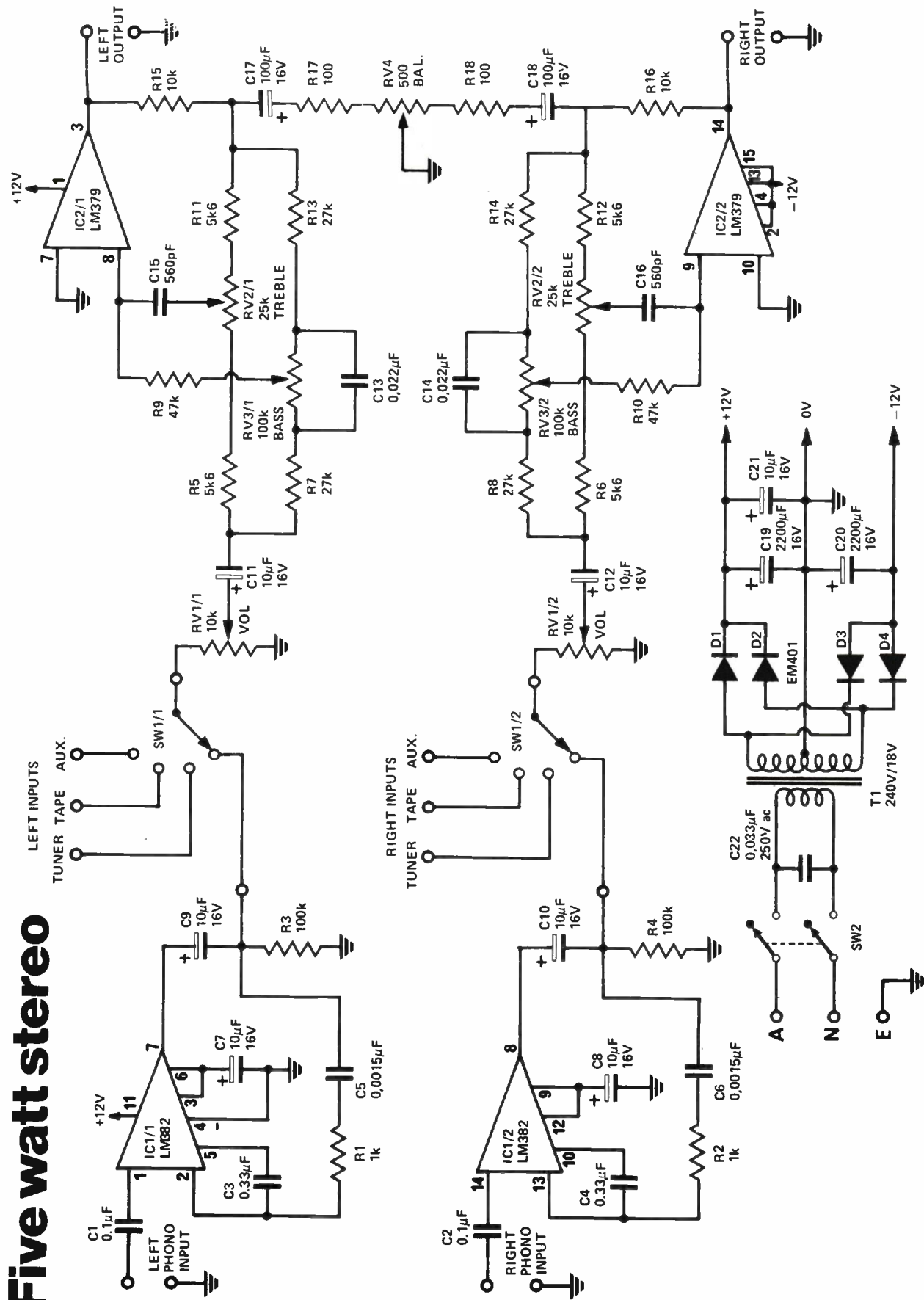


Fig. 1. Circuit diagram of the amplifier.



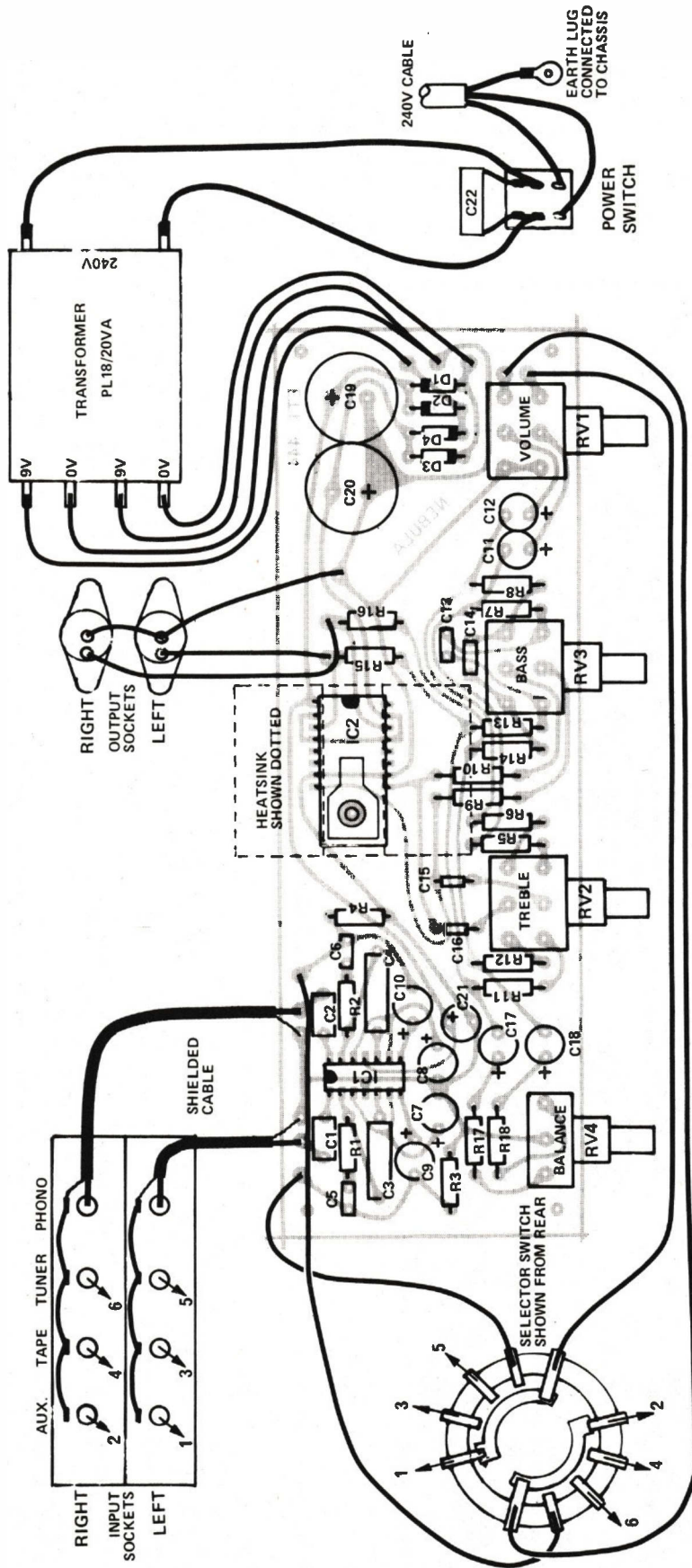


Fig. 2

PARTS LIST — ET1 444

Resistors	1 k	5%	1/2W	RV3	100 k lin rotary dual	C22	0.033 $\mu$ F 250 V ac
R1,2	100 k	"	"	RV4	500 ohm lin rotary	* 1000 $\mu$ F 16 V	is not available.
R3,4	5k6	"	"				
R5,6	27 k	"	"				
R7,8	47 k	"	"				
R9,10	5k6	"	"				
R11,12	27 k	"	"				
R13,14	10 k	"	"				
R15,16	10 k	"	"				
R17,18	100	"	"				
Potentiometers							
RV1	10 k log rotary dual						
RV2	25 k lin rotary dual						
<b>Capacitors</b>							
C1,2	0.1 $\mu$ F polyester						
C3,4	0.33 $\mu$ F polyester						
C5,6	0.0015 $\mu$ F polyester						
C7-C12	10 $\mu$ F 16 V electro						
C13,14	0.022 $\mu$ F polyester						
C15,16	.560 pF ceramic						
C17,18	100 $\mu$ F 16 V electro						
C19,20	2200 $\mu$ F 16 V electro						
C21	10 $\mu$ F 16 V electro						
<b>Switches</b>							
SW1	2 pole 4 position rotary						
SW2	2 pole toggle						
<b>Semiconductors</b>							
D1-D4	EM401 or similar						
IC1	LM382						
IC2	LM379						
<b>Miscellaneous</b>							
PC board ET1 444							
Chassis to Fig 5							
Cover to Fig 6							
Heat sink to Fig 7							
Front panel to Fig 3							
Transformer 240 V-18 V PL 18/20 VA							
3 core flex, plug, clamp, grommet and earth lug							
2 Two pin DIN sockets							
2 Four way RCA sockets							
4 Rubber feet							
2 6.4 mm spacers							
5 Knobs							

**PROTECT YOUR  
MAGAZINES  
ETI BINDERS  
hold 12 copies**

**electronics  
TODAY  
INTERNATIONAL**

Send \$4.50 plus 80c postage  
NSW & A.C.T., \$1.50 postage  
elsewhere with order to

Subscription Department,  
Modern Magazines (Holdings) Ltd.,  
15 Boundary Street,  
Rushcutters Bay. 2011.

**PROJECTS  
FOR YOU**

**IN EVERY ISSUE  
OF**

**electronics  
TODAY  
INTERNATIONAL**

**PLACE YOUR ORDER  
TODAY**

**USE THIS  
COUPON**

**GIVE THIS  
COUPON AND \$12  
TO YOUR LOCAL  
NEWSAGENT**

(If he already delivers your papers — as he probably does —  
there will be nothing more to say; if not, he may make a  
small charge for the service.)

NEWSAGENT .....

Please deliver **ELECTRONICS TODAY INTERNATIONAL**  
for the next 12 months, starting with the ..... issue to:

NAME .....

ADDRESS .....

POSTCODE .....

# Five watt stereo


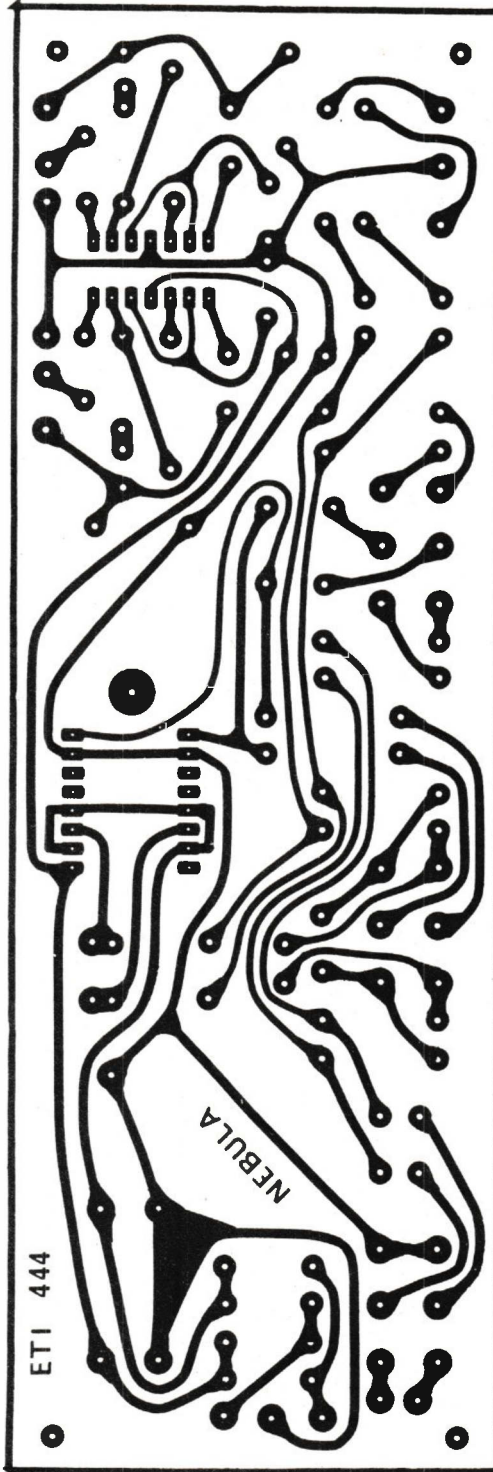


Fig. 3. Front panel artwork. The material we used was brushed anodized aluminium, silk screened black. For size see metalwork detail.

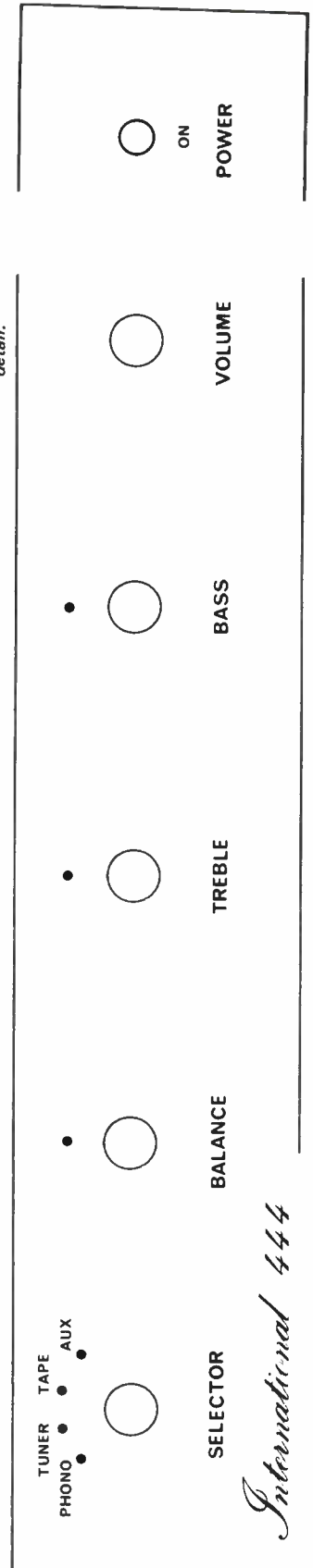




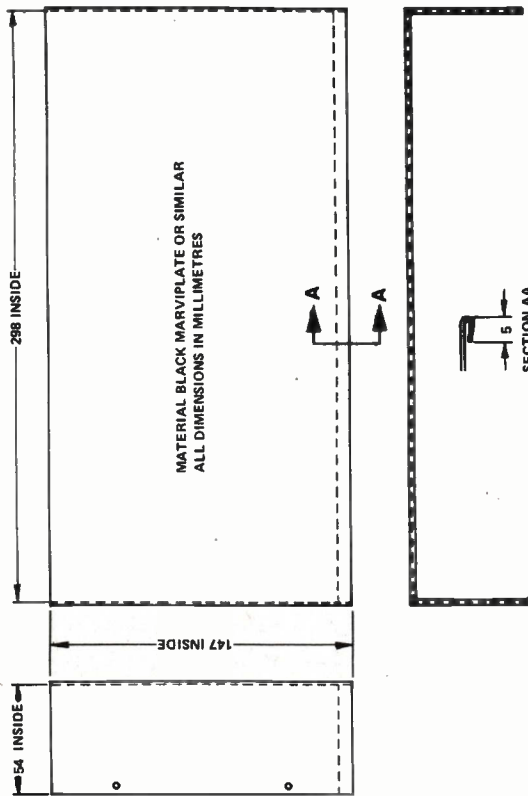


Fig. 6. Cover detail.

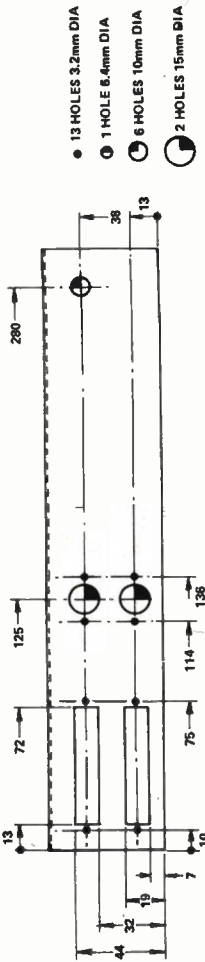

ALL DIMENSIONS IN MILLIMETRES

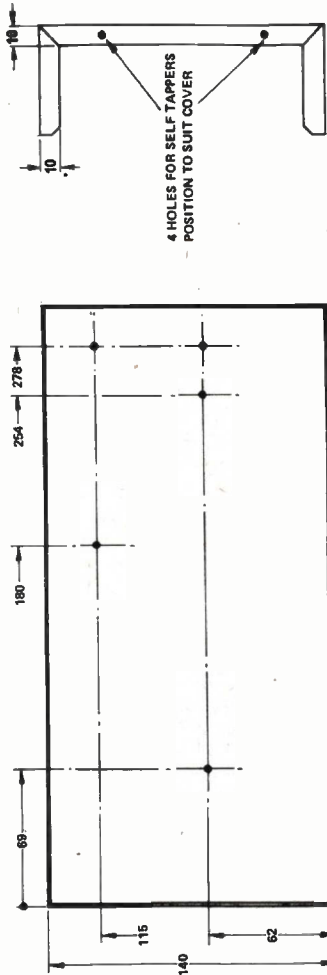


Fig. 5. Chassis metalwork.

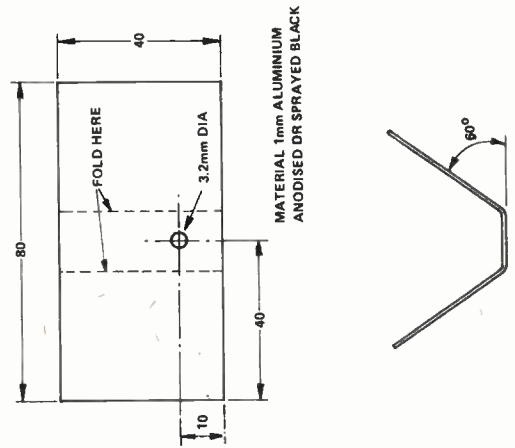
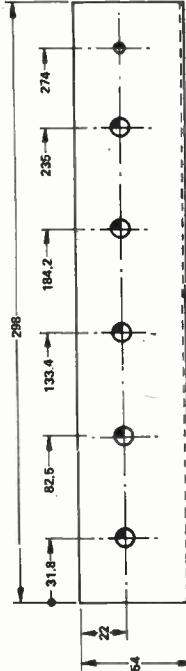


Fig. 7. The heatsink for the LM379. The heatsink described will get quite hot when the amplifier is run at full output. If it has been blackened by painting it may smell a little at first but this will soon pass away. For normal domestic listening this size heatsink will be found to be entirely adequate but if the amplifier is to be run continuously at full sine wave output it would be advisable to increase the size of the heatsink. No damage can be caused by using the smaller heatsink however as the IC is thermally protected and will simply shut down if it gets too hot.

### HOW IT WORKS ETI 444

THE output of a magnetic cartridge is normally of the order of 5 mV at one thousand hertz. However in the recording process the high frequencies are recorded at a higher amplitude than the low frequencies (in order to reduce noise). The curve of amplitude-versus-frequency used in the recording process is known as the RIAA curve. When the record is replayed the reverse characteristic of the gain-versus-frequency must be applied to restore a flat frequency response. This process in the amplifier is known as RIAA equalization.

The first stage of the ETI444 amplifier uses an LM382 dual low-noise preamplifier IC. This stage is designed to amplify and to equalize the output of a magnetic cartridge. The internal circuit diagram of this IC is shown on p73. Note that many of the resistors needed to bias the IC (and to provide equalization) are provided within the chip and very few external resistors are required to make it function as an RIAA compensated amplifier.

The second IC is an LM379 — a dual stereo power amplifier which provides six watts rms per channel with supply rails of

$\pm 13$  volts. The IC is unusual amongst power amplifiers in that it can be used in a similar fashion to conventional op-amps (except that it is capable of driving a low impedance load of 8 ohms).

The gain-versus-frequency response of the power amplifier is set by the bass and treble controls. The overall gain is set by the ratio of  $R15/(R17 + RV4)$ . The part of RV4 corresponding to a particular amplifier is that between the wiper and the outside tag connected to that amplifier. Thus the gain of the two amplifiers may be varied differentially by varying RV4 (which acts as a balance control). The level of the input to the power amplifier is selected by RV1 (which acts as a volume control). Switch SW1 selects the input to the power amplifier from either the RIAA preamplifier or from tuner, tape or auxiliary inputs as required.

The power supply is simply a bridge rectifier and centre-tapped transformer arrangement which provides  $\pm 12$  volts dc. With both channels driven this is adequate to provide an output of 5 watts per channel before clipping.

# ms Components



electronics pty Ltd

THE GREAT NAME FOR ELECTRONIC  
164-166 REDFERN STREET, TEL : 69 5922




COMPONENTS IN AUSTRALIA  
P.O. BOX 156, REDFERN, NSW 2016

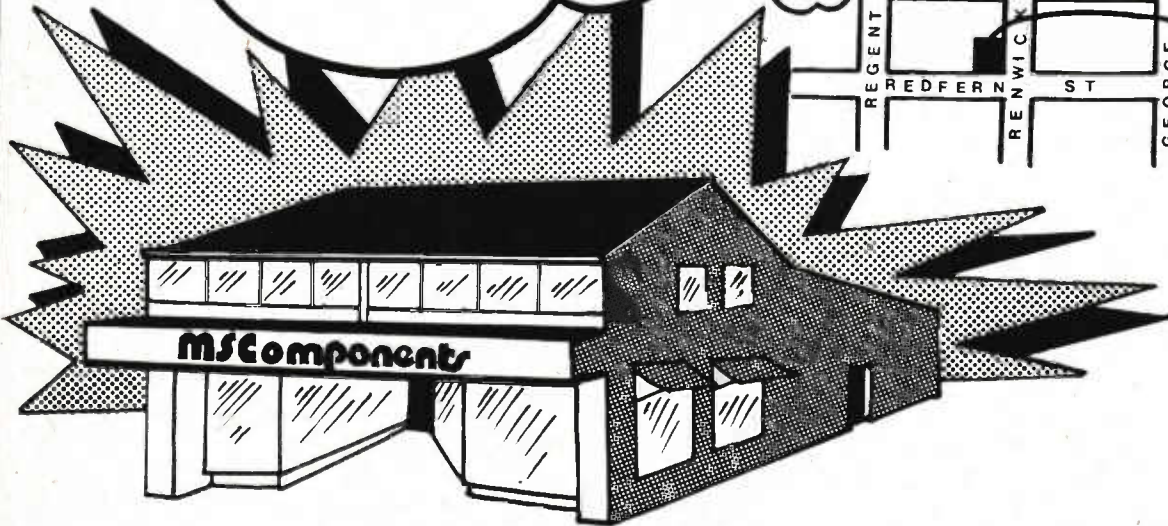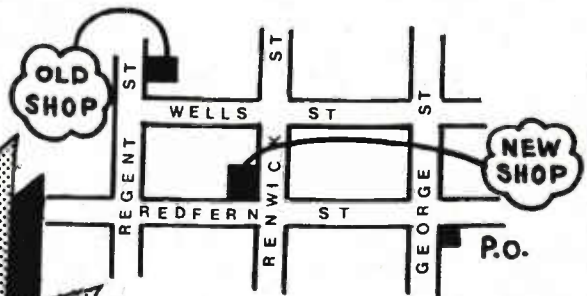*We've moved  
from 95 Regent St to  
**BIGGER & BETTER**  
PREMISES ..  
at 164-165 Redfern St  
..... you've just got  
to see what we've  
got now!!!*



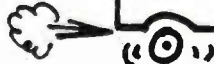**WATCH FOR MORE DETAILS  
NEXT MONTH !!!**



**Trading  
Hours**

MON-TUES-WED & FRI: 9am-5.30pm. THURS: 9am-7pm. SAT: 9am-1pm.  
C.O.D.'s: Please add \$2.40 to posting fee. NO ORDERS UNDER \$3.00 accepted. For replies please send  
S.A.E. Post and Packing 50c where not included in price. PLEASE . . . PLEASE PRINT YOUR NAME &  
ADDRESS ON ALL ORDERS AND CORRESPONDENCE.



# Train controller

A simple project offering auto-reverse, inertia, emergency brake and loop track facilities.

MODEL TRAINS HAVE ALWAYS BEEN popular with both lads and dads — with dads perhaps coming first. Many a boy has complained "Daddy won't give me a turn". It seems there is some inexplicable attraction in playing trains which never dims with the passing years. A couple of our friends have recently decided to buy train sets — for the kids (they say). Our model train controller project was designed to give them many features that are not found in commercially available controllers (for roughly the same cost). Most commercial devices cost around \$30 and consist of a transformer followed by a selenium rectifier, a high power rheostat and an automotive globe. Such controllers have numerous operating disadvantages mainly due to their very poor voltage regulation.

**Our controller** It may look a little complex but in fact it is very simple to build and quite inexpensive. If the full capability is used the features of the controller are:

- Forward or reverse control by a single slide potentiometer (centre for stop)
- Separate reversing switch for the main track
- Short-circuit proof
- Regulator-type control circuitry
- Emergency brake (which stops the train instantly regardless of the position of other controls)
- Simulated inertia (gives more realistic starts and stops)
- The facility to operate with track loops

**Loop operation** Although not possible with simple controllers, loop operation adds much operating fun and realism to any model railroad and the feature is well worth including. A typical loop is shown in Fig. 1, and the operational problems of such a loop are as follows:

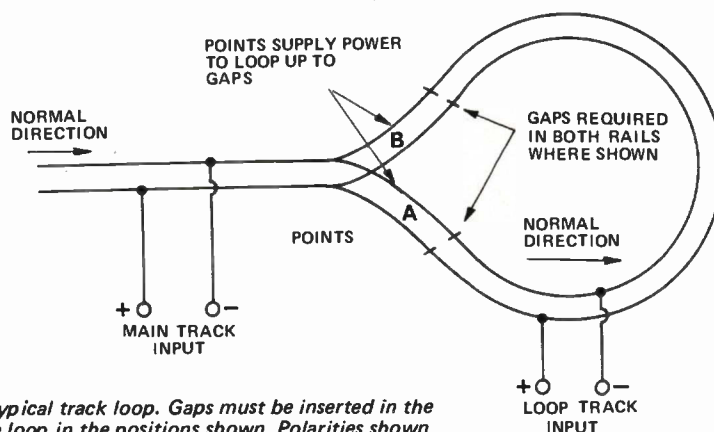
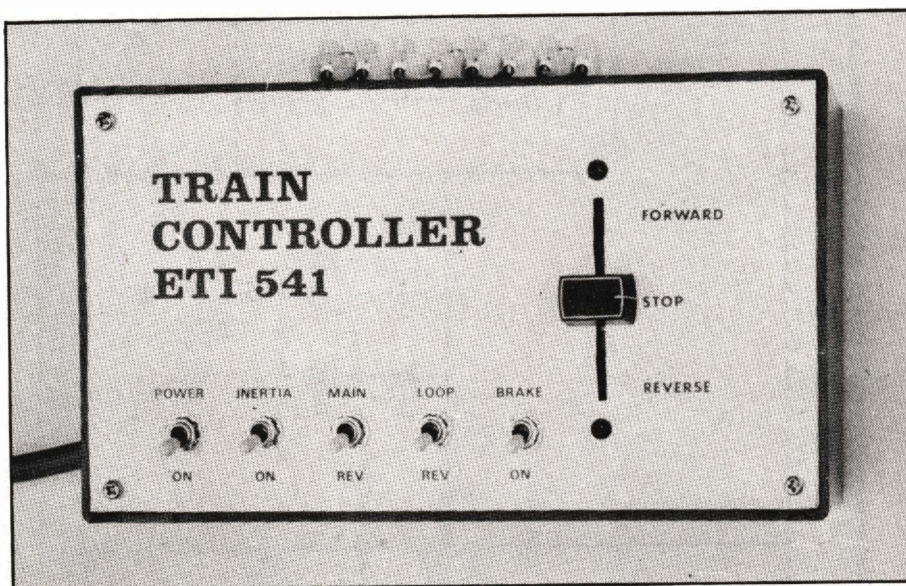


Fig. 1. A typical track loop. Gaps must be inserted in the rails of the loop in the positions shown. Polarities shown are with MAIN and LOOP track switches in the normal position.

If a train is approaching the loop and the 'main' and 'loop' switches are both set at normal, the polarity of the voltages to the track will be as shown. If the

points are set so that the train enters the loop towards 'B' it will continue normally around the loop. If the points are now set to 'B' so that the train may

(Continued on page 55)

# Train controller

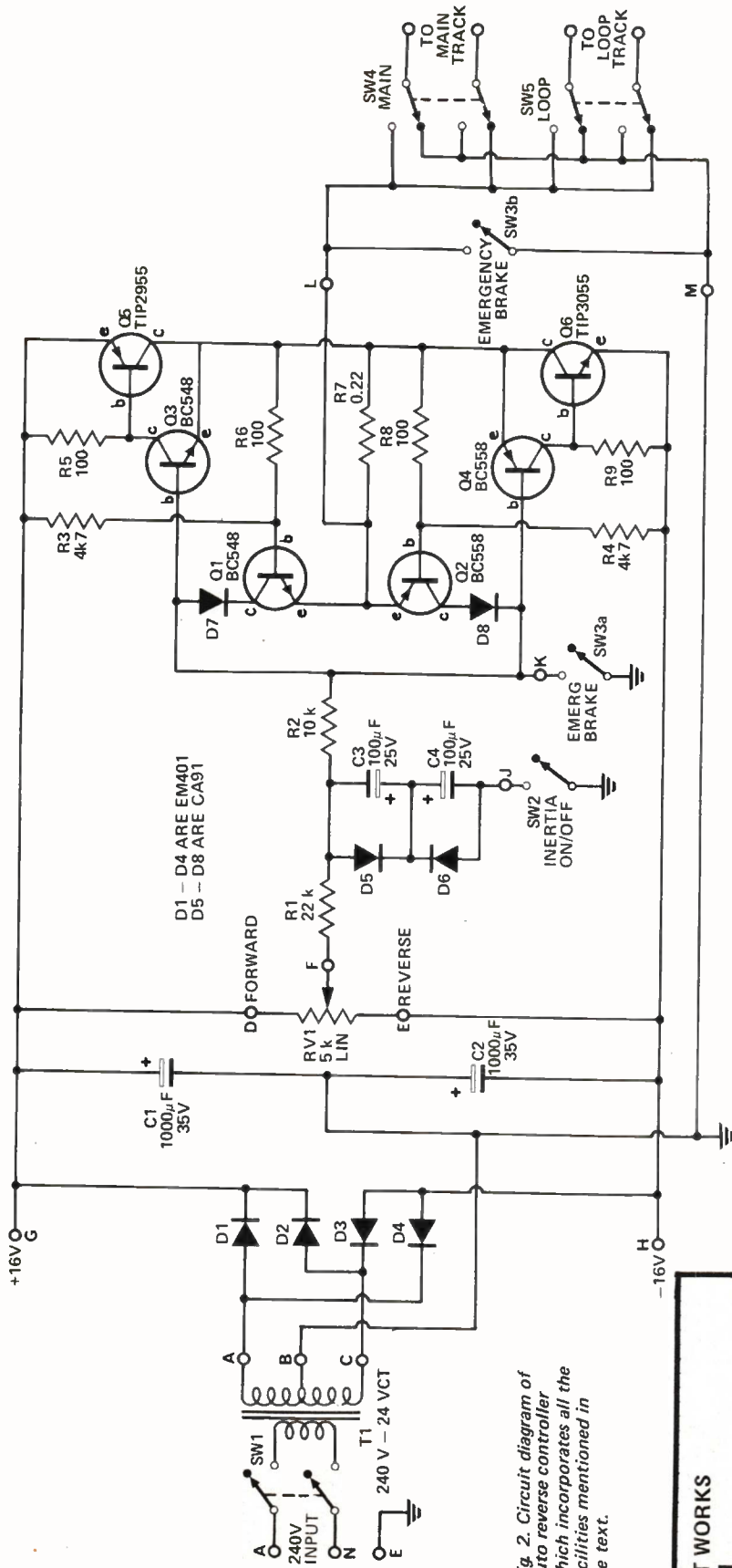



Fig. 2. Circuit diagram of auto reverse controller which incorporates all the facilities mentioned in the text.

## HOW IT WORKS

**ETI 541**  
 TRANSFORMER T1 reduces the 240 volt mains to a supply of 24 volts (centre tapped) which is then rectified by D1 to D4 to provide supplies of +16 and -16 volts d.c. The speed control potentiometer is connected between these supplies so that its wiper may select any potential between plus and minus 16 volts, depending on setting. The output of the potentiometer must be well buffered before it can supply enough power to run a train. This is achieved by transistors Q3 and Q5, for the forward direction (that is for output voltages between zero and +15 volts), and by Q4 and Q6, for the reverse direction (that is for output voltages between zero and -15 volts). The output voltage at the collectors of Q5 and Q6 will be about 0.6 volts closer to zero than the voltage at point 'K' (providing the voltage at point 'K' is more than 0.6 volts away from zero). This means that the control

## PARTS LIST

AUTOMATIC-REVERSE CONTROLLER	
Resistors	
R1	22 k 5%
R2	10 k " "
R3,4	4 k7 " "
R5,6	100 ohm " "
R7	0.22 ohm 5 W
R8,9	100 ohm ½ W
RV1	5 k lin 45 mm slide potentiometer

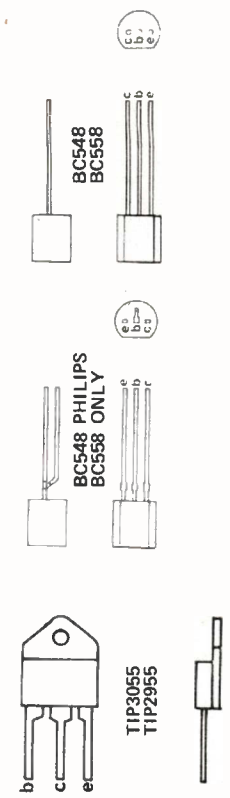



potentiometer will have a small dead band in the centre of its travel where the output voltage remains at zero. This is an advantage because it is frequently necessary to set the controller for exact zero output.

To protect the transistors from damage in the event of an overload or a short circuit, transistors Q1 and Q2 are used to monitor the output current (by measuring the voltage across R7) and the voltage across the output transistors. By this method the power dissipation in the output transistors is controlled such that when driving into a short circuit only about one ampere is available. Yet when set to about 12 volts, about two amps is available to drive normal loads. The diodes D7 and D8 are included to protect the transistors Q1 and Q2 against reverse bias which can occur under certain conditions.

To add the 'inertia' facility or 'momentum', as it is sometimes called by C3 and C4. This means that if the potentiometer is suddenly moved from stop to full forward (for example) the voltage applied to the transistor buffer rises only slowly. The train accelerates at a realistic rate without wheel spin. A similar action takes place when the train is stopped. If the controller is moved from full forward to full reverse the train will slow down and stop for a short time and then start off and increase speed in the reverse direction. The diodes D5 and D6 allow normal electrolytics to be used in this position.

If inertia is being used and an emergency situation occurs, eg train moving into a siding that it should not be entering, the brake facility may be used to short the track (SW3b) and also the input to the buffer stage (SW3a). The brake over-rides the speed control and by its use the train will be stopped in a much shorter distance than it would if the power were simply switched off.

When loops in the track system are used, as described in the introduction, a separate reversing switch is used to control the polarity in the loop with respect to the main line so that the train may go into and come out off the loop without any change in speed. The two controller outputs required for this mode of operation must each be reversible and this is performed by SW4 and SW5.

If a second controller is required for another train in the system then it may be built without the power supply. The second controller may be powered by linking the +16, 0 and -16 volt lines between the two controllers.

**Capacitors**  
C1,2 1000  $\mu$ F 35 V pc mounting electro  
C3,4 100  $\mu$ F 25 V pc mounting electro

**Transistors**

Q1, 3 BC548  
Q2, 4 BC558  
Q5 TIP 2955 \*  
Q6 TIP 3055 \*  
\* with insulation kit

**Diodes**

D1-D4 EM401 or similar  
D5-D8 OA91 or similar

**Miscellaneous**

PC board ET1 541  
Transformer PL24/20 VA or similar  
SW1 toggleswitch DPDT 240 V rated  
SW2 toggle switch SPDT  
SW3-SW5 toggle switch DPDT  
Plastic box 196x113x60 mm  
12 Pc board pins  
3 core flex, plug and clamp  
Heatsink/support to Fig. 8.  
8-way connector strip  
2-way connector strip  
2 6BA c/s screws & nuts 10 mm long  
Front panel (Scotchcal)

**FOR MANUAL REVERSE CONTROLLER**

Delete


R4, R8 and R9  
C2 and C3

Diodes D3-D8

Transistors Q2, 4 and 6

*If no loops are involved in the track layout SW4 and SW5 can be deleted on an automatic reverse controller and SW5 on a manual reverse controller.*

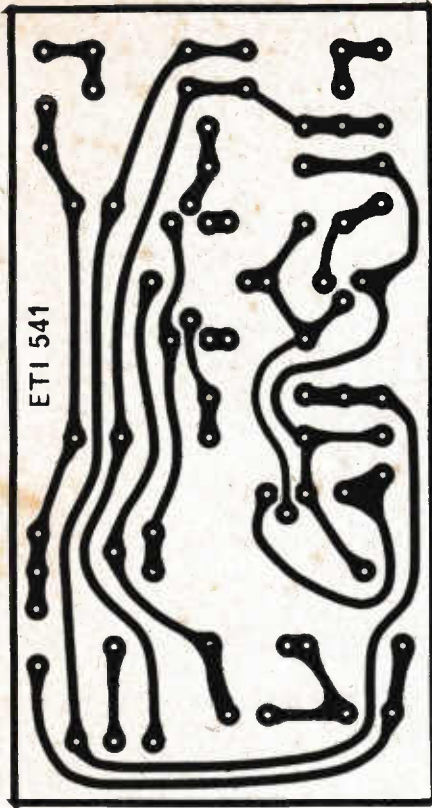*For a second controller delete T1, SW1, D1-D4 and the power cord in the second controller.*



Printed-circuit board layout ET1,541 train controller. Full size 65 x 105 mm.

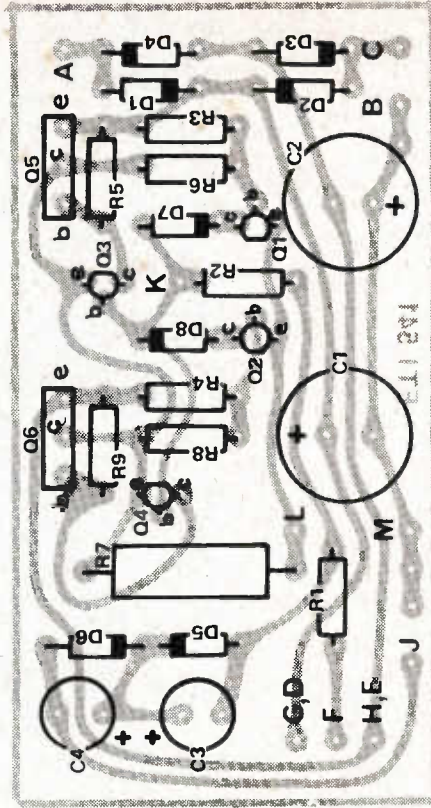


Fig. 3. Component overlay - auto reverse controller.

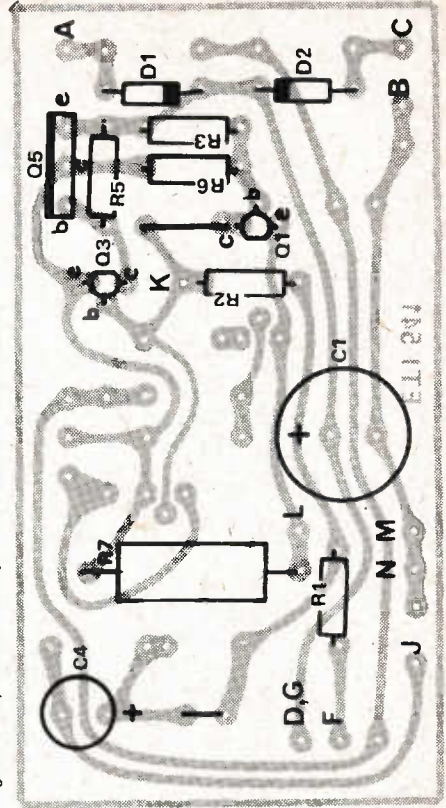


Fig. 4. Component overlay - simple controller.



# Train controller



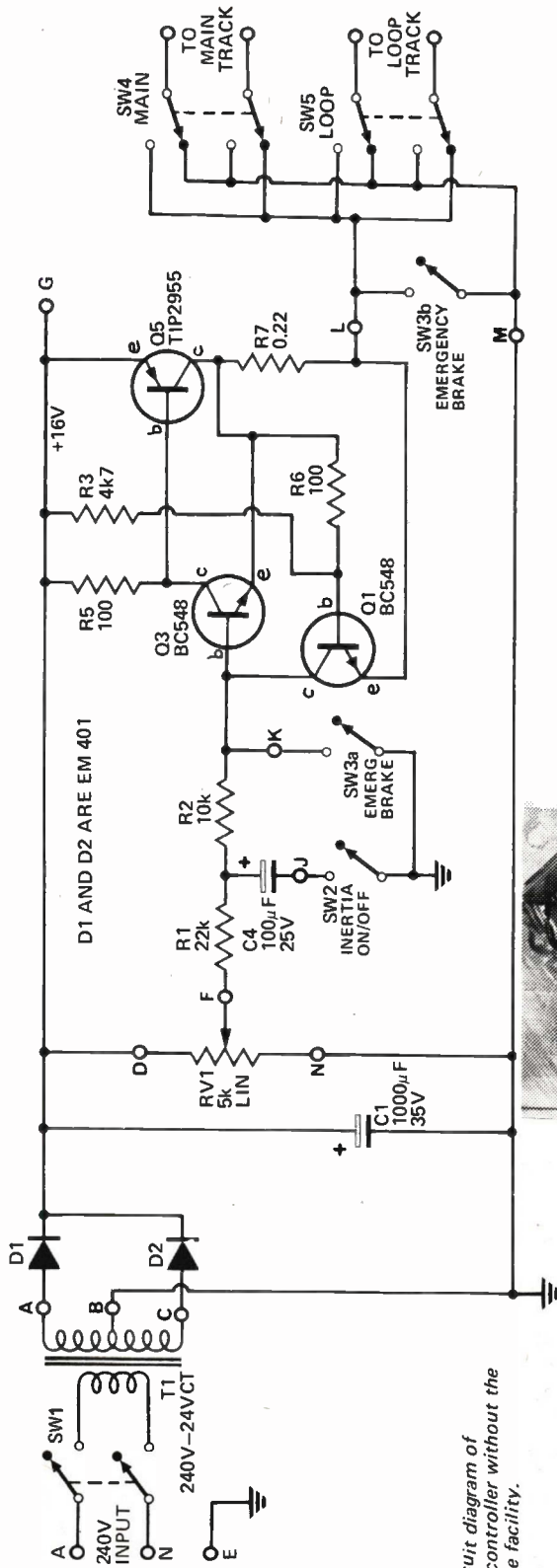


Fig. 5. Circuit diagram of simplified controller without the auto-reverse facility.

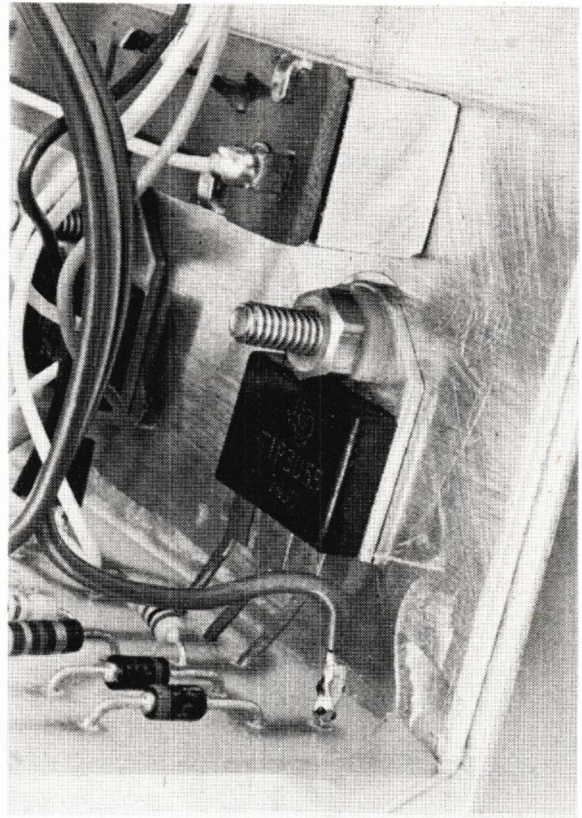

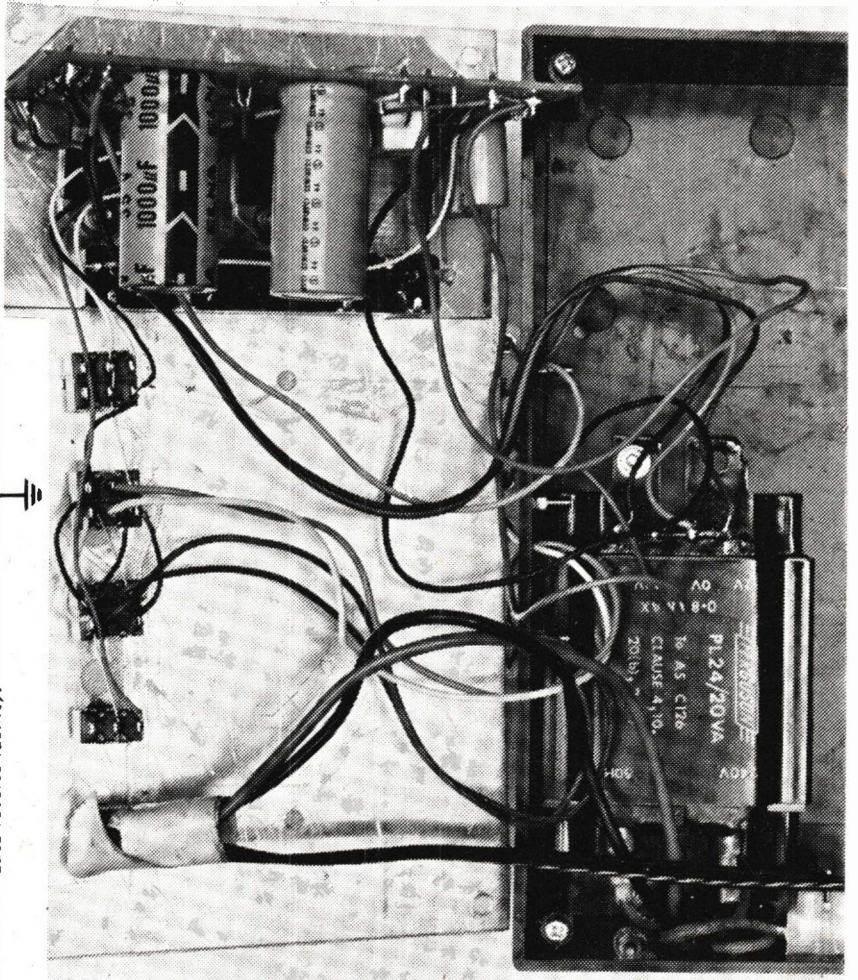The power transistors are mounted to a bracket with countersink bolts. They can, if desired, be mounted directly on the front panel. Note how the pcb is mounted — by epoxying to the bracket.



# AT LAST! a scientific calculator everyone can afford

## \$19.95

(plus \$2.50 post & packaging . . .)



### Deluxe scientific hand-held calculator

- Performs 25 functions.
- Sine, cosine, tangent, arc sine, arc cosine, arc tangent
- natural logarithms, logarithms,
- square root, squaring
- pi, e to a power, x to a power,
- reciprocals, change sign, exchange and display/register
- memory minus, memory plus, memory clear, memory exchange recall and clear/clear entry keys.
- Degrees/radians conversions.
- Fully addressable memory.
- Automatic constant in all four basic functions.
- Full 8 digit display with arithmetic, RNP logic and 3 level stack.
- Floating decimal plus underflow.
- Large, bright easy to read LED display.
- Complete with 9 volt battery for long term dc operation
- Weighs 6 ozs. and is 5 3/4" x 2 3/4" x 3/8".

#### NOTES:

The Unitrex 90SC is warranted for 90 days from original purchase date — under normal use and service — against defective materials or workmanship. Defective parts will be repaired or replaced at Unitrex's option when the calculator is returned prepaid to Unitrex of Australia Pty Ltd., 414 Collins St, Melbourne, Vic. 3000. The warranty is void if the calculator has been damaged by accident or misuse. Removal or alteration of serial number or repair by unauthorised personnel also voids warranty. The warranty contains the entire obligation of Unitrex of Australia Pty Ltd and no other warranties, expressed, implied or statutory are given — this warranty does not exclude limit restrict or modify any condition or warranty implied by the Trade Practices Act 1974, or other State laws or Acts . . .

The units can only be obtained as below. Electronics Today cannot supply directly nor undertake to demonstrate or discuss details or the units offered.

All units will be thoroughly inspected before despatch. The package should be carefully inspected before accepting delivery.

Acceptance should be refused if the package is damaged.

Orders must be addressed exactly as per the coupon. Due to postal delays, readers should expect a delay of between three to four weeks between posting an order and obtaining delivery.

Finally — in the event of the unit not working — please return it directly to Unitrex, 414 Collins St, Melbourne, Vic 3000, NOT to ETI. This offer closes on July 25th 1976.

My cheque/postal note for . . . . . is attached.  
 Make cheque/postal note payable to Calculator Offer.  
 Please forward \$22.45 (i.e. \$19.95 plus \$2.50 postage and packing) per unit.

Send to Calculator Offer  
 c/- Electronics Today International  
 15 Boundary St, Rushcutters Bay, NSW 2011.



**APPLIED  
TECHNOLOGY  
PTY. LTD.**

**THE ELECTRONIC MAILBOX**

P.O. BOX 355, HORNSBY, 2077

Phone: 476-3759

## Electronic Components by Post

### SPECIALS OF THE MONTH

SPECIALS OF THE MONTH \*Valid for Orders postmarked before July 31st, 1976

LM309K 5 Volt 1A Regulator	\$2.00	SAK140 Auto Tachometer	\$2.00
741 OP AMP	5 for \$2.00	UAA170 Spot-O-Light (16 LED) Driver	\$3.00
555 TIMER	5 for \$3.00	UAA180 Bar-O-Light (12LED) Driver	\$2.75
14553 3 Digit frequency counter	\$6.50	CA3089 FM Demodulator	\$6.75
14511 7 Segment Decoder driver	\$2.50	MC1310 FM Stereo Decoder	\$3.50
1N914 Diodes	20 for \$1.20		

### Voltage Regulators

LM723 Variable voltage regulator (DIP)	\$1.00
LM325 $\pm$ Volt 100mA Dual Regulator (DIP)	\$3.60
LM340-5 volt	
6 volt	} Amp (T0220) Regulator \$2.25
8 volt	
12 volt	
15 volt	
18 volt	
24 volt	

### DIL Sockets

8 pin .....	.30
14 pin .....	.35
16 pin .....	.40
18 pin .....	.50
24 pin .....	\$1.00

## SATURN 5

### UNIVERSAL VIDEO GAME

Play SQUASH, FOOTBALL, TENNIS, PING PONG, HOLE IN THE WALL, TARGET PRACTISE - WITH OPTIONAL SOUND EFFECTS, ON-SCREEN SCORING.


Build your own Saturn 5 and experience hours of fun and excitement playing these fascinating TV games with your family and friends!

Saturn 5 is an entirely new approach to video games and consists of a master control unit with plug in game options. This together with the remote dual slider player controls offers an unlimited range of game possibilities, including double/singles (tennis) and horizontal/vertical player movement (football/squash). Play tennis, ping pong and hole in the wall with the basic Saturn 5 kit. Football and squash options now available.

Why not design your own games and play golf, baseball, billiards, moving target etc. etc.

Optional kits are available to add sound effects and on-screen scoring if required. Saturn 5 is easily built and features CMOS technology and battery operation. A pre-built modulator is included which plugs into any TV set (colour or black and white) at the aerial terminals.

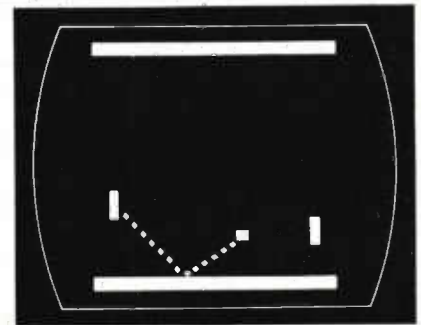With our exclusive assembly manual and technical support service, virtually anyone can construct this kit.



### THE HOTTEST ELECTRONIC TV GAME KIT IN TOWN!

Complete SATURN 5 basic kit with ping pong, tennis, hole in the wall games **\$37.50\***

<b>OPTIONS</b>	Sound effects	\$3.50*
	On-Screen scoring	\$7.50*
	Football	\$7.50*
	Squash	\$7.50*

\* Including post and packaging  
(No discount applies)



# ELECTRONIC HOBBY KITS

To-days Technology for Your Enjoyment

## eti PROJECT 740 FM TUNER

— high quality push button varicap FM stereo tuner sets new standards of performance

### THE FM TUNER KIT YOU HAVE WAITED FOR


The ETI 740 is a novel design for an FM tuner which achieves high performance and eliminates the critical setting up required with many other tuners. The front end is a ready built pre aligned module which then feeds CA3089 IF and demodulator integrated circuit via ceramic filters. The CA3089 provides AGC, AFC muting as well as signal strength and tuning meter drive voltages. Temperature compensated varicap tuning allows stations to be selected either by a ten turn tuning potentiometer or by a choice of three preset push button controls. The actual frequency selected is displayed on the unique "electronic dial" display mounted behind the front panel. The stereo decoder is based on a well proven integrated circuit phase locked loop which is followed with active filters to remove subcarrier harmonics and "birdies". A LED stereo beacon indicates when stereo transmissions are being received. The specially designed transformer has a built in electrostatic shield. The ETI 740 is available as a complete kit or assembled and tested.



**KIT PRICE**  
**\$120-00** (assembled & Tested \$155)

Plus \$6.00 Freight & packaging

## ETI 440 SIMPLE 25 WATT AMPLIFIER

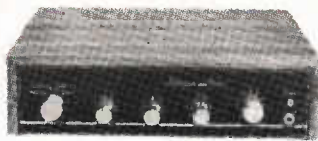

Designed by the ETI Team the International 440 is a remarkable combination of high performance, easy construction and low cost.

We offer our own exclusive step-by-step assembly manual, the choice of buying individual packs or the full kit and a really good looking Walnut Veneered Cabinet that guarantees you a professional finished product anyone would be proud to own. For pack prices, see December ETI.

With our full Technical support and Warranty Service (see below) you just can't fail to build this kit!

**\$85-00** Assembled and Tested \$115 nett  
nett Both plus \$6 freight and packaging

## ETI534 STOPWATCH/ CALCULATOR



By special arrangement with N.S. Electronics we are pleased to offer this NOVUS 650 calculator together with the complete set of components to build the ETI 534 Stopwatch/Calculator. The kit includes a specially designed fibreglass printed circuit board with a silk screened component overlay. With our unique STEP-BY-STEP ASSEMBLY MANUAL and TECHNICAL SUPPORT virtually anyone can build this exciting and useful project.

We thoroughly recommend it for beginner or professional.

**STILL**  
**\$16-75**

A & T \$21.75  
Post free

## ETI 704 CROSS HATCH/DOT GENERATOR



This incredibly popular project now given the HOBBY KIT treatment.

- Pre drilled/screened front panel.
- Fibreglass PC Corruptment Overlay.
- Pre-wound coils.
- Sockets for all IC's.

Complete to last detail including solder and hook up wire. Full warranty support applies. (Doesn't include battery.)

**\$27-50** nett

Delivered free in Australia

### FULL TECHNICAL SUPPORT AND WARRANTY SERVICE

All Applied Technology HOBBY KITS are covered by our exclusive 90 days warranty against faulty components and packaging (full details with each kit).

Yet another exclusive is the full technical support service. If you are unable to make your HOBBY KIT operational, help is just a phone call or a letter away. If you do have to return any KIT for factory attention, it will be repaired for a nominal service fee.

All Kits on display at our factory showroom.  
Hours: 9 - 5 weekdays, 9 - 12 Sat.  
Phone: 476-3759



109-111 Hunter Street,  
HORNSBY, N.S.W. 2077  
Phone (02) 476-4758  
Open Saturday morning

Please supply .....

Enclosed is my Cheque/Postal Note/Money Order for \$ .....  
made out to APPLIED TECHNOLOGY PTY. LTD.  
(PLEASE PRINT CLEARLY)


NAME .....

ADDRESS .....

..... P/C ..... ETI 5/76
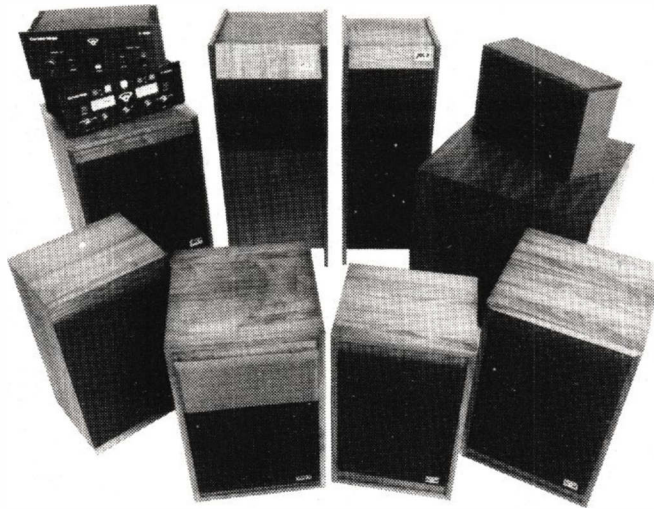
## Cerwin-Vega ads are nearly as rare as Cerwin-Vega speakers.

Up till now, only a handful of Cerwin-Vega speakers came into the country. And only those people with an ear to the ground and a fistful of dollars got their hands on a pair. But happily, the situation is changing. We can now offer a range of six living room systems. But unhappily, you'll still need a fistful of dollars. Prices range from \$424 to \$2500 a pair. Maybe a few consoling words would be appropriate. Cerwin-Vega speakers are built to take the absolute maximum power with the absolute minimum distortion. And they succeed. Like no other speakers you've ever heard before. The sound is always clean



**Cerwin-Vega**

Loud is beautiful...if it's clean.

and crisp, no matter what the volume. Which is why many of the world's leading rock groups use Cerwin-Vega. And why Cerwin-Vega won the contract to design and build the speaker systems for the movie 'Earthquake'. The result: an earth shattering realism, that won an Academy Award for the Sensurround System. An example, closer to home, are the Cerwin-Vega 2IIR living room speakers. An amp. with as little as 3 watts RMS will drive these speakers, and yet they will take as much as 100 watts RMS, and produce a sound level of 119db at 1 metre without distortion. The kind of performance that comes from putting our time and money into speaker development. Not into ads.

PKB88529

## Tests prove that Tracker cleans up the competition, as well as your records and tapes.


Various types of record cleaners have been available for decades. However, most of these products have failed to keep pace with modern advances in record materials and recording techniques. The Tracker RC-1 record cleaning solution was developed to meet these modern demands.

Tracker cleaning products went into stringent testing at the Chemistry Dept. at the University of Victoria, B.C., Canada in 1974 and as this chart shows, Tracker RC-1 dramatically reduced the records static charge.

Further information on the Canadian Tests is available by writing to us at Box No. 882, G.P.O. Sydney, 2001.

Tracker products are suited to all the new and advanced record materials, advanced sound techniques and delicate tape heads.

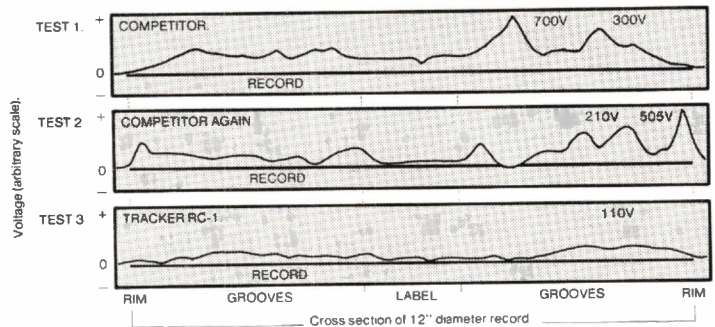*These 3 traces show static charge on the same record after cleaning twice with a major competitive solution, then once with Tracker RC-1 solution.*



There's the RC-1 Record Care Kit, that not only thoroughly removes the static, but helps to resist further build-up of negative static charge. This protects the grooves from being ground away by new particles of dirt. This modern cleaning kit consists of an exclusive formulation together with handy screw-on spray, plus a fine velvet pad. Refills are available.

And for your tape collection, Tracker provides delicate professional care with the HC-1 Tape Recorder Care Kit. Tracker came through the tests, so give your old cleaners the brush off and go with the winner!

Look for the Tracker RC-1 and HC-1 under our label, or branded under your hi-fi shop's name.



**tracker**

Better than anything you've used before.

PKB88530 A


ELECTRONICS TODAY INTERNATIONAL — JUNE 1976


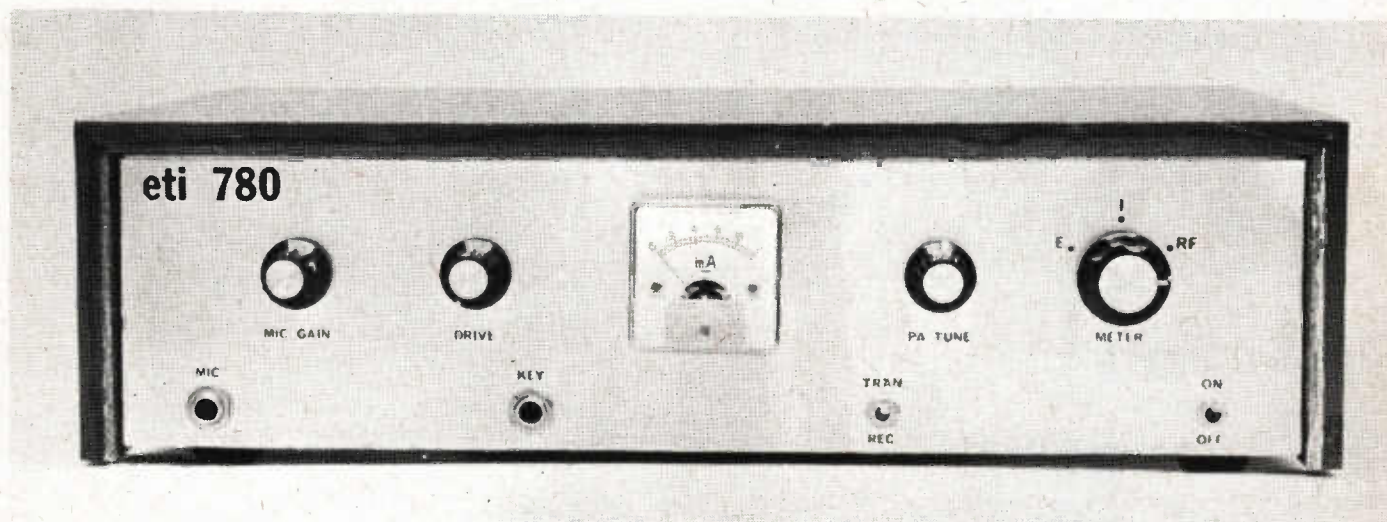
# Novice transmitter

Designed by Kevin Barnes

Last month we introduced the design philosophy of our transmitter and described its operation in general terms. We continue this month with full construction details.



COMMENCE CONSTRUCTION BY winding all the coils in accordance with the winding data shown on page 74. Then construct the heatsinks for the BDY92 (Q5) and the BD139 (Q3), as shown in Figure 6 and the photographs. Mount the BD 139 to its heatsink using a 6BA by 9 mm screw, an insulating mica washer and silicon grease. Now mount the BDY92 to its heatsink, using a mounting kit and silicon grease, but use two mica washers between the transistor and the heatsink to reduce the capacitance between the transistor case and earth. Do not mount either heatsink to the board at this time.

**Transmitter board** Mount the resistors and the fixed capacitors to the transmitter board, according to the component overlay. Note that R16 is also an inductor and is constructed by winding a length of jug element wire on a Philips ferrite bead. Resistor R16 acts as the current shunt for the meter. Its resistance of 0.5 ohms is best measured by passing one ampere through

a length of the wire and finding the length required to obtain a voltage drop of half a volt.

Resistor R17 is selected to give half scale reading on the meter for one amp of collector current through Q5. In the prototype the value required was 680 ohms. We suggest that you use this value temporarily and trim later if required. Capacitor C21 (emitter bypass for Q2) should have a ferrite bead on one lead. The capacitors in the output network must be polystyrene and rated at 630 volts.

The impedance matching network, consisting of C9, C10 and L1 has a low Q and on the prototype we found the response was broad enough. However if you have any problem in obtaining sufficient drive to Q5 (with insufficient drive one amp collector current can not be obtained) change the value of C9 (by small amounts) to correct this.

Once all the resistors and capacitors have been fitted to the board you can install the semiconductors, coils and

the crystal. The heatsink supporting the BD139 should now be screwed to the board and the leads of the transistor soldered into position. Note that the heatsink also acts as a shield (as does the BDY92 heatsink) and should therefore be earthed to the board by means of the mounting screws. Now mount the relay and the PA tuning capacitor C18.

The BDY92 heatsink bolts onto the rear of the chassis (not to the board). It is a good idea to first temporarily mount the board into the chassis and the heatsink to the rear panel. The tap on the toroidal transformer T4 should now be connected to a solder lug under the nearest bolt securing the BDY92 to the heatsink. Now connect the emitter of the BDY92 to earth on the pcb by a piece of very thick wire or a piece of pc board and wire as shown in Figure 6 and the photographs. Once this lead and the base lead of the transistor have been positioned the board and heatsink assembly can be

(text continued on page 78)

# Novice transmitter

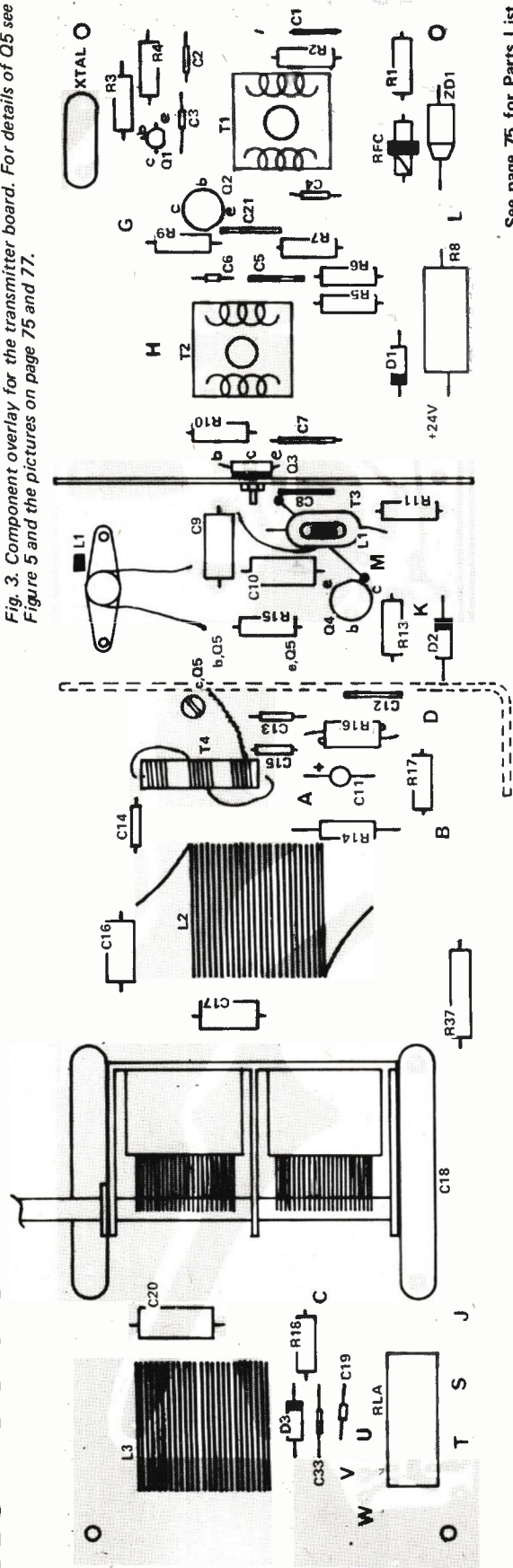


Fig. 3. Component overlay for the transmitter board. For details of Q5 see Figure 5 and the pictures on page 75 and 77.

See page 75 for Parts List

## HOW IT WORKS — ETI 780

The operating frequency of the transmitter is determined by a crystal oscillator consisting of transistor Q1, transformer T1, a crystal and other associated components. Capacitor C3 provides the feedback necessary to maintain oscillation. The output from the oscillator is link-coupled to the base of transistor Q2 — a buffer amplifier designed to minimise loading effects on the oscillator, and to deliver maximum power gain.

The emitter resistor for Q2, R9, is returned to earth via the normally-closed contacts of the morse-key socket and the transmit/receive switch (T/R switch). Thus if the morse key is inserted, or the T/R switch is in the receive position, Q2 is disabled. This prevents the output of the oscillator from reaching the power amplifier (PA). By this means the transmitter is disabled unless the morse key (if inserted) is operated or the transmit mode is selected.

The output from Q2 is link-coupled from T2 to Q3 which is a class-C RF power amplifier. The input to Q3 is shunted by R10 in order to keep changes in the input impedance low during the periods when Q3 is not conducting. The

emitter current of Q3 (and hence the drive power to the PA) is controlled by the effective impedance of Q4, as set by the potentiometer RV1. RV1 is therefore used to set the dc input power level to the PA.

The high output impedance of Q3 is matched to the low input impedance of Q5 (shunted by R15) by means of the transformer T3 and the 'T' network consisting of C9, C10 and L1. The Q of this network is kept low so that its frequency response is broad.

The low output impedance of Q5 is stepped up by the broad-band toroidal transformer T4 which feeds the RF into a double-pi network formed by C16, L2, C17, L3 and C20. This network reduces the harmonic content of the output to a safe level and additionally, adjustment of C18 makes the final impedance match to the antenna.

The output power is then fed to the antenna socket via the change-over relay. A sample of the output is taken by C19 and is converted to a dc signal by D3 and C33. This signal is used to drive a meter thus providing an indication of power output. On the supply-trail side of the transformer T4 capacitors C13 and 15 provide RF bypassing at HF and VHF frequencies whilst R14 and C11 provide

bypassing for frequencies below 3.5 MHz. The resistor R16 is a low value meter shunt and the current through Q5 develops a voltage across R16 which is monitored by the meter. This reading of current in Q5 together with a reading of the voltage at point 'A' allows the operator to measure the input power to the final stage.


Diodes D1 and D2 form an analogue AND gate which allows transistor Q3 to draw current from whichever of two supplies is the higher — the 13 volts to the oscillator or the output voltage from the modulator. Thus when Q5 is called on to supply peaks of power and this requires drive from Q3 beyond what can be provided by the 13 volt supply the additional drive capability is provided by the modulator.

**The modulator.** The output from the microphone is voltage amplified by IC1a and IC1b which have gains of 100 and 10 respectively. RV2 is a front-panel mounted gain control for the microphone, provided to allow the operator to use microphones with different sensitivities. Capacitors C22, 24 and 28 have been selected to tailor the audio-frequency response at the low end whilst C25 trims the response at the high end. Restricting the audio bandwidth in

this manner does not affect legibility but improves efficiency and reduces the bandwidth of the transmitter. Diodes D4 and D5 are clipping diodes which remove any positive or negative peaks from the audio modulation which would otherwise overmodulate the PA. A low pass-filter is formed by C27 and R26, and RV3 is used to adjust the gain so that a fully-clipped signal corresponds to 100% modulation. The output from RV3 is taken to IC1c which, as a low-pass active filter, removes the harmonics that were produced by the clipping process. If these harmonics are radiated they cause interference to nearby channels.

The series modulator is formed by IC1d, Q6 and Q7. The modulator is in effect a voltage amplifier with a high output current capability and a voltage gain of 100. The values of R36 and R34 are the same and therefore the voltage at the emitter of Q6 must be the same as that at the slider of RV4 if there are to be equal currents into the positive and negative terminals of IC1d — and if the circuit is to be balanced. Therefore any ac which is injected into the IC via C32 is balanced by a change in current through R36. Thus the voltage at the emitter of Q6 varies proportionally to the input voltage applied to R32.



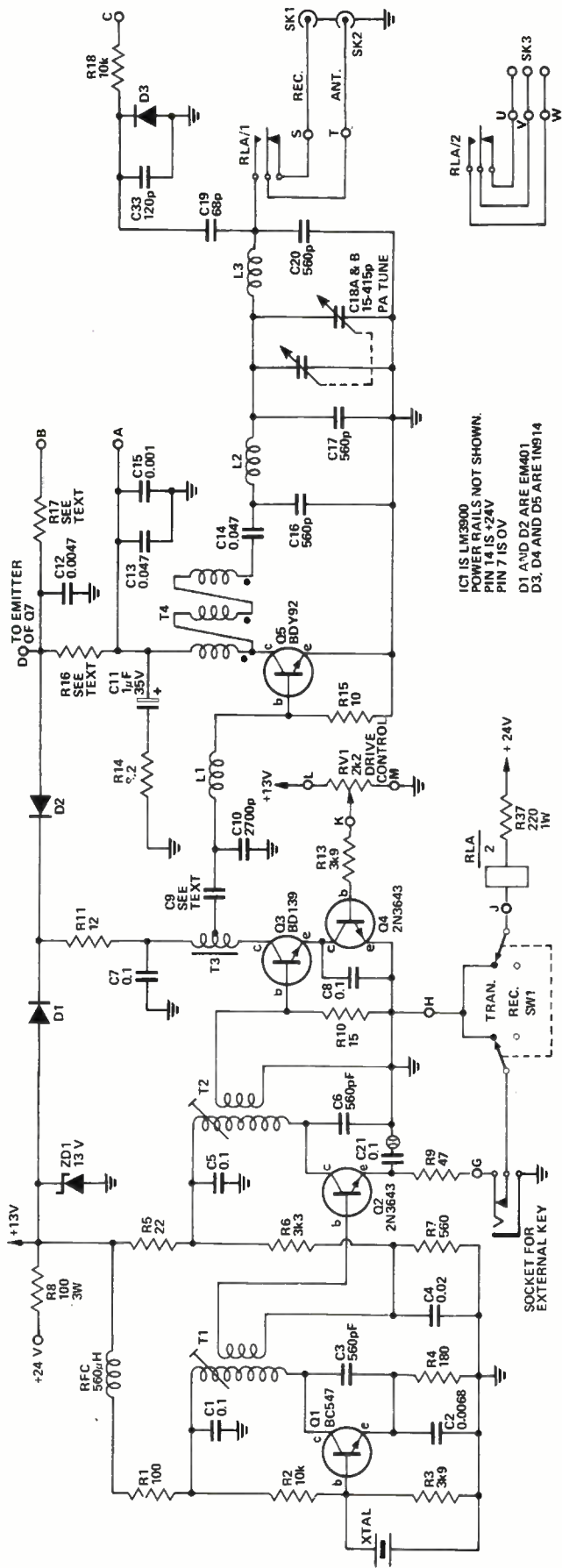

ALL RESISTOR VALUES IN OHMS  
ALL CAPACITOR VALUES IN MICROFARADS  
UNLESS OTHERWISE SPECIFIED.

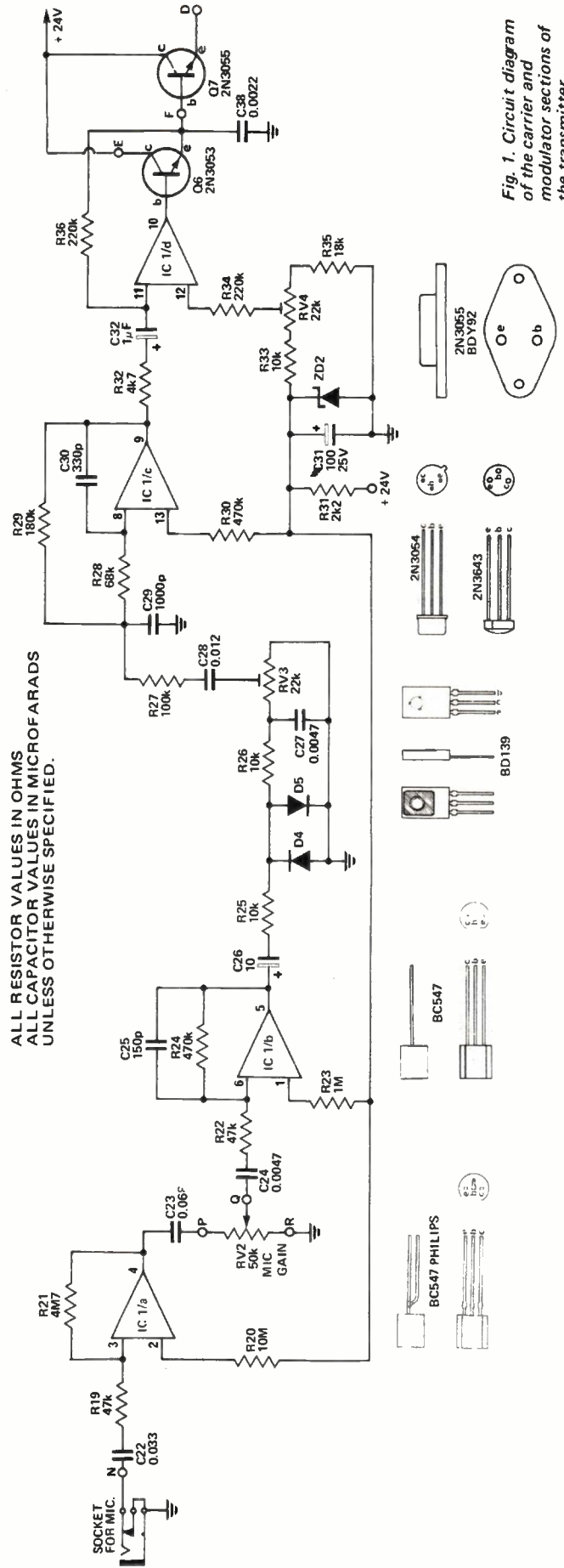


Fig. 1. Circuit diagram of the carrier and modulator sections of the transmitter.

# Novice transmitter


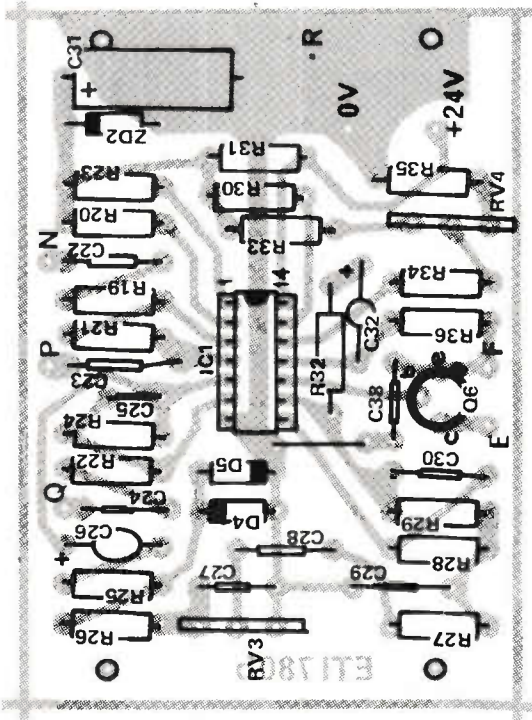


Fig. 4. Component overlay for the modulator board.

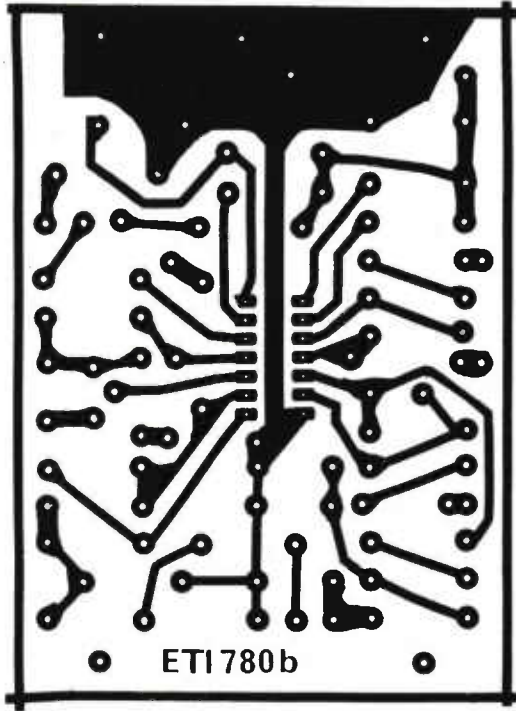

Printed-circuit layout for the modulator. Full size 63 x 92 mm.

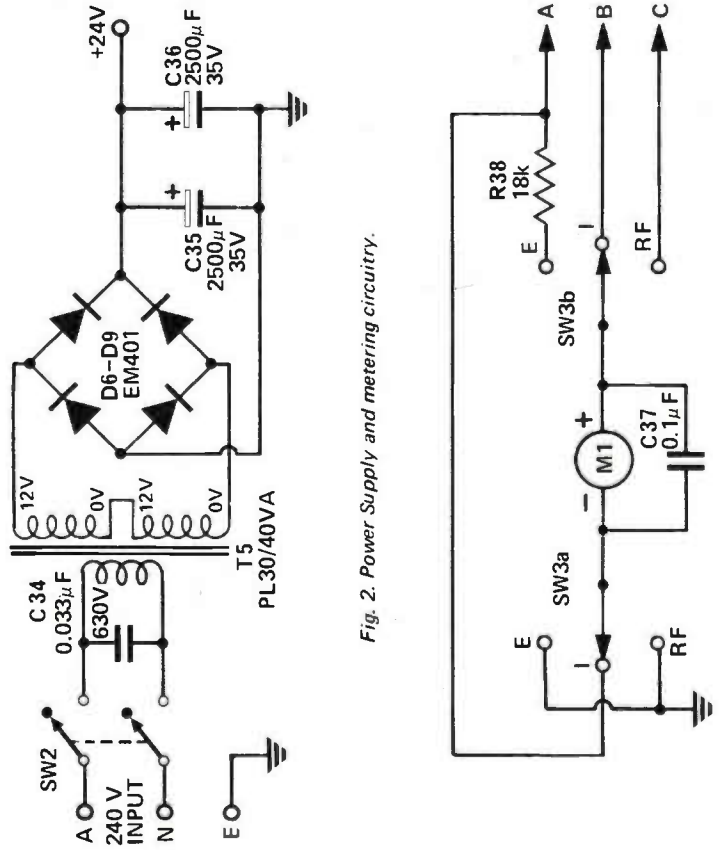


Fig. 2. Power supply and metering circuitry.

### WINDING DETAILS

T3

T4

**NOTE EACH TURN GOES THROUGH A DIFFERENT HOLE**

**TRANSFORMERS**  
 T1 and T2. Both these transformers are close wound on a Neosid former 7 mm diameter by 35 mm long. Primary windings are 28 SWG enamelled copper. Secondary windings are 22 SWG enamelled copper.

**INDUCTORS**  
 L1. Inductor L1 is wound on a 7 mm Neosid former, slug-tuned with an F29 slug.  
 Turns 8 turns close wound of 20 SWG enamelled copper.

**L2, L3.** Both these coils are 25 mm in diameter, air core, and are held together with 6 mm wide strips of masking tape.

**RESISTOR R16.**  
 This resistor is made by winding a length of lug element wire (see text) through a ferrite bead having dimensions of 6 mm diameter and 10 mm long.


**Transformer T1** Primary 21 Turns Secondary 2  
**Transformer T2** Primary 21 Turns Secondary 4 (no not 5)  
**Transformer T3** consists of four turns centre - tapped, wound on a 14 mm long ferrite TV balun.

**Former** Philips 4322 020 69750 or similar  
**Turns** 4 turns of 20 SWG enamelled copper  
**T4** Transformer T4 is trifilar wound (on a ferrite toroid) and has an outer diameter of 23 mm, an inner diameter of 14 mm and a height of 7 mm. The ferrite material is Philips type 4C6.  
**Toroid** Philips 4322 020 91070  
 Turns 6 turns trifilar wound of 1.2 mm wire.


**Bad type** Philips 4312 020 31500 or 4312 070 31550

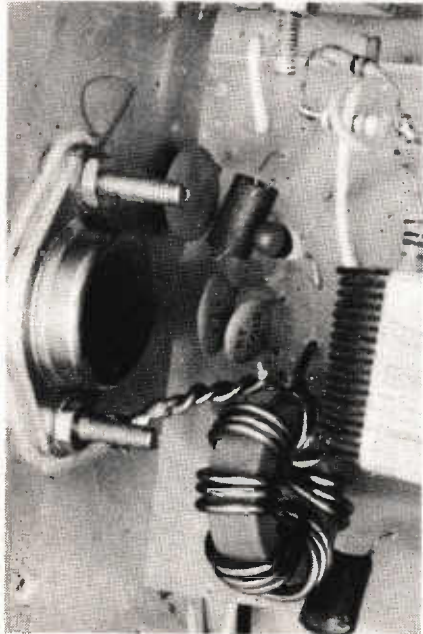**Left: Construction of T3.**  
**Right: Construction of T4.**






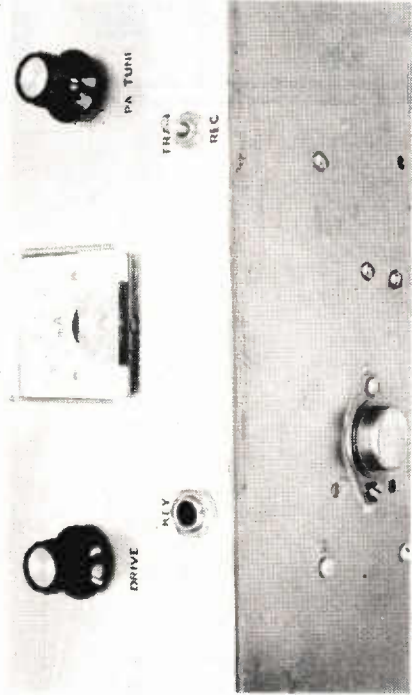The toroid (T4), one pi-tank coil (L2) and the PA transistor (Q5).



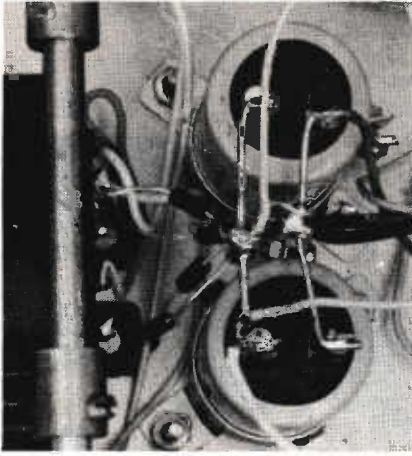Transistor Q7 is mounted underneath the chassis.



The power supply.

### PARTS LIST - ETI 780

Resistors	Value	Power	Notes
R1	100		
R2	10 k	1/2 W	
R3	3k9	"	
R4	180	"	
R5	22	"	
R6	3k3	"	
R7	560	"	
R8	100	5 W	
R9	47	1/2 W	
R10	15	"	
R11	12	"	
R12	not used	"	
R13	3k9	"	
R14	8.2 Ω	"	
R15	10	"	
R16	See text and table I.		
R17	See text		
R18	10 k	1/2 W	
R19	47 k	"	
R20	10 M	"	
R21	4M7	"	
R22	47 k	"	
R23	1 M	"	
R24	470 k	"	
R25	10 k	"	
R26	10 k	"	
R27	100 k	"	
R28	68 k	"	
R29	180 k	"	
R30	470 k	"	
R31	2k2	"	
R32	4k7	"	
R33	10 k	"	
R34	220 k	"	
R35	18 k	"	
R36	220 k	"	
R37	220	1 Watt	
R38	18 k	1/2 Watt	
R39			
R40			
R41			
R42			
R43			
R44			
R45			
R46			
R47			
R48			
R49			
R50			
R51			
R52			
R53			
R54			
R55			
R56			
R57			
R58			
R59			
R60			
R61			
R62			
R63			
R64			
R65			
R66			
R67			
R68			
R69			
R70			
R71			
R72			
R73			
R74			
R75			
R76			
R77			
R78			
R79			
R80			
R81			
R82			
R83			
R84			
R85			
R86			
R87			
R88			
R89			
R90			
R91			
R92			
R93			
R94			
R95			
R96			
R97			
R98			
R99			
R100			
C26			
C27			
C28			
C29			
C30			
C31			
C32			
C33			
C34			
C35			
C36			
C37			
C38			
C1			
C2			
C3			
C4			
C5			
C6			
C7			
C8			
C9			
C10			
C11			
C12			
C13			
C14			
C15			
C16			
C17			
C18			
C19			
C20			
C21			
C22			
C23			
C24			
C25			
D1, 2			
D3			
D4, 5			
D6-9			
ZD1			
ZD2			
Q1			
Q2			
Q3			
Q4			
Q5			
Q6			
Q7			
IC 1			
RV1			
RV2			
RV3			
RV4			
SW1			
SW2			
SW3			
T1, 2, 3, 4			
T5			
Relay			
Meter			
9 spacers			
and washers			
brackets to Fig 6			
chassis and cover			
2.6 mm x 75 mm extension shafts			
power cord and plug			
2 rubber grommets			
cable clamp and four rubber feet			
2 RCA sockets			
2 6mm jack sockets			
4 knobs			
1 5 pin socket			
Coils and transformers as per Table I.			
RFC choke 560 μH			
pc boards ETI 780 A and B			

# Novice transmitter

Printed-circuit layout for the transmitter board. Full size 295 x 77 mm.




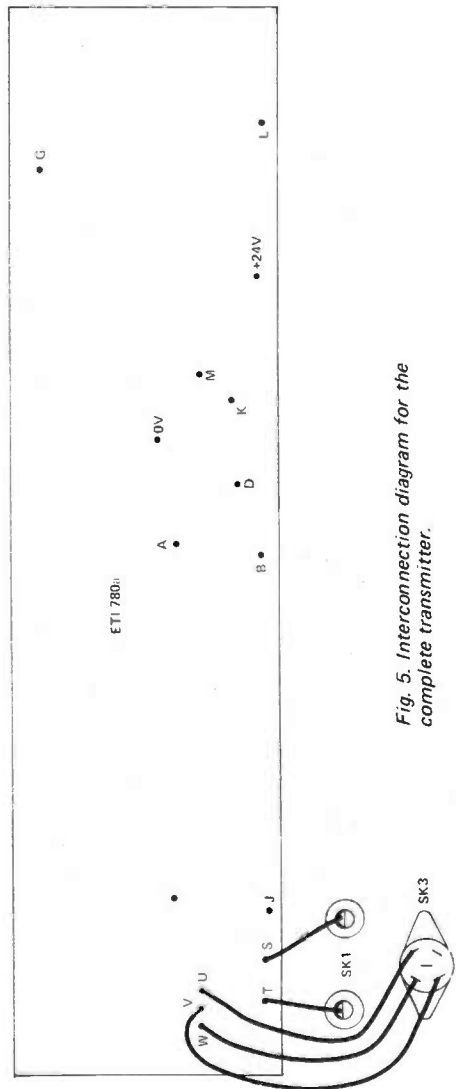
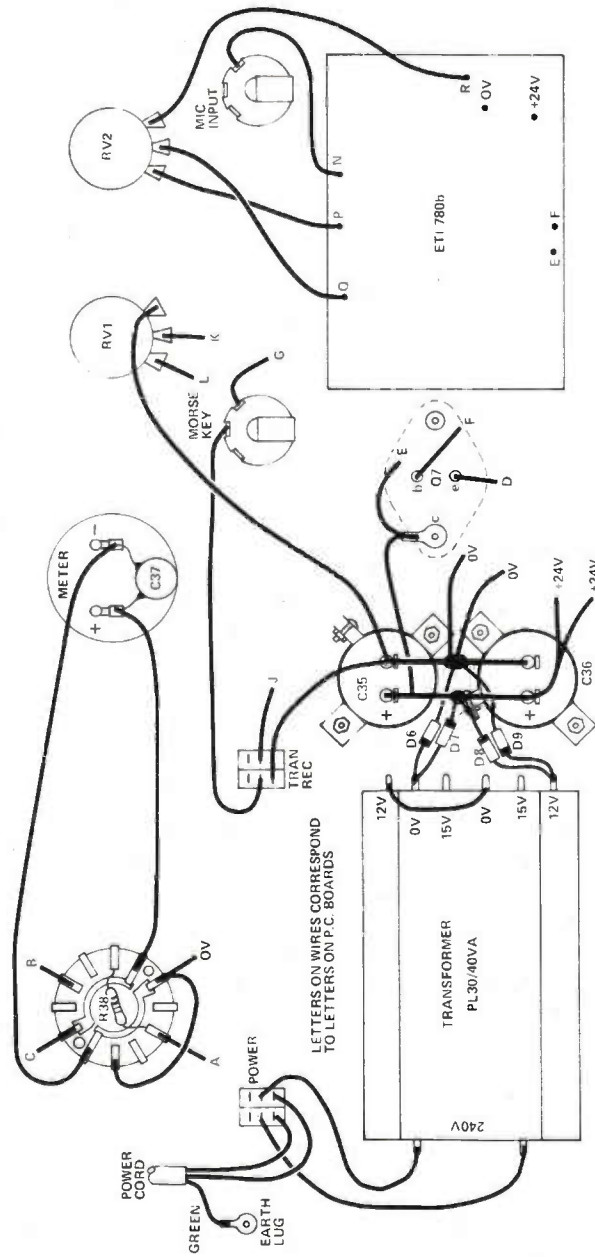


Fig. 5. Interconnection diagram for the complete transmitter.

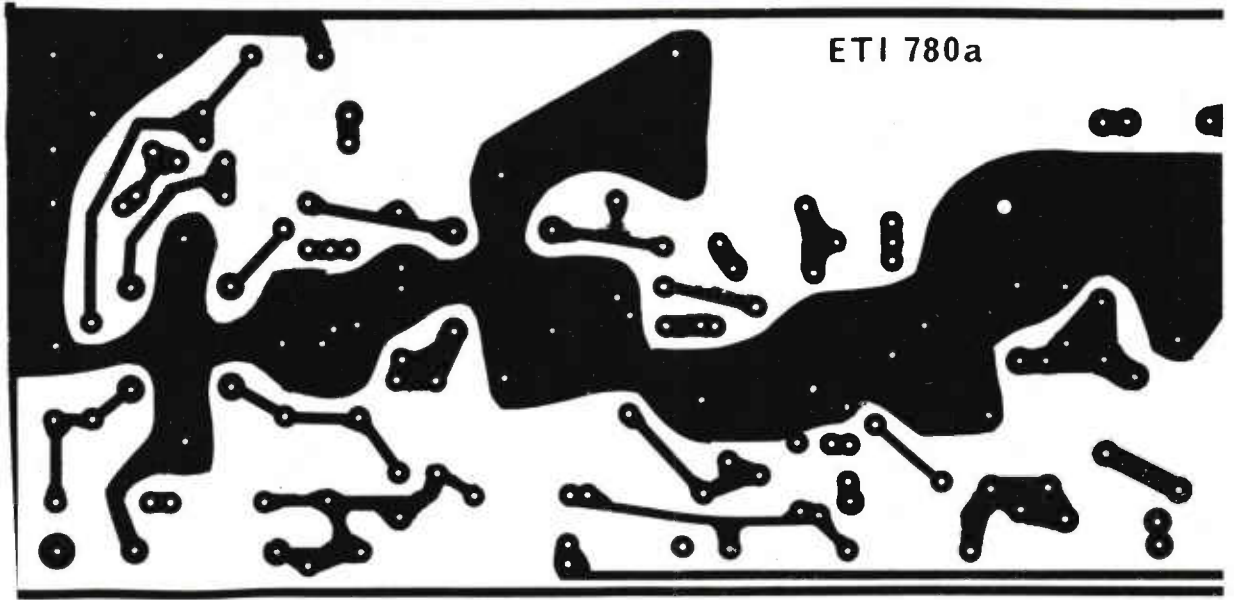

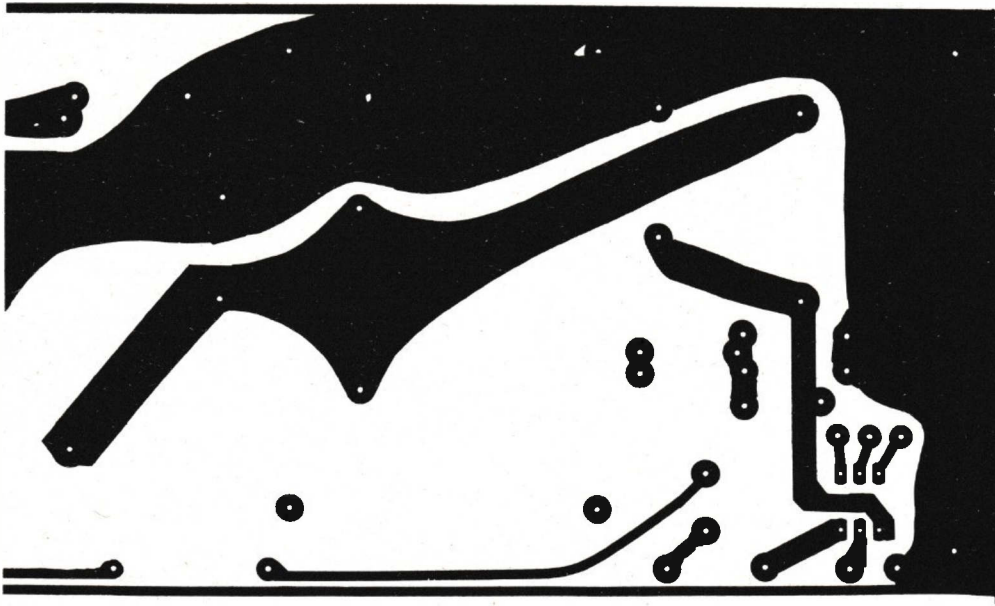


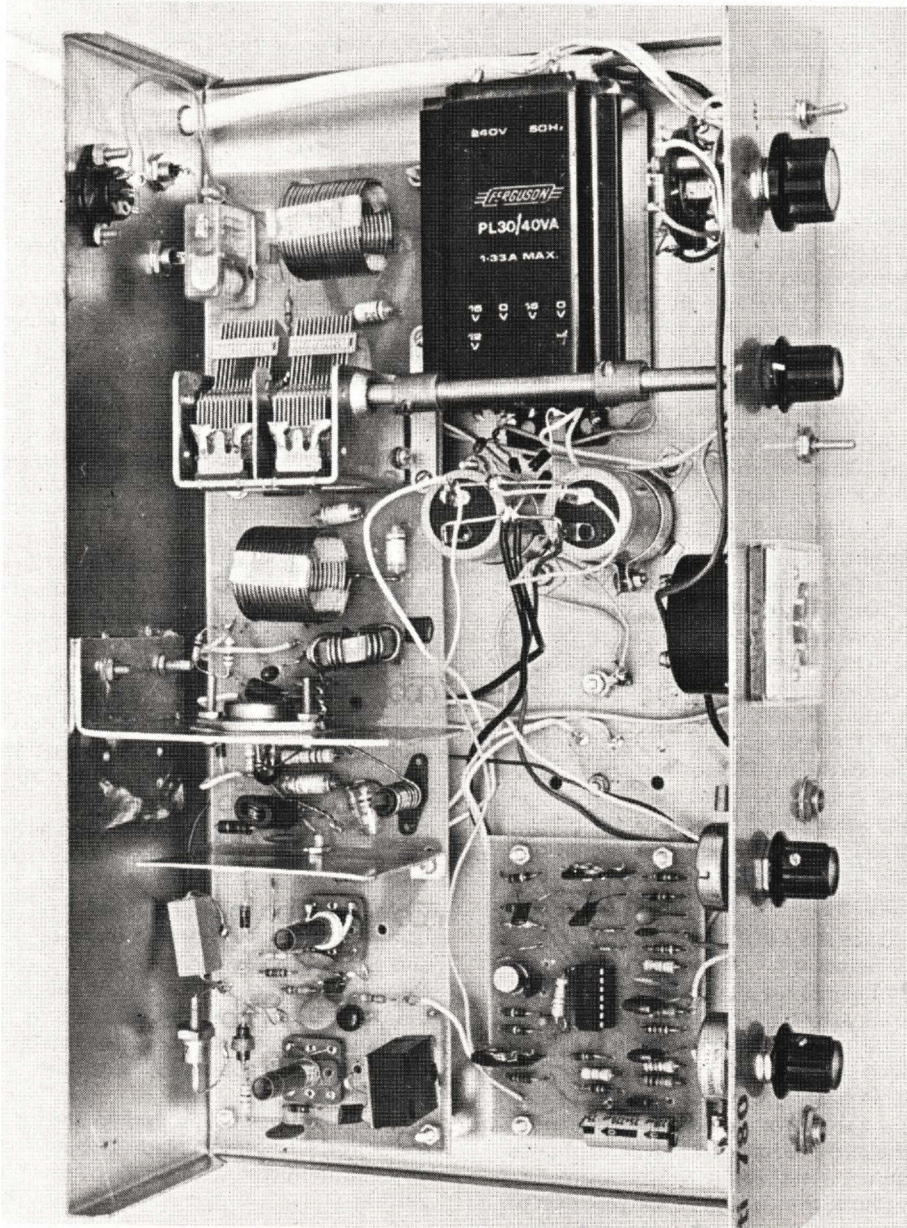Front panel artwork. Full size 334 x 82 mm.




Inside the transmitter. The modulator board is on the left and the RF board at the rear.

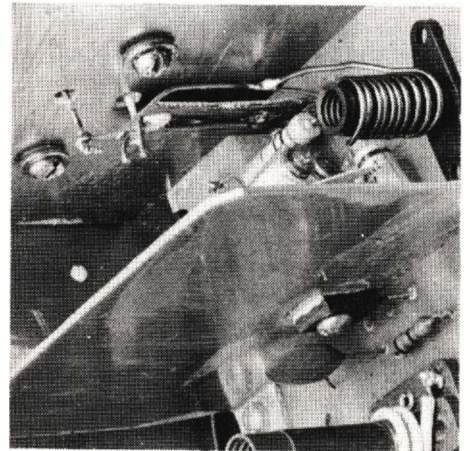The heatsink for the BDY92 is on the right and that for the BD139 (Q3) on the left. Note the emitter connection for Q5 constructed from a piece of PC board to which the emitter lead is soldered. See also Figure 6.



## eti 780

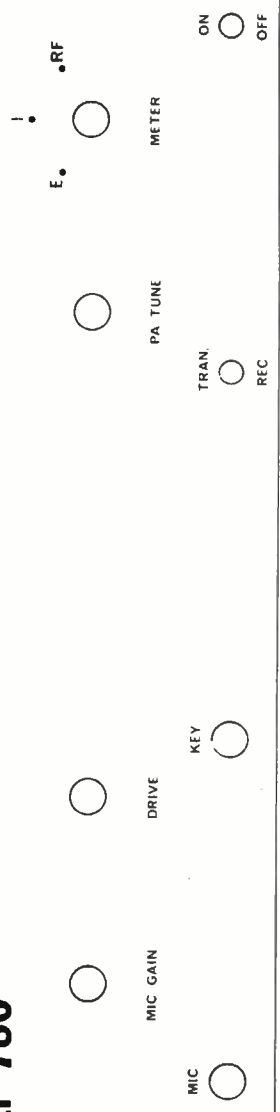

# Novice transmitter

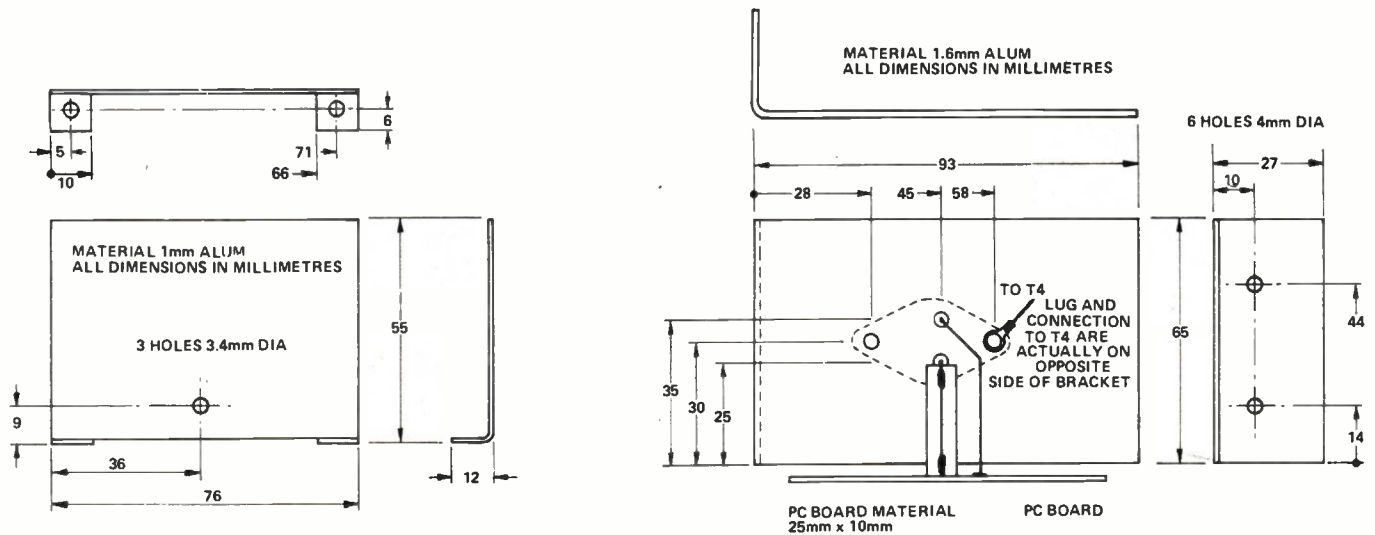


Fig. 6. Heatsinks for Q3, BD139 (left), and for Q5, BDY92 (right). Note the emitter lead for the BDY92 is constructed from a piece of pc board and a piece of thick tinned copper wire. See the photo on page 77.

Continued from page 71.

removed to solder these leads in position.

Using the interconnection diagram as a guide, attach a length of hookup wire to each point on the board which has to be terminated elsewhere and then bolt the completed board and heatsink assembly into the chassis. Note that all the standoffs are made of brass.

**Modulator board** Assemble components to the board as shown in the second component overlay, taking care to correctly orientate the integrated circuit, the transistors, electrolytics and the diode. Attach leads to all points which have to be terminated elsewhere and mount the board into position in the chassis. Now mount the 2N3055 (Q7) underneath the chassis using an insulation kit.

**Final assembly** Fit the power cord through a grommet in the rear of the chassis and secure with a cable clamp. Then terminate the cable as shown in the interconnection diagram. Fit the power transformer, filter capacitors and all switches and pots to the front panel. Interconnect components as shown on the wiring diagram and then extend the shaft of the PA-tuning capacitor out through a grommet in the front panel by means of two 6 mm diameter extension shafts.

Fit large rubber feet to the chassis so that Q7 has sufficient clearance and fit a plastic cover to the transistor to protect against accidental short circuits.

**Setting up** Commence the setting up procedure by adjusting RV4 to mid position and RV3 to its minimum position. Terminate the output of the transmitter into a 75 ohm dummy load, set the drive control, RV1, fully anticlockwise. Set the T/R switch to the 'receive' position.

Switch on the transmitter and ensure that Q5 is not drawing current. If it is check for a fault.

Now adjust the slug in transformer T1 until the oscillator is working. This may be determined by checking the voltage across the 100 ohm resistor, R1 — this should peak to a maximum as the slug is tuned. If the oscillator does not operate check the operating frequency of the coil and the capacitor with a GDO. If this is OK then the fault might be due to insufficient feedback. To cure this reduce the value of C2. Changing the value of C2 affects the resonant frequency of T1 so it may be necessary to modify the value of C3 in order to stay within the adjustment range.

Once the oscillator is working correctly switch the T/R switch to 'transmit' and adjust the slug in T2 for a voltage peak across R5 (22 ohms). Now whilst observing the current on the meter turn up the drive control until a quarter scale reading is obtained. Now adjust the tuning for maximum power into the dummy load (indicated by a peak on the meter in the RF position).


Check the voltage at the junction of

R16 and C13 and adjust RV4 to give 10 volts at this point. Now adjust the value of R1 to obtain a half scale reading on the meter in the 'E' position. This connects the meter to read the voltage to the PA. Continue to adjust the drive and PA tuning until the current read by the meter does not increase any further. Advance the drive slightly past this point. Check the meter 'I' calibration by measuring the voltage across R16 and then calculating the current.


**Audio** The settings required for RV2 and RV3 are best found by experiment when 'on-air'. An initial starting point can be found whilst running the transmitter and listening to the output on a receiver (make sure that the receiver is not overloaded) by putting RV3 in its minimum output position and adjusting RV2 for maximum recovered audio at the receiver (with least distortion). Now, whilst keeping the distortion as low as possible, increase the output from RV3 and decrease RV2 (keeping the recovered audio volume maximum) until the distortion starts to increase and a reduction in RV2 makes no difference to the audio level. At this point the clippers D4 and D5 are beginning to operate. Check for splatter and if excessive adjust RV3 until the splatter just stops.

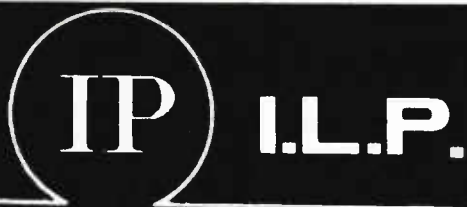That completes the setting up and the transmitter is now ready to help you communicate with the outside world.






# SHEER SIMPLICITY!

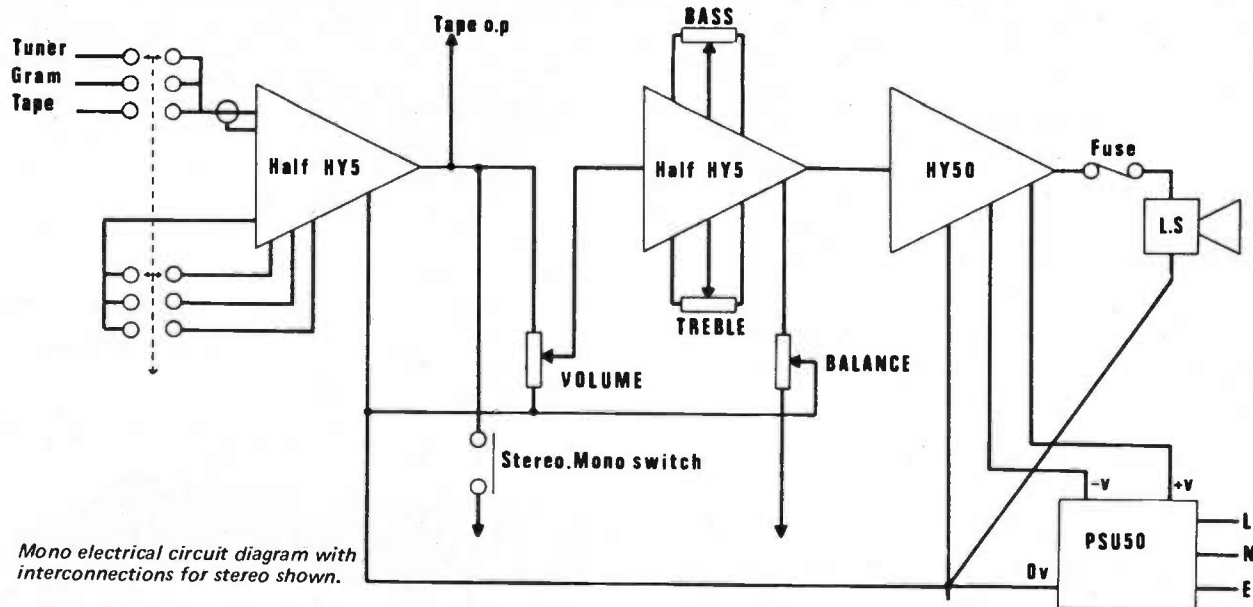

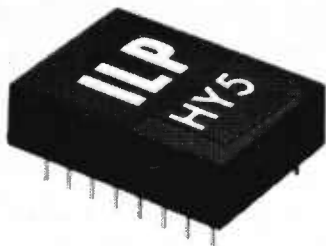Mono electrical circuit diagram with interconnections for stereo shown.



The HY5 is a complete mono hybrid preamplifier, ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

#### TECHNICAL SPECIFICATION

##### Inputs

Magnetic Pick-up 3mV, RIAA  
 Ceramic Pick-up 30mV  
 Microphone 10mV  
 Tuner 100mV  
 Auxillary 3-100mV  
 Input impedance 47kΩ at 1kHz.

##### Outputs


Tape 100mV  
 Main output Odb (0.775 volts RMS)

##### Active Tone Controls

Treble ±12db at 10kHz  
 Bass ±12db at 100Hz
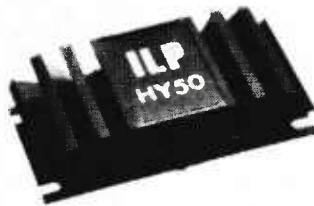
##### Distortion

Signal/Noise Ratio 0.05% at 1kHz  
 68db  
 Overload Capability 40db on most sensitive input  
 Supply Voltage +16-25 volts.  
 PRICE \$16.06 P&P \$0.30



The HY50 is a complete solid state hybrid Hi-Fi amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided: Input, output, power lines and earth.

#### TECHNICAL SPECIFICATION

Output Power 25 watts RMS into 8Ω  
 Load Impedance 4-16Ω


Input Sensitivity Odb (0.775 volts RMS)  
 Input Impedance 47kΩ

Distortion Less than 0.1% at 25 watts typically 0.05%

Signal/Noise Ratio Better than 75db  
 Frequency Response 10Hz-50kHz ±3db

Supply Voltage ±25 volts  
 Size 105 x 50 x 25 mm.

PRICE \$20.27 P&P \$0.40

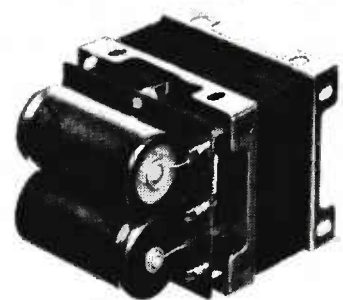

The PSU50 incorporated a specially designed transformer and can be used for either mono or stereo systems.

#### TECHNICAL SPECIFICATIONS

Output voltage 50 volts (25-0-25)

Input voltage 210-240 volts

Size L.70, D.90, H.60 mm.

PRICE \$20.41 P&P \$2.00

P&P \$2.00 FOR 1 COMPLETE SET OF HY5 + HY50 + PSU50

**TWO YEARS GUARANTEE ON ALL OUR PRODUCTS**

**K. D. FISHER & CO.**  
 P. O. Box 34, Nailsworth, S.A. 5083.  
 Telephone 269-2544.

Please Supply \_\_\_\_\_  
 Total Purchase Price \_\_\_\_\_  
 I Enclose Cheque  Postal Orders  Money Order

Name & Address \_\_\_\_\_  
 Signature \_\_\_\_\_

# MERCEDES. VOLVO. LUXMAN.

## SPECIFICATIONS ARE JUST THE START 'OF THE FEELING'



Luxman L100 integrated stereo amplifier.

You don't rush into building a \$1,000\* amp. And you don't rush into buying it.

You take your time, and 'feel' it.

Luxman believes that certain performance parameters of an amplifier; those *not* evaluated by the normal tests in universal use, are directly responsible for differences in sound quality. Accordingly, Luxman has adopted a combination of objective and subjective evaluation, including audition by highly qualified listening panels. It takes a little longer (but then Luxman is likely to spend a year designing a fascia panel); but when you are through, you know it doesn't just work right; it feels right.

By all means, start with the specifications of Luxman L100; like 110 watts per channel at 8 OHM load from 20 Hz to 20 KHZ, with less than 0.05% total harmonic distortion.

Consider the special concern for low phase shift and stability to minimise distortion; the exclusive 'Linear equaliser', the worlds first 'touch mute circuitry' to reduce volume instantly, and so on, and so on. But then, have a 'test drive'; a good long one. It's the only real way to get the 'total feeling'.



Luxman R1500 AM/FM stereo receiver.

We'll never make a 'cheap' amp., but we do make less expensive ones.

And we're very proud of them.



Luxman R800 AM/FM stereo receiver.

If you feel you don't need 110 watts per channel, consider Luxman R1500 which provides 75 watts, or Luxman R800 at 40 watts; and still maintain total harmonic distortion at 0.05%. Or any other fine amp. from the comprehensive Luxman range. What we *don't* leave out, is the way we go about designing them – with a dedication to build exceptionally fine pieces of equipment.

#### Available from:

• N.S.W.: M & G Hoskins Pty. Ltd., (Showroom) 400 Kent St., Sydney 2000. Telephone: 559-4545 & 559-3693. • QLD: Stereo Supplies, 95 Turbot St, Brisbane 4000. Telephone: 21-3623. • S.A.: Challenge Hi-Fi, 96 Pirie St, Adelaide 5000, Telephone 223-3599. • TAS.: Audio Wholesalers Pty. Ltd., 9 Wilson St, Burnie 7320. Telephone: 31-4111 • VIC.: Encei Electronics Pty. Ltd., 431 Bridge Road, Richmond, 3121 Telephone: 42-3761. • W.A.: Albert TV & Hi Fi, 282 Hay St, Perth 6000. Telephone: 25-2699. • A.C.T.: Duratone Hi-Fi, Cnr, Botany St & Aitree Crt, Phillip 2606, Telephone: 82-1388.

#### Sole Australian Distributors:

INTERNATIONAL DYNAMICS (AGENCIES) Pty. LTD.  
23 Elma Rd., North Cheltenham, 3192. Melbourne – 95-1280.

\* Prices vary.

ULTIMATE HIGH FIDELITY STEREO COMPONENTS




# SPECIFICATIONS ARE JUST THE START 'OF THE FEELING'

L/MVL



# Once again Europe sets the standard for speakers

## -and you install them yourself!

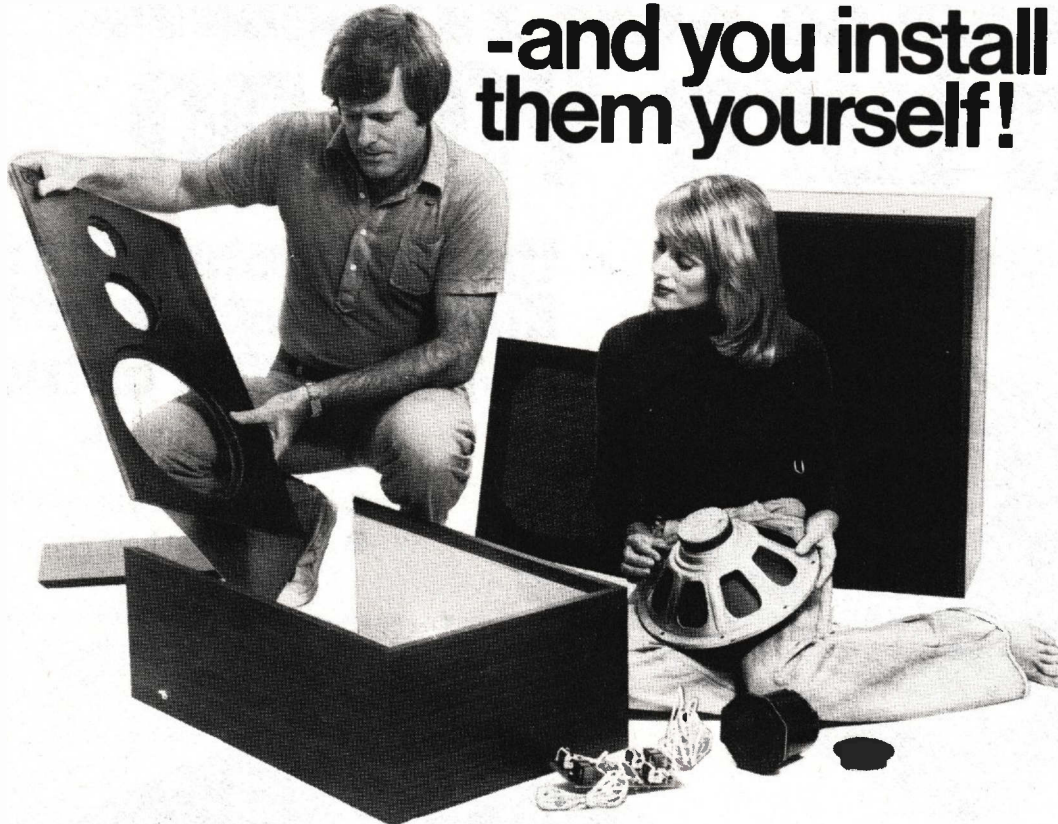

Sooner or later in the search for that perfect sound you come up against an inescapable fact. You have to turn to Europe.

Today's range of Philips High Fidelity Loudspeakers represents the finest that Europe has to offer. We can supply full instructions for you to install them yourself.

The Philips range comprises tweeters, squawkers and woofers which you can combine into systems to satisfy the hardest-to-please sound fanatic. Some of the systems are available in kit form complete with woodwork and full assembly instructions.

To assist you in your selection we supply full performance data and details on mounting and enclosure for each speaker.

If you would like to know more about these superb imported European units, then send in this coupon:—

#### Philips Electronic Components and Materials

Sydney.....	42 1261
Melbourne.....	69 0300
Brisbane.....	277 4822
Adelaide.....	223 4022
Perth.....	65 4199

Philips Electronic Components and Materials,  
P.O. Box 50, Lane Cove, N.S.W. 2066.

Please send me details and enclosure  
information on your  
High Fidelity Loudspeakers.

Name .....

Address .....

.....

.....

.....Postcode.....



**Electronic  
Components  
and Materials**

# PHILIPS

# C.E.C. has a turntable to turn YOU on...



BD1000

**the ideal system starter  
BD1000 complete with  
EMPIRE 2000E cartridge**

- Wow and flutter less than 0.12%.
- Rumble better than 40DB.
- Complete in fully imported base and cover.

Frequency response 10HZ to 30KHZ tracking 1 to 3GM.



BD7000

**for the audiophile  
BD 7000**

- DC Hall motor—Servo controlled.
  - Built-in strobe light.
  - Fine speed adjustment.
  - Auto or manual operation.
  - Wow and flutter less than .04% (WRMS).
  - Signal to noise ratio 65DB (DINB).
  - Tracking weight 0.25 to 3GM.
  - J-shaped tone arm with hydraulic cueing.
  - Magnificent, fully imported base and cover.
- The BD7000 is supplied without cartridge.

The  turntable range includes the semi-automatic BA300 and fully automatic BA600. One of the four models is right for you. All have the famous C.E.C. 5-YEAR WARRANTY.



 harman australia pty ltd

271 Harbord Road, Brookvale, Tel 939 29 22  
PO Box 6, Brookvale NSW 2100



# HAM RADIO SUPPLIES

MAIL ORDER SPECIALISTS

323 Elizabeth Street, Melbourne (2 doors from Little Lonsdale Street) 674286 67 7329  
new Richmond branch now at 390 Bridge Rd., Richmond Phone 42-5174



**MODEL C1000M MULTIMETER**  
Compact, handy and versatile, the C1000M is the ideal low cost pocket meter. Mirror Scale. Specifications: 1,000 Ohm/Volt DC; 1,000 Ohm/Volt AC; DC volts — 10; 50; 250; 1,000; AC volts — 10; 50; 250; 1,000; DC amps — 1 mA; 100 mA; Ohms — 150 K $\Omega$ ; Centre scale — 3 K $\Omega$ ; Decibel — 10 dB to 22 dB; Dimensions — 3-1/2" x 2-3/8" x 1-1/8" 90 x 60 x 30 mm.

**\$7.95**  
Post Free.



**MODEL C-7077/P MULTIMETER.**  
Specifications: 100,000 ohms/volt DC; 10,000 ohms/volt AC; DC volts — 5, 5; 25; 50; 250; 500; 1,000. AC volts — 10; 50; 250; 500; 1,000. DC amps — 10  $\mu$ A; 2-5 mA; 25 mA; 500 mA. Ohms — 10 K $\Omega$ ; 1 M $\Omega$ ; 10 M $\Omega$ ; 100 M $\Omega$ . Centre scale — 150  $\Omega$ ; 15 K $\Omega$ ; 150 K $\Omega$ ; 1-5 M $\Omega$ . Decibel — 20 to +22 dB. Dimensions — 151 x 102 x 48 mm Diode protected movement. Carrying case available Model C.

**\$29.50**  
P&P \$1.50.

**MODEL OL64 D/P MULTIMETER.** Very ruggedly constructed this model is particularly suitable for workshops. It features special scales for measurement of capacitance and inductance. Diode protected movement. Specifications: 20,000 Ohm/Volt DC. 8,000 Ohm/Volt AC. DC volts — 0.25; 1; 2.5V; 10; 50; 250; 1,000; 5,000. AC volts — 10; 50; 250; 1,000. DC amps: 50  $\mu$ A; 1 mA; 50 mA; 500 mA; 10 A. Ohms — 4 K $\Omega$ ; 400 K $\Omega$ ; 4 M $\Omega$ ; 40 M $\Omega$ . Centre scale — 40  $\Omega$ ; 4,000  $\Omega$ ; 40,000  $\Omega$ ; 400,000  $\Omega$ . Decibel: —20 to +62 dB. Dimensions: 6" x 4-1/5" x 2"; 152 x 107 x 51 mm. Capacitance: 250 pF to 0.02  $\mu$ F. Inductance: 0/5000H Carrying case available Model C.



**\$25.95** P&P \$1.50.

**MODEL AS100 D/P MULTIMETER.** This meter features double zener diode meter protection and 3 1/2" full view easy to read 2 colour scale. It is fitted with polarity reversing switch and housed in a strong moulded case with carrying handle. Specifications: 100,000 ohm/volt DC. 10,000 ohm/volt AC. DC volts — 0.3; 12; 60; 120; 300; 600; 1,200. AC volts — 6; 30; 120; 300; 600; 1,200V. DC amps — 2 K $\mu$ A; 200 K $\mu$ A; 20 M $\mu$ A; 200 M $\mu$ A. Centre scale — 20  $\Omega$ ; 2,000  $\Omega$ ; 20,000  $\Omega$ ; 200,000  $\Omega$ ; 20 M $\Omega$ . Decibel — 20 to +57 dB. Dimensions — 7-3/5" x 5-2/5" x 2-3/5" 193 x 137 x 66 mm. Carrying case available model I.



**\$39.50**  
P&P \$1.50.

## 27 MHz TWO-WAY RADIOS

FOR INDUSTRY, FARM, BOATS, SPORTS, ETC.

**MODEL NC-310 DE LUXE 1 WATT 3 CHANNEL CB. TRANSCEIVER**  
● WITH CALL SYSTEM  
● EXTERNAL AERIAL CONNECTION  
SPECIFICATIONS, NC-310




Transistors: 13. Channel Number: 3, 27.2400 MHz Citz. Band included. Transmitter Frequency Tolerance:  $\pm 0.005\%$  RF Input Power: 1 Watt. Tone Call Frequency: 2000 Hz.

Full range of crystals for 27 MHz novice band available \$6.50 pair extra.

**\$49.50 PER UNIT.**

## TARIFF REDUCED PRICE

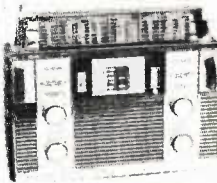

**BARLOW-WADLEY XCR-30**

a truly portable communications receiver, based on the WADLEY LOOP principle, the same principle as applied in

the DELTAHET and RACAL receivers. A truly crystal-controlled highly sensitive multiple heterodyne portable receiver of exceptional stability with continuous, uninterrupted coverage from 500 kHz to 31 MHz.

All for **\$239** F.O.R.

## AM/FM/VHF/TV. MONITOR MULTIBAND RADIO. NEW MODEL AC/DC.

Latest military design multi-band radio, 30 transistors and diodes. With exclusive (LED) light emitting diode tuning indicator for positive station selection. Battery and electric covers all popular AM and FM bands.

**\$39.50**

P & P \$2.50

Beware of more expensive imitations

## SOLID STATE 19 TRANSISTOR MULTI-BAND RADIO — 9 RANGES

AM, SW, FM, VHF, AIR, PB BATTERY/OPERATED COLOUR CODED 9 BAND DIAL

1. AM 535 to 1600 kHz, 2. Marine 1-5 to 4 MHz, 3 & 4. Combined SW 4 to 12 MHz, 5. 30 to 50 MHz, 6. 88 to 108 MHz, 7, 8 & 9. combined VHF Aircraft 145 MHz-174 MHz incorporating weather band. Slider controls, Dial light, Fine tuning control, Flip-up Time Zone map, Telescope antennas complete with batteries.

SPECIAL PRICE **\$59** Post Pack \$3.00

## HAM GEAR NOW IN STOCK

Uniden 2020 AC-DC transceivers 10 to 80 M. \$570 Trio Kenwood TS-520 AC-DC transceivers 10 to 80 M. \$560. Yaesu Museu FT-10-T-E AC-DC transceivers 10 to 160 M. \$670. Trio-Kenwood model QR-666 170 kHz to 30 mHz AC-DC receivers. \$300. Drake model SSR-1 Wadley loop 500 kHz to 30 mHz AC-DC receivers. \$325. Hy-gain antennas — 14AVQ 10-40 M. verticals, 19' tall, no guys. \$69. 18AVT-WB 10-80 M. verticals, 23' tall, no guys. \$95. FDK Multi-7 2M. FM 10 Watt transceivers with 12 sets of crystals, available at 7 repeater and anti-repeater frequencies plus channels 40, 50 and 52 \$230. Ken products KP-202 2 M. FM handheld transceivers with crystals for repeaters 1 to 4 incl. and channels 40 and 50. \$149. Kyokuto 2M. FM 12 Watt output transceivers with digital read-out and crystal synthesized PLL circuitry, 400 5 kHz transmit and 1000 5 kHz receive channels for normal simplex, repeater and anti-repeater operation. \$300. Icom IC-202 2 M. SSB handy transceivers 144.0-144.4 MHz. \$195. Antenna rotators — CDR AR-22 junior for light and vhf beams. \$55. CDR Ham-II senior for all but 40 M hf beams. \$175. KEN KR-400 for all medium hf beams with disc brake. \$105. All three models rotators complete with 230V AC indicator-control box.

**SE-360 SIGNAL TRACER & INJECTOR**  
SPECIFICATION: Single injector approx 1 kHz level 0.5V. Gain: 60 dB. Input impedance: Over 75K ohms. Attenuation Factor: 0.2-0.40-60 dB. Output impedance: 8 ohms and 600 ohms. Meter: VU200  $\mu$ A. Speaker: 2 1/2" Dynamic. Power Supply: 9 Volt Dry Cell. Size: 5 1/2" x 3 x 2". Supplied complete with two shielded test leads (AF & RF). R.F. probe and instruction manual. **\$37** P.P. \$2.00

## C.B. CRYSTALS

HC18 holders. Standard size fit. All modern transceivers with 455 kHz I.F. 27.065 mHz. 27.085 mHz. 27.125 mHz. 27.155 mHz. 27.185 mHz. 27.205 mHz. 27.225 mHz.

**\$6.50** a pair (receive & transmitter)

## SPECIFICATIONS:

**TE-20/D R.F. SIGNAL GENERATOR**  
SPECIFICATIONS: Frequency Range: 120kc/s — 500mc/s (6 Fundamental Bands and 1 Harmonic Band). Frequency Accuracy:  $\pm 2\%$ . Audio output: to 8 volts. Internal Modulation: Approx. 400c/s. Tube complement: 12BH7A, 6AR5, Silicon Diode and Germanium Diode. Printed Circuit for uniform characteristics. Power Source: 105/125, 220/240 volts AC, 50/60 cps 12 watts. Dimensions: 140 x 215 x 170mm. Weight: 2.8kg.

**\$52.50** p.p. \$2.00

## TE-22/D AUDIO GENERATOR

SPECIFICATIONS: Frequency Range: Sine Wave — 20 to 200,000c/s in 4 bands. Square Wave — 20 to 30,000cps. Frequency Response:  $\pm 1 1/2$  dB. Output Impedance: 1 Kohm. Frequency Accuracy:  $\pm 5\%$ . Output Voltage: Sine wave 7 volts (RMS). Square wave 7 volts (P-P). Distortion: Less than 2%. Tube complement: 6BM8, 12AT7, 6x4. Accessory: 1 — Output cable. Power Supply: AC 50/60 cps 220-240 volts. Dimensions: 215 x 170 x 140mm. Net Weight: 3 Kgs. **\$62.50** p.p. \$2.00

## TE-15 TRANSISTOR GRID DIP METER.

SPECIFICATIONS: Transistors: 3 and 1 diode. Meter: 500uA F/S. Battery: 9 volts PP3. Dimensions: 180 x 80 x 40mm. Weight: 730 g. Frequency Range: 400 kc/s — 280 mc/s with 6 coils; A coil 0.44-1.3 mc/s; B coil 1.3-4.4 mc/s; C coil 4-14 mc/s; D coil 14-40 mc/s; E coil 40-140 mc/s; F coil 120-280 mc/s.

**\$39.50** p.p. \$2.00

## FS5 SWR AND R.F. POWER METER.

Power Range: 0, 10W, 100W (2 ranges). SWR: 1:1, 1:3. Freq. Response: 3MHZ-150MHZ. Suitable Connector: M type. Impedance: 50 ohm, 75 ohm. Dimensions: 160 x 85 x 98 mm. Weight: 750 g. **\$29.50** p.p. \$2.00

# ELECTRONICS —it's easy!

## PART 31

### Digital computer systems — peripherals, stores and microprocessors.

ALL COMPUTING SYSTEMS HAVE a Central Processing Unit, (discussed previously) and a number of pieces of external equipment associated with them. Such additional units, known as peripherals are necessary to handle the flow of information between the outside world and the Central Processing Unit (CPU).

The range of peripherals available today is extensive. Basically the design aims are to provide interfaces between the human or automatic plant user and the computing system which are the easiest to use, the cheapest to implement and which have the means to transfer data as fast as is desired.

At present — though this will undoubtedly change in the future — we are unable to communicate with the computer by the same means that we communicate with each other — that is by direct speech and vision. Peripherals, are by necessity of our technological and economic limitations still very much compromises to the ideal, except in applications where the computer interfaces to hardware plant, such as in process control, when interface problems are easier to solve as such

systems communicate by the same signal formats.

**Card and Tape Punches and Readers** — In order to make good use of the high speed of electronic computing circuits, the input and output functions should ideally be capable of transferring the data at a comparable speed. Rarely has this ideal been realised. The throughput rate of peripherals has been speeded up enormously since the first EDP system but, similarly, the rate of computation has been increased.

Because of this shortcoming, data (in human operator use) is first prepared by hand onto a medium that can feed into the EDP system at rates far exceeding the operator's ability. It is then stored in the machine ready for access when the CPU needs it.

The earliest form of input/output medium used punched holes made in a pile of paper cards or a continuous tape. We inherited these from a 17th century weaving machine via the Hollerith census sorter. Figure 1 shows the commonly used Hollerith coded punched card. The holes are punched out in a code that represents the alphanumeric symbols shown above

each row. Figure 2 is a section of punched tape: these are available with 5,6,7 and 8 hole positions across the tape width. (The smaller hole is for the timing drive sprocket). Tape readers are built to read code from a specific width tape: that is, a 5-hole tape could not be used on an 8-hole system. Tapes and cards which are to be used extensively can be made in more durable materials such as oiled paper, Mylar and aluminium-Mylar.

The holes in cards are produced by mechanical punches. These comprise a punching head by which the appropriate holes are made for each character in response to a typewriter keyboard-input. Keyboard layouts are based on the familiar office typewriter. Extra keys are added for computer applications to enable a greater range of control by the operator. Such additions vary widely.

Tape can be punched automatically whilst the teleprinter type of terminal, such as shown in Fig.3, is used as a typewriter. Where the tape is generated as part of an automatic process — as in a data logger, a smaller punch unit is used which incorporates punch drivers activated by control signals — no keyboard is needed. Such a unit is illustrated in Fig.4.

Card and tape readers consist of a transport mechanism that passes the medium across reading heads. Recognition of a code represented by holes is accomplished by mechanical fingers making direct electrical contact (in the slower readers) or by solid-state optical sensing using LED lamps and photo-diode arrays set to sense the passage of light through a hole position. Some method of synchronising the code position with the data values is essential.

Cards can be punched by an operator at rates between 250-500 per hour. They are often checked on a verifier machine that determines if the card is punched in the same way as the check operator keys the code a second time. They can, by contrast, be machine read or sorted, at 200-1000 cards per minute depending upon the complexity of the task.

Tape punching is confined to similarly slow rates of production at the operator stage of preparation. When the punch is

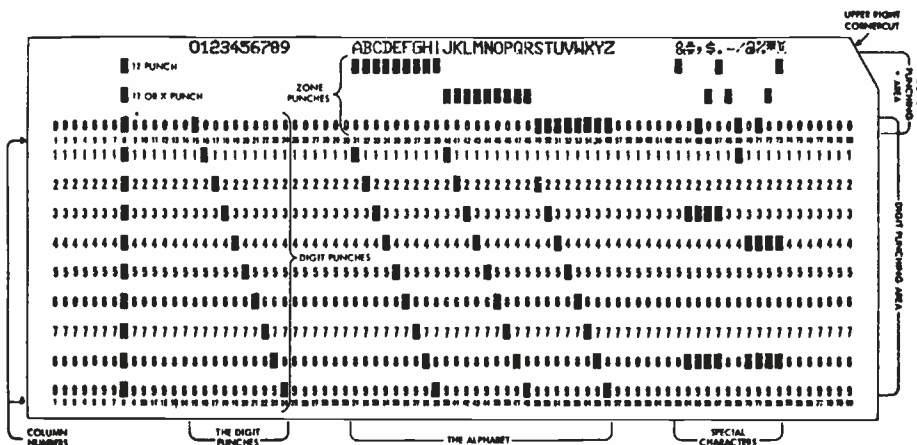


Fig. 1. Standard Hollerith Code used for punched cards.



Fig. 2. Section of 8-hole punched tape. Two rows on the wider side of the central sprocket holes are not used in this data.





Fig. 3. Keyboard teletype terminals provide hard copy and perforate a paper tape (seen lower left) at the same time. The same facility usually can also print hard copy from a ready made tape.

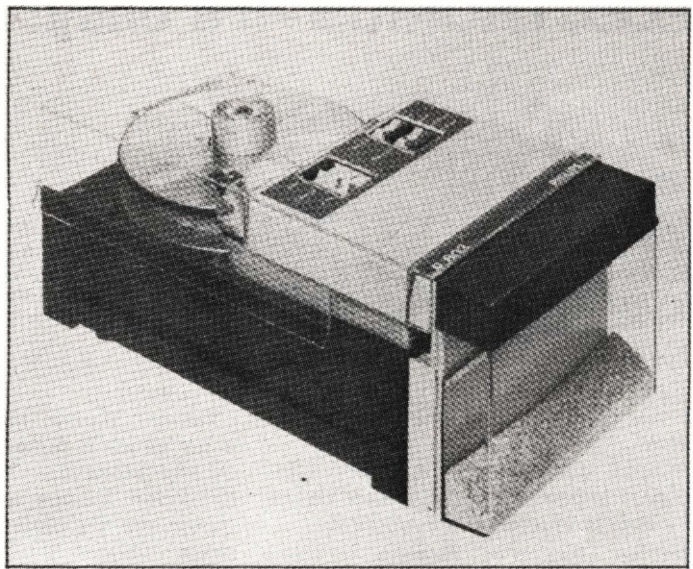


Fig. 4. This Philips P803 unit punches tape at 75 c.p.s.

machine operated, punching rates can rise to 150 characters per second. The speed at which punched tapes can be read varies from very slow, using mechanical sensing up to 600 characters per second or more with high-performance optical equipment.

A considerable amount of electronic logic and drive circuitry is needed to operate a punch unit. Figure 5 is the block diagram of a reader using brushes to sense the presence of holes. Input commands to the punch would emanate from the control unit of the EDP system.

**Magnetic Tape Input/Output Units** — Cards and paper tape store information about commands to the EDP system (the programme) and hold the numerical data to be manipulated. They are, therefore, a form of permanent data storage. They suffice (in the form described above) as a data store when the data quantity is not great. A recent trend, which has speeded up data transfer and reduced the bulk needed to store the programme and data, makes use of magnetic tape in cassette form.

The compact unit shown in Fig.6 can transfer data at 6000 bits per second at a density of 30 bits per millimetre of tape. (Total capacity on a cassette — five million bits). These can also be used as additional memory in the system. Printers — Teletype units are able to provide hard copy printout but due to the slow printout resulting from letter by letter operation they are not used as the main alpha-numeric output of an extensive EDP system. They can printout at only 10 characters per second or so.

The line printer was evolved to speed up this form of output. It prints all the characters of a complete line simultaneously. Line lengths are

typically 132 characters and the faster models can print lines at rates exceeding 1000 lines per minute. (For which an outlay of \$50,000 is required!)

Printing mechanism vary considerably, ranging from development of the fundamental typewriter method, to devices that print each character from a 5 x 7 matrix of dots. Line printers were originally bulky units. Today desktop, typewriter size units, are in common use (Fig.7).

Printers can be programmed via the EDP system to provide any format required — periodic reports, invoices, records, data lists, software record. A crude form of graphical display can also be produced using the position in a line

Fig. 6. Cassette form of magnetic tape is finding greater application as a standard EDP and computing calculator peripheral.



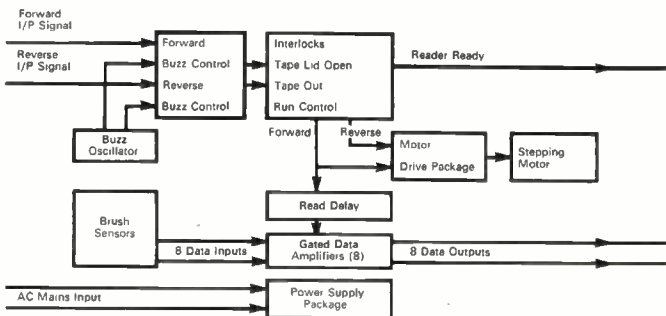


Fig. 5. Block diagram of early model Data Dynamics low-speed tape reader (30 c.p.s.).

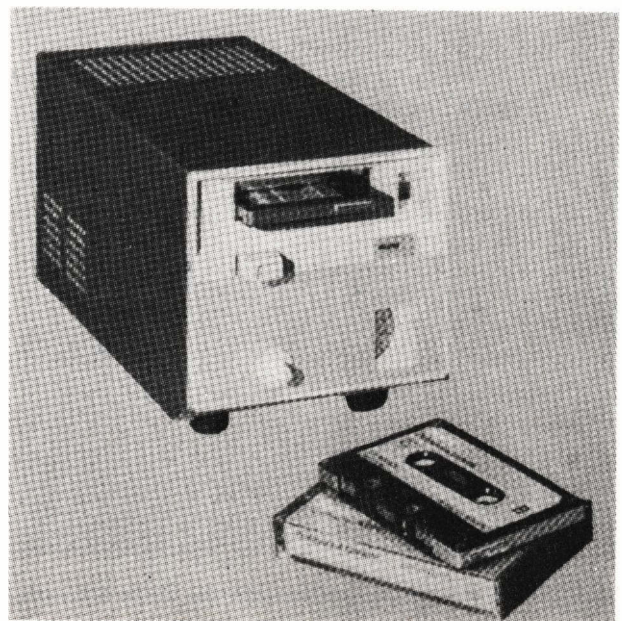

# ELECTRONICS—it's easy!

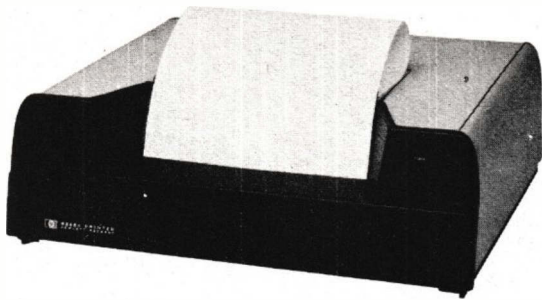

*Fig. 7. This Hewlett Packard 2607A desk-top line printer provides hard copy output (with 6 copies) at 200 lines per minute.*

as one ordinate and the lines as the other.

When computers are used for automatic pagination the printer can be one that produced print-type direct.

**Graphic Display — Plotters —** Many computational tasks ideally require a graphical display of output information not a long list of numbers. Plotters may be of x-y type or y-t type.

The x-y type of plotter is arranged so that the graph paper is held stationary and the pen is capable of being driven both vertically (y axis) and horizontally (x axis).

The y-t plotter has a roll of graph paper which is driven at a constant (and usually adjustable— speed; the pen can be driven in one axis only (y axis). Hence the y-t plotter basically plots a single variable against time. Plotters made particularly for computer operation will be provided with the interface facility that enables direct connection to the EDP system. (Normal plotters require an extensive amount of extra equipment to make them compatible).

Computer controlled plotting of x-y format has the ability to be scaled on

demand and to generate alpha-numeric legends on the plot. It is an easy matter to replicate the plot — the programme is run again.

Plotters may be of the analogue drive kind (a later part discusses plotters in detail) but due to the nature of digital processing the result may still have a quantized appearance if the resolution is not sufficiently small. Alternatively the axes may be driven with stepping motors — such machines are called incremental plotters.

Flat-bed style of x-y plotters are available which can handle paper of all sizes — from a few centimetres square to size of a wall. A medium-size computer controlled flat-bed plotter is shown in Fig.8.

Line drawing rates are limited by inherent electro-mechanical response to around 0.4 m/s in small plotters. The very large machines, when under tight control, are usually capable of around 0.1 m/s translation rates when working to precisions of 25  $\mu$ m. A desk top x-y plotter is shown in Fig.9.


Some y-t plotters incorporate bi-directional drive for the t axis (the paper drive) enabling very long lengths of paper to be driven back and forth along the roll in order to produce an x-y form of plot from a y-t format machine.

**Graphic Display — Visual Monitors —** Many applications require rapid call-up of data that is presented in a way that can be easily read by the operator. It may be quite unimportant to receive it as hardcopy. The cathode ray tube (television) type of display was an obvious choice. Such displays are known as visual display units, VDU for short.

Originally, visual display units were very limited because of the need for a



*Fig. 8. Series 500 automatic drafting system by Gerber Scientific.*

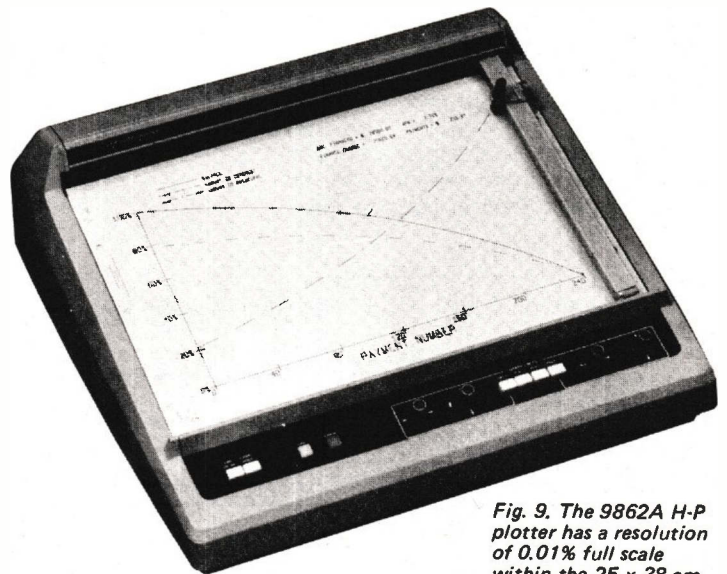

*Fig. 9. The 9862A H-P plotter has a resolution of 0.01% full scale within the 25 x 38 cm area. It will plot vectors at 30 cm per second.*



considerable amount of storage with which to generate written and graphical display forms. However solid-state mass data storage is now relatively inexpensive and VDUs in one form or another are now standard peripherals.

The simplest use of VDUs is to display alpha-numeric information — a section of the software programme, a readout of process plant variables, airline arrivals and departures. This is achieved using digital control and data storage to cause the beam of the CRT to deflect, blanking appropriately, to form the appearance of a static written page.

When the operator becomes involved with the data on the screen and is given the ability to manipulate it toward a desired task the terminal is said to be an interactive graphic terminal. An early example of this is given in Fig.10 which depicts a system whereby air traffic controllers are trained using display terminals.


Once it had been realised how the VDU could be used to produce line drawings designers sought ways to 'draw' on the screen. The result was the 'light-pen'. The operator holds a special stylus on the screen of the CRT. Closed loop controls cause the spot to lock onto movements of the stylus. If the trace path is to be retained, the x, y and intensity coordinates values are fed into the digital memory. Once a line is drawn it can be retained and regenerated in this way. Other operations enable the operator to automatically erase sections of line, straighten lines and smooth curves by computer processing. The complete drawing can then be permanently recorded as hard copy on a plotter or as a data set. Interactive methods have saved an enormous amount of time in tasks such as deciding the extremes of a motor-car wheel movement during the many combinations of springing and steering positions within the wheel arch.

Today's graphic terminals are extremely versatile. Completely self-contained units which incorporate a built-in processor are in common use. A recent release is shown in Fig.11.

Improvements in the storage-tubes used to hold the displays of a CRT system have been coupled with the power of modern computing to provide display terminals that have half-tone photographic quality presentation. Figure 12 shows the quality (after our recopying) obtainable. The images shown are entirely reconstructed on the VDU from digital, not analogue data. Colour displays are also coming into use adding yet more dimensions to the interaction available to the operator.

A recent project of the Australian National University gives some idea of the use of the interactive VDU. In the Department of Engineering Physics a team of research workers have


*Fig. 10. In this Litton digital simulator air traffic controllers learn their skills with make-believe aircraft movements that appear on their display monitors.*

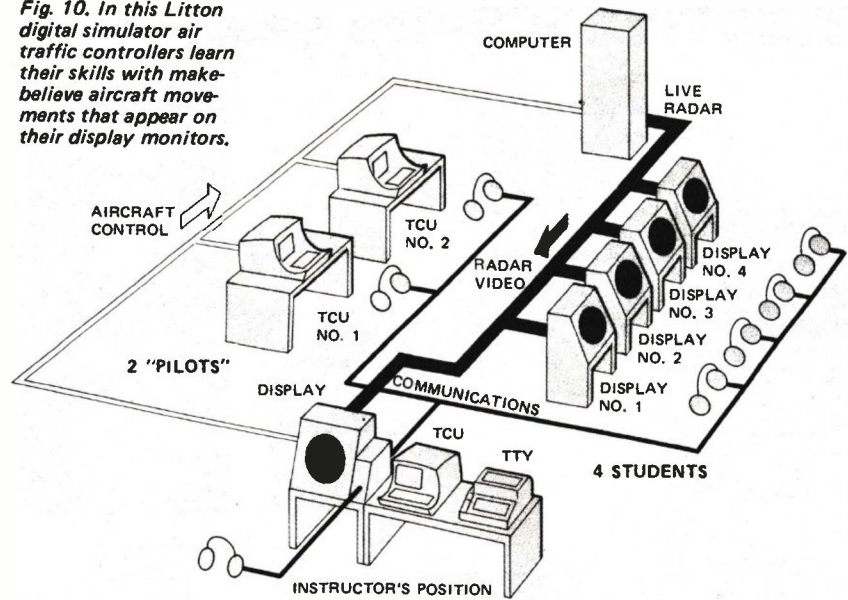

developed a colour display terminal that can call-up the data recorded by the ERTS satellite. The computing system has in its memory file copies of the original ERTS data. Using the graphic terminal the operator can select which form of photograph — IR, false colour, etc., to study. He can then rapidly zoom into a particular area using a joystick control expanding the spatial scale as the search becomes concentrated. Other control includes enabling the colours to be digitized into level zones and to be complimented.

**Instrumentation Interfaces** — When the digital computer has to manipulate measurement and control data from analogue processes, the system must be provided with the appropriate A to D and D to A converters, and the multiplexing arrangement which forms the data logger. These interface peripherals were mentioned in the 29th part of this series.

**MODEMS** and other links — When computer data has to be transmitted over considerable distances it becomes expedient to use telephone lines or

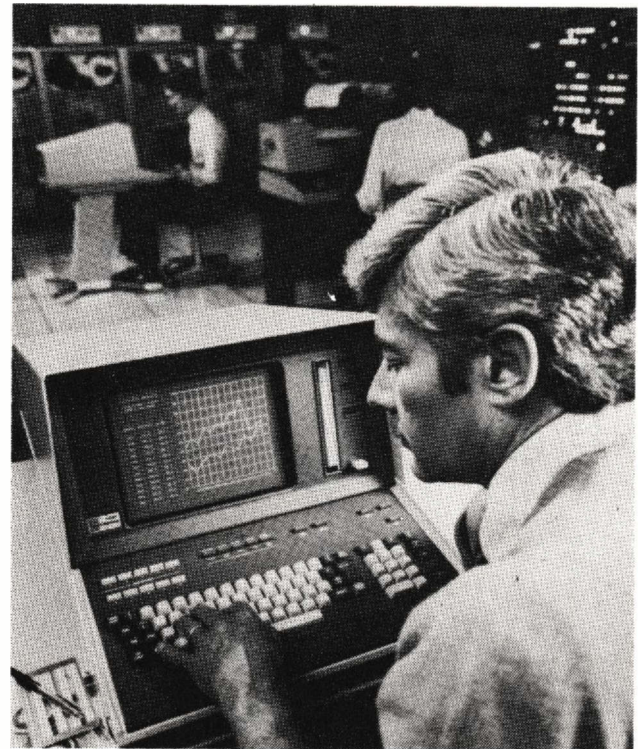

*Fig. 11. Interactive graphic units often now incorporate their own processing and memory to form an off-line self-contained unit — 4051 Tektronix BASIC graphic computing system.*




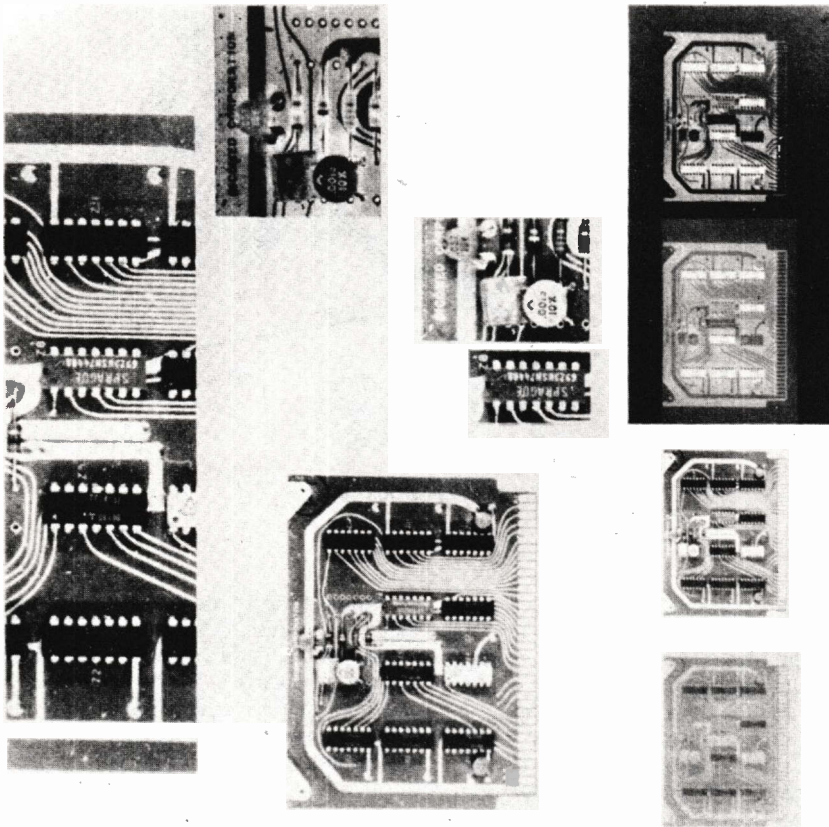


Fig. 12. This multiple image presentation is photographed from the screen of DICOMED digital image display unit.

Fig. 13. (a) When a large enough write current passes in one direction through the ferrite core the core becomes magnetised in one polarity. It thus records a bit.  
 (b) A second wire is added to act as an inhibitor or enhance line.  
 (c) Finishing touches being added to a Philips 3-D core store. (20 planes of 64 x 64 cores, one X wire, one Y wire, read and inhibit wires).

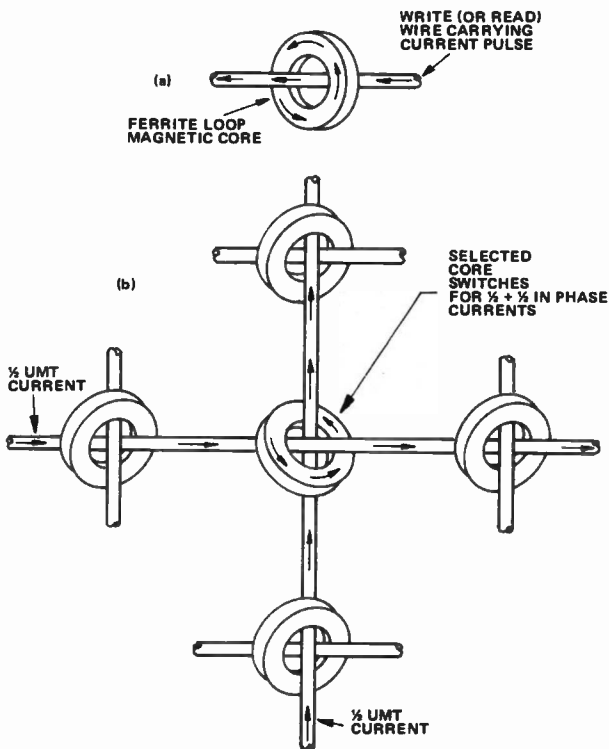

microwave links. Units interfacing computers over telephone lines have become known as MODEMS (a word built by combining Modulator and Demodulator). Links are dealt with in Part 32 — in which signals and transmission are covered.

**Miscellaneous Peripherals** — New methods for communicating with the power of an EDP system continue to be devised in an endeavour to overcome the interface difficulty humans have with electronic machines. We are still a long way from the stage where we need only casually to talk to the machine. Steps are, however, in progress toward this aim with research into spoken word and written word recognition. Neural research into brain waves may one day be coupled with electronic hardware to provide direct thought-links.

Special cases demand special solutions. Work at Warwick University in England has resulted in computer controlled production of braille maps for the blind. Automatic mapping and language translation are other areas where positive progress is being made into very complex human communication processes.

## STORAGE

Inside a CPU and external to it will be found a memory of some kind. This is used to store the vast quantities of coded data needed to perform the various tasks.

Memory within the CPU is characterised by the need for high speed access to any data bit needed. The requirement on capacity is less stringent. Memory external to the CPU will, by





the necessity of machine organisation, be a little slower to access but it will usually need much greater storage capacity.

**CPU Memory — Core — storage** is needed in the CPU to hold important programme instructions and to act as a temporary home for data generated in the course of a manipulation.

There are many options open to the designer but the storage method that has emerged as the optimum for CPU storage is magnetic core storage — known simply as the core store. (This situation will, however, soon change, the preference going to solid-state methods). Magnetic core storage makes use of the fact that magnetically hard materials, such as ferrite, will swing remanent magnetism polarity from one state to the other with the passage of a quite widely tolerated current through a wire passed through the core — see Fig.13a. To make a practical core store it is necessary that any chosen core can be switched on demand. If a second wire is passed through the loop this can be used to prevent or enhance the magnetic switching action by the passage of the current.

A core store comprises a plane of ferrites arranged in a grid as shown in Fig. 13b. Two half-current units appearing in the same direction in a core will switch that core but no other. Thus two lines will select a unique core in the plane as the place to store or readout one bit.

To read out the values it is necessary to interrogate the selected core using input signals in the write wires that will, if switching takes place, induce currents in an additional readout wire. As this process can destroy the data on the core a test means may be provided to rewrite it again ready for reuse. Figure 13c shows a stacked core-plane. Ferrite cores are typically 0.1 mm overall. Planes are either stacked one on the other or mounted flat on a printed circuit board to provide a memory unit. The capacity of core storage varies from thousands to millions of bits. Core-store is more usually quoted in word capacity, words being of 32-60 bit length. The terminology is to refer to capacity as, for example, 32 k of 16 bit words. (This is often incorrectly written as 32 K — the lower case k should always be used as this is the *only* correct abbreviation for '1000'). Core storage can be cycled in 100 ns (typically) with some systems taking only 10 ns. The disadvantages of core are the relatively high cost resulting from the labour intensive production method and the comparatively large space needed.

**Delay Lines** — Another reasonably fast storage system makes use of the delay-line concept. It is the property of materials, such as mercury, to pass only waves of acoustic energy at a given rate

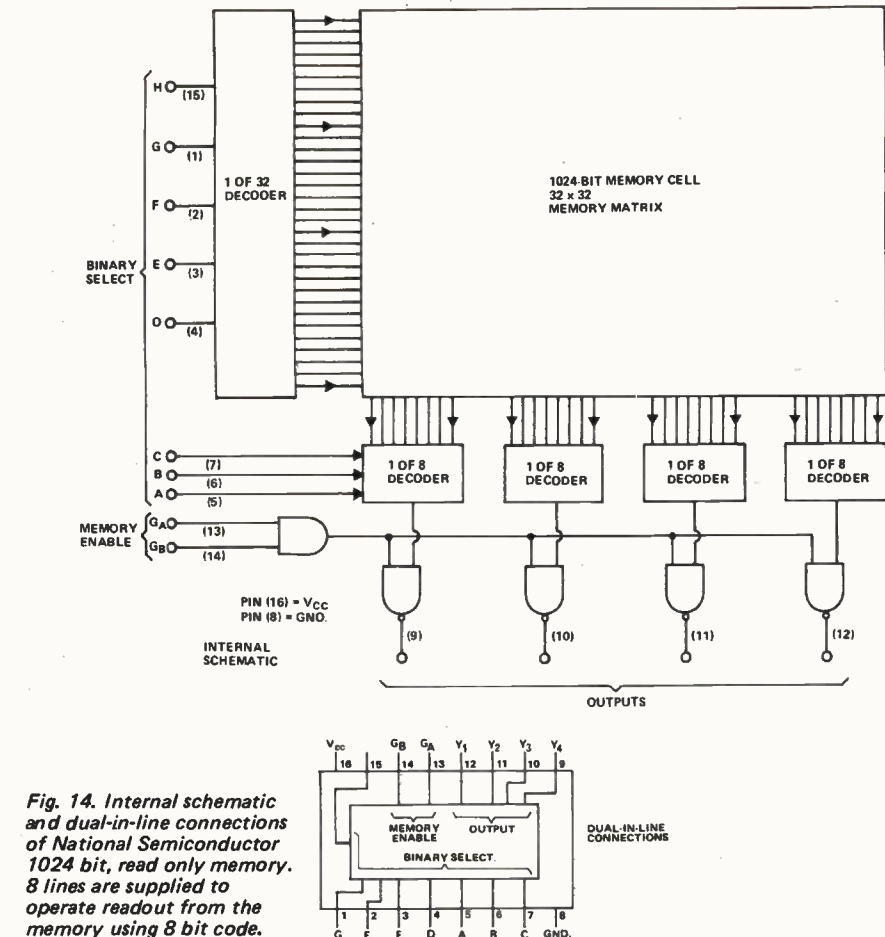


Fig. 14. Internal schematic and dual-in-line connections of National Semiconductor 1024 bit, read only memory. 8 lines are supplied to operate readout from the memory using 8 bit code.

of propagation. Early computers used mercury delay lines in which the acoustic equivalent of a binary word was sent down a tube of mercury to emerge at a later time at the other end. Whilst in transit the word was in storage. The method (if used at all in a computer today) would now be implemented using solid wires or clocked-on registers. It has the severe shortcoming of low storage capacity. **Solid-state** — Although core storage still forms part of many computer installations the current trend is clearly toward the use of a solid-state circuitry which stores bits in register style flip-flop systems. Read only memories (ROM), content addressable memories (CAM), random access memories (RAM), and Programmable ROM devices (PROM) are available as IC chips with typical arrays downward from 512 eight bit words — that is 4096 bits on a single IC chip. Figure 14 shows just one of a huge range of alternatives — 1024-bit read-only memory. Memories such as this exhibit a typical delay from address to output of 36 ns. Chips such as these are also available ready mounted as memory cards with as much as 65 536, 16-bit word capacity.

**Peripheral Memory** — The storage media listed above gives high-speed rapid

access but all are expensive. Many others and cheaper forms of storage can be used if short access time requirements are relaxed.

**Magnetic Tape** — This is basically the same as reel-to-reel domestic tape recording, magnetic tape storage used in computing however records digital rather than analogue data on the magnetic coating of the tape. Reels are generally 10.5 inch in diameter with multiple track use. They are run at much greater speeds than domestic units. They can store around 30 bits per millimetre and maybe run as fast as 25 metres/second. Speeds used are not standardised to any degree. Each track on the tape can only be accessed serially: to obtain a specific data word may involve the whole tape being run through with subsequently long access time. Figure 15 shows a typical reel-to-reel unit.

**Magnetic Disks** — These are thin disks coated with magnetic recording material. Their advantage is that they can be accessed at any point on the surface by moving the read in read out head to the appropriate part of the disk, as the disk rotates, (at speeds of 3000 r.p.m.). In an alternative procedure the reading is done by a fixed head for each



Fig. 15. The Hewlett-Packard 7970 magnetic tape unit designed as a peripheral to EDP systems.

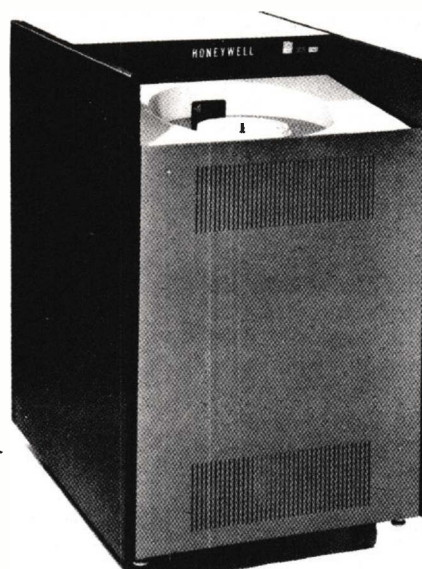


Fig. 16. Honeywell model 4720 moving-head disk storage device.

track. Each track may store 36 000 bits. The moving head disk storage unit shown in Fig.16 can store up to 7.5 million words.

Even greater storage is obtained by permanently stacking as many as 72 disks on top of each other on a common drive spindle. Each surface has its own head giving access to any part of any surface. Such a unit could store 600 million words. Access time is, however, limited by mechanical response times — typically 100-300 ms. Small interchangeable disk stacks are also

used. These are known as disk packs. Floppy disks are a variation of the disk memory.

**Magnetic Drums** — Where better access times than disks are needed, but not at the cost of magnetic core, the magnetic drum may be suitable. A large drum (0.3-0.6 m in diameter) coated with magnetic material rotates continuously at high speed. Reading heads are stacked up the drum. Access time with these is as low as 5 ms. Storage is upward of 2000 million characters.

Other magnetic arrangements include

short strips of tape that are individually selected to be drawn through a reading head, and magnetic cards which are held in magazines ready for automatic sorting in a special console. Card systems are not as slow as might be thought — any one of, say, 500 million characters can be accessed in 100 ms by a suitable design arrangement.

## MICROPROCESSORS

We saw in the previous part that computers are based upon the availability of a CPU, stores, input/output units and other peripherals. Integrated circuit manufacturing methods become economical only when very large volume sales result and it was to the computing systems market that the IC makers looked around 1970. The main problem, however, was the need to devise a basic general-purpose integrated-circuit that would satisfy a large enough group of users.

At first the trend was to manufacture special-purpose computing systems that were hardwired (connections made permanently) to cause the system to perform a stated computing function — such as a pocket calculator for commercial or scientific computation.

The trend then moved toward another philosophy — the microprocessor. These single card integrated-circuit systems (one is illustrated in Fig.17) possess the ability to be programmed to perform the task needed by the customer. Although the overall system is usually more complex than hardwired specials, the much greater increase in demand has reduced the price to quite unbelievable levels — a few hundred dollars buys a complete basic micro-processor system

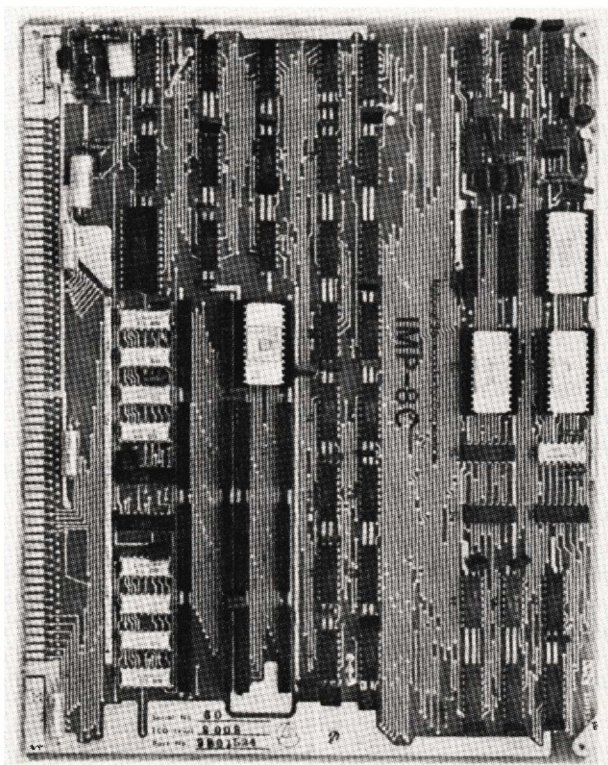


Fig. 17. This National Semiconductor IMP-8C general purpose processor uses MOS/LSI devices.



ABA Add Accumulators	INS Increment Stack Pointer
ADC Add with Carry	INX Increment Index Register
ADD Add	JMP Jump
AND Logical And	JSR Jump to Subroutine
ASL Arithmetic Shift Left	LDA Load Accumulator
ASR Arithmetic Shift Right	LDS Load Stack Pointer
BCC Branch if Carry Clear	LDX Load Index Register
BCS Branch if Carry Set	LSR Logical Shift Right
BEQ Branch if Equal to Zero	NEG Negate
BGE Branch if Greater or Equal Zero	NOP No Operation
BGT Branch if Greater than Zero	ORA Inclusive OR Accumulator
BHI Branch if Higher	PSH Push Data
BIT Bit Test	PUL Pull Data
BLE Branch if Less or Equal	ROL Rotate Left
BLS Branch if Lower or Same	ROR Rotate Right
BLT Branch if Less than Zero	RTI Return from Interrupt
BMI Branch if Minus	RTS Return from Subroutine
BNE Branch if Not Equal to Zero	SBA Subtract Accumulators
BPL Branch if Plus	SBC Subtract with Carry
BRA Branch Always	SEC Set Carry
BSR Branch to Subroutine	SEI Set Interrupt Mask
BVC Branch if Overflow Clear	SEV Set Overflow
BVS Branch if Overflow Set	STA Store Accumulator
CBA Compare Accumulators	STS Store Stack Register
CLC Clear Carry	STX Store Index Register
CLI Clear Interrupt Mask	SUB Subtract
CLR Clear	SWI Software Interrupt
CLV Clear Overflow	TAB Transfer Accumulators
CMP Compare Index Register	TAP Transfer Accumulators to Condition Code Reg.
COM Complement	TBA Transfer Accumulators
CPX Compare Index Register	TPA Transfer Condition Code Reg. to Accumulator
DAA Decimal Adjust	TST Test
DEC Decrement	TSX Transfer Stack Pointer to Index Register
DES Decrement Stack Pointer	TXS Transfer Index Register to Stack Pointer
DEX Decrement Index Register	WAI Wait for Interrupt
EOR Exclusive OR	
INC Increment	

Fig. 19. This flow chart shows how the Motorola Company produces a custom-tailored ROM ready to slip into their M6800 microprocessor system.

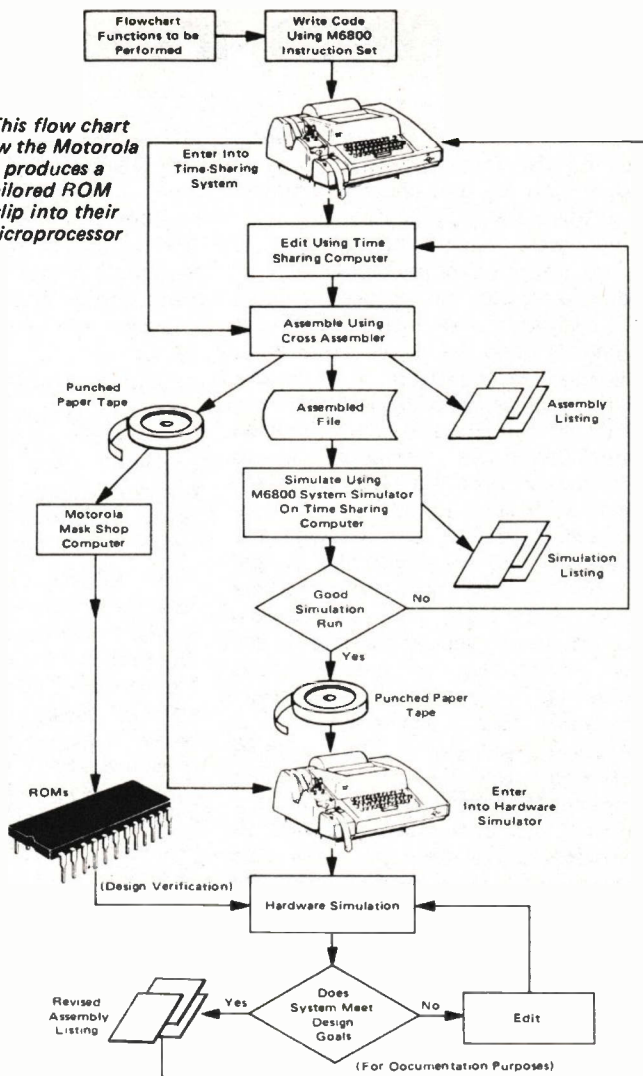


Fig. 18. Typical microprocessor instruction set.

with as much power as the minis of a decade ago. Predictions, at present, are that they could fall further to a mere \$50.

To make a programme microprocessor system, the user has to write a software programme at a basic machine-language level. Each microprocessor has its own instruction set built in — this tells the system what to do with data. It is

written in mnemonic code using code letters to denote operations — such a list is given in Fig.18.

The programme, thus written in mnemonic code, is further translated into the circuit binary form (object

code) with an assembler. The object form of code is then ready to be fed into the Random Access Memory (RAM) or Read Only Memory (ROM) of the microprocessor system. Figure 19 shows a system design and verification



**EMONA**  
enterprises

21 Judge St., Randwick,  
N.S.W. 2031. Phone: 399-9061.

**NEW — UNIQUE!**  
**EMONA E-4 ALL ELECTRONIC AM/FM STEREO DIGITAL CLOCK RADIO**



**\$79.95 (Incl. S.T.)**

(P & P: Interstate by reg. air mail or IPECAIR \$6.50. Within NSW \$3.50)

E-4 is a 24 hour dig. clock radio. It has all the features of E-2, plus: FM stereo; more output power; sliding balance, tone and volume controls; stereo headphone jack; stereo indicator; phono jack and external aerial connection.

**WARRANTY: E-4 & E-2 are fully guaranteed for 90 days.**

**EMONA E-2 ALL ELECTRONIC AM/FM DIGITAL CLOCK RADIO**



**\$45.95 (Incl. S.T.)**

(P & P: Interstate by reg. air mail or IPECAIR \$6.00. Within NSW \$3.50)

This 12 hour Digital Clock Radio is completely electronic — no moving parts — 100% solid state. You can listen to FM or AM wake up to music or alarm, or preset the radio program. It can be used as an accurate stopwatch. And there is even an indicator that blinks whenever there has been an AC power interruption.


**ELCON & PANASONIC CALCULATORS**

**Compare our prices**


Write, phone or call in. All calculators guaranteed for twelve months.

**ELCON RANGE:** • scientific-statistic SC-6010 — \$53.00 • scientific-statistic SC-60 — \$53.00 • scientific SC-44 — \$43.00 • financial computer FN-85 — \$49 • slide rule KP-460 — \$15.50 • super memory KP-450 — \$15.50 • algebraic 8513M — \$12.00.

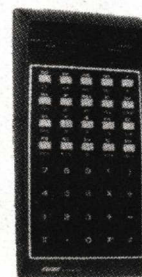**PANASONIC:** • full scientific JE — 8410U and JE — 5001U — \$29.00 each. To above add 15% S.T. if applicable (P&P inter. \$3.00, NSW \$2.00).



SC-6010

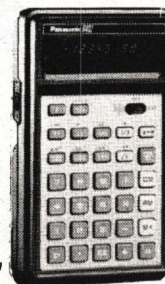

JE-8410U



# ELECTRONICS—it's easy!

procedure used to produce custom made ROMs. The peripherals are then interfaced to the unit and the complete computing system is ready to go.

The process may sound easy, but as can be imagined considerable skill is needed to set up a microprocessor. Such skill demands extensive customer training material — large handbooks, application and hardware — see Fig.20. In fact the stage has been reached where makers will soon have to face a situation where descriptive literature is as expensive or more expensive than the hardware itself. To this end they continually strive to reduce the complexity and to standardise design. We should soon be in the position where microprocessors are sold as standard tools which are each used in exactly the same way to service the enormous number of custom jobs available. Literature may degenerate to a short-form pamphlet. The actual computing part of an Everyman's Complete Microprocessor System is a very small part of the whole. Peripherals and software are now the major cost consideration. It is not feasible to describe microprocessors more fully in this series, however a short series of articles devoted specifically to microprocessors will be published in ETI soon.

**Further reading** — References listed in the previous part provide descriptions and illustrations of computer peripherals and storage methods. "Computers at Work" by J.O.E. Clark, Bantam Book, is a worthwhile discussion on how and where computer interface are used for all manner of needs.

Infotech International of Maidenhead, UK, have recently released 12 000 pages of state-of-the-art reports on computer operation and trends. They are, however, much too expensive for the reader to procure. The sets costs over \$2000 on an individual basis!

The subject of microprocessors has recently been discussed in depth in several electronics publications — Practical Electronics, Wireless World and Electronics Today International (UK edition) have each run introductory series. "Development and Trends of the Microprocessor" by J. Tobias, Control Systems (Sydney), 3, 17-31, 1975 is an extensive study and it includes a summary chart of dozens of systems offered.

"Microprocessors — an Introduction" by F. Horne, NS Application Note AN114, 1974, is a basic statement. "Microprocessors — Why They Evolved and What They Are" by M. Levi, N.S.

Imp Brief 1, 1974, is also useful as a starting point.

"New Blocks for the Computer Builder" by D. Aspinall, New Scientist, 18 September, 1975 gives a basic survey including some facts about production. An extensive self-contained introduction is "Introduction to Microprocessors", H. Tireford, Motorola Semiconductor Products, 1975.

Manufacturers of microprocessors will freely supply descriptive data to aid the user of their own style of unit.

## ELECTRONICS —it's easy!

is now produced in book form. The first two volumes in the series are on sale now. You'll find them at most newsagents — or you can buy them directly from the publishers:—

**ELECTRONICS TODAY**  
15-19 Boundary Street,  
Rushcutters Bay NSW 2011

Price is \$3.00 each volume  
(including postage).



Fig. 20. Array of support products for Motorola M6800 microprocessor systems.




# NEW! SCIENTIFIC KITS

Now you can build some of the most advanced digital electronic instruments with our new series of low-cost modular scientific kits. These kits will expand the range of your electronic applications enormously — and all at a surprisingly low cost.

The heart of the system is our 4-digit Decade Counter (Kit 012) which features a full 4-digit LED readout (you choose the size best suited to your application). Combine this with a 5-volt regulated power supply (Kit 030) and you have the basis of a wide range of sophisticated electronic instruments, including:

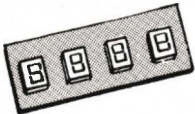- A Digital Voltmeter (DVM) . . . . . Kit 012 + Kit 030 + Kit 017
- Frequency Counter . . . . . Kit 012 + Kit 030 + Kit 016 + Kit 014 or 031
- RPM Counter . . . . . Kit 012 + Kit 030 + Kit 020 + Kit 032



## KIT 012 4-DIGIT DECADE COUNTER

Features include:

- On-chip internal oscillator for scanning speed.
- Overflow and count-extend outputs.
- Transfer, reset, count, blanking and true complement control inputs.
- Circuit board can be cascaded to 8-12-16 etc. digits.
- Kit includes all components, PCB's, and LED displays and full assembly instructions.

Kit 012a . . . . . \$23.95  
(with 0.25" displays)

Kit 012b . . . . . \$27.95  
(with 0.50" displays)

## KIT 030 5V REG. POWER SUPPLY

- Input voltage: 25V max.
- Output current: 1 amp max.
- Load regulation: 50mV.
- Output voltage: 5V
- Line regulation: .01% (Needs 8-20 volt transformer.)

Kit 030 . . . . . \$ 7.95  
(contains all parts except transformer)

## KIT 017 DIGITAL VOLTMETER

1.999V as basic, with polarity indication. 1 M ohm input impedance and accuracy to 1% if properly adjusted.

Kit 017 . . . . . \$15.95



## KIT 016 FREQUENCY COUNTER

Features FET input front end with trigger circuit for measuring complex waveforms. Measures from 0.1 Hz to 10 MHz when used with Kit 031. Measures from 0.1 Hz to 20 MHz when used with Kit 014.

Kit 016 . . . . . \$16.50

## KIT 020 RPM COUNTER

RPM Counter. Counts from 1 to 100,000 RPM.

Kit 020 . . . . . \$ 8.95

## KIT 014 1MHZ CRYSTAL TIME BASE

1 MHz crystal chain time base divider. Output: 1 MHz, 100 KHz, 1 KHz, 100 Hz, 10 Hz, 1 Hz, 0.1 Hz. Accuracy better than .005%.

Kit 014 . . . . . \$14.95

## KIT 031 TIME BASE

Uses power line (mains) frequency as reference. Output: 10 Hz, 1 Hz and 0.1 Hz. Accuracy 0.1%.

Kit 031 . . . . . \$ 7.95

\*\*\*\*\*

50 Hz chain time base. Output: 0.6 sec., 6 sec., 60 sec.

Kit 032 . . . . . \$ 8.95

## MORE TO COME...

Watch this space in future issues for additional kits, including Multimeter, Timer, Capacitance Meter, Thermometer and many more. With our kits and your imagination, you'll find dozens of new and exciting applications.

# AT LAST! 4 & 6 DIGIT PC BOARDS

- PC Board for 4 digit display MAN series or DL707 \$1.75
- PC Board for 6 digit display MAN series or DL707 \$2.25
- PC Board for 4 digit display FND503 \$2.00
- PC Board for 6 digit display FND503 \$3.00
- PC Board for 4 digit display DL747 \$2.50
- PC Board for 6 digit display DL747 \$3.00
- PC Board for 4 digit display DL727 \$2.25
- PC Board for 6 digit display DL727 \$3.00
- PC Board for 4 digit display FND70 \$1.75

All PC display Boards are multiplexed for adding additional digits.



# THE KING

INTRODUCING:

## FATIMA FOUR DIGIT TEMPERATURE KIT

FATIMA, the first in a series of time sharing kits to interface with THE KING.



FATIMA - FEATURES: **\$19.95**

- 1) 4-digit temperature display
- 2) Fahrenheit or Centigrade
- 3) Temperature 10 sec. display; time 20 sec. display
- 4) Complete C-Mos application
- 5) Kit uses 7002 4-digit counter

Kit includes all components, PC Board and instructions for interfacing with THE KING 6 digit alarm clock.

Watch next issue for yet another addition!

THE KING - FEATURES:

- 1) 6 digit, 12 hr. 60 cycle or 24 hr. 50 cycle alarm clock
- 2) Time sharing capability for display of additional information.
- 3) Built-in alarm generator and automatic output for intensity control of LEDs.
- 4) Single 12v. supply and a minimum of interface components.
- 5) AM-PM and automatic power failure indications.
- 6) 10 minute snooze
- 7) Complete data and construction manual enclosed.

THE KING **\$23.50**

- Kit No. 70250-1R (Red readouts)
- Kit No. 70250-1G (Green readouts)
- Kit No. 70250-1Y (Yellow readouts)
- Kit No. 70250-2R (DL727 readouts) ... \$27.50
- Kit No. 70250-3R (DL747 readouts) ... \$29.50



Kits contain all components, PCB's, switches, alarm speaker and instructions. (Does not include 12-15 volt transformer and case).

## DISPLAY SPECIAL



**\$1.30**

Fully multiplexed, common cathode. Goldplated. Ideal for mini 6 digit clock.




**DL747**  
Jumbo .6 in. high, and only 20mA per segment.  
\$2.75



**DL787**  
One of our best readouts .5 in. high, 20 mA per segment. Common anode.  
\$3.75



**DL707**  
Red, .30 in. high 15 mA per segment. Common anode \$1.25

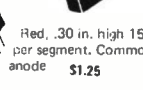

**DL33**  
If you like an array of displays, we have it. 10mA per segment. Common Cathode. \$1.45



**HP7730**  
.33 in. high, red very bright readout. 25mA per segment. Common anode. \$1.20



**MAN'S GREEN 1.50**  
**MAN'S RED 1.25**  
**MAN'S YELLOW 1.50**

Why not make a clock in 3 diff. colors. .27 in. high. Common anode.



**FND70**  
.25 in. high bright red readout. Common Cathode type by Fairchild .95



**FND503**  
New .5 in. display by Fairchild. Common Cathode. \$1.60 5 for \$7.50

**LED's**  
Mini red .12  
Jumbo red .15  
Jumbo green .20  
Jumbo yellow .25

## LSI INTEGRATION... (CHIPS W/SPECS.)

- MM5314 - 6 digit digital clock 24 pin dip w/spec. \$ 3.75
- MM5316 - 4-6 digit alarm clock 40 pin dip w/spec. \$ 4.25
- 7002 - 4 digit counter/latch decoder; 7 segment and BCD outputs. 28 pin dip w/spec. \$12.50
- 7005 - 4 digit counter/latch decoder; 7 segment output only. 24 pin dip w/spec. \$ 9.50
- 7007 - 4 digit counter/latch decoder with BCD output only. 16 pin dip w/spec. \$ 7.00
- 70250 - 4-6 digit alarm clock 28 pin dip w/spec. \$ 5.50
- 7038 - 4 digit non-multiplexed radio alarm clock featuring direct drive display output 40 pin dip w/spec. \$ 7.95
- PC Board for 70250 \$ 4.25
- PC Board for 7038 \$ 3.75

Duty may be payable on products imported.

## ORDERING INFO.

ALL PRICES ARE LISTED IN AUSTRALIAN DOLLARS. REMITTANCE BY BANK CHEQUE OR INTERNATIONAL MONEY ORDER. (RECEIPT MUST BE INCLUDED WITH ORDER IF THE LATTER IS USED). MINIMUM ORDER \$A5.00. UNLESS OTHERWISE INDICATED, PRICES INCLUDE AIR MAIL POSTAGE & PACKING.

**sabtronics**  
INTERNATIONAL

P.O. Box 64683, Dallas, Texas 75206, U.S.A.

**\* SATISFACTION GUARANTEED ON ALL ITEMS**



# "BUILD IT YOURSELF" THE PLAYMASTER 'TWIN 25' AMPLIFIER KIT

You have seen the beautiful Front Panels on the \$500 imported amplifiers - the metal used for these panels is only available overseas. Now Dick Smith has paid to have made overseas the same quality panel for the Twin 25 amplifier. Only Dick has this one! He specially imports this EXCLUSIVE Bronzed Anodized Front Panel for use with the amazing Twin 25 amplifier. Normally costing \$3.50 extra - NOW INCLUDED FREE!

## \$89.50

**EXCLUSIVE**  
Power Transistor Sockets  
At NO Extra Charge!

**EXCLUSIVE**  
LEVEL  
GRAVATIONS  
ON TREBLE &  
BASS CONTROLS

**EXCLUSIVE**  
Simplified  
complete  
instruction  
manual &  
assembly  
instructions

"It is about half the price of an imported amplifier with the same power output." "The overall performance of the new Playmaster is equal to that of many amplifiers costing up to three & four times the price." Says Leo Simpson in the *Electronics Australia* for April 1976.

**EXCLUSIVE**  
Special 'Professional' Knobs to match the fully imported Front Panel.

**SPECIAL**  
Silk Screened component overlay on the PC board for easy identification and assembly.  
Single Board Construction.

The Twin Twenty-five is the latest and the best in a long line of very popular Hi Fi amplifier kits. You really have to hear this amp. To believe that such quality is possible for such a low price. Even beginners can tackle this project! Dick has even arranged a special service offer for you. If the amp. wont go - check the power transistors with a multimeter. If they are O.K. return the completed circuit board together with S8 and we will service, replace any faulty parts and return to you.

**SPEAKER PROTECTOR KIT FOR THE TWIN 25 PLAYMASTER AMPLIFIER**  
Extremely simple to fit to your Twin 25 amplifier. Cat. K-3425 ... \$10.75

## IT LOOKS SO GOOD YOUR FRIENDS WON'T BELIEVE YOU BUILT IT!

### SPECIFICATIONS

Power Output: 25W/channel into 8ohm with one channel driven.  
Frequency Response: ± 1dB from 25 Hz to 20 kHz with tone controls level.  
Compensation: RIAA to within ± 1dB.  
Sensitivity: Phono 2mV into 56k for 25W output. Other inputs 150mV into 36k minimum.  
Overload: On phono 120mV @ 10mV and 25W. 70dB (other inputs).  
Crosstalk: Better than -45dB over 100 - 10kHz.  
Distortion: Less than 0.05% at normal listening levels.  
Bass / Treble Controls: ± 13dB nom. at 50 Hz & 10kHz.  
Stability: Unconditional.  
Cat. K-3410... .. \$89.50  
PACKING and POSTAGE... .. \$3.50




## BUILD YOUR OWN DIGITAL CLOCK

Dick has pioneered the low cost Digital Clock in Australia and this unit is the latest and best kit based on his experience of selling over 2,500 kits. This kit has a much simplified construction and even the beginner can successfully put this one together. Advanced constructors should be telling the time in less than an hour. Just look at these features:

- Well spaced components on silk-screened and fully tinned board simplify construction.
- Full hours, minutes and seconds display using big (10mm) bright orange gas discharge display.
- Panel type display is pre-wired; just plug into socket on PC Board.
- Time is accurately derived from 50 Hz mains frequency 12/24 hour operation.
- Circuit uses MM5314 IC, 13 transistors and 5 diodes.

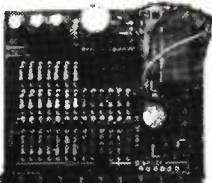Cat. K-3364... .. \$24.90  
or Complete with Plastic Case  
Cat. K-3368... .. \$29.90



6 DIGITS  
ONLY  
**\$24.90**

**NEW**  
SEE E.A.  
MAY 1976

## REVERBERATION UNIT KIT

Fantastic for Electronic Organs, Amplifiers, P.A. Systems, Car Stereo Systems etc. Complete kit includes all components and Reverb Spring Unit.

## \$14.75

Cat. K-3424 ... .. \$14.75

# DICK SMITH ELECTRONICS GROUP

Head Office tel:439 5311 telex:AA20036 cables:DIKSMIT Sydney  
Mail Orders P.O. Box 747, Crows Nest, 2065, N.S.W.


N.S.W. Branches  
CITY 125 York St  
tel:291126

GORE HILL  
162 Pacific Hwy  
tel:439 5311

BANKSTOWN  
361 Hume Hwy  
tel:709 6600

Shop hours:  
Mon-Fri 9-5:30 Sat 9-12
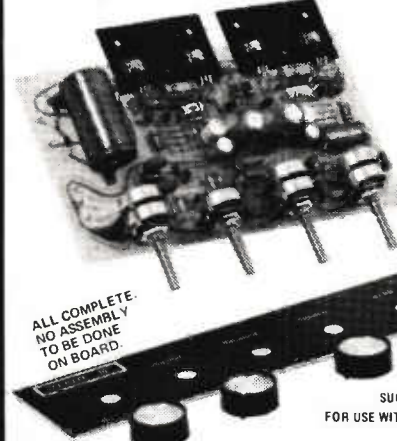
## PROJECT 30 FANTASTIC DO-IT-YOURSELF BUDGET REPLACES THE FAMOUS 'PROJECT 250' (OVER 2000 SOLD) HI FI SYSTEM



### FEATURES

- 14 watts R.M.S. per channel
- Full frequency response
- Low distortion
- 12 transistors, 6 diodes
- No messy wiring, Only 8 connections to be made
- Suits crystal or ceramic pickups
- Can be used with stereo tape decks or tuners
- Complete with knobs, anodised front panel and heatsinks
- Controls: Volume, Bass, Treble, Balance
- Dimensions: 205mm x 132mm inc. sinks
- Requires external transformer approx. 20, 27 V. I.A. Our M-6672 is ideal.
- Cat. F-4120 ... .. \$29.50
- Cat. M-6672 Transformer to suit ... \$6.50

ALL COMPLETE  
NO ASSEMBLY  
TO BE DONE  
ON BOARD

## STEREO AMP \$29.50

SUGGESTED ACCESSORIES  
FOR USE WITH THE PROJECT 30 AMPLIFIER

Famous Garrard Record Changer Model CC10, complete with ceramic stereo cartridge and cueing device. We sold previously at \$32.50.  
Cat. A-3068 200 Only at a low \$19.75  
10 Watt Ducted Horn System with 6" Base and Mid-range and 2" Tweeter. Now only \$35. pair.  
Cat. A-2462 ... .. \$17.50 ea.

Base to suit Garrard Record Changer (will take amplifier too) Cat. A-3430 ... .. \$9.50  
Acrylic Cover to suit above base.  
Cat. A-3420 ... .. \$11.00  
NOTE: The above 28 watt system costing just over \$100 complete would be hard to purchase built up for under \$200, so why not build one and save yourself a mint.

## NOVICE TRANSVERTER KIT



## \$99.50

DICK SMITH "NOVICE TRANSVERTER" SEE E.A. April '76  
10 metres to 80 metres at up to 30W p.e.p.

\* Designed by Australia's top R.F. Engineer, exclusively for us. **\$99.50**

- \* The cheapest and best way for a novice to get going on 80 metres.
- \* Put in any signal (AM/FM/SSB) on the 27Mhz novice band and it is instantly "Transformed" down to 80 metres.
- \* Inbuilt receiver converter "Transverts" 80 meter signals up to 10 meter novice bands.
- \* Max power 10 watts and 30 watts p.e.p. SSB from as little as 100mw input (and suitable 100mw-3 Watts)
- \* Easy to build (takes about 3 hours) fibreglass boards, fully reverse voltage protection
- \* Input and output 50ohm
- \* 13.8volt DC (max) operation - ideal for Mobile rigs

Cat. K3134 ... Very Special Offer \$99.50

## 45 WATT 2 METER AMPLIFIER KIT

## \$27.50

YOU CAN BUILD THIS UNIT IN UNDER AN HOUR!  
A fantastic 2M r.f. amplifier kit of the simplest design. Uses the 2N6084 45W transistor. Requires 8-12W drive to give 35-45W output from 13.8V supply (to suit you mobiles). Fully solid state switching, double sided fibreglass PCB. Everything supplied including explicit instructions - there's even provision on the board to wire in a VSWR meter (not supplied).  
Cat. K-3132... .. \$27.50  
Eddystone Box to suit:  
Cat. H-2210... .. \$4.00

## TV GAME KIT

WAS \$89.50  
**NOW \$39.50**



SEE E.A. MAY '76  
**SAVE \$50**

T.V. games open up a whole new vista of fun and this project must be the best of any yet! On the screen you get a net and top & bottom to the court. You can select ball or hole-in-the-wall. There are separate controls for each player plus an adjustable ball speed control. The ball bounces off the top and bottom edges. A special "interaction" control introduces a wobble on both sides for extra fun. We reckon there are 15 different games you can make up by adjusting the controls, some for 2 players and some you play against yourself. Circuit uses 13 IC's, 5 transistors and is battery powered with a separate modulator board and two control boxes. Highly recommended for the more advanced constructor.

Cat. K-3415 Build Yourself and SAVE ... .. \$39.50

## BOOKS

World Radio TV Handbook 1976. Complete directory of International Radio and Television. Over 500 pages. For every enthusiast.  
Cat. B-2080... .. \$10.90

RADIO AMATEURS HANDBOOK. FAMOUS ARRL PUBLICATION. This is the latest edition of this widely used book. 25 chapters and over 800 pages cover everything. Textbook, Data book and Construction Manual.  
Cat. B-2218... .. \$8.90

TTL COOK BOOK. A complete guide to the understanding and use of Transistor Transistor Logic (TTL) integrated circuits - the basics of TTL are given, what it is, how to power it and so on. Also contains a catalogue of TTL devices, giving physical and electrical specs on all devices mentioned in the book.  
Cat. B-1246 By D. Lancaster - 328 pages: \$10.75

### POSTAL CHARGES

Order Value	Charge
\$5 - \$9.99	\$1.00
\$10 - \$14.99	\$1.50
\$15 - \$19.99	\$2.00
\$20 - \$24.99	\$2.50
\$25 - \$29.99	\$3.00
\$30 or more	\$3.50

By Courier Freight: Minimum packing and handling charge \$1.00 on despatch freight on and you pay when you receive the goods.  
NEW MINIMUM MAIL ORDER AMOUNT \$5



**MIDLAND INTERNATIONAL**

**23 CHANNEL SSB TRANSCEIVER**

**\$39.75**

**\$239.50**



**HAND HELD 2 CHANNEL 1 WATT TRANSCEIVER**

**THIS UNIT IS DESIGNED FOR THE AMATEUR OR NOVICE WHO WANTS THE ULTIMATE IN PERFORMANCE AND RANGE. A REAL BEAUTY!**

**Specifications:**  
 Circuitry: 25 transistors, 2 FETs, 2 IC's 56 diodes  
 Channels: 23 channels—All crystals supplied  
 Modes of operation: AM, Lower and upper Sideband.  
 Controls: On/off/volume, variable squelch, mode selector  
 SSB clarifier/AM delta tune, PA/CB channel selector and  
 noise blanker switch.  
 Jacks & Connections: Mic., antenna, external speaker,  
 P.A. speaker and DC power.  
 Power source: 9 volt to 15 volt DC, 13.8 volt DC(E.I.A.)  
 Receiver—Receiving System: Dual conversion super-  
 heterodyne with tuned RF, A.V.C. and AGC circuits.  
 Sensitivity: AM—0.5uV for 10 dB (S+N)/N. SSB—0.25  
 for 10 dB (S+N)/N.  
 Selectivity: AM—5.0 kHz @ -6 dB. SSM—2.1 kHz @  
 -5 dB.  
 Clarifier: SSB clarifier #600 Hz.  
 Audio Output: 5 watts maximum.  
 SSB Transmitter—RF Input Power: 15 watts P.E.P.  
 SSB Generation: Balanced modulator, crystal lattice  
 filter.  
 Frequency Response: 300 to 2700 Hz @ 6 dB  
 Carrier Suppression: USB—60 dB LSB—64 dB.  
 AM Transmitter—Modulation: High level.  
 RF Input Power: 5 watts  
 Harmonic Suppression: 50 dB down.  
 Cat. D-1100. . . . . \$39.75

**\*\*\* FULLY PMG APPROVED \*\*\***

**FAMOUS MIDLAND 1 WATT TRANSCEIVER**

This is a rugged professional unit which is ideal for the boating enthusiast and sportsman. Sensitive superheterodyne receiver has tuned RF and 3 IF stages for increased reception power and sensitivity. AGC circuit reduces fading and distortion. Variable squelch cuts static and noise on standby. Has a range of up to 10 miles on land (depending on terrain) and 50 miles over water. Supplied with carrying strap, earphone and one set of crystals installed on 27.24 MHz or 27.38 MHz (please state preference). Has 11 transistors, 1 thermistor, 1 squelch transistor and 1 diode. Effectively converted into a high level push-pull Class B system. Has 2 1/2" PM speaker and 56" telescoping antenna. Powered by 8 penlight cells (has AC adaptor & battery charger connections) Has a sensitivity of 1.4 uV for 10 dB (S+N)/N.  
 Cat. D-1100. . . . . \$39.75

**MULTI-7 A MUST FOR ALL MOBILES**



**MULTI-7 VHF 2 METRE 23 CHANNEL TRANSCEIVER**

Compare this unit—no others have all the features.  
 • Exclusive receiver fine tuning for "off frequency" stations.  
 • Inbuilt centre zero discriminator meter for frequency adjustment  
 • Exclusive "AFB" (audio feed-back) squelch circuit opens on the weakest of signals.  
 • Helical resonator and crystal filter  
 • Speaker can be changed to top or bottom of cabinet  
 • Special "instantaneous" channel button allows instant QSY to nominated channel.  
 Frequency Range: 146.0 to 148.0 MHz. 23 Channel FM Transceiver  
 All solid state construction. RF power output 10W or 1W with switch. Receiver Sensitivity: 1.0uV @ 30 dB S/N Power Requirements: 13.5V DC @ 2.3A max. Size: 134Wx58Hx216D mm Weight: 1.8 kg. Comes with microphone, mobile mount, manual and DC leads.  
 Supplied complete with one set of crystals on channel 40 (146.00 MHz)  
 Cat. D-3007 . . . . . \$189.00

**ONLY \$189.00**

**SPECIAL**  
 Additional crystals available at \$6.00 per channel if purchased with the Multi 7 (Yes—this will give you 6 channels for only \$219.00—a bargain!). Crystals normally available for the Multi 7 include repeater and anti repeater 1, 2, 3, 4, 5, 6 and simplex channels 40, 50 and 52.

**SPECIAL KIT PARTS**

- RE-4 Reverb Spring. (See details below. Used in Reverberation Unit - Details opposite page) Cat. X-1035 \$9.75
- UB-5 Zipzy Box. (Used in TV Game Kit - Details opposite page) Cat. H-2755 \$1.10
- 76/VG5 Printed circuit board. (Used in TV Game Kit - Details opposite page) Cat. H-8308 \$5.50
- 76/M5 Printed circuit board. (Used in TV Game Kit - Details opposite page) Cat. H-8310 \$1.50
- 74C00 CMOS Integrated circuit. (Used in TV Game Kit - Details opposite page) Cat. Z-5410 \$0.50
- 74C02 CMOS Integrated circuit. (Used in TV Game Kit - Details opposite page) Cat. Z-5412 \$0.50
- 76/R4 Printed circuit board. (Used in Reverberation Unit - Details opposite page) Cat. H-8314 \$2.00
- 76/SA4 Printed circuit board. (Used in Twin 25 Amplifier Kit - See opposite) Cat. H-8302 \$3.95

**RESISTOR PACK**

**SAVE OVER 300 RESISTORS**

**\$6.00**



LESS THAN 2c EA. **\$5.90**  
 ALL USEFULL VALUES  
 WHAT A SENSATION! Now we have improved our already famous Computer Resistor Pack. 300 resistors, 60 values from 10 ohm to 1 Meg. No useless values - for example you get 2 x 560K and 20 x 1K. All resistors are 1/4 watt 5% tolerance carbon film high stability type.  
 Cat. R-7010. . . . . \$5.90

**GREENCAP PACK**



**\$5.75**  
 Tremendous Value! Get the values you really use and not a lot of weird rubbish. All brand new top quality greencaps. 125 V. 10%. Normal price over \$10.  
 Cat. R-7040 Save over \$4.00. . . . . \$5.75

**ELECTROLYTIC CAP PACK**



**\$5.00**  
 50 TOP QUALITY CAPACITORS! Values based on computer use listings—no useless values. Save over 70% on normal one-off purchasing. All single ended types.  
 Cat. R-7030. . . . . \$5.00

**12V NI-CAD Rechargeable PACK**



Replace all those penlight cells with a rechargeable Ni cad pack. This pack powers transceivers with 100 mW to 5 watt input as well as other portable equipment using 12 V DC power. Replaces 8 penlight cells.  
 Cat. S-3310. . . . . \$18.75

**Professional Pliers**

FOR THE BEST JOB USE THE BEST TOOLS!  
**CUTTER**—For all your precision work these cutters are a must. Ideal for P.C. board, transistor and I.C. work. Spring loaded insulated handle with box joint construction and fine, sharp, precise cutting edge.  
 Cat. T-3310. . . . . \$6.75

This professionally finished plier makes precision work simple. Beautifully finished, box joint, flat smooth jaws, positive non-destructive grip makes it ideal for use on delicate instruments.  
 Cat. T-3320. . . . . \$6.50

**Heatsink Clip Set**




Protect all those expensive components with these inexpensive Heatsink Pliers. Spring loaded and made from high thermal conductivity aluminium.  
 Cat. T-2620 75mm long Two per set. . . \$1.20

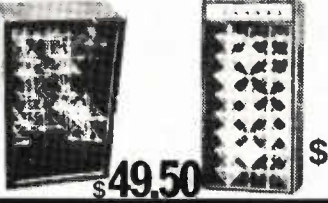**MINIATURE SOLID STATE BUZZER**



No moving contacts  
 No arcing or R.F. noise  
 Ideal for automotive monitoring and warning systems, test apparatus, timers, alarms etc. 4-15V DC @ 15mA Frequency 450 Hz. Output level 100dB min. at 3 feet. 32mm x 16mm x 16.5mm.  
 Cat. L-7009 . . . . . \$1.75




**COLOUR YOUR MUSIC**

See your sound in vibrant colours, these units can be used with almost any sound source equipped with external speakers. Simply connect to speaker terminals. The sound will not be affected as the music only switches the lights—it does not power them. Has 30 brilliant diamond pattern flashing lights with master sensitivity control. Colours are Red, Yellow, Green, Blue and Violet.  
 Cat. A-4950. . . . . \$49.50  
 Professional version of the above unit. Has 32 diamond flashing lights and 4 individual colour mixing controls.  
 Cat. A-4952. . . . . \$84.00

**3-4-5 DIGIT READOUTS**

BRAND NEW! FULLY GUARANTEED! Hewlett Packard Readouts. All readouts are end stackable so that they may be mounted next to each other and maintain the same spacing. They include a lens which gives a magnification to the display. All types give a red display. Ideal for all projects. Originally were selling at over \$20.00 each. Now from \$1.50 ea.

Full Data Sheet	5082 - 7400 - 3	3 Digit	\$1.50
Available	5082 - 7400 - 4	4 Digit	\$1.75
If Requested.	5082 - 7400 - 5	5 Digit	\$2.00

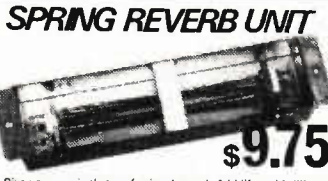

**SPRING REVERB UNIT**  
**\$9.75**  
 Give your music that professional sound. Add life and brilliance to otherwise flat sounds. The technique has been successfully used by many musicians and groups to give added impact to their performances. The natural string decay of guitars, for example, is greatly enhanced by reverb. Specifications: Input current - 350 MA. Driving coil imp. - 16 ohm. Pickup coil imp. - 10 Kohm. Frequency response - 100 to 3000 Hz. Attenuation - -30dB. Reverb. time - 25 to 30 msec. See article in E.A. May '76 for circuit details.  
 Cat. X-1035 . . . . . \$9.75

**MULTI BAND RADIO**  
**\$29.90**

- \* AM Broadcast Band 535 - 1605 KHz
- \* New FM Broadcast Band 88 - 108 MHz
- \* TV I (channels 2 to 6) 56 - 108 MHz
- \* TV2 (channels 7 to 13) 170 - 217 MHz

Covers Australian VHF Hi and Low Band. Listen to all the mobiles. Circuit has 12 transistors, 9 diodes and 2 rectifiers. 300mW output. 240V AC and 6V DC. Available in Black, Beige, Green or Mustard colours. Please state colour.  
 Cat. D-2840 . . . \$29.90

**Electronic Word Lettering Set**  
**\$4.75**

Give your project that professional look. Hundreds of words, letters, numerals and symbols. Easy to apply - just burnish with a pencil. Two sizes 3.1mm & 2.3mm high.  
 Cat. N-1800 Black 3.1mm \$4.75  
 Cat. N-1804 Black 2.3mm \$4.75  
 Cat. N-1806 White 2.3mm \$4.75

**Unique Design Breadboard**  
**\$1.50**

This versatile board has over 500 holes drilled in such a unique pattern that it will accommodate almost all types of integrated circuits and transistor packages as well as passive parts. Will take 24, 28, 36 and 40 pin DIL packages as well as 8, 14 and 16 pin packages.  
 Cat. H-5606 01" spacing x 80 x 127mm \$1.50

**DICK SMITH ELECTRONICS GROUP**

N.S.W. Branches  
 CITY 125 York St tel:29126  
 GORE HILL 162 Pacific Hwy tel:439 5311  
 BUNKSTOWN 361 Hume Hwy tel:709 6600

Head Office tel:439 5311 telex:AA20036 cables:DKSMIT Sydney  
 Mail Orders P.O. Box 747, Crows Nest, 2065, N.S.W.

Shop hours: Mon-Fri 9-5.30 Sat 9-12


**POSTAL CHARGES**

Order Value	Charge
\$5 - \$9.99	\$1.00
\$10 - \$24.99	\$1.50
\$25 - \$49.99	\$2.00
\$50 - \$99.99	\$3.00
\$100 or more	\$5.00

Minimum packing and handling charge \$1.00. We dispatch freight on order and you pay when you receive the goods.  
 NEW MINIMUM MAIL ORDER AMOUNT \$5

**Special Offer**

# LED WATCHES SOLID-STATE CLOCK RADIO

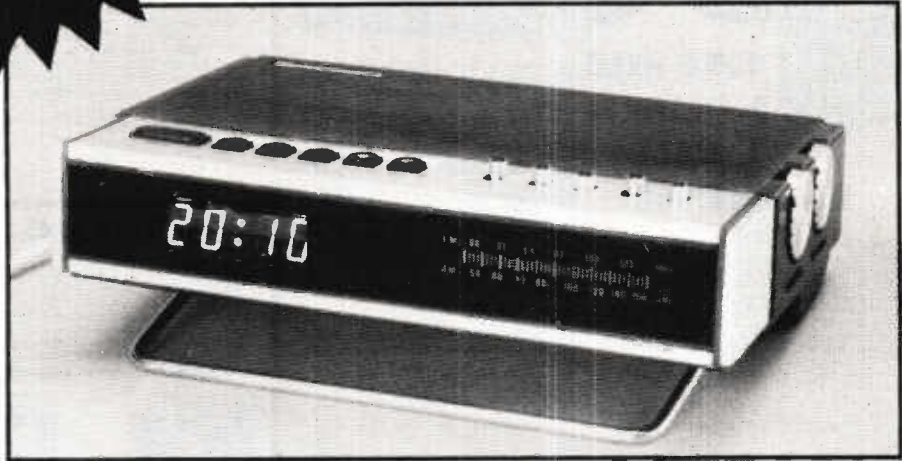

## LED WATCHES

3-function \$49.95 — 5-function \$89.95

- Basic three functions = hour, minutes, seconds
- Further functions on the dearer watch = day and date
- Both watches are shockproof, water resistant and antimagnetic
- Gold EP case and bracelet band

The two watches are warranted for a period of 12 months from original purchase date (clock — three months) under normal use and service against defective materials or workmanship.

In the event of the unit not working, it should be returned to Xenon World Imports, Box 33, Warradale, South Australia 5046, not to ETI.

The goods can only be obtained as below. Electronics Today International cannot supply directly nor can it undertake to demonstrate or discuss details of the units offered.

All units will be thoroughly inspected before despatch. The package should be carefully inspected before accepting delivery. Acceptance should be refused if the package is damaged.

Orders must be addressed exactly as per the coupon. Due to postal delays, readers should expect a delay of between three to four weeks between posting an order and obtaining delivery.

This offer closes 25th July 1976.

## SOLID-STATE CLOCK RADIO

\$55.95

- 100% solid-state — no moving parts except controls
- AM-FM radio
- 24 hour green seven-segment fluorescent display
- Wake-up alarm
- Blink indicator tells if mains power failure has caused clock to lose time
- Bright/dim switch
- Switchable minutes/seconds display converts units to accurate timer
- Guaranteed for three months

*This unit is currently being used by S.A. State schools for switching VTR recorders — simple modification is required.*

### ETI WATCH/CLOCK OFFER

Name .....

Address .....

..... P/Code

Please forward

Qty ..... 3-function LED watch at \$49.95 each

Qty ..... 5-function LED watch at \$89.95 each

Qty ..... solid-state clock radio at \$55.95 each


Add \$1.00 each item for certified mail delivery  
Please make cheques/postal notes payable to Electronics Today International

Send to:— WATCH/CLOCK OFFER,  
c/- Electronics Today International,  
15 Boundary Street, Rushcutters Bay, NSW 2011

Products described in this offer are normally available through Xenon World Imports, Box 33, Warradale, S.A. 5046.



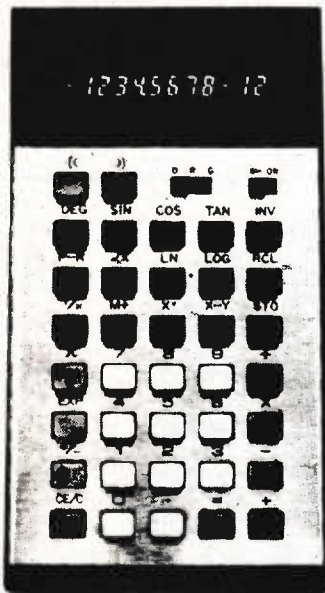**Polar ↔ Rectangular, Bracket  
Decimal Degree ↔ Degree, Minute, Second**



**Features:**

- \*37 function keys (8 with double function)
- \*Bright green display
- \*8-digit mantissa with sign and 2-digit exponent with sign
- \*Number entry in either floating point or scientific notation
- \*Scientific notation with 200 decade range ( $10^{-99}$  to  $10^{99}$ )
- \*Two levels of parenthesis
- \*One accumulating memory with overflow protection
- \*Algebraic operation
- \*Constant and repeat operations
- \*Most functions usually found in advanced calculators, including:
  - polar ↔ rectangular coordinate conversions
  - decimal degree ↔ degree, minute, second conversions
  - sin, cos, tan,  $\sin^{-1}$ ,  $\cos^{-1}$ ,  $\tan^{-1}$ ,  $10^x$ ,  $e^x$ , ln, log,  $x^y$ ,  $1/x$ ,  $\sqrt{x}$ , and  $x^2$
  - Trigonometric functions with arguments in degrees, radians or grads
- \*Full 12 months guarantee

**SALES TAX (EXEMPTIONS AND CLASSIFICATIONS) ACT**

TO : — THE COMMISSIONER OF TAXATION AND  
THE COMMONWEALTH OF AUSTRALIA

I hereby certify that the  
purchased by me from  
on (date) is for use in

(Goods Description)  
(Supplier)  
(Name of University or School) in or directly and essentially in connection with, the production of facts by means of observing, measuring, testing or otherwise experimenting with material phenomena, for the purpose of proving or illustrating natural principles or laws or in the study of pure or mixed mathematics. Exemption is accordingly claimed under item 63 (1) in the First Schedule to the Sales Tax (Exemptions and Classifications) Act

Signature of official of University or School  
Designation  
Name of University or School  
Date Signature of Student  
Address of Student

**\$34.00**  
TAX EXEMPTED

**HORNET  
SR-46**  
\$11.00 for Adaptor &  
rechargeable batteries  
plus 15% Sales Tax  
if applicable

**\$43.00**  
TAX EXEMPTED

**LOGITECH  
LC-40D**  
(including Adaptor  
& rechargeable batteries)  
plus 15% Sales Tax  
if applicable

- 1) Add 15% sales tax if applicable
- 2) Add \$2.00 for packaging & delivery

Model	Calculator only TAX EXEMPTED	With adaptor & rechargeable batteries	Guarantee Months	
SR-40	33.00	43.00	12	*Led display 10 digit mantissa and 2 digit exponent, memory
LC-10D		40.00	12	*Trig functions *Log functions *Hyperbolic functions: *Green display *Square root, & reciprocal *x to y power
LC-1233s	33.00	44.00	12	*Large green display - 8 digit mantissa and 2 digit exponent memory *Two levels of parenthesis *Trig functions: *Logarithmic functions: *Factorial functions: $x!$ $e^x$ , $a^x$ *Square root & reciprocal
LC-831s	22.00	33.00	12	*Green 8-digit display *Fully floating decimal point *One memory *Trigonometric functions: *Logarithmic functions: Power functions: $e^x$ , $x$
LC-20F	22.00	31.00	12	*Display: green, signed 8-digit floating point of signed 5-digit mantissa with signed 2-digit exponent *Scientific functions: sin, cos, tan, $\sin^{-1}$ , $\cos^{-1}$ , $\tan^{-1}$ , $e^x$ , $10^x$ , ln log, $x^y$ $1/x$ , $x$ , and $x^2$ *One independent memory *Two levels of parenthesis.
LC-21F	12.00	21.00	3	*Large green 8-digit display *Chain operation *Memory *Square root *Constant operation *Fully floating decimal point *Percentage calculation
ZENY-811	12.00	18.00 (adaptor)	3	

**CHAN MERCHANDISING CO. PTY. LTD.**  
906 CASSON AVENUE, MOUNT HUTTON, N.S.W., AUSTRALIA, 2290  
TELEPHONE: NEWCASTLE (049) 48 9676

# The hungry leader.

At Altec, we're not taking our leadership position for granted. We're always trying harder — challenging ourselves to develop studio monitor speakers that stay a step ahead of constant improvements in the contemporary recording process. And we can prove it. Here's the latest data on monitors installed in U.S. studios, as published in Billboard's 1974 International Directory of Recording Studios.

MANUFACTURER	NUMBER OF MONITORS USED IN U.S. STUDIOS
--------------	---

Altec	522
JBL	339
EV	82
KLH	39
AR	34
Tannoy	24

But we're not really satisfied — even with this impressive track record. We're still trying to better ourselves. In fact, Altec has three all-new studio monitors available right now. They're a whole new generation of speakers designed to meet the whole new range of tomorrow's dynamic recording techniques. Your studio may need them. Why not call us for full details.

Altec gives you the best of both worlds proven leadership, plus an unrelenting commitment to doing a better job. That's because we've really grown to enjoy being # 1 in studio monitor sales during the past three decades. And we intend to stay right there for at least the next three decades by always being our own biggest competitor — in research, in quality, in service and in satisfying the demanding needs of an ever-evolving industry. The domestic ALTEC recently introduced into Australia has already gained rapid response from the discerning Hi-Fi enthusiasts.



Domestic from

**\$320**

pair

**Number one.  
And have been for  
nearly 3 decades.**

Limited numbers of 604E professional monitors available at \$285 each.

**ALTEC**  
*the sound of experience.*

**KENT HI-FI**

(WHERE THE BEST EQUIPMENT COSTS LESS)

410 KENT STREET  
SYDNEY  
ph: 29-2743



# Ideas for experimenters


These pages are intended primarily as a source of ideas. As far as reasonably possible all material has been checked for feasibility, component availability etc, but the circuits have not necessarily been built and tested in our laboratory. Because of the nature of the information in this section we cannot enter into any correspondence about any of the circuits, nor can we produce constructional details. Electronics Today is always seeking material for these pages. All published material is paid for — generally at a rate of \$5 to \$7 per item.

## IR FINDER


The heart of the infra-red finder is a two-transistor oscillator whose output frequency is varied by a thermistor. IR rays falling on the thermistor alter its resistance and the output frequency.

Normally a low pitched sound will be heard. However, when the IR finder is pointed towards a heat source, the pitch increases. An ordinary flash-light was used for the housing and its reflector was used to focus the radiation onto the thermistor, thereby increasing the sensitivity of the unit.

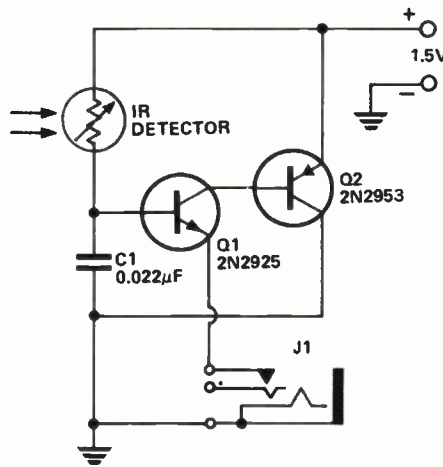The prototype IR finder responded to the heat of an ordinary candle 50 feet away. It may be used to locate miscellaneous warm objects such as water pipes and the electronics



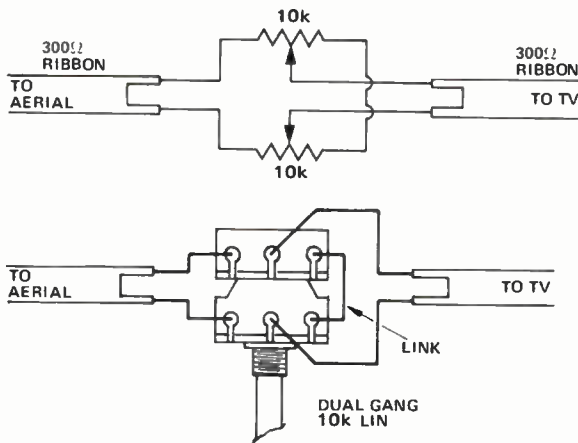handyman can use it to locate overheated components.



## TV SIGNAL ATTENUATOR

A useful circuit for anybody doing TV repairs is an aerial attenuator to check AGC and sync. It will also simulate low level signals if the repair shop has a

strong signal but the customer uses rabbit ears or lives in a poor signal area. Mismatch has never been found a problem.

## LAFAYETTE

27 MHz TWO-WAY RADIO  
FOR INDUSTRY, FARM,  
BOATS, SPORTS, ETC.



**MICRO 66** Only 1-15/16H x 5-3/16W x 6-13/16" D.  
5 WATTS  
6 CHANNELS **\$139.50** Crystals extra

The latest in the famous LAFAYETTE Micro series the MICRO 66 embodies the versatility, reliability and performance which have made LAFAYETTE famous throughout the world in 27MHz communications. With an extra sensitive receiver of better than 1µV for 10 dB S-to-N ratio, "Range Boost" modulation circuitry a built-in speaker plus push-button selected external speaker-microphone (supplied), the MICRO 66 is ideal for Boats or Base Station operation. Operates from 12V DC or 240V AC with optional Base Station Power Supply.



5 WATTS 12 CHANNELS  
**DYNA-COM 12A**  
\$139.50 (Crystals Extra)

A powerful 5-Watts input power in a hand-held transceiver! Excellent sensitivity and selectivity. Ruggedly designed for extra reliable performance. This high-power walkie-talkie operates from internal batteries (rechargeable Ni-cad batteries available) or an external 12V source.



1 WATT 3 CHANNELS  
**Model HA-310**  
\$73.50 (Incl. 27.240 MHz)

1,000's of LAFAYETTE HA-310 walkie-talkies in use in Australia, 100,000's throughout the world attest to their superior qualities. A professionally designed, studily constructed, commercial quality unit for top performance and long term reliability. Rechargeable Ni-cad batteries are available to suit.

All above transceivers are P.M.G. Type. Approved (Licence Required).

A LARGE RANGE OF ACCESSORIES IS AVAILABLE, ANTENNAS, CRYSTALS, CONNECTORS, ETC. PLEASE ENQUIRE FOR DETAILS.

## LAFAYETTE

ELECTRONICS

div. of Electron Tube Distributors P/L  
94 ST KILDA RD., ST. KILDA,  
VIC. 3182. Phone 94-6036.

Applications are invited for  
24 fulltime places\*



in a three-year film & television course  
beginning in March 1977 at

## The Film & Television School

The School's Fulltime Program is the only vocational course of its kind in Australia. It is designed to prepare creative film and television professionals

for the film and television INDUSTRIES; and  
for the production of EDUCATIONAL films and television.

All fulltime students gain practical experience in the main creative areas of BOTH FILM AND TELEVISION — including an introduction to screenwriting\* — and are encouraged to specialise in more than one.

All fulltime students have the opportunity to direct films and television programs. Some students will specialise in directing during their third year.

Applicants for the course in 1977 must nominate an initial preference for one of four first year creative workshops:

CINEMATOGRAPHY  
EDITING  
SOUND or  
PRODUCTION

\*Note that details of the School's screenwriting course will be separately advertised later this year.

There are no rigid age or educational requirements; but mature, imaginative young people educated to matriculation standard, and with experience or a demonstrable interest in film or video have an advantage.

Applicants must be domiciled in Australia.

The School is situated near Macquarie University at North Ryde in Sydney, NSW.

Students pay no fees but receive living allowances including allowances for any dependants. Assistance is available with relocation to Sydney for successful applicants from elsewhere in Australia.

Applications must be on the School's form and  
CLOSE on 9 JULY 1976.

For further information telephone: (Area code 02) 888 3066.

To: The Director, The FILM and TELEVISION SCHOOL, Box 245  
PO CHATSWOOD, N.S.W. 2067

Please send a Fulltime Program application form and course  
booklet to:


NAME .....

ADDRESS .....

.....POSTCODE.....



# Ideas for experimenters

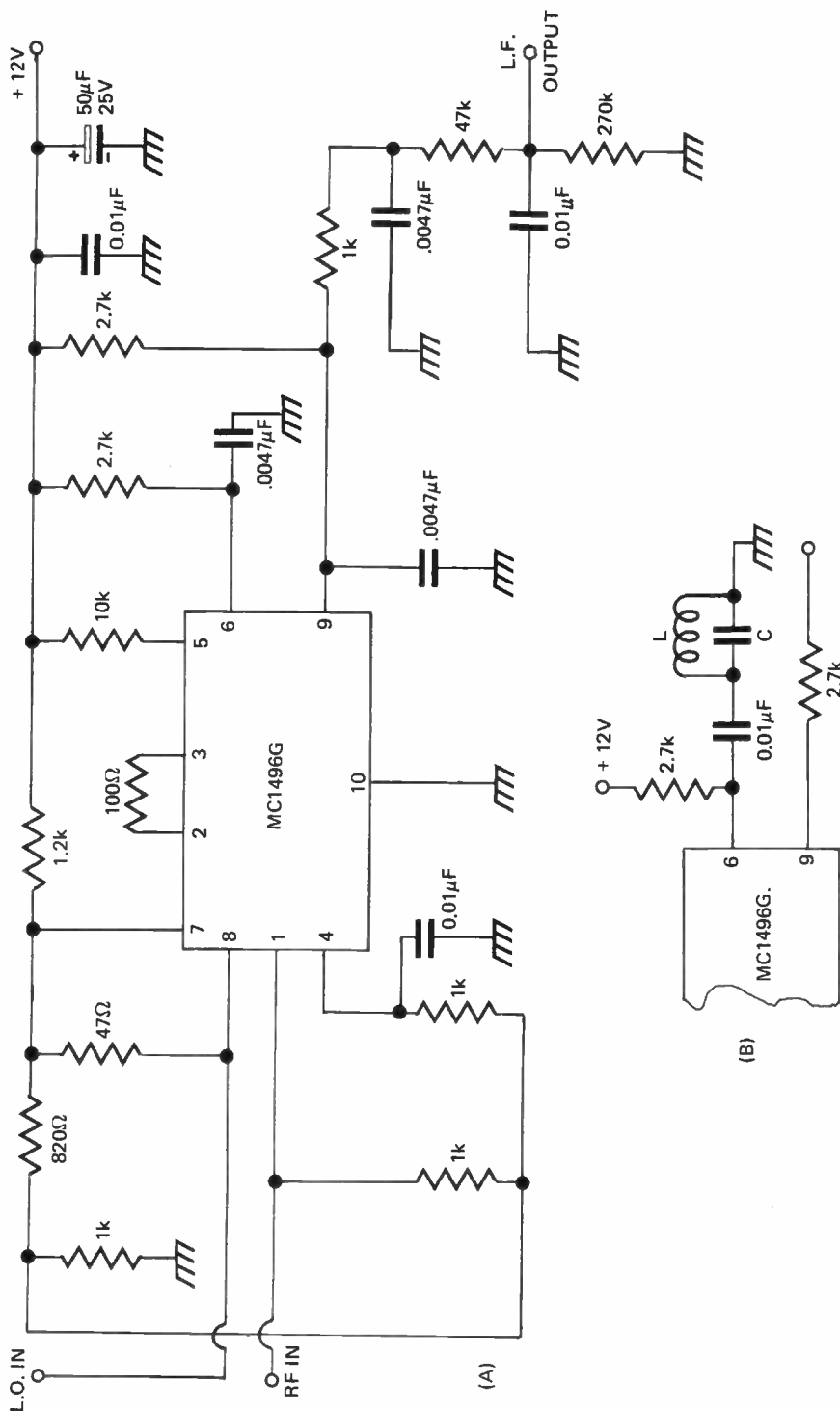

## IC BALANCED MIXER

Motorola put out a very good balanced mixer, type MC1446G, which makes an excellent RF to IF mixer and a product detector. The product detector circuit is shown in (a) above. About 3 to 5  $\mu$ V input is required at the LO input. The

input impedance is fairly low, as is the output impedance.

Only the output circuit needs to be changed (shown in (b)) to use the IC on IF frequencies.

# ELECTRONIC DISPOSALS

297 Lt. Lonsdale St., Melbourne. 3000

Phone: 663-1785

**TAPE RECORDER** Microphones Dynamic 200 ohms Switched \$3.50 P&P 50c.

**PHILLIPS G.C.065.S** Automatic Stereo Turntable complete with cartridge and stylus. Push button operation, lift and 10" platter. Brand new. **ONLY \$29.50 each.** P/P \$4.

**S.C.R. BT100A - 300R.** 300V. 4-5 amp. R.M.S. 2 amp average. 60c each. P/P 25c.

**PHILIPS** Tuning Capacitors for AM. SW and FM. \$2. each. P/P 60c.

**PHILIPS** Beehive Trimmers. 4 to 25PF. 10 for \$2. P/P 50c.

**6.5mm** Chassis Mount Switched Stereo Sockets. 40c each. P/P 25c.

**Stereo Amplifier and R.F. Board** 4 watts RMS per channel including circuit diagram. Boards are complete with all transistors, capacitors - resistors, etc. and are brand new - famous make. Only \$6 set P/P 60c.

**Stereo balance meters**, 1 1/2" x 7/8" x 1 1/4" 200ua. \$2 ea P/P 40c

**50Ω** 3 watt wire wound pots. \$1 ea. P/P 25c.

**10Ω** 3 watt wire wound pots. \$75c ea. P/P 25c

**6.8 μF** 100v polyester capacitors for speaker networks. 75c ea. P/P 20c.

**Dual 50k** push pull switch pots. (Astor/Philips) car radio 60c ea. P/P 25c

**M.S.P. 250v AC 3 AMP** toggle switch. 50c ea. P/P 25c

**Paddle switch.** D.P.D.T. 250v AC 5A. 40c ea P/P 25c.

**Transistors - AY 9150** PNP 60v 150w

- AY 8110 NPN 60v 115 80c ea. AY 8139 NPN - AY 9139 PNP 40v 10w 45c ea. AY 6120 NPN - AY 6121 PNP 50v 1A. 40c ea. 2N5088 NPN PN 3694 NPN 10c ea. BF 198 - BF 199 NPN 20c ea. P&P 30c.

**A.3065 TV/FM Sound System, I.C.** Silicone Dual In Line suitable for a wide variety of applications including T.V. sound channels - line operated and car F.M. radios and mobile communication equipment - brand new. Only \$1 ea. P/P 40c.

**Balance Meters** 1 1/2" x 7/8" x 1 1/4" Deep 200 UA \$2.25 ea. P/P 40c.

**M.S.P. 250V A.C. 3 AMP D.P.** Toggle switches 50c ea. P/P 25c.

**10Ω** 3 Watt. Wire wound pots 75c ea. P/P 25c.

**7" Dia.** Alum. Fans 240V A.C. \$6 ea. P/P \$1.

**Multiple Electrolytics.** 200 μF - 50 μF - 25 μF at 300V Plus 100 μF at 325V. VW/1. \$1 ea. P/P 30c.

**LEVEL METERS** 200 micro amp sensitivity size 1" x 1" x 3/4" \$1.50 P/P 40c.

**SOLENOIDS - tape recorder type.** 12V D.C. 5Ω coils. 1 1/2" x 1 1/2" x 3/4" \$2 ea. P/P 30c.

**TRANSISTOR RADIO.** 5k miniature switched pots. 30c ea. P/P 15c. Miniature 2 gang variable capacitors 30c ea. P/P 15c.

**Slide Pots.** Single gang. 500ΩA, 20KA, 25KA, 100KC, 200KA, 200KB, 500KA, 500KB, 1 meg.D, 35c ea. P&P 35c. Dual gang - 50KA, 250KB 1 meg.C, 2 meg.C, 60c ea. P&P 35c.

**Skeleton Preset Pots.** 100Ω - 220Ω 470Ω 2.2K, 10K, 22K, 47K 10c ea. P&P 20c.

**Philips 8Ω** dual cone 6" x 4" speakers \$2 ea. P&P 60c.

**LARGE RANGE OF COMPONENTS - GOVERNMENT AND MANUFACTURERS DISPOSAL EQUIPMENT, ALSO STEREO AND HAM GEAR ALWAYS IN STOCK.**

**PACKAGE OF TEN — DEDUCT 15%**

**PACKAGE OF ONE HUNDRED — DEDUCT 25%**

TTL					
7400	.16	7451	.20	74153	1.14
7401	.18	7452	.20	74154	1.29
7402	.17	7453	.20	74155	1.23
7403	.18	7460	.20	74156	1.23
7404	.22	7464	.40	74157	1.14
7405	.22	7465	.40	74158	2.06
7406	.40	7470	.35	74160	1.60
7407	.40	7472	.35	74161	1.44
7408	.21	7473	.40	74162	1.71
7409	.22	7474	.40	74163	1.60
7410	.18	7475	.66	74164	1.83
7411	.29	7476	.45	74165	1.83
7413	.63	7483	.91	74166	1.71
7414	.81	7485	1.27	74170	2.65
7416	.40	7486	.46	74173	1.71
7417	.40	7489	2.48	74174	1.86
7420	.18	7490	.59	74175	1.60
7422	.30	7491	1.12	74176	1.02
7423	.33	7492	.82	74171	.97
7425	.31	7493	.69	74180	1.04
7426	.30	7494	1.08	74181	3.43
7427	.33	7495	.91	74182	.91
7430	.23	7496	.91	74184	2.29
7432	.26	74100	1.50	74185	2.29
7437	.40	74105	.51	74187	4.50
7438	.40	74107	.46	74190	1.35
7440	.20	74121	.48	74191	1.35
7441	1.13	74122	.52	74192	1.25
7442	.89	74123	.69	74193	1.19
7443	1.00	74125	.62	74194	1.25
7444	1.00	74126	.72	74195	1.02
7445	1.02	74132	1.02	74196	1.44
7446	1.07	74141	1.20	74197	1.02
7447	1.02	74145	1.20	74198	2.06
7448	1.20	74150	1.12	74199	2.06
7450	.20	74151	.91	74200	5.90
				74279	1.08

**LOW POWER**

74L00	.29	74LS1	.33	74L90	1.71
74L02	.29	74LS5	.38	74L91	1.67
74L03	.29	74L71	.29	74L93	1.94
74L04	.29	74L72	.45	74L95	1.94
74L06	.29	74L73	.56	74L98	3.21
74L10	.29	74L74	.56	74L164	3.21
74L20	.38	74L78	.91	74L165	3.21
74L30	.38	74L85	1.44		
74L42	1.71	74L86	.79		

**LOW POWER SCHOTTKY**

74LS00	.36	74LS32	.38	74LS95	2.09
74LS02	.36	74LS40	.45	74LS107	.59
74LS04	.36	74LS42	1.40	74LS164	2.20
74LS08	.38	74LS74	.59	74LS193	2.20
74LS10	.36	74LS90	1.30	74LS197	2.20
74LS20	.36	74LS93	1.30		

**HIGH SPEED**

74H00	.25	74H22	.25	74H61	.25
74H01	.25	74H30	.25	74H62	.25
74H04	.25	74H40	.25	74H74	.39
74H08	.25	74H50	.25	74H101	.39
74H10	.25	74H52	.25	74H102	.49
74H11	.25	74H53	.25	74H103	.58
74H20	.25	74H55	.25	74H106	.58
74H21	.25	74H60	.25	74H108	.60

**SCHOTTKY**

74S00	.38	74S08	.52	74S22	.38
74S02	.45	74S10	.38	74S32	.52
74S03	.38	74S20	.38	74S74	.38
74S04	.45				

**8000 (NATIONAL)**

8091	.61	8220	1.49	8811	.65
8092	.61	8230	2.19	8812	1.02
8095	1.25	8288	1.49	8822	2.19
8121	.80	8520	1.16	8830	2.19
8123	1.43	8552	2.19	8831	2.19
8130	1.97	8563	.62	8836	.29
8200	2.33	8810	.70	8880	1.19
8214	1.49				

**8000 (SIGNETICS)**

8263	5.79	8267	2.59		
------	------	------	------	--	--

**9000**

9002	.40	9309	.79	9601	.89
9307	1.03	9312	.79	9602	.79

**DTL**

930	.15	937	.15	949	.15
932	.15	944	.15	962	.15
936	.15	946	.15	963	.15

**6 DIGIT LED CLOCK KIT**

INCLUDES:  
MM5314 clock circuit  
6 PND70 LED displays (250° red 7 segment)  
All necessary transistors, resistors & capacitors  
1 double sided PC board accommodates LED's & clock circuitry  
Schematic & instructions  
Does not include 12V-300 ma transformer, switches & case \$12.95

QUANTITY DISCOUNT NOT APPLICABLE ON THIS ITEM

**IC SOCKETS**

**Solder Tail - low profile**

8 pin	.19	24 pin	.45
14 pin	.22	28 pin	.59
16 pin	.24	40 pin	.69
18 pin	.35		

**WIRE WRAP - gold plate**

14 pin	.59
--------	-----

**CMOS**

4000A	.30	4018A	1.39	4066A	1.02
4001A	.29	4020A	1.49	4068A	.51
4002A	.29	4021A	1.39	4069A	.51
4006A	1.55	4022A	1.10	4071A	.30
4007A	.30	4023A	.29	4072A	.40
4008A	1.79	4024A	1.02	4073A	.45
4009A	.66	4025A	.29	4075A	.45
4010A	.62	4027A	.68	4078A	.45
4011A	.33	4028A	1.13	4082A	.40
4012A	.29	4030A	.51	4518A	1.89
4013A	.52	4035A	1.46	4528A	1.84
4014A	1.49	4040A	1.39	4585A	2.10
4015A	1.49	4042A	1.69	4901A	.45
4016A	.56	4049A	.68		
4017A	1.19	4050A	.68		

74C00	.25	74C74	1.20	74C162	2.93
74C02	.30	74C76	1.54	74C163	3.06
74C04	.51	74C107	1.30	74C164	3.06
74C08	.78	74C151	3.00	74C173	2.61
74C10	.40	74C154	2.62	74C195	2.66
74C20	.40	74C157	2.02	80C95	1.35
74C42	1.55	74C160	2.85	80C97	1.13
74C73	1.20	74C161	2.93		

**CALCULATOR CHIPS**

CT5002	12 digit, 4 function fixed decimal — battery operation	40 pin	2.79
CT5005	12 digit, 4 function plus memory, fixed decimal	28 pin	2.99
MM5725	8 digit, 4 function, floating decimal	28 pin	1.98
MM5736	6 digit, 4 function, 9V battery operation	18 pin	3.95
MM5738	8 digit, 5 function plus memory and constant floating decimal, 9V battery operation	24 pin	4.50
MM5739	9 digit, 4 function, 9V battery operation	22 pin	5.35

**MEMORIES**

1101	256 bit RAM MOS	16 pin	1.50	
1103	1024 bit RAM MOS	18 pin	1.95	
1702A	2048 bit static PROM elect. prog. - UV eras.	24 pin	14.95	
2102	1024 bit static RAM (2602)	DTL/TTL comp. 1 ms	16 pin	2.95
2102.1	Same as 2102, except 500ns		2.99	
5203	2048 bit static PROM elect. prog. - UV eras.	24 pin	10.95	
5260	1024 bit dynamic RAM MOS	16 pin	1.95	
5261	1024 bit dynamic RAM MOS	16 pin	2.19	
5262	2048 bit dynamic RAM MOS	22 pin	2.25	
7489	64 bit ROM TTL	16 pin	2.48	
82523	256 bit PROM SCHOTTKY	16 pin	3.69	
F93410	256 bit RAM bi-polar	16 pin	1.95	
74187	1024 bit ROM TTL	16 pin	5.95	
74200	256 bit RAM tri-state	16 pin	5.90	

**TANALUM CAPACITORS SOLID-DIPPED - 20%**

.1 mid 35V .25 ea.	6.8 mid 6V .30 ea.
.33 mid 35V .25 ea.	6.8 mid 50V .40 ea.
1 mid 35V .25 ea.	10 mid 25V .40 ea.
2.2 mid 20V .25 ea.	15 mid 10V .40 ea.
2.2 mid 35V .30 ea.	33 mid 10V .40 ea.
4.7 mid 16V .30 ea.	47 mid 6V .40 ea.

**SHIFT REGISTERS**

MM5013	1024 bit accum. dyn.	8 pin	1.75
MM5016	500/512 bit dyn.	8 pin	1.59
515-4025	Quad 25 bit	16 pin	1.29
2504	1024 bit multiplexed dyn	8 pin	4.95

**UNIVERSAL BREADBOARD**  
Silver plated copper circuit board 1.1" x 5.9" x .16" — 2 rows of 27 holes for DIP IC's — space for transistors, resistors & capacitors. Versatile and simple for bread-boarding IC circuits \$1.50 ea.

**CT5005 CALCULATOR CHIP**  
12 digit — 4 function with memory  
\$1.39

**7001 CLOCK CHIP**  
4-6 digit, 12-24 hr. alarm, timer and date circuits — with data  
\$6.95

**DVM CHIP 4 1/2 DIGIT**  
MM5330 — P channel device provides all logic for 4 1/2 digit volt meter, 16 pin  
DIP with data  
\$12.99

MM5378  
8 digit multiplexed — five function — chain operation 2 key memory — floating decimal — independent constant — interfaces with led with only digit driver — 9 V batt. oper. 24 pin  
\$3.95

**JULY SPECIALS**

1103	Memory	10/\$10.00	100/\$88
5260	"	10/\$11.90	100/\$104
5261	"	10/\$11.90	100/\$104
5262	"	10/\$13.90	100/\$122
5002	Calculator Chip	10/\$11.90	100/\$104
5005	"	10/\$13.90	100/\$122
5738	"	10/\$20.00	100/\$176
309K	5V Regulator	10/\$10.00	100/\$89
741	Operational Ampl.	10/\$2.50	100/\$22
3900	Quad amplifier DIP	10/\$3.20	100/\$29
74123	Dual Monostable Multivibrator	10/\$5.60	100/\$50
MAN 1	Display	10/\$11.90	100/\$104

**CLOCK CHIPS**

MM5311	6 digit multiplexed BCD, 7 seg 12-24 Hr, 50-60 Hz 28 pin	\$4.45
MM5312	4 digit multiplexed BCD, 7 seg 1 pps. 12-23 Hr, 50-60 Hz 24 pin	3.95
MM5314	6 digit multiplexed 12-24 Hr, 50-60Hz 24 pin	4.45
MM5316	4 digit, 12-24 Hr, 50-60 Hz, alarm 40 pin	5.39
CT7001	6 digit, 12-24 Hr, 50-60 Hz, alarm, timer and date circuits 28 pin	7.95

**MISC DEVICES**

ULN 2208	FM gain block 34dB mDIP	1.39
ULN 2209	FM gain block 48dB mDIP	1.59
2513	64 x 8 x 5 character generator	11.00
CA 3046	Transistor array 14 pin DIP	.86


**LINEAR CIRCUITS**

300	Pos V Reg (super 723) TO-5	.82
301	Hi Perf Op Amp mDIP TO-5	.33
302	Volt follower TO-5	.61
304	Neg V Reg TO-5	.92
305	Pos V Reg TO-5	.82
307	Op AMP (super 741) mDIP TO-5	.30
308	Micro Pwr Op Amp mDIP TO-5	1.02
309K	5V 1A regulator TO-1	1.35
310	V follower Op Amp mDIP	1.23
311	Hi perf V Comp mDIP TO-5	1.09
319	Hi Speed Dual Comp DIP	1.30
3201	Neg Reg 5.2, 15, 12 TO-220	1.60
320K	Neg Reg 5.2, 12 TO-3	1.60
322	Precision Timer DIP	1.96
324	Quad Op Amp DIP	1.75
339	Quad Comparator DIP	1.69
340K	Pos V reg (5V, 6V, 8V, 12V, 15V, 18V, 24V) TO-1	1.94
340T	Pos V reg (5V, 6V, 8V, 12V, 15V, 18V, 24V) TO-220	1.71
370	AGC/Squelch AMPL DIP	1.20
372	AF-IF Strip detector DIP	2.93
373	AM/FM/SSB Strip TO-5	2.42
376	Pos V Reg mDIP	.68
380	2w Audio Amp DIP	1.30
380-B	hw Audio Amp mDIP	1.25
381	Lo Noise Dual preamp DIP	1.75
382	Lo Noise Dual preamp DIP	1.75
531	High Speed rate Op Amp	2.95
540	Power driver TO-5	



# Ideas for experimenters


## TEMPERATURE STABILIZED RELAY

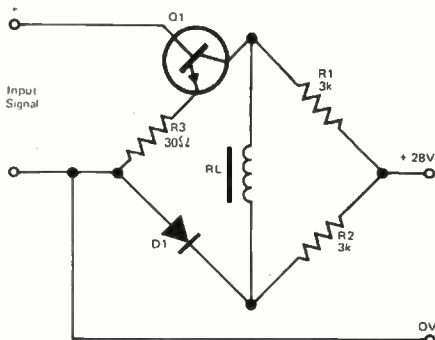

Accurate relay trip-point operation can be obtained over an ambient temperature range from  $-50^{\circ}\text{C}$  to  $+90^{\circ}\text{C}$  using this simple circuit.

The temperature sensitivity of the silicon transistor Q1 is balanced out by the silicon diode D1. Gain/temperature stabilization may be obtained if required by using a positive temperature co-efficient resistor for R3.

## BROAD BAND AMPLIFIER

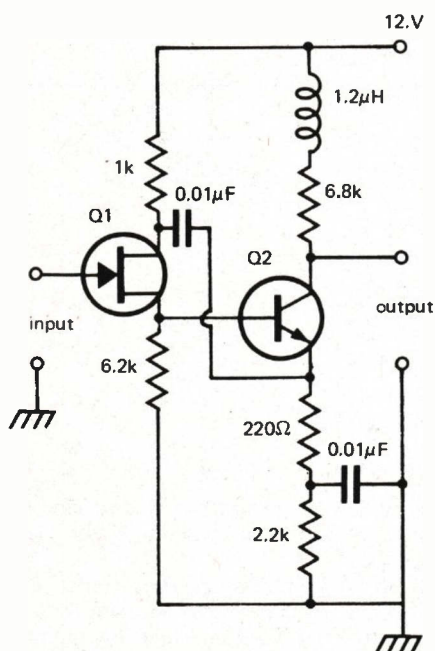

This circuit has a typical gain of 10dB and bandwidth of 90 MHz.


Input impedance is around 10 megohms in parallel with 1.0pF. Output impedance is reasonably high and depends mainly on Q2; output

capacitance will be around 2 to 3pF with careful construction.

FET, Q1, should be an n-channel type with low gate source capacitance and a high cutoff frequency.

The transistor, Q2, should have a high gain-bandwidth product and low collector-emitter capacitance. Careful selection can extend the bandwidth beyond 100 MHz.


## MODIFIED VOLTAGE DOUBLER

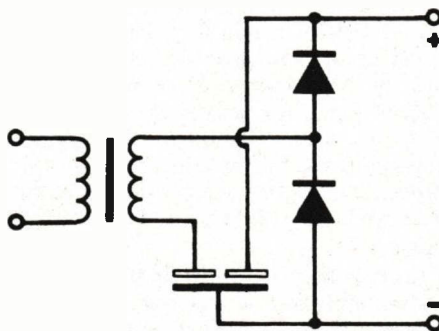

Twin electrolytic capacitors take up less space than two separate units but cannot normally be used in voltage doubler circuits.

However a slight modification to the circuit allows twin electrolytics to be used, with the can connected to chassis.

Alternatively, in low voltage circuits where high value electrolytic capacitors are used, two capacitors may be used without the necessity of insulating the case (generally the negative terminal) of one of them.



Manufacturers of: Electrical/  
electronic equipment, wound  
components and lighting  
control equipment.

## BRANCHES IN ALL STATES


FERGUSON TRANSFORMERS  
PTY. LTD.  
HEAD OFFICE:  
331 High St., Chatswood. 2067  
P.O. Box 301,  
Chatswood, NSW, Australia 2067  
Phone: 02-407-0261

# FIDELITY SERVICE
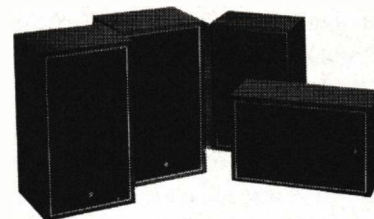
## Newsletter No. 2

Hello again. On the subject of high fidelity loudspeaker systems, most enthusiasts will be aware of some superb examples. They will also realise that a very considerable amount is required in order to purchase same. This month therefore, we draw your attention to a few selected speakers which maintain a high level of performance and yet remain within a low budget limit of \$200 per pair.

A genuine bookshelf sized unit, DENTON 2 is manufactured by the famous British firm of WHARFEDALE. A 200mm Bass speaker with rigid die cast chassis and compliant neoprene roll surround crosses over at 1200Hz to a plastic dome treble unit giving a frequency response of 60-16000 Hz within the very tight (for a speaker) limits of  $\pm 3$  dB. No apologies required at any price so take advantage of our special offer \$149 plus \$4 freight.



One of the world's largest speaker manufacturers, PIONEER have designed the CS-411 for shelf or floor placement. The particularly solid 250mm woofer drives from a well damped bass reflex enclosure giving a high sensitivity of 93 dB/watt/metre. Eminently suitable for lower powered amplifiers (to 30w) and covered by full 3 year parts and labour warranty, it is a top value buy at \$159 plus \$5 freight. Note. Smaller brother CS 311 — \$115 plus \$4 freight.

Finally we have the new (to Australia) North American speakers from PRO-LINEAR. The model EDS 3000 is an excellent 3 way system with a 300mm woofer coupled to a 125mm mid-range and 75mm tweeter. As well as fine all-round performance, foam grille & 5 yr parts warranty, it features a massive power handling capability of 60 watts R.M.S. An amazing price/performance ratio at \$195 plus \$5 freight.

P.S. Fully engineered for the home constructor by GOODMAN, the DIN 20 is a complete 2 way kit, handling 40w in recommended enclosure. \$96 per pair plus \$2 P&P. Send a 20c stamp for our latest catalogue.

### LIMITED STOCK SPECIALS

DEITRON	amplifier	12+12w.	\$119.
DEITRON	1515 amplifier	15+15w	\$149.
DEITRON	2525 amplifier	25+25w	\$169.

All above plus \$3 freight.

# FIDELITY SERVICE

19 Borman St., Slacks Creek, Qld. 4114  
Phone 208-2922.

S.O.

# STAR DELTA CO.

PTY. LTD.

TRANSFORMER  
MANUFACTURERS

We can supply transformers, chokes, etc. for most of the projects featured in Electronics Today at competitive prices.

We also manufacture a range of transformers in single and three phase up to 20 KVA, all manufactured to comply with the relevant Australian Standards.

8 East St.,  
Granville, N.S.W. 2142  
P.O. Box 31, Phone 637-7870


## "COWPER"

Cabinets and chassis for all projects featured in this magazine are available from

COWPER SHEETMETAL  
& ENGINEERING  
11 Cowper Street,  
Granville, N.S.W. 2142  
Phone 637-8737  
(P.O. Box 31)



## Ideas for experimenters



### CLOCK MODIFICATIONS

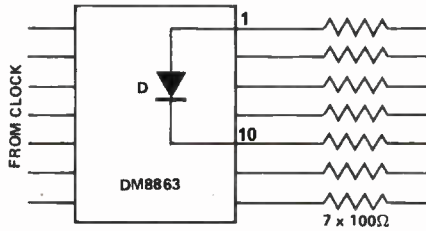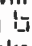
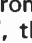


Here are a couple of modifications that can be made to the digital clock project in ETI January 1975.


To start with, the supply voltage to the DM8863 is not filtered, which in some cases can cause flickering of the display (or individual segments). A 220 nF capacitor between pins 18 and 9 will fix this. Although the supply voltage to the buffer is increased by this procedure (and thus the voltage to the display) it is still within the specified range.

A diode between pins 10 and 9 of the buffer will add a top bar to the 6, changing  to , which some people think looks better.

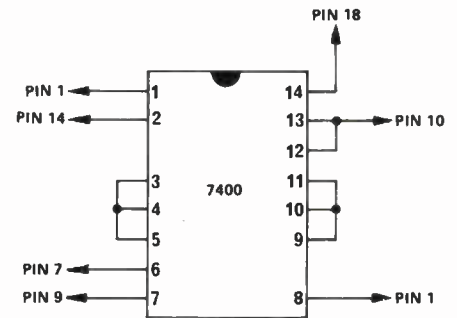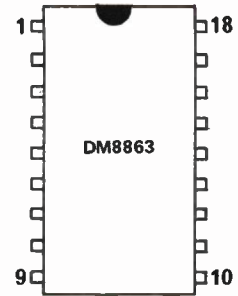
After changing the appearance of the 6, one really needs to change the 9 as well. If a logic Nand gate has one of its input connected to pin 1 and the other input to pin 14 of the DM8863, and the output from the Nand gate is connected to pin 7, the nine will change from  to .



ALL PINS TO  
DM8863

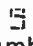to  without affecting any other number. The current needed to illuminate segment D for a nine is drawn from the Nand gate.

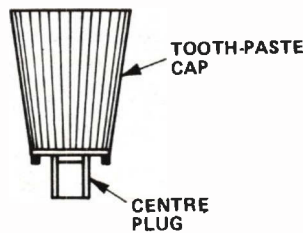The gate used was from a 7400, followed by an inverter, one of the other gates in the IC. If desired, the other two gates of the 7400 can be used instead of the diode for improving the number six.




### CASSETTE WINDER

This is a device for taking up the slack in cassettes. Take the centre "plug" from a Memorex cassette and glue it to the cap of a toothpaste tube.

It provides better grip than a pencil, and doesn't cost 75c.
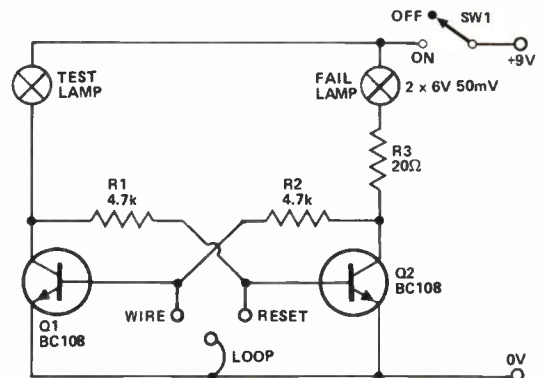
### CHEAT-PROOF BENDY WIRE GAME

This gadget is an amusing novelty at a fete or party. The aim of the game is for




the player to manipulate a loop along a bent piece of wire without the two touching.

If the player touches the loop to the wire, the fail lamp lights and will remain on until the reset contact is touched with the loop.

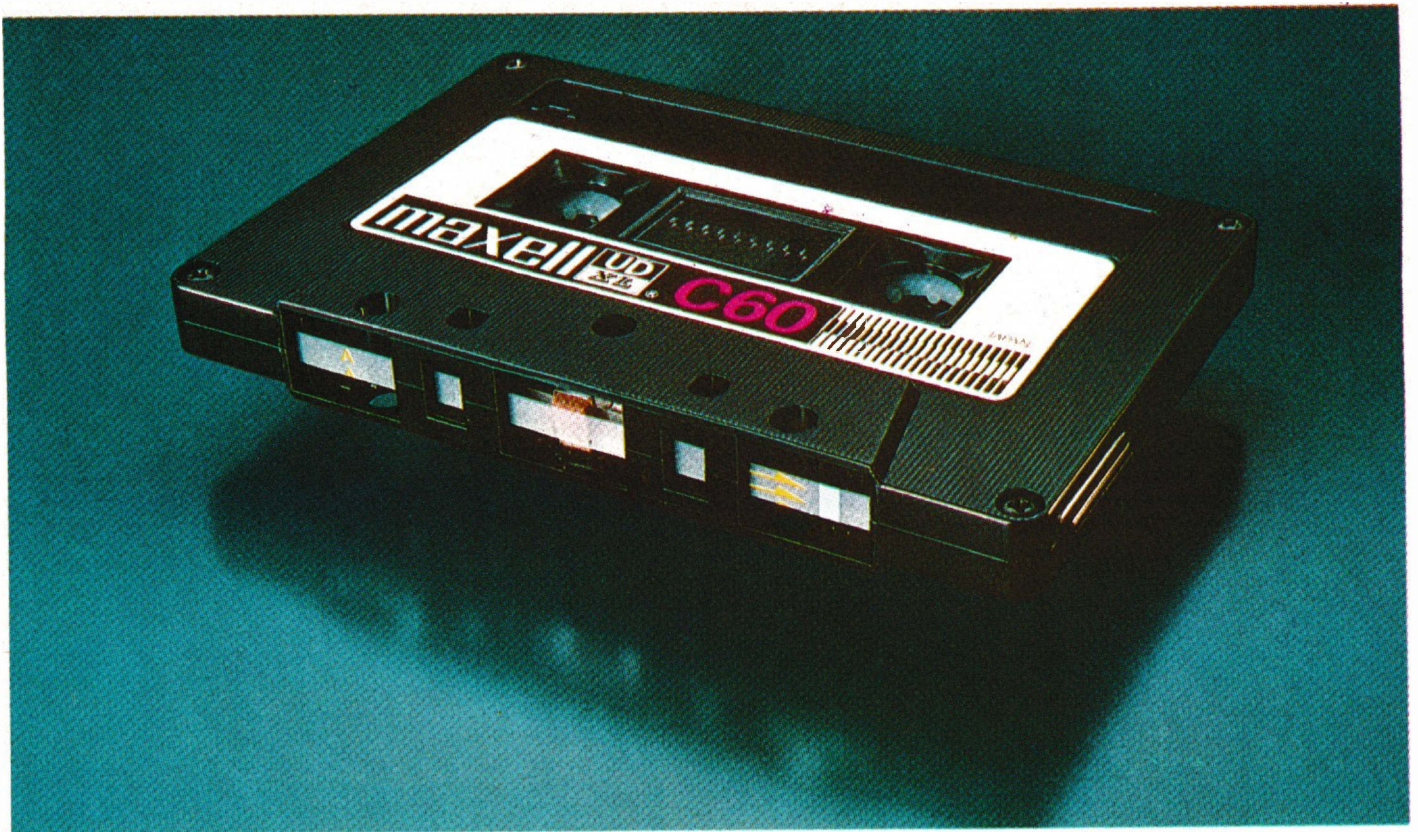R1 ensures that the fail lamp will light if the power supply is interrupted. The value may need experimenting with to achieve maximum lamp brightness, but still maintains its "cheat-proof" purpose.





# Introducing the revolutionary UD-XL EPITAXIAL cassette




Developed by MAXELL this completely new EPITAXIAL magnetic material combines the advantages of the two materials (gamma-hematite and cobalt-ferrite): the high sensitivity and reliable output of the gamma-hematite in the low and mid-frequency ranges and the excellent performance of the cobalt-ferrite in the high-frequency range. The result is excellent high-frequency response plus wide dynamic range over the entire audio frequency spectrum.

Compared to chrome tape, sensitivity has been improved by more than 3.5dB. Because EPITAXIAL is non-abrasive, it extends to the life of the head. Consequently, the UD-XL delivers smooth, distortion-free performance during live recording with high input. When using UD-XL it is recommended that tape selector be in the NORMAL position.





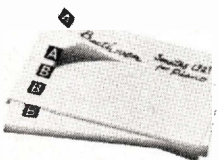Fidelity is also ensured by a precision-manufactured cassette shell with a special anti-jamming rib that provides smooth tape travel and helps eliminate wow and flutter.



Another good idea of the UD-XL cassette is a replaceable self-index label. Simply peel off the old label and put on a new one when you change the recording contents. No more mess on the label.

Magnetic material structure

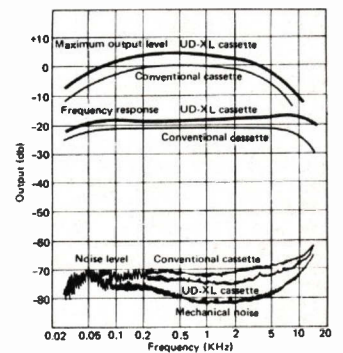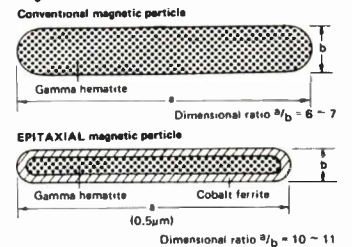

# maxell®


For further information please write to Maxell Advisory Service, P.O. Box 49, Kensington, N.S.W. 2033.

WT.GD. 76M



# A DC to 6MHz, CALIBRATED, TRIGGERED, OSCILLOSCOPE

## FOR UNDER \$200!

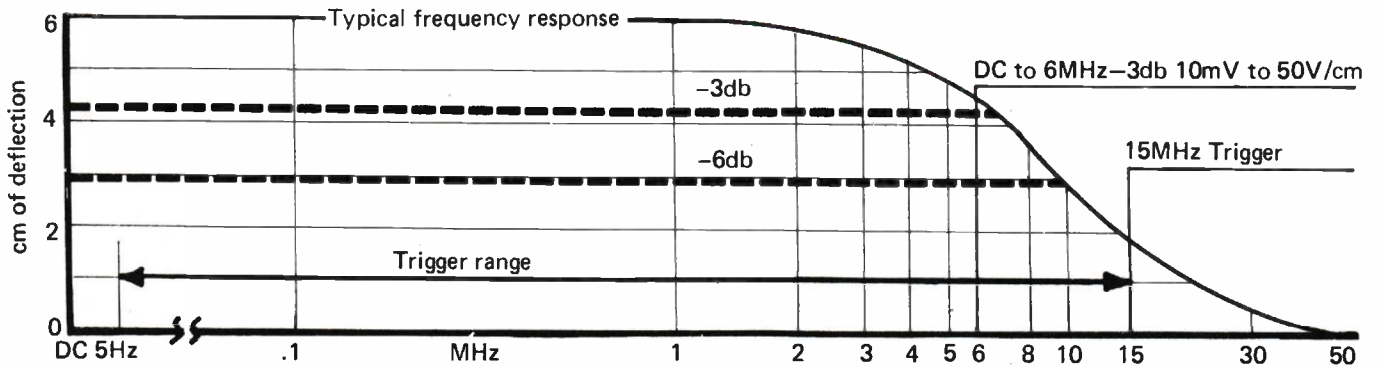

### bwd 504

5.5kg of high performance with 12 months warranty.

### JUST LOOK AT THIS SPEC

- |                    |               |
|--------------------|---------------|
| DC to 6MHz-3db     | bandwidth     |
| 10mV to 50V/cm     | sensitivity   |
| 5Hz to 15MHz       | triggering    |
| 0.5µSec to 1sec/cm | time base     |
| DC to 1MHz-3db     | X-Y operation |
| 8 x 10cm           | CRT screen    |
| 1.6KV              | EHT           |
| ±400V DC isolation | input ground  |


### PLUS

- 5% calibration including effects of a 10% line change.
- Completely automatic triggering of almost any waveform to 15MHz
- Phase corrected X-Y operation to <math><3^\circ</math> from DC to 50kHz.
- Usable frequency response to beyond 25MHz.

**AND LOOK INSIDE...**  
 there's an all silicon solid state circuit, an astatically wound 'C' core transformer, a completely balanced vertical amplifier with excellent pulse response, a FET input stage fully protected to ±400V and a compensated 12 step attenuator accurate to 2% at each step. Built in reliability with conservatively rated high stability components throughout.

*We invite you to our Mulgrave premises for a practical demonstration and discussion on oscilloscopes and other instruments in our range.*

MB7601B

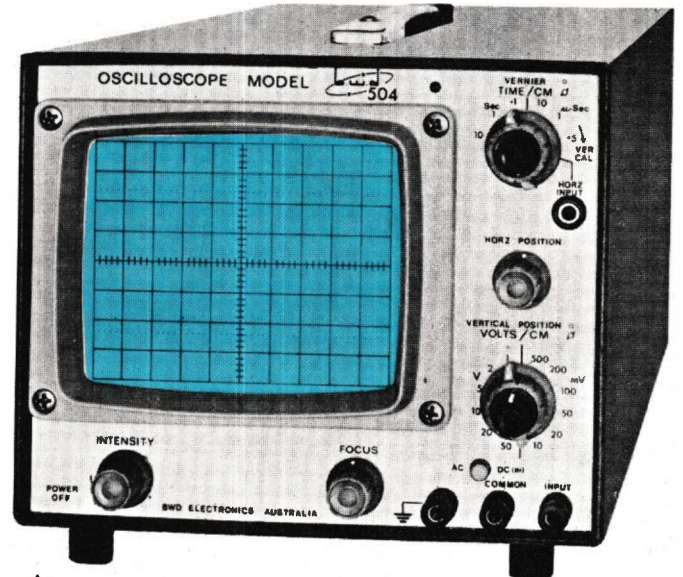

**\$199** as at 31/1/76 plus tax if applicable.  
 Ex distributor, Aust. Capital City.  
 Price includes x1 signal and ground probes.

### B.W.D. ELECTRONICS PTY. LTD.

MILES STREET, MULGRAVE, VIC., 3170  
 PHONE: (03) 561 2888  
 CABLES: 'OSCILLOSCOPE, MELB.'  
 N.S.W. PHONE: (02) 929 7452  
 DISTRIBUTORS: S.A.: (08) 269 1244  
 W.A.: (092) 25 3144  
 QLO.: (07) 52 7255  
 TAS.: (002) 23 1843




1955/1976 21 YEARS OF AUSTRALIAN DESIGN INNOVATION

B.W.D. Electronics Pty. Ltd.,  
 P.O. Box 325, Springvale, Vic., 3171  
**Please let me have full details on the bwd504 oscilloscope.**  
 Name .....  
 Company .....  
 Address .....




# SERVICEMEN

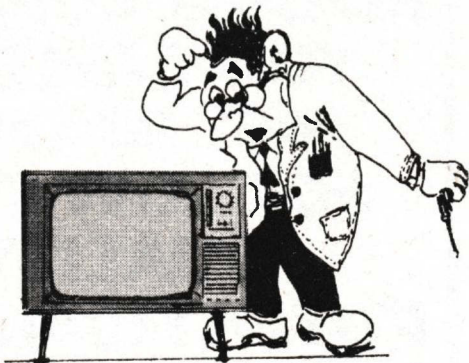

Scratching your head  
won't help  
**THIS WILL!**

15 Years of service

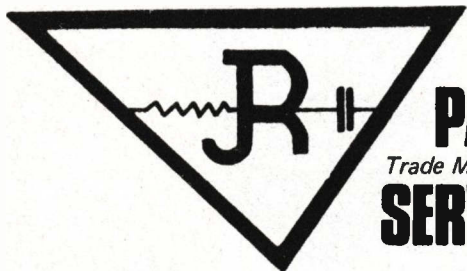

**PAL TELEVISION**  
*Trade Mark*  
**SERVICE HANDBOOK**

## Manuals on:

Colour and Monochrome. Also Cassettes and Transistor Radios.

## Colour TV Books!!

Patchett's: Colour TV with Part Ref to PAL System.  
Bohlman's: PAL-D Colour Receivers Questions & Answers.  
Bohlman's: Colour TV Picture Faults.

Send for your brochure:—

**J.R. PUBLICATIONS**  
P.O. Box 29  
CHESTER HILL  
2162

or call:  
53 Stanley St.  
Peakhurst  
N.S.W.  
Phone 53 6295

or:  
New Zealand series  
VITAL BOOKS LTD.  
P.O. Box 8601  
Symons Street  
AUCKLAND N.Z.

# POLYSTYRENE CAPACITORS

Allied Capacitors are continuing the manufacture of Polystyrene Capacitors to close tolerance such as 1%, 2% and values not readily available from overseas such as 63, 250, 400, 630 and 1000 volts.

## Tubes

Tubes are available from Ratheon for Transmission Receiving, Radar, Microwave, Cathode Ray, Photomultiplier.

## LED's

— from Monsanto  
The acknowledged world leaders for quality — when a guarantee of service is desirable ask for Monsanto Technical Data. Write or phone for our free quick reference chart for diodes and displays.

## Data Device Corporation

Now produce a most comprehensive catalogue of converter products-analog-to-digital, Synchro-to-digital Hybrid, Tracking Synchro converts, etc.

Catalogue \$5.00 post paid

# Allied Capacitors

214 Harbord Road,  
BROOKVALE, 2100  
P.O. Box 198,

Phone 938-2135 (Area code 02)

**This is the only  
tool needed  
to build  
the new 7BW  
Hi-Fi  
SPEAKERS**  
(AND IT'S SUPPLIED)



Do it yourself and save! The new G.H.E./Philips 7BW Hi-Fi speaker kits are available now. Kits include pre-cut timber panels all hardware and require no soldering. The popular 7B, 3 way system offers 28-20,000 HZ response and optimises 10-40W R.M.S. Amplifiers.



**7BW  
\$245  
PAIR**

Send coupon for specification brochure:

NAME: .....

ADDRESS: .....

**George Hawthorn  
Electronics**

966-968 HIGH ST, ARMADALE,  
MELBOURNE, VIC, 3143.  
TEL 509 0374, 509 9725



**WHEN IT  
COMES TO  
ROTARY CONTROL  
YOU CAN'T GO  
PAST SOANAR  
FOR LOW COST  
QUALITY  
POTENTIOMETERS**

A high quality range of rotary controls, widely used throughout the industry for applications in the professional, industrial and entertainment electronics field. Produced by advanced manufacturing techniques using the highest quality materials, these rotary controls conform to the Australian standard specification AS 1347 (1972)



**GANGED  
SINGLE  
SWITCHED**

**LOG  
LIN  
24 mm & 16 mm**

Technical literature  
available on request.

**SOANAR ELECTRONICS PTY. LTD.**

SALES OFFICES

VICTORIA: 89 0661

N.S.W. 78 0281

S. AUST.: 51 6981

QUEENSLAND: 52 5421

W. AUST.: 81 5500

30 Lexton Road, Box Hill, Vic., 3128,  
Australia. Telex 32286







# AUDIO FACTS

## JAPANESE CASSETTE

The Elcaset, developed jointly by Sony, Matsushita and Teac, is new competition for the Compact Cassette of Philips. The compact cassette uses 3.81 mm tape at 48 mm per second; the Elcaset uses 6.3 mm tape at 95 mm per second. The Elcaset carries a narrow cue track (for control of the playback equipment or synchronisation of slides or film) with each stereo pair. Machines are planned for later this year. Hopefully we will soon have machines for Europe's cassette rival, BASF's Unisetete.

## DRAMATIC ADVANCE IN RECORDED SOUND

During this past month we have been listening to dbx encoded gramophone records played back via a dbx type 124 decoder.

The results can only be described as remarkable. We have never before heard records reproduced with such clarity, dynamic range or total lack of surface noise. The performance quality was literally as good as that obtainable from studio master tapes.

The process electronically compresses the recorded signal by a factor of 2:1 at the time the master disc is cut, and expands the signal by a complementary factor of 1:2 at the point of playback. If a dbx encoded master tape is used, full dynamic range and freedom from noise will be realized upon playback. Master tapes produced with other types of noise reduction systems, or with no noise reduction at all, may be used and the played back disc will sound equal to the master tape.

dbx encoding eliminates the chief limitation which prevents conventional records from duplicating the quality of music performed live, namely, that ordinary discs are limited to a dynamic range of some 60 dB; whereas, music in concert performance may have well in excess of 100 dB dynamic range.

The dbx process compresses the dynamic range of the music to a "dynamic range envelope" which fits conveniently within the inherent limitations of the record medium, then expands the music to its full original dynamics at the point of playback. This compression and subsequent expansion reduces record surface noise and other unwanted background noise to inaudibility, so that when the musical programme stops, no sound of any kind is heard from the playback system.


The complete absence of background noise also makes the quiet portions of the music easier to hear, and the definition of individual voices and instruments in ensemble music is dramatically improved.

A significant advantage of the dbx disc encoding process is that it does not obsolete any existing manufacturing technique or equipment presently in use in the recording industry, nor does it increase actual product cost in any way. On the contrary, dbx encoding offers numerous opportunities for


reducing the cost of recorded music without compromising quality. For example, with dbx encoding, record grooves may be placed closer together, increasing the amount of music on a record by up to 30%. Also, dbx encoding places the quietest sound so far above the surface noise level that lesser cost record pressing materials may be substituted for virgin vinyl without audibly affecting playback quality. And finally, because dbx encoding makes many of the mechanical steps in record preparation and production less critical, much rework and fine tuning in the production process can be eliminated. The only cost to the record producer is the nominal one time investment in the required dbx encoding equipment used at the disc mastering stage.

Electronic expansion circuitry, similar in cost and complexity to Dolby B and quad matrices, is required at the point of playback to properly decode the dbx compressed signal. The decoder circuitry is now available to audio equipment manufacturers for inclusion in audio components and systems on a license basis. We understand that Teac are including it in some of their latest gear.

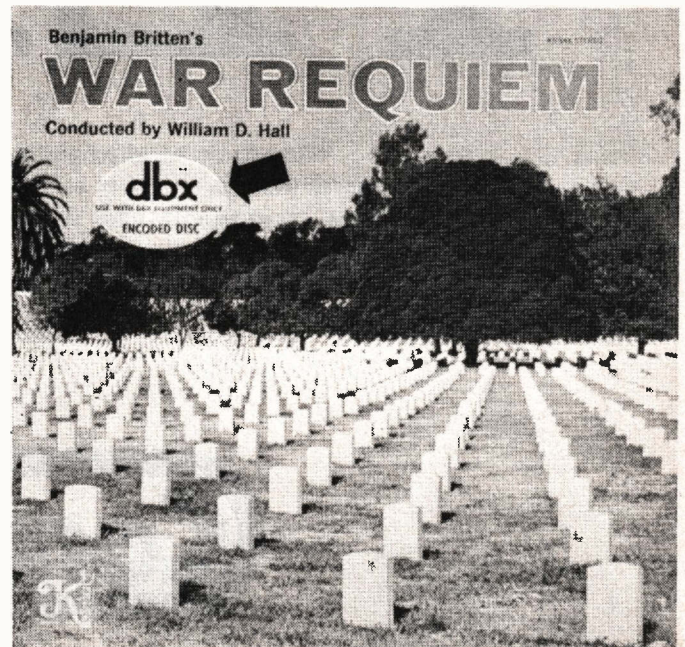Two commercial record labels have already announced discs in dbx encoded format. Klavier Records have produced a range




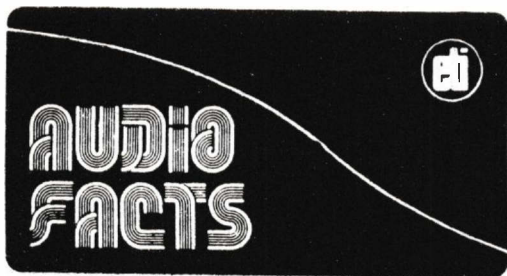dbx encoding labels may soon be a common sight.



of such recordings and Stan Kenton's Creative World label has recently completed several sessions with the Kenton band in dbx format and expects to issue future disc releases in dbx encoded as well as standard format.

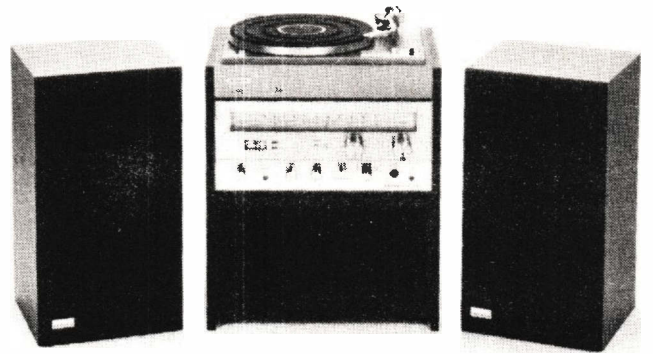We hope to be able to publish a full technical article dealing with the dbx encoding system very soon.



### NEW RONDO SYSTEM FROM PIONEER

Pioneer hi-fi equipment is invariably excellent value for money — particularly so with that company's 'package deal' systems.

The new Rondo 3000X is no exception. Heart of the system is a new AM/FM stereo tuner/amplifier which has a (continuous) power output of 13 watts per channel into the four ohm speakers supplied.

This new tuner/amplifier has a number of interesting

features. These include a volume control adjustable in 41 discrete steps and a phase locked loop in the stereo decoder — this ensures adequate stereo separation as well as rendering the circuitry less sensitive to changes in temperature and humidity — say Pioneer.

The speakers supplied with the new system are three-way bass reflex units incorporating a 200 mm woofer, 66 mm midrange and a similar sized dome tweeter.

---

# TEAC®

... likes to be handled and talked about by the salespeople and specialised technicians at CONVOY SOUND, even more so in their comfortable new showroom. Our cassette and open reel decks like to be connected with the other well known friends that CONVOY SOUND are experts at matching.

Good Effort.

## Convoy Sound



# Presenting a remarkable range of products... a remarkable philosophy.

The world's reviewers agree that each of the products presented here represents true state-of-the-art, design, engineering and performance.

None is cheap, but each item is realistically priced considering the standards achieved and maintained.

And that brings us to our Remarkable Philosophy.

We feel our equipment and your interests are worthy of the finest demonstration facilities, the most expert installation and the advice of interested, knowledgeable, and honest consultants who will help you . . . not pressure you.

To this end we have appointed a small number of Hi-Fi Specialists to bring you Stanton, Fons, S.A.E., Monitor Audio and Neal state-of-the-art components.

**We invite you to audition this remarkable equipment at the selected Hi-Fi specialists listed overleaf.**







# STANTON

STANTON pickups are the almost unanimous choice of recording studios, Radio Stations and TV stations.

They are unique in that they offer spectacular performance without fragility. They also lead the field in consistency—a quality lacking in most pick-ups.

From the illustrious Calibration Standard 681 EEE through the 681 EE and 500 EE to the Broadcast 500A (so popular with radio stations) there is a Stanton pick-up to meet the most exacting need.



Stanton 681 EEE, the New Calibration Standard . . . . Stanton's finest Cartridge.



Stanton 681 EE, for application where slightly greater tracking pressure than 681 EEE is required.



Stanton 500A, the Broadcast Standard Cartridge as used by the majority of radio stations throughout Australia.

## the remarkable products...




# Fons

FONS is a new name to the world of hi-fi. Bull in Scotland, the Fons CQ30 turntable has such exciting features as:—

- D.C. Servo controlled motor with gold plated commutator and silver plated brushes.
- Speeds, push button selected for 33, 45 and 78 RPM but continuously variable from 29 to 100 RPM.
- Hyper-concentric bearing typically better than  $\pm 0.000076$ mm.
- Rumble typically -79dB.
- Wow and Flutter better than  $\pm 0.03\%$ .
- Anti-feed back phase cancellation suspension system.

Fons claim that the virtual absence of wow and flutter, rumble and vibration lead to a noticeably cleaner sound, and direct comparisons with other units certainly confirm this. In fact, direct comparison with another highly regarded unit using the same Stanton 681 EEE cartridge showed a dramatic improvement.

Neal 102

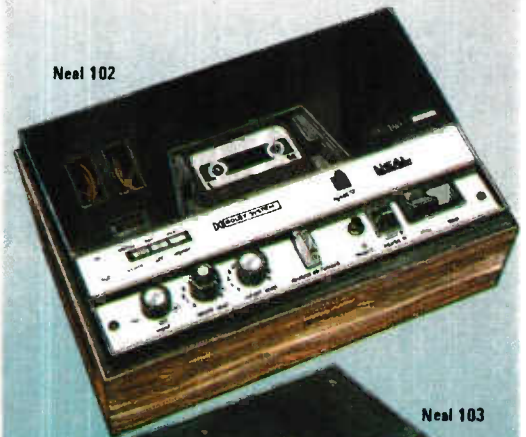

Neal 103



# NEAL

Neal is a name new to Australia but it has established a formidable reputation in the U.K. for quality, ruggedness and performance stability.

The Neal Transcription Cassette Recorder is the product of people who have many years experience in the design and manufacture of tape recording equipment.

The one word that sums up their design and their product is "Integrity". You will find no miracles, no way-out designs, no change for the sake of change, just an obsession with doing everything the right way.


Separate preamplifiers are used for each of the three stereo inputs to reduce noise. This also allows three stereo (or six mono) inputs to be mixed.

Bias is readily adjustable to optimize performance from any tape, thanks to Neal's exclusive Varitape facility.

Neal are the only cassette recorder company in the world to offer the ultimate quality control check. A cassette actually recorded on the machine you buy. This is your guarantee of quality.

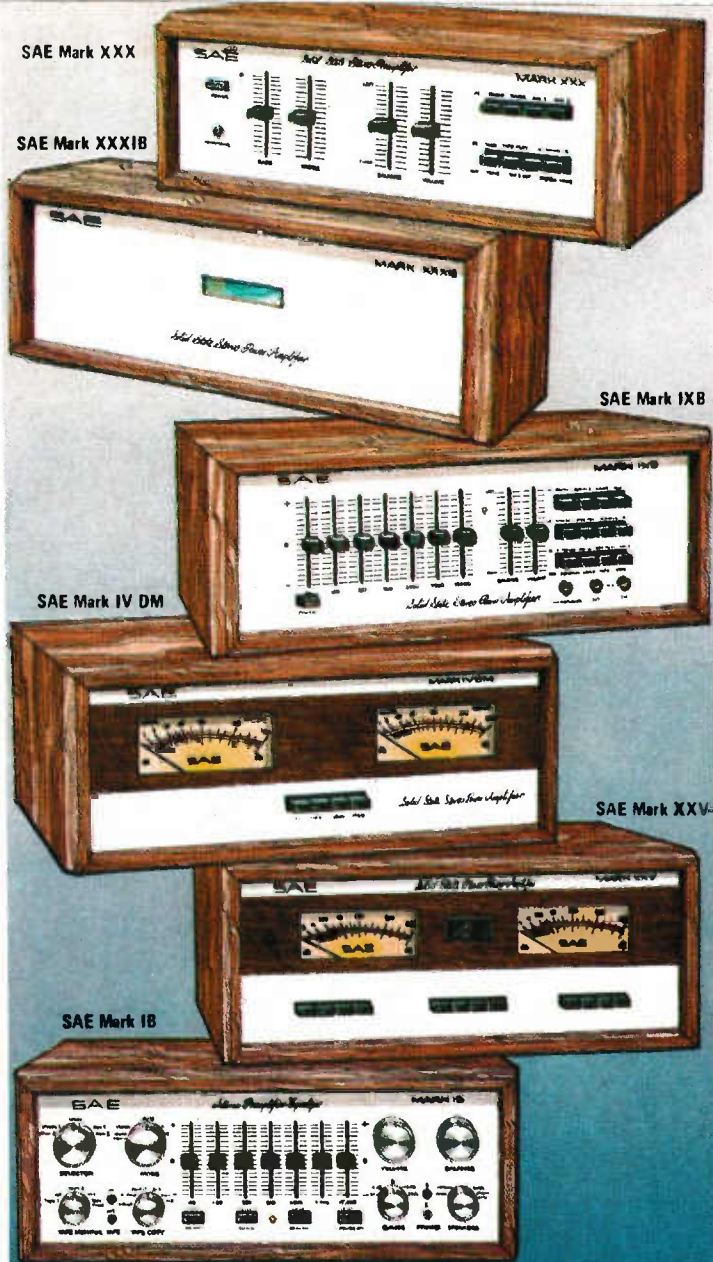"Hi-Fi for Pleasure" (August 1975) consider the Neal 103 as being "the obvious choice of the serious enthusiast or semi-professional".





SAE Mark XXX

SAE Mark XXXIB

SAE Mark IXB

SAE Mark IV DM

SAE Mark XXV

SAE Mark IB

# SAE

S.A.E. Preamplifiers, Power amplifiers and Equalizers have taken the professional field by storm. The acceptance of S.A.E. into their ranks has been almost unprecedented.

Mark XXX Preamplifier with Mark XXXIB Power Amplifier brings you Connoisseur Sound at budget prices. All unnecessary items have been omitted in the pursuit of the highest possible performance to price ratio.

The S.A.E. Mark XXXIB was tested by "High Fidelity" in May 1974, at 0.031% THD 20HZ to 20KHZ at 50 watts output per channel.

Mark IXB Preamplifier with Mark IVDM Power Amplifier. This combination brings you a versatile Equalizer Pre-amplifier with a power amplifier that was described in the "Popular Electronics" May, 1975 review as "True state-of-the-art performance with distortion levels that cannot be measured with any but the most advanced laboratory instruments." "For all purposes the Mark IVDM is a distortionless amplifier". Actual measurements were 0.005% at Rated 100 watts per channel and only 0.1% at 190 watts per channel!

Mark XXV Power Amplifiers. This is surely today's ultimate amplifier. It is rated at 300 watts per channel, both channels driven, into 8 ohms, and S.A.E. ratings are almost unreasonably conservative! Built-in forced air cooling ensures long life for all components.

Mark IB Preamplifier was designed for those who have, or intend to have, very complete audio installations.

"Stereo Review" October, 1975, says "When it comes to operating and control flexibility, the S.A.E. Mark IB has few peers."

The harmonic distortion, excluding hum which "was far below audibility" was 0.0075% at all frequencies up to 20,000Hz.



MA1

MA3

MA5

MA7

# Monitor Audio

MONITOR AUDIO is another new company. It has leapt to prominence in only two years. In the "Practical Hi Fi Audio" October 1975, comparison of ten loudspeakers including Spendor BCI, B & W DM4, Kef Cadenza, IMF Super Compact, the Monitor Audio MA5 Series 11 was chosen as best of all. Its very low colouration, sweet-sounding treble, openness, and light extended bass endeared it to the reviewers.

Similarly the tiny MA7 was chosen as the best of five speakers in a test conducted by "Popular Hi Fi" (June 1975) although it was the smallest and cheapest of the units tested.

At the top of the range is the mighty MA3 which retains the qualities that have established Monitor Audio at the pinnacle of loudspeaker design and manufacture, but combining these—possibly for the first time—with a power output which is awesome and a level of bass distortion which must set new standards.

"Practical Hi Fi and Audio" May 1975, measured the third harmonic distortion of the MA3 at 100 HZ at "close to 1 per cent" at 96dB sound pressure level. At the critical midrange the distortion is between 0.3% and 0.6%.

They go on to say "The first impression one gets when listening to the MA3 is one of physical presence, and this quality seems to be independent of the closeness of recording. This may be attributable to the exceptional smoothness of its midrange unit together with the use of a very analytical tweeter."

All we ask is that you give them a hearing.



# V.I.P

This is your special invitation to a full V.I.P. treatment at these selected Hi-Fi specialists throughout Australia. They guarantee you a personal hearing on our remarkable products.

**N.S.W.:** Kent Hi-Fi, 412 Kent St, Sydney.  
Hi-Tel Hi-Fi, Suptons Arcade, 541 High St,  
West Penrith.  
Hi-Fi House, Hurstville & Wollongong.  
Newcastle Hi-Fi, 642 Hunter St, Newcastle.  
Autel Systems Pty. Ltd.  
639 Pacific Hwy., Chatswood.

**VIC.:** Sound City, 360 Lonsdale St., Melbourne.


**QLD.:** Stereo Supplies, 95 Turbot St., Brisbane.

**W.A.:** The Audio Centre, 883 Wellington St., Perth

**TAS.:** United Electronics—Hobart, Launceston and  
Burnie.

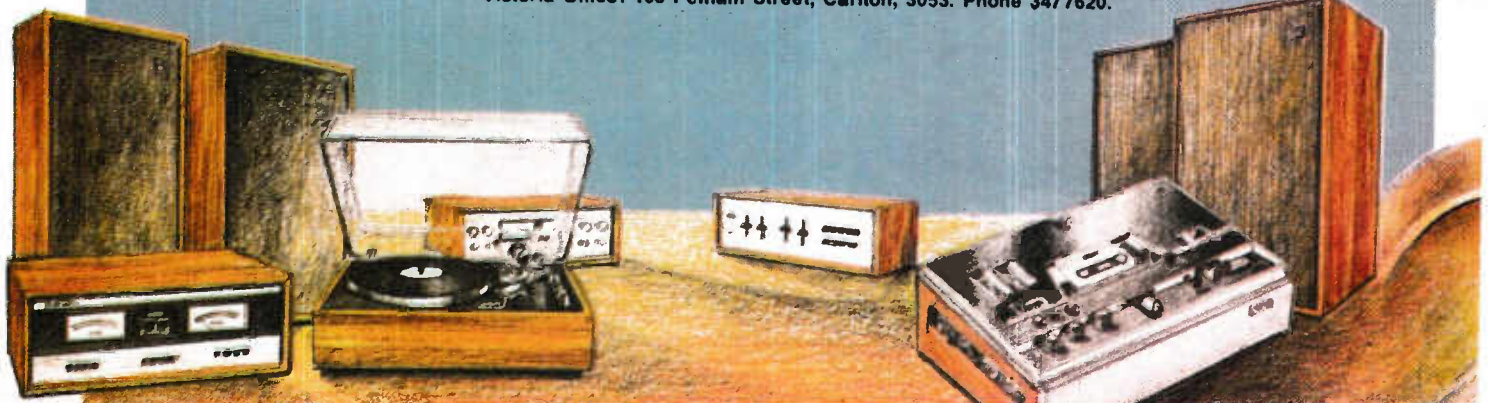 **LEROYA INDUSTRIES PTY**

Head Office: 156 Railway Pde., Leederville, Western Australia, 6007. Phone 81 2930.  
N.S.W. Office: 100 Walker Street, North Sydney, N.S.W. 2060. Phone 922 4037.  
Victoria Office: 103 Pelham Street, Carlton, 3053. Phone 347 7620.





# SALE

Saturday 19th JUNE

Over \$5000 worth of discontinued Electronic Equipment — Both brand new and used.

Most below cost —  
Up to 80% off normal trade price.

ALL MUST GO — Highest offers accepted. Be early for best deals.

Car Radio's — Stereo's — Test Equipment — Transceivers — Receivers — Aerials — Amps — Cassette units — Semi conductors — Components and many more.

9.00 AM TO 12 NOON

In Car Park

(Next door to Dick Smith's)  
160 Pacific Hwy. Gore Hill.

*NOLAN ENERGY WORKS*

## BURGLAR ALARMS

### WE STOCK:

Alarm Modules, Electronic Eyes, Photo Sensitive Cells, Microwave, Ultra Sonics, Gas/Heat/Smoke Sensors, Sirens, Bells, Pressure Mats, Door Monitors, Car/Caravan/Home/Office Hold Up Factory Alarms, Key Switches, Reed Switches, Relays, Shock Recorders, Aluminium Tape. You Name It. We Have It.

DO IT YOURSELF PRE-WIRED SYSTEMS EASY INSTALLATION.

### PORTABLE ALARMS

Microwave Systems concealed In Hi-Fi Speaker Enclosures or Desk Units, Mains Operated, Fully Automatic, Self-Resetting with battery standby.

Send 80c in Stamps for Illustrated Catalogue.

N.S.W. AGENT FOR NIDAC  
SOLID STATE SECURITY  
SYSTEMS

WHOLESALE SECURITY FROM

## PROTECTOR R.C. ALARMS

119-121 Pittwater Rd, MANLY  
N.S.W. 2095 PH: 977-6433

## HAM RADIO ELECTRONICS BARGAIN CENTRE

390 Bridge Road, Richmond, Vic.  
42-5174

Please allow for postage & packing when ordering by mail

Plenty of BARGAINS for the Radio Amateur or the Hobbyist.

2N3055 TRANSISTORS \$1 each  
58 ohm COAX CABLE 100 yd Rolls,  
1/8" diam. \$12 roll P&P \$1.75

52 ohm COAX CABLE 1/4" diam. 45c  
yd, 50c metre.

DOW KEY COAXIAL RELAYS 48 volt  
D.C. operation \$15 P&P 75c.

3 "N" TYPE CONNECTORS to suit  
above \$5


SPLIT STATOR CAPACITORS with  
screwdriver slot drive, 9 pF, 17 pF or  
25 pF. Brand new Eddystone type \$3  
each P&P 75c

SONAR SLIDER POTENTIOMETERS,  
2 7/8" x 3/8" x 3/8". Available in  
500 OHM, 20K, 25K, 100K, 500K  
and 1 MEC. 65c each or 10 for \$5.00  
P&P \$1.00.

CAR EXTENSION SPEAKER  
CONTROLS. Use both speakers  
together or separately. \$1.50 P&P  
30c.

JACKSON SLOW MOTION DRIVES  
6:1 ratio \$2.30 P&P 30c.

### THIS MONTH'S SPECIAL

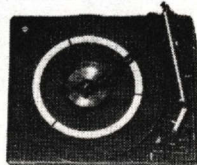

B.S.R. C129A  
STEREO  
RECORD  
CHANGERS

3 speed automatic fitted with good  
quality ceramic cartridge, adjustable  
arm weight, cueing lever, etc. 240V AC  
operation.

\$31.95 + \$3.50 post.

"PHILIPS" TYPE CONCENTRIC  
TRIMMER CAPACITORS  
with threaded stud for easy mounting  
25c each or 10 for \$2.00

"ZEPHYR" 2K ROCKING  
ARMATURE MICROPHONES  
desk type with P.T.T. switch in base.  
\$15.00 each.

NEW EX-ARMY MORSE KEYS  
Adjustable with metal cover enclosing  
moving parts.  
\$3.00 each.

NEW 4 TRACK STEREO CARTRIDGE  
PLAYERS. 5 watts output 12V D.C.  
operation. In sealed carton. \$15. P&P  
\$2.50.

6ft 240V AC POWER CORDS with  
moulded 3 pin plug 75c each or 10  
for \$6.50

STEREO TONE ARMS complete with  
ceramic cartridge \$5.90 each P&P  
30c.

EDGEWISE 0-1 mA METERS 2 1/2" x 1/2"  
face 3" deep calibrated 0-5 \$3 P&P  
75c

RF AMPLIFIER AM 4306/GRC  
Originally used in conjunction with  
PRC25 which covers 30-75 MHz FM.  
Requires 1-4 watts drive and gives a  
nominal 25 watts out. Brand new in  
sealed box. \$19 each \$3.50 p&p

MAIL ORDERS WELCOMED. Please  
allow pack and post items listed on this  
page, if further information required  
send a stamped S.A.E. for immediate  
reply from the above address.

## M. J. NEILSON AUDIO (SALES)

### POST FREE

SPECIAL INTRODUCTORY OFFER  
Sergeant TR 3M AM-FM pocket radios

features:

separate AM & FM tuner sections

455 KHz AM IF stage

10.7MHz FM IF stage

telescopic FM aerial

inbuilt ferrite rod AM aerial

complete with battery, earpiece

and carrying strap

very solid 'military style' case

overall dimensions:

1.3 X 8.3 X 4.3 cms

only \$13.00

The very popular high quality HITACHI  
range of blank cassettes.

	1-11	12-35	36+
C 60	1.50	1.35	1.25
C 90	1.85	1.75	1.65
C 120	2.40	2.25	2.15
UDC 60	2.00	1.90	1.80
UDC 90	2.35	2.25	2.15
UDC 120	3.15	3.00	2.80
UDR 60	2.35	2.25	2.15
UDR 90	3.00	2.80	2.65

Minimum order \$5.00. For any enquiries, please  
phone Murray Neilson (03) 819 8291 or send SAE.

P.O. Box 133 Hawthorn, Vic., 3122.

## Logan Brae Audio Sales

### PRICES DOWN! — RANGE UP!

HITACHI	less than 12	12 off	36 off
C90	\$1.75 ea	\$1.60 ea	\$1.50 ea
C120	\$2.30	\$2.10	\$2.00
UDC90	\$2.25	\$2.10	\$2.00
UDC120	\$3.05	\$2.80	\$2.65
UDRC60	\$2.25	\$2.10	\$2.00
UDRC90	\$2.85	\$2.65	\$2.55


BASF CRO2	C90SM	SONY	
C60	\$1.45	\$1.30	\$1.20
C90	\$1.85	\$1.70	\$1.60

Quantity discount applies to mixed  
orders. Ring or write for prices on larger  
orders

Clearance Sale: Genac Ultra Hi-Fidelity.  
\$1 ea.

POSTAGE: Up to 6, 60c or \$1.20  
airmail or N.S.W. \$1.20 plus 10c per  
doz. Vic., S.A., Qld., \$1.75 plus 25c  
per doz. W.A., Tas., N.T., \$1.90 plus  
40c per doz.

### RAMBLER ELECTRONIC CLOCK RADIO

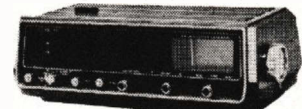

FEATURES: L.E.D. Display-Dimmer,  
Hour-Min-Sec AM/PM, Sleep timer —  
1-59 mins, 9 min snooze switch, power  
interruption warning, RADIO  
FEATURES: AM/FM Tone Control,  
Wide spread dial, good tone &  
sensitivity.

3 MONTHS GUARANTEE  
\$53 NSW. \$54 Interstate (post. incl).

P.O. Box 24, Carlton, NSW 2218  
Please send SAE with enquiries  
Telephone (02) 587-3475



## BROADCAST ENGINEER/ SENIOR TECHNICIAN/ TECHNICIAN

Radio 2UE Sydney wishes to make additional appointments to its technical staff. The positions will be filled by individuals seeking to further their careers and who can work accurately and with initiative in meeting the station's technical requirements.

Duties will cover all aspects of commercial radio operation and experience in this or an associated industry is important.

A BOCIP is essential and a higher qualification would be desirable.

An attractive salary will be negotiated to obtain the right men.

Working conditions are good and a superannuation scheme is available.

Applications in confidence stating experience and background to: -

The Manager,  
Radio 2UE Sydney Pty. Ltd.,  
Box 950,  
North Sydney 2060.

# TOP PROJECTS

VOL. 3 from Electronics Today.

Latest volume in our series of project books - Reprints of some of the most popular projects from recent issues - FM tuner, 25 watt amplifier, ET1 400 speaker system, Colour organ, Frequency counter, Digital voltmeter, Radar intruder alarm and more.

Available at all newsagents or direct from our Subscriptions Department, Modern Magazines (Holdings) Ltd, 15 Boundary Street, Rushcutters Bay, NSW 2011.




\$2.50  
(plus 40 cents postage)



A Modern Magazines Publication.
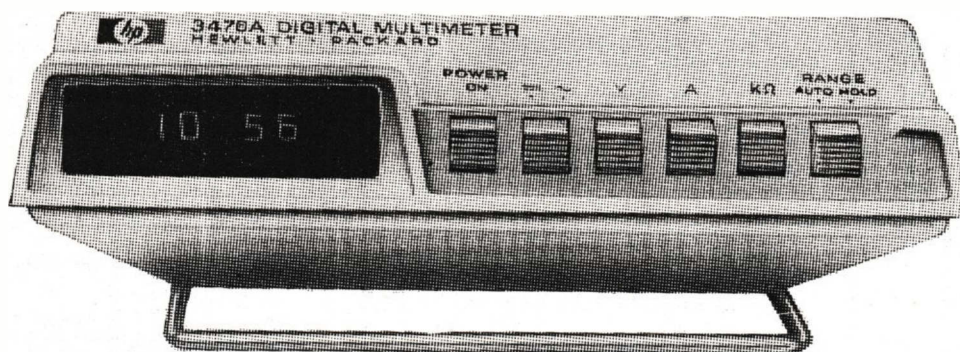
## Autoranging 5-Function Multimeter for \$209



- Auto-ranging with range hold button
- dcV, acV, dcA, acA, ohms
- All functions fuse protected at input
- Weight a low 770 grams for field portability
- Wide range of probe/carrying case accessories available
- 3476A - mains only; 3476B - mains and Ni Cd battery.
- ★ 3476A is \$209 Duty Free or \$261 Duty Paid. Batteries \$47 extra (or \$58 including Duty). Prices valid as at 28/1/76.

For data sheets/quotations on the 3476A phone your nearest HP office.

- ADELAIDE 272 5911
- BRISBANE 229 1544
- CANBERRA 95 3733
- MELBOURNE 89 6351
- PERTH 86 5455
- SYDNEY 449 6566

HEWLETT  PACKARD

906013



# NATIONAL RADIO SUPPLIES

332 Parramatta Road Stanmore 2048 Ph. 567398.

STEREO RADIOGRAM  
FM-AM - 3 piece



**SPECIAL  
AT  
\$49.00**

## ELECTRONIC CLOCK RADIO

AM-FM with alarm-seconds-snooze-sleep control.



**SPECIAL  
\$40.00**

## AUTO EJECT CASSETTE CAR STEREO

- 4-IC Circuit
- Fast Forward & Fast Rewind
- Auto Eject
- Indicator Light
- Separate Tone, Volume & Balance Controls
- 9 Watts Output

Four Star - 12 mths Warranty



**\$69.00 with Speakers**

### BASF TAPES

C 60 LHSM \$1.80  
C 90 LHSM \$2.00  
C 120 LHSM \$2.80

## SPECIAL

Yokes 110 Philips  
few at \$8.50  
3101 EHT \$9.00

### VALVES GALORE

- Cheaper than ever.

6X9 - \$1.20 6SN7 - \$1.00  
6U9 - \$1.20 6IN8 - \$1.30  
IS2 - \$1.00 6AL3 - \$1.15  
6DX8 - \$1.20 6U7 - 30c  
6GW8 - \$1.10 807 - 80c  
6Y9 - \$1.50 6BM8 - \$1.10 6K8 - \$1.00

### POWER PACKS

240V - 6-9V  
300ma - \$6.90  
Suitable for radio,  
calculator, etc.  
Eliminates battery  
costs.

## PACK SPECIALS AT LAST YEARS PRICES

**SPECIAL**  
C60 LHSM \$1.80  
C90 LHSM \$2.00  
C120 LHSM \$2.80

**POLYESTER PACK**  
Mixed 50 at \$2.00

**CERAMIC CONDENSOR PACK**  
100 for \$2.50

**RESISTOR WIRE-WOUND PACK**  
50 for \$5.00 - 3 & 5 & 10 watt

**MICA PACKS**  
50 for \$3.00 - 20 for \$1.80

**POTENTIOMETER PACK**  
20 for \$2.50

**DOUBLE POTENTIOMETER  
PACK**  
10 for \$4.00

**RESISTOR PACK**  
100 for \$1.50

**7 Transistor RADIO SPECIAL**  
with speaker and printed board.  
Ready to go.  
Only \$4.50

**STEREO FM-AM TUNER**  
FM 88 - 105 MC  
Complete in wood case  
\$62.00

**ELECTRIC CAR AERIAL**  
Complete, ready for installation.  
\$18.00

**T.V. BALUN**  
300 ohms to 75 ohms 80c ea.

**TRANSISTOR SPECIALS**  
MJ3055 eqv. 2N3055  
60c ea. or 10 for \$5.00

**TRANSISTOR SPECIALS**  
BC147, BC148, BC149  
10 mixed for \$1.20

**BRIDGE RECTIFIER**  
3.8 AMP 100v \$1.80  
25 AMP 200v \$3.50

**BATTERY ALLIGATOR CLIPS**  
Heavy Duty 50 AMP  
10 for \$5.00

**SPEAKER TRANSFORMERS**  
10k - 3.5 ohms - 7k - 15 ohms  
\$1.20 ea. or 10 for \$10.00

**VIBRATORS**  
6v 5211 A.W.A.  
still only \$1.00 each.

PLEASE INCLUDE 20% OF ORDER TO COVER POSTAGE & PACKING. C.O.D. IF NEEDED. ALL EXCESS POSTAGE REFUNDED.

## READERS' LETTERS

We make no charge for replying to readers' letters, however readers must enclose a foolscap-size stamped addressed envelope if a reply is required. Queries concerning projects can only be answered if the queries relate to the project as published. We cannot assist readers who have modified or wish to modify a project in any way, nor those who have used components other than those specified.

## TELEPHONE QUERIES

We regret that we cannot answer readers' queries by telephone.

## SUBSCRIPTIONS

Electronics Today International can be obtained directly from the publishers for \$14.00 per year (including postage) within Australia.

The cost for countries outside Australia is \$14.65 including postage (surface mail). Airmail rates will be quoted on application. Subscription orders and enquiries should be sent to the address below.

## BACK ISSUES

Our subscriptions dept can supply most back issues of ETI for the twelve months preceding the date of this current issue. Some earlier issues are also available.

The price of back copies is currently \$1.00, plus 40 cents postage and packing. Please address orders to Subscriptions Dept, Electronics Today, 15 Boundary St, Rushcutters Bay, NSW 2011.

## PHOTOSTATS

Photostats of any article ever published in ETI can be obtained from our subscription dept (address above). The price is currently 45 cents per page including postage.

## CONTRIBUTORS

Material is accepted from time to time from outside contributors. Payment is based on quality and is paid 30 days after the date of publication. Constructional projects will be considered for publication but the standard of design must be to fully professional level. All material must be typed using double spacing and wide margins. Drawings, circuit diagrams etc need not be to professional standards as they will be redrawn by our staff. It is advisable to contact the Editor before submitting copy.

A large stamped addressed envelope must be included if unsolicited material is required to be returned.

## ADVERTISING QUERIES

Queries concerning goods advertised in ETI should be addressed directly to the advertiser — not to ourselves.

## NEWS DIGEST

News Digest items are published free of charge. Manufacturers and importers should send material at least four weeks before the date of publication. Photographs should be of high contrast and preferably at least 100 by 150 mm. Press releases must be of a factual nature — these pages are not free advertising. The Editor reserves the right to accept or reject material at his discretion. Preference will be given to components and equipment of an essentially practical nature.

## BINDERS

Binders to hold 12 issues of ETI are available from our subscription dept (address above). Price is \$4.50 (plus 80 cents postage NSW & ACT — or \$1.50 all other States)

## COPYRIGHT

The contents of Electronics Today International and associated publications is fully protected by international copyright under the terms of the Commonwealth Copyright Act (1968).

Copyright extends to all written material, photographs, drawings, circuit diagrams and printed circuit boards reproduced in our various publications. Although any form of reproduction is technically a breach of copyright, in practice we are not concerned about private individuals constructing one or more projects for their own private use, nor by pop groups (for example) constructing one or more items for use in connection with their performances.

Commercial organisations should note however that no project or part project described in Electronics Today International or associated publications may be offered for sale, or sold, in substantially or fully assembled form, unless a licence has been specifically obtained so to do from the publishers, Modern Magazines (Holdings) Ltd or from the copyright holders.

Akai .....	32
Allied Capacitors .....	107
A.M.I. — TEAC .....	14
Applied Technology .....	68-69
A & R Sonar .....	108
Audio Engineers .....	33
Aust. Film & TV School .....	100
Autotronics .....	62
AWA .....	25
BWD .....	106
Chan Merchandising .....	97
Convoy .....	7,8,9,10
Dick Smith .....	94-95
Edge Electrix .....	26
Electronic Agencies .....	66
Electronic Disposals .....	101
Emona .....	91
Ferguson Transformers .....	103
Fidelity Services .....	103
George Hawthorn .....	108
Haco .....	2,105
Ham Radio .....	83,115
Harman .....	4,82
Hewlett Packard .....	116
I.C.S. ....	62
Inter. Dynamics .....	27,40,80,120
Inter. Electronics Unlimited .....	102
John Carr .....	39
J.R. Publications .....	107
Kent Hi-Fi .....	98
K.D. Fisher .....	79
Lafayette .....	99
Leroya .....	111-114
Logan Brae .....	115
Luke Electrics .....	14
Magnecord .....	57,70
M.J. Neilson .....	115
M.S. Components .....	50
National Radio .....	117
Nebula .....	57
Nolan Energy Works .....	115
Parameters .....	28
Philips Elcoma .....	59,65,81
Photimport .....	38,43
Pioneer .....	12,119
Pre Pak .....	62
Protector Alarm Systems .....	115
Radio 2UE .....	116
Radio Parts .....	28
Record & Tape Service .....	62
R.H. Cunningham .....	15
Sabtronics .....	93
Scope Laboratories .....	41
Star Delta .....	104
Video Hi-Fi .....	63
Weston Electronics .....	37
WHK .....	42

## ADVERTISING

Sydney: Terry Marsden (Manager),  
15 Boundary St., Rushcutters Bay, 2011.  
Tel 33-4282.

Melbourne: Clarrie Levy, Suite 24,  
553 St. Kilda Rd, Melbourne. Tel 51-9836.

Brisbane: David Wood, 11-14 Buchanan  
St, West End, Brisbane. Tel 44-3485

Adelaide: Ad Media Group, 68 North Terrace,  
Kent Town, 5067. 42-4858.

Perth: Aubrey Barker,  
38 Mounts Bay Rd. Tel 22-3184.

London: Electronics Today International, 36  
Ebury St, SW1 WOLW Tel 01-730 8282.

Electronics Today International is published  
by Modern Magazines (Holdings) Ltd, 15  
Boundary St, Rushcutters Bay, NSW 2011. It  
is printed (in 1976) by Wilke & Co Browns  
Road, Clayton, Vic and distributed by  
Australian Consolidated Press.  
\*Recommended price only. Copyright.



# Play with a loaded deck.



Packed with features from front to back, Pioneer's new CT-F9191 cassette deck stacks all the cards in your favor. A balanced combination of precision and convenience created by Pioneer to beat even the best reel-to-reel decks at their own game.

The CT-F9191 starts out by delivering top performance via access to the front. A newly designed tape carriage employs hexagonal reel shafts plus twin-link stays. The cassette is completely visible for checking tape movement and direction (a Pioneer exclusive). And since there's no rattle-prone ejection mechanism, changing tapes is a "snap."

In the CT-F9191, two motors provide the key to stable tape transport. An electronically controlled DC motor with built-in generator guarantees accurate record/play tape speed. A

second motor for high speed fast-forward and rewind. As a result, wow and flutter is no more than 0.07% and speed deviation is precise within  $\pm 1.0\%$ .

Next, a high-performance ferrite-solid head and a built-in Dolby\* Type-B noise reduction system join to increase the S/N ratio to more than 62dB.

Operating the CT-F9191 is easy. Feather-touch user-oriented controls activate solenoid circuits thereby eliminating inconvenient mechanical linkages. After that, an advanced Memory Rewind device permits quick location and playback from any point on a prerecorded tape automatically. There is an automatic chrome-tape detector plus separate BIAS and EQ selection. And for making music tapes with wide dynamic range, an LED peak level indicator reacts instantly to warn of any distortion +5dB over the

reference level.

Next in the series, the CT-F7171, 6161 and 2121. Created for those who want to play, but with a deck that's loaded slightly less. Of course, the stakes are lower as well.

Pioneer's new front-loading cassette decks. A full house of outstanding features. No matter how you play them, you'll wind up with a winning hand in every suit.

Pioneer Electronics Australia Pty. Ltd.  
178-184 Boundary Road, Braeside, Victoria  
3195, Phone: 90-9011, Sydney 93-0246,  
Brisbane 52-8213, Adelaide 433379,  
Perth 76-7776

 **PIONEER**  
leads the world in sound.

\*Dolby is a trademark of Dolby Laboratories, Inc.



# We built a good big sound that doesn't need a \$4,000 amp. to get there. (But which won't waste it if you've already got one.)

Today's popular, low-efficiency speakers require about 50 watts per channel to deliver lifelike sound levels. Even our Formula 2 will deliver that same sound level with only 25 watts; the Formula 4 with 20 watts and Formula 6 with only 9 watts.

B.I.C. Venturi can handle lots of power, too. Feed a typical low efficiency speaker more than about 50 watts, and you're likely to push it into distortion — even self-destruction!

With B.I.C. Venturi you can turn up the power, without distortion or speaker damage. Even our compact Formula 2 can safely handle 75 watts per channel.

Formula 6 — 125 watts!  
So much for the loud. With

most speakers, turn down the volume slowly and you reach a point where the sound suddenly fades out.

That's where our Dynamic Tonal Balance Compensation circuit (pat. pending) takes over. As the volume goes down it adjusts frequency response, automatically, to compensate for the ear's deficiencies. The result: aurally "flat" response, always!

Sole Australian distributors: International Dynamics (Agencies) Pty. Ltd., 23 Elma Rd., North Cheltenham, 3192. Melbourne. 95-1280.

Available from: N.S.W.: M & G Hoskins Pty. Ltd., (Showroom) 400 Kent St., Sydney 2000, Telephone: 559-4545 & 559-3693. Qld: Stereo Supplies, 95 Turbot St, Brisbane 4000, Telephone: 21-3623. S.A.: Challenge Hi-Fi, 96 Pirie St, Adelaide 5000, Telephone: 223-3599. Tas.: Audio Wholesalers Pty. Ltd., 9 Wilson St, Burnie 7320, Telephone: 314111. Vic.: Encel Electronics Pty. Ltd., 431 Bridge Road, Richmond, 3121, Telephone: 42-3761. W.A.: Albert TV & Hi Fi, 282 Hay St., Perth 6000, Telephone: 25-2699. A.C.T.: Duratone Hi Fi, Cnr. Botany St. & Atree Crt, Phillip 2606, Telephone: 82-1388.



**WE TOOK THE TROUBLE TO FIND OUT  
WHAT YOU REALLY WANTED. THEN WE  
BUILT IT, FROM THE GROUND UP.**



BIC-4