

MOTOR — STARTING Capacitors

● AEROVOX pioneered the motor-starting capacitor. Literally millions of these units are in daily use in electric refrigerators, oil-burners and other household appliances. And AEROVOX continues its leadership by making available the most complete line of motor-starting capacitors.

To the serviceman and others concerned with proper motor-starting capacitor replacements, AEROVOX offers a three-point service:

CATALOG . . .

● Your AEROVOX jobber has a handy wall chart listing all types of standard capacitor-start motors and their replacement capacitors. Look for that chart the next time you visit your jobber. Meanwhile, for your own convenience, be sure you have the latest catalog or supplement so you can estimate repair costs right on the job. Ask the jobber—or write for it.

CHART . . .

● There is at least one jobber within easy reach who carries a representative stock of AEROVOX motor-starting replacement capacitors. Look him up for your convenience in making prompt repairs. Or have us send you the name and address of the nearest jobber who carries an adequate stock of these items. Remember, new numbers are added just as capably as popular demand develops.

STOCK . . .

● Electrolytic or oil-filled; any style container; any kind of terminals; any mounting arrangement — the AEROVOX line has just the right unit for any standard capacitor-starting motor.

● Up to the minute catalogs and supplements listing all popular type capacitor-start motors and their corresponding replacement capacitors. One glance at the motor name plate for essential reference data, and you can find the correct replacement capacitor in the handy AEROVOX listings. So get your copy from your jobber—or write us direct.



AEROVOX CORPORATION
New Bedford, Mass.

Sales Offices in All Principal Cities



Radio Editors of magazines and newspapers are hereby given permission to reprint in whole or in part, with proper credit to the Aerovox Corporation, the contents of this issue of the Aerovox Research Worker.

The AEROVOX

Research Worker

The Aerovox Research Worker is a monthly house organ of the Aerovox Corporation. It is published to bring to the Radio Experimenters and Engineers authoritative, first hand information on condensers and resistances for radio work.

VOL. 10, NOS. 11 and 12

NOVEMBER-DECEMBER, 1938

10c per year in U.S.A.
60c per year in Canada

USEFUL DATA FOR THE PRACTICAL RADIO MAN

PART I

By the Engineering Department



In this combined November-December 1938 issue, we reprint, in response to many requests, charts and pertinent information which has been published during the past few years. The second part of the paper will appear in the January-February 1939 issue of the Research Worker.

AEROVOX PRODUCTS ARE BUILT BETTER

Printed in U. S. A.

Copyright 1938 by Aerovox Corporation

TO FIND CAPACITY AND POWER FACTOR AT 110V.-60 CYCLES From Ammeter, Wattmeter Readings

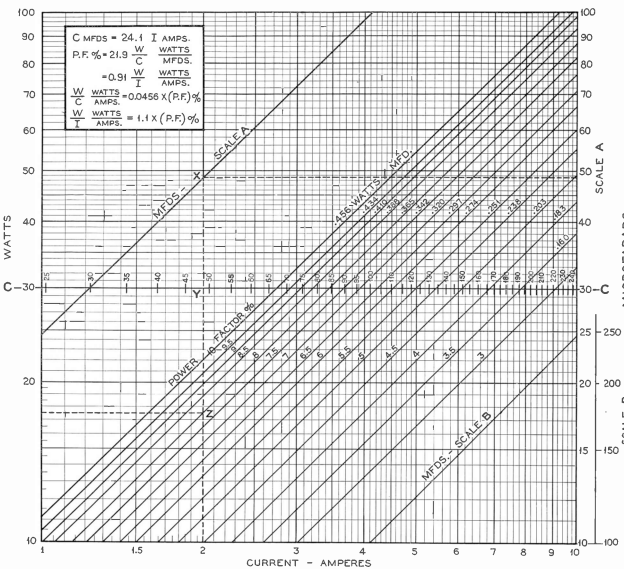


Figure 1

For 110 volt motor-starting condensers the chart of Figure 1 permits the rapid determination of capacitance and power factor when the ammeter, voltmeter, wattmeter readings have been made. It will also show the capacity from voltmeter and ammeter readings alone.

The use of the chart is as follows. It is assumed that all measurements are taken at 110 volts, 60 cycles. Then, reading the current, find the value of the current on the bottom scale, marked "amperes", follow the vertical line upwards until it intersects the line "A" or "B" marked "watts", and follow the horizontal line to the right reading the capacity at the right. The capacity can also be found directly also the corresponding current on the line "C-C".

To find the power factor from the wattmeter and ammeter readings, draw a horizontal line from the power scale at the left and vertical line from the amperes scale at the bottom.

Read the power factor at the intersection of the two lines. The capacitance is found from the ammeter reading as before.

Example: To find the capacity when the ammeter shows 2 amperes. At 2 on the current scale, follow the vertical line upwards to its intersection "X" with the line marked "watts scale A"; then follow the horizontal line towards the right and read the capacity on the right hand scale—16 mfds. The same can also be found at Y on the C-C scale.

To find the power factor of a condenser which draws 2 amperes and 17.5 watts from the 110 volt line. At 17.5 on the power scale draw a horizontal line. This intersects the vertical line erected at 2 on the current scale at the point Z. This point is situated on the line corresponding to 0.8 percent power factor.

The same problem can also be worked backwards; that is, when the capacity is given the current can be found from the chart and

when the power factor and the capacity are known, both meter readings can be predicted.

Example: Required to find the current drawn by a 200 mfds. condenser from a 110 volt line. Find 200 on the capacity scale B, follow the horizontal line to the left until its intersection with the oblique line marked "watts scale B"; then follow the vertical line down and read 8.2 amperes. Note: The current is 41 ma. per mfds. when a condenser is connected across a 110 volt 60 cycle line.

If the same condenser had a power factor of 3.5 percent, what would be the power indicated by a wattmeter? Follow the vertical line at 8.2 amperes until it crosses the 3.5 percent power factor line, then follow the horizontal line to the left and read 32 watts. The chart can be used for any other voltage. E. If both the power and the current scale are multiplied by the factor E/110.

Reprinted from The Research Worker, February 1938

CHOKE INPUT FILTER

	HALF WAVE Fig. 12	FULL WAVE Fig. 11	BRIDGE CIRCUIT Fig. 14	VOLTAGE DOUBLING Fig. 15
E_{ac} (av)	0.455 E_{ac}	0.455 E_{ac}	0.909 E_{ac}	—
I_{ac}	0.318 I_{ac}	1.41 I_{ac}	1.41 I_{ac}	—
E_{ac} (max.)	1.41 E_{ac}	0.707 E_{ac}	1.41 E_{ac}	2.83 E_{ac}
E_{ac} per plate	E_{ac}	0.5 E_{ac}	0.5 E_{ac}	E_{ac}
E inverse max.	2.83 E_{ac}	1.41 E_{ac}	1.41 E_{ac}	2.83 E_{ac}
I_{ac} per tube	I_{ac}	0.707 I_{ac}	0.707 I_{ac}	1.41 I_{ac}
I max. per tube	I_{ac}	I_{ac}	I_{ac}	I_{ac}
Sec. kva.	1.57 $E_{ac} I_{ac}$	1.57 $E_{ac} I_{ac}$	1.11 $E_{ac} I_{ac}$	1.11 $E_{ac} I_{ac}$
Pri. kva.	1.57 $E_{ac} I_{ac}$	1.1 $E_{ac} I_{ac}$	1.11 $E_{ac} I_{ac}$	1.1 $E_{ac} I_{ac}$
Ripple freq.	f.	2f.	2f.	2f.
Ripple voltage rms.	—	0.847 E_{ac}	0.471 E_{ac}	—

The study of receiver power supplies consists of two parts—the rectifier and the filter. These two parts must be studied jointly and they are interdependent. The action of the rectifier depends on the load into which it works, while the filter required for any particular application depends on the rectifier used and character of output required. There are four different types of rectifier circuits that may be used for receiver power supplies; the half wave rectifier, full wave rectifier, bridge type rectifier and voltage doubling type rectifier. Each has a definite field of application. Voltage characteristics of each are shown in the table. In the analyses of receiver power supplies, the following features must be taken into account:

E_{ac} —Transformer Secondary Voltage.

1. Output voltage required
2. Allowable ripple voltage
3. Static and dynamic regulation of the supply
4. Peak voltages across the condensers of the system

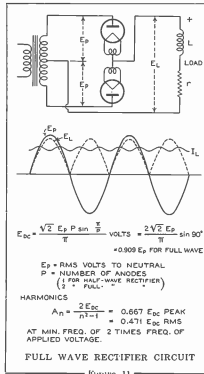


Figure 11

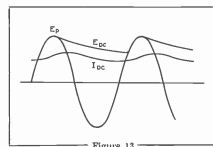


Figure 13

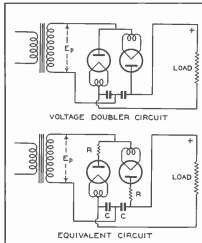


Figure 15

These various features depend on the type of circuit used and the constants of the circuit.

The curves of Figures 7, 9 and 10 are plotted for a DC voltage output of 100 volts with current as abscissa and the peak AC voltage as ordinates. The curves of Figure 7 are plotted for zero tube drop and must be corrected for the tube used and the tube current to obtain the AC voltage required to deliver 100 volts DC. The correction is made by finding the DC voltage drop in the tube used, from the curves of Figure 5 multiplying by 1.5708, the ratio of the peak voltage to the average value of a half sine-wave, and adding this voltage drop to the ordinate of curve 7. This value, when divided by 1.41 gives the RMS plate voltage to deliver 100 volts DC into the filter. To obtain any other DC voltage, the AC voltage must be multiplied by the ratio of the desired DC voltage to 100 volts.

Reprinted from The Research Worker, August-September 1933

AVERAGE PLATE CHARACTERISTICS OF RECTIFIERS

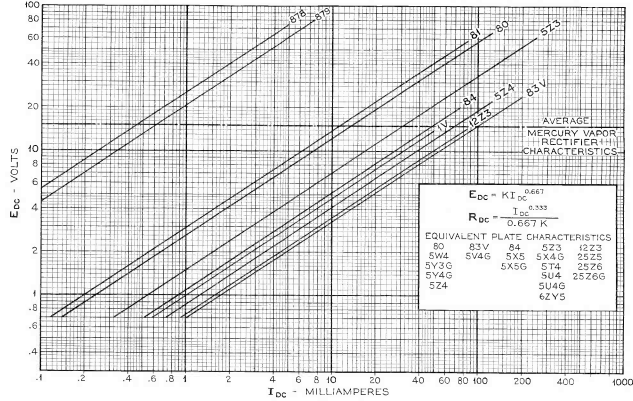


Figure 5

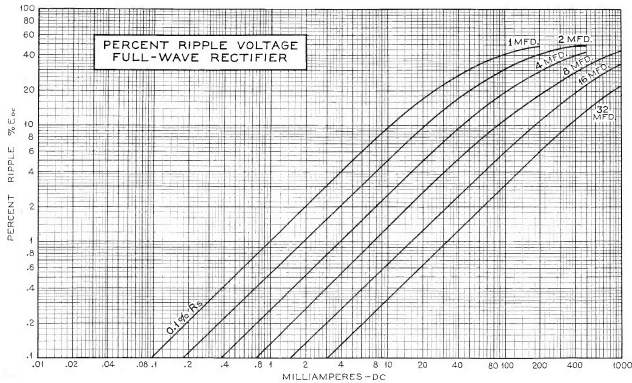


Figure 6

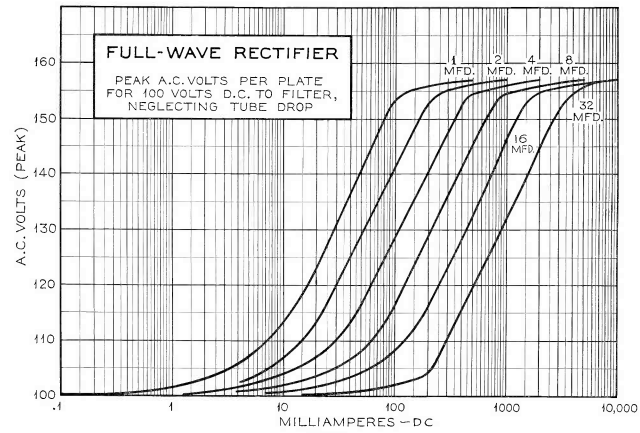


Figure 7

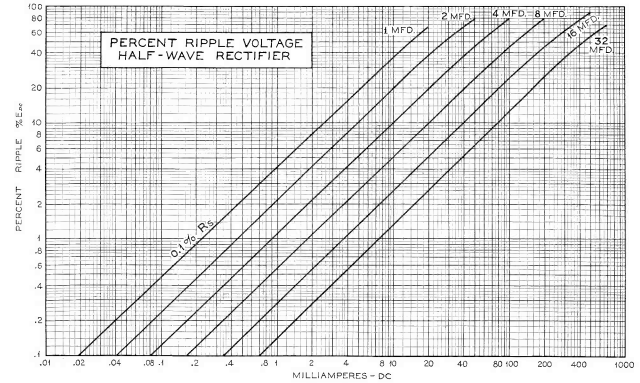


Figure 8