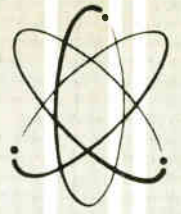




Techni-talk



COMPLETE ELECTRONIC SERVICING INFORMATION
radio • tv • hi-fi

VOL. 12 No. 2

MAR.-MAY, 1960

GE WIRELESS REMOTE CONTROL SYSTEM II

The transmitter portion of the General Electric remote control system was described in the last issue. In this issue the receiver circuits will be discussed. A block diagram of the wireless remote receiver is shown in Fig. 1 and the schematic in Fig. 2.

Receiver Circuit Analysis

The remote receiver utilizes two receiver type vacuum tubes in conventional circuitry. A ferrite rod antenna, mounted with the receiver unit, incorporates a variable trimmer capacitor for means of tuning the antenna circuit.

The signal, having been picked up by the antenna assembly, is amplified by a tuned r-f stage using a 6EW6 pentode as an amplifier. The amplified r-f signal is coupled to the triode section of a 6EA8 by means of a high "Q" double tuned interstage transformer. The triode acts as a bias detector and since limiting must also be accomplished by the triode, a sensitivity control (R605) is used in the plate circuit. This control allows the plate voltage of the triode to be adjusted so that plate saturation will occur with a predetermined amplitude of input signal to the receiver.

After detection, the audio signal is amplified and further limited by a power amplifier stage, using the pentode section of the 6EA8, and is then applied across the coil of the reed relay assembly. The applied audio signal causes a magnetic field to be developed in the relay coil which is modulated at an audio rate.

Metal Reeds

Since the metal reeds are located within the magnetic field of the coil, one of the reeds whose resonant frequency corresponds to the selected audio frequency, is made to vibrate. Each of the four reeds, in the reed assembly, is resonant to a different frequency, 30cps apart, therefore each of the individual reeds corresponds to a different function of the remote system.

The reed contact points are connected to a corresponding sensitive relay coil, and when the system is idling the reed contact points are normally open. When the audio mod-

(Continued on page 11)

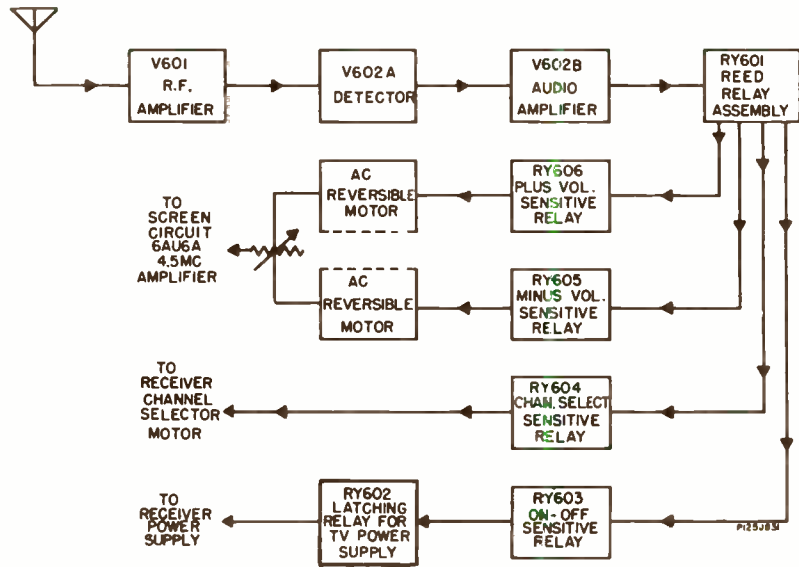


Fig. 1 Block Diagram of Remote Receiver



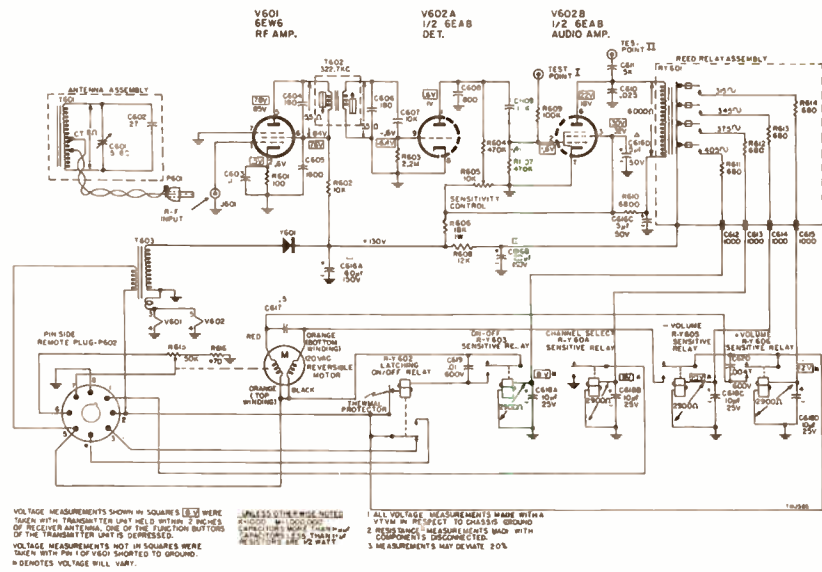


Fig. 2 Schematic Diagram of Remote Receiver

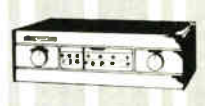

SUCCESSFUL SERVICE MANAGEMENT

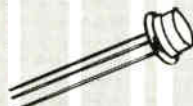

PLANNING FOR SUCCESS IN THE SOARING SIXTIES

By Andrew E. Kimball

Manager, Marketing Research, Receiving Tube Department
General Electric Company, Owensboro, Kentucky

The new decade has often been called "The Soaring Sixties". This is an appropriate description. The period should see spectacular developments leading to the most exciting and rewarding period in our history.

The long range future in the U.S. will be one of substantial economic growth and prosperity, with a few bumps but no major let-downs. This growth is soundly based on America's effective utilization of brains, manpower, materials and money plus a philosophy of investment for growth.

Perhaps the most spectacular growth industry of our time is electronics. The history of past growth will extend into the Sixties. We'll see continued growth and innovation in the consumer electronics field as well as the rapid development of new technologies in electronics for military, industrial, and space markets.

Today, electronics is the fifth largest industry in the U. S. In 1959, manufacturers produced \$9 billion worth of electronic goods. Distributing, serving and broadcasting revenues amounted to another \$5 billion, adding up to the impressive total of \$14 billion. This was over three times the total ten years ago. In the next ten years the industry should more than double again — to about \$30 billion.

Electronic Product Market

In the consumer electronics area, television will continue to be tremendously important. Inventions are expected to make color TV more economical and thus more widely used. Radical design changes may be expected as new types of screens become available. Radios will continue to be very important, with wrist-watch radios and transmitters a possibility.

Hi-fidelity phonographs will be even more widely used. New type recording devices to preserve both sound and picture of TV programs are possible consumer items. Electronic ovens, door openers, and electronic organs will become more popular consumer products. Electronic ignition systems for autos, plus electronic safety devices and traffic controls may well be in the sights of the Sixties. Even phonevision may become practical before many years go by — the combination of sight as well as voice in personal communication devices.

The following table illustrates the trend in the market of greatest interest to service dealers.

U.S. Service Market

TV Sets in use (millions)		
1955	1960	1965
32	52	65
Radio Sets in use (millions)		
116	137	160
Service & Parts Revenue (billions)		
\$2.1	\$2.5	\$3.0

The significant market growth facing service dealers presents both opportunities and challenges. Even in times of market growth, many businesses fail. This is a characteristic of our economy and is one of the conditions of our competitive free enterprise system which augments growth. The strongest and smartest competitors survive and the weakest firms with the least to offer die.

The servicing industry faces the challenge of increasing competitiveness within its own ranks. More than ever before, dealers will face this challenge. There will be plenty of opportunity in an enlarging market, but the greatest rewards will accrue to those who meet the challenge best.

Market Opportunities

A key to success in modern business is the ability and willingness to look ahead at the market opportunities, recognize the changing conditions and then set plans to be sure to earn a fair share of the market growth.

The successful service dealer will want to plan for improvement in technical skills. New products and new designs dictate a need for continuing self-development. Help is

provided by manufacturers, distributors, trade publications, technical books, and service associations.

The successful service dealer will want to plan for improvement in sales skills. He will want to learn how to develop his market — promote his business, attract new customers and keep them satisfied. These goals involve improvement in personal selling, in advertising and sales promotion, and customer relations abilities.

Improvement Areas

The successful service dealer will want to plan for improvement in business management skills, for example, better accounting systems, inventory control, expense control, hiring and training technicians, and generally running a more efficient and tighter shop. Recognition of service dealers desire to improve their own skills in business management and selling has prompted General Electric to provide our "Profitable Service Management" program.

The successful service dealer will want to plan for improvement in business practices. Pricing for profit is a key factor. The following three principles are important to remember in pricing for profit.

- Price fairly for both the customer and the dealer
- Price competitively
- Price so as to cover all costs (overhead, depreciation, materials, salaries) and provide an adequate return on money invested in the business.

The future should be exciting and rewarding — but the reward will be greatest for those who recognize the opportunities, accept the challenges, and convert them into *profitable* realities.

FULL LINE OF G-E AUDIO TUBES

A full line of General Electric audio tubes to deliver top performance in high-fidelity equipment is now available.

This audio tube line is termed a "break-through in performance," and includes eleven receiving tubes specifically designed to handle with top efficiency every tube function of high-fidelity equipment.

All tubes feature 3-ply (rectifiers) and 5-ply (power output) plate material.

The eleven tubes in General Electric's audio line are: 5AR4, 6BQ5, 6CA4, 6DZ7, 6L6GC, 7025, 7189A, 7247, 7355, 7408 and 7581.



G-E audio tubes deliver top performance in high-fidelity equipment.



Techni-talk

COMPLETE INDEX

Vol. 1, No. 1 through

Vol. 12, No. 2



	VOL.	No.		VOL.	No.
AFC Circuits			G-E Model 802, Capehart-Farnsworth Model 651P	3	3
“Horizontal” AFC Circuits	2	2	G-E Model 10C101, RCA Model KRS-20	3	4
AGC Circuits			G-E Model 910, RCA Model 630TS to 14 inch	3	5
Addition of A.G.C. to G-E 805 series T and S	2	4	G-E Model 815, Motorola Model VF-102	3	6
Correction for Overload “U2” Receivers	10	6	Motorola Model 12VT16	4	1
Video Detector, A.G.C. and Video Amplifier	1	5	RCA Model 630TS	4	2
Anti-Static Cleaner and Polish			D-C Restoration		
TV Anti-Static Cleaner and Polish	12	1	D-C Restoration and Sweep Circuits	1	6
Camera Tube			Easy Open-Easy Out Tube Carton		
New Super-Sensitive G-E Camera Tube GL-7629	11	6	New G-E Tube Carton	11	4
Capacitance-Resistance Bridge			Field Strength Meters		
How to Get the Most Out of Your Test Equipment — Capacitance-resistance Bridge	1	3	UHF Antenna Installations	6	4
Capacitor Substitution Boxes			Five Star Tubes		
Construction Details	2	6	Characteristics and Prototype Receiving Tube	11	4
Ceramic Tubes			G-E Service Policy Statement		
Type 7077	11	1	G-E TV Service Policy Statement	11	1
Color Box			Germanium Diodes		
Construction Details	6	2	Germanium Diodes in Video Detectors	2	3
Color TV			Horizontal Circuits		
Part I — Color Reproduction	5	6	D-C Restoration and Sweep Circuits	1	6
Part II — Construction of a Color Box	6	2	Deflection Waveforms and RF Supplies	2	3
Part III — Visible Spectrum and Chromaticity Charts	6	3	Excessive Width — “M4”	11	3
Part IV — Development of Color Signals	6	4	Excessive Width — “U2”	10	5
Part V — Color Signal Frequencies and Balanced Modulation	6	5	Horizontal AFC Systems	2	2
Part VI — Vectors	6	6	Horizontal Deflection Circuits and Kick-back Power Supplies	2	4
Part VII — Development of Chrominance Signal	7	1	Horizontal Jitter — “M4”	11	4
Part VIII — Color Signal Phase and Amplitude and Burst Signal	7	2	Horizontal Retrace Elimination Circuit	4	2
Part IX — Gamma Correction, Delay Lines and Block Diagram of Transmitter	7	3	Kill that Retrace — Horizontal	2	6
Part X — Aperture Mask and Post Acceleration Type Picture Tubes	8	2	Replacement Sweep Transformers	11	1
Color Receivers			How Electronic Components Are Made and Tested		
Part I — Tuner and Video 1-F Amplifiers	9	2	Birth of a TV Bulb	11	2
Part II — Video Detectors and Video Amplifiers Block Diagram and Schematic for General Electric “CL” Color Receiver	9	3	How G-E 110° Picture Tubes are Made	10	6
Part III — Burst Gate, Subcarrier Generation, Synchronous Detectors and Chroma Amplifiers	9	5	How G-E Picture Tube Phosphors are Made	12	2
Part IV — Matrixing Circuits and Aperture Mask Tube	10	1	How G-E Receiving Tubes are Tested	11	6
Part V — Mechanical Adjustments on Aperture Mask Tube	10	2	How G-E Semiconductors are Made	11	3
Part VI — Vertical Convergence System TV-Color-Horizontal Sync	11	5	How G-E Service Designed Tubes are Made	11	1
Conversion to Larger Picture Tubes			How G-E Transistors are Made	10	5
G-E Model 811, Admiral Model 4H16S	2	5	How to Build		
G-E Model 809, RCA Model 730TV2	2	6	Capacitor Substitution Boxes	2	6
G-E Model 820, Philco Model 48-1001	3	1	Color Box	6	2
G-E Model 12C101, Stromberg-Carlson Model TV-12	3	2	Complete Service Shop	8	4
			Picture Tube Tester	5	1
			Resistor Substitution Boxes	2	5
			Service Bench	3	1
			Transistor Tester	10	6
			Hum or Buzz		
			Hum or Buzz in TV Receivers I	11	6
			Hum or Buzz in TV Receivers III	12	1
			Stereo Hum Problem	11	1, 2, 3, 4, 5
			Sync Buzz — “U-2”	11	1

	VOL. No.
Indian Head Test Pattern	
Tele-Clues No. 181 thru 188	6 3
Inventory Guide	
TV Tube Inventory Guide	11 3
Lead-In	
Various Types — VHF and UHF	5 2
New 600 MA Series — String Tubes	
Substitution in G-E 20" and 21" Models	7 4
Substitution in 14", 16" and 17" Models	7 6
Noise Canceller Circuits	
"EE", "H", "J" and "O" Receivers	10 5
"G" and "K" Receivers	10 6
"S", "ST", "U" and "U2" Receivers	11 1
Oscilloscopes	
How to get the most out of your test equipment — Cathode Ray Oscillograph-1	2 3
How to get the most out of your test equipment — Cathode Ray Oscillograph-2	2 4
Selecting an oscilloscope for TV servicing	1 3
Phono Cartridges	
G-E "Golden Classic" and "Stereo Classic" Stereo Hi-Fi Cartridges	10 5
G-E "Stereo Classic" Hi-Fi Tone Arm	10 6
Variable Reluctance Stylus Wear Considerations	1 6
Picture Tubes	
Aluminized Picture Tube Replacement Guide	5 5
TV Picture Tube Warranty and Adjustment Policy	10 5
Picture Tube Tester — Construction Details	5 1
TV Picture Tube Warranty and Adjustment Policy	10 5
Open Heaters Due to Arc-over	7 5
Power Tuning	
TV — "U-2" Power Tuning Repairs	10 6
Printed Circuits	
Servicing Procedures and Tools	11 3
Cracked Boards and Arc-over	11 4
Servicing and Servicing Aids	11 5
Profit Program	
New G-E Profit Program Streamlines Your Tube Sales for Fast Turnover, Top Volume!	11 4
New G-E Profit Program	11 5
Radio Service Manuals	
Radio — 1960 Manual Registration Coupon	11 6
Radio and Phonograph Service Guide Order Coupon	11 6
Radio Service Notes	
Radio-Motorboating in Transistor Radios	12 2
Radio — P675 and P720 Current Readings	10 6
Radio — P715, P765 Antenna Support	11 5
Radio — P715, P765 Loose Leatherette	11 5
Radio — P745 and P750 Circuit Changes	10 6
Radio — P745 — Low Sensitivity	11 5
Radio — P755 Oscillation and Distortion	11 3
Radio — RP1120 and AS2 Tone Improvement	11 4
Radio — T120 Dial Cord Breakage	12 1
Radio — T120 No AM	11 2
Radio — T120 No AM on l.f. End of Band	11 1

	VOL. No.
Rectifiers	
G-E Silicon Controlled Rectifiers May Revolutionize the Electrical Industry	11 2
New General Electric Germanium TV Rectifiers with Replacement Guide	9 1
400 MA Germanium TV Rectifier IN1008	9 3
400 MA Germanium TV Rectifiers IN1008 and 1016	10 5
Remote Control Systems	
G-E Wireless Remote Control System I	12 1
G-E Wireless Remote Control System II	12 2
Replacement of 21AP4 with 21ZP4-B	
Replacement of 21AP4 Metal with 21ZP4-B Aluminized Glass Picture Tube	7 6
Resistor Substitution Boxes	
Construction Details	2 5
Retrace Elimination	
Horizontal Retrace Elimination Circuit	4 2
Kill that Retrace — Horizontal	2 6
Kill that Retrace — Vertical	1 4
Service Aids	
Bench Mirror ETR — 1275	8 6
Color Dot Magnifier ETR — 1761	10 5
Chassis Jack ETR — 1470	11 2
	10 1, 3
	11 3
	12 2
	10 6
Fuse and Heater Checker ETR — 981A	10 5, 6
Magnetic Swing-Beam Service Light ETR-1593	11 6
Miniature Pin Straightener ETR-2037	7 5
Picture Tube NEK-REST ETR-1169	10 2
	11 3, 6
	12 2
	10 5
Picture Tube Pillow ETR — 1469	11 4, 5
Profit Program ETR — 2033	11 6
Rear Control Extension ETR-2089	11 6
Safety Glass Puller ETR — 1592	10 5
	11 6
Series Heater Checker ETR — 981	7 3
Service Drop Cloth ETR — 1021A	4 6
Tele-Clue Binder ETR — 1095	3 3
Tube Puller ETR — 1094	1 5
	10 2
	11 2
Tube Inventory Display Rack ETR — 2033	11 4, 5
TV-Radio Service Call Board ETR — 2044	12 2
Twin-X Wrench Set ETR — 752	6 5
	10 3
	11 2
Service Cases	
Giant	11 5
Matched Service Case Set	9 5
Service Shop Plans	
A Plan for Success (Complete Service Shop)	8 4
Make Your Own Service Bench	3 1
Service — Designed Tubes	
New Types	10 5
Signal Generators	
AM Signal Generator in Place of Cross-Hatch Generator	4 2

HOW G-E PICTURE TUBE

In maintaining its reputation for product quality the General Electric Company relies heavily on the services of thousands of external suppliers of raw material, some large, some small. In the case of many critical items to insure maximum quality control and continued improvements the General Electric Company manufactures its own raw materials and parts. In the electronic tube field this includes such important items as certain of its glass requirements, bases, filaments, lead wires, critical chemicals and many others. In this article the General Electric manufacture of phosphor, an important picture tube ingredient, is described.

The story of television is not complete without a chapter on phosphor and its function in a television picture tube. Briefly a phosphor is a material which is capable of absorbing certain kinds of energy (ultraviolet, x-rays and cathode rays are examples), then releasing this energy in the form of visible light. When the exciting energy is absorbed, a slight change occurs in the structure of certain atoms in the phosphor. The light is emitted as the atom returns to its original structure. This sequence of events is called the process of luminescence.

The screen is made up of a uniform thin layer of fine phosphor particles. A fourteen-inch screen contains over three billion of these fine particles. A screen is formed by allowing the phosphor powder to settle out of suspension onto the faceplate of the glass bulb, then carefully decanting the liquid and drying.

A phosphor in general is composed of two essential parts: one is the base material or "matrix" while the other is the "activator" which is a specially chosen impurity incorporated into the base material in very small amounts at very high temperature. Often, and this is true of those phosphors used in picture tubes, a second special activator or "co-activator" must be used to enable the activator to locate properly in the matrix.

The quality of a picture tube phosphor is determined by the processes used by the phosphor manufacturer and the controls he exercises over these processes, just as the quality of the television picture tube is determined by the tube manufacturer's choice of materials (including, of course, phosphor) and processes and the effectiveness of his controls.

General Electric television picture tube phosphors are engineered and produced at Cleveland, Ohio, in facilities especially designed for phosphor operations. Here, critical control, as shown in the pictures, of the entire manufacturing process assures the quality of General Electric picture tubes.

PHOSPHORS ARE MADE

"Research, technical design, and manufacturing control are three keys to product quality. To these add liberal amounts of tested raw materials and mix well for utmost customer satisfaction."


Particle Size

Particle size distribution has a significant effect on screen appearance. Here, a technician is shown measuring the particle size of a General Electric picture tube phosphor using the recording sedimentation pan balance, a device developed by G-E engineers.




Pure Materials

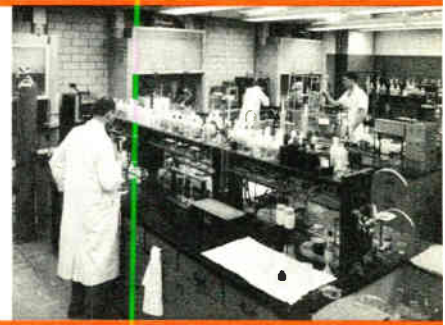Because extremely pure raw materials are required to assure bright picture tube screens, ultra-sensitive methods of chemical analysis have been developed in this laboratory.




Screen Settling

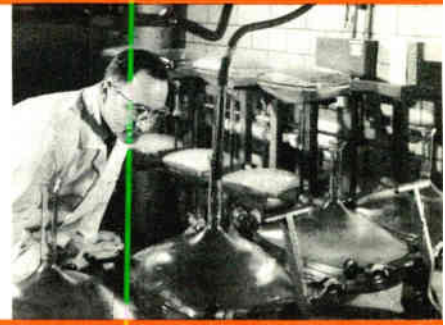An engineer in the phosphor plant is shown checking the screen settling properties of a new phosphor designed to improve the brightness and appearance of picture tubes. Before acceptance a lot will be sent to the tube factory and subsequent tests on production equipment will determine acceptability.



Phosphor Color Mix

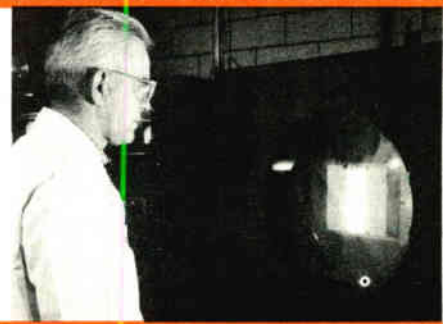A technician employs a demountable tube (an evacuated mechanical device simulating an operating tube) to evaluate phosphor color mix against a color standard plaque. This permits blending to desired standards and permits "lot to lot" uniformity.



Color Control

The engineer is operating a General Electric recording spectroradiometer used for color control of electronic phosphors. It can measure color many times more accurately than the human eye.




Turn Time into Dollars with



Your time is the most important thing you have to sell. Make every minute count, by organizing your working day for profits! General Electric's new Service Call Board makes this easy for you. At a glance, you are told what calls you must make, where and when . . . pick-ups and deliveries that are scheduled . . . customers to be seen or phoned. Everything is down in black and white.

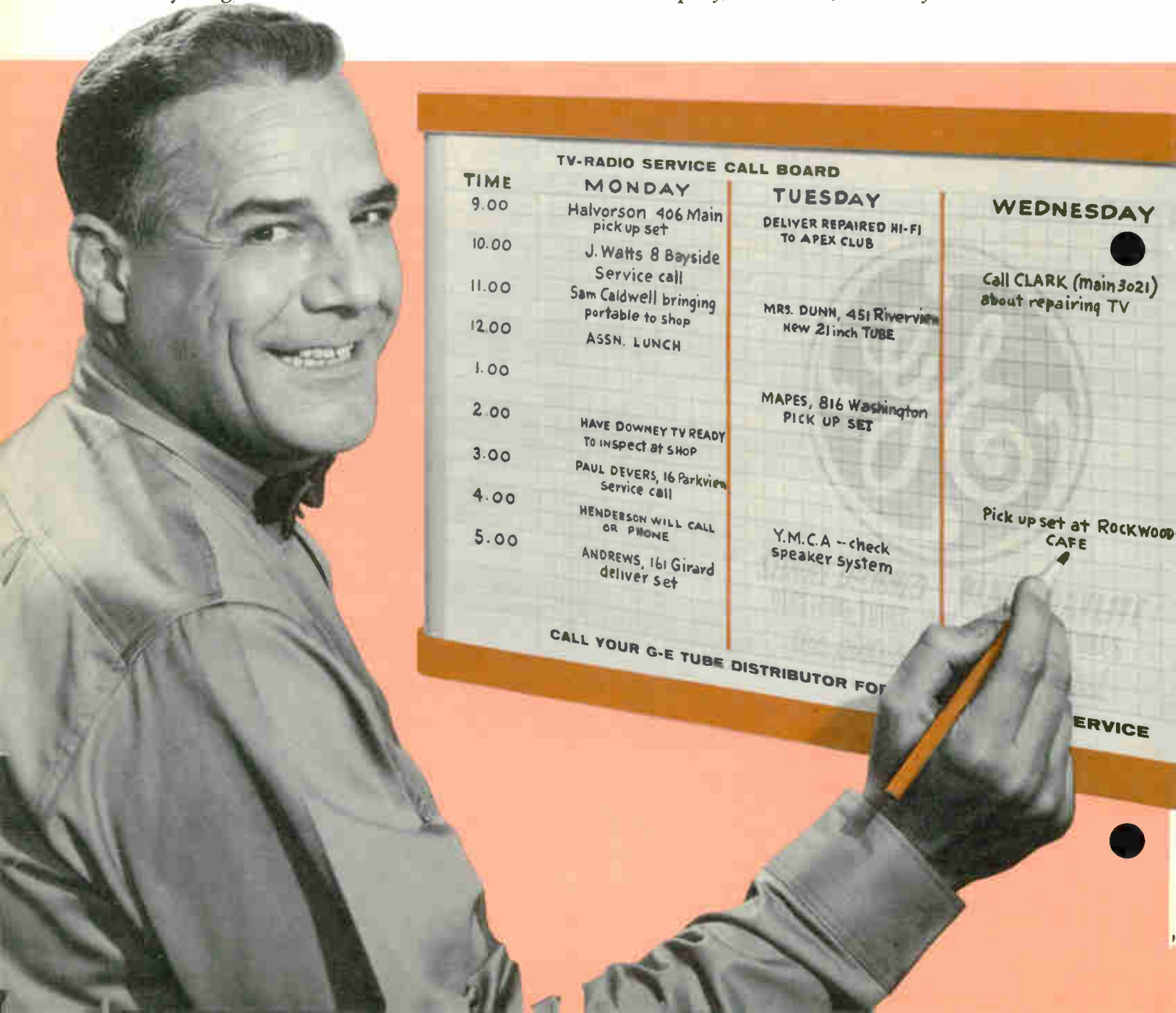No more pocket reminder slips, easily lost; no more trying to carry dates and hours in your head! With the Service Call Board, your day, week, month are efficiently programmed in advance. Study the picture and descriptive facts below and at right. Then use the convenient coupon to order! *Distributor Sales, Electronic Components Division, General Electric Company, Owensboro, Kentucky.*




TV-RADIO SERVICE CALL BOARD			
TIME	MONDAY	TUESDAY	WEDNESDAY
9.00	Halvorsen 406 Main pick up set	DELIVER REPAIRED HI-FI TO APEX CLUB	
10.00	J. Watts 8 Bayside Service call		
11.00	Sam Caldwell bringing portable to shop	MRS. DUNN, 451 Riverview New 21 inch TUBE	Call CLARK (main 3021) about repairing TV
12.00	ASSN. LUNCH		
1.00		MAPES, 816 Washington PICK UP SET	
2.00	HAVE DOWNEY TV READY TO INSPECT AT SHOP		
3.00	PAUL DEVERS, 16 Parkview Service call		
4.00	HENDERSON WILL CALL OR PHONE	Y.M.C.A -- check speaker system	Pick up set at Rockwood CAFE
5.00	ANDREWS, 161 Girard deliver set		

CALL YOUR G-E TUBE DISTRIBUTOR FOR SERVICE

NEW G-E SERVICE CALL BOARD!

- Big (21½" by 14"), easy to see and read.
- Notched at back to mount on shop wall at eye level.
- Write, erase—write, erase—again and again on transparent plastic roll-around cover!
- Crayon and erasing tissues are supplied with every General Electric Call Board.
- Strongly made in every way. The special tough plastic writing cover lasts and lasts. Handsome, neat, modern!

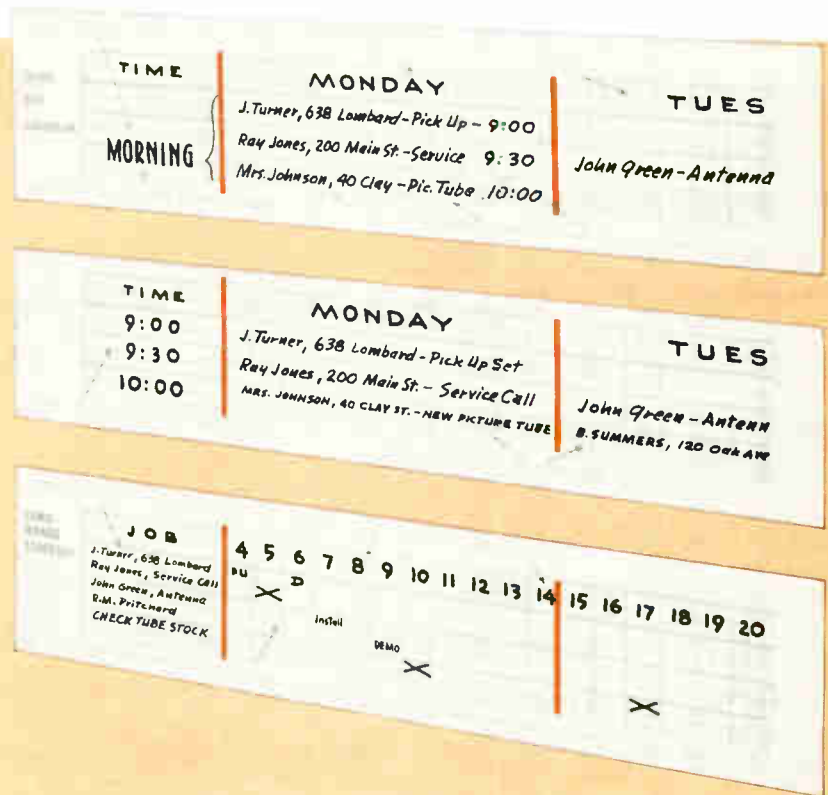**HERE ARE
THREE WAYS TO
USE THE SERVICE
CALL BOARD:**



● SEND 10 OF THESE PLUS \$3 TO RECEIVE YOUR CALL BOARD! Fill out and mail the coupon (right) enclosing \$3, also 10 carton-ends with type number of the popular, fast-moving G-E 6BQ7-A. Mail direct to Chicago warehouse address given on the coupon.

General Electric Company
3800 N. Milwaukee Ave., Chicago 41, Ill.

Enclosed is \$3, also 10 General Electric 6BQ7-A carton-ends. In return, ship me prepaid one new G-E Service Call Board.

MY NAME _____
STREET ADDRESS _____
CITY AND STATE _____

THIS OFFER EXPIRES
JULY 31, 1960

Progress Is Our Most Important Product

GENERAL  ELECTRIC

NEW "SHADOW GRID" 6FG5



NEW "SHADOW GRID" 6FG5
radio and television tube.

The football concept of a "blocking back" is used by General Electric in a new type of receiving tube containing an extra grid.

The tube is registered as the 6FG5, and is known as a "Shadow Grid" pentode. The extra grid is placed directly in front of, and precisely aligned with, the screen grid. It is grounded to the cathode and thus tends to repel electrons flowing from cathode to anode. As a result, the electrons are diverted around the wires of the screen grid. In effect, the additional grid partially shields each wire of the screen grid from the flowing electrons, and no electrons strike the screen grid directly.

This reduces screen current and opens the door to new standards of performance. Plate-to-screen current ratios as high as 60-to-1 have been obtained with this design — thus drastically reducing screen dissipation.

The first practical advantage of this "Shadow Grid" tube to the equipment manufacturer is to permit operation of the screen at the same voltage as the anode by tying the screen grid to the plate supply, thus completely eliminating the need for a dropping resistor and by-pass capacitor.

Another advantage lies in the fact that reduction in screen current permits exceptionally low noise figures as compared with standard pentodes used in VHF television tuner service.

Further, higher transconductance is achieved with this new tube, making it feasible in some cases to reduce a three-tube IF strip to two.

Basic development work at Gen-


eral Electric's Receiving Tube Department in Owensboro, Ky., centered around usage of the 6FG5 in VHF television tuner applications. Screen voltages varying from 135 to 265 volts d-c are usable, providing flexibility for equipment designers in aiming for significant cost savings.

Since with the "Shadow Grid" tube design the screen current will increase only slightly with changes in either screen or plate voltage, the transconductance of this kind of tube can be increased to allow additional reduction in noise figures as required by equipment designers.

Average characteristics of the type 6FG5 are listed at 9500 micromhos transconductance, 9 ma plate current, 0.42 ma screen current, plate and screen voltage of 250 volts d-c, with minus 0.2 volts on the control grid, and cut-off at minus 5 volts. Grid-to-plate capacity is reduced considerably, to 0.02 mmf, which helps eliminate band-pass "tilt" problems.

The new shadow grid structure also may offer improved service in AGC circuits. This would become possible if or when the new grid is brought out to a separate pin connection instead of being connected internally to the cathode—thus allowing separation of the signal and AGC bias points and minimizing cross-modulation.

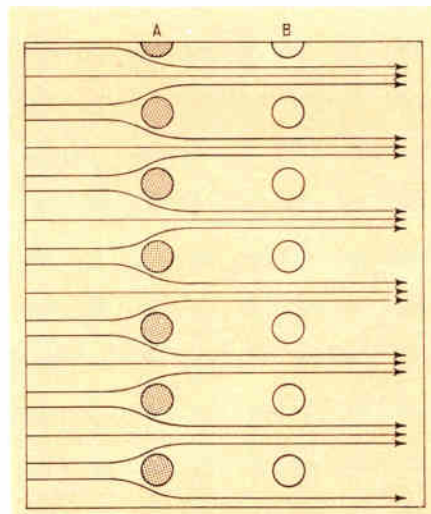The "Shadow Grid" tube is expected to be used in a wide variety of electronic equipment.



SHADOW GRID (A) diverts electron flow around screen grid (B) of General Electric's new 6FG5 — thus drastically reducing screen current and opening door to new standards of receiving tube pentode performance. With this design, the screen grid can be tied directly to the plate voltage supply, eliminating dropping resistors and by-pass capacitors. Also, the reduction of screen current permits exceptionally low-noise pentode operation.

BENCH NOTES

H V Insulator

I had a Motorola model #21T58MGA come in the shop with a high voltage leak at the bottom of the 3A3 HV Rectifier. After changing the two resistors at the bottom of the 3A3 and putting corona dope under the bottom of the HV Rectifier it still had the same arc over to the bottom of the metal cabinet. To correct this, I cut a strip of linoleum about six inches square and slid it under the 3A3. This can be done without removing any screws.

Howell's Radio & TV Service
1619 Gorman Street
San Antonio 2, Texas

Screws and Nuts Replaced Quickly

Often screws and nuts are difficult to replace due to close quarters. This is easily accomplished by scraping wax from the outside of paper condensers then placing wax in slot of screw and pushing screwdriver into it. This will hold the screw for easy replacement. For nuts, simply apply some of the wax around the outside rim then place nut in the holder and proceed to replace in set.

Glenn F. DePoe
445 N. Morris Street
Waynesburg, Pennsylvania

Slipping Tuner Turrets

In some of the early turret tuners it was common for the turret to slip on the shaft causing improper channel indication.

The factory had suggested drilling a small hole through the turret and shaft and pinning them with a nylon or fiber rod.

I have found a much easier repair which can also be used on other tuners where the shaft slips in relation to a turret or wafer.

First: Set the turret or wafer and selector knob for proper indexing.

Second: Apply one of the new epoxy resin glues to both turret or wafer and the shaft.

Epoxy resin glue hardens almost immediately and makes a permanent repair which is impossible to break even with force.

William J. Praetz
203 Covert St.
Brooklyn, New York

Instrument Protection

Pieces of foam rubber about half-inch thick cemented on the bottom of test instruments eliminate needless jarring and shocks during movement. This reduces the possibility of cracked cases and thereby prolongs the instrument's useful life.

H. Josephs
P. O. Box 22
Gardenville, Penna.

Those desiring to have letters published in this column should write the Editor Techni-Talk, Electronic Components Division, General Electric Company, Owensboro, Kentucky. For each such letter selected for publication you will receive \$10.00 worth of General Electric tubes. In the event of duplicate or similar items, selection will be made by the Editor and his decision will be final. The Company shall have the unlimited right without obligation to publish or otherwise use any idea or suggestion sent to this column.

Caution: The ideas and suggestions expressed in this column are those of the individual writers. These ideas and suggestions have not been tried by the General Electric Company and therefore are not endorsed, sponsored or recommended.

	VOL.	No.
G-E ST-16A Color Alignment Generator	8	6
I-F Alignment I	1	6
I-F Alignment II	2	2
Snivets		
Description and Photos	7	3
Snow		
TV Receiver Noise	4	1
Sparker		
Sparker to Check for "Gas" or "Air Leaker"	5	1
Speaker Enclosures		
General Electric "Stereo Classic" Speakers, Speaker Systems and Speaker Enclosures	11	2
Speakers		
General Electric Model 1201D Loudspeaker	1	6
General Electric "Stereo Classic" Speakers, Speaker Systems and Speaker Enclosures	11	2
TV — Speaker Phasing	11	4
Stereo Components		
High Fidelity Tuner	11	3
"Stereo Classic" Preamplifier	11	1
"Stereo Classic" High Fidelity Tone Arm	10	6
"Stereo Classic" Speakers, Speaker Systems and Speaker Enclosures	11	2
Variable Reluctance High Fidelity Cartridges	10	5
Stereo Hum Problem		
Part I	11	1
Part II	11	2
Part III	11	3
Part IV	11	4
Part V	11	5
Part VI	11	6
Successful Service Management		
1959 Business Outlook — A. E. Kimball	10	6
Dealer Modernization — H. B. Nelson	11	3
Electronic Components Preview of 1959 — L. B. Davis	11	1
Increased Electronic Business Forecast for 1960 — L. B. Davis	12	1
Planning for Success in the Soaring Sixties — Andrew E. Kimball	12	2
Profile of the "Boss" — L. M. Robb	11	6
"Swim — or Sink!" — G. E. Burns	10	5
The Interrelation of Large and Small Business — Senator J. Sparkman	11	2
You and Your Customers — W. F. Greenwood	11	4
Sweep Transformer Replacement		
TV — "EE" Sweep Transformer Replacement	11	1
Sync Signals and Circuits		
Synchronizing Pulses and Circuits	2	1
Techni-Talk Index		
Complete Index of Techni-talk Vol. 1, No. 1 thru Vol. 10, No. 2 by issue	10	2
Complete Index of Techni-talk Vol. 1, No. 1 thru Vol. 12, No. 2 — by subjects	12	2
Tele-Clue Index		
Tele-Clues Index	4	5

Tele-Clues

No. 1 thru 8	8
No. 9 thru 16	16
No. 17 thru 24	24
No. 25 thru 32	32
No. 33 thru 40	40
No. 41 thru 48	48
No. 49 thru 56	56
No. 57 thru 64	64
No. 65 thru 72	72
No. 73 thru 80	80
No. 81 thru 88	88
No. 89 thru 96	96
No. 97 thru 104	104
No. 105 thru 112	112
No. 113 thru 120	120
No. 121 thru 128	128
No. 129 thru 133	133
No. 134 thru 140	140
No. 141 thru 148	148
No. 149 thru 155	155
No. 156 thru 162	162
No. 163 thru 170	170
No. 171 thru 180	180
No. 181 thru 188	188
No. 189 thru 194	194
No. 195 thru 202	202
No. 203 thru 207	207
No. 208 thru 213	213
No. 214 thru 221	221
No. 222 thru 228	228
No. 229 thru 235	235
No. 241 thru 251	251
No. 252 thru 262	262
No. 263 thru 273	273
No. 274 thru 284	284

Tele-Clue Schematics

"N" Chassis	7	1
"S" Chassis	8	1
"MM" Chassis	8	3
"U" Chassis	8	4
"M4" Chassis	10	5
"U-3" Chassis	10	6
"U-4" Chassis	11	5
"M-5" Chassis	11	6

Tele-Tips

No. 1 thru 5	2	1
No. 6 thru 10	2	2
No. 11 thru 15	2	3
No. 16 thru 20	2	4
No. 21 thru 25	2	5
No. 26 thru 30	2	6
No. 31 thru 35	3	1
No. 36 thru 39	3	2
No. 40 thru 43	3	3
No. 44 thru 47	3	4
No. 48 thru 51	3	5
No. 52 thru 55	3	6
No. 56 thru 58	4	1
No. 59 and 60	4	4
No. 61	4	6
No. 63 and 64	5	3
No. 65	5	4
No. 65 thru 67	5	5
No. 68 and 69	5	6
No. 70	6	3
No. 71	6	5
No. 72 and 73	7	2
No. 74 and 75	7	5
No. 76	10	1
No. 77	10	3

	VOL.	No.
	1	5
	1	6
	2	1
	2	2
	2	3
	2	4
	2	5
	2	6
	3	1
	3	2
	3	3
	3	4
	3	5
	3	6
	4	1
	4	4
	4	6
	5	1
	5	3
	5	4
	5	5
	5	6
	6	2
	6	3
	6	5
	7	2
	7	3
	7	5
	9	5
	10	1
	10	3
	11	2
	11	3
	11	4
	12	1

	VOL.	No.
Test Equipment		
AM Signal Generator in Place of Cross-Hatch Generator	4	2
Capacitance-resistance Bridge	1	3
Cathode Ray Oscillograph — 1	2	3
Cathode Ray Oscillograph — 2	2	4
G-E ST-16A Color Alignment Generator	8	6
Signal Generator — 1	1	6
Signal Generator — 2	2	2
Tube Tester	1	2
Vacuum Tube Voltmeter	1	5
Transistors		
Transistor Theory	8	1
How to Make a Transistor Tester	10	6
Transistor Tester		
G-E Transistor Tester	8	1
How to Make a Transistor Tester	10	6
Tube Testers		
How to Get the Most Out of Your Test Equipment — Tube Tester	1	2
Tuners		
G-E Model FA-10 and FA-12 Hi-Fi Tuner	11	3
The G-E UHF 103 Tuner — I	5	3
The G-E UHF 103 Tuner — II	5	4
The Head-End — 1	1	3
The Head-End — 2	1	4
UHF Converters or Tuners	5	2
TV Antennas		
Television Reception 1	1	1
Television Reception 2	1	2
UHF Antennas	5	2
UHF Antenna Installations	6	4
TV Channel Frequencies		
Complete list of channel frequencies	4	3
Nationwide Table of TV frequency assignments (1952)	4	3
TV Circuit Description		
D-C Restoration	1	6
Deflection Circuit Waveforms and RF Power Supplies	2	3
Horizontal AFC Systems	2	2
Horizontal Deflection Circuits and Kickback Power Supplies	2	4
Synchronizing Pulses and Circuits	2	1
The Head-End — 1	1	3
The Head-End — 2	1	4
Video Detector, A.G.C. and Video Amplifier	1	5
Vertical Sweep Circuits	1	6
TV Picture Tubes		
Aluminized Picture Tube Replacement Guide	5	5
Part I — Phosphor Specifications and Implosions	4	4
Part II — Electron Gun and Gun Defects	4	5
Part III — Gun Defects continued and Cathode Images	4	6
Part IV — Construction of a Picture Tube Tester	5	1
Open Heaters Due to Arc-Over	7	5
Replacement of 21AP4 Metal with 21ZP4-B Aluminized Glass Picture Tube	7	6
TV Receiver Noise or Interference		
TV Receiver Noise	4	1
TV — "U-3" Apparent Ignition Interference	11	2

	VOL.	No.
TV Reception		
Report on UHF Reception	5	2
The Antenna — 1	1	1
The Antenna — 2	1	2
TV Service Guide		
Volume 3	11	1
TV Service Manuals		
1960 TV Manuals and Subscription Coupon	11	6
TV Service Notes		
Excessive Width — "U2" Receivers	10	5
Power Tuning Repairs — "U2" Receivers	10	6
Correction for Overload on Strong Signal — "U2" Receivers	10	6
Replacement Sweep Transformers	11	1
Apparent Ignition Interference On "U3" Receivers	11	2
Removal of the Metal Back on "M4" Models	11	2
Electrical Safety Test	12	2
Excessive Width — "M4" Sets	11	3
Slippage in Fine Tuning Control	11	3
Horizontal Jitter in "M4" Television Receivers	11	4
Speaker Phasing on 2-Speaker and 3-Speaker Models	11	4
Color Receiver — Models: 21T500, 21C700 and 21C701	11	5
1960 TV Manuals	11	6
"U2" Chassis Vertical Sync Buzz Trouble	11	6
TV Signal Description		
Synchronizing Pulses and Circuits	2	1
TV Sound Systems		
Delta Sound System	10	3
Repair of Ratio Detector Transformers	10	5
TV Test Tubes		
8YP4 Universal Picture Tube	10	6
UHF Reception		
Report on UHF Reception	5	2
UHF Antenna Installations	6	4
VOM & VTVM		
How to Get the Most Out of Your Test Equipment — VOM — How to Make HV-Multiplier	1	1
How to Get the Most Out of Your Test Equipment — Vacuum Tube Voltmeter	1	5
Vertical Circuits		
Kill that retrace — Vertical	1	4
Vertical Sweep Circuits	1	6
Video Amplifiers		
Video Detector, A.G.C. and Video Amplifier	1	5
Video Detectors		
Germanium Diodes in Video Detector Circuits	2	3
Video Detector, A.G.C. and Video Amplifier	1	5
What's Wrong with This Picture?		
What's Wrong With This Picture?	11	2
What's Wrong With This Picture?	11	3
What's Wrong With This Picture?	11	4

Copies of all issues are still available. If you are missing any copies and cannot obtain them from your distributor, send five cents for each issue to: Editor, Techni-Talk, General Electric Company, 316 E. Ninth Street, Owensboro, Kentucky.

TELEVISION — Electrical Safety Test

In a recent letter from a distributor, it was brought to light that it is possible through some service fault to create a hazardous condition in the transformerless type chassis often used in portable sets. With a little effort, service men can check each set before handling it back to the customer, thus insuring him against any possibility of injury.

The following procedure appeared in the "Q3" Final Service Manual:

Should the receiver become damaged, or the chassis removed to effect repairs, or for any other desirable reason, the following advised safety test should be performed.

The receiver on which the safety test is to be made must be in good operating condition and completely assembled.

With no power applied to the receiver, short the two prongs of the power plug together and connect one

probe of an ohm-meter to the shorted prongs of the power plug.

The power switch of the receiver should be "On" and the channel selector knob and one of the primary control knobs (contrast, vertical, brightness, or volume) removed. All built-in antennas should be connected to their proper connections on the antenna terminal board.

All readings obtained between the power plug and the following listed points should be over 125,000 ohms to be considered within the safety limits.

1. Cabinet body (to insure proper contact use a cabinet back retaining screw for test point).
2. Each individual antenna terminal.
3. VHF tuner selector shaft.
4. One of the primary control shafts.
5. Handle.
6. Rear chassis foot.
7. Interlock retaining screw.

RADIO — Motorboating in Transistor Radios

A slow rate of audio oscillation or motorboating may occur in several models of transistor radios if the filter electrolytic, connected in series with the resistor across the battery, drops below a certain value. The motorboating is eliminated when fresh batteries are installed but reoccurs if the batteries run down slightly. Therefore, if a customer complains that motorboating appears within a short time after batteries have been replaced, check the electrolytic capacitor or install an additional one in parallel.

After this has been done, check the operation of the radio at reduced battery voltage. (A variable power supply is handy for this.) The following table lists some transistor models which may be prone to motorboating if the electrolytic value drops too low:

MODEL NUMBER	CAPACITOR SYMBOL No.	RECOMMENDED VALUE
P715	C12	100 mf.
P765		
P720	C15	175 mf.
P725A	C16	175 mf.
P745	C16	50 mf.
P750	C16	175 mf.

Techni-talk SUGGESTION AND INQUIRY COUPON

If you would like to receive additional information on some specific G-E Electronic Component, just clip out this coupon, write in the material desired, and send it to the Editor. Information, if available, will be sent to you by return mail.

Please check your name and address on the reverse side. Make any necessary corrections below.

Name.....

Street Address.....

City, Zone No. and State.....

If you expect to move within next two months, please print new address above.

If you are receiving duplicate copies, please check this box and indicate mailing list number which appears at lower left corner of the address area on each copy you receive.

Have trouble holding record changers and TV or radio chassis in servicing position? The new G-E Chassis Jock can help you. Ask your distributor for ETR-1470.



Have trouble holding picture tubes in viewing position? Use G-E Nek-Rest. Quickly adjustable for all size tubes. Available at your distributor. Ask for ETR-1169.

G-E WIRELESS REMOTE SYSTEM

(Continued from page 1)

ulated magnetic field excites one of the reeds and causes it to vibrate, the reed contact is closed for each half cycle of reed vibration. This action causes a current to flow through a corresponding sensitive relay coil and the sensitive relay arm is made to pull in by the magnetic field built up in the relay coil. This closes the contact points of the relay and thus causes the proper function to be activated.

The off-on function is performed by a two position latching relay contained in the Remote Receiver. This operates in conjunction with the TV receiver off-on switch. The channel select function is performed by completing the a-c Power loop needed to supply power for the power tuning motor mounted in the TV receiver.

The increase volume or decrease volume function is performed by supplying power to an a-c reversible motor. The motor is mechanically coupled to a variable potentiometer (R615) which when varied, changes the screen voltage available to the 4.5 MC Audio I-F amplifier tube in the TV receiver.

The remote receiver unit contains its own transformer power supply utilizing a germanium diode in a half wave rectifier circuit for the B+ supply. An octal plug and socket is used to interconnect the remote receiver with the TV receiver, and Pins 2 and 5 of the socket are used for the 120 Volt a-c supply to the remote unit.

The power to the remote unit can be turned on or off by a slide switch located just above the antenna input terminals on the back of the TV receiver, and Pins 2 and 5 of the socket are used for the 120 Volt a-c supply to the remote unit. The power to the remote unit can be turned on or off by a slide switch located just above the antenna input terminals on the back of the TV receiver.

Under normal conditions the remote receiver unit should be left turned on so that it may receive the control signals sent out by the remote transmitter unit, however if it is planned not to use the unit over an extended period it can be turned off.

Color Dot Magnifier ETR 1761

Adequate magnification makes individual color dots visible on Color Picture Tube.

Dot visibility makes more accurate "purity" adjustments possible.

Can also be used to check phono needles for wear.



tubes

G-E Service Cases Now Have Suggested Tube Inventory

All three G-E Service Cases now contain a suggested inventory list packed in each case. The list includes most tubes used in television receivers

both old and new. Tube types used exclusively in color TV receivers are indicated with an asterisk. This list combined with your own

experience, will help you fill your service case most adequately for the particular type of field work you do.

ETR-2156
Tube Inventory List for Special "160" Service Case.



ETR-1478
Holds 85 Miniatures, 39 GT types and 38 Large Glass Tubes.

ETR-2155
Tube Inventory List for Service Master "240" Service Case.



ETR-1477
Holds 126 Miniatures 54 GT types and 48 Large Glass Tubes.

ETR-2157
Tube Inventory List for Giant Service Case.



ETR-2071
Holds 189 Miniatures 128 GT types and 48 Large Glass Tubes.



Techni-talk



ELECTRONIC COMPONENTS DIVISION
GENERAL ELECTRIC
OWENSBORO, KENTUCKY

BULK RATE
U.S. Postage
PAID
Schenectady, N.Y.
Permit No. 148

Vol. 12 No. 2 MAR.—MAY, 1960

In this issue: Page

G-E Wireless Remote Control System II	1
Planning for Success	2
Complete Index of Techni-Talk 1949-1960	3, 4, 9, 10
How G-E Phosphors are Made	5
Turn Time into Dollars	6-7
New "Shadow Grid" 6FG5	8
TV and Radio Service Notes	11

Techni-talk on AM, FM, TV Servicing, published bi-monthly by Electronic Components Division, General Electric, Owensboro, Ky. In Canada: Canadian General Electric Co., Ltd., 189 Dufferin St., Toronto 3, Ontario. R. G. Kempton, Editor. Copyright 1960 by General Electric Company.

Mr. Thomas Boyd
1018 North McCollough
San Antonio, Texas
Z-7-804

Form 3547 Requested

This copy of **Techni-talk** comes to you through the courtesy of your General Electric tube distributor.

NOTE: The disclosure of any information herein conveys no license under any General Electric patent and, in the absence of an express written agreement to the contrary, the General Electric Company assumes no liability for patent infringement (or any other liability) arising out of use of such information by others.