

73

magazine for radio amateurs


a JUST

\$1.00

November 1973

26009

A
CE

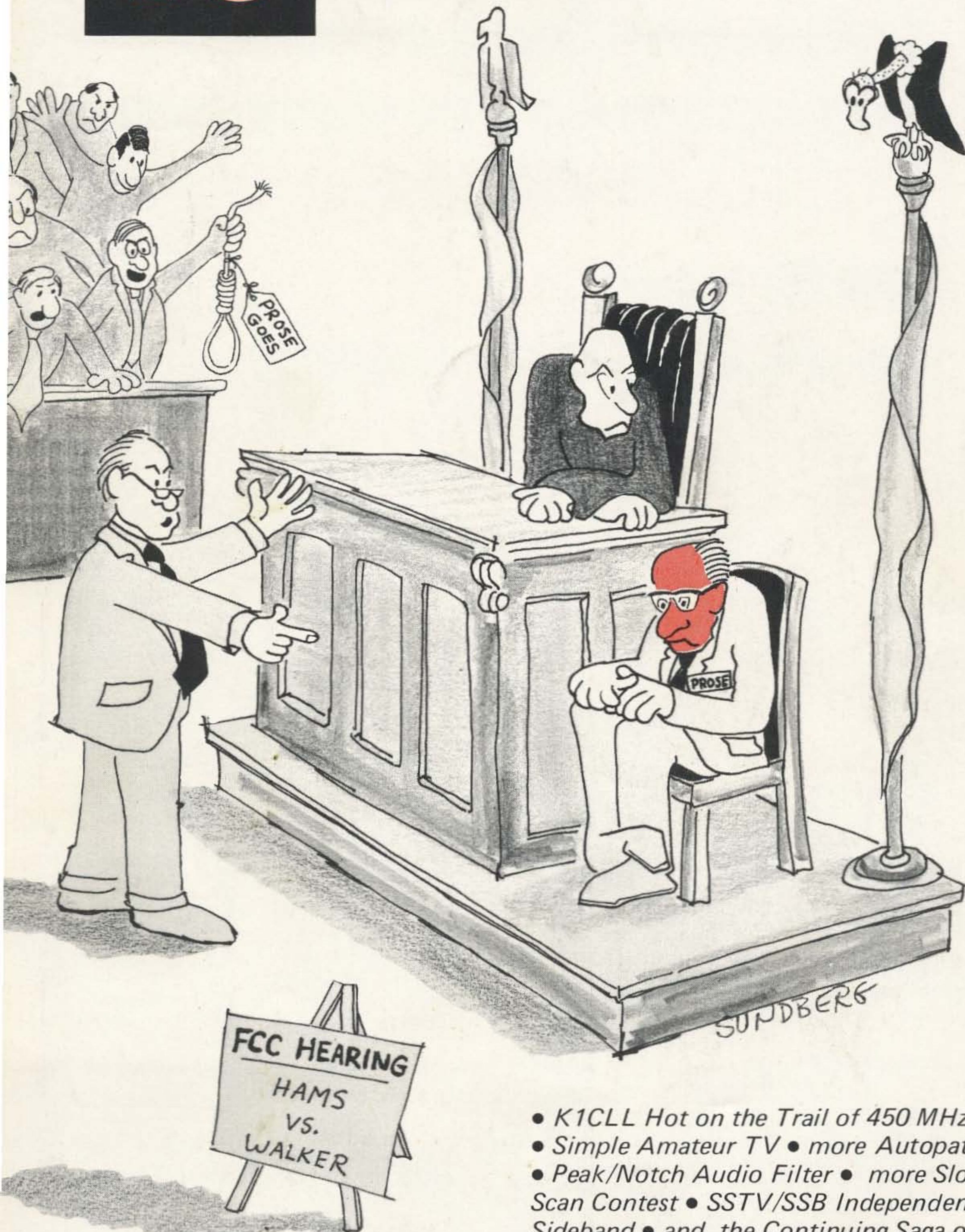

- K1CLL Hot on the Trail of 450 MHz
- Simple Amateur TV • more Autopatch
- Peak/Notch Audio Filter • more Slow Scan Contest
- SSTV/SSB Independent Sideband • and, the Continuing Saga of the Wandering Rules and Regulations

**for over 20 years we've
been designing VHF-FM
antennas for some
pretty tough customers.**

**we know
you're just as tough.**

A product in the amateur market gets a reputation very quickly. It measures up to what you expect in engineering, performance and quality — or else. That's why A/S amateur antennas are built to the identical design and construction standards as their commercial counterparts. Standards that have made them specified for more police and public safety vehicle installations than all other brands combined.

**HM-177
2 Meters**

Features new high conductivity copper and nickel coated 17-7 PH stainless steel whip. Shunt fed coil encased in waterproof PVC jacket. All fittings chrome plated brass. Easy snap-in mounting. 3 dB gain.*

**NEW! HM-223
1 1/4 Meters
(220 MHz)**

High performance 5/8 wavelength design for the new 220 MHz activity! Directly fed with low loss coil in new low-profile design. Spring and whip easily removable leaving only 1 3/16" high base for car wash clearance. 3 dB gain.*

**HM-175
3/4 Meters**

Collinear design with truly hot performance! Base fittings have silver plated contacts. Can handle 100 watts. Whip and phasing coil assembly is a one piece molded design to resist vibration and moisture. 5 dB gain.*

**HM-4
2 Meters**

Tough, virtually indestructible antenna for hand-holds. Completely insulated. Base fitting matches Motorola HT, E. F. Johnson, and Standard portables.

HM-5

Same as above but for Drake and other packset portables with SO-239 fittings.

NEW ASCOM® TOWERS

High strength, low maintenance aluminum towers for HF and VHF antenna installations. There is a complete line of ASCOM self-supporting towers — in heights from 30 to 90 feet — at attractive prices!

*Measured over a 1/4 wavelength whip

WRITE FOR FREE AMATEUR ANTENNA
and/or TOWER CATALOGS



**the antenna
specialists co.**

Division of ORION INDUSTRIES, INC., 12435 Euclid Ave., Cleveland, Ohio 44106

Export: 2200 Shames Dr., Westbury, L.I., New York 11590 Canada: A. C. Simmonds & Sons, Lt

EDITORIAL STAFF

Wayne Green W2NSD/1
Keith Lamonica W7DXX/1
Ron Subka WA9FPP/1
Yvette Grimes WA8ULU/1

ASSOCIATES

Gus Browning W4BPD
Mike Frye WB8LBP
Bill Hoisington K1CLL
Dave Ingram K4TWJ
Jim Kyle K5JKX
Harry Simpson A4SCF
Bill Turner WA0ABI

PRODUCTION

Ruthmary Davis
Karen Hebert
Biff Mahoney
Peri Mahoney
John Miller
Janet Oxley
Lynn Panciera-Fraser
Philip Price
Bill Suderman
Bill Sundberg

BUSINESS

Knud E.M. Keller KV4GG/1

CIRCULATION

Barbara Block
Jackie Garner
Dorothy Gibson

TRANSPORTATION

Kurt Schmidt
Jinx Townsend

PROPAGATION

John Nelson

DRAFTING

T.M. Graham W8FKW
Bill Morello
Wayne Peeler K4MVW

FEATURES

2	Amateur Radio News	15	QSL Contest
4	Never Say Die W2NSD/1	15	Ham Help
6	SSTV Scene	15	Intruder Chase
7	SSTV Contest	16	DXCC News
8	50 MHz Band	17	Hamburglar
9	Contests	17	New Products
10	Repeater Update	98	Letters
10	Traveling Ham	108	Caveat Emptor
11	FCC News	159	Circuits
12	Looking West	159	Phase Lock
14	AMSAT News	160	Ad Index
		160	Propagation

CONTENTS

21	Getting Started On 450 MHz	K1CLL
	Hurry before someone proposes a Class F!		
26	Getting Started On ATV	WA7NMO
	Simple circuits for the beginning ATVer.		
35	NI-CAD Battery Life-Saver	K2ETN
	Insures cold starts.		
39	The Heath GR-110 Scanning Receiver	W3WTO
	A plus for Heath.		
49	Is Your Autopatch Legal?	W3YVV
	Or are you just pretending. . .		
53	Frequency Aperture Modulation	W2BSP
	FAM makes another appearance.		
59	VOM Range Extender	W2EEY
	You can do more than just lengthen the test leads.		
63	AC Power Supply for Portable Rigs	WA3EEC/1
	You can't operate portable 100% of the time!		
65	A Radiating Loading Coil	W0FEV
	An indoor antenna that might pass as a weird lamp.		
69	Peak/Notch Audio Filter	W6AGX
	A worthwhile addition to your rig.		
73	Power Failure Protection	Ives
	Make sure brownout doesn't spell burnout.		
75	160 Meter Antenna Coupler	W2LT
	An improper antenna is no longer an excuse for staying away from 160.		
77	HT-100 - 1 Watt, PL and Touchtone	K6VGP
	Buy your way to happiness.		
83	Independent Sideband - SSTV/SSB	W9NTP & WB8DQT
	Narrate your Slow Scan program.		
87	The Elusive 100 Countries	VE3CEA
	This month's tale of International intrigue.		
93	Complementary-Pair Audio Amplifier	W5SOT
	Transistors get lonely too.		
103	Amateur Rules and Regulations, Part VI	FCC
	This month the Bounty sets its sails to the south hoping to find breadfruit.		

73 Magazine is published monthly by 73, Inc., Peterborough, New Hampshire 03458. Subscription rates are \$6 for one year; in North America and U.S. Zip Code areas overseas, \$7 per year elsewhere. Three years, \$14, and \$16 overseas. Second class postage paid at Peterborough NH 03458 and at additional mailing offices. Printed at Menasha, Wisconsin 54942 U.S.A. Entire contents copyright 1973 by 73 Inc., Peterborough NH 03458. Phone: 603-924-3873. Microfilm edition of 73 available from University Microfilms, Ann Arbor, MI 48106. Magnetic tapes available from Science for the Blind, 332 Rock Hill Rd., Bala Cynwyd PA 19904.

Amateur Radio

NOVEMBER MCMLXXIII

Monthly Ham



Noting the apparent impossibility of obtaining changes in the repeater rules via normal channels, members of SERCOM (WA3KXF) and the Central Pennsylvania Repeater Association (WA3KZG) arranged a meeting with Congressman Edwin D. Eshleman of the 16th Congressional District of Pennsylvania to explain the situation and appeal for help. Congressman Eshleman was quite receptive and immediately invited correspondence with Chairman Dean Burch of the FCC. Congressman Eshleman did point out that a single Congressman cannot have much affect and as this is a national problem, all interest groups should contact their own Congressional Representatives. The multitude of repeater organizations should easily be able to get Congress working on our behalf.

(photo by WA3MHP)

Saudi Arabia on Slow Scan

Reprinted from the West Coast DX Bulletin.

A couple of stations have been showing up regularly and with 7Z3AB about to be missed, some hope may still exist. HZ1AB has been showing up around 14250 kHz from 1900Z. Says handle is Terry, using Collins gear to a rhombic antenna. . .advised that he will be on most weekends from 1900Z onward and working by districts. HZ1SH has also been showing up regularly in the last month. Gives his name as Fasil and says to QSL to Box 2108, Jeddah, Saudi Arabia. Sometimes in the lower reaches of twenty phone from 1000Z, and sometimes a bit surprising as to what you may hear. Like the following. . .this on SSTV.

W-station: "Please repeat your name and I will send my picture."

HZ1SH: "My name is Fasil. I am the King of Saudi Arabia. Please send your picture."

W-station: "I did not get your name. Did you say you were a king?"

HZ1SH: "Yes. I am the King of Saudi Arabia and my name is Fasil. Please send me your picture."

W-station: "But, I am in my pajamas. I am in my pajamas. Is that okay, King?"

HZ1SH: "Yes. Please go ahead."

W-station: "Okay. . .here it comes."

The point may be obvious but should it not be, if you are on SSTV be prepared!!! You may never know whom you are going to encounter. At least have a presentable photo available for emergencies.

FCC PROBLEMS

An FCC release re the repeater extension mentioned that one of the reasons for the extension was excessive problems with defective amateur repeater station applications.

May I state that from my experience this is directly due to the FCC, not to stupidity on the part of the repeater groups — who are not stupid.

From the outset, 73 Magazine has tried to keep abreast of the rapidly changing Walkerequirements for repeater applications, only to be met with resistance and incommunicativeness. It has been estimated that well over \$35,000 has been spent on phone calls to the FCC just on the repeater application situation — and the result has been contradictions and evasions in many cases.

There has been no way to get the information on how to apply for a repeater license and publish it because the ground rules have been ever changing.

Take for instance the situation where Lou McCoy of the ARRL went to Washington, sat down with Walker and got the info on how to work out the height above average terrain (HAAT) calculations — something that appears so simple that even an idiot should be able to manage it, right? This, for some odd reason, was published under a nom-de-plume in QST and plaques and other awards were promptly given this mythical author. Hardly had the ceremonies concluded from all the award giving when Walker decided that this system of calculating HAAT was no longer acceptable.

Surely this is an exaggeration?

Of course the obvious answer is to get rid of the rules which are causing both amateurs and the FCC all the trouble. If the restrictions on antennas, power, crossbanding, tandem repeaters, control and such were removed, then a simple FCC form would suffice and there would be few problems.

News Pages

GEAR NEEDED

Anything and everything in ham gear is desperately needed by the radio clubs in Jordan. There are presently ten ham clubs there and each has an average of twenty active operators. King Hussein has given each club a rig for starters, but that doesn't scratch the surface. These hams want to operate and to build — and they need gear.

How about taking a good look in your closets, cellar, garage, attics, for workable transmitters, receivers, transceivers, exciters, test equipment, rotors, beams, and usable parts. Can you think of any better use to put these things to than helping new hams in a part of the world where radio parts and equipment just are not available?

By a special arrangement with His Majesty all equipment will be shipped at no charge from the Jordanian Embassy in Washington to Jordan — and there will be no import duty. The address is: Royal Jordanian Radio Amateur Society, c/o Royal Palace, Amman Jordan, via Embassy of Jordan, 2319 Wyoming Avenue NW, Washington DC.

Sideband and CW rigs will be particularly useful — and even VHF rigs will be helpful now that there is a repeater set up in Amman. If there is something wrong with the rig, make a note of it on a tag so they will have a good chance to fix it up over there. But remember that parts are incredibly difficult to get. They take months to arrive when ordered and there are NO radio stores as yet. Please drop a note to 73 and let us know what you've sent. Here is your chance to help out.

CLIPPINGS NEEDED

Please, when you see an article in the paper about amateur radio — clip it out and send it to 73 — or at least a copy of it! We use this material for our news pages — and for letters to congress. We need the material to work with if we are going to do a job for you.



Here is a Who's Who of the Arab Radio Net — just the chaps you'll want to contact to get that coveted Arabian Knights award. Left to right are 7Z3AB, ST2SA, 9K2AL, SU1MA, JY5GQ, JY5AT, JY1, JY4IA, 9K2AM, OD5FJ, JY5KA, JY5AA, OD5FI, JY5AH.

U.S. AMATEUR FREQUENCY ALLOCATIONS

	CW Only	Phone & CW
Extra Class	3.500— 3.775	3.775— 4.000
	7.000— 7.150	7.150— 7.300
	14.000—14.200	14.200—14.350
	21.000—21.250	21.250—21.450
	28.000—28.500	28.500—29.700
Advanced Class	3.525— 3.775	3.800— 4.000
	7.025— 7.150	7.150— 7.300
	14.025—14.200	14.200—14.350
	21.025—21.250	21.270—21.450
	28.000—28.500	28.500—29.700
General Class	3.525— 3.775	3.890— 4.000
	7.025— 7.150	7.225— 7.300
	14.025—14.200	14.275—14.350
	21.025—21.250	21.350—21.450
	28.000—28.500	28.500—29.700
Novice Class	3.700— 3.750	
	7.100— 7.150	
	21.100—21.200	
	28.100—28.200	
Technician Class	50.100 — 54.000, 145.000—148.000, 220 MHz band and above.	

SSTV Frequencies	
	Suggested
3.775— 3.890	3.845
7.150— 7.225	7.220
14.200—14.275	14.230
21.250—21.350	21.340
28.500—29.700	28.680
50.100—54.000	

LICENSE FEES	
Initial License\$ 9
Renewal\$ 9
New Class\$ 9
Modification\$ 4
Special Call Sign\$25

Use FCC Form 610 and mail with appropriate fee to:

Federal Communications Commission
Gettysburg PA 17325

RECIPROCAL LICENSING Between U.S. and: CE - CP - CT1 - CX - D - EI - F - G - HB9 - HC - HI - HK - HP - HR - LA - LX - OA - OH - PA - PY - SM - TG - TI - VE - VR2 - VU - YB - YN - YS - YV - ZL - ZP - 3A - 4X - 6Y - 8P - 9K - 9L - 9Y.

THIRD PARTY AGREEMENTS Between U.S. and: CE - CM - CO - CP - CX - EL - HC - HH - HI - HK - HR - JY - LU - OA - PY - TG - TI - VE - VO - XE - XP - YN - YS - YV - ZP - 4X - 4Z - 8R - 9Y. Also W/K/8P.

RESTRICTED COUNTRIES (don't work) are now down to only Vietnam(s) 3W8 and XV, with the exception of XV5AC being okay.



NEVER SAY DIE

...de W2NSD/I

EDITORIAL BY WAYNE GREEN

REPORTING OPPORTUNITY

The fine job that the two reporters from the Washington Post did in following up the Watergate questions is proof of what can be done when odd things like this are investigated carefully. Another such opportunity seems to have appeared for this type of investigative reporting, though it would not be of the magnitude of the Watergate revelations.

The patently ridiculous docket 19759 calls out for such an investigation. How could such a docket ever come to be presented for serious consideration? If it made it through the normal decision making procedures of the FCC, then there is something radically wrong with the way this works and changes need to be made before more such idiocies emerge. If there was skullduggery, then the dirty work needs to be exposed and the people involved flushed out.

A person with persistence could follow up all of the trails of the docket, starting with the Electronic Industries Association and the companies which have been paying the piper for this "license to make money."

If the FCC does have clean hands in this, then they should cooperate with an effort to prove it. If some of the FCC officials have hidden motives, then a cover-up can be expected, with secrecy and buck-passing. Frankly, I suspect that there is the material here for a good solid congressional investigation.

73 A LITTLE THINNER

There are two "non-profit" ham magazines, one by charter (QST) and the other because I run it that way. The major difference between the two, from the financial end, is that I put every dollar that is available into making 73 bigger and better — and QST puts it into the bank. The result is that they have, at their last report, \$1,072,000 in bank deposits and securities, and 73 has about one thousandth of that.

Normally this doesn't make any difference and 73 puts out as much magazine every month as the income will permit. The bind comes when something extraordinary comes along

— like an IRS suit. This can get expensive and this is why most people faced with such a thing have to just give up and pay, no matter how outrageous the decisions. You do read every now and then about someone who has had the guts (and the money) to fight this bunch — it usually takes the shape of a small newspaper story on a chap who has fought them through the IRS courts for several years and who was finally found innocent.

The methods used by the IRS agents are the closest thing I've seen to the good old German Gestapo. They threaten and intimidate witnesses — they seem to be able to spend any amount of money for the most trivial items.

I'm just beginning to learn about this outfit, and what I've seen so far is blood curdling. They seem to prey on small businesses, the ones that don't have enough money to fight back and who just have to be closed down. If the expenses we've had are any indication, perhaps you can see why most firms just have to fold up. Our legal expenses so far have been over \$20,000 — and that is just the beginning, with another \$20,000 at least for the trial. I'll leave it up to you what a sudden expense like this would do to you or your business.

The one-sidedness of the IRS is so manifestly unfair that you might wonder why you haven't seen articles about it in newspapers and magazines. From what people who have been involved tell me, the IRS is extremely vindictive and the slightest adverse article often brings on a full audit and investigation — and you've read enough to know that they *always* find that you owe them money. The fact is that publishers are scared silly of the IRS and throw out almost everything that might stir up this hornet's nest of people who have almost unlimited power — and know it.

What does get into the papers are the releases that the IRS public relations departments send out. These are totally biased in favor of the IRS and are usually the rankest propaganda — and the victim has no recourse. Not only won't the paper publish his side of the story, if he can get it to them, he is faced with the reactions of his former friends and neighbors who

have read one side and one side only — and harbor the strong suspicion that if the papers printed it, it must be true.

Well, at any rate, since 73 does not have any \$1,072,000 put away in reserves, the expenses of the IRS suit have to be covered by printing a little thinner magazine for a few months. We hope that you understand.

You probably want to know what the case is against 73. So far as we can tell the great crime that has been committed — and this is a criminal prosecution with the attempt to put me in jail — is that the IRS, without asking me about these things, has decided that some items taken by our bookkeeper as business expenses in the years 1966-67-68 were actually personal expenses of mine and therefore the IRS has been defrauded. Just what all these things are will be brought out at the trial, but from what I've seen, they've decided to disallow trips to hamfests and conventions where I spoke, showed slides, and sold subscriptions.

My trips to foreign countries have been valuable — I've worked from many rare spots and this makes for 73 to be better known — and gives me better perspective to write and edit 73 — and the articles that I have written in 73 about my trips have been well received. The recent article on Jordan is a good example — without wide DXing experience I never would have made it to Jordan in 1970 — and thus I would never have had the opportunity to meet King Hussein and convince him that amateur radio would be of great benefit to his country with the resulting explosion of amateurs. We don't know where this will stop, but it should be obvious that the few dollars spent in my going to Jordan were well invested — the whole trip cost about \$1000.

But what happens to a \$1000 expense that is disallowed? Well, that means that there is an extra \$1000 in personal income that was not reported — and this means perhaps \$400 in taxes (how much tax do *you* have to pay on an additional earned dollar?). Add a 50% fine to that for not reporting it and you have \$600 — then add interest to it for seven years at 6% and it magically escalates to \$902! But you're not through yet. Since that was disallowed as a business expense, that means that the business had \$1000 in unreported income — but the tax on that is probably only about 33% — or \$333. . . and then you add in the 50% fine to bring it to \$500. . . and then the interest for seven years brings it to \$752. Add the two together and you have a tax of \$1654 on a single disallowed \$1000 expense. Now you can see how the IRS comes

(Cont. on page 102.)

CONSIDERABLY SPECIAL CONSIDERING THE SPECS

2 METER FM TRANSCEIVER

Model SRC-146A



Frequency 143-149 MHz
(2MHz spread)
Number of channels 5
Supplied with 146.94 simplex,
146.34 / .94 (same plug in
crystals as SR-C826M)
R.F. output 2 watt minimum
Sensitivity better than 0.4
uv / 20 DB Q.S.
Audio output 500 mw
Meter monitors battery voltage on
Tx, S Meter on Rx
Current drain 620 ma Tx,
15 ma Rx standby
Size 8³/₈" high x 3" wide x 1⁵/₈" deep
Weight 24 oz., less batteries

Options: *Private channel (CTCSS), external mic, or mic-speaker, stubby flexible antenna, desk top charger, leather case.*


\$289 00

**Suggested
Amateur
Net Price**

NEW 2 METER REPEATER

SCA-RPT-1

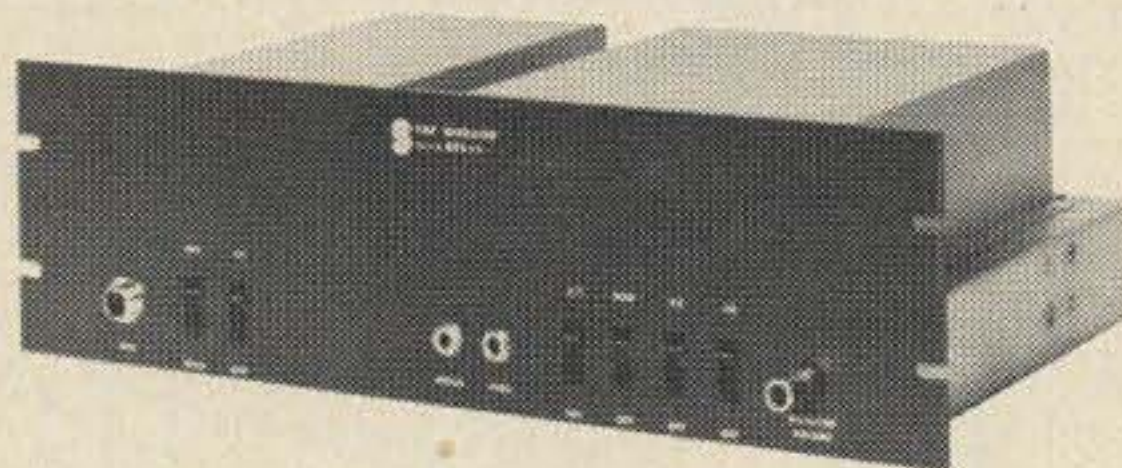All solid state, 2M, 10W, FM REPEATER. Built-in C.O.R., adjustable carrier delay and time out timer.



Write for complete specifications and cost.



**Standard
COMMUNICATIONS CORP.**

213 / 775-6284 • 639 North Marine Avenue, Wilmington, California 90744

SSTV SCENE

Dave Ingram K4TWJ
Rte. 11, Box 499, Eastwood Vil. 50N
Birmingham AL 35210

The 73 Slow Scan video program contest we first announced last month is off the ground, and happening right now until December 31, 1973, so get 'cracking on an outstanding program tape, (and I hear some of the gang really have some good ones planned) and win yourself a Robot Model 61 fast scan viewfinder. This contest is for the most interesting SSTV Program, with technical aspects also counting in the scoring. The "program" time limit is 6 minutes, and entry cassettes with sufficient return postage enclosed, should be sent to 73 Magazine. From here, they will go to "another" judge. The main objective of this contest is to get more fellows thinking and acting in terms of good programs, not just IDs and CQs. We're not stopping with just this contest, either. In February, we're joining with CQ Electronica of Italy in the 1974 Worldwide Slow Scan contest, and will present certificates to many U.S. and world leaders. More on this closer to that contest time.

Slow Scan continues to grow in popularity while also boasting some of the more exotic ideas in ham communication today. One example is a "SSTV Graphic Slate," which is presently being developed by W0LMD. This device would allow one to sketch out a Slow Scan picture, ID, schematic, etc., on the unit's built in cathode ray tube with a special "pen." This pen looks like a little pencil flashlight, but acts as a light sensor, rather than a light source. So, rather

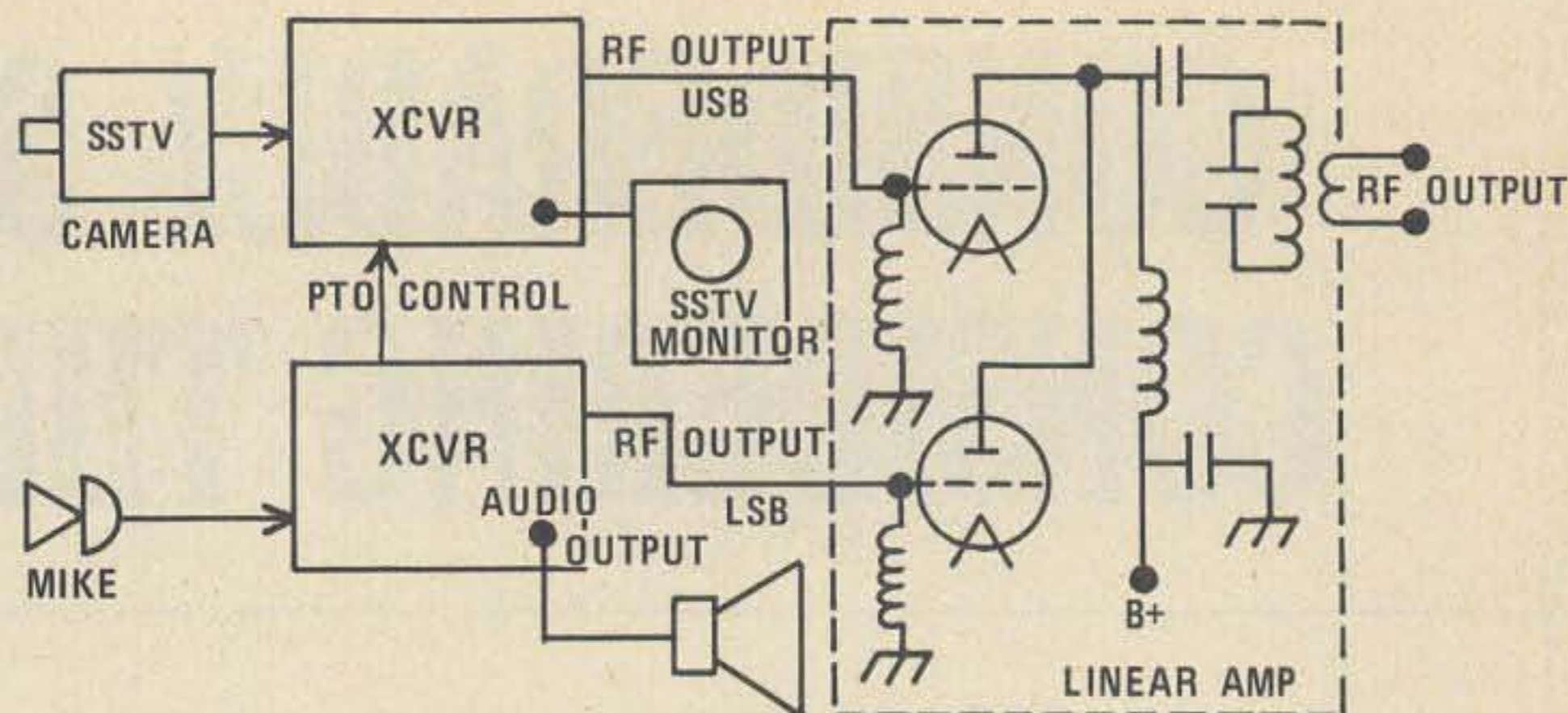


Fig. 2. ISB with two transceivers.

than actually marking on the crt face with ink, the "pen" makes lines which appear as black on the white raster of the crt. The drawn picture stays on the crt (and can be transmitted on Slow Scan) until the "memory erase" button is pushed, clearing the crt face, thus preparing for the next picture. Visualize the operation like this: An "overlay" of a schematic is placed on the crt, and traced out with the pen. The overlay is removed, and there, on the screen is the schematic. A block diagram of the unit appears in Fig. 1. Briefly, the unit works like this: A cathode ray tube produces a raster and a "light pen" generates a signal when light detection occurs at a spot pointed at. A 15,360 bit shift register memory traces the raster, and when the light detection occurs a blanking bit is set into the appropriate memory position. The detected light spot is then blanked on subsequent raster scans by a Z axis amplifier driven by the memory output. The drawn circuit, or message, is thus recorded on the refreshed crt "memory" screen. This drawing process continues until the desired picture is completed, then the memory clock slows down from 614 kHz to 1920 Hz to output memory at the SSTV rate. The crt is an old 9" TV crt, and the light pen uses a phototransistor and focusing lens

assembly. The unit's memory costs approximately \$60, and a complete unit would probably be around \$100. Incidentally, Robert also now has available schematics, scope patterns and descriptions of both the W0LMD SSTV keyboard and the W0LMD scan converter (approximately 13 pages worth!). Cost to reproduce and mail each set is \$1.25.

Another company, Venus Scientific Inc., of Farmingdale, New York, recently entered the Slow Scan field and should have their monitor available by the time you read this. Venus, as you may know, has built cathode ray tube high voltage modules for some time, so it was only natural for them to use some of them in such a related field as Slow Scan. Their monitor, designated the SS-2, is quite compact compared to other units and displays a picture of approximately 8.3 cm square. The unit is all solid state, completely self-contained, uses electrostatic deflection, and has a double purpose front panel control for either manual vertical retrace or frequency spectrum analysis (called accu-sync and similar to the system described in my June SSTV Scene column) of the incoming SSTV signal. The front panel crt bezel is constructed to accept an optional viewing hood or polaroid camera adaptor, and a front mounted "flip down foot" is provided for convenient viewing. The circuitry is primarily constructed on 3 plug in pc cards, which include LED sweep indicators for fast servicing in the field. Well, it sounds like manufacturers are getting hot on what Slow Scanners want, and are trying to deliver. I understand they are even working on a direct fast to Slow Scan converter. Fine! I have heard (through the "grapevine") the SS-2 crt is a special square face unit and suspect a special focus system may be used also. Since the "electron activity" is confined to a relatively small screen, brightness may be fairly high. Although I have not seen their unit as of this writing, I hope to shortly, so I can give you the full evaluation story.

An interestingly different approach to ISB (transmitting audio on one

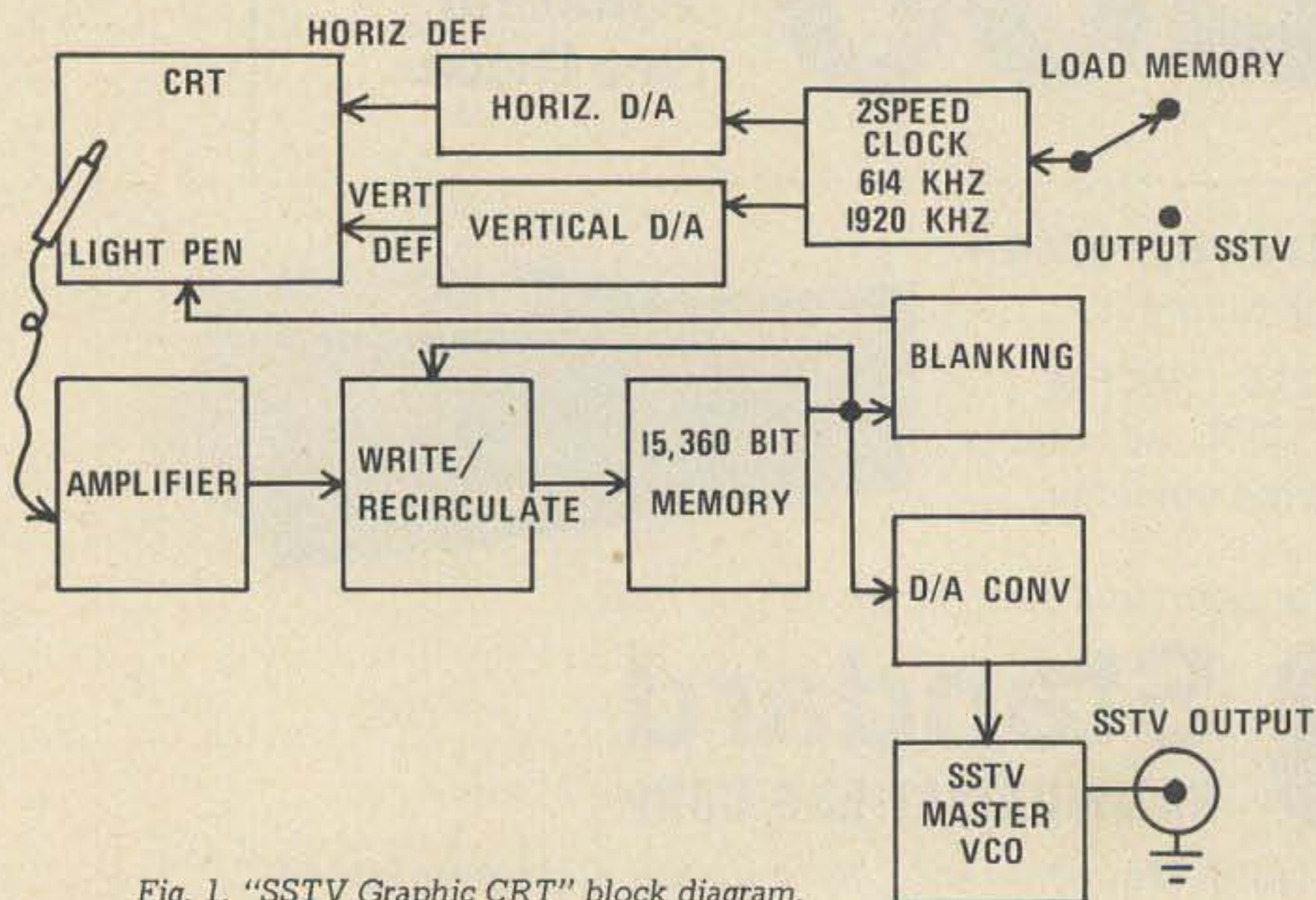


Fig. 1. "SSTV Graphic CRT" block diagram.

73

1st Annual



Magazine's RULES:

- 6 minute maximum time length
- Subject matter is limited only to your imagination — anything goes.
- Label cassette with your return address and include sufficient return postage. All programs will be returned.
- Decisions of the judges will be final.
- Contest starts now — entries must be mailed before December 31, 1973.

First Prize

ROBOT Model 61
Fast Scan Viewfinder

Other prizes to be announced.

Send your entry to: Slow Scan Contest, 73 Magazine, Peterborough, NH 03458.

band, and SSTV on the other band simultaneously) which is presently being investigated by Bill 4CVS, is shown in Fig. 2. Here, a pair of identical transceivers (like SB 01s) are shown feeding a common ear amplifier, (one using a pair of 400s, for example) whose plates are parallel, but control grids are fed independently from each transceiver. The "SSTV transceiver" is on upper band and the "audio transceiver" on lower sideband. Each tube in the ear amplifier amplifies its respective signal, and feeds it to the output tank circuit, thus resulting in an ISB output signal. A relay switching system connects each rig to a separate antenna on receive. Note, the two transceivers use common ptc, thus tracking together (but on opposite sidebands) to eliminate frequency "zeroing" problems. I believe Bob WA7MOV, tried a system somewhat similar to this a while back, in which the two transceivers fed one ear amplifier through a phasing line system, described in the Editors and Engineers Handbook as a "magic tee" network. I suspect others will be trying ISB before long by just using the old mobile rig on an extra antenna for audio, and the "big rig" on Slow Scan.

I have word that XW8CO, FM7WW and a certain KG6 should be on Slow

Scan about the time you read this, so you might like to keep your eyes and ears open (probably on 20m) for these new countries.

The Newtronics 4BTV Vertical



Model 4-BTV

Recently I found myself in need of a good omnidirectional antenna for the 40 through 10 meter bands. Often the band would be open in three

directions simultaneously, and I was missing too much DX which seemed to be always off the sides and back of my 3 element beam. Further, I was spending more time turning my beam than I was operating during large Slow Scan TV round tables. (There's enough fumbling in the shack already!)

At this point, I laid a dozen or so radials and erected my old (commercially built) trap vertical. My desires of coverage were met, and the results were gratifying. The bandwidth and SWR were not. In fact, the antenna was only usable on the upper portion of 20 meters, due to high SWR.

After careful study of the available antennas, a decision was made and a Newtronics 4BTV vertical was purchased. I put the antenna in my car (it's packaged in a nice, small box) and headed home.

The antenna and transmission line connectors went together smoothly within an hour, thanks to the fine instruction manual and tuning charts. If you go strictly by the chart, the antenna will work right off with low SWR on all bands. Naturally dimensions are given for either ground or roof mounting.

Then I went outside to mount the antenna and run more (approximately 15) radials. Here I found a dandy idea

Newtronics doesn't emphasize nearly enough. The antenna proper slips over and clamps to its base. Thus you can mount the base, run transmission line, radials, etc. Then just slip the antenna over it. This feature is extremely handy when tuning the antenna for your favorite frequency, as I will describe later.

The antenna worked perfectly from the start, with an SWR never over 1.3:1 on any part of any band. I was pleasantly amazed! QSOs with Europe and Australia the first day confirmed the antenna was working. Indeed, I often swapped between the beam and vertical during contacts, and the results were equal signal reports.

I measured the impedance with an Omega T noise bridge and again was surprised—48 to 52 ohms on all bands! (I'll never tell what my beam was.)

Newtronics was encouraging on fine-tuning the antenna, so I tried adjustment. Originally the resonant frequency (1:1 SWR and 51 ohms impedance) was 14.130 kHz. I retracted the 20 meter adjustment slightly, and moved the exact resonant frequency to 14.230 kHz, my favorite spot. Checking the extreme band edges now showed a 1.3:1 SWR. Thirty minutes later, I had the antenna tailored exactly to my needs on all bands.

The real proof of this antenna came during the first of 1973, as I tried for the 73 73 73 award (work 73 countries during the first 73 days of 1973). I accomplished it with over two weeks to spare, and used the 40-10 meter bands. Often the TR-4 was used barefoot. However, all contacts were made using only the 4BTV (and some of those were quite exotic DX).

Now the proof period is over and I'm still enjoying the antenna. Last night, for example, I exchanged good quality Slow Scan TV pictures with TU2DO on Africa's Ivory Coast.

I've heard a few people say verticals didn't work for them, or radiated poorly. Closer investigation with these people revealed they had not followed proper construction techniques (home brew) or instruction sheets (commercially built). Often the vertical(?) was mounted 15 or 20 feet above ground on a metal pipe, strapped to a chain link fence. Some used radials, some didn't. This is no good. *Follow the directions.* Either mount the antenna at ground level, with radials (preferably two for each band) or on the roof, *insulated* from ground with 45 degree drooped radials to form a ground plane. Then results will be optimum and I think you will agree the Newtronics 4BTV is tops.

K4TWJ

50 MHz BAND

Bill Turner WA0ABI
Five Chestnut Court
St. Peters MO 63376

The September contest came and went without much of a stir...the high point in the eastern half of the country was an excellent quality Aurora for a few hours Sunday afternoon. W8CCI, VE2DFO, WB2LZD/3 and several others were very active on scatter. Cross your fingers, perhaps December will be better.

How many suffered coronary problems when Rayburn KH6HPV, called CQ and recovered when they heard the portable 5 tacked on the end? Vern W0CYF, has returned to six after many years absence. Kevin W1GAO, mobiled from Boston to St. Louis and back making two meter contacts all the way. What, no six meter gear in the car?

Dick WA5CHK/DA1RG, writes from Germany that his tour of duty will be over after the first of the year and by early spring expects to be back in Houston with his TR-6, Mark 6B and four 9 element beams at 70'. Dick says he is active on the DC bands and 2 meters but nothing takes the place of six. He is looking forward to working scatter with K8LEE, K8MM, et al.

Bob WA2AAR writes to tell of a new narrow shift RTTY net becoming active on 50.130 in the New York-New Jersey area. The net, which doesn't have a name as yet, will meet Sundays at 11 AM eastern time. Anyone desiring more information may contact Bob at 164 Steuben Street, Jersey City NJ 07302.

From Art WA1EXN: "At about 1508 Z, July 30, W1ELP called me and stated he was hearing a CW signal at 50.158 and wanted me to monitor and see if I could also hear it. Here is what I got at S4 with QSB from 1510 Z to 1550 Z. Beam heading 160 degrees. GYS DE SWIE SP 768 K (with sometimes a K in place of the Y). We tried reciprocal headings, Bill could hear the signal, I could not...Does one of your readers have an answer as to just what we might be hearing?" In a later on-the-air conversation Art mentioned that the above had been heard again. Does anyone have the answer?

For several months I have been trying to find space for a lengthy and most interesting letter from Geoff Wilson VK3AMK. To get it in it has been necessary to edit rather severely and to bend Wayne's space limitations. Consider this my apology to both.

"The frequency allocation for all VK call areas is 52-54 MHz. Up until 1964 we had 50-54 MHz but lost the lower 2 MHz to TV. The band is now

sandwiched between our Ch. 0 (45-52) and Ch. 1 (56-63). The allocation of Ch. 0 was a very bad mistake as the QRM on this frequency is particularly bad during the summer sporadic E season when the three main high power Australian TV stations not only QRM each other but also cause QRM to TV reception in New Zealand on their CH. 1 (44-51). Operators in Melbourne and Brisbane suffer very much the same QRM troubles as U.S. stations operating near your Ch. 2. Despite this many stations are active in these areas. In fairly recent times there has been increased FM activity, mainly on 52.525 MHz and many stations use this frequency exclusively. The great majority of operators use AM or SSB, using the section 52.0-52.5. SSB is becoming increasingly popular with at present about 65% of the stations using this mode. AM on six is fast giving way to SSB except in the case of the younger operators just starting out, but even here some are going SSB. Until very recently there was no commercial gear available in VK apart from exservices or commercial equipment (surplus, ed.). At present about 50-60% of the SSB gear is commercial and with few exceptions consists of Yaesu FT-101s, FT-200s, etc., driving FTV-650 transverters. The power limits in VK are 150 W dc input or 400 W PEP output. But, very few stations are running this sort of power, mainly due to the extremely high cost of tubes.

The only recognized calling frequency is 52.050 MHz for SSB. This has been in use about two years and has worked out very well. There is virtually no CW on the band here except for meteor scatter operators. Many of the people on six are operating under similar licenses to your Technician class and *cannot* use CW.

The DX period is mainly late October to February which is our summer Es season. However, we are finding more and more that openings occur at any time and to help give a better picture of what is happening a number of beacons have been set up between 52-53 MHz, including several in VK0.

Normal contacts vary with location, equipment, etc. But, I can work most stations within 180 miles or so at any time with a pair of 6146Bs and a 6 element Yagi at 52'. I have kept daily skeds over a very mountainous path of 140 miles and never been unable to copy my report. Usual signals are about 5X6 each way with QSB to S9 plus at times.

Our normal Es season DX would average about 1000 miles single hop. From this area (Melbourne metropolitan) we mostly work stations on the Northcentral coast of VK4, about 300 miles north of Brisbane. I regularly work stations in this area during the summer months running 300 mW of SSB. We consider it a very bad season here if we don't

work VK1-8 at some time during the summer. There has not yet been a two-way QSO with the Antarctic continent. But another Melbourne station (VK3BFG) and I were copied by VKØPF during late 1971 but were unable to hear VKØPF's signals despite 20 meter liason. We usually work ZL stations each year but lack of activity there is discouraging. Stations in northern Australia regularly work JAs between 52 and 52.5. Very rarely do we get JAs further south, although they have been worked in VK7 fairly recently. The signals from JA come via F2 into northern VK and are carried from there to VK3 etc., via sporadic E extension. In other words, if the JAs are coming into VK4 and we also have sporadic E to that area we may hear and work JAs. In 10 years of concentrated activity there have been three really workable openings.

Back in 1958-59 VKs worked into XE, but since losing the lower 2 MHz of the band DX is much harder, not only because many stations do not operate in our section, but also because the MUF doesn't always rise that extra 2 MHz. (I often get ZL TV video on 46 MHz, but no sound on 50 MHz until the MUF really peaks up.) Northern VKs have worked HL, KX6, KH6, etc., apart from JAs recently."

With the recent increase in interest in reactivating TV Ch. 1 for educational purposes U.S. amateurs would do well to heed the warning in Geoff's letter and in the recent FCC 220 proposal.

...WAØABI



Tom DiBiase WB8KZD
708 6th Avenue
Steubenville OH 43952

CONTESTS

Oct. 27-28 CQ WWDX Contest, Phone
Nov. 2-5 CHC/FHC/HTH QSO Party
Nov. 5-11 QRPP CW QSO Party
Nov. 10-11 EX-G Contest
Nov. 24-25 CQ WWDX Contest, CW
Dec. 1-3 Delaware QSO Party
Dec. 15-16 EA (Spanish) Contest, CW

OCTOBER

CQ World Wide DX Contest, Phone
From 0000 GMT Oct. 27, to 2400 GMT Oct. 28, 1973. All bands 160 through 10. Three divisions: (a) single operator, single or all band (b) multi-operator, single transmitter (c) multi-operator, multi-transmitter. Only one signal per band permitted. Exchange

RS/T plus your CQ zone. QSO point values: 3 points between stations on different continents, 1 point between stations on the same continent but in different countries; contacts between stations in the same country are permitted for Zone and/or Country multiplier but have no QSO point value. Multiplier is sum of zones and countries worked on each band. CQ Zone and ARRL & DARC country lists are to be used. Final score: (a) single band - zones plus countries multiplied by QSO points (b) all band - sum of zones plus sum of countries from each band multiplied by total QSO points. Use a separate log sheet for each band, 40 contacts to the page. Indicate zone and country *only first time* it is worked on each band. See the appropriate issue of CQ for official rules and list of 25 trophies. Official log and summary sheets are available from CQ. Include a large SASE or IRCs. Address is: CQ World Wide DX Contest, 14 Vanderverter Ave., Port Washington, L.I., NY USA 11050.

SSTV PROGRAM CONTEST

The 73 Magazine SSTV Program Contest will no doubt be a big hit with Slow Scanners. There is plenty of time to get your program together since programs may be entered anytime between now until Dec. 31st. See page 7 for complete details.

NOVEMBER

CHC/FHC/HTH/QSO PARTY

From 2300 GMT Nov. 2, to 0600 GMT Nov. 5, 1973. More complete details available from IARS at the address below. Suggested frequencies are 3575, 3710, 7070, 7160, 14075, 21075, 21090, 21140, 28090, 3770, 3775, 3790, 3943, 3960, 7090, 7210, 7260, 7275, 14320, 14340, 21360, 21440, 28620, 28690, 50.1-50.5, 145-147. Exchange QSO number, RS/T, name, state and county (for U.S.), and give CHC number or FHC number. All who do not hold an IARS assigned CHC number are HTHers and send "HTH" as part of their exchange instead of CHC/FHC nr. Scoring system: CHCers score 1 point per QSO with other CHCers, 2 points if with an HTHer, count 1 additional point if contact - YL, blind/paralyzed, FHC, novice, VHF/UHF, CHC-200, merit, club station. Add above points. If contact was out of own country, double points for that contact. HTHers score 1 point per QSO with an HTHer, 3 points if with a CHCer, otherwise same as above. Same station can be worked on each band/mode. Each different continent, country, ITU zone and U.S. state is a multiplier. Each different band or mode

used is a multiplier. Multiply total QSO points by total multipliers. Multi-op stations divide total score by number of ops used. Appropriate awards. (CHC means Certificate Hunter's Club, FHC - Flying Ham's Club, HTH - Hunt the Hunters). Mail logs and contestant form (available from IARS) within 15 days after end of party to: IARS, Inc., Clif Evans K6BX, P.O. Box 365, Bonita CA 92002.

QRPP CW QSO PARTY

From 1300 GMT Nov. 5, to 2300 GMT Nov. 11, 1973. Exchange RS/T, state (or province or country), and QRP number. Non-members of QRP-ARCI send "NM" and power in watts instead of QRP number. Frequencies are, 3540, 7040, 14065, 21040, and 28040 (plus or minus 5 kHz of course). Stations may be worked once per band for multiplier points. Member contacts count 2 points, NM contacts count 1 point. Power multipliers are - under 1/2 watt output, X15, - under 2 watts, X10, - under 5 watts, X5, - over 5 watts output - no multipliers. Multiply total QSO points by total state/countries and multiply this by power multiplier for final score. Appropriate awards. Logs must be readable and include date, time, exchanges, stations worked, band and power used. Enclose a cover sheet showing your computation of equipment description and statement that all rules were observed. Logs must be postmarked by Dec. 3, 1973, and sent to Earl R. Lawler W5JLY, Rt. 2, Box 24-K, Burnet TX 78611.

EX - G CONTEST

From 0000 GMT Nov. 10, to 2359 GMT Nov. 11, 1973. Maximum operating time permitted is 24 hours. Minimum time off for short breaks is 15 minutes. The contest is in three sections: (1) reciprocal operators, (2) non-reciprocal operators, (3) United Kingdom operators. Any licensed frequency and mode. Suggested frequencies are, 3950, 7250, 14347, 21415, 28650. Only the first QSO between two stations shall count for QSO points. Contest exchange from reciprocal operators - RS/T, serial QSO number, club member yes/no, and original call. From non-reciprocal operators - RS/T, serial QSO number, club member yes/no. From UK stations - RS/T, serial QSO number, club member yes/no, original call (if reciprocal operator) and name of football (soccer) team they support. (All references to "club" above mean the EX-G club). Scoring: Reciprocal ops score 1 point per QSO with non-reciprocal operators, 2 points if with a reciprocal operator. Non-reciprocal

73 REPEATER ATLAS REGISTRATION

REPEATER CALL (WR only)		FORMER CALL		LOCATION (City)		STATE		
INPUTS	OUTPUTS	TT TB	Wh PL	FM RTTY	AM	AUTO PATCH	ERP	USEFUL RANGE (RADIUS)
			Hz					
			Hz					
			Hz					
			Hz					
REPEATER GROUP/SPONSOR		TRUSTEE		ID-TYPE OR MFR.				<input type="checkbox"/> SPLIT SITE <input type="checkbox"/> DIPLEXER
<input type="checkbox"/> I certify that I have received no outside assistance while completing this form.								
DATE	SOURCE (NAME/CALL)		SPECIAL OR EMERGENCY FUNCTIONS					



AL	WA4UAG	Huntsville	145.992-147.120
AL	WR4ACB	Birmingham	146.16-146.76
AL	WR4ADD	Birmingham	146.34-146.94
AZ	WR7ABM	Tucson	146.28-146.88
AZ	WR7ABL	Payson	Planned
CA	WR6ACK	Santa Monica	147.93-147.33
CA	WR6ABX	Sacramento	146.37-146.97
CA	WR6ACG	Bishop	146.34-146.94
CA	WR6AAA	Catalina Is.	147.69-147.09
CA	WR6ABB	L.A.	146.01-146.61
CA	WR6AAD	L.A.	147.96-147.36
CA	WR6AAE	L.A.	146.22-146.82
IL	WR9AAF	Chicago	146.34-146.94
IL	WR9ABQ	Elgin	146.19-146.79
IN	WR9ABA	Indianapolis	146.10-146.70
IN	WR9ABI	Elkhart	146.04-146.64
IN	WR9ABO	Muncie	146.13-146.73
IN	WR9ABR	Columbus	146.19-146.79
KS	WR8ABU	Kansas City	146.22-146.82
KS	WR8ABV	Lenexa	52.88-52.525
KY	WR4ACD	Owensboro	146.34-146.94
KY	WR4ACR	Lexington	146.16-146.76
MA	DL2AA/WR1	Medway	147.81-147.21
MO	WR8ABP	Barry	Closed
NC	WR4ABQ	Aurora	146.34-146.94
NB	WR8ABQ	Omaha	146.34-146.94
NY	WR2ABP	Bedford	147.705-147.105
NY	WR2ACD	Manhattan	146.40-147.00
OH	WR8ABT	Cheviot	146.07-146.67
OK	WR5ABW	Enid	146.34-146.94
SC	WR4ACD	Columbia	146.34-146.94
SD	WR8ABX	Sioux Falls	146.16-146.76
TN	WR4ACS	Nashville	146.16-146.76
TN	WR4ADA	Chattanooga	146.19-146.79
TX	WR5ABN	Midland	146.16-146.76
WI	WR9ABE	Baraboo	146.28-146.88
WI	WR9ABI	Madison	T2100 146.16-146.76

operators score 0 points with non-reciprocal operators, 2 points per QSO if with a reciprocal operator. Multiply QSO score by number of EX-G club members worked. Bonus points — multiply number of British stations (G, GB, GC, GD, GI, GM and GW prefixes only) operating from the UK by the following factors depending on your location: EU — X1, NA/SA — X3, AF, north of Lat. 10°N — X2, AF, south of Lat. 10°N — X3, ASIA, west of Long. 90°E — X3, ASIA, east of Long. 90°E — X4, AUSTRALASIA — X5. Multiply total QSO points by club member multiplier and add bonus points for final score. Appropriate awards. Logs before Dec. 25, to: Contest Committee, EX-G Radio Club, J. Kasser G3ZCZ/W3, Chairman, 1701 East-West Highway, Apt. 205, Silver Spring MD 20910 USA. SASE for results.

CQ World Wide DX Contest, CW
From 0000 GMT Nov. 24, to 2400 GMT Nov. 25, 1973. All other rules same as phone section. Complete details elsewhere in this column.

To date I have no information on the ARRL Sweepstakes Contests other than the dates. Nov. 10-11 is the Phone SS; the CW section is Nov. 17-18. You'll have to check the appropriate issue of QST for further details.

All contests this month appear to be international in coverage, so if you are a DXer, you could do worse than to enter a few of them. The CQ DX Test would be your best bet, of course. The SS Tests are not international in coverage, yet they are about the best contests around for USA and Canadian contest buffs. I will definitely be operating in the WWDX tests and the SS tests and hopefully a few of the others this month.

WB8KZD



Joe Kasser
1701 East-West Highway, Apt. 205
Silver Spring MD 20910

The frequency of the month is 144.480 MHz. It is widely used for simplex working in Europe and is also a repeater input frequency in Hong Kong. This month let's consider the two meter frequencies in use in Europe. Most countries in Europe have up to now "band planned" the occupancy of the 144-146 MHz (all

they have) on a geographical basis. Stations in one area concentrate their signals into a section of the band, stations in another area use a different section of the band. Thus, when tropospheric openings occur hams know where to tune for the DX. Separate country wide frequencies are allocated for beacons, SSB or CW. All this is done on a voluntary basis by the hams themselves through their national societies and is not written into their licenses.

HOLLAND

Holland has no repeaters at present, but they have allocated simplex channels on a regional basis as follows:

Amsterdam	144.480 MHz
The Hague	144.800 MHz
Utrecht	144.700 MHz
Rotterdam	145.600 MHz

ENGLAND

FM Calling Channel	144.480 MHz
Mobile Calling (AM and FM)	145.00 MHz
Working South of England	144.400 MHz
Working London Area	144.800 MHz
Working Midlands	145.200 MHz
Working North of England	145.600 MHz

Europe is channelising the 145.00 to 145.900 segment of the band for FM with channels spaced every 25 kHz. The agreed new IARU channels for England are:

FM Calling Channel	145.500 MHz
Working Southern	145.525 MHz
Working London	145.550 MHz
Working Midlands	145.575 MHz
Working Northern	145.600 MHz

The idea being to establish contact on the calling channel and then QSY to a working channel. It will be interesting to see what happens when repeaters come into general use in England. The calling channel will then be the repeater channel, I suppose.

G3ZGO writes from London as follows: He suggests that visitors have 145.000 MHz and a means of copying AM (I suggest that the visitor carry a police band monitor that tunes down to 144.000 MHz. I used one in conjunction with a TR-22 last time I visited Europe and it worked out fine.). For built up areas he suggests 144.480 MHz. For very built up areas have one of the working channels too. For London have 144.800 MHz, as it will be nearly impossible to QSO on 144.480 MHz during busy times. In England the TR-22 comes with the following three channels fitted as standard: 144.48, 144.72, 145.32 MHz. The two meter band is shared with aeronautical services in England and several spot frequencies must not be used by hams. One of them is 144.72 MHz. So the rigs are usually tuned up

to 144.725 MHz. Lastly, 145.32 MHz is used by SSB stations and they QRM the FM boys.

According to OHM Magazine there is at least one repeater in Hong Kong. The frequency is listed as 144.48 In — 145.64 Out, and there are over 20 VS6's active on two meters.

If you are going mountain climbing in Switzerland you might consider taking your handi-talkie with you. This summer one W3/HB9 worked into Italy, Austria and Czechoslovakia using an HT220 fitted for 145.000 MHz from the top of the Matterhorn. Some hams really live it up.

...G3ZCZ/W3



FCC NEWS

FCC EXTENDS TIME LIMIT FOR REPEATERS

Adopted: August 29, 1973 —
Released: August 30, 1973.

By Acting Chief, Safety and Special Radio Services Bureau.

1. The Commission has under consideration, on its own motion, the extension of the license term of all amateur stations licensed prior to October 17, 1972, and operating to automatically retransmit the radio signals of other amateur radio stations or as remotely controlled stations prior to that date. The purpose of our action herein is to preclude any unnecessary interruption of any on-going service due to delays in processing applications.

2. In Docket 18803 the Commission adopted rules pertaining to the licensing and operation of amateur repeater stations. Those rules became effective on October 17, 1972. All stations licensed after October 17 had to comply with those rules. However, to provide continuity of operation and to assure continued public service activities, existing repeater stations were granted a grace period to June 30, 1973, to bring their operations into full compliance with the rules and to obtain a new license. At the request of the American Radio Relay

League this period was extended to August 30, 1973.

3. We find that more than adequate time has been given to those previously existing stations to allow their operations to be brought into compliance with the rules. However, because of the initially heavy administrative work load imposed upon the Commission, the fact that initially filed applications were generally inadequate, and because of the lack of processing personnel during the summer months, we find that there has been inadequate time for all existing licenses to actually receive their license documents evidencing their full compliance with the rules. Therefore, we will allow all amateur stations licensed prior to October 17, 1972, which were operating to automatically retransmit radio signals of other stations or as a remotely controlled station, and for which a timely and sufficient application for renewal or modification was filed to continue operation until final action is taken on the application. An application will be considered as being timely filed if it was received by the Commission on or before August 30, 1973. The application will be considered as one for renewal or modification if it proposes to license transmitting apparatus which was previously operated as a repeater or remotely controlled station.

4. Accordingly, the Commission by the Chief, Safety and Special Radio Services Bureau, pursuant to the delegated authority in Section 0.331 (b) (1) of the Commission's Rules, ORDERS that all amateur stations licensed prior to October 17, 1972, which were automatically retransmitting radio signals from other amateur stations or licensed as remotely controlled stations and for which a timely and sufficient application has been filed, may continue to operate until such time as the Commission takes final action on the application.

FCC

Charles A. Higginbotham
Acting Chief, Safety
and Special Radio Services Bureau

..... BUT BLAMES AMATEURS FOR PROBLEMS!

There apparently has been some confusion among amateur licensees as to the actual effective date of the rules adopted in Docket 18803. The Commission reiterates what should be clear to all amateur licensees that the rules became effective October 17, 1972. Licensees have been informed in the Report and Order, the Memorandum Opinion and Order, and by several Public Notices and Orders, that full compliance was expected as soon as possible but not later than June 30,

subsequently all licensees have had adequate time in which to modify their operations and fully comply with our rules, although there may not have been sufficient time to obtain the licensing authorizations for repeater station, control station, and/or auxiliary link station. Licensees operating such stations under a previous authorization are cautioned their operations must otherwise fully comply with the rules. Licensees and control operators of stations not operated in compliance are subject to appropriate enforcement action.


An excessive number of problems are being encountered with defective amateur repeater station applications, contributing to wasted effort and length processing delays. The principle problems are lack of standardization, failure to supply the required information, and/or failure to present the information in a manner permitting expeditious processing. Using the experience in processing thousands of these applications, suggest application forms designed to eliminate the most frequently encountered errors, are being developed. Whether these forms will be adopted as official FCC forms is undetermined. However, properly prepared applications based upon these suggested forms will be acceptable for processing. Amateurs are encouraged to develop more universally accepted terms and symbols for use in their applications.

...FCC



Bill Pasternak WA2HVK/6
14732 Blythe Street #17
Panorama City CA

It is easy to blame Mr. Walker for all that has taken place, but in retrospect isn't a good part of it our own personal fault? Most of us just sat back and waited to see what would happen, instead of doing something about it. We looked to people like Wayne to carry the ball for us. We laughed at the idea of a professional Amateur Radio lobbyist fighting for the kind of legislation that would advance our hobby rather than retard its growth. We sat there and per-

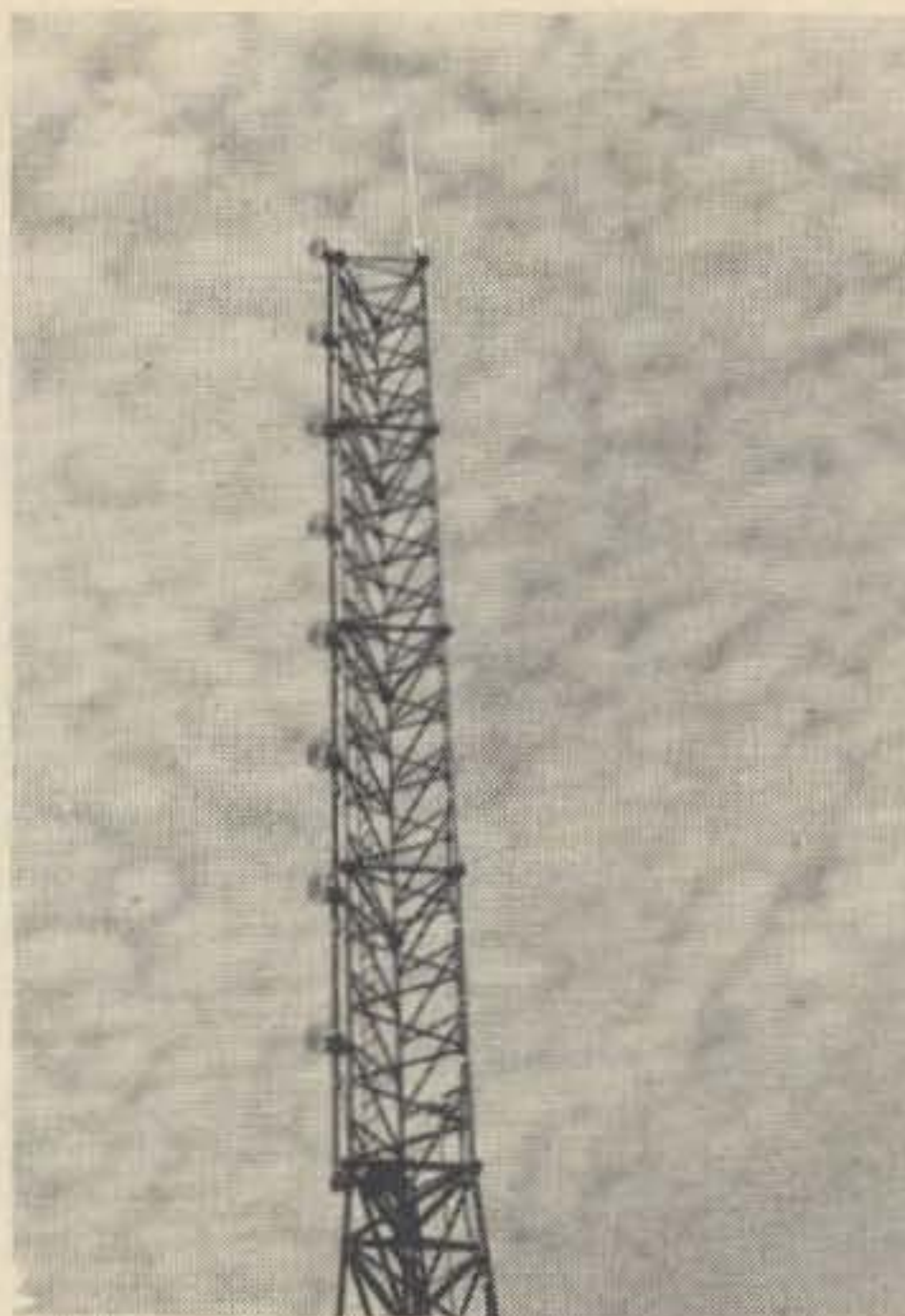

WR6ABE's new antenna atop Mt. Wilson.

mitted the rug to be pulled from under us. I only hope that it is now not too late to reverse the trend. If we don't our days may be numbered.

What we need is mass public support and an image both recognized and well respected by the general public. We can no longer afford to wrap ourselves up in our own private world of tubes, wires and transistors. We must get out of our shacks and meet the public face to face and convince them that we are a necessary minority in the American society. How? Contact local Civic groups and alike and offer to speak to these groups about what we are and what we can do. Get to know people at one of the local radio or TV stations, and if you are lucky, maybe you can convince them to do a spot or two highlighting amateur radio on their public affairs programs. There are many other ways, both thru the mass media and direct personal communication. Use your imagination.

Larry K6YLQ, in Oxnard reports to me about one real long haul repeater contact that transpired July 28 and 29, when a number of local amateurs found themselves keying up the KH6EQN 16/76 repeater some 3000 miles west of here in Hawaii. Now that's what I call DXing a repeater. Larry, who is with the WA6SIN repeater group drove up to the site to install a 16/ transmit crystal in the remote base portion of their machine and could hear the KH6EQN repeater atop Sulphur Mountain on his HT. He informed me that some of the other stations in this area who worked Hawaii during this opening were K6DYD, K6YNB and WB6OBB. He has a good part of it recorded on cassettes.

One of the guests who visited my home this summer was Abe Schwartz

WB2PQR, Vice President and one of the original founding members of the Kings County Repeater Association. Abe's visit was more than a vacation. I still keep an active interest in my old group back east and I knew that they were in need of some equipment to get ZWP back on the air again. By the same token, I knew that Burt K6OQK, needed a new transmitter for his WR6ABE repeater atop Mt. Wilson. Since Abe and KCRA had access to what Burt needed, and Burt possessed the goodies that KCRA was looking for, a coast to coast swap was arranged and both sides are more than content.

While on the topic of WR6ABE, they now have a new Super Stationmaster and Duplexer for the machine, along with the replacement transmitter. That Stationmaster is at the very top of the tower and has not only extended the already fantastic coverage, but virtually eliminated most of the old dead spots. It took an all night work part to do the installation, but the results were worth the effort.



Just add 150' of tower and 24' of antenna.

It looks like another 34/94 repeater has failed out here. This information comes from the source, the repeater's owner Bill Ogg WA6NGA. Like others in the past his effort to get a 34/94 open repeater going met the same strong opposition from those who use .94 as a simplex channel. After trying unsuccessfully to maintain the .94 output, Bill informed me that for the time being he has moved the output of WR6ABQ to 147.12, while maintaining the .34 input. Whenever the machine was put on the air there were numerous unidentified signals appearing on the input. This "jamming," coupled with the tremendous amount of high power simplex and remote activity already on .94, made the machine useless. It is evident that for the foreseeable future 146.94 will remain simplex. Though this is a loss to the traveling ham who visits L.A., it is evident that the majority of our 2m population seems to favor no repeater on 34/94.

... WA2HVK/6



I'm AL WØJJK

What's in a name? These below are leading manufacturers. Likewise, mine is known to thousands of hams around the country and, I believe, WØJJK has a reputation for fair and dependable service. Please let me quote your needs!

Best of DX - 73, Al WØJJK

galaxy Clegg Cush Craft CDE

hugain MILLEN

TRIPP LITE

Weller SUPEREX

JOHNSON

Calrad

SAMS

TRISTAO

Panel Meters

"VIBROPLEX"

TRIMM

SHURE

AMECO

E-Z WAY Products, Inc.

TEN-TEC

HUSKIER

TURNER

GONSET

SBE

LMB

AMIDON

TEMPO DRAKE MISCO

"KENWOOD"

WZAU

SWAN

B&W

PR CRYSTALS

Regency

Masley

hallicrafters

When you need "ham" gear & accessories.....call H. I. !




Hobby

Industry

CALL: Tues./Sat.-Noon/5PM
Al McMillan WØJJK
(712) 323-0142

WRITE: HOBBY INDUSTRY
Box 864
Council Bluffs, Iowa - 51501

AMSAT NEWS

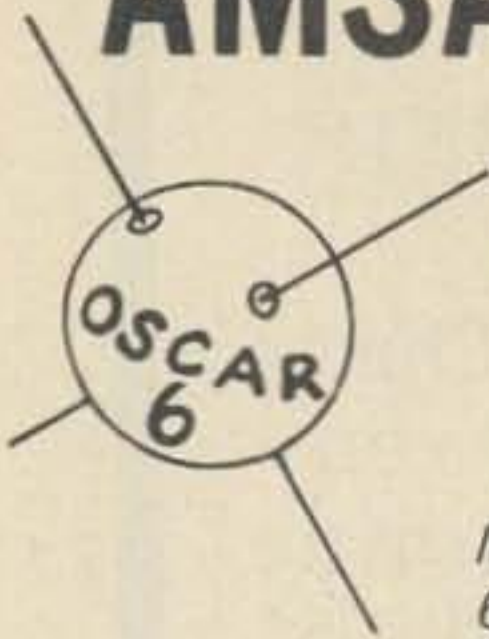

Michael Frye WB8LBP
640 Deauville Dr.
Dayton OH 45429

Activity at AMSAT headquarters is gaining momentum. With OSCAR 6 nearing its expected lifetime, AMSAT is moving full speed ahead on OSCAR 7. Already funds have been set up and work has begun with an eye toward an early 1974 launch.

Tracking OSCAR 6 can sometimes be a difficult task. Someone has finally come up with an idea to permit amateurs to track OSCAR reliably time after time. William D. Johnston WB5GBG, has devised a plan using some of the characteristics of the satellite's orbit to provide each amateur with a computer printout that details the time the satellite will be overhead, the azimuth and elevation, plus distances for the entire pass. Because OSCAR 6 is in such a stable orbit we can predict orbital data to a very accurate degree far into the future with relatively no loss of accuracy. Furthermore the satellite has a repeating period of 263 orbits which means that the orbital data is the same every 263 orbits. This occurs about every 21 days, so that every 21 days the azimuth and elevation are the same. There are a few discrepancies in this, but the error is only about 7 or 8 minutes over a few months time which is easy to correct. Interested amateurs can write for more information to Bill Johnston WB5CBC, 1808

Pomona Dr., Las Cruces, New Mexico 88001.

If you would like a printout please send your: 1. Name and mailing address. 2. Latitude (indicate north or south) and longitude (east or west) in degrees, minutes and seconds. The local county or city engineer has this information in most areas. 3. Altitude above sea level (in feet or meters). 4. A SASE 9" by 12" or larger (not required for stations outside the U.S.A.) postage should be 48¢ for first class or 66¢ for airmail. The cost is \$2.50 for U.S.A., Canada and Mexico \$3 for first class and \$3.20 for airmail (includes postage) and all other locations \$3.50.

Many interesting and unusual operations are being reported from amateurs using OSCAR 6. A few of these are DXpeditions by FP8AA, PJ7VL, PJ9JT and ZK1TA and an aeronautical mobile by W6OAL. OZ7DX reports preparing for maritime mobile operation from the "Dana," a Danish research vessel. RTTY operation has been reported by VK3YDB, G3CUO, W6OAL and WA3EWJ. W9NTP, WA9UHV and SM60H all reportedly have been active on Slow Scan Television, and WA6GUY reports successful facsimile transmission to WA3FVG/6 via the satellite. In addition, SSTV and audio tone ranging tests have been conducted by DJ4ZC, who uses the data for satellite orbit determination. Finally, all fifty U.S. states have been worked and confirmed by W3TMZ (shown in picture), who qualifies for the first OSCAR Worked All States award.

On June 30, AMSAT's board of directors authorized an acceleration of the AMSAT-OSCAR-B satellite project for completion in time for launching during the first quarter of 1974, and authorized additional expenditures (estimated at between \$38,000

and \$40,000) for the project. The required additional funding covers the salaries of two engineers and two aerospace technicians employed full-time by AMSAT. Also, funds for needed space-qualified components and ground support test equipment are provided by the ARRL and individuals who have made donations specifically for the purpose of completing the A-O-B spacecraft as rapidly as possible. General membership dues and general donations are not being used.

Assisting with A-O-B development are several groups in addition to the Washington area AMSAT members. These include the newly incorporated AMSAT Deutschland e.V., AMSAT's affiliate in Marburg, Germany (under the leadership of Dr. Karl Meinzer DJ4ZC, and Werner Haas DJ5KQ), QIA-Project Australis in Melbourne, Australia (particularly Dr. Peter Hammer VK3ZPI), the Jet Propulsion Laboratory Amateur Radio Club and the San Bernardino Microwave Society in southern California, and a group headed by Larry Kayser VE3QB, in Canada. Other individual AMSAT members in other locations include John Goode W5CAY, who is constructing another Codestore unit.

One final note for the amateur who would like to learn more about satellites and how they work, complete with a history of man's first attempts to orbit such a body. Stanley Macko's book 'Satellite Tracking' appears to be one of the easiest to understand and one of the most descriptive books I have found.


Orbit	Date (Nov.)	Time (GMT)	Longitude of Eq. Crossing W
4775	1	0008.7	49.8
4788	2	0103.6	63.5
4800	3	0003.5	48.5
4813	4	0058.5	62.2
4826	5	0153.4	76.0
4838	6	0053.3	61.0
4851	7	0148.3	74.7
4863	8	0048.2	59.7
4876	9	0143.1	73.4
4888	10	0043.1	58.4
4901	11	0138.0	72.1
4913	12	0037.9	57.1
4926	13	0132.9	70.9
4938	14	0032.8	55.8
4951	15	0127.7	69.6
4963	16	0027.7	54.6
4976	17	0122.6	68.3
4988	18	0022.5	53.3
5001	19	0117.4	67.0
5013	20	0017.4	52.0
5026	21	0112.3	65.7
5038	22	0012.2	50.7
5051	23	0107.2	64.4
5063	24	0007.1	49.4
5076	25	0102.0	63.2
5088	26	0002.0	48.1
5101	27	0056.9	61.9
5114	28	0151.8	75.6
5126	29	0051.8	60.6
5139	30	0146.7	74.3




Jack Colson W3TMZ, first to work WAS via OSCAR!

... WB8LBP

QSL CONTEST

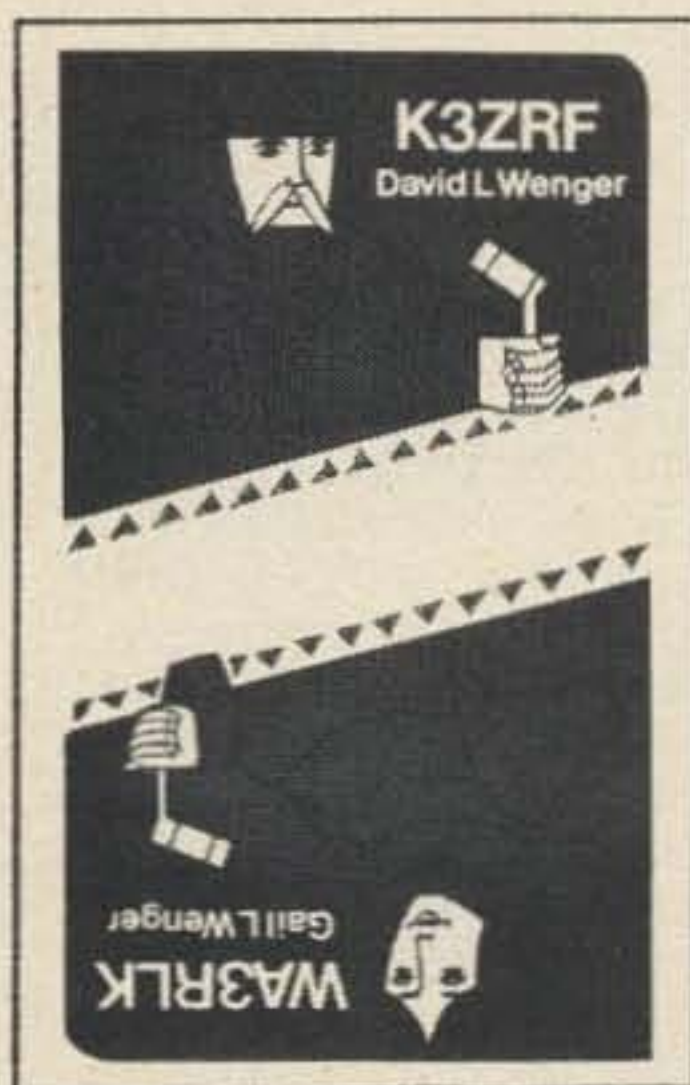

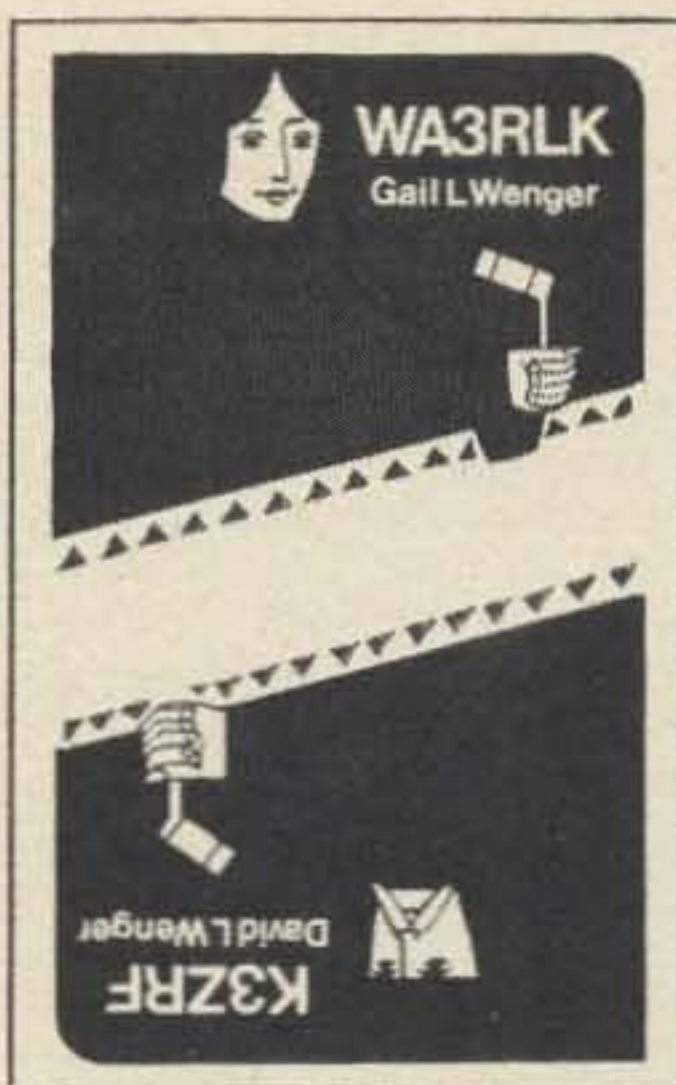The winner(s) of the November QSL Contest are David (K3ZRF) and Gail (WA3RLK) Wenger of Lititz PA. The total inability of our contest judge to decide which side was actually the top resulted in the card's being reproduced twice. Win a one year subscription! Send your entry to: QSL Contest, 73 Magazine, Peterborough NH 03458.



HAM HELP

This column is for those needing help in obtaining their amateur radio license.

If you are interested, send 73 your name, address and phone number. Don't be bashful—remember, it's always easier when you have someone to give you that added bit of confidence.

73 would appreciate amateurs and clubs looking this list over and helping whoever they can. Do you remember when you needed help?

Alan Kline
220 S. Common St.
Lynn MA 10905
598-6010

Ray Calabro
210 Country Club Dr.
Warwick RI 02888
401-781-4084

Greg York
RR 2, Box 434
Three Rivers MI 49093
616-279-2534

Robert White
365 Clinton River Dr.
Mt. Clemens MI 48043
468-4746

Allan Kowal
21-2800 Allwood St.
Abbotsford B.C. Canada
859-7928

John Diecker
9968 Northampton Dr.
St. Louis MO 63137
314-868-2905

James Taylor
1516 Sheley Rd.
Independence MO 64052
816-252-4844

INTRUDER CHASE

Jonathan Tara WB8DBN
16260 Greenfield
Detroit MI 48235

You're sitting there on 7240 having a nice QSO when suddenly your ears get socked with a 50 over carrier. Then, "This is the BBC transmitting to Australia." You grumble, "It's them damn ferren broadcasters again." But what can you do, it is legal if they don't point it at us, isn't it? Out of curiosity you look up at the time zone map. "Hmmm, it's 2:30 in the afternoon in Aust. . . England to Australia? . . . at 2:30 in the afternoon? They're out of their bleeping minds!" What to do? Write to the BBC? Naw, Heaviside was one of theirs, they will

claim that the ionosphere never sets on the British Empire. How about the Intruder Watch? That is no good either, they just sit there and watch. "Hey Joe, let's move up 5, I can't hear you through Big Ben. . ."

Sound familiar? Then, congratulations! You have just given in to an intruder! You are not alone, though. This is the reaction most hams have to intruders. You get mad at first, then realize that there is nothing you can do.

Introducing the 73 Intruder Chase! The Intruder Chase is just what the name implies. It is intended to get rid of intruders *now*, not at the next frequency allocations conference. If we wait that long, as the ARRL seems to be doing, *we* will be the intruders! Before you start yelling at me for trying to dump the ARRL, let's take a look at the intruder situation in general.

Who Are The Intruders?

Take a look at the frequency table. 160m and the first 400 kHz of 80m are allocated in various parts of the world to non-broadcast services. Ah ha! So that's what all those funny

FREQUENCY ALLOCATIONS

Frequency (kHz)	Intruders
1800-2000	Any U.S. or Canadian non-amateur except Loran. Broadcasting anywhere.
3500-3900	Broadcasting anywhere.
3900-4000	Broadcasting to or from Western Hemisphere. Any U.S. or Canadian non-amateur.
7000-7100	Any non-amateur.
7100-7300	Broadcasting to or from Western Hemisphere. Any non-amateur except broadcasting.
14000-14250	Any non-amateur.
14250-14350	Any non-amateur, except for fixed station in the U.S.S.R.
21000-21450	Any non-amateur.
28000-29700	Any non-amateur.

QTH CHANGE?

To be absolutely sure that 73 will follow you to your new QTH, try to notify our Subscription Department at least 8 weeks in advance of your move. Please include your old address and call as it appears on your current mailing label — or better yet, send the label itself.

OLD ADR (or mailing label)

NAME _____ CALL _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

NEW ADR

NAME _____ CALL _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

DXCC

DXCC Department
ARRL
Newington CT 06111

73 MAGAZINE
PETERBOROUGH
NEW HAMPSHIRE 03458

9 Sep 73

A trouble-making reader has been bugging me about a little DXCC problem — and perhaps you can clarify the situation. He points out that we accept (you accept, I should say) contacts with unlicensed ops in certain countries such as Turkey and Afghanistan. Then, since the UN building should count as a new country, even though it is in NYC (as Vatican and SMOM count in Rome), shouldn't unauthorized contacts from there count for that country? Please advise. To further complicate matters — embassies are on foreign ground too — as are some memorials — will operation from these spots count as more countries? Unless you change your DXCC rules it would appear that you will have to accept these. This could start a rash of HT operations from embassies — perhaps even low powered low band operations, clandestine or authorized. Would official authorization have any effect on the situation?

Perhaps we are on the verge of bringing out several thousand more countries?

73 . . . wayne green



THE AMERICAN RADIO RELAY LEAGUE, INC.

ADMINISTRATIVE HEADQUARTERS NEWINGTON, CONNECTICUT, U. S. A. 06111

HARRY J. DANNALS
WYTK, PRESIDENT
CHARLES G. COMPTON
WBRU, FIRST VICE PRES.
ROBERT W. DENNISTON
WBDL, VICE PRES.
ROEMER C. BEST
WQWV, VICE PRES.
DAVID H. HOUGHTON
TREASURER
JOHN HUNTON
WYRW, SEC. & SEN. MGR.

QST
OFFICIAL JOURNAL

September 17, 1973

Mr. Wayne Green
73 Magazine
Peterborough, New Hampshire 03458

Dear OM:

Thanks for your letter of September 9.

Sorry to hear one of your readers is making trouble for you. Afraid I can't be much help in clarifying that kind of thing for you. If I could, would I be sitting here at 06:45? However, was reading a book the other day that you might find interesting, if not helpful. The title was "I'm OK, You're OK."

Presuming you've read it, that bit in it about the games children play having to do with things like: . . . what would you do if you found yourself standing in the middle of a pool of liquified crud, up to your chin, and someone threw a bucket of slop at you? . . . sounds pretty much like what your reader is asking you. If you start from that point and take on from there, it may clarify the situation for you.

73-DX,

R. L. White, W1CW
Assistant Communications Manager

RLW/fr

SINCE 1914 — OF, BY AND FOR THE RADIO AMATEUR

NEWS

bleeps and bleeps are! Unfortunately, those bleeps and bleeps are legal. A common intruder in this part of the amateur spectrum is your local broadcast station — one of its harmonics. For some reason, this seems to be worse during the day. Maybe that is because more "cheapie" stations are on during the day.

40 METER PICNIC

Frequency	Station	Time	Language
050	R. Cairo (V. of the Arabs)	0300-0800	Arabic
065	R. Tirana	0430-0500	Arabic
090	R. Tirana	0430-	
120	R. Peking ¹	0100-0155	English
150	R. Moscow ¹	0100-0500	English
150	BBC ²	0545-0915	English
240	BBC ²	0545-0915	English

North American Service
Australian Service

40m is where the *real* fun begins. 7000 to 7100 kHz is an exclusive amateur band world wide, although you wouldn't know it by listening. *Anyone* other than an amateur caught between 7000 and 7100 kHz is illegal. 7100 to 7300 kHz is allocated to the broadcast service in the Eastern Hemisphere. The "catch" here is that they are not supposed to broadcast to the Western Hemisphere. Of course, this rule is not always observed. Some stations, like Radio Moscow, will come right out and say, "North American Service," in their schedules and on the air. Others are more sneaky, like the BBC case cited above. A good indication as to where they are *really* broadcasting to is where the letters on their mailbox program come from. If all the letters are from Podunk, Iowa, and they claim the broadcast is going to Outer Slabovia, you know there is something fishy. If there is a band on everyone's *WANTED* list after 220, it must be 40.

Intrusions occur less frequently on the higher bands, but they still happen. Usually the intruders on the higher bands will be "utility" type transmissions (Teletype, FAX, etc.). I remember once that there was a huge multiplex teletype signal parked on 20m. It had a signal every 2½ kHz from below 14000 up to about 14250! Another type of intruder in the higher amateur bands is harmonics from broadcast stations on lower frequencies. Thus, the same signal that is creating havoc on 40 can be QRM-ing 20 at the same time. After complaining to the BBC about a harmonic of theirs on 20m, they apologized and said that they had reduced the level of the harmonic 6 db, while at the same time maintaining that they did nothing illegal in the first place!

Next month I'll discuss what can be done about intruders. In the mean

time, if you want to know more about the Intruder Chase drop me a line. I plan on an Intruder Net, so if you are interested in the net, please let me know so we can get one started. Also, if you have any "contributions" to the intruder list, please send them in.
WB8DBN



The Hamburglar STRIKES AGAIN!

AF68 No. 10888	K5LKL	1/73
PMR8 No. 10918		
M1070 pwr supply		
Trio TR2200 No. 241969	WA2ZBV	1/73
Clegg 22er No. 1900-578	WIDHP	2/73
Standard 826M, No. 112007	WA8PCG	3/73
FM27B No. 27013-1141	W2LNI	4/73
FM-144-10L No. F459	WA6WOA	4/73
NPC 107m pwr supply		
2, 5AJ-IPL Onan Gen., No. 327885		
R4B No. 11578G	WA8GVK	6/73
T4XB No. 17801 G		
W4 wattmeter No. 8390		
Swan 250 No. F154806		
Swan ac pwr. sup. No. 0653556		
HR-2 No. 04-C2879	W6GSR	6/73
SB-34 No. 211828		
STD 826 No. 011268	WA2FSD	6/73
HT220 No. GJ7327	State Univ. of NY (Albany)	6/73
Yaesu FT-101	W4GF	7/73
No. 82G12279/CW		
HR-2 No. 0302030		
Clegg 27B No. 72013-1068	W3BXL	7/73
Std. 826MA No. 208078	WB2DEW	7/73
Drake ML-2 No. 10582	W3MSN	8/73
Tektronics 453 Scope	WB2FZU	8/73

NEW PRODUCTS

CASSETTE RECORDER SPECIAL



combination ac or self-contained battery operated cassette recorder — with the new one control feature instead of the old piano key type control.

This cassette recorder is ideal with 73's code course since it can be operated anywhere — at home — in the car — in the office (maybe in the drawer, with the earphone for silence). The single control switch is excellent for use in the car where you don't want to have to take your eyes off the road to use the recorder — to operate it for copying in your mind — for instant rewinding or fast forward. And this control doesn't have to be held either, a nuisance on most recorders.

Comes complete with four "D" batteries, ac power cord (plugging it in disconnects the batteries), earphone (you can even copy code without bothering the wife or family), and mike so you can make your own recordings of rare DX off the air when you get your license.

This cassette tape recorder is available for only \$23.95 (plus \$1.00 for

Publisher Tells All

Green Gets Life!

WASHINGTON (UPI) — In front of the Federal Court House Building this morning, Wayne Green, publisher of 73 Magazine in Peterborough, New Hampshire, admitted to this reporter that HE IS a Life Subscriber to 73. He further admitted that he feels that being a life subscriber to 73 would make you a special person --- so he is offering you this special deal. If you send in this Life Subscription Blank, along with a check for \$99, we will send you an order form from which you


may select, FREE, your choice of our excellent books totaling up to \$30.

The benefits of reading 73 are obvious . . . so why not treat yourself to a lifetime of interesting and informative reading about your favorite hobby. Short on cash? Just send \$25 as an initial payment, and make three consecutive payments of \$25 each.

The carefully hidden order form is on the reverse side of this column on the next page.

shipping and handling) to help you with our code course. Order it from 73 Magazine, Peterborough NH 03458.

2 METER PREAMP

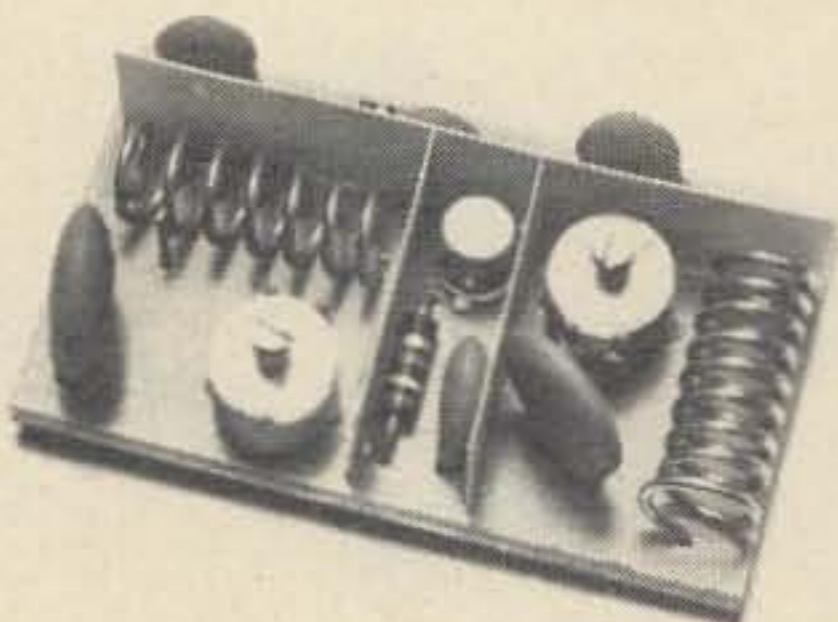

Data Engineering has come out with a nice 2 meter preamp using Mosfets. We installed one of the preamps on the 146.19 receiver at 73s WR1AAB Repeater and were very, very delighted with the results. Tests showed about 20 dB gain and a noise figure of less than 2.5 dB. To put it another way, before the preamp was installed our receiver was exhibiting .4 μ v for 20 dB quieting. With the preamp in the line the receiver is now good for .1 μ v (20 dB quieting). That does make a receiver super sensitive. Contact *Data Engineering, 554 Port Royal Rd., Springfield VA 22151.*

TOUCH-TONE DECODER

It looks as though the age of Repeater Sophistication Devices is here. Although Touch-Tone has been used on repeaters for some time, until recently decoding was done with the aid of either one of Ma Bell's decoders, such as the 247B, or a decoder built up by some enterprising individual at a rather healthy price.

Now however, one can find the perfect answer to Touch-Tone decoding. Data Engineering introduces their DE2171 Touch-Tone Decoder. Simply apply 5 volts and receiver audio to the decoder and you are all set to decode the standard 12 button Touch-Tone functions. The Data Engineering decoder has some very nice features. Probably the one thing about the decoder, in addition to its small size and layout, is the fact that the output from the decoder is via reed relays. If you have ever "zapped" a nice solid state device with a transistor logic output, you'll have no problems with this decoder. The reed relays, though small, can take just about all you can hand them. All in all, thanks to Data Engineering for a small Touch-Tone Decoder with all the features you could want at a price less than what you would pay for one of Ma Bell's units. If, of course, the Bell units were ever for sale. Contact *Data Engineering, 554 Port Royal Rd., Springfield VA 22151.*

MIT'S CALCULATOR

Very handy, one might pun.

Like many of the newer gadgets available, once you get one of these hand calculators the chances are that you will find yourself using it every day and wondering what you did before you had it. Like Kleenex. There was a time when there was no Kleenex. Some of the old timers may remember those olde days.

The recent MIT'S ads have been featuring their 150-series calculators. A rather thorough research of the available calculators — and there are a great many on the market these days — indicated that only a couple had the recently developed memory circuit. Users of any of the older calculators



will readily appreciate the importance of this for in any complex computation it has been necessary in the past to write down intermediate figures and then enter them later.

For instance, suppose you want to add 15% of \$200 and 15% of \$375? No longer do you have to do the two calculations separately and then add the results, with the new circuit you can do the 15% of \$200 and then put it up in the memory while you do the 15% of \$375 — and then add the memory number to the second calculation.

The number in the memory can be used for addition, subtraction, multiplication or division. Thus, if you have a series of discounts that you want to take on a series of prices, you can put the total discount percentage in the memory and use that to multiply the prices. Reading out the memory does not erase it, so you can make a long series of calculations quickly.

The 150 also has a clever system for setting the decimal and rounding off numbers. By touching the (.) (=) (2) keys you then end up with all calculations rounded off to two decimal places.

The X², 1/X, and √ keys are great for many radio and electronic problems. You can whip off a 1/62.79² in a flash. And you certainly don't need to cart around decimal equivalents of fractions anymore. The conversion from English to metric is fast with the calculator.

The % key is a small bonus for people who are not sure what a percent is and don't know that they'll get the same result by multiplying by the % number with a decimal point in front of it. 15% of \$375 can be done either by (1) (5) (%) (3) (7) (5) (=) or (.) (1) (5) (X) (3) (7) (5) (=). Well, you save punching one key.

YES

Make Me a Lifer Too!

I agree that I am a special person and as such I DEMAND that 73 Magazine make me a Life Subscriber too! Green may be the publisher, but that sure doesn't entitle him to be the only one to save money on a lifetime of enjoyment. I deserve the same break — and make sure that you don't forget to send me a personalized life subscriber certificate signed by Wayne, along with the list of 73's great books for me to choose from.

\$99 enclosed \$25 enclosed—bill me for the remainder

Name _____ Call _____

Address _____

City _____ State _____ ZIP _____

73 Magazine, Peterborough, NH 03458

There is a clever little battery saver circuit which turns off the readout numbers after about 15 seconds and indicates this with a little LED dash. Touching any key brings the figures back.

The MITS 150 is getting closer and closer to the Hewlett Packard unit, but without all those things that only a physicist might need. The 150 sells for about \$130, or for \$100 in kit form. The kit isn't all that difficult to manage, if you want to save \$30. And, at \$100, you will be hard put to find anything approaching this calculator anywhere.

Contact *MITS Inc, 6328 Linn Ave N.E., Albuquerque NM 87108.*

INSTANT CIRCUIT BOARDS



A set of drill mills are available which allow quality circuit boards to be fabricated from copper-clad material by simply drilling holes! Each mill, when powered by a hand drill or push-screwdriver, drills a small hole in the board and isolates a bit of the copper clad around the hole for soldering purposes. Three sizes are offered so the size of the isolated pad may be matched to the components you are using and the degree of miniaturization with which you are struggling. The largest is suitable for mounting standard sized components while the smallest can be used to fabricate mountings for in-line IC packages.

The drill-mills are extremely easy to use. After an outline of parts placement is drawn, the location of each proposed pad is marked through the layout onto a piece of copper-clad with a center punch, ice pick or other common workshop item. Then go to it with the drill-pads. If there are only a few holes to make, one needn't even get out the drill. The mills are extremely sharp and pads can be made in most board material at the rate of

two per minute with only a large knob mounted onto the shaft and a little wrist action. This method lends itself nicely to the "plan-as-you-build" school of construction and also to experimenting. . . mount a component — decide where the other lead will fit best — then drill the small isolated pad.

Unlike working with normal P.C. boards, isolated-pad circuitry can easily be modified. Since connections between components are not etched but wired, a little work with a soldering iron can change things around considerably without ruining the board. These little drill-mills are truly an experimenters tool!


The three sizes available will make isolated pads 0.20, 0.15 and 0.10 (inches) in diameter. Each is supplied with its own internally mounted no. 60 drill, which can be easily replaced. The price is \$6.95 each.

For more information contact *A. F. Stahler Co., P. O. Box 354, Cuertino CA 95014 402-262-4219.*

POWER AMPLIFIER BROCHURE

A 20-page brochure that describes basic concepts and techniques employed in the design of transistor audio power amplifiers and 38 silicon power transistors specially selected for use as input, driver, output and overload-protection devices in such amplifiers are available from RCA Solid State Division.

RCA Publication No. APA-550, "Audio Power Amplifiers," describes significant design features, basic circuit configurations, rating methods and stability requirements for transistor audio power amplifiers. The classes of amplifier operation and selection of the optimum class for a given output-power level are discussed, power-amplifier drive requirements are defined and the effects of operating conditions on circuit design are analyzed. The basic circuit con-

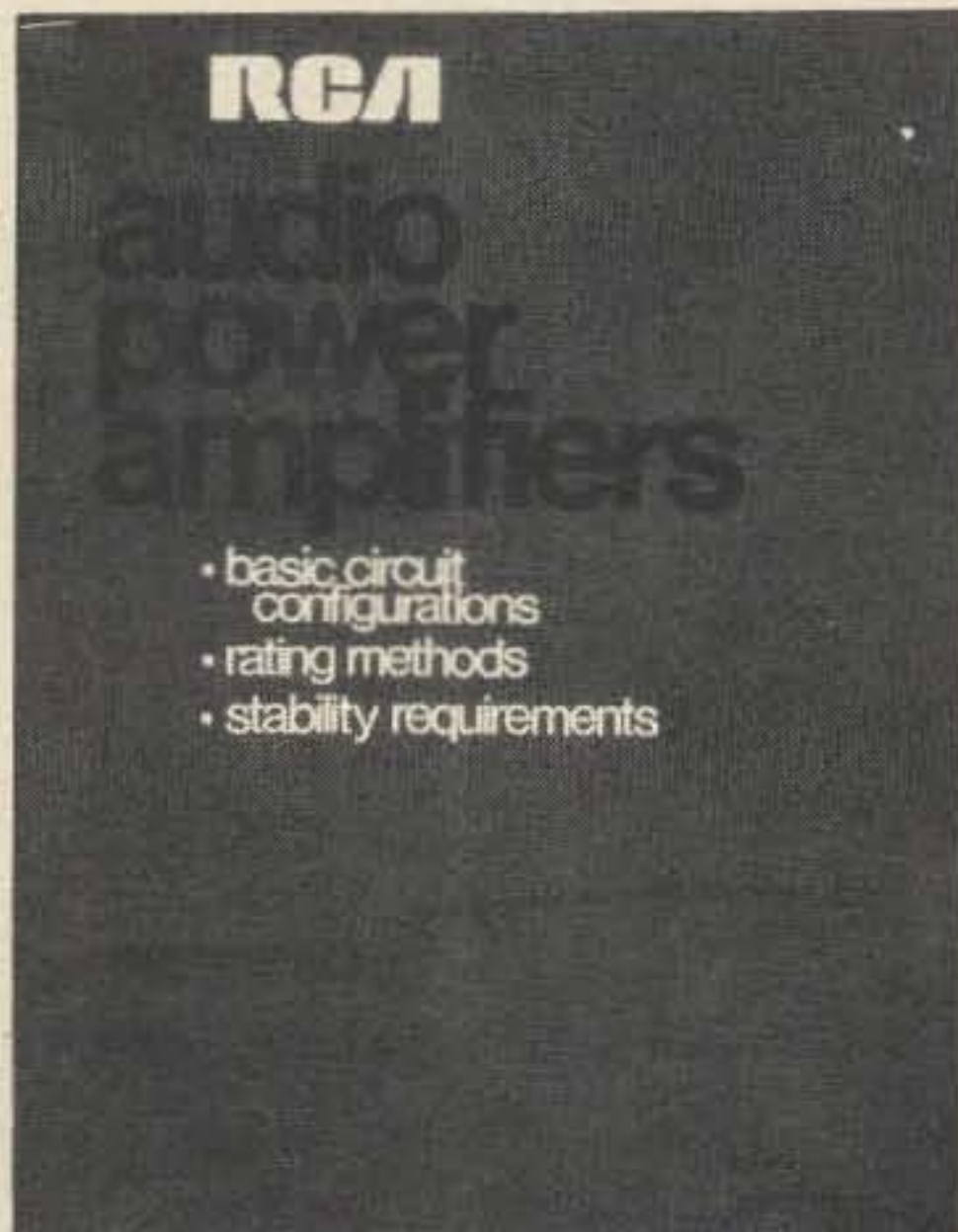


figurations used for audio-output stages are evaluated. The methods used for rating audio power amplifiers are compared and the power-output and dissipation capabilities of class B audio amplifiers are explained. The effects of changes in temperature, or large signal phase shifts and of excessive levels on amplifier stability and the techniques used to compensate for these effects are pointed out, and methods used to protect the output transistors against short-circuit load conditions are shown.

Anyone wishing to firm-up or expand their knowledge of audio amplifier design is invited to write for their copy of APA-550. Contact: *RCA Solid State Division, P. O. Box 3200, Somerville NJ 08876.*

2KW CB ANTENNA ANNOUNCED!

(hmmmmm)

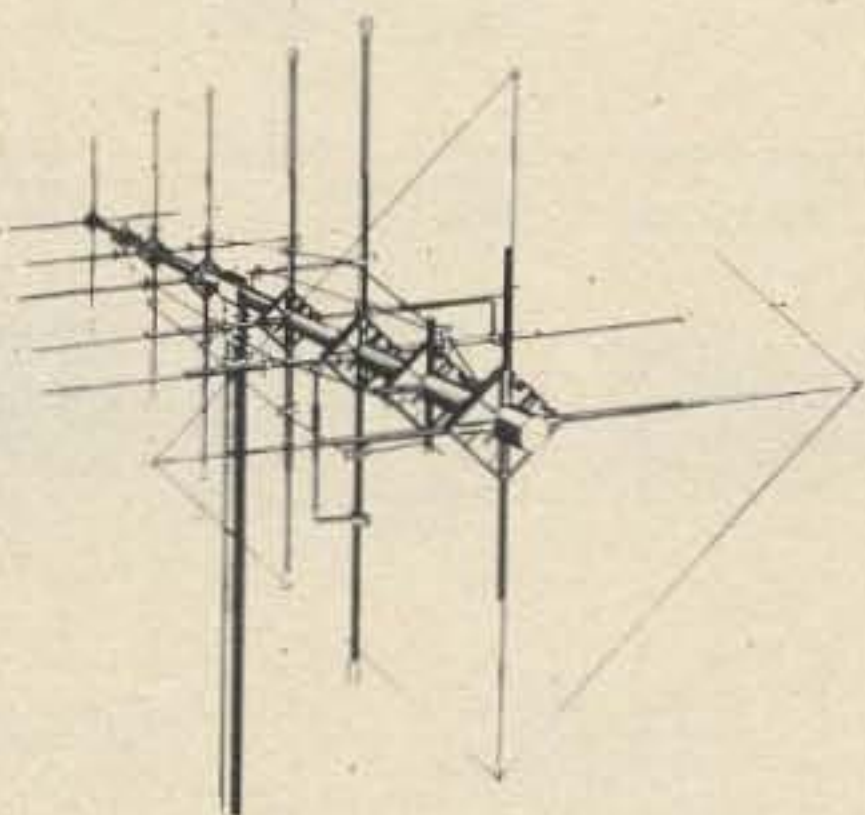

A new "super power" CB base antenna has been announced by Avanti R & D. Called the MOONRAKER 6, it is a 6-element, dual polarity beam combining five sets of crossed dipole type elements plus a quad type reflector for better rejection and gain. Tunable gamma matching on both the vertical and horizontal elements handles over 2,000 watts of power(!), gets the lowest possible SWR, is said to provide excellent lightning protection and to be virtually trouble-free.

In addition to the exceptionally high power potential, Moonraker 6 specifications include 17 db gain over isotropic, 44 db rejection, 24 db side rejection, and 1.2:1 VSWR. Contact: *Avanti Research and Development, 33 West Fullerton Avenue, Addison IL 60101.*

ALLIED ENGINEERING CATALOG

Allied Electronics (Division of Tandy Corporation) has published their new 1974 catalog #740. Previous catalogs have served as the electronics industry's "answer book," and the new catalog is even better. The prime feature of the Engineering Manual & Purchasing Guide catalog is the includ-

(Continued on page 111)



YAESU

YOUR ASSURANCE OF PERFORMANCE & QUALITY

SP101-P \$59.00
SP101 19.00

FV101 \$99.00
160M THROUGH 10M

FT101 \$649.00
TRANSCVR 260W PEP

FL2100 \$339.00
80M THROUGH 10M
1200W PEP



The SP101-P Landliner provides phone patch operation as well as speaker. Front panel: Patch switch, meter, TX and RX gain controls. Rear apron: Receiver 4 ohm output, receiver 600 ohm output, monitor null switch, balance control, line jack, transmitter high Z jack.

The FV-101 permits split frequency operation and control from either the FT-101 or FTDX401.

The FT-101 exciter covers 160, 80, 40, 20, 15, (CB), and 10 meters and comes complete with microphone cable and plug, fused DC power cable and plug. AC cable with plugs and all necessary plugs are furnished. AC and DC supplies are internal.

The FL-2100 linear amplifier needs only 3 wire cable and coax cable. Connectors are furnished.

FTDX401 \$599.00
TRANSCVR 560W PEP

FV401 \$99.00
EXTERNAL VFO
80M THROUGH 10M

FL2000B \$399.00
LINEAR AMP
1200W PEP

FRDX400 \$299.00
RECEIVER
160M THROUGH 10M



FTdx401 features high power, super sensitivity and sharp selectivity. The FTdx401 includes: AC power supply, noise blanker, 100 KC and 25 KC calibrators. VOX break-in, phone patch terminal, cooling fan. Covers 3.5 through 10 MHz plus WWV. 560 watts PEP. All that is required to get on the air is a microphone and speaker.

The FV-401 permits split frequency operation for the DX chaser or net operator. Covers 80 through 10 meters.

FL 2000 B 1200 watts PEP, 1000 watts CW, 600 watts AM. Drive power required 100 watts. Has two cooling fans and uses two 572 B tubes.

FRdx400 includes 2 mechanical filters plus "T" notch rejection tuning, and clarifier for easy zero set for SSB. Crystal control 1st mixer and tunable 1st I.F. provides stable operation and high spurious rejection. 100 KC and 25 KC calibrators. VFO can be used in transceive operation in conjunction with F series transmitter.

FLdx400 operates SSB, (USB LSB selectable), AM, CW and FSK. Circuitry can be built in for RTTY operation. 240 watts PEP. VOX, PTT, and break-in CW.


FL-2000B grounded grid linear uses a pair of 572 B tubes. Plate meter VSWR monitor, 2 fans, built-in power supply, 80 through 10 meters, 1200 watts PEP with distortion product in excess of 30 DB down.

FLDX400 \$399.00
EXCITER
80M THROUGH 10M

FL2000B \$399.00
LINEAR AMP
1200W PEP

SP401-P \$59.00
SP401 19.00
SPEAKER/PATCH

FP-2
AC POWER SUPPLY

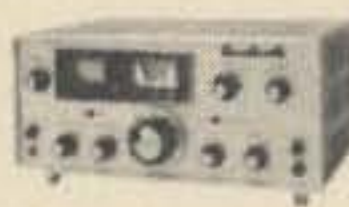

FT2FB \$239.00
144-148MHz
10W HIGH 1W LOW

FT2-AUTO \$379.00
144-148MHz



FP-2 AC power supply specifications: Output - 13.5 volts, 2 amps. AC input - 100/117/220/234 volts. Speaker - 5" x 3-1/5". Portable or home base operation can be achieved with the addition of the optional FP-2 power pack. This AC power pack provides regulated DC power for the transceiver and charging voltage for optional leak proof rechargeable colloidal type batteries. In addition, a high fidelity elliptical style speaker is built into the pack.

The FT-2FB opens the door to noise free broadcast quality 2 meter operation, and thanks to the repeater stations throughout the country, the 2 meter band is no longer restricted to line of sight. General coverage 144 to 148 MHz, 12 channels (3 supplied). Push to talk. Receiver .3 amps, transmit 1.7 amps, power source 13.5 volts + 10%. Dimensions 6-3/8" w. x 2-1/2" h. x 10" d., weight 4 lbs. Comes with dynamic microphone, connector plug, DC cord, fuse and mobile mount.

The FT-2 auto is a compact base or mobile VHF/FM transceiver, covering 146 to 148 MHz, featuring electronic scanning up to 8 stations between 146-148 MHz with priority channel sampling while locked on another channel. Adjustable tone burst push-button lock on for repeater actuation. The FT-2 auto is self-contained. Two power cables are supplied with the transceiver, including all mounting hardware, cables, connectors, and accessories required for both mobile and base installation, as well as dynamic push to talk microphone. Operates from various AC voltages or 13.5 DC. Dimensions 8-3/4" w. x 4-1/4" h. x 11-5/8" d. Weight 9 lbs.

YC355-D \$289.00
DIGITAL COUNTER-BUILT IN PRESCALER



Complete with
A.C. Power Cord 6 Ft.
D.C. Power Cord 6 Ft.
Signal Test Lead with
BNC Connector 3 Ft.

SPECIFICATIONS

	YC-355D		YC-355D		YC-355D
Frequency range	5Hz to 35MHz (50Hz to 200MHz)	MAX Input Voltage	60V p-p, less than 10 sec (5V p-p)	Weight	220(W)X80(H)X270(D) (8 3/4 W X 3 3/4 H 10 1/2 inches)
Accuracy	± time base stability + 1 count	Input Impedance	HIGH: 1 M ohm, Low: 56 ohms	Tube	Display tube 5
Display	5 Digit	Input Capacity	Less than 20pF	Semi-conductors	Silicon diode 12 Silicon transistor 9 FET 1 IC 26
Sampling time	1 milli-sec or 1 sec	Time base Frequency	1 MHz Crystal controlled		
Display time	0.1 sec 2 sec	Stability	0.0005% at 25° C 0.0025% at 0° - 40° C		
Frequency Unit	KHz, MHz	Power Requirements	100/110/117/200/220/234V 50/60Hz 18V A		
Display	Display tube		12~14.5V 1A		
Input Voltage	20mV-20V p-p (0.15V~5V p-p)				

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

FACTORY SERVICE IS AVAILABLE WHERE WARRANTY HAS EXPIRED. MK-160 (160M) KIT \$16.00 WITH XTAL PLUS LABOR. MODERNIZATION KIT MIR-1 FOR OLDER MODEL FT101 \$70.00 FACTORY INSTALLATION ONLY.

HAM RADIO CENTER
8342 OLIVE BLVD., ST. LOUIS MO 63132

ADIRONDACK RADIO SUPPLY
185-191 W. MAIN ST., AMSTERDAM NY 12020

HENRY RADIO STORES
Los Angeles, Anaheim, CAL., Butler, Mo.
HAM RADIO OUTLET
Burlingame, Cal.
RACOM ELECTRONICS
Renton, Wash.

FRECK RADIO & SUPPLY/704-254-9551
Asheville, N.C.
HARRISON RADIO/516-293-7990
Farmingdale, L.I. Valley Stream, L.I. New York

HAMTRONICS
4033 BROWNSVILLE RD., TREVOSE PA 19047

AMATEUR ELECTRONIC SUPPLY
621 COMMONWEALTH AVE., FL 32803

WEBSTER RADIO
2602 E. ASHLAN., FRESNO CA 93726

GRAHAM ELECTRONICS
133 S. PENNSYLVANIA, INDIANAPOLIS ID 46204

WILSON ELECTRONICS
Pittman, Nev.
ED JUGE ELECTRONICS
Fort Worth, Tex.
AMATEUR ELECTRONICS SUPPLY
Milwaukee, Wis.; Cleveland, Ohio



YAESU MUSEN USA INC.

7625 E. ROSECRANS AVE. UNIT 29 PARAMOUNT, CAL. 90723

TWX 910-346-7624
TEL 213-633-4007

GETTING STARTED ON 450MHz

Bill Hoisington K1CLL
Farover Farm
Peterborough NH 03458

The Basics -

- Crystal Controlled Signal Generator
- Modulator
- Infinite Attenuator
- Wavemeter

This article describes a good crystal oscillator signal source for 450 MHz FM work. It is one of a series on how to get going on 450 MHz FM. You have to work a little harder on this frequency, and this series will be of help. You must have – or make up – certain pieces of test equipment to help you get into the UHF region. But the real amateur fun you will get out of it, if you have even a drop of experimenter's blood in you, will be well worth your while.

General

This 450 MHz crystal controlled source is about as simplified and straightforward as you can get on 450 today. All three stages combine the results of many years of past work on my part, beginning in 1946 with an article entitled "Getting Started on 420." History does seem to repeat itself.

There are many pitfalls along the way to a really good signal source, surefire and reli-

able, on 450 MHz, and we will guide you through them, with luck, and you can go on from there. If you make this rig exactly as shown, it will provide you with a good signal source from 420 to 450 MHz, by changing crystals and retuning very slightly. You can use it first of all as a signal generator and by sliding it into an aluminum tube (as shown in Fig. 5) you can add an infinite attenuator to it. This will allow you to make repeatable low noise, high sensitivity tests on any receiver you build for 450 MHz. You can also use it as a guide for an L.O., or as the beginning of a one watt or more FM rig. I used a 48 MHz crystal because, being an old 2 meter DX'er, I have a lot of rocks lying around near the band edge. The 50 MHz one comes from my old 6 meter days.

Figure 1 shows the entire signal source. Note the simplicity throughout: all tuning

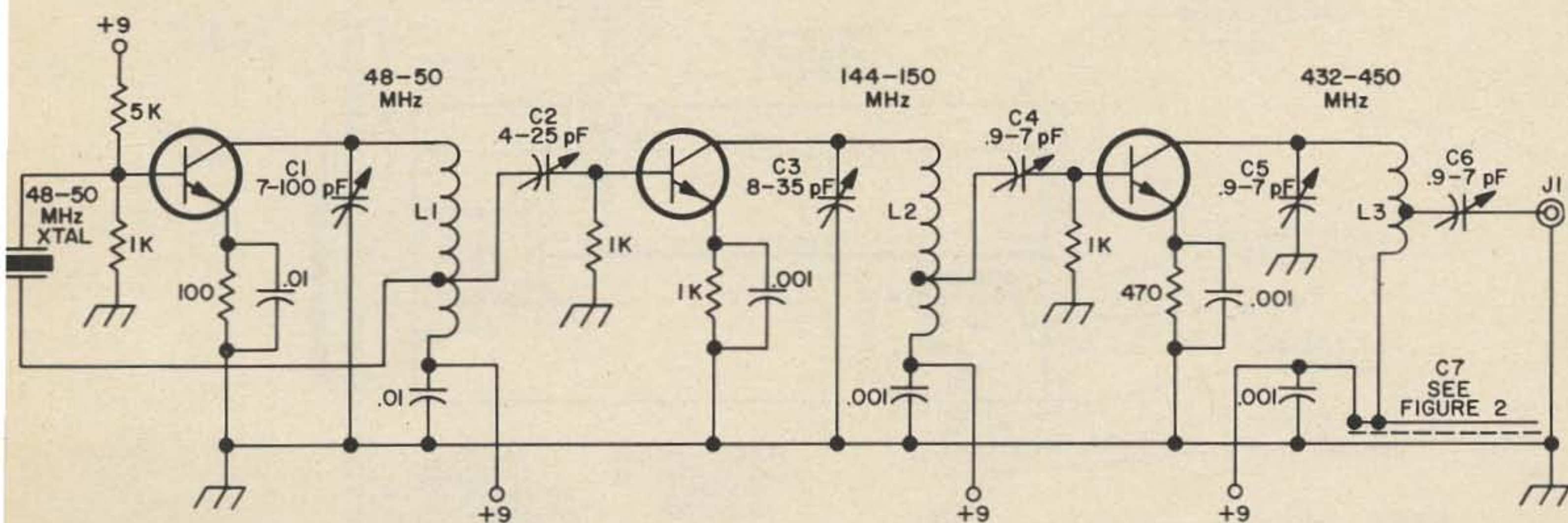


Fig. 1. 450 MHz signal source. All transistors are HEP 75. L1, 20 turns No. 24, 8mm long, 5mm diameter form. Tap at 8 turns from cold end; L2, 5 turns No. 20 tinned copper, 19mm long, air-wound, 8mm O.D.; L3, 3 turns No. 20, 11mm long, 5mm diameter. Tap in center.

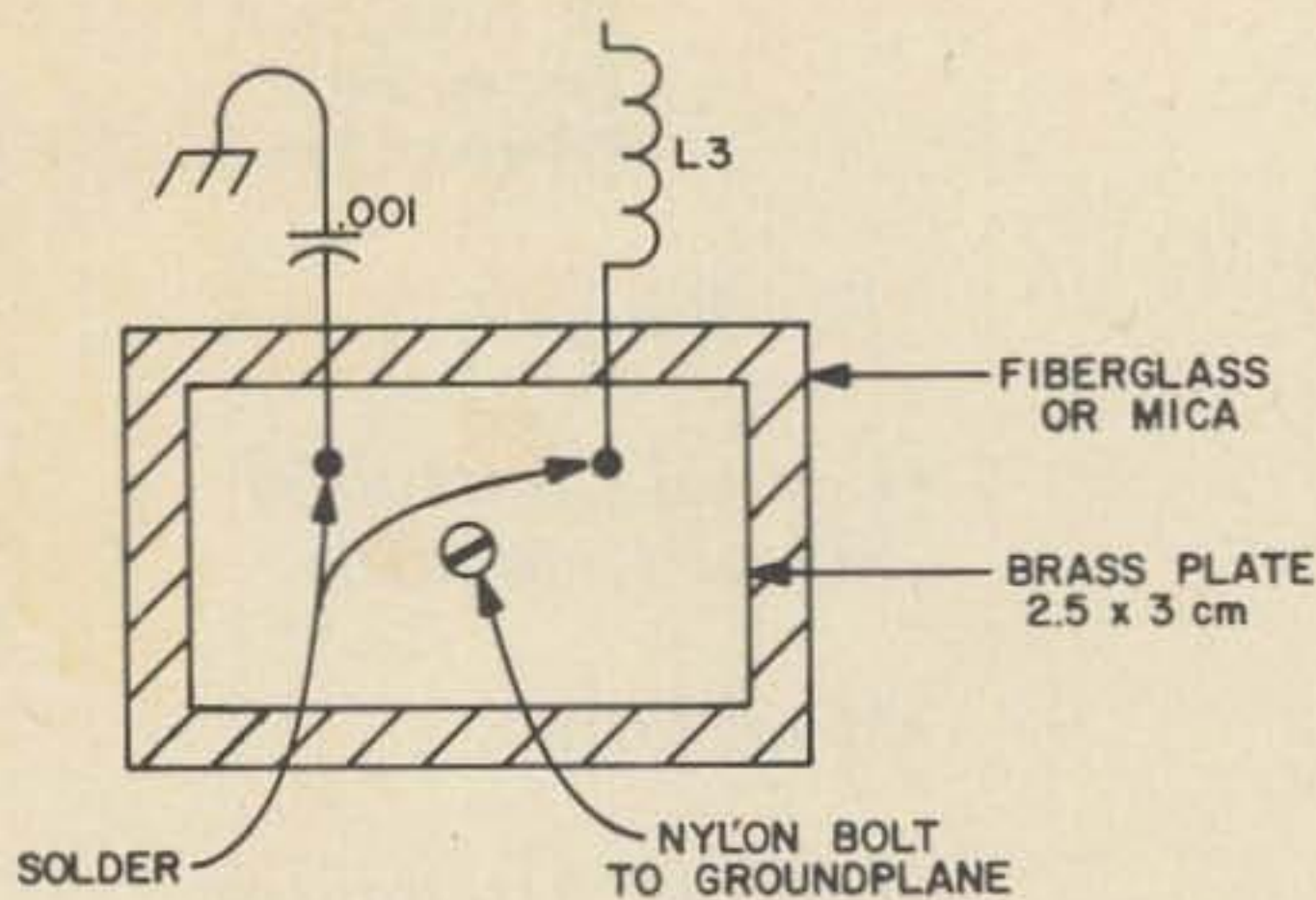


Fig. 2. Special UHF capacitor C7.

capacitors are mica compression Arco's, only three tapped coils, all base input capacitors are variable, no external bias needed on the two triplers, three similar transistors, HEP 75's, and only one special item, which requires a nylon bolt and nut.

Crystal Oscillator

This puts out enough power to drive the tripler base without external dc bias. Rf voltage at 48 MHz is developed in L1, tuned by C1. Remember, it is much simpler to describe oscillators when they are already running, and this one always will be if you make it as shown. The rf voltage is fed back in phase to the crystal. This of course is the wrong phase for the base, but the crystal has — at any given instant — plus on one side and minus on the other, so the base receives

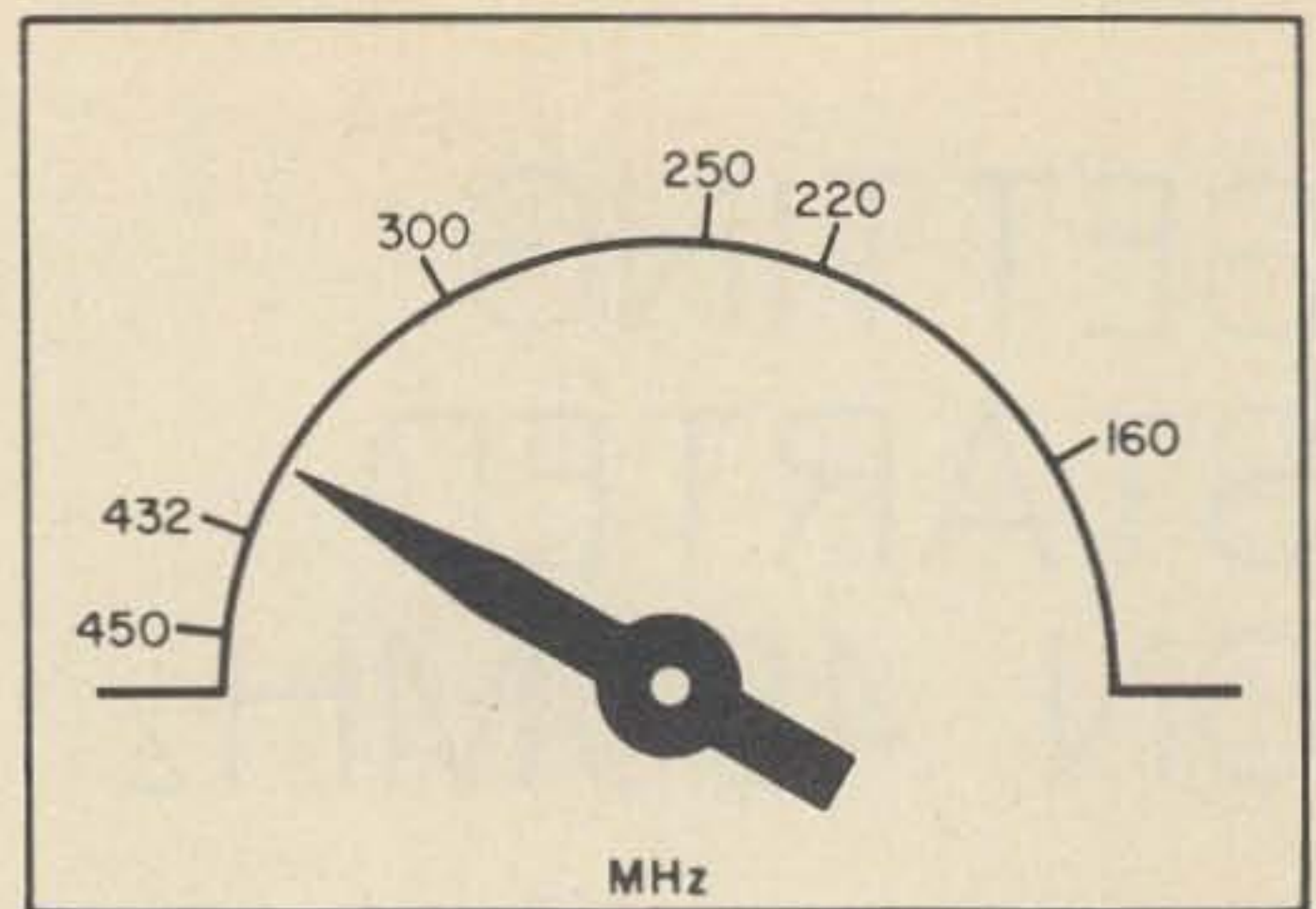


Fig. 3b. Front panel calibration for the wavemeter.

the rf voltage correctly out of phase, resulting in good, powerful, stable oscillation. Both the crystal and the base input of Q1 are of low impedance so the match is continued with a tap down on L1 for the feedback connection. I usually tune up the oscillator with a two or three turn link out of L1 into a tuned diode receiver on 48 MHz, which in this case showed some 20 to 30 mW output.

The First Tripler

A trimmer, C2, couples 48 MHz energy over to the base of Q2 in sufficient quantity so that no external dc bias is needed. L2 and C3 are tuned to 144 MHz. Be very sure you are on 144 and *not* on 96 or 192! Again, use a tuned diode receiver and an absorption wavemeter or a dipper in the diode mode.

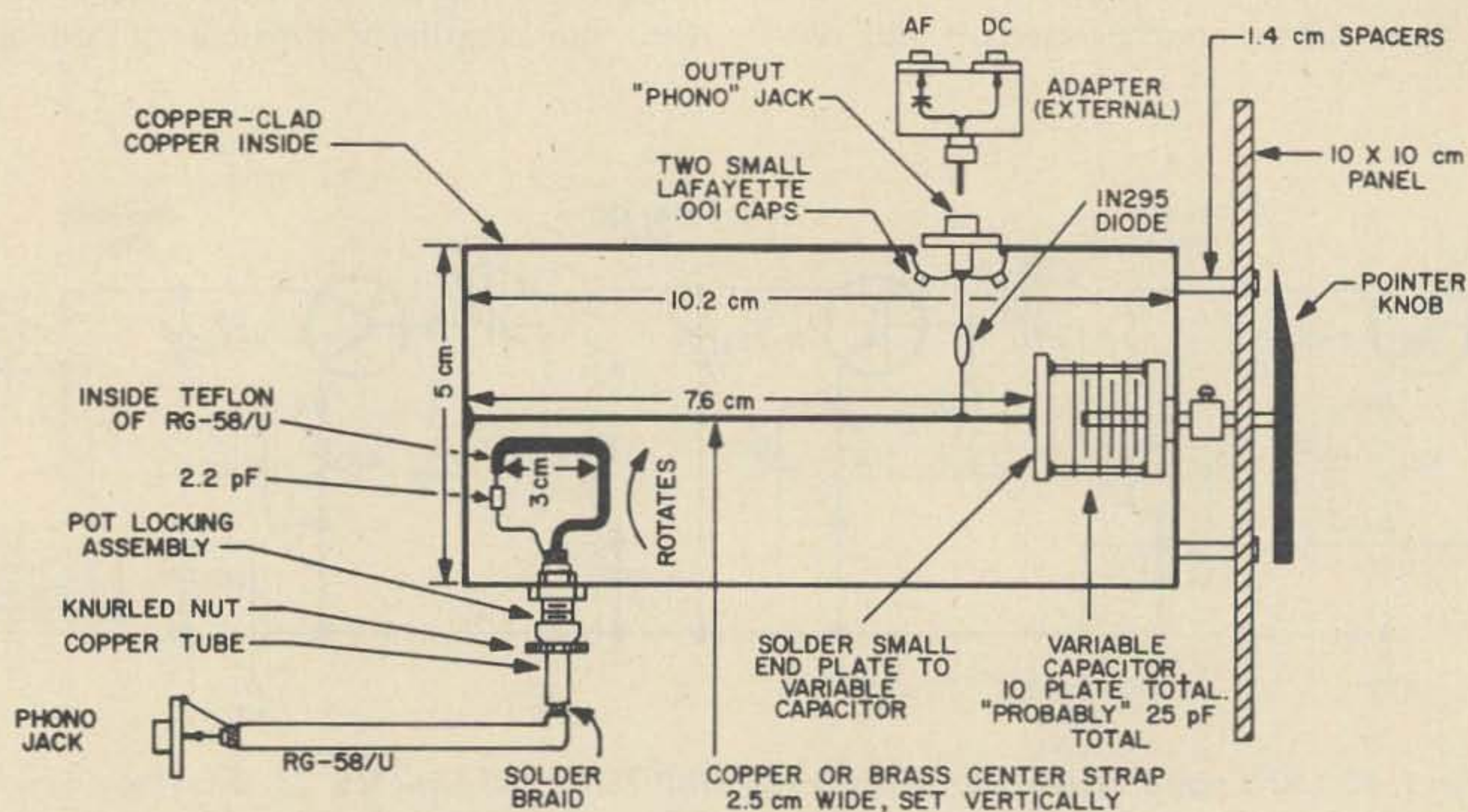


Fig. 3a. 150-470 MHz wavemeter.

Play around with C3 and L2, making sure it is on 144 MHz and that it does tune smoothly without discontinuous jumps and bumps, and that it does *not* affect the oscillator.

The Second Tripler, Q3

Almost the same story as the first. *Just pay a little more attention to short leads and to the special capacitor you need for the collector return of Q3, C7. In order to have the +12 return lead of L3 properly bypassed to the baseboard ground so that 450 MHz energy circulates correctly around the C5-L3 circuit, I generally use a flat brass plate capacitor, insulated from the baseboard as shown in Fig. 2. This is a very useful type of capacitor to know about, especially if you are going up later to 1296 and higher. I also bypass the bypass with one or more tiny, ultra-short lead .001 capacitors from Lafayette. These even work (sometimes) at 1296. They keep lower frequencies from sneaking through C7. Don't forget there are plenty of these low frequencies lurking in the output of Q2, just waiting for a chance to show. Don't say I didn't warn you! Now you must have a good diode receiver and/or a good absorption wavemeter for 420-450 MHz. A friend of mine, 10 to 15 years in VHF, built a 432 MHz receiver and could not hear anything on the band for a week. No wonder - his L.O. was off one harmonic away from where it should have been! Figure 3 shows the exact dimensions of the


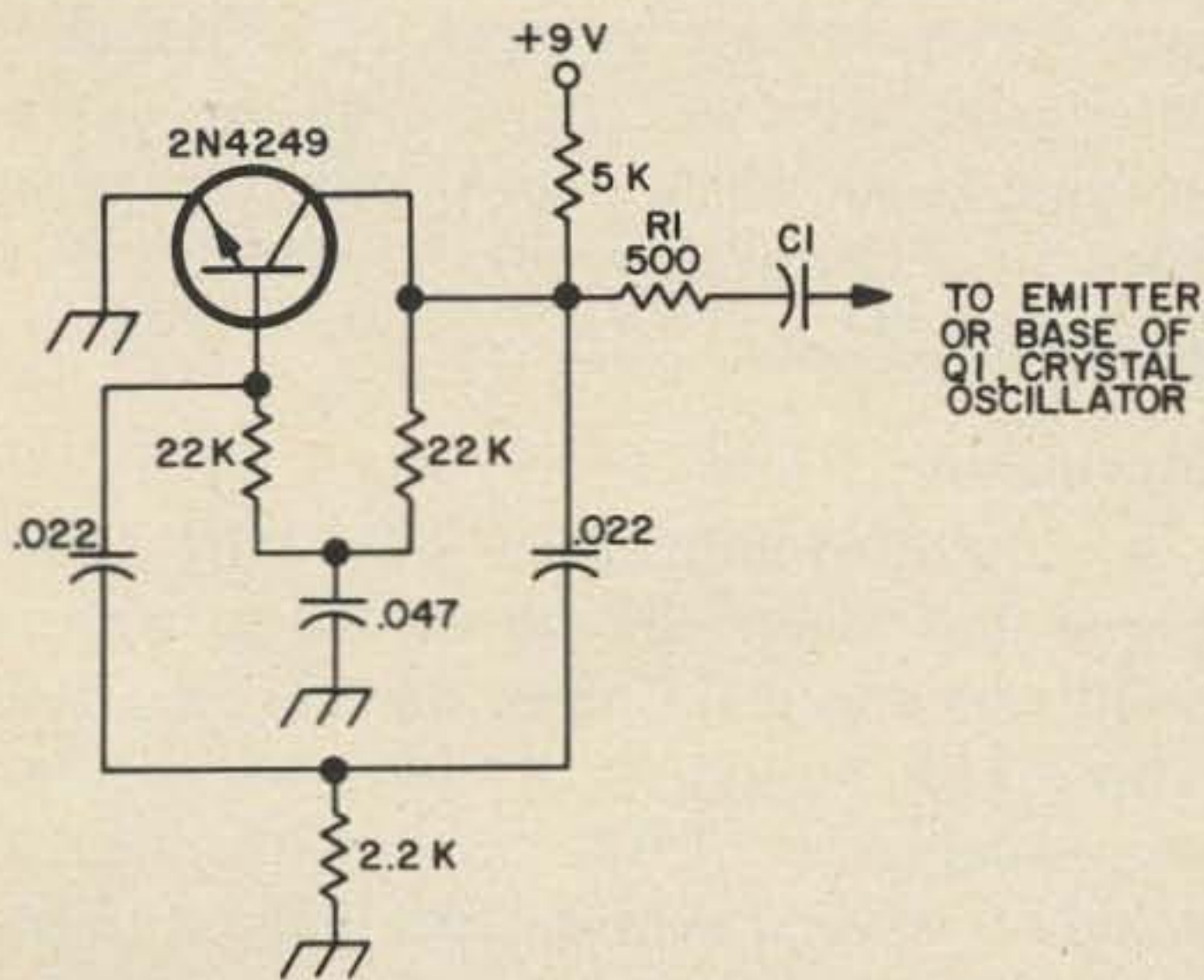


Fig. 4. AF oscillator modulator. The frequency is about 400 Hz, as shown. Adjust R1 and C1 for modulation needed. Any good AF transistor may be used.

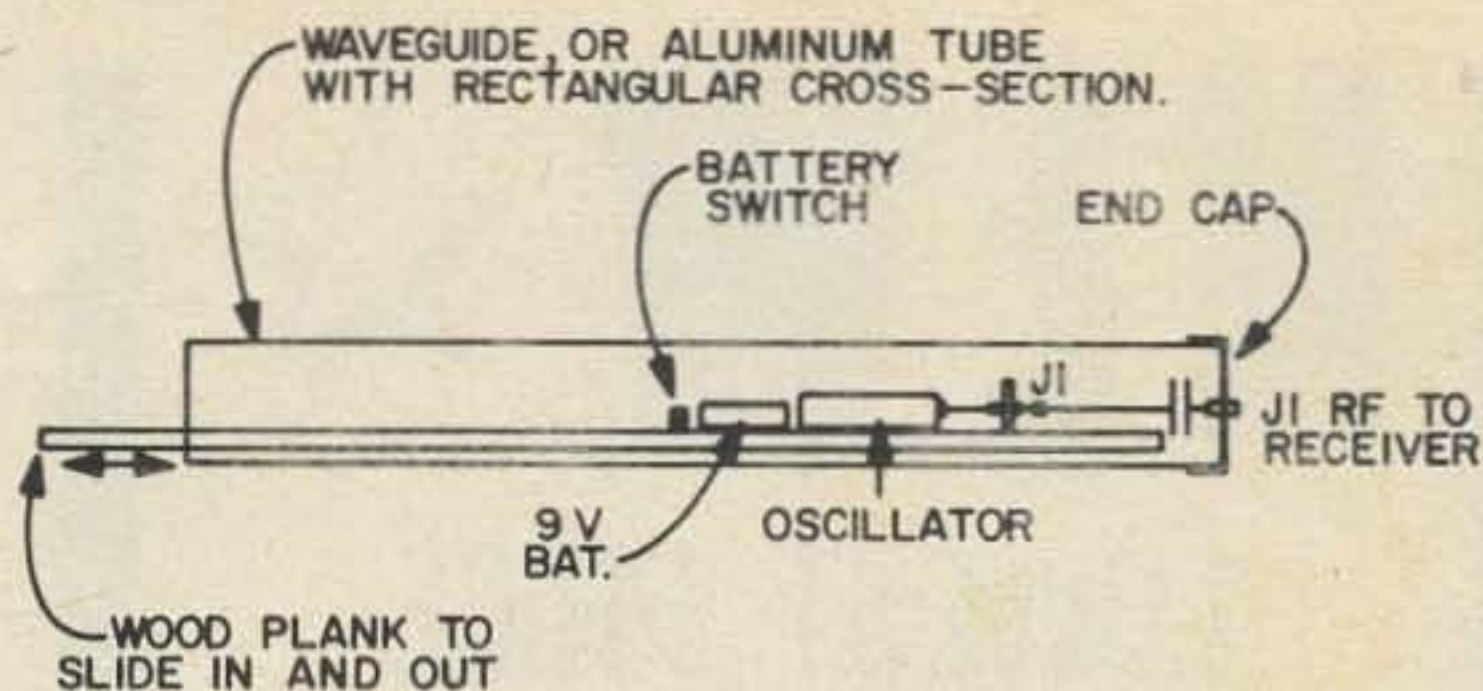

NOTE: NO WIRES TO THE OUTSIDE

Fig. 5. The infinite attenuator.

diode receiver I use. I have used this one for years on 220 as well as on 420 to 450 and it is very reliable. With this handy piece of test equipment plugged into J1, the 450 MHz output jack, you should begin to get some output. Be sure and get 144 MHz energy into the base of Q3 via trimmer coupling capacitor C4. Then, by playing around with C5, L3, and C4 you should be able to build this up to a good 1/2V dc output from the diode receiver. With a 50 μ A meter plugged into the output of this receiver, you can read nicely even small amounts of rf as it starts to arrive during the tuning. I usually put a 10K

PHONE ORDERS NOW ACCEPTED FOR 1 DAY C.O.D. SHIPMENT ON ALL OUR PRE-AMPS AND SOME OF OUR CONVERTERS AND FREQUENCY SYNTHESIZERS

If you need a low noise pre-amp in a hurry for communications or instrumentation, we can fill your order custom tuned to any frequency from 5 MHz. to 475 MHz. within 24 hours by air mail or special delivery. All you pay is our regular low price plus C.O.D. shipping charges. This rush service is also available on some of our stock converters and frequency synthesizers. To place an order or for information on any of our products call us between 9 A.M. and 4 P.M., Monday thru Thursday except holidays (no collect calls please). If line is busy keep trying.


PHONE: 212-468-2720

VANGUARD LABS

196-23 JAMAICA AVE.
HOLLIS, N.Y. 11423

NEW

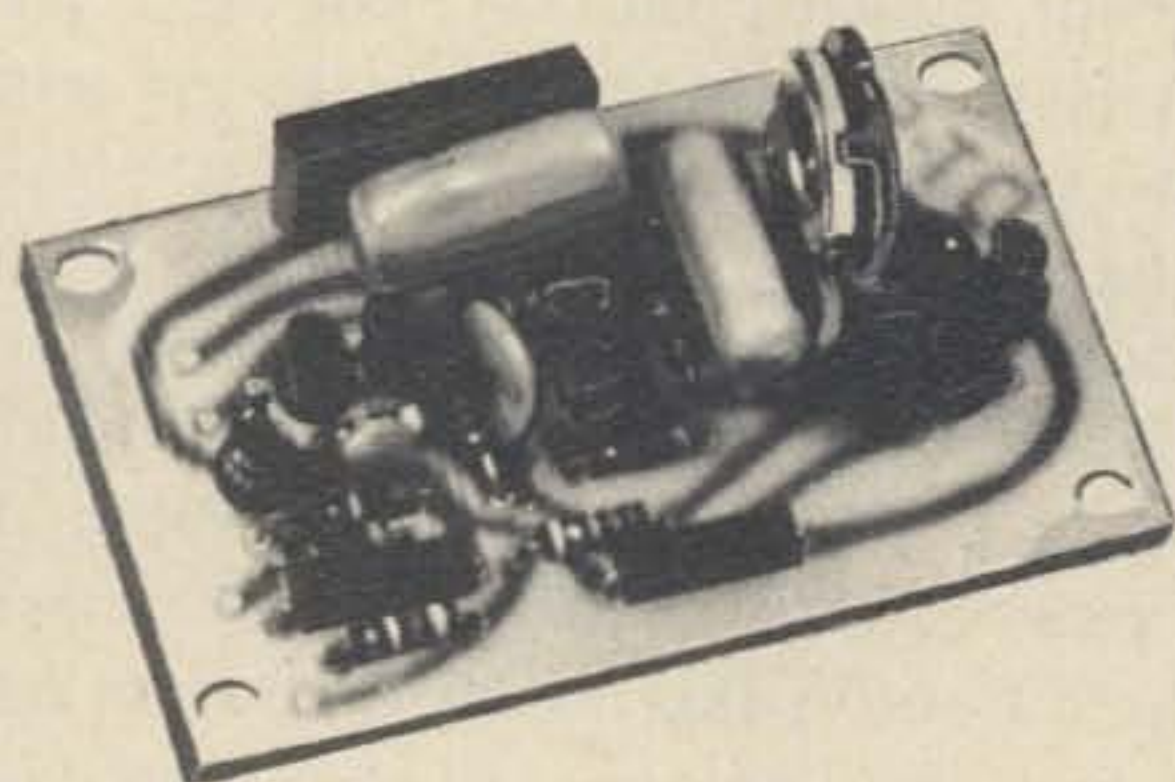LOWEST PRICE HIGHEST QUALITY SUB-AUDIBLE TONE



COMPLETE—No reeds required!

There's nothing else to buy, Alpha encoders and encoder/decoders are complete and ready to install. A free 32 page instruction manual is provided with each order, which includes helpful ideas on repeater applications and various tone uses.

Plug-in frequency modules are included. Specify frequency from 20 Hz. to 3,000 Hz.

QT-5 Encoder only

ASSEMBLED **29.95**

IN KIT FORM **22.95**

QT-10 Encoder-Decoder

ASSEMBLED **45.00**

PT-100 Burst Tone

ASSEMBLED **26.95**

IN KIT FORM **23.95**

ALPHA ELECTRONIC SERVICES

8431 Monroe Ave., Stanton, Calif. 90680
Phone 714-821-4400

pot in series with it, with calibration marks at .1, .5, 1.. and 5V for handy use. Build up carefully the 450 energy, watching the 48 and 144 tuned circuits as you go. It's very easy for them to jump around if you use coupling that is too tight, via C2 and C4. I often use two or more tuned diode jobs to keep an eye on those lower frequencies. You can't be too careful. Always use only enough coupling capacitance to get maximum energy into the base concerned and no more. Even a little less than maximum for the smoothest and safest all-round best tuning. Do not leave this source in a marginal operation, jumpy, condition. Remember, you are the one who is going to depend on it to tune up your 450 gear. You could get more output by substituting a 3866 for the HEP 56 as Q3, the last tripler, but as this is intended only as a signal source, you don't really need it.

Modulation

A little tone, mixed FM and AM, never hurts in a signal generator, so a convenient little af oscillator plank is shown in Fig. 4. This can be connected between ground and the emitter of Q1, the crystal oscillator. Attach it to the base for more modulation through a resistor.

Infinite Attenuator

This one has been shown several times in 73. Just mount the whole generator including the battery and switch on a long plank that will slide easily into a piece of aluminum waveguide or a piece of aluminum, rectangular cross-section, rain-gutter downspouting as shown in Fig. 5, and you can go down to a tenth or even a hundredth of a microvolt.

Conclusion

A simplified homebrew 450 MHz signal source has been described, along with a modulator and mention of an infinite attenuator. This could start you off on an interesting series of 450 projects planned to include receivers, transmitters and antennas. Don't forget, there are transistors available today with noise figures of 1½ dB at 500 MHz.

...K1CLL

EXPERIMENTERS
STUDENTS
HOBBYISTS
TECHNICIANS
INVENTORS
ENGINEERS
RADIO/TV SERVICE DEALERS
TEACHERS
ELECTRONIC REPAIRMEN

WIN!

\$2,500.00

SCHOLARSHIPS or any of 8 other
Scholarship prizes totaling \$9000
(All fully transferrable)



"Design-In" Contest

Original
Electronic
Project

Open to Men—Women—Boys—Girls—Any Age
Two contest categories: Non-Professional and
Professional — with equal prizes for each

**CONTEST ENTRY BLANKS AVAILABLE ONLY
AT MOTOROLA HEP SUPPLIERS** Pick up your
"Design-In" Contest Entry Blank Today!

Contest closes December 31, 1973

GETTING STARTED ON AMATEUR TELEVISION

*With a handful of transistors
and an old TV set!*


There are many ways to get on the air in ham TV. This article shows simple and graduated methods of transmitting TV. The first thing to have is a monitor. Then you can transmit your vertical and horizontal sync. Now you are on amateur TV. Next you can fill the picture with bars, dots, crosshatch, etc. If your resources are not too limited, you can build the simple flying spot scanner or a vidicon camera. This article shows the simplest ways to do these things with transistors; it is meant to be an idea article — to give you ideas on how to build up your station.

The Monitor "Jeep"

Of course you want to see your signal before you transmit it. The best way is to get an old TV set (no ac-dc models!) and disconnect the rf and video i-f, and connect your video output to the grid of the video amplifier. You can use the family set if you just insert a shorting phone jack between the detector diode and the grid. Then you can just plug in whenever you want. All you do is pull it out, and it's a TV set again. The signal level at this grid is compatible with the video output amplifier, generally 2V peak-to-peak, with negative going sync.

Sync Generators

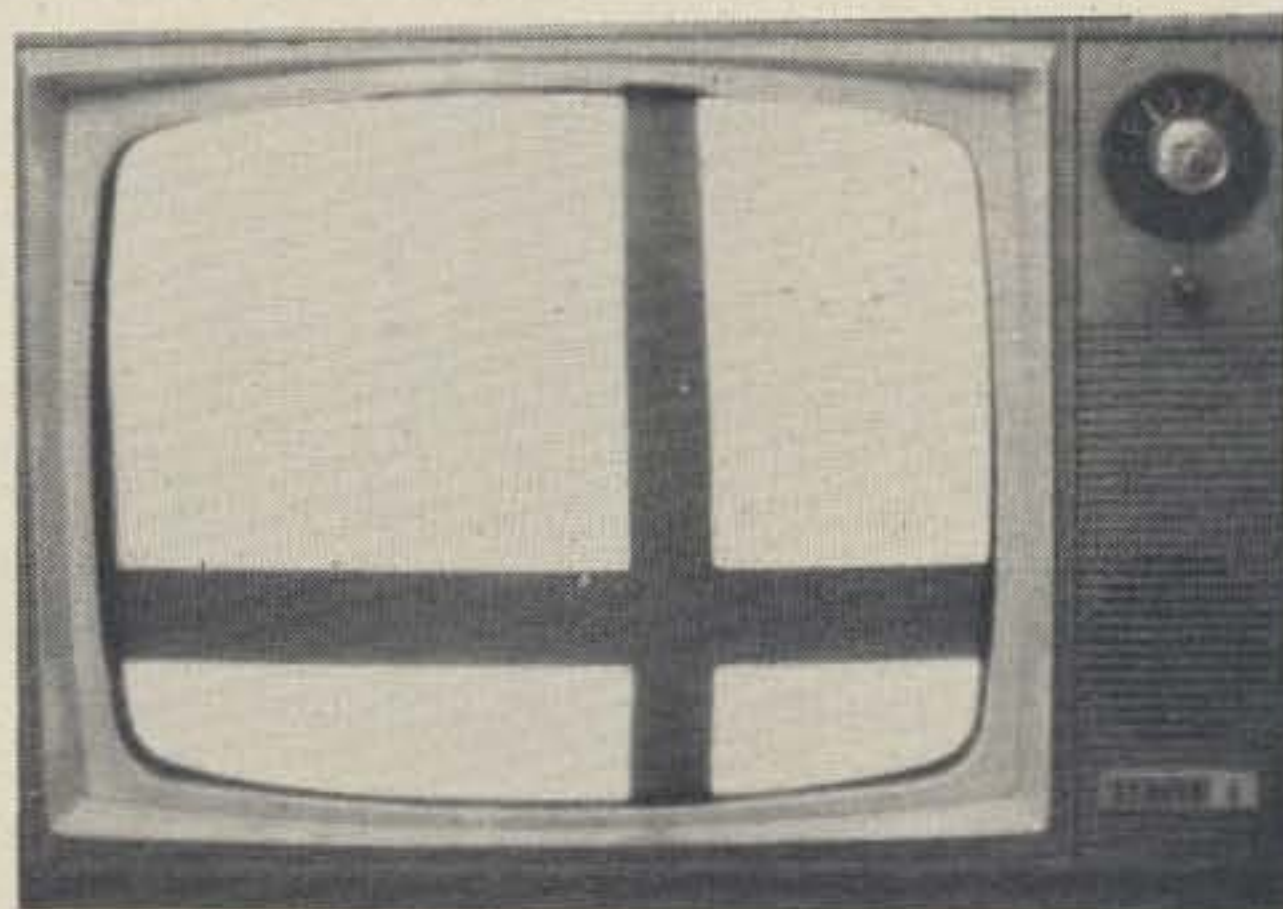Before anything can be done in video design, vertical and horizontal sync as well as composite must be available. The stability of the system is dependent on the quality of the sync generators. In simple, inexpensive designs many tradeoffs can be considered: random or interlaced scan, crystal control or free running, serrated vertical sync, color



burst, blanking, etc. Many of these are elite, but more than necessary to the beginner. The use of complex frequency dividers and critical tuned circuits is eliminated by random interlace and multivibrators. Furthermore, the circuits lend themselves to integrated circuit techniques.

Vertical Sync

A 60 cps sine wave is derived from the power supply and squared off in Q1. The negative going edge of the square wave turns off Q2 for a time determined by $T = .7RC = 7 \gamma (100,000 \times .02 \times 10^{-6}) = 1.4$ milliseconds for a standard 10:1 ratio of sync to scan time. The emitter followers give a low output impedance terminal capable of driving coax lines with 12V logic levels. The 2N3704 and 2N3702 are used for high gain at low cost.

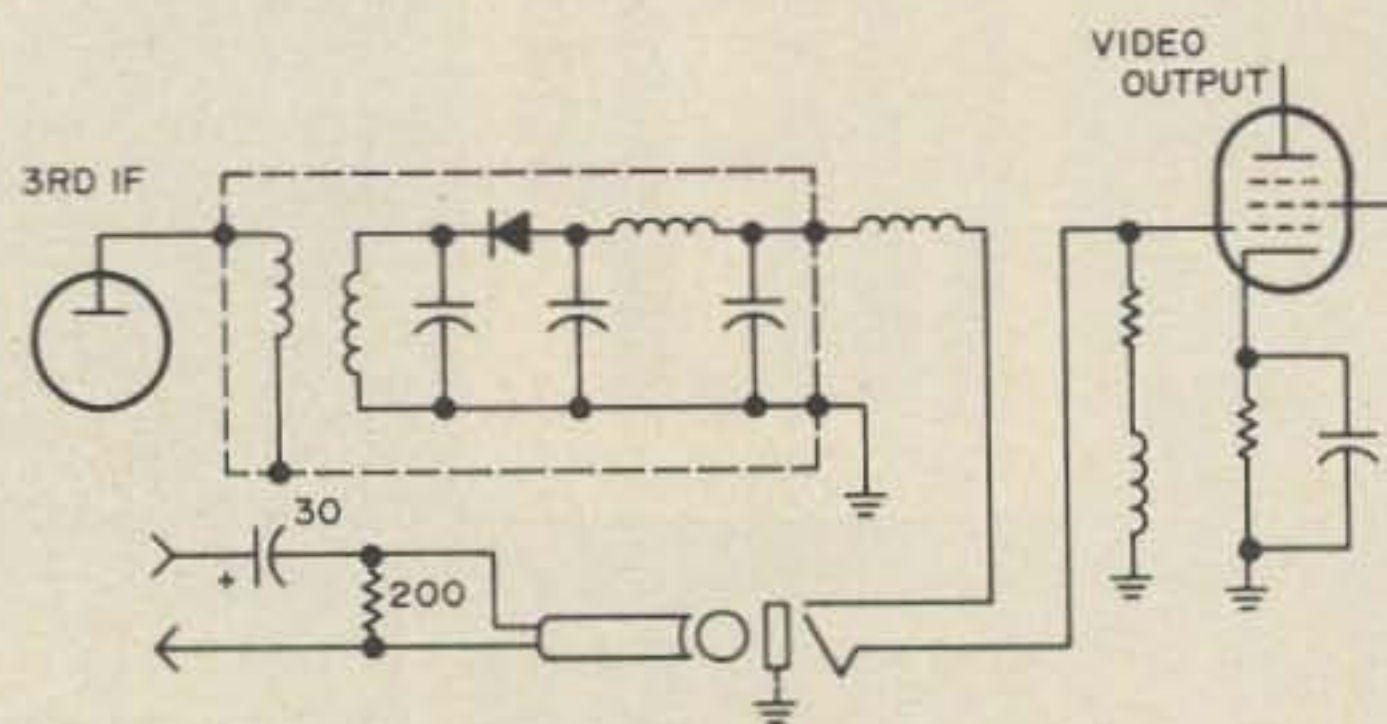


Fig. 1. An old television set can be used as a monitor by tapping into the grid of the video amplifier.

Horizontal Sync

Digital techniques here can eliminate tuned circuits and unstable blocking oscillators. A simple multivibrator is set to produce


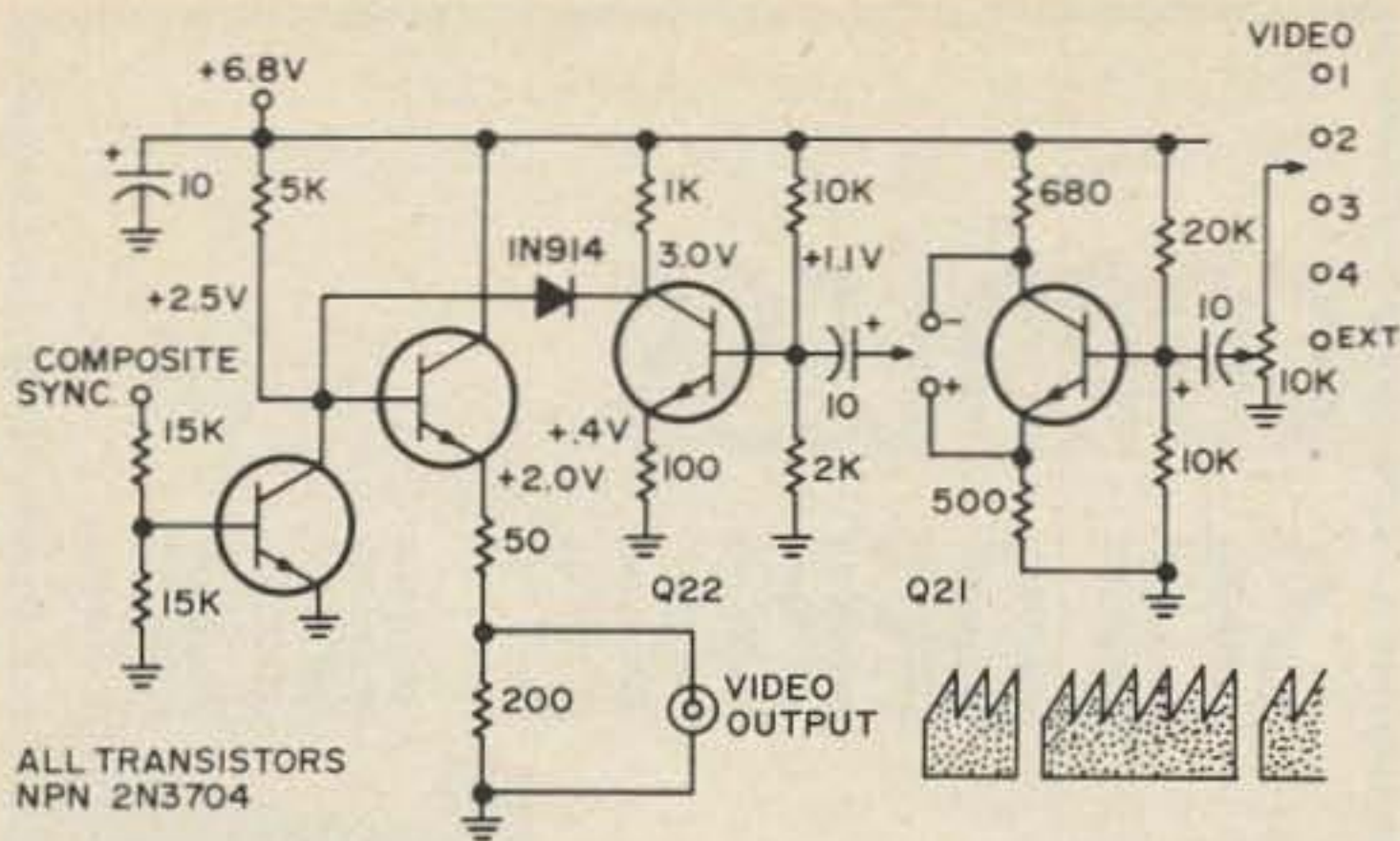


Fig. 6. The video output stage adds the composite sync signal to the video and produces a 1V signal suitable for modulating low powered rigs.

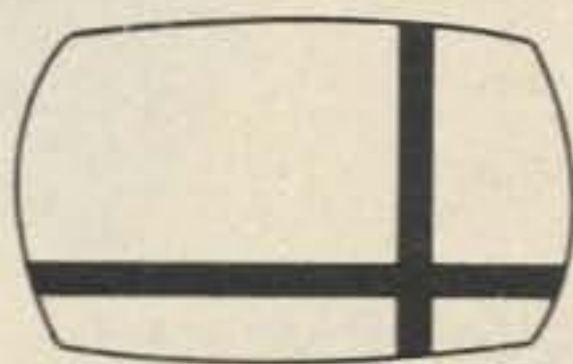By delaying the vertical sync pulse approximately $\frac{1}{2}$ frame and delaying the horizontal $\frac{1}{2}$ scan, then adding the signals, we get this:



The circuitry is simple, and the signal is eye-catching as well as good for aligning the rig.

Flying Spot Scanner

Patterns are fine, but it is also desirable to transmit "live." A camera requires expensive tubes and deflection circuits which are difficult to make work properly. Worse yet, there are so many knobs to adjust. A flying spot scanner can transmit live using a TV set to scan across the image. The sync information can be transmitted to the set on an unused channel or jeepped into a monitor (connected to the set after the video detector). The TV set scans a white raster; the image (crayon or electrical tape on Saran-wrap) cuts off the light. A light sensor picks up the variations in light. No available semiconductors could respond fast enough to high frequency video, so a photomultiplier tube was used. With this method, no lens system is needed. Pot 1 adjusts the sensitivity of the tube. Too sensitive, and the edges of the pictures are dark; not sensitive enough and no picture. Pot 2 compensates

for the finite decay time of the phosphors which shows up as smear on the set. While adjusting this pot the signal level will go down and must be compensated in Pot 1. Q17 and Q18 form a "bootstrap" amplifier; a method of getting constant high input impedance at high frequencies with transistors. Q18, Q19 and Q20 make a wideband video amplifier with *no* coils.

This is the thing for test patterns, call letters and calling CQ.

Video Output Amplifier

The final step of the video chain is the sync inserter. In this design Q21 is a phase inverter for positive or negative video. Q22, the final stage of amplification, drives Q23 emitter follower for a low output impedance. Q24 and the diode in its collector insert composite negative going sync. The output is standard 1V negative going sync suitable for modulating a low power rig and the monitor.

The TV Transmitters

The remainder of the video system includes the aural carrier, generator, and the UHF transmitter. It may also be necessary to monitor video without a direct connection to the monitor. A channel 3 transmitter is described which operates on standard 1V peak-to-peak negative sync, and can be placed anywhere in the line. A channel 10 or channel 11 transmitter is also described for use with the flying spot scanner described earlier. Its purpose is to transmit composite

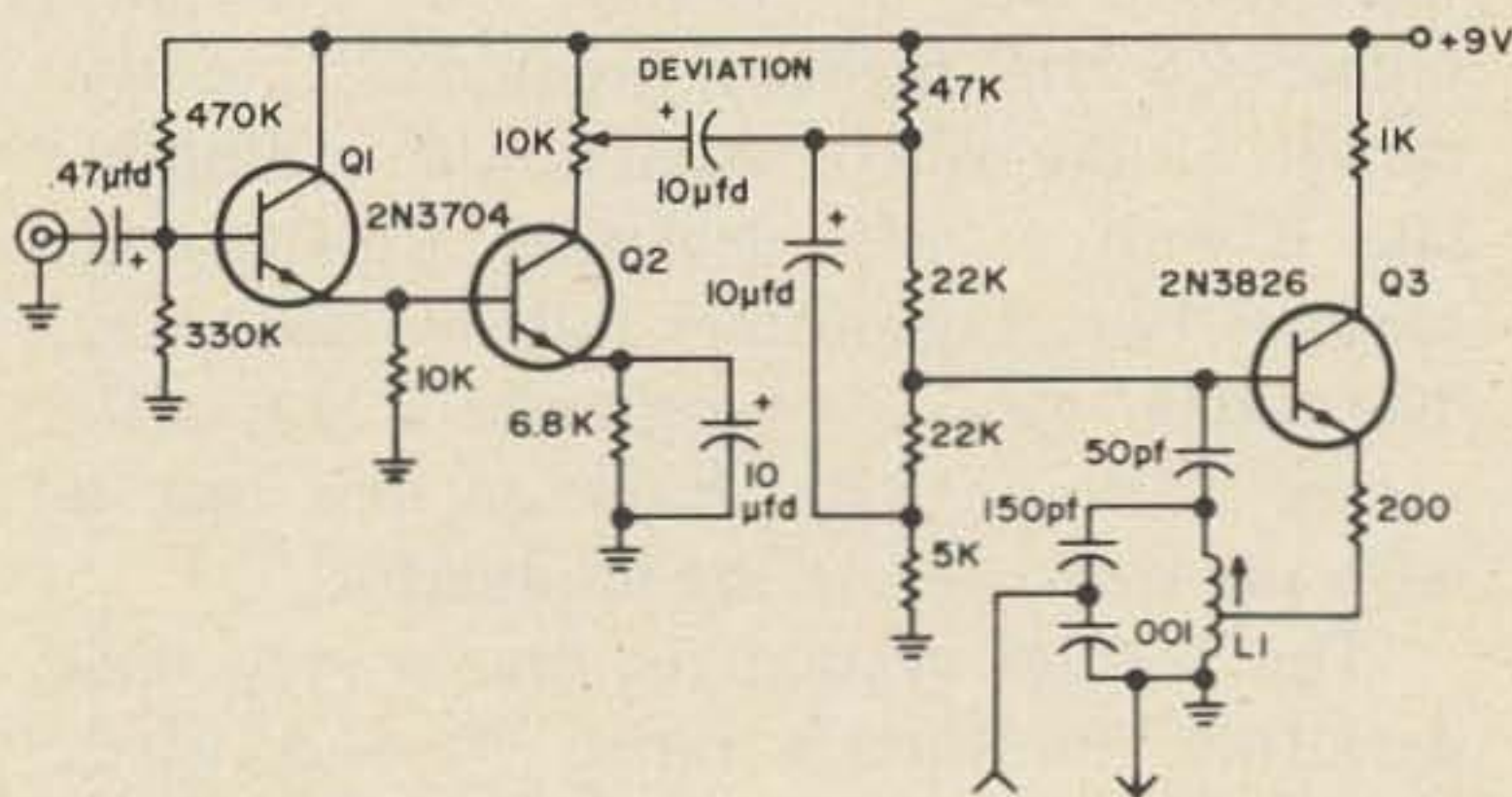


Fig. 7. Aural carrier generator. The 4.5 MHz FM output of this circuit can be mixed with the video signal for simultaneous transmission of both audio and video information. L1 - 50 turns, 2 strands of No. 36 in parallel on 3/8 in. (std) slug tuned form. Tap is 20 turns from ground.

K-ENTERPRISES



PRESCALER MODEL PD-301

\$45.50

Model PD 301 is a 300 MHz prescaler designed to extend the range of your counter ten times. This prescaler has a built-in preamp with a sensitivity of 50 mV at 150 MHz, 100 mV at 260 MHz, 175 mV at 300 MHz. The 95H90 scaler is rated at 320 MHz. To insure enough drive for all counters, a post amp. was built-in. The preamp has a self contained power supply regulated at 5.2V + .08%. (Input 50 Ohms, Output Hi Z)

All prescalers are shipped in a 4" by 4" by 1 1/2" cabinet. All are wired and calibrated.

K-ENTERPRISES

1401 NORTH TUCKER
SHAWNEE, OK 74801
405-273-1598

sync information to the scanning source TV set. With little modification it could be used as a video transmitter. The major goal to the ham radio operator is to transmit the video information in the 435 MHz region. Two UHF oscillators are discussed with their pros and cons and problems.

The Aural Carrier Generator

There are two ways of transmitting audio with video. One method is to have a transmitter 4.5 MHz higher in frequency than the carrier of the video; then frequency modulate it with 25 kHz deviation. This system requires two transmitters and two antennas. The other way is to generate a 4.5 MHz carrier with 25 kHz deviation and mix it with the video before the modulator.

The second system requires a very high deviation to carrier ratio: 5.56×10^{-3} , compared with $.75 \times 10^{-3}$ for commercial FM, and $.1 \times 10^{-3}$ for narrow band FM. Once generated it can be mixed with the video on the 1V peak-to-peak line requiring only .1V for the standard 10% video to audio ratio.

Greatest Advance in
Soldering Since Electricity

CORDLESS SOLDERING IRON

Industrial

- Completely Portable
- Heats in 5 Seconds
- Solders up to 150 Joints in One Charge!
- Recharges Automatically on its Own Stand
- New Working Freedom Anywhere . . .
SHOP - LAB - or IN THE FIELD

=7500 - Kit includes Cordless soldering iron, fine tip, automatic 110VAC recharging stand and instruction booklet. **\$19.95** postpaid. *No C.O.D.s*

Accessories . . .

- =7585 Automobile charger for cordless iron . . . **\$4.95**
- =7545 Fine replacement tip . . . **\$2.50**
- =7535 General purpose tip . . . **\$2.50**
- =7546 Heavy Duty, high temp. tip . . . **\$2.50**

Ideal Christmas Gift!



ALARM COMPONENT DIST. Dept. ST

33 New Haven Ave. W. Hartford, Conn. 06460

This circuit uses a Darlington amplifier for a high impedance microphone, and a conventional Hartley oscillator modifier for wide frequency modulation. Frequency modulation is accomplished in this oscillator by changing the interelectrode capacities of the transistor Q3.

The Composite Sync Transmitter

For the flying spot scanner, a TV set must be "in sync" to generate a scanning raster. A simple off-on transmitter will do the job, being on during sync and off during


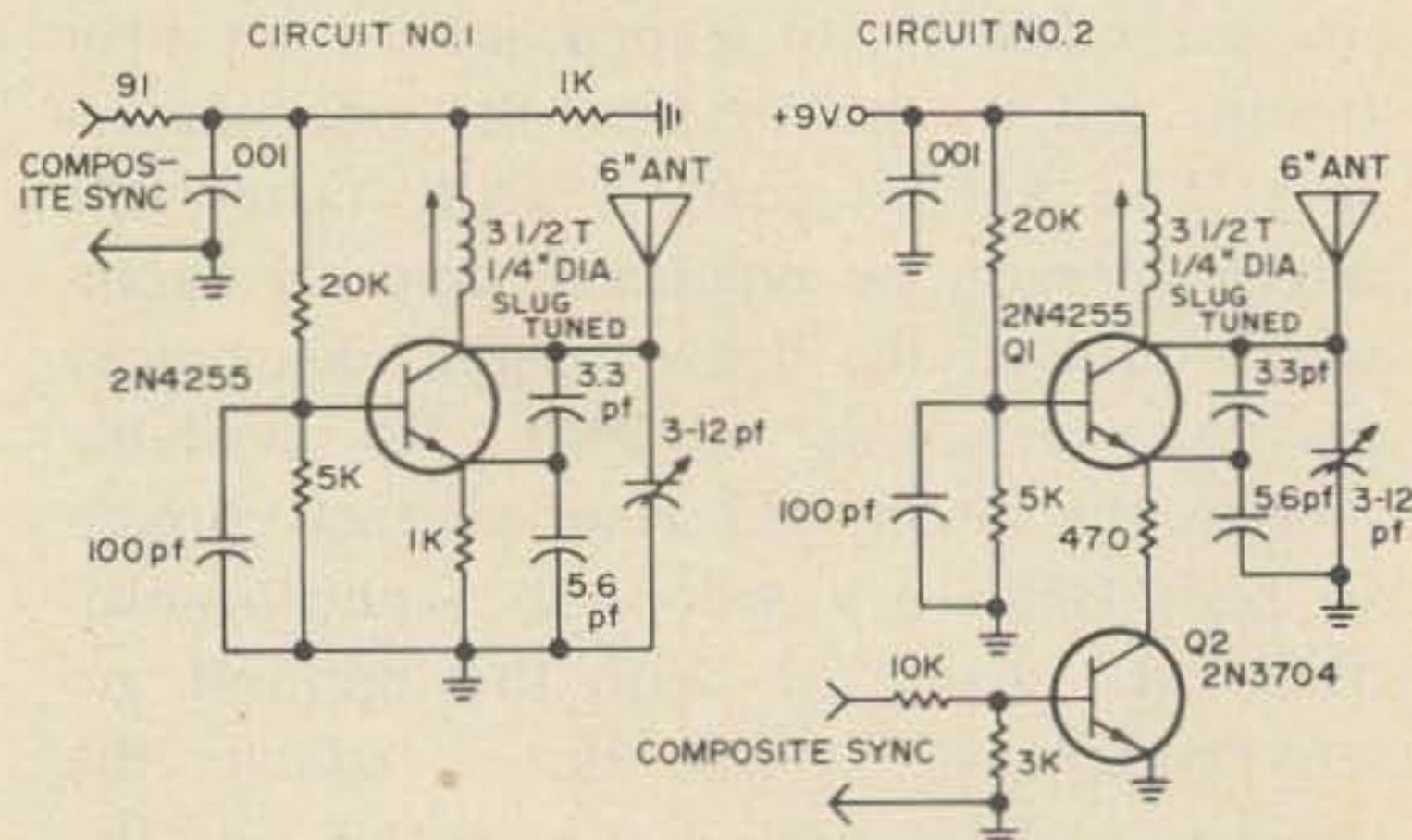


Fig. 8. Two simple composite sync transmitter circuits.

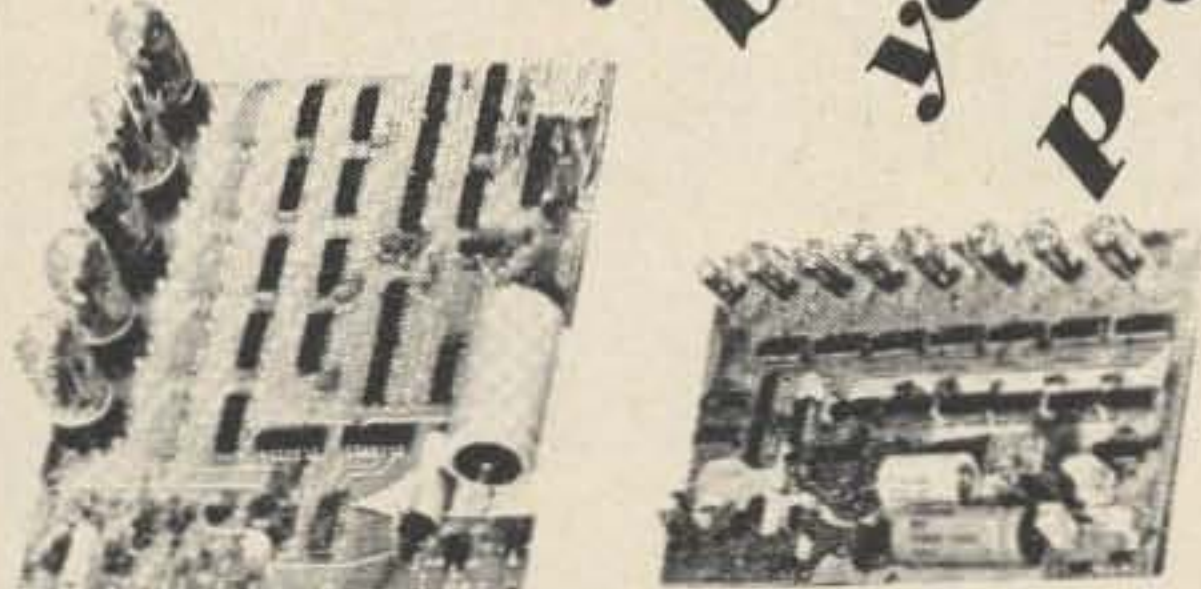now there is no excuse for not building your pet project!



SC 250 8 DIGIT COUNTER SEMI-KIT with built in prescaler, and p.s. good up to approximately 250 MHz. Fully assembled and tested board.
Send for data **\$165**

- ST-5A BOARDS ONLY (same size as those in the ST-6) \$ 5.25
- ST-5A KIT OF ELECTRONIC PARTS \$ 54.00
- ST-6 BOARDS ONLY (these are the 8 original by W6FFC) \$ 18.00
- ST-6 KIT OF ELECTRONIC PARTS \$128.50
- MOD. KIT FOR UPDATING THE ST-5 TO THE ST5A \$ 9.00
- AK-1 BOARD ONLY (same size as those in the ST-6) \$ 3.25
- AK-1 KIT OF ELECTRONIC PARTS (Same size as those in the ST-6)..... \$ 20.00
- PEMCO MODEL 50A FREQUENCY COUNTER SEMI-KIT \$125.00

This is a fully assembled and tested board with built-in power supply, cabinet, etc. Write for details.
You must supply the cabinet, A.C. cord, meter, switches, etc. on all kits except where noted otherwise. (All prices are postage paid - we pay shipping.)

If you have been putting off building because of circuit board layout, you have no problems . . . just send a schematic to PEMCO and we will design and build your circuit board to your specs using high quality G10-FR4 2 oz. copper and tin plated for long resistance to oxidation.

PEMCO ELECTRONICS
Inc. MANUFACTURING
422 18th St., N.E., Salem, Ore. 97301, (503) 585-1641

super sensitive PREAMPS

START
HEARING the
WEAK ONES



JANEL makes a preamp for improving the performance of almost any receiver. All are resistant to overload and fully diode protected. Top quality construction.

APPLICATION	MODEL	FREQUENCY
OSCAR VI	30PB	29.5 MHz
6 Meters	50PB	50.5 MHz
2 Meters	144PB	144 MHz
2 Meter FM	147PB	147 MHz
220 MHz	220PB	220 MHz
Aircraft	120PB	108-140 MHz
FM	100PB	88-108 MHz
TV	TV PB	Ch 2-13 (Specify)
High Band	160PB	146-174 MHz
432 MHz	432PA	432-438 MHz
440 ATV	432PA T	435-445 MHz
450 FM	432PA F	440-450 MHz
UHF FM	432PA U	450-470 MHz

PB models are only \$19.95 and the 432 PA models are only \$29.95. All are in aluminum cases, have BNC connectors (others available), require 12 vdc, and are postpaid and guaranteed. Specify model and frequency when ordering. Other models are available with AC power supply. Write for details.

Write for our *SANTA CLAUS WISH LIST* of Preamps and Converters.

JANEL laboratories
BOX 112, SUCCASUNNA, NJ 07876
Telephone: 201-584-6521

scan. The frequency can be adjusted to any unused channel. In this case, it was adjusted in between channel 10 and channel 11 to avoid interference.

Circuit #1, the original circuit, is a flea power oscillator, deriving power from the composite sync terminal. This circuit caused several not too serious problems, however:

1. Time for capacitors to charge delayed sync and shifted resultant picture to the right. (This can also be caused by overscan in the scan source.) This can be overcome

with very small bypass capacitors.

2. The slight difference in amplitude between horizontal and vertical sync caused the vertical and horizontal to be transmitted on different frequencies, making it hard to sync the TV set.

These problems were solved with one more transistor as shown in circuit #2. The lower emitter resistor allows it to oscillate at higher power. Constant voltage on the collector keeps the frequency from shifting. The transistor Q2 turns the transmitter off

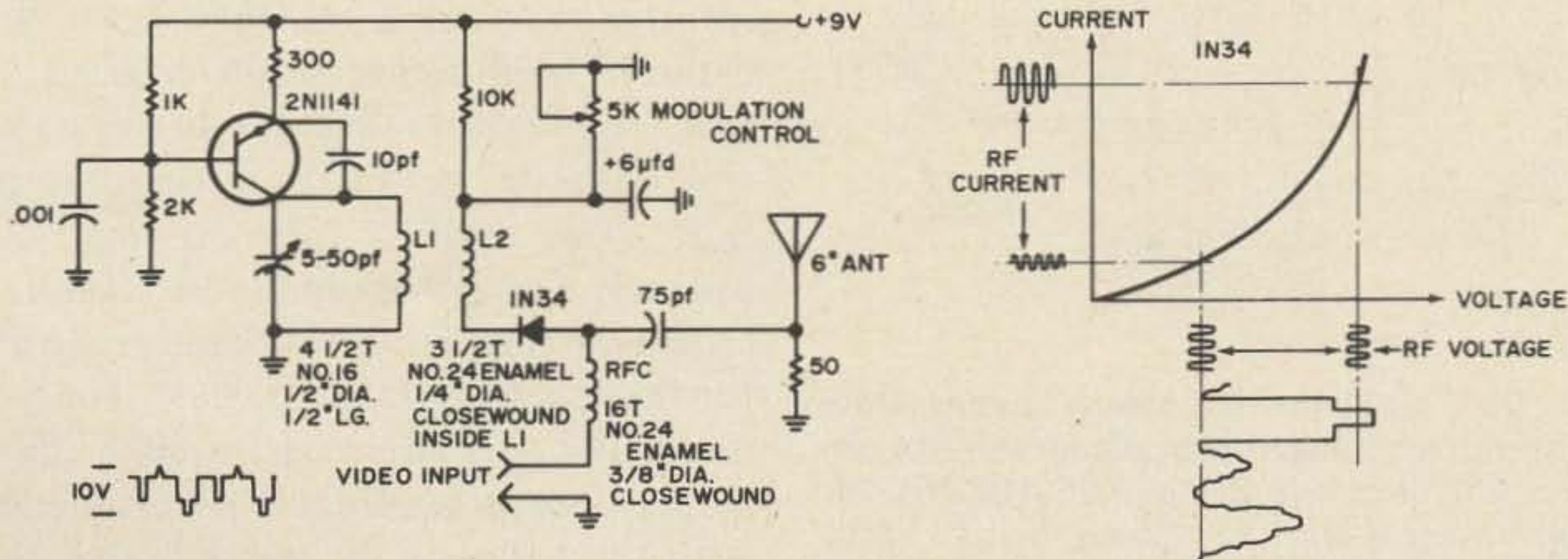


Fig. 9. A monitor transmitter for channel 3. See text for details on adjusting the modulation control. Modulate this circuit with Fig. 6.

and on, and since there is no capacitive load in the composite sync signal path, the sync signal is not delayed, and the picture is not shifted.

Monitor Transmitter Channel 3

This transmitter uses the same basic oscillator as the channel 10 sync transmitter. Operating with a 70 mW carrier the germanium diode is biased into conduction with current from the standard video line. As current in the diode increases, its resistance goes down and passes more rf to the antenna. As current decreases, the diode goes toward "cutoff" and doesn't conduct the rf voltage (see graph). The potentiometer is adjusted near the maximum voltage or white level and thus gives 100% modulation. This transmitter can be placed on the video line but is not a termination, so another monitor transmitter can also be on the line.

The UHF Transmitter

This simple 6J6 UHF oscillator works quite well as a low power transmitter in the UHF region. Standard video (1V negative sync) is ac coupled to the cathode for cathode modulation. It was the first one I had tried in the UHF band without the use of an antenna. The plate lines were 7.5 cm long. When the length of the plates and wires inside the tube and the length of the capacitor are added to the length of the lines, we have approximately a half-wavelength, which determines the frequency. Wave phenomenon are noticeable, providing the lines act as transmission lines. In

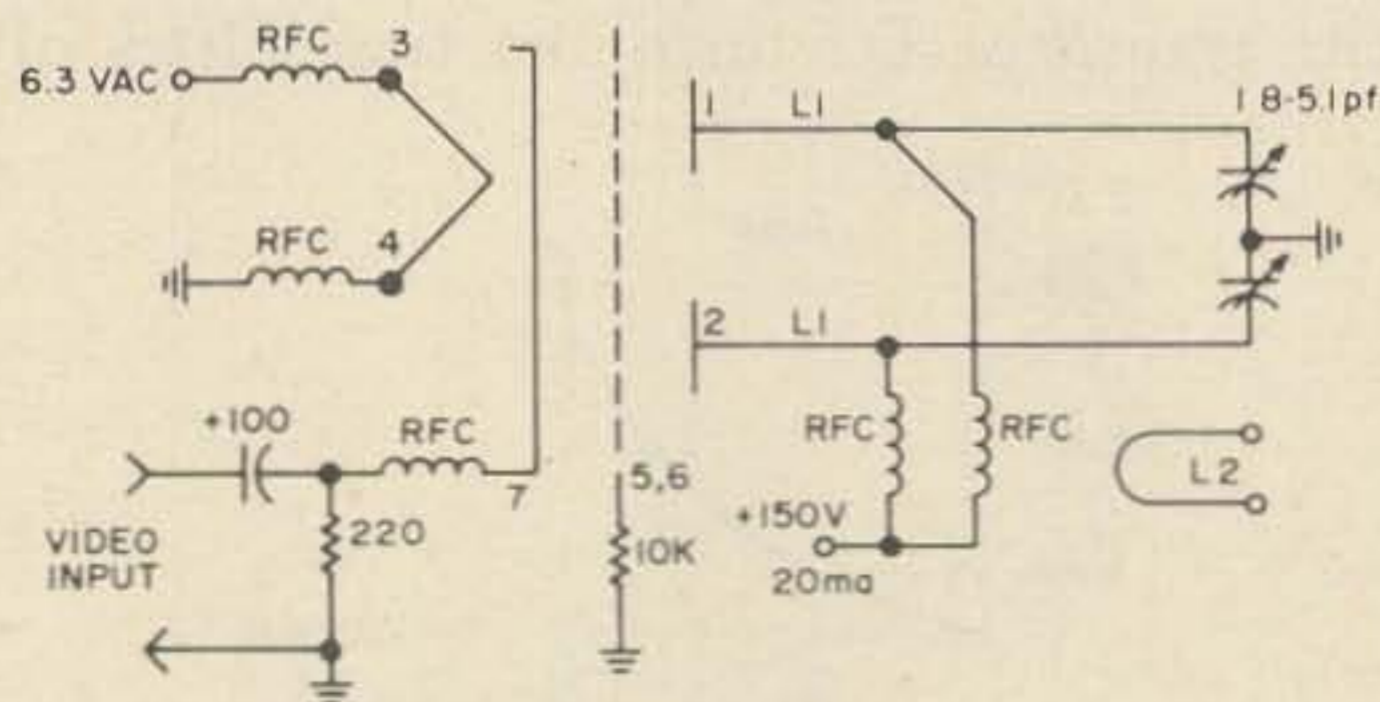


Fig. 10. A UHF oscillator that can be used as a low power transmitter. The video signal can be obtained from the circuit in Fig. 6. RFC-15T No. 24, 3mm diam. Channel 20, L1 - 7.5cm, No. 14 brass, spaced 16mm, tap at 25mm from tube. 435 MHz, 11.5cm No. 14 brass spaced 20mm, tap at 38mm from tube. L2-5cm No. 16, near L1.

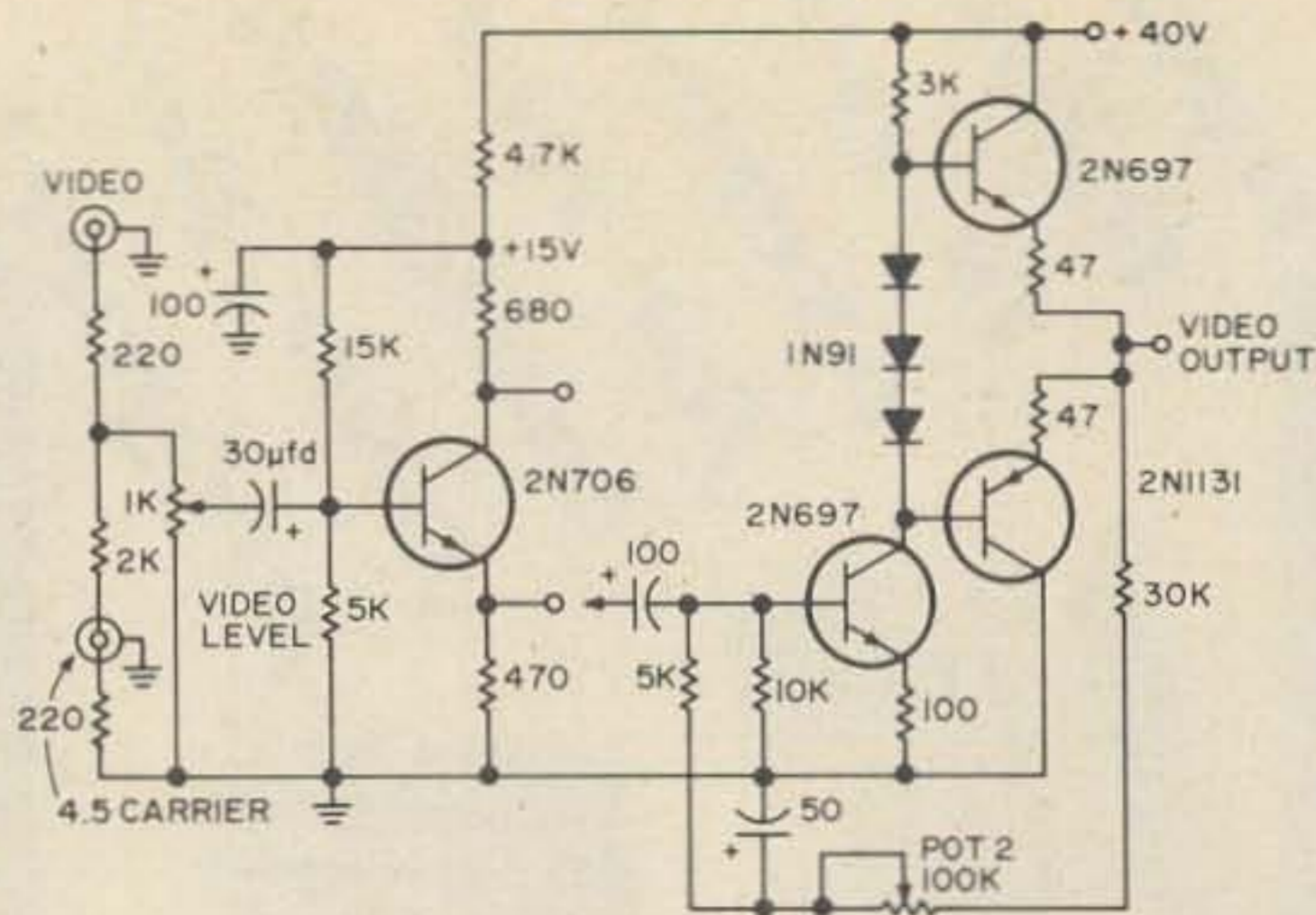


Fig. 11. A video modulator for driving higher power transmitters. It can be driven by the circuits in Figs. 6 and 7.

the dark a pencil draws little sparks at each end of the lines and pulls the frequency down considerably, indicating voltage maximums. The center, however, can be touched with a screwdriver and frequency doesn't change, indicating a voltage null. The rf chokes are tapped here. Of course amateur radio license allows TV transmission in the 450 MHz band, and 11.5 cm lines are used then.

The circuit is actually a push-pull tuned plate oscillator, whose feedback is plate to grid capacitance.

High Power Modulator

For modulating the grid or cathode of a high power oscillator, a larger voltage swing and a lower output impedance is necessary. The circuit shown here can develop a 35V swing, and is also a convenient place to mix the audio carrier with the video. The transistors are chosen for high gain, high voltage, and high frequency response. The phase inverter was used so that both grid and cathode modulation could be tried, because grid modulation requires positive going sync, and cathode modulation requires negative sync. The emitter follower pair is biased properly for rather small idle current and no crossover distortion, by diodes, and is used for the low impedance output. The potentiometer Pot 2 is adjusted to make the voltage at the output terminal 20V. Audio is mixed with the video at the input so that the video to audio ratio is constant.

...WA7NMO

BRING YOUR **BRICK** IN AT NIGHT!



Now . . . a universal AC power supply for your FM transceiver *and* your amplifier!

At last, you can get the power you want at the price you want, with the new PW-4 from E&L. Plug it into any 110-120 volt AC source and you get a rated output of 13 volts DC @ 12 amps, I.C. regulated to $\pm 3\%$! The PW-4 features a circuit breaker reset, modern cabinet design, and heavy duty components for reliability. Use it with most 12-13 volt DC transceivers, together with your 50-60 watt amplifier. The PW-4 sells for \$84.95, direct from the factory, or your local distributor.

Get your mobile rig into the house . . . get a PW-4!

Write to:



E&L INSTRUMENTS, INC.

61 First Street

Derby, Connecticut 06418

attn: Dick Vuillequez — W1FBS

NOW!!

an exciting addition to the magnificent Kenwood line...



The New TS-520 Transceiver

The new TS-520 is the transceiver you have wanted, but could not buy until now. A no-compromise, do everything, go everywhere 5 band transceiver for SSB or CW that performs equally well at home, in an automobile, airplane, boat or trailer. The top of the line TS-900 and the superb R-599A Receiver and T-599A Transmitter are already well known to all amateurs. Now the TS-520 fills out the line offering the famous Kenwood quality and reliability at a price most amateurs can afford.

★ Here are 30 special reasons you will want to own a TS-520. After you have operated one, you will doubtless give us 30 more why you're glad you own one. ★

- | | | |
|--|--|--|
| 1. Built-in AC power supply | reliable, with heater switch for mobile receive-only operation | 22. Full metering |
| 2. Built-in 12 volt DC power supply | | 23. Selectable SSB |
| 3. Built-in VOX with adjustable gain, delay and anti VOX | 13. Built-in cooling fan | 24. Selectable AGC operation for different modes |
| 4. 1 KHz dial readout | 14. Accessory external VFO & accessory external speaker | 25. VFO indicator light |
| 5. Ultra stable FET linear VFO | 15. Built-in speaker | 26. Built-in selectable ALC action for speech processing |
| 6. Built-in noise blanker | 16. Modern styling & functional design. Modular construction. | 27. Carrying handle |
| 7. Built-in RIT circuit and RIT indicator light | 17. Amplified ALC | 28. Rugged 6146 type final tubes |
| 8. 8 pole crystal filter | 18. TUNE position increases tube life | 29. Internal cross-channel operation. |
| 9. Built-in 25 KHz crystal oscillator | 19. Maximum TVI protection | 30. Push button WWV reception |
| 10. Provisions for optional CW filter | 20. Built-in fixed channel operation (4 channels) with indicator light | Proven Kenwood quality and reliability |
| 11. Break-in CW with sidetone | 21. Provisions for use with a VHF transverter | The Price: \$599.00 |
| 12. Completely solid state except final section. Compact, low current, | | subject to change without notice. |

Accessories: External VFO-(VFO-520), External speaker - (SP-520), CW Filter - (CW-520)

Available from
Kenwood dealers
throughout the U.S.

Henry Radio

11240 W. Olympic Blvd. Los Angeles, Calif. 90064 213/477 6701
931 N. Euclid Anaheim Calif. 92801 714/772 9200
Butler, Missouri 64730 816/679 3127

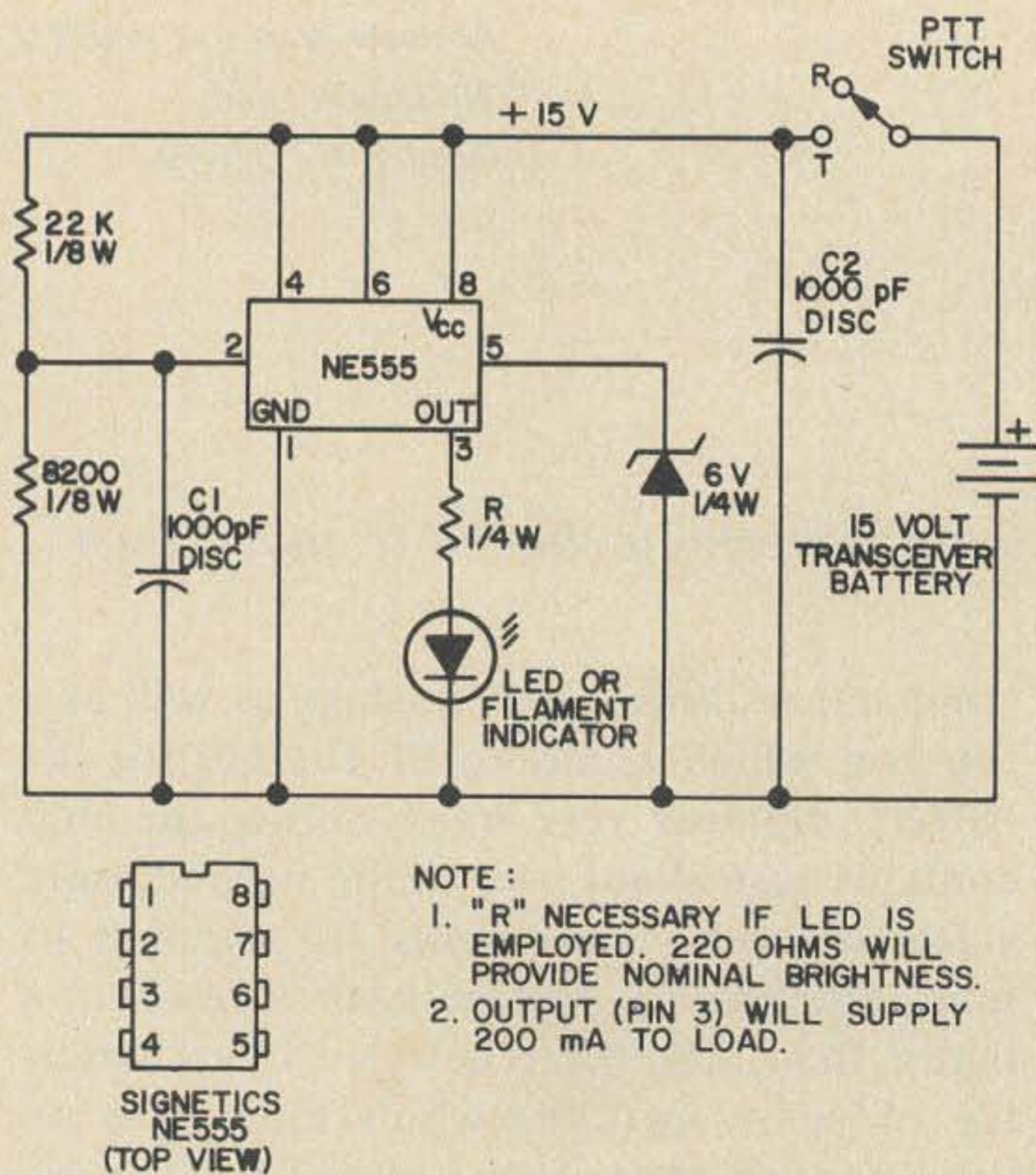


Fig. 2. The schematic of the voltage monitor.

between one and two mA to flow through the zener. The input to comparator A is connected to the battery voltage keeping its output high and resetting the flip-flop. As long as the input to comparator B is higher than 3V, both flip-flop inputs are high, and the output at pin 3 is low (ground). When the battery voltage drops below the threshold set by R1 and R2 (12V, in this case), comparator B output goes to ground setting the flip-flop and causing the output at pin 3 to go high. This output stage consists of two transistors in a totem pole configuration so that the device can supply high current as well as sinking current to ground. One of these transistors (only one) will be conducting at all times, and the chip is capable of supplying or sinking up to 200 mA. In this case it was found convenient to supply current to a load.

Almost any sort of indicator may be used; I found one of the tiny LEDs available from Industrial Devices to be very satisfactory. These are available in either red or green and are small enough to fit in the most compact rig. I mounted mine in the front cover of my HT220 just above the speaker grill so that it is just at eye level when transmitting. There is no current limiting within the NE555, so an external series

resistor is necessary if an LED is employed. If a filament type lamp is used this is not required. A small buzzer or even another NE555 used as an oscillator could be powered by the unit if space permits and an audible alarm is desired. The point at which the lamp will light is determined by the voltage applied to pin 2. This can be set by a fixed external divider (as shown on the schematic) or by a pot. I found that fixed resistors were more stable. The values given are for a 15V battery and will cause the warning light to go on when the voltage reaches about 12V. If a different battery is used, set the firing point to about 3/4 of the fully charged voltage. Capacitor C1 is required for an rf bypass and to prevent internal oscillation. C2 is another rf bypass; a larger value might be required for lower frequency operation on 10m or below.

The static current drain (light off) is about 12 mA. Since the battery voltage will show the biggest drop during transmit periods, the monitor should be connected across the transmit supply only (so as not to drain the battery during receive operation).

If room permits, a small PC board could be used, but in my rig there was precious little room available, and the entire assembly was mounted over the i-f amplifier IC in the HT220 slimline. The circuit was constructed by soldering the zener diode and the resistors between the pins of the NE555 chip. The LED was mounted over the speaker and the speaker ground was used for grounding the cathode of the LED. A drop of silicon rubber was used to secure the LED to the front. A note of caution — many LEDs have their anode connection as the outside case so that insulating will be necessary if a metal panel is used.

In use the battery monitor lets you know when your battery is getting close to requiring a charge too. Ni-cads will recover somewhat from a long, high current drain and after a minute or two of steady talking the light may come on to let you know it's time to let the battery rest for awhile. As the battery gets weaker this period of time decreases. When the light comes on almost immediately after pushing the PTT button it's time for the charger.

...K2ETN

Mann COMMUNICATIONS

Mann has the *NEW*
Motorola Metrum II



144 - 148 MHz 2 Meter Mobile

- 12 Channel Capability
- All Solid State
- 0.35 μ v at 20db Receiver Sensitivity
- 100db at 25 KC Selectivity
- Reversible Control Panel
- A.C. Power Supply Available

10 watt **\$399.95**

25 watt **\$499.95**

for further information call or write:

Mann COMMUNICATIONS & ELECTRONICS, INC.



28710 Canwood St.
Agoura, CA 91301
(213) 889-6666

and

2837 North 24th St.
Phoenix, AZ 85008
(602) 955-4570





New Heathkit 2-meter Transceiver ONLY \$179⁹⁵*

HW-202 SPECIFICATIONS—RECEIVER—Sensitivity: 2 dB SINAD* (or 15 dB of quieting) at $.5\mu\text{v}$ or less. **Squelch threshold:** $3\mu\text{v}$ or less. **Audio output:** 2 W at less than 10% total harmonic distortion (THD). **Operating frequency stability:** Better than $\pm.0015\%$. **Image rejection:** Greater than 55 dB. **Spurious rejection:** Greater than 60 dB. **IF rejection:** Greater than 75 dB. **First IF frequency:** 10.7 MHz ± 2 kHz. **Second IF frequency:** 455 kHz (adjustable). **Receiver bandwidth:** 22 kHz nominal. **De-emphasis:** -6 dB per octave from 300 to 3000 Hz nominal. **Modulation acceptance:** 7.5 kHz minimum. **TRANSMITTER—Power output:** 10 watts minimum. **Spurious output:** Below -45 dB from carrier. **Stability:** Better than $\pm.0015\%$. **Oscillator frequency:** 6 MHz, approximately. **Multiplier factor:** X 24. **Modulation:** Phase, adjustable 0-7.5 kHz, with instantaneous limiting. **Duty cycle:** 100% with ∞ VSWR. **High VSWR shutdown:** None. **GENERAL—Speaker impedance:** 4 ohms. **Operating frequency range:** 143.9 to 148.3 MHz. **Current consumption:** Receiver (squelched): Less than 200 mA. Transmitter: Less than 2.2 amperes. **Operating temperature range:** -10° to 122° F (-30° to + 50° C). **Operating voltage range:** 12.6 to 16.0 VDC (13.8 VDC nominal). **Dimensions:** 2 $\frac{3}{4}$ " H x 8 $\frac{1}{4}$ " W x 9 $\frac{7}{8}$ " D.

*SINAD = $\frac{\text{Signal} + \text{noise} + \text{distortion}}{\text{Noise} + \text{distortion}}$

It's an all solid-state design that you can build and completely align without special instruments. And this compact little beauty gives you 36 channel capability with independent push-button selection of 6 transmit and 6 receive crystals. 10 watts minimum output into an infinite VSWR without failure. And for the ultimate in convenience there's the optional tone burst encoder for front panel selection of four pre-settable tones. The HW-202 kit includes two crystals for set-up and alignment and simplex operation on 146.94; push-to-talk mike; 12-volt hook-up cable; heavy duty clips for use with temporary battery; antenna coax jack; gimbal bracket, and mobile mounting plate.


Kit HW-202, 11 lbs., mailable179.95*
Kit HWA-202-2, Tone Burst Encoder, 1 lb.24.95*
Kit HWA-202-1, AC Power Supply, 7 lbs.29.95*
Kit HWA-202-3, Mobile 2-Meter Antenna, 2 lbs.17.95*
Kit HWA-202-4, Fixed Station 2-Meter Antenna, 4 lbs.15.95*

... and here's 40 watts out for your 10 watts in

The Heathkit HA-202 2-Meter Amplifier works with any 2-meter exciter delivering 5-15 watts while pulling a meager 7 amps from any 12 VDC system. No additional power supplies are required. All solid-state components mount on a single circuit board for easy two-evening assembly. Manual shows exact alignment procedures using a VOM or VTVM. Connecting cable and antenna cable are included.

Kit HA-202, 4 lbs.69.95*

HA-202 SPECIFICATIONS—Frequency range: 143-149 MHz. **Power output:** 20W @ 5 W in, 30W @ 7.5W in, 40W @ 10 W in, 50W @ 15 W in. **Power input (rf drive):** 5 to 15W. **Input/output impedance:** 50 ohms, nominal. **Input VSWR:** 1.5:1 max. **Load VSWR:** 3:1 max. **Power supply requirements:** 12 to 16 VDC, 7 amps max. **Operating temperature range:** -30° F. to +140° F. **Dimensions:** 3" H x 4 $\frac{1}{4}$ " W x 5 $\frac{1}{2}$ " D.

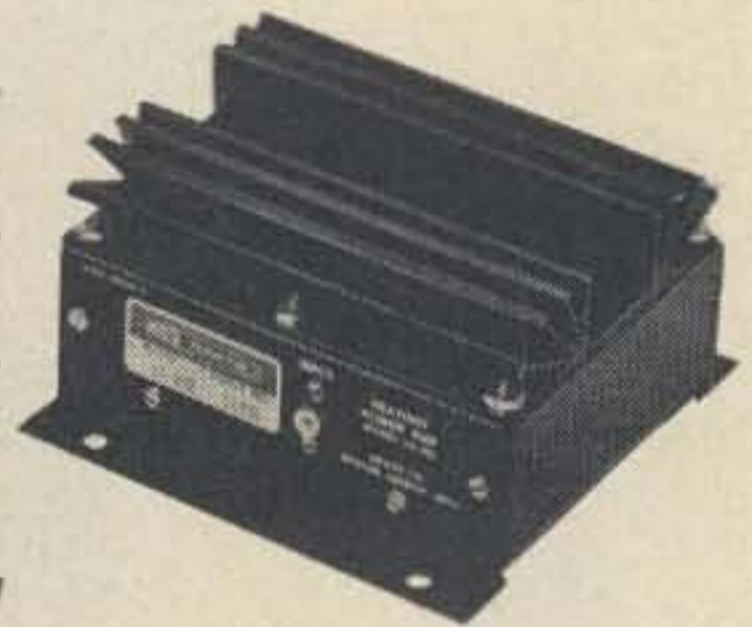

\$69⁹⁵*

... then there's this perfect 2-meter tune-up tool



\$29⁹⁵*

The Heathkit VHF/SWR Bridge tests transmitter output in power ranges of 1 to 25 watts and 10 to 250 watts $\pm 10\%$ of full scale. 50 ohm nominal impedance permits placement in transmission line permanently with little or no loss. Built-in SWR bridge for tuning 2-meter antenna for proper match, has less than 10-watt sensitivity.

Kit HM-2102, 4 lbs.29.95*

HM-2102 SPECIFICATIONS—Frequency range: 50 MHz to 160 MHz. **Wattmeter accuracy:** $\pm 10\%$ of full-scale reading.* **Power capability:** To 250 W. **SWR sensitivity:** less than 10 W. **Impedance:** 50 ohms nominal. **SWR bridge:** Continuous to 250 W. **Connectors:** UHF type SO-239. **Dimensions:** 5 $\frac{1}{4}$ " W, 5 $\frac{1}{8}$ " H and 6 $\frac{1}{2}$ " D, assembled as one unit.

*Using a 50 Ω noninductive load.

See them at your Heathkit Electronic Center —

HEATHKIT ELECTRONIC CENTERS — ARIZ.: Phoenix; **CALIF.:** Anaheim, El Cerrito, Los Angeles, Pomona, Redwood City, San Diego (La Mesa), Woodland Hills; **COLO.:** Denver; **CONN.:** Hartford (Avon); **FLA.:** Miami (Hialeah); **GA.:** Atlanta; **ILL.:** Chicago, Downers Grove; **IND.:** Indianapolis; **KANSAS:** Kansas City (Mission); **MD.:** Baltimore, Rockville; **MASS.:** Boston (Wellesley); **MICH.:** Detroit; **MINN.:** Minneapolis (Hopkins); **MO.:** St. Louis; **N.J.:** Fair Lawn; **N.Y.:** Buffalo (Amherst), New York City, Jericho; **L.I.:** Rochester; **OHIO:** Cincinnati (Woodlawn), Cleveland; **PA.:** Philadelphia, Pittsburgh; **R.I.:** Providence (Warwick); **TEXAS:** Dallas, Houston; **WASH.:** Seattle; **WIS.:** Milwaukee.

HEATH
Schlumberger

HEATH COMPANY Dept. 11-11
Benton Harbor, Michigan 49022

Please send FREE Heathkit Catalog.

Enclosed is \$ _____, plus shipping

Please send model(s) _____

Name _____


Address _____

City _____ State _____ Zip _____

*Mail order prices; F.O.B. factory AM-287

Kent A. Mitchell W3WTO
1760 Preston Rd.
Hagerstown MD 21740

HEATH GR-110 VHF SCANNING MONITOR

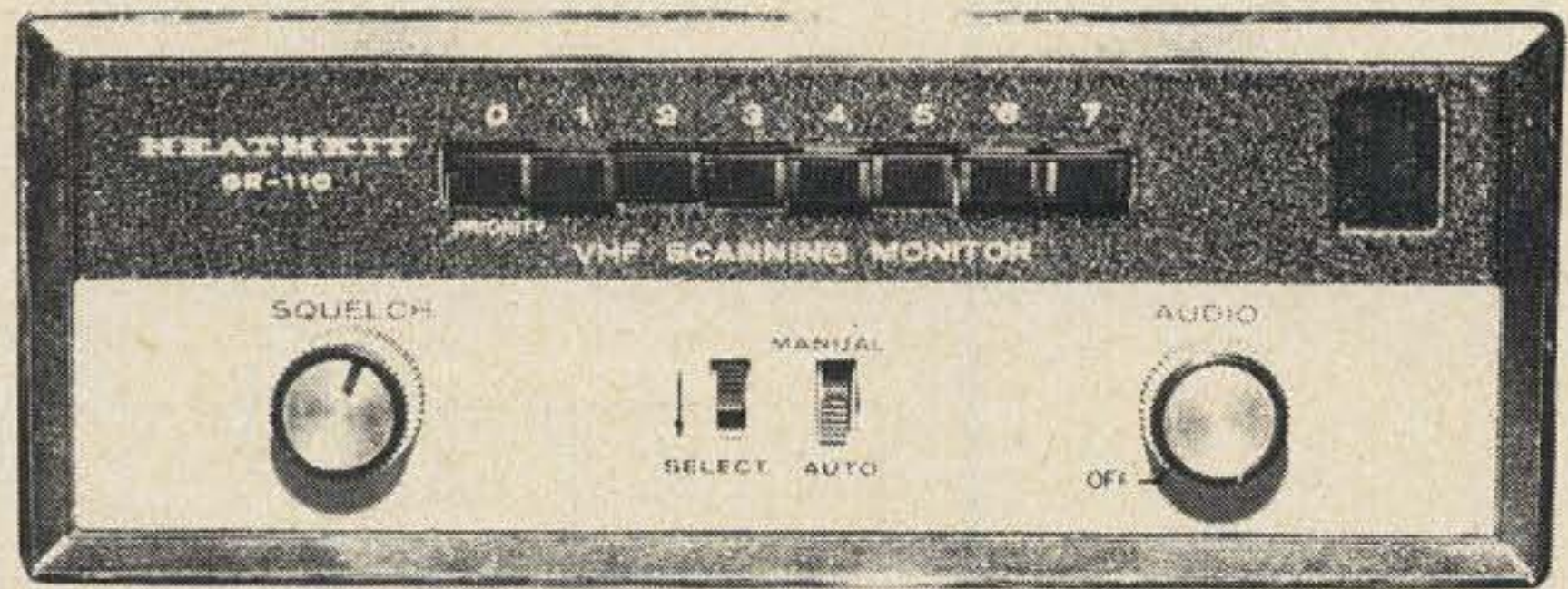

One of the popular fads these days is monitoring the radio transmissions of the local fuzz, fire companies and ambulance services. In fact, the local official parties concerned have no difficulty locating the scene of the crime, fire or accident. . .there is usually a crowd of "monitor freaks" which have beaten them to the event. The scanning type receiver is most often seen, as the chance of missing any excitement is eliminated. Most monitors around seem to be primarily brands available at the friendly neighborhood CB equipment store. One of these receivers had been on my want list for quite some time but, as I already had a shack full of gear and needed another receiver as much as the Senate Watergate Committee needed another witness, especially a non-ham band receiver, it was far down on the list. However, as usually happens, a Heathkit ad caught my eye because being offered was a unit with a frequency range that would enable me to monitor the local FM repeater gang (146.94) in addition to the police in my area (155.79) and at a price that is considerably less than other comparable units.

The Heath GR-110 circuits are comprised of 29 transistors, 8 ICs, 17 diodes and a 7 segment indicator tube. The unit operates either from a 120V power source via a conventional transformer-rectifier-filter arrangement or directly from a 12V battery in a mobile installation. The receiver front end consists of two rf stages and a mixer, all

of which are 40673 field effect transistors.

A feature of this monitor receiver is a "priority channel" which, if desired, will automatically take precedence over any other signal that is being received. For this purpose, a separate oscillator circuit, consisting of a 2N5232A and a X29A829, pulses the gating circuits and activates the priority channel crystal. If an rf signal is being detected on that frequency, the resultant voltage completes the gate logic and the receiver is locked on the priority channel as long as a signal is present, after which normal scanning is resumed.

Front panel pushbuttons allow selection or bypassing of any or all channels during the frequency scanning process, or a selector switch may be placed in the "manual" mode to continuously monitor one particular frequency. A "select" switch provides manual stepping to the desired channel or the scanning may be stopped by switching from auto to manual while the receiver is locked on a transmitted signal.

Assembly of the kit is facilitated by the use of three separate etched circuit boards and the usual Heath check-by-step assembly manual, which has improved over the years from a "Connect a 680 ohm resistor from N5 (S) to N7 (NS)" step on one page and an illustration on another page, to a combined step-with-arrow pictorial format that is easier to follow. However, after building Heathkits for twenty years, I've noticed that the usual paper bag full of resistors, capaci-


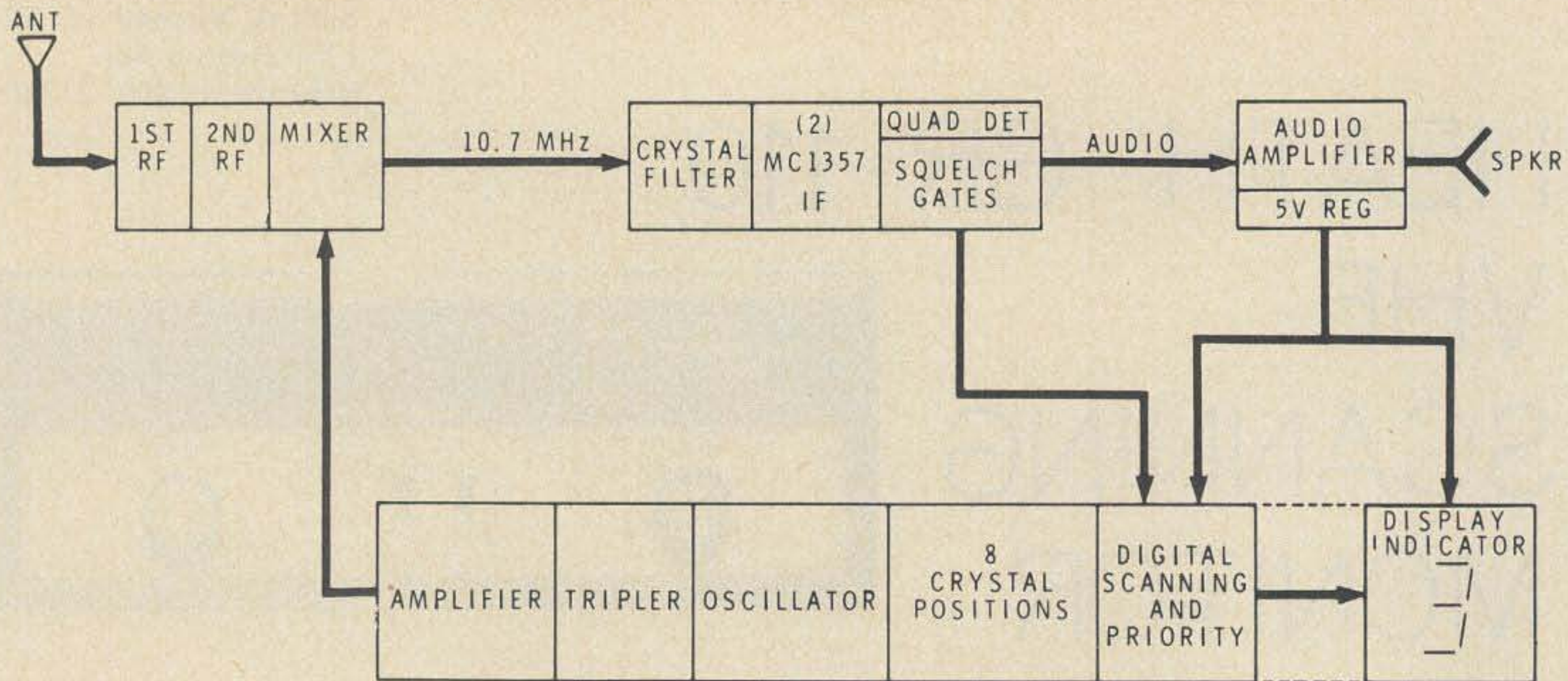


Fig. 1. Block diagram of the Heath GR-110 Scanning monitor.

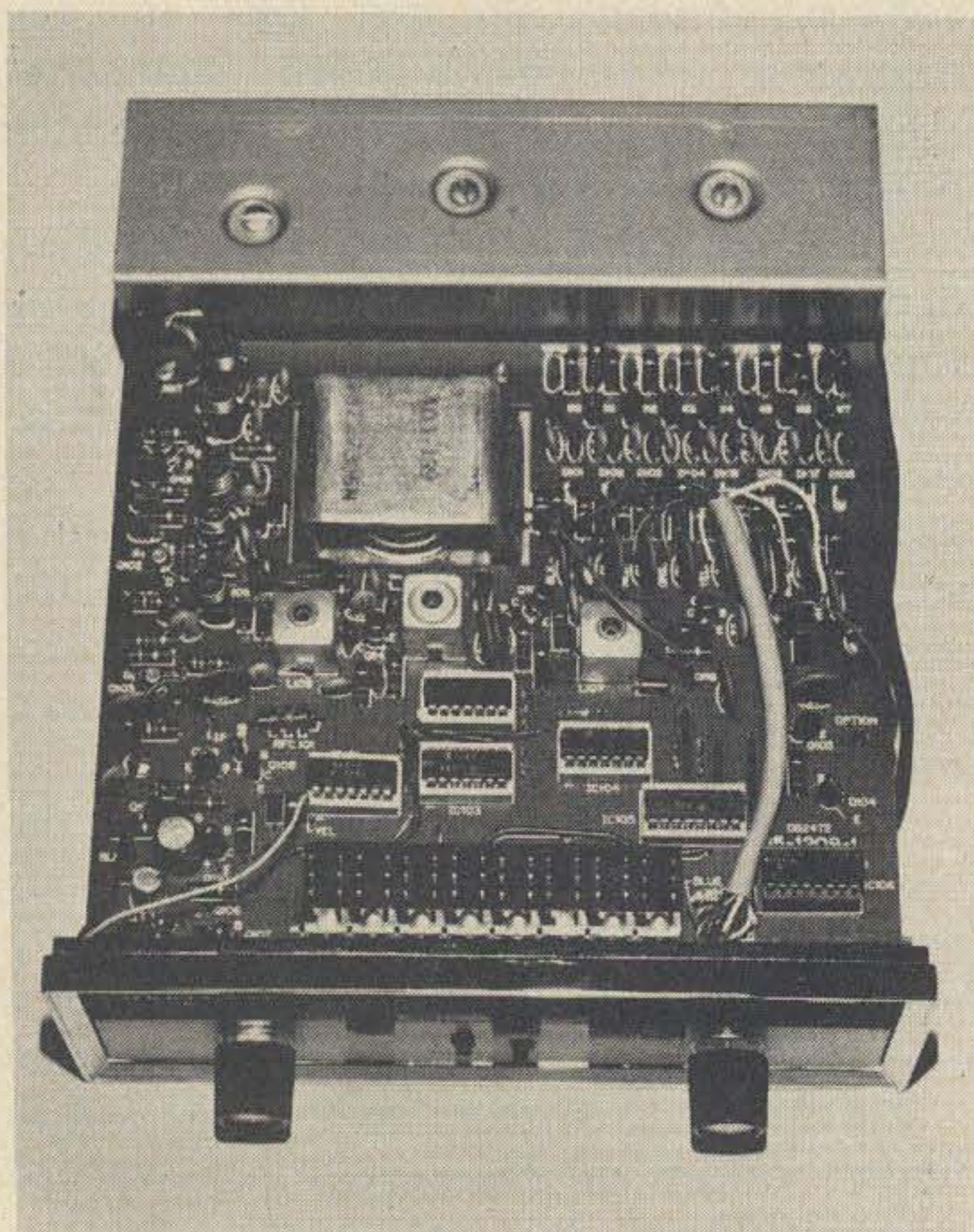tors, transistors and such has progressed (?) to a system wherein the bag and its contents are assigned a multitude of pack numbers, index numbers, Heath part numbers and the manufacturers part number. This may assist in some manner with Heath's inventory control or kit packaging process, but I personally feel that the inexperienced kit builder has enough problems without such numerical profusion.



The main circuit board contains the receiver front end (along left side), crystal oscillator circuitry (top right and center) and scanning circuitry (ICs at bottom).

The GR-110 is called a four-evening project. But, if you are a newcomer in the kit building world or are a Theodore Thumbs type, I recommend taking all the time that you personally require for a properly assembled unit. Good soldering techniques are a must. In fact, because I was trained in NASA methods of soldering, I went so far as to clean each circuit board foil pad and individual component lead prior to soldering, and cleaned the residual flux from the completed boards with alcohol upon completion. Also, I recommend the use of heat sinks on each transistor and diode lead while soldering. Alligator clips are fine.

Before the completed receiver can be aligned, at least one and preferably two, crystals must be installed. Crystals are *not* included with the kit, for obvious reasons. Heath does provide crystal certificates, at \$4.95 each, which should be ordered at the same time as the kit, and upon receipt, filled out with your desired local frequency and mailed immediately, directly to the crystal manufacturer. Hopefully, the arrival of a crystal and the finish date of the kit will be concurrent. Also, your local parts supplier more than likely has a supply of the more popular frequency crystals for your area in stock.

Alignment may be accomplished with or without instruments. The instrument method requires the use of an FM signal generator capable of covering the desired frequencies and a VTVM. If these instru-

If you like 2 METERS . . .

YOU'LL LOVE OUR

ALL NEW
HR-2B
NARROW BAND FM TRANSCEIVER



**15 OR 1 WATT POWER OUT/SWITCH SELECTABLE /
FULL 12 CHANNEL TRANSMIT AND RECEIVE CAPABILITY**

You'll like the crystal clear transmit and receive performance of this compact, 2 meter unit and so will those listening. The 12 transmit channels are provided with individual trimmer capacitors for the optimum in point-to-point and repeater applications. A HI/LO power switch provides 1 watt output or full rated output. The receiver has an audio output of 3 watts at excellent sensitivity. Solid state, American made quality at a low price.

\$229⁰⁰

AMATEUR NET

includes plug-in ceramic mike,
mounting bracket and transmit and
receive crystals for 146.94 MHz.

**Regency**
the first name in solid state

THE FM LEADER IN 2 METER AND 6 METER...AND NOW 220 MHz


Everyone has something.

FIXED STATION TRAP VERTICAL

40 THROUGH 10 METERS

HUSTLER

has everything!

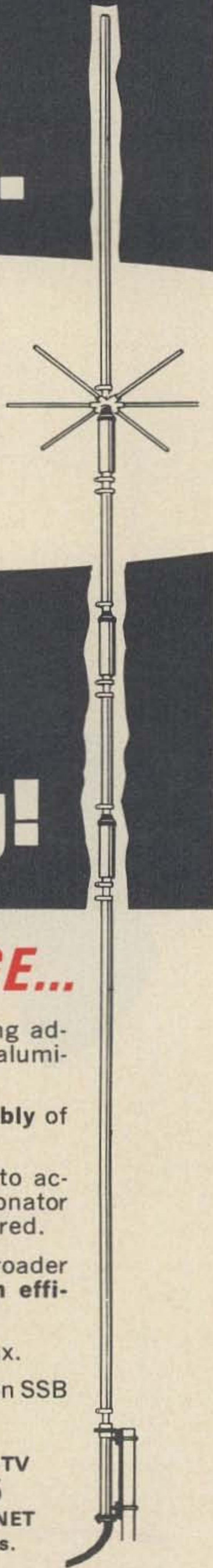

One Setting for TOTAL BAND COVERAGE...

- **Lowest SWR—PLUS!**
- Bandwidth at its **broadest!** SWR 1.6 to 1 or better at band edges.
- Hustler exclusive trap covers "**Spritz**" **extruded** to otherwise unattainable close tolerances assuring accurate and permanent trap resonance.
- Solid one inch **fiberglass trap forms** for optimum electrical and mechanical stability.
- Extra heavy duty aluminum mounting bracket with **low loss—high strength** insulators.
- All sections **1¼" heavy wall**, high strength aluminum. Length 21' 5".
- **Stainless steel clamps** permitting adjustment without damage to the aluminum tubing.
- Guaranteed to be **easiest assembly** of any multi-band vertical.
- Antenna has 3/8"-24 stud at top to accept RM-75 or RM-75S Hustler resonator for **75 meter operation** when desired.
- Top loading on 75 meters for broader bandwidth and **higher radiation efficiency!**
- Feed with **any length** 50 ohm coax.
- Power capability—**full legal limit** on SSB and CW.

Buy **HUSTLER** ... buy the verified
choice of thousands!

MODEL 4-BTV
\$49.95
AMATEUR NET
Wgt. 15 lbs.


*Available from all distributors
who recognize the best!*

NEW-TRONICS CORP.

15800 COMMERCE PARK DRIVE
BROOK PARK, OHIO 44142

World Wide Export, Roburn Agencies, Inc., 349 W. 14th St., New York, N.Y. 10014, Cable Address: Roburnage - New York

ments are not available, the monitor can be aligned with a simple one-transistor crystal oscillator signal generator kit that is furnished. This generator is very basically an up-converter and is a boot-strap operation in that it obtains its power from the receiver via an alligator clip, obtains an rf signal from the receiver i.o. tripler buffer with another clip, mixes this rf with its own 10.7 MHz oscillator output and feeds the resultant rf signal into the monitor's antenna jack. Using this method of alignment, with a high frequency and a low frequency pair of crystals installed for the desired scanning range of the receiver, was found to be entirely adequate for the type of reception normally expected.

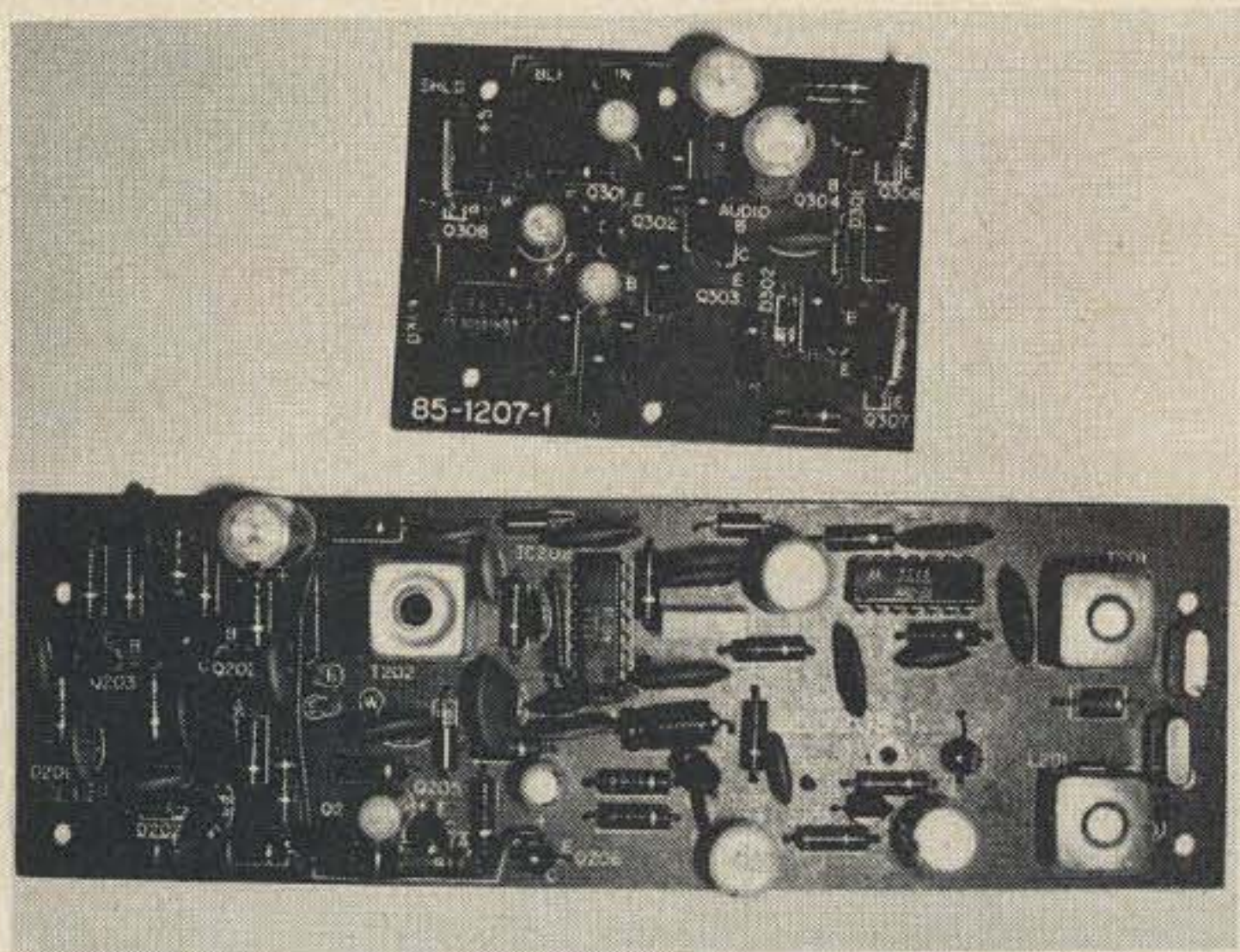

The audio (top) and i-f section (bottom) occupy separate pc boards.


Since completion, my GR-110 has been almost continually on, and it is somewhat satisfying knowing that I am not missing a thing that is happening around town.

Two modifications have been made to my unit already. First was the removal of the phono type antenna input jack and installation of a BNC type, which is more compatible with ham shack environs. Next, because I have on several occasions forgotten to turn off the squelched receiver prior to hitting the sack and consequently have been awakened by voices in the night, I installed a pilot light on the front panel.

Priced at \$119.95, Heath's GR-110 Scanning Monitor is a worthwhile addition to any ham shack...and will cause you to wonder how you got along without one.

...W3WTO

NOW GO PORTABLE WITH YOUR MOBILE UNIT! A self-contained rechargeable battery pack for amateur mobile systems which allows full portable operation. Automatic charging from automobile or fixed power sources during receive operation. Will operate an HR-2A for 4-5 hours of normal operation at full output power! 7 1/2" X 5 1/8" X 1 1/2", 12 VDC, 2.5 Amp Hour, 10 Amp Max current protection. Sealed lead-sulfide cells. High impact polymer case.

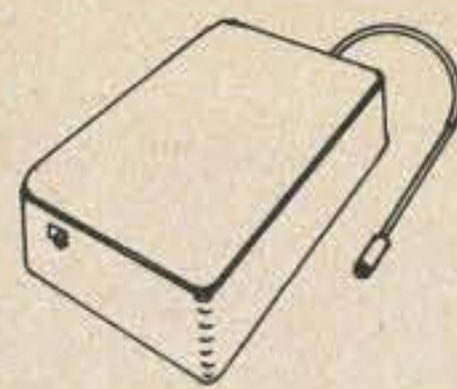

BP-1 39.95*
Shipping 1.00
*Oklahoma residents add 3% tax

DA Products
1208 Alan Lane
Midwest City, OK 73130

ECM-5 FM Modulation Meter

- Operates 30-500 Mhz
- Crystal controlled for fast and easy operation
- Peak reading
- Battery powered with AA pencils
- All solid state
- Built-in antenna
- Quality constructed with G-10 p.c. boards

Only \$75.00 less batteries and crystal



Phone or write "Skip" W9HAK for complete information
Dial 812-476-2121

Available by direct mail only. ORDER INFO: Send check or money order for \$75.00 plus \$1.00 for handling. Indiana residents add 4% sales tax. Crystals for 146.94 Mhz: \$3.95 ea. All other freqs: \$7.10

ECM

ECM Corporation
412 N. Weinbach Ave.
Evansville, Indiana 47711

from the Center of the Electronic World



VHF PRE-AMP
100 to 160 MHz
25 db gain
2.5 db noise figure
50 ohm input and output impedance
Price \$29.95



VHF CONVERTER
100 to 160 MHz
2.5 db noise figure
50 ohm input impedance
Better than .1 uv sensitivity
30 db gain
Price \$59.50



FREQ. PRESCALER
Up to 250 MHz
Available assembled, or kit form
Price \$96.50 assembled
\$69.50 kit

Q-TRONICS

310-B So. Meadow Lane
Golden Valley, Minn. 55416

SPACE-AGE TV CAMERA KITS & PLANS



BE A PIONEER IN HOME TELECASTING! Build your own TV CAMERA. Model XT-1A, Series D, \$116.95 pp. Solid-State. Step-by-step construction manual. High quality. Connects to any TV without modification. Ideal for hams, experimenters, education, industry, etc.

PHONE or WRITE for CATALOG.
DIAL 402-987-3771

Many other kits, parts and plans available including starter kits, focus/defl. coils, vidicon tubes, const. plans, etc.

1301 N. BROADWAY **ATV Research** DAKOTA CITY, NEBR. 68731

All types of Machines, Supplies & Gears

Send for New picture CATALOG

10¢

VAN'S
W2DLT
ELECTRONICS

fax too!

201-3636
302X Passaic Ave.
Stirling NJ 07080

TPL Communications offers the most complete line of RF power amplifiers for amateur and commercial applications available.

Two years and 4000 amplifiers have given TPL Communications the experience necessary to produce the finest VHF and UHF amplifiers made for the amateur and commercial market.

TPL presents rf power amplifiers for operation between 14 MHz and 512 MHz with power levels up to 120 Watts.

BUY DIRECT OR THROUGH ONE OF THE MANY TPL DISTRIBUTORS NATIONWIDE

TPL 14-30 MHz

FOR: SSB AM AND FM
14 to 30 MHz operation

60 Watts output AM
100 Watts output FM
120 Watts output SSB

ILLEGAL FOR CLASS D CITIZENS BAND

TPL 60 TO 120 WATT
POWER AMPLIFIER



ALL SOLID STATE, Absolutely no Tubes!!!

Part No: TPL 5010 and TPL 5010B [bi-linear]

TPL's "Battery Saver" series of amplifiers are designed to replace the bulky, high battery current TUBE AMPLIFIERS now in amateur and commercial service in the 14 to 30 MHz frequency range. TPL "Battery Saver" amplifiers are completely solid state, never require tuning, once adjusted, and can be operated for hours on an automobile battery without running it down. This is the perfect companion for commercial and amateur solid state transceivers in the 2 to 10 watt class. Power outputs of 100 watts and more are achieved with no more current than some tube amplifiers require for stand by current. This amplifier is truly a dollar per watt bargain, \$1.50 per watt of output to be exact, and a real battery saver.

Also available as accessories are a low noise receiver pre-amplifier utilizing a MOS FET transistor, an AC power supply, a control head that measures RF power output, DC voltage and turns the amplifier on and off remotely and a trunk mounting cable kit.

- FEATURES:** All Solid State, no tubes to ever replace or shake loose.
Low Stand-by current, typically 5 ma. (a comparable tube amplifier would require 5 to 10 amps)
Low transmit current, typically 12 amps. (a comparable tube amplifier would require 25 to 40 amps.)
Absolutely indestructible; immune to mismatch, over drive and over voltage.
Extremely compact:
No external cooling or ventilation required.
May be mounted anywhere; Trunk, under the seat, etc.
Many Accessories available; Trunk mounting cable kit, remote control/power output monitor, AC power supply and Bi-linear receiving amplifier with MOS-FET transistor.

talk
power
by

TPL

COMMUNICATIONS INC.

13125 YUKON AVENUE/HAWTHORNE, CALIF. 90250/(213) 679-0131

TPL has a COMPLETE line of RF Power Amplifiers for Six & Two meters and 450 MHz . . .

TPL 15 to 20W Amp. Give your handheld the punch it needs with as little as 50mw drive.



PA3 - 1AE/1AB (2 meters)

TPL 20 to 35W Amp. If your needs are 450, this is your amp. Up to 35 watts or more when driven by your mobile or handheld.



PA61 - AC2/BC2 (450)

TPL 80 to 120W+. If you want the ultimate in power & performance, look no farther. Turn your talkie or transceiver into a booming giant.



PA3 - 1EE/1AE/1DE (2 meters)

TPL REPEATER CONFIGURATION

If repeaters are your thing, TPL has the answer. Order any TPL amp in the repeater configuration. Designed to mount in standard 19" rack. Completely RF shielded with AC supply and forced air cooling.



talk
power
by

TPL

COMMUNICATIONS INC.

13125 YUKON AVENUE/HAWTHORNE, CALIF. 90250/(213) 679-0131

TPL IS 220




A brand new 220 MHz solid state FM transceiver. The 220 TR's power output is 10 watts. The receiver is double conversion with a tunable and crystal controlled receiver. FM is detected by a limiter discriminator featuring full noise saturation for weak signal reception. Sensitivity is typically .5 microvolts for 20 dB quieting. Variable tuning is accomplished in two bands, 220-222.5 MHz and 222.5-225 MHz. Its size . . . only 7"W x 2 3/8"H x 10 1/2"D.

TEMPO 220

Need extra mobile power? Here is the answer. Up to 100 watts or more on 220 for when you need that extra punch. Same high quality TPL construction and reliability.



MOBILE AMP

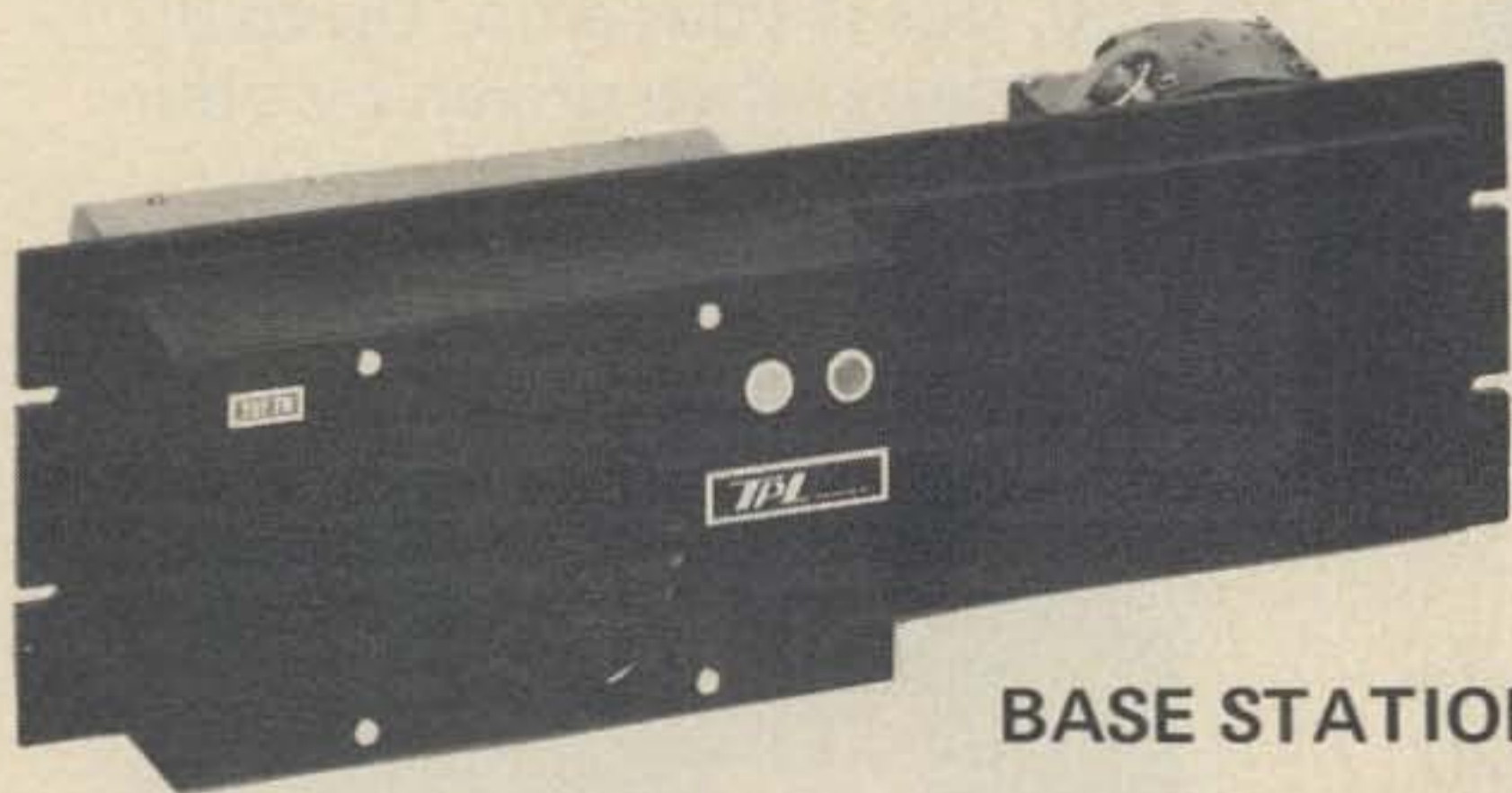

BASE STATION

Completely self-contained for home operation. Mounted in standard 19-inch rack with power supply and blower.

TPL NOW OPENS THE DOOR TO 220 OPERATION

Other great TPL products

PART NO.	INPUT POWER	OUTPUT POWER	FREQUENCY RANGE	PART NO.	INPUT POWER	OUTPUT POWER	FREQUENCY RANGE
PA3-1AE	50-250mw	15-25W	136-175MHz	PA3-1DD	5-15W	60-80W	136-175MHz
PA3-1AB	.75-3W	20-25W	"	PA3-1EE	50-250mw	80-120W	"
PA3-1EC	50-150mw	30-50W	"	PA3-1AE	.75-3W	80-120W	"
PA3-1AC	1-5W	35-50W	"	PA3-1DE	5-15W	80-120W	"
PA3-1DC	6-15W	30-55W	"	PA6-1DE	1-4W	20-30W	400-512MHz
PA3-1ED	50-250mw	60-80W	"	PA6-1AD	4-10W	25-35W	"

FCC type accepted for operation under parts 21, 81, 89, 91, 93, 95. Meets FCC specification: Part 5, subpart C, paragraph 5 103 (a).

Other products:

VHF FM 25-50 MHz Class C amplifiers

60W UHF FM Class C amplifiers

90W UHF FM Class C amplifiers

Wide band linear amplifiers in any frequency range on special order.

For complete specifications on any of the above units please write.

TPL amplifiers are for commercial applications. For non-commercial uses please contact your local Tempo dealer.

Dealer inquiries invited.

MANUFACTURED IN U.S.A.

talk
power
by

TPL

COMMUNICATIONS INC.

13125 YUKON AVENUE / HAWTHORNE, CALIF. 90250 / (213) 679-0131

12 VOLT SOLID STATE AMPLIFIERS FOR AMATEUR OPERATION

BAND	PART NUMBER	FREQUENCY	POWER IN	POWER OUT	AMATEUR NET PRICE
6M	TPL 1006	50-54MHz	10Watts	110Watts	\$185.00
6M*	TPL 2006	50-54MHz	10Watts	220Watts	\$270.00
2M	TPL 152	144-148MHz	1Watt	12Watts	\$ 59.00
2M	TPL 302	144-148MHz	1Watt	30Watts	\$ 93.00
2M	TPL 502B	144-148MHz	1Watt	50Watts	\$130.00
2M	TPL 802B	144-148MHz	1Watt	90Watts	\$195.00
2M	TPL 1202B	144-148MHz	1Watt	120Watts	\$239.00
2M	TPL 502	144-148MHz	10Watts	45Watts	\$113.00
2M	TPL 802	144-148MHz	10Watts	90Watts	\$191.00
2M	TPL 1202	144-148MHz	10Watts	120Watts	\$228.00
2M*	TPL 2002	144-148MHz	10Watts	200Watts	\$375.00
220MHz*	TPL 401	220-225MHz	10Watts	40Watts	\$118.00
220MHz*	TPL 901	220-225MHz	10Watts	90Watts	\$175.00
440MHz	TPL 300	420-450MHz	4Watts	25Watts	\$162.00
440MHz	TPL 300B	420-450MHz	1Watt	25Watts	\$190.00
440MHz	TPL 600	420-450MHz	4Watts	60Watts	\$245.00
440MHz	TPL 600B	420-450MHz	1Watt	60Watts	\$278.00
10M	TPL 5010	14-30MHz	100Watt FM 150Watt PEP SSB		\$169.80
80-10M*	TPL 2001	2-30MHz	400Watts PEP SSB		\$395.00

* Available Spring 1974

DEALERS! NOW CARRY THE BEST FROM TPL

Dealer/Distributor must agree to aggressively promote the sale of TPL products within the territory specified in the Dealer/Distributor Agreement.

• Dealer/Distributor is expected to follow up on sales leads supplied by TPL.

• Submission of advertising and catalog copy must be made for factory approval whenever the TPL logo or trademarks are utilized.

• Point of sales material is expected to be prominently displayed.

• The Dealer/Distributor is expected to coordinate advertising with TPL's national program.

WARRANTY AND SERVICE POLICIES

• **WARRANTY** – TPL COMMUNICATIONS, INC. warrants each instrument manufactured by them to be free from defects in material and workmanship. Our liability under this warranty is limited to servicing or adjusting any instrument which is returned to the factory for that purpose and to replacing any defective parts thereof. *This warranty on all parts and labor is effective for 180 days after delivery to the original purchaser on amateur and commercial products, provided that all instructions as to installation, use and operation are followed and the fault has not been caused by misuse, accidents, negligence, alteration, unauthorized repairs and the equipment has not been damaged by excessive input power, lightning, water flooding or freight damage.*

• **SERVICE POLICY** – If it is necessary to return any in-warranty equipment to the factory, return authorization should be obtained. If at all possible, *DO NOT return units without prior factory authorization.* This often permits solving problems without the necessity for return.

• **WARRANTY REGISTRATION** – TPL COMMUNICATIONS, INC., is under no obligation to extend the above warranty to any unit for which a Warranty Registration card has not been completed and mailed to the Corporation within ten days (10) after date of delivery. Warranty is extended to the *ORIGINAL* purchaser only!

• **ORDERING INFORMATION** – The following information will allow us to fill your order with maximum speed and efficiency. 1-Operating frequency \pm 1MHz. 2-Power input \pm 25%.

FOR COMPLETE INFORMATION CALL TPL NOW!

NEW!!!



"Cloverleaf"

SBE-450TRC TRANSCONVERTER

instant access to 450 from 144

Now . . . SBE opens up a new high speed route that leads to instant 450MHz operation from any 2 meter transceiver! Rev up—switch in the exclusive SBE, SB-450TRC "Cloverleaf"—arrive instantly on 450! Return at will!

Installation couldn't be more simple. Outwardly, "Cloverleaf" is a small black box that connects between your existing 144 MHz FM transceiver and its antenna, also to the microphone and car 12 volt battery. You plug the 450MHz antenna into another receptacle provided. SB-450TRC has no external tuning, no controls other than a switch that allows instant shift between the 144 and 450MHz ranges. No mods are necessary. **Your existing 144MHz transceiver remains intact.**

Transmitter-wise, SBE "Cloverleaf" is entirely **passive**—draws no DC power yet delivers 40% of the RF drive at three times the frequency. Example: 4 watts out on 450 MHz for 10 watts drive on 2 meters. This high efficiency frequency multiplication is accomplished by a power varactor diode in conjunction with multiple high Q tuned circuits. The 450MHz output is of course frequency modulated; overswing, due to fre-

quency multiplication, being compensated by a fixed pad in the microphone circuit within the unit.

Receiver-wise, "Cloverleaf" has a front end with unity conversion gain that converts 450MHz band signals to I-F frequencies corresponding to 144MHz channels. Limiter, discriminator, output audio and loud speaker in the 2 meter transceiver continue to function in the usual manner.

Mobile wise, this all-solid-state transceiver is ideal—a compact box that can mount wherever space is available. "Cloverleaf" current drain is negligible.

Price-wise, this SBE high value/performance breakthrough represents worthwhile savings over the cost of a complete 450MHz transceiver with comparable characteristics. Truly, SBE has done it again!

SBE



Unit with covers removed

LINEAR SYSTEMS, INC. 220 Airport Boulevard, Watsonville, Calif. 95076

AUTOPATCH INTERCONNECTION THE LEGAL WAY

Keep Ma Bell happy.

If you are presently operating an autopatch system or are planning to put an autopatch system on the air, it is felt this information will be of interest to you.

Voice communications equipment provided by you, the amateur and telephone company customer, may be electrically connected to the facilities of the telephone company system *only* through a voice connecting arrangement that is furnished, installed and maintained by the telephone company. This is described in state and interstate tariff regulations. In some states it is a criminal offense to make a direct connection to telephone company lines.

Today the equipment is available for just about any type of interconnection you might have need for. The big problem is communicating your needs to the telephone company marketing personnel. Most telephone company marketing personnel are not technically minded and do not understand what you, the customer and subscriber, might have in mind.

It is felt that the interconnecting devices described here are the best suited for autopatch operation. Which one you choose is determined by your particular needs. The C2A system is now being used with very satisfactory results and this information seems worth passing on.

These devices are known as Voice Connecting Arrangements C2A and SU6AQ. Technical references covering these arrangements are available from the American Telephone and Telegraph Company¹ as a guide for designers, manufacturers, and consultants of customer provided systems and

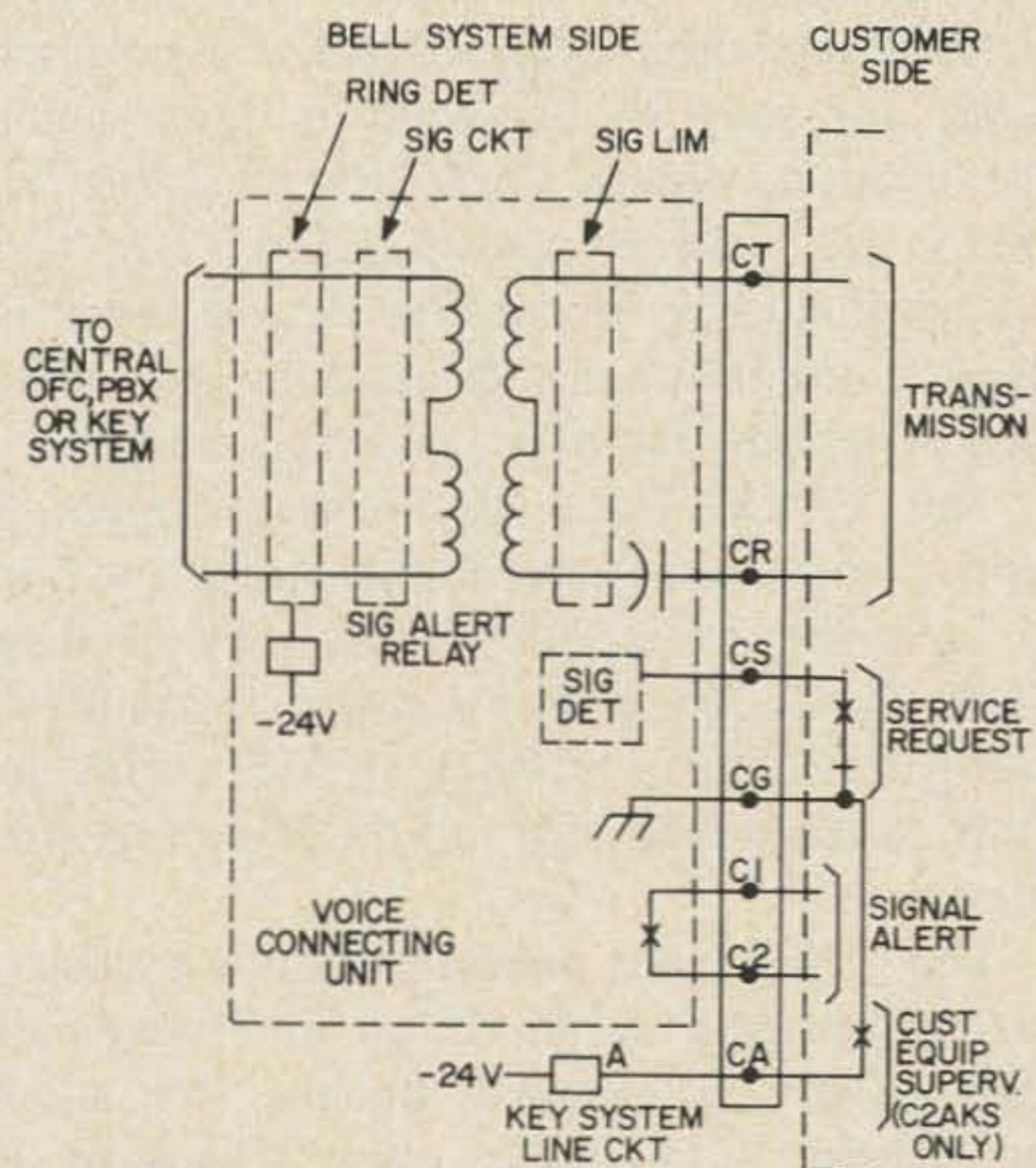


Fig. 1. Simplified schematic, voice connecting arrangements C2ACP and C2AKS.

equipment which connects with Bell System communication systems.

Voice connecting arrangement C2A provides a bridged connection to a line terminated at a telephone company telephone set, typically for use with customer provided call extending equipment. The unit is an 8 in. printed board installed by the telephone company in a 23 in. relay rack or cabinet mounting. A 24V dc power supply is required and is provided by the telephone company. A non-switched, grounded, ac outlet providing 117V ac $\pm 12V$, 60 Hz, fused at 15A must be available at the installation location. The temperature range of the unit is 0° to 55° C, with a humidity range of 5 to 95%.

The voice connecting arrangement C2A provides at the interface connecting block the following leads with associated functions for the customer's use:

- CT Two way voice transmsion
- CR and tone signaling
- CS Service request, answer/disconnect,
- CG and dc dialing pulses
- C1 Incoming ring
- C2 signaling

The CT-CR leads provide a two-way audio patch between the telephone line and the customer's equipment. Duplex operation may be used. This includes any TOUCH TONE® signaling. This circuit is a nominal 600 Ω and may be balanced or unbalanced. The insertion loss is 1 dB, 300 to 3000 Hz. There are several specifications for this circuit including maximum power level in dBm, audio frequency limitations and when used tone signaling levels and frequencies.

The CS-CG leads are normally open. A short of no more than 18 Ω provides a means of answering an incoming call, and initiating a call. Dc dialing pulses are also transmitted over these leads. Further specifications include voltage and current on leads and dial pulse rate.

The C1-C2 leads provide a contact closure during the ring cycle of an incoming call. The closure is opened during the silent interval and is normally open. The load on these leads may not exceed 250 mA non-inductive.

Voice connecting arrangement SU6AQ

and STS provides a means for automatically connecting customer provided equipment, capable of originating and/or receiving calls, such as alarm systems, to the telephone network. An associated telephone company provided telephone set may be used to

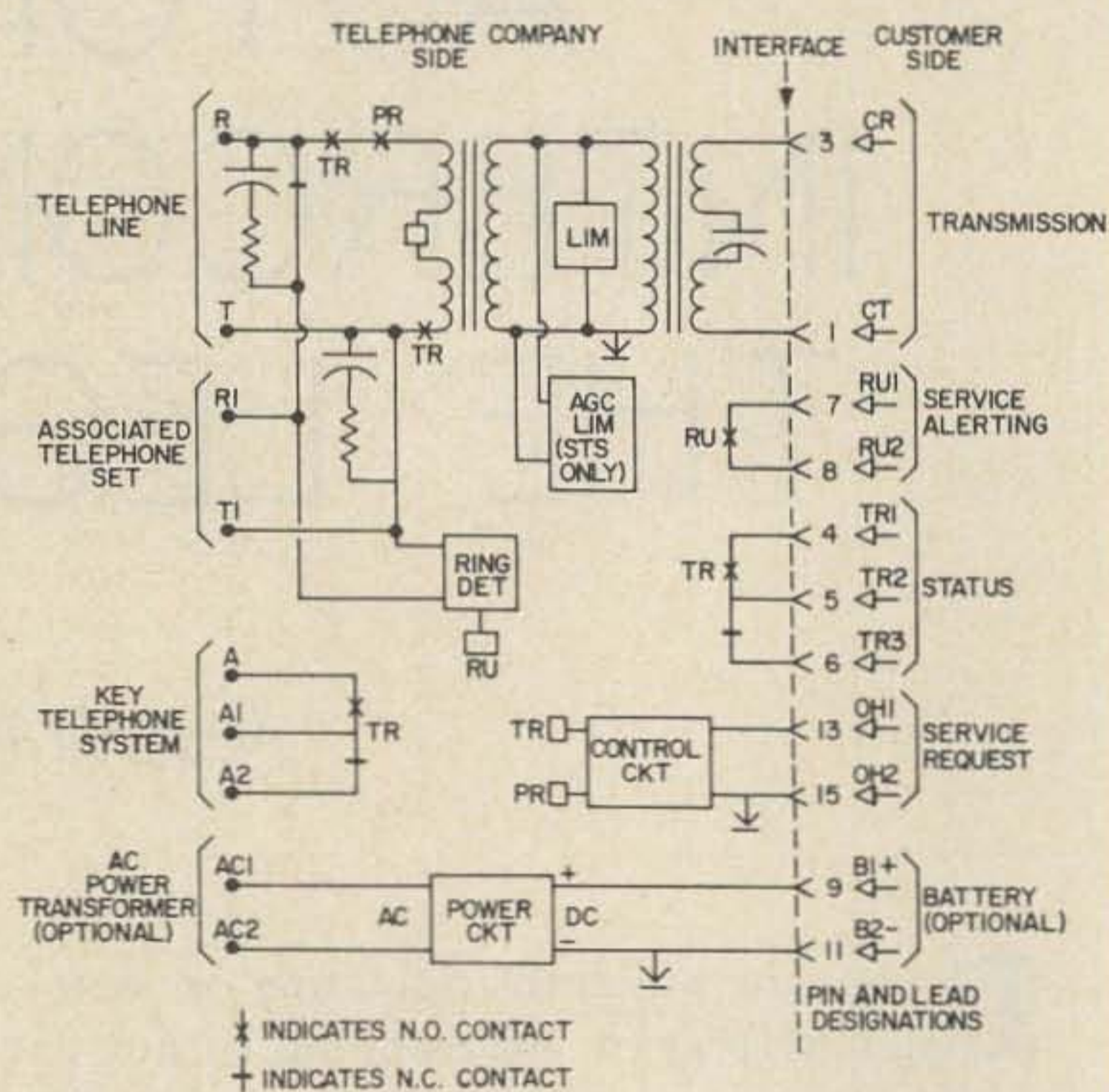


Fig. 2. Simplified schematic, voice connecting arrangements SU6AQ and STS.

provide normal telephone service. Arrangement STS has all features of the SU6AQ and, in addition, permits the customer provided equipment to transmit answer back tones to the distant party through an agc system which assures compliance with network protection criteria (audio level).

The arrangements consist of a printed circuit board housed in an apparatus box approximately 9 in. square and 3 in. deep, intended for wall or shelf mounting. Connection to customer provided equipment is made by means of a 15 pin female receptacle provided at the bottom of the arrangements. The customer must provide the mating plug (Cinch No.231-15-61-133 with hood No.239-13-99-069). These arrangements will operate from a customer provided battery (18V @ 150-500 MaH) or from a 177V ac, 60 Hz, current regulated transformer supplied by the telephone company. For emergency power the battery may be floated across leads B1+ and B2-. A charging current of 2.5 mA is available while the unit is being operated on ac.

The voice connecting arrangements SU6AQ and STS provide on the customer provided cable leads the following:

- CR Two way voice transmission
- CT and tone signaling
- RU1 Incoming ring
- RU2 signaling
- TR1
- TR2 Status
- TR3
- B1+
- B2- Battery

The CT-CR leads provide a two way audio path between the telephone line and the customer provided equipment. This includes TOUCH TONE® signaling. In addition, with arrangement STS these leads may be used to transmit and receive supervisory tones from the distant party. The insertion loss is 3 dB at 250 Hz and 1 dB over 300 to 3000 Hz. No voice signal amplification is

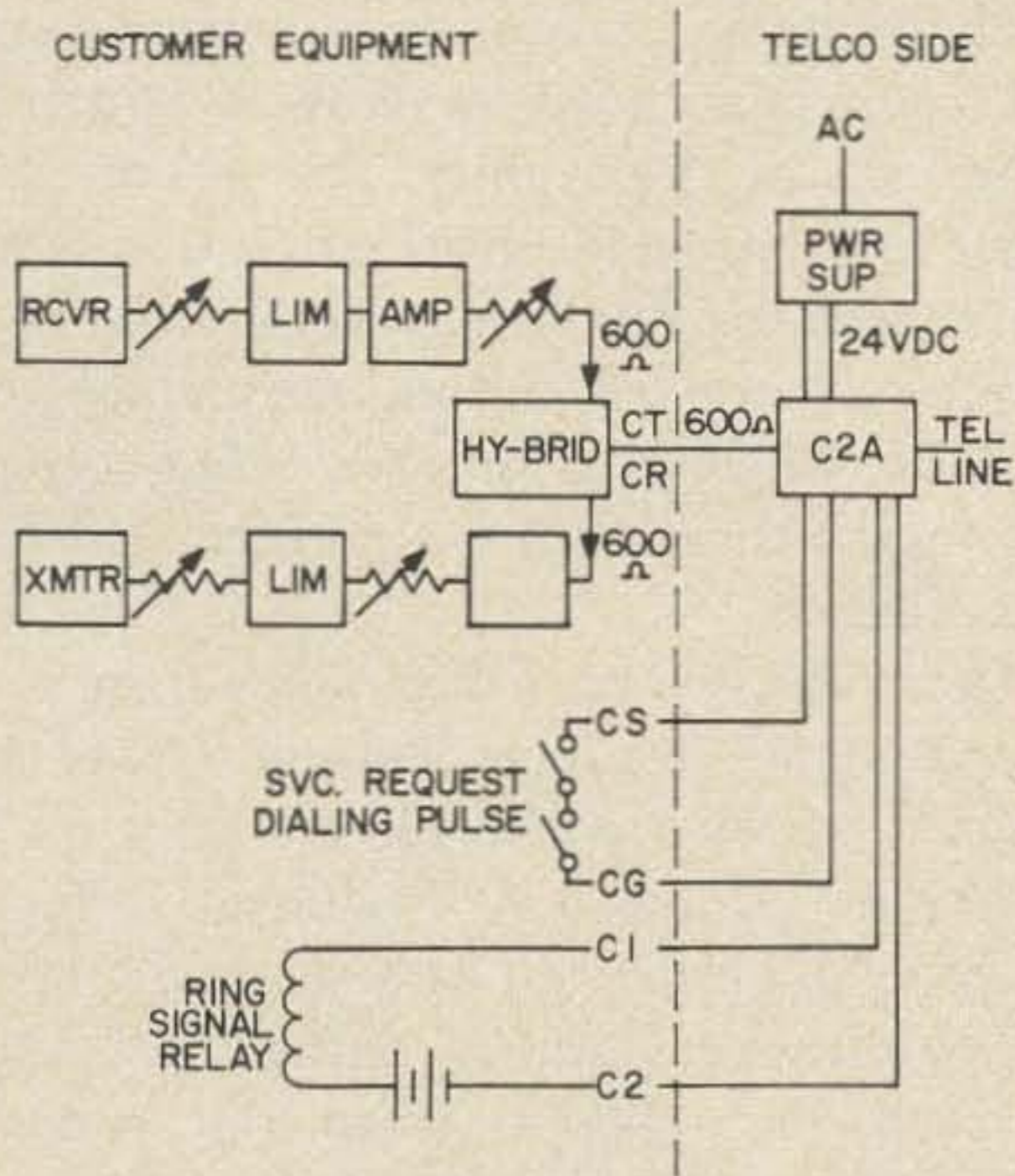


Fig. 3. Typical autopatch arrangement.

provided. For design purposes the impedance should be considered to be 600Ω. There are several specifications for this circuit, including maximum power level in dBm, audio frequency limitations and when used tone signaling levels and frequencies. The agc limiter incorporated in the transmission path of arrangement STS is to protect the telephone network from application of abnormally high tone signals. It has no effect on normal speech levels.

Leads TR1-TR2-TR3 provide isolated


WANT TO MEET SOME OLD-TIMERS ?

NEW VINTAGE RADIO BOOK

Re-live the early days of wireless and radio. Over 1,000 pictures. 1887-1929.

RADIO COLLECTOR'S GUIDE

Over 50,000 useful facts. 1921-1932

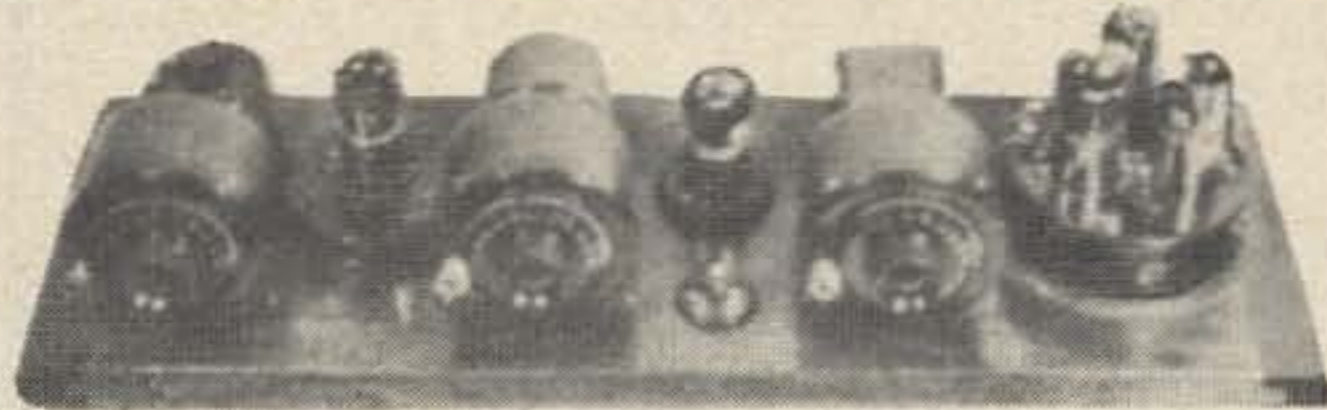

ORDER NOW! Send check to
McMahon's Vintage Radio, Box 2045,
Palos Verdes Peninsula, Calif., 90274

- Vintage Radio, hard cover \$6.95
- Vintage Radio, handbook 4.95
- Radio Collector's Guide 3.95

California residents add 6% State Sales Tax

Name _____

Street _____

City _____ State _____ Zip _____

THE IDEAL HOLIDAY GIFT!

When you want an authoritative, up to date, complete reference
It's the CALLBOOK



Over 285,000 QTH's
in the U.S. edition
U.S. CALLBOOK for 1973
(less service editions)
\$8.95



Over 180,000 QTH's
in the DX edition
DX CALLBOOK for 1973
(less service editions)
\$6.95

See your favorite dealer or Send today to
(Mail orders add 50¢ per CALLBOOK
for postage and handling)

WRITE FOR
FREE
BROCHURE



RADIO AMATEUR
callbook INC.

Dept. B 925 Sherwood Drive
Lake Bluff, Ill. 60044

MINIATURE METER0 100 μ A (approx.) - 1/2" dia. \$1.00**MINIATURE POWER SUPPLY**

Output 6Vdc - 100 Mils. \$1.00

5 Volt ZENER and Electrolytic for 5 Volt supply furnished for \$1.00 additional.

REED RELAYS

6 Vdc - SPST - 1/4 x 1" \$1.25

12 Vdc - SPST - 1/4 x 1/2" \$1.50

FULL WAVE SILICON BRIDGE RECTIFIER

200 PRV (line) 25 Amps - 1"sq. \$2.50

OIL CAPACITORS

4 MFD - 3KVdc G.E. 23F44

4 x 5 x 4 - 7 lbs. ea. 2 for \$10.00

100 MFD - 1500 Vdc - Sprague F1537

Use 2 in series for 50 MFD 3KV

13 x 6 x 5 25 lbs. ea. 2 for \$25.00

POWER SUPPLY

Input 115V/1/60 Output 28 Vdc 50 Amps filtered

Silicon studs - Cased transformer and choke

21 x 12 x 7 - 150 lbs. \$90.00

BIRD -8135 - 150 WATT - 50 OHM

Load - Brand new \$40.00

HP 212A PULSE GENERATOR. OK. \$35.00**G.R. VARIAC - W5HBB 0-240 VAL**

2.0A (500 Watts) New, boxed \$15.00

**OMNIBUS***Electronic Industries, Inc.*

383 CANAL STREET NEW YORK, NY 10013

(212) 226-3893

16 BROOKLYN AVENUE FREEPORT, L.I., NY



AT LAST! A service manual covering the Model CX7 and CX7A has been printed and is ready for delivery.

This informative manual includes the "A" modifications and late production changes. It also includes information to improve cross modulation, sensitivity, AGC action and transient suppression, plus other information such as phone patch hook-up, identification of accessory connection points and a simplified tune-up procedure. The manual is quality offset printed with a durable cover and comb-bound.

Order by mailing \$25.00 check or money order plus postage and handling (Midwest and Eastern states, \$2.00; Western states, \$1.50). Calif. add 6%.

PUBLISHED BY

THOMAS ADVERTISING CO.

715 Silver Spur Road, Suite 210
Rolling Hills Estates, California 90274
(213) 377-7284



ALSO - MANUALS FOR
STANDARD COMMUNICATIONS
SR-C806 AND SR-C826

contacts to the customer provided equipment to indicate the status of the connecting arrangement. During line seizure, leads TR1-TR2 are shorted and leads TR2-TR3 are open. When disconnected from the line, leads TR1-TR2 are open and leads TR2-TR3 are shorted.

Leads B1+ and B2- provide for a connection to a customer provided dc power source for operating the arrangements. The telephone company may, at the customer's option, provide a power source for the connecting arrangement. The customer must specify which power source is to be used.

Arrangements SU6AQ and STS are normally isolated from ground and therefore customer provided signaling and power supply connections must be isolated from ground. No mention is made about grounding for arrangement C2A except that it is expected that the customer provided equipment will be grounded.

There are several additional specifications which you may need to know if you decide to use one of these units. The intent of this article is to provide information about what is available for interconnection between the telephone network and an autopatch so the amateur will have an idea what type of equipment to ask for to perform the functions desired.

There are several other Voice Connecting Arrangements available, each intended for a specific purpose and available only on certain types of lines. A Technical Reference Catalog which lists all arrangements, respective publication number, and a brief resume on each, is available from the American Telephone and Telegraph Company¹

The cost of the mentioned arrangements is about \$7 per month (varies with the area) and is well worth the investment, mainly - no more worry about what the telephone repairman might find if he unexpectedly visited your shack or transmitter location.

...W3YVV

Publication #40000, Technical Reference Catalog (free). Publication #42207, Arrangement C2A (\$1.50 ea.). Publication #42210, Arrangement SU6AQ/STS (\$1.50 ea.). Available from: American Telephone and Telegraph Co., Supervisor Information Distribution Center, 195 Broadway, Room 208, New York NY 10007.

FREQUENCY APERTURE MODULATION

Phase II

Being a radio amateur for over forty years has been a pleasure and I have seen many developments in the art. Much of my operating has been on the phone frequencies and my first love was AM on the old 80 meter band. AM is gradually disappearing and one rarely hears an AM station on the low frequencies. SSB has made a big hit as it permits voice communication in a much smaller segment of frequencies. It is ideal in this respect, but to an old AM lover it still doesn't seem to be best. FM is terrific but here again we end up taking twice as much space in the spectrum for voice transmission. Let's keep trying for a better system! My attempt is FAM or Frequency Aperture Modulation described below.

Before going directly into FAM it is most important to understand FM. A pure un-

modulated carrier can be considered as having no bandwidth in the radio spectrum, yet it can be detected. Knowing that it is there, we can turn it on and off with a key and transmit code. This causes the radio frequency to evidence some bandwidth. If a receiver is very selective one can isolate the frequency quite well and receive the code. One way of looking at a carrier in the radio spectrum is the same as looking at the edge of a disc spinning in space. In Fig. 1a the disc looks like a very fine line. It is very difficult to see, like Saturn's ring when viewed edgewise. If we cause disc to wobble on its axis as in Fig. 1b, we can see it far better. We can compare this with AM Modulation. Now if we were to make the disc not only wobble on its axis but also cause the hub of the axis to move as in Fig. 1c we could say this is FM. (Bw represents band-

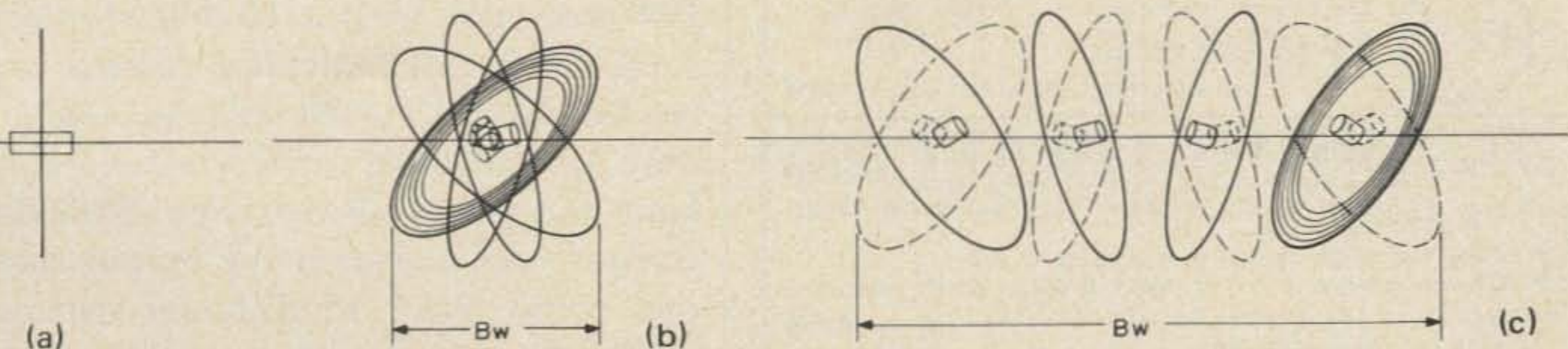


Fig. 1. W2BSP's disc analogy to describe modulation.

Outperforms ALL OTHERS!

NOW

Bomar Dealers have ample stock for all popular 2-meter transceivers and scanners plus certificates for special crystal needs.

WRITE FOR NAME OF NEAREST DEALER



BOMAR CRYSTALS

the "long playing" crystals

BOMAR CRYSTAL COMPANY

201 Blackford Ave., Middlesex, N. J. 08846
Phone (201) 356-7787

YAESU

Newly appointed dealer for the East Coast is now taking orders on Yaesu equipment. Send for literature and free list of used equipment available.

FRECK RADIO & SUPPLY CO.

40 Biltmore Avenue

P.O. Box 7287

Asheville, North Carolina, 28807

Telephone: 704-254-9551, W4WL

Isolated - Pad - Drill - Mill

Precision circuit board construction without etching. Fits hand drill, electric drill. Simple, fast, economical, safe.
Sizes: .20, .15, .10 inch dia.
With replaceable #60 drill.


\$6.95 ea.

Calif. residents add 5%.



A F STAHLER Co

P.O. BOX 354 CUPERTINO, CALIF 95014

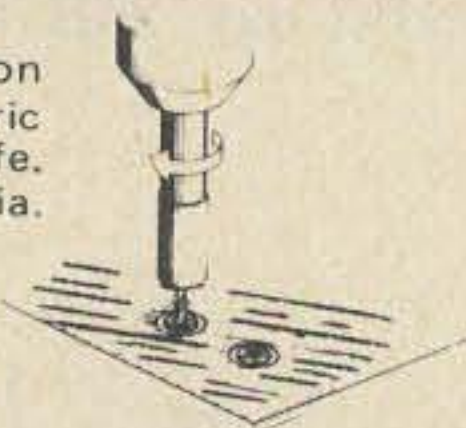

QRPP THE MILLIWATT QRPP

All about under-five watt amateur radio

If you've been wanting to try QRPP, then The Milliwatt is a MUST for you!!!

- Construction Projects
- Technical Articles
- Operating News
- WAS & QRPP DXCC Standings

RATES: \$3.40 yearly. Reprints: Vol. I—\$4.00; II & III—\$3.50 each (all three—\$10.00).

Sample 25¢

SUBSCRIPTIONS to: ADE WEISS K8EEG/8

213 Forest, Vermillion, SD 57069

width.) Note that the hub of the disc in the case of AM does not move and that in FM it does. This hub can be considered as the fundamental frequency of an oscillator. In AM we try to keep it in one spot of the radio spectrum. In FM we purposely move it and this motion is known as deviation. One of the first arrangements for generating FM was to use a condenser type microphone in an oscillator circuit so that the oscillator frequency was varied at voice frequencies. Deviation is a measurement of how far the frequency, or hub in this case, is moved up and down in frequency. In Fig. 1c, the movement in frequency would correspond to moving the hub from left to right and vice versa. An example would be to use a one cycle per second modulating signal and deviating the hub $\pm 75,000$ Hz in the radio spectrum, or a 1,000 Hz signal and deviating the same $\pm 75,000$ Hz. In narrow band FM the deviation is small and in FM broadcasting the deviation is very large.

When one frequency modulates a radio wave several things happen. If one modulates an FM broadcast carrier with a 1,000 Hz tone and watches the spectrum that is generated with a receiver that has a 500 Hz selectivity one finds individual radio frequencies every 1,000 Hz. They will vary in strength, but as many as 150 carriers can be detected if the deviation is a full ± 75 kHz. All these radio frequencies, commonly called carriers, are generated by the movement of the radio frequencies beating against themselves as the fundamental frequency is swept up and down the radio spectrum. Each audio frequency takes on the same configuration and one finds that when voice or music modulate the carriers a very complex conglomeration of frequencies is generated. If one were to modulate the above mentioned FM broadcast with a 10,000 Hz signal, the total number of individual carriers would be spaced 10 kHz apart and we could detect only 15 individual carriers, assuming that we keep the deviation the same. With these 15 carriers and a system for modulating each, one could make 15 different narrow band FM stations. Stereo broadcasting is done in somewhat the same way.

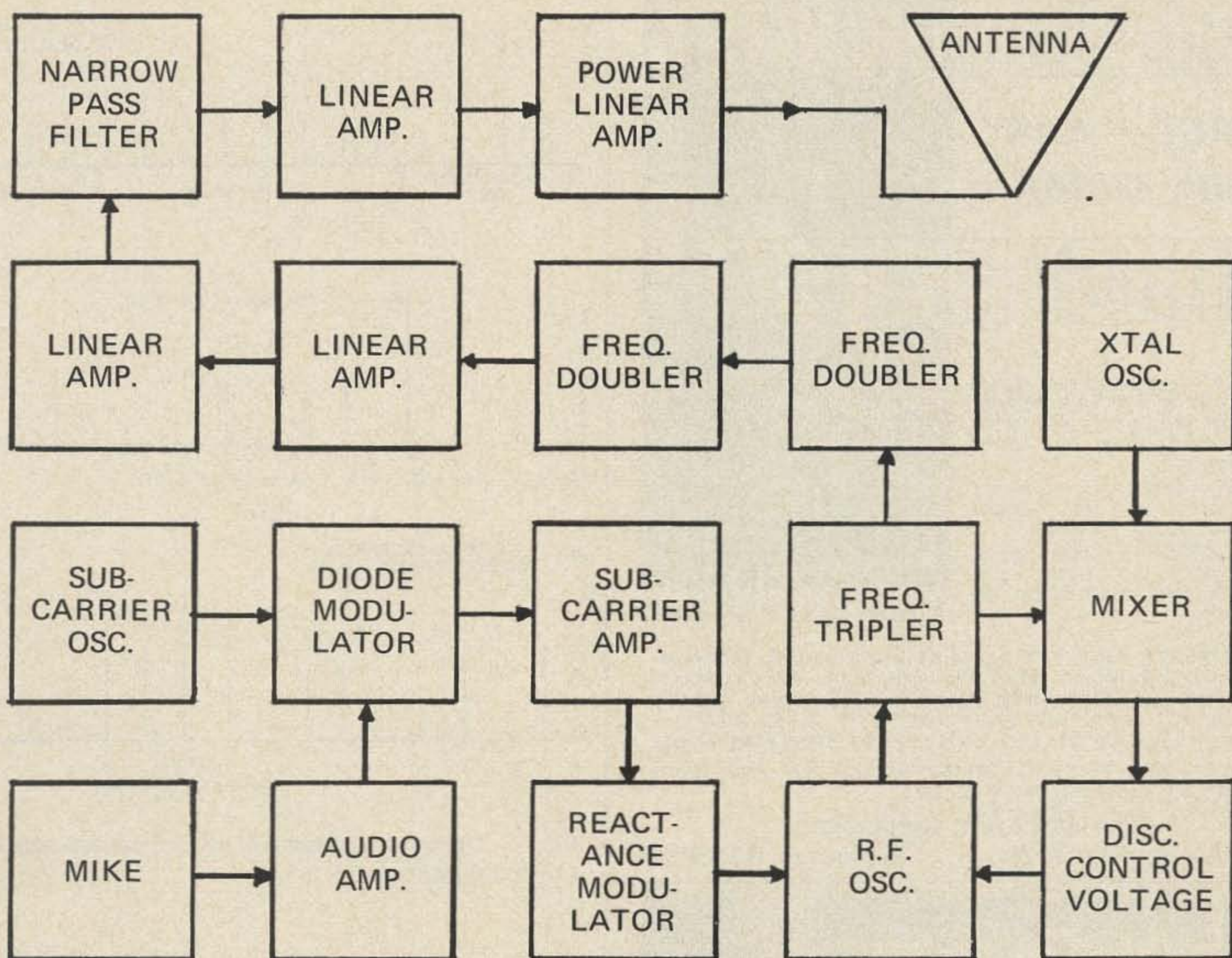


Fig. 2. Frequency Aperture Modulation system.

To move now from FM and into Frequency Aperture Modulation, we know that the normal voice takes about three to four thousand Hz for good understanding. This means that the space in the radio spectrum required for voice will be the same and we have made good radio receivers that can vary a slot or aperture to that extent. Now that we can receive a 3 to 4 kHz signal let us experiment a little. Take two carriers spaced 1,000 Hz apart in the radio spectrum and tune the receiver so that those carriers fall within the receiver's bandwidth. One will detect a beat in the speaker as an audio tone of 1,000 Hz. If one separates the carriers to 3 kHz one gets a 3 kHz tone in the receiver. When one separates the carriers to 5 kHz nothing is heard as the bandwidth of the receiver cannot pass 5 kHz. If the receiver is tuned to one side of a wide-band FM station modulated by 1,000 Hz the effect is similar.

If the FM broadcast station is modulated by a 5 kHz tone nothing can be heard. Note that when the FM broadcast station is not modulated no energy ever gets into the receiver because the carrier is off-side. The principle of Frequency Aperture Modulation is derived from this phenomenon.

The object in the FAM system is to generate a frequency modulated spectrum that contains all the voice information in a 3.5 to 4 kHz slot. The generation of a spectrum for FM broadcasting with good linearity requires a frequency modulated low frequency oscillator with its output multiplied till one gets the deviation required. In FM broadcasting large and small deviations are received because the FM receiver has a wide receiving bandwidth. A low amplitude signal that deviates say ± 5 kHz is received as well as a high amplitude signal with a ± 75 kHz swing and one sees that excellent

PRINTED CIRCUITS

FAST — EASY
with DATAK's

DIRECT ETCH SET

EASY—patterns rub down directly on the copper board and connect with rub-down lines or tapes supplied.

FAST—safe new etchants will etch a 2 oz. copper board in 30 minutes.

ACCURATE— $\pm .002$ " print tolerance so parts and connectors mate with no errors.




Circuit Made With ER-1

COMPLETE ER-1 SET contains hundreds of dry transfer DIP, flatpack, TO-5, IC, and transistor patterns; $\frac{1}{16}$ " and $\frac{1}{32}$ " etch resist tapes; 4 copper clad boards; $\frac{1}{4}$ lb. dry etch; tray and instructions. \$4.95 ppd.

IN STOCK AT ALLIED AND OTHER DISTRIBUTORS
WRITE FOR FREE CATALOG listing this and many other dry transfer marking sets.

The **DATAK** Corporation

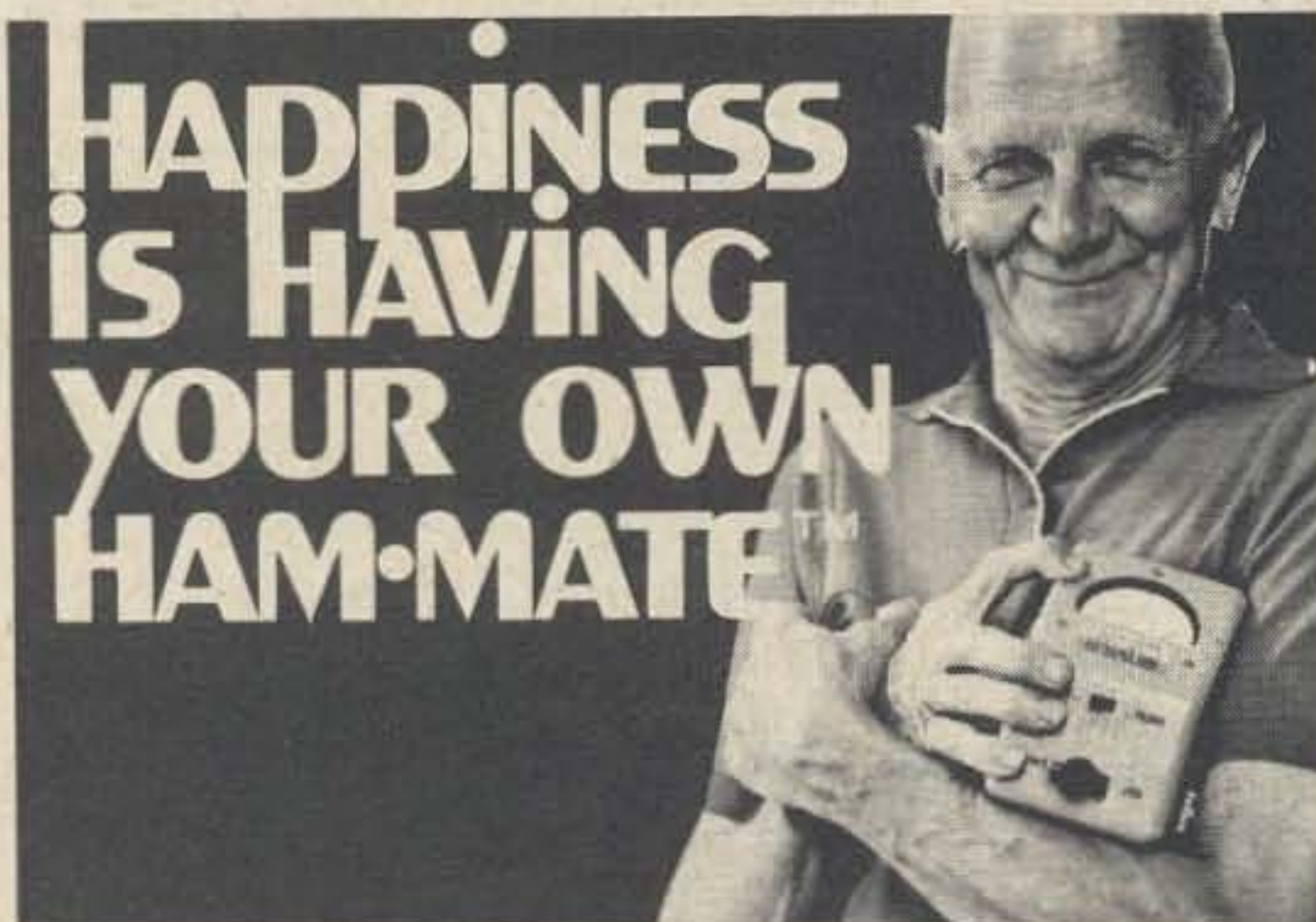65 Seventy-First Street • Guttenberg, NJ 07093



The New HAM-MATE™ Directional RF Wattmeter is a direct descendant of the famous model 43 THRULINE® — the professional standard of the industry. Designed specifically for the serious radio amateur, three models currently available measure forward and reflected power in the following ranges:

- 4350: 2000/200W, 1.8-30MHz (160 meters to 10 meters)
- 4351: 1000/200W, 1.8-30MHz (160 meters to 10 meters)
- 4352: 400/40W, 50-150MHz (6 meters, 2 meters)

All have an Insertion VSWR below 1.1 in 50-52 ohm lines, a minimum of 20dB Directivity, 8% Accuracy, S0-239 female UHF connectors and carry the 12 months guarantee of all Bird instruments.

ONLY \$79 (plus \$1 shipping)

Also available at Henry Radio, Hamtronics, etc.



BIRD ELECTRONIC CORPORATION

30303 AURORA RD. • CLEVELAND (SOLON) OHIO 44139
Phone 216-248-1200 • Cable BIRDELEC

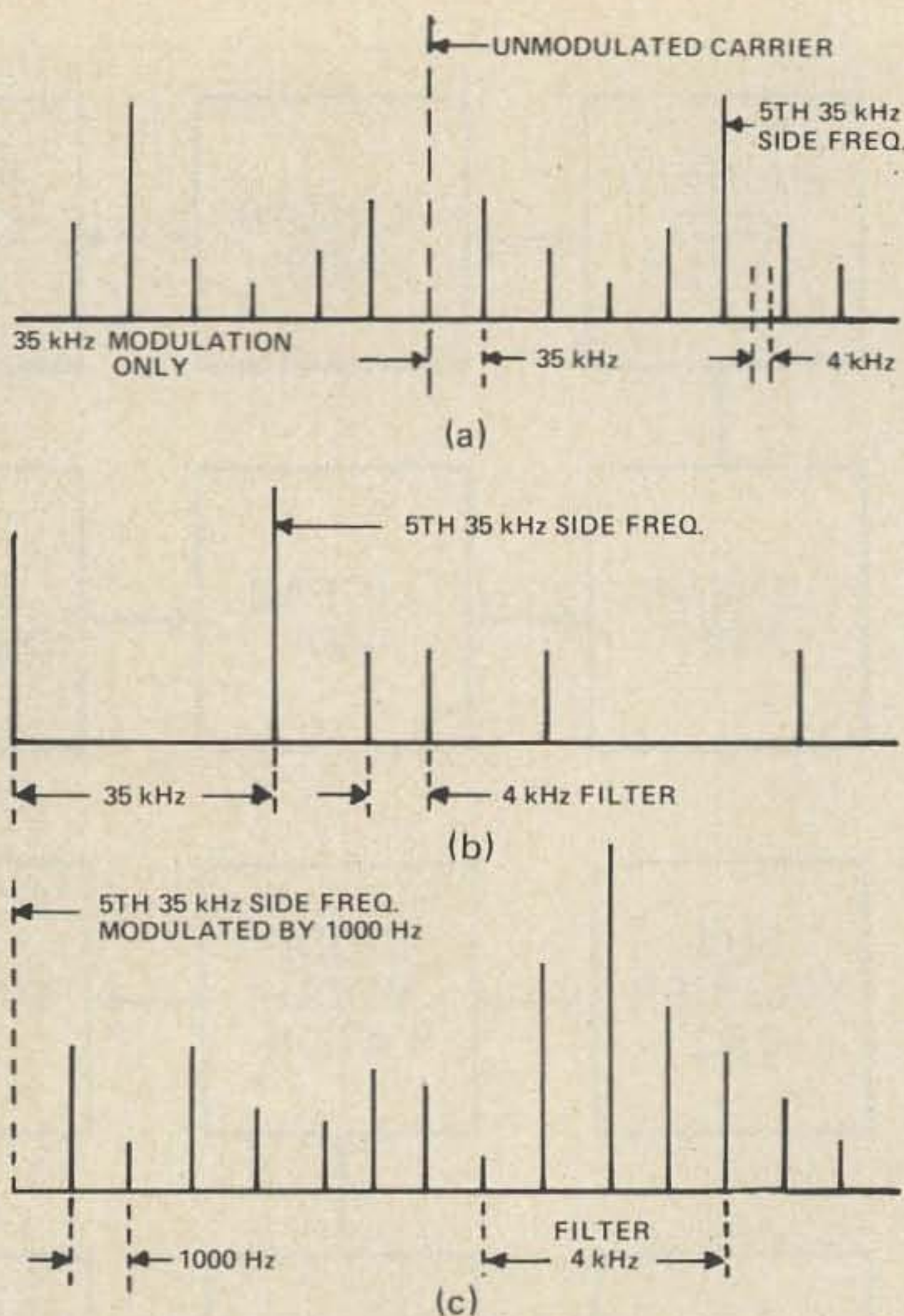


Fig. 3. Spectrum generated by sub-carrier amplitude modulation.

fidelity up to 10 or 15 kHz is possible. If one places the selective receiver to one side of the unmodulated FM broadcast carrier, say about 10 kHz higher, and then deviates the carrier ± 5 kHz with a 1,000 Hz audio tone no audio is received: If one increases the deviation more than ± 10 kHz the audio tone gets into the receiver. The Bessel-function analysis shows that as we vary the deviation or amplitude of the audio more or less signal will get into the selective receiver. Compressing the audio so that its amplitude varies less, and keeping the level constant, will help in getting more of the signal into the narrow band receiver. Clipping of the audio will also contribute to keeping the deviation constant.


Experiments show that the above mentioned control of the deviation by compression and clipping is insufficient to get fair quality signals in a narrow frequency range and it was decided to add a sub-carrier to the modulation. The sub-carrier amplitude modulated makes a spectrum that can be adjusted like a fine control. Most any

frequency above the audio range and not too high in frequency will work. A frequency of 35 kHz was chosen because available parts on hand dictated this frequency. The spectrum generated is shown in Fig. 3a, b and c. The doubling, tripling, and final stages when tuned to the upper side frequencies peaked at the upper 5th side frequency. This meant that frequencies 175 kHz away from the unmodulated carrier were amplified and used. The amplitude of the 35 kHz was adjusted so that it peaked at the 5th upper side frequency. To facilitate the tests two high Q resonant cavities made of two 55 gallon drums were constructed and were made to tune in the 30 MHz amateur band. They were hooked in tandem to give a band pass of less than 35 kHz. Considerable rejection of the unwanted frequencies was obtained and it was also discovered that some ac hum modulation was giving erroneous readings. The filter was adjusted so that its aperture was between the 5th and 6th upper side 35 kHz sub-carrier frequencies as shown in Fig. 3a, 3b and 3c. All the equipment before the filter operated at low level and shielding minimized spurious radiations. A power amplifier using three stages at the filter frequency was used to amplify the output and it was possible to get about ten to fifteen watts into a dummy load. A very good modulation of voice frequencies was monitored some distance from the dummy load using a long coax line as an attenuator. Accuracy of measurements was limited due to lack of additional test equipment but the results were very convincing. With a few refinements of the equipment an excellent FAM system can be built.

Here is a system that suppresses the carrier and has all the capabilities of SSB. The interference between stations is minimal, as one is able to understand the two stations the same as two people talking at the same time even when slightly off frequency with each other. The output of the filter can be heterodyned with an oscillator making lower frequency operation possible. No on-the-air tests have been conducted due to the fact that the FCC has not yet given its approval.

...W2BSP

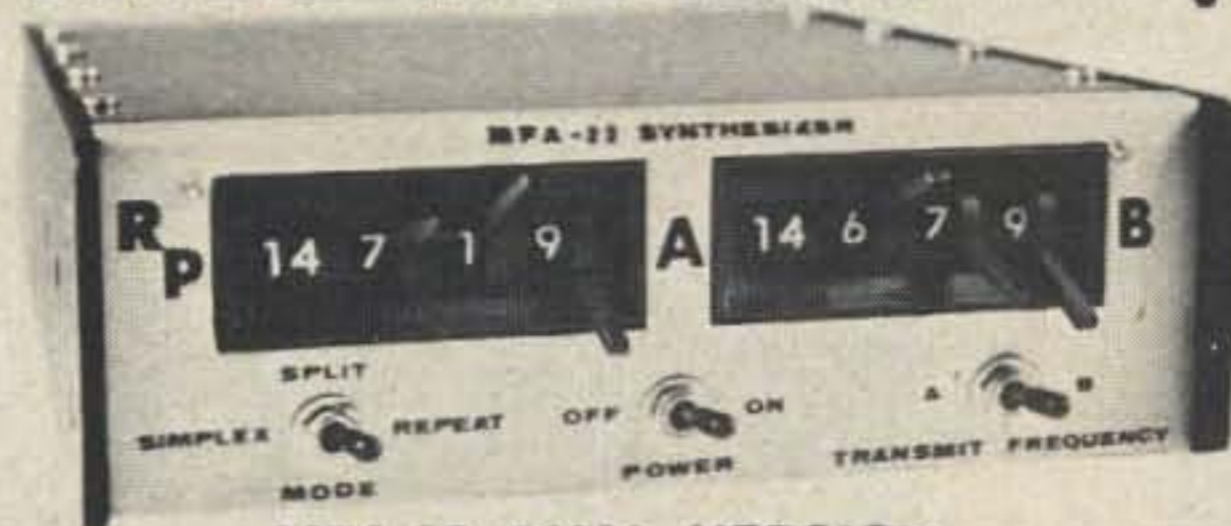SUPER CRYSTAL THE NEW DELUXE DIGITAL SYNTHESIZER!! FROM **R_P**



MFA-22 DUAL VERSION

Also Available **MFA-2 SINGLE VERSION**

- **Transmit and Receive Operation:** All units have both **Simplex** and **Repeater Modes**
- **Accurate Frequency Control:** .0005% accuracy
- **Stable Low Drift Outputs:** 20 Hz per degree C typical
- **Full 2 Meter Band Coverage:** 144.00 to 147.99 MHz. in 10KC steps
- **Fast Acting Circuit:** 0.15 second typical settling time
- **Low Impedance (50 ohm) Outputs:** Allow long cable runs for mobiles
- **Low Spurious Output Level:** similar to crystal output

• PRICES

MFA-22 \$275.00
MFA-2 \$210.00
Shipping \$3.00

R_P Electronics

Box 1201 B
Champaign, IL 61820

SEND FOR FREE DETAILS

FM YOUR GONSET

(or your Clegg 22'er, Poly-Comm 2, PC-62, Johnson 6N2, Aerotron 500, HA-460, TX-62 or VHF-1)

- **New!** Plug-in modulator puts the Communicator transmitter on FM.
- **No modification or rewiring** on your Communicator. Just plug into mike jack and crystal socket.
- **Compact self-contained modulator** measures 4" x 3" x 1½".



- Works with Communicator I, II, III, IV and GC-105, and other rigs listed.
- FM at a tenth the cost of a new rig.
- Frequency adjust for netting built in.
- \$34.50 postpaid U.S.A. \$36.50 for PC-2, PC-62, HA-460. Specify transmitter model. California residents add 5% sales tax. (HC-6/U crystal and 9 volt transistor battery not supplied.)
- Send for free descriptive brochure.

**PALOMAR
ENGINEERS**

BOX 455, ESCONDIDO, CA 92025

JUGE



TOTAL

Get total 146-148 MHz coverage without buying a crystal!

The modified Clegg FM 27B transceiver now covers the entire range of 146-148 MHz . . . and needs NO additional crystals. It's the only 2 meter rig *available now* with built-in total coverage that also offers greater than 25 watts output power, uses 10 IC devices, and has Teflon* wiring throughout. Not a single bi-polar device is in the RF path in transmitter or receiver . . . ensuring greater reliability. Accessory power supply and sub-audible tone on transmit are available too. At home or in your car, the FM 27B gives you the ultimate in total 2 meter performance. See your Clegg Dealer NOW or write or phone us today for detailed data sheet on our 2 meter leader.

Amateur Net \$479.95

CHECK THESE SPECIFICATIONS

GENERAL

POWER REQUIREMENTS: 12 to 14 VDC
Current Consumption at 13.5 VDC:
Receive: 4 amps squelched, 1.2 amps unsquelched.
Transmit: 6 amps max.

DIMENSIONS: 7 $\frac{1}{4}$ " x 3 $\frac{1}{2}$ " x 9 $\frac{1}{4}$ " deep; 4 lbs. net weight.

RECEIVER

TUNING RANGE: 146.00 to 148.00 MHz, continuously tuneable with reset capability of approx. 1 KHz to any frequency in range.

SENSITIVITY: .35 μ v max. for 20 db quieting; .1 μ v for reliable squelch action.

SELECTIVITY: 11 KHz at 3 db; Less than 30 KHz at 70 db. Adjacent (30 KHz spaced) channel rejection more than 70 db.

AUDIO OUTPUT: 2.0 watts (min.) at less than 10% THD into internal or external ohm speaker.

TRANSMITTER

TUNING RANGE AND CONTROLS: Same as RECEIVER.

POWER OUTPUT: 25 watts Min. into 50 ohm load. P/A transistor protected for infinite VSWR.

MODULATION: Internally adjustable up to 10 KHz deviation and up to 12 db peak clipping.

*DuPont trademark

ED JUGE ELECTRONICS, INC.

Home office:

3850 SOUTH FREEWAY
FORT WORTH, TX 76110
817-926-5221

Closed Sun. & Mon.

Hours: 9:00-5:30 Tues. thru Sat.

Dallas office:

2860 WALNUT HILL LANE
DALLAS, TX 75229
214-358-4641

VERSATILE TEST EQUIPMENT RANGE EXTENDER

A simple, relatively inexpensive IC amplifier provides accurate and stable voltage gains of either 10 or 100. It can be used to easily extend the sensitivity range of various dc and ac test instruments with a simple scale change factor.

Many amateurs use relatively simple test instruments, such as inexpensive voltmeters, oscilloscopes, etc., for routine maintenance work and construction projects. Simple instruments properly used can suffice for a wide variety of projects. However, there occurs those situations where more sensitive test instruments are needed to take proper measurements. For instance, take the case of those VOMs with a 10V maximum deflection on the low range and a 10,000 (or less) Ω/V sensitivity. Such an instrument is difficult to use when dealing with the low bias voltages on many transistor stages. This is because of the difficulty in reading low voltages on the scale and because of the loading effect caused by the instrument's low equivalent resistance on the 10V range.

A similar situation might exist with an inexpensive oscilloscope where the input impedance is high enough but the deflection sensitivity is low. Rather than buy more expensive test instruments, the "expensive" features of which are only occasionally needed, or do a poor measurement job with the instruments available, it is very worthwhile to use an outboard amplifier, which can both extend the low range on an instrument and provide a very high input impedance.

This article describes such a simple instrument amplifier. There is certainly

nothing new about dc meter amplifiers as such. However, the advent of IC operational amplifiers makes the construction of such a device particularly simple. Also, the IC amplifier is internally temperature-compensated, so its gain, once calibrated, will remain very stable under a variety of operating conditions — a very necessary quality if accurate instrument readings are to be obtained. Although some specific integrated circuits are mentioned, almost any operational amplifier can be used. The bandwidth and input impedance will vary with different amplifiers but these factors can be determined from a data sheet.

Figure 1 shows how the outboard amplifier functions when used with a simple VOM. It is placed between the test leads and the terminals on the VOM or other

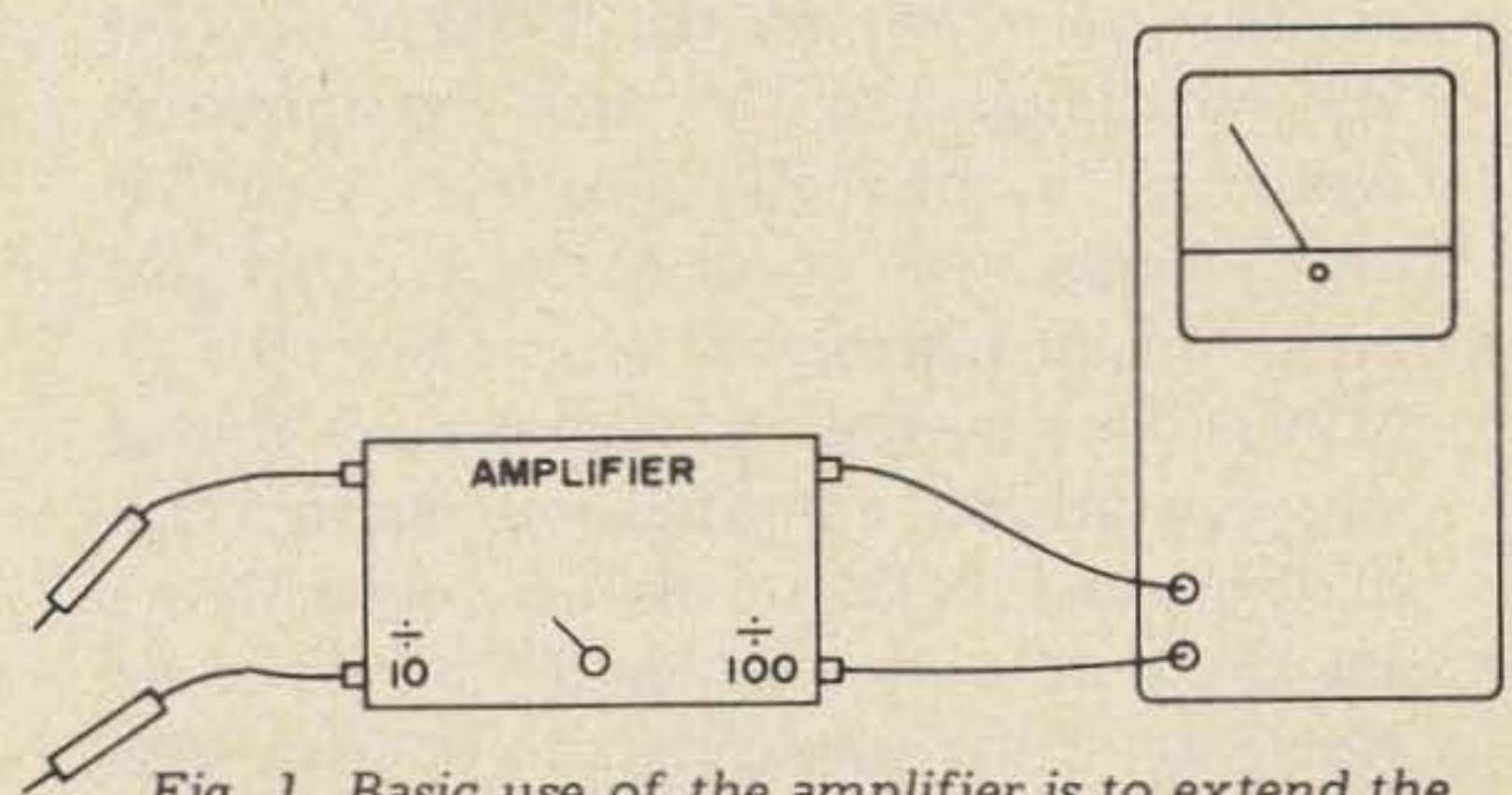


Fig. 1. Basic use of the amplifier is to extend the low voltage (ac or dc) range of a VOM. It also can provide a high input impedance to prevent loading of the circuit being tested.

HATRY ELECTRONICS

500 Ledyard St., Hartford, Ct. 06114

203-527-1881

See Ward, W1WRQ Take Airport Rd. Exit, Rte. 6, off I-91 or Rte. 15

- DRAKE – HF & VHF • HALLICRAFTERS – HF • GALAXY – HF
- TEN-TEC – QRP • SBE – VHF & UHF • REGENCY – VHF & UHF
- CLEGG – VHF & UHF

ANTENNA WIRE

Saxton #18 Copperweld 100 ft. Interconnected
 Saxton #14 Copperweld 100 ft. Interconnected
 Saxton #12 Copperweld 100 ft. Interconnected
 Saxton #14 Copper Enameled 100 ft. Interconnected
 Saxton #12 Copper Enameled 100 ft. Interconnected
 Saxton #14-7/22 Stranded Copper 100 ft. Interconnected

COAXIAL CABLE

Times FM-8, 50 ohm RG/U type Low-Loss
 Times T5-50, 50 ohm RG58/U type Low-Loss
 Belden—All Popular Types of Cable
 Belden RG8/U Put-ups – 25-50-75-100 Ft. with PL259 each end (Low-Loss Foam)

KEYERS & PADDLES

Vibroplex and Ten-Tec

COAX CONNECTORS

Amphenol & Gold Line – UHF – "N" BNC and many inter-series adaptors

INSULATORS

E.F. Johnson – Ceramic Stand offs and Antenna End and Center Insulators
 Hy-Gain – End and Center

BALUNS

Hy-Gain – 50 ohm 1:1
 W2AU-50 ohm 1:1 and 4:1

COAX SWITCHES

Barker & Williamson and Gold Line

NON-METALLIC GUY LINE

Saxton 1/8" Fibreglass-Plastic Covered 500 lb. Test-100 ft. I.C.
 Saxton 1/4" Fibreglass-Plastic Covered 1000 lb. Test-50 ft. I.C.

ANTENNAS

Mosley – New Tronics – Hy-Gain – Cushcraft – Antenna Specialists – Mark Products

TOWERS

Rohn #25 Sections & Accessories
 Cornell-Dubilier Rotors

MICROPHONES

Astatic – Turner – Electro-Voice
 SUPEREX and TELEX HEADPHONES
 WABER OUTLET STRIPS
 TERADO INVERTERS

OPEN WIRE FEED LINE

Saxton 450 ohm #18-1" spaced, 100 ft. spools
 Saxton 300 ohm #18-1/2" spaced, 100 ft. spools

TWIN LEAD

Belden 8210-75 ohm H.D. 1 KW
 Belden 8235-300 ohm H.D. 1 KW

CONNECTICUT'S OLDEST HAM STORE

Please include Postage

Canadian Amateurs Send U.S. Funds Only

F.O.B. Hartford

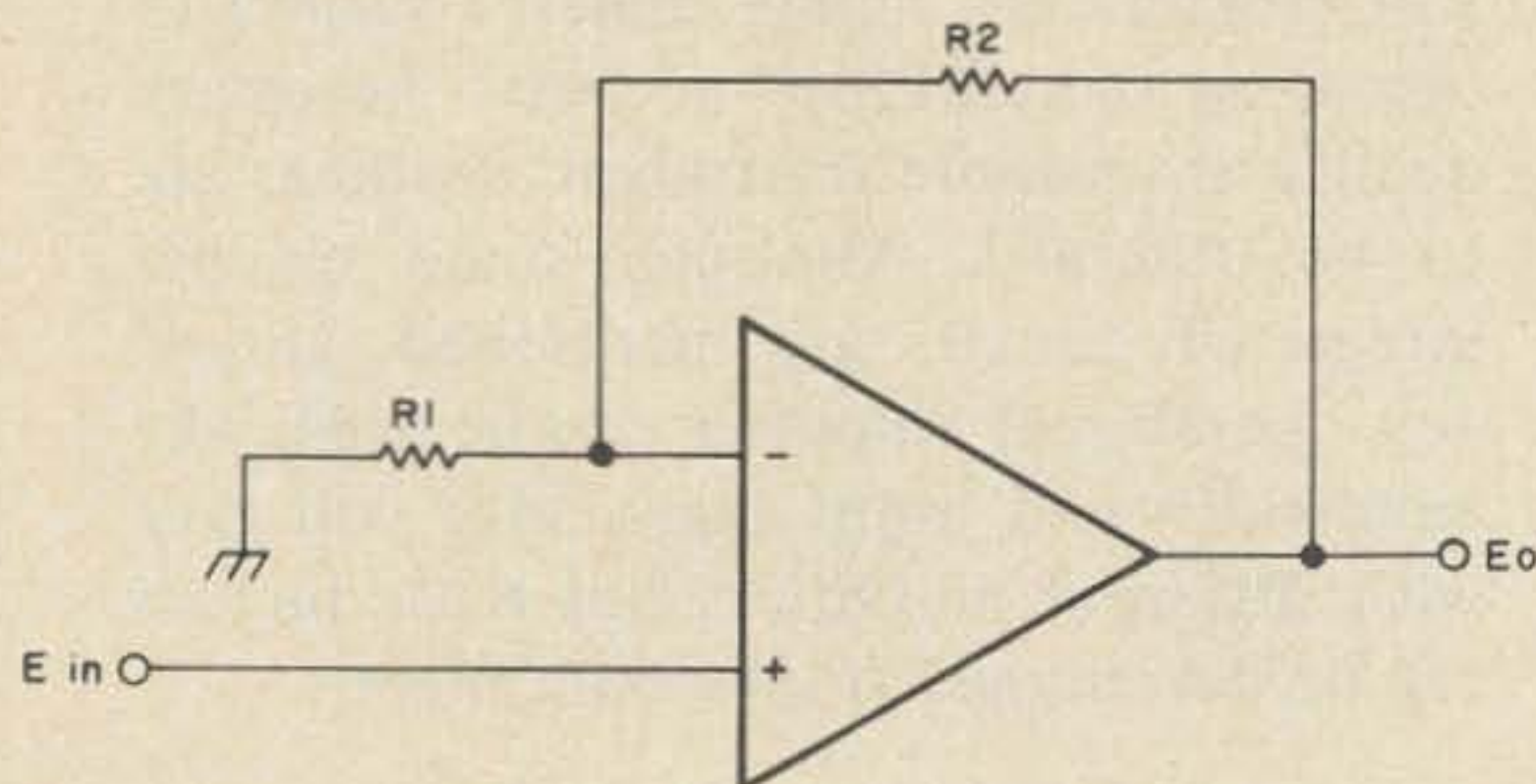


Fig. 2. Basic operational amplifier performance equations.

instrument. It can be used on *either* the ac or dc low range of the instrument. If the normal low range on the VOM is 10V, it will be changed to 1V when the amplifier switch is in the $\div 100$ position. A similar scale change will occur for any other low range on an instrument (e.g. 5V to 0.5 or .05V). The frequency response of almost any operational amplifier will match that of the usual VOM on its ac ranges where the response only extends to 20 kHz or so. However, if the amplifier is to be used with an oscilloscope or VTVM where the frequency response might extend to 1 MHz or more, an operational amplifier with corresponding bandwidth must be used.

Amplifier Circuit

The basic operational amplifier circuit is shown in Fig. 2. As shown in the figure, the gain of the amplifier (from dc up to the cutoff frequency of a specific amplifier) is determined by the ratio of the resistances. Therefore, by choosing and switching the resistors properly, one can produce an amplifier with specific gains for instrument reading expansion. Bypass and rolloff capacitors may be necessary for a specific amplifier to prevent spurious oscillations and to shape the frequency response.

Figure 3 shows a practical circuit using a Motorola MC1520 amplifier. The frequency response of this unit is quite broad – extending from dc up to 10 MHz. The circuit, however, is typical of that which can be used with other less-expensive operational amplifiers where such a high frequency response is not required. The input impedance is in the order of several megohms and the maximum input voltage that the unit can linearly amplify is $\pm 3V$. The amplifier

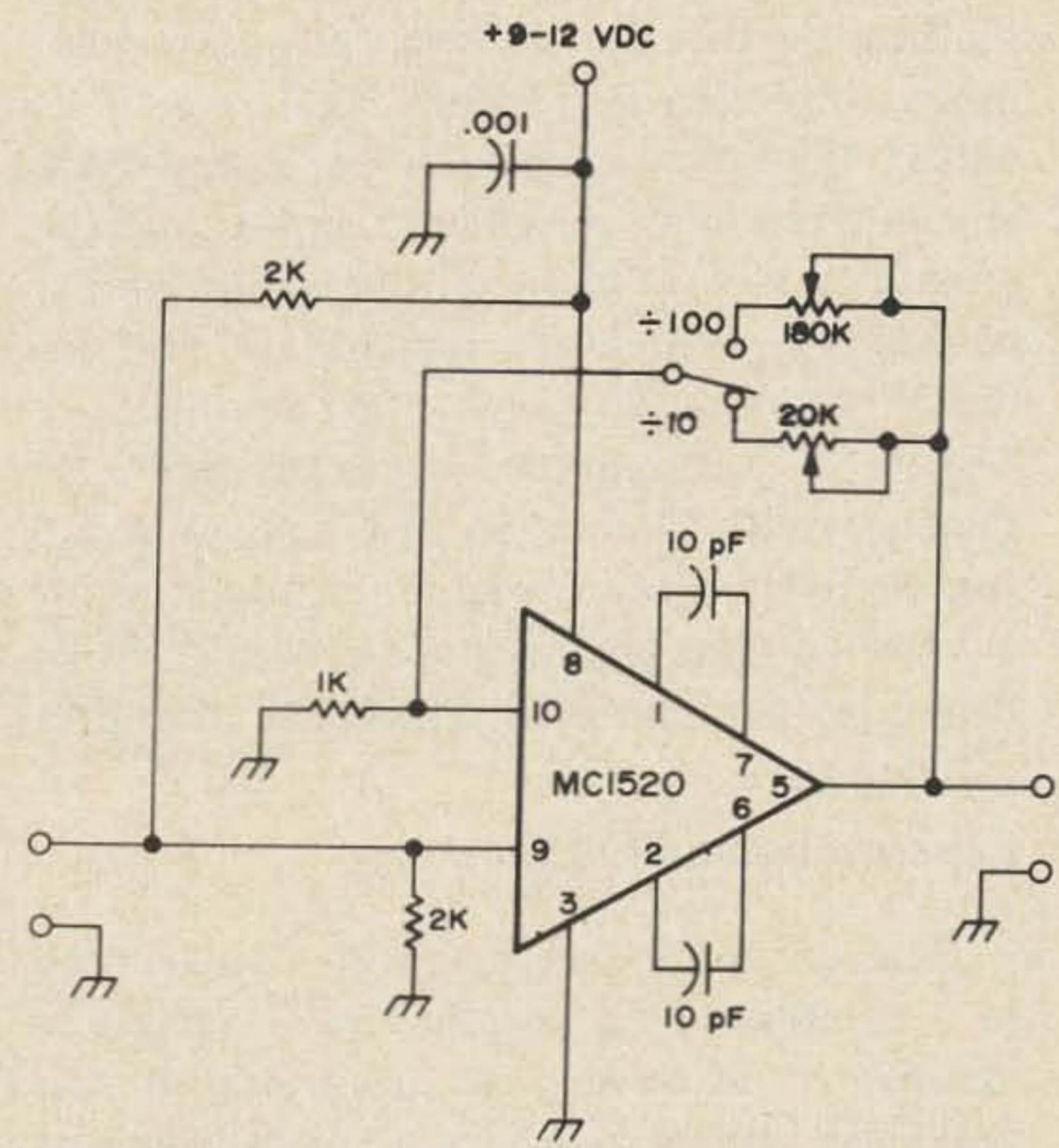
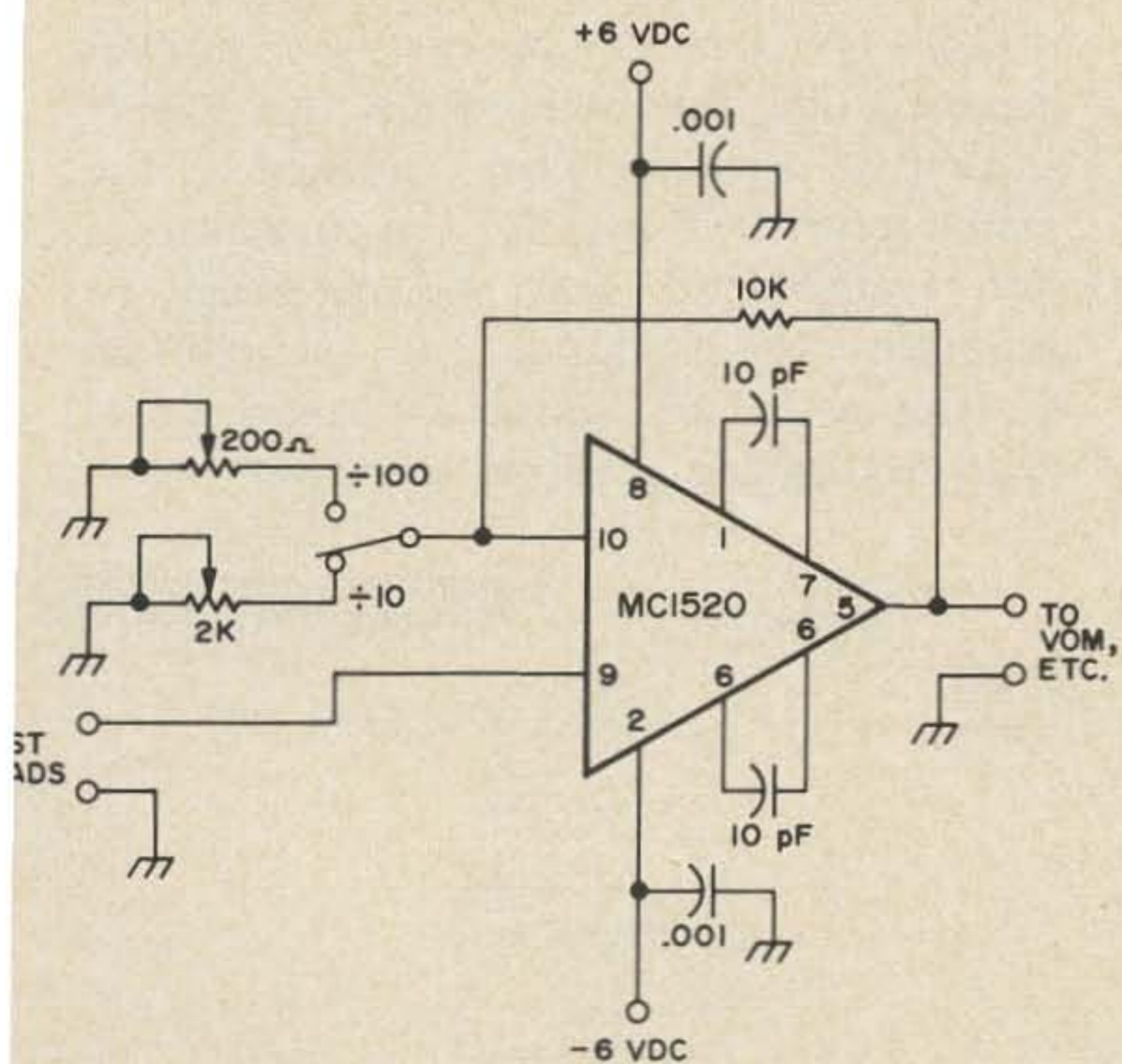


Fig. 3. The Motorola MC1520 general purpose operational amplifier can be utilized for extended measurements from dc to 10 MHz.

Fig. 4. One can rearrange the circuit of Fig. 3 so only a single battery is needed but the necessary bias arrangement reduces the input impedance.

action is noninverting. That is, positive-going inputs cause a positive-going output, and negative-going inputs cause a negative-going output. So, when measuring a voltage one has to reverse the test lead connections in a conventional manner, depending upon the polarity of the voltage being measured. Two 6V batteries are needed to power the amplifier (a maximum 10 mA current requirement). The absolute maximum supply voltage which can be used is 9V.

Although the current drain is such that small transistor batteries can be used, one may want to use only a single battery. This can be done using the bias arrangement shown in Fig. 4. The amplifier operation remains the same as before but the necessary placement of a bias resistor from terminal 9 to ground considerably lowers the input impedance of the amplifier.

Another amplifier circuit is shown in Fig. 5. The frequency response extends to

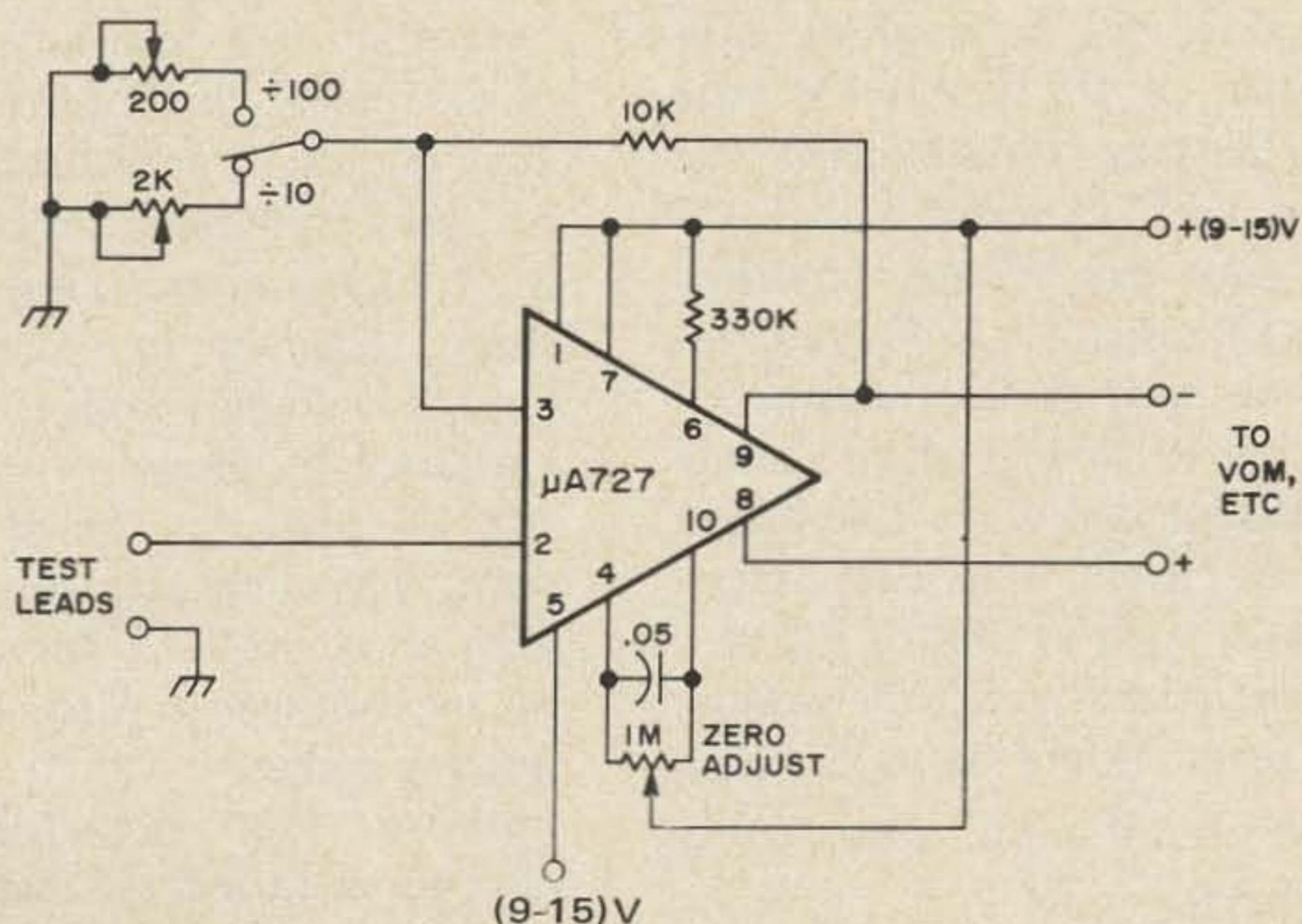


Fig. 5. Another example of the use of an operational amplifier for use as a calibrated gain amplifier. Input impedance for the unit used is an extremely high $1000 M\Omega$.

only a few hundred kilohertz. A unique feature of the unit is the extremely high input impedance ($1000\text{ M}\Omega$) which is better than that provided by many FET voltmeters. The maximum input voltage range is $\pm 10\text{V}$. A dual battery supply must be used as indicated. Because of the internal characteristics of the amplifier, a separate zero-adjust potentiometer is needed. With the input test leads shorted together, the potentiometer is adjusted for a zero voltage indication on the VOM or other instrument with which the amplifier is being used.

Construction and Calibration

The amplifier can be easily constructed in a minibox or a plastic case. A shielded enclosure, however, is preferable if the amplifier will be used for ac measurements above a few hundred kilohertz. Otherwise, there are no special precautions to be observed in the construction of the amplifier. Naturally, lead dress should be carefully done on amplifiers used in the megahertz range. The calibration potentiometers need be only small, inexpensive PC board types (Mallory MTC) since they only have to be adjusted once for calibration purposes. The zero-set potentiometer shown in the circuit of Fig. 5 should be a panel control.

The calibrating potentiometers can be set by using a fresh battery as a calibrating source with a voltage divider network across it to produce the appropriate voltages. For instance, if 0.1V and 1V were required, a 1.5V battery could be used. For 1V , a divider of $1\text{ k}\Omega$ in series with $2\text{ k}\Omega$ could be used with the voltage measured across the $2\text{ k}\Omega$ resistor. A low-voltage battery should be used (rather than a 9V battery) to obtain 0.1V in order to avoid errors due to divider resistance tolerances.

If an amplifier circuit with a low input impedance is used, such as that of Fig. 4, a divider resistance, across which the calibration voltage is read, should be used which has a resistance of not more than 10% of the input impedance.

The amplifiers of Figs. 3, 4, and 5 have a flat response from dc up to the cutoff

frequencies cited and so dc calibration suffices for ac measurements also. This will generally be the case where the rolloff capacitors used are those specified by the manufacturer. If data for the capacitors is not available, it may be necessary to calibrate the amplifier for accurate ac measurements by using an audio or rf generator having a calibrated output.

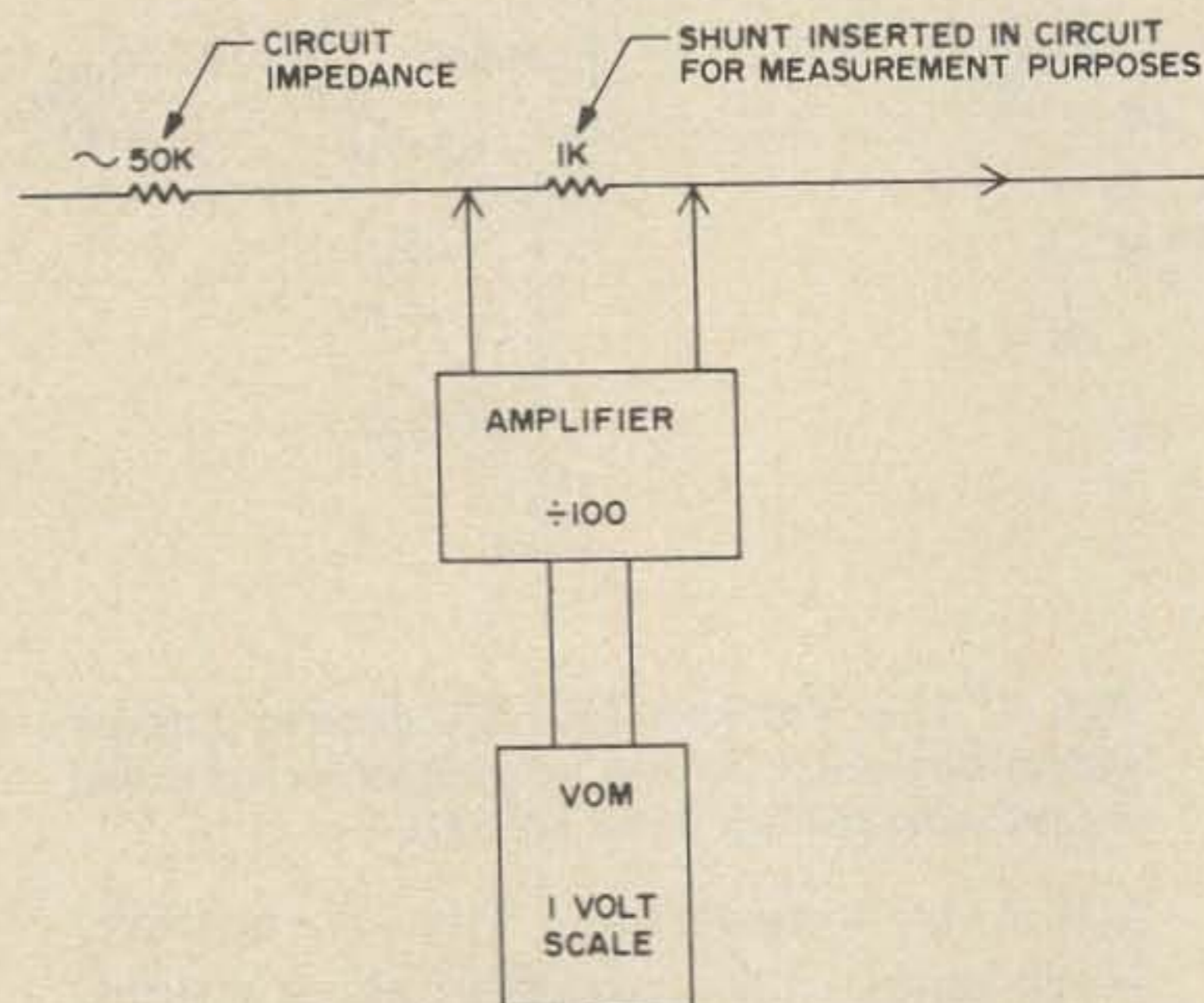


Fig. 6. Another use for the amplifier is to allow very low current measurements in high impedance circuits with simple instruments. In this case 1V scale on VOM is converted to a $10\text{ }\mu\text{A}$ range.

Other Uses

The amplifier unit can be used for a variety of purposes besides that of increasing the sensitivity of an instrument for ac and dc voltage measurements. A simple extension of its use is for the measurement of extremely small currents in high-impedance circuits. For instance, a VOM may not be able to measure directly a current in the low microampere range. By inserting a shunt resistance in the circuit and measuring the voltage across it with the aid of the amplifier, as shown in Fig. 6, one can turn the 1V scale on the VOM into a $10\text{ }\mu\text{A}$ scale. The amplifier can be used as an aid with an rf probe to increase the sensitivity of measurement. Also, because of its frequency range, it can be used as a general-purpose audio preamplifier, i-f amplifier, etc., for a variety of test and experimental purposes.

...W2EEY

A POWER SUPPLY FOR SMALL FM RIGS

Spend some time home with the family

The chief disadvantage of many small FM rigs is the lack of a built-in ac power supply. The current drain of most low power rigs is fairly low so a simple power supply can be built quite cheaply out of standard parts. This power supply can be used as a base on which to rest the rig while operating using ac power. While this supply cannot power amplifiers, in most areas no amplifiers are needed to work many stations. The batteries can be charged while using this supply so the rig will always be ready for portable use.

Circuit

The circuit used is a bridge rectifier and a series regulator using a 2N3055 transistor. The flag type 2N3055 will dissipate $3\frac{1}{2}$ W without a heatsink, while the TO-3 type will dissipate 5W without a heatsink. By keeping the dissipation below these levels heat sinking is not needed. The method used in this supply is to put the resistor R1 in series with the collector of the transistor. Thus the resistor and not the transistor dissipates the power. With an 8Ω resistor the transistor

dissipation is about .3W on receive and 1.25W on transmit, permitting cool operation.

The $1000\ \mu\text{F}$ capacitor in conjunction with a transistor beta of about 50 makes an effective filtering of about $50,000\ \mu\text{F}$. The result is negligible ripple in the millivolt range when the supply is operated at full output.

Construction

The supply is mounted on a piece of perf board in a gray hammertone minibox. The toggle switches and neon pilot lamps are located on one end with the output cable, line cord, and the fuse on the other end. The board is mounted upside down in the box using brass screws and hex nuts.

All parts including the transformer are mounted upon the circuit board. A negative bus of 14-gage wire runs along one side almost the whole length of the board. The layout is similar to the schematic.

The dropping resistor R1 is made from 4- 32Ω $\frac{1}{2}$ W resistors, although a 6.8 or 8.2Ω


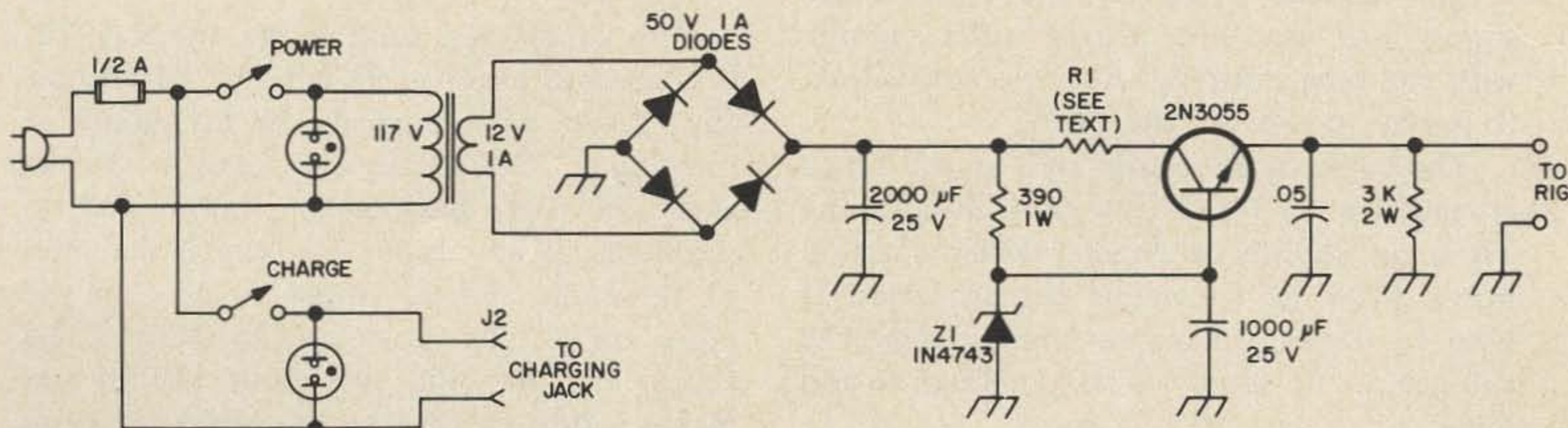


Fig. 1. Power supply schematic. L1, L2—neon pilot light assemblies. R1—see text. Z1—zener diode—Motorola 1N4743 or Radio Shack.

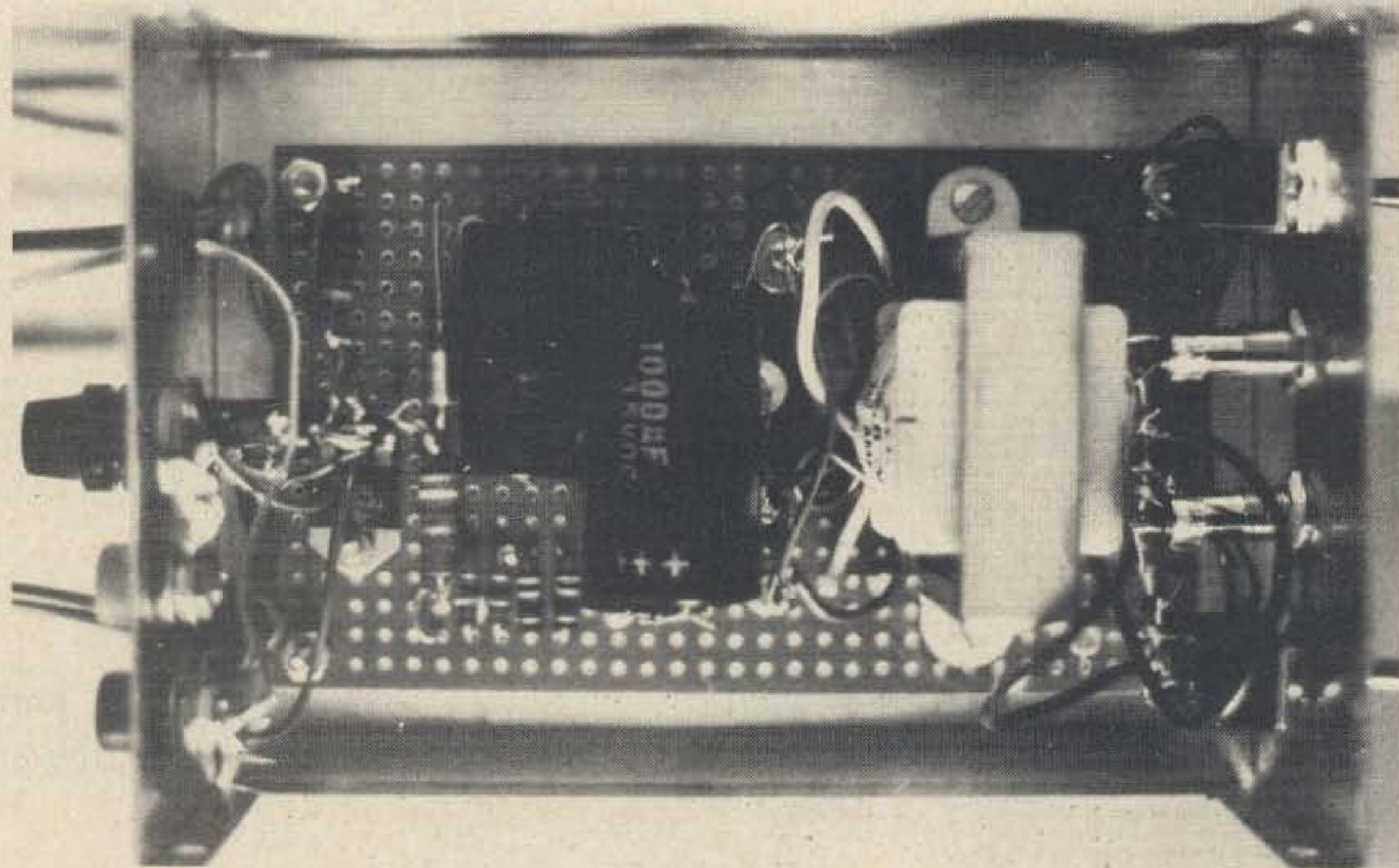

A view inside the power supply cabinet showing the circuit board.

5W resistor may be used if on hand. For rigs other than the TR22 (the rig with which I was working) the value for R1 may be calculated from the equation

$$R = \frac{V_s - V_{out} - .7V}{I_{xmit}}$$

where

V_s = Voltage at capacitor

V_{out} = Output voltage

I_{xmt} = Transmit current

For my supply there was 17V in and 12 out so $17 - (12 + .7) = 4.3V$. The transmit current is $\frac{1}{2}A$ thus an 8Ω resistor can be used. Resistor dissipation is 2W while transistor dissipation on transmit is .5W. The actual resistor value should be slightly less than the one calculated. Note that whatever the case the transistor is operated well within its ratings.

The banana jacks on the rear of the supply are used for testing other circuits with the power supply. A short cable is used to provide power for the TR22.

The cable to the charge jack on the TR22 is made from a TV cheater cord. Because the TR22 has an internal charger with-in, it only needs 110V ac to charge the batteries. If your rig does not have a built-in charger, the cabinet of the supply is large enough to add one.

The only precaution necessary before working on the power supply is to make sure

the capacitors are shorted out. Although there is a bleeder, with such high capacitance values the time constant becomes large. Some have said 12V cannot kill. While this may be true I still like to take some safety precautions.

Although a Radio Shack zener was used, a Motorola 1N4743 will provide about 12.3V out instead of the 11.5 I get with the one in the supply. I have noticed no degradation of signal strength or loss of transmitter power due to the low input voltage.

To test the supply do not connect the rig to the output. A friend did this and a shorted transistor drastically shortened the life expectancy of his rig. A 240Ω 2W resistor can simulate the TR22 on receive, while a 24Ω 10W resistor can serve on transmit. It's better to be safe than sorry.

Conclusion

This supply was built in December 1972. It is used to monitor 94 simplex 24 hours a day, seven days a week, in my home in Providence. Even after operating for weeks at a time there has been no failure and no problems of any type. No hum is detected on the audio and the ripple is less than the noise on a laboratory quality meter. The supply can be built for about \$15.00 and makes a fine addition to any shack. See you on the air.

...WA3EEC/1

A RADIATING LOADING COIL

John Risch WØFEV
3508 Whispering Woods Drive
Florissant MO 63031

For SWR adjustments in the shack.

How would you like to have an effective 80 meter antenna? If you would, but haven't the sufficient space to put up a "textbook" antenna, you should try this one. The overall length is about 230 cm and it can be located inside your shack or outdoors. It is effective. I've worked many VE3's from St. Louis, Missouri on 80 meters CW with reported signal strengths of 7 and 8 using only 80 watts input to a Heathkit DX605. The cost is less than \$5 and it can be constructed in one or two evenings. The swr is less than 1.2 to 1 as indicated by a Heathkit swr indicator HM-15 over the whole portion of the 80 meter CW band (by adjusting taps).

After unsuccessfully trying to load up a random wire antenna on 80 with a low swr and no rf in the shack, I decided I needed something else. A review of available antenna manuals, handbooks, etc., convinced me there was no way except to use a half wave wire or a dipole with quarter wave tuned feeders. I simply do not have that much free space at my QTH, not unless I erected a tower in my front and back yard.

I was about to give up ever working 80 meters until I got interested in shortened antennas. Most of these, however, required center (critically adjusted) loading coils or complicated matching devices.

One that appealed to me was the Helix, briefly described in the ARRL Handbook. It is nothing more than one half wavelength of wire, helical wound on a long coil form and operated as a quarter wave vertical against ground and fed with 52Ω coax.

The Handbook showed how an adjustable loading coil could be used to change frequency. My thoughts were, why not consider the whole helix as one continuous

linear loading coil, provide taps on it and feed it directly without any external coils, tuners, etc. That's what I did, and it worked.

Once you select the band you want to build for (you should be able to build a Helix for any band) you should consider where it will be located – indoors or out. If indoors, naturally it won't have to be quite as rugged and should be small enough to move conveniently. You could use almost any material for the form – plastic, paper tubes, wood dowels, etc., as long as it suits your needs and is considered low-loss at the rf frequencies you will be using.

I used cardboard (paper) mailing tubes as they were readily available at the local stationery store. Most tubes of this type have telescoping lids. Both the tube and the slip-off lid had formed-in metal end caps. Try to use this type of tube if possible, as they are easier to work with. The diameter can be anywhere from about 4–7.5 cm and the selection should be based on the band the antenna you are making will cover. Naturally, forms for 75 or 80 meters should be of a larger diameter than a 40 meter one to avoid crowding the turns. Obtain as many tubes as needed to make up the length of form you want. If you use those with metal ends, remove them with a small saw. Either use the "necked down" end of one tube to slip into the other tube or use a separate piece of smaller diameter tube to fasten them together. Use Duco cement, Elmer's Glue or any other good cement to join the tubes. Do a good job as it's difficult to reglue them after they are wound.

Whatever type of form or forms you used, you should end up with one long form 200–250 cm long and about 7.5 cm diame-



This particular model almost reaches the ceiling of the shack. A wire capacity hat was added to increase the effective height and bring more rf current up the coil.

ter (for 80 meters) with a metal end at each end only. If open-end tubes are used you will have to add some sort of mounting brackets. The completed tube should be thoroughly saturated with Spar Varnish or a good grade of shellac, inside and out. I poured varnish inside and rolled the tube around while tilting it back and forth before I glued it together. I would advise against using paint as there may be some metallic pigment in it which would affect the Q.

Prior to actual winding, determine the pitch (number of turns per inch) to use in order to uniformly wind the coil to fill the entire length of the tube. Leave a few cm at the bottom for possible additional turns — discussed later. This is easy for those who are excellent at math, but the rest of us will have to use the formula $C = \pi d$, where circumference equals pi (use 3.14) times the diameter of the form. You can calculate the length of wire to use, or look it up in the Handbook. You will need to wind one-half wavelength of wire on the form. Since you know the length of the winding space on your form, this formula will tell you how much wire (in length) will be needed for one turn. Divide this number into the total length of wire (40.84 meters for the 80m

band) to see how many turns your coil should have.


For my 7.5 cm diameter form it came to 174 turns. Since it was 225 cm long, it required 1 turn each 1.3 cm. Use a metric rule and mark the form at 1.3 cm intervals. When you wind be sure that the wire crosses each successive mark. It's all right if the pitch varies a little; it does not have to be perfect. The best way to wind is to have another person slowly rotate the form for you. I used No. 16 AWG solid enamel wire, but any suitable size could be used. It would depend on the power you intend to use and the total number of turns. I suggest that you not use anything smaller than 16 AWG.

When you have wound on about 90% of the wire or about 160 turns, you should tap every second turn from then on. These taps will be at the bottom of the antenna and will allow you to cover the entire band. Wind a few extra turns (about 5 or so, at least) to compensate for any miscalculations. To make the taps, scrape a few cm of the enamel insulation from the wire, (bare wire could be used if available) and twist a loop in it and solder before continuing to wind. After you have completed the winding, it can be terminated by drilling two holes through the form and threading the wire through each.

The completed coil should be given several coats of varnish or other low loss material to hold the turns in place. If you are going to use it outdoors, then additional weather proofing measures are necessary (coat with clear epoxy, etc.).

Mount on a suitable wood or plastic base. A 20 x 20 cm piece of plywood is satisfactory. Either run screws up from the bottom into nuts soldered to the bottom metal end cap or use several small "L" brackets. Mount a female coax connector to this base also with "L" brackets. Solder the free end of the coil to the center conductor of the coax connector along with a short length of flexible wire equipped with an alligator clip for reaching the taps. Mount a binding post on the mounting base and connect it to the coax shield for grounding.

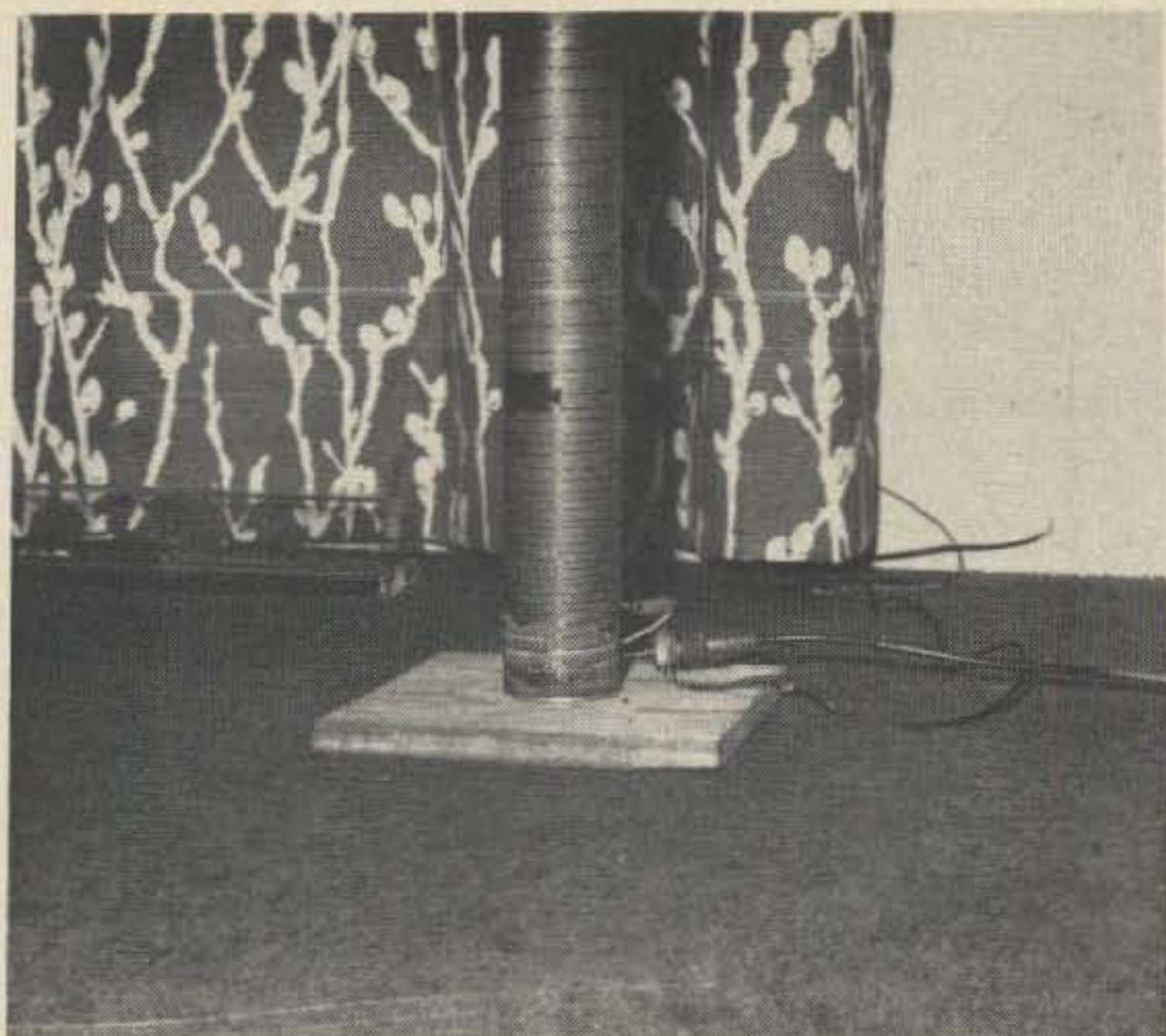A capacitive hat can be a metal disk about 30 cm in diameter or wire radials (No. 10–12 AWG solid wire) about 30 cm long.



The base is a piece of plywood with a coax connector attached for easy disassembly.

Solder the disk to the metal end cap or mount with small "L" brackets and connect to the top of the coil. If you use wire, simply poke them through one side of the form out the other side. Use about 6 or 8 pieces and solder them where they cross at the center. Then form a circle of stiff solid wire around the ends of them and solder to form a complete loop or halo with spikes.

Tune-up is straightforward. Try loading it up with reduced power first at the low end of the band. Use some sort of reflected power or swr indicator and check the loading. Soon you will find which tap to use for the low end of the band; then move up and repeat the procedure. If suitable loading at full power for your rig and low swr cannot be obtained, you may have to add more turns or unwind some from the bottom and add more taps.

As this antenna is used as a quarter wave vertical, it must be operated against ground. I used a single 200 cm ground rod driven in the ground outside the window of my shack and used a length of copper braid to the ground terminal on the antenna.

I imagine that an antenna of this type would work very well outside with a set of full size radials. I also imagine that a 20 or 40 meter antenna would work equally well. Using similar construction techniques a multiboard antenna form could be assembled in a few hours.

...W0FEV

GATEWAY ELECTRONICS

8123-25 PAGE BOULEVARD
ST. LOUIS, MISSOURI 63130
(314) 427-6116

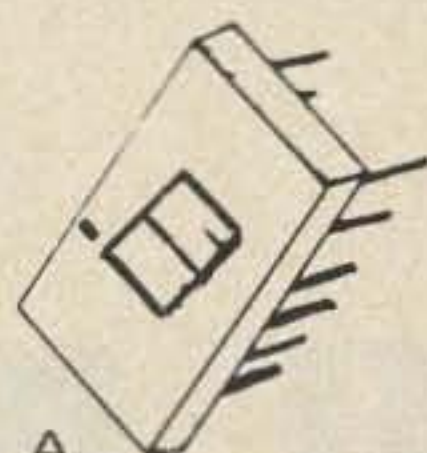


Fig. A

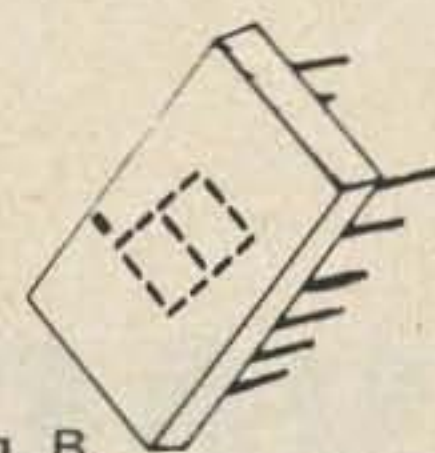


Fig. B

LED READOUTS

- Fig. A MAN-1 Style with diffused segments for improved visibility **\$2.75**
 Fig. B MAN-1 Style **\$2.75**
Giant 0.6 in. LED similar to Fig. B **\$3.95**
 Single LED lamp, red or clear, please specify.
\$0.35 each, 3 for \$1.00

IC SPECIALS

- Stereo Amp. 2 watt per channel dual in-line package w/data **\$2.00**
 Clock Chip - National 5314 12/24 hr 4 or 6 digit 24 pin pkg w/data **\$12.95**
 22 Pin PC card socket 0.156 spacing **\$.50**
 WE Touch Tone Pad 12 button new **\$19.50**
 5 MHz crystal miniature size w/wire leads **\$2.50**

IC SOCKETS


- | | | | |
|------------------|--------------|-----------|---------------|
| 14 pin solder | \$.50 | wire wrap | \$.55 |
| 16 pin solder | \$.55 | wire wrap | \$.60 |
| 24 pin wire wrap | | | \$1.20 |
| 28 pin wire wrap | | | \$1.30 |
- BUY 10 & DEDUCT 10%**

THUMBWHEEL SWITCHES

- STANDARD SIZE - 0.5 x 2.125 x 1.78
 10 position decimal **\$3.00**
 10 position BCD & compl. **\$4.00**
 End Plates (per pair) **\$1.45**

MINIATURE SIZE - 0.312 x 1.3 x 1.3

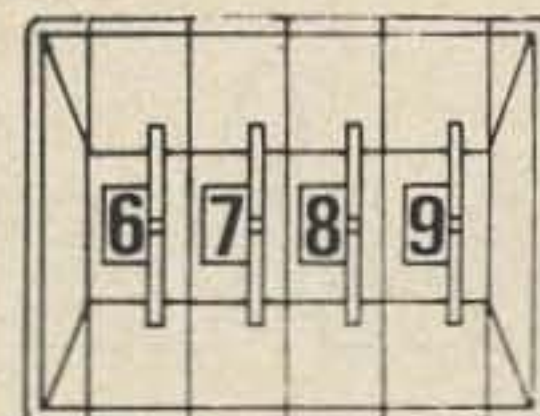- 10 position decimal **\$2.50**
 10 position BCD & compl. **\$3.75**
 End Plates (per pair) **\$1.00**
 Divider plates **\$1.25**




\$5 Minimum Order. Visit us when in St. Louis.
Please include sufficient postage.

ADIRONDACK

Recently Appointed

YAESU DISTRIBUTOR

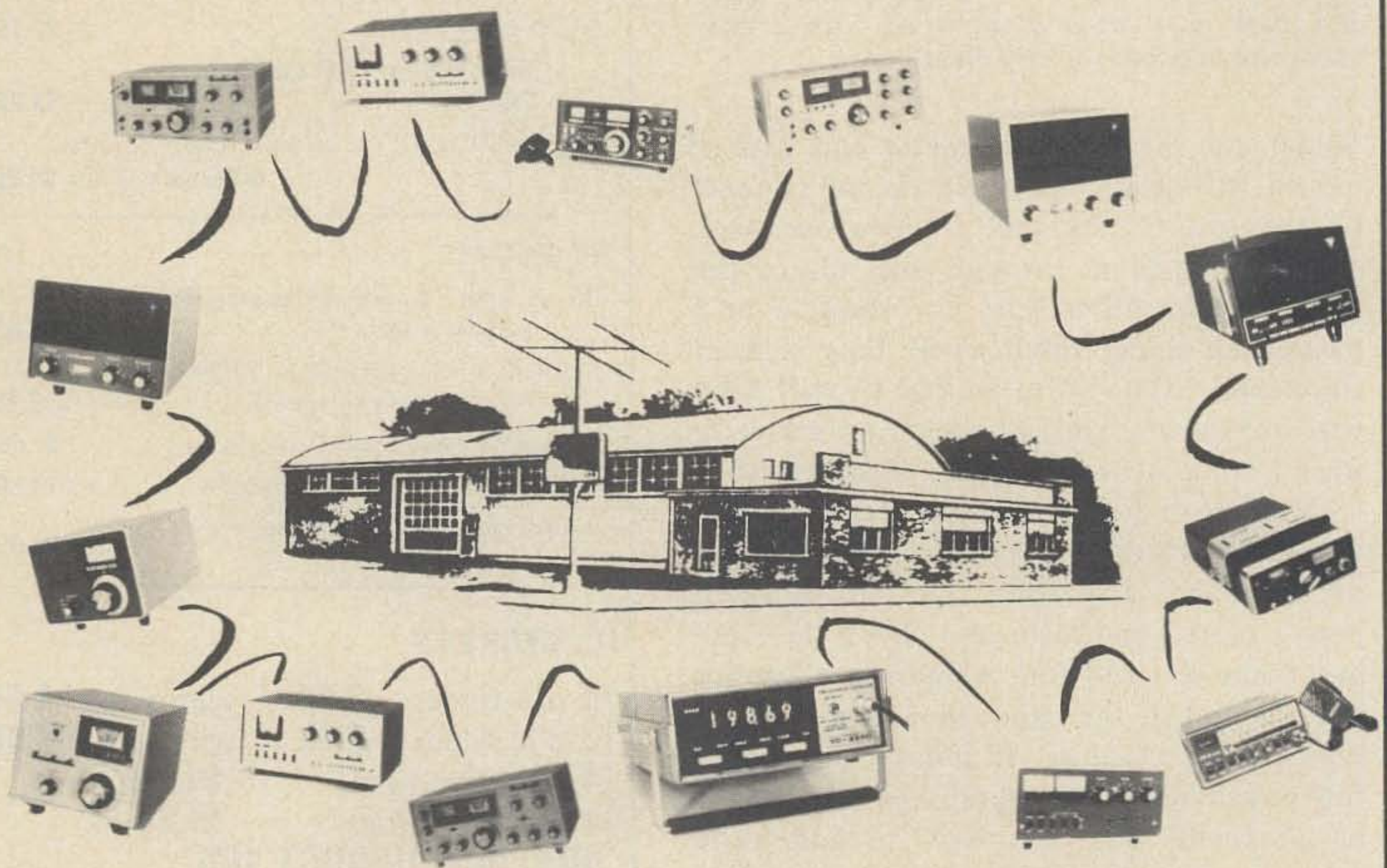

**NOW READY WITH YAESU EQUIPMENT
TO SERVE THE NORTHEASTERN AREA.**

See all the Great Yaesu Equipment in stock at . . .

ADIRONDACK

RADIO SUPPLY, INC.
Serving the radio amateur since 1936

185 W. Main St. Amsterdam, NY 12010 Tel. (518) 842-8350

PEAK / NOTCH IC AUDIO FILTER

Operational amplifiers such as the 709 and 741 have made it possible for the amateur builder to construct CW audio filters that have excellent characteristics. However, typically, these operational amplifiers require a dual power supply, i.e., $\pm 9V$. Most amateur equipment is designed to operate from a single power supply, +12 for example. Motorola has recently offered a

“monolithic quad single supply operational amplifier,” the MC3401P. Detailed specifications are described in their Bulletin No. DS 9191. It is essentially 4 internally compensated operational amplifiers in a single 14 pin TO-116 package. The power supply is + only; +5 to +25V.

Motorola’s Bulletin describes several possible uses for this chip. The unit that I

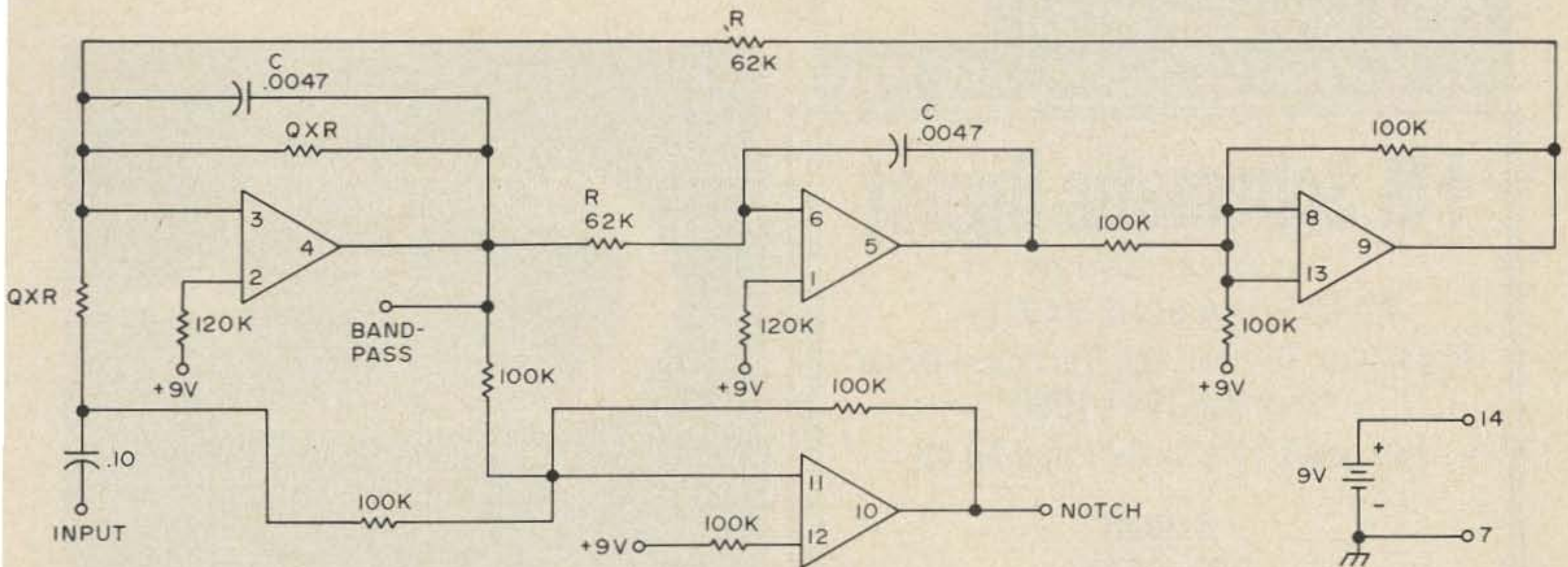


Fig. 1. Schematic of the peak/notch audio filter using the MC3401P.

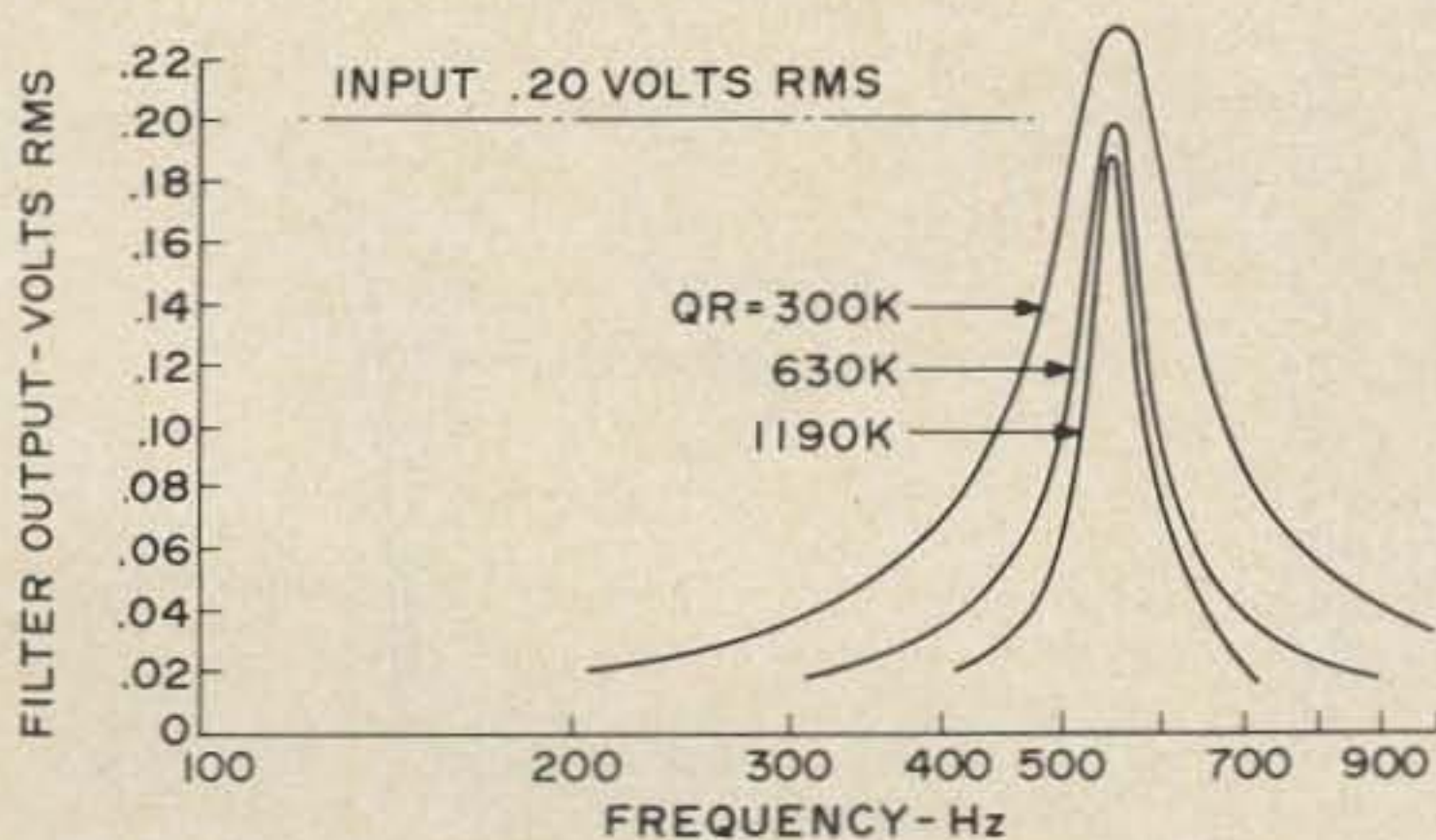


Fig. 2. Measured characteristics of the bandpass filter using different values at QxR.

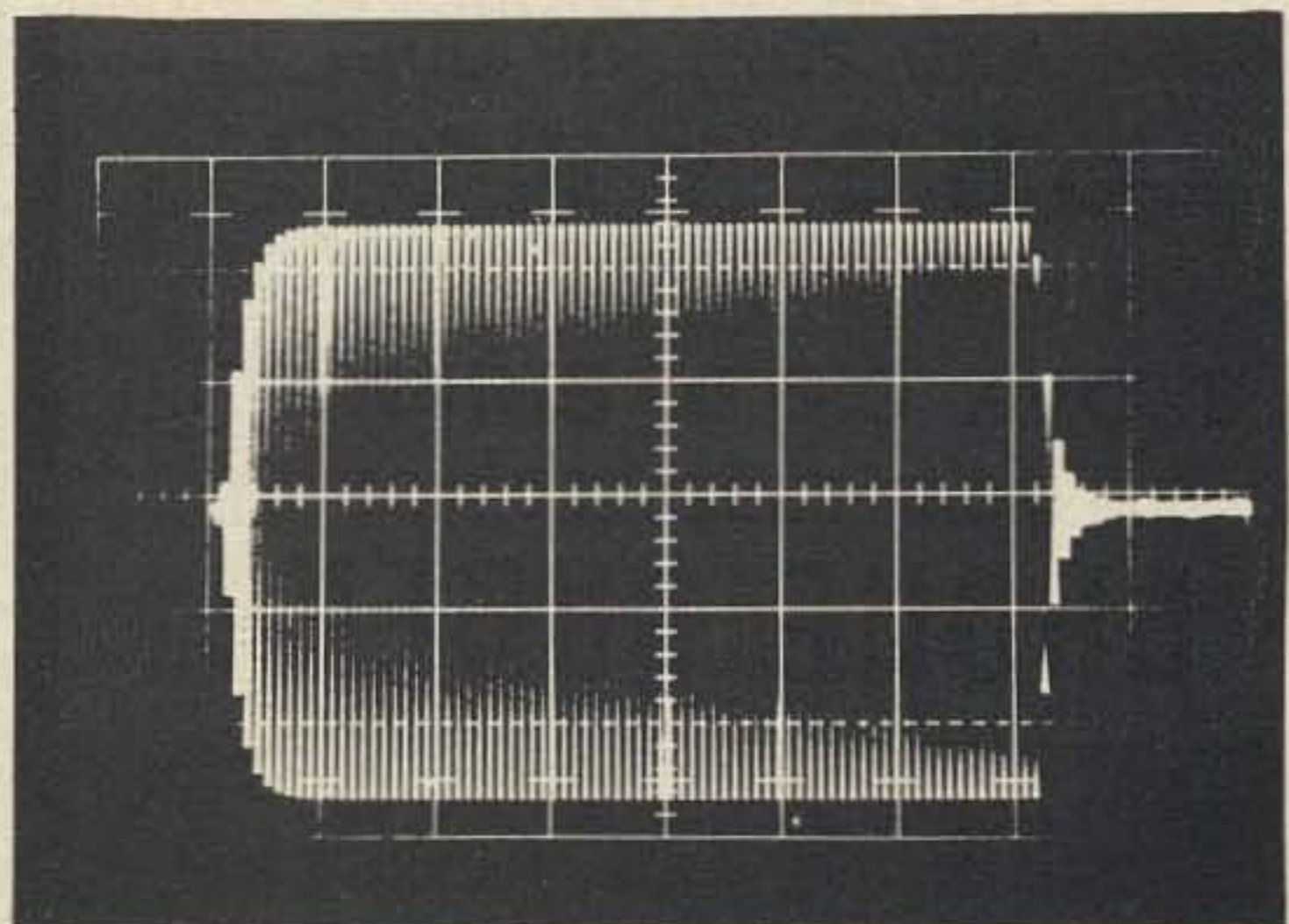


Fig. 3. Keyed waveform, QxR = 300K. Horiz. = 20 msec/cm.

**MORE RANGE . . .
with NO NOISE**

**FOR ALL
MOBILE UNITS**



CUSTOM SYSTEMS
KITS • ACCESSORIES

**ELECTRO-
SHIELD**

ELIMINATE IGNITION NOISE
ELECTRO-SHIELD®
YOUR ENGINE

FROM \$44.95

ESTES ENGINEERING CO.

543 W. 184th St., Gardena, Calif. 90247



FM Schematic Digest

A COLLECTION OF
MOTOROLA SCHEMATICS
Alignment, Crystal, and Technical Notes
covering 1947-1960
136 pages 11½" x 17" ppd \$6.50

S. Wolf
Box 535
Lexington, MA 02173

EXPERIMENTING IN FACSIMILE?

The leading manufacturer of 18" facsimile weather chart recorders is in the process of converting an existing network for fully automated weather chart transmission. This conversion will make available a number of used 18" weather map recorders ideally suited for use by anyone interested in experimenting with facsimile.

They include the recording head, all necessary electronics including automatic start, phase and stop circuits. Operating at speeds of 60, 90 or 120 rpm (depending on model), these recorders, with suitable receiver and FSK converter, can be used to monitor radio weather chart broadcasts from stations located around the world or modified to accept press wire photo transmissions or modified to receive transmissions from orbiting weather satellites.

These recorders are available strictly on a first-come, first-served basis.

Call or write Mr. Armand D. Bouchard
**ALDEN ELECTRONIC & IMPULSE
RECORDING EQUIPMENT CO., INC.**
Washington St., Westboro, Mass. 01581
617-366-8851

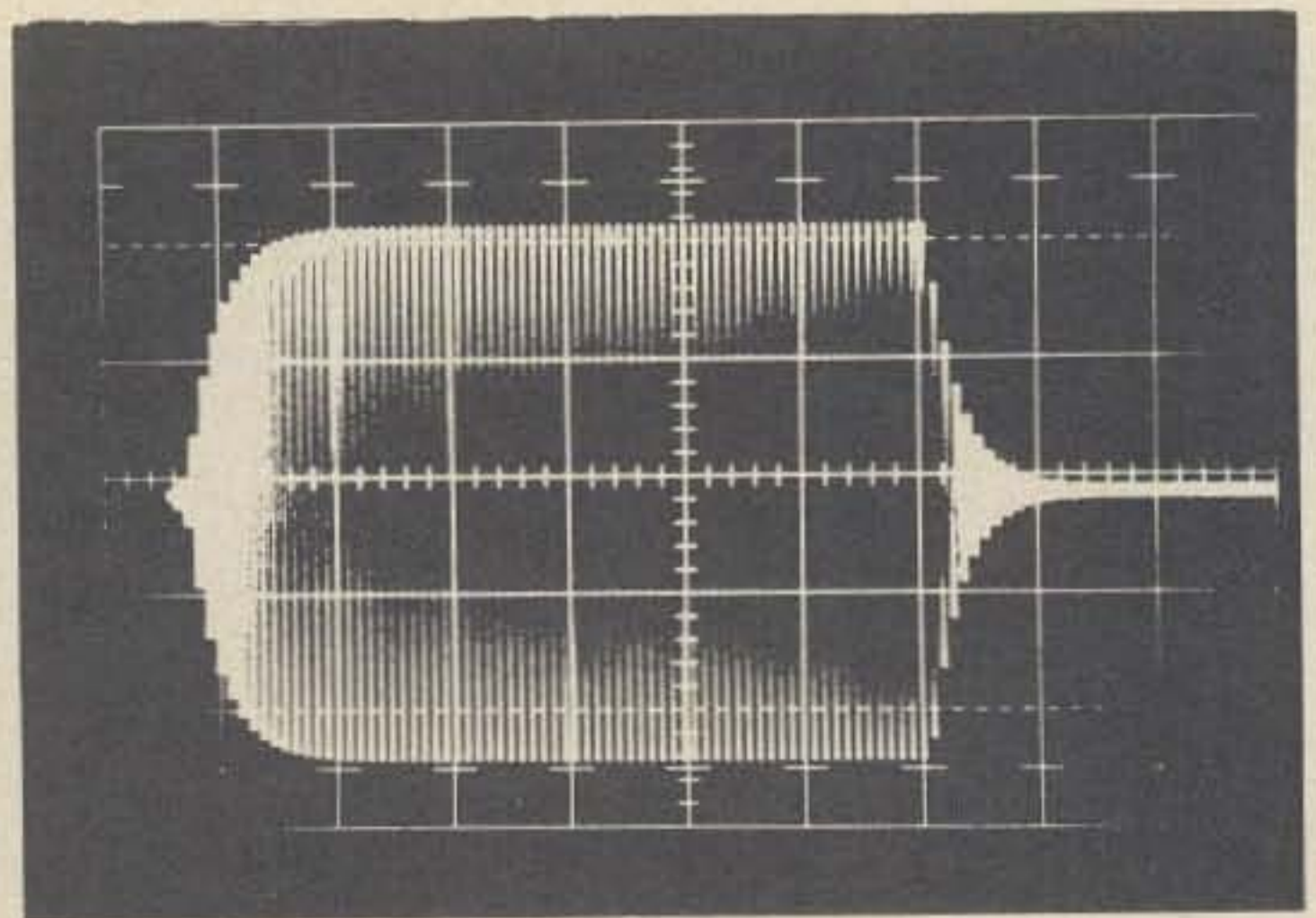


Fig. 4. Keyed waveform, $QxR = 630K$. Horiz. = 20 msec/cm.

constructed is a peak and/or notched CW audio filter. The single supply makes it particularly attractive to amateurs with receivers using only one supply.

Fig. 1, shows the schematic diagram of the filter. The center frequency of the bandpass or band reject is determined by R and C .

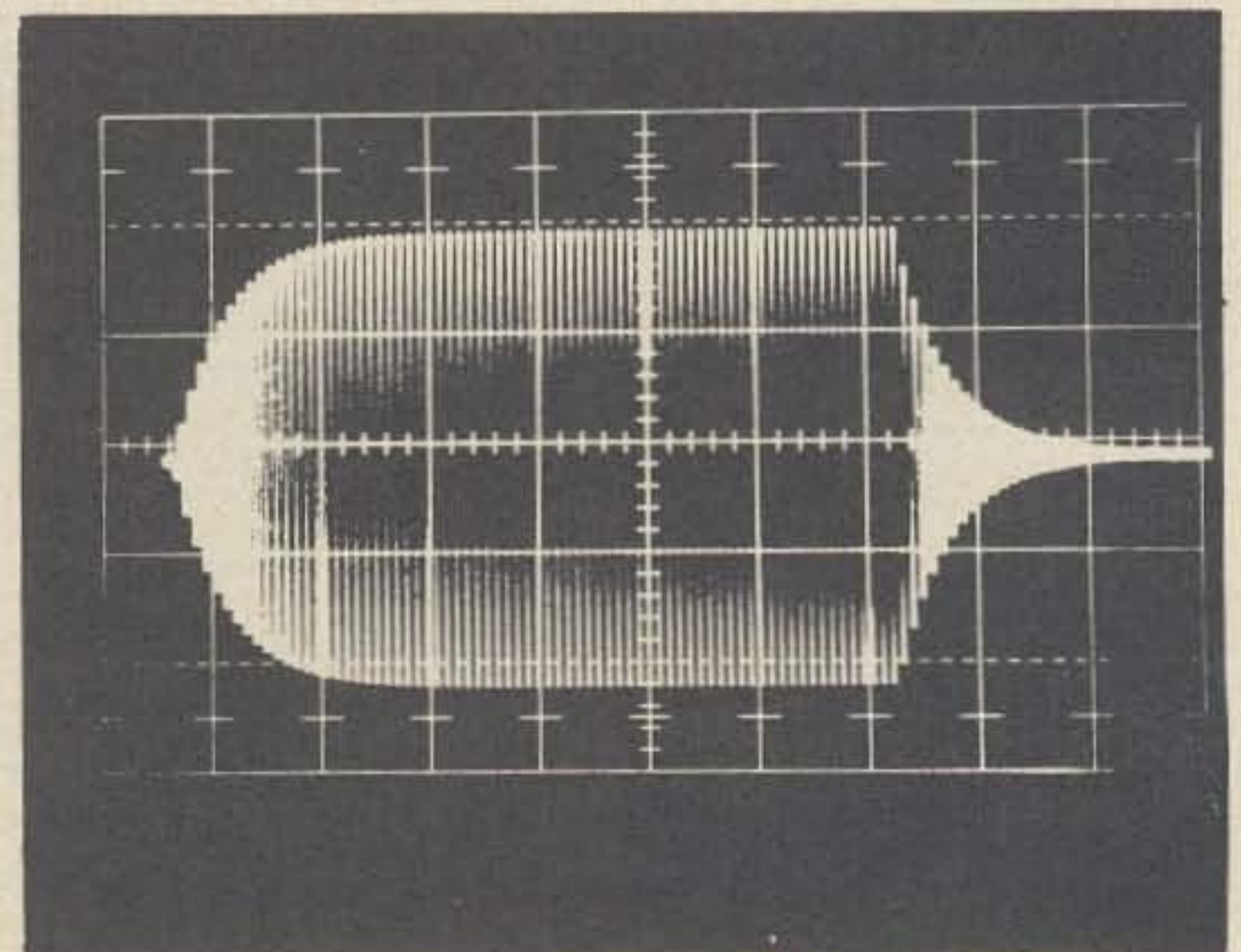


Fig. 5. Keyed waveform, $QxR = 1190K$. Horiz. = 20 msec/cm.

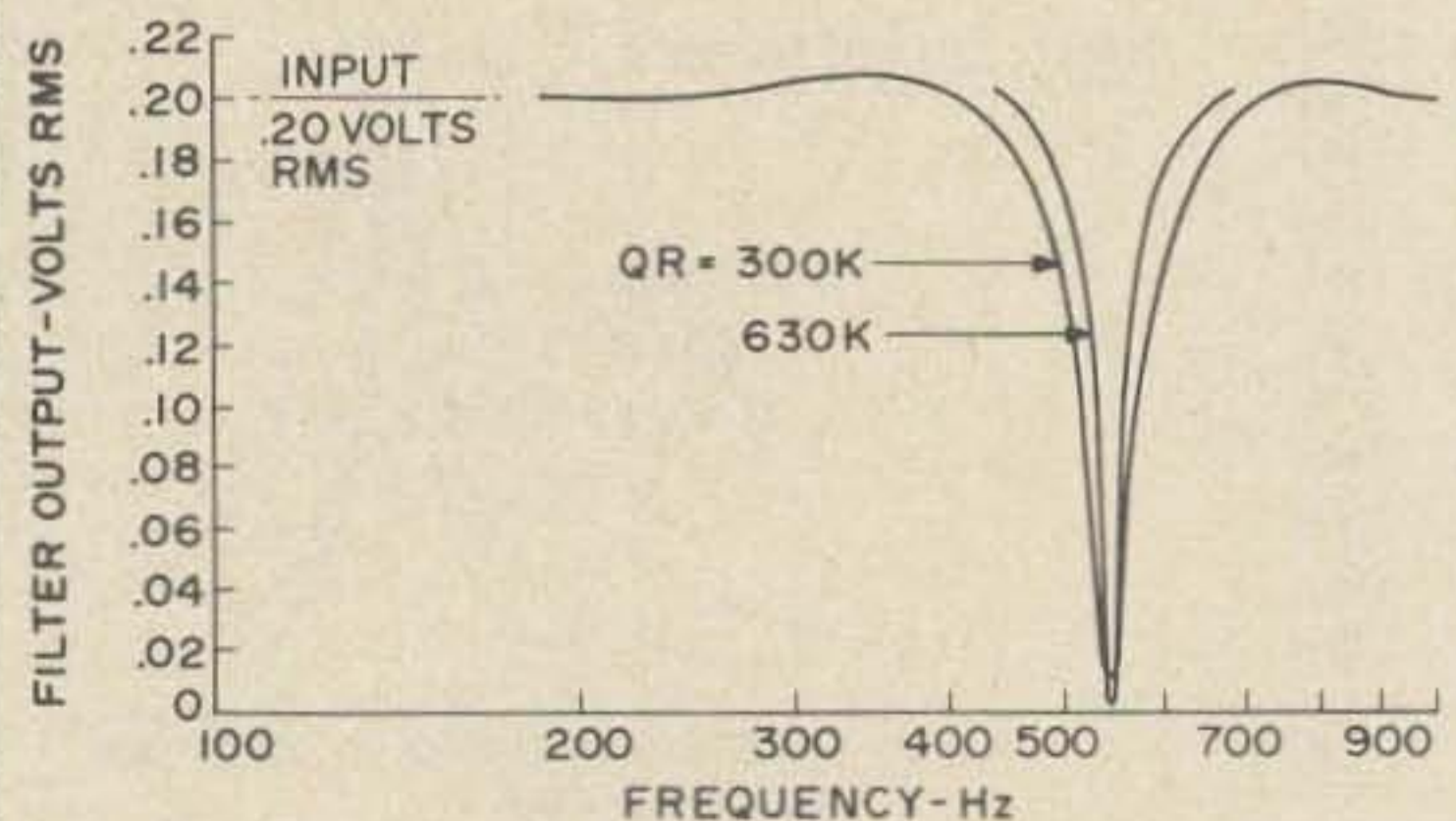


Fig. 6. Measured characteristics of the notch filter using different values at QxR .


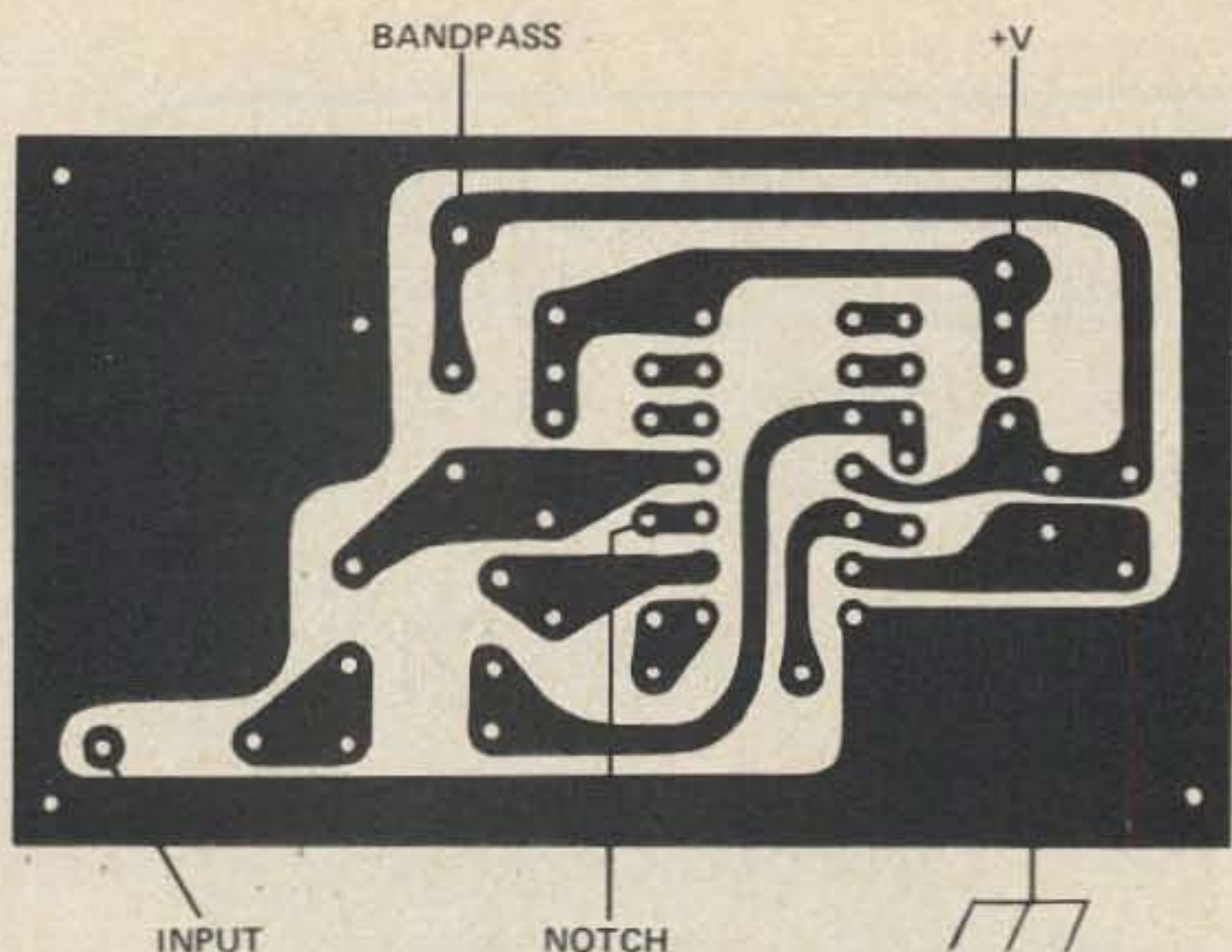



Fig. 7. Full size pc board layout (foil side) for the peak/notch filter.

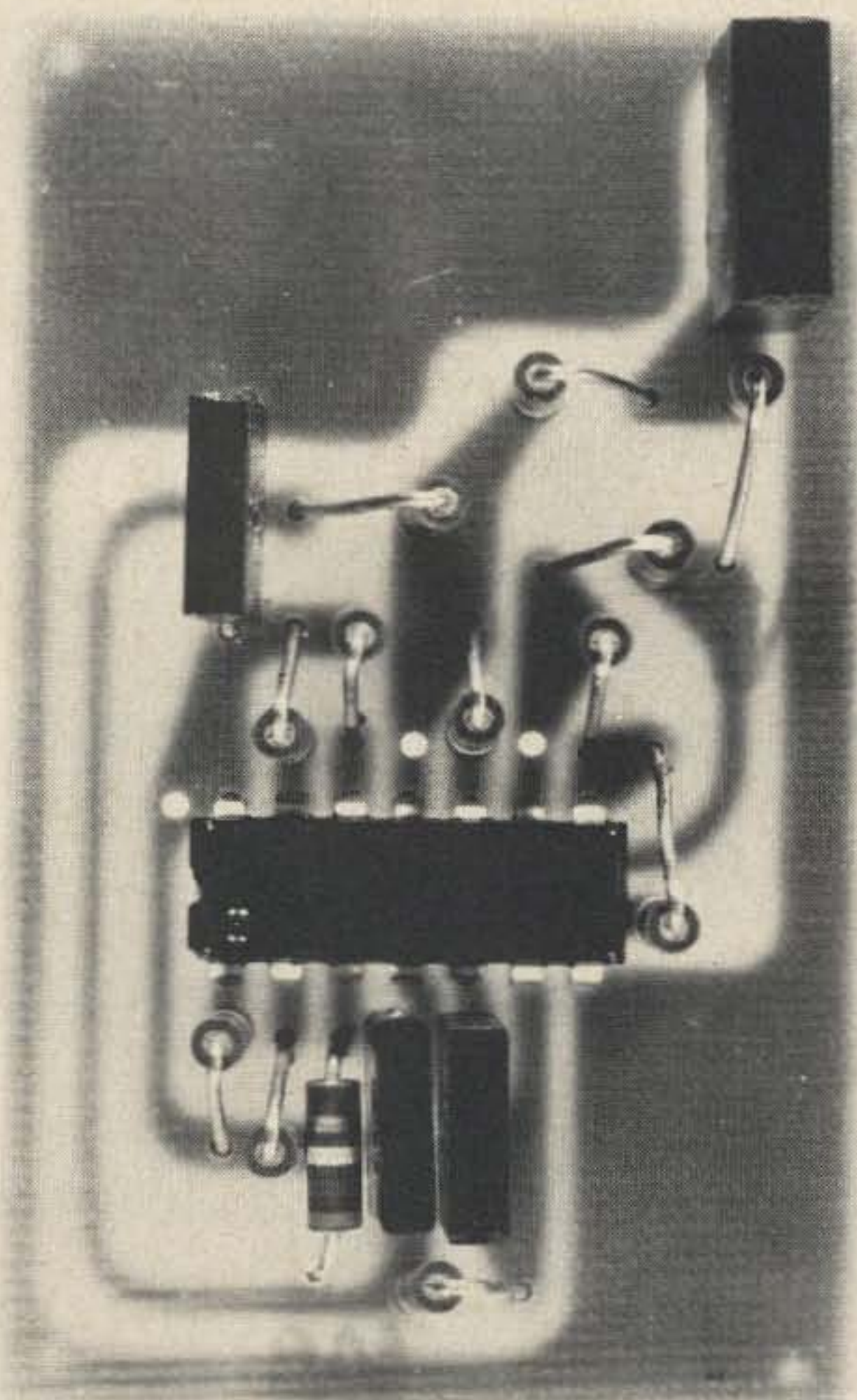For the unit shown $R = 62K$ and $C = .0047 \mu F$, which yields a center frequency of 540 Hz. The actual unit peaked/notched at 545 Hz. The measured performance of the peaking filter is shown in Fig. 2. The variations in bandwidth are achieved by varying the two resistors marked QxR. If these two resistors were grouped together, one could achieve variable bandwidth with



The input capacitor is at the top right in this photo.

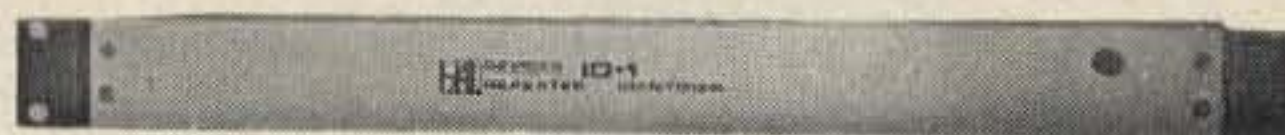HAL COMMUNICATIONS HAL ID-1 REPEATER IDENTIFIER



Circuit board wired & tested \$75.00
With rack w/cabinet \$115.00
TTL logic. Power line frequency counter for 3 minute or less timing and control. Easily re-programmable diode ROM uses only 27 diodes (depending on call) to send DE "any call". Low impedance audio with volume and tone control. All circuitry including PS on small G10 glass PC board. Write for full details. HAL COMMUNICATIONS, Box 365L, Urbana IL 61801

30 Hz Selectivity!



" . . . a must for anyone using an inexpensive receiver or a sideband transceiver on our crowded CW bands."

(73 Magazine test report)

Our Q-BOX audio filter features: Bandwidth CONTINUOUSLY VARIABLE from 30 Hz (almost 100x sharper than most xcvs!) to 2 kHz. Active filter (no coils). No insertion loss. Not a breadboard. Ready to plug into ANY rcvr/xcvr. Drives phones or ext. spkr. amp. Full instructions. In use worldwide. Plug one into your receiver today! . . . Only \$17.95 + \$1 shipping in U.S. (Add Sales Tax in Cal.) 10 day moneyback guarantee. SEND FOR FREE LITERATURE AND TEST REPORTS.

AUTEK research
Box 1494L, Canoga Park, California 91304

only one central knob. The gain of the circuit is nearly unity but it can be varied as described in the Motorola Bulletin.

The 6 db bandwidth of the sharpest filter tested was 66 Hz. Figures 3, 4 and 5 show the keyed waveform of the three bandwidths shown in Fig. 2. The keyed waveform is clean and sharp with rise and fall times determined by the filter bandwidth.

The notch characteristics of this filter are shown in Fig. 6. The gain of the filter outside the notch area is close to unity. A single pole double throw switch can be used to switch from bandpass to band reject, depending on the nature of the received signal. For example, bandpass would be best for CW while band reject could eliminate an undesired CW signal near a single side band signal without destroying the information content of the SSB signal.

Fig. 7, gives a full size template, foil side, for a printed circuit board. The price of the MC3401P operational amplifier is near a dollar, truly a bargain for such impressive performance.

. . . W6AGX



SEND FOR NEW
1973½ CATALOG

GREGORY ELECTRONICS CORP.

The FM Used Equipment People.


249 Route 46, Saddle Brook, N.J.07662

Phone (201) 489-9000

6 Meters — Excellent Condition!


Motorola Special Model X71GJT-1190B,

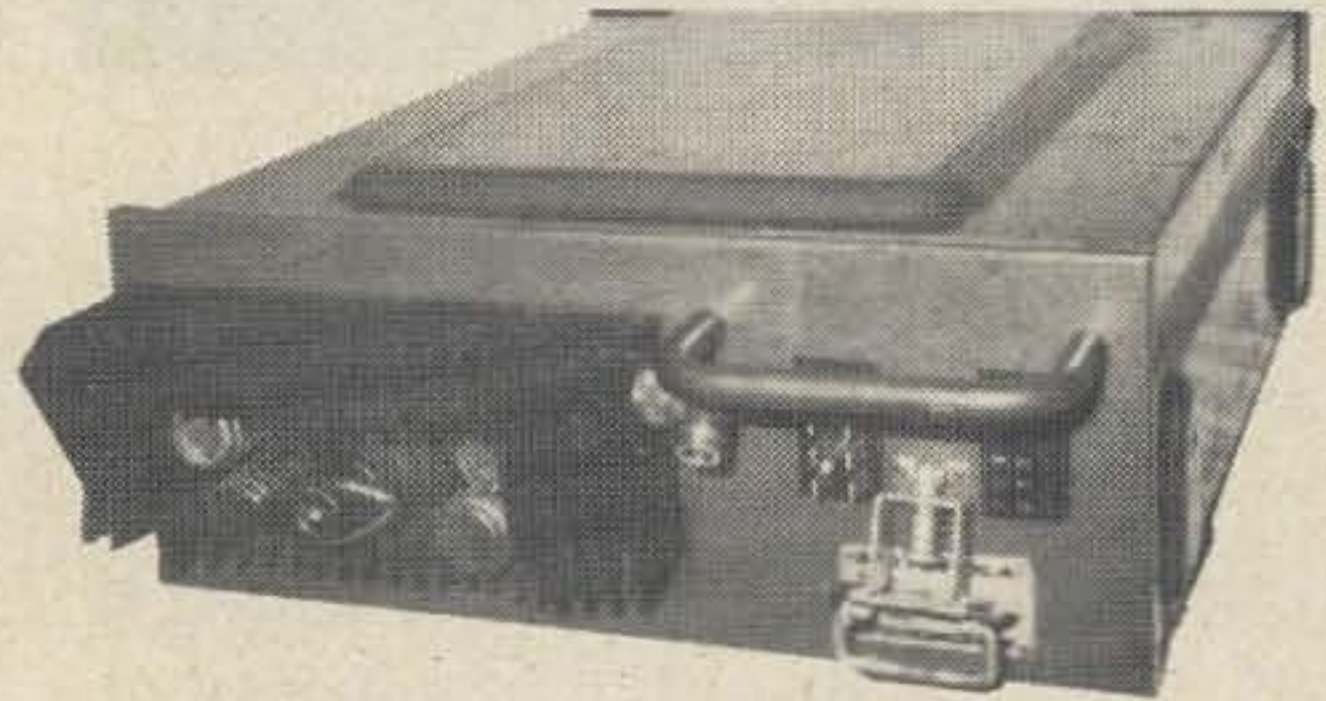12 volt transistor powered mobile in 15" case, 100 watts. 2 Freq. transmit and 3 freq. receive capability. 2 Freq. Tx. and 2 freq. Rx. on 40-50 MHz. range; a separate Rx. front end allows a 3rd Rx. freq. on 30-40 MHz.



With accessories . . .

\$228

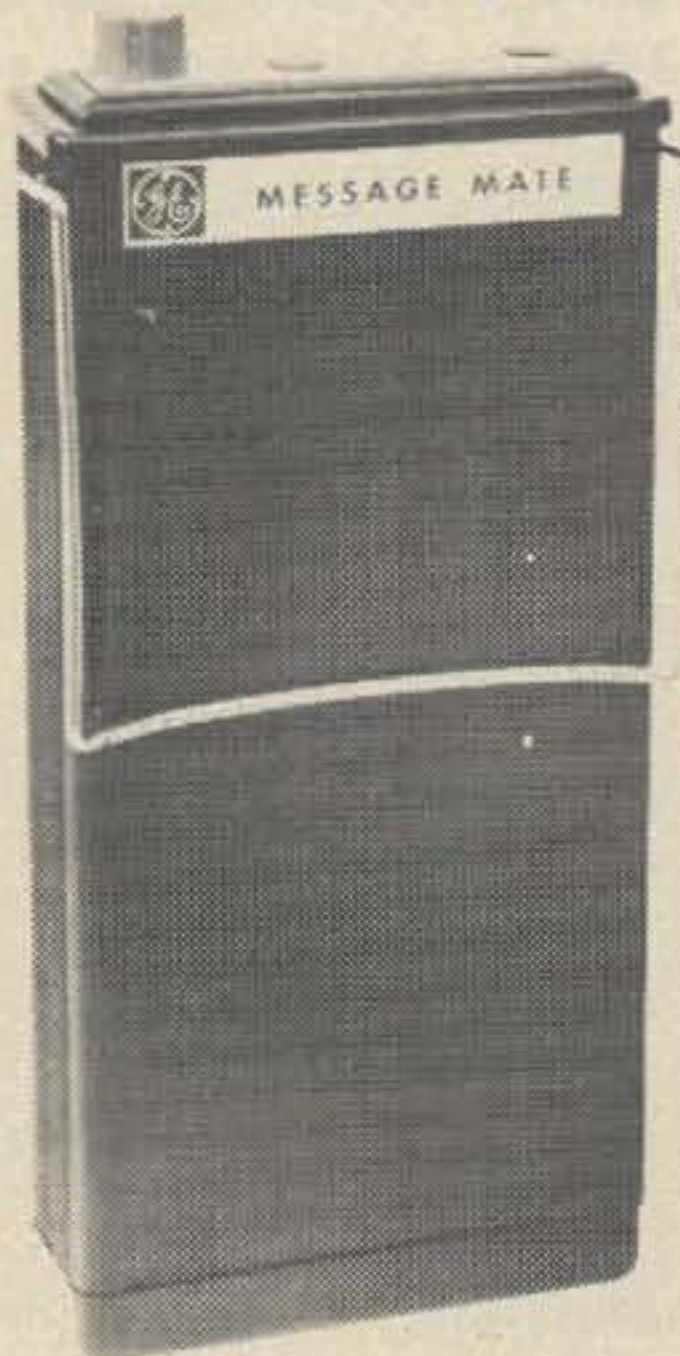

The General Electric

Message Mate

personal pocket
voice receiver
with sel-call

150-162 MHz, 162-174 MHz

Specify Frequency Range When Ordering.

\$78 less reeds

(Charger included with nickel-cadmium model)

With new mercury battery . . . **\$68**

Ask about low band models.

- Fully transistorized, 100% solid-state for the ultimate in reliability and performance.
- Selective signaling options provide for individual messages both inside and outside of buildings.
- Operates in full compliance with Part 15 of the FCC rules.

POWER FAILURE PROTECTION

Protect your QTH from the Energy Crisis!

Power interruptions in heavily-loaded and densely-populated areas are seldom simple on-off phenomena. In many residential areas if the power goes off for more than a few seconds it may take hours to restore complete service, even though the initial cause of the outage is corrected promptly. Because of the dependency of our modern culture on electrical power, extended outages can paralyze large areas, stopping everything from traffic lights to electric can-openers.

This extension of simple outages is brought about by the non-linearity of many electrical devices. Their starting current is many times greater than their running current. Many motors, for example, have starting currents from three to ten times their full-load running current. Lamps, similarly, and nonlinear having a cold resistance of from one fifth to one tenth their hot resistance.

In consequence of these characteristically heavy starting currents, if the power fails in a heavily-loaded area perhaps due to systemic overload, restoration of the power is likely to impose an immediate load several times greater than it was at the moment of interruption. This is likely to precipitate another outage beginning a vicious cycle which can only be broken by sectionalizing the loads at the power house or at some

convenient substation. Such repeated outages have occurred several times during the past few years in a number of our larger cities.

Remedial measures

When the power fails for any reason a recurrence of the failure on restoration of the power can be prevented if all power users turn off all heavy loads immediately. When the power has been restored the heavy loads can be turned on again, one by one, without imposing too great a starting load on the system. This simple instruction is much easier to give than to follow.

Automatic shutoffs

Because most power outages occur at odd times when "the man who knows what to do" is at work, out for a beer, or otherwise unavailable, some sort of automatic shutoff

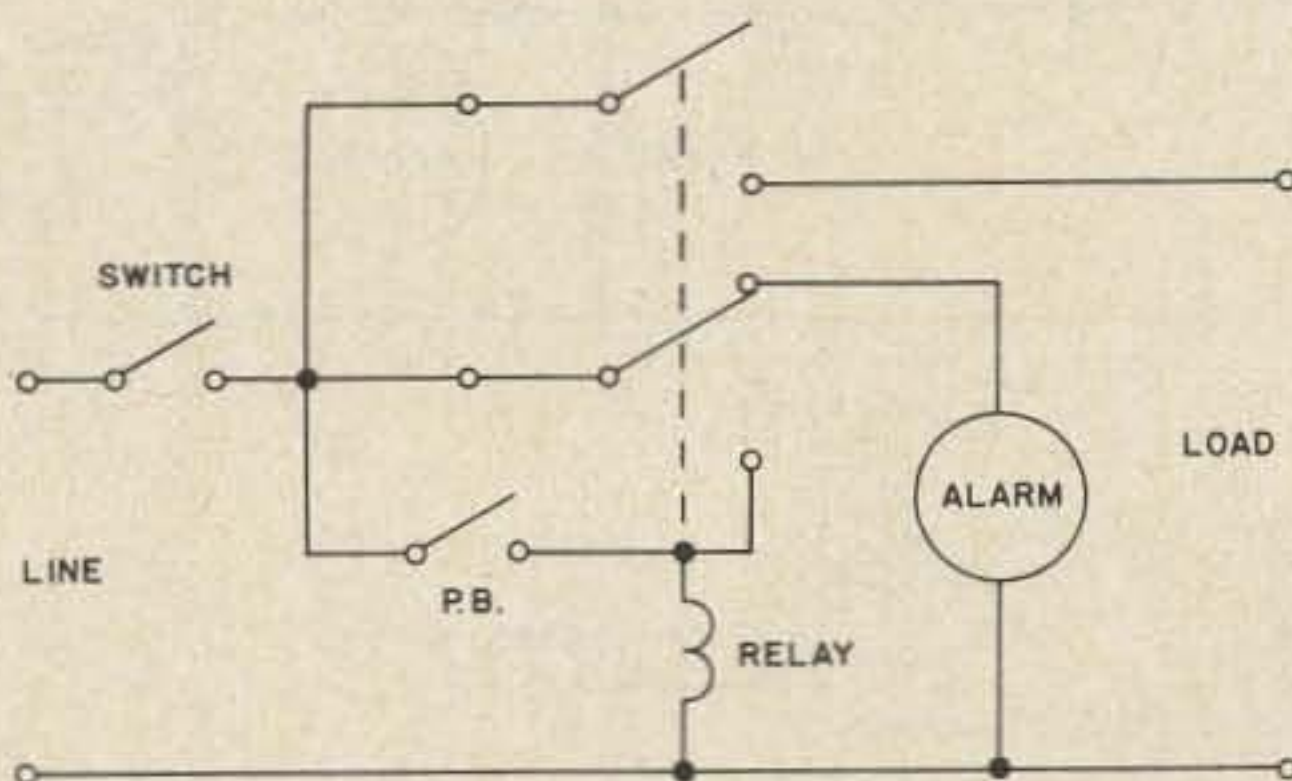


Fig. 1. Circuit of automatic shutoff.

for heavy loads such as deep-freeze, air conditioners, electric ovens, etc., is desirable. Most fortunately, such devices are relatively simple and not too costly, even for loads of up to 25 amperes (or more).

Circuit of one smoothly-working automatic shutoff which effectively disconnects the load from the line whenever the power fails, and which does not reconnect it when the power is restored, is shown in Fig. 1. This is one form of the self-holding relay circuit.

In operation with the power on the load is not connected until the switch is closed, and the push button momentarily depressed. This energizes the relay, connecting the load through the upper armature contact, and connecting the coil to the high side of the line through the lower armature contact. Opening the switch turns the load off.

If the power fails the relay armature releases, disconnecting both the load and the relay coil from the line, and putting the alarm in circuit. This can be anything from a neon lamp to a raucous ac buzzer. When the power is restored the alarm is energized, but the load is not. Depressing the push button momentarily reconnects the load to the line and deactivates the alarm so that the load operates normally until either it is shut off or the power fails again.

Higher power shutoff

Many relatively large lelectrical loads such as building air-conditioners, cannot be started merely by connecting them across the line, but must be run up to speed by use

of a control box or Variac. If the power is interrupted while they are running, and then restored, they tend to either pop the breakers, or to run at half speed and high heat eventually damaging the motors. They must be started each time from Variac zero.

Although some of the more modern air-conditioners have an automatic starter which gradually speeds up the motors when the power is applied keeping the current drain from the line within safe limits at all times, many systems now in use do not have this convenience and need protection in event of power failure. Circuit of an automatic disconnect so that the Variac must be returned to zero before the system can be started or restarted, is shown in Fig. 2.

Here we again use a self-holding relay in conjunction with a push button and a Microswitch controlled by a cam on the Variac shaft. When the Variac is set at zero, and only then, the pushbutton is connected to the line so that it can close the relay circuit. Once this is closed it is self-holding and the Variac is energized so that the motor can be run up to speed by the Variac control.

If the power fails, the relay releases, disconnecting itself, the Variac, and any load controlled by it from the line; and connecting the alarm. When the power is restored the alarm is energized, but the load cannot be reenergized until the Variac is set to zero which closes the Microswitch so that the push button is operative. The alarm automatically reminds the operator to either turn off the switch or to complete the starting cycle.

Construction and workmanship

Both of the devices here outlined are of a safety, or "insurance", nature. In consequence, they should be built with considerable care using components chosen with an adequate margin of safety. Layout should be chosen for maximum convenience of operation and construction be such that checking and maintenance are easy. Local electrical codes should be followed as closely as possible. If the local code does not cover, "due diligence" will be demonstrated if you follow the National Electrical Code.

... Ronald Ives

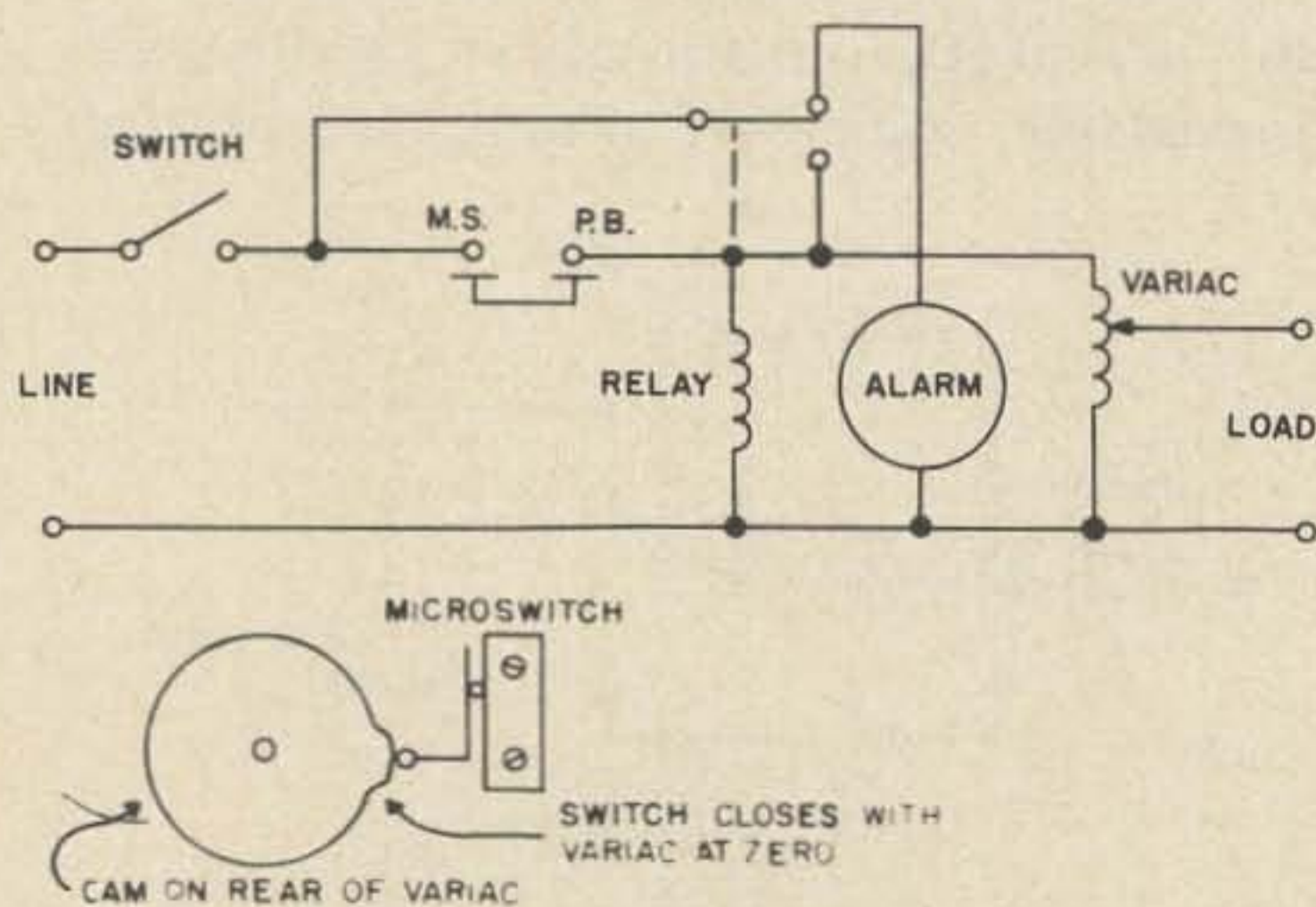


Fig. 2. Automatic disconnect for Variac starters.

160m ANTENNA COUPLER

Donald C. Mead W2LT
235 South Irving Street
Ridgewood NJ 07450

Work DX on 160m with a 2 meter beam

One-Sixty! Aw, come on, man, that's dc. No, I've never tried it. After all, who has a back yard big enough for a dipole that big!"

Doubters, rejoice and take heart. It is possible to give off good vibrations from a teeny wire on top band, if you know how. First, you must overcome the wavelength gap. That is, think positively and accept the fact that an antenna doesn't have to be self-resonant. Seems like we've been brainwashed to the point where antenna means a half wave center-fed dipole. Look at it this way: an antenna wire can be simply one plate in the capacitor of a parallel-tuned circuit. The other plate, as you can probably guess, is earth ground. Add a coil to resonate with the capacitance and you have a radiating system. Figure 1 shows the derivation, step-by-step.

As every Novice knows, the circulating current in a parallel-resonant circuit is maximum at resonance. He also knows that the more rf current in a conductor, the stronger the field around it. Thus, if you build a giant parallel-resonant circuit, say 30m or more in diameter, and pump rf through it, some of the rf will leak off and cause a desirable disturbance in a receiver a surprising distance away. If you tune the circuit to the same frequency as the pump (the transmitter) current and field strength are greatest.

As mentioned earlier, one capacitor plate is earth ground. The other plate is any metallic object spaced and insulated from ground. It can be a coax-fed doublet, a two-meter beam or just about any imaginable aerial adornment you're using on the other bands . . . just be sure it isn't grounded

outside the shack somewhere. If you have more than one antenna, you can connect the feed lines together. The more the merrier and the more capacitance to ground. In the case of coax-fed antennas, connect the shield to the center conductor and treat it as one wire.

In order to get rf into our newly discovered antenna circuit, we must solve the problem of matching a low impedance transmitter to a high impedance antenna. This turns out to be no problem at all if we take advantage of the fact that the inductance of the antenna circuit is available in the shack. Although we could wind a low impedance link on the antenna coil, it turns out to be far easier to let the transmitter share part of the antenna inductance, using the principle of the autotransformer. That is, in the same way you can tap off a small voltage from a large voltage, using a resistive voltage divider, you can tap off a small impedance from a large impedance using an inductive impedance divider.

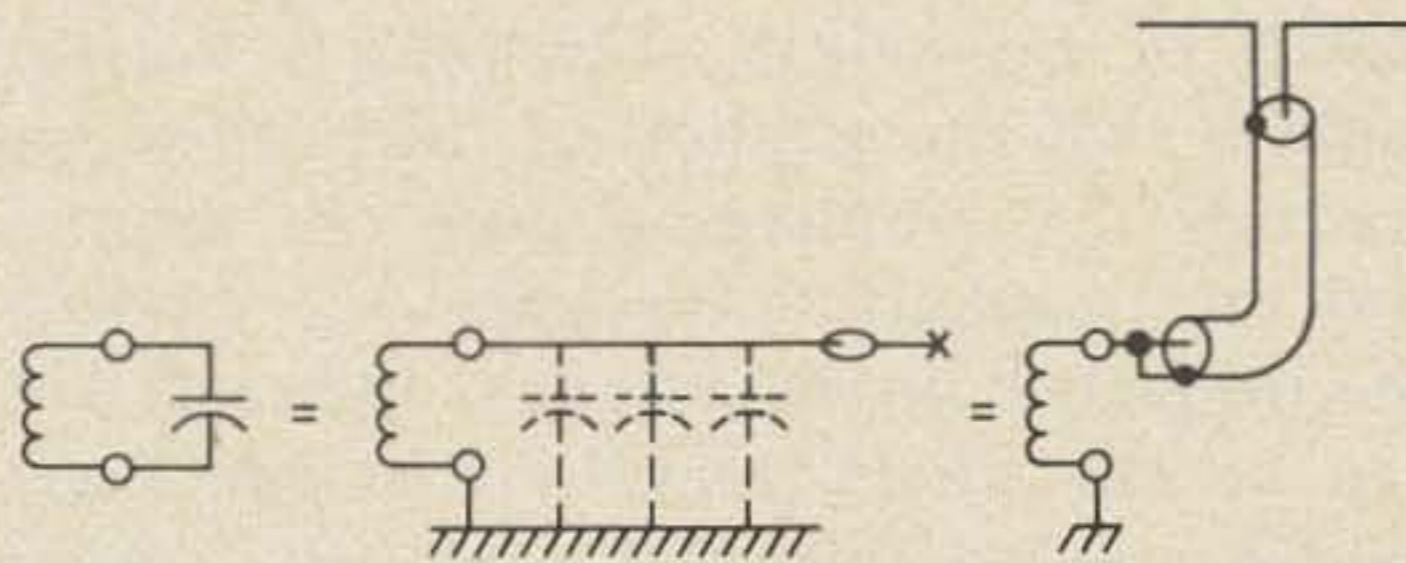


Fig. 1. An antenna is equivalent to a tuned circuit.

Enough theory! Let's get down to the nitty-gritty of practical circuits. And how simple it is! All that's required is one coil, two alligator clips and an rf current indicating device. The latter may be an rf ammeter, say 0-30A or so, or can be a couple

PHONE ORDERS

NOW ACCEPTED FOR
1 DAY C.O.D. SHIPMENT
 ON ALL OUR
PRE-AMPS
 AND SOME OF OUR
CONVERTERS
 AND
FREQUENCY SYNTHESIZERS

If you need a low noise pre-amp in a hurry for communications or instrumentation, we can fill your order custom tuned to any frequency from 5 MHz. to 475 MHz. within 24 hours by air mail or special delivery. All you pay is our regular low price plus C.O.D. shipping charges. This rush service is also available on some of our stock converters and frequency synthesizers. To place an order or for information on any of our products call us between 9 A.M. and 4 P.M., Monday thru Thursday except holidays (no collect calls please). If line is busy keep trying.

PHONE: 212-468-2720

VANGUARD LABS 196-23 JAMAICA AVE.
 HOLLIS, N.Y. 11423

of pilot lamps wired in parallel to share the current.

Figure 2 shows the lash-up. For operation on the 1.8–2.0 MHz band, the winding should be at least 5cm in diameter, about 13 cm long (the bigger the coil, the better) and have about 40 or 50 turns of bare or tinned copper wire. About any old coil will do. If you can't find one in surplus, wind it yourself.

Setting the taps on the coil is largely a matter of cut-and-try. The thing to keep in mind is that the position of the bottom tap controls the coupling between the antenna and the transmitter; the upper tap controls the resonance of the antenna. Although you can do the whole thing by trial and error, having a vswr meter in the coax line between the transmitter and the coil makes life simpler. If you have a grid-dip meter as well, it's a real breeze.

With test equipment, proceed as follows:

1. Connect the bottom of the coil to ground. This can be the plumbing in your house, a ground rod or whatever you use for a normal ground connection.

2. Connect a jumper from the outside plug shell of the coax line of your antenna to the center pin of the plug. Connect the shell to an alligator clip connected to the 30th turn from the bottom of the coil.
3. Couple a grid-dipper, tuned to 1.8 MHz, to the coil. Adjust the top tap by selecting a greater or lesser number of turns with the alligator clip until resonance is achieved.
4. Connect the coax outside braid on the line from your transmitter to the bottom of the coil (ground). Connect the center conductor to the 10th turn of the coil, using an alligator clip.
5. Turn on the transmitter (tuned to a vacant frequency) and adjust the bottom tap and the transmitter loading control for minimum reflected power. Be sure you don't exceed the maximum transmitter power input for your geographical area.
6. Readjust both taps until you have maximum antenna current and minimum reflected power.

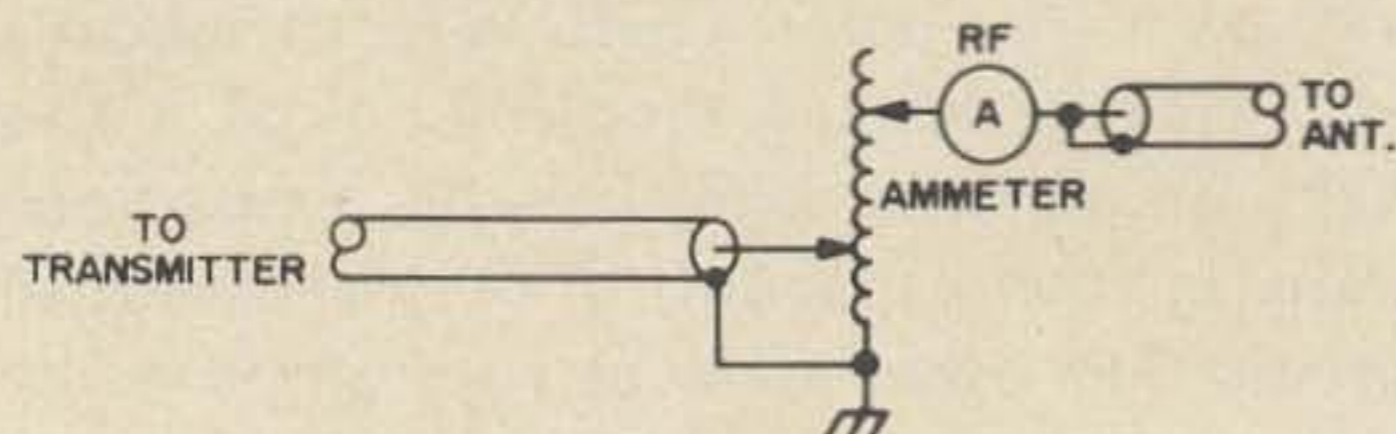


Fig. 2. The tuning system.

With no test equipment, simply adjust both taps and the transmitter loading control until you get maximum antenna current for any particular value of plate current.

High rf voltages are present in the circuit under key-down conditions, even with moderate transmitting power. Therefore, play it safe and do all your adjusting with the key up.

If you are a newcomer to 160, be sure to check the regulations on sub-band frequencies available and the maximum daytime and nighttime input power restrictions that apply to your state.

So, come on in and join the fun. 160 is open to both phone (mostly SSB) and CW. Even the most jaded DX-chaser will get a real kick out of working across the Atlantic when the signals start pouring in on those cold winter nights.

...W2LT

Richard W. McKay K6VGP
29315 Stonecrest Road
Rolling Hills Estates CA 90274

THE HT 120: ONE UP ON MOTOROLA

The relationship of the hand units with the silver dollar at the right is one of size comparison only.



Owning the very latest in Handi Talkies had always been the apex of many FMer's ambitions. I myself have looked on, green with envy, as one of my buddies showed me his new six channel five watt HT220; but the price stopped me dead. Well, if you aren't rich, but are the type who likes to be the first on your block with a new goodie, try this on for size: An HT with one watt output (minimum), receiver rated at $.3.35\mu\text{V}$ for 20 db quieting, Private Line, six channels, and even Touchtone, all in a box the size of an overgrown package of cigarettes and costing less than \$200! I should have you hooked, so read on.

Recently HT220s seem to be showing up everywhere.

It should be noted that the circuit boards that form the heart of these units are not always perfect, but whatever the problem they can usually be fixed. As an example, the circuit boards are constructed without trimming each component lead individually as it is installed. At the end of the production line a saw is used to trim all the leads simultaneously. Occasionally the saw takes a nip out of the board itself, forcing quality control to reject it. On others, a small wire jumper or component may have been installed on the rear of the board to circumvent a board problem; and although the board may

have been removed from a working and tested unit, Motorola, tightening their quality control, will no longer allow these jumpers in units offered for sale.

In these cases the unit is disassembled and Spectronics acquires the completed circuit boards for resale to amateurs. With a complete HT220 board, new case, parts, controls, hardware and the manual, you can come pretty close to rolling your own.

The basic HT220 is a compact single frequency version, rated at 1.8 watts output. Slightly larger housings make available such options as a 5 watt output deck (capable of up to 10 watts), Private Line, two, four or six frequency capability, and even Touchtone; or varying combinations of all of these.

By the time I was aware of all of this, I had already completely remade my HT220, and since the HT220 with all the additions of my HT200 would be close to the same size, I decided to hang on to my HT200 until I could acquire a radio that would represent a significant reduction in size.

Thus, I was quite happy until one night at SAROC in Las Vegas. While I was wandering around, I managed to stumble into a Motorola HT100. That's the little critter about half the size of the HT220, but rated at only 100 milliwatts output. I had once



The upper left corner of this picture shows the stock Motorola PL deck, which slips into the niche in the back of the unit. In the lower right corner is the PL reed plug.

considered the HT100, but thought the power output too low for reliable coverage. As the little gadget was discussed it was plugged into a wattmeter and checked out at 1.8 watts!

Well that took a little explaining. It seems that the HT220 and the HT100 share the same circuit board. The only real difference is that in the HT100 the final output transistor is eliminated and the driver is matched to the antenna for 100 milliwatts output. In addition, a higher impedance speaker is installed to lower the battery drain and a much smaller battery is installed, form fitting the case at the rear of the circuit board rather than below it. In this case the HT220 board had been installed in the HT100 housing and presto, the birth of the HT120 (HT120 is my own personal designation for the unit.), a 1.8 watt HT100.


There is of course an obvious fly in the ointment. Motorola portables are designed with an eight hour 5-5-90 duty cycle (5% transmit, 5% receive, and 90% standby). This is Motorola's criteria for choosing the battery size for a particular model. In the case of the standard sized HT220 this requires a 225 mA battery. So considering the HT100 uses a 70 mA battery, the apparent normal duty cycle of the HT120 would be 2½ hours at 1.8 watts. In practice, however, I have found that I have been able to use the unit for more than a full day by carefully choosing my words, not being long winded, and by detuning the radio to one watt output, thus further reducing the battery drain. More about that later.

Well, I had to have one. Of course I needed built in PL and multi-channel capability, but I was sure that I could do that, so I ordered all the parts. I then acquired the manuals for both the HT100 (Motorola part #68P81065A25-A, and the HT200 (Motorola part #68P81059A20-B).

A note on crystal ordering. Don't be too concerned with an improper receiver i-f crystal for the 146-148 MHz range. Different i-f crystals are specified to prevent a harmonic from interfering with the intended receive channel. Although my unit does have the wrong crystal for the 146-148 MHz range (16.8 MHz), I have encountered next to no difficulty. I am currently receiving on 146.61, 146.64, 146.82, 146.94, 147.33 and 147.36. Of all of these frequencies the only one I have encountered any problem with was 147.33, on which I found a slight harmonic carrier a bit off channel; but it was so low in level that it was just barely detectible.

After installing the crystals that I could in their stock locations, I used the exploded view of the unit in the HT100 manual to assemble it. Then referring between the HT100 and the HT220 manuals I connected the various color coded leads to the frequency control switch, volume control, PTT switch and the battery case. I found a parcel of wires that had been connected to the PL board in the HT220 installation; I cut these off as close to the board as possible.

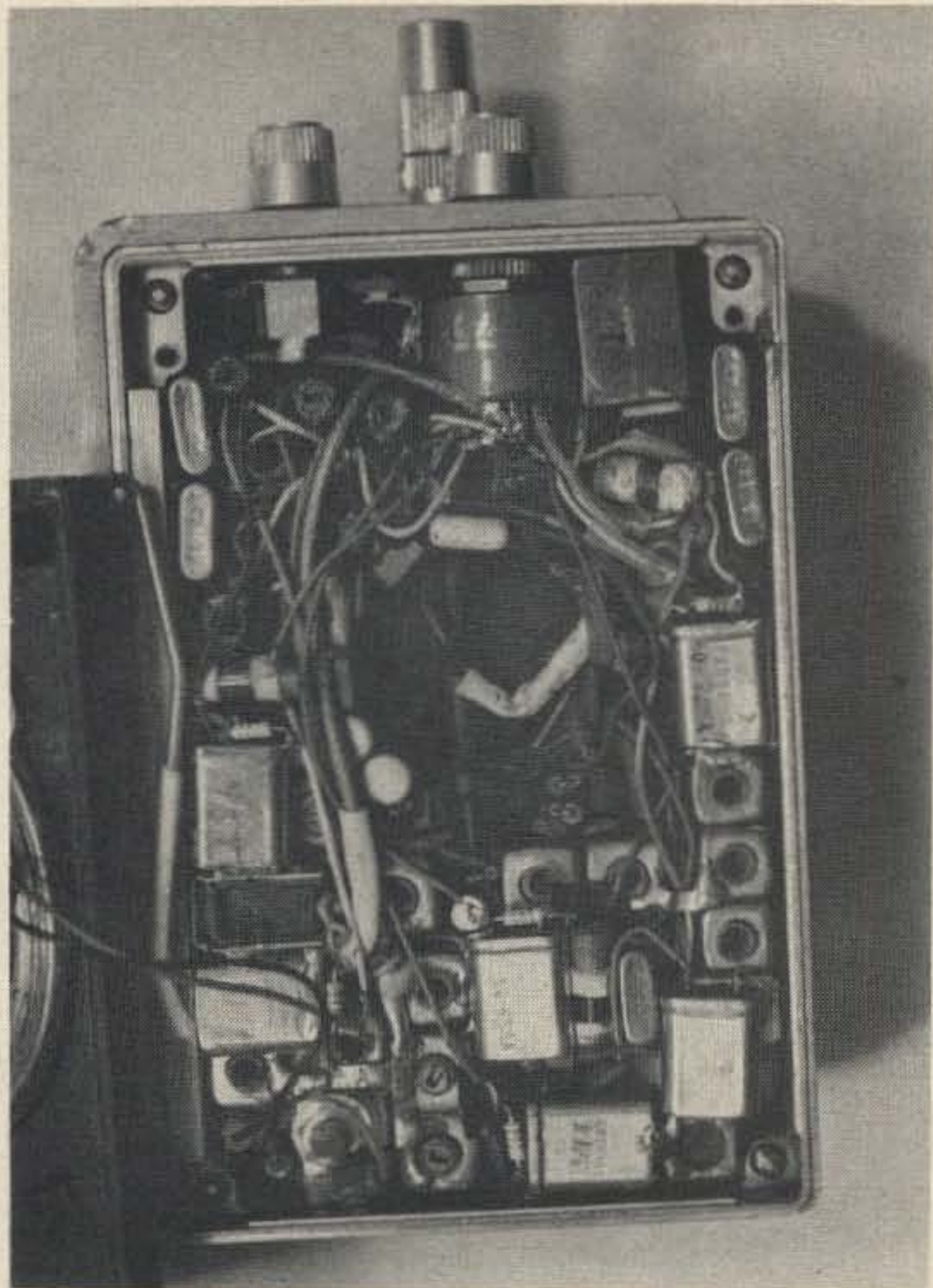Next it was necessary to remove the spring contactor that joins the coax output to the antenna on the matching case half,



If you take care, all those crystals can be sandwiched into the unit.

since they are in different spots in the HT220 and the HT100. There was one hole in the board in the correct place, and I drilled another to mate with the bottom half of the spring contactor. I then rerouted the coax and connected it to the spring contact, with the shield to ground (the metal case near the frequency switch). Next I connected R40 (the internal squelch control) to its corresponding wires. After checking the "A" line with a VOM to ground to insure a reasonable chance of having no problems, I connected 14V dc and turned it on for the smoke test. The first good sign was squelch noise.

It took very little tuning to get the receiver to better than its rated .35mV for 20 db quieting. The transmitter was just as easy. Considering the transmit time necessary for tuning, doing so on the battery could prove harmful. I would recommend a regulated current limited bench supply capable of 14V at 500 mA, such as the Heath IP 27.

The tuneup procedure was very straight forward, and I did not find it necessary to

add any padding capacitors to the unit. If you cannot tune to the factory specifications, refer to the manual for the value differences between the "H" capacitors (150.8-174 MHz) and the "L" capacitors (136-150.8 MHz) and add about 60% of the difference to the bottom of the board in the troublesome circuit and retune. I recommend 60% of the difference to optimize tuning in the 145-147 MHz range.

The largest caution in the tuning procedure is the current drain on transmit. I initially tuned my unit up on a bench supply without monitoring current drain. I was able to obtain three watts output, but found later that I was drawing in excess of 500 mA. Here again monitoring the tuneup on a current regulated supply will prevent many problems and save a lot of time. I found that even tuned to the rated 1.8 watts the current could range from 310 mA to about 500 mA.

I then correctly tuned the radio to 1.8 watts and 310 mA current drain, and connected it to the ni-cad battery. The battery proved capable of supplying the load, but it was obvious from the voltage drop that the battery couldn't handle this type of use over the long run. If you find 1.8-2.0 watts essential, the HT120 will reluctantly provide it for short transmit periods. I chose, however, to reduce the output to one watt, and through careful tuning and retuning of L107, 109, 111 and 112, I was able to minimize the current drain to 230mA. This will greatly increase the length of talk time available, and the time between replacement of the battery. Best of all it means that the output of my HT120 is less than 3 db worse than the standard HT220, and yet, 10 db better than the HT100, in the same size package — to me a reasonable compromise.

Next I decided to tackle the multi-channel problem. I wanted to try for six channels. The HT220 board makes the job an easy one, since all that is required to add channels is a crystal, a resistor, and a coil. I obtained the six channel switch, and installed it in the "squelch on/off/F1-F2 switch" position. Since my unit was a stock two frequency unit, I wired the first two switch positions to the circuitry already on the board. For the other crystal positions refer to the picture.

I first attached the load resistor directly to the leads of the crystal. I then soldered the crystal to a convenient transformer can to achieve both a mechanical mounting and an electrical ground. You will find many small spaces between the components on the board and the case where crystals can be placed on their sides and not interfere with assembly of the unit. I must caution you though, to use the most delicate soldering technique you can master. It is extremely easy to break the crystal within the case with even moderate heat. Next, I bent one lead of the crystal around and soldered it directly to its case. I then attached a teflon wire to the remaining crystal lead and routed it to the coil; the other lead of the coil being connected to the frequency switch. I placed two coils horizontally, one adjacent to the two stock receive crystals and the other next to the bottom of the unit. The remainder of the coils were placed in whatever holes I could find; primarily near the volume and frequency switch controls.

At this point you might wonder why I mounted the crystals and coils in the manner described and neglected that "chasm" between the frequency switch and the case. Looking again at the pictures you will find that this is where the subminiature reed for the Private Line oscillator mounts. If Private Line is not a necessity on your radio, I would indeed suggest this as an excellent place to mount both crystals and coils. Perhaps I should mention here that crystal lead length appears to be no problem. Several of my crystals are as far as they can get from the oscillator, and I have found no problem with them oscillating or getting them on channel.

To make the job more professional, I removed the stock two frequency escutcheon and took it to my jeweler. He was able to turn the plate over, elongate the holes to accommodate the volume and frequency switch shafts (the holes are slightly off center), and re-engage it with vol/off, F1 through F6, and my call. Although this cost \$7, I thought it worthwhile in ease of use and eye appeal.

As I mentioned earlier I needed PL in my unit. I decided to order the stock unit from



A belt clip fashioned from modified hair curler springs. The springs are epoxied into small holes drilled into the panel.

Motorola. The PL deck (Motorola part NLN 6801A) and the reed (Motorola part TLN 8904A) cost \$50, but I wanted the unit as professional as possible. Since I could never locate a picture of the HT100 with the PL deck installed several calls to Motorola gave me enough hints to get the job done.

The PL deck itself fits in one of the two niches in the section of the case that houses the antenna. The main body of the reed fits in that "chasm" I was talking about earlier, next to the frequency switch. The pins project through the circuit board, two of the pins going through holes you must drill. The reed plug mates to the pins of the reed from the non-component side of the board next to the frequency switch. The deck is then wired as per the instructions in the HT100 manual. A very simple connection to the transmit switched 14 VDC, ground and audio out.

This is perhaps the most unusual PL deck and reed that I have encountered. In many PL circuits the reed is under continuous oscillation since it usually takes about one to



A size comparison of the HT100 with the HT200 — big difference!

two seconds for the reed to “come up to speed.” This circuit and reed, however, receive no power until you begin transmitting, yet the PL tone is immediately at the full deviation level needed. On a modulation scope I could see no signs of any start up time, the full sine wave was immediately apparent. One other difference from most PL boards is that receive PL is not available. Due to space limitations the PL board provides a tone for transmit only, the receiver is not tone coded. This should be no handicap for repeater use, however.

A final addition to the unit is Touchtone. A year or so ago I developed a technique of adapting a Trim-line Touchtone pad to my HT200 using internal power. I later adapted the same Touchtone pad to my HT120 as a temporary Touchtone device. At the time I realized that I would eventually be using a much smaller device, but I did need tone control immediately. In mating the Touchtone pad with the HT I wanted a semi-permanent mounting that would allow the HT to be held in one hand with the push to talk activated, while the other hand was free to use the buttons on the pad. To accomplish this I mounted the pad in a small LMB box, making both the mechanical and electrical connection to the HT through a subminiature phonejack and plug. The bottom of the pad is stabilized on the HT

with small strips of “Velcro.” Luckily this technique for Touchtone was temporary, since the pad and box was nearly as big as the talkie itself.

I acquired a very small and reliable Touchtone device manufactured by Waller Electronics in Chevy Chase MD. John Waller currently has in production a device he calls the “Tesco pad.” It is available in kit form, wired or as a “sealed Tesco pad” (a sealed compact silver coated unit) for mounting on the HT220, HT100 or almost any other hand unit made. I acquired one of the latter specifically modified so that actuating a microswitch on the side of the pad converts the third vertical row to the fourth row using 1633Hz for additional control function. Unlike the Trim-line pad, this unit is more appropriately sized and covers about 65% of the surface area of the back of the HT120.

The pad I chose is the “sealed Tesco pad,” which I highly recommend if you are going to use it with a hand unit of any type. One of the primary problems in adapting the new hybrid Touchtone chips, such as this Waller pad uses, to ham use has been radio frequency interference. Of course if your needs are for a pad mounted on a dashboard, or with a base station, use of the standard kit or wired form is great. In a talkie however, the rf is within inches of the chip and RFI can cause the chip to change frequency and output level.

Initial tests with a chip mounted in an HT220 required extensive rf bypassing by trial and error to achieve a reliable tone output. Waller has gotten around this problem by producing a special RFI shielded package designed especially for hand units. The completed unit consists of the switch assembly and a machined piece of aluminum stock that provides mounting room for the integrated circuit, a tone level pot, and a row switching microswitch (optional). In this sealed pad the IC is actually removed from its case to make the package even smaller. After all the components are mounted, wired, and tested, the unit is potted, and then silver coated for rf isolation. No further shielding or isolation should be necessary.

As is the case of the PL board, the installation is very simple. One wire connects

CRYSTAL BARGAINS

Depend on . . .

We supply crystals from 16KHz to 100MHz. Over 6 million crystals in stock.



SPECIAL

Crystals for most amateur 2-Meter F.M. Transceivers:

\$3.75 Each

Inquire about quantity prices. Order direct. Send check or money order.

For first class mail add 15¢ per crystal...for airmail add 20¢ ea.

DIVISION OF BOB WHAN & SON ELECTRONICS, INC.

2400 Crystal Dr.
Fort Myers
Florida 33901
(813) 936-2397

Send 10¢ for new catalog with oscillator circuits and lists of thousands of frequencies in stock.

SPECIALS! CRYSTALS FOR:

Frequency Standards	
100 KHz (HC13/U)	\$4.50
1000 KHz (HC6/U)	4.50
Almost All CB Sets, Trans. or Rec.	2.50
(CB Synthesizer Crystal on request)	
Any Amateur Band in FT-243	1.50
(Except 80 meters)	4 for 5.00
80 Meter Range in FT-243	2.50
Color TV 3579.545 KHz (wire leads)	1.60
	4 for 5.00

Old Reliable Old Reliable Old

\$425.00 RX 1 ROTATOR \$425.00

10 years of proven service. The heavy duty rotator that will turn any beam array you want to install. Control box to match S Line. 115 VAC Selsyn Ind. 380 Degrees rotation. Limit switch unit is 9½" dia., 28" in height.

*Designed Built Backed
by*

ANTENNA MART
BOX 7 RIPPEY, IOWA 50235

SEE US FOR SALES & SERVICE REGENCY Electronics Equipment

Scanners for Fire • Police • Aircraft

A scanner for every need. We also have the HR-2 and HR-6 — in fact, the entire Regency Line.

Call NOW and HEAR OUR DEAL

617-838-2984

SAWYER'S RADIO SERVICE

48 Linden Street Berlin, MA 01503

to the transmit switch 14V, one to ground and one to the audio input. The pad comes with four tapped holes and matching hardware for mounting on various talkies. In the HT120 installation only the top two of these screws are used since the pad must be mounted on the rear of the talkie over the battery. To mount the pad this way we must modify the battery so that we can remove it by pulling it straight downward rather than lifting the bottom out as it was originally designed. To accomplish this first remove the clip from the battery, hold down the screw so it can be unscrewed all the way. Secondly, cut off the ridges at the bottom of the antenna slot on the underside of the battery pack that inhibit the battery from being pulled straight down. Once you are sure that you can move the battery in and out without first having to lift the bottom away from the talkie you are ready to mount the pad.

After removing the back from the talkie drill two holes, one in each niche on either side of the antenna slot. These holes are as close as practical to the battery compartment. One additional hole must be drilled to accept the three color coded wires. On my HT120, due to the curvature of the rear of the unit, I had to make two other alterations to make the bottom of the pad fit flush with the battery pack without any bottom pad mounting hardware. First, I used a small shim properly positioned between the two mounting screws to tilt the bottom of the pad towards the talkie so it exerts slight inward pressure against the battery. Secondly, since the case bulges out slightly I marked where the outline of the pad meets the battery, and within those limits, I carefully ground away a tiny pit of plastic by trial and error until I could slip the battery in under the pad with a flush all-around fit.

Now with the hardest part behind, simply connect the three wires as illustrated in the supplied data. Leads should be kept as short as possible, but that is the only precaution necessary. The audio level is easily adjusted through a hole in the side of the pad without having to disassemble anything.

...K6VGP

SSTV - ISB

Transmit video on one sideband and audio on the other.

Independent Sideband (ISB) is authorized to be used by amateur radio stations. This is a method of transmitting and receiving two signals on the same frequency. Regulations permit the transmission of voice on one sideband and video on the other sideband of one carrier frequency.

There is nothing particularly complicated about the generation and demodulation of ISB signals. There are many handbooks published on "sideband." With this information available as a guide it is easy to build equipment to generate and receive ISB or to add equipment to your present transmitter and receiver.

One of the easiest methods of transmitting and receiving ISB is to use two single sideband transmitters and two single sideband receivers which are tuned to the same frequency. Several slow scanners, who have the equipment, have used this method to generate and receive ISB. Fig. 1, shows the method where one transmitter and one receiver is tuned to the upper sideband and the other transmitter and receiver is tuned to the lower sideband.

Figures 2 and 3 show the method used at W7FEN's station to generate and receive ISB using a KWS-1 transmitter and a 75A4 receiver. This required a minimum of modification to the transmitter and receiver. The KWS-1 transmitter only required a small wiring change, the addition of a relay and a small switch. The switch was mounted in place of the dial drag knob shaft. A cathode follower was added to the 75A4 receiver on the chassis at the center rear.

The relay switches the transmitting ISB exciter to the 250 kHz injection plug in the

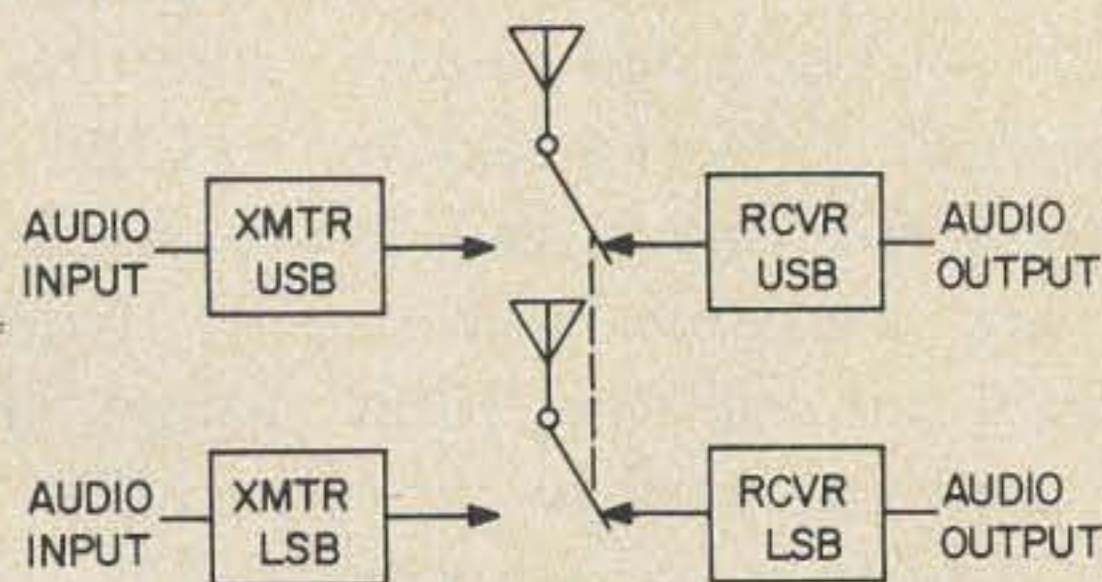


Fig. 1. Independent sideband using two transmitters and two receivers.

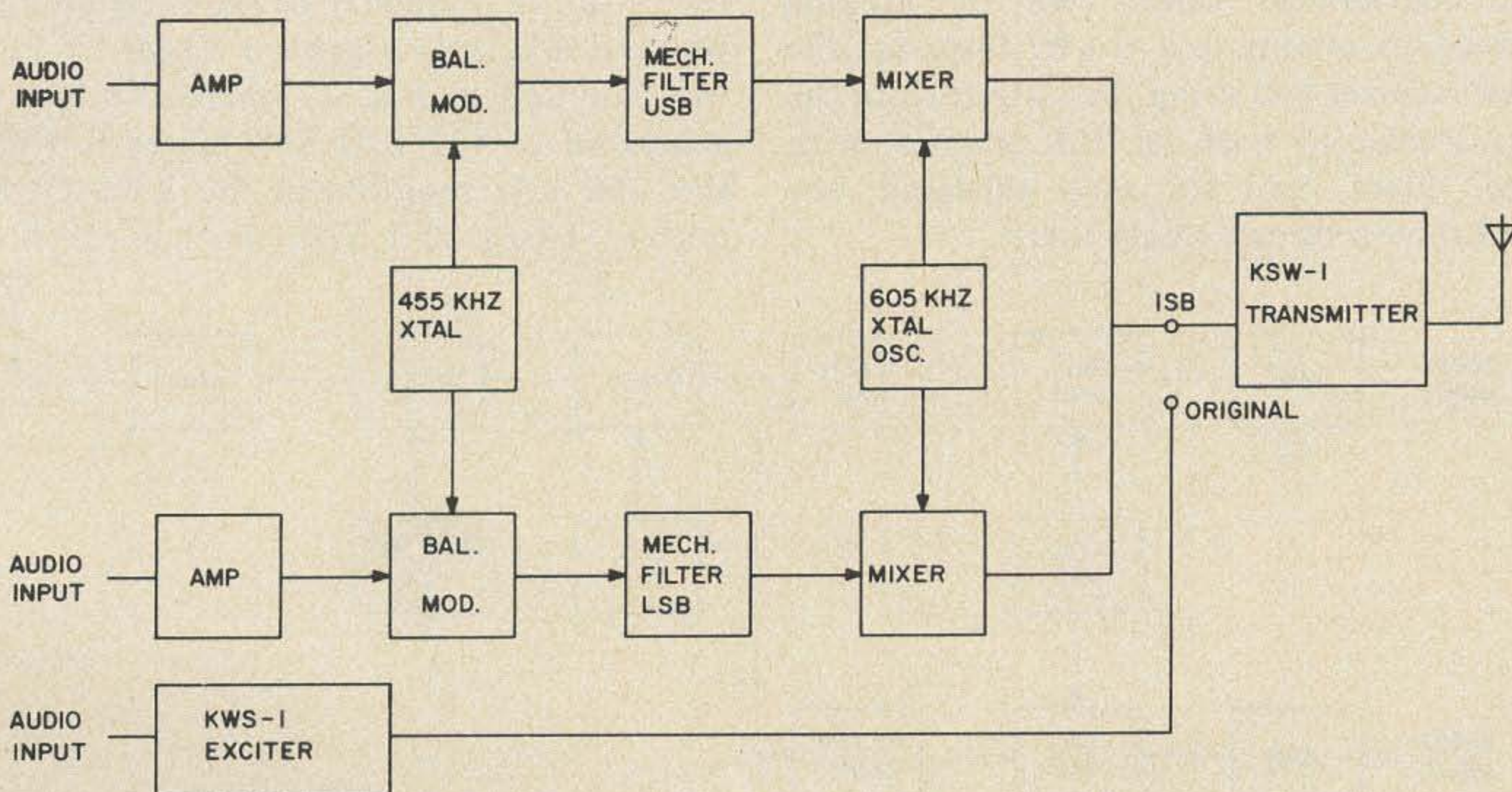


Fig. 2. Addition of ISB adapter to KWS-1 transmitter.

**IF YOU REALLY WANT THE BEST,
YOU'LL JUST HAVE TO ACCEPT THE FACT
THAT IT'S GOING TO COST YOU A LITTLE LESS**

***It's the little things that
make a GTX the value it is:***

- Operation over the entire 2-meter band (including MARS and CAP frequencies) *without* tuning
- No automatic shutdown on SWR bridge. Operate with mismatched antenna *without* damage, due to balanced emitter output transistors
- Lowest AM detection level of any comparable unit (including many commercial rigs)
- Power: the GTX-2 and GTX-200 boast 30 watts nom. output
- Lightweight: manufactured to aviation industry standards
- High-sensitivity receiver pre-amp included as standard (GTX-2 and GTX-200)
- 1/4" phone jack included as standard (GTX-2 and GTX-200)



GTX-200 **\$269.95***

(30 watts output power, nom., up to 100 channel combinations)



GTX-2 **\$259.95***

(30 watts output power, nom., accommodates 10 channels)



GTX-10 **\$209.95***

(10 watts output power, nom., accommodates 10 channels)

* Includes 146.94 MHz. Add'l. crystals \$6.50 ea.



**Don't Let An Honest Price Scare You Away—
See Your Amateur Dealer Today!**

General Aviation Electronics, Inc., 4141 Kingman Drive, Indianapolis, Indiana 46226 — Area 317 - 546-1111

CHARGE IT
ON



CHARGE IT
ON



**CALL
FREE**

**CALL
FREE**

**TOLL
FREE
NUMBER**

(Continental 48 States)

**800
325-3636**

**MO CUSTOMERS CALL
314-993-6060
COLLECT**

**TRADE
ON
NEW**

**TRADE
ON
USED**

CALL

Bill Du Bord, WØKF

(9 A.M.—5 P.M. Central, daily except Sunday)

**FOR
A SQUARE DEAL
ON**

- **DRAKE**
- **TEMPO/ONE**
- **HALLICRAFTERS**
- **CLEGG**
- **STANDARD**
- **YAESU**
- **SWAN**
- **COLLINS**
- **KENWOOD**
- **REGENCY**

We carry all major brands and a large stock of used reconditioned equipment

Write for used list

HAM RADIO CENTER INC.

8342 OLIVE BL.

ST. LOUIS, MO 63132

CLASS B COMPLEMENTARY PAIR

Many of you have encountered the words "complementary pair" and on occasion have come across "complementary-symmetry output stage." Perhaps you shrugged it off with the notion you would return at some later date to learn more about this particular use of transistors. I did return.

The Search

As I searched for practical information regarding this transformerless Class B audio circuit, it became clear that few circuit designers take the time to do more than star (*) those two transistors and add a footnote telling you these "must be factory matched pairs." The average well adjusted person would accept this and not bother to learn a bit more about why they should be matched pairs. After all, portable radio sets and economy model hi-fi amplifiers use them; they work. Who cares why? As a matter of fact, phono-amplifier modules, bought for less than \$5, deliver about 1W output power at low distortion levels. Reason told me to let well enough alone. I'm unreasonable.

The Circuit

I chose a relatively simple circuit from an old Sears & Roebuck company portable

receiver. I built it in duplicate for stereo use. The cost of the experiment was small and the pleasure of accomplishment was great. At the same time I learned something about matching complementary pairs. A piece of Vectorboard about 15 x 20 served as the chassis. The photographs are a clear indication of parts placement. The circuit is shown in Fig. 1. Readily available components were used. Miniaturization was not considered. The channels went together easily. I built the left channel first, probably because I'm left-handed. Use of transistor sockets is a must. This is particularly true if, as I have, you have several sacks of bargain transistors bought from 73 advertisers Poly Paks and Meshna stashed away waiting to see if they are compatible and can work as complementary-symmetry pairs. The transistors selected for the circuit I've shown work well at amplification levels from about 1/10 to 1/2W into a 16Ω speaker.

Selecting Transistors

Preliminary selection was made by using a transistor tester built from information contained in an article by Frank Jones W6AJK which appeared in the September 1966 issue of 73 Magazine. This tester provides an

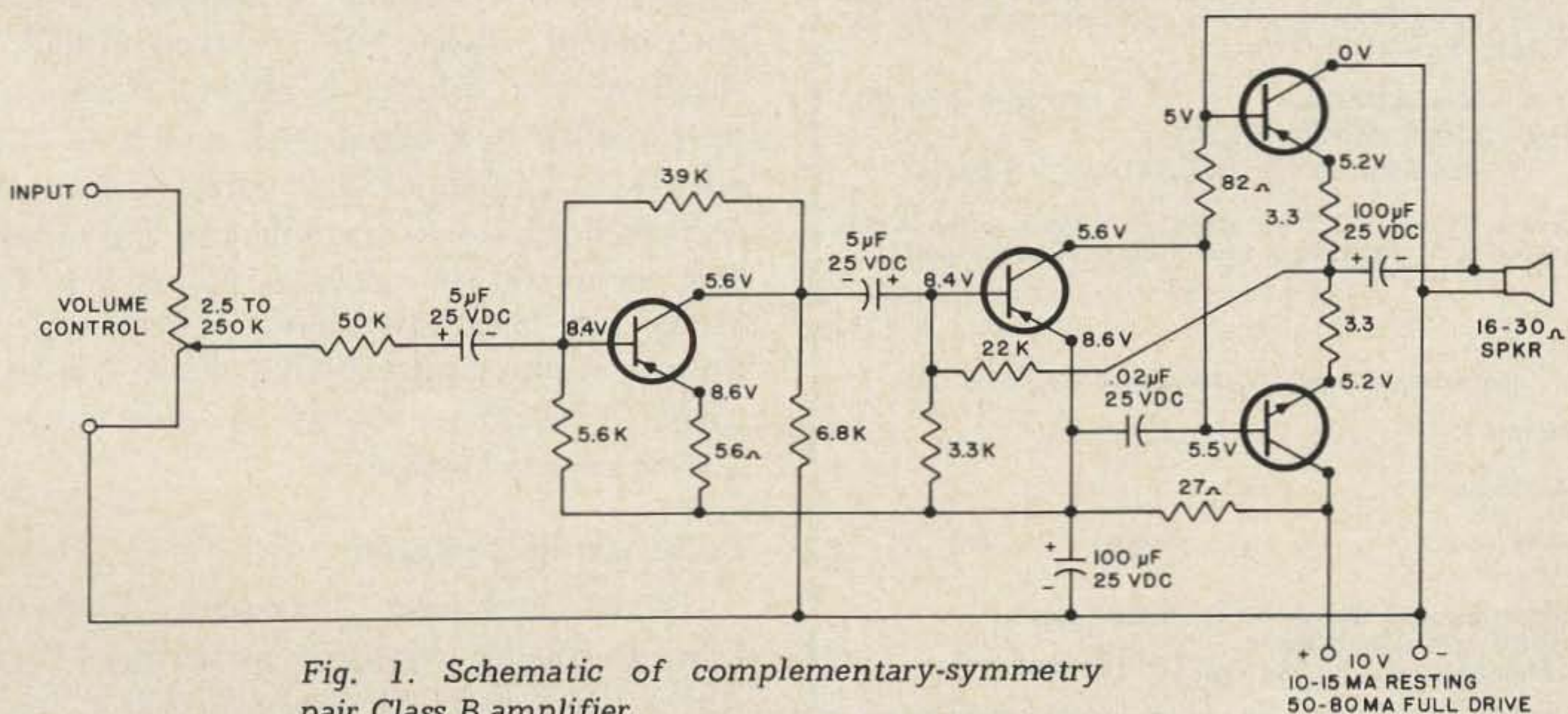


Fig. 1. Schematic of complementary-symmetry pair Class B amplifier.

THE \$39.⁹⁵

2 METER FM

TRANSMITTER

It's here . . . a single channel, crystal controlled solid state FM transmitter with built-in speech processing. A complete circuit board assembly (1½ oz., 3.75 cu. in.) NOT a Kit that doesn't have it all together. Includes miniature crystal microphone, complete technical data. Fully tested. Just connect battery, antenna and microphone, and you're in the 2 meter world.

TYPICAL PERFORMANCE SPECIFICATIONS

Transmitter output into 50 ohms:	200 MW typical @ 8.1v
Frequency Stability:	±0.0025% (-35°C to +55°C). nom. freq. ref.
Current Drain:	70 ma. @ 8.1v
FM Noise:	45 dB below 3.3 KHz, deviation @ 1000 Hz.
Modulation:	Phase Modulation
Audio Response:	±3 dB of 6dB/octave pre-emphasis over 300-3000 Hz.
Deviation:	±5 KHz (adjustable)

Available for limited time only. Fill out the order form below NOW and mail with check or money order payable to ComData Division, International Signal & Control Corp.

1-4 units \$39.95 5 or more \$34.90
INCLUDING MICROPHONE

146.94 or 146.34 or 146.16

Extra Crystals \$2.95 each, available only with order for transmitter. List Frequencies Below:

.....
(Pennsylvania residents, please add 6% sales tax.)

Name

Address

City State Zip

International Signal & Control Corp.
3050 Hempland Road
Lancaster, Pa. 17601 Tel. (717) 299-3671


approximate amplification factor when you divide the indicated base current into the indicated collector current. I found that when the NPN and PNP's showed similar dc characteristics, they generally worked as complementary pairs. The PNP transistors used in this experiment are 2N404's. The single NPN in each output stage is a 2N385. If the 2N385 is not available, 2N1206's can be substituted. Other NPN's work in this circuit but not as well as the combinations mentioned. I did not have newer types on hand to try. That is why I chose the 1963 circuit. The transistors used are germanium medium service switching types with an upper frequency limit of 4 MHz.

Testing the Circuit

With 0.5V input, the complementary pair will drive a 16 or 30Ω speaker to at least ½W music power. That doesn't sound like much power, yet in an average room, it is more than a person with sensitive hearing can comfortably stand for any length of time. A 10V supply such as shown in Fig. 2 was connected and power applied. I touched an input terminal with my forefinger to see if there might be some 60 cycle buzz getting through. To my utter surprise, music came burbling from the speaker! (Secret smile and fleeting thought - I knew I had music in my soul, but *finger tips*? There sure is a lot of life in the old boy yet!) Soon the announcer of the local radio station was heard and the fleeting thought disappeared. Well, now, here is an unexpected bonus. A radio set with no tuned circuits. Different lengths of clip leads were hooked to an input terminal until useful volume was achieved. (I had not wired in the volume control.) Here was a high quality test signal with which to check out the complementary pairs without the need to hook up a turntable and flip records. Our local station provides about 0.1 Voltmeter of radio frequency energy at my house. Testing of PNP-NPN's began in earnest. Needless to say, a wide range of distortion is available!

Close Match Required

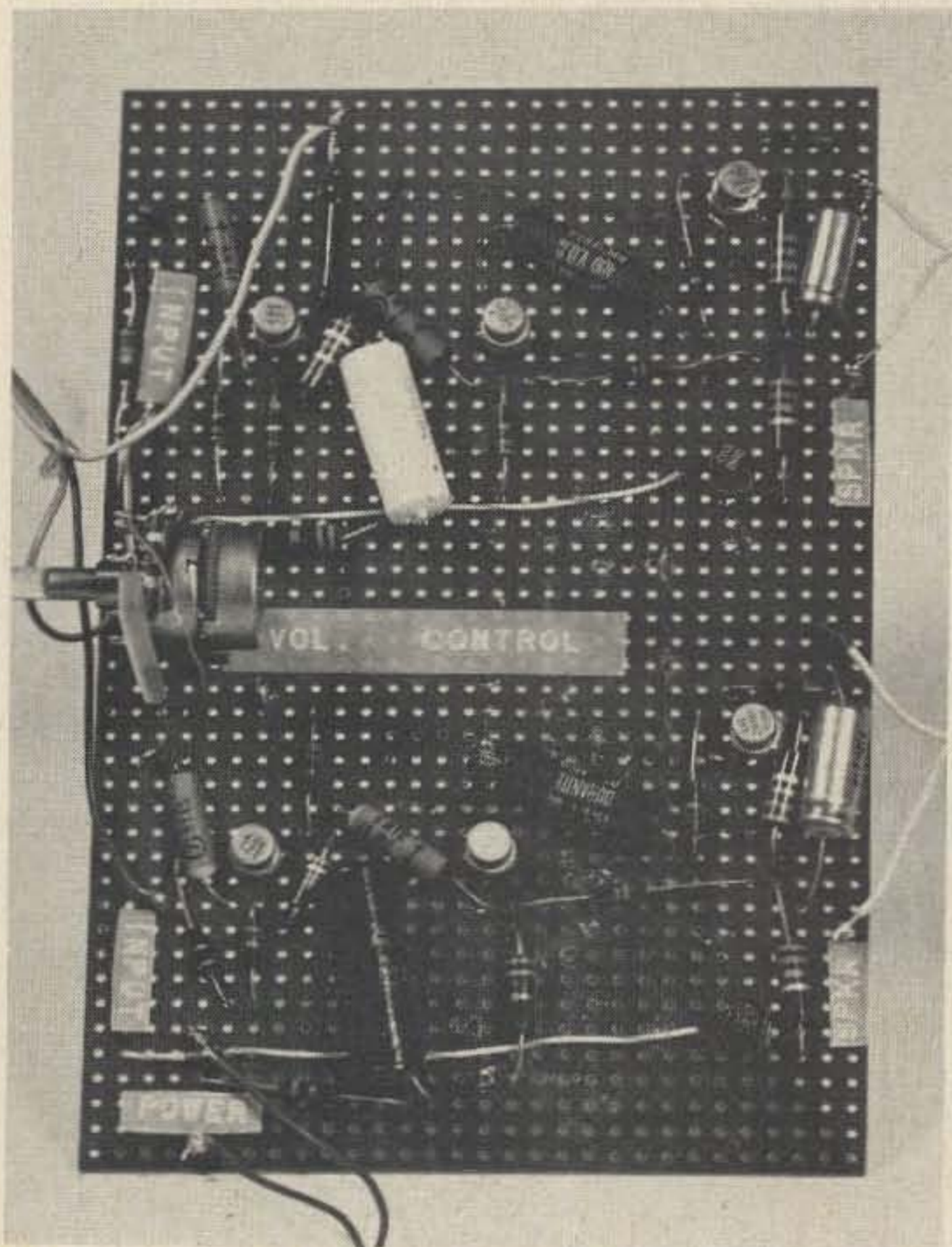Close matching between PNP-NPN Class B output transistors is required for the reason that each transistor is driven by the



Top view, complementary-symmetry pair Class B, stereo amplifiers. Photo by Dan Elliott Photo Shop.

same input signal. They respond oppositely to this signal. Any substantial difference in the characteristics of the output pair, such as leakage current, will result in discontinuities at the crossover point for the positive and negative half cycles. When the two half cycles of the amplified waveform do not accurately fit together, high order harmonics are produced which result in discordant speech or music. This is heard as highly objectionable distortion.

No Fly-wheel Effect

In the complementary-symmetry pair circuit there is no transformer to provide a "fly-wheel" effect which might help smooth the crossover swing. Therefore, careful choice of bias must be arranged. Appreciable idling current must flow to assist in avoiding crossover distortion. This type of distortion becomes noticeable in portable receivers when the battery voltage falls below the level which upsets the bias voltage for a given pair of transistors. The circuit I've shown works well between 6 and 10V.

Poly Quad

**UPGRADE TO
THE FINEST
ANTENNA**

POLY tri QUAD ANTENNA KIT

2 element . . . tri band . . .
power gain comparable to 3
el yagi . . . lower angle of
radiation . . . greater capture
area . . . more efficiency.

- 8 Zip-Glas Spreaders (13')
- 2 Universal Starmounts
- 1 Boom/Mast Adapter
- 1 Instruction Manual

\$89⁹⁵
Postpaid
in U.S.A.

TOPS!
EXCLUSIVE
ZIP GLAS
TELESCOPIC
FIBERGLASS
SPREADERS



Polygon's Exclusive... continuous fiberglass filaments drawn and woven under tension and impregnated with finest epoxy resins.


Fiberglass Spreaders Have Ultra-Violet Shield

These scientifically tapered and stressed spreaders are final-dipped with a rich blue vinyl coating that resists all types of weather deterioration, blocks out sun's destructive rays and adds to spreader life.

Polygon's patented processes give the Zip Glas spreaders great flexural strength, and unmatched durability — superior to anything on the market.

Exclusive Universal Starmount

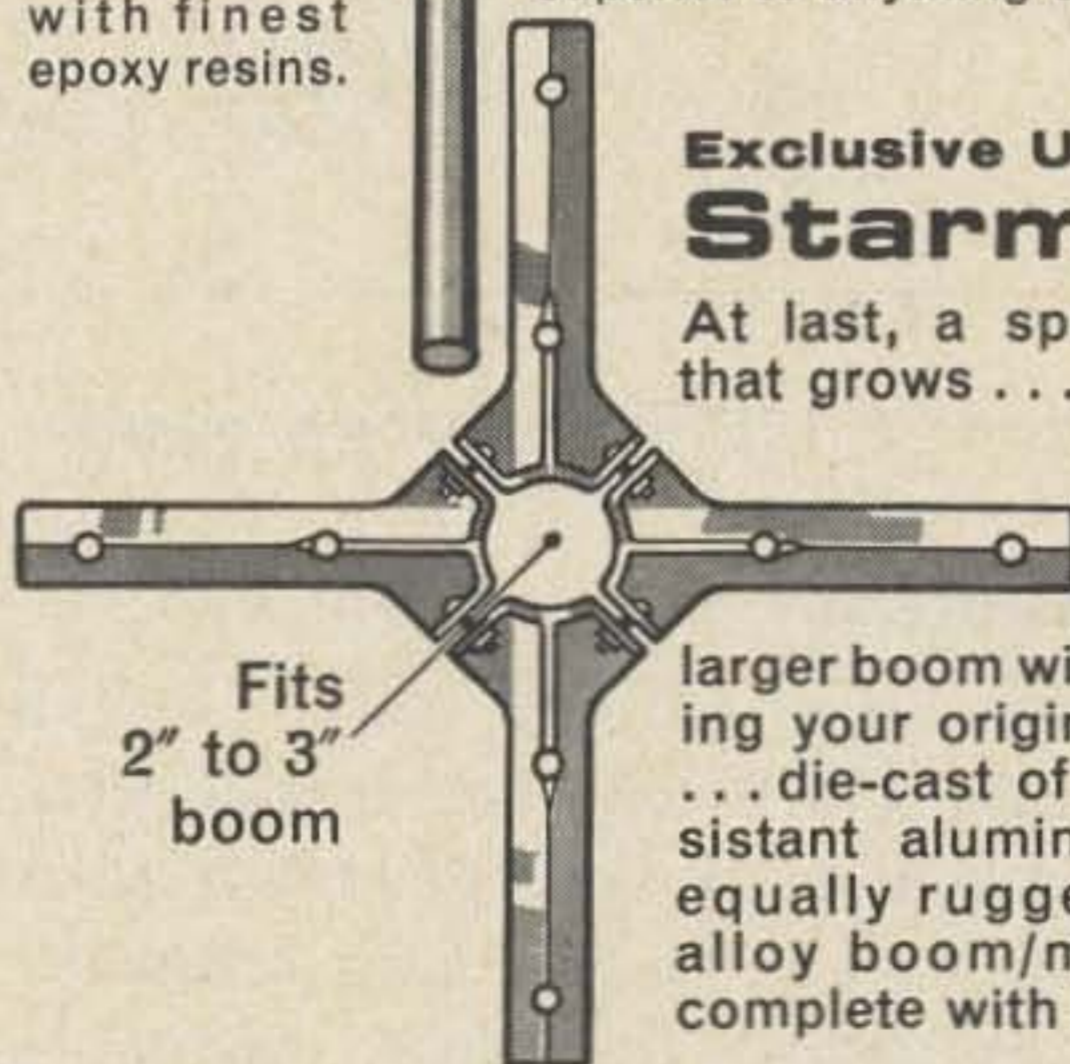At last, a spreader mount that grows . . . you can start with a 2" boom, later add more elements on a



larger boom without discarding your original Starmount . . . die-cast of corrosion resistant aluminum alloy . . . equally rugged aluminum alloy boom/mast adapter complete with hardware.

CHOOSE FROM SEVERAL POLY QUAD KITS

You can order 2, 3 or 4 element POLY tri QUAD kits—POLY duo QUAD (15-10) and POLY mono QUAD (10) kits also available. For further specifications plus complete list of kits and individual components, write . . .



POLYGON COMPANY

Division Plas/Steel Products, Inc.


2310 Industrial Park, Walkerton, IN 46574

MATCHED PAIR DIODES
70V $V_b - V_f = 1V \pm 5mA$
FOR USE IN DETECTORS,
MODULATORS, BRIDGES.
IN MOLDED PACKAGE.
#MPD-0570.... 2/\$1.00



CONSTANT CURRENT REGULATOR. A BEAUTIFULLY MADE MODULE DESIGNED AS A CONSTANT CURRENT REGULATOR. OP AMP CONTROLLED WITH IT'S OWN BUILT-IN $\pm 10V$ SUPPLY. HEAVYPASS TRANSISTOR-SERIES BREAKER-CONTROLLER ALL MOUNTED ON A BIG ALUMINUM HEAT SINK. UNIT CAN BE USED "AS IS" FOR CURRENT CONTROL. A SIMPLE MOD TURNS IT INTO A SERIES VOLTAGE REGULATOR USEABLE UP TO 3 AMPS. THERE ARE TWO VERSIONS OF THE MODULE. ONE HAS NPN DEVICES FOR CONTROLLING "POSITIVE" CURRENT/VOLTAGE, THE OTHER HAS PNP'S FOR NEGATIVE. EITHER, WITH DIAGRAMS..... \$4.25

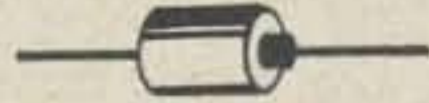8.3V, 1W METAL ZENER
SELECTED FOR USE WITH SILICON TRANSISTOR
IN 9V REGULATOR CIRCUIT. \$.30, ...4/\$1.00




LED READOUTS. MINIATURE, RED, 7 SEGMENT WITH DECIMAL. COMMON CATHODE FORMAT. CHARACTER SIZE IS 3/32" X 5/32". ONLY 10mA PER SEGMENT. MAN-3 SIZE. PRIME PARTS! STOCK # MOR10A.....\$1.50 ea,4/\$5.00

COMPUTER GRADE CAPACITORS.
JUST RIGHT FOR I.C. CIRCUITS.
HAS OPTIMUM RATINGS FOR 5
VOLT SYSTEMS. 5400uF @ 5 V.
#CGC-5542... \$.50, ...5/\$2.25



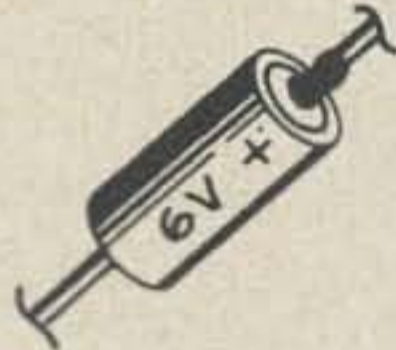SQUARE LOOP CORE. TAPE WOUND WITH 2 mil "SQUARE ORTHONOL". DESIGNED FOR POWER INVERTERS AND CONVERTERS. $B(sat) = 14$ to 15 KGauss @ .3 Oersted AT 6 KHz. MADE BY MAGNETICS, INC. \$.75, 10/\$6.00



TANTALUM CAPACITORS


0.47uF @ 6V	12/\$1.00
4.7 uF @ 6V	10/\$1.00
6.8 uF @ 6V	8/\$1.00

GLASS SEALED, NEW



TINY R.F. CHOKES. APPROXIMATELY 1uH..... 6/\$.25, 100/\$2.50

RECTANGULAR CASED FILM CAPACITORS

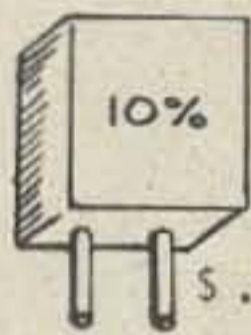


.22uF/250V
.22uF/63V

\$.10, 10/\$.75



TRANSISTOR MIX. THESE ARE NEW INDUSTRIAL SURPLUS, NOT REJECTS. SOME HAVE 2N NUMBERS, SOME HAVE INDUSTRIAL USER NUMBERS. SOME ARE COLOR CODED. PLASTICS, METALS, PNPS, NPNS, UNIUNCTIONS. 20/\$1

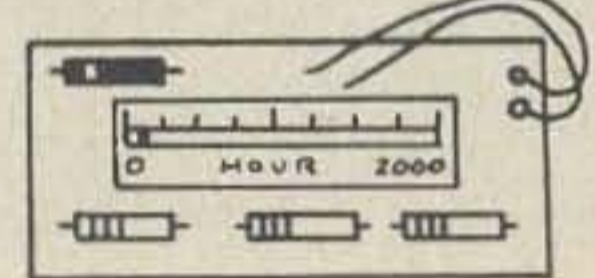RUNNING TIME INDICATORS. CURTIS INDICHRON 120-LC MERCURY TUBE MOUNTED ON A P.C. BOARD WITH ZENER REGULATOR. WITH DATA SHEET. NEW LOW PRICE..\$1.75



tri-tek, inc.

P.O. BOX 14206, DEPT 7
PHOENIX, ARIZONA 85063

NEW AND SURPLUS ELECTRONIC COMPONENTS FOR THE PRO AND SERIOUS AMATEUR. AN ORDER OR 8c STAMP PUTS YOU ON OUR MAILING LIST. MINIMUM ORDER \$3.00 U.S., \$15.00 FOREIGN. ALL ORDERS POSTPAID. PLEASE ADD INSURANCE

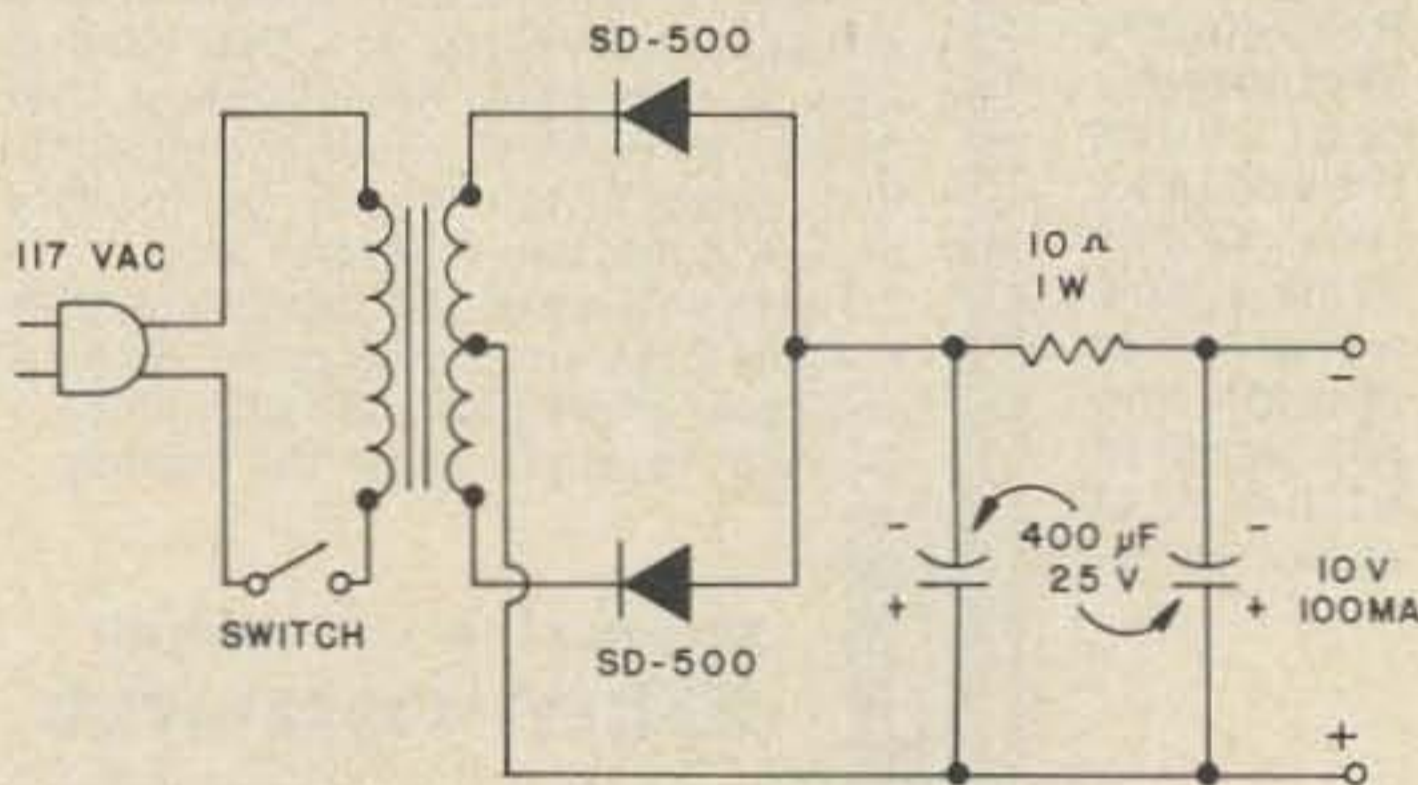


Fig. 2. Schematic of 10V 100 mA power supply.

Reducing Distortion

Those who have worked with Class B tube amplifiers will recall that it was often desirable to place a few volts of positive bias on the grids to aid in reducing crossover distortion. In many transistor circuits a similar scheme is found. This circuit is no exception. A bit of forward bias is used between base and emitter (in the low resistance direction) to overcome crossover dead time and make the amplifier a great deal more linear at all listening levels. In addition, ac and dc feedback is used to improve linearity and to extend the upper frequency

limit. Resting current is about 5 mA per channel and depends on the supply voltage. This is perhaps more resting current than is actually needed, and I believe the complementary pair is running Class A at low input levels. The 2N404 and 2N385 data sheets indicate 25V maximum supply to the transistors. That voltage would require more heat sink than I show. 10V is a good compromise. I tried 15V and the 3.3 ohm resistors in the emitters were barely able to keep the transistors out of thermal runaway. In 30 minutes the resting current slowly climbed to a higher value. The resting current was also sensitive to temperature. At 50°F and 15V, the transistors tolerated the supply voltage. At 75°F room temperature, they did not and began to show thermal runaway. A vacuum tube voltmeter was used to obtain the voltages shown in the schematic.

Surprise

This investigation of complementary-symmetry circuitry was not without other surprises. For instance, the right channel

FREQUENCY SYNTHESIZERS

IMMEDIATE
"OFF THE SHELF"
DELIVERY!

YOU'LL NEVER
HAVE TO BUY
CRYSTALS
AGAIN!



MODEL: ST-140

Price: \$129.95 ppd.

Tested, guaranteed and complete with mobile mounting bracket, tilt stand and transmitter matching kit.

NOTE: NY State residents add sales tax.

CHECK THE ADVANTAGES OF A VANGUARD SYNTHESIZER OVER OTHER BRANDS...

- No microphonics. Can be used mobile over bumpy roads.
- Reference frequency and spurious output down 70 dB. (excluding harmonics of output frequency which are used in the transmitter anyway.)
- All output frequencies are generated directly from the VCO without the use of multipliers and are therefore free of sub-harmonics.
- Now available with outputs in the 6, 8, 12 and 18 MHz. bands (corresponding to 144 MHz. dial reading) for direct substitution of transmitting crystals. More output frequencies are being made available. Call us if you don't see what you need.
- Entire frequency appears in-line in clear digits. No guesswork or mental additions. Thumbwheel switches provide fast, accurate selection of 1000 channels in 10 KHz. steps from 140.00 to 149.99 MHz.
- 50 ohm output and impedance transformer kit allows use at any distance from transmitter.
- Maintains an accuracy of .0005% (5 parts per million) over the entire range of -10° to +60° C. with a precision temperature compensated crystal that requires no oven. Operates at 5 MHz. for easy checking with WWV and includes a zero trimmer for correcting long term aging drift.
- Fast response time of only 3 milliseconds for a 10 KHz. step change in frequency and a remote control, gated output amplifier for push-to-talk operation.
- No hunting or false locks as with some other synthesizers.
- Operates from 10 to 15 VDC. 3 precision regulators eliminate input voltage fluctuations. Can also be used on 110 volts AC with a small 12 volt 1/2 amp power supply.
- Smallest size of any commercial synthesizer. Only 1-3/8" high, 3-5/8" wide, 8" long.
- All IC's are mounted in high quality insulated sockets and all parts are marked.

Manufactured by VANGUARD LABS renowned for quality since 1952.

NOTE: Our 45 MHz receive synthesizers are now in production. Call us for details.

IMPORTANT: When ordering be sure to state the output frequency you want.

VANGUARD LABS

Call 212 468-2720 for fast C.O.D. shipment.

196-23 JAMAICA AVE. HOLLIS, N.Y. 11423

broke into a magnificent howl when the volume control was backed off to zero. Apparently the input was effectively connected to the output through some sneak circuit and the feedback loop caused an oscillation which drew more than 100 mA from the 10V supply. This happened only when both channels were in use. Each separately was stable. I didn't check out the howl more than twice because the transistors are rated at 150 mW dissipation. The cure for the trouble wasn't especially scientific, but it was adequate. a 50 K Ω resistor was placed in series with the input base coupling capacitors and the arm of the volume control. This affords a measure of isolation. At the moment I don't know how to prevent such unwanted coupling.

Advantages

An attractive advantage of the PNP-NPN complementary-symmetry pair is that it can be driven by a single driver transistor. This eliminates the need for phase inverters and/or transformers. Direct coupling between transistors can be used to improve the

frequency range. Biasing can be done through the use of conventional resistors.

Conclusion

Simple methods can be used to select transistors for Class B transformerless work. A good starting point can be found in one of *Transistor Substitution Handbook No. 9*. It is advisable to have several transistors of the same kind on hand in order to select those which will work well together. Proper biasing is most important for good linearity with least distortion in the output signal. The new silicon planar transistors are good candidates for complementary-symmetry pair work. From what I can find in the literature, just about all silicons can be used for audio work without regard to their maximum frequency capability. Their low leakage allows direct coupling of audio stages without complicated temperature compensation. Thus a transformer can be eliminated. The major change required is biasing so as to provide about 0.6V base-emitter drop instead of the 0.2V needed for germanium transistors. I plan to try silicons next.

...W5SOT

ou goons don't ever proofr
easy man scripts from bab
bunch of rocks preening on
you ignored my comments in
I insist that you print ev

REJECTED LICENSE

I think the time has come to voice my feelings in amateur radio's public print regarding the current status of the FCC's procedures and practices in the area of amateur radio.

For the past 27 years I have been actively involved in radio broadcasting in the engineering and technical phases. During these years I have had ample opportunity to observe the operations of the commission in both the rule-making and regulatory areas. I have never before been as disturbed and uncomfortable as I am now.

This letter is really prompted by the recent rejection of my application for a repeater license by the Washington office of the commission. That rejection has made me stop and think about just what it is that the commission is trying to achieve, and frankly, I fail to understand either its goals or its motivations.

As chief engineer of several radio broadcasting operations, including both FM and AM directional stations, I thought that I was in reasonably good condition to present to the commission an application which would be properly set in engineering terms and timely filed. But, apparently I was wrong. The paperwork that I hand carried to Washington ended up in the circular file. The commission, in its infinite wisdom, did not accept the antenna that I had selected and installed some two years ago, on one of the towers of the AM directional station for which I am responsible. The installation of the antenna was accomplished during some major structural changes to the broadcast system, for which a major proof-of-performance was required on the directional array. I might add that the antenna which I chose and the commission subsequently rejected for lack of type approval is in widespread and common use in the commercial FM mobile radio service for base station applications. But, oddly enough, this antenna does not appear on the mysteriously-generated approved list of the commission.

The question that intrigues me is not the commission's reasons for refusing to accept this particular antenna, but rather why the commission has burdened the amateur radio service with approval requirements not deemed necessary in the commercial services. The sad facts for me are that by strict interpretation of the commission's rules, I cannot even remove the antenna from the tower to attempt pattern measurements because that action

would immediately generate a problem with the broadcast bureau, to whose rules I am bound regarding the operation and maintenance of the directional array.

After careful consideration I have arrived at the point where I am forced to wonder about the intentions of the gentleman who directs the attitudes and activities of the amateur and citizen's division. What the hell are they trying to prove? Are they not aware that they may be implimenting attitudes that could eventually destroy amateur radio if permitted to continue unchecked along the courses now being pursued????

It is reasonable to question the motives and methods of the individual who directs that division when one examines the manner of grossly restrictive rulemaking being foisted upon the amateur radio fraternity, and compare the same division's activities and attitudes towards its other area of responsibility, the citizen's radio service.

While it is obvious that the people in the broadcast bureau get their paychecks from the same coffers as the people in the amateur and citizen's division, it is also obvious that they don't talk to each other in terms of common policy guidelines and philosophy. The latter organization continues to blithely ignore the widespread malpractice, violation, and chaos rampant in the citizen's radio service, which it is also required to administer, while it concentrates huge efforts on what seem to many of us to be open attempts to put amateur radio out of business. Again I ask what the hell are they trying to prove? To require the amateur radio service to follow rules and procedures not required of comparable commercial services smacks of some kind of perverse thinking. It certainly deserves, if nothing more unflattering, the title of discriminatory treatment.

But again I ask not what they are doing...rather, why are they doing it? Is not the commission as a whole bound to be zealous of the public interest? Are not these people paid from our own pockets, servants of the public and thus subject to our overseeing and inquiry as to their actions and attitudes? I, for one, say yes and amen. I am paying their salaries. I am needful of their services. And as their employer, I say that the time has come to demand a full and extensive inquiry into the activities of

the men who are at the head of the amateur and citizen's division.

The question I raise is not what they are doing...that is obvious. I want to know why they are doing it and what factors are the basis for their totally inequitable attitudes and actions of the past two years.

During these same past two years, we in the broadcasting business, have watched while a series of strikingly well thought out new regulations issue forth from the broadcast bureau...rulemaking which is infused with the realization that the state of the broadcaster's art had advanced to the point where the existing rules were in dire need of revitalization. And while there is little doubt that the new rulemaking in the broadcasting bureau has much lobby pressure from the industry behind it, it is difficult to find any strong or serious opposition to the sweeping reregulation that has been legislated into broadcasting. Many sacred cows of broadcast law have been swept into the musty archives of history in the past two years...the first class radiotelephone license has, for all practical purposes, been delivered to the tender care of the Smithsonian Institute since it is no longer required for anyone except the chief engineer. The old hassle of taking transmitter readings for the operating logs on a half-hourly basis has been relegated to oblivion and stations of all categories, up to and including fifty kilowatt directionals are now permitted full remotely controlled unattended operation with readings to be taken at intervals up to three hours. The previous requirement of daily inspection of the transmitter site has been relaxed in the simpler cases to once every five days, and in the more stringent cases of the remotely-operated high power directional station, to once every fifty-four hours. The old saw of station identification every thirty minutes within two minutes of the hour or half hour has been relaxed to once an hour as near to the hour as is consistent with normal breaks in programming. I could go on ad infinitum quoting a long series of changes and deregulation of the past two years, but I think my point is clear.

I have been pained to see, in the past several years, an unhealthy schism develop within the ranks of amateur radio. Factions dividing the fraternity have served only to generate animosity among us — the spirit of amateur radio. Further, that schism has caused many of us to forget the true goals which amateur radio originally set out to achieve. In useless bickering among ourselves and between the various factions, we have lost track of what we are and where we should be going. We have lost that immense power that lies in unity and

Cont. on page 111

73 de W2NSD/1

73 Pine St.
Peterborough,
NH 03458
USA

(Style 1)
Actual Size




QSLs for 1¢

- two colors
- QSO info back
- LOW PRICES

Just when you're used to being abused by ever skyrocketing prices, 73 comes along with yet another way for Hams to save money! We have figured out a way for you to get *High Quality* QSL cards for as low as a **PENNY-A-PIECE** postpaid!

These cards are printed on *High Quality Glossy Card Stock* and are as good, or better than cards sold elsewhere for two or three times the price. By ganging up QSL printing between other jobs in our own print shop, we are able to offer you this fantastic low price. At this price, do you really have an excuse for not getting in a supply of these nice QSLs? Don't be one to give U.S. amateurs a bad name by not sending a card when requested.

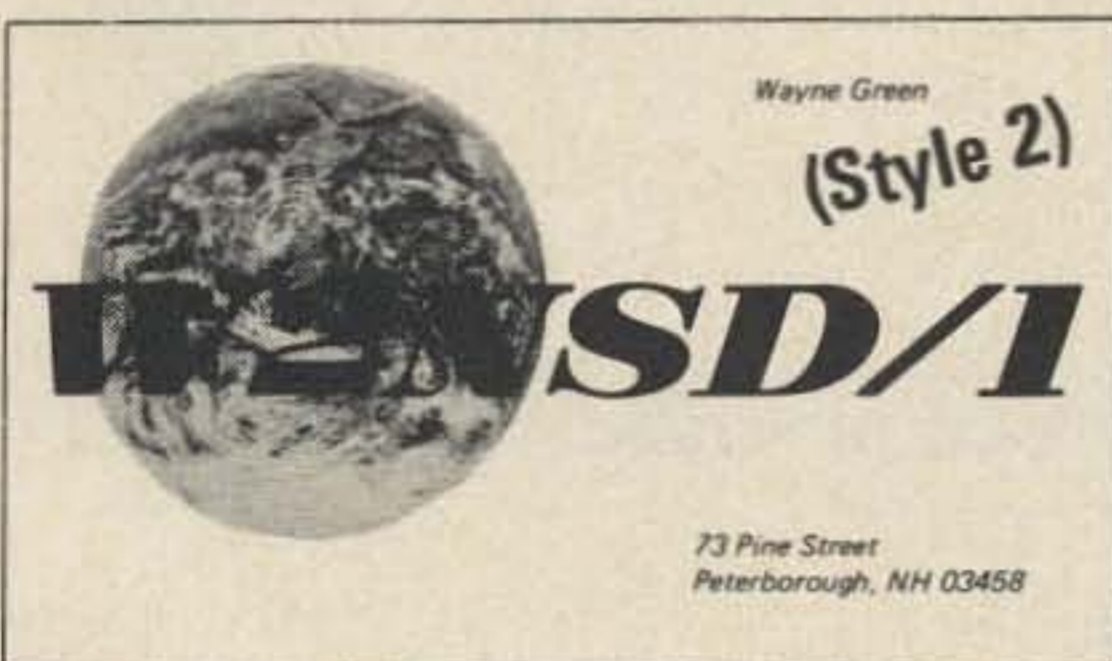

3 STYLES to choose from!

↙ ORDER - AND PAY ↘

250	\$6 (2.5¢ ea)
500	\$10 (2¢ ea)
1000	\$15 (1.5¢ ea)
2000	\$20 (1¢ ea)



ORDER BLANK

Name _____ Call _____
(First and last name is most friendly)

Address _____
(as brief as possible and still get through the mail)

City _____ State _____ ZIP _____ County _____
(a must) (if desired on the card)

Awards to be listed on card _____

250 500 1000 2000 cards Amount enclosed \$ _____

Style	
1	<input type="checkbox"/>
2	<input type="checkbox"/>
3	<input type="checkbox"/>

BOOKS

&

STUFF

73

Fascinating World of Radio Communications	\$4.00
Novice Class Study Guide	\$4.00
General Class Study Guide	\$6.00
Advanced Class Study Guide	\$4.00
Extra Class Study Guide, reduced price	\$5.00
VHF Projects for Amateur & Experimenter	\$5.00
VHF Antenna Handbook	\$3.00
How to Use FM, an introduction	\$1.50
FM Repeater Atlas, worldwide w/maps	\$1.50
*FM Repeater Circuits Manual	\$5.00
*Digital Control of Repeaters, new	\$5.00
RTTY Handbook, radio teletype A to Z	\$6.00
ATV Anthology, fast scan VHF TV	\$3.00
*SSTV Handbook, new, only slow scan avail.	\$5.00
Diode Circuits Handbook, galore	\$1.00
73 Transistor Circuits, all useful	\$1.00
Transistor Projects, mucho	\$3.00
Solid State Projects	\$4.00
IC Projects	\$4.00
108 Q & A, transmitting, receiving, ant.	\$2.00
TVI Handbook, why suffer	\$1.50
Coax Handbook, cables & connectors	\$3.00
DX Handbook, w/map	\$3.00
World DX Map, wall size, rolled	\$2.00
Custom DX Bearing Charts, beam headings	\$4.00
U.S. Maps, for WAS, etc (4 ea)	\$1.00
Call Sign Badges, for lapel, black or red	\$1.00
Magnetic Call Signs, for autos	\$4.00
73 Magazine Binders, beautiful red	\$5.00

* Hardbound versions available @ \$2.00 more. All items postpaid.

BOOKS ORDER FORM

Name _____

\$ _____ enclosed

Call _____

Books wanted:

Address _____

City _____

State _____ Zip _____

73 Magazine, Peterborough NH 03458 USA

Official

73

ORDER FORM

magazine

Mail to: Peterborough, NH 03458

Item	Quantity	Page No.	Price
_____	_____	_____	_____
_____	_____	_____	_____
_____	_____	_____	_____
_____	_____	_____	_____

Check

Cash

Bill Me
(Orders of \$5
or more only)

Name _____ Call _____

Address _____

City _____ State _____ ZIP _____

Total Enclosed
\$

November 1973


Cassette Code Course

Here is a cassette code course that is so simple that the average person can learn code fast enough to pass the Novice or Tech exam in a few hours.

One of the beauties of cassette tapes is that you can take them with you anywhere — at work for lunch break — even in the car while you are driving.

This cassette code course will teach the International Morse Code at five words per minute — all letters, numbers and punctuation. The tape not only gives all these characters, but gives them in a very simple order so you can start copying code within one minute of hearing it. This has got to be the easiest way to learn code ever invented.

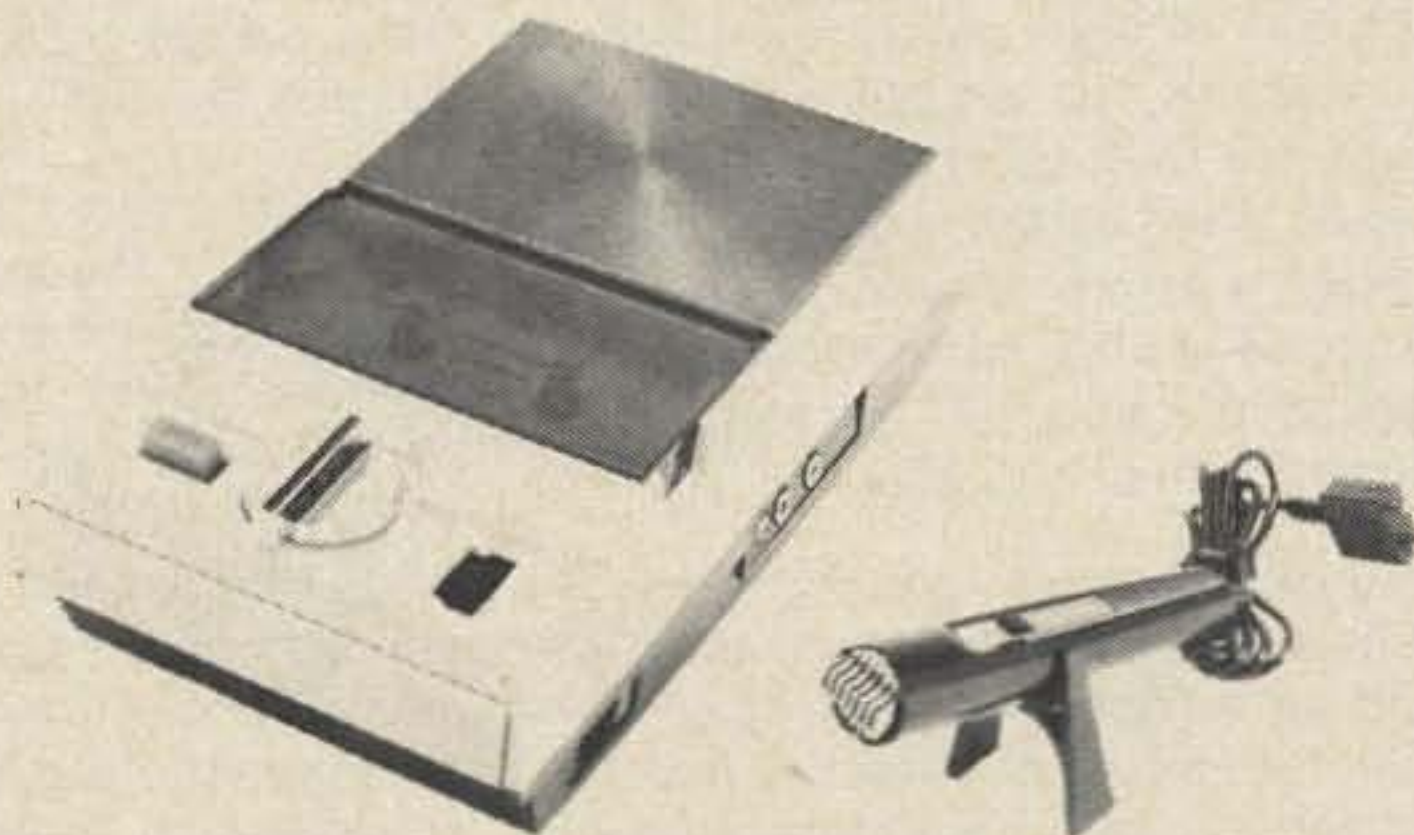The cassette actually has the code being sent at about six words per minute, allowing a margin for operator panic when the chips are down and the real exam is at hand. Send now for the 73 Morse Code Course — only \$3.95 postpaid from 73.



Cassette Recorder

Here is a cassette recorder that is ideal for use with the code course since it can be operated anywhere.

Comes complete with four "D" batteries, ac power cord, earphone and mike and is useful for dozens of ham applications. Cassette tape recorder is available for only \$23.95 (plus \$1.00 for shipping and handling).

Use Order Form

**The Famous Oliver Swan
"Band Pass" Designs
now improved by
KLM Electronics**

SEE - IT'S NOT SO BIG



KLM 13-30-7 For the man who wants an antenna farm on one boom, this log periodic covers 13-30 MHz continuous with max VSWR under 2:1 and is supplied with a 4 KW pep broad band balun. **\$289.95**


-Attention 6 Meter Enthusiasts-

Take advantage of sporadic E and tropo openings with our Super 11 Element Bandpass Antenna on a 30 foot boom priced for everyone for everyone's pocket at **\$89.95**

● Write for full Antenna Line Catalog and VHF Power Amp Line


KLM 144-148-16 Optimumly Designed for DXers, Tropo, Satellites, Meteors, Moon-bounce. **\$49.95** Complete.

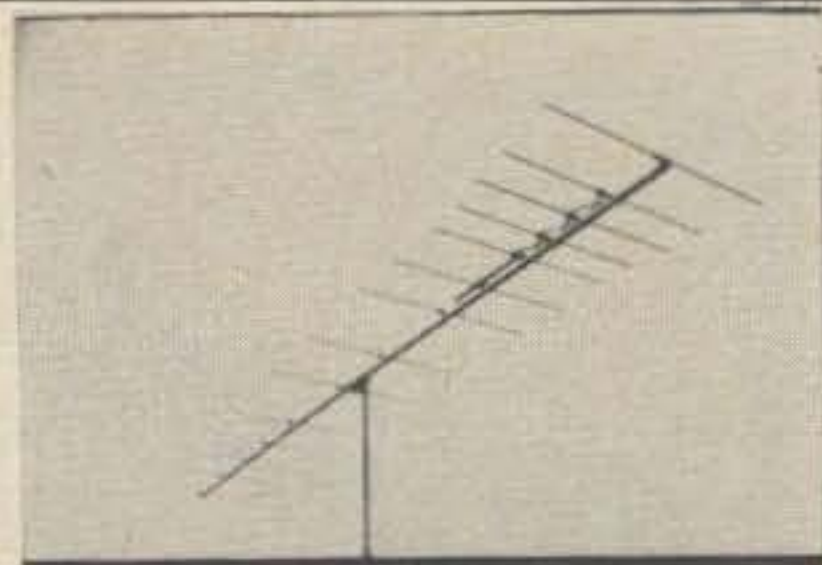Kit Price—Less Boom **\$37.95**
NOTE: Boom Dia. 1½". No boom brace reqd.



COVERS COMPLETE 2M BAND

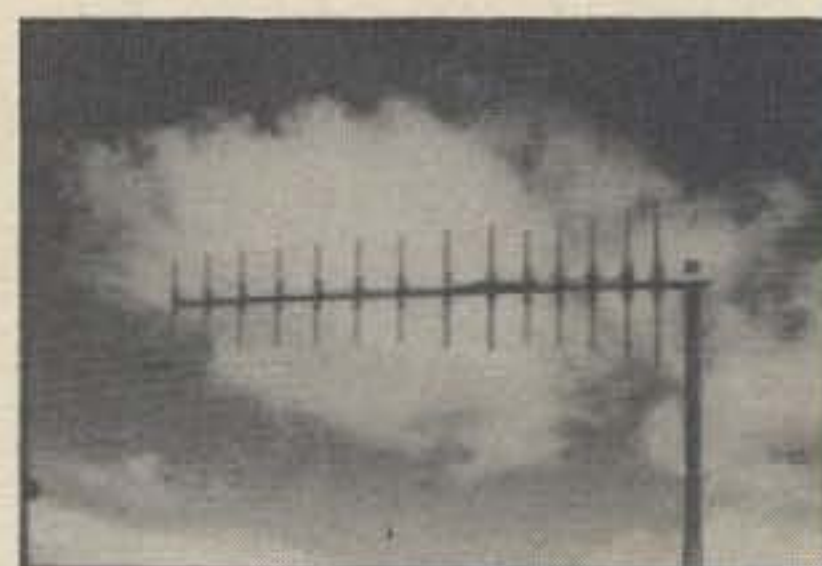KLM 420-450-14 Ideal for FM or the DXer. **\$19.95** Now Rear-mountable.



COVERS COMPLETE 420-450 MHz BAND

KLM ELECTRONICS

"THE COMMUNICATIONS EQUIPMENT INNOVATORS"

1600 Decker • San Martin, California 95046
(408) 683-4240 or (408) 842-7349

K6MYC
K6HCP
K6KBE

All prices FOB San Martin and are subject to change without notice.

Cont. from page 4.

up with those fantastic numbers in their suits against small businesses — and you can see how so few of them are able to do anything about it except try the best they can to settle — and that means pleading guilty, whether you are or not. It gives the IRS a nice record, but it leaves a lot of bitter people who find few ears willing to listen to their troubles.

By disallowing things that seem like obvious business expenses they can build up a frightening suit against the small businessman. And the first hint that there is anything serious breeding can come as an announcement in the newspaper that you have been indicted for fraud by a grand jury. When you try to find out what the IRS could possibly have told a grand jury to result in this you discover that all doors are closed — you have no way of finding out what was claimed against you other than the amount they claim you and your business owe.

The first hint I had that anything was afoot like this was when someone called to say that the local radio station had a news item that morning that I had been indicted by a grand jury on twelve counts of criminal fraud and that the amount involved was over \$100,000. Then it appeared in the paper — and a fellow publisher

made sure that all advertisers were aware of the IRS side of the story by sending out photo copies of the newspaper article. One of the ham publications rushed right into print with it — but just the IRS story.

It was quite a few days before I got a copy of the indictment — and even then I didn't know much more. The twelve counts sound dramatic, but actually the IRS disallowed business expenses for the three years 1966-67-68, and they are able to escalate that into twelve counts. It sounds better to the public — and that is apparently the whole object of their scheme — to impress the public and make them afraid of the IRS.

They euphemistically call it the Taxpayer Compliance Program — and the game seems to be to take one defenseless pigeon and call in hundreds of witnesses to the crucifixion so they will all go home and spread the word not to fool with the IRS.

The Watergate mess gives a hint as to how these Gestapo type people operate. They appear to live in a world where anything goes, no matter how dirty or illegal — where postal surveillance means opening your mail and checking it — where wire taps are an everyday occurrence — where frightening witnesses into saying things is the norm. They have their own investigators — their own lawyers —

their own courts — and unlimited budgets to crush anyone who tries to stand in their way.

The fear of persecution has kept the press from printing much in the way of IRS horror stories — but every now and then one comes to light where some individual has fought for years through their rigged courts before winning what should have been an open and shut case of acquittal on trumped up charges.

Well, you might say, why didn't you explain what the reasoning was for the business expenses when they examined you? Brother, they never ask you — they just make up their mind, with no comeback possible from you unless you can stand the cost of a jury trial and a very long bitter fight.

And going to trial is something else again, for here you need to line up some expert witnesses to testify about tax matters. Do you know that it is virtually impossible to get anyone on the witness stand, for any money, to do this? The experts are so frightened of IRS retaliation that you can't get them to help you. They've heard all about accountants who have been so persecuted by the IRS that they have committed suicide or died of heart attacks — of firms where every client

(continued on p. 109.)

FCC RULES AND REGULATIONS, PART 97 (VI)

CONTENTS THIS MONTH

STATION OPERATION AWAY FROM AUTHORIZED LOCATION

- 97.95 Operation away from the authorized permanent station location.
97.97 Notice of operation away from authorized location.
97.101 Special provisions for mobile stations aboard ships or aircraft.

Logs

- 97.103 Station log requirements.
97.105 Retention of logs.

EMERGENCY OPERATIONS

- 97.107 Operation in emergencies.

OPERATION OF ADDITIONAL STATIONS

- 97.108 Operation of a remotely controlled station.
97.109 Operation of a control station.
97.110 Operation of an auxiliary link station.
97.111 Operation of a repeater station.

STATION OPERATION AWAY FROM AUTHORIZED LOCATION

§ 97.95 Operation away from the authorized permanent station location.

(a) Operation within the United States, its territories, or possessions is permitted as follows:

(1) When there is no change in the authorized land station location, an amateur radio station other than a military recreation or an auxiliary link station may be operated under its station license anywhere in the United States, its territories or possessions as a portable or mobile operation, subject to § 97.61.

【§ 97.95(a)(1) amended eff. 10-17-72; VI(72)-1】

(2) When the authorized permanent station location is changed, formal application (FCC Form 610 for an individual station license and FCC Form 610-B for an amateur club or military recreation station license) must be submitted to the Commission prior to any operation and within 4 months of the move for the purpose of modifying the station license to show the new permanent station location. Operation at the new location is permitted under the license for the former station from the date the modification application is mailed until advised of Commission action on that application.

(3) For operations under subparagraphs (1) and

Continuing from last month the complete text of the FCC Rules & Regulations pertaining to the Amateur Radio Service.

(2) of this paragraph, advance notice, as required by § 97.97, must be given to the Engineer in Charge of each radio district in which operation is intended and the portable identification procedures specified in § 97.87 must be used.

(b) When outside the continental limits of the United States, its territories, or possessions, an amateur radio station may be operated as portable or mobile only under the following conditions:

(1) Operation may not be conducted within the jurisdiction of a foreign government except pursuant

to, and in accordance with express authority granted to the licensee by such foreign government. When a foreign government permits Commission licensees to operate within its territory, the amateur frequency bands which may be used shall be as prescribed or limited by that government. (See Appendix 4 of this Part for the text of treaties or agreements between the United States and foreign governments relative to reciprocal amateur radio operation.)

(2) When outside the jurisdiction of a foreign government, operation may be conducted within Region 2 on any amateur frequency band between 7.0 MHz and 148 MHz, inclusive; and when not within Region 2, operation may be conducted only in the amateur

PARTS! CORNELL TUBES!

FREE Send For FREE
CORNELL'S
 New Color
 Catalog
 48 Pgs. New Items

33¢ per tube
36¢ per tube

ORDER FREE
 IF NOT SHIPPED
 IN 24 HOURS!

IN LOTS OF 100

4215 S University Ave. San Diego, Calif. 92105

WEST COAST HAMS
 Good Deals

Ham Gear New-Used

M-TRON

DOUG MURRAY - W6HVN
 2811 Telegraph Ave., Oakland CA 94609

WORLD QSL BUREAU

5200 Panama Ave., Richmond CA USA 94804

THE ONLY QSL BUREAU to handle all of your QSLs to anywhere; next door, the next state, the next county, the whole world. Just bundle them up (please arrange alphabetically) and send them to us with payment of 5¢ each.

SP-600-JX General Coverage Receiver .54-54 MHz in 6 bands. Dual conversion. Variable selectivity to 200 Hz. 117/230 V 60 Hz. With instruction manual. Used \$255

Converter AM-1179/GRC 50-100 MHz, output 30 MHz. Requires 150 Vdc and 6.3 V. 10 lbs. Used \$9.95.



P. WOOD PO BOX 112
 GOLETA CA 93017

Synthesize Any FM Rig...With A GLB Channelizer!

- ★ EASILY CHANGED FROM RIG TO RIG
- ★ FASTEST LOCK-UP
- ★ CHOICE OF 10 or 5 KHZ STEPS
- ★ 5 PPM STABILITY
- ★ UNIVERSAL SWITCHING
- ★ DESIGNED FOR MOBILE ENVIRONMENT
- ★ 420-450 MHZ VERSION AVAILABLE

144-147.99 MHz Model 400B
 129.95 Kit
 189.95 Wired & Tested
 WRITE FOR BROCHURE
 Available By Direct Mail Only

GLB ELECTRONICS
 404 CAYUGA CREEK ROAD-SOUTH CHEEKTOWAGA, N.Y. 14227

Used IBM MTST magnetic tapes - contact

HELP!

the typing department

IB needs your... please for more information. 32


FREE CATALOG

HARD-TO-FIND PRECISION TOOLS

Lists more than 1700 items—pliers, tweezers, wire strippers, vacuum systems, relay tools, optical equipment, tool kits and cases. Also includes four pages of useful "Tool Tips" to aid in tool selection.



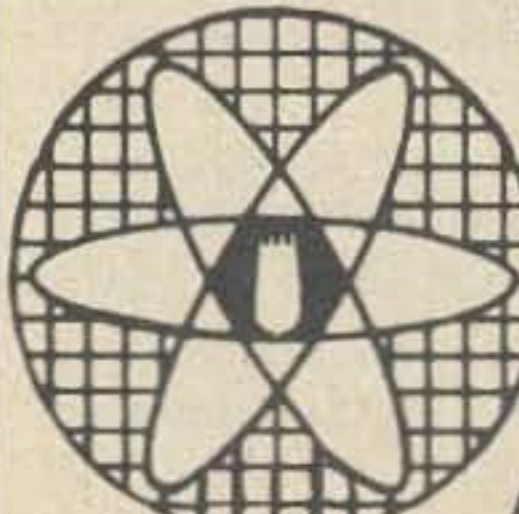JENSEN TOOLS and ALLOYS
 4117 N. 44th Street, Phoenix, Arizona 85018



DRAKE • REGENCY • HALLICRAFTERS
 ANT. SPEC. • SBE
 CUSH-CRAFT • MOSLEY • HUSTLER

WA9CFU LEE (217) 735-1265
 WA9OGD ROD

555 WOODLAWN ROAD LINCOLN, IL 62656

A-A-A SALES

bands 7.0-7.1 MHz, 14.00-14.35 MHz, 21.00-21.45 MHz, and 28.0-29.7 MHz.

NOTE: Region 2 is defined as follows: On the east, a line (B) extending from the North Pole along meridian 10° west of Greenwich to its intersection with parallel 72° north; thence by Great Circle Arc to the intersection of meridian 50° west and parallel 40° north; thence by Great Circle Arc to the intersection of meridian 20° west and parallel 10° south; thence along meridian 20° west to the South Pole. On the west, a line (C) extending from the North Pole by Great Circle Arc to the intersection of parallel 65°30' north with the international boundary in Bering Strait; thence by Great Circle Arc to the intersection of meridian 165° east of Greenwich and parallel 50° north; thence by Great Circle Arc to the intersection of meridian 170° west and parallel 10° north; thence along parallel 10° north to its intersection with meridian 120° west; thence along meridian 120° west to the South Pole.

(3) Notice of such operation, in accordance with the provisions of § 97.97, shall be given to the Engineer in Charge of the district having jurisdiction of the authorized fixed transmitter location.

§ 97.97 Notice of operation away from authorized location.

Whenever an amateur station is, or is likely to be, in portable operation at a single location for a period exceeding 15 days, the licensee shall give advanced written notice of such operation to the Commission's office specified in § 97.95. A new notice is required whenever there is any change in the particulars of a previous notice or whenever operation away from the authorized station continues for a period in excess of 1 year. The notice required by this section shall contain the following information:

- (a) Name of licensee.
- (b) Station call sign.
- (c) Authorized station location shown on station license.
- (d) Specific geographical location of station when in portable operation.
- (e) Dates of the beginning and end of the portable operation.
- (f) Address at which, or through which, the licensee can be readily reached.

[§ 97.97 revised eff. 10-17-72; VI(72)-1]

§ 97.101 Special provisions for mobile stations aboard ships or aircraft.

In addition to complying with all other applicable rules, an amateur mobile station operated on board a ship or aircraft must comply with all of the following special conditions: (a) The installation and operation of the amateur mobile station shall be approved by the master of the ship or captain of the aircraft; (b) The amateur mobile station shall be separate from and independent of all other radio equipment, if any, installed on board the same ship or aircraft; (c) The electrical installation of the amateur mobile station shall be in accord with the rules applicable to ships or aircraft as promulgated by the appropriate government agency; (d) The operation of the amateur mobile station shall not interfere with the efficient operation of any other radio equipment installed on board the same ship or aircraft; and (e) The amateur mobile station and its associated equipment, either in itself or in its method of operation, shall not constitute a hazard to the safety of life or property.

Logs

§ 97.103 Station log requirements.

An accurate legible account of station operation shall be entered in a log for each amateur radio station. The

log shall bear the call sign of the station and the signature of the licensee. The following information shall be recorded as a minimum:

(a) Written entries for all stations which are required only once, or when there is a change thereto.

(1) The signature of the control operator on duty and the call sign of his primary station, if he is other than the station licensee.

(2) The location of the station. Stations in mobile operation may enter the word "local" for amateur radio-communication conducted within 100 statute miles of the address shown on the station license, otherwise the location of the first and last radiocommunication of each day. Stations in mobile or portable operation shall make an entry showing compliance with § 97.97, if required.

(3) The input power to the transmitter final amplifying stage.

(4) The type of emission used.

(5) The frequency or frequency subband used for transmitting.

(b) Other entries for all stations which may be recorded in a form other than written but which can readily be transcribed by the licensee into written form:

(1) The dates of operation.

(2) Except for repeater stations, names of persons other than the control operator using the station, either directly or indirectly, for amateur radiocommunication.

(3) A notation of third party messages sent or received, including names of all participants and a brief description of the message content.

(4) The call sign of each station actually contacted, or other purpose of the transmission, i.e., those set forth in § 97.89. Stations in mobile operation and repeater stations may omit this entry. Control stations shall enter the call sign(s) of each station in the control link. An auxiliary link station shall enter the call sign of its associated station(s).

(5) All stations shall enter the times the station is put into, or taken out of, service. Stations other than those in mobile operation, control stations, auxiliary link stations, and repeater stations shall enter the times of commencing and terminating each exchange of radiocommunication.

【§ 97.103 revised eff. 10-17-72; VI(72)-1】

§ 97.105 Retention of logs.

The station log shall be preserved for a period of at least 1 year following the last date of entry and retained in the possession of the licensee. Copies of the log, including the sections required to be transcribed by § 97.103, shall be available to the Commission for inspection.

【§ 97.105 revised eff. 10-17-72; VI(72)-1】

EMERGENCY OPERATIONS

§ 97.107 Operation in emergencies.

In the event of an emergency disrupting normally available communication facilities in any widespread area or areas, the Commission, in its discretion, may declare that a general state of communications emergency exists, designate the area or areas concerned, and specify the amateur frequency bands, or segments of such bands, for use only by amateurs participating in emergency communication within or with such affected area or areas. Amateurs desiring to request the declaration of such a state of emergency should communicate with the Commission's Engineer in Charge of

MINIATURE SUB-AUDIBLE TONE ENCODER



- Compatible with all sub-audible tone systems such as Private Line, Channel Guard, Quiet Channel, etc.
- Glass Epoxy PCB, silicon transistors, and tantalum electrolytics used throughout
- Any miniature dual coil contactless reed may be used (Motorola TLN6824A, TLN6709B - Bramco RF-20)
- Powered by 12vdc @ 3ma
- Use on any tone frequency 67 Hz to 250 Hz
- Miniature in size, 2.5" x .75" x 1.5" high
- Wired and tested
- Complete with reed @ \$28.45 (specify frequency)
- Output 3v RMS sinewave, low distortion
- Postpaid - Calif. residents add sales tax

\$14.95

COMMUNICATIONS SPECIALISTS
P.O. Box 153, Brea CA 92621

HAL COMMUNICATIONS

HOT CARRIER DIODES:	HP2800	\$ 90.12/\$10.00	Matched by HAL	4/\$4.25
ZENERS:	1N4729(3.6v), 1N4733(5.1v), 1N4735(6.2v), 1N4738(8.2v), 1N4739(9.1v), 1N4742(12v), 1N4742(12v), 1 watt			\$ 75
LINEAR ICs:	709N	\$.75	709L, 710N	\$1.25
	MC1429G	\$3.75	MC1496G	\$3.25
			MC1590G	\$5.60
DIGITAL ICs:	F, L923	\$.90	MC767P	\$3.30
			MC723P	\$.95
MRTL:	MC788P	\$1.30	MC880P	\$3.50
	MC724P, MC725P, MC789P, MC792P		MC890P	\$2.00
	MC771P	\$1.75	MC970P	\$3.30
			MC9760P	\$5.45
DIP TTL:	7400, 7401, 7402, 7410, 7420, 7430, 7440			\$.48
	7404, 7405	\$.60	7441, 7495, 7496	\$3.00
	7472	\$.75	7473, 7474	\$1.05
	7486	\$1.15	7490, 7492, 7493	\$2.10
			MPF102	\$.60
FETS:	40673 MOSFET	\$1.60		
TOROIDS:	Indiana General CF102 Q6, CF102 Q1, CF101 Q2			\$.50
	CF102 Q3	\$1.25	FERROXCUBE FERRITE BEADS	10/\$1.25
CINCH IC SOCKETS:	8-ICS, 14-DIP	\$.60	10-ICS, 16-DIP	\$.70

MANY OTHER DEVICES AND COMPONENTS IN STOCK. WRITE FOR CATALOG.

HAL COMMUNICATIONS
Box 365L, Urbana IL 61801 • 217-359-7373

ACTIVE AUDIO FILTERS

IC'S FOR SUPER HIGH PERFORMANCE

CW FILTER (CWF-2) Get razor sharp selectivity; No impedance matching! BW (selectable) 80 Hz, 110 Hz, 180 Hz; Center frequency F=750 Hz; Skirts 60 db down at 1/2F and 2F; 4 op amps; 2"x3" PC board; \$14.95 wired, tested, guaranteed; \$12.95 kit.



CWF-2: \$12.95 KIT, \$14.95 WIRED

CW MINI FILTER (CWF-3) 1 1/2"x2" PC board; Center frequency F=750 Hz; 30 db down at 1/2F and 2F; BW 110 Hz; 2 op amps; \$8.95 wired, tested, guaranteed; \$7.95 kit.

LOW PASS FILTER (LPF-1) Resistors set cutoff 500 Hz to 20 KHz; Factory set to 2.5 KHz; Rolloff 48 db per octave; Input imp 1 M; Gain=1; 5 op amps; 2"x3" PC board; \$16.95 wired, tested, guaranteed; \$14.95 kit.

****please include 55¢ postage on all orders****

WRITE FOR FREE SPEC SHEETS!!!

MFJ ENTERPRISES

P.O. Box 494-C
Miss. State, Ms 39762



DYNAMIC ELECTRONICS INC.
Box 1131 Decatur AL 35601

WHY FIGHT QRM?

Copy code through the QRM with a NEW DE-101 Signal Discriminator. Built in ac Supply, factory tuned, and a one year warranty. \$29.95 plus \$2.00 shipping. Alabama residents add 5% tax.

SEMEX ELECTRONICS • 745 Cowper, #7 • Palo Alto, CA 94301
Order Desk: (415) 324-8460, 24hrs/day • Overnight service
Stocking: Schottky, High Speed, Low Power, & Standard TTL; DTL; Linears; C-MOS; LEDs; power transistors; etc; etc; etc...
in variety, quantity & quality equal to all the major advertisers and at prices competitively under. Call or write for complete information. (Pref. min. order: \$100). Money back guarantee on all goods.

27B

2-Meters... Need we say more?

ISC *Clegg* **DIVISION**
3050 Hempland Road
Lancaster, Pennsylvania 17601

the area concerned. Whenever such declaration has been made, operation of and with amateur stations in the area concerned shall be only in accordance with the requirements set forth in this section, but such requirements shall in no wise affect other normal amateur communication in the affected area when conducted on frequencies not designated for emergency operation.

(a) All transmissions within all designated amateur emergency communication bands other than communications relating directly to relief work, emergency service, or the establishment and maintenance of efficient amateur radio networks for the handling of such communications shall be suspended. Incidental calling, answering, testing or working (including casual conversation, remarks or messages) not pertinent to constructive handling of the emergency situation shall be prohibited within these bands.

(b) The Commission may designate certain amateur stations to assist in the promulgation of information relating to the declaration of a general state of communications emergency, to monitor the designated amateur emergency communications bands, and to warn non-complying stations observed to be operating in those bands. Such station, when so designated, may transmit for that purpose on any frequency or frequencies authorized to be used by that station, provided such transmissions do not interfere with essential emergency communications in progress; however, such transmissions shall preferably be made on authorized frequencies immediately adjacent to those segments of the amateur bands being cleared for the emergency. Individual transmissions for the purpose of advising other stations of the existence of the communications emergency shall refer to this section by number (§ 97.107) and shall specify, briefly and con-

cisely, the date of the Commission's declaration, the area and nature of the emergency, and the amateur frequency bands or segments of such bands which constitute the amateur emergency communications bands at the time. The designated stations shall not enter into discussions with other stations beyond furnishing essential facts relative to the emergency, or acting as advisors to stations desiring to assist in the emergency, and the operators of such designated stations shall report fully to the Commission the identity of any stations failing to comply, after notice, with any of the pertinent provisions of this section.

(c) The special conditions imposed under the provisions of this section shall cease to apply only after the Commission, or its authorized representative, shall have declared such general state of communications emergency to be terminated: however, nothing in this paragraph shall be deemed to prevent the Commission from modifying the terms of its declaration from time to time as may be necessary during the period of a communications emergency, or from removing those conditions with respect to any amateur frequency band or segment of such band which no longer appears essential to the conduct of the emergency communications.

OPERATION OF ADDITIONAL STATIONS

§ 97.108 Operation of a remotely controlled station.

(a) An amateur radio station may be operated by remote control only from an authorized control point, and only where there is compliance with the following:

(1) The license for the remotely controlled station must list the authorized remote control point(s). A photocopy of the remotely controlled station license must be posted in a conspicuous place at the authorized control point(s), and at the remotely controlled transmitter location. A copy of the system network diagram on file with the Commission must be retained at each control point. The transmitting antenna, transmission line, or mast, as appropriate, associated with the remotely controlled transmitter must bear a durable tag marked with the station call sign, the name of the station licensee and other information so that the control operator can readily be contacted by Commission personnel.

(2) The control link equipment and the remotely controlled station must be accessible only to persons authorized by the licensee. Protection against both inadvertent and unauthorized deliberate emissions must be provided. In the event unauthorized emissions occur, the station operation must be suspended until such time as adequate protection is incorporated, or there is reasonable assurance that unauthorized emissions will not recur.

(3) A control operator designated by the licensee must be on duty at an authorized control point while the station is being remotely controlled. Immediately prior to, and during the periods the remotely controlled station is in operation, the frequencies used for emission by the remotely controlled transmitter must be continuously monitored by the control operator. The control operator must terminate transmission upon any deviation from the rules.

(4) Provisions must be incorporated to automatically limit transmission to a period of no more than 3 minutes in the event of malfunction in the control link.

(5) A remotely controlled station may not be operated at any location other than that specified on the license without prior approval of the Commission except in emergencies involving the immediate safety of life or protection of property.

(6) A repeater station may be operated by radio remote control only where the control link utilizes frequencies other than the repeater station receiving frequencies.

【§ 97.108 added new eff. 10-17-72; VI(72)-1】

§ 97.109 Operation of a control station.

(a) Amateur frequency bands above 220 MHz, excepting 435 to 438 MHz, may be used for emissions by a control station. Frequencies below 225 MHz used for control links must be monitored by the control operator immediately prior to, and during, periods of operation.

(b) Where a remotely controlled station has been authorized to be operated from one or more remote control stations, those remote control stations may be operated either mobile or portable.

【§ 97.109 added new eff. 10-17-72; VI(72)-1】

§ 97.110 Operation of an auxiliary link station.

(a) An auxiliary link station may use amateur frequency bands above 220 MHz excepting 435 to 438 MHz for emissions. Frequencies below 225 MHz used by an auxiliary link station shall be monitored by the control operator immediately prior to, and during, periods of operation.

(b) An auxiliary link station may only be used for fixed operation from the location specified on the station license, and only when its associated station(s) is operated from its authorized land location.

【§ 97.110 added new eff. 10-17-72; VI(72)-1】

§ 97.111 Operation of a repeater station.

(a) Emissions from a repeater station shall be discontinued within 5 seconds after cessation of radiocommunication by the user station. Provisions to automatically limit the access to a repeater station may be incorporated, but are not mandatory.

(b) The transmitting and receiving frequencies utilized by the repeater station shall be continuously monitored by the control operator immediately prior to, and during, periods of operation.

(c) A repeater station may be concurrently operated on more than one frequency band, provided the necessary showings have been approved by the Commission for each frequency band of operation. Crossband operation of repeater stations is prohibited, i.e. both input (receiving) and output (transmitting) frequencies for a particular repeated transmission must be within the same frequency band. Operation on more than one output frequency on a single frequency band is prohibited except when specifically approved by the Commission. Repeater stations authorized to operate in conjunction with one or more auxiliary link stations may utilize an input frequency in a different frequency band provided the input frequency of the auxiliary link station(s) is in the same frequency band as the output frequency of the repeater station.

(d) A repeater station shall be operated in a manner so as to assure that the station is not used for one-way radiocommunication other than provided for in § 97.91.

(e) A station licensed as a repeater station may only be operated as a repeater station, excepting for short periods for testing or for emergencies.

【§ 97.111 added new eff. 10-17-72; VI(72)-1】

(To be continued next month.)

NES

NURMI ELECTRONIC SUPPLY

Department 27

1727 Donna Road · West Palm Beach, Florida 33401

PHONE — (305) 686-8553

HEP 170 2½A, 1000PIV, Diodes, Bulk Packs of 10, Factory Fresh.

10/\$3.00 — 100/\$25.00


RCA 40673 DUAL GATE MOS FET

Factory Fresh

5/\$6.00

KEYSTONE PERF BOARD

G-10 Glass Epoxy
Perf Board 3/64"
Thick.

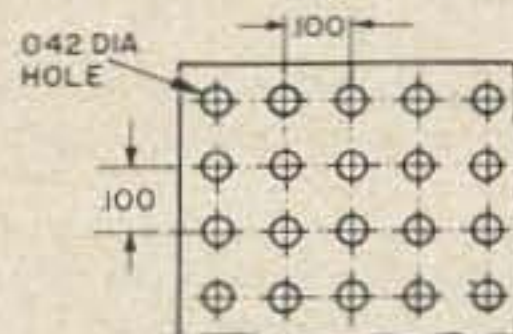

No.	Size (in.)	Price
--UNCLAD--		
4229	2 x 4½	\$.85
4230	2 x 6	1.09
4231	4½ x 6	1.55
4232	17 x 6	5.75
--COPPER CLAD ONE SIDE--		
4238	2 x 4½	1.35
4239	2 x 6	1.85
4240	4½ x 6	3.20
4241	17 x 6	6.70

JUMBO RED LED'S

Similar to Monsanto MV5020 Series

Your Choice of Lense

Red or Clear, TO-18

Size, 70MA., 140MW

3V, Another NES GUARANTEED SUPER

BUY.

2/\$1.00 — 12/\$5.00



LED READOUTS


MAN-1 Type, 0-9

Drive with 7447,

Characters 5/16 x 3/16.

20 MA per Section.

No. LRO-R	RED	\$2.95	4/\$11.00
No. LRO-G	GREEN	\$4.95	4/\$16.00

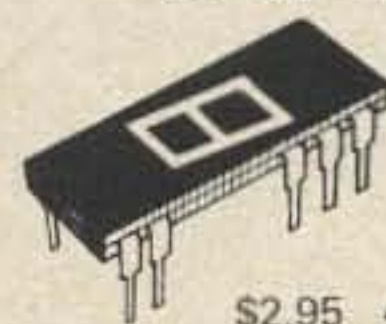

JUMBO LED READOUTS

Like MAN-1 Type Only BIGGER!!!!

Character Size: 3/4 x 7/16in.

Overall Size: 1 - 1/8 x 3/4 x 1/8

No. LRO-JR Only \$8.95

RF POWER TRANSISTORS

We did it again - All brand new with standard markings and most were manufactured this year. A major manufacturer dropped his RF power line and we bought his inventory.

2N5589	3 Watts Out	\$ 3.50
2N5590	10 Watts Out	6.00
2N5591	25 Watts Out	12.00
2N6080	4 Watts Out	5.00
2N6081	15 Watts Out	7.50
2N6082	25 Watts Out	10.00
2N6083	30 Watts Out	12.00
2N6084	40 Watts Out	15.00

All are Silicon NPN and power output ratings are good to 175 MHZ. Hurry some quantities are limited.



SPEAKER ASSORTMENT

1½ to 4 inch. Good Assortment of Low Z (8-16 ohm) speakers all new. Tell us what SIZE RANGE you want and we will do our best or just let us give you a full assortment. Thousands in stock. ALL NEW AND GUARANTEED.

Only 10/\$5.00

WE GUARANTEE WHAT WE SELL!!!!

We ship UPS whenever possible. Give street address. Include enough for postage, excess refunded in cash. Florida residents include 4% Tax.

Caveat Emptor?

Price — \$2 per 25 words for non-commercial ads; \$10 per 25 words for business ventures. No display ads or agency discount. Include your check with order.

Deadline for ads is the 1st of the month two months prior to publication. For example: January 1st is the deadline for the March issue which will be mailed on the 10th of February.

Type copy. Phrase and punctuate exactly as you wish it to appear. No all-capital ads.

We will be the judge of suitability of ads. Our responsibility for errors extends only to printing a correct ad in a later issue.

For \$1 extra we can maintain a reply box for you.

We cannot check into each advertiser, so Caveat Emptor . . .

WANTED: W.W.V. comparator, Lavoie LA-8000 or like equipment. Also need manuals for Lavoie. Stephen Gansky WA3AAO, Oak Hill Apts. N-408, Narberth PA 19072 215-664-0648.

SELL OR TRADE Hasselblad 500C camera with accessories \$1250, or factory sealed new 7553C or make offer! SASE for info. Jim K4YBB, 942 N. W. 116 St., Miami FL 33168.

PITTSBURGH Area Hams two improved lots for sale, Highest point in Allegheny County. Call WA8GFR evenings or weekends, 216-941-4751.

MUST SELL: New Signal One CX7A. Instruction & schematic manuals included., \$1300. Contact Lewis Grigsby Jr., Farmers State Bank, Pittsfield IL 62363 217-285-2194.

WE BUY late model Collins-Drake-Swan, top prices, cash, Associated Radio, 8012 Conser Overland Park, Kansas, 66204, Call: 913-381-5901.

ATTENTION C.A.P.ers, Regency RE-CAP2 with ASP-117 Antenna \$130, Hammarlund FM-50A with accessories, manual, Xtal's and GAM TG2 antenna \$90, Heath HM-2102, VHF Wattmeter \$20, Pat Butler, 1833 N. Indiana, Peoria IL 61603.

COMPLETE 36 page QSL catalog, 3rd edition. New "SPARKLING" QSLs. Hundreds of cuts, ten report forms, thirteen colored stocks, 25¢. Ten sample QSL cards. Corneilson's Quality QSLs, 321 Warren St., N. Babylon, N. Y. 11704.

EQUIPMENT FROM 73

The following list of gear, unless otherwise noted, consists of brand new equipment purchased for testing purposes only. Some have been tested, some remain unopened in original cartons. We are offering this gear at a considerable discount on a first-come-first-served basis. Please send Money Orders or Certified Checks only to 73 Magazine, Peterborough NH 03458.

Cap-Com 40m solid state SSB xcvr	\$150
Heath IB-101 counter with Vanguard Scaler	\$250
Clegg 27B 2m xcvr	\$380
IC-22 2m FM xcvr	\$246
Midland 13500 2m xcvr	\$200
Midland 13509 220 xcvr	\$200
Tempo CL-220 220 xcvr	\$200
Clegg FM-21 220 xcvr	\$255
Regency HR-6 6m xcvr	\$190
HR2MS 8 channel scanning 2m xcvr	\$255
TME-H-LMU 16 channel rcvr	\$255
Digital Logiclocks	\$ 80
Dycom 2m repeater	\$425
Wilson 7 element 10 & 15m beam (pick-up only)	\$250
Waller 60A power supply	\$105
Standard sr-c 120/5 power sup.	\$ 44
Gladding 12V power supply	\$ 60
SBE Scannavision	\$650
Robot Monitor	\$265
Robot Camera	\$265
AX 190 amateur rcvr	\$200
SX 190 SWL rcvr	\$200
Pickering KB-1 keyboard	\$200
TPL 502-B 2m Amp 1w/40w	\$110
TPL 502 2m Amp 10w/45w	\$ 90
Heath HW-202 w/encoder	\$180
Heath HWA-202-1	\$ 30
Heath HA-2022 amplifier	\$ 70
Gladding 8 channel scanner	\$110
Gladding HI-Scan	\$150
Regency TMR-8-U Scanner	\$140
Tempo fmh charger	\$ 30
Heath HM-2102 wattmeter	\$225
GTX-2 FM xcvr	\$350
Newsom 2m KW amplifier	\$275
Temp-ONE SSB xcvr	\$ 80
External VFO	\$ 80
AC-One power supply	\$480
FPM 300 SSB xcvr	\$ 90
Heath IC-2009 calculator	\$340
SBE 450 FM xcvr	\$130
MITTS calculator w/ac adaptor and case	\$320
Memory-Matic 8000	

FACSIMILE PAPER for DeskFax units: \$1.95 per box. 6 boxes for \$10.50; for weathermap recorders; \$4.25 per box, 4 boxes for \$16. Jim Cooper, P. O. Box 73, Paramus NJ 07652.

WANTED: ARC-5/VHF components. Mounting Backs MT-65 and MT-71. Control Unit C-42, Junction Box J-28. Also need connectors. WB8NLM, 146 Schonhardt St., Tiffin OH 44883.

"BRAND NEW": Clegg 66er in original factory carton, \$145. Money order or certified check. J. A. LaTorre, P. O. Box 521, Lawrence MA 01842.

COLLINS FOR SALE: Individual prices are indicated. For package deals please write. 32S3 SN 12091 \$650, 75S3 SN 14276 \$600, KWM 2 A SN 11535 \$750, 516F2 P. S. \$75, 312B4 station control \$125, 30L1 linear amp \$350. Jack Aviv, WA2KNC, 106 Glenn Avenue, Lakewood NJ 08701.

CANADIANS — FREE 120 page electronics catalog ETCO-B, 464 McGill, Montreal.

DESK-FAX TRANSCEIVERS as removed from commercial service (working). \$14.95 each, or \$25 pair. Jim Cooper, P. O. Box 73, Paramus NJ 07652.

MOBILE IGNITION SHIELD gives more range, no noise. Everything from economical suppression kits to custom shielding. Literature. Estes Engineering, 543-S West 184th Street, Gardena, Calif., 90248

MOTOROLA P33-BAC 5W Handi-Talkie, excellent condition with antenna, mike, Ni-Cads, 34/94 and 94/94 — \$95; Heath HX-20 80-10 meter SSB and CW transmitter, HR-20 80-10 meter SSB, CW, and AM receiver, and HP-20 AC power supply, good condition — \$195. FOB, W5PNY, 2506-A, 35th St., Los Alamos NM 87544.

PLEASE donate all of your unused amateur equipment, any ham band, to, Association for the Blind ARC, 1844 Broadway, Kansas City MO.

"DON AND BOB" new guaranteed buys. Discount prices plus full warranty. Write for low prices: Hy-Gain TH6DXX, TH3MK3, 204 BA, DB1015A, 402BA; Mosley CL33, CL36, S402; Triex MW50, MW65, W51 (FOB, Cal); Midland 13500 \$219.95, 13520 W-T \$209.95; Regency HR2B; SBE 144 \$199.95; Standard 826 MA, 146A; CDE Ham-M \$99.00, TR44 \$59.95, AR22R \$31.95, Belden 8448 rotor cable 10¢/ft; Belden 8214 RG8 FOAM 17¢/ft; 8237 RG8/U 15¢/ft; Amphol PL259 49¢; Hallicrafters FPM300 new demos, factory warranty repair needed, \$460.00 each; Rohn 25G, 45G tower, accessories stock; Used guaranteed: Collins 75A4 \$345.00, Kenwood R599 \$300.00; T599 \$350.00, write demo prices; Heath SB300, filters \$250.00; Write quote Swan, Drake, Eimac; Motorola HEP 170 epoxy diode 2.5A/1000 PIV 29¢, \$25.00/100 Lot; 1972 Radio Masters \$3.50; Motorola Semiconductor Data Series \$7.50; Calrad dual-meter SWR-relative power meter, to 150 MHz \$15.95; #15 antenna wire \$1.95/C; Write quote items not listed. Shipping charges collect. Madison Electronics, 1508 McKinney, Houston, Texas 77002. 713-2242-668 Nite/weekend 713-497-5683.

TELETYPE PAPER, surplus 2-copy, 12 rolls/\$8, 47 lb.; paper tape, 11/16" (175 mm) wide, 10 rolls/\$3, 12 lb.; Please add postage; Kleinschmidt ribbons 12/\$6 postpaid. SASE descriptive list. M. A. Massingill, 2500 Young Rd., Modesto CA 95351.

JEHOVAH'S WITNESSES who are amateurs please write: Bob Ellis WA4UQQ, 160 Lagoon Road SE, Winter Haven FL 33880, or call: 813-293-3595.

ANTIQUA RADIO BUFFS. Do you need a schematic for your radio? For information send S.A.S.E. showing make and model number. Joseph C. Crockett K3KUL, 762 S. Gulph Road, King of Prussia PA 19406.

MOTOROLA NICOR, MOTRAC CRYSTALS, All Sentry or Motorola. 146.10, .16, .19, .22, .25, .28, .34, .52, .76, .79, .82, .85, .88, .94, transmit and receive. Crystals \$4.00, Channel Elements \$5.00. WA0HBX, Box 55, Savannah, Missouri, 64485.

SB-144 TRANSCEIVER with Hamtronics preamp and extra 25-85 crystals, \$150. Normand Viens WA1LGP, 210 Nugent Hall, RPI, Troy NY 12181.

WANTED experienced electronic assembler. Install parts on chassis and panels. Prepare harnesses, wire and solder in accordance with schematics. Steady employment with scientific instrument manufacturer. Pleasant surroundings. Interesting work. Good pay with benefits. Located in San Fernando Valley. Write or call in person. W. D. Dillon & Co., Inc., 14620 Keswick St., Van Nuys CA 91407.

TUCSON HAMFEST, October 28, 144 West Lester, Tucson, Arizona. Inside flea market, prizes. Tucson Repeater Association, Old Pueblo Radio Club, Box 6497, Tucson AZ 85733.

PUNCH through the QRM, get 10 db talk power boost with AMPRESS speech processor, only \$39.95. C. E. Cox Company, 2415 S. Broadway, Santa Ana CA 92707.

HOOSIER ELECTRONICS — Your ham headquarters in the heart of the Midwest where only the finest amateur equipment is sold. Individual, personal service by experienced and active hams. Factory-authorized dealers for Standard, Clegg, Genave, Drake, Regency, Hallicrafters, Tempo, Kenwood, Ten-Tec, Midland, Galaxy, Hy-Gain, CushCraft, Mosley, Hustler, Ham-M, Sony, plus many more. Orders for in-stock merchandise shipped the same day. Write or call today for our quote and try our personal, friendly Hoosier service. Hoosier Electronics, R. R. 25, Box 403, Terre Haute IN 47802, 812-894-2397.

ENHANCE, frame and organize your QSL cards with 20 pocket plastic holders. Two for \$1, seven for \$3, prepaid-guaranteed. TEPABCO, Box 198M, Gallatin, Tennessee 37066.

W2NSD/1 cont. from page 102

has been audited. This drives accountants out of business in a hurry.

The whole IRS system is pernicious. Look what it does to judges—they are frightened too. No one is safe from an audit — and, as Milton Friedman pointed out recently in *Playboy* in an interview, no one is safe from being arrested and put in jail by the IRS on fraud, no matter how honest they are. Judges have to be extra careful with their careers if they want to move ahead — and what judge doesn't have an eye on the Supreme Court bench? A big black tax suit in his record could ruin him.

The system is no better on the IRS agents themselves, who are prisoners of a soul-destroying situation. They *have* to produce. When they audit they are expected to come up with money. And promotion is tied in with money produced, even though this is not the official policy of the IRS — this is the way it works. And an agent that loses a case loses his career and may end up as a bail bondsman in Fitchburg, Massachusetts. This results in desperate measures being brought against taxpayers and is the main reason why they stoop to phone taps and mail checking.

How far will they go? Well, our old records are not locked up with extreme care, and they have been gone over by the IRS agents several times. I recently went through what we had left to see what some of the checks might be that they had brought up as being personal expenses. Every single

record that we had of cancelled checks, invoices, all such records were missing. Were they kept by IRS agents? Did someone sneak into our attic and steal those particular papers, leaving all other records such as subscription sales, book sales, payments for articles, advertising sales, bulk sales, newsstand sales . . . etc? Weird.

This Gestapo-type branch of the legislative part of our government will operate in this way just as long as everyone is afraid of them and no one does anything to back them down. The revelations during the Watergate hearing of IRS use for political harassment brought this situation into the light for many taxpayers for the first time. The people who don't want to be bothered with this sort of mess are the ones that keep it going — and they are the ones who will get caught up and trampled eventually.

Now that the FBI has been backed off a bit — and the CIA is taking it easier — perhaps it is time to stop the really vile things that IRS is doing and get us a little more away from being a police state.

You can bet that I'll be taking notes on this case and let you know just what kind of police-state tactics are used against me. Frankly I don't see how the case can end up with anything but an apology from the IRS and perhaps even a prosecution of one or more of their agents for perjury.

Watch for more news.

SEPTEMBER REPEATER TEST

Are the new repeater rules being observed?

Repeater groups seem to agree that the new regulations not only are without the saving grace of reason, they are also extremely repressive. Now that all of the new regulations are in effect, how many repeater groups are abiding by them and how many are ignoring them — a la our more successful cousins on 27 MHz?

A test was made in mid-September to get a feel of how things are going. A team set up a test site on a high mountain and checked the number of repeaters on the various channels which were heard in a period of 10:00 to 10:30 PM, noting the number on each channel. Then, the next morning at 5:00 to 5:30 AM the same test was made. The results may be of interest. During the morning test a transmission was made four times on each channel asking if there was anyone on channel. No answers were received on any channel.

There were 30 repeaters clearly heard in the evening test. Twenty-five were there in the morning test. Fifteen of the twenty-five had identification. Only three of the five repeaters which had been turned off for the night had identification in the night test.

This would indicate that in this test 10% of the repeaters were operating according to the identification and monitoring rules. 83% were staying on the air and not being turned off at night. Ten had WR calls (30%).

So here we have about 90% of the active repeater groups openly flaunting the regulations. This is historical, in a way. In the past repeater

groups have always been in the forefront of legality — bending over backwards in most cases to make sure that everything was according to Hoyle. They haven't caught up with the CBers yet in their open disdain for rules, but it seems obvious that Walker has found a way to destroy the time-honored rapport between the FCC and the amateurs.

18803 RECONSIDERATION

In early August FCC Chairman Dean Burch called in response to the furor over the repeater regulations and suggested that a hearing be organized to familiarize the Commissioners with the scope of our problems and the proposed changes in the regulations that might set things right.

Chairman Burch agreed to have the seven Commissioners attend the hearing and I promised to have representatives of the major repeater councils present to present the case and answer any questions.

Mr. Burch further asked that a paper be provided the Commissioners a month before the hearing to familiarize them with the problems and suggested rule changes.

The above may come as quite a shock to the ARRL HQ staff who have been urging conciliation with Walker and who have been openly critical of my efforts to get through to a level that could help us get the changes we need. Hollaring does work now and then.

The hearing is scheduled for January 14th in Washington and I plan for those council representatives who are going to help with the hearing to be in Washington a day early so that the schedule for the presentation can be worked out carefully and areas of expertise be established for answering questions.

I have already been in contact with many of the major repeater councils and have asked each for a resume of the problems posed by 18803 — the proposed changes in the regulations — and the reasons for these changes.

If there are any councils that have not been contacted and who wish to field a representative for this critical hearing, please get in touch with me. There are several requirements, and they are important. A rep must be very familiar with both repeaters and the regulations — he must be well spoken and not given to any unnecessary talking — he must be able to think fast and not get sidetracked by personal questions or problems of his repeater — his group must furnish me with a resume of problems and proposed changes by November 15th — and he must appear in Washington at his or the council's expense for the

hearing. I hope that sounds reasonable.

In my past talks with FCC officials I have found that a great deal of their time has been wasted by excursions into individual problems — and listening to amateurs who have a serious need to talk, but who listen very little.

It is unfortunate that there are quite a few repeater owners who suffer from this problem. One in Connecticut comes to mind immediately — a chap who is a laughing stock at the Commission because his problem is so serious.

This is our chance to get the word right to the top — and, as far as I know, this is the first time anything like this has ever happened. I suspect that the July 9th session with the ARRL may have helped to open the ear to our troubles.

By the way, the hearing is for the purpose of discussing regulations already enacted, not any under consideration, so we'll have to soft pedal our screams of anguish on the 224 MHz CB proposal and stick to the repeater rules. There's plenty there to keep us busy.

FCC ACCUSED!

The Bureau of National Affairs, an organization which supplies legal and financial data to businessmen, recently charged that the FCC has become a haven for attorneys who are failures at the bar. The BNA pointed out that about 25% of the lawyers hired last year by the FCC failed the bar exams they were required to take.

No wonder the amateur regulations have gotten so screwed up in the last year! (Thanks WN5GUN)

NEWSWEEK ATTACKS TOO

The September 10th issue of Newsweek (page 53) put CB in fair perspective and this publicity should help to slow down the FCC's anxious drive to please the EIA at all costs. The false cry for help in New Mexico made headlines all over the country and helped to blacken the eye of CB — two hundred rescuers and 22 planes involved in the search — hoax. (Thanks W9BOZ)

WRITING CONGRESS SIMPLIFIED

Rather than have to sit down and work out a long and complicated letter to your congressman explaining what the problems are and what you would like him to do about it — a writing chore that manages to knock out about 99.99% of the letters that might otherwise get to congress — 73 has prepared a short newsletter (two sheets) which outlines the whole situation.

This newsletter is available for free from 73 Magazine — send a self-addressed stamped envelope (business size).

The newsletter discusses the purposes of amateur radio and how we are meeting those purposes with great success. It goes into the main areas of communications that amateurs have pioneered — and this is just about every major communications technique in use today. It explains why amateurs need help now, outlining some of the devastating regulations Walker has laid on us.

There is a brief explanation of why all of the major developments in communications have been made by amateurs — and also an explanation of what repeaters are and how they work. Just in case your congressman is not sure of the difference between CB and hams, this is also covered.

The ending of the paper tells your congressman how he can help us — and you.

Remember — it is extremely important to write to your congressman and to your senators — and it won't hurt to send along a copy of this letter we have made for you.

Why haven't we just bulk mailed the letter to congress? Because it takes your personal covering letter to get it past the round file in the mail room. We've worked hard to make this for you — will you help by seeing that it gets where it should?

When writing that covering letter, address it as follows — for,

Representatives:

The Honorable
House of Representatives
Washington DC 20515

Dear Mr.

and for Senators:

The Honorable
United States Senate
Washington DC 20510

Dear Senator

The address for the newsletters is 73 Magazine, Peterborough NH 03458, and don't forget the SASE.

FCC MEN GRIPE!


A little note in the Federal Times said that career civil servants in the FCC have been griping at the large number of ex-military men who have been brought in by an ex-Air Force officer. One division of the Commission has been called a "little Pentagon." (Thanks WB5BKM)

... WAYNE

common purpose because we have allowed ourselves to become divided. And unless this senseless division is healed and until the fraternity has been reunited in vigorous pursuit of its objectives, we will remain ineffective and powerless to stand up and fight for our priviledges which are in certain jeopardy.

The FCC is empowered to regulate the communication art by the Act of Congress of 1934, as amended. And I suggest that every concerned amateur look into this document which can be found in many public libraries and is available for a nominal charge from the United States government printing office. See what it is that the FCC is empowered to do and determine for yourself whether or not the amateur and citizen's radio service division is living up to those responsibilities with which it is charged. If you find, as I have, that there are questions to be answered and satisfaction required, then sit down and write your elected representatives, your senators, your congressmen, noted hams who are in the public eye. . .and there are many of them. Forget about which faction you belong to, or which magazine you subscribe to, or which publisher's views you adhere to, or what you feel about this or that league. Remember that you are a member of a unique fraternity of communicators and technicians and that the really important thing right now is the survival of the fraternity under honest and realistic

(More New Products)

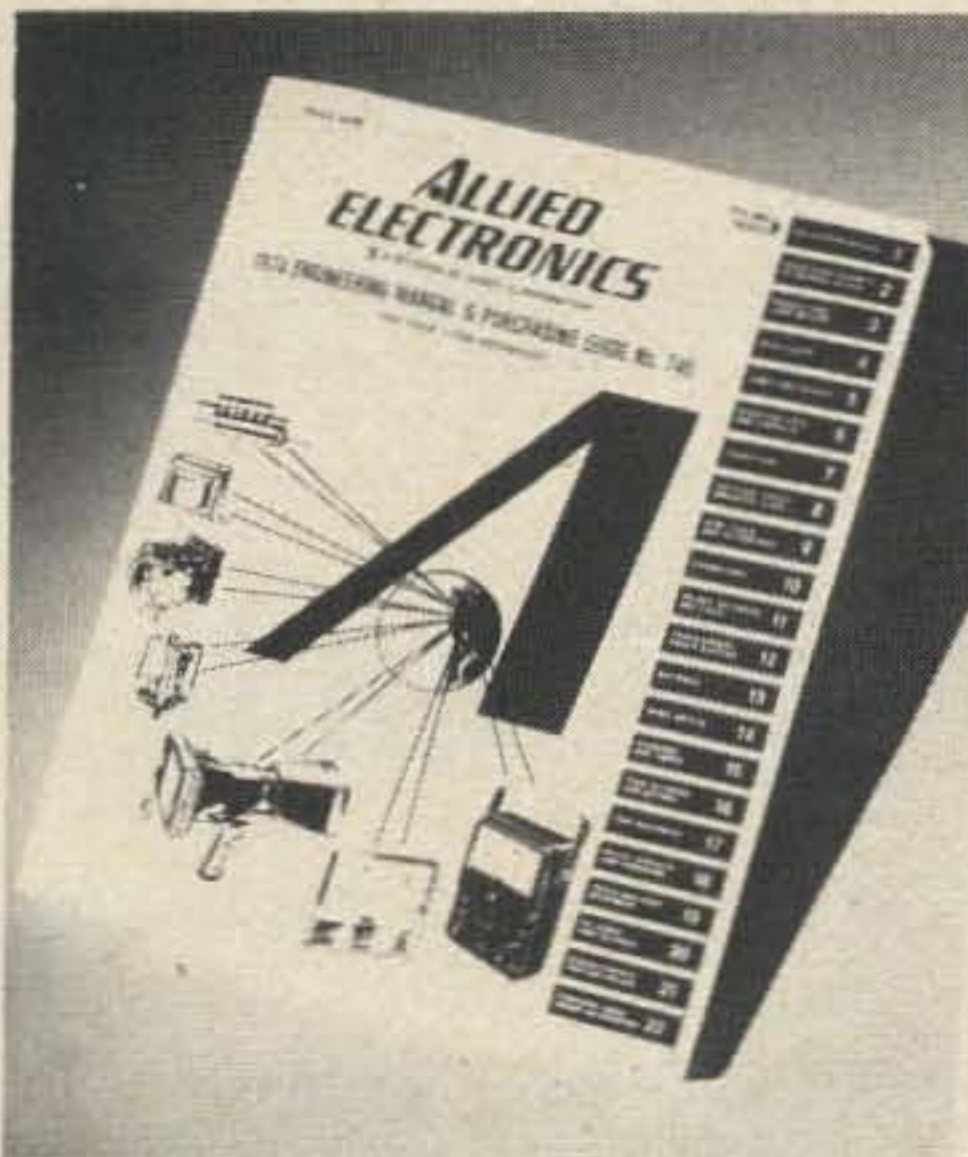

ing of *Engineering Drawings* of a electrical components. All physical dimensions are given to allow efficient design of electronic "packages" before components are purchased.

Allied has also introduced a new policy for obtaining their catalog: instead of the \$5 price, or \$10 order requirement, *anyone* can now obtain their catalog for the cost of postage and handling. For your copy, send \$1 for postage and handling to: *Allied Electronics, 2400 W. Washington Blvd., Chicago IL 60612.*

regulation. Don't ask for anarchy. . . ask for common sense application of logic in rulemaking.

If enough of us can see the real and hidden dangers in the present situation, there may be hope yet and time yet. But, if we wait for the other guy to do the job, we will all be lost.

Norman Joseph Sternberg
W2JUP/WB2ZWR
Levittown NY

AMEN!

HAM SOLITUDE

Just finished renewing my subscription to "73" for two more years.

Since I'm the only amateur radio operator in Big Stone City, S. Dak., I'm glad to have a friend like "73" to keep me up to date on the latest goings-on in the amateur radio world. Keep up the good work.


David L. Martin, Sr. WB0CIY

WANT A GUEST?

I wonder if there are amateurs in England, Europe, and Scandinavia who would enjoy a visit from a travelling American ham. I'm planning on making a trip to these areas next summer and as I found out last summer, a trip can be made much more enjoyable by having contacts with foreign hams.

Jon Forrest WB6EDM
21414 De La Osa St.
Woodland Hills CA 91364

P-C DESIGN TEMPLATE

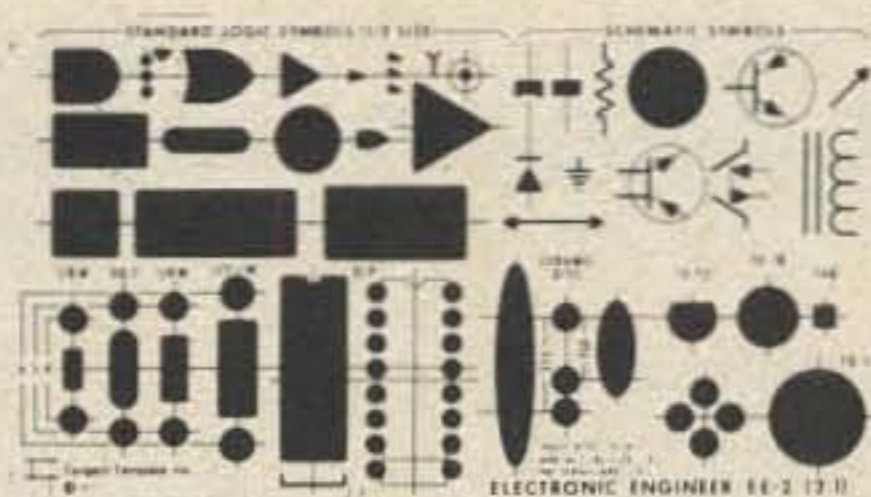

The *Electronic Engineer* template series incorporates on each template the most useful logic, schematic and component layout patterns necessary for the majority of electronic circuit design requirements. Each template features a complete set of usable schematic and logic diagrams. Also included are the basic component layout patterns required for laying out scaled printed circuit board designs. Featured are basic resistors, capacitors and semiconductors used in most electronic equipment.

The templates are made from green tinted plastic and are priced as follows: EE-1 (1:1) \$4, EE-2 (2:1) \$5 and EE-4 (4:1) \$7. The ratio indicates the size of the component layout patterns featured on each template.

Contact: *Tangent Template, Inc., P.O. Box 20704, San Diego CA 92120.*

ATTENTION ADVERTISERS

I quit the League in 1963, also the firms that cut you off their advertising budgets. How stupid they were, they cut off the wrong outfit and made a helluvamess.

I noted that one of the firms which I stopped patronizing in '63 began to advertise in 73 in February of this year. I read the ad, and on my way to Portland stopped off to see a friend in Albany where I looked at the new FPM300 Hallicrafter transceiver, tried it out - then didn't go to Portland! Came directly home with a new 300. If I hadn't seen their ad in 73, I wouldn't have even looked at it, as I was going to Portland to buy another make. Chalk up one for 73. When I registered the new 300, I said I saw the ad in 73 and hadn't bought any Hallicrafter equipment since 1963. There wasn't much room on the registration card, but I was able to imply that the big outfits should have gotten into the fight to save ham radio. Keep slugging, Wayne.

Paul J. Rasmussen K7EML
Sutherlin OR

LOBBY

I agree with you that ham radio needs more political support in Washington. Probably a lobby is the answer, and I would be willing to contribute money to support one.

Ivan T. Schultz, M.D. WQFDM
Benedict MN

SUCCESS STORY

I would like to compliment you on your fine magazine - especially the great construction articles. I have recently finished a homebrew project using IC's and printed circuit board. I don't remember what it is supposed to be as I misplaced the issue of 73 I built it from.

As most people do, I made several slight changes in the design. I eliminated the power supply as my house has 110 volt outlets all over and I could conveniently plug this little gem in wherever I wished - even in my ham shack. The black areas are soot from the smoke that poured forth when I first *fired* it up. I thought this was going to be a recurring problem but it hasn't happened since.

Hope to see more of the same solid state construction articles and also high power transmitter and amplifier projects. I really want to get my hands into something that uses 5 kV or so.

By the way, does it really save money in the long run to get a life membership to 73 Mag?

Jack R. Main W4Y CZ
Norfolk VA

If you start applying 5 kV to your IC projects it will certainly save US money!

ORDER

RUSH

RUSH

RUSH

(check one)

Name _____

Call _____

Address _____

City _____

State _____ Zip _____

\$ _____ enclosed

TRANSMIT	PAIR	RECEIVE
<input type="checkbox"/>	146.01-61	<input type="checkbox"/>
<input type="checkbox"/>	146.04-64	<input type="checkbox"/>
<input type="checkbox"/>	146.07-67	<input type="checkbox"/>
<input type="checkbox"/>	146.10-70	<input type="checkbox"/>
<input type="checkbox"/>	146.13-73	<input type="checkbox"/>
<input type="checkbox"/>	146.16-76	<input type="checkbox"/>
<input type="checkbox"/>	146.19-79	<input type="checkbox"/>
<input type="checkbox"/>	146.22-82	<input type="checkbox"/>
<input type="checkbox"/>	146.25-85	<input type="checkbox"/>
<input type="checkbox"/>	146.28-88	<input type="checkbox"/>
<input type="checkbox"/>	146.31-91	<input type="checkbox"/>
<input type="checkbox"/>	146.34-94	<input type="checkbox"/>
<input type="checkbox"/>	146.37-97	<input type="checkbox"/>
<input type="checkbox"/>	146.40-147.00	<input type="checkbox"/>
<input type="checkbox"/>	146.52-52	<input type="checkbox"/>
<input type="checkbox"/>	146.94-94	<input type="checkbox"/>
<input type="checkbox"/>	147.00-00	<input type="checkbox"/>
<input type="checkbox"/>	147.99-39	<input type="checkbox"/>
<input type="checkbox"/>	147.96-36	<input type="checkbox"/>
<input type="checkbox"/>	147.93-33	<input type="checkbox"/>
<input type="checkbox"/>	147.90-30	<input type="checkbox"/>
<input type="checkbox"/>	147.87-27	<input type="checkbox"/>
<input type="checkbox"/>	147.84-24	<input type="checkbox"/>
<input type="checkbox"/>	147.81-21	<input type="checkbox"/>
<input type="checkbox"/>	147.78-18	<input type="checkbox"/>
<input type="checkbox"/>	147.75-15	<input type="checkbox"/>
<input type="checkbox"/>	147.72-12	<input type="checkbox"/>
<input type="checkbox"/>	147.69-09	<input type="checkbox"/>
<input type="checkbox"/>	147.66-06	<input type="checkbox"/>
<input type="checkbox"/>	147.63-03	<input type="checkbox"/>
<input type="checkbox"/>	147.60-00	<input type="checkbox"/>

TRANSCEIVER

- Drake TR-22
- Drake ML-2
- Regency HR
- Ross & White
- Simpson
- SB-144
- Sonar 3601
- Standard 146(A)
- Standard 826
- Swan FM2X
- Tempo FMP
- Tempo FMV
- Tempo FMA
- Tempo FMC

TOTAL _____

VALPEY FISHER CORP. 1015 FIRST, HOLLISTON, MASS 01746

Crystals are available for the following two meter FM transceivers at this special price offer: Drake, Regency, Simpson, SBE, Sonar, Standard, and Tempo. Please specify the make and model transceiver when you place your order so we can be sure to send you the correct compensated Crystals. Crystals are available for other FM transceivers and other channels... please write for prices... very reasonable prices.

just \$3.⁷⁵ each

...plus 50¢ per complete order for postage and handling.

This low price for Drake — Regency — Simpson — SBE — Sonar — Standard — and Tempo. ONLY

Eastern customers may appreciate our fast mail service... it can save you days to weeks on your order. Western customers may appreciate getting crystals that work on channel the very first time and don't have to be returned for further compensation to match your set.

Valpey Fisher — 40 long hard years of experience.


VALPEY FISHER CORP.

A VALTEC CORPORATION
1015 FIRST, HOLLISTON MASS 01746


Dealers — *Have we got a deal for you!!!*

2nd generation slo-scan system

Venus Slo-Scan TV monitor

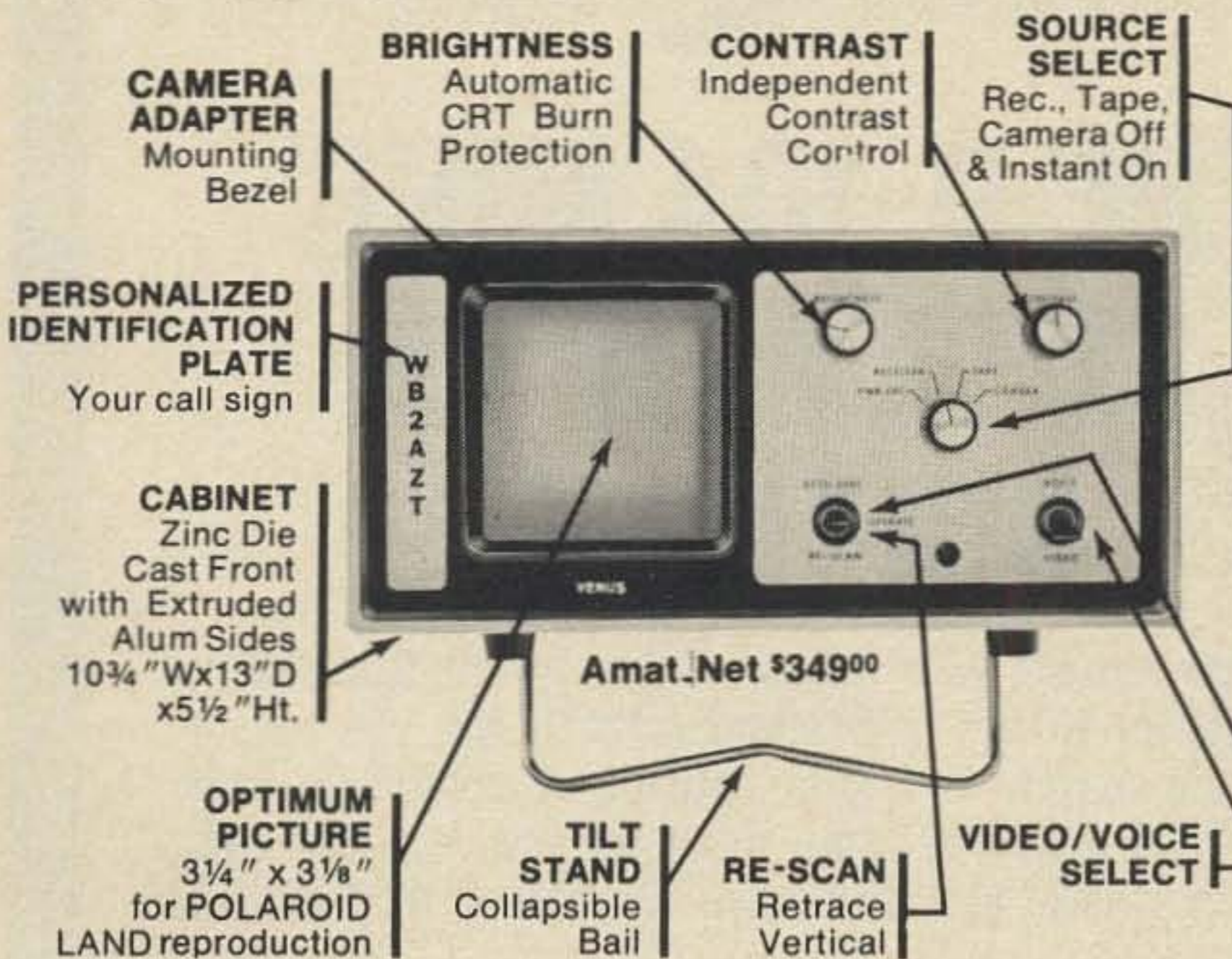


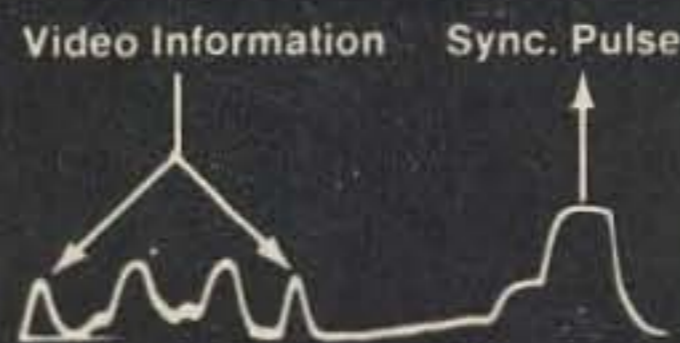
Actual unretouched photo taken from the Venus SS2 using a Polaroid Color Pack II Camera mounted on the Venus P-1 Camera Adapter



ACCU SYNC[®]
Diagnostic and Tuning Aid

CAMERA ADAPTER P-1 enables you to take photographs "right-off-the-air" and accepts a Polaroid Color Pack or a Polaroid Square Shooter.

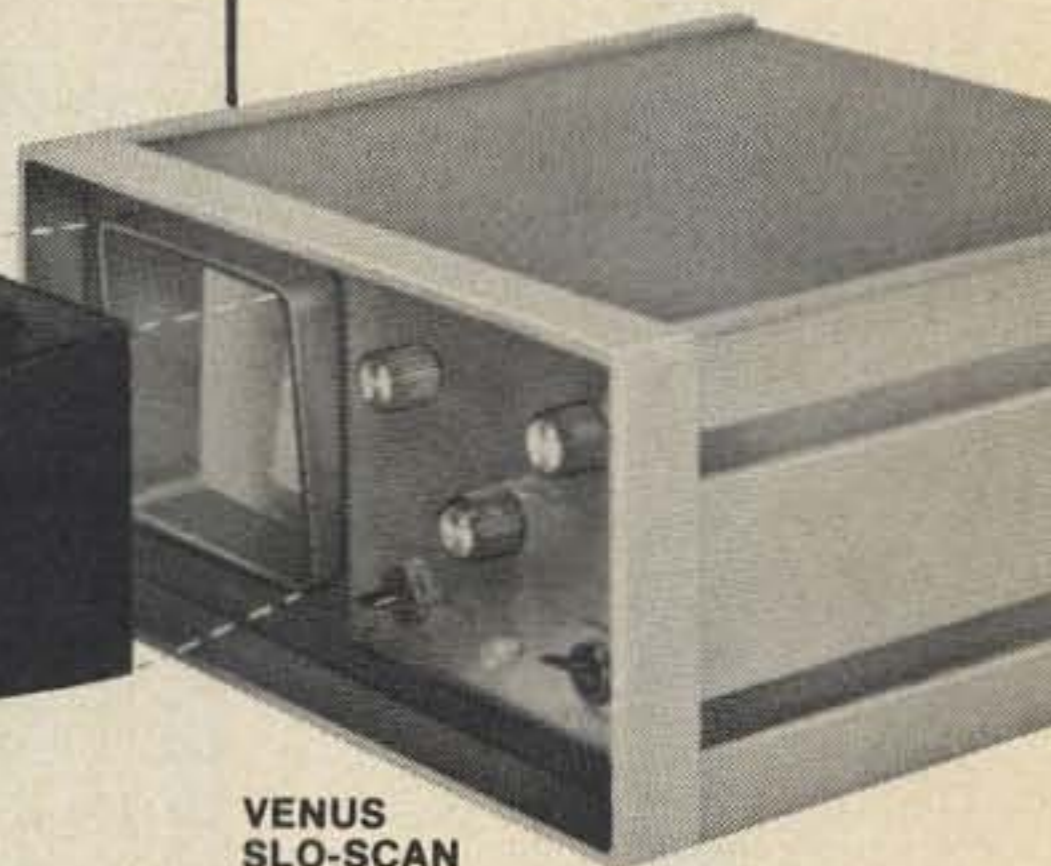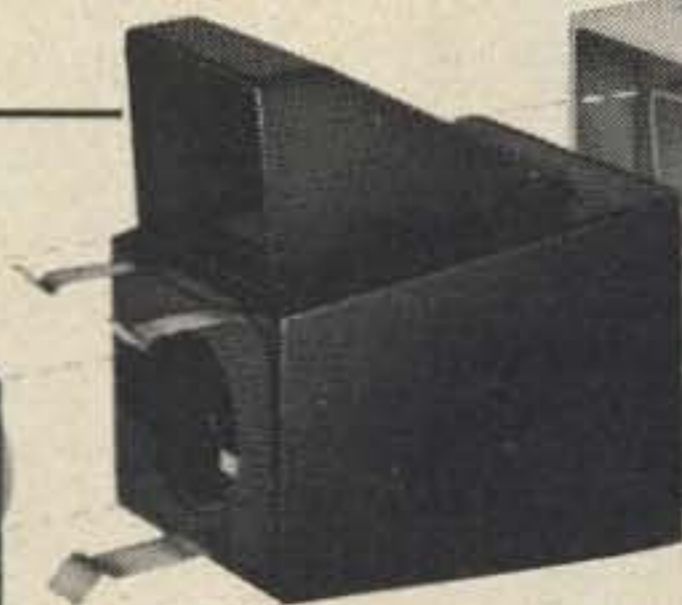- Allows photographing in a lit room
- Simple-snap mounting for quick and accurate picture taking
- Simultaneous hood viewing of picture being taken by camera
- Instant QSL via SSTV
- Amat. Net \$34⁵⁰



FRAME GRABBER

Venus' Cassette F and T Series are continuous loop cassettes that allow you to easily pre-record and send SSTV information

F1 Single frame cassette Amat. Net \$375


TG Grey Scale Generator Amat. Net \$650

TC Checkerboard Amat. Net \$650

V1 VIEWING HOOD

Uniquely designed for wide angle viewing by more than one operator.


Amat. Net \$1450

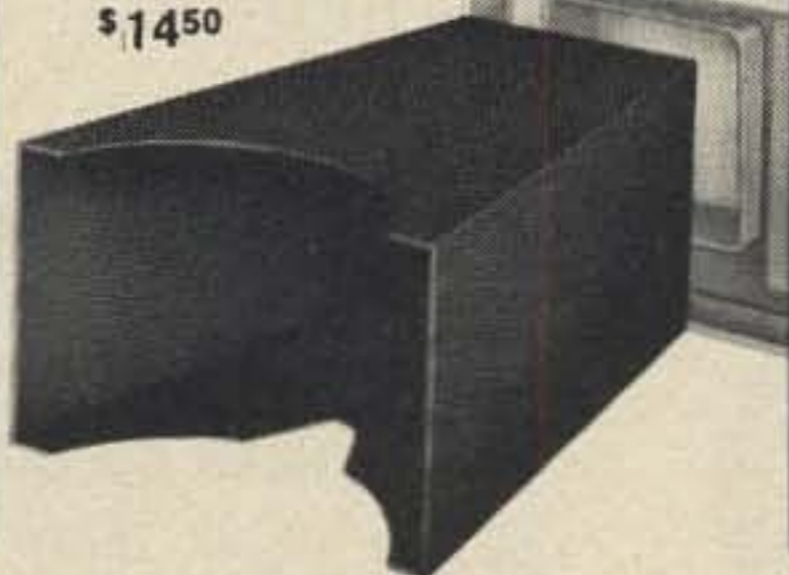

Coming in December CAMERA AND SCAN CONVERTER CC-1

Projects your VIDEO real time on any conventional home TV while simultaneously scan converting to SSTV

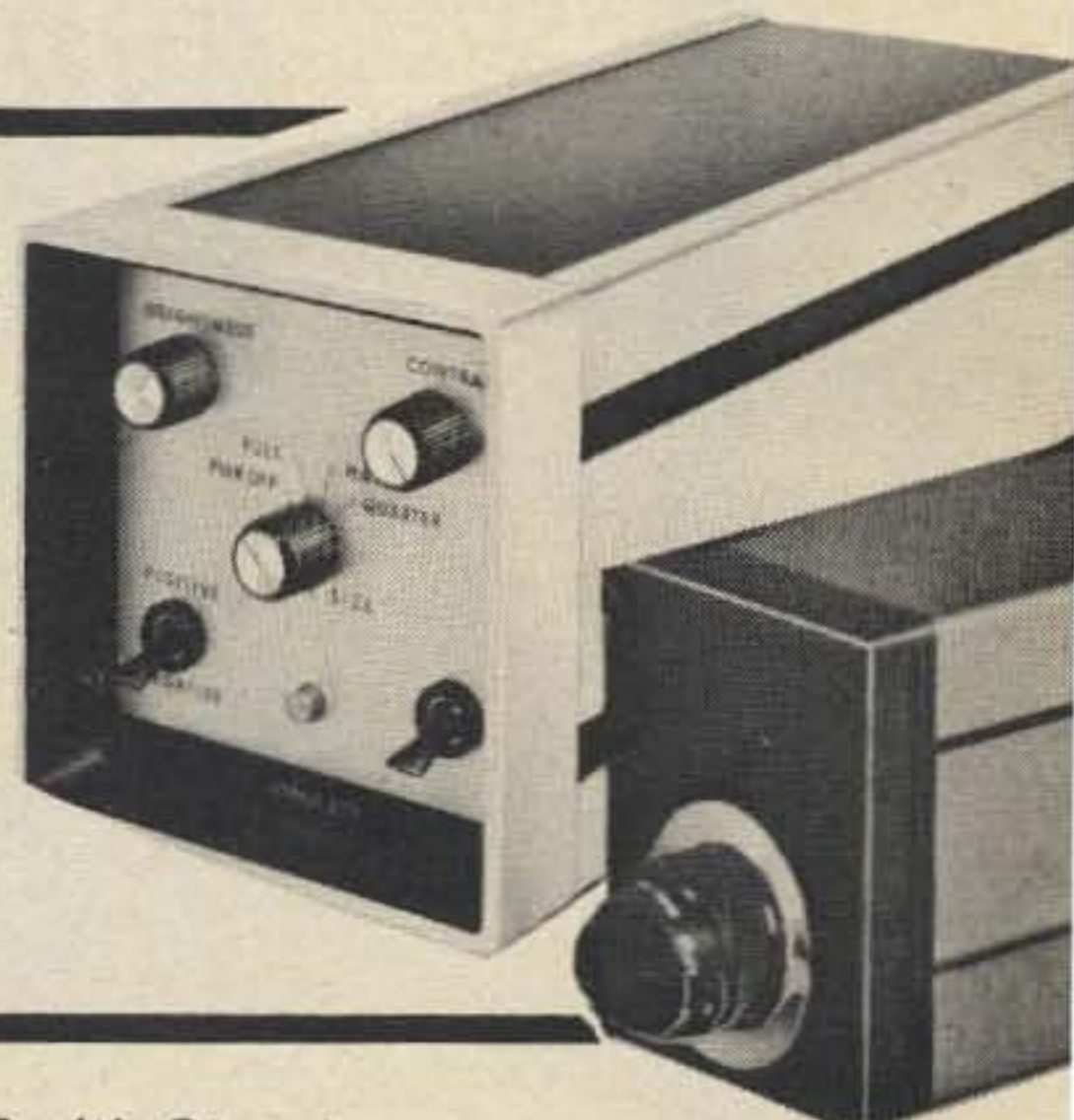- Full, half and quarter frame
- Positive, negative reversal
- RF output for viewing on conventional home TV set



ORDER DIRECT FROM FACTORY

Venus Scientific Inc.

The company that put high voltage on the moon, now brings you expanding amateur radio technology.

399 Smith Street
Farmingdale, N.Y. 11735
Phone 516-293-4100
TWX 510-224-6492

You may need the new T-UG8 desk stand or one of these STAND ADAPTOR KITS to convert to the new transistorized CB and ham outfits...but



THE D-104 MIKE STILL REIGNS SUPREME

When you convert your Astatic G Grip-to-talk Stand with a TG Adaptor Kit, or UG8 Stand with TU Kit, you obtain impedance match and gain control. A complete, new T-UG8 Stand does the same thing for you. Without buying a new mike, you still have the finest that money can buy.

- Kits and T-UG8 Stand provide sufficient level to fully modulate transmitters with any Astatic "Plug-in" Mike.
- Volume control under base adjusts with screw driver to prevent over-modulation from absent-minded fiddling or tampering, after you find the sweet spot.
- Rugged Silicon type transistors in a printed circuit.
- Noise-free, click-free switching with silver contacts which do not need cleaning.
- Internal slide switch for choice of relay or electronic type control (Available in T-UG8 Stand only).
- Powered by internal, 9-volt, readily available battery.

NOW AVAILABLE
AT YOUR DISTRIBUTOR
OR WRITE FOR FULL DETAILS.



THE ASTATIC CORPORATION

Conneaut, Ohio 44030 U. S. A.

In Canada: Canadian Astatic Ltd.,
Scarborough, Metro Toronto, Ontario

WORLD ACCLAIMED

UNIVERSAL TOWERS

FREE STANDING ALUMINUM TOWER

**LIGHTWEIGHT - RUST FREE - EASY TO ASSEMBLE - RUGGED STRENGTH
FOR TV - FM - HAM RADIO - INDUSTRIAL INSTALLATIONS - FIRE - POLICE - MARINE - CB**

Anyone interested in a tower should consider the tremendous advantages of aluminum over steel towers.

WHEN IT COMES TO ANTENNA SYSTEMS ELECTRONIC DISTRIBUTORS, INC., originated Antenna System "packages" over 23 years ago. These are RECOMMENDED matched systems designed to work together - yet with flexibility to meet YOUR needs. Many other combinations available, of course.

THE BEST ANTENNA PACKAGES YET!

EDI "STANDARD" PACKAGE U1140

- Universal 11-40 Tower - **
- Universal B-18 Hinge-Up Base
- Universal R-14 Rotor Mount,
2"x8'h.d. alum. mast
- CDR AR22R Rotator *
- 100 ft. Rotor Cable
- 100 ft. RG8/U Foam Coax

Complete with one of the following antennas:

- Hy-Gain TH2-MK3 . . . Reg. \$465. EDI \$335
- Hy-Gain TH3JR Reg. \$475. EDI \$345
- Hy-Gain Hy-Quad Reg. \$505. EDI \$370
- Hy-Gain 203BA Reg. \$515. EDI \$380
- Hy-Gain TH3-MK3 . . . Reg. \$520. EDI \$385
- Hy-Gain TH6-DXX. . Reg. \$555. EDI \$411

- *TR44 Rotator & Cable - Add \$ 29.
- *Ham-M Rotator & Cable - Add \$ 65.
- **11-50 (50') Tower w/B22 Base - Add \$ 84.

PRICES SUBJECT TO CHANGE


Light Weight - In addition to its weight advantages aluminum offers maintenance free life time beauty. Eliminates painting and ugly rust inherent in steel towers.

Strength - Important to your choice of a tower. Universal towers are tested for 80 m.p.h. winds and are designed to exceed that wind velocity.

Easy Assembly - Child's play to assemble. You can easily assemble a tower on the ground and walk it up, or assemble it erect section by section.

In addition to all of these advantages total cost of a Universal Aluminum Tower is less than similar steel towers extended over the life of the tower.

LET US RECOMMEND THE PROPER TOWER FOR YOU. Request WHOLESALE catalog.

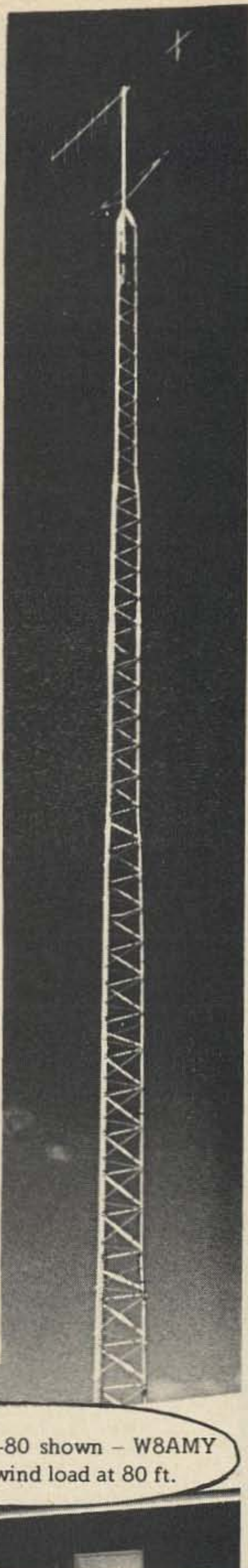

Model 11-80 shown - W8AMY
11 sq. ft. wind load at 80 ft.

ALSO COMPLETE LINES ANTENNA SYSTEMS AND HAM GEAR

Hy-Gain, Mosley, Telrex, Cushcraft, Wilson, A/S, Newtronics, Collins, Drake, Galaxy, Hallicrafters, Ten-Tec, Tempo, Regency, Swan, Clegg, Tri-Ex, Rohn, ect., ect.

(GECC revolving credit available)

LET US QUOTE AND SUPPLY your EVERY need. ONE-STOP service.

Available ANYWHERE IN THE WORLD directly from

ELECTRONIC DISTRIBUTORS, INC.

- Communication Specialists for over 35 years -

1960 Peck Street, Muskegon, Michigan 49441 Tel. (616) 726-3196
Telex 228-411

**Get the entire
Inoue ICOM family
at one of the dealers
listed below:**

ALABAMA

Wolfe Electronics
Box 358
Foley, AL 36535

ARKANSAS

Gavin Electronics
516 Ridgeway
Little Rock, AR 72205

ARIZONA

Ell Dee Enterprises
12612 N. 28th Dr.
Suite 3
Phoenix, AZ 85029

CALIFORNIA

Alpha Sound
1405 Dry Creek Road
San Jose, CA 95125

CDS Electronics & Hobbies Unltd.
235 Mitchell Drive
Atwater, CA 95301

Communications Headquarters, Inc.
1629 University Ave.
San Diego, CA 92103

Electro Service
240 Main Street
San Mateo, CA 94401

Gary Radio, Inc.
8199 Clairemont Mesa Blvd.
San Diego, CA 92111

Henry Radio
931 N. Euclid Ave.
Anaheim, CA 92801

Henry Radio Company
11240 W. Olympic Blvd.
Los Angeles, CA 90064

FM Sales
6234 A. Fountain Blvd.
Hollywood, CA 92028

Selectronics
1709 Markston Road
Sacramento, CA 95825

Sequoia Stereo
773 - 8th Street
Arcadia, CA 95521

Sichel Equipment Co.
245 E. Harris Avenue
S. San Francisco, CA 94080

Webster Radio
2602 E. Ashland
Fresno, CA 93726

Westcom Engineering Co.
Box 1020
Escondido, CA 92025

COLORADO

CW Electronic Systems
1401 Blake Street
Denver, CO 80202

LEC Electronics
P.O. Box 7515
Pueblo West, CO 81007

FLORIDA

Amateur Electronic Supply
621 Commonwealth
Orlando, FL

Goldsteins
Box 3561
Pensacola, FL 32506

GEORGIA

Bright Electronics
Box 76165
Atlanta, GA 30328

ILLINOIS

Erickson Communications
4653 N. Ravenswood
Chicago, IL 60640

INDIANA

Story Electric
2039 Fairfield Ave.
Fort Wayne, IN

Story Electric
441 Walnut
Wabash, IN 46992

KENTUCKY

Everhart Electronics
116 Sydney Street
Lexington, KY

MARYLAND

COM Electronics
900 Crain Hwy. S.W.
Glenn Burnie, MD 21061

MEXICO

NOVO Mex
Antonio de Mendoza
Nº320 Lomas
Mexico 10, d.f., Mexico

MONTANA

Conley Radio Supply
405 North 24th
Billings, MT 59101

NEVADA

Wilson Electronics
Box 794
Henderson, NV 89105

NEW MEXICO

Robert Foster
Box 198 - Star Rt.
Tijeras, NM 87059

NEW YORK

R.E. Nebel Laboratories
31 Whitehall Blvd.
Garden City, NY 11530

Barry Electronics
512 Broadway
New York, NY 10012

NORTH CAROLINA

Vickers Electronic Supply
506 E. Main St.
Durham, NC

OHIO

Amateur Electronic Supply
17929 Euclid
Cleveland, OH

H & C Electronics
6271 Hammell Avenue
Cincinnati, OH 45237

OKLAHOMA

Blacks Radio Company
413 N.E. 38th Terrace
Oklahoma City, OK 73106

Roland Radio Company
5923 E. 31st Street
Tulsa, OK 74114

OREGON

Portland Radio Supply
1234 S.W. Stark
Portland, OR 97205

PENNSYLVANIA

Hamtronics
4033 Brownsville Rd.
Trevose, PA 19047

Kass Electronics
2502 Township
Drexel, PA 19026

SOUTH CAROLINA

Accutek
420 Laurens Rd.
Greenville, SC 29607

Electronic Systems Inc.
1518 Gregg Street
Columbia, SC 29201

TEXAS

Bellaire Electronic Supply
5204 Bellaire Blvd.
Bellaire, TX 77401

Electronic Center, Inc.
2929 N. Haskell
Dallas, TX 75204

Trimble Electronics
1918 Mary Ellen
Pampa, TX 79065

UTAH

Utah FM Sales
1365 E. 5360 So.
Salt Lake City, UT 84117

VIRGINIA

Northern Virginia Communications
729 N. Edison
Arlington, VA 22203

WASHINGTON

ABC Communications
17541 - 15th N.E.
Seattle, WA 98155

ABC Communications
2002 Madison Avenue
Everett, WA 98200

Eichmeyer Electronics
Box 691 - Route 11
Spokane, WA 99208

HCJ Electronics
2718 Sprague Ave.
Spokane, WA

Progress Electronics
852 Commerce Street
Longview, WA 98632

WISCONSIN

Amateur Electronic Supply
4828 Fond Du Lac Ave.
Milwaukee, WI 53216

IF YOUR DEALER DOESN'T STOCK ICOM EQUIPMENT, LET THE ICOM DISTRIBUTOR FOR YOUR REGION KNOW.

joy for Christmas



Fill your Christmas Stocking with the exciting family of INOUE 2-meter FM gear!

Make your Christmas bright with the most advanced 2-meter gear around today . . . the all new, super-compact, 67-channel synthesized (with Inoue's unique *Phase Locked Loop System*), IC-230 for \$489 . . . or the 22-channel IC-22 for \$289 (including 10 xtals) . . . or the 24-channel base/mobile IC-21 with all the features you'd imagine . . . add on the unique optional rcv VFO for the 21, or the deluxe 3p base power supply for the 22 and 230.

*Put a whole lot of Jollies in your Christmas
by seeing or writing for the name of
your nearby ICOM-INOUE dealer today!*

Distributed by:



— Dealerships Available —

ICOM WEST, INC.
Suite 232 — Bldg. II
300 - 120th Ave. N.E.
Bellevue, Wash. 98005
(206) 454-2470


**ADIRONDACK
RADIO SUPPLY**
185 West Main Street
Amsterdam, N.Y. 12010

ICOM EAST
Div ACS, Inc.
Box 331
Richardson, Tex. 75080
(214) 235-0479

Take home this bundle of

WORLD'S LARGEST SELECTION OF

NEW & USED TV CAMERAS & ASSOC. EQUIPMENT

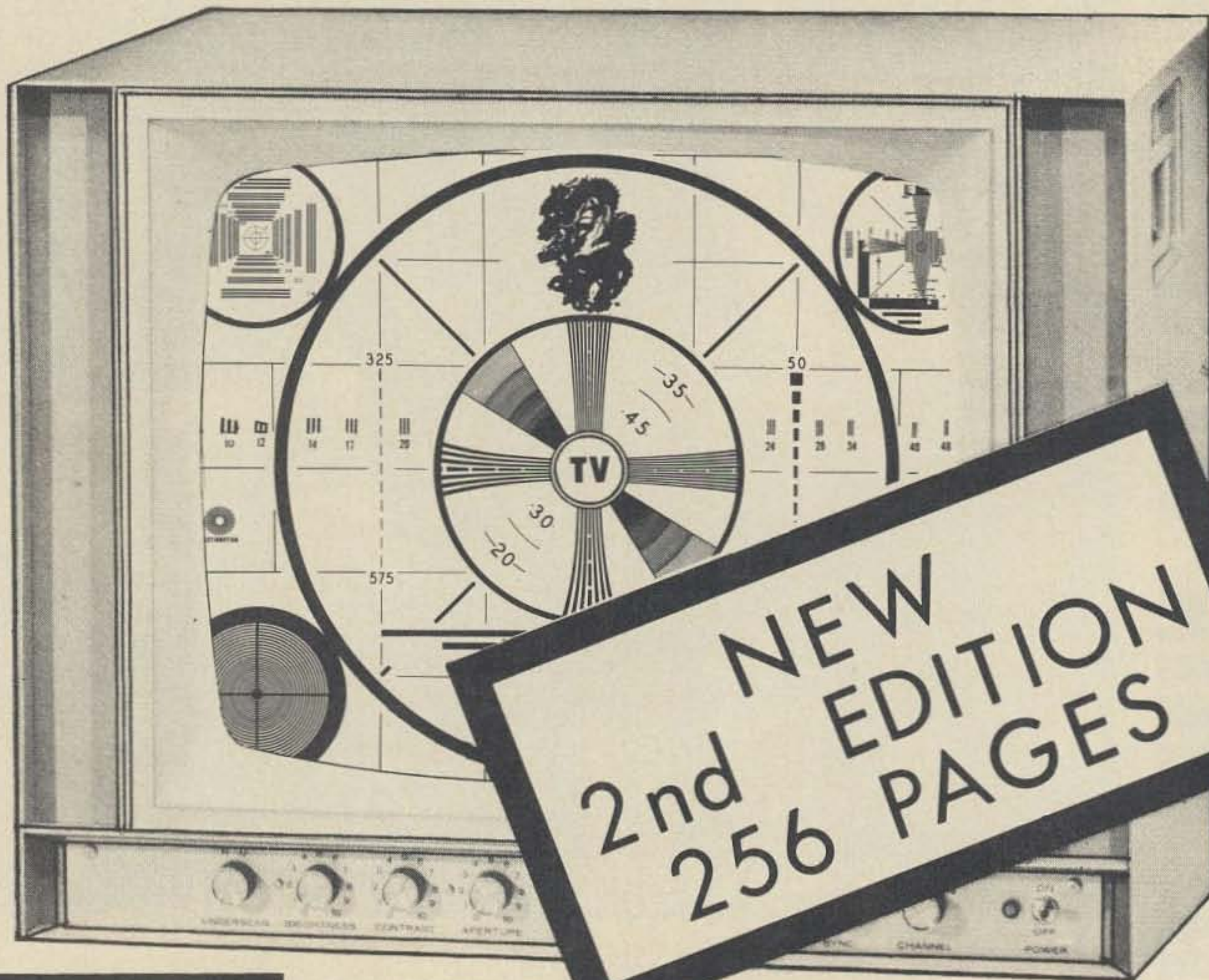

1973
1974

INDEX PAGE 142

Broadcast & Closed Circuit TV
Audio and Video Systems

PRICE
\$1.00

CATALOG #
973S1

\$1.00 ppd USA—\$2.00 Foreign.
Free to requests on Company
Letterhead.

THE DENSON ELECTRONICS CORP.

9AM - 4PM Monday thru Friday; otherwise by appointment.

OFFICE: Longview St. Tel. Area Code 203/875-5198

MAIL: Post Office Box 85

ROCKVILLE, CONN. 06066 USA

GODBOUT

BILL GODBOUT ELECTRONICS

BOX 2673, OAKLAND AIRPORT, CA 94614

LED 7 segment similar to DL 74 sims same as MAN 4, point 3 char

-\$2.75 ea 10/\$22.50
- 7 SEGMENT assembly 3 in 1 pac sim 2 and 33. Ideal for calculators. 8 digits and minus sign \$7.95
- 11 digits and minus sign \$10.50
- 7 SEGMENT readouts 2 in 1 pac plus space. Ideal for clocks. 6 digits for \$5.95
- CLOCKS shipped with prints #5314 \$9.50
- #5316 alarm clock \$13.50
- CALCULATORS shipped with prints 5001 basic 4 function \$6.95
- 5002 4 function/low power drain \$7.95
- 005 4 function with memory register \$9.95
- AA SIZE NI-CADS while they last 64c 10/5.95
- Low noise dual FETT's. Ideal for stereo preamp sim to 2N5454 2/1.00
- RF Sets sim to 2N4416 2/1.00
- RF dual sets \$1.00
- 2N2907 5/\$1.00
- 2N2222 5/\$1.00
- FET plug in replacement for 6AK4. Good for IF's etc. Ides 6-10-ma \$3.95 10/35.00

ICs, most TTL & LINEAR in stock - Send Stamp for FREE Catalog

CMOS	DIGITAL		LINEAR	
74C00	.70	CD4001	.70	LM 370 1.25
74C02	.70	CD4002	.70	LM 371 1.25 Replaces HEP 590
74C04	.95	CD4009	1.00	LM 372 1.25
74C10	.70	CD4010	1.00	LM 374 2.00
74C20	.70	CD4011	.70	LM 380 1.75
74C73	1.65	CD4012	.70	741T .45
74C74	1.50	CD4013	1.50	CA 3028 .75
74C76	1.65	CD4016	1.50	CA 3065 .75
74C107	1.65	CD4019	1.40	CA 3086 .45
74C151	3.00	CD4023	.70	
74C160	3.25	CD4025	.70	
74C161	3.25	CD4035	3.00	
74C162	3.25			
74C163	3.25			
74C195	3.50			

Buy 10 IC's - 10% discount
 Buy 100 IC's - 20% discount
 All IC's tested and guaranteed

LINEAR VOLTAGE REGS

- LM 309K 5V 1A REG 2.00
- LM 320K NEG Reg available in 5V 12V & 15V 2.25
- LM 340K POS Reg available in 6V 12V & 15V 2.25
- LM 723 Adjustable precision reg 1.00

TRANSISTOR GRAB BAG mixed NPN PNP 100 for2.95

ALL ITEMS IN STOCK and will be shipped within 24 hours of receipt of order!

Include 50¢ postage and handling on orders under \$10.00, all others postpaid.

Sorry, NO C.O.D.'s. CALIFORNIA RESIDENTS ADD 6% sales tax.

REWARD!

WANTED:

ALL TYPES OF
TUBES
ANY PIECE OF
COLLINS GEAR

We buy for cash any tube, transceiver, receiver,
or test gear at 5% over prevailing market price.

**THE
TED DAMES COMPANY**

308 Hickory Street, Arlington, N.J. 07032
(201) 998-4246 DAYS – (201) 998-6475 NIGHTS

DuPage FM

WILL NOT BE UNDERSOLD!

WHAT ARE YOU LOOKING FOR? *Do you want something special?*

In response to the telephone calls we have received, we have set up a "Want List" so that we can notify specific individuals when needed items arrive at our warehouse.

If you are looking for a particular item, drop us a postcard listing the make, model number and frequency that you need. We will put this in our "Want List" file and when we have your item we will call you to let you know price and condition. Be sure to include your name, address and complete phone number.

WHAT ARE WE LOOKING FOR? *Do you have a clue to its whereabouts?*

We are always looking for late model FM Gear made by Motorola, General Electric or RCA. If you know of any equipment presently in commercial service that is up for sale let us know where it is, who has it and the asking price if you know it. If we are the successful bidder we will give you \$25 off any order, which is money in your pocket. *Caution:* we want good equipment only — not rice boxes or boat anchors.

NOVEMBER GOODIES:

Handsets with transistor preamp and coiled cord . . . we have sold lots of these at our regular price of \$6.00, but as our way of saying "Happy Thanksgiving" — for November only — we will let these go for only \$4.50 each.

We still have lots of the RCA multi-freq control heads first listed in our June ad for only \$5.50 each.

TERMS: All items sold as is. If not satisfied, return for exchange or refund within five days of receipt, shipping charges prepaid. Illinois residents add 5% sales tax.

Send checks or money order to:

DuPage FM, Inc. P.O. Box 1
Lombard, Ill. 60148
312-627-3540

CW or RTTY, whichever way you go,
**HAL HAS TOP QUALITY
 YOU CAN AFFORD!**



TOP QUALITY RTTY...WITH THE HAL MAINLINE ST-6 TU. Only 7 HAL circuit boards (drilled G10 glass) for all features, plug-in IC sockets, and custom Thordarson transformer for both supplies, 115/230 V, 50-60 Hz. Kit without cabinet, only \$135.00; screened, punched cabinet with pre-drilled connector rails, \$35.00; boards and complete manual, \$19.50; wired and tested units, only \$280.00 (with AK-1, \$320.00).*



TOP QUALITY...WITH THE HAL 1550 ELECTRONIC KEYSER. Designed for easy operation; perfectly timed CW with optional automatic ID for sending call letters, great for DX and RTTY; TTL circuitry, transistor switching for grid block, cathode keying. Handsome rugged crackle cabinet with brushed aluminum panel. With ID, only \$90.00; without ID, \$65.00.*

OTHER HAL PRODUCTS INCLUDE:

- ID-1 Repeater Identifier (wired circuit board) . . . \$ 75.00*
- ID-1 (completely assembled in 1½" rack cabinet) . . . \$115.00*
- HAL ARRL FM Transmitter Kit . . . \$ 50.00*
- W3FFG SSTV Converter Kit . . . \$ 55.00*
- Mainline ST-5 TU Kit . . . \$ 50.00*
- Mainline AK-1 AFSK Kit . . . \$ 27.50*
- HAL RT-1 TU/AFSK Kit . . . \$ 51.50*



TOP QUALITY... WITH THE HAL MKB-1 MORSE KEYBOARD. As easy as typing a letter—you get automatic CW with variable speed and weight, internal audio oscillator with volume and tone controls, internal speaker, and audio output jack. Smooth operation; completely solid-state, TTL circuitry using G10 glass boards, regulated power supplies, and high voltage transistor switch. Optional automatic ID available. Assembled MKB-1, \$275.00; in kit form, \$175.00.*



NEW FROM HAL—TOP QUALITY RVD-1002 RTTY VIDEO DISPLAY UNIT. Revolutionary approach to amateur RTTY . . . provides visual display of received RTTY signal from any TU, at four speeds (60, 66, 75, and 100 WPM), using a TV receiver modified for video monitoring. Panasonic solid-state TV receiver/monitor, or monitor only, available. Complete, \$525.00; Panasonic TV receiver/monitor, \$160.00; monitor only, \$140.00.*

TOP QUALITY...WITH THE HAL RKB-1 TTY KEYBOARD. Gives you typewriter-easy operation with automatic letter/number shift at four speeds (60, 66, 75, and 100 WPM). Use with RVD-1002 video display system, or insert in loop of any teleprinter, for fast and easy RTTY. Completely solid state, TTL circuitry using G10 glass boards, regulated power supplies, and transistor loop switch. Optional automatic ID available. RKB-1 assembled, only \$275.00; in kit form, only \$175.00.*



HAL provides a complete line of components, semi-conductors, and IC's to fill practically any construction need. Send 24¢ to cover postage for catalog with info and photos on all HAL products available.

*Above prices do not include shipping costs. Please add 75¢ on parts orders, \$2.00 on larger kits. Shipping via UPS whenever possible; therefore, street address required.

HAL COMMUNICATIONS CORP., Box 365 L, Urbana, Illinois 61801

Standard
SRC-146A
\$289




Regency
HR-2MS **\$319**




Genave
GTX-10 **\$199⁹⁵**

Stop Wasting Time looking for a good deal

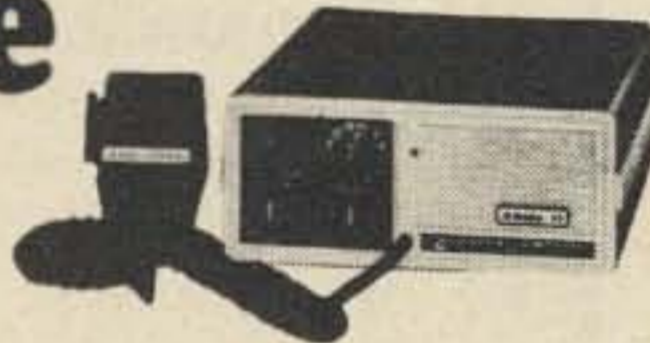

Gladding 25
\$249⁹⁵

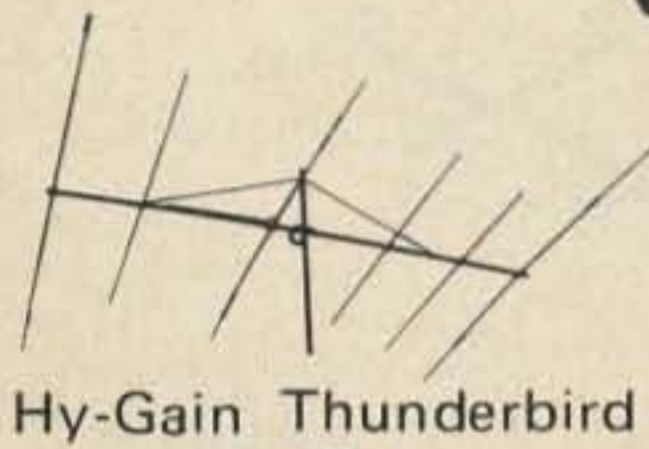

Hy-Gain Thunderbird
\$189

Get a
good deal more at:

LOU GOLDSTEIN - K4LAN

P.O. BOX 3561
PENSACOLA, FLA.
32506

Florida's newest and
fastest growing dealer.


*"If I don't have it,
you don't need it."*

A post card brings
results — write me
your needs.

Call around the clock
(904) 455-2533



Icon 230
\$447⁵⁰

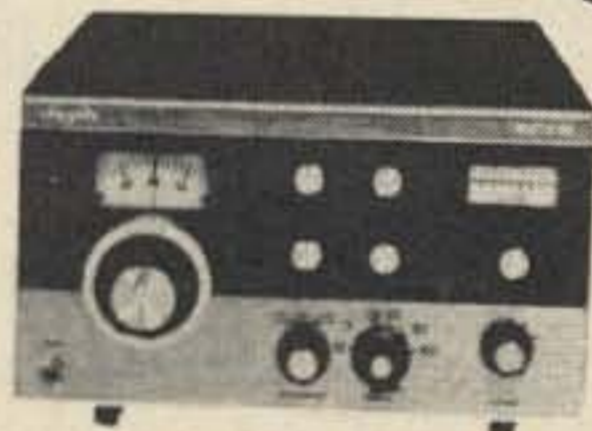

Hy-Gain
Galaxy
\$595




the REPEATER 2 Meter Fixed Station

Designed for the man who demands professional standards in 2 meter equipment. *REPEATER LINE* fixed station antennas are the 2 meter HAM's dream come true. With everything you need for top fixed station performance...toughness, efficiency and the gain to gain access to distant repeaters with ease. Work many stations, fixed or mobile, without access to a repeater.

The right antennas for the new FM transceivers...or any 2 meter fixed station.

REPEATER LINE Fixed Station Antennas

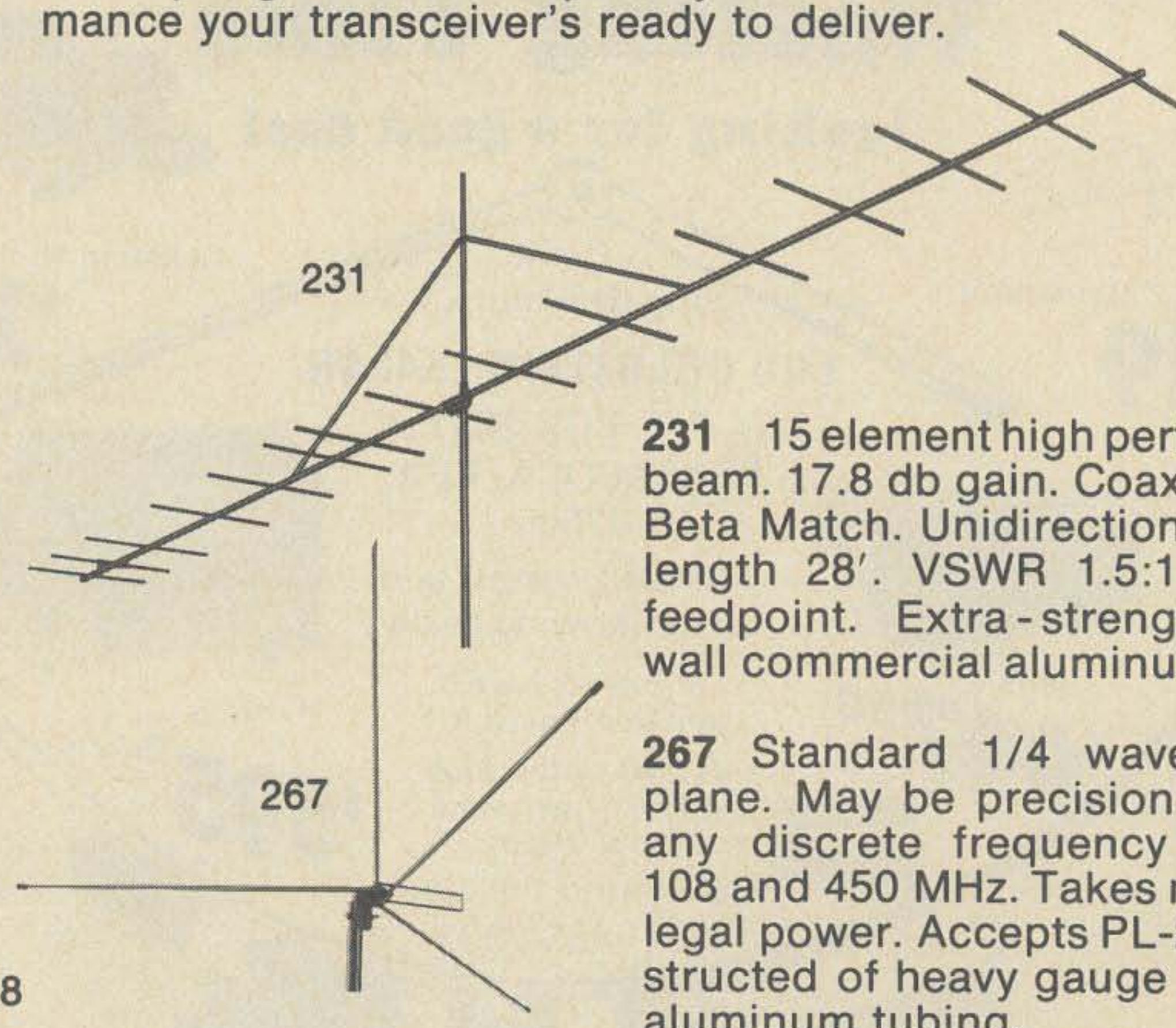Tough, high efficiency antennas with a long, low radiation. For the top signal and reception you want...and the top performance your transceiver's ready to deliver.



231 15 element high performance beam. 17.8 db gain. Coaxial balun. Beta Match. Unidirectional. Boom length 28'. VSWR 1.5:1 52 ohm feedpoint. Extra-strength heavy wall commercial aluminum tubing.

267 Standard 1/4 wave ground plane. May be precision tuned to any discrete frequency between 108 and 450 MHz. Takes maximum legal power. Accepts PL-259. Constructed of heavy gauge seamless aluminum tubing.


268

268 For repeater use. Special stacked 4 dipole configuration. 9.5 db offset gain. 6.1 db omnidirectional gain. Heavy wall commercial type construction. 144 thru 174 MHz. 1.5:1 VSWR over 15 MHz bandwidth eliminates field tuning. Extreme bandwidth great for repeater use. Center fed for best low angle radiation. DC ground. Complete with plated steel mounting clamps.


LINE from *hy-gain*

Antennas with real PUNCH!

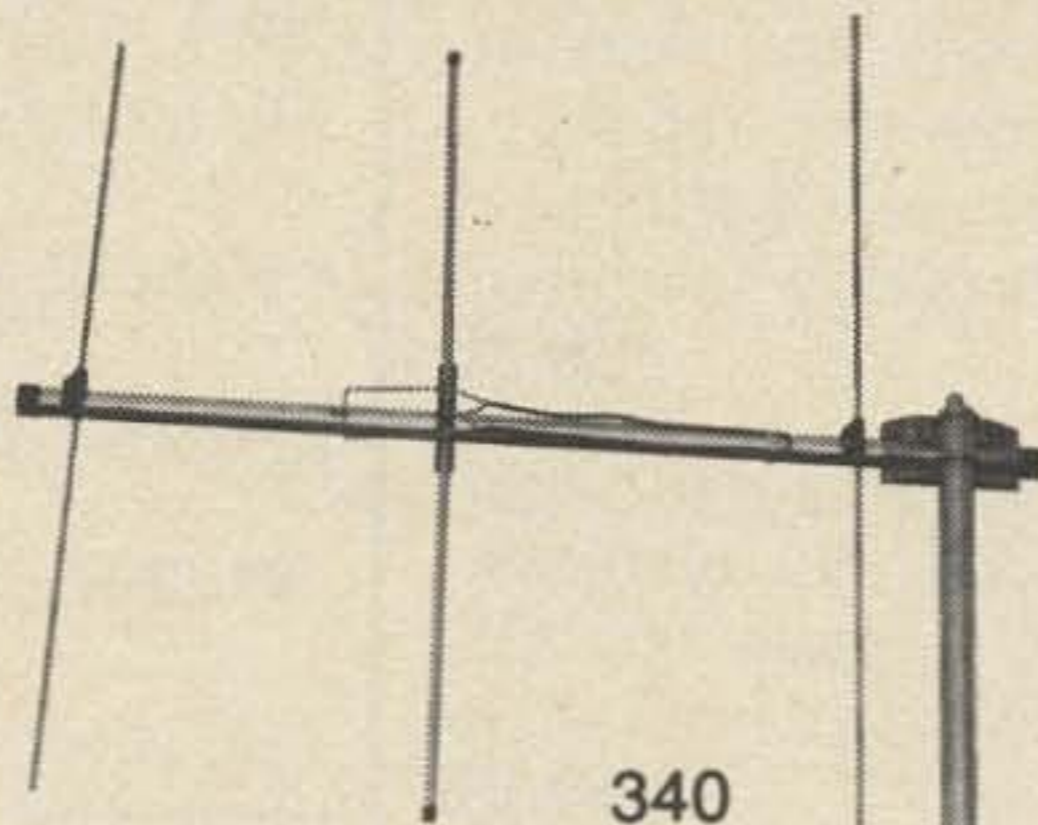
340 3 element high performance beam. 9 db gain. Coaxial balun. Special VHF Beta Match configuration. Unidirectional pattern. VSWR 1.5:1. 52 ohm impedance. Heavy gauge aluminum tubing and tough aluminum rod construction.



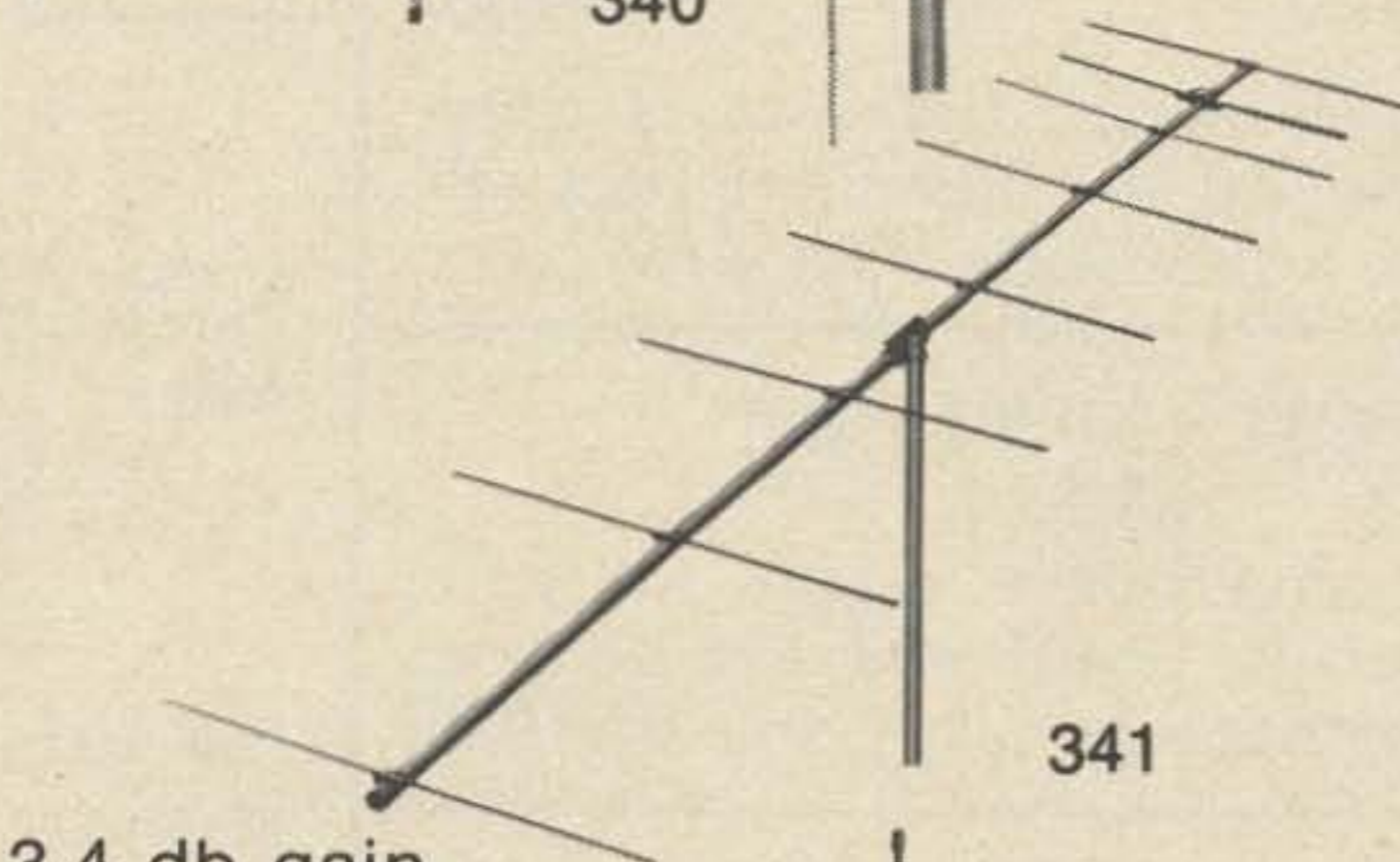
341 8 element high performance beam. 14.5 db gain. Coaxial balun. VHF Beta Match. Unidirectional. Boom length 14'. VSWR 1.5:1. 52 ohm feedpoint. Heavy gauge commercial type aluminum construction.



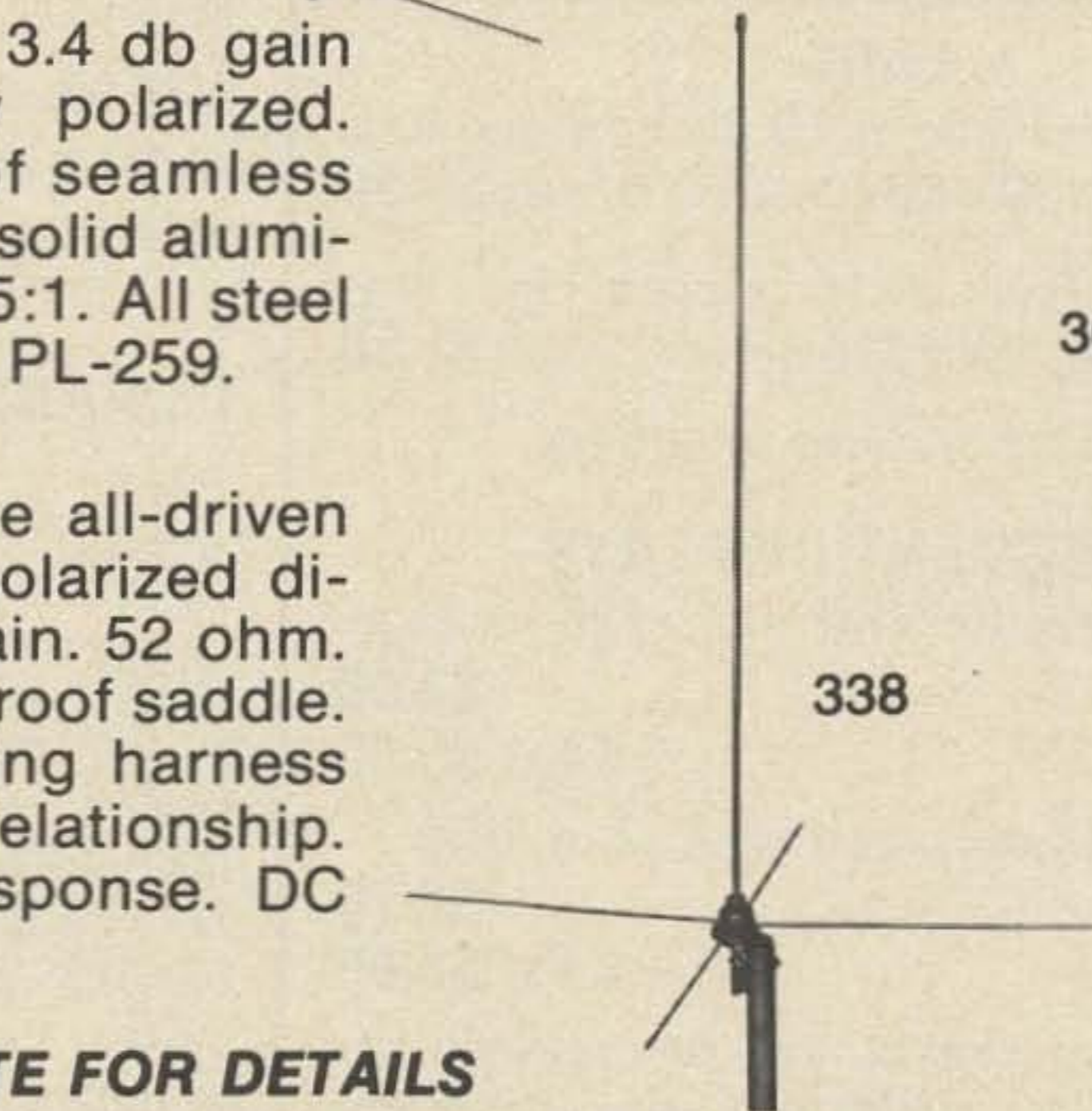338 Colinear ground plane. 3.4 db gain omnidirectionally. Vertically polarized. 52 ohm match. Radiator of seamless aluminum tubing; radials of solid aluminum rod. VSWR less than 1.5:1. All steel parts iridite treated. Accepts PL-259.



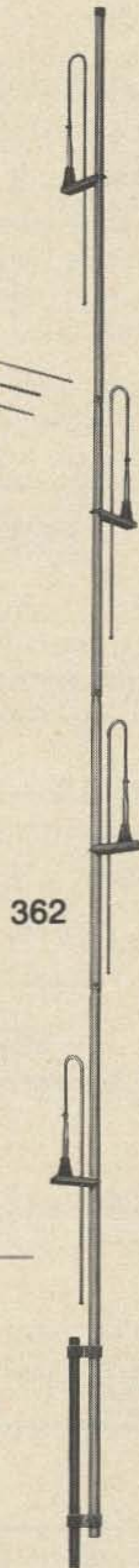362 SJ2S4 high performance all-driven stacked array. 4 vertically polarized dipoles. 6.2 omnidirectional gain. 52 ohm. May be mounted on mast or roof saddle. Unique phasing and matching harness for perfect parallel phase relationship. Center fed. Broad band response. DC ground.



WRITE FOR DETAILS

For top fixed station performance on 2 meters...
THE REPEATER LINE

From

HY-GAIN ELECTRONICS CORPORATION

Dept. CK, 8601 Northeast Highway Six
402/434-9151

Lincoln, NE 68507
Telex 48-6424

RGS ELECTRONICS

SPECIAL — LIMITED SUPPLY!

SURPLUS CLOCK CHIPS

MM5312 — 24 pin, 4 digits, any readout. Data sheet included. Cosmetic rejects — pinout reversed. Otherwise perfect. 4 NPN and 7 PNP transistors drive common cathode LED display. **\$6.00**

MM5316 — 4 digit 40 pin alarm clock chip. Data sheet included. No blanking; not usable with liquid crystals but OK with other readouts. 24 transistors drive LED readout. **\$9.00**

We only have about 100 each of these and we won't get any more, so orders will be filled on a first come, first serve basis.

POWER SUPPLY KIT

PS 5 - 1

5 volt 1 amp power supply kit with printed circuit board and instructions. Transformer has internal r.f. shield. **\$10.00**

LEDS

LED 1 OR — Pack of 10 discrete red lens LEDs, various MV5020-series types. **\$1.50**

LED 10C — Pack of 10 discrete clear lens LEDs, various MV5020-series types. **\$1.50**

Application note included.

7 - SEGMENT DISPLAYS

MAN 3 — common cathode, .125 in. high **\$2.00**
4 for \$6.00

MAN 4 — common cathode, .2 in. high. **\$2.75**
4 for \$8.00

We also have green, yellow, and amber discrete LEDs. Write for our flyer for details.

TRANSISTORS

NPN and PNP TO-18 general purpose silicon transistors. **\$0.15 ea.**

10 or more, \$0.10 ea.

Excellent for use with the clock chips.

2N2222 (NPN) TO-18 **\$0.25 ea.**

10 or more, \$0.20 ea.

2N2907 (PNP TO-18) **\$0.25 ea.**

10 or more, \$0.20 ea.

Mil. spec. rejects; meet commercial specs.

JUNCTION FETS

TO - 18 CASE

N-CHANNEL:

NO.	I_{DSS} (ma)		V_P (v)		PRICE
	min	max	min	max	
NJF10	1	25	.7	9	3/\$1.00
NJF11	5	170	.5	10	4/\$1.00
NJF12	.1	10	.5	8	4/\$1.00
NJF13	.02	1	.5	6	3/\$1.00
NJF14	.5	17	.5	8	4/\$1.00

P-CHANNEL:

PJF11	5	90	.5	10	4/\$1.00
PJF14	.3	20	.5	9	4/\$1.00

Notes:

*NJF10 is usable to 450 MHz;
NJF11 and PJF11 are complements, high-current and good to 100 MHz;
NJF12 is general purpose;
NJF13 is a low-current high-impedance type;
NJF14 and PJF 14 are complements, general purpose and good to 50 MHz.*

RGS ELECTRONICS (408) 247-0158

3650 Charles St., Suite K, Santa Clara, CA 95050

We sell many ICs and components not listed in this ad, including most 7400s and linears. Send a stamp for our free flyer. TERMS OF SALE: All orders prepaid; we pay postage. \$1.00 handling charge on orders under \$10.00. California residents add 5% sales tax. Please include name, address and zip code.

Semiconductor Supermart

• MOTOROLA • RCA • FAIRCHILD • NATIONAL • HEP • PLESSEY

POPULAR IC's

MC1550	Motorola RF amp	\$1.80
CA3020	RCA 1/2 W audio	\$3.07
CA3020A	RCA 1 audio	\$3.92
CA3028A	RCA RF amp	\$1.77
CA3001	RCA	\$6.66
MC1306P	Motorola 1/2 W audio	\$1.10
MC1350P	High gain RF amp/IF amp	\$1.15
MC1357P	FM IF amp Quadrature det	\$2.25
MC1496	Hard to find Bal. Mod.	\$3.25
MFC9020	Motorola 2-Watt audio	\$2.50
MFC4010	Multi-purpose wide band amp	\$1.25
MFC8040	Low noise preamp	\$1.50
MC1303P	Dual Stereo preamp	\$2.75
MC1304P	FM multiplexer stereo demod	\$4.95

FETs

MPF 102	JFET	\$.60
MPF 105/2N5459	JFET	\$.96
MPF 107/2N5486	JFET VHF/UHF	\$1.26
MPF 121	Low-cost dual gate VHF RF	\$.85
MFE3007	Dual-gate	\$1.98
40673	Dual-gate	\$1.75
3N140	Dual-gate	\$1.95
3N141	Dual-gate	\$1.85

NEW FAIRCHILD ECL HIGH SPEED DIGITAL IC'S

9258 Dual "D" FF toggles beyond 160 MHz
..... \$4.65

9582 Multi-function gate & amplifier ... \$3.15
95H90 300 MHz decade counter ... \$16.00
A 95H90 & 9582 makes an excellent prescaler
to extend low frequency counters to VHF - or
use two 9528s for a 160 MHz prescaler.

SIGNETICS PHASE LOCK LOOP

NE561B	Phase Lock Loop	\$4.75
NE562B	Phase Lock Loop	\$4.75
N5111A	FM/IF Demodulator	\$1.50
NE566V	Function Generator	\$4.75
NE567V	Tone Decoder	\$4.75

TTL BARGAINS

7400	\$.28
7401	\$.30
7404	\$.30
7410	\$.30
7420	\$.30
7446/7447	\$1.50
7475	\$1.00
7490	\$1.00
74192	\$2.00

NATIONAL CLOCK CHIP \$12.50

Set of circuit boards to build
a digital clock **\$5.00**

CORES AND BEADS

T200-2	\$2.00
KW Balun kit only	\$3.50
T68-2 3 cores	\$1.00
T50-2 3 cores	\$1.00
T50-6 3 cores	\$1.00
T50-10 3 cores	\$1.00
T44-10 3 cores	\$1.00

BEAD SPECIAL

Ferrite Beads 1 doz. \$1.00

NEW!

INTRODUCING DEVICES AT NEW LOW PRICES

LA3018 (Replaces CA3018)	\$1.60
LA3046 (Replaces CA3046)	1.60
LS370 (Replaces LM370)	4.00
LS1496 (Improved MC1496)	2.00
LS3028A (Replaces CA3028)	1.60
LP1000 (A new fun-type device to make LED flashers, audio osc, timer etc.)	1.60
LP2000 Microtransmitter	16.00

THINKING



DRAKE



R-4C

TR-4C

T-4XC

TR-22

Check us out

NOW OPEN FOR LOCAL SHOPPING STOP BY AND CHEW THE RAG

1110 N. Scottsdale Road
Hayden Plaza East

Please add 35¢ for shipping


Circuit Specialists

Box 3047, Scottsdale, AZ 85257

FACTORY AUTHORIZED DISTRIBUTOR FOR
Motorola HEP - Circuit-Stick - Plessey
All devices are first quality and are
fully guaranteed.

At Last Repeater Sophistication Is HERE

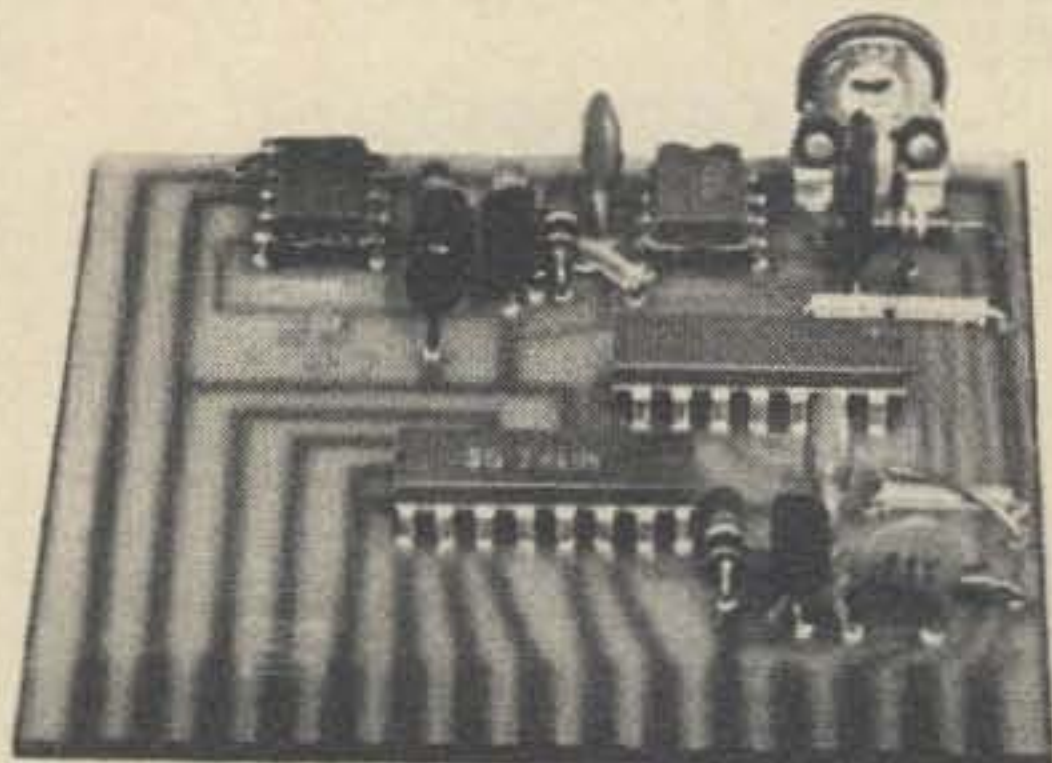Now at a realistic price you can have "Touch-Tone" command functions, autopatch, and control. It's the Signal Systems Decoder.




12/16 BUTTON TOUCH-TONE DECODER

Uses NE-567 decoder IC's and 7402 AND gates. Frequencies are pot variable. Response times are fixed by capacitors. (200 ms. unless otherwise specified).

Outputs are ANDed TTL logic highs. Requires: 5V

Board:		\$10.00
Kit:	12 button -	77.00
Kit:	16 button -	88.00
Tested:	12 button -	85.00
	16 button -	98.00

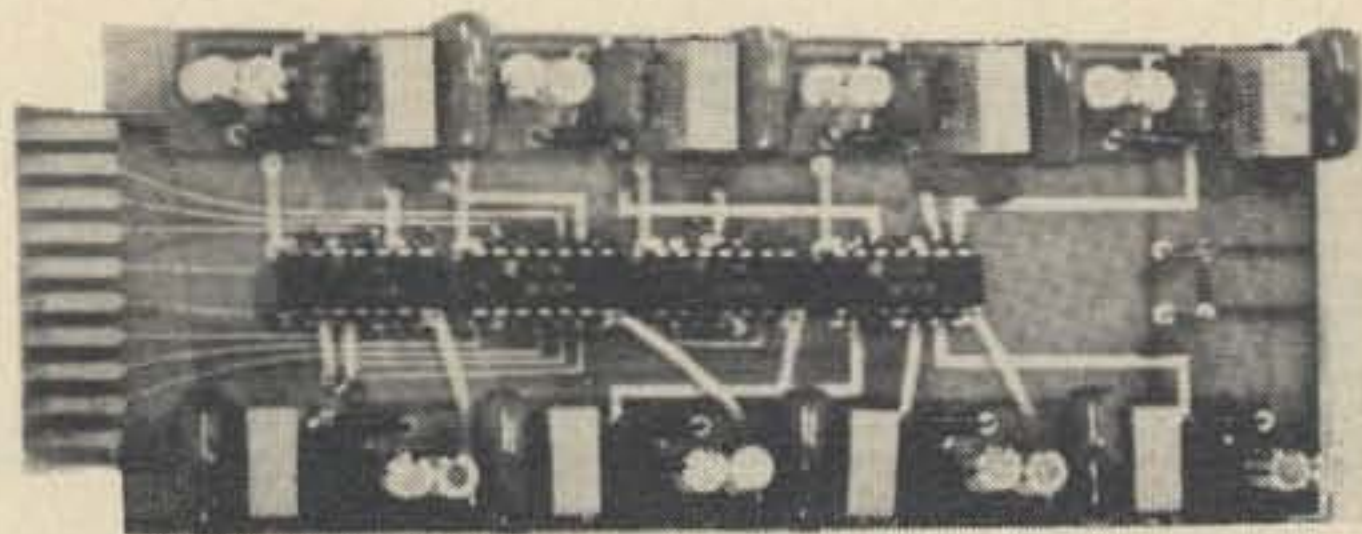


RTTY R-Y GENERATOR

Uses two NE-555 timers, 7420 and 7493 IC's. Outputs repetitive or clutched zero-bias test signals in Western Union format. Used to check printer range and aid proper adjustment. Requires 5 volts. Loop driver circuitry.

Board:		\$ 1.75
Kit:		8.00
Tested:		11.00

THE IDENTIFIER TO END ALL IDENTIFIERS

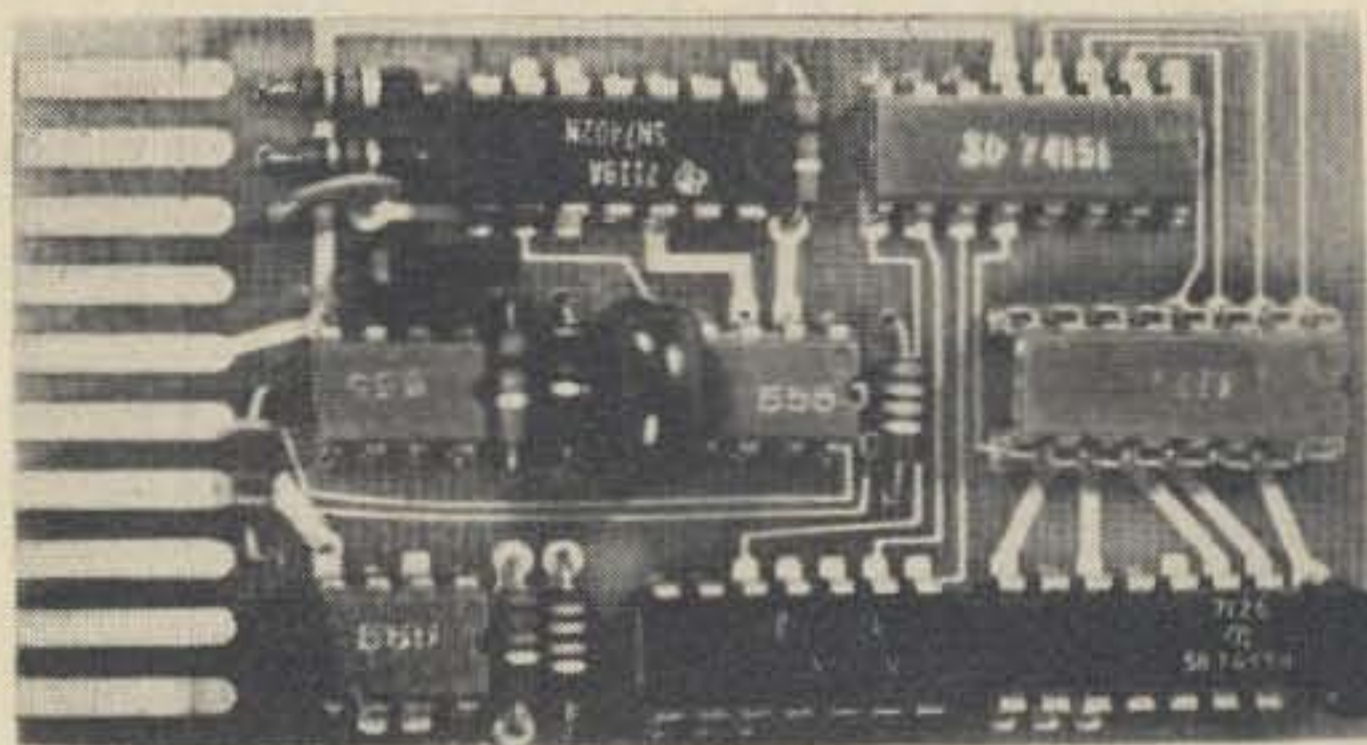

CW/RTTY/REPEATER IDENTIFIER

Uses 8223 Programmable read-only-memory. NE-555 timers for clock, tone generator and 5 minute timer. Apply 5 volts (200mA) and COR (ground) and it outputs tone (5 VPP) and PTT (5V).

256 bit plug-in memory is programmed to your specifications or call.

Dits and element spaces = 1 bit.

Letter space = 2 bits.

Dash = 3 bits.

Word space = 4 bits.

Typical full memory: CQ FD CQ FD
FD DE WAØVTU/Ø K

Can also be programmed to output up to 32 RTTY characters, 5 level Baudot, double stop. See ARRL Manual "FM and Repeaters" page 136. For 5 minute timer and tone oscillator add \$5.00 to Kit price and \$6.00 to Tested Unit price.


Additional factory programmed memories:	\$14.00
Board:	8.00
Kit:	25.00
Tested:	29.00

2 METER PREAMP

40673 or MFE3007 Dual Gate FET. Very small size—1 1/8 X 1 5/8 inches. 16 db. gain, 2.5 db. noise figure.

Board:	\$ 1.10
Kit:	9.00
Tested:	13.00

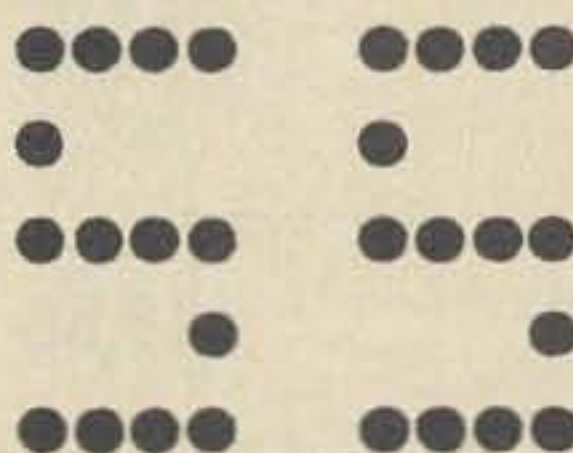Look for product review write-ups on these and other exciting new products from . . .



SIGNAL SYSTEMS

2650 Durango Dr.

Colorado Springs,

Phone 303-392-9073 CO 80910

ANOTHER SELECTRONIC SPECIAL
The R648/ARR 41 Receiver

Can be best described as a mini version of the R390A rec, and has most of the key features of the 390A.



Digital readout 500 kHz to 24.999 MHz
 1.4 kHz to 6 kHz mechanical filters
 500 kHz to if, Double conversion
 Xtal calibrator, 500 ohm output
 17 tubes
 8" x 17" x 12" - Weight: 34 pounds

Receiver has been tested, overhauled, and guaranteed. **Excellent condition Price: \$175.00**

Solid State 866A Direct Replacement

Price: \$5.95 ea. or 2/\$10.00

R508 VHF Rec. 118-148 MHz

Price: \$14.95 ea.

MODERN ALUMINUM BENCH RACK CABINET

11½" H x 18" D x 19" W. 8" panel openings w/rubber feet and disappearing handle. Lt Blue

Price: \$7.95 ea.

R.F. AMPLIFIERS

TUNES 50 to 100 mhz - COMPACT ALL ALUM. CASE 12" x 15" x 6¼" WITH SK 600 EIMAC SOCKET. 1 LARGE AIR VARIABLE CAP. - 2 SMALL AIR VARIABLE TRIMMERS - TEFLON MOUNTED ROTARY INDUCTOR - GOOD FOR LINEAR AMPLIFIER - CAN USE EITHER 4 CX150A or 4 CX250 - LESS TUBE, PRICE: . . . \$14.95 ea. WITH 4 CX150A, PRICE: . . . \$19.95 ea.

ADJUSTABLE PRINTED CARD BOX

For Rack Mount

5" to 7¼" - 16 slides and sockets includes 30 double contact position edge connector type

Price: \$9.95 ea.

Receiver type VHF-2RM 108-135 MHz crystal control Double Conversion AM with AVC noise limiter and squelch-tunable. 115 volts, 50-60 cycles. Price: \$24.95.

WINTRONIX MODEL 850 INDUCED WAVE FORM ANALYZER.

This unit, in conjunction with your present oscilloscope, permits you to view wave forms in the range from audio thru MHz without any direct connection. The probe is simply placed over the tube in question and the wave form is displayed on the oscilloscope. It may also be used as a high gain amplifier to increase scope sensitivity. Excellent for TV, radio, amplifier, and transmitter repair and maintenance. Brand new, with probe.

SHIP WT. 13 lbs. Price: \$19.95 ea.

MODULE TYPE POWER SUPPLY TRANSISTOR, REGULATED.

115V - 60 cycle in +12 -12 -6V @ 3 amp output. Front Panel adj + or -10%. On-off switch. Fuses. Barrier strip output. 6" x 5" x 7". Excellent Cond. Ship. Wt. 10# Price: \$14.95 ea.

DIGITAL READOUT SET

Make your own counter, frequency meter, digital voltmeter, readouts, etc.

Kit includes

- 6 nixies with 6 sockets
- 1 transformer
- 1 P/S board w/socket

PRICE: \$12.95, 2/\$20.00

B-7971 LARGE ALPHA NUMERIC READOUT

With sockets & driver board. Can be hardwired to form unusual house address numbers. 2 tubes, 2 sockets, mounted on one driver board. Save \$3.00

Price: 5/\$5.00

COMPUTER TYPE CAPACITORS

- 40,000 @ 20V
- 32,500 @ 25V
- 55,000 @ 15V
- 100,000 @ 8V
- 50¢ each or 5 for \$2.00

- 40,000 @ 10V
- 30,000 @ 10V

PRICE: 3 for \$1.00

Receiver R-36/GR 225-400 MHz. Crystal Control Double conversion FM with squelch and noise limiter. 600 ohms output. 115-230 Volts, 50-60 cps. Price: \$24.95

Coaxial relays, single pole - double throw, available in UHF, BNC, Type N. Specify.

Price: \$4.95 each.

Quality precision polished plate glass 2.200" by 9.540" by .250".

Price: 4 pc/\$1.00, 25 pc/\$5.00

We have a few receivers with AC power supply installed.

Price: \$199.50

Adapters BNC to SO-239.

Price: 2/\$1.00.

SPECIAL ONE OF A KIND

Sorenson Power Supplies:

- MA 28 30, 28 V, 30 A Price: \$125.00
- ERA 0-36 V, 50 A Price: \$150.00
- ERA 0-36 V, 20 A Price: \$100.00

Transmitter, 110 W FM, 406-420 Mc. Rack mount, with power supply.

Price: \$150.00

ALL PRICES ARE F.O.B. OUR WAREHOUSE, PHILADELPHIA, PA. ALL MERCHANDISE DESCRIBED ACCURATELY TO THE BEST OF OUR KNOWLEDGE. YOUR PURCHASE MONEY REFUNDED IF NOT SATISFIED. TERMS ARE CASH. MIN. ORDER \$5.00. ALL MERCHANDISE SUBJECT TO PRIOR SALE. RFE - REMOVED FROM EQUIPMENT.

SELECTRONICS


1206 South Napa Street
 Philadelphia, PA 19146
 215-468-7891 215-468-4645

S & R Enterprises

1344 E. Indian School Rd.-Phoenix, AZ 85014
(602) 277-2712

This Month's Specials

S&R makes economy exciting!

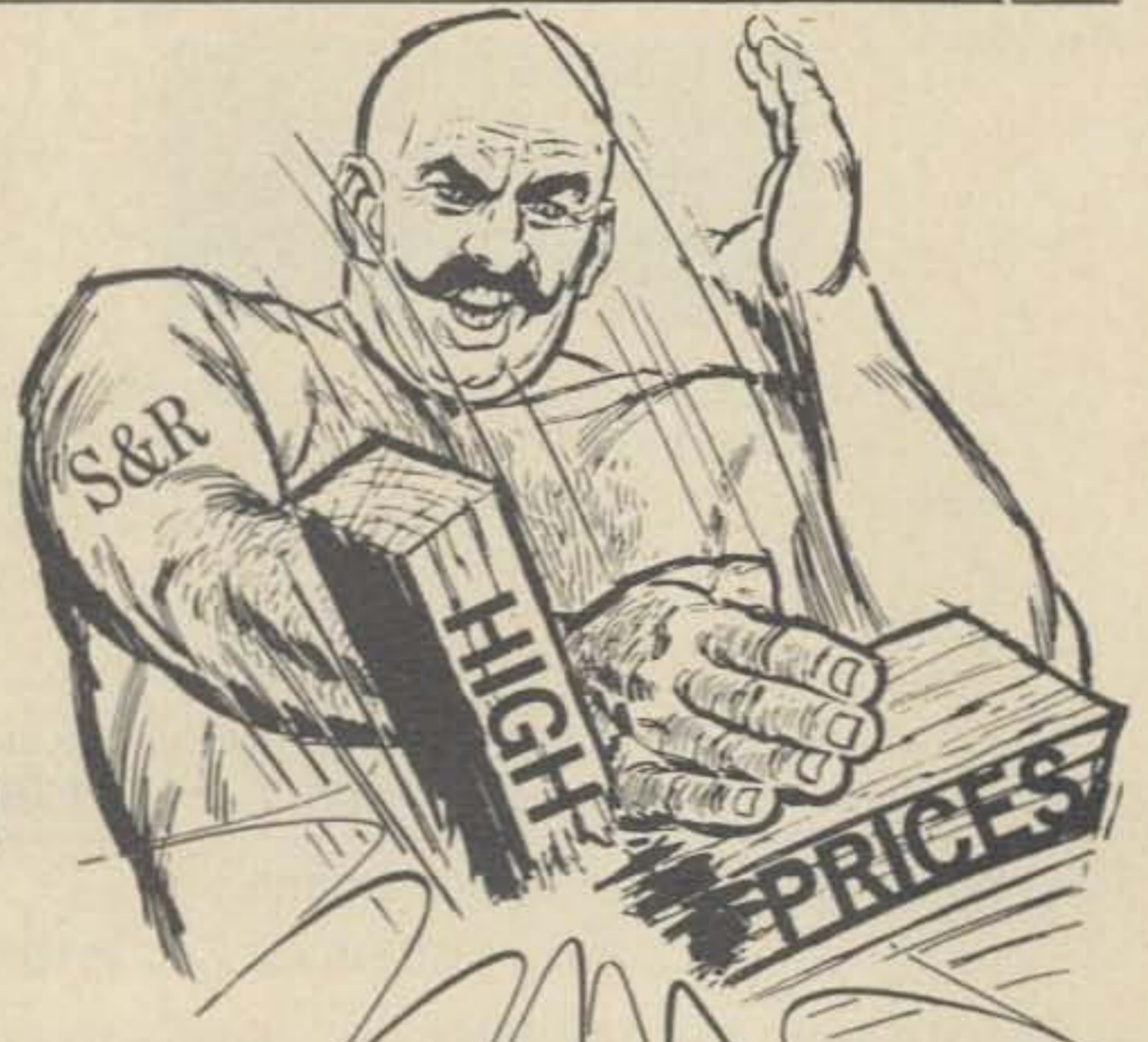

Motorola RF Transistors Unmarked

Type	Qty.	Price
2N3866	1352	3/1.50
2N5589	364	3/6.00
2N5590	112	3/9.50
2N5591	44	3/20.00
2N6080	222	3/6.00
2N6081	280	3/9.50
2N6082	173	3/16.00
2N6083	173	3/24.00
2N6084	260	3/30.00
2N6166	50	3/50.00
MRF304	17	3/30.00



Case 1 TO-3



Case 20(10) TO-72



Case 1440-04 0.280" DIA

BEST BUY ANYWHERE!

Motorola RF Transistors Marked

2N1692	3	2.00
2N1693	3	3.00
2N2857	1	1.00
2N2887	2	3.00
2N2947	9	8.00
2N3925	394	2.00
2N3950	13	10.00
2N4072	1963	.75
2N4073	2	1.00
2N5109	1361	1.25
2N5177	1	6.00
2N5179	1744	.35
2N5583	1	3.00
2N5590	30	5.00
2N5591	4	9.00
2N5643	14	10.00
2N5849	4	15.00
2N5862	11	20.00
2N5942	14	20.00
2N6081	20	6.50
2N6082	24	10.00
2N6083	25	15.00
2N6084	384	2/30.00
2N6097	21	15.00
2N6135	1	5.00
2N6166	40	30.00
2N6266	2	40.00
MM1500	2	2.00
2N5842	950	2.00
MM1620	2	10.00
MM1661	1	5.00
2N5645	1	5.00
MM8006	1000	1.00
MRF207	1	3.00
MRF209	4	8.00



Case 211 01 0.380" DIA



Case 145A 01 0.380" DIA



Case 211 02 0.500" DIA

Motorola HEP Semiconductors

RF Transistors

HEP 75	Price Each	\$ 2.95
HEP 76		4.95
S3001		3.75
S3002		8.20
S3003		20.00
S3005		9.55
S3006		19.90
S3007		24.95
S3008		2.18
S3010		4.90

Price Each	Our Price
\$ 2.95	2.00
4.95	4.00
3.75	3.00
8.20	6.50
20.00	15.00
9.55	7.00
19.90	15.00
24.95	19.00
2.18	1.60
4.90	3.00

Hot Carrier Diodes

HEPR0700

1.09 1.00

V. C. C.

HEPR2500	1.10	.88
R2501	1.10	.88
R2502	1.10	.88
R2503	1.10	.88
R2504	1.10	.88
R2505	1.10	.88

FETs

HEP801	1.59	1.20
803	3.39	3.00
F0021	1.89	1.50
F1035	1.29	1.00
F2004	2.50	2.00
F2005	2.90	2.00
F2007	2.90	2.00

★ You save

Specials


THE SCOTCHMAN'S DREAM

(Also HEP Cross Reference Available with Any HEP Ordered)

Bargains

Microwave Ass. A Components, Equipment Sale	Type and Manufacture	Qty	Price
	FXR S155A	1	10.00
	H. P. S370B	1	10.00
	H. P. 360A	1	10.00
	Airborne Inst. Inc. 7010	1	15.00
	Narda 730S	4	5.00
	Narda 730	1	5.00
	Waveline 611	1	5.00
	PRD 154	1	5.00
	M. C. S. P-265-1	2	7.00
	PRD 559A	1	15.00
	Narda 211	1	25.00
	Waveline 658	1	5.00
	H. P. HX292B	1	4.00
	Narda 614	1	6.00
	Narda 615	2	10.00
	Omni Spectra 201845/J	8	5.00
	Demornay Bonardi L-450	2	7.00
	Narda 350H	2	3.00
	Waveline 641	1	3.00
	Waveline 642	1	4.00
	Demornay Bonardi HJ-018	1	6.00
	Guide Ind. Inc. 1515-.5	2	4.00
	Aircom 106C00	1	7.00
	Unilinern 125	1	5.00
	Airborne Inst. Lab. 70B-49	1	15.00
	Frequency Eng. WG-1217-5B	1	20.00
	Frequency Eng. 5882-4N	1	20.00
	Frequency Eng. 8397-1	1	10.00
	H. P. X421A	1	10.00
	H. P. G487A	1	15.00
	H. P. X281A	1	5.00
	H. P. 420B	2	10.00
	H. P. 775D	1	50.00
	PRD X1410	1	5.00
	FXR X601A	1	6.00
	PRD 195A	2	6.00
	PRD 195B	2	10.00
	Rantec MX-200	2	4.00
	Waveline 554	4	4.00
	Narda 301	1	10.00
	FXR X1551	1	6.00
	PRD 188A	2	10.00
	FXR X410B	1	10.00
	Narda 1011	1	10.00
	H. P. H750D	1	10.00
	Varian VA1281B	1	7.00
	Gombos G-450	6	5.00
	Demornay Bonardi H480	13	5.00
	Demornay Bonardi J480	1	5.00
	Demornay Bonardi J102	2	5.00
	Demornay Bonardi XL-102	1	5.00
	PRD 585B	1	10.00
	PRD 130A	1	7.00
	Demornay Bonardi L-234	1	10.00
	Demornay Bonardi DBL-650	1	10.00
	Demornay Bonardi L-610	1	10.00
	Demornay Bonardi DBL-440A	1	10.00
	Waveline 260	1	15.00
	Demornay Bonardi L-010	1	10.00
	L. H. Terpening Co. 3232-550	1	10.00
	Guide Ind. Inc. 1516-.5	2	10.00
	H. P. 430C	2	20.00
	H. P. 430B	1	15.00
	Narda 438	1	20.00

Liveitup

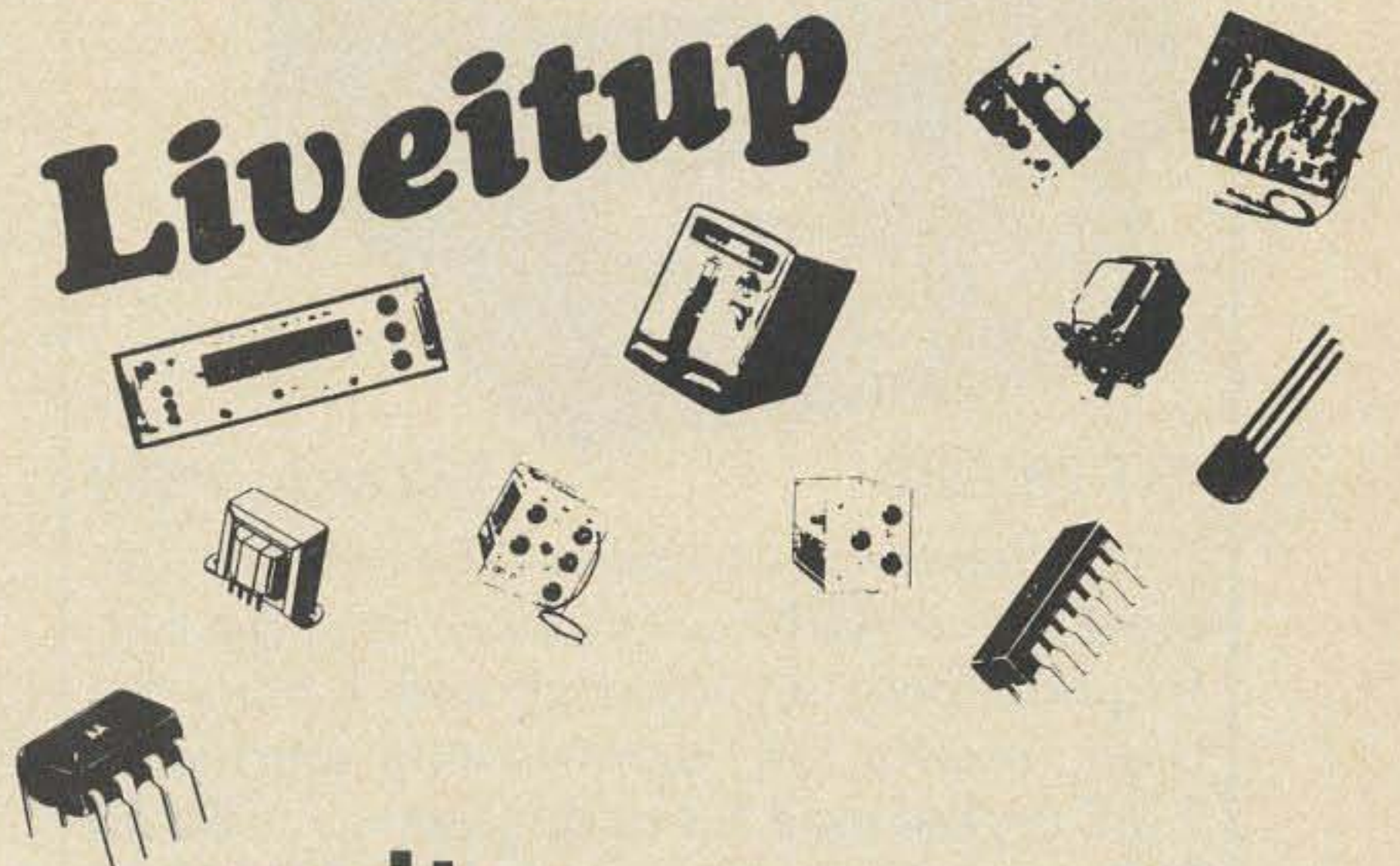

write
S & R
first

you'll save
time, postage
and MONEY

YOU NAME IT . . .

Tubes WE'VE GOT IT!

NEW	Price Each
6146A	\$ 4.00
8683	15.00
8106	2.00
8102	1.30
7984	3.95
6907	15.00
6360	5.00
8298	3.50
6146B/8298	4.50
5894A	17.00
2E26	2.00

Used and All Tested by JFF and Warranted by S and R Enterprises


6146	2.50
5894	8.00
2E26	1.25
6939	3.00
6883	2.00
6360	2.50
8032	2.00
8106	1.00
8458	5.00
6907	7.50
7377	7.50
8683	7.50
5762/7C24	100.00

Microwave Semiconductors Corp.	Price
MSC2001	35.00
MSC3001	60.00
MSC4001	87.00
MSC4003	125.00

Communications Corp.	
DI-28	3.75
DI0-28	19.00
EI-28	30.00

Dickson Fast Recovery Diodes	
IN3891	2.00
IN3890	2.00
IN3880	2.00




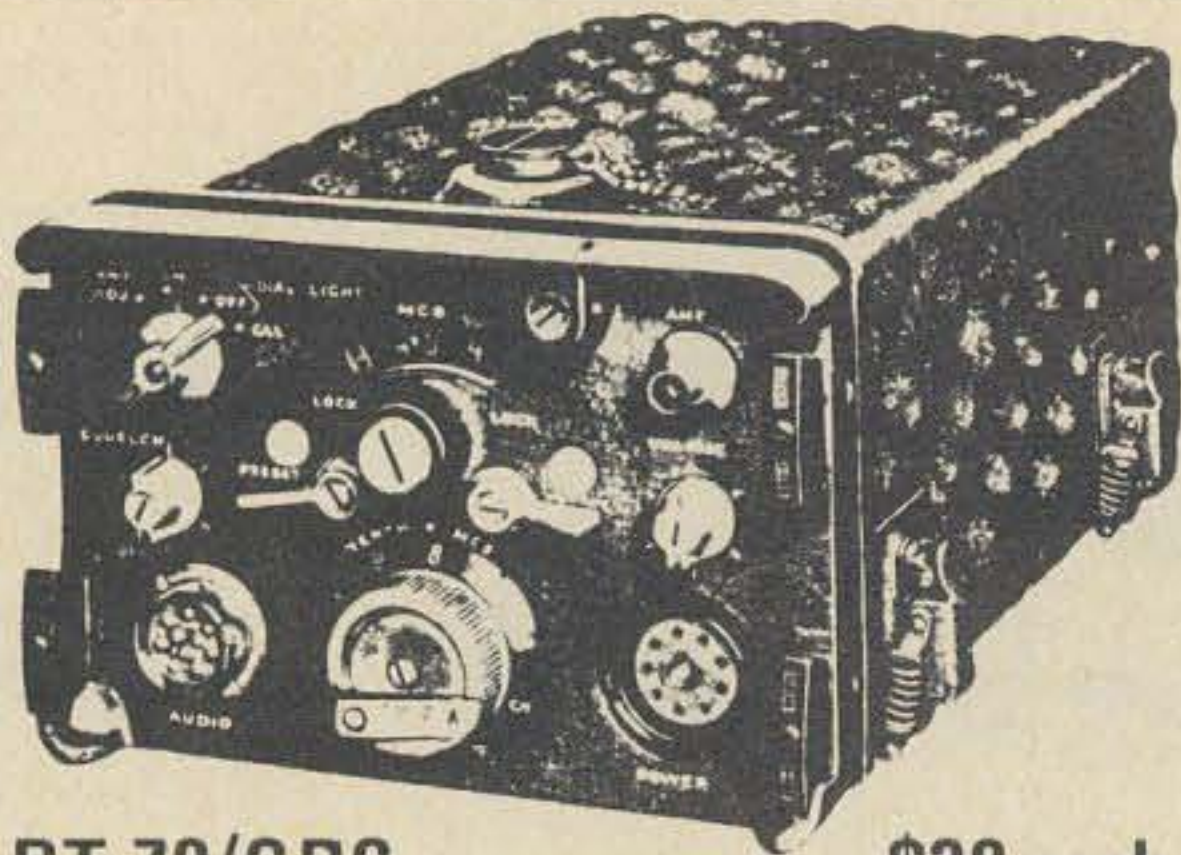


RT-70/GRC \$20 each, 3/\$50

Latest government release. Transmitter-Receiver RT-70/GRC covers 47 to 58.4 mc FM. Requires only 90 Volts dc and 6 volts dc. Used, visually OK, supplied with schematic. **1 MC crystal used for calibration \$4.00**
116 page maintenance manual for GRC \$2.00

LM FREQ METER \$35.00

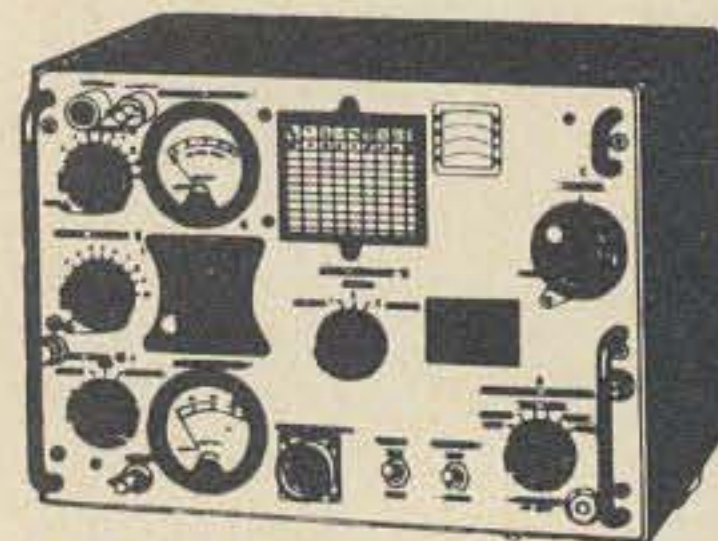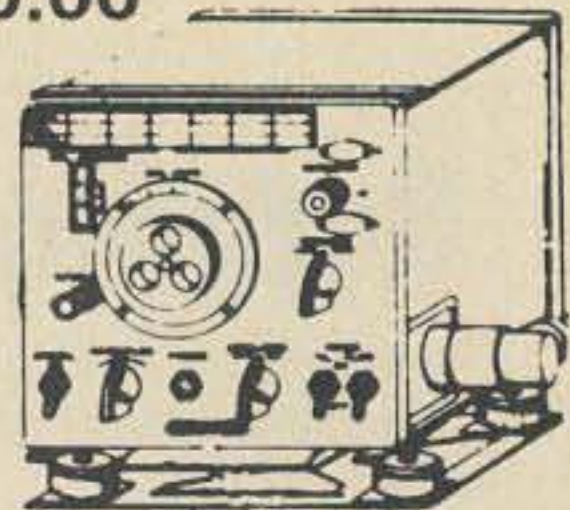
Lowest price yet. W/tubes, crystal and original calibration book. Look OK but unchecked. Typical schematic furnished. 8 lbs. #LM 35.00



TCS RCVR or XMTR

Used, look good, with schematic, receiver or transmitter. Frequency range 1.5 to 12 MC. Three bands, VFO or crystal, voice and CW. These sets Collins design, becoming scarce.

RCVR or XMTR \$35.00

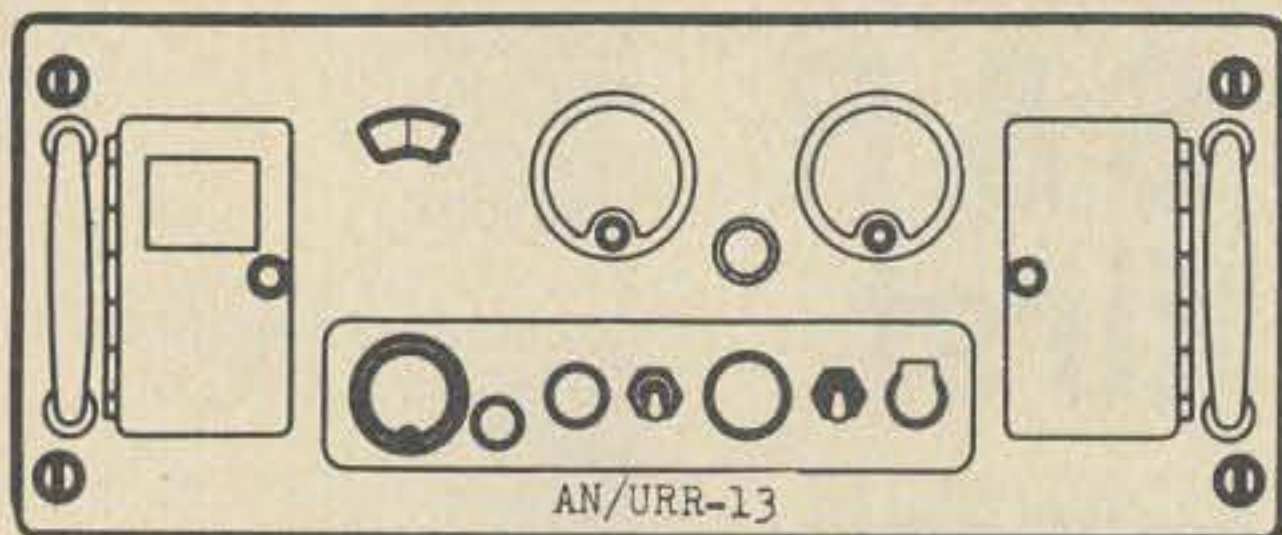

URR-13 RECEIVER

Listen in to jet planes, Air Force 1, U-2 spy planes, FBI, etc. They use the frequency covered by this receiver . . . 220 to 400 mc. Possibilities of covering the 220-450 mc band by re-tuning. Operates from regular 115 Volt 60 cycle, requires only antenna and speaker. Tuneable through the frequency, direct reading dial. Schematic and write up on this set furnished.

Visually OK condition . . . URR-13 - \$50.00

RCA INJECTION LASER DIODES

Another SUPER SCOOP by Meshna. Brand new RCA packaged, considered obsolete by RCA but what an exotic opto-electronic device for the sophisticated experimenter. Only several hundred on hand. Values shown are approx. as each diode characteristic varies. Each is marked with correct value.


6 WATT \$10.00

10 WATT \$15.00

RCA TD-XI TUNNEL DIODE

Original packaged, each factory marked, with spec sheet.

\$1.25 each, 5/\$5.00.

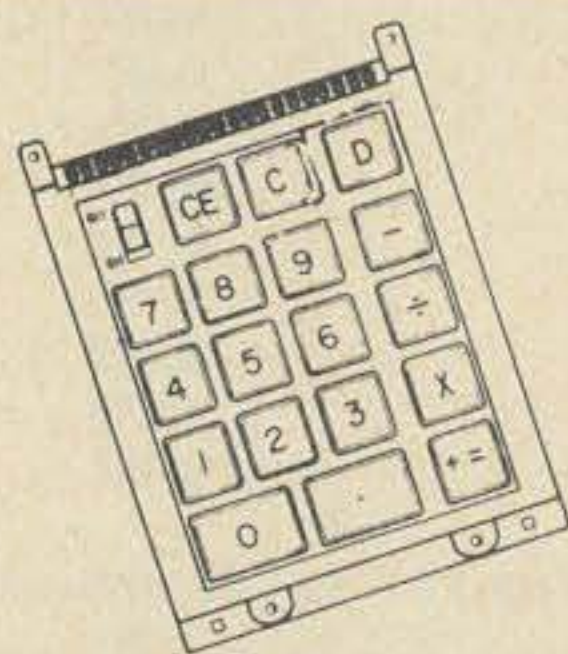

CALCULATOR KEYBOARD

A nice purchase by us due to contract termination. Brand new, 2 styles available, one for use with Gen. Inst. C-500 chip, another for use with Cal-Tex 5001 and 5002 chips or Mostek 5010 and 5012 chips. Measure approx. 2.6 x 3.7 inches.

Calculator Keyboard - \$8.00 (either one), any 2 for \$15.00

15 AMP BATTERY CHARGER

Brand new GE transformer, 25 amp fullwave bridge. Output approximately 15 volts up to 15 amps. Ideal battery charger or DC source for general use. With instructions , assembled in minutes.

PK-4 \$7.50

Meshna

Postage extra on above. MESHNA PO Bx 62 E. Lynn Mass. 01904

COMPUTER KEYBOARDS BRAND NEW


\$50 postpaid



Just arrived, a superb batch of brand new keyboards still in original manufacturers cartons. Beautifully finished in pastel colors with contrasting colored keytops. Made for table operation with fully enclosed metal cabinet. Two encoder boards mounted inside the cabinet with connections terminating on Spectra flat cable with plug. Key operation with bounceless magnet reed switch action. These computer keyboards were dumped as surplus by one of America's largest electronic companies and we were lucky enough to be on the receiving end. The price of \$50 includes prepaid insured shipment in the US and shipment same day as order received. Orders out of the US require an extra \$2.00.

LOGIC POWER SUPPLY

\$10

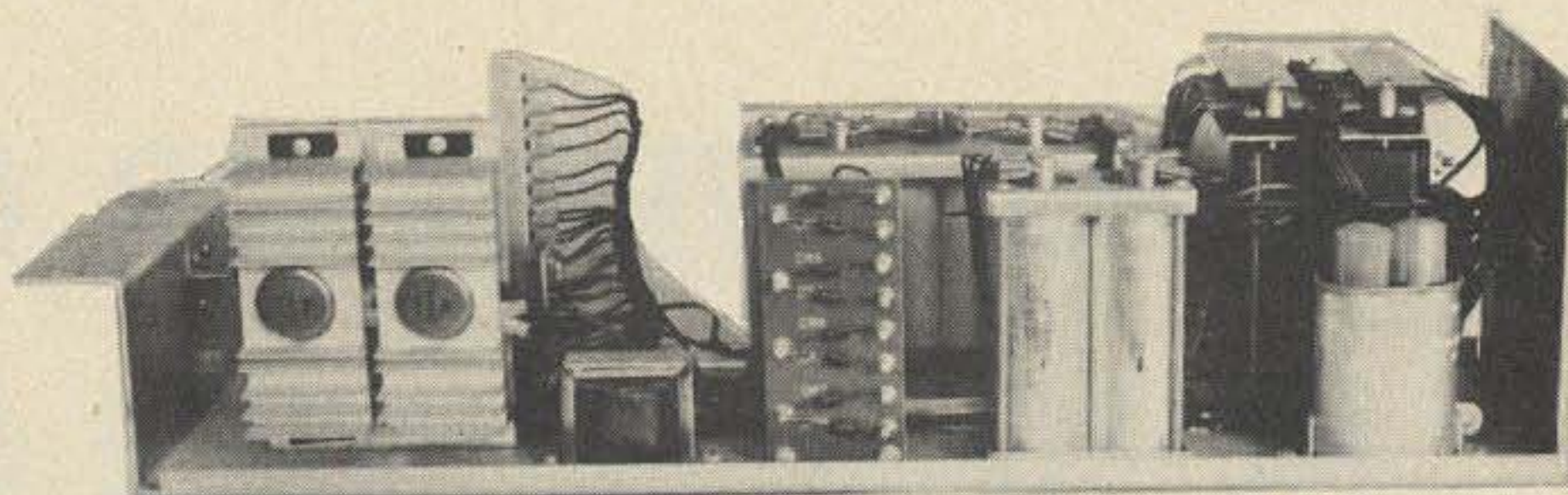

With 400 of these power supplies on hand, we figure we'd better sell them cheap and get them off the floor or all will collapse with a great crashing roar and land in a heap in the cellar.

These are from computer power supplies, used, good condition. Operate from standard house current. 4 output voltages MINUS 30 Vdc at 1 Amp, PLUS 30 Vdc at 1/2 Amp, PLUS 10 Vdc at 1 Amp, MINUS 10 Vdc at 1/2 Amp. Solid state construction with harmonic regulation on the transformer and transistor regulation on the 10 volt outputs. This is one helluva bargain and worth buying just to scrap for parts (if you're crazy enough to tear it apart). You've got 2 transistorized zener regulated plug-in boards with sockets and by changing the zener you can regulate from zero to 25 volts, 2 husky filter caps (18,000 μ f at 35 volts), power transistors on heat sinks, a nice transformer, and misc. other parts.

Ship. wgt. 37 lbs (you pay shipping)

\$10.00 each or 3/\$25.00

Meshna


Postage extra on above. MESHNA PO Bx 62 E. Lynn Mass. 01904

CAPACITOR ASSORTMENTS • ANTENNAS • INTEGRATED CIRCUITS • RESISTORS •

HEAT SINKS • IC TERMINALS • IC SOCKETS • DIODES • CAPACITORS • TRANSFORMERS • RESISTORS • INTEGRATED CIRCUITS •

HAVE A COPY OF OUR NEW CATALOG YET?

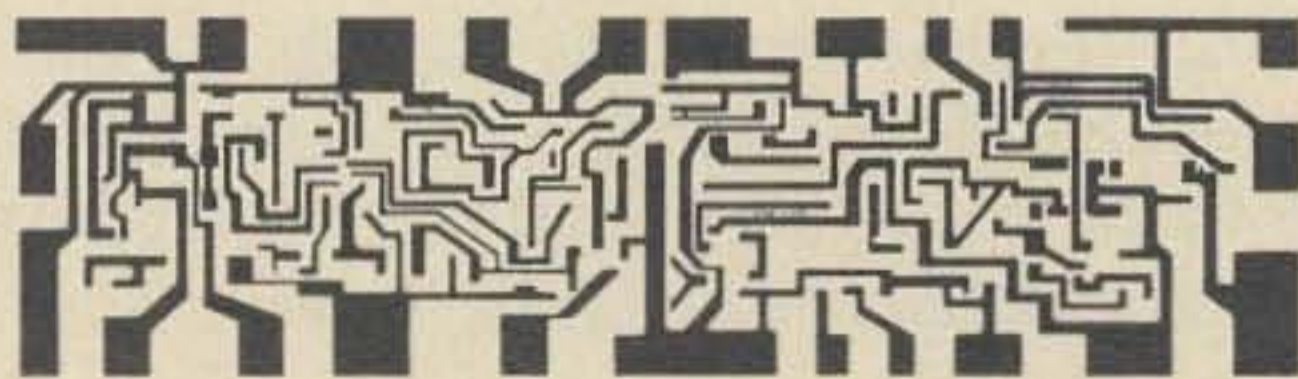IF NOT, WRITE OR CIRCLE READER SERVICE CARD FOR YOUR COPY NOW!




SOLID STATE SYSTEMS, INC.
P.O. BOX 773
COLUMBIA, MISSOURI 65201

(CALL TOLL FREE) 800-325-2981


UNIVERSAL DECADE COUNTING UNITS • RESISTOR ASSORTMENTS • LED DISPLAYS

TRANSFORMERS • CAPACITORS • DIODES • IC SOCKETS • HEAT SINKS • VECTORBOARDS • VECTORPINS • INCANDESCENT DISPLAYS

the problem solver

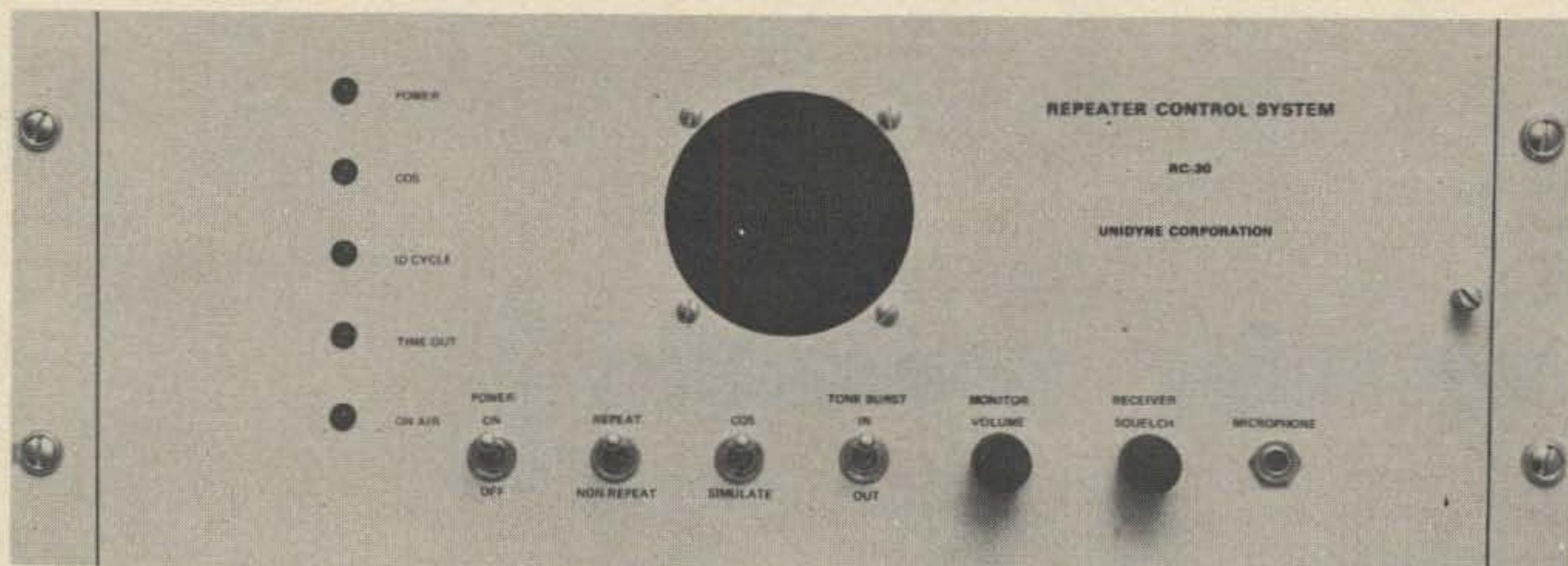

CONFORMS TO LATEST FCC RULES • SOLID STATE REPEATER CONTROL SYSTEM • COMPATIBLE WITH ANY RECEIVER, TRANSMITTER, POWER, FREQUENCY AND ID SYSTEM • 3 MINUTE TIME OUT • 5 SECOND DELAY DROP OUT • CARRIER OPERATED SENSOR • ID CONTROL • AUDIO INTEGRATION • OPTIONAL TONE BURST DECODER WITH AUDIO NOTCH FILTER • TELEPHONE REMOTE CONTROL • TONE DECODER VHF LINK REMOTE CONTROL • LOGGING CONTROL • 120 VOLT AC OPERATION WITH AUTOMATIC 12 VOLT DC SWITCHOVER • CYCLING TRICKLE CHARGER • FUNCTION STATUS DISPLAY LIGHTS AND CONTROLS • BUILT IN MONITOR AND SPEAKER • REMOTE RECEIVER SQUELCH • ALL FUNCTIONS ON PRINTED CIRCUIT CARDS • ADD NEW FUNCTIONS AT ANY TIME WITH BUILDING BLOCK CONCEPT • FLEXIBLE SYSTEMS FOR HIGHLY VERSATILE REPEATER STATION • TELEPHONE LINE FAILURE MONITOR

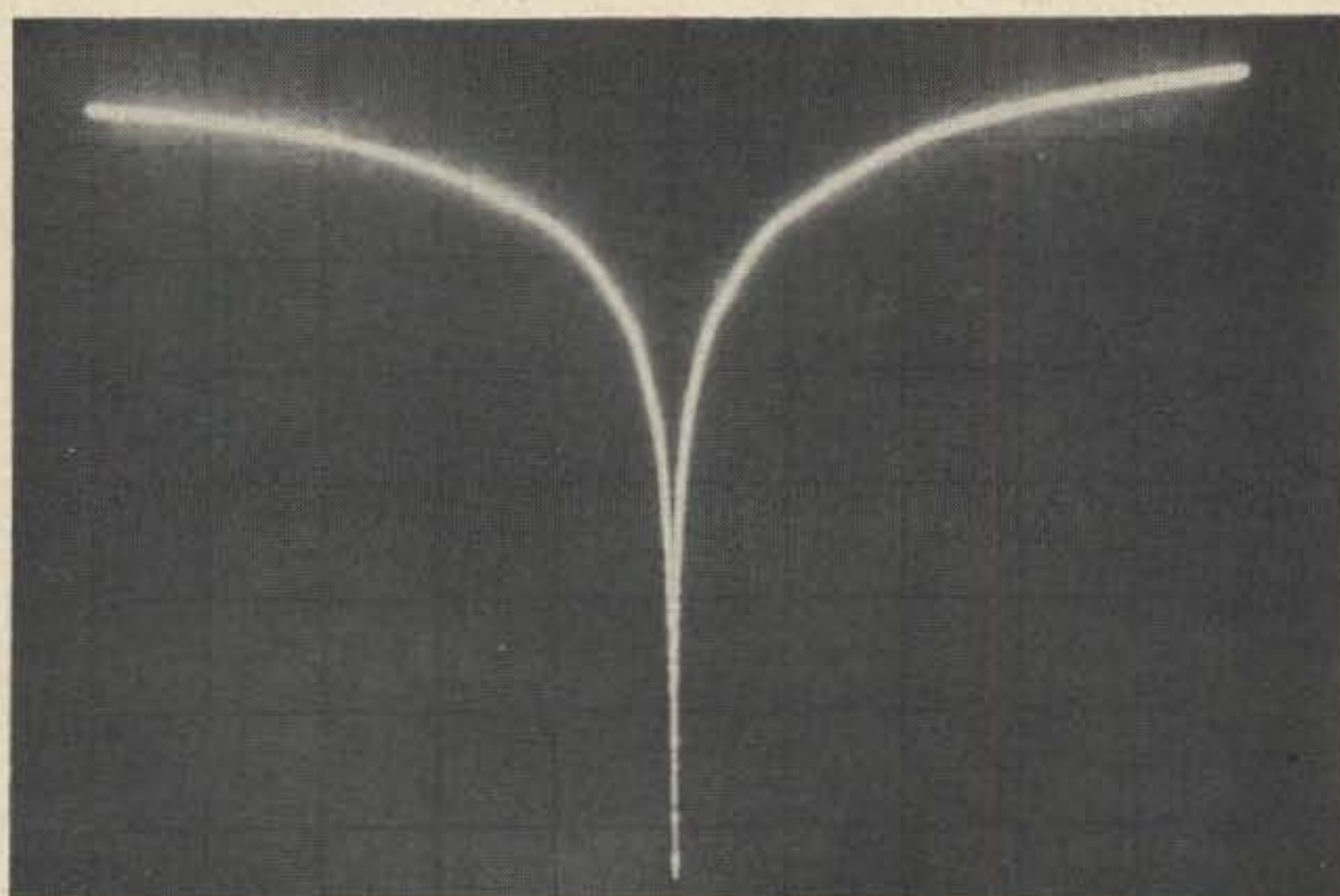

TONE BURST DECODER
NOTCH FILTER
SHOWING OVER 70 DB
ATTENUATION AT 1950 HZ

UNIDYNE CORPORATION

3224 Peachtree Road, N.E., Atlanta, GA 30305

INTERNATIONAL ELECTRONICS UNLIMITED

TTL								8000 Series	
7400	.25	7430	.25	7470	.50	74123	1.15	8091	.69
7401	.25	7432	.30	7473	.55	74145	1.25	8092	.69
7402	.25	7437	.50	7474	.55	74151	1.05	8093	.69
7403	.25	7440	.25	7475	.95	74153	1.45	8094	.69
7404	.29	7441	1.25	7476	.55	74154	1.75	8095	.69
7405	.27	7442	1.15	7483	1.25	74155	1.35	8123	1.75
7406	.55	7443	1.25	7485	1.20	74157	1.50	8214	1.95
7408	.29	7444	1.30	7486	.55	74161	1.65	8280	.95
7409	.29	7445	1.25	7489	3.25	74164	2.95	8520	1.45
7410	.25	7446	1.45	7490	1.25	74165	2.95	8551	1.95
7411	.35	7447	1.45	7492	1.05	74175	2.95	8810	.95
7413	.95	7448	1.50	7493	1.05	74181	4.50	8812	1.25
7420	.25	7449	.29	7494	1.10	74192	1.65	8831	1.95
7423	.37	7450	.32	7495	1.05	74193	1.65	8836	1.25
7425	.39	7451	.32	7496	1.05	74194	1.65		
		7453	.30	74121	.55	75195	1.15		
		7460	.30						

FIRST TIME OFFERED

9601 Retriggerable one shot \$1.15 ea

november specials

7453 ... 7/\$1.00 LM308 ... \$.95 ea LM747 ... \$.75 ea
 7454 ... 7/\$1.00 LM72350 ea 883640 ea
 7460 ... 7/\$1.00 LM739 ... 1.00 ea 960195 ea

SALE PRICES END NOVEMBER 30

Low Power Devices

74L00	.40	74L72	.60
74L02	.40	74L73	.80
74L04	.40	74L74	.80
74L10	.40	74L78	.80
74L16	.40	74L85	1.25
74L20	.40	74L86	.95
74L30	.40	74L90	1.75
74L42	.80	74L93	1.75
74L51	.40	74L95	1.75
74L71	.60	74L164	2.95

Linears

LM300 Pos V reg (super 723 V) TO5	\$.95 ea
LM301 Hi performance ampl TO5	.45 ea
LM302 Voltage follower TO5	.95 ea
LM304 Neg Volt regulator TO5	1.25 ea
LM305 Pos Volt regulator TO5	1.25 ea
LM307 Op Amp (super 741) TO5	.45 ea
LM308 Micro power Op Amp TO5	1.25 ea
LM309K 5V 1A power supply reg TO3	1.95 ea
LM309H 5V regulator TO5	1.25 ea
LM310 Volt follower Op Amp TO5	1.45 ea
LM311 Hi perf volt comp TO5	1.25 ea
LM320 -5.2V Neg regulator TO3	1.95 ea
LM320 -12V Neg regulator TO3	1.95 ea
LM320 -15V Neg regulator TO3	1.95 ea
LM380 2 watt audio amplifier Dip	1.75 ea
LM3900 Quad Amplifier Dip	.50 ea
LM709 Op Amp TO5 or Dip	.29 ea
LM723 Volt reg. Dip	.75 ea
LM741 Comp Op Amp TO5-Dip 10/\$3.95	.45 ea
LM747 Dual 741 Op Amp Dip 4/\$3.50	.95 ea

Phase Locked Loops

NE565 Phase locked loop dip	\$2.95 ea
NE566 Function Gen TO5-mini dip	2.95 ea
NE567 PLL/Tone Gen TO5-mini dip	2.95 ea

Memories - Are Made Of -

1101 256 Bit Ram Mos (2501)	2.95 ea
1103 1024 Bit Ram Mos	7.95 ea
7489 64 Bit Ram TTL	3.25 ea
8223 Programmable Rom	
Data Included with Memories	6.95 ea

LED

MV10B Visible red SUPER SPECIAL	.25 ea
MV50 type red emitting	.25 ea or 5/1.00
MV5020 type Large red	.35 ea or 3/1.00
ME4 Infra red TO18	.69 ea
MAN 1 The Original	4.25 ea
MAN 3 type	1.95 ea, 3 or more 1.49 ea
MAN 4 type	2.75 ea, 3 or more 2.50 ea
Data Lite 707 (MAN 1 repl)	4.25 ea

Opto Isolators

MCA 2 30 Darlington	.95 ea
MCD 2 Diodes	1.95 ea
MCT 2 Transistor	1.45 ea

MOS Shift Registers - Limited quantities

2506 Dual 100 bit dyn. shift reg. (mini)	.30 ea
2509 Tristate dual 50 bit st. shift reg.	.30 ea
2510 Tristate dual 100 bit st. shift reg.	.30 ea
2511 Tristate dual 200 bit st. shift reg.	.30 ea
2518 Hex 32 bit static shift reg.	.30 ea
2519 Hex 40 bit static shift reg.	.30 ea
2519 Hex 40 bit static shift reg.	.30 ea
2521 Dual 128 bit shift reg. (mini)	.30 ea
2522 Dual 132 bit shift reg. (mini)	.30 ea
2524 512 bit recirc. dyn. shift reg. (mini)	.30 ea
2525 1024 bit recirc. dyn. shift reg. (mini)	.30 ea
2527 Dual 256 bit static shift reg. (mini)	.30 ea
Assortment of any 2500 MOS items	4/1.00

NOTE: 2500 series MOS shift registers are factory seconds & have not been re-screened.

Calculator Chips

5001 LSI (40 pin) Add, subtract, multiply & divide 12 digit	
Data supplied with chip	6.95 ea
Data only-Refundable w/purchase	1.00 ea
5002 LSI Similar to 5001 except designed for battery power	
Data supplied with chip	8.95 ea
Data only-Refundable w/purchase	1.00 ea
5005 LSI (28 pin) Full four function memory, 12 digit display and calc. 7 segment multiplexed output	
Data supplied with chip	10.95 ea
Data only-Refundable w/purchase	1.00 ea

Digital Clock ... on a Chip

MM5311 (28 pin) Any readout. 6 digit BCD, with spec sheet	11.95 ea
MM5312 (24 pin) Any readout. 4 digit 1pps BCD, with spec sheet	8.95 ea
MM5314 (24 pin) LED-Incandescent readout 6 digit with spec sheet	10.95 ea
MM5316 (40 pin) Normal alarm, snooze alarm, sleep timer 12 or 24 hour operation, with spec sheet	15.95 ea

Grab Bag Specials

15 Assorted DTLs (dip)	1.00/bag
15 Assorted TTLs (dips)	1.00/bag

NOTE: Factory seconds, not tested.


Satisfaction guaranteed. All items except as noted are fully tested. Minimum order \$5.00 prepaid in US and Canada. California residents add sales tax. Orders filled within 3 days after receipt. Please add \$.50 per spec sheet for items priced at less than \$1.00 each.

INTERNATIONAL ELECTRONICS UNLIMITED

P.O. BOX 1708 S

MONTEREY, CA 93940


EXCITING NEW PRODUCTS

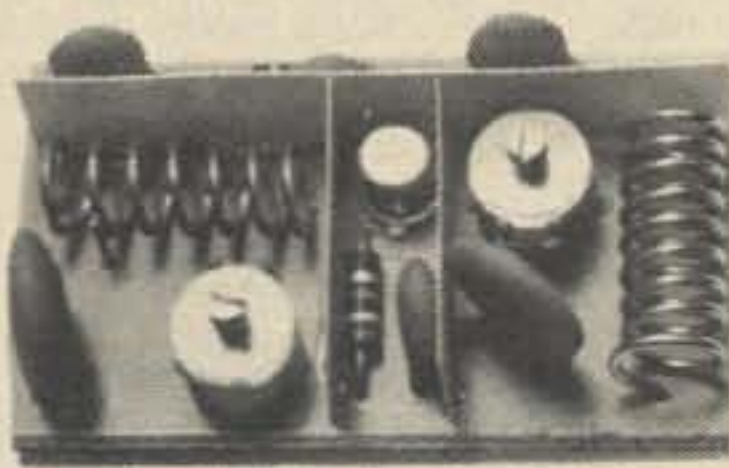

2-METER PREAMP

20 dB Gain, 2.5 N.F., 12V dc, Size 1" x 1 1/4" x 1/2". Diode protected MOSFET. 90-day guarantee. Sh. wt. 4 oz. Major Components Separately Shielded.

Kit \$9.50
Wired \$12.50

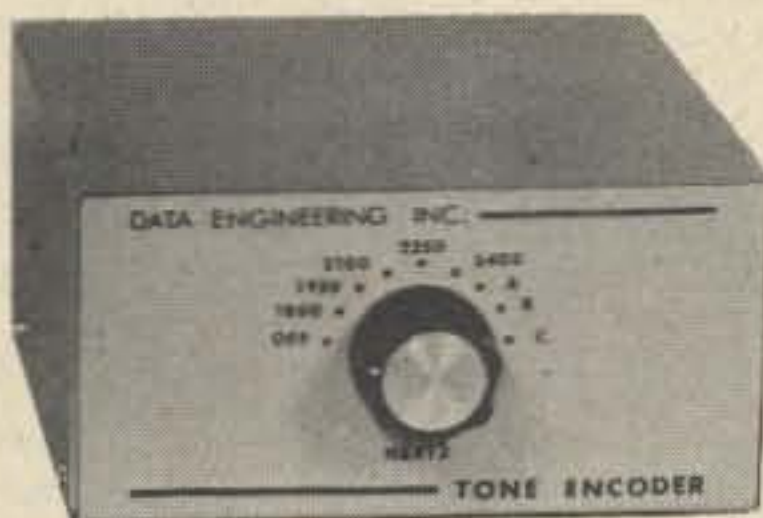

TONE ENCODER

Eight pre-adjusted tones. Duration and Output adjustable, PLL circuitry for extreme stability. Choice of continuous or tone burst operation. Tone burst operation requires no batteries. Easy to install. Includes three special single or dual tones.


TE8-K Kit \$31.95
Wired \$39.95



TOUCH-TONE DIALER

The electronic touch-tone dialer for home and car. It's safer and more accurate to use than a pad. Memory includes Access Code plus five phone numbers. Numbers easily updated. Built-in monitor. Complete PTT operation with transmitter hold.

TTD-4K
..... WIRED \$59.00
Kit \$49.00

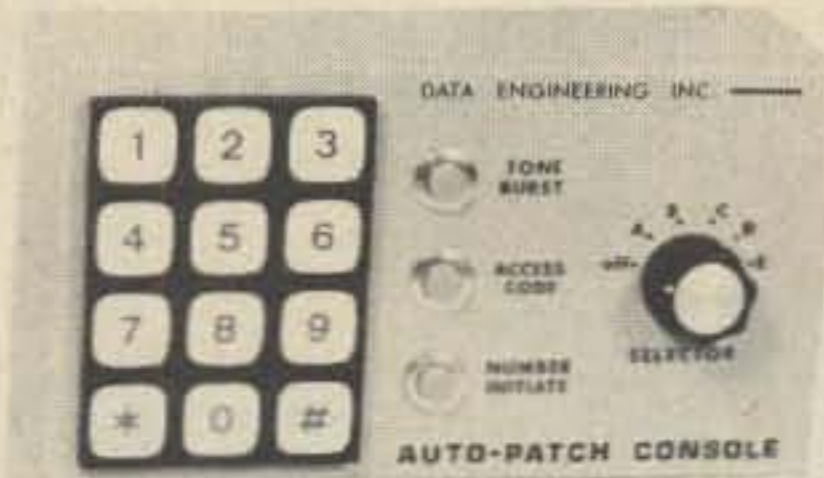

AUTO-PATCH CONSOLE

This mobile or home console includes all the features you need for complete auto-patch operation. A Touch-Tone Pad; an automatic dialer for sending one access code plus five Touch-Tone phone numbers; a single/dual tone burst encoder adjusted to your choice of frequency above 500 Hz, and a built-in motor. Complete PTT operation with one second transmitter hold.

APC-4K Kit \$84.50
APC-4A Wired \$98.50

TOUCH-TONE DECODER

A highly reliable twelve digit decoder with input protection, and PLL circuitry for extremely stable operation. Heavy duty output relays, small size, plug-in circuit board. All these major features at an UNBEATABLE price.

TTD-12K Kit \$89.50
TTD-12 Wired \$129.50



TOUCH-TONE PAD

In less than 15 minutes you can convert your portable transceiver to Touch-Tone operation.

TTP Assembled ... \$44.50
TTP Kit \$34.50

PAD-PULSER

Now you can also obtain pulsed operation from your Touch Tone Pad. Convert Touch-Tone frequencies to decimal pulses at 2805 Hertz with just a flip of the switch. Option can be added to TTP-2/K, TTD-4/K and APC-4/K.


PP-12K Kit \$22.95
PP-12 Wired \$29.95



VHF FREQUENCY STANDARD - FMS-5

Cal. receive and transmit crystals in 10, 6, 2 and 1 1/2 meter FM bands. Markers for all FM channels. Check deviation. Precision 12 MHz crystal. No unwanted markers. Osc. and output buffered. Sh. wt. 2 lbs. (Less Batteries) ... \$44.50

Kit \$37.50

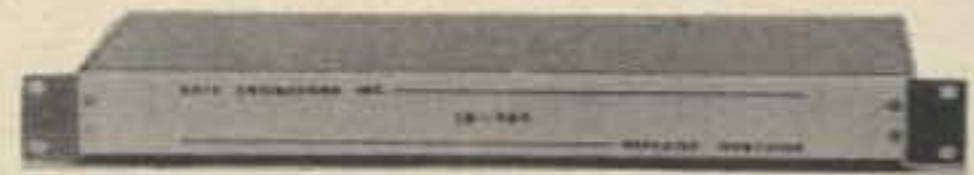

REPEATER ID

Highly stable oscillator for automatic timing. AC or DC operation. ROM provides for more than 25 characters, more than necessary for DC "any call" RPT. AUX is automatically added to ID if desired when main power is lost. Toneburst operation available.

ID-101K Kit \$49.95
ID-101 Wired/Tested
\$69.95

ID-101R assembled in 1 1/2" rack cabinet \$109.00



TONE DECODER

Versatile single/dual tone decoder. PLL circuitry for extreme stability. 1 amp output relay can be reset automatically or manually. Monitor position. Adjustable sensitivity. Internal strap selects single or dual tone operation.

TD-2K Kit \$31.95
TD-2 Wired \$39.95

5-year guarantees. Send for Catalog




Data Engineering, Inc. 5554 Port Royal Road

Ravenworth Industrial Park, Springfield VA 22151

Phone: 703-321-7171

VIDEO TAPE RECORDERS

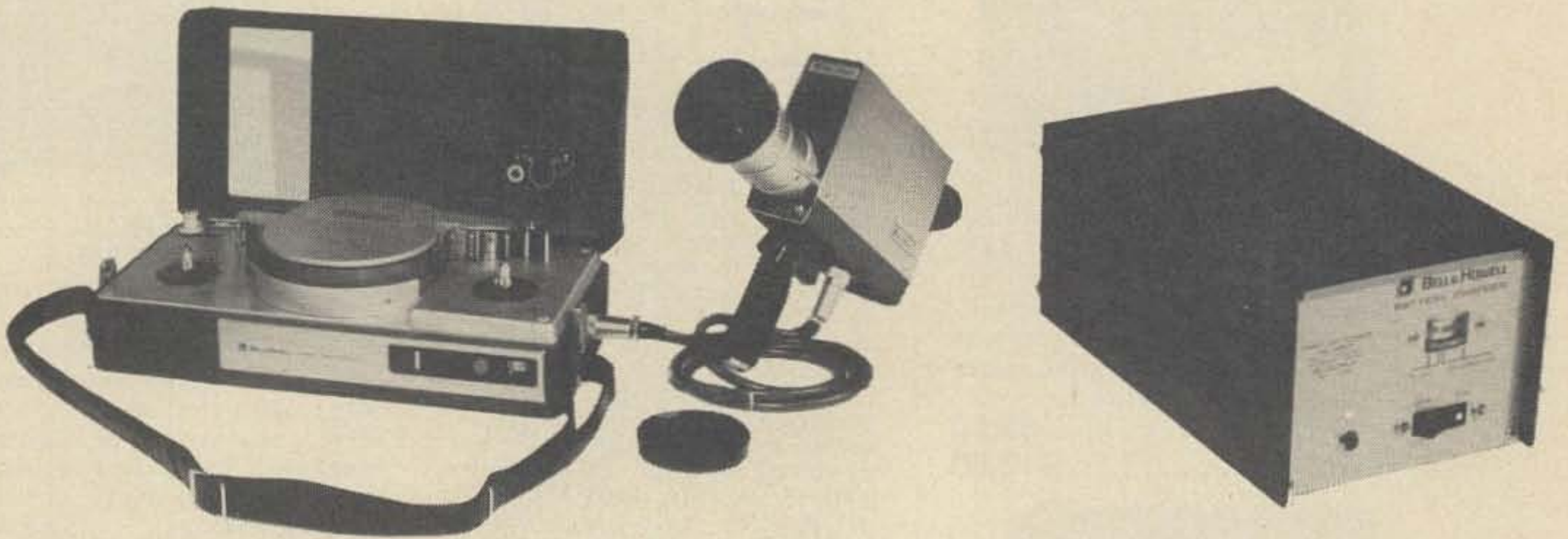

BELL & HOWELL MODEL 2965

This is a portable system and comes with recorder, camera and charger. A TV monitor is built into the recorder. Camera includes built-in Microphone and Zoom lens. Recording time is 20 minutes on 5" tape. Recording is both video and audio.

SPECIFICATIONS

RECORDER:

AGC: Audio & Video
 RESOLUTION: 525 lines, HOR. RESOLUTION: 300 lines
 AUDIO RESPONSE: 80-10,000 Hz.
 POWER REQUIREMENTS: 12V DC, 10 watts
 BATTERIES: 2/3G x 3/U Rechargeable (not included)
 CHARGER: Model 105905 included
 GENERATOR: Built-in 2:1 EIA Sync Generator

CAMERA:

RESOLUTION: 525 lines
 VERT. FREQ: 60 Hz (EIA)
 HOR. FREQ: 15,750 Hz (EIA)
 VIDEO OUTPUT: 1.0 p-p, 75 ohm, unbalanced
 MIN. ILLUMINATION: 30 lux.
 VIEWFINDER: 1 1/2" (1" CRT w/magnifier)
 LENS: 5:1 zoom F2 - 22
 SHIPPING WT. 35 lbs.

LIST: \$1595

OUR PRICE (NEW) \$550.00



BELL & HOWELL Model 2966 – SHIBADEN SV700VC (Assemble, Edit and Stop Motion)

This video recorder will record directly from a standard TV set or a TV camera. It will play back over your home TV set. Audio may be dubbed onto the tape. A 7" reel (2400') will record 1 hr. No home VTR unit under \$1000 can match the quality and capabilities of this unit.

SPECIFICATIONS

RESOLUTION: 525 lines, Standard TV or CCTV recording
 VIDEO: Input and output: 1.0V p-p, 75 ohms, unbalanced.
 Greater than 3.5 MHz freq. response. 300 lines plus Hor. resolution.
 AUDIO: Mike or line inputs. 60-10,000 Hz freq. range
 POWER REQUIREMENTS: 110V AC, 95 watts
 DIMENSIONS: 18 3/8" W x 10 3/16" H x 15 11/16" D
 AGC or Manual Audio & Video gain
 POWER REQUIREMENTS: 110V AC, 95 watts
 WEIGHT: 65 lbs.

LIST PRICE (1972) \$995.00

OUR PRICE (NEW) \$450.00

(USED) \$250.00

Experimenter's Special \$125.00

MAINTAINANCE
 MANUAL \$5.00

ORDER BLANK

Please rush _____ Bell & Howell model/s 2966 _____ Bell & Howell model/s 2965

_____ Rolls, Video Tape _____ Batteries _____ Color Adapters Price _____

to: Name _____ Shipping _____

Address _____ Total _____

City _____ State _____ ZIP _____

RECHARGEABLE BATTERIES — New, for Porta Pak . **\$36.00** a set.

COLOR ADAPTERS — limited number available, will work in almost any Black and White VTR to convert to NTSC color, record-playback — does not impair monochrome use. **\$400.00** ea. prepaid.

NEW NAME BRAND VIDEO TAPES — 2400 ft. (1 hr.) any quantity available, shipping wt. 2 lbs. **\$25.00** each.

CONDITIONS OF SALE:

NEW EQUIPMENT — sold new, but as is. Guaranteed 90 days. Replaced or repaired by us, if found defective upon arrival.

USED EQUIPMENT — sold *as is* in good working order. NO warranty. All units checked prior to shipment.

EXPERIMENTER'S DELIGHT — used *as is* repairable. Physically intact not beat to hell, but requiring some work. Problems and probable causes listed with each machine.

PARTS — available at near giveaway prices, through us.

SERVICE — units can be serviced by any competent video technician, as well as through Bell & Howell AV Service and Shibaden in Melrose Park, Illinois.

QUANTITY DISCOUNT — on orders of more than 10 machines.

DEALER INQUIRIES — are invited for sale of new equipment.

New machines have standard Japan EIA 8P connector to mate with all popular VTR monitors. Used machines have all coax and cannon xl connectors. Used machines do not have AGC or edit ability, but are otherwise identical and interchangeable.

All sales are final. Cash with order. Shipped best way. Add \$20.00 per VTR and \$12.00 per Porta Pak for shipping — excess refunded.

COMMUNICATIONS UNLIMITED

9519 MAIN STREET P.O. BOX 463
WHITMORE LAKE, MICHIGAN 48189

(313) 449-4367

We are also licensed
for
2-way radio repair



from

Lindy®

THE AMAZING NEW

W-2®

NO-STAIN INK BALL PEN

DO YOU KNOW...THE W-2.....

IS NON-TOXIC

ERADICATES FROM PAPER

PERMANENT ON LEGAL DOCUMENTS

HAS AN ALMOST INDEFINITE SHELF LIFE

WASHES OUT IN PLAIN WATER - HOT or COLD

NO RUB...NO SCRUB...NO SOAP or DETERGENT

UNCONDITIONALLY GUARANTEED

EXCLUSIVE PATENT #3,468,679 NO-STAIN INK



WASHES OUT IN PLAIN WATER



DARK BLUE INK

FEATURES:

THE NEW
"Grip-Clip"™

PAT. #3,466,708
that will not slip
out of your pocket.

#261-M
MEDIUM POINT

25c

#261-F
FINE POINT

29c



mfd. by LINDY PEN CO., INC.

north hollywood, calif. 91605, u.s.a.

"SPECIAL QUANTITY PRICES ON IMPRINTED ORDERS"

GET TO THE FAST TOP!

NOW YOU CAN CHANGE, ADJUST OR JUST PLAIN WORK ON YOUR ANTENNA AND NEVER LEAVE THE GROUND!

ROHN manufacturers towers that are designed and engineered to do specific jobs and that is why we have the FOLD-OVER TOWER . . . designed for the amateur.


When you need to "get at" your antenna just turn the handle and there it is. Like other ROHN big communication towers, they're hot dip galvanized **after** fabrication to provide a maintenance free, long lived and attractive installation. ROHN towers are known and used throughout the world . . . for almost a quarter century . . . in most every type of operation. You'll be in good company. Why not check with your distributor today?

ROHN **MANUFACTURING**
®
DIVISION OF 

P.O. Box 2000 / Peoria, Ill. 61601

MITTS Presents The New 908M Series Handheld Calculator

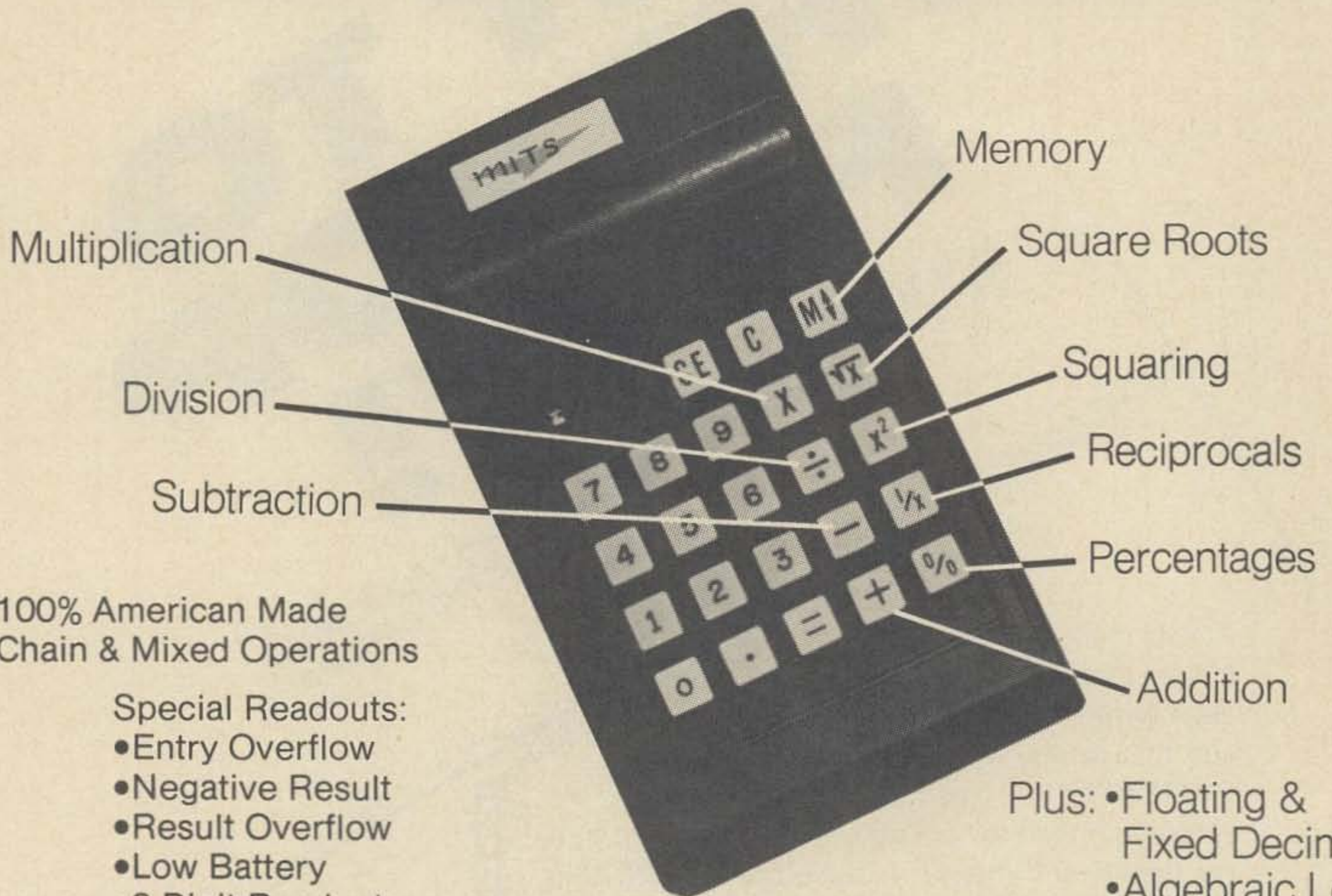...8 Functions Mean a Handful of Features!



100% American Made
Chain & Mixed Operations

Special Readouts:

- Entry Overflow
- Negative Result
- Result Overflow
- Low Battery
- 8 Digit Readout
(Always the most significant digits)
- Bright Led Display

- Plus:
- Floating & Fixed Decimal
 - Algebraic Logic

SIZE: 5-3/4" x 3-1/4" x 1-1/2"

PRICES* \$129.95 Assembled
\$ 99.95 Kit
Full 1 Year Warranty

AC Adapter for 110VAC Operation \$6.95
Carrying Case (leatherette) \$5.95

*Prices subject to change without notice.

MITTS®

**Micro Instrumentation &
Telemetry Systems, Inc.**

6328 Linn, N.E., Albuquerque, New Mexico 87108
505/265-7553 Telex Number 660401

Enclosed is a Check for \$ _____
or BankAmericard # _____
or Master Charge # _____
Credit Card Expiration Date _____
Include \$5.00 for Postage and Handling

Kit Assembled
 Please Send Information on Entire MITTS Line.

NAME _____
ADDRESS _____
CITY _____
STATE & ZIP _____

MITTS/ 6328 Linn, N.E., Albuquerque, New Mexico 87108 505/265-7553 Telex # 660401



UT-1

Portable Tune Up Meter with cables to plug into Motorola, Link, GE, Standard, etc. This unit gives you the meter functions of the radio being tested. It also operates as a portable dc voltmeter with the following full scale ranges: 1.5, 5, 15, 50, 150, 500, 1 KV with a special 3 volt range for GE Progress Line equipment. The UT-1 can be set zero center for discriminator readings. Also featured in the UT-1 is a field strength meter. Place your order now. Kit form **\$42.50**. Wired **\$49.95**. Extra cables of your choice (specify rig) **\$5.00 ea.** (\$2.00 for postage and handling.)


TESCO-PAD

The "TESCO-PAD" has no tuned coils to go off frequency, no tuning necessary or even there! It's all in one "Black Box I.C." ready to go. The "TESCO-PAD" has a 1 second hold-up for your transmitter, complete P.T.T. operation, available with dual audio output levels, 12 or 16 tone combinations.

KIT **\$34.95** **\$39.95** Wired

(Add \$1.00 for 16 tone version)
(Add \$2.00 for dual output version)

Add \$1.00 for postage and handling.)

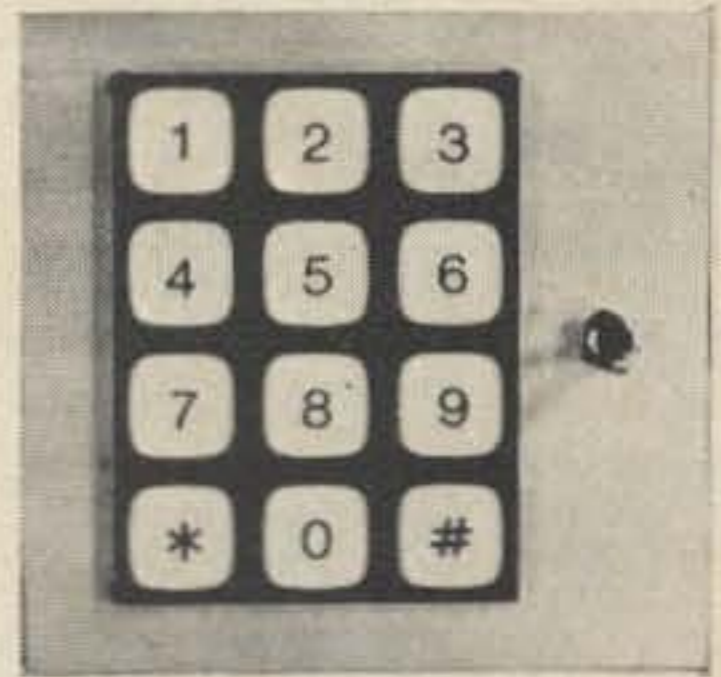

THE ULTIMATE IN 12V POWER SUPPLIES.....

- Tabletop size – 10¼" w by 8" h by 13" long
- 60 A @ slightly less than 12 Vdc
- Nominal Output: 50 A at 12 Vdc
- Voltage and current metering built-in
- Will run a mobile rig & even an amplifier from 110 Vac

\$100 KIT


\$125 WIRED


Shipped freight collect – 47 lbs.

ORDER NOW – PRICE INCREASE COMING IN EARLY 1974

Waller Electronics - Test Equipment Sales

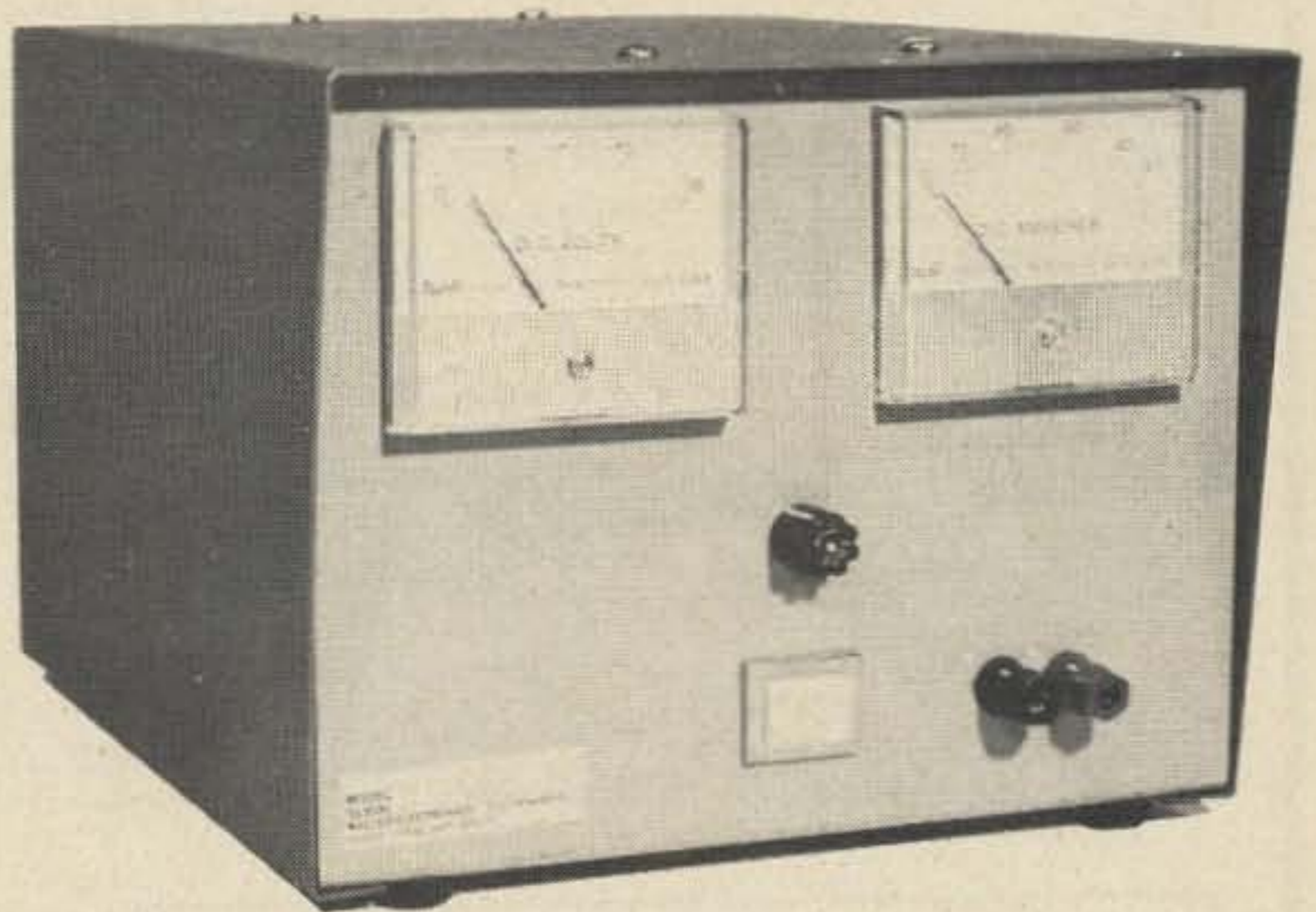P.O. Box 9913, Chevy Chase, Md. 20015 Telephone: 301-652-0996



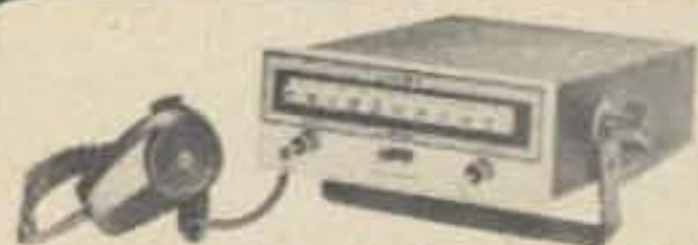

GTX-2 30 WATTS OUTPUT



GTX-200 30 WATTS OUTPUT

- 2 meter FM Transceiver**
- (1) GTX-2 (built-in DC PS) and 94/94 249.95
 - (2) AC REGULATED POWER SUPPLY 49.95
 - (3) 2 Extra crystals your choice (stock list) 12.00
- REGULAR \$311.90**
- OUR SPECIAL PACKAGE PRICE! \$249.95**

- 100 channel combinations; features independent selection of transmit and receive frequencies, and switch for pre-selected pairing.
- (1) GTX-200 (built-in DC PS) & 94/94 \$259.95
 - (2) AC REGULATED POWER SUPPLY 49.95
 - (3) 2 Extra xtals your choice (stock list) 12.00
- REGULAR \$321.90**
- OUR SPECIAL PACKAGE PRICE! \$259.95**

GTX-10

10 watts output

Simple conversion to 30 watts output



100% AMERICAN MADE

- (1) GTX-10 (built-in DC PS) & 94/94 \$199.95
 - (2) AC REGULATED POWER SUPPLY 34.95
 - (3) 2 Extra xtals your choice (stock list) 12.00
- REGULAR \$246.90**
- OUR SPECIAL PACKAGE PRICE! \$199.95**
- Please add \$10.00 Substituting HAMPAK for AC on GTX-10 Package. With HAMPAK & AC \$229.00



HAMPAC

Battery pack for GTX-10 portable operation. Uses 10 D cells (not included). (Includes portable antenna, carrying handle & mike clip) \$39.95



CLEGG FM-27Bs

(Reg. \$479.95), with Clegg AC (Reg. \$559)
Write for special deal!

Regency, Midland, Gladding 25, SBE, etc., also in stock. Please write for quote

* FLASH * FLASH * FLASH *

Look at what you get for NO REPEAT-NO EXTRA CHARGE. The GTX-2 and GTX-200 now have a super-sensitive Dual-Gate Mos Fet pre-amplifier BUILT IN the receiver front end for superb, less than .25 microvolt sensitivity. THE BEST receiver now even better!

30 WATTS OUTPUT. ALL SOLID STATE (no tubes). TRUE FM (not Phase modulation) for superb audio quality.


10 channels in GTX-2 & GTX-10 with 146.94/146.94 included. Three pole low pass filter on both transmit and receive. 1 watt low power position. Provision for tone encoder. Simple internal strapping provision allows multi-channel use of any crystal in GTX-2 and GTX-10. Microphone and mobile mounting bracket supplied. G-10 GLASS BOARDS. Professional level construction by distinguished Avionics Mfg. — General Aviation Electronics, Inc. The finest amateur FM transceiver available at any price. Size: 9 x 6 1/2 x 2 1/2. Weight 5 lbs. Current Drain: Receive: .09 amps, Transmit: High 5.0 amps, Low: 1.7 amps, Made in U.S.A.

	Reg.	Our Price		Reg.	Our Price		Reg.	Our Price
ALPHA			GONSET			NATIONAL		
Alpha-70 PA-70V vapor cooled linear, brand new cond.	1,275.00	895.00	6m Cumul IV	119.00	69.00	NCX-5 conv. to MK-2 w/NCX-A AC/spk, 100Kc cal.	429.00	325.00
AMECO			HALLICRAFTERS			NC-155 rcvr	119.00	69.00
TX-62 6 & 2 meter xmitter w/621 VFO, Dow Relay	149.00	95.00	SX-111 rcvr latest w/prod. dect.	129.00	99.00	NCX-5 MK II w/NCX-A AC/spk, 100Kc cal.	450.00	379.00
TX-62 6 & 2 meter xmitter	99.00	69.00	SR-150 xcvr w/AC/spk	350.00	249.00	SWAN		
BIRD			SX-146 rcvr, R-50 spk, HA-19 cal. (x ceives w/HT-46)	195.00	169.00	SW-240 w/117B AC/ps brand new cond.	229.00	179.00
43 wattmeters (new) limited quantity		95.00	SR-42A 2m xcvr, new cond, w/2 xtals	149.00	119.00	250C 6m xcvr w/117XC AC/spk, VOX, NS-1 noise silencer, new cond.	430.00	389.00
COLLINS			SR-46A 6m xcvr new cond. w/4 xtals	109.00	89.00	117X basic AC	65.00	39.00
625-1 VHF conv.	595.00	495.00	HA-26 6 & 2 VFO	39.00	29.00	TPL/TEMPO		
KWM-1 xcvr w/516F-1 AC and 312 B-3 (same as 312B-4, patch, SWR, etc.) latest, new cond.	495.00	395.00	HEATH			502 5-15/35-55 watt output 2m amp, new	105.00	79.00
CLEGG			HX-10 Marauder 180 watt SSB-AM xmitter	189.00	119.00	502B 1-3/45 50 watt output 2m amp, new	130.00	99.00
99-er 6m xcvr working, as is	59.00	29.00	HW-16 CW xcvr, 30, 40, 15	99.00	79.00	LW 1500 Dummy load w/117B AC/ps	119.00	79.00
Thor 6 xcvr w/AC mod	169.00	99.00	HG-10 VFO 80-2 meters	39.00	29.00	TC-102 24 hr. Digital clock, new	89.00	59.00
FM 27A FM xcvr, like new	339.00	289.00	SB-110A 6m SSB xcvr w/SB-500 2m transverter & HP-23A/AC like new, checked by Heath	439.00	329.00	TEST EQUIPMENT		
DRAKE			SB-500 2m transverter	129.00	89.00	Eico 378 Lab audio gen., like new	89.00	39.00
2B rcvr, 2BQ "Q" mult/spk	210.00	179.00	HD-1 "Q" mult w/built in AC ps.	10.00	10.00	Clemmons SB-83B sig. gen. like new	295.00	225.00
2A rcvr, 2AQ "Q" mult/spk and cal.	189.00	149.00	SB-A-300-3 6m Conv.	8.00	8.00	RCA WV-98C Senior VTVM, new	99.00	59.00
MN-2000 matching network	159.00	139.00	KNIGHT/ALLIED			Heath 10W-102 solid state scope, new	189.00	129.00
T4XB w/custom AC/spk by Drake, new cond, in carton	489.00	389.00	TR-108 15 watt 2m xcvr w/AC, DC, mic, like new	99.00	79.00	Winslow megohm meter (megger)	150.00	69.00
SW4A gen. cov. rcvr., new cond.	229.00	199.00	AX-190 ham rcvr, 80-10 + WWV, 1 KC. cal, etc.	199.00	149.00	LEADER write for prices		
GALAXY			MAGNUM			B & K write for prices		
FM-210 w/AC 210 amp, 6 xtals, mic.	189.00	125.00	Magnum 6 RF speech processor for Kenwood T-599, brand new, warranty	139.95	99.00	MIIDA T6854 4 1/2 digit digital auto-ranging multimeter, new	689.00	529.00
GLADDING						MIIDA T5108 10Hz to 550MHz freq. counter, new	950.00	725.00
Gladding 25 w/xtals 34/76, 94/94, 64/64, 22/82, 28/88, and 16T	199.00	159.00				MIIDA precision calculators	89.00	UP

COMING SOON!!!! Genave Touch-Tone Pad, Genave Repeater and MUCH MORE.



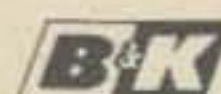NO ONE ANYWHERE BEATS OUR DEAL!
AMATEUR-WHOLESALE ELECTRONICS
8817 S. W. 129 Terrace-Miami, FL 33156



Telephone — days (305) 233-3631 — night and weekends — (305) 666-1347

We carefully and professionally service everything we sell. An employee always answers our night and weekend phone—not an answering service.

PRINTED CIRCUIT BOARD

2 oz. copper on glass epoxy base, approx. 5" x 6". Your choice copper on one or both sides.

LED READOUTS "Lowest Prices Ever"

3 for \$1.00

Similar to MAN-1. .33" high. 20 mA per segment. With decimal point.

Everyone checked - all segments operating Red - \$2.00 each, 6/\$10.00

Larger .7 inch readouts available - write for prices Green - \$3.00

LED - molded plastic dome shape with leads.

.312 inches in diameter

Red - \$.25 each, 5 for \$1.00

Green - \$.40 each, 5 for \$1.85

KODAK RED Wratten Filters

Perfect for light filter over red LEDs. 4" sq, .005" thick.

\$.35 each, 3 for \$1.00

LM 309 Voltage Regulator IC. 5 volts at 1 Amp. max. current.

\$2.00 each

ETCHANT FOR P.C. BOARDS

Ammonium persulfate, 1 lb. of crystals, just dissolve in H₂O.

\$1.00

IN 914 DIODES

10¢ ea/\$1.00 Dozen

TTL ICs

7400	\$.30	747455
740230	747585
740435	747660
740830	7490	1.00
7441	1.75	7412160
7447	1.40	74192	1.90
7448	1.65	741 op amp55
747355		

Please add shipping charges

MINIMUM MAIL ORDER \$2.00



SEND FOR LATEST FLYER OF SURPLUS AND NEW ELECTRONICS


JEFF-TRONICS

1916 Clark Avenue Cleveland, Ohio 44109



NEW and SURPLUS ELECTRONICS FOR THE HAM and EXPERIMENTER

SIZE:
3.55" X 6.20" X 2.12"

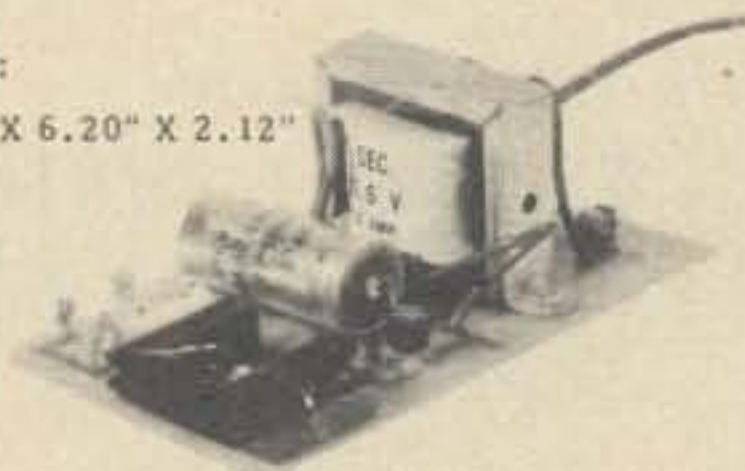

5VDC
3/4 AMP
POWER
SUPPLY
KIT

12.95

USES THE LATEST STATE-OF-THE-ART THREE TERMINAL REGULATOR CIRCUITRY.

HAS INTERNAL CURRENT LIMIT, THERMAL SHUTDOWN, AND SAFE-AREA COMPENSATION.

Greatest advance
in soldering since
electricity...

\$ 19.95

COMPLETELY PORTABLE
HEATS IN 5 SECONDS
SOLDERS UP TO 150 JOINTS
OR MORE PER CHARGE
RECHARGES AUTOMATICALLY
IN ITS OWN STAND
NO AC LEAKAGE OR INDUCED
CURRENT TO DAMAGE DELICATE
ELECTRONIC COMPONENTS.

WAHL




COMPLETE WITH RECHARGING STAND, FINE TIP AND INSTRUCTION BOOKLET

ALPHA-NUMERIC
KEYBOARD

\$ 50.00


MICRO SWITCH

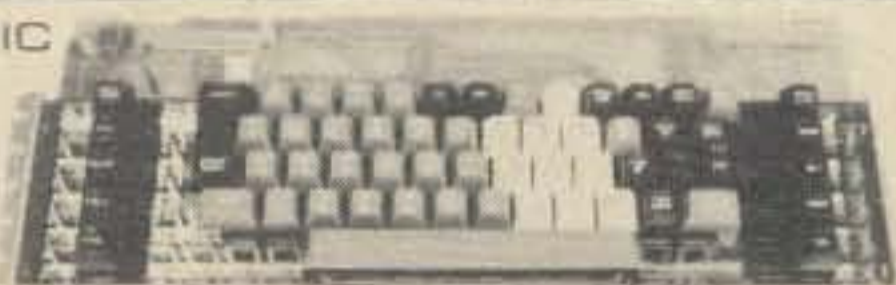

MODEL SW-10639 contains 61 #1SW11 Solid-State switches including key tops, ROM encoded into EBCDIC.

MODEL RW-01135 contains 56 #7A1MS Reed switches including key tops, diode encoded into EBCDIC.

"DIP CLIP" IC TEST CLIP

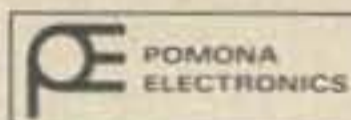

MODEL 3916

4.95




FOR 14 OR 16 DUAL-IN-LINE PACKAGES

The "Dip Clip" is specially designed to allow the attachment of test probes to 14 or 16 lead DIPS. The unique design greatly reduces the possibility of accidental shorting while testing live circuits. Numerous test probes may be quickly connected for hands-free testing.

MOS DIGITAL
CLOCK CHIP

\$ 14.95

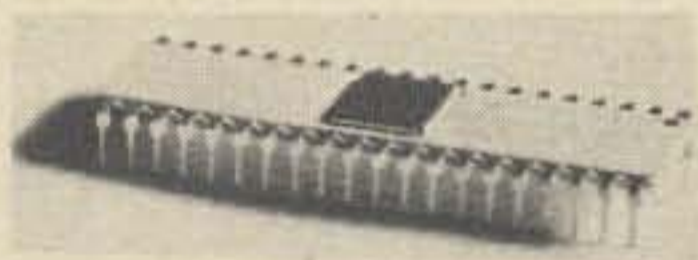

Four digit electronic clock LSI circuit in 40 pin DIP. Designed for direct output to Liquid Crystal Display. Internal options include: Alarm, Snooze, Seconds Display, Reset, and 24 hour operation.



POWER STRIPS

WITH: FUSE, SWITCH, AND LAMP



\$ 9.30

MODEL 11

Other Models Available




\$ 14.70

MODEL 12

NOBEX

DIGIBEZEL

alpha-numeric
display bezels

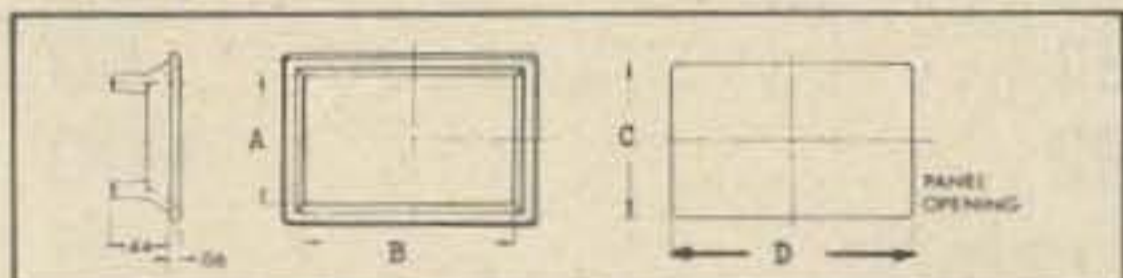


MODEL	DIMENSION				PRICE		
	'A'	'B'	'C'	'D'	1-24	25-99	100-UP
905-XX	.80	1.37	1.172	1.74	\$2.25	2.07	1.91
910-XX	.80	2.00	1.172	2.37	2.30	2.12	1.95
915-XX	.80	3.00	1.172	3.37	2.40	2.21	2.04
920-XX	.80	4.00	1.172	4.37	2.45	2.25	2.08
930-XX	1.38	5.00	1.750	5.37	2.75	2.53	2.33
940-XX	.80	5.58	1.172	5.95	2.65	2.43	2.25
950-XX	1.38	6.50	1.750	6.87	3.15	2.89	2.67

WHEN ORDERING REPLACE XX WITH FILTER COLOR CODE:

NEUTRAL = 15, RED = 60, AMBER = 70, GREEN = 90

example: 930-60 (Model 930 with RED Filter)


DOZY
BOXES

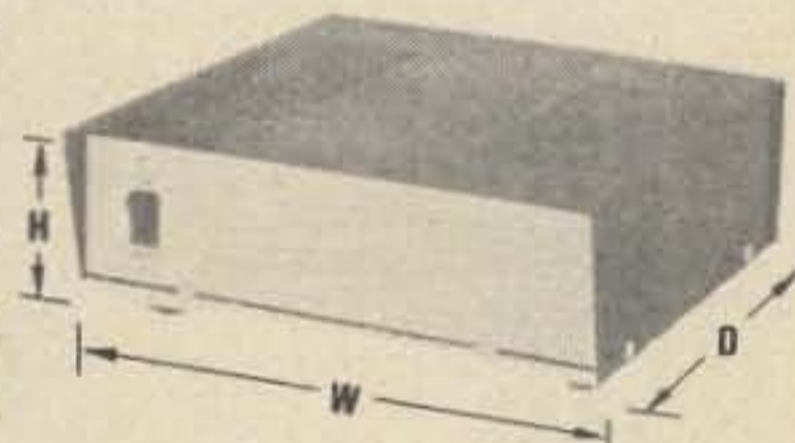

Deluxe Electronic
Equipment Enclosures

MODEL	DIMENSIONS			Screen Vented	RESALE NET
	W	H	DEPTH		
"A"	5 1/2	x 2 1/2	x 3	no	3.75
"B"	5 7/8	x 3 1/2	x 3 1/2	no	4.95
"C"	7 1/2	x 3 1/2	x 5	yes	6.95
"D"	8	x 2 1/2	x 8 (mobile mtg. avail.)	yes	8.75
"E"	6 1/2	x 3 1/2	x 7 1/4	yes	8.25
"F"	7 1/2	x 4 1/2	x 10	yes	9.95
"G"	10 1/4	x 3 1/2	x 9	yes	9.95
"H"	4 1/2	x 8 1/2	x 4	no	8.95
"D1"	Mtg. bracket set for "D"				.36
"H1"	"H" Panel with mounted Wide Vus meter, 3 1/2"				19.95
"HA"	0-1 ma DC & 2 Rocker switches				
"HA"	5 1/8 x 5 1/2 x 4 (Blank Panel)				8.95
"J"	5 x 3 1/2 x 5 3/4 (Sloping Panel)				7.45
"K"	4 3/4 x 7 3/8 x 11 W/handle				13.50
"L"	11 1/8 x 6 1/8 x 12 3/4				20.50
"M"	11 1/8 x 6 1/8 x 16 3/4				21.80

OTHER DISTRIBUTOR LINES:

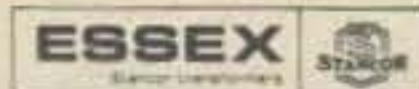

TAB BOOKS J.W. MILLER Co.

LUMINETICS Vector Electronic Company

projects WAHL unlimited

BUD RADIO, INC.

HUNTER TOOLS A Division of Marshall Industries



STEWART-WARNER MICROCIRCUITS DIVISION STEWART-WARNER CORPORATION



KA ELECTRONIC SALES 1312 SLOCUM STREET DALLAS, TEXAS 75207

WRITE FOR FREE CATALOG! (214) 747-3230 747-1662

VISIT OUR STORE MONDAY - FRIDAY 9AM to 5PM, SATURDAY 10AM to 4PM. LOCATED OFF STEMMONS FREEWAY NEAR OAKLAWN.



INTRODUCING: SUPER CRYSTAL —

The New DELUXE DIGITAL SYNTHESIZER from



MFA-22 Dual Version: \$275.00*

- SUPER ★ TRANSMIT and RECEIVE OPERATION — SIMPLEX and REPEATER MODES in both versions.
- SUPER ★ READOUT — DIRECT DIGITAL READOUT — fast acting lever switches.
- SUPER ★ LOW SPURIOUS OUTPUT LEVEL — low spurious output is similar to a crystal output, not spurious laden as with some other units.
- SUPER ★ FAST ACTING CIRCUITS — 0.15 second typical settling time.



MFA-2 Single Version: \$210.00*

- SUPER ★ ACCURATE FREQUENCY CONTROL — .0005% accuracy, both transmit and receive, on all channels.
- SUPER ★ STABLE LOW DRIFT OUTPUT — 20 Hz per degree C typical drift rate.
- SUPER ★ COVERAGE — FULL 2 METER BAND COVERAGE: 144.00 to 147.99 MHz in 10 KHz steps.
- SUPER ★ LOW IMPEDANCE OUTPUTS — 50 ohm output impedance allows long cable runs, both transmit and receive, for trunk or remote units.


SEND FOR FREE DETAILS TODAY

ORDER DIRECT or THROUGH YOUR DEALER

(*Add \$3.00 per unit shipping charge. UPS areas. \$5.00 otherwise. ILLINOIS RESIDENTS add 5% Illinois sales tax.)

TONE BURST ENCODERS AND DECODERS

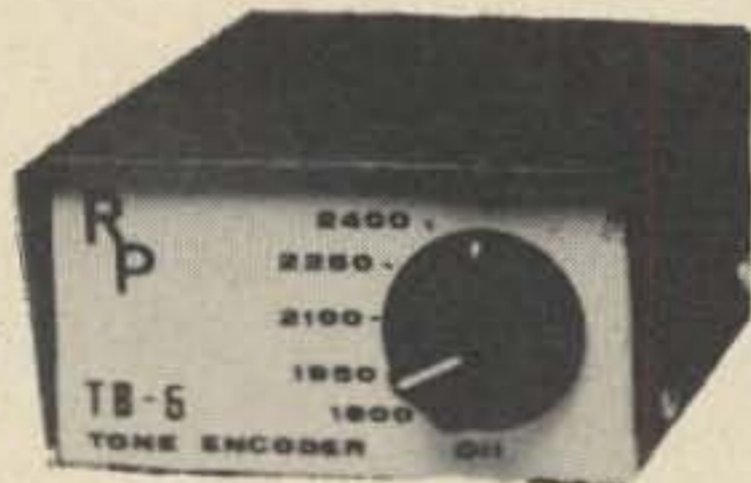- UP to 5 fixed tones (factory set)
- ADJUSTABLE — Duration — Output
- NO BATTERIES needed.
- FULLY ADAPTABLE
- EASY INSTALLATION
- CONTINUOUS TONE POSSIBLE
- FULL 1 YEAR RP Warranty



PRICES:


TB-5 5 tone std. encoder \$37.50
(1800, 1950, 2100, 2250, 2400 Hz.)

ST-2 Single tone decoder \$37.50
(Specify 1800, 1950, 2100, 2250, or 2400 Hz.)


Special tones — Inquire

Add \$1.80/unit for shipping
(Ill. residents add 5% tax)

A SPEECH COMPRESSOR THAT REALLY WORKS

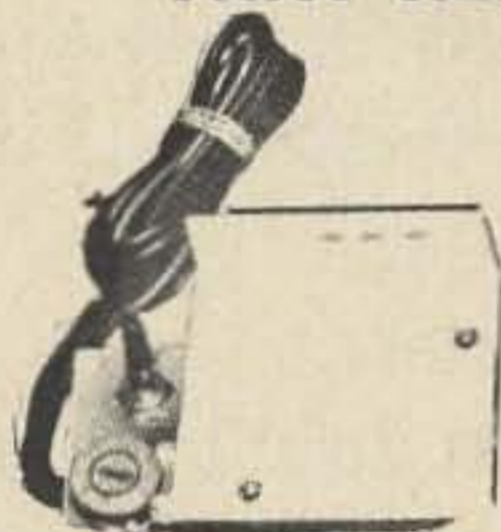

RPC-3,3U Internal Unit
(\$24.95)

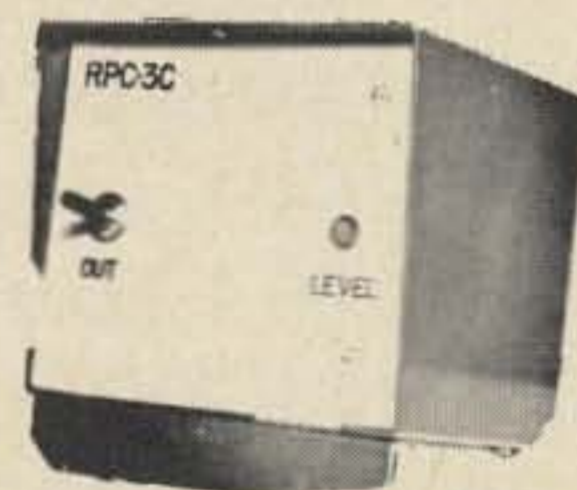

RPC-3C Cabinet Model
(\$34.95)

- Low distortion circuit.
- Fully wired & tested. NOT A KIT
- Works with phone patch.
- Internal units & modules work mobile.



RPC-3M Module
(ONLY \$22.50)

- FULL WARRANTY — ONE YEAR
- INTRODUCTORY LOW PRICES
(Illinois residents add 5% Sales Tax)
Add \$1.00/unit shipping (RPC-3, 3U, 3M)
Add \$2.00/unit shipping (RPC-3C)

RP ELECTRONICS


BOX 1201B
CHAMPAIGN, ILL. 61820

NEW.....

\$49.95

Wired and Tested

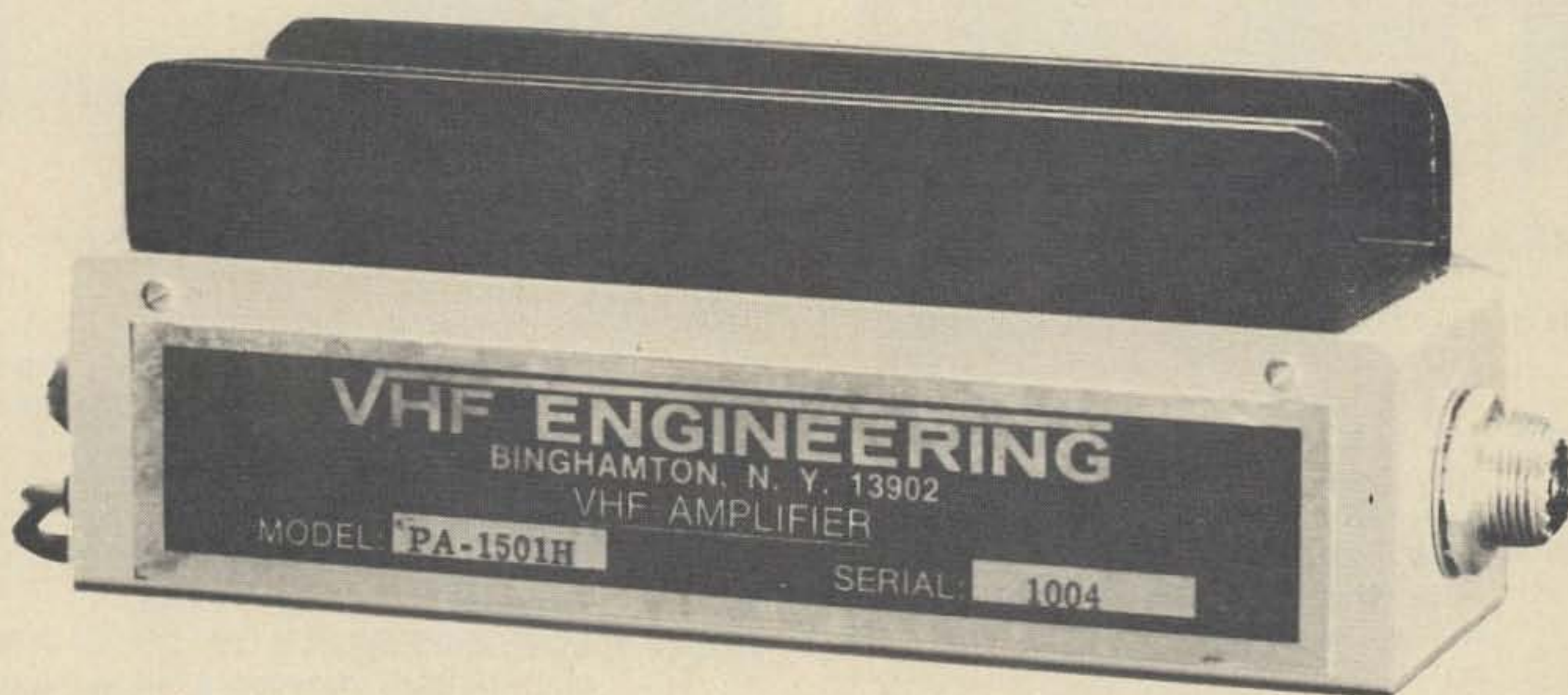- 1-2 WATTS IN
15 WATTS PLUS OUT
- SOLID STATE
SWITCHING
- 12-14 VOLTS
NEGATIVE GROUND
- LESS THAN 1 DB
LOSS ON RECEIVE



PA-1501 H

Only 2" x 2½" x 6½"

\$39.95 complete kit

Also available:

- RX-50C 30-60 MHz receiver kit w/crystal filter \$59.95
- RX-144/220A 2/220 receiver kit 59.95
- RX-144/220F 2/220 receiver kit w/ceramic filter 65.95
- RX-144/220C 2/220 receiver kit w/crystal filter 69.95
- TX-144 1 watt exciter 29.95
- TX-220 1 watt exciter 29.95
- PA-144/220 15 watt amp less cabinet, connectors, and switching . 29.95
- PA-144/220 25 watt amp less cabinet, connectors, and switching . 49.95
- PA-8005H 90 watt amp 5 watts in wired/tested 159.95
- PA-8020H 90 watt amp 25 watts in wired/tested 129.95
- PA-432 10 watt amp less cabinet, connectors, and switching 39.95
- PS-12 12 amp regulated 12-15 volt power supply kit 59.95
- PS-12W Wired/tested 69.95
- PS-24 24 amp same as PS-12 less case 69.95
- COR-1 COR with 3 second and 3 minute timers 19.95

Write for data sheets on any above units. Add postage. NY state residents add sales tax.



VHF ENGINEERING

— DIV. of BROWNIAN ELECT. CORP. —


320 WATER ST. POB 1921 BINGHAMTON, NY 13902 607-723-9574

2 Meter FM Price Reduced

New lower quantity prices on RF power transistors allows us to offer the same quality transmitter for only . . \$29.95 . .

COMPLETE WITH DRILLED BOARD

NOW ONLY
\$29.95

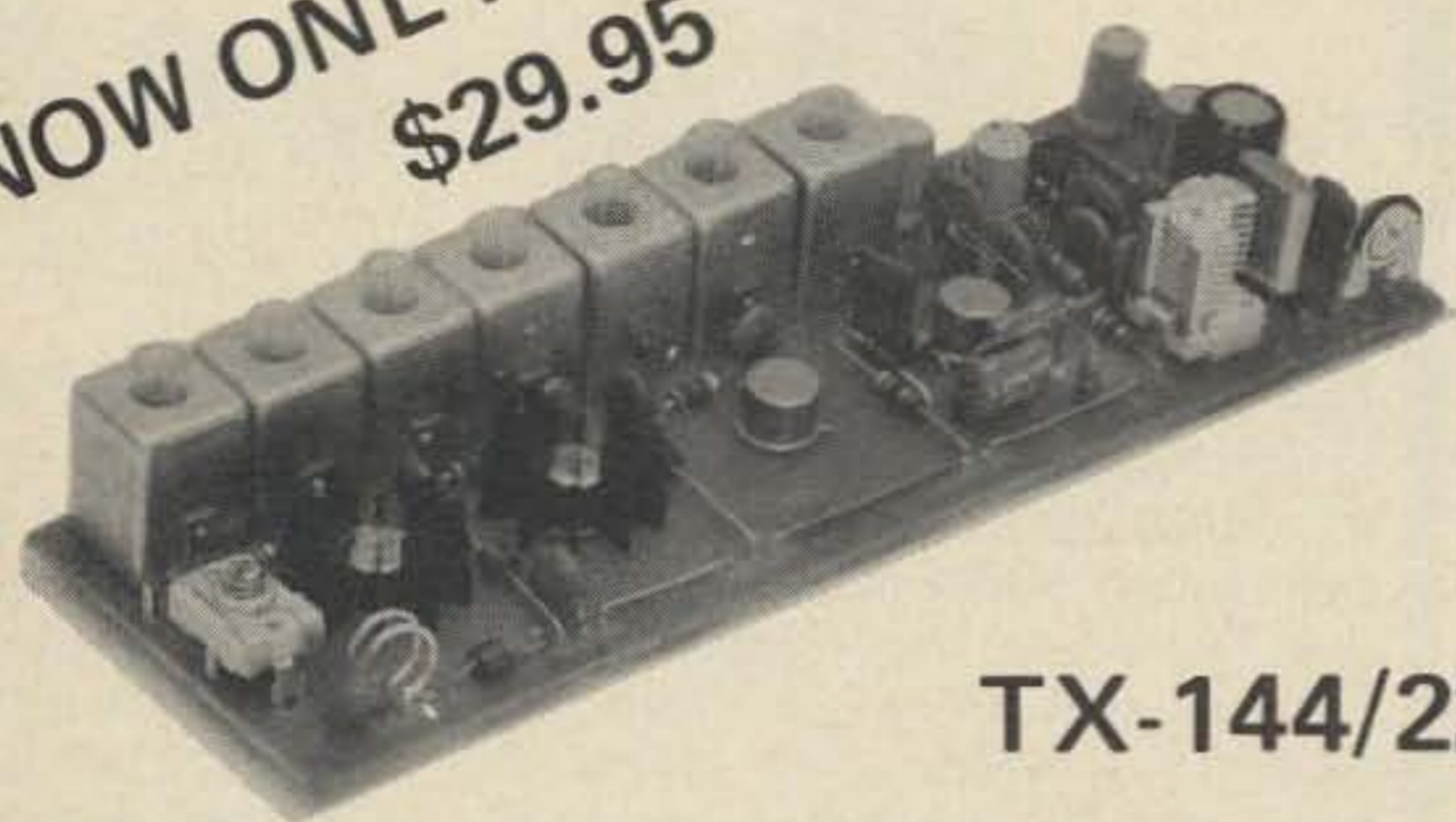


TX-144/220

- TYPICALLY 1 1/2 WATTS OUTPUT AT 12.6 VOLTS (1 WATT ON 220)
- ADJUSTABLE DEVIATIONS TO 10 kHz
- AUDIO CLIPPING AND ACTIVE FILTER
- CRYSTAL NETTING TRIMMER
- DOUBLE TUNED RF STAGES FOR A CLEAN SIGNAL
- STANDARD 12 MHz CRYSTALS (14 MHz FOR 220)
- ZENER REGULATED OSCILLATOR
- PROVISIONS FOR METERING EACH RF STAGE
- PREDRILLED AND TINNED GLASS CIRCUIT BOARDS
- MEASURES ONLY 2" x 6"

A one watt exciter using four RF transistors, two diodes, and one integrated circuit. The RF transistors are operating well below their ratings allowing long keying periods without damage. The exciter may be used alone as a transmitter or with our PA 144 or 220 amplifier for a fifteen watt station.

15 WATT AMP
\$29.95

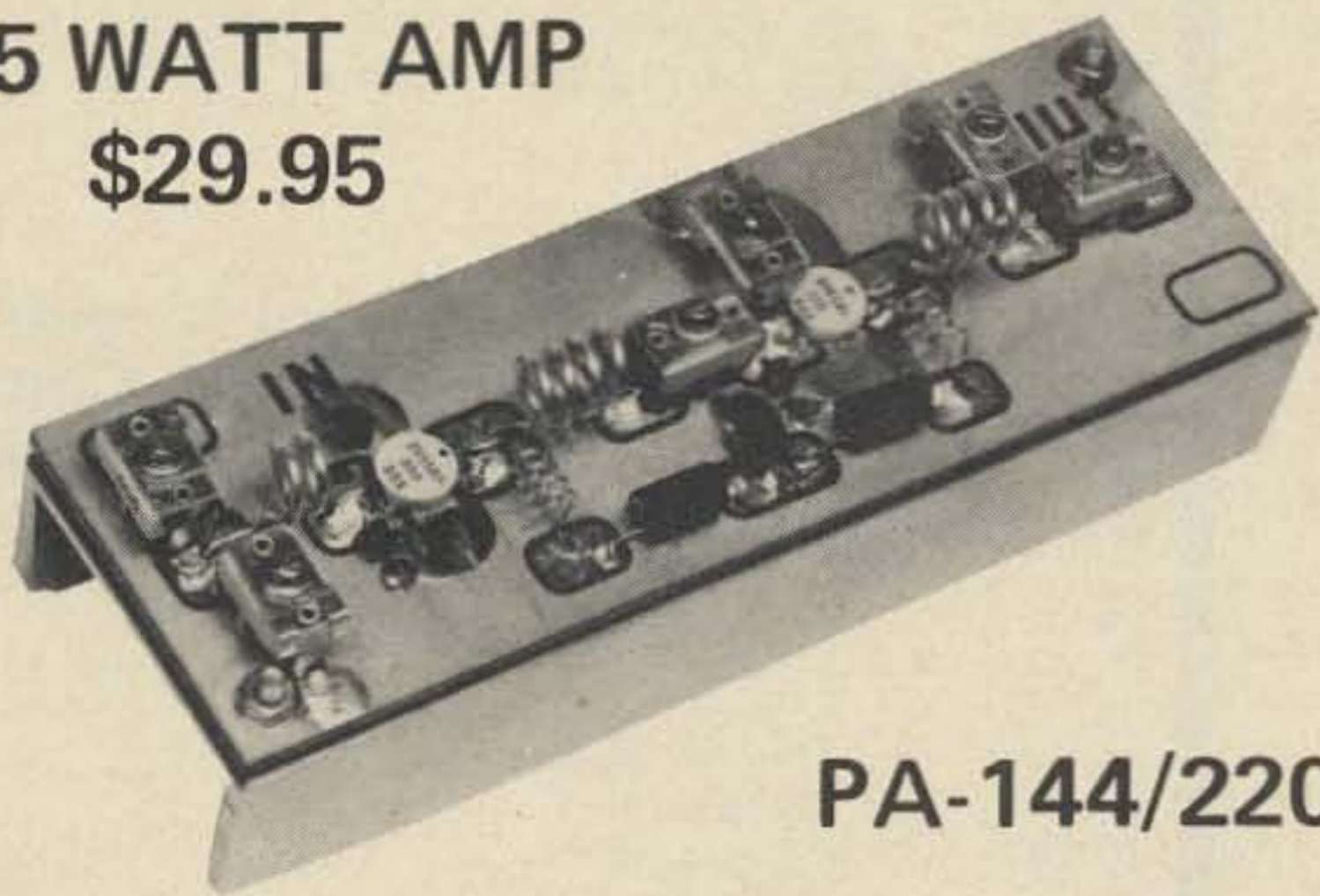

PA-144/220

- 15 TO 20 WATTS OUTPUT WITH 1 1/2 TO 2 WATTS DRIVE. (SLIGHTLY LESS ON 220)
- USES TWO BALANCE EMITTER RF POWER TRANSISTORS ABLE TO WITHSTAND A HIGH SWR.
- TYPICALLY DRAWS 3 AMPS FROM A 12 TO 14 VOLT NEGATIVE GROUND SUPPLY.
- COMPLETE WITH CIRCUIT BOARD AND ALUMINUM HEAT SINK.
- ADD YOUR OWN MINIBOX AND RELAY AND SAVE.

COMPLETELY PACKAGED PA144/220 AMP JUST \$49.95 with solid state switching. 1-2 watts in gets you 15++ watts out. Size 6 1/2 X 2 5/8 X 2 with PL-259 in and out.

Order TX-144 or TX-220, \$39.95 PA-144 or PA-220, \$29.95. Add 1.00 postage and handling for each kit ordered. New York State residents add sales tax.



VHF ENGINEERING

320 Water Street POB 1921
BINGHAMTON, NEW YORK 13902

the tempo line

...a reputation built on quality and value

IN LESS THAN THREE YEARS THE TEMPO LINE HAS ESTABLISHED A SOLID REPUTATION FOR FIRST RATE PERFORMANCE AT A REASONABLE PRICE. WHETHER YOUR INTERESTS LIE IN HIGH FREQUENCY SSB OR VHF/UHF FM, TEMPO DESERVES YOUR SERIOUS CONSIDERATION. YOU WILL NEVER BE SORRY.



THE TEMPO ONE SSB TRANSCEIVER

Look at the specifications . . . look at the price tag . . . ask any of the thousands of Tempo ONE owners about its reliability . . . and the reason for its unparalleled popularity will be obvious. The Tempo ONE is now the proven ONE.

FREQUENCY RANGE: All amateur bands 80 through 10 meters, in five 500 khz. ranges: 3.5-4 mhz., 7-7.5 mhz., 14-14.5 mhz., 21-21.5 mhz., 28.5-29 mhz. (Crystals optionally available for ranges 28-28.5, 29-29.5, 29.5-30 mhz.)

SOLID STATE VFO: Very stable Colpitts circuit with transistor buffer provides linear tuning over the range 5-5.5 mhz. A passband filter at output is tuned to pass the 5-5.5 mhz. range.

RECEIVER OFFSET TUNING (CLARIFIER): Provides ± 5 khz. variation of receiver tuning when switched ON.

DIAL CALIBRATION: Vernier scale marked with one kilohertz divisions. Main tuning dial calibrated 0-500 with 50 khz. points.

FREQUENCY STABILITY: Less than 100 cycles after warm-up, and less than 100 cycles for plus or minus 10% line voltage change.

MODES OF OPERATION: SSB upper and lower sideband, CW and AM.

INPUT POWER: 300 watts PEP, 240 watts CW

ANTENNA IMPEDANCE: 50-75 ohms

CARRIER SUPPRESSION: -40 dB or better

SIDE BAND SUPPRESSION: -50 dB at 1000 CPS

THIRD ORDER INTERMODULATION PRODUCTS: -30 dB (PEP)

AF BANDWIDTH: 300-2700 cps

RECEIVER SENSITIVITY: $\frac{1}{2} \mu\text{v}$ input S/N 10 dB

AGC: Fast attack slow decay for SSB and CW.

SELECTIVITY: 2.3 khz. (-6 dB), 4 khz. (-60 dB)

IMAGE REJECTION: More than 50 dB.

AUDIO OUTPUT: 1 watt at 10% distortion.

AUDIO OUTPUT IMPEDANCE: 8 ohms and 600 ohms

POWER SUPPLY: Separate AC or DC required. See AC "ONE" and DC1-A.

TUBES AND SEMICONDUCTORS: 16 tubes, 15 diodes, 7 transistors

TEMPO "ONE" TRANSCEIVER \$349.00

AC/ONE POWER SUPPLY 117/230 volt 50/60 cycle \$ 99.00

DC/1-A POWER SUPPLY 12 volts DC \$110.00

VF-ONE EXTERNAL VFO \$ 99.00



THE TEMPO 2001

LINEAR AMPLIFIER

Small but powerful, reliable but inexpensive, this amplifier is another top value from Henry Radio. Using two 8874 grounded grid triodes from Eimac, the Tempo 2001 offers a full 2 KW PEP input for SSB operation in an unbelievably compact package (total volume is .8 cu. ft.). The 2001 has a built-in solid state power supply, a built-in antenna relay, and built-in quality to match much more expensive amplifiers. This equipment is totally compatible with the Tempo One as well as most other amateur transceivers. Completely wired and ready for operation, the 2001 includes an internal blower, a relative RF power indicator, and full amateur band coverage from 80-10 meters. PRICE: \$545.00

YAESU

... a name proven through world-wide use.
... now available at Henry Radio. Come in,
phone or write for complete specifications.
We ship almost everywhere.

FT-101	Transceiver	649.00
FTdx-401	Transceiver	599.00
FL-2100	Linear Amp with tubes	339.00
YC-355D	Digital Counter	289.00
FV-101	External VFO	99.00
SP-101P	Speaker/patch	59.00
SP-101	Speaker	19.00
FV-401	External VFO	99.00
SP-401P	Speaker/patch	59.00
SP-401	Speaker	19.00
YD-844	Dynamic microphone	29.00
XF-3C/30C	C.W. filter	40.00
FA-9	Fan	19.00
MMB-1	Mobile bracket	9.00


Prices subject to change without notice.

Henry Radio


11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701
931 N. Euclid, Anaheim, Calif. 92801 714/772-9200
Butler, Missouri 64730 816/679-3127

GAM has what your repeater needs


8.2 dB GAIN OVER ISOTROPIC

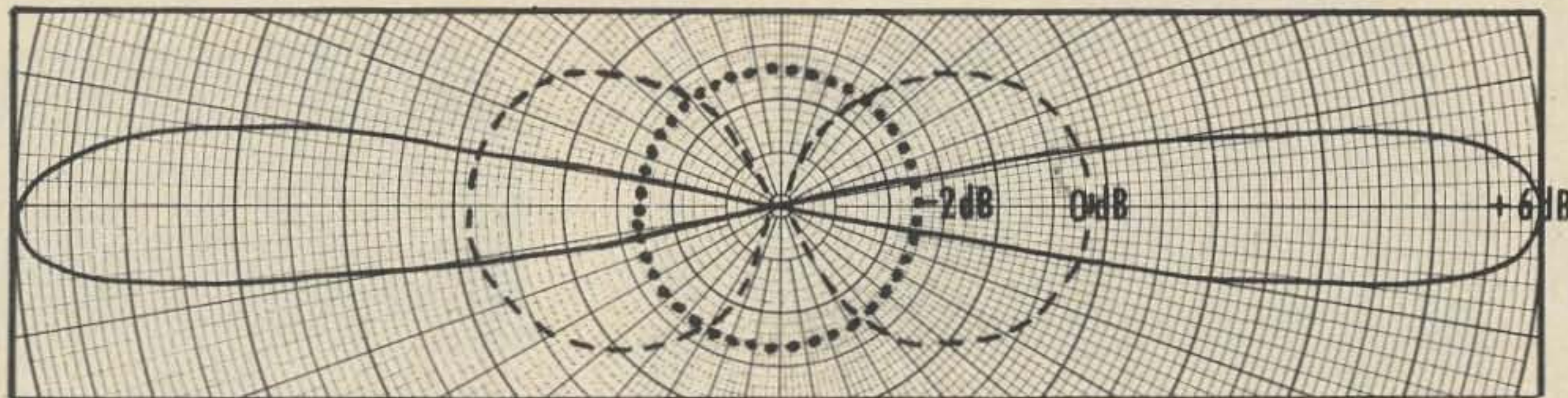

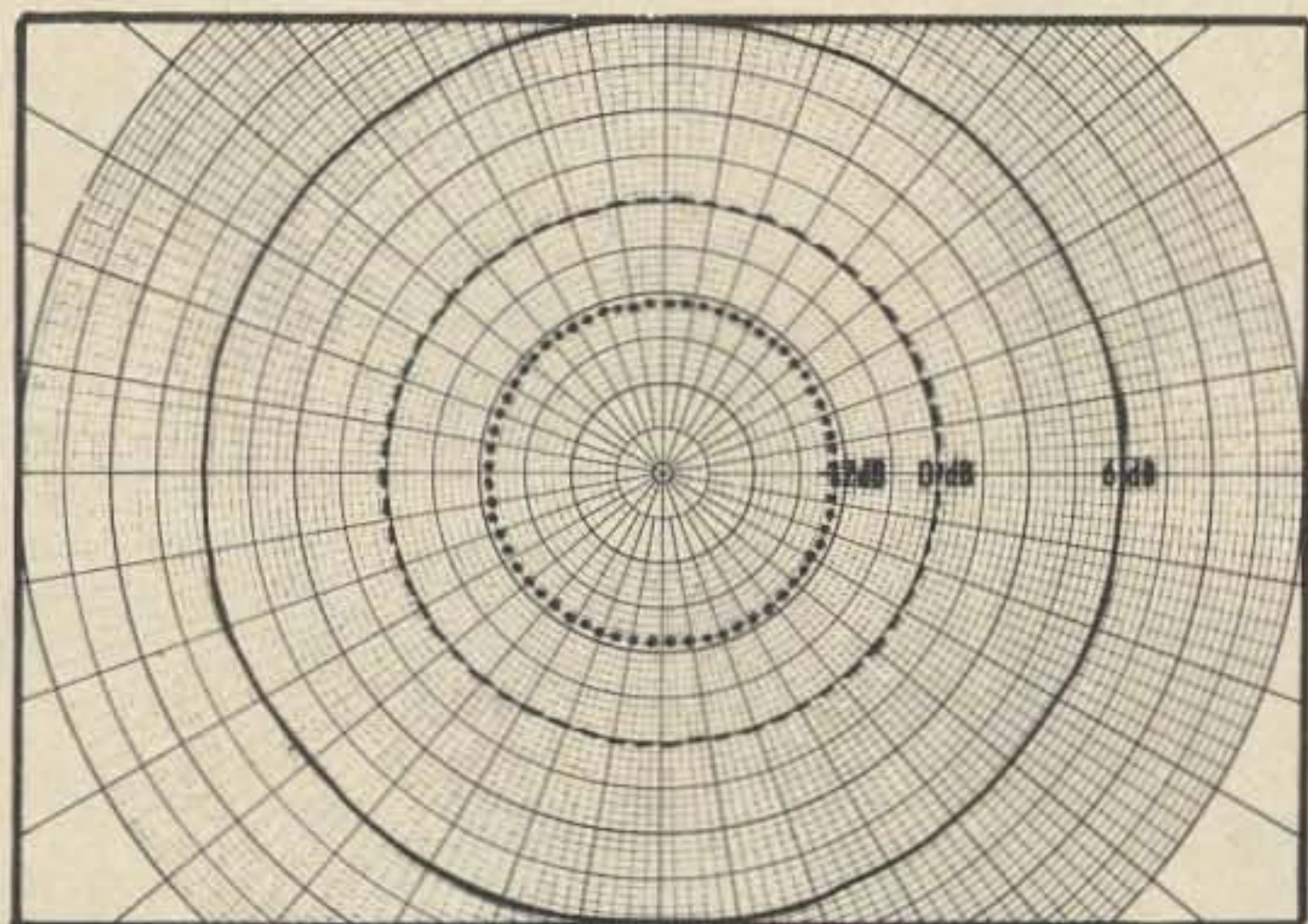Vertical Radiation Pattern — TG5-S
 --- Dipole
 Isotropic



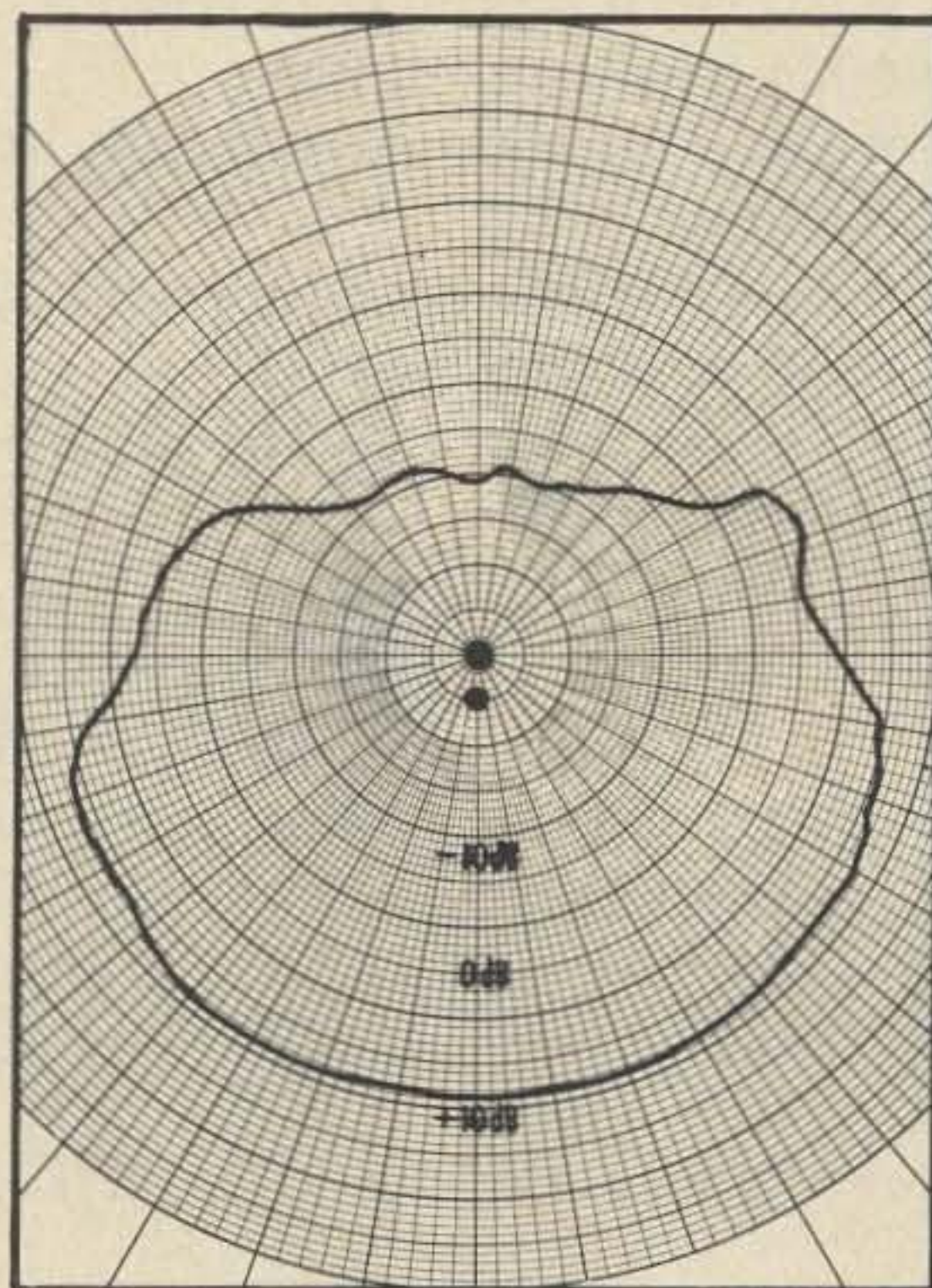Horizontal Radiation Pattern — TG5-S
 --- Dipole
 Isotropic



Offset Side Mount Radiation Pattern
 Reference: Dipole

(ON FILE WITH FCC)

MODEL TG5-S
\$104⁵⁰ LIST PRICE

Weight 3½ lbs.

GAM
Electronics

191 VARNEY STREET
 MANCHESTER NH 03102
 TEL. (603) 627-1010

A&W

YOUR HAM & PARTS HEADQUARTERS

hallicrafters FPM 300



- AC-DC power supply, built-in
- Modular construction
- Glass epoxy printed circuit board construction
- Latest solid state devices throughout
- All American-made
- Unique integrated circuit speech compressor

\$595

\$50.00 worth of other equipment FREE when you buy an FPM-300 at \$595.

hy-gain GALAXY GT 550A




- Crystals supplied for 3.5 to 4.0, 7.0 to 7.5, 14.0 to 14.5, 21.0 to 21.5, 28.0 to 29.0 MHz. Optional xtals may be installed for other 10 meter coverage.
- Plate Power Input: 550 watts PEP on SSB - 360 watts on CW and RTTY (50% duty cycle).
- Power Output: 300 watts PEP (nominal) on SSB - 180 watts on CW and RTTY.
- Receiver Selectivity: 2.1 kHz with 1.8 shape factor for SSB or 300 Hz sharp selectivity with optional CW filter.
- Freq. Stability: Within 10 Hz during any 30 minute warm-up period, less than 100 Hz in any 15 minute warm-up period, not more than 100 Hz with a plus or minus 10% line voltage variation.

\$595


Power Supply
\$99.95

\$50.00 worth of other equipment FREE when you buy a GT 550 A at \$595.

If you need antennas, we have them . . .

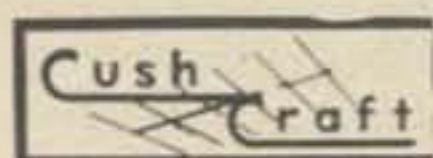

ROHN.

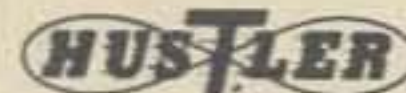

Shakespeare

ascm
TOWERS



the antenna
specialists co.

ALL 73 and ARRL PUBLICATIONS ALWAYS IN STOCK

500,000 electronic parts always in stock — SYLVANIA, ECG, WORKMAN, G.C., CALECTRO, JFD, RMS, PANASONIC, PIONEER, MARANTZ, SHARP and many many more ! !

A&W FM VHF UHF A&W

Clegg

FM27B

\$479.00



FM-21 220 MC \$299.00

We stock Hy-Gain,
Antenna Specialists, Hustler,
CushCraft and Shakespeare.

All 2 meter xtals
in stock . . . Bomar 3.95

We also stock VHF
and UHF amplifiers
TPL, Dy-Comm, Standard

with each Regency rig you purchase. . . you receive 4 FREE CRYSTALS of your choice!

Regency

HR-2B NEW

12 ch xmt-rcv
15W min

\$229.00

HR-220 NEW

12 ch 20W 220 MC

\$239.00

AR-2

80W 2 meter amp.

\$100.00

EC-175

175 MC counter

\$400.00

HR-6

6 meter 25W

\$239.00

HR-212

12 ch 20 watt

\$259.00

SBE

SB-144

12 ch 10 W

\$259.00

SB-450

12 ch 10W

450 MC

\$399.00

**Standard
Communications**

146A

2 meter walkie

\$289.00

SR815TH

25W 12 ch

\$589.00

826MA

12 ch 10 watts

\$398.00

SCARPT-1A

2 meter RPT

\$690.00

SRC14

24 ch 10 watt

base unit

\$598.00

SEND FOR OUR CATALOG WITH SPECIAL PRICES

A&W ELECTRONICS

491 Riverside, Medford, Mass. 02155
(617-396-5550)

PRC 9 Back Pack Walkie Talkie, FM 27 to 39 MC with Antenna and Battery Case, good for camping, hunting, etc. 2 for \$49.50
 each \$27.50

5 LEVEL TELEPRINTER TAPE READER WESTERN UNION MODEL 8C, 5 level tape reader.



Magnet tape advance good for high speeds. Excellent for use with Electronic.

Parallel-to-serial converter (Transmitting Dist.) \$7.95

TONE DIALS SIMILAR TO TOUCH TONE DIAL



but manufactured by AUTOMATIC ELECTRIC overhauled & checked out \$12.50
 in as is condition 4.95

(torroids can be used to build tone decoders) with data sheets.

TS 1060 TELETYPE DISTORTION TEST SET



Compact 3" Scope Indicator 110V 60 cy
 Power 6"x8"x14" \$14.95

MISCELLANEOUS

Linemen Belts, complete with safety strap \$9.95
 Pole Climbers, complete with leather pad and straps \$4.95

Cradle Telephone, with dial \$7.50
 with multiple stations \$9.95

TA-1, sound power unit, compact hand held. Just hook up wire and use. With built in generator for ringing. No batteries needed \$14.95 a pair
 \$7.95 each

SPECIAL - ARC-5 Q'5er \$7.95

TA-182 - Converter, Telegraph & Telephone signal conv. housed in a waterproof, metal case 12" x 7" x 6". Wt. - about 10 lbs. Complete with 110 V, 60 cy. power supply, (some hams have converted this unit to a teletype converter). With schematic. **Only \$4.95**


TERMS: remittance in full or 25% deposit on COD orders. Minimum order \$5.00 FOB LA, Calif.

OS-SE/S Oscilloscope This is the "E" model of this series which is a later version, portable 3" scope. Size 6"x8"x14" AC supply, 2 MC wide with carrying case. Wt. 12 lbs. \$39.50



APN 9 LORAN RECEIVER INDICATOR For boats & aircraft used to get your position on water, air or land - consists of receiver in the marine band also has 3" CR tube to show incoming signal. Complete with crystal \$24.50

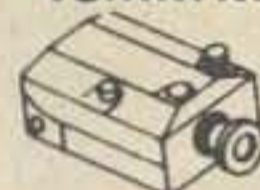16MM MOVIE CAMERA complete with F 3.5 lens.



magazine load type
 Motor driven only \$7.95

We Specialize in Telephone and Teletype Equipment. Please Write Us Your Needs.

Muffin Fans \$4.95
 24 Volt Power Supply, at 30 Amps. regulated rack mount \$37.50

Bodine Gear Reduction Motor, 10 rpm, 180:1 ratio. Torque 7.0 inch lbs. .6 Amp cont.duty 115 volts, 60 cy. \$4.95

Model 15 Teletype RO, Sync motor, good condition \$35.00

GRC EQUIPMENT

RT 66 FM transceiver, 20 to 28 MC \$27.50
 RT 67 FM transceiver, 27 to 39 MC 39.50
 RT 68 FM Transceiver, 38 to 54 MC 49.50
 R109 FM Receiver, 27 to 39 MC 27.50
 GR 758A Wavemeter 55-400 MHz, new \$9.95
 HP 212A Pulse Gen. (rack mtd.) 34.95
 HP 524D Counter (main frame) 229.50
 HP 522B counter 10 Hz to 12 kHz 107.50
 HP 540A Transf. Oscillator 149.50
 HP 624B "X" Band Test Set 199.50
 HP 686A Sweep Generator 189.50
 HP 803A VHF Bridge 79.50
 GR 716C Capacitance Bridge 127.50
 Gertsch FM-3 Freq. Meter, 20 MHz to 640 MHz 69.50

J. J. GLASS ELECTRONICS CO.

1624 South Main Street
 Los Angeles, CA 90015
 213-749-1179 213-749-1170


STUD 'TRIACS'



PRV 15 amp	25 amp
50 \$.65	\$.85
100 .85	1.05
200 1.25	1.45
300 1.45	1.65
400 1.85	1.95
500 2.55	2.25
600 —	2.65

"AEROSPACE" BABCOCK & LEACH CRYSTAL CAN RELAYS

12 for \$3.50

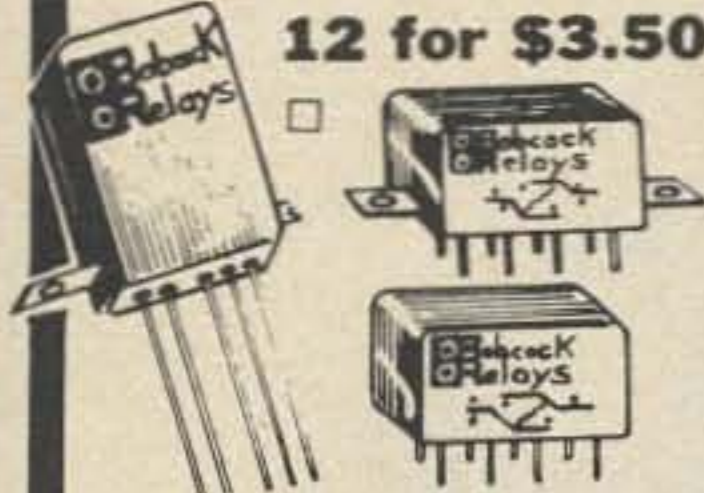

All hermetically sealed. Submini, 1/6, half, and full crystal can types in 6-12-24V in asst contacts up to 4PDT, 1 amp up to 10 amps. Such types as BR40, 41, 10, 44, 16, 24, etc. Sorry, no choosing voltages or types. From factory mixtures . . . to you! Good asst, if you are space-minded, at low prices.

SILICON TUBES

5U4	\$1.49
5R4	3.95
866	7.95

'HAM' UHF 400 MC HIGH POWER TRANSISTORS

3 for \$10. **\$3.95**


By RCA or equal 2N3632. NPN, 23 watts, 3 amps, TO-60 case, with stud mtg. VCEV max 65.

GI "GLASS AMP II" SPACE AGE FEATURE



Type	PIV	Sale
1N4245	200	\$.14
1N4246	400	.22
1N4247	600	.39
1N4248	800	.49
1N4249	1000	.59

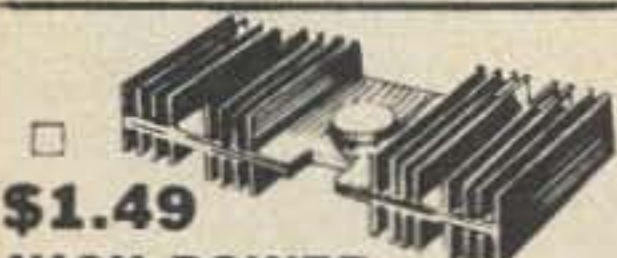
Meets critical JAN specs. A glass "ball of silicon strength" that meets JAN specs, high reliability, withstands avalanche power surges to 1K watts. ONE amp ratings with 2 amp capabilities. Axial leads.



\$1.49 HIGH POWER TRANSISTOR 3 for \$3 WITH HEAT SINK

Removed from new equipment! Includes popular 2N174 'doorknob' transistor TO-36, germanium, PNP, 150 watts, VCBO 80V, 15 amps, 40 hfe. For ignition, high power transmitters, etc. Mounted on heat sink 5 x 2 1/2 x 1 1/4".

Buy Any 3 — Take 10% Discount!

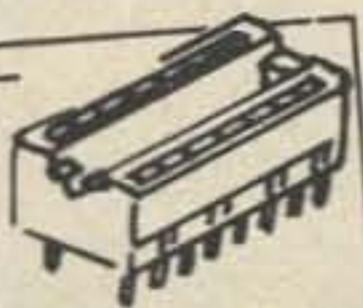

INTEGRATED CIRCUIT SOCKETS

14-Pin, DIP	\$.45
14-Pin, Wire Wrap	.59
14-Pin, Side Mount	1.00
16-Pin, DIP	.50
16-Pin, Wire Wrap	.59
TO-5, 8 or 10-Pins	.29

KRONOS WITH "TIME BASE"*



Cabinet is compact 6" x 5 1/2" x 6".

CHOOSE YOUR READOUT

Type	LED	Charac.	Sale
KR-101	MAN-3	.12	\$47.
KR-102	MAN-1	.27	47.
KR-103	MAN-4	.19	47.
KR-104	Nixie*	.45	47.
KR-105	707†	.33	47.
KR-106	704†	.33	47.
KR-107	SLA-1†	.33	47.
KR-108	Same as SLA-1 but GREEN, add \$12.		

† "MAN" LED readouts are "all LEDs" but the Litronix 707 and Opcoa SLA-1, like the MAN-1, are of the reflective bar segment technique, the 704 is the reflective bar version of the MAN-4. *The Nixie tube is a 7-segment device as others.

- Now two clocks in one!
- For 12VDC* and 110VAC!
- Now adaptable to boats, planes & cars too!
- The only clock of its kind in USA today!
- 12 or 24-hr clock, 6-digits!

\$47. Any Type Clock less time-base

NEW FOR 1974!

* With TIME BASE \$64.95

Scientific Devices introduces the new any LED Kronos digital clock. That's right, you can choose the "ALL-LED" Man-1, Man-3, and Man-4, and the new reflective bar types with the larger digits, at only one price, \$47. This is a Scientific Device first! We even have the GREEN LED readouts at a slightly extra cost. We have more . . . for \$19.95 we have available as an (*) extra option to Naval Observatory your clock, or making it an all-purpose all-duty unit. For indoor and outdoor activity. This "TIME BASE" is the simplest on the market today with the help of one of the largest time base manufacturers for the famous digital wrist watches. Therefore, current drain is negligible, not like other cumbersome types. It's easy to construct, easy to slip into the Kronos of your choice and connect with easy instructions. Its overall design is simple and easy to construct. The kit is complete with famous black-and-white TEN-TEC cabinet, plus all accessories with booklets. Features include 3 setting controls, 1-hour per second, 1-minute per second, and hold button.

CRYSTAL TIME BASE \$19.95 FOR ANY KRONOS

Includes precision crystal, time-base IC, pc board & accessories with info.

Scientific Device exclusive!

Lowest Prices Largest Selection TTL IC's

Brand New	"DIP" Packages	Order by type number! Spec sheets on request "ONLY"					
Type	Sale						
SN7400	\$0.30	SN7470	.45	SN74104	.55	SN74161	1.65
SN7401	.30	SN7430	.30	SN74105	.55	SN74162	1.95
SN7402	.30	SN7432	.30	SN74106	1.25	SN74163	1.95
SN7403	.30	SN7437	.60	SN74107	.70	SN74164	3.50
SN7404	.35	SN7438	.60	SN74108	1.25	SN74165	3.50
SN7405	.32	SN7440	.30	SN74112	1.25	SN74166	2.05
SN7406	.55	SN7441	1.40	SN74113	1.25	SN74174	2.10
SN7407	.55	SN7442	1.25	SN74114	1.25	SN74175	2.10
SN7408	.35	SN7443	1.50	SN74121	.80	SN74176	2.10
SN7409	.35	SN7444	1.50	SN74122	.85	SN74177	2.10
SN7410	.30	SN7445	1.50	SN74123	1.20	SN74179	2.10
SN7411	.35	SN7446	1.65	SN74139	1.50	SN74180	1.20
SN7413	.95	SN7447	1.50	SN74140	.50	SN74181	4.50
SN7415	.55	SN7448	1.50	SN74145	1.40	SN74182	1.20
SN7416	.55	SN7450	.35	SN74148	4.50	SN74192	1.95
SN7417	.55	SN7451	.35	SN74151	1.25	SN74193	1.95
SN7420	.30	SN7453	.35	SN74153	1.60	SN74194	1.95
SN7421	.35	SN7454	.50	SN74154	1.95	SN74195	1.35
SN7422	.35	SN7460	.35	SN74156	1.42	SN74196	1.50
SN7425	.30	SN7461	.35	SN74157	1.55	SN74197	2.10
SN7426	.37	SN7462	.35	SN74158	1.55	SN74199	2.65
		SN7464	.50	SN74160	1.95		
		SN7465	.50				

• Factory Marked

* Money Back Guarantee

Buy 100 — Take 20%

LINEAR Op Amps

• FACTORY GUARANTEED

• FACTORY MARKED

Buy Any 3 — Take 10% Off!

531	Hi slew rate op-amp (TO-5)	\$2.50
532	Micro power 741 (TO-5)	2.50
533	Micro power 709 (TO-5)	2.50
536	FET input op amp (TO-5)	3.95
537	Precision 741 (TO-5)	2.50
550	Precision 723 voltage reg. (DIP)	1.17
556	5 Times faster than 741C	2.10
560	Phase lock loops (DIP)	3.25
561	Phase lock loops (DIP)	3.25
562	Phase lock loops (DIP)	3.25
565	Phase lock loops (A)	3.25
566	Function generator (A)	3.25
567	Tone generator (A)	3.25
595	Four quadrant multiplier	3.10
702C	Hi-grain, DC amp (TO-5)	.49
703C	RF-IF, amp, 14 ckts (TO-5)	1.00
704	TV sound IF system	1.50
709C	Operational amp (A)	.49
709CV	Op amp (mini DIP)	.49
710C	Differential amp (A)	.49
711C	Dual diff. comp (A)	.49
723C	Voltage regulator (A)	.95
733	Diff. Video Amp	1.75
741C	Frequency compensator 709 (A)	.49
747C	Dual 741C (A)	1.25
748C	Freq. adj. 741C (A)	.49
748CV	Freq. adj. 741C (mini DIP)	.49
753	Gain Block	1.75
709-709	Dual 709C (DIP)	1.00
739-739	Dual stereo preamp	1.98
741-741	Dual 741C (A)	1.00
75150	Dual peripheral driver	.88
75154	Dual peripheral driver	.88
745512	Dual line driver	.39
PA265	5-Watt voltage regulator	1.95
ULN2300M	Op amp with SCR	1.50
CA3065	Video Audio system	1.50

Buy 3 or more 10% discount

NATIONAL 'OP' AMPS

BUY ANY 3 — TAKE 10%

Type	Description	Sale
LM-300	Super 723 V. reg.	\$1.49
LM-301	Hi-performance amp	.49
LM-302	Voltage follower	1.49
LM-304	Neg. V. reg.	1.49
LM-305	Pos. V. reg.	1.49
LM-307	Super 741	.59
LM-308	Hi-Q Fat Type Op Amp	1.50
LM-309H	5V 200 mil V. reg.	1.50
LM-309K	5V 1-amp V. reg.*	2.25
LM-311	Comparator	1.50
LM-320	Minus 5V 1-amp V.R.*	1.95
LM-320	Minus 12V 1-amp V.R.*	1.95
LM-320	Minus 15V 1-amp V.R.*	1.95
LM-350	Dual peripheral driver	.59
LM-370	AGC squelch op amp	1.49
LM-371	R-F, I-F, op amp	.69
LM-373	AM-FM, SSB, I.A.D.	3.75
LM-374	AM-FM, SSB, IVAD	3.75
LM-380	2-watt audio amplifier	1.95
LM-3028	Differential RF/IF amp	1.50
LM-3070	Chrome regenerator	1.50
LM-3071	TV chroma IF amp	1.50

*TO-3 case, — others TO-5

1" SQ MINI METERS



* Plastic case
* Red needle indicators **\$1.49**
Balancing, stereo, tape, amps. 3 for \$3.75
VU, side mtg, plus 3 minus 20 db.
VU, front mtg, plus 3 minus 20 db.




HIGH VOLT 1AMP	4000	1.65
PIV SALE	5000	2.25
2000*	6000	2.96
3000	8000	3.50
	10000	3.95

15¢ CATALOG on Fiber Optics, 'IC's', Semi's. Parts

POLY PAKS

P.O. BOX 942A LYNNFIELD, MASS. 01940

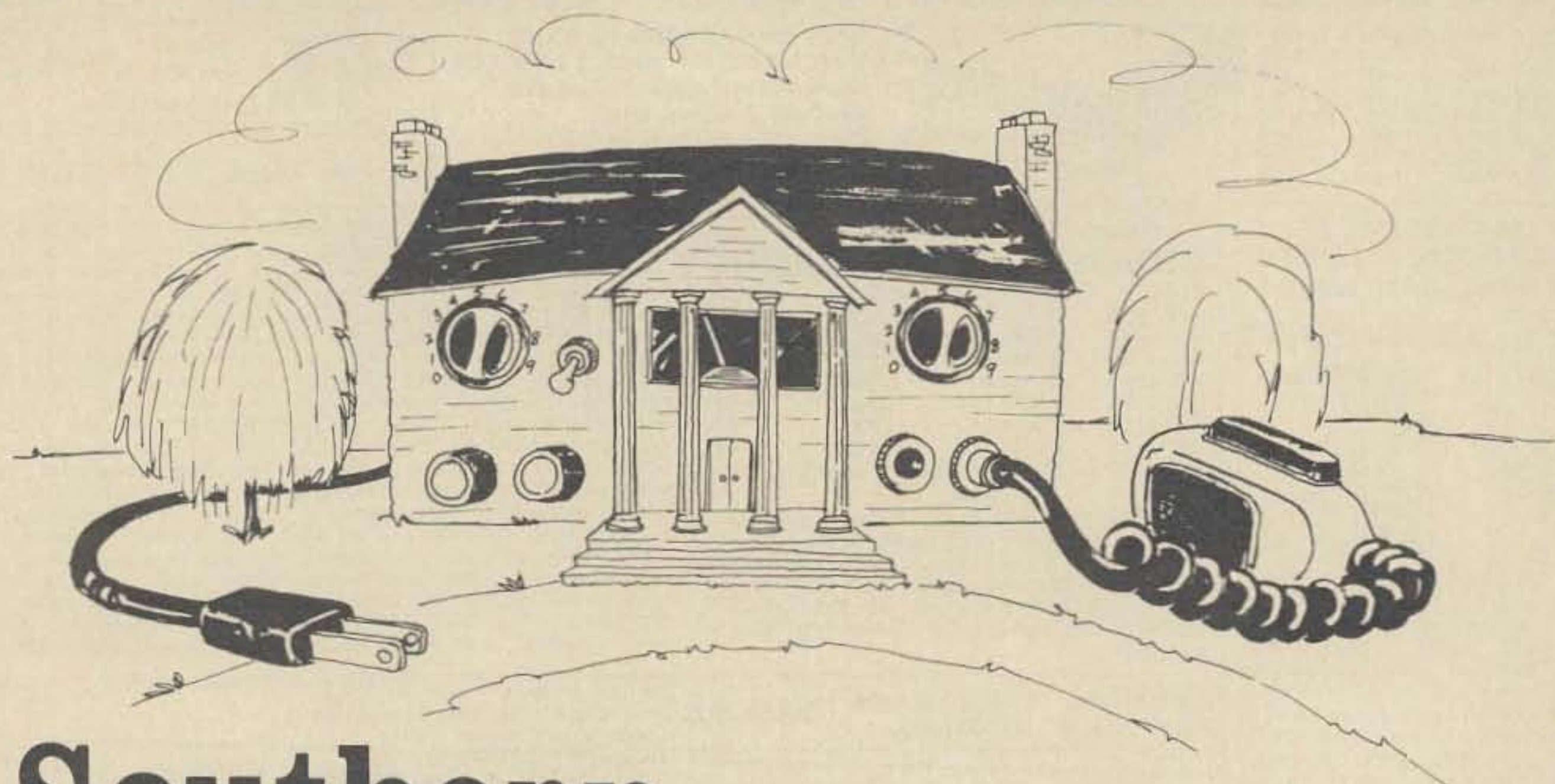Terms: add postage Rated: net 30
Phone Orders: Wakefield, Mass. (617) 245-3829
Retail: 16-18 Del Carmine St., Wakefield, Mass. (off Water Street) C.O.D.'S MAY BE PHONED



Southern Hospitality

For hundreds of years, the South has been famous for its hospitality and friendliness. Rex Johnson offers you the finest in new and used gear, along with service and follow thru in the true tradition of the South.

E - X - T - E - N - D - E - D "SOUTHERN HOSPITALITY" featured this month:

HR 2B \$229.00


Regency



146A \$289.00



HR 212 \$259.00

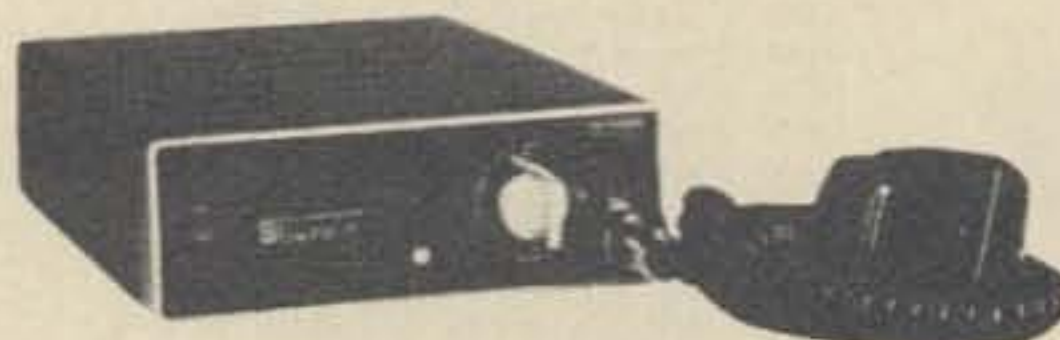

826MA \$398.00

STANDARD

Write us for our Free Used Equipment List and trade-in quote on all Major lines. Remember, the Southern tradition of friendliness and hospitality is alive and well at Johnson Electronic Sales.

1360 MERIWEATHER ST. (404) 228-3831
GRIFFIN, GEORGIA 30223

**JOHNSON
ELECTRONIC
SALES**

7 SEGMENT LED Readouts

All fit 14-pin IC sockets, 5V 10 to 20 mils, 0-to-9 numerals, plus letters & decimal. With spec sheets.
 *Monsanto Equal, MAN-1
 **MAN-1 Specs.
 †35-Diode Array.



MONSANTO "ALL LED" Type	Size	Color Display	Decimal	Driver	Each	Special
<input type="checkbox"/> MONSANTO MAN-1*	.27	Red	Yes	SN7447	4.50	3 for \$12.
<input type="checkbox"/> MONSANTO MAN-3*	.115	Red	Yes	SN7448	2.25	3 for \$6.
<input type="checkbox"/> MONSANTO MAN-3*	.115	Red	No	SN7448	1.49	3 for \$3.
<input type="checkbox"/> MONSANTO MAN-4*	.190	Red	Yes	SN7448	2.95	3 for \$8.
<input type="checkbox"/> MONSANTO MAN-4*	.190	Red	No	SN7448	1.79	3 for \$5.

"REFLECTIVE LITE BAR" (SEGMENT) LED READOUTS! **** Decimal right or left						
<input type="checkbox"/> LITRONIX 707** (MAN-1)	.33	Red	Yes	SN7447	3.50	3 for \$9.
<input type="checkbox"/> LITRONIX 704*** (MAN-4)	.33	Red	Yes	SN7448	3.50	3 for \$9.
<input type="checkbox"/> OPCOA SLA-1** (MAN-1)	.33	Red	Yes	SN7447	3.50	3 for \$9.
<input type="checkbox"/> OPCOA SLA-3H Giant Digit	.70	Red	Yes	SN7447	8.60	3 for \$24.
<input type="checkbox"/> OPCOA SLA-2 Plus/Minus/1	.33	Red	No	SN7447	3.50	3 for \$9.
<input type="checkbox"/> OPCOA SLA-11C (MAN-5)	.33	Green	****	SN7447	4.95	3 for \$13.
<input type="checkbox"/> OPCOA SLA-12 Plus/Minus/1	.33	Green	—	SN7447	4.95	3 for \$12.

LIGHT EMITTING DIODE GaAs INDICATORS

- 2-MV1*, Amber, visible jumbo epoxy lens upright. . . . \$1.00
- 1-MV2*, TO-18, Dome, green, visible 1.00
- 1-MV-2*, green small dome, green diff. lite 1.00
- 1-MV-2*, clear small plastic dome, green diff. lite 1.00
- 1-MV-3*, micro-mini 'pin head' dome, TO18, green lite 1.00
- 3-MV3*, visible, "coax pin pak", red, mini dome lens 1.00
- 1-MV4*, stud, high power, red, 2-watts 3.95
- 1-MV4H*, stud, high power, hi-dome, red, 2-watts 3.95
- 3-MV10B, visible, red, clear, dome lens, TO-18 1.00
- 3-MV10C visible, red, diffused, dome lens, TO-18 1.00
- 3-MV50*, axial leads, micro-mini dome, clear, red 1.00
- 3-MV55*, axial, micro-mini, red lite, red lens 1.00
- 3-MV5012*, visible, red, small dome lens 1.00
- 3-MV5020*, jumbo clear dome, TO-18, visible, red 1.00
- 3-MV5021*, jumbo red diffused lens, visible, lite RED 1.00
- 3-MV5022*, jumbo red lens, visible RED lite, spade, upri 1.00
- 3-MV5026*, jumbo red diffused lens, RED lite, spade 1.00
- 1-MV5040*, 4-LED red array, with 5-lead pak 1.49
- 3-MV5054*, visible, red, jumbo dome lens, upright 1.00
- 2-MV5080*, TO-18, micro-mini, clear dome, red 1.00
- 4-MV5082, visible, red, clear flat lens, TO-18 1.00
- 1-MV5222*, green hi plastic dome, diffused green lite 1.00
- 1-MV5222*, clear hi dome, diff. green lite 1.00
- 1-MV5222*, jumbo dome, green, panel snap-in 1.49
- 1-MV5322*, jumbo dome, GaAsp, panel snap-in Yellow 1.98
- 1-MV5491*, jumbo, Tri-State, RED, GREEN, OFF, special 1.98
- 1-MV9000*, cartridge panel lamp, sealed, red, clear lens 1.49
- 2-MT-2*, Photo Transistor, light sensor, TO-18 1.00
- 2-ME-1*, infra-red, parabolic lens, pin type 1.00
- 3-ME-3*, infra-red, invisible lite, "pinhead", single lead 1.00
- 3-ME-4*, infra-red "invisible", TO-18, diff. dome 1.00
- 3-ME-60*, infra-red, "invisible", axial, micro-mini 1.00

*Monsanto Equivalent

MUX'D DIGITAL CLOCK PC BOARD

Each board properly multiplexed for 6 digits, to hold MAN-1's, MAN-3's, MAN-4's, Litronics 707 (MAN-1) and 704 (MAN-4), and Opcoa's SLA-1 (MAN-1). Board 6 7/8" long with spec sheets. * Elec char. same as Monsanto devices MAN-1 or 4.

- Your choice \$2.50
- MAN-1 Litronics 707 (MAN-1*)
 - MAN-3 Litronics 704 (MAN-4*)
 - MAN-4 Opcoa SLA-1 (MAN-1*)
 - 6-MAN-3A's for above board. \$9.50.



- READOUT Char. Maker
- MAN-1 .27 h. Monsanto
 - MAN-4 .19 h. Monsanto
 - 707* .33 h. Litronics
 - 704** .33 h. Litronics
 - SLA-1* .33 h. Opcoa
- *Your choice of 5 red LED readouts!
- Buy 3 — Only \$9.99
 Take 10%

Scientific Devices "Digital Counting Modules" outperform any other DCM on the market today. More features than ever before! Not gaseous, not incandescents, not nixie but the modern LED. Choose from such famous manufacturers as Monsanto's MAN-1, MAN-4, Litronics 707 and 704, Opcoa's SLA-1 (the last 4 having character heights of 0.33 at no extra charge). Each kit includes 3x2" p.c board with fingers for a FREE edge connector, side-mounting dip socket, LED readout of your choice, resistors, 3 IC's, and Molex connectors (this ELIMINATES SOLDERING YOUR IC's), and booklet. INCLUDES P.C. EDGE CONNECTOR — FREE!

LED MITY DIGIT DCM

* Pin-for-pin MAN-1, ** Pin-for-pin MAN-4, elec. char. same

Terms: add postage Rated: net 30
 Phone Orders: Wakefield, Mass. (617) 245-3829
 Retail: 16-18 Del Carmine St., Wakefield, Mass. (off Water Street) C.O.D.'S MAY BE PHONED

15¢ CATALOG on Fiber Optics, 'IC's', Semi's, Parts

POLY PAKS

P.O. BOX 942A LYNNFIELD, MASS. 01940



OAK FEATHER-TOUCH SWITCHES

*For RTTY
 *Printed Circuits
 *For Unique Panel Switches Sale \$49

Mfd. by OAK (Ham's note, RTTY, too) data systems, same as used in Keyboard Calculator, SPST. Normally Open, 24V 1 amp contacts. Characters and letters easily changed, 3/8" high. Printed circuit.

*White top, black numbers.
 †Blue top, white characters.

Kit of 17 above switches for keyboard \$7.50



CALCULATOR KEYBOARD

3 for \$27 **9.95**

Etched calculator board with holes, as above, less switches . . . \$2.50 Board

Properly etched, drilled, "MULTIPLEXED," with proper diodes. Ready to go! Used with our own CAL TECH's 5001 chip advertised at \$ 9.95 or equal to Cal Tech or Mostek chip. Keyboard uses the new manufactured by OAK, printed-circuit low-profile FEATHER TOUCH switches. 0-to-9 in white with black letters. Decimal white with black dot. CE, CL and the 4 function switches are in blue with white characters. Designed by top maker. Size: 6 1/2 x 4 1/2 x 1/2". All etched connections link to take a 12-pin edge connector.

12-CALCULATOR ON A CHIP DIGIT

CT5001 Chip **9.95**
 Similar to Mostek 5001. Outperforms Texas 8-digit TMS1802. A 40-pin DIP. Adds, multiplies, subtracts, and divides. Use with 7-segment readouts, Nixies, and LED's. We include schematics, instructions to build calculator.
 CT5002-9 Volt version of above — \$9.95
 CT5005-Same as above with MEMORY — \$14.95



NATIONAL EQUAL "DIGITAL CLOCK on a CHIP"

Any "Chip" **\$12.88**

*Money Back Guarantee!

- 5311 28-pin, ceramic, any readout, 6-digits: A-B-D \$12.88 *With
- 5312 24-pin, ceramic, any readout, 4-digits: C-D \$12.88 Spec
- 5313 28-pin, ceramic, any readout, 6-digits: A-C \$12.88 Sheet!
- 5314 24-pin, plastic, LED and incandescent readouts, 6-digits: A-B \$12.88 Save!

Code: A—Hold Count. C—1 PPS Output. B—Output Strobe. D—BCD



POTTER BRUMFIELD MINI CAP RELAYS

Measures only 3/4 x 1 x 1 1/4". Plastic cased. Like KNP type. For pc board or socket, 14 lugs, 1-8/32 stud too! Both 4PDT. All ceramic construction. 3 amps, contacts. For r-f ant, switching. Wt. 1-oz.

Your choice 115 VAC \$2.49
 24 VDC 3 for \$6



SPERRY "ORANGE" TWIN DIGIT ARRAY

Type SP332, each digit is individually controlled, operates off 180VDC, 100 ua, 200 mw. Color: ORANGE. 7-digits, glass protection over digits. Character height: 0.33. P.C. mounting. Size: 3/4" x 3/4". 9-pins per digit. Driver: SN7447.

\$5.95
 3 for \$15.



SPECTROL CERMET "MICRO" POTS

Model No. 53-2-1, Cube 5/16" square, single turn, screw adjust front. Model No. 42-2-1, Rectangular 3/4" x 3/16" x 5/16", screw driver adjust, side. PC work. Both cermet sealed. Order by model number and value.

Your Choice Any 2 for \$1

- 10 1K
- 20 2K
- 50 5K
- 100 10K
- 200 20K
- 500 50K
- 100K
- 200K
- 500K
- 1 Meg



TABLE TOP CALCULATOR CASE + KEYBOARD
 Attractively designed!! Excellent craftsmanship. Case and keyboard (designed as one unit). Cabinet is made of high-impact plastic beige color with black bezel and amber window. Keyboard consists of a 3 position slide switch and 25 keys, 5 of which are used for memory function. 20 keys gray, 5 keys orange. All keys mounted on one printed circuit board.....



11" wide X 10.5" X 2.9" high

This modular unit is well suited for our calculator chips. Ideal for the CT5005

Case and keyboard complete only \$29.95

3 CHIP CALCULATOR

This calculator set provides all of the electronics for an eight digit, floating point calculator with left hand entry. Keyboard, display, clock generator, and display driver is all that need be added to make a calculator that will add, subtract, multiply, and divide. Overflow and negative signals are also provided. Complete instructions to build a calculator included.....

Chips and data-----\$7.95
 Data only-----1.00 (refundable)



CT5005 CALCULATOR

This calculator chip has a full four function memory, which is controlled by four keys, +M (adds entry into memory), -M (subtract entry from memory), CM (clear memory--without clearing rest of registers), RM (read memory or use as entry).



12 digit display and calc. fixed decimal at 0,1,2,3,4, or 5 leading zero suppression seven segment multiplexed output true credit sign display single 28 pin chip

Chip and data-----\$14.95
 Data only (refundable)----- 1.00

5001 CALCULATOR

40 pin calculator chip will add, subtract, multiply, and divide. 12 digit display and calculate. Chain calculations. True credit balance sign output. Automatic overflow indication. Fixed decimal point at 0, 2, 3, or 4 Leading zero suppression. Complete data supplied with chip.

Chip and data, only \$9.95
 Data only (refundable) \$1.00

All IC's are new and fully tested leads are plated with gold or solder Orders for \$5 or more will be shipped prepaid. Add 35¢ for handling and postage for smaller orders, residents in California add sales tax. IC orders are shipped within two workdays of receipt of order-kits are shipped within ten days of receipt of order. \$10.00 minimum on C.O.D.'s(phone in). (916) 9662111 Zip--95608

BABYLON ELECTRONICS P.O. Box J Carmichael California
 MONEY BACK GUARANTEE ON ALL GOODS...

General Telephone \$5.95

Ten push buttons (0-9) touch-tone, encoding, programming devices. Easy for panel mounting. Size: 3X2 1/2 X 1"



MEMORY SALE!!

256x1 BIT Random Access Memory Fully decoded---TTL Compatible input and output. No clock or refresh required.

INTEL 1101 MOS
 16 pin DIP-full data 2.56
 1¢ per BIT---- each \$22.56
 10 for

7400 series DIP

7400	\$.35	74H53	.50
74H00	.50	7454	.35
7401	.35	74L54	.50
74H01	.50	74L55	.50
7403	.35	7460	.35
7404	.35	74L71	.30
74L04	.50	7472	.50
74H04	.50	74L72	.60
7405	.35	7473	.65
74H05	.50	74L73	.90
74H08	.50	7474	.65
7410	.35	74L74	.90
74L10	.50	74H74	.90
74H11	.60	7476	.70
7413	1.75	74L78	1.00
7420	.35	7480	.65
74L20	.50	7483	1.30
74H20	.50	7486	.80
74H22	.60		
7430	.35		
74L30	.50	7491	1.15
7440	.35	7492	1.15
74H40	.50	7493	1.15
7441	1.60	7495	1.25
7442	1.30	74L95	2.00
7446	1.75	74107	.70
7447	1.75	74121	1.60
7448	1.15	74123	2.00
7450	.35	74154	2.50
74H50	.50		
7451	.35	74192	2.50
74L51	.50	74193	1.50
74H51	.50	74195	1.10
7453	.35		

RECTIFIERS

Varo Bridges
 VS447 2A 400V \$.90
 VS647 2A 600V 1.10

35A Stud 400V 1.10

MR810	50V 1A	.10
1N4997	50V 1A	.10
1N4001	1A	.10
1N4002	1A	.11
1N4003	1A	.12
1N4004	1A	.13
1N4007	1A	.17

SCR's


IR122	100V 8AMP	.50
IR122	200V 8AMP	.60
IR122	300V 8AMP	.80
IR122	400V 8AMP	1.00

LED's

MV-50 red emitting 10-40ma@2V 5 for \$.25
 1.00
 MV5054 red LED 15-100ma@2V \$.30
 10 for 2.50
 MV-10B Visible red 5-70ma @ 2V 10 for 2.50


GIANT "NIXIE"

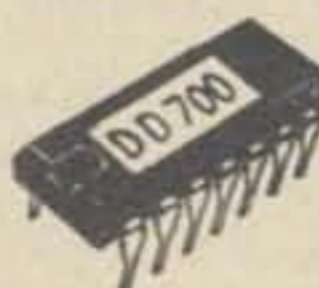Comes complete with Socket and DD700 202 Numeric Driver. Readability in high ambient light...200 footlamberts brightness!! All DC operation. Long life with no loss of brightness. Compatible with conventional solid state circuitry.



Only \$2.25

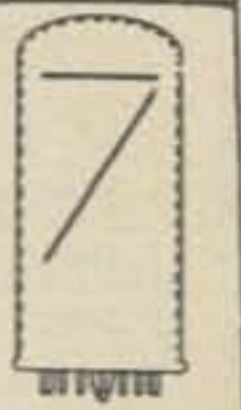These were used in the New York Stock Exchange



ACA 2010 NUMITRON

Popular digital display tube. This incandescent five volt, seven segment device provides a .6" high numeral which can be seen from a distance of 30 feet. The tube has a standard nine pin base (solderable) and a left hand decimal point....




\$5.00 each

\$4.00 each for 5 or more

MAN1

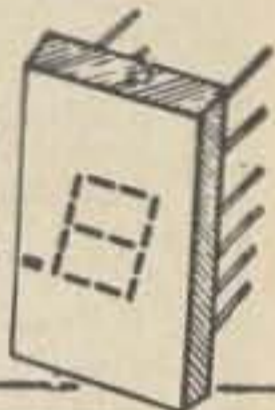
Seven Segment, 0-9 plus letters. Snaps in 14-pin DIP socket or Molex. Operates with IC voltage requirements. Long operating life



\$4.25 each

MAN4

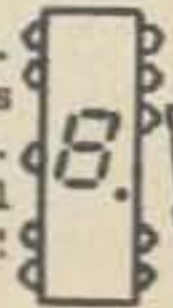Seven segment, 0-9 plus letters. Right hand decimal point. Snaps in 14-pin DIP socket or Molex. IC voltage requirements. Ideal for desk or pocket calculators!



Each.....\$ 3.00
 Ten or more..\$25.00 red lens

MAN3

0-9 plus letters. Right hand decimal point. Flat-Pack type case. Long operating life. IC voltage requirements. Ideal for pocket calculators !!!!!




Each.....\$ 2.50
 Ten or more..\$20.00 red lens

LINEARS


NE531	op amp TO-5	\$2.00
NE560	phase lock loop DIP	3.25
NE561	phase lock loop DIP	3.25
NE565	phase lock loop TO-5	3.25
NE566	function generator TO-5	4.00
NE567	tone decoder TO-5	4.00
NE5556	op amp DIP	1.00
709	popular op amp DIP	.45
710	voltage comparator DIP	.50
711	dual comparator DIP	.40
723	precision voltage regulator DIP	1.00
747	dual 741 op amp DIP	1.00
748	op amp TO-5	1.00
LM100	positive DC regulator TO-5	1.00
LM302	op amp voltage follower TO-5	1.25
LM1595	4 quadrant multiplier	\$2.00
LM311	comparator TO-5	1.75
LM380	2W audio amp DIP	1.75
LM703	RF-IF amp epoxy TO-5	1.00
LM309H	5V-200ma power supply TO-5	1.00
LM309K	5V-1A power supply module TO-3	2.00

'73 SPECIALS


A FEW CIRCUITS...

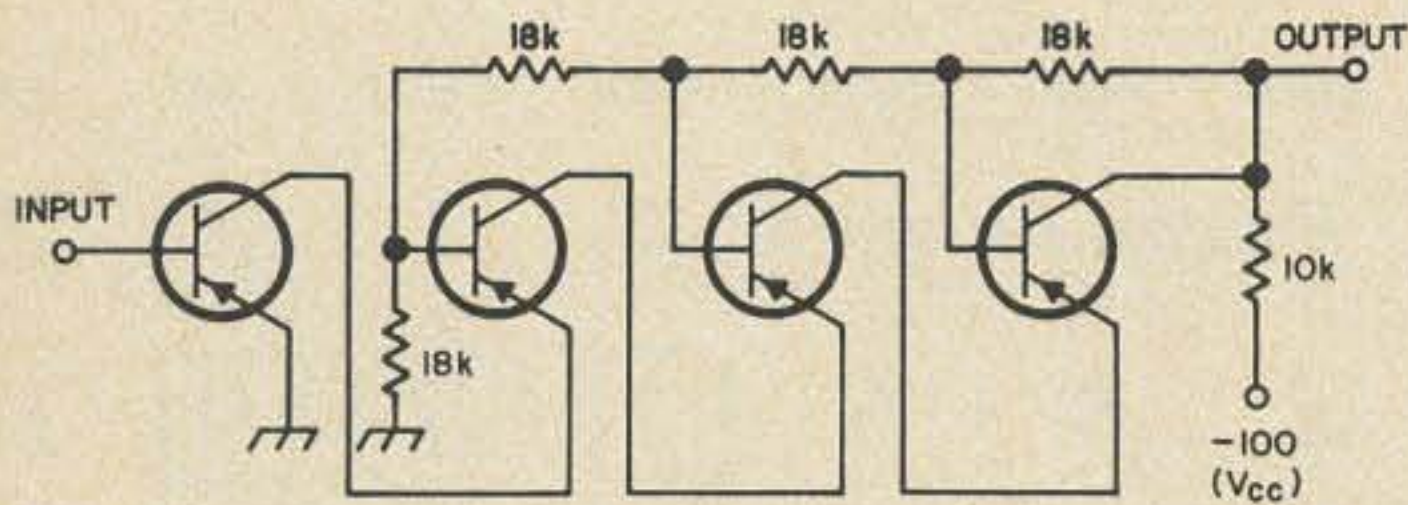

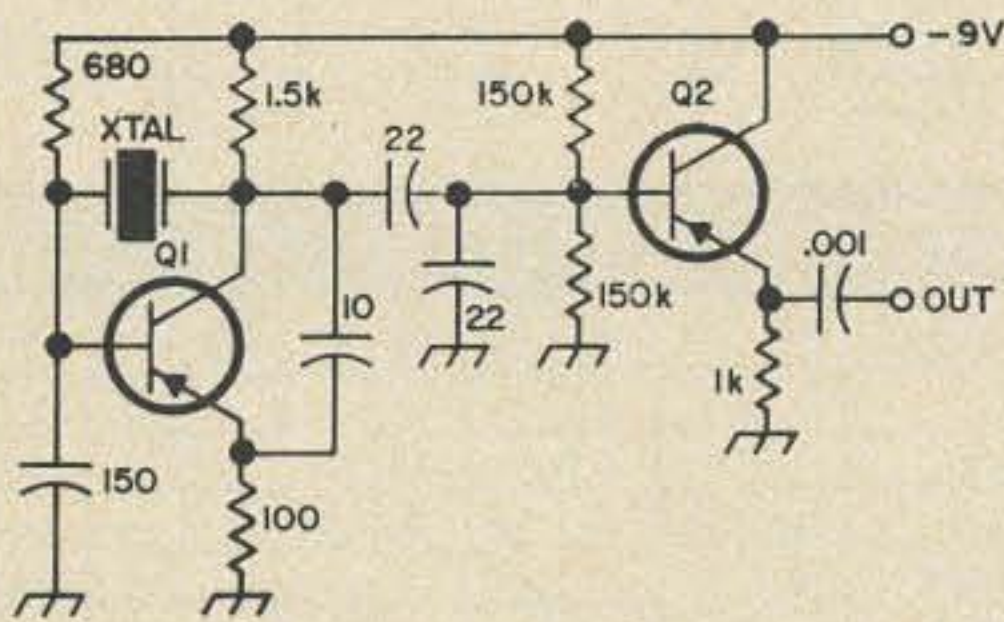
High voltage direct coupled amplifier. The gain of this amplifier is equivalent to both sections of a 12AU7. All transistors are SK3008, GE-9 or HEP-51.



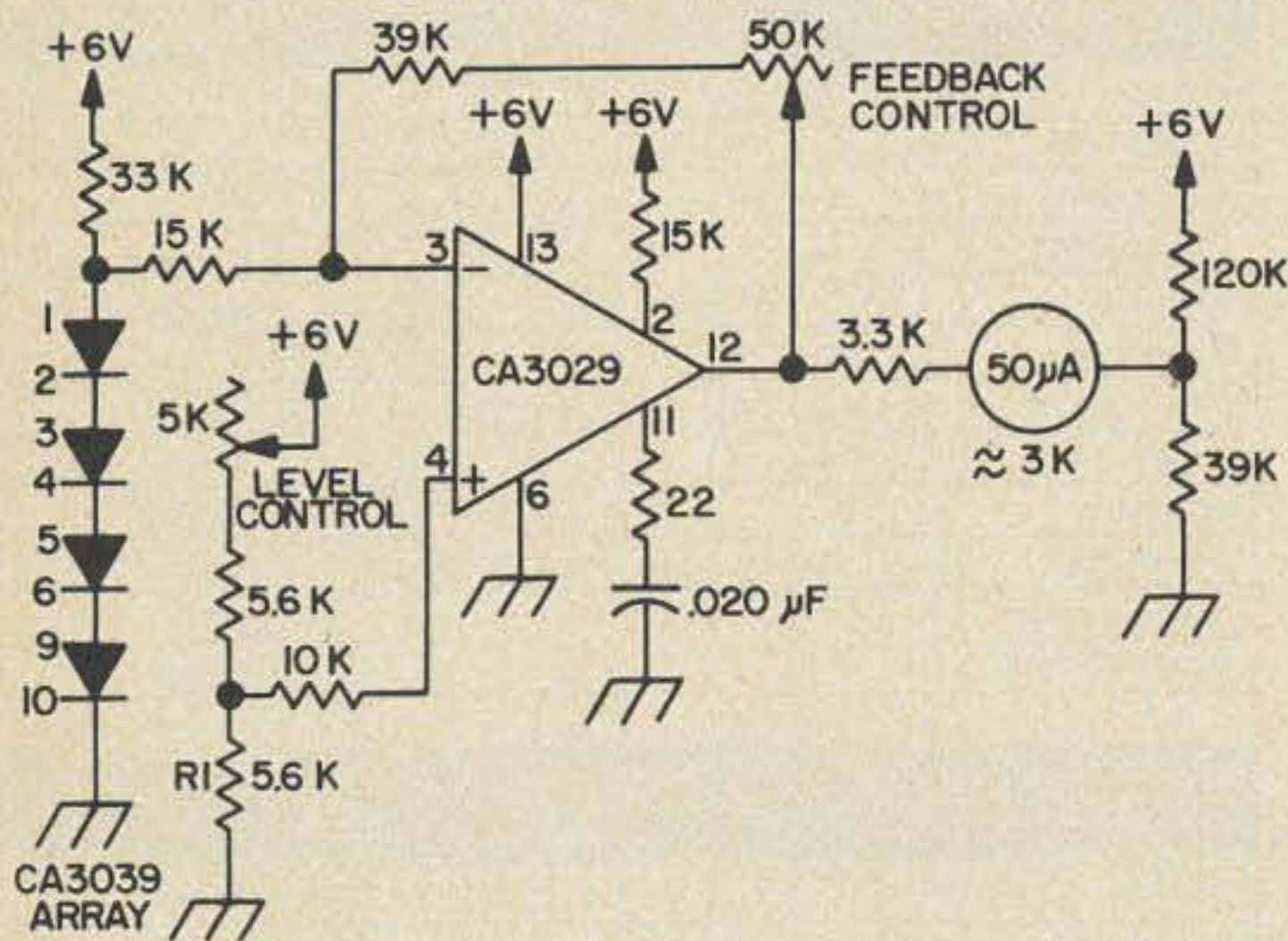This untuned crystal oscillator will oscillate with any crystal from 300 kHz to 10 MHz. Frequency stability is very good because the emitter follower buffer amplifier effectively isolates the oscillator from the load. Q1 and Q2 are GE-9, SK30006 or HEP-2.



An electronic thermometer using the CA3039 diode array as the sense element. A CA3029 op amp detects the change in voltage fed into it by the diodes against the level control's reference voltage and displays the amplified difference on the meter. The level control should be set so room temperature reads near mid-scale, while the feedback control adjusts the upper and lower extremes of 120° F and 0° F. From "Handbook of IC Circuit Projects," by Tab Books.

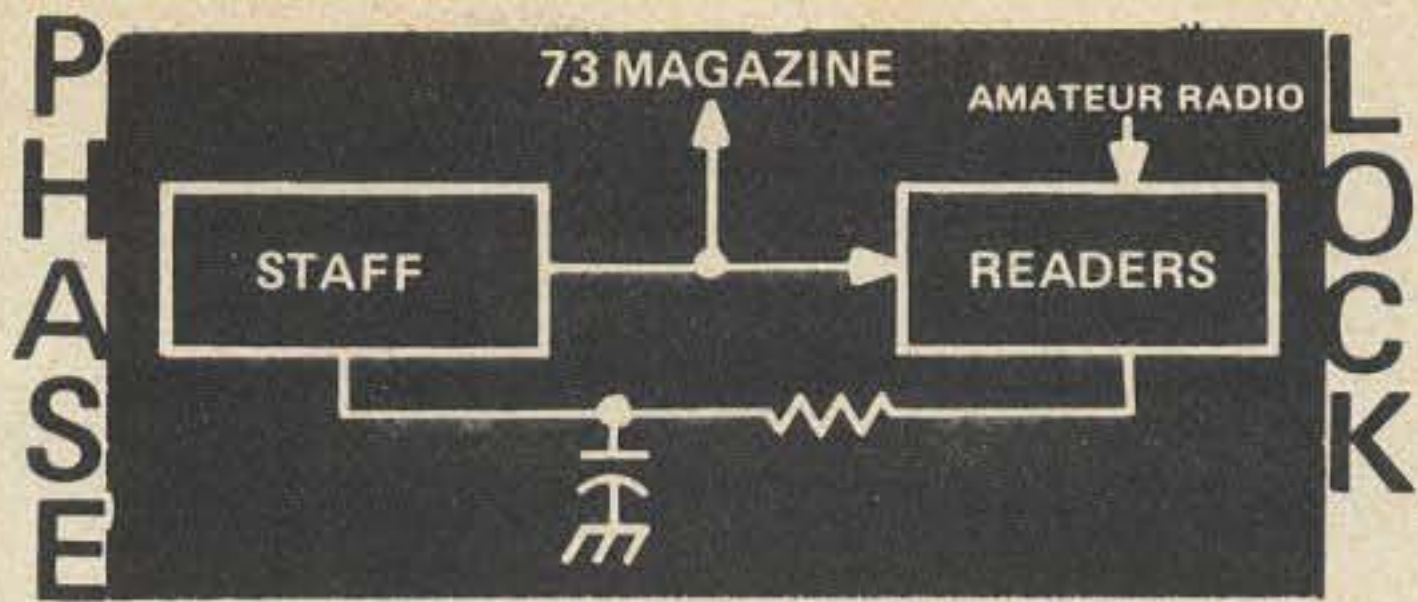

In this issue, do you think there is a need for more

	Yes	No
Simple construction projects	<input type="checkbox"/>	<input type="checkbox"/>
Complex construction projects	<input type="checkbox"/>	<input type="checkbox"/>
General interest articles	<input type="checkbox"/>	<input type="checkbox"/>
Humor articles	<input type="checkbox"/>	<input type="checkbox"/>
Specialized columns	<input type="checkbox"/>	<input type="checkbox"/>
Operating news	<input type="checkbox"/>	<input type="checkbox"/>

Comment (a):

Comment (b):

Comment (c):

Comment (d):

Do you receive 73 from subscription
newsstand

Fill out this form immediately and mail it with the Reader Service coupon on the reverse side (or vice versa).

READER SERVICE

Please either tear out this list of advertisers and send it in to 73 with as many boxes checked off as you would like to see brochures, data sheets or catalogs . . . or else make a copy and send that in. Include your zip code, please. Send money directly to advertisers.

ADVERTISER INDEX

- | | |
|---|--|
| <input type="checkbox"/> AAA Sales 104 | <input type="checkbox"/> Janel 31 |
| <input type="checkbox"/> Adirondack 68 | <input type="checkbox"/> Jeff Tronics 145 |
| <input type="checkbox"/> Alarm Comp 30 | <input type="checkbox"/> Jensen 104 |
| <input type="checkbox"/> Alden 70 | <input type="checkbox"/> Johnson 156 |
| <input type="checkbox"/> Alpha 24 | <input type="checkbox"/> Juge 58 |
| <input type="checkbox"/> Am Wholesale 144 | <input type="checkbox"/> K A Sales 146 |
| <input type="checkbox"/> Antenna Mart 82 | <input type="checkbox"/> K Enterprises 30 |
| <input type="checkbox"/> Antenna Spec C11 | <input type="checkbox"/> KLM Elect 102 |
| <input type="checkbox"/> Astatic 114 | <input type="checkbox"/> Lindy Pen 140 |
| * <input type="checkbox"/> ATV Research 43 | <input type="checkbox"/> Linear Systems 48 |
| <input type="checkbox"/> Autek 71 | <input type="checkbox"/> Mann 37 |
| <input type="checkbox"/> A & W Elect 152,153 | <input type="checkbox"/> Meshna 132,133 |
| <input type="checkbox"/> Babylon 158 | <input type="checkbox"/> MFJ 105 |
| <input type="checkbox"/> Bird 56 | <input type="checkbox"/> MITS 110 |
| <input type="checkbox"/> Bomar 54 | <input type="checkbox"/> Motorola 25 |
| <input type="checkbox"/> Callbook 51 | <input type="checkbox"/> M-Tron 104 |
| <input type="checkbox"/> Circuit Spec 127 | <input type="checkbox"/> Newtronics 42 |
| <input type="checkbox"/> Clegg 94,106 | <input type="checkbox"/> Nurmi 107 |
| <input type="checkbox"/> Comm Spec 105 | <input type="checkbox"/> Omnibus 52 |
| <input type="checkbox"/> Comm Unlimited 138,139 | <input type="checkbox"/> Palomar 57 |
| <input type="checkbox"/> Cornell 104 | <input type="checkbox"/> Pemco 31 |
| <input type="checkbox"/> Dames 120 | <input type="checkbox"/> Polygon 95 |
| <input type="checkbox"/> D A Products 43 | <input type="checkbox"/> Poly Paks 155,157 |
| <input type="checkbox"/> Data Eng 137 | <input type="checkbox"/> Q-Tronics 43 |
| <input type="checkbox"/> Datak 56 | <input type="checkbox"/> Regency 41 |
| <input type="checkbox"/> Densen 118 | <input type="checkbox"/> RGS 126 |
| <input type="checkbox"/> Dupage FM 121 | <input type="checkbox"/> Rohn 141 |
| <input type="checkbox"/> Dynamic Elect 105 | * <input type="checkbox"/> R P Elect 57 |
| <input type="checkbox"/> ECM 43 | <input type="checkbox"/> Savoy C111 |
| <input type="checkbox"/> Elect Dist 115 | <input type="checkbox"/> Sawyer Radio 82 |
| <input type="checkbox"/> E L Inst 33 | <input type="checkbox"/> Selectronics 129 |
| <input type="checkbox"/> Erickson 86 | <input type="checkbox"/> Semex 105 |
| <input type="checkbox"/> Estes 70 | <input type="checkbox"/> Sentry CIV |
| <input type="checkbox"/> Freck 54 | <input type="checkbox"/> Signal Systems 127 |
| <input type="checkbox"/> Gam 151 | <input type="checkbox"/> Solid State 134 |
| <input type="checkbox"/> Gateway 67 | <input type="checkbox"/> Solid State 134 |
| <input type="checkbox"/> Genave 91 | <input type="checkbox"/> S & R 130,131 |
| <input type="checkbox"/> J J Glass 154 | <input type="checkbox"/> Stahler 54 |
| <input type="checkbox"/> GLB 104 | <input type="checkbox"/> Standard Comm 5 |
| <input type="checkbox"/> Godbout 119 | <input type="checkbox"/> Thomas Advertising 52 |
| <input type="checkbox"/> Goldstein 123 | <input type="checkbox"/> TPL 44,45,46,47 |
| <input type="checkbox"/> Goodheart 90 | <input type="checkbox"/> Tri Tek 96 |
| <input type="checkbox"/> Gregory 72 | <input type="checkbox"/> Unidyne 135 |
| <input type="checkbox"/> Hal 105,71,122 | <input type="checkbox"/> Valpey 112 |
| <input type="checkbox"/> Ham Radio Ct 92 | <input type="checkbox"/> Vanguard 23,76,97 |
| <input type="checkbox"/> Hatry 60 | <input type="checkbox"/> Van W2DLT 43 |
| <input type="checkbox"/> Heath 38 | <input type="checkbox"/> Venus Scientific 113 |
| <input type="checkbox"/> Henry 34,150 | <input type="checkbox"/> VHF Eng 148,149 |
| <input type="checkbox"/> Hobby Industry 13 | <input type="checkbox"/> Vintage Radio 51 |
| <input type="checkbox"/> Hygain 124,125 | <input type="checkbox"/> Waller III |
| <input type="checkbox"/> Icom 116,117 | <input type="checkbox"/> Wolf 70 |
| <input type="checkbox"/> Inter Elect 136 | <input type="checkbox"/> P Wood 104 |
| <input type="checkbox"/> Jan 82 | <input type="checkbox"/> World QSL 104 |
| | <input type="checkbox"/> Yaesu 20 |

Coupon expires in 60 days

* Reader service inquiries not solicited. Correspond directly to company. NOVEMBER 1973

Mail to:

Reader's Service
73 Inc., Peterborough NH 03458

Please Print or Type

Name _____ Call _____

Address _____

City _____ State _____ Zip _____

PROPAGATION CHART

J.H. Nelson

Good (Open) Fair (□) Poor (O)

November 1973

SUN MON TUES WED THUR FRI SAT

Possible Aurora 10, 25.			1	2	3	
4	5	6	7	8	9	10
11	12	13	14	15	16	17
18	19	20	21	22	23	24
25	26	27	28	29	30	

EASTERN UNITED STATES TO:

	GMT:	00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14	7	7	3	3	3	3	7	7	14	14A	14	
ARGENTINA	14	7	7	7	7	7	14	21	21	21	21	12	14A
AUSTRALIA	14	7B	7B	7B	7B	7B	7	14	14	14	14	14	14A
CANAL ZONE	14	7	7	7	7	7	14	21	21A	21A	21	14	
ENGLAND	7	7	7	3A	7	7	14	14A	14A	14	7B	7	
HAWAII	14	7A	7	7	7	7	7	7B	14	21	21	21	
INDIA	7	7	7B	7B	7B	7B	14	14	7B	7B	7	7	
JAPAN	14	7B	7B	7	7	7	7	7	7B	7B	7B	14	
MEXICO	14	7	7	7	7	7	7	14	21	14A	14A	14	
PHILIPPINES	14	7B	7B	7B	7B	7	7	7	7	7B	7B	7	
PUERTO RICO	7	7	7	7	7	7	14	14A	14A	14A	14	14	
SOUTH AFRICA	7	7	7	7	7B	14	21	21A	21A	21	21	14	
U. S. S. R.	7	7	3A	3A	7	7B	14	14	14	7B	7B	7	
WEST COAST	14	7A	7	7	7	7	7	14	14A	21	21	14A	

CENTRAL UNITED STATES TO:

ALASKA	14	7A	7	3	3	3	3	7	7A	14	14A	14A	
ARGENTINA	14	7	7	7	7	7	14	21	21	21	21	21	
AUSTRALIA	21	14	7B	7B	7B	7B	7	7	14	14	14	21	
CANAL ZONE	14	7A	7	7	7	7	14	21	21A	21	21		
ENGLAND	7	7	7	3A	7	7	7B	14	14A	14	7B	7	
HAWAII	21	14	7	7	7	7	7	7	14	21	21	21	
INDIA	7	7	7B	7B	7B	7B	3B	7A	7A	7	7	7	
JAPAN	14	7A	7B	7	7	7	3A	7	7	7	7B	14	
MEXICO	14	7	7	7	7	3A	3A	14	14A	14	14	14	
PHILIPPINES	14	7A	7B	3B	7B	7	3A	7	7	7	7B	14	
PUERTO RICO	14	7	7	7	7	7	14	14A	21	21	21	14	
SOUTH AFRICA	14B	7	7	7	7B	7B	14	21	21A	21	21	14	
U. S. S. R.	7	7	3A	3A	7	7	7B	14	7A	7B	7B	7	

WESTERN UNITED STATES TO:

ALASKA	14	14	7	3	3	3A	3	3	7	14	14A	14A	
ARGENTINA	14A	14	7	7	7	7	7	14	21	21	21	21	
AUSTRALIA	21	14A	14	7B	7B	7B	7	7	14	14	14	21	
CANAL ZONE	14	14	7	7	7	7	7	14	21A	21A	21	21	
ENGLAND	7	7	7	3A	7	7	7B	7B	14	14	7B	7B	
HAWAII	21A	14A	14	7	7	7	7	7	14	21	21	21A	
INDIA	7	14	7B	3B	3B	7B	3B	7	7	7	7	7B	
JAPAN	21	14	7B	7	7	7	7	3A	7	7	7	14	
MEXICO	14	14	7	7	7	7	7	14	21	21	14A	14	
PHILIPPINES	21	14	7B	7B	7B	7	7	3A	7	7	7B	14	
PUERTO RICO	14	7	7	7	7	7	7	14	21	21	21	14A	
SOUTH AFRICA	14B	7	7	7	7B	7B	7B	14	21	21	21	14	
U. S. S. R.	7	7	7	3A	3A	7	3A	7	7A	7B	7B	7B	
EAST COAST	14	7A	7	7	7	7	7	14	14A	21	21	14A	

A = Next higher frequency may be useful also.
B = Difficult circuit this period.

Savoy



\$3.75

Postpaid in U.S.A.

TYPE 900 A

TYPE 901



HIGH ACCURACY CRYSTALS FOR OVER 30 YEARS

Either type for amateur VHF in Regency, Swan, Standard, Drake, Vari-
tronics, Tempo, Yaesu, Galaxy, Trio, Sonar, Clegg, SBE, Genave.

Quotes on request for amateur or commercial crystals for use in all
other equipments.

Specify crystal type, frequency, make of equipment and whether transmit
or receive when ordering.

BASSETT

High efficiency mobile
portable antennas
all amateur bands,
MARS, CB,
SECURITY,
PUBLIC SERVICE,
MARINE, AND
GOVERNMENT USE.

Models: 6-10-15-20-40-75

Identical size, cost,
and appearance

FULLY ADJUSTABLE
TO FREQUENCY
IN FIELD

Low weight, low drag,
High strength
fiberglass

Polished
chrome brass
standard 3/8-24 thread

High gain collinear
in 2 meters

MODEL DGA-2M

\$29.50 postpaid

in U.S.A.



BASSETT VACUUM TRAP ANTENNA SYSTEM

Complete packaged multi-band antenna systems employing the famous Bassett Sealed Resonators and Balun from which air has been removed and replaced with pure helium at one atmosphere. Operating bands are indicated by model designation.

MODEL DGA-4075	...	\$59.50
MODEL DGA-204075	...	\$79.50
MODEL DGA-2040	...	\$59.50
MODEL DGA-152040	...	\$79.50

BASSETT VACUUM BALUN



The famous sealed helium filled Balun . . . employed with the DGA Series Antenna Systems. Solderless center insulator and easily handles more than full legal power while reducing unwanted coax radiation. Equipped with a special SO-239 type coax connector and available either 1:1 or 4:1.

MODEL DGA-2000-B . . . \$12.95
Postpaid in U.S.A.

CONTACT YOUR DISTRIBUTOR OR WRITE FOR DATA

Savoy Electronics, Inc.


P.O. Box 5727- Fort Lauderdale, Florida - 33310

Tel: 305-566-8416 or 305-947-1191



Tired of Inflated Prices?

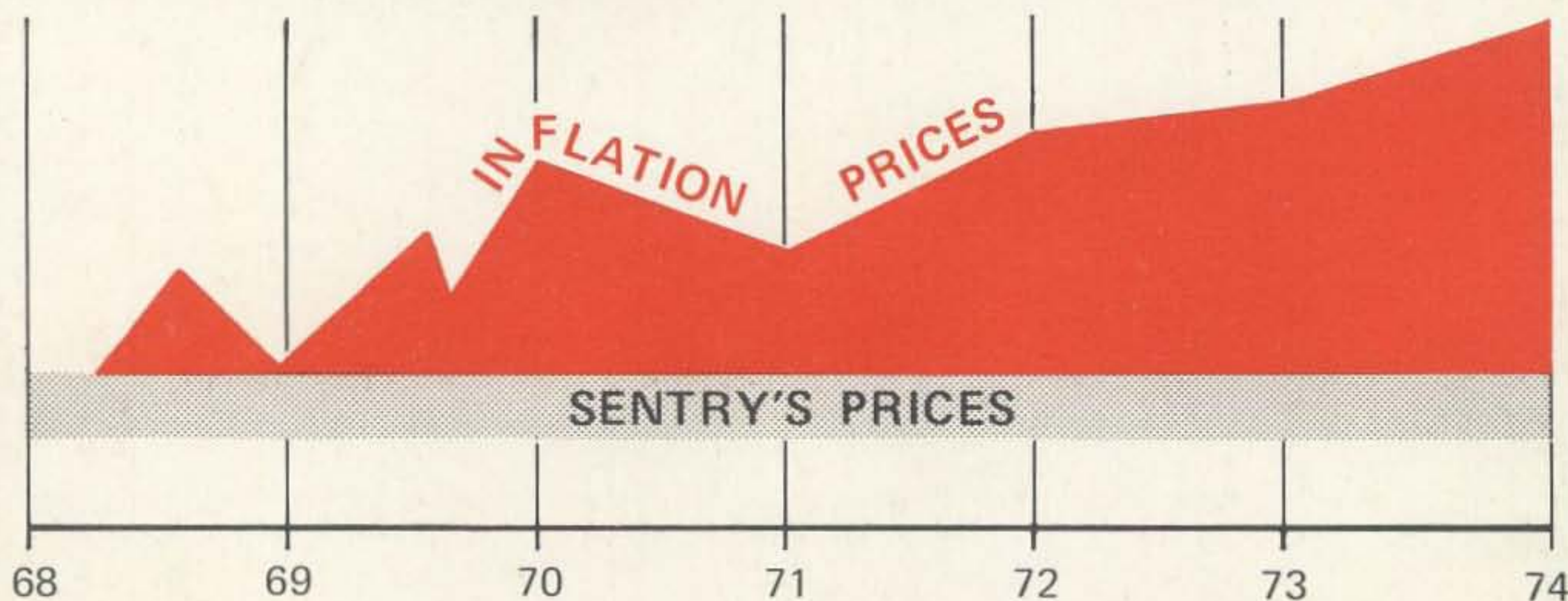Check Sentry's Pre-Season Offer to hold down your 2 Meter FM crystal expenses.



BUY ANY THREE Repeater or 2 Meter FM crystals at the regular price and receive **ONE CRYSTAL AT 25% OFF!**

NO PRICE CHANGE IN THE LAST 5 YEARS — and in some cases, volume prices have been slashed.

UNCHANGING POLICY OF:


- **Warranty** — Sentry guarantees any Sentry crystal to be free of defects in workmanship for an unlimited time.
- **Customer Service** — When you buy a Sentry crystal, service is part of the package.
- **Ease of Ordering** — You need only specify manufacturer, model and channel frequency. Sentry maintains up-to-the-minute files on all fixed station, mobile, aircraft and marine radios.
- **One Stop Shopping** — Sentry offers a complete series of amateur, general purpose, commercial, precision, CB, I.F., 2M FM, aircraft and marine crystals (32 KHz to 210 MHz) crystals to MIL 3098 also.
- **Fast Delivery** — Any tolerance on any crystal, 5 working days for one to three crystals.

All of this "PLUS" Inflation Fighting Prices.

OFFER EXPIRES
1 JANUARY 74,
SO PLACE YOUR
ORDER NOW.

When you order,
just say you
read it in
73 Magazine.

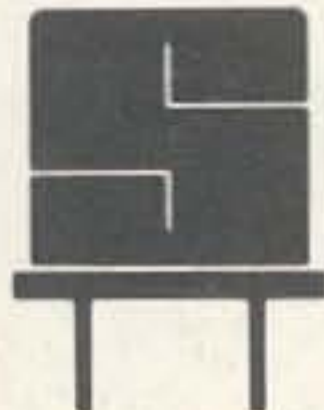If you don't have our 1974 catalog, write for yours today.



SENTRY MANUFACTURING COMPANY
Crystal Park, Chickasha, Oklahoma 73018

PHONE: (405) 224-6780 TWX - 910-830-6425