

75 cents

*hr*_m

focus
on
communications
technology . . .

ham **radio**

magazine

NOVEMBER 1973

this month

- motorola test set 12
- RTTY tuning unit 16
- ssb transceiver 32
- DX antennas 54
- repeater-site calculations 58



**low-power
solid-state
vfo transmitter
for 20 meters**

Savoy

BASSETT

High efficiency mobile and portable antennas for all amateur bands, CAP, MARS, CB, SECURITY, PUBLIC SERVICE, MARINE, AND GOVERNMENT USE.

- 2-6-10-15-20-40-75
- Identical size, cost, and appearance
- FULLY ADJUSTABLE TO FREQUENCY IN FIELD
- Low weight, low drag, high strength fiberglass
- Polished chrome brass standard 3/8-24 thread
- High gain collinear on 2 meters

MODEL DGA-2M
\$29.50 postpaid
in U.S.A.




\$3.75

Postpaid in U.S.A.

TYPE 900 A

TYPE 901

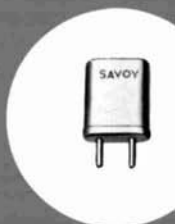

HIGH ACCURACY CRYSTALS FOR OVER 30 YEARS

Either type for amateur VHF in Regency, Swan, Standard, Drake, Vari-tronics, Tempo, Yaesu, Galaxy, Trio, Sonar, Clegg, SBE, Genave.

Quotes on request for amateur or commercial crystals for use in all other equipments.

Specify crystal type, frequency, make of equipment and whether transmit or receive when ordering.



BASSETT VACUUM TRAP ANTENNA SYSTEM

Complete packaged multi-band antenna systems employing the famous Bassett Sealed Resonators and Balun from which air has been removed and replaced with pure helium at one atmosphere. Operating bands are indicated by model designation.

MODEL DGA-4075	\$59.50
MODEL DGA-204075	\$79.50
MODEL DGA-2040	\$59.50
MODEL DGA-152040	\$79.50

BASSETT VACUUM BALUN



The famous sealed helium filled Balun employed with the DGA Series Antenna Systems. Solderless center insulator easily handles more than full legal power while reducing unwanted coax radiation. Equipped with a special SO-239 type connector and available either 1:1 or 4:1.

MODEL DGA-2000-B \$12.95
Postpaid in U.S.A.

CONTACT YOUR DISTRIBUTOR OR WRITE FOR DATA


Savoy Electronics, Inc.

P.O. Box 5727 - Fort Lauderdale, Florida - 33315

Tel: 305-566-8416 or 305-947-1191



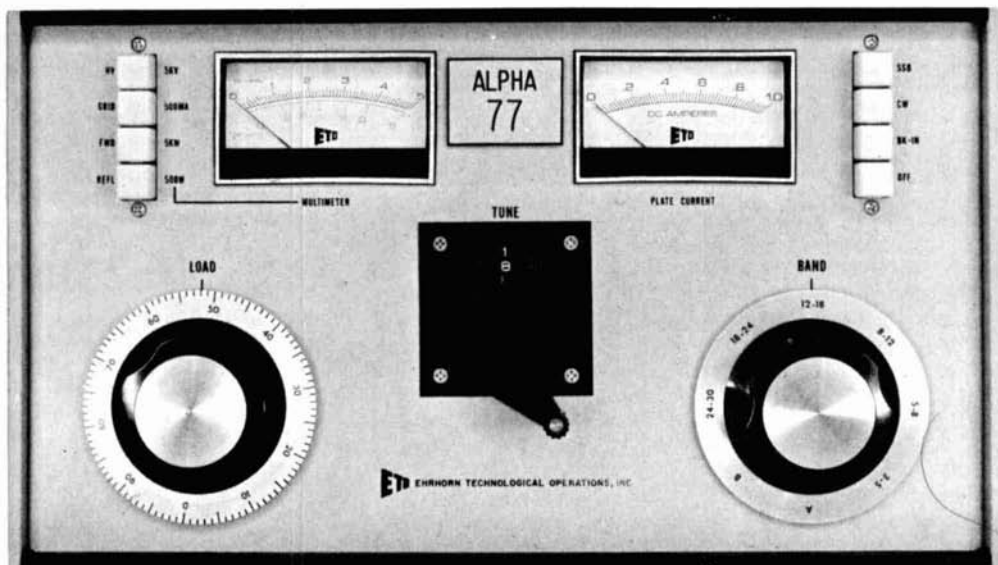“OPERATING ON-THE-AIR WITH THE ALPHA 77 IS A PURE PLEASURE”



*“IF THE AMATEUR WANTS TO GO FIRST CLASS
IN EVERY SENSE OF THE WORD,
THE ALPHA 77 IS ONE WAY TO DO IT.”*

(QST – March 1973)

The superb ALPHA 77 legal-limit amplifier is truly in a class by itself . . . a sleek desk-top powerhouse that delivers a *whole rack full* of performance. The '77 is engineered and built to operate *continuously* at maximum legal power-in *any mode* including FSK or SSTV – and to stay cool and quiet in the process.

Now the ALPHA 77 is the *only linear* to provide full *standard* coverage of 10 through 160 meters – a feature not available elsewhere even as an option.

You really have to *see and use* the ALPHA 77 to fully appreciate its unmatched quality and ruggedness. If *you* enjoy owning and using *the very finest*, you owe it to yourself to *at least investigate the ALPHA 77* by phoning or writing for detailed literature. Available direct from ETO and from selected dealers coast-to-coast. ALPHA 77 domestic net price, \$1995.



EHRHORN TECHNOLOGICAL OPERATIONS, INC.
BROOKSVILLE, FLORIDA 33512
(904) 596-3711

The Most Powerful Antennas Under the Sun




hy-gain

DB-24B

DuoBand Does It Best!

20 AND 40 METERS

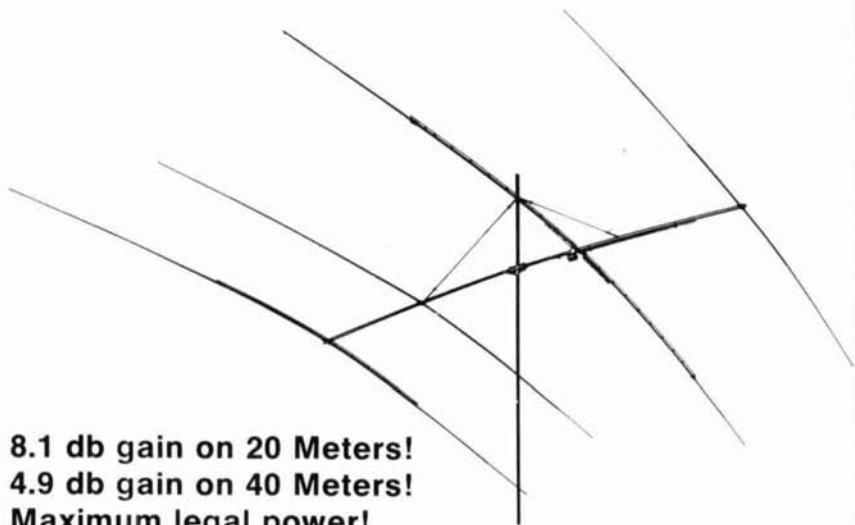

**8.1 db gain on 20 Meters!
4.9 db gain on 40 Meters!
Maximum legal power!**

The Hy-Gain DB-24B is the top combination for top performance on 20 and 40 meters. Uses three full-sized elements on 20 meters and two 2/3 size elements in conjunction with Hy-Gain's perfected linear loading on 40 meters. Unique linear decoupling stubs make two band operation possible without inductance and capacity traps. Feeds with 52 ohm coax and is equipped with balun and Beta Match for optimum energy transfer. F/B Ratio: 20 meters, 20-30 db; 40 meters, 10-20 db. Boom length 24 ft., longest element 43 ft., maximum input 1 kw, AM.

DB-24B...for top duoband performance!

Order No. 396

\$199.95

HY-GAIN ELECTRONICS CORPORATION

Dept. BL, 8601 Northeast Highway Six, Lincoln, NE 68507
402/464-9151 Telex 48-6424

November, 1973
volume 6, number 11

staff

James R. Fisk, W1DTY
editor

Patricia A. Hawes, WN1QJN
editorial assistant

Nicholas D. Skeer, K1PSR
vhf editor
J. Jay O'Brien, W6GDO
fm editor

Alfred Wilson, W6NIF
James A. Harvey, WA6IAK
associate editors

Wayne T. Pierce, K3SUK
cover

T.H. Tenney, Jr. W1NLB
publisher

Hilda M. Wetherbee
assistant publisher
advertising manager

offices

Greenville, New Hampshire 03048
Telephone: 603-878-1441

ham radio magazine is
published monthly by
Communications Technology, Inc
Greenville, New Hampshire 03048

Subscription rates, world wide
one year, \$7.00, three years, \$14.00
Second class postage
paid at Greenville, N.H. 03048
and at additional mailing offices

Foreign subscription agents
United Kingdom
Radio Society of Great Britain
35 Doughty Street, London WC1, England

All European countries
Eskil Persson, SM5CJP, Frotunagrand 1
19400 Upplands Vasby, Sweden

African continent
Holland Radio, 143 Greenway
Greenside, Johannesburg
Republic of South Africa

Copyright 1973 by
Communications Technology, Inc
Title registered at U.S. Patent Office
Printed by Wellesley Press, Inc
Framingham, Massachusetts 01701, USA


ham radio is available to the blind
and physically handicapped on magnetic tape
from Science for the Blind
221 Rock Hill Road, Bala Cynwyd
Pennsylvania 19440
Microfilm copies of current
and back issues are available
from University Microfilms
Ann Arbor, Michigan 48103

Postmaster: Please send form 3579 to
ham radio magazine, Greenville
New Hampshire 03048



contents

- 6 solid-state 20-meter transmitter**
C. Edward Galbreath, W3QBO
- 12 motorola test set**
David L. Marshall, KØBKD
- 16 variable-shift RTTY tuning unit**
Keith H. Sueker, W3VF
- 26 polarity inverter**
J. R. Laughlin
- 32 single-band ssb transceiver**
Charles H. Hill, W5BAA
- 40 single-frequency fm repeaters**
George R. Allen, W2FPP
- 46 impedance-matching baluns**
R. W. Johnson, W6MUR
- 50 compact keyer package**
Gene E. Brizendine, W4ATE
- 54 DX antennas**
Gerd H. Schrick, WB81FM
- 58 antenna and control-link calculations**
P. J. Ferrell, W7PUG
- 4 a second look** **62 ham notebook**
110 advertisers index **66 new products**
64 comments **110 reader service**
99 flea market

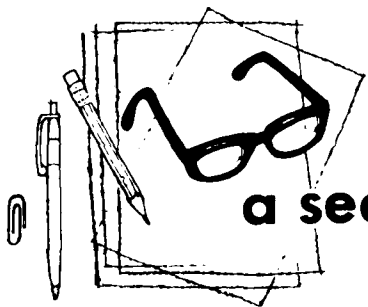

a second look

by jim
fisk

Because of an excessive number of problems being encountered by the FCC with amateur repeater license applications, and the lengthy processing delay, the Commission has extended the deadline date for all amateur stations licensed prior to October 17, 1972, which were automatically retransmitting radio signals from other amateur stations, *and* for which a timely and sufficient application has been filed. An application will be considered as being timely if it was received by the FCC on or before August 30, 1973.

According to the Commission, there apparently has been some confusion among amateurs as to the actual effective date of the rules adopted in Docket 18803. The FCC has reiterated that the rules became effective on October 17, 1972, and further, that full compliance was expected as soon as possible but not later than June 30, 1973. At the request of the American Radio Relay League this period was extended to August 30, 1973.

The FCC adheres to the view that all licensees have had adequate time in which to modify their repeater stations to fully comply with the rules set forth by Docket 18803, although there may not have been sufficient time to obtain the licensing authority for a repeater station, control station and/or auxiliary link station. Therefore, although the licensing deadline has been extended (apparently indefinitely), amateurs operating repeaters under previous authorization are cautioned that their operations must otherwise fully comply with the rules. The Commission has also pointed out that licensees and control operators of stations not operated in compliance with the rules of Docket 18803 are subject to appropriate enforcement action.


The FCC has complained that the main problems contributing to the lengthy processing delays are lack of standardization, failure to supply the

required information and failure to present the information in a manner permitting rapid processing. In as much as there has been considerable confusion as to what information was actually required and the Commission was apparently reluctant to supply any guidelines, this is not surprising. After a considerable amount of arm twisting a few suggestions were forthcoming but they were nebulous at best. To add to the muddle, FCC staff members reached the epitomy of bureaucratic vacillation by approving one application and then disapproving another which used exactly the same format. If the problem wasn't so serious it would be amusing.

The Commission is now, finally, developing suggested application forms that are designed to eliminate the most frequently encountered errors. This should have originally been done at the time they adopted Docket 18803 — it would have saved everyone a lot of grief. Although it has not yet been decided if these suggested forms will be adopted as official FCC forms, properly prepared license applications using them will be acceptable for processing. You can also help by using universally accepted terms and standard symbols in your repeater license applications. If there is any question about an abbreviation, for example, spell it out — terms commonly used in one part of the country may mean something completely different somewhere else.

In the meantime, if your repeater was licensed prior to October 17, 1972, *and* you have filed a new license application prior to August 30, 1973, you can continue to operate your repeater under its present license *providing* it complies with all the rules of Part 97 of the regulations, as amended by Docket 18803.

Jim Fisk, W1DTY
editor



**for over 20 years we've
been designing VHF-FM
antennas for some
pretty tough customers.**

**we know
you're just as tough.**

A product in the amateur market gets a reputation very quickly. It measures up to what you expect in engineering, performance and quality — or else. That's why A/S amateur antennas are built to the identical design and construction standards as their commercial counterparts. Standards that have made them specified for more police and public safety vehicle installations than all other brands combined.

**HM-177
2 Meters**

Features new high conductivity copper and nickel coated 17-7 PH stainless steel whip. Shunt fed coil encased in waterproof PVC jacket. All fittings chrome plated brass. Easy snap-in mounting. 3 dB gain.*

**NEW! HM-223
1¼ Meters
(220 MHz)**

High performance $\frac{5}{8}$ wavelength design for the new 220 MHz activity! Directly fed with low loss coil in new low-profile design. Spring and whip easily removable leaving only $1\frac{3}{16}$ " high base for car wash clearance. 3 dB gain.*

**HM-175
¾ Meters**

Collinear design with truly hot performance! Base fittings have silver plated contacts. Can handle 100 watts. Whip and phasing coil assembly is a one piece molded design to resist vibration and moisture. 5 dB gain.*

**HM-4
2 Meters**

Tough, virtually indestructible antenna for hand-helds. Completely insulated. Base fitting matches Motorola HT, E. F. Johnson, and Standard portables.

HM-5

Same as above but for Drake and other packset portables with SO-239 fittings.

NEW ASCOM® TOWERS

High strength, low maintenance aluminum towers for HF and VHF antenna installations. There is a complete line of ASCOM self-supporting towers — in heights from 30 to 90 feet — at attractive prices!

*Measured over a ¼ wavelength whip

WRITE FOR FREE AMATEUR ANTENNA
and/or TOWER CATALOGS




© "Stripes of Quality"

**the antenna
specialists co.**

Division of ORION INDUSTRIES, INC., 12435 Euclid Ave., Cleveland, Ohio 44106

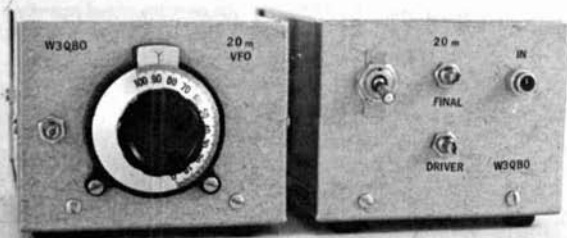Export: 2200 Shames Dr., Westbury, L.I., New York 11590 Canada: A. C. Simmonds & Sons, Ltd.



low-power solid-state vfo transmitter for 20 meters

Complete construction
details for
a two-watt
QRP transmitter
and Vackar vfo
for CW operation
on 20 meters

C. Edward Galbreath, W3QBO, 8326 Still Spring Court, Bethesda, Maryland

This article describes the construction of a 20-meter solid-state transmitter using a jfet Vackar vfo with a power output of two watts. This QRP transmitter has been used successfully for several months in many contacts, ranging geographically from New Zealand to the USSR. This has been done in a relatively few hours of operating time and — surprisingly — without the benefit of a beam; I use a 130-foot dipole, center-fed with open-wire line.


This past winter my kilowatt friends, skeptical as usual, challenged me to get on the air and try to work DX in a DX contest with this rig. I accepted their challenge, and despite lack of contest experience, I gave it a try for about two hours one afternoon during a recent DX contest. To the astonishment of all concerned I worked VP9HC, OK1TA, HB9KC, I5CFY, HA5KBM and I3ASE. Such accomplishments are only mentioned to show what can be done with two watts — I hope that more amateurs will give QRP a try.

The transmitter is built as two units, each in a 3x4x5-inch Minibox. The vfo, with the three buffer stages, is housed in a separate box only to meet my own

needs. The entire transmitter can easily be built in a single Minibox of appropriate size if you prefer.

vfo

The schematic of the vfo is given in fig. 1. Except for the values of the oscillator's frequency-determining components and the addition of a buffer-amplifier stage, the circuit is the same as that used in my 80- and 40-meter versions.¹ The two buffer stages and the buffer-amplifier provide excellent isolation of the oscillator from the driver and final. There is only a slight frequency pull by the final amplifier even though the transmitter operates straight through.

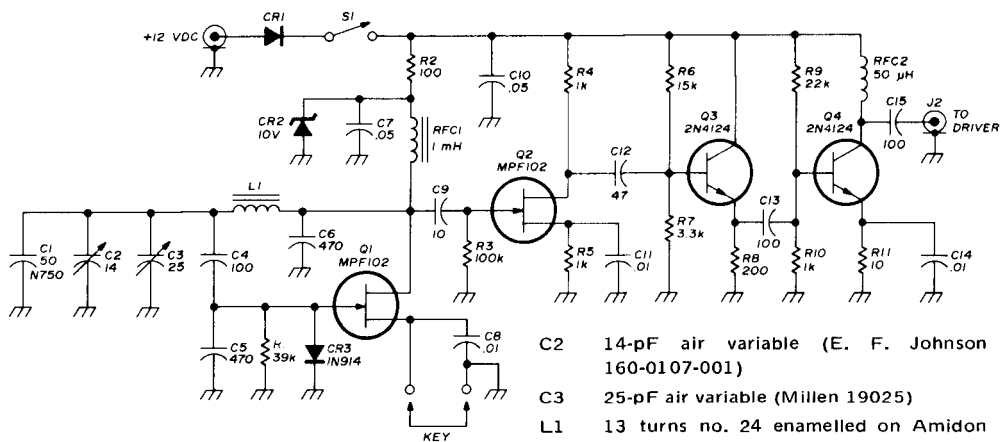

C1 50-pF, N750 temperature coefficient ceramic

tor, C1, is mounted on variable capacitor C3.

A clamping diode connected between the gate of Q1 and chassis ground has been added to the oscillator circuit. Wes Hayward, W7ZOI, when observing the gate voltage of an MPF102 on a high-frequency oscilloscope, found that, without the diode, the gate potential increased to the power supply potential on positive peaks.² The diode limits positive excursions to +0.7 volt, thus preventing conduction in the gate of the jfet and possible instability of the oscillator stage. Any small silicon diode such as a 1N914 will do the job.

All components of the oscillator stage

C2 14-pF air variable (E. F. Johnson 160-0107-001)

C3 25-pF air variable (Millen 19025)

L1 13 turns no. 24 enamelled on Amidon T-50-2 toroid core

RFC1 1-mH rf choke (Millen J300-1000)


RFC2 50- μ H rf choke (Millen 34300-50)

fig. 1. Circuit for the solid-state 20-meter vfo which tunes from 14.0 to 14.2 MHz is based on the very stable Vackar design. Protective diode CR1 is any silicon rectifier.

Frequency pull is so slight that there is no need to compensate for it when zero-beating a signal with the driver and final turned off.

The feedback inductor, L1, consists of 13 turns of number-24 enamelled wire, wound tight and evenly spaced on an Amidon T-50-2 toroid core. To assure short leads, the inductor is mounted on a perforated board on a standoff insulator between the tuning capacitor, C3, and the front panel of the Minibox. The leads are connected to soldering lugs. The negative temperature coefficient ceramic capaci-

except the inductor, variable capacitors and the negative temperature coefficient ceramic capacitor, C1, are mounted on two terminal strips: a 5-tie-point strip and a 3-tie-point strip. The center tie point is grounded in each case. The two terminal strips are mounted in line as a single 8-tie-point unit. This represents a constructional change from the earlier 80- and 40-meter versions and permits easy assembly of the components on the two strips as a unit before attaching them to the chassis. One simple way to do this is to bolt the terminal strips to a narrow

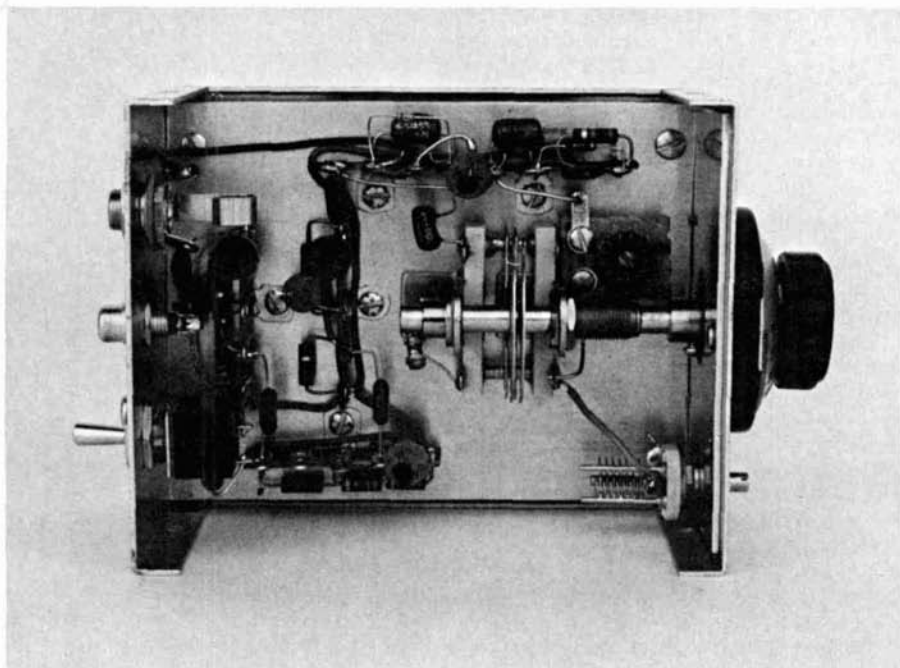

Layout of the vfo and buffer stages. Inductor L1 is mounted on the perf board just above the main tuning shaft. Transistors and other components are mounted on terminal strips. Key jack, on-off switch and output connector are mounted on rear panel, to the left.

piece of aluminum just as they would be mounted on the chassis. This unit can then be held in a vice while you attach the components.

To strengthen the Minibox, an aluminum chassis is built into it. The ends of the chassis are cut from half inch right angle aluminum stock available in most hardware stores. The aluminum angle strips are attached to the front and back panels at the base of the box and an aluminum plate is bolted to them. This chassis can be removed from the Minibox after fitting for easy assembly of the terminal strips, the tuning capacitor and the inductor.

A piece of aluminum is used to reinforce the front panel. It is held in position in the box against the front panel by the machine screws that fasten the chassis in place and by the dial and the trimmer capacitor, C2. Be sure that this piece, as well as the chassis, are cut just small enough to permit the cover to slip on the box. The extra reinforcement may be omitted, however, if the addi-


tional strength and rigidity are not desired.

A two-inch vernier dial is used to adjust the main tuning capacitor. It is a common item found in many radio stores but can also be ordered by mail. Holes for the dial can be marked for drilling only after the chassis has been fitted and the main tuning capacitor is in place. A key jack, two phono jacks and an on-off switch are mounted on the rear panel. One phono jack is for battery or power supply leads, the other for rf output.

driver and final

A Motorola 2N4124 transistor is used to drive an RCA 2N5189 in the final amplifier to 2 watts output (see fig. 2). Both transistors are inexpensive, priced in the 70 to 80 cent range. The 2N5189 is a very efficient transistor but it seems to have been overlooked by amateurs.

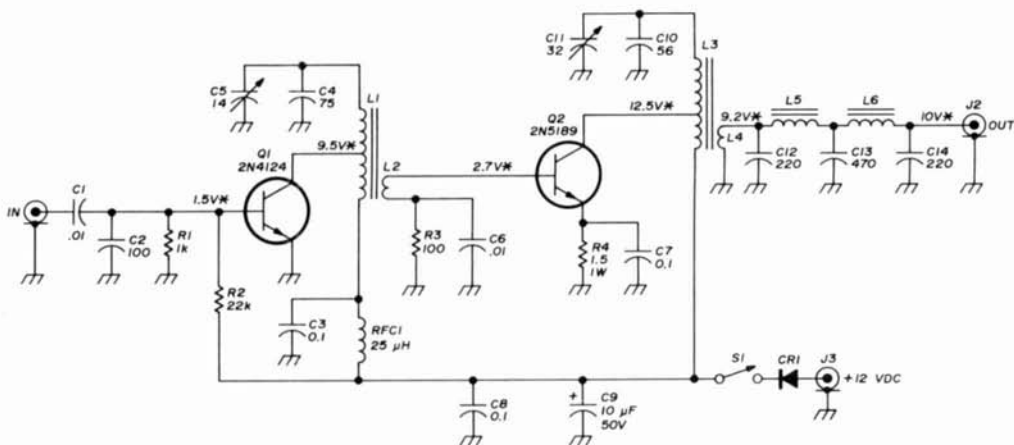The 2N4124 driver operates as a class-B amplifier with its base biased to approximately collector-current cutoff. With no signal applied to the base, col-



- C5 14-pF air variable (E. F. Johnson 160-0107-001)
- C11 32-pF air variable (E. F. Johnson 160-0130-001)
- L1 16 turns no. 24 enamelled on Amidon T-50-2 toroid core, tapped 6 turns from B+ end
- L2 2 turns small insulated wire wound over B+ end of L1

- L3 16 turns no. 20 enamelled on Amidon T-68-2 toroid core, tapped 3 turns from B+ end
- L4 3 turns small insulated wire wound over B+ end of L3
- L5 11 turns no. 20 enamelled on Amidon L6 T-50-2 core
- RFC1 25-μH rf choke (Millen J300-25)

fig. 2. Solid-state driver and final provides 2 watts output on twenty meters. The voltages marked with an asterisk are the rms rf voltages at those points. Protective diode CR1 is any silicon rectifier.


lector current is near zero, thus minimizing current drain during key-up condition. As a class-B amplifier, the stage is easier to drive than if operated class-C. A capacitor divider consisting of C1 and C2 provides the correct impedance match between the vfo and the base of the 2N4124.

A fixed-tuned tank circuit is used in the driver stage. Once the tank is correctly adjusted for maximum output in the center of the CW portion of the band, no further adjustment is required. The primary, L1, of the tank coil is tapped 6 turns from the B+ end to assure a proper low-impedance match for the collector of the 2N4124. Two capacitors are used to tune L1, a 75-pF dipped mica and a miniature variable, C5, which is mounted on the front panel.

The secondary of the driver tank, L2, consists of two turns of small insulated wire wound over L1 at the B+ end. This provides a low-impedance match to the base of the 2N5189. A 100-ohm resistor

in series with L2 and chassis ground helps protect the 2N5189 from damage.

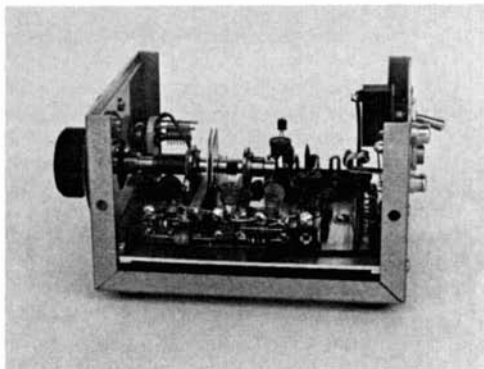The tank circuit of the 2N5189 final is similar to that of the driver stage. The collector is tapped to L3 at 3 turns from the B+ end. The variable capacitor, C11, is mounted on the front panel directly above C5. A double-pi network consisting




The vfo and buffer stages are built into a 3x4x5-inch Minibox. Extra chassis stiffness is provided by the 1/16-inch aluminum sub-chassis and panel stiffeners.

of L5, L6, C12, C13 and C14 is used in the output to assure good harmonic attenuation.

construction

Construction of the driver-final unit is similar to that of the vfo. An aluminum

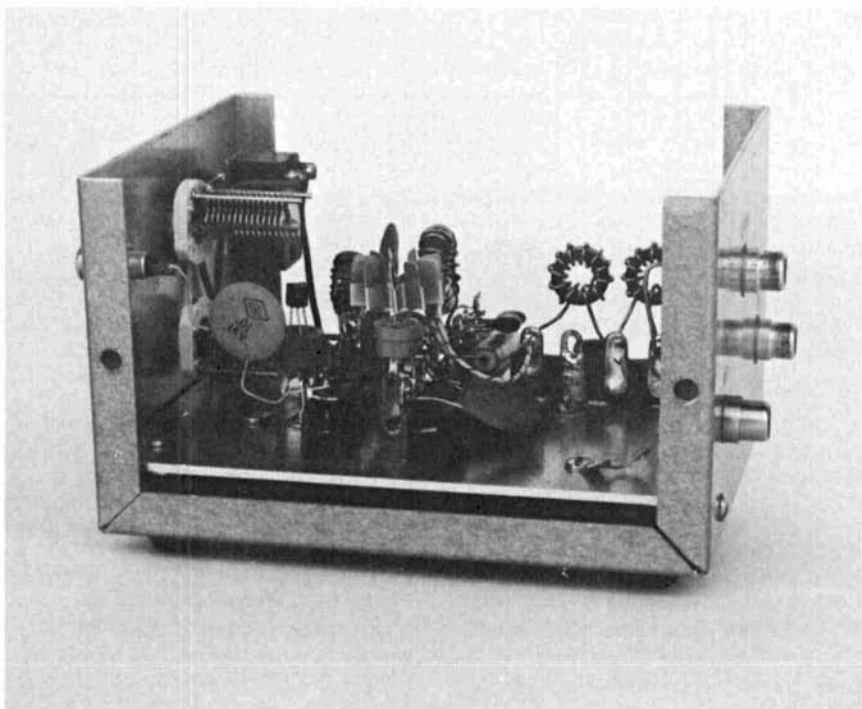The Minibox should now be drilled for the on-off switch, input jack and the two miniature variable capacitors on the front panel and the output jack and the B+ jack on the back. You may also want to include an antenna jack for connection to the receiver if one antenna is used for



Like the vfo, the driver and 2-watt output stage are built into a 3x4x5-inch Minibox. Transistor Q2, a 2N5189, is provided with a clip-on heat sink.

chassis is cut and fitted inside the Minibox using 1/2-inch right-angle stock and a piece of flat aluminum cut slightly smaller than the bottom of the box to permit the cover to slide in place. The chassis is then removed and all the components except the variable capacitors are mounted on it out of the box.

Components of each stage are mounted on two terminal strips — one 5- and one 3-tie-point strip — arranged as an in-line unit. The driver stage is near the front. The double-pi network is mounted at the back on a 4-tie-point terminal strip. This arrangement permits orderly assembly of components and short leads.

both transmitting and receiving. This jack should be connected to the transmitter output through a 68-pF capacitor, with reversed silicon diodes to ground on the receiver side of the capacitor to protect the receiver against damage.

testing


Check both units for possible shorts to the chassis before connecting them to a power supply (and before inserting the transistors, if you use sockets). If the units pass the short test — B+ to chassis — then insert the transistors and connect the output of the vfo to the input of the driver-final using a short, shielded jumper

cable. Output of the final should be attached to a 50-ohm dummy load; a two-watt resistor works well.

The units require 12 volts dc. I use a separate 12-volt lantern battery for each unit so as to contribute toward good voltage regulation for the vfo.

with your multimeter. If you have a sensitive reflected power and swr bridge meter, check for output. Adjust the front panel trimmer capacitors for maximum power output at the midpoint of the CW portion of the band.

This completes the adjustments and

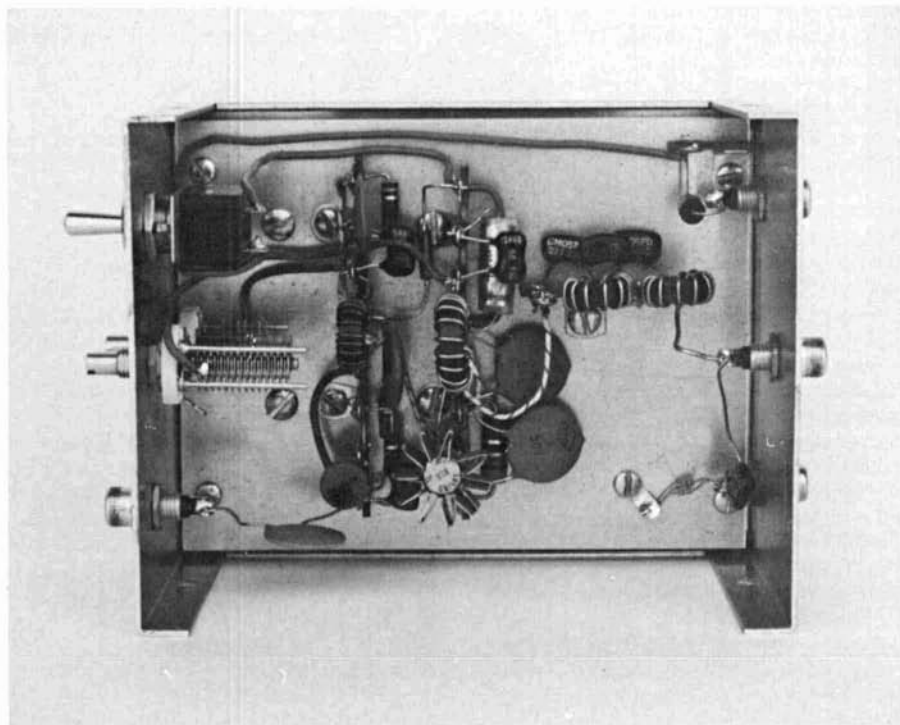

Layout of the driver and power output stages. All components are mounted on terminal strips. Tank circuits L1/L2 and L3/L4 are mounted just to the right of the air variable. Inductors L5 and L6 are mounted on another terminal strip near the rear panel.

Now, turn on the power supply switch for the vfo and, while keying, listen for the signal in your receiver. When you have found the signal, set the dial for full capacitance of the tuning capacitor and use the air trimmer to set the low band-edge at 14 MHz.


Next, turn on the driver-final unit and again key the vfo. You should now hear a stronger signal. If you have an rf probe and a vtvm, you can check for rf voltages at points given in the schematic. If you do not have an rf probe, rectify the rf output with a germanium diode and capacitor and read the rectified voltage

checking. The transmitter is ready to be put on the air. An antenna tuner is strongly recommended for matching the transmitter to the transmission line and for additional attenuation of harmonics. The extra resonant circuit provided by the antenna tuner also helps in receiving.

references

1. C. E. Galbreath, W3QBO, "A VFO for Solid-State Transmitters," *ham radio*, August, 1970, page 36.
2. Wes Hayward, W7ZOI, "A Second Generation MOSFET Receiver," *QST*, December, 1970, page 12.

ham radio

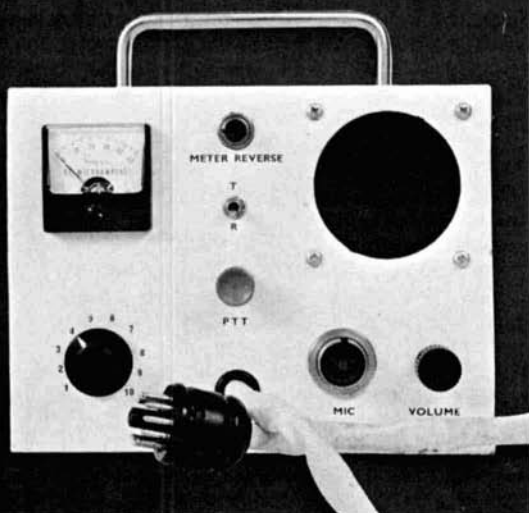

test set

for Motorola radios

Complete construction
details for
a test set for
most Motorola
business-band
fm radios


David L. Marshall, KØBKD, Albuquerque, New Mexico

Today is the day of vhf-fm communications. Although there are many amateur-band fm transceivers in use, retired business-band fm sets still hold a sizable portion of the market. This is due to their increased reliability resulting from their ruggedized construction suited to a mobile environment. Another reason is their reduced cost.

One minor disadvantage with old business-band radios is that they usually require specialized test equipment to keep them operating. The average amateur has no way to maintain his own equipment and has to rely on a friend in the two-way radio business. This is fine until the radio quits and test equipment is not available for one reason or another. In my opinion, half the fun of ham radio is maintaining your own equipment.

In this article I will describe a simple but comprehensive test-set for Motorola fm radios. Although you can buy a readymade test-set from Motorola, they cost about \$250, which is a bit expensive

AMPHENOL 86-PM77

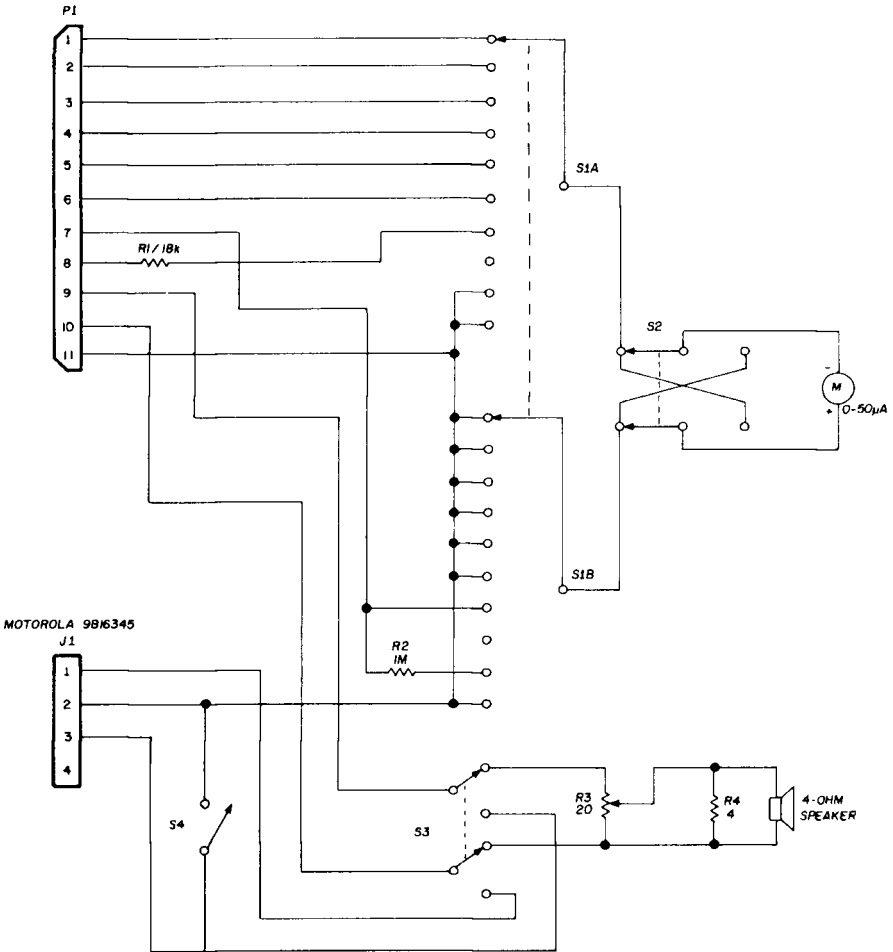

M1 50 μ A meter (Simpson 1212)

R1 18k, 1/2 watt, 5%

R2 1 megohm, 1/2 watt, 5%

R3 20-ohm potentiometer, 5 watt

R4 4 ohms, 2 watt

S1 2 pole, 10-position, non-shorting

wafer switch (Centralab PA-1005)

S2 snap-action, momentary contact

dpt switch (Alco MSPE-206R)

S3 miniature dpt toggle switch (Alco

MST-205N)

S4 spst momentary contact switch

fig. 1. Circuit for the test set for Motorola vhf-fm radios. Adapter cable for Motrac sets is shown in fig. 2.

for a piece of equipment that isn't (hopefully) used too often.

Fortunately, many years ago Motorola showed great insight by designing their radios to be compatible with a universal test-set. Today, the same test-set will

align 80Ds, 140BYs, Twin-Vs, T-Powers, utility base stations, Motracs, Motrans, Mocoms and Micors. There are many different models included under these different generic names so it is obvious that a test-set is a most handy piece of

equipment to have, regardless of what Motorola radio you may have. The few exceptions are the H23XXX hand-carry, the HT-200, the HT-220, the PT-200, PT-300, etc. Due to space limitations, these sets do not have meter sockets and are aligned with a volt-ohm-meter.

described here. Another useful addition to the basic test-set is the provision for transmitter push-to-talk and a microphone connector. These items are extremely useful when you are working on a transmitter with a remotely located microphone.

Although there is nothing critical about the construction of the test-set, there are a few considerations which are worthy of mention. From experience I have found that a cable about three feet long is optimum. To align Motrac, Motran, Mocom and Micor radios an adapter is necessary. This converts the normal eleven-pin test-set plug to a plug similar to a nine-pin tube except that it has four pins in the center. EECO logic modules have this kind of plug, or the adapter can be purchased from Motorola (TKN6025A, price \$9.50). If you do not anticipate working on any of these radios this adapter is not needed as the earlier radios used an eleven-pin socket which is compatible with the test-set plug.

Another area of flexibility is in the meter reversing switch. It can be incorporated into the selector switch so that position +4 is normal and position -4 is reverse. Since the reversing switch is used only for discriminator alignment it is recommended that the meter reversing switch be a separate pushbutton switch so that it is not necessary to switch through the reverse position every time. It is also recommended, for reliable operation, that the switch be a good quality, snap action microswitch. Quality switches are a must since changes in contact resistance, encountered with inexpensive switches, can change meter readings.

The selector switch should be a non-shortening type, also of good quality. I happened to use a shorting-type switch because I had it on hand; however, when using a shorting-type switch, if the unit is switched while measuring PA plate current, the power supply fuse will blow because of the momentary short circuit.

The fm test-set will be only as good as the meter, so a good quality meter movement is a must. I recommend using a Simpson meter since Motorola uses this

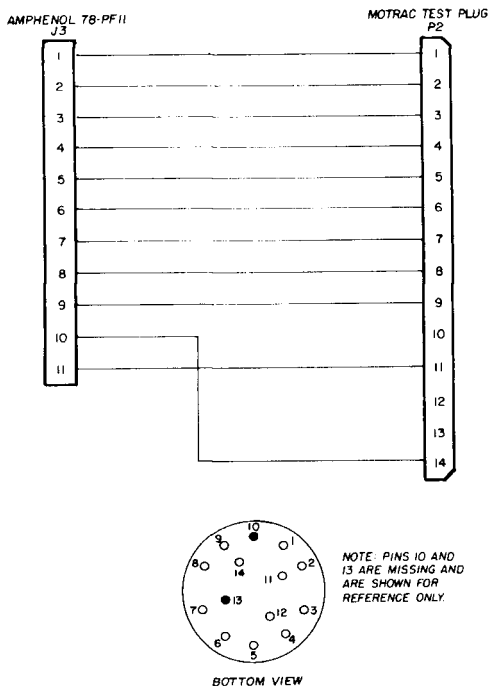


fig. 2. Motrac adapter cable for use with the test set shown in fig. 1. In the bottom view of the Motrac test plug, solid dots are pins, open dots are holes.

test-set

The basic test instrument for checking Motorola radios is a 50- μ A meter. By switching in suitable multipliers, a volt-meter can be built which will monitor all test points. There are two additions to this basic meter which make it even more valuable. One is bringing the receiver audio out to a speaker built into the test-set. This facilitates working on trunk-mounted radios where the normal speaker is some distance away. In the commercial version there is also an audio voltmeter used for making signal-to-noise measurements. For reasons of simplicity this feature was not included in the unit

type in their test-set so the difference in internal resistances should be small. Also, the largest available meter should be used to get the maximum needle swing — some of the indications are quite small.

The microphone connector is a special connector similar to an Amphenol 91-PC4F. Occasionally these can be found on a junked Motorola control head. If you can't locate an old one, connectors can be ordered from Motorola (9B16345, price \$.95).

I built my test-set into a Bud CU-3009A Minibox, 3½ x 6 x 8 inches. This size is large enough to allow for modifications such as a larger meter, yet is small enough to be easily portable. The unit has seen a great deal of service in mobile maintenance and working on repeaters. It has always been easily portable.


motorola alignment

For those of you who are not fortunate enough to own a manual on your particular radio, receiver alignment is very straight-forward. However, because of the different number of multiplier stages used in the various frequency ranges, Motorola has chosen to base the alignment on the power amplifier stage. The PA plate is always position seven. The PA drive is position six, the last multiplier is position five, etc. In a low-band radio the switch will go back only to position four. A uhf radio will go back to position one.

Receiver alignment is started by aligning the discriminator for a zero output with an on-frequency signal. There are several methods in use, but generally the primary is peaked with the secondary detuned and then the secondary is tuned for a zero voltage output. It is best to use a 455-kHz signal rather than relying on a received signal. When this is done the 455-kHz i-f stages are aligned again using a 455-kHz signal. The signal level should be kept below the point of saturation on meter position one. If the receiver is badly detuned, position two may be used for a more sensitive indication.

The 12-MHz i-f is aligned by coupling a signal at 12 MHz to the first mixer. The

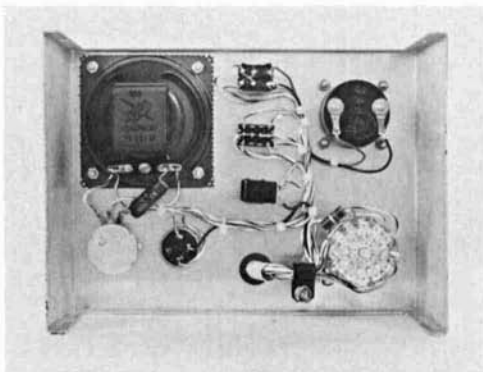high i-f is then aligned again using position one. At this point an on-channel signal should be copiable, even though weakly. Using this on-channel signal, the rf amplifier should be aligned. When this is done the signal should be further reduced and, using position two, the



All components for the Motorola test set are mounted behind the front panel.

complete alignment should be touched up for the best sensitivity.

The final step in the alignment procedure is to adjust the received frequency. This is done by adjusting the first oscillator trimmer for a zero-voltage indication at position four.

Transmitter alignment is simply a matter of tuning each stage for maximum meter indication with the exception of position seven. Position seven is adjusted for a dip in the PA plate current as in any class-C stage. If the loading and coupling controls are adjusted for maximum and then backed off to about 80% the output power will be reasonably close to what Motorola recommends for that particular radio. The final step is to adjust the transmit frequency. I use a 30-MHz frequency counter coupled to the output of the phase modulator. It is important not to load the oscillator as this will change the frequency when the counter is removed. By using a one-second time-base on the counter, you will obtain accuracy that is entirely adequate for amateur vhf operation.

ham radio



variable-shift RTTY terminal unit

And now the VS-1 —
with continuously variable
filter tuning
for improved response
in noise
and interference

Keith Sueker, W3VF, 110 Garlow Drive, Pittsburgh, Pennsylvania


Phase 1 of my RTTY experience began with the gift of a Model 26 Teletype machine from Mac McKinley, W30B. During my first attempt to print something off the air, a simple single-tone detector and vacuum-tube keyer were used.¹ This system worked but with poor results in noise and interference. At this point I began to learn something about TU problems and their solutions.

Phase 2 was introduced by a version of Irv Hoff's ST-5,⁵ which was modified to use tone pairs of 1000/1170 Hz and 1000/1850 Hz for narrow and wide shift respectively. These frequencies were chosen to allow the sharp CW selectivity in my SB-300 to be used for narrow shift without cluttering up the receiver with an odd-frequency BFO crystal for RTTY. This system unit worked well enough to allow some 20 meter DX.

Phase 3 began with some serious considerations of how to build a better TU in terms of noise and interference response. Advanced design units, such as the ST-6⁶ with switched discriminator filters, do an excellent job on narrow shift but have an excessively broad response for marginal

receiving conditions on wide shift. The phase-locked loop units⁷ have the same problem, since they are subject to interference through the whole lockup range of the vco. A solution is to use sharply tuned filters, in or ahead of the discriminator, which will pass only the individual tones of interest and their sidebands. When fixed-tuned filters are used, however, one runs into the problem of various amateur shifts and the many commercial stations that use shifts other than 170 and 850 Hz.

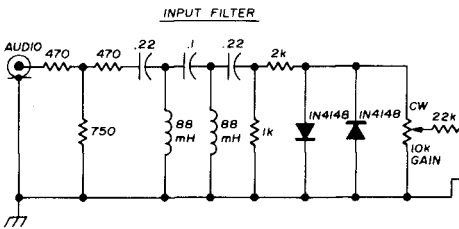The ST-6 discriminator filters at 170-Hz shift are about as narrow as one might wish to use. The 850-Hz shift



filters, however, are broad enough to provide a linear discriminator characteristic over 850 Hz. If we sharpen these filters, we can reduce the interference bandwidth, but we still must cope with the various intermediate shifts in use. Why not make one of the filters with a continuously adjustable center frequency? Then we can tune any shift.

the VS-1 TU

The filters are the key to the whole project. If one filter were continuously tunable, what kind of filter and tuning system could be used? Active filters using RC networks are popular, but high Q requires critical feedback adjustment and stability is questionable with simple techniques. Toroidal LC filters using 88-mH inductors provide excellent Q, but how

does one tune such a device? To accommodate the shift range between 170 and 850 Hz, one filter must be varied nearly 700 Hz — a task clearly impossible for an ordinary variable capacitor. Also, resistive loading would have to be continuously variable to keep the noise bandwidth matched to the fixed filter.

The solution to these and other problems turned out to be relatively simple: both audio tones were increased to higher frequencies so that one of the filters

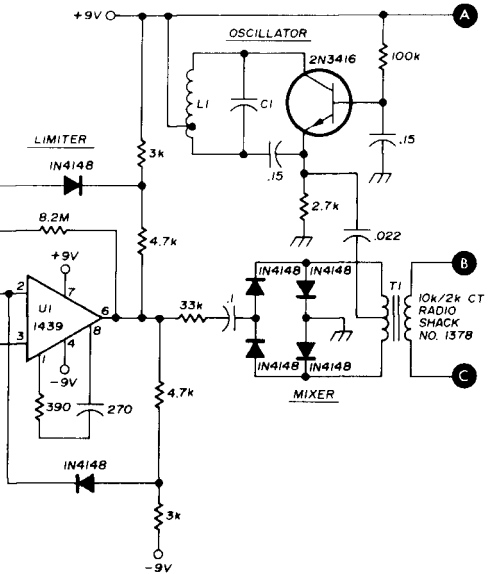


fig. 1. Input circuit and mixer for the RTTY terminal unit. For values of L1 and C1, see text.

could be tuned with a variable capacitor. Some calculations showed that a frequency of about 11 kHz would allow a sufficient tuning range with a 365-pF capacitor. At 11 kHz, the tuning range would be less than ten percent of center frequency, providing good noise balance without compensation.

By going to a high frequency, the absolute bandwidth would be increased by some four times over that obtainable

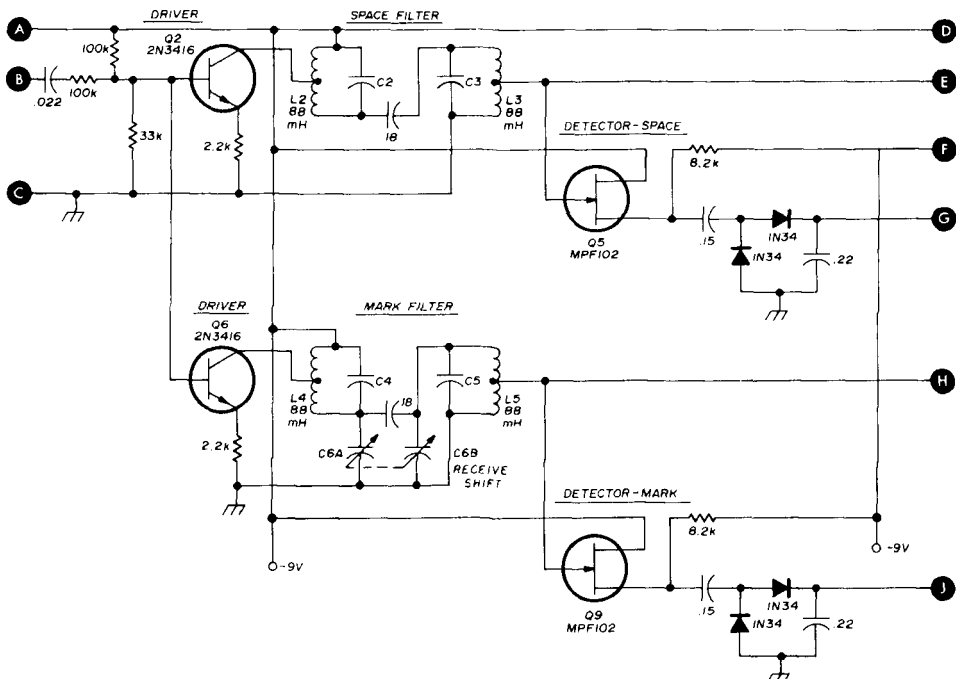


fig. 2. Mark - space filters and detectors for the RTTY terminal unit. For value of tuning capacitors, see text.

at the usual audio tones. This problem was resolved by using two filter sections with loose coupling and a dual-section capacitor for tuning. The selectivity turned out to be ideal.

input circuit and mixer

Whether using fm or limiterless a-m detection, it is important to restrict incoming audio to the frequencies of interest. Most modern receivers have i-f filters with sufficient high-frequency cutoff. However, the low-frequency response should extend no lower than the bottom of the i-f passband. Hence, a high-pass filter is used on the VS-1 input to reduce hum and noise (fig. 1). Toroidal 88-mH inductors are used, and the filter is designed for a low-frequency cutoff of 1000 Hz. The input pad allows satisfactory operation from any receiver output impedance. Measured attenuation is 1 dB at 1000 Hz, 13 dB at 700 Hz, 29 dB at 500 Hz, 38 dB at 300 Hz, and more than 40 dB for lower frequencies.

Op-amp U1 and the associated circuit form a high-gain stage, which can be operated as a linear amplifier or a symmetrical clipper (limiter) by varying the input gain control. The gain control could be replaced by a switch as in the ST-6; but a control provides more audio range.

Once the audio tones have been amplified and/or clipped, they are heterodyned to the filter frequencies by the local oscillator and balanced mixer. The oscillator is a Hartley circuit with a tap on L1, which is made by unwinding 50 turns from an 88-mH toroid, attaching a lead, and rewinding the turns in the same direction. Capacitor C1 tunes the oscillator to the desired injection frequency. (More about this later.) Use of an 88-mH toroid ensures that the oscillator and filters will track over a wide temperature range. The balanced modulator is conventional. It uses unmatched diodes and is coupled to succeeding stages through an inexpensive transistor interstage transformer.

filters

Transistors Q2 and Q6 are filter drivers (fig. 2). The high collector output impedance, coupled with feed at the center tap of the toroid, results in negligible filter loading. Each filter consists of two LC sections using 88-mH toroids with loose coupling provided by the 18-pF capacitors. Space filters L2,C2 and L3,C3 are fixed-tuned to the heterodyned space frequency. Mark filters L4,C4 and L5,C5 are identical to the space filters except for the dual variable tuning capacitor, C6, which tunes the filters to the heterodyned mark frequencies.

frequency selection

Up to this point discussion of the frequencies has been rather vague. This TU is basically a superhet receiver with dual i-f channels, one of which can be tuned. A nominal i-f must be used that can be varied by the frequency difference between maximum shift (usually 850 Hz) and minimum shift (usually 170 Hz) with a ganged capacitor of reasonable size. For a shift difference of 680 Hz and a dual 365-pF broadcast capacitor, the minimum possible filter frequencies are about 11,000 Hz and 11,680 Hz for the tunable filter. If the other filter is set at either 10,830 Hz (11,000-170 Hz) or 11,850 Hz (11,680 + 170 Hz), the entire range of shifts from 170 Hz to 850 Hz can be tuned with the variable capacitor.

space and mark. Common practice in amateur RTTY is to shift frequency down for space. If the receiver sharp filter is to be used, the lower of the two audio frequencies must fall at the lower end of the sharp passband — about 950 Hz in the Heath SB series. Narrow shift then has

table 1. VS-1 frequency relationships.

	frequency (Hz)	
	170 shift	850 shift
audio space	950	950
audio mark	1120	1800
oscillator	9880	9880
space filter	10,830	10,830
mark filter	11,000	11,680

space at 950 Hz and mark at 1120 Hz, while wide shift has space at 950 Hz and mark at 1800 Hz for reception on USB. If LSB is used, the frequencies will be inverted. Since the space frequency is fixed for USB reception, the mark filter should be tunable.

We have defined 11,000 Hz to 11,680 Hz for mark frequencies and 10,830 Hz or 11,850 Hz for space. At this point I chose 10,830 Hz so that (a) 170 Hz would fall at the maximum (counterclockwise) setting of C6, and (b) the dial could be calibrated clockwise in increasing shift frequency. The local oscillator must be tuned to the heterodyned space frequency of 10,830 Hz minus the audio space frequency of 950 Hz for a resultant

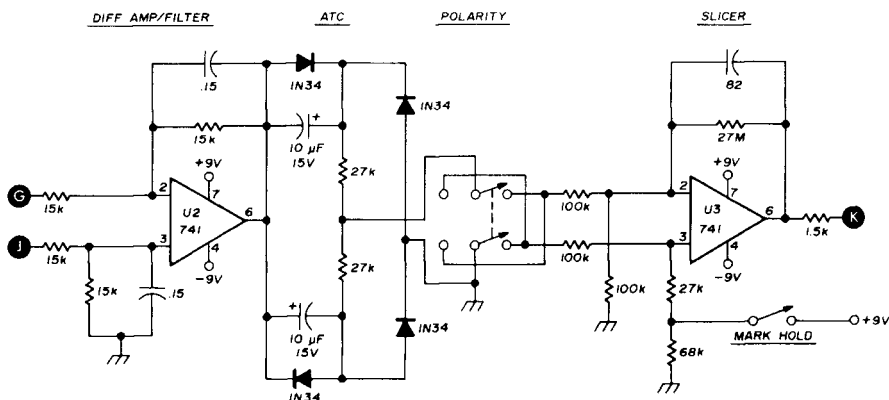


fig. 3. Schematic of the automatic threshold corrector (ATC) and slicer.

of 9880 Hz. Table 1 should make things a little less confusing.

oscillator tuning. The frequency conversion process has been described in some detail, because oscillator tuning must match the receiver bandpass characteristics, and some adjustments may be needed. Also, the oscillator can be moved in frequency to match the more usual tones of 2125 and 2975 Hz for 850-Hz shift if desired. An understanding of the

tial stage, which further squares the keying pulses and adds more filtering. It also has a mark hold input to lock up the keyer for transmitting. In my equipment, this switch is located next to the machine keyboard, and another pole is used to actuate the transmitter. Three positions are used: "Print," "Mark-hold," and "Transmit."

keyer and FSK

Transistor Q10 (fig. 4) drives the

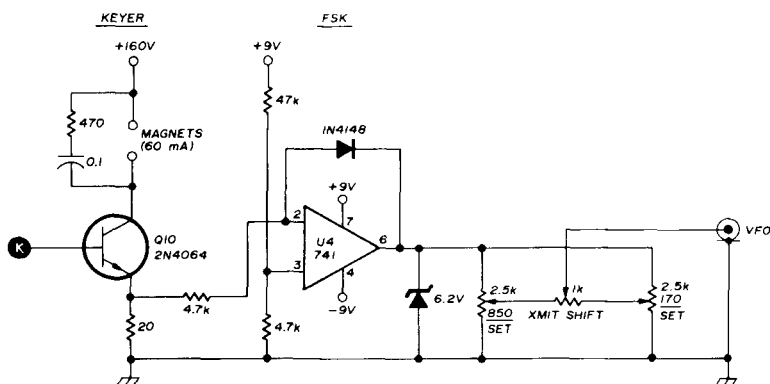


fig. 4. Circuit for the keyer and frequency-shift keyer used in the VS-1 RTTY terminal unit.

conversion process is necessary to customize this portion of the VS-1. Oscillator tuning can be by means of a front panel control if several different audio frequencies must be used. The filter frequencies may also be increased if a wider range of shifts must be accommodated, but selectivity will suffer.

detectors, ATC, and slicer

Source followers Q5 and Q9 provide stiff drive sources for the detectors while presenting negligible load to the filters (fig. 3). Mark and space detectors are identical voltage doublers using germanium diodes for low voltage drop. The outputs are combined in differential amplifier U2, which also provides some filtering. Filter time constants allow transmission rates to 100 wpm. ATC circuitry following the amplifier is from the ST-6, as is the polarity reversing switch. The slicer, U3, is another differen-

parallel-connected magnet circuit at the 60-mA level. The 20-ohm resistor in the emitter return provides a signal to the FSK circuit to detect mark current when the keyboard is actuated for transmitting. The mark signal is sufficient to drive U4, the FSK stage, sharply to zero from its "on" biased state. On space signals, it snaps back on to full output.

FSK control is simple but effective. The positive output voltage of U4 is clipped at +6.2 V nominal by the zener, and the feedback diode limits negative excursions to a negligible value. Thus, we have established two regulated voltages: +6.2 V for space and zero volts for mark. The two divider pots set the end points for the shift pot, so that a continuously variable positive space voltage can be supplied to the transmitter vfo. Note that the shift voltages are not affected by loop current or contact resistance in the keyboard.

Any of the usual transmitter FSK schemes can be used as long as the voltage requirement does not exceed 6.2 V. Mark and space can be inverted by simply inverting the inputs to U4. Output polarity can be reversed by reversing the feedback and zener diodes.

Keying turned out to be simple on my SB-401. The shift pot is connected across the vfo sideband selector diode. The diode is supplied from a high-resistance circuit, and the low output resistance of

used, because the waveforms at the sources of Q5 and Q6 are affected by detector loading. The 2N5550 transistors will deliver about 100 V p-p, which is enough to drive most small CR tubes. Both deflection channels are direct coupled to eliminate trace jumping from noise or overload. The variable bypass circuits in the emitters provide gain control independent of positioning. My VS-1 uses a 1EP1 CRT, but only because I found one at a hamfest for five bucks.

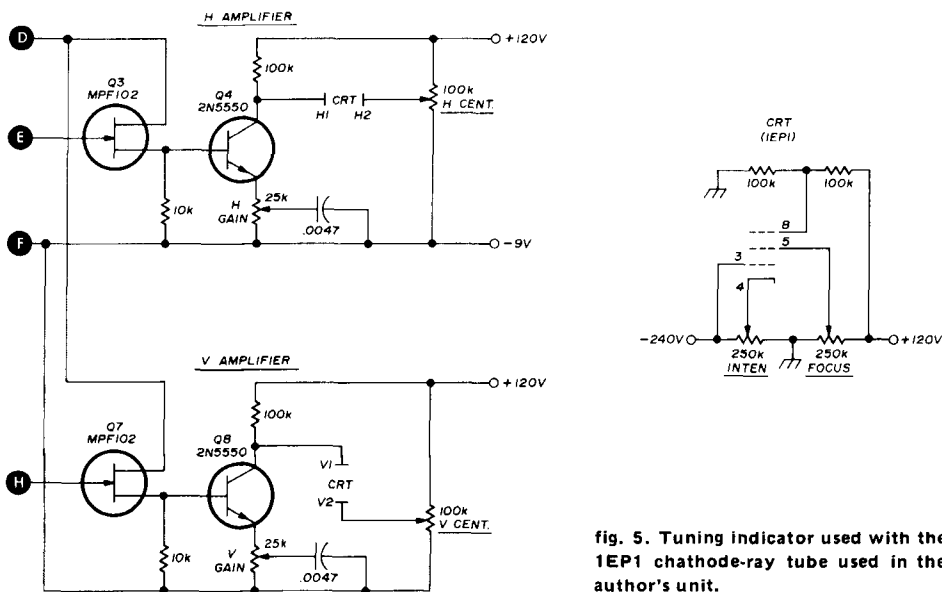


fig. 5. Tuning indicator used with the 1EP1 chathode-ray tube used in the author's unit.

the shift pot shorts out the normal bias and sets a new level in "transmit." The actual shift depends slightly on vfo tuning, but it is essentially constant over the usual RTTY frequencies, so the shift pot can be calibrated directly in shift frequency from 170 to 850 Hz. The control shown in the photos is a standard pot equipped with a homebrew stop at 180 degrees.

tuning indicator

AC outputs from the filters are isolated by source followers Q3 and Q7, which drive deflection amplifiers Q4 and Q8 (see fig. 5). Separate isolators are

These tubes are too expensive to buy new. Any of the small oscilloscope CR tubes can be used with equal success.


power supplies

Power for the dc loop and low-level stages is derived from a Stancor PS8416 transformer (fig. 6). Although rated for only 25 mA on the dc output, the lack of appreciable loading on the 6.3-V winding keeps transformer temperature reasonable. The 2-μF capacitor provides a higher inrush current on mark signals and allows the average mark hold current to be reduced to 50 mA without degrading print quality.

Low voltages are generated by a pair of voltage doublers and 9.1-V zener diodes. There is nothing mysterious about this arrangement; any low-ripple power supply would work as well. A pair of 6.3-V filament transformers provide an isolated supply for the CRT heater and dc supplies for the intensity, focus, and deflection circuits. Here again, any stand-

capacitor. If a CRT tuning indicator is used, the tube should be kept away from power transformers.

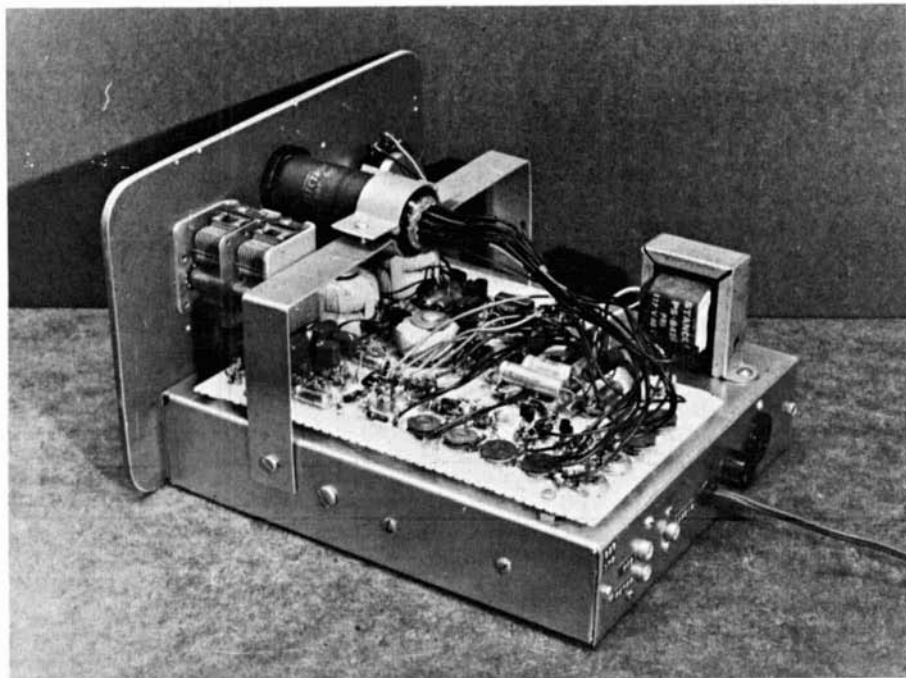Except for U1, which handles 10+ kHz signals, all op-amps can be garden-variety 741 types. These ICs are inexpensive and are exceptionally immune to damage. Dual units are available for about \$1.00 in TO-type packages from a number of *ham*



Construction of the VS-1 RTTY terminal unit. All circuits except power supply and keyer are mounted on a section of perforated circuit board. Power supply components are mounted under the chassis.

ard configuration⁸ could be used. However, the loop supply should not be used for accelerating or deflection voltage supplies, because the regulation causes trace problems.

construction and components

Few of the parts in this unit are at all critical, and the mechanical layout is not too important. Common-sense precautions should be taken to isolate filter input and output circuits, but no special bypassing or decoupling is required for stability. Leads to the mark tuning capacitor should be reasonably isolated to minimize coupling around the 18-pF

radio advertisers. Type 709 op-amps could be used, but they are more subject to latchup, require compensation, and will not tolerate output shorts.

Transistors and fets are also garden-variety types except for the high-voltage deflection and keyer units. The fets hang between the power-supply rails, so they should have voltage ratings of at least 20 V. Nearly any npn transistor can be used in place of the 2N3416s. Silicon diodes are low-leakage computer types, and the 1N4148 is suggested for those who must buy them. Power diodes can be any silicon types rated at least 0.5 A and of voltage ratings listed on the schematic.

Germanium diodes can be any rf type but should be checked for high leakage. Capacitor types are unimportant except for C1 through C6, which must be low leakage types such as mylar, polystyrene, or polycarbonate. Trim capacitors can be these types or mica. The total capacitance required at C1 through C5 is 0.002 to 0.003 μF .

Once the filters have been tuned, the oscillator coil should be tuned to roughly 9880 Hz. Next, run a steady signal through the receiver and adjust tuning until two incoming frequencies, 170 Hz apart, are centered in the narrow pass-band. Trim the local oscillator frequency in the VS-1 to place the lower audio frequency at the peak of the space filter.

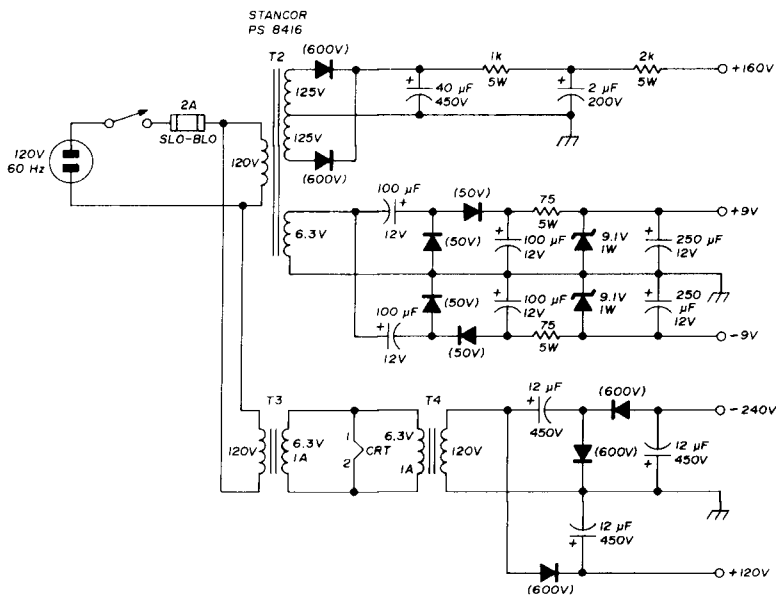


fig. 6. Power supply for the complete VS-1 RTTY terminal unit. Required PIV of diodes is indicated in parenthesis.

adjustments

After construction and wiring are completed, the usual dc voltage checks should be made. Assuming things look normal, the filters may then be tuned. A precise frequency source is not needed, since any errors in alignment will be compensated by the oscillator alignment.

Set the alignment generator to 10,830 Hz, add temporary 82-pF capacitors across L4 and L5, set C6 to maximum, and tune all sections for maximum output from Q5 or Q9. The unit may be fine tuned either by capacitor selection and trimming or by pruning turns. Remove padders, and filter alignment is complete. The variable capacitance of C6 provides the required frequency offsets.

It should now be possible to adjust C6 to place both space and mark signals at the peaks of their respective filters for any shift frequency from 170 Hz to 850 Hz. If a number of different receivers or different audio tones are to be used, a variable tuning capacitor can be used. A 730-pF unit will provide enough range.

modifications

Motor control and automatic mark hold circuits have been deliberately omitted from this unit, but they undoubtedly will be required by some operators. The tail-end circuitry of the VS-1 is sufficiently similar to the ST-6 so that the same circuit techniques are directly applicable. The power supply may have to

be beefed up to handle the additional load, however.

Some type of CRT display is definitely recommended, since the filters are much too sharp for hit-or-miss tuning. It may be possible to use one of the dual magic eye tubes, but it's doubtful if meter schemes are feasible.

The FSK system shown is by no means the only one that will work. Any of the standard techniques can be used for relay operation directly from the keyboard.



Station at W3VF. The design of the VS-1 is similar to the Heathkit transmitter and receiver used by the author.

For those interested in a hybrid scheme, the 741 at U4 will drive a high-sensitivity reed relay directly with a 12-Vdc coil. This will allow the VS-1 to be used with existing FSK installations. About 10-mA of current is available.

operation

Reception with the VS-1 requires accurate tuning and a reasonably stable receiver. The receiver is tuned to peak the space signal on the appropriate CRT axis, and the shift tuning is then varied to peak the mark signal. Selectivity may be a little scary at first, but only a poor receiver or a drifting transmitter will cause problems. The variations in shift are rather interesting to watch. Advantage should always be taken of the highest degree of receiver selectivity that will pass both space and mark signals.

performance

The VS-1 performs well. Filter selectivity is sharp enough to present a clean cross pattern on 170-Hz shift, and the print holds up until signals disappear into the noise. The ATC circuit works well at machine speed but can't cope with keyboard sending under poor conditions with severe signal fading, particularly for loss of the mark signal. A manual offset on the slicer would be required for this condition. Performance in interference is very good, and the improvement in print from using sharp receiver selectivity on 170-Hz shift is striking.

Despite the many words written about limiter/discriminator versus limiterless two-tone reception, the VS-1 shows little difference in print quality as the input gain is varied. Even under poor signal conditions, the limiter can be kept saturated with no increase in print errors. This condition is probably due to the narrow filters, but I'll leave that for others to comment on. The unit is a pleasure to operate, and it now occupies a permanent spot in my station. I hope this article serves to stimulate further work toward improvements.

references

1. *The Radio Amateurs Handbook*, 1969 edition, pp. 291-292.
2. Byron H. Kretzman, W2JTP, "The New RTTY Handbook," 1961, Cowan Publishing Company, New York.
3. Durward J. Tucker, W5VU, "RTTY From A to Z," *CQ*, August, 1964, through July, 1966.
4. Irvin M. Hoff, K8DKC, Series of articles in *QST*, January through October, 1965.
5. Irvin M. Hoff, W6FFC, "Mainline ST-5 RTTY Demodulator," *ham radio*, September, 1970, page 14.
6. Irvin M. Hoff, W6FFC, "Mainline ST-6 RTTY Demodulator," *ham radio*, January, 1971, page 6.
7. Paul E. Webb, Jr., W4FQM, "Phase Locked RTTY Terminal Unit," *ham radio*, January, 1972, page 8.
8. Anthony Sperduti, WB2MPZ, "Solid State RTTY Monitor Scope," *ham radio*, October, 1971, page 33.

ham radio



①

We guarantee you'll be satisfied with the complete line of Robot Slow Scan TV equipment.



②

① MODEL 70 A SSTV MONITOR

Displays amateur standard pictures from any SSTV audio source: station receiver, tape, camera. Six inch (diagonal) display.

Front panel controls for easy station operation. Connectors for receiver, transmitter, microphone, tape, waveform monitor, tuning indicator, and auxiliary demodulated SSTV output for external monitoring.

All solid state except cathode ray tube.

\$295

③ VIEWFINDERS

Choice of 4 inch diagonal (Model 60) or 6.5 inch diagonal (Model 61) display to fit your station.

Displays fast-scan video pictures to simplify setting camera focus and field of view. All solid state except cathode ray tube. Tripod mountable (Model 60 only).

Model 60: **\$249**

Model 61: **\$239**

⑤ VIEWING HOOD

Two piece detachable hood. Fits monitor bezel to block outside light.

\$25

CALIBRATION TAPES

Three inch reel or cassette tape recording aids setting monitors and cameras to SSTV standards.

Cassette **\$4**

Reel **\$3**

② MODEL 80 A SSTV CAMERA

Generates amateur standard SSTV pictures and fast scan video for viewfinders. Controls for contrast, brightness, vidicon beam, SSTV signal level, black/white reversal, 1/4-1/2 full frame selection.

All solid state except vidicon. All station cabling included; requires suitable C-mount lens.

\$295

④ LENSES

Lens	Focal Length in m.	Min. f stops (All 22 max)	Min. focus (in inches)	Price
A	12.5	1.9	10	\$ 49
B	25	1.9	24	\$ 25
E	25	1.4	6	\$ 54
F	50	1.9	42	\$ 43
G	150	3.2	96	\$ 79
H	18-90	2.0	60	\$220



④



③



All Robot equipment carries a one-year warranty. Four easy ways to purchase: cash, C.O.D., Master Charge, BankAmericard.

ROBOT

ROBOT RESEARCH, INC.
7591 Conroy Court
San Diego, California 92111
Phone 714-279-9430

Enclosed \$ _____ Please send the following equipment

via AIR or SURFACE

Name _____

Call _____

Address _____

City _____


State _____ Zip _____

California residents add 5% sales tax. Prices do not include shipping.



⑤

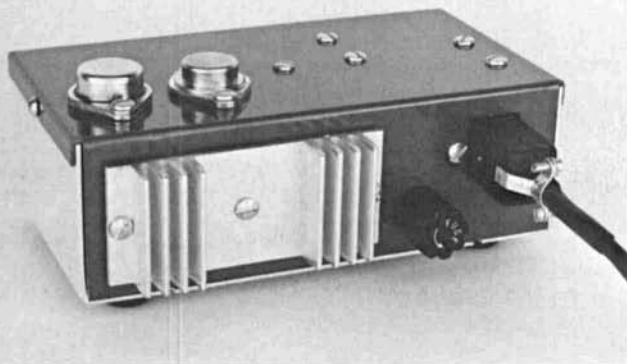"We have a limited supply of our Model 70's and Model 80's available at a 10% discount. Same full one year warranty as on all Robot equipment."



medium current polarity inverter

Complete
construction details
for a polarity converter
which will provide
a negative
voltage supply
from a positive source

J.R. Laughlin, San Jacinto College, Box 200, Pasadena, Texas 77505

Now you can go mobile with that favorite circuit that has been "grounded" for lack of negative power supply. An increasing number of semiconductor circuits and devices are appearing that require both a positive and a negative power supply for proper operation. For ac-powered installations this is no problem. However, in the automobile or for applications where only storage batteries are available a real problem can develop in supplying the needed negative power.


Often the designer can resort to trick circuitry in order to operate from a positive source. More often, especially in the case of ready made circuits, nothing within reason can be done. The polarity-inverter shown in fig. 1 offers a convenient solution to this problem by supplying a negative potential with power enough to suit most applications. This circuit operates with great efficiency and is virtually noiseless due to its high frequency of operation and lack of the usual power transformer. Filtering is a snap at this high frequency, requiring only nominal values of capacitance to do the job.

The output voltage is well regulated and is adjustable, and the 2-ampere maximum provides up to 22 watts of negative power from your auto battery.

circuit operation

A block diagram of the polarity inverter is shown in **fig. 1**. The square-wave generator is a stable unijunction transistor oscillator which drives a transistor (Q2) to produce the square wave. Charge time


fig. 1. Block diagram of the polarity inverter. With input from an automobile battery, this unit will furnish up to 200 mA at -13 volts, and up to 2 amps at -10 volts.

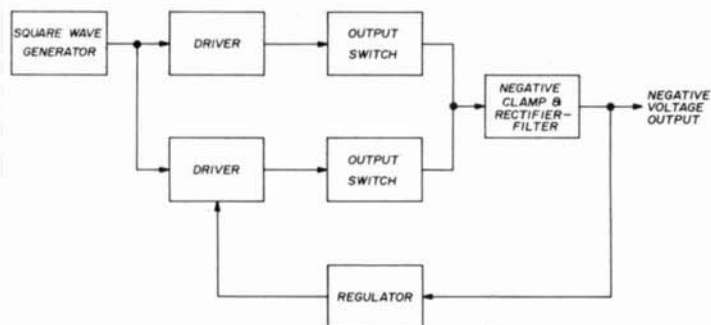

for C2 is controlled by the value of R1 (see **fig. 2**). Discharge time for this capacitor is controlled by R2.

While C2 is charging, Q2 is saturated; during the discharge time of C2, Q2 is turned off. By proper choice of values for R1 and R2, the output of Q2 will be a symmetrical square wave. Transistor Q3

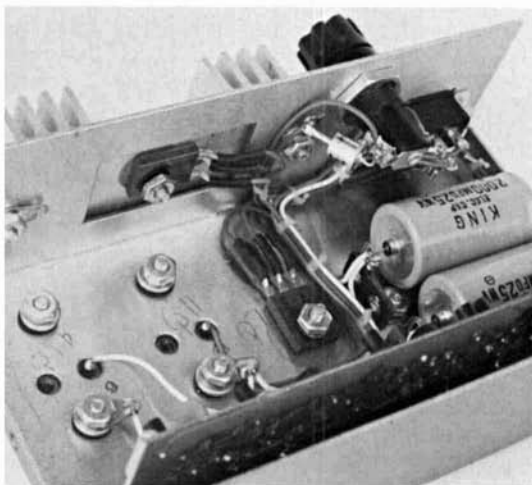Power transistor Q6 (2N3055) is mounted on heatsink through an opening in the enclosure. Transistor Q7 (2N2955) uses chassis for heat sinking.




buffers this output and furnishes driving power for Q4 and Q7. Transistor Q4 inverts the signal from Q3 and supplies base drive to Q5, an emitter follower, which has the capability of driving Q6 into complete saturation.

Transistors Q7 and Q6 are connected to form a complementary-symmetry output stage. These output switches are connected in a manner that allows them to be operated in a saturated mode and are driven hard to insure low V_{sat} when they are turned on. This minimizes voltage losses across the transistors and permits the highest possible output voltage.

The circuit configuration of transistors Q3, Q4 and Q5 insures that only one of the two output transistors can be turned on at a time. This arrangement is similar to the standard audio amplifier output circuits found in many stereo sets.

As Q7 and Q6 are alternately switched on and off, a square wave that alternates from ground to nearly battery potential is applied to the positive end of C3. Transistors Q10 and Q11 are connected as diode rectifiers. These are germanium transistors and their diode junctions can handle a lot of current with low voltage drop. Their low voltage drop prevents loss of output voltage that would have resulted if silicon diodes had been used.

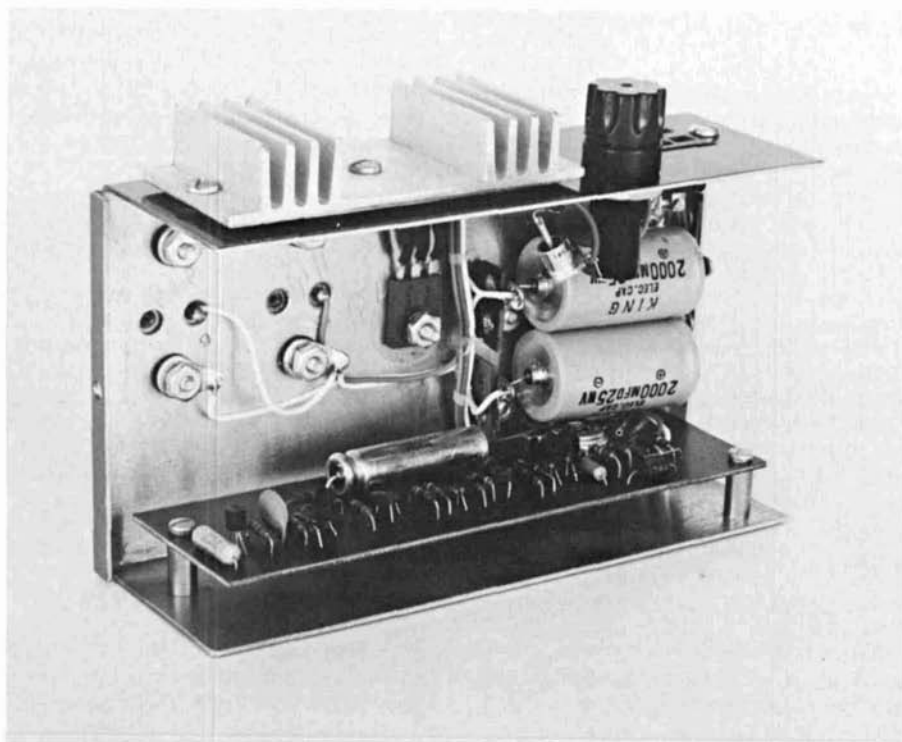Transistor Q11 works in conjunction with C3 to clamp the square wave output of Q6 and Q7 negatively. Thus, at the junction of C3 and Q11 and Q10 a square wave is present that varies from approxi-



Construction of the solid-state polarity inverter. Majority of components are mounted on printed circuit board (fig. 3) which is installed on half-inch spacers. Heatsink is for power transistor Q6. Transistors Q10 and Q11 are mounted on top of enclosure.

mately ground potential to a negative value almost equal to the positive value of the battery voltage. This negative-going square wave is rectified by Q10 and filtered by C4.

The value of negative voltage across C4 cannot be quite equal to the value of battery voltage because the combined voltage drops across Q6, Q7, and Q10 and Q11 combine to reduce the total output. Naturally, these losses increase with heavier output currents. Table 1 shows

table 1. Maximum available output voltage vs output current.

output current (amps)	output voltage (-Vdc)
0	14.0
0.2	13.0
0.4	12.7
1.0	11.4
1.5	10.9
2.0	10.0

available output voltage versus output current.

Regulation of the output voltage is performed by a transistor feedback loop consisting of Q9 and Q8. A zener diode, CR2, provides a stable reference voltage with which to compare the negative output. This comparison is done by Q9. If the negative output voltage attempts to increase, the conduction of Q9 will decrease. The positive-going collector of this transistor will increase the conduction of Q8, thereby preventing the base drive to Q5 from reaching its full positive value.

Reduction of this drive prevents Q6 from being turned on all the way during half of the cycle, resulting in a lower output voltage to the negative clamp circuit and rectifier. Thus, the output voltage is maintained automatically at a level which depends on the relative values of R15 and the series combination of potentiometer R17 and R16. If R16 is


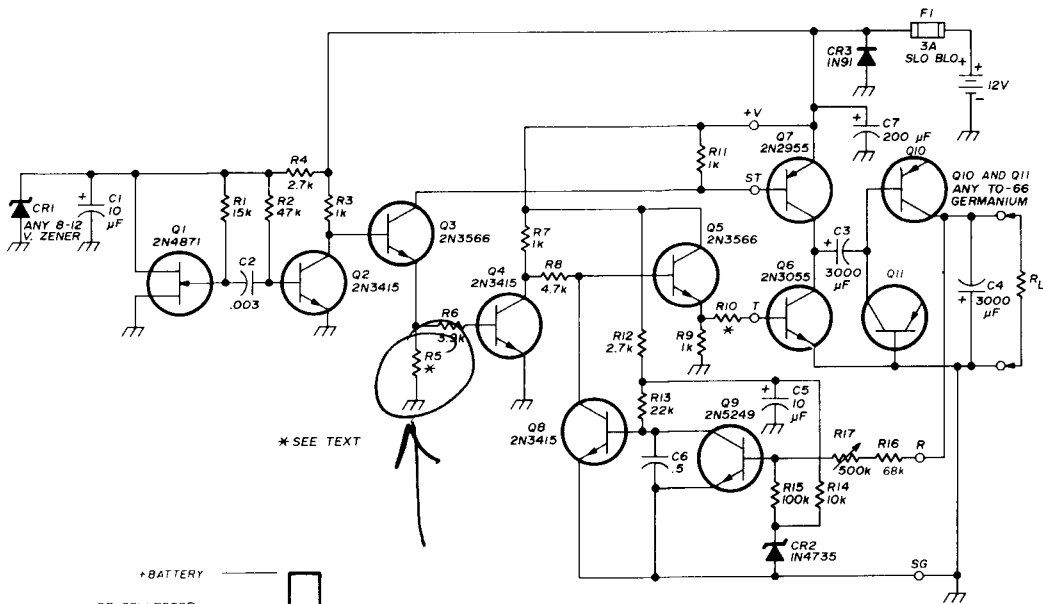


fig. 2. Schematic diagram of the polarity inverter and important waveforms. See text for value of R5.

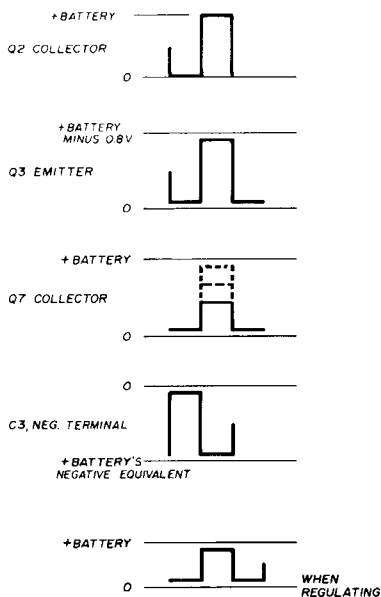

mately 2.2 amps. This additional 200 mA of battery current represents a loss of efficiency. Most of this 200 mA is current drive to the bases of Q6 and Q7 through their base-current limiting resistors, R10 and R11. This amount of base drive is not necessary if the inverter is to operate with loads lighter than 2 amps. These resistors may be increased as shown below for the reduced output currents.

maximum output current (amps)	R10 and R11 (ohms)
2	100
1	240
0.5	330
0.25	680

reduced in value, regulation will occur at a lower output voltage. Table 2 shows approximate output voltage levels for various values of R16 and R17.

Efficiency depends on the difference between the battery supply current and the output current. For example, with a 2-ampere output current the input supply current from the battery will be approxi-

Increasing these resistor values will substantially increase the operating efficiency for lower operating output currents.

construction

It is suggested that you use the circuit board shown in fig. 3. This can be

mounted into an aluminum box along with the other components. Heat sinking is not critical for any of the transistors except Q6. This transistor can dissipate quite a lot of power when delivering heavy output current at low output voltage level.

Diode CR3 is not a necessary part of the circuit but was included after the original unit was completed and connected to the battery in reverse! This diode will cause the fuse to open up instead of

should there be a wiring error. An ammeter in the battery line should indicate approximately 200 mA with the unit turned on and unloaded. This current will be less if higher values of R10 and R11 are used, as discussed earlier.

It is a good procedure to start at transistor Q1 with an oscilloscope and check each waveform as shown on the schematic. Verify the amplitude of each waveform. If all waveforms are normal, connect a 5-ohm power resistor across the

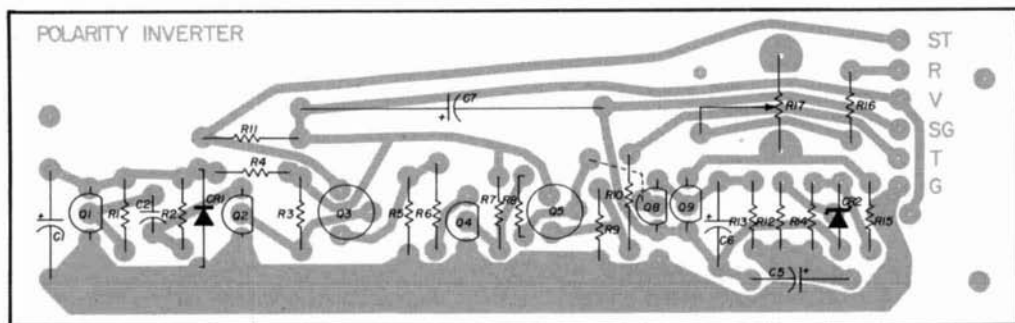


fig. 3. Full-size printed-circuit layout for the polarity inverter.

one or more output transistors if this should happen again. Transistors Q10, Q11 Q6 and Q7 are mounted to the aluminum chassis at widely spaced intervals to facilitate heat dissipation.

checkout

Be certain the fuse is in place before connecting the unit to a battery. Do not bypass the fuse during checkout. It may save a relatively expensive transistor

output terminals. With a 5-ohm load, an output voltage of ten volts represents full loading of the inverter. Of course, if you plan to operate at lower output current levels, a higher value resistor may be used for loading the output during the checkout.

Rotation of potentiometer R17 should produce a variation in the output voltage. Alternately connecting and disconnecting the load resistor will verify the regulator action. It should be noted that the maximum regulated output voltage cannot exceed that voltage shown in table 1 for the various values of peak output currents shown.

For example, if your audio power amplifier draws from 0.05 to 1.5 amps on peaks this inverter can supply 10.9 volts of negative regulated dc. If your requirements are from zero to 0.4 amps, the inverter can deliver -12.7 volts dc.

ham radio



table 2. Output voltage vs total resistance of R16 and R17 (battery maintained at +14.2 Vdc).

R16 + R17 (ohms)	output voltage (-Vdc)
220k	10
180k	8
160k	7
135k	6
110k	5
96k	4
70k	3

DYCOMM SUPER D 80 WATT KIT

DYCOMM OFFERS YOU THE BEST DEAL EVER
FOR A 2M FM (or Oscar CW) AMPLIFIER.

ONLY **\$49.95** SAVE \$60-\$100.00

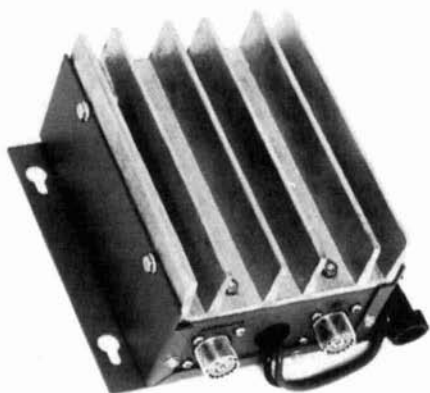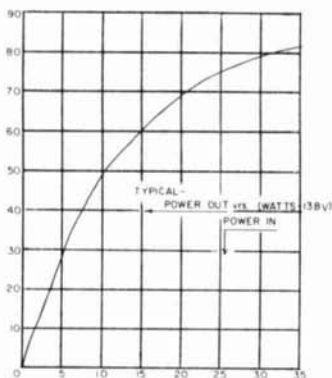

THE LIST PRICE OF THE TRANSISTORS IS MORE THAN TWO (2) TIMES THE PRICE OF THIS SUPER D KIT!!!

We use a pair of 2N6084 Transistors (each one rated 40 W Infinite VSWR) featuring EMITTER BALLASTED construction and of first Quality, so you can't burn them out in tuning or under any load mis-match; each Transistor has been individually Hand tested at DYCOMM before shipment.

Typical assembly time is 5 hours. Kit is complete with full assembly procedure, including lay-out Photos, and Manual.

Tune-up and alignment is easy and straight forward using a watt-meter, dummy load and VOM.


Kit includes: 6' control wire, 6' power cables (fused), 4' RG58 to make interconnect cable, 2 PL 259 connectors, and all other parts required for this PROFESSIONAL \$150.00 Amplifier.

SUPER D SPECIFICATIONS:


Frequency range: 140-150 MHz. Power output: 80W MAX for MAX input of 35W. Input/output Z: 50 ohms. Input VSWR 1:3:1 Max. Load VSWR: Infinite. Power required: 11-15 VDC @ .6 to 7A. Weight: 2 Lbs. Dimensions: 3" x 5" x 6". Operating modes: CW/FM.

SUPER D FEATURES

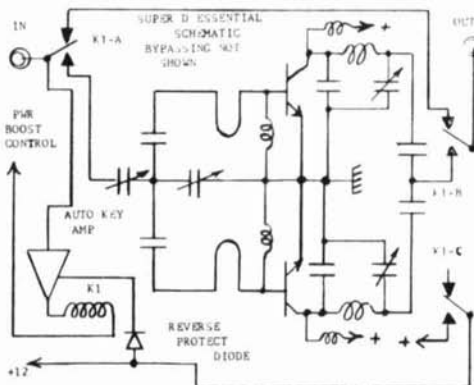Basic design proven in thousands of D's
Operates with ANY 2-35V Rig
Reverse Voltage Protected
Load VSWR Proof - 80db Spurious Outputs
Dashboard control available
Fully automatic operation on command
5 MHz Bandwidth, 140-150 MHz
Harmonics: At least 40 db down
Rx insertion loss less than .5 DB



Prices: KIT \$49.95; Wired and Tested \$149.95. Residents of Florida add 4% sales tax, shipping (UPS where possible) included. For Airmail add \$2.00. Foreign-add postage extra. EXTRA TRANSISTORS \$20.50 each (1/3 off list). All parts are guaranteed and if a defective part should be found it will be replaced free within 30 days of shipment. Quantities Limited. First come - First served; this Special offer ends January 10, 1974. Send check or money order to DYCOMM, 948 Ave. E., P.O. Box 10116, Riviera Beach, Florida, 33404. (305-844-1323)

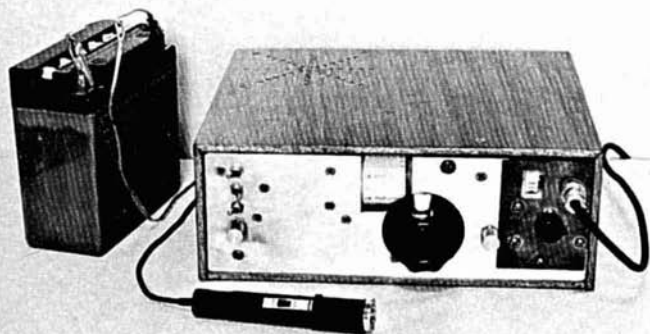

single-band ssb transceiver

using the LM373 communications IC

How to use
the versatile LM373
and several other ICs
to build
a compact
ssb transceiver
for 14 MHz

Charles H. Hill, W5BAA, 2510 Beatty, Houston, Texas 77023

About two years ago a new products announcement in *ham radio* described a linear communications IC, the National Semiconductor LM373. Although I have found the LM373 to be the most versatile IC for the communications field on the market, I have not seen any articles in the amateur publications which have given the LM373 the praise which I feel it deserves.

One of the strongest assets concerning the device is the very comprehensive data which the National Semiconductor Corporation supplies on request. With this data you can use the IC in a variety of signal processing roles with a minimum of brain work. In order to sing the praises of the device, I will describe a 20-meter QRP ssb transceiver which I have built around the LM373. Although sufficient information is provided in this article so that you may homebrew your own version, I would strongly suggest that you obtain the data sheets on the IC from National Semiconductor in order that you may fully appreciate the versatility of the device.*

communications IC

Fig. 1 is a functional outline of the LM373. National bills the device as an a-m/fm/ssb i-f strip; however, it is used for a host of other functions including dsb generators and receiver frontends. The package includes an agc-controlled gain stage, the output of which may be used to drive a crystal, mechanical or LC filter; a fixed-gain stage, which may be

transceiver

In the transceiver a common i-f strip is built using U1, an LM373 (see fig. 2). By switching the input signal applied to pin 2 from the output of the receiver frontend to the output of the dsb generator, the local oscillator signal at pin 6 from the 9-MHz bfo to the 5-MHz vfo, and the output at pin 7 from the audio amp to the 14-MHz filter, one LM373 IC acts as a

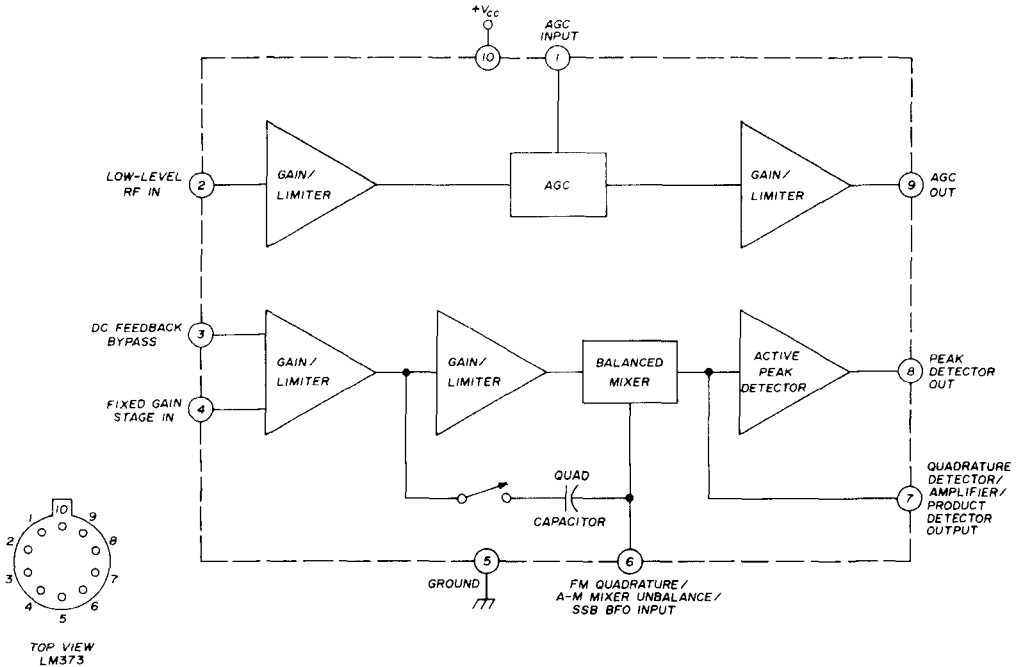




fig. 1. Block diagram of the versatile National Semiconductor LM373 communications IC. This IC can be used in a number of communications circuits, as illustrated in the 14-MHz transceiver circuit shown in fig. 3.

driven by one of the forementioned filters; a balanced mixer driven by the fixed gain stage and an agc generator which is matched to the agc controlled stage. In addition to the access points for the filter terminations, access is provided for nulling both the signal and local oscillator ports of the balanced mixer.

*National Semiconductor Corporation, 2975 San Ysidro Way, Santa Clara, California 95051.

both a receiver i-f strip with a built-in product detector and agc system, and transmitter filter and hf mixer with a built-in agc controlled speech compression. Of course, a 9-MHz ssb filter, FL1, placed between pins 9 and 4 provides the necessary filtering. All of the switching is handled by diode signal switches.

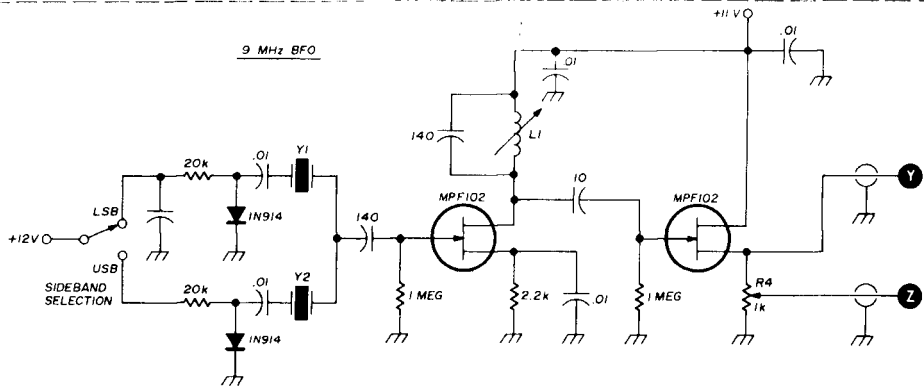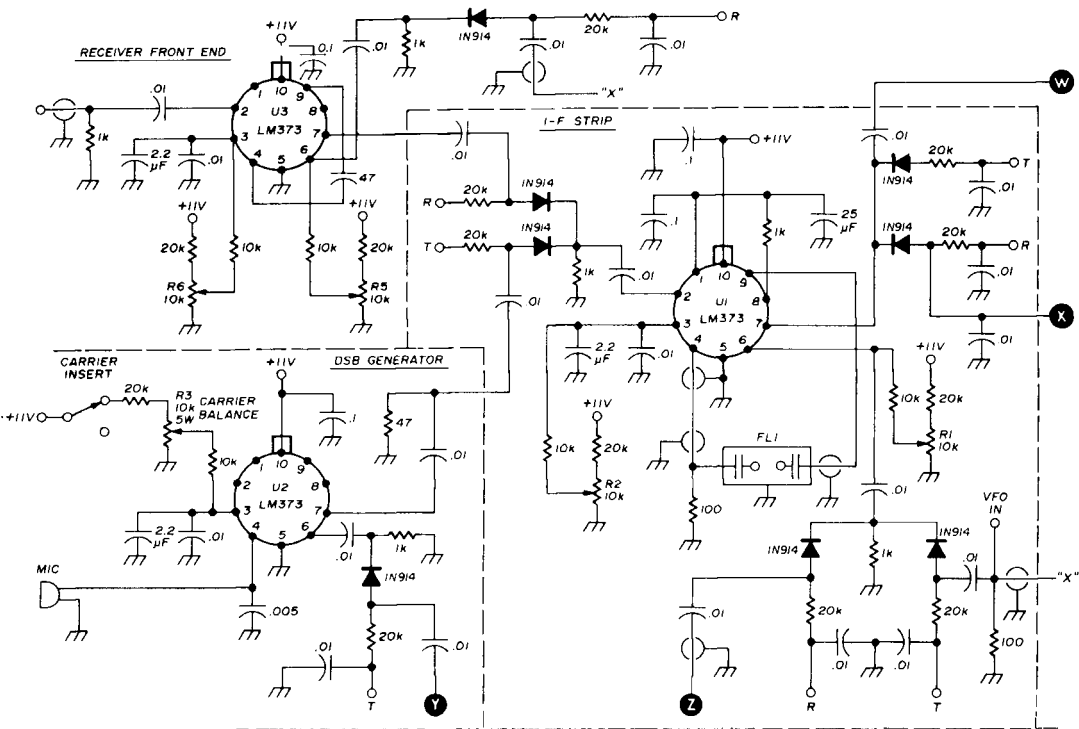In addition to i-f duties, the LM373 is also used as a dsb generator. In this case the output of a dynamic microphone is fed directly to pin 4 of U2, the fixed gain



- FL1 9-MHz crystal filter (KVG)
- FL2 Primary, 3 turns no. 26; tuned winding, 26 turns no. 26 on Amidon T-25 SF toroid core
- L1 24 turns no. 26, spacedwound to cover entire length of Miller 4300-2 slug-tuned, ceramic coil form
- Y1,Y2 Upper and lower sideband crystals for 9-MHz crystal filter (KVG)

fig. 2. Circuit diagram for the complete 14-MHz CW/ssb transceiver based on the National Semiconductor LM373 communications IC.

stage input. The 9-MHz bfo signal is switched to pin 6 during transmit, and the dsb output is taken at pin 7.

In the transceiver an LM373 is also used as a receiver front end. The input

signal is applied to pin 2 of U3, and a 47-pF capacitor couples the output of the agc controlled gain stage (pin 9) to the input of the fixed gain stage (pin 4). The 5-MHz vfo is switched to pin 6 during


circuit shown is taken directly from Motorola application notes.

The 14-MHz ssb signal from the i-f strip is separated from the 4-MHz product by the 14-MHz filter, FL2. This resonant circuit is tuned by a Motorola Epicap, MV2209. This allows the driver tune control, a variable resistor, to be remotely mounted on the front panel. An fet drain follower provides a low impedance output from the tuned circuit to the input of the linear amp. The first stage of the linear amplifier is an RCA CA3028A IC in a differential amplifier configuration which drives two 2N2102 emitter followers. These, in turn, drive two 2N2102 transistors in push pull. The final consists of two 2N3553 transistors in class B push pull. The output is transferred by transformer T2 through a coax relay to the 14-MHz input/output filter. This filter serves as both an output filter for the transmitter and an input filter for the receiver.


construction

The transceiver is built on a single piece of copper clad epoxy board with the 5-MHz vfo and linear amplifier mounted separately. The copper is left on to provide the necessary ground plane. Holes are drilled with a no. 60 drill to allow component leads to pass through the board. Ground connections are made directly by soldering to the copper foil. Leads above ground are isolated by reaming away the copper around the holes. The component leads are then hard wired on the non-copper side of the board. All capacitors are rated for 15 volts dc and all resistors are 1/4 watt. All diodes except the Epicap are 1N914 switching diodes. The ssb filter and matching crystals are manufactured by KVG. The only shielding required is around the 9-MHz bfo, around the vfo and between stages of the linear amplifier.

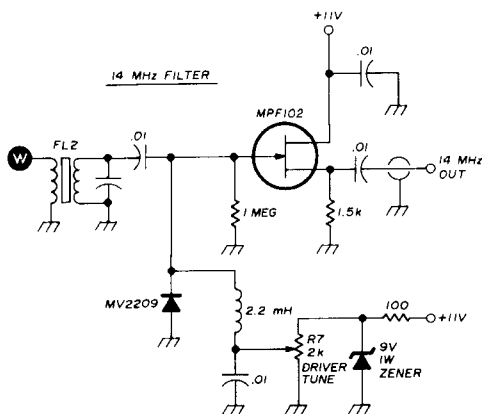
The layout I used is shown in the photograph. An exact layout is not provided here because the actual components I used may be unavailable to you, or may vary somewhat in size. To produce a




14 MHz FILTER

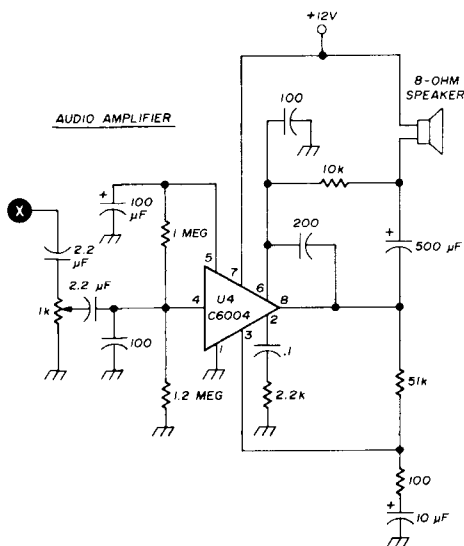

AUDIO AMPLIFIER

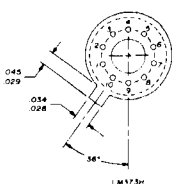

LM373P

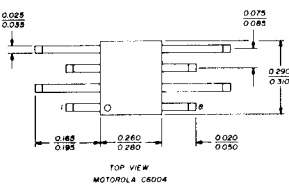

TOP VIEW
MOTOROLA C6004

receive, and the frontend output is taken from pin 7. All of these LM373 circuits are taken directly from the National Semiconductor application notes.

Audio amplification is provided by the Motorola C6004, U4, which is capable of producing a 1-watt output into an 8-ohm speaker without any transformers. The

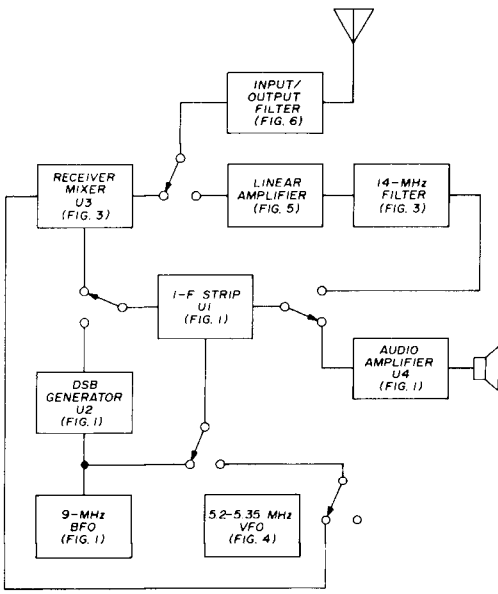


fig. 3. Block diagram of the 14-MHz transceiver in the receive mode. Complete diagram of the transceiver is given in fig. 2.

drilling template, I used ten-squares-per-inch grid paper on which to lay out the components to actual size. It is wise to make all leads as short as possible, and to use shielded lead where indicated in the diagrams. A rigid mechanical frame will insure adequate frequency stability.

tuneup

Since I have a limited amount of test equipment (5-MHz oscilloscope, a Q meter and a crystal calibrator) I had to use a boot-strap method to align the unit. First,

check the audio amplifier by touching pin 4 of the C6004 IC with a metal screw driver. The 60-Hz pickup should drive the audio amplifier to good audio output.

Next, the 9-MHz crystal bfo may be brought to life by monitoring its output with an oscilloscope (I am able to see the signal on my 5 MHz scope) or listening to the audio output for a rush of noise while adjusting inductor L1. The i-f strip may be aligned by switching the carrier insert switch to the carrier on position, the unit to transmit, and observing the output of U1 at pin 7 with the scope while adjusting R1 (the signal port null) for a maximum signal output.

Also, it will be necessary to adjust the local-oscillator port null, R2, but first it is necessary to null the carrier from the dsb generator. This is done by switching the carrier insert switch to carrier off and adjusting R3 for a null as observed at pin 7 of U1. Resistor R4 must be adjusted to a threshold point where the null is minimum. Now the i-f local oscillator port may be nulled by adjusting R2 for a null as observed at pin 7 of U1.

Since the signal port adjustment will interact with the local oscillator port null, R1, R2 and R3 must be adjusted in sequence several times to achieve maximum signal output at pin 7 with the carrier on, and for minimum signal with the carrier off.

At this point the i-f strip and the dsb generator are aligned. The receiver front-end may be aligned with or without a signal generator. To align the circuit with


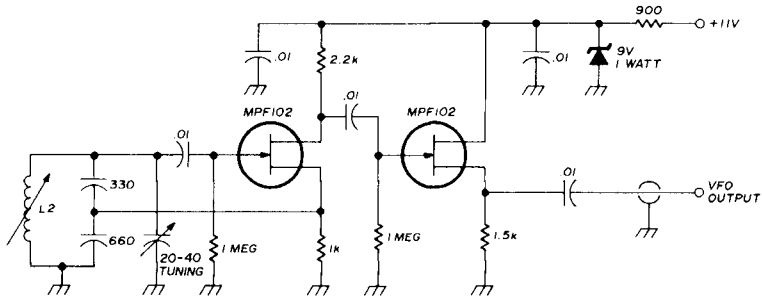


fig. 4. Vfo for the 14-MHz transceiver shown in fig. 3 covers the range from 5.2 to 5.35 MHz. All fixed capacitors are silver-mica units. Inductor L2 is 35 turns no. 26, scramble wound over one-half the length of a Miller 4300-2 ceramic coil form.

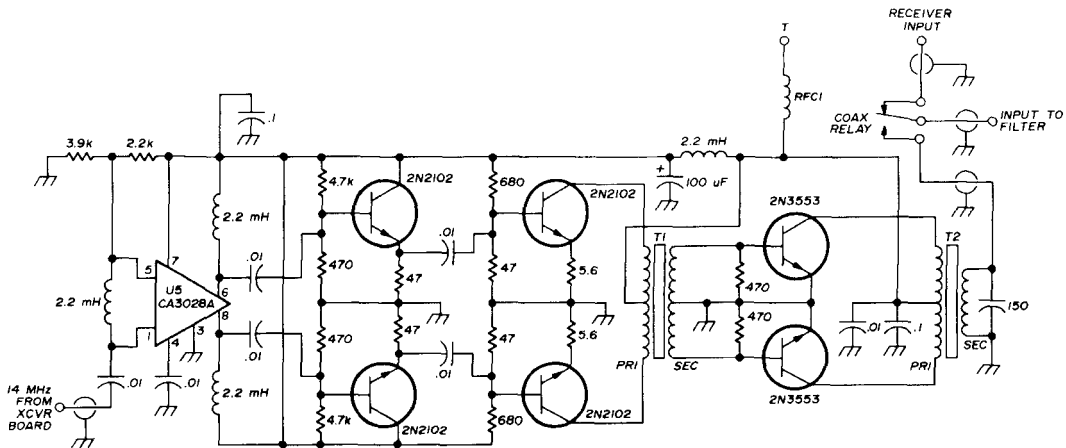

- RFC1 25 turns no. 16 on Amidon T-50 SF toroid core
- T1 Primary, 20 bifilar turns no. 26; secondary, 6 bifilar turns no. 26 on Amidon T-37 SF toroid core
- T2 Primary, 18 bifilar turns no. 26; secondary, 26 turns on Amidon T-68 SF toroid core

fig. 5. Solid-state linear amplifier provides up to 5 watts output at 14 MHz.

a signal generator, feed the 14-MHz generator output into the antenna terminal and tune L2 until a signal is heard. Next, adjust the signal port null control, R5, for a maximum signal as observed at pin 7 of U1. Also, check for peak tuning of the input/output filter by adjusting C1 for maximum signal at pin 7. If a signal generator is not available, attach an antenna during daylight hours and tune L2 until 20-meter signals can be heard, then adjust R5 and C1 as described above. Now the local oscillator port may be nulled by removing the antenna or signal generator and adjusting R6 for minimum signal at pin 9 of U1. This concludes the receiver frontend alignment.


The linear is a wideband amplifier and requires no alignment. However, if trouble is experienced, bypass the 14-MHz filter and feed the signal from pin 7 of U1 directly into the linear amplifier. This signal will contain a 4-MHz component which can be detected by the scope, thus facilitating normal amplifier troubleshooting procedures. To peak the signals into and out of the linear amplifier, adjust R7, the 14-MHz filter tuning, and C1, the input/output filter tuning, for a maximum signal as indicated

on the output meter. This should be done with a 50-ohm antenna or a 50-ohm dummy load attached to the antenna terminal, and the carrier insert switch in the carrier *on* position.

When you have reached this point you can calibrate the transceiver by whatever means available and try it out on the air.


performance

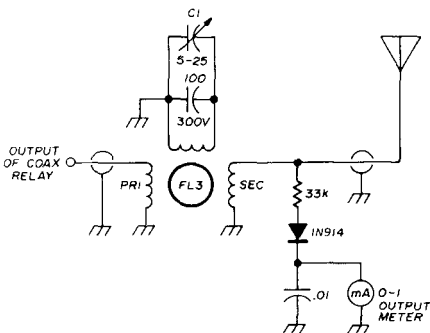With only 5 watts PEP output a little operator skill is required to communicate.



- FL3 Primary, 3 turns no. 16; secondary, 2 turns no. 16; tuned winding, 16 turns no. 16, all on Amidon T-50 SF toroid core

fig. 6. Input/output filter for the 14-MHz CW/ssb transceiver.

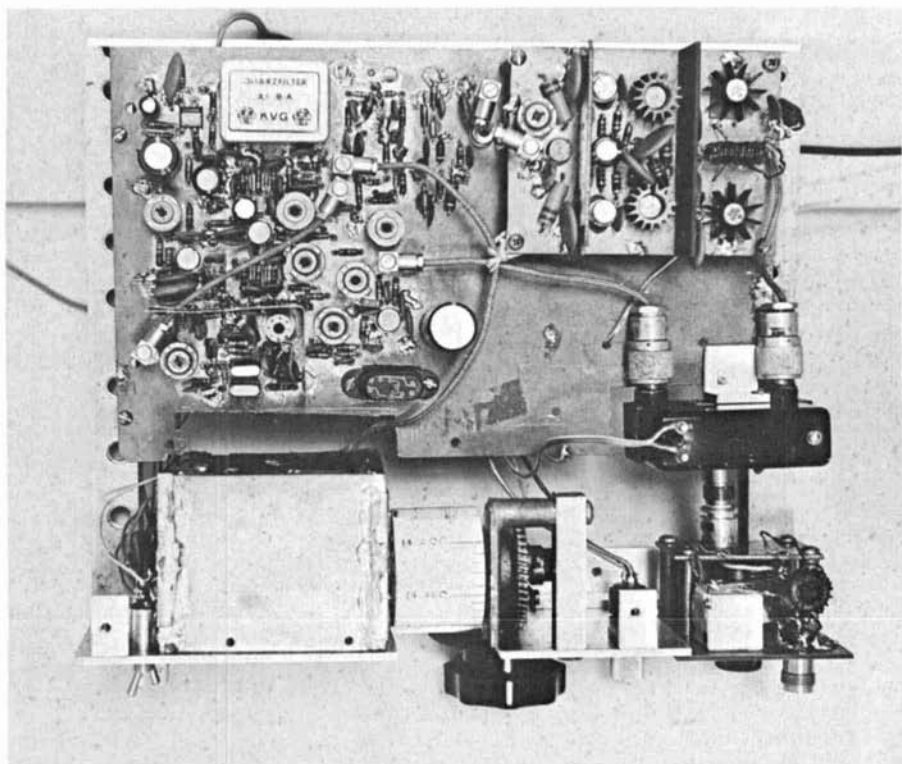

Layout of the 14-MHz transceiver, showing the location of the major components.

However, I never cease to be thrilled to announce that I am using QRP after receiving a good signal report. Always get a signal report before telling the other fellow that you are QRP — by some strange phenomenon my signal always goes down after announcing my power level. I must admit that several unsolicited compliments of the audio quality have been made which I attribute to the agc action of U1 during transmit.

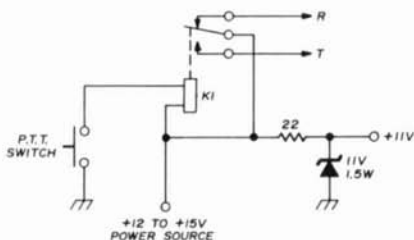


fig. 7. Dc power switching for receive/transmit control on the 14-MHz transceiver.

refinements

If you want to add 75-meter operation, a 4-MHz filter could be switched into the signal path between U1 and the linear amplifier, and a 4-MHz input/output filter switched in between the coax relay and the antenna. Also, a trimmer capacitor would have to be switched into the vfo tank circuit to obtain proper frequency coverage.

The fet oscillator circuits could be replaced by the National LM375 IC, which is a linear IC designed for oscillator/buffer duties. If more power output is desired, a linear amplifier built around the Motorola 2N6367 or 2N6368 might be considered. These transistors are silicon npn devices designed especially for hf ssb service. Motorola provides very good information on the use of these devices from 4 to 30 MHz.

ham radio

THINGS ARE LOOKIN' GOOD FOR CHRISTMAS



... By having your Inoue dealer wrap up one of these goodies for Christmas ... you'll be taking home one of the finest, most advanced pieces of 2-meter FM gear available today ... !

FOR EXAMPLE ... Upgrade your station with the advanced generation 4 Inoue IC-230 ... with Inoue's unique 67+ channel "Phase Locked Loop" synthesized system ... and not a xtal to buy ... Imagine! ... 67+ channels of rugged (all modular construction ... servicing is a snap—in and out) communications ability ... so compact (2.3" x 6.1" x 9.7") that you can snap it in and out of the smallest places (compact car, brief case, or apartment book shelf) ... For a few bucks more, you're getting 67+ channels of one of the most advanced pieces of 2-meter gear available today ... **the Inoue IC-230 @ \$489 ...**

Let Santa's Little Helper fill your Christmas Stocking by seeing ... or writing your nearby ICOM dealer today ... and see the entire family of Inoue's unique and advanced FM gear ... time's a wastin' ... !

Distributed by:



— Dealerships Available —

ICOM WEST, INC.
Suite 232 — Bldg. 11
300 - 120th Ave. N.E.
Bellevue, Wash. 98005
(206) 454-2470

**ADIRONDACK
RADIO SUPPLY**
185 West Main Street
Amsterdam, N.Y. 12010

ICOM EAST
Div ACS, Inc.
Box 331
Richardson, Tex. 75080
(214) 235-0479

single-frequency repeaters for vhf fm

A discussion of
single-frequency
fm repeaters
and how they might
be put to use
on the vhf
amateur bands

A **repeater**, by definition, is a device used to automatically relay radio, television, telephone or telegraph signals and is used to extend communications over a range not possible with direct communications. The type of repeaters which most people are familiar with are radio or television repeaters which receive on one frequency and transmit on another (fig. 1A). This type of repeater is very common and is the type of repeater which most of the electronics industry has been devoting its time to. However, there is another

type of repeater about which very little has been written. This is the single-frequency repeater — a repeater which transmits and receives on the same frequency. This article presents a discussion of the single-frequency repeater.

single-frequency repeater

The single-frequency repeater is broken down into two classes — the delayed type and the simultaneous type. The *delayed* repeater (fig. 2) can operate either on a single channel or use separate frequencies for input and output. This type of repeater records communications on the input channel and re-transmits the recorded communications on the output frequency at a later time. The received signal is not transmitted simultaneously with reception but is *delayed* for later transmission. This type of repeater is useful for data or teletype transmission but is not suitable for voice operation where the receiving station is expected to make an immediate reply.

The *simultaneous* single-frequency repeater uses the same frequency for input and output and appears to transmit the received signal during the period of reception. Comparatively little work has been done on this type of repeater in recent years, and a review of the *Applied Science & Technology Index* back through 1968 shows no references to papers or articles devoted to this type of repeater. Although I have heard rumors that both General Electric and Motorola have built and operated single-frequency repeaters, I haven't been able to find any details.

George Allen, W2FPP, 4059 Bay Park Drive, Liverpool, New York 13088

The simultaneous single-frequency repeater can be further broken down into two sub classes — continuous and time division. The continuous single-frequency repeater (fig. 3) transmits and receives continuously on the same frequency. To make this type of repeater work, the input and output must have separate

repeater site. Even if this degree of isolation could be achieved, other problems would make this type of repeater impractical. For one thing, transmitted signals would be reflected back from the geographical terrain and any objects in the vicinity of the repeater, so it would be nearly impossible to keep the transmitted signal from getting back into the receiver.

A more practical approach would be to use a time-division single-frequency repeater as shown in fig. 4. This type of repeater is similar to the delayed type in that the input is delayed slightly before transmission. The transmitter and receiver operate alternately, but at such a fast rate that they appear to be operating continuously and simultaneously.

Fig. 5A shows a simple plot of the operating period for the time-division SFR. Note that in a given time interval a portion is used for receiving and a portion is used for transmitting. During the receive interval the received information is saved, either by using a delay line or some type of recording device, such as a tape

antennas which are completely isolated. Total isolation between input and output must be achieved so that any signal from the transmitter must be below the receiver noise level. From a practical standpoint in the vhf region this is next to impossible to achieve using a single

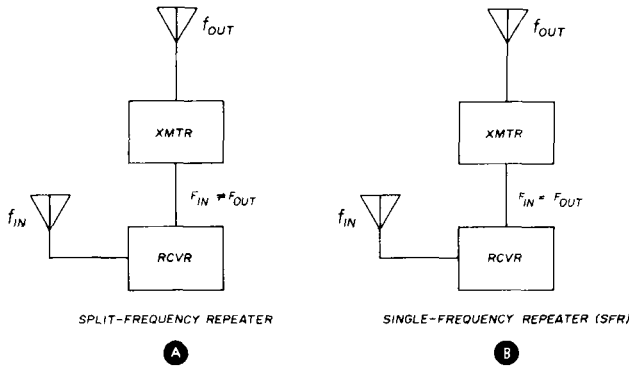


fig. 1. Two basic types of repeaters. The conventional split-frequency repeater shown in (A) transmits on one frequency and receives on another. The single-frequency repeater in (B) transmits and receives on the same frequency.

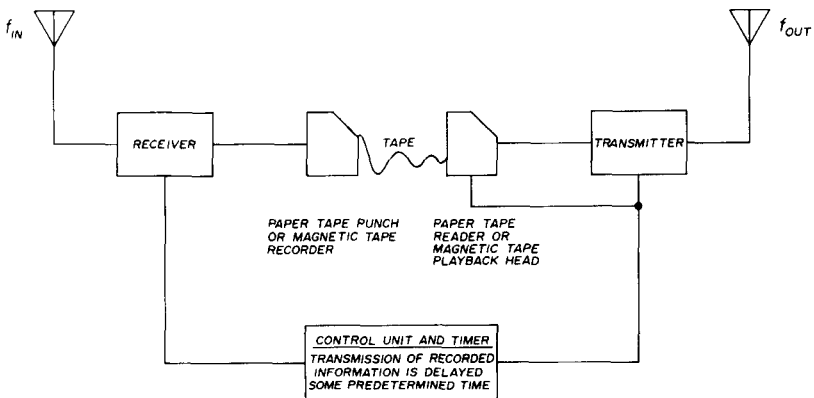


fig. 2. Basic layout of the delayed single-frequency repeater. Input and output frequencies are the same.

recorder. During the transmit interval, the recorded or delayed information is re-transmitted.

At this point several problems are introduced into the time-division SFR. First, receivers and transmitters do not turn on and off simultaneously. There is

the transmitter, it is necessary to wait some time interval t_{TS} before turning on the receiver to prevent the transmitter output from feeding back into the receiver. This is shown in fig. 5B.

Another problem arises due to the fact that the receiver is not receiving con-

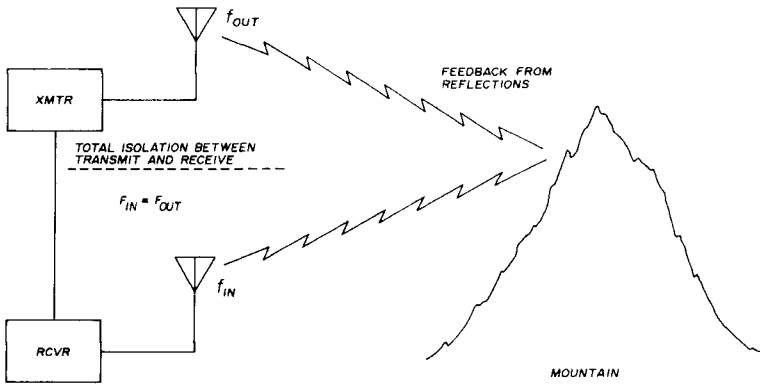


fig. 3. Continuous single-frequency repeater is not practical because any reflections from the transmitter are fed back into the receiver.

always turn-on and turn-off lag. Thus, after the receiving interval is finished it is necessary to wait for some time period t_{RS} to give the receiver a chance to turn off. This time interval will depend on the type of the receiver and the muting and blanking circuits involved. In regard to

continuously. There is a significant time period for which information is not received, but lost. This is a sampling mode of operation so the signal to be repeated is not repeated in its entirety, but only samples of the communication are repeated. This problem of lost information can

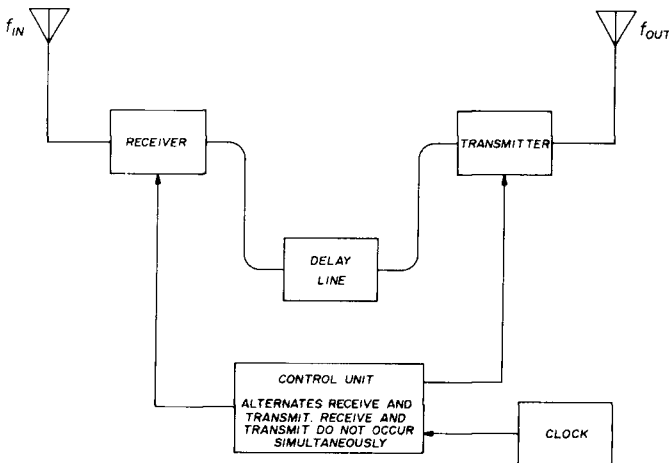


fig. 4. Time-division single-frequency repeater alternates transmission and reception. The repeater appears to be on continuously, but is not.

be solved by choosing the proper sampling interval.

The telephone companies have been using similar sampling techniques for overseas cables, so it is possible to select a sampling interval which will provide minimum loss of intelligibility. This interval, which is rapid enough to retain intelligibility, must be slow enough so that the receive-transmit times are greater than the settling times. If the settling time becomes too large as compared to receive-transmit time, then too much information will be lost and intelligibility will be impaired.

Another factor in the choice of time interval is the availability of delay lines. The delay line or recording media must delay the input for a period equal to the receive time plus the receive settling time.

mobile considerations

When attempting to receive a transmission from a time-division SFR a couple of things will be evident. For one, as shown in **fig. 6**, a noticeable buzz or noise could be apparent at the mobile receiver due to the fact that the transmitter is not transmitting continuously but is being on-off modulated in a pulsed mode. This pulsed modulation will appear as a buzz at the mobile receiver and may possibly override the information being repeated. Some means must be used to eliminate this undesired noise. One possible solution would be to use standard noise blanking techniques. Perhaps a more practical approach would be to use a type of synchronized, muted detector. This type of detector would be similar to the detector used to detect synchronous data transmissions. It would have a time interval sensing circuit that would use the first few time intervals to determine the length of interval that the repeater is using. After this interval has been determined, the detector would anticipate future time intervals and in turn, mute the received audio during non-transmit periods. This would eliminate the received pulse noise.

In regard to the mobile transmitter, it

appears that no changes would have to be made. In cases where the received mobile signal is stronger from the other mobile than from the repeater, the synchronized, muting detector would capture the mobile signal and operation would be as if there were no repeater. It might be

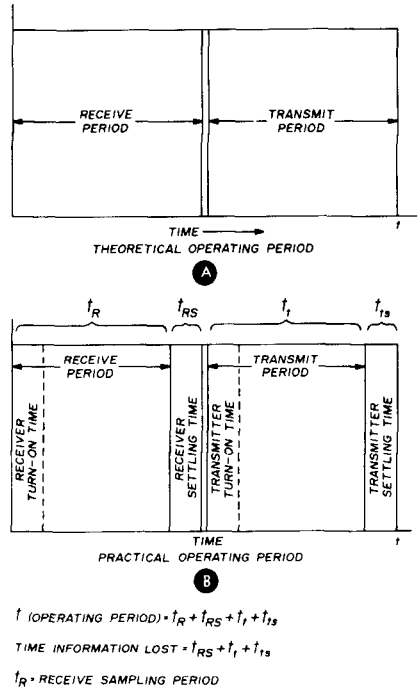


fig. 5. Operating period of the time-division single-frequency repeater.

mentioned that with this type of system, de-sensing would not occur when mobiles that were using the repeater were close to each other.

While all of the above considerations may appear to present a horrendous picture of impracticality for this type of repeater, you must recognize that each of the concepts are practical from a state-of-the-art standpoint. The only concept not proven is the sum total of all the techniques working together.

experimental single-frequency repeaters

A single-frequency repeater can be

built for experimental purposes provided that some assumptions are made. These preclude any exotic circuitry and emphasize simple compromise approaches. The first assumption is that a short timing cycle would present difficulty due to the complexity of high-speed switching circuitry. Thus, a long timing cycle must be used. Second, delay lines for storage of information from receive to transmit may not be available, so simple means such as tape loop delay lines must be used. Third, commercially available receivers and transmitters must be used to simplify repeater construction and permit use of existing transmit/receive circuitry. Finally, the information to be repeated must be slow in nature so that a signal loss of seconds would not result in a loss of information. It is also assumed that due to the long operating period, noise in the mobile receiver would not be a factor. Thus, this experimental repeater would be used basically to repeat frequency modulated telemetry or on-off tone signals of long duration.

practical single-frequency repeaters

The single-frequency repeater shown in fig. 8 is designed to repeat tone-frequency modulated telemetry. The basic unit consists of a transceiver such as a Standard 826MA, a clock which generates 0.1-second pulses, a slow speed tape recorder with separate playback head, and a simple control unit. The control unit is set up to count pulses and control the repeater in a manner such that the receiver receives for 9 pulses, waits for a 1


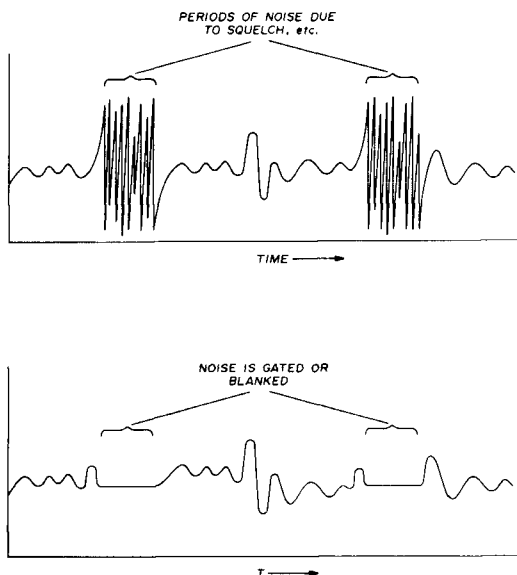


fig. 6. With a time-division single-frequency repeater the operator of a base or mobile station would hear a buzzing sound due to the periods between transmission as shown in (A). This could be solved with noise blanking or gating techniques as discussed in the text (B).

pulse settling period, the transmitter transmits for 9 pulses and waits for a 1 pulse settling period. The record head is connected to the receiver and the playback head is connected to the transmitter. The recorder is operated at the slowest possible speed. Note that it may be necessary to move the playback head or provide another playback head at a distance far enough from the record head to provide an approximate one-half second delay.

The single-frequency repeater shown

fig. 7. This practical single-frequency repeater is similar to the system shown in fig. 8 except that the tape recorder is replaced by a series of tone filters, tone oscillators and digital latches (see text).

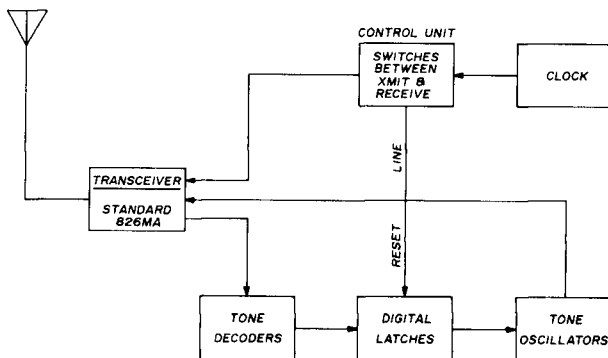

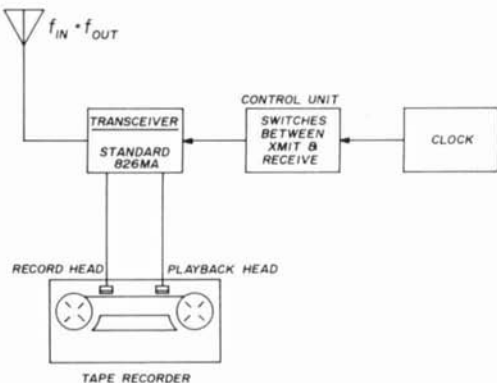


fig. 8. Practical single-frequency repeater. The time delay between record and playback is equal to one-half the operating period.

in fig. 7 is the same as SFR shown in fig. 8 except that it is designed to repeat on-off signaling. The tape recorder delay line is replaced by a series of tone filters, tone oscillators and digital latches. The tone filters determine which tones have been received and set the appropriate digital latches. When transmit time comes, the digital latches cause the proper tones to be re-transmitted. At the end of the transmit period, all latches are reset and the system is ready to receive.

Note that any transceiver may be used in either of the single-frequency repeaters. However, the Standard 826MA was chosen because of its commercial quality and reliability.

summary

The purpose of this article is to present a simple discussion of the single-frequency repeater and to stimulate discussion and experimentation on the subject. It is hoped that enough ideas have been presented to kindle an interest in other experimenters.

In regard to future work, I am presently working on the two practical SFRs as discussed in this article. I have filed a license application with the FCC for this type of repeater and will start on-the-air tests as soon as the license arrives. I expect to report the results of these tests within the next year.

ham radio

All Mobile Antennas are NOT alike.

Larsen
Antennas
with
exclusive
Kūlrod®
let you
HEAR the difference!



Mobile Antennas should be judged on the basis of ruggedness, ease of installation and performance . . . mostly performance. Larsen Kūlrod Antennas are "solid" on all scores. They have a low, low silhouette for best appearance and minimum wind drag. Hi-impact epoxy base construction assures rugged long life. The Larsen mount gives you metal to metal contact, has only 3 simple parts and goes on fast and easily.

And performance! Larsen Antennas for the 144-148 MHz range deliver a full 3 db gain over a 1/4 wave whip. V.S.W.R. is less than 1.3 to 1. The exclusive Larsen Kūlrod assures you no loss of RF through heat. Handles full 150 watts.

It all adds up to superior performance . . . just one of many reasons why Larsen Antennas are the fastest growing line in the commercial field in both the U.S. and Canada. Available as antennas only or complete with mounting hardware coax and plug. Write today for fact sheet and prices.

Sold with a full money back guarantee.
You hear better or it costs you nothing!

Need a BETTER 450 MHz Antenna?

Get the Larsen 5 db gain Phased Collinear. Same rugged construction and reliability as the 2 meter Larsen Antennas including exclusive Kūlrod. Write for full fact sheet.



©Kūlrod . . .
a trademark of Larsen Electronics

Larsen Antennas

1161 N.E. 50th Ave. • Vancouver, WA 98665
Phone: 206/695-5383

For fastest mail service address:
P.O. Box 1686 — Vancouver, WA 98663

open-wire impedance-matching baluns

How to design
and use
transmission
line sections for
impedance-matching
baluns

Greater emphasis on the low-frequency bands as the sunspot cycle decreases makes it desirable to more carefully consider the use of wire antennas. In two previous articles on this general subject I have described a two-band matching system using open-wire lines¹ and a means of using lumped capacitances instead of open stubs in a double-stub matching system.² In this article I will discuss two convenient wire-line baluns that will also serve as impedance transformers.

Baluns made of coaxial cable, or toroidal transformers, are limited in their

impedance transforming capability because you cannot conveniently change the Z_o of the coax or the turns on the transformer. The balun must be used in addition to the matching system. It is relatively easy, however, to make a balun using open-wire lines that will give a much wider choice of matching ratio, and thus combine the matching system and the balun into one unit to do both jobs at once.

In working with transmission lines it is helpful to use the pi equivalent circuit which is given in **fig. 1**. While this may not be physically realizable using lumped constants, except at one frequency, it is nevertheless a valid mathematical model which helps us to more easily visualize what is going on with transmission lines than if we try to work exclusively with the transmission line equations or graphical devices such as the Smith Chart. **Fig. 1B** shows the true balanced configuration; if you are unconcerned with balance to ground, simply make the top series reactance $jZ_o \sin \theta$ and eliminate the bottom one, as in **fig. 1C**.

Looking at **fig. 1** you can see that a transmission line without any connected reactances is always symmetrical; that is, the shunt arms are equal to each other. There is only one symmetrical pi network that will exhibit transformer action between two pure resistances, and that is the one in which each reactance is equal to $\sqrt{R_{in} R}$, and where the series and shunt reactances are of opposite sign. Thus, in **fig. 1** you must have $\sin \theta = 1/(\tan \theta/2)$. With the aid of trigonometric identities it is easy to show that this requires that θ

R. W. Johnson, W6MUR, Post Box 803, Ben Lomond, California 95005

be some odd multiple of 90° ; e.g., a quarterwave line. The transformation is simply $R_{in} = Z_o^2/R$ for this special case.

In other cases, transformer action between two pure resistances demands that there be some added reactance to one or the other of the shunt arms, so that the network becomes asymmetrical. This is why a stub or lumped reactance of some sort must be added to the general line to achieve a match, although there have been arrangements using an off-resonant

to ground. Thus, a coaxial cable can be attached to terminals 1 and 2 and a balanced antenna to terminals 3 and 4; conversely, a grounded antenna may be connected to terminals 3 and 4 and an open-wire line connected to terminals 1 and 2. Note also that with the load disconnected, the input resistance is zero since the bridge is essentially two series-resonant circuits in parallel. This facilitates tuning the network in cases where the reactances are made adjustable.

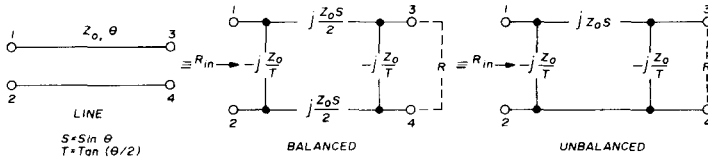


fig. 1. Pi equivalents of the transmission line.

antenna as the added reactance on the load side.

lattice networks

It is also desirable to consider the *lattice* network as an impedance transformer. The lattice is shown in fig. 2 in both conventional and bridge forms. Again, for the symmetrical network there is only one configuration where transformer action takes place between two pure resistances, that being where the shunt and series arms of the lattice network are pure reactances, equal in magnitude and opposite in phase, $X_1 = -X_2 = X$ in fig. 2. The transformation again is simply $R_{in} = X^2/R$ where X is the reactance of each of the lattice arms.

The important thing about the lattice network is that with this particular configuration, any one terminal can be grounded without disturbing the balance

Fig. 3 shows a lattice network made up of transmission line sections. A shorted line is shown for the inductive arm, and an open line for the capacitive arms, but this is not the only configuration that can be used; it is merely the one which results in the least total amount of line. Its bandwidth characteristics are also fairly good. The reactance of the shorted line is $jZ_o T$ and that of the open line is $-jZ_o (1/T_1)$, where T and T_1 are the tangents of the angles θ and θ_1 , respectively. For the symmetrical lattice matching section it is required that $X = \sqrt{R_{in}R} = Z_o T$, and also that $TT_1 = 1$, from which it can be shown that the total line length $\theta + \theta_1$ must be 90° , or a quarter wavelength. The tap point is given by

$$\tan \theta = \frac{\sqrt{R_{in}R}}{Z_o} \quad \text{and} \quad \theta_1 = 90 - \theta$$

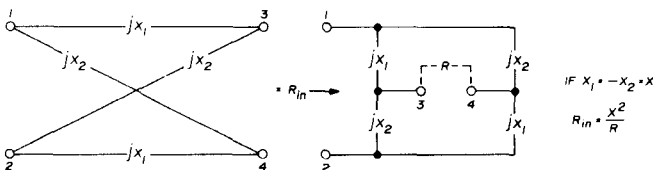


fig. 2. Reactive lattice network. In this configuration any one terminal can be grounded without disturbing the balance to ground. The transmission-line balun shown in fig. 3 is based on this equivalent circuit.

For the greatest bandwidth, $\tan \theta$ must be small rather than large. That is, the tap point must be near the shorted end of the total line in each case. This dictates that Z_o must be as large as convenient. In the special case where $R_{in} = Z_o$, where the same line impedance is used for matching as in the transmission line to be matched, $\tan \theta = \sqrt{R/Z_o}$.

The curves of **fig. 4** give the electrical length of the tap point for some typical Z_o values and antenna resistances, assuming you want to match to 50-ohm coax. The *physical* length, of course, depends on the frequency and v_p , the velocity of propagation on the line (typically 0.82 for twin lead, 0.66 for coax, and 0.96 or so for open-wire feeders). In feet, it is $2.73 (v_p/f)\theta$ where f is in MHz and θ is in degrees.

Fig. 5 shows one configuration as connected to and suspended from a balanced antenna. For a center-fed full-wave antenna of $R = 4000$ ohms and 300-ohm twin-lead for the balun, $\theta = 56.15^\circ$. The tap point is thus at 62.4% of the total length of the quarter-wave twin lead, measured from the shorted end on each line.

re-entrant crossed line

The re-entrant crossed line is another form of transmission line impedance-

matching balun that may be convenient in some cases, especially where you may want to feed a grounded vertical array using open-wire line. In this case the total length of line required turns out to be a full wavelength. The line and its equiva-

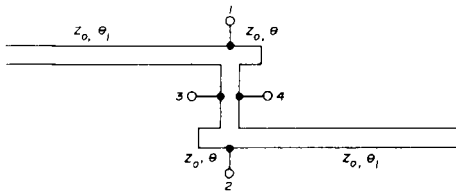


fig. 3. Open-wire transmission-line balun using the lattice network. Antenna is connected to terminals 1 and 2; transmission line is connected to terminals 3 and 4. Tap point for matching 50-ohm coaxial cable is given in **fig. 4**.

lent circuit is shown in **fig. 6**; note the *crossed* connections.

It turns out that for the case of interest, namely, a symmetrical lattice with arms equal and of opposite sign, the impedances across terminals 1-2 and 3-4 in the equivalent circuit of **fig. 6** must be anti-resonant. That is, $T = -T_1$, where in this case the T s are tangents of *half* the angle. You are left with the lattice itself in **fig. 6**, and for $S = -S_1$ simultaneously with $T = -T_1$ it is necessary that $\theta = 360 - \theta_1$. The result is

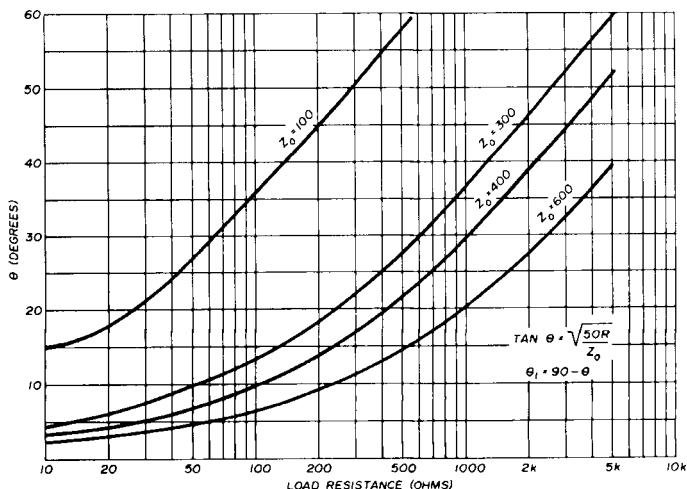


fig. 4. Balun tap point for matching 50-ohm coaxial cable to the open-wire balun shown in **fig. 3**.

$$\sin \theta = \frac{2\sqrt{R_{in}R}}{Z_0}$$

$$\theta_1 = 360 - \theta \text{ in degrees}$$

For this case Z_0 must be greater than $\sqrt{R_{in}R}$ for a real result since $\sin \theta$ cannot be larger than unity. This lattice can also be used as a balun — any one terminal of the network

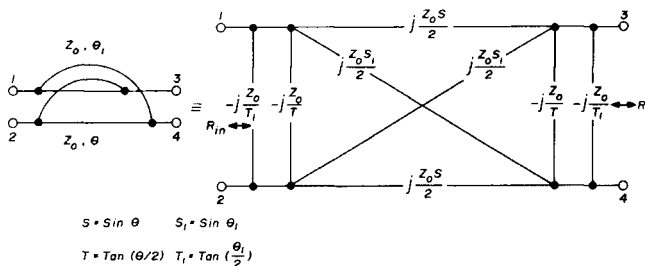


fig. 6. Crossed re-entrant line impedance-matching balun discussed in the text.

can be grounded without disturbing the balance to ground.

If it is assumed that you are matching to 50-ohm coaxial line, then for various characteristic impedance values for the re-entrant balun, you can match load resistances, R , up to the values shown below:

Z_0	R_{max}
300	450
460	1058
600	1800
800	3200
1000	5000

The maximum bandwidth will be achieved when the lattice arm reactance variation with frequency is the least. Since each arm is proportional to $\sin \theta$, it follows that when the variation of $\sin \theta$ is the least, broadest bandwidth will be

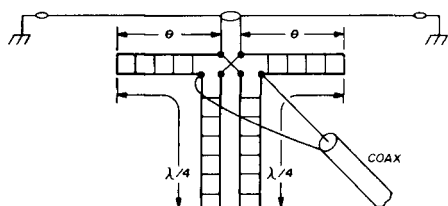


fig. 5. Typical open-wire impedance-matching balun based on the simplified circuit in fig. 3. In this case the balun is suspended from the center of a balanced antenna.

attained. This occurs when $\sin \theta$ is near unity, which means you ought to choose a value for Z_0 somewhere near (but always greater than) $2\sqrt{R_{in}R}$.

For $Z_0 = R_{in}$, $\sin \theta = 2\sqrt{R/Z_0}$ and Z_0 can be no smaller than $4R$. This matching

balun is not too well suited, therefore, to very high impedance antennas.


For an antenna resistance of, say, 400 ohms, to match a 50-ohm coax using 300-ohm twin lead for the balun requires $\theta = 70.5^\circ$ and $\theta_1 = 289.5^\circ$. The equivalent lattice arms are $(300 \sin 70.5^\circ)/2 = 141.4$ ohms and $(300 \sin 289.5^\circ)/2 = -141.4$ ohms. Transformation is $(141.4^2)/400 = 50$ ohms. The reactances across the input and output terminals are $(300)/(\tan 70.5/2) = 424.3$ ohms and $(300)/(\tan 289.5/2) = -424.3$ ohms, and are in anti-resonance.

As a final example, suppose you wanted to feed a grounded vertical antenna having a base resistance of 36 ohms, using 300-ohm twin-lead, and also wanted to use twin-lead for the balun matching section. $\theta = 43.85^\circ$ and $\theta_1 = 316.15^\circ$ for this case, so for 7.2-MHz operation you would need 13.64- and 98.32-feet of twin-lead for the two lines (remember to cross the connection).

references

1. R. W. Johnson, W6MUR, "Two-Band Antenna Matching with Stubs," *ham radio*, October, 1973, page 18.
2. R. W. Johnson, W6MUR, "Transmission Line Matching Using Two Fixed Capacitors," *ham radio*, September, 1973, page 58.

ham radio

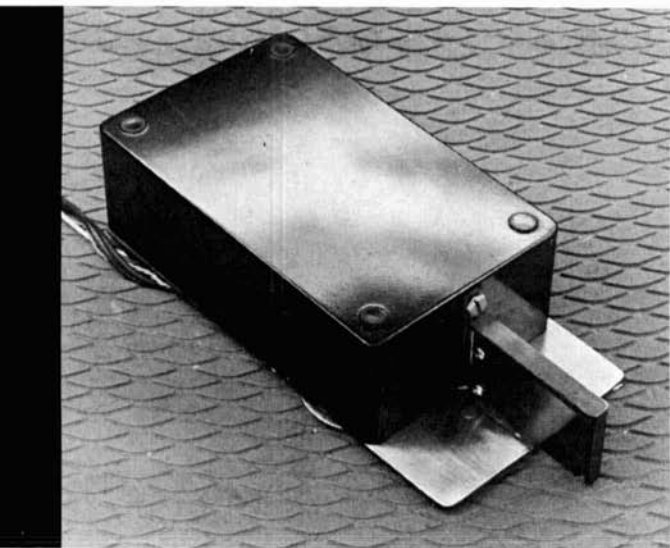

compact electronic keyer package

Complete
electronic keyer,
ac power supply
and squeeze paddle
in one
compact package

Gene Brizendine, W4ATE, Huntsville, Alabama 35803

As the panorama of amateur equipment design flows on, transceivers and compact solid-state power supplies have rendered operation from your boat, car or camper increasingly attractive. Strangely enough, in this enlightened age of integrated circuits, the electronic keyer has hardly kept pace, and it generally comes in two packages, or one bulky one.

Early labor-saving electronic keyers required sizeable power supplies and heat-radiating tubes and required considerable operating desk space. The keyer described in this article emphasizes compact packaging, rather than electronic features. Briefly, what is probably the most advanced squeeze paddle circuit, including 16 ICs, power supply and monitor, is housed in a package the size of a conventional bug. The circuit is essentially that used in the Pickering keyer.¹

construction

Printed-circuit board is used extensively because of its rigidity, shielding and

ease of working. A sheet of PC board forms the base, which supports all components. An inverted bakelite instrument case, approximately 6x3x2 inches, forms the cover. The cover is shielded with a sheet of heavy aluminum kitchen foil, cemented to all inside surfaces and ex-

are inserted into holes forming a square, with pin 8 (+) at the topmost corner and the ground lead, pin 4 (-) at the bottom corner. Thus, IC power wiring is completed by joining all top corners with a positive voltage bus and connecting the bottom corners to ground. This method

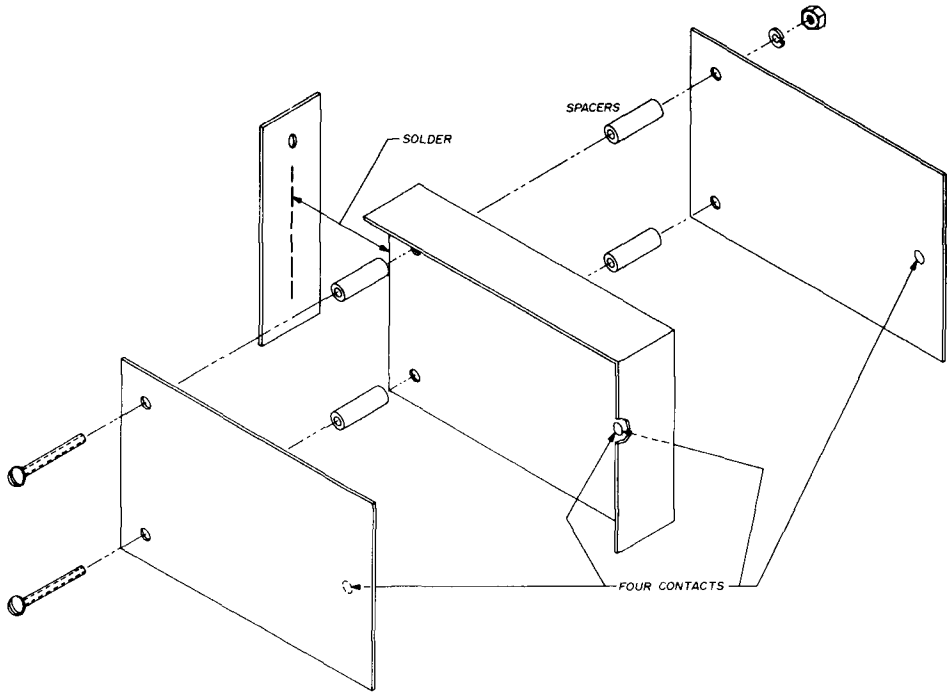


fig. 1. Squeeze paddle details. The middle double-sided PC board carries the stationary contacts. Single-sided PC board is used for the dot and dash paddles.


tending over the edges, where it is clamped against the base in final assembly.

The RTL logic was wired in when the keyer was designed several years ago. However, an even more compact design is now possible with DIP devices and printed-circuit techniques.

To simplify the IC wiring, perforated board is used, with holes punched in a 45-degree pattern. Eight leads of each IC

quickly connects 32 leads and also allows easy identification of the remaining pins.

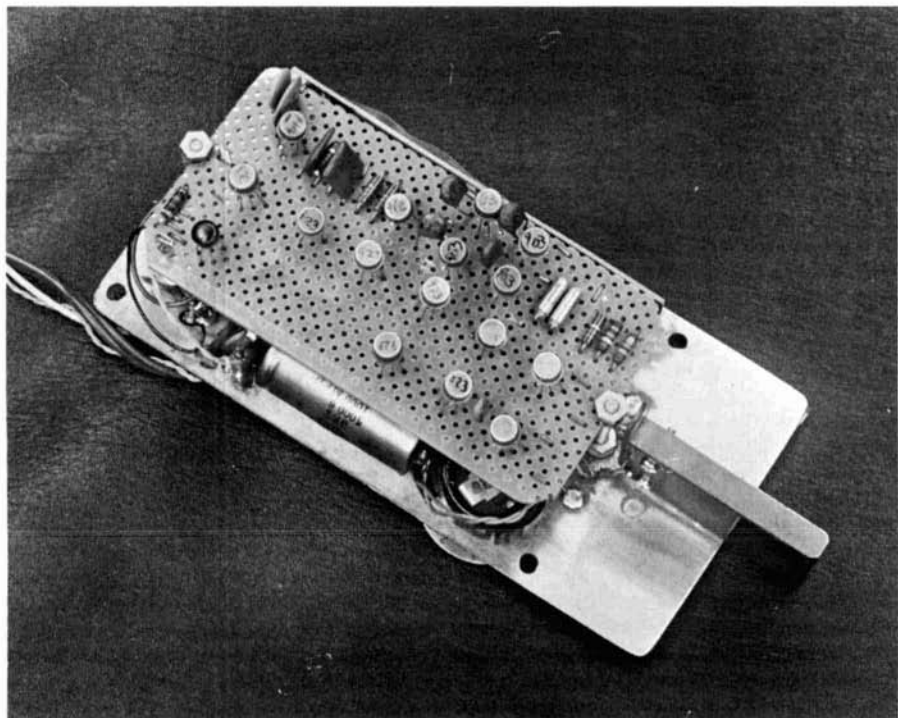
The 3-volt IC power supply components are mounted on vertical strips of PC material which are soldered to the base. A pocket transistor radio output transformer serves as a compact power transformer. After completing the IC board and power supply wiring the board is secured to the base with two studs.



Keyer with the cover removed showing the ICs and discrete components mounted on perforated circuit board. The speed control is located at the bottom left side of the keyer (foreground).

squeeze paddle

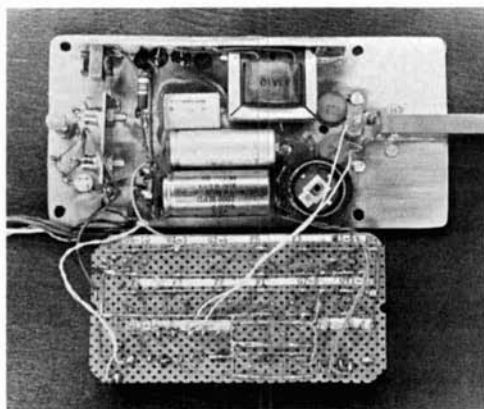The squeeze paddle assembly is also constructed of PC board as shown in fig. 1. The double-sided stationary portion is made very rigid by soldering strips along



Interior of the electronic keyer showing the arrangement of the power-supply components and the speed control.

the front, top and rear edges. The bottom edge and the rear strip are soldered to the base. The rear strip is also secured to the cover with one screw.

Coin-silver contacts are soldered at the front edge of the boards to provide maximum travel when pressure is applied at mid-paddle. Some experimenting with spacers between paddles may be necessary to satisfy your particular preference. If audible clicking is objectionable, the inner surfaces may be covered with sound-absorbing felt or flocking spray.

The light, compact package shown may be attached on the operating desk with double-sided masking tape. At my station it has given four years of carefree operating pleasure.

reference

1. T. Pickering, W1CFW, "The Micro-Ultimate," 73, June, 1966, page 6.

ham radio



Problem-solving handbooks

Highly popular Editors and Engineers books from Sams give amateurs everything they need to know about radio operation and technology. They're authoritative, clear, and easy to follow. You'll want them for your library.

Famous E&E RADIO HANDBOOK—19th Edition By William I. Orr, W6SAI

The completely updated electronics industry standard for engineers, technicians, and advanced amateurs. Shows how to design and build all types of radio-communications equipment. Includes ssb design and equipment, RTTY circuits, latest semiconductor circuits, IC's, and special circuitry. No. 24030—\$14.95

SINGLE SIDEBAND: THEORY & PRACTICE By Harry D. Hooton, W6TYH

A basic text covering the origin of ssb, derivation of signals, sideband selection, ssb generators, carrier-suppression techniques, carrier generators, speech amplifiers and filters, balanced mixers and converters, low-power ssb transmitters, linear r-f power amplifiers, and much more. No. 24014—\$6.95

SEMICONDUCTOR AMATEUR PROJECTS By Louis M. Dezettel, W5REZ

For the ham who still takes pride in using his hands and head, here are projects for 16 useful, money-saving accessories, using easy-to-build semiconductor circuitry. Units are for measuring equipment, increasing power and adding convenience, etc. No. 24025—\$4.95

MARINE SINGLE SIDEBAND By Donald M. Stoner and Pierre B. Goral

Covers the why and how of single sideband; interpreting specifications, alignment tests and measurements, installations, securing a limited coastal license, high-seas telephone service, and marine radio terminology. No. 24029—\$5.95

RADIO AMATEUR OPERATING HANDBOOK By Marshall Lincoln, W7DQS

This single-source working guide is a practical aid for improving the operating methods and techniques of hams. No. 24028—\$4.95

SOLID-STATE QRP PROJECTS By Edward M. Noll, W3FGJ

By building QRP equipment you learn solid-state technology, since these rigs include transistors and/or integrated circuits. The low-cost units described have power ratings from less than 100 milliwatts up to about 20 watts. Both cw and phone rigs are included. No. 24024—\$4.25

73 DIPOLE AND LONG-WIRE ANTENNAS By Edward M. Noll, W3FGJ

Detailed construction data for 73 different types of wire antennas. Appendices describe construction of noise bridges and line tuners, plus data on measuring resonant frequency, velocity factor, and SWR. No. 24006—\$4.50

73 VERTICAL, BEAM, AND TRIANGLE ANTENNAS

By Edward M. Noll, W3FGJ

Design and construction of 73 different antennas used by amateurs, each built and air-tested by the author. Also construction of noise bridges, transmission-line tuners, and measurement methods. No. 24021—\$4.95

ELECTRONICS FOR THE AMATEUR

By Louis M. Dezettel, W5REZ

Covers radio-wave propagation as it applies to amateur band frequencies, reception and transmission pertaining to ham equipment, and the special field of antennas and how to feed them. Provides you with everything needed to pass the theory sections of the FCC exams. No. 24022—\$7.95

RADIO TRANSMITTER PRINCIPLES AND PROJECTS

By Edward M. Noll W3FGJ

Basic and advanced subjects include radio-frequency oscillators, multipliers, and amplifiers; all modes of modulation; and the important electron devices used. Each chapter presents a related project for beginners and students. No. 24031 \$6.95

AMATEUR TESTS AND MEASUREMENTS

By Louis M. Dezettel, W5REZ

Shows how to accomplish virtually all performance tests on amateur transmitters, receivers, and antennas, and how to make required adjustments. No. 24007—\$5.50

FROM CB TO HAM BEGINNER

By J. A. Stanley

Tells and shows how to select and tune a communications receiver, listen in on ham bands, send and receive code, pass the Novice license exam, build or buy an amateur transmitter, erect an antenna, and put a ham station on the air. No. 20920 \$4.25

Order from your electronic parts distributor or send coupon below.



EDITORS AND ENGINEERS

Howard W. Sams & Co., Inc. HR113
4300 W. 62nd St., Indianapolis, Ind. 46268

Send me the following books. Nos. _____

_____ \$ _____ encl

Please include sales tax where applicable

Send FREE 1973 Sams Book Catalog

Name _____

PLEASE PRINT

Address _____

City _____ State _____ Zip _____

calculating gain vs height of DX antennas

Using a
simple graph
to predict
the gain
of your DX antenna
if you raise
its height
above the ground

Gerd H. Schrick, WB8IFM, 4741 Harlou Drive, Dayton, Ohio 45432

It is well known that the higher your antenna is, the better it is for working DX. Although some amateurs talk about optimum antenna height, it is generally accepted that the higher the better. The question is, how much better?

Recently, I replaced an 80-foot tower with a 100-foot tower; both towers were available temporarily so I could make some comparison measurements. With the same antennas mounted on both towers, any gain differences had to be attributed to the difference in height. A gain difference of 2 dB was consistently measured, whether I was working local stations or DX. However, comparison measurements with DX stations were more difficult because of fading and other long-distance communications problems.

theory

Any horizontal antenna works in conjunction with the ground and the mirror-image concept can be applied. The formula for radiated power density, P_d vs the radiation angle, α , is

$$P_d = \sin^2 (h^\circ \sin \alpha) \quad (1)$$

where h° is antenna height in degrees of wavelength (1 wavelength = 360 degrees).

The gain difference, in dB, for two different heights, h_1 and h_2 , is:

$$\Delta \text{dB} = 10 \log \frac{P_{d2}}{P_{d1}} = 20 \log \frac{\sin(h_2 \sin \alpha)}{\sin(h_1 \sin \alpha)}$$

For DX work a very small angle of radiation, α , a so-called grazing angle close to zero degree, can be used. Therefore, $\sin \alpha$ is a very small number, much less than 1. The factor \sin^2 becomes very small when the actual antenna height is in the order of a few wavelengths. This results in the following approximation:

$$\text{dB}_{\text{DX}} = 10 \log \frac{h_2^2}{h_1^2} = 20 \log \frac{h_2}{h_1} \quad (3)$$

This is a surprisingly simple formula. Since the wavelength factor has dropped out, it is no longer necessary to express antenna height in electrical degrees — absolute feet or meters will do. Doubling your present antenna height will give you a maximum gain of one S-unit (6 dB). This is shown in fig. 1.

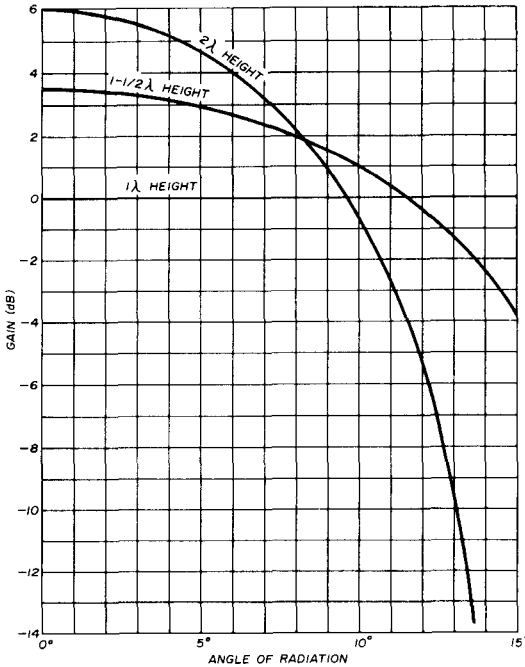


fig. 2. Power density vs angle of radiation for antennas 1½- and 2-wavelengths above ground, as compared to an antenna 1-wavelength above ground.

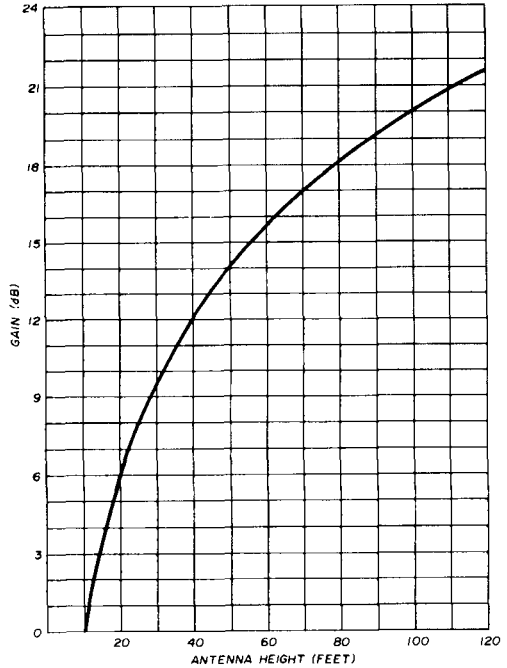


fig. 1. Antenna gain in dB for DX obtained by increasing height of an antenna above ground (angle of radiation less than 3 degrees). Referenced to zero dB gain at 10-foot antenna height.

example

In my case, where I increased my tower height from 80 to 100 feet, the expected power gain is predicted by eq. 3:

$$\text{dB} = 20 \log \frac{100}{80} = 20 \log 1.25 = 1.9 \text{ dB}$$

This is in very good agreement with the practical measurements described previously.

Fig. 2 shows the difference in power density in dB versus the angle of radiation for horizontal antennas 1-, 1½-, and 2-wavelengths above ground. This graph is based on the use of the exact formula given in eq. 2. It can be seen that the approximation in fig. 1 is quite accurate for radiation angles less than about 3 degrees. Certainly, it is not possible to obtain higher gain than that implied by fig. 2.

ham radio

the best of SEASON'S READINGS



... BOOKS from HR !



HAM NOTEBOOK *by The Editors of HAM RADIO Magazine*

The very best from the popular Ham Notebook section in HAM RADIO Magazine. Hundreds of short ideas, simple circuits and useful hints on virtually every subject. Ten chapters including such subjects as Antennas, FM and Repeaters, and Test Equipment. No amateur's technical library is complete without this vital new book.

Just \$3.95 postpaid

New!

Radio Transmitter Principles and Projects

by Edward M. Noll, W3FQJ

A brand new book by popular Ham Radio writer Ed Noll completely covering radio transmitters from basics to advanced subjects. All modes are discussed including CW, AM, SSB and FM. Both tube type and solid state circuits are covered in this valuable volume.

320 pages \$6.95 postpaid

New!

Amateur Radio Awards

by C. R. Emary, G5GH

An exciting new volume listing all of the major international operating awards. Describes over 90 awards including full details, pictures of many, plus instructions for applying. Also includes valuable DX operating data. An absolute must for any active DXer.

Just \$4.95 postpaid

order today from

comtec

Greenville, New Hampshire 03048



HANDBOOKS

We have all three



The Radio Amateur's Handbook

ARRL Staff

The standard reference for the radio amateur. Latest 1973 edition covers everything from the basics to such new areas as FM and slow-scan TV. The largest selling technical book ever published.

702 pages, softbound

Only \$4.50

RSGB:

Radio Communication Handbook

Amateur Radio's most complete technical reference. This book covers virtually every phase of radio theory and practise in very complete and useful detail. Whether you use HF or VHF, SSB or RTTY you need this handbook.

832 pages, hardbound

Just \$14.95

Radio Handbook, 19th Edition

by William I. Orr, W6SAI

Latest updated edition of this famous handbook which is the standard for engineers, technicians and advanced amateurs. Explains in detail how to design and build all types of radio equipment, RTTY circuits, latest semiconductor and computer circuitry. 896 pages; hardbound.

Only \$14.95

SPECIAL HANDBOOK PACKAGE

All 3 for just \$29.75

Save nearly \$5.00

SCANNER - MONITOR SERVICING DATA

Volumes I and II



Two important new books containing servicing data for over 50 of the most popular UHF and VHF receivers now in use. Last minute information includes schematics, voltages, alignment, parts lists, crystal data, pictorials and troubleshooting information.

Volume I contains B & K, Browning, Johnson, Midland, Pace, Pearce-Simpson, Penney's, Realistic, Sonar, and Teaberry.

Volume II has models by Electra, Midland, Regency, Tennelec and Unimetrics.

Either volume \$4.95

Both for \$9.00


Transistor Specifications Manual

6th Edition

by the Howard W. Sams Engineering Staff

Contains the electrical and physical parameters for virtually all of the transistors now in use. Also listed are frequency, gain, and leakage parameters. Includes a special section on rf power transistors. The book we use here at Ham Radio.

Only \$4.50

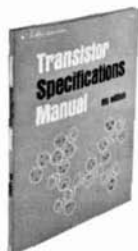

order today from

comtec

Greenville, New Hampshire 03048

antenna and control-link calculations for repeater licensing

How to calculate the
antenna patterns
and control links
required for
your new FCC
repeater license

The new FCC repeater regulations are admittedly a tough act to follow. In particular, the antenna pattern and control-link power justification seem to be difficult to obtain. These items may be calculated directly rather than measured, since either method is acceptable to the FCC. No attempt will be made to derive or justify the formulas employed, but references for each are included wherein they are most adequately treated. With-

out attempting to ruffle any feathers, I feel that anything tending to raise the amateur's technological level above that of appliance operation and CB can't be all bad.

the antenna pattern

The first problem is to produce an "antenna pattern" and the supporting data to satisfy 97.41 (f)(3,6 and 7) of the new repeater regulations. Any repeater group possessing an antenna range or instrumented helicopter can pass immediately to control-link calculations on page 60. Antenna patterns can be measured of course, but great pains must be taken to guard against reflections, to be certain that only the far-zone pattern is sensed and that the instrumentation is in calibration. All in all, it would require an effort far beyond the meager resources of our group.

A calculated pattern approaches the actual radiation pattern only when the antenna is well clear of obstructions. This condition tends to be met only at vhf and above. Calculating the radiation pattern for an arbitrary current distribution is an extremely messy proposition, but if the antenna can be characterized as a linear array with equal current elements, considerable simplification can be obtained using pattern multiplication. Simply stated, you can separately calculate the patterns due to length, to width and to the individual elements and obtain the overall pattern by multiplying them all together,

P. J. Ferrell, W7PUG, 6021 South 119th Street, Seattle, Washington 98178

provided the elements and their currents are all the same. Fortunately, the two most popular types of base-station antennas favored for repeater use meet this requirement.

Type 1, the J-pole or vari-loop antenna consists of dipole type elements mounted on a metal pole, separated about one wavelength and fed with a corporate feed insuring a nearly uniform and inphase current distribution.

Type 2 is typified by the Communications Products "Stationmaster" and the Prodelin "Big Stick" antennas. Home-built antennas of this type have been described in the amateur literature.¹ Some amateurs have "improved" them by specifying foam-dielectric coaxial cable, thereby insuring a non-uniform current distribution and a fair sized reduction in antenna performance. These antennas consist of 8 or 9 pieces of alternating series connected coax, each an exact half-wavelength internal electrical length. Special end elements are on the ends, and all elements are spaced about 0.3 wavelength apart and can be considered to have a shortened dipole pattern.

The vertical (E-plane) pattern of the antennas consists of an element part and an array part. We shall assume a *cosine* voltage pattern for the individual element. This is exact for a short dipole, and is a good approximation to a half-wave dipole. The normalized array part is given by:²

$$E = \frac{\sin(N\psi/2)}{N \sin(\psi/2)}$$

where $\psi = 2\pi D_e \cos \theta$,

N = number of colinear elements

D_e = interelement spacing in wavelengths

θ = elevation angle measured from broadside

The overall normalized E-plane voltage pattern is

$$E = \frac{(\cos \theta) \sin(N\pi D_e \cos \theta)}{N \sin(\pi D_e \cos \theta)}$$

You can see that this pattern depends only on the values of N (number of

elements) and D_e (spacing between any two elements).

The horizontal (H-plane) pattern of antenna type 2 is omnidirectional and that of antenna type 1 can be adjusted to be omnidirectional. It can also be adjusted to give either a figure-8 or a cardioid pattern. These last two cases are difficult to handle because of the reflections occurring due to the support pole.

A fair approximation may be obtained by replacing the reflecting pole with an *image* antenna fed with an equal current, leading in phase by twice the spacing between the element and the support pole. A typical value for element spacing is about 4 inches or 0.1 wavelength. The normalized voltage pattern in this case is given by:³

$$E = \cos [2 \pi D_s (\cos \theta - 1)]$$

where D_s = element spacing from the pole in wavelengths

θ = azimuth angle

Note that if we set $D_s = 0$, then $E = 1$ for all azimuth angles, which is just the omnidirectional case.

Having obtained both E- and H-plane normalized voltage patterns, all that remains is to calculate the gain associated with each and multiply them (add dB) to obtain the overall gain.

Gain is calculated by adding up the total power (integrating) at all angles, recalling that power is proportional to voltage squared. Gain is defined as the ratio of maximum to average (isotropic) power. The FCC regulations specify a half-wave reference dipole rather than the more common mythical isotropic antenna, so a factor of 1.64 (2.2 dB) is tossed in to meet that requirement. This is due to a half-wave dipole having a gain of 2.2 dB over an isotropic antenna.

Even this greatly simplified calculation is likely to prove tedious, and so the job was subcontracted to a digital computer. The *Tymshare Superfortran* program used is listed along with sample printouts in the appendix. The two examples are for a 4-element J-pole set for a cardioid pattern, and a 9-element (Stationmaster)

antenna. Both E- and H-plane patterns are symmetric about the point of maximum gain (0°) so that only half of each need be printed out.

A polar plot of antenna gain in dB, or field voltage for each pattern can be constructed from the printout. If no reflecting mount is present, answer zero when asked "offset from reflecting mount, wavelengths." In this case, no H-plane pattern is printed out. However, it would be wise to construct a circular plot entitled "azimuth pattern" for submission along with the E-plane pattern.

the control link

I now wish to demonstrate compliance with 97.67(b) of the FCC regulations for a repeater control link. A calculation of this sort is commonly referred to as a "power budget." The handiest procedure is to use decibels exclusively in the magic formula:⁴

$$A = 36.6 + 20\log F + 20\log D + M + L_t - G_t + L_r - G_r$$

where A = worst case loss in dB between transmitter and receiver

F = frequency in MHz

D = separation between antennas in statute miles

M = fading margin in dB (typically 20)

L = transmission line losses in dB

G = antenna gains above an isotropic reference in dB

Clearly, antennas, transmission lines and the propagation path can all be represented together as an attenuator of A dB.

A certain calculable amount of signal power is required at the receiver input to insure satisfactory link performance, and the necessary transmitter power output is just A dB above that amount. The required receiver input signal power may be calculated from:

$$R = -204 + 10\log B + NF + CNR$$

where R = required input signal power in dBW (dB below 1 watt)

B = receiver i-f bandwidth in Hz

NF = receiver noise figure in dB

CNR = required i-f carrier-to-noise ratio in dB to obtain satisfactory receiver performance. A typical value for an fm receiver is 12 dB

Finally, the required transmitter power is $T = R + A$, T in dB relative to 1 watt (dBW)

The following numerical example was submitted to the FCC with the Seattle Repeater Group's application for a repeater license. At 450 MHz, for the given 25-mile path, loss between isotropic antennas is given by $36.6 + 20 \log F + 20 \log D$.

118 dB	median path loss, Green Mountain to Seattle
2 dB	repeater uhf receiving antenna gain (dipole)
4 dB	repeater site transmission line loss
9 dB	control site antenna gain
5 dB	control site transmission line loss
116 dB	median loss between units
20 dB	fading and diffraction loss margin
136 dB	worst case path loss between transmitter and receiver
-159 dBW	thermal noise power in 32 kHz i-f bandwidth (KT = -204 dBW/Hz)
15 dB	receiver noise figure
15 dB	required SNR at detector input for reliable tone transmission
-129 dBW	signal power required at the uhf control receiver

The necessary control transmitter power is $136 - 129 = +7$ dBW. Converting to watts, 7 dBW = 5 watts.

references

1. K. W. Sessions, K6MVH, "Colinear Gain Antenna for VHF/UHF Repeaters," 73, July, 1971, page 42.
2. John D. Kraus, *Antennas*, McGraw-Hill, New York, 1961, page 78, equation 4-52.
3. op. cit., page 292, equation 11-55.
4. *Reference Data for Radio Engineers*, Howard W. Sams & Co., Inc., Indianapolis, 1968, page 26-19.

ham radio

LIKE FM OR CW ?



*Then you'll love
Data Engineering's
new catalog*

Write for your free copy today!

TOUCH TONE PADS

More features than any other pad including built-in monitor speaker and latest Phase-Lock loop circuitry.

TTP-1 Standard pad for portable transceiver mounting.

TTP-2 Standard pad in attractive case for home or mobile use.

TTP-3 Mini-pad in attractive case for home or mobile use.

TTP-4 Mini-pad for portable transceiver mounting.

TTP-1, 2, 3 & 4, Sh. wt. 1 lb. \$44.50

TTP-1K, 2K, 3K & 4K, Sh. wt. 1 lb. \$34.50

CRICKET 1


A popularly priced IC keyer with more features for your dollar. Cricket 1 is a small size, solid state keyer designed for the beginner as well as the most advanced operator. It provides the user with fatigue-free sending and its clean, crisp CW allows for easy copying at all speeds. Turned on its side, the Cricket can be used as a straight key for manual keying.

CRICKET 1 Sh. Wt. 3 lbs. \$49.95

2-METER PREAMP

Specially made for both OLD and NEW receivers. The smallest and most powerful preamp available. Provides 20dB gain at 2.5 N.F. to bring in the weakest signals.

Sh. wt. 4 oz. \$9.50 kit
\$12.50 wired

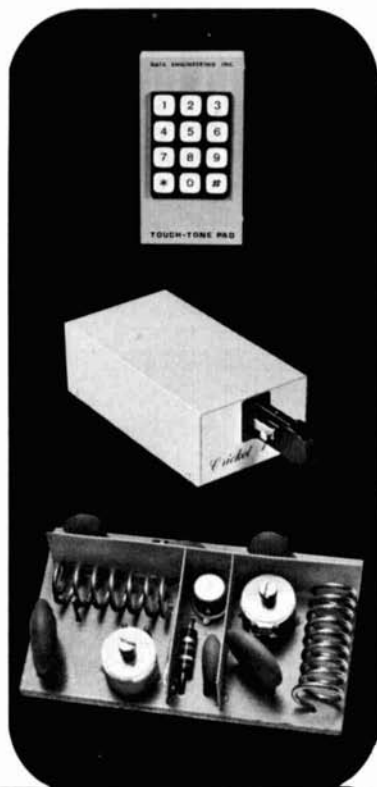


Please include sufficient postage for shipping.

DATA ENGINEERING INC.



Ravenswood Industrial Park, Springfield, Va. 22151

5554 Port Royal Road • 703-321-7171

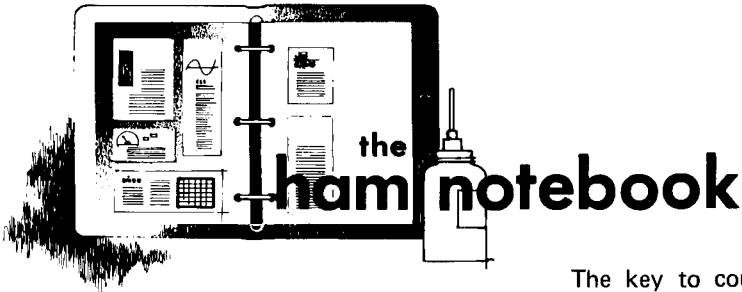

RTTY line length indicator

When using radio teletype it is my practice to try to type some of my reply while printing the transmission of my contact. To do this I use a model 15 typing unit which prints the incoming

The key to counting the number of words in a line is a stepping relay. I use a Guardian resetting type relay. Two microswitches are used to actuate the relay coils. These are mounted under the keyboard of the typing unit and are so positioned that when the space bar is pressed it also strikes the microswitch lever. This switch then closes the circuit to the advancing coil on the stepping relay, advancing it one step.

The other microswitch is positioned under the carriage return key. When this key is pressed this switch actuates the circuit to the relay reset coil. The relay is then reset and is again ready to count the spaces in the next line.

The usual practice is to have ten words per line. I connected my stepping relay to make contact on the 10th, 11th, 12th and 13th steps. When this contact is reached, the alarm circuit is energized. A bell, buzzer, light or other signal can be used. As this relay is a 115-volt ac unit, I use a GE B1A neon bulb in a red panel mounting. This bulb must be used in series with a 7500-ohm resistor. The light is mounted next to the keys and the frame of the typing unit.

After ten spaces or steps the light comes on and stays on for the next three steps. If advanced any further it will go out and you will know you have gone beyond the usual line length. You don't have to worry about over advancing the relay. It goes to the limit and that's all. The stepping relay should be mounted in an insulated box for quiet operation. I also shock mounted mine.

Hal Dressel, W2UVF

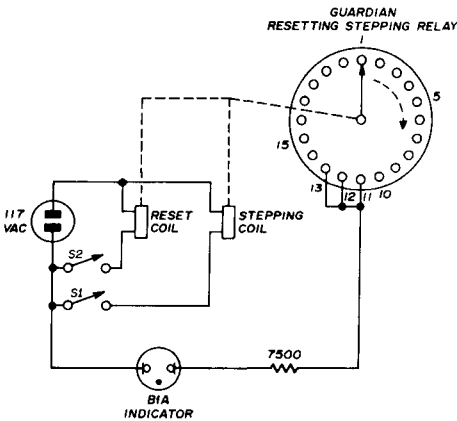


fig. 1. Circuit for the RTTY line length indicator uses a Guardian resetting-type stepping relay. Microswitch S1 is mounted under the space bar. Microswitch S2 is located under the carriage-return key.

signal while I am using the keyboard to punch a tape on my model 14 reperforator. As I cannot see what I am typing or tell when I reach the end of a line with this system, I have designed a system to count the words or spaces in the usual teletype line.

ssb filters

Recently, a short item on sideband location was published in *ham radio*, based upon information published in the instruction manuals for the Swan 500 and the Collin S-Line. There was mention of the need to maintain an adequate separation from a band edge. There are several other aspects of filter performance, some of which are easily demonstrated in a receiver or transceiver. By making these tests, a phone operator may have a better understanding of just where his sideband lies, and where he may produce or receive interference.

Without an antenna, or on a dead band, turn on the calibrator and set the dial to zero-beat with the signal. Then, turn the marker to that setting. Now, swing the dial and note the S-meter reading for the maximum signal strength off to one side. This maximum may be adjustable by the preselector tuning control, so that the bandwidth can be noted for different signal levels.

Turn the dial away from zero-beat until the beatnote has dropped to one of several convenient levels, and finally disappears in the noise. Make a note of these dial settings. Then change to the other sideband and repeat the test.

In the case of my Collins S-Line, the normal 2.1-kHz filter (for receiving only, it has also the 1.5 and 3.1 kHz filters) drops down or out about as follows:

Peak signal	LSB	USB
S7	+3.5 kHz	-3.5 kHz
S9 + 10 dB	+4.2 kHz	-4.2 kHz
S9 + 20 dB	+4.4 kHz	-4.4 kHz
S9 + 20 to S3	+3 kHz	-3 kHz

The size of an S-unit must not be taken as 6 dB. It is about 4½-dB on the Collins 75S3A meter at S9, and less than 3dB around S3. The marked range of 20 dB for S3 to S9 is about correct on my meter, indicating an average of 3.3-dB per S-unit. It takes only 10 dB to increase the meter from 40 to 60 dB as marked on the scale, but 20 dB above that.

The amount of interference, produced or received, varies with the power and the


conditions. If a station talks locally or under good skip conditions with an S9+20 dB signal, he should reduce power as soon as he hears that he is above S9, or suspects it from the strength of the station being worked. Minimum power is required by the Communication Act, Section 324. Otherwise, there may be considerable unnecessary "splatter" due to the filter skirts or equipment problems. In addition, there may be off-frequency emissions greater than those indicated by the filter skirts demonstrated by the above tests. Furthermore, the transmitter can have a somewhat different filter performance than the receiver.

FCC regulations, Section 97.63, says ". . . sideband frequencies . . . shall be confined within the authorized amateur band." It doesn't specify any number of decibels down. This means that the amount of attenuation that is acceptable, depends upon power and propagation conditions, not just -20 dB or -60dB, or any other particular figure. Some standards have been set - BBC Johore, in discussing their harmonic on 14240 kHz, indicated that ITU requires harmonics to be down 60 dB.

The test demonstrates that you must not operate as close to a band edge as previously suggested, even when you have the equipment to comply with the requirement that the frequency of the emissions shall be measured by independent means, and of an accuracy sufficient to assure operation within the band.

The test also shows that interference may be expected from other stations in the range given in the above table, depending upon his filter performance; and that you will produce interference on the opposite side by at least the amount shown, plus any additional hash produced above the filter curve. If you hear the calibrator on the "undesired" side of the zero beat, then you may expect to receive some interference there, and produce some on the opposite side when transmitting, because of the lack of pure *single* sideband operation.

Bill Conklin, K6KA

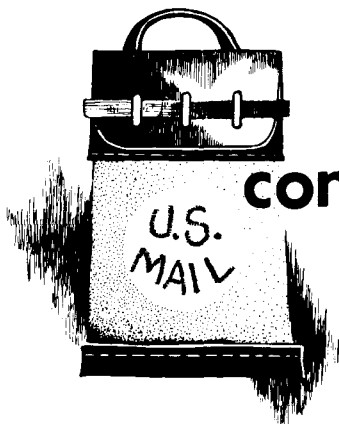

comments

frequency scaler

Dear HR:

Response to the construction article for the simple frequency scaler appearing in *ham radio* for September, 1972, has been most gratifying. That article stirred up the interest of a large number of hams and for many of them it was the impetus for their first-time experience with frequency counters as well as with scalers. To the serious experimenter the article presented no problems. Some difficulties cropped up for the less knowledgeable, however. One of these was that their high-sensitivity, high-impedance counter might indicate twice or even three times the frequency which was fed to the scaler.

Although the solution to this type of problem is really quite simple, a wide variety of schemes have been tried by amateurs in an attempt to solve this problem. One of these schemes is the one which W6MGI described in *ham notebook* of the February, 1973, issue (page 57). For his particular cable and for its particular length, it worked for him. His L-section approach does not provide a general solution, however. The characteristics of his filter will change with every foot of cable he adds or removes (50-ohm cable, for example, has about 28.5 pF per foot).

Any ECL or other very high-speed pulse circuit requires detailed attention to feedback and matching problems. Use of a ground plane which provides a good,

low-impedance ground current return path is one essential. A well regulated power supply is another. These can be and are provided within the scaler itself.

The matching problem can best be met outside of the scaler. Experience with and during development of the scalers manufactured by Belmont Spectrum Research clearly demonstrates that for interconnects of more than about 5 inches (some of this length is within the scaler) the matching problem can only be generally successfully met by providing an adequate line termination. This, of course, cannot be accomplished within the scaler. It is therefore standard practice for manufacturers to caution users that an interconnecting cable (scaler to counter) must be terminated in its characteristic impedance if waveform distortion cannot be tolerated. Whether it is called distortion, ripple, ringing or reflections, is immaterial; the steep multiple wave fronts of ECL or other high-speed pulse systems are what trigger the counter and disconcert the casual scaler user. So — the really simple solution to the matching problem is to terminate the line.

One means of providing a proper termination is to connect a resistor, equal to the characteristic impedance of the line you are using, across the input connector inside the counter. Another means, which is preferred because its use is more flexible and does not entail any change to the counter, is to use a "termination adaptor" at the counter end of the line. This method will provide a proper termination when the scaler is used and when unplugged will permit retention of the counter's regular input for use over its normal range. A BNC tee-connector (UG-274/U) at the counter, with the appropriate resistor connected to one arm of the tee, will do very nicely.

These tees are often available through surplus sources at very low cost.

An even better arrangement is to use the 50-ohm termination adaptor made by Tektronix (part no. 001-0049-01). This adaptor, originally intended for use with Tektronix scopes, is highly recommended. It currently sells for \$10.

Now, as to overall results. My Belmont Spectrum Research scaler will drive up to 18 feet of either 50- or 100-ohm coaxial cable without substantial waveform degradation when any one of these terminating arrangements are used.

F. Everett Emerson, W6PBC
Belmont Spectrum Research
Belmont, California

passive sideband generator

Dear HR:

Although I have been running my passive sideband generator at the signal levels indicated in the article,* (about 3 volts peak rf and 0.3 volt peak audio at the input ports), the audio level should be several volts. I forgot about the extra loss in the resistive output branch of the audio phase shift/network.

An appropriate audio signal level can be deduced as follows. Suppose the peak rf input is 3 volts. After going through the rf phase-shift networks this is reduced to 2.1 volts. A good guess at the modulator resistance is 1000 to 1500 ohms (500 for the balance pot, 200 or so for the diode and 300 to 800 for the load seen through the output rf transformer).

If we pick 1250 ohms, the rf current through a diode is about 1.7 mA. The modulating signal should be small compared to the carrier, ten percent being a usual limit, so the audio peaks should approach, but stay under, 0.17 mA.

The resistance of the audio phase-shift network output branch, including the modulator impedance, has been adjusted to 3900 ohms. Hence, the audio voltage

at an output of the phase shift network should be about 0.66 volt. As noted in Van Heddegem's article, the voltage across the 3-ohm input resistor will then be 1.32 volt, making the total peak input voltage 6.4 volts (about 1.4 watts). This is an upper limit. A third to half of this voltage is adequate while still being ten times what I have been using.

Incidentally, with this higher level of modulation, the carrier balance will be much less critical since a voltage gain of ten or so is thus moved from the sideband amplifier to the audio section.

Worthie Doyle, W7CMJ
Port Orchard, Washington

Dear HR:

Cheers to author Doyle for his fine article on the phasing-type ssb generator in the April issue. Some three or four years ago I built up a solid-state phasing exciter (not exactly passive like Doyle's) and I used a tired 6L6 linear amplifier. I worked Albuquerque, New Mexico, from Libertyville, Illinois, and was heard in Guantanamo Bay, Cuba, on 14 MHz.

For checking the Doyle passive audio phase-shift network I recommend use of an oscilloscope having separate X and Y axis inputs. Leave the *carrier input* of Doyle's fig. 1 disconnected for this test. Disable the sweep of the oscilloscope, and adjust both channels for equal gain. Hook the X input to one side of the phased audio output; the Y input to the opposite side. Talk into the microphone (or use a signal generator) and observe the pattern on the scope from 300 to 3,000 Hz. It should remain a nice circle, changing in diameter with signal level. If not, make adjustments to the circuit until you get the best circle.


Connecting the phase-shift network ground terminal to the oscilloscope chassis ground should cause no change to the geometry. This same method may be used to check the ninety-degree rf phasing as well, but probe lead length and amplifier phase differences inside the oscilloscope can give misleading information.

Paul Schmidt, W9IDP
Libertyville, Illinois

*W. Doyle, W7CMJ, "Phasing-Type SSB Generator," *ham radio*, April, 1973, page 22.

new products

two-meter fm transceiver

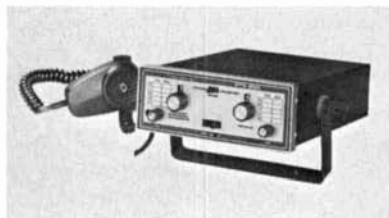

A complete new line of American-made 2-meter fm transceivers for the amateur has been introduced by General Aviation Electronics, Inc. (GENAVE). The new offering includes the GTX-10, the GTX-200, and the previously introduced and very popular GTX-2.

The new GTX-10 fm transceiver is a full 10-channel, 10-watt output unit and retails for \$199.95. The new GTX-200 features independent selection of 10 transmit and 10 receive frequencies, offers 30 watts nominal output power and retails for \$259.95. The well-received GTX-2 provides 10 push-button channels with backlighting for night operation, 30 watts nominal output power and retails for \$249.95.

The radios are manufactured in the same U.S. Government inspected facilities where precision aircraft instruments are fabricated, under the same watchful quality control procedures.

Internally, all radios are equipped with netting trimmers for each transmit crystal. All use standard, readily available, American-made semiconductors. High selectivity 8-pole second i-f filters are incorporated in the design of all three units, and rf output stages are vswr protected.

The GTX line is engineered for use with available tone encoders and auto-patch service, as well as simultaneous operation on MARS frequencies. Externally, all three radios have multi-position switches which include a low power (one-watt) setting for longtime low-power drain operation, and indexed volume and squelch controls.

Each GTX transceiver comes complete with a quick-disconnect power cable, SO-239 antenna connector, mobile mounting bracket and sturdy ceramic plug-in microphone. A 146.94-MHz communications channel is also included. The remaining plug-in crystals are available at \$6.50 each for installation at the factory or by the owner.

The new GTX-10 features superlative cross-mod performance, and is easily cross-wired for duplex crystal operation. The circuit board is laid out so that conversion to 30-watt output can be accomplished quite easily.


The new GTX-200, with independent selection of 10 transmit and 10 receive frequencies, offers 100 possible channel combinations. A switch for lock-in of preselected frequency pairs allows simple one-knob operation when desired. High sensitivity is assured by incorporation of a dual-gate mosfet in the receiver front-end. An external speaker jack is provided on the rear panel.

The popular GTX-2 has been refined and updated for superior sensitivity with the same dual-gate mosfet in the receiver front-end as is found in the GTX-200.

The new radios are founded on the technology and know-how derived from Genave's experience as a leading manufacturer of a full line of navigation and

communications radiotelephones for the marine industry. For more information, write to General Aviation Electronics, Inc., 4141 Kingman Drive, Indianapolis, Indiana 46227, or use *check-off* on page 110.

touch-tone encoder enclosures

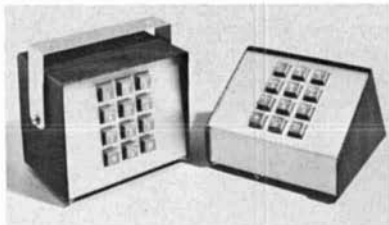


There has been a tremendous increase in the use of Touch-Tone encoders for use in autopatch and other special control systems in fm repeaters. Now two compact enclosures are available for Touch-Tone pads — one for base stations and one for mobile use. The Touch-Tone pad is held properly in position by pre-mounted internal brackets.

The top and sides of the enclosure are covered with walnut-grained vinyl. The satin anodized aluminum face is die punched to accept standard 12-button Touch-Tone pads such as those manufactured by Western Electric, Stromberg-Carlson, ITT-Kellogg, etc. (Automatic Electric Touch-Tone pads will not fit because they use non-standard spacing between the buttons.)

The mobile mount "M" Touch-Tone enclosure has an anodized pivoting gimbal bracket which provides multi-position mounting under the instrument panel, as well as top-of-equipment mounting on four rubber feet. The base station "B" enclosure holds the Touch-Tone pad at a convenient 30-degree angle. There is ample room inside both enclosures for transmitter keying circuitry. Either model is available for \$6.25 including postage from the Detroit Area Repeater Team, Post Office Box 201, Clawson, Michigan 48017. For more information, use *check-off* on page 110.

HUSTLER

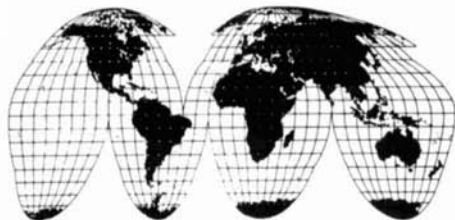

HF

VHF

UHF

AMATEUR ANTENNAS

Each Hustler antenna design is specifically optimized for amateur band performance. Every assembly is manufactured from the best available materials under carefully controlled quality standards to give you superior mechanical and electrical performance. For more than a decade, reliability has been our foremost desire!

COMMUNICATIONS WORLD has all **HUSTLER** models in stock at ALL TIMES. Ready for pickup or delivery to anywhere in the world. Write or call for free catalogue.

COMMUNICATIONS WORLD INC.

4788 STATE ROAD
CLEVELAND, OHIO 44109
(216) 398-6363

(Northeastern Ohio's most
complete communications
center)

L. I. Electronic Supermart (Off the wall self service)

New P.C. Boards — G10, 1 oz. - 1 side copper-fiber glass

6" x 6", 80¢ ea. — 6 x 12, \$1.50 ea. - 12 x 12, \$2.85 ea.

New P.C. Boards — G10, 1 oz. - 2 side copper-fiber glass

6" x 6", \$1.10 ea. - 6 x 12, \$2.00 ea. - 12 x 12, \$3.75 ea.

New P.C. Boards — G10, Fiber glass punch:

F Pattern 4.5 x 6.5, .062 holes, 5 per 1" \$1.30

P Pattern 4.5 x 6.5, .042 holes, 10 per 1" \$1.35

G Pattern, 4.5 x 6.5, .062 holes, \$1.30

Pkg. 10 Bircher P.C. Board, metal 2" slides \$1.00

Package of 50 flea clips for above punched Boards, .062 75¢

30 ¼ or ½ W resistors, packaged 5 per value your choice of values \$1.00

25-1W resistors, packaged 5 per value, your choice of values \$1.00

15-2W resistors, packaged 5 per value, your choice of values \$1.00

5 ¼ or ½ W, 1% resistors, packaged 5 per value, your choice of values .50

5 ceramic disk caps, .001-01, packaged 5 per value, your choice of values .50

5 mica dip caps, 1 pf-150 pf, packaged 5 per value, your choice of values .50

5 mica dip caps, 180 pf-820 pf, packaged 5 per value, your choice of values .75

5 mica dip caps, 910 pf-1500 pf, packaged 5 per value, your choice of values \$1.00

Wire Kit #22 solid PVC, 6 spools, 6 colors, 50' ea. spool \$3.50

Wire Kit # 22 stranded PVC, 6 spools, 6 colors, 50' ea. spool \$3.50

Wire Kit #24 Solid PVC, 6 spools, 6 colors, 50' ea. spool \$3.50

Wire Kit #24 stranded PVC, 6 spools, 6 colors, 50' ea. spool \$3.50

10' — Ten cond. ribbon wire, color coded, #22 or #24, stranded \$1.50

C & K #7101 mini switch, SPDT on-on \$1.05

C & K #7103 mini switch, SPDT on-off-on \$1.20

C & K #7201 mini switch, DPDT on-on \$1.35

C & K #7203 mini switch, DPDT on-off-on \$1.55

Alco 105D MST momentary on-off-momentary on \$1.25

Central Lab DPDT push momentary. SPEC. 4/\$1.00

Connectors, PL259, \$.45; PL258, \$.70; 175U or 176U, \$.20 ea.; UG 88 cu., \$.50; UG 201 a/u (N to BNC adapter), \$.75; RCA to UHF, \$.90.

Encapsulated chokes 1uh to 5 Mh, choice 3/\$1.00

Varo type mini bridge rectifiers, approx. ½" sq. size: 2 amp. - 50 v., \$1.25; 4 amp. - 50 v., \$1.25; 6 amp. - 50 v., \$1.25; 2 amp. - 100 v., \$1.25; 4 amp. - 100 v., \$1.25; 6 amp. - 100 v., \$1.25; 2 amp. - 200 v., \$1.50; 4 amp. - 200 v., \$1.50; 6 amp. - 200 v., \$1.50; 2 amp. - 400 v., \$1.50; 4 amp. - 400 v., \$1.50; 6 amp. - 400 v., \$1.50

Triacs — thermo tab package — 1 amp. - 400 v., \$.80 ea.; 3 amp. - 400 v., \$1.40 ea.; 4 amp. - 200 v., \$1.20 ea.; 6 amp. - 200 v., \$1.40 ea.; 6 amp. - 400 v., \$1.60 ea.; 6 amp. - 500 v., \$1.80 ea.; 8 amp. - 200 v., \$1.60 ea.; 8 amp. - 500 v., \$1.80 ea.

To-5 case, 1 amp. - 200 v., \$.70 ea.; 1 amp. - 400 v., \$1.00 ea.

SCR 200 v. - 8 amp. thermo tab \$1.80 ea.

SEND SELF ADDRESSED ENVELOPE FOR FREE MAILER. INCLUDES MANY HUNDREDS OF ITEMS NOT LISTED ABOVE.

Send check or money order - include 60¢ to cover parcel post and handling. UPS shipping available. Minimum order \$4.50.

FREE BONUS WITH EACH \$10.00 ORDER

50' SPOOL 600 V. #22 PVC WIRE

KRP


ELECTRONIC SUPERMART, INC.

219 WEST SUNRISE HIGHWAY

FREEMPORT, L. I., N. Y. 11520


516-623-3346-9

connector adapters

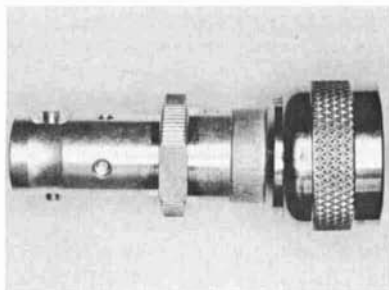

A new series of adapters is now available which will interconnect any combination of cables and connectors having BNC, RCA phono, microphone (Amphenol 5/8-27 type) or type-F (CATV type) terminations. These adapters are intended for use in test equipment, and in audio, video and rf applications. The adapters are priced at \$4.95 each, post-paid in the United States. Order from Adapters Unlimited, Post Office Box 48822, Los Angeles, California 90048. For more information, use *check-off* on page 110.

cw filter

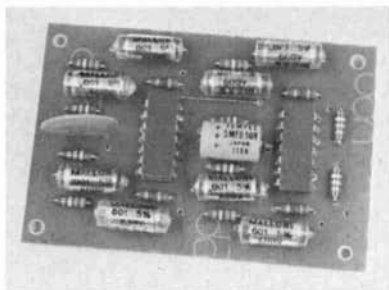

The new audio CW filter available from MFJ Enterprises offers three degrees of switch-selectable selectivity in the same filter. The three bandwidths are 180, 110 and 80 Hz. In the 80-Hz position, response is down 60 dB one octave away (one-half and twice the center frequency of 750 Hz).

There is no insertion loss when this audio filter is switched into the line. Also, with most narrow-band audio filters ringing can make copying impossible. In the new CWF-2 CW filter ringing is nearly

eliminated by the technique of cascading four low-Q stages. This provides very narrow bandwidth and extremely high skirt rejection without audible ringing.

The CWF-2 filter offers very low output impedance and a very high input impedance. This means that, unlike some other filters, no impedance matching is required for optimum performance. Loads greater than 500 ohms produce no distortion and loads less than 500 ohms, such as an 8-ohm speaker, produce some distortion which does not affect copying.

To use the CWF-2 you simply plug it into the phone jack of your receiver or connect it to the speaker terminals. It can also be installed between audio stages in your receiver. The circuit consists of four IC operation amplifiers in an active-filter design which eliminates all inductors and reduces the unit's size to a mere 2x3-inch printed-circuit board.

The CWF-2 CW audio filter is available in kit form for \$9.95, or completely wired, tested and guaranteed for \$12.95. For more information, write to MFJ Enterprises, Post Box 494, Mississippi State, Mississippi 39762, or use *check-off* on page 110.

two-meter collinear mobile antennas

Extremely low radiation angle, 5.2-dB gain over a 1/4-wave ground plane, low swr and wide bandwidth are features of Hustler CG-Series Super Gain two-meter collinear mobile antennas from New-Tronics Corporation.

Model CGT-144 is complete system including collinear antenna with stainless steel radiating sections, 180° swivel ball, heavy duty trunk lip mount for easy "no holes" installation on side or edge of trunk lip, and 17-foot RG-58/U coax with factory-attached connectors. Power rated at 200 watts fm, the completely operational CGT-144 has a swr of 1.1:1 (typical) at resonance and a swr within 1.5:1 over its 6-MHz bandwidth of 143-149 MHz. Overall length is 86 inches.

B&K professional test equipment for the HAM...



MODEL 1470 DUAL TRACE OSCILLOSCOPE

Displays dual waveforms in 6 modes, including chopped, add, alternate and Ch. 2 inverted. DC to 10 MHz bandwidth; 10 mV/cm sensitivity. Triggered, automatic sweep system, with 1 μ SEC/cm to .1 SEC/cm; to .2 μ SEC/cm with 5X magnification. Less probes (2 required).
PR-20 PROBE. Set of 2 \$39.50
MODEL 1470 DUAL-TRACE OSCILLOSCOPE
\$529.95



MODEL 1601 0-50VDC REGULATED SUPPLY

Foolproof overload protection — unit shuts down automatically when overload occurs. Simplified current limit setting — does not require application of short circuit to output terminals. 0.2 amps fully regulated output, in 4 ranges.
MODEL 1601 REGULATED POWER SUPPLY
\$159.95

PREPAID ANYWHERE IN U.S.A.

OHIO ONLY — ADD 4½% TAX

stotts-friedman

"TRU" — K8JUG

108 N. Jefferson Street
Dayton, Ohio 45402

International Electronics Unlimited

NOVEMBER SPECIALS

Sale Prices end November 30th

7453	7/\$1.00	LM308	.95 ea.	LM747	.75 ea.
7454	7/\$1.00	LM723	.50 ea.	8836	.40 ea.
7460	7/\$1.00	LM739	1.00 ea.	9601	.95 ea.

TTL					
7400	.25	7443	1.25	7493	1.05
7401	.25	7444	1.30	7494	1.10
7402	.25	7445	1.25	7495	1.05
7403	.25	7446	1.45	7496	1.05
7404	.29	7447	1.45	74121	.55
7405	.27	7448	1.50	74123	1.15
7406	.55	7450	.29	74145	1.25
7408	.29	7451	.32	74151	1.05
7409	.29	7453	.32	74153	1.45
7410	.25	7460	.30	74154	1.75
7411	.35	7470	.50	74155	1.35
7413	.95	7473	.55	74157	1.50
7420	.25	7474	.55	74161	1.65
7423	.37	7475	.95	74164	2.95
7425	.39	7476	.55	74165	2.95
7430	.25	7483	1.25	74175	2.95
7432	.30	7485	1.20	74181	4.50
7437	.50	7486	.55	74192	1.65
7440	.25	7489	3.25	74193	1.65
7441	1.25	7490	1.25	74194	1.65
7442	1.15	7492	1.05	75195	1.15

LOW POWER TTL					
74L00	.40	74L42	.80	74L85	1.25
74L02	.40	74L51	.40	74L86	.95
74L04	.40	74L71	.60	74L90	1.75
74L10	.40	74L72	.60	74L93	1.75
74L16	.40	74L73	.80	74L95	1.75
74L20	.40	74L74	.80	74L164	2.95
74L30	.40	74L78	.80		

8000 SERIES					
8091	.69	8123	1.75	8810	.95
8092	.69	8214	1.95	8812	1.25
8093	.69	8280	.95	8831	1.95
8094	.69	8520	1.45	8836	1.25
8095	.69	8551	1.95		

LINEAR					
LM301 TO5	.45	LM311 TO5	1.25		
LM302 TO5	.95	LM380 Dip	1.75		
LM304 TO5	1.25	LM709 TO5-Dip	.39		
LM308 TO5	1.25	LM723 Dip	.75		
LM309K TO3	1.95	LM741 TO5-Dip	.45		
LM309H TO5	1.25	LM747 Dip	.95		

PHASE-LOCKED LOOP MEMORIES-with data					
NE565	2.95	1101	2.95		
NE566	2.95	1103	7.95		
NE567	2.95	7489	3.25		
		8223	6.95		

LED					
MV10B Visible red SUPER SPECIAL	.25 ea.				
MV50 type red emitting	.25 ea.			5/1.00	
MV5020 type Large red	.35 ea.			3/1.00	
ME4 Infra red TO18				.69 ea.	
MAN 1 The original				4.25 ea.	
MAN 3 type	1.95 ea.	3 or more	1.49 ea.		
MAN 4 type	2.75 ea.	3 or more	2.50 ea.		
Data-Lite 707 (MAN 1 repl)			4.25 ea.		

CALCULATOR CHIPS					
5001 LSI (40 pin)					
Data supplied with chip				6.95 ea.	
Data only-Refundable w/purchase				1.00 ea.	
5002 LSI (40 pin) for battery power					
Data supplied with chip				8.95 ea.	
Data only-Refundable w/purchase				1.00 ea.	
5005 LSI (28 pin) four function memory					
Data supplied with chip				10.95 ea.	
Data only-Refundable w/purchase				1.00 ea.	

DIGITAL CLOCK . . . on a Chip					
MM5311 (28 pin) with spec sheet				11.95 ea.	
MM5312 (24 pin) with spec sheet				8.95 ea.	
MM5314 (24 pin) with spec sheet				10.95 ea.	
MM5316 (40 pin) with spec sheet				15.95 ea.	

Satisfaction guaranteed. All items except as noted are fully tested. Minimum order \$5.00 prepaid in U.S. and Canada. Calif. residents add sales tax. Orders filled within 3 days after receipt. Please add \$.50 per spec sheet for items priced at less than \$1.00 ea.

INTERNATIONAL ELECTRONICS UNLIMITED

P. O. BOX 1708H
MONTEREY, CALIF. 93940

The Hustler Model CG-144 consists of the 84-inch collinear antenna with 3/8-24 threaded base to fit standard mobile ball mounts. It has the same electrical characteristics as the Model CGT-144. For complete specifications contact New-Tronics Corporation, 15800 Commerce Park Drive, Brook Park, Ohio 44142, or use *check-off* on page 110.

base command



The PACE Communications division of Pathcom, Inc. today announced a new special purpose instrument called *Base Command* designed for sophisticated control of base station operation on the amateur two-meter band. Designed specifically to keep constant surveillance on the performance of your base station, the P5407 *Base Command* is placed in the transmission line between your transmitter and antenna to monitor and control the functions of your transmitter.

Antenna installation efficiency is measured by checking the standing-wave ratio. The transmitter power is measured on one of three scales; the 5-watt and 50-watt levels terminate in an internal dummy load. The 500-watt scale samples power while it's going through the line to the antenna.

The modulation capability of the transmitter is measured on the reference meter. The audio quality of your transmitted signal may be monitored continuously. The unit also provides a visual "on the air" indication. Performance of your hand-held or mobile sets can also be checked with the built-in field strength meter. A television interference filter is also built into the P5407.

This is where the name, *Base Command*, was designated since this versatile instrument not only monitors but controls the base-station transmitter. For more details, write to PACE Communications, Box 306, Harbor City, California 90710 or use *check-off* on page 110.

phase-locked loop handbook

The complete story of the phase-locked loop is told in a free 76-page paperback entitled *Signetics Linear — Phase-Locked Loops Applications Book*, recently published by Signetics Corporation, a subsidiary of Corning Glass Works. The book is a companion to the larger *Linear Specifications Handbook* which is also available, although it must be requested separately, according to Jack Mattis, manager of consumer product marketing in the company's linear department.

Phase-locked loops are a new class of monolithic integrated circuits developed by the Signetics research and development department in 1969 and marketed by the firm during the following year. They are based on frequency feedback technology which dates back 40 years. A phase-locked loop is basically an electronic servo loop consisting of a phase detector, a low-pass filter and a voltage-controlled oscillator. The controlled oscillator phase enables the PLL to lock or synchronize with an incoming signal.

In addition to the dash of history given in the book's introduction, other sections provide a short glossary and descriptions of the phase-locked loop principle and PLL "building blocks." Major sections include explanations of general loop setup and tradeoffs, PLL measurement techniques, monolithic phase-locked loops, expanding loop capability, and specific applications.

Some of the more interesting passages contain information on how the user of the PLL can apply the circuit to his own projects. As a functional building block, the phase-locked loop is suitable

You can step up to the "State-of-the-Art" in Electronics the easy way



Five easy-to-understand, plain language courses have been developed for you. Now, you can learn

practical electronic design techniques without the use of higher mathematics. You don't

have to take time off from work or home duties. You can do all the things

you want to

do and still be advancing your career. You get the highest degree

of personalized instruction on a one-to-one basis. Whatever you want to achieve in electronics . . .

we can help. Digital Design . . . IC Logic Design

. . . Power Supply Design . . . MOS/FET & J/FET

Circuit Design . . . UJT Circuit Design. The purpose

of each course is to develop your abilities on the job through advanced circuit knowledge. These

courses are structured in easy step-by-step learning patterns with programmed testing. You are a

classroom of one and you set the pace. Send for free details on how you can step up to the "State-

of-the-Art" in electronics to: Mr. Gene Presta, Vice President of Academic Affairs, The Center For

Technical Development, 2876 Culver Avenue, Dayton, Ohio 45429,

Telephone: (513) 296-1020.



Registration No. 73-06-0402H

a wholly owned subsidiary of Kurz-Kasch, Inc.



**CRAIG
RADIO**

**AMATEUR
RADIO
ELECTRONIC SURPLUS
USED COLLINS A SPECIALTY
WE BUY & SELL**

INTRODUCTORY SPECIALS

30S-1 with new spare 4CX-1000	\$895.00
62S-1	\$625.00
KWS-1 & 75A-4	\$700.00

Rte 1 Bypass, Southbound
Kittery, Maine
207-439-0474

Mail Address
P. O. Box 615
Portsmouth, N. H.
03801

**JIM CRAIG
W1FBG**

NEW! IC KEYER



Only
\$87.50
PPD
USA

- Self completing dots and dashes.
- Dot memory for easy keying.
- Precision feather-touch key built-in.
- Sidetone oscillator and speaker built-in.
- Relay output keys 300-V @ 100-ma.
- Keyed time base. Instant start.
- 5-50 wpm. Perfect dot-dash ratio.
- Send QSL or postcard for free brochure.

**PALOMAR
ENGINEERS**
BOX 455, ESCONDIDO, CAL. 92025

for a wide variety of frequency-related applications. These generally fall into one or more of the following categories: fm demodulation, frequency synthesis, frequency synchronization, signal conditioning, and a-m demodulation. Each category is covered by a section in the book.

A number of construction projects are suggested as a means of proving the feasibility of using the phase-locked loop circuit in specific applications. The book provides information on building an fm i-f amplifier and demodulator, a phase-locked a-m receiver, an i-f stage with agc and a-m/fm detection, a translation loop for precise fm i-f generation for tv, a phase-locked FSK demodulator and many others. For a free copy of the handbook, write to Signetics PLL Handbook, Signetics Corporation, 811 East Arques Avenue, Sunnyvale, California 94086.

integrated-circuit fm detector

A unique method of fm detection by a new technique of linear gating is featured in the new Signetics ULN2111 monolithic integrated circuit. This linear device comprises a three-stage limiter and a balanced product detector.

Applications for the ULN2111 device include tv sound channels, fm receivers, automatic frequency control systems and communication receivers. An outstanding feature of the ULN2111 is that only one, simple, low-cost, single-winding coil is required for tuning. Consequently, only one screwdriver adjustment is required to tune a detector circuit which uses the ULN2111.

The frequency range of the ULN2111 extends from 5 kHz to 50 MHz. Outputs of 0.6 V with a total distortion of less than 1% and a limiting threshold voltage of 400- μ V rms are typical. Another feature is a voltage gain of 60 dB. When ordered in small quantities, plastic in-line packages are priced at \$1.50 each.

For more information, write to Signetics Corporation, 811 East Arques Avenue, Sunnyvale, California 94086.


from cb to ham beginner

Whether you are a CBer or an SWL — or anyone else who wants to get started in amateur radio — this book answers your questions. It is an easy-to-read book that explains how to select and tune a communications receiver, listen in on the ham bands, acquire technical knowledge by building and experimenting, learn to send and receive code, build or buy an amateur transmitter, erect an effective antenna, and put an amateur station on the air.

In addition, the author, J.A. Stanley, presents a *fun* way of obtaining your Novice license. Instead of spending countless hours reading dry theory, simple tests are provided that use low-cost, readily available parts. A transmitter project is even included, so you can get on the air as soon as you get your license.

The book is filled with photos and drawings to simplify the subject matter. You need no technical background other than that obtained from operating a CB rig to understand and enjoy this book. It's an invaluable reference source that tells you how to become a Novice-class radio amateur. All the latest FCC Novice rule and frequency changes are included. 144 pages, softbound. \$4.25 from Comtec Books, Greenville, New Hampshire 03048.

non-linear filters

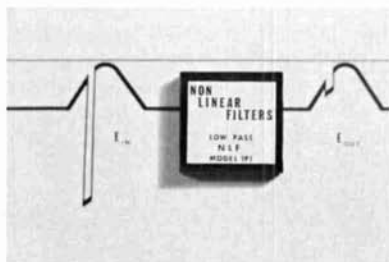

Non Linear Filters has introduced a non-linear low-pass filter module that attenuates frequencies above the corner frequency while introducing no phase shift, either above or below the corner

NES

NURMI ELECTRONIC SUPPLY

Department 28

1727 Donna Road - West Palm Beach, Florida 33401

PHONE — (305) 686-8553


HEP 170 2 1/2 A, 1000PIV, Diodes, Bulk Packs of 10, Factory Fresh.

10/\$3.00 — 100/\$25.00

RCA 40673 DUAL GATE MOS FET
Factory Fresh

5/\$6.00

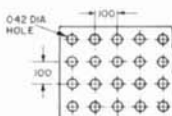KEYSTONE PERF BOARD
G-10 Glass Epoxy
Perf Board 3/64"
Thick.



No.	Size (in.)	Price
--UNCLAD--		
4229	2 x 4 1/2	\$.85
4230	2 x 6	1.09
4231	4 1/2 x 6	1.55
4232	17 x 6	5.75
--COPPER CLAD ONE SIDE--		
4238	2 x 4 1/2	1.35
4239	2 x 6	1.85
4240	4 1/2 x 6	3.20
4241	17 x 6	6.70

JUMBO RED LED'S

Similar to Monsanto MV5020 Series

Your Choice of Lens

Red or Clear, TO-18

Size: 70MA, 140MW

3V, Another NES GUARANTEED SUPER

BUY.



2/\$1.00 — 12/\$5.00

LED READOUTS

MAN-1 Type, 0-9

Drive with 7447,

Characters 5/16 x 3/16.

20 MA per Section.

No. LRO-R

RED

\$2.95


4/\$11.00

No. LRO-G

GREEN

\$4.95

4/\$16.00

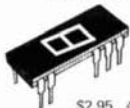

JUMBO LED READOUTS

Like MAN-1 Type Only BIGGER!!!!

Character Size: 3/4 x 7/16in.

Overall Size: 1 - 1/8 x 3/4 x 1/8

No. LRO-JR

Only \$8.95

RF POWER TRANSISTORS

We did it again - All brand new with standard markings and most were manufactured this year. A major manufacturer dropped his RF power line and we bought his inventory.

2N5589	3 Watts Out	\$ 3.50
2N5590	10 Watts Out	6.00
2N5591	25 Watts Out	12.00
2N6080	4 Watts Out	5.00
2N6081	15 Watts Out	7.50
2N6082	25 Watts Out	10.00
2N6083	30 Watts Out	12.00
2N6084	40 Watts Out	15.00

All are Silicon NPN and power output ratings are good to 175 MHZ. Hurry some quantities are limited



SPEAKER ASSORTMENT

1 1/2 to 4 inch, Good Assortment of Low Z (8-16 ohm) speakers all new. Tell us what SIZE RANGE you want and we will do our best or just let us give you a full assortment. Thousands in stock. ALL NEW AND GUARANTEED.

Only 10/\$5.00

WE GUARANTEE WHAT WE SELL!!!!

We ship UPS whenever possible. Give street address. Include enough for postage, excess refunded in cash. Florida residents include 4% Tax.

G&G CATALOG

24 PAGE Catalog, crammed with Gov't Surplus Electronic Gear — the Biggest Bargain Buys in America!

SEND FOR YOUR COPY

TG-34A CODE KEYSER, self-contained, automatic, reproduces code practice signals from paper tape. 5 to 12 WPM Built-in speaker. Brand new with tech manual, takeup reel and AC line cord. ... **\$24.50**
Code practice tapes for above P.U.R.



BRAND NEW BC-645 TRANSCEIVER

EASILY CONVERTED FOR 420MC OPERATION

This equipment originally cost over \$1000. You get all in original factory carton.



Dependable Two Way Communication more than 15 miles.

- FREQUENCY RANGE: About 435 to 500 Megacycles.
- TRANSMITTER has 4 tubes: WE-316A, 2-6F6, 7F7.
- RECEIVER has 11 tubes: 2-955, 4-7H7, 2-7E6, 3-7F7.
- RECEIVER I. F.: 40 Megacycles.
- SIZE: 10 1/2" x 13 1/2" x 4 1/2".

\$26.95

Makes wonderful mobile or fixed rig for 420 to 500 Mc. Easily converted for phone or CW operation

"SPECIAL PACKAGE OFFER"

TRANSCEIVER ONLY

\$16.95

APN-1 FM TRANSCEIVER 400-450 Mc. Freq. modulated by moving coil transducer. Easily converted for radio control or 70 cms. Complete with 14 tubes, dyn. **BRAND NEW \$9.95**



TERMS: F.O.B. NYC. 25% deposit with order, balance COD or remittance in full. MINIMUM ORDER \$5.00. Subject to prior sale and price change.

G&G RADIO ELECTRONICS COMPANY

45-47 Warren St. (Dept. H-A) New York, N. Y. 10007 212-267-4605

EL CHEAPO

Describes the price not the quality.

Announcing the New Line of Miniature power supply kits Zener or electronic integrated circuit regulated. Floating pos & neg output.

250MA and 1 amp types from \$7.95

1.5, 3, 4.5, 5, 6, 7.5, 9, 12, 15, 18, 20, 22, 24 volts

Use one to power your next project. Use for battery charges or battery eliminators. Call or write today for data on:

"THE POWER LINE"

EMC ASSOCIATES, INC.

9 Shields Lane • Ridgefield, Ct. 06877
203-438-0116

FULL FIVE YEAR GUARANTEE
SHIPMENT FROM STOCK

frequency. This filter is significantly more effective than linear filters for eliminating noise spikes. For example, high amplitude noise spikes occurring on fm carriers are highly attenuated before limiting. Since the non-linear low-pass filter introduces no phase delay distortion, it is useful where non-sinusoidal waveshapes are encountered, such as in wideband digital communications systems (square waves), spectroscopy (Gaussian-shaped peaks) and narrow-band telephone-line digital communications.

The non-linear low-pass filter is effective in systems that have undesirable commutating spikes such as samplers, encoder and time-shared demultiplexers. The filter can also be used to filter wide-band white noise without introducing any phase shift in the signal of interest.

The corner frequency of the non-linear low-pass filter module is set by the user by adding two external capacitors to the unit. The corner frequency can be set anywhere in the range from dc to 10 kHz. For more information and applications data, write to Non Linear Filters, Box 338, Trumbull, Connecticut 06611, or use *check-off* on page 110.

semiconductor replacement manual

A comprehensive 52-page Semiconductor Replacement Manual has just been released by the Sprague Products Company. Containing over 30,000 OEM part numbers, listed alpha-numerically, which can be replaced by Sprague's new line of 82 popular semiconductor devices, this manual also includes performance characteristics, outline drawings and pertinent parameters for the entire Sprague line.

Included in the new Sprague semiconductor replacement line are 42 small-signal and power transistors, 5 field-effect transistors, 6 silicon rectifiers, 14 linear integrated circuits and 15 LED devices.

These semiconductor devices provide exact replacements for components found in home/mobile entertainment and communications equipment. In addition,

the LED devices (which include visible light sources, infrared light sources, alpha-numeric displays and opto-electronic photo transistors) offer hobbyists new options and designs in electronic experimentation.

Copies of Semiconductor Replacement Manual, K-500, may be obtained without charge from Sprague distributors, by writing to Sprague Products Company, Marshall Street, North Adams, Massachusetts 01247, or by using *check-off* on page 110.

course in radio fundamentals

The new fifth edition of *A Course In Radio Fundamentals* is a completely-rewritten version of this long-time favorite, now in its 30th year. Modernizing the text, plus the introduction of much new material to increase the scope, has almost doubled the previous size of the book. If you are introducing someone new to amateur radio, this is a good book to start him off with.

Unlike the preceding printings, which used *The Radio Amateur's Handbook* as a text, the present volume is a complete and independent study manual. Paced at an intermediate technical level, the treatment is quantitative to the extent permitted by restricting mathematics to simple algebra.

The twenty-six chapters fall into two categories: electrical and radio circuit fundamentals and basic principles of electronic amplifying devices. Each chapter ends with a collection of questions and problems for testing the reader's understanding of the subject discussed. Answers to problems are given at the end of the book. The study text is followed by ten experiments using inexpensive, readily-available equipment. Detailed experimental data are contained in each.

The new soft-cover edition has 184 pages and contains well over 200 illustrations, including circuits and graphs. Priced at \$2.00 from your local electronics supplier, or order from Comtec Books, Greenville, New Hampshire 03048.



ONE DROP[®]

INDUSTRIAL STRENGTH
ALPHA CYANOACRYLATE

ADHESIVE

OVER 150 APPLICATIONS
IN EACH TUBE

THE SPACE AGE
MIRACLE ADHESIVE
THAT BONDS ALMOST
ANYTHING TO ANYTHING

JUST ONE DROP (Tensile Strength up to 5,000 lbs/in²) can take the place of bolts, nails, rivets, screws, clamps, locks, etc.

VERSATILE Bonds practically anything - It will help you put things together in a new, better fashion than ever before possible! glass · metal · ceramics · jewelry · rubber · plastics

Seconds To Bond... Years To Undo!

Literally thousands of uses; Repair printed circuit boards, cabinets, install knobs, controls, all types of hardware . . . metal, ceramic, porcelain, glass, etc. One Drop should be in every workshop. It's ideal for repairing jewelry, appliances, sporting goods, tools and countless other items.

If unavailable in your area order direct with 30 Day Money-Back Guarantee

132 Drop Dispenser (2 grams) \$3.00 postpaid
 SAVE . . . Order two for only \$5.00
 - Send check or money order - No C. O. D.'s.



Name _____

Address _____

City _____

State _____ Zip _____

Note: This One-Drop formula is not recommended for use on porous materials unless it is properly filled. Request Instant-Weld 240 for use on porous materials. No. 240 sets in about 3 minutes on most materials.



ELECTRONIC
MFG. INC.

Meadville, Pa. 16335

Save on Holiday



For a limited time only, SWAN ELECTRONICS and participating dealers are offering the best-buys-of-the-year in amateur radio . . . *complete* mobile or home stations . . . at very low "special package" prices. Act now. Be sure orders are placed early to assure early delivery — these special offers will expire December 25, 1973.



A LUXURY
SWAN TWINS
HOME
STATION
WITH
MATCHING DELUXE
SPEAKER AND QUALITY DESK MICROPHONE
COVERS ALL 5 AMATEUR BANDS — SSB/AM/CW

It's all here — the most envied and sought after amateur radio system — at a special reduced price that may never be repeated again. You'll save more than \$125 if you take advantage of this offer, now!

You get: The SWAN 600R/Custom Receiver including the ICAF 500 audio notcher-peaker and NB-500 noise blander; the 600 watt P.E.P. input SWAN 600T Transmitter with self-contained heavy-duty AC power supply; a deluxe SWAN 600SP Speaker and cabinet with FP-1 phone patch, headphone jack and tone control; plus, the SWAN 444 desk microphone . . . A \$1,228.90 retail value!

Among many features included are: • Mode selectors • Band selectors • Plate and antenna load matching controls • Selectivity and sensitivity controls • Hi-Lo power switch • Full break-in or semi-break-in CW with sidetone • VOX or PTT switch • Dual-ratio planetary tuning • Tuning eye and S-meters • Controlled AGC • VFO selector • and much more . . . practically every condition you'll ever want is at the control of your finger tips.

THIS COMPLETE DELUXE PACKAGE IS YOURS FOR \$1,099.95 or just \$110 down and no monthly payments until next year when ordered on an approved SWAN Revolving Credit Service account.

NEW 700CX CHAMPION SSB TRANSCEIVER

Less than 82¢ per watt! Punch through QRM for more contacts with 700 watts P.E.P. without an expensive accessory amplifier. The most power for the money available today . . . compare any others, you'll see it's a fact!

- SSB/CW/AM
- Dual-ratio planetary tuning
- 5.5 MHz crystal I.F. filter
- 5-Bands, 3 to 30 MHz
- ALC and AGC
- 2.7 kHz bandwidth

Choose a winner — SWAN'S 700CX CHAMPION — It's gotta lotta punch!



\$569.95

SWAN FM-1210A and Power Supply



2 Meter
FM
144
Channels
\$359.95

Independent switching of 12 transmit and 12 receive channels gives you up to 144 possible channel combinations for your communications pleasure. Now you can move off the crowded frequencies, effectively eliminating unwanted QRM. Eight crystals are included for the most popular frequencies.

The FM-1210A is the only 2 meter transceiver providing a crystal oven for superior stability in the coldest of weather conditions. Transmitter is fully solid-state. DC power cord is included for mobile operation and the heavy-duty pedestal type AC power supply is perfect for home station applications. Mobile mounting bracket and dynamic microphone is supplied.

The FM-1210A transceiver may be purchased without the AC power supply at just \$319 for mobile installation off any standard 12V DC system.


Specials from Swan Electronics

Compact Quarters? Need Space?
Try the 300B Cygnet *de novo* with
built-in speaker and AC power supply

Yes! A complete amateur radio station expertly
engineered into this newest generation of port-
able Cygnet SSB/CW transceivers. It's light-
weight, less than 25 pounds. An ideal traveling
companion for Hams on the move. Take it on
vacation — operate from motel room, hunting
cabin, boat or car. Connect an AC power source,
plug in your microphone and antenna — you're
on the air!

With 5 bands and 300 watts P.E.P. input, the
Cygnet *de novo* has all the control and power
necessary to work the world. A CW sidetone
monitor is provided along with capability for
CW semi-break-in with an optional VOX unit.
Requires plug-in DC converter for 12V DC
mobile operation

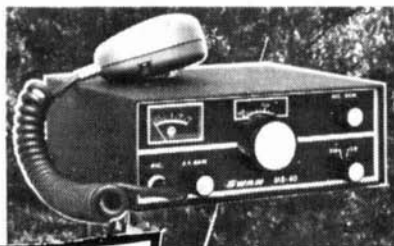300B Cygnet
de novo . . . \$499.95
VX-2, VOX
unit \$35.95
SWAN 14-A,
converter . . . \$44.95



**PACKAGE
#2**

ALL SOLID-STATE
SSB MONOBANDER
MOBILE
INSTALLATION
WITH YOUR CHOICE
OF 40 OR 80
METERS

Economical—Superior Quality—Amazing Clarity
—Easy to use! That's the reaction to this instal-
lation. Specifically designed for the mobile ham,
here is 50 watts P.E.P. input radiated through
the most efficient heavy-duty single-band mobile
antenna we know of. No tune-up time required.
Just flip on the power switch and you're in oper-
ation. An easy to see light emitting diode, on
the S-meter face, is activated to let you know
when you're transmitting. The built-in speaker
reproduces the most natural sounding voices
we've ever heard in a mobile rig.

Like its big brother, the SS-200, this mono-
bander needs no transmitter tuning and is in-
finitely protected from VSWR damage. Front-
end overload, distortion and cross-modulation
is virtually eliminated.

Select the MB-40 for 7.0 to 7.3 MHz use, or
the MB-80 if you prefer to work 3.5 to 4.0 MHz.
Whichever monobander you select, we'll include
the correct single-band coil and whip antenna
together with a bumper mount and microphone.
A total value of \$374.00 offered during this spe-
cial holiday season for only \$320. SAVE \$54.00.

Includes: SWAN MB-40 or MB-80 transceiver,
appropriate antenna coil, 6 foot whip and 36
inch antenna base section, SWAN BMT mount,
SWAN 404 microphone, and all necessary
mounting brackets, coax and connectors.

DON'T FORGET YOU CAN CHARGE YOUR PURCHASE TO YOUR SWAN REVOLVING CREDIT SERVICE PLAN

As little as 10% down will bring you any
item in this ad — including the Special Holi-
day Packages — on any ap-
proved SWAN Revolving
Credit Service account.

Also, after placing your
down payment, you do
not have to make any
further payments
until next year.

That's right,

**NO PAYMENTS
UNTIL 1974!!**

(If you don't have
a SWAN Credit
Card, see your
dealer or write the
factory for details.)



...More Swan



JOIN THE NEW AGE
OF AMATEUR RADIO
ELECTRONICS!
THRILL TO THE
SWAN SS-200 EXPERIENCE

Completely solid-state • 200 watts P.E.P. input • Operates directly from any 12V DC supply • 3 to 30 MHz • Broadband transmitter eliminates operator tuning adjustments • Full power maintained on all 5 bands • Selectable SSB/CW • Semi-CW break-in and monitor • Infinite VSWR protection • Crystal I.F. filter with 1.7 shape factor • 2.7 MHz audio bandwidth • Noise blanker with variable threshold control • and more! Also available in 15 watt P.E.P. input version. Home station power supplies may be purchased for 115V AC or 220V AC installations.

SS-15 (15 watts P.E.P.) \$579.00 PS-10 (115V AC power supply) \$89.00
SS-200 (200 watts P.E.P.) \$779.00 PS-20 (115V AC power supply) \$139.00

SWAN MARK 6B — Linear Amplifier.
2,000 watts P.E.P. input. Compatible
with SWAN 250C. 50 to 54 MHz.
Complete with power supply. \$679.95

SWAN VHF-150 — 2-Meter Amplifier.
150 watts P.E.P. input. Will operate class
"B" or "C". Rugged
self-contained power supply \$299.95

SWAN 117-XC — 117V AC power
supply with speaker, phone jack
and indicator light. Ready to
plug in and operate \$109.95

SWAN SS-16B — Super Selective I.F. Filter.
Exclusive 16 pole filter has a 1.28 shape factor
with an ultimate rejection in excess of 140 dB.
In easy-to-install kit form. \$79.95

2-METER MOBILE FM STATION FEATURING THE NEW FM-2XA TRANSCEIVER



Transmit 10 watts of RF power over 12 channels from 144 to 148 MHz. Operates directly from any 12V DC battery system. MOS FET front-end substantially eliminates cross modulation and overloading. Infinite VSWR protection. Dynamic microphone and all necessary cables and connectors are included. The 3 dB gain whip is stainless steel with tapped transformer moulded at the base. Your choice of roof or deck mounting. A real value, worth up to \$288.70. You save up to \$23.75 at this low bargain price of \$264.95 for this complete package deal.

SWAN FP-1 — Hybrid Phone Patch.
Separate receiver and transmitter gain
controls. Exact voice reproduction . . \$48.95

SWAN 55C — 5-Band Remote Control
Mobile Antenna. Power rated at 1000
watts P.E.P. A SWAN exclusive . . . \$129.00

SWAN 45 — 5-Band manual
switching version of the 55C \$79.00

SWAN TB-2A — 2-Element Beam Antenna
power rated at 2000 watts \$89.95

SWAN TB-3A — 3-Element Beam Antenna
power rated at 2000 watts \$108.00

GOLDEN SWAN 1040-V — Trap Vertical
Antenna. 10, 15, 20 and 40 meters,
PR @ 2000 W. \$69.95
75 Meter add-on kit \$36.95

2000 WATT P.E.P. INPUT MARK II LINEAR AMPLIFIER

Full frequency coverage from 10 to 80 meters plus MARS. Requires 100 watts of drive — compatible with SWAN 270B, 300B, 500CX, 700CX and 600T. All controls are easily accessible on the front panel. Provides full legal power limit on SSB, CW, AM and RTTY. Meter switch allows you to read Plate Voltage, Plate Current, Grid Current and Relative Output. Separate matching AC power supply included with 4 1/2 foot connecting cable.



\$679.95

Holiday Offers!

You may use this Special Holiday Purchase Form to place your order or you may want to use it as a HINT CHECK-LIST for your XYL or YL! Don't forget to point out the unique amateur radio gift counseling service available especially for her:

ATTENTION ALL XYL's and YL's - If you're in doubt about what to get the OM or YM, or if you have any question at all about SWAN equipment or services - call SWAN's Gift Information Service . . . collect! Call area code 714, 757-7525 (between 8 AM and 4 PM Pacific Time) and ask for our Gift Information Service. You'll receive our most courteous and confidential assistance.

CUT ALONG DOTTED LINE
AND MAIL TO SWAN OR BRING TO YOUR LOCAL SWAN DEALER

- | | | |
|--------------------------------------------------------------------------------------|---------------------------------------------------------------------------------------------------------------------------|-------------------------------------------------------------------------------------------------------------------------------------|
| <input type="checkbox"/> PACKAGE #1 - \$1099.95
LUXURY 600
HOME STATION | <input type="checkbox"/> PACKAGE #2 - \$320.00
<input type="checkbox"/> MB-40
<input type="checkbox"/> MB-80 | <input type="checkbox"/> PACKAGE #3 - \$264.95
<input type="checkbox"/> Roof Mount
<input type="checkbox"/> Deck Mount |
|--------------------------------------------------------------------------------------|---------------------------------------------------------------------------------------------------------------------------|-------------------------------------------------------------------------------------------------------------------------------------|
-
- | | |
|------------------------------------------------------------------------|-------------------------------------------------------------------|
| <input type="checkbox"/> 700CX Champion \$569.95 | <input type="checkbox"/> 117-XC, AC Power Supply . . . \$109.95 |
| <input type="checkbox"/> FM-1210A & AC Power Supply . \$359.95 | <input type="checkbox"/> SS-16B, Super Filter \$79.95 |
| <input type="checkbox"/> FM-1210A Mobile Unit \$319.00 | <input type="checkbox"/> 510X, Crystal Oscillator \$53.95 |
| <input type="checkbox"/> 300B Cygnet <i>de novo</i> \$499.95 | <input type="checkbox"/> FP-1, Phone Patch \$48.95 |
| <input type="checkbox"/> VX-2, VOX Unit \$35.95 | <input type="checkbox"/> WM-1500, Wattmeter \$49.95 |
| <input type="checkbox"/> 14-A, DC Converter \$44.95 | <input type="checkbox"/> 55C, Mobile Antenna \$129.00 |
| <input type="checkbox"/> SS-15 Solid-State Transceiver . . \$579.00 | <input type="checkbox"/> 45, Mobile Antenna \$79.00 |
| <input type="checkbox"/> SS-200 Solid-State Transceiver . . \$779.00 | <input type="checkbox"/> TB-2A, Beam Antenna \$89.95 |
| <input type="checkbox"/> PS-10, AC Power Supply \$89.00 | <input type="checkbox"/> TB-3A, Beam Antenna \$108.00 |
| <input type="checkbox"/> PS-20, AC Power Supply \$139.00 | <input type="checkbox"/> TB-3HA, Beam Antenna \$125.00 |
| <input type="checkbox"/> Mark 6B, Linear Amplifier \$679.95 | <input type="checkbox"/> TB-4HA, Beam Antenna \$148.00 |
| <input type="checkbox"/> VHF-150, 2-Meter Amplifier . . . \$299.95 | <input type="checkbox"/> 1040-V, Trap Antenna \$69.95 |
| <input type="checkbox"/> Mark II, Linear Amplifier \$679.95 | <input type="checkbox"/> 75 Meter Add-On Kit \$36.95 |

This check list can be used as an order form. Check the items you want, fill in all necessary data, and mail to SWAN or your favorite dealer. All shipping charges will be collect. Sales tax will be added where appropriate.

NAME _____ AMATEUR CALL _____
ADDRESS _____ PHONE _____
CITY _____ STATE _____ ZIP _____

Payment by: Check/Money Order C.O.D. SWAN Finance (10% or more down payment enclosed) BankAmericard # _____ Expires _____
 Master Charge # _____ Expires _____ Interbank # _____
 SWAN Account # _____ - Check here if this is an add-on order **HAM**

(All prices contained herein are subject to change after December 25, 1973)



SWAN
ELECTRONICS
A subsidiary of Cubic Corporation

305 AIRPORT ROAD
OCEANSIDE, CA 92054
TELEPHONE (714) 757-7525

BONUS COUPON

If your total purchase of SWAN equipment ordered from this advertisement exceeds \$600, present this coupon for an additional 2% discount off the total list price of your purchases. This coupon is not valid unless signed by an authorized purchaser.

Name _____ Date of Purchase _____
Signature _____

Expires December 25, 1973
clipped from **HAM** magazine

**VHF
DX OPS**

MODEL 60 SPEECH PROCESSOR — QRO the average-to-peak ratio of the speech waveform as much as 8 db using a logarithmic principle. Operates with FM, SSB and AM transmitters and transceivers. Low/High impedance Mic input. Two 9Vdc batteries provide a self-contained unit.

Model 60W (Processor Assembled) \$26.50
Model 60K (Processor Kit) \$21.90
200-15 (Processor Board Kit) \$12.95

MATRIX

BOX 185A • FRANKLIN, PA. 16323
PHONE: 814 432-3647

**QRO
?**

MODEL 20 DIGITAL DIAL — Available for Collins and Drake gear. Optional four digit readout and crystal time base. QSY your fixed or mobile transmitter, receiver or transceiver with 100 Hz accuracy and no last digit jitter. Simple one wire connects dial to rig and you're ready to go. Specify your type of rig.

Model 20 (5-5.5 Mhz VFO range) \$169.95
Model 20C (Collins) \$169.95
Model 20D (Drake) \$169.95
Options: [4 Digit Readout] \$ 29.95
[Crystal Time Base] \$ 29.95

DEALERS:

VE AMATEUR RADIO SALES, Downsview, Ontario, Canada •
SST ELECTRONICS, Lawndale, CA 90260 • AMATEUR
WHOLESALE ELECTRONICS, Miami, FL 33156 • AN-TEK
INDUSTRIES, Elkhart, IN 46517 • SIGNAL SYSTEMS, Bedford,
OH 44146 • KASS ELECTRONICS DISTRIBUTORS, Drexel Hill,
PA 19326 • M. WEINSCHENKER K3DPJ, Irwin, PA 15642 •
HAMTRONICS, Treviso, PA 19047

**CW
OPS**

MODEL 11A PADDLE — Designed with reliability in mind. No mechanical switches or bearings to fail. Paddle contact spacing adjusts easily.

Model 11A (Assembled) \$9.95

MODEL 10A ELECTRONIC KEYS — Has NEW features at no extra cost. Linear Speed Control and Operate/Tune Switch. Plus internal penlight cells and reed relay output provide a compact, portable, versatile unit.

Model 10AWA (Keyer & Sidetone Assembled) \$33.95

Model 10AW (Keyer Assembled) \$26.50

Model 10AK (Keyer Kit) \$21.95

200-2K (Keyer Board Kit) \$12.95

200-3K (Sidetone Board Kit) \$ 4.95

NEW MINIATURE CRYSTAL FILTERS — Made U.S.A.

Write us about your crystal filter needs
Model WF-4 Model WF-8



**WHEATLAND
ELECTRONICS**
P. O. BOX 343
ARKANSAS CITY
KANSAS 67005

No. Crystals	4	8
Center Freq.	9.0 MHz	9.0 MHz
Band Width at 6db	2.5kHz	2.5 kHz
60db/6db Shape	2.0 (45/6)	1.8 max.
Ultimate Rejection	45 db	100 db min.
In/Out Termination	120 Ω	140 Ω
PRICE	\$18.95	\$26.95

Matching Crystals USB (8998.5 kHz)
or LSB (9001.5 kHz) \$2.75 each
Include .75 for postage and handling.

Greatest Advance in Soldering Since Electricity

CORDLESS INDUSTRIAL SOLDERING IRON



*Ideal
Christmas
Gift*

- Completely Portable.
- Heats in 5 Sec.
- Recharges automatically on its own stand.
- Solders up to 150 joints per charge.
- New working freedom anywhere — SHOP — LAB — IN THE FIELD . . .

#7500 Kit includes cordless soldering iron, fine tip, automatic 110 VAC recharging stand and instruction booklet \$19.95 postpaid. No COD's Accessories

- #7585 Automobile charger for cordless iron \$4.95
- #7545 Fine Replacement Tip \$2.50
- #7535 General Purpose Tip \$2.50
- #7546 Heavy Duty, high temp. tip \$2.50

ALARM COMPONENT DIST.

Dept. HR, 33 New Haven Ave., Milford, CT 06460

SWAN**EAST COAST SERVICE CENTER**

We also service all other popular makes.

Complete professionally staffed laboratory fully equipped for all aspects of maintenance and service. Graduate Engineer on duty. Custom Design services available.

PROFESSIONAL ELECTRONICS CO., INC.

1710 JOAN AVE. EUDOWOOD BRANCH
BALTIMORE, MD. 21204
301-661-2123

GATEWAY ELECTRONICS

8123 PAGE AVENUE
ST. LOUIS, MISSOURI 63130
314-427-6116

5 Mhz crystal, miniature size w/wire leads \$2.50

GIANT 7 SEGMENT L. E. D. READOUT — 6/10

inch character height — NEW \$3.95

L. E. D. 7 SEGMENT READOUT — MAN 1

TYPE — NEW \$2.75

L. E. D. INDICATOR — STANDARD SIZE —

RED — NEW 35¢ 3/\$1.00

DIGITAL CLOCK CHIP — NATIONAL 5314 — 6

DIGIT — 12/24 hour — NEW \$12.95

STEREO AMPLIFIER "IC" 14 Pin, 2 watts per

channel — NEW \$2.00

THUMBWHEEL SWITCHES

— 0.5 x 2.125 x 1.78 — 10 position decimal \$3.00

— 10 position BCD & Complement \$4.00

— End Plates (per pair) \$1.45

MINIATURE SIZE

— 0.312 x 1.3 x 1.3 10 position decimal \$2.50

— 10 position BCD & Complement \$3.75

— End Plates (per pair) \$1.00

\$5 Minimum Order.

Visit us when in St. Louis.

Please include sufficient postage.

The most powerful signals under the sun!



hy-gain

Redesigned

HAMCAT


Out-hustles them all!

The famous HAMCAT...now redesigned for greater performance...*equals* or *exceeds* the performance of any other Amateur Mobile antenna. *We guarantee it!* And you need buy only one mast...whether you mount it on fender, deck or bumper. There's just one set of coils and tip rods...and they all stand up to maximum legal power. That's performance, that's value...*THAT'S HY-GAIN!*

Original Hy-Q "quick changer" coils wound on tough fiberglass coil forms for greater heat resistance, less RF absorption / Fiberglass shielded coils can't burn up, impervious to weather / Shake-proof, rattle-proof, positive lock hinge now even stronger...eliminates radio noise / All stainless steel tip rods won't bend or break / Full 5' mast gives you 10% more radiating area than the competition / Rugged swivel-lock stainless steel base for quick band changes, easy garaging.

Get the Hamcat...from Hy-Gain

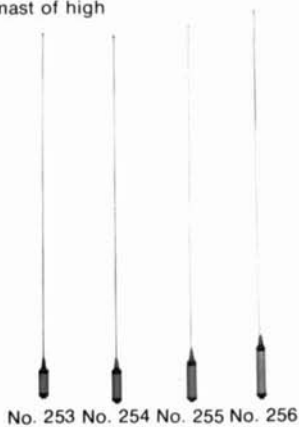- Order No. 257 All new design 5' long heavy duty mast of high strength heavy wall tubing **\$17.95**
- Order No. 252 75 meter mobile coil **\$19.95**
- Order No. 256 40 meter mobile coil **\$17.95**
- Order No. 255 20 meter mobile coil **\$15.95**
- Order No. 254 15 meter mobile coil **\$12.95**
- Order No. 253 10 meter mobile coil **\$11.95**
- Order No. 499 Flush body mount **\$ 9.95**



HY-GAIN ELECTRONICS CORPORATION

Dept. W1, 8601 Northeast Highway Six
402/434-9151

Lincoln, NE 68507
Telex 48-6424


WE WILL PUT YOU AT ANY *HEIGHT* YOU NEED ! REGARDLESS OF WHAT THAT *HEIGHT* MIGHT BE !

There's a Heights tower to fit every need and every budget. Crank ups, foldovers, TV stand-alones -- we've got 'em all....and they're all aluminum. You can make sure your antenna is mounted at the maximum legal limit the right way, the Heights way. And remember, Heights towers are all aluminum, Heliarc welded for light weight. They're extremely rugged, and very easy to erect.

Write for 12 page brochure giving dozens of combinations of height, weight and wind load. We think you'll be setting your operating conditions to new heights.

HEIGHTS MFG. COMPANY

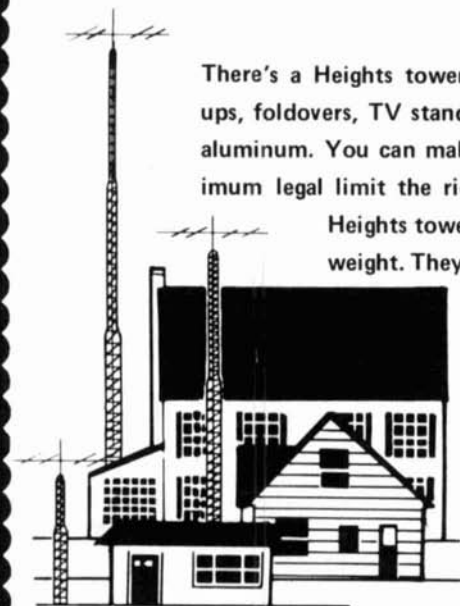Almont Heights Industrial Park "A"
Almont, Michigan 48003



MODEL "A" Frequency Counter Price \$299.00
10Hz to 80 MHz (± 1 Hz) Direct Count guaranteed (1Hz to over 100MHz) typical)
Read Out: 5 LED digits + LED Over Range
Sensitivity: Less than 100 millivolts over entire range.
Power Req.: Either 120 VAC or 12 VDC 15 watts approx.
Small Size: 2.34" x 5.68" x 8.18"
Overload protected input and DC power input.

MODEL "AS" Frequency Counter Price \$375.00
Exactly as above plus an internal 250MHz Scalar (± 10 Hz to well over the guaranteed frequency of 250 MHz.) No external power is required.
Shifting DECIMAL POINT gives a DIRECT READOUT of VHF Frequencies.
One BNC INPUT for both ranges. No cable changing from HF to VHF.
(CA residents add State Sales Tax)
Dealer inquiries invited



ELECTRONICS
P.O. BOX 1672
VISTA, CA. 92083
714-726-1313

THE KW2000B transceiver with speaker and power supply

- *160-10 meters
- *180 watts PEP
- *AUX VFO available
- *built-in VOX unit
- *CW side tone
- *Mechanical filter
- *Crystal controlled first mixer



- *Velvet-smooth two-speed VFO tuning

KW Electronics \$699
55 Bridge St. Plattsburgh NY 12901
In Canada: 214 Dolomite Dr.
ELECTRONICS Downsview Ont. M3J 2P8

Prod. in USA
& Canada
Money Back Guarantee

KITS



Encoder \$8.95
Wired \$13.95

Sub-Audible Tone Decoder \$9.95
Wired \$14.95



- Compatible with all sub-audible tone systems such as Private Line, Channel Guard, Quiet Channel, etc.
- Glass epoxy PCB's & Silicon xstrs throughout
- Any reeds, except special dual coil types may be used: Motorola, G.E., RCA, S.D.L., Bramco, etc.
- All are powered by 12 vdc
- Use on any tone frequency 67 Hz to 250 Hz
- Small size 1.5 x 4 x .75"
- All parts included except reed and reed socket

Postpaid — Calif. residents add 5% sales tax
COMMUNICATIONS SPECIALISTS
P. O. Box 153, Brea, CA 92621

MISC.

Scanomatic HighBand 8 channel scanner Write Kenwood Twins R-599 & T-599. Receiver and transmitter. Regular net \$818 for both. Excellent, guaranteed good as new \$618.00
 Henry 2K-4 Floor Model, mint, Write U.S. Callbooks \$ 8.95
 DX Callbooks \$ 6.95
 Complete Maintenance Manual for Signal/One CX-7 & CX-7A \$ 25.00
 Radio Handbooks latest 19th edition \$ 14.95
 Radio Handbook 18th Edition \$ 8.95
 Lafayette Telsat-SSB 25, Sideband CB Rig \$195.00
 Gonset 903A 2 meter amplifier, 5 watts in, 500 watts out all modes 15 V new condx., \$375.00
 NPC Power Supply, 115 VACN — 12 VDC out at 4 amp REGULATED at \$ 34.95
 Millen magnetic shields for 3" C.R. scope tubes with brackets Brand new \$ 6.95
 TP-9 Similar to EE-8 field telephone with built-in amplifier. Up to 50 mi. Less easily obtained batteries Brand New \$ 75.00
 115 Volt AC Power Supply for BC-221, slips into battery compartment. Also can be used with LM freq. meters \$ 29.50
ALUMINUM DIE CAST BOXES in many different sizes. Dossy boxes. Details in New Green Sheet No. 23. Write for latest prices.
 2. METER VHF DUMMY LOAD/WATTMETER Good up to 15 watts — w/SO-239 CONNECTOR and 3" METER \$ 15.95
 R-390 General coverage digital readout receiver just received Call or write
 Original J-38 Key new, \$ 12.50



Jackson G80 brass 50:1 anti-backlash dial drive 1/4" to 1/4". \$19.00 value \$ 5.50

INOUE IC-22

2 Meter Transceiver

10 WATTS OUTPUT PLUS TREMENDOUS RECEIVER — 22 CHANNELS

Ready to go with crystals for 5 frequencies at no extra charge

\$289.00

Many Inoue Crystals In Stock.

IC-3PA Power Supply \$99.00

\$89.00 when purchased with IC-22

BARKER & WILLIAMSON

Little Dipper, GDO \$ 94.50
 Dummy Load - Wattmeters - 52Ω
 333 DC-300 MHz, 5, 50, 125 or 250 watts int. \$ 79.95
 334A DC-300 MHz, 1000 watts \$139.95
 374 DC-300 MHz, 1500 watts int. \$169.95
 850A, 852 Inductors \$ 59.95
 851 Inductor \$ 29.95
 425 Low Pass Filter, 10-80 meters 1 kw \$ 24.95
 210 Audio Osc., ideal for lab & broadcast \$329.95
 410 Distortion Meter, ideal for lab & broadcast \$369.95
 AM-141 Amplifier, 2000 watts RF output, continuous 2-18 MHz, complete with coils and 833-A's. Built-in 115 VAC Supply, like new \$950.00

STANDARD

SRC-146A 2 meter handheld transceiver \$287.00

SBE

SBE-450 TRC, use with 10 watt, 2 meter transceiver to operate on 450 \$195.00

LITTLE LULU

**6 Meter AM Transmitter with VFO
 12 VDC/115 VAC Power Supply**

Available factory wired or as parts
 Write for details

BARRY HAS NEW

**VENUS SSTV IN STOCK
 COME TAKE A LOOK OR WRITE**

INVERTER/CONVERTER:

INVERTER, 12 volt DC input, 115 volt AC out. Model 12-115 solid state power supply, 200 watts continuous new, \$ 59.95

TELEX

610-2 Deluxe Economy 2000 ohm headset with cushions \$ 9.95
 EN-5 Stereo Headphones \$ 9.95

Tube Headquarters. Diversified Stock. Heavy inventory of Eimac tubes, chimneys, sockets, etc. 572B Barry Now Stocks Bogen, Electrovoice & University. Call or Write.

BARRY HAS ANTENNAS

C.D. HAM "M" ROTATORS, new complete \$99.95
 CD Ham-M for 220 VAC in stock \$175.00
 C.D. TR-44 ROTATORS, new (complete) \$ 63.95
 CABLE for Ham-M & TR-44 @ 14¢/ft.
 CD AR-22R complete rotator for small beams \$ 33.95
 BN86 Balun by HyGain \$ 14.95
 RG-8A/U 100 ft. rolls. VHF connector PL-259 one end Type "N" (UG-21E/U) other end \$ 12.50
 RG8A/U — 65 feet with PL-259 connectors on each end \$ 9.50
 Times Wire & Cable, T-4-50 (FM-8) 50 ohm lowest loss type RG-8 cable 25¢/ft.
 Columbia Superflex, RG-8A/U 50 ohm high quality foam 22¢/ft.
 Coaxial adapter for VHF to RG-17 (Amphenol 83-86) RG-17 plug to VHF female connector \$6.95
 BNC to RG-17 adapter UG-167C/U \$7.95
 B & W Vacationer apartment house antenna, 2, 6, 10, 15 & 20 meters. Hang out your window. Take along on your vacation \$ 24.95
 Authorized factory dealers for Antenna Specialists, CushCraft, Gam, Heights Towers, Hy Gain, Mor-Gain Antenna, Mosley, Newtronics, Tri-Ex, Rohn, E-Z Way, Times Wire, Telrex.
 Cush-Craft Trick Stick, universal dipole, 10-2 meters, 1.5 dB gain at 146 MHz \$ 8.95
 English deluxe balun, low power \$ 9.95
 RINGO AR-2 3.75 dB gain, 135-175 MHz \$ 14.50
 BBLT-144 Trunk Lip, 3.75 dB gain \$ 34.95
 Newtronics CGT-144 mobile 5.2 dB gain \$37.95
 Quick Disconnect by Newtronics for CGT, etc. \$ 10.95
 CG-1 Gutter Clip by Newtronics \$ 1.25
 2M MAGNETIC MOUNT w/RG58 & PL259 with 10 ft. RG 58 ready to go \$ 9.95
 14AVO/WB VERTICAL \$ 55.00
 18AVT/WB VERTICAL \$ 79.95
 HY GAIN 2 METER, 15 ele. beam, demo, \$ 35.00

CASH PAID . . . FAST! For your unused TUBES, Semiconductors, RECEIVERS, VAC. VARIABLES, Test Equipment, ETC. Write or call Now! Barry, W2LN1. We Buy! We ship all over the World.
 Send for Green Sheet Supplement 23.
 Send 50¢ postage & handling (refund 1st order).

BARRY 512 Broadway NY, NY 10012
 DEPT. H-11
 212-WA-5-7000 **ELECTRONICS**

See Page 112 for MORE from Barry

BROADBAND AMPLIFIERS, for amateur, MATV, CATV and commercial use

We offer a quality line of low noise, low IMD amplifiers covering the region from 2 MHz to 1.5 GHz. For communication use, simple filters at the input will yield coverage of the bands of your choice. Where remote location is necessary to offset line losses, coax powered versions are available with adapters or power supplies.



Depending upon model, gain to 50dB, flatness to ± 1 dB and Noise Figure less than 3 dB may be selected. Operation is from 12 to 15 volts d-c or 115 volts a-c. PIN diode protection for incident power to 25 watts is available. Prices vary from \$30 to \$130 depending upon model and options. Warranty is for one year on all parts and labor.

RADIATION DEVICES CO., P. O. Box 8450, Baltimore, Md. 21234

Please write for information on our other products including RF Multimeters, VSWR Bridges, Detectors, L-C, Crystal and Tunable Active Peak-N-Notch Filters.

FM Schematic Digest

A COLLECTION OF
MOTOROLA SCHEMATICS

Alignment, Crystal, and Technical Notes
covering 1947-1960

136 pages 11 $\frac{1}{2}$ " x 17" ppd \$6.50

S. Wolf

P. O. Box 535

Lexington, Massachusetts 02173

WE PAY **HIGHEST**
PRICES FOR ELECTRON
TUBES AND SEMICONDUCTORS

H & L ASSOCIATES

ELIZABETHPORT INDUSTRIAL PARK

ELIZABETH, NEW JERSEY 07206

(201) 351-4200

— PCB KITS —

RTTY SPEED CONVERTER Drilled PCB 5 & 11 VDC \$40.00
DRILLED PCB ONLY \$ 6.00
RTTY AFSK Gen. All Shifts & CW I.C. 9 VDC @ 2ma \$6.60
100 KHz XTAL CALIBRATOR Less Xtal 9 VDC @ 2ma \$4.75
POWER SUPPLY — 28 VDC @ 650 ma output \$8.95
PREAMP MICROPHONE, 26 DB Gain 9 VDC @ 1ma \$3.50
LIMITER PREAMP For High Z Mike 9 VDC @ 1ma \$4.80
PRODUCT DETECTOR For Your Receiver 9 VDC @ 1ma \$3.60
"S" METER KIT Less 1ma Meter 6.3VAC \$4.75
SWR METER, Stripline, Less 200 μ a Meter \$2.95
WVW CONVERTER 3.5-4.0 MHz Output 9 VDC @ 5ma \$5.25
Requires 6-6.5MHz Crystal
6 METER CONVERTER FET Front End 9 VDC @ 5ma \$5.95
7-11 MHz Output, Less 43 MHz Xtal
CW KEYING MONITOR, RF Keyed, Less Spkr. 9 VDC @ 9ma \$4.70
POWER SUPPLY - 9 VDC @ 50ma Output 115VAC \$4.85
6 OR 2 METER CASCODE PREAMP 80 VDC @ 4.5ma \$4.95
Wired & Tested Less 2 ea 6CW4
Nuvistors. Specify 6 or 2 Meter Model
DRILLS, #54, 56, 58 or 60 (each) \$.40
Finest Quality for PCB'S, Made in USA Three For \$1.00

EXCEPT AS NOTED ABOVE, ALL KITS ARE NEW, 100% SOLID STATE. AND COME COMPLETE WITH AN UNDRILLED G-10 PCB (PRINTED CIRCUIT BOARD) AND ALL PCB MOUNTED COMPONENTS. KITS ARE LESS POWER SUPPLIES, CHASSIS, AND ENCLOSURE HARDWARE. SEND SELF-ADDRESSED, STAMPED ENVELOPE FOR COMPLETE DATA SHEET AND SCHEMATIC.

SATISFACTION GUARANTEED. RETURN IN 30 DAYS FOR REFUND. ALL KITS POSTPAID. INCLUDE 25¢ HANDLING CHARGE. WASHINGTON RESIDENTS ADD 5.3% SALES TAX.

P. M. ELECTRONICS INC.

519 SOUTH AUSTIN, SEATTLE, WASH. 98108

CRYSTAL BARGAINS

Depend on . . .

We supply crystals from
16kHz to 100MHz. Over
6 million crystals in
stock.

JAN
CRYSTALS

DIVISION OF BOB
WHAN & SON
ELECTRONICS, INC.

SPECIAL
Crystals for most amateur
2-Meter F.M. Transceivers:

\$3.75 Each

Inquire about quantity
prices. Order direct. Send
check or money order.

For first class mail add 15¢ per
crystal...for air mail add 20¢ ea.

2400 Crystal Dr.
Fort Myers
Florida 33901
(813) 936-2397

Send 10¢ for new
catalog with
oscillator circuits
and lists of
thousands of
frequencies in
stock.

SPECIALS! CRYSTALS FOR:

Frequency Standards	
100 KHz: (HC13/U)	\$4.50
1000 KHz: (HC6/U)	4.50
Almost All CB Sets, Trans. or Rec. (CB Synthesizer Crystal on request)	2.50
Any Amateur Band in FT-243 (Except 80 meters)	1.50 4 for 5.00
80 Meter Range in FT-243	2.50
Color TV 3579.545 KHz: (wire leads)	1.60 4 for 5.00

CW or RTTY, whichever way you go,
**HAL HAS TOP QUALITY
 YOU CAN AFFORD!**



TOP QUALITY RTTY... WITH THE HAL MAINLINE ST-6 TU. Only 7 HAL circuit boards (drilled G10 glass) for all features, plug-in IC sockets, and custom Thordarson transformer for both supplies, 115/230 V, 50-60 Hz. Kit without cabinet, only \$135.00; screened, punched cabinet with pre-drilled connector rails, \$35.00; boards and complete manual, \$19.50; wired and tested units, only \$280.00 (with AK-1, \$320.00).*



TOP QUALITY... WITH THE HAL 1550 ELECTRONIC KEYER. Designed for easy operation; perfectly timed CW with optional automatic ID for sending call letters, great for DX and RTTY; TTL circuitry, transistor switching for grid block, cathode keying. Handsome rugged crackle cabinet with brushed aluminum panel. With ID, only \$90.00; without ID, \$65.00.*

OTHER HAL PRODUCTS INCLUDE:

- ID-1 Repeater Identifier (wired circuit board) . . . \$ 75.00*
- ID-1 (completely assembled in 1 1/4" rack cabinet) . . . \$115.00*
- HAL ARRL FM Transmitter Kit . . . \$ 50.00*
- W3FFG SSTV Converter Kit . . . \$ 55.00*
- Mainline ST-5 TU Kit . . . \$ 50.00*
- Mainline AK-1 AFSK Kit . . . \$ 27.50*



TOP QUALITY... WITH THE HAL MKB-1 MORSE KEYBOARD.

As easy as typing a letter—you get automatic CW with variable speed and weight, internal audio oscillator with volume and tone controls, internal speaker, and audio output jack. Smooth operation; completely solid-state, TTL circuitry using G10 glass boards, regulated power supplies, and high voltage transistor switch. Optional automatic ID available. Assembled MKB-1, \$275.00. In kit form, \$175.00.*



NEW FROM HAL — TOP QUALITY RVD-1002 RTTY VIDEO DISPLAY UNIT.

Revolutionary approach to amateur RTTY . . . provides visual display of received RTTY signal from any TU, at four speeds (60, 66, 75, and 100 WPM), using a TV receiver modified for video monitoring. Panasonic solid-state TV receiver/monitor, or monitor only, available. RVD-1002, \$525.00; Panasonic TV receiver/monitor, \$160.00; monitor only, \$140.00.*

TOP QUALITY... WITH THE HAL RKB-1 TTY KEYBOARD.

Gives you typewriter-easy operation with automatic letter/number shift at four speeds (60, 66, 75, and 100 WPM). Use with RVD-1002 video display system, or insert in loop of any teleprinter, for fast and easy RTTY. Completely solid state, TTL circuitry using G10 glass boards, regulated power supplies, and transistor loop switch. RKB-1 assembled, only \$275.00.*



HAL provides a complete line of components, semi-conductors, and IC's to fill practically any construction need. Send 24c to cover postage for catalog with info and photos on all HAL products available.

*Above prices do not include shipping costs. Please add 75c on parts orders, \$2.00 on larger kits. Shipping via UPS whenever possible; therefore, street address required.

HAL COMMUNICATIONS CORP., Box 365 H, Urbana, Illinois 61801

A COMPLETELY PORTABLE FREQUENCY COUNTER WITH . . .

- * 10 HZ to 65 MHZ range
- * Full six digit readout (L.E.D.)
- * Sensitive front end (LESS THAN 10 MV.)
- * Only \$199

FEATURES

- High capacity rechargeable Ni Cd batteries
- Crystal controlled time base (can be field calibrated)
- Convenient 3-position range select switch allows:
 1. Readout always in MHZ.
 2. Eight digit resolution by range selection
 3. Direct reading pre-scaler operation to 999.999 MHZ.
- "Battery save" switch for spot checks
- Less than 5 watts power consumption (5 volts @ 0.9 AMPS)
- Dimension 6" x 3.5" x 2.3"
- TTL input for use with pre scalar
- Can be operated on internal or external power, with trickle charge and full charge positions
- Sample control lets operator determine how often the readout is updated. Can "hold" present count without being updated



Mail orders directly to:
Great American Miniatures,
Inc.
P. O. Box 10990
Midwest City, Okla. 73110

Model C-65 Freq. counter \$199.00
Battery charger 8.00
Battery charger & eliminator 18.00

NATIONAL MOS

DYNAMIC shift registers
 MM502 dual 50 bit 1.25
 MM506 dual 100 bit 1.75
 MM5006 dual 100 bit 1.50
 MM5013 1024 bit 2.00
 CM5016 512 bit 1.50
STATIC shift registers
 MM504 dual 16 bit 1.50
 MM505 dual 32 bit 1.75
 MM550 dual differential analog switch 2.50

KEYBOARD General Telephone

Ten push buttons (0-9) touch-tone, encoding, programming devices. Easy for panel mounting.

\$5.95
Size: 3x2x1 1/2"

MV-50 red emitting 10-40ma @ 2v .39
 MV5020 red LED .45
 MV-108 Visible red 5-70ma @ 2v .45

TRIAC 2N6344 600V 8A TO-220 \$1.00

NE531 op amp TO-5 \$2.00
 NE561 phase lock loop DIP 3.25
 NE569 phase lock loop TO-5 3.25
 NE566 function generator TO-5 4.00
 NE567 tone decoder TO-5 4.00


MANI MANEM (Each) \$2.50
 10 for \$25.00 (Man Radio Specials!) Ten or more, 20.00

All IC's are new and fully tested, leads are plated with gold or solder. Orders for \$5 or more will be shipped prepaid. Add 35¢ for smaller orders. California residents add sales tax. IC orders are shipped with 24 hrs. COD's may be phoned in \$10. minimum. Money back guaranteed.
BABYLON P.O. Box J Carmichael California 95608
ELECTRONICS (916) 966-2111

CT5005

CALCULATOR ON A CHIP

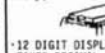This chip has a full four function memory. Memory is controlled by four keys, +M (adds entry to memory), -M (subtract entry from memory), CM (clear memory-without-clearing rest of registers), RM (read memory or use as entry).



12 DIGIT DISPLAY AND CALC. FIXED DECIMAL AT 0.1, 2, 3, 4, OR 5
 LEADING ZERO SUPPRESSION
 SEVEN SEGMENT MULTIPLEXED OUTPUT
 TRUE CREDIT SIGN DISPLAY
 SINGLE 28 PIN CHIP
 Chip and data--\$14.95
 Data only---- 1.00 (refundable)

1101/2501
 256 BITx1 MOS memory \$2.56

MANI Popular 7 segment diffused LED. Dual in line 14 pin capable of displaying all digits and nine distinct letters.
 \$4.00 each

LED FL 100

special 39 each
 3.50 for ten
 29.95 for 100

7400 TTL DIP

7400	-----	.35
7401	-----	.35
7402	-----	.35
7403	-----	.35
7404	-----	.35
7405	-----	.35
7411	-----	1.75
7410	-----	.35
7410	-----	.50
7420	-----	.35
7420	-----	.35
7440	-----	.35
7440	-----	.35
7441	-----	1.60
7442	-----	1.30
7446	-----	1.75
7448	-----	1.15
7450	-----	.35
7451	-----	.35
7453	-----	.35
7454	-----	.35
7460	-----	.35
7472	-----	.50
7473	-----	.65
7474	-----	.65
7476	-----	.70
7480	-----	.65
7483	-----	1.30
7486	-----	.80
7491	-----	1.15
7492	-----	1.15
7493	-----	1.15
7495	-----	1.25
74107	-----	.70
74154	-----	2.50
74192	-----	2.50
74193	-----	1.50
74195	-----	1.10

LINEARS

LM100	-----	\$ 1.00
LM309H	-----	.75
LM309K	-----	1.00
NE5556	-----	2.00
NE560	-----	3.25
741(MINI DIP)	-----	.45
747	-----	1.10
709	-----	.45
710	-----	.40
711	-----	.40
723	-----	1.00
LM350D (audio amp)	-----	1.75

CMOS

C04001	-----	.75
C04002	-----	.75
C0401	-----	.75
C04012	-----	.75
C04023	-----	.75

Many thousands of you have become very familiar with the various Radio Society of Great Britain books and handbooks, but very few of you are familiar with their excellent magazine, **Radio Communication**.

It includes numerous technical and construction articles in addition to a complete rundown on the month's events in amateur radio. Surely a most interesting addition to your amateur radio activities.

We can now offer this fine magazine to you along with the other advantages of membership in the RSGB (such as use of their outgoing QSL Bureau) for \$12.95 a year.

comtec

Greenville, New Hampshire 03048

for the EXPERIMENTER!

INTERNATIONAL EX CRYSTAL & EX KITS

OSCILLATOR • RF MIXER • RF AMPLIFIER • POWER AMPLIFIER



1. MXX-1 TRANSISTOR RF MIXER

A single tuned circuit intended for signal conversion in the 3 to 170 MHz range. Harmonics of the OX oscillator are used for injection in the 60 to 170 MHz range. Lo Kit 3 to 20 MHz, Hi Kit 20 to 170 MHz (Specify when ordering)\$3.50



2. SAX-1 TRANSISTOR RF AMP

A small signal amplifier to drive MXX-1 mixer. Single tuned input and link output. Lo Kit 3 to 20 MHz, Hi Kit 20 to 170 MHz (Specify when ordering)\$3.50



3. PAX-1 TRANSISTOR RF POWER AMP

A single tuned output amplifier designed to follow the OX oscillator. Outputs up to 200 mw, depending on the frequency and voltage. Amplifier can be amplitude modulated. Frequency 3,000 to 30,000 KHz.....\$3.75



4. BAX-1 BROADBAND AMP

General purpose unit which may be used as a tuned or untuned amplifier in RF and audio applications 20 Hz to 150 MHz. Provides 6 to 30 db gain. Ideal for SWL. Experimenter or Amateur\$3.75



5. OX OSCILLATOR

Crystal controlled transistor type. Lo Kit 3,000 to 19,999 KHz, Hi Kit 20,000 to 60,000 KHz. (Specify when ordering).....\$2.95



6. TYPE EX CRYSTAL

Available from 3,000 to 60,000 KHz. Supplied only in HC 6/U holder. Calibration is $\pm .02\%$ when operated in International OX circuit or its equivalent. (Specify frequency)\$3.95

for the COMMERCIAL user...

INTERNATIONAL PRECISION RADIO CRYSTALS

International Crystals are available from 70 KHz to 160 MHz in a wide variety of holders. Crystals for use in military equipment can be supplied to meet specifications MIL-C-3098E.

CRYSTAL TYPES: (GP) for "General Purpose" applications
(CS) for "Commercial Standard"
(HA) for "High Accuracy" close temperature tolerance requirements.




write for
CATALOG



CRYSTAL MFG. CO., INC.
10 NO. LEE • OKLA. CITY, OKLA. 73102

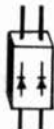MATCHED PAIR DIODES
70V $V_b - V_f = 1V @ 5mA$
FOR USE IN DETECTORS,
MODULATORS, BRIDGES,
IN MOLDED PACKAGE.
#MPD-0570.... 2/\$1.00



8.3V, 1W METAL ZENER
SELECTED FOR USE WITH SILICON TRANSISTOR
IN 9V REGULATOR CIRCUIT. \$.30, ...4/\$1.00

COMPUTER GRADE CAPACITORS.
JUST RIGHT FOR I.C. CIRCUITS.
HAS OPTIMUM RATINGS FOR 5
VOLT SYSTEMS. 5400uF @ 5 V.
#CGC-5542... \$.50, ...5/\$2.25




TANTALUM CAPACITORS

0.47uF @ 6V 12/\$1.00
4.7 uF @ 6V 10/\$1.00
6.8 uF @ 6V 8/\$1.00
GLASS SEALED, NEW



RECTANGULAR CASED
FILM CAPACITORS

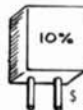

.22uF/250V
.22uF/63V

\$.10, 10/\$.75



TRANSISTOR MIX. THESE ARE NEW INDUSTRIAL SURPLUS,
NOT REJECTS. SOME HAVE 2N NUMBERS, SOME HAVE
INDUSTRIAL USER NUMBERS. SOME ARE COLOR CODED.
PLASTICS, METALS, PNPS, NPNS, UNIUNCTIONS. 20/\$1



tri-tek, inc.

P.O. BOX 14206, DEPT HR
PHOENIX, ARIZONA 85063

CONSTANT CURRENT REGULATOR. A BEAUTIFULLY MADE MODULE DESIGNED
AS A CONSTANT CURRENT REGULATOR. OP AMP CONTROLLED WITH IT'S OWN
BUILT-IN 10V SUPPLY. HEAVYPASS TRANSISTOR-SERIES BREAKER-CONTROLLER
ALL MOUNTED ON A BIG ALUMINUM HEAT SINK. UNIT CAN BE USED "AS IS"
FOR CURRENT CONTROL. A SIMPLE MOD TURNS IT INTO A SERIES VOLTAGE
REGULATOR USEABLE UP TO 3 AMPS. THERE ARE TWO VERSIONS OF THE MODULE.
ONE HAS NPN DEVICES FOR CONTROLLING "POSITIVE" CURRENT/VOLTAGE,
THE OTHER HAS PNP'S FOR NEGATIVE. EITHER, WITH DIAGRAMS..... \$4.25




LED READOUTS. MINIATURE, RED, 7 SEGMENT
WITH DECIMAL. COMMON CATHODE FORMAT.
CHARACTER SIZE IS 3/32" X 5/32". ONLY 10mA
PER SEGMENT. MAN-3 SIZE. PRIME PARTS!
STOCK # MOR10A.....\$1.50 ea, ...4/\$5.00

SQUARE LOOP CORE. TAPE WOUND
WITH 2 mil "SQUARE ORTHONOL".
DESIGNED FOR POWER INVERTERS AND
CONVERTERS. B(sat) = 14 to 15 KGauss
@ .3 Oersted AT 6 KHz. MADE BY
MAGNETICS, INC. \$.75, 10/\$6.00



TINY R.F. CHOKES. APPROXIMATELY
1uH..... 6/\$.25, 100/\$2.50

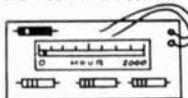RUNNING TIME INDICATORS. CURTIS INDIACHRON 120-LC
MERCURY TUBE MOUNTED ON A P.C. BOARD WITH ZENER
REGULATOR. WITH DATA SHEET. NEW LOW PRICE..\$1.75



NEW AND SURPLUS ELECTRONIC COMPONENTS FOR THE PRO
AND SERIOUS AMATEUR. AN ORDER OR 8c STAMP PUTS YOU
ON OUR MAILING LIST. MINIMUM ORDER \$3.00 U.S., \$15.00
FOREIGN. ALL ORDERS POSTPAID. PLEASE ADD INSURANCE

ON LINE SWR & POWER METERS



PRICE — \$29.95

FREQUENCY RANGE: 3 - 150 MHz
IMPEDANCE: 50 ohms
POWER: 0 - 1 Kw



PRICE — \$49.95

FREQUENCY RANGE: 3.5 - 150 MHz
IMPEDANCE: 50 or 75 ohms
POWER: 0 - 2 Kw

For further information and catalogs write, cable or call:

CARVILL INTERNATIONAL CORP.

P. O. Box 4039, Foster City, Ca., U.S.A. 94404

Cable "CARVILL" • Phone (415) 341-9959 • Telex 349334



BARGAINS!

KLEINSCHMIDT TELETYPE EQUIPMENT

- (1) TT-100 PAGE PRINTER. AS IS 60 OR 100 WPM \$59.95
- (A) TT-117 PAGE PR. OR (B) TT-179 REPERF. & TD, AS IS \$59.95
- ABOVE CHECKED OUT, OILED & ADJUSTED. EA. \$89.95
- (2) TABLE \$19.95 (C) TABLE \$34.95 (D) COPYHOLDER \$3.95
- (3) PAPERWINDER \$14.95 (4) TT-107 REPERF. ONLY \$49.95
- TH-5 CONVERTER TRANS/REC 100 CYCLES ADJUST TO 170 SHIFT \$49.95



Andy Electronics Co., Inc.

6431 Springer Street / Houston, Texas 77017

ALL PRICES FOB HOUSTON, TEX.

REEDLESS ENCODER



- SUB-AUDIBLE
- -30 TO 65°C OPERATION
- FAST STARTING TIME
- R F SHIELDED
- OPERATES ON 9 TO 18VDC
- SMALL SIZE ONLY
1.3" SQ X 1/2" HIGH

\$ 28.50

AVAILABLE FOR ANY EIA CODE
67.0 THRU 192.8 Hz

WRITE FOR COMPLETE SPECS AND DATA SHEET

Tobel ELECTRONICS

7920 Alida St La Mesa California 92041



YAESU

YOUR ASSURANCE OF PERFORMANCE & QUALITY

SP101 P \$59.00
SP101 19.00

FV101 \$99.00
160M THROUGH 10M

FT101 \$649.00
TRANSCVR 260W PEP

FL2100 \$339.00
80M THROUGH 10M
1200W PEP



The SP101-P Landliner provides phone patch operation as well as speaker. Front panel: Patch switch, meter, TX and RX gain controls. Rear apron: Receiver 4 ohm output, receiver 600 ohm output, monitor null switch, balance control, line jack, transmitter high Z jack.

The FV-101 permits split frequency operation and control from either the FT-101 or FTDX401.

The FT-101 exciter covers 160, 80, 40, 20, 15, (CB), and 10 meters and comes complete with microphone cable and plug, fused DC power cable and plug. AC cable with plugs and all necessary plugs are furnished. AC and DC supplies are internal.

The FL-2100 linear amplifier needs only 3 wire cable and coax cable. Connectors are furnished.

FTdx401 features high power, super sensitivity and sharp selectivity. The FTdx401 includes: AC power supply, noise blanker, 100 KC and 25 KC calibrators, VOX break-in, phone patch terminal, cooling fan. Covers 3.5 through 10 MHz plus WWV, 560 watts PEP. All that is required to get on the air is a microphone and speaker.

The FV-401 permits split frequency operation for the DX chaser or net operator. Covers 80 through 10 meters.

FL 2000 B 1200 watts PEP, 1000 watts CW, 600 watts AM. Drive power required 1000 watts. Has two cooling fans and uses two 572 B tubes.

Frdx400 includes 2 mechanical filters plus "T" notch rejection tuning, and clarifier for easy zero set for SSB. Crystal control 1st mixer and tunable 1st I.F. provides stable operation and high spurious rejection. 100 KC and 25 KC calibrators. VFO can be used in transceive operation in conjunction with F series transmitter.

FLdx400 operates SSB, (USB LSB selectable), AM, CW and FSK. Circuitry can be built in for RTTY operation. 240 watts PEP. VOX, PTT, and break-in CW.

FL-2000B grounded grid linear uses a pair of 572 B tubes. Plate meter VSWR monitor, 2 fans, built in power supply, 80 through 10 meters, 1200 watts PEP with distortion product in excess of 30 DB down.

FTDX401 \$599.00
TRANSCVR 560W PEP

FV401 \$99.00
EXTERNAL VFO
80M THROUGH 10M

FL2000B \$399.00
LINEAR AMP
1200W PEP

Frdx400 \$299.00
RECEIVER
160M THROUGH 10M



FLDX400 \$399.00
EXCITER
80M THROUGH 10M

FL2000B \$399.00
LINEAR AMP
1200W PEP

SP401 P \$59.00
SP401 19.00
SPEAKER/PATCH

FP-2 AC POWER SUPPLY



FT2FB \$239.00
144-148MHz
10W HIGH 1W LOW

FT2 AUTO \$379.00
144-148MHz



YC355 D \$289.00
DIGITAL COUNTER BUILT IN PRESCALER



Complete with
A.C. Power Cord 6 Ft.
D.C. Power Cord 6 Ft.
Signal Test Lead with
BNC Connector 3 Ft.

FP-2 AC power supply specifications: Output - 13.5 volts, 2 amps. AC input - 100/117/220/234 volts. Speaker - 5" x 3 1/2". Portable or home base operation can be achieved with the addition of the optional FP-2 power pack. This AC power pack provides regulated DC power for the transceiver and charging voltage for optional leak proof rechargeable colloidal type batteries. In addition, a high fidelity elliptical style speaker is built into the pack.

The FT-2FB opens the door to noise free broadcast quality 2 meter operation, and thanks to the repeater stations throughout the country, the 2 meter band is no longer restricted to line of sight. General coverage 144 to 148 MHz, 12 channels (3 supplied). Push to talk. Receiver .3 amps, transmit 1.7 amps, power source 13.5 volts + 10%. Dimensions 6-3/8" w. x 2-1/2" h. x 10" d, weight 4 lbs. Comes with dynamic microphone, connector plug, DC cord, fuse and mobile mount.

The FT-2 auto is a compact base or mobile VHF/FM transceiver, covering 146 to 148 MHz, featuring electronic scanning up to 8 stations between 146-148 MHz with priority channel sampling while locked on another channel. Adjustable tone burst push-button lock on for repeater actuation. The FT-2 auto is self-contained. Two power cables are supplied with the transceiver, including all mounting hardware, cables, connectors, and accessories required for both mobile and base installation, as well as dynamic push to talk microphone. Operates from various AC voltages or 13.5 DC. Dimensions 8-3/4" w. x 4-1/4" h. x 11-5/8" d. Weight 9 lbs.

YC-355D		SPECIFICATIONS		YC-355D	
Frequency range	5MHz to 25MHz (150kHz to 200MHz)	MAX Input Voltage	60V p-p, less than 10 sec (5V p-p)	220(V) XB01H X 220(D)	18 3/4 W X 3 3/4 H X 10 1/2 INCHES
Accuracy	± time base stability ± 1 count	Input Impedance	HIGH: 1 M ohm Low: 56 ohms	Tube	Display tube
Display	5 Digit	Input Capacity	Less than 20pF	Sem.	5
Sampling time	1 milli-sec or 1 sec	Time base Frequency	1 MHz Crystal controlled	conductors	12
Display time	0.1 sec - 2 sec	Stability	0.0025% at 25° C 0.0025% at 0° - 40° C		9
Frequency Unit	KHz MHz	Power Requirements	100/110/117/200/220/234V 50/60Hz 18V A		1
Display	Display tube		12-14.5V 1A		26
Input Voltage	20mV - 20V p (0.15V - 5V p-p)				

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

FACTORY SERVICE IS AVAILABLE WHERE WARRANTY HAS EXPIRED. MK-160 (160M) KIT \$16.00 WITH XTAL PLUS LABOR. MODERNIZATION KIT MIR-1 FOR OLDER MODEL FT101 \$70.00 FACTORY INSTALLATION ONLY.

HENRY RADIO STORES
Los Angeles, Anaheim, Cal.; Butler, Mo.
HAM RADIO OUTLET
Burlingame, Cal.
RACOM ELECTRONICS/Renton, Wash.
ADIRONDACK RADIO SUPPLY/Amsterdam, N.Y.

WILSON ELECTRONICS/Pittman, Nev.
ED JUGE ELECTRONICS
Fort Worth, Tex.
AMATEUR ELECTRONICS SUPPLY
Milwaukee, Wis.; Cleveland, Ohio; Orlando, Fla.
GRAHAM ELECTRONICS/Indianapolis, Ind.

FRECK RADIO & SUPPLY/Asheville, N. C.
HARRISON RADIO
Farmingdale, L.I., Valley Stream, L.I., New York City, N.Y.
HAMTRONICS
Trevose, Pa.
HAM RADIO CENTER/St. Louis, Mo.
WEBSTER RADIO/Fresno, Cal.

TWX 910-346-7624
TEL 213-633-4007



YAESU MUSEN USA INC.
7625 E. ROSECRANS AVE. UNIT 29 PARAMOUNT, CAL. 90723



CRYSTAL FILTERS and DISCRIMINATORS

1 27/64" x 1 3/64" x 3/4"



by
K.V.G.

9.0 MHz FILTERS

XF9-A	2.5 kHz	SSB TX	\$33.95
XF9-B	2.4 kHz	SSB RX	\$47.70
XF9-C	3.75 kHz	AM	\$51.40
XF9-D	5.0 kHz	AM	\$51.40
XF9-E	12.0 kHz	NBFM	\$51.40
XF9-M	0.5 kHz	CW	\$35.95

9.0 MHz DISCRIMINATORS

XD9-01	± 5 kHz	RTTY	\$25.30
XD9-02	± 10 kHz	NBFM	\$26.35
XD9-03	± 12 kHz	NBFM	\$25.30

9 MHz CRYSTALS (Hc25/u)

XF900	9000.0 kHz	Carrier	\$4.00
XF901	8998.5 kHz	USB	\$4.00
XF902	5001.5 kHz	LSB	\$4.00
XF903	8999.0 kHz	BFO	\$4.00
F-05	Hc25/u	Socket	.50

VHF CONVERTERS UHF

	MMc 50	MMc 144	MMc 220	MMc 432	MMc 1296
RF Freq. (MHz) +	50-54	144-148	220-224	432-436	1296-1300
IF Freq. +	28-32	28-32	28-32	28-32	144-148
N.F. (typical)	2.5dB	2.8dB	3.4dB	3.8dB	9.0dB
Nom. Gain	30dB	30 dB	26dB	28dB	9.0dB
	\$53.70	\$53.70	\$64.45	\$64.45	\$75.20

Power 12V D. C.

1 1/4" x 2 3/8" x 4 3/8" + connectors


Very low N. F. units on special order.

+Other ranges, amateur & commercial, to order.



**SPECTRUM
INTERNATIONAL**
BOX 1084 CONCORD
MASSACHUSETTS 01742

CW/RTTY/ REPEATER IDENTIFIER

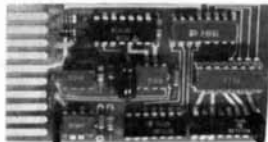

Uses 256 bit read-only-memory programmed for your CW call or RTTY message. NE555 timers for clock, tone generator and 5 minute timer. Apply 5 volts and COR and it outputs tone and PTT. Board \$8, Kit \$30, Tested \$35

OTHER BOARDS AND KITS AVAILABLE:

Two Tone Decoder: (2 NE567 decoder IC's, AND gate, dual flip-flop)

Board \$4.00; Kit \$22.00; Wired and Tested \$25.00

12/16 Button Decoder: (NE567 decoder IC's and 7402 AND gates)

Board \$10.00; Kit \$77.00 & \$88.00; Tested \$85 & \$98

Phase Locked Loop RTTY Converter: (NE565 PLL and two 741 Op-Amps)

Board \$4.25; Kit \$25.00; Tested \$30.00

RY Test Generator: (outputs 2 characters in repetitive or clutched modes)

Board \$5.00; Kit \$17.00; Tested \$20.00

AFSK Oscillator: Tested \$8.00

4 Channel Tone Burst Generator: Tested \$10.00

2-Meter Pre-Amp: Tested \$13.00

8-Channel Scanner: Tested \$25.00

WRITE FOR FREE CATALOG



SIGNAL SYSTEMS

2650 DURANGO DRIVE
COLORADO SPRINGS, CO. 80910

(303) 392-9073

OLD OLD OLD
RELIABLE RELIABLE
\$425.00 RX 1 ROTATOR \$425.00

10 YEARS OF PROVEN SERVICE. THE HEAVY DUTY ROTATOR THAT WILL TURN ANY BEAM ARRAY YOU WANT TO INSTALL. CONTROL BOX TO MATCH S LINE. 115VAC SELSYN IND. 380 DEGREES ROTATION. LIMIT SWITCH UNIT IS 9 1/2" DIA. 28" IN HEIGHT.

Designed Built Backed
by ANTENNA MART
Box 7, Rippey, Iowa 50235


DIGITAL:THEORY,DESIGN,
CONSTRUCTION

**LOGIC
NEWSLETTER** ©

SAMPLE COPY \$ 1.00
LOGIC NEWSLETTER
POB 252
WALDWICK,N.J. 07463

7 SEGMENT LED Readouts

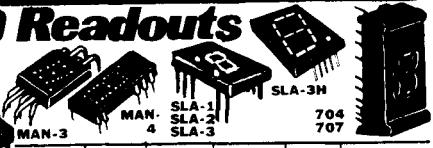All fit 14-pin IC sockets, 5V 10 to 20 mils, 0-to-9 numerals, plus letters & decimal. With spec sheets.
 * Monsanto Equal, MAN-1
 ** MAN-1 Specs.
 † 35-Diode Array.



MONSANTO "ALL LED" Type	Size:	Color Display	Decimal	Driver	Each	Special
<input type="checkbox"/> MONSANTO MAN-1*	.27	Red	Yes	SN7447	4.50	3 for \$12.
<input type="checkbox"/> MONSANTO MAN-3*	.115	Red	Yes	SN7448	2.25	3 for \$6.
<input type="checkbox"/> MONSANTO MAN-3*	.115	Red	No	SN7448	1.49	3 for \$3.
<input type="checkbox"/> MONSANTO MAN-4*	.190	Red	Yes	SN7448	2.95	3 for \$8.
<input type="checkbox"/> MONSANTO MAN-4*	.190	Red	No	SN7448	1.79	3 for \$5.

"REFLECTIVE LITE BAR" (SEGMENT) LED READOUTS! **** Decimal right or left						
<input type="checkbox"/> LITRONIX 707** (MAN-1)	.33	Red	Yes	SN7447	3.50	3 for \$9.
<input type="checkbox"/> LITRONIX 704*** (MAN-4)	.33	Red	Yes	SN7448	3.50	3 for \$9.
<input type="checkbox"/> OPCOA SLA-1** (MAN-1)	.33	Red	Yes	SN7447	3.50	3 for \$9.
<input type="checkbox"/> OPCOA SLA-3H Giant Digit	.70	Red	Yes	SN7447	8.60	3 for \$24.
<input type="checkbox"/> OPCOA SLA-2 Plus/Minus/1	.33	Red	No	SN7447	3.50	3 for \$9.
<input type="checkbox"/> OPCOA SLA-11C (MAN-5)	.33	Green	****	SN7447	4.95	3 for \$13.
<input type="checkbox"/> OPCOA SLA-12 Plus/Minus/1	.33	Green	—	SN7447	4.95	3 for \$12.

OAK FEATHER-TOUCH SWITCHES

*For RTTY
 *Printed Circuits
 *For Unique Panel Switches

Mfd. by OAK (Ham's note, RTTY, too) data systems, same as used in Keyboard Calculator, SPST. Normally Open, 24V 1 amp contacts. Characters and letters easily changed. 3/8" high. Printed circuit.

*White top, black numbers.
 †Blue top, white characters.
 Kit of 17 above switches for keyboard \$7.50



CALCULATOR KEYBOARD

3 for \$27 **9.95**

Etched calculator board with holes, as above, less switches ... \$2.50 Board

Properly etched, drilled, "MULTI-PLEXED," with proper drivers. Ready to go! Used with our own CAL TECH'S 5001 chip advertised at \$ 9.95 or equal to Cal Tech or Mostek chip. Keyboard uses the new manufactured by OAK, printed-circuit low-profile FEATHER TOUCH switches, 0-to-9 in white with black letters. Decimal white with black dot. CE, CL and the 4 function switches are in blue with white characters. Designed by top maker. Size: 6 1/2 x 4 1/2 x 1/2". All etched connections link to take a 12-pin edge connector.

LIGHT EMITTING DIODE GaAs INDICATORS

- 2-MV1*, Amber, visible jumbo epoxy lens upright... \$1.00
- 1-MV2*, TO-18, Small, dome, green, visible... 1.00
- 1-MV-2*, green small dome, green diff. lite... 1.00
- 1-MV-2*, clear small plastic dome, green diff. lite... 1.00
- 1-MV-3*, micro-mini "pin head" dome, TO18, green lite... 1.00
- 3-MV3*, visible, "coax pin pak", red, mini dome lens... 1.00
- 1-MV4*, stud, high power, red, 2-watts... 2.95
- 1-MV4H*, stud, high power, hi-dome, red, 2-watts... 1.00
- 3-MV10B, visible, red, clear, dome lens, TO-18... 1.00
- 3-MV10C, visible, red, diffused, dome lens, TO-18... 1.00
- 3-MV50*, axial leads, micro-mini dome, clear, red... 1.00
- 3-MV55*, axial, micro-mini, red, lite, red lens... 1.00
- 3-MV5012*, visible, red, small dome lens... 1.00
- 3-MV5020*, jumbo clear dome, TO-18, visible, red... 1.00
- 3-MV5021*, jumbo red diffused lens, visible, lite RED... 1.00
- 3-MV5022*, jumbo red lens, visible RED lite, spade, upri... 1.00
- 3-MV5026*, jumbo red diffused lens, RED lite, spade... 1.00
- 1-MV5040*, 4-LED red array, with 5-lead pak... 1.49
- 3-MV5054*, visible, red, jumbo dome lens, upright... 1.00
- 2-MV5060*, TO-18, micro-mini, clear dome, red... 1.00
- 4-MV5082, visible, red, clear flat lens, TO-18... 1.00
- 1-MV5222*, green hi plastic dome, diffused green lite... 1.00
- 1-MV5222*, clear hi dome, diff. green lite... 1.00
- 1-MV5222*, jumbo dome, green, panel snap-in... 1.49
- 1-MV5322*, jumbo dome, GaAsP, panel snap-in Yellow... 1.98
- 1-MV5491, jumbo, Tri-State, RED, GREEN, OFF, special... 1.00
- 1-MV5000*, cartridge panel lamp, sealed, red, clear lens... 1.49
- 2-MT-2*, Photo Transistor, light sensor, TO-18... 1.00
- 2-ME-1*, infra-red, parabolic lens, pin type... 1.00
- 3-ME-3*, infra-red, invisible lite, "pinhead", single lead... 1.00
- 3-ME-4*, infra-red, "invisible", TO-18, diff. dome... 1.00
- 3-ME-60*, infra-red, "invisible", axial, micro-mini... 1.00

*Monsanto Equivalent

MUX'D DIGITAL CLOCK PC BOARD

Each board properly multiplexed for 6 digits, to hold
 Your choice **\$2.50**

MAN-1 Litronics 704 (MAN-1*)
 MAN-3 Litronics 707 (MAN-4*)
 MAN-4 Opcoa SLA-1 (MAN-1*)
 6-MAN-3A's for above board, \$9.50.



READOUT	Char.	Maker	*Your choice of 5 red LED readouts!
<input type="checkbox"/> MAN-1	.27 h.	Monsanto	Buy 3 — Only \$9.99 Take 10%.
<input type="checkbox"/> MAN-4	.19 h.	Monsanto	
<input type="checkbox"/> 707*	.33 h.	Litronics	
<input type="checkbox"/> 704*	.33 h.	Litronics	
<input type="checkbox"/> SLA-1*	.33 h.	Opcoa	

Scientific Devices "Digital Counting Modules" outperform any other DCM on the market today. More features than ever before! Not gaseous, not incandescents, not nixie but the modern LED. Choose from such famous manufacturers as Monsanto's MAN-1, MAN-4, Litronics 707 and 704, Opcoa's SLA-1 (the last 4 having character heights of 0.33 at no extra charge). Each kit includes 3x2" p.c. board with fingers for a FREE edge connector, side-mounting dip socket, LED readout of your choice, resistors, 3 IC's, and Molex connectors (this ELIMINATES SOLDERING YOUR IC's) and booklet. INCLUDES P.C. EDGE CONNECTOR — FREE!

* Pin-for-pin MAN-1, ** Pin-for-pin MAN-4, elec. char. same

Terms: add postage. Rated: net \$0
 Phone Orders: Wakefield, Mass. (617) 245-3829
 Detail: 16-18 Del Carmine St., Wakefield, Mass.
 (off Water Street) C.O.D.'S MAY BE PHONED

15¢ CATALOG on Fiber Optics, 'IC's, Semi's, Parts

POLY PAKS

P.O. BOX 942H LYNNFIELD, MASS. 01940



12-CALCULATOR ON A CHIP DIGIT

CT5001 Chip **9.95**
 Similar to Mostek 5001. Outperforms Texas Instruments TMS1802. A 40-pin DIP. Adds, multiplies, subtracts, and divides. Used with 7-segment readouts, Nixies, and LED's. We include schematics, instructions to build calculator.
 CT5002-9 Volt version of above — \$9.95
 CT5005-Same as above with MEMORY — \$14.95

NATIONAL EQUAL "DIGITAL CLOCK on a CHIP"

Any "Chip" **\$12.88**

*Money Back Guarantee!

- 5311 28-pin, ceramic, any readout, 6-digits: A-B-D \$12.88 *With Spec!
- 5312 28-pin, ceramic, any readout, 6-digits: C-D \$12.88 Sheet!
- 5313 28-pin, ceramic, any readout, 6-digits: A-C \$12.88 Sheet!
- 5314 24-pin, plastic, LED and incandescent readouts, 6-digits: A-B \$12.88 Save!
 Code: A—Hold Count. C—PPS Output. B—Output Strobe. D—BCD

Measures only 3/4 x 1 x 1/2" **POTTER BRUMFIELD MINI CAP RELAYS**
 KNP type. For pc board socket, 14 lugs. 1-8/32 Your choice stud top! Both 4PDT. All **115 VAC \$2.49**
 ceramic construction. 3 24 VDC 3E for \$6
 amps, contacts. For r-f ant, switching. Wt. 1-oz.

Type SP332, each digit is **SPERRY "ORANGE" TWIN DIGIT ARRAY**
 individually controlled, operates of 180VDC, 100 ua, 200 mw. Color: ORANGE. 7-digits, glass protection over digits. Character height: 0.33, P.C. mounting. Size: 3/4 x 3/4, 9-pin per digit. Driver: SN7447. **\$5.95 3 for \$15.**

SPECTROL CERMET "MICRO" POTS

Model No. 53-2-1, Cube 5/16" square, single turn, screw adjust front. Model No. 42-2-1, Rectangular 3/4" x 3/16" x 5/16", screw driver adjust, side. PC work. Both cermet sealed. Order by model number and value.

Your Choice	Ohms	Any 2 for \$1
<input type="checkbox"/> 10	<input type="checkbox"/> 1K	
<input type="checkbox"/> 20	<input type="checkbox"/> 2K	
<input type="checkbox"/> 50	<input type="checkbox"/> 5K	
<input type="checkbox"/> 100	<input type="checkbox"/> 10K	
<input type="checkbox"/> 200	<input type="checkbox"/> 20K	
<input type="checkbox"/> 500	<input type="checkbox"/> 50K	



AT LAST! A service manual covering the Model CX7 and CX7A has been printed and is ready for delivery.

This informative manual includes the "A" modifications and late production changes. It also includes information to improve cross modulation, sensitivity, AGC action and transient suppression, plus other information such as phone patch hook-up, identification of accessory connection points and a simplified tune-up procedure. The manual is quality offset printed with a durable cover and comb-bound.

Order by mailing \$25.00 check or money order plus postage and handling (Midwest and Eastern states, \$2.00; Western states, \$1.50). Calif. add 6%.

PUBLISHED BY

THOMAS ADVERTISING CO.
715 Silver Spur Road, Suite 210
Rolling Hills Estates, California 90274
(213) 377-7284



ALSO - MANUALS FOR
STANDARD COMMUNICATIONS
SR-C806 AND SR-C826

**HAPPINESS
IS HAVING
YOUR OWN
HAM-MATE™**



The New HAM-MATE™ Directional RF Wattmeter is a direct descendant of the famous model 43 THRULINE® — the professional standard of the industry. Designed specifically for the serious radio amateur, three models currently available measure forward and reflected power in the following ranges:

- 4350: 2000/200W, 1.8-30MHz (160 meters to 10 meters)
- 4351: 1000/200W, 1.8-30MHz (160 meters to 10 meters)
- 4352: 400/40W, 50-150MHz (6 meters, 2 meters)

All have an Insertion VSWR below 1.1 in 50-52 ohm lines, a minimum of 20dB Directivity, 8% Accuracy, SO-239 female UHF connectors and carry the 12 months guarantee of all Bird instruments.

ONLY \$79 (plus \$1 shipping)

Also available at Henry Radio, Hamtronics, etc.



BIRD ELECTRONIC CORPORATION

30303 AURORA RD. • CLEVELAND (SOLON) OHIO 44139
Phone 216-248-1200 • Cable BIRDELEC

know this sign



To most people this is a symbol from Greek mythology. But to hundreds of thousands of active amateurs, Pegasus is the symbol of the Radio Amateur CALLBOOK the single most useful operating reference for active amateur stations. The U.S. Edition lists over 285,000 Calls, Names and Addresses in the 50 States and U.S. possessions while nearly 200,000 amateur stations in the rest of the World are listed in the DX edition.

Both editions contain much other invaluable data such as World Maps, Great Circle Maps, QSL Managers around the World, ARRL Countries list and Amateur Prefixes around the World, Time information, Postal Information and much, much more. You can't contest efficiently, you can't DX efficiently, you can't even operate efficiently without an up to date CALLBOOK.

To make the CALLBOOK even more valuable, three supplements are issued each year which bring your copy completely up to date every three months. These are available at a modest extra cost. Full details in every CALLBOOK.

Get your copies of the big new 1973 CALLBOOKS today.

US CALLBOOK

(less service editions)

Just \$8.95

US CALLBOOK

(with service editions)

\$14.95

DX CALLBOOK

(less service editions)

Just \$6.95

DX CALLBOOK

(with service editions)

\$11.45

Mail orders add 50¢ per CALLBOOK postage and handling.

See your favorite dealer or send today to:

WRITE FOR FREE BROCHURE  RADIO AMATEUR **callbook** INC.
Dept. E 925 Sherwood Drive
Lake Bluff, Ill. 60044

2 METER

or 144-146 MHz

25 WATTS

- 1-2 WATTS IN
PA-1501H — 15-20 WATTS OUT
PA-2501H — 25-30 WATTS OUT
- ONLY 2" x 2½" x 6"

- 12-14 VOLTS
NEGATIVE GROUND
- LESS THAN 1 DB
LOSS ON RECEIVE
- SOLID STATE
SWITCHING



PA1501H	\$49.95	WIRED & TESTED	\$39.95	COMPLETE KIT
PA2501H	\$69.95		\$59.95	

Also available:

• RX-50C 30-60 MHz receiver kit w/crystal filter.....	\$59.95
• RX144/220A 2/220 receiver kit	59.95
• RX-144/220F 2/220 receiver wit w/ceramic filter	65.95
• RX-144/220C 2/220 receiver kit w/crystal filter	69.95
• TX-144 1 watt exciter	29.95
• TX-220 1 watt exciter	29.95
• PA-144/220 15 watt amp less cabinet, connectors, and switching	29.95
• PA-144/220 25 watt amp less cabinet, connectors, and switching	49.95
• PA-8005H 90 watt amp 5 watts in wired/tested	159.95
• PA-8020H 90 watt amp 25 watts in wired/tested	129.95
• PA-432 10 watt amp less cabinet, connectors, and switching	39.95
• PS-12 12 amp regulated 12-15 volt power supply kit	59.95
• PS-12W Wired/tested	69.95
• PS-24 24 amp same as PS-12 less case	69.95
• COR-1 COR with 3 second and 3 minute timers	19.95

Write for data sheets on any above units. Add postage. NY state residents add sales tax.



VHF ENGINEERING

— DIV. OF BROWNIAN ELECT. CORP. —

320 WATER ST. POB 1921 BINGHAMTON, N.Y. 13902 607-723-9574



YAESU FT-101
now with 160 meters

SEE **WILSON**
for your Yaesu products

FTDX 401 Transceiver
FL2100 Linear Amplifier
FL2000B Linear Amplifier

Interested in trading Tempo One's
and other Yaesu equipment.

WILSON ELECTRONICS

BOX 794 HENDERSON, NEVADA, 89105
702-451-5791

LOW PRICES ON POPULAR COMPONENTS IF FILTERS

- Monolithic crystal filters at 10.7 and 16.9 MHz
- Ceramic filters at 455 kHz

SEMICONDUCTORS

- VHF power transistors by CTC-Varian
- J and MOS FETS
- Linear ICs — AM/FM IF, Audio PA
- Bipolar — RF and AF popular types

INDUCTORS

- Molded chokes
- Coil forms — with adjustable cores

CAPACITORS

- Popular variable types

QUALITY COMPONENTS

- No seconds or surplus
- Name brands — fully guaranteed
- Spec sheets on request

GREAT PRICES

- Price breaks at low quantities
- Prices below large mail-order houses

WRITE FOR CATALOG 173

AMTECH

P. O. BOX 624, MARION, IOWA 52302
(319) 377-7927 or (319) 377-2638



**A new book
from HR...
worth looking into!**

Here it is! HAM RADIO'S first book, a compilation of the best of our popular Ham Notebook section during our first years of publication.

Just loaded with clever ideas and nifty little circuits to make your time in the ham shack more productive and enjoyable.

The many chapter headings include:

Antennas and Transmission Lines
FM and Repeaters
Keying and Control
Measurements and Test Equipment
Oscillators
Power Supplies
Receivers and Converters
Transmitters
VHF and UHF
Station and Workshop

**Just \$3.95
postpaid**

comtec

BOOKS


Greenville, New Hampshire 03048

The Most Powerful Antennas Under the Sun



hy-gain 402BA

DX DEMON!

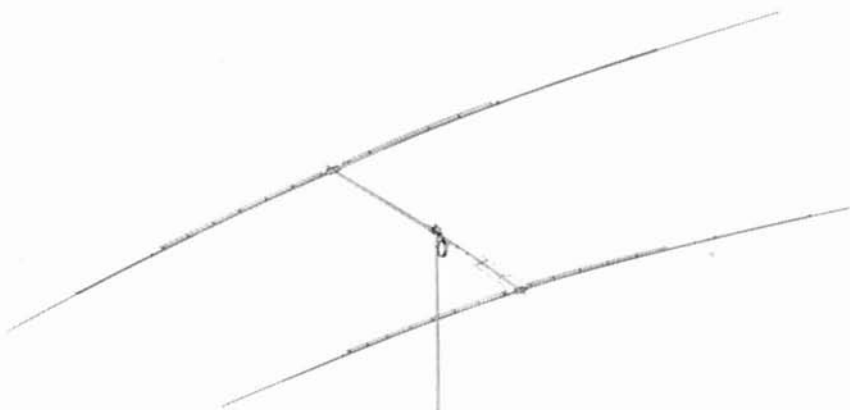

40 METERS

If 40 meters is your bag, try this one for best 40 meter performance...you'll work signals on 40 meters that you never knew existed!

The Model 402BA attenuates unwanted signals off the side and back at 12 to 25 db while amplifying signals for 4.9 db minimum forward gain. Unique linear loading stub delivers maximum performance without lossey center coils. Easily stacks with tribander or 20 meter beam; requires only 10' separation. 52 ohm feed. Beta Matched. 16 ft. boom, 43 ft. elements. Maximum power input 1 kw, AM.

Order No. 397

\$179.95

Hy-Gain 402BA... the 40 meter DX Demon!

HY-GAIN ELECTRONICS CORPORATION

Dept. WH, 8601 Northeast Highway Six
402/434-9151

Lincoln, NE 68507
Telex 48-6424



SMC. XTALS-8333-9000.
Silk Screened Panel.
18 Watts Output.

Price **49.95**

Net to Amateurs
Complete with Tubes
Power Supply \$9.95

SIX METER TRANSMITTER

- for
- MOBILE
 - FIXED STATION
 - EMERGENCY
 - AVIATION

TUBE COMPLIMENT
6U8 Oscillator Multiplier
12AX7 Speech Amplifier
2E26 Final Amplifier
6BQ5 Modulator



EXCELTRONICS RESEARCH LABS
MANUFACTURERS OF ELECTRONIC DEVICES
224-15 Linden Blvd. Cambria Heights, N. Y. 11411



THE EASIEST WAY YET...

To measure frequency to 250 MHz. Thru-line feature for transmitters, preamp and probe for receiver crystals. The 20dB gain preamp may be purchased separately for use with any counter. Write for details.

VHF Counter preamp w/probe \$35.00 ppd
Model 6-VHF-A Counter \$350 fob

PAGEL ELECTRONICS

6742-C TAMPA AVENUE
RESEDA, CALIF. 91335

SPACE-AGE TV CAMERA KITS & PLANS



BE A PIONEER IN HOME TELECASTING! Build your own TV CAMERA. Model XT-1A, Series D, \$116.95 pp. Solid-State. Step-by-step construction manual. High quality. Connects to any TV without modification. Ideal for home, experimenters, education, industry, etc.

PHONE or WRITE for CATALOG.
DIAL 402-987-3771

Many other kits, parts and plans available including starter kits, focus/det. coils, vidicon tubes, const. plans, etc.

1301 BROADWAY, N.W. **ATV Research** DAKOTA CITY, NEBR. 68731

STOP

REGENCY HR-2MS	\$319.00
REGENCY HR-212	\$259.00
REGENCY HR-220	\$239.00
HYGAIN TH6DX	\$179.95
HYGAIN 204BA	\$149.95
GALAXY GT-550A	\$595.00
HALLICRAFTERS SR400A	\$995.00
HALLICRAFTERS FPM300	\$595.00
ICOM IC-20	\$299.00
ICOM IC-21	\$399.00
GLADDING 25	\$249.95
STANDARD 146A	\$289.00
ICOM IC-22	\$279.00

LOU GOLDSTEIN, K4LAN


P.O. BOX 3561, PENSACOLA, FLA. 32506
Drop me a line for those unadvertised extras

Extend your VHF range without overextending your budget . . .

THE NEW . . . KLM VHF and UHF Booster Amplifiers

Check these "no compromise" features:

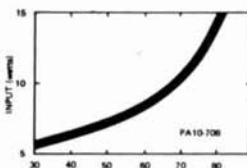- No tuning
- No Damage at any VSWR
- Fixed Tuned "Micro-Stripline" Circuits for Reliability and Optimum Performance
- Automatic Antenna Switching with Local or Remote Override - PA2-12B automatic only
- Models Compatible with All Popular FM Transceivers
- Warranty: 90 days on parts and labor
- DC Input: 11.5 to 14.5 Vdc



California residents add 5% - Add \$2.00 per unit for PPD U.S.A. Prices subject to change without notice.

Frequency (MHz)	Model	Input Range (w)	OUTPUT (watts)				Price
			Nominal P _o (w)	Nominal Amps	Size		
144	PA2-12B	1-4	12	1.8	2.25 x 5.2"	\$ 44.95	
	PA10-40B	5-15	40	5.0	6.5 x 5.2"	79.95	
	PA10-70B	5-15	70	7.0	6.5 x 7.5 x 2"	129.95	
	PA2-70B	1-4	70	8.0	6.5 x 7.5 x 2"	149.95	
	PA10-140B	5-15	140	18.0	6.5 x 10 x 2"	179.95	

PA10-140B
\$179.95

"THE COMMUNICATIONS EQUIPMENT INNOVATORS"

1600 Decker • San Martin, California 95046
(408) 683-4240 or (408) 842-7349

KLM ELECTRONICS

If you like 2 METER . . .

YOU'LL LOVE OUR

ALL NEW
HR-2B
NARROW BAND FM TRANSCEIVER



**15 OR 1 WATT POWER OUT/SWITCH SELECTABLE /
FULL 12 CHANNEL TRANSMIT AND RECEIVE CAPABILITY**

You'll like the crystal clear transmit and receive performance of this compact, 2 meter unit and so will those listening. The 12 transmit channels are provided with individual trimmer capacitors for the optimum in point-to-point and repeater applications. A HI/LO power switch provides 1 watt output or full rated output. The receiver has an audio output of 3 watts at excellent sensitivity. Solid state, American made quality at a low price.

\$229⁰⁰

AMATEUR NET

includes plug-in ceramic mike,
mounting bracket and transmit and
receive crystals for 146.94 MHz.

Regency
the first name in solid state


THE FM LEADER IN 2 METER AND 6 METER . . . AND NOW 220 MHz

HEAT SINKS • IC TERMINALS • IC SOCKETS • DIODES • CAPACITORS • TRANSFORMERS • RESISTORS • INTEGRATED CIRCUITS

TRANSFORMERS • CAPACITORS • DIODES • IC SOCKETS • HEAT SINKS • VECTORBOARDS • VECTORPINS • INCANDESCENT DISPLAYS

HAVE A COPY OF OUR NEW CATALOG YET?

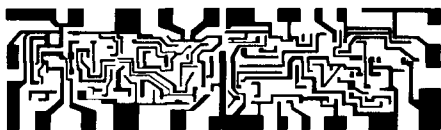IF NOT, WRITE OR CIRCLE READER SERVICE CARD FOR YOUR COPY NOW!



SOLID STATE SYSTEMS, INC.
P.O. BOX 773
COLUMBIA, MISSOURI 65201

(CALL TOLL FREE) 800-325-2981

UNIVERSAL DECADE COUNTING UNITS • RESISTOR ASSORTMENTS • LED DISPLAYS

flea market



■ **RATES** Commercial Ads 25¢ per word; non-commercial ads 10¢ per word payable in advance. No cash discounts or agency commissions allowed.

■ **COPY** No special layout or arrangements available. Material should be type-written or clearly printed and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** can not check out each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue. Deadline is 15th of second preceding month.

■ **SEND MATERIAL TO:** Flea Market, Ham Radio, Greenville, N. H. 03048.

SIGNAL ONE OWNERS, expert and prompt service by ex-Signal/One engineer. Also will purchase your functioning or not functioning unit or spare parts. Write or call for details. Larry Pace, K2IXP/7, 1071 W. Roller Coaster, Tucson, AZ. 85704 (602-888-5234).

YAESU TRANSCEIVER OWNERS — present and prospective. Join the international Fox-Tango Club. Send business-size SASE or IRC for information and sample Newsletter. Milton Lowens, WA2ADQ, 3977-F Sedgwick Ave., Bronx, N. Y. 10463.

ROCHESTER NY 1974 WNY hamfest dates are May 17 and 18. Exhibitors: space reservations now being accepted. WNY Hamfest, Box 1388, Rochester, N. Y. 14603.

FRAME & DISPLAY your QSL's with 20 pocket plastic holders. Two for \$1.00, seven for \$3.00 from your Dealer or direct, prepaid. Free sample to Dealers upon request. TEPABCO, Box 198H, Gallatin, Tennessee 37077.

DO-IT-URSELF DXPEDITION — Stay at ZF15B — Cayman Is. Vertical antenna and Caribbean at your doorstep. Diving/fishing if band folds. We arrange license. Write Spanish Bay Reef Resort, Box 800K, Grand Cayman, B. W. I.

SELL OR TRADE Hasselblad 500C camera with accessories \$1250.00 or factory sealed new 755°C or make offer! SASE for info. Jim K4YBB, 942 N. W. 116 St., Miami, Fla. 33168.

KEYBOARD FOR AUTO-PATCH CONTROL 3" x 4" keyboard by Chomerics, Inc. conductive elastomeric contact. Telephone format. Model EF 20071 touch-tone encoded \$9.40 each. Also What Sound Do You Need? Miniature audible signalling devices. Bleep-tone® either 2.5 kHz or 1.0 kHz 12V dc 6.6 ma. Either model \$6.45 each, includes mounting ring. Postpaid. Send money order for stock shipment. Technical distributor. C. A. Briggs Company, P. O. Box 151, Glenside, Pa. 19038, 215-885-2244.

PRINTED CIRCUIT DRILL BITS. Trumbull, 833 Balra Drive, El Cerrito, California 94530.

"**HOSS TRADER Ed Moory**" says he will not be undersold on Cash deals! Shop around for your best price and then call or write the "HOSS" before you buy! New Galaxy GT-550A transceiver, reg. \$595.00, cash \$449.00; New TR-22 Drake two meter transceiver, reg. \$219.95, cash \$175.00; Demo TR-4C, \$479.95; Demo Swan 500CX, \$429.00; New Collins in stock: New Rohn 50 ft. heavy-duty foldover tower, prepaid, \$255.00; New Mosley CL-33 and demo Ham-M rotor, \$215.00; Used equipment: R4-C, \$399.00; T4-XC, \$425.00; R4-B, \$309.00; Ham-M, \$85.00; Mint KWM-2, \$650.00; FPM-300, \$489.00. Moory Electronics Company, P. O. Box 506, DeWitt, Arkansas 72042, Tel: 501-946-2820.

TELETYPEWRITER PARTS, gears, manuals, supplies, tape, toroids. SASE list. Typetronics, Box 8873, Ft. Lauderdale, Fl. 33310. Buy parts, late machines.

MUST SELL: New Signal/One CX7A with both instruction & schematic manuals. \$1300.00. Contact Lewis Grigsby Jr., Farmers State Bank, Pittsfield, Ill. 62363 (217) 285-2194.

PRECISION HAND TOOLS, special ham-experimenter discount. Letter brings mailings. Artisan Tool Company, Box 36, Glenmont, New York 12077.

SURPLUS test equipment, VHF and microwave gear: Bulletins. D. Edsall, 2843 St. Paul, Baltimore, Md. 21218.

1000 PIV AT 2.5 AMP diodes. New Motorola HEP-170. 10 for \$2.50, 100 and up, 20¢ each, postpaid. K.E. Electronics, Box 1279, Tustin, California 92680.

WE BUY LATE MODEL Collins - Drake - Swan. Top prices. Cash. Associated Radio, 8012 Conser, Overland Park, Kansas 66204. Call: 913-381-5901.

WANTED: ARC-5/VHF components. Mounting racks MT-65 and MT-71. Control unit C-42, junction box J-28. Also need connectors. W8BNLM, 146 Schonhardt, Tiffin, O. 44883.

HOOSIER ELECTRONICS — Your ham headquarters in the heart of the Midwest where only the finest amateur equipment is sold. Individual, personal service by experienced and active hams. Factory-authorized dealers for Standard, Clegg, Genave, Drake, Regency, Hallicrafters, Tempo, Kenwood, Ten-Tec, Midland, Galaxy, Hy-Gain, CushCraft, Mosley, Hustler, Ham-M, Sony, plus many more. Orders for in-stock merchandise shipped the same day. Write or call today for our quote and try our personal, friendly Hoosier service. Hoosier Electronics, R. 25, Box 403, Terre Haute, Indiana 47802. (812)-894-2397.

STANDARD 146-A still in factory carton with warranty card. \$238.70. W40AQ, Box 17222, Nashville, Tenn. 37217, (615-834-8993).

TECH MANUALS for Govt. surplus gear \$6.50 each: R-389/URR, R-390/URR, R-220/URR, R-274/FRR, LP-5, RCK, URM-32, TT-63A/FGC, TS-382D/U, BC-779B, BC-610, CV-591A/URR, SP-600 JX, USM-16, BC-348JNQ, OS-8C/U, TS-497A/URR, TS-497B/URR, LM-21, TS-173-UR, TS-175/U, TS-34A/AP, BC-639A, TS-587B/U, URT-7, TS-403/U, TS-418/U, GRC-19, TS-148/UP, TS-172A/AP, W3IHD, 7218 Roanne Drive, Washington, D. C. 20021.

WANTED: tubes, transistors, equipment, what have you? Bernard Goldstein, W2MNP, Box 257, Canal Station, New York, N. Y. 10013.

DXER'S: CAN'T HACK IT? Need a bigger Hacker? Custom amplifiers built around the big tube of your choice. Wheelless and Burdette, Georgia Tech Box 33057, Atlanta, Georgia 30332.

MOTOROLA P33-BAC 5W Handi-Talkie, excellent condition with antenna, mike, Ni-Cads, .34/.94 and .94/.94 — \$95; Heath HX-20, HR-20, and HP-20, good condition — \$195; FOB W5PNY, 2506-A 35th St., Los Alamos, N. M. 87544.

WORLD QSL — See ad page 106.

QSLs. Second to none. Same day service. Samples 25¢. Ray, K7HLR, Box 331, Clearfield, Utah 84015.

TELL YOUR FRIENDS about Ham Radio Magazine.

FREQUENCY SYNTHESIZERS

IMMEDIATE "OFF THE SHELF" DELIVERY

**YOU'LL NEVER
HAVE TO BUY
CRYSTALS
AGAIN**



MODEL: ST-140

Price: \$129.95 ppd.

Tested, guaranteed and complete with mobile mounting bracket, tilt stand and transmitter matching kit.

Note: NY state residents add sales tax.

CHECK THE ADVANTAGES OF A VANGUARD SYNTHESIZER OVER OTHER BRANDS.

- No microphonics. Can be used mobile over bumpy roads.
- Reference frequency and spurious output down 70 dB. (excluding harmonics of output frequency which are used in the transmitter anyway.)
- All output frequencies are generated directly from the VCO without the use of multipliers and are therefore free of sub-harmonics.
- Now available with outputs in the 6, 8, 12 and 18 MHz. bands (corresponding to 144 MHz. dial reading) for direct substitution of transmitting crystals. More output frequencies are being made available. Call us if you don't see what you need.
- Entire frequency appears in-line in clear digits. No guesswork or mental additions. Thumbwheel switches provide fast, accurate selection of 1000 channels in 10 KHz. steps from 140.00 to 149.99 MHz.
- 50 ohm output and impedance transformer kit allows use at any distance from transmitter.
- Maintains an accuracy of .0005% (5 parts per million) over the entire range of -10° to +60° C. with a precision temperature compensated crystal that requires no oven. Operates at 5 MHz. for easy checking with WWV and includes a zero trimmer for correcting long term aging drift.
- Fast response time of only 3 milliseconds for a 10 KHz. step change in frequency and a remote control, gated output amplifier for push-to-talk operation.
- No hunting or false locks as with some other synthesizers.
- Operates from 10 to 15 VDC. 3 precision regulators eliminate input voltage fluctuations. Can also be used on 110 volts AC with a small 12 volt 1/2 amp power supply.
- Smallest size of any commercial synthesizer. Only 1 3/8" high, 3 3/8" wide, 8" long.
- All IC's are mounted in high quality insulated sockets and all parts are marked.
- Manufactured by VANGUARD LABS renowned for quality since 1952.

NOTE: Our 45 MHz. receive synthesizers may be ready by the time you read this. Call us for details.

IMPORTANT: When ordering be sure to state the output frequency you want.

VANGUARD LABS

Call 212 468-2720 for fast C.O.D. shipment.
For mail orders with personal checks allow 3 weeks.
196-23 JAMAICA AVE. HOLLIS, N. Y. 11423



KM-420 CW MESSAGE MEMORY Write for Brochures
100 OR 200 CHARACTERS \$299.95
EK-420 C-MOS DELUXE KEYS FOR QRP OR KW \$139.95

GURMS ELECTRO DEVICES TEL: (415) 964-3138 NEW FOR 1973
INC., BOX 4090, MOUNTAIN VIEW, CA. 94040

THE ULTIMATE MORSE KEYBOARD

- 64 character buffer
- Standard typewriter format with space
- Compatible with KM-420 memory

Available 1 November Model #KB-4200
Write for specifications \$499.95

GURMS ELECTRO DEVICES BOX 4090 • MOUNTAIN VIEW, CALIF. 94040 • TEL. (415) 964-3138

WANTS TO BUY

All types of military electronics equipment and parts. Call collect for cash offer.

SPACE ELECTRONICS division of MILITARY ELECTRONICS CORP.

76 Brookside Drive, Upper Saddle River
New Jersey 07458 • (201) 327-7640

DUAL BAND ANTENNAS

These ready to mount antennas consist of full 1/2 wavelength elements of No. 12 copperweld wire and can be used as either dipoles or inverted vees. No traps, coils, gimmicks, etc. are used to shorten the elements. 2KW rating. Single coax feedline required. Individually mounted dipoles with common center insulator: 80/40, \$21.95; 40/20, \$16.25; 20/15, \$14.10. Other combinations available. Send for free catalog listing dual band, monoband, and folded dipole antennas. Baluns available. Postpaid continental U. S. A.

HOUSE OF DIPOLES

P. O. BOX 8484
ORLANDO, FLORIDA 32806

AK-1 BOARD ONLY	\$ 3.25
AK-1 KIT OF ELECTRONIC PARTS	20.00
ST-5 BOARDS ONLY	5.25
ST-5 KIT OF ELECTRONIC PARTS	47.50
ST-5A BOARDS ONLY	5.25
ST-5A KIT OF ELECTRONIC PARTS	54.00
ST-6 BOARDS ONLY (These are the 8 original by W6FFC)	\$ 18.00
ST-6 KIT OF ELECTRONIC PARTS	\$128.50
MOD. KIT FOR UPDATING THE ST-5 TO THE ST5A	\$ 9.00
PEMCO 250 EIGHT DIGIT COUNTER WITH BUILT-IN PRE-SCALER AND POWER SUPPLY SEMI KIT	\$165.00
PEMCO MODEL 50A FREQUENCY COUNTER SEMI-KIT	\$125.00

These are fully assembled and tested boards only you add your own cabinet, etc. Write for details.

You must supply the cabinet, A.C. cord, meter, switches, etc. on all kits except where noted otherwise. (All prices are postage paid (we pay shipping).)

We will do most any printed circuit board for individuals or prototypes. If required we will also do the layout of the boards. All our boards are G-10 glass-epoxy solder plated and come drilled only. At present time we can do only single sided. All component parts used in our kits are new manufacturers stock. We Do Not Use Any Used or Surplus Parts. All inquiries are answered promptly.

PEMCO ELECTRONICS MANUFACTURING
422 18th St., N.E., Salem, Ore. 97301, (503) 585-1641

"DON AND BOB" NEW GUARANTEED BUYS. Discount prices plus full warranty. Write for low prices: Hy-Gain TH6DX, TH3MK3, 2048A, DB1015A, 402BA; Mosley CL33, CL36, S402; TriEx MW50, MW65, W51 (FOBCAL); Midland 13500 219.95; 13520 WT 209.95; Regency HR2B; SBE144 199.95; Standard 826MA, 146A; CDE Ham-M 99.00; TR44 59.95; AR22R 31.55; Belden 8448 rotor cable 10¢/ft; Belden 8214 RG8 foam 17¢/ft; 8237 RG8/U 15¢/ft; Amphenol PL259 49¢ Hallicrafters FPM300, new demos, factory warranty repair needed 460.00 ea; Rohn 25G, 45G tower, accessories stock; used guaranteed; Collins 75A4 345.00; Kenwood RS99 300.00; T599 350.00; Write demo prices; Heath SB300, filters 250.00; write quote Swan, Eimac, Drake; Motorola HEP170 epoxy diode 2.5A/1000 PIV 29¢, 25.00/100 lot; hardbound technical magazines from Petrochemical library 3.00/yr write; 1972 Radio Masters 3.50; Motorola Semiconductor data series 7.50; .001MFD/10KV doorknob 1.95; Calrad dualmeter SWR-relative power meter, to 150 MHz 15.95; #15 antenna wire 1.95/¢; write quote items not listed. Shipping charges collect. Madison Electronics, 1508 McKinney, Houston, Texas 77002. 713/224-2668, Nite/weekend 713/497-5683.

WESTERN UNION DESK-FAX TELEFAX Transceiver Manual: Complete theory of operation, adjustment, lubrication, preventive maintenance, troubleshooting, parts list. Includes all schematics and mechanical parts drawings. \$3.80 postpaid. Bill Johnston, 1808 Pomona Drive, Las Cruces, New Mexico 88001.

TONE-LOGIC Educational Systems for WWV, SSTV, RTTY. Eight 2 1/2" x 3" PCB's, plans, \$3. Hornung, Box 24614, San Jose, CA. 95154.

FOR YOUR FUTURE ROBYN RADIOS send your order to, Two Way Radio Sales, 1501 Monroe Street, Bogalusa, La. 70427 or 202 Farrell Street, Picayune, Miss. 39466.

TV-FM ANTENNA, New rollable (with perfect color band-width). Just unroll and stick on wall. Uses no masts, no rabbit ears, no dangerous plugging to AC lines, and No Signal Splitters since the VHF-UHF-FM terminals are available and usable At the Same Time. (New 1971 slotted design with U. S. Patent S/N 3577196). Made of decorative plastic yet rugged for use in yatch or RV. The antenna size is 18" x 48" unrolled. Can work behind picture or in front of reflector (bidirectional). Price is only \$10 for model with the following gains (VHF 6 dB), (FM-6 dB), (UHF-12 dB). Order Postpaid from Antenna Design Co., Subcontract Division; 11621 Hughes Ave., NE, Albuquerque, N. M. 87112.

IN AN EFFORT to encourage people to get their Amateur Extra Class License and to reward those who have gone to the trouble to get their license, we have decided to give, free, without any additional charge, an exact photostatic miniature wallet of a ham's Amateur Extra to those sending us an original and a self-addressed stamped envelope for the return of the original and the miniature duplicate photostat. Upon receipt of the original, the duplicate will be made and returned along with the unharmed original within about a week. The only thing asked is the inclusion of a self-addressed stamped envelope. This offer is open to Amateur Extras only and the license should be sent to: Duplicate — Amateur Extra, 1701 W. Devon — Box 60045, Chicago, Ill. 60660.

MOBILE IGNITION SHIELDING provides more range with no noise. Available most engines in assembled or kit forms, plus many other suppression accessories. Free literature. Estes Engineering, 543-H West 184th, Gardena, California 90248.

FAX FAX FAX. Paper for weather map recorders, \$2.95/box, 4 for \$10 (50 pounds). Paper for Desk-fax recorders, \$2.50/box, 6 for \$12 (50 pounds). Free list. Jim Cooper, W2BVE, POB 73, Paramus, N. J. 07652.

SELL: Packard Bell TV Camera Model 920, \$150; Picture/Sound Modulator Model MPS-15/16, \$50; together \$175. Quantum Physics Inc., Laser 3Mw, 6283 A with power supply \$125. K6LZM, (213) 342-4376.

ZENERS

All Units Tested And Guaranteed


400 MILLIWATT UNITS — 3, 3.3, 3.6, 3.9, 4.3, 4.7, 5.6, 6.2, 6.8, 7.5, 8.2, 9.1, 18, 22, 24, 27, Volts.
1 WATT UNITS — 10, 11, 12, 13, 15, 16, 18, 20, 22, 27, 30, 33, 39, 43, 47, 51, 56, 62, 68, 75, 82, 91, 100, 110, 120, 130, 150, 160, 180, Volts. ALL UNITS 10% — 4 for \$1.00 ppd. 5% — 3 for \$1.00 ppd.

NEW

JUST ARRIVED — Transformer, 115 VAC primary, 18 volt, 5 amp ccs or 7 amp intermittent duty secondary \$6.00 ea. ppd.

Power Transformer. 115 Volt AC Primary. Secondary #1: 32-0-32 Volt @ 1 Amp. Secondary #2: 6.3 Volts. Low Current For Pilot Lights. Size 2 1/2" x 2 1/2" x 3". Price: \$2.50 Each ppd.

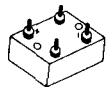400 Volt PIV at 25 Amp. Bridge Rectifier.
 \$4.00 ea. or 3 for \$10.00 ppd.



6.3 Volt 1 Amp Transformer. Fully Shielded \$1.60 Each ppd.

Toroids-Unpotted-Centertapped. Your choice — 88 mhy or 44 mhy 5 for \$2.00 ppd. or 15 for \$5.00 ppd.

Transformer — American Made fully shielded. 115 Volt Primary Secondary #1 18-0-18 Volts @ 4 Amps Secondary #2 5 Volts @ 2 Amps A very useful unit for LV Power supply use. Price — A low \$4.75 ppd.

General Purpose Germanium Diodes. Similar to 1N34s etc. 16 for \$1.00 ppd. All Cathode banded. 100 for \$5.00 ppd. Full leads. 1000 for \$40.00 ppd.

NEW

Transformer — American Made — Fully shielded. 115 V Primary. Sec. — 24-0-24 @ 1 amp with tap at 6.3 volt for pilot light. Price — A low \$2.90 each ppd.

Transformer, 115 VAC Primary, 12 Volt, 4 Amp Secondary \$4.00 Each ppd.

115 VOLT TRANSFORMER 17-0-17 Volt @ 150 ma. Secondary With Tap At 6.3 Volts for Pilot Light. \$1.50 Each ppd.

NEW NEW

TRANSFORMER. 115 volt primary, 12 volt 1/2 amp secondary. \$1.50 ppd.



Featherweight TO-5 Heat Sinks 2 for 25¢ ppd.

Major Brand 2N766 Transistors. 3 for \$1.00 ppd.



Miniature Terminal Strips. 1" Long x 1/2" High. 3 Term. plus Ground 20 for \$1.00 ppd.

SEND STAMP FOR BARGAIN LIST Pa. residents add 6% State sales tax ALL ITEMS PPD. USA

m. weinschenker
 K3DPJ BOX 353 · IRWIN, PA. 15642

COMPUTER KEYBOARD \$7.00 (as is)



Several styles on hand in poor condition, broken key/keys, broken case or no case, etc. Still a good value at \$7.00 for parts, switches, and each has encoder board in base.

2N2152	45 volt	170 watt	PNP-G	\$1.00
*2N3713	80	150	NPN-S	1.00
*2N3773	160	150	NPN-S	.75
*2N3789	60	150	PNP-S	.75
*2N5301	40	200	NPN-S	1.25
*2N5301	40	200	NPN-S	1.00

*Removed from used equipment

TRANSFORMERS

BRAND NEW, 115 volt AC input. OP - AMP XFMR, out puts: 16 VCT 1/2 amp, 17 VCT 1/2 amp. \$3.50

FILAMENT or BTRY CHARGER XFMR
output of 18 volts at 4.5 amp \$3.50

Postage Extra on all Items

JOHN MESHNA JR. ELECTRONICS

313,344 CORE MEMORY \$125.00

From SPECTRA computer, visually OK. 64 x 68 x 4 x 18 core stack. Figures out to 35K Byte.

LED 7 SEGMENT READOUT



Similar to MAN-1. Factory seconds but functionally OK. Fit 14 pin DIP socket.

7 segment w/left decimal	\$3.00
#LED-A-L	
7 segment w/right decimal	3.25
#LED-A-R	
7 segment no decimal	2.75
#LED-A	

Above LEDs—7 for the price of 5
Socket for above, gold plated leads 3/1.00

IC SALE YOUR CHOICE 3 for \$1.00

μI 900 BUFFER TO-5	
μI 914 DUAL 2 INPUT GATE TO-5	
μI 923 JK FLIP FLOP TO-5	
μI 926 Hi speed JK FLIP FLOP TO-5	
μI 931 JK/RS FLIP FLOP (DIP)	
10 pin socket for TO-5 IC	3/1.00

GIANT NIXIE B7971

Used \$1.00 Brand New \$2.00
With schematic for GIANT clock.


COMPUTER TAPE DECK \$75.00

Takes 1/2 inch tape, made by Computer Entry Systems. Visually ok, with electronics, no data available.

LASER DIODES, new listing just arrived, send SAE.

P. O. Box 62 E. Lynn, Mass. 01904

CW FILTER

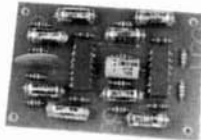

New Model CWF-2B—\$19.95.
Ready to use Please include
\$1.00 postage.

Model CWF-2—\$12.95, Kit.
\$14.95 Wired, tested, guaranteed.
Please include 55c postage.

- Get Razor Sharp selectivity from any receiver or transceiver.
- Extremely high skirt rejection.
- Drastically reduces all background noise.
- No audible ringing.
- No impedance matching.
- Ultra modern active filter design uses IC's for super high performance.

We have what we think is the finest CW filter available anywhere. The 80 Hz selectivity with its steep sided skirts will allow you to pick out one signal and eliminate all other QRM and QRN. Simply plug it into the phone jack or connect it to the speaker terminals of any receiver or transceiver and use headphones, small speaker, or speaker amplifier. Better yet, connect it between any audio stages to take advantage of the built in receiver audio amplifier.

Build the 2"x3" CWF-2 PC card into your receiver or get the self contained and ready to use CWF-2B and plug in!

SPECIFICATIONS

BANDWIDTH: 80 Hz, 110 Hz, 180 Hz (Switch selectable)
SKIRT REJECTION: At least 60 db down 1 octave from center frequency for 80 Hz bandwidth
CENTER FREQUENCY: 750 Hz
INSERTION LOSS: None. Typical gain 1.2 at 180 Hz BW, 1.5 at 110 Hz BW, 2.4 at 80 Hz BW
INDIVIDUAL STAGE Q: 4 (minimizes ringing)
IMPEDANCE LEVELS: No impedance matching required
POWER REQUIRED: CWF-2 6 volts (2 ma.) to 30 volts (8 ma.), CWF-2B standard 9 volt transistor radio battery
DIMENSIONS: CWF-2 2"x3" PC board, CWF-2B 4"x3 1/4"x2 3/16" (black winkle steel top, white aluminum bottom, rubber feet)

TRY this fantastic CW filter. If you don't think it is the best you have ever used, ask for your money back. We will cheerfully refund it. These filters carry a full one year warranty.

Write for FREE brochures and magazine test reports. Other IC active filters available. CW mist filter (110"x2"), low pass, high pass, and wide bandpass filters. Audio amplifiers: 1/2, 1, 2 watts. Crystal calibrator.

MFJ ENTERPRISES

P. O. Box 494-A, Mississippi State, MS 39762

NO ETCH CIRCUIT BOARDS FROM FULL SCALE TEMPLATES

Hardened chrome alloy steel, with #60 drill

ISOLATED - PAD - DRILL - MILL

Simple - Fast - Accurate - Safe

Sizes: 0.20", 0.15", 0.10" Dia. with

replaceable #60 drill \$6.95 ea.

A F STAHLER Co PO BOX 354

CUPERTINO, CALIF. 95014

Calif. Residents add 6%

LEARN RADIO CODE



\$9.95

Album contains three 12" LP's 2 1/2 hr. Instruction

THE EASY WAY!

- No Books To Read
- No Visual Gimmicks To Distract You
- Just Listen And Learn

Based on modern psychological techniques—This course will take you beyond 13 w.p.m. in LESS THAN HALF THE TIME! Available on magnetic tape LP's \$9.95 - Cassette, \$10.95

EPSILON [E] RECORDS

508 East Washington St., Arcola, Illinois 61910

ALMOST GONE

W6SAI's

RADIO HANDBOOK - 18th Edition

\$7.95 While They Last

COMTEC, Greenville, NH 03048

EMBROIDERED EMBLEMS AND PATCHES. Custom made from your design. 10 to 1000's. Write Russell, 1109 Turner St., Augusta, Maine 04210.

MANUALS for most ham gear made 45/65, some earlier. Send SASE for specific quote. Hobby Industry, W0JJK, Box H-864, Council Bluffs, Iowa 51501.

WANT OLD RADIO SHOW TRANSCRIPTION discs. Any size or speed. Send details to, Larry Kiner, W7FIZ, 7554 132nd Ave. N.E., Kirkland, Wa. 98033.

TUCSON HAMFEST, 28 October, 144 West Lester, Tucson, Arizona. Inside flea market, prizes. Tucson Repeater Association, Old Pueblo Radio Club, Box 6497, Tucson, AZ. 85733.

WANTED: Precision Selectivity Model Motorola Recvrs. PB116C or PB116D. Must be in good working condition, converted or non-converted. WBBNLM, 146 Schonhardt, Tiffin, O. 44883.

QRP TRANSMATCH, Vari Q filter, FM crystal logic oscillator kits, Write Peter Meacham Associates, 19 Loretta Road, Waltham, Mass. 02154.

SELL — Meteor SB175 xmtr \$40.; HM10A tunnel dipper \$20; 19" Emerson portable TV (needs work) new picture tube, \$8; BC-221T Zenith frequency meter, \$40; RT-35 A/M radio sonde xcvr (675-725 MHz) \$3; HA-26 VFO (unused) less manual, \$20; Britannica Junior Encyclopedia (1965) \$40; Collins F250A85 6409 filter (new) make offer; R-394/U 152-172 MHz receiver with power supply and cabinet for mounting receiver, transmitter & transmitter power supply, \$15; 600 watt AC power supply for SB-175 (two power supplies in one) \$25; 4 - 6UF 400 VAC Sprague vitamin Q capacitors #GA-51425, \$2 each; 4 - antenna relay #423/AR, \$7.75 each; Western Electric power supply, less tubes #J86219A-3 L-2A 300 V 0.45A D.C. less tubes, \$20. Richard Mayer, 3131 Decatur Avenue, Bronx, N. Y. 10467.

"BRAND NEW": Clegg 66'er in original factory carton, \$145. Money order or certified check. J. A. LaTorre, P. O. Box 521, Lawrence, Mass. 01842.

TELETYPEWRITER parts, supplies, manuals, SASE list. Typetronics, Box 8873, Ft. Lauderdale, FL. 33310. W4NYF. Wanted: Northern Radio 107.

WANTED: Old QSL cards. Vandy Johnson W6CWX, 4960 5th Street, Fallbrook, Calif. 92028.

TELETYPEWRITERS — Kleinschmidt — portable, fixed, sets, punches, parts, reconditioned, reasonable. Mark/Space Systems, 3563 Conquista, Long Beach, Calif. 90808. 213-429-5821.

FOR SALE: Commercial Test Equipment. Send SASE for equipment list. Northern Communications & Equipment, Inc., P. O. Box 1000, Auke Bay, Alaska 99821.

DX'ers — New Logarithmic Speech Processor. Nominal 8 dB increase in average power. Less than 5% distortion @ 1kHz. L/C filter. Hi-Z Meter. \$49.95. Also, low noise dual gate MOSFET receiver preamplifier. Nominal 20 dB gain. 10-30 MHz. \$39.95. With cabinets. Dynacomm, 1183 Wall Road, Webster, N. Y. 14580.

MOBILE OPS — Completely shielded ignition system kits available for most U.S. cars 1965-72. Alternator, generator and regulator filters, feed-thru capacitors, copper braid in stock. Write Summit Enterprises, 36 Winchup Road, Summit, N.J. 07901.

WE BUY ELECTRON TUBES, diodes, transistors, integrated circuits, Semiconductors. Astral Electronics, 150 Miller Street, Elizabeth, New Jersey 07207, (201) 354-2420.

SELL: SB-400, SB-301 w/cw filter, HD-15 and mike. Complete set-up \$425.00. WA2DGN, Walt Helinski, 159 Fisher Road, Rochester, N. Y. 14624.

PRINTED CIRCUIT BOARDS, \$.25 per sq. inch +\$1.50 to make negative from your art work. Plating and drilling extra. A. Gomeringer, 2556 'A' St., Philadelphia, Pa. 19125.

A "TIMELY" XMAS GIFT or gift-wrap one for your own shack!

**WORLD
TIME-TELLER**

**GREAT FOR
DX SKEDS**



A turn of knob and 2-color drum dial shows time your QTH and corresponding local time in all zones — also GMT.

Illustration shows hand-crafted acrylic cabinet style. List is \$18.50

ECONOMY MODEL at \$12.50

is now available. Unfinished mahogany cabinet approximately 10" x 7" x 2" deep. Excellent for wall mount or desk top.

Both styles feature 2-color map panel, enamel on aluminum, 9" in length.

Add \$1 for mailing cost.

**U-J
Industries**

**6605 SHOAL CREEK BLVD.
AUSTIN, TEXAS 78757**

F.C.C. EXAM MANUAL

PASS FCC EXAMS! Memorize, study — "1973 Tests-Answers for FCC First and Second Class Radio-telephone licenses. Newly revised multiple-choice questions and diagrams cover all areas tested in FCC exams. — plus "Self-Study Ability Test." \$9.95 Postpaid.

Tests-Answers for
FCC First and
Second Class
Commercial
Licenses

COMMAND PRODUCTIONS P.O. BOX 26348-K
RADIO ENGINEERING DIVISION SAN FRANCISCO, CALIF. 94126

NEW - 440 MHz PREAMPS

\$54.95

POSTPAID

432PA-1



Two stage preamps use KMC Bipolar and Mosfet Transistors. 20db gain, 20 MHz bandwidth. These are high quality preamps suitable for the most demanding applications. AC models have die cast case, others have metal enclosure.

432PA 3.5db NF 12VDC \$29.95
432PA-1 3.5db NF 117VAC \$54.95
432PC 1.5 to 2.0db NF 12VDC \$69.95
432PC-1 1.5 to 2.0db NF 117VAC \$94.95

Write for our Santa Claus wish list of Preamps and Converters.

**JANEL
LABORATORIES** P. O. BOX 112
SUCCASUNNA, N. J. 07876
201-584-6521

FREE Catalog
OF THE WORLD'S FINEST
GOVERNMENT SURPLUS
ELECTRONIC EQUIPMENT
And BETTER Than Ever!



Name _____
Address _____
City _____ State _____ Zip _____

Mail Coupon for Your FREE Copy, Dept. HR

FAIR RADIO SALES
1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

THE MOST COMPLETE 2 METER REPEATER AVAILABLE

DYCOMM ECHO III

DYCOMM
ECHO III

FM REPEATER

- INCLUDES EVERYTHING NEEDED BUT THE ANTENNA AND DUPLEXER
- DESIGNED TO COMPLY WITH NEW FCC REQUIREMENTS
- ASK FOR FLYER SHEET

DYNAMIC COMMUNICATIONS, INC.

948 Ave. "E" P.O. Box 10116

Riviera Beach, Fla. 33404 (305) 844-1323

... SPECIAL SALE ...

TS-505 VTVM



Here is one of the most popular portable military type VTVM's available. With 7 AC & DC ranges to 2, 4, 10, 20, 40, 100, 200 and DC to 400, 1000. Has 7 Ohm ranges, AC response to 500 MHz. Works on 115 VAC/60Hz — All units checked — guaranteed satisfaction or money back. FOB Monroe —

\$49

— OTHER TEST EQUIPMENT —

Also in stock, wide range of used test equipment, military and commercial. Signal generators, oscilloscopes, voltmeters, frequency standards, counters and more. HP, Tektronix, Fluke, Measurements, Polarad, etc. All equipment shipped same guarantee as TS-505 VTVM above — money back (less shipping cost) if not satisfied. Send self-addressed, stamped envelope for current list.

GRAY Electronics
P. O. Box 941, Monroe, MI 48161
Specializing in used test equipment

PRINTED CIRCUIT BOARDS

Available for any amateur project appearing with artwork in any amateur periodical.

Write for complete details and prices

D. L. "Mac" McClaren, WBURX

Printed Circuit Service for the Amateur

19721 Maplewood Ave. Cleveland, Ohio 44135

216-267-3263

STAR-TRONICS

INDUSTRIAL AND GOVERNMENT ELECTRONIC SURPLUS

PARTS & PIECES FOR SCHOOLS, SHOPS, HAMS & HOBBYISTS

SEND FOR OUR LATEST ALL DIFFERENT
MONTHLY PICTURE CATALOG. NOW!

Box 17127, Portland, Ore. 97217

SPACE SAVER TOWERS & MASTS

CZ series towers, cranks up, installs without guy wires. New lacing design creates greater strength.

Mini and Magna rotating masts . . . high strength galvanized tubing, self supporting crank-up.

For complete details and prices please check your local dealer or write
Certified Welders L.A. City License #634

CRISTAO TOWER CO.

P. O. Box 115, Hanford, California 93230

USED MYLAR TAPES — 1800 foot. Ten for \$8.50 postpaid. Fremerman, 4041 Central, Kansas City, Mo. 64111.

CANADA'S MOST UNUSUAL Surplus and Parts Catalog. Jam packed with bargains and unusual items. Send \$1. ETCO-HR, Box 741, Montreal, Canada.

RTTY BAUDOT TO ASCII CONVERTER accepts loop signal at any RTTY speed and delivers corresponding 6 or 8 level parallel ASCII, all on one 4 x 6 inch circuit board. Write for information. Petit Logic Systems, Box 51, Oak Harbor, Wa. 98277.

VERY in-ter-est-ing! Next 6 big issues \$1. "The Ham Trader," Sycamore IL 60178

FIGHT TVI with the RSO Low Pass Filter. For brochure write: Taylor Communications Manufacturing Company, Box 126, Agincourt, Ontario, Canada. MIS 3B4

HOME BREWERS: Stamp brings list of high quality components. CPO Surplus, Box 189, Braintree, Mass. 02184.

MORSAVERTER READS HAND-SENT CW 10-80 W.P.M. without adjustment and translates messages into RTTY Baudot or 6-level ASCII including necessary CR, LF, LTRS, FIGS codes. See review in August QST. TMC-1 translates RTTY loop signal into perfect Morse and includes 64-letter buffer memory. Write for information. Petit Logic Systems, Box 51, Oak Harbor, Wa. 98277.

RESISTORS: Carbon composition brand new. All standard values stocked. 1/2W 10% 40/\$1.00; 1/4W 10% 30/\$1.00 — 10 resistors per value, please. Minimum order \$5.00. 15W RMS 1C Audio Amplifier — Panasonic. Frequency response 20Hz-100 kHz. 1/2% distortion. Price \$6.95 Postpaid. Pace Electronic Products, Box 161-H, Ontario Center, New York 14520.

RECIPROCATING DETECTOR, write Peter Meacham Associates, 19 Loretta Road, Waltham, Mass. 02154.

FOR SALE: Eico 720 xmtr, Hallicrafters S-119 rcvr, Lafayette HA-230 rcvr, EMI Video Camera, Regency range gain trancvr, Hallicrafters CB-3A, regncvr, (convert them to ten), HD-11 Q-Multiplier, Heath and Lafayette VFO's, all in mint condition. Any or all, make offer. Bill Taylor, 208 Union Street, Brooklyn, N. Y. 11231.

RTTY PICTURE PERF TAPES. Error-free chad tape, hundreds available. Stamp for catalog. Joe Dickens, 601 South Dodson, Urbana, IL. 61801.

QSL'S — BROWNIE W3CJ1 — 3111B Lehigh, Allentown, Pa. 18103. Samples 10¢. Cut catalogue 25¢.

THE WHEATON COMMUNITY RADIO AMATEURS (WCRA) will hold their 12th Annual Mid-Winter Swap and Shop on Sunday, February 10, at the DuPage County Fairgrounds, Wheaton. Hours 8 a.m. to 5 p.m. Tickets \$1.50 advance; \$2.00 at the door. Two buildings again this year and unlimited parking. Bring your own tables. Free coffee and donuts 9:00 to 9:30 a.m. For info and advance tickets contact L. O. Shaw, W9OKI, 433 S. Villa Ave., Villa Park, Ill. 60181. Advance ticket orders must be postmarked no later than February 3, 1974.

+X- CALCULATOR OWNERS! Compute square roots, trigonometric functions, logarithms, and more! Quickly, Accurately, Easily! Manual \$2.00. Users say: "Splendid work!" . . . "Useful and fun" . . . "Excellent!" Unconditional money-back guarantee — and FAST service! Send today: Mallmann Optics and Electronics, Dept. -D, 836 South 113, West Allis, Wisconsin 53214.

HIGH-PERFORMANCE H.F. SYNTHESIZER replaces VFO and delivers output 1-30 MHz continuous coverage with accuracy, stability, resolution, and calibration to one Hertz. Write for information. Petit Logic Systems, Box 51, Oak Harbor, Wa. 98277.

YOUR AD belongs here too. Commercial ads 25¢ per word. Non-commercial ads 10¢ per word. Commercial advertisers write for special discounts for standing ads not changed each month.

2 METER FM

only **STANDARD**
sells more STANDARDS

than Erickson...and here's why!

**SRC-146A
ERICKSON
SPECIAL**

WITH

- Charger
- "Stubby" antenna
- Leather case
- Ni-Cads
- 94/94, 34/94 and one channel of your choice

\$369 List

-50 Package Discount

**\$319 Prepaid — Cashiers
Check or M.O.**

**ERICKSON
COMMUNICATIONS**

3501 W. Jarvis
Skokie, Ill. 60076 (312) 275-1166



WANT TO MEET SOME OLD-TIMERS ?

NEW VINTAGE RADIO BOOK

Re-live the early days of wireless and radio. Over 1,000 pictures. 1887-1929.

RADIO COLLECTOR'S GUIDE

Over 50,000 useful facts. 1921-1932



ORDER NOW! Send check to
McMahon's Vintage Radio, Box 2045,
Palos Verdes Peninsula, Calif., 90274

Vintage Radio, hard cover \$6.95
Vintage Radio, handbook 4.95
Radio Collector's Guide 3.95

California residents add 6% State Sales Tax

Name _____

Street _____

City _____ State _____ Zip _____

THE IDEAL HOLIDAY GIFT !

QRM QRM QRM

WHY FIGHT QRM?

Win the battle against CW QRM with the new DE-101 using advanced integrated circuit design. Connect it between your receiver and high impedance earphones for a guaranteed superior CW reception. Operate your receiver the same way as before except now you discriminate against QRM. No adjustments, the DE-101 is factory tuned and complete with built in ac supply. One year warranty. 4" x 2 1/2" x 6" \$29.95 plus \$2.00 shipping.

QRM
QRM
QRM



ATTENTION EXPERIMENTERS

Raise your printed circuits and breadboards with inexpensive 1/4 inch long plain metal spacers for a #4 screw. 30 for \$1.00 postpaid.

Ala. residents add 5% sales tax.

DYNAMIC ELECTRONICS INC.

BOX 1131 DECATUR, AL. 35601

QRM QRM QRM

A 5

Amateur Television Magazine

Be seen as well as heard

SUBSCRIPTIONS ONLY
\$2.50 A YEAR

P.O. Box 6512, Phila., Penna. 19138



THE ULTRA-BAL 2000

NOW ----- An extremely rugged, weather-proof BALUNI!

- Full 2KW, 3-30 MHz., 1:1 or 1:4 ratios.
- Special Teflon insulation, May be used with tuned lines and tuners.
- With dipole insulator and hang-up hook.

ONLY \$ 8.95ppd. (state ratio)

At your dealer or order direct

K.E. Electronics Box 1279, Tustin Calif. 92680

WORLD QSL BUREAU

THE ONLY QSL BUREAU to handle all of your QSLs to anywhere; next door, the next state, the next country, the whole world. Just bundle them up (please arrange alphabetically) and send them to us with payment of 5¢ each.

5200 Panama Ave., Richmond, CA USA 94804

DIGITALLY-TUNED RECEIVERS:

R-389/URR: 15-1500 kHz, OK grtd, w/book	375.00
R390: 0.2-32 MHz, OK grtd, w/oper. book	495.00
R390A adds mech. filters, w/oper. book	595.00
AN/WRR-2: 2-32 MHz, OK grtd, w/book	750.00

CV-591A SSB Conv., 455 kHz, OK, w/book	137.50
Nems-Clarke #1670 FM rcvr 55-260 MHz w/book	195.00
OCT-3 TTY FSK deviat. meter/rcvr, new	49.50
WWVB 60 kHz rcvr/comparator OK, w/book	295.00
Mot. 3 MHz Osc., 5 parts in 10 to eleventh	199.50
AIL 30 MHz rcvr/amplif/atten. calibrator	99.50

HIGH-SENSITIVITY WIDE-BAND RECEIVER

COMMUNICATIONS • BUG DETECTION
SPECTRUM STUDIES

38-1000 MHz AN/ALR-5; Consists of brand new tuner/converter CV-253/ALR in original factory pack and an exc. used, checked OK & grtd main receiver R-444 modified for 120 v. 50/60 Hz. The tuner covers the range in 4 bands: each band has its own Type N Ant. input. Packed with each tuner is the factory inspector's checkout sheet. The one we opened showed SENSITIVITY: 1.1 uv at 38.4 MHz, 0.9 at 133 MHz, 5 at 538 MHz, 4 1/2 at 778 MHz, 7 at 1 GHz. The receiver is actually a 30 MHz IF ampl. with all that follows, including a diode meter for relative signal strengths: an atten. calibrated in 6 dB steps to -74 dB, followed by an

AVC position; Pan., Video & AF outputs; switch select pass of ±200kHz or ±2 MHz; and SELECT AM or FM! With Handbook & pwr. input plug, all only 375.00

30 MHz PANADAPTER OK grtd 295.00

Buyers, Engineers, advanced Technicians:

We have the best test-equipment & oscilloscope inventory in the country so ask for your needs . . . don't ask for an overall catalog . . . we also buy, so tell us what you have. Price it.

R. E. GOODHEART CO. INC.

Box 1220-HR, Beverly Hills, Calif. 90213

Phone: Area Code 213, Office 272-5707

SUPER CRYSTAL THE NEW DELUXE DIGITAL SYNTHESIZER!! FROM Rp



MFA-22 DUAL VERSION

Also Available MFA-2 SINGLE VERSION

- Transmit and Receive Operation: All units have both Simplex and Repeater Modes
- Accurate Frequency Control: .0005 % accuracy
- Stable Low Drift Outputs: 20 Hz per degree C typical
- Full 2 Meter Band Coverage: 144.00 to 147.99 MHz, in 10KC steps
- Fast Acting Circuit: 0.15 second typical setting time
- Low Impedance (50 ohm) Outputs: Allow long cable runs for mobiles
- Low Spurious Output Level: similar to crystal output

SEND FOR
FREE DETAILS

Rp Electronics

Prices MFA-2 \$210.00 BOX 1201H

MFA-22 \$275.00 CHAMPAIGN, ILL.

Shipping \$3.00 extra 61820


STUD 'TRIACS'



PRV 15 amp	5.25	25 amp	5.25
100	1.05	1.05	
200	1.25	1.45	
300	1.45	1.65	
400	1.85	2.05	
500	2.25	2.25	
600		2.65	

"AEROSPACE" BABCOCK & LEACH CRYSTAL CAN RELAYS

12 for \$3.50

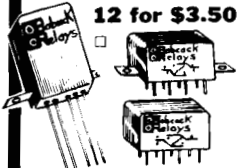

All hermetically sealed. Submini. 1/6" half, and full crystal can types in 6-12-24V in ast contacts up to 4PDT, 1 amp up 10 amps. Such types as BR40, 41, 10, 44, 16, 24, etc. Sorry, no churning voltages or types. From factory mixtures... to you! Good ass't, if you are space-minded, at low prices.

SILICON TUBES

5U4	\$1.49
5R4	3.95
666	7.95

'HAM' UHF 400 MC HIGH POWER TRANSISTORS

3 for \$10. **\$3.95**

By RCA or equal 2N3632. NPN, 23 watts, 3 amps, TO-60 case, with stud mtg. VCEV max 65.

GI "GLASS AMP II" SPACE AGE FEATURE

Type	PIV	Sale
1N4245	200	\$1.14
1N4246	400	.22
1N4247	800	.39
1N4248	800	.39
1N4249	1000	.59

Meets critical JAN specs. A glass "ball of silicon strength" that meets JAN specs, high reliability, withstands avalanche power surges to 1K watts. ONE amp ratings with 2 amp capabilities. Axial leads.



\$1.49 HIGH POWER TRANSISTOR 3 for \$3 WITH HEAT SINK

Removed from new equipment! Includes popular 2N174 "doorknob" transistor TO-36, germanium, PNP, 15 amps, 40 hfe. For ignition, high power transmitters, etc. Mounted on heat sink 5 x 2 1/2 x 1 1/2".



INTEGRATED CIRCUIT SOCKETS

14-Pin, DIP	\$.45
14-Pin, Wire Wrap	.59
14-Pin, Side Mount	1.00
16-Pin, DIP	.50
16-Pin, Wire Wrap	.59
TO-5, 8 or 10-Pins	.29

KRONOS WITH "TIME BASE"

NEW FOR 1974!

\$47. Any Type Clock less time-base

• with TIME BASE \$64.95



Cabinet is compact 6" x 5 1/2" x 6".

CHOOSE YOUR READOUT

Type	LED	Charac.	Sale
KR-101	MAN-3	.12	\$47.
KR-102	MAN-1	.27	47.
KR-103	MAN-2	.27	47.
KR-104	Nixie*	.45	47.
KR-105	707†	.33	47.
KR-106	704†	.33	47.
KR-107	SLA-1†	.33	47.
KR-108	Same as SLA-1 but GREEN, add \$12.		

† "MAN" LED readouts are "all LEDs" but the Litronix 707 and Opcoo SLA-1, like the MAN-1, are of the reflective bar segment technique, the 704 is the reflective bar version of the MAN-4. *The Nixie tube is a 7-segment device as others.

Scientific Devices introduces the new any LED Kronos digital clock. That's right, you can choose the "all-LED" Man-1, Man-3, and Man-4, and the new reflective bar types with the larger digits, at only one price, \$47. This is a Scientific Device first! We even have the GREEN LED readouts at a slightly extra cost. We have more... for \$19.95 we have available as well. (*) extra option to Naval Observatory your clock, or making it an all-purpose all-duty unit. For indoor and outdoor activity. This "TIME BASE" is the simplest on the market today with the help of one of the largest time base manufacturers for the famous digital wrist watches. Therefore, current drain is negligible, not like other cumbersome types. It's easy to construct, easy to slip into the Kronos of your choice and connect with easy instructions. Its overall design is simple and easy to construct. The kit is complete with famous black-and-white TEN-TEC cabinet, plus all accessories with booklets. Features include 3 setting controls, 1-hour per second, 1-minute per second, and hold button.

CRYSTAL TIME BASE \$19.95 FOR ANY KRONOS

Includes precision crystal, time-base IC, pc board & accessories with info. Scientific Device exclusive!

Largest Selection TTL IC's

Brand New	"DIP" Packages	Order by type number	Spec sheets on request "ONLY"
SN7400	\$0.30	SN7430	.30
SN7401	.30	SN7432	.30
SN7402	.30	SN7433	.30
SN7403	.30	SN7438	.60
SN7404	.35	SN7440	.30
SN7405	.32	SN7441	1.40
SN7406	.55	SN7442	1.40
SN7407	.55	SN7443	1.25
SN7408	.35	SN7444	1.50
SN7409	.35	SN7445	1.50
SN7410	.30	SN7446	1.65
SN7411	.35	SN7447	1.50
SN7412	.35	SN7448	1.50
SN7413	.55	SN7449	1.50
SN7414	.55	SN7450	.35
SN7415	.55	SN7451	.35
SN7416	.55	SN7452	.35
SN7417	.55	SN7453	.35
SN7418	.30	SN7454	.50
SN7419	.35	SN7455	.35
SN7420	.35	SN7456	.35
SN7421	.35	SN7457	.35
SN7422	.35	SN7458	.35
SN7423	.30	SN7459	.30
SN7424	.37	SN7460	.50
		SN7461	.50
		SN7462	.35
		SN7463	.50
		SN7464	.50
		SN7465	.50
		SN7466	.50
		SN7467	.50
		SN7468	.50
		SN7469	.50
		SN7470	.45
		SN7471	.35
		SN7472	.35
		SN7473	.52
		SN7474	.52
		SN7475	.95
		SN7476	.55
		SN7477	1.30
		SN7478	.95
		SN7479	.75
		SN7480	1.15
		SN7481	1.15
		SN7482	1.15
		SN7483	1.15
		SN7484	1.41
		SN7485	.55
		SN7486	4.25
		SN7487	1.50
		SN7488	1.50
		SN7489	1.30
		SN7490	1.30
		SN7491	1.30
		SN7492	1.30
		SN7493	1.30
		SN7494	1.30
		SN7495	1.30
		SN7496	1.30
		SN74104	.55
		SN74105	.55
		SN74106	1.25
		SN74107	1.25
		SN74108	1.25
		SN74109	1.25
		SN74110	1.25
		SN74111	1.25
		SN74112	.80
		SN74113	.85
		SN74114	1.25
		SN74115	1.25
		SN74116	1.25
		SN74117	2.10
		SN74118	2.10
		SN74119	2.10
		SN74120	2.10
		SN74121	1.20
		SN74122	1.20
		SN74123	1.20
		SN74124	1.20
		SN74125	1.20
		SN74126	1.20
		SN74127	1.20
		SN74128	1.20
		SN74129	1.20
		SN74130	1.20
		SN74131	1.20
		SN74132	1.20
		SN74133	1.20
		SN74134	1.20
		SN74135	1.20
		SN74136	1.20
		SN74137	1.20
		SN74138	1.20
		SN74139	1.20
		SN74140	1.20
		SN74141	1.20
		SN74142	1.20
		SN74143	1.20
		SN74144	1.20
		SN74145	1.20
		SN74146	1.20
		SN74147	1.20
		SN74148	1.20
		SN74149	1.20
		SN74150	1.20
		SN74151	1.20
		SN74152	1.20
		SN74153	1.20
		SN74154	1.20
		SN74155	1.20
		SN74156	1.20
		SN74157	1.20
		SN74158	1.20
		SN74159	1.20
		SN74160	1.20

• Factory Marked • Money Back Guarantee Buy 100 — Take 20%

LINEAR Op Amps

Buy Any 3 — Take 10% Off!

531	Hi slew rate op-amp (TO-5)	\$2.50
532	Micro power 741 (TO-5)	2.80
533	Micro power 709 (TO-5)	2.80
534	FET input op-amp (TO-5)	3.95
537	Precision 741 (TO-5)	2.50
550	Precision 723 voltage reg. (DIP)	1.17
556	5 Times faster than 741C	2.10
560	Phase lock loops (DIP)	3.25
561	Phase lock loops (DIP)	3.25
562	Phase lock loops (DIP)	3.25
565	Phase lock loops (A)	3.25
566	Function generator (A)	3.25
567	Tone generator (A)	3.25
595	Four quadrant multiplier	3.10
702C	Hi-grain, DC amp (TO-5)	.49
703C	RF-imp, amp, 14 ckts (TO-5)	1.00
704	TV sound if system	1.50
709C	Operational amp (A)	.49
709CV	Op amp (mini DIP)	.49
710C	Differential amp (A)	.49
711C	Dual diff. comp (A)	.49
723C	Voltage regulator (A)	.95
733	Diff. Video Amp	1.75
741C	Frequency compensator 709 (A)	1.25
747C	Dual 741C (mini DIP)	1.25
748C	Freq. adj. 741C (A)	.49
748CV	Freq. adj. 741C (mini DIP)	.49
753	Gain Block	1.75
709-709	Dual 709C (DIP)	1.00
739-739	Dual stereo preamp	1.00
741-741	Dual 741C (mini DIP)	1.00
75150	Dual peripheral driver	.88
75154	Dual peripheral driver	.88
745512	Dual line driver	.39
PA265	5-Watt voltage regulator	1.95
ULN2300M	Op amp with SCR	1.50
CA3085	Video Audio system	1.50

(A) TO-5 or DIP dual in line pak

POLY PAKS

15¢ CATALOG on Fiber Optics, IC's, Semi's Parts P.O. BOX 942H LYNNFIELD, MASS. 01940

NATIONAL 'OP' AMPS

BUY ANY 3 — TAKE 10%

Type	Description	Sale
LM-300	Super 723 V. reg.	\$1.49
LM-301	Hi-performance amp	.49
LM-302	Voltage follower	1.49
LM-304	Pos. V. reg.	2.25
LM-305	Pos. V. reg.	1.49
LM-307	Super 741	.59
LM-308	Hi-Q Fat Type Op Amp	1.50
LM-309H	SV 200 mill V. reg.	1.50
LM-309K	SV 200 mill V. reg.*	2.25
LM-311	Comparator	1.50
LM-320	Minus 5V 1-amp V.R.*	1.95
LM-320	Minus 12V 1-amp V.R.*	1.95
LM-320	Minus 15V 1-amp V.R.*	1.95
LM-350	Dual peripheral driver	.59
LM-370	AGC squelch op amp	1.49
LM-371	R-F, I-F, op amp	.69
LM-373	AM-FM, SSB, I.A.D.	3.75
LM-374	AM-FM, SSB, I.A.D.	3.75
LM-380	2-watt audio amplifier	1.95
LM-302B	Differential RV/IF amp	1.50
LM-3070	Chrome regenerator	1.50
LM-3071	TV chroma if amp	1.50

*TO-3 case, — others TO-5



1" SQ MINI METERS
• Plastic case
• Red needle indicators **\$1.49**
• Balancing, stereo, tape, amps. 3 for
• VU, side mtg, plus 3 minus 20 db. \$3.75
• VU, front mtg, plus 3 minus 20 db.

HIGH VOLT 1AMP
PIV SALE
2000* 1.00
3000 1.00
4000 1.65
5000 2.25
6000 2.95
8000 3.50
10000 3.95

Terms: add postage. Rated: net 30. Phone Orders: Wakefield, Mass. (617) 245-3829 Retail: 16-18 Del Corral, Wakefield, Mass. (off Water Street) C.O.D.'S MAY BE PHONED

NEW!!



"Cloverleaf."

SBE-450TRC TRANSCONVERTER

instant access to 450 from 144

Now . . . SBE opens up a new high speed route that leads to instant 450MHz operation from any 2 meter transceiver! Rev up—switch in the exclusive SBE, SB-450TRC "Cloverleaf"—arrive instantly on 450! Return at will!

Installation couldn't be more simple. Outwardly, "Cloverleaf" is a small black box that connects between your existing 144 MHz FM transceiver and its antenna, also to the microphone and car 12 volt battery. You plug the 450MHz antenna into another receptacle provided. SB-450TRC has no external tuning, no controls other than a switch that allows instant shift between the 144 and 450MHz ranges. No mods are necessary. **Your existing 144MHz transceiver remains intact.**

Transmitter-wise, SBE "Cloverleaf" is entirely **passive—draws no DC power yet delivers 40% of the RF drive at three times the frequency.** Example: 4 watts out on 450 MHz for 10 watts drive on 2 meters. This high efficiency frequency multiplication is accomplished by a power varactor diode in conjunction with multiple high Q tuned circuits. The 450MHz output is of course frequency modulated; overdrive, due to fre-

quency multiplication, being compensated by a fixed pad in the microphone circuit within the unit.

Receiver-wise, "Cloverleaf" has a front end with unity conversion gain that converts 450MHz band signals to I-F frequencies corresponding to 144MHz channels. Limiter, discriminator, output audio and loud speaker in the 2 meter transceiver continue to function in the usual manner.

Mobile wise, this all-solid-state transceiver is ideal—a compact box that can mount wherever space is available. "Cloverleaf" current drain is negligible.


Price-wise, this SBE high value/performance breakthrough represents worthwhile savings over the cost of a complete 450MHz transceiver with comparable characteristics. Truly, SBE has done it again!



LINEAR SYSTEMS, INC. 220 Airport Boulevard, Watsonville, Calif. 95076

The most popular three
band beam in the world!

hy-gain TH3Mk3

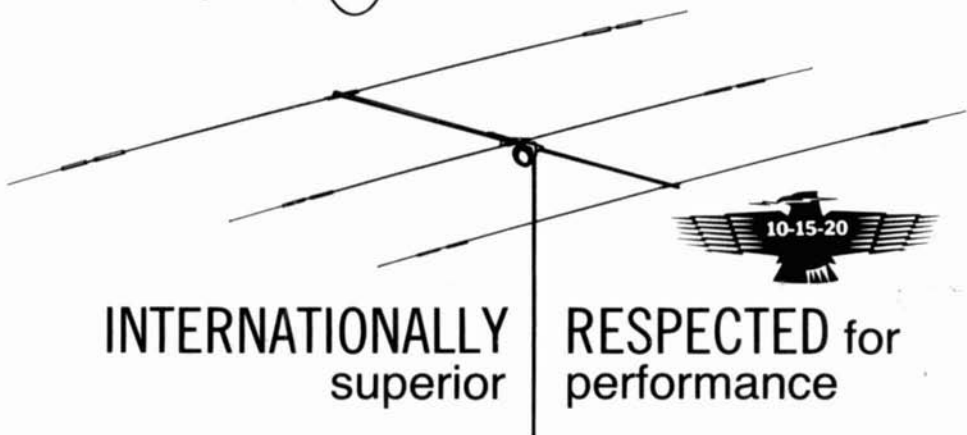

INTERNATIONALLY
superior

RESPECTED for
performance



Superior construction and performance make the difference in Hy-Gain's popular 3-element Thunderbird.

- Thunderbird's "Hy-Q" traps provide separate traps for each band. "Hy-Q" traps are electronically tuned at the factory to perform better at any frequency in the band—either phone or CW. And you can tune the antenna, using charts supplied in the manual, to substantially outperform any other antennas made.
- Thunderbird's superior construction includes a new, cast aluminum, tilt-head universal boom-to-mast bracket that accommodates masts from 1¼" to 2½". Allows easy tilting for installation, maintenance and tuning and provides mast feed-thru for beam stacking.
- Taper swaged, slotted tubing on all elements allows easy adjustment and re-adjustment. Taper swaged to permit larger diameter tubing where it counts! And less wind loading. Full circumference compression clamps are mechanically and electrically superior to self-tapping metal screws.
- Thunderbird's exclusive Beta Match achieves balanced input, optimum matching on all 3 bands and provides DC ground to eliminate precipitation static.
- Up to 8 db gain
- 25 db front to back ratio
- Power capability 1Kw AM, 2Kw PEP
- SWR less than 2:1
- Extra heavy gauge, machine formed, element to boom brackets with plastic sleeves used only for insulation. Bracket design allows full mechanical support.

Model 388 \$154.95

Other tri-band beams to choose from:

- | | |
|--------------------------------------|---------------------------|
| • 6-element Super Thunderbird TH6DXX | Model 389 \$189.95 |
| • 3-element Thunderbird Jr. TH3JR | Model 221 \$109.95 |
| • 2-element Thunderbird TH2Mk3 | Model 390 \$ 99.95 |

AVAILABLE FROM AMATEUR DEALERS THROUGHOUT THE WORLD

HY-GAIN ELECTRONICS CORPORATION

8601 Northeast Highway 6 Dept. BL Lincoln, Nebraska 68507
402/464-9151 Telex 48-6424

Advertisers check-off



... for literature, in a hurry —
we'll rush your name to the companies
whose names you "check-off"

- | | | |
|-------------------------------------|-------|-----------------------|
| —A-5 181 | INDEX | —KW 075 |
| —Adapters 170 | | —Larsen 078 |
| —Alarm 176 | | —Linear 081 |
| —Amtech 006 | | —Logic 133 |
| —Andy 007 | | —MFJ 082 |
| —Antenna Mart 009 | | —Metric 084 |
| —Ant. Specialists 010 | | —McClaren 155 |
| —Babylon 014 | | —Meshna 085 |
| —Barry 016 | | —Motorola 160 |
| —Bird 018 | | —New-Tronics 171 |
| —Carvill 135 | | —Non Linear 174 |
| —Center Tech. Dev. 178 | | —Nurmi 090 |
| —Command 029 | | —Oneida 144 |
| —Communications Specialists 030 | | —PM 091 |
| —Comm. World 031 | | —Pace 172 |
| —Comtec 151 | | —Pagel 092 |
| —Craig 177 | | —Palomar 093 |
| —Curtis 034 | | —Pemco 095 |
| —Data 037 | | —Poly Paks 096 |
| —Detroit 169 | | —Pro. Electronics 140 |
| —Dycomm 040 | | —RP 098 |
| —Dynamic Elect. 041 | | —Radiation 099 |
| —EMC 164 | | —Callbook 100 |
| —Ehrhorn 042 | | —Regency 102 |
| —Eimac 043 | | —Robot 103 |
| —Epsilon 046 | | —Sams 104 |
| —Erickson 047 | | —Savoy 105 |
| —Exceltrons 139 | | —Signal Systems 112 |
| —Fair 048 | | —Signetics 173 |
| —Gateway 052 | | —Solid State 106 |
| —Gen. Aviation 168 | | —Space-Military 107 |
| —Goldstein's 130 | | —Spectrum 108 |
| —Gray 055 | | —Sprague 175 |
| —Great American 132 | | —Stahler 142 |
| —H & L 056 | | —Star-Tronics 110 |
| —HAL 057 | | —Stotts Friedman 179 |
| —Ham Radio 150 | | —Swan 111 |
| —Heights 061 | | —Thomas 180 |
| —Henry 062 | | —Tobel 145 |
| —House Dipoles 036 | | —Tri-Tek 117 |
| —Hy-Gain 064 | | —Tristao 118 |
| —Icom 065 | | —UJ 119 |
| —International Crystal 066 | | —VHF Engineering 121 |
| —International Elect. Unlimited 141 | | —Vanguard 120 |
| —Jan 067 | | —Vintage 131 |
| —Janel 068 | | —Weinschenker 122 |
| —K. E. 072 | | —Wheatlands 156 |
| —KLM 073 | | —Wilson 123 |
| —KRP 074 | | —Wolf 124 |
| | | —World QSL 125 |
| | | —Y & C 126 |
| | | —Yaesu 127 |

Limit 15 inquiries per request.

November 1973

Please use before December 31, 1973

Tear off and mail to
HAM RADIO MAGAZINE — "check off"
Greenville, N. H. 03048

NAME.....
CALL.....
STREET.....
CITY.....
STATE.....ZIP.....

Advertisers Index

A-5	106
ATV Research	96
Alarm Components	80
Amtech	88
Andy Electronics	90
Antenna Mart	5
Antenna Specialists	86
Babylon Electronics	83, 112
Barry	92
Bird Electronic Corp.	88
Carvill International Corp.	71
Center for Technical Development, The	103
Command Production	82
Communications Specialists	67
Communications World, Inc.	56, 57, 86, 102
Comtec	72
Craig Radio	100
Curtis Electro Devices	61
Data Engineering	31, 104
Dycomm	106
Dynamic Electronics	74
EMC Associates	1
Ehrhorn Technological Operations, Inc.	105
Eimac, Div. of Varian Assoc.	Cover IV
Epsilon Records	102
Erickson Electronics	96
Exceltrons Research Labs	103
Fair Radio Sales	74
G & G Radio Supply Co.	80
Gateway Electronics	96
Goldstein's	106
Goodheart Co., Inc. R. E.	104
Gray Electronics	86
Great American Miniatures	84
H & L Associates	85
HAL Communications Corp.	94
Ham Radio	82
Heights Manufacturing Co.	Cover III
Henry Radio Stores	100
House of Dipoles	2, 81, 95, 109
Hy-Gain Electronics Corp.	39
Icom	87
International Crystal Mfg. Co. Inc.	70
International Electronics Unlimited	84
Jan Crystals	103
Janel Labs	106
K. E. Electronics	96
KLM Electronics	82
KRP Electronic Supermart, Inc.	45
KW Electronics	108
Larsen Electronics	90
Linear Systems, Inc.	102
Log's Newsletter	80
MFJ Enterprises	104
Metric	102
McClaren	104
Meshna, John, Jr.	102
Motorola	111
Nurmi Electronics Supply	73
Oneida Electronic Manufacturing Co., Inc.	75
PM Electronics	84
Pagel	96
Palomar Engineers	72
Pemco	100
Poly Paks	91, 107
Professional Electronics	80
RP Electronics	106
Radiation Devices	84
Radio Amateur Callbook	92
Regency Electronics, Inc.	97
Robot Research	25
Sams, Howard W. and Co., Inc.	53
Savoy Electronics	Cover II
Signal Systems	90
Solid State Systems, Inc.	98
Space-Military Electronics	100
Spectrum International	90
Stahler Co. A. F.	102
Star-Tronics	104
Stotts Friedman Co.	69
Swan Electronics	76, 77, 78, 79
Thomas Advertising Co.	92
Tobel Electronics	88
Tri-Tek, Inc.	88
Tristao Tower Co.	104
UJ Industries	103
VHF Engineering, Div. of Brownian Elect. Corp.	93
Vanguard Labs	100
Vintage Radio	105
Weinschenker, M.	101
Wheatlands Electronics	80
Wilson Electronics	94
Wolf, S.	84
World QSL Bureau	106
Y & C Electronics	82
Yaesu Musen USA	89

EXPERIMENTERS
STUDENTS
HOBBYISTS
TECHNICIANS
INVENTORS
ENGINEERS
RADIO/TV SERVICE DEALERS
TEACHERS
ELECTRONIC REPAIRMEN

WIN!

\$2,500.00

SCHOLARSHIPS or any of 8 other
Scholarship prizes totaling \$9000
(All fully transferrable)



"Design-In" Contest

Original
Electronic
Project

Open to Men—Women—Boys—Girls—Any Age
Two contest categories: Non-Professional and
Professional — with equal prizes for each

**CONTEST ENTRY BLANKS AVAILABLE ONLY
AT MOTOROLA HEP SUPPLIERS** Pick up your
"Design-In" Contest Entry Blank Today!

Contest closes December 31, 1973

BARRY

presents

CLEGG FM-27B



Total 146-148 MHz coverage without buying a crystal. 25w. out, fully synthesized.

\$479.95

Clegg FM-27B Regulated AC power supply **\$79.95**

BIRD 43 WATTMETER

\$100.00

Bird 43 Slugs specify frequency and power

HF **\$35.00 each**
VHF **\$32.00 each**

Also 4350 80-10M dual scale 200w/2kw HamMate — **\$79.00**

DRAKE

MS-4 Speaker \$ 22.00
AC-10 AC Supply for AA-10, TR-22, TR-72, 13.8 VDC @ 3 amps \$ 39.95
TR-22, in stock \$219.95
AA-10 Amplifier for TR-22 \$ 49.95
TR-72 2 meter FM transceiver, 23 channel, 1 & 10 watts, 13.8 VDC \$320.00
TR4/C new, \$599.95 T-4XC Trans. \$530.00
R4C Rec. \$499.95
AC-4 Drake A.C. Power Supply \$ 99.95

MARINE

Barry stocks and has fast availability Sonar, Pearce-Simpson, Andrea, SBE and Antenna Specialists VHF Transceivers, Antennas, Depth Finders and compasses by Andrea.

HALICRAFTERS

SR-150 Transceiver 10-80 meters AC or DC power supplies write
SR-160 Transceiver 80, 40, 20 meters write
PS-150-R DC power supply for SR-150 or SR-160 fpm. 109.50, sale unused, \$ 75.00
FPM-300 new, \$595.00

TEMPO

2 Meter Linear Amplifiers, 502, 5-12 watts input. 35-55 watts output \$105.00
802-B 1-2 1/2 w. input, 80-90 w. output \$195.00
CL-146 2 Meter, 15 watts \$299.00

SWR BRIDGE COUPLER, DC-800 MHz
TNC Connectors
(no indicator) full amateur power
\$90.00 Value
\$10.95

DX ENGINEERING SPEECH COMPRESSORS

DIRECT PLUG-IN FOR COLLINS 32S \$79.50 ppd. U.S.A.
DIRECT PLUG-IN FOR KWM 2
\$79.50 ppd. U.S.A.

Pay us a visit when you are in New York
Thousands of unadvertised specials.
Separate export department to expedite overseas orders.

TEN TEC

315 RECEIVER 10-80 meters SSB, AM, CW \$229.00
CW FILTER FOR 315 \$14.95
AC4 SWR Bridge KR2 \$ 12.95
\$ 14.95 KR40 \$ 89.95

E. F. JOHNSON

Matchbox complete with directional coupler and indicator, 10-80 meters.
2KW PEP, 1 KW AM — new, \$154.50
275 watts — new, \$ 94.95
151-1-4 Variable Capacitor, 250 pF, medium Xmitting type \$5.95 ea.

VIBROPLEX

Vibro Keyer Standard \$ 24.95
Deluxe \$ 32.95
Original Standard Vibroplex Bug \$ 29.95

INSTRUMENTS

Millen 90652 Solid State Dipper. New with 7 coils and carrying case. 1.6 - 300 MHz \$110.00
Pan Adapter BC-1031A ± 100 kc unused with spare parts & book useful with any short wave receiver \$ 55.00

SWAN

SS-200 Solid State SSB Transceiver with power supply & 16 pole filter Brand new, Write
Swan 350 with 117XC power supply \$300.00

DYCOMM

DYCOMM BRICK, 2w in 35w out \$ 79.95
DYCOMM BLOCK, 10 in 50w out \$ 99.95

ETO

ALPHA-77. The finest amplifier ever offered for amateur, commercial or military service. 3000 watts PEP continuous duty. Write

1 CX7A brand new, latest version, write or call



GE INDUSTRIAL SILICON RECTIFIER

1400 PIV

250 amp., GE #41A281049-11. Quantities in stock. \$90.00 value, brand new \$15.00

BARRY 512 Broadway NY, NY 10012
DEPT. H-11
212-WA-5-7000 **ELECTRONICS**

See Page 83 for MORE from Barry

it wasn't easy...but Kenwood improved the R-599 & T-599

THOUSANDS HAVE PROVEN THEMSELVES THROUGH DAILY USE. EVERYTHING THAT MADE THEM THE BEST REMAINS, BUT NOW KENWOOD DID THE IMPOSSIBLE BY MAKING THE "TWINS" EVEN BETTER. THE R-599A IS THE MOST COMPLETE RECEIVER EVER OFFERED... MANY FEATURES WHICH ARE "OPTIONAL AT EXTRA COST" IN OTHER RECEIVERS ARE STANDARD

the R-599A

Solid state... low power consumption, superbly reliable, small and lightweight • Full amateur band coverage... 10 through 160 • CW, LSB, USB, AM, AM.N, FM reception • Selectable AGC... slow or fast • Built-in calibrator • Monitor T-599A frequency to calibrate transmitter • Squelch circuit • 1 KHz frequency readout... smooth VFO action • Versatile cross channel operation with T-599A • Automatic or manual selectivity selection • Built-in SSB/8 pole, CW/8 pole and AM filters • RIT circuit with RIT tuning separate from RIT switch • Five built-in fixed frequency channel positions • Provisions for installation of 2 and 6 meter converters • Stable, accurate VFO • Built-in power supply for 115/230 VAC operation or 12 VDC operation • Built-in WWV reception • Built-in S-meter • Excellent sensitivity - .5 uv • Easily adaptable to use with Kenwood TS-900 • Modern, beautiful design

New Features:

New easy read dial, same 1 KHz readout... same smooth VFO action • Excellent built-in noise blanker • Improved 2 and 6 meter operation with optional accessory converters, easier installation • Continuous RF gain control replaces stepped attenuator • Built-in 11 meter coverage • AGC



The R-599A by Kenwood

turns off if desired • VFO indicator light for cross channel operation •

The R-599A... \$439.00 • Converters... \$31.00 • S-599 Speaker... \$18.00

the T-599A

Mostly solid state... only 3 tubes • Built-in power supply • Full metering: ALC, Ip, RF output, high voltage • CW, LSB, USB, AM operation • 1 KHz frequency readout, smooth easy VFO action • Built-in VOX, with delay, sensitivity and anti-VOX adjustments • Built-in semi-automatic CW with sidetone • Built-in calibrator function when used with the R-599A • Full amateur band coverage... 10 through 80 • Versatile cross channel operation with the R-599A • Stable, accurate VFO • Modern, beautiful design • ALC feedback • Maximum TVI protection • 200 watts PEP input nominal • Tube saving TUNE position • Built-in cooling fan • Selectable low or high microphone impedance

New Features:

Front panel MIC Gain control • Front panel CAR LEVEL control • Improved, easy read dial, same smooth VFO action • VFO indicator light for cross channel operation • New high reliability final amplifier layout • Improved keying characteristics • New chain drive •

The T-599A... \$459.00

Prices subject to change without notice.

Why buy from Henry Radio?

Over 40 years experience. No finance charges if paid within 90 days. Low interest contracts - 8%/yr add on (14% annual rate) - as long as 24 months. 10% down or trade-in down payments. Good used equipment. Most makes and models. Used equipment carries a 15 day trial, 90 day warranty and may be traded back within 90 days for full credit towards the purchase of NEW equipment. Write for bulletin. Export inquiries invited.

Henry Radio

11240 W. Olympic Blvd., Los Angeles, Calif. 90064
213/477-6701
931 N. Euclid, Anaheim, Calif. 92801 714/772-9200
Butler, Missouri 64730 816/679-3127

EIMAC's rugged 8877 powers Henry Radio's reliable 4K Ultra linear commercial amplifier.

When Henry Radio set out to design a sophisticated linear amplifier for high reliability communications in the high frequency range, they chose EIMAC's high-mu 8877 power triode.

The result is the new 4K Ultra, which operates with 4000 watts input in heavy-duty commercial service. The 4K employs continuous variable capacitive and inductive elements tunable over the 3.0 to 30 MHz range. Optimum input and load conditions are provided for a wide variation in antenna systems. EIMAC's 8877 enables the 4K to deliver over 2500 watts of continuous SSB or CW output with only 50 to 75 watts of drive. For RTTY the 4K will provide about 2000 watts of continuous duty output.

The 8877 is a ceramic-metal triode that delivers a lot of power and linearity in a package only three and one-half inches high. At 30 MHz, typical power gain is 15 dB. This impressive gain is achieved with 3rd order intermodulation products -38 dB below one tone of a two equal-tone drive signal.

With Henry Radio, you know quality counts. And they know you can't do better than EIMAC. For full specifications on the 8877, write to EIMAC Division of Varian, 301 Industrial Way, San Carlos, California 94070. Or contact one of the more than 30 Varian/EIMAC Electron Tube and Device Group Sales Offices throughout the world.




EIMAC
division
varian