

85 cents

*hr*


focus  
on  
communications  
technology ...

# *ham* **radio**

*magazine*

JANUARY 1974

## **cw memory** for RTTY identification

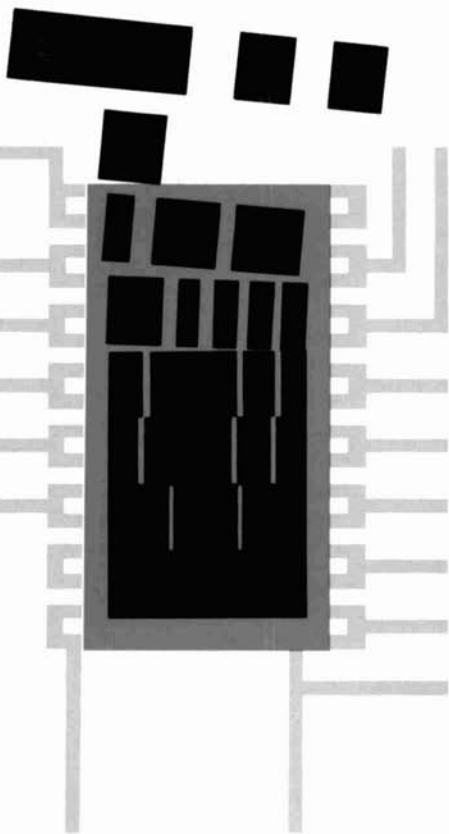

### *this month*

- linear amplifier 14
- IC logic families 26
- fm transceiver 36
- heatsink design 46

# Savoy

## BASSETT

High efficiency mobile and portable antennas for all amateur bands, CAP, MARS, CB, SECURITY, PUBLIC SERVICE, MARINE, AND GOVERNMENT USE.

- 2-6-10-15-20-40-75
- Identical size, cost, and appearance
- FULLY ADJUSTABLE TO FREQUENCY IN FIELD
- Low weight, low drag, high strength fiberglass
- Polished chrome brass standard 3/8-24 thread
- High gain collinear on 2 meters

MODEL DGA-2M  
\$29.50 postpaid  
in U.S.A.



**\$3.75**

Postpaid in U.S.A.

TYPE 900 A

TYPE 901



## HIGH ACCURACY CRYSTALS FOR OVER 30 YEARS

Either type for amateur VHF in Regency, Swan, Standard, Drake, Vari-tronics, Tempo, Yaesu, Galaxy, Trio, Sonar, Clegg, SBE, Genave.

Quotes on request for amateur or commercial crystals for use in all other equipments.

Specify crystal type, frequency, make of equipment and whether transmit or receive when ordering.



**BASSETT VACUUM TRAP ANTENNA SYSTEM**  
Complete packaged multi-band antenna systems employing the famous Bassett Sealed Resonators and Balun from which air has been removed and replaced with pure helium at one atmosphere. Operating bands are indicated by model designation.

MODEL DGA-4075 . . . .	\$59.50
MODEL DGA-204075 . . .	\$79.50
MODEL DGA-2040 . . . .	\$59.50
MODEL DGA-152040 . . .	\$79.50

## BASSETT VACUUM BALUN



The famous sealed helium filled Balun employed with the DGA Series Antenna Systems. Solderless center insulator easily handles more than full legal power while reducing unwanted coax radiation. Equipped with a special SO-239 type connector and available either 1:1 or 4:1.

MODEL DGA-2000-B . . . \$12.95  
Postpaid in U.S.A.

CONTACT YOUR DISTRIBUTOR OR WRITE FOR DATA

# Savoy Electronics, Inc.

P.O. Box 5727 - Fort Lauderdale, Florida - 33315

Tel: 305-566-1333 or 305-947-9925



# 2<sup>nd</sup> generation SLO-SCAN system

## Venus SLO-Scan TV monitor

**CAMERA ADAPTER**  
Mounting Bezel

**BRIGHTNESS**  
Automatic CRT Burn Protection

**CONTRAST**  
Independent Contrast Control

**SOURCE SELECT**  
Rec., Tape, Camera Off & Instant On

**PERSONALIZED IDENTIFICATION PLATE**  
Your call sign  
WB2AZT

**CABINET**  
Zinc Die Cast Front with Extruded Alum Sides  
10 3/4" W x 13" D x 5 1/2" Ht.

**OPTIMUM PICTURE**  
3 1/4" x 3 1/8" for POLAROID LAND reproduction

**TILT STAND**  
Collapsible Bail

**RE-SCAN**  
Retrace Vertical

**VIDEO/VOICE SELECT**

**Amat.Net \$349<sup>00</sup>**

Actual unretouched photo taken from the Venus SS2 using a Polaroid Color Pack II Camera mounted on the Venus P-1 Camera Adapter

**Video Information**    **Sync. Pulse**

**ACCU SYNC**  
Diagnostic and Tuning Aid

**CAMERA ADAPTER P-1** enables you to take photographs "right-off-the-TV" and accepts a Polaroid Color Pack II Polaroid Square Shooter.


Allows photographing in a lit room

Simple-snap mounting for quick and accurate picture taking

Simultaneous hood viewing of picture being taken by camera

Instant QSL via SSTV

Amat.Net \$34<sup>50</sup>

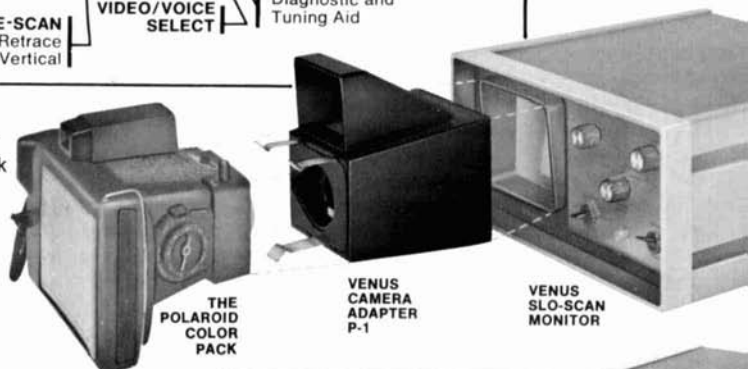

**CASSETTE ADAPTER**

Amat's Cassette F and T Series are continuous loop cassettes that allow you to pre-record and send SSTV information on a single frame cassette

Amat.Net \$37<sup>50</sup>

Grey Scale Generator

Amat.Net \$65<sup>00</sup>

Checkerboard

Amat.Net \$65<sup>00</sup>

**V1 VIEWING HOOD**

Uniquely designed for wide angle viewing by more than one operator.

Amat.Net \$14<sup>50</sup>

**Coming in December**

**CAMERA AND SCAN CONVERTER CC-1**

Projects your VIDEO real time on any conventional home TV while simultaneously scan converting to SSTV

- Full, half and quarter frame
- Positive, negative reversal
- RF output for viewing on conventional home TV set

ORDER DIRECT FROM FACTORY

# Venus Scientific Inc.

The company that put high voltage on the moon, now brings you expanding amateur radio technology.

399 Smith Street  
Farmingdale, N.Y. 11735  
Phone 516-293-4100  
TWX 510-224-6492



# There's a **DRAKE DEALER** near you...

Drake Dealers are dependable and friendly.  
For a good deal, see your nearby Drake Dealer:



## ALABAMA

**Birmingham** (35233)  
Ack Radio Supply  
3101 Fourth Avenue, S.  
James W. Clary Co.,  
1713 Second Avenue, S.

## ARIZONA

**Phoenix**  
Henshaw Electronics  
1644 E. McDowell (85006)  
**Tempe** (84281)  
Circuit Specialists  
1110 N. Scottsdale Road  
**ARKANSAS**  
**DeWitt** (72042)  
Moory Electronics Co.  
12th & Jefferson, Box 506  
**Wynne** (72396)  
Custom Builders Electronics  
513 Forrest Street

## CALIFORNIA

**Burbank** (91505)  
Electronic City, Inc.  
4001 W. Burbank Blvd.  
**Burlingame** (94010)  
Ham Radio Outlet  
999 Howard Avenue  
**Fresno** (93710)  
Al Roach's Dymonds  
46 E. Shaw  
**Los Angeles** (90064)  
Henry Radio  
11240 Olympic Blvd.  
**Oakland** (94609)  
M-Tron  
2811 Telegraph Avenue  
**Pasadena** (91106)  
Dow Sound City  
1759 E. Colorado Blvd.  
**Sacramento** (95825)  
Selectronics  
1912 Fulton Avenue  
**San Diego** (92101)  
Western Radio & TV Supply  
1415 India Street, Box 1728  
Gary Radio, Inc. (92111)  
8199 Clairemont Mesa Blvd.  
**San Jose** (95128)  
Quement Electronics  
1000 S. Bascom Avenue  
**Torrance** (90505)  
L. A. Electronix  
23044 Crenshaw Blvd.  
**COLORADO**  
**Denver**  
Burstein Applebee  
800 Lincoln (80203)  
CW Electronic Systems  
1401 Blake St. (80202)

## CONNECTICUT

**Hartford** (06114)  
Harry Electronics  
500 Ledyard Street

## DELAWARE

**Wilmington** (19801)  
Willard S. Wilson, Inc.  
403-405 Delaware Avenue

## D.C. (See Maryland & Virginia)

## FLORIDA

**Ellenton** (33532)  
Sig Electronics Company  
2412 Highway 301 North  
**Miami** (33137)  
Amateur Radio Center, Inc.  
2805 N.E. Second Avenue  
**Orlando** (32803)  
Amateur Electronic Supply  
621 Commonwealth

## GEORGIA

**Atlanta** (30309)  
Ack Radio Supply Co.  
554 Deering Road  
Specialty Distributing Co., Inc.  
763 Juniper St. N. E. (30308)

## HAWAII

**Honolulu**  
Honolulu Electronics  
819 Keeaumoku St. (96803)

## IDAHO

**Boise** (83702)  
Morton Electronics  
2113 North 26th Street

## ILLINOIS

**Lincoln** (62656)  
AAA Sales  
555 Woodlawn Road  
**Palos Heights** (60463)  
Green Mill Radio Supply  
12111 South 68 Court  
**Peoria**  
Klaus Radio & Electric Co.  
8400 N. Pioneer Pky (61614)  
**River Forest** (60305)  
Trigger Electronics  
1361 North Avenue

## INDIANA

**Angola** (46703)  
Lakeland Radio Supply  
525 S. West Street  
**Evansville** (47710)  
Castrop's Radio Supplies  
1014 W. Franklin Street  
**Indianapolis**  
Graham Electronic Supply  
133 S. Pennsylvania (46204)  
Van Sickle Radio Supply  
4131 N. Keystone Av. (46205)  
**South Bend** (46624)  
Radio Distributing Co.  
1212 High Street  
**Terre Haute** (47802)  
Hoosier Electronics  
Box 403, RR #25

## IOWA

**Council Bluffs** (51501)  
Hobby Industry  
1530 Avenue G.  
**Davenport** (52801)  
Klaus Radio & Electric Co.  
322 E. Fourth Street  
**Des Moines** (50310)  
Hunter Sales Inc.  
3621 Beaver Avenue

## KANSAS

**Kansas City** (66101)  
Henshaw Electronics  
1049 Minnesota Ave.  
**Overland Park** (66204)  
Associated Radio  
8012 Conner  
**Wichita** (67211)  
Amateur Radio Equipment  
1203 E. Douglas

## KENTUCKY

**Louisville** (40209)  
P & P Electronics  
719 Manning Road  
**Morehead** (40351)  
Ferguson Electronics  
137 E. First Street

## LOUISIANA

**New Orleans** (70130)  
Radio Parts, Inc.  
1331 Prytanias Street

## MAINE

**Lewiston** (04240)  
Down East Ham Shack  
57 Main Street

## MARYLAND

**Baltimore** (21211)  
Amateur Radio Center  
1117-19 W. 36th Street  
**Whitson** (20902)  
EISCO  
11305 Elkin Street

## MASSACHUSETTS

**Reading** (01867)  
Graham Radio Company  
505 Main Street

## MICHIGAN

**Ann Arbor** (48104)  
Purchase Radio & Supply  
327 E. Hoover  
**Detroit**  
Radio Supply & Engineering  
85 Selden Av. (48201)  
Reno Radio Co.  
1314 Broadway (48226)  
**Flint** (48507)  
Shand Electronics Inc.  
2401 S. Dort Highway  
**Grand Rapids** (49503)  
Radio Parts, Inc.  
542 Division Ave.  
**Marquette** (49855)  
Northwest Radio  
1010 West Washington  
**Muskegon** (49441)  
Electronic Distributors, Inc.  
1960 Peck Street

## MINNESOTA

**Duluth** (55802)  
Northwest Radio  
123 E. First Street  
**Minneapolis** (55401)  
Electronic Center, Inc.  
127-3rd Avenue N.

## MISSOURI

**Butler** (64730)  
Henry Radio  
211 North Main Street  
**Kansas City**  
Burstein Applebee Co.  
3199 Mercer Street (64111)  
Henshaw Electronics  
7622 Wornall (64114)  
**St. Louis** (63132)  
Ham Radio Center  
8342 Olive Blvd.

## MONTANA

**Great Falls** (59401)  
Electric City Radio Supply  
2315 - 10th Avenue S.

## NEW HAMPSHIRE

**Concord** (03301)  
Evans Radio Inc.  
Route 3A, Bow Jct.

## NEW JERSEY

**Camden** (08102)  
General Radio Supply Co.  
600 Penn St. at Bridge Plaza  
**Clifton** (07011)  
Wittie Electric Co., Inc.  
384 Lakeview Avenue  
**Eatonstown** (07724)  
Atkinson & Smith Inc.  
17 Lewis Street

## NEW MEXICO

**Albuquerque** (87108)  
Bowden Associates  
4318 Mesa Grande St., S.E.

## NEW YORK

**Amsterdam** (12010)  
Adirondack Radio Supply  
185-191 W. Main Street  
**Elmira** (14901)  
Chemung Electronics  
601 E. Church Street  
**Farmingdale** (11735)  
Arrow Electronics Inc.  
900 Broad Hollow Road  
Harrison Radio  
20 Smith Street  
**Lindenhurst** (11704)  
Delmar Electronics  
101 Eads Street

## NEW YORK

**Barry Electronics**  
512 Broadway (10012)  
**Grand Central Radio Inc.**  
124 E. 44th St. at  
Lexington Av. (10017)  
**Harvey Radio Co.**  
2 West 45th St. (10036)

## ROCHESTER (14614)

**Rochester Radio Supply**  
140 W. Main Street  
**Syosset** (11791)  
Lafayette Radio Corp.  
111 Jericho Turnpike  
**Williamsville** (14221)  
Hirsch Radio Company  
219 California Drive

## NORTH CAROLINA

**Ashville** (28801)  
Frack Radio Supply  
38 Baltimore Ave.

## DHIO

**Akron** (44327)  
Olson Electronics  
260 South Forge St.

## CINCINNATI

**Queen City Electronics**  
1563 McKim Av. (45231)  
United Radio Inc.  
Summit & Reinhold Dr. (45237)

## CLEVELAND (44112)

**Amateur Electronic Supply**  
17929 Euclid Avenue  
**Columbus** (43215)  
Universal Service  
114 N. Third Street

## DAYTON (45404)

**Srepco Electronics**  
314 Leo Street  
**Toledo** (43624)  
Warren Radio Co.  
1002 Adams Street

## YOUNGSTOWN (44503)

**Armies Electronics**  
322 W. Federal Street

## OKLAHOMA

**Oklahoma City** (73122)  
Hood's Amateur Radio Equipment  
5512 N. Donald

## TULSA (74119)

**Radio, Inc.**  
1000 S. Main Street

## OREGON

**Albany** (97321)  
Oregon Ham Sales  
409 W. First Avenue

## PORTLAND (97205)

**Portland Radio Supply Co.**  
1234 S. W. Stark

## PENNSYLVANIA

**Drexel Hill** (19026)  
Kass Electronics  
2502 Township Line Road  
**Pittsburgh** (15222)  
Tydings Company  
933 Liberty Avenue  
**Trevose** (19047)  
Trevose Electronics  
4033 Brownsville Road

## WILLOW GROVE (19090)

**Ham Buerger, Inc.**  
68 N. York Road

## RHODE ISLAND

**Warwick** (02888)  
W. H. Edwards Co.  
55 Electronics Drive

## SOUTH CAROLINA

**Columbia** (29202)  
Dixie Radio Supply  
1900 Barnwell Street

## SOUTH DAKOTA

**Watertown** (57201)  
Burghardt Amateur Center  
124 First Ave. N. W.

## TENNESSEE

**Knoxville** (37901)  
Bondurant Brothers  
906 Sevier Avenue  
**Nashville** (37203)  
Electra Distributing Co.  
1914 W. End Avenue

## TEXAS

**Corpus Christi** (78404)  
Douglas Electronics  
1118 S. Staples  
**Dallas** (75204)  
Electronic Center, Inc.  
2929 N. Haskell  
**Fort Worth** (76110)  
Ed Juge Electronics  
3850 South Freeway  
**Houston** (77002)  
Madison Electronics Supply  
1508 McKinney  
**Tyler** (75701)  
Cole Electronic Supply  
335 South Bonner

## UTAH

**Salt Lake City** (84115)  
Marwill Supply Co.  
2511 S. State Street

## VIRGINIA

**Annapoland** (22003)  
Arcade Electronics  
7048 Columbia Pike  
**Richmond** (23225)  
Electronic Equipment Co.  
6540 Midlothian Turnpike  
**Roanoke** (24016)  
Radio Communications Co.  
311 Shenandoah Avenue N. W.

## SANDSTON (23113)

**A & F Electronics**  
Rt. #1 La France Rd.

## WASHINGTON

**Seattle** (98108)  
Amateur Radio Supply Co.  
6213 - 13th Avenue South

## SPokane (99206)

**HCJ Electronics**  
E. 8214 Sprague

## TACOMA (98402)

**C & G Electronics**  
2502 Jefferson Avenue

## WISCONSIN

**Madison** (53713)  
Satterfield Electronics  
1900 S. Park  
**Milwaukee** (53216)  
Amateur Electronic Supply  
4828 W. Fond du Lac Ave.

## PUERTO RICO

**Hato Rey** (00918)  
Jose Arturo Fernandez  
208 Eleanor Roosevelt St.

## CANADA

**Alberta**  
**Sherwood Park**  
Omniket Electronics  
227 Cottonwood  
**British Columbia**  
**Vancouver 9**  
Rendel Paret Electronics Ltd.  
2048 W. 4th Avenue

## Manitoba

**Winipeg**  
Cam Gard Supply Ltd.  
397 William Avenue

## Ontario

**Toronto 590**  
Ray Hunter & Assoc.  
7 Westrose Ave.

## Downsview

**VE Amateur Radio Sales**  
3768 Bathurst Street

## London

**C. M. Peterson Co. Ltd.**  
575 Dundas Street E.

## Quebec

**Montreal 101**  
Payette Radio Ltd.  
730 St. Jacques

**R. L. DRAKE COMPANY**



**DRAKE**

540 Richard St., Miamisburg, Ohio 45342

Phone: (513) 866-2421 • Telex: 288-017

January, 1974  
volume 7, number 1

**staff**

James R. Fisk, W1DTY  
editor

Patricia A. Hawes, WN1QJN  
editorial assistant

Nicholas D. Skeer, K1PSR  
vhf editor  
J. Jay O'Brien, W6GDO  
fm editor

Alfred Wilson, W6NIF  
James A. Harvey, WA6IAK  
associate editors

Wayne T. Pierce, K3SUK  
cover

T.H. Tenney, Jr. W1NLB  
publisher

Hilda M. Wetherbee  
assistant publisher  
advertising manager

**offices**

Greenville, New Hampshire 03048  
Telephone: 603-878-1441

**ham radio** magazine is  
published monthly by  
Communications Technology, Inc  
Greenville, New Hampshire 03048

Subscription rates, world wide  
one year, \$7.00, three years, \$14.00  
Second class postage  
paid at Greenville, N.H. 03048  
and at additional mailing offices

Foreign subscription agents  
United Kingdom  
Radio Society of Great Britain  
35 Doughty Street, London WC1, England

All European countries  
Eskil Persson, SM5CJP, Frotunagrand 1  
19400 Upplands Vasby, Sweden

African continent  
Holland Radio, 143 Greenway  
Greenside, Johannesburg  
Republic of South Africa

Copyright 1973 by  
Communications Technology, Inc  
Title registered at U.S. Patent Office  
Printed by Wellesley Press, Inc  
Framingham, Massachusetts 01701, USA

**ham radio** is available to the blind  
and physically handicapped on magnetic tape  
from Science for the Blind  
221 Rock Hill Road, Bala Cynwyd  
Pennsylvania 19440  
Microfilm copies of current  
and back issues are available  
from University Microfilms  
Ann Arbor, Michigan 48103



# contents

**6 256-bit CW memory for RTTY**  
Howard L. Nurse, W6LLO

**14 five-band linear amplifier**  
John R. True, W4OQ

**20 high-impedance meter interface**  
J.R. Laughlin

**26 ic logic families**  
Henry D. Olson, W6GXN

**36 two-meter fm package**  
J.H. Ellison, W6AOI


**46 solving heatsink problems**  
Courtney Hall, WA5SNZ

**54 lowpass filter design**  
Frank Regier, OD5CG

**58 toroid antenna tuner**  
Gregory P. Widin, WB2ZSH

**62 windom antenna**  
James H. Morris, W4VUO

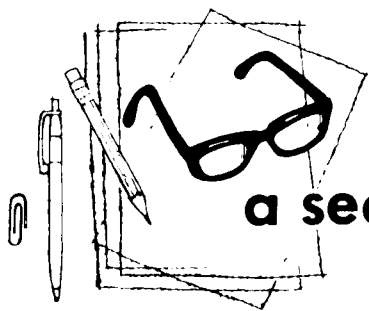**4 a second look**                      **66 ham notebook**  
**110 advertisers index**            **70 new products**  
**68 comments**                      **110 reader service**  
**99 flea market**



## a second look

by jim  
fisk

**More in '74.** If you haven't seen that motto or heard of the concept, you will, because in 1974 *ham radio* will be providing a whole new family of services to the amateur community, services that will help each amateur derive the most enjoyment from his hobby.

More in '74 means a lot of things to *ham radio* readers, including more editorial staff and more specialized publications as well as some other exciting new projects. Since some of these projects are still in the embryonic planning stages we can't tell you much about them, because the final product may be considerably different than the original concept, but complete details will be announced as soon as they are available and those announcements will be well worth waiting for.

More in '74, among other things, means a new editor for *ham radio* and a new role for me as editor-in-chief. However, a change in editorial staff does not mean a shift in editorial policy. *Ham radio* will continue to do what we do best, bringing you the latest and best in technical articles and construction projects each and every month. The new editor, Joe Schroeder, W9JUV, has been an active amateur for more than 25 years and is well known to many of you. He's been associated with the electronics industry in one way or another for 20 years, was the editor of *Instrument Digest* and, more lately, editor of *Guns Illustrated*. Until leaving Chicago recently, he was on the Technical Committee of the Illinois Repeater Council. Joe is also an Honor Roll DXer with more than 340

countries to his credit and is active on all bands from 160 meters to 450 MHz. You'll be hearing a lot more from him in the future. Between the two of us *ham radio* will be bigger and better than ever.

More in '74 means a brand-new newsletter, *HR Report*, which will keep you up to date with late-breaking news from the FCC, ARRL and industry sources, new DX activities, contest and hamfest announcements and up-to-the-minute propagation forecasts. The first issue of *HR Report* will be available in early January and will be sent out to subscribers twice monthly via airmail after that. In addition, special issues will be published as events warrant. If you want to know what's happening in the amateur world, you owe it to yourself to subscribe to *HR Report*. The subscription rate in the United States and Canada is \$12.00 per year (\$15.00 for overseas readers) with a guaranteed minimum of 24 issues per year.

More in '74 means a number of other new publications including new titles for your bookshelf and new operating aids for your station. For example, a new *Novice Radio Guide* is presently in production and will be available within a few months. Volume II of the popular *Ham Notebook* is currently in preparation and will be available later this year as will several other new titles.

These are only a few of the highlights — more announcements will be made as we progress through the year.

*Ham Radio . . . more in '74.*

**Jim Fisk, W1DTY**  
editor-in-chief

THE

# Triton



The TRITON is a One-of-a-Kind HF transceiver, totally solid state including the final amplifier. The new generation that does more things better than ever before.

One, you can change bands instantly. Just turn the band switch—and go!

Two, there is less internal heat to prematurely age components and no high voltage to break down insulation or cause accidental shock.

Three, it has ample reserve power to run at full rating even for RTTY or SSTV without limit. Great for contests or emergency service.

Four, it is light and compact with a detachable AC power supply to work directly from 12 VDC—For mobile operation without tedious installation.

Five, the TRITON is a delight to operate. SSB is clean, crisp and articulate.

Amplified ALC puts all available speech power into the antenna without splatter. CW is wave-shaped to cut through QRM and pile-ups. Instant break-in (not

"semi" which really isn't break-in) lets you monitor the frequency while transmitting.

And six, a lot more goodies such as excellent dial illumination, plug-in circuit boards, offset tuning, built-in SWR bridge, speaker, crystal calibrator, snap-up anti-parallelax front feet, light indicators for offset and ALC, direct frequency readout, WWV, entire 10 meter band coverage—and a lot more.

The TRITON brings together all that is new and exciting in Solid State for your greater enjoyment of Amateur Radio.

We'll be happy to send you full information.

TRITON I 100 watts input.....	\$519.00
TRITON II 200 watts input.....	606.00
Model 251 Supply for TRITON I.....	69.00
Model 252 Supply for TRITON II....	89.00

**TEN-TEC, INC.**  
SEVIERVILLE, TENNESSEE 37862



## CW memory for RTTY identification

Complete  
construction details  
for the RM-100 —  
a 256-bit  
CW memory  
using modern  
read-only memory ICs

Howard L. Nurse, W6LLO, 665 Maybell Avenue, Palo Alto, California 94306

Do you find it frustrating to stop typing in the middle of an RTTY QSO to comply with FCC rule 97.87? This rule requires that you, as an RTTY station operator, keep your CW key at the ready to identify properly. The RATTline RM-100 CW memory is designed to facilitate that required CW identification.

The RM-100 uses an integrated-circuit memory to allow automatic CW transmission of a message at the speed of approximately ten words per minute. It can be connected directly to the RY-170 AFSK generator described in the December, 1973, issue of *ham radio* (see fig. 1), or to any other keying line compatible with the npn open-collector output of the RM-100.

When you want to identify, a CW message such as "... de W6LLO" can be started locally with a front-panel switch, or remotely with a ground control signal. While the RM-100 is keying, an LED lights to indicate the circuit is busy.

This article shows how to construct the RM-100 CW Memory. Instructions are given for programming your own memory, or you can purchase one already programmed.\* The RM-100 circuit can be

\*JTM Associates, P.O. Box 843, Manchester, Missouri 63011 (\$12.50); Babylon Electronics, Carmichael, California 95068 (\$15.00).




built for under twenty-five dollars using the pre-programmed memory, or for under twenty if you program the memory yourself.

### programming the memory

At the heart of any automatic message generator is a means to store binary information. In the past, code wheels with cogs, or diode matrices, have been

The first step when programming is to decide what you want the memory to say. A Morse code *key-down* is defined as 1, while a *key-up* is 0. Using a pattern as shown in **fig. 2**, mark each of the eight rows of 32 memory cells where a Morse code *key-down* is desired. Remember that a dot will occupy one memory cell, a dash or letter space, three, and a word space, four. Ten consecutive *key-up* cells

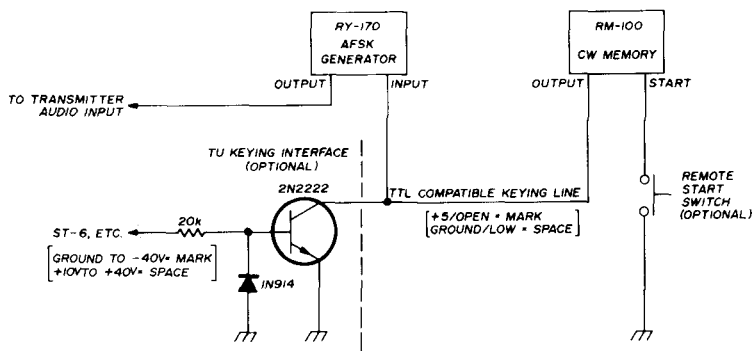

**fig. 1.** RATTline system interconnection showing RY-170 AFSK generator and RM-100 CW memory wired together with one possible interface circuit to a ST-6 RTTY terminal unit.

popular as memories. A relatively new type of memory is now available to amateurs from surplus suppliers. The programmable-read-only memory integrated circuit, abbreviated as PROM, P.ROM, or fPROM, depending on the respective manufacturer, can be custom programmed in the field by applying the correct voltages to its inputs, following the manufacturer's instructions.

The Signetics 8223 Programmable ROM IC I chose for the RM-100 is the easiest to find.\* The 8223 is supplied with all of its 256 memory cells at a TTL logic low or 0. The memory is programmed by fusing (burning out) microscopic wires in selected cells to generate a desired pattern of logic highs, or 1s. Once the memory has been programmed, the stored binary information can be recalled from each cell by applying an address word to the inputs of the device.

\*JTM Associates, previously foot-noted, or Poly Paks, P.O. Box 942, Lynnfield, Massachusetts 01940 (\$7.95).

indicate an "end-of-message." **Table 1** lists the letters of the alphabet and numbers from 0 to 9 with the required number of memory cells for each character. The CW message can occupy 246 memory cells after the 10-bit allowance has been made for the end-of-message code.

Once you have established the program matrix, the following procedure should be used with the circuit shown in

**table 1.** Memory cells required for letters, numbers and punctuation.

A 8	H 10	O 14	V 12
B 12	I 6	P 14	W 12
C 14	J 16	Q 16	X 14
D 10	K 12	R 10	Y 16
E 4	L 12	S 8	Z 14
F 12	M 10	T 6	
G 12	N 8	U 10	
1 20	6 14		, 22
2 18	7 16		? 18
3 16	8 18		. 20
4 14	9 20		/ 16
5 12	0 22	end of msg	10
		word space	4

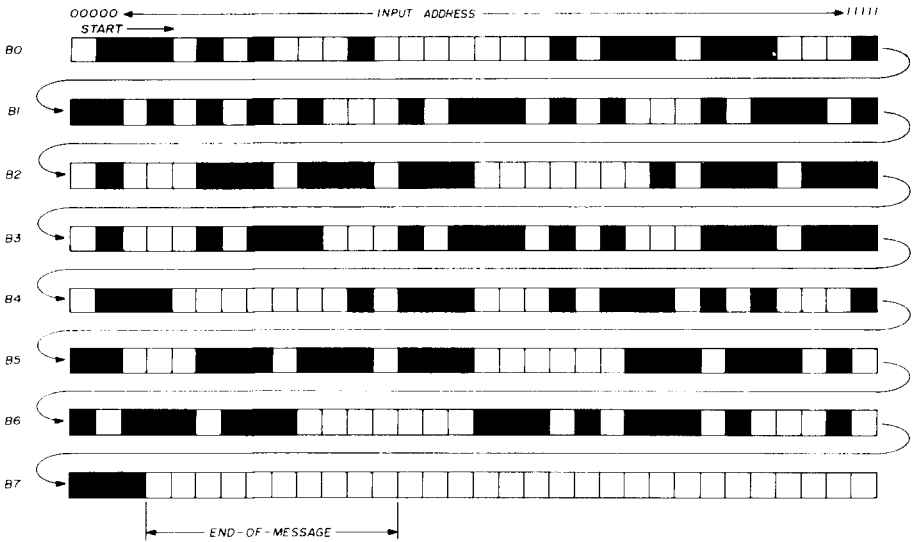


fig. 2. CW programming matrix consisting of eight rows of thirty-two memory cells, for a total of 256. Message shown here is "de W6LLO Palo Alto, Ca."

fig. 3 to program your memory.<sup>x</sup> Be careful — you only have one chance to correctly program each cell. Once the wire in a cell has been fused, it cannot be returned to its 0 logic state. If changes are required in the message, it is necessary to

program a replacement integrated circuit.

### programming procedure

The 8223 ROM IC is shipped with all outputs at logical 0. To write a logical 1 proceed as follows:


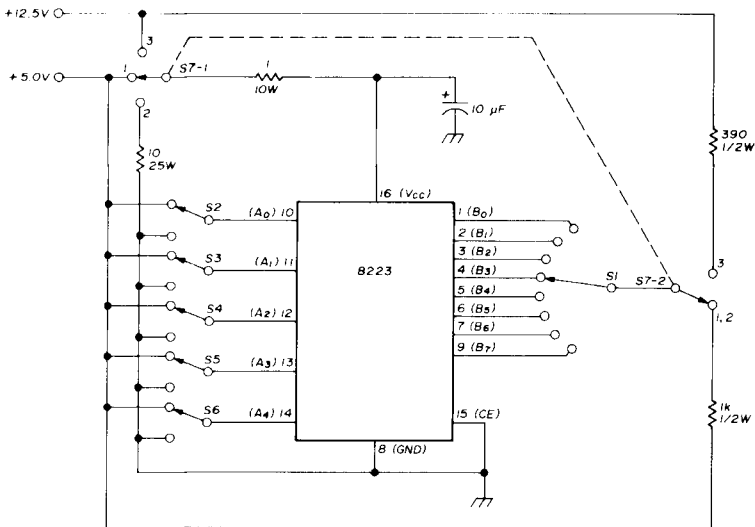


fig. 3. Programmer schematic for Signetics 8223 field-programmable read-only memory. The 10- $\mu$ F capacitor from pin 16 to ground is required to eliminate noise from the supply line. During programming switch S7 must be in position 2 long enough for the 1- $\mu$ F capacitor to discharge to less than 0.5 volt.

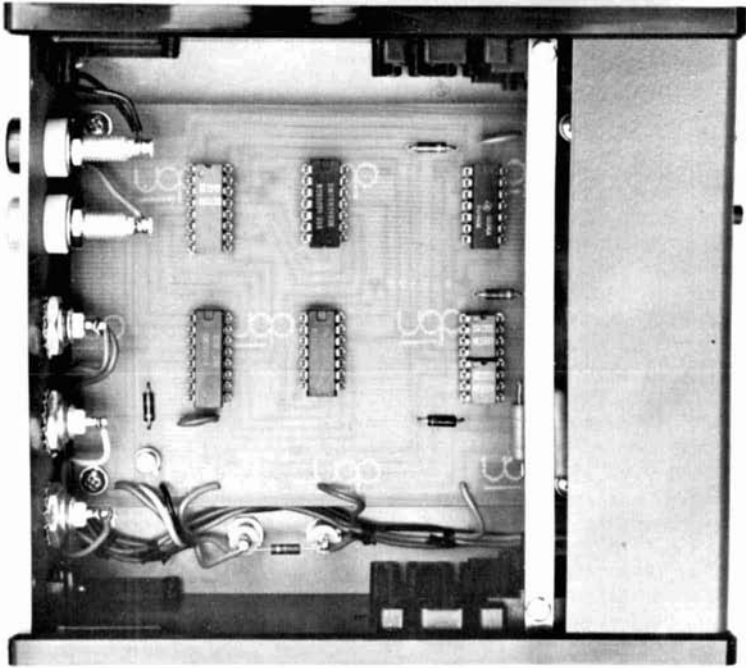- S1 single-pole, 9-position switch
- S7 2P3T rotary switch with ground connected to the middle position of the first section. As  $V_{cc}$  (pin 16) is taken from 5 volts to 12.5 volts it will momentarily go to ground.



Inside of RM-100 as viewed from top. Resistor mounted on stand-offs is for LED indicator light.

1. Start with pin 8 grounded and  $V_{cc}$  removed from pin 16.
2. Remove any load from the outputs.
3. Ground the Chip Enable.
4. Address the desired location by applying ground (i.e., 0.4 V maximum) for a 0, and +5.0 V (i.e., +2.8 V minimum) for a 1 at the address input lines.
5. Apply +12.5 V  $\pm$ 0.5 V to the output to be programmed through a 390-ohm, 10% resistor. Program one output at a time.
6. Apply +12.5 V to  $V_{cc}$  (pin 16 for 50 milliseconds to 1 second (maximum) with a  $V_{cc}$  risetime of 50 microseconds or less. If 1.0 second is exceeded, the duty cycle should be limited to a maximum of 25%. The  $V_{cc}$  overshoot should be limited to 1.0 V maximum. If necessary, a clamping circuit should be used. The  $V_{cc}$  current requirement is 40 mA maximum at +12.5

V. Several fuses can be programmed in sequence until 1.0 second of high  $V_{cc}$  time is accumulated before imposing the duty cycle restriction.

Note: Normal practice in text fixture



\*Programming instructions and fig. 3 adapted from Signetics Catalog, 1972, page 4-10.

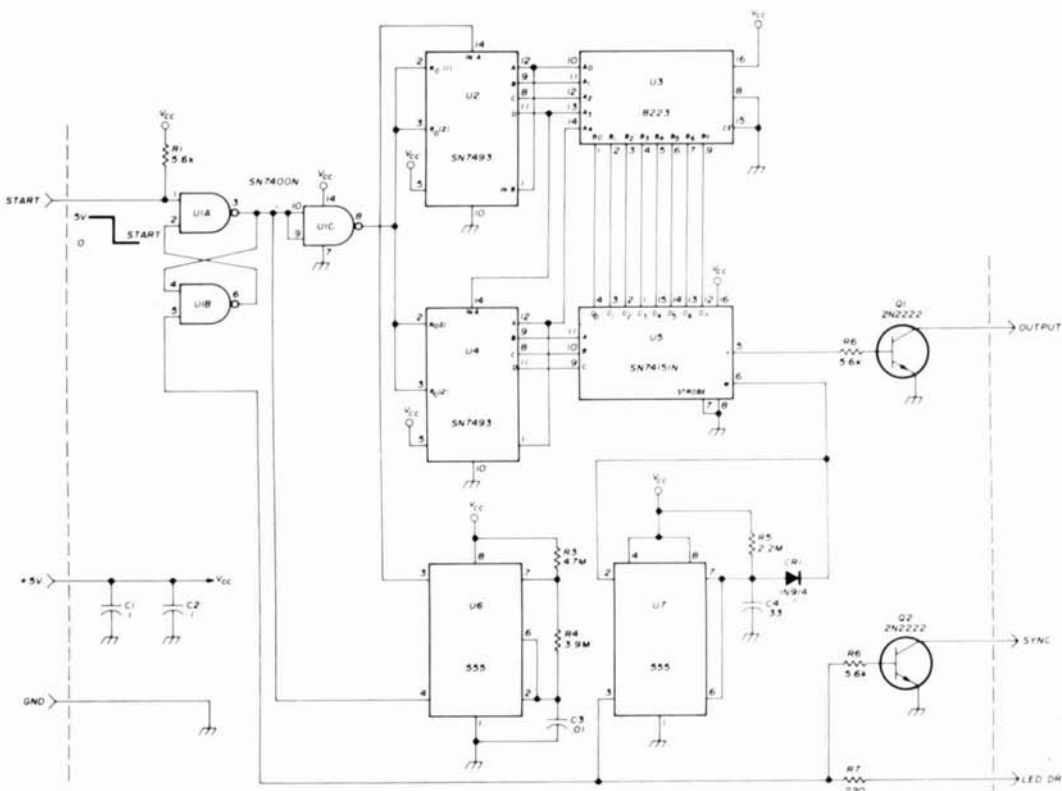


fig. 4. RM-100 CW memory schematic diagram.

layout should be followed. Lead lengths, particularly to the power supply, should be as short as possible. A capacitor of 10  $\mu$ F minimum, connected from +12.5 V to ground, should be located close to the unit being programmed.

7. Remove the programming voltage from pin 16.
8. Open the output.
9. Proceed to the next output and repeat, or change address and repeat procedure.
10. Continue until the entire bit pattern is programmed into your custom 8223 ROM IC.

By now you have obtained a programmed memory, either by programming it yourself, or by purchasing it pre-programmed. Now you are ready to use it in the RM-100 circuit.

## circuit description

The RM-100 CW memory consists of clock, divider, memory, data selector and end-of-message sense circuitry. The unit schematic is shown in fig. 4, and the component parts layout is given in fig. 5.



Rear panel of the RM-100.

Photographs of the completed RM-100 appear throughout this article.

The clock frequency established by timer U6, R3, R4 and C3 determines the dot length of the CW output. The code speed which results from a Morse dot length of 88 milliseconds was chosen, on suggestion from W6FFC, to keep the receiving RTTY machine in synchronism

Timer U7 detects when ten cells have passed without a keying event. Keying dots or dashes from the data selector discharges timing capacitor C4, whereas the timer is triggered on the trailing edge of each dot or dash. If a new keying bit does not discharge the capacitor within 880 milliseconds after the timer has been triggered, the timer output will reset the

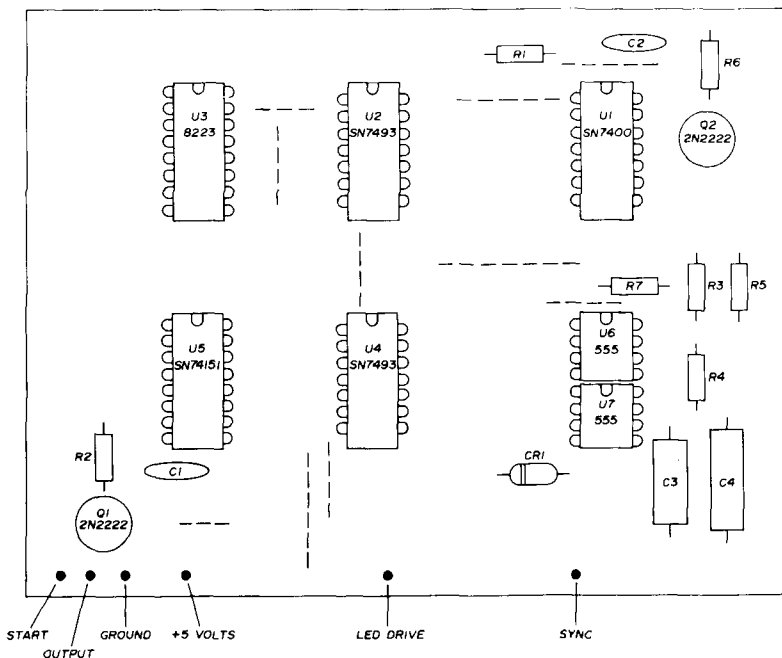


fig. 5. Suggested component layout for the RM-100. Dotted lines denote jumpers.

with the incoming pulses. Instead of printing garble, the machine will print blanks and Os in a combination which depends on the particular letter being sent.

The clock output frequency is divided by binary counters U2 and U4. The first five outputs from the dividers supply counts 0 through 31 to address the memory, while the last three outputs are used to address the data selector, U5.

The memory, U3, is read out through the data selector, one cell at a time, in the order shown in fig. 2. The Q output from the selector drives the base of keying transistor, Q1, while the  $\bar{Q}$  output is used by the end-of-message circuit.

control flip-flop U1A and U1B, and the counters. The RM-100 CW message can be started again after the counters have been reset.

The sync output from the memory is connected to an open-collector transistor switch which turns on for the duration of a message. The sync output will be used by upcoming RATTline accessories.

As with the RY-170, a separate supply is required to power the RM-100. A 5  $\pm$ 0.25 Vdc regulated supply capable of 150 mA should be used.

### construction

The RM-100 can be built using perforated or printed-circuit board. The cir-

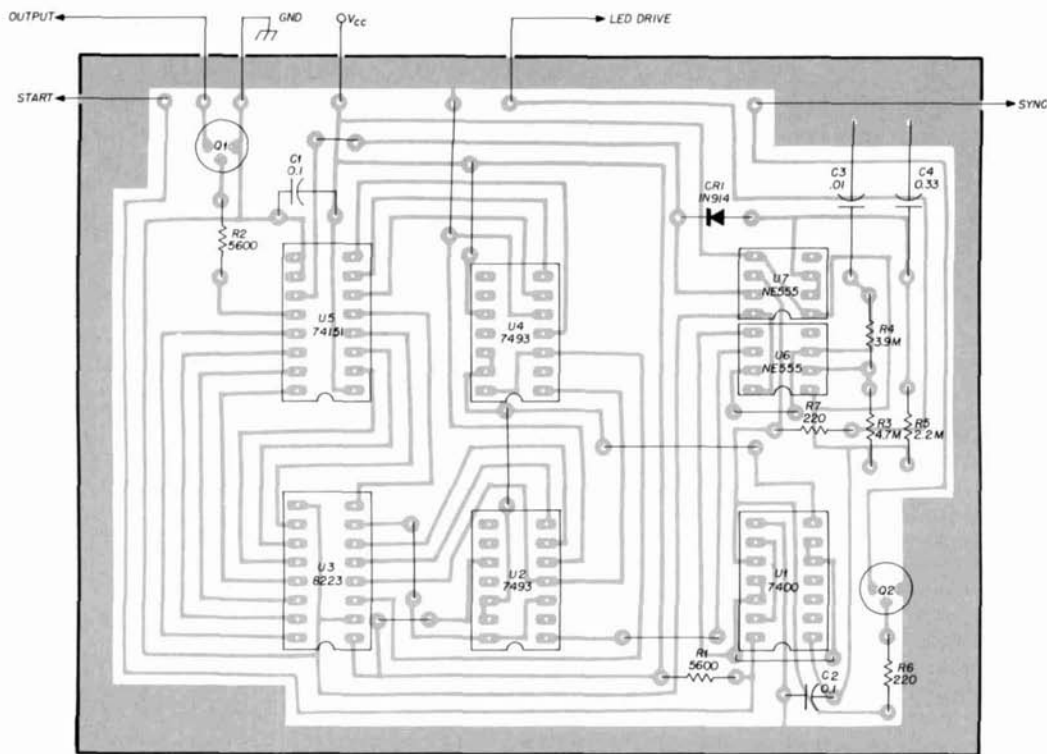


fig. 6. Full-size printed-circuit layout (foil side) for the 256-bit CW memory.


circuit should be placed in an enclosure, such as the Ten-Tec JG-5 shown in the photographs, to shield against rf.

An LED, powered from the 5-volt supply through a 220-ohm resistor, serves as a pilot light. A second LED is turned on by U7 when a message is being transmitted. A pushbutton switch on the front panel, which grounds the *start* control line, is used to trigger the memory.

The only critical components are the capacitors and diode used in the timers. High stability, low leakage capacitors should be used at C3 and C4 to maintain correct timing. A silicon diode is required at CR1 so that diode leakage will not effect timing in the end-of-message circuit.

Bypass capacitors should be used in at least two places on the circuit board. They should be near integrated circuits from  $V_{cc}$  to ground to filter transients. Molex pins hold the integrated circuits, and BNC jacks are used to connect signal inputs and outputs. Shielded cables are recommended when connecting the RM-100 with other parts of your system to reduce the possibility that strong rf fields will interfere with circuit operation.

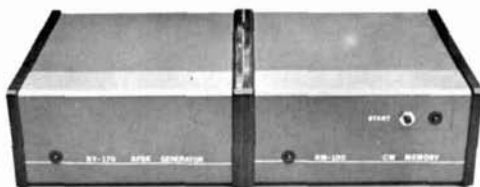Don't let rule 97.87 get to you! Now you can have automatic CW identification in your RTTY system with the RM-100 CW Memory.



RM-100 CW memory alongside the RY-170 AFSK generator.

ham radio

# Support Clean Air



SB-102 Transceiver



HW-101 Transceiver

## Heathkit Transceivers — for exceptional stability, razor sharp selectivity, cleaner copy on transmit or receive!

The Heathkit SB-102 gives you exceptional stability and dial linearity — made possible by an all solid-state linear master oscillator with 1 kHz calibration. The SB-102 stabilizes itself in a fast 10-minutes, drifts less than 100 Hz per hour after initial warm-up. The receiver section delivers an S+N/N ratio of less than 0.35  $\mu$ V for 10 dB — with front-panel selection of built-in 2.1 kHz SSB crystal filter or optional 400 Hz crystal filter. And there's a dial resettable to 200 Hz; 180 W PEP SSB input, 170 W CW input; switch selection of upper or lower sideband and CW; built-in sidetone for monitoring; built-in 100 kHz crystal calibrator; triple action level control to reduce clipping and distortion; built-in VOX, and complete metering.

The SB-102 is the value leader because you build it yourself to save on initial investment and service. Simple circuit board/wiring harness construction gets it all together easily.

- Kit SB-102, 24 lbs. . . . . 385.00\*
- Kit SB-600, 8 ohm matching speaker with mounting space for AC supply, 7 lbs. . . . 19.95\*
- SBA-301-2, 400 Hz CW crystal filter, 1 lb. . . . . 22.95\*
- Kit HP-23B, AC supply, 19 lbs. . . . . 51.95\*

With the HW-101 you get dial drive and added front-panel SSB/CW filter selection. Sensitivity better than 0.35  $\mu$ V for 10 dB S+N/N. Image and IF rejection better than 50 dB. 36-1 knob to dial ratio in a ball bearing drive mechanism. New preselector circuitry and thermal stabilized FET VFO with 5 kHz readout, for rock-solid drift-free tuning from 80 through 10 meters. Built-in 100 kHz crystal calibrated and zero reset button. Optional SBA-301-2 crystal filter installs in minutes, giving you the same remarkable two-way capability provided by its big brother, the Heathkit SB-102. CW filter offers razor sharp 400 Hz selectivity. Built-in SSB crystal filter delivers 2.1 kHz selectivity at 6 dB down for superior SSB copy.

The HW-101 is kit-form communication at its best — a low-cost easy-to-build transceiver that's comparable to units priced much higher.

- Kit HW-101, 23 lbs., mailable . . . . . 259.95\*
- Kit HP-23B, AC power supply, 19 lbs., mailable . . . . . 51.95\*
- SBA-301-2, 400 Hz crystal filter, 1 lb., mailable . . . . . 22.95\*
- Kit HS-24, mobile speaker, 4 lbs., mailable . . . . . 9.50\*

## See them at your Heathkit Electronic Center —

Units of Schlumberger Products Corp.

ARIZ.: Phoenix; CALIF.: Anaheim, El Cerrito, Los Angeles, Pomona, Redwood City, San Diego (La Mesa), Woodland Hills; COLO.: Denver; CONN.: Hartford (Avon); FLA.: Miami (Hialeah); GA.: Atlanta; ILL.: Chicago, Downers Grove; IND.: Indianapolis; KANSAS: Kansas City (Mission); KY.: Louisville; LA.: New Orleans (Kenner); MD.: Baltimore, Rockville; MASS.: Boston (Wellesley); MICH.: Detroit; MINN.: Minneapolis (Hopkins); MO.: St. Louis; N.J.: Fair Lawn; N.Y.: Buffalo (Amherst), New York City, Jericho; L.I.: Rochester; OHIO: Cincinnati (Woodlawn), Cleveland, Columbus; PA.: Philadelphia, Pittsburgh; R.I.: Providence (Warwick); TEXAS: Dallas, Houston; WASH.: Seattle; WIS.: Milwaukee.



HEATH COMPANY, Dept. 122-1  
Benton Harbor, Michigan 49022

Please send FREE Heathkit Catalog.

Enclosed is \$ \_\_\_\_\_, plus shipping

Please send model(s) \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

\*Mail order prices; F.O.B. factory AM-293

# five-band kilowatt linear

How to use  
beam power tetrodes  
efficiently and  
economically in the  
grounded-grid,  
grounded-screen  
configuration


John R. True, W4OQ, 10322 Georgetown Pike, Great Falls, Virginia 22066

With the proper design precautions, a power tetrode in a grounded-grid and grounded-screen configuration can provide more than 13-dB stable, parasitic-free gain in the high-frequency spectrum. An old 4-1000A which I use in this circuit (see fig. 1) operates at 2-kW PEP input when driven by an exciter rated at 100-watts output. Since power tetrodes have very high power gain characteristics, they require very little drive. Typically, the amplification factor of the grid is in the order of five to six times that of the screen. However, grid dissipation is very low and screen dissipation is considerably greater.

For amateur use, however, the high gain characteristic of the power tetrode is not always an advantage, because few amateurs use exciters that operate efficiently at less than 100-watts output. When the 100-watt exciter is used to drive a high-gain power amplifier, it must be loaded with a power attenuator, which wastes valuable power. One commercial linear recently offered on the market, for example, required a power-wasting 12-dB pad.

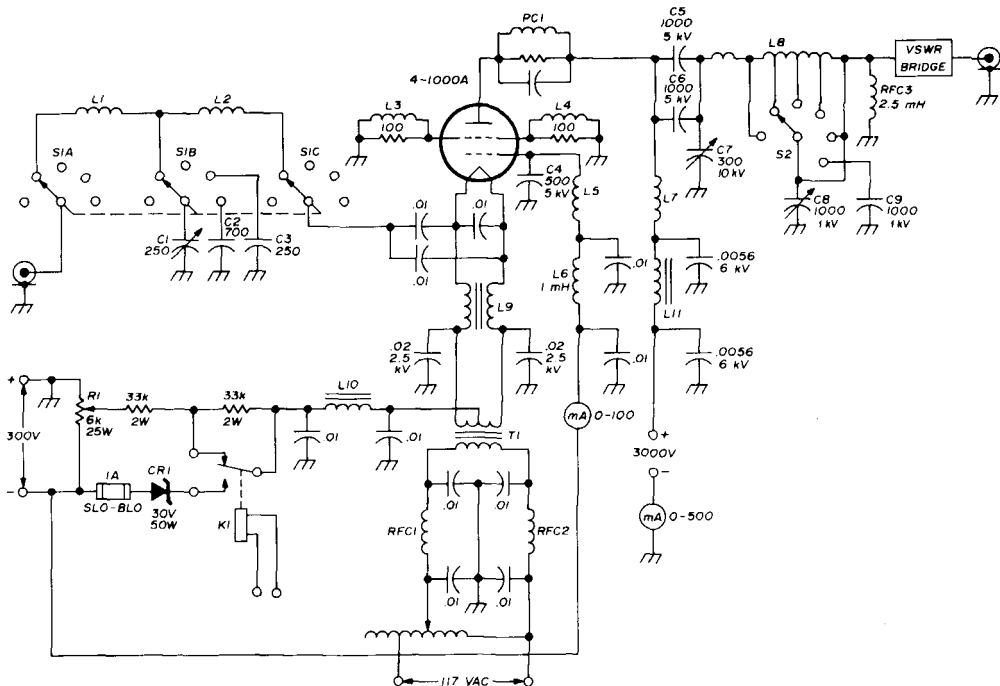The high gain of the power tetrode can also lead to other problems, such as vhf parasitics which require extensive suppression. Also, a tetrode, grounded-filament, class-AB2 linear amplifier re-





- |          |  |           |   |
|----------|--|-----------|---|
| C1       | 25-250 pF air variable, 1000-volt working                    | L9        | 33 turns no. 10 enamelled bifilar wound on 1/2" ferrite rod, 7" long  |
| C4       | 500 pF ceramic, 5 kV working (Centralab 858S)                | L10,L11   | 2 1/2" no. 18 wire wound around 1/2" ferrite rod  |
| C5,C6,C9 | 1000 pF ceramic, 5 kV working (Centralab 858S)               | K1        | spdt relay, 117-Vac coil  |
| C7       | 10-300 pF vacuum variable, 10 kV                             | PC1       | 20 pF ceramic capacitor (Centralab 852S) in parallel with four 470-ohm, 2-watt resistors and 4 turns no. 12 1/2" diameter, resonated to 110 MHz |
| C8       | 1000 pF air variable, 1000 V                                 | RFC1,RFC2 | 30 turns no. 16, closewound on 1/2" diameter wooden dowel   |
| L1,L2    | see table 1  | S1        | 3-pole, 7-position ceramic switch   |
| L3,L4    | 3 turns no. 12, 3/8" diameter, with 100-ohm, 2-watt resistor | S2        | 1-pole, 6 position switch (part of B&W 850A)  |
| L5,L6    | 1 mH rf choke  | T1        | filament transformer, 7.5 volts, 21 amps  |
| L7       | plate rf choke, 1 amp (B&W model 800)                        |           |   |
| L8       | plate tank assembly (B&W 850A)                               |           |   |

fig. 1. Modified grounded-grid, grounded-screen, beam-tetrode power amplifier. Plate and screen power supplies are shown in fig. 3. Grid bias is provided by the zener diode, CR1.


quires a well regulated grid and screen supply. Using two tubes in parallel just multiplies the problems.

In recent years the grounded-grid triode has been used extensively as a linear amplifier for ssb and CW. Among its many advantages are excellent input/output circuit isolation (which means less parasitic problems), high power gains (10 to 13 dB), possibility of fixed-tuned

bandpass input circuitry and no requirement for a regulated screen supply (or any screen supply at all, for that matter). Using the grounded-grid circuit, it is very easy to build a stable linear amplifier with low distortion products which is relatively free from harmonic distortion.

With all the advantages of grounded-grid triode power amplifiers, why even bother with a tetrode? Primarily because

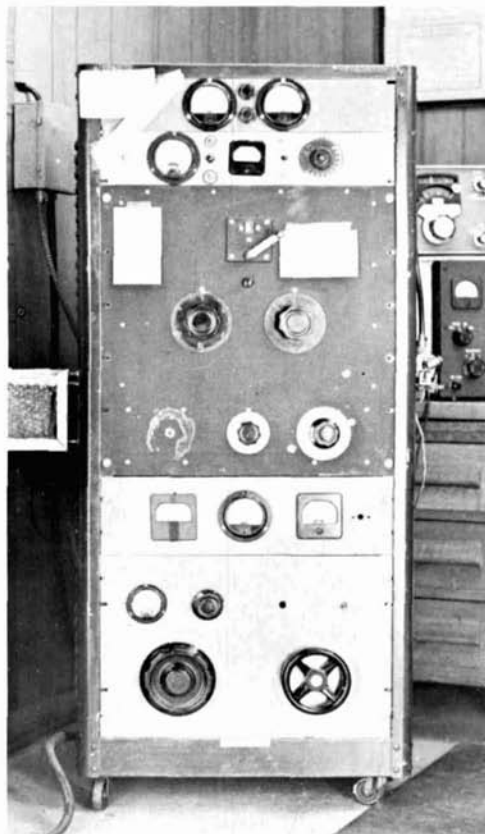tetrodes are in abundant supply at ridiculously low prices — the broadcast industry practically gives them away after a certain number of operating hours. This is less expensive for them than experiencing a failure in the middle of an important broadcast. There are also a number of



Rack-mounted linear amplifier includes meters for vswr, grid and plate current, and filament, grid, screen and plate voltage. Variac-controlled power supply is located behind bottom panel.

power tetrodes available on the surplus market. However, if you are selecting a tetrode for a linear amplifier, choose one with adequate plate dissipation and filament emission to get the job done properly.

Experience has taught me that all is not gold that glitters. If the tetrode is used with the grid and screen grounded, the power gain will be low due to degenerative feedthrough power. Addi-

tionally, the grid hogs control of the space current while the screen loaf. To drive the plate to full output, excessively high grid current is required.

In an effort to cure some of these shortcomings, I built an amplifier with the grid less than fully grounded. It was bypassed with a 500-pF capacitor and the dc brought out for metering through an rf choke. This simple technique reduced the grid current (and increased screen current) to an appropriate value, but power gain was reduced because the screen is not as effective as the grid in controlling plate current. There had to be a better way!

### the circuit

Considering the tremendous gain possible with a conventional grounded-filament, class-AB2 tetrode amplifier, I thought a hybrid compromise might be the answer. That is, to retain the isolation provided by the partially grounded grid and grounded screen, but to place some voltage on the screen to increase transconductance. That is easily managed with a grounded screen by biasing the filament negative in respect to ground. Thus, the screen becomes positive with respect to the filament. Unfortunately, so does the grid! Placing a zener diode in series with the filament return to the minus side of the screen supply will provide the grid with well-regulated bias for satisfactory idling as well as full input plate current.

However, this is not the complete answer. If you look carefully at the physical structure of the grid and screen of the 4-1000A, you will see that they form a sort of basket-woven cavity. When a positive voltage is placed on the screen, these cavities (with the filament) act as a triode oscillator above 100 MHz. By way of demonstration, if you ground the grid and screen of a 4-1000A and couple a grid-dipper to these leads, you will find that the screen is resonant at about 120 MHz. The grid is resonant at about 110 MHz, an ideal condition for *regeneration*.

Under these conditions, the screen is inductive in respect to the grid, the condition required for in-phase feedback.

In fact, a 4-1000A self-oscillates near 110 MHz, and the 4-400A at about 140MHz. A pair of parallel power tetrodes may act like a push-pull oscillator, oscillating at a frequency that is dependent upon the length of their interconnecting leads.

If the grid is made to resonate higher (or the screen to resonate lower), self-neutralization occurs since the screen is capacitive in respect to the grid, producing *degeneration*. This is easily accomplished. As noted before, the small 500-pF bypass capacitor slightly raises the resonant frequency of the grid. A small inductor in series with the screen shifts its natural resonance point below that of the grid, resulting in neutralization.


### power supply considerations

If you trace the plate-current path in **fig. 1**, you will find that the plate current flows through both the plate and screen supplies. Therefore, the screen supply must furnish both screen and plate current. The screen voltage must also be added to the plate voltage when calculating plate input power (subtract the zener voltage drop). It should be obvious, therefore, that the screen supply must provide very good voltage regulation.

Using the 4-1000A as an example, assuming a plate supply of 3000 volts, a screen supply of 300 volts and zener bias of 30 volts, the idling plate current will be about 125 mA. With 100-watts of excitation and a desired plate power

input of 1 kilowatt, grid current is approximately 30 mA, screen current is about 100 mA, and plate current is approximately 300 mA.

To reduce noise generation while receiving, some means must be provided for completely turning off the power tube

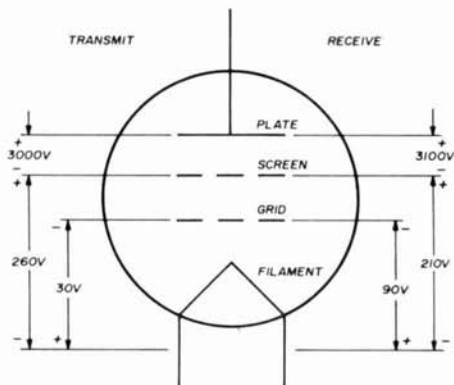


**fig. 2.** Operating voltages for the 4-1000A power amplifier during transmit and receive. Cutoff voltage on receive is provided through the contacts of relay K1 (see text).

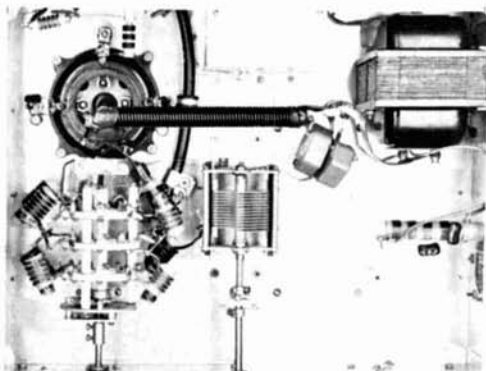when not transmitting. **Fig. 1** shows the circuit I use to accomplish this. When transmitting (relay K1 picked up), the grid is minus with respect to the filament by the voltage drop of the zener diode. When the relay drops out (receive position), the filament assumes the positive voltage offset from a tap on the screen supply bleeder resistor. A grid-filament bias of -90 volts is more than enough to completely cut off a 4-1000A with the plate and screen voltages indicated in **fig. 2**.

A complete schematic of the plate and screen power supplies is shown in **fig. 3**. All supply voltages are brought up to full operating levels with a variable transformer (Powerstat). The large filter capacitors require a lot of current to load them to full voltage, and this procedure reduces the surge current through the silicon diodes. Another Powerstat is used with the filament transformer to reduce the thermal shock of an instant-on filament switch.

The plate and screen power supplies



Underneath the linear amplifier chassis. Input matching network is at lower left.

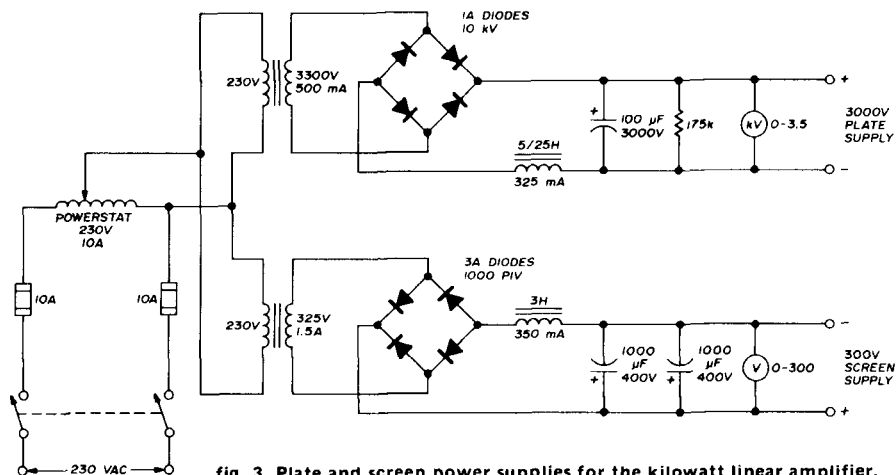


fig. 3. Plate and screen power supplies for the kilowatt linear amplifier.

use common protective fuses. This avoids the possibility of losing the plate supply with the screen supply still on, which would surely destroy the screen of the 4-1000A. The 1-amp slo-blo fuse between the grid-bias zener diode and the minus side of the screen supply protects against overloads, including parasitics. Any excessive dc cathode current will blow the fuse, automatically returning the grid-filament bias to the cutoff value.

### input network

Since normal voice waveforms have an approximately 3.5:1 peak-to-average ratio, this must be considered when computing the input impedance to the grounded-grid stage. At 1-kW input total required filament emission is 430 mA (300 mA plate current + 100 mA screen current + 30 mA grid current). With a 3.5:1 peak-to-average voice ratio, peak filament emission is 1.5 amperes (3.5 x 430 mA). Therefore, filament input impedance is

$$Z_i = \frac{P_i}{I^2} = \frac{100}{(1.5)^2} = \frac{100}{2.25} \cong 45 \text{ ohms}$$

where  $Z_i$  is the input impedance,  $P_i$  is the input (drive) power (100 watts), and  $I$  is the peak filament current.

The graphical design of a T-network for matching 50-ohm coaxial cable to the

45-ohm input impedance of the 4-1000A is shown in fig. 4.<sup>1</sup> In this graphical solution, the transfer impedance ( $Z_T$ ) was chosen to be 150 ohms. As can be seen,  $X_C = 51$  ohms,  $X_{L1} = 71$  ohms and  $X_{L2} = 69$  ohms. The Q of this network is approximately 3. Practical network component values for each of the high-frequency amateur bands are listed in table 1.

The T-network inductors L1 and L2 are wound on 1/2-inch polyethylene tub-

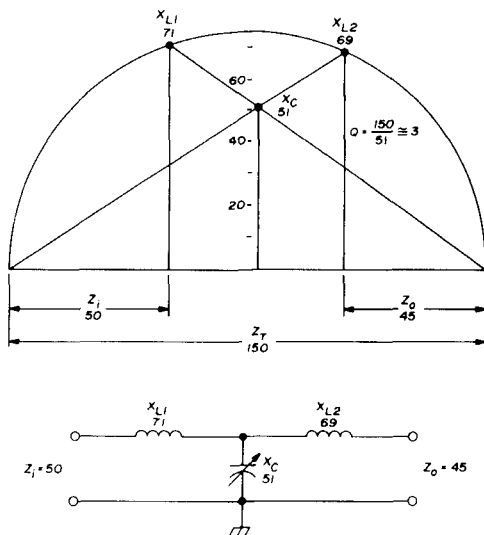


fig. 4. Graphical design of the T-network used at the input of the power amplifier.

ing. Number-14 Formvar is used for the 80- and 40-meter coils while number-12 Formvar is used for 10, 15 and 20 meters. A ½-inch wooden dowel is inserted in to the tubing during winding to keep the tubing from being deformed.

After the coils are wound, a short length of ½-inch OD ferrite rod (about 1-inch long) is inserted into the tubing and adjusted for the proper inductance value given in **table 1**. By using 5% fixed mica capacitors across the inductors and a grid dipper to check for resonance, it is possible to adjust them very close to their required inductance values. When the inductors are completed, coil dope is used to hold the turns and the ferrite slug in place.

### output network

The output pi network is based on the B&W model 850A bandswitching pi-network inductor which includes a built-in bandswitch. As shown in **fig. 1**, an additional switch contact was added to permit the use of a 1000-pF fixed capacitor in parallel with C8 on 75 meters.

The rear plate of the antenna loading capacitor (C8) is used as the common ground point for the output circuit. (The

rear plate of the input capacitor, C1, is used as the common ground point for the input circuit). Both the input and output coaxial cable connections are made at their respective common ground point and switch. These cables are connected directly to the exciter and the vswr bridge without any terminations at the chassis. This reduces input-output coupling.

**table 1. Component values for input T-network described in fig. 3 ( $X_C = 51$  ohms,  $X_{L1} = 71$  ohms,  $X_{L2} = 69$  ohms).**

frequency	L1	L2	C
3.60 MHz	3.14 $\mu$ H	3.05 $\mu$ H	865 pF
3.90 MHz	2.90 $\mu$ H	2.81 $\mu$ H	800 pF
7.15 MHz	1.58 $\mu$ H	1.54 $\mu$ H	436 pF
14.20 MHz	0.80 $\mu$ H	0.77 $\mu$ H	220 pF
21.25 MHz	0.53 $\mu$ H	0.52 $\mu$ H	147 pF
28.80 MHz	0.39 $\mu$ H	0.38 $\mu$ H	108 pF


### summary

As indicated by the brownish lace pattern at the base of the tube envelope, the "well-used" 4-1000A broadcast tube I am using must have had a zillion hours on it when I first got it. It has been in use for over three years at my station and is still going strong. If it goes out tomorrow, I will have had more than my money's worth from it and the spare I purchased for \$5 each.

Despite the work of building (and rebuilding) and debugging the modified 4-1000A grounded-grid linear it has been well worth the effort. My SB-401 exciter can drive the final to well over 2000-watts PEP without strain, and can loaf along at half power and still drive the final to a full 1-kW input. When connected to my five-band antenna system on one tower<sup>2</sup> the results are quite gratifying.


### references

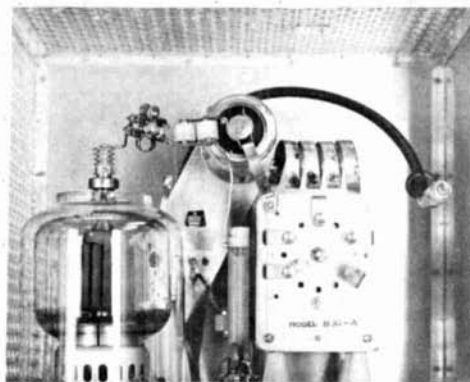1. I.L. McNally, "Graphical Solution of Impedance-Matching Problems," *ham radio*, December, 1969, page 26.
2. John R. True, W4OQ, "Grounded Vertical Tower Antenna System," *ham radio*, April, 1973, page 16; May, 1973, page 56.



Rear view of output components of the linear showing the 4-1000A and B&W pi-network inductor.

ham radio

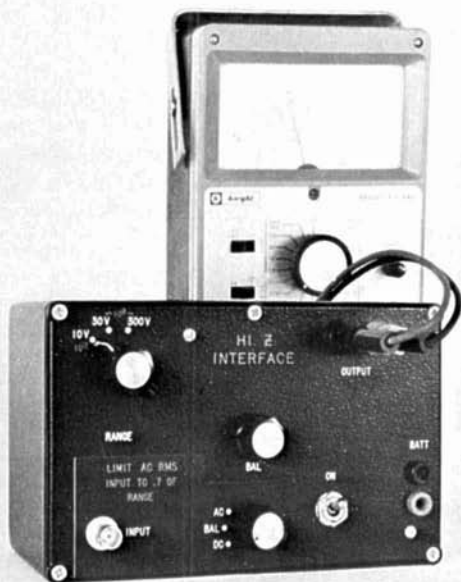

## high-impedance meter interface

A high accuracy  
meter-interface unit  
for ac and  
dc measurements  
that features up to  
1-million megohms  
input resistance

Making accurate measurements with a voltmeter is often difficult because of the input resistance of the meter itself. Errors due to the loading effect of the voltmeter are often nearly impossible to evaluate, particularly in transistor circuits where the dynamic characteristics of the circuit are difficult to accurately analyze. More importantly, many of these erroneous readings might go unnoticed as you hurry to check out a circuit. An accumulation of errors here and there often add up to a puzzling situation when troubleshooting a defective or inoperative circuit.

The standard vom with 20k  $\Omega$  input resistance can be a disaster in many circuits, either requiring tedious calculations to correct for its loading, giving misleading results to those not completely familiar with the meter and circuitry or simply being useless as a measuring tool. Even the heralded vtm, with its 10-megohm input resistance, will cause significant errors in many circuits.

J.R. Laughlin, 11918 Pompano Lane, Houston, Texas

Having long been troubled by volt-meter errors due to loading, I have made an effort to overcome and eliminate, as well as practically possible, this source of trouble. First, I decided that some type of interfacing unit should be designed to be used with existing equipment. Since my workshop contains a varied assortment of different types of meters, from the very cheapest to more expensive laboratory types, it would represent a needless waste of revenue to obsolete these. Also, the design of the interfacing unit would be greatly simplified by making use of the basic structure of these existing meters.

Portability, a must, dictates battery operation. To extend battery life and reduce operating costs, micropower operation is mandatory. The final instrument incorporates the basic specifications given in table 1.

### circuit

To achieve extremely high input resistance a special dual fet with exceptionally low gate-leakage current was chosen to form the heart of this instrument (see fig. 2). For maximum linearity and ac-

curacy the fet is combined with a high quality operational amplifier. The two are connected as a voltage follower with a gain of one. One important parameter of the op-amp is its very low power consumption. This results in truly low battery drain for the instrument as a whole, greatly prolonging battery life, reducing

operating expense and eliminating the annoyance of frequent battery replacement. The amplifier will handle an input voltage, without overload, of somewhat over 10 volts. When used within this range the input gate of the fet is connected directly to the circuit being measured. This mode of operation offers the highest input resistance obtainable from the amplifier. The only loading on the

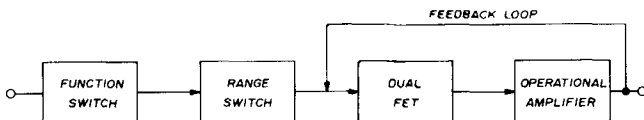


fig. 1. Block diagram of the high-impedance meter-interface unit. Instrument will solve dc measurement difficulties caused by circuit loading.

circuit being measured is the leakage current of the fet gate, this current being in the order of 0.2 picoamperes (0.0000002 microamps). Contrast this with the 50 microamps that a standard vom will draw, or the 0.1 microamps drawn by a vtm when measuring one volt full scale.


For measuring voltages in excess of ten volts a resistive voltage divider is necessary to keep the voltage level applied to the fet gate within its normal operating

table 1. Basic specifications of the high-impedance meter interface unit.

Dc input resistance, 0-10 volts	greater than 1-million megohms
Dc input resistance, 10 volts up	1000 megohms or greater
Supply voltage (battery)	± 22.5 volts dc
Current drain	500 $\mu$ A
Battery type	Eveready type 412
Battery life	295 hours, continuous usage
Accuracy, 0-10 volts	0.1% or better
Accuracy, higher ranges	depends on accuracy of dividers

curacy the fet is combined with a high quality operational amplifier. The two are connected as a voltage follower with a gain of one. One important parameter of the op-amp is its very low power consumption. This results in truly low battery drain for the instrument as a whole, greatly prolonging battery life, reducing

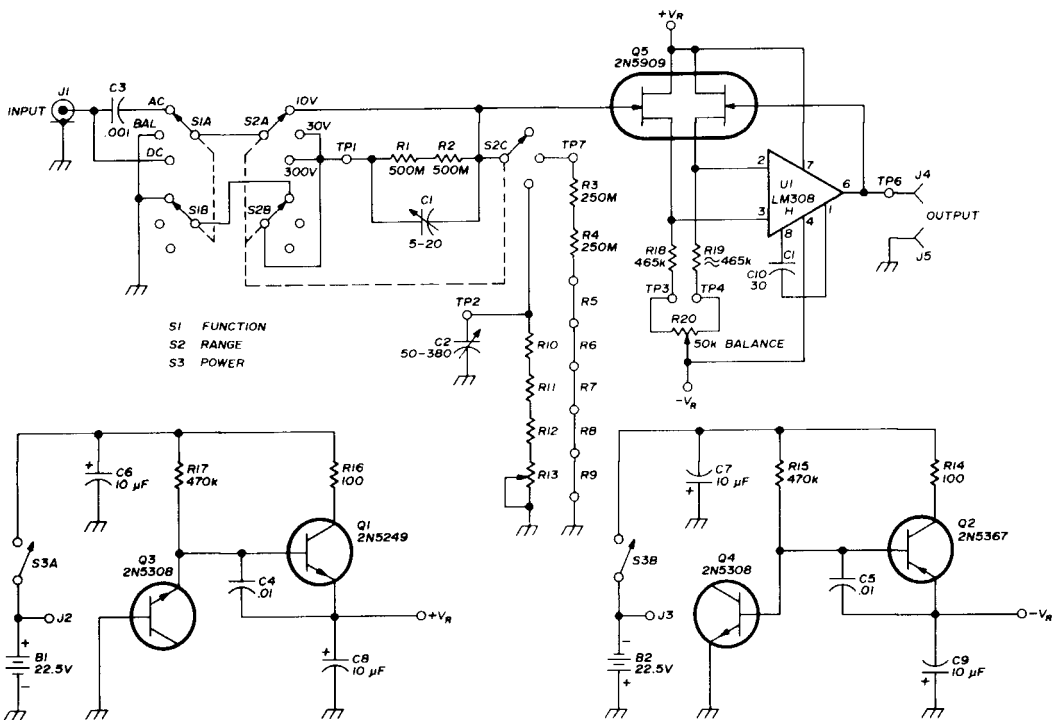range. This voltage divider necessarily reduces the input resistance of the amplifier. To minimize loading on the higher ranges a voltage divider with approximately 1000 megohms total resistance was chosen. Unfortunately, this is considerably lower than the intrinsic input resistance of the fet, as enjoyed on the



- |             |  |         |  |
|-------------|--|---------|--|
| C1          | 5-20 pF ceramic trimmer (Erie type 503). (Do not use a compression-type trimmer here.) | R13     | 2-3 megohm trimmer (Mallory 26L1 or 26L4)      |
| C2          | 50-380 pF compression trimmer (Elmenco type 465)                                       | R14,R16 | 100 ohm, 10% carbon                            |
| J1          | BNC connector (Amphenol UG-657/U)  | R15,R17 | 470k, 10% carbon                               |
| R1,R2       | to total 1000 megohms, 1% (matched pair)   | R18     | 465k, film-type preferable                     |
| R3,R4       | to total 500 megohms, 1% (matched pair)  | R19     | 465k, approximately (see text)                 |
| R5-R9       | values as required for balance (see text)  | R20     | 50k, 10-turn potentiometer                     |
| R10,R11,R12 | to total 33 megohms, 5%  | R21     | 220k, 10% carbon                               |
|             |  | S1      | 2-pole, 3-position ceramic wafer rotary switch |
|             |  | S2      | 3-pole, 3-position ceramic wafer rotary switch |
|             |  | S3      | dpdt toggle switch                             |

fig. 2. Schematic diagram of the high-impedance meter-interface unit. Three dc ranges are provided: 10, 30 and 300 volts; ac rms inputs are limited to 70% of dc range.

zero to 10-volt range, but it is still 100 times greater than the standard vtvm input resistance.

Although a higher value of resistance can be used in the divider network, this will cause degraded performance at higher operating temperatures. This brings up a point about fet gate leakage vs temperature — the gate leakage increases approximately 10 times for each 18°F increase in temperature. Hence, this instrument

should be kept cool (room temperature) for maximum input resistance on the zero to 10-volt range.

Two voltage regulators are used in the battery supply circuit. These were not put there because of a great need for supply regulation, although the regulation will certainly tighten drift specs some, but the primary purpose of the regulators is to allow use of battery voltage in excess of the voltage rating of the op-amp. The



absolute maximum supply voltage rating of the LM308H op-amp is  $\pm 18$  volts.

The closest available battery voltage that does not exceed this rating is a 15-volt unit. Use of a 15-volt supply would have placed the operating voltage of the amplifier uncomfortably close to the desired 10-volt input signal handling level. Of course, this 15-volt supply would have been the *starting* voltage of the battery and as the battery began to "droop" with usage the already uncomfortable margin would quickly become more narrow. A marginal situation like this would contribute to shortened battery service and danger of overload with normal input signal levels.

The input network consists of a resistive voltage divider with frequency compensating capacitors for better ac performance (frequency response), switching arrangement and blocking capacitor for ac amplification only, if desired. On the zero to 10-volt ac range the two 500-megohm resistors are switched from fet gate to ground. This provides the necessary dc path to ground for the fet gate, which otherwise would not exist due to the presence of the dc blocking capacitor, C3.

Resistors of the extremely high values used in this divider are not common stock items. Their procurement can be a real problem through standard channels. All of the resistors used here were supplied by the Resistance Products Company.\* This organization specializes in very high resistance products and can supply them in almost any tolerance desired. The parts list describes the type and part number of the resistors I used.

The actual total resistance of the resistive divider is not as important as the fact that it must be high and that the ratio between  $R1 + R2$  and the two ground legs must be close to that required for the proper division ratio. As used in this particular instrument, the voltage division ratios are 3:1 for the zero to 30-volt range and 30:1 for the zero to

300-volt range. This places the ratio between  $R1 + R2$  and the two ground legs at 2:1 and 29:1. For a 1000-megohm value for  $R1 + R2$  the zero to 30-volt ground leg is exactly 500 megohms. For the zero to 300-volt range the ground leg is 34.48 megohms.



The high-impedance meter interface instrument is built into a cast aluminum box, Bud type CU347.

The following is a general formula for figuring the resistance ratios for any voltage ratio:

$$\text{Resistance ratio} = E_{in}/E_{out} - 1$$

$$\text{Ground leg resistance} = \frac{R1 + R2}{\frac{E_{in}}{E_{out}} - 1}$$

These simple expressions will allow easy computation of resistors required for any situation.

The instrument described here was designed to be used primarily with a readout meter having scales ending in 10 and 30. Hence, the ranges of 10, 30 and 300. For meter scales different than the above, the ranges of the interface will undoubtedly need to be scaled to match.


### construction

The instrument is housed in a Bud Radio type CU347 cast-aluminum box. A good paint job with engraved legends will result in a professional appearance. The front panel must be drilled to accommodate the input jack, function switch, balance pot, range switch, power-on toggle switch, battery check jacks and out-

\*Resistance Products Company, 914 South 13th Street, Harrisburg, Pennsylvania 17104.

put terminals. Care should be exercised here to insure that the switches are not mounted too close to the edge so as to obstruct the case sides.

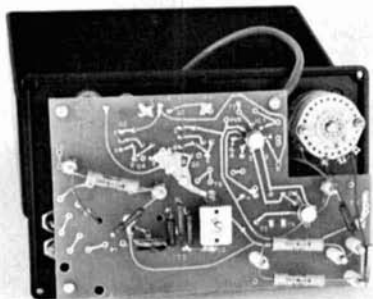The circuit board is mounted on standoffs 1.5-inch long. This provides adequate clearance between the board and panel-mounted items. Location holes for the standoff legs fall in the center of the



Most of the major components of the high-impedance interface unit are built on a printed-circuit board (see fig. 3). Switches, balance control and jacks are mounted on front panel.

small round mold marks on the inside surface of the front panel. Also, the circuit board can be used to dimension these holes. High quality Teflon standoff terminals were pressed into the circuit board to hold R1, R2 and R3. Input wiring was run point-to-point instead of bundling to reduce interwiring capacitance and leakage currents. Teflon wire was used throughout. Be certain to use only ceramic switch wafers on the range and function switches. The input jack should have a Teflon insulator.

Extra positions on the circuit board accommodate a number of resistors that may be connected in series to trim the exact value of the ground leg resistors in the voltage dividers. If quality resistors are purchased all of these positions will probably not be used.

Note. The circuit board contains pads for compensation components that are used on other types of micro power op-amps other than the LM308H shown in the parts list.

Here are some tips on placement of parts. The input gate is not connected to a board mounted pad but to a Teflon standoff. Room was provided on the board to accommodate very long resistors for R1 and R2. Some of these may be found surplus or purchased as replacements for elements in high-voltage probes. If short resistors are used as suggested in the parts list the standoffs will have to be positioned closer to the fet.

After mounting R1 and R2, C2 may be soldered directly to the standoffs holding these resistors as shown on the parts location diagram. When mounting the fet, Q5, be certain to form the leads so that they enter the proper pads on the board without shorting to each other. If the 2N5909 is used as suggested, the legs will not fall directly into the proper pads.

After completion of all wiring, the circuit board and all standoffs and switch wafers should be thoroughly cleaned with alcohol (pure) to remove all trace of rosin, fingerprints or other contaminants. The high megohm resistors should be cleaned also as their value can be significantly altered by contaminants on their surface.

### checkout

First, measure battery drain imposed on each battery. This current should be approximately 0.5 mA. Significantly higher currents indicate trouble and should be investigated before proceeding.

The output voltage of the regulators should be measured. This voltage level will vary but will usually fall between 15 and 18 volts. If higher than 18 volts, the cause should be found and steps taken to bring it to normal.

With the function switch in the *BAL* position, check to see if the balance control will vary the output + and - by approximately the same amount. Normal variation is around  $\pm 50$  millivolts.

On the 10-volt range, dc input voltages both, + and -, should be reproduced exactly at the output up to the overload point. Overload will normally occur at about 1 or 2 volts below the supply

voltage. Millivolt differences between input and output can be adjusted to zero with the balance control.

The two higher ranges should be checked, and trimmed if necessary, for accurate voltage division ratios. This procedure calls for an accurate and linear readout standard.

Input resistance levels as encountered

checking the ac characteristics of the interface. Stray capacitance plays an important role in the frequency response of the instrument. Consequently, the trimmer capacitors C1 and C2 must be adjusted a little at a time and the instrument put into its cabinet after each adjustment to note the effect. There is no adjustment necessary for the 10-volt range.

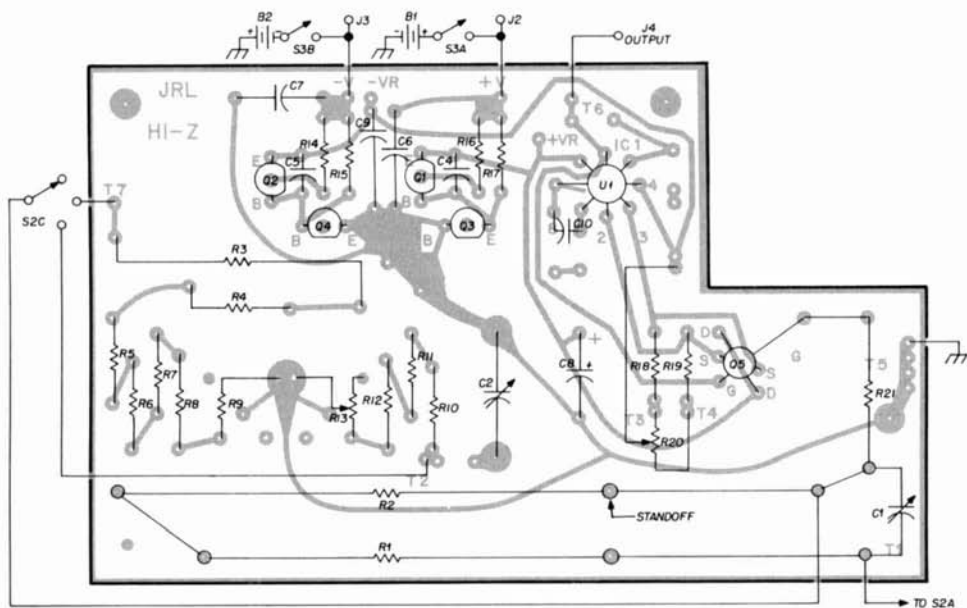


fig. 3. Printed-circuit layout for the high-impedance meter-interface unit.

here are difficult to measure with standard equipment. A simple check to demonstrate the high input resistance is to connect a standard 10-megohm vtvm in series with a 10-megohm resistor and apply a voltage to the series combination. Note the voltage reading on the vtvm; it should be approximately half the supply voltage. Now, alternately connect and disconnect the high-impedance interface to the probe of the vtvm while noting the change in reading of the vtvm. The 1000-megohm input resistance of the two higher ranges should cause only about a 1% change in the reading of the vtvm. The input resistance of the 10-volt range should cause no noticeable variation in the vtvm reading.

An audio oscillator is needed for

The simplest method of adjustment can be accomplished by feeding a 100-Hz square wave into the instrument and adjusting C1 on the second range for best response with the instrument in the cabinet. Next, C2 is adjusted with the range switch on the highest range for best square wave response, with the instrument in the cabinet. Be certain that your oscilloscope has sufficient response to exactly reproduce the square wave as it comes out of the generator.

If only a sine wave oscillator or a 60-Hz source is available, the adjustments can be made so that exact reproduction of the input amplitude occurs at the output terminals with the instrument in the cabinet.

ham radio

# IC logic families

A rundown on  
popular logic  
circuits, their  
interfaces, and  
compatibility

The use of the Fairchild  $\mu\text{L914}$ , and other members of the resistor-transistor logic (RTL) family, is well documented in the amateur radio periodicals. The Fairchild  $\mu\text{L900}$ ,  $\mu\text{L914}$ , and  $\mu\text{L923}$  (all from the RTL family) were the first digital integrated circuits to be offered in low-cost epoxy packages. An early article by Lancaster<sup>1</sup> pointed the way for many other experimenters, and for years RTL

was the most-used logic family among hams. A number of other firms rushed into production of RTL to "second-source" these popular ICs; all but several of them dropped out of the competition in a year or two. Motorola went Fairchild one better — offering an expanded RTL family in plastic dual-inline packages (DIP). Some of these plastic DIPs are also offered as part of the Motorola HEP line, which are more easily obtained than most other ICs. The HEP line also has RTL ICs in the TO5 metal can package.

The following selection guide should be helpful when planning your next project using ICs. A brief description is given of seven popular logic families together with information on interchangeability and compatibility. Additional data on device details and applications is available from the manufacturers mentioned.

## RTL logic

Although RTL is widely used in ham circles, and also fairly inexpensive, it has some limitations. RTL is a relatively slow form of logic. While some members of the family are rated up to 8 MHz, the family is not usually used above 1 or 2 MHz — especially the low-power versions. RTL requires a supply voltage of 3.6 Vdc at relatively high current. A modest logic array of RTL devices can often require

Hank Olson, W6GXN, Stanford Research Institute, Menlo Park, California 94025

several amperes. RTL has poor noise immunity, the level of ripple or transients on the power supply bus above which false triggering can occur. This low ripple limitation, together with the large current requirement, can make the power supply quite expensive.

The nice features of RTL, other than economy, are the ease of understanding and durability in the hands of the beginning electronic logician. As such, it is no wonder so many technical people cut their teeth on RTL. Fig. 1 shows an RTL two-input gate; it is similar to one-half of a  $\mu\text{L914}$  or HEP584. This circuit could also be built of discrete components — say a pair of 2N708s, a 470-ohm resistor, and two 620-ohm resistors (to use standard components).

**Operation.** If both inputs are grounded (or open circuited), no current will flow in either transistor, and the output voltage level will be at +3.6 V. Now, let input 1 be raised to +2.2 V. This will forward-bias Q1, the 450-ohm load resistor will conduct current, and the output voltage will drop. Assuming the base-to-emitter drop to be 0.6 V, that puts 1.6 V across the input resistor: base current =  $1.6\text{V}/640\text{ ohms} = 2.5\text{ mA}$ . This amount of base current is more than enough to saturate Q1, and output will drop to nearly ground level, say to +0.5 V. If we now make input 2 rise to +2.2 V, little change in the output will occur. So, if input 1 or input 2 is high, the output will be low.

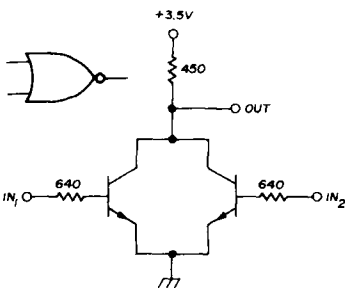


fig. 1. RTL 2-input NOR gate.

We will now define high as 1 (or true) and low as 0 (or false). Then, looking at our RTL gate we can say that if input 1 or 2 is 1, the output is 0. Since the output gives a false output to either of two true inputs we must call this gate a NOR gate (short for NOT-OR). Similarly, an inverter, as shown in fig. 2, is sometimes called a NOT gate. Such a NOT gate is contained in a Motorola MC789P, hex inverter (there are six in one package).

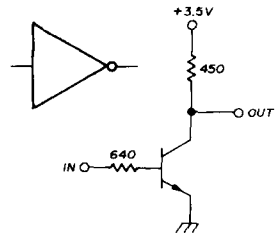


fig. 2. RTL inverter (NOT) gate.

By combining a NOR and NOT circuit we have an OR, as shown in fig. 3A. The output is 1 (true) if either input 1 or 2 is 1 (true). Similarly, by using a NOT gate ahead of each of the two inputs to the NOR gate, we can form an AND. This is shown in fig. 3B. The output is 1 (true) if both input 1 and input 2 are 1 (true).

A NOT gate can be made using a two-input NOR gate by simply grounding one of the two inputs. Therefore, all of the circuits thus far described can be constructed using one or more sections of  $\mu\text{L914}$  gates. If one wanted just one NOT, NOR, or OR function, the  $\mu\text{L914}$  would be the least expensive way of implementing it. Similarly, if just one AND function is desired, an MC724P is the cheapest way to build it. However, in larger systems (where a number of IC packages are used) gates are not usually used as inverters, since a hex inverter costs about the same as a quad two-input gate.

Although they are not usually drawn that way in logic diagrams, any of the several flip-flops can be made up of gates.

Fig. 4 shows how a number of flip-flops are made up, along with their usual logic circuit symbols.

**Load factor.** One of the nice features of IC logic is the simple system of fan-in and fan-out numbers that most manufacturers provide. In RTL, the Fairchild and

otherwise the transition circuitry can be built using discrete components.

## DTL logic

Historically, diode-transistor logic (DTL) comes right behind RTL as an IC. However, DTL was extensively used as a logic form in discrete circuitry before ICs

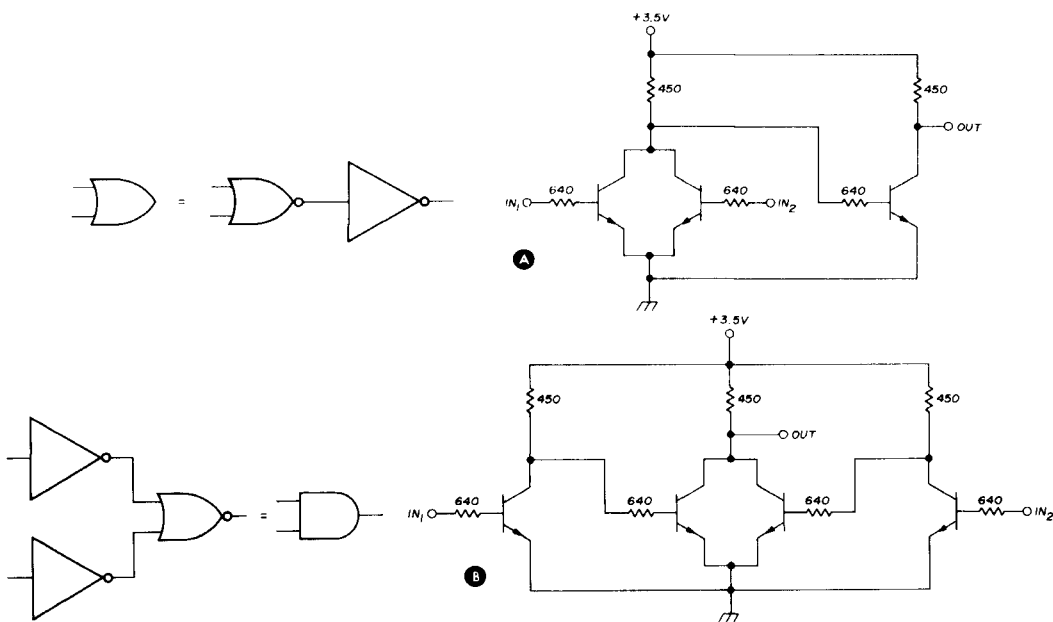


fig. 3. RTL OR gate (A) and AND gate (B).

Motorola fan-in and fan-out numbers are compatible. A fan-in of 1 is the loading that a low-power gate ( $\mu\text{L}910$ , say) puts on whatever is driving it. The fan-out is the number of such gates (as loads) an IC is capable of driving. For instance, the fan-out of a  $\mu\text{L}910$  is 4; it can drive one input of another  $\mu\text{L}910$  plus one input of a  $\mu\text{L}914$  (fan-in of 3).

These load factors apply only within the RTL family, however, and more care must be exercised when trying to interface RTL with other logic families. This is not just an academic problem — say getting from an RTL system into a TTL system — because field requirements often place unlike pieces of apparatus together. Fortunately, there are a number of family-interface ICs available, and

were developed. It is common to find old logic systems full of cards of 2N404s and 1N658s still in use in pieces of discrete DTL systems. Of course, all of the components on one whole card of such a system could be replaced today by one IC — less expensively! Such a discrete DTL gate is shown in fig. 5.

**$\mu\text{L}930$  family.** Usually, when one speaks of DTL, the  $\mu\text{L}930$  family is meant. There are a number of other DTL families around, but they are the “losers” in the industry-wide acceptance game. Like the  $\mu\text{L}900$  (RTL) series, Fairchild also originated the  $\mu\text{L}930$  (DTL) family.

In the  $\mu\text{L}930$  series, there are no round can packages available in plastic, although they are fairly common in

round metal can packages. The round metal can package is often referred to as TO5 because the can size is the same as that of a TO5 (three lead) transistor. While most round metal can ICs have 8, 10, or 12 leads and so cannot strictly be called TO5, the TO5 can description has been widely given to them. DTL is also

**Current-sinking logic.** Fig. 6 shows a DTL gate ( $\frac{1}{4}$  of  $\mu\text{L946}$  or MC846P). Note that both inputs are via diodes, which might at first look as though they are connected backward. Fear not, the diodes are shown correctly, because we must draw current out of the input when using this sort of logic. For this reason DTL is called

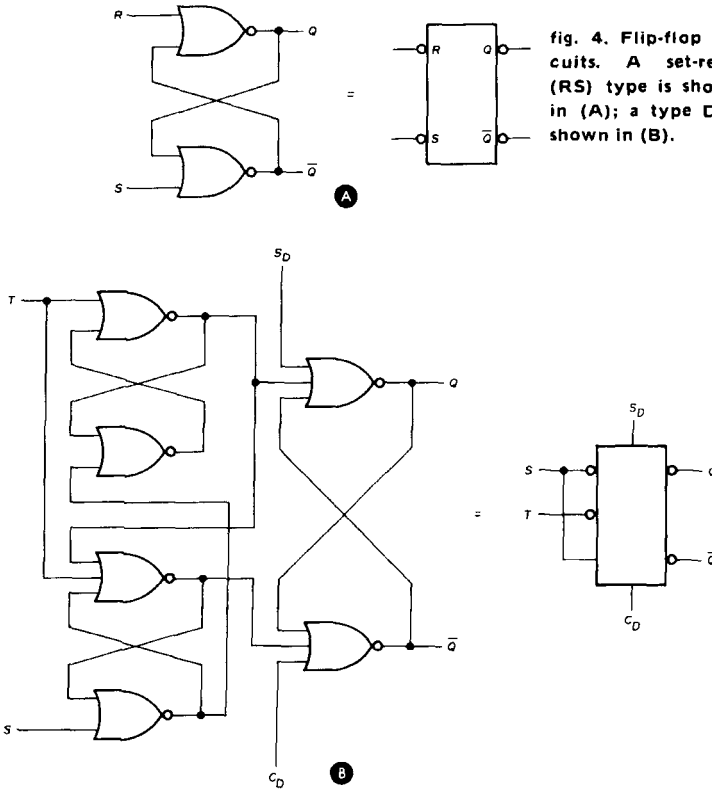


fig. 4. Flip-flop circuits. A set-reset (RS) type is shown in (A); a type D is shown in (B).

available in the dual inline package (DIP) both in plastic and ceramic, and in the ceramic flat-pack.

Amateur DTL users will probably be most interested in the plastic DIP form of DTL, but often the other styles are offered as surplus at low prices. In an earlier article, I showed how to use surplus flat-pack  $\mu\text{L930}$ s and  $\mu\text{L946}$ s in an amateur wind-direction indicator.<sup>2</sup> Of course, the flat-pack style IC is not limited to DTL; nearly all logic families use it for their MIL-spec package.

current-sinking logic. (We will see that some other forms of logic are also current sinking as we go on.)

Unlike RTL, if a DTL gate has its inputs left open, the transistors in it are conducting, and the output is low or zero. Also, for positive logic, a simple DTL gate is called a NAND gate. When input 1 and input 2 are high (or open) the output is low. By following the gate of fig. 6 with an inverter (such as 1/6 of an MC836P) we create an AND gate, as shown in fig. 7.

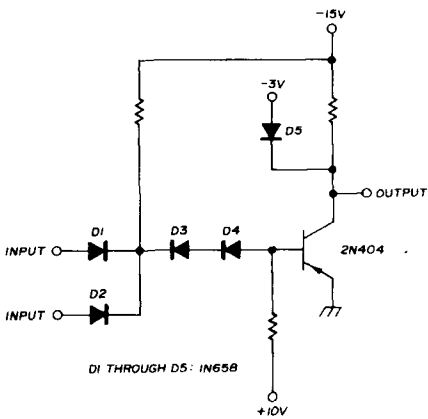


fig. 5. A DTL 2-input NAND gate using discrete components.

Similarly, by preceding each input of the NAND gate of an inverter, we create an OR gate, as in fig. 8. Note that this arrangement is just the opposite of the way we made the OR and AND functions with an RTL-NOR gate.

### TTL logic

Transistor-transistor logic (TTL or T<sup>2</sup>L) is a newer form of current-sinking logic. TTL was born in the IC age and has no discrete equivalent. A typical TTL two-input gate is shown in fig. 9. Note that the input transistor has two emitters. Each of these emitters acts much as one

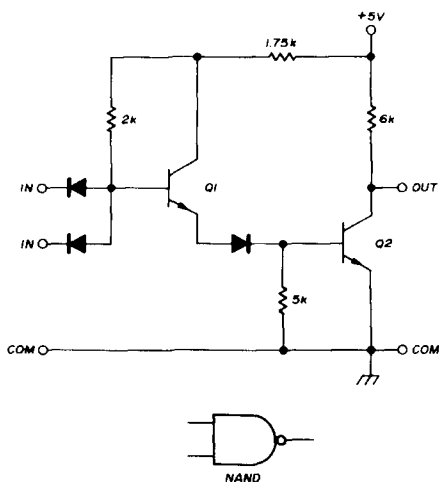


fig. 6. Example of current-sinking logic using 1/4 of an MC846P DTL gate.

of the input diodes in a DTL gate to control the single input transistor.

Since TTL is also a current-sinking logic, and also operates on  $V_{cc} = +5V$ , the logic levels are compatible with DTL. In general, TTL is faster than DTL, which imposes some restriction on the mixing of the two families, but at lower speeds they are compatible.

There are five major TTL families on the market today: Texas Instruments SN7400N, Sylvania SUHL, Fairchild TT $\mu$ L9000, Motorola MC3000-4000, and Signetics DCL.

**SN7400N and variations.** The SN7400N line was originally produced by Texas Instruments, but most of this line is second-sourced by other firms. There are about 200 members of the SN7400N series, and many more variations.

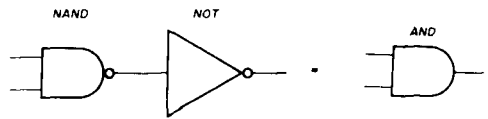


fig. 7. Formation of an AND gate using a NAND gate and an inverter.

tions are SN7400, SN5400N, and SN5400. The SN7400N is a plastic dual-inline package, SN7400 is a ceramic flat-pack, SN5400N is a plastic dual-inline package with MIL temperature specs, and SN5400 is a ceramic flat-pack with MIL spec temperature ratings.

In addition to the plastic dual-inline package, if one changes the N to a J at the end of the device number, the dual-inline package becomes ceramic. Further, if one puts an L between the SN74 and the next 2 or 3 digits, one gate is a lower-power version. If one puts an H in that same position, he gets a high speed version; and if an S is inserted, the ultra-high-speed Schottky version is specified that will toggle to 100 MHz. This method of variation is quite logical and creates a large variety from which to choose.

**Design considerations.** So that the electronic designer can "shift gears" when



adapting older DTL systems to TTL, Texas Instruments has devised a dual nomenclature system. Thus a quad 2-input gate is called both SN7400N and SN74-846N, so that the designer knows it has pin-for-pin compatibility (in addition to logic-level compatibility), which enables him to substitute SN7400N logic for  $\mu$ L930 logic on an etched circuit board with no changes (in many cases). Further, since TI also makes the  $\mu$ L930 DTL line, a family-to-family fan-in, fan-out number system is available.

In general, DTL can drive 8 DTL loads or 5 TTL loads; TTL can drive 10 TTL loads or 10 DTL loads. The DTL equivalent of the SN7400N, SN74-846N is (sensibly) the SN15-846N, for instance, if one is specifying TI parts. The L, H, and S versions of the SN7400N family (low power, high speed, and Schottky-clamped, respectively) are not as numerous as the standard series units, nor are they widely second-sourced.

In general, all the TTL families are compatible with each other (and with DTL). Details and pin arrangement are the biggest differences, but then details must be observed even when one is designing within one logic family.

### HTL logic

A special variety of DTL used with higher supply voltage than the  $\mu$ L930

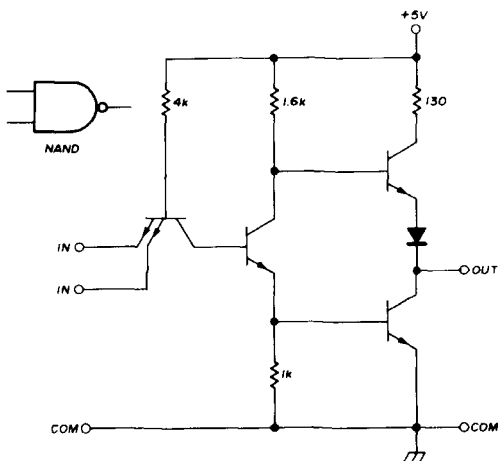


fig. 9. Typical 2-input TTL NAND gate consisting of  $\frac{1}{4}$  of an SN7400N.

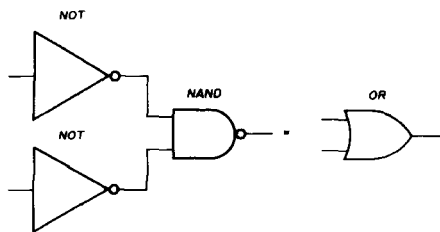


fig. 8. NAND gate inputs preceded by inverters equals an OR gate.

DTL is HTL (high-threshold logic). This family is, strictly speaking, offered only by Motorola, but HNIL (high-noise immunity logic) by Amelco Teledyne is essentially the same, as is HLLDT $\mu$ L (high logic level diode-transistor micro-logic) by Fairchild. These families all have the standard multiple diode inputs of DTL as shown in fig. 10.

Comparing fig. 10 with fig. 6, we see the really important difference between these two DTL forms: the diode coupling Q1 and Q2 in fig. 6 is replaced by a zener in fig. 10. This causes the HTL to have a much larger noise immunity. For this reason, HTL is often used in systems that contain electrically noisy components like relays and brush-type motors.

If we stick to  $V_{cc}$  of 12 to 15 volts, all these high-level families are compatible. The HNIL line will not operate above +15 V, however, as will the Motorola and Fairchild versions. All these HTL families have interface units available. Amelco and Motorola level-shift units will interface (either way) with DTL/TTL or RTL. The Fairchild level-shift units will interface only with DTL/TTL (either way).

### ECL logic

Emitter-coupled logic (ECL) is the only bipolar IC logic form that does not use transistors that flip between the nonconducting and saturated states. This nonsaturated logic, also referred to as current mode logic, was pioneered by Motorola. Motorola has produced four series of MECL (Motorola emitter-coupled logic): MECL I, MECL II, MECL III, and MECL 10,000. MECL I operated at speeds up to 30 MHz, MECL II

operated at speeds up to 120 MHz, MECL III operates up to 350 MHz, and MECL 10,000 has lower power consumption but speed similar to MECL II and III. MECL I and II are second-sourced by Stewart Warner in pin-for-pin equivalents. RCA,

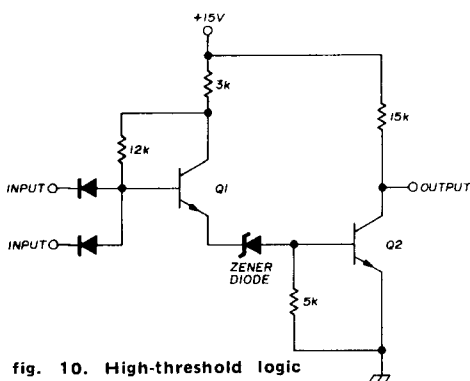


fig. 10. High-threshold logic (HTL) gate.

Fairchild, and Texas Instruments also offer their own lines of ECL, which have logic levels compatible with the Motorola family.

The curious thing about ECL is that the  $V_{cc}$  lead is usually grounded and the  $V_{ee}$  lead operated at -5.2 volts, yet ECL uses positive logic. Having the ECL units operating below ground makes ECL and other logic families awkward to operate together, because of the requirements for both positive and negative power supplies.

There are several logic-level translators available to interface ECL and DTL/TTL. MECL I has the single translators MC317 and MC318; MECL II has the single-level translators MC1017 and MC1018 plus the quad translator (MECL to DTL/TTL only) MC1039. There are no MECL III translators because there are no saturated IC logic families that can operate at speeds above about 100 MHz.

An ECL gate is shown in fig. 11; note  $R_e$ , the emitter resistor, from which the logic derives its name. The basic ECL gate is a differential amplifier, with the base of Q2 referenced to -1.15 volts. Since this differential pair is used in logic applications, either Q1 or Q2 is on. Since ECL

uses positive logic (as do the other logic families we've already looked at), 1 = -0.75 V and 0 = -1.55 V. If either Q1 or Q1' are in the 0 condition, then RC2 draws all the current. In either case, the total current drawn by the pair is nearly constant.

Since there are two outputs in opposite states, this form of logic gate offers both NOR and OR functions as a basic part of its circuit. This feature is quite useful and can save the addition of extra inverters.

As seen in fig. 11, each output has an emitter follower built in to provide better fan-out. The typical fan-out of ECL is 15, which is considerably larger than most other logic families. Because fan-out from standard ECL units is so large, no buffer gates are offered. Fig. 12 shows a Motorola MC306G in combination with a Motorola MC304G bias driver. The bias driver is simply a source of regulated reference voltage.

In the MECL II, III, and 10,000 lines, the bias driver is built into the gate chip, so no external source of  $V_{bb}$  is needed. Also, since the bias driver is built in, and the units are available in a plastic DIP, MECL II is generally less expensive than MECL I.


## MOS logic

Another category of IC logic is the metal-oxide semiconductor (MOS). I avoid calling MOS a family, because no one company's MOS catalog has an industry-wide acceptance. The result of the absence of a dominant MOS logic family is chaotic — every company has its own particular idea as to what process makes the best chips.

There are some general things that can be said about the various MOS ICs, however. Most of them operate on a negative  $V_{dd}$  of -10 V to -40 V, therefore having negative logic (where 0 = 0 volts and 1 = a more negative voltage). They are generally slower than bipolar ICs and are well adapted to large-scale integration (LSI) because of the ease of getting a large number of MOS circuits per unit area on the chip.

Because MOS is so well adapted to LSI, wherein we are talking of hundreds or thousands of gate sections per chip, and because no dominant MOS family has emerged, we find that MOS is mostly available as large arrays, such as memories. A few companies, like Fairchild, offer individual logic circuits such as 3-input gates, 5-input gates, and dual flip-flops as building blocks. That is, these building blocks are offered specifically

fig. 11. Emitter-coupled logic (ECL) gate.

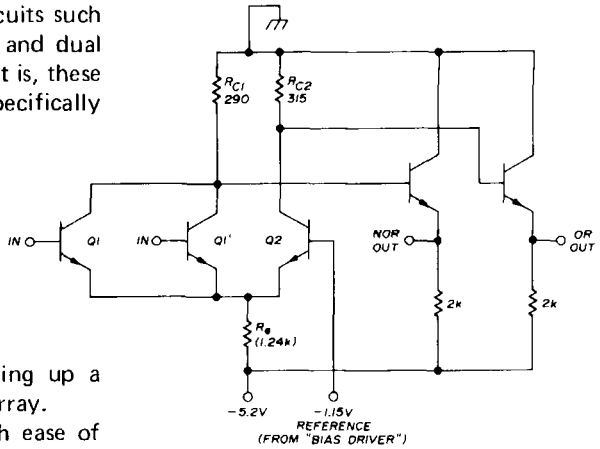

for the engineer who is mocking up a breadboard for a custom-made array.

One reason MOS offers such ease of LSI construction is that all the elements on the chip are tiny fets. Some are used as resistors and some as fets, but all are similar types. As an example, fig. 13 shows a Fairchild 3102 three-input gate and how it can be used as a NOR gate, NAND gate, or how two units can form an RST (set-reset) flip-flop. The cost of the 3102 is \$6.00 compared with an SN7410N triple 3-input gate at \$0.60 (TI-TTL). It's no wonder MOS isn't used for small logic systems, since the cost per gate is quite high. However, in an LSI array the cost per gate can drop to pennies in production quantities.

**CMOS logic**

A new type of MOS logic that's gaining industry-wide acceptance is complementary MOS (CMOS). While conventional MOS logic owes its existence to the fact that many gates can be placed on one small chip, CMOS doesn't offer this advantage to as large a degree. The main selling point of CMOS is that it offers nearly zero standby power, the power drawn when the logic is in the 1 or 0 state. CMOS essentially draws current only during a transition from a 1 to a 0 or vice versa.

So, for logic systems that require low

power, especially when fairly low data rates are to be handled, CMOS is very attractive. RCA was first to offer CMOS units, but now Motorola and others are also in the business, and the prices of these very fine logic ICs are likely to

approach those of TTL as volume use develops.

CMOS operates on +5 to +15 V, as opposed to MOS, which operates on generally larger negative voltages. The +5 to +15 V supply voltage means that it's a simple task to interface CMOS with DTL, TTL, or HTL.

Fig. 14 shows a CMOS gate; note that it has in it both P-channel and N-channel mosfets. Like conventional MOS logic, the mosfets in CMOS logic are enhancement-mode types. This means they are like zero-bias triodes; they are non-conducting until the gate (grid) is forward biased. Enhancement-mode N-channel mosfets have been almost nonexistent as

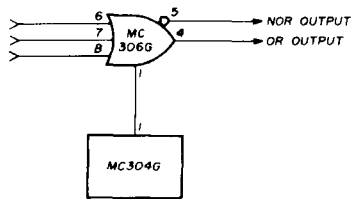


fig. 12. The MC304G bias driver provides a regulated reference voltage source for an MECL gate.

discrete devices, which is probably why CMOS has become available only recently — i.e., a whole new MOS technology has had to be developed.

### conclusion

We have looked at a number of logic

been made in reference to ICs specifically made for family interfacing. The interfacing of RTL with DTL or TTL is fairly easy. My own preference is to use a  $\mu\text{L900}$  (RTL buffer) to drive DTL or TTL from RTL. Driving RTL from DTL or TTL is usually direct; most DTL or

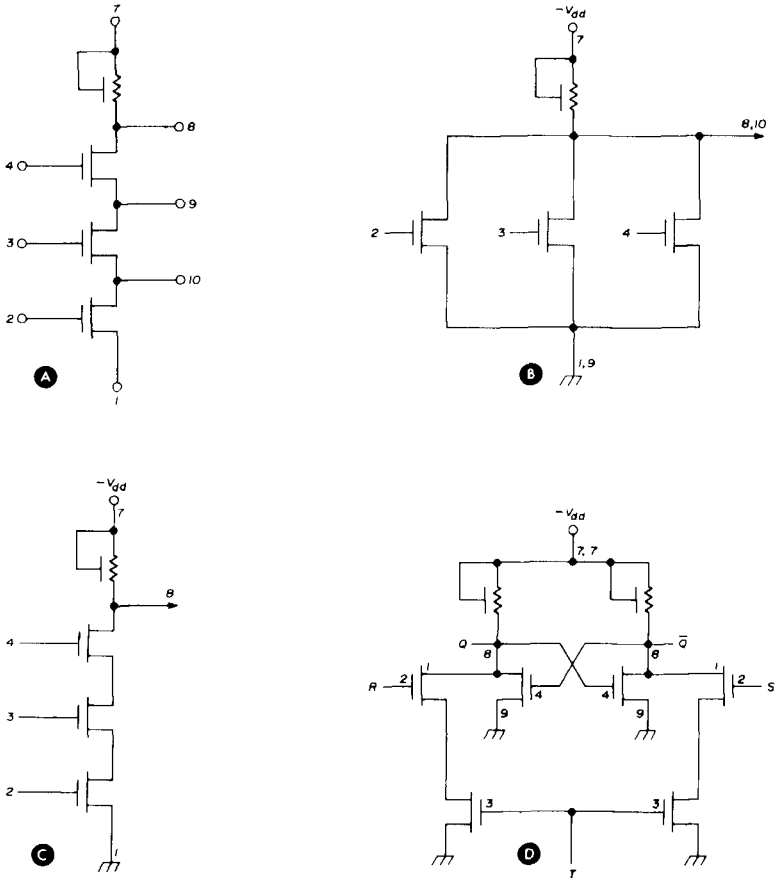


fig. 13. Fairchild 3102 3-input gate (A). A NOR gate, NAND gate, and RST flip-flop are shown in (B), (C) and (D).

families I feel are either common enough or inexpensive enough that amateurs will be likely to use them. There certainly are other logic families, which have been left out, because my intent was to present only the mainstream of IC logic; not the rare, expensive, or unique.

One often perplexing problem remains: that of interfacing logic families. Some comments on this have already

TTL gates will provide enough voltage output to drive an RTL IC.

Interfacing ECL and DTL/TTL has been mentioned in the discussion of ECL. As expected, the same interface ICs that drive DTL/TTL from ECL are also useful to drive RTL from ECL. The usual case is not to drive ECL from the lower-speed logic families (RTL, DTL, and TTL). The units that drive DTL/TTL and RTL from

ECL are MC317, MC1018, and MC1039. An example of the use of the MC1018 to convert between ECL and RTL is shown in reference 3.

There is even a readily available way to interface ECL and HTL. Motorola outlined this method at the 1969 series of digital integrated circuit seminars, using the MC1580. The method is shown in fig. 15.

The directly available DTL/TTL to HTL and RTL to HTL interface ICs have been mentioned in the discussion on HTL. These interface ICs can also be useful to drive some types of digital readout devices from RTL, DTL, or TTL.<sup>4</sup>

As pointed out in the discussion on MOS, there is no dominant MOS family yet; and so the interfacing of MOS with other logic forms is equally obscure — if not more so! In most cases the so-called bipolar-to-MOS interface circuits concentrate on converting the magnitude of shift from 0 to 1 and ignore the absolute values. This usually means that one ends up with the  $V_{SS}$  of the MOS portion of

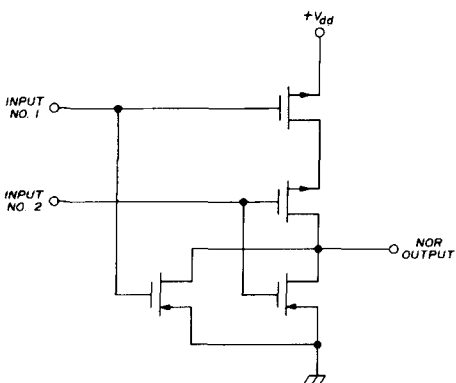


fig. 14. Complementary metal oxide semiconductor device (CMOS) 2-input NOR gate.

the circuit operating at +5 volts (when interfacing MOS and TTL) instead of at ground.

The interface may be constructed of discrete components as in reference 5. Several companies offer hybrid ICs that are quite similar to discrete-wired inter-

face circuits, which are quite expensive compared to monolithic ICs.<sup>6,7</sup> Fairchild has a pair of ICs available that convert nicely from TTL/DTL to MOS or MOS to TTL/DTL; these are respectively 9624 and 9625. Texas Instruments also makes a rather versatile IC called the SN75450,

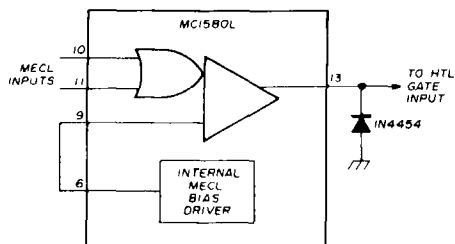


fig. 15. Interfacing MECL and HTL logic using an MC1580L.


which will interface MOS with TTL or vice versa. It requires a few external components, but it is very flexible.<sup>8</sup>

We've covered RTL, DTL, TTL, ECL, HTL, MOS, and CMOS families of IC logic in a sort of whirlwind fashion. Many logic ICs may also be used in circuits that are, strictly speaking, not logic functions, such as crystal oscillators. Many of the companies point up these uses in their data sheets, application notes, and handbooks.

#### references

1. D. Lancaster, "Using New Low Cost Integrated Circuits," *Electronics World*, March, 1966, page 50.
2. H. Olson, W6GXN, "Digital Wind Direction Indicator," *ham radio*, September, 1968, page 14.
3. F. Cody, "A 50-MHz Digital Counter," *Electronics World*, March, 1969, page 40.
4. H. Olson, W6GXN, "The 7-Segment and Cold-Cathode Displays," *Electronic Products*, January, 1970, page 120.
5. J. Karp, "Bipolar/MOS Interface Circuits and Techniques," Philco Application Note No. 403, January, 1968.
6. Philco, "MOS Clock Driver, PH0007," Data Sheet 470-10, April, 1970.
7. MEPCO, "DTL/TTL to MOS Level Shifter," Spec Sheet MC6-669M.
8. Texas Instruments, "Systems Interface Driver SN75450," Texas Instruments Spec Sheet DL-S7011342, June, 1970.

ham radio

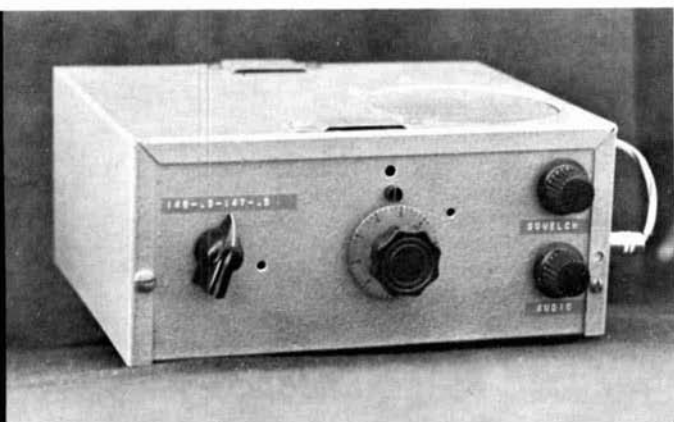

## compact package for two-meter fm


Design and  
construction details  
for a low-power  
fm transceiver  
for 144 MHz

J.H. Ellison, W6AOI, Menlo Park, California 94025

This article describes a compact package containing a low-power two-meter fm transmitter and a double-conversion, continuous-tuning fm receiver suitable for either fixed or mobile use. Although this description is primarily directed at the homebrew builder who balks at the cost of commercial equipment but lacks the time to develop his own design, the unit also includes several features which can be worked into different designs. The entire package, including everything but the power supply, is housed in a cabinet which is small enough to be accommodated in any automobile.
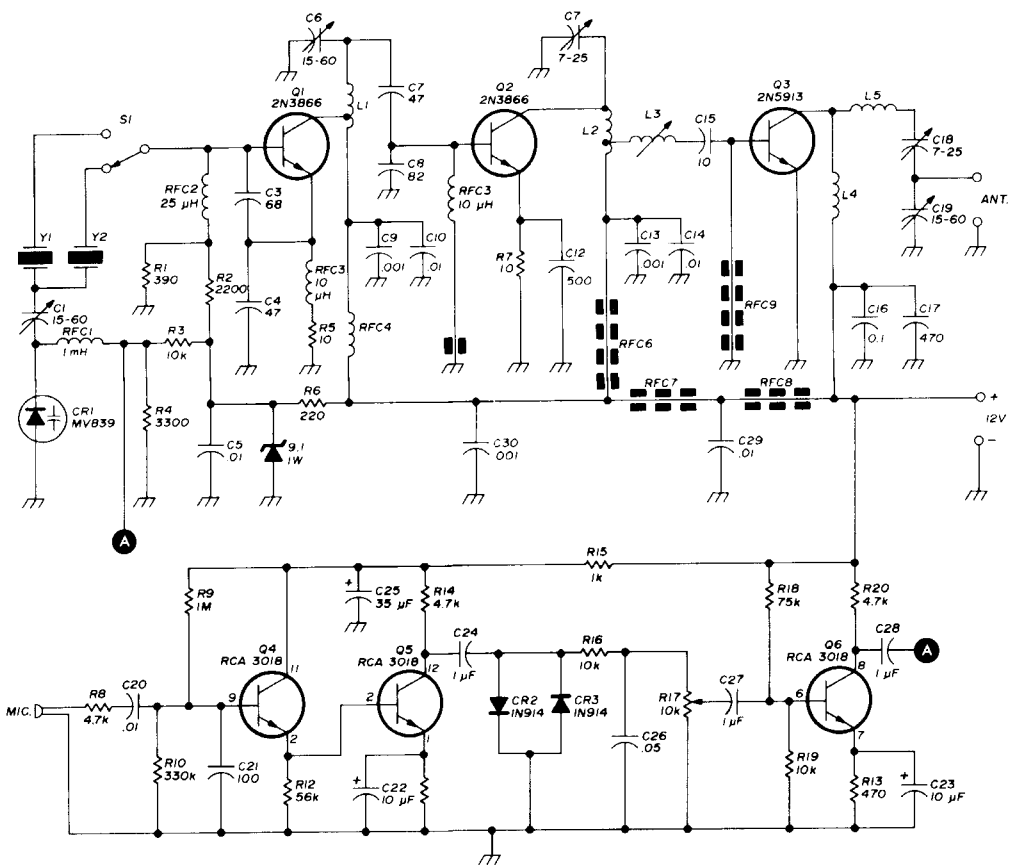
### transmitter

Because this project is a combination of a previously described transmitter and an original receiver, design of the transmitter will be discussed first, and only with regard to certain minor changes and its performance. The transmitter is the Pip-Squeak, Mk II, described by WICER.<sup>1</sup> The complete schematic is shown in fig. 1 for reference to the



- |    |  |        |  |
|----|--|--------|--|
| L1 | 5 turns no. 16 tinned bus wire, 1/4" ID, 5/8" long, tapped at 2 1/2 turns        | L5     | 5 turns no. 16 tinned bus wire, 5/16" ID, 1/2" long  |
| L2 | 3 turns no. 16 tinned bus wire, 1/4" ID, 3/8" long, tapped 1/2 turn from C13 end | RFC6   | 4 Amidon ferrite beads on 1/2" length of no. 24 wire |
| L3 | 4 turns no. 22 enamelled wire, closewound, 1/4" ID                               | RFC7   | 3 Amidon ferrite beads on 1/2" length of no. 24 wire |
| L4 | 25 turns no. 28, closewound on body of 100k, 1-watt resistor                     | Y1, Y2 | 18-MHz crystal ground for 20-pF load capacitance     |


fig. 1. Schematic for the two-meter fm transmitter. Transistors Q4, Q5 and Q6 are part of an RCA CA3018 IC.

changes mentioned above. In this circuit transistors Q4, Q5 and Q6 are part of an RCA CA3018 IC. Two 1N914 diodes should be used for symmetrical clipping rather than using the emitter-base junctions of transistors within the CA3018 IC.

When building the unit, RFC5 and RFC9 should be placed on the foil side of


the PC board. Emitter resistor R7 should consist of two 1/4-watt resistors in parallel, dressed flat against the board for best stability. For further construction details, refer to the original article.

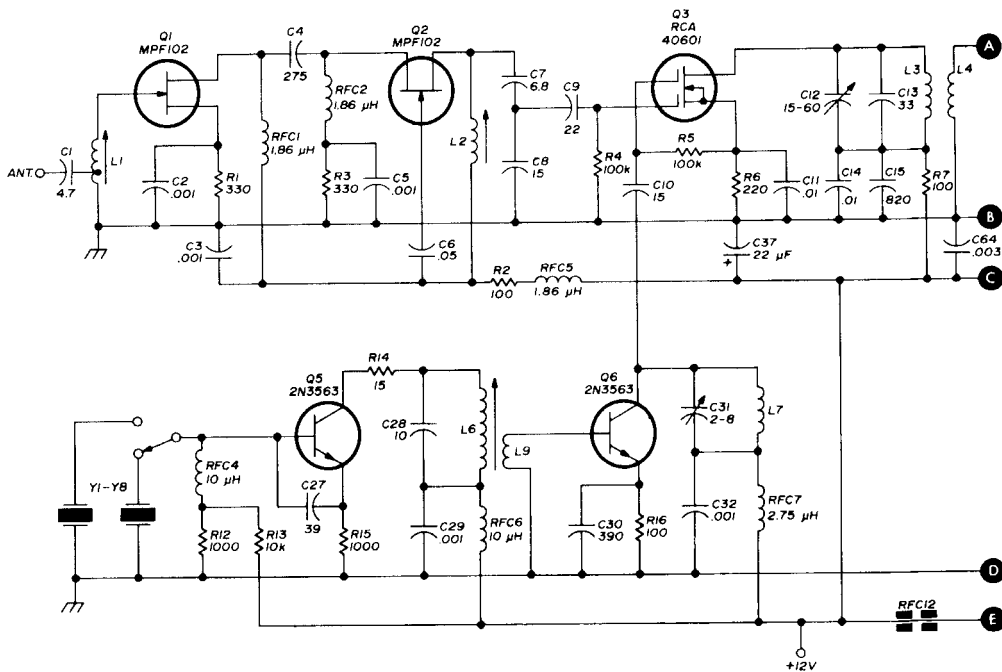With these simple circuit changes, performance was easily duplicated in another transmitter which I built for a friend. The power output with a 12-volt power sup-




- |       |   |                       |   |
|-------|---|-----------------------|---|
| L1,L2 | 5 turns no. 20, 1/4" ID, 1/2" long  | L8                    | 14 turns no. 32 closewound on 13/32" slug-tuned ceramic form (Millen 69041) |
| L3,L4 | 23 turns no. 30, closewound on 0.219" ceramic form (no slug), 1/4" between windings | L9                    | 2 turns no. 30 wound over cold end of L6                                    |
| L5    | 38 turns no. 30 wound on 0.375" toroid core   | L10,L11, L12,L13, L14 | 28 to 60 μH (J.W. Miller 9054)  |
| L6    | 11 turns no. 28, closewound on 0.219" ceramic form                                  | RFC12                 | 2 ferrite beads   |
| L7    | 6 turns no. 20, 1/4" ID, 1/2" long  |                       |   |

fig. 2. Tunable, continuous-coverage receiver for two-meter fm.

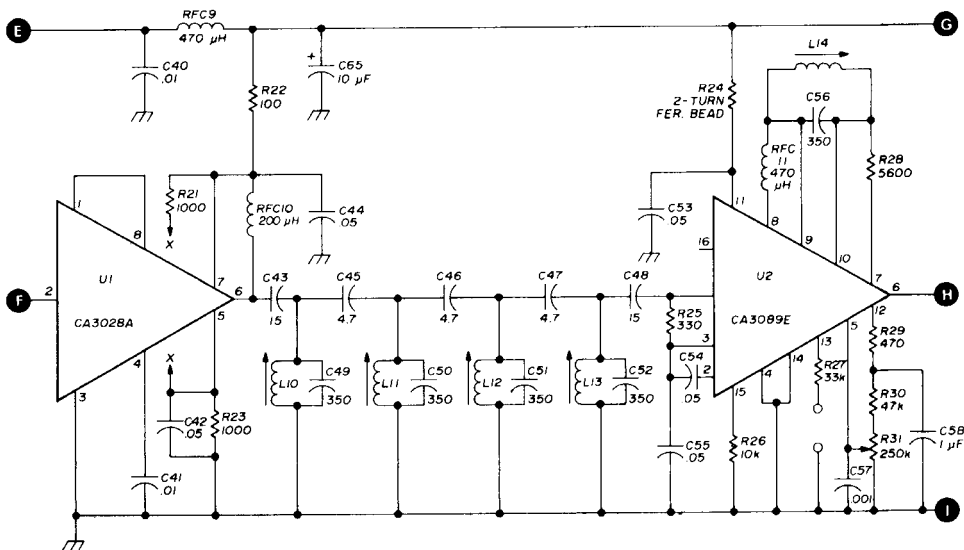




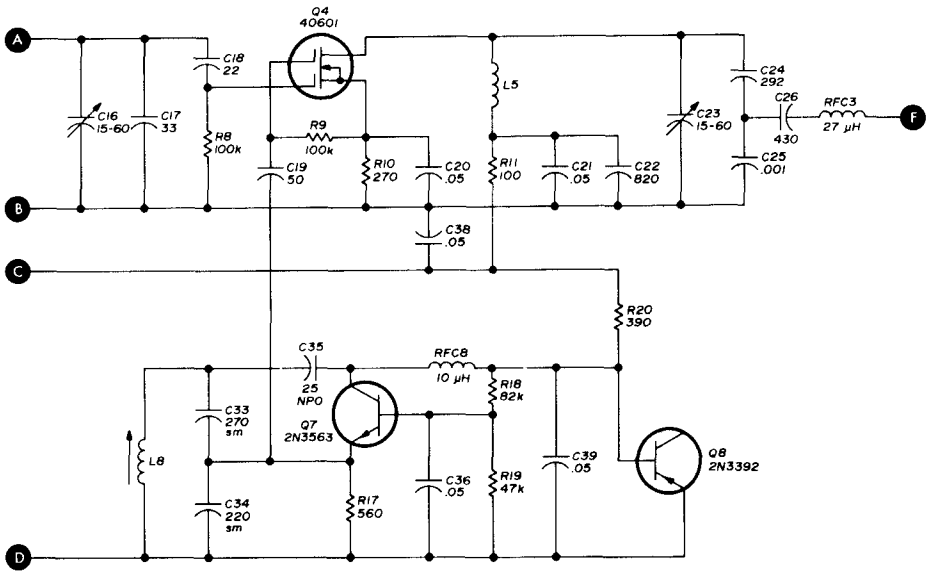


ply is about 1½ watts. This is sufficient to reliably trigger a local repeater from the mobile 10 miles away.

While the transmitter shown in the photographs uses only two crystals operated by a slide switch, it would be equally satisfactory to omit the crystal sockets on the PC board and replace the slide switch with a single external socket for use with any crystal you wish. Tuning can be compromised to use crystals whose two-meter outputs are 1 MHz apart.

The receiver input stage, consisting of transistors Q1 and Q2, is a cascode amplifier using fets. This circuit is particularly satisfactory in that it is not critical as to component values, other than the input and output inductors, it is completely stable and gives a voltage gain of 20 to 25 dB. The inductor shields, not intended to be helical resonators, are thin-wall brass tubes with 6-32 nuts soldered to the tops to permit using 3/16-inch tuning slugs for trimming to frequen-

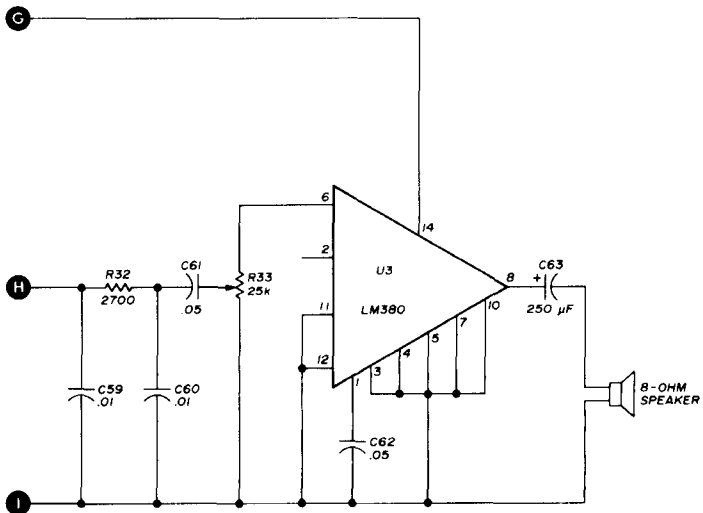

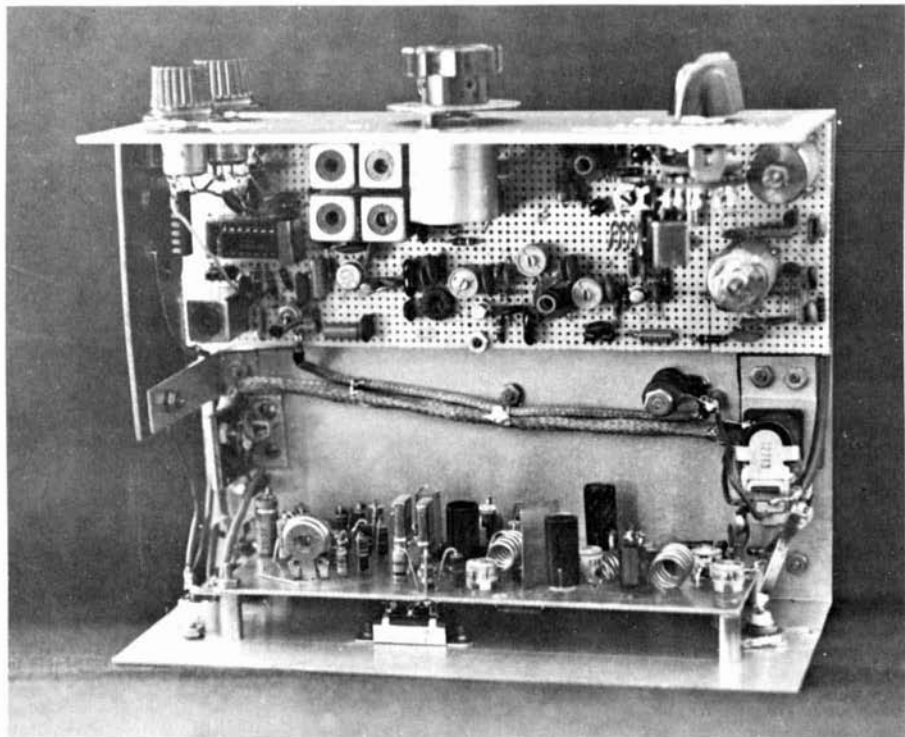

Construction of the two-meter package. The transmitter section is mounted along the rear wall of the enclosure (bottom). The tunable receiver is laid out on perf board and mounted toward the front of the chassis (top). Transmit/receive relay is to the right.

cy. The tubes themselves are secured by wire pins, passing through the PC board and soldered to the foil side beneath.

The PC board is a standard Vector product, pre-punched in a rectangular grid of 0.10-inch spacing between holes, coated with 2-ounce copper foil on one side. This board is comparatively inexpensive and lends itself to circuit carving with high speed hand tools such as those made by Dremel, Casco, etc. The only drawback is that the board is only 6½-inches long, which required patching on the additional length required. The attractive feature of this type of PC board is that parts may be laid out on the top surface, adjusted to existing holes, interferences resolved and the necessary circuitry drawn in pencil first and then transferred to the foil side for engraving.

Returning to the circuitry, I decided that the second i-f should be somewhere near the top of the broadcast band for

reasons which will be discussed later. Since I had also decided that continuous tuning of the entire two-meter band was desirable and practical, it quickly became apparent that 500-kHz segments would be a reasonable target if a medium high first i-f frequency were chosen.

In order that no harmonics of the second conversion oscillator fall into the two-meter band, it develops that the lowest tuning range of the second conversion oscillator must be in the 11.385 to 12.000-MHz range (13th harmonic of 11.385 MHz = 148 MHz, 12th harmonic of 12.000 MHz = 144 MHz). If the second oscillator is set to cover 11.440 to 11.940 MHz, the median frequency is 11.690 MHz. Subtracting the second i-f gives a median frequency of 10.230 MHz for the first i-f. Therefore, the first i-f bandpass range is 9.980 to 10.480 MHz which is comfortably clear of the commercial fm tuners i-f of 10.7 MHz.

This juggling of frequencies does not come by divine inspiration or revelation but happily turns out to be an acceptable solution which does not require extreme measures in the way of second oscillator stabilization.

With the first i-f established at 10.230 MHz and covering plus and minus 250 kHz, you can pick the frequencies for your crystals for the first conversion oscillators. For example, if you want to cover the band from 147.00 to 147.50 MHz, take the median frequency of 147.250, subtract the median i-f frequency of 10.230 MHz to get the first oscillator injection frequency of 137.020 MHz. This means you must order a third-overtone 47.673-MHz crystal and triple that to feed into the first mixer.

The first oscillator circuit is conventional, with its collector tuned to the third overtone of the crystal and driving the base of a second transistor operating as a tripler. Using a second transistor gives a cleaner injection signal and insures adequate drive for the mixer. The dual-gate mosfet mixer is greatly preferred over plain fet mixers with regard to overall performance and the amount of drive required. Tuning the oscillator tripler circuit permits establishing the optimum amount of required injection drive, and the mixer output can be significantly improved by such tuning.

The first mixer feeds the second mixer input through a pair of bandpass circuits. The second mixer is also a mosfet. Its output is tuned to the second i-f frequency of 1460 kHz. The output impedance is stepped down by a capacitive divider to match the low input impedance of the CA3028A IC. Drive to the CA3028A is applied through a series tuned circuit which provides the desired low impedance drive and also discriminates against any first i-f and second oscillator signals appearing in the second mixer drain circuit.

### **variable oscillator**

The second oscillator, covering the tuning range of 11.440 to 11.940 MHz, was one of the major hurdles of the

whole design. Capacitance tuning was tried, rather pessimistically, and I was not disappointed. As expected, it was noisy, tuning was much too critical and the capacitor occupied too much space. Next, I tried slug tuning the inductor with various slugs, both powdered iron and ferrite. This eliminated the noise but, with any reasonably compact coil, would not cover the desired tuning range.

Finally, a small Millen coil from the junk box was tried. This is a ceramic coil, 13/32-inch in diameter, 1/2-inch long with a threaded mounting boss, and tuned with a silver-plated slug, the threaded screw of which projects through the mounting boss (Millen part number 69041).

This coil form turned out to be a prime solution to the tuning problem. The required 500 kHz can be tuned in three turns, which gives adequate spread, and if the slug is properly positioned in the winding, tuning is nearly linear. (This is with the external 1-inch aluminum shield shown in the photographs. Without the shield, the tuning rate is much faster.) As indicated in the schematic, the collector voltage of this oscillator is zener regulated, using the base-emitter junction of a 2N3392 which regulates at 8.6 volts.

The maximum drift of the entire receiver, after two hours operation, is less than 20 kHz, i.e., 10 units on a 100 unit dial. How much of this is attributable to the tunable oscillator I don't know, and quite frankly, don't care. The tuning is smooth, absolutely noiseless and perfectly retraceable. The slug travel is established by the mechanical limit in the coil form at one end, and by positioning and locking a 1/4-inch bakelite rod threaded on the slug screw. The tuning dial is on the bakelite rod.

The 1460-kHz output of the second mixer drives a CA3028A in cascode configuration strictly for gain purposes, which in turn feeds a 4-pole filter for high selectivity. This filter consists of four Miller pot-core miniature rf inductors. These inductors are available in a series of ranges, the type 9054 being the most suitable. The aluminum shields on

these inductors must be removed to connect a miniature ceramic capacitor across the winding to provide a shielded tunable circuit. The shields must, of course, be replaced. This requires some study and care in handling. If the Miller 9054 is not available, other inductors can be used with appropriate size capacitors to insure that they can be tuned to the 1460-kHz i-f.

## detection and audio output

From the above filter the signal goes to the CA3089 IC. This IC has been both touted and castigated. It is a multi-purpose device of great potential, but is extremely intolerant of careless circuit board layout. Briefly, it can provide hard limiting for fm purposes, considerable gain, agc, afc, quadrature fm detection, audio output and — a violent headache. It also has a squelch output and provision for driving a tuning meter. The squelch output is very effective in handling ignition noise when operating mobile. Considerable information, in detail, on the CA3089 is available on request from RCA. It is recommended that anyone contemplating using this IC take advantage of this material.

While the CA3089 was developed for commercial fm reception, it seemed the better part of valor not to attempt using it at the 10.7-MHz level, in view of the reported difficulties in taming it. On the other hand, the internal capacitances in the device which sum up the limiting control are so small that I felt it would be self-defeating to try to use it at a frequency as low as 455 kHz. Hence, the choice of the top of the BC band for the second i-f. At this frequency CA3089 performance, while a little ticklish, is all that could be wished for. Limiting is good, the audio recovery of narrowband fm is excellent and the tuning meter output, either voltage-wise or current-wise, is as described.

The audio amplifier is the LM380 IC made by National Semiconductor. This is a 14-pin DIP that will give nearly 1.4 watts output with a 12-volt power supply. No peripherals are required other

than signal input and output and power-supply connections! The LM380 has an optional connection for high frequency bypass and the device will drive an 8-ohm speaker through a capacitor. It does require a 6-square-inch heatsink for its full rating of 2 watts. The photographs show the heatsink (a piece of copper-clad phenolic board) with the IC mounted on it at the end of the receiver PC board. The coupling capacitor is mounted directly on the speaker. The miniature phone jack mounted on the heatsink board permits using either the speaker in the cabinet or a remote speaker. Of course, a remote speaker will require its own coupling capacitor.

With regard to additional items not mounted on the transmitter or receiver boards, there is a miniature closed-circuit phone jack below and behind the heatsink. This is a practical necessity for adjusting and loading the transmitter when first put into operation. A 500-mA meter on a miniature phone plug should be used. Above the meter jack is the power input jack to take a plug from either a car battery or from an ac-operated power supply. Below the power jack is the three-connector microphone jack. The lead from the audio input to the transmitter board is less than 1-inch long.

The push-to-talk microphone lead transfers the input power from receiver to transmitter via the relay seen at the other end of the cabinet. This relay is a two-pole double-throw affair salvaged from some surplus equipment, and is used both as the power transfer relay and the antenna switching relay. It is similar to the type (and size) of those found in Command Sets. Although it is stamped, "28 Vdc," it has a 300-ohm coil which indicates that it would be easy on the power supply. By adjusting the fixed stop on the armature to reduce the air gap somewhat, and by adjusting the relay contacts to make lighter pressure, it was possible to make this relay operate on 10.5 volts. This is not unique with these relays, others have been similarly treated. It is also possible to shim up the contact assembly on some types to reduce the

armature air gap even more. This solved the problem of a suitable relay and the price was right. There is a fixed 100-ohm resistor connected in parallel with the receiver power input to equalize the loads in the transmit and receive positions when using a zener-regulated power supply, but it is not essential.

No-signal power drain is 60 mA at 12 volts in the receive position, kicking up another 100 mA or so with strong signal input. In the transmit position at 12 volts current drain, including relay current, is

while the complete receiver comes off with a measured sensitivity of 0.8 micro-volt.

### alignment

Receiver alignment can be done with a CW signal except for final adjustment of the quadrature coil. First, disable both oscillators and open the series circuit to the CA3028A input. Feed a low-level 1460-kHz signal to the choke input to the CA3028A. Using a voltmeter on the CA3089 meter lead as indicator, peak the

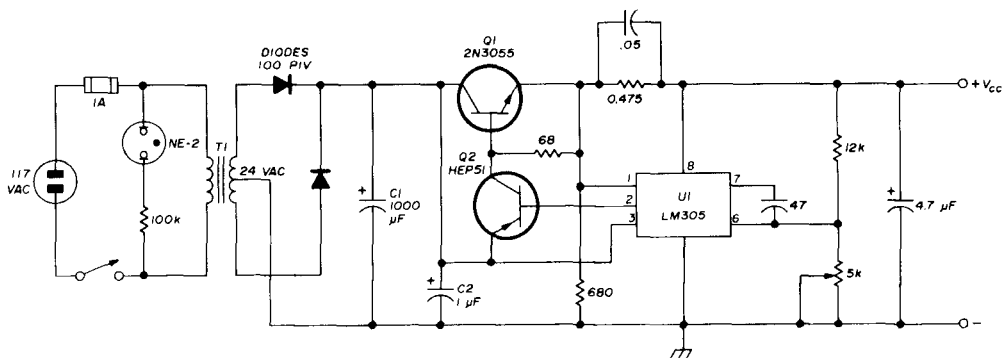


fig. 3. Ac power supply for operating the two-meter package at the base station.

350 to 425 mA. This economical power requirement is within the capability of portable battery supply.

### converter

I have built a converter for a friend to be used with an automobile BC radio, using the rf amplifier, first mixer and first oscillator to give an i-f output in the 550- to 1550-kHz range. The converter board also contained a broadly tuned i-f transformer from a transistor radio which could be peaked to the approximate i-f, while the car radio is used as a tunable i-f and audio amplifier. With this arrangement two crystals can be used to cover half the two-meter band, the other half of the band appearing as a simultaneous image, not so confusing as might appear at first blush. One set of signals tunes up in frequency while the other tunes down. This unfelicitous arrangement comes out with a measured sensitivity of 2 microvolts, (lacking somewhat in selectivity)

four inductors of the second i-f filter and adjust for equal response roll-off each side of the peak. Reconnect the series input to the CA3028A and shift the 1460-kHz signal input to the vicinity of the second mixer input and tune the second mixer output for maximum indicator response.

Remove the short from the second oscillator coil and tune the second oscillator to 11.690 MHz. Couple a low-level 10.230-MHz signal to the vicinity of the first mixer input and tune both bandpass circuits for maximum response. It may be necessary to resistively load one circuit for smooth response curve (don't forget to remove the loading when alignment is completed). Restore first oscillator operation and provide an appropriate two-meter signal to the receiver input.

Peak the output circuit of the cascode amplifier and then the input circuit. The former will peak sharply while the latter will have broad peak. Return to the first

oscillator and adjust the tripler circuit to vary injection voltage to the first mixer for best response to a medium-strength signal. Finally, tune in an fm station on two meters and adjust the quadrature coil for best undistorted audio recovery. If you get on an active repeater frequency, you will have a variety of signal qualities to pick from.

## ac power supply

A suitable power supply for fixed

undertake a project of this magnitude on faith alone, but, hopefully, many readers can use some parts of the design. Some experience with the use of the high-speed carving tools is an absolute necessity.

One of the major problems of compact construction is the source of components. This applies particularly to the physically small items. One prolific source is surplus boards — assuming that the items are quickly identifiable by the seeker. The best source, by far, for new components

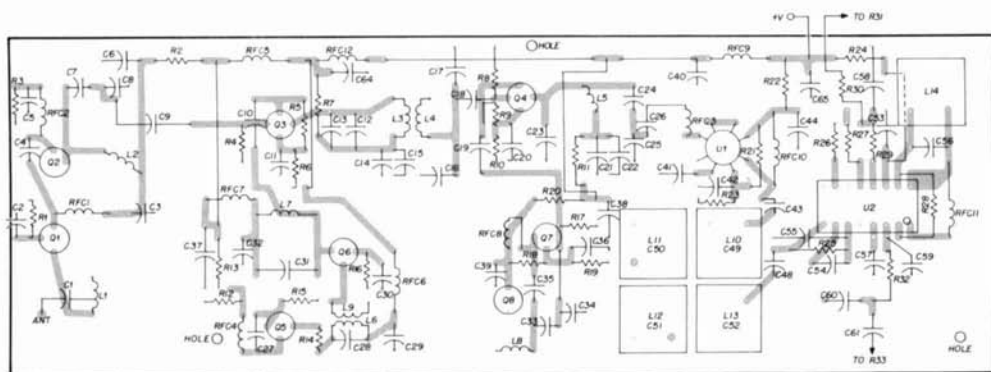


fig. 4. Printed-circuit layout for the tunable two-meter fm receiver. This layout is approximately two-thirds actual size.

station use is shown in fig. 3. The LM305 voltage-regulator IC is in a TO-5 can. It provides excellent regulation and current limiting. With the value of R3 indicated it will limit at about 1 ampere. The 2N3055 should have a heatsink and it is desirable that Q2 and the IC also have heatsinks. The tantalum capacitors are specified as such by National Semiconductor as safeguards against parasitics in either the power supply or the load. With the component values shown in fig. 3 the supply will provide 400 mA at 12.3 volts. The output voltage may be reduced considerably, for preliminary test purposes, by means of the 5k pot. All the components for the power supply, except the transformer and 1000- $\mu$ F filter, can easily be accommodated on a 3-inch-square board.

## summary

I don't expect that many amateurs will

is Newark Electronics in Chicago. However, you must have their industrial catalog available for ordering parts, and this approach is not inexpensive.

There is considerable satisfaction in operating equipment using solid state devices. In addition to compact size, light weight and low power requirements, there is the assurance that, barring mechanical damage, the performance will remain undiminished for the indefinite future. I have been very well satisfied with the performance of this equipment pending the time when some inventive soul produces a 10-watt vhf power transistor in a TO-5 can with integral heatsink. Then back to the drawing board!

## reference

1. Doug DeMaw, W1CER, "The Pip-Squeak Gets Smaller," *QST*, September, 1972, page 37.

ham radio



# PERFORMANCE WHEN IT COUNTS

**SWAN ELECTRONICS Equipment:** Major choice of the **Baja Amateur Radio Racing Fellowship** operators who manned the communications network for the 1973 Baja 1000 Off-Road Race from Ensenada to La Paz, B.C., Mexico. More than 50% of the operators used SWAN gear. Among other units, a SWAN SS-200 completely solid-state 5-band transceiver and two FM-2XA 2-meter transceivers were in action at the finish line.

Officials and participants agreed that communications, for the gruelling 875 mile course, was the best in the history of off-road racing. Here are a few of their comments:

**Valor Smith** (Pit-Crew Chief for the "Baja Bug" class winner) — "We've had nine entries in Mexican races, and this is the finest communications we've ever had."

**Ing. Alfredo Arenas** (Executive Director of the Baja Sports Committee) — "I think the radio communications were very good. We're very grateful to all the people involved."

**Driver Carl Adams** (Winner of the "Mini-Pickup" class) — "We got correct answers every time we asked . . . and we went out to win . . . Without communications, it'd be a big guess."

**Marilynn Greaves** (Official Scorer and Time Keeper) — "Overall communications was exceptionally great . . . In spite of all the dust at the finish line, there was no problem with the SWAN FM-2XA . . . Communications between the radio room and the finish line worked out beautifully."

WHEREVER THE ACTION IS IN AMATEUR RADIO, YOU'LL FIND SWAN ELECTRONICS

## SWAN MOBILE TRANSCEIVERS

*designed for 12V DC power source*

SS-200 (5-Band, 200 watts P.E.P.)	\$779
SS-15 (5-Band, 15 watts P.E.P.)	\$579
FM-2XA (2-meter, 10 watts P.E.P.)	\$259
PS-20 (SS-200 AC Power Supply)	\$139
PS-10 (SS-15 AC Power Supply)	\$89
FM-2XA Snap-Pack (AC Power Supply)	\$39.95

DEALERS THROUGHOUT THE WORLD  
or order direct from



**SWAN**  
ELECTRONICS

A subsidiary of Cubic Corporation

Home Office: 305 Airport Road • Oceanside, CA 92054  
Telephone: (714) 757-7525

THE BEST PRACTICAL DEVELOPMENTS IN AMATEUR RADIO

# how to solve transistor heatsink problems

A complete discussion  
of transistor heatsinks  
and how to choose  
the one you need  
for your application

**How much heatsink is enough?** That's a question which can be answered by whether or not the transistor survives when power is applied to the circuit, but this is an expensive way of finding the solution to heatsink design problems; a better way is to calculate heatsink requirements, and select a suitable heatsink using manufacturers' specifications, or make your own heatsink based on empirical data.

A heatsink problem is just one part of the larger problem of designing a transistor circuit to do a particular job; after the performance requirements of the circuit have been established, answers to the following questions must be found. How much power must the transistor dissipate? Will the selected transistor dissipate this much power? If so, how much heatsinking is required?

## estimating dissipation requirements

Power dissipated by the transistor is that power which is wasted in heating the transistor; it is equal to the power delivered to the transistor minus the power the transistor delivers to its load. A typical example is shown in **fig. 1**. The total power into the transistor is the sum of the signal power into the base plus the dc power delivered to the transistor by the power supply; power wasted in bias resistors does not count. Power delivered by the transistor to its load is the power into the output matching network.

Let's put some hypothetical numbers on the circuit of **fig. 1**. Let's say the amplifier is operated class A, dc collector current is 200 mA,  $V_{CC}$  is 12 volts, and the emitter voltage,  $V_E$ , is 2 volts. Let's further assume that there is no dc voltage drop in the primary of the output matching network. Therefore, the dc voltage from collector to emitter is equal to 12

Courtney Hall, WA5SNZ, 7716 La Verdura Drive, Dallas, Texas 75240



minus 2, or 10 volts. With 200 mA of collector current, the dc power into the collector is

$$P_C = V_{CE} I_C = (10 \text{ volts})(0.2 \text{ amp}) = 2 \text{ watts}$$

If the dc beta, or current gain, of the transistor is 50, then the base current is

$$I_B = \frac{I_C}{\beta} = \frac{200 \text{ mA}}{50} = 4 \text{ mA}$$

Assume the base-emitter voltage of the transistor is 0.6 volt; then the dc power into the base will be

$$P_B = I_B V_{BE} = (4 \text{ mA})(0.6 \text{ volt}) = 0.0024 \text{ watt}$$

This is insignificant compared to collector power and may be neglected.

Assume the transistor delivers 0.9 watt of ac power to the output matching network, and the transistor has a power gain of 10. In this case the signal power into the transistor is

$$\frac{0.9}{10} = 0.09 \text{ watt,}$$

and total power into the transistor would be 2.09 watts. The transistor must dissipate the difference between total input power and output power, or

$$2.09 - 0.9 = 1.19 \text{ watt}$$

When the input signal is removed, however, the transistor must dissipate 2 watts because none of the power from the collector power supply goes into the load.

Class-B and class-C amplifiers can be handled in much the same way, the important difference being that the transistor does not dissipate appreciable power when the input signal is removed. Transistor dissipation will still be approximately equal to the difference between the dc power furnished by the collector power supply and the signal power delivered to the collector load.

Fig. 2 shows an example of a class-C rf

amplifier. The dc power from the power supply is 2.4 watts, and the power into the T matching network is 1.5 watts. Therefore, the power which must be dissipated in the collector of the transistor is 2.4 minus 1.5 or 0.9 watts. If the power gain of the transistor is 10, then 0.15 watt must be fed into the base of

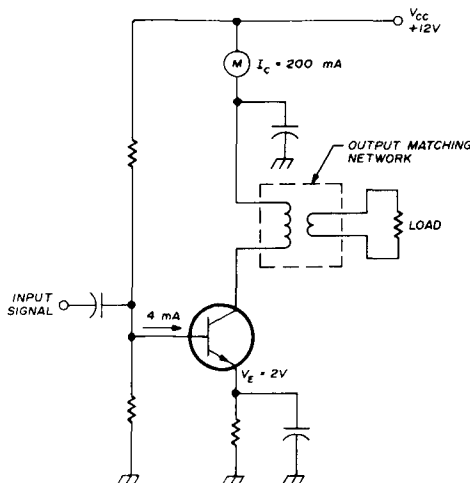


fig. 1. Class-A transistor power stage used to illustrate power dissipation (see text).

the transistor, making a total of 0.9 plus 0.15, or 1.05 watt, which must be dissipated by the transistor.

Transistors used in power supply regulators often require heat sinks. Fig. 3 shows a simple regulator which delivers 12 watts to the load. Neglecting the transistor base current and zener diode current, the power into the regulator from the rectifiers is

$$18 \text{ volts} \times 1 \text{ amp} = 18 \text{ watts}$$

The transistor must dissipate the difference between input power and output power, or 6 watts.

### transistor capabilities

After the power dissipation is estimated, a transistor may be selected which meets the power requirement; this is done by studying the data sheets of transistors

which meet other circuit requirements such as gain and frequency range.

Most transistor data sheets show one or both of the following power ratings. One is total device dissipation at (or below) 25°C *free-air* temperature; this is

to simply mount the transistor on a heatsink and allow air at room temperature (25°C) to circulate around it. This method will not hold the case temperature at 25°C, so a reduced power rating must be accepted for the device.

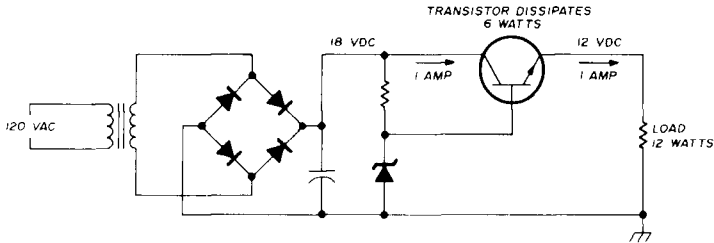


fig. 3. The series regulator transistor in this simple power supply dissipates 6 watts.

the maximum power the transistor may dissipate without any heatsink if the temperature of the air around the transistor is 25°C or less.

The other rating is total device dissipation at (or below) 25°C *case* temperature; this is the maximum power the transistor may dissipate if the transistor case temperature is held to 25°C or less. One way to hold the case temperature at 25°C is to mount the transistor on a heatsink which has integral cooling coils through which ice water is pumped. This is rather expensive, however, and the usual procedure is

Included with the free-air and case-temperature ratings are derating factors which say that the device must be derated linearly to some temperature (free-air or case) at the rate of so many watts-per-°C. Derating factors may be shown as footnotes on the data sheet.

Some transistor data sheets include dissipation derating curves which are merely graphs showing what has already been specified; if the data sheet does not include it, one may easily be drawn. Fig. 4 shows derating curves for the 2N3724A transistor. This device is rated for 1-watt dissipation at 25°C free-air temperature (no heatsink) with a derating factor of 5.71 mW-per-°C to 200°C. Notice that if the free-air temperature is 200°C, no power may be dissipated by the transistor. If the free-air temperature is 50°C, then the amount of derating is 25°C times 5.71 mW-per-°C, or 143 mW; this derating is subtracted from the 1-watt rating to find how much power may be dissipated at 50°C free-air.

$$1000 \text{ mW} - 143 \text{ mW} = 857 \text{ mW}$$

The case temperature curve applies if a heatsink is used. If the transistor dissipates, say 3 watts, then, according to fig. 4, the heatsink must be large enough to hold the case temperature to 95°C or less. Operation must always be on the curve or below it. It is good design practice to

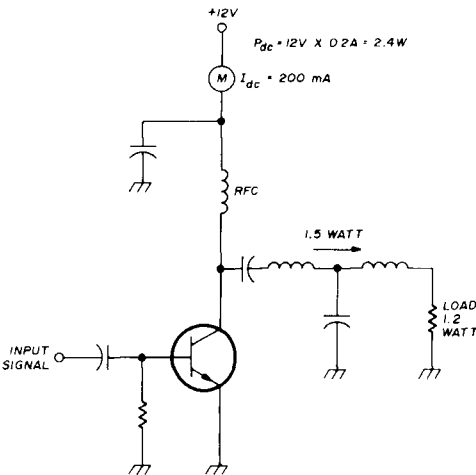


fig. 2. The transistor dissipates 1.05-watt in this class-C rf amplifier stage.

allow some safety factor by operating somewhat below the curve, i.e., use a slightly larger heatsink than is called for. As mentioned above, practical heatsinks will not hold the case temperature to 25°C, so you should not expect to operate this device at 5-watts dissipation.

Some transistors have power ratings specified at 50°C or 100°C case temperatures, with appropriate derating factors for case temperatures above those values. Fig. 5 shows the derating curve for the 2N5387. This transistor is rated for 100 watts at (or below) 100°C case temperature and has a derating factor of 1 watt-per-°C to 200°C case temperature. It is possible for transistors with such ratings to dissipate their full power rating using an air-cooled heatsink, provided the heatsink is good enough.

### thermal resistance

Thermal resistance is expressed in the units, °C-per-watt. This is the temperature difference that will occur between two points for each watt of power that is dissipated at one of the points, the higher temperature being at the point where power is dissipated. The reciprocals of the derating factors discussed above are thermal resistances.

$$\text{Thermal Resistance } \frac{^{\circ}\text{C}}{\text{watt}}$$

$$= \frac{1}{\text{Derating Factor } \frac{\text{watts}}{^{\circ}\text{C}}}$$

Theta ( $\theta$ ) is the mathematical symbol used for thermal resistance, and subscripts are used to denote which two points the thermal resistance is between:

- $\theta_{J-A}$  junction-to-ambient
- $\theta_{J-C}$  junction-to-case
- $\theta_{C-HS}$  case-to-heatsink
- $\theta_{HS-A}$  heatsink-to-ambient

Junction is the term used for the point or points inside the transistor where the power is actually dissipated. Case means the point or points on the transistor

package where the heatsink makes contact. Ambient is the medium into which heat is ultimately conducted or radiated, and it usually is free-air at 25°C.

If the transistor or heatsink is mounted inside an equipment cabinet

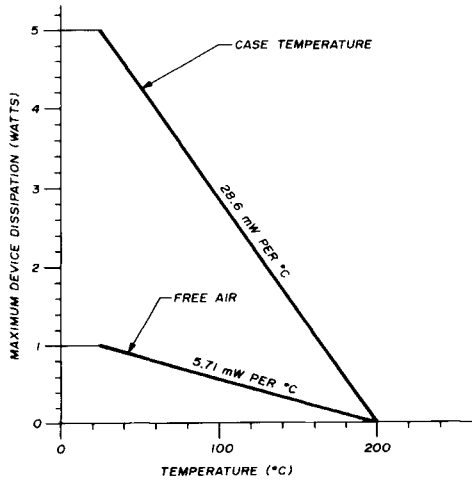


fig. 4. Dissipation derating curves for the 2N3724A transistor.

where the temperature is higher than room temperature due to heat-generating components, such as transformers, tubes, power resistors or the power transistor itself, then ambient means the temperature inside that cabinet. Fig. 6 is a scale showing the relationship between °C and °F for those accustomed to expressing temperature in °F.

The reciprocal of the free-air derating factor is  $\theta_{J-A}$

$$\theta_{J-A} = \frac{1}{\text{Free-air Derating Factor}}$$

For the 2N3724A (see Fig. 4),

$$\theta_{J-A} = \frac{1}{5.71 \frac{\text{mW}}{^{\circ}\text{C}}} = 0.175 \frac{^{\circ}\text{C}}{\text{mW}}$$

$$= 175 \frac{^{\circ}\text{C}}{\text{watt}}$$

This thermal resistance value tells you how many °C the junction temperature will rise above ambient temperature for a

given transistor power dissipation. If the ambient temperature,  $T_A$ , is  $25^\circ\text{C}$ , and 1 watt of power,  $P$ , is dissipated at the junction, then the junction temperature,  $T_J$ , will be

$$T_J = T_A + P\theta_{J-A} \quad (1)$$

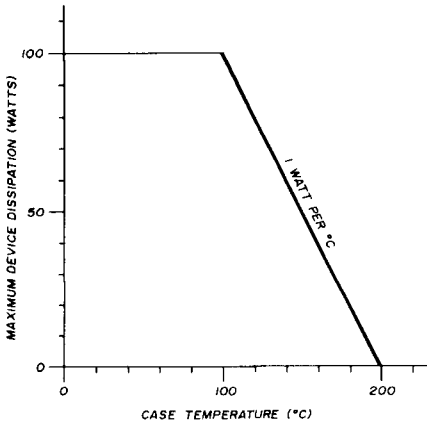



fig. 5. Dissipation derating curve for the 2N3724A transistor.

$$T_J = 25 + (1 \text{ watt})\left(175 \frac{^\circ\text{C}}{\text{watt}}\right) = 200^\circ\text{C}$$

It is obvious from this and fig. 4 that the maximum allowable junction temperature for the 2N3724A is  $200^\circ\text{C}$ . *The entire purpose of heat sinking is to prevent the junction temperature from exceeding the maximum allowable value specified by the manufacturer.*

Eq. 1 is the basic thermal equation used to determine if a certain power

fig. 6. Relationship between the Centigrade and Fahrenheit temperature scales.

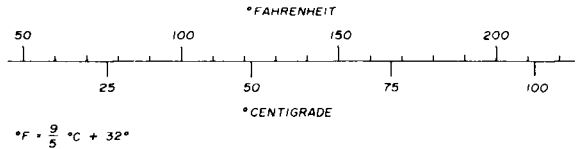

dissipation will cause the transistor's maximum allowable junction temperature to be exceeded.  $T_A$  should be the highest actual ambient temperature encountered. Don't use  $T_A = 25^\circ\text{C}$  if the transistor is to be operated in the trunk of a car on hot summer days; 50 to  $75^\circ\text{C}$  would be more realistic.

When the transistor is fastened to a heatsink,  $\theta_{J-A}$  breaks down into three quantities;

$$\theta_{J-A} = \theta_{J-C} + \theta_{C-HS} + \theta_{HS-A} \quad (2)$$

Combining eqs. 1 and 2 gives

$$T_J = T_A + P(\theta_{J-C} + \theta_{C-HS} + \theta_{HS-A}) \quad (3)$$

$\theta_{J-C}$  is the reciprocal of the case temperature derating factor shown on the transistor data sheet;

$$\theta_{J-C} = \frac{1}{\text{Case Temperature Derating Factor}}$$

For the 2N3724A (see fig. 4),

$$\theta_{J-C} = \frac{1}{28.6 \frac{\text{mW}}{^\circ\text{C}}} = 0.035 \frac{^\circ\text{C}}{\text{mW}} = 35 \frac{^\circ\text{C}}{\text{watt}}$$

This value of thermal resistance tells you that the junction temperature will be  $35^\circ\text{C}$  higher than the case temperature for each watt of power dissipated in the junction. If 5 watts of power are dissipated in the junction, then the junction temperature will be  $175^\circ\text{C}$  higher than the case temperature. Therefore, the case temperature *must not* exceed  $25^\circ\text{C}$  if the junction temperature is not to exceed  $200^\circ\text{C}$ , its maximum allowable value.

Case-to-heatsink thermal resistance,  $\theta_{C-HS}$ , depends on several varying factors. How much torque is used in tightening the nuts or screws which hold the transistor to the heatsink? How smooth

are the mating surfaces of the transistor and heatsink? Is the heatsink anodized? Is an insulating mica washer used between the transistor and heatsink? Is a silicone grease, or other thermal compound, applied to the mating surfaces? How and to what extent do these factors affect  $\theta_{C-HS}$ ? All these factors have an effect.

A mica washer will increase the thermal resistance about 0.3 °C-per-watt, and thermal compounds may decrease the thermal resistance about 0.1 to 0.2 °C-per-watt. Anodized surfaces are about 0.25 °C-per-watt higher than unfinished surfaces. A fair rule-of-thumb is to allow

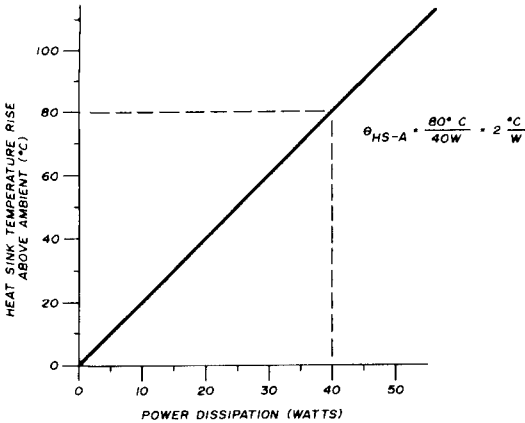


fig. 7. Typical heatsink performance curve.

about 0.2 °C-per-watt for  $\theta_{C-HS}$  when the mating surfaces are bare metal; 0.5 °C-per-watt should be used if the heat sink is anodized or a mica washer is used.

$\theta_{C-HS}$  is usually not very significant at moderate power levels, but if the power dissipation is 100 watts, the temperature difference between the transistor case and the heatsink could be on the order of 50°C. Mating surfaces should be smooth and clean, and the transistor should be mounted tightly to the heatsink.

The last term in eq. 3,  $\theta_{HS-A}$ , is the heatsink-to-ambient thermal resistance. Heatsink manufacturers may specify the thermal resistance of their heatsinks in °C-per-watt, or they may provide a performance graph such as shown in fig. 7. Since the curve is usually a straight line, the slope of which is thermal resistance,  $\theta_{HS-A}$  may be derived from the curve as shown. The manufacturer may label the vertical axis in fig. 7 case temperature rise above ambient in °C; in this case  $\theta_{C-HS}$  is included in the heatsink rating, so the slope of the line is equal to  $\theta_{C-HS} + \theta_{HS-A}$ .

## finding the right heatsink

To choose a suitable heatsink it is necessary to determine the value of  $\theta_{HS-A}$  you need, then select a heatsink having that value, or less, of thermal resistance. Some examples will illustrate.

Suppose a circuit includes a TIP29 power transistor; the maximum power,  $P$ , which the transistor must dissipate is 15 watts. To allow for operation in non-air-conditioned places on hot summer days, ambient temperature,  $T_A$ , is assigned a value of 50°C. The TIP29 data sheet specifies that the maximum continuous device dissipation at (or below) 25°C case temperature is 30 watts, and this rating is to be derated to 150°C case temperature at the rate of 0.24 watt-per-°C. Thus, the maximum allowable junction temperature,  $T_J$ , is 150°C, and the junction-to-case thermal resistance is

$$\theta_{J-C} = \frac{1}{0.24 \frac{\text{watt}}{^{\circ}\text{C}}} = 4.17 \frac{^{\circ}\text{C}}{\text{watt}}$$

It is desired to use an insulating mica washer when mounting the TIP29 to its heatsink, so  $\theta_{C-HS}$  is assumed to be 0.5°C-per-watt. All of this information is substituted into eq. 3 as follows

$$T_J = T_A + P(\theta_{J-C} + \theta_{C-HS} + \theta_{HS-A})$$

$$150 = 50 + 15(4.17 + 0.5 + \theta_{HS-A})$$

Solving for  $\theta_{HS-A}$ ,

$$\theta_{HS-A} = 2 \frac{^{\circ}\text{C}}{\text{watt}}$$

Thus, an acceptable heatsink would be one which has a thermal resistance of 2 °C-per-watt or less. Armed with this information, you can quickly select a suitable heatsink from the manufacturers' catalogs. The Thermalloy Company's 6123 heatsink is rated at 1.3 °C-per-watt and would be quite adequate.

As a second example, assume a 2N5387 (see fig. 5) must dissipate 100 watts, and the ambient temperature is 25°C. From fig. 5, or from the derating information, the maximum allowable junction temperature is 200°C, and the

junction-to-case thermal resistance is

$$\theta_{J-C} = \frac{1}{1 \frac{\text{watt}}{^{\circ}\text{C}}} = 1 \frac{^{\circ}\text{C}}{\text{watt}}$$

The transistor is to be mounted directly to the bare metal of the heatsink, so  $\theta_{C-HS}$  is taken to be  $0.2^{\circ}\text{C-per-watt}$ . Plugging these values into eq. 3 gives

$$T_J = T_A + P(\theta_{J-C} + \theta_{C-HS} + \theta_{HS-A})$$

$$200 = 25 + 100(1 + 0.2 + \theta_{HS-A})$$

Solving for  $\theta_{HS-A}$  yields

$$\theta_{HS-A} = 0.55 \frac{^{\circ}\text{C}}{\text{watt}}$$

The Thermalloy 6560B heatsink should handle the requirement. It is a black anodized heatsink, but the catalog information indicates that for 100-watts dissipation, the transistor case temperature will be  $45^{\circ}\text{C}$  above ambient. This means

$$\theta_{C-HS} + \theta_{HS-A} = \frac{45^{\circ}\text{C}}{100 \text{ watts}} = 0.45 \frac{^{\circ}\text{C}}{\text{watt}}$$

Putting this into eq. 3,

$$T_J = T_A + P(\theta_{J-C} + \theta_{C-HS} + \theta_{HS-A})$$

$$T_J = 25 + 100(1.0 + 0.45) = 170^{\circ}\text{C}$$

which is  $30^{\circ}\text{C}$  less than the maximum allowable junction temperature; it would be unnecessary to remove the anodize where the transistor mounts to the heat-sink.

### homemade heatsinks

Heatsinks may be improvised by using sheet metal. Weight, volume and shape play some part in heatsink effectiveness, but exposed surface area is the prime factor on which thermal resistance depends. Fig. 8 is a graph showing approximate  $\theta_{HS-A}$  vs area of one side for 1/8-inch thick square aluminum and copper sheet metal. This data applies to square plates mounted so the plane of the plate is vertical, with the transistor fastened to the center of the plate.

The thermal conductivity of copper is

nearly twice that of aluminum which explains why copper gives better results. Brass has a thermal conductivity about one-half that of aluminum, and should be avoided; steel is poor also. Aluminum is the best compromise between performance and cost, and it is widely used.

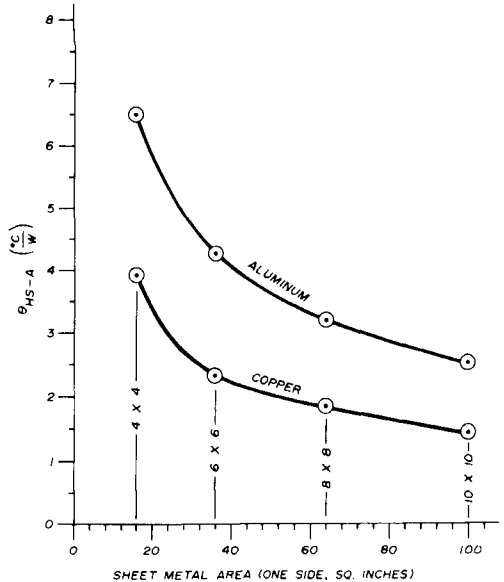


fig. 8. Thermal resistance vs area of 1/8" thick sheet metal.

Fig. 8 may be used to estimate the size of sheet metal needed after the required value of  $\theta_{HS-A}$  has been determined. An aluminum chassis may be used as a heatsink by mounting the transistor to it, but the horizontal portion of the chassis does not get rid of heat as well as the vertical portions. Air rises when it is heated, and all heatsinks should be mounted so most of the surface area is vertical. This permits the most efficient flow of air past the heatsink due to convection currents.

### forced air cooling


Blowing air across the surface of a heatsink by means of a fan or blower can dramatically improve the heatsink's performance. For example, air blown at a velocity of 500 feet-per-minute will reduce  $\theta_{HS-A}$  to around one-third to one-

half its still-air value; this corresponds to a light breeze of about 5.7 miles-per-hour.

Fans and blowers are rated in cubic feet-per-minute (cfm). To determine the approximate velocity of air out of a blower, the cfm rating is divided by the cross-sectional area of the blower's output hole. For example, suppose a small blower is rated at 20 cfm, and its output hole is 2 x 2 inches. The cross-sectional area is 4 square inches, or 0.0278 square feet, so the output air velocity is

$$\frac{20 \text{ cfm}}{0.0278 \text{ sq ft}} = 720 \frac{\text{feet}}{\text{minute}}$$

fig. 9. Power dissipated in a junction by a square wave.

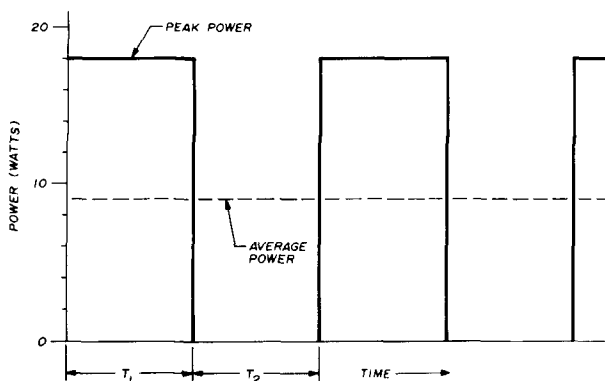

If the blower cannot be mounted so that its output flows directly onto the heat-sink, ducting may be used to channel the air stream to the heatsink. More detailed information on forced-air cooling may be found in heatsink catalogs.

### thermal time lag

A finite amount of time is required for the junction temperature to rise to its steady-state value after power is applied. This fact allows the transistor to operate at higher ac peak power ratings than is possible at dc. Fig. 9 shows a graph of the power dissipated in a transistor junction by a square wave; peak power is 18 watts, and average power is 9 watts.

Assume that the transistor and its heatsink are such that only 10 watts of power may be safely dissipated. If the frequency of the square wave in fig. 9 is 500 kHz,  $T_1$  and  $T_2$  will each be 1 microsecond. The thermal time constant of most power transistors is large compared to 1  $\mu$ s, so the junction temperature will be determined by the average power dissipation of 9 watts, and the

junction will operate within its rating.

Now suppose the frequency of the square wave is decreased to a very low value, say one cycle-per-hour;  $T_1$  and  $T_2$  would each be 30 minutes, and 18 watts would be applied to the junction for 30 minutes during the first cycle, quickly

destroying the device. This is an extreme example, but it points out the necessity of taking frequency into consideration when determining heatsink requirements.

Many power transistors have thermal time constants such that the use of average power in eq. 3 would lead to an inadequate heatsink at the lower audio frequencies. Therefore, it is not a bad idea to use peak power in eq. 3 for audio frequency applications.

Some transistor data sheets show a family of curves to be used in adjusting the value of  $\theta_{J-C}$  according to pulse width and duty cycle, and these should be studied and used when available.

### conclusion

It is hoped that this article will introduce the reader to the basic concepts involved in solving transistor heatsink problems; these principles may also be applied to other semiconductor devices such as thyristors and power zeners. More insight into heatsink technology may be derived by studying power transistor data sheets and heatsink catalogs. ham radio

# simple lowpass filter

## for audio


This simple  
lowpass audio filter  
provides high performance  
and a minimum  
of design effort —  
a design graph  
is provided

Lowpass audio filters have many applications in amateur radio, such as restricting transmitter bandwidth and establishing the bandwidth of direct-conversion receivers. Simple tee- and pi-section filters are often used in these applications but do not provide sharp cutoff. The circuit presented here is substantially better than a tee or pi but is nevertheless inexpensive and simple to build.

So-called modern filters are the best that can be made for a given number of components, but these components are

likely to have awkward, nonstandard values. The filter to be described here performs very well and is much easier to make than a comparable modern filter. It consists of three unmodified telephone toroids and four identical capacitors — nothing more.

The filter is composed of a constant-k pi-section with an m-derived half-section at each end. For best matching to a resistive load, such half-sections are usually made with  $m = 0.6$ . If, however, you let  $m = 0.5$ , for only a slight degradation in performance you achieve two important simplifications. First, all capacitors in the circuit assume the same value, and second, each end inductor assumes exactly one-quarter of the value of the center inductor. This latter property makes it possible to use an 88- or 44-mH telephone toroid for the center inductor and half of a similar toroid for each of the end inductors. The resultant filter is shown in **fig. 1**. It is important that it be terminated in its proper load resistance,  $R$ .

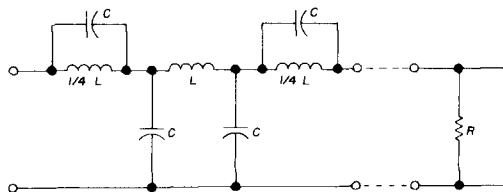

**fig. 1.** Simple lowpass audio filter uses three inductors and four capacitors. For  $L = 88$  mH, the values of  $R$  and  $C$  may be obtained from **fig. 2**.

Frank Regier, OD5CG, American University of Beirut, Lebanon



## design

The design of a particular filter begins with the choice of a cutoff frequency. Then, with the value of  $L$  known, the values of  $R$  and  $C$  are obtained from the equations


$$R = \pi L f_c \text{ ohms} \quad (1)$$

$$C = \frac{0.75}{\pi^2 L f_c^2} \text{ farads} \quad (2)$$


where  $L$  is in henrys and  $f_c$  is the cutoff frequency in Hz.

If 88-mH toroids are used, the values of  $R$  and  $C$  may be obtained graphically from **fig. 2** for a considerable range of cutoff frequencies. For 44-mH toroids, the values of  $R$  should be half, and the values of  $C$  double, those shown in **fig. 2**.

To test the design, a filter was built using  $L = 88$  mH and  $C = 0.1 \mu\text{F}$ . These values lead to a cutoff frequency of 2940 Hz and require a load resistance of 812 ohms. Each of the two 22-mH end inductors was formed by paralleling the two windings of an 88 mH telephone toroid. These toroids have very low core losses at audio frequencies, so their  $Q$  is determined almost entirely by winding

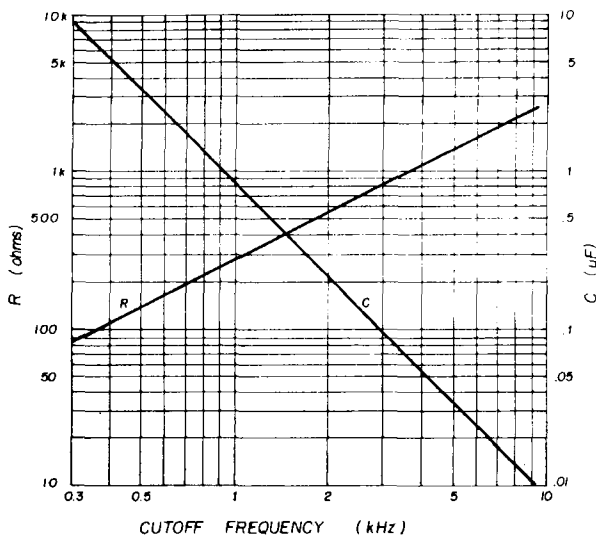

**fig. 2.** Values of  $R$  and  $C$  as functions of the cutoff frequency for the lowpass filter circuit shown in **fig. 1** with  $L = 88$  mH. For  $L = 44$  mH,  $C$  should be doubled and  $R$  halved.

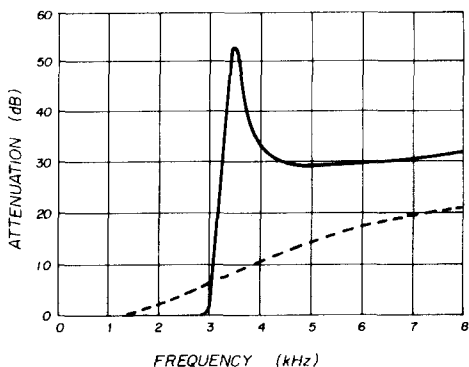

**fig. 3.** Measured attenuation characteristics of the lowpass filter shown in **fig. 1** with a 2940-Hz cutoff frequency. The dashed line shows the measured attenuation characteristics of a comparison pi-section filter with the same nominal cutoff frequency and load resistance.

resistance. The  $Q$  of the end inductors can therefore be almost doubled, without changing the inductance, if the two windings are paralleled. For correct polarity, the two braid-covered ends should be joined, and the other two ends should also be joined. The four capacitors were matched to within 1%, and a load resistance accurate to within 1% was made by paralleling higher-value resistances.

## operating characteristics

The attenuation characteristics of the resultant filter were measured and are shown in **fig. 3**. Also shown (dashed curve) are the measured attenuation characteristics of a comparison pi-section filter having the same cutoff frequency and load resistance. The superiority of the filter circuit of **fig. 1** is obvious.

ham radio

# Improve energy transfer for optimum performance!



**hy-gain**

## Broad Band Ferrite Balun BN-86

Hy-Gain's ferrite balun couples any 52 ohm unbalanced transmission line to any 3 to 30 MHz 52 ohm balanced beam antenna system.

It improves energy transfer to the antenna and eliminates stray RF from the feedline and supporting tower. Shuts out unwanted currents from coax shield that disrupt pattern and upset front-to-back ratio. Stops attendant TVI and effective power drain with no insertion or feed-through loss.

The BN-86 is entirely frequency independent and will operate over all Ham bands. It comes complete with all hardware required for beam or doublet installation.

Bandwidth	3-30 MHz Continuous
VSWR	1:1 when terminated with balanced 52 ohm load
Power Rating	1 kw CW
Impedance Ratio	1:1 at 52 ohms
Input Connector	SO-239
Insertion Loss	Negligible
Feed-through Loss	Negligible

Order No. 242

\$14.95

**hy-gain**

**ELECTRONICS CORPORATION**

Dept. BA, 8601 Northeast Highway Six, Lincoln, NE 68507  
402/464-9151

Telex 48-6424

Distributed in Canada by ELECTRON RADIO SALES, LTD. 211 Hunter Street West, Peterborough, Ontario

# hy-gain

## REPEATER LINE

All you need to know about  
2 meter mobile antennas!

**263** Special no-hole trunk lip mount. 3 db gain. 130-174 MHz. 5/8 wave. 16' coax. DC ground. Base matching coil for 52 ohm match. 17-7 ph stainless steel whip.

**264** High efficiency, vertically polarized omnidirectional roof top whip. 3 db gain. Base matching coil for perfect 52 ohm match. DC ground. Coax and connector furnished.

**265** Special magnetic mount. 3 db gain. Performance equal to permanent mounts. 12' coax and connector. Base matching coil for 52 ohm match. 17-7 ph stainless steel whip. DC ground.

Rugged, continuously loaded, flexible VHF portable antennas. Completely insulated with vinyl coating. Bend at all angles without cracking or breaking. Cannot be accidentally shorted out.

**723N** With UHF connector.

**269** With 5/16-32 base for Motorola HT; Johnson; RCA Personalfone; Federal Sign & Signal; and certain KAAR, Aerotron, Comco and Repco units.


**723A** With BNC connector.

**260** Commercial duty, 1/4 wave, claw mount, roof top whip. Precision tunable to any discrete frequency 108-470 MHz.

**261** Same as above, with 18' coax and connector.

**262** Magnetic mount whip, 108-470 MHz. 52 ohm match. Complete with coax and connector.

*Write for details*

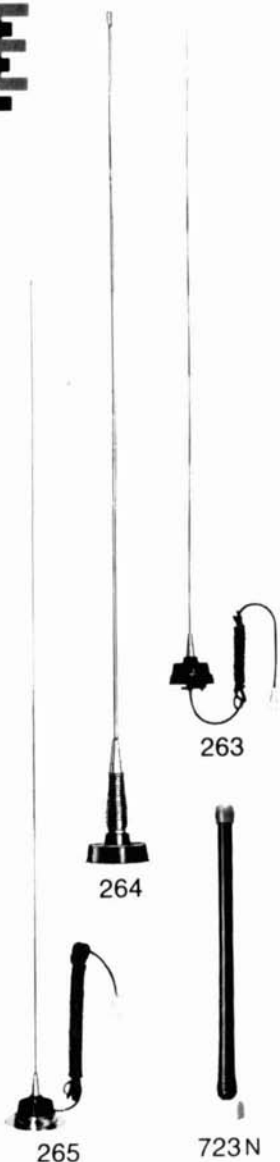

# hy-gain

## ELECTRONICS CORPORATION

Dept. BA, 8601 Northeast Highway Six, Lincoln, NE 68507  
402/464-9151 Telex 48-6424

Distributed in Canada by LECTRON RADIO SALES, LTD. 211 Hunter Street West, Peterborough, Ontario

# medium-power toroidal antenna tuner


Design and  
construction of  
a compact  
antenna tuner  
that will handle  
up to 500 watts

Though numerous designs have been presented for antenna tuners, most are anything but simple and convenient to use. Moreover, the tuners described for limited space applications are themselves often far from compact.

The antenna tuner described here overcomes these problems by attacking the primary culprit — the inductor. Designs using plug-in, rotary or clip-tapped inductors are superseded with the use of

a switch-tapped toroidal coil, thereby substantially reducing space requirements and the inconvenience of bulky tap connections. The circuit is based on the recommendations of W2EEY,<sup>1</sup> and provides matching to random length wires. An indicator is included for "hands-free" tuning.

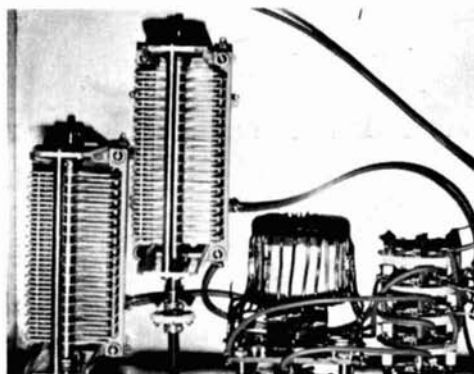The coupler provides nine different circuits using two capacitors and one coil (see fig. 2). Configurations A through E are provided by switch S2, and the forward/reverse function is accomplished by switch S1. The different circuit arrangements provide for a variety of impedance-matching situations.



Closeup of the matching network components in the toroid antenna tuner. Variable capacitors C1 and C2 are to the left, toroid inductance L1 is to the right.

Gregory Widin, WB2ZSH, Box 248, Gambier, Ohio 43022

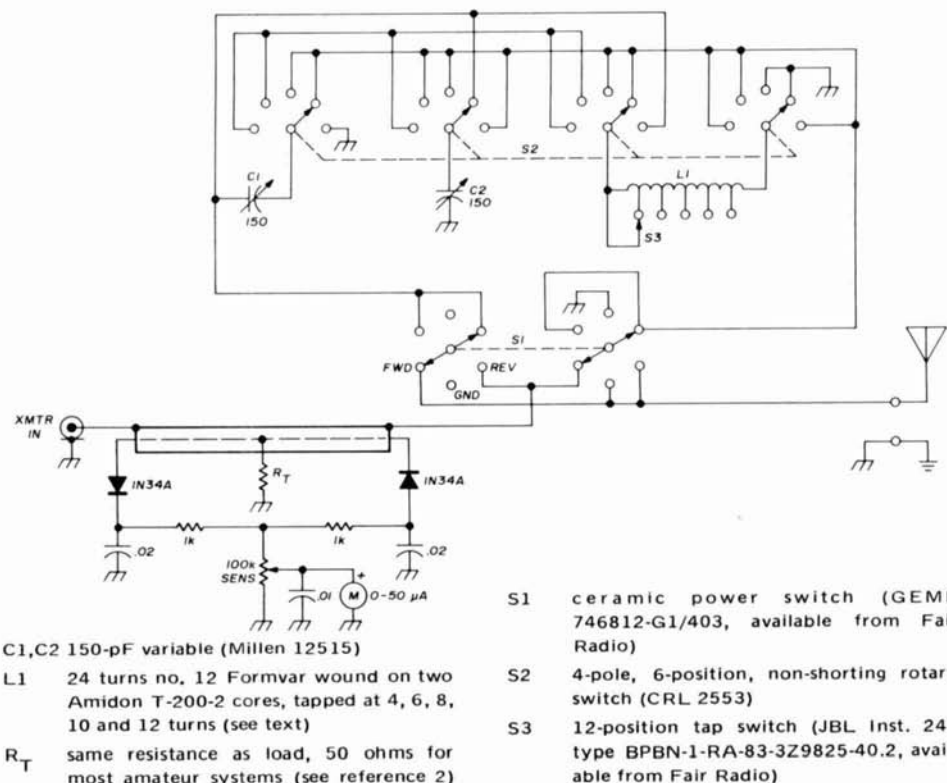


fig. 1. Schematic diagram of the toroid antenna tuner. This tuner will handle up to 500 watts CW without arcing, and is designed primarily for matching long-wire antennas from 80 through 10 meters.


## construction

Building the toroidal antenna tuner is relatively straightforward. The toroid is the most unusual part of the circuit and consists of two Amidon T-200-2 toroidal cores epoxied together. The entire surface of each of the toroids is covered with epoxy to prevent flashover from the coil to the cores. Spacers of 1/4-inch polystyrene are then cut out as shown in fig. 3 and glued to the ends of the dual toroid.

When the epoxy has cured, the wire may be wound on the toroids — 24 turns of number-12 Formvar-insulated wire are required. Care should be taken not to flex the wire more than necessary, as this will work harden the wire. Also, the neater the job, the less likely you will have arcing problems in the finished tuner.

Leave enough wire at each end to secure the coil to the tap switch.

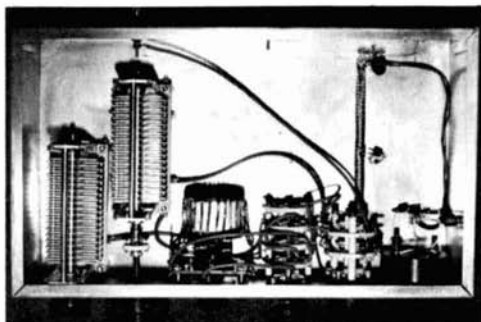The tap leads from the coil are connected before the coil is wired to the



Construction of the toroid antenna tuner. All components are mounted in a small aluminum chassis.

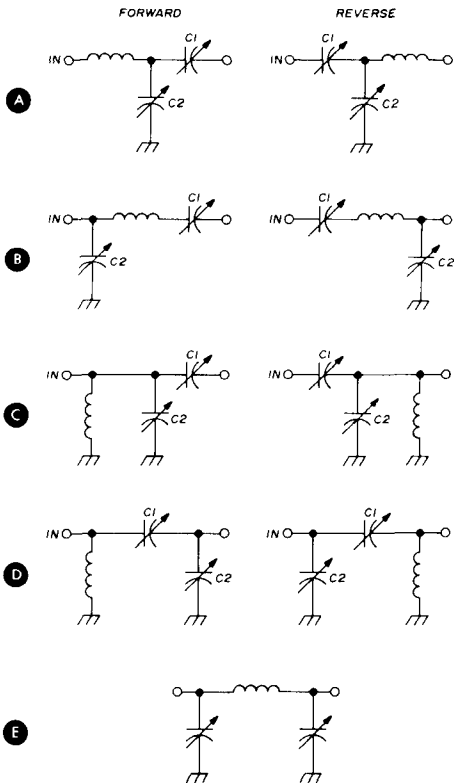


fig. 2. Different matching network arrangements possible with the antenna tuner shown in fig. 1.

switch. Beginning after the first 4 turns, taps are connected every 2 turns, for a total of 12 leads, including those at each end of the coil. To connect the taps, scrape away the insulation on the proper turn on the outside of the coil between the spacers. Another piece of number-12 wire with a clean end is then wrapped to this point with several turns of small

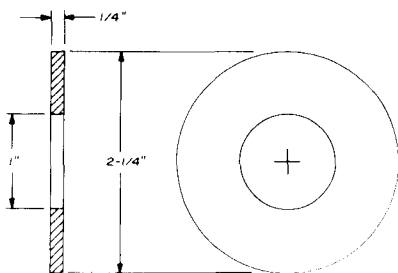


fig. 3. Polystyrene end spacers for the toroidal core (see text).

gauge wire. Then the connection is soldered.

When the tap leads are all connected, the coil may be wired to the switch. The first contact is left blank, and the second contact connects to the first tap after the initial 4 turns on the coil. The wires are connected around, in turn, and support the coil. The wiper should be connected to the end of the coil with the 4-turn tap.

The capacitors were obtained, in new condition, from a surplus A-27 Phantom Antenna unit.\* These units also supplied the ground and antenna binding posts, which are more rugged than most. Note that one capacitor must be fully insulated from ground.

Since the forward/reverse switch provides 3 positions, the center position is used to ground the antenna when the equipment is not in use. A dummy load might be connected to the input side in this position to provide a tune option.

The swr indicator shown in fig. 1 is a modification of an earlier design.<sup>2</sup> I used a pickup braid 8-inches long to give significant indication in the transmitter tune-up position. The sensitivity control used was a subminiature type, but a front-panel adjustment would be more satisfactory. The indicator portion of the tuner should be shielded to prevent possible rfi effects.

The tuner could easily be built into a small enclosure. Front panel space is the main limitation on compactness. The finished unit is capable of handling 500 watts CW without arcing. Using a long-wire antenna of sufficient length, the tuner will easily match transmitter outputs from 80 through 10 meters.

#### references

1. John J. Shultz, "Random-Length Antenna Couplers," *ham radio*, January, 1970, page 32.
2. Gregory P. Widin, "SWR Bridge," *ham radio*, October, 1971, page 55.
3. E. L. Klein, W4BRS, "The Whole of the Doughnut," *73*, June, 1967, page 6.

ham radio

\*A-27 Phantom Antenna units, used, are priced at \$2.95 plus shipping (3 pounds) from Fair Radio Sales Co., Post Box 1105, Lima, Ohio 45802.

# for the EXPERIMENTER!

## INTERNATIONAL EX CRYSTAL & EX KITS

OSCILLATOR • RF MIXER • RF AMPLIFIER • POWER AMPLIFIER



### 1. MXX-1 TRANSISTOR RF MIXER

A single tuned circuit intended for signal conversion in the 3 to 170 MHz range. Harmonics of the OX oscillator are used for injection in the 60 to 170 MHz range. Lo Kit 3 to 20 MHz, Hi Kit 20 to 170 MHz (Specify when ordering).....**\$3.50**



### 2. SAX-1 TRANSISTOR RF AMP

A small signal amplifier to drive MXX-1 mixer. Single tuned input and link output. Lo Kit 3 to 20 MHz, Hi Kit 20 to 170 MHz (Specify when ordering).....**\$3.50**



### 3. PAX-1 TRANSISTOR RF POWER AMP

A single tuned output amplifier designed to follow the OX oscillator. Outputs up to 200 mw, depending on the frequency and voltage. Amplifier can be amplitude modulated. Frequency 3,000 to 30,000 KHz.....**\$3.75**



### 4. BAX-1 BROADBAND AMP

General purpose unit which may be used as a tuned or untuned amplifier in RF and audio applications 20 Hz to 150 MHz. Provides 6 to 30 db gain. Ideal for SWL. Experimenter or Amateur .....**\$3.75**



### 5. OX OSCILLATOR

Crystal controlled transistor type. Lo Kit 3,000 to 19,999 KHz, Hi Kit 20,000 to 60,000 KHz. (Specify when ordering).....**\$2.95**



### 6. TYPE EX CRYSTAL

Available from 3,000 to 60,000 KHz. Supplied only in HC 6/U holder. Calibration is  $\pm .02\%$  when operated in International OX circuit or its equivalent. (Specify frequency) .....**\$3.95**

## for the COMMERCIAL user...

### INTERNATIONAL PRECISION RADIO CRYSTALS

International Crystals are available from 70 KHz to 160 MHz in a wide variety of holders. Crystals for use in military equipment can be supplied to meet specifications MIL-C-3098E.

**CRYSTAL TYPES:** (GP) for "General Purpose" applications  
(CS) for "Commercial Standard"  
(HA) for "High Accuracy" close temperature tolerance requirements.



write for  
CATALOG



CRYSTAL MFG. CO., INC.  
10 NO. LEE • OKLA. CITY, OKLA. 73102

# four-band high-frequency windom antenna

The rebirth of  
the Windom antenna —  
a high performance  
multiband antenna  
popular in  
the 1930s

Hal Morris, W4VUO, 354 Krams Avenue, Philadelphia, Pennsylvania 19128

**Do you have antenna space limitations?** Can't swing a rotary beam? Need a good field-day antenna? Then the old standby, the Windom antenna, may be your answer. It offers four-band operation with a single feedline, and in most cases does not require an antenna tuner.

It's odd how ideas crop up in ham radio and then fade into oblivion. The Windom is a good, simple, multiband antenna system that is unheard of among today's hams. So, let's revive it and simplify the feed system. (This will be old hat to you if you remember when you weren't one of the boys on 75 meters unless you had an RME-45 receiver and a Windom antenna.)

## theory of operation

If the impedances present along the length of a half-wave dipole in free space are plotted, the values vary from about 3600 ohms at the ends to 72 ohms at the center. **Fig. 1** is a plot of antenna impedance versus length along a dipole. The center impedance of 72 ohms, coupled with the ease of using coaxial cable, has given rise to the extensive use of low-impedance feedlines and single-band dipoles. Today, open-wire feeders and other than 50- or 72-ohm coaxial feedlines are rare.

However, one way of feeding a dipole with open wire-line is to tap the antenna



equidistant from the center to match the feedline impedance. Fig. 2 illustrates a method of matching 600-ohm line to a dipole. Note that the dipole does not have to be split into two parts with an insulator. This is called the delta match and is used extensively by vhf enthusiasts for matching stacked arrays.

**preplanning**

Lets calculate the length required for a four-band antenna. Since the highest frequency band, ten meters, will be the most sensitive to antenna length, overall antenna length must be some multiple of a half-wavelength at ten meters. From the handbook formula for long-wire antennas

$$\text{length in feet} = \frac{492 (N - 0.05)}{\text{frequency (MHz)}}$$

where N is number of half waves.

For an antenna nine half-wavelengths long at 28.9 MHz, the length is slightly more than 152 feet. This is a bit long for 80-meter operation. Plugging in eight half waves and turning the crank gives

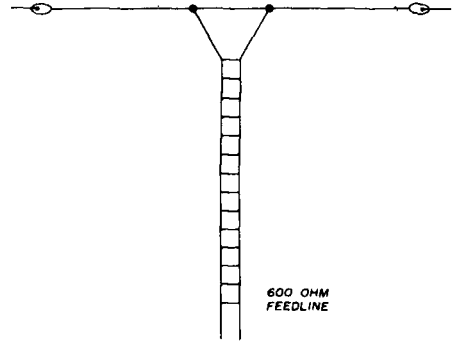


fig. 2. Classic single band antenna uses an open-wire feedline and a delta match. No center insulator is required.

135.342 feet. This looks good. Round the length off to 136 feet.

Now, using the formula for a half-wave dipole, and working backwards to find resonant frequency

$$f_{\text{MHz}} = \frac{492}{\text{length}} = \frac{492}{136} = 3.617 \text{ MHz}$$

This looks good. The 80- and 75-meter bandedge mismatch will be a small percentage of antenna length.

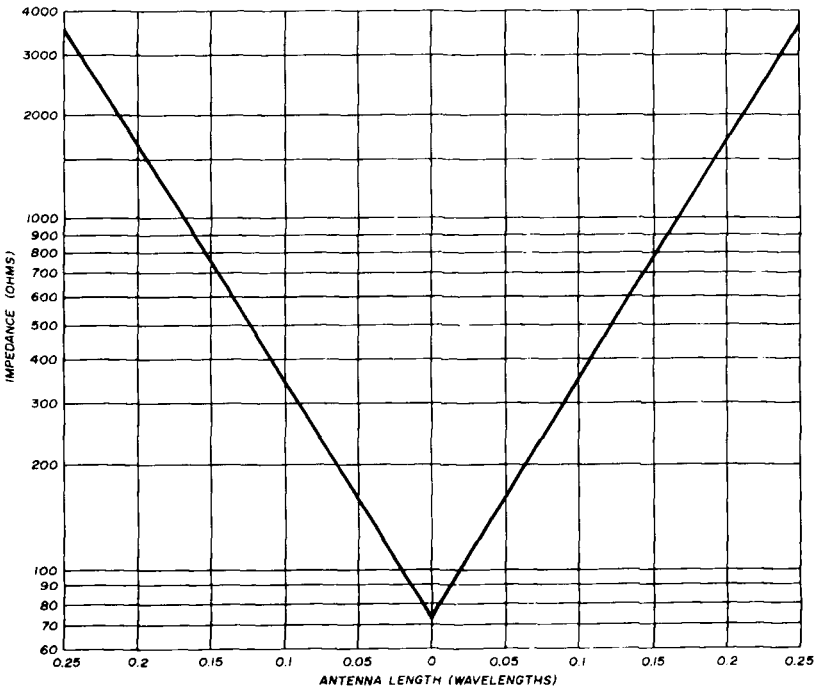


fig. 1. Plot of input impedance along a half-wave antenna in free space.

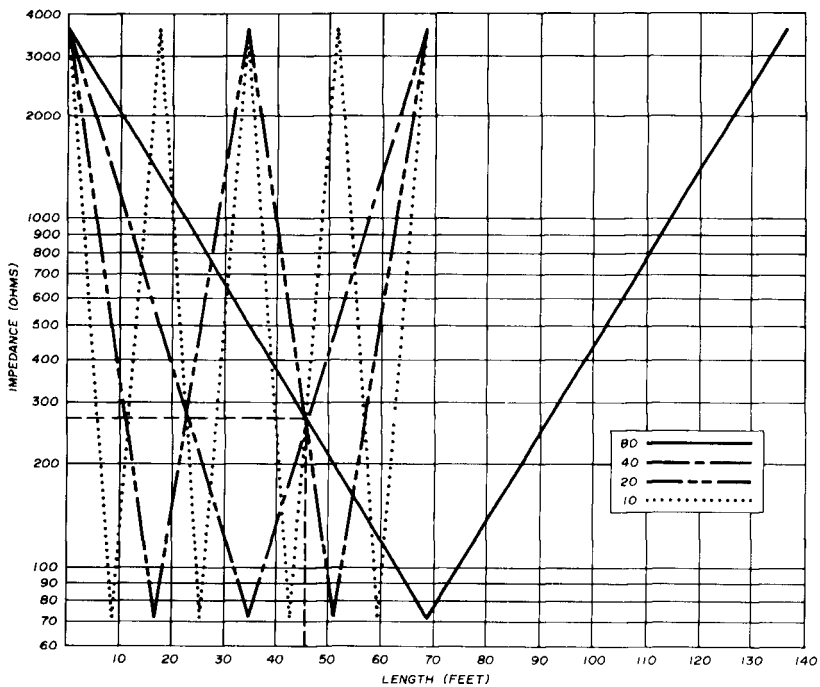


fig. 3. Impedance along a 136-foot antenna on 80, 40, 20 and 10 meters. Approximately 45 feet from one end of the antenna the impedance plots cross at 270 ohms — providing a fairly good match to 300-ohm feedline.

If the impedances present along this 136-foot antenna are plotted for the 80, 40, 20, and 10-meter bands, at a point 45 feet from one end, all four band plots cross at about 270 ohms (see fig. 3). If the antenna wire is broken at this point and the two wires are fed with 300-ohm twinlead, a fairly good match will be obtained for all four bands. In practice, certain lengths of feedline have been

found to be preferred for easier transmitter loading. These lengths are multiples of 44 feet.

The advantages of both types of feedline, coax and twinlead, can be achieved by combining the optimum length of 44-feet of 300-ohm twinlead with a balun to match 75-ohm coax. A random length of coax can then be run to the hamshack as shown in fig. 4.

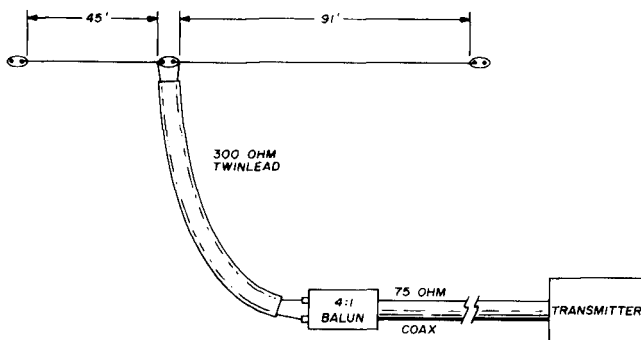


fig. 4. Windom antenna for four amateur bands uses 300-ohm twinlead, a 4:1 balun and 75-ohm coax to the transmitter.

## construction

After obtaining 140-feet of number-12 Copperweld antenna wire, three egg insulators and 50-feet of 300-ohm twinlead, you are ready to proceed. Using the dimensions shown in fig. 4, install the three insulators. The distances shown are *between* insulators. Attach the pre-measured 44-feet of 300-ohm twinlead (or multiples thereof) between the feed-point insulator and the balun. Install the antenna as high and as in the clear as possible.

Route the 300-ohm feedline away from the feedpoint at a 90-degree angle for as far as possible. The balun should be waterproofed if it is exposed to the weather. One method is to completely wrap it with Scotch Brand vinyl tape of the type used by electricians and carried by most hardware stores.

There are several good commercial broadband baluns on the market that can be used, as well as toroidal kits for assembling a kilowatt unit in a small Minibox. The *ARRL Handbook* provides construction details for an easily made toroid balun.

There is one note of caution that applies to any multiband antenna system. Any harmonics generated on the lower bands will be efficiently radiated by this antenna. A conventional antenna tuner can be substituted for the balun, or used at the transmitter end of the coax to eliminate harmonics reaching the antenna. However, the use of an antenna tuner defeats the basic simplicity of the balun-to-coax feed system with its automatic bandchanging and no tuning to fuss with. Several excellent antenna tuners have been described in the amateur magazines.<sup>1,2,3</sup>

## references

1. Ed Noll, W3FQJ, "Antenna Tuners," *ham radio*, December, 1972, page 58.
2. Gregory Widin, WB2ZSH, "Medium Power Toroidal Antenna Tuner," *ham radio*, January, 1974, page 58.
3. Ed Marriner, W6BLZ, "Match Box Antenna Tuner," *73*, September, 1966, page 38.

ham radio

All Mobile Antennas are NOT alike.

Larsen  
Antennas  
with  
exclusive  
Külrod®  
let you  
HEAR the difference!



Mobile Antennas should be judged on the basis of ruggedness, ease of installation and performance . . . mostly performance. Larsen Külrod Antennas are "solid" on all scores. They have a low, low silhouette for best appearance and minimum wind drag. Hi-impact epoxy base construction assures rugged long life. The Larsen mount gives you metal to metal contact, has only 3 simple parts and goes on fast and easily.

And performance! Larsen Antennas for the 144-148 MHz range deliver a full 3 db gain over a 1/4 wave whip. V.S.W.R. is less than 1.3 to 1. The exclusive Larsen Külrod assures you no loss of RF through heat. Handles full 150 watts.

It all adds up to superior performance . . . just one of many reasons why Larsen Antennas are the fastest growing line in the commercial field in both the U.S. and Canada. Available as antennas only or complete with mounting hardware coax and plug. Write today for fact sheet and prices.

Sold with a full money back guarantee.  
You hear better or it costs you nothing!

## Need a BETTER 450 MHz Antenna?

Get the Larsen 5 db gain Phased Collinear. Same rugged construction and reliability as the 2 meter Larsen Antennas including exclusive Külrod. Write for full fact sheet.



©Külrod . . .  
a trademark of Larsen Electronics

**Larsen Antennas**

1161 N.E. 50th Ave. • Vancouver, WA 98665  
Phone: 206/695-5383

For fastest mail service address:  
P.O. Box 1686 - Vancouver, WA 98663

## spurious causes

While intruder-watching, and doing associated Official Observer work when an unusual signal turns out to be amateur rather than an intruder, much is learned about the causes of troubles.

Recently, there have been noted many cases of key chirps or clicks spaced many kilohertz from the normal signal. Sometimes it is noise, which may be keyed normally or back-keyed, or voice peaks in phase with the desired signal. Several hams have found tubes to be the cause, though plugging the offending tube back in the same socket may not again give trouble.

It has been suggested that this may be the result of generation of spurious frequencies due to a temporarily corroded tube pin or socket contact, which is self-cleaned by removing the tube and plugging it in again.

Therefore, it is suggested that all tubes in transmitters and receivers, particularly those associated with the generation of the transmitted signal, periodically be wiggled or even pulled out and plugged back in. It would seem that this could be done several times a year, to keep contacts clean, so that some screen or suppressor does not lose its voltage or its rf ground connection.

Bill Conklin, K6KA

## line voltage monitor

It should be of interest to most hams to know the deviation from normal line voltage available at any time in their shack. Several line voltage monitors have been described, but these generally have

been complicated by incorporating features that are not necessarily required. Self-calibration, for instance, requires a significant increase in the number of components as well as requiring high-cost, precision items.

The expanded scale-line voltage monitor I have built reduces the number of components significantly and does not compromise the accuracy to any great extent. As indicated by the schematic in

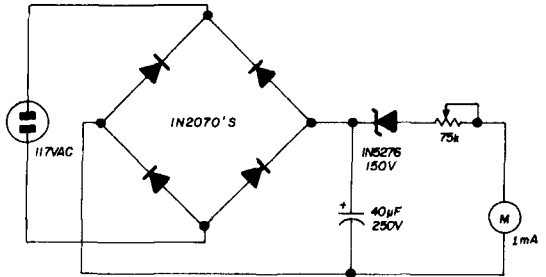


fig. 1. Simple expanded-scale line-voltage monitor reads from 115 to 125 volts on a 1-mA meter. Calibration is discussed in the text.

fig. 1, it consists of five active components, all of which were scrounged from my junk box.

However, for the recently licensed ham who may not have accumulated any sort of junk box, the cost of new parts, including the Minibox, cord terminal strips, etc., is under \$7.50 (half of which goes for the milliammeter).

The whole circuit is mounted on terminal strips, so isolated from the chassis. Calibration was accomplished on a one-time basis using a Variac and a Simpson vom. With the Variac adjusted for 120 volts ac, the potentiometer was adjusted to give a mid-scale reading. The voltage was varied to 115 volts ac and 125 volts

ac and the meter indication went to either end of the scale.

Intermediate points at 1-volt intervals were marked on the face of the meter for instant reference. Although a trace of non-linearity was detected on the high side the line-voltage monitor tracked remarkably well to within a few percent.

Finally, if it is desired to obtain a larger variation (i.e., plus or minus 10 volts or some other value) a lower value zener, 140 volts or lower, may be substituted.

Alfred J. Parker, WA8VFK

## two-meter power amplifier

TRW Semiconductors has announced the first in a series of reasonably priced, npn power transistors designed specifically for amateur radio equipment. The first transistor in the series, the PT5757, provides 10-watts output at 150 MHz with a 12.5-volt power supply and is designed for operation on the 2-meter amateur band. A single PT5757 will boost the 1-watt output of a 2-meter rig to 10 watts. A simple circuit is shown in fig. 2.

The PT5757 can also be amplitude

single quantities, and is available from any TRW distributor or from Ham Radio Center, 8342 Olive Boulevard, St. Louis, Missouri 63132.

Jim Fisk, W1DTY

## ic lead former

In making layouts for printed-circuit boards and in using breadboard circuits, difficulty has been encountered in connecting TO-5 can leads. Since the standard dual-inline-pack (DIP) configuration is very convenient for these applications, I decided to use this configuration for all ICs.

To accomplish the above, a lead former was constructed by drilling two rows of holes, 0.3 inch apart, with holes spaced on 0.1 inch centers in a piece of scrap printed circuit board stock. To use the lead former, the IC leads are inserted in appropriate holes, the IC pressed down, and the leads trimmed on the reverse side of the former.

In some applications, it is more convenient to use alternate holes (0.2 inch spacing) to provide additional spacing for an 8-lead IC such as the CA3028A. With this spacing, an 8-lead IC fits a standard

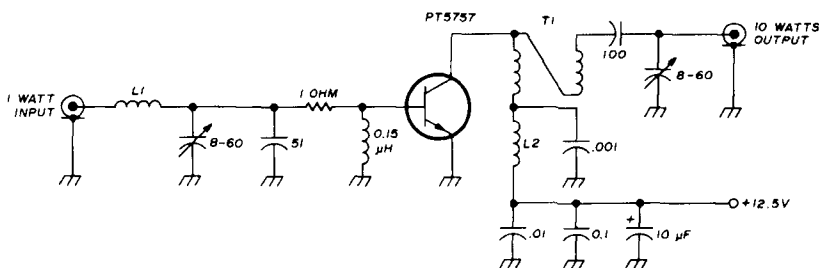



fig. 2. 10-watt 144-MHz power amplifier using the new TRW PT5757 transistor. L1 is 4 turns no. 20 enamelled, 3/32" ID; L2 is 10 turns, no. 20 enamelled, 3/32" ID. Transformer T1 is a 4:1 transmission-line transformer made from a 3" length of twisted pair, no. 20 enamelled wire.

modulated to approximately 60% without damage. Ideal for mobile operation, the PT5757 has better than 70% collector efficiency at 10 watts and 12.5 volts. For hand-held rigs at reduced power, excellent performance can be obtained with collector voltages as low as 8 volts. Best of all, the PT5757 is priced at \$10.00 in

14-pin DIP socket. For further simplification, the unused leads of the IC may be clipped off near the can before connection.

This simple device provides a means of forming TO-5 can leads for the experimenter, simplifying his layouts.

Bill Stauffer, W5ICV

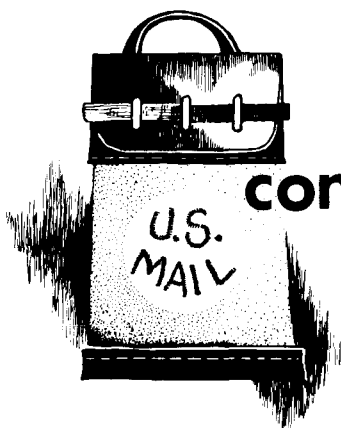

# comments

## receiver selectivity

Dear HR:

There have been articles over the years, and several recently, outlining the advantages and desirability of improving the front-end selectivity of the receiver. To see how a receiver of recent design checked in this respect, I checked out a Hammarlund HQ-215. This is a solid-state version of the Collins 75S receiver. Both have a 200-kHz bandpass i-f between the first and second mixers. The HQ-215 has

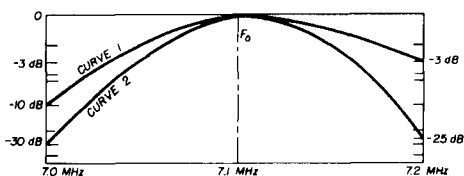


fig. 1. Passband characteristics of the HQ-215. See K4ZZV's letter for operating conditions for curves 1 and 2.

three tuned circuits ahead of the first mixer — the 75S only two.

It can be seen from fig. 1 (curve 1) that there is quite a wide passband to the incoming signals as far back as the second mixer input where the signal was recorded without agc. This was taken with the original rf swamping resistors removed to help the selectivity as much as possible!

Curve 2 was run with the i-f swamping resistors removed and everything peaked up for the band center. There are four tuned circuits in the HQ-215's first i-f.

Nothing was changed in their intercoupling. Quite an improvement in the selectivity can be seen.

The noise figure of the receiver was halved with the additional gain so the first rf tuned circuit was stepped down enough to restore the original noise figure which would also improve the front-end overload characteristics. It looks like the next project should be a vari-cap network ganged to the vfo to make full use of the improved first i-f selectivity.

There are receivers that do tune the first i-f to their advantage. The Collins 75A4 is a good example. Getting as much selectivity as close to the antenna as possible really makes for the ultimate in reception. If one wants to confine their operation to a few Hz as the fixed-channel stations do, or guard a special traffic net frequency, a crystal filter at the antenna input is just the thing to clean things up. Maybe some day a variable frequency filter will be developed that will do what a few coupled LC circuits cannot.

There are trade-offs in receiver design though, and at least one solid-state receiver uses a tube in the front-end to handle the strong signals. It should make the old timers happy to know that tubes are still being used in modern design.

Wayne W. Cooper, K4ZZV  
Miami Shores, Florida

## code speed

Dear HR:

I certainly enjoyed VE2ZK's recent article on code speed, which mentioned that the FCC and ARRL use 50-bit words such as PARIS to establish the speed, and other government agencies use the 60-bit word CODEZ.

As a series of dots have equal "up-key" spaces between them, a string of dots is actually a number of dot cycles. Thus 25 dot cycles is the same as 50 continuous bits. This might clarify the author's mention of dividing by 25 to get the speed.

However, one of the most simple methods of determining speed without any mathematics is to merely send continuous number one (1) characters. Count the number sent in 24 seconds and this is the wpm for 50-bit rate. For 60-bit rate, count the 1's sent in 20 seconds. You could also use a digital counter with an automatic keyer although some counters might give erroneous results on the pulsed output of the keyer. Divide the counter reading by 25 to indicate wpm. It should at least get you in the ballpark, and many amateurs own digital counters these days.

The article was very interesting and it is the first time I can recall any author attempting to explain the 50- and 60-bit words and where they are used.

Irv Hoff, W6FFC  
Los Altos Hills, California

## attenuation pads

Dear HR:

I found the comments by Mike Goldstein, VE3GFN, on tuner overload memory in *ham notebook* of the January, 1973, issue, provoking. The problem I had was with converter overload when I was operating on 6 meters. Two other hams in my town who operated on 6 meters lived within half a block of me, so the old tubes of the converter would really light up when either of them came on.

I wanted to attenuate incoming signals without changing the impedance of my receiving system. A T-pad is just the device to do that. The Mallory RT-50, a 50-ohm pad, while designed for audio work, performed beautifully for me. As an experiment, I put it between my Heath Mohawk and the International Crystal converter and found that with the attenuation control set to zero, signals came in stronger on the Mohawk with the

T-pad in the circuit than without it. I attribute this to better impedance matching created by inserting the T-pad between the converter and receiver. The pad would not only be helpful for converter overload due to strong signals, but also to receiver overload caused by too much converter output.

The Mallory RT-50 pad comes with knob, dial plate, mounting hardware and hook-up instructions, and can be obtained from many electronic stores and mail-order houses. If you have difficulty obtaining one, you can send \$3.60 plus postage to Scott Electronic Supply Corporation, 4040 Adams Street, Lincoln, Nebraska 68504.

James Worrest, KØHNO  
Lincoln, Nebraska

## sporadic-E openings

Dear HR:

The article on predicting sporadic-E openings by Morrie Goldman in your October, 1972, issue is quite informative. In fact, its usefulness extends beyond the author's original purpose. Several times in the past I have been plagued with spurious responses in my receiving equipment which were caused by the presence of nearby high-power paging transmitters. Your **table 1** will be quite useful in chasing down these problems in the future.

A second point which radio amateurs should find useful is the direct correspondence between **table 2** and our amateur call areas.

W0, K0	KA, KB	W5, K5	KK, KL
W1, K1	KC, KD	W6, K6	KM, KN
W2, K2	KE, KF	W7, K7	KO, KP
W3, K3	KG, KH	W8, K8	KQ, KR
W4, K4	KI, KJ	W9, K9	KS, KT

This correspondence makes it unnecessary to have to continually refer to the chart while monitoring a band opening.

Lewis D. Collins, K4GGI  
Arlington, Massachusetts

# new products

## motorola vhf-fm radio for amateurs



Motorola, long a leader in two-way vhf-fm equipment, has now entered the amateur vhf-fm market through their subsidiary, Modar Electronics Inc., with the introduction of the new *Metrum II* two-meter vhf-fm radio. This radio, which covers the 144-148 MHz amateur band, is totally solid-state unit with a number of unique features. It is offered in 10- and 25-watt versions, both switchable to 1 watt.


The modern, attractively styled line features a shadow bronze finish, 12-channel capability, the dependable Motorola microphone and field-proved circuitry. It incorporates a rotary on/off volume control, a variable squelch control, an illuminated control instrument panel, detent high-low power, detent repeater input and two detent auxiliary switches for custom adaption by the radio operators.

With built-in antenna mismatch protection, the *Metrum II* radio will continue functioning without damage to the unit even if the antenna is damaged, disconnected or improperly connected. Reverse polarity protection provides added safeguards against improper installation.

A specially designed reversible control panel allows the radio to be mounted in almost any position while maintaining clear visibility of all controls. A universal mounting tray permits installation at virtually any location. Indirect, non-glare back lighting of the *Metrum II* control panel means all controls can be read easily. Optional accessories include ac power supply, quarter-wave whip antenna, crystals, dimmer mod kit and rf indicator kit.

Manufacturer's suggested list prices for the 25-watt, 12-channel model and the 10-watt, 12-channel model version are set at \$499.95 and \$399.95, respectively. For further information on the *Metrum II* fm amateur radio, write to Modar Electronics, Inc., 2100 North Meacham Road, Schaumburg, Illinois 60172, or use *check-off* on page 110.

## fm modulation meter

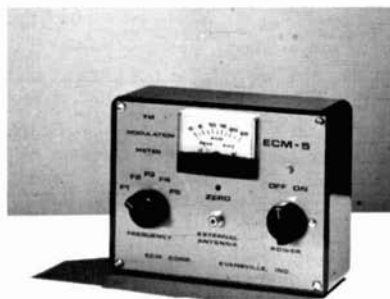

The ECM Corporation has announced the first commercially available fm modulation meter designed especially for the amateur. The ECM-5 covers all ham bands between 52 and 450 MHz, and features a peak reading meter. Deviation of any fm transmitter can be accurately adjusted between 5 kHz and 25 kHz in seconds, using voice or tone modulation.



The ECM-5 fm modulation meter closely follows the circuits used in professional equipment except that frequency is crystal controlled. This allowed ECM engineers to eliminate many expensive circuits needed only when frequency selection is vfo controlled. The net result was a tremendous reduction in price without sacrificing quality. The frequency selecting crystals are the popular, subminiature, third-overtone type used in many of today's fm receivers. These crystals were chosen for their low price and availability.

The peak reading meter has a special time-constant circuit that causes the needle to deflect upscale rapidly and downscale slowly. This allows the needle to follow voice peaks and increases the accuracy of readings when checking deviation using voice modulation. Other features include a builtin or external antenna, all solid-state construction, battery powered by inexpensive AA pencils, and a battery condition indicator.

The ECM-5 is priced at a low \$75.00, less batteries and crystals. For more information, write ECM Corporation, 412 North Weinbach Avenue, Evansville, Indiana 47711, or use *check-off* on page 110.

## multifrequency antennas


An antenna farm in your own backyard! That is what Don McVicar, VP7DX/VE2WW, has claimed to have developed in his new Mark IV, V and VIII multifrequency directional wire beams. Don has been experimenting many years with antennas and has developed an all-band antenna system which is economical, mechanically sound, inconspicuous and easy to install. It gives good gains with a low angle of radiation at moderate installation heights.

Electrically, the Mark IV antenna has a minimum theoretical forward gain over a reference dipole of about 5.5 dB. While this is encouraging, consistent forward gains of up to 3 S-units have been achieved on both transmission and recep-

\* patents pending

new Slinky® dipole\* with helical loading

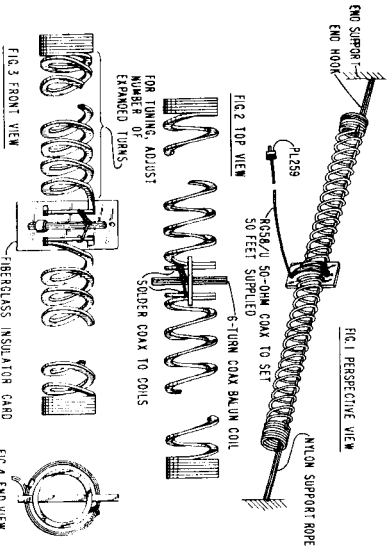radiates a good signal at 1/10 wavelength long!



- This electrically small 80/75, 40, & 20 meter antenna operates at any length from 24 to 70 feet • no extra balun or transmatch needed • portable — erects & stores in minutes • small enough to fit in attic or apartment • full legal power • low SWR over complete 80/75, 40, & 20 meter bands • much lower atmospheric noise pickup than a vertical • kit includes special 4" coils, balun, 50 ft. RG58/U coax, PL259 connector, & nylon rope • this new antenna was developed for a government application, and really works •

Send for your antenna to: code HR  
**TELETRON CORP.**, 2950 Veterans Hwy., Bohemia, L.I., N. Y. 11716  
 Kit #80-40-20 \$29.95 plus \$1 shipping  
 Coils only (pair of 4" dia. special coils) \$17.95 plus \$1 shipping  
 (N. Y. residents add 7% sales tax)  
 name.....  
 street.....  
 town..... zip.....  
 enclose check with order - we ship UPS upon receipt of order

## FREQUENCY STANDARD



Only  
**\$32.50**  
(less batteries)  
POSTPAID USA

- Precision crystal
- Fully guaranteed
- Markers at 100, 50, 25, 10 or 5 kHz selected by front panel switch.
- Zero adjust sets to WWV. Exclusive circuit suppresses unwanted markers.
- Compact rugged design. Attractive, completely self contained.
- Send for free brochure.

## PALOMAR ENGINEERS

BOX 455, ESCONDIDO, CA 92025

### 46 Element Multibeam For 432 MHz Band

The ultimate UHF antenna for long distance communication. #70/MBM 46



Gain: 17.3 dB over Dipole  
Length: 104"; Width: 18"  
Weight: 6 Lbs.  
Hor. Beamwidth (-3 dB: 24°)



Broadband — works over entire  
420-450 MHz. Band.

**70/MBM 46 \$52.50 FOB**

VHF Communications Magazine  
1974 Subscription Rate \$5.75

Distributor



## VHF COMMUNICATIONS

EAST

WEST

915 N. MAIN ST.

53 ST. ANDREW

JAMESTOWN, N. Y. 14701 RAPID CITY, S. D. 57701

tion. Don assumes that these low-angle gains are due to the sloping inverted-vee configuration. On 40 and 80 meters the front-to-back and front-to-side ratios are from 9 to 20 dB and deep pattern nulls are not evident. On 20, 15 and 10 meters the front-to-back and front-to-side ratios vary between 12 and 30 dB. The feed-point impedance is 52 ohms, power capacity is 2-kW PEP and the antenna uses a single-line, all-band feed system.

Mechanically the system consists of two or more sloping inverted-vee antennas, one-half or 3/2-wavelengths long, fed at their apex through a unique rf switch which causes the elements to react parasitically on one another. The switch is built for heavy-duty outdoor use. The antenna wire (not supplied) can be number-14 or equivalent, and the system tends to be self guying.

The rf switch may be installed on an existing rotator shaft beneath a Yagi or quad on any mast or tower such as an inexpensive 50-foot telescoping mast. For more information on this unique antenna system, write to World Wide Antennas, Box 467, Miami Springs, Florida 33166, or use *check-off* on page 110.

### triggered-sweep 10 MHz oscilloscope




The new Eico Model TR-410 oscilloscope claims to be the industry's lowest priced lab quality, wideband triggered-sweep oscilloscope. It is expressly designed for speedy precision servicing, lab work, production testing and vocational instruction with such advanced features as automatic sweep which locks with complex tv signals, 10-MHz bandwidth,

all solid-state design with protected fet input stage, and single dual probe to convert quickly from direct to 10:1 low capacitance operation. The instrument may be operated from a standard 120-volt line, low 100-volt or 220-230 volts — all 50/60 Hz. Included are three calibration voltages, 2, 5 and 10. The horizontal and vertical dc balance controls are adjustable with a screwdriver from the front panel for convenience and accuracy. Included are vertical and horizontal selection of ac or dc modes of amplification. The gate signal is available at a jack to enable the operator to synchronize other equipment to the trace displayed on scope. The astigmatism control is on the rear panel because once it has been set, readjustment is seldom, if ever, required. The removable sides, top and bottom provide easier and more accurate servicing and calibration. Standard bezel and bushings are provided for camera mounting.


The new Eico model TR-410 oscilloscope is priced at \$379.95 and is available from your local Eico dealer. For more information, use *check-off* on page 110.
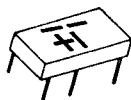
## voltage-controlled attenuators

An economical series of three voltage controlled PIN diode attenuators cover the frequency range of 5-200 MHz for agc or leveling or other closed loop applications. Models VCA-1, 40 dB, 5-100 MHz; VCA-2, 30 dB, 5-100 MHz; VCA-3, 20 dB, 5-200 MHz; are offered. Maximum insertion loss is 6 dB. Vswr varies from 3.0 to less than 1.5:1, depending upon the attenuation setting. Rise and fall times of attenuation to specified values permit wideband modulation of rf signals. Units require up to 105 mA supply current and less than 5 mA control current. Positive or negative supply and control voltages may be specified. Connectors available include BNC, JCM (SMA compatible) and TNC. For more information, use *check-off* on page 110, or write to Radiation Devices Company, Post Box 8450, Baltimore, Maryland 21234.



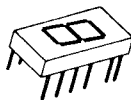
Uses Standard 7447 Decoder-driver. Seven Segment Readouts. All tested and guaranteed. Specs included. Fit standard 14 pin DIP socket. Full .335 inch high. Color, RED.  
Less Decimal \$2.00 ppd.  
With Decimal \$2.25 ppd.  
With Colon \$2.50 ppd.



Same unit only contains numeral 1 and plus and minus sign. \$2.25 ppd.

GI Printed Circuit type bridge rectifiers.

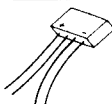200 v PIV @ 1.5 A  
50¢ ea or 3 for \$1.25  
400 v PIV @ 1.5 A  
60¢ ea or 3 for \$1.75



LED Pilot Lites.  
Full 3/16 inch Dia.  
4 for \$1.00 ppd.



JUMBO Seven Segment Readouts. Full .770 inches high. RED. Uses 7447 Decoder-driver. Specs included.

With Decimal point. \$5.00 ppd.  
Same unit only numeral 1 and plus & minus sign. \$5.00 ppd.




**NEW NEW NEW**  
6 foot Koil-Cord with molded PL-55 plug. Very nice.  
75¢ Each, 3 for \$2.00 ppd.

General Purpose Germanium Diodes.  
Similar to 1N34a etc. 16 for \$1.00 ppd.  
All Cathode banded. 100 for \$5.00 ppd.  
Full leads. 1000 for \$40.00 ppd.
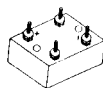
## NEW

Transformer — American Made — Fully shielded. 115 V Primary. Sec. — 24-0-24 @ 1 amp with tap at 6.3 volt for pilot light.  
Price — A low \$2.90 each ppd.

400 Volt PIV at 25 Amp. Bridge Rectifier.  
\$4.00 ea. or 3 for \$10.00 ppd.



6.3 Volt 1 Amp Transformer. Fully Shielded  
\$1.60 Each ppd.

## NEW

JUST ARRIVED — Transformer, 115 VAC primary, 18 volt, 5 amp ccs or 7 amp intermittent duty secondary \$6.00 ea. ppd.

## NEW NEW

TRANSFORMER. 115 volt primary, 12 volt 1/2 amp secondary. \$1.50 ppd.



Featherweight TO-5 Heat Sinks  
2 for 25¢ ppd.

Major Brand 2N706 Transistors.  
3 for \$1.00 ppd.



Miniature Terminal Strips.  
1" Long x 1/2" High. 3 Term. plus Ground  
20 for \$1.00 ppd.

SEND STAMP FOR BARGAIN LIST  
Pa. residents add 6% State sales tax  
ALL ITEMS PPD. USA

**m. weinschenker**  
K 3DPJ BOX 353 · IRWIN, PA. 15642

## CW FILTER



**New Model CWF-2BX—\$19.95.**  
Ready to use. Please include  
\$1.00 postage.



**Model CWF-2—\$12.95, Kit.**  
\$14.95 Wired, tested, guaranteed.  
Please include 55¢ postage.

- Get Razor Sharp selectivity from any receiver or transceiver.
- Extremely high skirt rejection
- Drastically reduces all background noise.
- No audible ringing.
- No impedance matching.
- Ultra modern active filter design uses IC's for super high performance.

We have what we think is the finest CW filter available anywhere. The 80 Hz selectivity with its steep sided skirts will allow you to pick out one signal and eliminate all other QRM and QRN. Simply plug it into the phone jack or connect it to the speaker terminals of any receiver or transceiver and use headphones, small speaker, or speaker amplifier. Better yet, connect it between any audio stages to take advantage of the built-in receiver audio amplifier. Build the 2+3 CW-F-2 PC card into your receiver or get the self contained ready to use CWF-2BX and plug in!

### SPECIFICATIONS

**BANDWIDTH:** 80 Hz, 110 Hz, 180 Hz, 180 Hz (Switch selectable)  
**SKIRT REJECTION:** At least 60 db down 1 octave from center frequency for 80 Hz bandwidth  
**CENTER FREQUENCY:** 750 Hz  
**INSERTION LOSS:** None. Typical gain 1.2 at 180 Hz BW, 1.5 at 110 Hz BW, 2.4 at 80 Hz BW  
**INDIVIDUAL STAGE Q:** 4 (minimizes ringing)  
**IMPEDANCE LEVELS:** None. Impedance matching required  
**POWER REQUIRED:** CWF-2: 6 volts (2 ma.) to 30 volts (8 ma.). CWF-2BX: standard 9 volt transistor radio battery.  
**DIMENSIONS:** CWF-2: 2+3" PC board. CWF-2BX: 4+3 1/4" x 2 3/16" (black wrinkle steel top, white aluminum bottom, rubber feet)

TRY this fantastic CW filter. If you don't think it is the best you have ever used, ask for your money back. We will cheerfully refund it. These filters carry a full one year warranty.

Write for FREE brochures and magazine test reports. Other IC active filters available: CW mini filter (1+1/2" x 2"), low pass, high pass, and wide bandpass filters. Audio amplifiers: (1+1/2" x 2"), watts. Crystal calibrator.

### MFJ ENTERPRISES

P. O. Box 494-A, Mississippi State, MS 39762

## low-noise 432-MHz preamps



As part of an expanding line of quality vhf/uhf products, Janel Labs has announced a series of 432-MHz preamps. Four models are available, offering low noise figures in a choice of two price ranges, each having the option of an ac power supply. Models without power supply (432PA and 432PC) have a compact sheet aluminum enclosure while those with power supply (indicated by the suffix -1) feature a rugged cast-aluminum case.

The gain of all models is an ample 20 dB. The 3-dB bandwidth is about 20 MHz. Stock units can be supplied for any center frequency between 420 and 470 MHz. Other frequencies are available on special order.

The basic circuit is a two-stage amplifier. This uses a KMC bipolar transistor first stage and a 3N159 dual-gate mosfet second stage. The 432PA uses a K2073 first stage to produce an outstandingly sensitive 3.5-dB noise figure. The 432PC uses the new K6007 to achieve an extremely sensitive 1.5- to 2.0-dB noise figure. The low cost 432PA and 432PA-1 are expected to see wide use for 450-MHz fm as well as for general purpose applications such as DX, ATV, and OSCAR.

The 432PC and 432PC-1 meet the needs of the most demanding applications such as moonbounce and weak-signal CW work. Prices range from \$29.95 for 432PA to \$94.95 for the 432PC-1. All are postpaid and guaranteed. For more information, write to Janel Laboratories, Box 112, Succasunna, New Jersey 07876, or use *check-off* on page 110.

## FREE CATALOG

CRAMMED WITH GOV'T SURPLUS  
ELECTRONIC GEAR **WRITE TODAY!**



### BC-348 RADIO RECEIVER

200-500 Kc & 1.5 18 Mc, 8-Tube  
6-Band Communications Receiver, Excellent  
Used, with tubes and Dynamotor.  
Checked out..... **\$58.50**

### BC-603 FM RECEIVER

Converted for 35-50 mHz. 10 preset pushbutton  
channels or manual tuning. Complete with 10  
tubes, checked out, like new..... **\$36.50**

AC Power Supply, New..... **\$14.95**  
DM-34 12V Power Supply, New..... **\$ 4.45**  
DM-36 24V Power Supply, Exc. Used..... **\$ 2.25**  
Technical Manual..... **\$ 2.50**  
Set of 10 tubes for BC-603 Receiver..... **\$ 5.95**



### TG-34A CODE KEYS, self-contained, automatic, reproduces code practice signals from paper tape.

5 to 12 WPM Built-in speaker. Brand new with tech  
manual, takeup reel and AC line cord. **\$24.50**  
Code practice tapes for above P.U.R.



**BC-1206-C RECEIVER** Aircraft Beacon Re-  
ceiver 200 to 400 Kc. Operates from 24V DC 1.5A.  
Continuous tuning, vol control, on-off switch and  
phone jack. Very sensitive. Compact.  
Complete with tubes, NEW..... **\$12.50**



**APN-1 FM TRANSCEIVER 400-500 Mc. \$9.95**


**R-4/ARR-2 RECEIVER 11 TUBE, NEW, \$8.95**

## G&G RADIO ELECTRONICS COMPANY

45-47 Warren St. (Dept. H-D) New York, N.Y. 10007 212-267-4605

TERMS: F.O.B. NYC. 2% deposit with order, balance COD or remittance  
in full. MINIMUM ORDER \$5.00. Subject to prior sale and price change.

## rf directional couplers

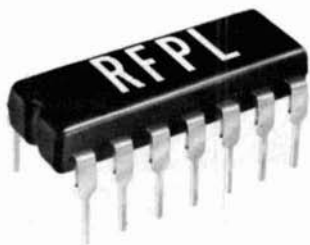

RF Power Labs have introduced a new line of low-cost miniature wideband rf bidirectional couplers which should be very useful to amateurs who build their own high-frequency and vhf equipment. These versatile couplers can be used for power sampling for waveform monitoring and power level checkpoints, for load impedance and vswr measurements, and for direct readout of forward and reflected power over wide frequency ranges with excellent accuracy. Units are available in both dual-inline packages and *flat pak* configurations, and are capable of handling rf power levels up to 3 watts over their specified bandwidth.

Four models of the bi-directional coupler are available: the DC-14/14A, covering 2 to 300 MHz; the DC-14B/14C, covering 1 to 300 MHz; the DC-14D, covering 500 kHz to 100 MHz; and the DC-14E, covering 50 kHz to 100 MHz. Prices in small quantities range from \$13.90 to \$15.90 each. For more information, write to R.F. Power Labs, Inc., 92 - 104th Ave. N.E., Suite 103, Bellevue, Washington 98004, or use *check-off* on page 110.

## digital catalog

ES Enterprises has announced the availability of a new 6-page catalog that describes their total line of digital products. Standard products include low cost programming instruments and controls, timers, clocks, counting and measuring devices. Also included is a complete listing of their modular display units for custom digital instrumentation

More Details? CHECK-OFF Page 110

# NEW RINGO RANGER

## for Amateur FM

Get extended range with this exciting new antenna. A one eighth wave phasing stub and three half waves in phase combine to concentrate your signal at the horizon where it can do you the most good.

6.3 dB Gain over  $\frac{1}{4}$  wave whip

4.5 dB Gain over  $\frac{1}{2}$  wave dipole

ARX-2 146-148 MHz  
\$22.50

ARX-450 435-450 MHz  
\$22.50

ARX-220 220-225 MHz  
\$22.50

Extend your present AR-2 Ringo with this RANGER KIT. Simple installation.

ARX-2K .....\$8.95

IN STOCK AT  
YOUR LOCAL DISTRIBUTOR

Cush  
Craft  
CORPORATION

621 HAYWARD STREET  
MANCHESTER, N. H. 03103

## 6T-HR2

6 frequency crystal deck  
Improved circuit board, layout  
and foil.



INCREASES THE REGENCY HR-2 OR HR-2A RADIOS TRANSMIT CAPABILITY TO SIX ADDITIONAL FREQUENCIES. NO MAJOR CHANGE HAS TO BE MADE TO THE RADIO WHEN INSTALLING THE 6T-HR2 DECK

KIT ..... \$ 9.95      WIRED ..... \$13.95

## HF144U MOS FET PREAMP



OUR FAMOUS 2-METER PRE-AMP STILL OUTSTANDING IN THE HIGH BAND PRE-AMP FIELD GIVES 17dB OF AMPLIFICATION WITH ONLY 3dB OF NOISE INSERTION.

KIT ..... \$11.95      WIRED ..... \$17.95



## SCAN-2

with search back

DECKS MOUNTS IN HR-2 WITH OUT ANY MAJOR MODIFICATION TO THE RADIO. GIVES USER A SCANNING TYPE RADIO AT A FRACTION OF THE COST. INCORPORATES "SEARCH BACK" A NEW AND EXCITING FEATURE TO SCANNING TYPE OPERATION.


WIRED ONLY ..... \$19.95



Topeka FM Communications and Electronics  
125 Jackson, Topeka, KS 66603 · 233-7580 or 2343



WRITE FOR  
FREE 1974  
CATALOGUE

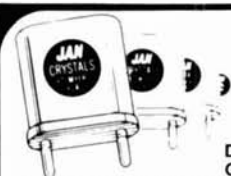

## For FREQ. STABILITY

Depend on JAN Crystals.  
Our large stock of quartz  
crystal materials and components assures Fast  
Delivery from us.

### CRYSTAL SPECIALS

2-METER FM for most Transceivers ea. \$3.75  
144-148 MHz — .0025 Tol.

Frequency Standards  
100 KHz (HC 13/U) 4.50  
1000 KHz (HC 6/U) 4.50

Almost all CB Sets, Tr. or Rec. 2.50  
(CB Synthesizer Crystal on request)

Any Amateur Band in FT-243 1.50  
(80-meter, \$3.00 - 160-meter not avail.) 4 for 5.00

For 1st class mail, add 20¢ per crystal. For  
Airmail, add 25¢. Send check or money order.  
No dealers, please.



Division of Bob Whan  
& Son Electronics, Inc.  
2400 Crystal Drive  
Fl. Myers, Florida  
33901


All Phones  
(813) 936-2397

Send 10¢ for new catalog with 12 oscillator  
circuits and lists of frequencies in stock.

and a section outlining their digital clock, multimeter and frequency counter kits.

The catalog contains descriptions of basic features, custom capability, standard options and warranty information. A price list and ordering instructions accompany the catalog. For a copy of the catalog, write to ES Enterprises, 10418 La Cienega Boulevard, Inglewood, California 90304, or use *check-off* on page 110.

## general-coverage receiver

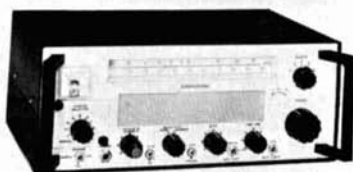

Up to ten crystal-tuned frequencies can be preselected for drift-free automatic tuning on the latest high-quality general-purpose communications receiver from the British firm of Eddystone. The Model 1001 receiver has the unusual feature of a rechargeable internal power supply, consisting of a nickel-cadmium cell, which serves as a temporary standby in case of main circuit failure. The set will also work off an external 12V dc battery supply.

Covering frequencies from 550 kHz to 30 MHz, the set incorporates automatic gain control, wide/narrow selectivity control, carrier-level meter and both coarse and fine tuning knobs.

Frequency calibrations for tuning are marked on a horizontal scale drum which splits the 550-kHz to 30-MHz range into five bands. The scale display is about 6-1/2" long; a secondary scale below the main calibration can be used in conjunction with a vernier dial to provide a useful logging facility. Dial illumination can be switched on and off.

Aimed at the serious radio amateur, short-wave listener and DXer, the Model 1001 is designed to the most stringent

professional specifications, and incorporates a variety of solid-state devices including integrated circuits and field-effect transistors. It drives its own pair of miniature speakers, and has output facilities for headphones, external speaker and tape-recorder. Price of the Model 1001 is about \$900 delivered, including duty and taxes. The North American distributor will welcome inquiries from U.S. customers and prospective dealers. Write to Conway Electronic Enterprises Ltd., (Mr. J.W. Cave, General Sales Manager) 88/90 Arrow Road, Weston, Ontario, Canada, or use check-off on page 110.

## radio transmitter principles and projects

Amateur radio operators, communications technicians and transmitter experimenters will profit from this new and completely up-to-date book by Ed Noll, W3FQJ. Devoted entirely to the subject of radio transmitters, this book also is perfect for those studying for the various grades of amateur or commercial FCC license examinations.

The first three chapters contain information on electron devices — the fet, bipolar transistor and the vacuum tube. Different modes of modulation — CW, a-m, fm and ssb — are discussed in other sections. Chapter 4 describes hybrid transmitter circuits using tubes and transistors. Double-sideband and single-sideband generation and circuits are covered in Chapter 5. There is a chapter on linear amplifiers and mixers; another explains integrated circuits. The final three chapters cover vhf circuits, frequency modulation and transmitter testing.

Each chapter begins with basic principles and advances to more detailed information. The projects are based on the basic principles and are designed to further the reader's understanding through actual experience. They also provide the radio amateur with complete plans to build his own gear. 320 pages, \$6.95 (softbound). Order from Comtec Books, Greenville, New Hampshire 03048.

**NES**

### NURMI ELECTRONIC SUPPLY

Departments 1-7

1727 Donna Road - West Palm Beach, Florida 33401  
PHONE — (305) 686-8553




**HEP 170's**



**THE "DO EVERYTHING" 2 1/2 AMP, 1000 VOLT DIODE**  
Motorola is catching up on the backlog and we've got thousands of them back in stock 10/\$3.00 100/\$25.00

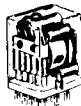**REG 40673'S**

**THE MOST POPULAR DUAL GATE PROTECTED MOS FET**  
around. Good to over 400 MHZ. We got 'em and you get 'em for only . . . . . 5/\$6.00



**POTTER BRUMFIELD  
MINI CAP RELAY**

Only \$2.00 each 3/\$5.50 Mix or Match

Measures only 1/2 x 1 x 1 1/4". Plastic cased. Like KNP type. For pc board or socket, 14 lugs. 1/8" 32 stud tool! Both 4PDT. All ceramic construction. 3 amps. contacts. For r.f. ant. switching. Wt 1 oz. Wherever space is prime, you need a "mini cap" relay.

115 VAC 60 cps  
24 VDC

**RG - 174/U**

**WE WENT THROUGH 20 MILES OF IT LAST TIME!**  
We are authorized Belden Distributors and new shipments have come in from the factory. Split a 500' spool with a friend and save \$5555

BELDEN NO 8211 100' \$4.80 500' \$17.85

**LED Readouts**



	SIZE	COLOR	DECIMAL	EACH	SPECIAL
OPCOA SLA 1	33	Red	Yes	2.95	4/\$11
OPCOA SLA 11C	33	Green	Yes	4.95	4/\$16
OPCOA SLA 3H	70	Red	Yes	7.95	4/\$28

All use 7447 Drivers. Spares included.

**RF POWER TRANSISTORS**

We did it again. All brand new with standard markings and most were manufactured this year. A major manufacturer dropped his RF power line and we bought his inventory.


2N5589	3 Watts Out	\$ 3.50
2N5590	10 Watts Out	6.00
2N5591	25 Watts Out	12.00
2N6080	4 Watts Out	5.00
2N6081	15 Watts Out	7.50
2N6082	25 Watts Out	10.00
2N6083	30 Watts Out	12.00
2N6084	40 Watts Out	15.00

All are Silicon NPN and power output ratings are good to 175 MHz. Hurry some quantities are limited.



**KEYSTONE PERF BOARD**

G 10 Glass Epoxy  
Red Board 3/64" Thick

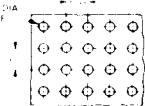

No.	Size (in.)	Price
<b>UNCLAD</b>		
4229	2 x 4	\$ .85
4230	2 x 6	1.00
4231	4 x 6	1.55
4232	17 x 6	5.75
<b>COPPER CLAD ONE SIDE</b>		
4238	2 x 4	1.35
4239	2 x 6	1.85
4240	4 x 6	3.20
4241	17 x 6	6.70

**WE GUARANTEE WHAT WE SELL!!!!**

We ship UPS whenever possible. Give street address. Include enough for postage, excess refunded in cash. Florida residents include 4% Tax.

# THE FM PEOPLE DO IT AGAIN!!! ...JUST FOR YOU!

GENERAL  ELECTRIC


## VOICE COMMANDER III

- PORTABLE  
FM TRANSCEIVER
- ALL SOLID STATE
- 1 WATT OUTPUT
- CONVERTIBLE  
TO 2 METERS

INCLUDES

Rechargeable Battery  
Pack. Proper Charger  
(While they last)

**\$98<sup>00</sup>**  
Plus  
Shipping

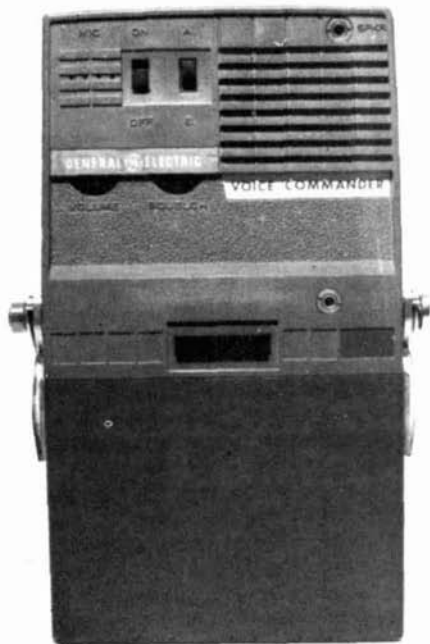

WE'RE SURE YOU'VE SEEN THESE UNITS ADVERTISED ELSEWHERE FOR UP TO \$60 MORE. AT SUCH A MONEY SAVING PRICE SUPPLIES WON'T LAST FOREVER . . . **DON'T DELAY** . . . CALL OR WRITE **NOW** FOR THE BEST DEAL POSSIBLE ON THE VC III OR ANY OTHER FM NEED.



### SPECTRONICS


1009 GARFIELD STREET  
DEPT. H-11  
OAK PARK, ILL. 60304  
(312) 848-6778

AMATEUR SALES ONLY / SPECTRONICS / The FM People





# SHOPPED AT THE FM SUPERMARKET LATELY?

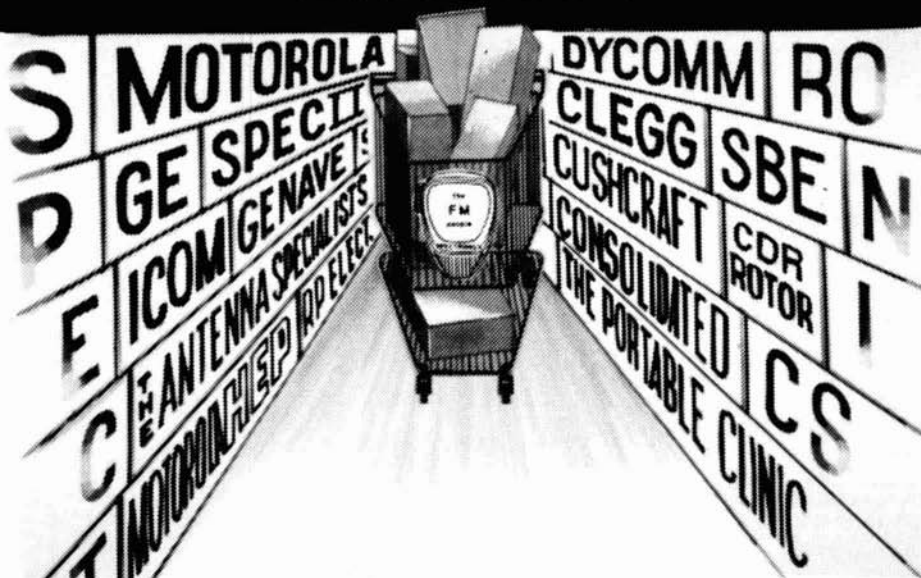

*IF YOU HAVE . . . YOU KNOW HOW CONVENIENT  
ONE-STOP SHOPPING CAN BE!*

WHETHER YOU NEED A COMPLETE FM STATION OR ACCESSORIES TO IMPROVE YOUR PRESENT STATION . . . AT THE FM SUPERMARKET YOU CAN CHOOSE FROM ALL OF THE MAJOR MANUFACTURERS ABOVE . . . AND MORE. TRULY ONE STOP FM SHOPPING.

WHY CHASE ALL OVER THE COUNTRYSIDE LOOKING FOR THE GEAR YOU NEED?? WHEN WITH ONE PHONE CALL OR LETTER YOU CAN FIND THE BEST IN SERVICE, PRICE AND PRODUCT AT THE FM SUPERMARKET BROUGHT TO YOU BY "THE FM PEOPLE" . . . WHO ELSE???

**TERMS OF SALE:** Sales to licensed Radio Amateurs for use on Amateur freqs only. All prices FOB Oak Park, IL. Check with order, COD or you can charge to your BankAmericard or Master Charge.

**STORE HOURS:** Mon.-Thurs. 9:30-6:00, Fri. 9:30-8:00, Sat. 9:30-3:00. Closed Sun. & Holidays  
INQUIRIES WITHOUT ZIP CODE OR CALL . . . NO ANSWER



**NEW 1974 CATALOG  
NOW BEING PREPARED**



**SPECTRONICS**

1009 GARFIELD STREET  
DEPT. H-11  
OAK PARK, ILL. 60304  
(312) 848-6778

PLEASE SEND ME YOUR NEW 1974  
CATALOG WHEN IT IS AVAILABLE:

NAME \_\_\_\_\_  
CALL \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_  
STATE \_\_\_\_\_ ZIP \_\_\_\_\_  
AREA OF INTEREST \_\_\_\_\_

H-11

### March 1968 (first issue)

**FEATURING:** 5-band SSB exciter, IC-regulated power supply, Remotely-tuned 10-meter beam, Transistor curve tracer, Double-balanced mixers.

### May 1969

**FEATURING:** Potpourri of integrated-circuit applications, FM repeater receiver performance, RTTY converter, IC noise blanker, The ionospheric e-layer.

### August 1969

**FEATURING:** Homebrew Parabolic Reflector, Solid-state Q-5er, Frequency calibrator with mos IC's, New multiband quad antenna, Troubleshooting with a scope.

### September 1969

**FEATURING:** FM techniques and practices, IC power supplies, 1296-MHz varactor tripler, Tunable bandpass filters, Amateur microwave standards.

### October 1969

**FEATURING:** Hot Carrier Diodes, Low-cost linear IC's, Diversity antennas, solid-state 432-MHz exciter, Tropospheric duct communications.

### November 1969

**FEATURING:** Op Amps theory, selection & application, WWV receiver, Multiband antenna, Electronic key, Six-meter collinear.

### August 1970

**FEATURING:** High-performance filter/preamplifier for vhf-uhf receivers, 100 MHz digital frequency scaler, Tunable audio cw filter, Stable solid-state vfo, Cubical-quad antenna design.

### October 1970

**FEATURING:** An swr meter for accurate rf power measurements, Direct-conversion receiver, IC voltage regulators, 432MHz converter, Introduction to thyristors.



### June 1971

**FEATURING:** A practical approach to 432-MHz SSB, FM carrier-operated relay, Audio agc systems, Practical IC's, Low-noise 1296-MHz preamp.

### June 1972

**FEATURING:** 5 Band solid-state communications receiver, FM repeater control, SSTV synch generator, microwave experimenting.

### August 1972

**FEATURING:** Frequency synthesizer for Drake R-4, 2304 MHz preamp, audio filters, RTTY Monitor scope, mobile touch-tone.

### September 1972

**FEATURING:** HF power amplifier pi-network design, HF log periodics, RTTY distortion, frequency scaler, repeater timers.

### October 1972

**FEATURING:** 4 channel spectrum analyzer, HF frequency synthesizer, all-band dipole, 160 meter vertical, multi-function IC's.

### December 1972

**FEATURING:** Satellite communications, UHF swr bridge, RTTY monitor, receiver, FM channel elements, helical mobile antenna.

### January 1973

**FEATURING:** Matching networks, digital readout VFO, fm repeater recoder, six-meter pre-amp, tuneable phase locked loop.

### February 1973

**FEATURING:** Communications receiver design, rf speech clipper, fm receiver scanner, Plessey SL600 integrated circuits, solid-state noise blanker.

### March 1973

**FEATURING:** Solid-state 80-meter transceiver, reciprocating-detector receiver, AFSK generator, electronic keyers, mobile touch-tone.

### June 1973

**FEATURING:** Digital RTTY auto-start, fm repeater installation, micropower receiver, broadband amplifiers, logic oscillators.

### July 1973

**FEATURING:** SSTV test generator, carrier operated relay, VHF receiver, two-meter frequency synthesizer, antenna matching.

### September 1973

**FEATURING:** 220 MHz fm power amplifier, i-f sweep generator, speech processor, frequency synthesizer, log-periodic antennas.

### October 1973

**FEATURING:** Keyer with random access memory, AFSK keyer, touch-tone decoder, antenna matching, rf power meter, VHF pre-scaler.

### November 1973

**FEATURING:** Low power transmitter for 20 meters, Motorola test set, RTTY tuning unit, ssb transceiver, DX antennas, repeater-site calculators.

There's no place like a good collection of HAM RADIO back issues to find answers you're looking for. Go over the list above and find the ones you need.



Just 85¢ each ppd. worldwide.

Enclosed is \_\_\_\_\_ for the issues I have checked.

Name..... Call.....

Address.....

City.....

State..... Zip.....

### See page 106 for Ham Radio Binders


- March 1968 (first issue)
- May 1969
- August 1969
- September 1969
- October 1969
- November 1969
- August 1970
- October 1970
- June 1971
- June 1972
- August 1972
- September 1972
- October 1972
- December 1972
- January 1973
- February 1973
- March 1973
- June 1973
- July 1973
- September 1973
- October 1973
- November 1973

# NEW—2 METER POWER BOOSTER

110 WATTS *PLUS* WITH YOUR CLEGG 27  
80 WATTS *PLUS* WITH YOUR REGENCY




PA-110/30 —  
\$149.95 WIRED  
& TESTED

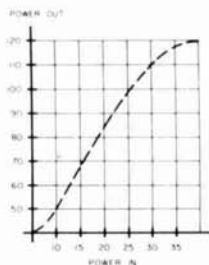

**SOLID STATE**  
24 AMP REGULATED SUPPLY

10-15 VOLTS  
3% REGULATION

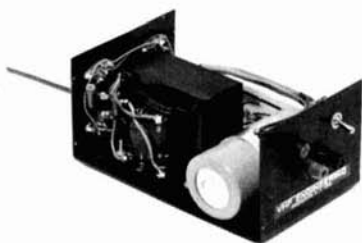

50 MV RIPPLE  
24 AMP MAXIMUM OUT

COMPLETE KIT LESS COVER (CHASSIS INCLUDED)  
ONLY \$69.95

ALSO AVAILABLE PS-3 CARD ONLY — \$8.95

## COMING ATTRACTIONS

**2 METER**

WELL UNDER \$100.00  
EARLY NEXT YEAR



# VHF ENGINEERING

— DIV. OF BROWNIAN ELECT. CORP. —

320 WATER ST. POB 1921 BINGHAMTON, N.Y. 13902 607-723-9574

# A COMPLETELY PORTABLE FREQUENCY COUNTER WITH . . .

- \* 10 HZ to 65 MHZ range
- \* Full six digit readout (L.E.D.)
- \* Sensitive front end (LESS THAN 10 MV.)
- \* Only \$199

## FEATURES

- High capacity rechargeable Ni Cd batteries
- Crystal controlled time base (can be field calibrated)
- Convenient 3-position range select switch allows:
  1. Readout always in MHZ.
  2. Eight digit resolution by range selection
  3. Direct reading pre-scaler operation to 999.999 MHZ.
- "Battery save" switch for spot checks
- Less than 5 watts power consumption (5 volts @ 0.9 AMPS)
- Dimension 6" x 3.5" x 2.3"
- TTL input for use with pre scaler
- Can be operated on internal or external power, with trickle charge and full charge positions
- Sample control lets operator determine how often the readout is updated. Can "hold" present count without being updated



Mail orders directly to:  
Great American Miniatures,  
Inc.  
P. O. Box 10990  
Midwest City, Okla. 73110

Model C-65 Freq. counter \$199.<sup>00</sup>  
Battery charger 8.<sup>00</sup>  
Battery charger & eliminator 18.<sup>00</sup>

<b>NATIONAL</b>	<b>MOSCT5005</b>	<b>7400</b>	<b>7411</b>
DYNAMIC shift registers TO-5	CALCULATOR ON A CHIP	7400 . . . . . \$ .35	7411 . . . . . 1.75
MMS02 dual 50 bit \$1.25	This CHIP has a full four	7401 . . . . . .50	7412 . . . . . .50
MMS06 dual 100 bit 1.75	function memory. Memory is	7402 . . . . . .35	7413 . . . . . .35
MMS006 dual 100 bit 1.25	controlled by four keys, M	7403 . . . . . .35	7414 . . . . . .35
MMS013 1024 bit 2.25	(adds entry to memory), JK	7404 . . . . . .35	7415 . . . . . 1.75
MMS016 512 bit 1.50	(subtracts entry from mem-	7405 . . . . . .35	7416 . . . . . .35
STATIC shift registers	ory), CM (clear memory--	7410 . . . . . .50	7420 . . . . . .35
MMS04 dual 16 bit 1.50	without clearing rest of	7410 . . . . . .50	7420 . . . . . .35
MMS05 dual 32 bit 1.75	registers), RM (read memory	7430 . . . . . .35	7440 . . . . . .35
MMS50 dual differential	or use as entry).	7440 . . . . . .35	7441 . . . . . 1.60
analog switch 2.50		7441 . . . . . 1.30	7442 . . . . . 1.30
<b>KEYBOARD</b>		7442 . . . . . 1.75	7448 . . . . . 1.15
<b>General Telephone</b>		7450 . . . . . .35	7451 . . . . . .35
Ten push buttons (0-9)	12-Digit Display and Calc.	7452 . . . . . .35	7453 . . . . . .35
touch-tone, encoding,	Chip and data. \$14.95	7454 . . . . . .35	7460 . . . . . .35
programming devices.	Data only. . . . . 1.00	7460 . . . . . .35	7472 . . . . . .50
Easy for panel mount-	(Refundable)	7460 . . . . . .35	7473 . . . . . .65
ing.	1101/2501 256 BITx1 MOS	7474 . . . . . .65	7475 . . . . . 1.75
	memory \$3.00; 10/\$27.50	7476 . . . . . .70	7480 . . . . . .65
	7037 - Equal to Intersil	7483 . . . . . 1.30	7480 . . . . . 1.50
	8038	7491 . . . . . 1.15	7491 . . . . . 1.15
	PRECISION WAVEFORM GENER-	7492 . . . . . 1.15	7493 . . . . . 1.15
	TOR/VOLTAGE CONTROLLED OS-	7495 . . . . . 1.25	7495 . . . . . 1.25
	CILLATOR	7497 . . . . . .70	7497 . . . . . 2.50
	Sine, Square, Triangle	7499 . . . . . 2.50	7499 . . . . . 1.50
	Outputs	7500 . . . . . 1.00	7500 . . . . . 1.00
	Wide Frequency Range of	7501 . . . . . 1.00	7501 . . . . . 1.00
	Operation 0.001 Hz to	7502 . . . . . 1.00	7502 . . . . . 1.00
	1.0 Mhz	7503 . . . . . 1.00	7503 . . . . . 1.00
	14 Pin DIP \$4.95	7504 . . . . . 1.00	7504 . . . . . 1.00
		7505 . . . . . 1.00	7505 . . . . . 1.00
		7506 . . . . . 1.00	7506 . . . . . 1.00
		7507 . . . . . 1.00	7507 . . . . . 1.00
		7600 . . . . . 1.00	7600 . . . . . 1.00

**LED FL100**  
SPECIAL!!  
.35 Each  
3.00 for ten  
\$25.00 for 100

**TRIAC**  
2N6344 650V  
GA TO-220 \$ .75

**MANI | MANEM**  
Each \$ 2.75 HAM RADIO Specials!! Each \$ 2.50  
10 for 25.00 10 for 19.00  
All IC's are new and fully tested. Leads are plated with gold or solder. Orders for \$5 or more will be shipped prepaid. Add 35c for smaller orders. California residents add sales tax. IC orders are shipped within 24 hrs. COD's may be phoned in, \$10 minimum. Money-back guarantee.

**BABYLON ELECTRONICS**  
P. O. Box J Carmichael,  
California 95608  
(916) 966-2111

## A FASCINATING HOBBY!

VINTAGE RADIO brings you the pioneer days of wireless and radio in pictures. The collector's bible, it opens the doors to a new hobby. Great browsing, too. Over 1,000 pictures, 263 pages. 1887-1929.



**AVOID DELAY; SEND TODAY**  
Mail check to Vintage Radio, Dep't H,  
Box 2045, Palos Verdes Peninsula, CA., 90274

Vintage Radio, hard cover \$6.95   
Vintage Radio, handbook 4.95   
Radio Collectors Guide 3.95   
Postage Paid, California residents add 5% Tax.

Name \_\_\_\_\_  
Street \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

**ENJOY THE OLD DAYS!**



# YAESU

YOUR ASSURANCE OF PERFORMANCE & QUALITY

Amateur Price Net  
Subject to Change

## IT'S HERE NOW The NEW FT101B

### With These Added Features and NO INCREASE IN PRICE

1. VFO (warning lite) on or off
2. Clarifier (warning lite) on or off
3. Noise blanker on insert card
4. 8 pole filter for better rejection
5. Sidetone output
6. Antitrip input



\$649.00

Amateurs and Maritime operators around the world have discovered the FT101's versatility and reliability. Many of the outstanding signals you hear are using the FT101. It's all here—AM, CW, SSB. Receiver sensitivity 0.3 microvolts 10dB signal to noise ratio. 160 meters through 10 meters. Citizen's Band, WWV, 25 and 100 kc calibrators, 5 kc clarifier for net or mobile operation. The built-in noise blanker assures in-motion mobile-peak performance with minimum of noise.

Transmitter stability under most adverse conditions is superb. PEP 260 watts SSB, 80 watts AM, 180 watts CW. 117 V AC supply built-in. 12 V DC fused power cable, AC cable, all accessory plugs are furnished. Matching units available for FT101B, FP101 patch, FP101, speaker FV101 VFO, FL2100 linear. See your local dealer for demo and brochure.

**DEALER'S SERVICE POLICY—Factory Service available after warranty has expired.**

ADIRONDACK RADIO SUPPLY 518-842-8350  
185 West Main Street, Amsterdam, New York 12010  
AMATEUR ELECTRONIC SUPPLY 414-442-4200  
4828 W. Fond du Lac Ave., Milwaukee, Wisc. 53216  
AMATEUR ELECTRONIC SUPPLY 305-894-3238  
621 Commonwealth Avenue, Orlando, Florida 32803  
FRECK RADIO SUPPLY 704-254-9551  
38 Biltmore Avenue, Asheville, North Carolina 28807  
GRAHAM ELECTRONICS 317-634-8486  
133 S. Pennsylvania St., Indianapolis, Indiana 46204  
HAM RADIO CENTER 314-993-6060  
8342 Olive Blvd., St. Louis, Missouri 63132  
HAM RADIO OUTLET 415-342-5757  
999 Howard Avenue, Burlingame, California 94010  
HAMTRONICS 215-357-1400  
4033 Brownsville Rd., Treve, Pennsylvania 19047

HARRISON RADIO 516-293-7990  
20 Smith Street, Farmingdale, LI, New York 11735  
HENRY RADIO 213-272-0861  
11240 W. Olympic Blvd., Los Angeles, Calif. 90064  
JUGE ELECTRONICS 817-926-5221  
3850 S. Freeway, Fort Worth, Texas 76110  
QUEEN CITY ELECTRONICS, INC. 513-931-1577  
1583 McMakin Ave., Cincinnati, Ohio 45231  
RACOM ELECTRONICS 206-255-6656  
15051 S.E. 128th St., Renton, Washington 99055  
WEBSTER RADIO 209-224-5111  
2602 Ashlan, Fresno, California 97326  
WILSON ELECTRONICS 702-451-6650  
P.O. BOX 116, Pittman, Nevada 89044

# 5% PRICE REDUCTION

ON ALL KVG FILTERS, DISCRIMINATORS & CRYSTALS

IT DOESN'T HAPPEN OFTEN IN THESE INFLATIONARY TIMES, BUT THANKS TO A RECENT STRENGTHENING OF THE U.S. DOLLAR ABROAD WE ARE NOW ABLE TO BRING YOU THESE SAVINGS. ACT FAST AS THIS UNIQUE OPPORTUNITY COULD END AT ANY TIME.

See our ad on page 79 in the December Issue of Ham Radio for full details on these KVG Products.



SPECTRUM  
INTERNATIONAL  
BOX 1084 CONCORD  
MASSACHUSETTS 01742

## PRINTED CIRCUIT BOARDS

for any amateur project in any amateur periodical.

Get your homebrew projects off to a professional start

Write for Complete Details and Prices

D. L. "Mac" McClaren, W8URX

Printed Circuit Service for the Amateur

19721 Maplewood Ave. Cleveland, Ohio 44135  
216-267-3263



## BARGAINS!

KLEINSCHMIDT TELETYPE EQUIPMENT

- |   |         |
|---|---------|
| (1) TT-100 PAGE PRINTER, AS IS 60 OR 100 WPM            | \$59.95 |
| (A) TT-117 PAGE PR. OR (B) TT-179 REPERF. & TD, AS IS   | \$59.95 |
| ABOVE CHECKED OUT, OILED & ADJUSTED, EA                 | \$89.95 |
| (2) TABLE \$19.95 (C) TABLE \$34.95 (D) COPYHOLDER      | \$3.95  |
| (3) PAPERWINDER \$14.95 (4) TT-107 REPERF. ONLY         | \$49.95 |
| TH-5 CONVERTER TRANS/REC 100 CYCLES ADJUST TO 170 SHIFT | \$49.95 |



Andy Electronics Co., Inc.

6431 Springer Street / Houston, Texas 77017

ALL PRICES FOB HOUSTON, TEX.

VHF  
DX OPS



**MODEL 60 SPEECH PROCESSOR** — ORO the average-to-peak ratio of the speech waveform as much as 8 db using a logarithmic principle. Operates with FM, SSB and AM transmitters and transceivers. Low-High impedance Mic input. Two 9Vdc batteries provide a self-contained unit.

**Model 60W** (Processor Assembled) \$26.50  
**Model 60K** (Processor Kit) \$21.90  
**200-15** (Processor Board Kit) \$12.95

**MATRIC**

BOX 185A • FRANKLIN, PA. 16323

PHONE: 814 432-3647

ORG  
?



**MODEL 20 DIGITAL DIAL** — Available for Collins and Drake gear. Optional four digit readout and crystal time base. QSY your fixed or mobile transmitter, receiver or transceiver with 100 Hz accuracy and no last digit jitter. Simple one wire connects dial to rig and you're ready to go. Specify your type of rig.

**Model 20** (5-5.5 Mhz VFO range)..... \$169.95  
**Model 20C** (Collins)..... \$169.95  
**Model 20D** (Drake)..... \$169.95  
**Options:** [4 Digit Readout]..... \$ 29.95  
[Crystal Time Base]..... \$ 29.95

DEALERS:

VE AMATEUR RADIO SALES, Downsview, Ontario, Canada •  
SET ELECTRONICS, Lawrenceville, GA 90260 • AMATEUR  
WHOLESALE ELECTRONICS, Miami, FL 33156 • AN-TEK  
INDUSTRIES, Elkhart, IN 46517 • SIGNAL SYSTEMS, Bedford,  
OH 44146 • KASS ELECTRONICS DISTRIBUTORS, Drexel Hill,  
PA. 19026 • M. WEINSCHENKER K3DPJ, Irwin, PA 15642 •  
HAMTRONICS, Treviso, PA 19047

CW  
OPS



**MODEL 11A PADDLE** — Designed with reliability in mind. No mechanical switches or bearings to fail. Paddle contact spacing adjusts easily.

**Model 11A** (Assembled)..... \$9.95

**MODEL 10A ELECTRONIC KEYS** — Has NEW features at no extra cost! Linear Speed Control and Operator/Tune Switch. Plus internal penlight cells and reed relay output provide a compact, portable, versatile unit.

**Model 10AWA** (Keyer & Sidetone Assembled)..... \$33.95  
**Model 10AW** (Keyer Assembled)..... \$26.50  
**Model 10AK** (Keyer Kit)..... \$21.95  
**200-2K** (Keyer Board Kit)..... \$12.95  
**200-3K** (Sidetone Board Kit)..... \$ 4.95

# Meet the unique Inoue family of ICOM 2 meter fm gear



**IC-21**  
24 Channel Base  
AC/DC  
Modular Construction

**IC-21**  
VFO  
(Receive Only)



**IC-230**  
67+ Channels  
PLL Synthesized  
IC 5P  
Power Supply

**IC-20**  
12 Channels  
10 Watt  
Modular Construction

**IC-22**  
22 Channels  
IC 3P  
3 Amp  
Power Supply

The most advanced line of unique state-of-the-art 2 meter gear available today... where you pay a few bucks more to get the quality and performance you deserve out of today's state-of-the-art technology.

Get the facts on this truly unique family of Inoue FM gear from your nearby INOUE-ICOM dealer.



*Distributed by:*

**ICOM WEST, INC.**  
Suite 232 - Bldg. 2  
300 - 120th Ave. N.E.  
Bellevue, Wash. 98005  
(206) 454-2470

**ADIRONDACK  
RADIO SUPPLY**  
185 West Main Street  
Amsterdam, N.Y. 12010

**ICOM EAST**  
Div ACS, Inc.  
Box 331  
Richardson, Tex. 75080  
(214) 235-0479

**DOLLARD ELECTRONICS, LTD.**  
3883 Oak Street  
Vancouver 9, B.C.  
(604) 733-9819

- Dealerships Available -

# SUPER CRYSTAL THE NEW DELUXE DIGITAL SYNTHESIZER!! FROM **RP**



**MFA-22 DUAL VERSION**

Also Available MFA-2 SINGLE VERSION

- Transmit and Receive Operation: All units have both Simplex and Repeater Modes
- Accurate Frequency Control: .0005% accuracy
- Stable Low Drift Outputs: 20 Hz per degree C typical
- Full 2 Meter Band Coverage: 144.00 to 147.99 MHz. in 10KC steps
- Fast Acting Circuit: 0.15 second typical settling time
- Low Impedance (50 ohm) Outputs: Allow long cable runs for mobiles
- Low Spurious Output Level: similar to crystal output

SEND FOR  
FREE DETAILS

**RP Electronics**

Prices MFA-2 \$210.00 BOX 1201H  
MFA-22 \$275.00 CHAMPAIGN, ILL.  
Shipping \$3.00 extra 61820



**YAESU FT-101**  
now with 160 meters

SEE **WILSON**  
for your Yaesu products

FTDX 401 Transceiver  
FL2100 Linear Amplifier  
FL2000B Linear Amplifier

Interested in trading Tempo One's  
and other Yaesu equipment.

**WILSON ELECTRONICS**

BOX 794 HENDERSON, NEVADA, 89105  
702-451-5791

## LEARN RADIO CODE



### THE EASY WAY!

- No Books, To Read
- No Visual Gimmicks To Distract You
- Just Listen And Learn

**\$9.95**

Album contains three 12" LP's 2 1/2 hr. Instruction

Based on modern psychological techniques—This course will take you beyond 13 w.p.m. in LESS THAN HALF THE TIME!  
Available on magnetic tape \$9.95 — Cassette, \$10.95

**EPSILON  RECORDS**

508 East Washington St., Arcola, Illinois 61910

## WORLD QSL BUREAU

THE ONLY QSL BUREAU to handle all of your QSLs to anywhere; next door, the next state, the next country, the whole world. Just bundle them up (please arrange alphabetically) and send them to us with payment of 5¢ each.

5200 Panama Ave., Richmond, CA USA 94804

## THE ULTRA-BAL 2000

NOW.....An extremely rugged, weather-proof BALUN!  
• Full 2KW, 3-30 MHz., 1:1 or 1:4 ratios.  
• Special Teflon insulation. May be used with tuned lines and tuners.  
• With dipole insulator and hang-up hook.

ONLY \$9.95ppd. (state ratio)  
At your dealer or order direct

**K.E. Electronics** Box 1279, Tustin Calif. 92680

QRM QRM QRM

QRM

QRM

QRM



QRM QRM QRM

## WHY FIGHT QRM?

Win the battle against CW QRM with the new DE-101 using advanced integrated circuit design. Connect it between your receiver and high impedance earphones for a guaranteed superior CW reception. Operate your receiver the same way as before except now you discriminate against QRM. No adjustments, the DE-101 is factory tuned and complete with built in ac supply. One year warranty. 4" x 2 1/2" x 6" \$29.95 plus \$2.00 shipping.

### INTRODUCING THE NEW DE-101A

Same as the DE-101 with a 3 watt audio amplifier for driving a speaker. Simple plug in installation. \$39.95 plus \$2.00 shipping. Write for details on other units.

Ala. residents add 5% tax

**DYNAMIC ELECTRONICS INC.**

BOX 1131 DECATUR, AL. 35601



The most powerful signals under the sun!



**hy-gain**

**550A**

## The Total Communication System



The Hy-Gain 550A is the complete amateur system. Designed from the ground up to work together for total performance. Each element is matched to the system, for simple, plug-in expansion of your capabilities.

**GT-550A Transceiver** The matchless heart of the 550A System. No other transceiver can give you this performance for the price. Operating fixed station or mobile, the GT-550A is guaranteed to have top frequency stability after warm-up. A graph showing stability during final check-out is included with each unit. 25 KHz calibrator and VOX, optional.

**Frequency Coverage**—3.5-4.0, 7.0-7.5, 14.0-14.5, 21.0-21.5, 28.0-29.0 MHz crystals supplied. Other 10 meter coverage optional. Power Output—300 watts PEP (nominal) on SSB, 180 watts on CW and RTTY, into 50 ohm resistive load.

**Harmonic and Spurious Radiation**—Carrier suppression in excess of 45 db down, unwanted side bands minus 55 db oscillator feed through and mixer spurious products down 50 db. Second harmonic minus 40 db and third order distortion in excess of minus 45 db.

**Noise Level**—In excess of 40 db below single tone carrier.

**Audio Frequency Response**—Minus 6 db approximately 300/2400 Hz determined by side band filter.

**RF Compression Characteristics**—Up to 10 db RF compression without distortion.

**Receiver Sensitivity**—Better than .5 uv for 10 db S+N/n ratio.

**Receiver Selectivity**—2.1 KHz with 1.8 shape factor for SSB or 300 Hz sharp selectivity with optional CW filter.

**Receiver Spurious Response**—Image rejection better than 40 db down. Internal spurious below 1 uv equivalent input.

**Frequency Calibration**—Interpolation to 1 KHz in 5 KHz increments.

**Frequency Stability**—Within 10 Hz during any 30 minute warm-up period, less than 100 Hz in any 15 minute warm-up period, not more than 100 Hz with a plus or minus 10% line voltage variation.

**Calibration Accuracy**—Interpolation to 1 KHz after calibration.

**Back Lash**—Not more than 50 Hz.

**Output Impedance**—Variable 50 ohms nominal capable of matching up to 2-1 SWR (30-100 Ohms).

**Automatic Volume Control**—Fast attack, slow release on all receiver modes.

Order No. 855 Ham Net \$595.00

**RF550A** contains high accuracy watt meter; calibrated in 400 and 4,000 watt scales; switch for forward or selected power; switch to select 5 antennas or dummy load. Order No. 857 Ham Net \$75.00

**RV550A** is a solid state VFO. Function switch selects the remote unit to control Receive-Transceive-Transmit frequency independently. Order No. 856 Ham Net \$95.00

**SC550A** Speaker Console with headphone jack. AC400 power supply will mount inside. Order No. 858 Ham Net \$29.95

**AC400** Power Supply is heavy duty solid state to operate GT-550A at full power, on SSB or CW, and with switch selection of 115/230 VAC, 50/60 Hz input voltages. Order No. 801 Ham Net \$99.95

**G-1000** 12V D.C. Mobile power supply with cables. Order No. 802 Ham Net \$129.95

## HY-GAIN ELECTRONICS CORPORATION

Dept. BA, 8601 Northeast Highway Six, Lincoln, NE 68507  
402/434-9151 Telex 48-6424

# hr REPORT

prepared  
by the  
editors of  
Ham Radio  
Magazine

An entirely new concept in an amateur publication. A twice monthly newsletter mailed to you via air mail. You'll get the news as it happens not weeks or months later. When major stories break *hr Report* will have an issue in the mail just 24 hours later with the full story.

*hr Report* will cover everything. Late breaking news from the FCC, ARRL, industry and overseas sources, up-to-the-minute propagation, special DX news, contest and hamfest reminders and much, much more.

You'll get the story behind the story the way you've never been able to before. This will set a whole new standard in amateur journalism. The integrity and authority of Ham Radio's editorial staff plus a dedication to the idea that a better informed amateur radio is a stronger amateur radio equals the most significant publishing event since the beginning of *Ham Radio* six years ago.

First issue published January 2nd. Make sure that one has your name on it.

**ONE YEAR (24 or more issues)**

All copies sent Air Mail

**\$12.00 US and Canada**

**\$15.00 Worldwide**

*Any orders prior to January 1, 1974 only \$10.00*



**hr REPORT**  
GREENVILLE, NH 03048

# LIKE FM OR CW ?



*Then you'll love  
Data Engineering's  
new catalog*

Write for your free copy today!

## TOUCH TONE PADS

More features than any other pad including built-in monitor speaker and latest Phase-Lock loop circuitry.

TTP-1 Standard pad for portable transceiver mounting.

TTP-2 Standard pad in attractive case for home or mobile use.

TTP-3 Mini-pad in attractive case for home or mobile use.

TTP-4 Mini-pad for portable transceiver mounting.

TTP-1, 2, 3 & 4, Sh. wt. 1 lb. .... \$44.50

TTP-1K, 2K, 3K & 4K, Sh. wt. 1 lb. .... \$34.50

## CRICKET 1

A popularly priced IC keyer with more features for your dollar. Cricket 1 is a small size, solid state keyer designed for the beginner as well as the most advanced operator. It provides the user with fatigue-free sending and its clean, crisp CW allows for easy copying at all speeds. Turned on its side, the Cricket can be used as a straight key for manual keying.


CRICKET 1 Sh. Wt. 3 lbs. \$49.95

## 2-METER PREAMP

Specially made for both OLD and NEW receivers. The smallest and most powerful preamp available. Provides 20dB gain at 2.5 N.F. to bring in the weakest signals.

Sh. wt. 4 oz. \$9.50 kit  
\$12.50 wired

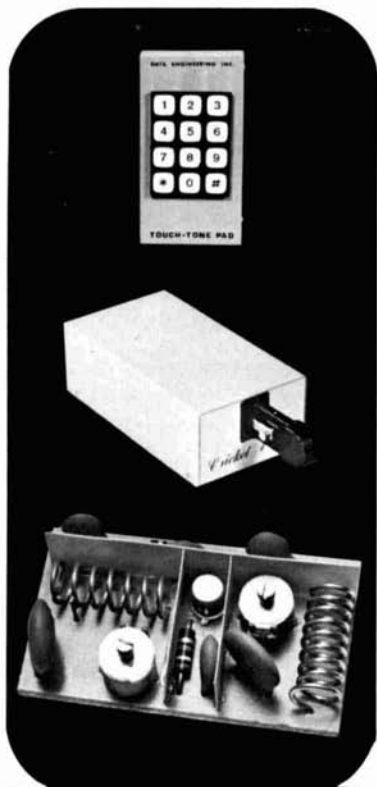Please include sufficient postage for shipping.



# DATA ENGINEERING INC.



Ravenswood Industrial Park, Springfield, Va. 22151


5554 Port Royal Road • 703-321-7171

# NEW

## THE TELEPRINTER HANDBOOK

by

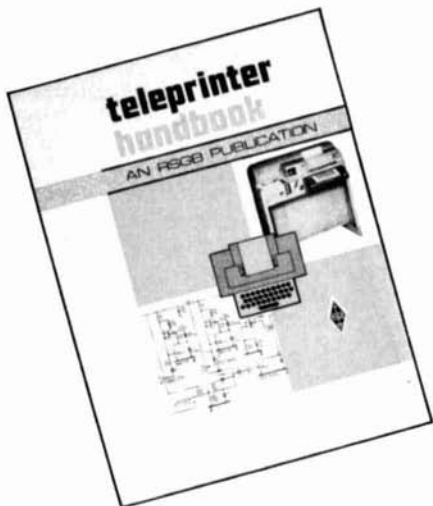*D. J. Goacher, G3LLZ & J. G. Denny, G3NTT*



**The Largest & most complete handbook on RTTY  
ever published**

In over 360 pages this beautiful hardcover handbook covers in extensive detail most of the popular page printers and auxiliary equipment, both American and European. You will also find all of the other equipment that goes to make up a modern complete RTTY station such as demodulators, power supplies, filters, control systems and test equipment.

The presentation is very thorough and not only gives the complete description and theory of the equipment involved, but also covers the maintenance, adjustment and repair of each model. The text is profusely illustrated with many hundreds of photographs, line drawings and diagrams so that nothing is left to your imagination.

This is a book that everyone has been waiting for. More than four years went into its preparation and contributors include a number of the world's leading RTTY amateurs from both sides of the Atlantic.

If RTTY figures at all in your amateur activities present or future, be sure to order your copy today.

**hr**  
**BOOKS**

GREENVILLE, NH 03048

**THE TELEPRINTER HANDBOOK**  
**\$14.95 postpaid**

CW or RTTY, whichever way you go,

# HAL HAS TOP QUALITY YOU CAN AFFORD!



**TOP QUALITY RTTY... WITH THE HAL MAINLINE ST-6 TU.** Only 7 HAL circuit boards (drilled G10 glass) for all features, plug-in IC sockets, and custom Thordarson transformer for both supplies, 115/230 V, 50-60 Hz. Kit without cabinet, only \$135.00; screened, punched cabinet with pre-drilled connector rails, \$35.00; boards and complete manual, \$19.50; wired and tested units, only \$280.00 (with AK-1, \$320.00).\*



**TOP QUALITY... WITH THE HAL 1550 ELECTRONIC KEYSER.** Designed for easy operation; perfectly timed CW with optional automatic ID for sending call letters, great for DX and RTTY; TTL circuitry, transistor switching for grid block, cathode keying. Handsome rugged crackle cabinet with brushed aluminum panel. With ID, only \$90.00; without ID, \$65.00.\*

### OTHER HAL PRODUCTS INCLUDE:

- ID-1 Repeater Identifier (wired circuit board) . . . \$ 75.00\*
- ID-1 (completely assembled in 1 1/2" rack cabinet) . . . \$115.00\*
- HAL ARRL FM Transmitter Kit . . . \$ 50.00\*
- W3FFG SSTV Converter Kit . . . \$ 55.00\*
- Mainline ST-5 TU Kit . . . \$ 50.00\*
- Mainline AK-1 AFSK Kit . . . \$ 27.50\*



### TOP QUALITY... WITH THE HAL MKB-1 MORSE KEYBOARD.

As easy as typing a letter—you get automatic CW with variable speed and weight, internal audio oscillator with volume and tone controls, internal speaker, and audio output jack. Smooth operation; completely solid-state, TTL circuitry using G10 glass boards, regulated power supplies, and high voltage transistor switch. Optional automatic ID available. Assembled MKB-1, \$275.00. In kit form, \$175.00.\*



**NEW FROM HAL—TOP QUALITY RVD-1002 RTTY VIDEO DISPLAY UNIT.** Revolutionary approach to amateur RTTY... provides visual display of received RTTY signal from any TU, at four speeds (60, 66, 75, and 100 WPM), using a TV receiver modified for video monitoring. Panasonic solid-state TV receiver/monitor, or monitor only, available. RVD-1002, \$525.00; Panasonic TV receiver/monitor, \$160.00; monitor only, \$140.00.\*

**TOP QUALITY... WITH THE HAL RKB-1 TTY KEYBOARD.** Gives you typewriter-easy operation with automatic letter/number shift at four speeds (60, 66, 75, and 100 WPM). Use with RVD-1002 video display system, or insert in loop of any teleprinter, for fast and easy RTTY. Completely solid state, TTL circuitry using G10 glass boards, regulated power supplies, and transistor loop switch. RKB-1 assembled, only \$275.00.\*



HAL provides a complete line of components, semi-conductors, and IC's to fill practically any construction need. Send 24¢ to cover postage for catalog with info and photos on all HAL products. Above prices do not include shipping costs. Please add 75¢ on parts orders, \$2.00 on larger kits. Shipping via UPS whenever possible; therefore, street address required.

**HAL COMMUNICATIONS CORP.**

Box 365 L, Urbana, Ill. 61801 • 217-359-7373





- 13-500 **MOBILE 2-METER FM TRANSCEIVER.** 15-watt, 12-channel with crystals for .16/.76, .34/.94, and .94/.94. Includes microphone and mounting hardware. **219.95**
- 13-509 **220 MHz FM MOBILE TRANSCEIVER.** 10-watt, 12-channel with crystals for 223.00 MHz simplex. Includes microphone and mounting hardware. **209.95**
- 13-520 **2-METER FM HAND-HELD TRANSCEIVER.** 2-watt, 6-channel with crystals for .16/.76, .34/.94, and .94/.94. Includes case with carrying strap. **209.95**

**MADISON ELECTRONICS SUPPLY, INC.**

1508 MCKINNEY AVE. — HOUSTON, TX. 77002

713/224-2668

Nite/Weekend 713/497-5683

**KITS**



**Encoder \$8.95**  
**Wired \$13.95**

Sub-Audible Tone  
Decoder **\$9.95**  
Wired **\$14.95**



- Compatible with all sub-audible tone systems such as Private Line, Channel Guard, Quiet Channel, etc.
- Glass epoxy PCB's & Silicon xstrs throughout
- Any reeds, except special dual coil types may be used: Motorola, G.E., RCA, S.D.L., Bramco, etc.
- All are powered by 12 vdc
- Use on any tone frequency 67 Hz to 250 Hz
- Small size 1.5 x 4 x .75"
- All parts included except reed and reed socket

Postpaid — Calif. residents add 5% sales tax

**COMMUNICATIONS SPECIALISTS**

P. O. Box 153, Brea, CA 92621

**FM Schematic Digest**

A COLLECTION OF  
MOTOROLA SCHEMATICS

Alignment, Crystal, and Technical Notes  
covering 1947-1960

136 pages 11½" x 17" ppd **\$6.50**

**S. Wolf**

**P. O. Box 535**

**Lexington, Massachusetts 02173**



8MC. XTALS—8333—9000.

Silk Screened Panel.

18 Watts Output.

**SIX METER TRANSMITTER**

- for
- MOBILE
  - FIXED STATION
  - EMERGENCY
  - AVIATION

**Price 49.95**

Net to Amateurs  
Complete with Tubes  
Power Supply \$9.95

**TUBE COMPLIMENT**  
6U8 Oscillator Multiplier  
12AX7 Speech Amplifier  
2E26 Final Amplifier  
6BQ5 Modulator



**EXCELTRONICS RESEARCH LABS**

MANUFACTURERS OF ELECTRONIC DEVICES

224-15 Linden Blvd. Cambria Heights, N. Y. 11411

# LED MITY DIGIT "DCM'S" \*Your choice of 5 red LED readouts!

Scientific Devices "Digital Counting Modules" outperform any other DCM on the market today. More features than ever before! Not gaseous, not incandescents, not nixie but the modern LED. Choose from such famous manufacturers as Monsanto's MAN-1, MAN-4, Litronics 707 and 704, Opco's SLA-1 (the last 4 having character heights of 0.33 at no extra charge). Each kit includes 2x2" p.c. board with fingers for a FREE edge connector, side-mounting dip socket, LED readout of your choice, resistors, 3 IC's, and Molex connectors (this ELIMINATES SOLDERING YOUR IC's), and your choice of P.C. EDGE CONNECTOR — FREE!

Buy 3 — Take 10%  
**\$9.99**

READOUT Char. Maker  
 MAN-1 .27 h. Monsanto  
 MAN-4 .19 h. Monsanto  
 707\* .33 h. Litronics  
 704\*\* .33 h. Litronics  
 SLA-1\* .33 h. Opcoa \* Pin-for-pin MAN-1. \*\* Pin-for-pin MAN-4, elec. char. same

## CALCULATOR KEYBOARD SWITCH KITS

**Kit of 17 for \$7.50**

10-pc. kit, 0-to-9 only, same type as above. **3.50**

Each switch made by Oak #215, SPST normally open, 24V 1 amp contacts. Kit includes 0-to-9 (10 switches) white with black numerals) decimal, white with black dot, and CE, CL and 4 functions blue with white characters.




**Money-Back GUARANTEE on all items**

## WEST COAST MAKER OF LED'S

- 4-MV5054 Jumbo red lens, red lite TO-18 ..... \$1.00
- 1-MV5222 Jumbo yellow lens, red lite, TO-18 ..... 1.49
- 1-MV5232 Jumbo green lens, yellow lite, TO-18 ..... 1.98
- 4-MV5080 Micro red dome red lite, TO-18 ..... 1.00
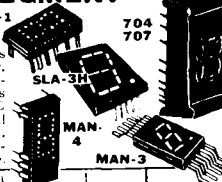
## LITRONIX-OPCOA-MAN "7-SEGMENT" LED Readouts

All fit 14-pin IC sockets. All 7-segments. MAN Series "all LED" and made by well-known West Coast mfg. Others Reflective Bar type made by OPCOA and LITRONIX. The Reflective Bar types are low-cost versions of the MAN's except .33 character height! If one LED blows you lose a segment. MAN's you DO NOT! All readouts 0-to-9 numerals, plus letters and decimal. \*\*Opcoa and Litronix products pin-for-pin replaceables for MAN-1 MAN-4. All 5V TTL compatible.



ALL LED READOUTS	character TYPE	Color Display	Decimal	Mils	Driver	Each	Special
<input type="checkbox"/> MAN-1 equal	.27	Red	Yes	20	SN7447	\$4.50	3 for \$12.
<input type="checkbox"/> MAN-1A equal*	.27	Red	Yes	20	SN7447	4.95	3 for \$13.
<input type="checkbox"/> MAN-3 equal	.115	Red	Yes	10	SN7448	2.50	3 for \$6.
<input type="checkbox"/> MAN-3A equal*	.115	Red	Yes	10	SN7448	2.50	3 for \$6.
<input type="checkbox"/> MAN-3M equal*	.127	Red	Yes	10	SN7448	2.50	3 for \$6.
<input type="checkbox"/> MAN-3 equal	.115	Red	***	10	SN7448	1.95	3 for \$5.
<input type="checkbox"/> MAN-3M equal*	.127	Red	Yes***	10	SN7448	1.95	3 for \$5.
<input type="checkbox"/> MAN-4 equal*	.190	Red	Yes	15	SN7448	3.25	3 for \$9.
<input type="checkbox"/> MAN-4 equal*	.190	Red	Yes***	15	SN7448	2.75	3 for \$8.

"REFLECTIVE LITE BAR" (Segment LED Readouts)

<input type="checkbox"/> 707** (MAN-1)	.33	Red	Yes	20	SN7447	3.25	3 for \$9.
<input type="checkbox"/> 704** (MAN-4)	.33	Red	Yes	20	SN7448	3.25	3 for \$9.
<input type="checkbox"/> SLA-1** (MAN-1)	.33	Red	Yes	20	SN7447	3.25	3 for \$9.
<input type="checkbox"/> SLA-2 + - 1	.33	Red	No	15	SN7447	3.25	3 for \$9.
<input type="checkbox"/> SLA-3H Giant	.70	Red	Yes	20	SN7447	6.50	3 for \$18.
<input type="checkbox"/> SLA-11C** (MAN-5.33)	Green	Yes	40	SN7447	5.95	3 for \$15.	
<input type="checkbox"/> SLA-12** ± 1	.33	Green	No	40	SN7447	3.50	3 for \$ 9.

\* Red epoxy case, others clear. \*\* Litronix and Opcoa's pin-for-pin equals and electrical specs as MAN-1 or MAN-4. \*\*\* LED "dot" missing.

## HIGH POWER TRANSISTOR \$1.49 WITH HEAT SINK

Removed from new equipment! Includes popular 2N174 doorknob transistor for TO-36, germanium, PNP, 150 watts, V<sub>CEO</sub> 80V, 15 amps, 10 hf. For ignition, high power transmitters etc. Mounted on metal sink 3 x 2 1/2 x 1 1/2.

3 for \$3



## Potter & Brumfield KAP RELAYS

Year choice 3 for \$7.50 **\$2.98**

3PDT  12 VDC  115 VAC

Excellent for "HAM" use as antenna switching, latching, transmit, receive, etc., and 100's of commercial or industrial uses. Includes plastic dust-cover with diagram and hookup info, 11-pin plug-in base. Contacts mounted gold flashed silver, stationary overlay, with silver cadmium oxide movable. All contacts 10 amp 3PDT. Coil data: 16VAC 2250 ohms, 17.5 ma, 12 VDC 21 mls 16V ohms. Size: 2 1/2" x 1 1/2" x 1 1/2", Wt. 4 ozs. Center pin missing. Comar Mfg. type equal too.

## 1" SQ MINI METERS

- \* Plastic case
- \* Red needle indicators
- \* Balancing, stereo, tape, amps. **\$1.49**
- \* VU, side mtg, plus 3 minus 20 db. 3 for \$3.75
- \* VU, front mtg, plus 3 minus 20 db.



## LINEAR Op Amps

FACTORY GUARANTEED FACTORY TESTED

Buy 3 — Take 10% off

<input type="checkbox"/> 531 Hi speed rate-op amp (TO-5)	\$2.50
<input type="checkbox"/> 532 Micro power 741 (TO-5)	2.50
<input type="checkbox"/> 533 Micro power 709 (TO-5)	2.50
<input type="checkbox"/> 536 FET input op amp (TO-5)	2.50
<input type="checkbox"/> 537 Precision op amp (TO-5)	3.25
<input type="checkbox"/> 538 Precision 723 voltage reg. (DIP)	1.17
<input type="checkbox"/> 556 S Times faster than 741C	2.10
<input type="checkbox"/> 558 Dual 741 (TO-5)	1.00
<input type="checkbox"/> 560 Phase lock loops (DIP)	3.25
<input type="checkbox"/> 561 Phase lock loops (DIP)	3.25
<input type="checkbox"/> 562 Phase lock loops (DIP)	3.25
<input type="checkbox"/> 563 Phase lock loops (DIP)	3.25
<input type="checkbox"/> 566 Function generator (TO-5)	3.25
<input type="checkbox"/> 567 Tone decoder (A)	3.25
<input type="checkbox"/> 702C Hi-grain, DC amp (TO-5)	.49
<input type="checkbox"/> 703C RF-IF, amp, 14 chks (TO-5)	1.00
<input type="checkbox"/> 704 TV sound IF system	1.50
<input type="checkbox"/> 709C Operational amp (A)	.49
<input type="checkbox"/> 709CV Op amp (mini DIP)	.49
<input type="checkbox"/> 710C Differential amp (A)	.49
<input type="checkbox"/> 711C Dual diff. comp (A)	.49
<input type="checkbox"/> 723C Voltage regulator (A)	.95
<input type="checkbox"/> 739 Diff. Video Amp	1.75
<input type="checkbox"/> 741C Frequency compensator 709 (A)	.49
<input type="checkbox"/> 741CV Freq. comp 709 (Mini DIP)	.49
<input type="checkbox"/> 747C Dual 741C (A)	1.25
<input type="checkbox"/> 749C Freq. sel. 741C (A)	1.25
<input type="checkbox"/> 803 Gain Block	1.20
<input type="checkbox"/> 709-709 Dual 709C (DIP)	1.00
<input type="checkbox"/> 739-739 Dual stereo preamp	1.98
<input type="checkbox"/> 741-741 Dual 741C (A)	1.00
<input type="checkbox"/> PA265 3-Watt voltage regulator	1.95
<input type="checkbox"/> ULN2300M Op amp with SCR	1.50
<input type="checkbox"/> CA3065 Video Audio system	1.50

(A) TO-5 or DIP dual in line pak

## Lowest Prices Largest Selection TTL IC's

Buy 3 or more, 10% discount

Brand New	Sale	DIP Packages	Order by type number	Spec sheets on request	ONLY
SN7400	.30	SN7437	.55	SN7472	.50
SN7401	.30	SN7440	.55	SN7473	.55
SN7402	.30	SN7441	.55	SN7474	.55
SN7403	.30	SN7442	1.40	SN7475	1.00
SN7404	.35	SN7443	1.50	SN7476	.65
SN7405	.35	SN7444	1.50	SN7477	.95
SN7406	.45	SN7445	1.50	SN7478	.95
SN7407	.55	SN7446	1.65	SN7479	1.25
SN7408	.35	SN7447	1.45	SN7480	1.25
SN7410	.35	SN7448	1.50	SN7481	1.25
SN7411	.35	SN7449	1.50	SN7482	.99
SN7413	.95	SN7450	3.00	SN7483	1.41
SN7415	.55	SN7451	.30	SN7484	1.41
SN7416	.55	SN7452	.30	SN7485	1.41
SN7417	.55	SN7453	.30	SN7486	1.41
SN7420	.30	SN7454	.30	SN7487	1.41
SN7421	.55	SN7455	.30	SN7488	1.41
SN7422	.35	SN7456	.30	SN7489	4.50
SN7425	.50	SN7457	.30	SN7490	1.49
SN7430	.30	SN7458	.30	SN7491	1.35
SN7432	.35	SN7459	.30	SN7492	1.35
		SN7460	.30	SN7493	1.35
		SN7461	.35	SN7494	1.35
		SN7462	.35	SN7495	1.35
		SN7463	.30	SN7496	1.35
		SN7464	.30	SN7497	.95
		SN7465	.50	SN7498	.95
		SN7466	.50	SN7499	.70
		SN7467	.50	SN7500	.95
		SN7468	.50	SN7501	.95
		SN7469	.50	SN7502	.95
		SN7470	.50	SN7503	.95
		SN7471	.55	SN7504	.95

Factory Marked \* Money Back Guarantee Buy 100 — Take 20%

## NATIONAL EQUALS ON "DIGITAL CLOCK" WAS \$12.88 on a CHIP! as Low as \$8.88

**Money Back Guarantee! With Spec Sheet!**

\* With spec sheets & for all readouts

<input type="checkbox"/> MMS311 28-pin, 6-digit*	\$11.50
<input type="checkbox"/> MMS312 24-pin, 4-digit*	8.88
<input type="checkbox"/> MMS313 24-pin, 6-digit*	9.95
<input type="checkbox"/> MMS314 24-pin, 6-digit*	11.50
<input type="checkbox"/> MMS316 40-pin, 4-digit*	11.50

normal alarm sleep timer, snooze alarm, 12-or-24-hr. .... 14.95


## INTEGRATED CIRCUIT SOCKETS

Buy Any 3 Take 10% Discount!

<input type="checkbox"/> 14-Pin, DIP	\$ .45
<input type="checkbox"/> 14-Pin, Wire Wrap	.59
<input type="checkbox"/> 14-Pin, Side Mount	1.00
<input type="checkbox"/> 16-Pin, DIP	.59
<input type="checkbox"/> TO-5, 8 or 10-Pins	.20

## 'HAM' UHF 400 MC HIGH POWER TRANSISTORS \$3.95

By RCA or equal 2N3632, NPN, 23 watts, 3 amps, TO-60 case, with stud mtg. VCEV max 60.




Terms: add postage. Rated: net 30  
 Phone Orders: Wakefield, Mass. (617) 245-3829  
 Retail: 16-18 Del Carmine St., Wakefield, Mass. (off Water Street) C.O.D.'S MAY BE PHONED

15c CATALOG on Fiber Optics, 'IC's, Semi's, Parts

## POLY PAKS

P.O. BOX 642H LYNNFIELD, MASS. 01960

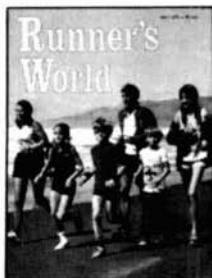

**RUNNER'S WORLD** — The one magazine written by, for and about active runners on all levels. Features in-depth how-to articles and interviews.

**1 year (12 issues) \$7.00**



**BOWHUNTER**, a must for the hunting archer. Written for, by and about bowhunters. Authoritative, informative, entertaining and well-illustrated how-to and where-to-go articles.

**1 year (6 issues) \$3.50**



**DRAMA REVIEW** explores trends in avant-garde performance. Illustrated articles on staging, acting and directing, use of film, video-tape and dance make this journal indispensable to the theatre-head. 160 pages.


**1 year (4 issues) \$9.50**



**FORUM** — A monthly magazine and mid-month newsletter featuring commentary, politics, issue proposals and book reviews to bridge the gap between ideas and politics.

**1 year (24 issues) \$10.00**
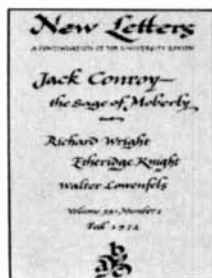
## SPECIAL INTEREST MAGAZINES OF SPECIAL INTEREST TO YOU




**NEW LETTERS** — Specialist in highest quality writing and photography, often neglected, unpublished work by well-knowns such as Richard Wright, Ben Shah. American Libraries calls it "a magazine to be envied."

**1 year (4 issues) \$8.00**



•A monthly journal of Rock Culture, Boogie and Burger Visions. Unbeatable coverage of the contemporary scene, movies, books, sports, politics, trash and especially the music. Truly outrageous articles.

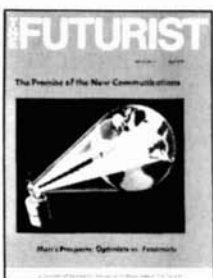**1 year (12 issues + free record) \$7.00**




•THE **FUTURIST**, a journal of forecasts, trends, and ideas about the future, is for anyone interested in the far-reaching social, technological, and human relations changes in the years ahead.

**1 year (6 issues) \$10.00**



•Stimulating commentary on politics and the arts from the best minds of our time. View point of this time tested weekly moderate to liberal.

**1 year (48 issues) \$15**

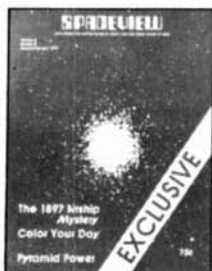

•**SPACEVIEW** — The Magazine of the Occult. Regular features include astrology horoscope, UFO reports, ESP research, articles on ghosts, astral projection, sleep learning, hypnotism and much more.

**1 year (6 issues) \$4.00**



**TAKE ONE** — America's most popular film magazine. Articles on current hits and golden oldies. Interviews with actors and directors, and always plenty of reviews and regular columns.

**2 years (12 issues) \$4.50**



•**TRACK & FIELD NEWS**—Reporting all major track and field events, from high school to the Olympics, plus interviews, feature articles, action photos. The world-recognized bible of the sport.

**1 year (18 issues) \$9.00**





•ANTIQUE MOTOR NEWS is an invaluable guide to finding cars, parts and equipment. Most famous for its Master Calendar telling of all events dealing with old cars.  
**1 year (12 issues) \$4.00**



•MEXICO'S WEST COAST MAGAZINE — Be the one who knows where to stay, where to go, where to eat, what to drink, where to swim, dance—and what to do tomorrow.  
**2 years (12 issues) \$5.00**



•WEEK END FLYER, The News-magazine of Flying Fun. More Western news, activities, pictures and classified ads than any other flying publication. Subscribe today.  
**1 year (12 issues) \$3.00**



HAM RADIO is the largest, independent amateur radio magazine. Clear, concise, easy to understand articles bring our readers the latest in radio communications equipment and technology.  
**1 year (12 issues) \$6.00**

## SPECIAL INTEREST MAGAZINES OF SPECIAL INTEREST TO YOU

Some magazines don't try to please everybody. Instead, they try to please people with special interests. Not surprisingly, they're called "special interest" magazines. Whatever your age, occupation, geographical location, hobby, sex, field of study, avocation, pastime, intellectual tastes or religious, political or philosophical persuasion, chances are there's a special interest magazine for you, published by people who share your special interest.

There are over 20,000 special interest publications in the U.S. today. Several of the best are presented here. You may subscribe to any one — or ones — that interest you, under the rates specified, and under this

guarantee: if you're not entirely satisfied, each publisher guarantees that you may cancel at any time and receive an immediate and unquestioned refund covering the balance of your subscription.

Look over the selections carefully. Isn't there a special interest magazine here that specially interests you? One that you've been meaning to subscribe to? Now's your chance. To order, just fill in the coupon and return it. Send no money — the magazines you choose will bill you.

(Note: You must send payment with your order only on magazines marked \*)

Just fill in and return the coupon to subscribe to any of these magazines on a guaranteed basis

MSN		<b>912</b>
Magazine Selection Network		
350 S. Kellogg Ave., Suite S, Goleta, CA 93017		
Please enter my subscription(s) to the Special Interest magazine(s) indicated below:		
<input type="checkbox"/> Antique Motor News	<input type="checkbox"/> Creem	<input type="checkbox"/> The Futurist
<input type="checkbox"/> Mexico's West Coast Magazine	<input type="checkbox"/> Runner's World	<input type="checkbox"/> New Republic
<input type="checkbox"/> Week End Flyer	<input type="checkbox"/> Bowhunter	<input type="checkbox"/> Spaceview
<input type="checkbox"/> Ham Radio	<input type="checkbox"/> Drama Review	<input type="checkbox"/> Take One
<input type="checkbox"/> New Letters	<input type="checkbox"/> Forum	<input type="checkbox"/> Track & Field News
Name _____		
Address _____		
City _____ State _____ Zip _____		
Fill in coupon, clip it out and return it — with your check or money order if necessary — to the address above.		

## RECEIVERS, OK GRTD, WITH BOOKS:

SP-600-JX: AM, CW, 0.54-54 MHz continuous	275.00
R388/URR: AM, CW, 1/2-30 1/2 MHz linear dial, PTO	325.00
R390A/URR: 1/2-32 MHz by digits, PTO tuning	595.00
AN/FRR-59B (later version WRR-2): 2-32 MHz digital tune each 500 Hz or continuous. A1, 2, 3, 9, F1, 4. FSTTY, SSB, carrier suppressed, either band or both for 2 different intelligences. Stable and accurate enough to use as freq. meter! Net wt. 276 lbs. in 2 cabinet in rack cradle	750.00
WWVB 60 KHz rcvr/comparator	295.00
WWVB 1 KHz tones, use to calib. 100 KHz	175.00
38-1000 MHz by Band Switching, 4 bands: Separate antenna for each band. AN/ALR-5 modified for 117 v 50/60 cy line. AM/FM. The Tuner is a plug-in converter; the receiver is 30 MHz IF and all that follows IF. Choose selectivities 200 KHz or 2 MHz each side of center. Factory checkout sheet, typical for the original-pack tuner you get, says sensitivity ranges from 1.1µV at 28 MHz to 7 at 1 gHz. IF attenuator is calibrated in 6 dB steps to -74 dB. Diode current meter makes this rcvr useful for relative field strength measurements and harmonic finder. Rcvr unit is exc. used and checked out OK	375.00
30 MHz PANADAPTER may be useful with above	295.00
A.I.L. #132 30 MHz rcvr/amplifier/atten. calib.	99.50
EDDYSTONE AM/CW/FM/NB/MF 19-165 MHz rcvr	295.00
CV-591A: SSB Converter either sideband	137.50
MOTOROLA 3 MHz OSCIL. 5 parts in 10 to 11th	199.50

### Attention!

#### Buyers, Engineers, advanced Technicians:

We have the best test-equipment & oscilloscope inventory in the country so ask for your needs . . . don't ask for an overall catalog . . . we also buy, so tell us what you have. Price it.

**R. E. GOODHEART CO. INC.**  
Box 1220-HR, Beverly Hills, Calif. 90213  
Phone: Area Code 213, Office 272-5707

# GATEWAY ELECTRONICS

8123 PAGE AVENUE  
ST. LOUIS, MISSOURI 63130  
314-427-6116

IC FUNCTION GENERATOR (FUNCTION GENERATOR ON A CHIP) provides Sine, Square, & Triangle wave. 0.001 Hz to 1 MHz — w/data sheet \$8.00

LANGEVIN PROFESSIONAL SLIDE POTENTIOMETER — 10 K — audio taper — NEW \$3.00

6 VOLT GEL CELL — 1 amp hr. 2" x 1 1/8" x 1 1/8" rechargeable \$3.50

CLOCK CHIP — National 5314 12/24 hr — 4 or 6 digit — 24 pin package w/data \$12.95

IC STEREO AMPLIFIER (STEREO AMPLIFIER ON A CHIP) 2 watts per channel — 14 pin DIP package w/data sheet — \$2.00

IC STEREO PREAMPLIFIER (STEREO PRE-AMP ON A CHIP) MC1339P — w/data sheet \$1.25


LASER DIODE — w/data sheet \$7.50

LENS — 8 1/4" (209mm) focal length coated lens f4.5 — aperture adj. down to f 32 \$12.50

\$5 Minimum Order.

Visit us when in St. Louis.

Please include sufficient postage.

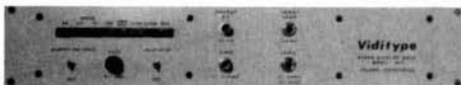

### RTTY VIDEO DISPLAY UNIT

800 CHARACTERS—ANY TV SET  
**VIDITYPE**  
MODEL 872 \$550  
WRITE FOR BROCHURE

**LELAND ASSOCIATES**  
18704 GLASTONBURY RD.  
DETROIT, MI. 48219

## STAR-TRONICS

### INDUSTRIAL AND GOVERNMENT ELECTRONIC SURPLUS

PARTS & PIECES FOR SCHOOLS, SHOPS, HAMS & HOBBYISTS

SEND FOR OUR LATEST ALL DIFFERENT MONTHLY PICTURE CATALOG. NOW!

Box 17127, Portland, Ore. 97217

# STOP

TEN-TEC-TRITON II	\$606.00
TEN-TEC-TRITON I	\$519.00
MAGNUM 6 RF PROCESSORS	
MOR GAIN ANTENNAS	\$ 40.00
GENAVE-2	\$249.95
MOSLEY-CLASSIC 36	\$188.10
REGENCY HR-212	\$259.00
HYGAIN TH6DXX	\$179.95
GALAXY GT-550A	\$595.00
HALLCRAFTERS SR400A	\$995.00
GLADDING 25	\$249.95
STANDARD 146A	\$289.00

## LOU GOLDSTEIN, K4LAN

P.O. BOX 3561, PENSACOLA, FLA. 32506  
Drop me a line for those unadvertised extras

**NOW**

EXCLUSIVE 66 FOOT

NO TRAPS — NO COILS — NO STUBS — NO CAPACITORS

Fully Air Tested — Thousands Already in Use



**IS BACK**

#16 40% Copper Weld wire annealed so it handles like soft Copper wire—Rated for better than full legal power AM/CW or SSB Coaxial or Balanced 50 to 75 ohm feed line—VSWR under 1.5 to 1 at most heights—Stainless Steel hardware—Drop Proof Insulators—Terrific Performance—No coils or traps to break down or change under weather conditions—Completely Assembled ready to put up—Guaranteed 1 year—ONE DESIGN DOES IT ALL; 75-10HD—ONLY \$12.00 A BAND!

Model 75-10HD	\$60.00	66 Ft	75 Thru 10 Meters	Model 75-40HD	\$40.00	66 Ft	75 Thru 40 Meters
Model 75-20HD	\$50.00	66 Ft	75 Thru 20 Meters	Model 40-20HD	\$33.00	35 Ft	40 Thru 20 Meters
			Model 80-40HD	\$42.00		69 Ft	80-40-15 Meter (CW)

ORDER DIRECT OR WRITE FOR FULL INFORMATION



300H Shawnee  
Leavenworth, Kansas 66048  
OR THRU YOUR FAVORITE DISTRIBUTOR

# If you like 2 METER . . .

## YOU'LL LOVE OUR



**15 OR 1 WATT POWER OUT/SWITCH SELECTABLE /  
FULL 12 CHANNEL TRANSMIT AND RECEIVE CAPABILITY**

You'll like the crystal clear transmit and receive performance of this compact, 2 meter unit and so will those listening. The 12 transmit channels are provided with individual trimmer capacitors for the optimum in point-to-point and repeater applications. A HI/LO power switch provides 1 watt output or full rated output. The receiver has an audio output of 3 watts at excellent sensitivity. Solid state, American made quality at a low price.

### \$229<sup>00</sup>

AMATEUR NET

includes plug-in ceramic mike,  
mounting bracket and transmit and  
receive crystals for 146.94 MHz.

**Regency**  
the first name in solid state

### THE FM LEADER IN 2 METER AND 6 METER . . . AND NOW 220 MHz

# INTERNATIONAL ELECTRONICS UNLIMITED

## TTL

7400	\$ 25	7446	\$1 45	74122	\$ .55
7401	25	7447	1.45	74123	1.15
7402	25	7448	1.50	74126	.95
7403	25	7450	.29	74151	1.25
7404	29	7451	.32	74150	1.25
7405	27	7453	.32	74151	1.05
7506	55	7454	.45	74153	1.45
7407	53	7455	.32	74154	1.75
7408	29	7480	.30	74155	1.35
7409	29	7481	.30	74156	1.90
7410	25	7484	.45	74157	1.50
7411	.35	7485	.45	74181	1.85
7413	95	7470	50	74182	1.80
7415	50	7472	45	74164	2.95
7416	50	7473	55	74185	2.95
7417	50	7474	55	74186	1.95
7420	25	7475	95	74173	1.85
7421	.32	7476	55	74175	1.95
7422	.32	7478	65	74178	.95
7423	37	7483	1.25	74177	.95
7425	39	7485	1.20	74180	1.15
7428	55	7486	1.20	74181	4.75
7427	39	7489	3.25	74182	1.10
7430	25	7490	1.25	74180	1.65
7432	30	7491	1.40	74182	1.85
7437	50	7492	1.05	74183	1.65
7438	55	7493	1.05	74184	1.65
7440	25	7494	1.10	74185	1.10
7441	1.25	7495	1.05	74186	1.35
7442	1.15	7496	1.05	74187	1.15
7443	1.25	74100	1.40	74188	2.50
7444	1.30	74107	.65	74189	2.50
7445	1.25	74121	.65		

### Low Power TTL

74L00	\$ 40	74L42	\$1.75	74L85	\$1.25
74L02	40	74L45	1.45	74L86	.95
74L03	40	74L51	40	74L90	1.75
74L04	40	74L71	60	74L91	1.50
74L06	40	74L72	60	74L93	1.75
74L10	40	74L73	80	74L95	1.75
74L20	40	74L74	80	74L94	2.95
74L30	40	74L78	.90		

### 8000 Series TTL

8054	\$ 45	8123	\$1.75	8570	\$2.95
8060	30	8182	1.75	8600	1.15
8061	69	8214	1.95	8618	.95
8082	69	8230	2.95	8612	1.25
8093	69	8290	.95	8622	2.95
8098	69	8295	.95	8630	1.50
8122	1.05	8520	1.45	8831	2.95

Specify spec. sheets required with order. Add \$ .50 per spec sheet for items less than \$1.00 ea.

### ALL DIP PKGS.

## Linear

LM 300	Pos V Reg (isop 723)	TO6	\$ .95 ea.
LM 301	Hi performance AMPL	TO6	.45 ea.
LM 302	Voltage Follower	TO6	.55 ea.
LM 304	Negative Voltage Regulator	TO6	1.25 ea.
LM 305	Positive Voltage Regulator	TO6	1.25 ea.
LM 307	Op AMP (isop 7411)	TO6	.45 ea.
LM 308	Micro Power Op Amp	TO6	1.25 ea.
LM 309H	5 V Regulator	TO6	1.25 ea.
LM309K	5 V I Regulator	TO6	1.25 ea.
LM 310	Voltage Follower Op Amp	TO6	1.45 ea.
LM 311	Hi Perf. Voltage Comp.	TO6	1.35 ea.
LM 320	5.2 V Negative Regulator	TO3	1.95 ea.
LM 320	12 V Negative Regulator	TO3	1.95 ea.
LM 370	AGC/Squelch Amp	DIP	1.25 ea.
LM 372	AF - I/F Strip-Divector	DIP	.95 ea.
LM 378	Pos Voltage Regulator	DIP	.95 ea.
LM 380	2 watt Audio Amplifier	DIP	1.15 ea.
LM 550	Precision Voltage Regulator	DIP	.95 ea.
LM 709	Op Amp	TO6 or DIP	10/83.25 .39 ea.
LM 723	Voltage Regulator	TO6 or DIP	6/53.25 .75 ea.
LM 741	Comp. Op Amp	TO6 or DIP	10/83.95 .45 ea.
LM 747	Dual 741 Op Amp	TO6 or DIP	4/83.50 .95 ea.
LM 8000	Quad Amplifier	DIP	.50 ea.
LM 75451	Dual Peripheral Driver	DIP	.48 ea.
LM 75452	Dual Peripheral Driver	DIP	.48 ea.

Specify TO6 or Dip Package  
for items less than \$1.00 ea.

## Phase Locked Loops

NE 985	Phase locked loop frequency generator	TO6 or DIP	\$2.95 ea.
NE 986	Phase locked loop	TO6 or DIP	2.95 ea.
NE 987	PLL/TONE Gen.	TO6 or DIP	2.95 ea.

## Memories

1101	256 bit RAM MOS (2801)	\$2.50 ea.
1103	1024 bit RAM MOS	7.95 ea.
7489	94 bit RAM TTL	3.25 ea.
8223	Programmable ROM	6.95 ea.

\* NEW ITEM \*  
MM 5280 1024 bit RAM Second generation version of 1103. Featuring 16 pin DIP rather than 18 pin. . . . 30% less power consumption. Introductory Price . . . . . 9.95 ea.

# NEW YEAR SPECIALS

### 5002 LSI Calculator Chip

Battery powered version of 8001  
with 12 MAN 3M LED  
Complete with Data . . . . . \$19.95/ret

1101	256 Bit RAM MOS 2501	\$2.00 ea.
8223	Programmable ROM	6.95 ea.
LM309K	5 V I Regulator	1.75 ea.
8001	Reprogrammable One Shot	.85 ea.
LM75461	Dual Peripheral Driver	39 ea.
7437	Quad 2-in NAND Buffer	3/81.00
7438	Quad 2-in NAND Buffer	3/81.00
7453	Expandable AND-OR-INVERT gate	4/81.00
7490	Decade counter	1.10 ea.
74121	One Shot (monostable multivibrator)	.39 ea.
74183	Up/down binary counter	1.39 ea.

### MOS Grab Bag

\$ Untested MOS MIX (dip) . . . . . \$ 2.00  
50 Untested MOS MIX . . . . . \$10.00

## NEW YEAR SPECIALS IN EFFECT THROUGH JANUARY

### 5001 LSI Calculator Chip

Overstocked on this popular calculator chip.  
This month only . . . . . With Data . . . . . \$ 4.95 ea.

### 4000 Series - RCA Equivalent

CD 4001	.85	CD 4011	.85	CD 4025	.85
CD 4002	.85	CD 4012	.85	CD 4030	.85
CD 4008	1.90	CD 4016	1.50	CD 4036	3.85
CD 4010	.85	CD 4023	.85		

### CMOS

74C00	\$ .90	74C73	\$1.70	74C181	\$3.25
74C02	.90	74C74	1.50	74C182	3.25
74C04	1.10	74C78	1.70	74C183	3.25
74C10	.90	74C107	1.50	74C182	3.25
74C20	.90	74C157	2.25	74C186	3.00
74CA2	2.16	74C180	3.30	80C87	1.50

### Calculator Chips

5001 LSI (40 pin) Add, subtract, multiply & divide 12 digit  
Data supplied with chip . . . . . \$8.95 ea.  
Data only Refundable w/purchase . . . . . 1.00 ea.  
8002 LSI Similar to 5001 except designed for battery power  
Data supplied with chip . . . . . \$8.95 ea.  
Data only Refundable w/purchase . . . . . 1.00 ea.  
9006 LSI (28 pin) Full four function memory, 12 digit display and calc. 7 segment multiplexed output  
Data supplied with chip . . . . . \$10.95 ea.  
Data only Refundable w/purchase . . . . . 1.00 ea.

### LED

MV108 Visible red SUPER SPECIAL . . . . . \$ .25 ea.  
MV50 type red emitting . . . . . .25 ea. 3/81.00  
MV5000 type Large red . . . . . .35 ea. 3/81.00  
ME I infra red 1018 . . . . . .80 ea.  
MAN 1 The Original . . . . . 3.95 ea.  
MAN 3 type . . . . . 1.95 ea. 3 or more 1.49 ea.  
MAN 4 type . . . . . 2.75 ea. 3 or more 2.50 ea.  
Data-Lite 707 (MAN 1 repl) . . . . . 3.25 ea.

### Opto Isolators

MCA 2 30	Darlington Diode	\$ .95 ea.
MCD 2	Diode	1.35 ea.
MCT 2	Transistor	1.45 ea.

### Digital clock . . . on a Chip

MM 5311 (28 pin) Any readout 8 digit BCD with spec. sheet . . . . . \$11.95 ea.  
MM 5312 (24 pin) Any readout 4 digit type BCD with spec. sheet . . . . . 8.95 ea.  
MM 5313 (28 pin) Any readout 6 digit type BCD with spec. sheet . . . . . 10.95 ea.  
MM 5316 (28 pin) LED readout second readout 8 digit with spec sheet . . . . . 10.95 ea.  
MM 5318 (40 pin) Normal alarm, snooze alarm, sleep timer 12 or 24 hr. operation with spec. sheet . . . . . 16.95 ea.

### UNTESTED SECONDS

MM502	Dual 25-bit dynamic shift register	TO6	\$ .35 ea.
MM503	Dual 50-bit dynamic shift register	TO6	.35 ea.
MM504	Dual 18-bit static shift register	TO6	.35 ea.
MM505	Dual 32-bit static shift register	TO6	.35 ea.
MM506	Dual 100-bit shift register	TO6	.35 ea.
MM5010	Dual 84-bit accumulator	TO6	25 ea.
MM5016	6 1/2 bit dynamic shift register	TO6-DIP	.25 ea.
MM5013	1024 bit dynamic shift register/counter	TO6-DIP	.55 ea.
MM5018	Dual 256 bit mask prog. shift register	TO6	.25 ea.
MM5050	Dual 32-bit static shift register	TO6	.35 ea.
MM5063	Dual 100-bit static shift register	TO6	.25 ea.
MM5054	Dual 64/72/80-bit static shift register	DIP	.35 ea.
MM5230	2048-bit read only memory	DIP	1.00 ea.
MM5240	2560-bit static character generator	DIP	1.00 ea.
MM1403	1024-bit dynamic shift register	DIP	.65 ea.
MM1404	1024-bit dynamic shift register	DIP	.85 ea.

### MOS Shift Registers 2500 Series

2502	2506	2509	2510	2511	2518	2519	2521	2522	4/10
Untested seconds . . . . . 1.35 ea.									

Grab Bag Specials  
15 Assorted TTL's (dip) . . . . . \$1.00/bag  
25 Assorted 01L's (dip) . . . . . \$1.00/bag

### ON ORDERS OVER \$25.00 DEDUCT 10%

Satisfaction guaranteed. All items except as noted are fully tested. Minimum order \$5.00 prepaid in U.S. and Canada. Calif. residents add sales tax. Orders filled within three days from receipt.

### INTERNATIONAL ELECTRONICS UNLIMITED

P.O. BOX 1708R  
Montreay, Calif. 93940

# flea market



■ **RATES** Commercial Ads 35¢ per word; non-commercial ads 10¢ per word payable in advance. No cash discounts or agency commissions allowed.

■ **COPY** No special layout or arrangements available. Material should be typewritten or clearly printed and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** can not check out each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue. Deadline is 15th of second preceding month.

■ **SEND MATERIAL TO:** Flea Market, Ham Radio, Greenville, N. H. 03048.

**GOOD NEWS** — SRRC Hamfest June 2, 1974 at fabulous new site in Princeton Illinois Fairgrounds. SRRC-W9MKS, R.F.D. #1, Box 171, Oglesby, Illinois 61348.

**LOGIC Educational Systems** for WWW, SSTV, RTTY. Eight 2 1/4" x 3" PCB's, plans, \$3. Hornung, Box 24614, San Jose, Ca. 95154.

**FRAME & DISPLAY** your QSL's with 20 pocket plastic holders. Two for \$1.00, seven for \$3.00 from your Dealer or direct, prepaid. Free sample to Dealers upon request. TEPABCO, Box 198H, Gallatin, Tennessee 37077.

**FOR YOUR FUTURE ROBYN RADIOS** send your order to, Two Way Radio Sales, 1501 Monroe Street, Bogalusa, La. 70427 or 202 Farrell Street, Picayune, Miss. 39466.

**CALCULATOR OWNERS:** Use your +—X÷ calculator to compute Square Roots, Trigonometric Functions, Logarithms, Exponentials and More! Quickly, Accurately, Easily! Send Today for the Improved and Expanded Edition of the First and Best Calculator Manual — now in use throughout the World . . . only \$2.00 Postpaid! Be sure to try this manual before buying a more expensive calculator — Absolutely Unconditional Money-Back Guarantee — and FAST Service! Mallmann Optics and Electronics, Dept.-F, 836 South 113, West Allis, Wisconsin 53214.

**QSLs CATALOG SAMPLES** 35¢. Ritz Print Shop, 5810 Detroit Avenue, Cleveland, Ohio 44102.

**HEATHKIT SB-102**, CW filter, AC and DC supplies, mobile mount, remote LMO, speaker, manual, asking \$475. Heathkit SB-110, AC supply, speaker, manual, \$225. Also Hallicrafters HA-1 keyer, \$50. All good condition. John Boston WB4RUA, Box 354, Calhoun, Georgia 30701. (404) 629-3048.

**MOBILE IGNITION SHIELDING** provides more range with no noise. Available most engines in assembled or kit forms, plus many other suppression accessories. Free literature. Estes Engineering, 543-H West 184th, Gardena, California 90248.

**SIX ONLY PT4164C**, TRW 25W RF transistor, same as 2N5591/SS4153, \$6 each, all for \$30. Bill Latta, 7309 Greentawn, Louisville, Ky. 40222.

**TREASURE COAST HAMFEST**, March 9-10 — sponsors, Vero Beach Amateur Radio Club, Inc. and St. Lucie Repeater Association, Community Center, Vero Beach, Fla. 32960. Free continental breakfast — first prize 80-10 transceiver. Dozens of others. Speakers. Swappers row. Tickets and information, write: Ike Roach, K4QM, Box 3088, Vero Beach, Fla. 32960.

**THE WEST ALLIS MIDWINTER SWAPFEST** is Sunday, January 27, 1974 at Waukesha County Exposition Center located on Waukesha County Trunk Highway FT, southwest of the Waukesha County Airport. Directions: Take Waukesha County Trunk Highway F exit on I-94 south 1.2 miles to County FT and west .8 miles to swapfest. Doors open at 8 A.M. Refreshments available. Talk in station on 3985 and 146.94. Rain or shine. Tickets \$1 advance; \$1.50 at the door. For details write WA9KRF, 4582 South Ahmedi Avenue, Milwaukee, Wisconsin 53207.

**SIGNAL ONE OWNERS**, expert and prompt service by ex-Signal/One engineer. Also will purchase your functioning or not functioning unit or spare parts. Write or call for details. Larry Pace, K2LXP/7, 1071 W. Roller Coaster, Tucson, AZ. 85704 (602-888-5234).

**CIRCULATORS** 1.65 - 2.1 gip \$21.00 pp. Joe McCormick of Lake City has been using on 2.3 in tropo with v.g. results. Some 2.0 - 2.4 gip \$35.00 pp. Most have sn sheets, charts. Eimac 1K20XN-A, new \$16.00 pp. TWS 12 or TWS15 TWT G.E., 1.7 - 2.7 gip 30 mw in 20 watt out, most with sn sheet. New \$165.00 REA only. Eimac WL200, mixers, isolators, wave meters, most x band. Ramcor M & L 1200B Densimeter sn L band & ant. book and chart, \$55.00 pp. If you have my last list take 20% on any piece of equipment, or clean me out. Doug Craton, 5625 Balfrey Dr., W. Palm Bch, Fla. 33406.

**P.C.'s Need a project for winter?** Send a SASE for list of available boards. Semtronics, Charles R. Sempirek, Route #3, Box 1, Bellaire, Ohio 43906.

**432 MHz TRANSMITTER CONVERTER**, 5 watts out, 6939 mixer, 6939 amplifier and solid state LO chain. 4 1/2 x 7 1/2 cast aluminum box. Send for more information. Carmichael Communications, P. O. Box 256, Carmichael, CA 95608.

**MANUALS** for most ham gear made 45/65, some earlier. Send SASE for specific quote. Hobby Industry, W2JJK, Box H-864, Council Bluffs, Iowa 51501.

**TOUCH-TONE PADS** . . . twelve button . . . lighted \$15.00 . . . unlighted \$11.00 . . . postpaid/insured . . . Swank Roberts, WA5GNT, 1130 Fuller Drive, Apartment 223, Dallas, Texas 75218 . . . (214) 328-9307.

**PRINTED CIRCUIT DRILL BITS**. Trumbull, 833 Balra Drive, El Cerrito, California 94530.

**FOR SALE:** 30S-1; 51S-1; 55G-1; 312B-4; 32S-3; 516F-2; Hallicrafter keyer: Vibroplex key. Package: \$2,875. You pay shipping — Certified check or money order. All in excellent physical and functional order. No time to use. KBACF - 15317 W. Brant Road, St. Charles, Michigan 48655. Phone (517) 585-2966 - nights or weekends (517) 636-9333 - days.

**EMBROIDERED EMBLEMS AND PATCHES**. Custom made from your design. 10 to 1000's. Write Russell, 1109 Turner St., Augusta, Maine 04210.

**WORLD QSL** — See ad page 86.

**10 POUNDS ELECTRONICS PARTS \$10**, Tubes for sale too . . . Williams, P. O. 7057, Norfolk, Va. 23509.

**HIGH-PERFORMANCE H.F. SYNTHESIZER** replaces VFO and delivers output 1-30 MHz continuous coverage with accuracy, stability, resolution, and calibration to one Hertz. Write for information. Petit Logic Systems, Box 51, Oak Harbor, Wa. 98277

**SEND PERFECT MORSE WITH YOUR RTTY** and save over \$150 on price of a comparable Morse keyboard. TMC-1 RTTY to Morse converter connects right into your loop trouble-free and accepts input from keyboard or paper tape reader. Entire circuit including 64-letter buffer memory on one 4 x 6 inch board for \$310. Write for information. Petit Logic Systems, Box 51, Oak Harbor, Wa. 98277

# The 1974 Callbook is here.



## Hallelujah!

Here they are, the Brand New 1974 Callbooks. Both the U.S. and DX Callbooks have been completely updated in these exciting larger than ever editions.

Buy your 1974 Callbooks today and you will enjoy the very latest edition for 12 full months as the next new ones are a year away. Put it off and only you will be the loser.

The CALLBOOK is a vital part of every amateur radio station. Over 285,000 listings in the US CALLBOOK and approximately 200,000 in the DX edition make these two volumes an indispensable reference. Not only do the CALLBOOKS list QTH's, but they also have page after page of valuable charts, tables and maps all designed to make your operating more efficient and more fun.

To makes these volumes even more valuable special service editions are issued each 3 months, but only to owners of the 1974 CALLBOOKS, which give complete cumulative updated information for the 1974 CALLBOOKS.



<b>US CALLBOOK</b> (less service editions) Just \$9.95	<b>DX CALLBOOK</b> (less service editions) Just \$8.95
<b>US CALLBOOK</b> (with service editions) \$15.95	<b>DX CALLBOOK</b> (with service editions) \$14.95

Mail orders add 50¢ per CALLBOOK postage and handling.

See your favorite dealer or send today to:

WRITE FOR  
FREE  
BROCHURE

RADIO AMATEUR  
**callbook** INC.  
Dept. E 925 Sherwood Drive  
Lake Bluff, Ill. 60044

**1000 PIV AT 2.5 AMP DIODES.** New Motorola HEP-170. 10 for \$2.50, 100 and up 20¢ each, postpaid. K. E. Electronics, Box 1279, Tustin, California 92680.

**QSLs.** Second to none. Same day service. Samples 25¢. Ray, K7HLR, Box 331, Clearfield, Utah 84015.

**LAKE COUNTY IND.** Amateur Radio Club Banquet. For the 21st consecutive year, the Lake County Amateur Radio Club, Inc., proudly announces its annual banquet. The date is February 9, 1974, and the time is 6:30 p.m., CST (We start on time). The place is the Sherwood Club, 600 E. Joliet St., Schererville, Ind. (Two miles east of Rt. 41, ¼ mile north of Rt. 30). Chicken dinner — all you can eat — awards, fellowship, speeches, entertainment, gifts, all for \$6.00 per ticket. Come. Bring your wife or girl friend. Tickets available from club ticket volunteers or from the ticket chairman, Herbert S. Brier, W9EGQ, 385 Johnson St., Gary, Indiana 46402. Positively no tickets sold at the door!

**RTTY BAUDOT LOOP TO ASCII CONVERTER** accepts loop signal at any RTTY speed and delivers corresponding 6 or 8 level parallel ASCII, all on one 4 x 6 inch circuit board for \$120. Petit Logic Systems, Box 51, Oak Harbor, Wa. 98277

**TELETYPEWRITERS** — Kleinschmidt — portable, fixed, sets, punches, parts, reconditioned, reasonable. Mark/Space Systems, 3563 Conquista, Long Beach, Calif. 90808. 213-429-5821.

**ACTIVE HAMS** — Monthly mailer of reconditioned and new equipment specials. Sell - Buy - Trade. Write: Associated Radio, 8012 Conser, Overland Park, Kansas 66204.

**TRAVEL-PAK QSL KIT** Converts photos, post cards to QSLs! Send call and 25¢ for personal sample. Samco, Box 203H, Wynantskill, N. Y. 12198.

**WE BUY** Late Model Collins-Drake-Swan. Top prices cash. Associated Radio, 8012 Conser, Overland Park, Kansas 66204. Call: 913-381-5901.

**FOR SALE:** Commercial Test Equipment. Send SASE for equipment list. Northern Communications & Equipment, Inc., P. O. Box 1000, Auke Bay, Alaska 99821.

**TECH MANUALS** for Govt. surplus gear — \$6.50 each. R-220/URR, R-389/URR, R-390/URR, R-274/FRR, SP-600JX, BC-639A, BC-779B, USM-16, URM-32, TS-497B/URR, OS-8C/U, TT-63A/FGC, CV-591A/URR, BC-160, GRC-19, TS-403/U, URM-25D, RCK, LM-21, TS-148/UP, BC-348JNQ, TS-382D/U, PRC-10, ALR-5. Thousands more available. Send 50¢ (coin) for list. W3IHD, 7218 Roanne Drive, Washington, D. C. 20021.

**SILVER PLATING BREAKTHRU!** No mess or lethal chemicals. Simply brush on. 6 liquid ounces plates 1800 square inches copper - brass. Durable. \$6.50. Abar Research, 11118 Parker, Mokena, Ill. 60448.

**HAM ASTRONOMERS:** Complete standard Questar, 3½ inch, full aperture sun filter, Exacta 35mm. SLR camera, adaptors, Linhof tripod, etc. WABYNI, 1720 N. Broadway, Hastings, MI 49058.

**WE BUY ELECTRON TUBES, diodes, transistors, integrated circuits, Semiconductors.** Astral Electronics, 150 Miller Street, Elizabeth, New Jersey 07207, (201) 354-2420.

**SELL:** IRE Proceedings Unbound 1928 thru 1972. 45 volumes - best offer. Gonset G50 6m XCVR \$110. WA2DWV, R. D. 1, Box 155, Freehold, N. J. 07728.

**USED MYLAR TAPES** — 1800 foot. Ten for \$8.50 postpaid. Fremerman, 4041 Central, Kansas City, Mo. 64111.

**VERY in-ter-est-ing!** Next 5 big issues \$1. "The Ham Trader," Sycamore IL 60178

**DAYTON HAMVENTION** expands to three days April 26, 27, 28, 1974 at HARA Arena and Exhibition Center. Brochures mailed March 15th. Write for information if you have not attended the last two years. P. O. Box 44, Dayton, Ohio 45401.

**MOBILE OPS** — Completely shielded ignition system kits available for most U.S. cars 1965-73. Alternator, generator and regulator filters, feed-thru capacitors, copper braid in stock. Write Summit Enterprises, 36 Winchip Road, Summit, N. J. 07901.

**TEXTRONIX 535A OSCILLOSCOPE:** Dual trace, triggered sweep. Less probes, laboratory calibrated, \$575 or best offer. You pay shipment. H. Karimi, Box 405, Fairborn, Ohio 45324.

## L. I. Electronic Supermart (Off the wall self service)

**New P.C. Boards — G10, 1 oz. - 1 side copper-fiber glass**  
6" x 6", 80¢ ea. — 6 x 12, \$1.50 ea. - 12 x 12, \$2.85 ea.

**New P.C. Boards — G10, 1 oz. - 2 side copper-fiber glass**  
6" x 6", \$1.10 ea. - 6 x 12, \$2.00 ea. - 12 x 12, \$3.75 ea.

**New P.C. Boards — G10, Fiber glass punch:**  
F Pattern 4.5 x 6.5, .062 holes, 5 per 1" \$1.30  
P Pattern 4.5 x 6.5, .042 holes, 10 per 1" \$1.35  
G Pattern, 4.5 x 6.5, .062 holes, \$1.30  
Pkg. 10 Bircher P.C. Board, metal 2" slides \$1.00  
Package of 50 flea clips for above punched Boards, .062 75¢

30 ¼ or ½ W resistors, packaged 5 per value your choice of values \$1.00

25-1W resistors, packaged 5 per value, your choice of values \$1.00

15-2W resistors, packaged 5 per value, your choice of values \$1.00

5 ¼ or ½ W, 1% resistors, packaged 5 per value, your choice of values .50

5 ceramic disk caps, .001-01, packaged 5 per value, your choice of values .50

5 mica dip caps, 1 pf-150 pf, packaged 5 per value, your choice of values .50

5 mica dip caps, 180 pf-200 pf, packaged 5 per value, your choice of values .75

5 mica dip caps, 910 pf-1500 pf, packaged 5 per value, your choice of values \$1.00

Wire Kit #22 solid PVC, 6 spools, 6 colors, 50' ea. spool \$3.50

Wire Kit #22 stranded PVC, 6 spools, 6 colors, 50' ea. spool \$3.50

Wire Kit #24 Solid PVC, 6 spools, 6 colors, 50' ea. spool \$3.50

Wire Kit #24 stranded PVC, 6 spools, 6 colors, 50' ea. spool \$3.50

10' — Ten cond. ribbon wire, color coded, #22 or #24, stranded \$1.50

C & K #7101 mini switch, SPDT on-on \$1.05

C & K #7103 mini switch, SPDT on-off-on \$1.20

C & K #7201 mini switch, DPDT on-on \$1.35

C & K #7203 mini switch, DPDT on-off-on \$1.55

Alco 105D MST momentary on-off-momentary on \$1.25

Central Lab DPDT push momentary, SPEC. 4/\$1.00

Connectors, PL259, \$.45; PL258, \$.70; 175U or 176U, \$.20 ea.; UG 88 cu., \$.50; UG 201 a/u (N to BNC adapter), \$.75; RCA to UHF, \$.90.

Encapsulated chokes 1uh to 5 Mh, choice 3/\$1.00

Varo type mini bridge rectifiers, approx. ½" sq. size 2 amp. - 50 v., \$1.25; 4 amp. - 50 v., \$1.25; 6 amp. - 50 v., \$1.25; 2 amp. - 100 v., \$1.25; 4 amp. - 100 v., \$1.25; 6 amp. - 100 v., \$1.25; 2 amp. - 200 v., \$1.50; 4 amp. - 200 v., \$1.50; 6 amp. - 200 v., \$1.50; 2 amp. - 400 v., \$1.50; 4 amp. - 400 v., \$1.50; 6 amp. - 400 v., \$1.50

Triacs — thermo tab package — 1 amp. - 400 v., \$.80 ea.; 3 amp. - 400 v., \$1.40 ea.; 4 amp. - 200 v., \$1.20 ea.; 6 amp. - 200 v., \$1.40 ea.; 6 amp. - 400 v., \$1.60 ea.; 6 amp. - 500 v., \$1.80 ea.; 8 amp. - 200 v., \$1.60 ea.; 8 amp. - 500 v., \$1.80 ea.

To-5 case, 1 amp. - 200 v., \$.70 ea.; 1 amp. - 400 v., \$1.00 ea.

SCR 200 v. - 8 amp. thermo tab \$1.80 ea.

**SEND SELF ADDRESSED ENVELOPE FOR FREE MAILER. INCLUDES MANY HUNDREDS OF ITEMS NOT LISTED ABOVE.**

Send check or money order - include 60¢ to cover parcel post and handling. UPS shipping available. Minimum order \$4.50.

**FREE BONUS WITH EACH \$10.00 ORDER**

**50' SPOOL 600 V. #22 PVC WIRE**

# KRP

## ELECTRONIC SUPERMART, INC.

219 WEST SUNRISE HIGHWAY  
FREEPORT, L. I., N. Y. 11520  
516-623-3346-9

# SPACE SAVER TOWERS & MASTS

CZ series towers, cranks up, installs without guy wires. New lacing design creates greater strength. Mini and Magna rotating masts . . . high strength galvanized tubing, self supporting crank-up.

For complete details and prices please check your local dealer or write  
Certified Welders L.A. City License #634

## CRISTAO TOWER CO.

P. O. Box 115, Hanford, California 93230

## NEW - 440 MHz PREAMPS

**\$54.95**

POSTPAID

432PA-1



Two stage preamps use KMC Bipolar and Mosfet Transistors. 20db gain, 20 MHz bandwidth. These are high quality preamps suitable for the most demanding applications. AC models have die cast case, others have metal enclosure.

432PA 3.5db NF 12VDC	\$29.95
432PA-1 3.5db NF 117VAC	\$54.95
432PC 1.5 to 2.0db NF 12VDC	\$69.95
432PC-1 1.5 to 2.0db NF 117VAC	\$94.95

**JANEL  
LABORATORIES**

P. O. BOX 112  
SUCCASUNNA, N. J. 07876  
201-584-6521



**MODEL "A" Frequency Counter Price \$299.00**  
10Hz to 80 MHz ( $\pm 1$ Hz) Direct Count guaranteed (1Hz to over 100MHz) typical)  
Read Out: 5 LED digits + LED Over Range  
Sensitivity: Less than 100 millivolts over entire range.

Power Req.: Either 120 VAC or 12 VDC 15 watts approx.  
Small Size: 2.34" x 5.68" x 8.18"  
Overload protected input and DC power input.

**MODEL "AS" Frequency Counter Price \$375.00**  
Exactly as above plus an internal 250MHz Scaler ( $\pm 10$ Hz to well over the guaranteed frequency of 250 MHz.) No external power is required.

Shifting DECIMAL POINT gives a DIRECT READOUT of VHF Frequencies.  
One BNC INPUT for both ranges. No cable changing from HF to VHF.

(CA residents add State Sales Tax)  
Dealer inquiries invited



**ELECTRONICS**  
P.O. BOX 1672  
VISTA, CA. 92083  
714-726-1313

DIGITAL:THEORY,DESIGN ,  
CONSTRUCTION

## LOGIC NEWSLETTER<sup>®</sup>

SAMPLE COPY \$ 1.00  
LOGIC NEWSLETTER  
POB 252  
WALDWICK,N.J. 07463

NO ETCH CIRCUIT BOARDS  
FROM FULL SCALE TEMPLATES  
Hardened Chrome Alloy Steel

ISOLATED - PAD - DRILL - MILL

Simple - Fast - Accurate - Safe

Sizes: 0.20", 0.15", 0.10" Dia. with  
replaceable #60 drill \$6.95 ea.

A F STAHLER Co PO BOX 354-H  
CUPERTINO, CALIF. 95014  
Calif. Residents add 5%



## SPACE-AGE TV CAMERA KITS & PLANS



BE A PIONEER IN HOME TELECASTING! Build your own TV CAMERA. Model XT-1A, Series D, \$116.95 pp. Solid State. Step-by-step construction manual. High quality. Connects to any TV without modification. Ideal for home, experimenters, education, industry, etc.

PHONE or WRITE for CATALOG.

DIAL 402-967-3771

Many other kits, parts and plans available including starter kits, focus/drift, coils, vidicon tubes, const. plans, etc.

1301 BROADWAY, N.W. **ATV Research** DAKOTA CITY, NEBR. 68731

## LOW PRICES ON POPULAR COMPONENTS IF FILTERS

- Monolithic crystal filters at 10.7 and 16.9 MHz
- Ceramic filters at 455 kHz

### SEMICONDUCTORS

- VHF power transistors by CTC-Varian
- J and MOS FETS
- Linear ICs — AM/FM IF, Audio PA
- Bipolar — RF and AF popular types

### INDUCTORS

- Molded chokes
- Coil forms — with adjustable cores

### CAPACITORS

- Popular variable types

### QUALITY COMPONENTS

- No seconds or surplus
- Name brands — fully guaranteed
- Spec sheets on request

### GREAT PRICES

- Price breaks at low quantities
- Prices below large mail-order houses

**WRITE FOR CATALOG 173**

## AMTECH

P. O. BOX 624, MARION, IOWA 52302  
(319) 377-7927 or (319) 377-2638



**"DON AND BOB" DISCOUNT PRICES** Plus Full Warranty. Call or write fast quotes. All items new, guaranteed. SBE144 199.95; Midland 13500 2MFM 15W mobile 219.95; 13509 W-T 2W. 209.95; SBE-450TRC, converts 2M-3/4M 149.00; 20% plus off list: Hy-Gain TH6DXX 143.00; Mosley Classic 33 124.00; Ham-M 59.00; TR44 59.95; Belden 8-wire rotor cable 8448 10¢/ft; 8214 RG8 foam coax 17¢/ft; Hy-Gain 400 rotor (230.00L) 179.00; 5COND. rotor cable 19¢/ft; 15% off list Triex, Rohn tower; 3/16" cable clamps 18¢ ea; #15 antenna wire 1.95/C; Motorola HEP170 epoxy diode 2.5A/1000 PIV 29¢, 25.00/100 lot; .001MFD/10KV doorknob (CDE) 1.95; Hammarlund HF50 1.95; Motorola semi-conductor data series 7.50; Sorensen ACR-2000VA AC regulator 150.00; write quote: Swan, Eimac, Drake, Kenwood Ten-Tec; Calrad KW SWR relative power dualmeter bridge, to 150MHz 15.95; all items guaranteed. Free flyer, Prices FOB Houston, include postage with small orders, excess refunded. Madison Electronics, 1508 McKinney, Houston, Texas 77002. 713/224-2668, nite/weekend 713/497-5683.

**SELL:** Every issue of '73 Magazine. All offers considered. John Hill, W4WXJ, 2885 Lyncrest Drive, Nashville, Tn. 37214, 615-883-2163.

**FIGHT TVI** with the RSO Low Pass Filter. For brochure write: Taylor Communications Manufacturing Company, Box 126, Agincourt, Ontario, Canada. MIS 3B4

**HOME BREWERS:** Stamp brings list of high quality components. CPO Surplus, Box 189, Braintree, Mass. 02184.

**SELL:** G. E. 2 meter progress line desk top base. 60 watts, with preamp, 2 frequency, 3 pair of crystals. Very clean. Best offer over \$75.00. Also TR22, good condition, \$150. Paul S. Smith, WB9JSE, 7723 W. Bender Ave., Milwaukee, Wis. 53218.

**FREE** with the purchase of a new Genave GTX-200 at \$259.95: 18 crystals of your choice. Send cashier's check or money order for same-day shipment. For equally good deals on Drake, Standard, Clegg, Regency, Hallicrafters, Tempo, Kenwood, Midland, Ten-Tec, Galaxy, Hy-Gain, CushCraft, Mosley, Sony, and Hustler, write to Hoosier Electronics, your ham headquarters in the heart of the Midwest. Become one of our many happy and satisfied customers. Write or call today for our low quote and try our individual, personal service. Hoosier Electronics, Inc., R. R. 25, Box 403, Terre Haute, Indiana 47802. (812)-894-2397.

**RESISTORS:** Carbon composition brand new. All standard values stocked. 1/2W 10% 40/\$1.00; 1/4W 10% 30/\$1.00 — 10 resistors per value, please. Minimum order \$5.00. 15W RMS 1C Audio Amplifier — Panasonic. Frequency response 20Hz-100 kHz. 1/2% distortion. Price \$6.95 Postpaid. Pace Electronic Products, Box 161-H, Ontario Center, New York 14520.

**QRP TRANSMATCH,** Vari Q filter, FM crystal logic oscillator kits, Write Peter Meacham Associates, 19 Loretta Road, Waltham, Mass. 02154.

**RECIPROCATING DETECTOR,** write Peter Meacham Associates, 19 Loretta Road, Waltham, Mass. 02154.

**ANEMOMETER** — make your own wind gauge — D.C. motor generator and instructions \$3.00 postpaid. W2GKF, 55 Runnymede Rd., Berkeley Heights, New Jersey 07922.

**SPARE PARTS,** tubes, xfmers, SSB-CW equip., and assy. SASE brings list. P. O. Box 437, North Hollywood 91603.

**TEFLON WIRE** #22 gauge stranded, silver plated. \$1.75/100 ft. Rich Shyer, 625-4 S. Palomares, Pomona, Ca. 91766.

**SWAN 500C,** 117X, 14C, \$425. Triplett Model 221-T, 0-1000VDC, 0-1000ma, Model 420, 0-500VDC, 0-300 ma. \$15 ea. Ballentine 303 400. P. O. Box 1645, Grand Junction, Colo. 81501.


**'THE WHEATON COMMUNITY RADIO AMATEURS (WCRA)** will hold their 12th Annual Mid-Winter Swap and Shop on Sunday, February 10, at the DuPage County Fairgrounds, Wheaton. Hours 8 a.m. to 5 p.m. Tickets \$1.50 advance; \$2.00 at the door. Two buildings again this year and unlimited parking. Bring your own tables. Free coffee and donuts 1:00 to 9:30 a.m. For info and advance tickets contact L. O. Shaw, W9OKI, 433 S. Villa Ave., Villa Park, Ill. 60181. Advance ticket orders must be postmarked no later than February 3, 1974.
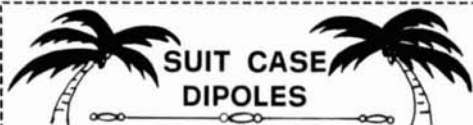
# Drake C-Line



Shipments against our orders placed months ago are arriving daily. No long wait for the world's most popular ham gear.

*SERVING HAMS for 35 YEARS*  
**ELECTRONIC DISTRIBUTORS, INC.**  
1960 Peck Muskegon, MI 49441  
Tel. (616)-726-3196  
HRS. 8:30 - 5:30 SAT. 9 - 4



## SUIT CASE DIPOLES

- #16 stranded copper wire
- Insulated for cleaner, easy handling
- Pretuned and tested guaranteed resonance
- Available 80 thru 10 meters amateur radio bands
- Clips included for portable use allowing same coax to be used for different antennas (small coax only)

**CI10 - \$6.95 CI15 - \$7.95 CI20 - \$9.95**  
**CI40 - \$12.95 CI80 - \$17.95**

RG-58/U & RG-59/U available at \$12.95 per 100 feet.  
Information available or order direct

**CATRONICS INTERNATIONAL**  
P. O. BOX 132 • MIAMI, FLORIDA 33156



## NEW! GLOBALMAN TRANSKEY

**EK-108D**  
with built in monitor  
**\$64.95 ppd.**

Jam-Proof IC Circuitry • 5-50 wpm self completing • Output heavy-duty TR switch 250v. 2 amps • Power: 2 flashlight batteries or external 6VDC

1 year unconditional guarantee — 10 day return privilege

Write for specs & photos. Dealers Wanted

**W6PHA — GLOBAL IMPORT CO.**

714-533-4400 Telex 678496 Box 246, El Toro, Calif. 92630

**TOP  
QUALITY  
!**




**NEW  
LOW  
PRICE**

JUST ARRIVED, ANOTHER SHIPMENT OF BRAND NEW KEYBOARDS. IF YOU MISSED OUT ON OUR LAST OFFERING OF THIS BEAUTIFUL, COMMERCIAL GRADE KEYBOARD, HERE'S YOUR CHANCE TO GET ONE AT THIS NEW LOWER PRICE. IDEAL FOR AUTOMATIC MORSE CODE KEYERS, COMPUTER CONSOLES, AND VIDEO DATA TERMINALS. FROM A LEADING VIDEO TERMINAL MANUFACTURER, WELL MADE WITH THE LOOK AND FEEL OF AN EXPENSIVE ELECTRIC TYPEWRITER. SIXTY FIVE KEYS - SPACE BAR, ALL ALPHABET - 10 NUMERALS - 28 CONTROL KEYS - 1 LOCKING "SHIFT" KEY. DIODE MATRIX FOR ASCII IS EASILY CONVERTED TO USE AS MORSE OR TTY KEYS. ATTRACTIVE SLANTED TIER, TRI-COLOR KEY SCHEME. PREVIOUSLY SOLD FOR \$39.50, NOW - POSTPAID - ONLY \$34.95

**LOW PRICES  
ON POPULAR COMPONENTS**

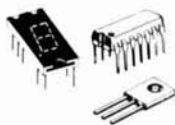TYPE 8038 VCO FUNCTION GENERATOR. SUPERIOR TO THE POPULAR 566. SINE, SQUARE, TRIANGLE GENERATOR. USEABLE FROM .001 HZ TO OVER 1 MHZ. VOLTAGE CONTROL, 1000 to 1. CAN BE USED WITH SINGLE OR DUAL SUPPLY. VARIABLE DUTY CYCLE, SWEEPABLE, EXTERNAL DISTORTION CONTROL. PERFECT FOR USE IN SIGNAL GENERATORS, FM GENERATORS AND PHASE LOCKED LOOPS. W/FULL SPECS.....\$5.75



**TRI-tek, inc.**

P.O. BOX 14206 DEPT H  
PHOENIX, ARIZONA 85063

NEW AND SURPLUS ELECTRONIC COMPONENTS FOR THE PRO AND SERIOUS AMATEUR. AN ORDER OR 8c STAMP PUTS YOU ON OUR MAILING LIST. MINIMUM ORDER \$3.00 U.S., \$15.00 FOREIGN. ALL ORDERS POSTPAID. PLEASE ADD INSURANCE

**NEW MINIATURE CRYSTAL FILTERS — Made U.S.A.**



	Data sent with S.A.S.E. Model WF-4 Model WF-8	
No. Crystals	4	8
Center Freq.	9.0 MHz	9.0 MHz
Band Width at 6db	2.5kHz	2.5kHz
60db/6db Shape	2.0 (45/6)	1.8 max.
Ultimate Rejection	45 db	100 db min.
In/Out Termination	120 Ω	140 Ω
PRICE	\$22.95	\$30.95

Matching Crystals USB (8998.5 kHz) or LSB (9001.5 kHz) \$3.00 each  
Include .75 for postage and handling.

**WHEATLAND ELECTRONICS**  
P. O. BOX 343  
ARKANSAS CITY  
KANSAS 67005

**USED TEST EQUIPMENT**

All checked and operating unless otherwise noted. FOB Monroe. Money back (less shipping) if not satisfied.

Boonton 190A Q-mtr 20-260 MHz Q5-1200	375
Boonton 202B Sig Gen AM-FM 54-216 MHz	310
GR546C Audio Microvolter .5uv-1v	85
GR1302A Audio Osc.-low distortion	125
HP100D-Freq. stand. w/scope-Acc. 1ppm	85
HP185A Scope w/186B amp sampling 1gHz	335
HP330C Dist anal 20 Hz-20kHz .1%	225
HP540B Trans osc. for 524 to 12.4gHz	185
HP608D (TS510A/U) sig. gen. 10-420 MHz	450
Kay 860A Vari-sweep 2-215MHz. cal. attn	175
Nems Clark 1671 FM rcvr 175-260MHz	125
Polarad MSG34-Sig. Gen 4.2-11gHz calib. attn. AM-FM-Pulse mod.	495
Polarad R uwave rcvr .4-84gHz with plug-in AM, FM, CW, Pølse — less plug-in	225
Polarad TSA Spec. Anal .01-44gHz with plug-in — less plug-in	125
Republic VA260 Q-mtr (sim. Boonton 160A)	185
Solitron 200A SCR tester-checks anode, gate volts current, leakage and holding	165
Stoddart NM10A (URM-6) RF intens mtr 10-250 kHz, complete with acc.	630
Stoddart NM20A (PRM-1) RF intens mtr .15-25MHz, complete with acc.	825
Stoddart NM52A-RFI mtr. .375-1gHz, w/ acc.	985
Tek RM 15-DC-15MHz GP scope	265
Tek 181 Time mark generator	95
Tek 190A Const. Ampl. Sig. Gen .35-50MHz	125
Tek 531 DC-15MHz scope-takes letter plug-in	175
FR6/U Freq. mtr .001% acc 100-500MHz	145
SG24/TRM3 Sweep Gen. 15-400 MHz, CW, AM, FM Xtal markers, scope-Dev. to 20%	245
TS-403A-Sig. Gen. (HP616) 1.8-4gHz	385
URM 7 RI-FI mtr (sim. NF-105) 20-400MHz	750

(Send SASE for complete list)

**GRAY Electronics**  
P. O. Box 941, Monroe, MI 48161  
Specializing in used test equipment

**WANTS TO BUY**

All types of military electronics equipment and parts. Call collect for cash offer.

**SPACE ELECTRONICS division of  
MILITARY ELECTRONICS CORP.**

76 Brookside Drive, Upper Saddle River  
New Jersey 07458 • (201) 327-7640

**THE ULTIMATE MORSE KEYBOARD**

- 64 character buffer
- Standard typewriter format with space
- Compatible with KM-420 memory

Available 1 November Model #KB-4200  
Write for specifications \$499.95

**GURTS ELECTRO DEVICES** BOX 4090 • MOUNTAIN VIEW, CALIF. 94040 • TEL. (415) 964-3136



KM-420 CW MESSAGE MEMORY 100 CHR 200 CHARACTER \$299.95 Write for brochures EK-420 MORSE DELUXE KEYSER 47 CHRS \$199.95

**GURTS ELECTRO DEVICES** TEL. (415) 964-3136 NEW FOR 1973 INC., BOX 4090, MOUNTAIN VIEW, CA 94040

"HOSS TRADER Ed Moory" says he will not be undersold on cash deals! Shop around for your best price and then call or write the "HOSS" before you buy! New Galaxy GT-550A Transceiver with supply and microphone, package \$599.00: New Drake TR-22, reg. \$219.95, cash \$175.00: New Swan 270B, \$375.00: New Collins in stock: New Rohn 50 ft. heavy-duty foldover tower, prepaid \$255.00: New Mosley CL-33 and demo Ham-M rotor, \$215.00: Used equipment: R4-C, \$399.00: T4-XC, \$425.00: R4-B, \$309.00: Ham-M, \$85.00: Nice KWM-2, \$549.00: FPM-300, \$489.00: Used TR-4C, \$449.00. Moory Electronics Company, P. O. Box 506, DeWitt, Arkansas 72042. Tel: 501-946-2820.

**QSL'S — BROWNIE W3CJI** — 3111B Lehigh, Allentown, Pa. 18103. Samples 10c. Cut catalogue 25c.

**SURPLUS TEST EQUIPMENT, VHF and microwave gear;** write for bulletins. David Edsall, 2843 St. Paul, Baltimore, Md. 21218.

5939's, 6360's, Guaranteed good, \$2.50 each. Jack W6TNR, 15718 Mayall, Sepulveda, Calif. 91340.

**STOLEN EQUIPMENT** — Standard Model SRC-146A FM transceiver in leather case, serial 208070, was stolen from aircraft at Los Angeles International Airport on October 5, 1973. Contact: Lt. W. L. Robinson, SLPD, Chief Security, Salt Lake City International. Phone (801) 328-7652 or P. O. AMF Box 22084, Salt Lake City, Utah 84122.

**DO-IT-URSELF DXPEDITION** — Stay at ZF15B — Cayman Is. Vertical antenna and Caribbean at your doorstep. Diving/fishing if band funds. We arrange license. Write Spanish Bay Reef Resort, Box 800K, Grand Cayman, B. W. I.

**DIGITAL** frequency display for your receiver and transmitter. Detailed plans \$3.00. Communications Electronics Specialties, 814 Orwell Ave., Orlando, Fla. 32809.

**TELETYPewriter PARTS,** gears, manuals, supplies, tape, toroids. SASE list. Typetronics, Box 8873, Ft. Lauderdale, Fl. 33310. Buy parts, late machines.

**KLM AND MADISON ELECTRONICS** present the best in VHF-UHF antennas. 143.5-148.5 MHz 7EL 21.95 up to 16EL. 49.95 — Write specifications. 220MHz: 432MHz 27EL. 41.95; write for quotes, prices FOB Calif. or Houston. Madison Electronics, 1508 Mc Kinney, Houston, Texas 77002. 713/224-2668, nite/weekend 713/497-5683.

**PRECISION HAND TOOLS,** special ham-experimenter discount. Letter brings mailings. Artisan Tool Company, Box 36, Glenmont, New York 12077.

**WANT OLD RADIO SHOW TRANSCRIPTION** discs. Any size or speed. Send details to, Larry Kiner, W7FIZ, 7554 132nd Ave. N.E., Kirkland, Wa. 98033.

**CANADIAN JUMBO SURPLUS** and Parts Catalogs. Bargains Galore. Send \$1. ETCO-HR, Box 741, Montreal "A" H3c 2V2.

**WANTED:** tubes, transistors, equipment, what have you? Bernard Goldstein, W2MNP, Box 257, Canal Station, New York, N. Y. 10013.

**REMOTE CONTROLS** for mobile installations. I have several brand new Hartman remotes, complete with 18 ft. cable, Shure mic., mtg. bracket. All units are boxed and never used. \$24.95 including postage to M. Cohen, 45 Pennington Way., Spring Valley, N. Y. 10977.

**NEED PARTS?** We carry parts for R-388-390-390A-391-392-1051-51S1 - Nems Clark-Racal-Pack sets - PRC-25-41-47-62-70-71-73-74-77. If you need a part no matter what you have. If its U.S. government we have it or can get it. Also we want to buy or trade all aircraft communications. All ground radio communications. All plug-in modules control heads. No matter what cond. they are in - bent or busted ok. We will buy or trade. We have R-390-388-390A-392-1051-51S1 Nems Clark - Racal - and new ham gear for trade. D & R Electronics, R. D. #1, Box 56, Milton, Pa. 17847. Phone 1-717-742-4604 after 6:00 P.M.

**STANDARD 146-A** still in factory carton with warranty card. \$238.70. W4OQAQ, Box 17222, Nashville, Tenn. 37217, (615-834-8999).

## ECM-5 FM Modulation Meter

Only \$75.00

less batteries and crystal

- Operates 30-500 MHz
- Crystal controlled for fast and easy operation
- Peak reading
- Battery powered with AA pencils
- All solid state
- Built-in antenna
- Quality constructed with G-10 p.c. boards



Phone or write "Skip" W9HAK

for complete information

Dial 812-476-2121

Available by direct mail only. ORDER INFO: Send check or money order for \$75.00 plus \$1.00 for handling. Indiana residents add 4% sales tax. Crystals for 146.94 MHz \$3.95 ea. All other freqs. \$7.10

# ECM

ECM Corporation  
Dept. E  
412 N. Strubach Ave.  
Evansville, Indiana 47711

## FREE Catalog

OF THE WORLD'S FINEST  
GOVERNMENT SURPLUS  
ELECTRONIC EQUIPMENT



SPECIAL OFFER  
LIMITED SUPPLY



### RG-8A/U COAXIAL CABLE

52 ohm. Two (2) PL-259 Coaxial Connectors included. Used, Good Condition: 68 Ft. Length \$5.50 — 50 Ft. Length \$4.50 — 25 Ft. Length \$2.50

### RG-54A/U COAXIAL CABLE

58 ohm .250 O.D. Polyethylene. Unused. 370 Foot Roll \$10.00 — 185 Foot Roll \$6.00

Prices are F.O.B., Lima, Ohio • Order Dept. HR  
SEND TODAY FOR BIG FREE CATALOG

## FAIR RADIO SALES

1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

LOWER  
PRICES

AC1

Two models



TIME  
TELLER

DX Operating Aid

MC1

A turn of knob and 2-color drum dial shows time your QTH and corresponding local time in all zones . . . also GMT. Both models feature 2-color map panel of enamel on aluminum 9" in length.

MODEL

AMATEUR NET

MC1 Unfinished mahogany cabinet \$9.90

AC1 Polished acrylic cabinet 14.75

Add \$1.25 for mailing cost

U-J  
Industries

6605 Shoal Creek Blvd.  
Austin, Texas 78757

## SB-144 2 meter FM TRANSCEIVER



12 CHANNEL 10 WATT 2 METER  
FM TRANSCEIVER COMPLETE  
WITH 3 SETS CRYSTALS  
MICROPHONE, MTG. BRACKET

List 259.95 Your Cost 199.95 FOB Houston

MADISON ELECTRONICS SUPPLY  
1508 MCKINNEY AVE. • HOUSTON, TEXAS  
713/224-2668

## — PCB KITS —

RTTY SPEED CONVERTER Drilled PCB 5 & 11 VDC \$40.00  
DRILLED PCB ONLY \$ 6.00  
RTTY AFSK Gen. All Shifts & CW I.C. 9 VDC @ 2ma \$6.60  
100 KHZ XTAL CALIBRATOR Less Xtal 9 VDC @ 2ma \$4.75  
POWER SUPPLY — 28 VDC @ 650 ma output \$8.95  
PREAMP MICROPHONE, 26 DB Gain 9 VDC @ 1ma \$3.50  
LIMITER PREAMP For High Z Mike 9 VDC @ 1ma \$4.80  
PRODUCT DETECTOR For Your Receiver 9 VDC @ 1ma \$3.60  
"S" METER KIT Less 1ma Meter 6.3VAC \$4.75  
SWR METER, Stripline, Less 200µa Meter \$2.95  
VWV CONVERTER 3.5-4.0 MHz Output 9 VDC @ 5ma \$5.25  
Requires 6-6.5MHz Crystal  
6 METER CONVERTER FET Front End 9 VDC @ 5ma \$5.95  
7-11 MHz Output, Less 43 MHz Xtal \$4.70  
CW KEYING MONITOR, RF Keyed, Less Spkr. 9 VDC @ 9ma \$4.70  
POWER SUPPLY - 9 VDC @ 50ma Output 115VAC \$4.85  
6 OR 2 METER CASCODE PREAMP 80 VDC @ 4.5ma \$4.95  
Wired & Tested Less 2 ea 6CW4  
Nuvistors. Specify 6 or 2 Meter Model  
DRILLS, #54, 56, 58 or 60 (each) \$ .40  
Finest Quality for PCB'S, Made in USA Three For \$1.00

EXCEPT AS NOTED ABOVE, ALL KITS ARE NEW, 100% SOLID STATE. AND COME COMPLETE WITH AN UNDRILLED G-10 PCB (PRINTED CIRCUIT BOARD) AND ALL PCB MOUNTED COMPONENTS. KITS ARE LESS POWER SUPPLIES, CHASSIS, AND ENCLOSURE HARDWARE. SEND SELF-ADDRESSED, STAMPED ENVELOPE FOR COMPLETE DATA SHEET AND SCHEMATIC.

SATISFACTION GUARANTEED. RETURN IN 30 DAYS FOR REFUND. ALL KITS POSTPAID. INCLUDE 25¢ HANDLING CHARGE. WASHINGTON RESIDENTS ADD 5.3% SALES TAX.

## P. M. ELECTRONICS INC.

519 SOUTH AUSTIN, SEATTLE, WASH. 98108

## DUAL BAND ANTENNAS

These ready to mount antennas consist of full  $\frac{1}{2}$  wavelength elements of No. 12 copperweld wire and can be used as either dipoles or inverted vees. No traps, coils, gimmicks, etc. are used to shorten the elements. 2KW rating. Single coax feedline required. Individually mounted dipoles with common center insulator: 80/40, \$21.95; 40/20, \$16.25; 20/15, \$14.10. Other combinations available. Send for free catalog listing dual band, monoband, and folded dipole antennas. Baluns available. Postpaid continental U. S. A.

## HOUSE OF DIPOLES

P. O. BOX 8484  
ORLANDO, FLORIDA 32806



Your HAM RADIO Magazine collection is valuable and it deserves the organization and protection our handsome rugged binders can provide.

Each binder cover comes complete with date labels to properly identify each year's issues.

BINDERS \$4.50 each  
or 3 for \$12.00 ppd

order today

**ham  
radio** magazine

Greenville, NH 03048

## BRITISH READERS

You may now purchase Ham  
Radio Binders directly from

RADIO SOCIETY OF GREAT BRITAIN  
35 DOUGHTY STREET  
LONDON WC1N 2AE

£1.40 each

The voice of



*is heard around the world*



## Here's why Thunderbirds outperform all other tri-banders:



- **Thunderbird's "Hy-Q" traps** provide separate traps for each band. "Hy-Q" traps are electronically tuned at the factory to perform better at any frequency in the band—either phone or CW. **And** you can tune the antenna, using charts supplied in the manual, to **substantially** outperform any other antennas made.

- **Thunderbird's superior construction** includes a new, cast aluminum, tilt-head universal boom-to-mast bracket that accommodates masts from 1 1/4" x 2 1/2". Allows easy tilting for installation, maintenance and tuning and provides mast feed-thru for beam stacking.

Taper swaged, slotted tubing on all elements allows easy adjustment and readjustment. Taper swaged to permit larger diameter tubing where it counts! And less wind loading. Full circumference compression clamps are mechanically and electrically superior to self-tapping metal screws.

- **Thunderbird's exclusive Beta Match** achieves balanced input, optimum matching on all 3 bands and provides DC ground to eliminate precipitation static.

- 25 db front-to-back ratio.

- SWR less than 1.5 to 1 on all bands.

- 24-foot boom...none longer in the industry.

- Extra heavy gauge, machine formed, element to boom brackets, with plastic sleeves used only for insulation. Bracket design allows full mechanical support.

- Interlaced, optimum spaced elements for higher gain and better pattern control.

- 3 active elements on 20 and 15 meters. 4 active elements on 10 meters.

**New 6-Element Super Thunderbird**  
Model 389

Suggested retail price, **\$189.95**

**Improved 3-Element Thunderbird**  
Model 388

Suggested retail price, **\$154.95**

**Fabulous 3-Element Thunderbird, Jr.**  
Model 221

Suggested retail price, **\$109.95**

**Popular 2-Element Thunderbird**  
Model 390

Suggested retail price, **\$99.95**

**hy-gain**

**ELECTRONICS CORPORATION**

Dept. BA, 8601 Northeast Highway Six, Lincoln, NE 68507  
402/464-9151 Telex 48-6424

Distributed in Canada by LECTRON RADIO SALES, LTD. 211 Hunter Street West, Peterborough, Ontario

**SBE**

# "CRUNCHER"

turns mild mannered 2 meter mobile FM transceivers into 70-90 watt roaring tigers!



SEND FOR DETAILED BROCHURE

**SBE**

LINEAR SYSTEMS, INC. 220 Airport Boulevard, Watsonville, CA 95076

**SB-1PA**, Class C amplifier, connects between FM transceiver and antenna and to car battery — **boosts output power approximately 10 times** (i.e., 7W in, 70W out, etc.) And broad band — covers 143-149 MHz.

Small — less than 1/10 cu/ft. — rugged cast housing readily mounted in car. Built-in antenna relay operates from rectified RF. All solid state using highest commercial quality **CTC** transistors — not surplus culls. Long-life — minimum drain.

AK-1 BOARD ONLY	\$ 3.25
AK-1 KIT OF ELECTRONIC PARTS	\$ 20.00
ST-5 BOARDS ONLY	\$ 5.25
ST-5 KIT OF ELECTRONIC PARTS	\$ 47.50
ST-5A BOARDS ONLY	\$ 5.25
ST-5A KIT OF ELECTRONIC PARTS	\$ 54.00
ST-6 BOARDS ONLY (These are the 8 original by W6FFC)	\$ 18.00
ST-6 KIT OF ELECTRONIC PARTS	\$128.50
MOD. KIT FOR UPDATING THE ST-5 TO THE ST5A	\$ 9.00
PEMCO 250 EIGHT DIGIT COUNTER WITH BUILT-IN PRE-SCALER AND POWER SUPPLY SEMI KIT	\$165.00
PEMCO MODEL 50A FREQUENCY COUNTER SEMI-KIT	\$125.00

These are fully assembled and tested boards only, you add your own cabinet, etc. Write for details.

You must supply the cabinet, A.C. cord, meter, switches, etc. on all kits except where noted otherwise. (All prices are postage paid (we pay shipping).)

We will do most any printed circuit board for individuals or prototypes. If required we will also do the layout of the boards. All our boards are G-10 glass-epoxy solder plated and come drilled only. At present time we can do only single sided. All component parts used in our kits are new manufacturers stock. We Do Not Use Any Used or Surplus Parts. All inquiries are answered promptly.

**PEMCO** ELECTRONICS MANUFACTURING  
422 18th St., N.E., Salem, Ore. 97301, (503) 585-1641

WE PAY **HIGHEST**  
PRICES FOR ELECTRON  
TUBES AND SEMICONDUCTORS

**H & L ASSOCIATES**

ELIZABETHPORT INDUSTRIAL PARK  
ELIZABETH, NEW JERSEY 07206  
(201) 351-4200

**SWAN**

**EAST COAST SERVICE CENTER**

We also service all other popular makes.


Complete professionally staffed laboratory fully equipped for all aspects of maintenance and service. Graduate Engineer on duty. Custom Design services available.

**PROFESSIONAL ELECTRONICS CO., INC.**  
1710 JOAN AVE. EUDOWOOD BRANCH  
BALTIMORE, MD. 21204  
301-661-2123

DON'T MISS  
**HR REPORT**  
PAGE 88

## COMPUTER KEYBOARD

\$7.00 (as is)

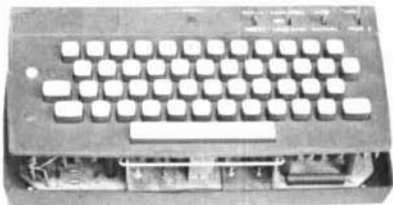

Several styles on hand in poor condition, broken key/keys, broken case or no case, etc. Still a good value at \$7.00 for parts, switches, and each has encoder board in base.

2N2152	45 volt	170 watt	PNP-G	\$1.00
*2N3713	80	150	NPN-S	1.00
*2N3773	160	150	NPN-S	.75
*2N3789	60	150	PNP-S	.75
*2N5301	40	200	NPN-S	1.25
*2N5301	40	200	NPN-S	1.00

\*Removed from used equipment

## TRANSFORMERS

BRAND NEW, 115 volt AC input, OP - AMP XFMR, out puts: 16 VCT 1/2 amp, 17 VCT 1/2 amp. \$3.50

## FILAMENT or BTRY CHARGER XFMR

output of 18 volts at 4.5 amp \$3.50



## CALCULATOR KEYBOARD

Brand new keyboards for hand held calculators. Two styles available.

One for use with calculator chip CAL TEX 5001-5002-5012 or MOSTEK 5010-5012. Another for use with Gen. Inst. chip C500. Priced at \$8.00 each or two for \$15.00.



## CT 5005 CALCULATOR CHIP

Single MOS chip with all logic required for 12 digit 4 function desk top calculator with extra storage register for memory or constant. Multiplexed 7 segment outputs for LED, Incandescent, Fluorescent, or Gas Discharge displays. Brand new, bargain priced, with specs. \$8.00 each, 2 for \$15.00



## HP LED DISPLAYS

Brand new 4-on-a-strip LED readouts. End-butts two strips and come up with 8 digit readout. An unheard of Super Value . . . \$8.00 per strip, 2 strips \$15.00

Another strip . . . this one a Clock Chip readout. 2 digits . . . a space . . . and 2 more digits. Just right for a clock reading hours and minutes. This one only \$8.00

JOHN MESHNA JR. ELECTRONICS

## 313,344 CORE MEMORY \$125.00

From SPECTRA computer, visually OK. 64 x 68 x 4 x 18 core stack. Figures out to 35K Byte.

## LED 7

## SEGMENT READOUT



Similar to MAN-1. Factory seconds but functionally OK. Fit 14 pin DIP socket.

7 segment w/left decimal	#LED-A-L	\$3.00
7 segment w/right decimal	#LED-A-R	3.25
7 segment no decimal	#LED-A	2.75

Above LEDs—7 for the price of 5  
Socket for above, gold plated leads 3/1.00

## IC SALE YOUR CHOICE 3 for \$1.00

µl 900 BUFFER TO-5		
µl 914 DUAL 2 INPUT GATE TO-5		
µl 923 JK FLIP FLOP TO-5		
µl 926 Hi speed JK FLIP FLOP TO-5		
µl 931 JK/RS FLIP FLOP (DIP)		
10 pin socket for TO-5 IC		3/1.00

## GIANT NIXIE B7971

Used \$1.00 Brand New \$2.00  
With schematic for GIANT clock.

## COMPUTER TAPE DECK \$75.00

Takes 1/2 inch tape, made by Computer Entry Systems. Visually ok, with electronics, no data available.

LASER DIODES, new listing just arrived, send SAE.

## CMOS 4814 HEX INVERTER

CMOS HEX INVERTER, dual inline package. 3-18 volt range, dual diode protection against static charge. Dielectrically isolated complimentary MOS. \$1.00 each 12 for \$10.00

## DUAL 16 BIT MEMORY

Dual 16 bit memory, serial MOS by Philco TO-5 case, brand new with 2 page specs.

#PLR 532 \$1.00 each \$10/12

## 2048 BIT MOS MEMORY

2048 bit MOS LSI random access memory NEC 6003. All inputs except clock are TTL compatible. 2048 word by 1 bit. 22 pin ceramic dual-in-line. With specs.

\$9.00 each 2 for \$17.00

## ASCII KEYBOARDS LIKE NEW \$45.00

From Raytheon, with encoder board in base, output on blue ribbon connector. This is the same keyboard we sell at \$50 except this one has no case. 5 extra function buttons each side. Price includes shipping world wide.



Postage Extra on all Items

P. O. Box 62 E. Lynn, Mass. 01904

# Advertisers check-off

... for literature, in a hurry — we'll rush your name to the companies whose names you "check-off"

## INDEX

—Amtech 006	—Logic 133
—Andy 007	—MEJ 082
—Babylon 014	—Madison 083
—Barry 016	—Matic 084
—Catronics 189	—McClaren 155
—Communications Specialists 030	—Meshna 085
—Curtis 034	—Modar 195
—Cush Craft 035	—Mor-Gain 089
—Data 037	—Nurmi 090
—Drake 039	—PM 091
—Dynamic Electronics 041	—Palomar 093
—ECM 190	—Pemco 095
—EICO 194	—Poly Paks 096
—Eimac 043	—Pro. Elect. 140
—Electronic Dist. 044	—RP 098
—Epsilon 046	—Radiation 099
—Exceltronics 139	—Callbook 100
—Fair 048	—Regency 102
—G & G 051	—Savoy 105
—Gateway 052	—Space-Military 107
—Global 053	—Spectronics, FM 191
—Goldstein's 130	—Spectrum 108
—Gray 055	—Stahler 142
—Great American 132	—Star-Tronics 110
—H & L 056	—Swan 111
—HAL 057	—Teletron 188
—Ham Radio 150	—Ten-Tec 114
—Heath 060	—Topeka FM 115
—Henry 062	—Tristao 118
—House of Dipoles 036	—Tri-Tek 117
—Hy-Gain 064	—UJ 119
—Icom 065	—VHF Communication 129
—International Crystal 066	—VHF Engineering 103
—International Elect. Unltd 141	—Venus 192
—Jan 067	—Vintage 131
—Janel 068	—Weinschenker 122
—K. E. 072	—Wheatlands 156
—KRP 074	—Wilson 123
—Larsen 078	—Wolf 124
—Leland 193	—World QSL 125
—Linear 081	—World Wide Antennas 196
	—Y & C 126
	—Yaesu 127

Limit 15 inquiries per request.

## January 1974

Please use before February 28, 1974

Tear off and mail to  
**HAM RADIO MAGAZINE — "check off"**  
Greenville, N. H. 03048

NAME.....

CALL.....

STREET.....

CITY.....

STATE..... ZIP.....

# Advertisers iNdex

ATV Research .....	102
Amtech .....	102
Andy Electronics .....	84
Babylon Electronics .....	82
Barry .....	111, 112
Catronics .....	103
Communications Specialists .....	92
Curtis Electro Devices .....	104
Cush Craft .....	75
Data Engineering .....	89
Drake Co., R. L. .....	2
Dynamic Electronics .....	86
ECM Corporation .....	105
Eimac, Div. of Varian Assoc. .....	Cover IV
Electronic Distributors, Inc. .....	103
Epsilon Records .....	86
Exceltronics Research Labs .....	92
Fair Radio Sales .....	105
G & G Radio Supply Co. .....	74
Gateway Electronics .....	96
Global Import Co. .....	103
Goldstein's .....	96
Goodheart Co., Inc. R. E. .....	96
Gray Electronics .....	104
Great American Miniatures .....	82
H & L Associates .....	108
HAL Communications Corp. .....	91
Ham Radio .....	80, 88, 90, 106, 108
Heath Company .....	13
Henry Radio Stores .....	Cover III
House of Dipoles .....	106
Hy-Gain Electronics Corp. .....	56, 57, 87, 107
Icom .....	85
International Crystal Mfg. Co. Inc. .....	61
International Electronics Unlimited .....	98
Jan Crystals .....	76
Janel Labs .....	102
K. E. Electronics .....	86
KRP Electronic Supermart, Inc. .....	101
Larsen Electronics .....	65
Leland Associates .....	96
Linear Systems, Inc. .....	108
Logic Newsletter .....	102
MFJ Enterprises .....	74
Madison Electronic Supply .....	92, 106
Matic .....	84
McClaren .....	84
Media Selection Network .....	94, 95
Meshna, John, Jr. .....	109
Mor-Gain, Inc. .....	96
Nurmi Electronic Supply .....	77
PM Electronics .....	106
Palomar Engineers .....	72
Pemco .....	108
Poly Paks .....	93
Professional Electronics .....	108
RP Electronics .....	86
Radio Amateur Callbook, Inc. .....	100
Regency Electronics, Inc. .....	97
Savoy Electronics .....	Cover II
Space-Military Electronics .....	104
Spectronics, FM .....	78, 79
Spectrum International .....	84
Stahler Co. A. F. .....	102
Star-Tronics .....	96
Swan Electronics .....	45
Teletron Corp. .....	71
Ten-Tec, Inc. .....	5
Topeka FM Communications & Electronics .....	76
Tristao Tower Co. .....	102
Tri-Tek, Inc. .....	104
UJ Industries .....	105
VHF Communication .....	72
VHF Engineering, Div. of Brownian Elect. Corp. .....	81
Venus Scientific .....	1
Vintage Radio .....	82
Weinschenker, M. .....	73
Wheatlands Electronics .....	104
Wilson Electronics .....	86
Wolf, S. .....	92
World QSL Bureau .....	86
Y & C Electronics .....	102
Yaesu Musen USA .....	83



# BARRY

presents

## CLEGG FM-27B



Total 146-148 MHz coverage without buying a crystal. 25w. out, fully synthesized.

**\$479.95**

Clegg FM-27B Regulated AC power supply  
**\$79.95**

### DYCOMM

DYCOMM BRICK, 2w in 35w out ..... \$ 79.95  
DYCOMM BLOCK, 10 in 50w out ..... \$ 99.95

### DRAKE

R4B Receiver ..... xInt. \$295.00  
W/xtr xtals ..... mint \$325.00  
AA-10 Amplifier for TR-22 ..... \$ 49.95  
AC-10 AC Supply for AA-10, TR-22, TR-72, 13.8 VDC @ 3 amps ..... \$ 39.95  
TR-22, in stock ..... \$189.00  
TR-72 2 meter FM transceiver, 23 channel, 1 & 10 watts, 13.8 VDC ..... \$320.00  
TR4/C new, \$599.95 T-4XC Trans. \$530.00  
R4C Rec. \$499.95 MS-4 Speaker \$22.00  
AC-4 Drake A.C. Power Supply ..... \$ 99.95

### BIRD 43 WATTMETER

**\$100.00**

Bird 43 Slugs specify frequency and power

HF ..... \$35.00 each  
VHF ..... \$32.00 each

Also 4350 80-10M dual scale 200w/2kw HamMate — \$79.00

### HALLICRAFTERS

SR-160 Transceiver 80, 40, 20 meters ..... write  
FPM-300 ..... new, \$595.00

### TEMPO

2 Meter Linear Amplifiers, 502, 5-12 watts input, 35-55 watts output ..... \$105.00  
802-B 1-2 1/2 w. input, 80-90 w. output ..... \$195.00  
CL-146 2 Meter, 15 watts ..... \$299.00

**SWR BRIDGE COUPLER, DC-800 MHz**  
TNC Connectors  
(no indicator) full amateur power  
\$90.00 Value  
**\$10.95**

### ETO

ALPHA-77. The finest amplifier ever offered for amateur, commercial or military service. 3000 watts PEP continuous duty. Write

Signal/One CX7A ..... Write or Call  
Complete Maintenance Manual for Signal/One CX-7 & CX-7A ..... \$ 25.00

### MARINE

Barry stocks and has fast availability Sonar, Pearce-Simpson, Andrea, SBE and Antenna Specialists VHF Transceivers, Antennas, Depth Finders and compasses by Andrea.

Pay us a visit when you are in New York  
Thousands of unadvertised specials.

Separate export department to expedite overseas orders.

### E. F. JOHNSON

Matchbox complete with directional coupler and indicator, 10-80 meters.

2KW PEP, 1 KW AM — new, Write  
275 watts — new, Write

151-1-4 Variable Capacitor, 250 pF, medium Xmitting type ..... \$5.95 ea.

### GE INDUSTRIAL SILICON RECTIFIER

**1400 PIV**

250 amp., GE #41A281049-11. Quantities in stock. \$90.00 value, brand new ..... \$15.00

### SWAN

SS-200 Solid State SSB Transceiver with power supply & 16 pole filter ..... Brand new, Write

### TEN TEC

TRITON II 5 Band Solid State Transceiver 200 W pep R.I.T. ..... \$606.00  
AC Power Supply 252 ..... \$ 89.00  
315 RECEIVER 10-80 meters SSB, AM, CW ..... \$229.00  
CW FILTER FOR 315 ..... \$14.95  
AC4 SWR Bridge ..... KR2 \$ 12.95  
\$ 14.95 ..... KR40 \$ 89.95

### INSTRUMENTS

Millen 2kw matchbox: ..... Write  
Millen 90652 Solid State Dipper. New with 7 coils and carrying case. 1.6 - 300 MHz \$110.00  
PAN ADAPTER BC-1031A ± 100 kc unused with spare parts & book useful with any short wave receiver ..... \$ 55.00

### VIBROPLEX

Vibro Keyer ..... Standard \$ 24.95  
Deluxe \$ 32.95  
Original Standard Vibroplex Bug ..... \$ 29.95

**BARRY** 512 Broadway NY, NY 10012  
DEPT. H-1  
212-WA-5-7000 **ELECTRONICS**  
TELEX 12-7670

**STANDARD**

SRC-146A 2 meter handheld transceiver \$289.00

**MISC.**

Collins Radio, 152J-1 Phone Patch & Station Control. Circuitry similar to 312B-4, xtInt condition, with schematic \$ 24.95  
 Scamatic HighBand 8 channel scanner Write TMC - 0-330 B/FR 2 to 6 MHz VFO Exciter, New Condition, Deluxe Quality, Write U.S. Callbooks \$ 9.95  
 DX Callbooks \$ 8.95  
 Radio Handbooks latest 19th edition \$ 14.95  
 Lafayette Telsat-SSB 25, Sideband CB Rig \$195.00  
 NPC Power Supply, input 115 VAC — 12 VDC out at 4 amp REGULATED at \$ 34.95  
 Millen magnetic shields for 3" C.R. scope tubes with brackets Brand new \$ 6.95  
 TP-9 Similar to EE-8 field telephone with built-in amplifier. Up to 50 mi. Less easily obtained batteries Brand New \$ 75.00  
 115 Volt AC Power Supply for BC-221, slips into battery compartment. Also can be used with LM freq. meters \$ 29.50  
 ALUMINUM DIE CAST BOXES in many different sizes. Dossy boxes. Details in New Green Sheet No. 23. Write for latest prices.  
 2 METER VHF DUMMY LOAD/WATTMETER Good up to 15 watts — w/SO-239 CONNECTOR and 3" METER \$ 15.95  
 Original J-38 Key new, \$ 12.50



Jackson G80 brass 50:1 anti-backlash dial drive 1/4" to 1/4". \$19.00 value \$ 5.50

**INOUE IC-22****2 Meter Transceiver**

10 WATTS OUTPUT PLUS TREMENDOUS RECEIVER — 22 CHANNELS

Ready to go with crystals for 5 frequencies at no extra charge

**\$289.00**

Many Inoue Crystals In Stock.

Inoue IC-230 synthesized, no crystals to buy. 2 meter transceiver **\$489.00**

IC-3PA Power Supply, Deluxe Regulated for IC-22 or IC-230 **\$99.00**

**BARKER & WILLIAMSON**

Little Dipper, GDO \$ 94.50  
 Dummy Load - Wattmeters - 52Ω  
 333 DC-300 MHz, 5, 50, 125 or 250 watts int. \$ 79.95  
 334A DC-300 MHz, 1000 watts \$139.95  
 374 DC-300 MHz, 1500 watts int. \$169.95  
 850A, 852 Inductors \$ 59.95  
 851 Inductor \$ 29.95  
 425 Low Pass Filter, 10-80 meters 1 kw \$ 24.95  
 210 Audio Osc., ideal for lab & broadcast \$329.95  
 410 Distortion Meter, ideal for lab & broadcast \$369.95

**DX ENGINEERING****SPEECH COMPRESSORS**

DIRECT PLUG-IN FOR COLLINS 32S \$79.50 ppd. U.S.A.  
 DIRECT PLUG-IN FOR KWM-2 \$79.50 ppd. U.S.A.

**BARRY HAS NEW VENUS SS2  
 SLOW SCAN MONITOR IN STOCK \$349.00  
 COME TAKE A LOOK OR WRITE**

**INVERTER/CONVERTER:**

INVERTER, 12 volt DC input, 115 volt AC out, Model 12-115 solid state power supply, 200 watts continuous new, \$ 59.95

**SBE**

SBE-450 TRC, use with 10 watt, 2 meter transceiver to operate on 450 MHz \$195.00

**BARRY HAS ANTENNAS**

C.D. HAM "M" ROTATORS, new complete \$99.95  
 CD Ham-M for 220 VAC in stock \$175.00  
 C.D. TR-44 ROTATORS, new (complete) \$ 63.95  
 CABLE for Ham-M & TR-44 @ 14¢/ft.  
 CD AR-22R cmplt. rotator for small beams \$33.95  
 BN86 Balun by HyGain \$ 14.95  
 RG-8A/U 100 ft. rolls. VHF connector PL-259 one end Type "N" (UG-21E/U) other end \$ 12.50  
 RG8A/U — 65 feet with PL-259 connectors on each end \$ 9.50  
 Times Wire & Cable, T-4-50 (FM-8) 50 ohm lowest loss type RG-8 cable 20¢/ft.  
 Columbia Superflex, RG-8/U 50 ohm high quality foam 20¢/ft.  
 Coaxial adapter for VHF to RG-17 (Amphenol 83-86) RG-17 plug to VHF female connector \$ 6.95  
 BNC to RG-17 adapter UG-167C/U \$ 7.95  
 B & W Vacationer apartment house antenna, 2, 6, 10, 15 & 20 meters. Hang out your window. Take along on your vacation \$ 24.95  
 Authorized factory dealers for Antenna Specialists, CushCraft, Gam, Heights Towers, Hy Gain, Mor-Gain Antenna, Mosley, Newtronics, Tri-Ex, Rohn, E-Z Way, Times Wire, Telrex.  
 Cush-Craft Trick Stick, universal dipole, 2 to 10 meters, 1.5 dB gain at 146 MHz \$ 8.95  
 English deluxe balun, low power \$ 9.95  
 RINGO AR-2 3.75 dB gain, 135-175 MHz \$ 14.50  
 BBLT-144 Trunk Lip, 3.75 dB gain \$ 34.95  
 Newtronics CGT-144 mobile 5.2 dB gain \$37.95  
 Quick Disconnect by Newtronics for CGT, etc. \$ 10.95  
 CG-1 Gutter Clip by Newtronics \$ 1.25  
 2M MAGNETIC MOUNT w/RG58 & PL259 with 10 ft. RG 58 ready to go \$ 9.95  
 14AVQ/WB VERTICAL \$ 55.00  
 18AVT/WB VERTICAL \$ 79.95  
 HY GAIN 2 METER, 15 ele. beam, demo, \$ 35.00

**TELEX**

610-2 Deluxe Economy 2000 ohm headset with cushions \$ 9.95  
 EN-5 Stereo Headphones \$ 9.95

**LITTLE LULU**

**6 Meter AM Transmitter with VFO  
 12 VDC/115 VAC Power Supply**

Available factory wired or as parts

Write for details

Tube Headquarters. Diversified Stock. Heavy inventory of Eimac tubes, chimneys, sockets, etc. 572B \$ 17.50  
 Barry Now Stocks Bogen, Electrovoice & University. Call or Write.

CASH PAID . . . FAST! For your unused TUBES, Semiconductors, RECEIVERS, VAC. VARIABLES, Test Equipment, ETC. Write or call Now! Barry, W2LN1. We Buy! We ship all over the World.  
 Send for Green Sheet Supplement 23.  
 Send 50¢ postage & handling (refund 1st order).

**BARRY** 512 Broadway NY, NY 10012  
 DEPT. H-1  
 212-WA-5-7000 **ELECTRONICS**  
 TELEX 12-7670

# WHEN YOU BUY KENWOOD ...YOU BUY PRIDE, PLEASURE & PERFORMANCE

Pride in knowing that you own today's ultimate in state-of-the-art technology . . . pleasure in operating a rig whose day in, day out performance will show you why the Kenwood name is world-famous for reliability and value.

Kenwood's superb  
solid state SSB transceiver

## TS-900



... the ultimate transceiver. The promise of the transistor has been fulfilled. Here is the transceiver you will want to own . . . whatever you have now, get ready to trade up. Its important features are far

too numerous to list. Its specifications are superb. The TS-900 is unquestionably the best transceiver of its kind ever offered. The price . . . \$795.00  
PS-900 (AC Supply) \$120.00, the DS-900 \$140.00



## TS-520 Kenwood's go every place ... do everything transceiver

The new TS-520 is the transceiver you have wanted, but could not buy until now. It is a non-compromise, do everything, go everywhere 5 band transceiver for SSB or CW that performs equally well at home, in an automobile, airplane, boat or trailer. The TS-520 features built-in AC power supply, built-in 12 volt DC power supply, built-in VOX with adjustable gain delay and anti-VOX.

The price . . . \$599.00

## Kenwood's winning pair

The R-599A is the most complete receiver ever offered. It is solid state, superbly reliable, small and lightweight, covers the full amateur band . . . 10 thru 160 meters, CW, LSB, USB, AM,

AM, N and FM.

The price . . . \$439.00


The T-599A is mostly solid state . . . only 3 tubes, has built-in power supply, full metering (ALC, Ip, RF output and high voltage), CW-LSB-USB-AM operation.

The price . . . \$459.00

See the Kenwood line at the following dealers: CALIFORNIA Communications Headquarters, San Diego ● Gary Radio, Inc., San Diego ● Ham Radio Outlet, Burlingame ● Henry Radio, Anaheim ● Henry Radio, Los Angeles ● Sequoia Stereo, Arcata ● Webster Radio, Fresno ● FLORIDA Amateur Electronic Supply, Orlando ● Amateur-Wholesale Electronics, Miami ● IDAHO United Electronics Wholesale, Twin Falls ILLINOIS Erickson Communications, Chicago ● Klaus Radio, Inc., Peoria ● INDIANA Graham Electronics, Indianapolis ● Hoosier Electronics, Terre Haute ● Radio Distributing Company, South Bend ● IOWA Hobby Industry, Council Bluffs ● KANSAS Associated Radio Communications, Overland Park ● LOUISIANA Trionics, Inc., New Orleans ● MARYLAND Electronic International Service Corp., Wheaton ● Professional Electronics, Baltimore ● MICHIGAN Electronic Distributors, Muskegon ● Radio Supply & Engineering Company, Detroit ● MINNESOTA Electronic Center, Minneapolis ● MISSOURI Ham Radio Center, St. Louis ● Henry Radio, Butler ● MONTANA Conley Radio Supply, Billings ● NEW JERSEY Simon Side Band Company, Oak Ridge ● NEW YORK Adirondack Radio Supply, Inc., Amsterdam ● Harrison Radio Corp., Farmingdale NORTH CAROLINA Vickers Electronics, Durham ● OHIO Amateur Electronic Supply, Cleveland ● Communications World, Cleveland ● Queen City Electronics, Cincinnati ● Srepco Electronics, Dayton ● OKLAHOMA Derrick Electronics, Broken Arrow ● Radio, Inc., Tulsa ● OREGON Portland Radio Supply, Portland PENNSYLVANIA JRS Distributors, York ● Kass Electronics, Drexel Hill ● SOUTH CAROLINA Accutek, Inc., Greenville ● SOUTH DAKOTA Burghardt Amateur Center, Watertown ● TEXAS Douglas Electronics, Corpus Christi ● Electronics Center, Inc., Dallas ● Industrial Distributors, Dallas ● Ed Juge Electronics, Inc., Fort Worth ● Madison Electronics, Houston ● UTAH Manwill Supply Company, Salt Lake City ● WASHINGTON Amateur Radio Supply Company, Seattle ● WISCONSIN Amateur Electronic Supply, Milwaukee

Prices subject to change without notice.
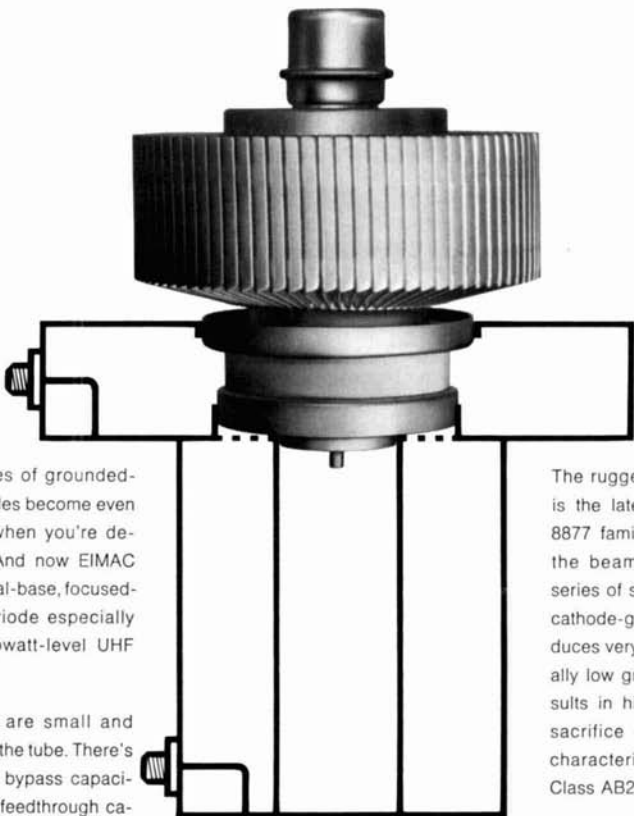
# Simplify UHF circuits with EIMAC's 8938 high mu triode.



All the advantages of grounded-grid, high-mu triodes become even more important when you're designing at UHF. And now EIMAC introduces a coaxial-base, focused-beam, high-mu triode especially designed for kilowatt-level UHF applications.

At UHF, cavities are small and closely coupled to the tube. There's no room for bulky bypass capacitors, rf chokes, or feedthrough capacitors. With the 8938 in cathode driven (grounded-grid) service, there's no need for the grid circuit bypass capacitor; and no need for screen capacitors, bias or screen power supplies and associated decoupling circuitry. The internal tube structure is simple and the surrounding circuitry is much less complicated.

The rugged, ceramic/metal 8938 is the latest addition to EIMAC's 8877 family of tubes. Because of the beam focusing action of a series of strip electron guns in the cathode-grid region, the 8938 produces very high mu with exceptionally low grid interception. This results in high power gain with no sacrifice of low intermodulation characteristics in cathode-driven Class AB2 amplifier service.

It's one more example of EIMAC's ability to provide tomorrow's tube today. For details, contact EIMAC Division of Varian, 301 Industrial Way, San Carlos, California 94070, (415) 592-1221. Or any of the more than 30 Varian/EIMAC Electron Tube and Device Group Sales Offices throughout the world.

