

\$1.50


# ham radio

magazine

*hr* 

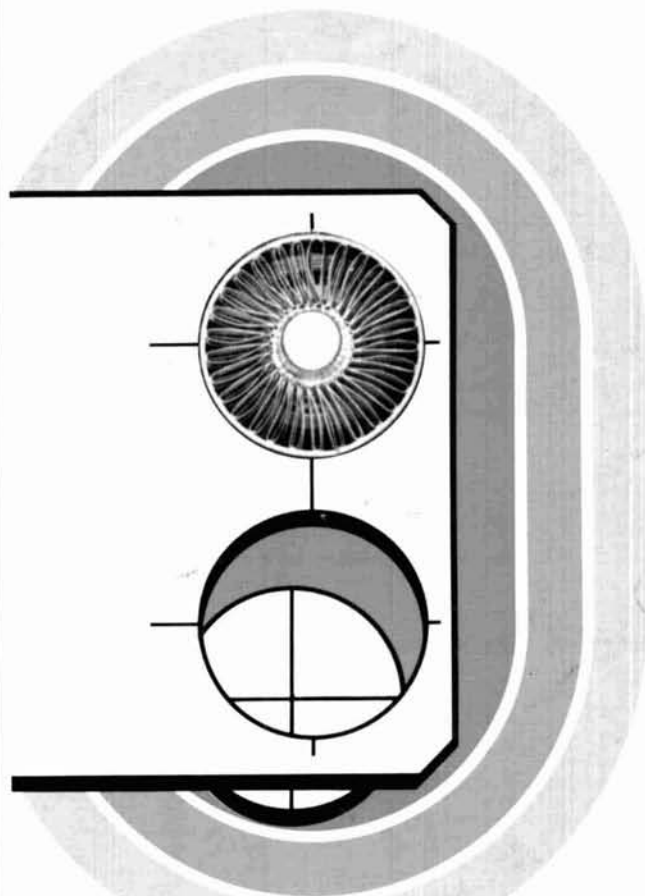**OCTOBER 1977**

- syllabic vox system 29
- 10-GHz mixer 34
- 20-meter receiver 48
- low-cost power supply 74
- microprocessors 79
- and much more . . .



**stripline  
kilowatt**  
for two meters

# TEMPO

# VHF/ONE PLUS



**MORE POWER** / 25 OR 5\* WATTS OUTPUT SELECTABLE

**REMOTE TUNING** / ON MICROPHONE

**NEW LOWER PRICE** / NOW ONLY \$399.00

**SIDEBAND OPERATION WITH SSB/ONE ADAPTER / MARS OPERATION CAPABILITY / 5 KHz NUMERICAL LED**

The Tempo VHF/One Plus is a VHF/FM transceiver for dependable communication on the 2 meter amateur band • Full 2 meter coverage, 144 to 148 MHz for both transmit and receive • Full phase lock synthesized (PLL) • Automatic repeater split—selectable up or down • Two built-in programmable channels • All solid state • 800 selectable receive frequencies with simplex and +600 KHz transmit frequencies for each receive channel. \*Adjustable internally 3 to 15 watts



## TEMPO FMH-2, FMH-5 & FMH-42 (UHF)

6 channel capability • selectable 1 or 2 - 1 or 5 Watts output • Solid-state • Battery level meter • Earphone jack • Built-in charging terminals and separate charging jack for Ni-cad batteries • Flex antenna • Carrying case standard • Excellent frequency stability allows use with booster amplifier for high power output over 100 Watts • 8 AA batteries or 10 AA Ni-cads.\*

\*Not furnished.  
FCC Type accepted models available

## TEMPO VHF & UHF AMPLIFIERS

### VHF (135 to 175 MHz)

Drive Power	Output	Model No.	Price
2W	130W	130A02	\$199
10W	130W	130A10	\$179
30W	130W	130A30	\$189
2W	80W	80A02	\$169
10W	80W	80A10	\$149
30W	80W	80A30	\$159

### UHF (400 to 512 MHz)

Drive Power	Output	Model No.	Price
2W	70W	70D02	\$270
10W	70W	70D10	\$250
30W	70W	70D30	\$210
2W	40W	40D02	\$180
10W	40W	40D10	\$145
2W	10W	10D02	\$125

FCC Type accepted models available.

## TEMPO POCKET RECEIVERS

MS-2, 4 channel scanning receiver for VHF high band, smallest unit on the market. MR-2 same size as MS-2 but has manual selection of 12 channels. VHF high band. MR-3, miniature 2-channel VHF high band monitor or paging receiver. MR-3U, single channel on the 400 to 512 UHF band. All are low priced and dependable.



Sold at Tempo dealers throughout the U.S. and abroad. Please call or write for further information.

Prices subject to change without notice


11240 W. Olympic Blvd., Los Angeles, Calif. 90064  
931 N. Euclid, Anaheim, Calif. 92801  
Butler, Missouri 64730

213/477-6701  
714/772-9200  
816/679-3127

**Henry Radio**
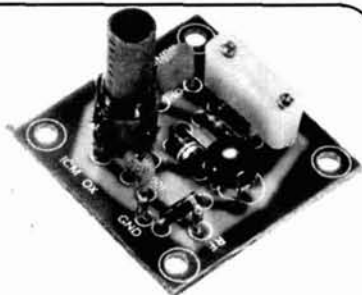
# for the experimenter!

INTERNATIONAL CRYSTALS & KITS  
OSCILLATORS • RF MIXER • RF AMPLIFIER • POWER AMPLIFIER



### OX OSCILLATOR

Crystal controlled transistor type. 3 to 20 MHz, OX-Lo, Cat. No. 035100. 20 to 60 MHz, OX-Hi, Cat. No. 035101. Specify when ordering.

\$3.95 ea.



### MXX-1 TRANSISTOR RF MIXER

A single tuned circuit intended for signal conversion in the 30 to 170 MHz range. Harmonics of the OX or OF-1 oscillator are used for injection in the 60 to 179 MHz range. 3 to 20 MHz, Lo Kit, Cat. No. 035105. 20 to 170 MHz, Hi Kit, Cat. No. 035106. Specify when ordering.


\$4.50 ea.



### PAX-1 TRANSISTOR RF POWER AMP

A single tuned output amplifier designed to follow the OX or OF-1 oscillator. Outputs up to 200 mw, depending on frequency and voltage. Amplifier can be amplitude modulated. 3 to 30 MHz, Cat. No. 035104. Specify when ordering.


\$4.75 ea.

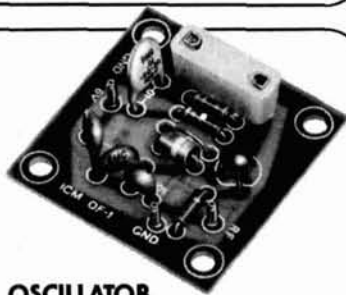

### OF-1 OSCILLATOR

Resistor/capacitor circuit provides osc over a range of freq with the desired crystal. 2 to 22 MHz, OF-1 LO, Cat. No. 035108. 18 to 60 MHz, OF-1 HI, Cat. No. 035109. Specify when ordering.


\$3.25 ea.

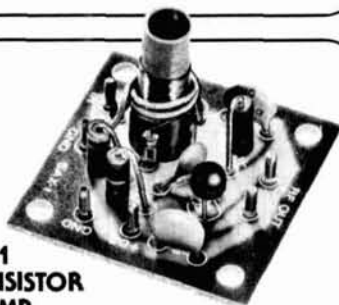

### SAX-1 TRANSISTOR RF AMP

A small signal amplifier to drive the MXX-1 Mixer. Single tuned input and link output. 3 to 20 MHz, Lo Kit, Cat. No. 035102. 20 to 170 MHz, Hi Kit, Cat. No. 035103. Specify when ordering.

\$4.50 ea.

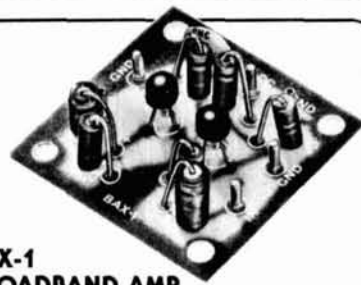

### BAX-1 BROADBAND AMP

General purpose amplifier which may be used as a tuned or untuned unit in RF and audio applications. 20 Hz to 150 MHz with 6 to 30 db gain. Cat No. 035107. Specify when ordering.

\$4.75 ea.



.02% Calibration Tolerance  
**EXPERIMENTER CRYSTALS**  
(HC 6/U Holder)

Cat. No.	Specifications	
031080	3 to 20 MHz — for use in OX OSC Lo	\$4.95 ea.
	Specify when ordering	
031081	20 to 60 MHz — For use in OX OSC Hi	\$4.95 ea.
	Specify when ordering	
031300	3 to 20 MHz — For use in OF-1L OSC	\$4.25 ea.
	Specify when ordering	
031310	20 to 60 MHz — For use in OF-1H OSC	\$4.25 ea.
	Specify when ordering.	

Shipping and postage (inside U.S., Canada and Mexico only) will be prepaid by International. Prices quoted for U.S., Canada and Mexico orders only. Orders for shipment to other countries will be quoted on request. Address orders to:  
M/S Dept., P.O. Box 32497,  
Oklahoma City, Oklahoma 73132.



**International Crystal Mfg. Co., Inc.**  
10 North Lee  
Oklahoma City, Oklahoma 73102

# Call toll-free 800-647-8660 for products by MFJ ENTERPRISES



**\$69<sup>95</sup>**

### MFJ-16010 ST Super Antenna Tuner

This NEW MFJ Super Antenna Tuner matches everything from 160 thru 10 Meters: dipoles, inverted vees, long wires, verticals, mobile whips, beams, balance lines, coax lines. Up to 200 watts RF OUTPUT. Built-in balun, too!

- Operate all bands with one antenna • Works with all solid state and tube rigs • Ultra compact: 5 x 2 x 6 inches • Uses toroid cores



**\$39<sup>95</sup>**

### MFJ-16010 Antenna Tuner

Now you can operate all bands — 160 thru 10 Meters — with a single random wire and run your full transceiver power output — up to 200 watts RF power OUTPUT.

- Small enough to carry in your hip pocket, 2-3/16 x 3-1/4 x 4 inches • Matches low and high impedance by interchanging input and output • SO-239 coaxial connectors • 12 position tapped inductor. Stacked toroid cores • At 1.8 MHz tuner matches 25 to 200 ohms.



**\$29<sup>95</sup>**

### CWF-2BX Super CW Filter

This MFJ Super CW Filter gives you 80 Hz bandwidth, and extremely steep skirts with no ringing or razor sharp selectivity that lets you pull signals out of heavy QRM. Plugs between receiver and phones or connect between audio stage for speaker operation.

- Selectable BW: 80, 110, 180 Hz • 60 dB down one octave from center frequency of 750 Hz for 80 Hz BW • Reduces noises 15 dB • 9 V battery • 2-3/16 x 3-1/4 x 4 inches • CWF-2PC, wired PC board, \$19.95.



**\$69<sup>95</sup>**

### MFJ-8043 IC Deluxe Electronic Keyer

This NEW MFJ Deluxe Keyer gives you more features per dollar than any other keyer available.

- Uses Curtis-8043 keyer chip • Sends iambic, automatic, semi-automatic, manual • Use squeeze, single lever, or straight key • Dot memory, self-completing dots and dashes, jam proof spacing, instant start • RF proof • Solid state keying  $\pm 300$  V max • Weight, tone, volume, speed controls • Uses 4 C-cells; external power jack • 6 x 6 x 2 inches • Sidetone and speaker • Optional squeeze key: \$29.95



**\$54<sup>95</sup>**

### CMOS-8043 Electronic Keyer

State of the art design uses CURTIS-8043 Keyer-on-a-chip.

- Built-in Key • Dot memory • Iambic operation with external squeeze key • 8 to 50 WPM • Sidetone and speaker • Speed, volume, tone, weight controls • Ultra reliable solid state keying  $\pm 300$  volts max. • 4 position switch for TUNE, OFF, ON, SIDETONE OFF • Uses 4 penlight cells • 2-3/16 x 3-1/4 x 4 inches



**\$59<sup>95</sup>**

### LSP-520BX II Log Speech Processor

Up to 400% more RF power. Plugs between your microphone and transmitter.

- Gives your audio punch power to slice through QRM • 30 dB IC log amp and 3 active filters • RF protected • 9 V battery • Two Mic jacks: 1/4" phone jacks, uncommitted 4 pin jack • Output cable • 2-1/8 x 3-5/8 x 5-9/16 inches • LSP-520BX, in standard MFJ enclosure, electronically identical, \$49.95.



**\$29<sup>95</sup>**

### SBF-2BX SSB Filter

Dramatically improves readability.

- Optimizes your audio to reduce sideband splatter, remove low and high pitched QRM, hiss, static crashes, background noise, 60 and 120 Hz hum • Reduces fatigue during contest, DX, and ragchewing • Plugs between phones and receiver or connect between audio stage for speaker operation • Selectable bandwidth IC active audio filter • Uses 9 volt battery • 2-3/16 x 3-1/4 x 4 inches



**\$29<sup>95</sup>**

### MFJ-200BX Frequency Standard

Provides strong, precise markers every 100, 50, or 25 KHz well into VHF region.

- Exclusive circuitry suppresses all unwanted markers • Markers are gated for positive identification, CMOS IC's with transistor output. • No direct connection necessary • Uses 9 volt battery • Adjustable trimmer for zero beating to WWV • Switch selects 100, 50, 25 KHz or OFF • 2-3/16 x 3-1/4 x 4 inches



**\$49<sup>95</sup>**

### MFJ-1030BX Receiver Preselector

Clearly copy weak unreadable signals (increases signal 3 to 5 "S" units).

- More than 20 dB low noise gain • Separate input and output tuning controls give maximum gain and RF selectivity to significantly reject out-of-band signals and reduce image responses • Dual gate MOS FET for low noise, strong signal handling abilities • Completely stable • Optimized for 10 thru 30 MHz • 9 V battery • 2-1/8 x 3-5/8 x 5-9/16 inches



**\$29<sup>95</sup>**

### MFJ-40T QRP Transmitter

Work the world with 5 watts on 40 Meter CW.

- No tuning • Matches 50 ohm load • Clean output with low harmonic content • Power amplifier transistor protected against burnout • Switch selects 3 crystals or VFO input • 12 VDC • 2-3/16 x 3-1/4 x 4 inches

MFJ-40V, Companion VFO ..... \$29.95  
MFJ-12DC, IC Regulated Power Supply,  
1 amp, 12 VDC ..... \$29.95



**\$17<sup>95</sup>**

### CPO-555 Code Oscillator

For the Newcomer to learn the Morse code.

For the Old Timer to polish his fist.

For the Code Instructor to teach his classes.

- Send crisp clear code with plenty of volume for classroom use • Self contained speaker, volume, tone controls, aluminum cabinet • 9 V battery • Top quality U.S. construction • Uses 555 IC timer • 2-3/16 x 3-1/4 x 4 inches

TK-555, Optional Telegraph Key ..... \$1.95



**\$19<sup>95</sup>**

### C-500 Digital Alarm Clock

This digital alarm clock is also an ID Timer. Assembled, too!

- Gives ID buzz every 9 minutes automatically, or after tapping ID/doze button • Pressing ID/doze button displays seconds • Large 63 inch digits • Easily zeros to WWV • AM and PM LED indicators • Power out indicator • Fast set, slow set buttons • 110 VAC, 60 Hz • 3-1/8 x 3-3/4 x 3-3/8 inches • One year warranty by Fairchild

Order any product from MFJ and try it. If not delighted, return within 30 days for a prompt refund (less shipping).  
Order today. Money back if not delighted. One year unconditional guarantee. Add \$2.00 shipping/handling.

Order By Mail or Call TOLL FREE 800-647-8660 and Charge It On



**MFJ ENTERPRISES** P. O. BOX 494  
MISSISSIPPI STATE, MISSISSIPPI 39762  
In Europe contact: ING I. STERN, Lohkoppelstrasse 27, 2000 Hamburg 76, West Germany. Tel.: (040) 299-6110, Telex: 2161808 STEX D



# ham radio

magazine

OCTOBER 1977

volume, 10, number 10

**T. H. Tenney, Jr., W1NLB**  
publisher

**James R. Fisk, W1HR**  
editor-in-chief

**editorial staff**

Charles J. Carroll, K1XX  
Alfred Wilson, W6NIF  
assistant editors

Patricia A. Hawes, WA1WPM  
Thomas F. McMullen, Jr., W1SL  
Joseph J. Schroeder, W9JUV  
associate editors

Wayne T. Pierce, K3SUK  
cover

**publishing staff**

Harold P. Kent, WA1WPP  
assistant publisher

Fred D. Moller, Jr., WA1USO  
advertising manager

James H. Gray, W1XU  
assistant advertising manager

Therese R. Bourgault  
circulation manager

ham radio magazine  
is published monthly by  
Communications Technology, Inc  
Greenville, New Hampshire 03048  
Telephone: 603-878-1441

**subscription rates**

U.S. and Canada: one year, \$12.00  
two years, \$22.00  
three years, \$30.00

Europe, Japan, Africa:  
(via Air Forwarding Service)  
one year, \$25.00  
two years, \$45.00

North America, South America, Australia  
and Asia (except Japan):  
(via Surface Mail)  
one year, \$18.00  
two years, \$34.00

**foreign subscription agents**

Foreign subscription agents are  
listed on page 99

Microfilm copies  
are available from  
University Microfilms, International  
Ann Arbor, Michigan 48106  
Order publication number 3076

Cassette tapes of selected articles  
from ham radio are available to the  
blind and physically handicapped  
from Recorded Periodicals  
919 Walnut Street, 8th Floor  
Philadelphia, Pennsylvania 19107

Copyright 1977 by  
Communications Technology, Inc  
Title registered at U.S. Patent Office

Second-class postage  
paid at Greenville, N.H. 03048  
and at additional mailing offices  
Publication number 23340



## contents

**10 two-meter stripline kilowatt**

Frederick J. Merry, W2GN

**26 improving the accuracy  
of your frequency counter**

Clifford A. Harvey, W1RF

**29 S-line syllabic vox system**

H. Rommel Hildreth, W0IP

**34 10-GHz hybrid-tee mixer**

R. J. Harry, G3NRT

**38 calculator aided circuit analysis**

Leonard H. Anderson

**48 high performance 20-meter receiver**

M. A. Chapman, K6SDX

**70 repeater kerchunk eliminator**

Robert K. Morrow, WB6GTM

**74 low-cost power supply**


Budd M. Meyer, K2PMA

**79 microprocessors: data converters**

Perry Pollins, WA1MOP

**4 a second look**  
**126 advertisers index**  
**99 flea market**  
**110 ham mart**

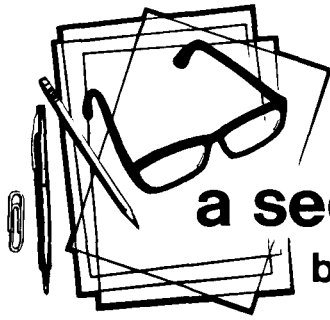**86 ham notebook**  
**79 microprocessors**  
**90 new products**  
**6 presstop**



## a second look

by Jim Fisk

**In the last few months there has been** an increase in the number of inquiries and complaints received by the FCC concerning state and local laws which deal with radio and television. Most of the calls and letters are related to CB, and ask whether a particular ordinance is constitutional, or complain about the enforcement of a state statute that is thought to be in conflict with the FCC regulations. To answer these questions, the FCC recently released Public Notice 87276 which provides information to amateurs, CBers, and other FCC licensees who feel they have run into improper local regulation of radio communications.

As the Public Notice points out, as early as 1912 the Congress recognized that radio communications was inherently interstate in nature, was a form of commerce, and was uniquely adaptable to uniform regulation by the federal government. The Radio Act of 1927 increased the federal government's authority to regulate this area, and the passage of the Communication Act of 1934 substantially completed the trend toward comprehensive federal regulation of interstate and foreign communications by wire and radio. To execute and enforce its provisions, the Act also provided for the establishment of the FCC.

It was the primary goal of the Communications Act to make available, "to all people of the United States a rapid, efficient, nation-wide, and world-wide wire and radio communication service . . ." The Act proposed to execute this policy by "centralizing authority" and by "granting additional authority with respect to interstate and foreign commerce in radio communication . . ." Furthermore, the Act claims complete jurisdiction over radio energy for the federal government, as stated in Section 301:

It is the purpose of this Act, among other things, to maintain the control of the United States over all the channels of interstate and foreign radio transmission; and to provide for the use of such channels . . . under licenses granted by Federal authority . . . No person shall use or operate any apparatus for the transmission of energy or communications or signals by radio . . . except under and in accordance with this Act and with a license in that behalf granted under the vision of this act, 47 U.S.C. §301.

In addition, Congress granted the Commission the authority to establish a pervasive system of regulation in the various radio services. Section 303 of the Act gives such numerous powers to the FCC as to leave no doubt as to the extent of this regulatory scheme. These and other sections of the Act indicate the clear intention of Congress that radio be regulated by the federal government.

Under the Supremacy Clause of the United States Constitution, state and local statutes may be pre-empted when (1) a local law conflicts with a law enacted by Congress, or (2) when Congress has adopted pervasive legislation in a particular field with the intent that regulation in the area will be conducted exclusively by the federal government. Furthermore, local ordinances which unreasonably burden interstate commerce may be invalidated under the authority granted to the federal government by the Commerce Clause of the United States Constitution.

Whether or not a particular local statute has been pre-empted by federal legislation is a question of law, and when a conflict between federal and state law arises, the courts, both state and federal, are usually called upon to make the final decision. For proper resolution the specific local law in question must be reviewed, and each case must be carefully judged on its own facts.

In general it may be said that in matters involving purely local concerns, the courts have found that reasonable local statutes are not in conflict with the Communications Act; such things as local zoning ordinances limiting antenna heights, and the right of local courts to adjudicate property rights involving licensee's facilities have all been upheld. On the other hand, where a local law conflicts with the FCC's regulatory scheme for radio services, the federal law will prevail; state laws involving the censorship of material carried on broadcast stations, for example, and those requiring FCC licensees to refrain from activities required by the Communications Act have been struck down.

The FCC does not have the resources to routinely monitor state and local laws which affect radio communications, nor can the FCC intervene in every local court proceeding in which the validity of various laws is tested. However, amateurs and other FCC licensees who feel victimized by improper local laws may raise federal pre-emption in their own behalf, and local legislative bodies should consider the issue when contemplating the enactment of ordinances in areas regulated by the Communications Act. Since many of the inquiries received by the FCC directly concern CB (and indirectly, amateur radio), local lawmakers should also be aware that the FCC has issued extensive regulations governing this area. Therefore, local ordinances designed specifically to regulate CB (or amateur) transmissions could be invalid according to the legal principles discussed above.

**Jim Fisk, W1HR**  
editor-in-chief



# That's all, Folks!

All you need for All Mode Mobile, that is.

All Mode Mobile is now yours in a superior ICOM radio that is a generation ahead of all others. The new, fully synthesized **IC-245/SSB** puts you into FM, SSB and CW operation with a very compact dash-mounted transceiver like none you've ever seen.

- **Variable offset:** Any offset from 10 KHz through 4 MHz in multiples of 10 KHz can be programmed with the LSI Synthesizer.
- **Remote programming:** The **IC-245/SSB** LSI chip provides for the input of programming digits from a remote key pad which can be combined with Touch Tone\* circuitry to provide simultaneous remote program and tone. Computer control from a PIA interface is also possible.

\* a registered trademark of AT&T.

- **FM stability on SSB and CW:** The **IC-245/SSB** synthesis of 100 Hz steps make mobile SSB as stable as FM. This extended range of operation is attracting many FM'ers who have been operating on the direct channels and have discovered SSB.

The **IC-245/SSB** is the very best and most versatile mobile radio made: that's all. For more information and your own hands-on demonstration see your ICOM dealer. When you mount your **IC-245/SSB** you'll have all you need for All Mode Mobile.

#### SPECIFICATIONS

FREQUENCY COVERAGE  
MODES  
SUPPLY VOLTAGE  
SIZE (mm)  
WEIGHT  
TRANSMITTER  
TX OUTPUT  
CARRIER SUPPRESSION

144.00 to 148.00MHz  
FM, DTMF  
100W (A3), CW (A1)  
DC 13.8V ± 15%  
90x115x90x230mm  
2.7  
F3 10W  
100W (PEP), A1 10W  
40 dB OR BETTER

SPURIOUS RADIATION  
MAXIMUM FREQUENCY  
DEVIATION  
MICROPHONE IMPEDANCE

RECEIVER  
SENSITIVITY

-60 dB BELOW CARRIER  
1.5KHz  
600 OHMS

\*ALL AT 0.5 MICROVOLT  
INPUT GIVES 10 dB S+N  
F3 IS 4 MICROVOLTS OR LESS  
FOR 20 dB QUIETING  
S+N = 13N AT 1 MICROVOLT  
INPUT, 30 dB

SQUELCH THRESHOLD  
SPURIOUS RESPONSE

SYNTHESIZER  
FREQUENCY RANGE  
STEP SIZE

STABILITY

6 dB OR LESS (F3)  
60 dB OR BETTER

1.44 MHz to 148 MHz  
5 KHz for FM

100 Hz or 3 KHz for SSB  
PER C IN THE RANGE OF -10  
TO +40C ±0.00004%

\*VALID WITH SSB UNIT ONLY

VHF/UHF AMATEUR AND MARINE COMMUNICATION EQUIPMENT

Distributed by:



ICOM WEST, INC.  
Suite 3  
13256 Northrup Way  
Bellevue, Wash. 98005  
(206) 747-9020

ICOM EAST, INC.  
Suite 307  
3331 Towerwood Drive  
Dallas, Texas 75234  
(214) 620-2780

ICOM CANADA  
7087 Victoria Drive  
Vancouver B.C. V5P 3Y9  
Canada  
(604) 321-1833



THE TYPE ACCEPTANCE and 10-meter amplifier ban dockets themselves — Dockets 20117 and 20116 — were not discussed at recent FCC meetings, only the ARRL's request for oral argument on those two propositions. After considerable discussion it was decided to reserve the decision on the League's request until later, concurrent with the Commission's actual discussion of the dockets. At this point it seems likely that formal consideration of those two proposals should occur in early October.

MARITIME MOBILES ABOARD U.S. VESSELS gained many new frequencies effective September 12. All U.S. licensed Amateurs operating on the high seas (not in the waters of a foreign power) will be permitted to operate on any frequency that Amateurs are authorized in that ITU Region. For example, in nearby waters (ITU Region 2) maritime mobiles may use all domestic U.S. Amateur frequencies, from 160 up. In the other ITU Regions Amateurs are more limited, of course — a U.S. maritime mobile off the coast of Europe or Africa would be restricted to 7000-7100 on 40 meters, 144-146 on two, and forbidden 6 and 220.

ARMA PRESIDENT DENNIS HAD tendered his resignation to the ARMA membership in a three-page letter. In the letter Denny cited the heavy burden the ARMA presidency had placed on him personally and on Dentron, a burden that — with a few notable exceptions — had not been shared by other ARMA members. Another factor in his resignation decision was criticism from a few of the ARMA members, criticism that reflected on his personal motives and integrity in his efforts to establish and maintain ARMA, while some of these same critical members were the ones whose catering to the illegal CB market had brought ARMA into being in the first place.

Rumors of a possible split in the organization have been in the air recently, with a vocal minority of ARMA members more and more openly critical of the majority's support of the "Amateur equipment for Amateurs" concept. The problem of those members whose "unethical conduct," Dennis said, "has brought on the legal and regulatory problems we now face..." is a prime reason that he decided to resign.

STATE LICENSING OF CBers and Novice and Technician Class Amateurs has been proposed in Michigan by State Senator Basil Brown. Licensing would apply only to radios used in cars, would require a \$2 yearly registration fee, a description of the rig along with details of where it was obtained, and a description of the car it is installed in.

The Proposal, Senate Bill 409, exempts General and higher class Amateurs as well as visitors from out of state. It has been referred to the Senate Judicial Committee, which is chaired by Senator Brown. Michigan Amateurs wishing to comment on it can write Senator Brown or their own state senators in care of the Michigan Senate, Lansing, Michigan 48902.

CENTRAL STATES VHF CONFERENCE in Kansas City presented the John Chambers award to W6PO for his outstanding contribution to rf power amplifier design and assistance to VHF and EME oriented people. The F9FT antennas captured honors on both 144 and 432 MHz with gains that measured upwards of 1.0 dB above its nearest competitor which included such notables as KLMS and Quagis. The best 144-MHz noise figure was registered by WAØRDX using a neutralized 2N5297. At 432 MHz, K2UYH's V244 GaAs fet measured 1.25 dB while WB5LUA's entry, an NE645 bipolar, was close behind at 1.35 dB. Next year's plans call for the conference to be held in Rochester, Minnesota starting on August 18.

KH6BZF EXCHANGED 599s with N4DT (WB4PAG) on OSCAR orbit 12634B, culminating a series of skeds which also include K1HTV, K2SWZ, W1JR, WA8UUY, VE3BNO, and W2KLN. Other east coasters wishing a sked with KH6BZF should write including an SASE.

AN ASCII OK and other benefits of the FCC's "bandwidth docket" (20777) may not be far off. Safety and Special Bureau Chief Charley Higginbotham told the audience at a session on regulatory matters at the APCO (Associated Public Service Communications Officers) Convention in Chicago that they could expect a report and order on 20777 to come out "this fall."

INTERFERENCE ON 160 and possibly the high end of 75 meters could result from the FCC's recent approval of wide-band swept anti-theft systems. The three bands authorized for such systems are 1.7-2.3, 4.05-4.95, and 7.4-9.0 MHz, with a maximum field strength of 100 microvolts per meter at 30 meters.

Anti-Theft Systems must not interfere with radio communications, so can be shut down if they bother Amateur operations.

CW SENDING TEST is being dropped by the FCC for all Commission administered Amateur examinations, shortening and simplifying (since examiners won't need CW qualifications) the exam.

Novice Exams Administered by volunteer examiners will still require a sending test, however, to weed out really bad fists.



# Now there are two MLA amplifiers. DenTron announces the NEW! MLA-1200

The MLA-1200 linear amplifier was designed to give you a choice. We know that not all amateurs want to run 2000 watts PEP, but we also feel the demand for a luxury styled amplifier. Hence the MLA-1200.


**Basically it's built on success.** The MLA-1200 incorporates the same sleek styling of the famous MLA-2500, but employs a single Eimac 8875 triode, yielding 1200 watts PEP SSB and 1000 watts DC CW with as little as 70 watts of drive.

There are many features common to both MLA's, like forced air cooling, and a plug-in PC board containing ALC and metering circuitry. The MLA-1200 covers 10-80 and MARS frequencies. Be assured that all DenTron amplifiers far exceed the FCC harmonic emissions standards.

**It's a different kind of luxury.** The MLA-1200 is a compact dynamo only 10"W x 6 1/4"H x 10"D and weighs only 10 pounds! Twin outboard power supplies are available for AC or DC mobile operation. Picture that on your home, boat or car!

MLA-1200 \$399.50. AC-1200 \$159.50. DC-1200 \$199.50.  
I'll bet you knew DenTron would give you a choice.

**DenTron**  
Radio Co., Inc.

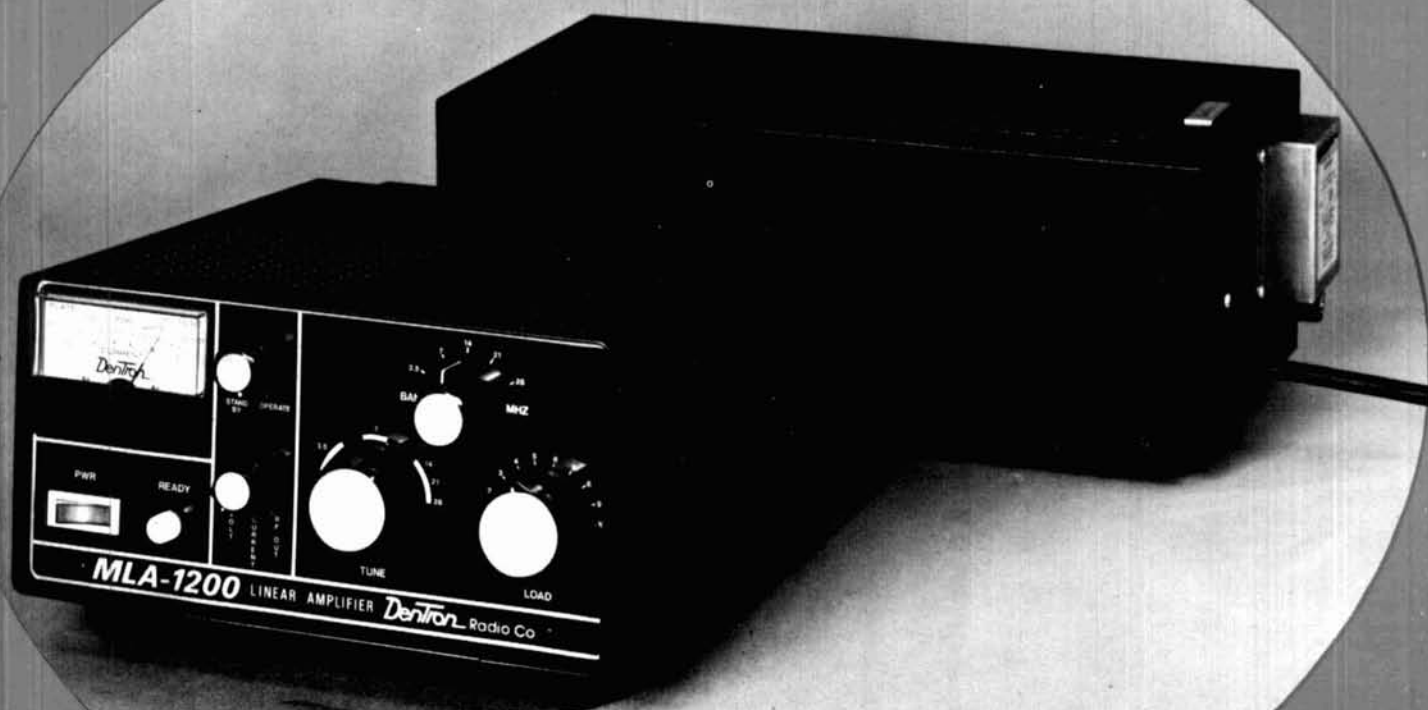

2100 Enterprise Parkway  
Twinsburg, Ohio 44087  
(216)425-3173

# Sooner or later . . .

every Ham will probably own at least one

**Small size . . .  
giant performance**

**TWO MODELS AVAILABLE:  
2.5 Watt MARK II and  
4 Watt MARK IV**

**SPECIFICATIONS:**

- Range: 144-148 MHz
- 6 Channel Operation
- Individual Trimmers on all TX and RX Xtals.
- Current Drain: RX 15 mA, TX - Mark II, 500 mA, Mark IV 900 mA
- 12 KHz Ceramic Filter
- 10.7 MHz and 455 kHz IF
- Spurious and Harmonics: 50 dB below carrier
- BNC (Twist type) Antenna Connector
- .3 Microvolt Sensitivity for 20 dB Queiting
- Uses special rechargeable Ni-Cad Battery Pack
- New improved Rubber Duck included
- One pair Xtals 52/52 included
- Weight: 16 oz. (.45 Kg) inc. batteries
- Size: 6" x 1.770" x 2.440"

**ACCESSORIES AVAILABLE**

Include LC-4 Leather Case, WC12 AC Wall Battery Charger, BC4 Desk Type Battery Charger, SM4 Speaker Mic, Touch Tone Pad, Tone Options.

# Wilson Hand-Held

**NEW!**

The new arrivals to the Wilson family of quality high performing hand-held radios are the small American-made small sized MARK II and MARK IV. The ultimate hand-held for the amateur who demands quality, performance and value.

**FEATURES:**

- Lightweight and compact size - fits comfortably in the palm of your hand.
  - Rugged Lexan® case.
  - Same dependable performance as all Wilson Hand-Helds.
  - Microswitch Speaker-Mic built in.
- Priced at

**\$199<sup>95</sup>** MARK II  
(2.5 watt)

**\$239<sup>95</sup>** MARK IV  
(4 watt)



FOR SIZE COMPARISON, THE NEW MARK IV IS ILLUSTRATED NEXT TO WILSON'S 1405SM SWITCHABLE 1 & 5 WATT RADIO.

Other Wilson units available are the VHF Models 1402SM, 2.5 watt, Model 1405SM Switchable 1 and 5 watt and 4502SM, 450 MHz, 2202SM, 220 MHz UHF units and Wilson's WE800 synthesized 2 meter portable rig.

**DON'T MISS OUT ON THE EXPLODING HAM MARKET!**

**ATTENTION AMATEUR DEALERS:**

Wilson is accepting new dealers in many areas . . . contact us if you are interested.

For an illustrated Amateur Products Buyers Guide, write:



## Wilson Electronics Corp.

P.O. Box 19000 • Las Vegas, Nevada 89119 • (702) 739-1931 • TELEX 684-522

# Wilson's

# SYSTEM ONE

## TRIBANDER ANTENNA IS HERE...

**SYSTEM ONE**  
**FOR 20, 15 and 10 METERS**  
 Monoband performance  
 with 4 elements on 20 meters  
 on a 26' boom.

THE SY 1000 TRIBANDER  
 ANTENNA IS SHOWN HERE  
 WITH THE WR 500 ROTOR  
 AND SST-64 CRANK-UP  
 TOWER @ 50 FT.  
 (Guy System not shown)




The new standard of performance for Tribanders is the Wilson System One!!! A DX'er's delight operating 20 meters on a full 26' boom with 4 elements, 4 operational elements on 20-15-10, plus separate reflector element on 10 meters for correct monoband spacing. Featured are the large diameter High-Q Traps, Beta matching system, heavy duty Taper Swaged Elements, rugged Boom to Element mounting . . . and value priced at \$259.95. Additional features: • 10 dB Gain • 20-25 dB Front-to-Back Ratio • SWR less than 1.5 to 1 on all bands.

### MODEL SY-1 SPECIFICATIONS:

Matching Method:	Beta	F/B Ratio	20-25 dB	Mast Diameter	2" O.D.
Band MHz:	14-21-28	Boom Length	26'	Boom Diameter	2" O.D.
Maximum Power Input:	Legal Limit		(2" O.D.)	Surface Area	7.3 sq. ft.
Gain	10 dB	No. of Elements	5	Windload Area	146 lbs.
VSWR (at Resonance)	1.5 to 1	Longest Element	26' 7"	Shipping Weight	50 lbs.
Impedance	50 ohms	Turning Radius	18' 6"		





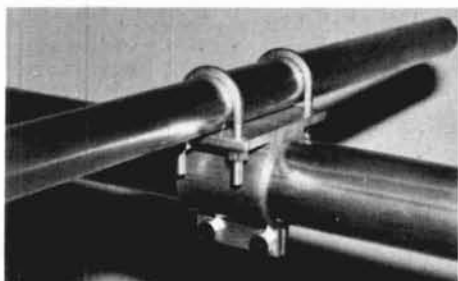
ADVANCED DESIGN LARGE DIAMETER  
HIGH-Q TRAPS FOR MINIMUM LOSS AND  
MAXIMUM POWER CAPACITY



HEAVY DUTY BOOM  
TO ELEMENT EXTRUSION



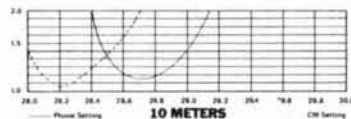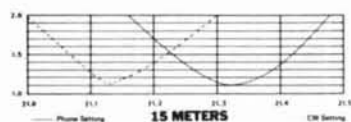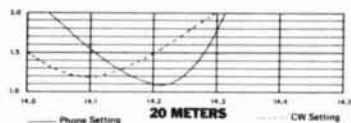INSULATED DRIVEN ELEMENT WITH  
PRECISION BETA MATCH AND HEAVY  
DUTY ELEMENT MOUNTS




**AMATEUR PRODUCTS DEALERSHIPS  
FOR MANY AREAS ARE AVAILABLE!!!**  
 If you are interested in the profits you can  
 make as a Wilson Dealer, contact us.

For complete specifications on the above products or a copy of our new Amateur Products Buyers Guide, write:  
 Consumer Products Division


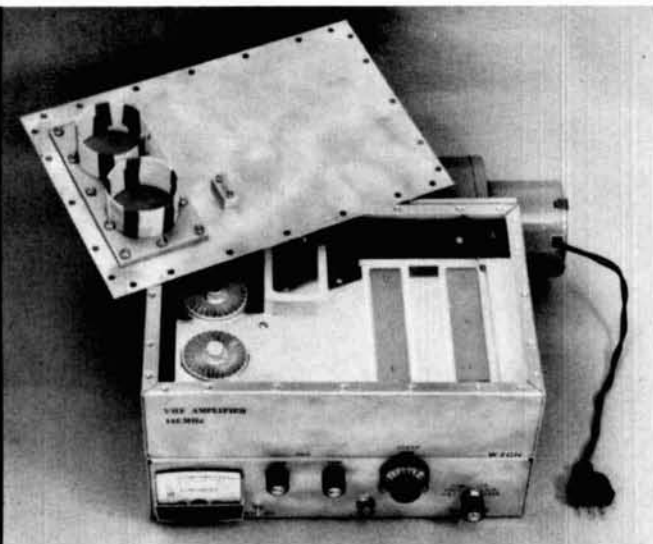
# Wilson Electronics Corp.

P.O. BOX 19000 • LAS VEGAS • NEVADA • 89119 • (702) 739-1931 • TELEX 684-522



# stripline kilowatt for two meters

Complete layout  
and construction details  
for a compact  
two-meter kilowatt  
based on the  
popular K2RIW design  
for 432 MHz

The stripline rf power amplifier designed by K2RIW for 432 MHz and described in *QST* several years ago has gained wide acceptance and use.<sup>1</sup> At the present time it's estimated that 300 to 400 of these amplifiers are in use around the world. The techniques outlined by K2RIW — using a pair of inexpensive ceramic tetrodes in a parallel stripline configuration — were used in a two-meter power amplifier designed by W9OJI.<sup>2</sup> A number of other single-tube stripline power amplifiers for two meters have also appeared in the amateur magazines. In this article I will try to put all this background and experience into construction information for a two-meter power amplifier packaged in the same com-

pact box as K2RIW's original design for 432 MHz. Such a unit could possibly become as popular on 144 MHz as the K2RIW amplifier has on 432.

Several stripline power amplifiers based on the layout described in this article have already been built and thoroughly tested on the air. When operated in the class AB1 linear mode, the amplifier provides 600 watts output with 6 to 8 watts drive. The all-mode two-meter transceivers now on the market have more than ample output to drive this amplifier to full output; the sharply tuned circuits in the amplifier help to attenuate any out-of-band products from the driver.

Any of the tubes from the 4CX250 series are suitable for the amplifier. However, the cooling problem is simplified by using 8930 tubes which are similar to 4CX250Rs except that they have a 2-inch (50mm) diameter anode. The dimensions for the plate line, chimneys, and top cover will be given for both tube types, but 8930s are the recommended choice.

Referring to the schematic, **fig. 1**, the plate line is a quarter wavelength long, with the plate blocking capacitor in the form of a Teflon sandwich at the cold end. Plate tuning is accomplished by a combination of fixed copper plate and beryllium copper flapper capacitor mounted below and near the plate end of the line, **fig. 2**. The capacitive loading to the output is adjusted by a flapper capacitor above the plate line which is also at the plate end of the line.

**By Fred Merry, W2GN, 35 Highland Drive, East Greenbush, New York 12061**




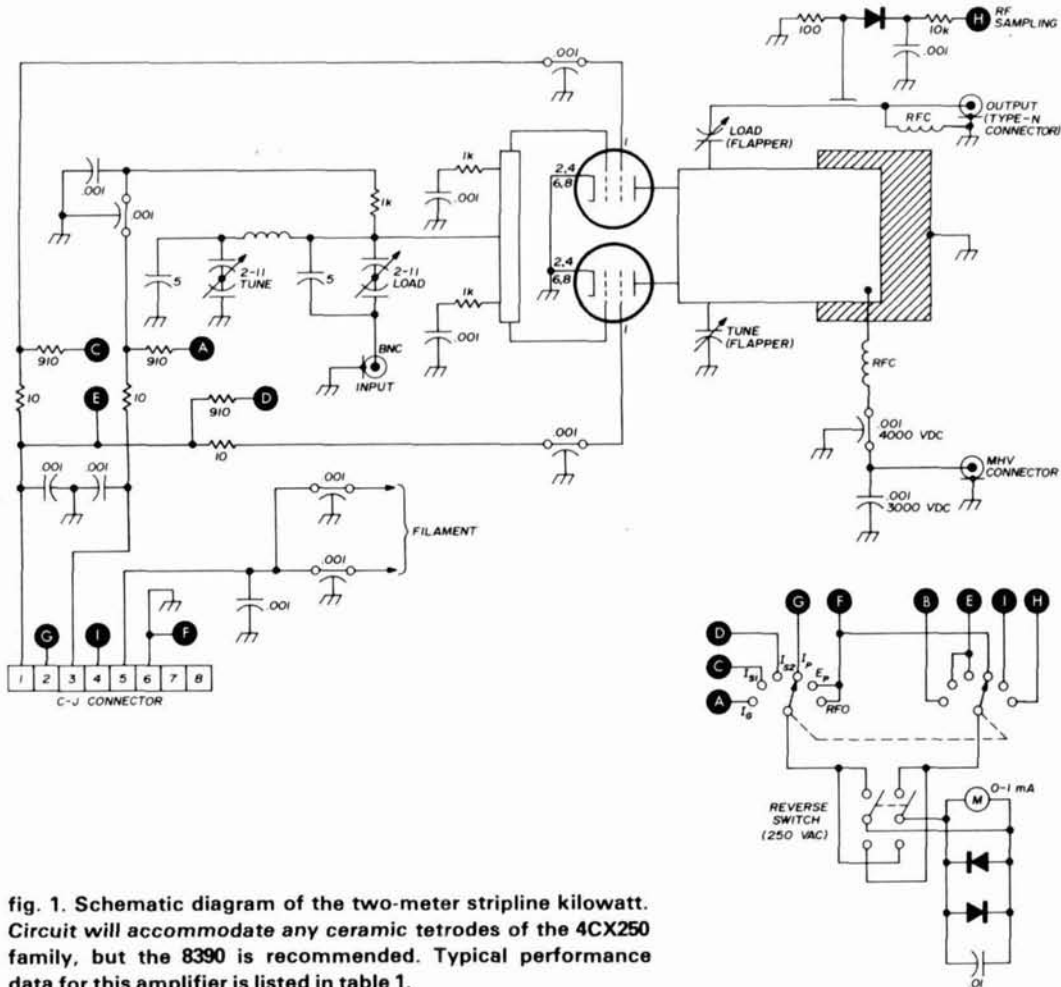


fig. 1. Schematic diagram of the two-meter stripline kilowatt. Circuit will accommodate any ceramic tetrodes of the 4CX250 family, but the 8390 is recommended. Typical performance data for this amplifier is listed in table 1.

The grid circuit consists of a 3-turn inductor tuned by a butterfly capacitor at the end away from the grids. Capacitive coupling is used for the input circuit. Eimac 620A or 630A sockets plus the construction and bypassing techniques used provide stability. Stability is further assured by loading the grid circuit down to approximately 300 ohms (derived from the grid bias resistor and two other 1000-ohm resistors mounted close to the grid socket connections of each tube, fig. 1).

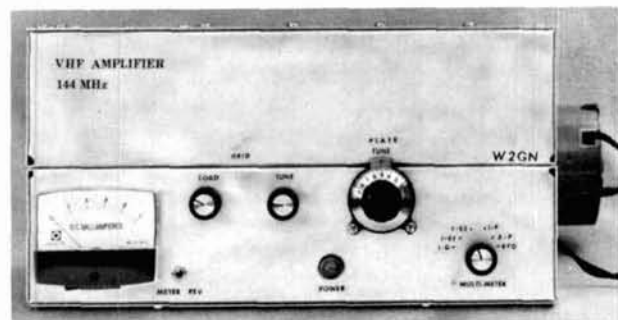

Stripline kilowatt for two meters is compact, and measures only 6-inches (15cm) high, 12-inches (30.5cm) wide, and 8-inches (20cm) deep.

Chassis construction involves the use of three standard chassis: two 8 x 12 x 3 inches (20.3x30.5x7.6cm) and one 5 x 7 x 3 inches (12.7x17.8x7.6cm), plus a top plate and a bottom cover. The chassis preparation is covered by the illustrations accompanying this article which include complete drilling, punching, and cutting details. A good starting point is the top cover which is a piece of 3/32-inch (2.5mm) thick aluminum cut and drilled as shown in fig. 3. The large holes are made with a hole saw, 2-1/4 inches (5.7cm) for 8930 tubes, or 1-3/4 inches (4.5cm) for 4CX250s. The vent plate, which is 3/16-inches (4.5mm) thick can also be drilled and hole sawed at the same time. A piece of aluminum screening is cut to the size of the vent plate; the screen is fastened between the top plate and the vent plate with 1/2-inch (12.5mm) long screws, 6-32 (M3.5) lockwashers, and nuts.

The plate loading adjustment block is cut from a piece of 1/2-inch (12.5mm) square aluminum bar stock, drilled and tapped as shown in fig. 3. This block is fastened to the top plate with 3/4-inch (19mm) long 4-40 (M3) screws. The 8-32 (M4) nylon adjustment screw is cut to size and inserted in the block. This completes the top cover assembly.

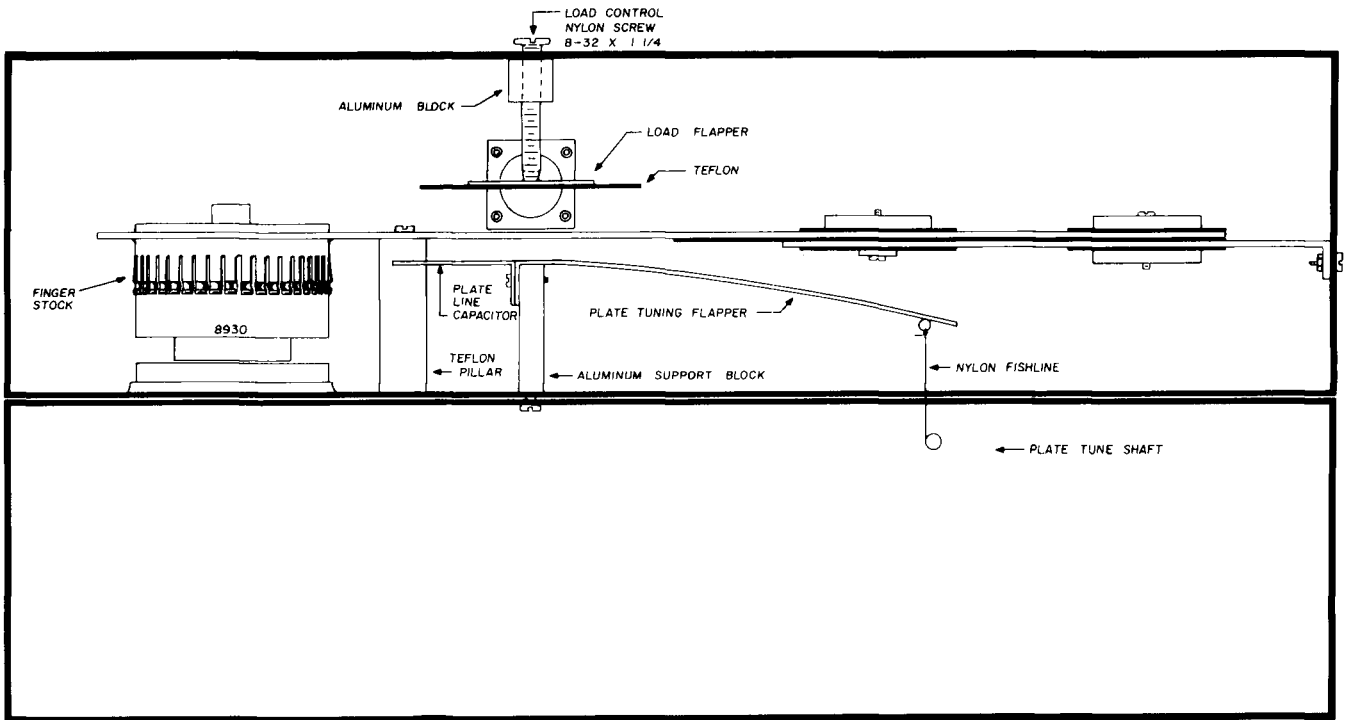


fig. 2. Cross-sectional view of the two-meter kilowatt showing the location of the plate circuit components.

The upper chassis is now prepared as shown in figs. 4, 5, and 6. Chassis punches 2-1/4 and 1-3/4 inch (5.7 and 4.5cm) in diameter are required for the socket holes and the air intake. Note also that the plate with a 1-3/4-inch (4.5cm) hole requires the use of a hole saw to get through the 3/16 inch (4.5mm) thickness. This screened air intake plate must be chosen for either a hose-connected blower, or a blower mounted directly on the chassis. The drawing


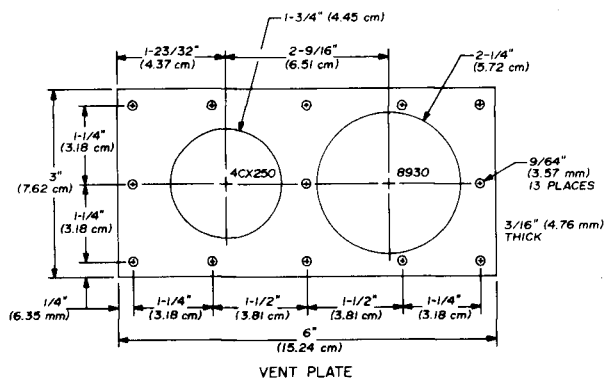


fig. 3. Bottom view of the top plate of the two-meter kilowatt. Top plate is made from 3/32-inch (2.5mm) aluminum sheet; vent plate is made from 3/16-inch (4.5mm) thick aluminum. The dashed 1-3/4-inch (4.5cm) circle is for 4CX250R and similar tubes; the 2-1/4-inch (5.7cm) circle is for the recommended 8930 tubes. A piece of aluminum screen is cut to the same dimensions as the vent plate and mounted between the top plate and the vent plate.

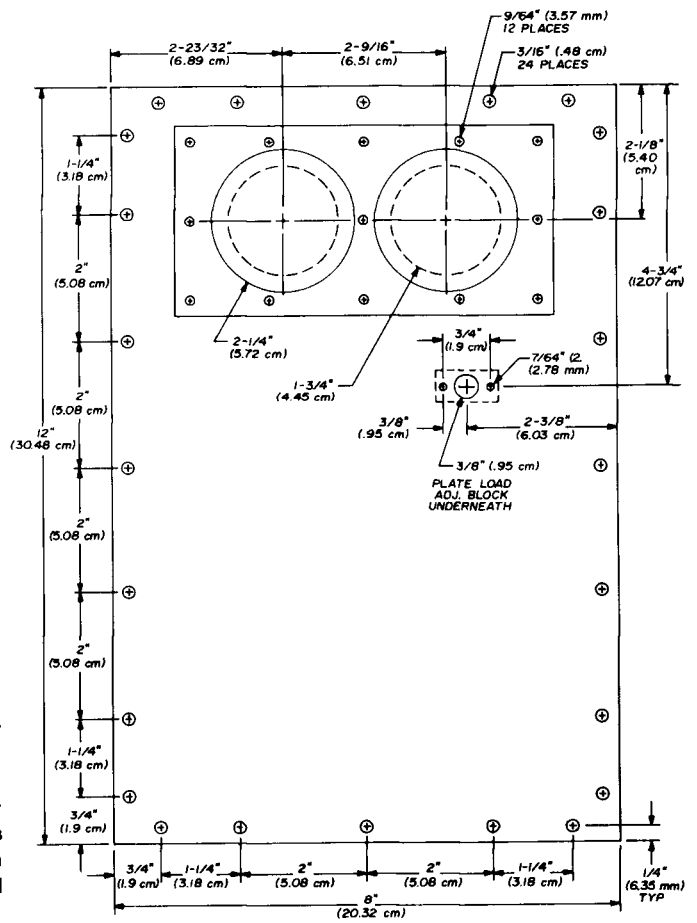

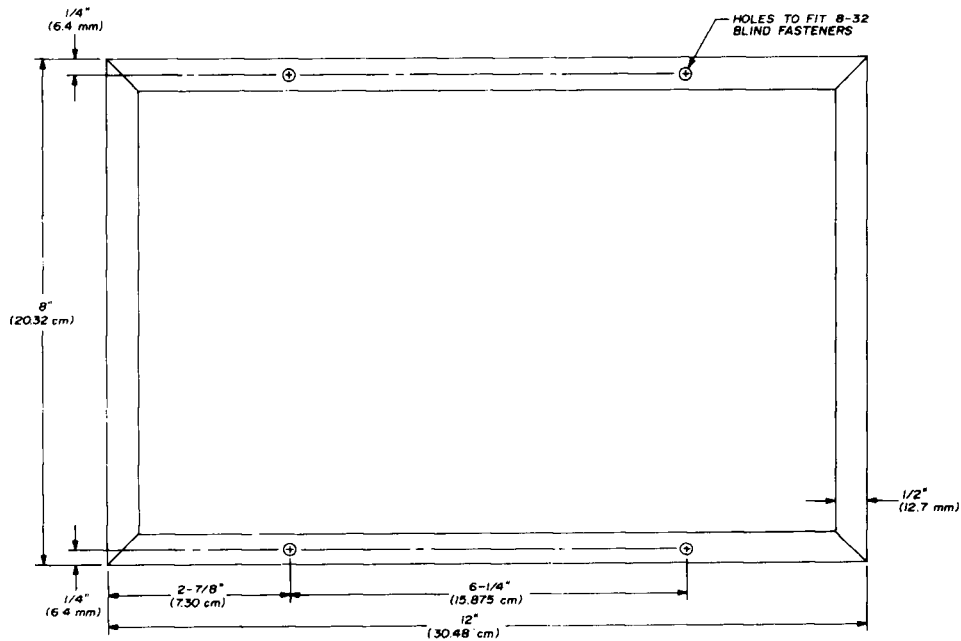


fig. 5. Top view of the upper chassis showing the top plate mounting holes. All holes are drilled to fit 8-32 (M4) blind fasteners.

for the chassis-mounted blower shows drilling and tapping for a Dayton 4CO1 blower.

Although chassis-mounted blowers have been used successfully, vibration can be a problem. The intake plate for hose-connected blowers is drilled for a Nutone plastic fitting type 366. This fitting will accept a hose with a 2-1/4-inch (5.7cm) inside diameter. For hose-connected blowers, use a blower

having 100 cfm free air rating into a 2-1/4-inch (5.7cm) aperture as a minimum. If 8930 tubes are used, the direct-mounted blower may be rated as low as 60 cfm into the same aperture.

Here are a couple of tricks to assure accurate drilling: lay the work out on masking tape which has been placed on the areas to be cut or drilled, and always use a 1/16-inch (1.5mm) pilot (starter) drill to

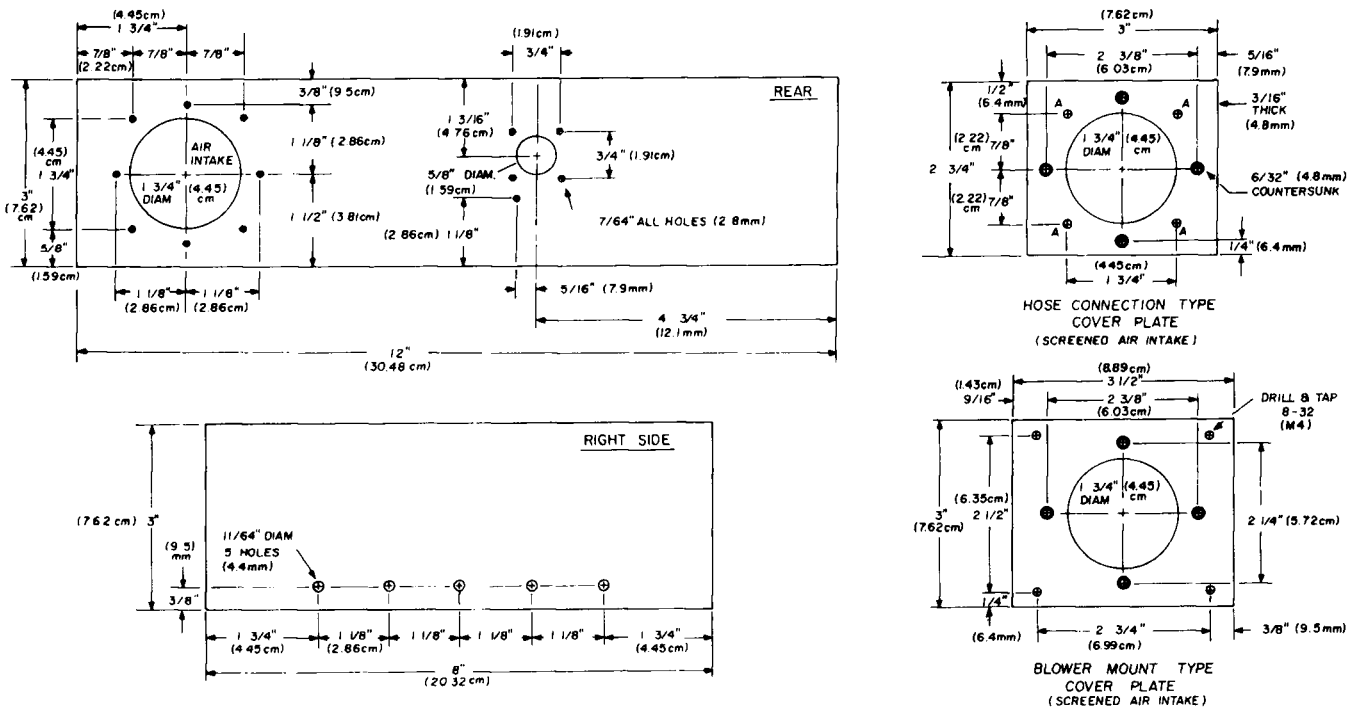


fig. 4. Top chassis for the two-meter kilowatt is made from 8 x 3 x 12-inch (20x7.6x30.5cm) aluminum chassis (Bud AC424 or equivalent). All holes not marked are 9/64 inch (3.5mm). Aluminum screening is mounted between vent cover plate and the air intake hole in the top chassis. Bottom view of the top chassis is shown in fig. 6.

center your holes. Although a drill press is convenient for all drilling operations, access to one is required only for the large holes through the 3/16-inch (4.5mm) thick material which requires the use of a hole saw.

To minimize alignment errors, one part with the 1/16-inch (1.5mm) pilot holes can be used as a drilling template for the matching parts. For example, use the top plate as a template for drilling the top of the upper chassis; use the vent plate as a template for the blower opening in the rear of the upper chassis.

Accuracy in drilling is essential, especially the socket holes, top plate vents, and plate line. These holes must line up nearly perfectly to assure alignment of the tubes, chimneys, and top vents.

It is best to use blind fasteners to secure the top plate to the upper chassis. Either 8-32 or 6-32 (M3.5 or M4) size is okay. The bottom plate may be fastened with self-tapping screws or blind fasteners with blind fasteners being the best choice. All other fastening is done with 6-32 or 4-40 (M3.5 or M3) screws, nuts, and lockwashers of suitable length.

The grid box is drilled and punched as shown in


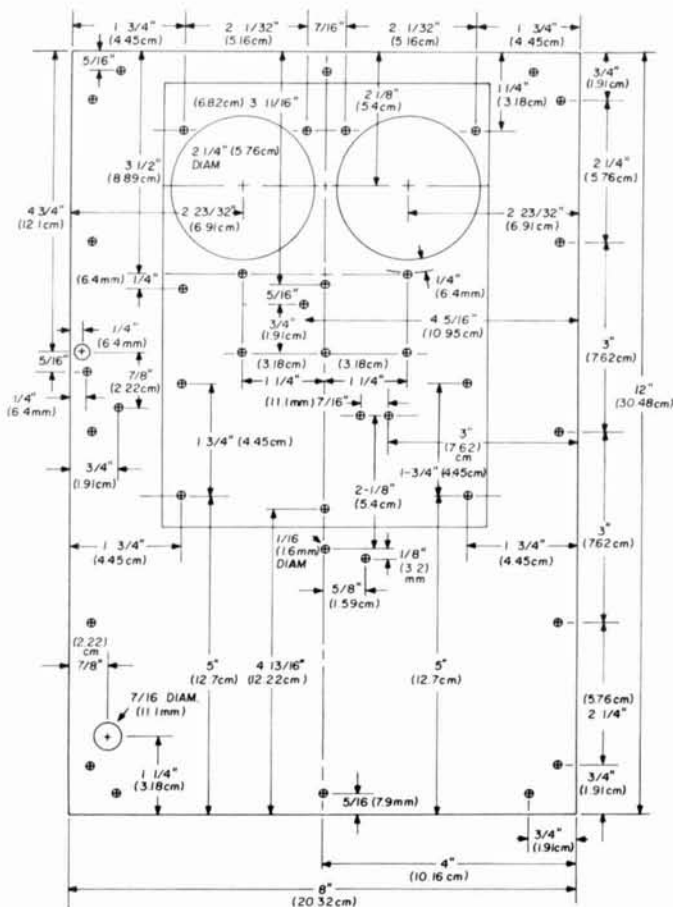


fig. 6. Bottom view of the upper chassis showing the layout of the tube cutouts and other mounting holes. All holes not marked are 9/64-inch (3.5mm) diameter.

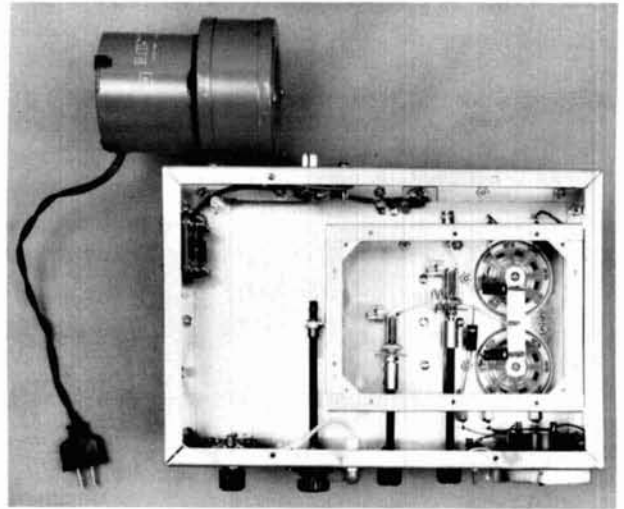

Bottom view of the stripline two-meter kilowatt showing the wiring of the grid compartment.

figs. 7 and 8. To ensure alignment of the socket holes with those in the upper chassis, the grid box pilot holes, including the pilot holes for the sockets, are drilled using the upper chassis as a template.

The top of the lower chassis is cut out as shown in fig. 9. This can be done with a nibbling tool, a small hand saw, or if you are very careful, on a table saw. The meter hole in fig. 11 is for a Calectro D10912 — a 0-1 mA meter with 100 ohms resistance. Any 0-1 mA meter not more than 2-3/4-inches (7cm) high can be used; the clearance for the meter behind the front of the chassis is 1-1/4 inch (3cm).

The holes in the rear of the lower chassis may be changed to suit your choice of power connectors. The MHV high-voltage connector (Amphenol) is recommended for the B + lead.

The vent holes in both the grid box and the lower chassis can be covered with screening by using a 1-1/8 inch (2.9cm) punch to cut the center out of the pieces punched from the 2-1/4 inch (5.7cm) socket holes. This provides a ring-shaped clamp which is drilled to match the holes in the chassis.

The bottom plate shown in fig. 8 does double duty as it is fastened to both the lower chassis and the grid box. First drill the pilot holes in the bottom plate and then, using it as a template, drill the pilot holes in the bottom of the lower chassis and the grid box. This completes the chassis work operations.

## plate line


Before starting assembly and wiring, do the cutting and drilling for the plate line, the grid line, and the output flapper. The plate line consists of two pieces of copper clamped together in a Teflon sandwich by clamping bars (fig. 12). The cutting and drilling dimensions are shown in fig. 13. Note that only two of the clamping bars are drilled and tapped.



The third bar is drilled only 9/64 inch (3.5mm).

The finger stock is soldered on the under side of the plate line; this requires a soldering tool in the 200-watt range. The finger stock is held in place, flush with the upper side of the line, with a Pyrex beaker or some other cylinder of heat-resistant material about 2 inches (5cm) in diameter (1-5/8 inch or 4cm for 4CX250s) which is wrapped with Teflon tape to provide a squeeze fit which will hold the finger stock in place while soldering. Note that the smaller piece of the copper plate line is equipped with self clinching nuts; as an alternative, brass nuts may be soldered to the copper plate. The Teflon support for the plate line at the tube end is made from 1/2-inch (13mm) diameter Teflon rod, drilled and tapped 1/2-inch (13mm) deep on each end.

Fig. 14 shows the various components of the plate tuning and output flapper capacitors. The plate capacitor consists of two sections: the flapper and a piece of copper on the same mounting block which provides the additional capacitance needed to resonate the line. Semi-hard beryllium copper seems to make the best flapper material; it also has the advantage of taking silver plating which, while not

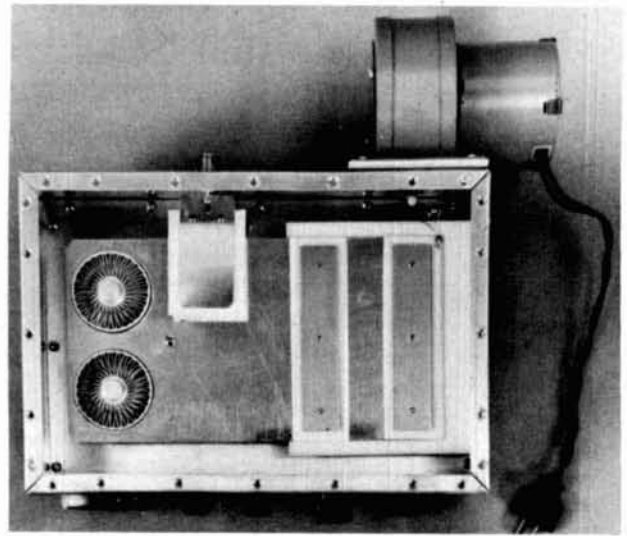

Top view of the two-meter kilowatt showing the plate stripline, the output coupling flapper (upper center), and Teflon sandwich at the cold end of the line (right).

essential, is desirable for all of the rf parts in both the plate and grid compartments of this amplifier.

Note the details for the aluminum support block in

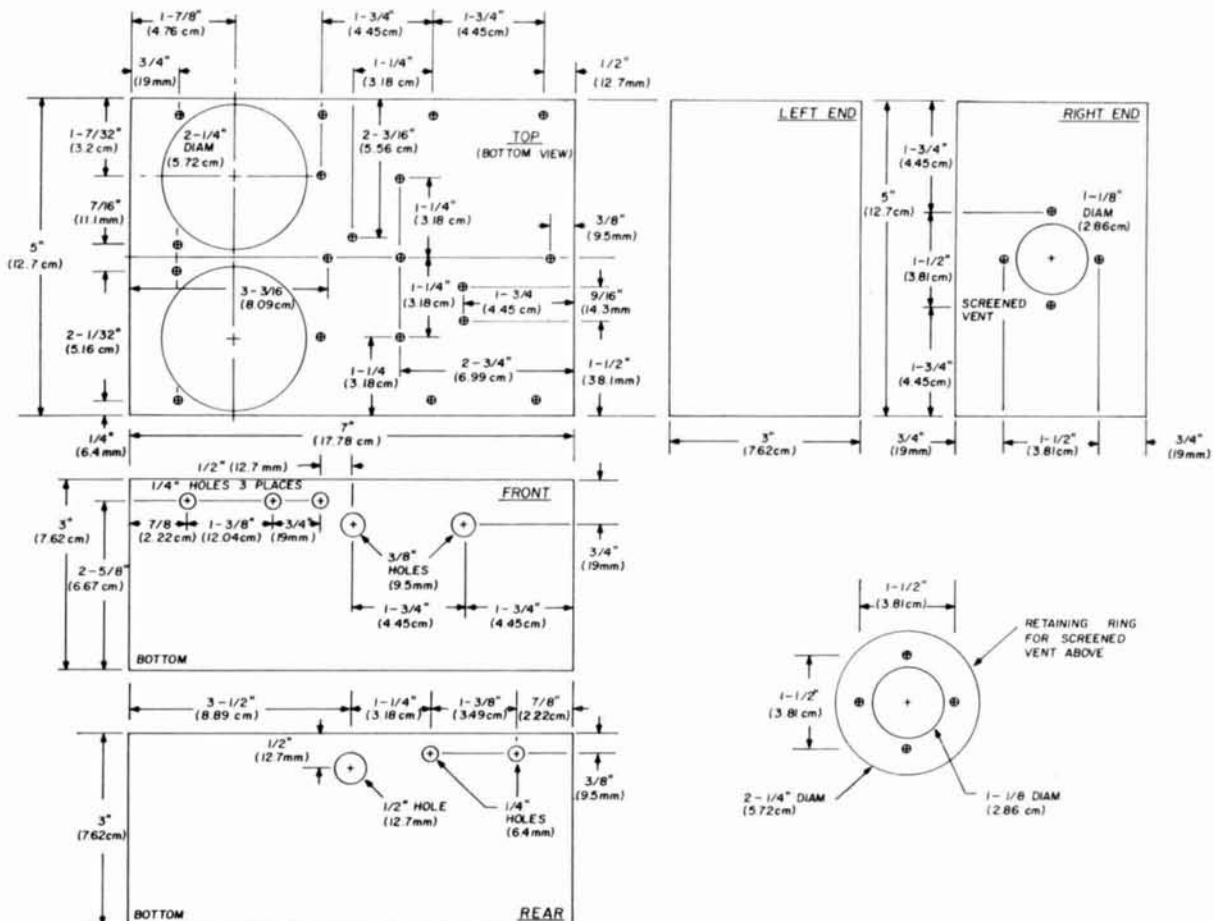


fig. 7. Construction of the grid box for the two-meter kilowatt. The aluminum chassis measures 5 x 7 x 3 inches (12.7x17.8x7.6cm) (Bud AC429 or equivalent). A piece of aluminum screen 2-1/4 inches (5.7cm) in diameter is clamped inside the box with the retaining ring. All holes not marked are 9/64 inch (3.5mm) in diameter.

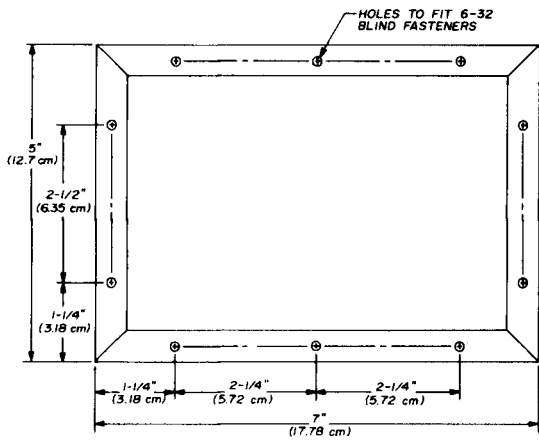


fig. 8. Bottom of the grid box and layout of the cover plate (Bud BPA 1519 or equivalent). The holes in the bottom of the grid box are drilled using the bottom plate as a template.

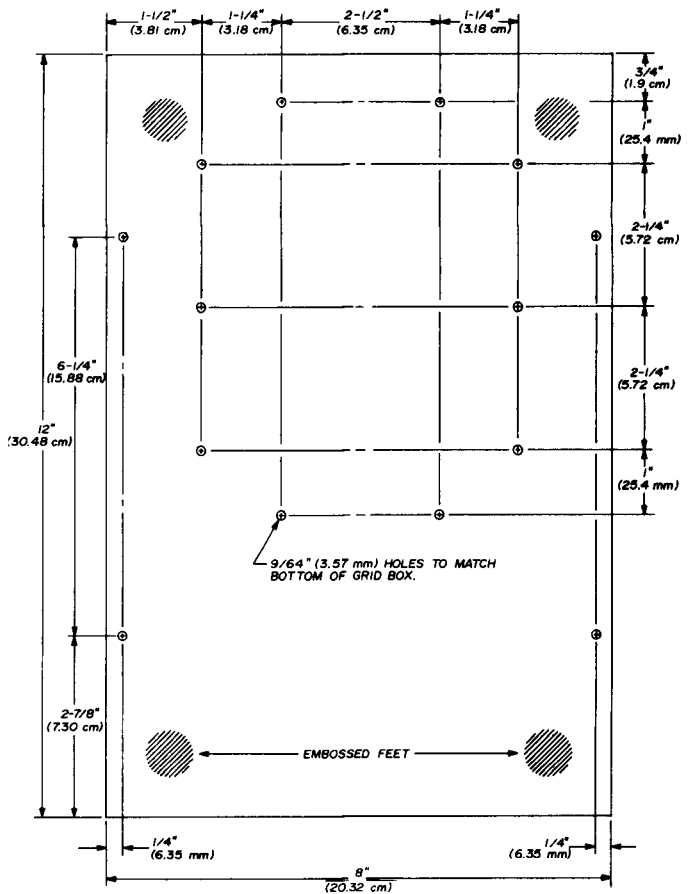


fig. 14; the flapper and fixed capacitor piece are mounted together with 8-32 (M4) hardware. The support itself is mounted to the chassis with 6-32

(M3.5) hardware. Dimensions for the bakelite shaft and bearing bracket for the plate flapper are also shown in fig. 14.

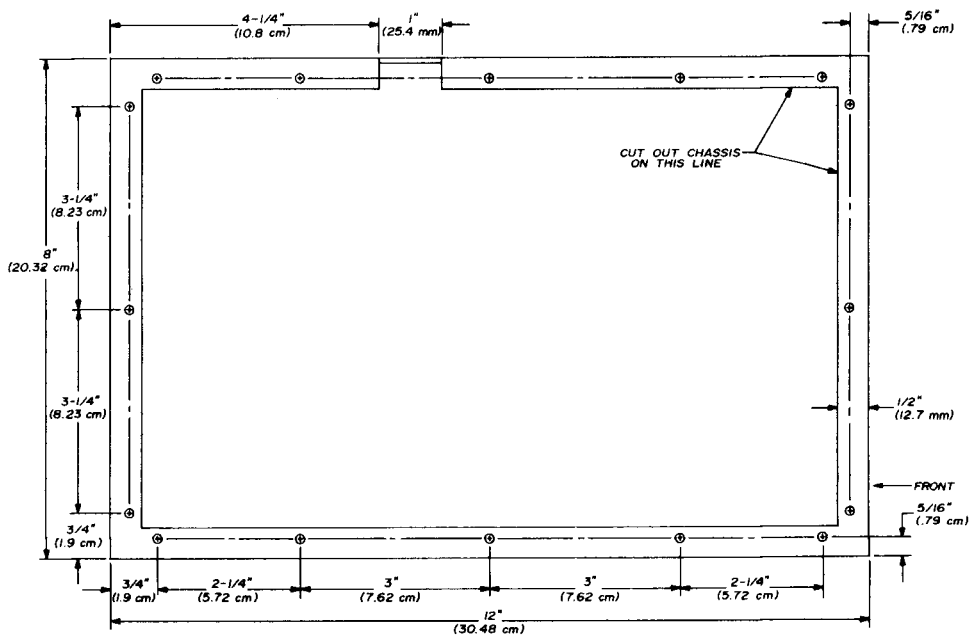


fig. 9. Top view of the lower chassis showing the large cutout made with a nibbling tool. Chassis is a Bud AC424 or equivalent. All holes are 9/64 inch (3.5mm).

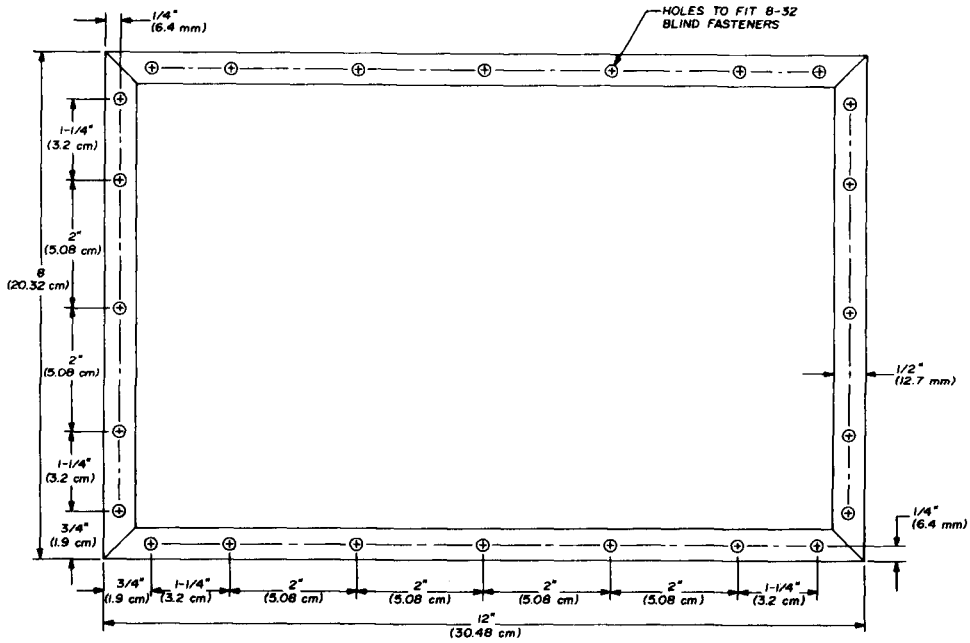


fig. 10. Bottom view of the lower chassis for the two-meter kilowatt.

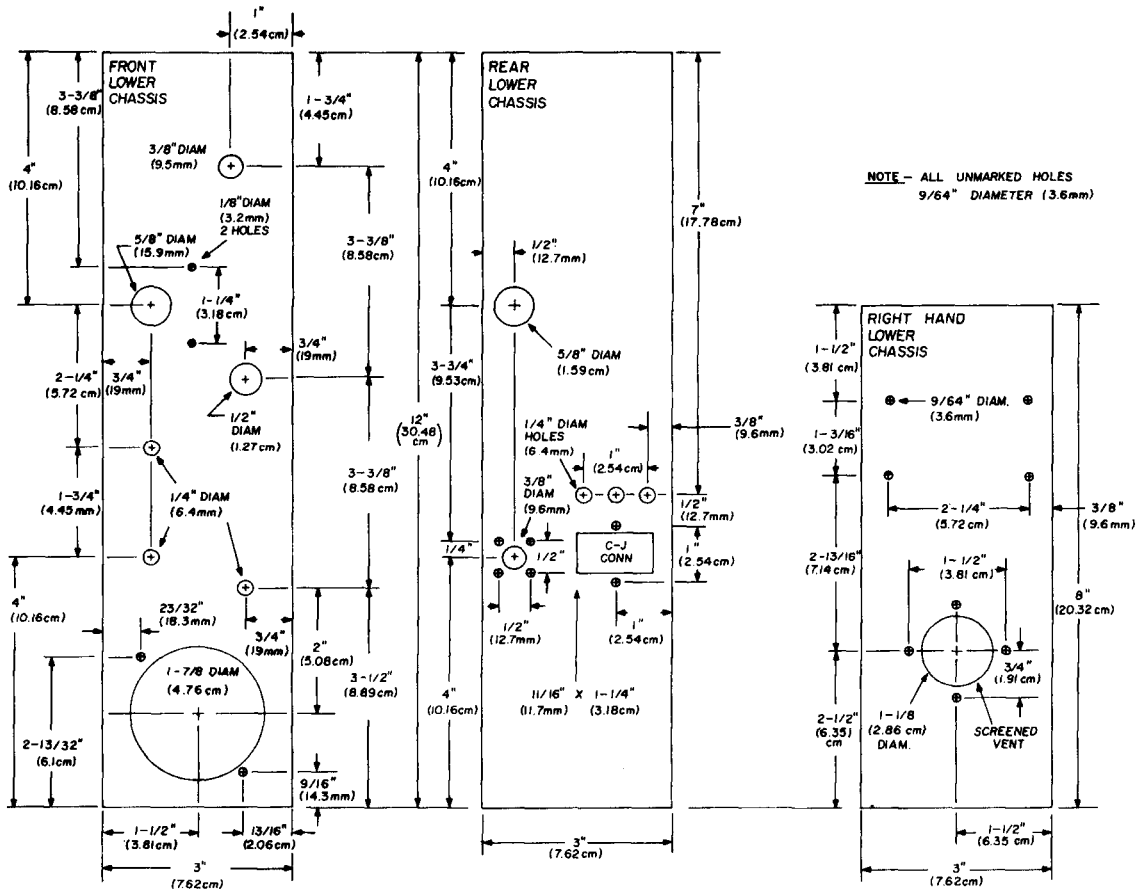


fig. 11. Layout of the front, rear, and right-hand side of the lower chassis (there are no holes in the left-hand side of the chassis). See fig. 7 for construction of the retaining ring for the screened vent. The meter hole in the front panel of the chassis is for a Calectro D109121 mA meter.


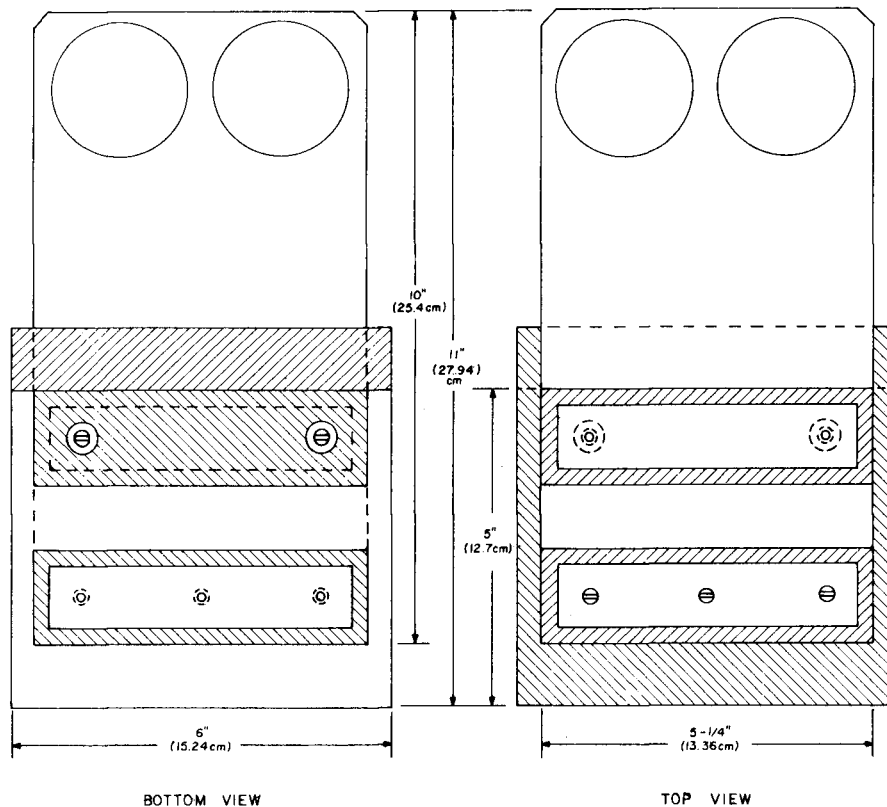


fig. 12. Construction of the plate line for the two-meter kilowatt. Material is .060 inch (1.5mm) copper (should be silver plated for best results). The shaded areas are 0.030-inch (0.8mm) Teflon sheet. Construction of the individual parts for the plate are shown in fig. 13.

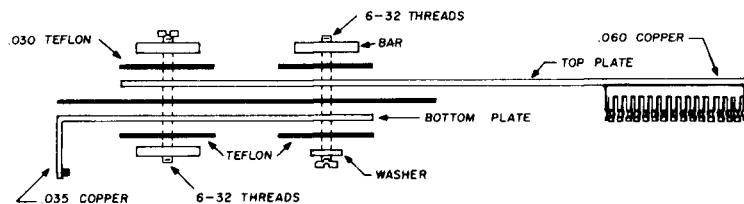

A slot is sawed in the inner conductor of a type-N coaxial chassis connector to accept the output flapper (see fig. 2) which is soldered into the position shown. The two holes in the output flapper serve to mount a piece of Teflon underneath the flapper which prevents contact with the high voltage on the plate line. The dimensions of these items are shown in fig. 14.

Also prepare the short piece of 1/4-inch (6.5mm) diameter copper tubing for the rf sampling assembly and the piece of 1/4-inch (6.5mm) diameter Teflon

rod for the rf choke form (fig. 14). A copper strap for connecting the grid terminals together, and mounting details for the grid butterfly capacitors and their respective shafts are shown in fig. 15.\*

### assembly

Begin by mounting the parts and wiring the lower chassis. Connect all leads except the five leads from the grid box and the cable to the rf sampling assembly. Keep the wires formed into a bundle in the corner of the bottom of the chassis. Run in this manner, the wires will show only at the points of termination and can be laced into a cable with wire ties after they are all in place. Use a color scheme such as black for ground, green for filament, yellow for grid, and blue for screen.

\*Many parts and assemblies for this two-meter amplifier are available from ARCOS, Post Office Box 546, East Greenbush, New York 12061; telephone (518) 477-4990. A price list will be furnished upon receipt of a self-addressed, stamped envelope.



Turning now to the upper chassis, install the rf sampling assembly as shown in **fig. 17**. Also install the high-voltage feedthrough capacitor at this time. Fasten the upper and lower chassis together with 6-32 (M3.5) 1/4-inch (6.5mm) long screws.

Install the bulkhead BNC input connector and the five feedthrough capacitors on the grid box. Install the grid box and the sockets, making certain that

socket terminals 1 and 3 are opposite their respective feedthrough capacitors. Run the five wires from the grid box to the resistor assembly board and the RG-174/U coaxial cable to the rf sampling assembly. This completes the wiring of the lower chassis.

Mount the butterfly capacitors (see **fig. 15**). Note that there are two holes in the area where the grid tuning capacitor mounts. The capacitor assembly is

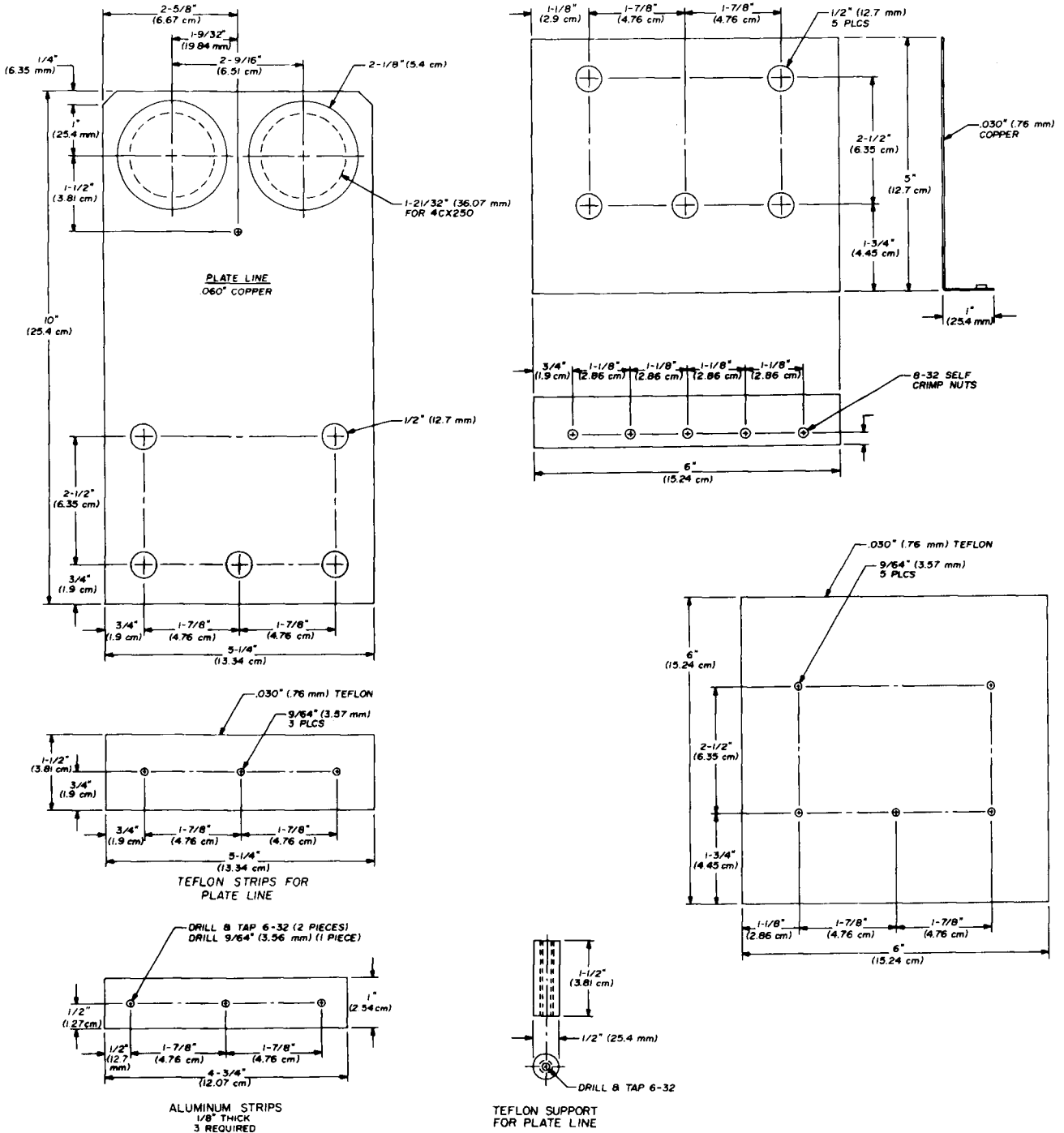


fig. 13. Plate line parts for the two-meter stripline kilowatt.

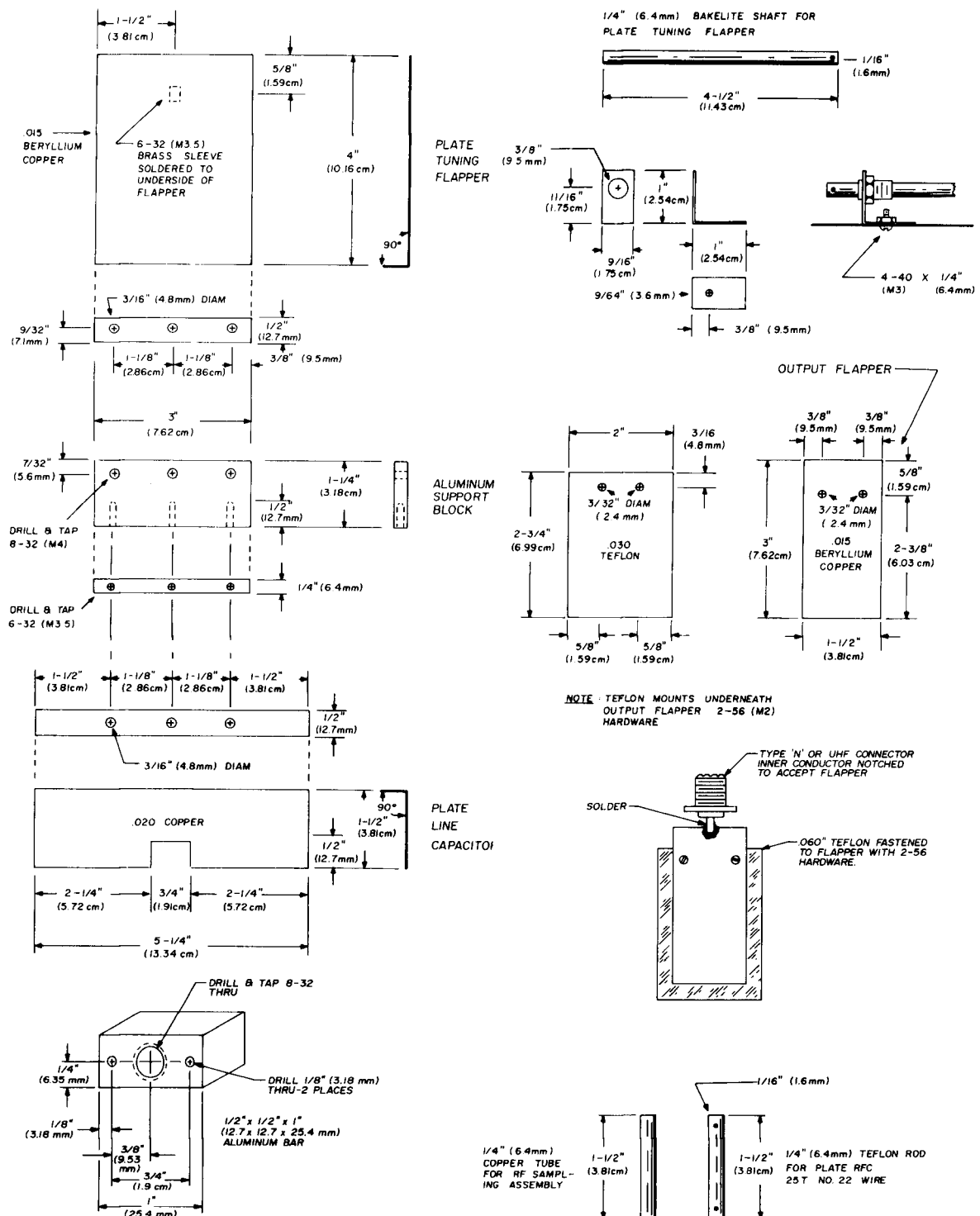


fig. 14. Construction of the plate line tuning and output flapper capacitors.

installed in the hole nearest the front of the chassis. Before mounting the tuning capacitor, put a spade bolt (with top cut off) in the rear hole. Tin the spade bolt. Now mount the capacitor assembly, adjusting the upper lug of the capacitor so it has some tension against the concave top of the spade bolt. Line up

the coupling shaft and tighten the nut on the spade bolt holding the capacitor. Make sure the capacitor turns smoothly.

Using a 200-watt iron, carefully solder the upper lug of the butterfly capacitor to the spade lug. This is a very important connection and becomes inacces-

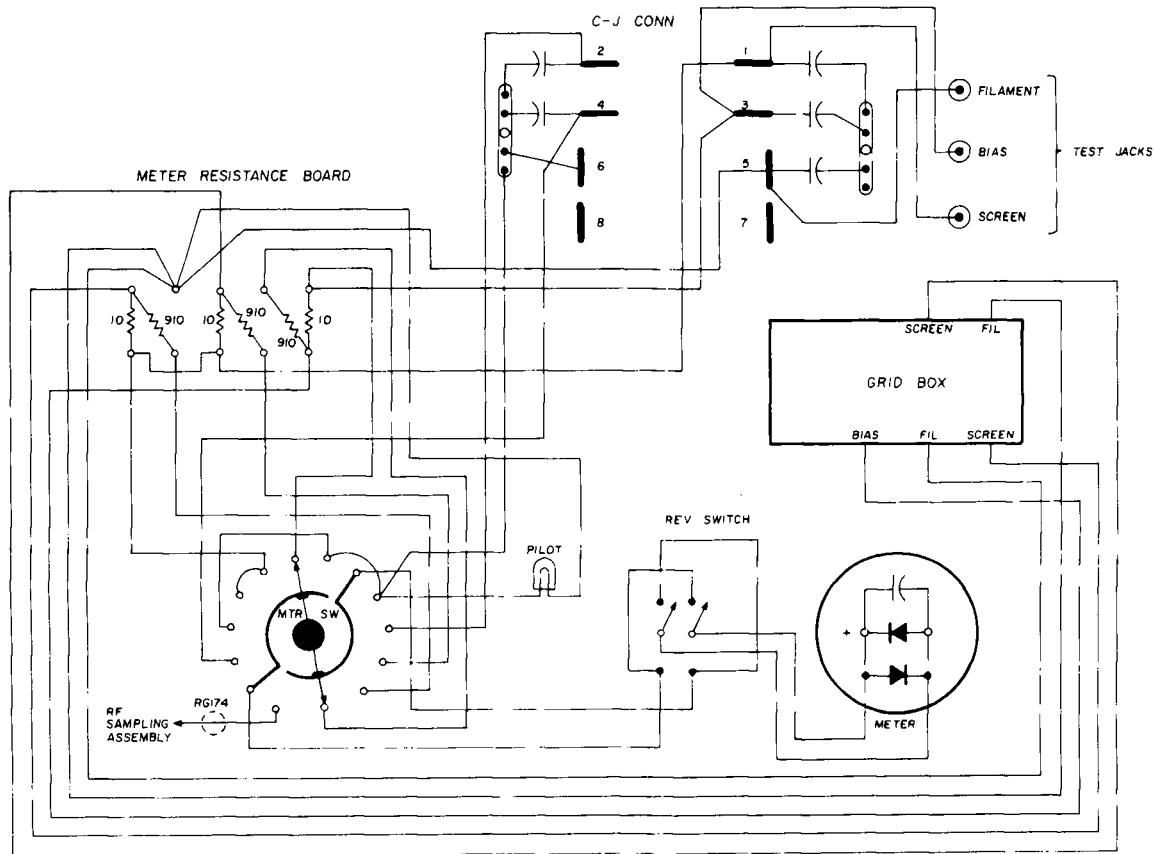


fig. 16. Wiring diagram for the two-meter kilowatt. Details of the rf sampling assembly are shown in fig. 17.

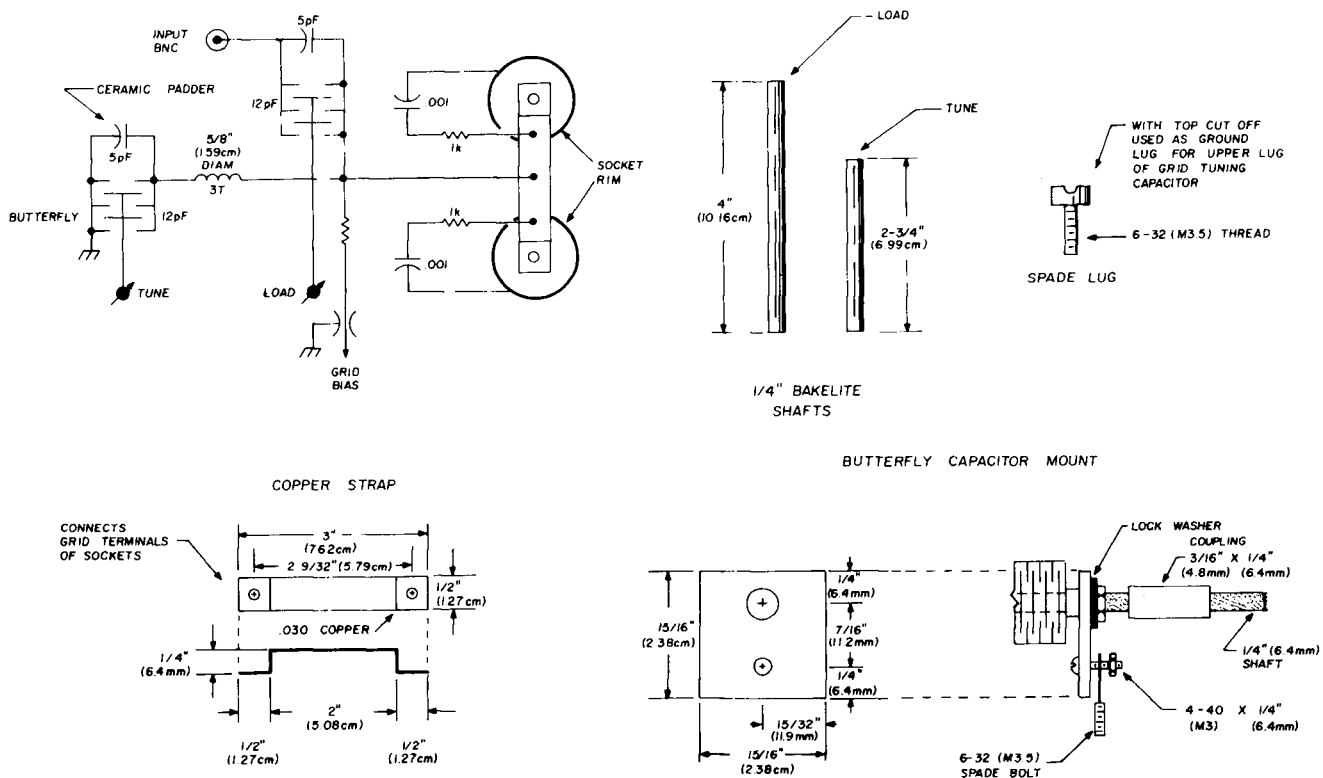


fig. 15. Grid circuit details for the two-meter stripline kilowatt.

sible later, so make sure it's a good solder joint. The other butterfly capacitor (loading) is not grounded so it is just a matter of making sure it operates freely. The balance of the grid circuit may now be installed.

Now mount the shaft bearing bracket and the bearing for the plate flapper tuning control. Install the plate tuning dial and the shaft. Make sure the shaft turns freely in the dial hub; this will facilitate placing the flapper tuning in the proper range. Install the Teflon support at the plate end of the plate line.

Assemble the two parts of the plate tuning capacitor to the aluminum support block and bolt the support block to the chassis. (The fishline control should be made fast to the plate tuning flapper before mounting the flapper assembly to the chassis, and the plate flapper positioned to about 1-3/4 inch (4.5cm) above the chassis.) Assemble the plate line (see fig. 12) and mount it to the chassis. Before tightening up the Teflon sandwich make sure that the large piece of Teflon between the plates is centered in the mounting holes.

Install the rf choke and the output flapper (which should be bent up to within 1/4 inch or 6.5mm of the top of the chassis). Position the rf sampling capacitor about 1/8 inch (3mm) away from the output flapper


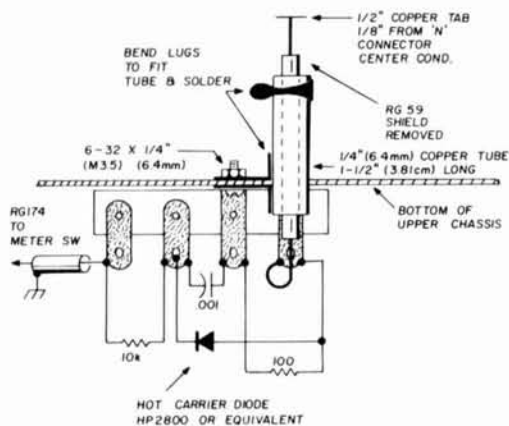


fig. 17. Side view of the rf sampling assembly. Adjust the position of the copper tab for approximately 0.6 mA on the meter at 600 watts output.

and type-N connector. Now assemble the top plate vent and the loading adjustment block. Fasten the top plate and bottom cover to complete the assembly of the amplifier.
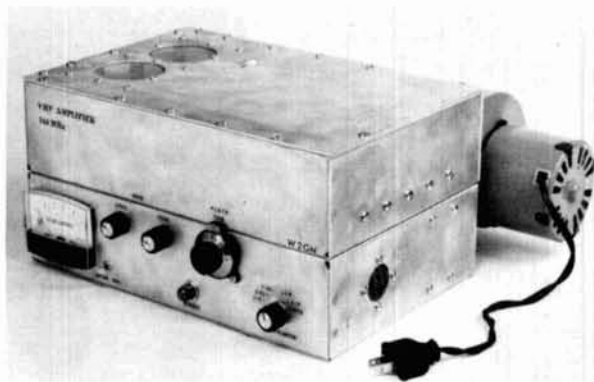
### power supply

A power supply suitable for this amplifier is shown in fig. 21. The voltage-doubling circuit offers a 1000 volt source for the screen dropping resistor. Since no grid current will flow with linear operation, the bias supply can be the simple zener regulated type



The entire amplifier is assembled in two mated chassis.

shown. The protective features of this supply include a high voltage fuse and a diode protective resistor in the transformer secondary lead. A delay tube maintains cutoff bias until the tubes warm up. The filament voltage is 8 volts at the transformer winding and offers ample control of the voltage at the sockets with the adjustable 1/2-ohm series resistor.

This power supply will deliver 2000 volts at 500 mA with a no-load voltage of 2200 volts. At 1 ampere the output voltage drops to 1850 volts. With a transformer weight of 30 pounds (13kg) the total weight of the unit is only 45 pounds (20kg). This is quite a relief from the 80 to 100 pound (35-45kg) power supplies of the past.

### test and check out

An inexpensive dummy load for a high power vhf amplifier can be set up with 100 feet or 30 meters (or more) of RG-8/U with a Heath Antenna at the end. This will stand up on 144 MHz for about ten minutes or so at 600 watts output before the cooling oil in the dummy load starts to boil. The driver for this amplifier *must* have an adjustable output control unless it is capable of less than 5 watts maximum output because the amplifier is very power sensitive; it is not possible to adjust it properly if it is over-driven.

After connecting the amplifier to the power supply

table 1. Typical operation of the two-meter stripline kilowatt using 8930 ceramic power tetrodes (grid bias = -77 volts, screen supply = 409 volts, idling current = 100 mA).

drive power	grid current	screen 1 current	screen 2 current	power input	power output
2 W	0	-6 mA	-6 mA	800 W	200 W
4 W	0	-8 mA	-10 mA	1000 W	400 W
8 W	-1 mA	+1 mA	+2 mA	1360 W	830 W

Plate voltage during these tests ranged from 2100 volts at 200 mA idling current, to 1700 volts at 830 watts output.

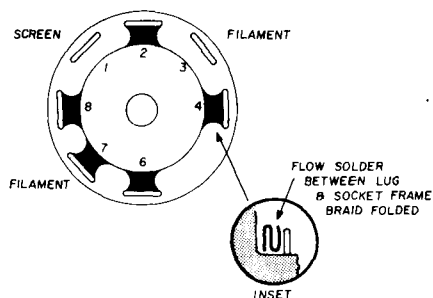


fig. 18. Grounding for the Eimac 620A socket. The 630A socket requires this modification only on terminal 7.

and making the usual checks of filament voltage, bias, screen voltage, and blower operation, establish an idling current of about 150 mA for initial tests. Applying a watt or so of excitation, adjust the grid circuit controls for a rise in plate current. Then resonate the plate circuit by observing power output. If the plate circuit will not resonate, change the range of the plate tuning flapper controls until the dial is mid-range for your chosen operating frequency.

The next step is to increase drive until the amplifier is at about 400 watts or so output with the loading screw about 1/8 inch (3mm) above the top plate. Now the grid circuit controls should be set for minimum swr toward the driving source. The reverse power will drop to an unreadable value. Once grid tuning is established, adjust the load control on the top of the amplifier for a compromise between maximum output and minimum plate current at an output level of 600 watts. Keep the loading on the heavy side.

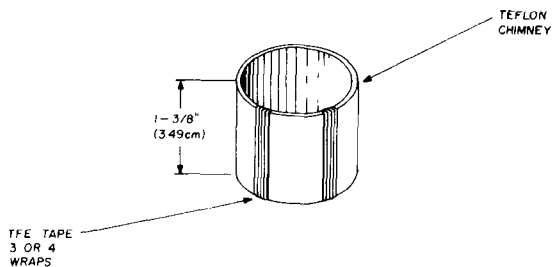


fig. 20. Tube chimneys for the two-meter kilowatt are made from 0.010-inch (0.25mm) Teflon, 1-3/8-inches (35mm) wide. Roll the Teflon for a tight fit in the top vent plate; secure with 1/4-inch (6.5mm) Teflon tape wrapped vertically around the roll. 12 inches (30cm) of Teflon is required for 4CX250s; 24 inches (60cm) is required for 8390s.

Once the proper setting for the load control is found, there should be no reason to change it unless you wish to operate the amplifier at a lower power level or with different voltages. Having set up the initial operating conditions, further tests and adjustments can be made for best linearity.

Check for blower operation each time the amplifier is turned on. If the air supply should fail, the solder on the plate line will melt and the finger stock usually springs out, grounding the plate supply and operating the breaker within about 30 seconds. The tubes survive but it is a messy job to repair the plate line.

## safety

Like any other piece of radio equipment operating at high voltages, this innocent looking aluminum box can be a killer — it is absolutely unforgiving of careless moves. Just to repeat the safety rules, disconnect the B+ line before taking covers off. Don't operate the amplifier with the covers off. If you must take a reading inside with the cover off, disconnect the power, connect the meter with well-insulated leads, stand back and take the reading *after* you have put the power plug back in. One hand in the pocket while you are testing is the time-tested rule

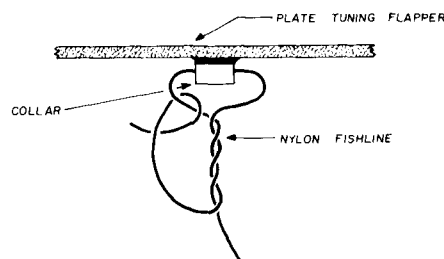



fig. 19. Knot for fastening nylon fishline to the collar on the plate tuning flapper, and to the tuning shaft. Pull the knot tight to prevent unraveling.

for staying alive. Another precaution in dealing with this level of rf power is to stay out of the path of the rf radiated from the antenna.
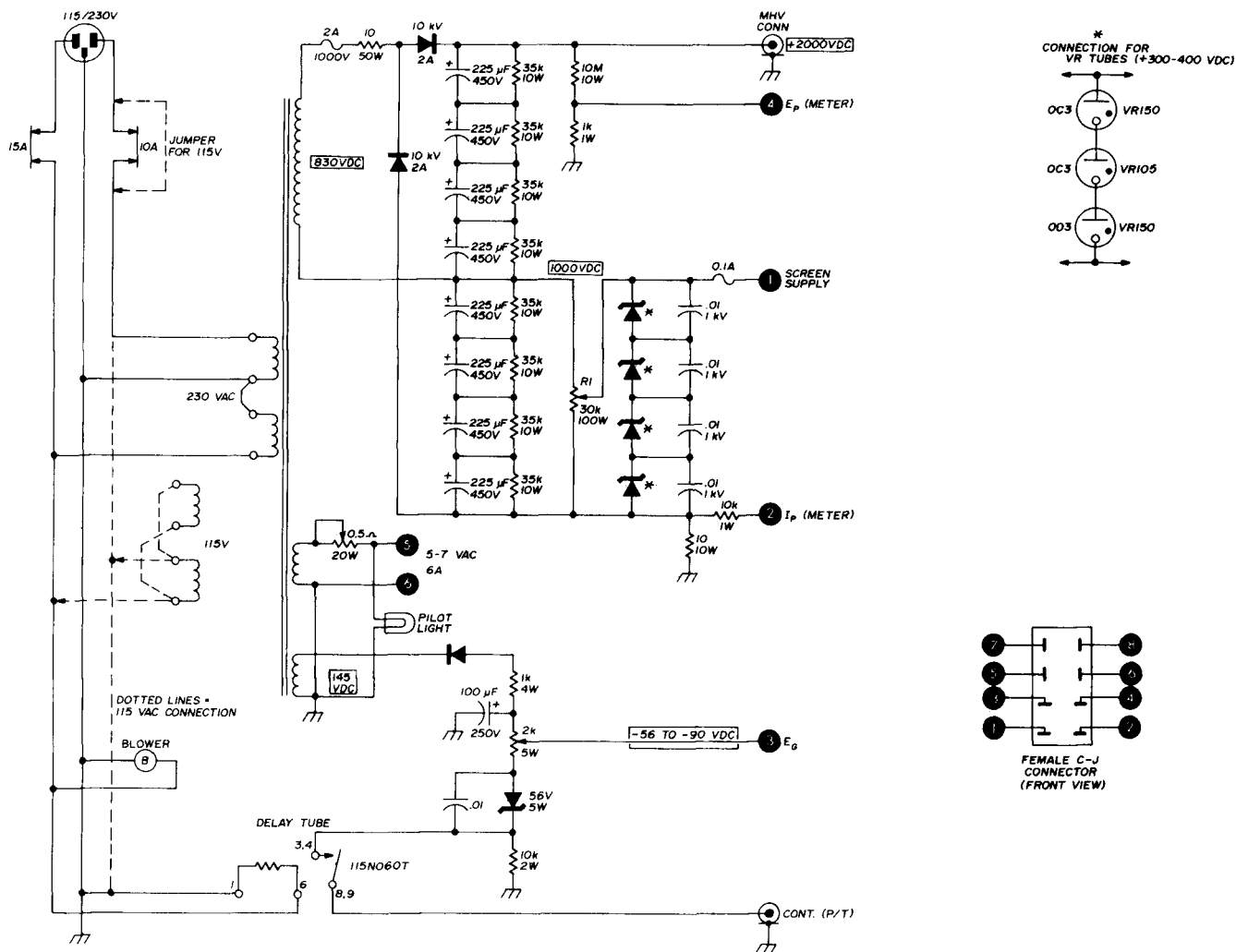
## operation

To adjust the amplifier for linear operation, perhaps the simplest setup is to use a directional wattmeter at both the input and the output. Set the idling current at 200 mA. Using the test values of 2, 4, and 8 watts drive, (see table 1) adjust the loading control and the plate tuning control for best linearity at the lowest value of peak plate current. When the proper adjustment is reached the power output will be approximately 200, 400, and 800 watts, respectively. These tests can be made at the bench and the adjustments will be valid for a 50-ohm antenna system with low swr.

For CW operation the bias can be set higher for an idling current of 100 mA or less, and the loading control and plate tuning optimized for best output at the least plate current. At 1 kilowatt input, 600 watts output is the objective. About 5 watts drive is required.



Voltage: no load, 2300 V; 500 mA, 2000 V; 1 A, 1900 V  
 Bias: -55 to -95 volts (no grid current)

Standby bias: -150 volts (P/T contacts open)  
 Weight: 45 pounds (20 kg)

fig. 21. Recommended power supply for the two-meter stripline kilowatt is rated at 1 kilowatt continuous duty, 2 kW PEP. Adjust R1 (30k, 100W) for 500 volts at the screen terminal with the zener diodes (or VR tubes) disconnected. Readings in boxes were taken at 1 kilowatt output.

The temperature of the exhaust ports can be checked by setting a candy thermometer on top of the amplifier in a nearly vertical position (put a pair of stiff wire legs on it). This does not give a reading of the temperatures at the tube seals, but is a relative indicator. Based on many hours of testing these amplifiers, a suggested limit for the exhaust air temperature read in this manner is 200°F (95°C). The tubes will not fail under continuous operation at this temperature limit. The 8930s will stay well within this level but the 4CX250s will tend to exceed it.

The filament voltage for the two-meter amplifier has been set at 6 volts on the assumption that the effects requiring 5.5 volts on the filaments at 432 MHz are not as significant at 144 MHz.

The grid current should be at zero or barely

negative for AB1 operation. Screen current will go negative (read with the meter reverse switch) to 10 mA more or less. It may become barely positive on modulation peaks. The screen voltage is regulated at 350 to 400 volts.

Once you have this amplifier on the air, properly adjusted, you will find that no further attention is required except perhaps an occasional tweaking of the plate tuning to match the antenna.

### references

1. Richard T. Knadle, Jr., K2RIW, "A Stripline Kilowatt for 432 MHz," *QST*, April, 1972, page 49; May, 1972, page 59.
2. Steve Gross, W9QJL, "A Parallel 4CX250B Amplifier for 144 MHz," *QST*, May, 1975, page 11.

ham radio



# TECHNICALLY SPEAKING, HEATH HAS THE BEST 2-METER AROUND.



**\$269<sup>95</sup>**

With Standard Microphone

Shown with optional MICODER™ installed

## Take our HW-2036 Frequency-Synthesized 2-Meter Transceiver for example

### Our circuit designs prove it

The HW-2036 offers true digital frequency synthesis for real operating versatility. No extra crystals are needed and there are no channel limitations. Advanced digital circuitry uses a voltage-controlled oscillator (VCO) that is phase-locked to a highly stable 10 MHz crystal-controlled reference. Double-tuned stages following the VCO in the receiver and transmitter provide clean injection signals. The result is a signal that has spurious output more than 70 dB below the carrier (see spectrum analyzer photos below). Additionally, the "add 5 kHz" function is accomplished digitally in the HW-2036 so that no frequency error is introduced.


### True FM

Careful attention to the transmitter audio circuitry and the use of true FM gives exceptional audio quality. A Schmitt-trigger squelch circuit with a threshold 0.3  $\mu$ V or less provides positive,

clearly-defined squelch action. Other design advantages include diode-protected dual-gate MOS FET's in the front end, IC IF and dual-conversion receiver.

### Outstanding Specifications

The HW-2036 puts out a minimum 10 watts and operates into an infinite VSWR without failure. Receiver sensitivity is an excellent 0.5  $\mu$ V for 12 dB Sinad making the HW-2036 ideal for use in crowded signal areas. We think you'd be hard-pressed to find a comparably-priced 2-meter transceiver that gives you the features and performance of the HW-2036.

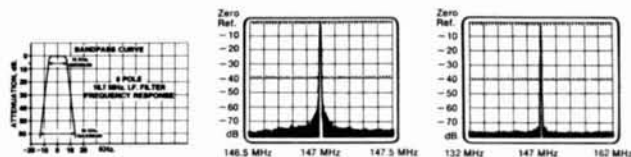

An 8-pole IF crystal filter greatly reduces adjacent channel interference.

Actual spectrum analyzer photos of the HW-2036 transmitter output operating at 147 MHz. Spurs within 20 MHz of carrier are down a full 70 dB!

*There's more for the Ham at Heath*

## FREE HEATHKIT CATALOG

Read about other fine Ham equipment and our wide variety of outstanding electronic kits — everything from lamp dimmers to color television is in our big FREE catalog.

**Send for yours today!**

Heath Company, Dept. 122-340, Benton Harbor, Michigan 49022

HEATH  
Schlumberger

Heath Company, Dept. 122-340  
Benton Harbor, Michigan 49022

Please send me my FREE Heathkit Catalog.  
I am not on your mailing list.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

AM-343 \_\_\_\_\_ Zip \_\_\_\_\_

# how to improve the accuracy of your frequency counter

Circuit details for  
a phased-lock time base  
and sensitive  
wideband probe  
that will improve  
the accuracy and usefulness  
of your frequency counter

**Most electronic equipment** requires a warmup period to allow them to stabilize and become ready for use, and the solid-state frequency counter is no exception; many instruction manuals caution that no critical frequency measurements should be made until the counter has warmed up for 30 minutes or more. If you have an accurate frequency standard, you can use the output of this standard to eliminate any warmup drift and to greatly improve the accuracy of your frequency measurements.

Some years ago, being interested in accurate frequency measurement, I built an oven mounted, tem-

perature controlled 100 kHz crystal oscillator, divided the frequency to 60 Hz, and used the amplified output to run a synchronous electric clock with a sweep second hand. I can set this clock to the exact time as broadcast by WWV and, with a little care, the crystal frequency can be adjusted so the clock keeps exact time. If the clock stays within one second of WWV time for a 12-day period, this means that the 100-kHz oscillator is accurate to one part in  $10^6$ ; if it can be held to one second in 4 months, this represents an accuracy of one part in  $10^7$ , or a little more than one cycle per second in 14 million. This accuracy can be easily translated to the time-base oscillator in your frequency counter.

The construction details of the 100-kHz standard

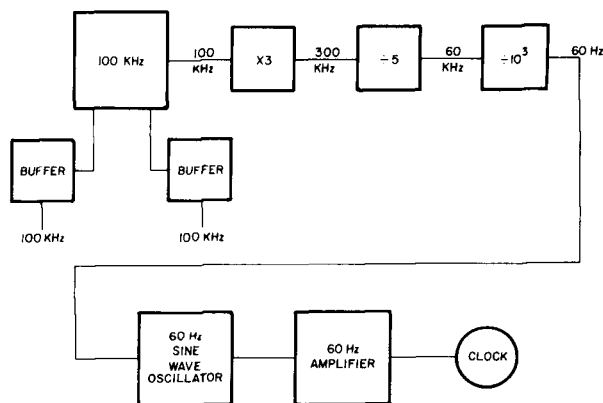


fig. 1. Block diagram of the 100-kHz frequency standard used by W1RF to drive a clock. This same basic circuit can be used to provide excellent time-base stability when used in a frequency counter.

By Clifford A. Harvey, W1RF, Box 88, Sturbridge, Massachusetts 01566


are beyond the scope of this article, but the block diagram of **fig. 1** shows the basic idea. The schematic of the crystal oscillator and associated count-down circuitry in my counter is shown in **fig. 2**. I used a 4-MHz crystal in the oscillator because I had a number of old 75-meter phoneband crystals on hand, and it was a simple matter, with a little careful grinding to move one up to 4 MHz. With a different division ratio, you can use a different frequency crystal.

The total capacitance in series with the crystal, necessary for setting it precisely to 4 MHz, consists of a fixed capacitor in parallel with a variable capacitor in parallel with a voltage variable capacitor, a varicap diode, or in my case, a silicon rectifier diode. The control voltage for this diode is developed by a Motorola MC4044P phase frequency detector and associated amplifier and filter. As shown, the 4-MHz signal is divided by four in a 7473 IC, and further divided by 10 in a 7490; the output is at 100 kHz. Part of this output is taken off through a 330-ohm resistor

and the main output being further divided by additional 7490s (down to 1 Hz in my counter).

The output from the 100-kHz buffer is less than 0.5 volt, so I had to provide additional gain with Q1 so U2A would saturate properly. There are hundreds of transistor types which can be used for Q1, Q2, and Q3; the ones I used came from surplus board assemblies so the type numbers are unknown.

A good way to select proper component values is to put an oscilloscope probe on pin 1 of the MC4044P and adjust C3 and R1 for a symmetrical square wave with clean leading and trailing edges. Capacitor C3 in my unit is 68 pF; R1 is 300k. These values will vary, depending on the types of NPN transistors you use. The 470-pF capacitor from the collector of Q2 to ground was required in my circuit to remove a high-frequency oscillation appearing on the leading edge of the square wave. Gates U2B, U2C, and transistor Q3 form a lock indicator circuit; when the 4-MHz crystal oscillator is locked to the 100-kHz standard,

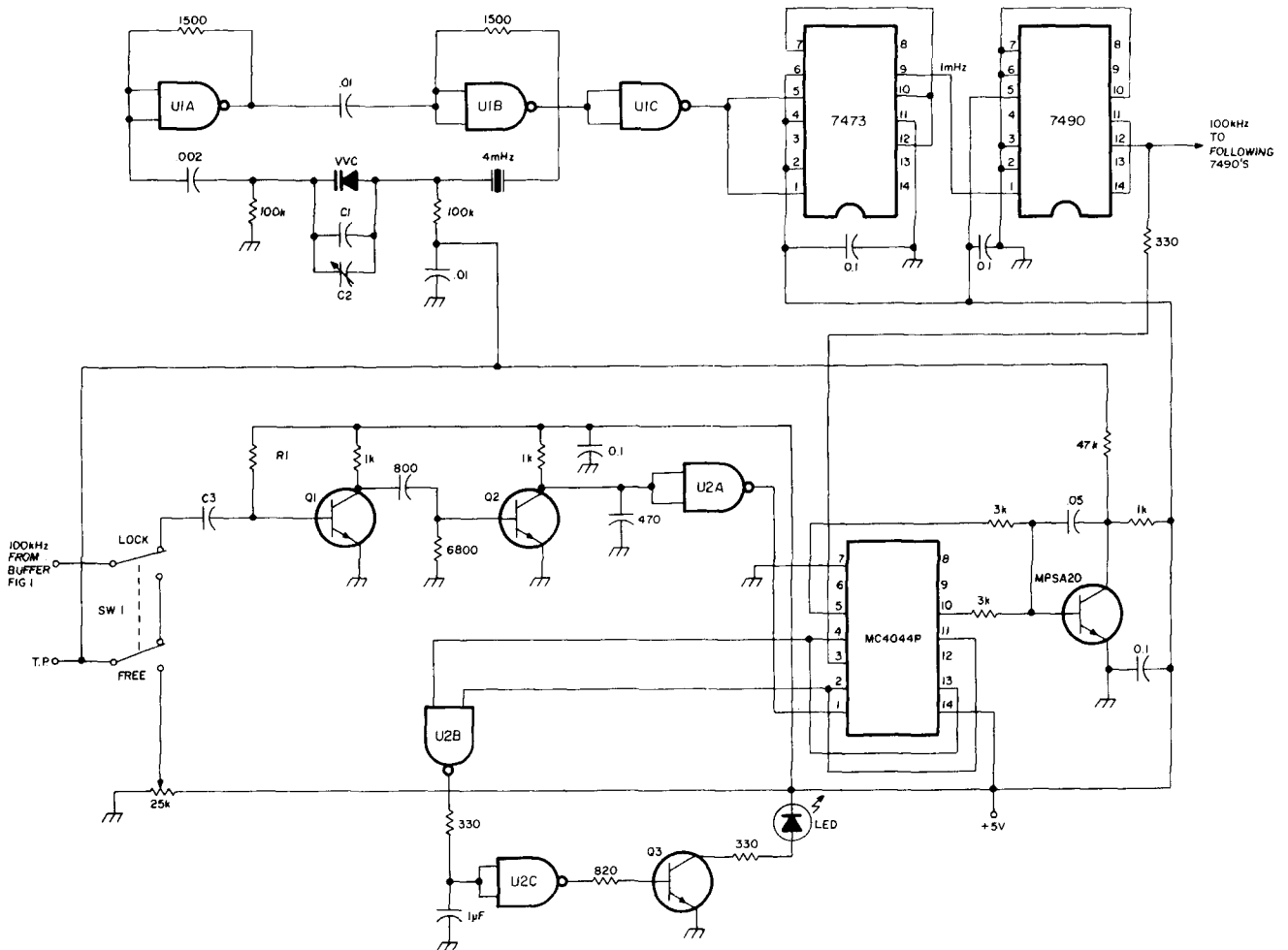

**fig. 2.** Circuit diagram of the phase-locked frequency standard. The author used a 4-MHz crystal, but other frequencies are possible if the division ratio is changed accordingly. The oscillator circuit is phased locked to the output of a high-stability 100-kHz frequency standard (see fig. 1). U1 and U2 are SN7400s.

the LED will light. Don't forget that the LED is a diode and will light only when properly connected into the circuit.

Switch S1 is helpful in initially setting up the circuit, and allows the counter to be used for normal accuracy readout anytime it is not necessary or desirable to have it phased locked to the frequency standard. With S1 in the *free* position and a vtvm connected to test point TP, set the 25k pot so the meter reads about 3 volts. With C2 set at about the mid-capacitance position, select a value for C1 such

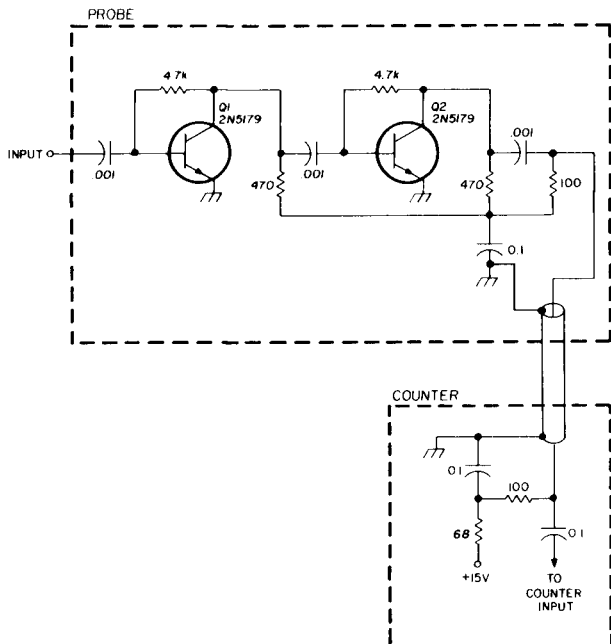


fig. 3. Rf probe for frequency counters which greatly increases sensitivity at the higher frequencies. Power for the probe is provided through the coaxial input cable.

that the crystal oscillator is very nearly on the correct frequency. In my circuit C2 is a 5-35 pF trimmer set for about 20 pF, and C1 is 20 pF.

With the 100-kHz standard connected and S1 in the *lock* position, the LED should light and the vtvm should read somewhere between 1 and 5 volts. C2 should now be readjusted for a vtvm reading of about 3 volts. If the counter is now connected to read out the frequency of a stable external oscillator, note that varying C2 will not change the readout but will only vary the control voltage. If the LED does not light and no lock is obtained regardless of the setting of C2, the vtvm will probably read 5 volts; this indicates that the crystal is too far off frequency to be brought in by the varicaps, or the varicaps do not have enough range.

In my counter, running free and measuring a 5-MHz external oscillator, varying the 25k pot from zero to 5 volts changes the readout from 4 999 980 to

5 000 184 Hz. Using a silicon power diode as a varicap is somewhat questionable as some diodes have much greater capacitance range than others of the same type. If you run into trouble, a Motorola MV-series varicap should be tried (such as MV2110).

With the time-base oscillator locked to a good frequency standard you can be sure that both the accuracy and the stability of your counter is greatly improved. Some years ago, after completing a similar phase-locked counter, I set up the counter to read out the frequency of my transmitter exciter. One evening I tuned in on the ARRL Frequency Measuring Test. Due to skip conditions I could hear only two of the transmitted frequencies, but it was a simple matter to zero beat W1AW with my exciter and read out the frequencies. When the actual transmitted frequencies were published a month or two later, I was pleased to note that of the two readings I submitted, one was precisely as published and the other was 1 Hz off! If you want to get to the top of the list in a Frequency Measuring Test, all you need is a phase-locked oscillator in your counter, and a little luck!

Another useful accessory to my counter is a probe based on the broadband amplifier described previously in *ham radio*.<sup>1</sup> One trouble you run into when measuring high frequency signal in low-power circuits is the difficulty of obtaining sufficient voltage to actuate the counter. If you connect the circuit under test to the counter with coaxial cable, capacitance of two or three feet (1 meter) of cable can produce a relatively low impedance, and an unwanted load. The broadband amplifier appeared to be a solution to the problem, but I disliked hooking up the amplifier and associated power supply every time I wanted to use it so I modified it slightly and built it into a probe. The simple modification shown in fig. 3 allows the amplifier to be powered over the same coax that carries the amplified input.

If you have 15 volts at about 20 mA available in your counter to power the amplifier, the probe is very convenient to use. If you are handy with a lathe the probe can be made to look quite professional; mine is 3/4 inch (1.9cm) in diameter and 5 inches (12.7cm) long. With the probe I need only 5 millivolts at 40 MHz, 2 millivolts at 2 MHz to operate my counter. Since the center conductor of the coax connector on the counter is carrying 15 volts, be sure to use an external isolating capacitor if a direct connection is made to the circuit under test.

## reference

1. Randall Rhea, WB4KSS, "General-Purpose Wideband RF Amplifier," *ham radio*, April, 1975, page 58.

ham radio

# syllabic vox system

## for the Collins S-Line

Full break-in capability  
is featured with  
the Collins S-Line,  
using an array  
of switching transistors

**Rapid, silent switching** of transmitter-receiver functions will always improve a station's "on-the-air" effectiveness. By eliminating the slow dynamic operation of mechanical relays, caused in part by conventional vox systems, the operator may then enjoy a higher quality of communications. There never will be a situation of *doubling* with another station because you can be interrupted at any time with the help of this high-speed switching network.

Recently Ray Hitchcock, W6RM,<sup>1</sup> updated my earlier vox system<sup>2</sup> by using logic circuitry which offered many advantages over the older style. This article concerns itself with the conversion of his syllabic vox for the Drake equipment to the Collins S-Line. When he and I are using ssb, the conversation is essentially the same as using the telephone. If a visiting operator were to use the station, he could use the equipment in a normal fashion and not be aware of any modifications except that he would be hearing between his transmitted syllables and code elements. There are no external devices which require adjustment nor is defacement of the equipment necessary. The 5 Vdc power supply (fig. 1), is housed in the speaker cabinet. The original vox controls (*vox gain* and *anti-vox*) perform the same basic functions as previously. The *vox delay* circuit is rendered inoperative by this modification.

Unless two separate antennas are used, the most critical portion of the syllabic vox system is at the antenna change-over location. W6RM has refined the diode antenna switch into a well designed, trouble-free device and suggests the appropriate name, "Diode-Biased Antenna Gate." The actual switching takes place 200  $\mu$ s before the rf appears and is accomplished by forward biasing the diode with a dc voltage. No rf rectification occurs as in former T/R switches.

Directions for initial setup and the logic theory of the system are given in W6RM's paper; you are urged to consult this excellent article. One serious problem arose with the 32S-3 conversion: an intolerable audio oscillation occurred with only a moderate degree of vox gain. The vox was thrown into activation making correction of this defect mandatory.

You will note differences around the LM3900 (U1A), see fig. 2, as compared to the schematic diagram in W6RM's article. The input to the LM3900 comprises a highpass filter, and the 74122 (U2) delays vox activation for 2.1 milliseconds.

The syllabic vox amounts to a very high speed vox without the use of relays. In the original relay circuitry each set of contacts opens and closes a single circuit. In the new vox, each set of contacts has been replaced by a switching transistor. The circuits are coordinated so that each syllable or code element controls the transmitter-receiver functions. All switching is done in the proper sequence.


### construction

The technique that I followed was point-to-point hand wiring with number 22 AWG (0.6mm) tinned wire. Teflon sleeving is used to cover this wire where required. To facilitate the connections to the innumerable power and ground points, the periphery of the usable portion of the board is enclosed by two wire loops, each terminating at the rear of the board. A solder lug is bolted to the board at each termination point (see photograph). Solder lugs are bolted to

By H. Rommel Hildreth, MD, W0IP, 15022  
Claymoor Court, Chesterfield, Missouri 63017

each point where interconnecting cables are attached. The 6.3 Vac jack, at the left rear, supplies the power to the 5 Vdc source (the spare jack may be used for the 5 volt input).

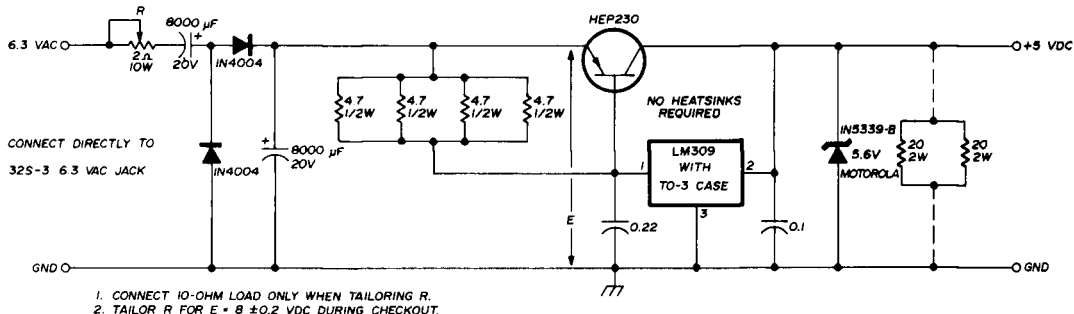For the most part, the general layout follows that of the schematic diagram. The 2-mH choke is fastened to the rear of the bfo using one of the already available screws.



1. CONNECT 10-ohm LOAD ONLY WHEN TAILORING R.  
2. TAILOR R FOR E = 8 ± 0.2 VDC DURING CHECKOUT.

fig. 1. Power supply for the integrated circuits. The 6.3 Vac is obtained from the connector on the rear panel of the transmitter.

A second circuit board was mounted at the opposite end of the chassis as shown in the photograph. It holds the high-voltage transistors and is convenient to the high-voltage chassis connections. The 100k resistor becomes so hot that it must be elevated above the board for ventilation. All other components are barely warm to the touch after a prolonged operating period.

### diode-biased antenna gate

A metal box measuring 1-1/2 x 2 x 2-3/4 inches (38x51x70mm) houses the gate. Two coax fittings are mounted at the ends and two phono jacks are on top of the box. The coax fittings are connected by RG-8/U coaxial cable cut 2 inches (51mm) longer than necessary. The vinyl is removed, leaving the center 1 inch (25mm) of the braid unexposed. The wire sheathing is skinned back over the center and the wire is cut to fit into the notches after removing a bit of the foam, center insulation. Solder the wire. At one end solder one terminal of the 50 pF capacitor after covering the wire with Teflon. Then cover both bare ends with tape so that when the shielding is brought forward it may be soldered to lugs in the screws holding the fittings and thus provide proper rf shielding. The remaining parts for the gate are easily placed within the box.

The Collins coax fitting did not lend itself well to rigid mounting, so the shortest possible length of coax was used. The entire length, including fittings, was only 4 inches (100mm).


The two gates shown by W6RM are to be used when the linear amplifier is placed at a distance from the exciter. Note that the relay in each box

automatically places one or the other of the gates into the circuit. The relays play no part in the rf operation.
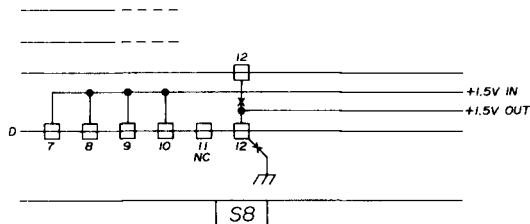
### 32S-3 modifications

Upon inspection of the chassis when placed upside down, the vox relay is at the left center. The drawing (fig. 3) will help identify the contacts of the

relay. Attached to the front panel, in front of this relay, is the *emission* switch (S8). Wafer D is the wafer closest to the front panel. At its top (when upside down) is terminal 12 of wafer D with a connection to terminal 12 of wafer C. Terminal 11 is unused. Terminals 10, 9, 8 and 7 continue to the left.



1. At section 2 of the vox relay disconnect the lead to the antenna relay from the normally open, non-movable contact.
2. At section 4 of the vox relay disconnect the lead to ground at the movable contact (later this lead will be used to ground the several cable shields which converge in this region). Next, connect the circuit board extension lead labelled "Mute Line" to the movable contact.
3. At section 3 of the vox relay connect the circuit board extension lead labelled "Mixer Hold" to the movable contact.
4. At section 1 of the vox relay connect the circuit board extension lead labelled "+ 270 V" (non-movable contact).
5. At the movable contact of section 1 of the relay connect the circuit board extension lead labelled "+ 275 V".



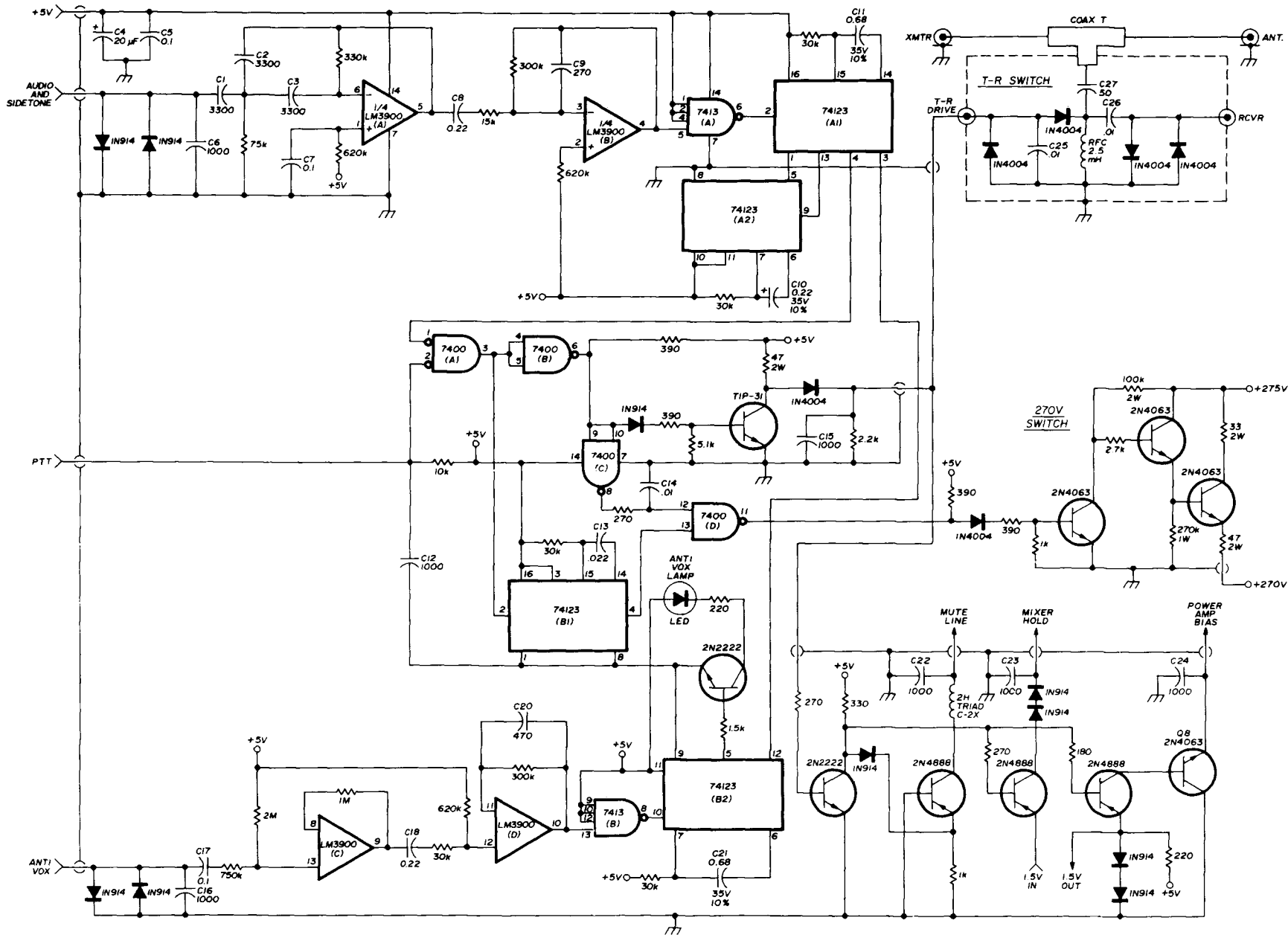


fig. 2. Schematic diagram of the control circuitry for the syllabic vox system. CR4-CR7, CR9, and CR10 are 1N4004 or equivalent diodes; all others are 1N914 or equivalent. The rf choke is a 2.5 mH, 200 mA transmitting type. All resistors are 1/2 watt, 10 per cent, unless otherwise specified.

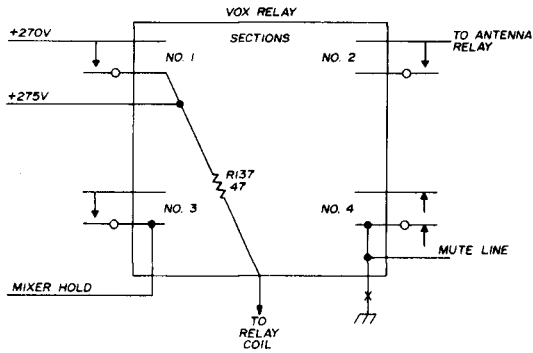


fig. 3. View of the vox relay in the transmitter with the chassis upside down.

6. One end of the 47-ohm, 2-watt resistor is connected to a relay coil terminal. The opposite end of the resistor is attached to the movable contact of section 1.

7. Remove the knobs from the vox and anti-vox controls. Also, remove the nuts so that the terminals of these potentiometers may be reached.

8. At the movable contact of the PTT switch (S10), connect the circuit board extension lead labelled "PTT", (fig. 4A).

9. At the wiper of vox gain control R74, connect the circuit board extension lead labelled "Audio and Sidetone".

10. At the wiper of anti-vox control, R85, connect the circuit board extension lead labelled "Anti-Vox".

11. Remove tubes V10, V14, and V12 since the high frequency oscillator of the receiver is ordinarily not used. This reduces the load on the power transformer.

12. Disconnect the plate lead to terminal 1 of V11.

13. Disconnect the lower end of R87 (470 ohms) from the PTT line. This resistor is near S8.

14. Disconnect the lead from the two parallel 2-watt resistors, R89 and R112. These two are also near S8, and alongside R87.

15. At S8, disconnect the lead between terminal 12 wafer D and ground. Also open the lead between terminals 12 of wafers D and C, (fig. 4B).

16. At terminal 12 of wafer D connect a circuit board extension lead labelled "+ 1.5 V Out".

17. At the bus wire connecting terminals 7, 8, 9 and 10, wafer D, connect a circuit board extension lead labelled "+ 1.5 V In".

18. Disconnect the lead to the antenna relay jack. Connect a circuit board extension lead labelled "Power Amplifier Bias" to the antenna relay jack.

19. At the vox relay, ground the several sheaths earlier mentioned. Use the ground lead already disconnected from the "Mute Contact".

20. Remove the cover of the rf section. The five screws are removed to reach the antenna relay contacts.

21. Short the antenna relay rf contacts with a short piece of wire (the rf side is near the pi network).

22. Disconnect the lead attached to the jack marked "Receive Antenna". This lead is now the rf output.

### 30L-1 modifications

The Collins 30L-1 linear amplifier requires a slight

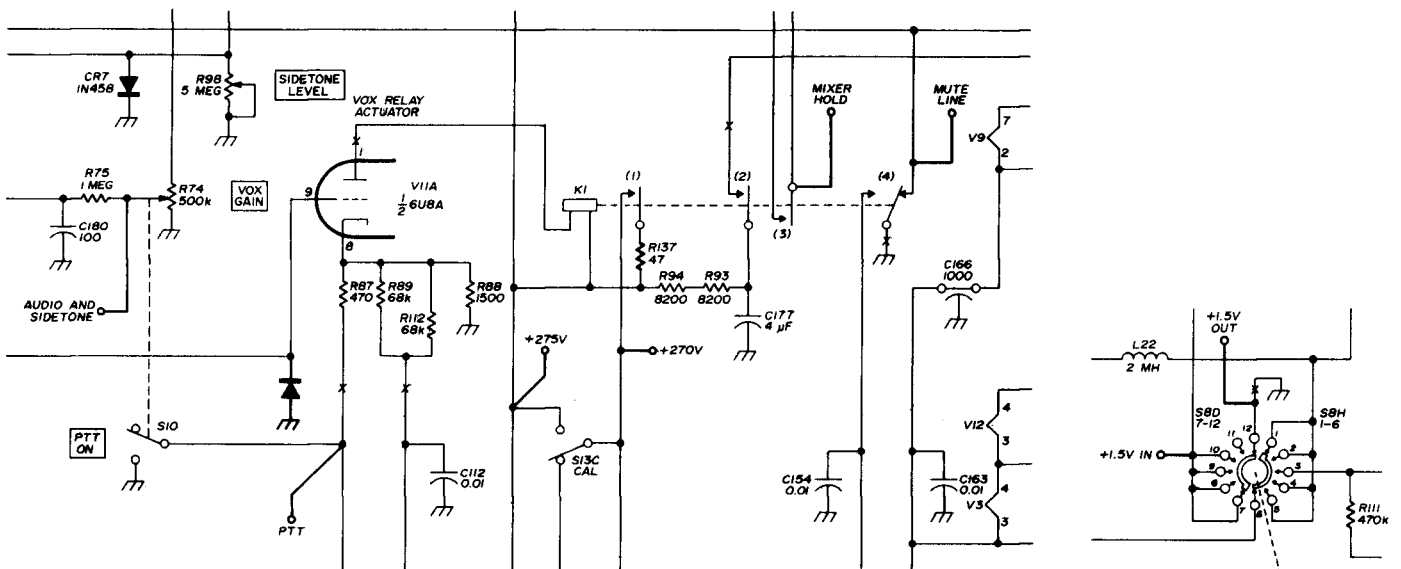


fig. 4. Circuit modifications for the 32S-3 transmitter which will permit instantaneous vox operation.

modification in the grid bias stage. Referring to fig. 5, the changes in the standard wiring diagram are indicated. The only components to be added to this area are as follows: 22k, 2-watt resistor; 1N4004 diode; and the 200  $\mu$ F, 200-volt electrolytic capacitor. Be sure to observe the polarity of the diode connections. The revised circuit now uses a switching transistor to control cut-off during receive. The bias line is grounded through Q8 (2N4063) in accordance with transmitted voice syllables or code elements. The relay in the 30L-1 (K1) is now wired to be continuous-

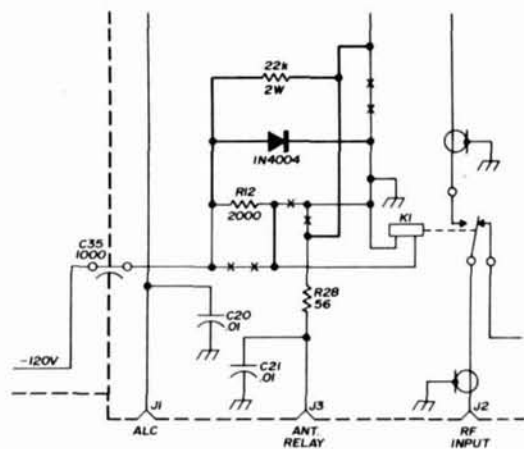


fig. 5. The bias circuit in the Collins 30L-1 amplifier requires changes to interface with the transistor in the control circuitry. The 200  $\mu$ F capacitor can be epoxied to the chassis.

ly energized; this relay is controlled with the main power switch. The large 200  $\mu$ F capacitor is held in place with epoxy cement in the power compartment.

Some of the newer amplifiers have their grid bias lines wired in a similar fashion. The purpose of the modification is to maintain the tubes at cut-off bias during reception. The duty cycle during CW or ssb is short so the tubes operate at a much cooler level.

## results

For the past nine years I have been operating with equipment using no relays, in both the CW and ssb modes. The many advantages of high-speed, silent switching are numerous and add greatly to the pleasure of operating. The Collins conversion has added to that pleasure and has been most gratifying. My sincerest thanks are extended to W6RM, for without his guidance, the conversion would never have been accomplished.

## references

1. R. W. Hitchcock, W6RM, "Syllabic Vox System for the Drake Equipment," *ham radio*, August, 1976, page 24.
2. H. R. Hildreth, W0IP, "An Experimental All-Electronic Vox System for SSB," *QST*, March, 1968, page 36; "Instantaneous Voice Interruption," *QST*, October, 1968, page 40; "More on Instant Voice Interruption," *QST*, June, 1972, page 19.

ham radio

# the famous HAM KEYS

The keys that are easy  
to put your fingers on!



JUST DIAL  
**1-800-325-3636**  
TOLL FREE



### Model HK-1

- Dual-lever squeeze paddle
- Use with HK-5 or any electronic keyer
- Heavy base with non-slip rubber feet
- Paddles reversible for wide- or close-finger spacing

**\$29<sup>95</sup>**



### Model HK-2

- Same as HK-1, less base for incorporation in own keyer

**\$19<sup>95</sup>**



### Model HK-3


- Deluxe straight key
- Heavy base no need to attach to desk
- Velvet smooth action

**\$16<sup>95</sup>**

### Model HK-3A

- Same as above less base

Navy type knob, only \$2.75

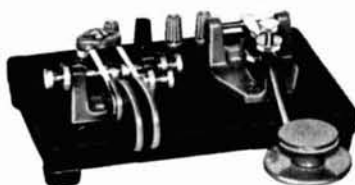

### Model HK-4

- Combination of HK-1 and HK-3 on same base

**\$44<sup>95</sup>**

- Base only with rubber feet \$12.00

Terminals, red or black, \$75 each



### Model HK-5 Electronic Keyer

- Iambic Circuit for squeeze keying
- Self-completing dots and dashes
- Dot memory
- Battery operated with provision for external power

**\$69<sup>95</sup>**

- Built-in side-tone monitor
- Speed, volume, tone and weight controls
- Grid block or direct keying
- For use with external paddle, such as HK-1

Same day shipment . . . PREPAID

We welcome the use of your



## HAM RADIO CENTER, INC.

8340-42 Olive Blvd. • P.O. Box 28271 • St. Louis, MO 63132

# hybrid-tee mixer for 10 GHz

How to use  
a hybrid-T  
waveguide junction  
to build a  
balanced mixer  
for 10-GHz receivers

The majority of amateur microwave receivers use front-ends which consist of a local oscillator coupled to a mixer diode. Radio-frequency amplifiers are available for the microwave frequencies but they are usually too expensive for amateur use. Receiver performance is therefore limited by the noise figure of the mixer, and to some extent by the following i-f amplifier, so any method which can improve mixer performance is well worth it.

At present two mixer types are prevalent among amateurs working at 10 GHz. The first is the self-oscillating mixer<sup>1</sup> (usually a Gunn device) which has the advantage of simplicity; the second is the mixer

diode with a separate local oscillator. In the latter system optimum mixer performance can be obtained by adjusting local-oscillator injection and mixer impedance matching.

Some improvement in mixer performance can be achieved by using a balanced mixer. The design described in this article offers some improvement in mixer performance, and is simple to build.

## design

The hybrid-T waveguide junction shown in **fig. 1** has the following properties: power fed into port 3 will divide equally and in phase between ports 1 and 2; no power will appear at port 4. Power fed into port 4 will also divide equally between ports 1 and 2, but out of phase. Therefore, a balanced mixer may be constructed by placing mixer diodes at ports 1 and 2, injecting local oscillator power via port 3, and connecting the antenna to port 4. This arrangement has the advantage over the single-ended mixer in that the a-m noise sidebands associated with the local oscillator are cancelled out in the mixing process. In the single-ended mixer the local-oscillator noise sidebands are transferred to the i-f signal in the mixing process. System sensitivity is therefore limited by the quality of the local-oscillator signal. Further information on balanced mixers can be found in **references 2 and 3**.

The hybrid-T junction has useful properties as a power divider and isolator and may be constructed as a unit on its own. In commercial models it is usual


By **R. J. Harry, G3NRT**, Aldwickbury Crescent, Harpenden, Herts, AL5 5SE, England

to insert irises and matching stubs to compensate for the mismatch at the junction of the four ports. In the unit described here no attempt has been made to compensate for the inherent mismatch.

It is also necessary to match the mixer diodes to the waveguide. This is achieved by placing matching stubs (tuning screws) in front of the diode mounting. An improved match could be obtained by using a tapered diode mounting, however, the matching stub approach simplifies construction.

## construction


The mixer assembly is made from three pieces of waveguide (0.4 x 0.9 inch or 1 x 2.3cm internal dimensions) as shown in **fig. 2**.<sup>\*</sup> The exact lengths are not critical but piece 1 should be at least 3 1/4 inches (8.3cm) long. Start by cutting the waveguide to length and neatly finishing off the ends. The slots in piece 1 should be scribed using the external dimensions of the waveguide for reference. The best way to remove the slots is to insert into the waveguide a piece of wood trimmed to the internal dimensions of

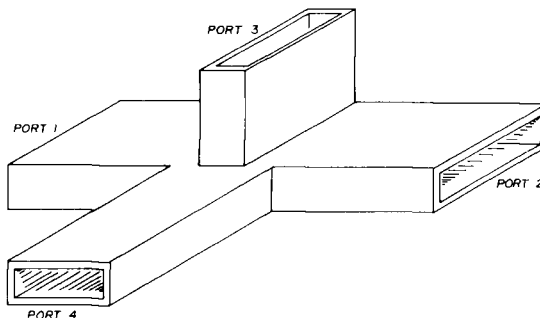

**fig. 1. The hybrid-T waveguide junction. Power fed into port 3 will divide equally and in phase between ports 1 and 2; no power will appear at port 4. Power fed into port 4 will also divide equally between ports 1 and 2, but out of phase. This property can be used to build a balanced mixer: the mixer diodes are installed at ports 1 and 2, local-oscillator power is injected at port 3, and the antenna is connected to port 4.**

adjacent waveguide wall because this will introduce discontinuities into the guide and permit solder to flow into the interior.

The slots should be filed out for a snug fit. Check that pieces 2 and 3 do not protrude into the inside of

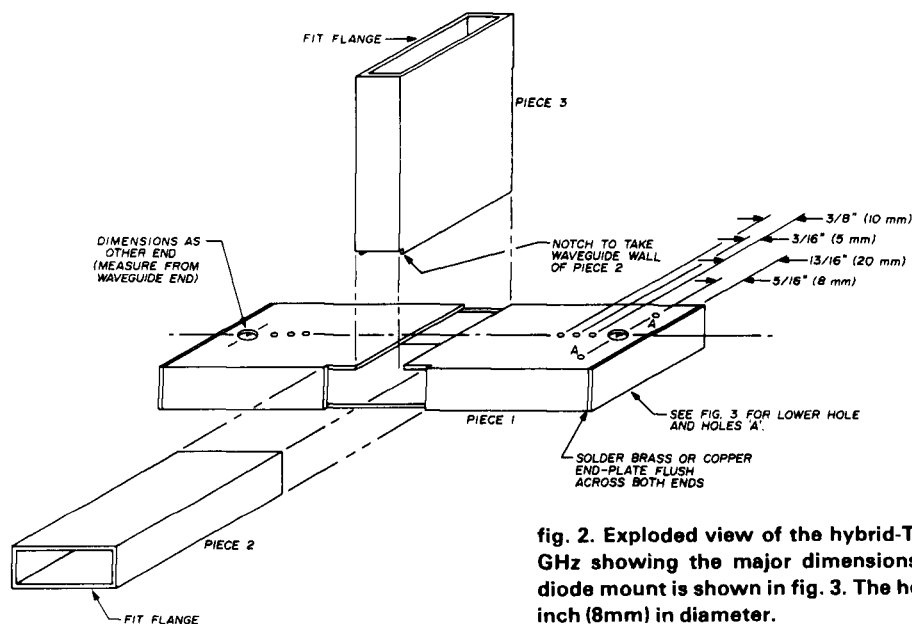

**fig. 2. Exploded view of the hybrid-T balanced mixer for 10 GHz showing the major dimensions. Construction of the diode mount is shown in fig. 3. The hole for the diode is 5/16 inch (8mm) in diameter.**

the guide. A neat cut will be obtained by using a small hacksaw and sawing on the inside of the scribed lines. It is important not to cut too deeply — the presence of sawdust in the metal cut will assist in judging the depth of the cut. Do not cut into the

<sup>\*</sup>Following is a list of some of the common classifications used for 10-GHz waveguide. If in doubt check the internal dimensions — they should measure 0.4 x 0.9 inch (1x2.3cm).

WG16	United Kingdom
WR90	United States (EIA)
RG-52/U	United States (JAN)
R100	IEC

the guide by looking into the open end of piece 1. When a good fit has been achieved, drill the matching screw holes and tap to suit the thread.<sup>\*</sup>

The diode holes should be made by first drilling the smaller hole through both broad faces in one operation, this will ensure good alignment. The hole for the body of the diode can be entered as shown or from the opposite broad wall — this is a matter of choice.

<sup>\*</sup>Any size screw thread of about 1/16" (1.5mm) diameter may be used.

The diode mounts are very simple in construction, but a word of caution: some diodes available on the surplus market are electrically sound but are out of specification mechanically. Therefore, use the dimensions given here only as a guide and check with your favorite diodes for a good fit. The diode should be a firm sliding fit into the collar (fig. 3). The collar height should be such that the diode, when fitted in the waveguide, has its shoulder at the pin end touching the lower interior guide wall.

The insulation between the diode mount and the waveguide is ordinary cellophane tape (e.g., Scotch tape). The nylon retaining screws should be cut so they are flush with the inside wall of the waveguide when secured. When all drilling has been completed and all internal burrs are removed, soldering can be started. Pieces 1, 2, and 3 should be soldered first, followed by the waveguide flanges. A damp rag should be wrapped around the T junction to prevent

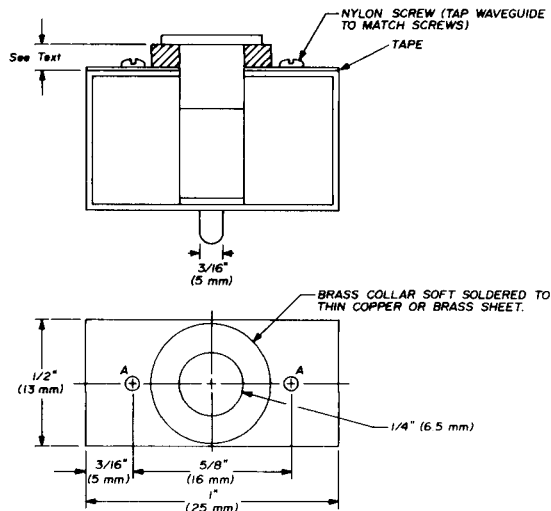


fig. 3. Construction of the diode mount for the 10-GHz balanced mixer. The i-f connection is made to the diode through a solder lug placed under the head of one of the nylon screws (see fig. 4 for i-f and metering connections).

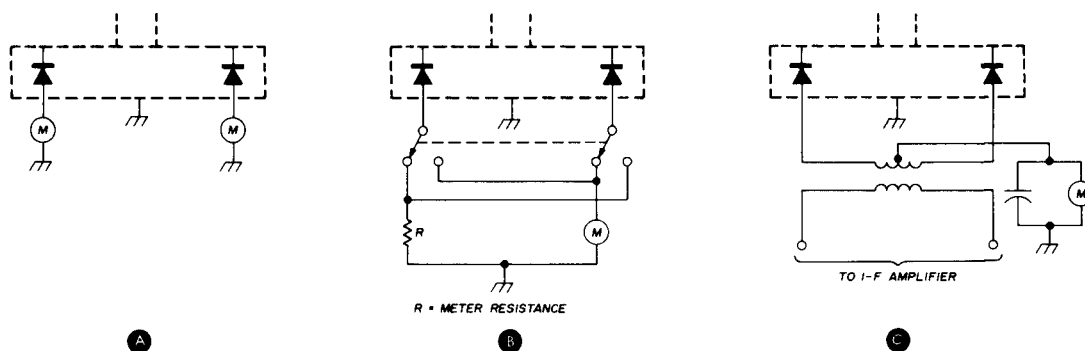


fig. 4. Metering and i-f connections to the hybrid-T waveguide balanced mixer. When initially setting LO injection, two identical meters should be used as shown at A, although the metering circuit at B is acceptable. Connections to the i-f transformer are shown at C.

the joint falling apart when soldering the flanges and end-pieces.

All soldering is best carried out with the work placed on a flat sheet of aluminum. This provides a firm base for the work, and avoids the possible embarrassment of soldering the waveguide to unwanted objects. A small gas jet should be used in preference to a soldering iron.

### adjustment

When connected to a local oscillator (5 -10 mW) the tuning screws should be adjusted for maximum mixer current. Ideally, this should be done with identical meters in series with each diode (fig. 4A), but if this is not possible the arrangement shown in fig. 4B can be used.

The tuning screws should be held in position with lock nuts. After the local-oscillator level has been adjusted for the recommended diode current, the metering circuit can be removed. A single meter for

monitoring purposes can be placed in series with the i-f transformer center-tap (fig. 4C).

### conclusion

Performance will depend on the diodes you use (preferably a matched pair). No performance figures are given because a meaningful set of measurements is beyond my present resources; the main object has been to describe the construction of a simple balanced mixer for 10 GHz which will encourage other amateurs to copy, experiment, and hopefully improve the design.

### references

1. G. Burt, GM30XX, "The GM30XX Portable 3cm Transciever," *Radio Communications* (England), June, 1975, page 450.
2. F. E. Terman, *Electronic and Radio Engineering*, McGraw-Hill, New York, 1955, section 5-9.
3. *The Services Textbook of Radio*, volume 5 (England), Her Majesty's Stationery Office, 1958, chapter 7.

ham radio



# YOUR BEST BUY IN KITS

# FREQUENCY COUNTERS

**WOW — FREE** FROM NOW UNTIL DECEMBER 31, 1977  
 RECEIVE ABSOLUTELY FREE — A SIX-DIGIT 12- OR 24-HOUR ELECTRONIC CLOCK KIT, COMPLETE WITH POWER SUPPLY AND CASE. WITH THE PURCHASE OF ANY ONE OF THE FOLLOWING FREQUENCY COUNTER KITS, HAL-600A, HAL-300A, HAL-50A OR THE ANALOG DIGILAB. JUST MENTION THIS AD WAS FOUND IN HAM RADIO MAGAZINE.  
 OR RECEIVE A GIFT CERTIFICATE WORTH \$15.00 ON YOUR NEXT PURCHASE OF \$50.00 OR MORE.

**6 GOOD REASONS** FOR BUYING A HAL-TRONIX FREQUENCY COUNTER  
 (1) 100% COMPLETE KIT, (2) EASY ASSEMBLY, (3) COMPLETELY ENCLOSED IN METAL CABINET, (4) IC SOCKETS USED THROUGHOUT FOR EASY TTL REPLACEMENT (5) EASY ON YOUR POCKET BOOK, AND (6) NO EXPENSIVE CHIPS TO REPLACE (EXAMPLE — IF YOU LOSE A DECODER, LATCH OR DRIVER IN A HAL-TRONIX COUNTER, THE AVERAGE COST OF REPLACEMENT OF THE LOW-COST TTLS IS LESS THAN \$1.00 EXCLUDING THE PRE-SCALE CHIP. IN SOME OF THE NEWER COUNTERS NOW BEING MARKETED BY MY COMPETITION, THEY ARE USING THE EXOTIC SINGLE CHIP AND WOULD COST YOU CLOSE TO \$30.00 TO REPLACE). THIS IS SOMETHING YOU SHOULD CONSIDER.



## ANALOG-DIGILAB KIT \$139.50

DESIGNED BY HAL-TRONIX AND MIKE GOLDEN OF R. E. T. S. ELECTRONICS SCHOOL OF DETROIT. FOR RUGGED CLASSROOM USE.

FOR THE RADIO AMATEUR, THE STUDENT, THE EXPERIMENTER OR DESIGNER

**SPECIFICATIONS:** OUTPUT VOLTAGES: +5V, +12V, -12V; USABLE CURRENT: 750mA; % Regulation at 500mA: 0.2%; Short-circuit limited at 1.0 amp; Thermal overload protected. Power requirements: 117VAC, 60HZ, 40 Watts. Function Generator: Frequency range: 1HZ to 100 HZ in 5 bands. Amplitude adjustable from 0 to 10 VPP. DC offset adjustable from 0 to ± 10V. Waveforms: Sine, square, triangular and TTL Clock. TTL Clock 0 to +5V level, 200 ns rise and fall time, Frequency determined by Function Generator. Output impedance 1.2K ohm. Most of all, it's easy to construct and service. PC boards are predrilled, plated thru and solder flowed. Over 1000 units sold to schools.

### 6-DIGIT CLOCK

12/24 HOUR

COMPLETE KIT CONSISTING OF 2 PC G10 PRE-DRILLED PC BOARDS, 1 CLOCK CHIP, 6 FND 359 READ-OUTS, 13 TRANSISTORS, 3 CAPS, 9 RESISTORS, 5 DIODES, 3 PUSH-BUTTON SWITCHES, MOLDED POWER TRANSFORMER CORD AND INSTRUCTIONS. DON'T BE FOOLED BY PARTIAL KITS WHERE YOU HAVE TO BUY EVERYTHING EXTRA.

PRICED AT \$12.95

### 4-DIGIT ALARM CLOCK

12 HOUR ONLY

COMPLETE KIT CONSISTING OF 2 PC G10 PRE-DRILLED PC BOARDS, 1 CLOCK CHIP, 4 FND 503 READ-OUTS, ALL NECESSARY TRANSISTORS, CAPS AND RESISTORS INCLUDING 5 PUSH-BUTTON SWITCHES, MOLDED POWER TRANSFORMER CORD PLUS SPEAKER; COMES COMPLETE WITH INSTRUCTIONS.

PRICED AT \$16.95

### CLOCK CASE

Available and will fit any one of the above clocks  
 Regular Price . . . \$6.50 But Only \$4.50 when bought with clock

### 60-HZ TIME BASE

CRYSTAL TIME BASE KIT. WILL ENABLE MOST ALL DIGITAL CLOCKS TO OPERATE FROM 12 VDC. LOW PROFILE UNIT, EASY 3-WIRE HOOKUP. ACC 2PPM, ADJUSTABLE. COST ONLY \$5.95 EACH OR 2 FOR \$10.00 — OR ONLY \$4.50 WITH CLOCK PURCHASE.

### 10-MHz CRYSTALS

HI-QUALITY CRYSTALS, DESIGNED FOR FREQUENCY CONTROL AND ELECTRONIC TIME PIECES; AGING FACTOR 5PPM. MEETS OR EXCEEDS MIL-C-3098 SPECS. MADE ESPECIALLY FOR HAL-TRONIX BY SENTRY. PRICE \$5.95 OR 2 FOR \$10.00



**EXCEL CIRCUITS**

ETCH-IT-YOURSELF

PRINTED CIRCUIT KIT ONLY \$19.95 PLUS \$1.00 SHIPPING


KIT INCLUDES:

4 PCS PHOTO-SENSITIZED GLASS EPOXY BOARD; DEVELOPER & RESIST STRIPPER; DRY ETCHANT CRYSTALS; 1 - 8 x 12 x 3 PLASTIC TRAY AND COVER. 2 - 8 1/2 x 11 SHEETS OF .100 GRID PAPER. 2 - 8 1/2 x 11 SHEETS OF .002 MYLAR; 1 PAIR OF PLASTIC GLOVES, MISC. ART-WORK SUPPLIES.

DISTRIBUTOR FOR **A P PRODUCTS, INCORPORATED**



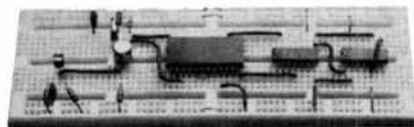**SUPER STRIP**  
 SS-2 #923252  
 PRICE \$17.00



**COMPLETE KITS:** CONSISTING OF EVERY ESSENTIAL PART NEEDED TO MAKE YOUR COUNTER COMPLETE.  
**HAL-600A** 7-DIGIT COUNTER WITH FREQUENCY RANGE OF ZERO TO 600 MHz. FEATURES TWO INPUTS: ONE FOR LOW FREQUENCY AND ONE FOR HIGH FREQUENCY; AUTOMATIC ZERO SUPPRESSION. TIME BASE IS 1.0 SEC OR .1 SEC GATE WITH OPTIONAL 10 SEC GATE AVAILABLE. ACCURACY ± .001%, UTILIZES 10-MHz CRYSTAL 5 PPM.

**COMPLETE KIT \$149.00**

**HAL-300A** 7-DIGIT COUNTER WITH FREQUENCY RANGE OF ZERO TO 300 MHz. FEATURES TWO INPUTS: ONE FOR LOW FREQUENCY AND ONE FOR HIGH FREQUENCY; AUTOMATIC ZERO SUPPRESSION. TIME BASE IS 1.0 SEC OR .1 SEC GATE WITH OPTIONAL 10 SEC GATE AVAILABLE. ACCURACY ± .001%, UTILIZES 10-MHz CRYSTAL 5 PPM.

**COMPLETE KIT \$124.00**

**HAL-50A** 8-DIGIT COUNTER WITH FREQUENCY RANGE OF ZERO TO 50 MHz OR BETTER. AUTOMATIC DECIMAL POINT, ZERO SUPPRESSION UPON DEMAND. FEATURES TWO INPUTS: ONE FOR LOW FREQUENCY INPUT, AND ONE ON PANEL FOR USE WITH ANY INTERNALLY MOUNTED HAL-TRONIX PRE-SCALER FOR WHICH PROVISIONS HAVE ALREADY BEEN MADE. 1.0 SEC AND .1 SEC TIME GATES. ACCURACY ± .001%. UTILIZES 10-MHz CRYSTAL 5 PPM.

**COMPLETE KIT \$124.00**

## HAL-TRONIX BASIC COUNTER KITS

### STILL AVAILABLE

THE FOLLOWING MATERIAL DOES NOT COME WITH THE BASIC KIT: THE CABINET, TRANSFORMER, SWITCHES, COAX FITTINGS, FILTER LENS, FUSE HOLDER, T-03 SOCKET, POWER CORD AND MOUNTING HARDWARE.

**HAL-600X** (Same Specifications as HAL-600A) \$124.00

**HAL-300X** (Same Specifications as HAL-300A) \$99.00

**HAL-50X** (Same Specifications as HAL-50A) \$99.00

## PRE-SCALER KITS

**HAL-0-300PRE** (Pre-drilled G10 board and all components) \$19.95

**HAL-0-300P/A** (Same as above but with preamp) \$29.95

**HAL-0-600PRE** (Pre-drilled G10 board and all components) \$39.95

**HAL-10GHZ** (New Item - Available in December) \$124.95

## PRE-BUILT COUNTERS AVAILABLE

(HAL-600A — \$229.00) (HAL-300A — \$199.00) HAL-50A — \$199.00). ALLOW 4- TO 6-WEEK DELIVERY ON PRE-BUILT UNITS.



**HAL-TRONIX**

P. O. BOX 1101

SOUTHGATE, MICH. 48195

PHONE (313) 285-1782

"HAL" HAROLD C. NOWLAND  
 WBZKH

**SHIPPING** ORDERS OVER \$15.00 WILL BE SHIPPED POSTPAID EXCEPT ON ITEMS WHERE ADDITIONAL CHARGES ARE REQUESTED. ON ORDERS LESS THAN \$15.00 PLEASE INCLUDE ADDITIONAL \$1.00 FOR HANDLING AND MAILING CHARGES.

**INFORMATION:**

SEND SASE FOR FREE FLYER

# calculator-aided circuit analysis

Techniques to use  
your programmable,  
hand-held calculator  
to analyze the operation  
of your own circuits —  
before you even  
pick up  
your soldering iron

**Circuit analysis gives the** frequency response of components selected by circuit design. Design tells you what the circuit *should* do while analysis tells you what *actually* happens. Analysis can be done with a programmable pocket calculator on filters, matching networks, or other circuits with the same accuracy as big computers — and at far less cost. Programs and methods for the HP-25 programmable calculator are given here but there is enough data for conversion to other calculator types.

A programmable calculator allows accurate analysis of a circuit before it is built. Analysis takes a little time but it can literally save days otherwise spent in fiddling with marginal or unusable circuits. An advantage is that you get to know your circuits rather than just putting components together. It works with your own design or with published circuits.

The HP-25 can be purchased for less than \$150 — about the average day's computer time charge — and the built-in functions are good for complex number handling. It is assumed you already know impedance and admittance, and rectangular and polar forms. All are needed to understand the methods. If these are unfamiliar, take time for a review before going on.

## basic ladder model

A *model* for circuit analysis is a block diagram made from *branches* connected by *nodes*. The branches are component combinations having two common connection points or nodes. A branch may have one or many components and its impedance or admittance value is described by a single expression. Any circuit may be modeled in this manner.

The *ladder* configuration is a shunt-series-shunt branch arrangement as shown in **fig. 1** for five branches. A ladder can be any odd-number branch arrangement. A model not in the ladder form can be transformed in subsections until the ladder is achieved. The simple ladder model allows only one signal source. This source is not considered a full branch.

**Fig. 1** shows all branches as impedances. Actual

**By Leonard H. Anderson, 10048 Lanark Street, Sun Valley, California 91352**

model values have shunt branches as admittances, series branches as impedances. This convention is used for the calculator solution program and the rationale may be seen by examining the model and identities plus the solution for output voltage.

Output voltage,  $e_o$ , will be a relative term and solely a function of branch values. Actual output voltage can be found by multiplying it by actual input current expressed in complex form. Most network responses are expressed in dB relative to a reference value so the current source can be unity without destroying validity.

There is one important fact about this model form: The admittance of the signal source *must* be a part of the input shunt branch. Excluding it will destroy the method of solving output voltage.\*

Compare the terms in the final  $e_o$  expression with the model diagram and identities. Each term represents the total admittance,  $Y$ , or impedance,  $Z$ , at a particular point in the model, looking towards the load. The progression of identities from  $Y_{12}$  to  $Z_{45}$  show this and the arrows of the diagram locate the total network impedance seen by the current source. Each successive  $Y$  and  $Z$  is both the sum of all preceding values and a term of the output voltage expression.


You can solve for both  $e_o$  and total  $Z_{in}$  by setting up the calculator to repeatedly request branch value entry, adding the entry to existing values, inverting the sum, multiply partial products by  $e_o$  by the sum (accumulating), then returning for next branch entry. This follows the identities of **fig. 1** and is the main loop (repeated operations) or **Program 1**.

A beginner in step-programming may be a little confused when confronted by only a program. The

flow chart in **fig. 2** represents the ladder network calculation of **Program 1**.

## ladder network flow chart

Flow charts are to programming what schematics are to circuits. Each chart symbol represents a component of the program. Lines with arrows indicate progression from one operation to the next. Rectangles with square sides are general operations, rounded-side boxes are program stops to display data, and slanted-side boxes are data entry stops. Diamonds represent decision points in the flow; program flow can change depending on what decision is made with particular data.

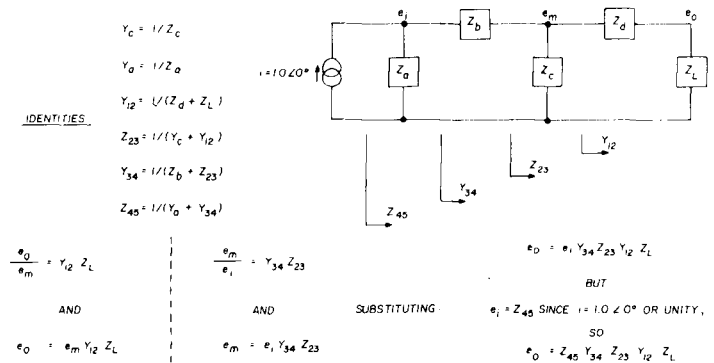

**fig. 1. Basic ladder network which can be quickly and easily analyzed with a hand-held, programmable calculator.**

The loop is at upper left. Branch value entry uses the rectangular form while inversion and multiplication is done in polar form. Partial products of  $e_o$  accumulate in memory while successive  $Y$  and  $Z$  remains in the stack.† The loop must stop after the last entry calculation so a counter is used for control.

The counter is just a memory register. Initialization at program start sets the counter to the number of branches in the model. After each loop is complete, the counter is decremented (reduced by one) and its value tested. A positive, non-zero value causes the program to jump back to loop start. Loop iteration stops when the counter is zero and program flow changes to the lower-right group.

The program is designed to give output voltage in dB relative to a reference,  $e_{ref}$ . Since the output voltage is unknown, reference to 0 dB is also unknown. The reference is automatically set if the first solution has the memory register for  $e_{ref}$  preset to zero. In this case,  $e_o$  is compared to  $e_i$  (input voltage = total

\*Exclusion of signal-source admittance does not affect input impedance.

†An algebraic-type calculator requires different storages so the program must be written from the original formulas of **fig. 1**.

Computer Aided Design, or CAD as it's known in industry, has been widely used by engineers and researchers to design and analyze electronic circuits. With the availability of low-cost, hand-held, programmable calculators, many of the benefits of this powerful analytical tool are now available to amateurs and experimenters.

In 1970 the author had to quickly find some time-delay equalizing networks for an avionics system's detector bank. Time was short and some components were in stock that *might* work. But would they? A fellow engineer told Anderson about the company's computer program and helped him check the circuit out on the terminal. The computer program had time-response capability and a half-hour of printout said the circuit would work fine. The circuit was built in the lab and checked out — the scope display was *identical* to the computer printout. The total elapsed time from assignment to results was less than five hours. The author has been a strong advocate of CAD ever since.

**Editor**

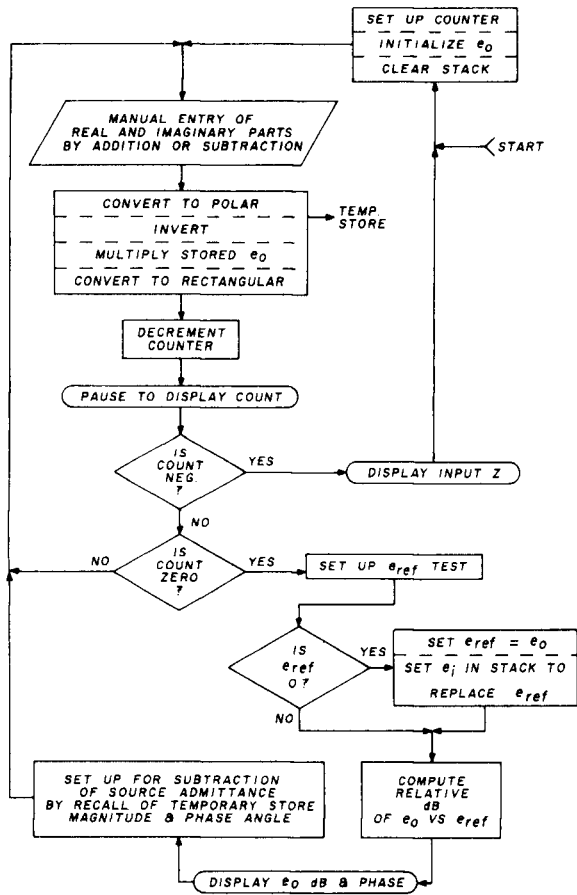


fig. 2. Flow chart for Program 1, ladder network analysis.

input impedance) and the first  $e_0$  display represents insertion loss/gain. All other  $e_0$  displays compare to  $e_{ref}$  unless the memory register is reset. An analysis usually requires one frequency at which relative output is 0 dB so this frequency should be solved first.

The lower-left block is a special operation. This sets up conditions for subtracting source impedance from total network admittance to find input impedance of only the network. This is very useful for filters and other circuits that require input impedance data. Each successive  $Y$  or  $Z$  calculated in the loop is also placed in temporary memory storage. In this part of the program the temporary storage contains total input admittance so this is recalled to the stack and flow jumps to loop start. At loop finish the counter will be  $-1$  so the flow is directed to input impedance display.

### program listing and details

The memory register block of Program 1 should be noted. Only three registers, R4, R5, and R6 must be preset before any run. Register R4 contains the constant 20 used in computing voltage gain in dB; holding constants in memory saves program steps. R5 is initially zero to establish the 0 dB reference

voltage for subsequent frequency solutions. R6 is set to the number of branches (do not count the current source as a branch).

Registers 0 and 1 accumulate the output voltage. Output phase angle is proportional to zero-degree input current. Input voltage phase angle is a function of total input impedance phase angle and must be calculated outside of this program. Successive  $Y$  and  $Z$  from the loop are stored in R2 and R3.

Steps 01 through 06 initialize the program run (upper right-hand corner of fig. 2). Register R0 is set to one so the partial products of  $e_0$  can be accumulated by register arithmetic. Register arithmetic allows any memory register to be added, subtracted, multiplied, or divided by the X register content without altering the X register.

The loop is contained in steps 07 - 21. Steps 07 and 08 do nothing on the first pass through the loop since both X and Y stack registers are zero. These steps are required on return jumps and will then contain the data indicated.

Branch value entry must be done manually by addition or subtraction, depending on sign. This is required to fit the limited number of program steps. Order of entry is always real part first, imaginary part second. Rectangular form is used here for both program and value-precalculation convenience.

Output voltage partial products are accumulated at steps 16 and 20 using register arithmetic. Polar form is more convenient here. Inversion of the polar form

STEP	KEY	X	Y	Z	T	REMARKS
01	RCL 8	NO				INITIALIZE
02	STO 7	NO				COUNTER
03	I	1	NB			
04	STO 0	1	NB			INIT, $e_0$ MAGN.
05	E STK	0	0	0	0	CLEAR STACK
06	STO 1	0	0	0		INIT, $e_0$ PHA
07	R $\downarrow$	(MAG)	(PHA)			LOOP START
08	E $\rightarrow$	REAL	IMAG			RECT. CONVERT
09	R/S	REAL	IMAG			INPUT REAL
10	X $\leftrightarrow$ Y	IMAG	REAL			
11	R/S	IMAG	REAL			INPUT IMAG
12	X $\leftrightarrow$ Y	REAL	IMAG			
13	g $\rightarrow$	MAG	PHA			POLAR CONVERT
14	g $\leftarrow$ X	1/MAG	PHA			RECIP INVERT
15	STO 2	1/MAG	PHA			TEMP. STORE
16	STO X	1/MAG	PHA			ACC. $e_0$ MAGN.
17	X $\leftrightarrow$ Y	PHA	1/MAG			
18	STO 3	PHA	1/MAG			TEMP. STORE
19	CHS	-PHA	1/MAG			FINISH INVERT
20	STO + 1	-PHA	1/MAG			ACC. $e_0$ PHA
21	X $\leftrightarrow$ Y	1/MAG	-PHA			
22	RCL 7	N	1/MAG	-PHA		
23	I	1	N	1/MAG	-PHA	DECREMENT
24	I	N-1	1/MAG	-PHA		COUNTER
25	STO 7	N-1	1/MAG	-PHA		
26	E PAUSE	N-1	1/MAG	-PHA		(OPTIONAL)
27	g $\leftarrow$ X	N-1	1/MAG	-PHA		
28	GTO 49	N-1	1/MAG	-PHA		JMP Z DISPLAY
29	g $\leftarrow$ X	N-1	1/MAG	-PHA		
30	GTO 07	N-1	1/MAG	-PHA		JMP LOOP START
31	RCL 0	N-1	1/MAG	-PHA		
32	RCL 5	C OF	0	1/MAG		
33	g $\leftarrow$ X	C OF	0	1/MAG		
34	GTO 38	C OF	0	1/MAG		JMP DB OUTPUT
35	R $\downarrow$	C OF				
36	STO 5	C OF				SET KEY REFER.
37	RCL 2	0	C OF			
38	R $\leftarrow$	RATIO	C OF			SETUP TO FIND
39	R $\leftarrow$	LOG	LOG			NETWORK INPUT
40	RCL 4	20	LOG			IMPEDANCE
41	X	DB				
42	R/S	DB				DISPLAY $e_0$ MAG
43	RCL 1	PHA	DB			
44	R/S	PHA	DB			DISPLAY $e_0$ PHA
45	RCL 3	Y PHA	DB			SETUP TO FIND
46	RCL X	Z OF	Y PHA			NETWORK INPUT
47	g $\leftarrow$ X	Y MAG	Y PHA			IMPEDANCE
48	GTO 08	Y MAG	Y PHA			JMP LOOP CONV.
49	R $\downarrow$	Z MAG	Z PHA			DISPLAY Z IN

MEMORY	REGISTER	INITIAL VALUE
R0	$e_0$	"MAGNITUDE"
R1	$e_0$	"PHASE ANGLE"
R2	MAGNITUDE	(TEMPORARY)
R3	PHASE ANGLE	(TEMPORARY)
R4	20	(CONSTANT)
R5	0	(REFERENCE)
R6	NUMBER OF BRANCHES	(CONSTANT)
R7	N	COUNTER

Program 1. Ladder Network Calculation.

is at **steps 14** and **19**. The intermix of steps may be confusing at first glance but is required to reduce the program size.

The pause at **step 26** is optional but useful when becoming acquainted with the program. The one-second display will show the branch number to be entered *next*. This assumes the first shunt branch is 1, the next series branch is 2, and so on. A zero display indicates that entries are complete and  $e_o$  display is next.

The first decision point is at **steps 27** and **28** on the new state of the counter contained in X. Program flow can be stated as, "If the contents of X is less than zero (negative), then go to **step 49**; otherwise continue with statement in **step 29**." The next decision point follows directly and is interpreted, "If the contents of X is *not* zero, then go to **step 07**; otherwise continue with **step 31**."

Many functions on the HP-25 require the *g* or *f* key prefix so make certain you use the correct one when entering the program steps. Strange results could happen from **steps 27** and **29** if the *f* key was mistakenly used.

**Steps 31** and **32** set up the  $e_{ref}$  test actually performed in **steps 33** and **34**. The 0 shown in Y and Z stack registers is the counter state; the program would not have reached **step 31** unless the counter was zero. Reference test is done on polar form magnitudes only. The content of R2 is now equal to total  $Z_{in}$  or equal to  $e_i$ . **Step 37** and the register roll-down of **step 35** are equivalent to replacing  $e_{ref}$  by  $e_i$ .

**Steps 38 - 41** compute voltage ratio in dB, displayed at **42** stop. Any register may now be examined manually since the following steps order the stack contents by recall. This is also true after the phase angle display stop at **step 44**.

**Steps 45 - 48** set up for source admittance subtraction. Phase angle in register R3 is in admittance form since the storage instruction of **step 18** came before the **step 19** sign change for inversion completion. R2 is an impedance since it was stored after inversion; this was a requirement of recall at **step 37** to reduce size. **Step 47** completes the magnitude inversion so the jump to **step 08** has X and Y in admittance form. Source admittance is subtracted within the loop and the resulting impedance magnitude is displayed at **step 49**. Exchanging X and Y manually will display impedance phase angle. Depressing the *R/S* key will return to **step 01** restarting for the next run.

Precalculation of all branch values is required before a solution is done. All frequency-sensitive branches must be precalculated at each solution frequency. If either real or imaginary part of the branch is zero, the particular entry may be skipped. It is im-

**table 1. Keyboard operations and displays using HP-25 Program 1 to analyze the R-C lowpass filter shown in fig. 3.**

keyboard	display	
	0.0000	(first stop after restart)
enter load G	1. -05	(EEX, CHS, 5)
add	1.000000-05	
R/S	0.0000	
enter 0.005 $\mu$ F B	0.000062832	
add	0.0001	
R/S	4.0000	(pause display for 1 second)
	2470.4410	
enter 10k res.	1. 04	(EEX, 4)
add	12470.4410	
R/S	-15522.2751	
(skip entry, X = 0)		
R/S	3.0000	(pause display for 1 second)
	3.1455036-05	
(skip entry, G = 0)		
R/S	3.9152883-05	
enter 0.05 $\mu$ F B	0.000628319	
add	0.0007	
R/S	2.0000	(pause display for 1 second)
	70.4467	
enter 1k res.	1. 03	(EEX, 3)
add	1070.4467	
R/S	-1494.8706	
(skip entry, X = 0)		
R/S	1.0000	(pause display for 1 second)
	0.0003	
enter source G	0.01	
add	0.0103	
R/S	0.0004	
(skip entry, B = 0)		
R/S	0.0000	(pause display for 1 second)
	-3.2067	$e_o$ magnitude in dB
R/S	-65.0970	$e_o$ phase angle in degrees
R/S	0.0103	total input conductance
enter source G	0.01	
subtract	0.0003	
R/S	0.0004	total input susceptance
(skip entry, B = 0)		
R/S	-1.0000	(pause display for 1 second)
	1838.6121	filter input Z magnitude
x $\leftrightarrow$ y	-54.3943	filter input Z phase angle
RCL 5	90.0090	$e_{ref}$

portant to keep entry order of real-part-first in mind; solution is invalid if these are mixed.


### example using program 1

The two-section R-C lowpass filter of **fig. 3** is a simple example. Capacitors are assumed lossless. There are only five branches in the model. The first branch has an admittance of  $0.01 + j0$  mho due to the source resistance of 100 ohms. Load admittance of 10 micromho is constant in branch 5 but the susceptance of the 0.005  $\mu$ F is in parallel. Branches 2 and 4 are purely resistive while branch 3 (0.05  $\mu$ F) is purely susceptive. To reiterate, all shunt branches are entered as admittances while series branches enter as impedances.

**Fig. 3** shows a tabulation of capacitor susceptance

as well as solved output voltage and filter input impedance. Susceptance is zero at dc, the reference frequency, so the reference solution required only resistive or conductive values entries. Insertion loss will display negative but some circuits have voltage gain; a voltage gain displays positive at the reference frequency.

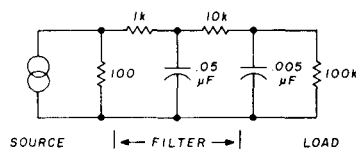Memory register 6 is set at 5 for the number of branches and R5 is set at zero for the reference run at dc. A tabulation of keyboard operations and resulting displays are shown in **table 1**. Display is set fixed at 4-decimals and the run is at 2 kHz.



frequency (kHz)	susceptance (mho)	
	0.05 $\mu$ F	0.005 $\mu$ F
1	0.000314159	0.000031416
2	0.000628319	0.000062832
3	0.000942478	0.000094248
4	0.001256637	0.000125664
5	0.001570796	0.000157080
10	0.003141593	0.000314159
20	0.006283186	0.000628319

frequency (kHz)	output voltage		input	filter impedance
	dB	phase angle		
0*	0.0	0.0000°	111000	0.0000°
1	-0.9499	-36.0202°	3162.84	-68.8897°
2	-3.2067	-65.0970°	1838.61	-54.3943°
3	-5.8972	-86.4955°	1456.26	-43.9354°
4	-8.5755	-102.1197°	1288.50	-36.5079°
5	-11.0862	-113.7452°	1198.50	-31.0653°
10	-20.7912	-143.2080°	1057.05	-17.3493°
20	-32.1027	-160.9919°	1014.94	-8.9974°

\*Reference frequency, insertion loss = 0.09065 dB

**fig. 3.** Susceptance, output voltage, and filter input impedance for an R-C lowpass filter, calculated with a programmable, hand-held calculator.

The tabulation looks formidable but operation takes less time than reading the listing. The RCL 5 at the end is not required; it was included only to show the internal  $e_{ref}$  value in memory.

For simple circuits such as this one, 5 significant

\*The question of accuracy sometimes comes up when calculator results are compared to computer printouts. Large computers don't automatically imply great accuracy — only when *long precision* (10 digits) or *double precision* (14 digits) are used does this happen. A recent computer run on an audio lowpass filter for an ssb rig indicated a *dc* insertion loss of 0.0002 dB with a  $-0.3723^\circ$  phase angle! Since inductor  $Q$  was not modeled in this program, insertion loss should be 0 dB. The computer program's phase angle can only be explained by the way the program was written and by the 7-digit precision.

digits of entry value should be sufficient. At least 6 digits should be used for larger models or those having reactance and susceptance in each branch. Most big computer analysis programs have only 7 significant digits for all calculation while the HP-25 uses ten — the program can actually be more accurate than computer results!\*

Analysis of L-C networks, especially filters, can be tiring when R or G is absent or a constant value. **Program 2** was designed for filter analysis when the source and load resistance is equal and the shunt branch conductance is always the same value. Top-coupled bandpass filters can be analyzed by this program. In this case the shunt conductance is calculated by  $B_L/Q$  at center frequency and  $Q$  is the mean value of parallel inductor and capacitor.

### modified ladder network program

**Program 2** is a rewritten version of **Program 1** and requires only the imaginary part of branch value be entered. Series branches are assumed nearly lossless; common shunt conductance is also added to the series branches by the program so solutions are valid only when series reactance is high compared to parallel reactance. It does serve to show how the basic program can be changed to achieve the same results.

Initialization, loop, and output voltage calculation in dB are the same as **Program 1** with a few exceptions. There is no temporary storage since this is occupied by constants  $1/R_L$  and  $G_s$ , the common shunt conductance. This leaves no room for finding  $Z_{in}$  by the program or automatically setting an  $e_{ref}$  value. Each of these can be set manually on the first run. The loop of **Program 1** starts and ends in polar form. **Program 2's** loop starts and ends in rectangular form so that shunt conductance and end conductance may be added by the program.

A notable exception is that the number of branches stored in R6 is one less than the model. This is a requirement of steering program flow at **steps 29** and **30** so that end conductance can also be added via **steps 32 - 34**. Load-end conductance is added by the GTO32 at **step 07** while source-end conductance addition results from decision steering.

A negative count at loop ending steers the program to output voltage calculation. The initial value of  $e_{ref}$  should be some number like one to prevent an error stop at **step 38** from division by zero. The first  $e_o$  display will be meaningless.

Total input impedance has been carried in the stack in rectangular form. This is converted to polar form after output voltage phase angle display. Manual register operations should be avoided until the stop at **step 48** since stack data could disappear.



STEP	KEY	X	Y	Z	T	REMARKS
01	RCL 6	NB				INITIALIZE COUNTER
02	STO 7	NB				
03	I	1	NB			
04	STO 0	1	NB			INIT. $e_0$ MAG.
05	F STK	0	0	0	0	CLEAR STACK
06	STO 1	0	0	0	0	INIT. $e_0$ PHA
07	GTO 32	0	0	0	0	JMP TO GL ADD
08	R↓	REAL	IMAG			LOOP START
09	RCL 3	GS	REAL	IMAG		
10	+	REAL	IMAG			ADD GS
11	X↔Y	IMAG	REAL			ENTER IMAGINARY PART BY MANUAL ADD OR SUBTRACT
12	R/S	IMAG	REAL			
13	X↔Y	REAL	IMAG			
14	g →P	MAG	PHA			POLAR CONVERT
15	g 1/X	1/MAG	PHA			BEGIN INVERT
16	STO X 0	1/MAG	PHA			ACC. $e_0$ MAGN.
17	X↔Y	PHA	1/MAG			
18	CHS	-PHA	1/MAG			FINISH INVERT
19	STO - 1	-PHA	1/MAG			ACC. $e_0$ PHA
20	X↔Y	1/MAG	-PHA			
21	I →R	REAL	IMAG			RECT. CONVERT
22	RCL 7	N	REAL	IMAG		DECREMENT COUNTER
23	I	N	REAL	IMAG		
24	-	N-1	REAL	IMAG		
25	STO 7	N-1	REAL	IMAG		(OPTIONAL)
26	I PAUSE	N-1	REAL	IMAG		
27	g X<0	N-1	REAL	IMAG		
28	GTO 35	N-1	REAL	IMAG		JMP OUTP. CALC.
29	g X=0	N-1	REAL	IMAG		
30	GTO 08	N-1	REAL	IMAG		JMP LOOP START
31	R↓	REAL	IMAG			
32	RCL 2	GL	REAL	IMAG		
33	+	REAL	IMAG			ADD END GL
34	GTO 09	REAL	IMAG			JMP TO GS ADD
35	R↓	REAL	IMAG			BEG. OUTP. CALC.
36	RCL 0	$e_0$	REAL	IMAG		
37	RCL 5	$e_{ref}$	REAL	IMAG		
38	I	RATIO	REAL	IMAG		(REFERENCE)
39	I LOG	LOG	REAL	IMAG		R6 NUMBER OF BRANCHES
40	RCL 4	Z0	LOG	REAL	IMAG	MINUS ONE
41	X	DB	REAL	IMAG		
42	R/S	DB	REAL	IMAG		DISPLAY $e_0$ MAG
43	R↓	REAL	IMAG			
44	RCL 1	PHA	REAL	IMAG		
45	R/S	PHA	REAL	IMAG		DISPLAY $e_0$ PHA
46	R↓	REAL	IMAG			
47	g →P	MAG	PHA			
48	R/S	MAG	PHA			DISPLAY Z MAG
49	X↔Y	PHA	MAG			DISPLAY Z PHA RESTART BY [R/S]

Program 2. Modified Ladder Network Calculation.

Network input Z must be calculated manually in this program.

Insertion loss at the reference frequency can be found as follows: Store total Z magnitude in register R7 by STO 7 after the stop at step 48. Continue to step 49 and record total Z phase. Depress RCL 0, STO 5 to set  $e_{ref}$  in memory, then RCL 7 and DIVIDE to find  $e_0/e_i$  ratio. Using R7 at this point will not disturb the program since a restart will initialize the counter, destroying any previous data there.

Program 2 is convenient for branch entry but inconvenient for reference and network input impedance. Tradeoffs must be made due to program size. The last steps of both programs can be altered to suit the reader's application.

### precalculation techniques

Branch values at each solution frequency must be known before applying either Program 1 or Program 2. This can be done by another calculator program and tabulation of values. Precalculation should begin at the last branch and work forward. Tabulation will then have the same order of entry as either solution program.

Fig. 4 shows a simple bandpass filter to be analyzed. The model will have only three branches. Source and load resistances are equal and capacitor Q is assumed much higher than inductor Q. Equivalent shunt conductance due to Q is calculated from inductive susceptance only.

Program 3 is an example of precalculation for fig. 4. Frequency is the only variable and all component values are stored in memory. This lets the calculator do all the work of sign and decimal-point placement for the least error.

Register arithmetic is used extensively and programming is linear (no loops or jumps). The memory block shows two values for registers R0 through R5, excluding R2. The first value is the preset constant while the second is frequency modified. Note that inductance and C2 is preset inverted, C2 is also signed negative. Since calculation will require this anyway, it saves program steps to store constants in this form.

Steps 02 through 08 change the memory by register arithmetic and also store the entered frequency. Steps 33-39 restore memory contents to original value. Register arithmetic is quite useful for repetitive operations like this and saves program steps. A little study will show how it is done.

Inductive susceptance is shown with a negative sign. A negative  $B_L$  is a positive quantity required for equivalent conductance due to Q. The subtraction at steps 17 and 31 properly sets the total susceptance sign. The negative  $B_L$  is a subtle reminder to remember the basics of admittance.

Computation is straightforward with display stops in order from load to generator, real part first, imaginary part second. Shunt branches are in admittance, series in impedance. Steps 19 and 20 are strictly


STEP	KEY	X	Y	Z	T	REMARKS
01	R/S	FREQ				ENTER
02	STO X 0	FREQ				RADIAN FREQ.
03	STO 7	FREQ				STORE TEMP.
04	RCL 0	$\omega$	FREQ			SET RAD. FREQ
05	STO + 1	$\omega$	FREQ			FIND -B(L)
06	STO X 3	$\omega$	FREQ			FIND B(C1)
07	STO + 4	$\omega$	FREQ			FIND X(C2)
08	STO X 5	$\omega$	FREQ			FIND B(C3)
09	RCL 1	-B(L)				BEGIN LOAD G
10	RCL 2	GL	-B(L)			
11	I	G(OL)				
12	RCL 4	G(LOAD)	G(OL)			
13	+	GL				END LOAD G
14	R/S	GL				
15	RCL 3	B(C1)				
16	RCL 1	-B(L)	B(C1)			
17	-	BL				LOAD B
18	R/S	BL				
19	RCL 0	0				SERIES R
20	R/S	0				
21	RCL 4	X(C2)				R0 2 PI
22	R/S	X(C2)				RPI F ( $\omega$ )
23	RCL 1	-B(L)				BEGIN GENR. G
24	RCL 2	GL	-B(L)			
25	+	G(OL)				
26	RCL 4	G(LOAD)	G(OL)			
27	+	G(GEN)				END GENR. G
28	R/S	G(GEN)				GEN G
29	RCL 5	B(C3)				
30	RCL 1	-B(L)				
31	-	B(GEN)				
32	R/S	B(GEN)				GEN B
33	RCL 0	$\omega$				
34	STO X 1	$\omega$				MEMORY RESET
35	STO + 3	$\omega$				MEMORY RESET
36	STO X 4	$\omega$				MEMORY RESET
37	STO + 5	$\omega$				MEMORY RESET
38	RCL 7	FREQ				2PI RESTORE
39	STO + 0					JMP TO START
40	GTO 01					
41						
42						
43						
44						
45						
46						
47						
48						
49						

Program 3. Precalculation Example.

reminders that the real part of the series branch is zero; these can be deleted.

**Steps 23-28** are duplicates of **09-14** since both inductors are the same value. The program can be written to hold end conductance in the stack after **step 14**, then bring it back for display. A better alternative is to let register R2 hold the constant  $1/(L Q_L)$  and add two register arithmetic steps. This would delete four steps from the program shown. It is always better to hold constants in memory so the program needs fewer steps to compute the desired value.

The original frequency entry will be displayed when the run is finished and jumps back to stop at **step 01**. This is a good reminder for tabulation. If you hit the **R/S** key at **step 01** without entering a new frequency, all displays will repeat the previous run.

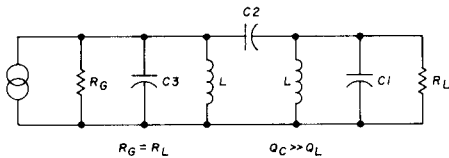

**fig. 4.** Bandpass filter for the precalculation example discussed in the text.

Run through all displays when this occurs so that memory is restored. A mid-program change requires reloading memory.

Many variations of the precalculation program are possible. They are written to fit the particular circuit to be modeled. Adopting the style of **Program 3** has these advantages:

1. Only one entry for frequency, all other stops are displays.
2. Component storage in memory with inversions and signs as necessary will reduce program steps.
3. Register arithmetic forms reactance and susceptance directly in memory with the fewest steps.
4. Calculation is simple and direct.

More than one program may be required. It is suggested that the load-end values are all calculated first. This fits the back-to-front ordering of the solution programs.

Scaling to megahertz, microhenries, and microfarads is useful for rf work. Results will still be in ohms and mhos. Other scaling can be used but should only be done if you're very familiar with impedance and admittance.

**the branch jumping adjacent nodes problem**

This situation normally defeats the ladder configuration. The remedy is to use a transformation pro-

gram on precalculated values until the ladder is formed. **Fig. 5** illustrates the method using a delta-to-tee transformation on a subsection. Circled numbers are nodes above ground. Nodes 1 and 3 will carry over but the original node 2 is reformed.

**Program 4** follows the formulas given in **fig. 5** with rectangular form entry and polar form solutions. Available program size requires more manual steps. Both parts of each delta branch must be entered in the sequence: Input real part, press **ENTER**, input imaginary part, press **R/S** to continue. A manual conversion to rectangular is required at each tee branch solution.

The program accumulates the common denominator of the transformation using the rectangular form with storage in registers R6 and R7. Numerators require multiplication so the polar form is used to reduce program size. The memory register block may seem confusing but the memory contents change as the program progresses.

After  $Z_A$  is entered, a direct store is used to begin accumulation. Registers R0, R1 and R2, R3 both hold the polar form of  $Z_A$  while R6, and R7 holds the rectangular form. Entering  $Z_B$  will make R6, R7 equal to  $Z_A + Z_B$  and R0, R1 equal to  $Z_A \times Z_B$  via register arithmetic. A direct store places  $Z_B$  in R4, R5. The numerator of  $Z_I$  has been formed in memory. Entry of  $Z_C$  will complete accumulation of the denominator and remaining numerators by register arithmetic.

**Steps 31-40** recall the denominator, convert it to polar form and place the solutions in memory. Memory registers R0-R5 are then recalled in order

STEP	KEY	X	Y	Z	T	REMARKS
01	R/S					ENTER ZA
02	STO 7	IMAG A	REAL A			BEGIN DENOMIN.
03	X↔Y	REAL A	IMAG A			
04	STO 6	REAL A	IMAG A			ACCUM. DENOMIN.
05	g → P	MAG A	PHA A			POLAR CONVERT
06	STO 0	MAG A	PHA A			Z1 NUMERATOR
07	STO 2	MAG A	PHA A			Z2 NUMERATOR
08	X↔Y	PHA A	MAG A			
09	STO 1	PHA A	MAG A			Z1 NUMERATOR
10	STO 3	PHA A	MAG A			Z2 NUMERATOR
11	R/S	IMAG B	REAL B			ENTER ZB
12	STO + 7	IMAG B	REAL B			ACCUM. DENOMIN.
13	X↔Y	REAL B	IMAG B			
14	STO + 6	REAL B	IMAG B			ACCUM. DENOMIN.
15	g → P	MAG B	PHA B			POLAR CONVERT
16	STO 4	MAG B	PHA B			Z3 NUMERATOR
17	STO x 0	MAG B	PHA B			Z1 NUMERATOR
18	X↔Y	PHA B	MAG B			
19	STO 5	PHA B	MAG B			Z3 NUMERATOR
20	STO + 1	PHA B	MAG B			Z1 NUMERATOR
21	R/S	IMAG C	REAL C			ENTER ZC
22	STO + 7	IMAG C	REAL C			ACCUM. DENOMIN.
23	X↔Y	REAL C	IMAG C			
24	STO + 6	REAL C	IMAG C			DENOM. COMPLETE
25	g → P	MAG C	PHA C			POLAR CONVERT
26	STO x 2	MAG C	PHA C			Z2 NUMERATOR
27	STO x 4	MAG C	PHA C			Z3 NUMERATOR
28	X↔Y	PHA C	MAG C			
29	STO + 3	PHA C	MAG C			Z2 NUMERATOR
30	STO + 5	PHA C	MAG C			Z3 NUMERATOR
31	RCL 7	IMAG D				ZC ZC PHA
32	RCL 6	REAL D	IMAG D			Z2 NUMER. PHA
33	g → P	MAG D	PHA D			R4 ZB MAG
34	STO ÷ 0	MAG D	PHA D			Z1 SOLVE
35	STO ÷ 2	MAG D	PHA D			Z2 IMPEDANCE
36	STO ÷ 4	MAG D	PHA D			Z3 MAGNITUDES
37	X↔Y	PHA D	MAG D			
38	STO - 1	PHA D	MAG D			Z1 SOLVE
39	STO - 3	PHA D	MAG D			Z2 IMPEDANCE
40	STO - 5	PHA D	MAG D			Z3 ANGLES
41	RCL 1	Z1 PHA				
42	RCL 0	Z1 MAG	Z1 PHA			
43	R/S	Z1 MAG	Z1 PHA			Z1 DISPLAY
44	RCL 3	Z2 PHA				
45	RCL 2	Z2 MAG	Z2 PHA			
46	R/S	Z2 MAG	Z2 PHA			Z2 DISPLAY
47	RCL 5	Z3 PHA				
48	RCL 4	Z3 MAG	Z3 PHA			
49	GTO 01	Z3 MAG	Z3 PHA			JMP START DISH

MEMORY	
R0	ZA MAG
R1	ZB MAG
R2	Z1 NUMER. MAG
R3	Z1 PHA
R4	ZB PHA
R5	ZB PHA
R6	Z1 NUMER. PHA
R7	ZC MAG
R8	ZC MAG
R9	Z2 NUMER. MAG
R10	Z2 PHA
R11	Z2 NUMER. PHA
R12	Z3 PHA
R13	Z3 PHA
R14	Z3 MAG
R15	Z3 MAG
R16	Z3 PHA
R17	Z3 PHA
R18	Z3 PHA
R19	Z3 PHA
R20	Z3 PHA
R21	Z3 PHA
R22	Z3 PHA
R23	Z3 PHA
R24	Z3 PHA
R25	Z3 PHA
R26	Z3 PHA
R27	Z3 PHA
R28	Z3 PHA
R29	Z3 PHA
R30	Z3 PHA
R31	Z3 PHA
R32	Z3 PHA
R33	Z3 PHA
R34	Z3 PHA
R35	Z3 PHA
R36	Z3 PHA
R37	Z3 PHA
R38	Z3 PHA
R39	Z3 PHA
R40	Z3 PHA
R41	Z3 PHA
R42	Z3 PHA
R43	Z3 PHA
R44	Z3 PHA
R45	Z3 PHA
R46	Z3 PHA
R47	Z3 PHA
R48	Z3 PHA
R49	Z3 PHA
R50	Z3 PHA

**Program 4.** Delta-to-Tee Transformation.

and the stops display each tee branch magnitude. Tee branch phase angle is in the Y register at each stop. The stop for  $Z_3$  is at **step 01**. This not only reduces steps but permits an automatic return to start for transforming the next set of delta values.

**Program 4** will work with either impedance or admittance. The only change is from rectangular form to polar form. As an example, enter

$$Z_A = 3 - j4$$

$$Z_B = 4 + j5$$

$$Z_C = 5 + j3$$

The solutions (converted to rectangular) are

$$Z_1 = 2.375 - j0.875$$

$$Z_2 = 1.750 - j1.500$$

$$Z_3 = 1.300 + j2.650$$

Note the difference in signs for the imaginary part.

### transforming the other way

A prime example is the parallel-T circuit. To form the basic ladder a tee-to-delta transformation is required. This places each transformed delta branch in parallel with the other. Transformation formulas are as follows using the branch designations shown in **fig. 5**

$$Z_N = Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3$$

$$Z_A = Z_N / Z_3$$

$$Z_B = Z_N / Z_2$$

$$Z_C = Z_N / Z_1$$

**Program 5** performs conversion using the above relations.

A difficulty in programming is the common numerator expression. **Program 4** is needed only to form a sum of three quantities for the common denominator. **Program 5** must form the common numerator from the sum of three products. This eats up program steps so **Program 5** is a bit harder to work with.

All entries must be in polar form. This can be done by entering rectangular values and converting manually. Attention must be paid to the magnitude and angle location in the stack. This is especially true at  $Z_2$  entry since the Z and T stack registers cannot be disturbed from locations shown.

Registers R0 through R5 store only the individual impedances. The numerator product terms are formed in the stack, converted to rectangular, then accumulated in registers R6-R7. The  $Z_1 Z_2$  term is formed when **step 12** is reached.  $Z_1 Z_3$  is complete by **step 25**. **Program 5** requires stack register manipulation and more steps as a result of the common numerator expression.

Limitation of HP-25 program size results in solutions stored *inverted* in memory. Input impedance and the direct solution is in admittance but both are

STEP	KEY	X	Y	Z	T	REMARKS
01	R/S					ENTER Z1
02	STO 4	MAG Z1	PHA Z1			ZC DENOM. MAG
03	X↔Y					
04	STO 5	PHA Z1	MAG Z1			ZC DENOM. PHA
05	R/S					ENTER Z2
06	STO 2	MAG Z2	PHA Z2	PHA Z1	MAG Z1	ZB DENOM. MAG
07	R↔					
08	STO 3	PHA Z2	PHA Z1	MAG Z1	MAG Z2	ZB DENOM. PHA
09	+					
10	X↔Y	MAG Z1	PHA Z1			
11	RCL 2	MAG Z2	MAG Z1	PHA Z1		
12	X↔Y					Z1Z2 COMPLETE
13	E →R	RE 12	IM 12			RECT. CONVERT
14	STO 6	RE 12	IM 12			ACCUM. NUMERAT.
15	R↔					
16	STO 7	IM 12				ACCUM. NUMERAT.
17	R/S					ENTER Z3
18	STO 9	MAG Z3	PHA Z3			ZA DENOM. MAG
19	RCL 4	MAG Z1	MAG Z3	PHA Z3		
20	X↔Y					
21	X↔Y	PHA Z3	MAG Z3			
22	STO 1	PHA Z3	MAG Z3			ZA DENOM. PHA
23	RCL 5	PHA Z1	PHA Z3	MAG Z3		
24	+					
25	X↔Y	PHA Z1	MAG Z3			Z1Z3 COMPLETE
26	E →R	RE 13	IM 13			RECT. CONVERT
27	STO 8	RE 13	IM 13			ACCUM. NUMERAT.
28	R↔					
29	STO 7	IM 13				ACCUM. NUMERAT.
30	RCL 1	PHA Z3				
31	RCL 3	PHA Z2	PHA Z3			
32	+					
33	RCL 0	MAG Z3	PHA Z3			
34	RCL 2	MAG Z2	MAG Z3	PHA Z3		
35	X	MAG Z2	PHA Z3			Z2Z3 COMPLETE
36	E →R	RE 23	IM 23			RECT. CONVERT
37	STO 6	RE 23	IM 23			ACCUM. NUMERAT.
38	R↔					
39	STO 7	IM 23				ACCUM. NUMERAT.
40	RCL 7	IM N				
41	RCL 6	RE N	IM N			NUMERATOR
42	Q	MAG N	PHA N			POLAR CONVERT
43	STO 0	MAG N	PHA N			YA SOLVE
44	STO 2	MAG N	PHA N			YB ADMITTANCE
45	STO 4	MAG N	PHA N			YC MAGNITUDES
46	X↔Y	PHA N	MAG N			YA SOLVE
47	STO 1	PHA N	MAG N			YB ADMITTANCE
48	STO 3	PHA N	MAG N			YC ADMITTANCE
49	STO 5	PHA N	MAG N			YC ANGLES

ALL ENTRIES PLACED IN ORDER IN STACK AS SHOWN IN POLAR FORM

MEMORY

R0	Z3 MAG
	YA MAG
R1	Z3 PHA
	YA PHA
R2	Z2 MAG
	YB MAG
R3	Z2 PHA
	YB PHA
R4	Z1 MAG
	YC MAG
R5	Z1 PHA
	YC PHA
R6	REAL PART
	NUMERATOR
R7	IMAG PART
	NUMERATOR

RESTART BY [R/S]

**Program 5. Tee-to-Delta Transformation.**

in polar form — the input/output is opposite that of **Program 4**. Solutions are manually recalled after the forced stop at **step 49**

$Y_A$  magnitude in R0, angle in R1

$Y_B$  magnitude in R2, angle in R3

$Y_C$  magnitude in R4, angle in R5

The admittance form is not a disadvantage. Recalling the parallel-T, the transformations have all delta branches in parallel. Admittance addition is the easiest calculation of parallels.

### other transformations

Lattice networks and similar circuits can be programmed to tee or delta sections and the formulas are available in most textbooks. In most cases a circuit can be divided into relatively simple subsections represented by a single branch; a precalculation program can be used instead of transformation. The circuit to be analyzed should be carefully studied and divided into branches that minimize pre-solution work.

A key indicator of the necessity for transformation is the model's signal path or current flow. The parallel-T has two separate signal paths so transformation is unavoidable. Branch  $Z_B$  of **fig. 5** represents a second signal path vs flow from node 1 through node 2 to 3.

Schematics can sometimes be misleading. Often they are drawn to fit available space and parallel components may appear widely separated. Copying the schematic on scratch paper is useful; branches

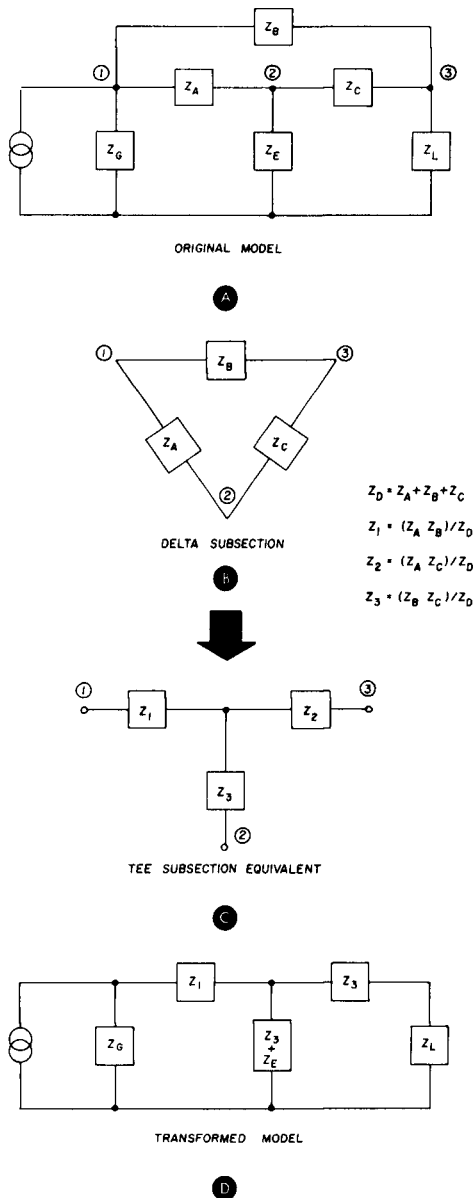


fig. 5. Model transformation. The delta subsection of the original model is first transformed to an equivalent tee network, then added to the original to form the transformed model.

can be marked or outlined without harming the original source.

### preparation

Practice with the calculator so you know what happens when you inadvertently key in a wrong instruction. Treat it like a piece of test equipment. In this application that is just what it is.

Use a separate pad of paper for branch value tabulation. When transformation is required, precalculate only the sub-sections and write down the solutions on the tabulation sheet first. The ordinary branches can be calculated later.

Remember to order branch values from back to front. It is probably easier to group values by frequency, making little blocks of values on the tabulation sheet. Calculate at more frequencies than you think you need. Network solutions will tell you which ones to skip over.

Five or six significant digits will give you good accuracy. A minimum is four digits, but only for simple circuits.

### group delay

Any circuit with inductance and/or capacitance has time delay and such delay is frequency sensitive. Group delay is the average time delay over a small increment or *group* of frequencies. It is a function of frequency increment and the differential phase angle within the increment. The formula is:

$$td = (\Delta \text{phase angle}) / (360 \cdot \Delta \text{Frequency})$$

where:  $\Delta \text{phase angle}$  = positive differential angle in degrees within the frequency increment

$\Delta \text{Frequency}$  = differential frequency over a small increment

Scaling can be seconds and Hz, milliseconds and kHz, or microseconds and MHz.

Frequency increments should be constant and small. For a bandpass filter, at least ten frequencies within the passband should give an accurate picture of group delay. Since the frequency increment is constant, the denominator of  $td$  is also constant.

Linear group delay in ssb filters will improve audio quality since all sideband components have the same amount of delay. Knowledge of rf to i-f to detector signal delay in receivers is useful when applying noise blankers of the Lamb or Collins type because the blanking signal must arrive before the noise reaches the blanking gate.

### is it worth the trouble?

Only if you do your own circuit designs or want to know what happens inside that collection of components. Programming is not difficult with the HP-25. Hewlett-Packard supplies a good applications manual free and the examples can give a quick insight to the various functions. The same is true for machines made by Texas Instruments.


Computer aided design is used extensively in industry for design analysis. Calculator aided design should be equally useful to the amateur. A few extra hours of *testing on paper* will let you know how the circuit works before cutting metal or etching boards. You can spot errors that would otherwise cost money and time.

ham radio


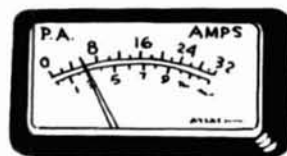
## THE ALL SOLID STATE ATLAS 350-XL

*Its face has many interesting features:*




**350  
WATTS  
SOLID  
STATE  
POWER**

P.E.P. and CW input.
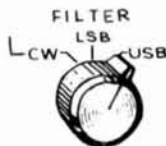
### SSB/CW TRANSCEIVER

SSB with PTT or VOX operation and full break-in CW operation.



### CW-LSB-USB FILTER


Selection of upper or lower side-band with 2700 Hz bandwidth, 1.6 to 1 shape factor, or 500 Hz CW bandwidth with 2.5 to 1 shape factor.

### A.F. NOTCH



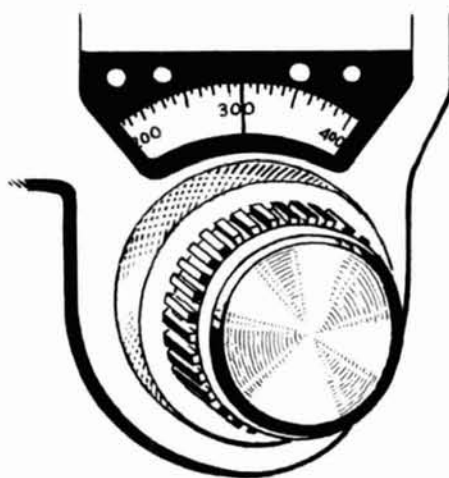
### AF NOTCH FILTER

Provides better than 40 dB rejection of an audio frequency, adjustable from 300 to 3000 Hz.


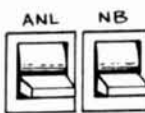
### ANALOG DIAL SCALE

0 to 500 kHz dial scale in 5 kHz increments. Velvet smooth dual speed tuning, with 18 kHz per revolution of fine tuning control.




### ANL AND NOISE BLANKER

Automatic Noise Limiter reduces hash type noise interference which is not intermittent pulse type. Blanker effectively reduces or eliminates pulse type noises.


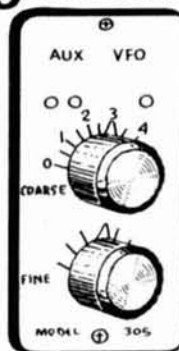
### RECEIVER INCREMENTAL TUNING

Permits receiving up to 5 kHz above or below your transmitting frequency. Especially useful for CW operation or in a net of SSB stations that are on different frequencies.



### PLUG-IN AUXILIARY VFO (Optional)

Can be either a tunable VFO with the same 500 kHz tuning range as primary VFO or a crystal controlled fixed channel oscillator with choice of up to 11 crystal controlled channels.

### 10-160 METERS COVERAGE

Provides a full coverage of all amateur bands in 500 kHz segments.



### AUXILIARY RANGES

Up to 10 additional 500 kHz ranges between 2 and 23 MHz can be added by plugging in auxiliary crystals. (Will not operate between 23 and 28 MHz.)

- ATLAS 350-XL (less options) . . . . . \$995.
- Model DD6-XL Digital Dial Readout . . . \$229.
- Model 305 Plug-in Auxiliary VFO . . . . \$155.
- Model 311 Plug-in Auxiliary  
Crystal Oscillator . . . . . \$135.
- Model 350-PS Matching Power Supply \$229.
- Plug-in Mobile Mounting Bracket . . . . \$ 65.



### DIGITAL DIAL READOUT (Optional)

Provides precise frequency readout within 50 Hz. All L.E.D. Dot Matrix 6 digit display.



**ATLAS  
RADIO INC.**

417 Via Del Monte, Oceanside, CA 92054  
Phone (714) 433-1983  
Special Customer Service Direct Line  
(714) 433-9591



# high-performance 20-meter receiver with digital frequency readout

Design and construction  
of a dual-conversion receiver  
featuring varactor tuning  
in the front end  
and digital display  
of the received  
signal frequency

**Described in this article** is an all-solid-state dual-conversion receiver for 20 meters. It features varactor tuning in the rf, mixer, and high-frequency oscillator and a digital display of the received-signal frequency.

Although the design is for the amateur 20-meter band, it may be easily adapted for a single-band

receiver operating in any amateur or shortwave band between 3 — 30 MHz.

Various LC networks and voltage combinations are used with the high-frequency oscillator, which allows limiting bandwidth to the CW or ssb portions of a band or expanding bandwidth to full amateur-band or shortwave-band segments in the order of 1 MHz.

The receiver portion uses a combination of dual-gate mosfets, fets, bipolar transistors, and ICs. The counter portion uses TTL, low-power TTL, and Schottky TTL logic devices. With suitable selection of HFO and LO frequencies within the capabilities of the Schottky logic upper-frequency limit, the counter may be used up to the 6-meter amateur band with no design changes.

## the receiver

**Fig. 1** is a block diagram of the receiver. It uses the straightforward dual-conversion design approach. Voltage-controlled varactor diodes are used for frequency selection in the HFO and tuning of the rf and mixer input stages. Local and BFO oscillator frequencies are established with crystal control for stability of the i-f. Intermediate frequency amplification and selectivity are obtained with a single integrated circuit in combination with a Collins narrow bandpass mechanical filter (2.1 kHz nominal).

**By M. A. Chapman, K6SDX, 935 Elmview Drive, Encinitas, California 92024**



A simple 5-digit, 7-segment LED display system provides  $\pm 1$  kHz accuracy for the receiver frequency display. It uses input signals from all receiver oscillator sections rather than just the HFO.


A nominal position is provided in the BFO selector switch to provide for interpolating the received signal resting carrier frequency. Incorporated into the audio system is an active lowpass filter, which minimizes spurious noise and i-f heterodyne signals, thus optimizing the receiver signal-to-noise ratio.

**Frontend.** Fig. 2 illustrates the frontend design. Moderately high Q coils are used in the rf and first mixer input. High Q coils in the rf section provide excellent signal-to-noise ratios, good selectivity, and high initial gain. Back-to-back varactor diodes are used for tuning the rf LC circuits by front-panel potentiometer control of the varactor diode bias voltage.

From fig. 2 we see that the first i-f is 1500 kHz, and the second conversion i-f is 455 kHz. As shown in fig. 2, the gates of the second mixer stage incorporate bias adjustment to optimize both device gain and signal-to-noise ratios. Gate biasing for rf and mixer may not be immediately apparent from fig. 2. Fig. 3 shows how the mosfets in the rf and mixer are biased and the method used to compensate for tolerances in the LC circuits to permit gang tuning of both stages.

The upper section of fig. 3 is a simplified ac model illustrating the tuned-circuit relationships. It's important to note that, from an rf standpoint, the cold end of the LC circuits is at ground potential as are the source and control gates of both devices. The lower section of fig. 3 includes the varactor diode and source-swamping-resistor relationship to the device. Here again, we see that the cold ends of the LC circuits are at ac ground and that the source swamping resistor is shunted to ground.

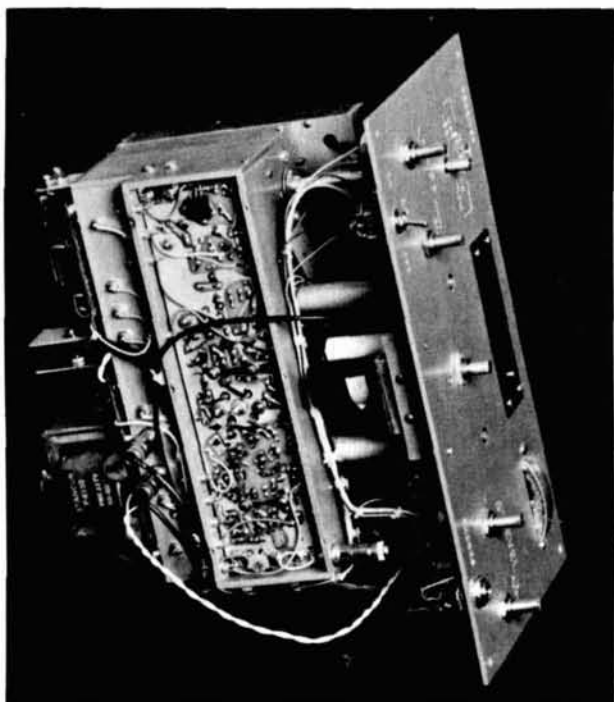Since the rf amplifier and mixer are depletion mode devices, you can adjust the input voltage to the gates of Q1 and Q2 so that the gate-to-source bias is approximately  $-0.5$  volt. Tuning the varactor diode is accomplished by applying a positive voltage greater than that required for bias of the gate source



Bottom view of the receiver. A portion of the power supply board can be seen on the left.


terminations. The varactor must be reverse-biased for it to operate in a nonconductive state and act as a variable capacitance across the inductors. For initial setting of the rf and mixer stages, bias voltage no. 1 should be adjusted for 0.5 volt differential bias to the source voltage point no. 3, with the control gate at maximum voltage (approximately 8 volts dc).

The initial bias and source-point voltages will be approximately  $+0.75$  volt. Examining the voltage divider network in the varactor diode tuning circuit, we see a minimum positive voltage of approximately 2.25 Vdc, providing a 1.50-volt reverse bias in the worst case and an 8 Vdc bias in the high case. You can optimize the voltage-divider circuit after assembly and test to increase or decrease the band-spread capabilities. Tuning the 20-meter band will require about 1.5 volts of differential. If you wish, optimizing can be implemented, so that the differential occurs on the major portion of the potentiometer adjustment range.

To minimize alignment difficulties, Q1 and Q2 should be matched for nominal  $I_{DSS}$  values, so that bias voltages 1 and 2 will require a minimum amount of adjustment to compensate for varactor diode and shunt-capacitance tolerance. Much variation exists between varactor nominal capacitance and capacitance change, with respect to voltage change when tuning the rf circuits. Compounding the problem is the nonlinearity that exists with the diode elements themselves. Since the Q of the rf input and mixer input circuits is quite high ( $\sim 75$ ), any differences be-

Author Chapman has provided much detail in his description of the design and construction of this receiver. The article is in two parts. Part one describes the basic rf and i-f circuits, and part two deals with the digital readout system. The digital readout system may be readily adapted to almost any receiver design. If you're interested in duplicating the receiver without the digital readout, you'll find the information you'll need in the following material. Part two, to be published in a subsequent issue of *ham radio*, wraps up the entire project and provides much useful information on calibration and alignment. Editor.



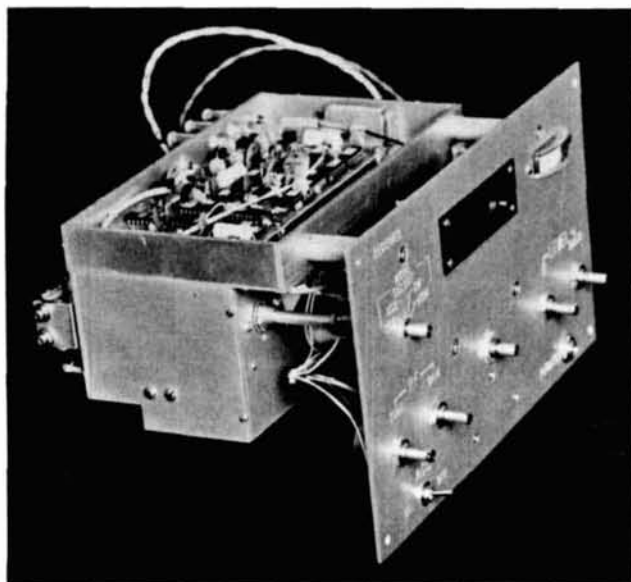

Side view of the receiver showing the rugged mechanical construction.

tween the diode-versus-voltage capacitance will result in circuit detuning.

Referring to **fig. 2**, the mixer gain control gate (G2) is at a fixed-voltage point and the rf stage uses a variable resistor to control the rf gain. One disadvantage of this scheme is that, as we vary the voltage

limited segments of a band (for example, the CW section), then very little rf **TUNE** adjustment is required. However, if a number of changes are made to the mixer gain, a corresponding adjustment to the **TUNE** control is necessary.

**I-f amplifier.** I-f amplifier gain and bandpass filtering is accomplished with an LM373H IC and a narrow bandpass Collins mechanical filter (**fig. 4**). The LM373H (U1), in addition to providing high i-f gain, also acts as the detector for both CW and ssb. Incorporated in its design is the ability to use agc or external manual i-f gain. An agc-level sensitivity control is included.

The voltage value indicated for initial adjustment of U1 represents an agc threshold setting of approximately 300 microvolts. To provide isolation of the detected audio output to the S meter and audio filter stages, a simple fet amplifier stage is incorporated (Q4). Almost any depletion-type device may be used in this stage by adjusting the source and drain resistors to obtain a voltage gain of approximately 5, as indicated. The minimum source bypass capacitance should be in the order of 10  $\mu$ F.

The Q4 output coupling capacitor should provide a low reactive impedance to the S meter and audio filter input to minimize signal loss at the low (150 Hz) signal levels. However, scaling of the S-meter input

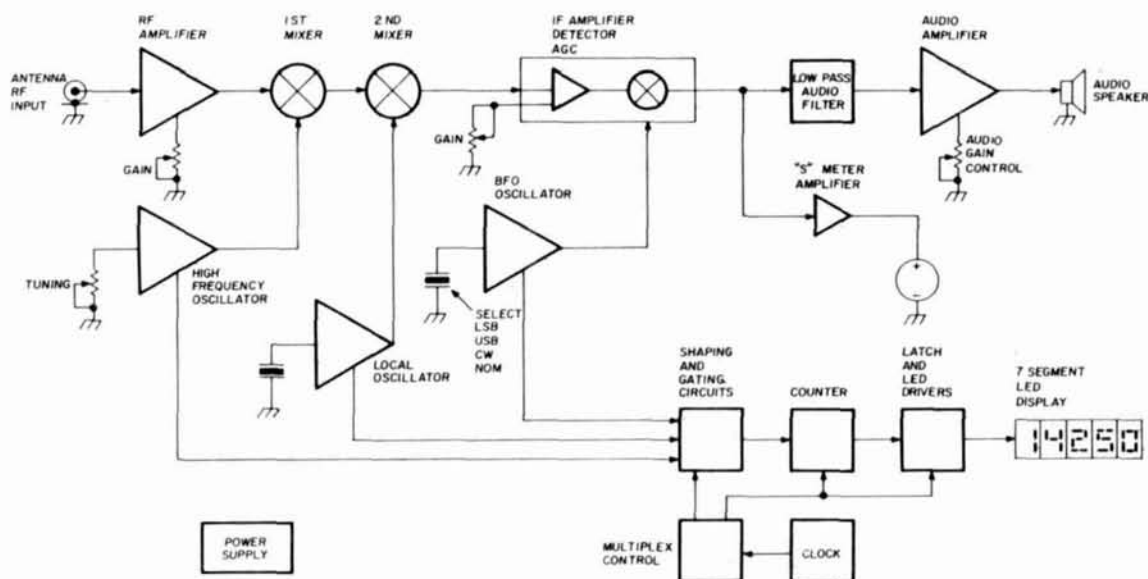


fig. 1. Block diagram of the 20-meter high-performance receiver.

of Q1 gate 2, causing a change in the varactor diode bias and its capacitance, a slight detuning occurs in the LC circuits.

When the gain level is adjusted to any appreciable extent, then the **TUNE** control must be repeaked to maintain overall-receiver gain. When operating over

is possible, since at this point we are only interested in the audio voltage level — very little current is drawn by this or the succeeding stage.

The S-meter amplifier is fully described in reference 1. The builder may elect to use either of the S-meter circuits described in the referenced article

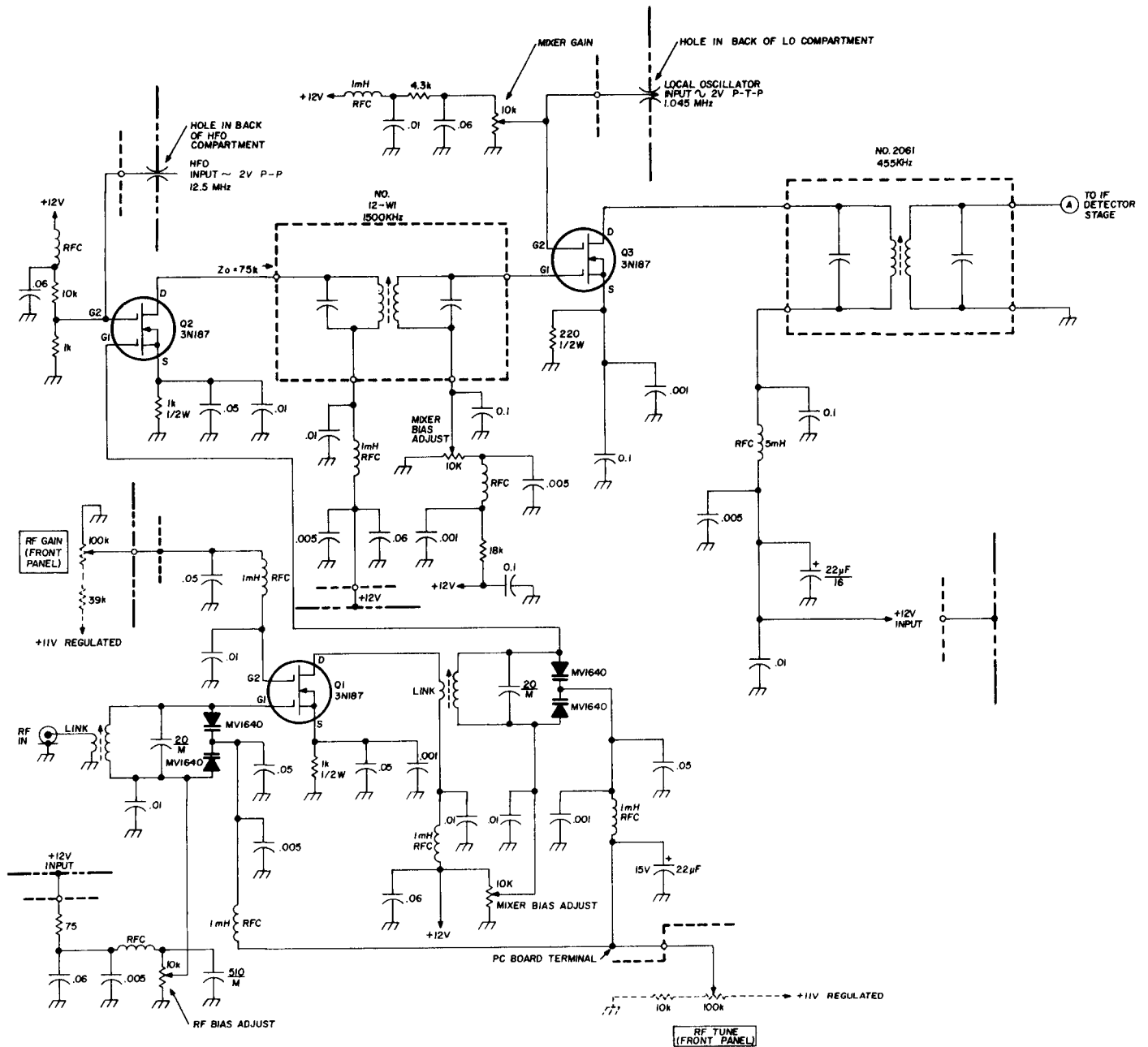


fig. 2. Rf and mixer schematic.

depending upon panel layout preference, and availability of meters.

**High-frequency oscillator.** An extremely high stability HFO is illustrated in fig. 5. This is an adaptation of the design discussed in reference 2 using a Goral buffering scheme. I've used this oscillator technique from 1 to 50 MHz with various LC combinations, changing only the source and emitter load inductors. An alternative device providing equal or better output voltages is the Motorola MPS-A09 bipolar transistor. Since the mixer-stage gate and counter input circuitry are high impedances, very lit-

tle signal loss occurs, and you should expect to see the output levels indicated on the diagram.

Substitution of alternative inductive loads can affect the output voltage levels. Use care to obtain the peak-to-peak values indicated in all oscillator stages.

Tuning of the varactor (VVC, MV1654) is accomplished using a positive voltage of approximately 6 to 7.5 Vdc. Since the first i-f is 1500 kHz, and down conversion is used, the HFO output, then, is between 12.5 MHz - 12.85 MHz to cover the 20-meter band (14 - 14.35 MHz). Considering that 1.5 volts of differential bias on the varactor is necessary, the fre-

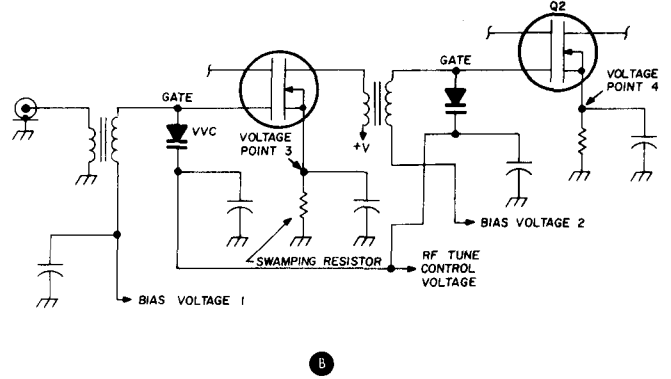
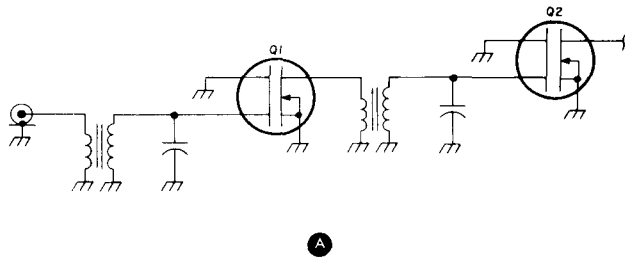


fig. 3. Rf amplifier tuning and bias schematics. Sketch A is a simplified ac model illustrating the tuned-circuit relationships. Sketch B includes the varactor diode and source-swamping-resistor relationships.

quency stability is more sensitive to power-supply ripple variations than the oscillator described in reference 3; therefore, a high-performance voltage reference supply is necessary to maintain a stable voltage on the varactor to minimize frequency drift. Presuming that the power-supply scheme illustrated later is used, and that good packaging and component selection is followed, you can expect a frequency drift of less than  $\pm 100$  Hz/hour after thermal equilibrium.

**Local and beat-frequency oscillators.** The local and beat oscillators are described in figs. 6 and 7 respectively. Simple fet oscillators are used. Many fet substitutes will perform equally as well. The output voltages are as indicated on the schematic. Good-quality parallel-resonant crystals should be used, with only the nominal 455-kHz crystal requiring careful selection of the shunting capacitor, since this

will determine your transmit-frequency reference in the counter display.

Any errors introduced into the local-oscillator center frequency can be compensated by shifting the HFO frequency and tweaking the 1.5-MHz i-f transformer (fig. 2).

Caution note: the LM373H (U1) of the i-f detector stage is sensitive to excessive BFO injection voltages. The nominal input voltage to U1 for BFO detection is 60 millivolts rms. Slightly higher levels will increase the detected audio levels. A too-high injection level will result in audio motorboating and distortion; too low an injection level will result in poor or weak audio detection. To minimize generation of spurious and harmonic frequencies from feeding into other parts of the receiver, generous use is made of RC decoupling and bypass capacitors. Feel free to substitute capacitor values in these circuits with

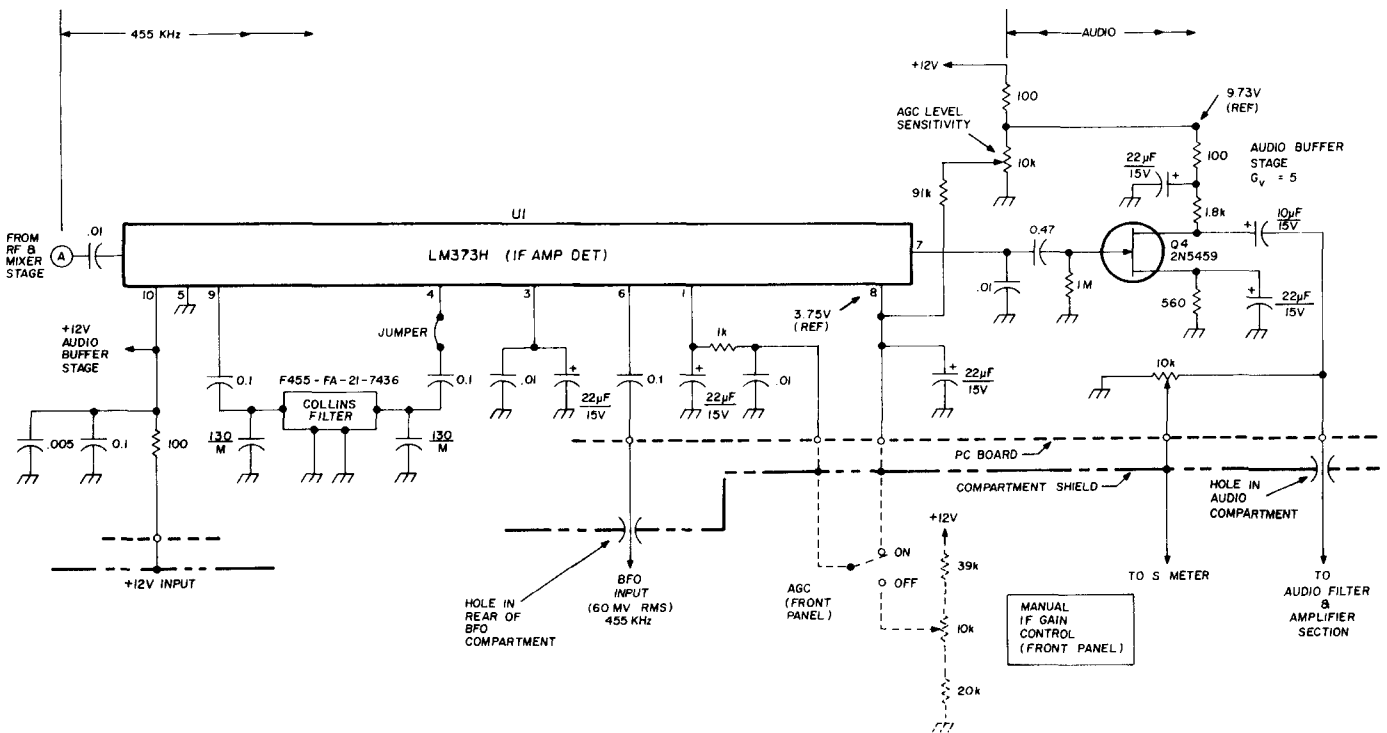


fig. 4. I-f amplifier, detector, and audio buffer schematic.

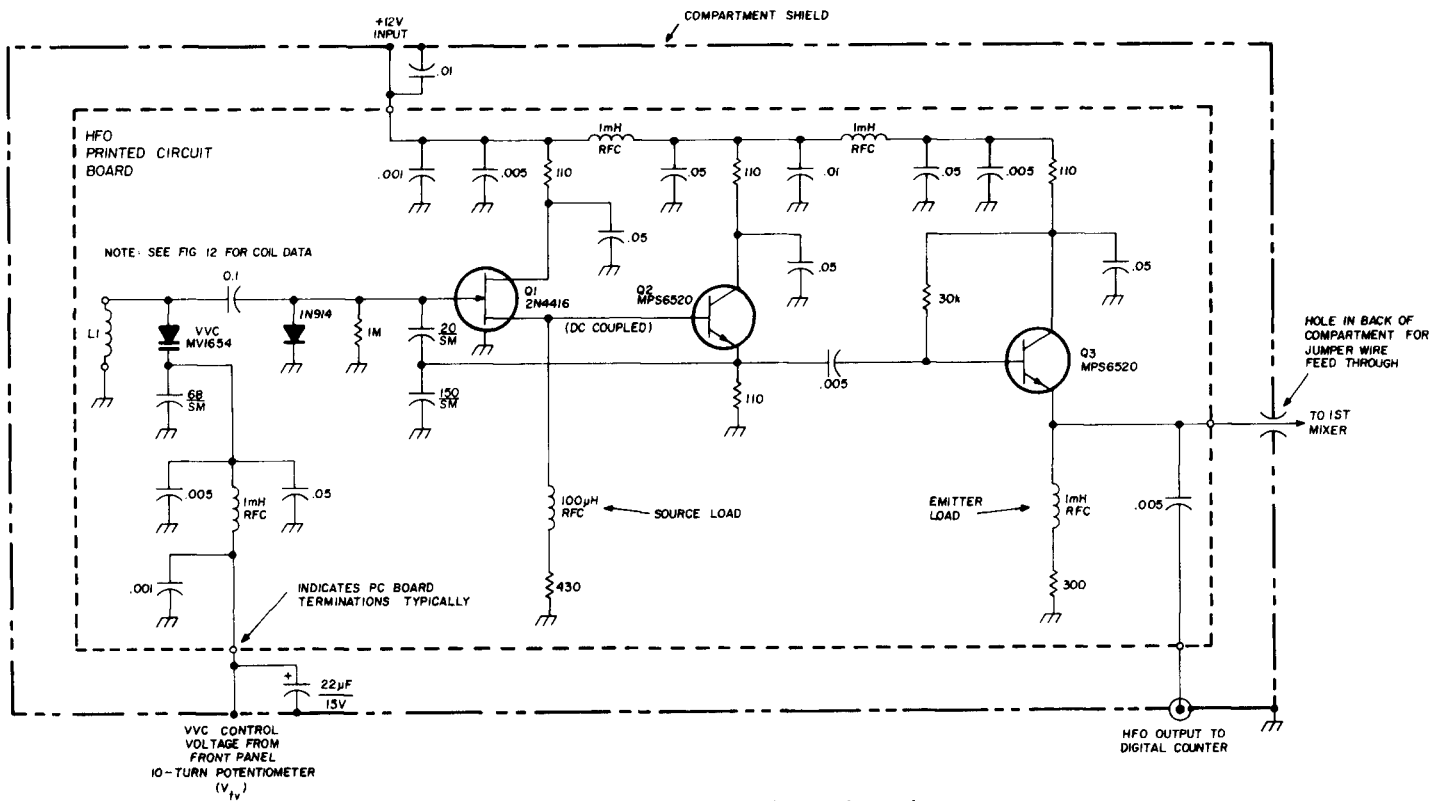


fig. 5. High-frequency oscillator schematic.

whatever is available, so long as the dc input is kept reasonably clean of the oscillator-frequency components.

The LSB and USB crystal frequencies may be determined by either measuring the Collins 455-kHz mechanical filter for the 20-dB passband points or by ordering a filter that has been measured by the manufacturer for the L20 and H20 dB points. An additional description is given in reference 4 and in the alignment and calibration sections of the article.

**Audio filter and amplifier.** The detected audio from Q4 is passed through an active lowpass filter-operational amplifier arrangement and further amplified in a one-stage 2-watt audio amplifier U3 (fig. 8). The U1 and U2 lowpass filter design is discussed in considerable detail in references 4 and 5. Normally, U1 and U2 operate from a plus and minus voltage source; however, a simple voltage-divider circuit on pin 3 of U2 establishes an artificial ground for both U1 and U2. The lowpass rolloff starts at 2500

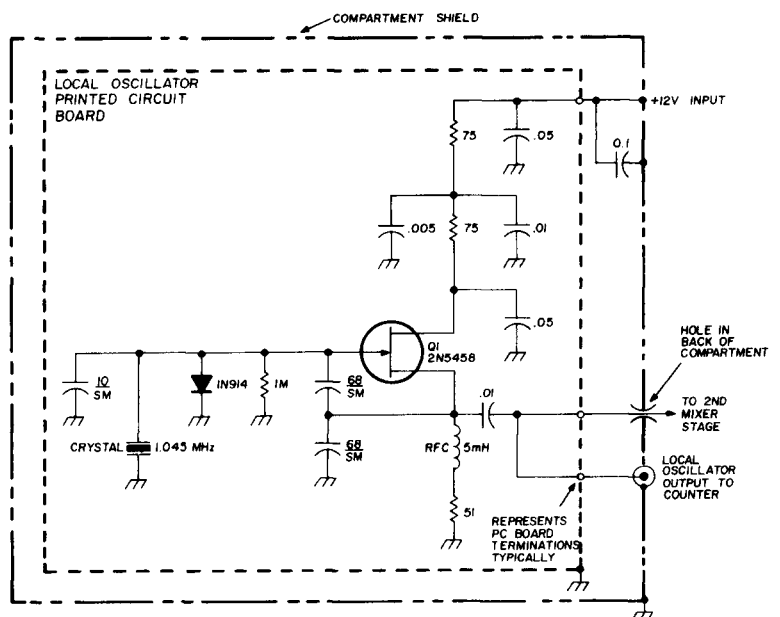


fig. 6. Local-oscillator schematic.

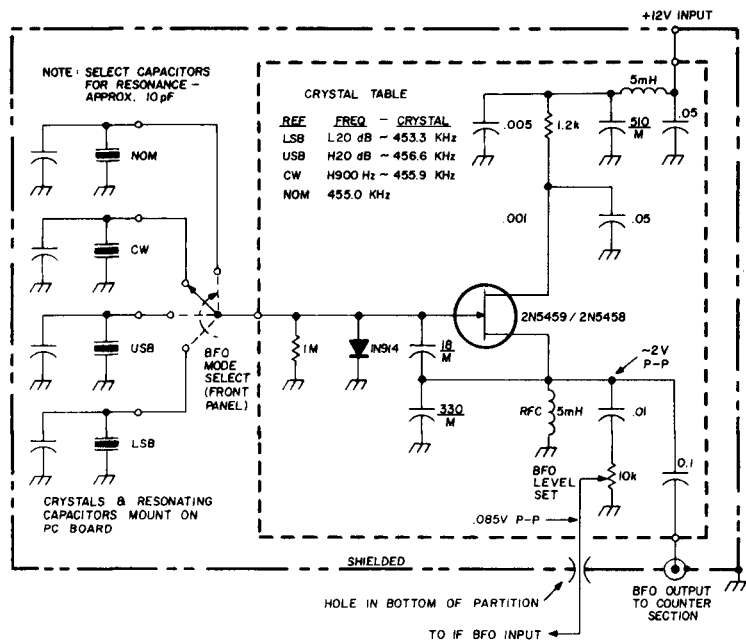


fig. 7. BFO schematic.

Hz, and a 15-20 dB attenuation of all higher audio frequencies is achieved. The normal i-f heterodyne hiss is greatly attenuated, and the receiver overall signal-to-noise ratio is enhanced. An additional high-frequency audio rolloff is achieved by the selection of the 680 pF mica feedback compensating capacitor of U3.

Audio and rf have many common grounding and feedback problems. To minimize circulating ground loops and achieve low-noise performance, a single-

point ground system should be used with the audio circuit. As an aid, those items of special significance are indicated as notes in fig. 8.

Notes 1 and 2 are self-explanatory; note 3 deserves some additional comment. A 1-meg level-set pot is shown between U2 pins 2 and 7. As the name implies, it establishes U1 and U2 output gain in combination. Ideally the gain is unity; however, since we're operating these devices  $\pm 6$  volts dc the overall gain will be in the order of 0.8-0.9. To obtain the best

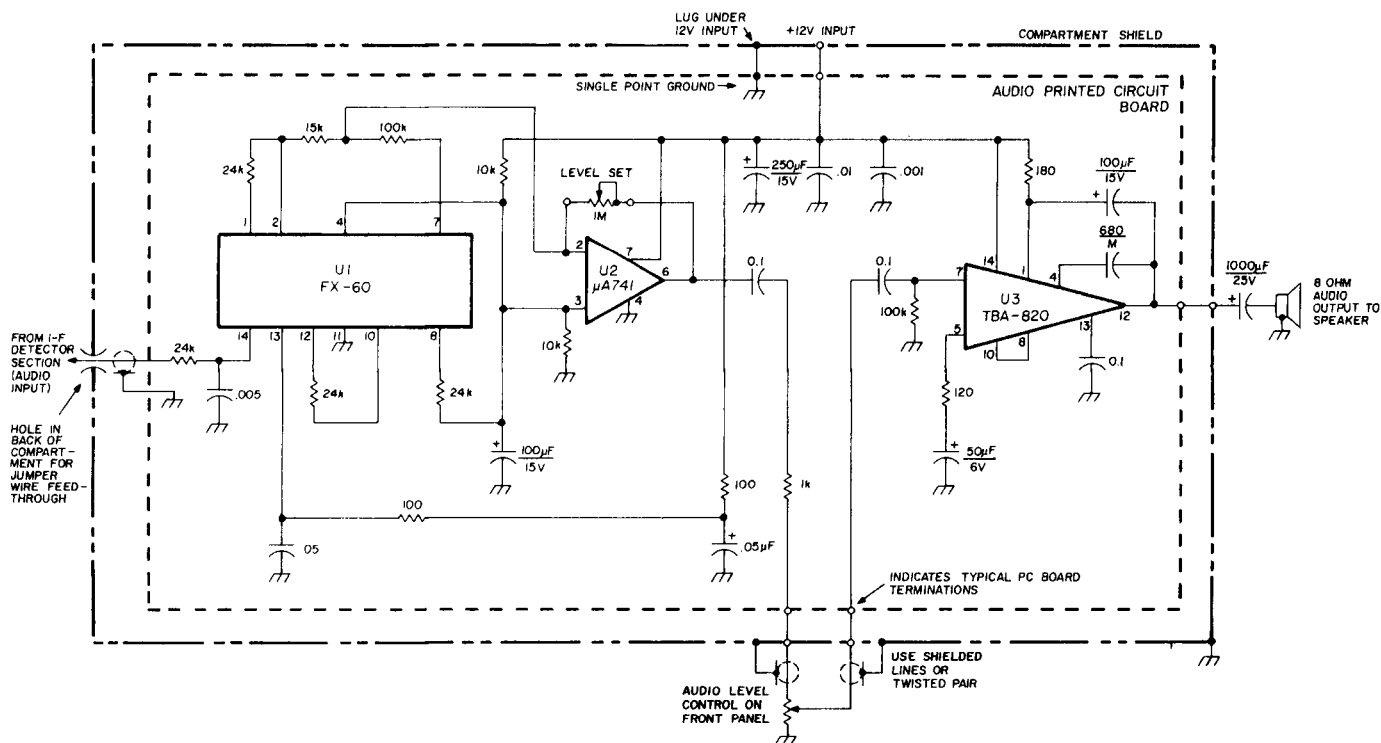


fig. 8. Audio filter and amplifier schematic.

setting for the level set, a low-level 50-100 millivolt audio signal should be coupled to U1 input through a 0.01  $\mu\text{F}$  capacitor while monitoring U2 and U3 output with a high-impedance scope. The level-set pot should be adjusted where the gain is about 90 per cent of maximum over the frequency range 150 Hz-2500 Hz. Then the pot may be removed and a fixed resistor installed with a value closest to that measured on the pot. The value of this resistor will be approximately 100k.

As in the other low-level audio-signal processing circuits, this is not the place to use an inexpensive, exposed wiper-type volume control. The added cost of a sealed, 2-watt type component with the case securely grounded to the chassis and panel will minimize wiper contact noise and ground problems. Use of 1/2-watt resistors in the low-level audio stages has been included in the PC design layout for additional noise control.

**Power supply.** The power supply and high-frequency oscillator varactor control system are illustrated in fig. 9. Three-terminal 7800-series voltage regulators are used for the +12 and +5 Vdc requirements. To minimize power dissipation and provide for a constantly changing current demand from the LED displays, a preregulator/derippler circuit is used ahead of the +5 Vdc regulator. A small amount

of series resistance isolates the display voltage from the +5 volt logic voltage.

To establish a stiff reference voltage for the HFO varactor diode ( $V_{FV}$ ), a precision voltage regulator is used (U2). Ripple rejection is in the order of 80 dB, and voltage stability is in the order of a few millivolts per degree F. Two small 10-turn trim pots allow fine tuning of the high and low end of the 10-turn  $V_{FV}$  voltage pot. A similar voltage control system is described in reference 3. Additional capacitive filtering will aid in the reduction of  $V_{FV}$  ripple content and may be added at your discretion.

Filtering across the  $V_{FV}$  10-turn pot should not be added, because such filtering will increase the HFO control-voltage time constant. Any added filtering should be used ahead of the trimpot or preferably U2.

### construction

Modular PC board construction is used, with each major function individually packaged on a separate board and isolated in an rf-tight housing. The photos clearly illustrate the relative board positions and techniques for interfacing the rf and audio circuits, as well as the method for isolating and developing the +12 source voltage between the receiver stages. Each functional section has its own +12-volt input

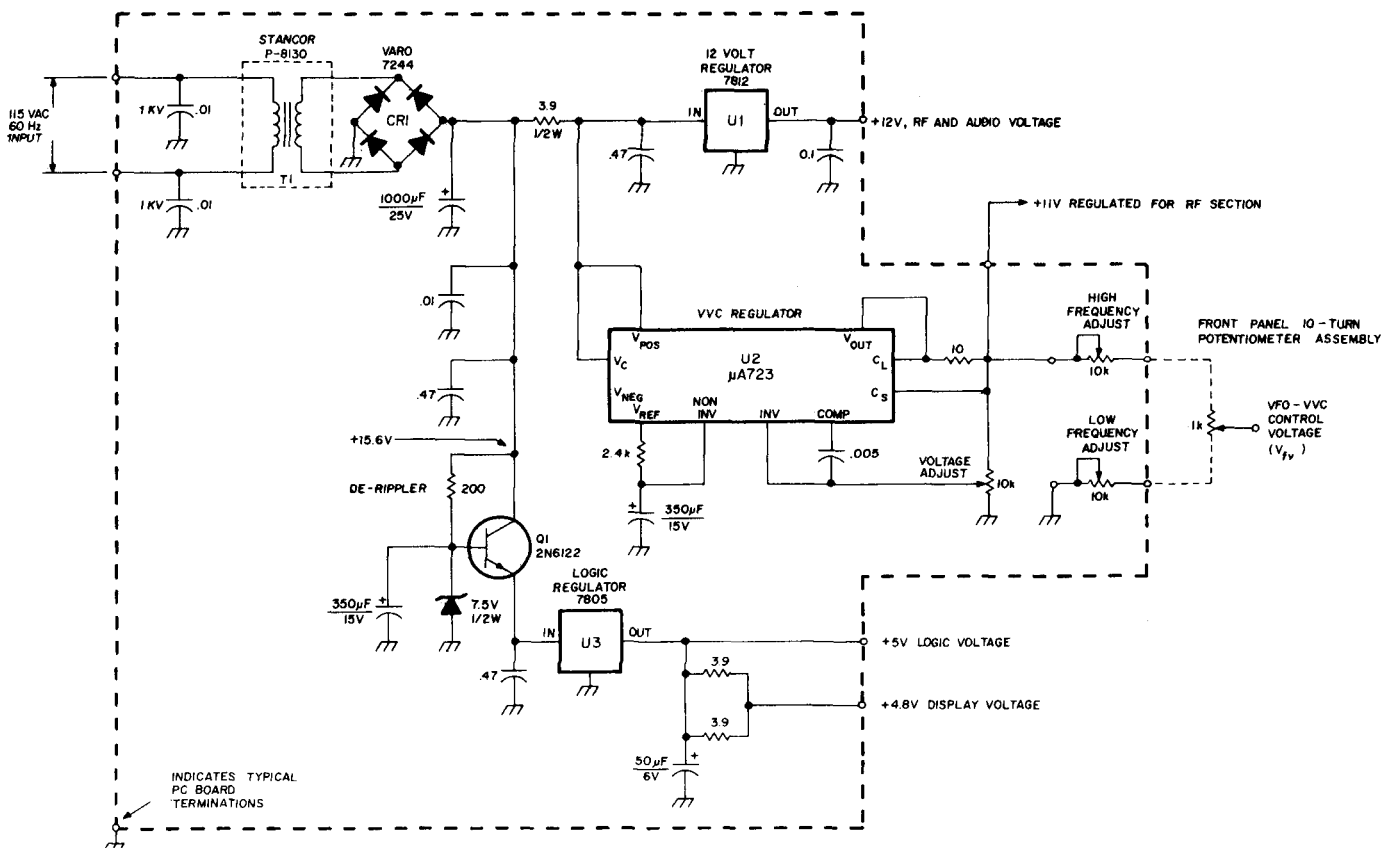


fig. 9. Power-supply schematic.

terminal, which is filtered at the board termination point.

**Front end and i-f amplifier/detector.** The rf, mixer, i-f and detector functions are located on one inline PC board (fig. 10). Heavy, well grounded shields are used between the rf, mixer, and i-f/detector sections, which also provide convenient mounts for the large coils of the rf circuits. Two standard, readily available i-f transformers are used in the drain circuits of Q2 and Q3, which are shielded with their own housings. Many 455-kHz i-f transformers having the same or similar geometry as the 2051 unit used here are available. If necessary, the board could be cut open and the alternative unit mounted in piggyback style.

If you'd like to operate the receiver at frequencies above 15 MHz, the 12-W1 transformer may be opened and the internal padding capacitors changed to allow for a higher first i-f more consistent with a good 10:1 rf mixer frequency ratio. If you elect to use an unprotected dual-gate mosfet device in the rf stage, provisions exist for the installation of back-to-back 1N914 gate-protection diodes; however, at higher frequencies this additional shunt capacitance could materially affect the signal level.

The Collins mechanical filter mounts directly to the board. However, several foreign-made filters of comparable performance are available, which will mount in this area of the board. Short jumper wires can be installed to interface with the input-output pins of the LM373H. Provisions are included on the board for an impedance-matching resistor to be installed in place of the jumper wire input to U1 and the i-f detector from the filter.

Inexpensive 0.1-inch (2.6mm) center trim pots

were used; however, after measuring the desired resistance values required for the S-meter, agc, and bias circuitry, fixed carbon composition resistors mounted vertically to the board could be used.

**High-frequency oscillator.** The high-frequency oscillator PC component layout is shown in fig. 11; fig. 12 shows the winding and coil data. As discussed in reference 3, a variety of LC, varactor-diode combinations are possible for this construction. Provisions exist for mounting two varacaps back-to-back on the board, and space is available for the addition of an extra shunt capacitor. The HFO output signal to the mixer should have the shield terminated on the HFO board and should be unterminated at the mixer input. Note that the board should be *well-grounded* to the chassis. Since the  $V_{FV}$  voltage is at a dc level, there should be no need to use shielded wiring unless an alternative packaging technique required different routing of this wire.

**Local oscillator.** The local oscillator is mounted on an independent PC board, as shown in fig. 13. Wiring and installation is straightforward. Many crystal sizes can be accommodated on this board. Provisions are included for an optional ceramic or air type trimmer capacitor. However, an error of 2 or 3 kHz is not harmful since this error can be compensated for in the final HFO trimming and adjustment. Crystals with low ESR (sluggish) will not operate well in this circuit and may have a slight tendency to drift, so purchase good-quality crystals or use an alternative circuit similar to the oscillator circuit described in reference 4.

**Beat-frequency oscillator.** The beat-frequency oscillator is also mounted on an independent PC

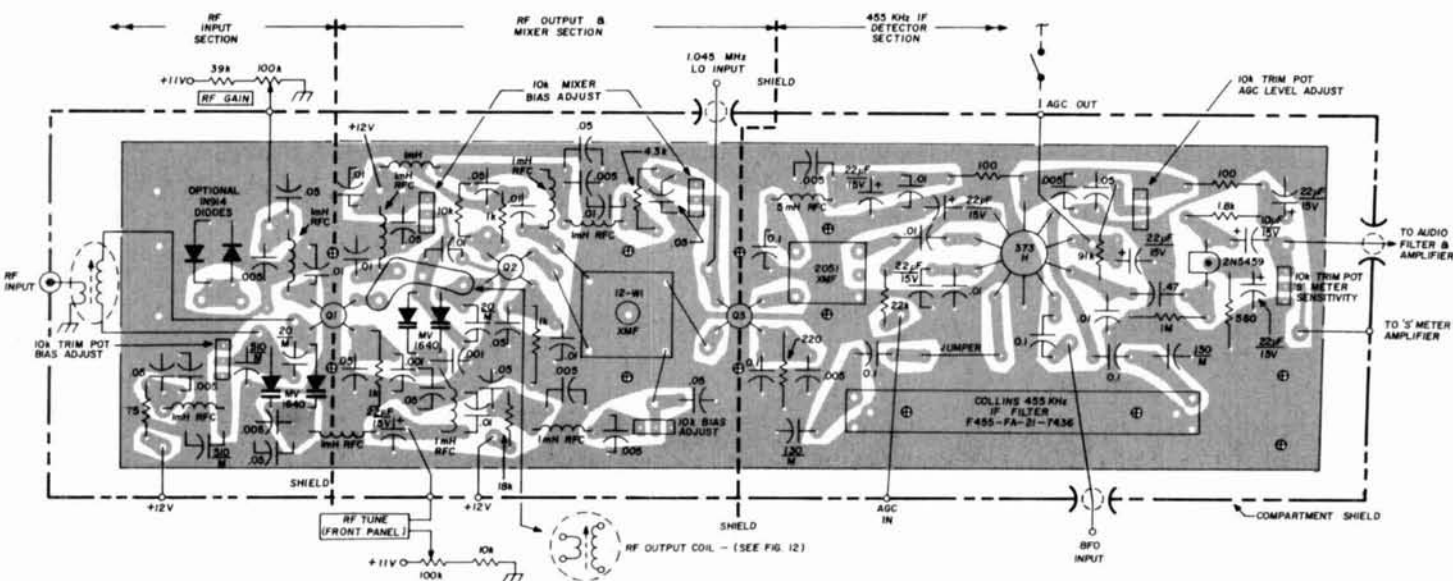


fig. 10. RF amplifier, mixer, and i-f/detector PC-board assembly. A complete set of circuit board layouts is available by sending a self-addressed, stamped envelope to *ham radio*, Greenville, New Hampshire 03048.



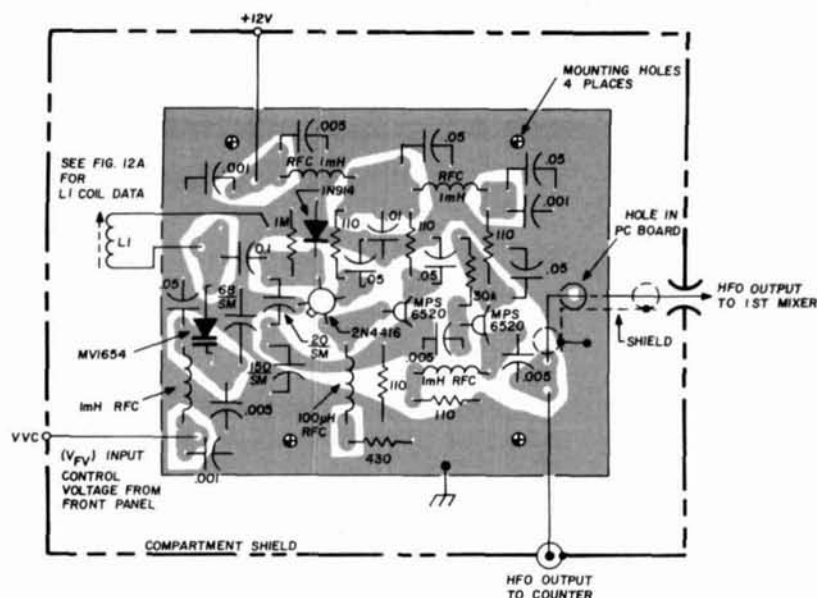


fig. 11. HFO PC board layout. Printed circuit boards for the rf portion of the receiver are available from the author for \$11.25, ppd.

board (fig. 14). The board assembly mounts directly to the switch mounting hardware behind the switch deck. The switch is a Centralab PA-3 with a PA-2 nonshorting 2-6-position deck. Wiring from the PC board to the switch terminals is illustrated in the figure.

As in the local-oscillator board, the crystals are soldered directly to the board; either standard or wire-type crystals may be used. I recommend that all crystals be of the same type to minimize any temperature variations and to provide equal output levels to the counter and mixer input circuits.

As previously mentioned, the USB and LSB crystals depend on the filter 20-dB passband points. With foreign mechanical filters, my experience has

been that the filter center frequency may not be at the nominal 455-kHz resting point, but may vary as much as  $\pm 5$  kHz from this point. If an alternative i-f filter is used, the center-frequency response and that at 20-dB points should be measured as accurately as possible for optimum receiver performance.

The CW crystal is normally  $\pm 800$ -1000 Hz from the center i-f filter frequency. It should be selected according to your preference. Use an audio oscillator to determine the preferred beat oscillator note, when ordering a corresponding BFO CW crystal.

A unique calibration scheme is described in part 2 of this article, which uses the CW and BFO frequency. During tests of the BFO, an accurate measurement of the CW BFO oscillator frequency should be

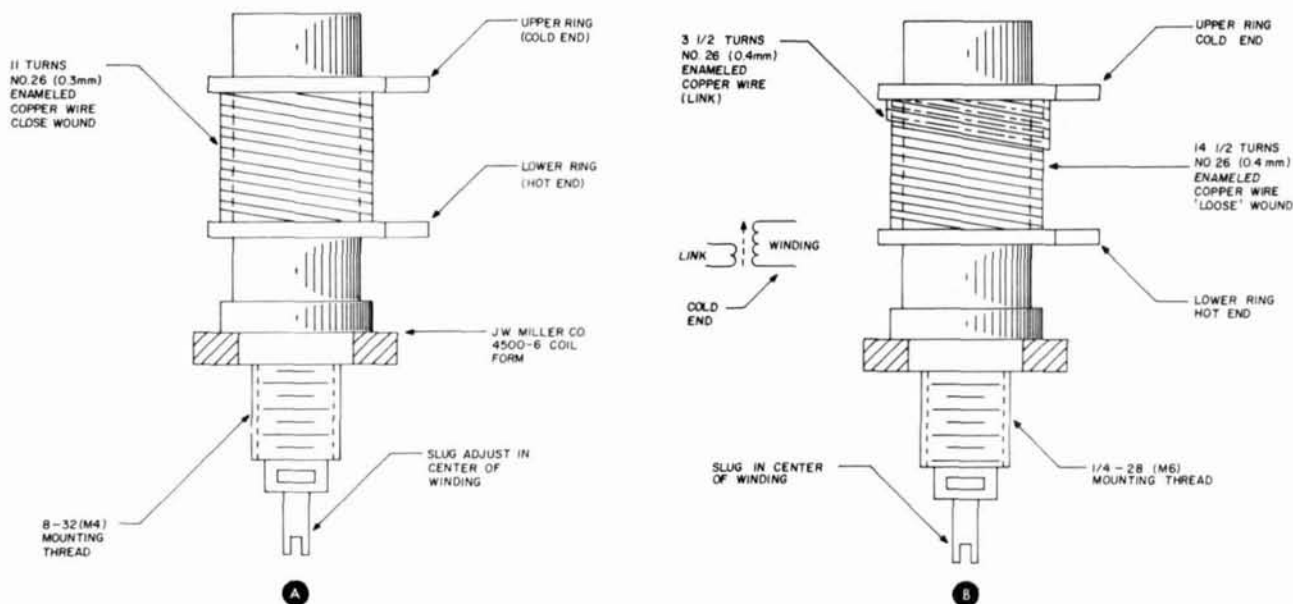


fig. 12. Construction details for the hf oscillator coil, A, and rf and mixer coils, B.

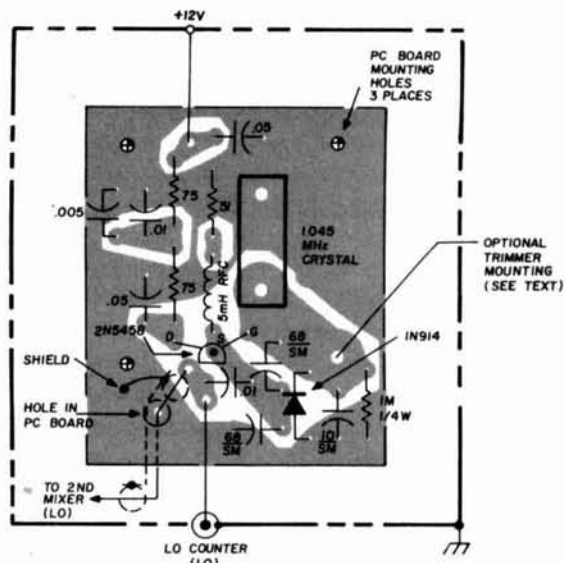


fig. 13. Local oscillator PC-board layout.

made if the crystal frequency is other than  $\pm 1000$  Hz from the filter center frequency. This will allow you to adjust the clock frequency accurately in the counter for the correct display. Both the local oscillator and BFO oscillator PC assemblies should be hard mounted to the chassis, using short aluminum standoffs for good grounding.

**Audio filter and amplifier.** The audio filter and amplifier are included on one PC board assembly, fig. 15. Terminals from U1 and U2 must be removed from the integrated circuits before installation. The FX-60 device may be mounted to a 14-pin DIP socket or soldered directly to the board. Grounding within the audio section is important, so a single-point

grounding scheme illustrated in the component layout of fig. 15 is recommended. The PC board should be isolated from the chassis using nylon hardware. The audio input shielded lead should be grounded at the PC board input and left floating at the detector output. Because of the large size of the audio output capacitor, I recommend that this component be located externally, near the speaker or speaker output terminal.

**Power supply.** The power supply component layout is shown in fig. 16. Heatsinking of Q1, U1 and U3 is mandatory because of the power dissipation of the regulator devices. The power supply photograph illustrates the technique I used, wherein a small piece of aluminum sheet was bent up, with holes drilled in the side and bottom. Since Q1 collector is not operating at ground potential, its case must be insulated from the heatsink. However, the common terminals of U1 and U3 are at ground potential, and their cases may be tied directly to the heatsink. A small amount of silicone grease under the mounting surfaces of these components will aid in thermal conduction. The peak power dissipation values are indicated on the schematic (fig. 9), as a reference for the builder to size the heatsink.

A small aluminum angle bracket is mounted on the end of the PC board assembly to support the HFO trimming resistors; however, these parts can be located at any convenient point on the chassis or next to the 10-turn HFO control on the front panel. The precision voltage regulator, U2, may be mounted to a standard 14-pin DIP socket or soldered directly to the board. Do not forget to add the short jumper wire shown on the back side of the PC board layout of fig. 16.

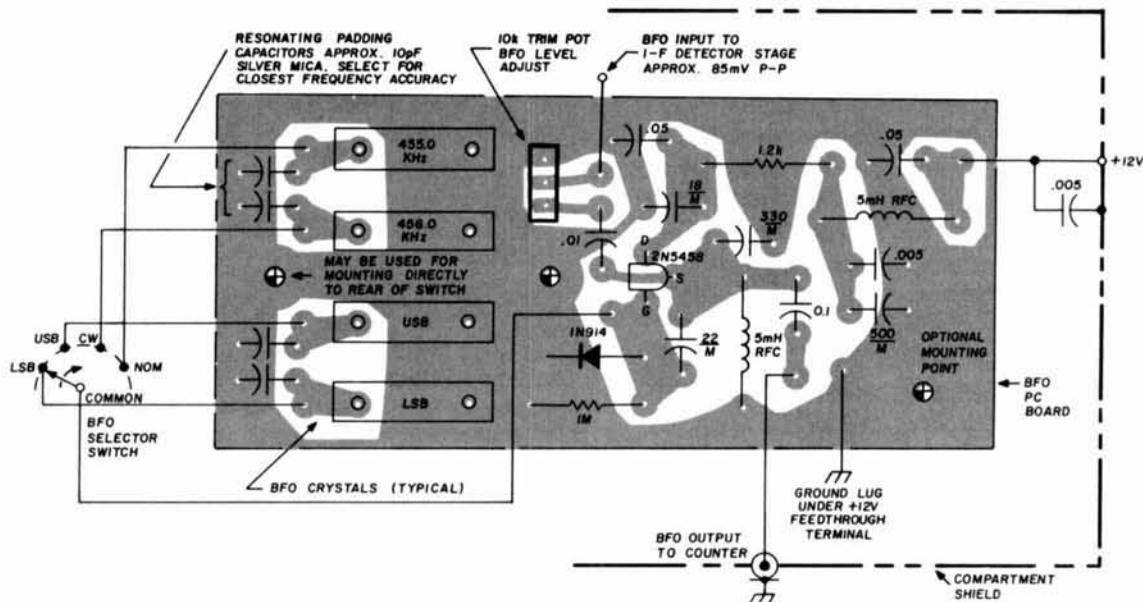


fig. 14. Beat-frequency oscillator PC-board component layout.



Remove the temporary 0.01- $\mu$ F capacitor from G2 of Q3.

2. Temporarily install a 0.01- $\mu$ F capacitor to Q2 gate 1 on the foil side of the board, as in **step 1**. With external controls set in the positions as previously indicated, apply a 1.5 MHz CW signal of 1 millivolt to the 0.01  $\mu$ F capacitor.

Adjust the mixer bias controls for Q2 and Q3 and the 1.5 MHz interstage transformer in the drain circuit of Q2, with power applied. Monitor the audio output as in **step 1**. With the signal level indicated, a minimum detected audio output of 6 volts peak-to-peak should be observed. Remove the 0.01- $\mu$ F capacitor from Q2 gate 2.

3. Temporarily install a 0.01- $\mu$ F capacitor to the drain terminal of Q1, foil side. With the front panel controls set as previously described, apply +12 V power and approximately +6.5 volts on the VVC  $V_{FV}$  voltage point of the HFO module. Apply a 1 millivolt signal of 14.125 MHz to the temporarily installed capacitor and adjust the rf gain and rf tune controls for maximum detected output. Adjust the rf bias pot on G1 of Q1 so that reverse biasing of the tuning diodes is ensured. With a CW signal applied as described, and all bias adjustments optimized, a 4.5-volt minimum peak-to-peak signal should be obtained at the audio monitoring point.

Remove the 0.01- $\mu$ F capacitor from the Q1 drain.

Note that some minor adjustment of the +6.5-volt  $V_{FV}$  voltage will be necessary to obtain conversion of the injected signal but should be somewhat less than 8.0 Vdc if the HFO oscillator slug is properly positioned.

4. Install a 0.01- $\mu$ F capacitor on the antenna input

link of the rf input tuned circuit. Position all controls as previously indicated, apply power and VVC  $V_{FV}$  control voltage. Inject a 30- $\mu$ V signal at 14.125 MHz, unmodulated, to the input capacitor. Adjust the  $V_{FV}$  voltage for obvious beat-detected audio output. Peak the rf tuning and bias adjustments along with the first and second i-f transformers. Repeaking of these controls should be done several times to optimize the detected audio signal.

With a 30- $\mu$ V signal applied as indicated, a clear detected audio output of approximately 7 volts peak-to-peak should be observed. Reduce the input signal to 0.5  $\mu$ V. A 1.0-p-p signal should be observed at the audio output.

Temporarily ground the input to the receiver and observe the audio output, which should be in the order of 0.25 volt peak-to-peak while varying the  $V_{FV}$  voltage from +4 to +12 volts. There should be no observable birdies or spurious audio output spikes over this frequency translation of the HFO. Using these values, the noise figure under test conditions is given by:

$$\frac{\text{signal} + \text{noise}}{\text{noise}} = 20 \log \frac{V_1}{V_2}$$

$$\frac{\text{signal} + \text{noise}}{\text{noise}} = 20 \log \frac{1.0}{0.25} \quad (1)$$

$$\text{signal} + \text{noise} \cong 12 \text{ dB}$$

Additional reduction of the input signal should indicate observable detected signals with input levels of 0.1  $\mu$ V or less.

5. Measure the  $V_{FV}$  voltage required by the HFO varactor diode to produce the differential frequency

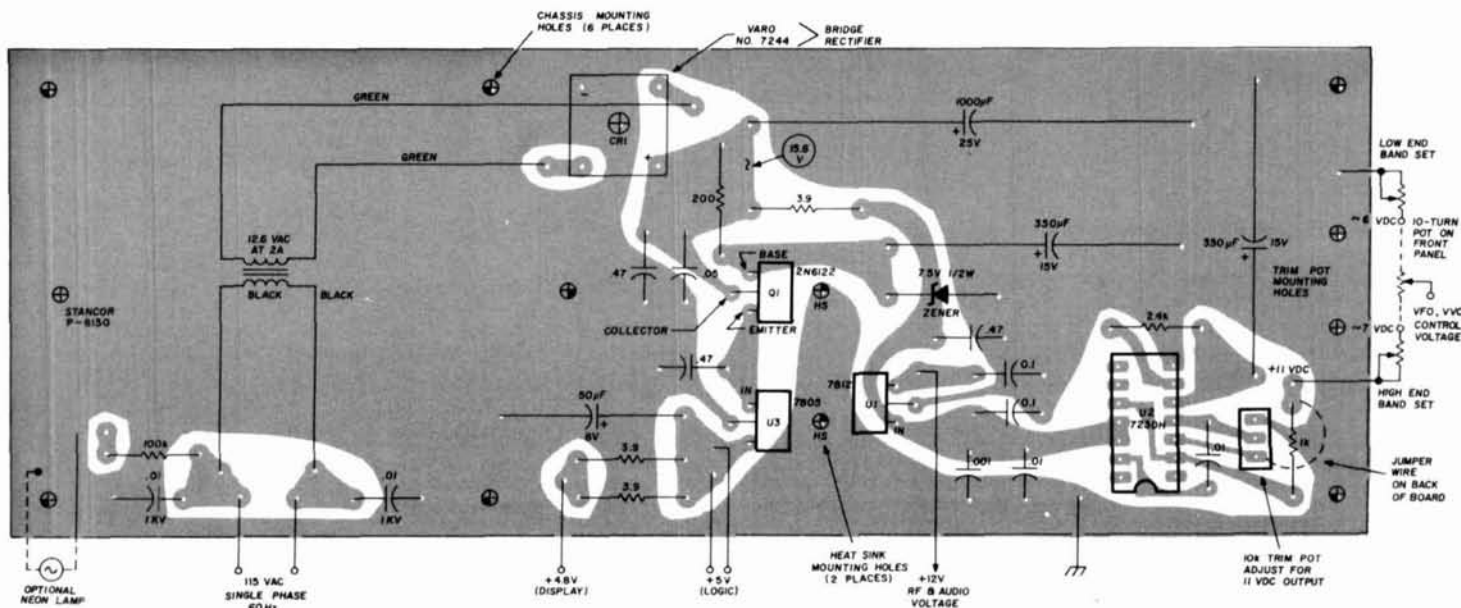


fig. 16. Power supply PC-board layout.



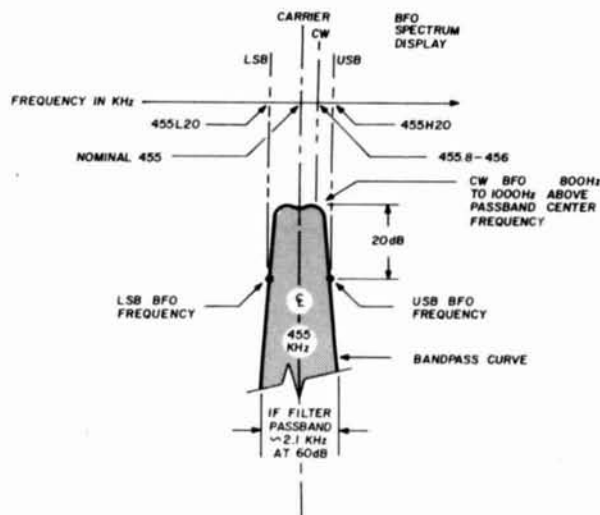


fig. 17. BFO versus i-f bandpass relationship (see text).

range desired; i.e., 12.5-12.85 MHz for standard 20-meter-band use. This voltage should be approximately 6-7.5 Vdc.

Apply ac line voltage to the power supply and adjust the trimpots for the  $V_{FV}$  voltage to correspond to the measured values determined above.

6. Mount the power supply and interconnect the wiring. Using an external signal generator, introduce a 10- $\mu$ V signal of 14.0 MHz and adjust the low end  $V_{FV}$  voltage for detected audio. Do the same at 14.35 MHz, while adjusting the high-end trimpot on the power supply. Repeat as necessary for full-band coverage.

In part two of this article, a simple voltage-divider circuit is discussed, which will allow you to extend the tuning resolution of the HFO. At this point you should be familiar enough with the receiver operation to incorporate any special features desired. In part two, I will present the companion digital display circuit, and offer some useful suggestions.

### references

1. M. A. Chapman, K6SDX, "Solid State S-Meters," *ham radio*, March, 1975, page 20.
2. Donald L. Stoner, W6TNS, "High Stability Crystal Oscillator," *ham radio*, October, 1974, page 36.
3. M. A. Chapman, K6SDX, "Varactor-Controlled Variable-Frequency Oscillator," *ham radio*, November, 1975, page 50.
4. M. A. Chapman, K6SDX, "i-f and Detector Module," *ham radio*, August, 1976, page 34.
5. M. A. Chapman, K6SDX, "Multiband High Frequency Converter," *ham radio*, October, 1976, page 32.
6. M. A. Chapman, K6SDX, "Audio Filters for SSB and CW Reception," *ham radio*, November, 1976, page 18.
7. "Small Signal RF Design with Dual-Gate Mosfets," *Application Note AN-478A*, Motorola Semiconductor Products, Inc., Phoenix, Arizona.

ham radio


# HELP AGAIN



**RF Power Meter** - identical to HP Model 430C - Read article April '77 HR Mag., Pg. 44 for use. Copies of article available on written request. Our special purchase is your gain at \$34.95 ea. Note: This is Gen'l Microwave, 451. Bolometer/thermistor mount available with purchase. \$15 to \$35 depending on type.
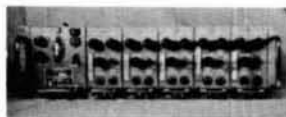
### Audio Compressor AN/GSA-33

Five identical plug-in compressor amps with power supply in 19 inch rack, all solid state, 600 $\Omega$  in & out, great for auto patch and phone patch. Weighs less than 30 lbs. Built like a battleship. \$34.95



**SG16 Signal Generator**, 10-450 MHz, AM/FM Sweep, Pulse, phase lock for stability \$185.00

**HYBRIDS** - Two wire to four wire Telco with network build out capacitors, super for auto patch. \$5.95

### RECEIVERS



**ARR-41/R-648 Collins Airborne version of R-390**. Mechanical filters, Digital Tuning, 28 VDC. Easily converted to 115VAC, 190-500 kHz, 2-25 MHz. Modular construction. \$185.00 checked

**GPR-90RX** - 0.54 to 31.5 MHz, 110V, 60 Hz, info on request. \$375.00

**R-388/51J** - Collins 0.54 to 31 MHz \$375.00

**R-390A** - 0.54 to 31 MHz, overhauled complete \$595.00

**RACAL Model 6217A**, 980 kHz, 32 MHz, All Solid State, takes about 3 inches of rack space, digital tuning \$1600.00

**Stoddart UHF tunable preamps**, 375 MHz to 1 KMHz - It's really a converter, IF output 21.4 MHz. \$175.00

### SPECTRUM ANALYZERS

**SPA-4A** Singer 10 MHz to 44 GHz. \$475.00

**SA84-WA** Polarad 10 MHz to 63 GHz. \$475.00

**BIRD 1 KW Dummy Load**, 250w continuous, 1 KW intermittent - Small - contained inside test set (incl. meters, switches, etc.). Complete for \$29.95

**GPT-750 Transmitter** mfd. by the Technical Material Corp., 2 to 32 MHz, CW/USB/LSB/ISB, one KW to the antenna, 24 hrs. a day if you're so inclined - with documentation, fair condition, built like a battleship - unfortunately it also weighs like a battleship (822 lbs.) WOW! However, if you have the room, here's a rig that will run forever. \$375.00



**Standard T/T pad** mounted in a sturdy steel case incl. 2 volume pots & 1 push button labeled "Stereo" - Also has 2 phone jacks for headphones, microphone, etc. Will make a fine control head. \$24.95

**T/T Decoder Board** - This board was removed from a language lab remote control system. You draw the schematic (because there wasn't one with the board). \$34.95



**Line Filters** - 20 A or better at 115/230 VAC. Made by Filtron. \$8.95

**TRANSCIVER** - RF Commun. Inc. Model RF301, 2 to 15 MHz, 1 kHz steps, synthesized. \$975.00  
Write for complete brochure.

**Computer Freakies Take Note!** Astrodata Universal Time Code Translator Model 6220 plus Astrodata tape search and control model 6225 and a relay program control Model 6530. All for \$225.00

**Telonic 2003 Sweep Generator System** - plug-ins to cover 0.1 to 300 MHz - Physically excellent - Needs work - with documentation. \$175.00

**Wanted:** Cables, Accessories, Test Set, etc. for RT400/ARC65, Especially Radio Set Control, C-451A/ARC-21.

**DISC-CAP**, 19075 BRAEMORE RD.

NORTHRIDGE, CA. 91326

213-360-3387

Cal. Residents - add State Sales Tax. Unfortunately, Disc-Cap can only service U. S. customers.

# KENWOOD

...pacesetter in amateur radio

# TS-520S

AND DG-5 DIGITAL FREQUENCY DISPLAY



The TS-520S combines all of the fine, field-proven characteristics of the original TS-520 together with many of the ideas and suggestions for improvement from amateurs worldwide.

#### FULL COVERAGE TRANSCEIVER

The TS-520S provides full coverage on all amateur bands from 1.8 to 29.7 MHz. Kenwood gives you 160 meter capability, WWV on 15,000 MHz., and an auxiliary band position for maximum flexibility. And with the addition of the TV-506 transverter, your TS-520S can cover 160 meters to 6 meters on SSB and CW.

#### DIGITAL DISPLAY DG-5 (option)

The Kenwood DG-5 provides easy, accurate readout of your operating frequency while transmitting and receiving.

#### OUTSTANDING RECEIVER SENSITIVITY AND MINIMUM CROSS MODULATION

The TS-520S incorporates a 3SK35 dual gate MOSFET for outstanding cross modulation and spurious response characteristics. The 3SK35 has a low noise figure (3.5 dB typ.) and high gain (18 dB typ.) for excellent sensitivity.

#### NEW IMPROVED SPEECH PROCESSOR

An audio compression amplifier gives you extra punch in the pile

ups and when the going gets rough.

#### VERNIER TUNING FOR FINAL PLATE CONTROL

A vernier tuning mechanism allows easy and accurate adjustment of the plate control during tune-up.

#### FINAL AMPLIFIER

The TS-520S is completely solid state except for the driver (12B-Y7A) and the final tubes. Rather than substitute TV sweep tubes as final amplifier tubes in a state of the art amateur transceiver,

Kenwood has employed two husky S-2001A (equivalent to 6146B) tubes. These rugged, time-proven tubes are known for their long life and superb linearity.

#### HIGHLY EFFECTIVE NOISE BLANKER

An effective noise blanking circuit developed by Kenwood that virtually eliminates ignition noise is built into the TS-520S.

#### RF ATTENUATOR

The TS-520S has a built-in 20 dB attenuator that can be activated by a push button switch conveniently located on the front panel.

#### PROVISION FOR EXTERNAL RECEIVER

A special jack on the rear panel of the TS-520S provides receiver signals to an external receiver for increased station versatility. A switch on the rear panel determines the signal path... the receiver in the TS-820 or any external receiver.

#### VFO-520 — NEW REMOTE VFO

The VFO-520 remote VFO matches the styling of the TS-520S and provides maximum operating flexibility on the band selected on your TS-520S.

#### AC POWER SUPPLY

The TS-520S is completely self-contained with a rugged AC power supply built-in. The addition of the DS-1A DC-DC converter (optional) allows for mobile operation of the TS-520S.

#### EASY PHONE PATCH CONNECTION

The TS-520S has 2 convenient RCA phono jacks on the rear panel for PHONE PATCH IN and PHONE PATCH OUT.

#### CW-520 — CW FILTER (OPTION)

The CW-520-500 Hz filter can be easily installed and will provide improved operation on CW.

#### AMPLIFIED TYPE AGC CIRCUIT

The AGC circuit has 3 positions (OFF, FAST, SLOW) to enable the TS-520S to be operated in the optimum condition at all times whether operating CW or SSB.

The TS-520S retains all of the features of the original TS-520 that made it tops in its class: RIT control • 8-pole crystal filter • Built-in 25 KHz calibrator • Front panel carrier level control • Semi-break-in CW with sidetone • VOX/PTT/MOX • TUNE position for low power tune up • Built-in speaker • Built-in Cooling Fan • Provisions for 4 fixed frequency channels • Heater switch.

## TS-520 Specifications

Amateur Bands: 160-10 meters plus WWV (receive only)  
 Modes: USB, LSB, CW  
 Antenna Impedance: 50-75 Ohms  
 Frequency Stability: Within  $\pm 1$  kHz during one hour after one minute of warm-up; and within 100 Hz during any 30 minute period thereafter  
 Tubes & Semiconductors:  
 Tubes ..... 3 (S2001A x 2, 12BY7A)  
 Transistors ..... 52  
 FETs ..... 19  
 Diodes ..... 101  
 Power Requirements: 120/220 V AC, 50/60 Hz, 13.8 V DC (with optional DS-1A)  
 Power Consumption: Transmit: 280 Watts Receive: 26 Watts (with heater off)  
 Dimension: 333(13 1/4) W x 153 (6-0) H x 335(13 (13-3/16) D mm(inch)  
 Weight: 16.0 kg(35.2 lbs)

#### TRANSMITTER

RF Input Power: SSB: 200 Watts PEP CW: 160 Watts DC  
 Carrier Suppression: Better than -40 dB  
 Sideband Suppression: Better than -50 dB  
 Spurious Radiation: Better than -40 dB  
 Microphone Impedance: 50k Ohms  
 AF Response: 400 to 2,600 Hz

#### RECEIVER


Sensitivity: 0.25  $\mu$ V for 10 dB (S+N)/N  
 Selectivity: SSB: 2.4 kHz/-6 dB, 4.4 kHz/-60 dB  
 Selectivity: CW: 0.5 kHz/-6 dB, 1.5 kHz/-60 dB (with optional CW-520 filter)  
 Image Ratio: Better than 50 dB  
 IF Rejection: Better than 50 dB  
 AF Output Power: 1.0 Watt (8 Ohm load, with less than 10% distortion)

AF Output Impedance: 4 to 16 Ohms

#### DG-5
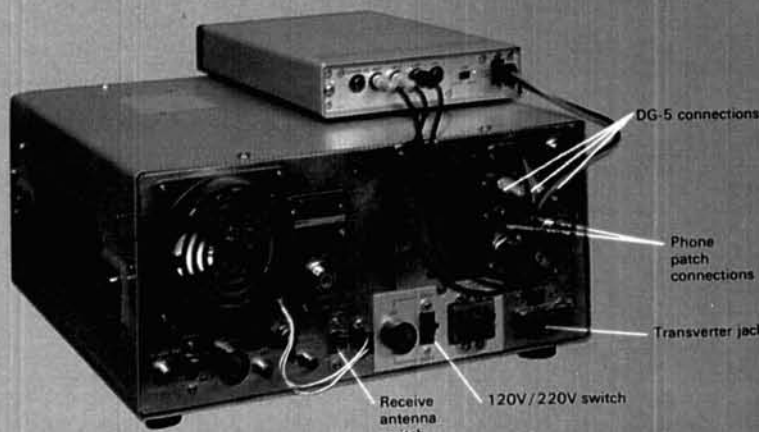
##### SPECIFICATIONS

Measuring Range: 100 Hz to 40 MHz  
 Input Impedance: 5 k Ohms  
 Gate Time: 0.1 Sec.  
 Input Sensitivity: 100 Hz to 40 MHz... 200 mV rms or over, 10 kHz to 10 MHz... 50 mV or over  
 Measuring Accuracy: Internal time base accuracy  $\pm 0.1$  count  
 Time Base: 10 MHz  
 Operating Temperature: -10° to 50° C/14° to 122° F  
 Power Requirement: Supplied from TS-520S or 12 to 16 VDC (nominal 13.8 VDC)  
 Dimensions: 167(6-9/16) W x 43(1-11/16) H x 268(10-9/16) D mm(inch)  
 Weight: 1.3 kg(2.9 lbs)



## DG-5

The luxury of digital readout is available on the TS-520S by connecting the DG-5 readout (option). More than just the average readout circuit, the counter mixes the carrier, VFO, and heterodyne frequencies to give you your exact frequency. This handsomely styled accessory can be set almost anywhere in your shack for easy to read operation... or set it on the dash board during mobile operation for safety and convenience. Six bold digit display your operating frequency while you transmit and receive. Complete with DH (display hold) switch for frequency memory and 2 position intensity selector. The DG-5 can also be used as a normal frequency counter up to 40 MHz at the touch of a switch. (Input cable provided.)  
 NOTE: TS-520 owners can use the DG-5 with a BK-520 adapter kit.



# KENWOOD

...pacesetter in amateur radio



# TS-820S

## WITH DIGITAL FREQUENCY DISPLAY

We told you that the TS-820 would be best. In little more than a year our promise has become a fact. Now, in response to hundreds of requests from amateurs, Kenwood offers the TS-820S\*... the same superb transceiver, but with the digital readout factory installed. As an owner of this beautiful rig, you will have at your fingertips the combination of controls and features that even under the toughest operating conditions make the TS-820S the Pacesetter that it is.

Following are a few of the TS-820S' many exciting features.

**PLL** • The TS-820S employs the latest phase lock loop circuitry. The single conversion receiver section performance offers superb protection against unwanted cross-modulation. And now PLL allows the frequency to remain the same when switching sidebands (USB, LSB, CW) and eliminates having to recalibrate each time.

**DIGITAL READOUT** • The digital counter display is employed as an integral part of the VFO readout system. Counter mixes the carrier VFO, and first heterodyne frequencies to give *exact* frequency. Figures the frequency down to 10 Hz and digital display

reads out to 100 Hz. Both receive and transmit frequencies are displayed in easy to read, Kenwood Blue digits.

**SPEECH PROCESSOR** • An RF circuit provides quick time constant compression using a true RF compressor as opposed to an AF clipper. Amount of compression is adjustable to the desired level by a convenient front panel control.

**IF SHIFT** • The IF SHIFT control varies the IF passband without changing the receive frequency. Enables the operator to eliminate unwanted signals by moving them out of the passband of the receiver. This feature alone makes the TS-820S a pacesetter.

\*The TS-820 and DG-1 are still available separately.

# TS-600




Experience the excitement of 6 meters. The TS-600 all mode transceiver lets you experience the fun of 6 meter band openings. This 10 watt, solid state rig covers 50.0-54.0 MHz. The VFO tunes the band in 1 MHz segments. It also

has provisions for fixed frequency operation on NETS or to listen for beacons. State of the art features such as an effective noise blanker and the RIT (Receiver Incremental Tuning) circuit make the TS-600 another Kenwood "Pacesetter".


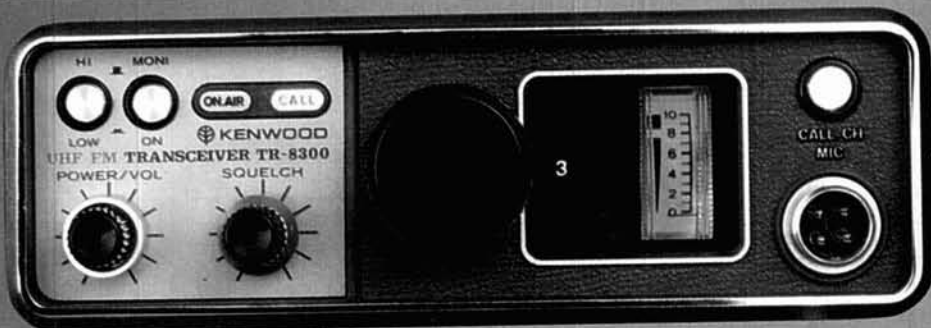
# TV-506

An easy way to get on the 6 meter band with your TS-520/520S, TS-820/820S and most other transceivers. Simply plug it in and you're on... full band coverage with 10 watts output on SSB and CW.



# TR-8300

Experience the luxury of 450 MHz at an economical price. The TR-8300 offers high quality and superb performance as a result of many years of improving VHF/UHF design techniques. The trans-

ceiver is capable of F<sub>3</sub> emission on 23 crystal-controlled channels (3 supplied). The transmitter output is 10 watts. The TR-8300 incorporates a 5 section helical resonator and a

two-pole crystal filter in the IF section of the receiver for improved intermodulation characteristics. Receiver sensitivity, spurious response, and temperature characteristics are excellent.

**KENWOOD**  
...pacesetter in amateur radio

# TS-700S

WITH DIGITAL FREQUENCY DISPLAY



Check out the new "built-ins":  
digital readout, receiver pre-amp,  
VOX, semi-break in, and CW sidetone!  
Of course, it's still all mode, 144-148  
MHz and VFO controlled.

Features: Digital readout with "Kenwood Blue" digits • High gain receiver pre-amp • 1 watt lower power switch • Built in VOX • Semi-break in on CW • CW sidetone • Operates all modes: SSB (upper & lower), FM, AM and CW • Completely solid state circuitry provides stable, long lasting, trouble-free operation • AC and DC capability (operate from your car, boat, or as a base station through its built-in power supply) • 4 MHz band coverage (144 to 148 MHz) • Automatically switches transmit frequency 600 KHz for repeater operation. Simply dial in your receive frequency and the radio does the rest... simplex, repeater, reverse • Or accomplish the same by plugging a single crystal into one of the 11 crystal positions for your favorite channel • Transmit/Receive capability on 44 channels with 11 crystals.




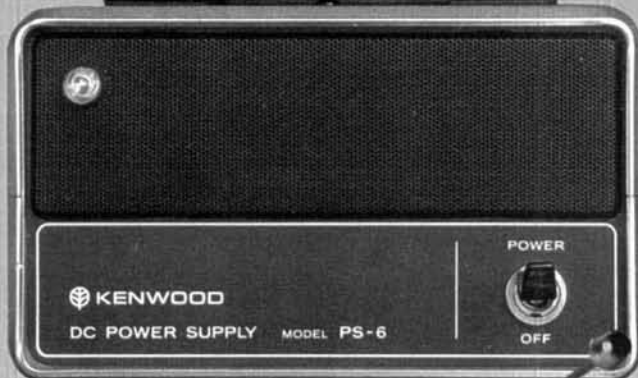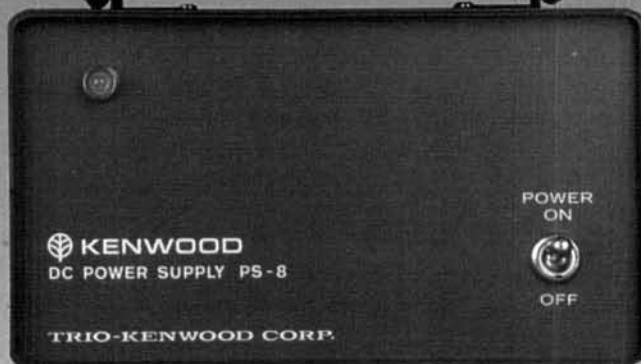
## VFO-700S

Handsomely styled and a perfect companion to the TS-700S. This unit provides you with the extra versatility and the luxury of having a second VFO in your shack. Great for split frequency operation and for tuning off frequency to check the band. The function switch

on the VFO-700S selects the VFO in use and the appropriate frequency is displayed on the digital readout in the TS-700S. In addition a momentary contact "frequency check" switch allows you to spot check the frequency of the VFO not in use.





# TR-7400A

Features Kenwood's unique Continuous Tone Coded Squelch system, 4 MHz band coverage, 25 watt output and fully synthesized 800 channel operation. This compact package gives you the kind of performance specifications you've always wanted in a 2-meter amateur rig.

Outstanding sensitivity, large-sized helical resonators with High Q to minimize undesirable out-of-band interference, and give a 2-pole 10.7 MHz monolithic crystal filter combine to give your TR-7400A outstanding receiver performance. Intermodulation characteristics (Better than 66dB), spurious (Better than -60dB), image rejection (Better than -70dB), and a versatile squelch system make the TR-7400A tops in its class.


Shown with the PS-8 power supply  
(Active filters and Tone Burst Modules optional)

# TR-7500

This 100 channel PLL synthesized 146-148 MHz transceiver comes with 88 pre-programmed channels for use on all standard repeater frequencies (as per ARRL Band Plan) and most simplex channels. For added flexibility, there are 6 diode-programmable switch positions. The 15 KHz shift function makes these 6 positions into 12 channels. 10 watt output,  $\pm 600$  KHz offset and LED digital frequency display are just a few of the many fine features of the TR-7500. The PS-6 is the handsomely styled, matching power supply for the TR-7500. Its 3.5 amp current capacity and built-in speaker make it the perfect companion for home use of the TR-7500.
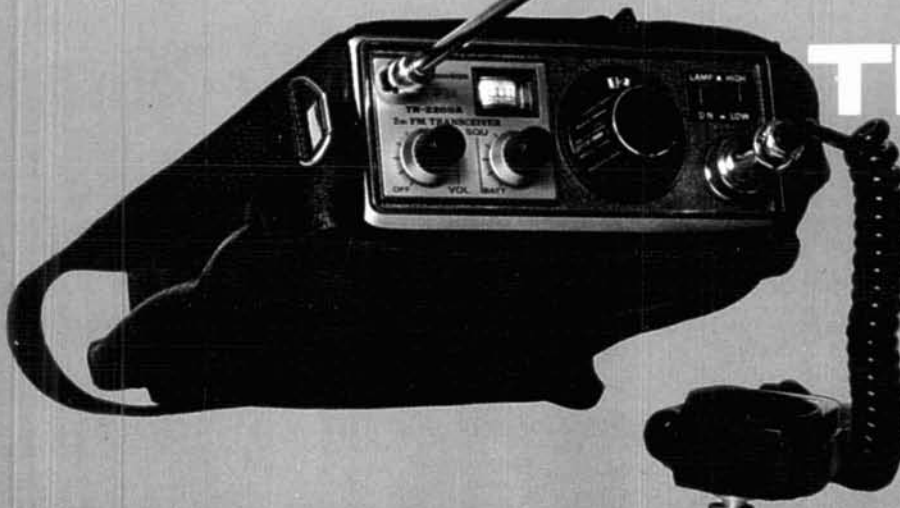
# TR-2200A

The high performance portable 2-meter FM transceiver. 146-148 MHz, 12 channels (6 supplied), 2 watts or 400 mW RF output. Everything you need is included: Ni-Cad battery pack, charger, carrying case and microphone.



# KENWOOD

...pacesetter in amateur radio

Kenwood developed the T-599D transmitter and R-599D receiver for the most discriminating amateur.

The R-599D is the most complete receiver ever offered. It is entirely solid-state, superbly reliable and compact. It covers the full amateur band, 10 through 160 meters, CW, LSB, USB, AM and FM.

The T-599D is solid-state with the exception of only three tubes, has built-in power supply and full metering. It operates CW, LSB, USB and AM and, of course, is a perfect match to the R-599D receiver.

If you have never considered the advantages of operating a receiver/transmitter combination... maybe you should. Because of the larger number of controls and dual VFOs the combination offers flexibility impossible to duplicate with a transceiver.

Compare the specs of the R-599D and the T-599D with any other brand. Remember, the R-599D is all solid state (and includes four filters). Your choice will obviously be the Kenwood.



## R-599D

## T-599D

# R-300

Dependable operation, superior specifications and excellent features make the R-300 an unexcelled value for the shortwave listener. It offers full band coverage with a frequency range of 170 KHz to 30.0 MHz • Receives AM, SSB and CW • Features large, easy to read drum dials with fast smooth dial action • Band spread is calibrated for the 10 foreign broadcast bands, easily tuned with the use of a built-in 500 KHz calibrator • Automatic noise limiter • 3-way power supply system (AC/Batteries/External DC) ... take it anyplace • Automatically switches to battery power in the event of AC power failure.





*Fine equipment that belongs in every well equipped station*

#### HF LINES

##### 820 Series

- TS-820S... TS-820 with Digital Installed
- TS-820... 10-160 M Deluxe Transceiver
- DG-1... Digital Frequency Display for TS-820
- VFO-820... Deluxe Remote VFO for TS-820/820S
- CW-820... 500 Hz CW Filter for TS-820/820S
- DS-1A... DC-DC Converter for 520/820 Series

##### 520 Series

- TS-520S... 160-10 M Transceiver
- DG-5... Digital Frequency Display for TS-520 Series
- VFO-520... Remote VFO for TS-520 and TS-520S
- SP-520... External Speaker for 520/820 Series
- CW-520... 500 Hz CW Filter for TS-520/520S
- DK-520... Digital Adaptor Kit for TS-520

##### 599D Series

- R-599D... 160-10 M Solid State Receiver
- T-599D... 80-10 M Matching Transmitter
- S-599... External Speaker for 599D Series

- CC-29A... 2 Meter Converter for R-599D
- CC-69... 6 Meter Converter for R-599D
- FM-599A... FM Filter for R-599D

#### SHORT WAVE LISTENING

- R-300 General Coverage SWL Receiver

#### VHF LINES

- TS-600... 6 M All Mode Transceiver
- TS-700S... 2 M All Mode Digital Transceiver
- VFO-700S... Remote VFO for TS-700S
- SP-70... Matching Speaker for TS-600/700 Series
- TR-2200A... 2 M Portable FM Transceiver
- TR-7400A... 2 M Synthesized Deluxe FM Transceiver

- TR-7500... 100 Channel Synthesized 2 M FM Transceiver
- TR-8300... 70 CM FM Transceiver (450 MHz)
- TV-506... 6 M Transverter for 520/820/599 Series

#### POPULAR STATION ACCESSORIES

- HS-4... Headphone Set
- MB-1A... Mounting Bracket for TR-2200A
- MC-50... Desk Microphone
- PS-5... Power Supply for TR-8300
- PS-6... Power Supply for TR-7500
- PS-8... Power Supply for TR-7400A
- VOX-3... VOX for TS-600/700A

Trio-Kenwood stocks a complete line of replacement parts, accessories, and manuals for all Kenwood models.

#### MORE ACCESSORIES:

Description	Model #	For use with
Rubber Helical Antenna	RA-1	TR-2200A
Telescoping Whip Antenna	T90-0082-05	TR-2200A
Ni-Cad Battery Pack (set)	PB-15	TR-2200A
4 Pin Mic. Connector	E07-0403-05	All Models
Active Filter Elements	See Service Manual	TR-7400A
Tone Burst Modules	See Service Manual	TS-700A; TR-7400A
AC Cables	Specify Model	All Models
DC Cables	Specify Model	All Models



The Kenwood HS-4 headphone set adds versatility to any Kenwood station. For extended periods of wear, the HS-4 is comfortably padded and is completely adjustable. The frequency response of the HS-4 is tailored specifically for amateur communication use. (300 to 3000 Hz, 8 ohms).



The MC-50 dynamic microphone has been designed expressly for amateur radio operation as a splendid addition to any Kenwood shack. Complete with PTT and LOCK switches, and a microphone plug for instant hook-up to any Kenwood rig. Easily converted to high or low impedance. (600 or 50k ohm).

TRIO-KENWOOD COMMUNICATIONS INC.  
1111 WEST WALNUT/COMPTON, CA 90220

**KENWOOD**  
...pioneer in amateur radio

# repeater kerchunk eliminator for mobile rigs

The ubiquitous  
555 timer IC  
surfaces again —  
this time in a circuit  
that eliminates  
repeater noise  
in your receiver

Many repeaters, especially those on common channels, appear to be susceptible to endless testing and *kerchunking* by some mobile operators, usually to see if they are either getting into the machine, or if there is a repeater on a particular channel. Most of the time this is harmless, but quite often I've become irritated by so much noise and shut off the rig, thus missing an important call later.

The circuit shown here will eliminate most of these repeater squelch tails from just about any receiver employing its own squelch, but will allow normal communications to pass through. This is accom-

plished by placing the circuit between the receiver squelch gate and the point where the squelch acts on the audio amplifier. When a signal is received, and the receiver squelch gate is tripped, the kerchunk eliminator counts approximately 3 seconds before turning on the audio amplifier. If the received signal is gone before the 3 seconds is up, the radio remains silent, and the circuit resets itself. In this manner, the typical kerchunk will not be heard.

On the other hand, if the received signal lasts for longer than 3 seconds, which usually occurs if the repeater is interrogated, the receiver begins operating normally, squelch and all. Normal operation continues until the rig is turned off, then on again, which resets the kerchunk eliminator to give another 3-second squelch delay in the manner described.

The receiver also begins operating normally, without the 3-second squelch delay, if the operator uses the transmitter in the rig. In this way, a call may be made, and a reply received, without losing part of the message.

## circuit description

This circuit (fig. 1) is designed to work with receivers using a low voltage level to squelch the audio amplifier. If the input and output are inverted using switching stages similar to Q1, the circuit will then work with receivers using a high voltage level to squelch.

The NE-555 timer is wired for use as a monostable multivibrator (one-shot), and is triggered through inverting transistor Q1 and capacitor C1 each time the receiver squelch is tripped, provided that the scr is in the *off* mode. The output of the NE-555 goes

By Robert K. Morrow, Jr., WB6GTM, 9792  
Oma Place, Garden Grove, California 92641




high for about 3 seconds, which is determined by the R1, C2 time constant, and is applied to Q2 base. Transistor Q2, which now acts as the squelch gate, also receives the output of inverting transistor Q1, and remains saturated as long as Q1 is cut off (no incoming received signal) and/or the output of the NE-555 is high (3-second timer delay is activated). When Q2 is in the *cutoff* state, the receiver audio amplifier is turned on, and incoming signals are heard. In addition, the scr is triggered, which eliminates the NE-555 from the circuit, so the squelch may now operate normally through Q1 and Q2. This same result is also accomplished whenever the transmit power bus is activated for any length of time. The entire system is reset when power is temporarily removed from the rig.



You may have noticed by now that the NE-555 is grounded through a diode. This is required because the forward voltage drop of the triggered scr is too high (about 0.7 volt) to reset the NE-555. By floating the ground of the NE-555 slightly above that of the scr cathode, this problem is eliminated.

## construction and installation

The printed circuit board diagram and parts placement are shown in **fig. 2**. Before beginning construction, make sure that your rig has a place to mount a circuit board of this size and shape. Parts placement is not critical, of course. Mount the PC board some-

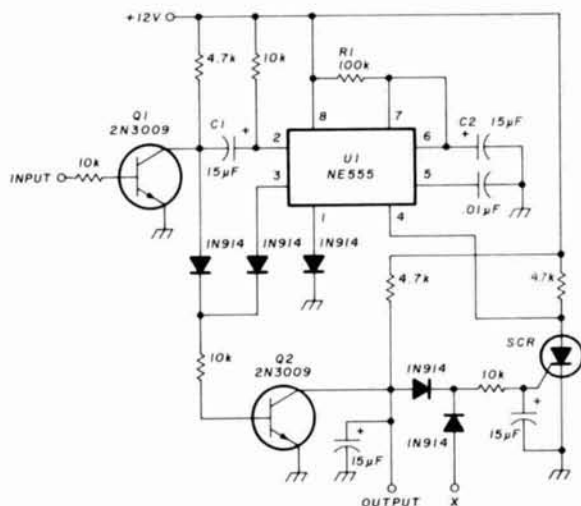

**fig. 1.** Schematic of the repeater kerchunk eliminator. If the printed circuit shown in **fig. 2** is used, resistors should be 1/4 watt, and the 15  $\mu$ F capacitors either tantalums or vertical-mount electrolytics. Although a Radio Shack part number is given for the SCR, just about any type that will fit on the PC board will work. Likewise, any npn silicon switching transistor will work for Q1 and Q2. The input is routed from the squelch gate in the receiver, and the output connects to the squelch control point on the receiver audio amplifier.

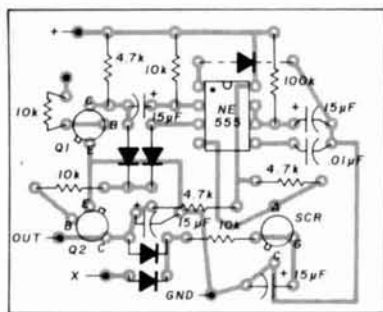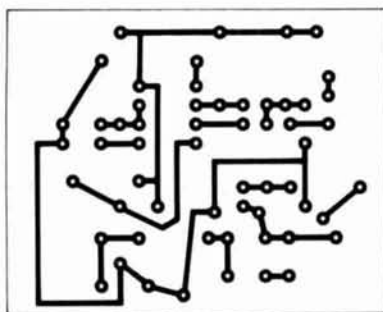

**fig. 2.** Full-size printed circuit board (foil side) and parts-layout diagrams. The diode which grounds the NE-555 is mounted on the foil side of the PC board.

where in the rig, and connect wires from  $V_{CC}$ , ground, and the transmit power bus from the TR switch to their appropriate places on the circuit board.

Now find the place where the squelch gate controls the audio amplifier in the rig, break the connection here, and run wires from these two points to the circuit board.

## testing

The system may be tested without an incoming signal by turning the squelch control fully counter-clockwise. The characteristic background noise should become audible after about 3 seconds have elapsed. Turn the rig off, then on again, to reset the system with the squelch control set to eliminate background noise. Transmit briefly, and turn off the squelch again. Background noise should be audible with no delay encountered.


## results

After installing this kerchunk eliminator, I find that my rig is used much more often than before. An added advantage was discovered the next time I took a long trip: Distant repeaters that drifted noisily in and out of squelch did not activate the kerchunk eliminator until I was close enough to get a reasonably good signal. The kerchunk eliminator should prove to be a valuable addition to any mobile rig.

ham radio


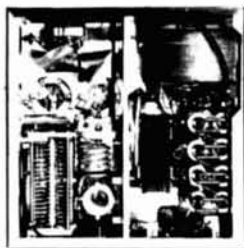
## COMPARE! NEW SIGMA XR3000D LINEAR AMPLIFIER



INTRODUCTORY PRICE **\$789**

2 DAY AIR SHIPMENT ANYWHERE IN U.S. \$35 ALASKA AND HAWAII SLIGHTLY HIGHER

- FULL BAND COVERAGE 160-10 METERS INCLUDING MARS.
- 2000 WATTS P.E.P. SSB INPUT. 1000 WATTS INPUT CONTINUOUS DUTY, CW, RTTY & SSTV.
- TWO EIMAC 3-500Z CONSERVATIVELY RATED FINALS
- ALL MAJOR HV AND OTHER CIRCUIT COMPONENTS MOUNTED ON SINGLE G-10 GLASS PLUG IN BOARD. HAVE A SERVICE PROBLEM? (VERY UNLIKELY) JUST UNPLUG BOARD AND SEND TO US.
- HEAVY DUTY COMMERCIAL GRADE QUALITY AND CONSTRUCTION SECOND TO NO OTHER UNIT AT ANY PRICE!
- WEIGHT: 90 lbs. SIZE: 9 1/2" (h) x 16" (w) x 15 1/4" (d).

### FEATURES

CUSTOM COMPUTER GRADE COMMERCIAL COMPONENTS, CAPACITORS, AND TUBE SOCKETS MANUFACTURED ESPECIALLY FOR HIGH POWER USE—HEAVY DUTY 10KW SILVER PLATED CERAMIC BAND SWITCHES • SILVER PLATED COPPER TUBING TANK COIL • HUGH 4" EASY TO READ METERS—MEASURE PLATE CURRENT, HIGH VOLTAGE, GRID CURRENT, AND RELATIVE RF OUTPUT • CONTINUOUS DUTY POWER SUPPLY BUILT IN • STATE OF THE ART ZENER DIODE STANDBY AND OPERATING BIAS PROVIDES REDUCED IDLING CURRENT AND GREATER OUTPUT EFFICIENCY • BUILT IN HUM FREE DC HEAVY DUTY ANTENNA CHANGE-OVER RELAYS • AC INPUT 110V OR 220V AC, 50-60Hz • TUNED INPUT CIRCUITS • ALC-REAR PANEL CONNECTIONS FOR ALC OUTPUT TO EXCITER AND FOR RELAY CONTROL • DOUBLE INTERNAL SHIELDING OF ALL RF ENCLOSURES • HEAVY DUTY CHASSIS AND CABINET CONSTRUCTION AND MUCH, MUCH MORE.



**SIGMA RF-2000 SWR & POWER METER**  
Introductory Price **\$29** Cal PWR Scales 200W-2000W  
Freq Range 3.5 - 150 MHz Please do not confuse the RF2000 with similar appearing lower priced units - RF2000 is an individually calibrated professional quality instrument - Unequaled at many times the price - Size 7" (w) x 2 1/2" (h) x 2 1/3" (d).



## NEW AM/FM ANALYZER SIGMA AF-250L

INTRODUCTORY PRICE **\$199**  
Deviation/Modulation Meter - FM: 0-20 KHz,  
AM: 0-100%. Size: 5 1/2" (h) x 10 1/4" (w) x 7 1/4" (d)  
Weight 7 lbs. Frequency: 1.8MHz-520MHz



ALSO MODEL AF-251LW WITH BUILT IN 125WATT CALIBRATED WATT METER & DUMMY LOAD. PRICE **\$289**. PLEASE WRITE FOR COMPLETE INFORMATION.

NEW—CDR HAM ROTATORS—Reg. **\$159.95** **\$125**

## STANDARD NEW 2 METER FM TRANSCEIVERS Model SRC 146A SPECIAL SALE

SRC 146A	\$314
4 Xtals. 34/94 and 94/94	NC
USA 2 Deluxe Base Charger	\$40
PT3644 Leather Case	\$10
AT 19 Rubber Ant and Whip	\$6
NI-Cads	\$30

Reg. \$400  
**Our Price \$289**

**NEW!!!** Touch Tone pad completely wired and ready to plug in—\$69.00



## NEW! FMSC-2 SCANNER FOR KDK FM-144

14 CHANNEL PROGRAMMABLE  
INTRODUCTORY PRICE \$109



## NEW! 7400 SCANNER

FOR KENWOOD TR-7400A  
14 CHANNEL PROGRAMMABLE  
INTRODUCTORY PRICE \$109



**FMSC-1 - \$169**



**7400 Scanner II - \$189**

## TWO NEW SCANNERS!

FMSC-1 Scanner for KDK FM 144 and 7400 Scanner II for Trio Kenwood TR 7400A.  
• Full scan 146 and 147 MHz consecutively or 1 MHz, or any MHz range • Scan rate: 1 MHz/2 seconds adjustable • Controls: Scan/Hold, Latch/Delay, 600 KHz offset (off, up, down), program 1 MHz • Simple installation.



### ACCESSORIES FOR KDK FM 144

FMPS 4R	Regulated AC/PS	\$49
FMTP 1	Touch Tone Pad	\$59
FMTP 2	Touch Tone Pad with 10 Number Programmable Memory	\$99
FMMC 1	Microphone with Built in Touch Tone Pad	\$59
FMTD 1	Private Call Decoder for use with and Programmed by Any Touch Tone Pad	\$129
SC 12A	Audible Tone Encoder Decoder	\$119
FMSC 1	Scanner - Random Any Range	\$169
FMSC 2	Scanner - Programmable 14 Channels	\$109
MARS CAP	Option Kit - Any Frequency	
	Any Split	\$12
FMDF-1	Offset Option Kit - 2 Extra Positions. Crystals Required	\$19
FMDF 2	±1 MHz Offset Option Kit (No Crystals to Buy)	\$19
FMTE 1	Sub Audible Tone (100 Hz - Adjustable 67.203 Hz)	\$29
FMAT 1	1/2 Wave Portable Antenna for Hotel Motel or Apartment	\$7.95
	Extra DC Cord & Plug	\$3.50
	ACC. Socket 5 Pin Din Plug	\$1.50
	Owners Manual (Extra)	\$5.00
	Service Manual	\$2.00
	Mounting Bracket (Extra)	\$6.00



## NEW — TEMPO 2020

A brilliant new SSB transceiver providing advanced engineering and unique operating features. Please write for information.



**YAESU FT 101E/FT 301D  
TRANSCEIVER'S**  
write for special deal.



## NEW! \$285 NYE VIKING MODEL MB-II 3,000 WATTS

Antenna Impedance Matching Network. Copper ribbon-wound, silver plated variable inductor. Heavy duty 7000 volt variable output capacitor. 10,000 volt fixed capacitors. Silver plated RF conductors. Large precision, easy-to-read dials. 360° readout. Overload protection for SWR meter.

## ATLAS 210X-215X and 350-XL

Please write for special bonus and package offers.



The indispensable **BIRD 43 THURLINE WATTMETER** Authorized Bird Distributor. Please write for special deal.

ATLAS, COLLINS, DEN-TRON, CUSHCRAFT, BIRD, STANDARD, KLM, HYGAIN, KENWOOD, TEMPO, MINI-PRODUCTS, MIDLAND, VHF MARINE, EIMAC, ICOM, AMCOMM, etc. Please write for quote.

# AMATEUR-WHOLESALE ELECTRONICS

8817 S.W. 129th Terrace, Miami, Florida 33176

COURTEOUS PERSONAL SERVICE—SAME DAY SHIPMENT • Prices subject to change without notice.

TELEPHONE: (305) 233-3631 • TELEX 51-5628 • STORE HOURS: 10-5 MON.- FRI.

OUR CREW: S.I. GREGORY WA4KGU J.R. MAGGIO Mgr. W8CXL  
Owner/Gen. Mgr.

S.E. GLICKMAN  
WB4HFJ



# NEW! FM144-10SXRII



All Solid State-PLL digital synthesized — No Crystals to buy! 5KHz steps — 144-149 MHz-LED digital readout PLUS MARS-CAP.\*

- 5MHz Band Coverage — 1000 Channels (instead of the usual 2MHz to 4MHz — 400 to 800 Channels)
- Priority Channel
- Audio Output 4 Watts • 15 Watts Output
- Unequaled Receiver Sensitivity and Selectivity — 15 POLE FILTER, MONOLITHIC CRYSTAL FILTER AND AUTOMATIC TUNED RECEIVER FRONT END — COMPARE!!
- Superb Engineering and Superior Commercial Avionics Grade Quality and Construction Second to None at ANY PRICE.

- **FREQUENCY RANGE:** Receive: 144.00 to 148.995 MHz, 5 KHz steps (1000 channels). Transmit 144.00 to 148.995 MHz, 5 KHz steps (1000 channels) + MARSCAP.\*
- **FULL DIGITAL READOUT:** Six easy to read LED digits provide direct frequency readout assuring accurate and simple selection of operating frequency.
- **AIRCRAFT TYPE FREQUENCY SELECTOR:** Large and small coaxially mounted knobs select 100KHz and 10KHz steps respectively. Switches click-stopped with a home position facilitate frequency changing without need to view LED'S while driving and provides the sightless amateur with full Braille dial as standard equipment.
- **FULL AUTOMATIC TUNING OF RECEIVER FRONT END:** DC output of PLL fed to varactor diodes in all front end R-F tuned circuits provides full sensitivity and optimum intermodulation rejection over the entire band. **No other amateur unit at any price** has this feature which is found in only the most sophisticated and expensive aircraft and commercial transceivers.
- **TRUE FM:** Not phase modulation — for superb emphasized hi-fi audio quality second to none.
- **FULLY REGULATED INTEGRAL POWER SUPPLIES:** Operating voltage for all circuits, i.e., 12v, 9v and 5v have independently regulated supplies. 12v regulator effective in keeping engine alternator noises out and protects final transistor from overload.

- **MONITOR LAMPS:** 2 LED'S on front panel indicate (1) incoming signal-channel busy, and (2) un-lock condition of phase locked loop.
- **DUPLEX FREQUENCY OFFSET:** 600KHz plus or minus, 5KHz steps. Plus simplex, any frequency.
- **MODULAR COMMERCIAL GRADE CONSTRUCTION:** 6 unitized modules eliminate stray coupling and facilitate ease of maintenance.
- **ACCESSORY SOCKET:** Fully wired for touch-tone, phone patch, and other accessories.
- **RECEIVE:** .25 uv sensitivity. 15 pole filter as well as monolithic crystal filter and automatic tuned LC circuits provide superior skirt selectivity.
- **AUDIO OUTPUT: 4 WATTS.** Built in speaker.
- **HIGH/LOW POWER OUTPUT:** 15 watts and 1 watt, switch selected. Low power may be adjusted anywhere between 1 watt and 15 watts, fully protected—short or open SWR.
- **PRIORITY CHANNEL:** Instant selection by front panel switch. Diode matrix may be owner re-programmed to any frequency (146.52 provided).
- **DUAL METER:** Provides "S" reading on receive and power out on transmit.
- **OTHER FEATURES:** Dynamic microphone, mobile mount, external speaker jack, and much, much more. Size: 2½ x 6½ x 7½. All cords, plugs, fuses, mobile mount, microphone hanger, etc., included. Weight 5 lbs.



## NEW! 6 METER FM50-10SXRII

Same specifications as above except transmit/receive: 51.00-53.995 MHz. 600 channels  
Introductory Price \$389.00



SUMMER SPECIAL  
FM144-10SXRII  
\$389.00  
VALUE \$599.00  
Regulated AC/PS  
Model FMPS-4R ... \$49.00

NEW!  
TONE  
ENCODER/  
DECODER  
SC 12A 12 CHANNELS ... DUAL TONE  
Introductory Price \$119.00

Touch-Tone  
Pad  
MODEL FMTP-1  
... \$59.00

Manufactured by one of the world's most distinguished Avionics manufacturers, Kyokuto Denshi Kaisha, Ltd.

First in the world with an all solid state 2 meter FM transceiver.

## AMATEUR-WHOLESALE ELECTRONICS

8817 S.W. 129th Terrace, Miami, Florida 33176  
Telephone (305) 233-3631 • Telex: 51-5628  
U.S. DISTRIBUTOR

PLEASE ORDER FROM YOUR LOCAL  
DEALER OR DIRECT IF UNAVAILABLE.  
DEALER INQUIRIES INVITED.

Regional Sales & Service Centers:  
Northeast: Buzzards Bay Electronics  
Buzzards Bay, Mass.  
East: Sanford Communications, Inc.  
Colonia, N.J.  
West: Consumer Communications, Inc.  
Seattle, Wash.



# low-cost all-mode-protected power supply

Here's a power supply  
that is ideal  
for vhf transceivers  
and other equipment  
using solid-state devices

It seems that vhf repeater activity is the only game in town nowadays. However, with the many transceivers in use, many of which were probably purchased for mobile work, many amateurs have opted to use the rig in the house powered by ac line voltage. Now comes the hitch: a *good* power supply at reasonable cost.

The power supply described here, which I call the "gutless wonder," surely answers this need. Take a

look at the schematic and you'll understand why I call it the gutless wonder: parts count is very low, but specifications are very high. Output is rock steady at  $13.7 \pm 0.7$  volts dc using line voltage between 98 and 128 Vac. Regulation is within tenths of a volt, from zero to 5 amperes. The design includes short-circuit, overcurrent, and overvoltage protection. Because of the small parts count, a PC board isn't needed. A couple of small 6-lug terminal strips do the job for mounting most components, and a 4-lug strip is used for ac-line wiring. Simple, but effective!

## regulator

The heart of the supply is one of the 3-terminal regulator ICs currently available. Not long ago, I spent many hours working out empirical formulas to determine a circuit that would most efficiently provide proper output voltage with protective circuitry. Invariably problems occurred with tolerances and temperatures, which made trimming controls mandatory. Today, all you have to do is choose a voltage and current and, lo and behold! You can buy a small piece of plastic containing three leads that will do the job — the overall size is about 1 inch by 0.4 inch (25 by 10mm) including leads.

Included in this little device are overcurrent and thermal-protection circuits as well as tight regulation characteristics. The family is known as the 7800 series IC, made by Motorola, Fairchild, Signetics, and others. Many variations are available based on fixed output voltage, maximum allowable current, and packaging. **Table 1** shows some of the devices

**By Budd Meyer, K2PMA, 6505 Yellowstone Boulevard, Forest Hills, New York 11375**

table 1. Rundown of some regulator ICs presently available for use in the power supply.

regulator type	package	Maximum load (amperes)	load current regulation (percent)	P <sub>D</sub> (free air) watts
78XXC	TO3	1.5	2	3.0
78XXC	TO220	1.5	2	2.0
78MXXC	TO39	0.5	2	1.0
78MXXC	TO220	0.5	2	1.0
78LXXC	TO92	0.1	2	0.7
78LXXC	TO39	0.1	2	0.8
77XXC	TO220	0.75	2	2.0
77XXC	TO39	0.75	2	1.0
209	TO3	1.0	2	3.5 (Fixed 5V output)
309	TO3	1.0	2	3.0 (Fixed 5V output)
723C	TO100	0.15	0.6	0.85
723C	TO116	0.15	0.6	1.0

standard output voltages: 5, 6, 8, 12, 15, 20, 24. The 7700 series has an additional 20 volts.

presently available. In most cases, the chip must be mounted on a heat sink. The basic circuit using such a chip is shown in fig. 1. What could be simpler?

### the power supply

I wanted a minimum of 5 amperes at 13.6 volts for my power supply. No regulator chip is available that will handle this requirement, therefore it was necessary to add an external pass transistor to handle the required current. Also, no chips were available that provide exactly 13.6 volts (the resolution of this problem is discussed later).

The type 109-series regulators, familiar to most amateurs, uses a series-pass npn transistor to increase current-carrying capability. The circuit described here uses a pnp type MJ2955, which is the complement of the ubiquitous 2N3055. Any pnp transistor with a minimum  $h_{fe}$  of 20 or more at 4 or 5 amperes, and a rated dissipation of more than 150 watts, will be adequate for Q2. The limiting factor will be temperature rise of the transistor when mounted in your heat sink.

The gutless wonder schematic is shown in fig. 2. No chips were available for the required voltage, so the regulator IC was put on a voltage pedestal, which is the secret of success in this supply. I used an 8-volt regulator chip arbitrarily; alternative values of resistance for R3, R4 are given should you wish to

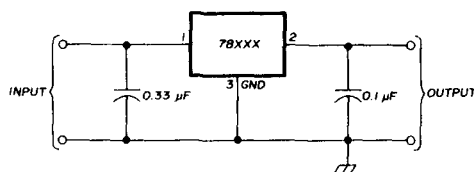


fig. 1. Basic circuit of the three-terminal voltage-regulator.

use a 12-volt regulator chip. Including all tolerances, the resulting output voltage was exactly as required.

The regulator chip specifications include a 5% tolerance. My output measured 7.8 volts, which is the average from the meter readings I used. If your supply output is off a couple millivolts, so be it.

### pedestal voltage

The pedestal voltage,  $E_p$ , is the voltage added to the rated chip voltage. It is approximately

$$E_p \approx I_p R4 + I_q R4$$

where

$$I_p \approx \left[ \frac{E_o}{R3 + R4} \right]$$

$$E_o \approx E_{chip} + E_p$$

$$I_q = \text{typical chip quiescent current (4.3 mA)}$$

Considering the interdependent parameters involved, it's best to use 40 mA for  $I_p$ . Operating the pedestal current at this value eliminated temperature and  $I_q$  variations prevalent among the various regulator chips.

### circuit protection

As mentioned above, the 7800-series regulators are overcurrent protected, but the external pass transistor is not, hence the reason for adding one more pnp transistor, Q1, a 2N6049. This transistor should have a current rating of 2 amperes because, when turned on, it must carry the "short-circuit" current of the regulator chip, which is about 250 mA. R2 turns on Q1 at a specified current. R2 consists of ten 1.2-ohm 1/2-watt resistors in parallel to provide 0.12 ohm. When the load current reaches 5.4 amperes, Q1 turns on and its collector removes drive to Q2, causing the output voltage to decrease to zero.

Another feature of building the supply overcurrent protection in this manner is that, by adding another 1-ohm resistor in parallel with R2, the current limit can be increased to 6 amperes. Adding two 1.5-ohm resistors instead will increase the limit to 6.25 amperes; adding two 1-ohm resistors to R2 increases the current limit to 6.7 amperes. If you must go above 8 amperes, however, change the regulator chip to a 7808.

### heat sink


Transistor Q1 is a 40-watt device in a TO66 case, with an  $h_{fe}$  of 20 at 1.5 ampere. Transistors Q1 and Q2 are mounted on a heat sink. The heat sink specified is ideal for this application, because the mounting holes are predrilled for both transistors. The bad news is that the heat sink isn't anodized; therefore both devices *must* be insulated from the heat sink. Be sure to use oxide-filled silicone grease (type DC 340) on *both* sides of the mica insulator. Use shoulder washers to insulate the transistor-

mounting screws. Remember that the transistor cases are above ground, so avoid contact with external objects that may cause them to short circuit to ground.
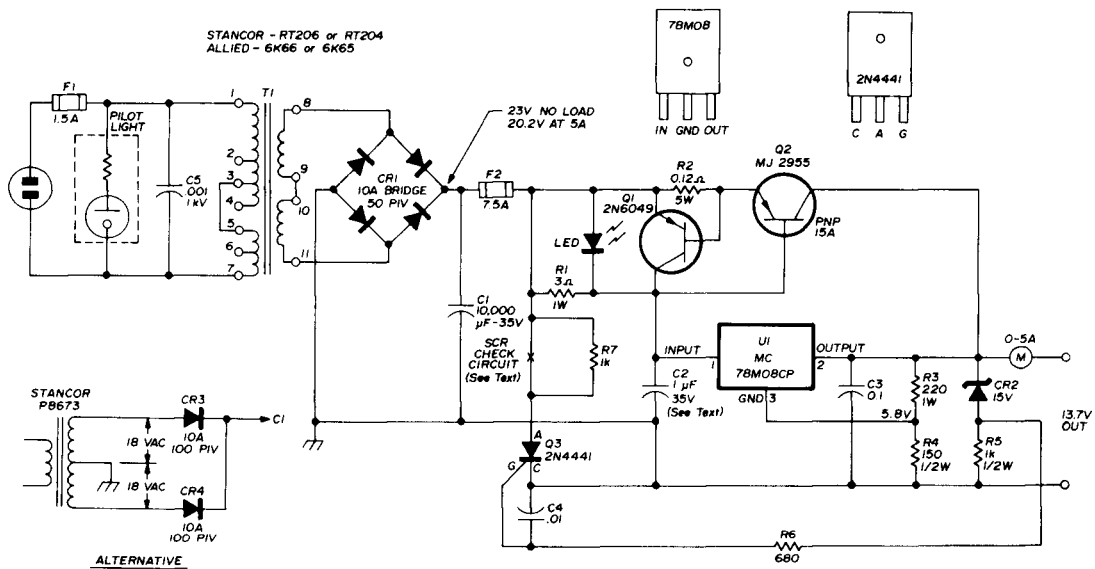
### operating mode

This power supply operates in the so-called constant-voltage, current-limited mode. Let's be sure we understand what these fancy words mean.

The current through the pass transistor is limited by the value of R2; however, when the load is a low value of resistance or dead short circuit, a path to ground through the transistor causes the current to continue to flow, although it is limited. A voltage across Q2 exists, depending on the transformer secondary voltage, the electrolytic capacitor value, the transformer secondary resistance, and the impedance of the diodes in the bridge. In my supply this voltage turned out to be 16 volts. Multiply this voltage by the current, which is 5.4 amperes, and you'll find that the transistor is dissipating close to 90



- |          |   |               |  |
|----------|---|---------------|--|
| C1       | 10k μF, 35V electrolytic                                      | R7            | 1k, 1/2 watt   |
| C2       | 1 μF, 35V tantalum  | T1            | multitap transformer. (For 6 amperes, Allied 6K66 or Stancor RT206; for 4 amperes, Allied 6K65 or Stancor RT204)   |
| C3       | 0.1 μF discap   | U1            | MC78M08CP (8V); 78M12 (12V)  |
| C4       | 0.01 μF discap  |               |  |
| C5       | 0.001 μF, 2kV discap  |               |  |
| CR1      | bridge rectifier, 10A at 50 PIV                               | <b>Notes:</b> |  |
| CR2      | 15V, 5% Zener   | 1.            | Q1, Q2 are mounted on Radio Shack part no. 276-1361 heat sink. Mounting hardware: Radio Shack 276-1370, 276-1371.  |
| CR3, CR4 | 10A, 100 PIV  | 2.            | U1, Q3 must be insulated from chassis.   |
| R1       | 3 ohms, 1 watt  | 3.            | Open jumper across R7 for checking crowbar circuit (see text).   |
| R2       | 0.12 ohm, 5 watt (ten 1.2-ohm 1/2 watt resistors in parallel) | 4.            | LED short-circuit indicator must be a gallium-arsenide phosphide (GAsP) device; Vf approximately 1.8 volts.  |
| R3       | 220 ohms, 1 watt (alternative for 12V chip, 300 ohms)         | 5.            | T1 can be 18 Vac at 4 amperes for full-wave bridge rectifier. For a full-wave center-tapped circuit use Stancor P8673 or equivalent (see alternative circuit). |
| R4       | 150 ohms, 1/2 watt (alternative for 12V chip, 39 ohms)        |               |  |
| R5       | 1k, 1/2 watt  |               |  |
| R6       | 680 ohms, 1/2 watt  |               |  |

fig. 2. Power-supply schematic. The voltage-pedestal method is used to obtain desired output voltage.



watts! You'd better believe that the transistor gets *damn hot*, so the addition of the LED overcurrent indicator (described below) becomes more meaningful. If you need a higher capacity, at the very least mount the power devices on a *larger* heat sink!

### transient response

C2, C3 improve chip transient response. I've also found that C2 is a must to prevent oscillation under certain conditions. C2 can be anything from 0.33  $\mu\text{F}$  and higher. Tantalum capacitors are recommended for their high-frequency bypass characteristics. If you can't find a tantalum capacitor, use a minimum of a 10- $\mu\text{F}$  electrolytic with a 0.01- $\mu\text{F}$  discap in parallel.

### overvoltage protection

A means of cutting off the power supply if an overvoltage condition occurs is the most important protective device I could add. Some transceivers have this protection built in — others don't. The thought of zapping a string of hard-to-find transistors in the transceiver for lack of a simple protective circuit is scary. The overvoltage-protection circuit shown is simple but effective — I know, because I tried it under dynamic operating conditions, and both primary and secondary fuses blew when 18 volts was applied to the meter end of zener CR2. The scr, Q3, is an 8-ampere rms device and I saw it do a job on the fuses! The scr turn-on time is 1 microsecond.

Capacitor C1 should be 10k  $\mu\text{F}$  at 35 volts. It can be made up of several caps in parallel if necessary. I've used capacitance as low as 3k  $\mu\text{F}$ , but the ripple voltage increased to a value higher than I cared to under high-current load conditions.

Transformer T1 was obtained from Allied Radio. A transformer with a secondary voltage of about 18 V at rated current is ideal but hard to come by. We must pay dearly for the multiple taps on the transformer, but I have the utmost confidence in the scrounging abilities of my fellow hams. Because of the intermittent nature of transmitter operation, a 3- or 4-ampere current rating should suffice for T1.

### construction

Photographs show the method of construction. Most of the wiring is no. 18 (1mm) wire to eliminate voltage drops. A separate terminal strip is used to mount the ten 1/2-watt resistors. As mentioned earlier, only two 6-lug terminal strips are required for mounting all the other components. A separate 4-lug strip is used for the 117-V wiring.

Both the regulator chip and the crowbar circuit scr are mounted on the bottom of the cabinet. Both must be insulated from the chassis using the mica washer supplied with the device. Use silicone grease

here also. The regulator chip will handle up to 500 mA; however, above 200 mA the MJ2955 handles the output current. The MJ2955 and 2N6049 are both mounted on, but isolated from the heat sink with the wiring between the two made at the heat sink. Only four wires are needed from the terminal strip on the back cover through a hole in the cover to the power transistors. If you'd like to add a luxurious touch to your supply, install a 25 Vdc volt-meter and a 5-10 amp ammeter.

### checkout

Testing is done before connecting the supply to your rig. Turn on the supply and check the output voltage. If it doesn't come out right, note the voltages indicated in fig. 2. With so few parts involved, problems are usually caused by defective transistors. If you have power resistors, hook them up and check regulation. The output voltage shouldn't drop until you draw somewhat higher than 5 amperes, depending on the value of R1.

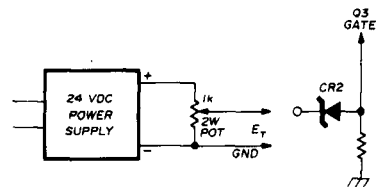


fig. 3. Test setup to determine exact trip point of the SCR crowbar circuit in fig. 2.

If you wish to check out the crowbar-circuit operation for the exact trip point, set up an external supply as shown in fig. 3. Disconnect CR2 from the output bus and remove the jumper from across R7. Connect a voltmeter between the scr anode and cathode. Turn on the supplies and rotate the arm of the pot toward the high-voltage end of the pot. Watch the voltage across the scr. When the test voltage fires the scr, the voltage across the scr will drop to about 1 volt. Measure the voltage between the pot arm and ground ( $E_T$ ); this is the trip voltage. Remember to reconnect the zener and reinstall the jumper across R7.

The LED overcurrent indicator is turned on by the voltage across R1. It serves as a warning that something is wrong. If it lights up, turn off the supply and check the equipment connected as a load. Be sure you are using a GAsP LED — not a GaP; the voltage drops across the two are different. Fairchild, Monsanto, Litronix, and Hewlett-Packard devices are GAsP; Opcoa LEDs are GaP.

So now you have it. An excellent piece of equipment that will perform flawlessly under all conditions without jeopardizing your expensive transceiver.

ham radio



# The DRAKE TR-33C



\$229.95

## Amateur VHF FM Transceiver

### DRAKE TR-33C SPECIFICATIONS

**GENERAL:** • **Frequency Coverage:** 146-148 MHz, 12 channels (2 supplied: 146.52 and 146.94). Crystal determines receive frequency. • **Transmit frequency offset** for repeater operation determined by 5-position switch: Simplex, +600 kHz, and -600 kHz supplied; any two additional offsets available with accessory crystals. • **Power requirements:** 13.0 volts dc  $\pm$  15% external supply OR internal battery supply. • **Current Drain (Batteries):** Squelched receive: 30 mA; transmit: 400 mA. External supply: above plus 45 mA for channel switch indicator lamp. • **Antenna:** 50 ohm external antenna through SO-239 connector OR screw-on telescoping whip antenna supplied, may be replaced with rubber helix antenna. • **Dimensions:** 5.5" x 2.8" x 8.5" (13.8 x 5.8 x 21.6 cm). • **Weight:** 4.4 lbs (2 kg).

**RECEIVER:** • **Sensitivity:** less than .5  $\mu$ V for 20 dB noise quieting. • **Selectivity:** +30 kHz adjacent channel rejection greater than 75 dB. • **Modulation acceptance:** at least  $\pm$  7 kHz. • **Intermodulation Rejection:** 70 dB referenced to sensitivity level. • **First IF:** 10.7 MHz with monolithic crystal filter. • **Second IF:** 455 kHz with ceramic filter. • **Audio Output:** nominal 1 watt at less than 10% distortion into 8 ohm built-in speaker or external speaker.

**TRANSMITTER:** • **Rf Output Power:** 1.5 watts minimum with 13.0 volts dc supply. • **Frequency Deviation:** Direct frequency modulation adjustable to at least  $\pm$  7 kHz deviation, factory set at  $\pm$  5 kHz. • **Separate microphone gain and deviation adjustments** • Drake 1525EM Push Button Encoding Mike can be used direct with no modification.

- **Hand Held Convenience, 12 Channel Capability**
- **SCPC (Single Crystal Per Channel) Frequency Control**
- **Lower Receiver Battery Drain**
- **Expanded Portable Antenna Choice**

• 12 Channels—only one crystal per channel provides simplex OR repeater operation on ANY channel, 2 channels supplied. 5 transmit offset positions, 3 supplied. • All FET front-end crystal filter for superb receiver intermod rejection. • Small convenient microphone included. • New lower power drain circuit on squelched receive. • Nicad rechargeable batteries supplied. • Built-in battery charger. • Ac and dc power cords supplied. • Telescoping screw-on antenna supplied, rubber helix optional. • Channel indicator light when using external dc supply. • Carry strap supplied. • Meter Indicates receive strength, xmit output, or battery voltage. • External speaker jack on rear panel. • Auxiliary jack on rear panel—may be used for tone-pad connections, etc. • Traditional R.L. Drake service backup.

### DRAKE TR-33C ACCESSORIES

#### Drake AA-10 Power Amplifier

10 dB power increase greatly adds to the transmitting distance covered by any 2-meter fm transceiver running up to 1.8 watts output

Small size: 2"H x 2.1"W x 5.5"D (51 x 52 x 140 mm)



#### Drake AC-10 Power Supply

Powers the AA-10, TR-22C, TR-33C and TR-72. Simultaneously can charge the TR-22C/33C nicads. Supplies 13.8 volts up to 3 amps from 120 V-ac 60Hz input. • **Accessory Crystals.** • **Model No. 1333 Drake MMK-33 Mobile Mount.**

- **Model AA-10 Power Amplifier** ..... \$49.95 ea.
- **Model AC-10 Power Supply** ..... 49.95 ea.
- **Accessory Crystals** ..... 6.30 ea.
- **Model MMK-33 Mobile Mount** ..... 12.95 ea.
- **Model 7079 Vinyl Carrying Case** ..... 9.95 ea.

#### Drake 1525EM Push Button Encoding Mike



- Microphone and auto-patch encoder in single convenient package with coil cord and connector. Fully wired and ready for use.
- High accuracy IC tone generator, no frequency adjustments.
- High reliability Digitran® keyboard.
- Power for tone encoder obtained from transceiver through microphone cable. No battery required. Low current drain.
- Low output impedance allows use with almost all transceivers.
- Four pin microphone plug: directly connects to Drake TR-33C without any modification in transceiver. Compatible with all previous Drake and other 2 meter units with minor modifications.

**Drake 1525EM, microphone with tone encoder — \$49.95**  
**Drake 7073DM without tone encoder — \$19.00**


To receive a FREE Drake Full Line Catalog, please send name and date of this publication to:

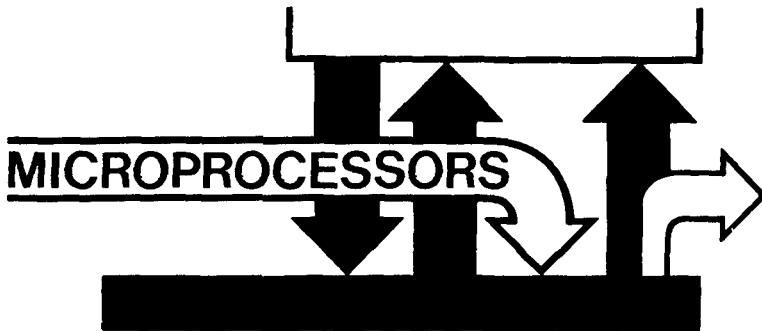**R. L. DRAKE COMPANY**



540 Richard St., Miamisburg, Ohio 45342  
Phone: (513) 866-2421 • Telex: 288-017

Western Sales and Service Center, 2020 Western Street, Las Vegas, Nevada 89102 • 702/382-9470



## data converters: the microprocessor and the amateur

In the future, the microprocessor will be faced with many new and unique amateur radio applications. Unfortunately, though, a large problem exists when trying to interface the digital world of the microprocessor to the analog world of amateur radio. Of the numerous articles written on the microprocessor, many assume interfacing a foregone conclusion, being contained within the microprocessor. Nothing could be further from the truth! This article will provide the necessary guidance to fill this void by demonstrating how data converters perform this valuable interface.

Two types of data converters will be discussed; one changes voltage to a digital code and the other performs the opposite function, transforming a digital code to an analog voltage or current. The former is an analog-to-digital converter (ADC), while the latter is a digital-to-analog (DAC). The digital code is in the format necessary for processing by the microprocessor. In effect, the two devices provide a means by which the microprocessor can acquire analog information, massage it, and deliver an output, in analog form, to an external source or terminal capable of controlling or displaying a function of the original analog input.

It may appear that a number of circuits or black

boxes other than a microprocessor can do this. Certainly, but remember, this type of circuit is a fixed design, its cost is high, and extremely costly if hardware changes are required to change functions. The microprocessor/data converter combination is superior due to its low initial cost (by comparison) and the flexibility of being able to handle a multitude of assignments with no change in hardware. The microprocessor/data converter system is used in industry to control such variables as temperature, flow, pH, viscosity, and weight of a liquified processed chemical. Furthermore, if the process formula is ever changed the hardware is left intact while the program is altered. It is this feature that makes the microprocessor/data converter system attractive.

Choosing the correct ADC or DAC is based to a great extent on the type of analog input and output to be associated with the respective data converters. There are many types of data converters that provide an assortment of functions, but those most applicable to amateur radio are the integrating and successive approximation ADC, and the voltage/current and multiplying DAC. A description of the functional peculiarities of each type is necessary to fully understand their application.

### digital-to-analog converter

Fig. 1 illustrates a simple  $n$ -bit binary DAC. The digital input is applied to the terminals labeled LSB to MSB. Each digital input drives a fet switch that connects the binary weighted summing resistors to the reference or to ground depending on the individual state of each of the digital inputs. Note that by virtue of the R-2R resistor configuration, binary weighting is achieved as the current flowing through each resistor is divided by a factor of two at each junction. With this scheme, the impedance as seen by the op

By Perry Pollins, WA1MOP, 14 Peachtree Road, Lexington, Massachusetts 02173

amp is constant and only two resistor values are required.

The output voltage ( $E_o$ ) is directly related to the number of switches which are connected to the reference by the 1 applied to the digital input. On the other hand, a zero applied to the digital input grounds the R-2R resistors, resulting in zero voltage at the output of the DAC. Thus, all 1s would give a maximum voltage at the  $E_o$  and all 0s, of course, is a binary code which produces an output voltage directly proportional to the digital code. This type of DAC delivers output voltage by virtue of the op amp inserted at the summing point and will, in most cases, fill the need of most amateurs. A current DAC does not contain an output op amp and delivers a current to its load.

The current DAC, due to its fast settling time and small glitches, is ideal when the interface is with a CRT display. The glitches are voltage spikes on the output that are caused by the switching transients. They are particularly large at the major transitions, i.e., going from all 1s to all 0s and vice versa. One method of reducing the spikes is to insert a lowpass filter before the display; another is to use a deglitcher after a current DAC. This is essentially a sample-and-hold type circuit, usually built from discrete components.

There may be times when it's necessary to multiply a digital word by a range of analog voltages to pro-

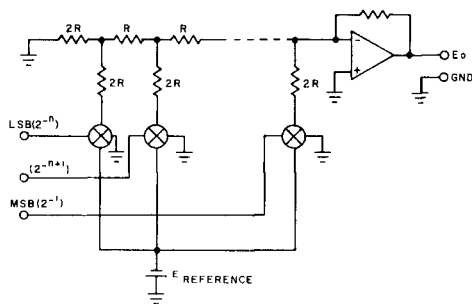


fig. 1. Schematic diagram of a basic digital-to-analog converter. The fet switches connect the 2R resistors to either ground or the reference voltage.

duce an output voltage or current representing their product. This is accomplished through the use of a multiplying DAC (MDAC) in which the internal reference is supplemented by an analog input. Of course, it's possible to use the MDAC as a conventional voltage or current DAC by applying an external reference voltage to the analog input terminals. This becomes particularly advantageous when more than one DAC is used in a system. A number of MDACs can share the same reference source, thus saving money on the cost of a conventional DAC and at the same time

making the stability characteristic of each MDAC identical to one another by virtue of the common reference voltage.

## analog-to-digital converter

The successive approximation ADC is shown in fig. 2 and functions as follows. First, the most significant bit (MSB) of the DAC is turned on by the control logic, and the output is compared to the ana-

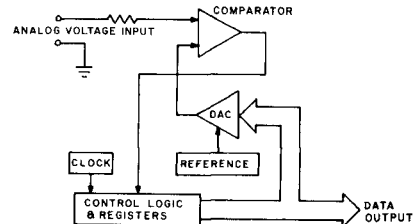


fig. 2. Block diagram of a successive approximation type analog-to-digital converter. The analog voltage is compared to an internally generated voltage. The control circuitry that operates the internal DAC also generates the final digital output.

log input voltage. If the comparator determines that the input is less than the DAC output, the bit (MSB) is turned off. If it is greater than the DAC output, it is left on.

The next MSB is then turned on and the same sequence of events repeated adding to the previous bits whether left on or turned off. This process is continued until a digital code (binary, 2's complement, offset binary, etc.) is formed, producing a voltage output from the DAC that in turn produces zero output from the comparator. In short, the output voltage from the DAC equals the analog input voltage to the ADC.

The state of the code present at the output registers is now a digital representation of the input analog voltage. Actually, this digital output does not cover each finite voltage applied to the input but a quantized incremental voltage step, the number of which is determined by the resolution of the ADC. An ADC with a resolution of 12 bits, for example, would have 4096 discrete quantized voltage levels or digital states. A 10-bit unit would have 1024, an 8-bit, 256.

The integrating ADC has a much slower conversion speed than the successive approximation type, but is a less complicated device and therefore, less expensive. It is used primarily with a slowly changing analog input as from a thermistor, thermocouple, or strain gauge input. An additional advantage of most integrating ADCs is their ability to convert in 16.67 microseconds, giving them exceedingly high common mode rejection to 60 Hz.

This type ADC, as shown in fig. 3, integrates the

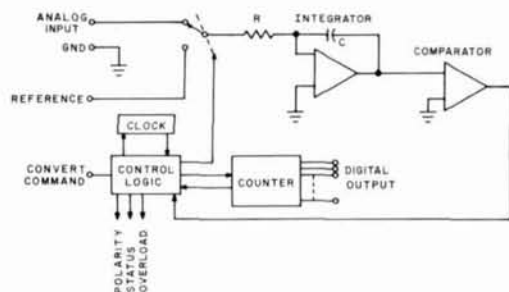



fig. 3. An integrator type ADC is used for slowly varying analog inputs.

analog input signal for a fixed period of time determined by a counter. The resulting integrated voltage is returned to zero by integrating a reference voltage of the opposite polarity. The resultant time of the integrator to return to zero as measured by the counter is proportional to the average value of the analog input over the integration period. Pulses from the counter are loaded into a register and deliver a specific output code to the microprocessor. ADCs of this type frequently have other options such as polarity indication, over-range output, ratiometric measurement capability, and auto zero. They are the basic ingredients of a digital panel meter and the digital voltmeter.
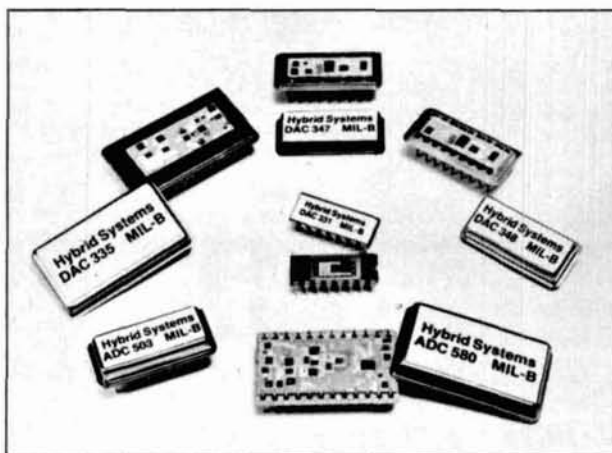
### choosing the right converter

Speed is a major consideration; this is known as settling time for DACs and conversion time for ADCs. In the former case, the time it takes a DAC to reach its rated output voltage/current after strobing is of prime concern when considering the response of the circuit it feeds.

The DAC, of course, does not respond coincidentally with its command to convert. It takes time for the fet switches to close and the op amp to reach its proper output magnitude. ADC conversion time is



selected as a function of how rapidly the input analog voltage varies. A general rule of thumb requires the conversion time to be at least twice that of the input frequency in order to digitally reproduce the input analog voltage.


If a thermal input representing rf power were applied to an ADC, for example, its slowly varying nature would dictate the use of an integrating ADC. On the other hand, digitizing voice frequencies would

table 1. Manufacturers of data converters.

Analog Devices, Inc. P.O. Box 280 Norwood, Massachusetts 02062 (617) 329-4700	Hybrid Systems Corp. Crosby Drive Bedford, Massachusetts 01730 (617) 275-1570
Analogic Corp. Audubon Road Wakefield, Massachusetts 01880 (617) 246-0300	ILC Data Devices Corp. Airport Int'l Plaza Bohemia, New York 11716 (516) 567-5600
Beckman Instruments, Inc. Helipot Division 2500 Harbor Blvd. Fullerton, California 92634 (714) 871-4848	Intech Function Modules 282 Brokaw Road Santa Clara, California 95050 (408) 244-0500
Burr Brown Int'l Airport Industrial Park P.O. Box 11400 Tucson, Arizona 85734 (602) 294-1431	Micronetworks Corp. 324 Clark Street Worcester, Massachusetts 01606 (617) 852-5400
Cycon, Inc. 1240 Elko Drive Sunnyvale, California 94086 (408) 734-1535	Motorola Semiconductor Products Box 20912 Phoenix, Arizona 85036 Contact Distributors
Datel Systems, Inc. 1020 Turnpike Street Canton, Massachusetts 02021 (617) 828-6395	National Semiconductor Corp. 2900 Semiconductor Drive Santa Clara, California 95051 Contact Distributors
Dynamic Measurements Corp. 6 Lowell Street Winchester, Massachusetts 01890 (617) 729-7870	Phoenix Data, Inc. 3384 West Osborn Road Phoenix, Arizona 85017 (602) 278-8528
Teledyne Philbrick Allied Drive Dedham, Massachusetts 02026 (617) 329-1600	Precision Monolithics, Inc. 1500 Space Park Drive Santa Clara, California 95050 (408) 246-9222
Teledyne Semiconductor 1300 Terra Bella Avenue Mt. View, California 94043 (415) 968-9241	Zeltex, Inc. 940 Detroit Avenue Concord, California 94518 (415) 686-6600

require the use of successive approximation type. Assuming the maximum voice frequency to be digitized is 5 kHz, a conversion time of no more than 100 microseconds would be required to produce an accurate digital representation of the input (a faster conversion speed would more precisely duplicate the input voltage).

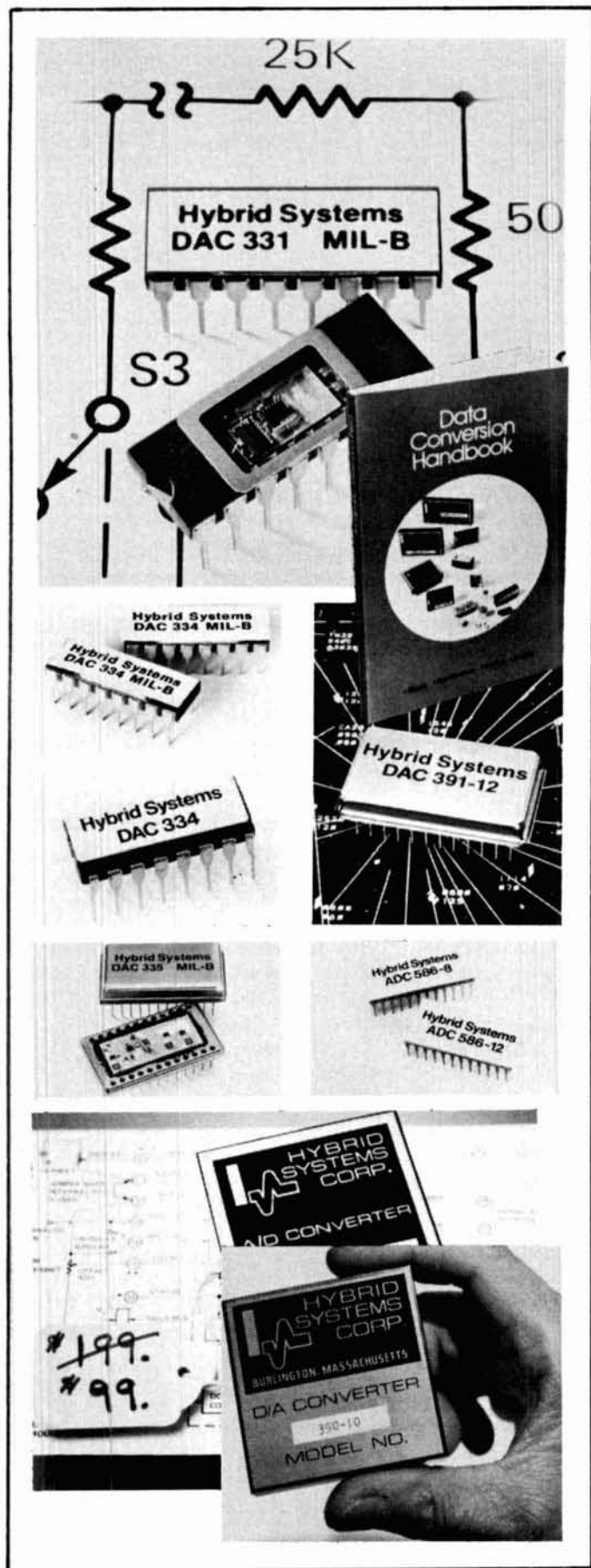When the rate of the signal being digitized also



varies at a rapid rate, it becomes necessary to retain the original signal for a period of time sufficient to perform the digital conversion. Simply feeding this signal to the ADC will not guarantee an accurate conversion. However, this can readily be achieved by inserting a sample-and-hold circuit between the analog input and the input to the ADC. The sample-and-hold will track the input signal, acquire it on command, and hold it while the ADC performs the conversion. At the completion of conversion the ADC generates a reset pulse and puts the sample-and-hold back into the sample or track mode. This sequence is repeated successively as determined by the nature of the measurement or control function desired.

Resolution, or the number of bits, of either the DAC or ADC determines the incremental accuracy and the linearity. In effect, it determines the number of increments the analog input or output has been divided into. A high resolution converter naturally yields a more accurate representation of its input over the complete range of its input than would a lower resolution device.

There are many specifications that are related to the converter's temperature environment. Close examination of each manufacturer's specification is necessary to understand a converter's parameters when subject to changes in temperature. Reference is made to the bibliography at the end of this article for those readers who wish more detailed knowledge on data converters. Many of the manufacturers listed in **table 1** have applications notes and technical papers available which discuss the various details of data converter products.

## interfacing

The ADC and the DAC in **fig. 4** represent memory locations for the microprocessor similar to those occupied by RAMs and ROMs that are normally associated with microprocessor/microcomputer systems. Access to the converters is gained by the assignment of an address code similar to those allotted to conventional peripherals such as displays, Teletype machines, and printers. This arrangement provides direct access to the converters without the necessity of using the microprocessor memory.

Although **fig. 4** does not show it, a *programmable* or *peripheral* interface element can be inserted between the ADC and the microprocessor. This IC handles addressing and decoding generation of instructions, interrupt, and bus access signals.

Controlling a DAC is a simple process and is accomplished by performing a store operation; that is, transferring data from the microprocessor to the latches or registers associated with the DAC. The DAC now only requires an instruction to deliver its output to its load. The ADC is accessed by fetching



data from its memory location or by having the programmable or peripheral interface element perform this function under instructions from the microprocessor. Of course, if the total system involves a multichannel arrangement of DACs or multiplexed ADCs, each individual channel must be separately addressed and fetched. Systems this complex depend entirely on the programmable and peripheral interface element to perform the addressing.

This has been an overview of how the amateur can utilize the microprocessor to automatically control his equipment or perform measurements in a

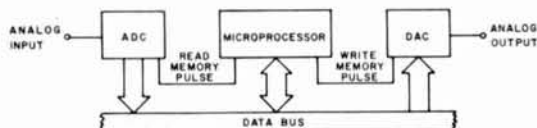


fig. 4. Block diagram of the interface between a microprocessor and data converters. Either data converter can be eliminated, depending upon the analog voltage requirements.

systematic fashion. It shows the necessity of the data converters as a means of connecting the microprocessor to a vco, a voltage-controlled attenuator, an rf power meter, or other device that performs equipment adjustments or measurements. It will hopefully provide many amateur radio enthusiasts with a tool that will provide many interesting hours of thought and experimentation.


### bibliography

1. Brown, C.H. and Fishbeck, J., "Application of Dual-Slope Integrating A-D Converters," *Computer Design*, November, 1972, page 126.
2. Bruck, Donald B., *Data Conversion Handbook*, Hybrid Systems Corporation, Bedford, Massachusetts.
3. Davis, Sidney, "Selection Criteria for A-D & D-A Converters," *Computer Design*, September, 1972, page 67.
4. DeFreitas, Richard E., "Which A/D Converter Best Fits Your Application," *Electronic Products Magazine*, February 18, 1974.
5. Eleccion, Marce, "A/D & D/A Converters," *IEEE Spectrum*, July, 1972, page 63.
6. Fullagar, David, et. al, "Interfacing Data Converters and Microprocessors," *Electronics*, December 9, 1976, page 81.
7. Gordon, Bernard M., "Spec the Right Converter for your Application," *The Electronic Engineer*, April, 1972.
8. Miller, William D., "Pick the Right DAC," *Electronic Design*, May 10, 1974.
9. Schmidt, Herman and Mrozowski, George, "Mating Microprocessors with Converters," *Electronic Design*, September 1, 1975, page 76.
10. Sheingold, Daniel H. and Ferrero, Richard A., "Understanding A/D & D/A Converters," *IEEE Spectrum*, September, 1972, page 47.
11. Sheingold, Daniel H. and Ferrero, Richard A., "Understanding Converter Circuitry," *IEEE Spectrum*, October, 1972, page 80.
12. Sheingold, Daniel H., *Analog-Digital Conversion Handbook*, Analog Devices, Inc., Norwood, Massachusetts.

ham radio
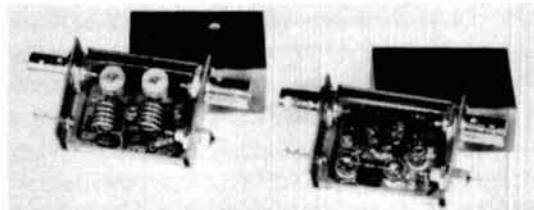
## PREAMPS from LUNAR

Originally developed by Chip Angle N6CA, the "Anglelinear" receiving preamplifiers meet the most demanding needs where low noise figure is important.



Model	Noise Figure	Gain	Bandwidth 3 dB	10 dB	List Price
28N	1.25	15	1.3	4	34.95
28W	1.25	10	2.6	7	34.95
50	1.5	12	2.5	5	34.95
144N	1.5	12	2.5	8	34.95
144W	1.5	11	5	15	34.95
222	2.0	11	6	18	34.95
432-2	1.6	15	150	400	39.95
E432-3	1.0 ± .1	11	180	325	125.00
450-2	1.7	15	150	400	39.95
490-2	1.7	15	150	400	44.95

BNC Connectors standard, except E432-3 SMA only. Others, specify RCA Phono, TNC, etc.

New "Anglelinear" line products coming soon: Preamps thru 2.5 GHz, converters & transverters systems filters 28 MHz thru 2.5 GHz.

Write for descriptive brochure on all Lunar Products.


Please add \$3.00 shipping/handling

California residents add 6%. Order today at your dealer or direct from:

**LUNAR electronics**

SUITE 10  
2785 KURTZ ST.  
SAN DIEGO, CA 92110  
714-299-9740  
Louis N. Anciaux WB6NMT

## K-ENTERPRISES

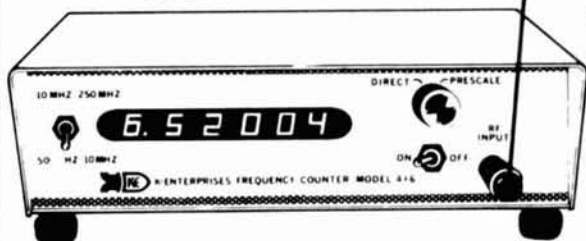

**MODEL 4X6C**  
50 HZ—250 MHZ ..... \$270.00

**300 and 500 MHZ PRESCALERS**  
**FREQUENCY STANDARDS**  
**MARKER and PEAKING GENERATORS**  
**POWER SUPPLIES AMPLIFIERS**

**WRITE FOR FREE CATALOG**



Phone:  
918-676-3752



**K-ENTERPRISES**

Box 410 (N.W. of town)

FAIRLAND, OK 74343

# This is easy- anyone can solder- WITH KESTER SOLDER

**KESTER  
SOLDER**



## Handymen! Hobbyists! DO-IT-YOURSELFERS!

Let Kester Solder aid you in your home repairs or hobbies. For that household item that needs repairing — a radio, TV, model train, jewelry, appliances, minor electrical repairs, plumbing, etc. — Save money — repair it yourself. Soldering with Kester is a simple, inexpensive way to permanently join two metals.

When you Solder go "First Class" — use Kester Solder.

For valuable soldering information send self-addressed stamped envelope to Kester for a FREE Copy of "Soldering Simplified".



**KESTER SOLDER**

Litton 4201 WRIGHTWOOD AVENUE/CHICAGO, ILLINOIS 60639

## VHF-FM RECEIVER Compact — High Performance LOW COST KIT

Model 144-5

Sensitivity under .15  $\mu$ V SINAD



Power saver circuit,  
case/speaker/control kit,  
other crystals available

• 5 channels, remote switchable, with 146.94 supplied • 6 pole crystal filter provides better than 75 dB adjacent channel rejection • Image rejection better than 75 dB; all other spurious better than 100 dB • Compact — 2.35 x 4" board, ideal for pocket receiver or can be built into existing equipment, home-brew transceiver • Operates from 7-12 VDC; 15 mA nominal drain, squelched

**\$49.95**  
INTRO  
PRICE

**Kp** Valley Instrument Products  
P.O. BOX 339 - BARTLETT, ILLINOIS 60103 (312) 741-8820

Also 220 MHz Model 220-5 at \$49.95

**Kp** Valley Instrument Products  
P.O. Box 339, Bartlett, IL 60103

BANK AMERICARD

Please ship \_\_\_\_\_ 144-5 receiver kits at \$49.95 each.

VISA

Please ship \_\_\_\_\_ 220-5 receiver kits at \$49.95 each.

Note: Illinois residents add 5% sales tax.

Name \_\_\_\_\_ Call \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Check or money order for \$ \_\_\_\_\_ enclosed

Charge my VISA/BankAmericard # \_\_\_\_\_

Card expires \_\_\_\_\_ Signature \_\_\_\_\_

## ALUMA TOWERS

60 Ft.  
Ham Crank-Up  
Model T-60-H

40 Ft.  
Crank-Up  
Ham Model T-140

HIGHEST QUALITY

MADE IN ALUMINUM

★ TELESCOPING  
(CRANK UP)

★ GUYED

★ TILT OVER MODELS

QUALITY MADE

*Excellent for*

**HAM  
COMMUNICATIONS**

MANY MODELS MFG.

Towers to 100 feet. Specials  
designed & made. See dealer  
or send for free catalog.

**ALUMA TOWER CO.**  
BOX 2806HR  
VERO BEACH, FLA. 32960  
PHONE (305) 567-3423



Radio  
Amateurs  
Reference  
Library  
of Maps  
and Atlas

**WORLD PREFIX MAP** — Full color, 40" x 28", shows prefixes on each country . . . DX zones, time zones, cities, cross referenced tables

\$1.25

**RADIO AMATEURS GREAT CIRCLE CHART OF THE WORLD** — from the center of the United States! Full color, 30" x 25", listing Great Circle bearings in degrees for six major U.S. cities; Boston, Washington, D.C., Miami, Seattle, San Francisco & Los Angeles.

\$1.25

**RADIO AMATEURS MAP OF NORTH AMERICA!** Full color, 30" x 25" — includes Central America and the Caribbean to the equator, showing call areas, zone boundaries, prefixes and time zones, FCC frequency chart, plus useful information on each of the 50 United States and other Countries

\$1.25

**WORLD ATLAS** — Only atlas compiled for radio amateurs. Packed with world-wide information — includes 11 maps, in 4 colors with zone boundaries and country prefixes on each map. Also includes a polar projection map of the world plus a map of the Antarctica — a complete set of maps of the world. 20 pages. Size 8 3/4" x 12"

\$2.50

Complete reference library of maps — set of 4 as listed above

\$3.75

See your favorite dealer or order direct.  
Mail orders please include \$1.25 per order  
for shipping and handling.

RADIO AMATEUR

**WRITE FOR  
FREE  
BROCHURE!**





**callbook** INC.

Dept. E 925 Sherwood Drive  
Lake Bluff, Ill. 60044



# ATB-34

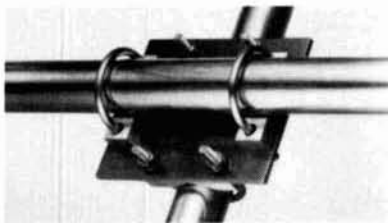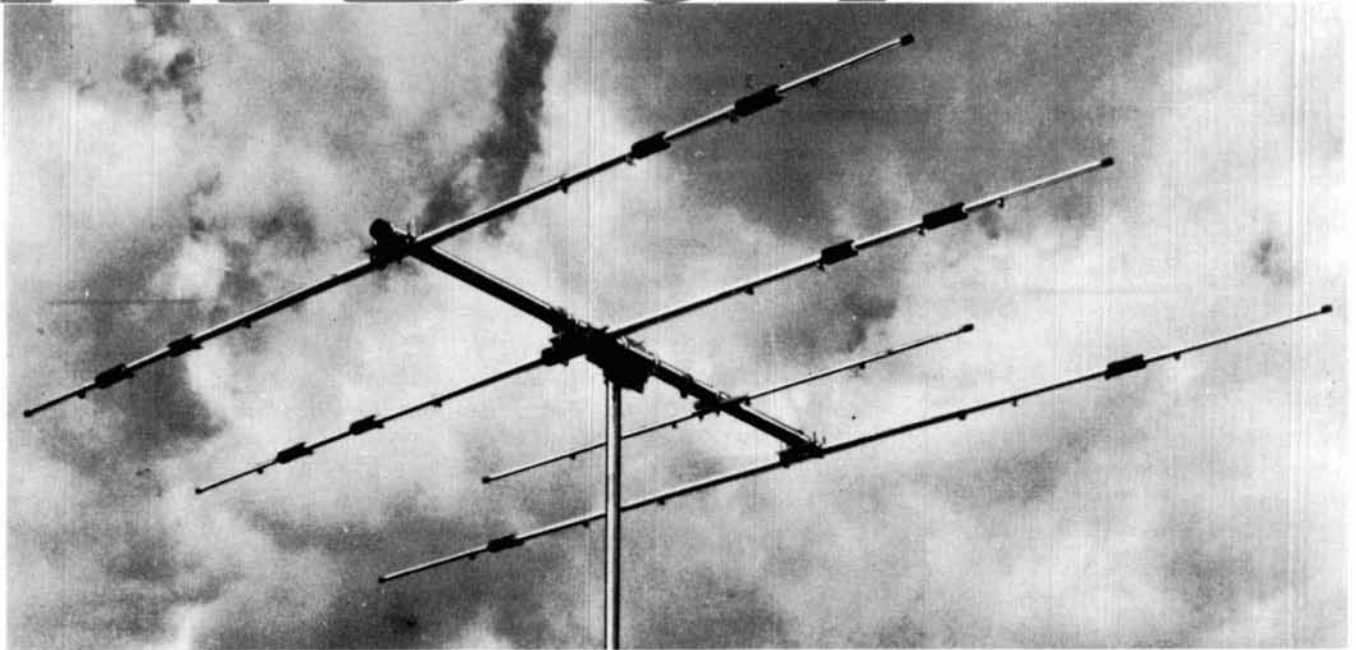

## 4 ELEMENT-3 BAND 10-15-20 METER BEAM

Cushcraft engineers have incorporated more than 30 years of design experience into the best 3 band HF beam available today. ATB-34 has superb performance with three active elements on each band, the convenience of easy assembly and modest dimensions. Value through heavy duty all aluminum construction and a price complete with 1-1 balun.

Enjoy a new world of DX communications with ATB-34!

### SPECIFICATIONS

FORWARD GAIN -	7.5 dBd	WIND SFC -	5.4 Sq.Ft.
F/B RATIO -	30 dB	WEIGHT -	42 Lbs.
VSWR -	1.5-1	WIND SURVIVAL -	90 MPH.
POWER HANDLING -	2000 WATTS PEP		
BOOM LENGTH/DIA. -	18' x 2 1/8"		
LONGEST ELEMENT -	32'8"		
TURNING RADIUS -	18'9"		

# \$239.95

COMPLETE

NO EXTRAS TO BUY

UPS SHIPPABLE


IN STOCK WITH DISTRIBUTORS WORLDWIDE



# cushcraft

CORPORATION

BOX 4680, MANCHESTER, N.H. 03108

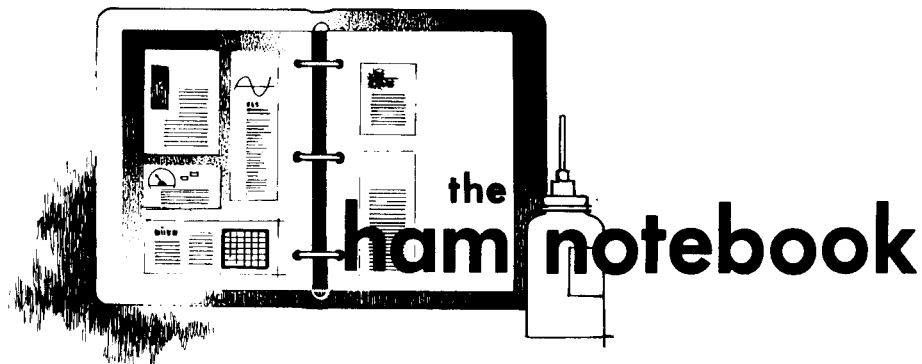

## increasing the capacity of the RAM RTTY message generator

I was very interested in K4EEU's 146-character message generator

(*ham radio*, January, 1975, page 8) and immediately built it. I am particularly impressed with its performance in conjunction with my ST-6. I recently changed the clock because the Motorola MC724P is now reserved for maintenance, and I used

the double monostable 74123 which is more readily available.

From time-to-time the number of available characters was not sufficient, so after I discovered INTEL's 2102 (1024-bit RAM), I decided to multiply the original capacity of 146 characters by four. Now I can store 585 seven-bit RTTY words. The cell array of the 2102 is organized is 32 rows and 32 columns; that is to say, it's necessary to have two five-bit counters instead of the two four-bit counters (7493) for correctly decoding the 1024 positions.

It is possible to add one bit to each of the four-bit counters with the state of the fifth bit changing each time output D of the 7493 falls from logic 1 to logic 0. A dual JK master-slave

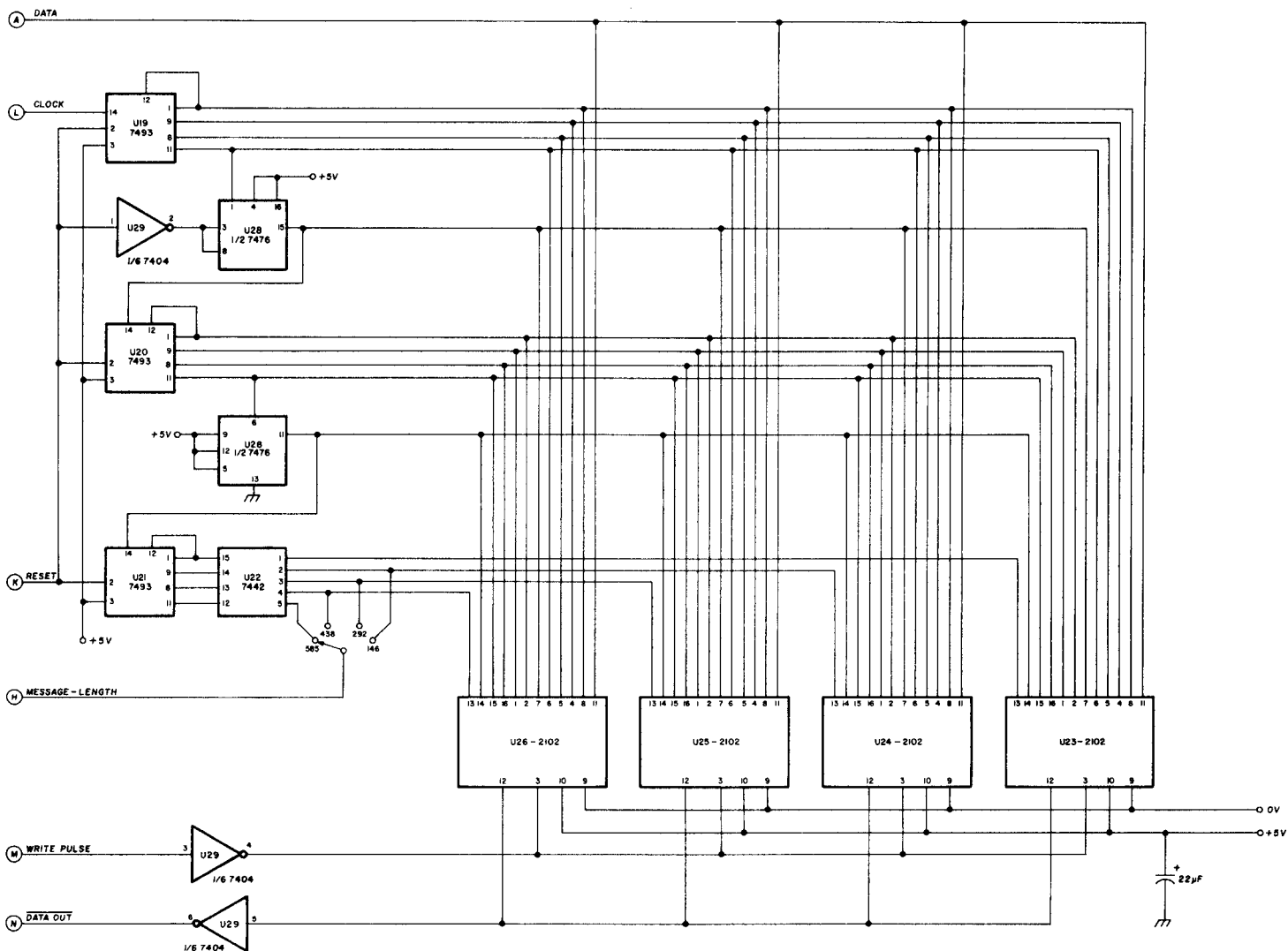


fig. 1. Schematic diagram of the improved RTTY message generator.

flip-flop (7476) does the job nicely by connecting one flip-flop to the D output of U19 and the other to the D output of U20.

To be sure that the Q output is set to zero when beginning a message, it is necessary to apply a zero to the clear input at the same time U19, U20 and U21 are reset. In these circuits the reset level is logic 1, so it is inverted by one-sixth of a 7404. With this arrangement, the 1024 positions of each 2102 memory can be decoded correctly, the chip-select circuit being the same.

In addition to the different pin configurations of the 1101 and 2102, two other points are changed. First, the read-write levels are inverted, so I used another part of the 7404 to correctly set the levels. Second, the 2102 offers only a DATA OUT and we must have a DATA OUT, so I inverted the output of the memories with an inverter (part of the 7404). Everything is now set to enter 585 RTTY characters and recall them at will.

The new integrated circuits were mounted on wire-wrap sockets installed in a 0.1 by 0.1 inch (2.5 by 2.5 mm) grid-drilled epoxy board. The connections between these circuits have been wrapped, the 1101s removed from their sockets, and the connections between the original circuit and the additional circuit are hard-wired with 10-inch (25cm) wires.

The first test was okay and the entire system worked well with the new, added circuit. It is possible to install the new circuit on spacers in the former box, but it would be better to design a printed-circuit board that could be connected directly to the 1101 sockets. In the latter case, only seven connections would have to be made with single-contact connectors.

Jean-Claude Piat, F2ES

## Heath SB-102 headphone operation

The phones jack on the SB-102 is fed from a high-impedance source

and should be used with headsets of high impedance. If low-impedance headphones are used, the *phone volume* control must be wide open to achieve a good balance between speaker and headsets. To provide a

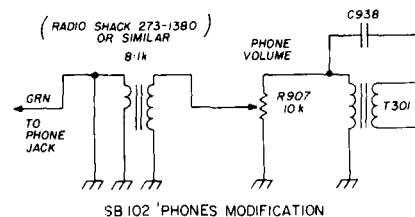


fig. 2. Shows addition of a small output transformer to the headphone circuit of a Heathkit SB-102 to permit use of low-impedance headphones.

better impedance match and control over the volume, a small imported output transformer was used as shown in fig. 2. Rather than add the circuitry externally, the transformer was mounted on the *bias* pot by soldering the frame to the pot body with the primary high-impedance winding facing the rear of the chassis and the *phone volume* pot. A two-terminal lug was attached to the chassis with one of the circuit-board mounting screws opposite the *bias* pot. The leads were transferred from the *phone volume* pot to the terminal strip, the secondary of the transformer wired to the terminal strip and the primary to the *phone volume* pot. Now, balance between speaker and headphones is more easily achieved and no distortion is noted.

Paul K. Pagel, K1KXA


## NCX-500 modification for 15 meters

If the NCX-500 transceiver is not carefully aligned, the fourth harmonic of its 5.2-MHz carrier oscillator, which appears at 20.8 MHz, creates a strong spurious signal in the receiver. A simple trap installed on the 15-meter mixer coil minimizes this spurious response.

The trap consists of a coil and parallel capacitor, prepared in the following manner.

Close wind 10-3/4 turns of no. 18

AWG (1.0mm) enameled wire on a 3/8-inch (9.5mm) diameter, 1-inch long (25mm) coil form. Place a 56 pF fixed capacitor in parallel with an 8-60 pF compression trimmer-type variable capacitor and place the parallel combination across the coil. Wrap approximately two turns of electrical tape around the top of L14 to obtain a tight fit and fit the trap to the top of L14 of the NCX-500. Adjust the coils so that the spacing between the two windings is about 5/8-inch (16mm).

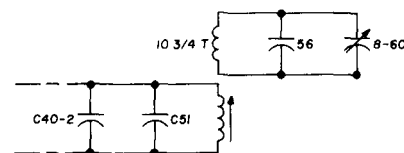

## adjustment instructions

1. Remove crystal Y3 (25.1 MHz) from the transmitter.
2. Tune the transmitter to the 20.8 MHz spurious frequency.
3. Adjust the variable capacitor on the trap for **minimum** transmitter output or plate current reading. (Use whichever gives the most sensitive indication).
4. Re-adjust the distance between the windings by moving the trap a little closer or further away from coil L14 and retune the trap as per **step 3**.
5. Replace the 25.1 MHz crystal, retune the transmitter to 21.1 MHz and re-adjust the slug in L14 for **maximum** transmitter power output. Note that the core in L14 should be sitting at the top end of the coil, farthest from the chassis.
6. Repeat **steps 1** thru **5**, because adjustment of either the trap or coil L14 will influence the other.

The trap will effect the performance of the NCX-500 receiver section at 21 MHz, hence coupling between L14 and the trap should be as loose as possible to minimize this effect. Finally, fix the trap to coil L14, using a little adhesive such as *Duco* cement.

Conrad J. Espinola WA1KY0

DICK  
K4RYR

**CENTRAL FLA.**

BOB  
W4YYS

**KLM • HY-GAIN • CUSHCRAFT  
MINI-PRODUCTS • SHURE  
ASTATIC • BEARCAT-210 • ROHN • CDE  
REGENCY • LARSEN • DENTRON**

**LAFAYETTE RADIO ELECTRONICS**

ASSOC.  
STORE

1811 HWY 17-92, MAITLAND, FL. 32751

305-831-2271



**ROTOR PROTECTION  
WITH AUTOBRÄK DELAY**



Have you had rotator damage? Removed the rotator? Been off the air? Waited for parts? No more! AUTOBRÄK is a complete conversion kit, including punched and finished cabinet for all HAM-M series 1 through 5 rotator control units.

AUTOBRÄK reduces the inherent problem of damaged rotator components due to instant brake engagement. AUTOBRÄK allows the antenna array to come to a coasting stop before brake engagement, thereby reducing stress on rotator components.

Other features include Zener regulated meter circuitry, adjustable brake delay, and handsome up-to-date styling compatible to most Ham gear. Cabinet measures 6" X 7 1/4" X 7 1/4"

Price \$39.95. Shipping and handling \$1.75 in U.S. Illinois residents add 5% sales tax.

**Kampp Electronics Inc.**  
Box 43, Wheaton, IL 60187  
312-665-3556



NEW LSI TECHNOLOGY

## FREQUENCY COUNTER

TAKE ADVANTAGE OF THIS NEW STATE-OF-THE-ART COUNTER FEATURING THE MANY BENEFITS OF CUSTOM LSI CIRCUITRY. THIS NEW TECHNOLOGY APPROACH TO INSTRUMENTATION YIELDS ENHANCED PERFORMANCE, SMALLER PHYSICAL SIZE, DRASTICALLY REDUCED POWER CONSUMPTION [PORTABLE BATTERY OPERATION IS NOW PRACTICAL], DEPENDABILITY, EASY ASSEMBLY AND REVOLUTIONARY LOWER PRICING!



1 3/4 LBS.  
COLOR:  
BLACK

SIZE:  
3" High  
6" Wide  
5 1/2" Deep

### FEATURES AND SPECIFICATIONS:

DISPLAY: 8 RED LED DIGITS .4" CHARACTER HEIGHT  
GATE TIMES: 1 SECOND AND 1/10 SECOND  
[AUTO DEC. PT. PLACEMENT]  
RESOLUTION: 1 HZ AT 1 SECOND, 10 HZ AT 1/10 SECOND.  
FREQUENCY RANGE: 10 HZ TO 60 MHZ. [65 MHZ TYPICAL].  
SENSITIVITY: 10 MV RMS TO 50 MHZ, 20 MV RMS TO 60 MHZ TYP.  
INPUT IMPEDANCE: 1 MEGOHM AND 20 PF.  
[DIODE PROTECTED INPUT FOR OVER VOLTAGE PROTECTION.]  
ACCURACY: ± 1 PPM [± .0001%]; AFTER CALIBRATION TYPICAL.  
STABILITY: WITHIN 1 PPM PER HOUR AFTER WARM UP [.001% XTAL]  
IC PACKAGE COUNT: 8 [ALL SOCKETED]  
INTERNAL POWER SUPPLY: 5.2 V DC AT 800 MA. REGULATED.  
INPUT POWER REQUIRED: 8-12 VDC OR 115 VAC AT 50/60 HZ.  
POWER CONSUMPTION: 4 WATTS  
INPUT CONNECTOR: BNC TYPE

ORDER BY PHONE OR MAIL  
COD ORDERS WELCOME

KIT #FC-50C ..... 60 MHZ COUNTER WITH CABINET & P.S. .... \$119.95

KIT #PSL-650 ..... 650 MHZ PRESCALER [NOT SHOWN] ..... 29.95

MODEL #FC-50WT ..... 60 MHZ COUNTER WIRED, TESTED & CAL. .... 165.95

MODEL #FC-50/600WT ..... 600 MHZ COUNTER WIRED, TESTED & CAL. .... 199.95

KIT #FC-50C IS COMPLETE WITH PREDRILLED CHASSIS ALL HARDWARE AND STEP-BY-STEP INSTRUCTIONS. WIRED & TESTED UNITS ARE CALIBRATED AND GUARANTEED. PRESCALERS WILL FIT INSIDE COUNTER CABINET.

TERMS: FOR SHIPPING, HANDLING & INSURANCE  
TO US & CANADA ADD 5% ALL OTHERS 10%.  
FLORIDA RES. ADD 4% SALES TAX. COD  
CHARGE \$1.00.



**OPTOELECTRONICS, INC.**

BOX 219 • HOLLYWOOD, FLA 33022 • (305) 921 2056

**TEXAS INSTRUMENTS  
INCORPORATED**

### Electronic Calculators



TI-30-SP	\$18.95
TI-1750	21.95
TI-5015	69.95
TI-5050M	84.95
TI-5040	99.95
TI-5100	44.95
Bus. Anal.	29.95
SR-40	25.95
SR-51-II	49.95
SR-57	65.95
SR-58	99.95
SR-59	229.95
PC-100A	149.95
Software	29.95



**Texas Instruments Microelectronic  
Digital Watches from \$9.95 (TI-503)**

**Hewlett-Packard Calculators  
10% discount from list.**

Add \$2 per unit for shipping. CA shipments add 6% sales tax. Send cashiers check or money order for immediate delivery (personal checks must clear). Most items shipped from stock within 48 hours.

**The Calculator Shop**

1160 Marsh Street  
San Luis Obispo, CA 93401  
(805) 544-1432



**TEN-TEC 544 DIGITAL.** Another ahead-of-its-time achievement from the pioneers in solid-state HF amateur radio technology. The 544 Digital joins its successful companion, Triton IV, to chart new paths in engineering.

**THE RECEIVER.** Deserving of all superlatives. Range: 3.5-30 MHz (plus "160" with option). MOSFET RF Amplifier with Resonate Control for a sensitivity of  $0.3 \mu\text{V}$  for 10 dB S+N/N. And overload minimized. Noise Blanker option: remarkably effective against impulse noise, functions in the IF, controls from the front panel. Hetrodyne crystal mixed VFO: steady as a rock. 8-pole 9 MHz Crystal-Lattice IF filter for a selectivity curve straight out of the text books: steep skirts, flat top, and narrow (2.5 kHz bandwidth, 1.8 shape factor at 6/60 dB points). Offset Tuning, with LED indicator, permits independent tuning of the receiver through a 10 kHz range (approx.). As one owner put it, "it makes SSB nets a breeze." And that beautiful Digital readout: six 0.43" LED digits, 5 in red and the least significant 6th in green, reading to 100 Hz with an accuracy of  $\pm 50$  Hz, settable to WWV. (Who needs a calibrator? And, indeed, it has none). WWV reception at 10 & 15 MHz. The sound? So beautifully clean and clear, it wins raves from all. Less than 2% distortion. Built-in speaker to clear the operating position. And External Speaker/Phone jack. CW Filter option, 2-position, 150 Hz width. Zero-Beat Switch for right-on CW. Whether you operate SSB or CW or both, you'll agree the 544 has a truly superior receiver section.

**THE TRANSMITTER.** 200 Watts Input - all bands, SSB or CW. Instant band change *without* tuneup! And no danger of off-resonance damage, even with the wrong antenna. 8-Pole SSB Filter. Automatic Sideband Selection, reversible. Push-Pull Output with the heat *outside* of the cabinet. 100% Duty Cycle so you can use it for RTTY and SSTV. Front panel ALC control with LED to show operation in the ALC region. Meter shows SWR when transmitting. VFO circuit is permeability tuned, has less than 15 Hz change per F° after 30 min. warmup, less than 10 Hz

change from 105-125 VAC with accessory power supply. SSB speech quality is completely natural, CW signals clean, articulate. And *full* CW break-in! So right you wonder why it wasn't done before - turns monologs into conversations. Sidetone is adjustable in pitch and volume. Automatic CW offset of 750 Hz. P-TT. Hi-Z mic. input. RF Output-Z 50-75 ohms, unbalanced.

**THE CONSTRUCTION.** Styled for today and tomorrow - etched aluminum front panel, black nomenclature, black top and sides. Ruggedized chassis stands up to the rough handling of mobile/portable use. Modular construction: 10 plug-in assemblies, 9 fixed circuit boards (65 transistors, 38 diodes, 14 ICs, 1 LSI, 6 LED displays). Snap-up front feet. Size:  $4\frac{1}{2} \times 13\text{-}5/8 \times 13$ . Net weight: 12 lbs.

**THE ACCESSORIES.** Model 242 Remote VFO for six-mode operation; 241 Crystal Oscillator for 6 spot freqs.; 240 Converter for 160 Meter operation at slightly reduced power level; 215P Microphone & Stand; 252G protected power supply; 262G power supply plus VOX plus 2 speakers; 207 Ammeter for supply monitoring; 249 Noise Blanker; 245 CW Filter; 212 Crystal for 29.0-29.5 MHz; 213 Crystal for 29.5-30.0 MHz. Plus various sized matching blank enclosures.

**TEN-TEC 544 DIGITAL.** So right, so advanced, it may well be the last rig you'll ever need to buy!

544 Digital - \$869

540 Non-digital - \$699

See the 544 and its companion 540 non-digital transceiver at your nearest TEN-TEC dealer, or write for full details.

**TEN-TEC, INC.**  
SEVIERVILLE, TENNESSEE 37862  
EXPORT 5715 LINCOLN AVE., CHICAGO, ILL. 60648

# ENCORE! ENCORE! TRITON GOES DIGITAL







## The French Atlantic Affair

In the midst of so much mistaken publicity about amateur radio, wherein problems caused by CB stations are blamed on the ham by an uninformed press, it is refreshing to see a book that has amateur radio woven into the plot as one of the "good guys." Moreover, the book is not one that would normally rate just a casual glance and then be placed back on the shelf.

The *French Atlantic Affair*, by Ernest Lehman, is a novel of such length that it will keep the average reader at it for several evenings, if he can force himself to put it down, or all night if he cannot. There is almost continuous action throughout the story, and the way author Lehman has brought amateur radio into focus early in the converging lives of the characters portrayed almost guarantees that it will play a significant part in the unfolding story.

Not that hams are all portrayed as knights in shining armor — their feet of clay are clearly evident so that the uninformed reader can see that they are ordinary human beings like everyone else. As such they have their hang-ups, problems, and families whose patience with this obsession wears thin at times. The attitudes and opinions about hams and their technical vices are all too familiar to many of us who have been the focal point of similar comments from friends and wives who are not

completely dedicated to the hobby of chasing DX or burning the midnight hours away conversing with a stranger in a far corner of the land.

To an experienced amateur, it would seem that the author knows about ham radio from the inside — the equipment is real, the procedures are correct, the language is right, and the bands go dead at the right time; there is even the right kind of nit-wit who clobbers the frequency in the middle of an important exchange. To balance the scale against the baddies, there is the good guy who provides a phone-patch across the continent to overcome the dead-band problem, and a very understanding ham on Long Island who cancels out of an important golf engagement to take part in the high drama.

The author *does* know about amateur radio — he is K6DXK, and has been as busy on the air as at the typewriter. The way he tells it, the time spent at the ham rig at times overshadowed the writing, so the book was somewhat of a combination of the two important factors in his life.

However, Lehman is definitely accustomed to writing top-grade material; he has written screen plays for several well-known films such as *West Side Story*, *The King and I*, and *Who's Afraid of Virginia Woolf*, and others. He has received six Writer's Guild awards and six Academy Award nominations.

*The French Atlantic Affair* was not written for hams alone — you don't pin your hopes of making a best seller

on a potential audience of a few hundred thousand. The book is written to appeal to people who would be spell-bound with such stories as *Hotel*, *Airport*, and *Where Eagles Dare*; it can be very favorable compared to these best sellers. The action is almost non-stop, and one segment builds suspense that is guaranteed to evoke interest in the next page or chapter — this reviewer suffered the consequences of lack of sleep all the next day because of the irresistible urge to see how things ended.

The book is recommended for adult reading, and, while it is unlikely that any of you hams who read it will become heroes of the level attained by the operators involved in this story, you will be comforted to know that you are not alone in being a member of a group whose hobby, ability, and dedication is misunderstood and underrated.

Amateur radio plays a vital part in *The French Atlantic Affair*, and the resulting publicity should be most beneficial to our hobby and image. If the story makes it into a hit movie (the screen rights have been purchased by MGM), that's all to the better.

*The French Atlantic Affair* has been selected by the Literary Guild and by the Playboy Book Club, and is being published by Atheneum Publishers; it is available from Ham Radio's Communications Bookstore, Greenville, New Hampshire 03048; \$10.95 postpaid. Not recommended for young readers.

## 80-Meter DX handbook

To a large number of amateurs, the 80- or 75-meter band is most useful as a rag-chewing spot. Daytime coverage is strictly local, and long paths open during the dark hours. Average contacts take place across distances that reach from one coast to the other during favorable conditions.

However, in the true amateur spirit, there is a core of DXers who are constantly probing to see what can be done on this "local" band to extend the communications range to the farthest parts of the globe.

John Devoldere, ON4UN, has compiled a handbook of things to do to squeeze the most out of this rag-chewer's haven; the *80-Meter DX Handbook*.

The handbook is a complete work on the art of DXing in this part of the HF spectrum, from why it happens (or does not happen), to what to build and how to use it. The book is arranged in four chapters: Propagation, Antennas, Stations, and Operating Practices. The propagation section covers magnetic disturbances, seasonal effects, twilight periods, paths, and more. As might be expected, the antenna section is the largest part of the book, with 15 distinct subjects — starting with the fundamentals and working through ZL-specials and Beverage antennas.

The section on stations contains a concise discussion of popular transmitters and receivers, and some hints as to their proper use. In Operating Practices, the author gives you information about what band segments are used in various countries, talks about procedures, types of operation, and points out some of the awards that have been won, and some that are much sought after.

The *80-Meter DX Handbook* ends up with a very good Bibliography for those who would like to explore some of the reference works in greater detail.

Published by Communications Technology, Inc., the *80-Meter DX*

## ...every tower in the world should be made this good.

Once in a while something really big comes along like Tri-Ex's all new W-80. So big we decided to call it the "Big W".

It's the big one of Tri-Ex's "W" Series towers.

Early on was the W-51. A superb performer and very popular still.

Last year came the W-67. Higher, bigger, stronger.

Now the W-80, Tri-Ex's "Big W" tower.

### Excellent Performance

Provides good DX capability at low costs. And if you're watching the sunspot cycle—it's now on an upswing for better than average transmission and reception.

"Big W" is a free-standing, crank-up tower that goes a full 80-feet up. You can lower it with relative ease under windy conditions using "Big W's" comfortably positive pull-down cable to protect your antenna load.

### Inherently Strong

As with all "W" Series towers, the W-80 is made of high strength steel tubing legs with solid rod "W" bracing. Stable? You bet!

Hot dipped galvanized after fabrication. Long lasting. Five sections. Included is a free rigid base mount. And the top plate is pre-drilled for a TB-2 thrust bearing.

Is Tri-Ex's "Big W" your kind of tower? Better believe it! Write today or see your nearest dealer. Ask about the W-80. It's real.

# NEW "BIG W"

  
**Tri-Ex**<sup>®</sup>  
TOWER CORPORATION

7182 Rasmussen Avenue, Visalia, California 93277



# How You Can Convert Your Rohn 25G Tower to a FOLD-OVER

**CHANGE, ADJUST OR JUST  
PLAIN WORK ON YOUR  
ANTENNA AND NEVER LEAVE  
THE GROUND.**

If you have a Rohn 25G Tower, you can convert it to a Fold-over by simply using a conversion kit. Or, buy an inexpensive standard Rohn 25G tower now and convert to a Fold-over later.

Rohn Fold-overs allow you to work completely on the ground when installing or servicing antennas or rotors. This eliminates the fear of climbing and working at heights. Use the tower that reduces the need to climb. When you need to "get at" your antenna . . . just turn the handle and there it is. Rohn Fold-overs offer unbeatable utility.



Yes! You can convert to a Fold-over. Check with your distributor for a kit now and keep your feet on the ground.

**AT ROHN YOU GET THE BEST**



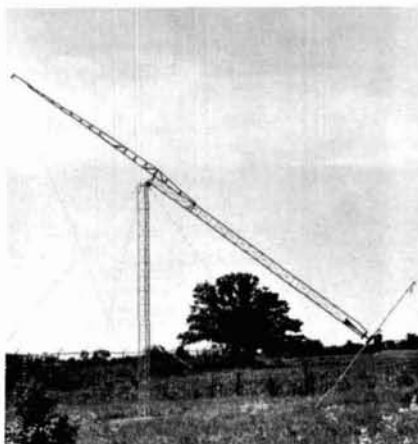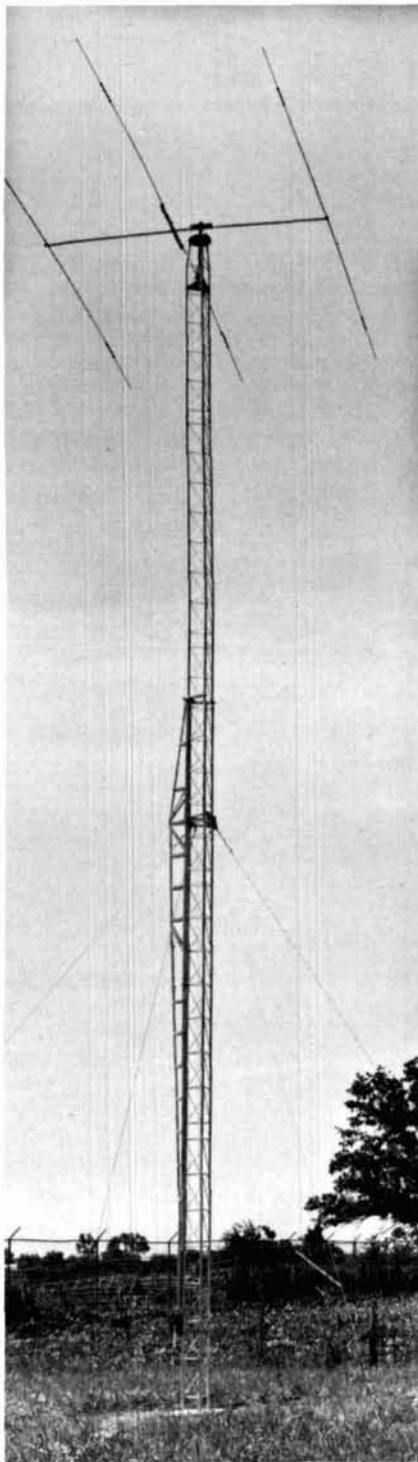**Unarco-Rohn**

Division of Unarco Industries, Inc.  
P.O. Box 2000, Peoria, Illinois 61601



*Handbook*, by ON4UN, is available from Ham Radio's Communications Bookstore, Greenville, New Hampshire 03048. Order HR-80M, \$4.50 postage paid.

## **active filter design**

This new book by Claude Lindquist is an invaluable reference for engineers, technicians, and amateurs who must understand signal processing and filtering, and who must specify, design, or adapt active filters to their own uses. The book features standard design curves and tables, practical design examples such as *Touch-Tone*, Dolby B, amplitude and delay equalizers, and presents numerous problems with solutions (which form an encyclopedia of active filter design). Also included are extensive references and unpublished research results (including delay analysis, high-frequency filters, tuned filters, discriminators, etc.).

Hardbound, 749 pages, \$21.95 postpaid from Steward & Sons, Post Office Box 15282, Long Beach, California 90815.

## **printed circuit board kit**

Excel Circuits Company has recently introduced a kit for making your own printed circuit boards. The kit contains materials that will allow you to produce your own boards, starting with the artwork and ending with a finished board. In contrast to other processes, this kit uses a photo-positive method, meaning that no image reversal and hence darkroom facilities are required.

Included in the materials are sufficient supplies to do the layout of small PC boards. The kit contains integrated circuit layouts, tape and pads, 10 x 10 graph paper, and a mylar-based paper to hold the layout. With no image reversal being necessary, the finished layout can be used to expose the board. One other advantage of using a photo-positive system is that dirt and dust on the

layout will not cause holes in the eventual circuit traces. Also, the neat plastic container can be used to hold the etchant while etching a board.

From start to finish, the Excel Circuits Company has provided materials that permit the fabrication of quality circuit boards. In addition, they've eliminated the problems of obtaining supplies from different sources. The price of the complete kit is \$19.95, postpaid. For more information write to Excel Circuits Company, 4412 Fernlee, Royal Oak, Michigan 48073.

### new wire-wrapping tool does all



The new WSU-30M "Hobby Wrap" tool performs the complete wire-wrapping function. First, the tool wraps 30 AWG (0.25mm) wire onto standard 0.025-inch (0.6mm) square DIP socket posts. Also, the tool unwraps and, finally strips 30 AWG (0.25mm) wire nick-free through a unique stripping blade.

Particularly important, the WSU-30M produces the "modified" style of wrap, in which approximately 1 1/2 turns of insulated wire are wrapped in addition to the bare wire for added mechanical stability.

Designed for the serious amateur, the WSU-30M features compact, all-metal construction for years of dependable service. At only \$6.95, this tool is a remarkable value, performing the work of three separate tools at a fraction of their comparable prices. It's available from your local electronics distributor or directly from O.K. Machine and Tool Corporation, 3455 Conner Street, Bronx, New York 10475.

# INTRODUCES THE VERSATILE NEW

# HR-312

- More Channels...at the flip of a switch**  
 Unlock the unique mode switch and 12 channels become 144
- More Sensitivity, Less Interference.**  
 .25  $\mu$ V Sensitivity plus 75 db adjacent channel selectivity and 70 db image rejection
- More Power Out**  
 35 watts nominal with a minimum of 30 watts across the band

... for a lot less

## \$269<sup>00</sup>

Amateur Net

© 1976 **Regency ELECTRONICS, INC.** 7707 Records Street  
 Indianapolis, Indiana 46226

## THE FM LEADER

2 METER

6 METER

220 MHz

440 MHz

# Attention: CW Operators using Drake!


**These crystal filters  
are for you!**

All filters contain specially-treated high-Q crystals.  
**600 Hz 6-Pole First-IF Filter for Drake R-4C**

Improve the early-stage selectivity. Eliminate those high-pitched beat notes from signals that leak around the switchable second-IF filter. Minimize the chance of strong signals overloading the second mixer, causing intermodulation and desensitization. Both the existing filter and our CF-600/6 can be mounted in the receiver and relay switched to retain phone capabilities. CF-600/6 \$75.00 Relay switch kit \$29.00

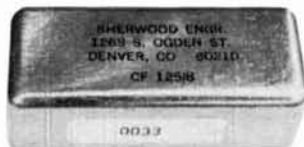**125 Hz 8-Pole Second-IF Filter for Drake R-4C**

Sharpest available! 300 Hz at -60db! Cuts QRM. Ideal for DX and contest work. Unexcelled under crowded band conditions. Does what no audio filter can do. More selective than audio filters. Puts selectivity in AGC loop. Unlike audio filters, receiver gain not reduced by QRM outside passband. Yet works well with an audio filter to improve receiver performance. Plugs directly into an accessory filter socket of the R-4C. CF-125/8 \$125.00



**Sherwood Engineering Inc.**

Dept. A  
1268 South Ogden St.  
Denver, Colo. 80210  
(303) 722-2257

Money back if not satisfied

Dealer Inquiries Welcome



## QUALITY KENWOOD TRANSCEIVERS ... from KLAUS RADIO

The TS-820 is the rig that is the talk of the Ham Bands. Too many built-in features to list here. What a rig and only \$830.00 ppd. in U.S.A. Many accessories are also available to increase your operating pleasure and station versatility.



**TS-820  
160-10M TRANSCEIVER**

Super 2-meter operating capability is yours with this ultimate design. Operates all modes: SSB (upper & lower), FM, AM and CW. 4 MHz coverage (144 to 148 MHz). The combination of this unit's many exciting features with the quality & reliability that is inherent in Kenwood equipment is yours for only \$599.00 ppd. in U.S.A.



**TS-700A  
2M TRANSCEIVER**

Guess which transceiver has made the Kenwood name near and dear to Amateur operators, probably more than any other piece of equipment? That's right, the TS-520. Reliability is the name of this rig in capital letters. 80 thru 10 meters with many, many built-in features for only \$629.00 ppd. in U.S.A.



**TS-520  
80-10M TRANSCEIVER**



**TR-7400A  
2M MOBILE TRANSCEIVER**

This brand new mobile transceiver (TR-7400A) with the astonishing price tag is causing quite a commotion. Two meters with 25W or 10W output (selectable), digital read-out, 144 through 148 MHz and 800 channels are some of the features that make this such a great buy at \$399.00 ppd. in U.S.A.

Send SASE NOW for detailed info on these systems as well as on many other fine lines. Or, better still, visit our store Monday thru Friday from 8:00 a.m. thru 5:00 p.m. The Amateurs at Klaus Radio are here to assist you in the selection of the optimum unit to fulfill your needs.

# KLAUS RADIO Inc.

8400 N. Pioneer Parkway, Peoria, IL 61614  
Jim Plack W9NWE — Phone 309-691-4840

## HAM RADIO HORIZONS



**well worth  
exploring**  
*the exciting  
path into  
the great  
ham radio  
adventure!*

That's Ham Radio HORIZONS; the monthly Amateur Radio magazine that presents this fascinating hobby in a straight forward language that enables a beginner to grasp the whole exciting story: Getting your license, putting a station on the air, communicating by OSCAR satellites, single sideband and much, much more.

**One Year — 12 issues  
Only \$10.00**

## HAM RADIO Greenville HORIZONS NH 03048

- Send me a sample copy, here's \$1.00 to cover postage and handling
- Sign me up for One year — enclosed is \$10.00 or charge it
- BankAmericard
- Mastercharge

Account No. \_\_\_\_\_

Exp. Date \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_



# 3 for the adventure of it!

**The adventure of 80 METER DXing**  
 by John Devoldere, ON4UN  
 Invaluable knowledge for any DXer, with a special section on Grey-line propagation. Discussion of antennas, basic to advanced.  
 Order HR-80M **\$4.50**

**Pure adventure: FRENCH ATLANTIC AFFAIR**  
 by Ernest Lehman, K6DXK  
 Intrigue and adventure on the high seas where Amateur Radio is the hero! Award-winning author — as reviewed in the August issue of QST. (recommended for mature readers)  
 Order A-FAA hardcover **\$10.95**

**The adventure of 160 to 190 kHz LOW & MEDIUM FREQUENCY RADIO SCRAPBOOK**  
 by Ken Cornell, W2IMB  
 Everything you want to know about the license-free 160-190 kHz band! See W1FB's review in the May issue of QST.  
 Order HR-LF **\$6.95**

**Ham Radio's Communications Bookstore**  
**GREENVILLE, NH 03048**

**Enclosed is check or MO for the following**

80 METER DXing     FRENCH ATLANTIC AFFAIR     LOW & MEDIUM FREQUENCY RADIO SCRAPBOOK

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE \_\_\_\_\_ ZIP \_\_\_\_\_

## New From Davis Electronics

**500 MHz FREQUENCY COUNTER**  
 10 Hz to 500 MHz  
 ± .0002% Accuracy  
 30 mv Sensitivity



- All Metal Cabinet
- 8 Digit 4" Display
- Oven Controlled Crystal (optional)
- Built in VHF-UHF Prescaler
- High Input Sensitivity
- Automatic Dp. Placement
- 12V D.C. Operation (optional)
- Selectable Gate Times 1 ms. & 1 sec.

**ORDER NOW**  
 Call Toll Free  
 1-800-828-7422  
 Immediate Shipping

**DAVIS** 500 MHz kit, CTR-2-500K with TCXO . . . . . \$249.95  
 500 MHz Factory Assembled CTR-2-500A . . . \$349.95

**DAVIS ELECTRONICS 636 Sheridan Dr., Tona., N.Y. 14150 716/874-5848**

# TEST REPORT



## ALPHA 374

**It's a no tune-up power house . . . and the fine print is on your side**

You could safely load your ALPHA 374 to a full KW, lay a brick on the key, and leave town for the weekend. It's built to take it. Every ALPHA linear amplifier, from the moderately priced ALPHA 76 rock-crusher to the most deluxe models, is engineered and built for continuous "brick on the key" service.

Contests, dxing, and lots of rag chews are just about as demanding as a brick on the key. Wouldn't it be great to own an ALPHA and know that the fine print clearly says "maximum legal power in all modes with no time limit?"

When you go ALPHA you forget about duty cycle limits. You forget about service hassles, too. The fine print in ETO's 18 month factory

warranty protects you six times as long as most guarantees!

Flip the bandswitch and instantly your ALPHA 374 is ready to deliver QRM — piercing maximum legal power — even on RTTY and SSTV — 10 thru 80 meters. The ultra convenient ALPHA 374 needs no tune-up in normal amateur service, and it's quickly set up for MARS or other special operation by simply switching to the auxiliary manual tune controls. Put your signal on top with ALPHA POWER. Contact your dealer, or Ray Heaton at ETO for literature on all ALPHA's. And ask for a copy of "Everything You Always Wanted to Know About (Comparing) Linears . . . But Didn't Know Whom to Ask."



Regardless of what transmitter you're using, for an even bigger signal the new ALPHA/VOMAX split band speech processor can boost your SSB



easy to install and use. need it most, for just \$179.50. Like the ALPHA linears, VOMAX is exceptionally low in distortion, compatible with all popular exciters, and

**ALPHA: Sure you can buy a cheaper linear . . . But is that really what you want?**

**ETO** Ehrhorn Technological Operations, Inc.

P.O. Box 708 Industrial Park · Canon City, Colorado 81212 · (303) 275-1613



## Apollo Products-Little Giant Trans Systems Tuner Kit — \$122.50

Designed and engineered after "Apollo" — "Little Giant" 2500X-2, for an "engineered performance" Trans Systems Tuner and Adaptations of the Lew McCoy Transmatch, with power handling at the KW plus level!



### Kit includes:

1 200 pfd wide-spaced variable with isolantite insulation rated 3,000 volts  
1 200 pfd dual section parallel condenser isolantite  
2 finger-grip pointer knobs 2" diam, white indented  
1 pvc insulated shaft couplings 1/4 to 3/4  
3 SO-239 coax chassis connectors. Tunes 52 ohm or 52-300-600\* or random wires

1 heavy inductance for 10-15-20-40-80 meters  
6 pvc stand-offs, 4 for condensers and 2 for inductance  
1 HD switch for band catching 10 thru 80 meter coverage  
1 pkg 12-gauge tinned round wire  
Cabinet included — Apollo "Shadow Boxes" M Kit includes schematic. Recommend parts layout.  
INFO NOTE \*377 OHM and \*\*600 OHM "Open wire spaced ladder line" air dielectric.  
\*53 x wire diam. \*\*84 x wire diam. info only — not supplied.

Apollo Products, Box 245, Vaughnsville, Ohio 45893 419-646-3495  
Subsidiary "Little Giant Antenna Labs"

## THE SQ-AUTO KEYS



- Iambic Sending
- Dot and Dash Memories
- Built-in Key
- Regulated AC Power Supply
- Sidetone with volume/tune control. Pitch internally adj.
- Available with Reed Relay or Transistor grid block output
- Heavy Alum. two-tone Cabinet.

Available at your dealer or order direct.  
SQ-Auto with Key \$56.95  
SQ-Auto without Key \$47.95

Specify — R Reed Relay Output  
— T Transistor Grid Block

### K. E. ELECTRONICS

2931 "F" WEST CENTRAL AVE.  
SANTA ANA, CALIF. 92704

## DIPLOLE ANTENNA CONNECTOR



**HYE-QUE (HQ-1)** dipole connector has coax SO-239 socket molded into glass filled plastic body to accept coax PL-259 plug on feedline. Drop cap keeps coax fittings dry. Instructions included. Guaranteed. At your dealers or \$3.95, postpaid. Companion insulators 2/\$3.99.

BUDWIG MFG. Co. PO Box 97H, Ramona, CA 92065

## THE BEVERAGE ANTENNA HANDBOOK

Construct and operate your own Beverage Antenna. Defeat the broadcast stations on 40 meters. Has plans for three band Beverage, 18-9.72 MHz, with steerable null and direction switching. Contains: Theory for single wire Beverage and two wire Beverage. Null steering. Direction switching. Antenna patterns. Effect of height, wave velocity, distributed losses. End terminations. Ground system. Construction diagrams. Circuit diagrams. Impedances. Short Beverage. \$5.00 postpaid. Spiral bound, 116 pgs. Published by Vic Mizek, W1WCR, Watson Road, Hudson, N. H. 03051.

# ALL-MODE VHF amplifiers

FOR BASE STATION & REPEATER USE



MODEL	INPUT	OUTPUT	PRICE
V70	10-20W	60-70W	\$298
V71	1-5W	60-70W	\$329
V130	25-40W	110-130W	\$389
V131	1-5W	110-130W	\$419
V135	5-10W	110-130W	\$419
V180	10-15W	180-200W	\$525
Universal 19" Rack Mount			\$25

- ☆ 143-149 MHz No Tuning
- ☆ AM - FM - CW - SSB
- ☆ 60dB Harmonics
- ☆ Heavy Duty
- ☆ No Power Supply Needed
- ☆ Illuminated Panel Meter
- ☆ + 13.5V/3Amp Socket

- ☆ 115 or 230V AC
- ☆ 60dB Spurious
- ☆ Fully Protected Output
- ☆ Internal T/R Switch
- ☆ U.S. Manufactured
- ☆ 19" Rack Panel Option
- ☆ Size 8-1/2 x 13 x 7" H

Only two things are needed to put this power house on the air with your handy-talky or mobile transceiver: a two foot piece of coaxial cable and a 115 or 230 volt AC outlet. That's all. You do not need anything else. The mobile transceiver can be powered directly from the accessory socket located in the rear panel of the RFPL amplifier. It puts out + 13.5 volts at 3 amperes. This is sufficient for powering most 15 watt transceivers.



DEALER INQUIRIES INVITED



RF POWER LABS, INC.

11013-118th Place N.E. • Kirkland, Washington 98033 • Telephone: (206) 822-1251 • TELEX No. 32-1042

## 10's OF THOUSANDS OF CRYSTALS IN STOCK!



H25C CASE  
SCANNER  
MONITOR  
10.7  
AMATEUR  
HAM  
2 METER  
CB  
STANDARD

Immediate delivery on most frequencies!  
OTHERS ARE SPECIAL ORDER

CRYSTAL BANKING SERVICE  
P.O. BOX 683  
LYNNFIELD, MASSACHUSETTS  
01940

# SPECSCAN-S Programmable Scanner

... The ONLY Digital Scanner made for the IC-22S. It adds a whole new dimension to 2M FM. If any other accessory can make your IC-22S as versatile as the SPECSCAN-S does, Buy It!

- Scans the entire 146-147 MHz Band in 15 kHz steps, automatically, or manually
- Exclusive VARI-SCAN™ control allows full control of scan rate in either direction!
- Full compatibility with the duplex mode.
- Uses state of the art CMOS logic.
- Low current drain. Less than 500 mA.
- RF immune. Unaffected by nearby equipment and in high RF areas.
- Large LED display lets you see every channel at a glance.
- Manual mode feature lets you scan past any portion of the band and manually select a desired channel.
- Can be used as a remote unit with the radio hidden under the seat, etc.
- Easy installation. Uses only one matrix position leaving the other 21 useable for manual programming.
- Automatically reads out your other 21 channels when they are used.
- Plugs into 9 pin accessory socket.
- Adjustable scan delay feature.
- 90 day limited warranty



ONLY **149<sup>95</sup>** Amateur Net

**SPECIAL PRE-WIRED PRICE**  
BRAND NEW IC-22S WITH  
SPECSCAN DIGITAL SCANNER  
Both for only **\$398.00**

## DIGITRAN KEYBOARD

12 Key **\$8.00**      LOW PROFILE YET ALMOST 1/16" STROKE


16 Key **\$10.00**



This very popular item at the 1976 Dayton Hamvention is **NOW OFFERED TO YOU** at these low prices. Incorporates the ideal "tactile feel" leaving no doubt that contact has been made. These **NEW** keyboards, manufactured by **THE DIGITRAN COMPANY**, are furnished with instructions for combining with a **MOSTEK** or **MOTOROLA** chip and a crystal (plus several small components) to become a Tone Encoder.

12 Key (2 of 7 Matrix) 2" x 2.7" x 5/16" . . . \$8.00  
16 Key (2 of 8 Matrix) 2.5" x 2.7" x 5/16" . . . \$10.00

## NEW MOSTEK AUTO-PATCH TONE GENERATOR

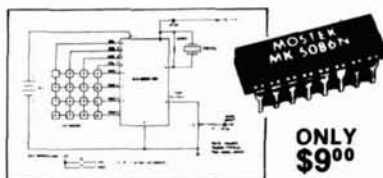

ONLY **\$9<sup>00</sup>**

Economical DTMF generating system combines CMOS logic, D-to-A converters, an operational amplifier and bipolar transistors on a single IC chip. Uses inexpensive 3.58 MHz crystal. Dual tones mix internally. Tones are 14-step synthesized sine waves for low distortion. Compatible with Digitran® keyboard. Common key function outputs. For 5-10 V. **Model MK 5086**. Interfaces to either a 2-of-8 keyboard or other electronic systems . . . . . **\$9.00**



## NEW!

**\$49<sup>95</sup>**

### Drake 1525EM

Pushbutton encoding microphone is pre-wired for use with TR-33 transceiver; can be used with almost any FM transceiver by modifying connections. No internal battery; takes 12 VDC from transceiver. Uses state-of-the-art IC technology. Reliable Digitran® keyboard. Impedance: 500 ohms. Wt.: 1 lb.

**\$49.95** incl. shipping continental U.S.



**Model 43**  
**\$120 + shipping**



... If you have been having difficulty locating the Wattmeter or element just right for you. . . . You may have been looking in the wrong places. Our large inventory of most common elements lets you get what you want when you need it. Give us a call first for your BIRD needs.

See us at the **Midwest ARRL Convention**, Wichita, Kansas — October 7, 8, 9.

Thanks for your great response to our 1977 Buyers Guide. The **78 Buyers Guide** will be available soon. Watch our ads to get your **NEW BUYERS GUIDE**.



## SPECTRONICS, INC.

1009 GARFIELD  
OAK PARK, IL. 60304  
312-848-6777  
TELEX 72:8310

## HOURS

### STORE HOURS:

Mon-Thurs 9:30-6:00, Fri. 9:30-8:00  
Sat. 9:30-3:00, Closed Sun. & Holidays.





Watch for our supermarket bargains each month!

# HOT NEWS!

FEATURING THE BARGAINS OF THE MONTH!!!!

# POLY PAKS® IS THE WORLD'S LARGEST ELECTRONIC DISCOUNT SUPERMARKET

OCTOBER, 1977, HAM SPECIALS



**RCA High quality "POCKET" VOM**  
• 1000 ohms per volt  
Model WV-539A. Features 1% precision, movements diode protected against burnout. Measures DC volts 0-15-150-1000; AC volts 0-15-150-1000; DC current 0-150ma; resistance X1000. Sensitivity 1000 ohms/volt AC-DC. Uses penlite cell, not included. Size 2 3/4 x 3 1/2 x 1 3/4". Wt. 6 ozs. Cat. No. 10H3921

**\$5.50 TV GAME & HI-FI JOY STICK**  
Includes four 100K pots for TV & computer games, and quadrophonic balanced 1 1/2 x 1 1/2 x 1 1/2". With 1 1/2" handle. Wt. 6 ozs. Cat. No. 10H3808

**NOISE-CANCELLING CB-HAM MIKE**  
Cuts noise of machinery, highway for clear transmission!  
• Virtually all rills, everywhere!  
Lo-impedance, freq. resp. 300-5000 Hz. With 9' coiled cord. Includes instructions for 100's of CBs. Wt. 20 ozs. No. 10H3902


**ECCO 10-POSITION BCD THUMBWHEEL SWITCH**  
1-2-4-8 BCD encoding! Positions labeled 0-7, F, L 3 for (F coded for 8, L coded for 9). White numerals on black background. Ecco 900 series. 1 1/4 x 1 1/4 x 1/2". Cat. No. 10H3846

**GE NI-CAD POWER PAKS**  
AA penlite cells, ganged in series! 1.25V each cell. Rechargeable! Wt. 2 oz. per cell. No. Cells. Vols. Sale!  
• 10H3888 2 2.5 \$2.50  
• 10H3889 3 3.75 3.50  
• 10H3890 4 5 4.50

**POLY PAKS "RAMS" 2102-1 PRICES**  
New from top U.S.A. makers. Tested for 500 msec. speed! Cat. No. 10H3548 FOR \$9.95

## QUAD AM-FM-MPX TUNER AMP

BUILT-IN QUAD STEREO TAPE PLAYER

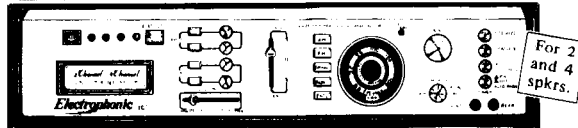

The finest unit we've ever offered. The "SYMPHONY" plays quad 8-track tapes in full dimension quad. Also features Matrix-Quad, derives quad sound from stereo records, tapes and FM. [86"] phono input cables and has outputs for 4 speakers, jacks for "Quad tape-output", and terminals for external FM antenna. Fits easily into wide console or cabinet of your own design. FM stereo indicator. Pushbutton switches select stereo. Matrix, 4D detribe, power On/Off. Bass and treble slide control. Additional multifunction switch selects AM, FM, FM-MPX, phono, tape; blue panel lights indicate these functions. Master slide volume control with individual balance controls for each channel. Output jacks for quad headphones. Tape deck with digital light indicates when a quad tape is inserted. Other lamps indicate the track being played. 116 VAC. Size: 22 x 8 x 6" deep. Wt. 9 lbs.

**J. C. PENNEY'S S-Track TAPE TRANSPORT**  
• Shielded preamp  
• 115V VAC fan-cooled motor  
• Slides easily into modular cabinet

**1-AMP REGULATED POWER SUPPLY**  
• In 5-12-15 volts!  
• 1.55V 2 for Cat. No. Volts  
• 10H3854 5  
• 10H3855 12  
• 10H3856 15

**MOTHERBOARD EDGE CONNECTOR**  
100 pins (53 on each side). Use with IMSAI & ALTAIR 1.025" pin crps, goldplated 3/16" wire wrap leads. Open ends, 8 wide PC boards, 8 ozs. Cat. No. 10H3887

**TRW 900 MHz UHF POWER TRANSISTOR**  
2 for NPN! CB'er's, Hams take note! Replaces many transmitter driver and output transistors. TO-18 case, 3/16" dia, with 1/2" leads. Two emitter leads. Buco 25V. Hfe (beta) 30-60. Ic 1.25 amp. Wt. 1.25 gm.  
• No. 10H3942 \$4.95

**MINI'S** We know we have the lowest prices!

Type	Sale	& Type No.	& Type No.
SN7400	\$0.14	SN7460	.20
SN7401	.14	SN7461	.14
SN7402	.14	SN7462	.14
SN7403	.14	SN7463	.14
SN7500	.14	SN7560	.14

# BARREL KITS

TEST 'EM YOURSELF 'N SAVE! EXCLUSIVE GUARANTEED 50% YIELD ON UNTESTED.....

**BARREL KIT #203**  
CALCULATOR KEYBOARDS  
10 for \$1.98

**BARREL KIT #204**  
LINE CORDS  
8 for \$1.98

**BARREL KIT #205**  
4 DIGIT READOUT MODULES  
5 for \$1.98

**BARREL KIT #206**  
HOBBY 1702A ROMS  
3 for \$1.98

**BARREL KIT #207**  
SHIELDED CABLE  
40 ft. \$1.98

**BARREL KIT #208**  
SOUND TRIGGERS  
3 for \$1.98

**BARREL KIT #209**  
MINI BLOCK CAPACITORS  
50 for \$1.98

**BARREL KIT #210**  
10V INDICATORS  
15 for \$1.98

**BARREL KIT #211**  
20 AMP INLINE BRIDGES  
20 for \$1.98

**BARREL KIT #212**  
1/2 WATT METAL FILM  
150 for \$1.98

**BARREL KIT #213**  
JUMBO RED LEDs  
15 for \$1.98

**BARREL KIT #214**  
MINI TRIM POTS  
30 for \$1.98

**BARREL KIT #215**  
HOBBY VOLTAGE REGULATORS  
25 for \$1.98

**BARREL KIT #216**  
T-3 BARRELED DUMPS  
10 for \$1.98

**BARREL KIT #217**  
PANEL SWITCHES  
30 for \$1.98

**BARREL KIT #218**  
MINI-DIP IC'S  
100 for \$1.98

**BARREL KIT #219**  
AXIAL ELECTROS  
40 for \$1.98

**BARREL KIT #220**  
UPRIGHT ELECTROS  
40 for \$1.98

**BARREL KIT #221**  
TERMINAL STRIPS  
100 for \$1.98

**BARREL KIT #222**  
SLIDE VOLUME CONTROLS  
10 for \$1.98

**BARREL KIT #223**  
RESISTOR SPECIAL  
200 for \$1.98

**BARREL KIT #224**  
PHOTO ELECTRIC CELLS  
10 for \$1.98

**BARREL KIT #225**  
HALF WATTERS  
200 for \$1.98

**BARREL KIT #226**  
NAT. IC BONANZA  
100 for \$1.98

**BARREL KIT #227**  
LM-340T VOLTAGE REGULATORS  
15 for \$1.98

**BARREL KIT #228**  
CAPACITOR SPECIAL  
100 pcs. \$1.98

**BARREL KIT #229**  
2 WATTERS  
100 for \$1.98

**BARREL KIT #230**  
POLYSTYRENE CAPS  
100 for \$1.98

**BARREL KIT #231**  
SLIDE SWITCHES  
30 for \$1.98

**BARREL KIT #232**  
HOBBY PNP POWER TRANSISTORS  
15 for \$1.98

**BARREL KIT #233**  
METALLIC RESISTORS  
100 for \$1.98

**BARREL KIT #234**  
PREFORMED DISCS  
200 for \$1.98

**BARREL KIT #235**  
2 WATTERS  
100 for \$1.98

**BARREL KIT #236**  
PLASTIC TRANSISTOR  
100 for \$1.98

**BARREL KIT #237**  
HIGH VOLTAGE RECTIFIERS  
200 for \$1.98

**BARREL KIT #238**  
LONG LEAD DISCS  
100 for \$1.98

**BARREL KIT #239**  
PRECISION RESISTORS  
200 for \$1.98

**BARREL KIT #240**  
VOLUME CONTROL  
30 for \$1.98

**BARREL KIT #241**  
SWITCHING DIODES  
100 for \$1.98

**BARREL KIT #242**  
DIP IC'S  
75 for \$1.98

**BARREL KIT #243**  
HIGH VOLTAGE RECTIFIERS  
200 for \$1.98

**BARREL KIT #244**  
DIPPED MYLARS  
60 for \$1.98

**BARREL KIT #245**  
PRECISION RESISTORS  
200 for \$1.98

**BARREL KIT #246**  
VOLUME CONTROL  
30 for \$1.98

**BARREL KIT #247**  
SWITCHING DIODES  
100 for \$1.98

**BARREL KIT #248**  
DIP IC'S  
75 for \$1.98

**BARREL KIT #249**  
HIGH VOLTAGE RECTIFIERS  
200 for \$1.98

**BARREL KIT #250**  
DIPPED MYLARS  
60 for \$1.98

**BARREL KIT #251**  
PRECISION RESISTORS  
200 for \$1.98

**BARREL KIT #252**  
VOLUME CONTROL  
30 for \$1.98

**BARREL KIT #253**  
SWITCHING DIODES  
100 for \$1.98

**BARREL KIT #254**  
DIP IC'S  
75 for \$1.98

**BARREL KIT #255**  
HIGH VOLTAGE RECTIFIERS  
200 for \$1.98

**BARREL KIT #256**  
DIPPED MYLARS  
60 for \$1.98

Terms: Add postage. Rated: net 30. Phone: Wakefield, Mass. (617) 245-3829. Retail: 16-18 Del Carmine St., Wakefield, MA. **POLY PAKS** P.O. BOX 942H LYNNFIELD, MA. 01940

# flea market



**RATES** Non-commercial ads 10¢ per word; commercial ads 60¢ per word both payable in advance. No cash discounts or agency commissions allowed.

**HAMFESTS** Sponsored by non-profit organizations receive one free Flea Market ad (subject to our editing). Repeat insertions of hamfest ads pay the non-commercial rate.

**COPY** No special layout or arrangements available. Material should be typewritten or clearly printed (not all capitals) and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** cannot check each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue.

**DEADLINE** 15th of second preceding month.

**SEND MATERIAL TO:** Flea Market, Ham Radio, Greenville, N.H. 03048.

**MOBILE IGNITION SHIELDING** provides more range with no noise. Available most engines. Many other suppression accessories. Literature, Estes Engineering, 930 Marine Dr., Port Angeles, WA 93862.

**QRP TRANSMATCH** with Preamp for HW7 Ten-Tec. Send stamp for details to Peter Meacham Associates, 19 Lorreta Road, Waltham, Mass. 02154.

**WANTED:** Janel preamps 432 pc/144 pb (W6RQZ), 1330 Curtis St., Berkeley, CA 94702.

**TECH MANUALS** for Govt. surplus gear — \$6.50 each: SP-600JX, URM-25D, OS-8AJU, TS-173/UR. Thousands more available. Send 50¢ (coin) for 22-page list. W3IHD, 7218 Roanne Drive, Washington, DC 20021.

**MAGAZINES** — Ham Radio 1968 through 1974. QST 1968 through 1974. Will ship to best offer. Otto Cordray, P.O. Box 242, Caldwell, Texas 77836.

**DISCOUNTS** — KLM, Larsen, Brimstone, Stereo Systems, Police Monitors, etc. Catalog available. BankAmericard & Mastercharge. 201-962-4695 Narwid Electronics, 61 Bellot Road, Ringwood, N.J. 07456.

## Foreign Subscription Agents for Ham Radio Magazine

Ham Radio Austria  
Karin Ueber  
Postfach 2454  
D-7850 Loerach  
West Germany

Ham Radio Belgium  
Sterehouse  
Brusselsesteenweg 416  
B-9218 Gent  
Belgium

Ham Radio Canada  
Box 114, Goderich  
Ontario, Canada N7A 3Y5

Ham Radio Europe  
Box 444  
S-194 04 Upplands Vasby  
Sweden

Ham Radio France  
Christiane Michel  
F-93117 Parly  
France

Ham Radio Germany  
Karin Ueber  
Postfach 2454  
D-7850 Loerach  
West Germany

Ham Radio Holland  
MRL Electronics  
Postbus 88  
NL-2204 Delft  
Holland

Ham Radio Italy  
STE. Via Maniago 15  
I-20134 Milano  
Italy

Ham Radio Switzerland  
Karin Ueber  
Postfach 2454  
D-7850 Loerach  
West Germany

Ham Radio UK  
P.O. Box 63, Harrow  
Middlesex HA3 6HS,  
England

Holland Radio  
143 Greenway  
Greenside, Johannesburg  
Republic of South Africa

**WANTED** — Panadapter and inexpensive Oscilloscope. Also all kinds of radio and electronics magazines and service literature for library. New or old. Donald Erickson, 6059-L Essex, Riverside, California 92504. 714-687-5910.

**CANADIANS** 1,000,000 surplus parts. Bargains galore. Free catalog. Etco-HR. Box 741, Montreal, H3c 2v2.

**PORTA PAK** the accessory that makes your mobile really portable. \$67.50 and \$88.00. Dealer inquires invited. P.O. Box 67, Somers, Wisc. 53171.

**COLLECTOR ITEMS:** Collins 75A2, sn183; 32V2, sn2450, both operational, both for \$135.00. ALSO: Galaxy Vmark 2, SC-35 speaker, AC-35, DC-35 supplies. Complete for \$295.00. K0JUSC; 1014 East 22nd, Hutchinson, Kansas 67501.

**RADIO MUSEUM** now open. Free Admission. 15,000 pieces of equipment from 1850 telegraph instruments to amateur and commercial transmitters of the 1920's. Amateur station W2AN. Write for information. Antique Wireless Assn., Main St., Holcomb, N. Y. 14469.

**WANTED:** IC-22S, Atlas 180/210 or Digital Multimeter. To trade or sell; Midland 13-500, Eumig Zoom Lens TV Camera — both new, with warranty. W6DOM, 6017 Majorca Ct., San Jose, California 95120. (408) 997-0132.

**QSL** — **BROWNE W3CJL** — 3035B Lehigh, Allentown, Pa. 18103. Samples with cut catalog 50¢.

**TRAVEL PAK QSL KIT** — Send call and 25¢; receive your call sample kit in return. Samco, Box 203, Wynantskill, N.Y. 12198.

**BUY-SELL-TRADE** write for free mailer. Give name, address and call letters. Complete stock of major brands new and reconditioned equipment. Call for best deals. We buy Collins — Drake-Swan etc. SSB & FM, Associated Radio, 8012 Conser, Overland Park, Kansas 66204. 913-381-5901.

**STOP LOOKING** For a good deal on amateur radio equipment — you've found it here — at your amateur radio headquarters in the heart of the Midwest. We are factory-authorized dealers for Kenwood, Drake, Collins, ICOM, Ten-Tec, Atlas, Regency, Tempo, Swan, Midland, Alpha, Standard, Dentron, Hy-Gain, Mosley, Cushcraft, and CDE, plus accessories. Thousands of thrifty hams from coast to coast already know us and we invite you to join them by writing or calling us today for our low quote and trying our personal and friendly Hoosier service. HOOSIER ELECTRONICS, P. O. Box 2001, Terre Haute, Indiana 47802. (812)-238-1456.

**PC BOARDS** prescaler — \$3.00 — HR Dec. 1975 Capacitor Checker — \$3.50 — April 1975. Glass, Plated, Drilled, Instructions. RTC Electronics, Box 2514, Lincoln, Nebraska 68512.

**MOTOROLA HT220, HT200,** and Pageboy service and modifications performed at reasonable rates. WA4FRV (804) 320-4439, evenings.

**WANTED:** SX-146 S-meter. T.E. Coates, W3HHB, 14303 Barkwood Drive, Rockville, MD. 20853.

**RECONDITIONED TEST EQUIPMENT** for sale. Catalog \$50. Walter, 2697 Nickel, San Pablo, Ca. 94806.

**MOTOROLA** — Hi Band Pager — #HO3BNC1107BO w/charger \$120.00; UHF Pager — #HO4BNC1103AO w/charger \$120.00; Mocom 30 VHF D33 CMT 3100 AM \$125.00; HT200 VHF \$150.00. J. Stephens K6UZP — 714-298-7832.

**FOR SALE** — Clegg FM-DX with touch-tone pad. \$450.00; EC-175 Regency frequency counter (LED) 175-MHz — XTAL oven \$375.00; HAL ST-6 (RTTY) demodulator/keyer \$350.00. Bob Goodman, P.O. Box 452, Alexandria, LA 71301 — phone (318) 640-1466.

**UHF REPEATER,** Vhf engineering strips, H.D. Power Supply, Phelps Dodge 638 duplexer, 2' Bud cabinet. COMPLETE, VERY CLEAN, WORKS PERFECTLY. \$475.000 firm. WR6BAL/7, 424 E. El Camino Dr., Phoenix, Arizona 85020, (602) 944-0528

**WANTED:** Schematics, Manual or any information on Morrow Twins. Also need dial but will buy whole unit. 356 E. 9th N., Logan, VT. 84321 WB70DA.

**UHF MOTOROLA MOTRAC U64LHT,** 4 freq., Trunk mount, PC, dimmer head, with 446/446 plus 3 sets of elements included. VERY CLEAN, \$375.00, WB6PBN/7, 424 E. El Camino Dr., Phoenix, Arizona 85020.


**HEATHKIT HX-10 XMTR,** SSB, CW, TTY, AM. 280 PEP. \$75.00. Shipping wt. 92 lbs. T.A. Carr, 452 Highland Ave., San Mateo, CA 94401.

**HEATHKITS BUILT** — 20 years experience. Write for details. K4TO, 1207 Monte Sano, Huntsville, AL 35801.

# NEW NEW NEW

## Exciting Products

### DATA SIGNAL AND DIGITRAN KEYBOARDS

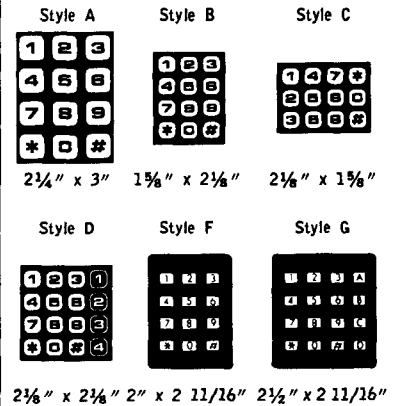

## SUB-MINIATURE TOUCH TONE ENCODERS

**MODEL SME** — Smallest available Touch Tone Encoder. Thin, only .05" thick, keyboard mounts directly to front of hand-held portable, while sub-miniature tone module fits inside. This keyboard allows use of battery chargers. Price \$34.50, with your choice of keyboards.

**MODEL DTM** — Completely self-contained miniature encoder for hand-held portables. Only 5/16" thick. Three wire connection. Automatic PTT keying optional. With your choice of keyboards. Price: **DTM - \$49.50, DTM/PTT - \$59.50.**

## TOUCH TONE ENCODER WITH AUTOMATIC DIALER

**MODEL 204** — Completely self-contained 12-digit Touch Tone Encoder with one automatic telephone number. Only 5/16" thick, for use on hand-held portables. Price **\$89.50** with your choice of keyboard.

**MODEL 205** — 16-digit keyboard allows for 12-digit manual encoding with automatic pushbutton keying of up to four telephone numbers. For hand-held portable operation. Price **\$109.50**, Styles D and G keyboards only.

## DO-IT-YOURSELF KITS

Or, if you prefer, all components necessary to build your own encoder may be purchased "ala carte".

Your choice of any keyboard ..... **\$8.50**  
Digital T.T. Encoder IC 14410 ..... **\$9.50**  
1 MHz ULTRA SMALL Crystal ..... **\$5.95**  
P. C. Board 0.8" x 1.2" and all resistors and capacitors ..... **\$3.50**



**DATA SIGNAL, INC.**  
2403 Commerce Lane  
Albany, GA 31707  
912-883-4703

250 MHz . . . ONLY \$129<sup>95</sup>

**STOP!** Don't order that counter kit until you see what EEB has come up with.

The NEW B & K 1827, 30 MHz counter (assembled and tested), a famous pre-scaler kit, hardware and complete instructions to result in 250 MHz Counter. ALL FOR \$129.95 postpaid!



### Model 1827

- 30 MHz reading guaranteed, 50 MHz typical.
- Full 6-digit display with range switch allows 8-digit accuracy.
- 1Hz resolution — even at 30 MHz and beyond.
- Completely portable for use anywhere.
- Exclusive battery saver features auto-shutoff of display to reduce battery drain.
- Operates on AA size batteries, AC with optional charger/adaptor or 12VDC with optional power cord/adaptor.

#### SPECS:

**FREQUENCY CHARACTERISTICS**  
Range: 100Hz to 30 MHz (guaranteed); 50 MHz typical. Accuracy:  $\pm 1$  count. Resolution: 1 PPM of a 6 digit scale.

**INPUT CHARACTERISTICS**  
Impedance: 10 K $\Omega$  minimum. Connector: RCA Phono. Sinewave Sensitivity: 100mV RMS; 200 kHz—30MHz, 200mV RMS; 100Hz—200kHz. INTERNAL TIME BASE CHARACTERISTICS (25° C).

Frequency and Type: 4.0MHz crystal oscillator. Setability:  $\pm 0.25$  PPM ( $\pm 1$ Hz). Temperature Stability: Better than  $\pm 0.001\%$  (i.e.  $\pm 10$  PPM) from 0-50°C ambient.

Model 1827 only	\$119.95
Prescaler Kit	22.50
Misc. & Instructions	12.50
	<b>\$154.95</b>

**YOU PAY ONLY \$129.95**

AC Charger and NICADS	\$31.00
Test Antenna (BNC)	\$4.00

## NEW MS-15 MINISCOPE



A Serviceman's Small Oscilloscope with Big, Big Performance and a Low, Low Price. The Model MS-15 by Non-Linear Systems, Inc.

#### FEATURES

- 15 megahertz bandwidth.
- External and internal trigger.
- Time Base — 0.1 microseconds to 0.5 Sec/div — 21 settings.
- Battery or line operation.
- Size: 2.7"H x 6.4"W x 7.5"D
- Automatic and line sync modes.
- Power consumption less than 15W.
- Vertical Gain - 0.01 to 50 volts/div 12 settings.
- Weight is only 3 pounds.

• \$289.00

Guess who's got your **BIRD**



- EEB DOES, and here's why . . .
- We pay the AIR FREIGHT on all prepaid or credit card orders.
  - Call our order desk collect: 703-938-3511.
  - We stock in depth: Bird 43 Thru-line, All Table 1 elements, CC-1 & EC-1 cases.

**\$120.00**

**AUTHORIZED BIRD DISTRIBUTOR**

All Prepaid & Charge Orders Shipped NO CHARGE To You. Sales tax 4% to Virginia residents only.

**ELECTRONIC EQUIPMENT BANK, INC.**  
516 Mill St., Vienna, VA 22180  
Call COLLECT 703-938-3511

# flea market

**SWAN TV2-B** two meter transverter. \$200 K3RYL 215-691-0669.

**TRANSMITTING TUBES**, HV and filament xfms, rotary inductors, transmitting capacitors. Send stamp for flyer. T.S. Marinich Electronics, 102 Bell St., Weirton, W. Va. 26062.

**OLD QSTs WANTED**, Motorola HT100 wanted, state asking prices. For sale or trade: Life Library of Photography, other photo literature. Al Blank, W1BL, 727 Pine St., Bristol, CT 06010.

**YOUR CALL** on a Bumper Sticker. Red letters on White or Black \$1.25 postpaid. R. Schweizer, Box 4675, Margate, Florida 33063.

**TELETYPE EQUIPMENT** for beginners and experienced operators. RTTY machines, parts, supplies. Beginner's special: Model 15 Printer and demodulator \$139.00. Dozen black ribbons \$6.50; case 40 rolls 11/16 perf. tape \$17.50 FOB. Atlantic Surplus Sales, 3730 Nautilus Ave., Brooklyn, N. Y. 11224. Tel: (212) 372-0349.

**COLLINS 755-3**, \$360 — Nems Clarke Rcvr. 15o1, \$180. Skysweep Rcvr. \$60 — all books. WA2EUS, 110 Lafayette St. Copiague, NY 11726.

**MOBILE BONDING STRAPS** under 50¢ each. Literature. Estes Engineering, 930 Marine Drive, Port Angeles, Wash. 98362.

**QSL FORWARDING SERVICE** — 30 cards per dollar. Write: QSL Express, 30 Lockwood Lane, West Chester, PA. 19380.

**FERRITE BEADS**: w/specification and application sheet - 10/\$1.00. Assorted PC pots - 5/\$1.00. Miniature mica trimmers, 3-40 pf. - 5/\$1.00. Postpaid. Includes latest catalog. Stamp for catalog alone. CPO Surplus, Box 189, Braintree, MA 02184.

**FREE catalog**. Solar Cells, Nicads, Kits, Calculators, Digital Watch Modules, Ultrasonics, Strobes, LEDs, Transistors, ICs, Unique Components. Chaney's, Box 27038, Denver, Colo. 80227.

**THE "CADILLAC"** of QSL's! New! Samples: \$1.00 (Refundable) — MAC'S SHACK; Box #1171-D; Garland, Texas 75040.

**CASH** for any Collins unit, 618T, 490T, modules, parts, accessories. Air Ground Electronics, P.O. Box 416, Kearny, NJ 07032.

**MODERN CODE PRACTICE**. 0-22wpm on four 60 min. cassettes, \$10. Royal, P. O. Box 2174, Sandusky, Ohio 44870.

**FOR SALE**: 6 pole 250 Hz crystal filter for FT101, FR101 — \$41. Koichi Kawai JA2UEO Denden Tomioka 1, A506, 2154, Sugita, Isogo-ku, Yokohama 235, Japan.

**EXCLUSIVELY HAM TELETYPE** 23rd year, RTTY Journal, articles, news, DX, VHF, classified ads. Sample 35¢. \$3.50 per year. 1155 Arden Drive, Encinitas, Calif. 92024.

**FIGHT TVI** with the RSO Low Pass Filter. For brochure write: Taylor Communications Manufacturing Company, Box 126, Agincourt, Ontario, Canada M1S 3B4.

**RUBBER STAMP**, name/call/QTH \$2.50 ppd. (CA residents add tax). LWM Press, Box 22161, San Diego, CA 92122.

**COMPUTER HOBBYISTS** — Classified advertising newsletter. Ads, New Products, etc. Every 3 wks. — Since Jan 76 \$3.75/year. Free Sample. ON LINE, 24695 Santa Cruz Hwy., Los Gatos, CA 95030.

**TELETYPEWRITER PARTS**, gears, manuals, supplies, tape, toroids. SASE list. Typetronics, Box 8873, Ft. Lauderdale, FL 33310. Buy parts, late machines.


**TEKTRONIX 7000** series plug ins. Late eng. models. Work like new 7A22 2 \$250, 7B70 2 \$350, 7B71 @ \$350. Walt Williams, 1901 SEM Inter #76, Hillsboro, OR 97123.

**LET LaRue BE YOUR VHF GURU!** Factory-authorized dealer for: ICOM, Regency, Standard, Cushcraft and CES Touch-Tone pads. Antenna Specialists 2-meter 5/8 wave mobile antennas in stock. Bomar 2-meter crystals for the above radios on most standard ARRL repeater frequencies \$4.50 each postpaid. Mastercharge and BankAmericard accepted. For the greatest deal call or write LaRue Electronics, 1112 Grandview St., Scranton, Pennsylvania 18509. (717) 343-2124.

**FOR SALE**: Brand new boxed advanced coax relays. 6.12.24.100VDC. 117VAC. \$15.00 with aux. contacts, \$12.00 each without. Antique R.R. Sounders (new) \$50.00 each — have four. Add \$1.00 for shipping.

# PARTS PANIC

## POPULAR TOROID ASSORTMENT

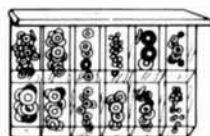

**ONLY \$9.95** (\$15.00 Value)

We Stock a Complete Line of Powdered Iron and Ferrite Products.

**FOR CONVENIENCE AND LOWER COST, ASSORTMENT INCLUDES: 2 pcs. each, T25-2, T25-6, T37-2, T37-6, T37-10, T37-12, T50-10, T50-12, T68-10, T80-2, T80-6, T94-2. 3 pcs. each, T50-2, T50-3, T50-6, T68-2, T68-3, T68-6 AND CONVENIENT STORAGE BOX AND SPEC SHEETS.**

#### FERRITE BEAD ASSORTMENT


Includes convenient plastic storage box and one dozen each of FB43-101, FB43-801, FB64-101, FB64-801, FB73-101 and FB73-801 plus new spec sheets. Value \$7.50 for \$6.95.

#### NOW IN STOCK

Transmitting Variables — Roller Inductors — Counter Dials — Air Wound Coils — Couplings — Knobs — Receiving Variables — Toroids — R. F. Chokes — Coil Forms and more from Millen - E. F. Johnson - Barker & Williamson - JW Miller - Hammarlund. Send First Class Stamp for Flyer. Add \$2.00 to each order for shipping and handling. Prices subject to change.

**G.R. WHITEHOUSE & CO.**  
10 Newbury Drive, Amherst, N. H. 03031

## PRE-AMP

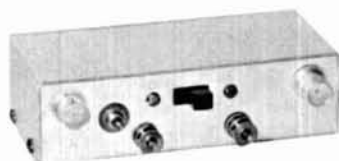

### HIGH GAIN • LOW NOISE

35dB power gain, 2.5-3.0 dB N.F. at 150 MHz 2 stage, R.F. protected, dual-gate MOSFETS. Manual gain control and provision for AGC. 4 3/8" x 1 7/8" x 1 3/8" aluminum case with power switch and choice of BNC or RCA phono connectors (be sure to specify). Available factory tuned to the frequency of your choice from 5 MHz to 250 MHz with approximately 3% bandwidth. Up to 10% B.W. available on special order.

N. Y. State residents add sales tax.

Model 201 price: 5-250 MHz \$29.95

**Vanguard Labs**

196-23 JAMAICA AVE.  
HOLLIS, N. Y. 11423





# MADISON SUPER STATION BUYS

**OMNI-J** 2-meter mobile or portable antenna. 1/2" thread, 5dB gain (1.5dB gain over conventional 1/2-wave mobile whip antenna) \$29.95; 220-MHz \$27.95. Guaranteed results.

**ANTENNA SPECIALISTS** VHF antenna line. Write Don for catalog and quote.

**PREMAX** 4-foot ground rod plus clamp \$4.50

**MIDLAND** 23-136 dual meter reads SWR and relative power. Handles 1 kW from 3-150 MHz. \$21.95

**YAESU FT-101EE** - Hy Gain 18AVT/WB vertical antenna \$649.00

**YAESU FT-101EX** - Hy Gain 18AVT/WB vertical antenna \$589.00

**HY GAIN 18AVT/WB** 100 feet RG8 coax \$100.00

**HY GAIN 18V** vertical Model 214 2m Yagi \$19.95

**Model 214 2m Yagi** \$21.50

**Hy-Gain 2BDQ Dipole** \$39.95

**VHF SPECIALS:** Kenwood TS-700A List \$599 Call for quote

**KLM:** Antennas, Linears, Accessories All In Stock

**FREE** balun w/2 meter base antenna.

**JANEL PREAMPS:** In Stock. Technical Books (ARRL, Sams, Tab, RCA, T.I., etc.)

**HAM X ROTOR** (New Model) Turns 28 sq. ft. of antenna List \$325 Order Now Your Price \$289

**COE Big Talk Rotor** \$79.00

**CDE HAM-II** \$129.00

**BIRD 43 WATTMETERS** plus slugs in stock.

**SWAN METERS:** WM 6200 VHF Wattmeter \$49.95; SWR 1A \$21.95

**TELEX HEADSETS:** In Stock

**CETRON 572B** \$24.95 ea.

**ADEL nibbling tool,** \$6.45; punch \$3.50

**CABLE** 5/32", 6-strand, soft-drawn guy cable. For mast or light tower, 3' foot.

**BELDEN COAX CABLE:** 8237 RG8 19' ft. 5-14 RG8 foam 23' ft., 8448 8-wire rotor cable 14' ft., 8449 7' ohm kw twinlead \$19/100 ft., 8435 200 ohm kw twinlead \$12/100 ft., Amphelot PL 259 59', UG175 adapter 19', PL 258 dbf female \$1.00.

**NYLON CORD** 9000 ft. per roll \$15.00

**BELDEN** 14 gauge copper stranded antenna wire \$5.00/100 ft.

**RG8 foam Xtra-Flex coax,** 100' Braid coverage, 23' ft.

**22 gauge plastic covered ant. wire** for loop wire, radials \$3.50/1000 ft.

**KESTER SOLDER** 1 lb. 60/40 .062 \$6.50

**Leader** - Amateur Test Equip. - 10% off list.

**Mallory** 2.5A 1000PIV epoxy diode 19' ea.

**CALL FOR QUOTES ON:** YAESU FT301D, FT301, KENWOOD TS520S, TS820S, TS600A, TR7400A, FT101E, TEMPO 2020 & ETO-ALPHA. ALL IN SEALED CARTONS. CALL FOR QUOTES ON ITEMS NOT LISTED.

**CALL FOR FAST QUOTE, OR WRITE AND INCLUDE TELEPHONE NUMBER. IF WE HAVE YOUR BARGAIN, WE'LL CALL YOU PREPAID.**

**TERMS:** All prices FOB Houston. Prices subject to change without notice. All Items Guaranteed. Some items subject to prior sale. Send letterhead for Amateur dealers price list. Texas residents add 5% tax. Please add postage estimate, excess refunded.

# MADISON ELECTRONICS SUPPLY, INC.

1508 MCKINNEY HOUSTON, TEXAS 77002  
713/658-0268 Nites 713/497-5683

# flea market

**VERY in-ter-est-ing!** Next 4 Issues \$1 "Ham Trader Yellow Sheets," Sycamore, IL 60178.

**POWER SUPPLIES** - Brand New 2.5 amp. Less regulator circuit. You add. With circuit plans. \$13 PP. Telstar Ent., E. 16109 Longfellow, Spokane, WA 99216.

**THE VIDEO AMATEUR** is a new publication of, by and for the video enthusiast. Look to us for service tips, modifications, bargains on video gear and a wide exchange of products and information. Send for a free copy to P.O. Box 250, Coyote, CA 95013.

**BUY-SELL-TRADE.** Write for free mailer. Give name, address and call letters. Complete stock of major brands new and reconditioned equipment. Call for best deals. We buy Collins-Drake-Swan etc. SSB & FM. Associated Radio, 8012 Conser, Overland Park, Kansas 66204. 913-381-5901

**LET'S TRADE.** I have new HORNET ANTENNAS. 6-10-15 & 20 meter beams; 10 to 80 element 2-meter antenna systems; stacking kits, antenna hardware, etc. I need good clean transmitters, receivers, transceivers, test equipment. Jack W5AJZ, Box 880, Duncan, OK 73533.

**R-4C, FL-6000, FL-1500, FL-500, FL-250, 4-NB** noise blander, 12 xtals and MS-4 speaker \$650.00; T-4XC, AC-4 power supply, two xtals \$550.00; MN-4 matching network with Waters 384 dummy load \$130.00; SB-610 monitor scope \$100.00; SB-620 scanalyzer \$120.00; SB-630 station console \$75.00; SB-650 Freq. Disp. \$150.00; Astatic T-UG8 transistorized stand with Astatic 77L dynamic cardioid microphone \$75.00; Brown CTL-A paddle and key \$25.00; Everything above mint \$1750.00; Ralph Conner, WA3OBW, 149 Gladstone St., Phila., PA 19148. Phone 215-HO 2-9293.

**SEVERAL NEW COAXIAL RELAYS,** 12 Vdc, leads, use favorite connectors, \$5; Three new regulated, variable, 12 Vdc 5A power supplies, \$20 each FOB. List shack cleanup SASE. W4API, Box 4095, Arlington, Virginia 22204.

## Coming Events

**THE FOUNDATION FOR AMATEUR RADIO** annual Hamfest at the Gaithersburg Fairgrounds, Gaithersburg, MD., Sunday, October 23rd, 1977. Large flea market, food service, exhibits, ladies events, supervised children's program, and many prizes. Main events are all indoors. Picnic grounds, free parking; will be held rain or shine; participation fee is \$2.00; sales space for flea market \$5.00 first-come basis; commercial exhibitors \$10.00, pre-registration required prior to October 20th; nearby motel rooms available. For information write or call Hugh Turnbull, W3ABC, 6903 Rhode Island Avenue, College Park, MD. 20740; telephone (301) 927-1797.

**WESTERN MICHIGAN UNIVERSITY** will hold its 23rd annual VHF Conference, November 19, 1977. Contact Dr. Glade Wilcox, W9UHF/B, Dept. of Electrical Eng., WMU Kalamazoo, Michigan 49008.

**"GREATER LOUISVILLE HAMFEST** Sunday Sept. 25, 1977. Kentucky Fair and Exposition Center, West Wing Pavilion. Indoor exhibitors area. Indoor and Outdoor Flea Market. Admission \$2.00. Vendors, admission plus \$2 indoors space or \$1 outdoors space. For further info, or hotel, motel or camping reservations contact K4GOU, Denny Schnurr, 2415 Concord Dr., Louisville, KY 40217, phone #502) 634-0619."

**REPEATER ASSOCIATION DOWNRIVER AMATEUR RADIO** Swap & Shop Hamfest - October 16, 1977 9 AM to 3 PM at Kennedy High School, Northline Road (East of US 24) Taylor Michigan. Talk in on 147.93/33 .52 and .94 simplex. Door prizes, food, fun. Admission \$2 - YLs free. For information: RADAR, Inc., Box 1023, Southgate, MI 48195.

**HAMFEST** Lima, Ohio, October 9. The Northwest Ohio ARC 3rd annual hamfest at the Allen Country Fairgrounds. Two large buildings, tables and table space available. Dealers welcome. For information and reservations write: N.O.A.R.C., P.O. Box 211, Lima, Ohio 45802. Phone 640-1433 or 991-2716.

**AMSAT** annual meeting Saturday, October 8, 1977 at the Goddard Space Flight Center Employees Recreation Center in Greenbelt, MD. Everyone invited. The afternoon of technical and general interest talks has been greatly expanded and will begin at 1 P.M. The meeting location is easily accessible by major highways, and parking is at the door. For a map and a list of talks please send an SASE to AMSAT, Box 27, Washington, DC 20044.

## ALDELCO SEMI-CONDUCTOR SUPERMARKET RF DEVICES

2N3375 3W 400 MHz.....5.50	2N8080 4W 175 MHz.....5.40
2N3866 1W 400 MHz.....1.15	2N6081 15W 175 MHz.....8.45
2N5589 3W 175 MHz.....4.75	2N6082 25W 175 MHz.....12.95
2N5590 10W 175 MHz.....7.80	2N6083 30W 175 MHz.....10.30
2N5591 25W 175 MHz.....10.95	2N6084 40W 175 MHz.....16.30
2SC517.....3.95	2SC1307.....5.25
2SC1226.....1.25	2N4427.....1.35
2SC1306.....4.30	2N5109.....2.05

**NOW NEW IMPROVED DIGITAL ALARM CLOCK KIT** Hours + Minutes + Seconds displayed on six BIG 0.5 Fairchild 7 Segment Display LEDs. 12-hour format 24-hour alarm with snooze feature, plus elapsed time indicator and freeze feature. Eight pages of pictorials and instructions. NEW on-board power transformer and circuitry for optional time base with simulated wood grain cabinet \$23.95

**12/24 Hour Clock Kit** Six big .5 LEDs freeze feature with simulated wood cabinet. \$23.95

**COMBINATION DIGITAL CLOCK AND FREQUENCY COUNTER KIT** 6 digit 40 MHz counter AND 12-24 hour clock kit. Battery operated with 110V charger.

5 A.A. NiCad batteries not included. 2" x 4-1/4" x 6" cabinet. ONLY \$99.95 Assembled unit complete for \$139.95

**VARIABLE POWER SUPPLY KITS** - 600 Ma, 5-15 VDC \$6.95 12-28 VDC \$8.95 75 cents per unit shipping

**NOW!**

## Dual Digital 12-24 hour clock kit



MODEL ALDS:

Six big .5 display LEDs in an attractive black plastic cabinet with a red front filter. Great for a ham or broadcast station. Set one clock to GMT for the other to local time. Or have a 24 hour format on one clock and 12 hour on the other. Freeze feature lets the clock be set to the second. Each clock is controlled separately. Cabinet measures 2" x 4-1/4" x 9-1/2". Complete Kit \$44.95.

We have 7400 series ICs send stamp for catalog.

Add 5% for shipping. Min. order \$10.00. Out of USA send Certified Check or Money Order. Include postage.

# ALDELCO

2281H Babylon Tnpk., Merrick, NY 11566  
(516) 378-4555

## TEST EQUIPMENT

All equipment listed is operational and unconditionally guaranteed. Money back if not satisfied - equipment being returned must be shipped prepaid. Include check or money order with order. Prices include UPS or motor freight charges.

BOONTON 190A Q-mtr 30-200MHz	\$425
BOONTON 202E AM-FM sig gen	
54-216MHz	425
DEI TDU-4 30MHz video display	55
GR1001A LF sig gen 5kHz-50MHz	385
HP100ER Freq stand .05 parts/mil	
Outputs 10,100Hz; 1,100,100kHz	155
HP160B (USM105) 15mHz scope with reg horiz, dual trace vert plugs	375
HP166B (Mil) Delay sweep for above	130
HP170A (USM140) 30mHz scope with reg horiz, dual trace vert plugs	475
HP175A 50mHz scope with reg horiz, dual trace vert plugs	565
HP185A Sampling scope to 1ghz	
186B xstr rise time plug	585
HP202B LF Osc .5Hz-50kHz 10v out	75
HP205AG Lab audio gen .02-20kHz	195
HP212A Pulse gen .06-5kHz PRR	65
HP524D Freq counter-basic range 10Hz-10mHz extends w/plug-ins	195
HP540B Trans osc to 12.4ghz for use w/HP524-tyoe counters	145
HP616 Sig gen 1.8 4ghz FM-CW	365
HP686 Sweep gen 8.2-12.4ghz sweep range 4.4mHz-4.4ghz	495
HP803A VHF Ant bridge 50-500MHz	135
SOLITRON 200A SCR tester - all functions w/scope output	135
Tek181 Time mark scope calib.	55
Tek190 Sig gen (const ampl) 50mHz	125
Tek536 11mHz X-Y scope - uses two letter-series plug-ins	295
Tek565 Dual beam 10mHz scope less plug-ins (3 series)	625
TS505 Std VTVM (rf-500mHz)	65

For complete list of all test equipment send stamped, self-addressed envelope

## GRAY Electronics

P.O. Box 941, Monroe, Mich. 48161  
Specializing in used test equipment.



## CHOOSE ONE OF THESE TWO GREAT 2-METER FM TRANSCEIVERS. BOTH SYNTHESIZED FOR STANDARD AND "ODD-BALL" REPEATER SPLITS!

**Model FM-28** Check these outstanding features: Fully-synthesized from 144 to 148 MHz in 5 KHz steps. Bright six-digit frequency display. Supplied with simplex, plus 600 and minus 600 KHz offsets. Up to two additional "non-standard" offsets available. Clean 25 watt transmitter. 0.25 UV receiver with helical front end. Modular construction. All solid state. Complete with base station and mobile mounts, hardware, DC cable, microphone and manual. **Introductory priced at only \$359.95.**

**Model FM-DX** Compare the specifications of this unchallenged performer: 40 watt transmitter output. Extended frequency coverage from 143.5 to 148.5 MHz to facilitate MARS and CAP. Supplied with simplex, plus 600 and minus 600 KHz offsets. Up to three additional "non-standard" offsets available. LED frequency display. Selective, single conversion receiver. Rugged extruded chassis and modular construction will withstand the most severe environment. Engineered and built in USA. Shipped with mobile mounting hardware, power cables, microphone and manual. **Limited time pricing only \$499.00.**

**Optional accessories:** Include base station, power supplies, tone encoders, antennas and solid state power amplifiers. Write or telephone today for detailed specifications.

**Count on Clegg superior service.** Clegg's well staffed, well equipped organization is always available to you. Whether you need free product literature, replacement parts, service or just information, make a free Watts-line call from anywhere in the USA (except Pennsylvania) at no cost. Just dial 1-800-233-0250. In Pennsylvania, call (717) 299-7221 collect.

Should your Clegg product ever require service, you can expect the fastest turn-around time in the industry—typically 48 hours—almost always less than one week.

**Direct to you.** Because Clegg considers licensed amateurs a professional group, you can purchase directly from Clegg and save dealer and middleman markup. And you're protected.

All Clegg products are sold with a 10-day money-back guarantee.

To place your order, send check (Visa or Master Charge accepted) to Clegg Communications Corporation, 208 Centerville Road, Lancaster, Pennsylvania 17603. Better yet—phone us on our TOLL-FREE line and we'll ship today.

# Clegg

Advanced technology in action!



## Tone Encoders


For Continuous Tone Coded Squelch Systems (CTCSS)

Compatible with subaudible tone systems such as Private Line, Channel Guard, and most others


And a new dual encoder for both CTCSS & DTMF
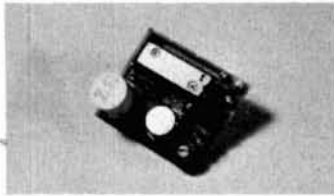
### Features:

- Temperature and frequency stability of  $\pm 0.1$  Hz from  $-25^{\circ}\text{C}$  to  $+80^{\circ}\text{C}$
- Frequency accuracy of  $\pm 0.25$  Hz
- Plug-in-type tone elements
- Low-distortion sinewave
- Immunity to RF
- All EIA frequencies available, 67.0-203.5 Hz
- Other EIA frequencies available on special order
- 9-16 VDC, reverse-polarity protection
- Adjustable tone output level



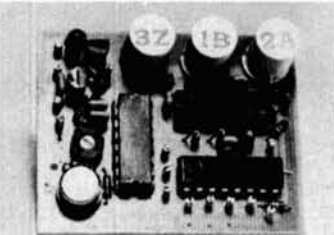TG-1A miniature encoder. Will fit into most FM radios. Only three connections to make—ground, +VDC, and tone output. Wired and tested, with one tone element. Size: approximately 1" x 1.2" x 0.6". Price: \$24.95.



TG-3A three-frequency encoder. Wired and tested. Includes three tone elements and frequency-selecting switch. Size: approximately 1.6" x 2.0" x 0.6". Price: \$56.95.



2027 A/B CTCSS and DTMF encoder. Both types of encoding are combined onto one small board for most hand-held and mobile radios. Only three connections are required from the encoder board: +VDC, ground, and tone output. Wired and tested, with one tone element and a 12- or 16-key DIGI-TRAN<sup>®</sup> keyboard. Size: approximately 1.8" x 2.3" x 0.6". Price: \$71.95 for 2027A (12 key); \$78.95 for 2027B (16 key).

NEW! MTG-1 Tone Encoder Fits HT220 slim line, PL model, and OMNI PL models. Price: \$27.95 wired & tested with one tone element.

Additional tone elements \$3.00 each.

Illinois residents add 5% sales tax.

Send your order today, to:

—TransCom

Post Office Box 120  
Addison, Illinois 60101  
Phone: (312) 653-6724

## flea market

**SANGAMON VALLEY** Radio Club Second Annual Hamfest on Sunday, September 25th, at the Sangamon County Fairgrounds, New Berlin, Illinois, 16 miles west of Springfield. Indoor display area and covered pavilion. Exhibits, food and ladies activities. Overnite camping! Tickets: \$1 advance, \$1.50 at gate. First Prize — Wilson HT. Talk-in: 146.28/88 and 52 MHz. Information: WB9-QWR, Carole Churchill, 622 Magnolia, Rochester, IL, 62626.

**OCTOBER 9, 1977** in Yonkers, NY at Redmond Field, Cooke Ave. Talk In 146.265 and 146.52 simplex. Further info from Douglas McArtin, WA2AUJ, 411 Bellevue Ave., Yonkers, NY 10703.

**PAN AMERICAN HAM JAMBOREE/EXPOSITION.** Ft. Lauderdale, FL, October 29 & 30 at the National Guard Armory (State Road 84). Hours: Saturday, Noon to 10 PM; Sunday, 9 AM to 5 PM. Talk-in on 31/91 or 52 simplex. Additional info from WA4ZRW (305) 581-2718.

**FLORIDA GULF COAST CONVENTION.** Clearwater Beach, November 19 & 20. Sponsored by Florida Gulf Coast A.R.C. Exhibits, flea market, technical sessions, FCC exams, forums and much more. Full info and reservation for Sheraton Hotel, contact: F.G.C.A.R.C. Convention, P.O. Box 157, Clearwater, FL 33517.

**THE MARION AMATEUR RADIO CLUB'S** Annual "Heart of Ohio Ham Fiesta" is Sunday, October 23, at the National Guard Armory from 8 AM to 5 PM. Free Parking. Admission \$1.00 advance, \$2.00 at gate. Tables must be reserved \$3.00 each. Refreshments available. Write Earl Adey WB8EDO, 2697 Curren Drive, Marion, Ohio 43302.

**THE REPEATER ASSOCIATION** of Downriver Amateur Radio (R.A.D.A.R.) Hamfest will be held on Oct. 16, 1977 at the Kennedy High School in Taylor, Michigan, on Northline Rd. east of Telegraph (U.S. 24). Talk-in will be on 52-52, 34-94, 93-33. Door prizes and food. Admission \$2.00/YI's free. Reserved Tables \$1.00. Open 9 AM until 3 PM. For further info write: R.A.D.A.R. Inc., P.O. Box 1023, Southgate, Michigan 48195.

**RADIO AND ELECTRONIC SWAP AND SHOP,** sponsored by the Marshall County Amateur Radio Club, will be held on Sunday, October 30, 1977, at the Plymouth, Indiana National Guard Armory, located at 1220 West Madison Street, from 8 AM to 5 PM. Free tables, no charge for set-up. Tickets \$2.00 at the door. Food, drink, and door prizes. Talk-in on 146.07-67 and 146.52 simplex. For further information contact Wayne Zehner, WA9INM, Rt. 3, Box 526, Plymouth, Indiana 46563.

**BLOSSOMLAND** annual fall Swap-Shop, October 2nd, Berrien County Youth Fair Grounds, Berrien Springs, Michigan. Large, convenient facilities. Prizes, refreshments, fun. Open all night for set-up. Table space restricted to radio and electronic items. Advance ticket donation \$1.50. Tables \$2. Write: John Sullivan, P.O. Box 345, St. Joseph, Mich. 49085. Make checks payable to Blossomland Hamfest.

**MEMPHIS IS BEAUTIFUL IN OCTOBER!** The Memphis ARRL-sponsored Hamfest, bigger and better than the 4,500 who attended last year, will be held at State Technical Institute, Interstate 40 at Macon Road, on Saturday and Sunday October 1 and 2. Demonstrations, displays, MARS meetings, flea market, ladies flea market, too! Hospitality room, informal dinners, XYL entertainment, many outstanding prizes. Dealers and Distributors welcome. Contact Harry Simpson W4SCF, PO Box 27015, Memphis, TN 38127 for further information.

**NORTHEASTERN STATES** 160 Meter Amateur Radio Association annual election and banquet. Saturday, October 8, 1977 at Kozel Tavern, 5 miles northeast of Hudson, NY on Rt. 9H. Flea market in rear parking lot starting at 1 PM. Dinner at 6 PM. For any further information, write or contact W1EUB, Sec. Treas. on 160 meters.

**HAMARAMA '77 & Mid-Atlantic States VHF Conference.** Conference to be held Oct. 1, Treadway Inn on Easton Rd., Willow Grove, PA 19090. Flea Market to be held Oct. 2, Bucks Country Drive-In Theater, Easton Rd., Warrington, PA. For further info contact Ron Whitsell, WA3AXV, P.O. Box 353, Southampton, PA 18966. Phone: 215-355-5730.

**NEW YORK** Radio Amateurs of Greater Syracuse (RAGS) Hamfest Saturday, October 8 from 9 A.M. to 6 P.M. at the Syracuse Auto Auction, 4 miles south of Syracuse, N.Y. on U.S. Route 11 between Nedrow and LaFayette. Flea market, CW and wiring contests, forums, panels and eyeball QSOs. Lunch counter, nearby campsite and Apple Festival for the family. Talk-in on 31/91. Tickets are \$1.50 before October 1 and \$2.00 at the gate. For further information, contact Roger Hamilton, WA2AEW, c/o RAGS, P.O. Box 88, Liverpool, New York 13088.

PARAFRAME

## PARABOLIC ANTENNA FRAMEWORKS

FOR...

- EME
- TV DXing
- Radio Astronomy
- Experimenting
- Student projects

Apertures available —

12', 16', 20' TBA: 24'

With PARAFRAME you can build a complete 20' parabolic antenna for \$1300. With interchangeable feeds you can have several antennas for the price of one.

**JAMES K. VINES**

611 Farmview Rd.  
Park Forest South, IL  
60466  
(312) 534-0889  
after 7 PM CDT



ICOM



**IC-22S**  
146 MHz FM 10 W  
TRANSCEIVER



**IC-211**  
144 to 148 MHz  
SSB/FM/CW  
10 W TRANSCEIVER

IMMEDIATE DELIVERY  
SHIPPING PREPAID IN USA

**MASTERS COMMUNICATIONS**

7025 N. 57th DR.  
GLENDALE, AZ 85301



PHONE  
602-939-8356



**DIODES/ZENERS**

1N914	100v	10mA	.05
1N4005	600v	1A	.08
1N4007	1000v	1A	.15
1N4148	75v	10mA	.05
1N753A	6.2v	z	.25
1N758A	10v	z	.25
1N759A	12v	z	.25
1N4733	5.1v	z	.25
1N5243	13v	z	.25
1N5244B	14v	z	.25
1N5245B	15v	z	.25

**SOCKETS/BRIDGES**

8-pin	pcb	.25	ww	.45
14-pin	pcb	.25	ww	.40
16-pin	pcb	.25	ww	.40
18-pin	pcb	.25	ww	.75
22-pin	pcb	.45	ww	1.25
24-pin	pcb	.35	ww	1.10
28-pin	pcb	.35	ww	1.45
40-pin	pcb	.50	ww	1.25
Molex pins	.01	To-3 Sockets		.45
2 Amp Bridge		100-prv		1.20
25 Amp Bridge		200-prv		1.95

**TRANSISTORS, LEDS, etc.**

2N2222	NPN	(Plastic .10)	.15
2N2907	PNP		.15
2N3906	PNP		.10
2N3054	NPN		.35
2N3055	NPN	15A 60v	.50
T1P125	PNP	Darlington	.35
LED Green, Red, Clear			.15
D.L.747		7 seg 5/8" high com-anode	1.95
XAN72		7 seg com-anode	1.50
FND 359		Red 7 seg com-cathode	1.25

**C MOS**

4000	.15
4001	.20
4002	.20
4004	3.95
4006	1.20
4007	.35
4008	.95
4009	.30
4010	.45
4011	.20
4012	.20
4013	.40
4014	1.10
4015	.95
4016	.35
4017	1.10
4018	1.10
4019	.60
4020	.85
4021	1.35
4022	.95
4023	.25
4024	.75
4025	.35
4026	1.95
4027	.50
4028	.95
4030	.35
4033	1.50
4034	2.45
4035	1.25
4040	1.35
4041	.69
4042	.95
4043	.95
4044	.95
4046	1.75
4049	.70
4050	.50
4066	.95
4069	.40
4071	.35
4081	.70
4082	.45

7400	.15
7401	.15
7402	.20
7403	.20
7404	.15
7405	.25
7406	.35
7407	.55
7408	.25
7409	.15
7410	.10
7411	.25
7412	.30
7413	.45
7414	1.10
7416	.25
7417	.40
7420	.15
7426	.30
7427	.45
7430	.15
7432	.30
7437	.35
7438	.35
7440	.25
7441	1.15
7442	.45
7443	.85
7444	.45
7445	.65
7446	.95
7447	.95
7448	.70
7450	.25
7451	.25
7453	.20
7454	.25
7460	.40
7470	.45
7472	.40

7473	.25
7474	.35
7475	.35
7476	.30
7480	.55
7481	.75
7483	.95
7485	.95
7486	.30
7489	1.35
7490	.55
7491	.95
7492	.95
7493	.40
7494	1.25
7495	.60
7496	.80
74100	1.85
74107	.35
74121	.35
74122	.55
74123	.55
74125	.45
74126	.35
74132	1.35
74141	1.00
74150	.85
74151	.75
74153	.95
74154	1.05
74156	.95
74157	.65
74161	.85
74163	.95
74164	.60
74165	1.50
74166	1.35
74175	.80

**- T T L -**

74176	1.25
74180	.85
74181	2.25
74182	.95
74190	1.75
74191	1.35
74192	1.65
74193	.85
74194	1.25
74195	.95
74196	1.25
74197	1.25
74198	2.35
74221	1.00
74367	.85
75108A	.35
75110	.35
75491	.50
75492	.50
74H00	.25
74H01	.25
74H04	.25
74H05	.25
74H08	.35
74H10	.35
74H11	.25
74H15	.30
74H20	.30
74H21	.25
74H22	.40
74H30	.25
74H40	.25
74H50	.25
74H51	.25
74H52	.15
74H53J	.25
74H55	.25

74H72	.55
74H101	.75
74H103	.75
74H106	.95
74L00	.35
74L02	.35
74L03	.30
74L04	.35
74L10	.35
74L20	.35
74L30	.45
74L47	1.95
74L51	.45
74L55	.65
74L72	.45
74L73	.40
74L74	.45
74L75	.55
74L93	.55
74L123	.55
74S00	.55
74S02	.55
74S03	.30
74S04	.35
74S05	.35
74S08	.35
74S10	.35
74S11	.35
74S20	.35
74S40	.25
74S50	.25
74S51	.45
74S64	.25
74S74	.40
74S112	.90
74S114	1.30

74S133	.45
74S140	.75
74S151	.35
74S153	.35
74S157	.80
74S158	.35
74S194	1.05
74S257 (8123)	.25
74LS00	.35
74LS01	.35
74LS02	.35
74LS04	.35
74LS05	.45
74LS08	.35
74LS09	.35
74LS10	.35
74LS11	.35
74LS20	.35
74LS21	.25
74LS22	.25
74LS32	.40
74LS37	.35
74LS40	.45
74LS42	1.10
74LS51	.50
74LS74	.65
74LS86	.65
74LS90	.95
74LS93	.95
74LS107	.85
74LS123	1.00
74LS151	.95
74LS153	1.20
74LS157	.85
74LS164	1.90
74LS367	.85
74LS368	.85

**LINEARS, REGULATORS, etc.**

8266	.35
MCT2	.95
8038	3.95
LM201	.75
LM301	.25
LM308 (Mini)	.75
LM309H	.65
LM309K (340K-5)	.85
LM310	1.15
LM311D (Mini)	.75
LM318 (Mini)	.65

LM320K5 (7905)	1.65
LM320K12	1.65
LM320T5	1.65
LM320T12	1.65
LM320T15	1.65
LM339	.95
7805 (340T5)	.95
LM340T12	1.00
LM340T15	1.00
LM340T18	1.00

LM340T24	.95
LM340K12	2.15
LM340K15	1.25
LM340K18	1.25
LM340K24	.95
LM373	2.95
LM380	.95
LM709 (8,14 PIN)	.25
LM711	.45

LM723	.50
LM725	1.75
LM739	1.50
LM741 (8-14)	.25
LM747	1.10
LM1307	1.25
LM1458	.95
LM3900	.50
LM75451	.65
NE555	.50
NE556	.95
NE565	.95
NE566	1.75
NE567	1.35

**9000 SERIES**

9301	.85
9309	.35
9322	.85
95H03	.55
9601	.75
9602	.50

**MEMORY CLOCKS**

74S188 (8223)	3.00
1702A	6.95
MM5314	3.00
MM5316	3.50
2102-1	1.75
2102L-1	1.95
TR 1602B/	
TMS 6011	6.95
8080AD	15.00
8T13	1.50
8T23	1.50
8T24	2.00
2107B-4	4.95

**INTEGRATED CIRCUITS UNLIMITED**

7889 Clairemont Mesa Boulevard, San Diego, California 92111  
(714) 278-4394 (Calif. Res.)

All orders shipped prepaid

No minimum

Open accounts invited

COD orders accepted

Discounts available at OEM Quantities

California Residents add 6% Sales Tax

All IC's Prime/Guaranteed. All orders shipped same day received.

24 Hour Toll Free Phone 1-800-854-2211

MasterCharge / BankAmericard / AE

**SPECIAL DISCOUNTS**

Total Order	Deduct
\$35 - \$99	5%
\$100 - \$300	10%
\$301 - \$1000	15%
\$1000 - Up	20%

# 2 METER FM

and HF too . . .

## SATELLITE HEADQUARTERS

See Erickson for all of your Oscar communications needs!



Call or Write for Erickson's Deal

- Ameco • ASP • Atlas
- Belden • Bird • CDE
- CES • Collins • Cushcraft
- Dentron • Drake • HAL
- Hy-Gain • Icom • KLM
- Kenwood • Larsen • MFJ
- Midland • Mosley • NPC
- Newtronics • Nye
- Regency • Shure • Swan
- Standard • TPL • Tempo
- Ten-Tec • Wilson • Yaesu



Hours: 9:30-9 Mon. & Thurs.  
9:30-5:30 Tues, Wed. & Fri.  
9-3 Sat.



**E** ERICKSON COMMUNICATIONS  
5935 N. Milwaukee Ave.  
Chicago, IL 60646  
(312) 631-5181

## Ham Radio Humor

by R. W. Johnson, W6MUR

The first of its kind! A collection of limericks, poems, famous advertisements, jokes and one liners, prose and miscellany both reprints and originals — all which an element of humor you're sure to enjoy. Round out your ham library with this light-hearted book!

Order RWJ-HU

Just \$4.95



Greenville, NH 03048



Enclosed is \$4.95 — send me a copy of Ham Radio Humor.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE \_\_\_\_\_

ZIP \_\_\_\_\_

# Move Ahead at Microwave Speed...

We're Microwave Associates, Inc., a brisk pace-setter in the rapidly expanding telecommunications field. With a growth rate of some 35% and sales in excess of \$60,000,000, we're moving ahead dramatically. Right now our Communication Equipment Group — a select and respected team — needs several professionals with the capability to keep pace with us.

## R-F Development Engineer

You'll develop solid state microwave sources and design microwave transistor amplifiers and varactor multipliers. A minimum of 5 years design experience in the development of VHF through microwave utilizing transistors and varactor type sources, plus B.S.E.E. or equivalent is required.

## R-F Technician

You will be assisting in the development of various circuits ranging from low frequency of UHF region. An Associates Degree or equivalent plus 3 years related experience is required.

## Electronic Technician

An Associates Degree or equivalent is necessary. Duties include the development of power supplies, logic circuitry, analog and digital controls and logic equipment.

In addition, to the above positions, we also have openings for experienced P.C. Board and Mechanical Drafts Persons.

If you are interested in moving ahead in one of the fastest-growing areas of technology, please call or send resume—including salary requirements and indicating your area of interest—to Martha Hoo, (617) 272-3000 ext. 886.

Microwave Associates, Inc. offers excellent salaries and company benefits, including our new Employee Stock Ownership Plan, and a firm commitment to promote from within.



# MICROWAVE ASSOCIATES, INC.

COMMUNICATIONS EQUIPMENT GROUP

Third Avenue, Burlington, Massachusetts 01803

An Equal Opportunity Employer

# NEW

## Frequency Counter

### \$79<sup>95</sup> kit



UTILIZES NEW MOS-LSI CIRCUITRY

You've requested it, and now it's here! The CT-50 frequency counter kit has more features than counters selling for twice the price. Measuring frequency is now as easy as pushing a button, the CT-50 will automatically place the decimal point in all modes, giving you quick, reliable readings. Want to use the CT-50 mobile? No problem, it runs equally as well on 12 V dc as it does on 110 V ac. Want super accuracy? The CT-50 uses the popular TV color burst freq. of 3.579545 MHz for time base. Tap off a color TV with our adapter and get ultra accuracy — .001 ppm! The CT-50 offers professional quality at the unheard of price of \$79.95. Order yours today!

- CT-50, 60 MHz counter kit ..... \$79.95
- CT-50 WT, 60 MHz counter, wired and tested ..... 159.95
- CT-600, 600 MHz prescaler option for CT-50, add ..... 29.95

#### SPECIFICATIONS

- Sensitivity: less than 25 mv.
- Frequency range: 5 Hz to 60 MHz, typically 65 MHz
- Gate time: 1 second, 1/10 second, with automatic decimal point positioning on both direct and prescale
- Display: 8 digit red LED .4" height
- Accuracy: 10 ppm, .001 ppm with TV time base!
- Input: BNC, 1 megohm direct, 50 Ohm with prescale option
- Power: 110 V ac 5 Watts or 12 V dc @ 1 Amp
- Size: Approx. 6" x 4" x 2", high quality aluminum case
- Color burst adapter for .001 ppm accuracy available in 6 weeks.
- CB-1, kit ..... \$14.95



#### CLOCK KIT

##### 6 digit 12/24 hour

Want a clock that looks good enough for your living room? Forget the competitor's kludges and try one of ours! Features: jumbo .4" digits, Polaroid lens filter, extruded aluminum case available in 5 colors, quality PC boards and super instructions. All parts are included, no extras to buy. Fully guaranteed. One to two hour assembly time. Colors: silver, gold, black, bronze, blue (specify).

- Clock kit, DC-5 ..... \$22.95
- Alarm clock, DC-8, 12 hr only ..... 24.95
- Mobile clock, DC-7 ..... 25.95
- Clock kit with 10 min ID timer, DC-10 ..... 25.95
- Assembled and tested clocks available, add \$10.00

#### VIDEO TERMINAL KIT \$149.95

A compact 5 x 10 inch PC card that requires only an ASCII keyboard and a TV set to become a complete interactive terminal for connection to your microprocessor asynchronous interface. Its many features are single 5 volt supply, crystal controlled sync and baud rates (up to 9600 baud), 2 pages of 32 characters by 16 lines, read to and from memory, computer and keyboard operated cursor and page control, parity error display and control, power on initialization, full 64 character ASCII display, block type set thru cursor. Keyboard/computer control backspace, forward space, line feeds, rec. line feeds, home, returns cursor. Also clears page, clears to end of line, sets page 1 or 2, reads from or to memory. The card requires 5 volts at approx. 900 ma and outputs standard 75 ohm composite video.

- TH3216 Kit ..... \$149.95
- TH3216, Assembled and Tested ..... 239.95
- VD-1, Video to RF Modulator Kit ..... 6.95

#### CAR CLOCK KIT \$27.95



- 12/24 Hour 12 Volt AC or DC
- High Accuracy (1 minute/month)
- 6 jumbo .4" LED readouts
- Easy, no polarity hookup
- Display blanks with ignition
- Case: mounting bracket included
- Super instructions
- Complete Kit, DC-11 ..... \$27.95

#### AUTO DIMMER \$2.50

Automatically adjusts display brightness according to ambient light level. For DC-11 Car Clock.

## MINI-KITS

#### STONE DECODER KIT

A complete tone decoder on a single PC Board. Features: 400-5000 Hz adjustable frequency range, voltage regulation, 567 IC. Useful for touch-tone decoding, tone burst detection, FSK demod, signaling, and many other uses. Use 7 for 12 button touch-tone decoding. Runs on 5 to 12 volts.



- Complete Kit, TD-1 ..... \$4.95

#### SUPER-SNOOP AMPLIFIER

A super-sensitive amplifier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or as a general purpose test amplifier. Full 2 watts of output, runs on 6 to 12 volts, uses any type of mike. Requires 8-45 ohm speaker.

- Complete Kit, BN-9 ..... \$4.95

#### FM WIRELESS MIKE KIT

Transmit up to 300' to any FM broadcast radio, uses any type of mike. Runs on 3 to 9 V. Type FM-2 has added super sensitive mike preamp.

- FM-1 ..... \$2.95
- FM-2 ..... \$4.95

#### COLOR ORGAN/MUSIC LIGHTS

See music come alive! 3 different lights flicker with music or voice. One light for lows, one for the mid-range and one for the highs. Each channel individually adjustable, and drives up to 300 watts. Great for parties, band music, nite clubs and more.

- Complete Kit, ML-1 ..... \$7.95

#### LED BLINKY KIT

A great attention getter which alternately flashes 2 Jumbo LEDs. Use for name badges, buttons, or warning type panel lights. Runs on 3 to 9 volts.

- Complete Kit ..... \$2.95

#### POWER SUPPLY KIT

Complete triple regulated power supply provides variable 1.5 volts at 200 mA and +5 volts at 1 Amp. 50 mV load regulation good filtering and small size. Kit less transformers. Requires 6-8 V at 1 Amp and 18 to 30 VCT.



- Complete Kit, PS-3LT ..... \$6.95

#### SIREN KIT

Produces upward and downward wail characteristic of police siren. 5 watts audio output, runs on 3-9 volts, uses 8-45 ohm speaker.

- Complete Kit, SM-3 ..... \$2.95

#### DECADE COUNTER PARTS

Includes: 7490A, 7475, 7447, LED readout, current limit resistors, and instructions on an easy to build low cost frequency counter.

- Kit of parts, DCU-1 ..... \$3.50

#### CHEAP CLOCK KIT \$8.95

- DC-4 Features: Does not include board or transformer
- PC Board \$2.95
- Transformer \$1.49

#### 600 MHz PRESCALER



Extend the range of your counter to 600 MHz. Works with all counters. Less than 150 mv sensitivity. Specify 110 or 1100. Wired, tested, PS-1B ..... \$59.95

#### 30 watt 2 meter Power Amp

The famous RE class C power amp now available mail order! Four Watts in for 30 Watts out, 2 in for 15 out, 1 in for 8 out, incredible value, complete with all parts, instructions and details on T-R relay. Case not included.

- Complete Kit, PA-1 ..... \$22.95

#### CALENDAR ALARM CLOCK

Has every feature one could ever ask for. Kit includes everything except case, build it into wall, station or even car!

- 6 Digits, 5" High LED
- Calendar shows mo./day
- True 24 Hour Alarm
- Battery back-up with built-in chip-time base
- Complete Kit, less case, DC-9 ..... \$34.95

LINEAR			REGULATOR		TRANSISTORS		
5314 Clock	\$2.95	555	\$.50	78MG	\$1.49	MRF-238 30W VHF	\$11.95
74S00	.35	556	.75	309k	.89	NPN 2N3904 type	10/\$1.00
74S112	.75	566	1.49	309H	.99	PNP 2N3906 type	10/\$1.00
7447	.79	567	1.49	340K-12	.99	NPN Power Tab 40W	3/\$1.00
7473	.35	1458	.50	7805	.89	PNP Power Tab 40W	3/\$1.00
7475	.50	LED DRIVER		7812	.89	FET MPF 102 type	3/\$2.00
7490A	.55	75491	.50	7815	.89	UJT 2N2646 type	3/\$2.00
74143	3.50	75492	.50	7818	.89	2N3055 NPN Power	.75

- DIODES: 1KV, 2.5A ..... 5/\$1.00
- 100V, 1A ..... 10/\$1.00
- 1N914A type ..... 50/\$2.00

#### LED DISPLAYS

- FND 359 ..... .75
- FND 510 ..... 1.25
- DL 707 ..... 1.25
- HP 7730 ..... 1.25



Red Polaroid Filter ... 4.25" X 1.125" ... \$9

#### 741 OP-AMP SPECIAL

Factory prime mini dip with both Xerox and 741 part numbers

- 10 for \$2.00

#### SOCKETS

- 14 PIN 5/\$1.00
- 16 PIN 5/\$1.00
- 24 PIN 2/\$1.00
- 40 PIN 3/\$2.00

#### FERRITE BEADS

- with info and specs 15/\$1.00
- 6 hole Balun Beads 5/\$1.00

# ramsey electronics

P.O. Box 4072 Rochester NY 14610

(716) 271-6487

TELEPHONE ORDERS WELCOME



Satisfaction guaranteed or money refunded. C.O.D., add \$1.00. Orders under \$10.00 add \$.75. NY residents add 7% tax.



 <p><b>T-TONE PAD HOUSING</b> BLACK ONLY \$2.75</p>	<p><b>CRYSTAL OSCILLATOR</b> 4 MHz OSC. DIP SQU.WAVE Vcc 5V \$3.50</p>	<p><b>MOLEX PINS</b> 200 EACH \$1.95 1000 EACH \$7.95</p>	<p><b>115 AC PLUG WITH ON/OFF SW &amp; GND.</b> 75¢</p>	<p><b>DANGER HIGH VOLTAGE diode</b> 12,000 PIV 500 MA IF 60 AMP SURG. \$3.50</p>	<p><b>ALPHA NUMERIC 5 X 7 DOT MATRIX TIL-305</b> same as MAN-2, DL 57 \$3.50</p>	<p><b>50 ohm COAX</b> RG 174 U 50 FT. \$2.75 PHOTO CELL 2.7K WITH 1:10,000 T0-5 PACKAGE \$1.95</p>
<p><b>NICADS</b> 4 'AA' SIZE CELL 500 MILL. AT 5 V 63.95</p>	<p><b>HEAT SHRINK</b> ASSORTED SIZE 10 FOOT BUNDLE 95¢</p>	<p><b>TRANSFORMER</b> 12.8 VAC 4 AMPS CENTER TAP \$5.95</p>	<p><b>100 PIN EDGE CONNECTOR</b> IMSAI/ALTAIR S-100 BUSS -125 CENTERS \$3.95</p>	<p>SO-239 65¢ PL-259 65¢ 10/\$6.00 MIX/MATCH</p>	<p><b>CIGARETTE LIGHTER PLUG</b> 79¢</p>	<p><b>SPECTRA STRIP</b> 12 CONDUCTOR 22AWG 5 FOOT \$2.50</p>
<p><b>PROTECT YOUR EQUIPMENT</b> INSTALL A <b>THERMAL SWITCH</b> CLOSES AT 240°F OPENS AT 200°F \$3.25</p>	<p><b>Variable Power Supply</b> *12-28V ADJUSTABLE POWER SUPPLY AT 28V 250MA THERMALLY PROTECTED. *5-12V ADJUSTABLE POWER SUPPLY AT 12V 500MA ADJUSTABLE POT. <b>ALL PARTS INCLUDED</b> *TRANSFORMER *PC BOARD *POT &amp; RESISTOR *HEAT SINK *OSC. SUPPRESSION CAP. *DIODES *1000UF CAP. *INSTRUCTIONS *REGULATOR 7805 OR 7812 *HARDWARE PS1 5-12V \$5.95 PS2 12-28V \$5.95</p>	<p><b>DIODES</b> 1N4001 16/1.00 1N4002 14/1.00 1N4003 12/1.00 1N4007 10/1.00 HM*2a 1k 6/1.00 5SA05 5a 50piv 4/1.00</p>	<p><b>COMPUTER GRADES</b> 450 UF 75V \$1.50 6,000 UF 10V 1.25 10,000 UF 55V 2.95 39,000 UF 45V 3.25 90,000 UF 20V 2.95 150,000 UF 10V 2.95 240,000 UF 10V 3.95</p>	<p><b>JOY</b> X-Y FUNCTION 10K LINEAR POTS \$3.95</p>		
<p>UG-175 25¢ BNC-F/UHF-M \$2.25 "N"-F/BNC-M \$2.75 UHF-F/UHF-F \$1.25 BNC-F/BNC-F \$3.25</p>	<p>THIS USEFUL PIN WILL FIT OVER ANY .025 SQUARE OR ROUND PIN. SOLDERED OR CRIMPED. MANY USES OPTION CHANGES, ADDRESSING, LOGIC BOARDS, OR BREADBOARDS. 100 for \$1.00</p>	<p><b>1N914</b> NEW HOUSE MARKED 1N914 100 for \$2.95</p>	<p><b>.1 ohm FIVE WATT RESISTOR</b> 5/\$1.00</p>	<p><b>SPECIAL MONTHLY SPECIAL</b> WIREWRAP IC SOCKETS 14 PIN \$.35 EACH. 16 PIN .38 EACH. 24 PIN .75 EACH. 100' SPOOLS, 30 AWG. WIRE. LT. GREEN, DK. GREEN, RED. \$2.50</p>		
<p><i>Marlin P. Jones and Associates</i></p>		<p>P.O. BOX 9023 DEPT HR RIVIERA BEACH, FLA. 33404 305-848-8236</p>	<p>FLA. RES. ADD 4% SALES TAX PLEASE ADD \$1.00 FOR ORDERS UNDER \$10.00. POST. &amp; HAND MC &amp; BA ACCEPTED.</p>	<p>SEE YOU AT FT. LAUDERDALE HAMFEST. PANAMERICAN HAM EXPOSITION JAMBOREE. OCTOBER 29-30, 1977</p>		

## 1977 ARRL FLORIDA GULF COAST CONVENTION

Clearwater Beach, November 19 and 20

Sponsored By

Florida Gulf Coast Amateur Radio Council



Only **REAL** Convention in the Southeast with Exhibitors, Flea Mkt., Technical Sessions, FCC Exams, Forums, QCWA, AWA, SMIRK, 10-10 Club, etc. Full Ladies activities plus hotel facilities on the Gulf.

Ray Spence, FCC Chief Eng., Bob and Ellen White, of ARRL as guest speakers at Forums. Saturday Eve Banquet with IARU President, Noel Eaton, VE3CJ, as guest speaker.

Tickets: Adv'd. \$3 Single; \$5 Family + 2 Bonus tickets. Banquet: \$9 (Reserve early)

Full Info and reservation for Sheraton Hotel contact:  
F.G.C.A.R.C. Convention  
P. O. Box 157  
Clearwater, Florida 33517

## RADIO WORLD

CENTRAL NEW YORK'S FASTEST GROWING HAM DEALER



FT-101E

TRITON IV

Featuring - Yaesu, Atlas, Dentrone, Ten-Tec, Swan, Regency, Standard, Tempo, KLM, Hy-Gain, Mosley, Larsen, Midland, Wilson. We service everything we sell! Write or call for quote. **YOU WON'T BE DISAPPOINTED.**

We are just a few minutes off the NYS Thruway (I-90) - Exit 32.

## RADIO WORLD

ONEIDA COUNTY AIRPORT  
TERMINAL BUILDING  
ORISKANY, NY 13424  
315-337-2622

Warren  
K2IXN

Joe  
WB2GJR

Plug it in like a key and send perfectly timed Morse code as easily as typing a letter. Sidetone and buffer register make it simple to send at the speed you select.



# ATRONICS

BOX 77, ESCONDIDO, CA 92025

(714) 745-1971

Available directly from the factory for only \$225 plus post-age & handling. Mastercharge or BankAmericard accepted. Call or write to order or request complete specifications and options.



# NEW for 220 MHz

FROM **Vhf engineering**



## Synthesizer 220

Compatible with virtually all 220 transceivers; Clegg, Midland, Cobra, etc. . . .

The Synthesizer 220 is a 1 $\frac{1}{4}$  meter frequency synthesizer. Frequency is adjustable in 5 KHz steps from 220.00 MHz to 225.00 MHz with its digital readout thumb wheel switching. Transmit offsets are digitally programmed on a diode matrix, and can range from 100 KHz to 10 MHz. No additional components are necessary!

### FEATURES

- T<sup>2</sup>L Logic
- Maximum offset versatility — easily programmed to any IF and transmitter offset between 100 KHz and 30 MHz in even 100 KHz increments.
- Simple jumper wire change enables use on rigs with 18, 9, 6 MHz transmit crystals.
- All frequencies locked to one master crystal oscillator.
- 2 pole output filter on receive line.
- Virtually no measurable difference in spurious outputs between crystal or SYN 220.
- Lockup time typically 150 milliseconds.
- Easily interfaced to most rigs.

### SPECIFICATIONS

- Frequency: 220 — 225 MHz
- Transmit offsets: Simplex, +1.6 MHz, -1.6 MHz plus 3 additional field programmable offsets.
- Output: 3 volts to a 50 $\Omega$  load.
- Input voltage: 11 — 18 VDC at .900 amps.
- Size: 8" long x 5 $\frac{1}{2}$ " wide x 2 $\frac{1}{4}$ " high  
20.32CM x 13.97CM x 5.715CM
- Complete kit including all electronics, crystal, thumb wheel switch, cabinet, etc.
- Shipping weight 2 lb. 4 oz.

**KIT \$169.95 — Wired & Tested \$239.95**

Prices and specifications are subject to change without notice. Export prices are slightly higher.

IN AREAS NOT SERVED BY A VHF ENGINEERING DEALER, SEND THIS ORDER FORM.

THE WORLD'S MOST COMPLETE LINE OF  
VHF - FM KITS AND EQUIPMENT

**Vhf engineering**

DIVISION OF BROWNIAN ELECTRONICS CORP.

BOX H / 320 WATER ST. / BINGHAMTON, NY 13901  
Phone 607-723-9574



### ORDER FORM

Item	Price Each	Quantity	Total Price
Synthesizer 220 Kit	\$169.95		
Synthesizer 220 Wired & Tested	\$239.95		

Name \_\_\_\_\_ Total \_\_\_\_\_  
 Address \_\_\_\_\_ Shipping \_\_\_\_\_  
 City \_\_\_\_\_ NYS Resident \_\_\_\_\_  
 State \_\_\_\_\_ Zip \_\_\_\_\_ Sales Tax \_\_\_\_\_  
 Master Charge or BankAmericard No. \_\_\_\_\_ Total Enclosed \_\_\_\_\_  
 Bank No. \_\_\_\_\_ Expiration Date \_\_\_\_\_



*Ham Radio's guide to help you find your local*

### *Alabama*

**LONG'S ELECTRONICS**  
3521 TENTH AVE. NORTH  
BIRMINGHAM, AL 35234  
800-633-3410  
Call us Toll Free to place your order

### *Arizona*

**MASTERS COMMUNICATIONS**  
7025 N. 57th DRIVE  
GLENDALE, AZ 85301  
602-939-8356  
Rohn tower distributor, Atlas,  
Icom, Tempo, HyGain & service.

**POWER COMMUNICATIONS**  
6012 NORTH 27th AVE.  
PHOENIX, AZ 85017  
602-242-8990  
Arizona's #1 Ham Store.

### *California*

**C & A ELECTRONICS**  
2529 EAST CARSON ST.  
P. O. BOX 5232  
CARSON, CA 90745  
213-834-5868  
Not the biggest, but the best —  
since 1962.

**CARSON ELECTRONICS**  
12010 EAST CARSON ST.  
HAWAIIAN GARDENS, CA 90716  
213-421-3786  
Dealing exclusively in ICOM  
communications equipment.

**COMMUNICATIONS CENTER**  
705 AMADOR STREET  
VALLEJO, CA 94590  
707-642-7223  
Who else has a Spectrum  
Analyzer?

**HAM RADIO OUTLET**  
999 HOWARD AVENUE  
BURLINGAME, CA 94010  
415-342-5757  
Visit our stores in Van Nuys  
and Anaheim.

**QUEMENT ELECTRONICS**  
1000 SO. BASCOM AVENUE  
SAN JOSE, CA 95128  
408-998-5900  
Serving the world's Radio Amateurs  
since 1933.

**TOWER ELECTRONICS CORP.**  
24001 ALICIA PARKWAY  
MISSION VIEJO, CA 92675  
714-768-8900  
Authorized Yaesu Sales & Service.  
Mail orders welcome.

### *Colorado*

**C W ELECTRONIC SALES CO.**  
1401 BLAKE ST.  
DENVER, CO 80202  
303-573-1386  
Rocky Mountain area's complete  
ham radio distributor.

**MILE-HI COMMUNICATIONS, INC.**  
1970 SOUTH NAVAJO  
DENVER, CO 80223  
303-936-7108  
Rocky Mountain's newest  
ham store. Lee Tingle KØLT.

### *Florida*

**AGL ELECTRONICS, INC.**  
1800-B DREW ST.  
CLEARWATER, FL 33515  
813-461-HAMS  
West Coast's only full service  
Amateur Radio Store.

**CENTRAL EQUIPMENT CO.**  
18451 W. DIXIE HIGHWAY  
NORTH MIAMI BEACH, FL. 33160  
305-932-1818  
Specializing in Amateur, CB  
& Marine Equipment.

**RAY'S AMATEUR RADIO**  
1590 US HIGHWAY 19 SO.  
CLEARWATER, FL 33516  
813-535-1416  
West coast's only dealer:  
Drake, Icom, Cushcraft, Hustler.

### *Illinois*

**ERICKSON COMMUNICATIONS, INC.**  
5935 NORTH MILWAUKEE AVE.  
CHICAGO, IL 60646  
312-631-5181  
Hours: 9:30-9 Mon. & Thurs. 9:30-5  
Tues., Wed., Fri. 9-3 Sat.

**KLAUS RADIO, INC.**  
8400 NORTH PIONEER PARKWAY  
PEORIA, IL 61614  
309-691-4840  
Let us quote your Amateur needs.

**SPECTRONICS, INC.**  
1009 GARFIELD STREET  
OAK PARK, IL 60304  
312-848-6777  
Chicagoland's Amateur Radio  
leader.

### *Indiana*

**HOOSIER ELECTRONICS**  
P. O. BOX 2001  
TERRE HAUTE, IN 47802  
812-238-1456  
Ham Headquarters of the Midwest.  
Store in Meadow Shopping Center.

### *Iowa*

**BOB SMITH ELECTRONICS**  
12 SOUTH 21ST STREET  
FT. DODGE, IA 50501  
515-576-3886  
For an EZ deal.

### *Kansas*

**ASSOCIATED RADIO**  
8012 CONSER P.O.B. 4327  
OVERLAND PARK, KS 66204  
913-381-5901  
Amateur Radio's Top Dealer.  
Buy — Sell — Trade.

### *Kentucky*

**COHOON AMATEUR SUPPLY**  
HIGHWAY 475  
TRENTON, KY 42286  
502-886-4535  
Yaesu, Ten-Tec, Tempo, Dentrone.  
Our service is the BEST.

### *Maryland*

**COMM CENTER, INC.**  
9624 FT. MEADE ROAD  
LAUREL PLAZA RT. 198  
LAUREL, MD 20810  
301-792-0600  
New & Used Amateur Equipment.  
Wilson, Ten-Tec, R. L. Drake, Tempo

**PROFESSIONAL  
ELECTRONICS CO., INC.**  
1710 JOAN AVENUE  
BALTIMORE, MD 21234  
301-661-2123  
A professional place for amateurs.  
Service-sales-design.

### *Massachusetts*

**TUFTS RADIO ELECTRONICS**  
386 MAIN STREET  
MEDFORD, MA 02155  
617-395-8280  
New England's friendliest  
ham store.

*Dealers - You should be here too! Contact Ham Radio today for complete details.*

# Amateur Radio Dealer

## Michigan

**RADIO SUPPLY & ENGINEERING**  
1207 WEST 14 MILE ROAD  
CLAWSON, MI 48017  
313-435-5660  
10001 Chalmers, Detroit, MI  
48213, 313-371-9050.

## Minnesota

**ELECTRONIC CENTER, INC.**  
127 THIRD AVENUE NORTH  
MINNEAPOLIS, MN 55401  
612-371-5240  
ECI is still your best buy.

## Missouri

**HAM RADIO CENTER, INC.**  
8340-42 OLIVE BLVD.  
ST. LOUIS, MO 63132  
800-325-3636  
See Our Ads  
In This Issue.

**MIDCOM ELECTRONICS, INC.**  
2506 SO. BRENTWOOD BLVD.  
ST. LOUIS, MO 63144  
314-961-9990  
At Midcom you can try before you  
buy!

## Nebraska

**COMMUNICATIONS CENTER, INC.**  
2226 NORTH 48 ST.  
LINCOLN, NE 68504  
800-228-4097  
Yaesu, Drake, Tempo, Swan,  
HyGain - call Toll Free

## New Hampshire

**EVANS RADIO, INC.**  
BOX 893, RT. 3A BOW JUNCTION  
CONCORD, NH 03301  
603-224-9961  
Icom, Dentron & Yaesu dealer.  
We service what we sell.

## New Jersey

**ATKINSON & SMITH, INC.**  
17 LEWIS ST.  
EATONTOWN, NJ 07724  
201-542-2447  
Ham supplies since "55".

## New Mexico

**ELECTRONIC MODULE**  
601 N. TURNER  
HOBBS, NM 88240  
505-397-3012  
Yaesu, Kenwood, Swan, Dentron,  
Tempo, Atlas, Wilson, Cushcraft

## New York

**ADIRONDACK RADIO SUPPLY, INC.**  
185 W. MAIN STREET  
AMSTERDAM, NY 12010  
518-842-8350  
Yaesu dealer for the Northeast.

**CFP COMMUNICATIONS**  
211 NORTH MAIN STREET  
HORSEHEADS, NY 12010  
607-739-0187  
Jim Beckett, WA2KTJ, Manager  
Bryant Hozempa, WB2LVW, Sales

**GRAND CENTRAL RADIO**  
124 EAST 44 STREET  
NEW YORK, NY 10017  
212-682-3869  
Drake, Atlas, Ten-Tec, Midland,  
Hy-Gain, Mosley in stock

**HARRISON**  
"HAM HEADQUARTERS, USA"  
ROUTE 110 & SMITH STREET  
FARMINGDALE, L. I., N. Y. 11735  
516-293-7990  
Since 1925 . . . Service, Satisfaction,  
Savings. Try Us!

**RADIO WORLD**  
ONEIDA COUNTY AIRPORT  
TERMINAL BLDG.  
ORISKANY, NY 13424  
315-337-2622  
New & used ham equipment.  
See Warren K2IXN or Joe WB2GJR

## Ohio

**UNIVERSAL SERVICE**  
114 N. THIRD STREET  
COLUMBUS, OH 43215  
614-221-2335  
Give U.S. a try when ready to buy.

## Oklahoma

**RADIO STORE, INC.**  
2102 SOUTHWEST 59th ST.  
(AT 59th & S. PENNSYLVANIA)  
OKLAHOMA CITY, OK 73119  
405-682-2929  
New and used equipment —  
parts and supply.

## Pennsylvania

**ELECTRONIC EXCHANGE**  
136 N. MAIN STREET  
SOUDERTON, PA 18964  
215-723-1200  
New & Used Amateur Radio  
sales and service.

**"HAM" BUERGER, INC.**  
68 N. YORK ROAD  
WILLOW GROVE, PA 19090  
215-659-5900  
Communications specialists.  
Sales and service.

**HAMTRONICS, DIV. OF  
TREVISE ELECT.**  
4033 BROWNSVILLE ROAD  
TREVISE, PA 19047  
215-357-1400  
Same location for 25 years.

## South Carolina

**AMATEUR RADIO ELECTRONICS**  
100 STATE ST.  
WEST COLUMBIA, SC 29169  
803-796-7957  
Featuring Swan Equipment

## Tennessee

**GERMANTOWN AMATEUR SUPPLY**  
3203 SUMMER AVE.  
MEMPHIS, TN 38112  
800-238-6168  
No monkey business. Call  
Toll Free.

**J-TRON ELECTRONICS**  
505 MEMORIAL BLVD.  
SPRINGFIELD, TN 37172  
615-384-3501  
Ten-Tec dealer — call or  
write for best trade.

## Texas

**AGL ELECTRONICS**  
3068 FOREST LANE, SUITE 309  
DALLAS, TX 75234  
800-527-7418  
Out-of-State, Call our  
Toll-Free Number 800-527-7418

**HARDIN ELECTRONICS**  
5635 E. ROSEDALE  
FT. WORTH, TX 76112  
817-461-9761  
Your Full Line Authorized  
Yaesu Dealer.

## Wisconsin

**AMATEUR  
ELECTRONIC SUPPLY, INC.**  
4828 WEST FOND du LAC AVENUE  
MILWAUKEE, WI 53216  
414-442-4200  
Open Mon & Fri 9-9, Tues, Wed,  
Thurs, 9-5:30, Sat, 9-3.

## Washington

**AMATEUR RADIO SUPPLY CO.**  
6213 13TH AVENUE SOUTH  
SEATTLE, WA 98108  
206-767-3222  
First in Ham Radio in Washington  
Northwest Bird Distributor

## Wyoming

**DENCO COMMUNICATIONS CENTER**  
1728 EAST 2nd STREET  
CASPER, WY 82601  
307-234-9197  
Sales, Service to Wyoming  
and the Northern Rockies.

MICRO-MODULE VHF and UHF CONVERTERS and TRANSVERTERS

Make your selection from the best of top national brands. Choose from dozens of models and a variety of equipment to handle anything from 160 meters to 1296 MHz. Products like the Atlas 350XL. Wilson HT's. Mosley Tri-bander. Clegg FM-DX, FM-76, Mark 3, TT-2. Micro-module VHF and UHF converters and transverters. Repeaters. Power supplies. And much more.

For details on this new supersales service, call toll FREE 800-233-0250, in Pa. call (717) 299-7221 collect. Or visit the new Clegg supersales center, 208 Centerville Road, Lancaster, Pa. 17603.



**NOW! A NEW SUPERSERVICE TO FILL ALL YOUR HAM NEEDS.**

*Clegg*

Advanced technology in action!

MOSLEY TRI-BANDERS POWER SUPPLIES CLEGG FM-DX FM-28 FM-76

**Get the most from your antenna!**



With the Omega-t Antenna Noise Bridge you can test for resonant frequency and impedance... adjust and retest... until your antenna performs at its optimum. Use the Noise Bridge to trim RF lines for best performance, too.

This patented design uses your sensitive receiver as a bridge detector, outperforming more expensive test equipments.

Reduce power loss due to mismatch — now! Get more details or order today.

Model TE7-01... 1-100 MHz range: \$34.95  
Model TE7-02... 1-300 MHz range: \$44.95



P.O. BOX 1395  
RICHARDSON, TEXAS 75080  
TELEPHONE (214) 231-9303

Sold at Amateur Radio Dealers or Direct from Electrospace Systems, Inc.

**MAXI TUNER SOLVES ANTENNA PROBLEMS!**



**THE FINEST ANTENNA TUNER AVAILABLE**

- Presents 50-75 Ohm Resistive Load to Your Transmitter Using Virtually Any Antenna System
- Improved Ultimate Transmatch Circuit Matches Coax, Random Wire and Balanced Antennas
- Continuous 1.7-30 MHz Coverage
- 229-203 Rotary Inductor (28 μH)
- Rugged Cast Aluminum Turns Counter
- Handles 3 KW PEP
- Monimatch SWR Circuit
- Heavy Duty Balun
- Velvet-Smooth 6 to 1 Vernier Tuning
- 0-100 Logging Scale on Capacitors
- Available in Kit Form or Assembled
- One Year Factory Warranty
- Available without SWR for use with your present SWR meter or wattmeter.
- Custom Vacuum Capacitor Designs and Individual Components Available

Call or Write for Pricing, Spec Sheet, and FREE Amateur Market Antenna Tuner Comparison Chart That Tells It Like It Is! Dealer Inquiries Invited.

**RF POWER COMPONENTS**

P. O. Box 11  
Ladysmith, WI 54848  
(715) 532-3971

**IMPROVES ALL SSB & CW STATIONS PR-1000 VARIABLE AUDIO FILTER**



Greatly improves reception and audio selectivity of even the best ham receiver. Easy to operate and quickly connects between any ham receiver, transceiver or SWL receiver and speaker (or headphone). Provides variable selectivity bandpass of 40 Hertz to 3000 Hertz with selectivity skirts a minimum of 80db! Super sharp 70db variable notch rejects nearby CW stations as close as 100 Hertz! Incorporates the latest electronic audio filtering circuitry. Five (5) integrated circuits with self-contained 110 volt AC power supply and one watt audio amplifier. Attractive low profile eggshell white cabinet with walnut-like sides.

PRIME ELECTRONICS, INC. Dept. HR  
221 West Market St. Derby, KS. 67037

- Please send me more information
- Rush me \_\_\_\_\_ PR-1000 Variable Audio Filters @ \$59.95 each plus \$1.50 postage & handling. Check or M.O. enclosed.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Distributor and dealer inquiries invited.

**MILITARY SURPLUS WANTED**

Space buys more and pays more. Highest prices ever on U.S. Military surplus, especially on Collins equipment or parts. We pay freight. Call collect now for our high offer. 201 440-8787. SPACE ELECTRONICS CO. div. of Military Electronics Corp. 35 Ruta Court, S. Hackensack, N.J. 07606

**TEMPO-ONE OWNERS**

**A NEW RIG FOR \$90\***  
More RX gain and selectivity. TX like undistorted kilowatt, extra carrier suppression. Details Holdings, 39/41 Mincing Lane, Blackburn, BB2 2AF, England. Tel. (0254) 59595/6. \*Int. price air postpaid, BankAmericard, Mastercard, check.



**IAMBIC KEYS**



Fully Iambic, both DIT & DAH paddle memories, self completing characters, automatic spacing & weighting, sidetone output, transistorized output that keys grid block or cathode keyed rigs, speed from 5 to 40+ wpm. The Paddles are on a beautiful finished wood base.

Kit \$39.75 with Paddles \$65.00  
Assembled \$56.95 with Paddles \$80.00  
**DAYTRONICS COMPANY** DTR P. O. BOX 426  
12 OAKDALE AVE. SELDEN, N. Y. 11784

# 3 new ones from Ham Radio's Bookstore.

Already a best-seller in Europe!

New English language edition



Profusely illustrated with many diagrams, charts and photographs.

## OSCAR — Amateur Radio Satellites

by Stratis Caramanolis  
The comprehensive book on Amateur satellites. Learn the principles and then examine OSCAR from concept to actual use. A handsome volume.

200 pages, softbound

Order RS-O

**Just \$8.50**

**New 4th Edition!  
Just Released!**


## RADIO DATA REFERENCE BOOK

by T. G. Giles, G4CDY  
& G. R. Jessop, G6JP

A handy reference for both Amateurs and engineers. Completely revised and updated. Over 25% more essential data in a convenient and more useful form.

Hardbound

Order RS-DF **Only \$6.95**

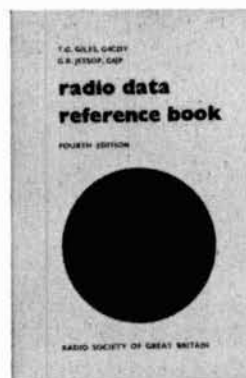

The bible on SSB  
— originally published  
by Collins Radio Company

New softcover edition from Ham Radio!



## AMATEUR SINGLE SIDEBAND

A complete introduction to SSB and its equipment. Covers tests, measurements, and much more. A very readable must for anyone involved with SSB.

Order HR-SSB **Just \$4.95**

Reissued by tremendous popular demand

To Order  
CALL  
Today  
TOLL FREE!  
800-258-5353

or send to:

Ham Radio's Communications Bookstore  
Greenville, NH 03048

- RS-O . . . . \$8.50  
 HR-SSB . . . \$4.95  
 RS-DF . . . . \$6.95

Charge my:

VISA (BankAmericard)

Mastercharge

Acct. # \_\_\_\_\_

Exp. date \_\_\_\_\_ Interbank # \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_



State  
of the art



by  
**K.V.G.**

### CRYSTAL FILTERS and DISCRIMINATORS

#### 9.0 MHz FILTERS

XF9-A	2.5 kHz	SSB TX	\$31.95
XF9-B	2.4 kHz	SSB RX/TX	\$45.45
XF9-C	3.75 kHz	AM	\$48.95
XF9-D	5.0 kHz	AM	\$48.95
XF9-E	12.0 kHz	NBFM	\$48.95
XF9-M	0.5 kHz	CW (4 pole)	\$34.25
XF9-NB	0.5 kHz	CW (8 pole)	\$63.95

Export  
Inquiries  
Invited

Shipping  
\$1.25  
per filter

#### 9.0 MHz CRYSTALS (Hc25/u)

XF900	9000.0 kHz	Carrier	\$4.00
XF901	8998.5 kHz	USB	\$4.00
XF902	9001.5 kHz	LSB	\$4.00
XF903	8999.0 kHz	BFO	\$4.00
F-05	Hc25/u	Socket Chassis	.50
F-06	Hc25/u	Socket P.C. Board	.50

#### ALSO AVAILABLE FROM KVG

10.7 MHz CRYSTAL FILTERS  
OSCILLATOR CRYSTALS 50 kHz TO 150 MHz  
Write for Details

### PRE-SELECTOR FILTERS



3 POLE, INTERDIGITAL  
LOW LOSS 0.15 dB  
420-450 MHz PSf432 \$36.70  
1250-1340 MHz PSf1296  
\$36.70

Shipping \$3.50

### LINEAR AMPLIFIERS

COMPATIBLE WITH OUR LOW  
POWER TRANSVERTERS.

10W DRIVE, 50Ω IN/OUT

EDL432, 50W (ILLUS) \$139.95



EDL432P, INCL. POWER SUPPLY/CABINET \$299.95

EDL144, 100W 2M, IN CABINET, WITH 115V POWER SUPPLY \$299.95

UPS Shipping at Cost

### ANTENNAS (FOB) CONCORD

144-148 MHz

8 OVER 8 J-SLOT + 12.3 dBd D8/2M \$39.95

8 BY 8 VERTICAL POL. D8/2M-VERT. \$48.70

8XY/2M \$34.95



420-450 MHz  
MULTIBEAMS

48 EL. GAIN + 15.7 dBd 70/MBM48 \$44.95

88 EL. GAIN + 18.5 dBd 70/MBM88 \$69.95

1250-1340 MHz

1296 MHz LOOP YAGI

26 LOOPS GAIN + 20 dBi 1296-LY \$54.45

Send 26¢ (2 stamps) for full line catalogue of KVG crystal products and all your VHF & UHF equipment requirements.

**si**

Spectrum  
International, Inc.  
Post Office Box 1084  
Concord, Mass. 01742, USA



GREGORY ELECTRONICS  
The FM Used  
Equipment People.

## 2 METER F.M. SPECIALS

### MOTOROLA T43A SERIES

150 MHz, 12 volt, 30 watts,  
transmitter narrow band with  
dynamotor power supply,  
receiver wide band (Sensicon  
"A" type) with vibrator power  
supply, 15" case, less  
accessories (not bench tested)



W 15"  
H 6"  
D 18"

\$10.00

power and control cable, set \$5.00  
control head (less mike and bracket) \$3.00

### G.E. MA/E33

150 MHz, 6/12 volt, 30 watts, vibrator power  
supply, transmitter narrow band, receiver  
wide band, less accessories and xtal ovens  
(not bench tested)

\$18.00

power and control cable, set \$5.00  
control head (less mike and bracket) \$5.00



## GREGORY ELECTRONICS CORP.

245 Rt. 46, Saddle Brook, N.J. 07662  
Phone: (201) 489-9000

talk  
power  
by **TPL**  
*Econo-line*



- Quality for an Economy Price
- Solid State Construction
- Linear Switch (FM/SSB)
- Broad Band

Model	Input	Output	Typical	Frequency	Price
702	10W-20W	50W-90W	10W in/70W out	143-149MHz	\$149.00
702B	1W- 5W	60W-80W	1W in/70W out	143-149MHz	\$179.00

Now get TPL COMMUNICATIONS quality and reliability at an economy price. The solid state construction, featuring magnetically coupled transistors and a floating ground, gives you an electronically protected amplifier that should last and last.

The Linear Bias Switch allows you to operate on either FM or SSB. The 702 and 702B are exceptionally well suited for 2-meter SSB. Typical power output levels as high as 100W PEP can be achieved with the proper drive.

The broad band frequency range means that your amplifier is immediately ready to use. No tuning is required for the entire 2-meter band and adjacent MARS channels on TPL's new *Econo-line*.

See these great new additions to the TPL COMMUNICATIONS product line at your favorite radio dealer.

**TPL**

Call or write for prices and information on TPL's complete line of amateur and commercial amplifiers.

COMMUNICATIONS INC.


1324 W. 135TH ST., GARDENA, CA 90247 • (213) 538-9814

Canada: A.C. Simmonds & Sons Ltd., 285 Yorkland Blvd., Willowdale, Ontario M2J 1S8  
Export: EMEC Inc., 2350 South 30th Avenue, Hallandale, Fla. 33009
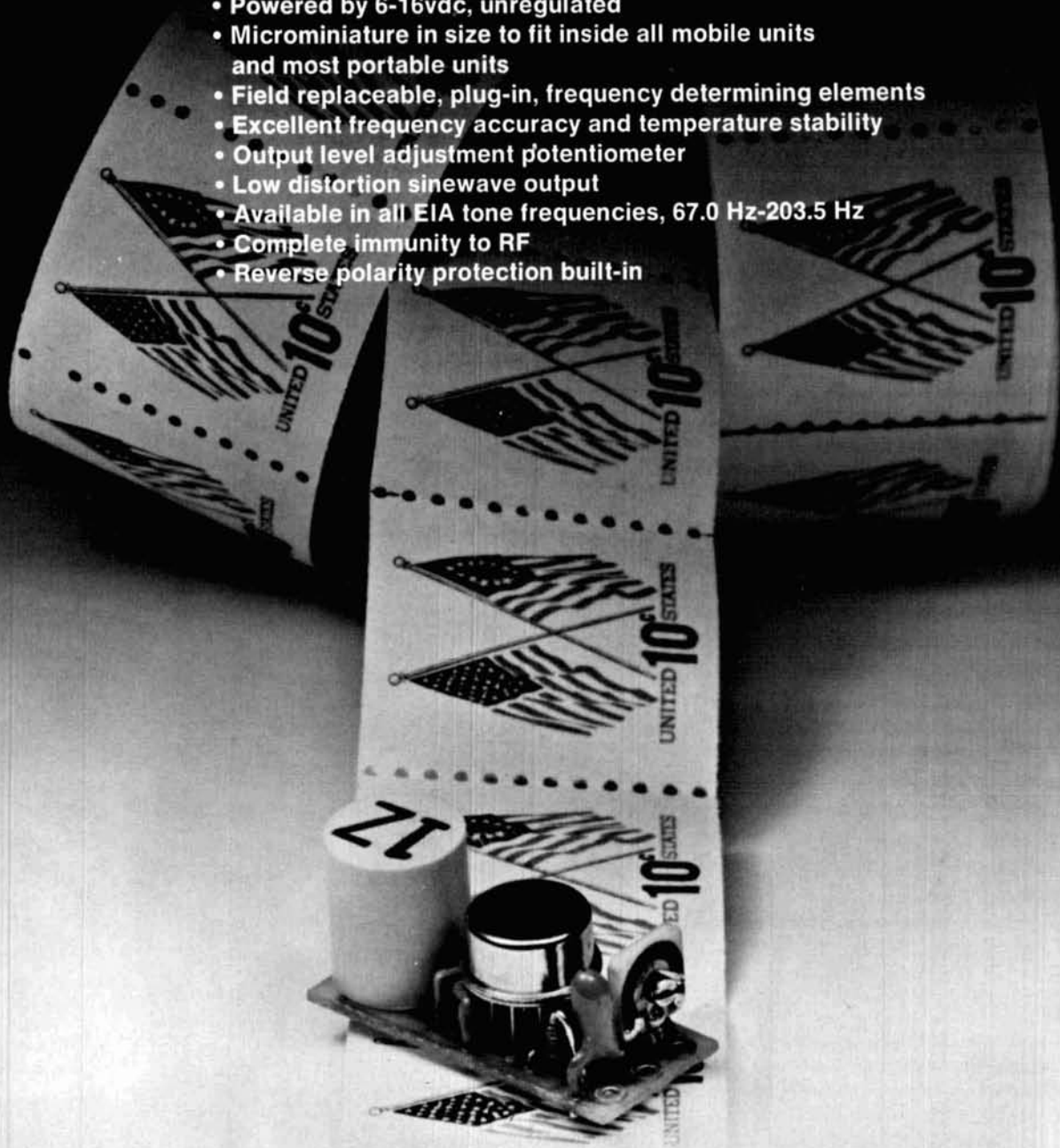
# ME-3 microminiature tone encoder

Compatible with all sub-audible tone systems such as: Private Line, Channel Guard, Quiet Channel, etc.

- Powered by 6-16vdc, unregulated
- Microminiature in size to fit inside all mobile units and most portable units
- Field replaceable, plug-in, frequency determining elements
- Excellent frequency accuracy and temperature stability
- Output level adjustment potentiometer
- Low distortion sinewave output
- Available in all EIA tone frequencies, 67.0 Hz-203.5 Hz
- Complete immunity to RF
- Reverse polarity protection built-in



**\$29.95 each**

Wired and tested, complete with K-1 element

**communications specialists**

P. O. BOX 153  
BREA, CALIFORNIA 92621  
(714) 998-3021



K-1 FIELD REPLACEABLE,  
PLUG-IN, FREQUENCY  
DETERMINING ELEMENTS

**\$3.00 each**

## FREQUENCY STANDARD



- ✓ Precision crystal.
- ✓ Markers at 100, 50, 25, 10, 5 KHz.
- ✓ Zero adjust sets to WWV.

The Palomar Engineers Frequency Standard gives sharp clear markers throughout the high frequency band from 160 through 6 meters. With the panel switch in 100 KHz position the markers can be heard every 100 KHz for checking calibration of your receiver, transceiver, or VFO. Additional markers can be turned on with the panel switch every 50, 25, 10 or 5 KHz.

The exclusive Palomar Engineers circuit generates only the wanted markers. No extra "ghost" markers appear.

Connection to your receiver is simple. A twisted-wire capacitor from the Standard to the receiver rf amplifier or mixer. Or a short "antenna" connected to the Standard may radiate enough marker signal.

The Frequency Standard is factory set to frequency and the setting can be checked and adjusted with the "zero" trimmer while listening to WWV or a broadcast station. All markers are as accurate as the WWV calibration, typically .0001%.

Don't take chances; check your frequency. Use the Standard with the wide range of selectable markers, the time-proven Palomar Engineers Frequency Standard.

Send for free brochure.

The price is \$37.50 (9-v battery not included) and we deliver postpaid anywhere in the U.S. and Canada. California residents add sales tax. **ORDER YOURS NOW!**

# PALOMAR ENGINEERS

BOX 455, ESCONDIDO, CA 92025  
Phone: (714) 747-3343

## TONE ENCODER PAD

MODEL TTP-03

- DIGITRAN® Keyboard
- Output Level Set Pot
- Crystal Controlled-Digitally Synthesized Tones
- Strapping for Hi-Low Z Output
- Internal 5 V. Regulator
- Supply Voltage Range 7 to 24 V.
- RFI Suppression
- Velcro and Case Included
- Size 2.80 - 2.00 - 0.60 Inches



**\$54.95**

POSTPAID  
IN U.S.A.

TEXAS RESIDENTS  
ADD 5% SALES TAX  
CHECK OR M.O.  
SEE UP-COMING AD FOR NEW  
AUTOMATIC UNIT: ATD-70  
2 NUMBERS, FIELD PROGRAM-  
MABLE. \$79.95

SATISFACTION  
GUARANTEED

**CLENG** CLENG ELECTRONICS COMPANY  
BOX 12171 DALLAS, TEXAS 75225

## ENERGY CRISIS SOLVED!

Personal energy crisis? Get precious RF on DX target with World Record Breaking antenna that won W6TYP the QRP ARC 1,000,000 miles/watt award.

### THE JOYSTICK VFA

(Variable freq. ant) gives low angle, omnidirectional, harmonic free radiation on all bands 160 thru 10! - MARS and receive on all BC & SW! 1000's of glowing reports in our files of the VFA in use, often in poor QTH and/or under QRP, contests, etc.

**SYSTEM 'A' \$75.00**

250W P.E.P. &/or Receiving Only

**SYSTEM 'J' \$99.00**

500W P.E.P. &/or Improved Q Factor Receive

Air Mail cost included. (Each system 3 sections easily assembled to make unit 7" 6" long. Matching ATU! Not only will you save space but you will save \$\$\$ at present low exch. rate and by buying direct UK manu! Rush your order - Mastercharge or check, or ask for brochure.

**PARTRIDGE (HR)  
ELECTRONICS LTD.**


Broadstairs, Kent, England  
Tel. Thanet 62635

G3CED

G3VFA

## SUB-AUDIBLE GENERATOR for FM

THE CUBE

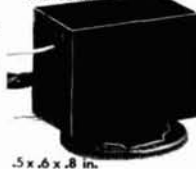

.5 x .6 x .8 in.

Price \$19.95

Freq. set at  
factory  
\$5.00 extra

Call. res. add 6%

vle  
products

- Inexpensive multi tone encoder
- Compatible with PL-CG-QC
- Low distortion sinewave
- Input 8-18 VDC unregulated
- Rugged, plastic encased with leads
- Adjustable frequency (98-250 Hz), Lower available
- Excellent stability

Send for more info

Dept. hr P.O. Box 2083 Santa Clara, CA. 95051

**NEW ELECTRONIC PARTS**  
IC'S - TRANSISTORS - PROTOBOARDS - RESISTORS  
CAPACITORS - DIODES - SWITCHES - CONNECTORS  
VOLTAGE REGULATORS - CABINETS - HEAT SINKS  
FUSES & MUCH MORE - STAMP BRINGS CATALOG

## SPECIALS

### KEYBOARD ENCLOSURES

TWO SIZES	W	D	H	PRICE
	14	8.3	3	\$13.50*
	14	11.3	3	\$14.50*

BLUE BASE SPECIFY  
WHITE OR BLACK TOP

### BREADBOARD KIT \$10.75\*

2" X 6"



BANKAMERICAN

\*SHIPPING INCLUDED

NuData Electronics

104 N. EMERSON ST., MOUNT PROSPECT, ILLINOIS 60056



with

## JAN QUARTZ CRYSTALS

for

- CB Synthesized • CB Standard
- General Communications
- Industry • Two-Meter
- Monitor • Scanners
- Marine VHF • Amateur Bands

Dependable USA Mfg. for


- Frequency Control
- Frequency Stability
- High Performance

Write or phone for more details Send 10¢ for our latest catalog



2400 Crystal Drive  
Ft. Myers, Florida 33901  
all Phones (813) 936-2397

## WANTED FOR CASH

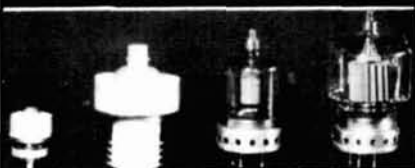

4CX150 4CX1000 4-65 4-250  
4CX250 4CX1500 4-125A 4-400  
4CX300A 4CX3000 4-1000  
4CX350A 4CX5000 304TL  
4CX10,000  
5CX1500

Other tubes and Klystrons also wanted.  
See last month for other items available.

**The Ted Dames Company**

308 Hickory St. Arlington, N.J. 07032  
(201) 998-4246 Evenings (201) 998-6475



# A Message from Art ... About AGL

We'll See You —

October 7th, 8th & 9th at the **ARRL WEST GULF  
DIVISION CONVENTION**, Austin

October 28th, 29th & 30th at the **LAKE TEXOMA HAMFEST**

K9TRG



## AGL Electronics

LARRY ISSARY  
President

ART HOUSHOLDER  
Vice President

GORDON FOGG  
Secretary-Treasurer

OM:

A.G.L. is a comparatively new company with an old-fashioned philosophy about giving our customers the best service we can deliver at the most competitive price.

Everyone at A.G.L. is a licensed ham operator with a strong electronics background, and although A.G.L. is new, we've probably met and talked with most of you at hamfests for the past many years. (We would rather not discuss how many).

We think we have accumulated one of the most complete inventories of electronics in the southwest. We've combined that, with our own skills and backgrounds and created a business that we hope you will like doing business with.

By the way, if you like to "horse trade" on equipment, you are more than welcome. In fact, we encourage it.

Stop in and see for yourself, you are going to like A.G.L.

73,

*Art Housholder*

Art Housholder, K9TRG  
Vice President

3068 Forest Lane, Suite 309 • Dallas, Texas 75234 • 214/241-6414



**CALL US TODAY TOLL FREE AT 1-800-527-7418**

CALL 214-241-6414 (in Texas)

LARRY WA5WWH

GORDON N5AU

MIKE WA5UOB

MIKE WB5ACM

TOM K5TM

BOB W5XC



## AGL Electronics



3068 FOREST LANE, SUITE 309 • DALLAS, TEXAS 75234



# TOROID CORES



- ✓ All the popular sizes and mixes.
- ✓ Fast Service. Same day shipment via first class mail or air.
- ✓ No minimum order.

## IRON POWDER TOROIDS:

CORE SIZE	MIX 2 5-30 MHz u=10	MIX 6 10-90 MHz u=8.5	MIX 12 60-200 MHz u=4	SIZE OD (in.)	PRICE USA \$
T-200	120			2.00	3.25
T-106	135			1.06	1.50
T-80	55	45		.80	.80
T-68	57	47	21	.68	.65
T-50	51	40	18	.50	.55
T-25	34	27	12	.25	.40

## RF FERRITE TOROIDS:

CORE SIZE	MIX Q1 u=125 .1-70 MHz	MIX Q2 u=40 10-150 MHz	SIZE OD (in.)	PRICE USA \$
F-240	1300	400	2.40	6.00
F-125	900	300	1.25	3.00
F-87	600	190	.87	2.05
F-50	500	190	.50	1.25
F-37	400	140	.37	1.25
F-23	190	60	.23	1.10

Chart shows uH per 100 turns.

## FERRITE BEADS:



\$2.00 DOZEN

## WIDE BAND CHOKES



95¢ EACH

TO ORDER: Specify both core size and mix for toroids. Packing and shipping 50 cents per order USA and Canada. Californians add 6% sales tax.

Fast service. Free brochure and winding chart on request.

# PALOMAR ENGINEERS

BOX 455, ESCONDIDO, CA 92025  
Phone: (714) 747-3343

## YOU'VE SEEN THE MAGAZINE ARTICLES

Here's what you can expect from the **DX ENGINEERING** RF Speech Processor

- 6 db INCREASE IN AVERAGE POWER
- MAINTAINS VOICE QUALITY
- IMPROVES INTELLIGIBILITY
- NO CABLES OR BENCH SPACE REQUIRED
- EXCELLENT FOR PHONE PATCH
- NO ADDITIONAL ADJUSTMENTS — MIKE GAIN ADJUSTS CLIPPING LEVEL
- UNIQUE PLUG-IN UNIT — NO MODIFICATIONS REQUIRED



This is RF Envelope Clipping—the feature being used in new transmitter designs for amateur and military use.

Models Now Available  
Collins 32S, KWM-2 ..... \$ 98.50 ea.  
Drake TR-3, TR-4, TR-6, TR-4C,  
T-4, T-4X, T-4XB, T-4XC \$128.50 ea.  
Postpaid — Calif. Residents  
add 6% Tax

Watch for other models later!

## DX Engineering

1050 East Walnut, Pasadena, Calif. 91106

## SST T-1 RANDOM WIRE ANTENNA TUNER



All band operation (160-10 meters) with most any random length wire. 200 watt output power capability. Ideal for portable or home operation. Toroid inductor for small size: 3 x 4-1/4 x 2-3/8. Built-in neon tune-up indicator. SO-239 coax connector. Guaranteed for 1 yr., 10 day trial. Compact — easy to use... only \$29.95 postpaid. (Add Sales Tax in Calif.) (213) 376-5887

SST ELECTRONICS, P.O. BOX 1, LAWNSDALE, CA. 90260

See our **HAM MART** listings to find the **Amateur Radio** dealers nearest you.

## Microcomputer Interfacing Workshop December 8-10, 1977

A three-day workshop based on the popular 8080 and 8085 microprocessors. Over 20 operating microcomputers are available for participant use.

## Digital Electronics for Automation Workshop, December 6-7, 1977

A two-day workshop based on the small scale and medium scale TTL integrated circuits. Many hours of laboratory time with individual breadboarding stations will be provided along with in depth lectures. For more information on these workshops contact Dr. Norris Bell, V.P.I. and S.U. Continuing Education Center, Blacksburg, Virginia 24061, (703) 951-6328.

# BIRD



Mobile Communications  
Support Test Equipment

AVAILABLE FROM YOUR

AUTHORIZED DISTRIBUTOR

WEBSTER COMMUNICATIONS

115 BELLARMINE  
ROCHESTER, MI 48063

CALL TOLL FREE

800-521-2333

MICHIGAN 313-375-0420

this  
publication is  
available in  
microform



Please send me additional information.  
**University Microfilms**

**International**

300 North Zeeb Road  
Dept. P.R.  
Ann Arbor, MI 48106  
U.S.A.

18 Bedford Row  
Dept. P.R.  
London, WC1R 4EJ  
England

Name \_\_\_\_\_  
Institution \_\_\_\_\_  
Street \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_



## TS-1 MICROMINIATURE ENCODER-DECODER


- Available in all EIA standard tones 67.0Hz-203.5Hz
- Microminiature in size, 1.25x2.0x.65" high
- Hi-pass tone rejection filter on board
- Powered by 6-16vdc, unregulated, at 3-9ma.
- Decode sensitivity better than 10mvRMS, bandwidth,  $\pm 2$ Hz max., limited
- Low distortion adjustable sinewave output
- Frequency accuracy,  $\pm 25$ Hz, frequency stability  $\pm 1$ Hz
- Encodes continuously and simultaneously during decode, independent of mike hang-up
- Totally immune to RF

Wired and tested, complete with K-1 element

**\$59.95**

K-1 field replaceable, plug-in, frequency determining elements

**\$3.00 each**

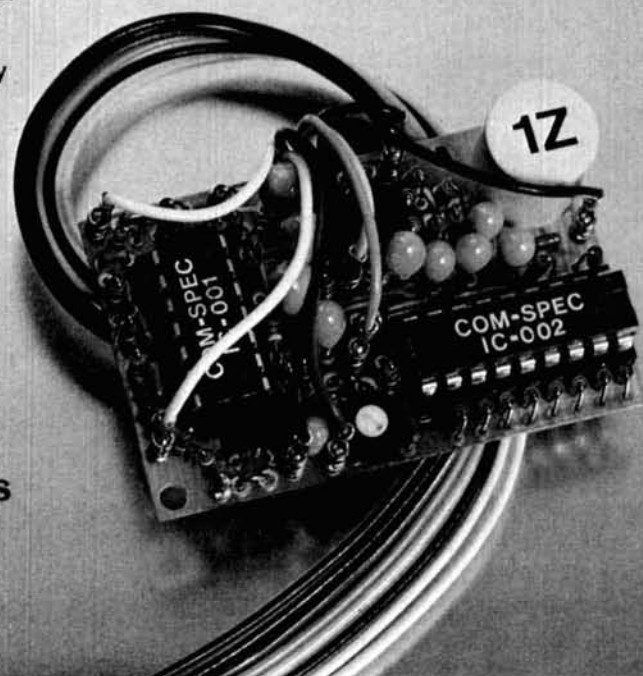

### COMMUNICATIONS SPECIALISTS

P.O. BOX 153  
BREA, CALIFORNIA 92621  
(714) 998-3021



## The Leader in the Northwest!

ATLAS ICOM KENWOOD YAESU



KENWOOD TS-520S



ATLAS 350-XL



YAESU FT-101E



KENWOOD TS-820S



YAESU FT-301D



**ABC**  
COMMUNICATIONS


17550 15th AVE. N.E.  
SEATTLE, WASH. 98155  
206-364-8300



TO PLACE ORDER  
CALL TOLL FREE  
IN STATE OF WASH.  
1-800-562-7625

Other locations:  
(Walk-in customers only)  
Bellevue - 12001 N. E. 12th  
Everett - 6920 Evergreen Way

# R-X NOISE BRIDGE

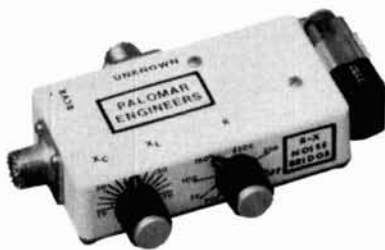

- ✓ Learn the truth about your antenna.
- ✓ Find its resonant frequency.
- ✓ Adjust it to your operating frequency quickly and easily.

If there is one place in your station where you cannot risk uncertain results it is in your antenna.

The Palomar Engineers R-X Noise Bridge tells you if your antenna is resonant or not and, if it is not, whether it is too long or too short. All this in one measurement reading. And it works just as well with ham-band-only receivers as with general coverage equipment because it gives perfect null readings even when the antenna is not resonant. It gives resistance and reactance readings on dipoles, inverted Vees, quads, beams, multiband trap dipoles and verticals. No station is complete without this up-to-date instrument.

Why work in the dark? Your SWR meter or your resistance noise bridge tells only half the story. Get the instrument that really works, the Palomar Engineers R-X Noise Bridge. Use it to check your antennas from 1 to 100 MHz. And use it in your shack to adjust resonant frequencies of both series and parallel tuned circuits. Works better than a dip meter and costs a lot less. Send for our free brochure.

The price is \$49.95 and we deliver postpaid anywhere in U.S. and Canada. California residents add sales tax.

Italy write i2VTT, P.O. Box 37, 22063 Cantu. Elsewhere send \$52.00 (U.S.) for air parcel post delivery worldwide.

Fully guaranteed by the originator of the R-X Noise Bridge. ORDER YOURS NOW!

## PALOMAR ENGINEERS

BOX 455, ESCONDIDO, CA 92025  
Phone: (714) 747-3343

# CFP . . . FOR ALL YOUR AMATEUR NEEDS

ATLAS  
CUSHCRAFT  
CIR (ASTRO 200)  
DENTRON



DRAKE  
TEMPO  
TEN TEC  
YAESU\*

**YAESU FT-101EX \$589 LIST**  
*For the economy-minded Amateur*

\*REMEMBER, YOUR DEALER IS RESPONSIBLE FOR WARRANTY REPAIRS DURING WARRANTY PERIOD.  
Mail Orders accepted. N. Y. residents add sales tax. SASE will get our list of used Amateur Equipment.

**WANTED: GOOD CLEAN TRADES!**

Transmitter sales to licensed amateurs only.

Store Hours  
Tues. to Fri. 10-6 p.m.  
Sat. 10-4 p.m.

## CFP COMMUNICATIONS

WA2KJTJ  
WB2LVW



211 NORTH MAIN STREET  
HORSEHEADS, N. Y. 14845  
PHONE: 607-739-0187



Fri. & Sat. subject to Hamfest weekends  
Closed Sun. & Mon.

## ALL BAND TRAP ANTENNA!



5 BAND OPERATION - ONLY ONE NEAT SMALL ANTENNA. FOR CONGESTED HOUSING AND APARTMENT DWELLERS!  
FOR ALL AMATEUR HF TRANSMITTERS GUARANTEED FOR 1,000 WATTS POWER. LIGHT, NEAT WEATHERPROOF.

Complete as shown total length 102 ft. with 90 ft. of 52 ohm RG58U coax and PL259 connector. Hi-impact molded resonant traps. (wt. 3 oz. 1" x 5" long) You just tune to desired band for excellent reports! Excellent for ALL world-wide receivers and amateur transmitters. FOR NOVICE AND ALL CLASS AMATEURS! NO EXTRA TUNERS OR GADGETS NEEDED! Eliminates 5 separate antennas with excellent performance guaranteed. Can be used as inverted V. NO HAYWIRE HOUSE APPEARANCE! EASY INSTALLATION!  
80-40-20-15-10 meter bands. Complete . . . . . \$39.95  
40-20-15-10 meter bands. 54-ft. ant. . . . . \$38.95  
20-15-10 meter bands. 24-ft. ant. . . . . \$37.95  
SEND ONLY \$5.00 (cash, ck., mo.) and pay postman balance COD plus postage on arrival or send full price for pp. del. BankAmericard - - - Master Charge - - - Ph 308-236-5333 Free info: available only from. WESTERN ELECTRONICS Dept. AH-10 Kearney, Nebraska, 68847

## PLANET XP-7 CALLING EARTH

Takes you "to the exciting frontiers of astronomy, with a sense of great adventures to come"  
Dinah Moché THE PHYSICS TEACHER

"Lively, human, thought-provoking"  
Ron Bracewell IEEE SPECTRUM

"An inspiration to any young scientist"  
Bernard Burke PHYSICS TODAY

## BIG EAR

228 pages Illustrated

Cygnus-Quasar Books, Box 85, Powell, Ohio 43065  
\$3.25 paper, \$6.25 hard, postpaid

## COLLINS & MORE

Collins 51S1 Receiver	\$1450.00
Collins 75S3B, Ham rcvr	\$725.00
Collins 75S3B, late, round	\$875.00
Collins 312B4, Exc. cond., round	\$250.00
Collins KWM-2 transcvr. V.G.	\$650.00
Collins CP-1 crystal Pack	\$195.00
Collins 32S3, Ham Xmtr.	\$750.00
Drake SPR-4, new, boxed, w/options	\$550.00
Collins 30S1, like new	\$1750.00
Heath VHF-1 Seneca, 6/2m xmtr.	\$125.00
HP 608D 10-420 MHz sig gen.	\$595.00

We stock good, used equipment from Collins, Drake, Heath and other manufacturers. Hundreds of test items also available. Call for specific requirements, or write for free catalog.

## DAMES COMMUNICATION SYSTEMS

201-998-4256  
10 SCHUYLER AVENUE  
NORTH ARLINGTON, N. J. 07032



3000 MFD @ 30 Volt Capacitors.

1" Dia. x 3" — 90¢ ea. or 3/\$2.25 ppd.

3000 MFD @ 20V Capacitors. Same size as above. 80¢ ea. or 3 for \$2.00 ppd.

### ELECTROLYTIC CAPACITOR — PHILCO

QUAD SECTION 4" x 1 3/4" dia. TWISTAB MTG.

100x150 MFD @ 400V and at 350V D.C. and 20x50 MFD @ 250V — A nice unit for Xceiver, etc. \$1.10 ea. or 3/\$2.95 ppd.

CRL Disc Capacitors. .1 MFD, 10V 3/8" dia., long leads. 10 for \$1.00 ppd. 100/\$8.40, 500/\$36.60 (U.P.S. Only)

UNPOTTED TOROIDS — center tapped 88MHY Limited Q'tys 44 MHY 5/\$2.95 5/\$3.95 ppd.

SEND STAMP FOR BARGAIN LIST PENNSYLVANIA RESIDENTS - ADD 6% ALL ITEMS PPD. USA



### SEMTECH BRIDGES

Heat sink w/center hole mtg. 10 Amp — Tested —  
200V P.I.V. \$1.75 ea. ppd.  
400V P.I.V. \$1.95 ea. ppd.  
600V P.I.V. \$2.15 ea. ppd.



25 AMP — TESTED  
200V P.I.V. \$2.25 ea. ppd.  
400V P.I.V. \$2.50 ea. ppd.  
600V P.I.V. \$2.85 ea. ppd.



CARBON TRIMMERS  
Miniature 1/4 watt units. PC type. Values: 200, 700, 1000, 1.5K, 250K, 700K  
30¢ ea. or 5/\$1.35 ppd.



NEW SIZES — VERTICAL MOUNT PC BOARD POTENTIOMETERS  
American made (CRL) Cermet sizes: 25K, 100K ohms. 5/\$1.30 ppd. CTS Blue wheel. Values: 750, 1K, 1.5K, 50K, 300K ohms. 5/\$1.25 ppd.

**m. weinschenker**  
electronic specialties-BOX 353, IRWIN, PA 15642

# SAROC™

## HAWAII WEEK

INCLUDING

### SAROC'S THIRD HAWAIIAN CONVENTION November 1 to 8, 1977

SPEND 8 FABULOUS DAYS IN EXCITING HAWAII ON SAROC'S HAWAII WEEK



**Your holiday includes:**

- Attendance at SAROC Hawaiian Convention, Saturday and Sunday, November 5 and 6.
- Seven nights at the fabulous HYATT KUILIMA RESORT HOTEL and COUNTRY CLUB on Oahu's North Shore.
- Roundtrip air transportation, double occupancy in hotel room and SAROC Advance Registration just \$350 per person. Limit 2 pieces of luggage per person. Tax and gratuity included.
- Departs Los Angeles, November 1, 1977 — Returns November 8, 1977. (United Airlines OTC Flight)
- \$100 deposit immediately, full payment by September 15, 1977.
- SAROC Advance Registration \$3.00, with Saturday Banquet \$11 per person.

*Write for further details*

### SAROC™

BOX 945, BOULDER CITY, NEVADA 89005



When the winter winds blow you need...

# TOWER POWER

by **TRISTAO**

Superior Quality and Construction at a price you can afford.

Tristao is a pioneer. Years of designing and manufacturing show in structural performance and practical pricing. Certified welded construction; sand-blasted surfaces; hot-dipped galvanized; heavy duty for capacity, strength, safety. Send for FREE Catalog.

Dealer Inquires always invited.

Self-supporting or Guyed  
**TOWERS**

#### CZ SERIES

Self-supporting 38' to 84' for most tri-band beams in 60 mph winds. Equipped with heavy duty winch.

#### CTL SERIES

Guyed crank up 18' thru 105' for tri-band beams to 8 sq. ft. Takes CDR HAM II and similar rotors. Complete installation packages available.

### TRISTAO MAST MASTER

Self-supporting Rotating - Crank-up

#### SUPER AND STANDARD MINI-MASTS

Supports 10 sq. ft. antenna in 50 mph winds. Self-supporting. With winch and cable. Models from 40' to 67'.

#### FULL-LINE OF MINI-MAST ACCESSORIES

**NEW EXCLUSIVE ROTOR BASE**  
For standard CDE or others including HAM II. Entire mast is rotated from ground level.

CUSTOM TOWERS BUILT TO YOUR SPECIFICATIONS

Masts priced from \$198.50

All specs available on request.

## TRISTAO TOWER

Division of Palmer Industries, Inc.

415 E. 5th St. - P.O. Box 115  
Hanford, CA 93230 / Ph. (209)582-9016  
Send me your complete catalog.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_

# TEE/AX PRESENTS; THE FIRST COAX TOGGLE SWITCH

## \$39<sup>95</sup>

### TEE/AX, INC.

5701 N.W. 31st AVENUE  
FT. LAUDERDALE,  
FLORIDA 33309

Distributor Inquiries  
Invited

Mail Orders Accepted — Add 75¢ for Postage

Patent Pending



Model SW-5000

- 52 ohms
- SPDT, DPDT
- Power 1 KW
- All Brass Construction
- Teflon Insulated
- Captivated Internal Contacts
- Available in UHF, BNC, N, F, all series

## YOUR KENWOOD HEADQUARTERS



**TS-520S**  
10-160 meter transceiver  
Digital dial available  
Price \$649



**TR-7400A**  
2-meter FM transceiver  
Digital dial 800 channels  
Price \$399

### ELECTRONIC DISTRIBUTORS, Inc.

Communication Specialists  
for over 38 years

1960 PECK ST., MUSKEGON, MICH. 49441  
TEL. (616) 726-3196 TELEX 22-8411

**LOGIC PROBE**

Compare these features

- > 100 kΩ input Z
- Probe tip protected against overvoltage
- Automatic pulse memory
- Counts < 15 ns pulses
- Assembled and tested
- Use in almost any logic system

ONLY \$24.95

L.S.I., Box 7197, Univ. Sta., Provo, Utah 84602  
SEND CHECK OR MONEY ORDER

**Radio Amateur Labels**

FOUR DESIGNS  SIX COLORS

FOR SAMPLES AND PRICES WRITE TO:  
**Artistic Label Co.**  
P.O. BOX 1662 ENGLEWOOD, COLO. 80150

**GROTH-Type**

**COUNTS & DISPLAYS YOUR TURNS**

- 99.99 Turns
- One Hole Panel Mount
- Handy Logging Area
- Spinner Handle Available

Case: 2x4"; shaft 1/4" x 3"

Model TC2: Skirt 2-1/8"; Knob 1-5/8"

Model TC3: Skirt 3"; Knob 2-3/8"

**PRICES** POST PAID

TC 2	—	\$8.00
TC 3	—	\$8.75
Spinner (\$)	—	\$1.00

Add \$0.75 for Air or UPS

**R. H. BAUMAN SALES**  
P.O. Box 122, Itasca, Ill. 60143

# LUNAR

## proudly announces a NEW 2-Meter AMPLIFIER/PREAMPLIFIER the 2M10-80P

The Marriage Between Power Amplifiers and Receiving Preamplifiers is Finally Consummated! Lunar Offers an SCS 2M10-80L Power Amp and an "Anglelinear" 144W Preamp in a Single, Functionally-Designed Package that Combines Two Superior Products Into One!



### Features:

- ★ Ten watts input — eighty watts output
- ★ Harmonic reduction exceeds -60 dB to meet FCC R&O 20777 Specifications
- ★ Variable T-R Delay for CW/SSB
- ★ Functionally-Designed Extrusion Includes Mounting Lip
- ★ Preamplifier Selectable Independently of Power Amplifier
- ★ Automatic T-R Switching of Amp & Preamp
- ★ Preamp gain: Nominally 11 dB  
Noise Figure: Nominally 2.5 dB  
(Including Relay Losses)
- ★ Remote Control Head Available Separately

**Introductory Price: . . . . . Lunar Model 2M10-80P . . . . . \$189.95**

Please add \$3.00 shipping and handling

### Also From Lunar:

- Available Now: Complete Line of Separate Preamplifiers  
50-450 MHz
- Coming Soon: Complete Line of 50-450 MHz Amp/Preamp  
Combinations  
Preamps Through 2.5 GHz  
Transverter Systems 50 MHz-2.5 GHz  
Converters and Filters 28 MHz-2.5 GHz



# LUNAR

## electronics

SUITE 10  
2785 KURTZ ST.  
SAN DIEGO, CA 92110  
714-299-9740  
Louis N. Anciaux WB6NMT

California residents add 6%. Order today at your dealer or direct from:


# BULLET ELECTRONICS

P.O. BOX 19442  
DALLAS, TX. 75219  
(214) 823-3240
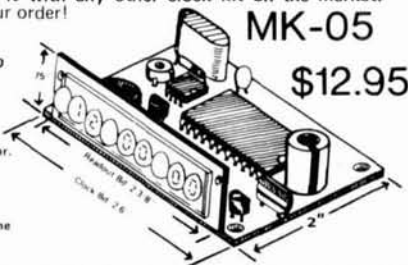
### 6 DIGIT MINI MOBILE ALARM CLOCK KIT

Many of our customers who have bought our other mobile clock kits (MK-03 & MK-04), have requested a small mobile clock for in dash mounting. We put our engineer to work on it and the result is the compact MK-05. Designed to be a mobile clock from the ground up. There has been no compromise on quality. Take a look at the specs, price, size and compare it with any other clock kit on the market. We will be waiting for your order!

- Quartz crystal timebase
- Toroid and zener noise & voltage protection
- Magnified 15 inch, 6 digit LED readout with spacing between hours, minutes, & seconds
- Top Quality epoxy glass PC boards are drilled & plated
- No additional components are required
- Complete with presettable 24 hr. alarm (speaker NOT included)
- Can be used as elapsed timer
- Easy, quick assembly
- 9-14 VDC @ 40 to 50 ma
- Readouts can be turned off & the clock continues to keep time
- PC board Clock: 2.6" x 2"
- Readout board: 2.3/8" x .75"



**MK-05**  
**\$12.95**

### PS-12 HIGH CURRENT VARIABLE POWER SUPPLY KIT A LOW COST WAY TO HAVE A QUALITY VARIABLE BENCH SUPPLY.

ALL ELECTRONICS SUPPLIED Regulation: 240mv Load & Line  
LARGE COMPUTER GRADE FILTER Ripple: Less than .5V @ 30V & 10A.  
PLATED PC BOARD  
UNIQUE PRE-REGULATOR ALLOWS COOLER OPERATION AT HIGH CURRENTS.  
3 to 16V & 15 to 30V (two ranges) @  
10A CONTINUOUS (15A with fan cooling)  
ADJUSTABLE CURRENT LIMITING  
SHORT CIRCUIT PROTECTION  
Add \$3.70 for UPS shipping. Outside continental U.S. Add \$10.00 for Parcel Post & Insurance.

**\$49.95**

### OUR CUSTOMERS WRITE ABOUT OUR CDI KIT:

"...great kit."  
"...unbelievable value", "...good design!"  
"...fantastic kit and service. Send three more."  
**\$9.95**

The CDI kit is all these things and more. Get in on a one-time deal. Complete electronics.  
Requires heatsink (not included) also works for voltage source for high intensity strobe.

### Mini Grandfather Clock Kit

**\$39.95 kit**     **\$59.95 (assembled & checked out)**

- Completely Electronic
  - 100% Solid State
  - All CMOS IC Construction
  - 2 Quality Plated PC Boards 6.5" x 4.5"
  - New, revised easy to follow instructions
  - Large 1/2" LED readout with AM/PM & colon indicators
  - Simulated LED swinging pendulum with synchronized tick-tock sound.
  - Chimes the hour (ie: 3 times for 3 o'clock)
  - Adjustable volume tone and sustain on the chime.
  - LOW COST
  - Complete with all parts including transformer & speaker.
- We offer a beautiful solid hard wood case in either ash or walnut with front ruby filter. Designed and cut specifically for the mini grandfather clock kit.  
Unfinished Case - \$15.95  
Finished Case - \$19.95  
Please specify type of wood desired. Case is shipped unassembled.

### OVERVOLTAGE PROTECTION KIT     **\$6.95**

The OVP-1 is an overvoltage protection circuit designed to protect your expensive gear if the series pass regulators short or unauthorized hands tamper with the voltage setting on a variable supply. Set the OVP-1 for 1 or 2 volts over the normal operation voltage and it will instantly go into current limiting; (if the supply has this feature), or blow the fuse. The kit comes complete with PC board, all components including the 25A SCR and complete easy to follow instructions. Designed specifically for the PS-12 Power Supply Kit.

### MK-03 AIRCRAFT/CLOCK TIMER KIT.

You don't have to be a pilot to need the MK-03. If you want a mobile clock that offers: six .4" LED readouts, 24 hour real time readout, 24 elapsed time readout, alarm, snooze, display blanking. Timer and clock share same set of readouts but are totally independent of each other. Timer has reset and freeze feature. Many other options are available. Sold less case and switches because of the various mountings and options available.  
**\$26.95/complete electronics and boards less switches and case.**

TERMS: NO COD's \* Send check or M.O. \* Add 5% postage Tx. Residents add 5% sales tax \* Foreign add 10% (20% airmail) Orders under \$10. add 60c handling \* Repair service available Accepting phone orders on Master Charge and BankAmericard.



# GREAT VALUES from Amateur Radio's most complete selection!

## March 1968 (first issue)

**FEATURING:** 5-band SSB exciter, IC-regulated power supply, Remotely-tuned 10-meter beam, Transistor curve tracer, Double-balanced mixers.

## May 1969

**FEATURING:** Potpourri of integrated-circuit applications, FM repeater receiver performance, RTTY converter, IC noise blanker, The ionospheric e-layer.

## August 1969

**FEATURING:** Homebrew Parabolic Reflector, Solid-state Q-5er, Frequency calibrator with mos IC's, New multiband quad antenna, Troubleshooting with a scope.

## September 1969

**FEATURING:** FM techniques and practices, IC power supplies, 1296-MHz varactor tripler, Tunable bandpass filters, Amateur microwave standards.

## October 1969

**FEATURING:** Hot Carrier Diodes, Low-cost linear IC's, Diversity antennas, solid-state 432-MHz exciter, Tropospheric-duct communications.

## November 1969

**FEATURING:** Op Amps . . . theory, selection & application, WWV receiver, Multi-band antenna, Electronic key, Six-meter collinear.

## June 1970

**FEATURING:** Communication experiments with light emitting diodes, FM modulation standards, Designing phase-shift networks, Transistor frequency multipliers, RTTY frequency-shift meter.

## October 1970

**FEATURING:** An SWR meter for accurate RF power measurements, Direct-conversion receiver, IC voltage regulators, 432 MHz converter, Introduction to thyristors.

## December 1970

**FEATURING:** SSB generator, RF interference, Antenna bridge, QRP transmitter, AFSK oscillator.

## June 1971

**FEATURING:** A practical approach to 432-MHz SSB, FM carrier-operated relay, Audio agc systems, Practical IC's, Low-noise 1296-MHz preamp.

## June 1972

**FEATURING:** 5 Band solid-state communications receiver, FM repeater control, SSTV synch generator, microwave experimenting.

## October 1972

**FEATURING:** 4 channel spectrum analyzer, HF frequency synthesizer, all-band dipole, 160 meter vertical, multi-function IC's.

## February 1973

**FEATURING:** Communications receiver design, rf speech clipper, fm receiver scanner, Plessey SL600 integrated circuits, solid-state noise blanker.

## HAM RADIO BINDERS

Collectors items deserve the best protection you can give them, and we know of no better than our handsome Ham Radio Binders. Bound in washable buckram and supplied with year labels to identify each volume. Each binder holds 12 issues.

**Large Size Only \$5.95 each  
3 for \$15.95**

## HAM RADIO BOUND VOLUMES

Here is a handsome addition to your library. Twelve issues (a full year) of Ham Radio bound into a rugged, good looking hard cover book. Certainly the most deluxe way to collect Ham Radio and perhaps the only way to acquire some out of print back issues. Years 1973, 1974, 1975 and 1976 available.

**\$19.95 each or All Four \$67.95**

## March 1973

**FEATURING:** Solid-state 80-meter transceiver, reciprocating detector receiver, AFSK generator, electronic keyers, mobile touch-tone.

## June 1973

**FEATURING:** Digital RTTY autostart, fm repeater installation, micropower receiver, broadband amplifiers, logic oscillators.

## July 1973

**FEATURING:** SSTV test generator, carrier operated relay, VHF receiver, two-meter frequency synthesizer, antenna matching.

## December 1973

**FEATURING:** Two-meter power amplifier, AFSK generator, VHF cavity filter, Bandpass filter design, High-gain wire antenna.

## January 1974

**FEATURING:** CW memory for RTTY identification, Linear amplifier, IC logic families, FM transceiver, Heatsink design.

## April 1974

**FEATURING:** Communications techniques for Oscar 7, Active filter design, Telefax conversion, FM receivers, Wideband amplifier, Antenna radiation patterns.

## May 1974

**FEATURING:** 5th annual antenna issue, Log periodics, Parabolic antennas, Antennas for satellite communications, Ground systems, Antenna measurements.

## August 1974

**FEATURING:** High-power solid-state linear power amplifier, Wind loading on antenna structures, VHF FM scanners, SSB transceivers, Variable-speed RTTY.

## February 1975

**FEATURING:** 2304-MHz power amplifier, Bandpass filter design, Speech processing RTTY terminal unit, GHz frequency scalars.

## April 1975

**FEATURING:** Integrated-circuit electronic keyer, 1296 MHz preamplifiers, Touch-tone encoder, Capacitance meter, Wide-band RF amplifier.

## June 1975

**FEATURING:** A phasing-type single-side-band transmitter, Slim-line touch-tone, UHF prescaler, Crystal oscillators, Noise-figure measurements.

## July 1975

**FEATURING:** UHF double-balanced mixers, Tone encoder, Cubical quad antenna, ATV sync generators, 432 MHz converters, Sweepstakes winners.

## August 1975

**FEATURING:** 500 watt power amplifier for 160 meters, FM alignment techniques, Programmable keyer memory, Solid-state 432 MHz linear amplifier, Adjustable IC voltage regulators.

## September 1975

**FEATURING:** Inductively-tuned six-meter kilowatt, RTTY terminal unit, SSB speech splatter, 432 MHz power amplifier, Hand-held touch-tone, VHF mobile antenna.

## October 1975

**FEATURING:** Special receiver issue, Receiver sensitivity and dynamic range, High dynamic range receiver input stages, High-frequency communications receiver, Pre-amplifier for satellite communications, Crystal discriminator.

## November 1975

**FEATURING:** High-performance VHF FM receiver, RTTY line-end indicator, Tunable audio filter, SSTV preamplifier, Binaural CW reception, Master frequency oscillator.

## December 1975

**FEATURING:** S-line frequency synthesizer, Introduction to microprocessors, 1296-MHz bandpass filters, UHF frequency scaler, Cumulative index.

## January 1976

**FEATURING:** 50-MHz frequency counter, microprocessors, wideband linear amplifier, 432-MHz Yagi, audio power ICs.

## June 1976

**FEATURING:** Survey of FM detectors, audio speech processing techniques, SSB linearity meter, receiver troubleshooting and microprocessors.

## October 1976

**FEATURING:** High-frequency receiver design, multiband HF converter, microwave amplifier design, two-channel VHF-FM receiver, four-band VHF converter.

## December 1976

**FEATURING:** High-frequency communications receiver, loop antennas, broadband mospower amplifier, ASCII-to-Morse code translator, CUMULATIVE INDEX, first issue thru 1976.

## ham radio

GREENVILLE, NH 03048

There's no place like a good collection of HAM RADIO back issues to find answers you're looking for. Go over the list above and find the ones you need.

Enclosed is \_\_\_\_\_ for the items I have checked.

Name \_\_\_\_\_

Call \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

- |   |   |
|---|---|
| <input type="checkbox"/> March 1968 (first issue) | <input type="checkbox"/> April 1974     |
| <input type="checkbox"/> May 1969                 | <input type="checkbox"/> May 1974       |
| <input type="checkbox"/> August 1969              | <input type="checkbox"/> August 1974    |
| <input type="checkbox"/> September 1969           | <input type="checkbox"/> August 1974    |
| <input type="checkbox"/> October 1969             | <input type="checkbox"/> February 1975  |
| <input type="checkbox"/> November 1969            | <input type="checkbox"/> April 1975     |
| <input type="checkbox"/> June 1970                | <input type="checkbox"/> June 1975      |
| <input type="checkbox"/> October 1970             | <input type="checkbox"/> July 1975      |
| <input type="checkbox"/> December 1970            | <input type="checkbox"/> August 1975    |
| <input type="checkbox"/> June 1971                | <input type="checkbox"/> September 1975 |
| <input type="checkbox"/> June 1972                | <input type="checkbox"/> October 1975   |
| <input type="checkbox"/> October 1972             | <input type="checkbox"/> November 1975  |
| <input type="checkbox"/> February 1973            | <input type="checkbox"/> December 1975  |
| <input type="checkbox"/> March 1973               | <input type="checkbox"/> January 1976   |
| <input type="checkbox"/> June 1973                | <input type="checkbox"/> June 1976      |
| <input type="checkbox"/> July 1973                | <input type="checkbox"/> October 1976   |
| <input type="checkbox"/> December 1973            | <input type="checkbox"/> December 1976  |
| <input type="checkbox"/> January 1974             |   |

Just \$1.50 each ppd.

3 for \$3.95

Binders \$5.95 each 3 for \$15.95

Bound Volumes \$19.95 Specify year(s)

Calling All Hams...



...All Hams Call Us!

It's Toll Free... So Dial Away!

1-800-325-3636

**FOR NEW OR USED AMATEUR RADIO GEAR**... we're specialists and carry in stock most of the famous-brand lines. Or, we will talk trade.

**FOR FAST, DOOR-STEP DELIVERY**... give us a call. You'll be amazed; for we guarantee we'll ship your equipment the same day. Plus, most shipments are PRE-PAID.

**TO SAVE MONEY**... join thousands of our satisfied customers who buy from us as easily as from their local supplier. So, remember your call is Toll Free.




We welcome your Master Charge or Bank Americard



**HAM RADIO CENTER, INC.**

8340-42 Olive Blvd. P.O. Box 28271 St. Louis, MO 63132

**ADVA**

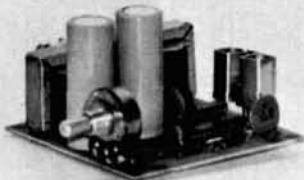

**KIT \$11<sup>95</sup>**

ASSEMBLED \$17.95  
ADD \$1.25 FOR POSTAGE/HANDLING

**VARIABLE POWER SUPPLY**

- Continuously Variable from 2V to over 15V
- Short-Circuit Proof
- Typical Regulation of 0.1%
- Electronic Current Limiting at 300mA
- Very Low Output Ripple
- Fiberglass PC Board Mounts All Components
- Assemble in about One Hour
- Makes a Great Bench or Lab Power Supply
- Includes All Components except Case and Meters

**OTHER ADVA KITS:**

**LOGIC PROBE KIT**—Use with CMOS, TTL, DTL, RTL, HTL, MNVL and most MOS IC's. Built-in protection against polarity reversal and overvoltage. Draws only a few mA from circuit under test. Dual LED readout. Complete kit includes case and clip leads. **ONLY \$7.95**  
**FIXED REGULATED POWER SUPPLY KITS**—Short-circuit proof with thermal current limiting. Compact size and typical regulation of 0.5% make these ideal for most electronic projects. Available for 5V @ 500mA, 5V @ 500mA, 9V @ 500mA, 12V @ 400mA, 15V @ 300mA. Specify voltage when ordering. **\$8.95 ea.**

These easy-to-assemble kits include all components, complete detailed instructions and plated fiberglass PC boards. Power supply kits do not include case or meters. Add \$1.25 per kit for postage and handling.

**1 MAIL NOW! FREE DATA SHEETS** supplied with many items from this ad. **FREE ON REQUEST**—741 Op Amp with every order of \$5 or more—749 Dual Op Amp or two \$1000 FET's with every order of \$10 or more, postmarked prior to 3/31/77. One free item per order. **ORDER TODAY!**—All items subject to price sale and prices subject to change without notice. All items are new surplus parts—100% functionally tested.

**WRITE FOR FREE CATALOG #76** offering over 350 semiconductors carried in stock. Send 13¢ stamp.

**TERMS:** Send check or money order (U.S. funds) with order. We pay 1st Class postage to U.S., Canada and Mexico (except on kits). \$1.00 handling charge on orders under \$10. Call resellers add 8% sales tax. Foreign orders add postage. COD orders—add \$1.00 service charge.

**MORE SPECIALS:**

RC4195DN • 15V @ 50mA VOLTAGE REGULATOR IC. Very easy to use. Makes a neat Highly Regulated -15V Supply for OP AMP's, etc. Requires only unregulated DC (18-30V) and 2 bypass capacitors. With Data Sheet and Schematics. 8-pin PDIP \$1.25  
LM741 FREO COMPENSATED OP AMP,  $\mu$ A741, MC1741, etc. PDIP 5/S1  
MC1458 DUAL 741 OP AMP PDIP 3/S1  
RC4558 DUAL 741 OP AMP PDIP 3/S1  
2N3904 NPN TRANSISTOR AMPLIFIER/SWITCH to 50 mA  $\mu$ 100 6/S1  
ZENER'S—Specify Voltage 3.3, 3.9, 4.3, 5.1, 6.8, 8.2 400mW 4/S1 00  
9, 11, 10, 12, 15, 16, 18, 20, 22, 24, 27, or 33V (1-10%) 1 Watt 3/S1 00

- MONEY-BACK GUARANTEE
- ALL TESTED AND GUARANTEED

**ADVA ELECTRONICS**  
BOX 4181 O, WOODSIDE, CA 94062  
Tel. (415) 851-0455

**FREE** IC or FET's WITH \$5 & \$10 ORDERS.1 DATA SHEETS WITH MANY ITEMS.

DIODES	TRANSISTORS	TRANSISTORS	TRANSISTORS	LINEAR IC'S
ZENER'S & RECTIFIERS	2N718 34	2N4001 3/S1	2N6638 2/S1	LM304K 6 \$1.75
1N456 10	2N720 48	2N4012 3/S1	2N6660 2/S1	LM307 5 1.75
1N458 6/S1	2N718 3/S1	2N4122 3/S1	CP643 \$5.00	LM307 6 1.75
1N483 10	2N1913 30	2N4124 5/S1	CP651 \$4.00	LM307 15 1.75
1N488 6/S1	2N1711 28	2N4248 4/S1	E100 4/S1	LM307 24 1.75
1N748 10	2N1890 38	2N4249 5/S1	E101 3/S1	LM370N* 55
1N750 4/S1	2N1893 38	2N4250 4/S1	E102 3/S1	LM370N 2.50
1N914* 15/S1	2N2219 24	2N4274 5/S1	E175 3/S1	LM3090N 1.20
1N962 10	2N2222 6/S1	2N4322 50.28	MPF112** 3/S1	NE555A 0.80
1N974 4/S1	2N2222A* 5/S1	2N4333 29	MPF104 3/S1	NE556A 0.80
1N3064 6/S1	2N2369 5/S1	2N4338 31	MPF112 4/S1	LM7909C 29
1N3080 6/S1	2N2906 10	2N4368 2/S1	MP0515 3/S1	LM7909C 29
1N4001* 12/S1	2N2909 52	2N4391 31	SE1001 4/S1	LM723H 2/S1
1N4002 12/S1	2N2905 50.24	2N4392 50.90	SE1002 4/S1	LM723H* 3/S1
1N4003 12/S1	2N2906A 24	2N4616 2/S1	SE2001 4/S1	LM720N \$1.00
1N4004 12/S1	2N2927* 5/S1	2N4818A 50.80	SE2002 4/S1	LM741C 3/S1
1N4005 10/S1	2N3553 51.50	2N4850 10	SE5001 10	LM741CN* 4/S1
1N4006 10/S1	2N3563 6/S1	2N4851 10	SE5003 3/S1	LM741CN14 3/S1
1N4007 10/S1	2N3564 4/S1	2N4887E 2/S1	SE5020 53.00	LM741C 30
1N4148 15/S1	2N3565 6/S1	2N4888E 2/S1	TI571 10	740C DIP 30
1N4154* 25/S1	2N3568 6/S1	2N4891 52.50	TI575 3/S1	740C DIP 1.00
1N4370 10	2N3738 6/S1	2N4898 6/S1	DIGITAL IC'S	844CP mDIP 80
1N4372 10	2N3738A 6/S1	2N4905 3/S1	MM5738N \$2.50	LM1458N* 3/S1
1N4444 15/S1	2N3641 5/S1	2N5007 4/S1	SN7400N 10	LM2111N \$1.40
1N4728 10	2N3642 5/S1	2N5008 4/S1	SN7410N 10	XR2506CP 1.50
1N4753 3/S1	2N3643 6/S1	2N5120 10	6/S1	74001 1.80
1N5211 10	2N3644 4/S1	2N5125 10	6/S1	SN7400N 10
1N5226 4/S1	2N3646 4/S1	2N5130 5/S1	SN7400N 10	CA3028A 1.75
	2N3688 10	2N5139 3/S1	SN7401N 10	CA3046 84
	2N3688 10	2N5163 3/S1	SN7476N 35	LM3070N 1.45
	2N3690 10	2N5197 50.50	SN7476N 35	CA3000* 55
	2N3891 10	2N5199 2.50	SN7476N 35	LM3900N 55
	2N3821 80.80	2N5210 3/S1	SN7400N 44	RC4194D 1.50
	2N3822 70	2N5208 2/S1	LINEAR IC'S	RC4194K* 2.50
	2N3823 40	2N5207 51.50	LM101H 51.50	RC4195DN* 1.25
	2N3866 75	2N5432 1.90	LM301A 27	RC4195TK* 2.25
	2N3903 10*	2N5457 3/S1	LM301H 27	LM370CN 2.00
	2N3906 10	2N5458 2.38	LM3080N 88	RC4558N 55
	2N3918 55.00	2N5484 3/S1	LM308K 1.25	NE555B 95
	2N3922 5.00	2N5486 2/S1	LM311N 80	NE555B 50
	2N3954 3.20	2N5543 53.00	LM320K 5 1.35	LM3705K 1.75
	2N3958 1.15	2N5544 2.50	LM320K 12 1.35	LM3705K 3.75
	2N3970 1.00	LM220K 15 1.35	LM220K 15 1.35	DM7582 89

**\*SUPER SPECIALS:**

1N914 100V/10mA Diode	20/S1	MPF102 200MHz RF Amp	3/S1
1N4001 100V/1A Rect.	15/S1	40673 MOSFET RF Amp	\$1.75
1N4154 30V 1N914	25/S1	LM324 Quad 741 Op Amp	.94
BR1 50V $\mu$ A Bridge Rec.	4/S1	LM370 Pos Volt Reg mDIP	.55
2N2222A NPN Transistor	6/S1	NE555 Timer mDIP	2/S1
2N2907 PNP Transistor	6/S1	LM723 2.37V Reg DIP	3/S1
2N3055 Power Xistor 10A	69	LM741 Comp Op mDIP	4/S1
2N3904 NPN Amp/Sw $\mu$ 100	6/S1	LM1458 Dual 741 mDIP	3/S1
2N3906 PNP Amp/Sw $\mu$ 100	6/S1	CA3086 5 Trans Array DIP	.55
CP650 Power FET $\mu$ Amp	55	RC4195DN 15V/50mA mDIP	1.25
RF391 RF Power Amp Transistor 10.25W @ 3.30MHz to 3			\$5.00
555X Timer 1/2 The Different pinout from 555 (w/data)			2/S1
RC4194K Dual Tracking Regulator -0.2 to 30V @ 200mA to 66			\$2.50
RC4195TK Dual Tracking Regulator -15V @ 100mA (TO 66)			\$2.25
8038 Waveform Generator 1/2 Wave With Circuits & Data			\$3.75

# Advertisers check-off

... for literature, in a hurry — we'll rush your name to the companies whose names you "check-off"

Place your check mark in the space between name and number. Ex: Ham Radio  234

## INDEX

ABC	571	Jan	067
AGL	558	Jones	626
ARRL Gulf Coast *		K-Enterprises	071
Active Filter *		KE Electronics	072
Adva	265	Kampp	613
Aldelco	347	Kenwood *	
Aluma	589	Kester	492
Am. Wholesale		Klaus	430
Elect.	003	Lafayette	598
Apollo	011	Logic	493
Artistic Label	326	Long's	468
Atlas	198	Lunar	577
Atronic	382	Lyle	373
Bauman	017	MFJ	082
Beverage Ant. *		Madison *	
Budwig	233	Masters	555
Bullet	328	Microwave Assoc. *	
CFP	022	NuData	455
Calculator Shop *		OK Mach. *	
Clegg	027	Optoelectronics	352
Cleng	465	Palomar	093
Comm. Spec.	330	Partridge	439
Crystal Banking		Poly Paks	096
Service	573	Prime	627
Cushcraft	035	RF Power	
Cygnus-Quasar	549	Comp.	542
DX Eng.	222	RF Power Labs	602
Dames	324	Callbook	100
Dames Comm.	551	Radio World	592
Data Signal	270	Ramsey	442
Davis	332	Regency	102
Daytronics	612	Rohn	410
Dentron	259	SST	375
Disc-Cap	449	SAROC *	
Drake	039	Sherwood	435
E. T. O. *		Space	107
80-Meter DX Hdbk *		Spectronics	191
Elect. Dist	044	Spectrum Int.	108
Elect. Equip.		TPL	240
Bank	288	Tee/Ax	615
Electrospace	407	Ten-Tec *	
Erickson	047	Trans Com	552
Excel Circuits	535	Tri-Ex	116
French Atlantic Aff. *		Tristao	118
Gray	055	University	
Gregory *		Micro. Int.	628
Hal-Tronix	254	VHF Eng.	121
Ham Radio	150	Valley Instr.	583
Ham Center	491	Vanguard *	
Hamtronics	246	Varian	043
Heath	060	Vines	614
Henry	062	Webster Comm.	423
Holdings	252	Weinschenker	122
Icom	065	Western Elect.	601
Int. Circuits	518	Whitehouse	378
Int'l Xtal	066	Wilson	123
James	333	Yaesu	127

\*Please contact this advertiser directly.

Limit 15 inquiries per request.

October 1977

Please use before November 30, 1977

Tear off and mail to

HAM RADIO MAGAZINE — "check off"  
Greenville, N. H. 03048

NAME.....

CALL.....

STREET.....

CITY.....

STATE..... ZIP.....



## There's nothing like it !

### RADIO AMATEUR callbook

Respected worldwide as the only complete authority for radio amateur QSL and QTH information.

The U. S. Callbook has nearly 300,000 W & K listings. It lists calls, license classes, names and addresses plus the many valuable back-up charts and references you come to expect from the Callbook.

Specialize in DX? Then you're looking for the Foreign Callbook with almost 235,000 calls, names and addresses of amateurs outside of the USA.

U.S. Callbook \$14.95

Foreign Callbook \$13.95

Order from your favorite electronics dealer or direct from the publisher. All direct orders add \$1.25 for shipping. Illinois residents add 5% Sales Tax.

RADIO AMATEUR **callbook** INC.  
Dept. E 925 Sherwood Drive  
Lake Bluff, Ill. 60044

# Advertisers iNdex

ABC Communications	119
AGL Electronics	117
ARRL Gulf Coast Convention	108
Active Filter Design	92
Adva Electronics	125
Aldelco	102
Aluma Tower Co.	84
Amateur Wholesale Electronics	72, 73
Apollo Products	96
Artistic Label	122
Atlas Radio	47
Atronic	108
R. H. Bauman Sales Co.	122
Beverage Antenna Handbook	96
Budwig Mfg. Co.	96
Bullet	123
CFP Communications	120
The Calculator Shop	88
Clegg	103, 112
Cleng Electronics	116
Communications Specialists	115, 119
Crystal Banking Service	96
Cushcraft	85
Cygnus-Quasar	120
DX Engineering	118
Dames, Ted	116
Dames Communications Systems	120
Data Signal, Inc.	99
Davis Electronics	95
Daytronics Company	112
Dentron Radio Company	7
Disc-Cap	61
Drake Co., R. L.	78
Ehrhorn Technological Operations	95
80-Meter DX Handbook	91
Electronic Distributors	122
Electronic Equipment Bank	100
Electrospace	112
Erickson Communications	106
Excel Circuits	92, 120
French Atlantic Affair	90
Gray Electronics	102
Gregory Electronics	114
Hal-Tronix	37
Ham Radio Publications	106, 113, 124
Ham Radio Center	33, 125
Hamtronics, Inc.	127
Heath Company	25
Henry Radio Stores	Cover II
Holdings Photo Audio Centre	112
Icom	5
Integrated Circuits Unlimited	105
International Crystal	1
James Electronics	101
Jan Crystals	116
Jones, Marlin P. & Assoc.	108
K-Enterprises	83
KE Electronics	96
Kampp Electronics Inc.	88
Trio-Kenwood Communications, Inc.	62-69
Kester Solder	84
Klaus Radio, Inc.	94
Lafayette Radio Electronics	88
Logic Systems, Inc.	122
Long's Electronics	128
Lunar Electronics	83, 123
Lyle Products	116
MFJ Enterprises	2
Madison Electronic Supply	102
Masters Communications	104
Microcomputer Interfacing Workshop	118
Microwave Associates	106
NuData Electronics	116
OK Machine & Tool	93
Optoelectronics	88
Palomar Engineers	116, 118, 120
Partridge (HR) Electronics	116
Poly Paks	98
Prime Electronics	112
RF Power Components	112
RF Power Labs	96
Radio Amateur Callbook	84, 126
Radio World	108
Ramsey Electronics	107
Regency Electronics	93
Unarco-Rohn	92
SST Electronics	118
SAROC	121
Sherwood Engineering	94
Space Electronics	112
Spectronics	97
Spectrum International	114
TPL Communications	114
Tee/Ax, Inc.	122
Ten-Tec	89
Trans Com	104
Tri-Ex Tower Corp.	91
Tristao Tower	122
University Microfilms International	118
VHF Engineering, Div. of Brownian	109
Valley Instrument Products	84
Vanguard Labs	100
Varian, Eimac Division	Cover IV
Vines, James K.	104
Webster Communications	118
Weinschenker	120
Western Electronics	120
G. R. Whitehouse & Co.	100
Wilson Electronics	8, 9
Yaesu Electronics Corp.	Cover III

## EVER WISH YOUR RECEIVER COULD HEAR THE WEAK ONES?

Almost every amateur and commercial VHF/UHF receiver can be more sensitive with these popular preamps. Over 7000 in use throughout the world!

**P8 KIT \$7.95**      **P16 W/T 16.95**

Recommended for mounting inside transceivers — only 1/2 x 2-3/8 inches



MODEL	RANGE
P8-30	20-83MHz
P8-150	83-190 MHz
P8-220	220-230 MHz
P16 (W/T)	Give exact freq.

**P9 KIT \$9.95**      **P14 W/T \$19.95**

Premium model where space permits — 1-1/2 x 3 inches. Ideal for OSCAR!



MODEL	RANGE
P9-30	26-88 MHz
P9-150	88-172 MHz
P9-220	172-230 MHz
P14 (W/T)	Give exact freq.

**P15 KIT \$15.95**  
**P35 W/T \$34.95**

- Available for any band 380-520 MHz
- 20 dB gain



## VHF AND UHF CONVERTERS

- Low noise FET front end
- All common i-f's
- Great for OSCAR!
- Low power drain
- Crystals available for any desired freq scheme



**MODEL C25 VHF CONVERTER KIT (shown) \$25.95**

- Models for 2M, 6M, 10M, 220 MHz, aircraft, com'l, etc.
- Stable cascode rf stage
- 0.3-0.5 uV sensitivity
- 10-20 dB gain
- Compact 2-1/2 x 4-1/2" pcb
- Any i-f 10-50 MHz
- Featured in HR mag article

**MODEL U20-450 UHF CONVERTER \$19.95**

- For 432-435 MHz ssb, atv, OSCAR, 450 MHz fm, aircraft, com'l, etc.
- Economy converter
- Use with P15 Preamp for optimum performance
- Any i-f 10-160 MHz

**XTAL (either of above) \$5.50**

## FM/CW TRANSMITTER KITS



**200 MW EXCITER MODULE KITS**

T40-11 Eleven Channel Exciter for 2M, 6M, or 220 MHz..... \$39.95  
T40-1 One Channel Exciter..... 34.95

**T20 Tripler/Driver Module Kit, 150 mW 2M input, 200 mW 450 MHz output \$19.95**



**RF POWER AMPLIFIER MODULES**

- NO TUNING
- VSWR PROTECTED
- 150 MW DRIVE
- COMPLETELY STABLE

T80-150, 140-175 MHz, 20-25W output, wired and tested, simply connect your cables..... \$79.95  
T80-450, 430-470 MHz, 13-15W 79.95

## TEST PROBE KITS



**ONLY \$7.95/ea.**

TE-3 RF Detector Probe for VTVM, good from 100 kHz to over 500 MHz  
TE-4 Direct Probe for ac/ohms, etc.  
TE-5 DC Probe w/res for 11 meg. input VTVM  
TE-6 Blocking Capacitor Probe for counter, signal generator, etc.  
TE-7 Wideband Detector Probe for scopes  
TE-8 High Z/ Low Capacitance scope probe



**Larsen Antennas**

We have a large stock of these popular whips. Pick the mount and whip which are right for you! All whips and mounts are interchangeable. Request catalog for more information.

LM-150 5/8 wave 2meter whip..... \$23.85  
LM-220 5/8 wave 220 MHz whip... 23.85  
LM-440 Colinear 450 MHz whip.... 23.85  
Q 1/4 wave whip 144-450 MHz 2.65

MM-LM-K Magnet Mount..... \$14.60  
LM-K 3/4" Blind Hole Mount.. 6.35  
GC-LM-K Gutter Clip Mount..... 14.60  
TLM-LM-K Trunk Lip Mount..... 14.05  
AMB-K Trunk Gutter Mount..... 9.10



We have large stock of popular antennas. Call or write for quote or more information.

## VHF/UHF FM RCVR KITS



**VHF MODELS FOR ANY BAND 28-240 MHz**

R60-( ), 0.5-1 uV sens, incl VHF Converter and IF/Audio Boards..... \$64.95  
R69-( ), 0.2-0.4 uV sens, incl P9 Preamp, VHF Converter, and IF/Audio ... \$69.95  
Crystals (We stock common freq and will gladly order specials)..... \$5.50



**UHF MODELS FOR ANY BAND 380-520 MHz**

R60-450, 5-10 uV economy rcvr, incl UHF Conv & IF/Audio Boards only.... \$59.95  
R80-450, 2-5 uV sens monitor rcvr, incl UHF Conv, VHF Conv, and IF/Audio . \$84.95  
R95-450, 0.4-1 uV sens rcvr, incl P15 Pre-amp, UHF Conv, VHF Conv, and IF-Audio Boards..... \$94.95

FAMOUS ANTENNAS **hy-gain** STOCKED IN DEPTH

REQUEST CATALOG FOR MORE DETAILS

14AVQ	10-40M Vertical	\$67.00
18AVT	10-80M Vertical	97.00
18HT	10-80M Hy-Tower Vert	279.95
TH3-MK3	Tribander	199.95
TH3-JR	Tribander	144.50
TH6-DXX	Tribander, 6 element	249.95
2BDQ	80-40M Trap Dipole	49.95
5BDQ	80-10M Trap Dipole	79.95
263	2M 5/8 wave Trunk Lip	28.95
265	2M 5/8 wave Mag Mt	29.95
214	14 el 2M Beam	26.95



**SUPERIOR QUALITY ~ Yet only \$189.95**

IF YOU'VE HEARD THE NEW HY-GAIN 2M HT, YOU ALREADY KNOW IT'S FANTASTIC! WE HAVE THEM IN STOCK COMPLETE WITH CRYSTALS AND ACCY'S

## Inexpensive DC POWER SUPPLIES

Model	Price	Intermittent	Cont
12CB4	\$29.95	2.5A	1.5A
103R	39.95	4A	2.5A
104R	49.95	6A	4A
108RA	79.95	12A	8A
108RM*	99.95	12A	8A
109R*	149.95	25A	10A

\*Indicates model which has panel meter(s)

# hamtronics, inc.


182H BELMONT RD., ROCHESTER, NY 14612

- CALL OR WRITE NOW FOR FREE CATALOG OR TO PLACE YOUR ORDER!
- PHONE 716-663-9254, 9AM-9PM EST DAILY.
- Use your credit card or C.O.D.
- Specify operating freq • Add \$1 shipping and handling.



# Buy an 820S & get a VFO FREE!

Call 1-800-633-3410 for Kenwood

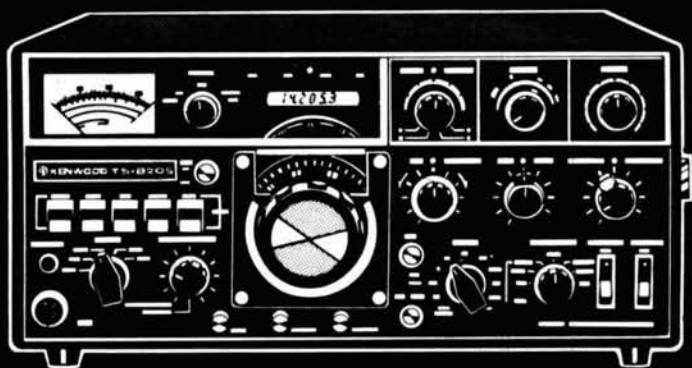

## The NEW KENWOOD TS-820S transceiver

TS-820S features: • Factory installed digital readout • 10 thru 160 meters coverage • 200 watts PEP • Integral IF shift • Solid-state, except for drive and final stages • Noise blanker • VOX circuit • PLL circuitry • DRS dial • IF out, RTTY, XVTR capabilities • Phone patch IN and OUT terminals • RF speech processor • Ask about optional equipment.

**1048.00** is list price. Call Toll-Free to order.

## The NEW KENWOOD VFO-820

The VFO-820 has solid-state construction. It matches the TS-820, perfectly. Features: • Covers bands between 1.8 and 30.0 MHz • Allows controlled cross-channel operation • Built-in RIT circuit • Indicators for both RIT & VFO circuits • Oscillation frequency: 5.0 to 5.5 MHz • Output voltage: 1V ± 3dB (across a 470 ohm load)

**145.00** is list price. Call Toll-Free to order.



## KENWOOD TR-7500 2m FM transceiver

TR-7500 has what you need for 2 meters! • PLL synthesized • 100 channels (88 pre-programmed, 12 extra diode programmable) • Single knob channel selection • 2-digit LED frequency display • Powered tone pad connection • 10 watts HI output, 1 watt LOW output.

**299.00** list price. Call for quote.



## KENWOOD TS-520S transceiver

TS-520S has: • 10-160 meter coverage • Optional DG-5 digital frequency display • New speech processor w/audio compression amplifier • AC power supply (DC optional) • RF attenuator, front panel activated • Provisions for separate receive antenna • Phone patch provisions.

**649.00** list price. Call for quote.



## KENWOOD TR-2200A 2m FM transceiver

TR-2200A features: • Solid-state construction • 2 watts HI output, 0.4 watts LOW output • 12 fixed channels (6 supplied) • ¼ wave telescoping antenna • Rechargeable Ni Cad batteries included • Lighted ch. indicators • Hand mike • Carrying case & strap • Battery charger • DC power plug with lead.

**229.95** list price. Call for quote.

Remember, you can call TOLL-FREE: 1-800-633-3410 in U.S.A. or call 1-800-292-8668 in Alabama for our low price quote. Store hours: 9:00 AM til 5:30 PM, Monday thru Friday.



# Long's Electronics



MAIL ORDERS: P.O. BOX 11347 BIRMINGHAM, AL 35202 • STREET ADDRESS: 3521 10TH AVENUE NORTH BIRMINGHAM, ALABAMA 35234





Years Ahead With Yaesu!

*Introducing . . .*

# THE ALL-NEW YAESU FT-227R 144-148 MHz 800 CHANNEL

**1980's RADIO  
TODAY!**

**"MEMORIZER"!**



**UNDER  
\$300!**

*Compare These Features And You'll Know What We  
Mean When We Say "Years Ahead With Yaesu"*

- one knob channel selection using optical sensing to select 800 channels
- memory circuit that allows instant return to any frequency selected between 144-148 MHz
- large 4 digit LED frequency readout
- fully synthesized frequency control, using PLL techniques in 5 KHz steps
- built-in tone burst, plus optional tone squelch encoder/decoder
- spurious well below minus 60dB requirement—superior cross modulation, overload and image rejection
- standard 600 KHz offsets plus any split within the band using the memory circuit
- automatic final protection, PLL "unlock" protection and busy channel indicator
- selectable 10 watt/1 watt output

*See this sensational new two meter transceiver at your YAESU DEALER now!*

Yaesu Electronics Corp., 15954 Downey Ave.,  
Paramount, CA 90723 ● (213) 633-4007  
Eastern Service Ctr., 613 Redna Terrace  
Cincinnati, OH 45215

YAESU  
**The radio.**

Look over DenTron's low profile, stylized MLA-2500 amplifier. Two EIMAC high-mu 8875 power triodes are the heart of the modularized design. The combination of DenTron's cathode-driven circuitry and EIMAC's 8875s provides simplicity, economy and high power all in one compact package.

Unexcelled for rugged amateur service, the 8875 is a natural choice for DenTron, just as it and other EIMAC power tubes are the choice of most principal manufacturers of amateur, commercial and military communication equipment.

Whether you build or buy your equipment—go EIMAC. The EIMAC name is your assurance of power, dependability and quality. Send today for your free copy of the EIMAC Quick Reference Catalog which provides information on all popular EIMAC products. Write Varian, EIMAC Division, 301


Industrial Way, San Carlos, California 94070. Telephone (415) 592-1221. Or contact any of the more than 30 Varian Electron Device Group Sales Offices throughout the world.


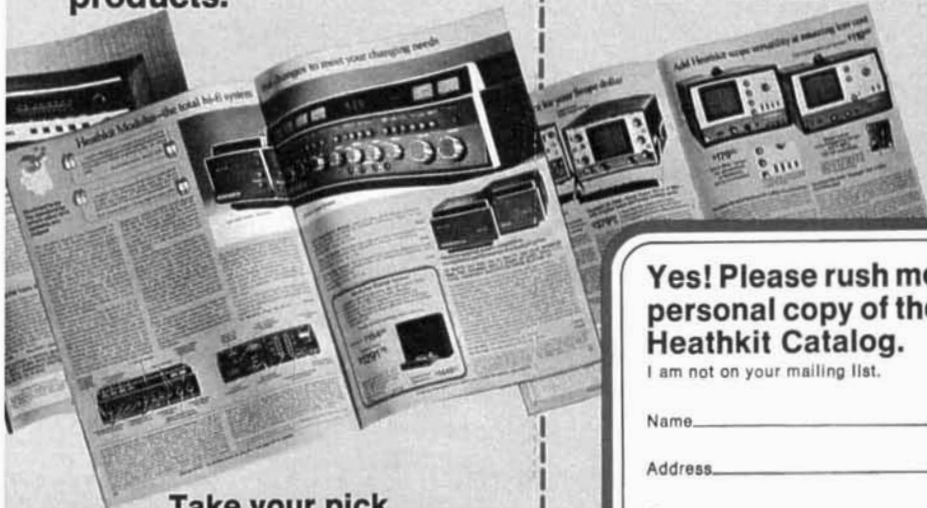
# EIMAC 8875s Power DenTron's MLA-2500 Linear Amplifier.



Send for your copy of the  
world's largest catalog of  
quality kit-form electronic  
products.



Take your pick  
of nearly 400 fun-to-build and  
practical money-saving kits — all  
backed by Heath — world leader  
in better electronic kits since 1947.

**FREE!** mail card now ▶

# FREE!

FILL IN THIS  
CARD AND  
MAIL TODAY

Yes! Please rush me my  
personal copy of the **NEW**  
Heathkit Catalog.

I am not on your mailing list.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

Zip \_\_\_\_\_

Dept. 122-34  
Ham Radio

PC-124

Get your very own copy of the latest

# HEATHKIT

MAIL-ORDER KIT CATALOG

## FREE!

Kits for almost everything in electronics; auto and marine accessories, TV, stereo hi-fi, home products and much more. All are easy to build with crystal-clear, step-by-step Heathkit assembly manuals.



SEND FOR IT TODAY!

**PUT STAMP  
HERE**

The Post Office  
will not deliver  
mail without postage

# HEATH COMPANY

BENTON HARBOR MI 49022