

Mid-Summer Edition

Price, 15 Cents

# RADIO MANUAL

Copyright, 1923, by The Sun Printing and Publishing Association (The Sun and The Globe).



*Published by*

The  Sun  
and The  Globe

NEW YORK



# Confidence

**C**ONFIDENCE is the backbone of this business. From the beginning the policy of the Rova Radio Stores has been *not merely to make a sale but to make a customer*, and our entire organization has been trained along these lines to this end.

With the remarkable improvements in radio the Public's need for an institution upon which it can depend absolutely for reliability and accuracy, was completely fulfilled by the Rova Radio Stores.

The Public immediately appreciated the service by giving us a tremendous volume of business, for which we are grateful.



2 New York Stores  
167 West 18th St. 233 Fulton St.  
Newark Store  
132 Branford Place

*More Interesting ROVA News  
In the Middle of this Book*

# The RADIO MANUAL

A Comprehensive Treatise on Radio Telephone Reception, With Helpful Hints for the Beginner and Constructive Suggestions for the Experimenter

Including Diagrams of the Armstrong Super-Regenerator, Flewelling and Various Forms of Reflex Sets

Compiled By

E. L. BRAGDON  
*Editor, Radio Sun-Globe*

AND

F. C. EHLERT  
*Technical Editor, Radio Sun-Globe*



Published By

THE SUN PRINTING AND PUBLISHING ASSOCIATION  
280 BROADWAY, NEW YORK, N. Y.

1 9 2 3

# General Outline of Radio Manual

General description of types of receiving sets.

## Crystal Sets

How operated.  
Range.  
How to make.  
Selection of parts for crystal sets.  
Effect of wire sizes.  
Importance of sensitive crystals.  
Advantage of crystal sets.

## Discussion of Vacuum Tube Action

### Simplest One Tube Receiver

Range.  
Selection of parts.  
Making of parts.  
Assembly.  
How to operate.  
How this set can be improved.  
Amplification.

### Multi-tube Sets

Range.  
Selection of parts.  
Making of parts.  
Assembly.  
How to operate.  
How this set can be improved.

## Radio Frequency

Explanation.  
How to add R. F. to sets already in operation.  
What may be expected from additions.

## Combination Sets

Crystal and Tube.  
Simple amplification.  
Reflex amplification.

## Receivers with Super-regenerative Basis

Armstrong.  
Flowelling.

## Explanation of Regeneration

## Discussion of Action and Use of Individual Parts

Variocoupler vs. loose coupler and tuning coils.  
Honeycombs.  
Spider-webs.  
Variometers.  
Bank Wound—Long Wave—Couplers.  
Condensers—fixed and variable.  
Grid Leaks.  
Rheostats—high and low resistance.

Potentiometers.  
Batteries—A and B types.  
Use of storage B and dry A.  
Panel materials.  
How to wire set.  
Precautions to observe.

## Short Description of Storage Battery

**How to Charge Storage Battery**  
Home-made rectifiers generally unsatisfactory.  
Connections for commercial chargers  
Costs for recharging at different rates.

## The Best Tube for the Use

Dry Cell-WD11.	UV201A.
UV199	UV216A.
UV200.	UV202.
UV201.	N Tube.

Use of each and its characteristics explained.

## Phones

Operation.  
Selection of.

## Loud Speakers

Description of various types.

## Last Chapter

Latest developments up to date.

# Buying the Radio Set

## Simple Suggestions That Will Help the Beginner Select the Most Desirable Receiver From the Bewildering Array That Confronts Him.

IF, as has been variously reported, there are upward of two and one-half million radio enthusiasts in this country, then the simple, fundamental question, "What kind of a receiving set should I buy?" has been asked at least that number of times. In fact, it is probable that the same question has been asked repeatedly by each neophyte before he could gather sufficient courage to take the initial plunge. For it is a difficult question to answer, and out of ten persons to whom it is addressed there will be on the average four contradicting replies. With this preamble, which more or less will excuse the apparently contradicting statements to be made, the following paragraphs will attempt to simplify the selection of the first set for the man, woman or child who has yet to go through this interesting experience.

There are two general classes of radio receiving equipments. The classification is made according to the type of detector utilized in the outfit, namely crystal or vacuum tube, and while some receivers with crystal detectors have and are selling at higher prices than some brands of sets with vacuum tube detectors, the crystal set is usually considered the cheaper and simpler.

The simplest receiving set that could be employed would consist of a collector wire called an aerial or antenna, a small coil of wire wound on a pasteboard or other insulating tube, a piece of lead ore, called galena, a telephone receiver and a connection to a handy cold water pipe. Such an array of equipment could be purchased complete for \$2, but its ability as a receiver of radio-telephone broadcasts is not considerable. Even with an antenna of high quality

this set would be useless if installed in a locality more than ten miles from a broadcasting station. At this distance the signals, if heard, would be exceedingly weak.

In another particular—that of interference from both broadcasting and code stations—this ultra-simple crystal set has its outstanding drawbacks. Though the broadcasts were heard satisfactorily, the lack of selectivity which is inherent in the apparatus would permit the intermittent dots and dashes of amateur and commercial code stations to interrupt the music and speech. Moreover, it is probable that more than one broadcasting station would be heard simultaneously, thus destroying the programmes of each.

### How to Select the Receiving Set.

In order to form some basis on which the prospective purchaser of a radio set may base his selection, let an imaginary instance be conceived. Brown—the man's name—lives fifty miles from a city, such as Chicago or New York, where there are several broadcasting stations of high power. He has heard about radio from his friends and has decided that he must get a set for himself and family. But as usual each of his friends has an idea of his own. Jones uses a crystal set and hears two stations more or less regularly. He paid \$18 for the complete outfit, including enough wire for an antenna 150 feet long and 40 feet high.

"Buy a set like mine," says Jones. "You'll hear the two best stations around here. You won't have to buy a storage battery or dry cells. There are no tubes to burn out."

Adams, his next door neighbor, is a man of means. And now, after

gradual progressive stages, he is sporting a four tube receiver that is a "Rolls Royce" when compared to the "flivver" crystal set of Jones.

"Don't put your money in a cheap set," he tells Brown. "That's the way I started and now the set is gathering dust in the attic. A radio set is no good unless you can reach out two or three hundred miles every night and pick the station you want to hear. If you want to go at it right, pay out your good money for a good set. Pay \$250 if necessary."

And lastly, as an exponent of the middle course, is Brown's lodge friend Burrows. Burrows was given a single tube receiver by an appreciative relative and since its coming has paid out only a few pennies for upkeep. His set is operated from dry cells and so far he has used the set two or three evenings a week for four months and it seems to work as well as ever. He hears the city stations loud and clear, and one night—he always relates this accomplishment whenever his friends commence their radio fanning bee—one night he happened to be listening in around midnight when, lo and behold, he heard a man's voice saying, "This is Station WBAP, Fort Worth, Texas."

"Eight hundred and fifty-six miles by air line," he adds, "and with a single tube, too."

Is it any wonder that Brown is radio perplexed? One friend recommends the \$18 outfit and the other the \$250 set.

If the bewildered man could talk with a broadminded, unbiased radio expert this would be the gist of the talk:

How much do you want to spend on a radio set? Yes, I know you want to spend as much as is neces-



## THE RADIO CENTER OF NEW YORK

THE LARGEST AND MOST COMPLETE STOCK  
OF STANDARD, RELIABLE AND TESTED

RADIO APPARATUS and PARTS

IN GREATER NEW YORK

*Honest and Dependable Merchandise  
At Prices That Are Right*

WE HAVE ALL THE HARD-TO-GET RADIO SUPPLIES

Let Us Answer Your Radio Problems  
Free Instruction by Acknowledged Expert

# Electric Service Engineering Co.

105 West 47th Street Telephone Bryant 2743-2744-2030 New York City

### KEY TO SYMBOLS OF APPARATUS

Alternator		No Connection	
Ammeter		Coupled Coils	
Antenna		Variable Coupling	
Arc		Crystal Detector	
Battery		Galvanometer	
Buzzer		Gap, Plain	
Condenser		Gap, Quenched	
Variable Condenser		Ground	
Connection of Wires		Switch, D.P. D.T.	
Inductance		Switch, Reversing	
Variable Inductance		Telephone Receiver	
Key		Telephone Transmitter	
Resistance or Leak		Thermoelement	
Variable Resistance		Transformer	
Switch, S.P. S.T.		Vacuum Tube	
Switch, S.P. D.T.		Voltmeter	
Switch, D.P. S.T.		Magnet	
Variometer		Electromagnet	
Slide Tuning Coil		Induction Coil	
Multiple Point Switch			
Choke Coil			

sary to get a good outfit. But how much could you put out right now without missing it? Do you want to spend \$250, as Jones did? No? Well, would \$100 be too much? Still a little high? All right, let's compromise on \$65. Fine. Now listen to me.

#### The Handy Man Can Build His Set.

If you were a mechanic or were handy with tools, could read simple drawings and follow instructions that must of necessity be semi-technical, you could build your own set from purchased parts. The completed set would be twice as extensive in scope as a purchased set for the same money. Not twice as good; I don't want you to get that idea. It might not be half as good. 'Twould all depend on the degree of skill you used in assembling and selecting the parts. What I mean is that with the \$65 you could buy a receiving set having one vacuum tube, batteries, head 'phones, and antenna material, while for the same amount expended in parts you could assemble a set consisting of two vacuum tubes, the same batteries and antenna wire, and so forth. A two tube set, you know, is better for distance and for loudness. The second tube magnifies, or, as they say in the trade, amplifies the sound as it comes from the first tube.

But I know you have not had the training that would make it advisable for you to assemble a receiver of this type. So you should buy one complete.

With \$65 to spend, you should forget all about the crystal type of receiver. A vacuum tube set is your goal.


#### Best Receivers Are the Simplest.

Suppose you get out among the shops and see the radio sets on display. For one thing you will be surprised at the wide range of prices for what seems to you to be identical sets. The similarity is the same as is found in the clothing industry. There are suits of wool and suits of shoddy. To the man in the street there appears to be no difference between the two goods. But time and wear soon differentiate between them.

The "all-wool" radio sets are usually the simplest in construction and design. Skilled engineers have "cut"

them until all non-essentials have been eliminated. Complete control is secured with the minimum number of knobs and dials.

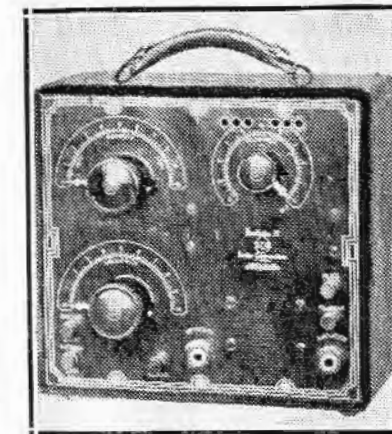The "shoddy" set, on the other hand, is more apt to be housed in a



One of the Newer Sets. Flashlight Batteries Operate the Tubes.

beautiful cabinet and equipped with more dials than the switchboard of a submarine. If anything, this type of set is liable to be the larger of the two, for its builders know that the few extra dollars spent on a larger panel and a slightly larger cabinet make an infinitely better impression on the newcomer.

The "all-wool" set can be taken home, connected to an antenna and ground and made to work, merely by following the few instructions that come with it. Six months later the



A Self-Contained Set. The Loop of Wire in the Top of the Cover Is the Antenna.

set will still be working, even better if anything.

The "shoddy" set gives no trouble as far as fundamental connections are concerned but when it comes to operating it—

The beginner finds that the multiplicity of dials is terrifying. After a sound is finally heard in the 'phones the poor man is at a total loss as to his next move. Five or more dials confront him. Which shall he turn! He takes a chance, reaches for one of them, twists it ever so slightly—a hiss, a squeal, a cluck and the sounds disappear. Whatever he does from that point on brings no results, so he turns everything off and starts again from zero.

Finally if through sheer persistence he brings in a station so that it is more or less plain he discovers that the slightest movement of his hand or body distorts the sounds into squeals of divergent pitches. And any radio man—beginner or expert—will tell you that there is mighty little enjoyment in listening to a concert while holding the hands and body in a rigid position.

Perhaps this little story will emphasize the importance of making sure that a radio receiving set is a good one. It also emphasizes the advantage of paying a bit more for the same kind of set in order to get one which is fool-proof.

To get back to that \$65 which is waiting to be spent for a receiver. In company with an expert the prospective owner goes to a radio shop and finds that he can buy a single-tube receiving set complete with a pair of head 'phones and all the necessary batteries for \$40. The set has two or perhaps three controls. This price includes a hundred feet of stranded copper wire, some heavily insulated wire, several porcelain insulators and a funny looking device, called a lightning arrester.

The expert explains that this receiving set uses a vacuum tube which has a filament lighted by an ordinary dry cell—the kind of battery that rings the door bell at home. This feature makes it unnecessary to buy a bulky and expensive storage battery.

#### The Ideal Set Contains a Loud Speaker.

With only \$40 spent there remains a balance of \$25. If the buyer is a family man there is only one answer to this riddle, viz.: use the money to buy a second pair of head-phones. A loud speaker cannot, as a rule, be operated from a receiving set having only one vacuum tube, hence if there is more than one person in the family there will be frequent calls for two sets of 'phones. Two sets can

be attached to a single receiver without reducing the strength of the signals or affecting the tone.

In the preceding paragraph a statement was made concerning the use of a loud speaker on a radio receiver. The ideal set, it should be mentioned here, incorporates a loud speaker. In the beginning the head 'phones are satisfactory enough, but as the first novelty wears off there will come a desire for a loud speaker. Head 'phones require the listeners to sit near the set and conversation is impossible.

Providing that the owner lives within 25 miles of a powerful broadcasting station, a loud speaker may be used on a receiver comprising two bulbs, that is, a detector bulb and a second bulb to amplify the detecting sounds. But for general purposes and to use the loud speaker on stations a hundred or more miles away, two amplifying bulbs are advisable.

Because of the foregoing facts there are few receiving sets made with two bulbs. After the single bulb set comes the three-tube set.

The three-tube outfit may consist of vacuum tubes that are operated from a storage battery or the three tubes may all be of the dry cell type, with one dry cell attached to each tube.

The three-tube receiver is an exceptionally good one for the average installation. If the unit is well designed, this set when used with an outside antenna should enable the owner after a little experience to hear on the loud speaker all broadcasting stations within 100 miles and on the 'phones all stations within 1,000 miles.

In the majority of three-tube sets provision is made for the use of either one, two or three tubes according to the strength of signals desired. The change from one to the other combination is effected by the simple insertion of a small plug much like that used by the telephone operator on a telephone switchboard. Some sets are even arranged so that the insertion of the plug automatically extinguishes the vacuum tubes that are not in use.

At first thought it may seem strange that the amplification of signals is not continued beyond the two amplifying tubes. The novice may wonder why this strengthening of signals is not continued by adding tubes until even the weakest station, perhaps those clear across the

continent, is brought in at loud speaker volume.

The answer is simple. These amplifying tubes are not specialists in their field. They refuse to be selective. They amplify everything that comes along. And not only that, but frequently they amplify undesirable sounds in greater proportion than broadcast sounds.

Then again the tubes themselves are not silent in operation. In the very act of amplifying the sounds they produce other sounds which are then passed on to the following tubes, where they are further amplified along with the vocal and instrumental sounds which originated in the detector tube.

#### Amplification Limited to Two Stages.

It has been found through extensive trials that two stages of amplification after the detector are the limit. Beyond that the foreign sounds begin to predominate and drown out the musical notes.

This amplification by the two tubes which follow the detector does not represent the ultimate limit in the magnification of radio signals. By the system of "radio frequency amplification" the electrical impulses as they enter the receiving set may be amplified many times before they strike the detector. This form of high frequency amplification may be continued through two to five or even ten or more stages. Unfortunately, however, this method of amplification is not so efficient nor so productive of increased volume as the "audio frequency amplification." The limitation is presented by the design of vacuum tubes. As this limiting feature is studied and the tubes are improved the use of radio frequency amplification will increase. And as the amplification increases, the efficiency of the set will increase, local stations will be received with greater volume on fewer tubes and distant stations now too weak to be heard will come in as loud as local stations do now.

#### Use of Radio Frequency Amplification.

During the last year the number of receiving sets using one or more stages of radio frequency amplification in conjunction with one or two stages of audio frequency amplification has increased. It is this type of set which now will be discussed.

In general the use of a single stage of radio frequency amplification is not considered warranted by the results obtained. This is due to the fact that when radio frequency is employed it is seldom advisable to utilize the regenerative feature. That is, since the effect produced in a circuit by regeneration clashes with the action of the same circuit when radio frequency is being employed, the regeneration must be eliminated. But the increase in signal strength with one stage of radio frequency amplification is not quite equal to that obtained with regeneration. Therefore, say experts, why drop one thing to utilize another which is not so satisfactory?

But this objection does not hold in every instance. The single step of radio frequency amplification will help but little on local stations, but it will assist greatly on signals from distant stations or on weak impulses from nearby stations. This last named feature comes in handily when an outside antenna is not possible. In such cases a loop of wire containing about ninety feet of conductor arranged in the form of a square will absorb so little energy that the detector—a sluggish individual—will neglect to catch it. But if a stage of radio frequency is interposed between the antenna and the detector this anemic energy will be magnified and made virile enough to operate the detector.

There are excellent receiving sets on the market using one stage of radio frequency amplification, a detector and two or three stages of audio frequency amplification. The cost complete with tubes and batteries varies from \$125 to \$200.

#### Reflex Receivers Build Up Energy.

Still another type of receiver is the reflex receiver, so called because of the fact that the energy from the antenna does not pass in progressive stages from detector through the audio frequency amplifiers, but instead is passed back and forth from one stage to those preceding it. By so doing a greater amplification is possible without additional tubes, since each tube is amplifying at both radio and audio frequencies.

As would be expected, the successful operation of a reflex receiver depends on the exact and proper adjustment of the apparatus in each separate circuit.

# The Aerial and the Ground

## How to Select the Proper Type and Location—How to Arrange for Stringing the Wires and Installing the Precautionary Measures Demanded by Insurance Companies.


The problem of the antenna, once a serious one, is no longer such a determining factor in radiophone reception. Better methods of transmission, higher power at the transmitting stations, and more efficient receivers have made of the antenna one of the lesser parts of a receiving set.

There was a time when the antenna had to be as high as possible if any kind of receiving was to be done. But now, in the phrasing of the times, "anything goes." An outside aerial works best and will give the loudest signals, but if the radio enthusiast lives in an apartment house with no access to the roof or in a crowded section of the city or town where a stretch of wire is out of the question, he may still enjoy radio broadcasts, not only of local stations but from distant stations as well, merely by utilizing one of the other forms of antenna.

The ideal antenna still remains as of old: a single wire as high as possible and as long as the wave length will permit.

The length of the antenna is determined by the shortest wave length to be received. In broadcasting circles this is now about 250 meters. To work efficiently the natural wave length of the antenna should be something less than this figure. Roughly, the fundamental wave length of any single wire antenna can be figured by multiplying its length—to which must be added the length of the lead-in wire and that of the ground connection—by the number 1.4. This will give the result in meters. Thus, if the lengths of antenna, lead-in and ground combine to give 100 feet, the wave length would be 140 meters. Therefore it can be seen that the very longest antenna must not have a length greater than 175 feet. Usually this means that the main portion of the antenna cannot be greater than 125 feet in length.

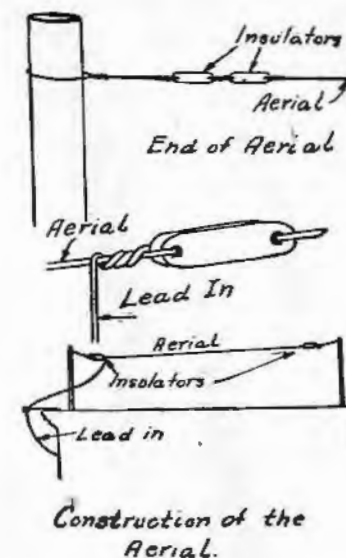If it is possible to set up an outside antenna a few simple rules should



be followed: Keep the wire away from trees. If a tree is used for one end-support arrange the wire with a rope so that it hangs free and clear of the branches.

#### Erect Antenna Free of Trees and Wires.

Never run an antenna under or over other wires. One of the wires may break and drop across the other, causing an unknown amount of damage.

If electric light wires are near the antenna it is best—but not absolutely essential—to place the antenna wire at right angles to the other. If this is not done the receiving set is apt to hum continually, due to magnetic induction.

Choice of wire for the antenna need not be a serious problem. Almost any kind will do. Even iron wire has been known to make a workable aerial. Stranded copper wire is best, copper clad is next and solid copper the easiest to obtain. Any size from No. 14 to No. 18 will do. No. 16 is ideal, because of its ample surface and its medium weight. No. 14 will give more surface and is stronger, but its weight

is against it, while No. 18 is so small that a wind storm is apt to rupture it. If the wire is insulated so much the better. The insulation is helpful rather than harmful, except in so far as it adds to the weight.

The antenna should be insulated at its ends with special insulators. Usually these are of porcelain or of a fibrous texture. Ordinary cleats or knobs such as are used in wiring the house are suitable for this work. When placing the antenna end in a tree arrange to have the insulator well away from the branches, otherwise its exact position is immaterial.

After the antenna comes the lead-in. This is another wire similar in size and composition to the main wire. To make the connection between the two scrape a place bare on the main wire and bare one end of the lead-in. Twist the lead-in tightly around the main wire at least ten times. Make a neat and effective job of it by arranging each turn close beside the preceding turn. When completed solder if possible. A hot soldering iron heated over the gas stove and rushed out to the antenna before it cools will do the work. Otherwise a blow torch is necessary. Place a little soldering flux or paste on the joint, hold the iron beneath the joint, and touch the strip of solder to the wire as it is heated. If it is not possible to solder the joint, wrap it tightly with tinfoil and then cover thoroughly with several layers of electricians' insulating tape. This will be effective for several months.

A still better way to arrange for the solderless lead-in is to make the antenna and lead-in in one piece. This merely means that the conductor should be run through an insulator at the house end, tied around the insulator with a short piece of wire to prevent a back and forth movement, which would eventually cut through the copper by friction, and then carry the wire directly to the lightning protector.

There is always some discussion


as to the best type of antenna to use; that is, whether it should be perfectly flat, whether it should slope up or down, and whether it should be pointed in any particular direction. In reality the best type of antenna for radiophone reception is the one that is easiest to erect. An antenna that is 35 feet high at its farthest end and 15 feet high at its lowest end will be no better nor worse than one which is 35 feet high along its entire length.

As for direction, this is another subject that allows considerable leeway. Certain types of antenna are directional, but this directional effect refers more to the minimum signal than the maximum signal strength. If there is a navy station near by it would be best to place the antenna so that it runs at right angles with the compass direction of this station.
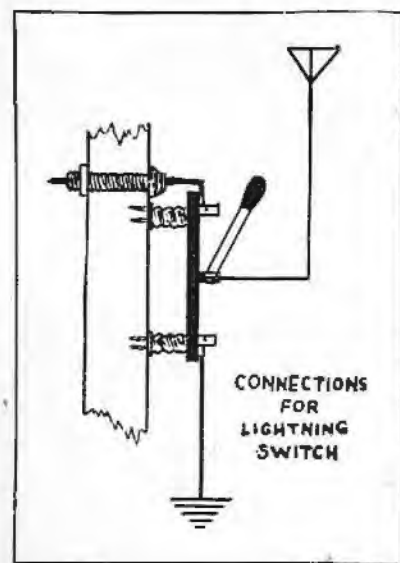
#### Lightning Protector Belongs on the Outside.

But the beginner should not think that he is to gain greater signal strength by pointing his wire at a particular station. That station would be received with the same approximate strength if the antenna were to be pointed 60 degrees away from the straight line connecting the receiver with the transmitter.

In connecting the lead-in to the antenna, if the two are separate,



follow out the same idea. Make the connection where it is handiest. If this point is 20 feet away from the near-end make it there. The only effect will be to reduce the fundamental

wave length slightly, which is a benefit rather than a handicap.

Every outside antenna should have a lightning protector, not to take care of direct lightning strokes, but to drain the antenna of accumulated charges that appear there winter and



How the Antenna Wire Is Connected to the Insulator.

summer. Insurance companies require this protection and good sense demands it. The cost is little and the self-satisfaction is immense. Buy one that has been approved by the Board of Fire Underwriters. The announcement will be found on the outside of the box and also on the arrester. Put it up according to specifications and forget that there ever was such a thing as lightning. You won't need to be told to keep away from the receiving set during a thunder storm. The noises that then will be present are the best assurance that you will shun it at such times.

If the radio man lives in a thickly populated and built-up section he is permitted to place this protector inside the house, but it is by far the best policy to place it on the outside if it is in any way possible to do so. Build a small box, cover the top and sides with tar paper or oilcloth, and place the protector inside. Bring the lead-in to the box and carry a wire from the proper binding post on the protector straight down to the ground. The best ground for this purpose is a pipe 6 feet long driven into the earth with the wire from the protector securely soldered to it.


This ground wire should be at least No. 4 in size.

Bring another wire from the lightning protector in through a porcelain tube into the house. The hole for this tube may be drilled straight through the clapboards or siding or it may be bored through the window casing. The hole should slope upwards so that water from the wire will not drain in through the tubing. This is the wire which leads to the antenna post on the receiving set.
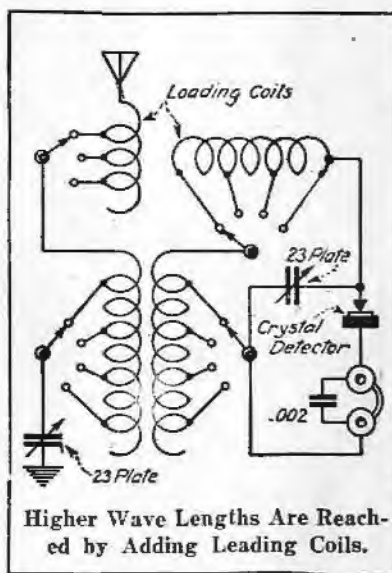
#### Ground Wire Should Be Short as Possible.

From the ground binding post of the set carry a wire about No. 14 in size to the nearest and best ground. This will probably be a cold water pipe. But if the nearest cold water pipe is 20 feet or more away and there is a steam or hot water radiator nearer utilize that. Ordinarily the effectiveness of these heating systems as a ground does not rank with that of a cold water pipe, but the advantages in the latter are overbalanced if the ground wire must be more than 20 feet in length to reach it.

Use heavily insulated wire for the ground and attach it to the pipe in the same manner as the lead-in was attached to the aerial. A ground clamp, purchasable at any electrical store, will simplify the ground connection.



Keep away from gas pipes as grounds. Too often there is an insulating bushing near the gas meter which prevents the gas pipe from being a real "ground."

# The Crystal Set

## How the Simplest Receiving Set Operates, When It Should Be Used, and How a Workable Outfit Can Be Made at Home With a Few Tools.

In entering upon the radiophone as a hobby, the beginner is confronted with a tremendous problem in the choice of apparatus. He may buy the parts and build his own receiving set and transmitter; he may buy the separate pieces of apparatus, all finished and ready to be connected with other instruments to form a complete set; or he may buy a complete receiving set and sending set wired ready to be used.

If the average beginner is only interested in radiophone receiving service and does not care to be troubled with even an elementary knowledge of radio, then by all means the simplest type of radio apparatus is urged. In that event it is well to purchase a complete receiving set already wired and as compact and self-contained as possible. Such a set need only be connected to the aerial and ground for immediate results.

If the layman wishes to do a little experimenting and thereby master slowly the theory and data of radio it will be well for him to purchase separate radio units, each one com-

plete with some suitable receiver. All that is necessary is an aerial, which for this purpose may be a single wire elevated twenty or more feet off the ground and extending about 100 feet. The use of this aerial or antenna is to absorb the energy in the transmitted radio wave, concentrate



The Galena Crystal Requires a Fine Contact Wire.

it and redirect it into the receiving apparatus. The aerial upon being erected should never be longer than 150 feet. There is no advantage in running a longer wire, for the simple reason that the wave lengths of radiophone stations lie between 285 and 492 meters and it is best to have the natural period of the aerial as near as possible to the average of these values.

Should the aerial be longer than 150 feet it will be necessary to insert a variable condenser in series with the antenna to lower the wave length of the aerial. This oftentimes decreases the efficiency of the set.


When placing the aerial in position the ends should be well insulated by attaching small antenna insulators a few feet from the extremities. A well insulated aerial will exhibit a great gain in efficiency, especially when seeking stations at long distance.

Aside from this simple aerial a ground connection is essential. In cities or towns an excellent ground connection can be made with water and steam pipes. The best means

for making this connection is through the use of a standard ground clamp, which can be purchased from any electrical or radio shop for a few cents. In homes where a meter measures the water the meter should be short-circuited, as shown in the sketch, using heavy wire, about No. 4. Should there happen to be other water pipes near where the first ground is made, it would be advisable to connect them all with copper wires or strips. This would increase the efficiency of the ground.


Under certain circumstances it is not an easy task to find a good ground, especially in rural districts. One form can be made by taking an old wash boiler and soldering the ground wire to one of the handles or sides. The boiler should then be sunk a few feet in the ground or, better still, lowered into an abandoned well. Should it happen that none of these grounds can be utilized there is the cistern or water pump in the yard to which the ground wire can be soldered.

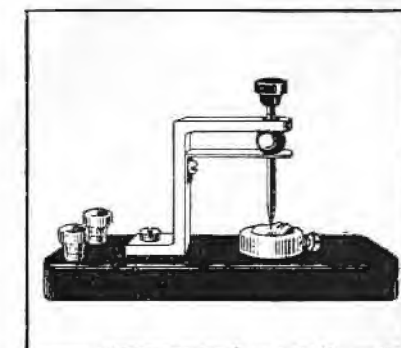As will be explained in detail further on, the receiving set to use de-



Carborundum Works Best With a Stiff Point.

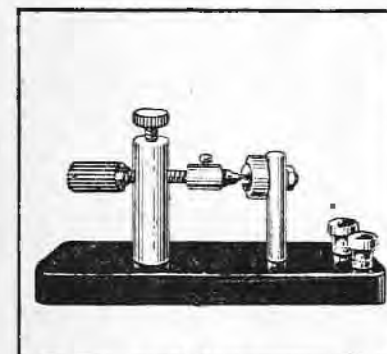pends entirely on the distance between the receiving station and the broadcasting station. Thus, within a twenty-five mile range a simple crystal receiving set will do. Beyond this range and up to seventy-five miles a better receiving set, with storage battery or dry cells to oper-



The Perikon Detector Consists of Two Minerals in Contact.

plete in itself, but arranged to permit its use with other units.

Some manufacturers to-day offer the parts for a complete receiving set, thus facilitating the work of the man who builds his own receiver.

Radiophone service of the present is available to every one provided

ate the vacuum tube detector which replaces the crystal detector used for shorter ranges. It must be understood that crystals are good only for a range of approximately twenty-five miles.

After erecting the aerial and securing a good ground the next step is to consider the receiving equipment. The simplest receiving set comprises a crystal detector and telephones. The detector is a device which changes the frequency of the incoming waves from radio frequency to audio frequency, so that it may be heard in the telephone receivers. While the crystal detector is far more sensitive than the earlier forms of detectors employed during the pioneer days of radio, it is not nearly as efficient as the vacuum tube, which is explained at another place in the Manual further on. However, the crystal detector is inexpensive and may be used with the simplest equipment. Another advantage is that with most of the crystals used to-day no batteries are required.

The simplest receiver, therefore, consists of a ground and antenna connected to a crystal detector and a pair of head telephones in parallel. At short distance from a powerful broadcasting station this outfit is satisfactory, but where two or more stations are in operation some means must be added whereby the receiver can be made selective or, as the act is described, tuned.

There are several methods of tuning devices now in use. One of these is the inductance coil, which consists of fifty or more turns of wire wound in a single layer on a solid tube, three or four inches in diameter, and

provided with some means for varying the number of turns of wire which are to be used.

A method of varying the number of turns is a sliding contact which moves over a path scraped bare along the turns of wire. The adjacent wires must, of course, be insulated from each other and the proper contact afforded between slider and wire.

#### Making the Tuning Coil for Crystal Sets.

In constructing the tuning coil first secure a cardboard tube about three inches in diameter and eight inches long. The cartons containing cracker dust or oatmeal are quite suitable. Next purchase about one-half pound of number 22 single cotton covered wire and two pieces of wood five inches square and one-half inch thick, the latter being needed for the end supports.


Buy two brass rods, one quarter inch square by nine inches long, and two sliders to fit the rods. Secure also one one-eighth inch round brass rod nine and one-half inches long, threaded for a short distance at both ends and fitted with nuts. Four binding posts and four round head brass wood screws complete the list of necessary parts.

The insulating tube is first given a coat of high grade shellac. When this becomes "tacky," the wire should be wound on. Begin one-half inch from the end and wind on the wire evenly until a point is reached one-half inch from the other end. Another thin coat of shellac will hold the wire in place. Find the exact centre of the end pieces and

with a compass draw a circle equal to the inside diameter of the tube. Within the bounds of this circle on both ends fit a crosspiece. Drill one one-eighth inch hole in the two corners of each end piece. In these holes fit the binding posts, the posts projecting from the side opposite to that occupied by the cross pieces.

Now put the ends on the coil, insert the one-eighth inch brass rod through the centre holes and screw up the nuts until the coil and the ends make a firm unit. Connect the right hand end of the coil to binding post G and also connect post G with post 2. Drill one-eighth inch holes one quarter inch from each end of the slider rods. Put the sliders on the rods. Fasten one slider on the top and one on the side of the coil. Connect the top slider rod with binding post marked A, and the slide rod with post 1. The instrument is now complete. Its function is to adjust the wave length of your set in the wave length of the transmitting station. By moving the slides, thereby adding to or subtracting from the number of turns of wire in the circuit, the inductance, which is one of the wave length determining factors, is accordingly increased or diminished. This tuning coil will give a wave length range from 200 meters to about 600 meters.

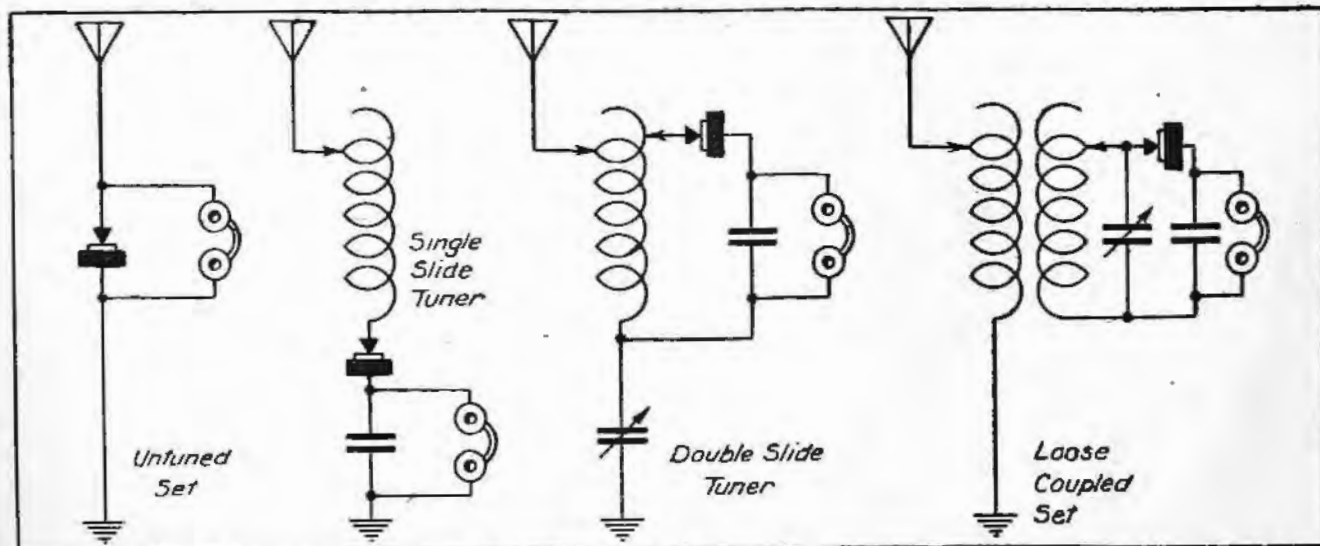Two sliders on the coil will permit greater selectivity; in fact, the tuner then operates like an auto transformer, the turns between the aerial slider and the ground end of the coil considered as the primary and the turns from the ground end of the coil to the other end of the slider considered as the secondary. Some-




Four Familiar Forms of Tuning Units for Crystal Sets.

times a variable condenser connected in the ground lead will be found to sharpen the tuning.

Still greater selectivity in tuning may be obtained by using a loose coupler or variocoupler.
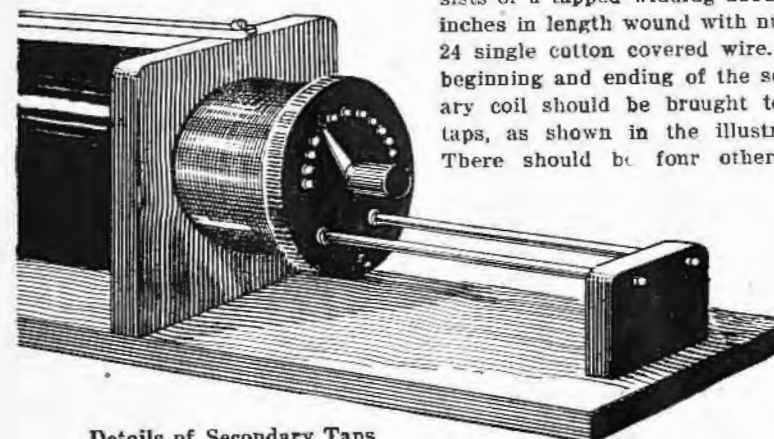
#### Principle and Construction of Loose Coupler.

Although a little more complex in construction than the tuning coil, the



Details of Secondary Taps

loose coupler is superior to it in many ways. Finer tuning and closer coupling is possible. This means greater selectivity and less interference from powerful stations. Signals are somewhat stronger because of this selectivity.

The loose coupler may be classed as an improved type of tuning coil. It has two windings, primary and secondary. The primary or outer coil is usually wound on a cardboard or composition tubing with a large sized wire, while the secondary is wound on a smaller tube with the smaller wire. The secondary is designed so that it can slide in and out of the larger tube or primary.

#### Constructing the Loose Coupler.

In constructing the loose coupler two tubes will be needed, one large one for the primary, and one smaller one for the secondary. If a piece of composition tubing is handy it is much better. A piece of tubing measuring four inches in diameter and about eight inches long will be needed. A tube which will fit inside of this tube with a clearance of about one-fourth or one-half inch will then be needed for the secondary.

Both primary and secondary tubes should first receive a good coat of

shellac. The primary tube is wound with one layer of number 22 single cotton covered wire for about six inches of the primary tube, leaving a clearance of about one inch at either end. A thin coat of shellac will serve to hold the winding in place.

White or orange shellac can be used if thinned down with a little wood alcohol.

The winding of the secondary consists of a tapped winding about four inches in length wound with number 24 single cotton covered wire. The beginning and ending of the secondary coil should be brought to two taps, as shown in the illustration. There should be four other taps

useless, since they would rub against the inside of the primary tube. There is another reason. The end of the secondary tubing is fitted with a wooden head carrying a knob and switch points connected to the tapped sections. It is more convenient to bring the taps to this head from the inside than from the outside of the tube. Two binding posts make connection with two flexible leads. There are two brass rods for the secondary tube to slide on. The primary is, of course, suitably mounted on end pieces and provided with a rod and slider. Two rods and sliders can be used, although there is but slight advantage in so doing.

#### Winding the Tubes.

One thing that must be watched when winding the tubes is the direction of the winding. The two coils should be wound in the same direction. The wires should travel as though the winding was carried out on one coil and the tube cut in two later on.


#### Description of the Variocoupler

The feature of the variocoupler is the employment of the rotor for the secondary in place of the sliding coil. The rotor, which is ball shaped, is mounted so that it can be revolved through ninety degrees to change the coupling between the primary and secondary winding. This acts the same as withdrawing the secondary from the primary, as was done in the

taken from points in between the two taps mentioned.
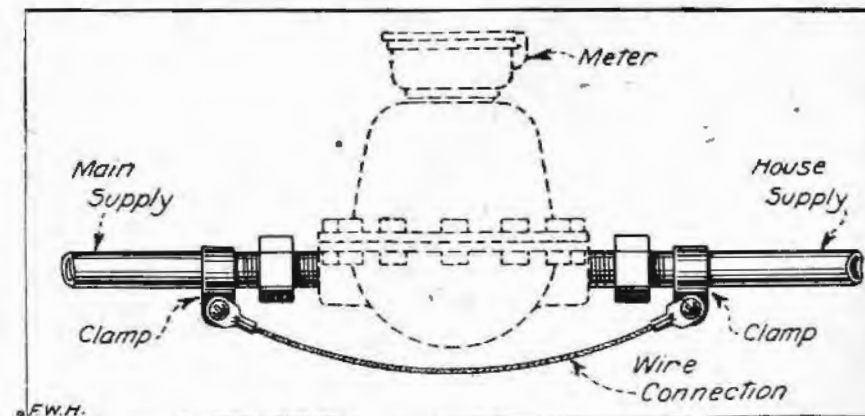
#### Method of Tapping the Coupler

Taps are taken from the secondary in a different manner than usual. Instead of bringing the tap out on the surface of the tube, a hole is punched at the point of tapping and a loop of the wire is forced inside of tube and drawn out for about six inches. The



A Loop of Wire Around the Meter Will Improve the "Ground."

Loop is then twisted and the winding continued for another half inch, when the tapping is repeated. The reason for the manoeuvre is that the secondary must slide inside the primary tube, and outside taps would be

loose coupler. Saving in space, together with simplicity of mechanical construction, are gained by this method of varying the coupling between the coils. It is not necessary to tap the secondary coil, as the in-

ductance is varied by other means, as will be later described.

The primary consists of a tube of insulating material approximately four inches in diameter and five inches long. It is wound with sixty turns of number 22 single cotton covered wire, in one even layer. The winding is then tapped off on the 1-10-20-30-40 and 50th turn. They are tapped off from one to the tenth turn. This then will give six taps of ten turns each and ten single taps. The tapping is carried out diagonally along the tube to make it easier to carry connections from the primary to the taps on the panel.

A quarter-inch hole is drilled through the primary tube for the secondary shaft bearing. This hole should be one-half inch from the top.

#### Making the Secondary of the Variocoupler.

A three-inch rotor ball should be purchased from a radio shop. If one cannot get a three-inch rotor ball a piece of insulating tubing one and one-half inches long and of such diameter as to allow it to rotate freely within the primary tube will suffice. On this should be wound forty to fifty turns of number 23 or 24 single cotton-covered magnet wire. A quarter-inch shaft is then inserted through the hole in the primary and then through the centre of the secondary tube and fastened with lock nuts. The shaft projects through the hole in the primary and a knob and dial fastened to the shaft end. Connections from the secondary winding is made by pieces of flexible cord twisted about the shaft. Enough slack should be left in the pigtail to allow the secondary to rotate freely inside of the primary through a 180 degree angle.

#### Selection of Parts for Crystal Sets.

If no provision is made for tuning, a receiving set must perform to a low order of efficiency. Furthermore, all signals come in at the same time if several transmitters happen to be working in the immediate vicinity. By providing the simplest kind of tuning device the efficiency of the crystal receiver is immediately improved.


There are several types of tuning devices, most of which were described in the previous pages. We have explained the one- and two-slide tuning coils and the inductive coupled

receivers employing the loose coupler or variocoupler. Most crystal sets are of the direct coupled type, with the sliding arrangement on the tuning coil.

There is still another element other than inductance which is used in vary the wave length. This is

parallel to the coil, the wave length is increased in proportion to the amount of capacity used. The value of the condenser lies in the fine adjustment of which it is capable.

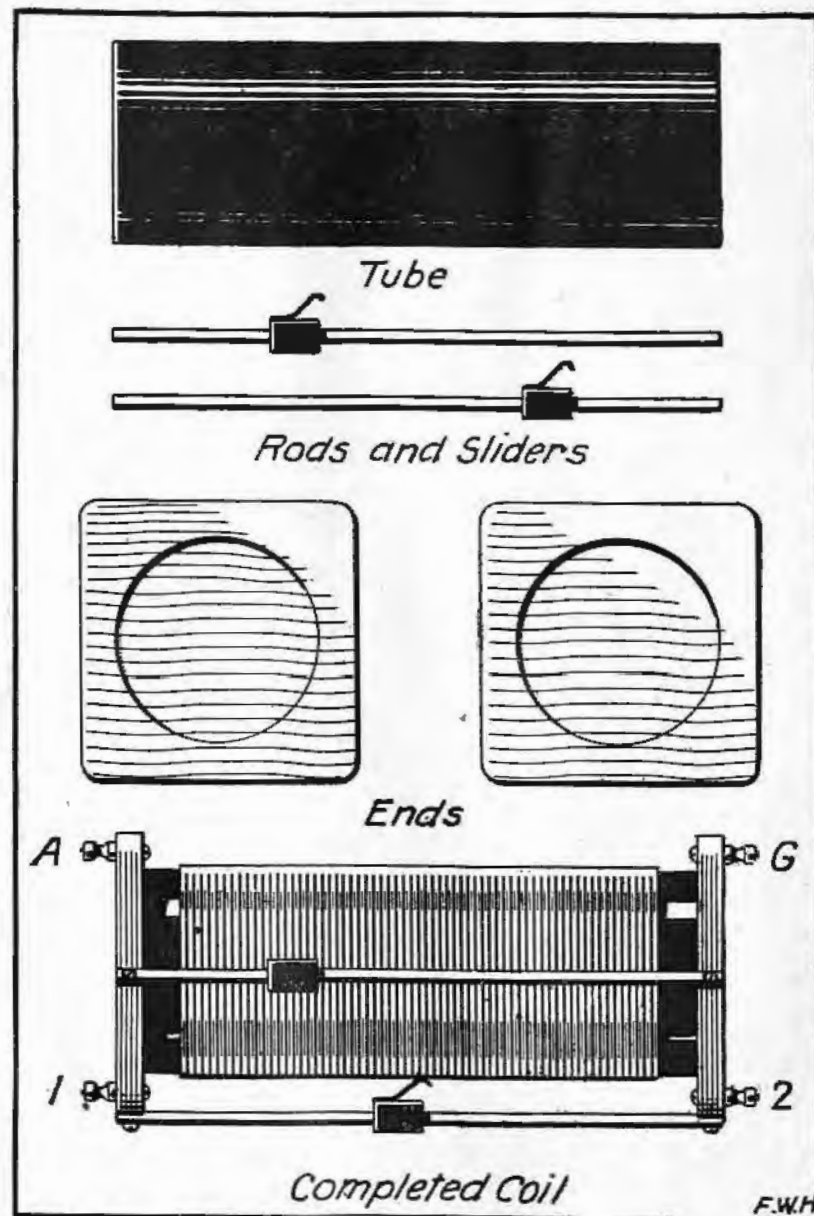A crystal detector ordinarily consists of a mineral crystal, set in a suitable cup or clamping device. Con-



Detail View of Parts of Loose Coupler.

capacity. Capacity is supplied by an instrument called a condenser. The condenser may be either fixed or variable.

Various forms of variable condensers are available, some with movable and fixed plates hinged so that one set of plates is moved toward or away from the other set of plates. When a condenser is placed in series with a coil of wire the wave length is reduced, and when placed in shunt or

tact is made with the crystal by means of a short piece of springy steel or bronze wire. The crystal is set in an easily fusible alloy, such as Woods metal.

The operation of the crystal detector is based upon its uni-directional or one-way conductivity. If the wire or catwhisker be brought into contact with an appropriate spot on the surface of the crystal, the high frequency currents will traverse the

device in one direction far more easy than in the other.

A good crystal will have many sensitive spots, whereas a poor sample will contain relatively few.

There are many crystals used for receiving radiophone signals. The principal ones are galena, silicon, carborundum, zincite-boroite, iron pyrites and copper pyrites. Some of these minerals need an external battery for best action, but the majority do not. Of the different crystals used galena or lead sulphide is probably the most common. It requires no battery current whatsoever and requires only a needle-point adjustment. When using this mineral cleanse the surface once a month

with a slight application of alcohol. This liquid carries away the grease spots received from the fingers. A better method is to keep the crystal covered in an airtight case.


#### Testing for Sensitivity in Crystal.

For those desirous of making sure of their crystal detector adjustment it is best to use what is known as "the buzzer test." This calls for a small buzzer, such as used in bell circuits. The buzzer is connected in the usual manner with a push button and one cell of dry battery, but a wire is brought out from one side of the buzzer interrupter to the ground connection of the receiving

set. When the buzzer is operated the electro-magnetic waves given off by the buzzer interrupter are impressed on the receiving set and the detector can be adjusted for sensitiveness in the same manner as though the operator were searching for a transmitting station.


A schematic diagram shows the method of connecting the test buzzer to any crystal receiver.

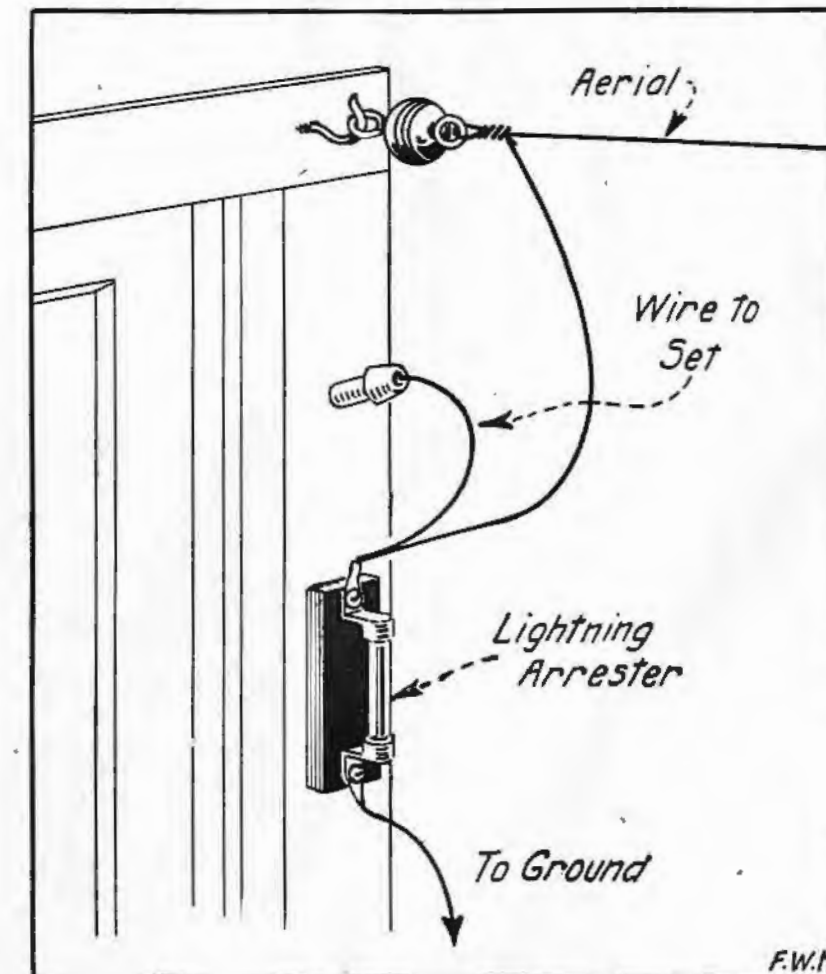Crystals lose their sensitiveness easily, due to jars or to powerful signals from a nearby station. Whenever a crystal is affected by these signals the tuning coils should be loosely coupled. If this is done the spot on the crystal will remain sensitive for a greater length of time.



A Lightning Arrester on the Outside Is Generally Preferred.




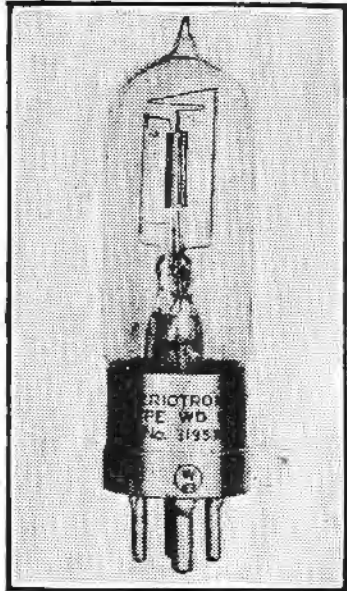

WD11



UV199

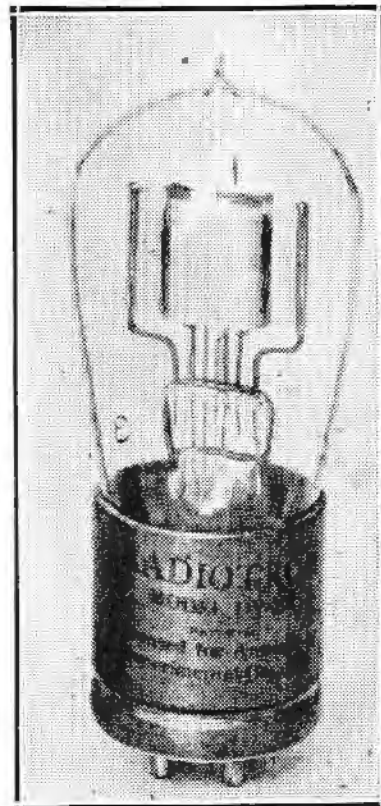

UV200

- UV200—**  
Requires a 6-volt storage battery.  
Takes 22 volts on the plate.  
Consumes one ampere of current.  
Used only as a detector.
- UV201—**  
Requires a 6-volt storage battery.  
Takes up to 150 volts on the plate.  
Consumes one ampere of current.  
Primarily an amplifier, but used also as a detector.
- UV201A—**  
Requires either a storage battery or four dry cells.  
Takes up to 200 volts on the plate.  
Consumes only one-quarter ampere.  
Primarily an amplifier, but is also a sensitive detector.
- UV199**  
Requires three dry cells.  
Takes up to 80 volts on the plate.  
Consumes .06 ampere of current.  
A good detector and amplifier. Particularly good as a radio frequency amplifier.
- WD11**  
Requires one dry cell.  
Consumes one-quarter ampere.  
Takes up to 120 volts on the plate.  
An excellent detector and radio frequency amplifier.  
The WD12 is the same tube as the WD11 except the former is supplied with a standard base.

The Three Principal Forms of Vacuum Tubes Used in Receiving Sets.

# The Vacuum Tube

## A Simple Explanation of Its Early Development From the Original Two-Element Tube and a Discussion of the Modern Three-Element Tube.

To go into the most minute action of a vacuum tube would require more space than a treatise of this nature allows. Moreover, such treatment would be unwarranted, for when the experimenter arrives at the point where he must acquire an intimate knowledge of the fundamentals of a three-element tube he would naturally seek one of the comprehensive hooks on the subject. The most that can be expected in these few pages is a skeleton outline of the action which takes place within the little glass tube when used as a detector and as an amplifier. For although there is no outward change when the same tube is made to operate as a detector or amplifier, the operations themselves are entirely independent, otherwise it would be impossible for a tube to function in the circuit known as regenerative. Reflex action also would be impossible and much of the flexibility associated with the vacuum tube would be missing.

When a minute fibre of metal or other resistance material, such as the filament in an electric bulb, is heated to incandescence, millions of little charges of electricity fly away from the boiling surface. These electrons are negative. Now the terms positive and negative when applied to any electrical action are to a certain extent merely arbitrary. But, as will be remembered from early experiments with horseshoe magnets, any metal that is charged with negative electricity will be attracted by the positive pole of the magnet and vice versa.

If a sheet of metal is now placed around the glass tube in which the filament glows—the plate may be either inside or outside—and if this sheet is connected to a small dry battery in such a way that the positive end of the battery is nearest the sheet of metal, the negative electrons will be attracted away from the glowing filament at an even greater rate.

The filament in this experiment

corresponds to the filament of a vacuum tube and the metal sheet to the plate of the tube. This combination was first discovered by Thomas Edison and has since been known as the Edison effect. A little later and independently, Professor Fleming in England noticed the same action while experimenting on wireless telegraph detectors. He immediately recognized the value of the phenomenon for the detection of radio signals and patented the device known as the Fleming valve.\* For several years the Fleming valve with its filament and plate was considered the most sensitive detector known. Even to-day, now that the patents on the Fleming valve have expired, firms are making them, a little better and a little more sensitive, and selling them to radio telephone fans to take the place of crystal detector. The valve, however, is seldom an improvement over the crystal detector and has the added disadvantage of requiring a battery to operate it.

One of the most ardent experimenters with the Fleming valve on this side of the Atlantic was Dr. Lee De Forest. After hundreds of experiments looking toward a further improvement in the valve to adapt it to radio, Dr. De Forest finally stumbled on the one improvement that has accomplished more for wireless and radiotelephony than any single invention, not excepting the epochal Armstrong regenerative patent. Dr. De Forest retained the filament and the plate and in addition inserted a third element which he termed the grid.

Heretofore, the Fleming valve acted only as a rectifier, due to the fact that current passed in one direction from the plate to the filament with greater ease than from the filament to the plate. Thus the oscillating come-and-go waves of the entering signals were retarded when the direction of movement was in one direction and accelerated when the movement was reversed.

But the insertion of the grid changed the action of the tube completely. The incoming energy—the signal waves—were brought in on the grid. The plate and the filament formed a secondary circuit which operated normally independent of the grid circuit. But the grid, being placed between the filament and the plate, had the last say in the matter of electron transportation.

In this respect the grid can be considered as an all-powerful gate-keeper. When the gate opened, the electrons were free to travel from the filament to the plate, the intensity of this movement depending entirely on the degree of opening of the gate. When the gate shut against the flood of minute charges, not a single electron could find its way by the barrier.

It should not be understood that this gate action is mechanical. The action is far too rapid for that. The checking was accomplished through the effect of electrical charges placed on the grid by the energy from the antenna.

As mentioned in a previous paragraph, a positive charge attracts a negative but repels another positive. Remembering this, it is not difficult to understand the action which takes place within a vacuum tube whose grid is connected to an antenna, whose plate is connected to a battery and whose filament is lighted in order to produce electrons.

Suppose that at the start there is no energy in the antenna. The electrons fly off the filament and to the plate in a steady unwavering stream. The grid is merely a screen through which they pass without trouble. But along comes a series of transmitted waves to the antenna. These waves set up other waves in the receiving set. These oscillations, as they are called because they pass first from antenna to ground and then from ground to antenna at a tremendous rate, pass on to the grid. First the grid is subjected to a positive wave, a fraction later to a negative wave.

# THE RADIO FAN WHO USES



SAVES

LABOR — MONEY — DISAPPOINTMENT

The Leads  
Are Soldered

YOU, who have achieved the pleasure of perfect reception and point with pride to the receiving set built with your own hands, know the importance of correctly attaching the leads to the taps of the variocoupler; quite naturally, therefore, you advise your friend to buy none other than a FISCHER.


Quality  
for  
Less Money

YOU, who have paid dearly for silk covered wires and fancy trimmings and painfully have learned that they do not increase the efficiency of your variometer or variocoupler,—you are no longer a novice and the sign of your experience is that you Demand a FISCHER Product every time; and of course you see to it that your friend buys none other than a FISCHER.

Unreserved  
Guarantee  
No  
Disappointment

YOU, who struggled through the experience of building set after set, trying one make after another, and were plagued with loose connections and loose wires, and then listened with disgust to the dealer's apology,—you finally found your difficulties ended by using FISCHER; and knowing that FISCHER makes good his guarantee, could you do otherwise than warn your friend to buy none other than FISCHER?

Guaranteed to  
Reach New  
Wave Bands

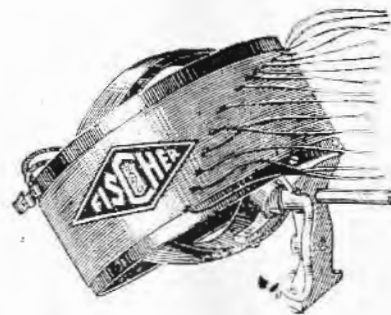


ALL FISCHER  
Products  
Designed to Make  
Sharp Tuning Simple

More FISCHERS  
Used Than Any  
Other Make

G. H. Fischer  
MANUFACTURER  
Glendale, L. I.

Radio Clearing House  
SOLE DISTRIBUTOR  
123 Liberty St., N. Y. C.

Quality  
Performance  
Guarantee

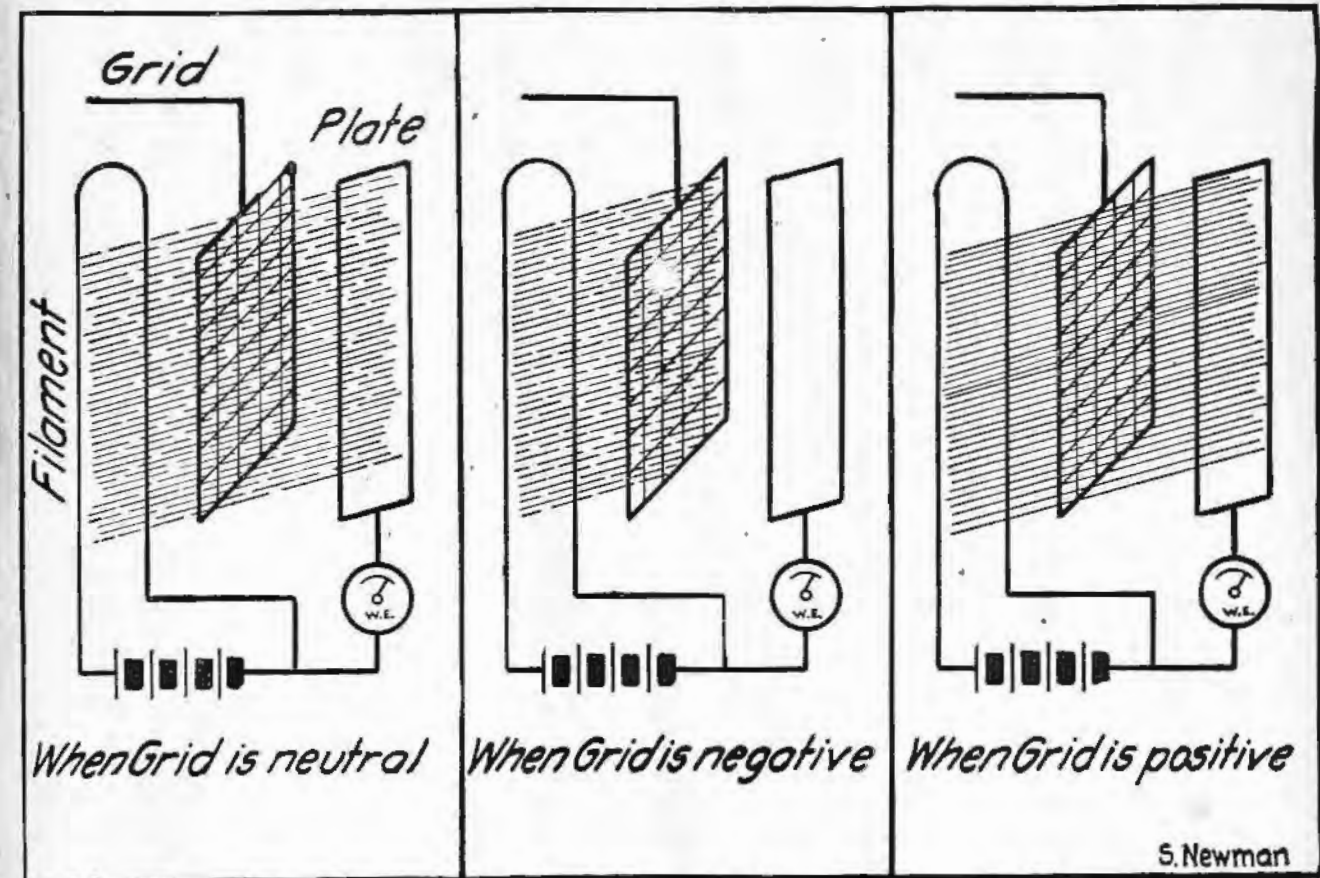

This Diagram Illustrates the Three Conditions of the Vacuum Tube.

When the grid is made positive the electrons from the filament are drawn at an increased rate through the grid to the filament. It is much as if the electrons were running a gantlet, but instead of being impeded as they pass down the lane they are given slight added pushes which increase their speed.

But now, an instant later, the grid is negative, and the action is entirely altered. Negative repels negative; they abhor one another. So the negative charge on the grid acts as a traffic policeman with a "stop" sign. The electron flow is cut off instantly, the degree of stoppage depending on the intensity of the negative charge. An instant later the grid is again positive and the electrons go their merry way.

During this time something must have happened in the wire which connects the plate with the battery. It is in this circuit that the 'phones are placed. If we had been listening during the experiments just outlined the various phases of action of the vacuum tube would have been evident through the change in sounds.

As long as waves were not striking the antenna, the current through the plate circuit—which also means

through the 'phones—was constant. It did not vary. But as soon as those little impulses from the antenna passed down the wire to the grid the placid current in this plate circuit was thrown into the wildest excitement. Each time the slightest change was brought about the action was made evident in the 'phones by a movement of the thin diaphragm, and this 'phone diaphragm movement coincided exactly with the variation in the waves striking the antenna. Thus if these waves formed a message in dots and dashes the 'phones reproduced them. If the incoming waves were part of a radio 'phone concert the 'phones reproduced the sound of the human throat or that of the musical instruments with absolute precision.

#### Different Types of Vacuum Tubes.

When the radiophone was in its infancy in 1920 those interested in the new form of entertainment had but two types of vacuum tubes from which to make a selection. These were denoted by the terms UV200 and UV201. Each tube performed a particular kind of work. The UV200 was and is mainly a detector tube

and is unsatisfactory as an amplifier. The UV201 is primarily an amplifying tube, although popular with some experimenters as a detector.

The two tubes are identical in appearance; the only difference in construction lies in the fact that the UV201 is evacuated to a high degree, while the UV200 is sealed off while a small volume of gas remains in it. The UV201 is called a "hard" tube and the UV200 a "soft" tube. These terms merely indicate the degree of vacuum within the bulbs.

Because of the gas which remains in the UV200, the tube requires a much more delicate control to operate its action properly. Moreover, unless adjusted to the exact operating point, the tube is either insensitive to the incoming signals or is noisy and harsh and distorts the sounds.

When the UV201 is utilized as a detector its control is less delicate, but it does not compare with the soft tube in sensitivity.

Both of these tubes require a source of current with a potential or voltage of 6 volts. This means that a storage battery must accompany each set, and a storage battery

S. Newman

# Federal

## Pioneers in the Movement to Guarantee Radio Products

**T**HANKS to Federal's initiative, the Radio user can now purchase a complete line of equipment protected by a positive guarantee.

For nearly a quarter century Federal has been producing guaranteed communication apparatus—the determination of Federal to protect the Radio user now marks a new era in the buying and selling of Radio equipment.

### The Federal Guarantee

To appreciate the positive value and far-reaching effects of the Federal Guarantee, it is only necessary to read its statement:—

*"We hereby guarantee Federal Standard Radio Products to be free from all mechanical and electrical defects and to function properly when installed in accordance with our authorized directions, and we agree to replace, at our expense, any unit or part which may prove defective."*

Look for the Federal Guarantee tag before you buy any piece of Radio Equipment—wasted time, money and disappointment are thereby avoided.

### Many Millions of Dollars

Behind this Guarantee as a pledge of its good faith stand the entire resources of the Federal organization. The Federal Guarantee is a deliberate policy—not merely a claim.

*Write today for the Federal Catalog of Standard Radio Products, fully covered by the Federal Guarantee.*

**Federal Telephone & Telegraph Company**

Buffalo, N. D.

requires some method for recharging it. In addition to these drawbacks is that of bulkiness. A storage battery, with its many lead plates, must of necessity be heavy and bulky. This precludes the use of the two tubes mentioned with any type of light weight, portable receiving set.

#### Engineers Design Tube for Dry Cells.

Engineers early recognized this fault and concentrated their efforts on the design and perfection of a vacuum tube which could draw its current from a dry cell. Finally the first dry cell tube, called the WD11, was placed on the market.

The WD11 was slightly smaller than the UV200 and 201. Instead of requiring a potential of 6 volts it could be operated satisfactorily on a single dry cell having a potential of only 1½ volts. The filament of the dry cell tube consisted of a fine metal wire coated with radioactive material which made it unnecessary to heat the filament to incandescence in order to provide the proper emission of electrons. Thus the WD11 was operated with a current consumption of ¼ of an ampere, compared with the 1.1 ampere of the first tubes.

Naturally when these tubes became available the radio public became curious as to their real possibilities. Being smaller than the UV200, there was a demand to know if the WD11 would do all that the larger tubes would do. Were they sensitive detectors, or were they suitable only for amplifying purposes?

It was stated at the time that the smaller dry cell tube would do all that the larger tubes would do. They were excellent detectors and efficient amplifiers. But since that time experience with a quantity of the tubes indicates that the dry cell tube is not quite as good as the average 6-volt UV200, either as a detector or as an amplifier. Some experts have stated that it is only 80 per cent. as good. Others have said that the tube lost but 10 per cent. in efficiency through its change in design. At any rate it is probable that the advantage to be gained through the use of a dry cell in place of the storage battery more than compensates for the possible loss of even as much as 20 per cent.

As amplifiers the WD11 tubes have been found to vary widely. Some operate perfectly in both the first and second stages of the amplifier.

Others refuse to amplify properly in the second stage unless the voltage on the grid of that tube is made negative by the addition of a small supplementary battery called the "C" battery.

At first the WD11 tube was supplied with a very special form of base for the express purpose of preventing the accidental placing of the low voltage tube in the higher voltage socket adapted to the 6-volt tubes. The manufacturers felt that the sudden appearance of the dry cell tube on the market before the radio public had been properly educated in its application would result in the destruction of many tubes and the consequent dissatisfaction of thousands of beginners.

#### Special Socket Prevents Tube Destruction.

But lately the firms making the tube have concluded that radio fans can understand the difference between the tube for storage batteries and the tube for dry cells, and accordingly are supplying the same tube with a standard base arranged so that the tube may be inserted into any standard socket. To distinguish the two tubes the newer tube is given the name of the WD12. And it should be understood here that, except for this one feature of the alteration in the base, there is no difference whatsoever in the tubes.

One other point has evidently bothered the radio public concerning these tubes. Thousands have asked, "Is the same tube used as either detector or amplifier?" The answer to this is in the affirmative. The WD tubes are "hard" tubes, but they are extremely sensitive detectors.

Within the last few months two other tubes have appeared on the horizon and both are now being seized upon and put to work. The first to arrive was a companion to the UV tubes and was given the name of the UV201A.

The UV201A is a 5-volt tube, but requires so little current that it can be operated from the proper number of dry cells. Since each dry cell delivers only 1½ volts, four such cells should be connected in series to supply the required potential. But the current drawn by the tube is no more than that taken by the WD11 and 12, hence one set of four dry cells should last for 500 to 1,000 hours of actual operation.

The UV201A is an excellent de-

detector and an unusually good amplifier. In time it is expected that this tube will replace the UV201, since it performs better and more economically than the latter.

When the 201A is used in a circuit either as detector or amplifier the resistance of the rheostat which controls the current should be increased from the normal 6 ohms to 30 ohms. Either the rheostat with the lower resistance must be replaced with one having five times the resistance or a permanent resistance of 24 or 25 ohms must be connected in series with the main rheostat.

Because of the high potential which can be applied to the plates of these tubes the amplification can be carried to a higher value than with either the WD11 or the UV20 tubes.

The second of the new arrivals in tubedom is the UV199, a semi-"peanut tube." A "peanut tube" is the name given to a tube specially designed during the war for compact sets, but never released for public consumption. The UV199 is the nearest commercial approach to the real "peanut tube" that has been developed.



This tube is only 1¼ inches in diameter and 3 inches high. The style of contacts on its base requires its use in a special socket, although adapters are now available by which it may be made to fit the standard socket.

The UV199, like the 201A, is an exceedingly good detector and amplifier. It requires a potential of 3 volts and consumes but .06 of an ampere, or about one-fourth of that consumed by the WD11 and the UV201A. Because of this low current demand the UV199 can be operated from a set of three flashlight cells. It is probable that these cells would supply the needed current for several weeks, while three ordinary size dry cells would operate the filament of the tube for six months or a year. The principal advantage in the use of the flashlight cells is that the tube then becomes suitable for the most compact of portable sets. The batteries can be included within the cabinet without increasing its bulk or its weight.

This small semi-peanut tube has also been found to be unusually well adapted to receiving circuits involving the amplification of currents at radio frequencies, but this particular subject will be dealt with more fully under that general heading.

# Fahnestock Products

"STANDARD IN THE RADIO FIELD"

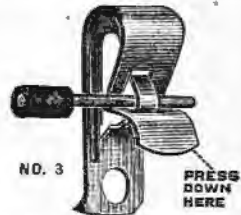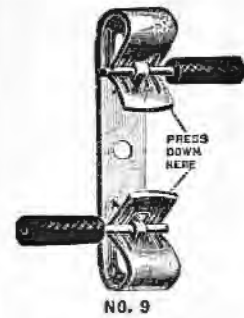


## Fahnestock Spring Binding Posts and Connectors

have been standard equipment for many years on telephone, telegraph and fire alarm systems throughout the United States and Canada.


- GRIP LIKE A VISE
- CANNOT JAR LOOSE
- PERFECT ELECTRICAL CONTACT
- EASILY ATTACHED
- BROKEN AND LOOSE CONNECTIONS ELIMINATED

The millions in use in Radio work where perfect contact is so essential absolutely prove them to be the final connection.
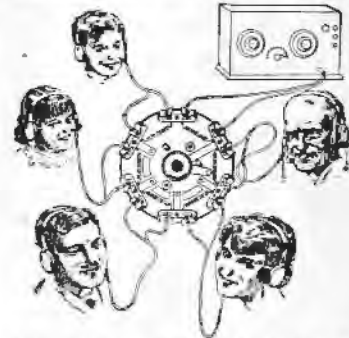
## Fahnestock 5 Way Radio Connecting Block




LETS THE WHOLE FAMILY "LISTEN IN"

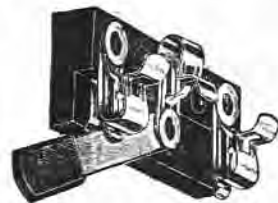

NO. 6 S. P. D. T. SWITCH

AT YOUR DEALER'S OR DIRECT FROM

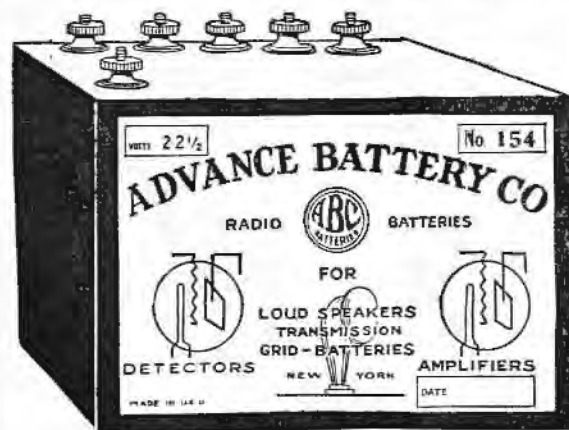**FAHNESTOCK ELECTRIC CO., Long Island City, N.Y.**



ABC Batteries are designed especially for Radio receiving apparatus and differ in many ways from dry batteries manufactured for other purposes.

We guarantee our batteries to be noiseless in operation and to give long service life.

Manufactured by experts of over twenty years' experience in the battery business.

At all good dealers.

**Advance Battery Co.**  
506 West Broadway  
New York City.



Greatest Volume  
Purest Tone


Sold Direct by Manufacturer

This Accounts for the Low Price


**\$15**

NEW MODEL  
**Vitalitone**  
Loud Speaker

## Vitalitone Storage B Battery

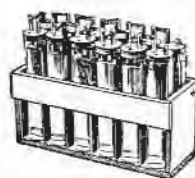

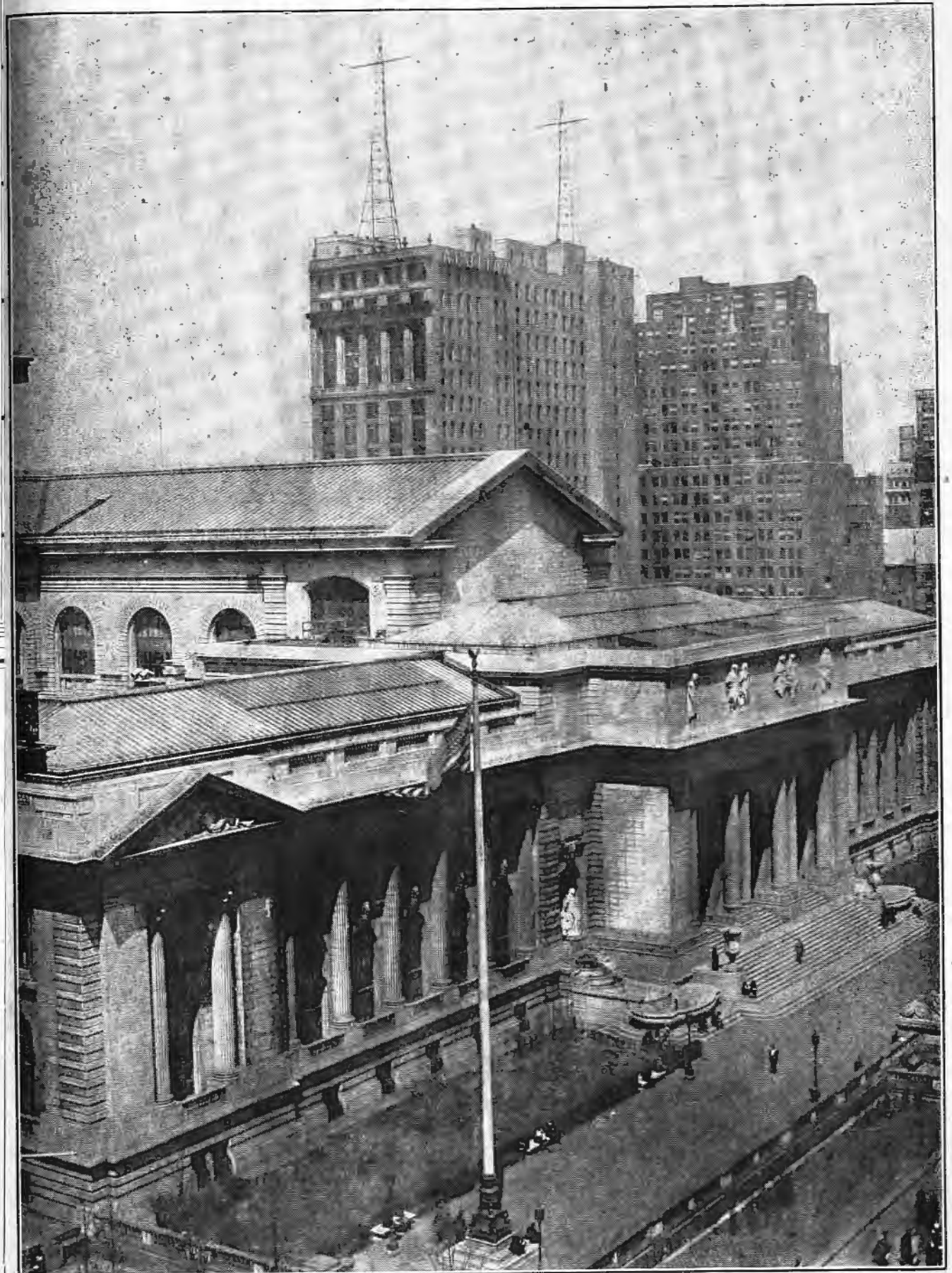24 Volts, 1 1/2 Ampere Hour.  
Saves Battery Expense.  
PRICE DIRECT, \$3.50  
Mfd. and Guaranteed by  
**VITALIS HIMMER**  
15-17 WEST 18TH ST., N. Y.  
Send for Literature.



WJZ and WJY Transmit Simultaneously From This Antenna

SECO

## STANDARD RADIO PRODUCTS

The SECO HEADSET embodies the highest accomplishments in the manufacture of receivers. Young and old marvel at its sensitiveness. It reproduces speech and music clearly and distinctly. Its light weight (complete less than 12 oz.) makes one feel that you were just listening in without the annoyance usually caused by heavy and clumsy headsets.


**A RADIO HEADSET**


"THE SMILE THAT WON'T COME OFF"

 TYPE 201  
 2000 OHMS, List Price **\$5.00**


 TYPE C  
 2500 OHMS, List Price **\$8.00**

 Weight complete, 12 oz.  
 Specially Designed for  
 Wireless Receiving

**VARIABLE GRID LEAK AND  
 MICA CONDENSER COMBINED**

 Resistance  
 0 to 5 Megohms  
 Capacity  
 .00025 MFD.
List Price **1.00**Mounting For Panel **1.25**

Varies resistance from zero to 5 megohms, giving wonderful control over receiving set, which permits receiving of mellow tone music or speeches on a standard head set or loud speaker. This eliminates all unnecessary buzzing and hissing and also increases life of battery.

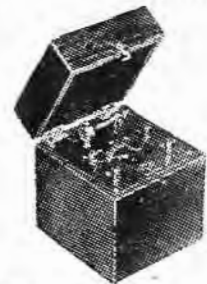**THE SECO IMPROVED  
 RECEIVING SET**

 LIST  
 PRICE  
**5.00**

Finely constructed, set in strong, hinged-top cabinet. 30 mile receiving radius. The equal of high-priced crystal sets selling for many times this price. As many as 4 Pair of Headsets can be attached to SECO, giving the same clear results.

JOBBERS and DEALERS—Write for Samples and Prices

**SPIELMAN ELECTRIC COMPANY, INC.**

OFFICE: 116 WEST 65TH ST.

NEW YORK CITY, N. Y.

FACTORY: 1931 BROADWAY.

# Standard Receivers

Although Less Spectacular in Performance, the Simple Regenerative Set Still Leads the More Radical Types in Popularity and Ease of Construction.

Radio receivers are usually distinguished by the type of circuit employed in their construction. There is the single-circuit, double-circuit, three-circuit and four-circuit receiver. Sometimes the difference between them is made even more distinct by specifying them as inductively or capacitatively coupled, as the case may be.

These various receivers will be treated individually at their proper places in the Radio Manual.

At this time only the single circuit set will be described at length.

This is perhaps the simplest receiver to build, although not always the easiest to operate. It is, however, an excellent outfit for the beginner to start on, particularly if the separate parts are to be assembled into a complete set.

Commencing in a logical order, the construction of the antenna comes first. All that is necessary is a single wire elevated thirty or more feet off the ground and running not longer than one hundred feet. With a much longer wire it becomes necessary to insert a condenser in series with the aerial, which reduces its efficiency. More complete data on the erection of an antenna will be found under that heading in the table of contents.

Next to the aerial is the need of a good ground. This may be obtained through a connection to the steam radiator or cold water pipe. In making this connection scrape a clean place on the pipe with a file, bind a dozen or more turns of the wire around this spot, twist the wire tightly and drop solder on the turns. A better way is to use a ground-clamp around the pipe at the place where the scale has been removed.

**Parts Required to Construct  
 This Simple Set.**


In order to keep down both size and cost the set has been simplified to the last degree. Most of the tuning can be done with the variable condenser. A variocoupler is used

as the inductance, with the wire-wound rotating ball arranged to produce regeneration. With these parts and a vacuum tube and socket the set may be inserted in a cabinet to fit, the combination producing a receiver that is attractive and workable.

The actual parts needed for this set are listed below. The aerial should consist of one hundred feet of stranded copper aerial wire, one

parts. Purchase a tube that has a known reputation and one that can be used as a detector tube. In this case the UV 200 is suggested, provided a storage battery is to be available. If dry cells are to be the source of supply, the UV 199, WD 11 or WD 12 is recommended.

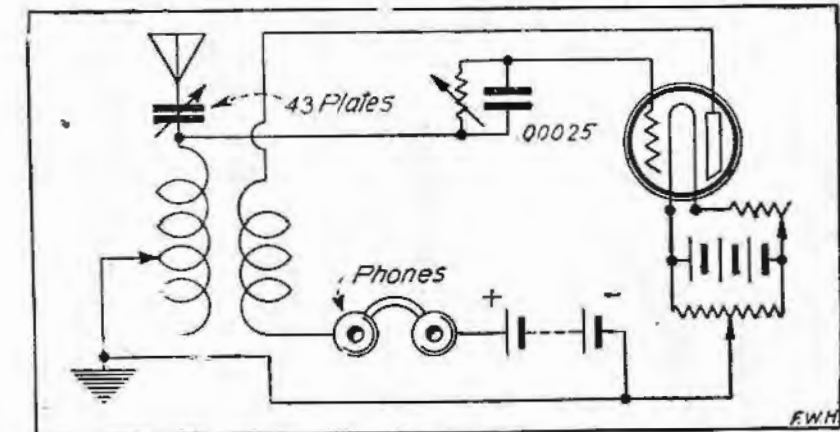It is mainly a matter of taste in the selection of the remainder of material. The most important part of the tube socket is the four-



One Popular Form of Single Circuit Receiver.

forty-three-plate variable condenser, one one hundred and eighty-degree variocoupler, a vacuum tube detector, a tube socket with necessary grid leak and condenser, a rheostat, a twenty-two-volt B-battery and the proper A-battery. The 'phones should be at least of two thousand ohms resistance.

**Constructional Details of the  
 180° Variocoupler.**

This piece of apparatus is really the heart of the whole receiver, and its selection therefore should be made with care. It is best to secure one which is made of tubing of high insulating quality, as this material will not absorb moisture. See that the coupler is ruggedly made, so that the wires will not loosen when assembling the set. Study the connections to get an intimate idea of the relationship of the

spring strips on the bottom of the socket. These should make firm contact with the four legs of the tube.

Two dials are needed, one for the condenser and the other for the rotor ball. The rheostat should make a positive contact throughout its range and should revolve easily without jerks. A switch arm with some contact points and a few binding posts complete the list of necessary materials for tuning the complete set.

The three specific claims made for this somewhat unusual adaptation of familiar circuits are simplicity, selectivity, and efficiency. It is a very simple arrangement—one glance at the diagram or the wiring of a complete set would satisfy the most skeptical on that point.

The input tuning is effected by an ordinary variocoupler and a .00025 microfarad variable condenser. All

# TRI-COIL

*The Radio Frequency  
 transformer with the  
 compensating coil*

—whose merit has already been established, not only by a Certificate of Excellence from the New York Tribune but by the popular demand of enthusiastic users.

The simple truth about TRI-COIL RADIO FREQUENCY TRANSFORMER is a revelation in the development of coupling.

This is the transformer that was successfully used in a steel subway car under the East River.

The "Tri-Coil" is highly recommended for the Reflex circuit and is also adaptable to W. D. 11 tubes.

Type "A" Specially Designed for 201-A Tubes.  
 Radio Apparatus Division  
 Brooklyn Metal Stamping Co.  
 BROOKLYN, N. Y.


 At all  
 radio  
 dealers

 List  
 Price

**\$2.00**

## "RADIANT" VARIABLE CONDENSERS

Have Proven To Be a Positive Success

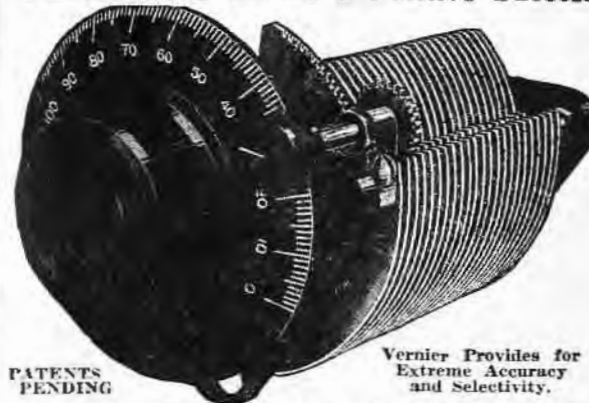
 Vernier Provides for  
 Extreme Accuracy  
 and Selectivity.

**SUPERIOR CONSTRUCTION—RIGIDITY OF FRAME  
 FIRM ACCURATE BEARINGS  
 BUILT LIKE A WATCH**

 The Condenser with the  
 Perfectly Hard Flat Plate

 13 Plate, Approx. 0.00025—M.F.D., \$5.00  
 25 Plate, Approx. 0.0005 —M.F.D., 5.50  
 45 Plate, Approx. 0.001 —M.F.D., 6.50

 PRICE INCLUDES GENUINE CONDENSITE DIAL.  
 DISTRIBUTORS IN NEW YORK

 J. H. Bunnell & Co. | Continental Radio & Elec. Corp.  
 W. R. Ostrander & Co. | Manhattan Elec. Supply Co., Inc.  
 Stanley & Patterson, Inc.

 Dealers Out of New York Please Write for  
 Name of Nearest Distributor.

**HEATH RADIO AND ELECTRIC MFG. CO.**  
 206-208-210 FIRST ST., NEWARK, N. J.

# Insist on RADION

Reg. Trade Mark

Panels, Dials,  
V. T. Sockets, Knobs,  
Antenna Insulators.

It's furnished in 18 stock sizes, each panel packed in envelope to protect the supreme finish.

It's the easiest panel to cut, drill, engrave with simple tools at home. It never warps or shrinks, chips or cracks.

It has the lowest phase angle difference, lowest dielectric constant and highest resistivity.


Radion is the supreme insulation for wireless use.

Obtainable from most dealers. Try it and notice the difference in results.

Size	List Price		Size	List Price	
	Black	Mahoganyite		Black	Mahoganyite
6 x 7 inches	\$0.75	\$0.90	7 x 21 inches	\$2.65	\$3.25
6 x 10 1/2 inches	1.15	1.40	7 x 24 inches	3.00	3.70
6 x 14 inches	1.50	1.85	9 x 14 inches	6.00	7.40
6 x 21 inches	2.25	2.75	10 x 14 inches	2.25	2.75
7 x 9 inches	1.15	1.40	10 x 12 inches	2.15	2.60
7 x 10 inches	1.25	1.55	12 x 14 inches	2.85	3.45
7 x 12 inches	1.50	1.85	12 x 21 inches	4.25	5.20
7 x 14 inches	1.75	2.20	14 x 18 inches	4.25	5.20
7 x 18 inches	2.25	2.75	20 x 24 inches	8.50	10.35

American Hard Rubber Co., 11 Mercer St., New York

## NOVO "B" BATTERIES

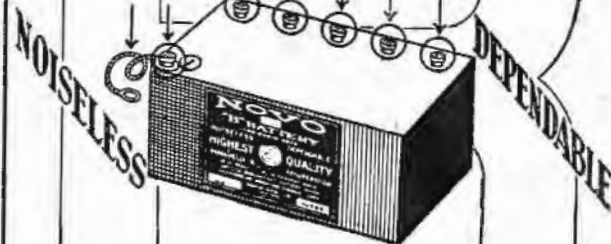

NOTE THE INSULATED  
BINDING POSTS AND  
7 IN. WIRE CONNECTOR

NOVO M'FG CO.  
424 W. 33<sup>rd</sup> ST. NEW YORK  
531 SO. DEARBORN ST. CHICAGO

## RADIO TUBE SPECIALISTS WE SAVE YOU MONEY



When you have a radio tube problem come and see us!

### REPAIR SERVICE

Send us your dead tubes—we put new life into them. If they cannot be repaired we will make an exchange and save you money anyway.

### NEW TUBES

We sell all makes of new tubes. As new tubes come out we have them first. Large stocks on hand at all times. Try us for tubes first and save time as well as money.

### ADVISORY SERVICE

When you build a new set or improve your old one consult our tube experts. If it's a tube question we can answer it.

### RADIO PARTS


We also manufacture and carry reliable radio parts.

### MAIL SERVICE

No matter where you may live you may still have our complete service. Send your tube by mail or ask for information. Prompt attention to mail orders.

RADIO PRODUCTS CO.  
115 West Broadway, N. Y. C. Phone Canal 2039

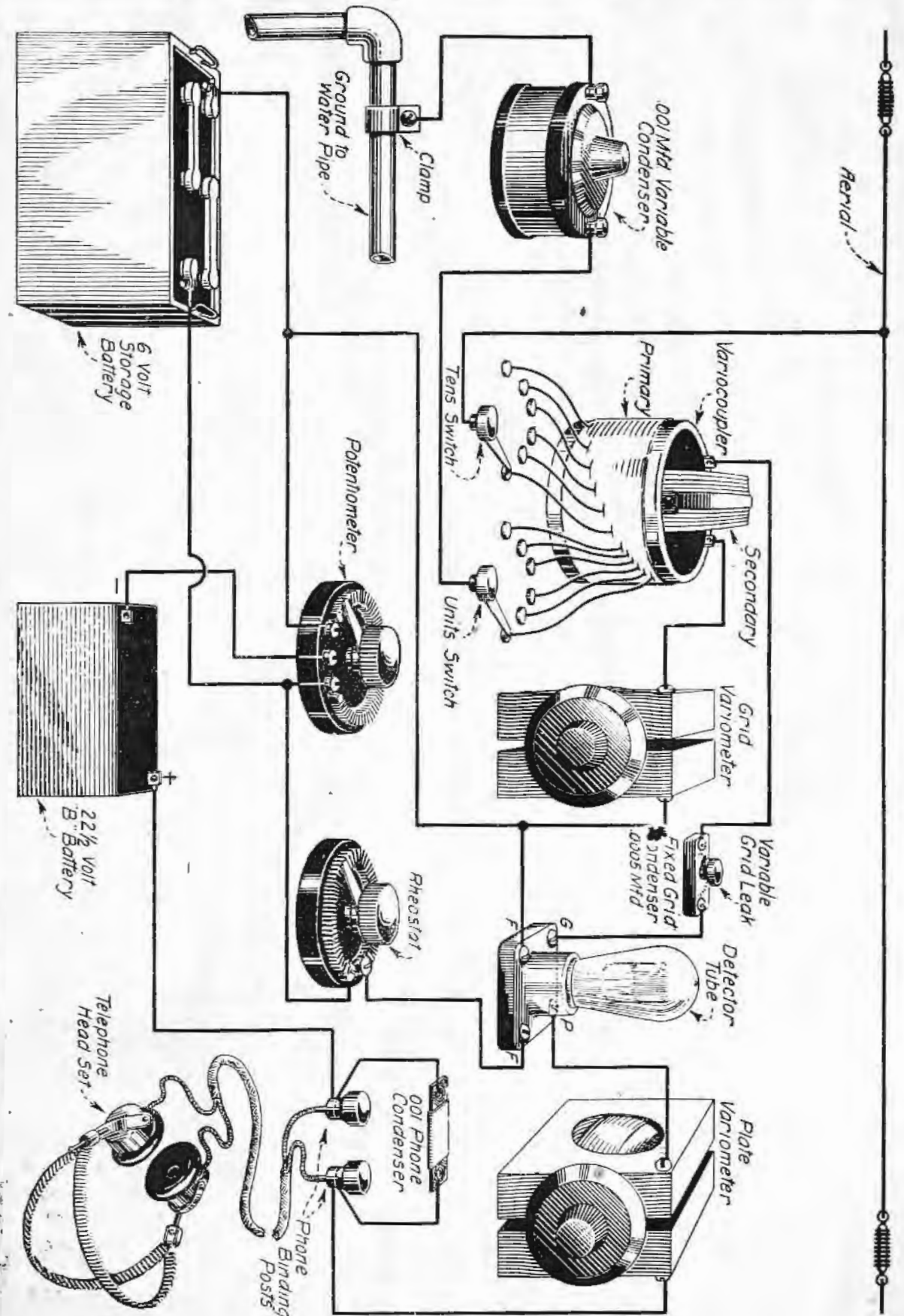Graphical Arrangements of Standard One-Tube Regenerative Receiver Employing Variocoupler and Variometers.



**"PROVEN IN SERVICE"**

THE BEST IN THE WORLD FOR THE MONEY

**3,200 OHMS RESISTANCE**

**\$3.65 PER PAIR**  
WORTH \$8.00

SENT PARCEL POST PREPAID ANYWHERE  
IN U. S. A. UPON RECEIPT OF PRICE

Dealers, Write for Quantity Prices.

**THEODORE STAVE CO.** 30 CHURCH ST.  
N. Y. CITY

# Signal Corps RADIO HEAD PHONES



the other details in the circuit are the same as that required in any other single-tube regenerative type; that is, grid leak and condenser, plate and filament batteries, vacuum tube, tube socket, and 'phones.


The connection on the aerial side of the variocoupler stator is the peculiar feature in the circuit. At

this particular circuit which causes it to differ from other single-circuit receivers lies in the fact that it does not reradiate unless the natural period of the aerial is exactly the same as the wave length that is being received. Such a combination is extremely rare. A condenser with only a small maximum capacity must be

of condensers as in the circuit known as the Eaton oscillator.

The diagram illustrates one way in which the Eaton oscillator may be incorporated into a receiving set of two units. One unit contains the tuning elements and the other the vacuum tube apparatus.

The Eaton oscillator, which con-

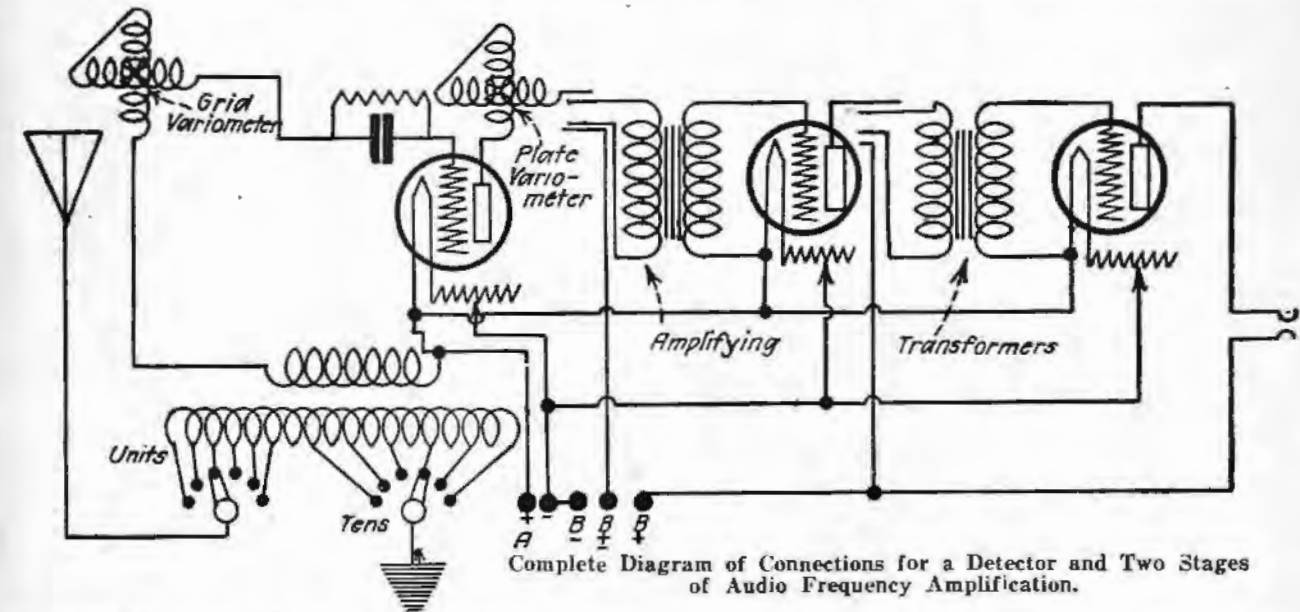

the maximum, there are only six turns actually in the aerial to ground circuit. A four-point switch is used to vary this number in steps of one, two, four, and six respectively. These six coils are actually a part of the stator windings and by induction produce in the turns across the grid and filament the voltage which produces the signal in the 'phones.

The connection is known as the direct or conductive type of coupling and the operation is analogous to that of an auto-transformer. The rotor of the variocoupler is used as a tickler for producing regeneration in the usual manner. A feature of


used in the primary circuit in order to secure the best results in tuning; a large condenser will make adjustments difficult. It is also advisable to use a well-constructed variocoupler that will allow 180 degrees change in the inductive coupling.

**Regenerative Circuit of the Inductive Type.**

Regenerative receivers with inductive feedback arrangements of the tickler coil, as explained previously, are in common use at many amateur stations. Another method of obtaining regeneration action which does not require coils is through the use

of condensers in series is incorporated in the unit containing the tuning device which is of the loose coupler or variocoupler type. A secondary shunt condenser of the variable air type is also mounted in this unit to assist in tuning the secondary circuit.

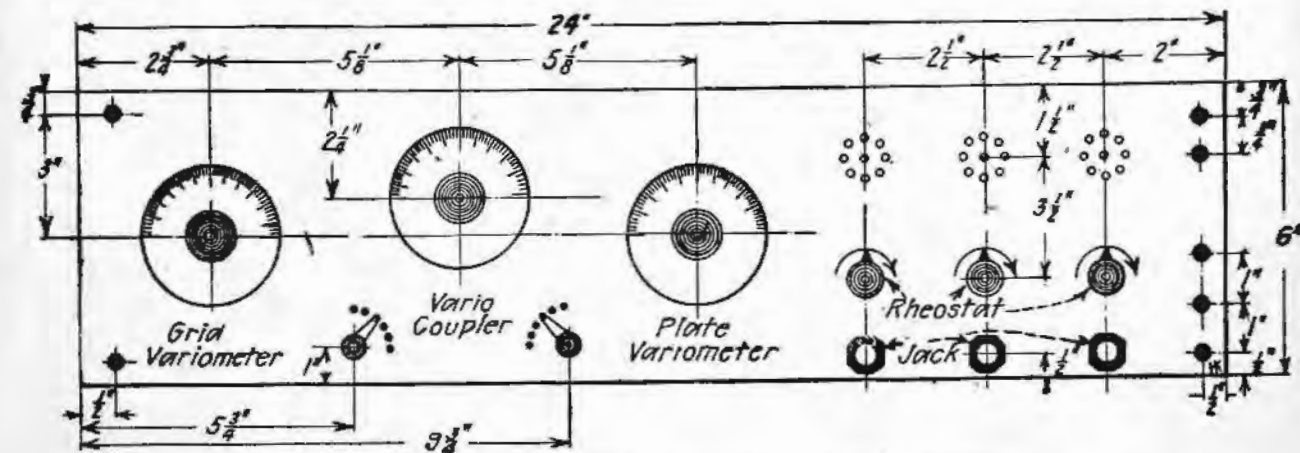
The unit at the right contains a vacuum tube detector of the usual type with a lead running directly from the plate to a binding post which is strapped across to one side of the secondary circuit. The other side of the secondary circuit connects to the grid condenser (C4) which may be of the variable air type. A



Panel Layout Suggested for Variocoupler-Variometer Receiver.

**STATIC and Interference is reduced to a minimum**

**Better Reception with the NASSAU**



Pat. Pend.  
Price \$35.00

Jobbers and Dealers write for Proposition.

**LOOP TUNER**  
TRADE MARK

Eliminates Aerial and ground  
The Secret is in the Patented Winding  
1500 MILES ON LOUD SPEAKER  
With 2 stages radio and 2  
2 stages audio frequency amplification.  
Write for Circular "G"  
Manufactured by  
**NASSAU RADIO CO., Inc.**  
60 Court St., Brooklyn, N.Y.

We Will Mail You One

**"VERILOUD" SYNTHETIC RADIO CRYSTAL**

COMPARE IT WITH WHAT YOU ARE NOW USING. OURS IS BETTER MAIL US. 30 CENTS

**IF NOT Return it at Our Expense**

ZOBEL-STEIN LABORATORIES  
322 9th ST. BROOKLYN, N.Y. SOUTH 2650

**1789 3rd AVE GRAND 1714 2nd AVE**  
Near 99th St. Near 89th St.

TEL. LENOX 9126 STORES TEL. LENOX 8423

Open Evenings and Sundays.  
WE CARRY A

**COMPLETE STOCK**  
ALL STANDARD RADIO PARTS  
As Cheap as Anywhere in the City  
We Build Sets to Your Order and Drill Panels.  
WE SPECIALIZE ON  
COCKADAY FLEWELLING  
REINARTZ D. X. FLEX

CIRCUITS  
**FREE EXPERT ADVICE TO ALL**  
It Will Pay You to Visit Us

When You Buy Direct You Save the Difference

**ESSEX STANDARD PHONES**  
2300 OHMS

The phones with the giant grip magnets. The Essex STANDARD PHONES have been built with a conscience—and built to stand up under the most severe conditions; the magnets are absolutely permanent and will not become demagnetized.

**WONDERFUL FOR LOUD SPEAKER.**

Sold on a money-back guarantee.  
List \$3.00 Direct \$1.65  
Phonograph attachment free with each pair.



**ESSEX REFLEX SPECIAL AUDIO TRANSFORMERS**

The Essex has the unique record of 12,500 sold in four months and many of our customers state they are wonderful for any style tube.

List, \$5.00. Direct, \$3.00.

**MALCON REFLEX RADIO TRANSFORMER.**

150 to 800 Meters  
THE SECRET OF THE reflex circuit is the matching of transformers. These transformers match the Essex Audio and give you perfect reception on the reflex circuit.

List, \$5.00. Direct, \$3.00.  
Although these transformers are especially made for the reflex circuit they are guaranteed to give you better results in any circuit.

**ESSEX LIGHTNING ARRESTER**

Made of porcelain with bracket for installing. Gap of 3-1000 part of an inch. Heavy terminals will carry hundreds of amperes of current. Built for outdoor use, but attractive enough for inside installation. List Price \$1.50 Our Price .95



**PALL MALL 180° Vario Coupler**  
Is the Coupler That Makes a Good Set BETTER

The Pall Mall coupler is the result of ten months' experimental work and is all that can be desired in a coupler—it is smaller in diameter than any other coupler and takes up less space on your panel—it is very popular in that it works wonders—in either a bulb or crystal circuit and especially in the Reflex Circuit. Price \$1.75.

**SPECIALS**

	List	Our Price
Single Jacks	.65	.35
Double Jacks	.90	.45
Mica Condensers, 002, 001,		
6095, 00025	.35	.18
Reco Porcelain Rheostats	.75	.39
23 Plate United Variable Condensers	3.75	1.45
3-in. Molded Dials	.75	.19
2-in. Molded Dials	.50	.15
Taper Knob Switches	.50	.15

We Carry a Complete Line of Sets and Parts. It Will Pay You To Get Our Prices.

**UNION RADIO TIP JACKS**

They take the place of binding posts and assure you of positive contact at all times. Wonderful for battery connections. Price 25c per pair.

FREE—a Pair of Tips with Each Pair of Jacks.  
**BELL BAKELITE SOCKETS**  
The Bell Socket is without a doubt the peer of all sockets. The notch is made extra heavy to prevent breaking and it's BAKELITE. List, \$1.00; our price, 45c.

**BAKELITE PANELS**

If every radio fan knew what Uncle Sam and the licensed operator knows about Bakelite, it would be the only panel material sold. If you want your set to give you 100% results take a tip from them.

STOCK SIZES	
1-8	3-16
7 x 10	\$1.05
7 x 12	1.36
7 x 14	1.47
7 x 16	1.68
7 x 18	1.89
7 x 18	\$2.24
7 x 18	2.52
7 x 20	2.80
7 x 21	2.94
7 x 24	3.36
7 x 30	4.20

Special Sizes Cut to Order, 2 1/2" Square Inch.

MAIL ORDERS SHIPPED 24 HOURS AFTER RECEIPT OF ORDERS. WE PAY PARCEL POST ON PURCHASES OF \$5.00 OR OVER. We maintain an experimental department. If there is any problem you wish solved or any look-up you desire, we will be pleased to accommodate you FREE. Enclose return postage.

**ESSEX MANUFACTURING CO.**  
117 Mulberry St., Newark, N. J.

**RADIO SUPPLIES**

IF YOU are looking for better quality merchandise that will give you satisfaction, sold with our absolute guarantee, or money back, visit our Radio Department. Orders taken for all parts, or complete sets, at any of our Stores.

Send for Our Complete Catalog.

**Times Square Auto Supply Co., Inc.**  
1743 Broadway, N. Y. C.  
363 Fulton Street, Brooklyn.  
Special Mail Order Dept.,  
56th St. and Broadway.  
Established in 1904



**RADIO CABINETS**


For Consumer and Dealer.  
We manufacture a complete line of radio cabinets, of mahogany, walnut, oak, and white wood, in all sizes, and in any finish. Best of construction. Dirt, dust and moisture proof. Quick deliveries—quantity production prices. Send us your specifications, or a sample of your cabinets, and get our prices. We also make indoor loop aerals. Send for our price list.

Cabinet Work Since 1900  
**E. ESHOO CABINET WORKS**  
635 HERKIMER ST. BROOKLYN, N. Y.  
Telephone Lafayette 2324

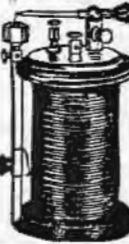
**RITTER'S LOOP AERIAL**

A knock-down aerial, including wire, can be assembled in 10 minutes. Endorsed by New York Globe and Mail. Results Guaranteed; Ritter Loop reduces interference, static and lightning troubles. No outside aerial or ground needed. Sold direct from our factory. By Mail 10c. extra. We also manufacture the now famous **RITTER GRAND CRYSTAL SET, PRICE \$3.50**

**Ritter Radio Corporation**  
232 Canal Street, Near Centre, New York



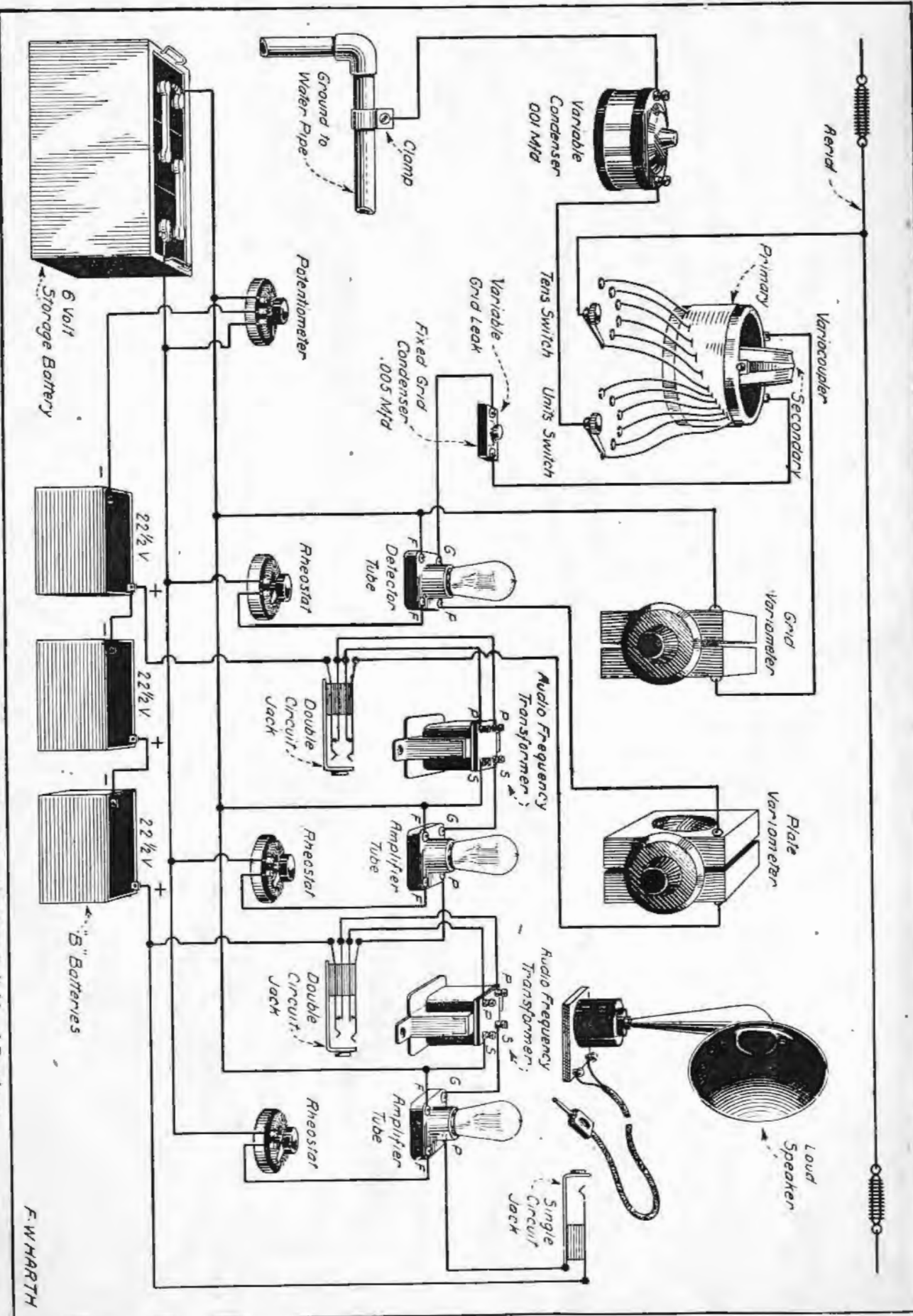A Regenerative Detector and Two Stages of Audio Frequency Amplification Form the Most Reliable of Receivers.



F. W. HARTH





# BERWICK *Supreme* HEADSETS

**Guaranteed 100% for Efficiency and Quality**

Or Money Back

**Experience is a great teacher**

And you who buy radio headsets should know that an organization offering its products on a "money back" guarantee has learned the lesson that quality counts. In Berwick Supreme Headsets you buy an efficient product of sound Mechanical and Electrical Construction. Made by experienced men who use Good Materials with Painstaking Craftsmanship.

*Reputation was always Built on Quality.*

**TRIANGLE ELECTRO TRADING CO., INC.**

Manufacturers

632-634 BROADWAY, NEW YORK CITY

Aluminum Cups

—Lightweight—  
—Comfortable—

PRICE

2200 Ohms, \$6.00  
3000 Ohms, \$8.00

bridging condenser (BC) is connected from the plate to negative side of the filament battery. This condenser has an approximate capacity of .002 mfd.

The condensers C1 and C2 constitute the oscillator or feedback portion of the circuit, while the con-

necting condenser (BC), but spark signals will not be received with their normal characteristic tone.

In operation a certain amount of the plate potential is fed back and impressed upon the grid by the condensers C1 and C2, which form a capacity feedback in contrast to the

connected series across the secondary terminals, with the grid on one side and the filament in the middle with the plate on the other side.

While not particularly adapted to short wave work it has been possible to get down to 200 meters with this device. Good regeneration is obtained up to several thousand meters. A receiver of this type is comparatively simple to operate.

So far we have spoken about regeneration when referring to the vacuum tube when used as a detector. With crystal receivers regeneration is impossible.

The detector tube requires careful adjustment of the plate battery for best results. As a matter of fact, there are no two tubes possessing the same characteristics either in the filament current or the plate voltage.

It is very easy to make adjustments on the filament, since the rheostat gives fine control of the current. A vernier is even better for proper filament control. One form of these vernier rheostats has an extra arm built on the same shaft as the regular arm, but travelling over a single wire tightened around the body of the instrument. This enables the operator to regulate the filament temperature very closely.

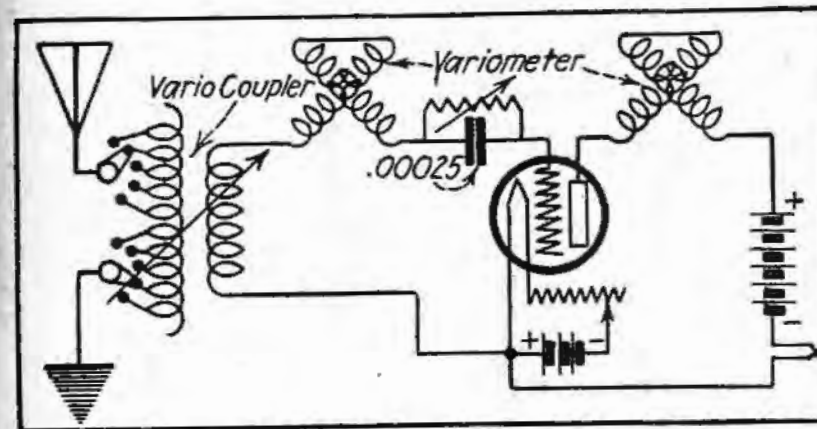


Diagram of Connections of Popular Variometer-Variocoupler Set.

denser (BC) is important in the adjustment of the system for the reception of damped or undamped waves. For receiving damped waves, condenser (BC) is set at maximum, while for undamped waves it is adjusted to minimum. The circuit may be operated without employing the

inductive arrangement usually employed.

The circuit may be applied to any loose coupler or variocoupler and tube detector without materially changing the circuits or dismantling the apparatus. The condensers C1 and C2 are two fixed condensers in

Money Back Guarantee

Mail Orders Solicited



"The House of Satisfaction"

Agents for Standard

## RADIO SETS AND PARTS

GLOBE RADIO SHOP

115-117 W. 23d Street

Tel. Chelsea 1342

New York



### MULTIPLE RHEOSTAT

Range 0 to 28 ohms

3/4 Amp. Capacity  
Fine for D-X work

List Price  
\$3.00



### ADJUSTABLE GRID LEAK

Resistance up to 10 Megohms; smooth increase, no jumps. Wonderfully efficient in obtaining quality and naturalness of both vocal and instrumental work on any circuit.

List price with cover.... \$1.00  
without cover..... .70



### RADIO-PHONO ATTACHMENT

The simplest, cheapest and best method of utilizing Victrolas as loud speakers with any tube-amplified set. Send for descriptive circular.


List price..... \$ .40  
Send Stamp for Catalog No.45G

J. H. BUNNELL & COMPANY  
32 Park Place New York City, N. Y.



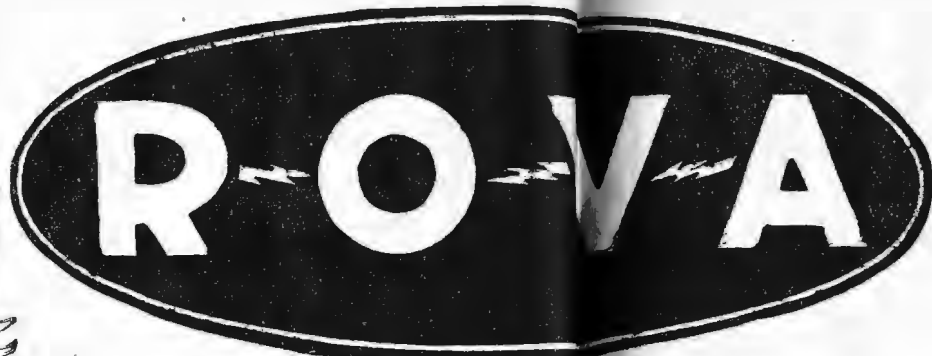A Ground Clamp Simplifies the Ground Wire Problem.





2 NEW YORK STORES

167 W. 18th St. ♦ 233 Fulton St.

Open Evenings Till 10 P. M.

Open Till 6.30

NEWARK STORE

132 Branford Place

# Complete lines of Newest Developments by RADIOLEADERS of the WORLD

**R**ADIO is for the home, for the school, for the automobile, for the farmhouse, beach or bungalow—radio is for everybody, everywhere. Rain or shine radio delivers. A turn of a dial or a knob and you flood the atmosphere with music, lectures, news, etc.

But—are you getting the most out of your set? Are you perfectly satisfied with its performance? Have the parts in your outfit been made by experts who know how? Dependable parts are the assurance of absolute satisfaction. Buy your needs where your choice is unlimited and where every item is backed by our guarantee. Sets and accessories are offered at the R-O-V-A Stores in extensive varieties. Every part is made to last and serve.

\* \* \* \* \*


**W**HAT follows is a partial list of the many reputable, nationally-known concerns who contribute to our enormous stocks:

RADIO CORPORATION OF AMERICA  
WESTINGHOUSE ELEC. & MFG. CO.  
GENERAL ELECTRIC CO.  
WESTERN ELECTRIC  
CUTLER-HAMMER CO.  
FRAMINGHAM CO.  
DICTOGRAPH PRODUCTS CORP.  
GENERAL RADIO CO.  
BRISTOL LOUD SPEAKER CO.  
CHELSEA RADIO CO.

FEDERAL TEL. & TEL. CO.  
ATWATER-KENT MFG. CO.  
RAVEN RADIO PRODUCTS  
MAGNAVOX CO.  
NATHANIEL BALDWIN, Inc.  
A. H. GREBE & CO.  
AUTOMATIC BATTERY CHARGER CO.  
FROST RADIO CO.

DAYTON FAN MOTOR CO.  
JEFFERSON ELEC. CO.  
SERVICE RADIO CORP.  
RADIO SERVICE LAB.  
ACME APPARATUS CO.  
PARAGON RADIO CO.  
JEWELL METER CO.  
KOEHLER MACHINE CO.  
RHAMSTINE CO.

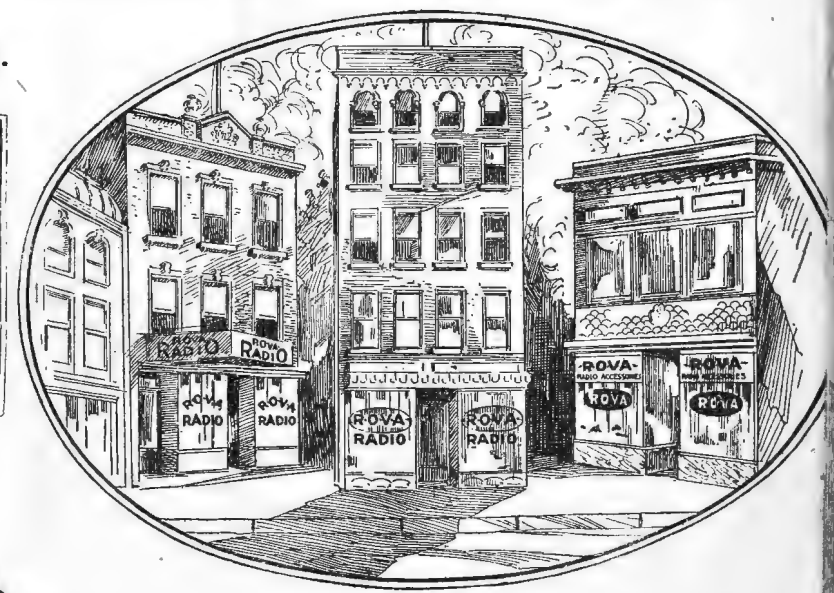3 WELL-STOCKED STORES  
Left  
UPTOWN STORE  
167 WEST 18 ST.  
Center  
DOWNTOWN STORE  
233 FULTON ST.  
Right  
NEWARK STORE  
132 BRANFORD PL.



# RICO

TRADE MARK  
REG.

## A REVOLUTION IN 'PHONE PRINCIPLES

A new development in the Radio World—Rico TUNED 'Phone gives you most efficient control in the volume of sound and tonal quality without chatter or loss of undertone. The TUNED feature in conjunction with the Tri-Pole Magnet principle assures perfect sound reproduction because of the use of a pure Para rubber gasket. The simple, easy adjustment of the diaphragm regulates the quality of reproduction to meet every particular need. It improves your radio set immeasurably, adding strength to the weakest of sounds. "Rico" TUNED 'Phones are unquestionably superior to any product of their kind in existence.

## INSIST ON "RICO" Tuned Headsets

Your insistence will give you the most PERFECT 'phones made.

"RICO" Melotone Loud Speakers  
Complete with Base Fibre Horn and 5 Foot Cord.  
**\$6.00**  
Rico TUNED Super-Sensitive 'Phones resistance 4,000 ohms Complete **9.50**

### "RICO" MELOTONE SPEAKERS ARE UNIQUE

"Rico" MELOTONE Loud Speakers mean that everybody in the room can hear the whole evening's program simultaneously. The MELOTONE is a combination of the "Rico" Tuned Loud Speaker and an acoustically perfect fibre-horn. The 'phone rests in a heavy solid base with a layer of felt on bottom to prevent table mars. The same rigid characteristics are employed in the MELOTONE Loud Speakers as in the "Rico" Tuned 'Phones. No distortion of sound is possible, instead you hear sound that is both resonant and pleasing. Try one and prove for yourself the difference between other loud speakers and "Rico" MELOTONE Loud Speakers.

**RADIO INDUSTRIES CORPORATION**

131 DUANE ST. New York City


WE prefer having you buy from your regular dealer. If for any reason he cannot supply you write to us direct. "Rico" TUNED 'Phones and Melotone Loud Speakers are sold on a 5-day trial, Money Back, basis.

In Effect June 1, 1923.

- No. 20—2000 ohms, Double Head Set, Tuned..... \$6.00
- No. 30—3000 ohms, Double Head Set, Tuned..... 7.00
- No. 40—4000 ohms, Double Head Set, Tuned..... 9.50
- No. 10—1000 ohms, Single Head Set, Tuned..... 3.50
- No. 15—1500 ohms, Single Head Set, Tuned..... 4.00
- No. 2—1000 ohms, Receiver Only, Tuned..... 2.50
- No. 3—1500 ohms, Receiver Only, Tuned..... 3.00
- No. 25—Tuned Loud Speaker 'Phone With 5-ft. Cord... 4.50

## AT LAST—THE PERFECT GRID LEAK VARIOTONE VARIABLE RESISTANCE LEAK

Unbroken Range—Zero to Five Megohms

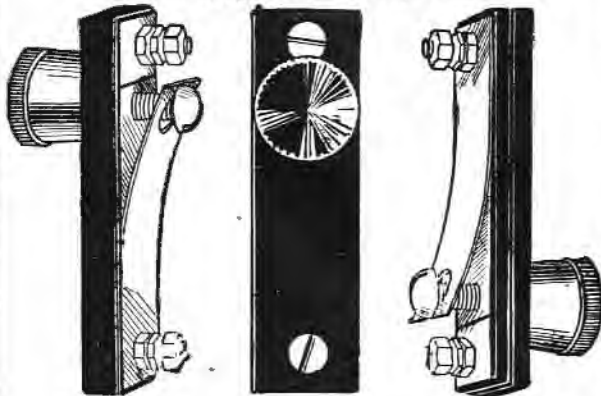

SIDE VIEW Without Condenser 50c  
FRONT VIEW  
SIDE VIEW With mica Condenser 75c

Different in construction. Insures better results. Compact. Neat. Nothing to wear out. Varies resistance gradually and smoothly.

Mounted Back of Panel. Adjusted from Front.

Ready for delivery on or about June 15th.

For Best Results Say VARIOTONE.


At your dealers or send purchase price and we will supply you promptly.

MANUFACTURED BY  
**The NATIONAL RADIO DISTRIBUTING CO.**  
51 West 19th Street, New York City
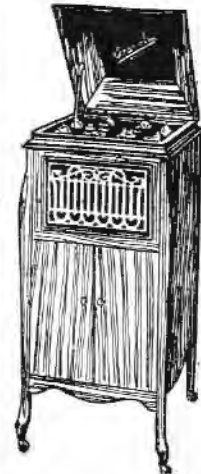
## WONDER OF THE RADIO WORLD

NO AERIAL USED

Loop Antenna self-contained in artistic piano-finished cabinet eliminates any wiring by purchaser



NO EXPENSE has been spared to make my product the best in every detail. Having passed through the experimental stage, I am prepared to stand behind each instrument with my unqualified guarantee.

MY KEYNOTE is simplicity of operation. No knowledge of electricity or wireless is required.

Weather conditions of any kind do not interfere in any way with your perfect enjoyment of this instrument

**THE Oranola**  
REG. U.S. PAT. OFF.

MANUFACTURED BY  
EDWARD R. JORDAN, JR.  
89 CHAMBERS STREET

## Modern Receiving Sets


The Armstrong Super-Regenerative Receiver and Others Similar to It Based on the Same General Idea—Future Outfits May Be Developed From One of These Forms.

Unless scores of pages were available for the purpose, it would be far from feasible to attempt to explain in any detail whatsoever the electrical fundamentals of the super-regenerative circuit. Using electrical terms the explanation is not a difficult matter, but unless the reader happens to be an engineer versed in the theory of alternating currents the task is both impossible and inadvisable.

Any user of a regenerative receiver knows that when the tickler or variometer knob is moved just so far and the signals increased in strength to a certain point, a limit is reached after which farther regeneration distorts the sounds and creates a hissing noise which obliterates all that the distortion does not affect.

Met by this limiting factor early in his experiments with the simple regenerative set which he invented, Major Edwin H. Armstrong for years sought a method to eliminate this limit so that regeneration could be carried further, and stronger signals secured, without the addition of other tubes. He finally succeeded in developing what he termed the "super-regenerator." By the arrangement of certain circuits he was able to make the vacuum tube oscillate at a frequency which had a certain relation to the incoming oscillation of the energy waves. This new arrangement did not prevent the vacuum tube from starting to hiss or oscillate when the limit of regeneration was reached, but it did effectually prevent the generation of continuous oscillations. That is, as soon as the set commenced to oscillate a local action blocked it for an instant. Then the incoming signal registered an instant before the oscillations recommenced, but again the local action blocked it, thus making it possible to carry regeneration far beyond the critical point.

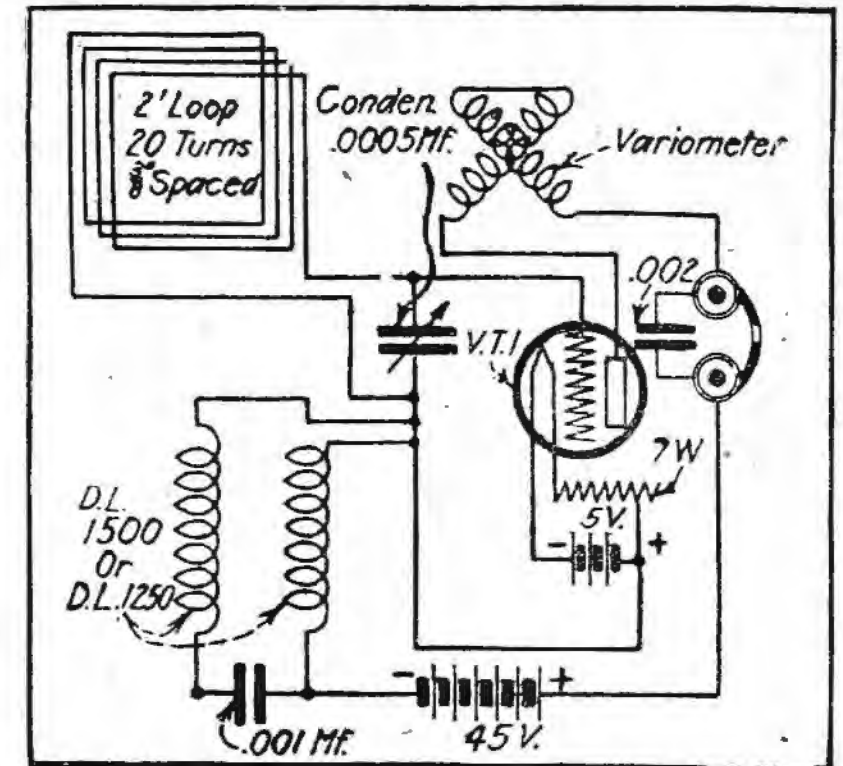As would be expected, if the idea is reasoned out, there is a hum or whining sound that is always present



An Excellent One Tube Super-Regenerator.

in super-regenerative sets, unless extensive means are taken to filter it out. This whine is of such a high pitch, however, that it is soon lost in the broadcast sounds and is not objectionable.

Because of the principle upon which it is based the super-regenerative set is fundamentally a short wave local receiver. Its efficiency decreases rapidly as the wave length is increased. The shorter the wave the more efficient it is. Likewise on distant stations the set does not compare in sensitiveness with the more common simple regenerative sets.

### Multi-Tube Super-Sets Are Preferable.

The most desirable forms of super-regenerative sets incorporate three tubes, one being used as an oscillator, one as a detector, and the third as an audio frequency amplifier.

There are single-tube super-regenerative sets, but it will be understood that it is much more difficult to adjust the three circuits when one tube is acting as a combined generator, detector, and amplifier than when each of these functions is being carried out by a single tube.


In the paragraphs that follow directions are given for the construction of a workable one tube super-regenerator. In view of what has just been said concerning the added difficulty to be encountered in making what is known as a "flivver" super-regenerator, it may seem strange that this is the only one to be described in this manual. The selection is made for one reason—available space. It seemed to the editors to be a better procedure to treat a smaller set more fully than to skim over the general details of a more extensive outfit. And the re-



WIRELESS



APPARATUS

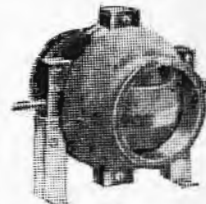

## "The Complete Quality Radio Line"

### ASK YOUR DEALER FOR BESTONE

VARIOMETERS	VARIOCOUPERS	TRANSFORMERS
CRYSTAL DETECTORS	HEAD SETS	V. T. SOCKETS
INSTRUMENT DIALS	TELEPHONE PLUGS	RADIO JACKS
RHEOSTATS	POTENTIOMETERS	INSULATORS
VARIABLE CONDENSERS	FIXED CONDENSERS	BINDING POSTS
SWITCH POINTS	SLIDERS	IND. SWITCHES
BATTERY SWITCHES	B BATTERIES	RECEIVING SETS

Made by a reliable firm, known throughout the world, who for many years have been marketing quality electrical and metal specialties.

**HENRY HYMAN & COMPANY, Inc.**


Executive Offices?  
476 Broadway  
New York

Manufacturers

Branch:  
212 W. Austin Ave.  
Chicago, Ill.



715

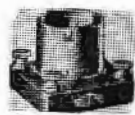

721



714



730



711



723

## Battery Charging

Don't send your battery out for recharging—

Get away from inconvenience. Charge it at home with a

### King Battery Recharger

with safety, ease and speed.

Both types—vibrator or bulb. Every safe charging rate for home use.

Be sure of the name—RADIO A for the vibrator type, and ELECTRON for the bulb type. Both have unusual features that make their operation simple, safe and sure. All good dealers. Insist upon the product of the

**KING ELECTRIC MFG. CO.,**  
INC.

Buffalo, N. Y.

**Southgate & Company**

Eastern Sales Agents  
35 Warren St., New York, N. Y.

## The Neon Lightning Arrester

The foremost Lightning Arrester on the market.

It protects against Lightning and Light-service circuits.

Helps eliminate static.

Approved by the Underwriter Laboratories and the Tribune Radio Laboratory.

For indoor and outdoor use. Everlasting.



Price \$1.50

THE NEON LIGHTNING ARRESTER can also be used as rectifier for small currents of Max. 5 M. A. NEW NEON RECTIFIER, capacity 150 M. A.; operating voltage, 220 volts up. Ideal for charging B Batteries. No filament. No moving parts.

PRICE \$6.00

SHIPPED PREPAID TO ANY PART OF THE U. S. A.

**THE NEON LAMP WORKS, Inc.**  
62 WEST 14th STREET NEW YORK CITY

## ALPHA VACUUM TUBES

For Wireless Reception. Patent applied for.

Alpha Type I, 5 volt. .25 Amperes.  
Alpha Type II, 1½ volt. .25 Amperes. 1 Drycell.  
Newest Alpha Type III, 2½ volt. .08 Ampere. 2 Drycells.  
Plate voltage, 20 to 90 volts. All standard bases.  
The quality of these Vacuum Tubes is of the highest and fully guaranteed.

PRICE \$5.00—Any part of U. S. A.

Manufactured by **F. ALEXANDER, 62 W. 14th St., New York City** DEALERS WANTED


ceiver pictured is a most successful one, with a minimum of parts and of critical adjustments. As a matter of fact, its adjustments are but two, a variometer to control the regeneration and the condenser for close tuning.

With a 20-inch loop this receiver should do remarkable work on stations within fifty miles and on powerful stations within twenty-five miles should amplify sounds sufficiently to operate a loud speaker.

For the vacation trip this small compact set will add greatly to the pleasure to be derived. A list of all the necessary parts is given: One .0005 variable condenser type; one DL1,250 honeycomb coil; one DL1,500 honeycomb coil; one .001 fixed condenser; one .002 fixed 'phone condenser; 45-volt plate battery; one variometer; VT 1-vacuum tube, better known as the J tube; one rheostat; three dry batteries, and the necessary hardware. In laying out the variometer and the condenser the builder may have to place extension shafts on the present shafts in order to mount the instruments away from panel.

Nine small flashlight batteries should be purchased and soldered together. This would give about 40 volts. When soldering the connections together a wad of tape should be rolled around the dry cells, merely as a support to hold them together.

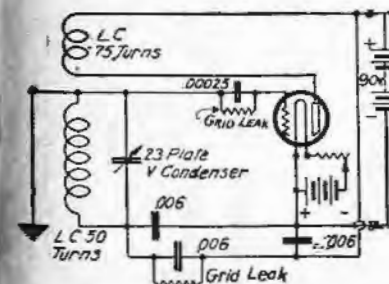The source used to supply the necessary filament current to the tube is a dry battery, three cells giving



The Flewelling Circuit.

enough voltage to hold out for at least two days' entertainment. Should the set be used at home where a storage battery is available it would be a great advantage to the experimenter if this source of power could be used. Dry cell batteries are only intended for use when the set is actually on the road.

Secure a piece of composition panel 8x14 inches, measure off the necessary dimensions as supplied in

the accompanying sketch. Drill the necessary holes, bevelling off the ends of the panel in order to make a snug fit when the panel is mounted in the cabinet.

The variometer should be purchased complete. By doing this better results will be secured. A purchased variometer is far more efficient than a home-made one, and as only one tube is to be used every little advantage must be taken into consideration to get results. The variometer should be mounted on the right of the panel, ample room being allowed in order to secure the DL1,250 above this. After the variometer has been securely fastened to panel place the DL1,250 honeycomb coil in a position above the variometer so that it lies horizontally, say about one-half inch above. The DL coil can be secured by using a small piece of composition panel strip and brass bracket as shown in the photograph.

The vacuum tube socket in this case is mounted in the centre of the panel toward the base of it. A good vacuum tube socket should be purchased, especially one made of high grade composition.

The condenser should be mounted on two strips of panel measuring 4 inches long, ½ inch wide, and about ¼ inch thick. A piece of brass sheeting measuring 4¼x3½ inches should be neatly fastened by screws to the strips. On top of this, in its proper location, is mounted the condenser.


This second honeycomb coil is mounted underneath the condenser instead of on top, as in the case of the variometer. Ample room will be found for it. It should be secured in the same manner as the other coil. In placing the two coils either can be used in either place, but where a DL1,250 is used a 1,500 must be used in the corresponding space.

The loop aerial used in conjunction with this portable set measures 2 feet square. Two strips of composition panel were used. The strips measured ¼ inch square. A groove was made every half inch to hold the wire. When clamping both strips an other piece 5 inches square was used, and clamped as shown in photograph. The conductor was No. 20 silk-covered wire wound to twenty turns. Two terminals are brought down to make connection with the binding post at the top of cabinet.

The cabinet for this set measures 8x14 inches. The purchase of the panel is advised, since the construc-

tion of a cabinet ready-made is far better than the builder can turn it out himself. The cabinet itself should be fitted with a cover.

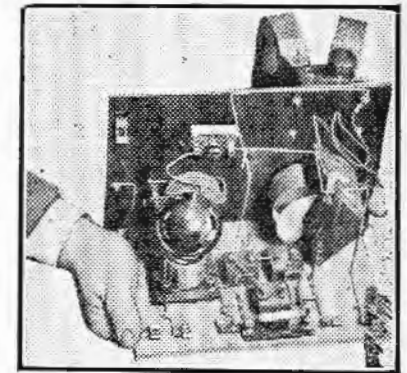To listen in, turn up the rheostat until the tube shows a fair brilliancy. Never allow the filament to burn brightly, as it may mean the destruction of the tube. Adjust the condenser dial to the wave length desired. Turn variometer handle for proper amplification, and finally turn the loop to increase the volume.



Rear of Completed Flewelling.

One of the most interesting of receivers embodying in some degree the fundamentals of the super-regenerative set is the Flewelling. As in the case of the Armstrong the details of the action are much too complicated and obscure for this treatise, but fortunately the details of construction are such that any one with a knack of following suggestions may build an outfit that should prove satisfactory.

### Flewelling Set Obviates Large Coils.

The principal feature of the Flewelling circuit is the bank of three condensers and the critical grid leaks. The other materials needed are two honeycomb coils, a DL50 and a DL75, a 23-plate vernier condenser, a hard vacuum tube such as the WD11, the 201A, or the VT2, about 90 volts of B battery and a suitable A battery for the particular tube used. A two-coil mounting should be provided in order that the coupling between the two duolaterals may easily be varied. Some experimenters, it should be stated here, have obtained excellent results by substituting a variocoupler for these two coils. If this is done the number of turns on the secondary must be increased by about 100 per cent. Since the number of turns already on the rotor varies with the make of instrument, the use of a var-

ASK ANY "ALL-WAVE" COUPLER USER. THEY ALL GET

## DX STATIONS LOUD AND CLEAR

WITH THE GENUINE AND GUARANTEED

### "ALL-WAVE"

(TRADE MARK)

## COUPLER

And any one of the Several Simple Super Sensitive Single  
Circuit DX Hookups

**GIVEN FREE** with each Genuine and Guar-  
anteed "All-Wave" Coupler


It is an established fact that any one of the simple Single Circuit  
hookups used in conjunction with the Genuine and GUARANTEED  
"ALL-WAVE" COUPLER will bring in "DX" stations louder and  
clearer than any double circuit can.

WAVE LENGTH 150 to 3000 Meters

PRICE, \$9.00 effecting a real saving  
inasmuch as

ALL VARIOMETERS, VARIOCOUPERS AND LOADING COILS ARE ELIMINATED  
6 HOOKUPS SENT UPON RECEIPT OF 10c TO COVER COST OF MAILING.

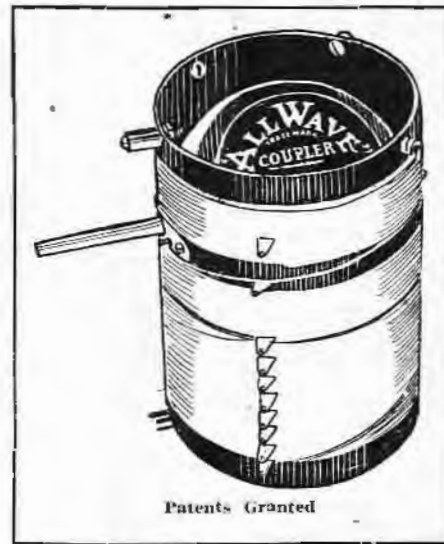Capitol Phonolier Corporation 58-60 LAFAYETTE ST.  
NEW YORK CITY



locoupler frequently calls for consid-  
erable experimentation before the  
correct turns are found.

The three condensers in the bank  
have a capacity each of .006mfd. Only  
first-grade mica condensers should  
be used here. Paper condensers are  
apt to be punctured by the high fre-  
quency currents they must withstand,  
and when this happens it is difficult  
to lay the trouble at their door un-  
less very special testing apparatus  
is employed. So to play safe it is  
far more economical to buy the bet-  
ter grade first.

The Flewelling set will work with  
either antenna or ground, with both  
or with neither. Usually it will work  
best with a good antenna or a good  
ground, hence if either one is avail-  
able plans should be made to utilize  
it. Reception without antenna and  
ground is possible, but except in cer-  
tain well-balanced receivers the re-  
sults are unsatisfactory.

The DL 50 coil is both primary  
and secondary with the 23-plate  
vernier condenser directly across it  
for tuning purposes. The DL 75 is  
the tickler coil and is inserted in the  
plate circuit. The position of the  
condensers is best shown by the dia-  
gram. This wiring diagram should  
be followed in every detail.

As mentioned previously, the grid  
leaks are exceedingly critical, par-  
ticularly the one across the bank of  
condensers. In selecting the leak  
care should be taken that the instru-  
ment used has the most gradual of

adjustments. The figures noted on  
the drawings are the values that  
have been found most suitable by a  
number of radio fans who have built  
the set.

#### Steps to Take in Operating the Flewelling.

The first step is to place the two  
dnolateral coils close together. Set  
the twenty-three-plate condenser so  
that the movable plates are half way  
in mesh. Place the phones just for-  
ward of the ears, so that the sudden  
start of the oscillations when the  
tube is lighted will not affect the  
ear drums. Then light the tube. Im-  
mediately the phones should indicate  
the presence of the "Flewelling whis-  
tle." If no sound results, adjust the  
two grid leaks either simultaneously  
or singly until a noise is heard. It  
may even be found necessary to  
vary the condenser slightly at the  
same time. If connections are fol-  
lowed and all parts are perfect one  
or more of these moves should result  
in the generation of oscillations by  
the tube. When these start the next  
move is to loosen the coupling be-  
tween the two coils. "Loosening the  
coupling" means to separate them.

As this is done it is probable that  
the tone of the whistle will change  
gradually, growing higher. If the  
whistle breaks and stops before a  
broadcast station is brought in, bring  
the coils together again, alter the po-  
sition of the condenser slightly and  
try again. At some point the stations  
will be heard. Their presence will


first be denoted by the familiar  
"whisp," as in any regenerative set.  
Once the location of the station has  
been found it should be easily tuned  
in by means of the condenser and the  
vernier.

When the station is tuned in  
clearly it is possible that the whistle  
is still so loud that the sounds are  
smothered. To clear up the whistle  
alter the grid leaks slightly until the  
pitch of the whistle becomes so high  
as to be negligible.

While some remarkable distance  
records have been scored with the  
Flewelling, it, like the Armstrong, is  
essentially for local work. High  
amplification is gained by increasing  
the plate voltage, the limit of this  
voltage being determined by the type  
of tube used. With a WD11 tube this  
is reached at about 135 volts, with a  
201A at about 200 volts and with the  
VT2 at 250 volts.

One disagreeable property of the  
Flewelling circuit is the presence of  
an exorbitant amount of stray ca-  
pacity. This bothersome feature can-  
not be entirely eliminated perhaps,  
but it can be reduced to a point  
where operation is made easier by  
shielding the inside of the panel  
with a copper sheet. This bit of work  
might as well be done while the set  
is being assembled, because it is cer-  
tain that later on the user will find  
it absolutely necessary and the labor  
in taking down a set after once get-  
ting it in working order is not to be  
disposed of lightly.

## Pilot Radio Products!

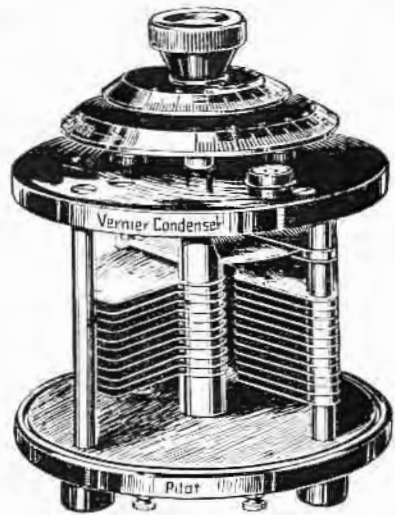

MFRS. OF HIGH GRADE

Condensers, Plugs,  
Jacks, Etc.

PILOT ELECTRIC MFG. CO., INC.  
113-119 Broadway, - BROOKLYN, N. Y.

## MURDON DRY CELL TUBE

is ideal under all conditions for  
clear and dependable reception.  
One dry cell, 1½ volt, will  
operate efficiently.

The New Murdon Super .08 oper-  
ates on two dry cells for first and  
subsequent relays. It draws .08  
Amp.

Also the Murdon A 5 works from  
3 to 5 volts; draws ¼ amp. Highly  
recommended for volume.

Each tube is fully guaranteed

New List Price on Each \$5.50


MURDON APPLIANCE CO.

160 Fifth Ave.

New York

Sold to dealers only

Radio fans inquire of your dealers.

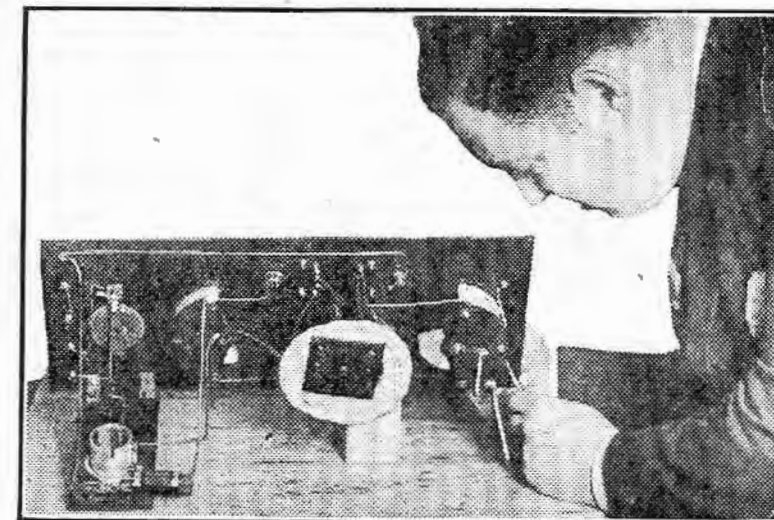

Rear view of the popular Reinartz circuit, known for its selectivity.

# A Letter That Will Interest Every Radio Fan

Form No. 308

200 Bks-10-22-D.P.

THE MARCONI WIRELESS TELEGRAPH COMPANY OF CANADA, LIMITED  
S. S. "METHVEN"

Radio Dept.,  
U. S. Tool Co.,  
Newark, N. J.

STATION March 2, 1923.  
Avonmouth, G. B.

Gentlemen:—

I purchased two of your 43 plate condensers with 3 Plate verniers from H. V. McKinnon, New Brunswick Radio Office, 108 Prince William St., St. John, N. B.

These condensers I connected in a set using a tickler feed back circuit. There are in all about 45 connections in my set just held by nuts, and not one is soldered. I am sure you will agree that according to the enclosed cutting, your condensers work.

I've had no difficulty in picking up distant C.W. or radio concerts with them and have used them commercially (average 12 hours a day) for the past 5 months, in which time they have stood the test, given good results and are just as good as new.

Yours truly,

*Harold W. Guiner.*

Marconi Operator on S.S. Methven between Fastnet and Queenstown, off the Irish Coast, on Feb. 24, 1923, using U. S. TOOL CONDENSERS and one tube, heard W. G. Y., Schenectady, N. Y.

Over 200,000 satisfied amateurs to date—increasing at the rate of 1000 daily.

You can purchase U. S. TOOL CONDENSERS at practically all Radio, Electrical and Hardware stores. If for some reason your nearest dealer cannot supply you notify us and we will be glad to see THAT YOU ARE TAKEN CARE OF PROMPTLY.

**U. S. TOOL CO., Inc.**  
MANUFACTURERS — ENGINEERS  
117 Mechanic Street  
NEWARK, N. J.

N. Y. City Distributor New Jersey Distributor  
WIRELESS KLEIN CO. E. M. WILSON & SON  
25 Church St., 11 Lafayette St.,  
N. Y. City Newark, N. J.

## More SALES More PROFITS

IMPORT NOVELTY CO. supplies in your window attract customers to your store. And IMPORT NOVELTY CO. dealer discounts allow you to sell lower and make more.

### INITIALED BINDING POSTS



Little sales mean other sales. Set builders want initialed binding posts to save panel-marking. They buy them from you and naturally buy the rest of their supplies in the same store if the price is right. Our liberal discounts make your prices low.

WHICH 15¢ EACH COMPLETE SET ONE DOLLAR

Manufactured and Distributed Exclusively by  
IMPORT NOVELTY CO., Inc.  
147 West 23rd Street Phone WAtkins 0213 NEW YORK CITY

### DISTRIBUTORS FOR

Scranton Button Dials  
Klosner Rheostats

Warkrite Products  
Cico Plugs

### IMNOVELCO PRODUCTS

Spaghetti Transformers  
Fada Type Switch Levers  
Cico Two-Way Plugs  
Suneco WD 11 Adapter Lugs  
Initial Binding Posts  
Composition Binding Posts  
Switch Levers  
2" Scranton Dials  
3" Scranton Dials

3 1/2" Scranton Dials  
Warkrite Variometers  
Warkrite Variocouplers  
Switch Points  
Switch Stops  
3" Auburn Dials  
Framingham Plain Rheostats  
Framingham Vernier Rheostats  
Rheostats  
Double Binding Posts  
Pilot Plugs

**Import Novelty Co., Inc.**

Manufacturers and Distributors

147 West 23d Street

New York City

## "CURTANTENNA"

(Patent Pending)

At Last — The Loop  
All Radio Fans Have  
Been Waiting For

The only—really—portable loop. Rolls up without injuring or disarranging the wires. The largest and most efficient loop when opened—the smallest when closed. Can be set up in a few moments. Comes with wall bracket swivel or can be attached to door. Ideal for sharp tuning—volume can be varied at pleasure. Positive in results, attractive in appearance. Cheaper than majority of loops half the size, more effective than any irrespective of price. Over 1,200 miles have been covered on the "Curtantenna."

Ask your dealer to save you one. Samples and demonstrations at our offices.

Descriptive Circular on Request

**GREAT EASTERN RADIO CORP.**

25 West Broadway, Cor. Park Place  
NEW YORK

(Manufacturers of Great Eastern 5 Tube Receiver)

## Reflex Receivers

### Theory of These New and Sensitive Sets, With Suggestions on the Selection of Parts and the Construction of One- and Two-Tube Outfits.

One of the remarkable developments of this epoch-making year is the so-called reflex system of reception. This circuit causes the same amplifying tubes to act as magnifiers of radio and audio frequencies without interference in such a manner that three tubes do the work of six or two tubes do the work of four.

A reflex amplifier can be made from a single electron tube and crystal detector, the single tube serving both as a radio frequency and as an audio frequency amplifier. If it is desired to have sufficient amplification to operate a loud speaker it is usually necessary to add two stages of audio frequency amplification. In a reflex circuit this is accomplished by three tubes. The first two tubes serve as radio amplifiers and also as audio amplifiers. The third tube acts as the detector tube.

### A Workable Single Tube Reflex Circuit.

The circuit about to be described is very simple and can be made up by the beginner at a small cost. The idea of this simple set is to make use of the tube for both functions, as previously explained. The incoming oscillations are amplified at radio frequency by the vacuum tube and then passed on through the radio frequency transformer to the crystal detector circuit, where they are rectified and changed to audio frequency oscillation.

These oscillations are then fed back into the tube only to be again amplified by the tube, whence the amplified signals are then passed on to the detector tube. Thus it can be seen that with one tube we have what is generally accomplished with two in other circuits.


Besides these advantages there are two other outstanding features of note. The circuit is quiet in operation, inasmuch as there are no tube noises. This is of extreme importance on very weak signals. Last, but not least, the circuit brings back

the crystal detector, which makes possible a distortionless rectifying circuit.

A circuit shown is a one-tube reflex with crystal detector. If this set is made up, the builder should see that the leads are kept short and direct, thus making the set much more efficient.

One tube that works particularly well with the reflex is the new

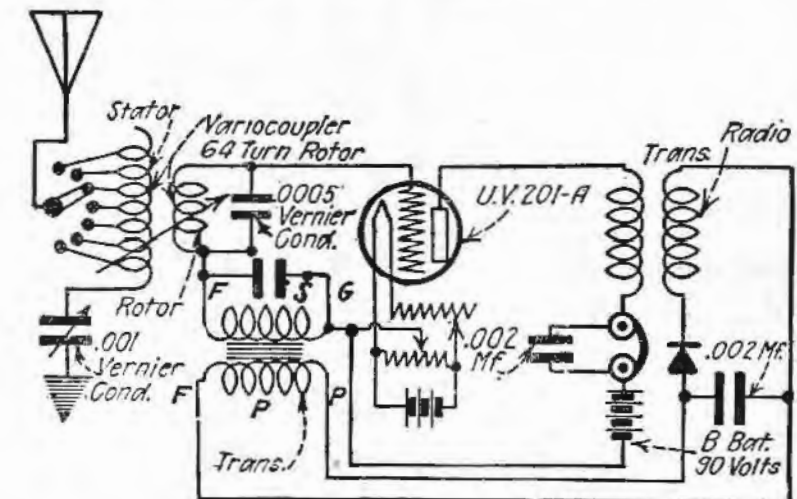of the rotor. The condenser in the aerial is optional. The fan who is considering the conversion of his crystal set into a vacuum tube set should study this circuit, for he may still use his crystal detector to good advantage. The only additional items needed in changing over that of the plain tube circuit is the use of two transformers and the crystal detector.



A One-Tube Reflex Receiver.

U201A. The WD11 or WD12 does not seem to produce results, for the simple reason that the plate of the tube will not stand up under the plate load. The small "N" tube, if available, would be a tube from which some results could be expected. The main point, however, is to see that the tube has sufficient plate to stand up under plate voltages recommended for the set.

### How to Operate the One-Tube Reflex.

To operate this outfit the cat-whisker should be in contact with the crystal. Turn on the filament, lighting the tube gradually. Continue turning the rheostat until a screeching or rumbling sound is heard in the head telephones. This noise may be stopped by adjusting the secondary variable condenser and the secondary

A final word about purchasing apparatus. Do not be influenced entirely by price. Pick out merchandise that is trademarked and that has a reputable manufacturer's name, together with proper research facilities behind it. In radio work we deal with such minute electrical impulses that the best should be the rule rather than the exception. A little additional outlay will well repay the builder by superior and consistent results.

### Construction of a Two-Tube Reflex Set.

The two-tube set is the equivalent of two stages of audio frequency amplification and two stages of radio frequency amplification. Using this set with a loop antenna, the fan will find that the signals come in clear and strong with a fairly good range.

# U. S. BUREAU OF LIGHTHOUSES INDORSES SPIDER WEB COILS

Eugene T. Turney's patent on Spider Web Winding is the only one granted by the Government.



TURNEY SPIDER WEB PLEX

Turney Spider Web Coils are wound on automatic machines, also patented. Absolute uniformity is certain.

Yes, Government Bureau tests tell the story—Spider Web Windings have proved to be the best form of Inductances in Radio today. And so they will be used in Government Lighthouse Sets.

Turney Spider Web Coils are wound by a newly patented machine that keeps the wire completely surrounded by dielectric, 95% of which is air. Result—harmonics which are exceptionally pure and many times more resonant than ordinary hand-wound coils. And cheaper, less bulky, more efficient than Duolateral Coils.

Wave length range—960 meters with condenser in shunt. No body capacity. Eliminates the Variocoupler as a Tuning unit.

The Radio News says editorially: "We make the prediction that Spider Web, or basket weave, Coils will be used by Radio Experimenters exclusively before many months have passed."

See your dealer, or mailed direct on receipt of cash or money order (no stamps or checks). **\$4.50**. Hookups for tube and crystal sets included.

## TRISTAN SALES CORPORATION

No. 1 UNION SQUARE, NEW YORK CITY

Sole National Distributors

## Advance Battery Co.



FOR



LOUD SPEAKERS  
TRANSMISSION  
GRID-BATTERIES

MADE IN U. S. A.

DATE

Especially designed for Radio Work. Noiseless operation and long life.


Manufactured by experts of over twenty years' experience in the battery business.

At all good dealers.

## ADVANCE BATTERY CO.

506 West Broadway  
NEW YORK CITY

## Koehler Vernier Condenser

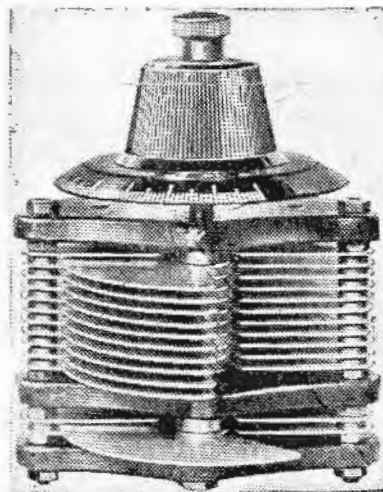

List of Koehler Products:

### CONDENSERS

- 3-Plate Condenser
- 5-Plate Condenser.
- 11-Plate Condenser.
- 21-Plate Condenser.
- 43-Plate Condenser.

### VERNIER TYPE

- 14-Plate Vernier Condenser, with bakelite dial.
- 24-Plate Vernier Condenser, with bakelite dial.
- 46-Plate Vernier Condenser, with bakelite dial.

### VARIOCOUPERS

- 180 deg. Fibre tubing, brown covered wire.
- 180 deg. Genuine natural bakelite tubing, green silk covered wire.
- Genuine natural colored bakelite variometer, green silk covered.
- Wave Trap, with 3-inch bakelite dial.

MANUFACTURED BY

## KOEHLER MACHINE & TOOL CO.

152 Sussex Avenue, Newark, N. J.

The only additional feature is the use of a by-pass condenser across the secondary of the audio frequency transformer.

In the two-tube reflex circuit shown, the tubes act as radio frequency amplifiers for the purpose of building up the incoming signal, to be later rectified by means of the crys-

The by-pass condenser will be found of great value to the experimenter and constructor, especially when inserted around head telephones or loud-speaking devices. If this by-pass condenser is left out of the circuit around the head telephones the 'phones have a tendency to act as a choke coil. These small

The coupling used to the best advantage on these short waves is that of the transformer. It eliminates tube noises and allows the circuit to operate quietly.


Using the crystal detector brings us back to the old days when such detectors were in power. The crystal is used in the reflex to great advantage. It eliminates the noises from the tubes and batteries and make the set distortionless. These gains offset the loss in signal strength.

A loop aerial is recommended with the reflex circuit, but an outside aerial will function as well. Of course, the inherent tube noises and atmospheric static noises will be greatly eliminated if the loop is used.
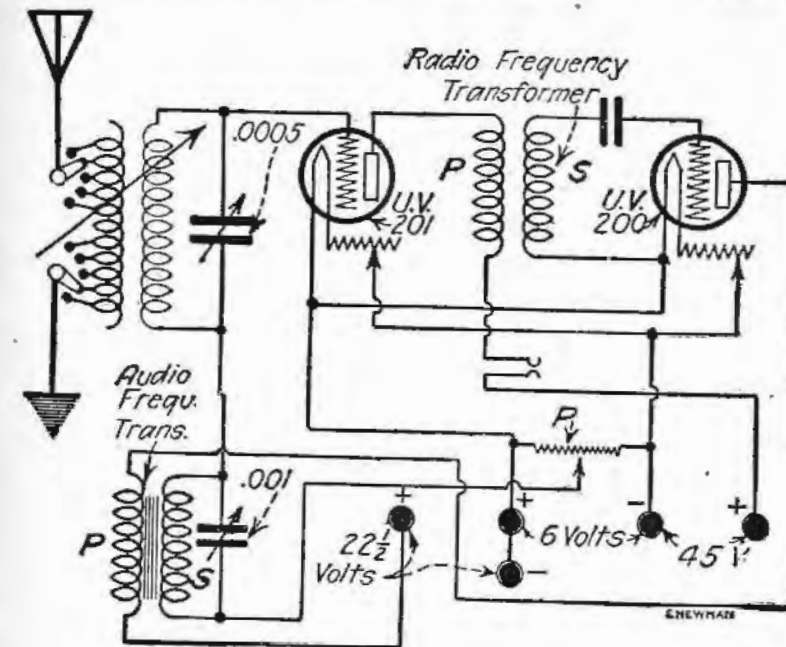
### Potential of B Battery Is Important Factor.

The two-tube circuit differs slightly from the one-tube set in that it uses a tube as a means of detection. The plate voltage of this set depends on whether a hard or soft tube is used. A soft tube is recommended, but in such a case a vernier rheostat must be employed in the circuit. When constructing such sets extreme care should be taken in the wiring, keeping all wires that run parallel as far apart as possible, and making sure that there is no chance for a short circuit. If further amplification of the signals is desired the batteries of the amplifier should be separated from those of the circuit proper.

If amplifier tubes are used in all three stages the B battery should be



A Two-Tube Reflex Receiver.

tal or vacuum tube detector. The entire receiver can be enclosed in a compact case and made to operate successfully on a loop aerial.


In the actual application of this circuit there are several difficulties that have to be overcome. The tubes, for instance, must be coupled for both radio and audio frequency circuits, but in placing an audio frequency amplifying transformer in a circuit in which radio frequency currents are flowing the windings of the secondary act as a choke coil and prevent the radio frequency currents from passing.

To overcome this a condenser is shunted around the secondary windings of the audio frequency transformer, unless the secondary winding of the audio frequency transformer has a sufficiently high distributed capacity to make its impedance low. The American-made tube has a high internal capacity which is bad for R. F. amplification.

The amateur attempting to build reflex sets should not employ regeneration, for once the tube starts oscillating the whole set may become paralyzed, due to the tubes becoming choked.

by-pass condensers, which are of .002 mfd. capacity, are essential, and no reflex circuit will function satisfactorily unless they are properly placed in the circuit. They must also be of the correct value.

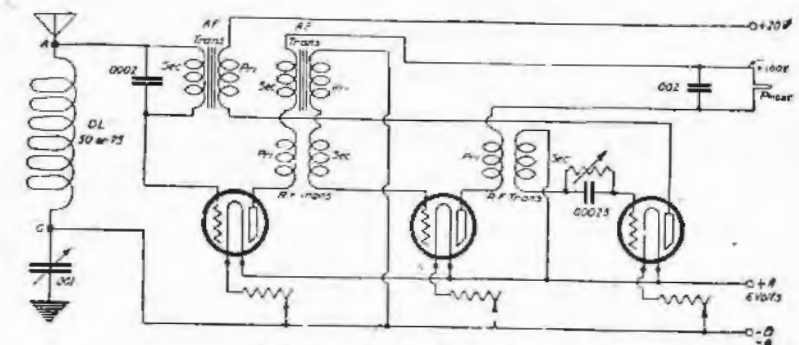There are various ways in which coupling may be employed. For the



Reflexing With Three Tubes.

shorter waves the coupling may consist of an ordinary choke coil, radio frequency transformer, or a tuned impedance. Due to the fact that we are most interested in the 360-meter to 492-meter wave lengths of the various broadcasting stations, we must give our attention to that wave.

regulated so that the proper voltage is applied to the respective plates. This is accomplished by experiment. Usually between 40 and 70 volts are found best for the plates of the tubes, and sometimes as high as 125 volts. In the diagram the plate current is indicated as 1,000 volts, but the real



**HERE IS A PHONE**

That has stood the exacting test of one of the Best Radio Laboratories in the country.

**"The National Ultratone"**

Loud and Clear. Twice the amount we are quoting this headset at could not purchase a better one. Guaranteed to give satisfaction.

LIST \$7.50  
SPECIAL

**\$3.85**



**It Does Make a Big Difference**

**WHERE YOU PURCHASE YOUR RADIO GOODS**

*New York's Leading Radio Retailer*

**WE** gained our prestige in the Radio Field and the honor of the above title because we served the public best.

**T**HOUSANDS of Radio Parts and Sets always in stock at reduced prices.

**S**OUR EIGHT LARGE SHOW WINDOWS

**E**OUR WONDERFUL UP-STAIRS SHOW ROOMS.

**E**OUR ADVERTISEMENTS IN THE PAPERS.

**LIBERTY RADIO CO.**

106 Liberty Street, New York City

WHOLESALE

RETAIL

MAIL ORDER


**THE TODD BATTERY**

*The Right Battery for Best Results*

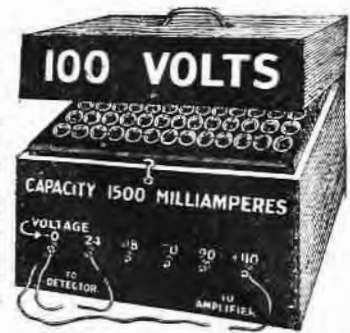**ONE THAT WILL LAST YOU A LIFE TIME**

A Portable Outfit  
**Efficient**

THE TODD BATTERY is an indestructible rechargeable Storage "B" Battery, made up of Edison Storage Battery Elements. Will work any Radio Set. Entire capacity can be utilized.



**ECONOMICAL**

This remarkable battery will repay itself in less than 1 year. Actual amount of current required for charging costs about 2 cents, and each charge will last from 2 to 6 months.

We make them in 2 sizes:—

45 Volts at... \$ 9.25

100 Volts at... 16.50

**SAFE**

Has no internal discharge, therefore it can safely stand on your shelf for a lengthy period without danger of discharging itself. Unlike lead-acid or dry-cell batteries, the TODD will not be injured by a short-circuit.

MAIL ORDERS PROMPTLY FILLED

**TODD RADIO & ELECTRIC CO.**  
178 LAFAYETTE ST., Near Grand St., N. Y.



**SABCO**

**JUNIOR**

Single Heat

**ELECTRIC SOLDERING IRON**

Specially constructed to meet the requirements of radio work.

*A tool that will give you absolute satisfaction.*

The Sabco Junior is a worthy little brother of the famous family of Sabco Electric Soldering Irons and is absolutely guaranteed against defects in workmanship or material for a period of one year.

*Do not accept a substitute. If your dealer cannot supply you we will send your SABCO, carefully packed, carriage prepaid, on receipt of \$5.00; west of Mississippi River \$5.50.*

**STRAUSS & BLUM, Inc.**

DEPT. G., 254 WEST 41st STREET, NEWYORK CITY, N. Y.

value is obtained only by experiments.

In the actual application of this circuit there are several difficulties to be overcome. The tubes, for instance, must be coupled for both radio and audio frequency circuits, but in placing an audio frequency amplifying transformer in a circuit in which radio frequency currents are flowing the windings of the secondary act as a choke coil and prevent the radio frequency currents from passing. To overcome this result a condenser is shunted around the secondary of the audio frequency transformer, unless, as sometimes happens, the secondary winding of the audio frequency transformer has a sufficiently high distributed capacity to make its impedance low.

If the UV201A is used the builder should purchase a 25-ohm rheostat, in order to control the tubes properly.


Different tubes have a decided effect on the set as a whole and if not properly considered the whole circuit may be a total failure. Many radio frequency transformers in combination with various audio frequency transformers have been tried out.

With this set either aerial or loop may be used. The loop is recommended and the one used successfully with this set was wound on a frame with fourteen turns spaced three-eighths of an inch apart, the outer turn having a diameter of 23 inches. Number 20 wire, either col-

ton covered or bare, can be used to make up the loop.

When the amateur begins to tune in for DX stations he will hear considerable howling, which can be easily eliminated. Some of this

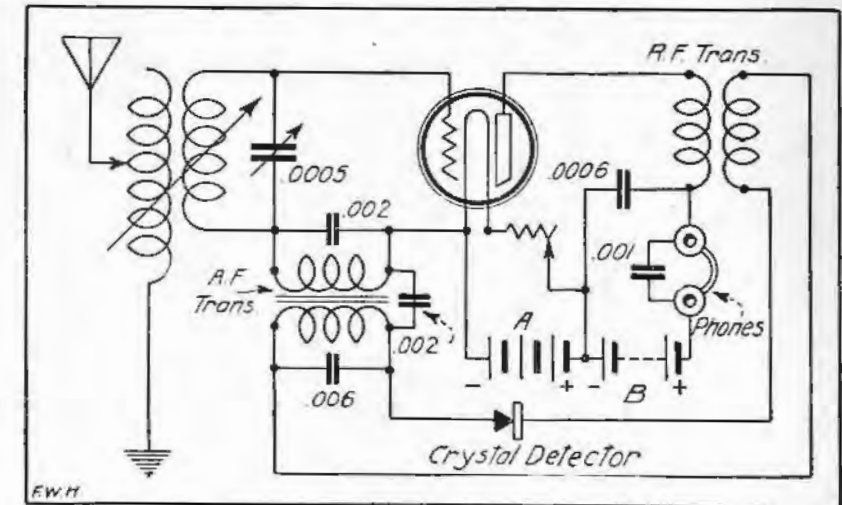positive side of the 100-volt line and the primary side of the radio frequency transformer in the second tube amplifier. The coil used for the inductance in the set is a DL50 or 75 with a .001 mfd. variable condenser




A Single Tube Reflex That Has Proved Its Worth.

howling can be easily reduced by regulating the filament rheostat. Careful adjustment of the filament voltage of the second amplifier tube and detector will be found to be the critical adjustments.

It will be noted that for stations of the 360-meter class the detector filament will require more current than for some of the 455- and 492-meter stations. The variable grid leak also is an important factor. The phones are placed across the plus or

in series when the aerial and ground are used as means of antenna.

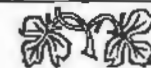If the loop aerial is used it will sometimes tend to make the tubes "spill over." Should the tube oscillate too much, reduce the value of the capacities in the condensers that are in shunt to the secondaries of the audio frequency transformers. In using the UV201A amplifying tubes it will be found that most of the tuning will be done with the condenser and filament rheostat.





TWO STORES:  
18TH STREET AND 33RD STREET TO  
7TH AVENUE 34TH STREET  
At the Subway Station Just East of Seventh Ave.

## The Road to Good Results

The road to good results with your radio begins at the Dixie door. Your set cannot function properly unless each instrument is of the best quality. And what is greater assurance of quality than

### The Dixie Creed?

"The best standard parts sold at low prices with an unconditional guarantee." That is the Dixie Creed.

### Whatever You Need

for complete radio enjoyment, buy it at Dixie. Convince yourself that the best radio merchandise can still be sold at prices that save you money.

"COMPARE and You'll Come to DIXIE"

## The SATURN "AUTOMATIC" RADIO PLUG \$1.25



THE PLUG WITH THE RED SEAL *The More You Pull the Better the Contact*

No more taking apart to make connections. Just insert the terminals into the Saturn and a perfect contact is made. So constructed that pulling on the cord makes the connection more positive. Let your customers try this test themselves. It will convince them that the Saturn "Automatic" is far superior to any plug on the market. Instantaneous disconnection just by touching this lever.  
Every plug is sealed and fully guaranteed.

## THE SATURN PERFECT JACK THIS IS OUR NO. 3.



This Jack is an improvement on all other Jacks on the market. The crossfoot offset allows easy soldering. The bracket is made of Brass, Nickel Plated; rounded corners. The Blades are of Spring German Silver. The Contact Points are Genuine Silver. The Nipples are shoulder type and are furnished with two washers, Nickel Plated and Polished.

- No. 1—Single Circuit Open ..... \$0.50
- No. 2—Single Circuit Closed ..... 0.55
- No. 3—Double Circuit Closed ..... 0.70
- No. 4—Single Filament Control ..... 0.75
- No. 5—Double Filament Control ..... 0.80

Write for catalog and discounts. Amateurs: If dealer cannot supply, order direct



**The Saturn Mfg. & Sales Co., Inc.**  
48 BEEKMAN STREET NEW YORK CITY  
Dept. G.

# The Storage Battery

## Its Design, Formation, and Construction, With Suitable Hints to Be Followed in Testing the Cells for Condition and Arranging for the Proper Recharging of Depleted Cells.

A storage battery is an essential with receiving sets incorporating certain types of vacuum tubes. These tubes—namely the UV200, UV201, VT1, and VT2—require such a high current for heating the filament to full brilliancy that some high capacity source of electricity must be utilized. This is best supplied by the storage battery.

The oldest type of storage battery is made up of lead cells. There are two classes of lead cells, the classification being based on the method of forming the active plates. One of these methods has the active material of the positive plates formed directly on the surface of the plates, an invention attributed to M. Plante. The other is called the "Faure" type and has the active material applied to the surface of the plates in the form of a paste.

The Plante type cell is considered heavier and stronger than the Faure type, and possesses greater durability when subjected to severe working conditions. Since the Faure type of cell is not so heavy for a given output it is usually adopted for use in vehicles.

### To Illustrate the Principle of Plate-Formation.

If two clean lead strips are placed in a solution of dilute sulphuric acid and their unimmersed ends connected with a galvanometer or sensitive voltmeter no deflection is noticeable. If a current from a primary cell or from any direct current source be allowed to pass from one strip to the other through the acid solution for a few minutes, and the circuit then broken and the strips again connected to the sensitive voltmeter, a movement of the meter will be noted. By observing the portions of the lead strips immersed in the solution it will be seen that one strip has undergone no change while the other has become coated with a brownish film. This

brownish coated film is peroxide of lead formed by the action of the electric current. The two lead strips are now dissimilar and act exactly as a primary cell.

The plates which make up these small cells of electrical energy are



(Photo by K. & H.)

The hydrometer shows the condition of the storage battery.

constructed chiefly of lead. The plates are generally cast and the pores filled with oxides whose component parts are varied, one combination producing what is known as the positive and another the negative plate.

The positive plate consists of minium, 70 per cent.; litharge, 8 per cent.; graphite, 12 per cent., and white of eggs, 10 per cent., the latter ingredient acting as a binder. For the negative plates the litharge is 95 per cent., the remaining 5 per cent. consisting of finely divided asbestos fibre or powdered porcelain.

The plates are made in various sizes, depending upon the capacity called for, capacity in turn being figured on size and area of plate, and the number of groups of plates assembled. When a cell is ready for assembly an even number of positive plates are connected to

together by a strap, preferably burned on by heat and an uneven number of negative plates attached in the same manner to another strap. It must be remembered that there is always one more negative plate than positive.

The electrolyte commonly used in lead storage batteries consists of a mixture of chemically pure acid, sulphuric acid, and pure distilled water. The acid should be made from sulphur and not from pyrites. The acid mixture is usually designated by its specific gravity, i. e., its weight compared with an equal volume of water. One pint of pure water weighs approximately 1 pound, while a pint of pure concentrated sulphuric acid weighs 1.835 pounds and is alluded to as eighteen thirty-five acid. The proper acid electrolyte is one having a specific gravity of about 1.225 at ordinary temperatures when the cells are fully charged. The final specific gravity on discharge should not fall below 1.185.

In mixing the acid and water to make the electrolyte, the water should first be put into a glazed earthenware jar and the acid slowly added in a very fine stream to prevent excessive production of heat and possible explosion. Never pour the water onto the acid. While mixing the acid with the water stir gently with a glass rod. Just after being mixed, the electrolyte is hot and has a lower specific gravity than when cold. The final adjustment of the specific gravity may be made by adding a small quantity of pure water to the cooled solution.

The electromotive force and internal resistance depend largely on the density of the acid electrolyte. The greater the density the greater the E. M. F., while the specific resistance of diluted sulphuric acid is least at a specific gravity of about 1.260 and increases or decreases from this value.

The voltage of a lead cell when

# Goodbye Aerials!

## SO LONG STATIC SHORT CUT ANTENNA

Replaces aerials, loops, socket-plugs, etc. Eliminates LIGHTNING dangers. Reduces STATIC and other interferences. Gives clearer signals and truer tone. Works on all standard vacuum tube sets. Makes your set PORTABLE. (Size 6 3/4 x 2 1/8 ins.) Send for your SHORT CUT to-day.

Postpaid anywhere in U. S. for \$5.00

Satisfaction Guaranteed or money refunded.



**SHORT CUT RADIO CORPORATION**  
DEPT. G.M.  
243 West 54th Street  
NEW YORK CITY



## The New Radio "A" Battery BEST BY TEST FOR RADIO

Written 18 Months' Bonded Guarantee

Sold by Radio Dealers Everywhere  
If Your Local Dealer Does Not Carry Them  
Write To Us Direct.

**SUTTER BATTERY CORPORATION**  
Formerly Ajax Battery, Distributors  
266 Sutter Ave. Dickens 0386  
Brooklyn, N. Y.

# Greenwich Radio Company

185 GREENWICH STREET  
NEW YORK CITY

We carry a complete line  
of

## Radio Parts

All Makes of Sets a Specialty

EVERY ITEM  
FULLY GUARANTEED

Wholesale and Retail  
MAIL ORDERS FILLED

# Recognized Standard Radio Accessories

## LOOP AERIAL R-C



In Knock Down Form  
Assembled in 5 Minutes

Retail Price

**\$1.00**

Eliminates Summer Static

## R-C CABINETS



High Grade Mahoganette  
To Match Home Furnishings

Hinge top. Lift Knob. So  
constructed that panel is  
locked in—top and bottom  
eliminating use of screws or  
drilling of panel for attach-  
ing.

Furnished complete with  
"Arceelite" Radiole Panel or  
without panel. A dust cover  
comes with each cabinet.  
Look for "R-C" label. Re-  
tail prices lower than for other  
cabinets of inferior make.

## R-C NUMBER 3 CABINET

To meet requirements for those seeking  
a serviceable low priced cabinet. Mahog-  
any finished.

### RETAIL PRICES

7 x 10, \$2.00 each	7 x 18, \$2.50 each
7 x 12, 2.15 each	7 x 21, 2.75 each
7 x 14, 2.25 each	7 x 24, 3.00 each



Ask Your Dealer. Look for Labels.  
We will send you dealer's name.

**The R-C MILLS, Mfrs.**

303 Fourth Avenue  
Gramercy 4139 New York City

fully charged is about 2.5 volts and  
should never be allowed to fall below  
1.8 on discharge.


Storage batteries are rated in am-  
pere-hours. The ampere-hour rating  
means that the battery will deliver

scale marked 1.000 to 1.300 on paper  
within and the lower part of the tube  
being enlarged to about twice its  
diameter. This base contains lead  
shot or some heavy substance that  
will cause it to stand upright as it

for testing the density of the acid.  
By slightly compressing the bulb and  
inserting the slender tube through  
the vent hole in the cover of the cell  
sufficient acid may be drawn up to  
float the hydrometer within the  
large glass tube and the reading made  
at once. The acid is returned to the  
cell by again compressing the bulb  
and the reading of the next cell  
taken. Should the hydrometer show  
a reading of less than 1.180 the bat-  
tery should be placed on charge.

After the storage battery has been  
in use for a short time its voltage  
becomes less than when first put  
into service and it becomes necessary  
to recharge the battery. The re-  
charging may be done from direct  
current wires or from alternating  
current mains if some form of rec-  
tifying device is employed to convert  
the alternating current into direct  
current.

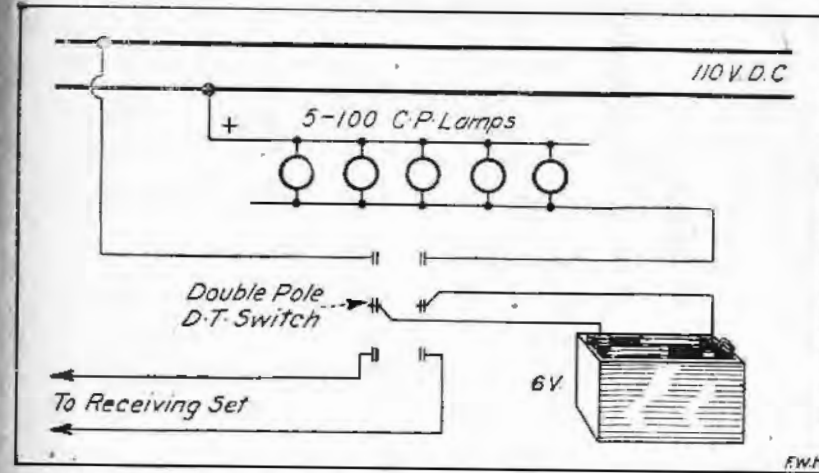All vent caps should be removed  
from the batteries while charging.  
Distilled water should be used. Al-  
ways keep the plates covered with  
water at least 1/2 inch over their  
tops. See that the polarities of the  
batteries are correctly right to that  
of the charger. See that the charger  
is connected up properly to the  
source of supply. The battery should



How to Connect the Parts for Charging a Battery From D. C. Lines.

a certain number of amperes for a  
certain number of hours. Take a  
40-ampere-hour battery. This bat-  
tery will deliver 1 ampere for 40  
hours or 5 amperes for 8 hours.  
The higher the ampere-hour rating  
the longer the battery will go with-  
out charging.


sinks in the electrolyte. The hydro-  
meter may be placed in the solution  
where the cells have open tops, but  
usually the solution is drawn up into  
the chamber of a syringe which con-  
tains the hydrometer. The hydro-  
meter syringe is a convenient device

### Storage Battery Capacity Rated in Ampere-Hours.

If a vacuum tube detector alone is  
being used, a 40-ampere-hour battery  
is sufficient. If amplifiers are em-  
ployed an 80- or even a 110-ampere  
battery is more suitable. Vacuum  
tubes of the standard type require  
about 1 ampere each, so that an 80-  
ampere battery should operate a re-  
ceiving set of 3 tubes for about 25  
hours, after which the battery must  
be recharged.

There are a number of ways to  
gauge the condition of a battery  
when it is discharged. They are the  
voltmeter process, the ampere-hour  
meter process, and by the use of  
what is called a hydrometer. With-  
out any of these instruments it is  
possible to judge the condition of a  
cell by applying it to the filament of  
the tubes. Should they decline to  
light up brilliantly when the full  
voltage of the battery is impressed,  
it is an indication that the battery  
needs charging.

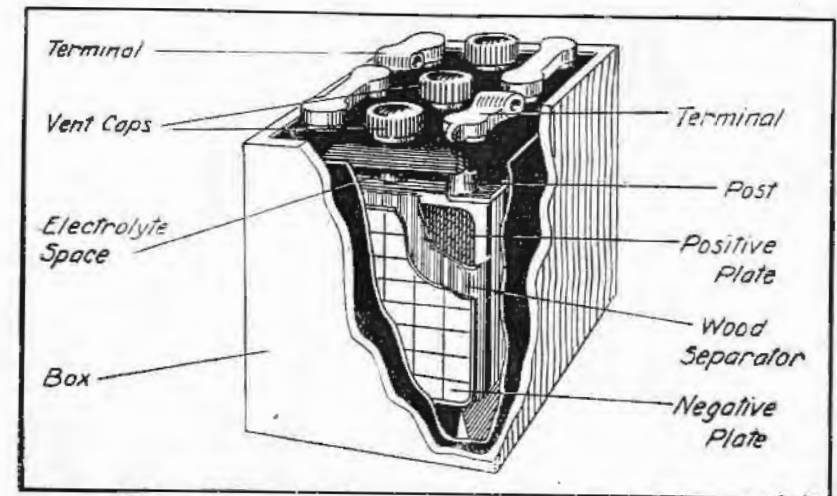However, the most useful instru-  
ment to note the condition of a cell  
or battery is a hydrometer. This is  
a glass tube containing a graduated



Storage batteries consist of alternating sets of positive and negative plates  
spaced in each instance by an insulating separator and surrounded on all sides  
by a solution of sulphuric acid called the electrolyte. In building a battery the  
positive and negative plates are punched or drawn in the form of grids and,  
plastered with a pasty mixture of oxides of lead. They are then given a long  
charge from a source of direct current which "forms" the plates. This term  
means that the oxides on the positive plates are further oxidized and changed  
into lead peroxide, a brown chemical. The current acts in the opposite manner  
on the negative plate and reduces the degree of oxidation, thereby changing  
the original lead oxide to the dull gray "spongy lead."

In the storage batteries used for radio all the positive plates in one cell  
are connected together and all the negative plates. Then the positive plates  
from one cell are connected by metal strips to the negative plates of the next  
cell, and so on through the three cells.

# NIAGARA

SUPER QUALITY

## RADIO "B" BATTERIES



### ASSURE NOISELESS RECEPTION

"HUMMING" and "SIZZLING" noises are en-  
tirely eliminated.

Powerful cells of scientifically proportioned  
pure ingredients assembled under expert laboratory  
supervision guarantee LONG LIFE—DEPEND-  
ABLE SERVICE—ECONOMICAL MAIN-  
TENANCE.

Every size for every type of set.

Ask your dealer or write us direct for bulletin.

**NIAGARA SEARCHLIGHT CO., INC.**

General Sales Department  
3 Waverly Place, New York City

## All Standard Makes of Radio Supplies

### At Reasonable Prices

It will pay you to send for our mail order  
price list.

Prices quoted on sets and parts desired.

MONEY BACK GUARANTEE

**Long Island Wireless Tel. Co.**  
1171-1173 Gates Ave., Brooklyn, N. Y.

## A NATIONAL RADIO TUBE SERVICE

Send us your burned out or broken Detectors or Amplifiers  
and receive maximum allowance on the purchase of NEW  
TUBES.

UNLIMITED QUANTITY ALWAYS ON HAND FOR  
IMMEDIATE SHIPMENT.

We allow you Seventy-Five Cents on an old U V 200 in the  
purchase of a new one and One Dollar on W D 11 and 12 when  
buying new Tubes. Corresponding allowances on all makes.

### RADIO TUBES REPAIRED IN ONE WEEK

Customers who purchase new tubes from us are entitled to a  
special discount on repair work. In other words, we sell you  
new tubes and then keep them in shape for you.

We also usually have on hand a quantity of uncalled for re-  
filled licensed tubes at very moderate prices, all guaranteed.  
"OUR REPAIRED TUBES SPEAK FOR THEMSELVES"

Write to-day for Circular M 9 which will explain all the  
details.

SHIPMENTS PROMPTLY MADE C. O. D. TO ALL POINTS  
IN THE U. S. A.

### RADIO TUBE LABORATORIES,

VACUUM TUBE SPECIALISTS,  
776 BROAD STREET, NEWARK, N. J., U. S. A.

# BRACH

## VACUUM RADIO PROTECTOR

The choice of foremost Engineers for over 17 years.

Sold by all dealers



Approved by National Board of Fire Underwriters



## SOLDERALL

Metal in Paste Form




Handy Tubes 25¢ Every Electrical Connection Needs

Solderall for Perfect Reception The Only Convenient Metal Solder

L.S. BRACH MFG. CO., Newark, New Jersey

## "ANCHOR" Lightning Protector

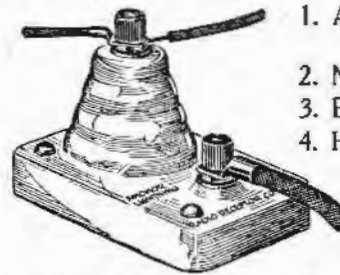

1. Absolutely Weather Proof
2. Nothing to Deteriorate
3. Easy to Install
4. High Insulation
5. Preserves Signal Energy

Price \$1.50

For INDOOR or OUTDOOR USE

Approved by National Board of Fire Underwriters

### VARIABLE-VERNIER CONDENSERS

PRECISION MADE  
BAKELITE INSULATED  
ACCURATE CAPACITY  
ALL SIZES  
PRICES ON REQUEST



No. E 5815

ACKERMAN BROS. CO., INC.  
Dept. "GM," 301 W. 4th St., New York City

## POTTER PRECISION

## RADIO RECEIVERS

FOR DX



Unrivaled for Loud-speakers

"MAKE PRECISION YOUR DECISION"

Manufactured By

S. A. Potter T. & M. Works

1914 Park Avenue, N. Y. City

## Amplification Perfection

with all standard tubes

An audio transformer will give the same results with all tubes which are alike in A. C. Impedance and Amplification Factor.

WD-11  
UV-199  
UV-201-A  
UV-201

WD-12  
C-299  
C-301-A  
C-301

These tubes all have nearly the same A. C. Impedance.

## AMERTRAN



is universally acknowledged the greatest of all amplifiers. It also produces perfect amplification with lower impedance tubes such as Western Elec. 216A, V.T.-2 and Radio Corp. U.V. 202, C-302.

Price \$7

American Transformer Company

Designers and builders of radio transformers for over 22 years.

184 Emmet St.

Newark, N. J.

placed and kept on charge until the reading of the electrolyte shows at least 1.225 or more on the hydrometer. Frequent readings should be taken while the battery is on charge.

An attempt should never be made to light the filaments of the set while the batteries are being charged. If this is done the tubes will be destroyed. When the battery is fully charged shut off the power and disconnect the battery from the charger. Care should be taken that the vent holes are closed up and the battery thoroughly cleaned. A little attention in keeping the battery clean will maintain its condition, thereby preventing short circuit from any material that may find its way in and around the terminals of the cells.

When connecting up the battery to the set see that the terminals are cleaned off. Use a small piece of sand paper. It may be noticed from time to time, as the battery is used, that the terminals show signs of a white deposit called "sulphation." A small amount of vaseline or petroleum placed about the terminals will tend to keep sulphation at a minimum.

For those who have direct current in their homes, a battery charger is

moving one lamp, one ampere will be lost from the charging rate. The correct charging amperage is generally marked on the battery by the maker. It is always best to charge the battery at a low rate. Remember, the slower the rate of discharge the longer the battery will last. Do not try to overload a battery nor discharge a battery too quickly.

The following list of don'ts for the storage battery user has been collected from battery experts:


- Don't charge faster than the rate that will keep the temperature of the liquid below 110 degrees Fahrenheit.
- Don't use any water except distilled water.
- Don't let the electrolyte get below the plate.
- Don't overcharge the cells.
- Don't let the cells stand idle longer than five weeks without giving them a charge.
- Don't let dirt or other mineral matter get into the cells.
- Don't charge a battery before removing the caps so gas may escape.
- Don't light any matches near the battery while it is being charged.

The vacuum tube is said to be the most sensitive electrical device in existence. The slightest electrical charge on the grid controls faithfully and instantly a strong current flowing between the filament and plate. In this manner it becomes possible to control a strong force by a weak force. The vacuum tube can be used for many purposes. It is a rectifier of alternating current, that is, it converts alternating current of almost any frequency and of any strength within its capacity into direct current. It also can convert direct current into alternating current of a wide range of frequencies. As stated previously it makes possible the control of a powerful current by a weak current. This feature is the basis of the amplifier. When the weak current from the detector is impressed on the amplifier tube a current several times as powerful is produced in the second tube, giving a much louder response in the telephone receiver.


Radio receiving sets employing vacuum tubes either for detector or amplifier must be equipped with some sort of battery for supplying them with a high voltage. This battery is called the B-battery to distinguish it from the other battery which lights the filament and is

known as the A-battery. The proper voltage of the B-battery is about twenty-two volts.

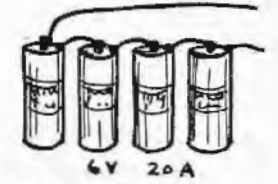The operator of a set should be sure that both batteries are connected correctly, for if the B-battery happens to become connected to the



6V 20A

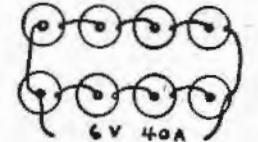

6V 40A



6V STORAGE BATTERY

Series Connection (Above) and Parallel Connection (Centre) of Dry Cells.

filament circuit the tube will burn out almost instantly.

There are several different types of B-batteries on the market, most of them satisfactory. The principal requirements are to have a battery that will supply a high voltage and a low amperage, since the actual drain on the battery is small. In fact, the B-battery usually succumbs to old age long before the current is consumed by the tube. The B-battery can be placed somewhere on a shelf at the back of the set and forgotten for several months.



### "B" Battery Needed to Supply Higher Voltage to Tubes.

The first type of B-battery to be considered is the small size, which delivers about twenty-two volts. These little batteries are good enough for ordinary work, but in some sets it is desirable to vary the voltage from the B-battery and in such a case as this it is best to secure one which is supplied with taps so that the voltage may be varied. The amateur may find that his particular vacuum tube will work the best with only twelve to eighteen volts on the plate, but as the battery gets older the voltage will need to be raised.

A little wrinkle in battery use may interest amateurs or novices.



Large Battery with Taps

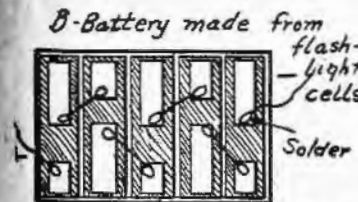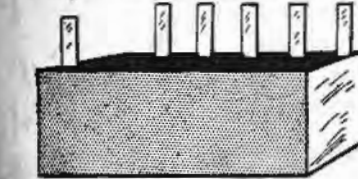

Handy "B" Batteries May Be Made From Flashlight Cells.

not needed. As indicated in the sketch, four or five lamps properly connected will suffice to charge the battery in first class condition. The lamps should be about 100 watts each and all connected as shown. The charging current will average between four and five amperes. By re-

# PERFECTION

119 W. 23<sup>rd</sup> ST. near 6th Ave. WATKINS 4767  
 59 CORTLAND ST. Elliotts Drug Store CORNER GREENWICH  
 128 CHAMBERS ST. near WEST BROADWAY

Visit Our New Store—78 CORTLANDT ST.  
 "The Stores That Sell on a Money-Back Guarantee"

## WHY IT PAYS TO PATRONIZE PERFECTION

Because first and foremost Perfection's success has been built upon satisfactory service to its patrons, making it possible to increase its business locations from one to four stores within one year.

Because Perfection stands back of every sale with its guarantee to cheerfully refund money on any purchase, and no questions asked.

Because Perfection carries only Standard Radio equipment, and a more complete stock than any Radio store in the U. S. at the lowest prices possible.

Because when you purchase a Radio Set from Perfection, you have the privilege of using its Service Department free of charge for one year.

Because Perfection serves its patrons by erecting aerials, making sets, installing sets, giving free hook-ups, and free advice.

"MAKE PERFECTION YOUR SELECTION"

# "INSULATE"

(Moulded Shellac Composition)  
 On the Market 20 Years



100 Styles of Knobs, Binding Posts, Dials, Headset Caps, Insulators, etc.

In Stock for Prompt Shipment

Insist on "INSULATE" from your regular dealer

Facilities Large—Deliveries Prompt

## GENERAL INSULATE CO.

999 Atlantic Ave. Brooklyn, N. Y.

Established 1904

# Something Really New!!

## A One-Control, One-Tube Set That Operates a Loud Speaker.

A new Radio Circuit has been perfected. It is a remarkable circuit, that cannot be imitated. The receiver is so constructed that the circuit is kept secret. The receiver is built so that if taken apart the circuit is entirely disarranged and incapable of being copied.

In tests recently made with this circuit, broadcasting stations over 1,000 miles were heard. It was possible to tune in Philadelphia while WOR was broadcasting. When used on local stations the signals are so powerful that headphones are uncomfortable, and a loud speaker on this set can be heard all over a large room. Tuning is accomplished with a single control.

The Wave Length Range of this set is such that it can easily tune to all the new longer wave lengths which broadcasting stations will soon be using.

The small dimensions of the set—2-inch x 6-inch x 8-inch—make it especially suitable for camping and other purposes requiring a light, compact receiver. It can be operated on any dry cell tubes.

By careful selection of parts and improved methods of manufacture by The Atlantic & Pacific Radio Company, the price of the receiver has been kept down to \$12.50.

## Set Is Now on Demonstration at The Atlantic & Pacific Radio Co.

131 West 37th Street New York City

Complete Line of Standard Radio Sets and Supplies  
 WHOLESALE & RETAIL

## GO WHERE THE CROWD GOES!

### COLUMBUS SHOP

874 Columbus Ave. at 103<sup>rd</sup> St.

B'way Subway to 103rd, 2 Blocks East  
 6th-9th Av. "L" to 104th, 1 Block South

SEVERAL RADIO ENGINEERS  
 ALWAYS IN ATTENDANCE

## We have on hand a complete stock of PARTS AND SETS

Manufactured by the following radio manufacturers

- |                   |                 |
|-------------------|-----------------|
| B. R. P. Products | Grebe           |
| Westinghouse      | Cutler Hammer   |
| Western Electric  | Dictograph      |
| De Forest         | Fischer         |
| Baldwin           | R. C. A.        |
| Federal           | Acme            |
| Panels            | Marko Batteries |

Atwater-Kent

SETS BUILT TO ORDER

Our Aerial Construction Department is under the supervision of George Mitchell, Associate Institute of Radio Engineers.

Estimates Cheerfully Furnished

Instead of buying large B-batteries go to any electrical store and purchase a number of small flashlight batteries. They are usually sold in a box containing five, but the supply is unlimited. Leave the batteries in the box or build a special box for them and connect them all in series with short pieces of wire, soldered by a little solder. There are two pieces of brass on each of the flashlight batteries. These are the terminals. The long one is the one connected to the zinc of the battery and is the negative pole. The other, shorter one, is the positive.

In connecting them up leave the first long one for the external connection, then connect the short piece of brass on the first cell to the long piece on the second cell. Keep this up until all the batteries are connected together. It will be found that a short lead will be left on the other end of the series. Always connect B-batteries in this way. If more batteries are needed for an amplifier simply buy several additional boxes of the batteries and proceed to connect them in the same way.


If the voltage must be varied take a small battery clip or spring clip and solder a piece of wire to it. It is then a simple matter to vary the number of cells in use by moving the clip from electrode to electrode. Remember, though, to place the clip always on the positive side. A B-battery of this type should last many months before it needs renewing. Even then the operator will be able to pick out the cells that have deteriorated and replace them with new cells, thereby saving the expense of purchasing a whole new B-battery.

### The "A" Battery, or Filament Lighting Battery.

The use of a vacuum tube in a radio receiver involves a battery to supply current for the filament. This is referred to as the A-battery. The A-battery in the case of the more common tubes is a six-volt battery, but the tube known as the WD11 or 12 operates on an ordinary dry cell. Another tube, known as the UV199, operates on two dry cells, while the remainder, or majority, operate on the six-volt storage battery. Should the owner of a radio receiver possess six-volt tubes but desires to use dry cells he may readily do so, but it is inadvisable to begin operation with such an ar-

range, as the life of dry cells is limited and it is a matter of a few days only when they will need to be replaced by a new set of dry cells. If dry cell tubes are used it is

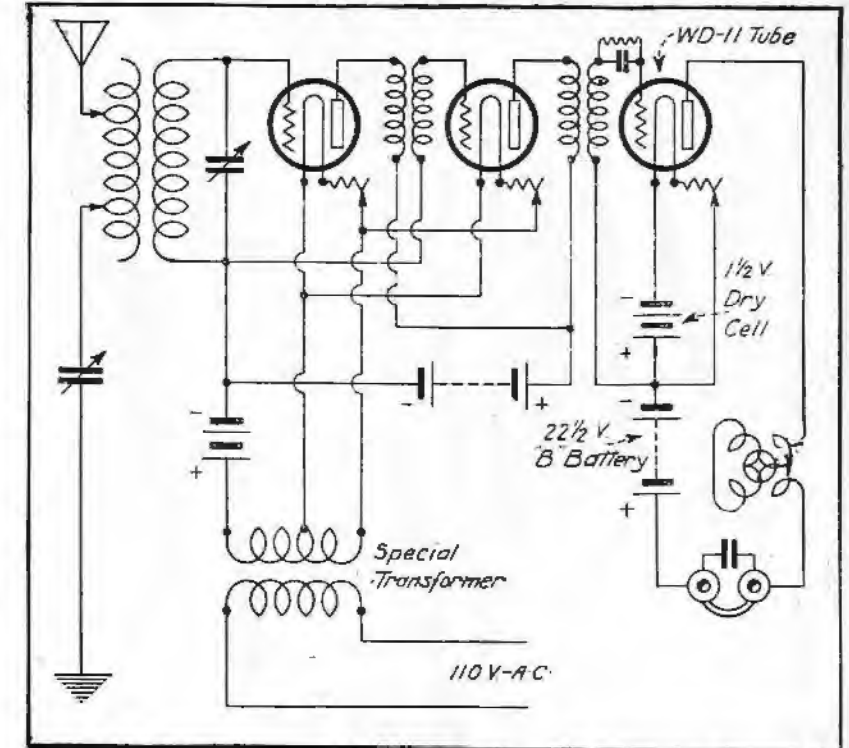consumed. Where a storage battery is employed to light several vacuum tubes the drain on the battery is considerable and a home charging outfit will be found to pay good divi-



Filaments of Amplifier Tubes May Be Lighted From A. C. Lines.

advisable to have them connected in parallel in order that their life may be lengthened. To do this connect all the carbon rods, or centre posts, of the dry cells together, and all the outside or zinc posts together. This then makes the outside polarity negative, while the carbon rods, or centre posts, form the positive connections. This mode of connection allows the voltage to remain at one and one-half volts, the correct value for the dry cell tube, but the amperage or life of the battery will be four times that of a single one.

Still, there is nothing that really takes the place of the storage battery for the six-volt tubes. This is especially true when more than one tube is being used, as, for instance, when one or two stages of amplification are added to the detector. The storage battery may be of any standard type, but a battery of large capacity is preferred. A battery in the vicinity of eleven ampere hours is a satisfactory size. Then if a loud speaker is added at a later date the battery will be large enough to handle the added demands.

A storage battery must be recharged after its charge has been

consumed. The storage battery then may be recharged whenever necessary at a minimum of expense and without losing valuable time.

### House Lighting Current for Filament Supply.

The question: "Why is it not possible to use the house lighting current on the filaments of vacuum tubes?" is frequently asked. The fact of the matter is we are dealing with delicate fluctuations in the tubes. If the filament voltage should vary even in the slightest degree the electronic flow would likewise vary and cause a corresponding noise in the head telephones. Therefore, for absolute quiet in the head telephones it becomes necessary to use a steady, non-varying direct current source, such as the storage battery. The lighting current could be easily cut down to six volts, regardless of whether it be direct or alternating current, but in either case there would be a distinct hum, which, in the head telephones, would drown out the signals. This prevents the use of the lighting current on the detector.

## How to Locate Troubles in Radio Receivers

Whatever the type of receiving set, the first step is to test out each piece of equipment individually. A small flashlight lamp and battery form a simple testing outfit.


If no sounds are heard in the 'phones, begin at the lightning arrester and test each part. With the lamp and battery across the arrester the lamp should not light. A light indicates a short circuit. Applying

the test to the tuning unit, the lamp should light when the terminals are connected across the primary, and also across the secondary. It is a good idea to test out the separate taps on the primary to see that none of the small pigtails have become broken inside the flexible tubing.

When connected across the condenser, the lamp should not light. If it does, this indicates a defective

condenser, whether it be variable or fixed.

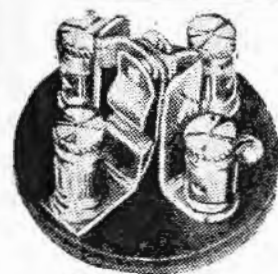The only satisfactory way to test a tube is to take it to some other receiving set known to be in working order and substitute it for one of the tubes in use. A tube with a filament that lights up when connected to a battery is not necessarily a good tube. There is always the possibility of grounds between the elements.



**SAVE  
TIME—MONEY—WORRY**  
**DEMAND AND USE  
IMPROVED  
ANTI-CAPACITY RADIO  
JACKS AND SWITCHES**

Designed especially for Radio. Eliminate soldering. Binding post connections. Use improved products. Oh, what a difference!

Ask Your Favorite Dealer!

Double Circuit Closed



## IMPROVE THE APPEARANCE OF YOUR RADIO SET 100%

by using "BRUNO ENGRAVINGS," illustrated below



**MAKES THE PANEL APPEAR  
ENGRAVED.**

A "Decalomania"

**EASY TO APPLY—NEAT IN APPEARANCE  
—PERMANENT—ECONOMICAL**

In Packages with full instructions and Special Cement.  
Ready to Use.

- |   |         |
|---|---------|
| SET NO. 1—For Tuner Detector<br>3-Stage of Audio and Radio frequency, with<br>many extra pieces ..... | 50 cts. |
| SET NO. 2—For Tuner Detector<br>2-Stage amplification .....   | 35 cts. |
| SET NO. 3—For Tuner Detector .....  | 20 cts. |

Order from Your Dealer or Write to

**BRUNO RADIO CORPORATION**

286-300 WATER STREET,

NEW YORK CITY

68 WEST 23<sup>RD</sup> ST  
111<sup>TH</sup> EAST  
OF 6<sup>TH</sup> AVE

**MARKS** GRAMERCY 4868  
MAIL ORDERS SOLICITED

The Better Kind of Standard Sets and Parts.

## Our Policy is Truthful Advice

Coupled with Real, Honest-to-Goodness Service by an Expert.


DeForest Radio Phones Brandes & Baldwin Headsets. Workrite Manufacturing Co.	Radio Improvement. (Anti-Capacity Jacks & Switches.) Radio Corp. (U. V. 200-201A-W. D. 11-W. D. 12 and U. V. 199.)
--	--

Complete Stock of All the Above Material  
Always on Hand.

Discounts to Dealers and Makers of Sets.  
Member Radio Dealers' Ass'n.

## EXCELSIOR 108° COUPLER

NEW LIST  
\$3.00

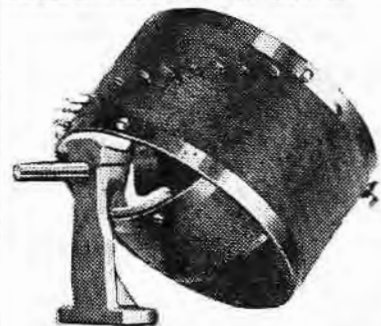

Takes all new wave lengths effectively. Genuine Bakelite Dielecto, Rotor and Stator wound with silk covered wire. Recommended by Haynes-Griffin Co. as being the best coupler for all circuits.

## New Departure Jacks

Made in three types, as follows: Double Closed, Single Closed and Single Open. Positive contact, anti-capacity, small space. No screws or soldering necessary in making wire connections.


### LIST PRICES

Single Open, 65c each  
Single Closed, 75c each  
Double Closed, 95c each

Dealers Write for  
Discounts

**J. W. CHRISTIE,** FACTORY REPRESENTATIVE

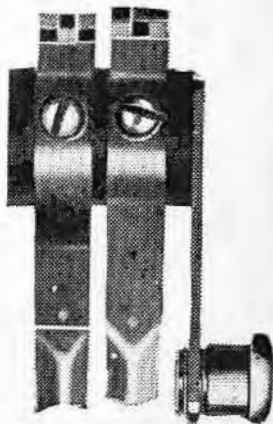6 CHURCH STREET  
Phone Rector 1397 NEW YORK



# Regeneration and Its Effects

## A Brief Talk on the Methods of Obtaining and Controlling This Very Desirable Condition, Together With Working Diagrams.

Three million good and honest American citizens or citizens-soon-to-be are using receiving sets in which regeneration plays an important part. These radio enthusiasts, most of them, know when the set is regenerating. They know how to produce it, but why the effect is made manifest by such insignificant accessories as a simple variometer or even a single slide tuning coil is beyond their ken. As a matter of fact, they don't have to know. It is because of this last statement that this treatise, like many others intended for consumption by the average man, will not attempt to enter into the technicalities of regeneration. Rather, the phenomenon will be described briefly in terms that it is hoped will give a general idea of its cause and effect.

Many receiving sets are now sold which are non-regenerative. But friends of the buyers soon inform them that the sets can be improved by making them regenerative. All that is necessary to bring this about is the insertion of a variometer in a certain position in the plate circuit of the detector tube.

Even after Dr. Lee De Forest developed the three-element tube it was used as a straight rectifier of incoming waves for many years. Peculiar effects were undoubtedly observed originating in the tube under certain circumstances, but no one seems to have studied them until Edwin H. Armstrong, a student at Columbia, while carrying out experiments on tubes and tube circuits, happened to notice that the plate circuit of a tube which he was using as a detector contained something other than rectified currents in the plate circuit. He experimented further and discovered that this plate circuit was carrying high frequency currents in addition to the low frequency rectified currents. If this were so, he figured, then by tuning this circuit and allowing the energy to feed back into the secondary circuit of the receiver the incoming signal would be greatly re-

inforced. He placed a variable tuning coil in the plate circuit, tuned it to resonance and the signals fairly boomed out with their added volume. He had made one of the most astounding discoveries of the age and one that in later years was to affect the entire complexion of the radio industry, broadcasting as well as reception.

### Small Current in Grid Controls Large Plate Current.

As was stated in the chapter devoted to the fundamental action of the vacuum tube, the presence of a very small amount of energy in the grid of the vacuum tube will control a much larger amount of energy in the plate circuit. If the action of the two circuits is considered as being entirely independent of one another the analogy is much the same as that of the motorman of a trolley car, who by the application of a small amount of force on the air brake handle liberates a large amount of force at the air brake and thereby controls the movement of a car weighing many tons.

In the vacuum tube, which is arranged for possible regeneration, this energy in the plate circuit can be tuned to be in phase or in step with the incoming wave, and thus increase the initial force on the grid. Of course the complete action is instantaneous, but an idea of the manner of working may be clarified if the following word picture is understood.

For purposes of the example assume that a force of 1 pound is impressed on the grid. Through the amplifying action of the tube this original force is increased to 4 pounds. This quadrupled force is then arranged to be in step with the first force and is fed back to the grid, where the two forces combine to form a force of 5 pounds. This force of 5 pounds, acting through the tube, is increased to 20 pounds in the plate circuit and so on.

If this seems like perpetual motion

the radio fan should not become too enthused since the design factors of the tube themselves soon form a limit beyond which this amplification cannot go. After a certain point in regeneration is reached the tube is set off into oscillations, which means that it is no longer acting as a pure receiver but is also functioning as a transmitter. When this point is reached the signals will lose their real tone and will become mushy and distorted. With code signals this does no harm, but radiophone sounds are made unintelligible.

### Regeneration Can Be Secured in Several Ways.

There are several methods of obtaining regeneration. One method has already been mentioned, that of tuning the plate circuit of the tube with a tuning coil or variometer. Another method makes use of a wire-wound tube called a "tickler," which is placed near the rotating element of the primary tuner or variocoupler. Still another form of feed back is that made possible by a condenser inserted between the grid and plate of the detector tube. This last named method is not usually satisfactory with the apparatus in the hands of amateurs.

Of all these methods it is probable that the "tickler" form of regeneration is the most satisfactory, although it is not incorporated in receivers so frequently as the tuned plate method, using a variometer to control the regeneration. With the "tickler" it is easier, as a rule, to carry the regeneration to a higher point before the tube breaks into oscillations.

One very satisfactory form of "tickler" is that made by winding forty to fifty turns of wire on a rotor ball similar to that comprising the secondary tuning inductance and placing this "tickler" ball at the opposite end of the wire-wound tube which comprises the primary tuner. Thus the complete tuning accessories are included in one unit with

# 3,000 MILES

—And as Clear as a Bell



All Hissing, Howling and disagreeable noises eliminated by the

## ARTHUR PUDLIN VARIABLE HIGH RESISTANCE LEAK

on a Rosenblum Circuit or any other circuit. The only Resistance that meets all requirements. Endorsed highly by Flewelling, Rosenblum and other noted Radio Engineers.

Price with .00025 Mica Condenser, \$1.00.  
Price without condenser, 75c.

We Also Manufacture **THE ARTMICA CONDENSER** in all capacities 25c

Our Products handled by all up-to-date dealers. If your neighborhood dealer does not carry them, send purchase price, also Dealer's name to

**Arthur Pudlin Engineering Co.**

1540 Broadway New York, N. Y.

# COMPLETE SETS and PARTS

of all the latest circuits are on hand in our store, which is open every evening until 10 o'clock.

We invite you to drop in with any of your difficulties. A constant corps of technical experts is available at all times to give you assistance and help in the construction of your set.

New hook-ups and working models of various circuits are on display for your use.



## 20TH CENTURY RADIO CORPORATION

102 Flatbush Ave.  
Brooklyn, N. Y.  
Phone: Sterling 3324

the primary as the permanent coil, one rotor in one end of the primary as the secondary coil and another rotor in the opposite end of the primary as the "tickler."

In arranging these coils for regenerative circuits it sometimes happens that while the receiver will work the regenerative effect is lacking. This usually may be remedied by switching the connections leading to the two ends of the "tickler" coil.

### Variocoupler-Variometer Outfit Is for Short Waves.

The variocoupler two-rotor receiver or the variocoupler-variometer set is suitable only for short waves from 150 to 550 meters. As now covered by regulations, these limits are sufficient to accommodate all broadcasting stations. But for experimenters who feel the urge to listen to the code signals of the powerful transatlantic stations here and in Europe some other form of receiver must be built. With few exceptions this is the honeycomb set.

All parts of a regenerative set utilizing honeycomb or duo-lateral

coils instead of couplers for tuning purposes are similar to those using couplers and variometers except for the substitution of these coils themselves and the means for tuning them.

Honeycomb or duolateral coils are coils containing many turns of fine wire wound criss-cross in such a way that the separate turns of wire touch only at certain times and places. In short, this scheme of winding reduces to a minimum what is known as "distributed capacity," a factor that reduces the efficiency and tuning range of tuning coils.

In following out this scheme of winding the inventors were able to compress the enormous inductances needed for long waves into a relatively small space. Thus the old coils for receiving 15,000-meter stations consisted of several thousands of turns of wire wound on a 6- to 8-inch insulating tube, 6 or more feet long. The honeycomb or duolateral coil for this wave length is only 1½ inches thick and 6 inches in diameter.

These coils are seldom tapped, hence it becomes necessary to connect a variable condenser across

them to tune the circuit to the desired wave length. The following table suggests the sizes to use for various wave lengths, the size in each instance having been figured for use with a 43-plate variable condenser (capacity .0011) across them. The "tickler" is more frequently employed without this condenser.

### TABLE OF HONEYCOMB COIL SIZES FOR ALL WAVE LENGTHS.

Wave Lth.	Primary	Second.	Tickler.
150-350	DL50	DL25	DL50
300-700	DL100	DL50	DL100
450-1,050	DL150	DL100	DL150
850-2,000	DL250	DL150	DL250
1,750-4,000	DL500	DL250	DL500
4,000-8,500	DL1,000	DL500	DL1,000
6,000-12,000	DL1,500	DL1,000	DL1,500
12,000-20,000	DL1,000	DL1,500	DL1,000
15,000-25,000	DL1,500	DL1,500	DL1,500

When a receiver is built with honeycomb tuning coils the same set may be utilized for the reception of broadcasts or of 20,000-meter code signals. All the owner need do is remove the smaller coils from the mounting and replace with the larger coils for the longer wave lengths.



## The VOICE of YOUR RADIO

Is it clear and distinct or muffled and subdued? The difference in many cases is in the head phones. Diamond De Luxe Phones are the Nation's Choice. Made with watch-maker's precision and rigidly tested. Polished black ear pieces are shaped to fit the head comfortably. A large disc gives greater volume and splendid tone. Permanently magnetized. 3000 ohms. Every set carries the broad guarantee of the manufacturer. At present low price they are a great bargain.

RETAIL PRICE **\$3.60**

SPECIAL ATTENTION TO RETAILERS AND JOBBERS

Made by the manufacturers of the famous Diamond B. Batteries.

**Diamond Electric Specialties Corp.**

101 So. Orange Ave. Newark, N. J.

## CICO TWO WAY PLUG TYPE A

A Radio Plug embodying the most advanced Engineering principles. Has provision for taking two sets of head phones simultaneously or one set individually. Fits all standard Jacks. Takes all types of tips, forked, straight and plain wire. Perfect contact, no tools of any nature required to connect. Built of finest material obtainable.



View Showing Internal Construction



View Showing Plug Assembled


PRICE **60c.**

COMPLETELY GUARANTEED

MANUFACTURED BY

**Consolidated Instrument Company of America, Inc.**

41 EAST 42nd STREET, NEW YORK, N. Y.

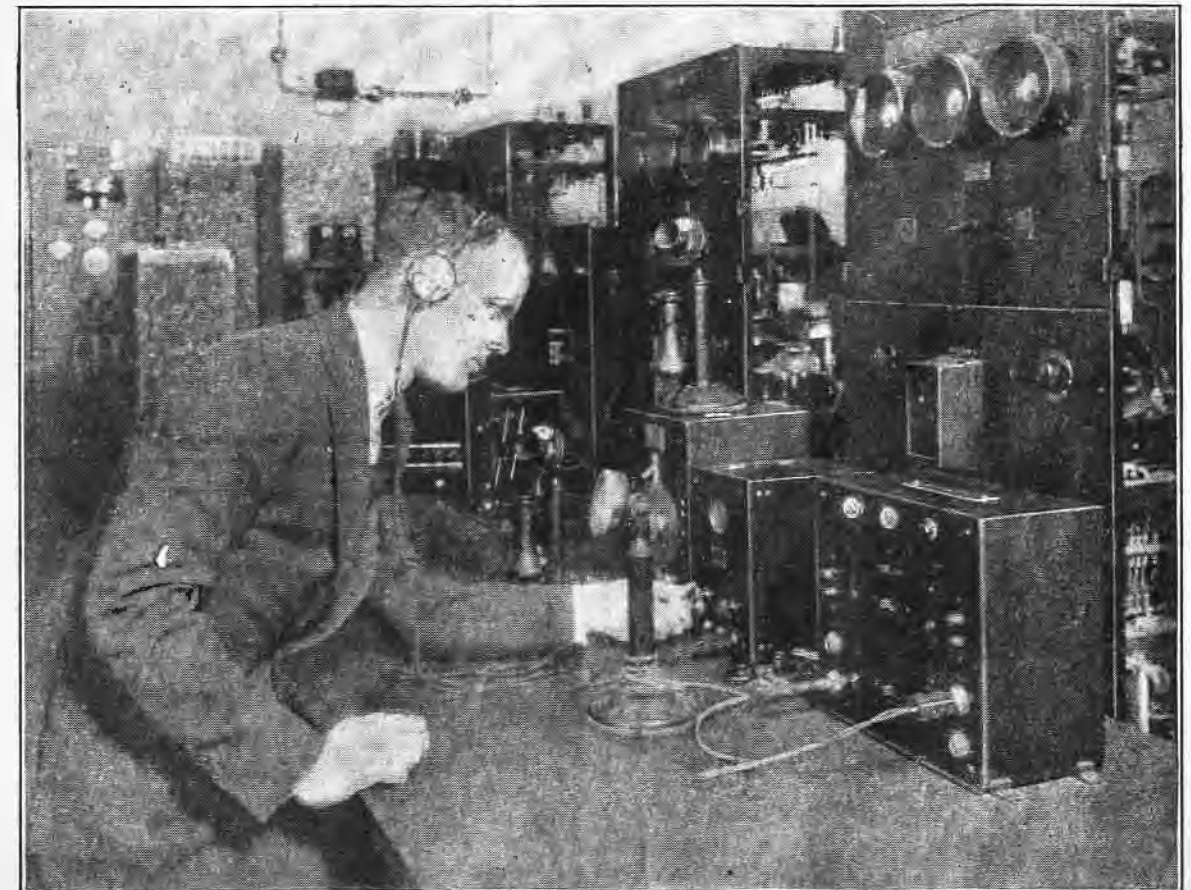

All the Intricate Operations of a Broadcasting Station Are Controlled From This Table.

# 'Phones and Loud Speakers

## Head Sets Are Essential for Crystal Sets and for Weak or Distant Stations, but the Ideal Receiver for the Home Requires a Loud Speaker.

The radio head 'phone has never had the credit it deserves. Without it there is no telling what intricate and supersensitive apparatus would be necessary to take its place and carry out its function of translating the fast-moving impulses of electricity into audible sounds.

The amount of energy picked up by an antenna is so small as to be measurable by only the most sensitive of special indicating instruments. Yet the headphone, in the case of the crystal receiver, is set into motion by these trains of almost insignificant energy.


A 'phoue consists of several thousands of turns of very fine wire—No. 40 to 44 silk covered or enameled—wound carefully on two little spools, through the centre of which run cores of soft iron. Around the outside of the case holding these spools are several circular pieces of somewhat harder iron which have been permanently magnetized.

The spools are placed in the centre of the case in such a position that the tops of the iron cores are slightly below the level of the outside of the case. Then across the top of the case a thin diaphragm of iron is laid.

The permanent magnets hold the diaphragm in a slightly dished position. The electro magnets formed by the wire-wound spools have no effect on the diaphragm until a signal impulse passes through the

set. When a high-frequency wave strikes the grid of a vacuum tube the current in the plate circuit, where the 'phones are located, is also made variable, although the changes are


regular in shape, but are a mixture of many odd-shaped waves. As these peculiarly modulated waves strike the grid of the tube they create a disturbance in the 'phone circuit that is practically similar to the words spoken at the transmitter. As these currents pass through the fine winding on the spools a temporary magnetic field is formed. This new magnetism may help or "buck" the magnetism of the permanent circular magnets. When they help, the diaphragm is drawn down with considerable force; when they "buck" the total effect is less than that of the permanent magnet alone and the diaphragm tends to return to its normal position.

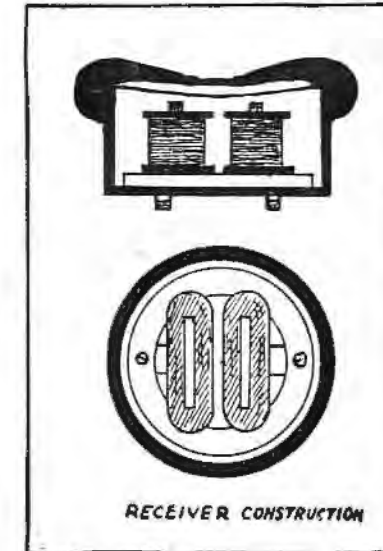

'Phones Should Not Be Bought by Ohms.

In advertisements and store windows 'phones are usually specified according to the number of ohms, such as "2,200 ohms" or "3,000 ohms." The 'phones with higher ohmage are more apt to carry a higher price tag, leading the unknowing purchaser to believe that the 'phones are better in proportion to the amount of resistance.

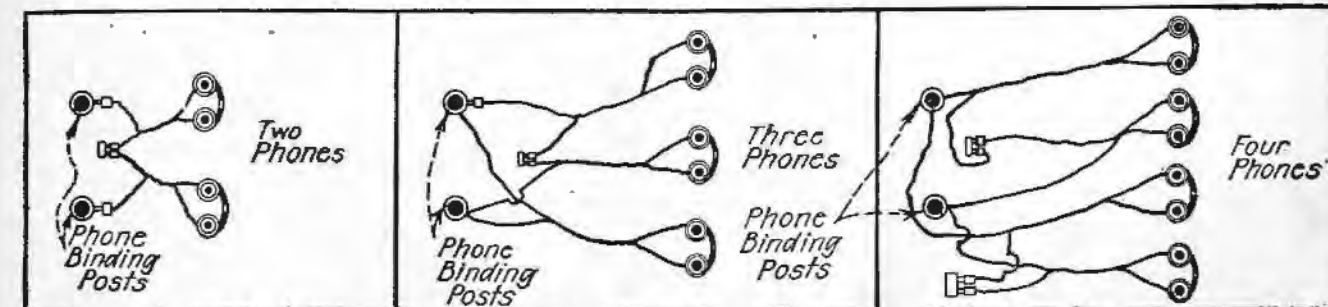To explain this fact a bit further, the term ohms is merely a measure of resistance. Thus an electric bulb of the type used to light the home may have a resistance of 200 ohms. But no one buys a lamp according



Proper Connections to Follow When Two or More 'Phones Are Connected to One Set.

## DODGE TONE AMPLIFIERS

### THE PERFECT TONE RADIO LOUD SPEAKERS FOR HOME USE



Model No. 10  
WITH SPECIAL SPEAKING UNIT IN MAHOAGANY CABINET

Size: 12" high, 9 1/4" wide, 8 1/4" deep; complete, ready for immediate use, \$25.00.



Model No. 3  
Size: 9 1/2" high, 6 1/2" wide, 6 1/2" deep; on stand with Baldwin cap (no 'phone), \$8.00; on stand with special speaking unit, \$12.00; horn, without stand, with Baldwin cap, \$6.00; horn without stand, with special speaking unit, \$10.00.



Model No. 6  
WITH BALDWIN SPEAKING UNIT, IN MAHOAGANY CABINET

Size: 13 1/2" high, 12 1/4" wide, 6" deep; complete, ready for immediate use, \$30.00.



Model No. 5  
Size: 13" high, 10" wide, 6 1/2" deep; on stand with Baldwin cap (no 'phone), \$10.00; on stand with special speaking unit, \$14.00; horn, without stand, with wall hook and Baldwin cap, \$8.75; with hook and special speaking unit, \$12.75.

In the Dodge Tone Amplifiers, the radio fan is offered the latest development in loud speakers—made to produce that refinement of tone that is now being exacted of loud speakers for home use—rather than noise.

The Dodge Tone Amplifiers are scientifically perfect instruments, made of wood pulp composition (formula patented), designed by one of the foremost acoustical specialists. This, together with their shape and interior dimensions, insures the most delicate reproduction of voice or music and positively eliminates distortion and metallic sound.

Models No. 10 and No. 6 are complete, ready for immediate use with any set of three tubes or more—no batteries necessary—no adjustments—merely hook-up and listen.

In Models No. 3 and No. 5 the radio fan is offered Dodge Tone Amplifier horns or sound chambers, mounted or unmounted, for use where the more elaborate speaker is not required—or where they might be desired for installation in sets or cabinets.

Order a Dodge Tone Amplifier and enjoy the news and fine concerts being broadcasted.

## ACKERMAN BROTHERS CO., INC.

Dept. "GM" 301 W. 4th Street, New York, N. Y.

# S-S-S

355 Bowery 65 W. 18 St.

RADIO'S MODEL STORES

110 West 23 Street

**The Little Counter** TWO years ago the SSS Organization began at a little counter. It was narrow and uncomfortable. It was always crowded. We gave advice with the right side of our tongue, chewed lunch with the left, welcomed fans with one hand and sold with the other. And the fans continued to come. There was a reason. We had something besides the counter. We had an idea.

**The Idea that Won** WE were in Radio to stay. We had not come to make easy money and quit. The SSS Organization was a vision we had from the start. First, Real Advice. We were determined to sell a fan what he needed, to enter into his plans and to give his requirements thought. Secondly, Standard Merchandise. We were determined to sell him merchandise that would stand the test because we intended to keep his trade. Thirdly, Low Prices. We were determined to sell as low and lower than the get-rich-quick-and-get-out dealer. All this meant hard work. But the idea won.

**The Big Result** STEADILY we worked, and the fans recognized our sincerity. New faces showed up at the little counter, and the old faces came back again and again. We increased our organization and broadened our original idea. The big result is at your service today. Three convenient stores, backed up by SSS principles, and our fourth store about to open. We are proud of our achievement and thank our old patrons while we invite the new ones to buy at

RADIO'S MODEL STORES The SSS RADIO STORES

Member of Radio Dealers' Association

We have a special buying plan for men in uniform, clubs and schools.

Mail Order Department at 110 West 23d Street Store

Money orders must accompany orders.

WHOLESALE & RETAIL

## FAMOUS "A" CYCLONE "B" WORLD'S BEST BATTERY

SPECIALLY BUILT FOR YOUR RADIO SET. HIGHEST QUALITY GUARANTEED.



For DISTANCE, CLEARNESS and LONG LIFE INSIST ON CYCLONE YOUR DEALER HAS IT.

STANDARD ELECTRIC NOVELTY COMPANY

## CRYSTAL FANS WAKE UP!

"The Vacuum Tube's Only Rival." Lasts Indefinitely.  
50c SUPER CRYSTAL 50c  
Approved by Mail, Tribune, Radio World.  
Make your set sound like a brass band.

RADIO CORPORATION OF AMERICA OPERATIVES use the L. D. R. Crystal as detector in conjunction with one or more stages of amplification. Satisfaction Guaranteed or money refunded.  
FREE. The Jaynxon Muttiple Catwhisker. Fits all detectors. Applied in a jiffy. Will make your set loud and clear.  
FREE. Information and hook-up how to receive 475 miles on a crystal.  
FREE. How to amplify your crystal set.  
FREE. The Jaynxon One-Tube Reflex. Local on loud speaker, D. X. on phones.  
FREE. SEND FOR THESE RIGHT NOW.  
DEALERS WAKE UP. SOME MEOW!  
JAYNXON LABORATORY, 57 Dey St., N. Y. City

to the ohmage. In the same way it is unwise to purchase radio 'phones by their resistance. The ohmage may, however, be considered in the case of reputable 'phones, since the increased number of ohms indicates the greater number of "ampere-turns" in the receivers. And ampere-turns are the determining factors which make one receiver better than another.

One ampere of current flowing once around a magnet is one ampere-turn. It makes no difference what kind of material the conducting wire is made of. But when a 'phone is specified as having 3,000 ohms, the magnet coils within the case may be wound with a comparatively few turns of some odd kind of wire having a high resistance. Thus there would be few turns in the receiver, although the label would be quite right in stating the resistance value.

It is understood that the beginner in radio cannot, nor does he want to, bother with these technical terms. For him it is best to buy only those 'phones that are made by reliable firms. The cost will be higher, but the intrinsic value will accompany the cost. If the cost is beyond his financial means, then he should insist on a trial of the 'phones, with an option of returning them if unsatisfactory.

The crystal set operates best with high-grade 'phones of about 2,300 ohms resistance, but the modern tube set frequently gives best results with 'phones of higher resistance, the value sometimes running as high as 6,000 ohms. For general purposes, however, the reliable makes of 3,000 ohm 'phones are the most suitable for the average receiving set.

#### The Ideal Receiver Requires a Loud Speaker.

The extension of radiophone entertainment has brought into prominence other types of head 'phones, one in particular having a diaphragm operated by levers terminating in a small iron bar floating in a magnetic field. As this field is varied the bar is moved back and forth. This movement is then magnified through the leverage and the final force exerted on the diaphragm. These receivers

produce a greater volume of sound and are known colloquially as "loud talking receivers." These 'phones form the basis of phonograph adapters and are excellent for the purpose. For head sets, however, some of the makes are so heavy as to be uncomfortable, although their increase in volume over other types sometimes compensates for this disadvantage.

#### Loud Speakers Available in Several Styles.

A receiving set is not complete until it contains a loud speaker. Head 'phones are essential until the detected sounds have been built up through amplification to a point where they are powerful enough to operate the mechanism of a loud speaker. This usually requires at least two stages of amplification. For experimental purposes a head set is superior to any other type of sound translator, but the family receiving set will fail in its ultimate usefulness unless the sounds as delivered from the set are thrown out into the room for all who may be there to hear.

There are several widely differing types of loud speakers. Some of them are nothing more than horns made of tin, white metal, plaster of Paris, wood pulp, or wood strips, to the base of which a loud-speaking receiver is attached. Others are equipped with two horns at the base to which the complete head set may be attached, one 'phone on each horn.

Strictly speaking these devices are not loud speakers, but are merely resonators. They take the sound waves as they issue from the telephone and by resonance increase the volume. The action is like that of a megaphone through which an announcer speaks.

All too often these horns are designed incorrectly or built of wrong materials. They pick up one or more of the sounds from the 'phone and amplify it out of proportion to all other sounds. Conversely, certain sounds will not be amplified at all. This selective resonance produces foreign or "tinny" sounds which have the effect of distorting the speech.

The most satisfactory type of loud speaker is either the one which embodies a special diaphragm built into

the throat of the horn or, better still, that type which utilizes a specially designed diaphragm of the amplifying type.

In the first class will be found many exceptionally fine reproducers of the broadcast programmes. These loud speakers require no extra equipment, but are inserted in the output of the receiver just as a pair of 'phones would be placed.

The second class of loud speakers is connected to the output of the receiver, but in addition two leads are taken from the storage battery, for the purpose of supplying the current for the supplementary magnetic field in which the bar of iron floats.

Few suggestions can be given to aid the novice in selecting the loud speaker. There is but one criterion. It is not the price, but the sound. Before buying any loud speaker, the prospective purchaser should be permitted to listen to several types, one after the other, as it is switched into the same receiving set. Even though the set is improperly adjusted, this method provides a comparison which quickly separates the speaker of highest quality from the others.

Loud volume does not always accompany tone. The loud speakers with the sweetest and purest tones are not, as a rule, those which "fill a room with noise." The loud speaker for the home should be selected on the merits of its tone, first, last, and always.

#### Engineers Are Developing Better Loud Speakers.

No radio or acoustical engineer is so rash as to believe that the ideal loud speaker has been even approached by those now available. The last year has seen some distinct improvement in this line of radio equipment, but there is still much to be desired. It is not a simple problem to amplify the wide range of sounds encountered in radio transmission. These sounds range from the low notes of the bass singer and of the church organ to the high shrill notes of the violin and wind instruments. The perfect loud speaker must amplify these tones, each in its proportion to the others, otherwise strange notes are sure to be introduced.

# Radio Frequency Amplification

## Higher Amplification, Greater Distance and Finer Selectivity Are Possible With the Proper Application of This Feature.

"Use audio frequency amplification for volume and radio frequency amplification for distance and selectivity." This is the admonition of radio engineers. Thousands have followed the advice without knowing why. An equal number have attempted to apply radio frequency units to receiving sets already in existence with utter failure, due to the fact that their understanding of the devices was meagre.

When a broadcasting station transmits sounds in the form of waves these waves travel at a high rate of speed, depending on the wave length. Thus a wave with a length of 400 meters occurs with a frequency of 750,000 times a second. A wave of 800 meters occurs at just half this rate. The reason for the use of this high frequency is a technical one and refers to the efficiency of the aerial as a radiator of waves. Its exposition has no place here.

But referring to the section on crystal detectors, it will be recollected that the function of the crystal detector was to change this high frequency of the transmitted wave to the very low frequency at which the

human ear will function. The vacuum tube operates as a detector for the same reason.

The frequency at which waves are transmitted is called radio frequency. That at which the waves are heard is called audio frequency.

In receiving sets that do not employ radio frequency amplification it is the intention of the designer to change the radio frequency waves into similar waves of audio frequency as quickly as possible. Waves of high frequency are much more difficult to control and keep in their proper path than waves of lower frequency. So as soon as the antenna picks up these waves and leads them down to the tuning unit they are tuned by means of coils and condensers, and are then immediately passed into the "slowing down" or detector tube. In this tube—in the case of a 400-meter wave—the waves which were travelling at the rate of 750,000 a second are toned down to a mere 800 to 2,000 a second, for these latter limits are those to which the human ear is sensitive.


But if the slowed-down waves can be amplified, why shouldn't the high-

frequency waves be treated likewise? This question occurred to engineers who, after considerable experimenting, found that not only could it be done, but that results obtained were well worth the doing.
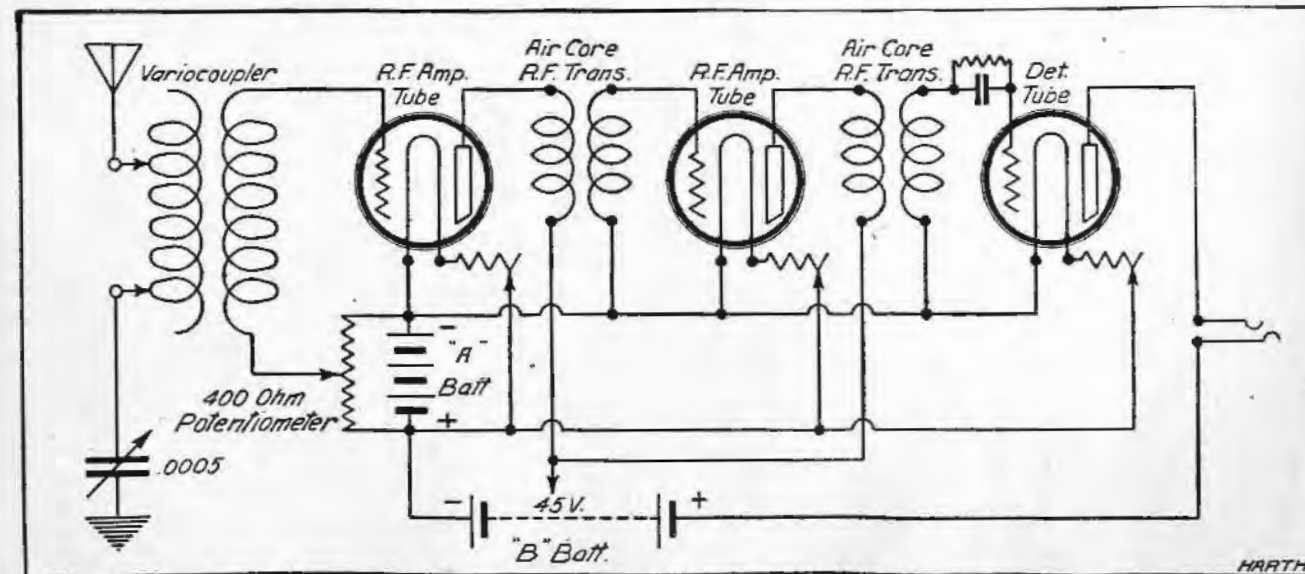
#### How High Frequency Waves Are Amplified.

Radio frequency amplification means that the infinitesimally weak waves coming in from the antenna are passed through one or more vacuum tube units and given an added push or energy before they are sent through the detector tube. To do this requires the use of tubes and other devices placed between the tubes, just as transformers are placed between tubes in stages of audio frequency amplification.

In one form of radio frequency amplification utilizing two stages the incoming waves are first tuned with the usual tuning device. They are then passed into a vacuum tube. From the vacuum tube they pass through a specially constructed radio frequency transformer, out of the transformer into a second tube, through the plate of the second tube



How to Connect a Radio Frequency Receiver Using Inter-stage Transformers.



to a second transformer, and from the transformer into the detector tube.

These radio frequency transformers differ considerably from the audio frequency transformers. In the first place, as a usual thing, they are not built over a core of soft iron, although some types do use a metallic core. Furthermore, the windings of the input—called the primary—and the output—called the secondary—usually consist of the same number of turns, whereas in audio frequency transformers the secondary turns are frequently ten times those in the primary.

#### Several Types of Radio Frequency Amplification.

Radio frequency amplification is obtainable in several widely differing forms. There is the transformer type, sketched in hasty outline above; there is also the resistance coupled type described in one of the diagrams shown in this article, and, thirdly, there is the choke coil type of coupling. For the short waves and corresponding high frequencies with which the radio en-

thusiast works the transformer type of coupling is by far the more suitable.

The resistance-coupled R. F. amplifiers have the advantage of being equally effective over a wide range of wave lengths, but at any given wave length their effectiveness does not equal a well-designed transformer coupling.

The reactance or choke coil type of coupling is of interest to the experimenter who enjoys the careful manipulation and manifold adjustments required to fit the reactance to the particular stage of amplification and to the wave length being received.

The highest degree of amplification is obtainable with transformers of careful, conservative design. Unfortunately the amount of amplification and the

stability of the amplifying tubes do not go hand in hand. One must be sacrificed to feature the other. Hence, the best radio frequency transformer is one which effects a healthy compromise between amplification, minimum distortion, and stability.

It should be mentioned here, however, that due to the characteristics of transformer coupled amplifiers the same transformer cannot be used for all wave lengths. There is usually

**"Just the Set for This Summer"**

**DE FOREST'S  
D-10  
PORTABLE REFLEX**

and a complete line of  
**De Forest Sets, Parts, Tubes  
and Accessories.**

OUR FEATURE IS UNUSUAL SERVICE  
Authorized Metropolitan Distributors



Manufacturers  
Distributors

112 East 23rd St.  
New York

**Triangle  
Radio Supply Co.**  
INCORPORATED

THE PYRAMID OF SERVICE

## Government Radio Publications

The following list of books is reprinted from various official lists because the information contained in them will be found to be valuable in supplementing the data in the RADIO MANUAL. The publications may be secured by mailing the indicated amount to the Superintendent of Documents, Government Printing Office, Washington, D. C. Remittances should be sent in the form of money orders.

Elementary Electricity, Signal Office Training Pamphlet No. 1	15c
Elementary Principles of Radio Telephony (Radio Communication Pamphlet No. 1)	10c
Principles Underlying Radio Communication (600 pages)	\$1.00
Radio Instruments and Measurements (Technical)	60c
Construction and operation of a simple home made radio receiving outfit (Standards Circular No. 120)	5c

Construction and operation of a variocoupler receiving set with crystal detector (Standards Circular No. 121)	5c
Description and operation of electron tube detector unit for simple radio receiving outfits (Standards Circular No. 133)	10c
List of Commercial and Government Radio Stations	15c
List of Amateur Radio Stations of U. S.	25c
Sources of Elementary Radio Information (Standards Circular No. 122)	5c

In addition to the foregoing publications the Department of Commerce publishes a monthly pamphlet called the Radio Service Bulletin. This Bulletin contains the names and call letters of all new broadcasting stations, all government regulations affecting commercial and amateur stations and general information relating to the entire radio industry. The Radio Service Bulletin will be mailed to any address for 25 cents a year.

one point at which the amplification will be best. Just how wide a band of wave lengths one transformer will accommodate will depend on the design. A transformer with an iron core will cover a wider band than another with an air core. But exceeding care must be used in selecting the iron and arranging the windings with respect to the core, otherwise the amplification will be uneven as the wave changes from a given value.

#### Radio Frequency Useless With Regeneration.

Most receiving sets in use to-day employ the regenerative feature. To add radio frequency amplification to these sets requires that the regenerative feature be eliminated, else the intermeshing of frequencies will result in feed backs and heat notes, causing those squeals and hisses for which some outfits are noted. Regeneration in itself is a function of radio frequency currents, hence to combine the two phenomena is only wishing for trouble.

But regeneration, if properly controlled, means the life of the detector unit. To drop it means that one tube will do only one-third the work possible with regeneration. Hence, if

the receiver is to be rearranged to include radio frequency units, it is useless to think of utilizing fewer than two stages of radio frequency.

If regeneration is omitted, the loss is not quite fully made up with one stage of radio frequency. With two stages of radio frequency the loss is compensated for, and in addition the amplification is increased. But the employment of radio frequency stages has the advantage of providing a filter circuit through which extraneous noises and other wave lengths can penetrate only with difficulty. This tends to provide sharper tuning and greater selectivity.

#### Radio Frequency Efficient in DX Work.


In one department of radiophone broadcasting radio frequency amplification is in a class by itself. This is the reception of distant stations. Without radio frequency amplification the detector will detect only those impulses that are sufficiently virile to actuate the circuits of which the tube is the nucleus. Thus many signals that are too weak pass through the detector tube without causing any effect in the 'phone receivers.

When radio frequency units are

present, these puny waves are built up through the two or more stages to a point where they exert a sufficiently powerful force on the grid circuit to cause a sizable change in the plate circuit and in the 'phones. Thus with R. F. the signals from distant stations can be brought in loud and clear enough to be recognized.

In arranging radio frequency units the various leads should be shortened to a minimum and should not be allowed to run together for any distance. The greatest enemy of successful R. F. amplification is the presence of capacity, and wires running parallel are fruitful sources of this deterrent. For the same reason switches should not be used except when essential. It is not a good idea to install switches to cut in or out the radio frequency units, for the reason that the mechanism of the change-over switch and the wires leading to it are prolific sources of capacity.

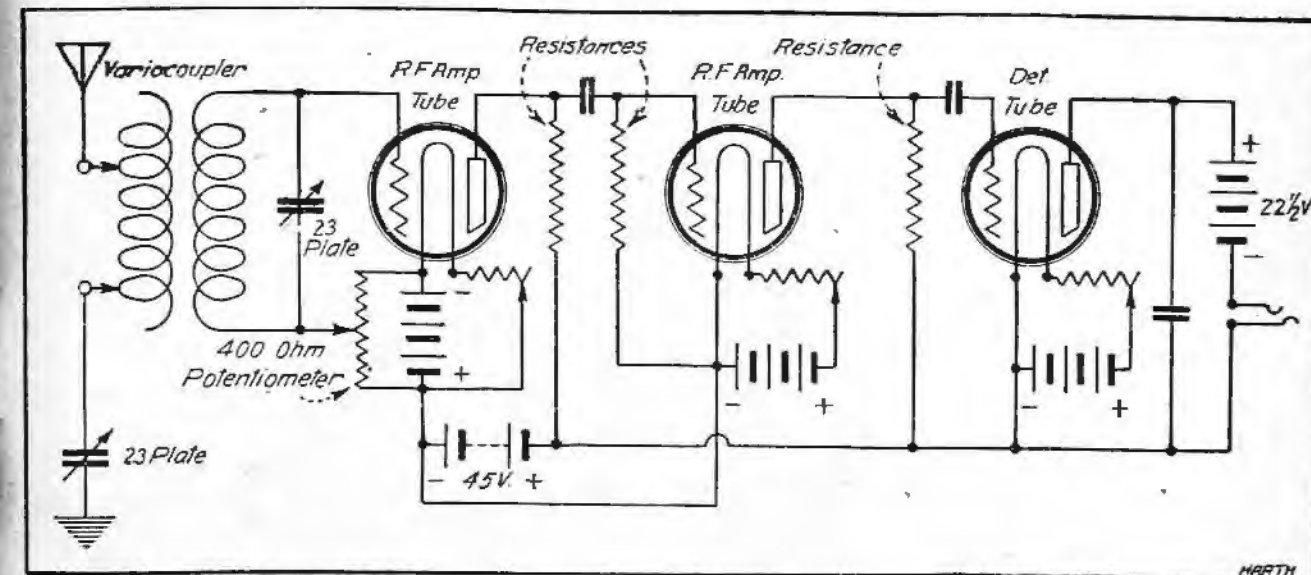If one will stop for an instant and consider the substance he is dealing with, it will be evident that plugs and jacks are useless in the radio frequency side of the receiver. The impulses then are still at the high inaudible frequencies and the insertion of a jack would reveal nothing.



Radio Frequency Amplification Utilizing the Reactance Form of Coupling Between Stages.

# AMBASSADOR

Long Range PHONES



AMBASSADOR Phones have no superior as to sensitiveness, clearness, balance and long range. Their quality is the best because they are produced in a new modern factory by master builders and every phone is backed by a one-year, written money-back guarantee.

Your set is no better than the phones and if you want to locate stations heretofore impossible to hear, use AMBASSADOR phones.

THE AMBASSADOR SALES CO.

Telephone Cortlandt 6296

78 CORTLANDT STREET

NEW YORK

If your dealer cannot supply you, write us his name or call at our store. Mail orders sent C. O. D. Immediately, fully covered by money-back guarantee.

## Ambassador Phones

- |   |  |
|---|--|
| 1. Are superior as to sensitiveness—  | 4. Contain powerful magnets, aged and magnetized by a special process to assure permanency—      |
| 2. Are better balanced as to volume—  | 5. Are accurately wound with special wire to give maximum number of turns and correct reactance. |
| 3. Have aluminum cups and well-designed head band to assure feather lightness with maximum wearing comfort— | 6. Sold under a written money-back-one-year guarantee.   |

# The Radio Guild

Inc.

## Is There Anything You Don't Quite Understand About Radio Frequency Amplification?

You don't need to wade through involved mathematical discussions to find the explanation you want. Kenneth Harkness makes it all plain in this one volume written in straightforward English.

## New! "The Theory and Practice of Radio Frequency Amplification" New!

By KENNETH HARKNESS

Let Kenneth Harkness, Chief Engineer of the Radio Guild, give you inside information on the design and wiring of commercial radio frequency amplifying receivers.

With scores of revealing photographs, drawings and wiring diagrams this book will tell you in simple and direct language:

1. The theory of radio frequency amplification.
2. How you can construct at low cost your choice of three different types of radio-audio frequency receivers of standard make—the most sensitive and selective on the market today.
3. Specifications of the best and patented type of radio frequency transformer. This information, with series of photographs, is released for the first time.
4. Complete details of a new and special tuning device for use with radio frequency amplification. It ensures the highest possible selectivity with long distance reception.
5. How to make a high frequency oscillator covering all wave-lengths.
6. The construction of a "Neutrodyne" receiver, with all the latest details.

### HOW TO OBTAIN YOUR COPY

Nothing we can say will describe the pleasure and instruction you will derive from reading this latest and most comprehensive work on radio reception. Mail the coupon below NOW and receive your copy in return.

Don't delay! Mail the coupon NOW

### SEND NO MONEY

Simply mail the coupon. When the book arrives pay the postman only \$1.00 plus postage.

## The Radio Guild, Inc.

256 West 34th Street, New York, N. Y.

These are only a few of the many subjects of current interest which are described in detail in this remarkable book. Nothing like this has ever been published before in one volume. It fills your need for authoritative information on the subjects which are most important to you today—long distance reception and selective reception. It will tell you in easy-to-grasp language how to make a receiver which will be so far superior in both appearance and operation to the sets your friends have that they will envy your success. And this book will tell you WHY your set operates as well as HOW to operate it to the best advantage.

The Radio Guild, Inc.,  
256 West 34th Street,  
New York, N. Y.

Please send my copy of "The Theory and Practice of Radio Frequency Amplification," by Kenneth Harkness. I will pay the postman \$1.00 plus the postage upon delivery. (Note: If you are likely to be out when the postman calls you may send cash with order now.)

Name .....

Address .....

City ..... State .....

(Outside U. S., \$1.10 cash with order)

# De Forest Radio Products Are Standard of the World!


De Forest makes many types of receiving sets, but probably the most successful have been the reflex circuit sets, one of which is illustrated below.

D-7-A with indoor loop has many transcontinental receiving records clear from California to New Jersey. The reflex is also made in Portable form—"3,000 miles in one hand" which operates with the new De Forest DV-6-A tubes on dry batteries, self-contained in the cabinet.

At the left are illustrated some of the laboratory precision De Forest parts, which every real radio fan knows all about. Note especially the new DV-6-A tube, designed for operation either with the standard type of A Storage Battery or with dry batteries. This tube operates in all models of the reflex set. Send for catalog and descriptive literature of complete De Forest line.

DE FOREST RADIO TEL. & TEL. CO.

Dept. G  
Jersey  
City,  
N. J.

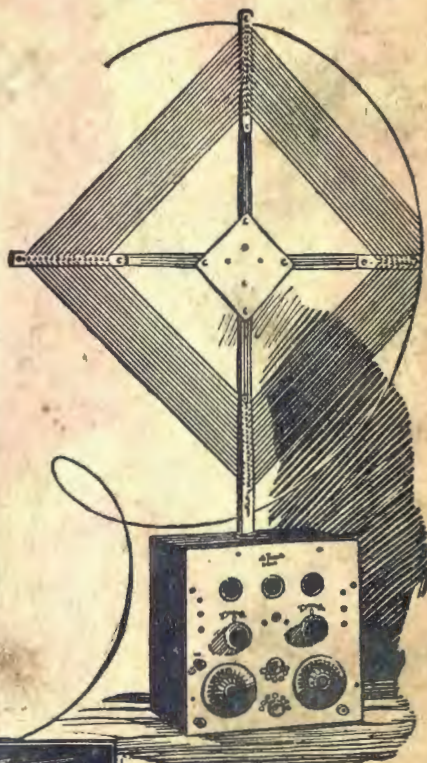

The Famous De Forest D-7-A Reflex. Price with Indoor Loop, \$125.00. Made also in Portable Form (D-10) with Dry Batteries Inside Cabinet, \$150.00.



Radio Fans Who "Build Their Own" Always Prefer De Forest Parts.

## RadioCraft Regenerative Receivers Are Made of De Forest Parts!

The RadioCraft Company, owned by the De Forest Company, manufactures RadioCraft Regenerative Receivers under Armstrong patent No. 1,113,149.

The RadioCraft Company uses in the manufacture of these sets the well-known and tested De Forest parts. Illustrated are D-6 with a receiving range of approximately 2,500 miles, which uses outdoor antenna,


and A and B batteries; and D-4, one of the lowest priced Regenerative receivers on the market, with a range of several hundred miles.

If you are interested in Regenerative sets send for the RadioCraft catalog.

THE RADIOCRAFT CO.  
INC.  
Dept. G.  
139 Franklin St.,  
Jersey City, N. J.



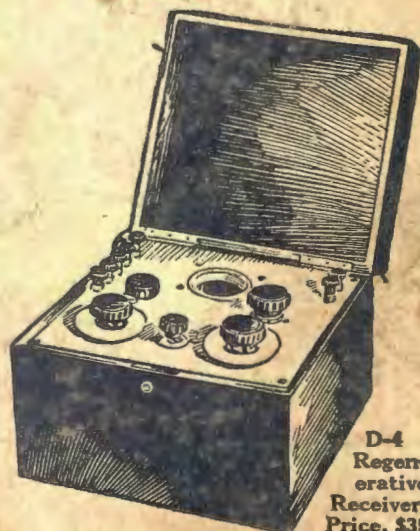RadioCraft's D-6 Receiver,  
Price \$130.00.



D-4  
Regenerative  
Receiver.  
Price, \$35