

# ELECTRONIC


## Servicing & Technology

JULY 1987/\$2.25

Troubleshooting low voltage regulator circuits

Solid-state rectifiers • Electronic steering
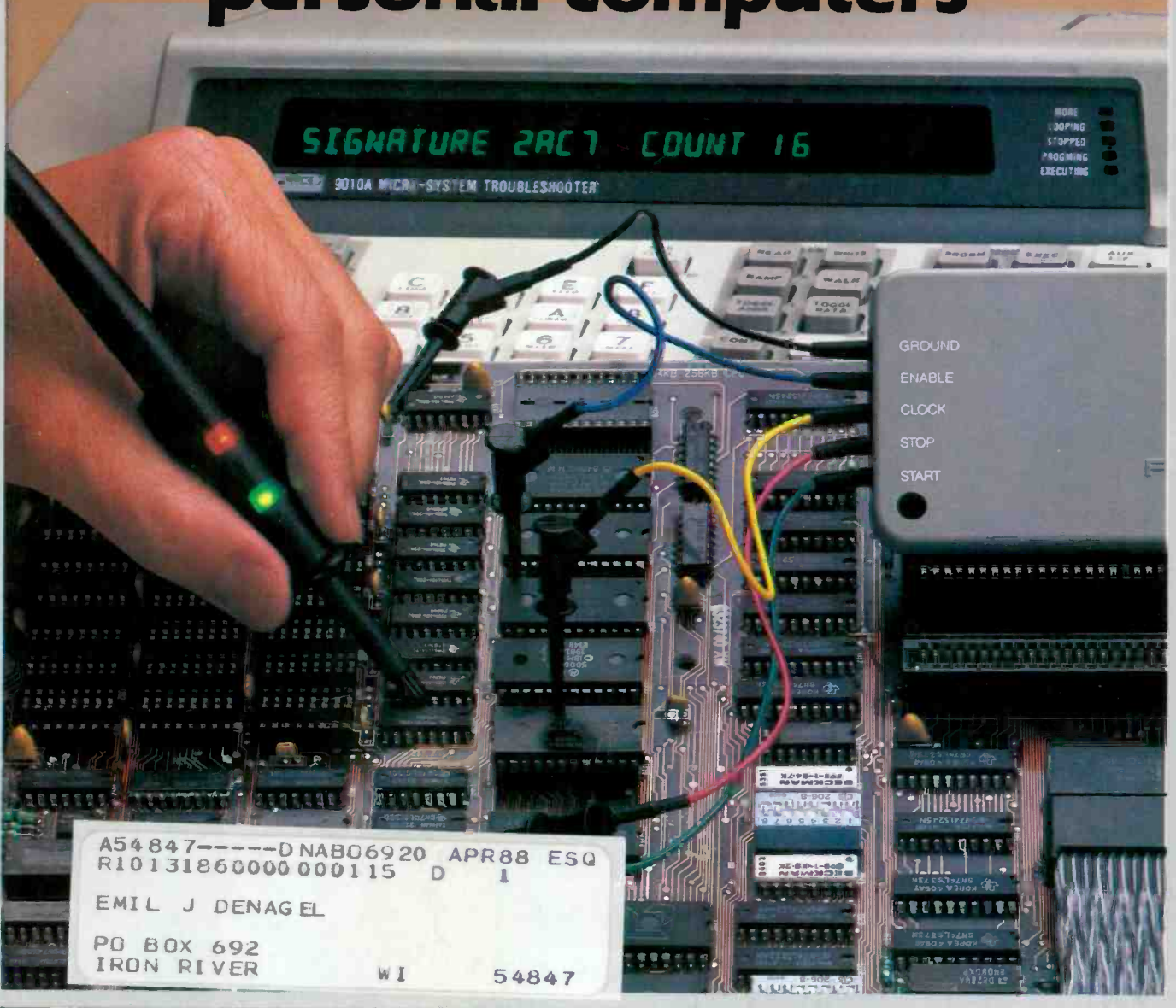
### Test equipment for personal computers



# Oops Proof. Now Even Better.

*Industry's Most Popular Heavy-Duty DMMs...  
Now Even Better With Dual-Fuse Protection  
And A Tougher Case.*

**The tough just got tougher.** When Beckman Industrial introduced heavy-duty DMMs tough enough to withstand accidental drops, input overloads and destructive environments, they quickly became the industry's most popular.

Now they're even tougher, thanks to the best dual-fuse protection you can buy and a new case. Covered by a one-year, no-fault guarantee against damage to the meter other than gross abuse.

For overloads, all voltage ranges can withstand transients up to 6KV. Resistance ranges are protected to 600 volts. Current ranges are protected by a 2 amp/600 volt fuse. The 10 amp range is protected by a 15 amp, 600 volt high energy fuse with 100,000 amp interrupt rating.



Our heavy-duty DMMs can withstand accidental drops, literally bouncing back for more, thanks to a new case made of Valox,<sup>®</sup> one of the most impact and corrosive chemical resistant thermoplastics around. Sensitive components are shock mounted for impact protection.

Even oil, water and industrial grime can't keep our heavy-duty DMMs away from the action. *Everything* is sealed with o-rings for maximum protection.

Of course, even the toughest DMM isn't much good if it can't deliver accuracy and the right combination of capabilities at the right price.

Check the HD DMM specs for yourself: Maximum voltage rating of 1500 volts DC, 1000 volts AC; tested to 40KHz; diode test function; and exclusive INSTA-Ohm<sup>®</sup> capability, now with an audible beeper, to make your HD even easier to use.

What's more, you can select just the model you need without paying extra. Start with the economical HD-100 at \$169.00 for solid, all-around meter performance. Choose the HD-110 with continuity beeper. Or, the HD-110T that lets you select Fahrenheit or Celsius temperature measurement with a simple field adjustment, accurately measuring from -4°F to +1999°F, and works with any K-type thermocouple. It also has a measurement range of 32°F to 392°F with the thermocouple provided.

You can even get the true RMS capability on the HD-130,



or with a 4 1/2 digit display required by the HD-140's accuracy.

HEAVY DUTY DMMs	HD100	HD110	HD110T	HD130	HD140
Digits		3 1/2			4 1/2
Accuracy (Vdc)		0.25%		0.1%	0.05%
Input Impedance		22 Megohms			10 Megohms
AC Conversion Type		Average		True RMS	True RMS
Bandwidth (AC Volts)		10KHz		40KHz	10KHz
Current Range Min. Reading		0.1µA			0.01µA
Max. Reading	2A	10A (20A for 30 Seconds)			
Continuity Beeper		✓			
Battery Life (Alkaline type)		2000 Hours			100 Hours

Visit your local Beckman Industrial distributor today. Compare. And discover why the toughest are tougher than ever.

*In Service  
Instruments,  
We're The One.*

**Beckman Industrial<sup>™</sup>**

Beckman Industrial Corporation Instrumentation Products Division  
A Subsidiary of Emerson Electric Company  
3883 Ruffin Rd. San Diego, California 92123-1898  
(619) 565-4415 • FAX: (619) 268-0172 • TLX: 249031  
© 1987 Beckman Industrial Corporation



## 2

August 10-15  
NPEC '87

Basic and advanced technical seminars, including a 40-hour VCR school, are interspersed with lighter moments.

## 4

Test your electronics knowledge

By Sam Wilson, CET

Experienced technicians will recall troubleshooting skills to breeze through this month's quiz.

## 5

No film? No processing?  
Instant playback?  
This is a CAMERA??

Coming to consumers: an untraditional electronic camera.

## 12

Test equipment for personal computers

By Conrad Persson


Specialized test equipment gives accurate, speedier diagnoses of microprocessor's digital circuitry; such equipment is described.

## 18

Solid-state rectifiers: using, abusing and selecting

By Joseph J. Carr, CET

What to do with what goes "pop" when lighting booms, or there is a high-voltage surge.

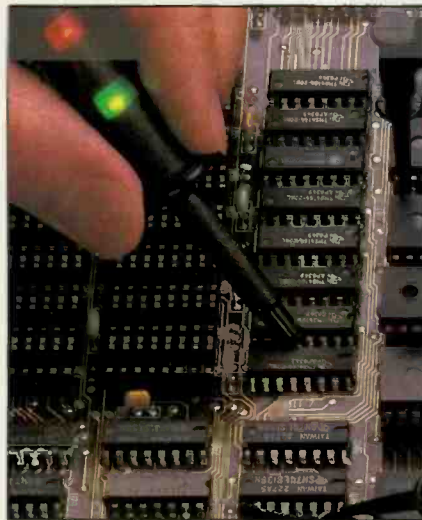

Page 12

Because software influences computer operation, computer circuitry tests can be misleading.



Page 10

Miniaturized lasers can bring laser technology to areas that previously were inaccessible.

## Departments:

- 6 Editorial
- 8 News
- 10 Technology
- 31 Profax
- 55 Literature
- 56 Books
- 57 Photofact
- 58 Products
- 60 Video Corner
- 62 Computer Corner
- 64 Audio Corner
- 66 Readers' Exchange
- 68 Advertisers' Index

## 26

New 4-wheel steering is electronically assisted

Recently introduced is this electronic automotive refinement that utilizes all four wheels to steer when a vehicle is being turned, promising better cornering, quicker response and straight-line stability.

## 41

Troubleshooting low-voltage regulator circuits

By Homer L. Davidson

"Symptoms of intermittent operation, HV shutdown...might be caused by defects in the low-voltage-regulator and not in...one of the circuits that is usually the source of these problems." Case histories highlight this article that also points out the increased number of complicating, integrated circuits involved with LV regulator dysfunction.

## 50

What do you know about electronics — a high-speed model

By Sam Wilson, CET

Not only the *model* that is diagrammed, but also explanations describing electron flow move at *high-speed* from the respected to the ridiculous. The author passes on strange theories he has encountered through the years, some of which may be familiar to **ES&T** readers.

**Aug. 10-15**

**NPEC '87**

**Register now  
for technical  
seminars  
(and good  
fun, too)**

An array of technical seminars is being lined up for the 1987 National Professional Electronics Convention that will be held August 10-15 in Memphis, TN.

The highlight of the educational lineup will be a 6-day, 40-hour, hands-on, basic VCR school. Normally presented only to instructors by the Electronic Industries Association's Consumer Electronics Group, this year's school will also be open to interested technicians. (However, student numbers will be limited for the hands-on session and it will be open only to those who commit to take the entire 40-hour course.)

On Saturday, Sharp Electronics and Toshiba America will split the day with two courses for more advanced technicians. Sharp will conduct an advanced VCR servicing school, while Toshiba instructs in servicing digital VCRs. On Tuesday, Hitachi will conduct a full-day session on Servicing Video Camcorders.

Other seminars that have been scheduled (although dates and times were not firmly set when this issue was printed) are: (1) Servicing Tough-Dog VCR Servos (Sencore); (2) Logically Servicing a Systems Control Microprocessor (Sencore); and (3) an all-day session on Servicing the New NEC Multispeed Computer.

Two additional seminars have been arranged expressly at the request of instructors. These forums (which are open to all attendees) will deal with (1) Job Placement for Graduating Students and (2) Trade School Curriculum Changes Required by Advancing Technology. Other technical seminars are being considered and may be added to the final agenda. The week-long convention also features golf and tennis outings on Monday, business management seminars on Tuesday, an electronics trade show on Wednesday and all day Thursday, then an opportunity for dealers to meet manufacturing officials on Friday. Special social events are planned

throughout the week.

The 1987 NPEC will be held at the famed hotel, The Peabody, near Memphis' Beale Street jazz district. Prices may include numerous sponsored meals, admission to the trade show, golf or tennis outings, all technical or management seminars, and all other activities for the 6-day event. Check with NPEC.

At the door and mail-in rates are \$160 for the first registrant from a family or business and \$140 for each additional member. The rate for children is \$75.

For a list of companies and other organizations that will have booths at the trade show, see the accompanying box.

For more information, write to NPEC '87, 2708 W. Berry St., Ft. Worth, TX 76109, or call 817-921-9061.

## **Meet these exhibitors at NPEC '87**

Borg Warner  
(Extended warranties)  
EIA/CEG  
Electronic Servicing  
& Technology  
GC Electronics  
GE/RCA  
Hitachi  
ISCET  
Kinyo (Head cleaners)  
NAP  
NEC  
NESDA  
Ogment  
Panson  
Projector/Recorder Belt  
PTS  
Radio Electronics  
Sencore  
ServicePlan  
Sharp  
Shield Electronics  
Tech Serv  
Ted Ferguson Insurance  
3M  
Video Aid



**REGISTRATION FORM**

Complete this form, detach and mail to **NPEC '87, 2708 W. Berry St., Ft. Worth, TX 76109; Phone 817-921-9061**

Name \_\_\_\_\_  
 Firm name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_  
 Zip \_\_\_\_\_ Phone \_\_\_\_\_

Full convention Registration includes all programmed meal functions and banquet, golf and tennis outings, door prize drawings, trade show, dealer's/manufacture's sessions and all meetings and workshops.

Indicate the number of people in your group to participate in each of the following:

Mon. Golf Outing	Mon. Tennis Tourney	Mon.-Fri. Instructors Conference	Tues. Mgmt. School	Wed. House Meet.	Thurs. Trade Show	Fri. Mgrs. Session	Sat. Tech. School	Sun. Night Banquet
------------------	---------------------	----------------------------------	--------------------	------------------	-------------------	--------------------	-------------------	--------------------

Member of (check appropriate boxes):  
 NESDA;  ISCET;  TESDA;  Non-Member;  Distributor  
 Dealer;  Mfr.;  Speaker;  Electronics Instructor;  
 Press;  Sales Rep.;  Other \_\_\_\_\_

Print legibly the names (including nicknames) of all attendees as the names should appear on the name badges:

1. (you) \_\_\_\_\_
2. (spouse) \_\_\_\_\_
3. \_\_\_\_\_

Send, or pay at door	Full registered (fully paid) adult:	Each add'l. adult from same family or business:	Totals
	<b>\$160</b>	<b>\$140</b>	<b>\$ _____</b>
Daily Registration Rate	\$40	\$40	\$ _____

Special program for children and young adults may include some separate meal and/or social functions.

Young Adults;  
 Ages 13-19 (List names and ages below). No. at \$90 each \_\_\_\_\_; Amt. \$ \_\_\_\_\_  
 Children's program;  
 Ages 5-12 (List names and ages below). No. at \$75 each \_\_\_\_\_; Amt. \$ \_\_\_\_\_  
 Tot. No. \_\_\_\_\_ Tot. No. \_\_\_\_\_ Check No. \_\_\_\_\_ Date: \_\_\_\_\_ Tot. Amt. \$ \_\_\_\_\_  
 Adults: \_\_\_\_\_ Children: \_\_\_\_\_ No.: \_\_\_\_\_ Date: \_\_\_\_\_  
 Arrival Day \_\_\_\_\_; Date \_\_\_\_\_; Time \_\_\_\_\_; Departure Day \_\_\_\_\_; Date \_\_\_\_\_; Time \_\_\_\_\_

Make check payable to **NESDA**: mail to 2708 W. Berry, Fort Worth, TX 76109  
 Visa  ; MasterCard  No. \_\_\_\_\_

4. \_\_\_\_\_
5. \_\_\_\_\_
6. \_\_\_\_\_

**Special Room Rates:** Single or double, \$70. Children under 18 free if using same accommodations.

**Room Reservations:** Will be handled solely by the hotel but through NESDA. When we receive your convention registration, we will send you a card for making room reservations directly with The Peabody at our special convention rates. But do register early to ensure a room. To guarantee a room at The Peabody, reservations must be made by July 10, 1987.

# A New Vacuum

## For Field Service

### Model AAA with *An-ionic\** filtration retains particles as small as .3 micron.

The new high performance Atrix Model AAA field service vacuum features *An-ionic* filtration. Electro-chemically charged filter media traps and retains sub-micron particles immediately—does not depend on coarse particle buildup to eliminate fine particle bypass. The all-purpose AAA sets new vacuum standards for performance, dependability and economy.


- Efficient—retains minute paper and toner particles, ideal for laser printers, copiers, computers and peripherals
- Static safe—operator and unit fully grounded for ESD protection
- Cool operation—intake to exhaust ratio of 4:1 prevents overheating—unit has filter status indicator
- Economical—uses throwaway cannister for neat, low-cost disposal

\*Economical new *An-ionic* filters are available for existing competitive field service vacuums.

Call the Atrix Easy-Order 800 Number for fast service.



**Atrix Model AAA**

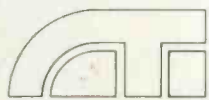

**ATRIX, INC**

14221 Ewing Avenue South, Burnsville, MN 55337

612-894-6154

Fax 612-894-6256

1-800-222-6154

Telex 910 240 0139

Circle (36) on Reply Card

# Test your electronics knowledge

By Sam Wilson, CET

The questions in this quiz deal mostly with troubleshooting subjects. So, it should be easy for experienced technicians.

- When a logic 1 is delivered to point A in Figure 1 the output should be at
  - logic 0.
  - logic 1.
- You suspect that the local oscillator is dead in a certain table model AM radio. You tune the radio to a strong station 1.1MHz. Assuming it has an IF frequency of 455kHz, it should play if you inject a pure sine wave frequency of \_\_\_\_\_ kHz into the converter at the oscillator input.
- You want to determine the impedance of a speaker so you put the circuit of Figure 2 together and adjust R2 for
  - zero current.
  - maximum positive deflection.
  - maximum negative deflection.
  - 20mA.
- After you have correctly adjusted R2 in the circuit of Figure 2, you remove it from the circuit and measure its resistance. If the speaker has an impedance of  $8\Omega$  the resistance of R2 should be approximately \_\_\_\_\_  $\Omega$ .

5. Identify the type of diode illustrated in Figure 3.

6. The cathode of the diode in Figure 3 is connected to lead

A.) x.

B.) y.

7. A milliammeter is connected across the on-off switch of a small AM radio. (See Figure 4.) This radio has an RF section. It also has two IF sections. The audio power section has push-pull amplifiers. In addition to checking the on-off

switch, the milliammeter in this test setup can be used to check the

A.) IF stages.

B.) RF stages.

C.) audio power section.

D.) the local oscillator.

8. An emitter-base short of the transistor in Figure 5 is shown with a broken line. The collector voltage should be

A.) 12V.

B.) 0V.

9. The amplifier in Figure 5 is connected in a

A.) common emitter configuration.

B.) common base configuration.

C.) common collector configuration.

10. If the resistor marked R in the circuit of Figure 5 is open, the transistor will be

A.) saturated.

B.) cut off.

Answers are on page 63.

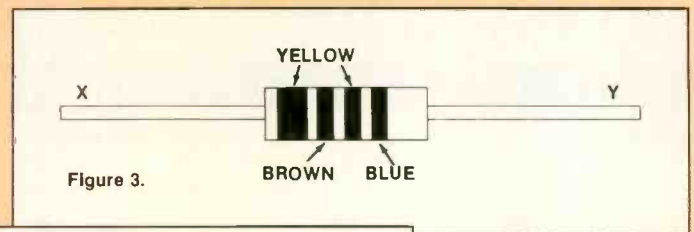


Figure 3.

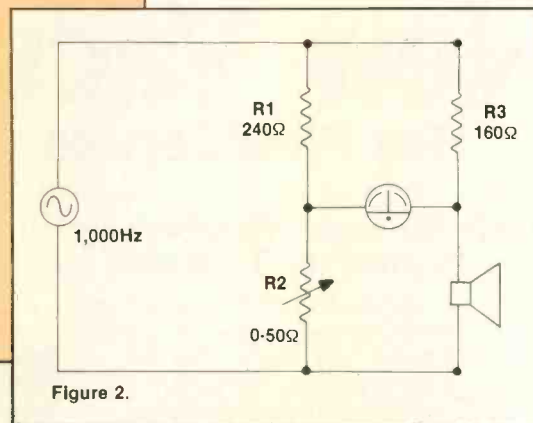


Figure 2.

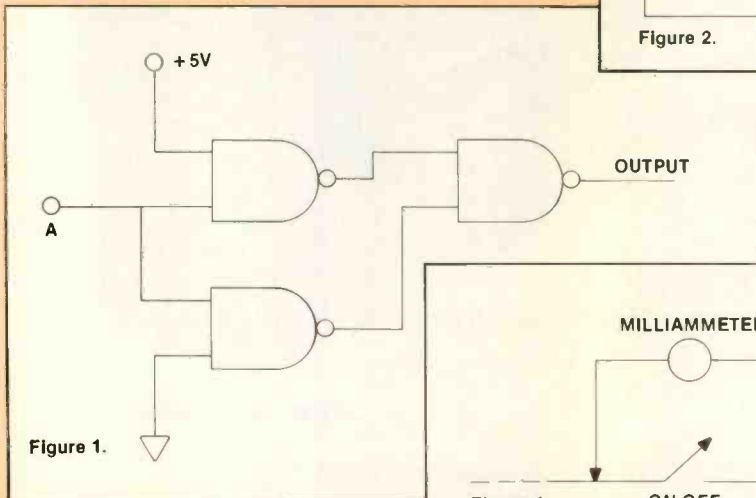


Figure 1.

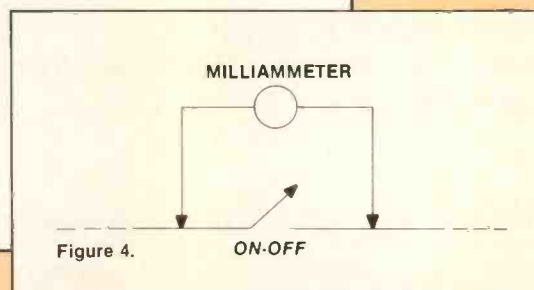


Figure 4.

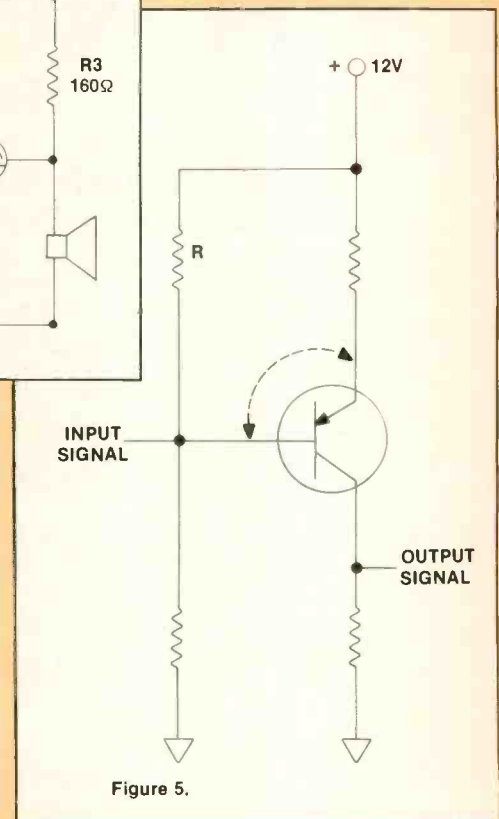


Figure 5.

**No film?  
No processing?  
Instant playback?**



# This is a CAMERA??

The untraditional Casio VS-101 electronic camera records and stores images on standard video floppies, playing them back instantly through any standard television. The camera-TV connection is simple and direct. Printouts are possible with the optional color video printer (VP-10).

The action is fast and furious? This still camera incorporates a high-resolution auto-exposure system with shutter speeds up to 1/1000s to freeze the fastest

movements into a sharp, clear image available for instant replay or later reference.

Up to 50 frames for recording/playback can be stored on a single video magnetic floppy disk. A built-in erase function allows multiple reuse of each disk.

Introduced at the Summer Consumer Electronics Show, Chicago, in June, the VS-101 will be available to consumers after Dec. 1, 1987.



## Good as Gold.

### The 70 Series Multimeter: The Shining Standard By Which Others Are Measured

These multimeters give you solid value for your money. A 3-year warranty keeps you from paying the price over and over for lesser quality meters.

Choose from either the basic 73 or the feature-rich 75 and 77. You'll find the features you need at the price you can afford. Touch Hold™ for holding readings. Audible tones for continuity checks. Autoranging for simple operation.

Uncompromised quality at competitive prices. Get your hands on a 70 Series Multimeter at leading electronics distributors nationwide. Or call toll free 1-800-227-3800, ext. 229 for more information.

FROM THE WORLD LEADER  
IN DIGITAL MULTIMETERS.

#### FLUKE 73, 75, 77

\$79, \$109, \$145	3-year warranty
0.7%, 0.5%, and 0.3% basic dc accuracy	Audible continuity (75 & 77)
Analog/digital display	Range hold (75 & 77)
Volts, ohms, 10A, diode test	Multipurpose holster (77)
Autorange	Touch Hold function (77)
2000+ hour battery life	



© 1987, Fluke



# So you're not interested in computers

Want a good reason to learn about servicing personal computers? How's this? According to the 1987 edition of the "Consumer Electronics Annual Review" published by the Consumer Electronics Group of the Electronics Industry Association, "...many manufacturers feel that by the year 2000 consumers will be spending more for home information processing and communications equipment than they will for purely entertainment products.

"Functions normally associated with a business office are performed in nearly every home. Income and expenses have to be kept track of, appointments to be made and messages to be taken and delivered. There's correspondence to be handled, and where there are students in the house, reports to be researched and written. For many years businesses have turned to electronics for products that simplify and improve information handling. Now similar, though much more affordable, and often less complex products that bring office-like efficiencies to the home are being made and marketed by consumer electronics manufacturers.

"Almost 3.8 million personal computers were sold for home use last year and, with software and accessories, represented a \$3.8 billion business. Today a personal computer housed in a typewriter-like console, and with brain power equal to that of the room-sized multimillion dollar computers of the 1960s, can be purchased for less than \$300, though prices run up to \$2,000 depending on

the functional capabilities, memory power and accessories included.

"The term 'computer literate' has become more than a catch phrase to describe those in the know. It's now a requirement for graduation from many high schools and colleges, and some colleges include the cost of a computer for each student in their tuition. 'Keyboarding,' or how to interact with a computer, is being taught at the elementary grade level.

"In the home, computers are used for financial and family function planning, record keeping, educational enrichment, training and word processing. Connected to the telephone lines through a built-in or add-on device known as a modem, computers provide access to outside data banks containing a vast variety of research information, along with business, professional and transportation directories, games and message centers that serve as electronic bulletin boards for computer owners with similar interests. Modems also let computers be used for home shopping, banking and travel reservation services that are now becoming available."

If you have made the decision not even to consider servicing personal computers that are used in the home without at least considering what's involved in learning about them and getting geared up to service them, you may be taking a chance on letting the consumer electronics revolution pass you right by.

*Nile Conrad Perren*



# LEADER

**NOW  
Battery  
Powered!**

Choose the New LBO-315 for ac/dc,  
or the current LBO-325 for ac only.

**Sometimes it's hard to  
go back for a scope!**

**60-MHz full-function  
field-service Attache Case  
Oscilloscope is so light and  
small it will be taken  
everywhere, every time.**

LBO-325 packs all the power and performance of a cumbersome, backbreaking, 60-MHz workbench oscilloscope into an easy-to-carry, ultra-compact, featherweight unit. Although its 3½-inch CRT is as big and clear as screens on large field-service scopes—LBO-325 weighs only 9 lbs. So it won't weigh field-technicians down, no matter how far afield they go! LBO-325 is so small it fits inside a 3-inch deep attache case with room to spare for a multimeter, service manuals and some tools. The ideal full-function scope for a cramped work area or crowded bench.

**Reduces the cost of  
service calls.**

Time is money. A scope left in the vehicle takes time to retrieve. One kept in the shop causes repeat service calls. The LBO-325


Attache Case Oscilloscope is so easy to carry and use, techs will take it everywhere, every time. And the time saved translates into extra profits for years to come.

**Outperforms all other  
portables:**

- 60 MHz • Dual channel • ALT TIME BASE simultaneously displays main waveform and any expanded portion
- ALT TRIG for stable display of 2 asynchronous signals • Bright, sharp 12-kV trace • Large 3½-inch PDA CRT • Illuminated graticule
- Comprehensive triggering • TV-V and TV-H sync separators • Variable trigger hold-off • Delay line shows sharp leading edges • CH-1 output drives low-sensitivity instruments
- Measures only 3 x 9 x 11½ inches • Weighs 9 lbs.

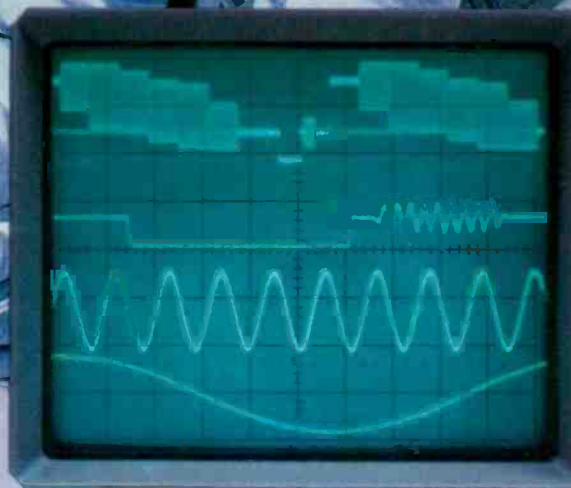**Two-year warranty.**

Built tough to provide long use, LBO-325 is backed by Leader's 30-year reputation for reliability and by factory service depots on both coasts.



LBO-325 CRT is shown actual size.

Call toll-free  
**(800) 645-5104**  
In NY State  
**(516) 231-6900**

Request an evaluation sample, our latest Test Instrument Catalog with over 100 outstanding products, the name and address of your nearest "Select" Leader Distributor, or additional information.

For professionals  
who  
know  
the  
difference.

**LEADER**  
Instruments Corporation

380 Oser Avenue  
Hauppauge, New York 11788  
Regional Offices: Chicago, Dallas  
Los Angeles, Boston, Atlanta  
In Canada call Omnitrax Ltd.  
(514) 337-9500

For Demonstration Circle (5) on Reply Card

For Information Circle (4) on Reply Card



## 1987 Source Code and Data Code booklet

If you've ever puzzled over the manufacturer or vendor source of any electronics product, this booklet is for you. The Engineering Department of the Electronic Industries Association publishes its "Source Code and Data Code" booklet annually.

Alphabetic and numeric symbols are assigned and registered by the EIA's Engineering Department. This service, which is free to EIA members, is available to all manufacturers of electronic equipment and components for an annual registration fee of \$30.

The EIA code provides for adding numerals to the source code symbol to identify the year and week of production. Altogether, coded electronic products may be identified as to production sources, or as to the vendor assuming product responsibility, as well as to the time period in which they were manufactured. The Source Code and Data Code booklet contains an

alphabetical and numerical listing of those code numbers that are stamped or marked on all electronic products.

Copies of this booklet are available for \$1 each from the EIA Engineering Department, EIA, 2001 Eye St. NW, Washington, DC 20006.

## Diehl files bankruptcy

The United States Bankruptcy Court, Northern District of Texas, has announced the filing of a petition for Relief under Chapter 7 of Title 11, U.S. Code, on February 13, 1987, by Vince E. Diehl (525-80-3413) and Judy A. Diehl (194-36-3580) doing business as Diehl Enterprises; Diehl Industries; Diehl Engineering; Diehl Publications, 6004 Estacado Lane, Randall County, Amarillo, Texas 79109.

The Case Number is 287-20088-7, dated April 29, 1987.

The announcement bears this statement: "Creditors: File your

claims NOW. Claims not filed by claims bar date generally are not allowed. BAR DATE is August 19, 1987."

Three items are brought out in the announcement.

Item No. 1—Section 341(a) Meeting Date: May 21, 1987, at 3:45 p.m. in Room 112, U.S. Courthouse, 205 E. 5th, Amarillo, TX 79101.

Item No. 2—Filing deadline for Section 523(c)/Section 727 Complaints: July 21, 1987.

Item No. 3—Section 524(d) Discharge Hearing: August 17, 1987 at 1:30 p.m. in Room 314, U.S. Courthouse, 205 E. 5th, Amarillo, TX 79101.

## There's still time for free summer workshops

VCR and digital/microprocessor 1-, 2- and 5-day workshops have been organized by the Consumer Electronics Group of the Electronic Industries Association (EIA) in the listed cities and on the

The how-to magazine of electronics

# ELECTRONIC

*Servicing & Technology*

Editorial, advertising and circulation correspondence should be addressed to: P.O. Box 12901, Overland Park, KS 66212-9981 (a suburb of Kansas City, MO); (913) 888-4664.

## EDITORIAL

Nils Conrad Persson, *Editor*  
 Carl Babcoke, *Consumer Servicing Consultant*  
 Dan Torchia, *Group Managing Editor*  
 Marjorie Riggin, *Associate Editor*  
 Joy Culver, *Editorial Assistant*  
 Darryll Fortune, *Editorial Assistant*  
 Alisa Carter, *Editorial Assistant*  
 Ramona M. Vassar, *Editorial Assistant*

## CONSULTING EDITORS

Homer L. Davidson, *TV Servicing Consultant*  
 Christopher H. Fenton, *Circuit Fabrication Consultant*  
 Bud Izen, *Computer Servicing Consultant*  
 Victor Meeldijk, *Components Consultant*  
 Kirk G. Vistain, *Audio Consultant*  
 Sam Wilson, *Electronics Theory Consultant*

## ART

Kevin Callahan, *Art Director*  
 Tim Lynch, *Graphic Designer*

## BUSINESS

Cameron Bishop, *Group Vice President*  
 Eric Jacobson, *Publisher*  
 Greg Garrison, *Sales Manager*  
 Stephanie Fagan, *Promotions Manager*  
 Kelly Hawthorne, *Promotions Coordinator*  
 Dee Unger, *Advertising Supervisor*  
 Julie Chilson, *Advertising Coordinator*

## ADVERTISING

Regional advertising sales offices are listed in classified pages.

## ADMINISTRATION

R. J. Hancock, *President*  
 Doug Riemer, *Circulation Director*  
 Jo Ann DeSmet, *Circulation Manager*  
 Dee Manies, *Reader Correspondent*

**ELECTRONIC SERVICING & TECHNOLOGY** is the "how-to" magazine for technicians who service consumer electronics equipment. This includes service technicians, field service personnel and avid servicing enthusiasts, who repair and maintain audio, video, computer and other consumer electronics equipment.

**SUBSCRIPTION PRICES:** one year \$18, two years \$30, three years \$38 in the USA and its possessions. Foreign countries: one year \$22, two years \$34, three years \$44. Single copy price \$2.25; back copies \$3.00. Adjustment necessitated by subscription termination to single copy rate. Allow 6 to 8 weeks delivery for change of address. Allow 6 to 8 weeks for new subscriptions.

**PHOTOCOPY RIGHTS:** Permission to photocopy for internal or personal use is granted by Intertec Publishing Corp. for libraries and others registered with Copyright Clearance Center (CCC), provided the base fee of \$2 per copy of article is paid directly to CCC, 21 Congress St., Salem, MA 01970. Special requests should be addressed to Eric Jacobson, publisher.  
 ISSN 0278-9922 \$2.00 + 0.00



Member, Audit Bureau of Circulation



Member, American Business Press



Member, Electronic Servicing Dealers Association



©1987 All rights reserved.



indicated dates. For specific sites and local contacts, call the national headquarters of co-sponsoring service organizations: NESDA/ISCET in Ft. Worth, 817-921-9061 or 9101 (for Philadelphia and Chicago courses call NARDA/NASD, Chicago, 312-953-8950).

April 1986. For the first four months of 1987, camcorder sales were 50% ahead of the sales in the same time period, last year.

Color television also is enjoying strong sales: The industry is selling color TV sets this year at the

average rate of 48,000 per day. Projection and B&W television sales reflect a reduced demand (10% and 14%, January through April), but sales of VCRs continue to run slightly ahead of 1986, as of the end of April.

**ES&T**<sub>inc</sub>

#### Some subjects in VCR course

- Electrostatic sensitivity
- Isolation transformer
- Dismantling of VCR
- Cleaning tape heads, paths, belts
- VHS, Beta systems
- Theory of recording
- High, low frequency problems
- Types of power supply
- Record, playback paths
- Switching (EE/VV modes)
- TV signal selection
- Demodulation

#### Some exercises from digital workshop

- Power supply
- Light emitting diodes; dip switch and binary counting
- Logic levels; logic probes; logic pulsers; logic gates
- Voltage and binary comparators
- Monostable and astable applications for the 555
- D/A and A/D converters
- Phase lock loop
- Microprocessor and memories

Ohio	VCR	July 6-10
Memphis	VCR	July 13-17
Kansas City, MO	VCR	July 21-25
Macon, GA	VCR	July 27-31
Tacoma, WA	mp	August 21-22
Norfolk, VA	VCR	August 25-29
Boston	VCR	Aug. 31-Sept. 4
Philadelphia	VCR	To be set
Chicago	VCR	To be set

The following workshops are structured specifically for instructors in vocational education, and are co-sponsored by State departments of vocational education.

Nebraska	mp	July 6-10
California	mp	July 6-10
Nevada	mp	July 13-17
Alabama	mp	July 20-24
Michigan	mp	July 27-31
West Virginia	mp	July 27-31
North Dakota	mp	August 10-14
Memphis	VCR	August 10-15

#### Camcorders up 103% in April '87 vs. April '86

Sales of camcorders, the camera/VCR combinations designed for family moviemaking, zoomed to more than 107,000 units in April of this year, compared with 53,000 sold to the nation's dealers during

**... Over 3,000,000 Sold and Still The Best General Purpose Multimeter! ...**



The Reason Is Clear . . .

**Simpson 260<sup>®</sup> VOM**  
Has Features No Digital Can Match!



Latest 260<sup>®</sup> Series 7 \$124.00

- "Instant" null, peak, trend and continuity indications
- High immunity to transients, RF interference
- dB measurement capability at no extra cost
- Resistance indication from zero to infinity
- Self-powered voltage, current and dB ranges—no batteries to fail
- Reliable, accurate performance even under extreme environments
- Easy, low-cost maintenance—no expensive "chips" to fail
- UL Listed per UL-1244 Standard for Safety—Electrical and Electronic Measuring and Testing Instruments
- Complete line of UL recognized accessories
- Options include mirrored scale, extra overload protections, roll top carrying case

See the World Famous 260 Series 7, the 260-6XL, the 270 and the Pocket-Size 160<sup>®</sup> at Leading Electronics/Electrical Distributors



#### SIMPSON ELECTRIC COMPANY

853 Dundee Avenue, Elgin, IL 60120  
(312) 697-2260 • Telex 72-2416 • Cable SIMELCO  
Canada: Bach-Simpson Ltd., London, Ontario  
England: Bach-Simpson (U.K.) Ltd., Wadebridge, Cornwall

Circle (6) on Reply Card

## Miniaturized, more powerful lasers introduced



New microlaser product: Infrared and green-light microlasers in a wide range of powers will be available in this same package which measures 4-inches long by 1 3/4-inches in diameter.

A family of miniaturized laser products developed from revolutionary microlaser technology has been introduced.

"Vastly smaller, more efficient, and superior in performance, microlasers can be mass produced at significantly reduced costs," according to Tom Wolfram, general manager of Amoco Laser Company, the company that developed the technology. "A technological breakthrough, microlasers will not only replace existing gas tube discharge lasers, but also will stimulate new product development in consumer markets."

"Capable of improving the quality of high resolution projection television, film scanners and color


printers, microlasers also will facilitate new radar scanners for aircraft and automobile collision avoidance systems," Wolfram adds.

These microlasers represent the first uniform technology that can address virtually all laser applications requiring green, blue, red or infrared laser light. Unique hybrids, microlasers combine laser diodes, the size of a grain of salt, to optically pump solid-state laser materials with nonlinear optical crystals to provide frequency modification.

Amoco Laser Company's plans were to introduce its first microlasers in mid-May 1987. The initial products are infrared microlasers operating at wavelengths of



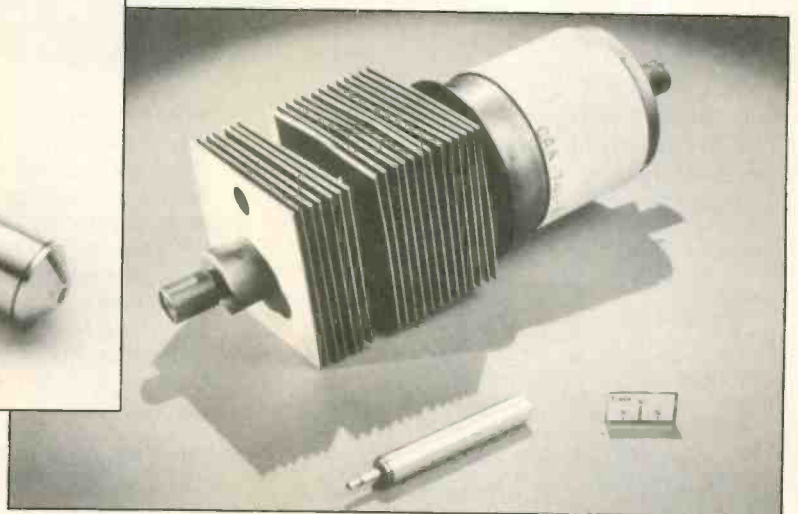Low cost, high-volume laser products will be available in the near future in this ultra compact module.



The microlaser (pictured bottom right) is expected to rapidly replace current air-cooled ARGON-ION lasers (pictured center).





1,064nm and at 1,320nm in the power range of 25mW to 100mW. A low noise power supply will be introduced with the new infrared and the green-light microlasers.

The second introduction, scheduled for fall, will launch two frequency-doubled, green-light, 525nm microlasers. One version will be at 2mW with a higher power model offered at 5mW CW.

Combining the high efficiency, small size and ruggedness of laser diodes with the excellent beam quality and broad range of wavelengths of solid-state lasers, these new microlasers will have immediate applications in optical instrumentation, telecommunications, optical sensing and scanning, color display and optical memory, according to Wolfram.

Shrinking not only the laser but also the power supply from the size of a refrigerator to a hand-held package, the microlaser requires only 2W of electrical power while equivalent gas discharge-tube lasers consume 2kW of power.

Other operating advantages microlasers have over gas-discharge tube lasers include:

- Efficiency—up to 1,000 times higher
- Size—up to 100 times smaller
- Optical Noise—up to 1,000 times less
- Voltage—100 to 1,000 times lower
- Service Life—up to 50 times longer
- Power Control and Modulation

Microlasers represent a major advance in laser efficiency, compact size, ruggedness, power and versatility.

Because these devices can be mass produced, product prices are expected to drop by orders of magnitude over the next few years. Amoco foresees a price reduction from the current ten thousand dollar range for comparable products to below one-hundred dollars in the next five to seven years.

This technology is expected to open large new markets in the same way that transistors not only replaced vacuum tubes in existing products, but also ushered in vast new markets for electronic devices.


Like the first computers that were the size of rooms evolving into hand-held calculators, the microlaser has been miniaturized to fit easily into consumer products. Because of their low cost, ruggedness and efficiency, microlasers will go places lasers have never gone before, such as into the living room in color projection television. And they will dramatically improve applications in optical instrumentation, telecommunications, optical sensing and scanning, color display, laser printers, optical memory, as well as target designation and range finding.

Microlasers are unique hybrids combining laser diodes to optically pump solid-state laser materials with nonlinear optical crystals to provide the laser with a broad range of colors: infrared, red, green, blue and ultraviolet lasers to serve virtually all markets.

Based on a proprietary design that lends itself to low-cost manufacturing methods, microlasers are designed for high-volume OEM customers, but all customers will benefit from Amoco reduced costs.
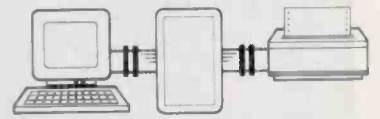
# Test RS232C In A Zip.

Test RS232C data communications interfaces—like computers to printers, computers to modems, and computers to computers—fast and easy in the palm of your hand with Beckman Industrial's low-cost, easy-to-use line of testers. Each is self-contained in a Toughpak case, including five models in a durable zippered pouch, and a 10-year warranty on every model. Prices start as low as \$49.95.



See your nearest Beckman Industrial distributor today, or send for free brochure. We'll send it to you in a zip.

*Quick Cable Customizing*

*Fast RS232C Interfacing and Testing*

*LED Identification of Cable Configurations*

*Pocket and Hand-held Compactness*

*Speeds Up Trouble Shooting*

*10 Standard, Low-Cost Models*



EasyPATCH™ 704

Easy BOB™ 750

**In Service  
Instruments,  
We're The One.**

**Beckman Industrial™**


Beckman Industrial Corporation Instrumentation Products Division  
A Subsidiary of Emerson Electric Company  
3883 Ruffin Rd., San Diego, California 92123-1898  
(619) 565-4415 • FAX: (619) 268-0172 • TLX: 249031  
© 1987 Beckman Industrial Corporation

Circle (34) on Reply Card

**ES&T**



# Test equipment for personal computers

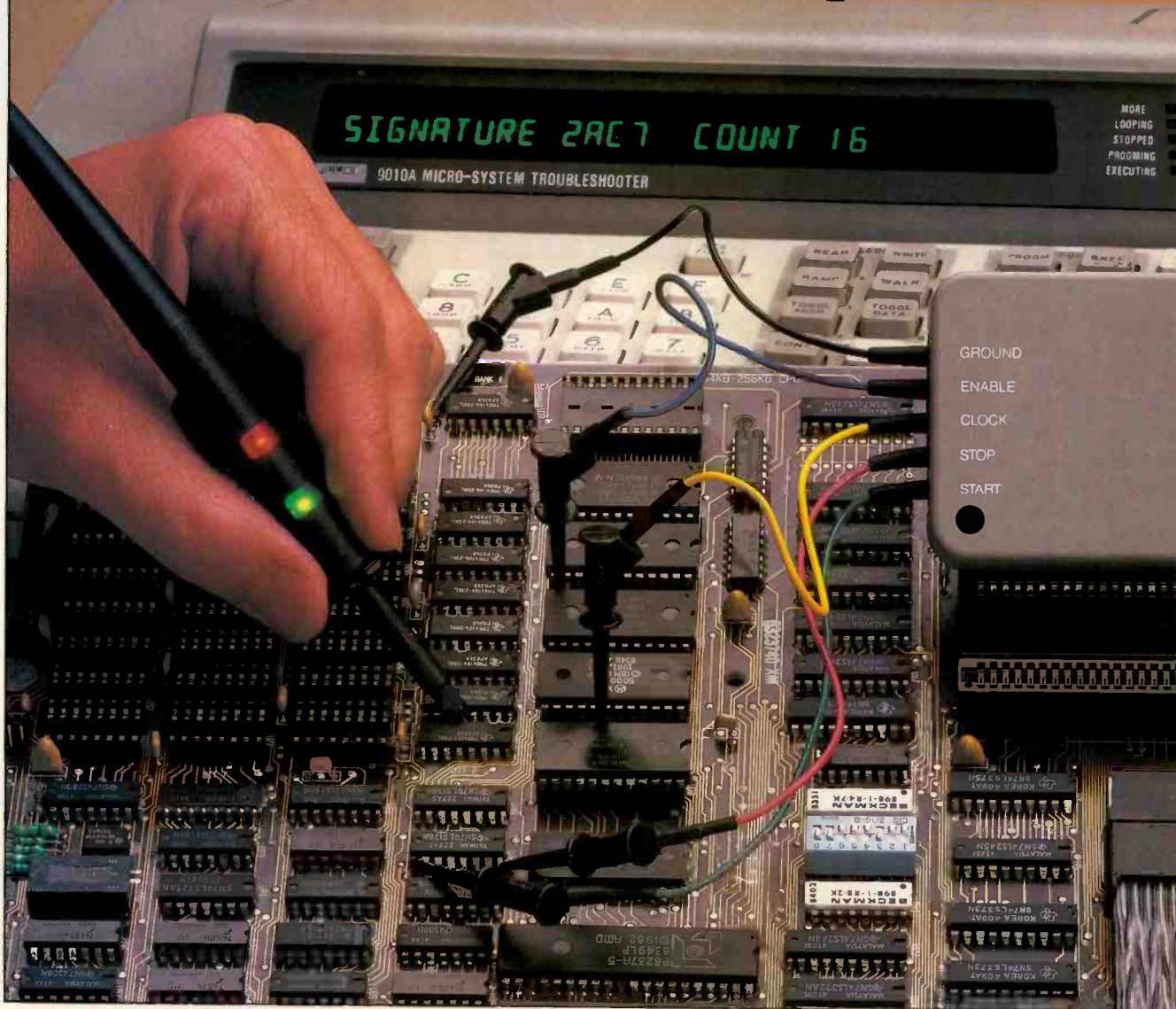

By Conrad Persson

Besides a thorough knowledge of the theory of operation of the unit being serviced, in this case computers, the most important tools to bring to servicing are the right pieces of test equipment. For starters, of course, there are the standard pieces of test equipment that are on the bench of any competent technician: a good DMM and a good wideband oscilloscope.

## Specialized test equipment

Unlike most consumer elec-

tronics equipment, the operation of a personal computer is determined by the software used to operate it as well as the physical circuitry it's composed of. For that reason, observation of symptoms and drawing of conclusions as to the nature of the problem based on those observations, while a valid approach to the problem, may be misleading. Furthermore, while they can solve some problems, the DMM and oscilloscope have limitations when applied to computers. Specific digital test equipment can isolate problems that analog test equipment wouldn't even be able to

touch, and in many cases, can speed the diagnosis of even those problems that could have been solved otherwise.

## The kinds of digital test equipment

Test equipment for personal computers runs the gamut of sophistication from the simplest nodal testers up through the extremely sophisticated units that can be plugged right into the microprocessor socket to exercise the complete microcomputer system and automatically track down the circuitry where the fault lies.



# New GPS Series: Tek sets the pace with SmartCursors™ and push-button ease.

Work faster, smarter, with two new general purpose scopes from Tektronix. The four-channel, 100 MHz 2246 and 2245 set the new, fast pace for measurements at the bench or in the field. They're easy to use and afford, by design.

**On top: the 2246 with exclusive integrated push-button measurements.** Measurements are accessed through easy, pop-up menus and implemented at the touch of a button. Measure peak volts, peak-to-peak,  $\pm$  peak, dc volts and gated volts with new hands-off convenience and on-screen readout of values.

SmartCursors™ track voltmeter measurements in the 2246 and visually indicate where ground and trigger levels are located. Or use cursors in the manual mode for immediate, effortless measurement of waveform parameters.

**Both scopes build on performance you haven't seen at the bandwidth or prices.** Lab grade features include sweep speeds to 2 ns/div. Vertical sensitivity of 2 mV/div at full bandwidth for low-level signal capture. Plus trigger

Features	2246	2245
Bandwidth	100 MHz	100 MHz
No. of Channels	4	4
Scale Factor Readout	Yes	Yes
SmartCursors™	Yes	No
Volts Cursors	Yes	No
Time Cursors	Yes	No
Voltmeter	Yes	No
Vertical Sensitivity	2 mV/div	2 mV/div
Max. Sweep Speed	2 ns/div	2 ns/div
Vert/Hor Accuracy	2%	2%
Trigger Modes	Auto Level, Auto, Norm, TV Field, TV Line, Single Sweep	
Trigger Level Readout	Yes	No
Weight	6.1 kg	6.1 kg
Warranty	3-year on parts and labor including CRT	
Price	\$2400	\$1875

sensitivity to 0.25 div at 50 MHz, to 0.5 div at 150 MHz.

Accuracy is excellent: 2% at vertical, 2% at horizontal. And four-channel capability includes two channels optimized for logic signals.

**Best of all, high performance comes with unmatched convenience.** You can see it and feel it — in the

responsive controls and simple front-panel design, in extensive on-screen scale factor readouts, and in simplified trigger operation that includes Tek's Auto Level mode for automatic triggering on any signal. Start to finish, the GPS Series saves steps and simplifies tasks.

**Get out in front! Call toll-free today to order, to get more details or a videotape demonstration.**

**1-800-433-2323**

In Oregon, call collect 1-627-9000



Featuring four channels, flexible triggering, extensive CRT readouts and push-button ease of use, the new Tek 2246 (left) and 2245 (above) bring high-quality, low-cost analysis to diverse applications in digital design, field service and manufacturing.

**Tektronix**  
COMMITTED TO EXCELLENCE

### The logic probe

As we discussed just last month in the June 1987 issue of *ES&T* in an article entitled "IC Tester," if you have the knowledge and skills to trace a problem in a personal computer system to a specific area of the circuitry, you may isolate the problem using a logic probe.

The logic probe indicates the

logic state of a point being tested, whether it is at a logic HIGH or LOW. A sophisticated probe will have indicators to show if the test point is HIGH or LOW or exhibiting pulses. Some will even have a memory or pulse stretcher that will show the presence of a one-shot pulse that is of such short duration that either it's insuffi-

cient even to light the indicator, or lights it too briefly to be recorded by the human eye.

### The logic pulser

The logic pulser is the active counterpart to the logic probe. When you place its tip against an IC pin and push the button, it will inject a pulse, or a train of pulses, into the IC to seek an aberrant response.

### The logic current tracer

Another piece of low-level test equipment that can help in locating problems in personal computer and other digital circuitry is the current tracer.

Even in an extremely thin printed circuit conductor, a change in current induces a magnetic field. A number of test-equipment manufacturers have designed probes that will sense a minute magnetic field and hence current changes in printed circuit wiring.

This device is called a current tracer and is useful in troubleshooting personal computer circuits; for example, to locate solder or copper bridges, or stuck nodes.

To locate a short (see Figure 1), you can use the current tracer in conjunction with the logic pulser. Simply place the pulser on the circuit wiring near the pin that's the source of the signal that's disappearing. Then place the current tracer downstream from the pulser and slowly move the tracer

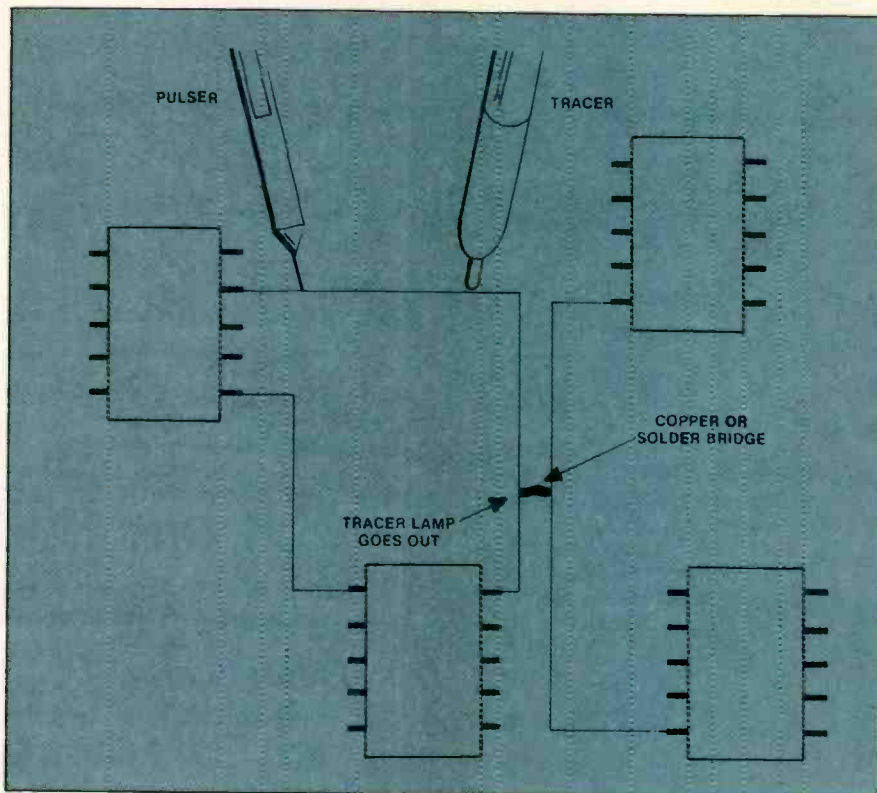


Figure 1. You can use the current tracer in conjunction with the logic pulser to locate short circuits caused by solder or copper bridges.

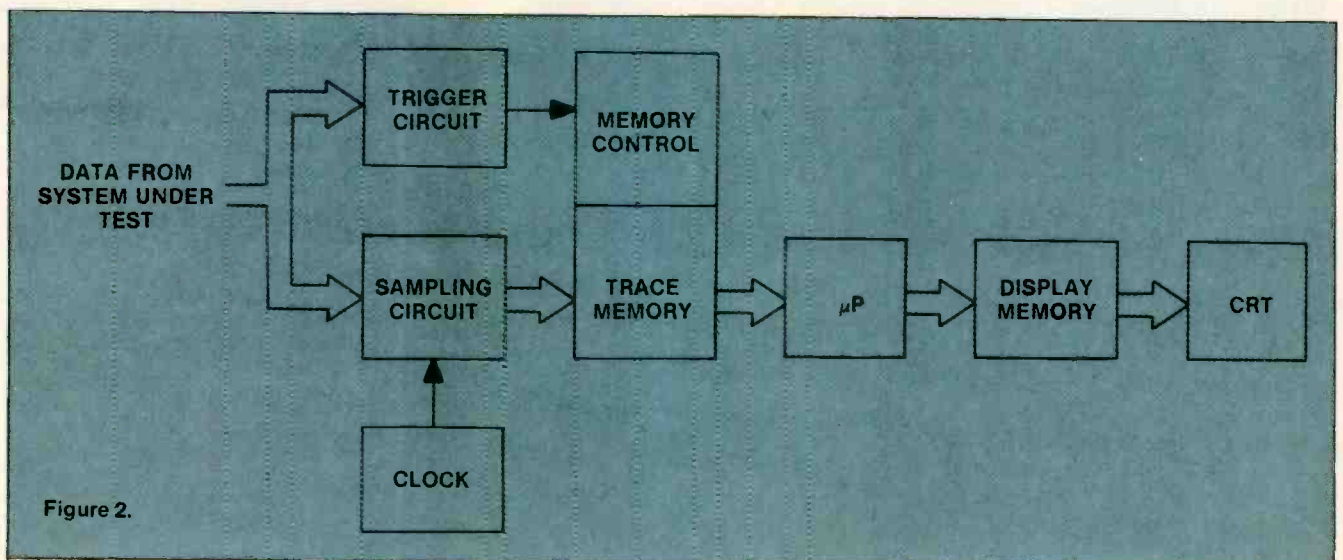


Figure 2.

Figure 2. A timing analyzer works by sampling the input waveforms to determine whether they are high or low. It is concerned with only one voltage threshold.



along the circuit foil. When the current tracer's light goes out, you've just passed the point where the short is located.

### Logic test clips

A logic test clip is a testing device that clips directly over an integrated circuit package. As you release the spring tension on the clip after placing it over the IC, one test probe comes into contact with each pin on the IC. Each test probe is connected to an LED that indicates whether that point in the circuit is at a logic HIGH or LOW.

### Logic analyzers

Most logic analyzers are really two analyzers in one. The first part is a timing analyzer, while the second part is a state analyzer.

A timing analyzer is the part of a logic analyzer that is analogous to an oscilloscope: They can be thought of as close cousins. The timing analyzer displays information in the same general form as a scope, with the horizontal axis representing time and the vertical axis as voltage amplitude.

### Sampling the input signals

A timing analyzer works by sampling the input waveforms to determine whether they are high or low. It cares about only one voltage threshold. If the signal is above threshold when it is sampled, it will be displayed as a 1 or high by the analyzer. By the same criterion, any signal sampled that is below threshold is displayed as a zero or low. From these sample points, a list of ones and zeros is generated that represents a 1-bit picture of the input waveform. As far as the analyzer is concerned, the waveform is either high or low—no intermediate steps. This list is stored in memory and also used to reconstruct a 1-bit picture of the input waveform, as shown in Figure 2.

### The state analyzer

A state analyzer is used most often to trace the execution of instructions through a processor system. Each memory cycle's data, address and status codes are captured and displayed as they occur on a microprocessor's buses.

A state, for a logic circuit, is a sample of a bus or line when it is valid (the state of the signal is sampled).

For example, take the simple "D" flip-flop, like the one in Figure 3. Data at the "D" input will not be valid until a positive-going clock edge comes along. Thus, a state for the flip-flop exists when the clock edge occurs.

Now imagine that you have eight

of these flip-flops in parallel (Figure 4). All eight are connected to the same signal as a clock. When a positive transition occurs on the clock line, all eight will capture data at their "D" inputs. Again, a state occurs each time they get a positive transition on the clock line. These eight lines are analogous to a microprocessor bus.

If you connected a state analyzer to these eight lines and told it that

**CALL TOLL FREE**

Include work address and phone number for Free Catalog.

**800-824-2873**

### DIGITAL MULTIMETERS

#### BECKMAN Beckman Industrial

- All 300, HD, and Circuitmate series
- All accessories in stock

MODEL	PRICE
HD100	\$169
HD110	\$199
HD130	\$259
HD140	\$279
300	\$179
310	\$145
320	\$179
330	\$219
350	\$229
360	\$289
4410	\$239

#### FLUKE

- Autorange  Analog display
- Touchhold function
- 0.3% accuracy  Heavy duty

MODEL	PRICE	MODEL	PRICE
21	\$ 99	75	\$109
23	\$145	77	\$145
25	\$229	8010A	\$289
27	\$259	8012A	\$359
37	\$215	8020B	\$199
52	\$189	8024B	\$249
73	\$ 79	8050A	\$399

FLUKE 77 Digital Multimeter

**SALE \$119**

LIST \$145

### WAYNE KERR

MODEL	PRICE
4210	\$2200
4225	\$1500

### SCOPES

#### HITACHI



Denshi America, Ltd.

- All 20 models in stock
- 2-3 year warranties
- 20-100 MHz

MODEL	PRICE
VC6041	\$3900
V209	\$798
V222	\$575
1050	\$1299
1100A	\$2490
422	\$740
425	\$845
680	\$1275

#### HITACHI V-509

Portable Dual Trace Scope

**SALE \$1199**

LIST \$1445

#### IWATSU



- All 14 models in stock
- 2-3 year warranties
- 20-250 MHz

### IWATSU (CONT.)

MODEL	PRICE
5702	\$ 535
5705	\$ 899
5706	\$ 749
5710	\$1245
5711	\$1695
5712	\$2999

### POWER SOURCES

#### POWER DESIGNS

- Low and high voltage power sources
- 1-5 year warranties

MODEL	PRICE
TP340	\$750
TP343A	\$795
TW347	\$590
TW5005W	\$505
TW6050A	\$748
2K20	\$695
2020B	\$750
4050	\$560
6150	\$615

### SOLA POWER

MODEL	PRICE
SPS800	\$ 873
63-13-114	\$ 237
63-13-150	\$ 456
63-13-175	\$ 580
63-13-210	\$ 672
750VAUPS	\$1976
750VAUPSI	\$2580


**USED TEST EQUIPMENT, TOO!—OVER 3,000 MODELS AVAILABLE AT HUGE DISCOUNTS WITH WARRANTIES!**

■ Quantity Discounts Available ■ Dealers Welcome ■ Freight and Tax Extra ■ Immediate Availability of Equipment

**United States Instrument Rentals, Inc.**

A U.S. Leasing Company  
2988 Campus Drive  
San Mateo, CA 94403

Circle (7) on Reply Card

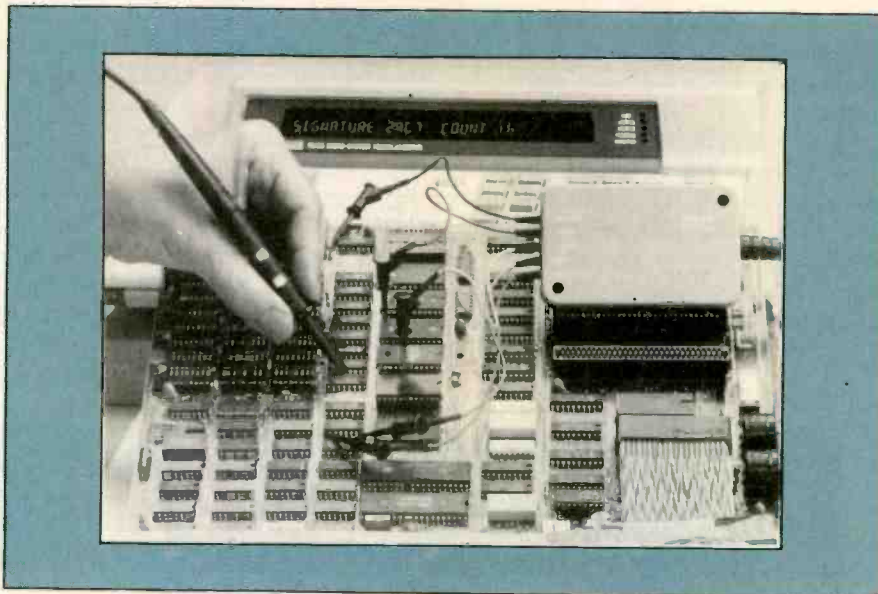

A computer-system tester, such as this series 9000 unit by Fluke, plugs directly into the microprocessor socket. Software written by the tester's manufacturer, or in some cases the user, exercises all elements of the computer system and offers a diagnosis of the problem.



This test device, the AID/88 by Vu-Data, is designed specifically to test one type of personal computer, IBM PCs and compatibles that are based on the 8088 processor. The software (or more correctly *firmware*) for this unit comes in the form of ROM that is preprogrammed and plugged into the tester.

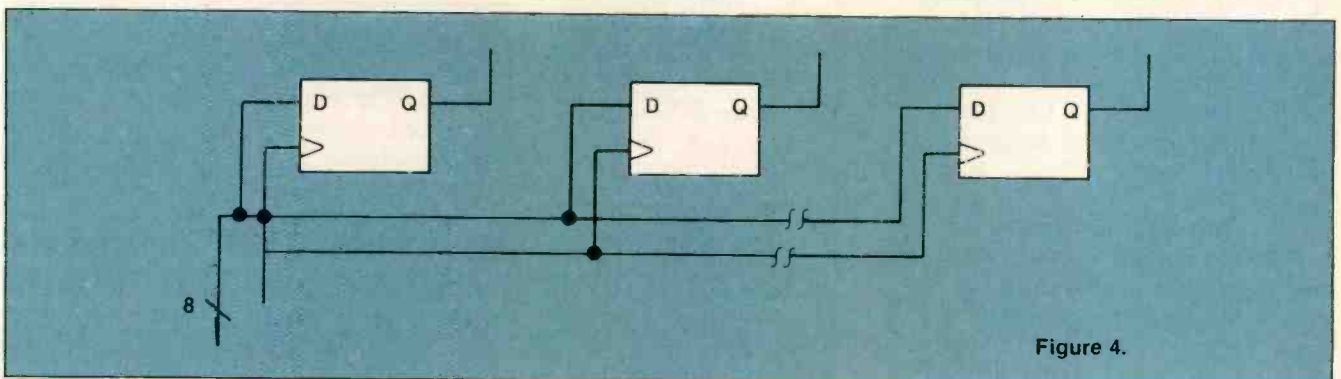


Figure 4.

Figure 4. If you connect a state analyzer to these eight lines and tell it to collect data when there is a positive transition on the clock line, the analyzer will follow your directions.

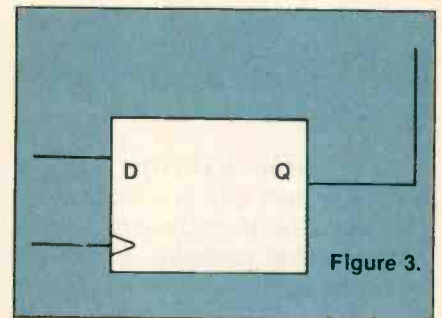


Figure 3.

Figure 3. A state for a logic device such as this "D" flip-flop is a sample of a bus or line when it is valid.

a positive transition on the clock line is the instant when you want to collect data, the analyzer would obey. Activity on the inputs will not be captured by the state analyzer unless the clock is going from a low to a high state.

#### Computer-system testers

The heavy artillery of the personal computer testers are the testers that can be plugged right into the microprocessor socket and used to operate the system in a controlled manner that systematically leads to location of the fault. In other words, the piece of test equipment replaces the microprocessor chip itself, and under software written by the testing unit's manufacturer, or in some cases, by the user, sends commands to the rest of the system being tested that are designed to test every point in the system. Then it records the responses and from the data collected makes a determination of the nature of the fault.

It's kind of like having a super-fast technician pulsing and probing every point in the system, recording the results then interpret-



ing the data to make a determination as to the cause of the problem.

There are several different types of computer-system testers. Some of these units are designed to test only one brand of computer, or only computers based on one kind of microprocessor. Other computer-system testers can test just about any kind of microcomputer system using so called *personality* modules that adapt them to the particular system being tested.

One of these test units is the Fluke 9000 series of Micro-system Troubleshooters. According to the brochure for the 9010A, a programmable test device, "There's no need to learn a processor's programming language to operate a Fluke Micro-System Troubleshooter. Four built-in, preprogrammed test routines are provided to automatically check the entire  $\mu$ P kernel-Bus, RAM, ROM, and I/O. One keystroke initiates all four. Each is a comprehensive routine with descriptive diagnostics to help guide you to the fault."

The brochure goes on to provide a partial list of processors supported: 1802, Z80, 6502, 6800, 6802, 6809, 8048, 8080, 68000 and more.

Another unit, not programmable, but designed to operate with software developed on the 9010A, is the 9005A.

#### Another PC tester

Because the IBM PC is such a popular computer, a lot of attention has been given to producing everything for use with it from software to accessories. Such is the case with test equipment.

Another manufacturer of test equipment, called the AID/88 for this personal computer, is Vu-Data Corporation. According to this company's brochure, "The basic AID/88 PC Tester is intended to be used to troubleshoot to the component level the system board in the IBM PC 1 PC, XT and portable personal computers. Functions of the AID/88 are applicable to any PC that is IBM PC compatible, using an 8088 microprocessor."

Because the AID/88, unlike the Fluke test units, is specifically designed to test the IBM PC, its test programs actually are installed in the unit in a hardware memory

(ROM), also called *firmware*, so it is neither necessary nor possible to program the unit, or to load software into it prior to testing.

#### The choice is broad

No one ever said that consumer electronic servicing would be easy. As the range of consumer electronic products and their complexity becomes ever greater, merely

choosing the level of test equipment needed becomes a difficult exercise. As demonstrated here, the range of choice of test equipment for personal computers is broad: everything from DMMs and oscilloscopes, through simple logic testers, right up to sophisticated programmed or programmable test units that all but automatically test the unit.

**ES&T**



## Because Your Customers Deserve the Best



### Hitachi Original Replacement Parts

Quality, reliability, service...they're the touchstones of the Hitachi tradition, as recognizable as our trademark. And now those same standards that have earned us our reputation as a technological leader in consumer products, back up our new line of **Hitachi Original Replacement Parts**.

We know that for the service professional, time wasted is profit lost. Which is why Hitachi makes it easy for you. With our complete line of parts, we provide you with a single source for all your repair needs—and a profitable addition to your business. From VCR kits, IC chips and

diodes—to battery packs, video, audio accessories and technical publications.

What's more, our nationwide network of distribution centers means that you can get the parts and accessories you need, when you need them. And, of course, **Hitachi Original Replacement Parts** are included in our total service support program...because your customers deserve the best.

For more information, call toll-free  
**1-800-447-2882.**

**HSC SERVICE COMPANY**  
division of Hitachi Sales Corporation of America

401 W. Artesia Blvd.  
Compton, CA 90220  
(213) 537-8383

Circle (8) on Reply Card

# Solid-state using, abusing

By Joseph J. Carr, CET

It's inevitable every summer. An afternoon thunderstorm makes its hour-long sweep across town, pouring out torrents of rain and causing a dancing display of electrical pyrotechnics to light up the sky. That magnificent temper tantrum of nature throws scores of

transient high-voltage slugs of electrical energy onto the power lines—and pops the rectifiers in dozens of pieces of electronic equipment.

Although most don't meet their demise in so spectacular a manner, solid-state power supply rectifiers

are a major source of failure in electronic equipment. During a period when I worked in a large service organization, we kept records on repairs made by both in-house technicians and contractors. Power supply problems formed the overwhelmingly large percentage of faults, and the rectifier diode was a big contributor.

Some rectifier problems are caused by high voltage transients on the power lines, as in the little scenario given above. In other cases the problem is that the engineers who designed the circuit underspecified the rectifier, and the owner eats the mistake for years to come. I recall one famous HF single-sideband transceiver that was reknowned for reliability problems. It turned out, however, that almost all repairs involved not the transceiver but its ac power supply. When used in mobile applications, the set worked well (and long) for the customer. But when it was taken inside and made a base station—BLAM!—the darn thing would go down every few months. The entire problem was the solid-state rectifiers: they were underspecified. Beefing up the rectifier to the correct type removed the problem, eliminated costly (and embarrassing) call-backs and made the owner think we were the only people for about 50 miles who knew any smoke about radio transmitters.

## What is a rectifier?

The word *rectify* means "to make right" or "to remove impurities." You probably can guess that the main requirement for a rectifier is that it convert bidirectional ac into a unidirectional form of current. Although industry once used mechanical switches and vacuum tubes to accomplish that job, all


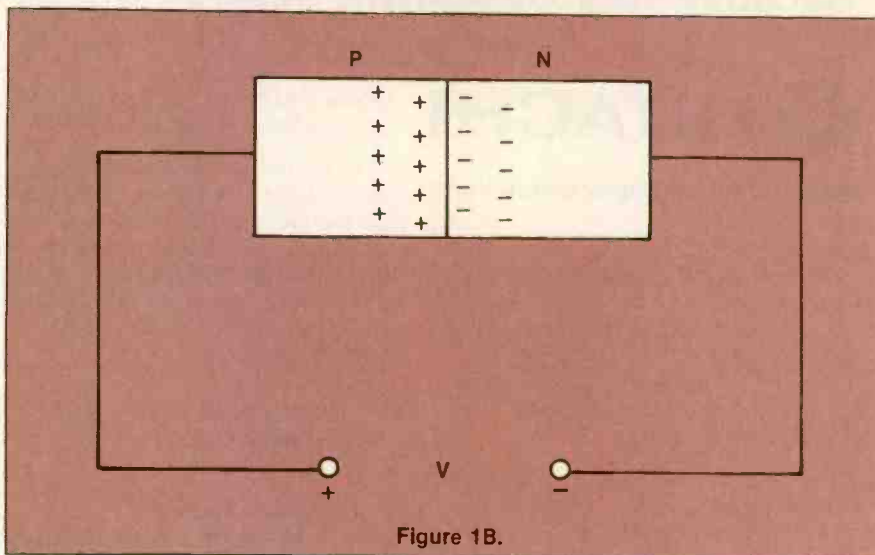


Figure 1. Because a semiconductor diode allows current flow when biased in the forward direction but impedes current when biased in the reverse direction, it is useful in rectifying ac to dc.

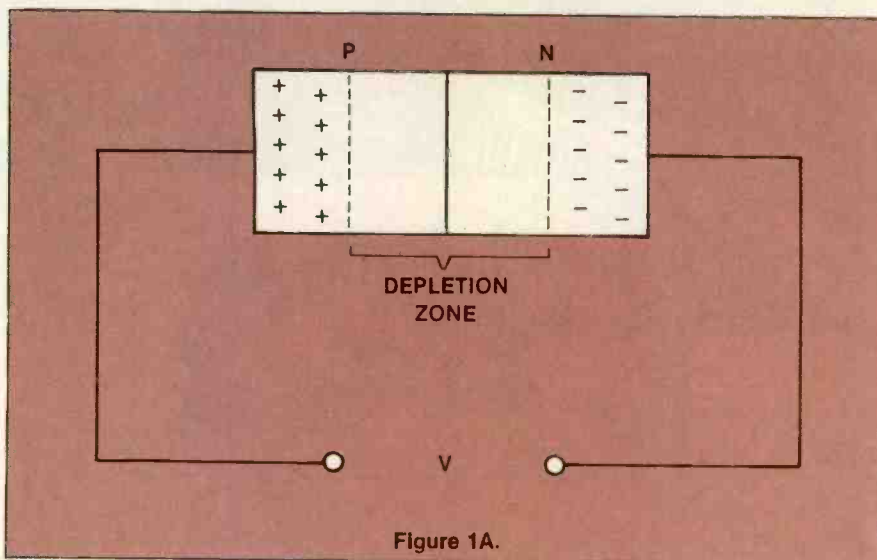

# rectifiers: and selecting

modern circuits rely on solid-state PN junction rectifiers.

The modern solid-state rectifier really isn't so modern after all. Various versions of the rectifier date back to the dawn of the radio—indeed the electrical—age. But all common rectifier diodes in use today are silicon PN junction diodes (see Figure 1), and those date back 25 years. During my apprentice days in the late fifties, we used 500mA “tophat” rectifiers to replace the older selenium types. In fact, many technicians simply bridged the silicon rectifier across the terminals of the dead selenium unit—until they found that practice caused more problems than it solved.

The PN junction diode rectifier (Figure 1) consists of a piece of silicon semiconductor material that is doped with impurities to form N-type material at one end, P-type material at the other end. The charge carriers (which form electrical current) in the N-type material are negatively charged electrons, while the charge carriers in the P-type material are positively charged “holes.”

The reverse bias situation is shown in Figure 1A. In this case the negative terminal of the voltage source (V) is connected to the P-type material, while the positive terminal is connected to the N-type material. Positive charge carriers are thus attracted away from the PN junction toward the negative voltage terminal, as negative charge carriers are drawn away toward the positive terminal. That leaves a *depletion zone* in the region of the junction that contains no carriers. Under this condition, there is little or no current flow across the junction. Theoretically, the junction current is zero, but in real diodes there is

always a tiny leakage current (the smaller the better).

The forward biased case is shown in Figure 1B. Here the polarity of voltage source V is reversed from Figure 1A. The positive terminal is applied to the P-type material, and the negative terminal is applied to the N-type material. Because like-charges repel, the charge carriers in both P- and N-type material are driven away from the power supply terminals toward the junction. The depletion zone disappears and current flows in the circuit.

From the above description, you can tell that a rectifier diode is able to convert ac into dc because it allows current to flow in only one direction.

Figure 2 shows the standard circuit symbol for the solid-state rectifier diode (Figure 2A), along with some common shapes of actual diodes. The *input* side where ac is applied is the anode, while the dc output is the cathode. The diodes shown in Figures 2B through 2G are positioned so that the respective anodes and cathodes are aligned with those of the circuit symbol in Figure 2A. Rectifiers 2B through 2E are epoxy or plastic package devices, and are the type seen by most readers. The cathode end will be marked with a rounded end (2B), a line (2C), a diode arrow (2D) or a plus sign (2E).

The diode shown in Figure 2F is the old-fashioned (now obsolete) tophat type. Unless otherwise specified, the tophat type can safely pass a current of 500mA, while those in Figures 2B through 2E generally pass 1A (or more, for larger packages).

The stud-mounted type shown in Figure 2G is a high-current model. These diodes will be rated at currents from 6A or more (50A and

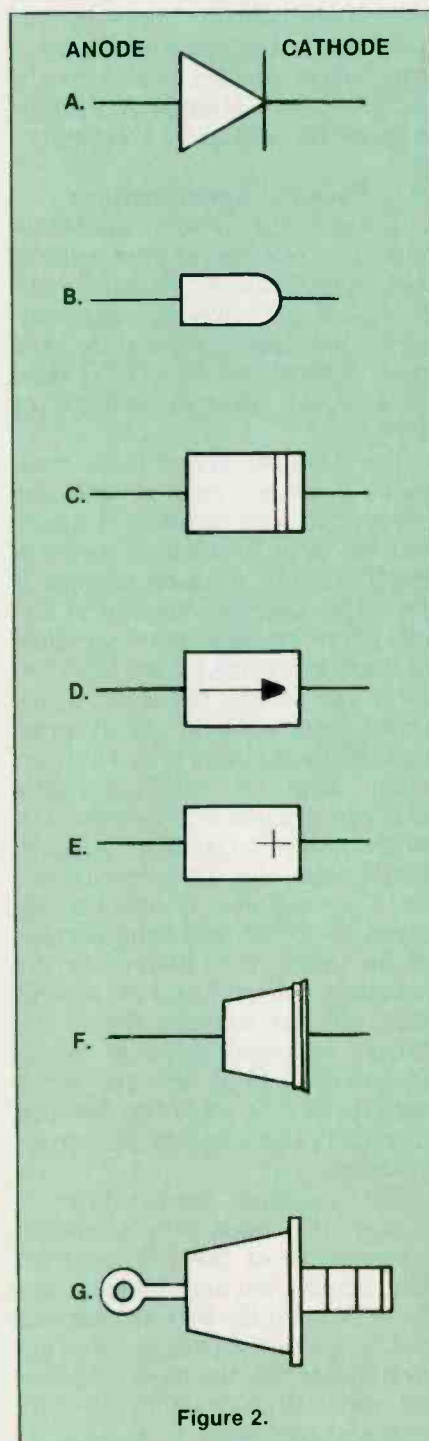


Figure 2.

Figure 2. Semiconductor diodes come in a number of different shapes and sizes.



100A models are easily obtained). These diodes are mounted, using a threaded screw at one end, which also forms one electrical connection. The other electrical connection is the solder terminal at the other end. Unless otherwise specified, the solder terminal is the anode, and the stud-mount is the cathode terminal. Exceptions to the polarity rule are sometimes seen. The reverse polarity diodes either will have an arrow symbol pointing in the opposite direction (the arrow always points to the cathode), or an *R* suffix on the type number (for example, 1NxxxxR).

### Rectifier specifications

The use and abuse of solid-state rectifiers revolve around several key specifications: forward current, leakage current, surge current, junction temperature and peak inverse voltage (PIV) (also called peak reverse voltage or PRV).

The forward current is the maximum constant current that the diode can pass without damage. For the popular 1N400x series of rectifiers, the forward current is 1A. The leakage current is the maximum current that will flow through a reverse biased junction. In an ideal diode, the leakage current is zero while in quality practical diodes it is very low. The maximum surge current is a rating that can get you into trouble. The surge current typically is much larger than the forward current, so it sometimes is erroneously taken to be the operating current of the diode. It is defined as the maximum short-duration current that will not damage the diode. "Short duration" typically means 1/60-second. Don't use the surge current as if it were the forward current (a common but disastrous mistake).

The junction temperature is merely the maximum allowable temperature of the PN junction. The actual junction temperature depends upon the forward current and how well the package (and environment) rids the diode of internal heat. Although typical junction temperatures range from +125°C to +150°C, good design requires as low a temperature as possible.

One reliability guide asks us to keep the junction temperature to a maximum of +110°C.

Several years ago an itinerant "wholesale" parts company made the rounds of the shops on the East Coast offering what seemed to be tremendous deals on electronic parts. The 1,000V PIV @1A rectifiers they offered were, well, a little short of the mark. It turned out that they would not work for long in color TV sets unless the entire lead length were left uncut on the diode. That made for very sloppy-looking repairs! The problem was that the diodes were overspecified. The unscrupulous dealer needed some 1A diodes, so he made them from 500mA types by a little creative spec writing. After all, why go buy some 1A diodes when you can make them with a magic marker. Be careful of "deals."

The peak inverse voltage (PIV) is the maximum allowable reverse bias voltage that will not damage the diode. This rating usually is the limiting rating in certain power supply designs, and the least often heeded. Later in this article we will learn how to select the PIV rating for practical power supplies.

### Rectifier circuits

Figure 3 shows a solid-state rectifier diode (D1) in a simple half-wave rectifier circuit. In Figure 3A, the diode is forward biased: The positive terminal of the voltage source is connected to the anode of the rectifier. In this case, current (I) flows through the load resistance (R). In Figure 3B, we see the opposite situation. Here the negative terminal of the voltage source is applied to the anode, so the diode is reverse biased. No current flows.

The circuit of Figure 3 is called a *1/2-wave rectifier* for reasons that become apparent when examining Figure 3C. In this figure, the output current through the load (R) is graphed as a function of time when an ac sine wave is applied. From time T1 to T3 the diode is forward biased, so current flows in the load (also from T3 to T4). But during the period T2 to T3 the diode is reverse biased, so no current flows. Because the entire sine wave

takes up the period T1 to T3, only half of the input wave is used. The output waveform shown in Figure 3C is called a *1/2-wave rectified pulsating dc* wave. The "pulsating" part comes from the fact that it is not pure dc.

The *1/2-wave rectifier* is inexpensive, but wastes energy due to its use of only one-half of the input ac waveform. We increase efficiency by making use of the entire waveform in a fullwave rectifier circuit. Figure 4A shows the standard full-wave rectifier based on a special transformer that has a center-tapped secondary winding. Because the center tap (CT) is used as the 0V reference (and in most circuits is grounded), the polarities at the ends of the secondary are always opposite each other. One one-half cycle, point A, is positive with respect to the CT, while point B is negative. On the next half cycle, point A is negative and point B is positive with respect to the CT. This situation makes D1 forward biased on one half cycle, while D2 is reverse biased. Alternatively, on the next half cycle, D1 is reverse biased and D2 is forward biased.


Let's follow the circuit of Figure 4A through one complete ac cycle (times T1 through T3 in Figure 4B). On the first half cycle (T1 to T2), point A is positive, so D1 is forward biased and conducts current; D2 is reverse biased. Current I1 flows from the CT, through load R, diode D1 and back to the transformer at point A. On the alternate half cycle, current I2 flows from the CT, through load R, diode D2 and back to the transformer at point B. Now notice what happened: I1 and I2 are equal currents, generated on alternate half cycles, and they *flow in load R in the same direction*. Thus, we have unidirectional current through load R flowing on both halves of the ac sine wave. The waveform resulting from this action is shown in Figure 4B, and is called *fullwave rectified pulsating dc*.

We can eliminate the center-tapped secondary requirement by using the fullwave bridge rectifier circuit of Figure 5A. This circuit requires twice as many rectifier diodes, but allows us to use a simpler transformer. The opera-



2 year warranty

## HM 205-2

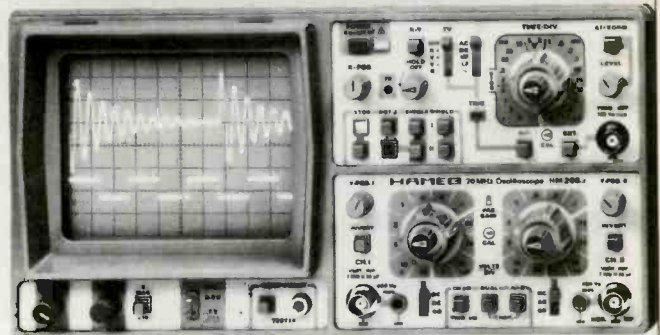


### A new Storage Oscilloscope with 5 MHz sampling rate.

This instrument offers all the outstanding features of a state-of-the-art 20MHz realtime oscilloscope. In addition, it provides digital storage capability for signals between 50s and 5μs duration. Maximum memory is 1024x8 bits for each channel. A Dot Join feature permits linear interpolation between sample points. An X-Y recorder option and an optional GPIB interface allow full integration in automatic test systems.


In many cases, the HM205-2 can easily replace considerably more expensive digital storage oscilloscopes.

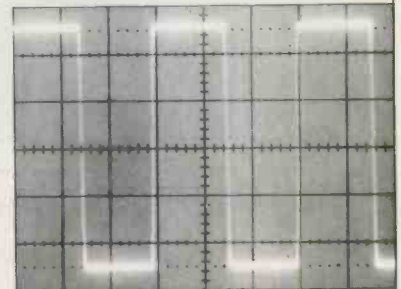**Price incl. 2 Probes 888,- \$**

Demonstration of the excellent transmission performance of the HM205-2 in analog mode with a fast risetime 1MHz square wave signal. All HAMEG Oscilloscopes are specified to have less than 1% aberrations and overshoot.



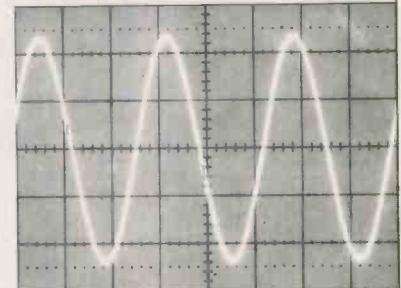This screen photo shows a 20kHz sine wave signal in storage mode. The screen resolution of 1024 x 256 points offers an outstanding display that can easily be compared to those found on analog instruments.



Write or call toll free 800 247 1241

## HAMEG, INC.

88-90 Harbor Road · Port Washington N.Y. 11050  
Phone (516) 883.3837 · TWX (023) 497.4606

Circle (9) on Reply Card

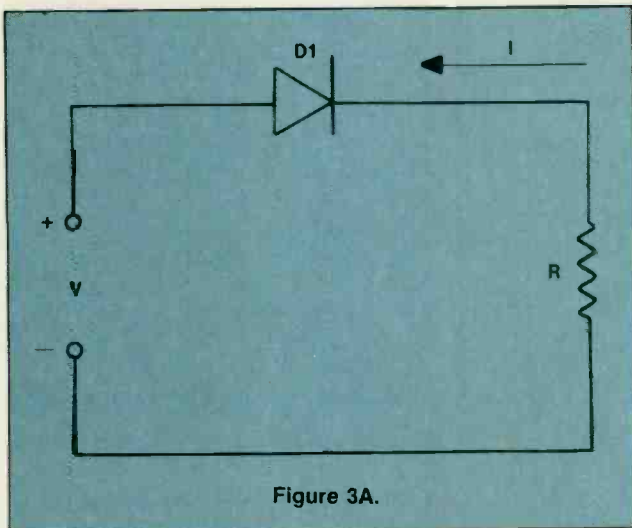


Figure 3A.

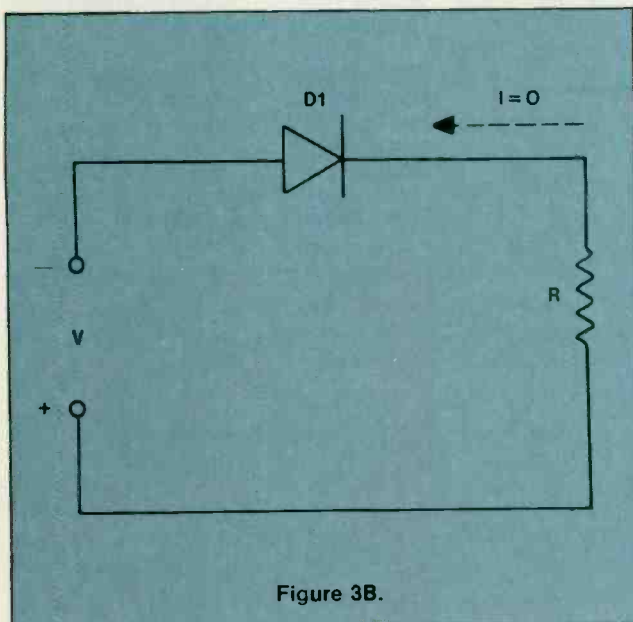


Figure 3B.

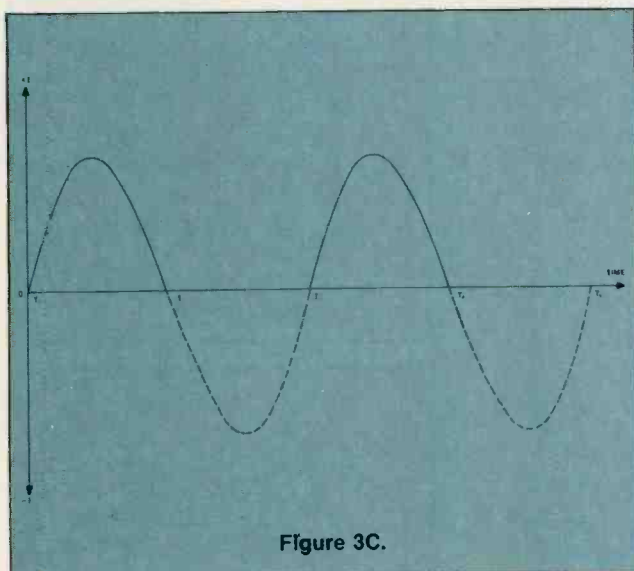


Figure 3C.

Figure 3. Connected this way, a semiconductor acts as a 1/2-wave rectifier. The output of a 1/2-wave rectifier is a pulsating dc, as shown in C.

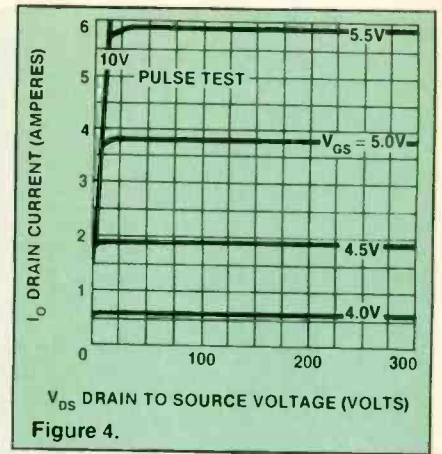
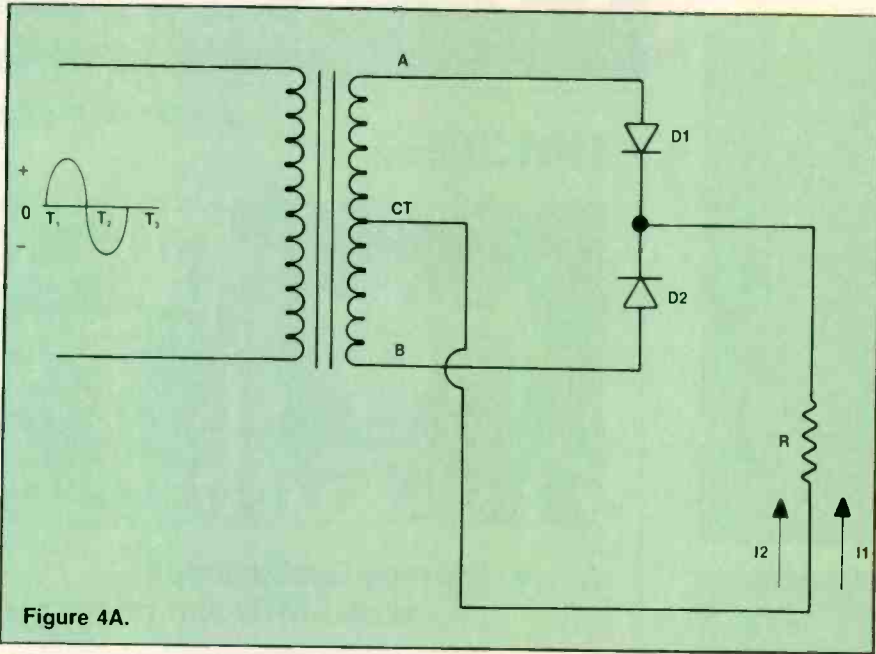


Figure 4. Using a center-tapped transformer and two diodes, you can construct a fullwave rectifier as shown here. The output is a pulsating dc, see B.



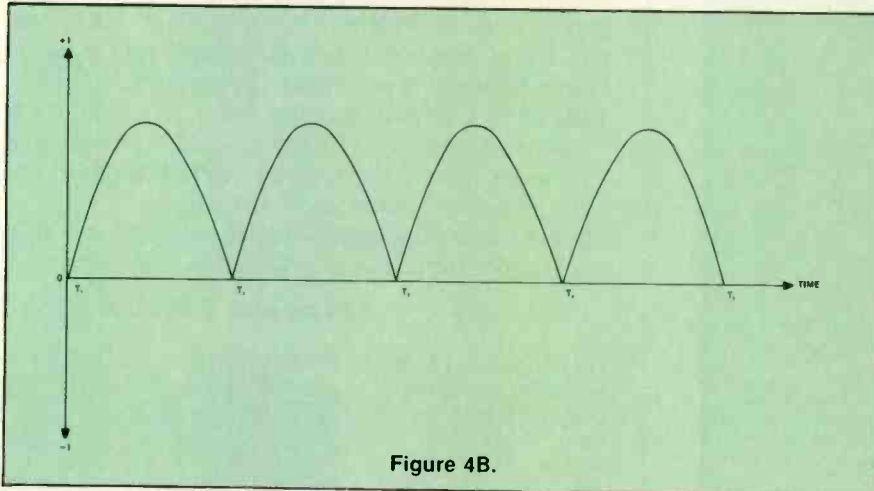
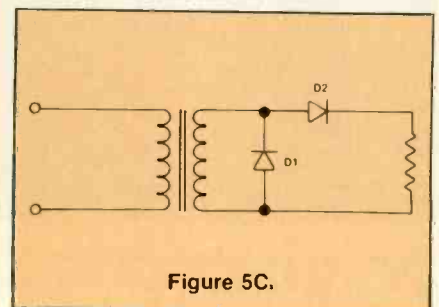


Figure 5. Another way to construct a full-wave rectifier is to connect four diodes in a bridge configuration (A). Because a bridge rectifier is such a commonly used circuit, it is available in prepackaged units (B). Another rectifier configuration is the half-bridge rectifier (C).

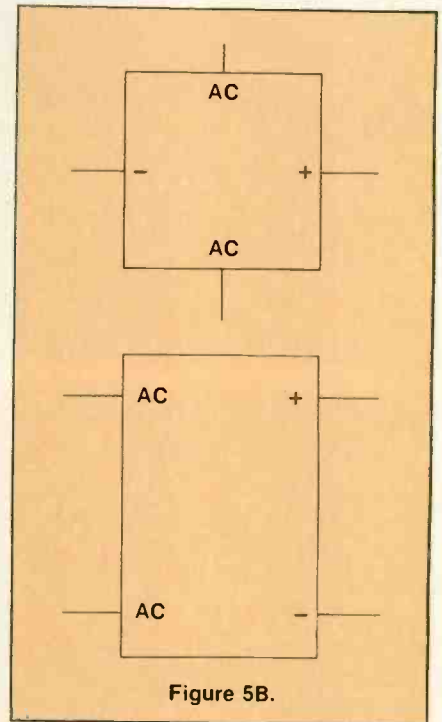

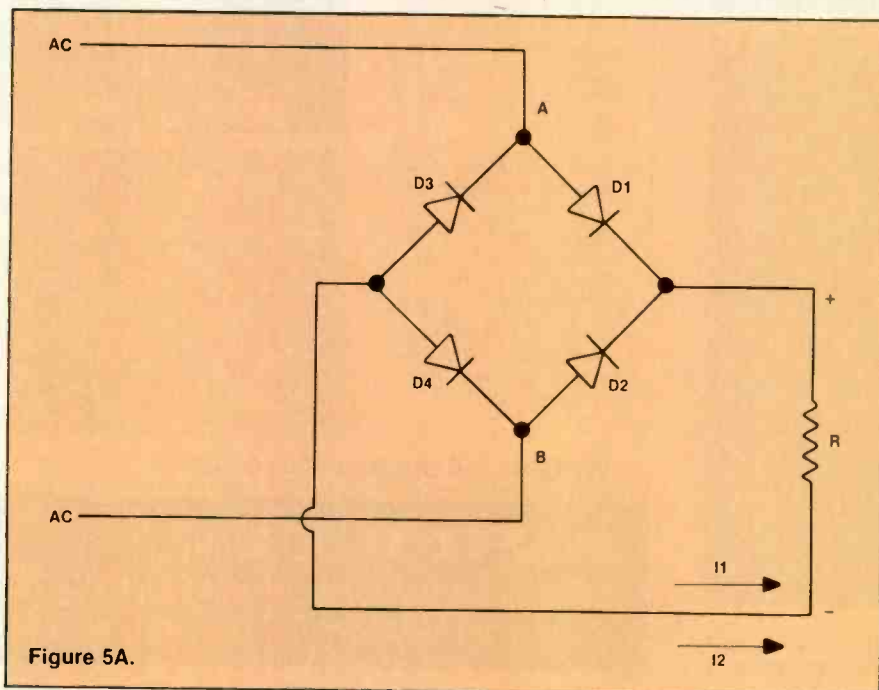

tion, however, is similar. On one half cycle, point A is positive and point B is negative. Current I2 flows from the transformer at point B, through D4, load R, diode D1 and back to the transformer at point A. On the alternate half cycle, point A is negative and point B is positive. In this case, current I2 flows from point A, through diode D3, load R (in the same direction as I1), diode D2 and back to the transformer at point B.

In some cases, you might want to build a bridge rectifier using four discrete diodes (D1 to D4). In most modern equipment, however, a bridge stack is used. These parts comprise a bridge rectifier built into a single package with four leads coming out. Figure 5B shows the two alternate circuit symbols for bridge rectifier stacks.

Figure 5C shows a half-bridge rectifier. This circuit is used more today because of the dual polarity power supplies used in a lot of equipment. Operational amplifiers and some CMOS devices typically require  $\pm 12V$  dc power supplies. We can take a fullwave bridge rectifier stack and couple it to a center-tapped transformer to make a pair of  $\frac{1}{2}$ -wave rectified dc power supplies. The CT is the common (or ground), while the bridge positive terminal supplies the positive voltage and the negative terminal supplies the negative voltage.

The pulsating dc waveform is almost as useless for electronic circuits as the ac input. However, we can filter the pulsating dc output to form nearly pure dc. Although the subject of filtering is beyond the scope of this article, we must consider at least the simplest form of power supply filter in order to correctly select a rectifier for any given application. Figure 6A shows a simple power supply with a brute-force filter capacitor (C) shunting the load to filter the pulsating dc into nearly pure dc. This capacitor will charge to a potential equal to the peak voltage, which is 1.414 times the applied rms voltage.


#### Selecting rectifier diodes

The two parameters that you will use most often to specify prac-

tical power supply diodes are the *forward current* and *peak inverse voltage*. Get these right, and in almost all cases the rectifier will work long and hard for you.

The forward current rating of the diode must be at least equal to the maximum current load the power supply must deliver. That's common sense. But in the real world there also is a necessity for a safety margin to account for toler-

ances in the diodes and variations of the real load (as opposed to the calculated load). It also is true that making the rating of the diode larger than the load current will greatly improve reliability. A good rule of thumb is to select a diode with a forward current rating of 1.5 to 2 times the calculated (or design goal) load current, or more if you can get it. Although selecting a diode with a very much

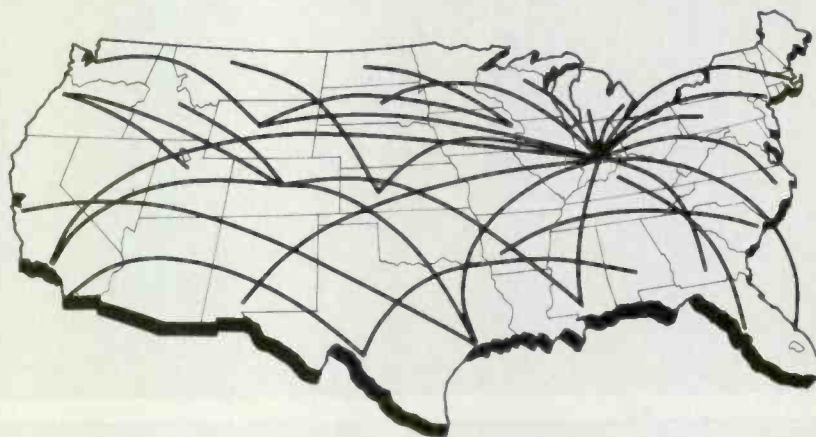

## Over 5,000 PTS modules delivered non-stop daily.

Every day over 5,000 professional technicians choose PTS. Fast turnaround. Availability.

Over a million modules a year. And every PTS module undergoes a complete 13-step rebuilding process including recommended

automatic updates and live on-air tests in an actual chassis. Every module.

Your PTS module meets or exceeds all manufacturer's specifications. You've made PTS America's Number One Independent Electronics Rebuilder.



**PTS CORPORATION**  
**PTS Rebuilds America.**

Corporate Headquarters • P.O. Box 272 • Bloomington, IN 47402 • (812) 824-9331

Arvada, CO (303) 423-7080 • Detroit, MI (313) 862-1783 • Jacksonville, FL (904) 389-9952  
Longview, TX (214) 753-4334 • Norfolk, VA (804) 853-5844 (804) 853-5847  
North Highlands, CA (916) 334-2012 • Pittsburgh, PA (412) 787-3888  
Westfield, MA (413) 562-5205 • Yeadon, PA (215) 622-0450

Circle (10) on Reply Card

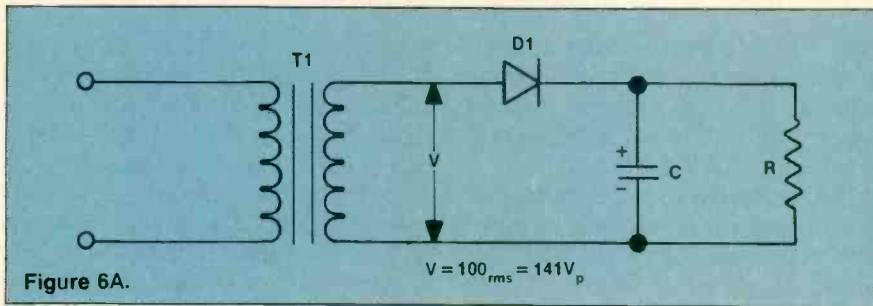


Figure 6A.

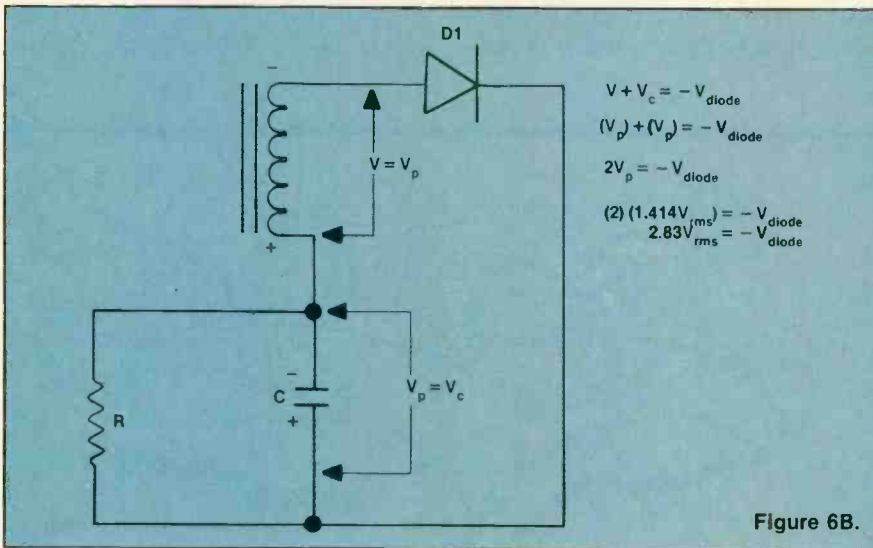


Figure 6B.

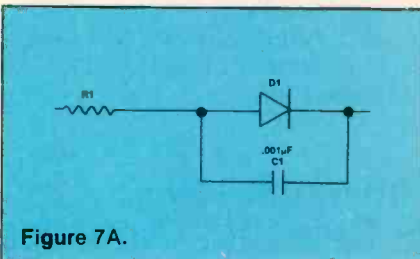
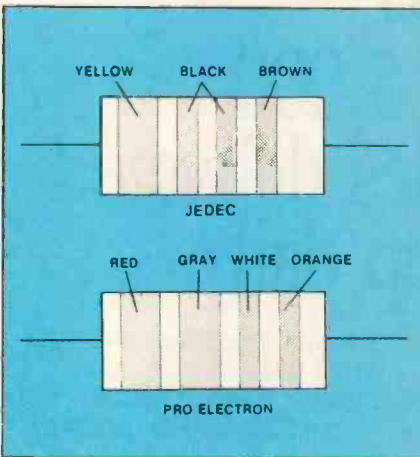


Figure 7A.

Figure 7. A resistor in series with the diode limits the forward current (A). A parallel capacitor will bypass high-voltage transient spikes around the diode that otherwise could destroy the PN junction. In B, several diodes in series increase the PIV rating. The resistors equalize the forward voltage drop across each diode.

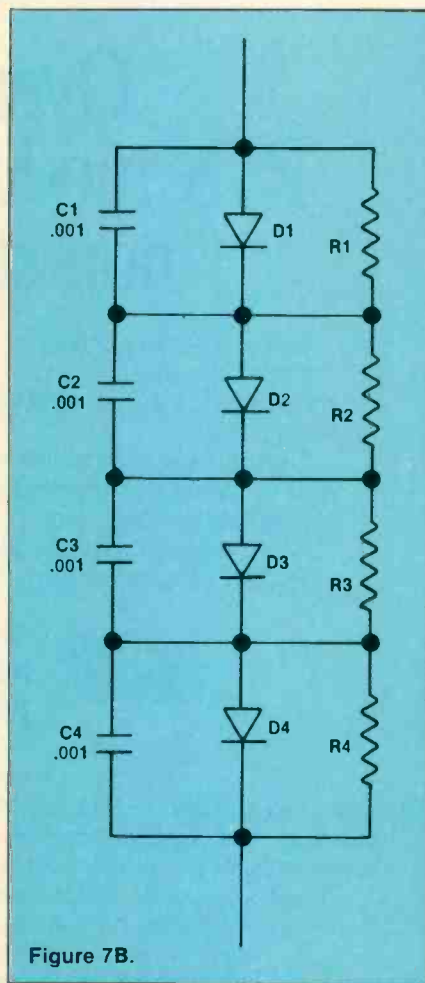


Figure 7B.

Figure 6. A capacitor is used to smooth the rectifier's dc output (A). When the capacitor voltage and the transformer voltage are additive, their sum appears across the diode (B). Thus, choose a rectifier diode with PIV rating of at least 2.83 times the applied rms voltage.

larger forward current (for example, 100A for a 1A circuit) is both wasteful and likely to make the diode not work like a diode, it is generally the rule to make the rating as high as feasible. The 1.5-to-2-times rule, however, should result in a reasonable margin of safety.

The peak inverse voltage (PIV) rating can be a little more complicated. In unfiltered, purely resistive circuits, the PIV rating need only be greater than the maximum peak applied ac voltage ( $1.414 \times \text{rms}$ ). If a 20% safety margin is desired, then make it  $1.7 \times \text{rms}$  voltage.

Most rectifiers are used in filtered circuits (Figure 6A), and that makes the problem different. Figure 6B shows the simple capacitor filtered circuit redrawn to illustrate better the circuit action. Keep in mind that capacitor C is charged to the peak voltage with the polarity shown. The voltage across the transformer secondary (V) is in series with the capacitor voltage. When voltage V is positive, the transformer voltage and capacitor voltage cancel out, making the diode reverse voltage nearly zero. But when the transformer voltage (V) is negative, the two negative voltages (V and  $V_c$ ) add up to twice the peak voltage, or approximately  $2.83 \times \text{rms}$  voltage. Therefore, the absolute minimum value of PIV rating for the diode is 2.83 times the applied rms. If you prefer a 20% safety margin (a good idea), then make the diode PIV rating  $3.4 \times \text{rms}$  (or more).

### Using rectifier diodes

In most cases, especially low-voltage power supplies needed by most electronic equipment, you can get away with using the diodes as shown in the circuits above. In Figure 7A, however, note the so-called proper way to use the solid-state diode rectifier. The resistor in series with diode D1 (R1) is used to limit the forward current. Many circuits, especially those with



capacitor-input filter circuits, exhibit a surge current at initial turn-on. This current sometimes can pop the diode, so R1 is used to limit the possible damage. The value of resistance used for R1 is typically  $5\Omega$  to  $20\Omega$ . In most cases, however, you can eliminate R1 by using a diode with a rating larger than the load current (for example, the two-times rule).

Capacitor C1 in figure 7A is used to bypass high voltage transient spikes around the diode. These spikes possibly could blow the diode PN junction. In fact, high voltage line spikes make diodes pop with disgusting routine. Placing the capacitor in parallel with the diode will eliminate much of that problem. The working voltage (WVdc) of the capacitor should be equal to or greater than the PIV rating of the diode.

By use of 1,000V PIV diodes even in low-voltage circuits, you can eliminate much of the damage caused by transients, therefore, you would not need the capacitors. You also can eliminate the capacitors if a metal-oxide varistor (MOV) spike suppressor is used across the ac supply voltage.

Figure 7B shows the method for using several diodes in series to increase the PIV rating. Assuming that the PIV ratings of the diodes are equal, then the overall rating is four times the rating of one diode. In general, we use 1,000V PIV diodes in these circuits, so for the

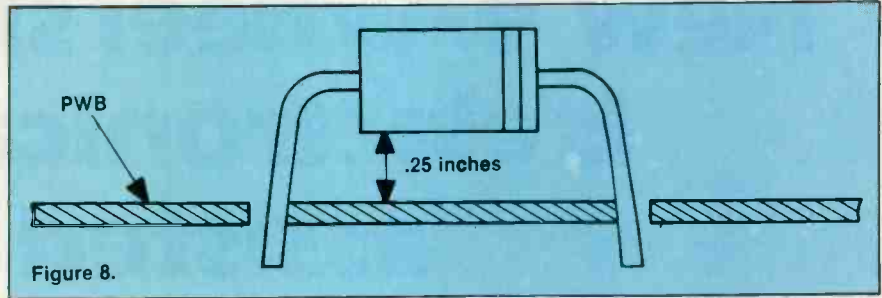


Figure 8. Mounting a diode a fraction of an inch above the circuit board allows air to circulate, keeping the diode cooler to protect the board from diode heat.

circuit shown the PIV rating is 4,000V.

The capacitors used in Figure 7B are for exactly the same purpose as in Figure 7A. The resistors, however, are needed for a different purpose. They equalize the forward voltage drop across each diode. A  $470\Omega$  1W resistor typically is used for 1,000V PIV diodes. The wattage rating is required not because of the power dissipation of the resistors, but for the voltage rating (yes, resistors *do* have voltage ratings).

Figure 8 shows the proper method for mounting an axial lead rectifier on a perfboard or printed circuit board. This method is used anytime except where excessive vibration is expected, which includes most stationary projects or equipment. The space beneath the diode body allows air to circulate (keeping the diode cooler) and prevents diode heat from damaging the board.

Older equipment that comes in for repair often uses hard-to-get or expensive vacuum-tube rectifiers. We can use solid-state diodes to replace these tubes in almost all cases. For smaller rectifiers, we need only wire the solid-state diode across the pins of the rectifier tube socket. In other cases we need to use an external perf-board or other tactic to mount the diodes. Such cases include those with multiple diode rectifiers such as Figure 7B.

### Conclusion

Although solid-state rectifiers are among the most common electronic components used by technicians, they also are among the most common causes of failure in electronic projects or repaired equipment. By following the rules given above, you will successfully select the correct rectifier, and prevent reliability problems.

**ES&T**

## TENTEL® MAKES IT EASY TO DIAGNOSE VCR MECHANICS

<p>Award winning Tentelometer tape tension gauge for proper interchange and tape handling. One gauge for Beta, VHS and U-Matic.</p> <p><b>T2-H7-UM \$295</b></p>	<p>Head protrusion and eccentricity gauge to determine the amount of wear remaining on the VCR heads; safe, easy, measures in microns.</p> <p><b>HPG-1 \$479</b></p>	
<p>Torque gauge NEW from Tentel to save you money—Universal and accurate for Beta and VHS—0 to 600 gm cm. Take-up, FF and Rew torques.</p> <p><b>TQ600 \$139</b></p>	<p>Spindle height and elevator latch and alignment gauge to diagnose cassette binding and edge damage problems. Finds problems not detected by any other method.</p> <p><b>TSH-V4 \$395</b></p>	

Tentel manufactures a complete line of gauges for U-matic, 1" Type "C", Betacam and other recorders, too. If you've suffered the frustration of having a master tape ruined, or if you are responsible for maintaining and repairing VCRs— There's no faster, easier method to test the various mechanics that make VCRs work properly. Call our technical engineering dept. for details—ask about the combo discount for all 4 gauges. We've been helping customers for years and want to help you too—your satisfaction is guaranteed.

**TENTEL® CORP.** 1506 Dell Ave.  
Campbell, CA 95008

(408) 379-1881  
800 538-6894 (Not in CA)

Circle (11) on Reply Card

# New 4-wheel steering is electronically assisted

The growth of electronics in all areas of consumer products has been accompanied by a great deal of fanfare. Few people are unaware of such developments as microwave ovens, compact disc players, satellite TV. The electronics revolution in automobiles has been far more subtle: electronic innovations such as trip computers, computerized fuel injection, etc., have been introduced into cars somewhat quietly.

A recently introduced electronic

automotive refinement is 4-wheel steering.


Mazda Motor Corporation has presented an active 4-wheel-steering (4WS) system as an option on selected passenger car models.

The system will be available beginning this summer in the Japanese domestic market, and later this year in the United States. It will be a highlight of Mazda's international size passenger car.


Four-wheel steering utilizes all

four wheels to steer the vehicle when it is being turned. The system is unique because of its speed-sensing capability; the direction and amount of the rear wheel steering angle during cornering is determined not only by the driver's input to the steering wheel, but also by electronic controls that measure and respond to the vehicle's speed.

The driver's input to the steering wheel is mechanically transmitted by the rotation of a shaft that con-

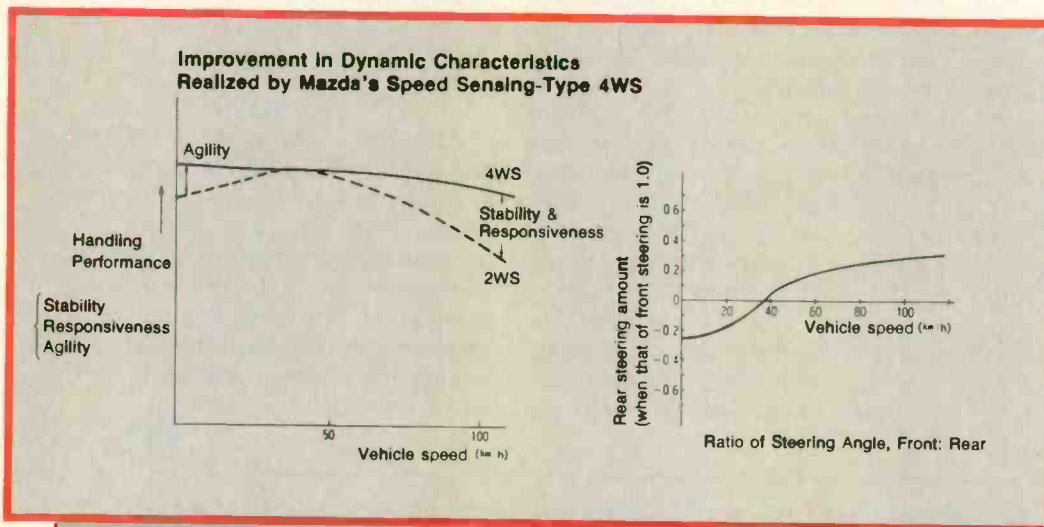

**Figure 1.** With 2-wheel steering system, vehicle handling may become less stable and responsive as driving speed increases. Change in vehicle characteristics at varying speeds is small with 4-wheel steering system.

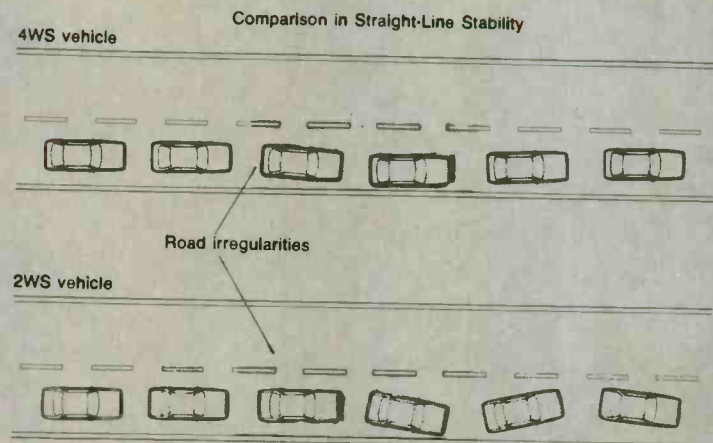




# Advantages of 4-wheel steering system

Some major advantages of the system are:

- **Cornering Capability**  
The vehicle's cornering behavior is more stable and controllable at high speeds and slippery roads.
- **Steering Response**  
The vehicle's response to steering input becomes quicker and more precise throughout the vehicle's entire speed range.
- **Straight-Line Stability**  
The vehicle's straight-line stability at high speeds is improved; negative effects of road irregularities and crosswinds on its stability are minimized.

- **Lane Changing**  
Stability in lane changing at high speeds is improved. High-speed slalom-type operations become easier, and the vehicle becomes less likely to go into a spin even in situations when the driver must make a sudden change of direction.
- **Low-Speed Maneuverability**  
By steering the rear wheels in the direction opposite of the front wheels at low speeds, the vehicle's turning circle is greatly reduced. Making it easier to maneuver on narrow roads and during parking.

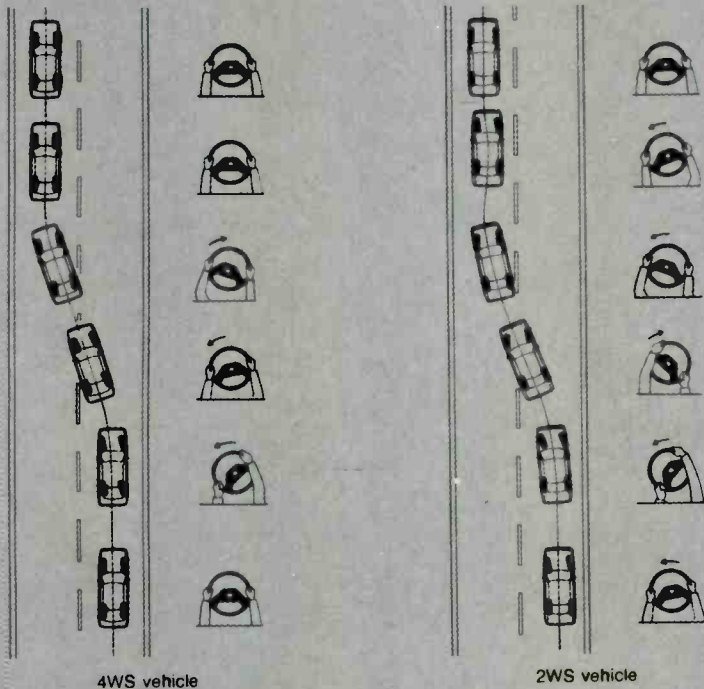Comparison in Stability during Lane-Changing



4WS vehicle


2WS vehicle
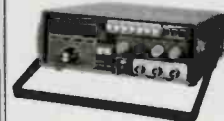
## ELENCO PRODUCTS AT DISCOUNT PRICES!



**20 MHz Dual Trace Oscilloscope**  
**\$359.95** MO-1251

Two 1x, 10x 100 MHz probes, diagrams and manual included. Write for specs.  
**35 MHz \$499.95 MO-1252**



**GF-8016 Function Generator**  
with freq. counter


**\$239.95**

Sine, Square, Triangle  
Pulse, Ramp, 2 to 2 MHz  
Frequency .1 thru 10 MHz

**GF-8015 without freq. meter \$179**

**Triple Power Supply XP-660**


0-20V @ 1A  
0-20V @ 1A  
5V @ 5A

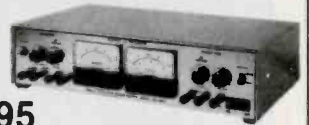

**\$159.95**

Fully regulated, short circuit protected  
with 2 limit cont. 3 separate supplies

**3 Amp Power Supply XP-650**

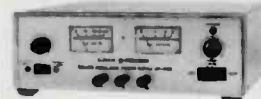

0-40V @ 1.5A  
0-20V @ 3A

**\$129.95**

Fully regulated, short circuit protected  
current limit control

**Color Convergence Generator**



**SG-200**  
**\$69.95**

Finest in the industry  
10 rock steady patterns

**Multimeter with Capacitance  
and Transistor Tester**

**Model CM-1500A**  
with case  
**\$64.95**

Reads volts, ohms, current,  
capacitors, transistors, diodes



**Digital LCR Meter** **\$148.95**



**Model LC-1800**  
Measures: Inductors  
Capacitors, Resistors  
Inductors .1uH to 200H  
Capacitor .1Pf to 200uF  
Resistor .01 Ohms to 20M Ohms  
Ranges 6 Ind, 7 cap, 7 res

C&S Sales, 8744 W North Ter.  
Niles, IL 60648 800-292-7711  
312-459-9040 ASK FOR CATALOG  
Add 5% P&H (\$10 Max per item)  
IL Res., add 7% sales tax



Circle (12) on Reply Card

nects the front and rear steering systems. The rear steering system incorporates a mechanism to transform the steering input and an electronic system to control it.

During cornering at speeds of more than 22 mph, the rear wheels are steered in the same direction as the front wheels to provide improved handling and stability compared with conventional 2-wheel-steering vehicles. When maneuvering at speeds lower than 22 mph—such as when parking the


vehicle—the system steers the rear wheels in the direction opposite from the front wheels.

The electronic system with sensors regulates the steering ratio between the front and rear wheels according to the vehicle's speed to optimize the vehicle's dynamic characteristics at any speed.

This advanced 4WS system facilitates vehicle handling at high speed and, it is said, helps to reduce driver fatigue in sustained driving at highway speeds. **ES&T**




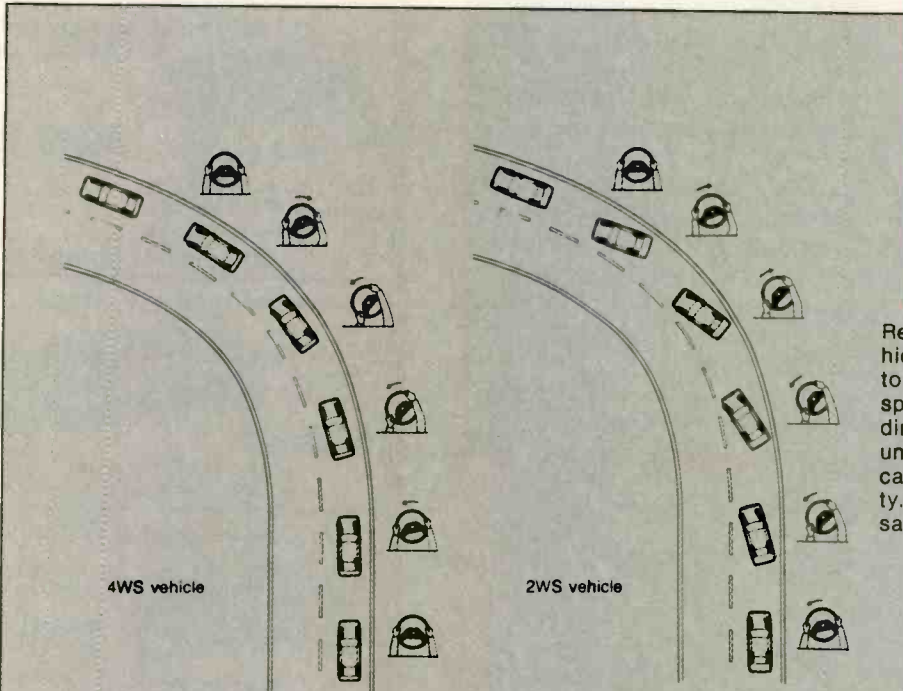Rear wheels on 4-wheel steering vehicles can turn right or left, responding to both driver's steering and vehicle speed: a maximum of 5° in the opposite direction of the front wheels at speeds under 22 mph, as when parking, significantly increasing vehicle maneuverability. Above 22 mph, rear wheels turn in same direction as front wheels.




Comparison in Vehicle Behavior During Cornering

**Reduced Turning Circle with 4WS**

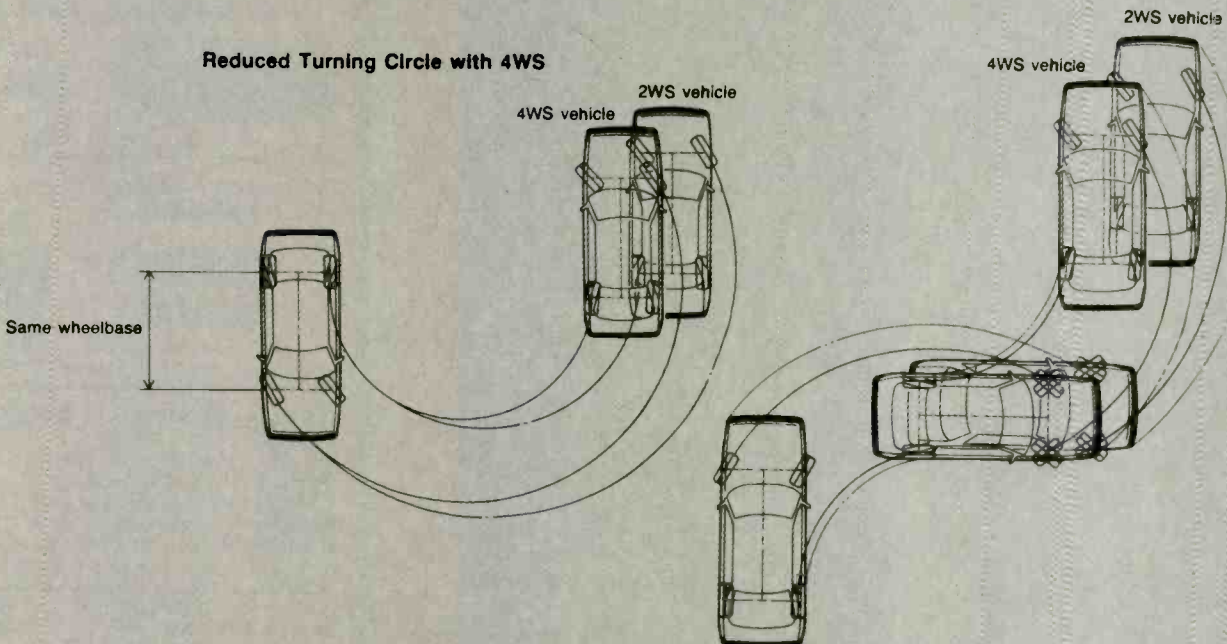



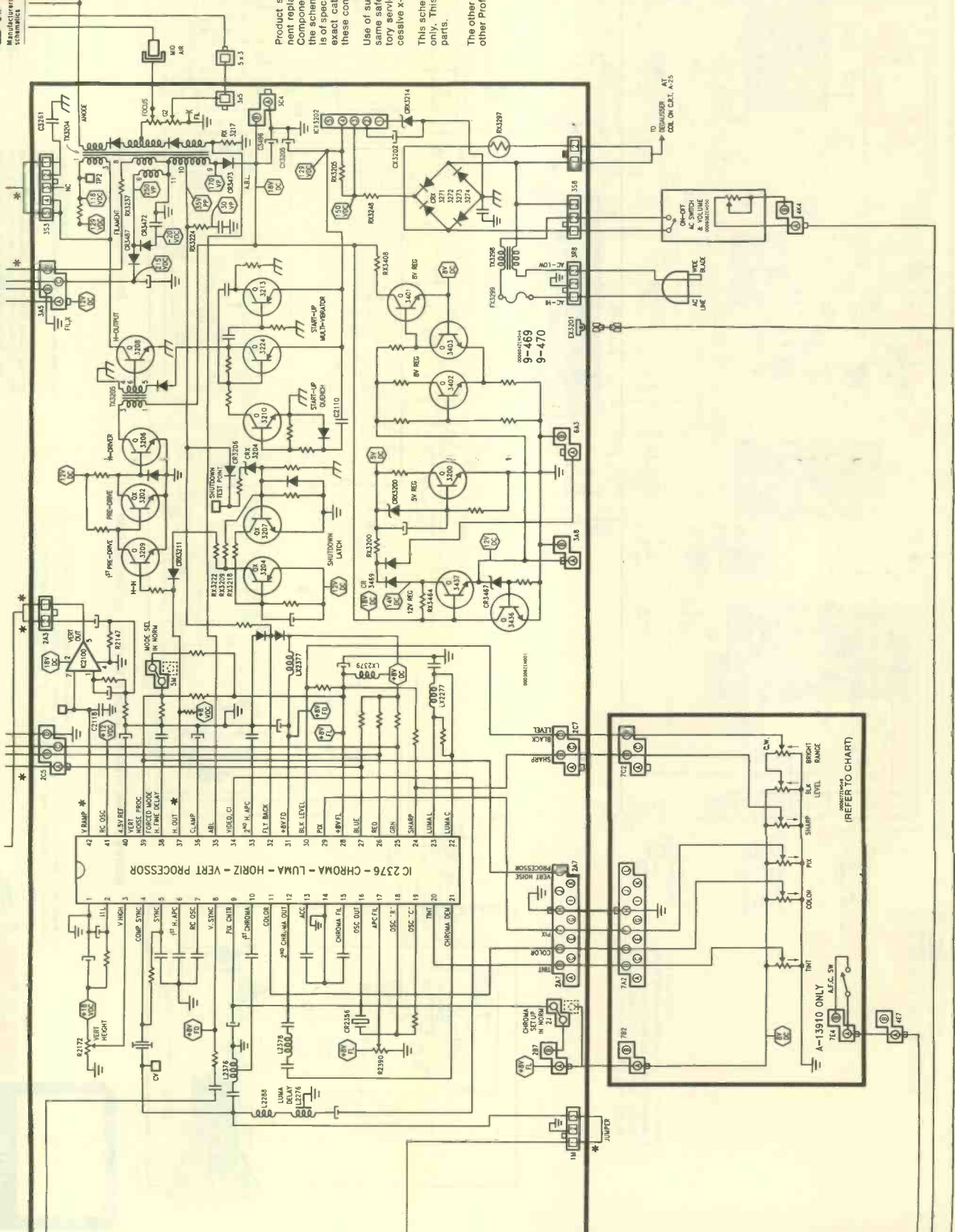

Product safety should be considered when component replacement is made in any area of a receiver. Components marked with a  $\Delta$  and shaded areas of the schematic diagram designate sites where safety is of special significance. It is recommended that only exact cataloged parts be used for replacement of these components.

Use of substitute replacement parts do not have the same safety characteristics as recommended in factory service information may create shock, fire, excessive X-radiation or other hazards.

This schematic is for the use of qualified technicians only. This instrument contains no user-serviceable parts.

The other portions of this schematic may be found on other Profax pages.

### SYSTEM SCHEMATIC

A system schematic is a hybrid troubleshooting aid consisting of a functional block diagram and simplified module schematics. It provides an overview for tracing major circuits and includes these features: key voltages, the makeup of individual cables, all connections between modules and assemblies, major components and the main lines of interaction related to these components.

The intention of the system schematic is to provide sufficient information to analyze the TV as a system for determining which major component is faulty. For complete module and assembly schematics, refer to the appropriate service manual.

Profax schematics are for the use of qualified technicians only.


VIDEO SIGNAL LOOP

AUDIO SIGNAL LOOP

Use of substitute replacement parts do not have the same safety characteristics as recommended in factory service information may create shock, fire, explosive radiation or other hazards. The other portions of the schematic may be found on other Profax pages.

Product safety should be considered when component replacement is made in any area of a television set. Components marked with the triangle symbol in the schematic diagram are safety critical components. It is recommended that only exact cataloged parts be used for replacement of these components.

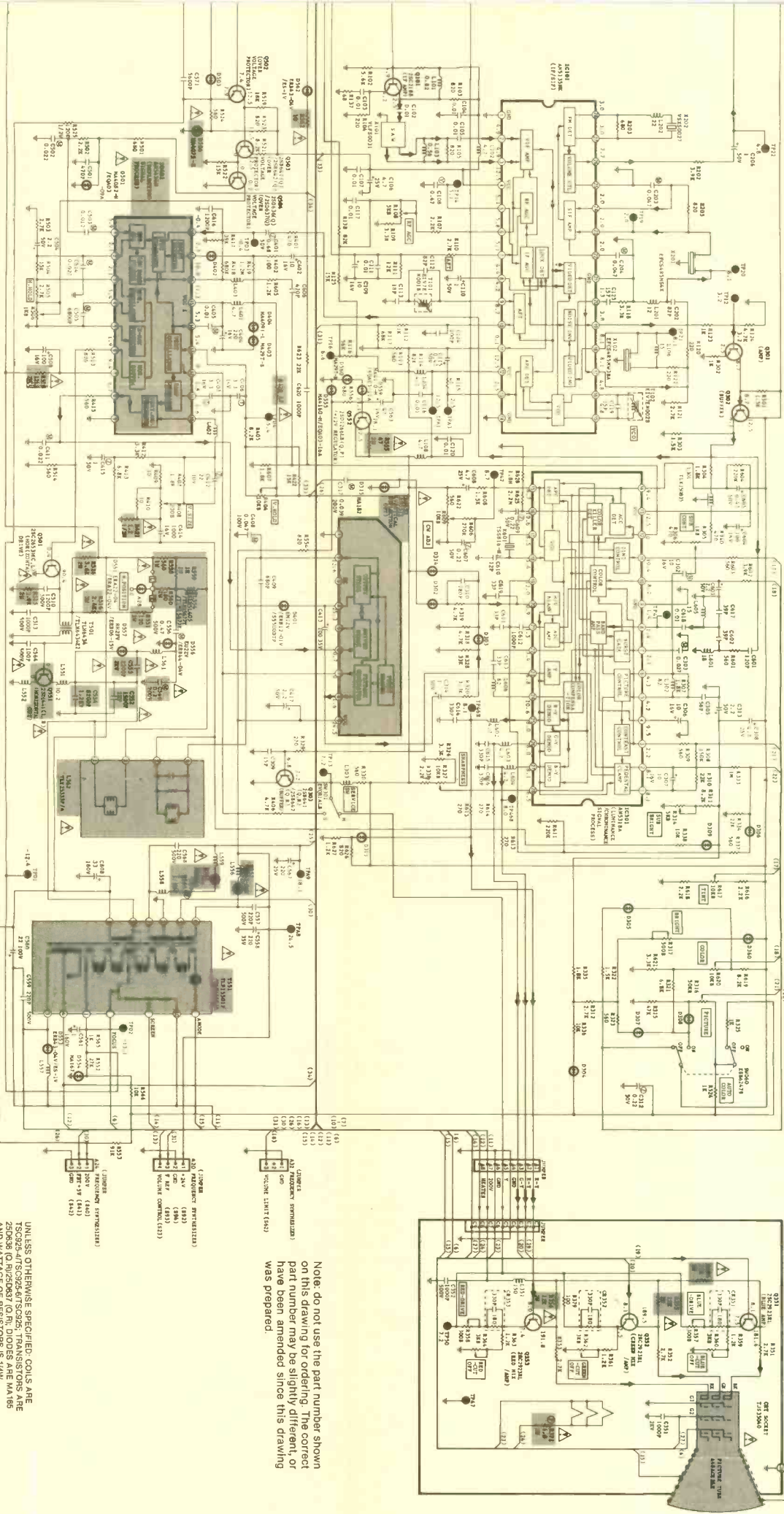MAIN SCHEMATIC DIAGRAM MK-1 Chassis (model 8-1938)




Note: do not use the part number shown on this drawing for ordering. The correct part number may be slightly different, or have been amended since this drawing was prepared.

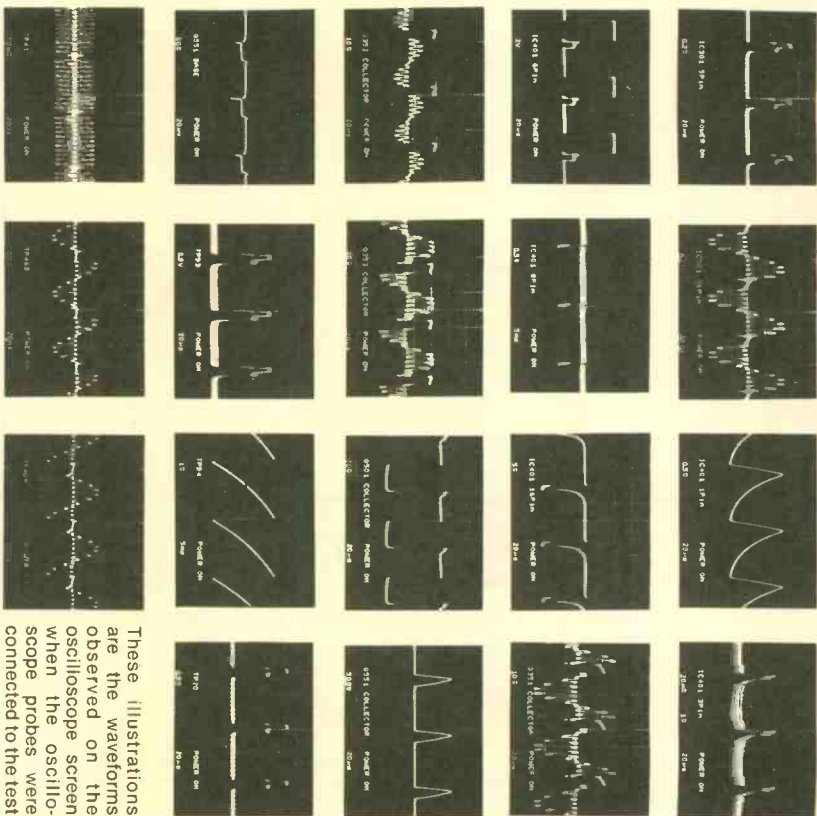- 1.00000 250V RESISTOR (PRE-TERMINALIZED)
- 1.00000 1/2W 100K (182)
- 1.00000 1/2W 100K (183)
- 1.00000 1/2W 100K (184)
- 1.00000 1/2W 100K (185)
- 1.00000 1/2W 100K (186)
- 1.00000 1/2W 100K (187)
- 1.00000 1/2W 100K (188)
- 1.00000 1/2W 100K (189)
- 1.00000 1/2W 100K (190)
- 1.00000 1/2W 100K (191)
- 1.00000 1/2W 100K (192)
- 1.00000 1/2W 100K (193)
- 1.00000 1/2W 100K (194)
- 1.00000 1/2W 100K (195)
- 1.00000 1/2W 100K (196)
- 1.00000 1/2W 100K (197)
- 1.00000 1/2W 100K (198)
- 1.00000 1/2W 100K (199)
- 1.00000 1/2W 100K (200)
- 1.00000 1/2W 100K (201)
- 1.00000 1/2W 100K (202)
- 1.00000 1/2W 100K (203)
- 1.00000 1/2W 100K (204)
- 1.00000 1/2W 100K (205)
- 1.00000 1/2W 100K (206)
- 1.00000 1/2W 100K (207)
- 1.00000 1/2W 100K (208)
- 1.00000 1/2W 100K (209)
- 1.00000 1/2W 100K (210)
- 1.00000 1/2W 100K (211)
- 1.00000 1/2W 100K (212)
- 1.00000 1/2W 100K (213)
- 1.00000 1/2W 100K (214)
- 1.00000 1/2W 100K (215)
- 1.00000 1/2W 100K (216)
- 1.00000 1/2W 100K (217)
- 1.00000 1/2W 100K (218)
- 1.00000 1/2W 100K (219)
- 1.00000 1/2W 100K (220)
- 1.00000 1/2W 100K (221)
- 1.00000 1/2W 100K (222)
- 1.00000 1/2W 100K (223)
- 1.00000 1/2W 100K (224)
- 1.00000 1/2W 100K (225)
- 1.00000 1/2W 100K (226)
- 1.00000 1/2W 100K (227)
- 1.00000 1/2W 100K (228)
- 1.00000 1/2W 100K (229)
- 1.00000 1/2W 100K (230)
- 1.00000 1/2W 100K (231)
- 1.00000 1/2W 100K (232)
- 1.00000 1/2W 100K (233)
- 1.00000 1/2W 100K (234)
- 1.00000 1/2W 100K (235)
- 1.00000 1/2W 100K (236)
- 1.00000 1/2W 100K (237)
- 1.00000 1/2W 100K (238)
- 1.00000 1/2W 100K (239)
- 1.00000 1/2W 100K (240)
- 1.00000 1/2W 100K (241)
- 1.00000 1/2W 100K (242)
- 1.00000 1/2W 100K (243)
- 1.00000 1/2W 100K (244)
- 1.00000 1/2W 100K (245)
- 1.00000 1/2W 100K (246)
- 1.00000 1/2W 100K (247)
- 1.00000 1/2W 100K (248)
- 1.00000 1/2W 100K (249)
- 1.00000 1/2W 100K (250)

UNLESS OTHERWISE SPECIFIED, COILS ARE TOKO; CAPACITORS ARE SONY; TRANSISTORS ARE 250696 (Q1) 250697 (Q2 R); DIODES ARE MA 165 AND WATTAGE OF RESISTORS IS 1/4W







These illustrations are the waveforms observed on the oscilloscope screen when the oscilloscope probes were connected to the test points on the signal circuit board corresponding to the numbers on the schematic diagram.

**ESST**  
Manufacturers Schematics  
**PROFAX**

JULY 1987


Zenith  
Color TV, chassis D13085/D1910B  
GE

Schematic  
3007  
Color TV, chassis MK-1.....3008

Product safety should be considered when component replacement is made in any area of a receiver. Components marked with a  $\Delta$  and shaded areas of the schematic diagram designate sites where safety is of special significance. It is recommended that only exact cataloged parts be used for replacement of these components.

Use of substitute replacement parts do not have the same safety characteristics as recommended in factory service information may create shock, fire, excessive x-radiation or other hazards.

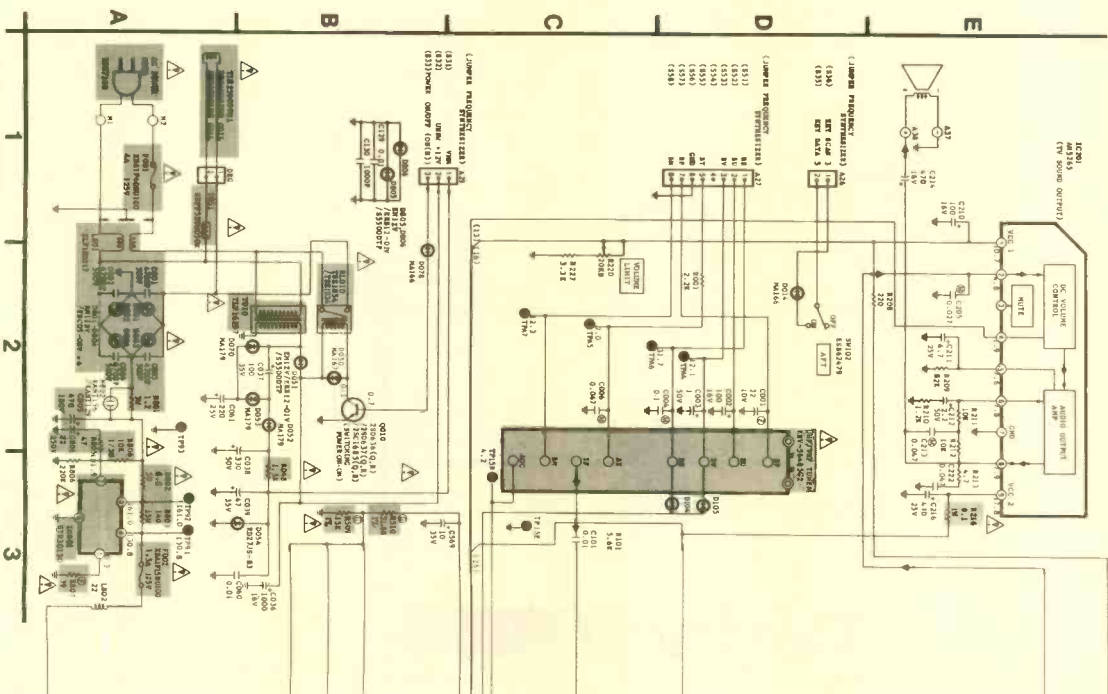The other portions of this schematic may be found on other Profax pages.





# TROUBLESHOOTING

## low-voltage regulators

By Homer L. Davidson

Symptoms of intermittent operation, HV shutdown, horizontal picture pulling, hum bars, insufficient width or height, weak locking, poor color and noisy sound might be caused by defects in the low-voltage regulator, and *not* in the horizontal deflection, vertical deflection, sync clipper or one of the other circuits that is *usually* the source of these problems. This can be very confusing. The conditions of power-supply voltages are easy to overlook during the initial stages of troubleshooting, but they are vitally important and *must be tested*.

Some important duties of the low-voltage regulator circuits are to regulate or stabilize the dc voltages applied to several stages or circuits of a TV receiver. And most important of these is the horizontal-output stage. If the horizon-

tal-output transistor's supply voltage is permitted to rise as much as 10V, the dc high voltage might increase by several-thousand volts, causing arcs, or activating the HV shutdown circuit that stops all picture and sound.

Of course, lower voltage at the output transistor's collector produces a smaller picture or a black screen without high voltage. Other symptoms and repairs will be described in the case histories.

### Basic voltages and resistances

Some tests never change: The basic voltage and resistance measurements are two of them. Other essentials are in-circuit and out-of-circuit transistor tests.

The newer low-voltage regulator circuits (Figure 1) feature more integrated circuits (ICs), which can be tested in-circuit only for shorts and leakage. If you are certain a transistor or diode junction is inside the IC and connected between two pins, it can be tested with the diode voltage-drop test featured by some digital multimeters (DMMs).

Test the dc voltage at each terminal of the IC and (with power off) check the resistance from pin to ground of all terminals that had voltage (or should have had voltage according to the schematic). A low resistance reading might be caused by leakage in another component connected to the same terminal. Disconnect any paralleling capacitors, zeners or resistors while testing the IC pin's resistance to ground.

All of the regulators discussed in this article have the same basic principle. A large power transistor is used as a variable series resistance between raw B+ and regulated B+. The resistance and conductivity of this power transistor is adjusted automatically by a control circuit that varies the transistor bias as needed to maintain a specific regulated output dc-voltage supply. Most of the models provide an adjustable control that can be rotated to obtain the desired output voltage. And then the circuit holds that voltage over a wide range of output current.

In addition, most regulators of this type have one or two large resistors that are connected in parallel with the collector and emitter of the power transistor. When the power transistor is biased to cut-off, these resistors continue to pass current, providing a minimum output voltage. The total power load (and its heat) is divided among three components (transistor and two resistors) in three locations, so elaborate heat sinks are unnecessary.



One of the first tests during low-voltage regulator troubleshooting is to remove the horizontal-output transistor and compare the collector voltage with and without the transistor connected.

Power ICs, such as IC 901, have a high rate of failure. Also, an ohmmeter test is not sufficient. Sometimes the IC regulator breaks down under load, therefore, it must be replaced to actually locate the defective component.

### No sound and no picture

Perhaps the first step should be measuring the dc voltage at the horizontal output transistor's collector (case) to determine if the low-voltage power supply is working. Very low voltage might indicate a defective output transistor or regulator. Remove the horizontal-output transistor (or the fuse for that stage) and notice what the dc voltage does. A higher voltage indicates a defect in the horizontal-deflection circuit, such as a shorted output transistor. Therefore, the attention should be directed there.

A low or no voltage at the collector might point to a defective regulator or low-voltage power supply. Rotate the B+ control and notice if the output voltage changes. If the B+ adjustment control has no effect on the B+ dc voltage, the regulator or power supply definitely is defective. Remove the horizontal-output transistor or the B+ fuse that supplies it and proceed to repair the regulator circuit first, using dc voltage and resistance

methods. Diodes are prone to failure in regulator circuits.

An open principal filter capacitor can cause low voltage both into and out of the regulator. Check the individual diodes of the bridge, if the voltage is slightly low and has 60Hz hum that is difficult to filter. (Ripple from a true bridge should have a 120Hz frequency.)

Check the power-supply/regulator area visually looking for burned resistors, loose connections on the board or any other obvious signs.

In a Sharp SKC-1310A portable (Photofact 1851-2), I found fuse 4A F701 open and only +18V applied to the Q602 horizontal-output transistor. This voltage increased very little when the transistor was removed from the circuit, thus indicating power-supply/regulator problems.

Regulator transistor Q701 and diode D751 were tested in-circuit and appeared to be normal. I removed one end of D751 from the circuit and tested it for leakage. The diode was not leaky (Figure 2). At first, regulator Q701 was suspected of breaking down under load, but with the output transistor removed, the voltage remained too low. The principal (and only) filter capacitor (C705) was paralleled by a known-good capacitor with no improvement.

Finally, zener diode ZD751 was

tested in-circuit and registered leakage. But when it was removed from the board, it was open in both directions and without leakage. Evidently, the zener had developed a *hot spot* in it that fragmented part of the solid-state element. I have seen the phenomenon of a traveling short, high leakage or open circuit before with power transistors and SCRs, but this was a first for zeners. The defective zener was reducing the Q701 base voltage.

Installation of a new 55V zener diode for ZD751 and minor adjustments brought normal operation with a full +120V from the regulator.

### Fuse blows repeatedly

Although it is possible for a shorted component in the regulator circuit to repeatedly blow a fuse or trip a circuit breaker, the low-voltage circuits cause most fuse problems. If the B+ fuse continues to blow, remove the horizontal-output transistor to find if that stops the overload. If it does, the transistor probably is defective or has a very heavy collector load.

When the power-line fuse will not hold, check for a leaky or shorted diode rectifier perhaps in the bridge circuit where one or two diodes might be leaky. I use the DMM's diode test to check for such leakage. Some technicians prefer the high range of a VOM.

The overload often burns open a large high-wattage, current-limiting resistor that supplies the bridge. Of course, this must be replaced. And then the chassis must be handled safely during tests. There are two general ways of doing this (both have been discussed before). One is to connect a 100W incandescent light bulb in place of the fuse in the incoming ac line. The bulb resistance limits the amount of current that the TV can draw, while the bulb's brightness indicates approximately the amount of current. The other method is to use a variable-voltage transformer for the ac power. Operation with low voltage to prevent component failures during tests is an excellent procedure that has been described in detail in


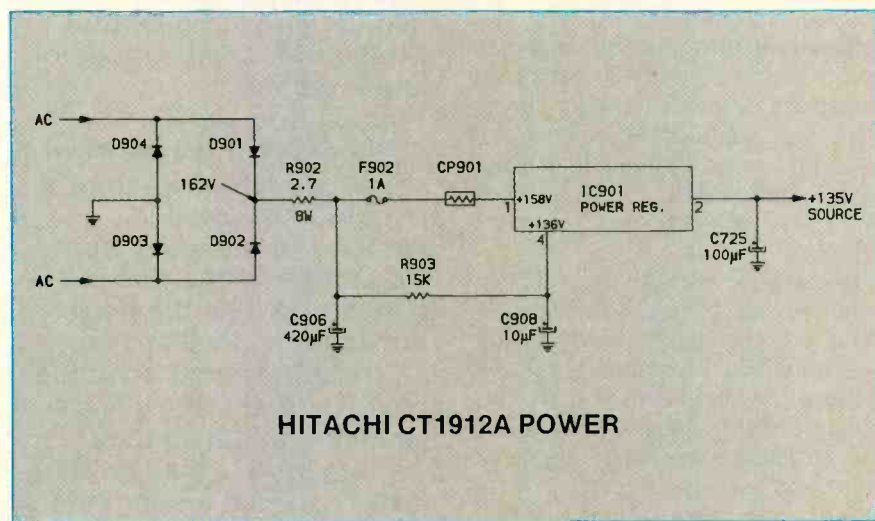



Figure 1. In the Hitachi CT1912A receiver (Photofact 2200-1), the functions of several transistors (including one power type) have been packed into one IC901 integrated circuit. Also, there is no adjustment control for the output voltage. The circuit is much more simple than the ones using discrete components.

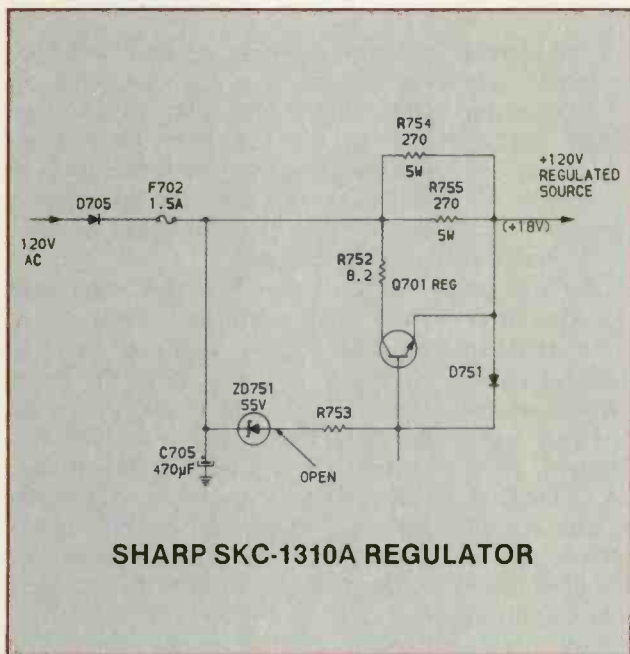



**SHARP SKC-1310A REGULATOR**

**Figure 2.** A leaky ZD751 zener diode produced a dead chassis in one Sharp SKC1310A color receiver. Only +18V were measured at the collector of the horizontal-output transistor, at the beginning. After the transistor was removed, the voltage increased a volt or so; nothing significant. Resistance tests finally determined that zener ZD751 was open. (In later tests it was shorted and in others it showed leakage. Obviously damaged by heat.)

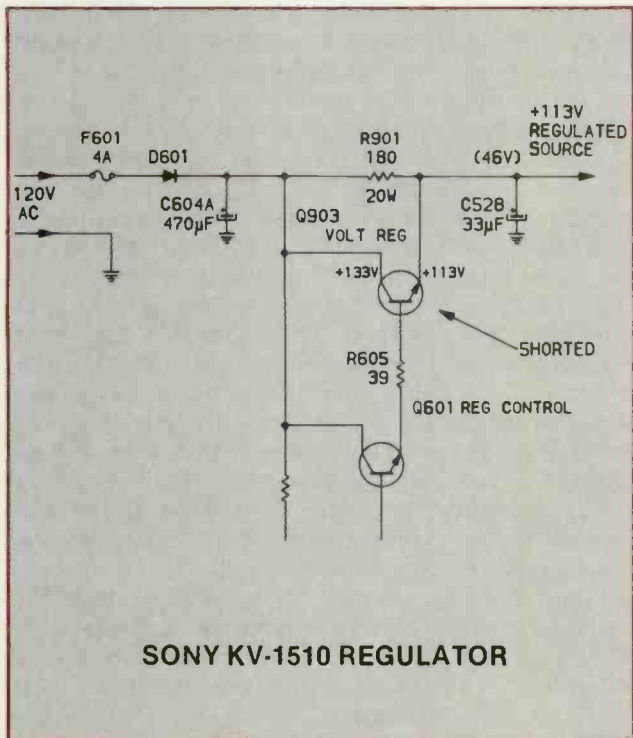

**SONY KV-1510 REGULATOR**

**Figure 3.** A shorted Q903 voltage-regulator transistor in a Sony KV-1510 (Photofact 1322-2) produced hum bars. The first clue to this was the +146V at the collector of the Q903 voltage regulator where the voltage should have been +113V. In fact, the base, emitter and collector each measured +146V, obviously from internal leakage.

# See what MCM has for you.



## Are these the things you're looking for in a catalog?

- Quality
- Wide selection
- Hard-to-find items
- Low prices
- Easy ordering
- Quick shipments

Isn't it nice to know you can find them all in one place! The latest edition of the MCM Catalog will put an end to your search.

**TOLL-FREE 1-800-543-4330**

In Ohio 1-800-762-4315

In Hawaii or Alaska 1-800-858-1849

The new MCM Catalog is yours FREE with no obligation to buy. Call today and see what MCM has for you!




**MCM ELECTRONICS**

858 E. CONGRESS PARK DR.  
CENTERVILLE, OH 45459

A PREMIER Company

SOURCE NO. ES-23

Circle (13) on Reply Card

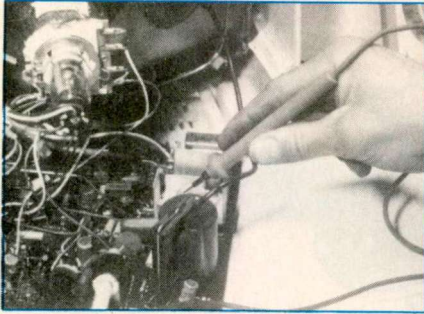

A convenient point to check the regulated LV supply is the collector of the horizontal-output transistor. This is one of the important points that must be monitored by meter as the variable-voltage transformer gradually increases the 60Hz voltage applied to the chassis. Other important voltages are the incoming variable ac voltage and the HVdc.

previous articles. When performed correctly, it is very satisfactory, allowing many tests while protecting the horizontal-output transistor from failure.

#### Hum bars

One or two hum bars moving upward in the picture usually are produced by a leaky regulator transistor or zener diode in the regulator circuit. First, try to adjust out the bars by correctly adjusting the B+ control. Sometimes a misadjustment of the B+ control will reduce the amount of regulation, causing the hum. Intermittent horizontal *pulling* of the picture might be a symptom, also, of the incorrect B+ control adjustment.

If the B+ voltage cannot be adjusted for the correct voltage, check each APF or regulator transistor for leakage. Remove the suspected transistor and perform another leakage test out-of-circuit. Sometimes the flat power transistors (TO-220 type) test leaky in-circuit but normal when removed. My advice is to replace them.

A high +146V from the low-voltage regulator and hum bars in the picture were the symptoms of a Sony KV-1510 portable (Photofact 1322-2). All three pins of the D903 voltage-regulator transistor tested the same voltage, and it was very high for the circuit (Figure 3). An in-circuit test showed D903 had leakage between all pins. We re-

placed D903 with a universal ECG277 transistor, which restored the picture and produced a normal +113V voltage source from D903.

#### Picture pulling

Usually, excessive horizontal tearing or pulling of the picture might be caused by defective filter capacitors or leaky components in the horizontal oscillator circuits. Also it is possible for leaky active-power-filter or AVR-regulator transistors to produce both faint hum bars and picture pulling. A leaky diode in the regulator circuit can cause the same symptoms.

Excessively high dc voltage was measured at the horizontal-output transistor's collector in a Panasonic CT-118 (Photofact 1858-1) that showed faint hum bars and erratic pulling of the picture. DMM tests of the Q801 AVR regulator transistor found excessive dc voltage at all terminals (Figure 4). When Q801 was removed from the chassis, it tested high leakage between collector and emitter.

Replacement of Q801 with a GE-35 universal replacement (and a small adjustment of R810, the +115V control) restored a normal picture.

#### HV shutdown

Many receivers have a shutdown circuit that can be triggered into stopping the horizontal deflection (and with it all receiver functions) by either of two general overloads.

*Excessive HV*—Usually, the most obvious trigger comes from a signal taken from the flyback. This pulse amplitude varies in step with the HV pulses (and the rectified dc HV). The circuit is designed to stop all receiver operation if the HV pulse exceeds a certain level. Therefore, the shutdown circuit primarily monitors *voltage*.

*Excessive current*—The second shutdown triggering signal comes from circuits that monitor the *current* (usually) at the *cold* end of the flyback's HV winding. (This is done by the current that flows

through a series resistor, producing dc voltage. All variations of this voltage are sent to another part of the shutdown circuit, so shutdown is triggered (usually in a different way than for the pulses) by any abnormal increase of HV-winding current.

This increased current can come from many sources, such as a shorted picture tube. A shorted CRT gun or spark gap can force the CRT to conduct many times its normal current, which is sufficient to trip the shutdown. Therefore, the raster lights up, usually with just one bright color, then shutdown occurs after a second or so.

Shorted turns in a flyback winding or defective HV-rectifier diodes that increase the HV-winding current can activate the shutdown.

#### Low voltage vs. HV shutdown

Excessive output from the low-voltage regulator can cause shutdown by applying too much B+ voltage to the horizontal-output's collector. Of course, a higher horizontal transistor's voltage in turn produces a greater HVdc, forcing the circuit into shutdown. Good tests require a variable-voltage 60Hz transformer for ac power. Begin with the receiver's input voltage at about 30Vac (after you have dcV meters connected to the high voltage and to the collector of the horizontal-output transistor). Slowly increase the receiver's ac voltage and compare the two meter readings. If the dc high voltage reaches the rated value, but the ac line voltage is only 90V or 100V and the transistor collector has the full B+ voltage, it is certain a problem exists in the low-voltage regulator: The low-voltage supply is too high.

For excessive voltage look for defective regulator and reference amp and driver transistors, leaky diodes (also zeners) and open resistors.

*Sanyo shutdown*—When shutdown occurred, the low-voltage source increased to +149V in a Sanyo 31C40A (Photofact 1986-1). Of course, the regulator definitely





(Photofact 1817-2), the sound was heard and the raster appeared before shutdown occurred. A variable-voltage ac transformer was connected to supply the 60Hz power, and a DMM probe was at-

tached to the collector (case) of the horizontal-output transistor. Then the ac voltage was increased from a low voltage up to 120Vac. The collector voltage reached +167V before the ac voltage reached

120V. It was a classic case of B+ regulator failure.

Because voltage-regulator transistors have a tendency to break down, we replaced Q701 with a GE-35 universal (Figure 6). Next, both zener diodes were replaced. ZD752 was replaced with a 120V zener and ZD751 was replaced with a 55V zener.

After the regulator transistor and the two zener diodes were replaced, the receiver operated for hours. Performance, good; intermittent shutdown, gone.

### Flashing raster

Both sound and raster would flash off and on at a rapid rate in an NTC 1300-CL portable television (Photofact 1777-2). At the horizontal-output transistor's collector, the dc voltage was a high +129V and pulsating (Figure 7). Adjustments of VR811 changed the B+ output only slightly. When the line voltage was reduced to provide +115V at the output transistor's collector, the flashing disappeared. The diagnosis was definite: The regulator was not reducing the dc voltage properly.


Q803 voltage-regulator and Q805 regulator-control transistors were checked in-circuit, testing normal. Similarly, diode D810 and zener diode D809 both tested good in-circuit. All resistors around the critical area were tested and found to be within tolerance.

After we replaced Q803 and Q805 regulator transistors, the B+ control could be adjusted for the normal +115V, and none of the adjustments slightly above and below that point caused any flashing or other instability.


### Intermittent raster

Intermittent-raster problems appear with many different symptoms. A raster with picture might light normally and then black out immediately, or the receiver might operate normally for several minutes before losing the raster. There are a number of defects that could cause such intermittent operation. These are some of the conditions, components or circuits that should be tested:

- Momentary loss or change of

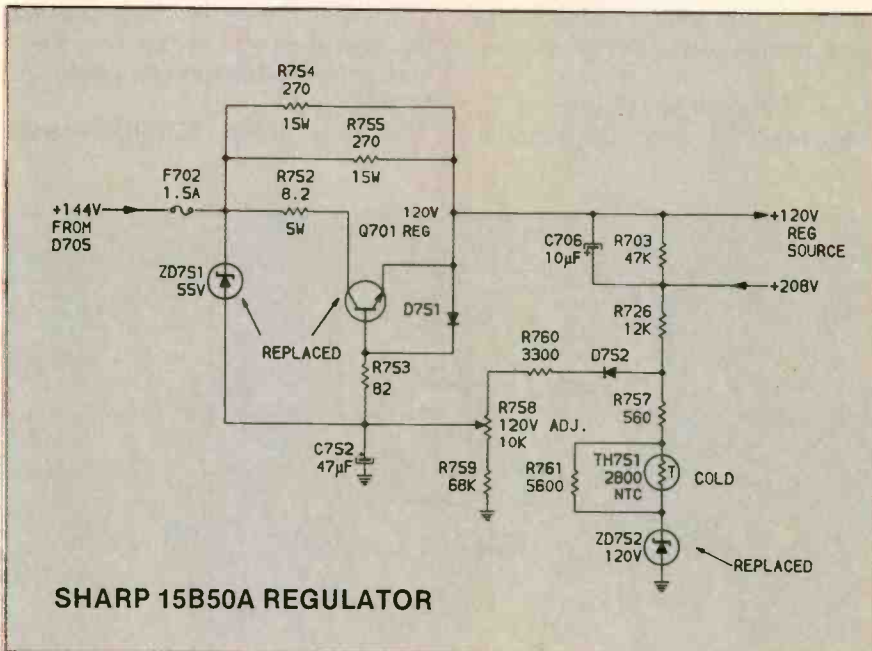

**Figure 6.** The low-voltage regulator circuit of the Sharp model 15B50A model (Photofact 1817-2) follows the general patterns of the others by having a power transistor that functions as a variable-resistance series resistance to vary the voltage drop as needed. But it is different in not having any smaller transistors or ICs. When the cause of the shutdown could not be found with the resistors, we replaced Q701 the power transistor, and two zeners, ZD752 and ZD751. These can't be tested adequately, except by replacement. The receiver operated properly.

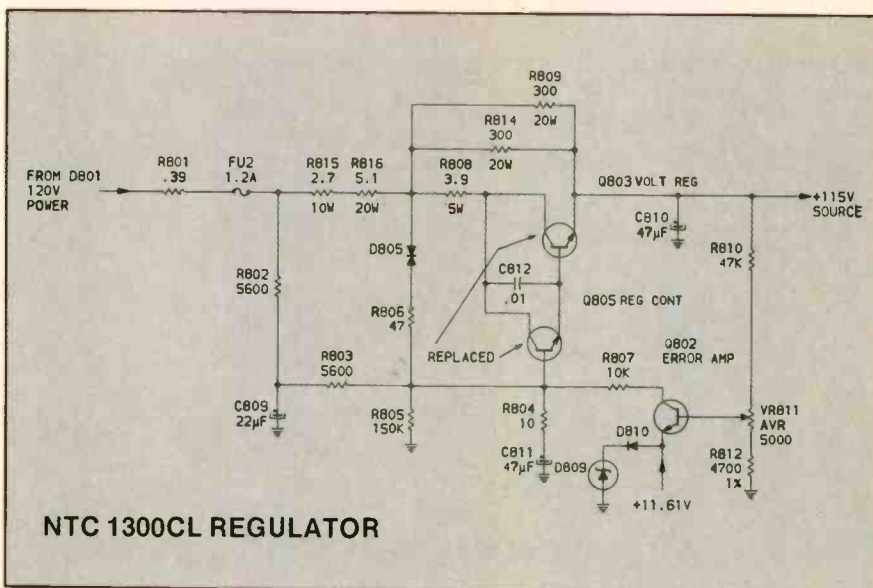

**Figure 7.** A pulsating +129V at the horizontal-output's collector gave a raster that would flash on and off rapidly with an NTC 1300-CL portable (Photofact 1777-2). Resistors, diodes, zeners and transistors were tested in-circuit without any defects being found. On a guess, Q803 regulator and Q805 regulator-control transistors were replaced, and the pulsating voltage with flashing raster returned to normal.



## Exclusive, triple patented dynamic cap and coil analyzing . . . guaranteed to pinpoint your problem every time or your money back

CRT grid voltage, screen voltage, heater power and other CRT problems including socket defects;

- A video problem that biases the CRT into cut-off intermittently;
- Any overload that forces the receiver into shut-off.

In addition to defective electronic components, intermittent rasters can be caused by corroded circuit-board connectors, loose mounting or ground screws and loose connections to or inside resistors. There are many more similar problem sources.

With an older Admiral 4M10 color portable (Photofact 1591-1), the raster would go black for about a minute and then return. When the chassis was cold and functioning correctly, the R901 B+ adjustment varied the voltage source from +114V to +130V (Figure 8). But when the raster went black, the +120V source measured +135V.

We replaced the Q900 pass driver, but the conditions were unchanged. All the resistors, one diode and one zener (forward conduction) in the regulator circuit were tested in-circuit and none found defective. Finally, during a power-on test, I noticed zener D901 had +132V across it. This was incorrect, because D901 is included to stabilize the voltage there at +125V.

Installation of a new 125V zener to replace D901 stopped the intermittent raster, giving a good, dependable picture.

### Lightning damage

Damage from lightning that comes in through the 60Hz-power wiring can be minor or extensive and all degrees in between. For the first step, give the chassis a thorough visual inspection, particularly around the power-supply area. In addition to burned resistors, insulation of wires and plastic connectors, look for damage to the circuit board. If large holes have been burned in the board, destroying much wiring, it might be wise to judge it beyond repair.

When the chassis shows no major visible signs of damage, the next steps are to test the line fuse, the line-rectifier diode (or diodes),



with the all new LC75 "Z METER 2"  
Capacitor Inductor Analyzer  
Patented \$995

The "Z METER" is the only LC tester that enables you to test all capacitors and coils dynamically — plus, it's now faster, more accurate, and checks Equivalent Series Resistance (ESR) plus small wire high resistance coils.

Eliminate expensive part substitution and time-consuming shotgunning with patented tests that give you results you can trust every time. Test capacitor value, leakage, dielectric absorption, and ESR dynamically; with up to 600 volts applied for guaranteed 100% reliable results — it's exclusive — it's triple patented.

Save time and money with the only 100% reliable, in- or out-of-circuit inductor tester available. Dynamically test inductors for value, shorts, and opens, automatically under "dynamic" circuit conditions.

Reduce costly parts inventory with patented tests you can trust. No more need to stock a large inventory of caps, coils, flybacks, and IHVTs. The "Z METER" eliminates time-consuming and expensive parts substituting with 100% reliable LC analyzing.

Turn chaos into cash by quickly locating transmission line distance to opens and shorts to within feet, in any transmission line.

Test troublesome SCRs & TRIACs easily and automatically without investing in an expensive second tester. The patented "Z METER 2" even tests SCRs, TRIACs, and High-Voltage Diodes dynamically with up to 600 volts applied by adding the new SCR250 SCR and TRIAC Test Accessory for only \$148 or FREE OF CHARGE on Kick Off promotion.

To try the world's only Dynamic LC Tester for yourself, CALL TODAY, WATS FREE, 1-800-843-3338, for a FREE 15 day Self Demo.



Call Today Wats Free 1-800-843-3338

**SENCORE**

3200 Sencore Drive  
Sioux Falls, SD 57107  
605-339-0100 In SD Only


*innovatively designed  
with your time in mind.*

Circle (14) on Reply Card

the filter capacitor, any low-resistance current-limiting resistors, the *on-off* switch and the voltage regulator transistor (or SCR). It's possible for a minor lightning strike to ruin only those components just listed. But a stronger bolt can fuse conductors

and burn components at many areas of the receiver, including some that have no direct connection with the 60Hz power or the antenna. Many of those receivers will be declared a total loss.

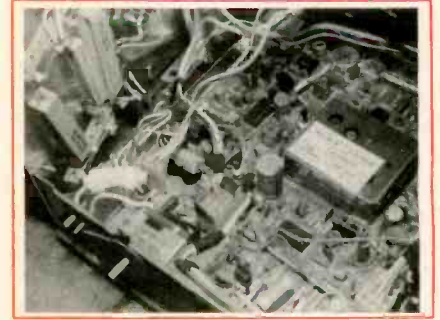When a Sanyo 91C64 portable color receiver (Photofact 1929-3)



After lightning strikes (or affects) a TV chassis, always check each regulator transistor, all diodes and voltage-dropping resistors. Also, check the circuit board for burned or damaged wiring.

was brought to the shop, we discovered it had been damaged by lightning. I replaced the F001 4A fuse, the RA2 low-voltage rectifier, the R002 2.2Ω current-limiter resistor, the R017 1.8Ω isolation resistor and the Q901 power-regulator transistor (Figure 9).


With all these components installed, the receiver had a raster, but that raster had hum bars and the +120V source checked only +106.5V, also the B+ control had no effect on the regulator's output voltage.

Finally, replacing IC001 (LA5112N) with a universal SK9188 power regulator increased and adjusted the +120V source while it eliminated the hum bars. The portable color receiver was ready for the customer.
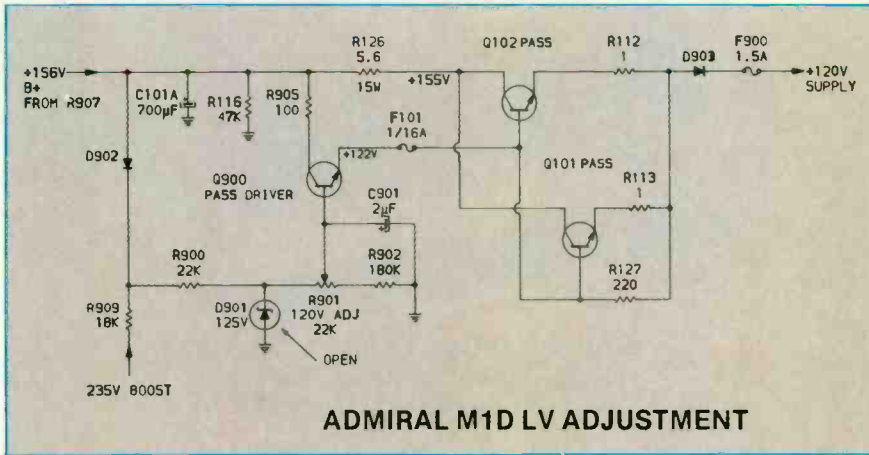
### An unusual problem


Sometimes when the chassis of a Goldstar KMC1311 was moved or jarred, the raster and sound would disappear. Yet, the receiver might operate for three or four hours without any problems. Or, the circuit might shut down at turn-on. When the chassis was dead, no voltage was applied to the horizontal-output transistor's collector.

The low-voltage power supply and regulator circuit were checked for loose soldered connections and intermittent components, but we found none. When the receiver was dead, a touch with the DMM probe would bring the receiver to full activity. After several attempts, we found the ac voltage was missing from the silicon



ADMIRAL M1D LV ADJUSTMENT

**Figure 8.** An older Admiral 4M10 color portable (Photofact 1591-1) developed an intermittent loss of raster. During the usual in-circuit testing of components, it was noticed that 125V zener D901 had +132V across it. The zener was there to hold that voltage to +125V, so the zener must be open. Installation of a new D901 stopped the intermittent.

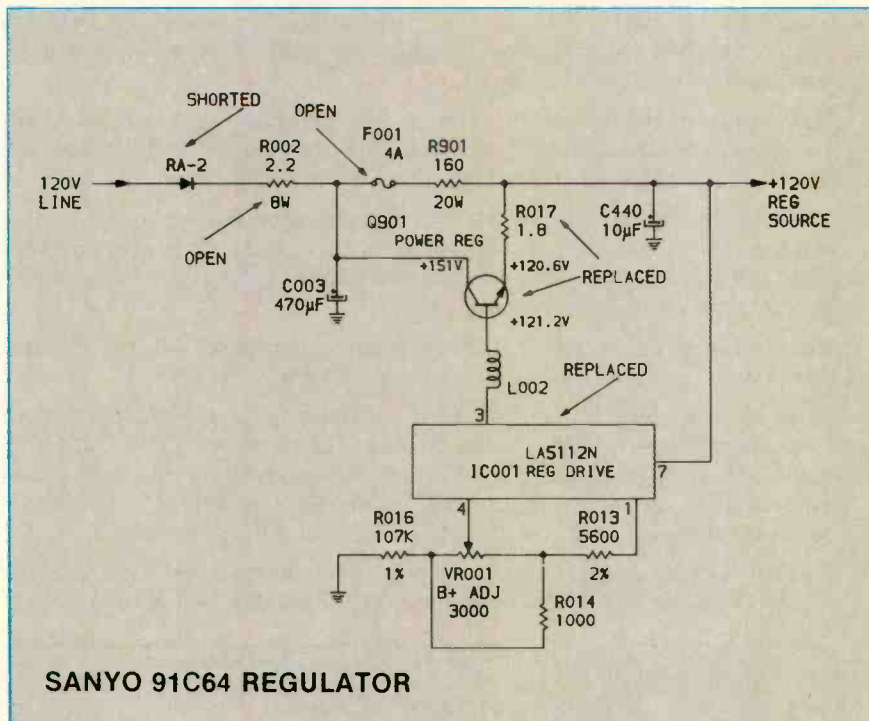

SANYO 91C64 REGULATOR

**Figure 9.** After a nearby lightning strike zapped a Sanyo 91C64 (Photofact 1929-3), we had to replace the F001 4A fuse, the RA2 rectifier, the R002 2.2Ω resistor, the R017 1.8Ω resistor and the Q901 power-regulator transistor. It was necessary also to replace IC001 before the performance was good.



# Analyze defective waveforms faster, more accurately, and more confidently — every time or your money back

diodes when the set was dead. Then the ac voltage was traced back to the 3A fuse holder. Just a touch on the fuse, and the chassis began to operate.

Evidently, the fuse or holder was involved. All connections from the fuse holder to the board wiring were good, but one fuse-clip end was bright and the other was dark. *The fuse holder was defective!* Instead of replacing the fuse holder with a new one, we decided to solder a 3A slow-blow *pig-tail* fuse direct to the circuit board in parallel with the old fuse holder. And that solved the mystery of the intermittent power.

## Comments


Here are a few suggestions that didn't find a place in the case histories. Because of the heavy wattage they must handle, power-regulator transistors cannot be checked adequately with the test equipment we have. Leakage that is very small when checked by a meter sometimes begins to multiply as the in-circuit voltage and current are increased. Therefore, the only certain test of a power transistor that has good junctions but is still questionable is to replace it and observe the results. A correctly operating transistor was defective, regardless of test results.

Remember, when the horizontal-output transistor is removed for tests, the B+ adjustment probably will not vary the B+ regulated voltage. The B+ will be too high or too low, but it's not likely to be the correct voltage until the horizontal transistor furnishes a normal load.

Make a habit of tightening all power-transistor mounting screws. Many intermittents originate from those loose screws.

For your safety and to protect your equipment, always use an isolation transformer for the 60Hz power. Also, a variable-voltage 60Hz-line transformer is essential for testing shutdown problems or cases of severe overload. *Both transformers are essential.* A variable transformer does not isolate, and an isolation transformer does not vary the voltage.

**ES&T**<sub>sm</sub>

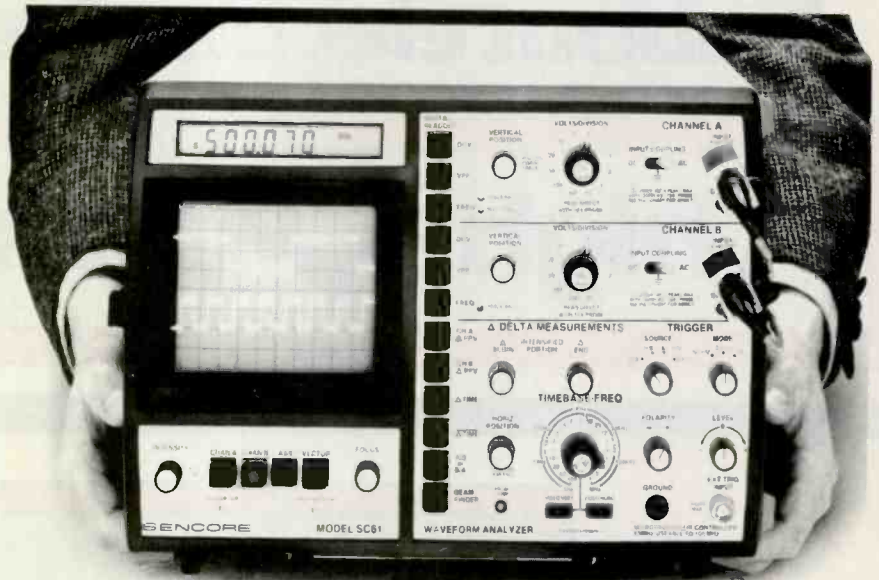

with the SC61 Waveform Analyzer  
Patented \$2,995

If you value your precious time, you will really want to check out what the exclusively patented SC61 Waveform Analyzer can do for you. 10 times faster, 10 times more accurate, with zero chance of error.

**End frustrating fiddling with confusing controls.** Exclusive ultra solid ECL balanced noise cancelling sync amplifiers, simplified controls, and bright blue dual trace CRT help you measure signals to 100 MHz easier than ever.

**Accurately and confidently measure waveforms from a tiny 5 mV all the way to a whopping 3,000 V without hesitation** with patented 3,000 VPP input protection — eliminates expensive "front end" repairs and costly equipment downtime.

**Make only one circuit connection and push one button for each circuit parameter test:** You can instantly read out DC volts, peak-to-peak volts and frequency 100% automatically with digital speed and accuracy. It's a real troubleshooting confidence builder.

**Confidently analyze complex waveforms fast and easily.** Exclusive Delta measurements let you intensify any waveform portion. Analyze glitches, interference signals, rise or fall times or voltage equivalents between levels; direct in frequency or microseconds.

**Speed your digital logic circuit testing.** Analyzing troublesome divide and multiply stages is quicker and error free — no time-consuming graticule counting or calculations. Simply connect one test lead to any test point, push a button, for test of your choice, for ERROR FREE results.

To see what the SC61 can do for your troubleshooting personal productivity and analyzing confidence, CALL TODAY, WATS FREE, 1-800-843-3338, for a FREE 15 day Self Demo.



Call Today Wats Free 1-800-843-3338

**SENCORE**

3200 Sencore Drive  
Sioux Falls, SD 57107  
605-339-0100 In SD Only

*innovatively designed  
with your time in mind.*

Circle (15) on Reply Card

# What do you know about electronics?

## A high-speed model

By Sam Wilson, CET

**F**igure 1 shows a model that often is used to describe the operation of a bipolar transistor. The arrows show the relative amounts of current flow in the base and collector when the transistor is properly biased for operation.

The general approach is to explain that a positive voltage on the base causes many charge carriers (electrons in this case) to move from the emitter to the base region. Once in the base, these charge carriers fall under the influence of the collector potential, and most pass into the collector.

I was talking to a friend about some very strange theories I've heard during my years of experience in electronics. He told me about a model for bipolar transistor operation that he was taught when he was a student at the university. The same illustration was used (Figure 1). Here is the way the explanation goes:

*The electrons in the emitter are attracted by the positive base and collector voltages. By the time they cross over the emitter-base junction they are going so fast that only a few can make the turn and go out the base lead. Most of them just plow into the collector region.*

I know this explanation will sound silly to you, but think about this: If you were trying to teach young people about transistors, you might sell them on that model. You could tell them that this is just a convenient way to look at the transistor.

I don't know what to say about

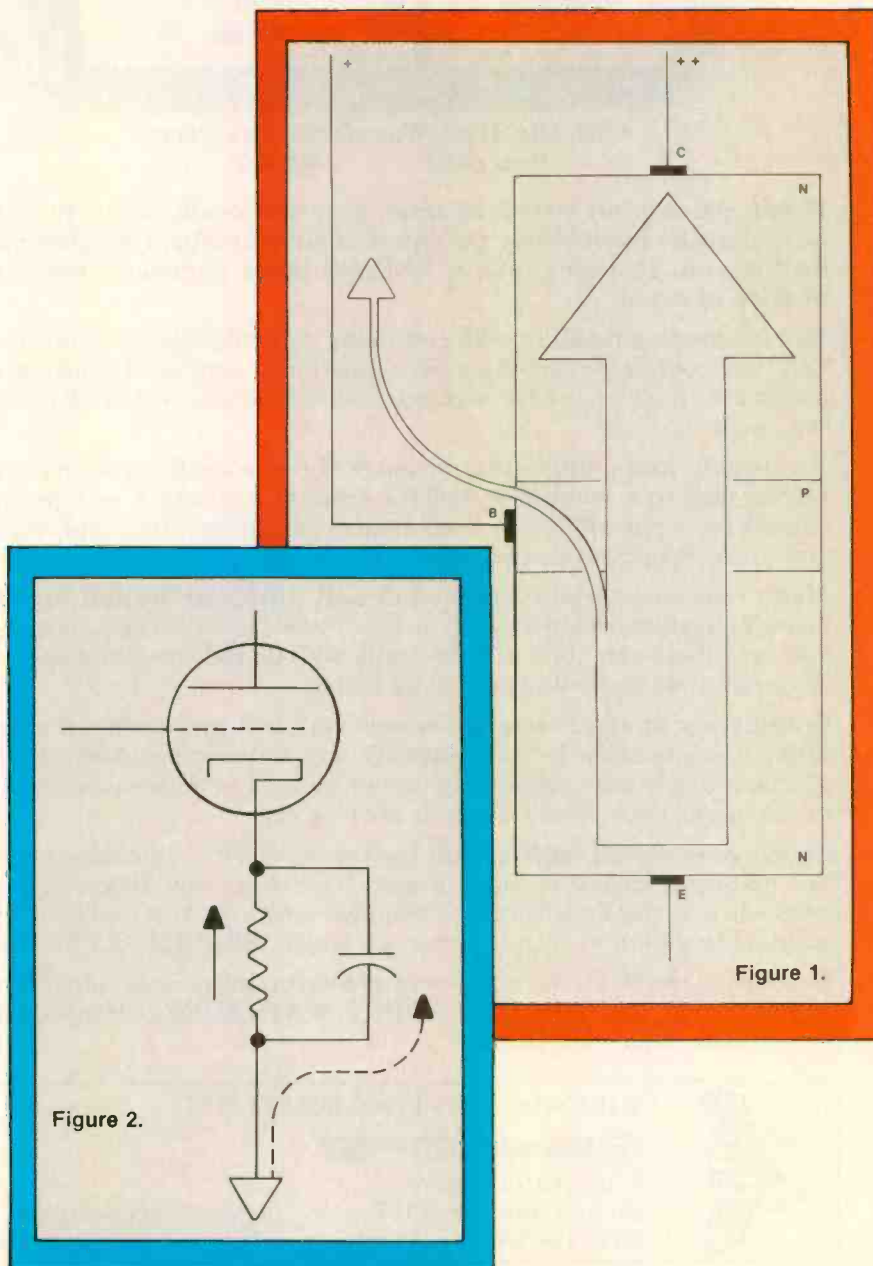


Figure 2.

Figure 1.



Now test and restore every CRT on the market . . . without ever buying another adaptor socket or coming up embarrassingly short in front of your customer . . . or your money back



with the new improved CR70 "BEAM BUILDER"™  
Universal CRT Tester and Restorer  
Patented \$995

**Have you ever?**

**Thrown away a good TV CRT, data display CRT, or scope CRT** that could have been used for another two or three years because you had no way to test or restore it?

**Lost valuable customers because you advised them that they needed a new CRT** when another technician came along and restored the CRT for them?

**Lost the profitable extra \$35 or more** that you could have gotten for restoring a CRT while on the job and locked in the profitable CRT sale later?

**Avoided handling profitable trade-ins or rentals** because you were afraid you'd have to replace the picture tube when you could have restored it?

**Had a real need to test a CRT on the job, but didn't have the right adaptor socket or setup information** in your setup book?

If any of these things have happened to you, **CALL TODAY, WATS FREE, 1-800-843-3338**, for a **FREE 15 day Self Demo**.

"BEAM BUILDER" is a trademark of Sencore, Inc.



Call Today Wats Free 1-800-843-3338

**SENCORE**

3200 Sencore Drive  
Sioux Falls, SD 57107  
605-339-0100 In SD Only

*innovatively designed  
with your time in mind.*

Circle (16) on Reply Card

the idea of telling this to university students.

**Planned obsolescence**

Whenever I'm with a group of technicians and the subject of strange theories comes up I find that everyone has a story to tell.

When I started my first full-time teaching job, I was required to sit in the class of the oldest and most venerated instructor on the campus. On the first day he was explaining the operation of the cathode bypass capacitor shown in Figure 2. Here is the way it went:

*Instructor*—On one half-cycle, the electrons flow through the resistor (solid arrow). On the next half-cycle, the electrons flow into the capacitor (broken arrow). This cycle repeats over.

*Puzzled Student*—"It seems to me that the capacitor would eventually get full of electrons."

*Instructor* (With his most feared "You are stupid" tone)—"Well, young man, that is why radios can't operate forever."

**The 4-layer diode**

For several years I have been writing about the characteristics of a 4-layer diode and some of its applications. However, it is next to impossible to buy such a diode without getting them in quantity, so there haven't been any good lab experiences with this component.

Sometime recently I ran across the solution to this problem. Unfortunately, I can't find that reference. The idea is that an SCR

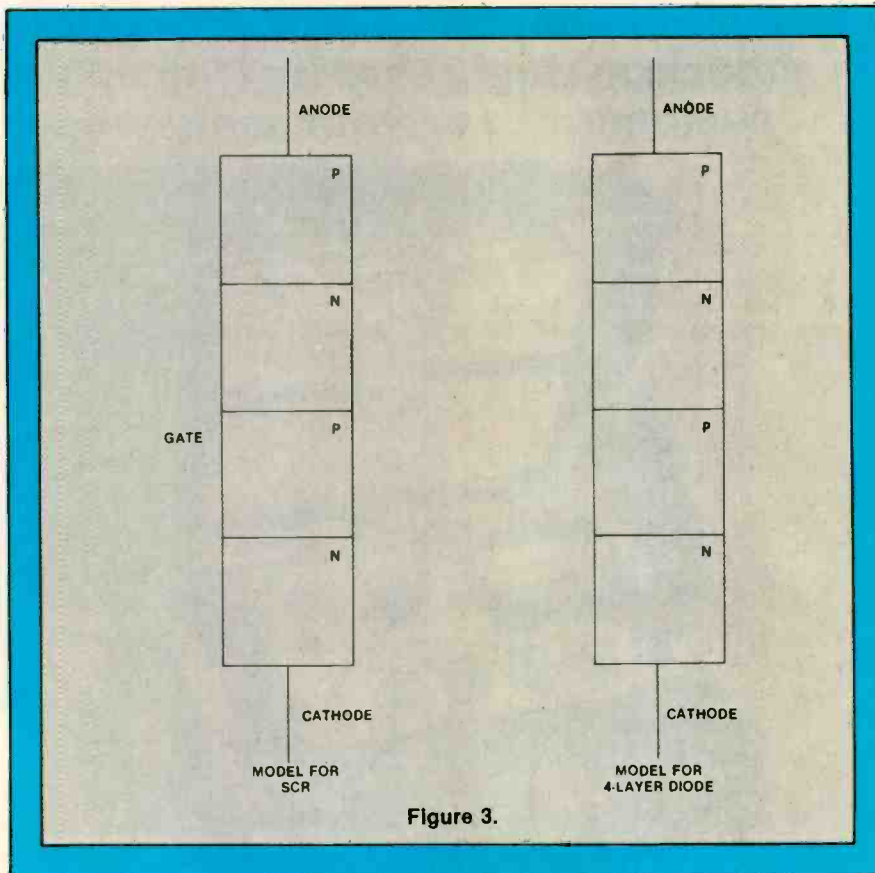


Figure 3.

can be used as a 4-layer diode if you leave the gate open.

Figure 3 shows the model most often used for an SCR. It shows why it can be used as a 4-layer diode (also shown).

By way of review, refer to Figure 4. The 4-layer diode is a breakover device in the forward direction. In other words, when it is forward biased, it behaves like a neon lamp.

When reverse-biased, it behaves like two identical reverse-biased diodes in series.

Four-layer diodes are also known as Shockley diodes.

I haven't had a chance to try the SCR idea. My next step is to try this in the lab. In a future issue, I'll tell you how well it works.

In the meantime, I will tell you what *hasn't* worked. That is to put two junction diodes in series to try to get the 4-layer characteristic.

### Here we go again!

There are some problems and questions related to electronics that make the rounds every two or three years. I don't want to give them the dignity of calling them classical questions. I'm not sure whether any point is proven by being able to solve them (or, not being able to solve them). Printing those problems and giving the solutions does not, unfortunately, make them go away.

Figure 5 illustrates an example. It was given to me recently by a student at New England Institute of Technology. (This school is located in Palm Beach, Florida. I wonder if there is a Palm Beach Institute of Technology in Maine.)

The question is: What is the resistance between terminals A and B? All of the resistors on the cube have the same value.

Attempts to solve this problem with series and parallel resistances usually result in failure.

The best approach is to assume a voltage across the terminals. Current flowing into R1, R2 and R3 will divide evenly because each of these resistors looks into two identical parallel resistors. So, the three resistors are in parallel.

By similar reasoning, R3, R4 and R5 are also in parallel.

It follows that R1, R2 and R3

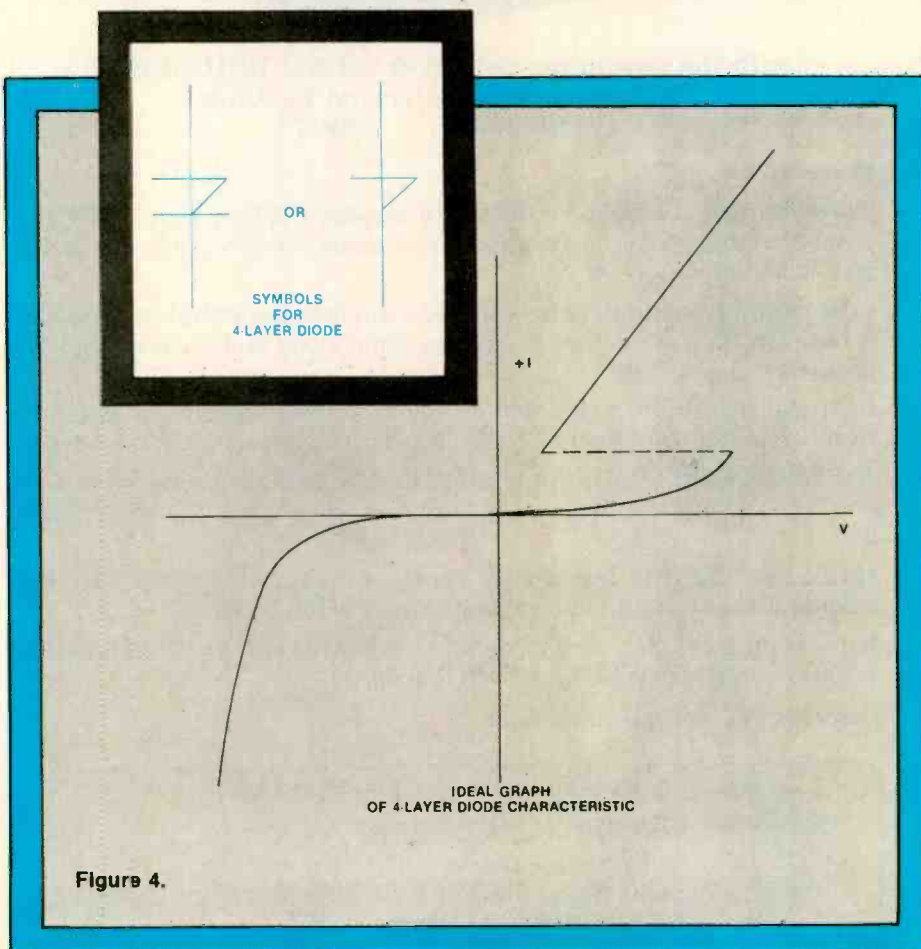


Figure 4.



terminate at equal voltage points because they have identical currents and resistances. Likewise, R4, R5 and R6 also terminate in equal voltages.

Figure 6 shows the result of this reasoning.

Because the remaining six resistors are connected between these equal voltage points, they must be in parallel.

When three identical resistors are connected in parallel, the resistance of the combination is one-third the value of one resistor. Likewise, six identical parallel resistances will have a resistance that is one-sixth of a single value.

Figure 7 shows the result. The circuit resistance is:

$$\begin{aligned} & \frac{1}{3} R + \frac{1}{6} R + \frac{1}{3} R \\ &= \frac{2}{6} R + \frac{1}{6} R + \frac{2}{6} R \\ &= \frac{5}{6} R \end{aligned}$$

The resistance of the circuit between A and B is 5/6 the value of one of the resistors.

If you know of an example of one of these nonsense problems, you can do me a great favor by sending it to someone else.

### A critical look at electron current

Until the invention of the bipolar transistor in 1948, there were two theories of current that were strong rivals. Electrical engineers, physicists and many other scientists used "conventional" current flow. In other words, they assumed that current flows from positive to negative.

People at all levels of electronic jobs used electron flow—that is, they assumed that current flows from negative to positive.

The argument for electron flow was based, in part, upon tube theory. If electrons flow from cathode to plate, it follows, supposedly, that current goes that way too. The opposing argument is that an electron wouldn't go to the plate unless there was a positive place (hole) for it to go to. That hole goes from the plate, where

## Walk "tough dog" troubles out of any TV & VCR in half the time . . . or your money back



with the exclusive, patented,  
VA62 Universal Video Analyzer . . . \$3,295

Would you like to?

**Reduce analyzing time:** Isolate any problem to one stage in any TV or VCR in minutes, without breaking a circuit connection, using the tried and proven signal substitution method of troubleshooting?


**Cut costly callbacks and increase customer referrals** by completely performance testing TVs & VCRs before they leave your shop? Own the only analyzer that equips you to check all standard and cable channels with digital accuracy? Check complete, RF, IF, video and chroma response of any chassis in minutes without taking the back off the receiver or removing chassis plus set traps dynamically right on CRT too? Simplify alignment with exclusive multiburst pattern?

**Reduce costly inventory from stocking yokes, flybacks, and other coils and transformers, for substitution only,** with the patented Ringing Test. Run dynamic proof positive test on any yoke, flyback, and integrated high voltage transformer . . . in- or out-of-circuit?

**Protect your future** by servicing VCRs for your customers before they go to your competition? Walk out "tough dog" troubles in any VCR chrominance or luminance circuit — stage-by-stage — to isolate problems in minutes? Have proof positive test of the video record/play heads before you replace the entire mechanism?

**Increase your business** by meeting all TV and VCR manufacturers' requirements for profitable warranty service work with this one universally recommended analyzer?

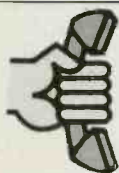To prove it to yourself, CALL TODAY, WATS FREE, 1-800-843-3338, for a FREE Self Demo . . . or learn how the VA62 works first by calling for your free simplified operation and application instruction guide, worth \$10.00.



Call Today Wats Free 1-800-843-3338

**SENCORE**

3200 Sencore Drive  
Sioux Falls, SD 57107  
605-339-0100 In SD Only

*innovatively designed  
with your time in mind.*

Circle (17) on Reply Card

Figure 5.


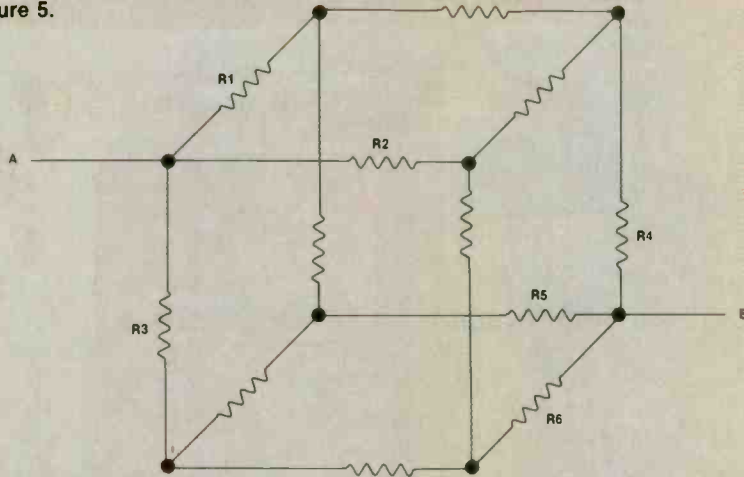


Figure 6.

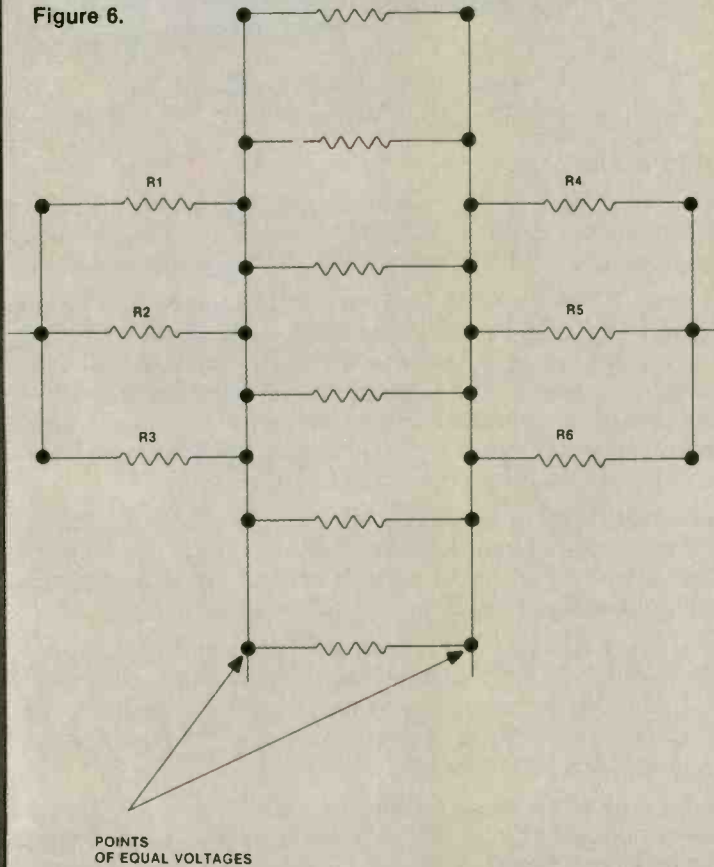

POINTS OF EQUAL VOLTAGES

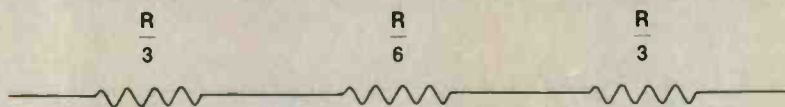


Figure 7.

the electron is, to the cathode, where the electron was.

Another argument for electron flow was the motion of electrons through a copper wire. It consists of a flow of *free electrons*. In fact, this is true for current flow in all metals. According to this argument, there can be no current flow unless there are free electrons to carry the current. So, current must be electron flow.

It can be argued that electrons can't go from one place to another unless a hole goes in the opposite direction.

Consider the following numbers.

A cubic centimeter of germanium at room temperature has about

44,000,000,000,000,000,000,000 atoms. The resistance between opposite faces is about 47Ω due to its 25,000,000,000,000

free electrons. It has an equal number of holes.

A cubic centimeter of lightly doped P-type material has a resistance of only about 10Ω. It has about

368,000,000,000,000 holes, and only about 1,700,000,000,000

free electrons. In other words, there are about 216 times more holes than electrons.

The low resistance of doped P-type germanium cannot be accounted for in terms of free electrons. So, current flow through the P-type material must be due to hole flow: *positive to negative!*

If you look at modern textbooks for electronics engineering or technology, you will find conventional current being used. However, if you look at textbooks for technicians, you see electron flow still being used.

The overall result is a mess. When technicians communicate with engineers, they have to sit on opposite sides of the table to get the current to flow in the same direction for both.

**Question:** Which way do the arrows in semiconductor symbols point?

**Answer:** In the direction of *conventional* current flow.

**Question:** Why can't we put this concept of electron current to sleep once and for always? **ES&T**



# Literature

## 64-page Blue Book

*Non-Linear Systems'* 1987-88 full-line catalog describes the company's latest offerings that encompass over 2,000 models of digital panel meters and battery operated portable test instruments. Test instruments included in the catalog are digital multimeters, oscilloscopes, frequency meters and circuit/component analyzers.

Circle (128) on Reply Card

## Interchangeability guide

*Batt-Tronic Corporation* has published a guide for watch/calculator battery interchangeability. The guide features interchangeability information for both foreign and American watch and calculator batteries. Valuable tips are included on proper battery

replacement along with a complete catalog of products and services.

Circle (129) on Reply Card

## Test and measurement catalog

The latest edition of the *Phillips Test and Measuring Instruments* catalog for 1987-88 is a 270-page document that provides details on Phillips' range of test instruments, with full information on all new products introduced in the last year. Product model number indexing enables fast location of any instrument. Full information is provided to allow ordering of any of the equipment from Philip's sales offices worldwide.

Circle (130) on Reply Card

and cross-reference charts facilitate product comparisons.

Circle (131) on Reply Card

## Multiple-outlet strips catalog

*Sockets Plus Multiple-Outlet Strips* catalog from *Perma Power Electronics* lists features and detailed specifications for 113 models, having as many as 12 outlets each. Special models for industrial/laboratory, hospital-grade and high-abuse environments are included, many with rack-mount options. Strips are available with a patented surge suppressor, master switch and indicator light. Photos and diagrams are included.

Circle (132) on Reply Card

## Heat sink catalog

*Thermalloy* is offering its 1986/87 catalog that includes 20 new stamped heat sink designs.

Over 250 extruded heat sink profiles have been added. There are six pages of labor-saving options.

Circle (133) on Reply Card

**ES&T**<sub>W</sub>



# Moving?

## Take us with you.

Just peel off the subscription mailing label and attach it to the address change card located at the front of this issue. Please allow 6-8 weeks to process your address change.

# ELECTRONIC

*Servicing & Technology*

# PSP

Service Software System  
only \$495.00  
all this for one low price!

- Tracking through complete repair cycle...
- Billing (automatically tabulates interest)...
- Aged Receivables...
- Manages & tracks Technician's workload...
- Assigns information to Warranty forms...
- Handles Consignment or Rental of parts & equipment...
- Generates: Receipts, Inventory Control Sheets, Status Reports, Authorization Slips, Daily Repair Reports, etc....
- And more!!

For any IBM Compatible from PC to AT.  
Minimum: 10 meg-hard disk & 256K RAM

PSP, 3840 S. Palo Verde, #204, Tucson, AZ 85714  
(602) 889-8888

Circle (18) on Reply Card

## Books

**Editor's note:** Periodically *Electronic Servicing & Technology* features books dealing with subjects of interest to our readers. Please direct inquiries and orders to the publisher at the address given, rather than to us.

**CD-I and Interactive Videodisc Technology**, by Steve Lambert and Jane Sallis; Howard W. Sams, 224 pages, \$24.95 softbound.

A source book for programmers and producers of interactive media, computer and audio-visual enthusiasts, this guide describes techniques and methods for creating interactive videodisc (IVD) and compact disc-interactive (CD-I) applications. There are chapters of a technical nature along with chapters delineating the user's role within the high-tech environment. Topics include:

- Interactive videodisc development and technical overview.
  - Types of laser videodiscs.
  - Videodisc formats.
  - Levels of interaction.
- With their work in industry and

optical media journalism, the editors, Lambert and Sallis, have been following this emerging technology since its beginning.

Published by Howard W. Sams and Company, 4300 W. 62nd St., Indianapolis, IN 46268; 1-800-428-SAMS.

**Elements of Electronic Instrumentation and Measurement, 2nd edition**, by Joseph J. Carr; Prentice-Hall, 515 pages, \$42.67 hardbound.

This updated edition relates to the many changes in instrumentation that have developed since the original text was published in 1978—the present, widespread use of digital electronic control, for example. Electronic instruments for measuring have proliferated to such an extent that technicians and others in the field find themselves heavily involved with an array of electronic devices.

In this book, readers will study instrumentation techniques, be introduced to certain commercial products and will come to understand the what and why of measuring, and the instruments in use.

Published by Prentice Hall, Inc., Englewood Cliffs, NJ 07632; 1-800-223-2336.

**Electronic Principles: Integrated and Discrete**, by James F. Cox and S. Roger Everett; Prentice-Hall, 553 pages, \$41.33 hardbound.

Here are authors who believe that some electronics instruction is

as obsolete as teaching Model-T repair in today's Space Age. For readers who understand the basics, this easy-to-follow book provides concise yet thorough coverage of discrete circuitry, IC op-amps, combining integrated and discrete electronics, transducers and optoelectronics. There are troubleshooting sections at the ends of each of the 13 chapters.

Published by Prentice-Hall, Inc., Englewood Cliffs, NJ 07632; 1-800-223-2336.

**Solid-State Projects You Can Build**, by Rudolf F. Graf and George J. Whalen; Howard W. Sams, 176 pages, \$10.95 softbound.

These do-it-yourself building projects require only simple tools and a VOM. A sampling of the projects includes:

- Electronic dice.
- Television remote-sound system.
- Wireless video camera link.
- Computing thermometer.
- Proximity or touch alarm.
- Sing-along light controller.
- Rally-mate time-piece.

There are complete step-by-step construction procedures, illustrated with drawings and photographs.

Published by Howard W. Sams & Company, 4300 W. 62nd St., Indianapolis, IN 46268; 1-800-428-SAMS.

**Troubleshooting Techniques for Microprocessor-controlled Video Equipment**, by Robert L. Goodman; Tab Books, 352 pages, \$16.50 paperback, \$24.95 hardbound.

To facilitate servicing the *electronic brains* now used in everything from color televisions to VCRs and videodisc players, this book breaks down the intricacies of microprocessors and digital electronics with step-by-step demonstrations. Following a short course on digital electronics, there is an introduction to troubleshooting techniques for logic circuits, using digital logic probes, logic monitors and oscilloscopes. Finally, the highly sophisticated troubleshooting method, *signature analysis* developed by Hewlett-Packard, is detailed in one complete chapter.

Published by Tab Books, Inc., P.O. Box 40, Blue Ridge Summit, PA 17214; 717-794-2191.

**ES&T**

**Learn  
how to repair  
VCRs...**

**Read**

**Video Corner**

**each month  
in ELECTRONIC  
Servicing & Technology**




# Photofact

These Photofact folders for TV receivers have been released by Howard W. Sams since ES&T's last report.

<b>AOC</b> C9163MB .....	2507-1	<b>MITSUBISHI</b> CS-1453, CT-1454R .....	2506-2
<b>EMERSON</b> ECT1900/A/B .....	2503-1	<b>PHILCO</b> Chassis 19C511, 19C529 .....	2508-2
<b>EMERSON</b> MS30R, MS30RA .....	2507-2	<b>RCA</b> Chassis CTC120D SUB1 .....	2502-1
<b>EMERSON</b> ECR222 .....	2508-1	<b>RCA</b> Chassis CTC130C .....	2504-1
<b>HITACHI</b> CT1365 .....	2505-1	<b>SEARS</b> 564.42090550 .....	2502-2
<b>HITACHI</b> CT2066, CT2066J, CT2066WJ .....	2506-1	<b>SHARP</b> 20KP75 .....	2504-2
<b>MAGNAVOX</b> 25C201-AA/2-AA/3-AA/4-AA/5-AA/6-AA .....	2503-2	<b>SHARP</b> 25KV785 .....	2505-2
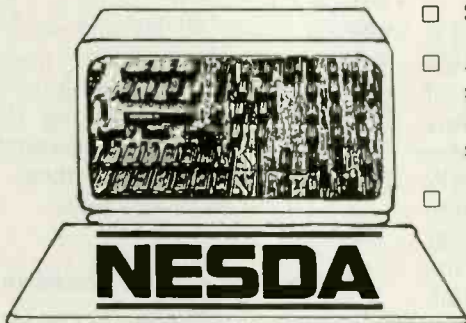
## NESDA Computer Group

COMPUTER SALES AND SERVICE DEALERS  
WORKING TOGETHER



- Service training.
- Assistance in selecting in-house equipment and software.
- Specialized software for service management.

- Factory contacts for service literature and parts.
- Involvement in a stable and productive national trade association.

FOR MORE INFORMATION SEND BUSINESS CARD TO:  
NESDA COMPUTER GROUP, 2708 WEST BERRY STREET  
FORT WORTH, TEXAS 76109; PHONE (817) 921-9061

## ATTENTION CAMERA TECHS!

Equipment you need  
at prices you can afford!



Model TR100 CB  
Camera Light Box  
with transparencies

- Stainless steel
- (2) 3200° Kelvin Lamps (meets mfr. spec.)
- 7-Bar color transparency
- 11-step gray scale transparency
- Transparencies mounted in acrylic with optical scratch-resistant surface.
- 1 year conditional guarantee

(313) 939-4710

Fax # (313) 939-6040

**TRONIX**  
inc.

34816 Mound Rd., Sterling Hts., MI 48077


The method most  
manufacturers  
recommend

Circle (19) on Reply Card

# Products
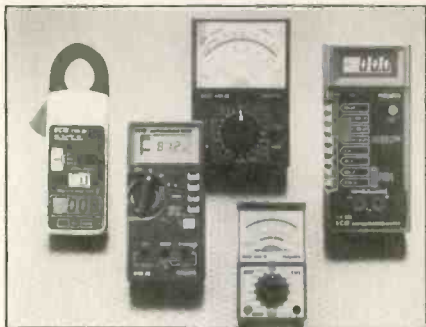
## Test equipment, accessories

*Philips ECG* has announced the addition of five multimeters to the company's Test Equipment & Accessories line.



The new products include the pocket-sized AM-14, a versatile yet economical analog multimeter, AM-20, a general purpose VOM analog multimeter; CM-30, clamp-on digital meter for reading ac current; CX-920, a digital capacitance meter; and DM-76, an auto-ranging digital multimeter.

Circle (75) on Reply Card

## 32-channel logic analyzer

The *Advanced Microcomputer Systems* logic and data analyzer PC Logic 1 and PC Logic 2 from Advanced Microcomputer Systems is an analyzer that is compatible with the IBM PC bus with up to 32 channels of data-capture input at a sample rate of 50MHz. The analyzer includes a completely menu driven software package that displays logic diagrams as




well as data dumps in binary, octal, Hex, and ASCII format on the PC monitor. The expansion and compression of channels and samples provides for maximum data

analyzing flexibility. The software also allows the user to save and load data onto the disk.

Circle (76) on Reply Card
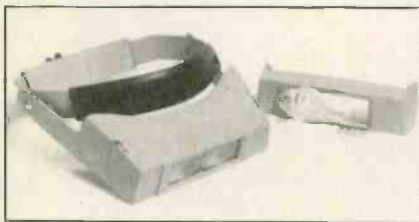
## Magnifier for work or hobby

The Mark II Magni-Focuser by Edroy Products is a binocular magnifier with a single, shatter-resistant, optical quality lens. The absence of a center post in the lens




provides an unobstructed field of view. Weighing only 4½ ounces, the Magni-Focuser is comfortable throughout many hours of use. Its contoured, padded vinyl headband is adjustable, self-locking, fully washable and replaceable. Front lens plate units are interchangeable, snapping on and off to meet various distance and magnification requirements. The Magni-Focuser may be worn over regular or safety glasses and flips up, out of the way when not needed. The flip unit is constructed of high-impact ABS plastic, with nothing to wear out, corrode or stick.

Circle (77) on Reply Card
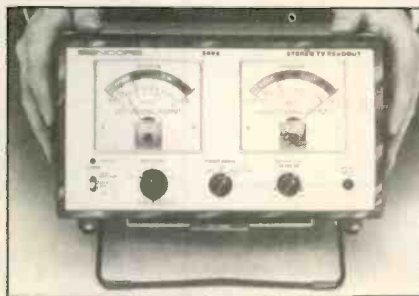
## Stereo-TV readout

*Sencore Electronics* announces a method to accurately analyze stereo TV audio.

The SR68 Stereo-TV Readout is reported to allow the service technician to measure the output of audio amplifiers; either at the line or speaker outputs. It incorporates dummy loads that provide to 100W per channel of power dissipation to catch even elusive problems that may show only when components are stressed to their full potential.



This testing device provides dual meters to visually monitor the outputs, and measures the audio

levels directly either in dB or watts. Audio separation of stereo circuits may be automatically measured to as low as -40dB by simply turning one knob.

Circle (78) on Reply Card

## High resolution monitor tester introduced

*Network Technologies* has introduced the Montest-RGB5, a portable tester for high resolution CRT monitors. The tester is designed for use with monitors implementing scan rates of 50kHz and having 798 lines of resolution.



Most often used with CAD/CAM and desktop publishing software, these monitors must be maintained for proper resolution and clarity. The MONTEST-RGB5's battery-powered portable design allows it to be taken directly to the field rather than requiring that monitors be returned to a central depot for repair and alignment.

Circle (79) on Reply Card

## Temperature probe converts DMM

*John Fluke Manufacturing* presents the 80T-150U Universal Temperature Probe, a measurement accessory that converts any digital multimeter into a thermometer. The 80T-150U uses a P-N junction temperature sensor housed in a low thermal-mass tip to provide fast responding, high accuracy readings.

The unit is switch-selectable for readouts in °F or °C. The 80T-150U can make temperature measurements of live circuits, with



350V peak ac standoff capability. Small components can be accurately measured without cooling due to mass of the probe tip.



The probe is suitable for surface, gas and non-corrosive liquid measurements. This includes most industrial solvents, water lubricants and fuels, as shallow as 1/2-inch.

Circle (80) on Reply Card

### Surge suppressors

A line of high performance surge suppressors has been introduced by *General Electric* to protect

home entertainment equipment from sudden impact voltages that could destroy or harm their delicate circuitry. The triple outlet VNS-21D incorporates a radio frequency interference (RFI) filter to guard against static-causing, TV interfering powerline noise.

Altogether, there are five different SurgePro devices designed for solid-state stereos, VCRs and TV sets, offering up to six connections through a single outlet.

Circle (81) on Reply Card

### Videotape teaches VCR maintenance

*Ucando VCR Educational Products* has released a new video tape that shows how to perform many of the common repair jobs required on every VHS video cassette recorder.

This video tape brings expert advice about the inner workings of the VCR. After viewing the 2-hour program, viewers will be able to properly clean the heads, rollers and guides in a VCR, as well as to replace the belts.

There are no special skills or tools required for performing the


maintenance and repair work shown in this video tape.

Circle (82) on Reply Card
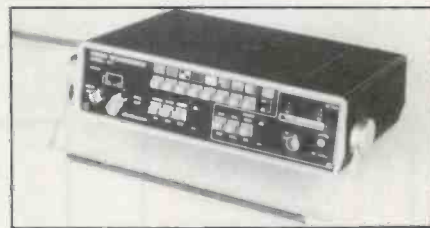
### Pattern generator

A portable audio-video pattern generator with four times the number of patterns and one-third the usual volume has been introduced by *NCM Electronics*.

The Video Wonderbox features 32 standard B&W and color patterns, including NTSC color bars. Its portability has been achieved through the use of NCM's in-house custom-designed LSI circuits.



The unit is designed for testing, troubleshooting and aligning VCR's, computer monitors and monochrome, color and cable-ready televisions.

Circle (83) on Reply Card

**ES&T**

## MTS DECODER/ SYNTHESIZER KIT

Build your own television stereo decoder/synthesizer with the TELEVONIC Series 500 kits. Decodes MTS formatted broadcasts and automatically synthesizes non-MTS broadcasts. Kits include TELEVONIC's proprietary synthesizer chip not available anywhere else. All kits include PC board, schematic and instructions.

Model 501\*—Partial Kit: \$16.95  
(without components)

Model 502—Complete Kit: \$26.95

Prices include shipping and handling within Continental U.S. Thirty day money back guarantee. Allow 14 days for delivery. Send check, money order, Visa or Mastercard (no C.O.D.) to:

**TELEVONIC**  
SOUND SYSTEMS

P.O. Box 46066  
Department E  
Denver, CO 80201


\*Components available at most electronic supply centers.

TELEVONIC is a registered trademark of Spectrum 2000, Inc.

Circle (20) on Reply Card

**SAVE  
TIME**

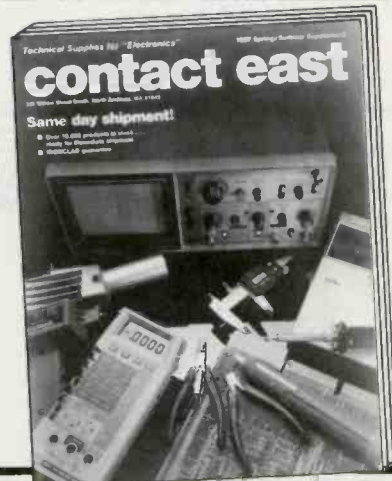*For fast, accurate service, please remove the peel off label used to address your magazine, and attach it to the Reader Service Card, the Address Change Card or to any correspondence you send us regarding your subscription.*



## FREE CATALOG TEST INSTRUMENTS & HARD-TO-FIND TOOLS

Packed with over 5,000 quality products for testing, repairing, and assembling electronic equipment. A full selection of test instruments, power protection equipment, precision hand tools, tool kits, soldering supplies, and much more. Products are shown in full color with detailed descriptions and pricing. All products come with a 100% satisfaction guarantee. SAME-DAY shipment program.

*In a hurry to receive your catalog?*


Call (800)-225-5370

In Massachusetts call (617)-682-2000

Contact East, Inc., Dept. R409  
P.O. Box 786 No. Andover, MA 01845

Circle (21) on Reply Card

## Overall block diagram

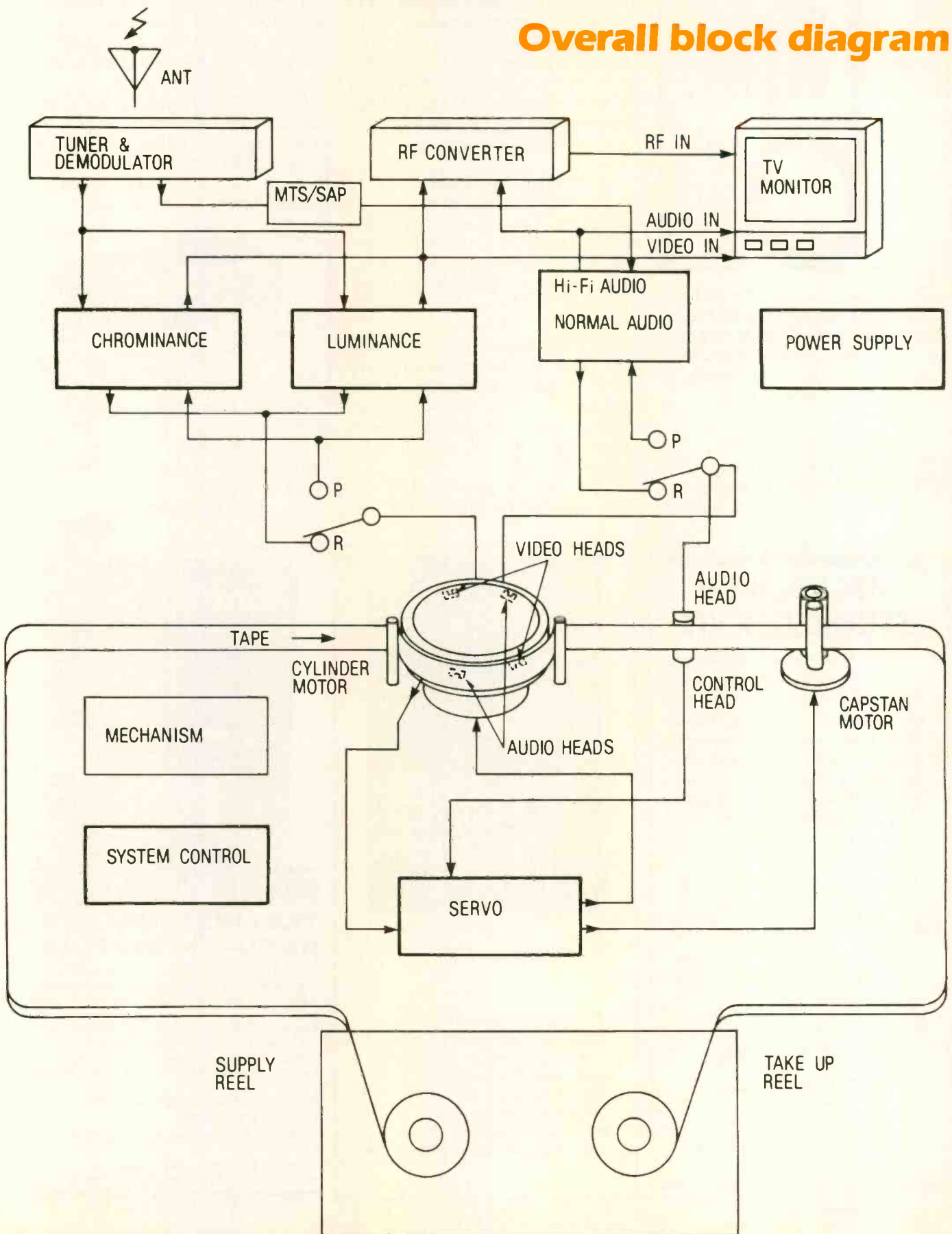



A lot has been made of the fact that VCRs are complex machines. They are. Servicing manuals on these units run over 100 pages. Many of those pages are multifold pages that contain the equivalent of three sheets worth of information. Block diagrams and schematic diagrams for VCRs can run for page after page.

This can't be helped, given the complexity of the products, but trying to understand basic principles of operation can be seriously impeded because of the sheer volume of information that has been waded through.

Given all of this complexity, when a piece of information comes along that makes it easy to grasp the general principles of the technology almost in a single glance, it's worth making interested people aware of it.


Take a look at the overall block diagram of a GE VCR on the opposite page. Of course it's highly simplified, but it provides you with an immediate grasp of what goes on in a VHS VCR.

In this case, the PLAY/RECORD switch is in the RECORD position. When the VCR is in this condition, using a local broadcast station for a source, it tunes the signal, demodulates it, processes the chrominance and luminance, and audio signals to apply them to the video and audio heads, respectively, where they are converted into magnetic information and impressed onto the tape.

The mechanical system controls the speed of rotation of the video head cylinder and the capstan motor, based on signals from the control head and the head cylinder. Notice that the direction of the arrowheads indicates input or output, or, in some cases, both.

Again, this overall block diagram of a VCR can't give details of operation of a VCR. It's too simple. But a grasp of the principles it shows can give you a head start toward understanding the details later.

**ES&T**

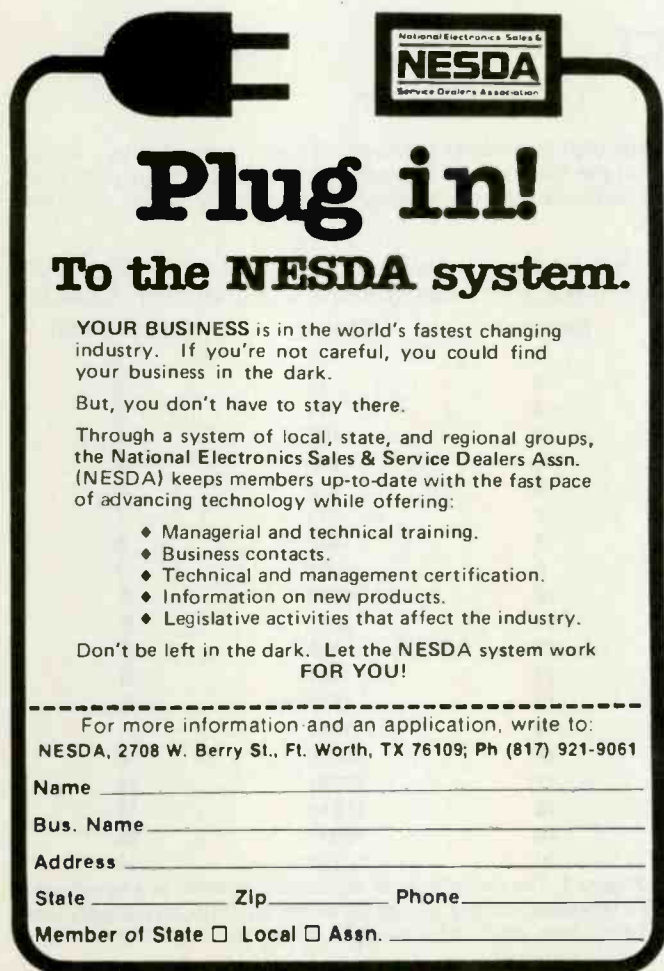

National Electronics Sales & Service Dealers Association  
**NESDA**

## Plug in!

### To the NESDA system.

**YOUR BUSINESS** is in the world's fastest changing industry. If you're not careful, you could find your business in the dark.

But, you don't have to stay there.

Through a system of local, state, and regional groups, the National Electronics Sales & Service Dealers Assn. (NESDA) keeps members up-to-date with the fast pace of advancing technology while offering:

- ◆ Managerial and technical training.
- ◆ Business contacts.
- ◆ Technical and management certification.
- ◆ Information on new products.
- ◆ Legislative activities that affect the industry.

Don't be left in the dark. Let the NESDA system work **FOR YOU!**

---

For more information and an application, write to:  
NESDA, 2708 W. Berry St., Ft. Worth, TX 76109; Ph (817) 921-9061

Name \_\_\_\_\_

Bus. Name \_\_\_\_\_

Address \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_ Phone \_\_\_\_\_

Member of State  Local  Assn. \_\_\_\_\_

## When You Want the Best Buy the Best

**Free Offer\***

When your problems require the attention of a professional, call NU DATA, the company that originated the "Break-Out-Box" 17 years ago. The Model 921-T3 is the only battery free breakout with pulse trap.

- Dual LED Tri-State Design
- Battery Free Operation
- Guaranteed for Life
- GSA Approved



**\$176.00**

\*Buy a Model 921-T3 and get a free Interface Monitor, a \$50 value.

Call for information on our complete line of testers.

**(201) 842-5757**

**NU DATA**

32 Fairview Avenue  
Little Silver, NJ 07739-1515


Circle (23) on Reply Card

## Working with hexadecimal numbers

Hexadecimal. It's a word that strikes fear and loathing in the hearts of the stoutest men. It's as if the "hex" part puts a hex on people. It has something to do with computers and numbers, but what?

Hexadecimal (hex, for short) really isn't that hard to understand. It just takes a little reflection on the way we make numbers. Take decimal, for example. In decimal, we count using the digits 1, 2, 3, 4, 5, 6, 7, 8, 9.

It might have been possible to create a digit for every number, but that would have been cumbersome in the extreme, and would have made calculation exceedingly difficult. Instead, it was decided to use only nine digits, then when it was necessary to represent ten of whatever was being counted, the digit would be moved one place to the left to show that the 1 represented one *group of ten* rather than simply one (see Figure 1). Presumably, it was decided to do this at the number ten because humans have ten fingers. In forming the decimal number ten, the zero is

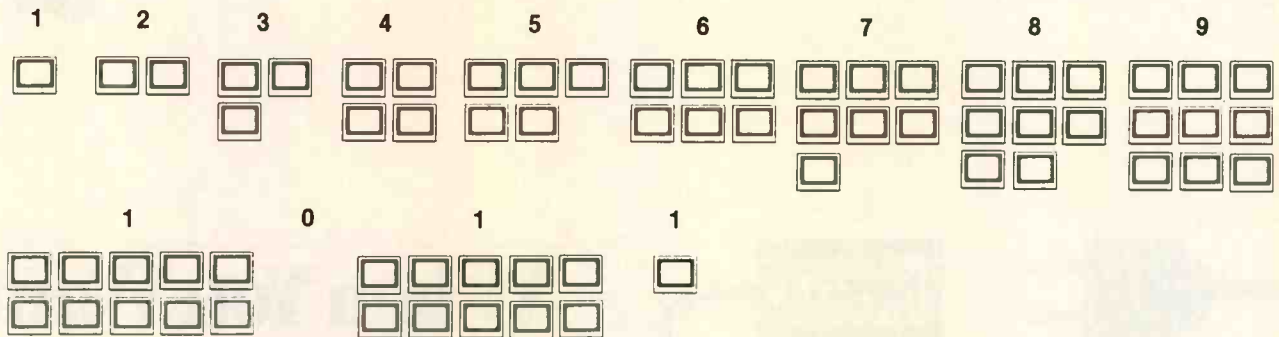

**Figure 1.** Decimal numbers are formed as shown here. Each individual digit represents a quantity. To form a number ten, we use positional notation (shift the 1 digit one place to the left) to show that the 1 represents a group of ten rather than one unit. The 0 in the number 10 shows that the 1 has been shifted. To form larger numbers, we use 11 as one group of ten plus one, 12 as one group of ten plus two, etc.

placed to the right of the digit to show that, in fact, it has been shifted to the left. Then we can continue counting: 11 represents one group of ten plus one, 12 represents one group of ten plus two, and so forth.

In hex, for reasons that will be presented in a moment, it was considered advantageous to create several more digits. In hex, counting proceeds: 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, F, 10, 11, etc. Thus in hex, the numbers ten, eleven, twelve, thirteen, fourteen and fifteen are represented by A, B, C, D, E and F respectively. Please note that it would have been possible, and might have been better, to create some new numeric digits for those hex numbers, but the letters A through F were already in existence, so what the heck!

What does all that have to do with computers? Well, nothing and everything. Some computers are said to operate in hex, but that is not, strictly speaking, correct. If we take a look at the correlation between hex and binary the whole thing becomes clear.

You might want to refer to the Computer Corner in last month's *ES&T*, in which binary numbers were discussed. Counting in binary proceeds; 1, 10, 11, 100, 101, 110, 111, 1000, 1001, 1010, 1011, 1100, 1101, 1110, 1111 (those are the numbers one through 15 in binary).

Now take a look at Figure 2. Notice how conveniently a single hex digit represents a binary number that takes four binary digits. That's essentially what is meant by a com-

puter operating in hex. A computer, as we have emphasized many times, operates only in binary. Its 2-state devices can't operate any other way. But the computer operates such that its binary digits are taken four at a time (or some integral multiple of four at a time).

So the computer continues to operate in binary. The advantage to hex is to the operator or programmer. Let's say a human is trying to deal with the computer's operation and it includes a binary number like 10110101100010111111. That's twenty digits. I defy you to manipulate that many digits that are all alike without transposing digits or accidentally changing a 1 to a 0 or vice versa. But if you replace each group of four digits with its hex equivalent you have the hex equivalent of the binary number: B58BF (see Figure 3). You're a lot less likely to mess up *that* number when you're working with it.


Of course it's not especially easy to work with hex. It takes a couple of serious mental leaps to treat letters of the

alphabet like numbers, and to treat numbers with a single digit that you're used to representing with two digits. But

Decimal	Binary	Hexadecimal
1	1	1
2	10	2
3	11	3
4	100	4
5	101	5
6	110	6
7	111	7
8	1000	8
9	1001	9
10	1010	A
11	1011	B
12	1100	C
13	1101	D
14	1110	E
15	1111	F
16	10000	10
17	10001	11
18	10010	12
19	10011	13
20	10100	14

**Figure 2.** The hexadecimal numbering system is a handy way to represent binary numbers (which quickly can get very long using four digits at a time) in a way in which they're more easily handled.



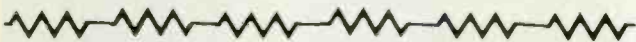

starting with a basic understanding of what hex is all about, you can play with the numbers until you have at least reached peaceful coexistence, even if you're never quite comfortable with them.


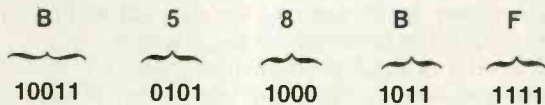


Figure 3.

Figure 3. You can take a binary number four digits at a time and represent each group of four digits with its hex equivalent. The whole point of hex is to make it easier for us to deal with strings of binary digits.

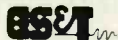

## Answers

Questions are on page 4

1. B. The logic levels at the inputs and output of each gate are shown in Figure A. Remember, the only way to get a logic 0 out of a NAND is to have all inputs at logic 1.
2. 1,555kHz. The radio will play if the local oscillator is dead. Remember: Oscillator frequency = RF frequency + IF frequency.
3. A. The circuit is a Wheatstone Bridge, balanced when there's no current thru the meter.
4. 12Ω. The equation for the balanced bridge is  $R1/R2 = R3/\text{speaker } Z$   
If it is an 8Ω speaker:  
 $R2 = R1 \times \text{speaker } Z/R3 = 12\Omega$
5. IN4146. The IN prefix is understood. The colors represent the same numbers as for resistors.
6. A. The wide band indicates the cathode side.
7. C. Assume the radio is dead but the power supply is OK. When the radio is tuned through a strong station, the current meter should show a strong increase in deflection. With no audio input, the push-pull amplifiers are nearly cut off. The input audio drives the transistors into conduction.
8. B. With an emitter-base short, the transistor is cut off. No current flows in the collector resistor, so there is no voltage drop.
9. A. The input signal is at the base and the output signal is at the collector. The emitter is common to the input and output signals.
10. B. With R open, base has no forward bias.

**Technicians,  
Get Serious  
About Your  
Profession**



Being a certified electronics technician lets people know that you are a professional in your field. It tells them that you are serious about your work and can perform up to CET standards.

Now you can order the "Study Guide for the Associate-Level CET Test" from the International Society of Certified Electronics Technicians. It includes material covering the most often missed questions on the Associate CET exam. 8½" x 11", paperback, 60 pages.

For More Information Contact:

ISCET, 2708 W. Berry, Fort Worth, TX 76109; (817) 921-9101

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_  
ZIP \_\_\_\_\_

\_\_\_\_\_ copies @ \$5 (+ \$1 postage.)

\_\_\_\_\_ send material about ISCET and becoming certified.

## FREE! New Catalog of Hard-To-Find Precision Tools



Jensen's new catalog is jam-packed with more than 2,000 quality items. Your single source for hard-to-find precision tools used by electronic technicians, scientists, engineers, schools, instrument mechanics, laboratories and government agencies. This popular catalog also contains Jensen's world-famous line of more than 40 tool kits. Call or write for your free copy today!

**JENSEN®** 7815 S. 46th Street  
**TOOLS INC.** Phoenix, AZ 85044  
(602) 968-6241

Circle (24) on Reply Card



## CHEMICAL SOLUTIONS

### FREE CHEMTRONICS CATALOG!

Comprehensive new source for over 200 products used in electronic manufacturing and field service. Precision cleaning agents, flux removers, bulk solvents, circuit refrigerants, precision dusters, non-residual wipers, foam swabs, premoistened pads/swabs, antistatic compounds, conformal coatings, lubricants, adhesives, desoldering braids, rosin core solder and solder masking agents. Complete with technical specifications and application guide.

**Chemtronics Inc.**  
681 Old Willets Path  
Hauppauge, N.Y. 11788  
516-582-3322

Circle (25) on Reply Card

## Breaking the CLV servo loop

As mentioned in past columns, CD players are chock full of servos, and if you've ever encountered tough problems in them, you know the true meaning of the phrase *going around in circles*.

What is a servo? It's a circuit that uses part of its output as an input. This principle is familiar to anyone who has worked with audio amplifiers. A certain amount of the output is always *fed back* to the input in order to cancel distortion products. But servos are generally part of an electro-mechanical device, something with a motor in it. A servo system functions to maintain the correct operating position of a mechanical assembly by comparing a position signal (feedback) to a reference signal.

Specifically, a CD player has tracking/sled, focus and disc motor (CLV) servos. The tracking coil and sled motor are separate, but they share a good portion of the servo circuitry before going their own ways. Simply put, the sled takes care of the *coarse*, and tracking the *fine* control of the optical block.

Thanks to safety shutdown circuits, one of the more common symptoms encountered in home CD players is a dead disc motor. Many home units are designed so that focus must be achieved (FOK) in order for the motor to start. (Although, most of the portables I've seen run the motor up as soon as you push PLAY.) Sometimes, the disc will start to spin, then shut down if TOC is not read, perhaps due to RF PLL or tracking trouble. Because one of the first things we need to do on a defective player is check the RF (eye pattern), we're in trouble unless we can get the disc motor to run. *No rotation equals no eye pattern*.

It's times like these that make you appreciate manufac-

turers who build diagnostics into the set, at least something that allows you to defeat shutdown. Some units have a pin on the microprocessor that eliminates certain shutdown processes when grounded, but few are documented well enough to let you know what actually is being defeated. The pin may be marked TEST, ADJ, SERVICE, or something more arcane, such as BATT2, but, you usually can figure that activating it will, at the very least, prevent the player from coughing the disc out while you're trying to adjust or troubleshoot the machine.

Back to the original problem now; the CLV motor is dead and you need to check the laser. Most of the time, you're just going to have to get in and rewire a few circuits to do it. Take a look at Figure 1. Many CLV motors are of the brushless, slotless type, which among other things, means that speed control is probably effected by changing the bias on a Hall-effect device. Assuming the power supply to the motor is OK, you can disconnect the speed control input from the servo circuitry and substitute a variable external power supply. Bias voltages are usually in a 0Vdc to 2Vdc range, and quite often negative. Be sure to check the schematic for the unit you're fixing.

You'll need relatively precise control over motor speed, and thus, bias voltage. If your supply has a precision, multiturn pot that is quiet and effective down at the lower end of its range, you're all set. But if you have one like I use, the control is so erratic below 6V, that it's impossible to get stable control of the motor. You can go out and spend a few hundred dollars on a new supply, or you can dig through your bin of forgotten parts for a couple of resistors to make a 10:1 voltage divider. Something around 900k $\Omega$  and 100k $\Omega$  ought to do nicely. The Hall devices need

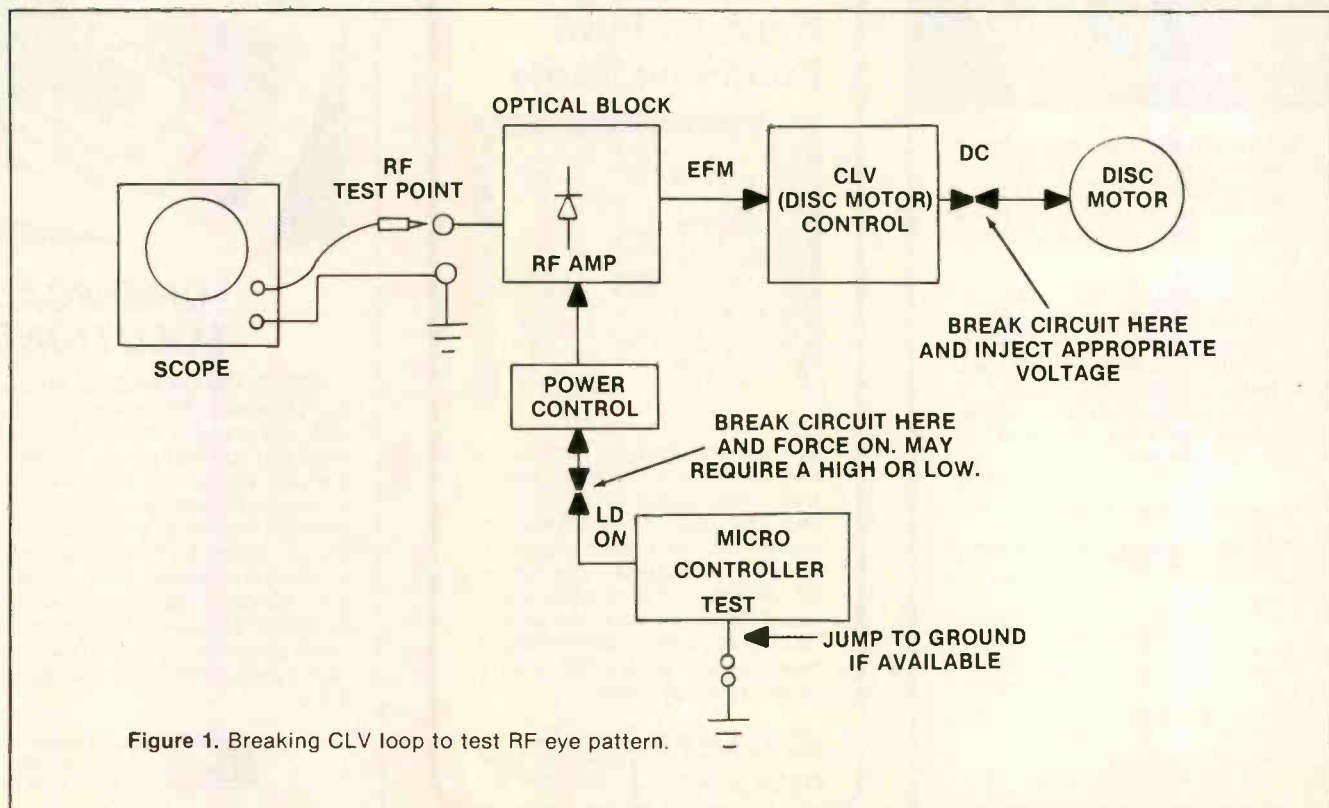


Figure 1. Breaking CLV loop to test RF eye pattern.



voltage, not current. Now your power supply can operate in a comfortable 10V to 20V range where the output level control works smoothly. In the field, a 1.5V battery (Oops! I mean "cell") works nicely, but you still have to rig up a potentiometer to vary the voltage.

Lately, I've noticed some portable players using the simpler, brush-and-commutator type of dc disc motor. These have only two wires. The servo provides both power and control, unlike circuits designed for BSL motors that only need to supply a control voltage.

Of course, making the motor turn is merely one step in the process. In order to see an eye pattern, the laser must be on and the focus servo operational. Once again, the microcontroller usually feeds some sort of enabling signal to the optical block. It might be termed LD, LDON, or something else, but you usually can figure it out by studying the schematic. Even with the test mode engaged, it is often necessary to force this signal to the proper level to get the laser to stay on long enough.

Now that we have the laser turned on and the disc motor spinning at around 300 rpm, you ought to get some sort of eye pattern, assuming a disc is in the machine, the RF amp is working and the focus servo is OK. But what if focus is bad? Sometimes, that will make the test impossible, but often, there is enough slop in the sled assembly that the nimble-fingered technician can move the optical block

enough to find a good focus point, if only for just a moment. If the RF is OK, you can make the working assumption (one we can discard later if it gets us nowhere) that the laser is not the cause of the apparent motor problem. By the way, make sure the optical block is positioned into the disc where data density is normal. In the TOC (table of contents) and between tracks, you'll see an anemic pattern.

As with any troubleshooting procedure, practice makes perfect. You also need to understand the circuit well enough to make a good guess exactly where to break the loop and inject voltages. Top troubleshooters are also experimenters, unafraid to fail several times in the pursuit of improved technique.

Next time we'll break a few more loops, and maybe even find a way to test the RF PLL with a dead optical block.

By the way, a few columns back, I mistakenly claimed that 1/2-inch PCM audio and CDs use the same sampling frequency. Thanks to Dennis Machesky of Sony Corporation for setting me straight. PCM uses 44.056kHz; CD, 44.1kHz. To a guy like me, brought up on analog equipment, two frequencies are essentially identical if they are within 0.09% of one another. But to a digital circuit, the difference is significant. The standards committees set it up this way so direct digital copies of CDs could not be made on 1/2-inch PCM equipment.

**ES&T**

## ATTENTION TECHNICIANS

- ★ JOB OPENINGS
- ★ MONTHLY TECHNICAL TRAINING PROGRAM
- ★ BUSINESS MANAGEMENT TRAINING
- ★ LOW COST INSURANCE
- ★ CERTIFICATION
- ★ TECHNICAL SEMINARS

All of this in a nonprofit international association for technicians

FIND OUT MORE:



604 N. Jackson St.  
Greencastle, IN 46135

## ATTENTION! ELECTRONICS TECHNICIANS

EARN YOUR  
**B.S.E.E.  
DEGREE**



### THROUGH HOME STUDY

Our New and Highly Effective Advanced-Placement Program for experienced Electronic Technicians grants credit for previous Schooling and Professional Experience, and can greatly reduce the time required to complete Program and reach graduation. No residence schooling required for qualified Electronic Technicians. Through this Special Program you can pull all of the loose ends of your electronics background together and earn your B.S.E.E. Degree. Upgrade your status and pay to the Engineering Level. Advance Rapidly! Many finish in 12 months or less. Students and graduates in all 50 States and throughout the World. Established Over 40 Years! Write for free Descriptive Literature.

## COOK'S INSTITUTE OF ELECTRONICS ENGINEERING

**CI** EST. 1945  
347 RAYMOND ROAD  
P.O. BOX 20345  
JACKSON, MISSISSIPPI 39209

Circle (26) on Reply Card

### PORTASOL™ MAIL OFFER

**HOT  
NEW  
IRON!**



**A Truly  
Portable Butane  
Soldering Iron.**

Order your  
Portasol™ now!  
**Only \$35.95**

- Safe butane-powered no open flame
- Adjustable from 10-60W power
- Compact only 7" long
- Each unit comes with 2.4mm tip
- Extra tips available at \$9.95 each  
Choose 1.2, 2.4, 3.2, or 4.8mm

Send check or money order for \$35.95 plus \$2.00 shipping and handling (VA res. add 4.5% sales tax) to:

Portasol Mail Offer  
4358 Harvester Farm Lane  
Fairfax, VA 22032

Phone Orders Call (703) 323-8000

Name \_\_\_\_\_  
Company \_\_\_\_\_  
Street \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_  
Zip \_\_\_\_\_ Phone \_\_\_\_\_

Quantity Discounts Available

**Dealers Invited**

Circle (27) on Reply Card



# Readers' Exchange

## Beginning July 15...

No ad requests will be accepted for Readers' Exchange without a *full, verifiable name, address AND phone number*. This information is necessary for **EST** files. Phone numbers will not be published, if so requested. All ad requests received prior to the above date will be processed as received. **Editor.**

## Wanted:

Schematic/information for old Shenendoah Five, Henry Field radio. Will make it worth your time. *Wayne Burmahl, 12607 E. McCoy St., Independence, MO 64055.*

Schematic/service manual for Farfisa Sabre Reverb-1 amplifier used with Farfisa Compact Duo. Will buy or copy and return at my expense. *Dan Graziadei, Stereo Service Center, 227 5th Ave., Pelham, NY 10803.*

Drive wheel for old Zenith stereo, EVG No. 1499-37. *William Blankinship, Blankinship TV, 1216 N. Main, Rusk, TX 75785; 214-683-5070.*

Sony No. 1-222-235 volume control W/switch for KV-1210U television. *Charles T. Huth, 229 Melmore St., Tiffin, OH 44883.*

Loan of manual for Heathkit oscillograph 10-104 so that I can copy needed information to repair my scope. Will return promptly. *Charlie Martel, 95 Bay State Road, Belmont, MA 02178.*

GE radio transformer, catalog No. RT-5958, for clock radio, GE model C-4390A. Will buy. *Frank Massi, 714 Walnut Drive, Apt. 310, Darien, IL 60559.*

Information about Seville model SC1382 color television. *Jorge Miranda, Miranda Repair Shop, 4911 Murphy Place, West New York, NJ 07093.*

Service manual for B&K model 1431 oscilloscope. Will buy or copy and return. *George Demaris, 7387 Pershing Ave., Orlando, FL 32822.*

Service information for the following—Unicom Electronics power supply, model PS11R; Tandy 64K Color Computer II, model 26-3127; EMP/GTS manual Mini Modem, model MM-101 (manufactured by Elec and Eltec Company, Hong Kong); Heathkit oscilloscope calibrator, model IG-4505; Leader RF signal generator, model LSG-11; Garrard turntable, model Lab 95B; Johnson Messenger CB, model 323; Apple IIe Pro System Duo-Disk Imager/Printer Monitor II; Icom model 735 ham transceiver. Will purchase or copy, my cost. *Mike Adams, Haney Vo-Tech Center, 8016 Hwy 77, Panama City, FL 32405; 904-769-2191.*

Please state price and/or condition in correspondence for the following—two transistors, MRF 455A; one antenna tuner, MFJ 962, 949C, 941D or 989; five tubes, No. 7868; ten lamps, No. 12 6V for Bogen PA amps; one each band-switch for Panasonic RF 2800 receiver, No. RSR 98W or equivalent; one printer and disk drive for Tandy Color Computer II, model 26-3127; one each Z-80/CPM and modem board for Apple IIe ProSystem. *Mike Adams, Haney Vo-Tech Center, 3016 Hwy 77, Panama City, FL 32405; 904-769-2191.*

TV, VCR parts, modules, service manuals and test equipment—only new or excellent condition components; books, publications and troubleshooting guides for televisions and related electronics equipment. *Tim Rowell, 1200 Barton St., Johnson City, TN 37601.*

Two timing wheel support assemblies for Accutrax +6 (BSR) phono No. PN B114235. Will consider buying junker. Pay any fair price. *TV Central, 870 Pio Nono Ave., Macon, GA 31204; 912-743-1451.*

Flyback transformer for Zenith model No. T2585p, part No. 95-3243-02. Zenith says N.L.A. *Tektronics, 17 W. Granada Blvd., Ormand Beach, FL 32074; 904-672-1175.*

## For Sale

Hickok Universal TV-FM alignment signal generator, model 610A, with manuals, good condition. \$75; Philco wideband oscillator amplifier, model 8300, good condition. \$10; Rider service manual, volume 16, \$15; Supreme radio service manual (1926-1938), Supreme radio service manual (1941), \$5 each; Sams Photofact sets No. 69 through No. 496, 75¢ each or all 275 sets for \$150, or best offer; Sams record changer service manuals, CM-2 through CM-9, RC-11 and RC-12, \$2 each or all 10 manuals for \$15. All prices plus shipping. *John Brouzakis, 247 Valley Circle, Charleroi, PA 15022; 412-483-3072.*

Sams Photofact sets, No. 1224 through No. 1475, complete \$250; Sylvania CK1500X Chek-A-Color test jig with over 75 adapters, already modified for up to 38kV testing, excellent condition. \$250; Castle Mezzar FSM-V VHF field-strength meter, Sencore B124 battery eliminator and Sencore B156 7-in-1 dc bias supply, all three items in excellent condition, \$90. Instructions with everything. All prices plus shipping. *Baros TV Service, 6113 Isleta Blvd. SW, Albuquerque, NM 87105; 505-877-5688.*

Sencore—VA62 video analyzer, VC63 VCR analyzer and NT64 NTSC pattern generator, \$2,800 for all three; Diehl Mark VI, \$350; CR70, \$750; LC53, \$750. Will sell package for \$4,300. All equipment like new, with leads and manuals. VA62 and LC53 used once; all other units, unused. Illness forces sale. *J. Collins, 11 Michael St., Woodcliff Lake, NJ 07675; 201-391-8425.*

Hewlett-Packard model AR120 oscilloscope, with manual on fiche; Beckman/Berkley Eput meter, model 7150, 5A2 scope CRT in box. Best offers. Other equipment available. *Kenneth Morvant, Route 4, Box 1290, Abbeville, LA 70510; 318-643-6867.*

Sencore—SC61, VA62, VC63, NT64, CR70, LC53, PR57, TF46—with all accessories, one-half of *new* prices; Sams Photofact folders No. 1200 through No. 2172, \$1,000; No. 2299 through No. 2480, \$500. *C. Hugh Harrell, P.O. Box 6691, Newport News, VA 23606; 804-877-7915.*

TV parts from Admiral 1M30, RCA CTC40P, Sears 528.41940 and 528.41950, Zenith 25CC50 and MGA 19-inch console. Picture tube from RCA 19VLNP22, with yoke, used two months. Many other chassis on hand. *D.J. Ajjala, 50 Fir Circle, Babbitt, MN 55706.*

Sencore SG165 AM-FM stereo analyzer, \$545; Sencore VA62 video analyzer, with VC63 VCR test accessory, \$2,095. Equipment in excellent condition, complete with manuals and probes. *John's TV, 34 Hillside Ave., Soudertown, PA 18964; 215-721-1563.*

Sencore SG165 AM-FM stereo analyzer, like-new condition, with test leads and service manual, \$250, cashier's check only. *John Schultz, 3611 Orchard Road, Quincy, IL 62301; 217-224-8227.*

B&K 820 digital capacitance meter, \$95; Precision E-200C signal generator, \$55; B&K 666 Dynajet tube tester, \$65. All mint condition, all prices plus shipping. *Ted Youngman, 2225 Vigo St., Lake Station, IN 46405.*

Heathkit IT-5230 CRT tester and rejuvenator, \$50; Knight tube tester, model KG-600B, \$35. Precision signal generator (two available), model E200, \$40 each; B&K model 667 tube tester, \$35; Sprague Jud Williams curve tracer, model A, \$50; Roberts tape recorder, model 771X, \$100. *Ralph Dorrough, 117 Pecan St., Terrell, TX 75160; 214-563-7105.*

Argon discharge tubes, Sylvania type R-4410 and type S-501, used to discharge HV capacitors through magnetostriction sounding heads, \$6 each; 100W ferrule-type resistors, 20k $\Omega$ , \$3.50 each. Twelve each available; items no longer in production. Prices do not include shipping; send shipping instructions with M.O. *Unitronix, P.O. Box 247, Galveston, TX 77553-0247; 409-763-2207.*

Sony 13-inch monochrome monitor, model CVM131, \$50; Conrac 8-inch monochrome monitor, \$35; Texas Instruments model Silent 700 printer, with cable and paper, \$35. Hewlett-Packard 130C oscilloscope, \$200; 202A low frequency function generator, \$60; 650A test oscillator, \$60; 400H VTVM, \$60; 2401B integrating digital voltmeter, \$200; Tektronix RM529 TV waveform monitor, \$150; 180A time mark generator, \$85; 3B3 time base plug-in, \$100; Fluke 8300A digital voltmeter, \$400. All this test equipment works OK. Include \$12 to help pay shipping. *Fred Jones, P.O. Box 702, Niceville, FL 32578; 904-678-1803.*

B&W picture tubes—19DUP4, 19CUP4, 19BLP4, 17DA/17DR/19AB/21EV, 21FDPA. All new, \$10 each. Price does not include shipping. *Ray's TV, 4821 East View Drive, New Orleans, LA 70126; 504-246-6205.*

SAT-250 audio dummy load, 2-channel/250W per channel, 8 $\Omega$  500W, 4 $\Omega$ . Excellent. \$70, we ship. *Dan's Radio-TV, 866 Cy Ave, Casper, WY 82601.*

PF Reporter magazines, 50¢ each; Sams Photofacts, \$1 each. Send s.a.s.e. for list. *George Otto, 1045 Magnolia Ave., Beaumont, TX 77701.*

Xerox copies on original factory-service manuals for Zenith, Admiral and Motorola color television. Literature on transistor radios, auto radios, 8-tracks, portable cassette players and turntables—too many to list. Send s.a.s.e. with your needs. *Kenneth L. Miron, 401 E. San Pedro Ave., Perry, FL 32347; 904-584-2116.*

Panasonic parts, large quantity, older, also used for Bradford. Parts are for televisions, tape recorders and stereos; part numbers, model numbers and descriptions needed. Send s.a.s.e. with your needs; I will return prices. *T&T Electronics, 200 Main St., Williamstown, MA 01267.*

**EST**



## PLEASE NOTE

# SYMCURES and T.TIPS

Beginning in January, ES&T will pay the following rates for reader-submitted items accepted for publication:

**SYMCURE** per page - \$60

**TROUBLESHOOTING  
TIPS** - \$25 each

If you have solved one or more difficult servicing problems, share these unusual experiences with other ES&T subscribers.

Write for guidelines.  
**ELECTRONIC SERVICING &  
TECHNOLOGY**  
P.O. Box 12901,  
Overland Park, KS 66212

## Acu-Min® Precision Miniature Tools for Industry

- ⊖ Slotted Screwdrivers
- ⊕ Cross Recess Drivers
- English Hex Drivers
- Metric Hex Drivers
- Open End Wrenches
- Socket/Nut Drivers
- Spline Drivers
- ⊖ Tweezers

# Precision Miniature Tools

For Electronics Professionals Worldwide



**PLUS** An all new line-up of high quality Precision Measuring Tools, including micrometers, calipers, dial indicators, scribers and more.

1-800-223-9036  
Sales & Customer Service  
401-885-0911  
In Rhode Island and Alaska

Over 400 Precision Products  
in our NEW Catalog.  
Call now for your copy.

**Moody Tools, Inc.**  
42-60 Crompton Avenue  
East Greenwich, RI 02818

Circle (35) on Reply Card

## Classified

Advertising rates in the Classified Section are 85 cents per word, each insertion, and must be accompanied by payment to insure publications.

Each initial or abbreviation counts a full word.

Minimum classified charge is \$20.00.

For ads on which replies are sent to us for forwarding (blind ads), there is an additional charge of \$30.00 per insertion to cover department number, processing of replies, and mailing costs.

Classified columns are not open to advertising of any products regularly produced by manufacturers unless used and no longer owned by the manufacturer or distributor.

### FOR SALE

**AUTOMOBILE RADIO** and tape replacement parts. Delco, Chrysler, Philco-Ford, Motorola, Panasonic and many others. Large inventory. Laran Electronics, Inc., 3768 Boston Road, Bronx, NY 10469. (212) 881-9600. National (800) 223-8314, NY State (800) 446-4430. 1-85-tfn

**PHOTOFACTS:** Individual folders #1 to #1400 \$3.00. Above #1400 \$5.00. Sent same day first-class postpaid. Loeb, 414 Chestnut Lane, East Meadow, NY 11554. 4-87-6t

**SERVICE MANUALS.** Large Shop has 18 yr. collection of duplicates. All original manufacturer. All new. Audio \$2.00, video \$5.00. Send SASE for list. Tape Recorder Clinic; 4850 E. Speedway; Tucson, Arizona 85712. 11-86-tfn

**ELECTRONICS PARTS** 10c on the dollar! \$50.00 samples \$5 postpaid. Free Bargain Catalog! Dependable TV, Box 1645 C'sted, St. Colix, V.I., U.S.A. 00820. 7-87-2t

**COMPLETE VCR TEST SHOP:** Sencore SC61 Wave form analyzer, VA62 video analyzer, VC63 VCR head test acc, NTSC pattern generator, PR57 powerite Isolation transf. Tentelometer tape tension gauge, Tentel VHS spindle height gauge, Tentel head protrusion gauge, with S1 stand, Zenith torque gauge. Call (414) 835-1793. 7-87-1t

**VCR REPAIR SOLUTIONS FOR VHS MODELS.** Volume I—150 Symptoms and cures—\$11.95. Volume II—\$11.95. All 300, \$19.95. Eagle Electronics, 52053 Locks Lane, Granger, IN 46530. 7-87-6t

**SERVICE MANUALS:** Most major brands of HiFi Component service manuals. 1960's thru 1985, approx. 4500 manuals, \$2000.00 for the lot. Celetronics 1473 12th St., Los Osos, Ca. 93402. 7-87-1t

**MUST LIQUIDATE** 1986 Sencore test equipment, SC61 wave form analyzer, 1VC63 VCR test accessory, 1 PR57 variable isolation transformer; 1 LC53 cap/coll analyzer; 1VA62 universal video analyzer; 1 NT64 pattern generator. Original cost—\$9,000.00, asking \$4,000.00. Almost brand new. Call 215-678-4136 after 7 pm. 7-87-1t

**TV/VCR "TUFF TIPS"** listed by mfg. and model. Over 200 unique tips. Send \$5.95 for TV, \$6.95 for VCR or \$10.95 for TV/VCR listing to: Tech Cures, 4825 Fredericksburg Road, San Antonio, Texas 78229. 7-87-2t

**TV TROUBLESHOOTING.** Over 130 schematic ILLUSTRATED problems-solutions of difficult repairs. Also, 12 steps to easier TV repair, 25 pages \$12.00. Remarkable diagnostic tool. Determine operation of high voltage circuits every time, no mistakes. \$5.00. Jones, Box 702, Niceville, Fla. 32578 7-87-3t

**TV/VCR FAILURE HISTORIES**—Multiple cures for most problem areas. Send \$6.95 with mfg. and model number to Tech Cures, 4825 Fredericksburg Road, San Antonio, Texas 78229. Money will be refunded with free sample. If model is not on database. 7-87-2t

**DIEHL MARK III SCANNER**, new, manual included, \$250, shipping paid. Jones, Box 702, Niceville, FL 32578. 7-87-3t

### BUSINESS OPPORTUNITIES

**T.V. SALES & SERVICE.** Well established business located northern Virginia. Owner retiring and will help with financing. Call 703-972-7027 after 7:00 p.m. EST. 6/85-tfn

**ELECTRONIC REPAIR**, inventory & equipment. 11 years at same location. Small recreational town in Idaho. Owner wishes to retire. \$15,000. 208-756-2916, Box 488, Salmon, Id. 83467. 5-87-3t

**T.V. SALES & SERVICE.** Top quality shop. Fully equip in Miramar, Florida. Unlimited potential for right party. (305) 961-1011. 7-87-1t

**TV-AUDIO-VIDEO SERVICE & SALES** in sunny Florida. Owner retiring after 13 years. 1400 sq. ft. building in excellent location. Over \$20k inventory and equipment. Nearly complete Sams file. \$90k negotiable. Flori-Day Electronics—44 Ave. E—Apalachicola, FL 32320. (904) 653-9657. 7-87-1t

**AUDIO-VIDEO REPAIR SHOP.** Largest repair shop in northern California, north of Santa Rosa; serving 3 counties. Authorized warranty for 20 manufacturers; commercial accounts. \$65k. 266 E. Smith St., Ukiah, CA 95482. 7-87-1t

**COMPUTER AND TV SALES** and service business in Colorado mountains. Only computer store in city. Inventory, at cost, approx. \$40,000. Selling for \$25,000. Great opportunity in fabulous area. Retiring owner will help. 1-303-641-0555 days, -4678 eves. 7-87-1t

### EDUCATION

**CABLE TV TRAINING**—Training in Cable Television Technology. Learn construction, installation, and maintenance. Cable Correspondence Courses, Inc., P.O. Box 1319, St. Charles, MO 63302. 7-87-tfn

### HELP WANTED

**VIDEO/AUDIO technician** needed. Top pay and benefits for well trained and experienced technicians who are expert with consumer TV and audio equipment. Training by manufacturers such as: Sony, Hitachi, RCA, Panasonic, etc. are necessary for job experience. Write or call: Atlantic Electronics, Inc., 1232 NE 26th St., Ft. Lauderdale, FL 33305, 305-564-8274 (10 AM 6:30 PM). Ask for Dave or Joe. 06-86-tfn



## HELP WANTED (CONT.)

**CAMERA-VIDEO Technicians** needed. Top pay and benefits for well trained and experienced technicians who are expert with consumer and/or industrial cameras and VCR's. Training by manufacturers such as Sony, Hitachi, Panasonic, etc., are necessary for job experience. Come to sunny Florida and enjoy your work & leisure time. Write or call ATLANTIC ELECTRONICS INC., 1232 NE 26th St., Ft. Lauderdale, FL 33305. (305) 564-8274 10 AM to 6:30 PM. Ask for Dave or Joe. 8-85-tfn

**ELECTRONIC TECHNICIANS** - Part time for field service and preventative maintenance. Openings nationwide. Must have own transportation, flexible hours, and some equipment. \$15.00 per hour. Send Resume to Field Service, Best Power Technology, P.O. Box 280, Necedah, WI 54646. 6-87-2t

**SERVICE TECHNICIANS** Northwest's leading communications contractor is looking for qualified service technicians for its Seattle office. Applicants should be experienced in professional audio, telephone, nurses call, C.C.T.V., M.A.T.V., and school communication systems. Qualified applicants should forward their resumes in confidence to: ELECTROCOM 6815 216th Street SW, Lynnwood, Washington 98036, (206) 774-6600. An equal opportunity employer. 7-87-1t

## SERVICES

**TV TUNER REBUILDING:** UHF, VHF, Cable ready. Electronic varactor or mechanical, any make. One year warranty. \$14.95 plus major parts & shipping. ROCHESTER TUNER SERVICE, 25 HOWARD RD., ROCHESTER, N.Y. 14606 (716) 647-9180. 7-87-1t

**TELEVISION TUNER REBUILDING,** all makes & models. 24-hour turnaround, one year limited warranty. Competitive pricing. Contact: Electrodyn, 917 South Rogers St., Bloomington, In. 47401. Telephone: 812-334-1023. 6-87-2t

**TVRO EQUIPMENT REPAIR,** satellite receivers, antenna actuators and down converters. 72-hour turnaround, 90-day limited warranty. Contact: Electrodyn, 917 South Rogers St., Bloomington, In. 47401. Telephone: 812-334-1023. 6-87-2t

**VCR REPAIR,** all makes and models. 72-hour turnaround, 90-day limited warranty. Contact: Electrodyn, 917 South Rogers St., Bloomington, IN 47401. Telephone: 812-334-1023. 6-87-2t

## WANTED

**WANTED:** Good used Huntron Tracker. Call with Price, Condition, Age and Model. Dick Scott, (206) 943-1393. 7-87-1t

# Advertisers' Index

	Page Number	Reader Service Number	Advertiser Hotline
Accutest Instruments, Inc.	68	32	609/259-0460
Atrix, Inc.	3	36	800/222-6154
B&K Precision Dynascan Corp.	IBC	2	312/889-9087
Beckman Industrial Corp.	IFC, 11	1,34	714/671-4800
C + S Sales	27	12	800/292-7711
Chemtronics, Inc.	63	25	800/645-5244
Computer Service Center	55	18	602/889-8888
Contact East	59	22	800/225-5370
Cooks Inst. Elec. Engrg.	65	26	601/371-1351
Dandy Mfg. Co.	68	29	800/331-9658
ETA	65		
Fluke, John Mfg. Co., Inc.	5	3	800/227-3800
Hameg Inc.	21	9	516/883-3837
Hitachi Sales Corp. of America	17	8	516/921-7200
Iscet	63		817/921-9101
Jensen Tools Inc.	63	24	602/968-6231
Leader Instrument Corp.	7	4,5	514/337-9500
MCM Electronics	43	13	800/543-4330
Moody Tools	67	35	800/223-9036
NESDA	57,61		817/921-9061
Nu Data Corp.	61	23	201/842-5757
Projector Recorder Belt Corp.	68	28	800/558-9572
PTS Corp.	23	10	812/824-9331
RD/Portasol	65	27	703/323-8000
Sencore, Inc.	47,49	14,15	800/843-3338
Sencore, Inc.	51,53	16,17	800/843-3338
Simpson Electric Co.	9	6	312/687-2265
Spectrum 2000 Inc.	59	20	800/922-6333
Sperry Tech, Inc.	68	30	800/228-4338
Tektronix, Inc.	12A-12B,13	33	800/433-2323
Tentel	25	11	800/538-6894
Tronix, Inc.	57	19	313/939-4710
U.S. Instrument Rentals	15	7	800/824-2873
Unity Electronics	68	31	201/351-4200
Zenith	BC		

**PERSONALIZED 24-HOUR SERVICE ON OVER 10,000 ELECTRONIC COMPONENTS & PRODUCTS...**

CALL TOLL FREE

1-800-558-9572 IN WIS 1-800-242-9553  
24 HOUR ORDERING: FAX: 414/473-4727

**PRB**  
PROJECTOR-RECORDER BELT CORP.

P.O. Box 176 • Whitewater, WI 53190  
TLX 4994411 PRBUSA

Circle (28) on Reply Card

### A MUST FOR THE TV TECHNICIAN

**UNIVERSAL CRT ADAPTER.** Don't buy another socket for your CRT Tester! Join 10,000 satisfied buyers & WIN the Socket War! GUARANTEED to fit your tester. Test/clean/restore ALL Color, B/W, Projection. \$63.95ppd w/Setup book, Visa, MC, COD.

1-800-331-9658

DANDY MFG. CO.

2323 Gibson, Muskogee, Oklahoma 74403

Circle (29) on Reply Card

Tech's Guide To Pricing

### "Tech's Guide To Pricing"

updated new 5th edition...a framework for setting rates that apply to Hi-Tech products...a formula that guarantees SUCCESS!

Call Toll Free for details  
1-800-228-4338 8/5 CST

Circle (30) on Reply Card

### ELECTRONIC TEST EQUIPMENT Reduced Prices - High Quality

Custom Reconditioned & New Products  
FREE CATALOG AVAILABLE  
Accutest Instruments, Inc.

CLARKSBURG, N. J. 08510  
(609) 259-0460 (NJ) or 1-800-524-0747

Circle (32) on Reply Card

**ELECTRONIC SERVICING & TECHNOLOGY** Volume 7, No. 7 (USPS 462-050) is published monthly by Intertec Publishing Corp., 9221 Quivira Road, P.O. Box 12901, Overland Park, KS 66212. Second Class Postage paid at Shawnee Mission, KS, and additional mailing offices. POSTMASTER: Send address changes to ELECTRONIC SERVICING & TECHNOLOGY, P.O. Box 12952, Overland Park, KS 66212-9981.

NEW 20-PAGE CATALOG FREE

### 7 MILLION TUBES

Includes all current, obsolete, antique, hard-to-find receiving, transmitting, industrial, radio/TV types. **LOWEST PRICES.** Major brands in stock.

Unity Electronics Dept. E  
P.O. Box 213, Elizabeth, N.J. 07206



Circle (31) on Reply Card

### ADVERTISING SALES OFFICES

**ELECTRONIC**  
Servicing & Technology

#### ALL U.S. TERRITORIES

Greg Garrison, Sales Manager  
P.O. Box 12901  
Overland Park, KS 66212  
Phone: (913) 888-4664



# "I thought a DSO that did all that would cost a fortune..."



"Isn't that the new B&K-PRECISION 2520 digital storage oscilloscope?"

"Right, Jim . . . It's quite a performer, with dual-channel real-time and digital operations, 2 megasample per second sampling and 1024 x 8 bit per channel storage. It's even got an analog output for a plotter."

"Those specs sound pretty good, Bob, but why a DSO? Won't your analog scope do the job?"

"This DSO really opens new doors . . . For instance . . ."

Let's say I need to look at a non-repetitive waveform . . ."




"Like our mechanical stress tests?"

"Exactly . . . or a one-shot pulse, or even a power line glitch . . . Looking at those on a regular scope is darn near impossible, even with a camera. On the 2520, I can pretrigger at 0%, 25%, 75%, or 100%. When the event pops, it's frozen on the screen. I can also compare test results from one event to the next."



"I see, Bob. Freeze one event on one channel, look at the new events on the second channel, and zoom in for a closer look. What other jobs will it simplify?"

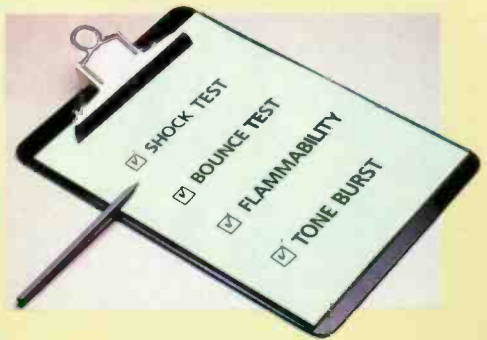"Here are just a few ideas: Shock testing — without trigger data loss; Bounce testing on switches and breakers; capturing a PCM tone burst; and flammability tests using two thermocouples . . . Our bio lab can even use it for



nerve response tests . . . Best of all the 2520 costs just \$1990."

"\$1990? I thought a DSO that did all that would cost a fortune. Where do I get mine?"

You can get your own 2520 from your local B&K-PRECISION distributor. Also ask about the new 2521 with automatic time and voltage measurements and optional 2502 waveform processor. For complete details and a free list of DSO applications contact:



**BK PRECISION**

DYNASCAN CORPORATION


6460 W. Cortland St. • Chicago, IL 60635  
312-889-8870

International Sales, 6460 W. Cortland St., Chicago, IL 60635

Canadian Sales, Atlas Electronics, Ontario

South and Central American Sales, Empire Exporters, Plainview, NY 11803

Circle 72 on Reply Card

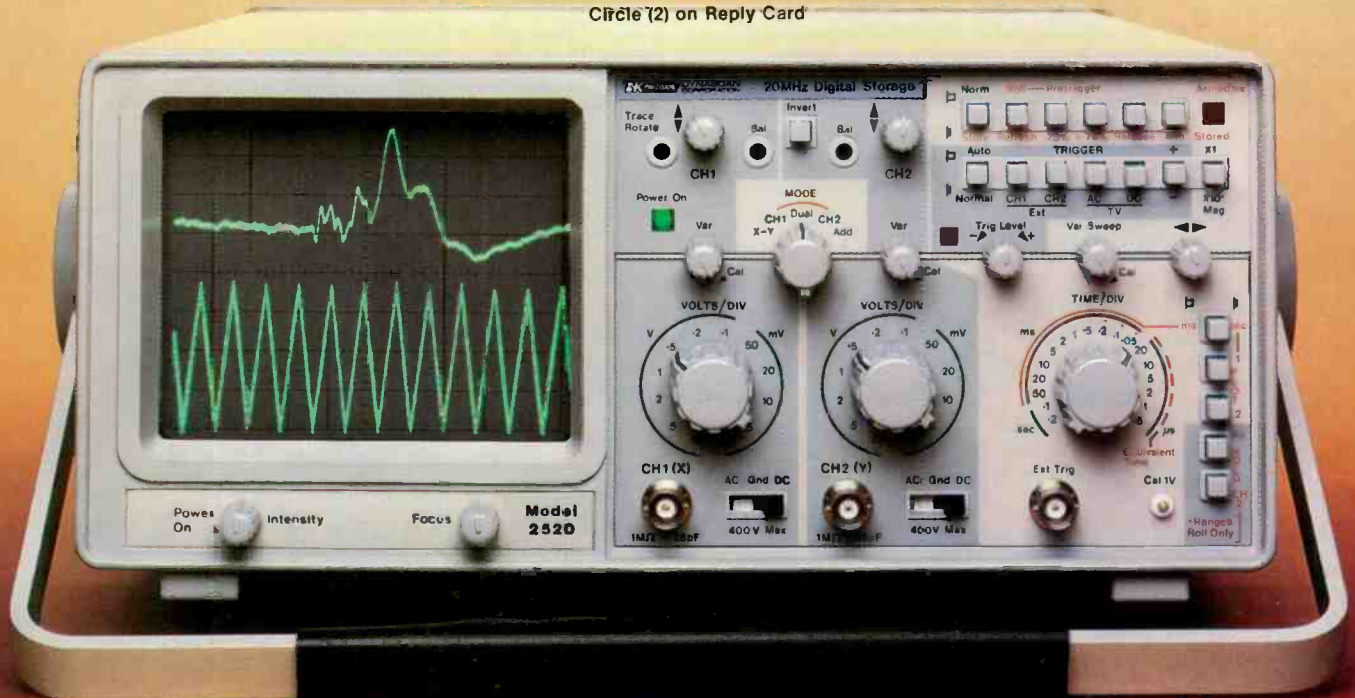



# ZENITH


# VIDEO ACCESSORY HEADQUARTERS



# NOW! SO YOU CAN MAKE IT BIG SELLING VIDEO ACCESSORIES!

## NEW!

## NEW!

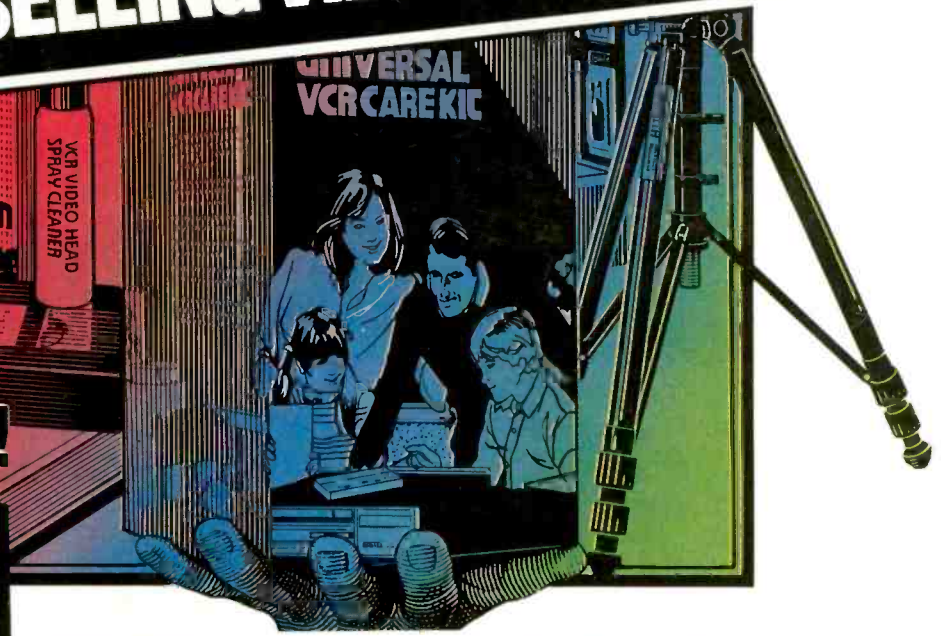

## ZENITH VCR HEAD CLEANERS FOR ALL VHS MAKES AND MODELS INCLUDING CAMCORDERS... EVEN VHS-C CAMCORDERS!

Call your Zenith distributor's Accessory Sales Manager with your order now... and see for yourself how quickly the ready-made selling power of the Zenith name helps you make it big in video accessories.