

The Transistor's 10th Birthday — Special Issue

MAY 1958
K

Radio-Electronics

TELEVISION • SERVICING • HIGH FIDELITY

HUGO GERNSBACK, Editor

**SPECIAL
TRANSISTOR
FEATURES**

Plus:

A VTVM
Calibrator



More About
Cathode Followers



Build a 6-Band
Transistor Portable



Birth of a
Transistor ▶

(See page 4)

35c

U.S. and Canada




NORELCO[®] presents

the world's second finest*
pickup cartridge



a new MAGNETO-DYNAMIC design by Philips of the Netherlands

*The world's finest pickup cartridge is carefully guarded at the great Philips audio research center in Eindhoven, the Netherlands. It is the laboratory prototype of the new NORELCO "Magneto-Dynamic" pickup cartridges—a special pilot model hand-built to zero tolerances by Europe's most renowned electro-acoustic research team. This reference standard must, of necessity, be a shade superior to the production models, which are constantly quality-controlled against it. It is an indispensable laboratory tool that obviously cannot be sold. But the world's **second finest** pickup cartridge—meaning any and every NORELCO production model—can be and is sold by leading hi-fi outlets everywhere, for the astonishingly low price of \$29.95.

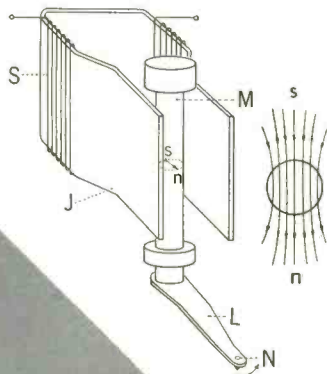


THE MAGNETO-DYNAMIC PRINCIPLE—The armature is a thin rod M, 1/32" in diameter and approximately 1/2" long, made of "Ferroxdure," a special high-coercivity ferrite material developed by Philips. This armature is magnetized perpendicularly to its axis (s — n) and is rotated about the axis by the transverse vibrations of the cantilever stylus bar L, which is driven by the 1-mil diamond stylus N. This rotation induces a varying flux in the core J, which results in the development of a corresponding AC voltage in the coil S. The inherent advantages of the system include very high compliance (more than 5×10^{-6} cm/dyne), very low dynamic mass (2.8 milligrams), high output (35 millivolts at 10 cm/sec), low stylus force (5 grams), and vanishingly low distortion. Frequency response is flat within 2 db from 10 to 20,000 cps.



NORTH AMERICAN PHILIPS CO., INC.
High Fidelity Products Division, Dept. REC2
230 Duffy Avenue, Hicksville, L. I., N. Y.

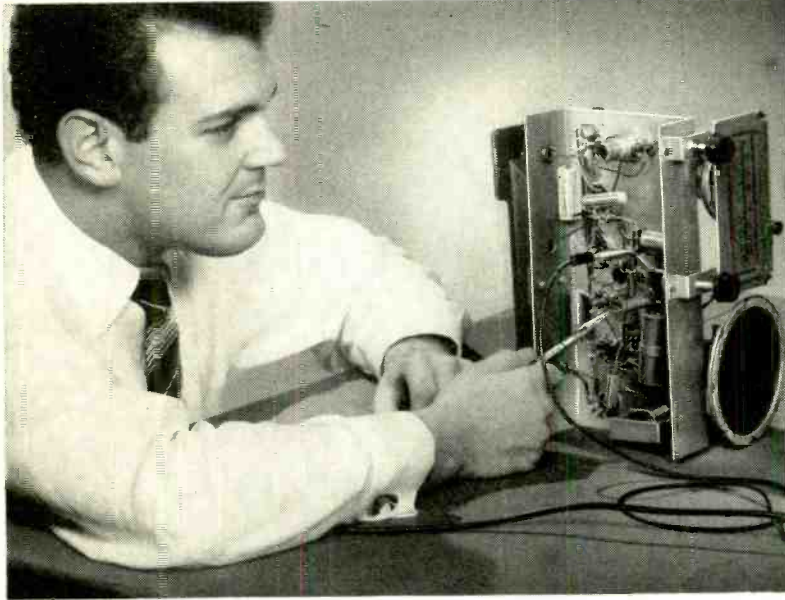For a Successful Career in Radio-Television



Train at Home in Spare Time with N. R. I. **OLDEST and LARGEST** Home Study Radio-Television School

N.R.I. Trained These Men

ENGINEER STATION WHPE
 "Thanks to NRI, I operated a successful Radio repair shop. Now I am an engineer for WHPE." VAN W. WORKMAN, HIGH POINT, NORTH CAROLINA



QUICK SPARE TIME CASH
 "Knew nothing about Radio-TV when I enrolled. After 15 lessons started repairing sets. My future looks bright." DONALD B. ACKERMAN, MINNEAPOLIS, MINNESOTA



HAS OWN TV BUSINESS
 "Quit my job to do Television work full time. I love it and do all right financially." WILLIAM F. KLINE, CINCINNATI, OHIO



Prosperous Fast Growing Industry Offers You GOOD PAY-BRIGHT FUTURE-SUCCESS

It's the trained man who gets ahead—gets the better job, drives a better car, lives in a better home, is respected for what he knows and can do. For a job with a future—find out how you can train at home for Radio-Television.

TODAY'S OPPORTUNITY FIELD

Training PLUS OPPORTUNITY is the ideal combination for success. And today's OPPORTUNITY field is Radio-Television. Over 125 million home Radios plus 30 million sets in cars, plus 40 million TV sets mean big money for trained Technicians. More than 4,000 Radio and TV broadcasting stations offer interesting and important positions. Color television, portable TV sets, Hi-Fi, assure future growth. Find out about NRI. Since 1914—for more than 40 years—NRI has been training ambitious men

at home in spare time for Radio-TV. With NRI 50-50 method, you study basic principles AND learn by practicing with actual equipment NRI furnishes. You learn with your hands and your head. You get dependable training, backed up by the reputation of the oldest and largest home study Radio-TV school.

ADD TO YOUR INCOME SOON \$10-\$15 A WEEK IN SPARE TIME

Soon after enrolling many start earning extra money fixing sets. Many open their own full time Radio-TV shops after getting NRI Diploma. MAIL COUPON. Get FREE Sample Lesson and 64-page Catalog showing equipment supplied, outlines of courses, opportunities in Radio-TV. Price is low—terms easy. Address: NATIONAL RADIO INSTITUTE, Dept. 8EF, Washington 16, D. C.

You Learn Servicing—Broadcasting at Home—By Practicing with Kits N.R.I. Sends



Nothing takes the place of practical experience. That's why NRI training is Learning-by-Doing. With Servicing Course you build Radio shown at top and other equipment. With Communications Course you build Transmitters at left and other equipment. Catalog shows all equipment you get.

Available To **VETERANS** Under G.I. Bills



SAMPLE LESSON AND CATALOG FREE

MAIL COUPON TODAY

National Radio Institute
 Dept. 8EF, Washington 16, D. C.

Mail me Sample Lesson and 64-Page Catalog FREE. (No salesman will call. Please write plainly.)

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

ACCREDITED MEMBER, NATIONAL HOME STUDY COUNCIL



MAY, 1958

Radio-Electronics

GERNSBACK PUBLICATIONS

Formerly RADIO-CRAFT ■ Incorporating SHORT WAVE CRAFT ■ TELEVISION NEWS ■ RADIO & TELEVISION

EDITORIAL

33 Transistor Trends—Hugo Gernsback

SPECIAL FEATURES

- 34 Ten Years of Transistors—R. M. Ryder
- 38 Transistors—Past, Present, Future—George R. Spencer
- 42 More Jobs for Semiconductors—Paul Penfield, Jr.
- 43 Transistor Bookshelf—Rufus P. Turner

AUDIO—HIGH FIDELITY

- ✓ 45 The Transistor "Fifth"—I. Queen
- 46 New Discs and Stereo Tapes—Reviewed by Chester Santon
- 48 Audio Filter Has Variable Bandpass—Dr. Carl F. Rothe
- ✓ 50 More About the Cathode Follower—Norman H. Crowhurst
- 54 Final Touchup for Your Amplifier—Harold Reed

ELECTRONICS

- 57 Using the Varicap—Rufus P. Turner
- 60 Tecnetron—Competitor to the Transistor?—E. Aisberg
- ✓ 62 Train Your Fan With Transistors—James A. McRoberts
- 64 Transistor Dictionary—H. Barr

RADIO

- ✓ 83 6-Band Transistor Portable—J. E. Pugh, Jr.

TELEVISION

- 88 Transistors in the TV Set—Louis E. Garner, Jr.
- 96 TV Service Clinic—Conducted by Robert G. Middleton
- 107 Speaking of Dogs—Harry M. Layden

TEST INSTRUMENTS

- ✓ 109 Transistor Null Detector and Sensitive Indicator—Ted Ladd
- 116 Vtvm Calibrator—J. H. Sutton

- | | |
|----------------------------------|-------------------------------|
| 146 Books | 128 Patents |
| 141 Business and People | 131 Radio-Electronic Circuits |
| 145 Corrections | 144 Technical Literature |
| 10 Correspondence | 120 Technicians' News |
| 135 New Devices | 139 Technotes |
| 124 New Tubes and Semiconductors | 133 Try This One |
| 6 News Briefs | 127 50 Years Ago |

ON THE COVER

A single crystal of germanium is being formed as it is drawn slowly out of the pool of molten germanium in the white crucible. Parts of the copper-tubing induction-heating coil can be seen in the rear.

Color original courtesy
Texas Instruments, Inc.

Hugo Gernsback
.....Editor and Publisher
M. Harvey Gernsback
.....Editorial Director
Fred Shunaman
.....Managing Editor
Robert F. Scott
.....WZPWG, Technical Editor
Larry Steckler
.....Assistant Editor
I. Queen
.....Editorial Associate
Robert G. Middleton
.....Television Consultant
Elizabeth Stalcup
.....Production Manager
Cathy Cocozza
.....Advertising Production
Wm. Lyon McLaughlin
.....Tech. Illustration Director
Sol Ehrlich
.....Art Director
Fred Neinast
.....Staff Artist
Lee Robinson
.....General Manager
John J. Lamson
.....Sales Manager
G. Aliquo
.....Circulation Manager
Adam J. Smith
.....Director, Newsstand Sales
Robert Fallath
.....Promotion Manager



Average Paid Circulation
Over 195,000



RADIO-ELECTRONICS is indexed in *Applied Science & Technology Index* (Formerly *Industrial Arts Index*)

RADIO-ELECTRONICS, May, 1958, Vol. XXIX, No. 5. Published monthly at Mt. Morris, Ill., by Gernsback Publications, Inc. Second-class mail privileges authorized at Mt. Morris, Ill. Copyright 1958 by Gernsback Publications, Inc. All rights reserved under Universal, International and Pan-American Copyright Conventions.
SUBSCRIPTION RATES: U. S., U. S. possessions and Canada, \$4.00 for one year; \$7.00 for two years; \$9.00 for three years; single copies 50c. Pan-American countries \$4.50 for one year; \$8.00 for two years; \$10.50 for three years. All other countries \$5.00 a year; \$9.00 for two years; \$12.00 for three years.
SUBSCRIPTIONS: Address correspondence to Radio-Electronics, Subscription Dept., 404 N. Wesley Ave., Mt. Morris, Ill., or 154 West 14th St., New York 11, N. Y. When requesting a change of address, please furnish an address label from a recent issue. Allow one month for change of address.
GERNSBACK PUBLICATIONS, INC. Executive, Editorial and Advertising Offices, 154 West 14th St., New York 11, N. Y. Telephone ALgonquin 5-7755. Hugo Gernsback, Chairman of the Board; M. Harvey Gernsback, President; G. Aliquo, Secretary.
BRANCH ADVERTISING OFFICES and FOREIGN AGENTS listed on page 150.
POSTMASTER: If undeliverable, send Form 3579 to: RADIO-ELECTRONICS, 154 West 14th St., New York 11, N. Y.

*Trademark registered U. S. Pat. Office.

RADIO-ELECTRONICS

**GREATEST
ADVANCE IN
SHOP-METHOD
HOME TRAINING**

EARN MORE MONEY...GET INTO TELEVISION ELECTRONICS - RADIO

Learn ALL 8 PHASES in ONE MODERN HOME-STUDY COURSE
At Home - In Spare Time

YOU GET ALL THIS NEWEST PRACTICAL EQUIPMENT

- Parts to build a modern TV set, including all tubes plus a large screen Picture Tube
- Parts to build a powerful Superhet Receiver, standard broadcast and short wave
- Parts to conduct many experiments and build Continuity Checker, RF Oscillator, TV Circuits, Audio Oscillator, TRF Receiver, Signal Generator
- A Valuable Professional Multitester



**19 BIG KITS
YOURS TO KEEP**

YOUR NATIONAL SCHOOLS TELERAMA COURSE COVERS ALL 8 PHASES

- | | |
|------------------------------------|--------------------------------|
| 1. TELEVISION, INCLUDING COLOR TV | 5. PREPARATION FOR FCC LICENSE |
| 2. RADIO, FM AND AM | 6. AUTOMATION |
| 3. INDUSTRIAL ELECTRONICS | 7. RADAR AND MICRO WAVES |
| 4. SOUND RECORDING AND HI FIDELITY | 8. COMMUNICATIONS |

YOU ARE NEEDED IN THE TELEVISION-ELECTRONICS-RADIO INDUSTRY!
You can build a secure future for yourself if you get into Electronics NOW! Today's shortage of trained technicians creates tremendous opportunities. National Schools Shop-Method trained technicians are in constant and growing demand for high-pay jobs in Broadcasting and Communications, Electronic Research, Servicing and Repair, and many other branches.

Let National Schools, a Resident Technical School for over 50 years train you for today's unlimited opportunities in electronics! Our Shop-Method trains you to be a MASTER-TECHNICIAN. Completely up to date, developed by experienced instructors and engineers, your Telerama Course will teach you all phases of the industry quickly, clearly and correctly. You can master the most modern projects, such as Color TV, printed circuits - even prepare for FCC License without taking a special

course. You can handle sales, servicing, manufacturing, or make good money in your own business. SEND FOR FACTS TODAY!

EARN AS YOU LEARN. Many of our students earn their entire tuition and more in Spare Time jobs we show them how to do while learning.

YOU GET EVERYTHING YOU NEED - Clear, profusely illustrated lessons, shop-tested manuals, modern circuit diagrams, practical job projects - all the valuable equipment shown above

- many other materials and services
- consultation privilege with our qualified staff, and Graduate Employment Service. EVERYTHING YOU NEED for outstanding success in Electronics

RESIDENT TRAINING AT LOS ANGELES

If you wish to take your training in our Resident School at Los Angeles, the world's TV capital, start NOW in our big, modern Shops, Labs and Radio-TV Studios. Here you work with latest Electronic equipment - professionally installed - finest, most complete facilities offered by any school. Expert, friendly instructors. Personal attention. Graduate Employment Service. Help in finding home near school - and part time job while you learn. Check box in coupon for full information.



FREE! Fully illustrated "Career" Book in TV-Radio-Electronics. PLUS actual sample lesson - yours at no cost, no obligation. CLIP COUPON NOW... MAIL IT TODAY!



MEMBER



APPROVED FOR G.I. TRAINING
NATIONAL SCHOOLS

4000 S. FIGUEROA ST., LOS ANGELES 37, CALIF.

NATIONAL SCHOOLS

TECHNICAL TRADE TRAINING SINCE 1905
LOS ANGELES 37, CALIFORNIA

GET FAST SERVICE - MAIL NOW TO

NATIONAL SCHOOLS, DEPT. RG-58
4000 S. FIGUEROA ST.
LOS ANGELES 37, CALIF.

Rush free TV-Radio "Opportunity" Book and sample lesson. No salesman will call.

NAME _____ AGE _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

Check if interested ONLY in Resident School training at Los Angeles.
VETERANS: Give date of Discharge _____

News Briefs



SPACE GUIDANCE, Doppler navigation and coded communications are among the possible applications of the first portable maser oscillator, announced by the Polytechnic Research and Development Co. of Brooklyn, N. Y. The fundamental principles of the maser were described in **RADIO-ELECTRONICS**, June, 1955.

The 20-pound unit is a sealed, ammonia type oscillator which generates a 23.8701294-kmc signal. Its stability exceeds one part in a billion.

A device for recirculating ammonia back to its reservoir after 50 hours of operation eliminates the need for auxiliary pumping equipment. The high vacuum essential to the system is maintained by using a getter-ion tube, which flashes periodically to remove the residual and rare gasses. Stability by the resonant cavity is assured by a temperature control system.

FIVE NEW TV STATIONS reinforce the nation's networks this month:

WETV, Atlanta, Ga.....	30
KTVU, Oakland, Calif.....	2
KDUH-TV, Hay Spring, Neb.....	4
WPBZ-TV, Lockhaven, Pa.....	32
WSUR-TV, Ponce, Puerto Rico.....	9

WETV is an educational station. WSUR-TV, Ponce's second TV station, is an affiliate of San Juan's WAPA-TV, channel 4.

Call letters have been amended:	
WECT, Wilmington, N. C.....	6
(formerly WMFD-TV)	
KOCO, Enid, Okla.....	5
(formerly KGEO-TV)	

Our March issue reported new call letters, WNEP-TV, for WARM-TV, Scranton, Pa., channel 16. WNEP-TV is the result of a corporate merger between WARM-TV and WILK-TV, Wilkes-Barre, Pa., channel 34. The latter station will temporarily remain on channel 34 as a satellite.

Our total of US operating stations is now up to 539 (444 vhf and 95 uhf). Of these, 31 are noncommercial.

RADAR NAVIGATORS are scheduled to go into operation in the New York Air Traffic Control Area. Made by the Decca Radar Navigator Co., London, England, the installation will be used initially by New York Airways helicopter service. However, it may develop into a test of the system to see if it can solve the air traffic-control problem.


The system provides area coverage particularly suited to helicopter service and does not confine pilots to main air lanes. The basic unit of one master and three slave stations, placed 70 miles apart, sends up a continuous pattern of

The Satellite Antenna with amazing rotating BALL— rotates 360° in every direction to mount anywhere on any car!

**MOUNTS TOP FENDER, SIDE FENDER,
TOP COWL, SIDE COWL, REAR DECK OR ROOF.**

- ★ Mounts easily, quickly from the outside. New, simplified split-washer mounting base twists easily into position beneath cowl. Reduces installation costs.
- ★ Triple chrome, 3 section mast adjusts to any desired angle. Length 25" to 57".
- ★ 48" Mylar 100% shielded, detachable cable.
- ★ Guaranteed in writing for the full life of the car.

Model **BT-1**

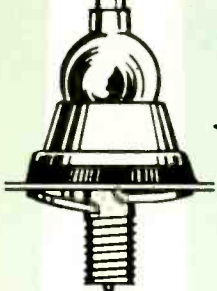

The TENNA Manufacturing Co.

7580 GARFIELD BLVD. • CLEVELAND 25, OHIO
World's largest maker of automobile antennas!

Look what's coming in

RADIO-ELECTRONICS


- Common Fallacies in Color TV Servicing
- Tape Recorder Test Adapter
- Rain and Humidity Alarm
- Five European Hi-Fi Amplifiers
- Streamlining the One-Man Shop
- Improving Your Small Receiver

The **JUNE** issue of **RADIO-ELECTRONICS** goes on sale May 22 at all better distributors and newsstands

SUBSCRIPTION RATES


1 Year \$4 2 Years \$7 3 Years \$9

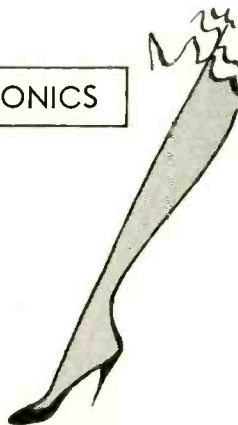RADIO-ELECTRONICS 154 West 14th Street New York, 11, N. Y.



For A Real OPPORTUNITY, Look Into

ELECTRONICS

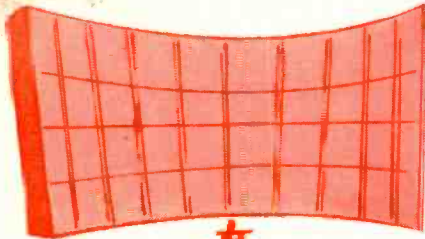

DeVry Tech can prepare you for a profitable future in many branches of Electronics from

RADAR to GUIDED MISSILES, etc.
No Previous Technical Experience Required!



Now that Electronics is so important in our daily lives...now that industry is moving so rapidly into Automation and Industrial Electronics, good job opportunities for the trained man never appeared brighter than they do today.

To prepare to enter the field of Electronics, one of the modern marvels of the 20th Century, you need no advanced education. Believe it or not, you don't need previous technical experience either.

Men 17 to 55, send coupon below for FREE facts! Learn how you may get ready to enter this fascinating, profitable field in your spare time at home or in day or evening classes in our well-equipped Chicago or Toronto laboratories.

CAN YOU DO IT?

Laborers, clerks, farmers, salesmen, men of nearly every calling have taken the DeVry Tech program and today have better jobs or Electronic service shops of their own — REAL PROOF of the effective training offered by DeVry Tech.



FREE EMPLOYMENT SERVICE

DeVry Tech's effective employment service is available to all graduates at no additional cost.



Send for FREE BOOKLET!

"Electronics and YOU" shows how you may take advantage of the opportunities in this fast-growing field.

Check These Opportunities In Electronics:

INDUSTRIAL ELECTRONICS



COMMUNICATIONS



AUTOMATION ELECTRONICS



COMPUTERS



TELEVISION



YOUR OWN SERVICE SHOP



DeVry Technical INSTITUTE

CHICAGO 41, ILL.

Formerly DeFOREST'S TRAINING, INC.
 Accredited Member of National Home Study Council

"One of North America's Foremost Electronics Training Centers"



MAIL TODAY FOR FREE FACTS

DeVry Technical Institute
 4141 Belmont Ave., Chicago 41, Ill., Dept. RE-5-O
 Please give me your FREE booklet, "Electronics and YOU," and tell me how I may prepare to enter one or more branches of Electronics as listed above.

Name _____ Age _____

PLEASE PRINT

Street _____ Apt. _____


City _____ Zone _____ State _____

Check here if subject to Military Training.
 DeVry Tech's Canadian Training Center is located at
 2043 626 Roselawn Avenue, Toronto 12, Ontario

Leading Set Makers
Specify Tung-Sol

High

IN PERFORMANCE

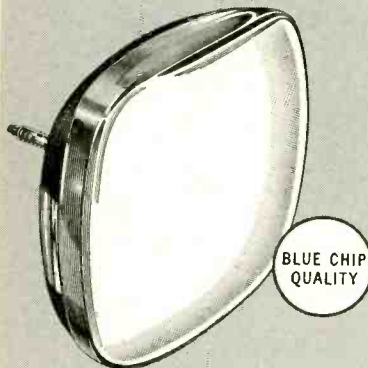

BLUE CHIP
QUALITY

Leading Independent
Service Dealers
Choose Tung-Sol

LOW

IN CALLBACKS



BLUE CHIP
QUALITY

TUNG-SOL®

Magic Mirror Aluminized
PICTURE TUBES
RECEIVING TUBES

ELECTRON TUBE DIVISION
TUNG-SOL ELECTRIC INC., NEWARK 4, N. J.

NEWS BRIEFS (Continued)

radio waves which gives the pilot a reference grid by which to navigate.

NEW STEREO DISC system was announced by CBS. Press time was too early to permit learning details, which were to be described at the Institute of Radio Engineers' convention in New York City, by Peter Goldmark, William Bachman and B. B. Bauer, but it was understood that it would resemble the Westrex system.

DEAF MAN HEARS AGAIN thanks to a combination of surgery and electronics. According to *Press Medicale* (Paris, France), when tumors blocking his ears were removed, the hearing structure was also destroyed. A miniature coil was imbedded in his ear, with one end connected to the hearing nerve. A separate unit containing a microphone, amplifier, and large coil is used as external equipment. Audio signals fed to the large coil induce electric currents in the coil attached to the hearing nerve.

The patient can now distinguish some words, although sounds he hears are said to be distorted and metallic.

AUTOMATIC FACTORIES of the future were foreshadowed in a recent demonstration of the *Digitape* electronically controlled metal-parts production line. The new technique was shown to a large press delegation by Hughes Aircraft Co. at Los Angeles.

The *Digitape* technique arranges electronically controlled machines to perform operations in sequence, thus turning out a complete part that may require several operations of different types. The battery of machines demonstrated consisted of a milling machine, a combination drill which alone permits selection of any of 20 drill sizes and a boring machine for larger holes.

The electronic portion of the system consists of computerlike elements using transistors and diodes, and is actuated by punched tape. The tape is automatically switched from machine to machine during the sequence of operations, so that work can be started on a new production run without waiting for all operations to be finished on the last piece of the old run.

This flexibility combined with automatic sequencing is precisely the new

and essential feature of this technique. Electronically controlled single machines have been used, and the complete automatic fabrication of a single part is possible by mechanical means, using a large number of machines, each performing a single operation. The new system has two main and immediate advantages. The first is its great flexibility, permitting it to perform a large number of operations without the expensive tooling up that at present makes short runs so expensive. Thus small numbers of parts or even a single experimental item may be made economically. The second is the great saving of time in fabricating small numbers of parts, which would normally progress very slowly through a machine shop. A third and very important advantage is that spare-parts inventories can be cut down drastically. Instead of holding a large stock of rarely called-for repair parts, the tape can be stored and a new part machined whenever needed.

Calendar of Events

Western Joint Computer Conference, May 6-8, Ambassador Hotel, Los Angeles, Calif.

National Aeronautical & Naval Electronics Conference, May 12-14, Dayton Biltmore Hotel, Dayton, Ohio.

Spring Assembly Meeting of Radio Technical Commission for Marine Services, May 13-15, Benjamin Franklin Hotel, Philadelphia, Pa.

1958 Electronic Parts Distributors Show, May 19-21, Conrad Hilton Hotel, Chicago, Ill. **RADIO-ELECTRONICS** and the **GERNSBACK LIBRARY** will exhibit in Room 601. (This is a closed show for manufacturers, representatives and distributors.)

EIA Conference on Maintainability of Electronic Equipment, May 27-28, University of Pennsylvania, Philadelphia, Pa.

Armed Forces Communications and Electronics Association's Show, June 4-6, Sheraton Park Hotel, Washington, D. C.


National Symposium on Production Techniques, June 5-6, Hotel New Yorker, New York, N. Y.

Southwest High Fidelity Show, June 6-8, Shamrock Hilton Hotel, Houston, Tex.

National Convention on Military Electronics, June 16-18, Sheraton Park Hotel, Washington, D. C.

French Electronic Components Show, June 20-26, 23 Rue de Lubeck, Paris.

END

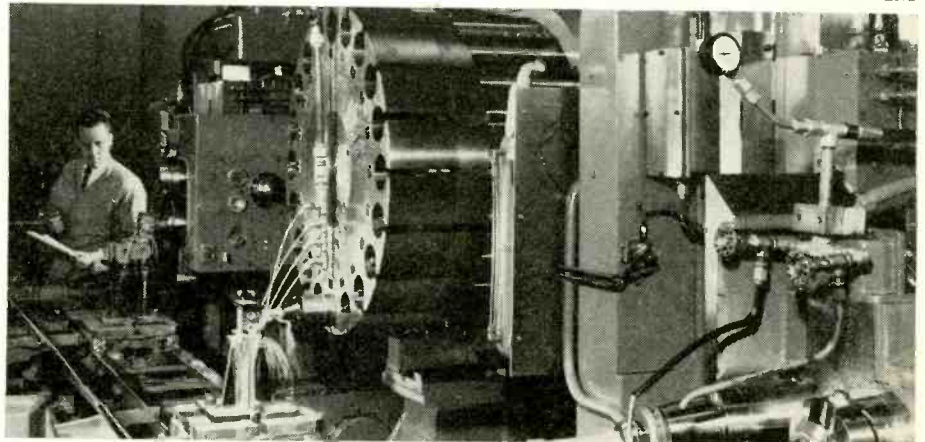

The electronically controlled production line. At left is the milling machine; center, the drill, and foreground, the boring machine.


FREE!

ALLIED'S 1958 CATALOG

404 value-packed PAGES

the only **COMPLETE** catalog for everything in electronics

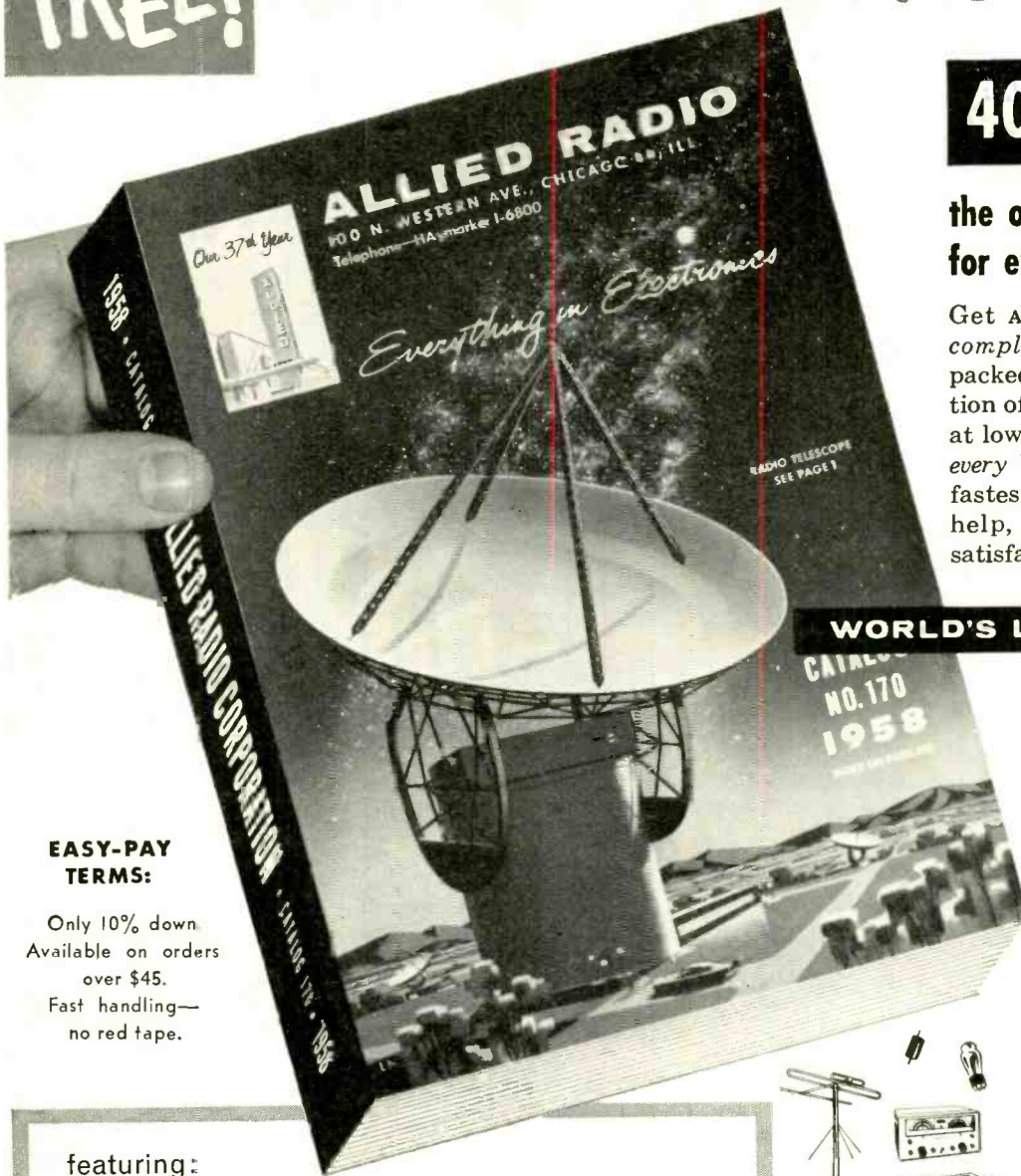Get ALLIED'S 1958 Catalog—it's complete, up-to-date—404 pages packed with the world's largest selection of quality electronic equipment at lowest, money-saving prices. Get every buying advantage at ALLIED: fastest shipment, expert personal help, lowest prices, guaranteed satisfaction...



WORLD'S LARGEST STOCKS

- Latest Hi-Fi Systems and Components
- Money-Saving, Build-Your-Own KNIGHT-KITS
- Recorders and Supplies
- Public Address Systems and Accessories
- TV Tubes, Antennas and Accessories
- Amateur Receivers, Transmitters, Station Gear
- Test & Lab Instruments
- Specialized Industrial Electronic Equipment
- Huge Listings of Parts, Tubes, Transistors, Tools, Books

EASY-PAY TERMS:

Only 10% down
Available on orders over \$45.
Fast handling—no red tape.

featuring:

ALLIED'S money-saving knight-kits:

Finest electronic equipment in money-saving kit form. Over 50 quality kits available—Hi-Fi amplifier, tuner and speaker kits, Hobby kits, Test Instruments, Ham kits (see our KNIGHT-KIT values elsewhere in this publication). ALLIED KNIGHT-KITS are easiest to build and they SAVE YOU MORE.

EVERYTHING IN HI-FI

World's largest selection of quality Hi-Fi components and complete music systems—available for immediate shipment from stock. Save on exclusive ALLIED-Recommended complete systems. Own the best in Hi-Fi for less!



send for the leading electronic supply guide

FREE!

ALLIED RADIO CORP., Dept. 2-E8
100 N. Western Ave., Chicago 80, Ill.

Send FREE 404-Page 1958 ALLIED Catalog

Name _____

Address _____

City _____ Zone _____ State _____




Our 37th Year

ALLIED RADIO

World's Largest Electronic Supply House

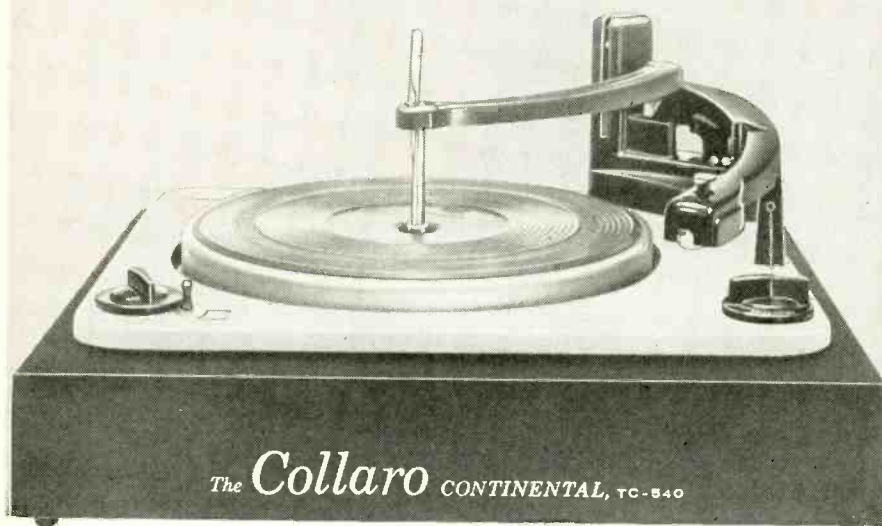New Transcription-Type Tone Arm Makes Collaro World's First True High Fidelity Changer



The Turntable That Changes Records

From Collaro Ltd., world's largest manufacturer of record playing equipment—comes the most significant development in years—the exclusive new transcription-type tone arm, which transforms the conventional record changer into a TRANSCRIPTION CHANGER, with features of the finest professional equipment.

The arm is a one-piece, spring-damped, counter-balanced unit which will take any standard high-fidelity cartridge. It is free of any audio spectrum resonances.

Stylus pressure between the first and last record in a stack remains virtually constant at less than a gram of difference, compared to 4 to 8 grams on conventional changers. Vertical and horizontal friction are reduced to the lowest possible level, insuring longer life for records and styli.

In its superb performance, the new Collaro Continental, Model TC-540, meets the rigid requirements for high fidelity equipment, offering professional quality at a record changer price. The Continental is \$46.50. Other Collaro changers are priced from \$37.50 up. (Prices slightly higher west of Mississippi.)



FREE: Colorful new catalog, containing guide on building record library plus complete Collaro line. Write to Dept. D-016.

ROCKBAR CORPORATION
MAMARONECK, N. Y.

Rockbar is the American sales representative for Collaro Ltd. and other fine companies.

Correspondence



LET'S STOP PAY TV

Dear Editor:

During the four years I have subscribed to RADIO-ELECTRONICS I have read a number of interesting and entertaining discussions in the Correspondence column. Until the pay TV issue came along I have never entered the ring. However, this is something I cannot overlook.

Television is our main entertainment facility at home. The programs we watch are being paid for by the advertisers and in turn by us. Then, too, we have to buy the set. Why should we be deprived of much of this entertainment? Why not stop this corruptive idea, which would seriously injure the blessings of our democratic way of life?

I suggest that you attach a petition to the next issue of RADIO-ELECTRONICS demanding legal action against pay TV on the behalf of the readers. I am confident that at least 95% of your readers would sign such a petition. This problem concerns us and we must solve it. Let's do it now before it gets later than you think!

M. CIKETIC

Los Angeles, Calif.

JUST FIX IT

Dear Editor:

The article "Do You Do a Maximum or Minimum Job" by Art Margolis in the December, 1957, issue certainly needs some honest clearing up. Some of these writers are trying to teach their customers the gentle art of repairing their own sets while fixing them and apologizing for each tube, resistor, dead rat or what-not they replace. I am not in the habit of running to my customers and saying, "Look, mighty sir, this tube has a silvery, pink or green glow and do you, august sir, agree to a new tube which I will guarantee for ever and ever!"

My customers let me do my work and I tell them nothing except that their set is economically beyond repair or that there may be some abnormally high fee necessary and I would like their OK to go ahead with the job.

For years I have given my customers an honest estimate of charges for work to be done. If they don't want the set repaired, they pay me for the estimate. I never worry about the customer who doesn't want to pay more than a couple of dollars to jack up his set and slip a new chassis under it. They generally return to me later, and of course sadder, and then they are my customers.

I do not do cheap jobs. It is the best
(Continued on page 14)

**How To
Increase your
Income
in
Electronics**

FREE

**tells
how**

**Get your FCC
Commercial License
—or your money back**

The Master Course in Electronics will provide you with the mental tools of the electronics technician and prepare you for a First Class FCC License (Commercial) with a radar endorsement. When you successfully complete the Master Course, if you fail to pass the FCC examination, you will receive a full refund of all tuition payments.

**EFFECTIVE
JOB FINDING
SERVICE HELPS CIRE
TRAINEES GET
BETTER JOBS**

“License and \$25 raise due to Cleveland Institute training”

“I sat for and passed the FCC exam for my second class license. This meant a promotion to Senior Radio Technician with the Wyoming Highway Department, a \$25 a month raise and a District of my own for all maintenance on the State’s two-way communication system. I wish to sincerely thank you and the school for the wonderful radio knowledge you have passed on to me. I highly recommend the school to all acquaintances who might possibly be interested in radio. I am truly convinced I could never have passed the FCC exam without your wonderful help and consideration for anyone wishing to help themselves.”

**CHARLES C. ROBERSON
Cheyenne, Wyoming**

**HERE’S PROOF
FCC LICENSES
ARE OFTEN SECURED
IN A FEW HOURS
WITH OUR
COACHING**

Name and Address	License	Time
John H. Johnson, Boise City, Okla.	1st	20 weeks
Prentice Harrison, Lewes, Delaware	1st	27 weeks
Herbert W. Clay, Phoenix, Arizona	2nd	22 weeks
Thomas J. Bingham, Finley, North Dakota	2nd	9 weeks
William F. Masterson, Key West, Fla.	2nd	24 weeks


**EMPLOYERS
MAKE JOB OFFERS
LIKE THESE TO OUR
GRADUATES EVERY
MONTH**

**Employers Make Job Offers Like These
To Our Graduates Every Month**

Broadcast Station in Illinois: “We are in need of an engineer with a first class phone license, preferably a student of Cleveland Institute of Radio Electronics; 40 hour week plus 8 hours overtime.”
West Coast Manufacturer: “We are currently in need of men with electronics training or experience in radar maintenance. We would appreciate your referral of interested persons to us.”

**Your FCC Ticket
is recognized by
employers as proof
of your technical ability**

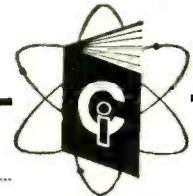**Cleveland Institute of Radio Electronics
Desk RE-17, 4900 Euclid Bldg., Cleveland 3, Ohio**



Act Now!

Please send Free Booklets prepared to help me get ahead in Electronics. I have had training or experience in Electronics as indicated below:

Military Amateur Radio Telephone Company
 Radio-TV Servicing Broadcasting Other _____
 Manufacturing Home Experimenting

In what kind of work are you now engaged?.....

In what branch of Electronics are you interested?.....

Name..... Age..... Address.....


City..... Zone..... State.....

RE-17

SERVICE MAN — SALESMAN — DEALER — JOBBER
 HOME WORKSHOPPER — PROFESSIONAL REPAIRMAN

THEY ALL SAY

It's a Honey!

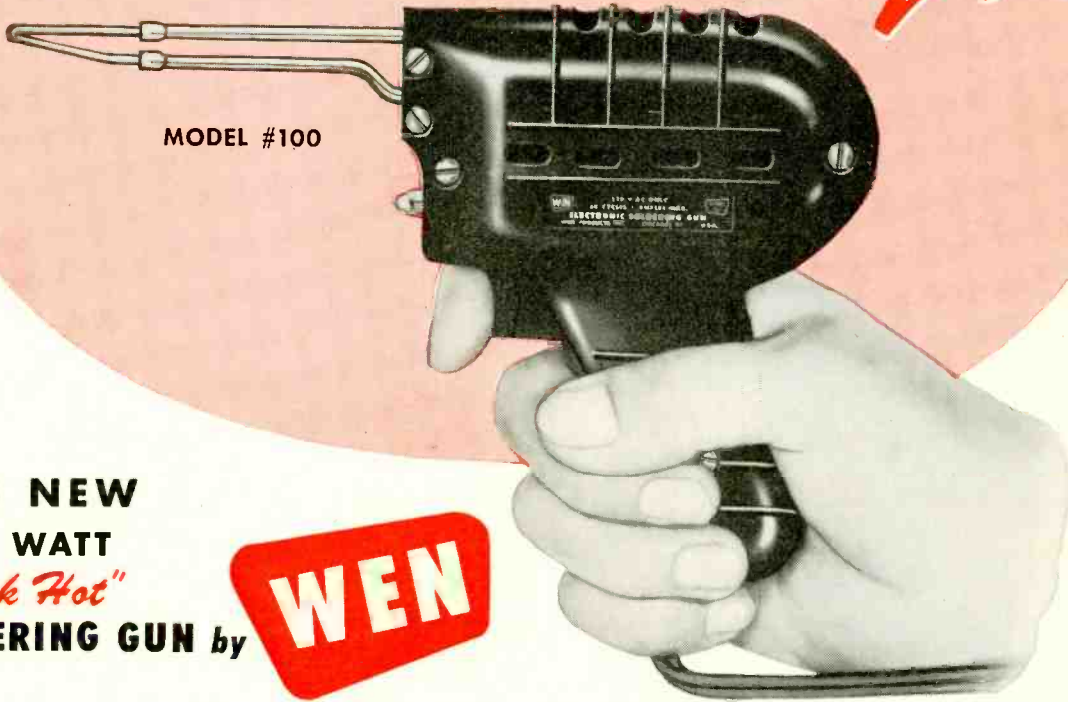

THIS NEW
 100 WATT
"Quick Hot"
 SOLDERING GUN by



This lowest priced electronic soldering gun on record has other exclusive features that would make it preferred regardless of price.

- It's smaller, slimmer, more compact — beautifully balanced — handy as your hand.
- It's lighter — weighs only 19 ounces. Doesn't tire you.
- Heats in 3 seconds on ordinary 110-120 Volt AC, 60 cycle.
- Cools quickly too when trigger is released.
- Has automatic spotlight that's focused on the tip.
- Has long reach, long life soldering tips that are replaceable and interchangeable with hot-cutting or flat iron finish-repair tips.
- Sturdy, ebony black plastic handle and housing are heat and impact resistant.

And only
\$595
 LIST

IDEAL FOR 90% OF ALL YOUR SOLDERING REQUIREMENTS

OTHER **WEN** POWER TOOL LEADERS



2 SPEED
 3/8" POWER DRILL

\$29.95
 LIST

1000-3000 RPM as needed, on 120 Volt AC/DC. Speed change quick, positive. Provides just the right speeds for different jobs. Geared Jacobs chuck. All you need in an electric drill in this 1 tool. With attachments — it is a whole work shop.



8 SAWS IN 1
 POWER SAW

\$29.95
 LIST

Has no equal. Cuts almost anything smoothly, swiftly — 2 x 4's in seconds, 1/2" steel, plastics, conduits. Cuts circles, scrolls, dovetails, straight lines or angles. Makes own starting holes. Blows sawdust off guide lines. 3 blades, coarse, medium, fine. Operates on 110-120 Volt AC/DC.



PRODUCTS, INC. 5808 NORTHWEST HIGHWAY, CHICAGO 31, ILL.

(Export sales, Scheel International, Inc., Chicago)

ALL WEN PRODUCTS ARE SUPERBLY MADE — U.L. APPROVED — FULLY GUARANTEED

NRI'S PROFESSIONAL TELEVISION TRAINING

A Fast Way To Reach The Top In TV Servicing

Oldest and Largest Home Study Radio-TV School Trains You to Fix Any Set Easily, Quickly, Correctly

Professional Television Servicing is a field for the *trained* man, for the expert. The man who knows a "little" will soon be left behind. Time wasted in locating defects by "trial and error" methods can cost *you* money; easily made mistakes can mean callbacks, unhappy customers, even parts that cost money to replace.

Take time to get the training you need to get ahead, enjoy the high pay jobs. That is what NRI's Professional Television Training can do for you. *It is not for the beginner.* NRI's Professional Television Training is planned for the man with some knowledge of Television or Radio but who realizes his need to know *more*; so he can make Television repairs more quickly, confidently and accurately.

All-Practice Method

NRI's Professional Television Training is practical, complete. You do more than read about circuits or just build them. NRI is all-practice, guided training. NRI has spent years in developing training equipment you use to conduct Television Servicing experiments, make tests and thoroughly understand the causes and effects of Television problems. You get practical experience, first hand knowledge of Television Receiver defects, learn how to diagnose them and how to service them.

All equipment is yours, to keep. The professional quality 5" Oscilloscope you build will be a valuable part of your Servicing Equipment. You get other kits, developed to speed your knowledge and confidence, including a 17" picture tube



and all components for a TV receiver that you build to learn circuitry and make tests; setting up defects just as they might occur in actual servicing.

Color TV Manuals Early

The day you enroll, NRI sends you special Color TV manuals to give you knowledge of this growing phase of TV. Full color pictures, diagrams help speed your training.

There is no better way to get Professional Television Training than through NRI. NRI is the oldest, largest home study Television-Radio school. For over 40 years, NRI's business has been TRAINING men for success in Television-Radio. NRI graduates hold jobs in every part of the industry. NRI methods are tested, proved. You train at home in spare time, get personal attention from instructors who are specialists in Television techniques.


Not For Beginners

NRI's Professional Television course condenses knowledge and experience that would take years of hit-and-miss learning. You learn how *experts* diagnose and repair TV defects. You are shown *professional* techniques to help you service

ANY MAKE, ANY MODEL Television receiver properly and without wasted time and effort. You know the "what" and the "why" of TV Servicing so you can compete with other professionals.

Send For FREE Catalog

Mail the coupon now for free catalog of what you learn, equipment supplied. Cost of entire course, all training equipment, Color TV manuals, etc. is low. Monthly terms if desired. NATIONAL RADIO INSTITUTE, Dept., 8EFT, Washington 16, D. C.



**"The man who
learns more ...
earns more"**

The professional TV Serviceman earns good money, enjoys respect and the opportunity of a secure, growing profession. But you can't afford to "guess." You must have training to succeed. NRI can provide it for you.

J.E. Smith
FOUNDER

National Radio Institute

DEPT. 8EFT, WASHINGTON 16, D. C.

Please send my FREE copy of "How to Reach the Top in TV Servicing." I understand no salesman will call.

Name.....Age.....

Address.....

City.....Zone.....State.....

Accredited Member National Home Study Council

First

from

PACO

Manufacturers of quality electronic equipment in kit form.



TRANSISTOR and Crystal Diode TESTER in kit form

Model T-65
only \$39.95

60% of all 1958 electronic equipment will include transistors and diodes.

PACO, the only test instrument kit line produced under the auspices of a major test equipment manufacturer, is the first to bring you a comprehensive transistor tester in kit form—available at your local distributor. This is the instrument you *must* have to maintain modern electronic equipment!

Produced in accordance with the recommendations of leading transistor manufacturers, PACO's T-65 provides comprehensive tests for I_{cbo} , gain, leakage, shorts, etc., on low, medium and high-power transistors of both the p-n-p and n-p-n types, as well as tetrode transistors.

25 YEARS OF PRECISION KNOW-HOW IS YOURS IN PACO KITS

MODEL V-70 VACUUM TUBE VOLTMETER KIT
• wide-range • peak-to-peak **NET PRICE: \$31.50**

MODEL B-10 BATTERY ELIMINATOR KIT
• less than 0.3% ripple • no external filters required
NET PRICE: \$41.95

MODEL G-30 RF SIGNAL GENERATOR KIT
• 160 Kc to 240 Mc in 8 bands • 120 Mc fundamental
NET PRICE: \$28.50

MODEL G-30-PC Same as Model G-30 but with pre-wired and precalibrated front end. **NET PRICE: \$35.50**

MODEL S-50 5" CATHODE RAY OSCILLOSCOPE KIT
• push-pull vertical and horizontal amplifiers.
NET PRICE: \$49.50


MODEL C-20 RESISTANCE-CAPACITY-RATIO BRIDGE KIT
• 10 mmfd to 2000 mfd • ½ ohm to 200 megs
NET PRICE: \$20.95

MODEL T-60 TUBE CHECKER KIT
• full free-point lever selector system
NET PRICE: \$38.75

MODEL Z-80 RF-AF SIGNAL TRACER KIT
• High gain RF & AF amplifier
• Visual-audible indicator **NET PRICE: \$29.50**

MODEL M-40 HIGH-SENSITIVITY V-O-M KIT
• 20,000 ohms/volt DC • 10,000 ohms/volt AC
NET PRICE: \$31.50

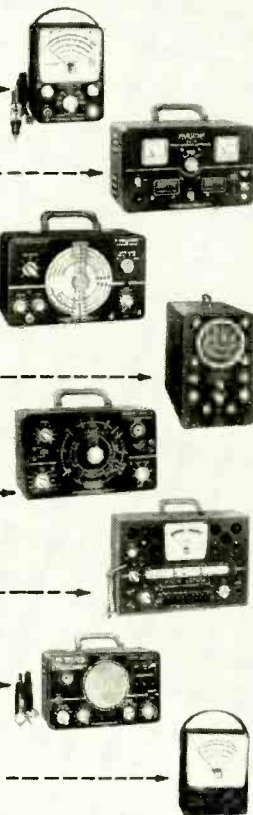► Available and on display at leading electronic parts distributors.
Write for free descriptive bulletin.



PACO ELECTRONICS CO., INC.
70-31 84th Street, Glendale 27, Long Island, New York

A DIVISION OF **PRECISION Apparatus Company, Inc.**
Export: 458 B'way, N. Y. 13, U.S.A., Canada: Atlas Radio Corp., Ltd., 50 Wingold Ave., Toronto 19.

CORRESPONDENCE (Continued from p. 10)

way to lose a customer you don't really want. I repair a set the way I know how or nothing doing. I haven't lost a thing by doing this and some of you boys who are afraid of losing two-bit customers can chew on this for a while.

Please have enough faith in your professional service to the public, to let them remain the public. They have their job and you have yours. If repairing radio and TV sets were so simple, they wouldn't need you in the first place, and wouldn't have called. *Clearwater, Fla.* HOWARD L. NOWRY

FAST-MOVING ELECTRONICS

Dear Editor:

Here are two indications of how swiftly progress in transistor development is being made.

In my article "More About Transistor Types," in the November, 1957, issue, I stated that double-diffused transistors were not yet commercially available. No sooner had that issue hit the stands than Charles Clough of Texas Instruments (TI) wrote to say that since the article was written TI had introduced four models of "diffused-junction silicon transistors" which he said were actually double-diffused.

In the December issue, readers noted my prediction (page 109) that the high-frequency transistor of the foreseeable future would be a micro-alloy thin-base unit. In that same issue (page 6) you may have noticed this prediction reduced to fact. Philco has introduced just such a transistor, which they call the MADT model.

In this field you have to keep running just to stand still!
Cambridge, Mass. PAUL PENFIELD, JR.

WHY WIND COILS?


Dear Editor:

Why is it that most authors of construction projects have an aversion to using commercially available coils? In most of the projects in your magazine there is the necessity for winding at least one coil.

Looking at the practical side of these construction projects, it seems that the majority of people who build them would prefer using available coils. Using the article "Vanguard 108" by Richard Graham in the January, 1958, issue as an example, how many people have a roll of No. 16 tinned or No. 30 enameled wire? Few, if any. To wind these coils, which require only a few inches of the specified wire, the builder must purchase a roll of several feet of the wire. This is expensive and the chances are that he'll never need the wire again. Oh yes, I forgot to mention the necessity of obtaining the specified coil forms.

With the thousands of commercially available coils on the market, I see no reason why the coils in the Vanguard converter could not be ready-made.

(Continued on page 16)

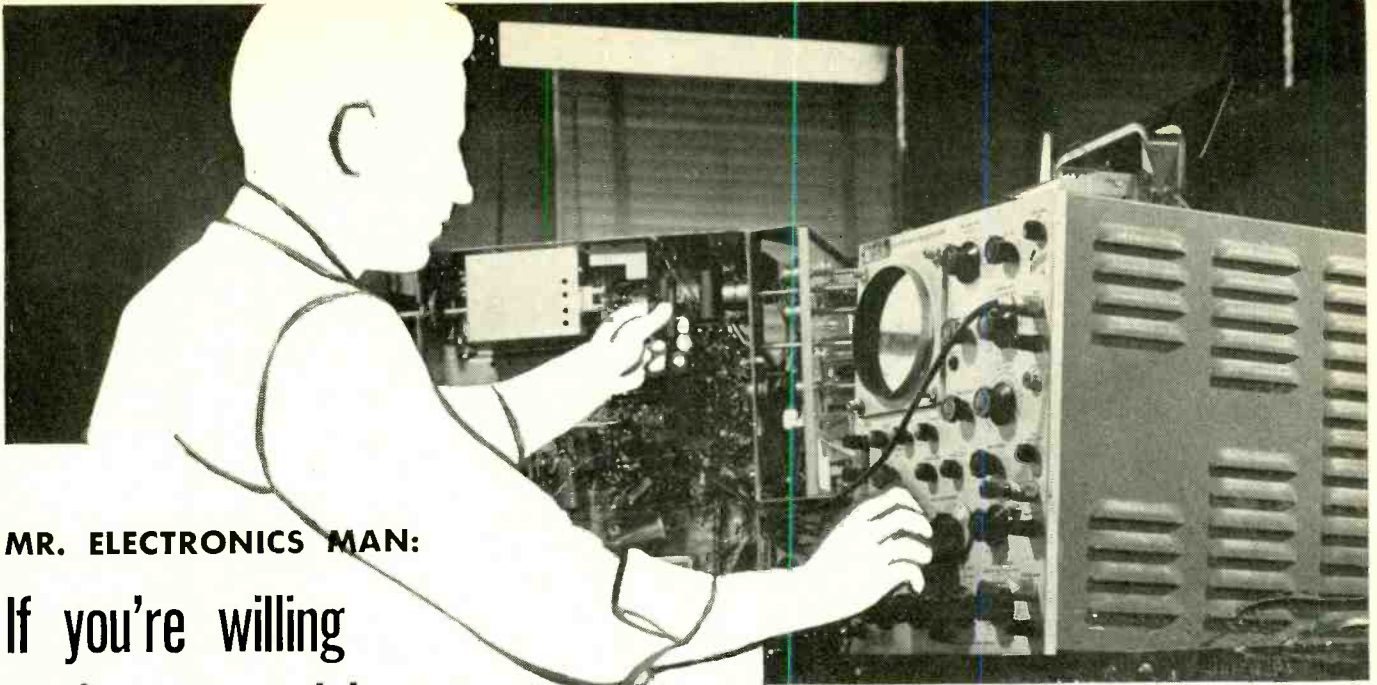

MR. ELECTRONICS MAN:

**If you're willing
to lose your job tomorrow
to a technically-trained man,
turn the page, mister**

But if you're interested in an honest-to-goodness career in the vigorous young electronics industry, here's how you can step ahead of job-competition, move up to a better job, earn more money, and be sure of holding your technical job, even if the brass is firing instead of hiring.

The "how" is advanced, professional home study training in Electronic Engineering Technology including SERVO-MECHANISMS; COMPUTERS; RADAR; AUTOMATION; AERONAUTICAL ELECTRONICS; BROADCASTING; COMMUNICATIONS AND MANUFACTURING, and the ELECTRONIC PRINCIPLES ASSOCIATED WITH GUIDED MISSILES, TELEMETERING, ASTRONAUTICS, and INSTRUMENTATION. You don't have to be a college graduate. You *do* have to be willing to study—at home. You can do it while holding down a full-time job.

Thousands have. Since 1927 CREI has provided alert young men with the technical knowledge that leads to more responsibility, more job security, more money. And CREI has constantly kept pace with the rapid expansion and progress in electronic achievement.

Remember this: CREI starts with fundamentals and takes you along at your own speed. You are not held back by a class, not pushed to keep up with others. You set your own pace. CREI instructors guide you through the lesson material and *grade* your written work personally. You master the fundamentals, then get into more advanced phases of electronic engineering principles and practice. Finally you may elect training in highly specialized principles of electronic engineering technology as applied to guided missiles, servomechanisms, radar, com-

puters, telemetering, automation, instrumentation and other applications.

How good is CREI training? Ask an electronics engineer. Ask a radio station engineer. CREI courses are accredited by the Engineers' Council for Professional Development; CREI is a member of the National Council of Technical Schools.

Look at this partial listing of organizations that recommend CREI training for their own personnel: United Air Lines, Canadian Broadcasting Corp., Trans-Canada Airlines, Douglas Aircraft Co., The Martin Co., Columbia Broadcasting System, All-American Cables and Radio, Inc., Gates Radio Co., Canadair Ltd., Federal Electric Corp., and U. S. Information Agency (Voice of America).

What's the next step? *Certainly get more information than we can cram into one page. Fill out and mail the coupon below today. or write Capitol Radio Engineering Institute, Dept. 145-E, 3224 16th St., N.W., Washington 10, D. C.*

CREI ALSO OFFERS RESIDENCE TRAINING at the same high technical level in Washington, D. C. Classes start at regular intervals. Qualified residence school graduates earn degree, "Associate in Applied Science." Check coupon if you prefer residence study.

VETERANS: If eligible for training under the new G.I. Bill of Rights, check the coupon for full information.

MAIL THIS COUPON FOR FREE BOOKLET!

CAPITOL RADIO ENGINEERING INSTITUTE

ECPD Accredited Technical Institute Curricula • Founded 1927

Dept. 145-E 3224 16th St., N.W., Washington 10, D. C.

Please send me your course outline and FREE illustrated Booklet "Your Future in the New World of Electronics" . . . describing opportunities and CREI home study courses in Practical Electronic Engineering Technology.

- CHECK FIELD OF GREATEST INTEREST
- Radar, Servo and Computer Engineering Technology
 - Electronic Engineering Technology
 - Broadcast (AM, FM, TV) Engineering Technology
 - Television Engineering Technology
 - Aeronautical Electronic Engineering Technology

13

Name.....Age.....

Street.....

City.....Zone.....State.....

Check: Home Study Residence School Korean Veteran

NOT FOR BEGINNERS. If you have had a high school education, and experience in electronics—and realize the need of high-level technical knowledge to make good in the better electronic jobs—you can qualify for CREI home study training. (Electronics experience is not required for admission to CREI Residence School.) Please fill in the following information:

EMPLOYED BY

TYPE OF PRESENT WORK


EDUCATION: YEARS HIGH SCHOOL

YEARS COLLEGE


ELECTRONICS EXPERIENCE

Customers Impatient?

It's full speed ahead

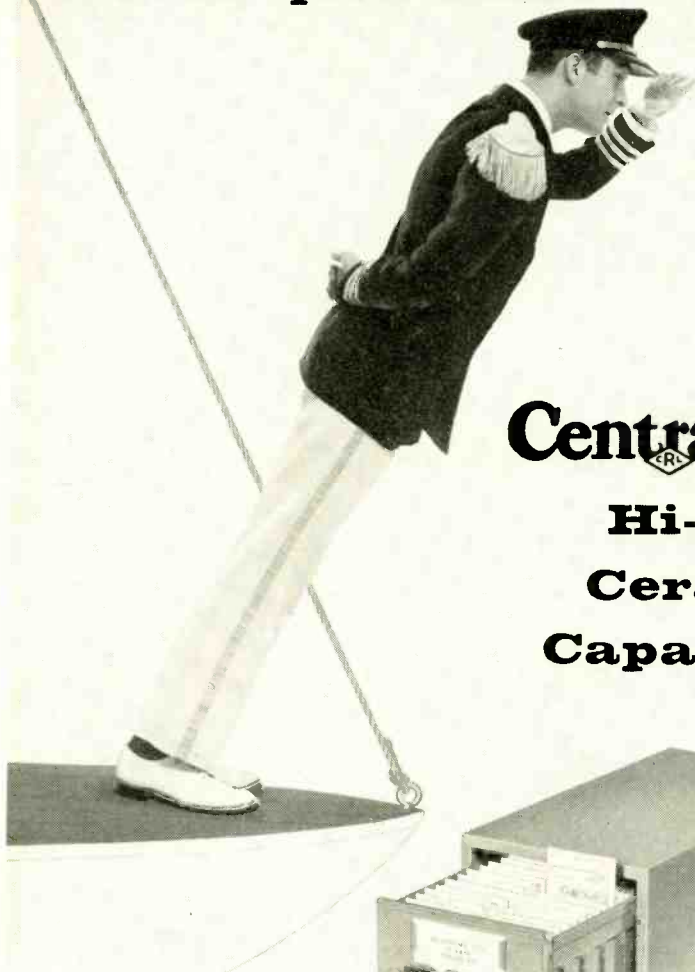

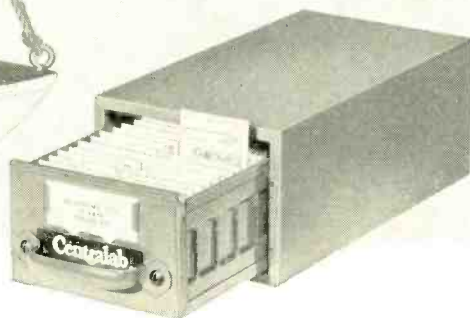with
Centralab
Hi-Kap*
Ceramic
Capacitor
Kits



No delays! It's always smooth sailing when you use Centralab ceramic capacitor kits. No extra trips to your distributor, no wasted time. The units you need are on hand when you need them.

To keep you on an even keel, these heavy gauge steel kits contain balanced inventories of the most frequently used values. Individual values are prominently and clearly labeled, so you can locate the Hi-Kap you need, instantly. The new rigid plastic package permanently separates and protects the units—yet is easily opened to remove a single capacitor.

So don't be left at sea. Ask your distributor about these four time-saving kits—and while you're at it, be sure to get your free copy of Catalog 30, listing the full line of Centralab capacitors and other quality components.

FREE: \$4.75 cabinet (4"x7"x11") with each kit.

D6K-200 Kit—200 Tubular Ceramic BC Hi-Kaps (27 values)
DDK-200 Kit—200 Standard Ceramic Disc Hi-Kaps (31 values)
TCK-80 Kit—80 TC (Temp. Compensating) Hi-Kaps (40 values)
HVK-150 Kit—150 High Voltage Disc Hi-Kaps (19 values)

Centralab products are listed in COUNTERFACTS, PHOTOFACETS, and THE RADIO-ELECTRONIC MASTER.

Centralab
*Trademark

A DIVISION OF GLOBE-UNION, INC.
922 E. KEEFE AVE. • MILWAUKEE 1, WIS.
In Canada: 804 Mt. Pleasant Rd. • Toronto, Ontario

D-5829

SWITCHES • PACKAGED ELECTRONIC CIRCUITS • CERAMIC CAPACITORS
CONTROLS • ENGINEERED CERAMICS • SEMI-CONDUCTOR PRODUCTS

CORRESPONDENCE (Continued from p. 14)

I have been building magazine projects for many years and when I see a home-wound coil, I pass it up.

Chicago, Ill. KEN GREENBERG

(The J. W. Miller Co. has a very complete line of coils and transformers on the consumer market, but their catalog does not list coils that may be used as exact replacements for L1, L2, L4, L5 and L6 in the Vanguard 108. As frequency goes up, the coil's Q becomes increasingly important. Also, coils with the required Q and inductance are not available with taps or additional windings as needed. You may consider that the transformer formed by L5 and L6 could possibly be replaced by a shortwave antenna coil designed for 6-10 mc or so. This would work, but then you would have to tune it with a capacitor of around 200 μf or more. The high ratio of capacitance to inductance would not permit the user to get optimum performance from the combination.

J. W. Miller type 1454 and 1456, 88-108-mc antenna and oscillator could have been used for L1 and L4, respectively, with slight modifications in the circuit. There is one drawback. These coils are not listed by many mail-order catalogs and are not stocked by many radio parts suppliers. Most retailers are reluctant to order single units such as this and the manufacturer doesn't sell retail.

We feel that it is doing you and other readers a disservice to specify an item when we know that it is not universally available and that many readers will have trouble in getting it. Similarly, why specify a coil that may cost \$5 when you can wind it for about one-tenth the price.—Editor)

WHERE DO YOU TURN?

Dear Editor:

What is happening to the radio parts retailing industry? I've been an active experimenter and constructor for over 25 years and I've never seen conditions more discouraging. Sales personnel don't know what they have in stock nor are most of them even remotely aware of the characteristics or applications of even the most common components. They are only interested in pushing TV and radio replacement parts.

Manufacturers are continuously introducing new components of interest to the experimenter, but retailers and distributors are not cooperative. Try and get a photocell, a set of all-wave coils for a receiver, or a sensitive relay. Most manufacturers don't sell retail and retailers won't accept orders for single units.

Recently I decided to build the Twin-Coupled Amplifier from details in the November, 1957, issue. I went from store to store trying to obtain any of the four brands of output transformers specified for the amplifier. All stores carried products made by at least two of the four manufacturers, but none
(Continued on page 20)

Do you WISH you were EMPLOYED in ELECTRONICS?

F.C.C. License — the Key to Better Jobs

An FCC *commercial* (not amateur) license is your ticket to higher pay and more interesting employment. This license is Federal Government evidence of your qualifications in electronics. Employers are eager to hire *licensed* technicians.

Which License for Which Jobs

The **THIRD CLASS** radiotelephone license is of value primarily in that it qualifies you to take the second class examination. The scope of authority covered by a third class license is extremely limited.

The **SECOND CLASS** radiotelephone license qualifies you to install, maintain, and operate most all radiotelephone equipment except commercial broadcast station equipment.

The **FIRST CLASS** radiotelephone license qualifies you to install, maintain, and operate every type of radiotelephone equipment (except amateur, of course) including all radio and television stations in the United States, its Territories and Possessions. This is the highest class of radiotelephone license available.

The Grantham Communications Electronics Course

prepares you for a **FIRST CLASS** FCC license, and it does this by **TEACHING** you electronics. Each point is covered simply and in detail, with emphasis on making the subject easy to understand.

OUR GUARANTEE

If you should fail the FCC exam after finishing our course, we guarantee to give you additional training at **NO ADDITIONAL COST**. Read details in our free booklet.

FCC-TYPE EXAMS

FCC-type tests are used throughout the Grantham course. Constant practice with these FCC-type tests helps you prepare for the actual FCC examination.

TWO COMPLETE SCHOOLS: *To better serve our many students throughout the entire country, Grantham School of Electronics maintains two complete schools — one in Hollywood, California and one in Washington, D. C. Both schools offer the same rapid courses in FCC license preparation, either home study or resident classes.*

Get
Your First Class Commercial

F.C.C. LICENSE

in
12 Weeks!

Learn by Correspondence or in Resident Classes

Grantham School of Electronics *specializes* in preparing students to pass FCC examinations. Correspondence training is conducted from Washington and Hollywood; resident **DAY** and **EVENING** classes are held in both cities. Either way, we train you quickly and well — **NO** previous training required.

This booklet
FREE!

This free booklet gives details of our training and explains what an F.C.C. license can do for your future. Send for your copy today.



Here's Proof...

that Grantham Students prepare for FCC examinations in a minimum of time. Here is a list of a few of our recent graduates, the class of license they got, and how long it took them:

	License	Weeks
James M. Farish, 926 Cardone Ave., Reno, Nev.	1st	12
Francis Krug, Station WNCC, Barnesboro, Pa.	1st	14
Steve Galvan, 1911 Brockwell, Monterey Park, Calif.	1st	13
Douglas Moore, 5102 Flambeau Rd., Madison, Wisc.	1st	11
Bernard Kirschner, 504 E. Fifth, New York, N.Y.	1st	12
Richard Meelan, 166 Jerome St., Brooklyn, N.Y.	1st	10
Charles Page, General Delivery, Yuma, Ariz.	1st	16
Edwin Harman, 6162 Bonner, North Hollywood, Calif.	1st	12
Albert D. Meeleib, Box 136, Elrama, Pa.	1st	12
Guido Elias, 66 S. Elliott Pl., Brooklyn, N.Y.	1st	12

Grantham School OF ELECTRONICS

Hollywood
Division

1505 N. Western Ave.
Hollywood 27, Calif.
Phone: HO 2-1411

Washington D.C.
Division

821 - 19th Street, N.W.
Washington 6, D.C.
Phone: ST 3-3614

for **FREE** Booklet **CLIP COUPON** and
mail in envelope or paste on postal card.

MAIL COUPON TO SCHOOL NEAREST YOU

Grantham Schools, Desk 84-E

821 - 19th Street N.W.
Washington 6, D. C.

OR

1505 N. Western Ave.
Hollywood 27, Calif.

Please send me your free booklet telling how I can get my commercial F. C. C. license quickly. I understand there is no obligation and no salesman will call.

Name _____ Age _____

Address _____

City _____ State _____

I am interested in: Home Study, Resident Classes

EVEN THOUGH THE DADDY OF

**3 reasons why there are
NO printed circuits in Zenith TV chassis**



standard HANDcrafted circuitry means:

1 LESS SERVICE HEADACHES



standard HANDcrafted circuitry means:

**2 EASIER SERVICING FOR DEALER
AND SERVICEMAN ALIKE**



standard HANDcrafted circuitry means:

**3 MORE SATISFIED CUSTOMERS
FOR ZENITH DEALERS**

We think it's worth the extra cost and extra care of HANDcrafted standard circuitry to get the best performance and least service headaches and so do thousands of dealers who would sooner sell customer satisfaction than a price tag.

ZENITH RADIO CORPORATION
Chicago 39, Illinois

The quality goes in before the Zenith name goes on.
Backed by 39 years of leadership in radionics exclusively.
Also makers of Radio, High Fidelity Instruments and fine Hearing Aids.



PRINTED CIRCUITRY IS HEAD OF
ZENITH'S RESEARCH DEPT.*, THERE'S

NO PRINTED CIRCUITRY IN ZENITH TV CHASSIS



*Even though Dr. Alexander Ellett, head of Zenith's research department, is recognized as the daddy of printed circuitry through his work on radio proximity fuses, still Zenith uses no printed circuitry in its TV chassis because it means more service headaches and often causes service delays.

QUALITY BY

ZENITH

®

NEW

New AM-FM Tuner puts wide band FM, wide range AM within your budget!


Completely new in styling . . . in engineering . . . in performance . . . the H. H. Scott model 300 AM-FM tuner embodies many new engineering features found nowhere else.

- Selectivity is superior to conventionally designed tuners because of the wide-band detector.
- Circuitry is completely drift-free . . . without the need for troublesome AFC.
- Cross-modulation is minimized so strong local stations do not appear at several points on the dial.
- AM section features wide-range circuitry. Reception is so good on fine AM stations you'll think you are listening to FM.

When you tune the H. H. Scott 300 to a weak FM station next to a strong one, it stays in tune perfectly. Ordinary tuners using AFC rather than Wide-Band, wander from the weak station to the strong, making it impossible to tune to weak stations. Smooth acting slide-rule dial is extra-long giving better band spread, so stations are easy to separate.



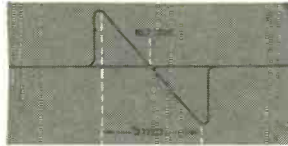Precision-ray tuning eye makes it simple to tune precisely on both AM and FM.



Wide-band FM circuitry eliminates co-channel and adjacent channel interference — makes tuning drift-free.



Famous musicians like Metropolitan Opera singer Jerome Hines choose H. H. Scott components for their own homes.

Additional Technical Information — Model 300

FM sensitivity 3 microvolts for 20 db of quieting; 2 megacycle wide-band detector; 10 kc sharp-tuned whistle filter; outputs — main, multiplex, tape; tuned RF stage insures high sensitivity and selectivity on both AM and FM; two position AM bandwidth for Normal and High Fidelity programs; size in mahogany accessory case 15 1/2" w x 5 h x 12 1/2" d. \$159.95. Choice of handsome accessory cases at \$9.95 and \$19.95.



The new 300 is a perfect match to H. H. Scott's Best Buy Amplifier . . . the famous "99". This 22 watt complete amplifier is only \$109.95. This means that for only \$269.90 you can have a complete H. H. Scott system.



CORRESPONDENCE (Continued from p. 16)

stocked the required units. In some cases, the clerks disclaimed any knowledge of the specific parts. Others admitted that they had seen manufacturers' circulars describing the transformers, but would not accept an order.

I started telephoning manufacturers' sales representatives. The usual answer was that "ABC Electronics Distributors carries our complete line. If they don't have the type transformer you need, they'll order it from us." The distributors named did not have the item in stock, but would order it if the order was placed through a local retailer. Some distributors claimed that the desired transformer was a fast-moving item and that they had sold quite a few to retailers, but couldn't tell me where I could lay my hands on one. Only through luck and persistence was I finally able to locate the necessary pair of transformers.

If I'd known the trouble I was in for, I never would have considered the project. In the future, I'll submit the complete parts list to a retailer and will place the order only on an all-or-nothing basis.

New York, N. Y.

E. WILHELM

NOTE TO TV DXERS

Dear Editor:

A new publication, available from the Government Printing Office, Washington 25, D.C., may be of interest to serious TV dxers. Titled "Broadcasting Stations of the World, Part 4," it contains information about FM and TV stations outside the USA. It gives frequencies, power and other technical data. Information is arranged by country and also by frequency. The printing office number is: PR 34.659:-957/Pt. 4. Its price is 75 cents.

Many other books and pamphlets about radio, TV, and electronics are available from the Government Printing Office and a request will bring recent lists to anyone interested.

ROBERT W. WILLIAMS

Fairfield, Conn.

LIKE THAT AMPLIFIER

Dear Editor:

I would like to take this opportunity to thank you for the wonderful amplifier in RADIO-ELECTRONICS, November, 1957 ("Twin-Coupled Amplifier," by Norman Crowhurst).

I have completed the unit and have had it in constant use for about six weeks. I believe it to be as clean sounding an amplifier as I have heard. I find its 15 watts more than ample and its sound second to none. It has completely amazed some of the local dealers. I hope that you will print an article on a similar amplifier with greater power. This is the first piece of electronic equipment that I have ever built from a schematic and you can imagine how happy and proud I was at my success and to acquire such an instrument.

GEORGE E. MOCK

Indianapolis, Ind.

END

H. H. Scott, Inc., 111 Powdermill Road, Maynard, Mass.

Export: E-5 Telesco International Corp., 36 West 40th Street, New York City

"RUSH me free copy of your completely new catalog E-5."

NAME.....

ADDRESS.....

CITY.....STATE.....

www.americanradiohistory.com




**WE'RE MAKING IT EASIER THAN EVER TO BECOME A WELL PAID
RADIO-TELEVISION SERVICE TECHNICIAN**

**NOW - Just \$6 Starts You Training in
RADIO-TELEVISION
the SPRAYBERRY "Learn-by-Doing" Way . . .**

**25 BIG, COMPLETE KITS
of PARTS & EQUIPMENT**

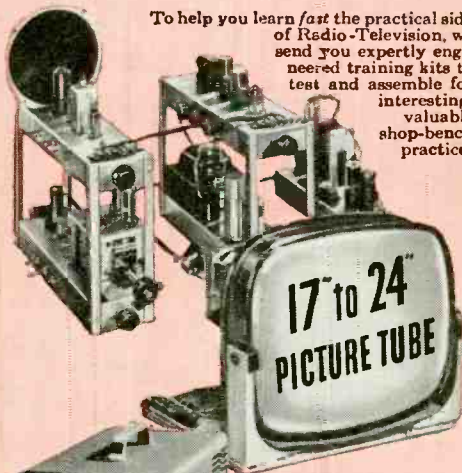To help you learn *fast* the practical side of Radio-Television, we send you expertly engineered training kits to test and assemble for interesting, valuable shop-bench practice!





• The new Sprayberry Training Television Receiver, built and tested in 5 sections.

• Now offered . . . this fine modern oscilloscope.

• You build this powerful two-beam superheterodyne radio receiver.

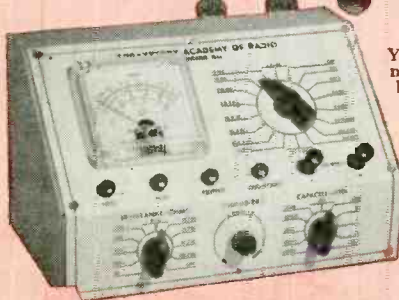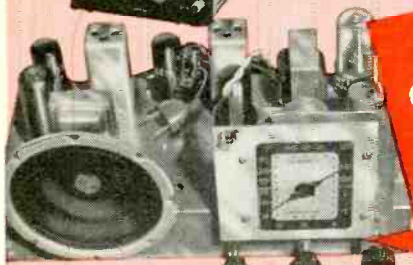**Big New
CATALOG
AND
Sample Lesson
FREE!**



You build the new Sprayberry tester—a complete 18-range Volt-Ohm-Milliammeter test meter.

★ ★ ★ ★ This great industry is begging for trained men . . . to step into good paying jobs or a profitable business of their own! Our new plan opens the doors of Radio-Television wide to every ambitious man who is ready to act at once!

Men by the thousands . . . trained Radio-Television Service Technicians . . . are needed at once! Perhaps you've thought about entering this interesting, top paying field, but lack of ready money held you back. Now—just \$6 enrolls you for America's finest, most up to date home study training in Radio-Television! Unbelievable? No, the explanation is simple! We believe Radio-Television *must* have the additional men it needs as quickly as possible. We are willing to do our part by making Sprayberry Training available for less money down and on easier terms than ever before. This is your big opportunity to get the training you need . . . to step into a fine job or your own Radio-Television Service Business.

Complete Facts Free—Act Now; Offer Limited

Only a limited number of students may be accepted on this liberal and unusual basis. We urge you to act at once . . . mail the coupon below and get complete details plus our big new catalog and an actual sample lesson—all free. No obligation . . . no salesman will bother you.

HOME STUDY TRAINING IN SPARE TIME

Under world-famous 27-year old Sprayberry Plan, you learn entirely at home in spare time. You keep on with your present job and income. You train as fast or as slowly as you wish. You get valuable kits of parts and equipment for priceless shop-bench practice. And everything you receive, lessons and equipment alike, is all yours to keep.

LET US PROVE HOW EASILY YOU CAN LEARN!

Radio-Television needs YOU! And Sprayberry is ready to train you on better, easier terms, than any ambitious man can afford. *Just \$6 starts you!* Mail coupon today . . . let the facts speak for themselves. You have everything to gain. Let us prove the kind of opportunity that's in store for you!

SPRAYBERRY Academy of Radio-Television
1512 Jarvis Avenue, Dept. 20-G, Chicago 26, Illinois

Mail This Coupon Now—No Salesman Will Call

Sprayberry Academy of Radio-Television
Dept. 20-G, 1512 W. Jarvis Ave., Chicago 26, Ill.

Please rush all information on your ALL-NEW Radio-Television Training Plan. I understand this does not obligate me and that no salesman will call upon me. Include New Catalog and Sample Lesson FREE.

NAME..... Age.....

ADDRESS.....


CITY.....ZONE.....STATE.....





GOLDEN INVADER

The Antenna That Beats Them All!

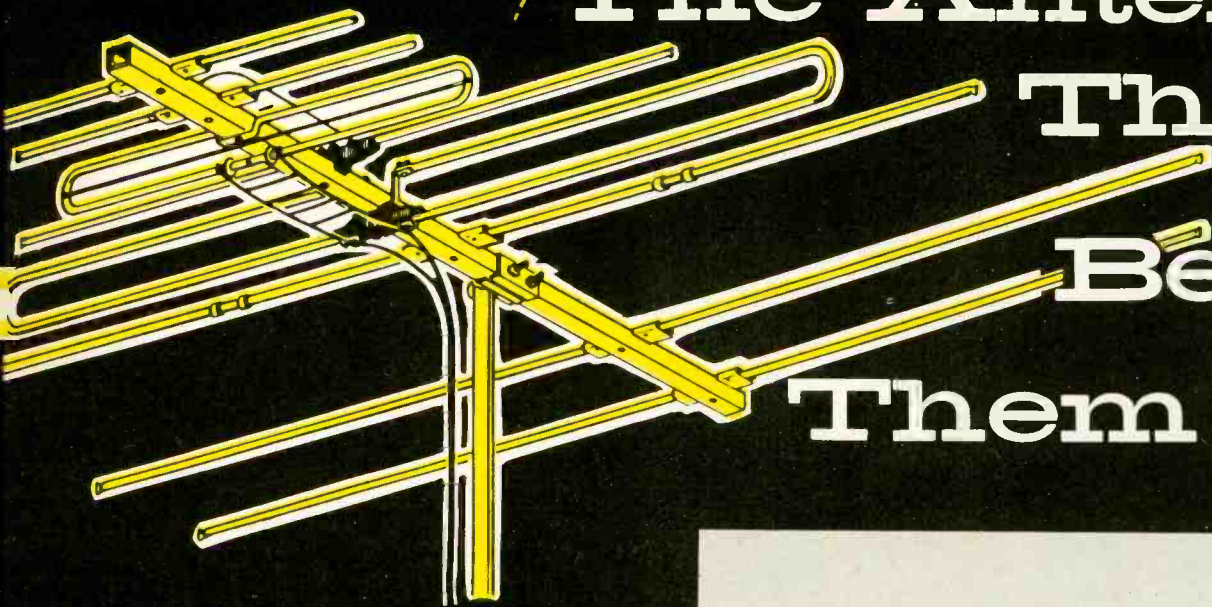

TRY TELCO'S NEW GOLDEN INVADER, the powerful antenna for VHF fringe areas and UHF primary areas. Extensive tests prove its uni-plane design can pull in stations from as far as 200 miles away. Ghosts and co-channel interference are eliminated. The **GOLDEN INVADER**, for color or black-and-white TV, comes pre-assembled with the new Snap-Lock construction that makes it easier to handle, easier to install. Available in single bay (illustrated), two-bay or four-bay models.

- SUPER SHARP DIRECTIVITY
- BEAUTIFUL GOLD ANODIZING
- NEW SNAP-LOCK DESIGN
- RECEPTION UP TO 200 MILES AWAY

SEE US
AT THE
PARTS
SHOW

No. A-8121 Single Bay.....List \$29.95
A-8122 Two-Bay.....59.95

VALUABLE BONUS FOR YOU!

Enclosed with each TELCO GOLDEN INVADER is a special Golden Bonus Certificate. Look for these Certificates . . . save them. They're valuable to you!

UNCONDITIONAL GUARANTY...

A Telco Exclusive! TELCO guarantees the GOLDEN INVADER and all Telco Antennas to be free from defects in materials and workmanship. This guarantee on the Golden Invader is for *three* years. All other antennas are guaranteed for one year.




TELCO ELECTRONICS MFG. CO.


Division of G-C - Textron Inc. • Los Angeles 18, Cal. • Rockford, Ill., U.S.A.

THE COMPLETE LINE OF TELCO POWER PACKED ANTENNAS


CONICALS

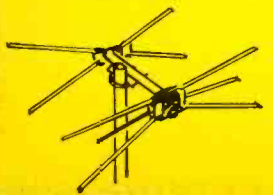


YAGIS

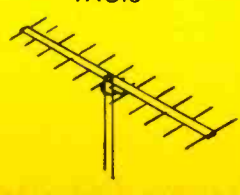


INLINES

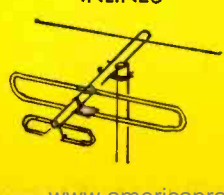

BOW TIES

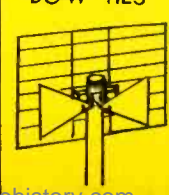


INDOORS

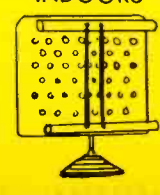

ANTENNA KITS



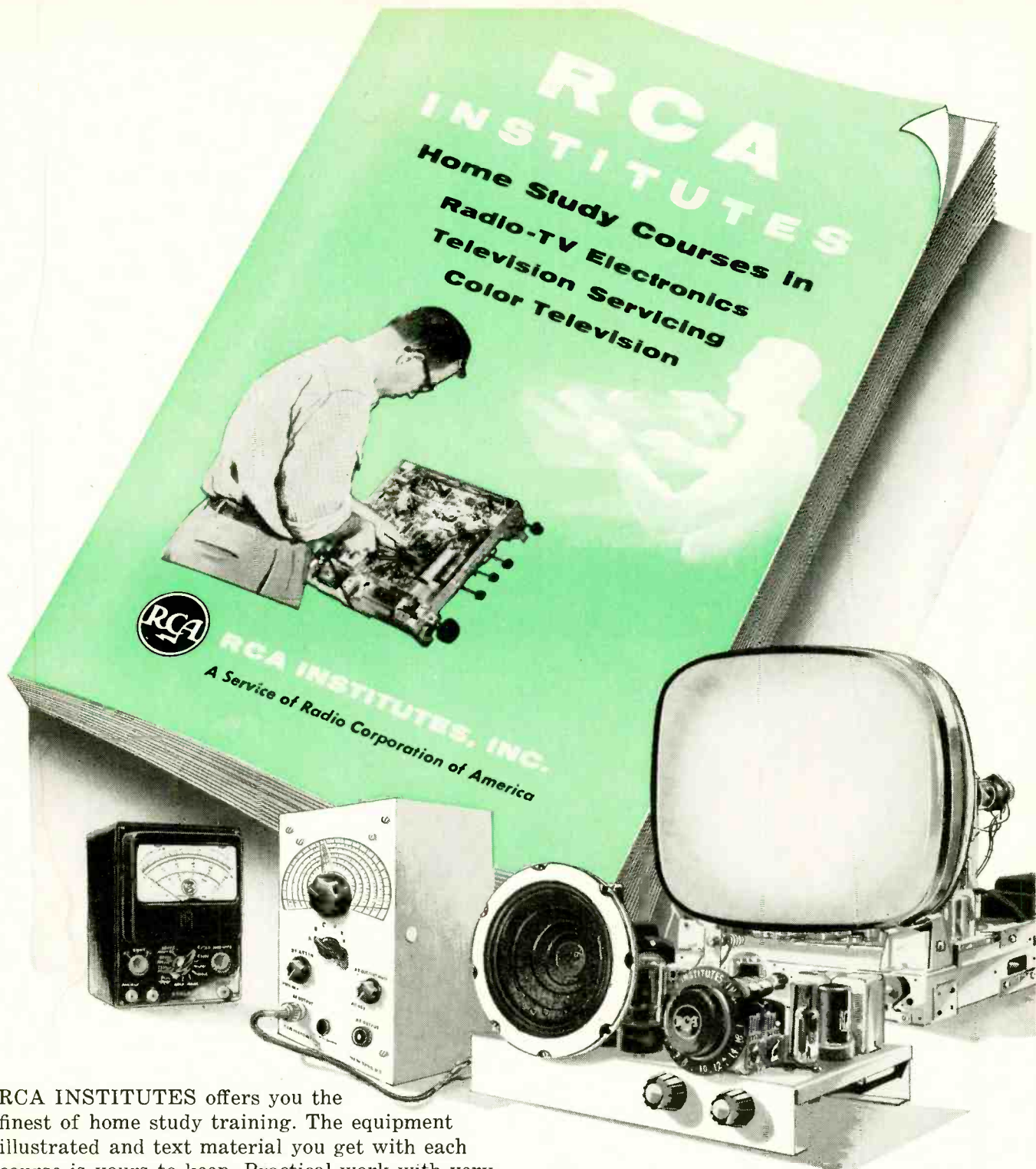

RCA INSTITUTES offers you the finest of home study training. The equipment illustrated and text material you get with each course is yours to keep. Practical work with very first lesson. Courses for the beginner and the advanced student. Pay-as-you-learn. You need pay for only one study group at a time.

**Send for this
FREE Book Now** 

[RESIDENT SCHOOL courses in New York City offer comprehensive training in Television and Electronics. Day and evening classes start four times each year. Detailed information on request]

RCA INSTITUTES, Inc. Home Study Dept. RE-58

A Service of Radio Corporation of America

350 West Fourth Street, New York 14, N.Y.

Without obligation, send me FREE 52 page CATALOG on Home Study Courses in Radio, Television and Color TV. No salesman will call.

Name please print

Address


City Zone State

Korean Vets! Enter discharge date


In Canada — RCA Victor Co., Ltd.
5001 Cote de Liesse Rd., Montreal 9, Que.

To save time, paste coupon on postcard.

Write a numeral here

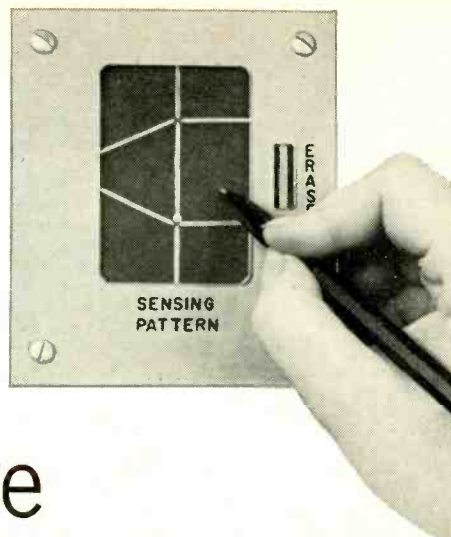

and read it here

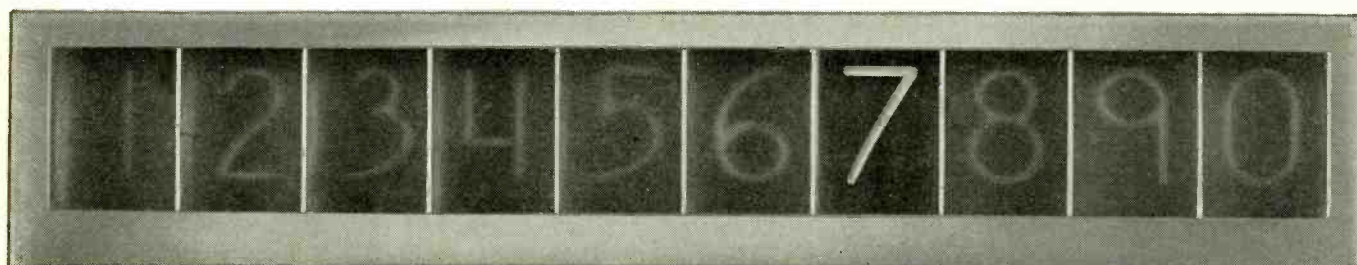


on new Bell Labs machine

A new device invented at Bell Laboratories "reads" a numeral while it is being written and instantly converts it into distinctive electric signals. The signals may be employed to make a numeral light up in a display panel, as above, or they may be sent to a computer or to a magnetic "memory" for storage.

The writing is done with a metal stylus on a specially prepared surface. Two dots, one above the other, are used as reference points. Seven sensitized lines extend radially from the dots. Transistorized logic circuits recognize numerals according to which lines are crossed.

The concept of a number-reader has interesting possibilities as a new means of communication from humans to machines. For example, in an adjunct to a telephone, it might provide inexpensive means of converting handwritten data into signals which machines can read. The signals could be transmitted through the regular telephone network to a teletypewriter or computer at a distant point. In this way, a salesman might quickly and easily furnish sales data to headquarters, or a merchant might order goods from a warehouse.

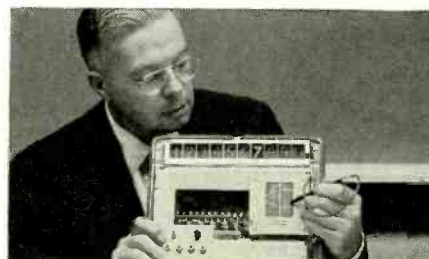Modern communication involves many more fields of inquiry than the transmission and reception of sound. The experimental number-reader is but one example of Bell Telephone Laboratories work to improve communications service.



Tom Dimond, a B.S. in E.E. from the University of Iowa, demonstrates an experimental model of his number-reading invention. A similar device can also be made to read alphabetical characters. Small size and low power requirements result from transistor circuitry.



BELL TELEPHONE LABORATORIES
World Center of Communications Research and Development

FREE from HOWARD W. SAMS!...valuable all-steel file cabinets with your purchase of **PHOTOFACT**—
the world's finest TV-Radio Service Data

FREE! FOR REGULAR PHOTOFACT SUBSCRIBERS

You get your File Cabinets FREE if you are a regular subscriber to PHOTOFACT Folders and buy all new Sets as issued each month. Your Folders come to you in special envelopes, each including a "Bonus Certificate." Sixty (60) of these entitle you to a single-drawer File Cabinet ABSOLUTELY FREE...



FREE! FOR PHOTOFACT LIBRARY PURCHASERS

Get FREE File Cabinets as you complete your profit-building PHOTOFACT Library... here's how:



FREE!
Single-Drawer File Cabinet with your purchase of 60 Sets of PHOTOFACT Folders.
Cabinet Worth... \$895



FREE!
Two single-drawer File Cabinets with your purchase of 120 Sets of PHOTOFACT Folders.
Cabinets Worth... \$1790



FREE!
Three single-drawer File Cabinets with your purchase of 180 Sets of PHOTOFACT Folders.
Cabinets Worth... \$2685



FREE!
Four single-drawer File Cabinets with your purchase of 240 Sets of PHOTOFACT Folders.
Cabinets Worth... \$3580

NEW EASY-BUY PLAN

It's easy to complete your present PHOTOFACT Library or start a PHOTOFACT Library. Use the EASY-BUY PURCHASE PLAN:

- NO INTEREST
- NO CARRYING CHARGE
- AS LITTLE AS \$10 DOWN
- UP TO 24 MONTHS TO PAY

Get the world's finest TV-Radio Service Data... get FREE File Cabinets with your PHOTOFACT purchases...take advantage of the Easy-Buy Plan. See your Sams Distributor today, or write to Howard W. Sams for full details.



get the full details of the HOWARD W. SAMS money-saving way to build your complete profit-making PHOTOFACT Library!

HOWARD W. SAMS & CO., INC.
2205 E. 46th St., Indianapolis 5, Indiana



Send details on your FREE File Cabinet offer and EASY-BUY Plan.

I'm a Service Technician: full time; part time

My Distributor is: _____

Shop Name: _____


Attn.: _____

Address: _____


City _____ Zone _____ State _____




This is

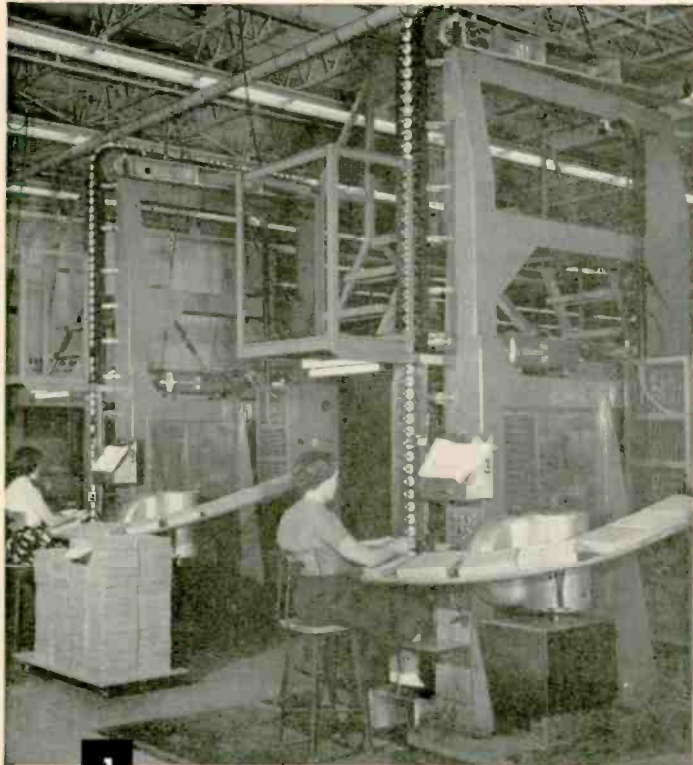

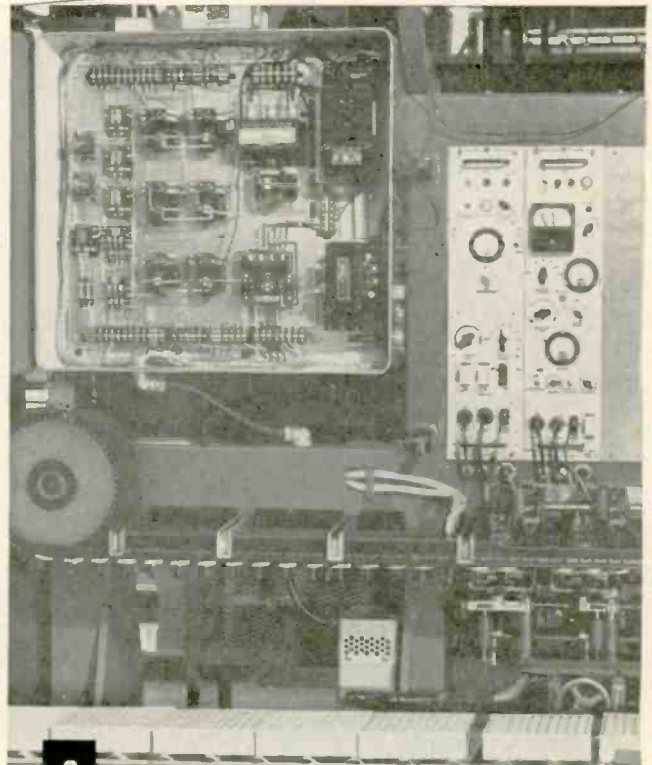1 Overall view of two automatic testers highlights "chain belt" where tubes are preheated in preparation for tap tests. Operator loading tubes checks pins for straightness.



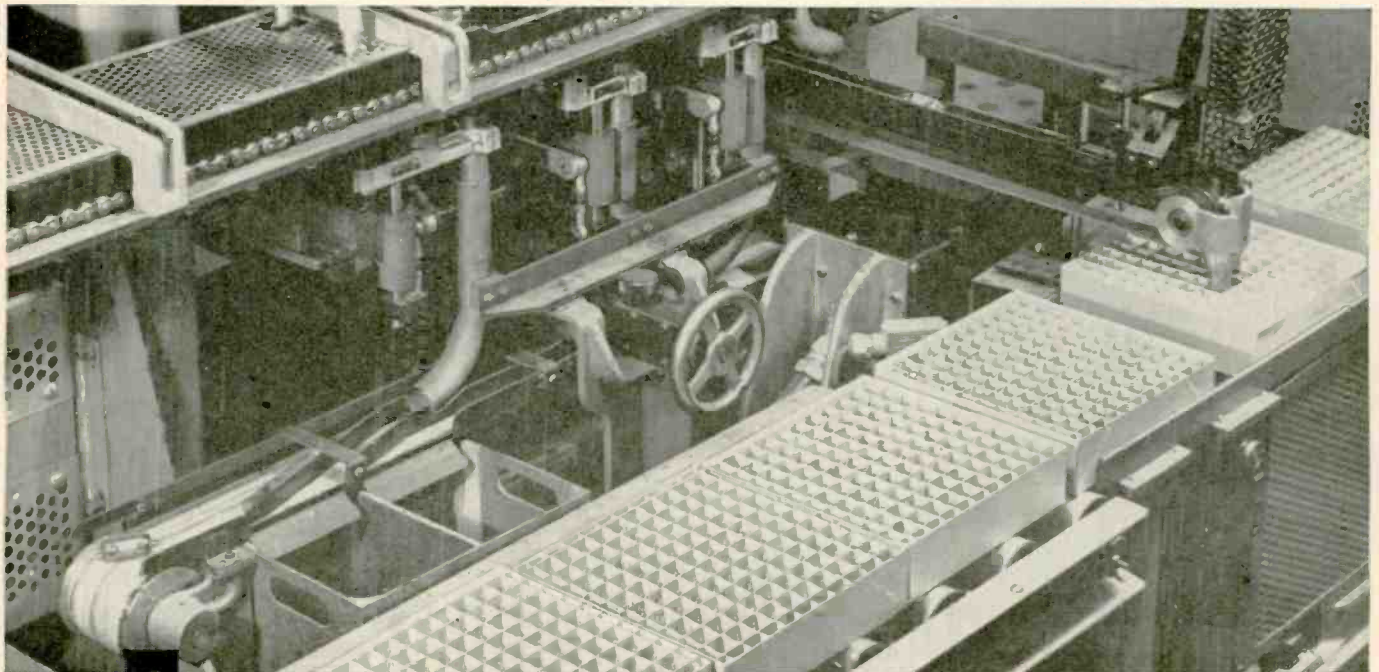
2 Electronic brain of the tester is designed by Sylvania so that any tube type can be tested simply by plugging in its proper adapter (about the size of a pack of cigarettes).



4 —Automatic unloading of "good" tubes into cartons comes after all tests have been made and

"inoperatives" separated. Rejects are dropped to conveyor belt, collected into bins, and scrapped.

Sylvania Williamsport

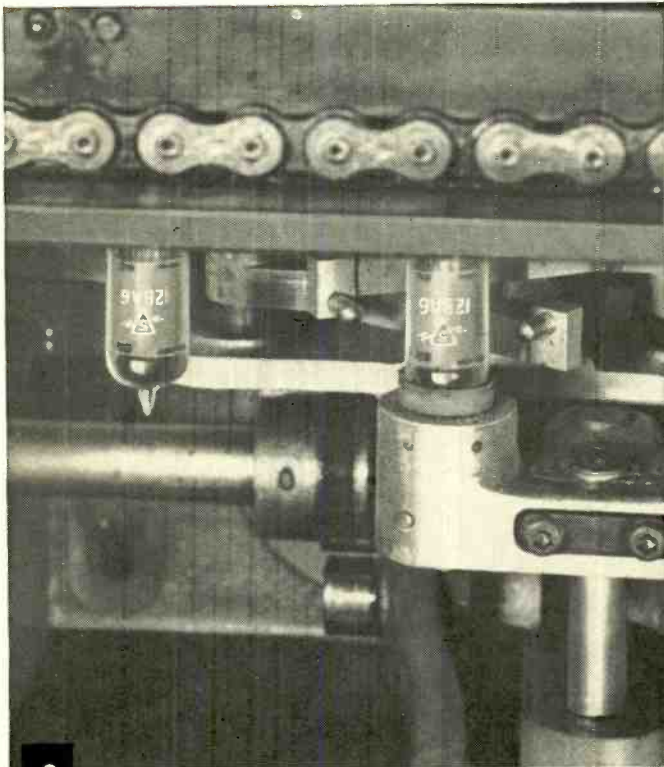

3

Close-up of tap test position. Here each tube is automatically tapped with 100 g (100 times gravity's force). Tube is tapped in two positions in two planes 90° apart—first for opens; second for shorts.



5

—Testing the tester. As a constant check on the accuracy of the automatic tester—samples from each lot tested, are retested on similar equipment used as a standard. Records are kept of all tests serving as data to feed back to design, manufacturing, and quality-control groups.

—where automation is at work to keep your tube stock free from “inoperatives”



For every four thousand tubes tested at Sylvania's plant in Williamsport, Pa., not more than one “inoperative” will escape Sylvania's automatic testing “dragnet” or reach your shelves.

Like Williamsport, all major tube-finishing plants are equipped with automated testers designed and built by Sylvania. Automation makes it possible to test each tube individually and more efficiently for *opens, shorts, leakage* and *emission*. As a result, Sylvania maintains the industry's lowest percentage of inoperatives. For you this means more efficient and profitable servicing—bothersome, time-consuming returns are kept to an absolute minimum.

Why not try using Sylvania exclusively as many dealers do? You'll find that's the best way to profit from Sylvania's exclusive testing program.



SYLVANIA

SYLVANIA ELECTRIC PRODUCTS INC.
1740 Broadway, New York 19, N. Y.
In Canada: Sylvania Electric (Canada) Ltd.
University Tower Bldg., Montreal

LIGHTING • TELEVISION • RADIO • ELECTRONICS
PHOTOGRAPHY • ATOMIC ENERGY • CHEMISTRY-METALLURGY

Mr. Independent Service Dealer:



When you buy tubes are you robbing yourself?

Not when you buy Raytheon TV and Radio Tubes

First of all, Raytheon has no factory TV-radio service organization that competes with you for profitable servicing business — you're not helping a "competitor" when you buy Raytheon Tubes.

Then, too, when you buy Raytheon TV and Radio Tubes you get the finest quality tubes money can buy — tubes designed for top performance in all makes and models of receivers. Raytheon does not manufacture sets and therefore must make tubes that will meet the rigid performance requirements of the many sets pro-

duced — tubes ideal for all replacement work.

And last, but by no means least, when you buy Raytheon Tubes you deal with local *independent* tube distributors who are anxious to give you the best in service and technical assistance. They are eager to supply you with the hundreds of helpful shop and sales aids Raytheon makes available for you — helps that make your job easier, more efficient and more profitable.

Make all of your tube dollars work for you — always ask your Tube Distributor for Raytheon quality TV and Radio Tubes.



RAYTHEON MANUFACTURING COMPANY

Receiving Tube and Semiconductor Operations

NEWTON 58, MASS.
55 Chapel Street

CHICAGO, ILL.
9501 Grand Ave. (Franklin Park)

ATLANTA 6, GA. 1150 Zonolite Rd. N.E.
LOS ANGELES 7, CALIF. 2419 So. Grand Ave.

Raytheon makes
all these

Receiving and Picture Tubes, Reliable Subminiature and Miniature Tubes,
Semiconductor Diodes and Transistors, Nucleonic Tubes, Microwave Tubes.




portable . . . or permanent



BOGEN FLEX-PAK[®]

MAKES EVERY PA JOB AN EASY ONE

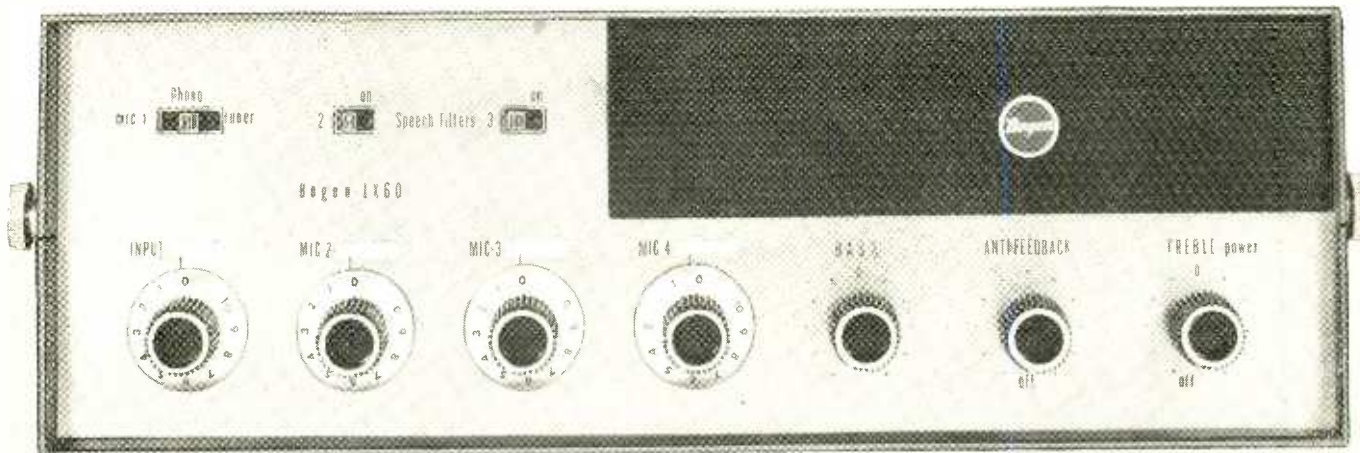

pre-engineered to serve 90% of your sound installations



Deluxe LX30 30-Watt Amplifier

4 Microphone Inputs (panel switch converts one microphone channel for phono or tuner); Built-In Remote Gain-Control Circuit; Exclusive Anti-Feedback Control; Speech Filters; Separate Bass and Treble Tone Controls.

H. 5 $\frac{3}{4}$ " W. 16 $\frac{1}{4}$ " D. 13" Wgt.: 25 lbs.



Superb LX30 30-Watt Amplifier


3 Microphone Inputs (panel switch converts one microphone channel for phono or tuner); Speech Filters; Separate Bass and Treble Tone Controls.

H. 5 $\frac{3}{4}$ " W. 14 $\frac{1}{4}$ " D. 13" Wgt.: 24 lbs.

BOGEN'S FLEX-PAK LINE has the flexibility you need to meet virtually every PA installation problem. Flex-Pak units are light, compact, portable, and can be used separately or grouped together. The amplifiers are available in every popular price range and power output . . . 13 models in all. That's why, with Flex-Pak, you can tailor the sound system to fit the job, with none of the fuss and bother of custom installations.

And remember—you can look to Bogen for *all* your sound equipment needs . . . speakers, microphones, turntables, tuners, and accessories. See your Bogen distributor today.

EASY SERVICE . . . EASY INSTALLATION

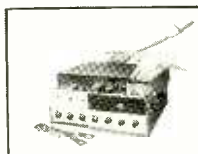


Loosen 4 thumbscrews and the lid's off for fast, easy servicing.



Folds back when not in use in easy-sliding wall-mount bracket.



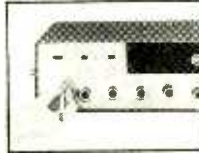4 thumbscrews attach accessory record player mount.



Easily erased write-in's on gain controls mark level settings.

Bogen EVERYTHING IN SOUND

A Division of The Siegler Corporation

David Bogen Company, Paramus, N. J., Dept. Q-5
Gentlemen: Please send me descriptive catalog on your BOGEN FLEX-PAK Public Address Equipment and 24-page, illustrated brochure, "What You Should Know About Sound Systems."

NAME _____


FIRM _____
Check one dealer distributor sound specialist

CITY _____ ZONE _____ STATE _____

MAIL COUPON TODAY

MANUFACTURERS OF HIGH-FIDELITY COMPONENTS PUBLIC ADDRESS EQUIPMENT AND INTERCOMMUNICATION SYSTEMS

For
“TOPS”
 in

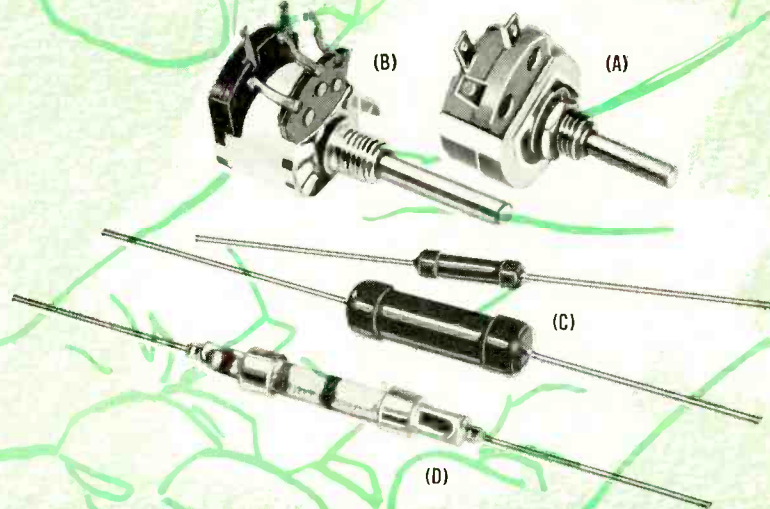

TRANSISTORIZED CIRCUITS

Clarostat*

Miniaturized Controls and Resistors

So typical of Clarostat's application engineering! These miniaturized controls and resistors are geared to transistorized circuits. They achieve the highest degree of space-saving consistent with high level of performance.

It takes specialized skill and long experience to produce such tiny controls and resistors. Clarostat, "The House of Resistors,"* places over three and a half decades of collaboration with electronic designers, engineers and manufacturers, at the disposal of transistor users. Count on Clarostat!

Typical Clarostat "Miniatures" . . .

- (A) Series 49 wire-wound potentiometer. Only 2½" dia. Molded phenolic casing. With or without switch. Single or dual. 1.5 watt rating. 1 to 20,000 ohms. Also Series 48 composition-element. ¾" dia. 0.2 watt rating. Linear, 200 ohms to 5 megohms; tapered, 1500 ohms to 2.5 megohms. With or without switch. Single or dual.
- (B) Boiled-down version of popular 1½" control, Series 44 is no bigger than a dime! 0.2 watt rating. 0.015 lb. 500 ohms to 5 megohms. With or without switch. Popular in hearing aids, pocket radios and other compact assemblies.
- (C) Fixtohm* deposited carbon precision resistors. ¼, ½, 1 and 2 watt ratings. Plus/minus 1% tolerance. Extremely stable. Excellent characteristics. Popular in critical electronic assemblies and fine instruments.
- (D) Glasohm* flexible power resistors. Wire winding on fiber-glass core. Fiber-glass braided covering. Axial pigtail leads. 2-watt rating. Plus/minus 10% standard tolerance. 5 to 2000 ohms.



Ask for literature. either from your local Clarostat distributor, or from us. Submit your transistorized requirements and problems to us.

*Reg. U. S. Pat. Off.

Controls and Resistors

CLAROSTAT MFG. CO., INC. • DOVER, NEW HAMPSHIRE
 In Canada: **CANADIAN MARCONI CO., LTD., Toronto 17, Ont.**

the experts say... in High Fidelity the best buys are **EICO**[®]

EICO
KITS and WIRED

BETTER ENGINEERING Since 1945 EICO has pioneered the concept of test instruments in easy-to-build kit form — has become world-famous for laboratory-precision instruments at low cost. Now EICO is applying its vast experience to the creative engineering of *high fidelity*. Result: high praise from such authorities as Canby of AUDIO, Marshall of AUDIOCRAFT, Holt of HIGH FIDELITY, Faniel of POPULAR ELECTRONICS, Stocklin of RADIO TV NEWS, etc. — as well as from the critical professional engineers in the field.†

SAVE 50% Mass purchasing, and a price policy deliberately aimed to encourage mass sales, make this possible.

EASY INSTRUCTIONS You need no previous technical or assembly experience to build any EICO kit — the instructions are simple, step-by-step, "beginner-tested."

DOUBLE 5-WAY GUARANTEE Both EICO, and your neighborhood distributor, guarantee the parts, instructions, performance . . . as well as *lifetime* service and calibration at nominal cost . . . for any EICO kit or wired unit.

BEFORE YOU BUY, COMPARE At any of 1200 neighborhood EICO distributors coast to coast, you may examine and listen to any EICO component. Compare critically with equipment several times the EICO cost — then you judge. You'll see why the experts recommend EICO, kit or wired, as best buy.

† Thousands of unsolicited testimonials on file.



HFS2
Speaker System



HFT90 FM Tuner
with "eye-ronic" tuning



HF61 Preamplifier



HF60, HF50 Power Amplifiers



HFS2 Speaker System: Uniform loading & natural bass 30-200 cps achieved via slot-loaded split conical bass horn — of 12-ft path. Middles & lower highs from front side of 8½" cone, edge-damped & stiffened for smooth uncolored response. Suspensionless, distortionless spike-shaped super-tweeter radiates *omni-directionally*. Flat 45-20,000 cps, useful to 30 cps. 16 ohms. HWD: 36", 15¼", 11½". " . . . rates as excellent . . . unusually musical . . . really non-directional" — Canby, AUDIO. "Very impressive" — Marshall (AUDIOCRAFT). Walnut or Mahogany, \$139.95. Blonde, \$144.95.

HFT90 FM Tuner equals or surpasses wired tuners up to 3X its cost. New, pre-wired, pre-aligned, temperature-compensated "front end" — drift-free. Sensitivity, 1.5 uv for 20 db quieting, is 6X that of other kit tuners. DM-70 traveling tuning eye. Response 20-20,000 cps±1 db. Cathode follower & multiplex outputs. Kit \$39.95*. Wired \$65.95*. Cover \$3.95. *Less cover, excise tax incl.

HF61A Preamplifier, providing the most complete control & switching facilities, and the finest design, offered in a kit preamplifier, " . . . rivals the most expensive preamps . . . is an example of high engineering skill which achieves fine performance with simple means and low cost." — Joseph Marshall, AUDIOCRAFT. HF61A KIT \$24.95, Wired \$37.95, HF61 (with Power Supply) Kit \$29.95. Wired \$44.95.

HF60 60-Watt Ultra Linear Power Amplifier, with Acro TO-330 Output Transformer, provides wide bandwidth, virtually absolute stability and flawless transient response. " . . . is one of the best-performing amplifiers extant; it is obviously an excellent buy." —AUDIOCRAFT Kit Report. Kit \$72.95. Wired \$99.95. Matching Cover E-2 \$4.50.

HF50 50-Watt Ultra-Linear Power Amplifier with extremely high quality Chicago Standard Output Transformer. Identical in every other respect to HF60 and same specifications up to 50 watts. Kit \$57.95. Wired \$87.95. Matching Cover E-2 \$4.50.

HF30 30-Watt Power Amplifier employs 4-EL84 high power sensitivity output tubes in push-pull parallel, permits Williamson circuit with large feedback & high stability. 2-EZ81 full-wave rectifiers for highly reliable power supply. Unmatched value in medium-power professional amplifiers. Kit \$39.95. Wired \$62.95. Matching Cover E-4 \$3.95.

HF-32 30-Watt Integrated Amplifier Kit \$57.95. Wired \$89.95.

HF52 50-Watt Integrated Amplifier with complete "front end" facilities and Chicago Standard Output Transformer. Ultra-Linear power amplifier essentially identical to HF50. The least expensive means to the highest audio quality resulting from distortion-free high power, virtually absolute stability, flawless transient response and "front end" versatility. Kit \$69.95. Wired \$109.95. Matching Cover E-1 \$4.50.

HF20 20-Watt Integrated Amplifier, complete with finest preamp-control facilities, excellent output transformer that handles 34 watts peak power, plus a full Ultra-Linear Williamson power amplifier circuit. Highly praised by purchasers, it is established as the outstanding value in amplifiers of this class. Kit \$49.95. Wired \$79.95. Matching Cover E-1 \$4.50.

*Prices 5% higher in the West

HF12 12-Watt Integrated Amplifier, absolutely free of "gimmicks", provides complete "front end" facilities & true fidelity performance of such excellence that we can recommend it for any medium-power high fidelity application. Two HF12's are excellent for stereo, each connecting directly to a tape head with no other electronic equipment required. Kit \$34.95. Wired \$57.95.

HF51 Two-Way Speaker System, complete with factory-built cabinet. Jensen 8" woofer, matching Jensen compression-driver exponential horn tweeter. Smooth clean bass; crisp extended highs. 70-12,000 cps ± 6 db. Capacity 25 w. Impedance 8 ohms. HWD: 11" x 23" x 9". Wiring time 15 min. Price \$39.95.

THE HI-FI EXPERTS SAY:

"For those who have been looking for a well-engineered yet inexpensive power amplifier, the newly-released EICO Model HF20 unit might offer a simple solution to their problem. Not only does this unit provide 20 watts of power but the circuit incorporates a preamplifier and a variety of controls on a single chassis."

William A. Stocklin, Editor, RADIO TV NEWS

"The new EICO 'standard' speaker system . . . produces sound that to my musical ears rates as excellent, from high top to clean low bottom."

Edward Talmall Canby, AUDIO Magazine

Fill out coupon on other side for FREE CATALOG



HF52, HF20
Integrated Amplifiers



HF12 Integrated Amplifier



HF30 Power Amplifier



HF51
Speaker System



33-00 Northern Boulevard, L. I. C. 1, N. Y.
Over 1 Million EICO instruments in use the world over.

©1958


the specs prove it . . .
your BEST BUY is

EICO®

for COLOR & Monochrome TV servicing

FREE CATALOG

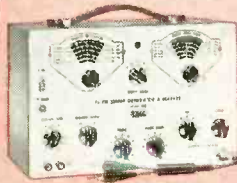shows you HOW TO SAVE 50%
on 50 models of top quality
professional test equipment.
MAIL COUPON NOW!




NEW!
**TV-FM SWEEP
GENERATOR &
MARKER #368**
KIT \$69⁹⁵ WIRED \$119⁹⁵

Entirely electronic sweep circuit (no mechanical devices) with accurately-biased inductor for excellent linearity. Extremely flat RF output: new AGC circuit automatically adjusts osc. for max. output on each band with min. ampl. variations. Exceptional tuning accuracy: edge-lit hairlines eliminate parallax. Swept Osc. Range 3-216 mc in 5 fund. bands. Variable Marker Range 2-75 mc in 3 fund. bands; 60-225 mc on harmonic band. 4.5 mc Xtal Marker Osc., xtal supplied. Ext. Marker provision. Sweep Width 0-3 mc lowest max. deviation to 0-30 mc highest max. dev. 2-way blanking. Narrow range phasing. Attenuators: Marker Size, RF Fine, RF Coarse (4-step decade). Cables: output, 'scope horiz., 'scope vertical. Deep-etched satin aluminum panel; rugged grey wrinkle steel cabinet.

**NEW! RF
SIGNAL GENERATOR
#324**
KIT \$26⁹⁵ WIRED \$39⁹⁵




150 kc to 435 mc with ONE generator! Better value than generators selling at 2 or 3 times its cost! Ideal for IF-RF alignment, signal tracing & trouble shooting of TV, FM, AM sets; marker gen.; 400 cps audio testing; lab. work. 6 fund. ranges: 150-100 kc, 400-1200 kc, 1.2-3.5 mc, 3.5-11 mc, 11-37 mc, 37-145 mc; 1 harmonic band 111-435 mc. Freq. accurate to ±1.5%; 6:1 vernier tuning & excellent spread at most important alignment freqs. Etched tuning dial, plexiglass windows, edge-lit hairlines. Colpitts RF osc. directly plate-modulated by K-follower for improved mod. Variable depth of int. mod. 0-5C% by 400 cps Colpitts osc. Variable gain ext. amplifier: only 3.0 v needed for 30% mod. Turret-mounted coils slug-tuned for max. accuracy. Fine & Coarse (3-step) RF attenuators. RF output 100,000 uv; AF sine wave output to 10 v. 50-ohm output Z. 5-way jack-top binding posts for AF in/out; coaxial connector & shielded cable for RF out. 12AU7, 12AV7, selenium rectifier; xmfr-operated. Deep-etched satin aluminum panel; rugged grey wrinkle steel cabinet.

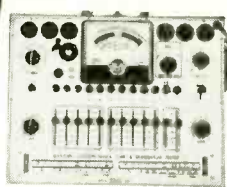

**NEW! DYNAMIC
CONDUCTANCE
TUBE & TRANSISTOR
TESTER #666**
KIT \$69⁹⁵ WIRED \$109⁹⁵

COMPLETE with steel cover and handle.
SPEED, ease, unexcelled accuracy & thoroughness. Tests all receiving tubes (and picture tubes with adapter). Composite indication of Gm, Gp & peak emission. Simultaneous set of any 1 of 4 combinations of 3 plate voltages, 3 screen voltages, 3 ranges of continuously variable grid voltage (with 5% accurate pot). New series-string voltages: for 600, 450, 300 ma types. Sensitive 200 ua meter. 5 ranges meter sensitivity (1% shunts & 5% pot). 10 SIX-position lever switches: freepoint connection of each tube pin. 10 pushbuttons: rapid insert of any tube element in leakage test circuit & speedy sel. of individual sections of multi-section tubes in merit tests. Direct-reading of inter-element leakage in ohms. New gear-driven rollehart. Checks n-p-n & p-n-p transistors: separate meter readings of collector leakage current & Beta using internal dc power supply. Deep-etched satin aluminum panel; rugged grey wrinkle steel cabinet. CRA Adapter \$4.50

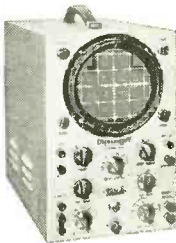

NEW!
**COLOR
and Monochrome
DC to 5 MC LAB & TV
5" OSCILLOSCOPE
#460**
KIT \$79⁹⁵ WIRED \$129⁵⁰
• Features DC Amplifiers!

Flat from DC-4.5 mc, usable to 10 mc. VERT. AMPL.: sens. 25 rms mv/in; input Z 3 megs; direct-coupled & push-pull thruout; K-follower coupling bet. stages; 4-step freq-compensated attenuator up to 1000:1. SWEEP: perfectly linear 10 cps-100 kc (ext. cap. for range to 1 cps); preset TV V&H positions; auto. sync. ampl. & lin. PLUS: direct or cap. coupling; bal. or unbal. inputs; edge-lit engraved lucite graph screen; dimmer; filter; bezel fits std photo equip. High intensity trace CRT. 0.06 usec rise time. Push-pull hor. ampl., flat to 400 kc, sens. 0.6 rms mv/in. Built-in volt. calib. Z-axis mod. Sawtooth & 60 cps outputs. Astig. control. Retrace blanking. Phasing control.




**NEW! PEAK-to-PEAK
VTVM #232 & UNI-
PROBE (pat. pend.)**
KIT \$29⁹⁵ WIRED \$49⁹⁵

Half-turn of probe tip selects DC or AC-Ohms. Uni-Probe - exclusive with EICO - only 1 probe performs all functions!

Latest circuitry, high sensitivity & precision, wide ranges & versatility. Calibration without removing from cabinet. New balanced bridge circuit. High Z input for negligible loading. 4½" meter, can't burn-out circuit. 7 non-skip ranges on every function. 4 functions: +DC Volts, -DC Volts, AC Volts, Ohms. Uniform 3 to 1 scale ratio for extreme wide-range accuracy. Zero center. One zero-adj. for all functions & ranges. 1% precision ceramic multiplier resistors. Measure directly peak-to-peak voltage of complex & sine waves: 0-4, 14, 42, 140, 420, 1400, 4200. DC/RMS sine volts: 0-1.5, 5, 15, 50, 150, 500, 1500 (up to 30,000 v with HVP probe & 250 mc with PRF probe). Ohms: 0.2 ohms to 1000 megs. 12AU7, 6AL5, selenium rectifier; xmfr-operated. Deep-etched satin aluminum panel, rugged grey wrinkle steel cabinet.




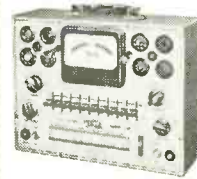**5" PUSH-PULL
OSCILLOSCOPE
#425**
KIT \$44.95
Wired \$79.95




**7" PUSH-PULL
OSCILLOSCOPE
#470**
KIT \$79.95
Wired \$129.50

Pix Tube Test Adapter\$4.50

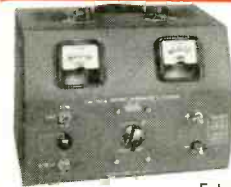

**6V & 12V
Battery Elim
& Charger
#1050:**
KIT \$29.95
Wired \$38.95

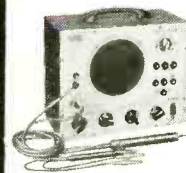Extra filtered for transistorized eqpt, #1060:
KIT \$38.95, Wired \$47.95



Sep. hi-gain RF & lo-gain audio inputs. Special noise locator. Calibrated wattmeter.
KIT \$24.95
Wired \$39.95


DELUXE MULTI-SIGNAL TRACER #147



**20,000 Ohms/Volt
MULTIMETER #565**
KIT 24.95
Wired 29.95



**1000 Ohms/Volt
MULTIMETER
#536**
KIT \$12.90
Wired \$14.90

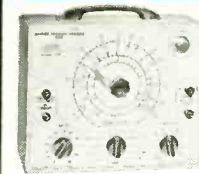

Reads 0.5 ohms - 500 megs, 10 mmd-5000 mfd, power factor.

KIT \$19.95
Wired \$29.95

R-C BRIDGE & R-C-L COMPARATOR #950B



VTVM PROBES	KIT	Wired
Peak-to-Peak	\$4.95	\$6.95
RF	\$3.75	\$4.95
High Voltage Probe-1	\$6.95	
High Voltage Probe-2	\$4.95	

SCOPE PROBES	KIT	Wired
Demodulator	\$3.75	\$5.75
Direct	\$2.75	\$3.95
Low Capacity	\$3.75	\$5.75

EICO, 33-00 Northern Blvd. Long Island City 1, N. Y.

C-5

Show me HOW TO SAVE 50% on Test Equipment and Hi-Fi. Send me FREE Catalog and name of neighborhood distributor.

Name.....
Address.....
City..... Zone..... State.....

TURN PAGE
FOR MORE
EICO VALUES

EICO®

Send for
FREE CATALOG
now

Prices 5% higher on West Coast.

33-00 Northern Blvd., Long Island City 1, N.Y.

TRANSISTOR TRENDS

... Transistor Evolution Has Only Begun ...

BEFORE 1948—a brief decade ago—the transistor was unknown. Electronics, with a few exceptions, was based chiefly on the vacuum tube, which in various ways supplied us with the indispensable stream of electrons for our instrumentation. Free “hot” electrons were generated in incandescent filaments or heated cathodes, which had their initial start in the Edison effect in 1883.

The transistor ushered in a new and revolutionary era which in many ways repeated—and often excelled—the history of the vacuum tube. It did away with heated filaments and cathodes and, consequently, with the cumbersome and uneconomic heating currents. Instead of the vacuum tube’s “hot” electrons, the transistor works with free, “cold” electrons.

Nor does the transistor require the high voltages needed by the vacuum tube for its best functioning. Less than 15 volts is required in the average transistor radio set, as contrasted to the 115 to 300 volts of the vacuum-tube receiver.

Great as the transistor’s progress has been to date, its evolution has but begun. In the beginning, great difficulties in manufacture were encountered. Over 80% of all assembled transistors were rejected. This trouble has now been mostly overcome and the industry is settling down to mass production with smaller and smaller percentages of rejections.

In 1955, when we produced only 12¼ million transistors—against 28¼ million in 1957—the present writer in the August, 1955, editorial ventured the opinion that 50c (retail) transistors were on the horizon. (Vacuum tubes sold for 33c each wholesale in 1955.) It is thus not surprising that recently a high-placed spokesman of the industry predicted that 25c transistors are now a distinct possibility.

So far transistor production lags far behind vacuum-tube manufacture. The reasons for this great disparity are simple. Vacuum tubes wear out and break. Transistors are most rugged and so far no one has determined how long they will last. A probable life may be 50 years. Hence, there may not be much of a replacement market for generations. Further, transistor radios are still in the luxury class—they cost almost twice as much as comparative vacuum-tube sets. Why? Being, as a rule, so much smaller, they are more tedious to assemble and the miniature parts are more expensive, as is the labor. This, however, is a transitory stage, familiar to the industry. The day will come when good six- to eight-transistor sets will sell for around \$10—not this year or next, but in the foreseeable future. The reason for this forecast is, of course, automation—mass production.

One of the reasons for the more than 100% manufacturing increase of transistors last year is found in the flood of new types. In 1956 there were only about 275 transistor types. Now there are over 750! And this rapid increase will continue for a long time.

New uses for transistors are found daily. Research in practically every endeavor and art requires advanced and specialized types. This trend is increasing.

Take, for instance, space electronics. One cannot well imagine a modern rocket or a satellite without a vast array of many types of transistors—all built with an eye to shock-proof ruggedness, minimum weight and minimum dimensions.

From outer space to a defective beating heart may be a far jump, but it demonstrates the ubiquity of the transistor. Recently, Dr. Folkman of Children’s Medical Center and Dr. Watkins of Harvard Medical School visualized how a defective heart block could be corrected, thus saving the patient’s life. They knew that a blocked ventricle could be stimulated and made to contract electrically by applying electrodes to it. An electronic consultant, C. F. Vanderschmidt, constructed a tiny R-C-coupled, two-transistor amplifier. It amplifies the minute 5-millivolt auricular pulse into an 0.5-volt pulse required to contract the ventricle.

A dog with a heart block was used for the first experiment. He was operated on and electrodes sewn to the right auricle and right ventricle. Special insulated stainless steel wires connected the heart electrodes to the amplifier, which in turn was firmly attached to the dog’s back. His recovery was uneventful and rapid. Subsequent improvement in technique gave affected dogs a life of several months. It probably will not be many years before humans with heart blocks, instead of resting in their graves, will be walking the streets with tiny transistor amplifiers firmly strapped to their chests.


Despite the 750 existing transistor types, here are a few important needed ones, which are distinct future possibilities. Let us remember—the transistor has only begun.

Atomic Transistors, frequently mentioned in this magazine, are technically feasible and have been demonstrated in the laboratory. Such a type, when finally evolved commercially, will make radio and television sets independent of batteries and outside current supply. They will last for many years without attention. They will all be truly portable and can be used and operated anywhere. Their upkeep will be minimal.

Transistor Picture Tubes. Today’s television scanning tubes are of the cathode-ray variety. To function, they must use a high voltage (15,000 and over) and the electron beam must oscillate rapidly from side to side. In the future, it is almost certain that the huge television picture tube of the present will not prevail. Already there are a number of patents for thin and flat picture tubes. All of these, however, still require high operating voltages.

We can imagine the future flat-thin TV picture tube, atom-transistor equipped in which electroluminescence is used to produce the image. The entire screen is made up of several hundred thousand electroluminescent points, all “steered” by transistors. The latter, being atomic, supply a sufficient current to light the screen vividly. There will be no moving ray, no motion at all. Only luminiscent points, lighting, extinguishing as necessary to create the image. Such a TV receiver will be truly portable, even in a large screen size. Self-powered, it can be used anywhere within reach of a TV transmitter.

—H.G.

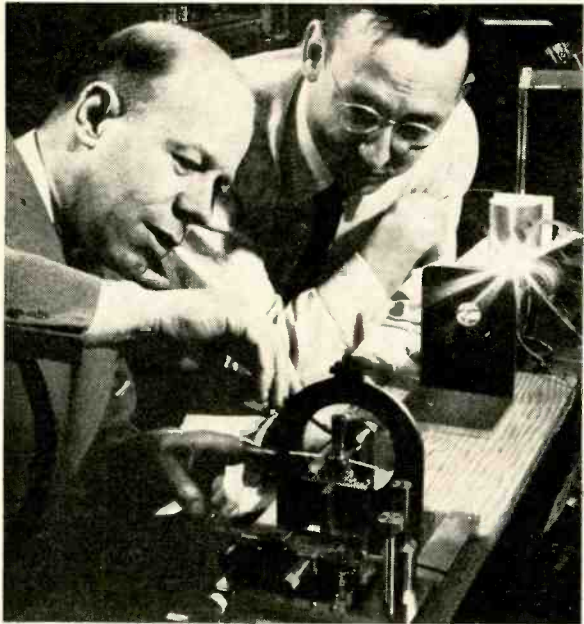

Testing the alignment of phototransistors used to "read" information stored by electronic computers, are Dr. J. N. Shive (left), who developed the phototransistor and Dr. R. M. Ryder, both of Bell Telephone Laboratories.

end of the bar. By repeated sweeps, undesirable impurities can be reduced to less than 1 part in 1,000,000,000. The technique takes advantage of the fact that the solubility of impurities in liquid semiconductor material is different from the solubility in the solid.

The importance of the purification process is apparent when you realize that active impurities of as little as 1 part in 1,000,000,000 can affect transistor operation. It is essential that the material be as pure as possible to begin with, so that the desirable properties can be obtained by introducing controlled amounts of the desired impurity.

Throughout the semiconductor development process, efforts were made to improve the frequency range of transistors, both as oscillators and as amplifiers. One approach was to reduce the thickness of the center layer of the sandwich, but certain limitations were encountered. A major step in overcoming these limitations was achieved with the invention of the tetrode transistor⁷. By 1955, this transistor had been developed to the point where it could be made to oscillate at more than 1,000 mc, thus breaking into the microwave region for the first time with solid-state amplifiers.

Operation at such high frequencies was achieved by adding a fourth electrode to the basic junction transistor, plus other refinements. This fourth electrode permitted the center layer of the transistor to be biased in a way that reduced its effective thickness. This, combined with an actual reduction in thickness to less than 0.2 mil, provided operation at ultra high frequencies.

The field-effect transistor

The foregoing discussion has revolved around a particular type of transistor

⁷R. L. Wallace, Jr., L. G. Schimpf and El Dikten, "A Junction Transistor Tetrode for High-Frequency Use"; *Proceedings of the IRE*, Vol. 40, p. 1395, November, 1952.

action, namely the injection of charge carriers by a p-n type junction into a thin slice of semiconductor and their collection by another junction. It is also possible to get amplification by other means, as in the field-effect transistor, where a transverse electric field controls the flow of current. A number of such "unipolar" transistors were described by Shockley in 1952⁸. This type of operation may have important advantages; in particular, high input impedance of the order of 10 megohms and the possibility of very high frequency response. Very similar in concept are the "analog" transistor and the spaciator.

A field-effect transistor using an external "gate" is shown schematically in Fig. 3, while Fig. 4 shows a field-effect transistor using a p-n junction to produce a capacitor "gate" within the body of the semiconductor.

Another significant step in high-power and high-frequency operation was the introduction of the p-n-i-p, or "intrinsic-barrier" transistor⁹. This transistor is in essence a club sandwich, in which a layer of comparatively pure material is interposed between two of the layers of a conventional transistor. This layer permits closer control of the stream of charge carriers, isolates input and output areas and reduces the stored energy to make functioning at higher frequencies possible. The increased separation of input and output areas also permits operation at higher voltages than possible with earlier transistors. The intrinsic layer might be compared very roughly with the screen grid in a vacuum tube.

Intrinsic barrier type transistors can provide uniform amplification over bands of hundreds of megacycles, and theoretically units can be made which

⁸W. Shockley, "A Unipolar Field-Effect Transistor"; *Proceedings of the IRE*, Vol. 40, p. 1377, November, 1952.

⁹J. M. Early, "P-n-i-p and N-p-i-n Junction Transistor Triodes"; *Bell System Technical Journal*, Vol. 33, p. 517, May, 1954.

will oscillate at 3,000 mc. They can also be designed to produce some 3 to 10 times more power than earlier junction transistors at high frequencies.

The surface-barrier transistor¹ represented another step toward high-frequency operation. In this unit, both sides of a thin wafer of germanium are electrolytically etched away until only an extremely thin layer remains. Electrodes are then deposited electrolytically. Because of the very thin base layer, high-frequency operation is possible. This transistor has since been further improved by incorporating a diffused base and by closely controlled alloying of the junctions.

The diffusion technique

In 1954, Bell Laboratories announced a development which has proved to be a major breakthrough in transistor technology — the diffusion technique. Diffusion is a process by which minute amounts of impurities are introduced into a material in a controlled manner. As mentioned previously, one of the limitations in extending the operation of conventional junction transistors to ever higher and higher frequencies is the difficulty of reducing the thickness of the center layer of the transistor sandwich. By introducing impurities in a controlled manner by the diffusion process, this layer can be made as thin as 30/1,000,000 inch.

The diffusion technique^{8,9} can be used for other semiconductor devices as well. Among these devices is the Bell solar battery.¹⁰ This battery consists of a thin wafer cut from a single crystal of n-type silicon into which a small amount of boron has been diffused to produce a thin layer of p-type silicon. When illuminated, this cell produces electricity. In direct sunlight, its conversion efficiency may run as high as 11%.

¹W. E. Bradley, et al, *Proceedings of the IRE*, December, 1953.

⁸M. Tanenbaum, D. E. Thomas and C. A. Lee, "Diffused Emitters and Bases for Silicon and Germanium Transistors"; *Bell System Technical Journal*, January, 1956.

⁹C. S. Fuller and J. A. Ditzenberger, "Diffusion of Donor and Acceptor Elements in Silicon"; *Journal of Applied Physics*, Vol. 27, May, 1956.

¹⁰D. M. Chapin, C. S. Fuller and G. L. Pearson, "The Bell Solar Battery"; *Bell Laboratories Record*, July, 1955.

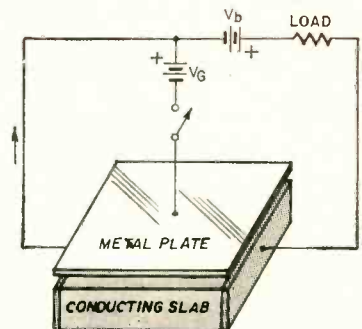


Fig. 3—Schematic representation of field-effect transistor in a cross-section designed to illustrate how curby applying the slab can be controlled by a voltage to the metal plate.

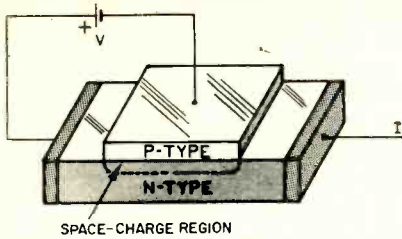


Fig. 4—A field-effect transistor using a p-n junction to produce a “capacitor” within the body of the semiconductor. A voltage that is applied between the p- and n-type material causes a penetration of space charge, creating a region within the body of the n-type material that will not contribute to current flow through the semiconductor.

At present, it appears that the diffusion technique will achieve widespread recognition as a reliable, controllable process for making transistors and many other semiconductor devices. Enough information has been obtained on this process to make it adaptable to mass-production operations. Units have been fabricated which will oscillate and amplify at well over 1,000 mc, and the frequency barriers are continually being forced higher and higher.

The “drift transistor” emphasizes another feature which has importance for high-frequency transistors.¹¹ By control of the distribution of impurities in the thin central layer, one can obtain a “built-in” electrical field which speeds up the electron stream and thereby makes the transistor somewhat faster. Experimentally, the easiest way to achieve an appropriate structure is by diffusing the base as just mentioned above. Typically, the frequency response improves 10 or 100 times by making the base layer thinner while the built-in field gives a further improvement of the order of 1.5–4 times.

Last year a new device was announced which combines high-frequency operation with high-power output to an extent not previously attained. This new transistor can provide an output of better than 5 watts at 10 mc, either as an oscillator or an amplifier. It has alpha-cutoff frequency of about 100 mc and has produced an output of better than 1 watt at this frequency.

To achieve the combination of high power and high frequency required extensive research and the utilization of many different techniques. The unit employs the basic p-n-i-p type of construction and so takes advantage of the intrinsic-layer idea. Silicon is employed to permit operation at higher temperatures and thus allow greater heat dissipation. Diffusion techniques are used to form the emitter and collector regions. And the electrode areas themselves are kept as small as possible consistent with the desired power-handling capacity. Thus, by combining a number of techniques, both frequency and power barriers have been lifted.

¹¹ H. Kromer, “Theory of the Germanium Rectifier and the Transistor”; *Zeitschrift Physik*, Vol. 134, pp. 435–50, March 25, 1953.

Electronic computing machines are one of the newest fields that transistors are expected to dominate because of their size, power, speed and reliability. Closely related is the field of automatic telephone switching, which now uses electromechanical switches such as relays but which is expected to go increasingly electronic in coming years. A prominent new device for use here is expected to be the p-n-p-n diode, a four-region transistor switch, invented by Shockley. As now realized in diffusion techniques in silicon, the device in the off condition has a resistance of 100 megohms. When switched on either by a pulse or by a high voltage, its on resistance is only about 2 ohms, with a less than 1-volt sustaining voltage. The device can be switched between these conditions at megacycle rates if necessary.

New fabricating processes

A major problem in fabricating transistors, particularly those intended for high-frequency operation, is attaching leads to the semiconductor material. A significant advance in this field is the development of the thermocompression bonding technique at Bell Laboratories. In this technique, the leads are attached by a combination of temperature, pressure and time. One method that works very satisfactorily in the laboratory is to force the lead against the semiconductor surface with a heat-

ed wedge-shaped tool. Neither the temperature nor the pressure is great enough to damage the semiconductor surface nor to introduce any impurities, and the time can be kept short enough to permit rapid assembly.

Advantages of this method over soldering or welding are many. There is less danger of contamination; leads can be attached to very small areas—particularly useful in high-frequency transistors—and the bond between the lead and the semiconductor is stronger than the lead itself.

Although today’s practical transistors all use germanium or silicon, at least passing mention must be made of a new family of materials called intermetallic semiconductors. Silicon and germanium are in Group IV of the periodic chart; that is, they each contain four valence electrons in the outer ring. Compounds formed by taking elements from Group III (three valence electrons) and Group V (five valence electrons) will have an “average” of four valence electrons, and thus may exhibit characteristics similar to the materials now used.

A great deal of exploratory work is being carried out in laboratories both in this country and abroad to determine the characteristics of these intermetallic compounds. Particularly active in this field is H. Welker, in Germany. Results have been very encouraging—it appears that these materials may be useful for producing more versatile transistors and other devices. In fact, intermetallic diodes are now on the market. Notable among the compounds under investigation are indium antimonide, gallium arsenide and indium phosphide.

More complex compounds having an average of four valence electrons in the outer ring are also being investigated, and it is reasonable to expect that within a few years materials will be available which are superior in specific areas to either germanium or silicon.

Important areas of exploration, at present, are in the areas of surface phenomena and external contamination. To produce reliable transistors having the desired characteristics without excessive rejects requires careful control of all the steps in the manufacturing process, with particular emphasis on avoiding contamination of any kind. Past efforts in this direction have paid off handsomely. Work is also under way to increase power and frequency capabilities of transistors to approach more closely the performance now available from electron tubes.

An attempt has been made here to touch on the highlights of the last 10 years of transistor development. Many important contributions and contributors have of necessity been omitted for lack of space. It is important to emphasize that in this field, as well as any other scientific endeavor, notable advances are the result of the combined efforts of a number of scientists striving to unlock the secrets of nature. END

The Author

Robert M. Ryder was born March 8, 1915, in Yonkers, N. Y. He graduated from Yale in 1937, receiving a Bachelor of Science degree in physics. He obtained a PhD degree, also from Yale, in 1940.

In July, 1940, he became a member of the technical staff of Bell Labs, working on microwave amplifier circuits. During World War II, he contributed to Bell Labs’ research on the signal-to-noise performance of radars. In 1945, he joined the Electronic Development Department to work on microwave oscillators and amplifier tubes for radar and radio relay applications. He is currently a transistor development engineer, particularly interested in transistor development for high-frequency and other transmission applications.

In 1957, Dr. Ryder received an award from the Institute of Radio Engineers “for contributions to the development of microwave tubes and applications of transistors.”

He is a member of the American Association for the Development of Science, Sigma Xi and the Yale Engineering Society.

TRANSISTORS

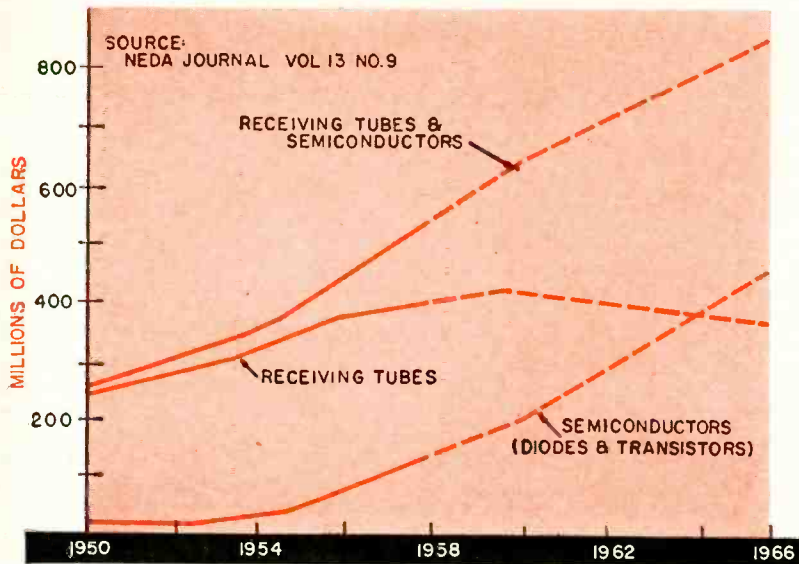


Fig. 1—The trend in semiconductor vs receiving tube sales.

A survey of the uses of transistors from their inception, 10 years ago, to their predicted future

By **GEORGE R. SPENCER***

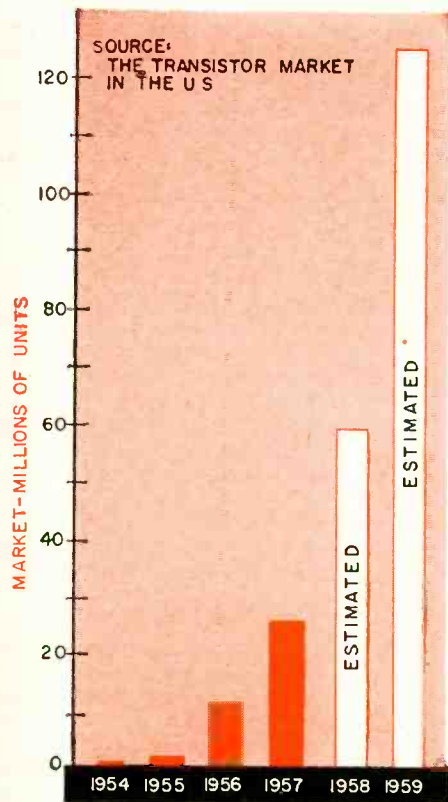


Fig. 2—Six-year survey of transistor sales.

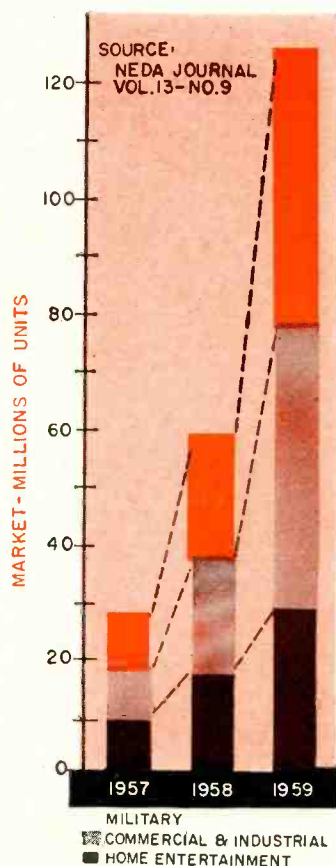


Fig. 3 (right)—Projected transistor sales broken up into types of application.

A DECADE has passed since Bardeen and Brattain of Bell Telephone Laboratories announced the invention of the transistor. At that time the transistor was expected immediately to rival the vacuum tube for many of the amplifier applications that the vacuum tube held as a monopoly. The advantages of this new device were its small size, predicted long life, ruggedness and, of course, the lack of heater power.

However, as might be expected for a new invention, development into commercial reality was slow and beset by many obstacles. The operation of these devices was understood in a general way, but the commercial practicability of the transistor was not feasible as a large area of unexplained and puzzling limitations in their manufacture still existed. Some of these limitations were:

1. *Performance*—Early transistors were characterized by low gain, poor noise figure, low frequency response and poor power-handling capabilities. Furthermore, it was difficult to design and develop transistors to overcome these deficiencies.

2. *Reproducibility*—Units intended to be alike varied considerably from one another. Improved manufacturing processes and material combined with a better technological understanding of transistor devices have resulted in transistor production becoming more of

*Raytheon Manufacturing Co., Semiconductor Div., Newton, Mass.

a science and less of an art. However, a fundamental difference still exists between vacuum tubes and transistors. Tubes are generally manufactured to be a given type, while transistors are manufactured to be a family separated into two to several types by selective testing.

3. *Poor reliability*—Certain percentages of the devices changed excessively with time, temperature or humidity, while others remained stable. The early problems affecting reliability are now minimized to the extent that the transistor's *inherent* ruggedness and long life can be realized. These inherent properties can be appreciated by comparing the complex structure of a vacuum tube to the relatively simple mechanics of a transistor, and by recalling that the life of a vacuum tube is dependent on how long its cathode will support emission.


These limitations resulted directly in poor availability and high initial cost of transistors for the first few years after their invention. As a result, their application and use in commercial and military equipment were on a small scale compared to the existing market for vacuum tubes. This first 10 years of transistor progress has shown considerable improvement over these limitations and transistors are now available with good engineering performance at a competitive price. Furthermore, there is a definite trend toward standardizing packages and types. For example, the 2N425, 2N426, 2N427 and 2N428, germanium n-p-n computer types, are manufactured by three separate companies in the standard JETEC 30 case, a package which is also common to numerous other types.

The growth of transistor sales since 1948 has been tremendous and should continue for the next decade with the same acceleration. Fig. 1 shows the overall sales growth of semiconductors (transistors and diodes) compared to that of receiving tubes and is projected to the year 1965. This chart indicates that, although increasing technology will increase the number of amplifier and related applications, the sale of receiving tubes is expected to level off and eventually decline during the next decade.

Fig. 2, a chart of the transistor market, projected to 1959, indicates that 125 million transistors will have been sold in 1957. The question that arises is: in what applications have these transistors been used and what applications are likely in the future? Also of interest are the fields that transistors are least likely to invade in the near future—those fields where receiving tubes will maintain definite advantages.


10 years of transistor progress

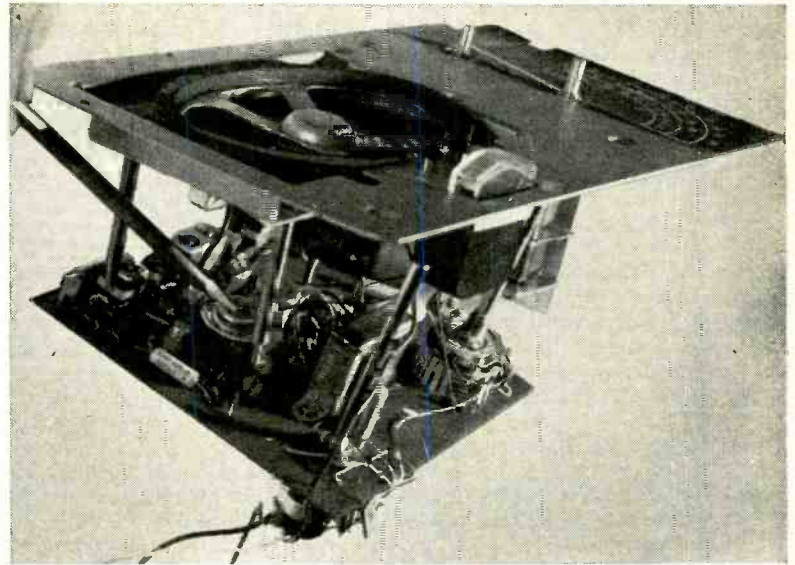About 30 companies in the United States are manufacturing transistors, and there are over 500 EIA types now registered, in addition to more than 400 non-EIA types. These can be classified broadly as point contact, junction



(Above) Internal view of an all-transistor direction finder. Pencil points at a power transistor.

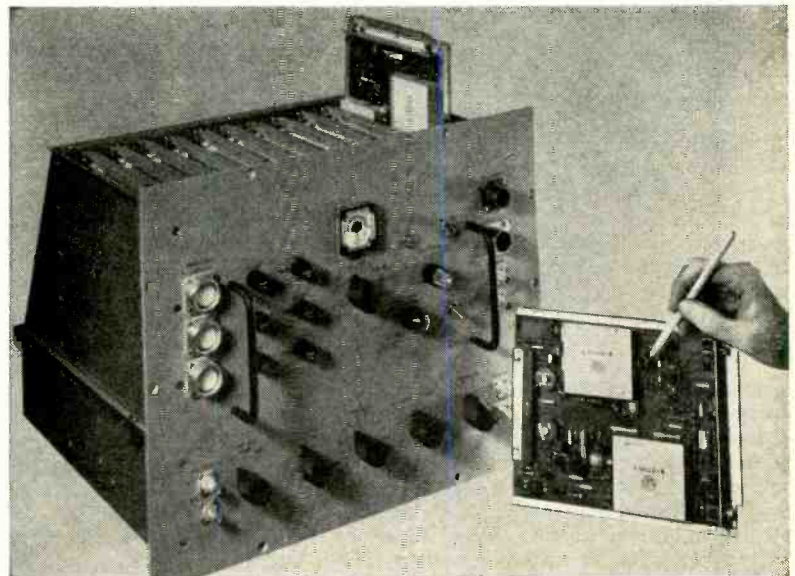(Below) This transistor pulse code modulator allows simultaneous transmission of multiple channels of information in coded form.



or surface barrier; with the point-contact transistors now relegated to a minor role. A review of EIA types indicates that the following characteristics are now available, which clearly shows the progress made in the last decade.

1. *Frequency response*—The low-frequency response of early transistors limited their application to a large degree. The alpha-cutoff frequency characteristic of a transistor is frequently used to predict frequency response for a given application as it is the frequency at which the common base current amplification drops to 70% of its low-frequency value. The alpha-cutoff frequency of transistors is limited by the time it takes the signal carriers (electrons or holes) to diffuse or move from emitter (input) to collector (out-

put). Recent techniques in the construction of transistors have extended this upper operating frequency limit an order of magnitude, and transistors are now available that operate throughout the vhf well into the uhf band. The 2N502, a Philco microalloy diffused-base transistor (MADT) will give a minimum power gain of 8 db at 200 mc and has a maximum frequency of oscillation over 500 mc.

2. *Power and temperature*—Transistors were limited, to a large extent, by their inability to give satisfactory gain at the high current levels needed for power stages. Power transistors are now available that will stand more than 40 watts of collector dissipation at 25°C and give a class-A gain in excess of 30 db. Typical of these is the Motorola type MN21, a germanium

p-n-p power transistor rated at 45 watts at 25°C with a power gain of 35-40 db in a class-A single-ended circuit. This unit is also rated for a maximum collector to base voltage of 80.

Transistor performance depends on the surrounding ambient temperature to a much greater degree than vacuum tubes. Germanium transistors are generally rated for a maximum junction temperature of 75° to 100°C, whereas silicon transistors are usually rated for a maximum of 160° to 200°C. As power dissipation raises the internal junction temperature higher than the surrounding ambient temperature, precautions must be taken to assure that power dissipation does not raise the internal temperature over the allowable rating. For example, a germanium transistor rated for 40 watts at 25°C ambient temperature might be limited to 10 watts dissipation at 80°C.

The availability of silicon transistors means that applications requiring a minimum power dissipation at high ambient temperatures can now be fulfilled by transistors. Furthermore, collector current of a silicon transistor with its emitter open-circuited (cutoff current) is typically 100 to 1,000 times lower than for a germanium counterpart. This low cutoff current has resulted in the use of transistors in dc amplifiers and similar critical applications, as cutoff current doubles with every 8° to 10°C rise in temperature. Although a typical value of 10 μa dc for a germanium transistor does not seem excessive, the effect of collector cutoff current of a common-emitter amplifier is usually 10 to 100 times higher, depending on the input termination to the amplifier and the alpha (short-circuit current gain) of the transistor.

Silicon transistors cost more than germanium types and their main use has been in military applications where operation over a wide range of temperatures is necessary. Typical is the use of Raytheon 2N329 transistors in both the Vanguard and Explorer satellites. This higher cost of silicon transistors may not continue forever if refinement processes can be improved to


produce lower-cost refined silicon. This also could result in the obsolescence of germanium transistors.

3. *Noise*—Today there are many audio transistors that have equal or better signal-noise ratios than vacuum tubes; examples are Raytheon's 2N422, RCA's 2N105 and Philco's 2N204-A. Raytheon's type 2N422, a germanium p-n-p transistor, is a typical low-noise unit presently available. It has a maximum noise figure of 6.5 db, and its size is such that over 350 units (exclusive of leads) could fit in a volume of 1 cubic inch. Low noise figure coupled with no heater power to give hum troubles has resulted in the transistor finding wide usage in preamplifier circuits. The transistor portable radio with sensitivity comparable to receiving tube sets and the use of transistors in commercial hearing aids are evidence of their advantages in applications where noise problems could be prevalent.

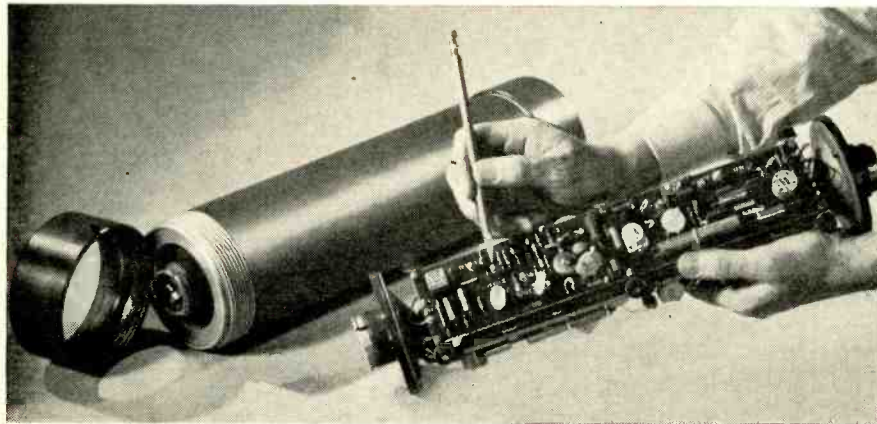4. *Reliability*—The early encapsulation of transistors was not adequate for all applications. Transistors were apt to fail under extreme moisture conditions or when subjected to high heat. Considerable work has been done on the development of hermetic seal encapsulations with the result that reliability is now excellent.

For example, in a recent test at Raytheon a random group of 200 germanium switching transistors were life-tested for 1,000 hours (200,000 transistor hours). One half of the lot was operated at 45-mw dissipation at 65°C (149°F), the remaining units were storage-tested at 85°C (185°F) with no operating voltages. There were no failures, and the average current gain of the transistors showed only a negligible change with life. Raytheon also has data which indicates that their fusion-alloy process of manufacture results in less than one open in 800,000 hours. This data was secured on life tests over the last 2 years.

During 1958, transistor production is expected to rise to 60 million units (Fig. 3). Of these, 55,000,000 will be germanium and 5,000,000 will be silicon types. Approximately 17,000,000 units



Transistor line repeater developed for the US Signal Corps. These units are inserted at 1-mile intervals along the transmission cable.

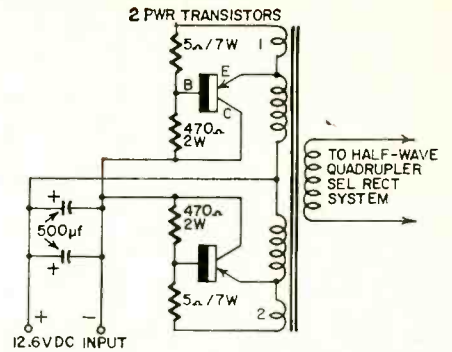


Fig. 4—Primary circuit of the Telecom 2D11 transistor power converter. Windings 1 and 2 are feedback windings for maintaining oscillations.

will be used for radios and consumer electronic products, 22,000,000 for commercial and industrial electronic equipment and 21,000,000 for military applications.

7,000,000 power transistors

Power transistors are expected to account for more than 7,000,000 of the transistors used, the majority turning up in auto radios. Their advantage for this use is, of course, the necessary minimum of 2-3 watts of audio output can be obtained without using a vibrator power supply. Because of the ability of power transistors to control large amounts of current with relatively small voltage drops, they have been used widely in both commercial and military equipment, in power regulating systems, servomechanism devices and a host of control and instrumentation devices.

A 6CD6 beam power tube at 0 grid bias with 150 volts on the screen grid, requires 50 volts on the plate to pass 0.45 ampere. The total consumed power, including heater and screen power, is approximately 50 watts. A typical germanium power transistor can pass 3 amperes with less than 0.5 volt on its collector, using only 1.5 watts. The transistor power converter typifies the efficiency and practical application of power transistors.

A unit now on the market, the Telecom 2D11 transistor power converter, converts 12.6 volts dc to simultaneous power outputs of 500 volts at 200 ma and 250 volts at 100 ma with an overall efficiency of 80%. A schematic of the primary circuit is shown (Fig. 4). The transistors are being used as power oscillators at 1,000 cycles.

High-frequency transistors are expected to account for about 45% of this year's production. Fusion-alloy and grown-junction types were limited to about 5 mc due to low alpha-cutoff frequencies and high collector capacitances. Development work in the last decade has turned up several types of high-frequency transistors, such as drift, surface-barrier and field-effect types. There are transistors that will give useful gain at frequencies in excess of 50 mc. As examples, the 2N384 has a minimum power gain of 15 db,


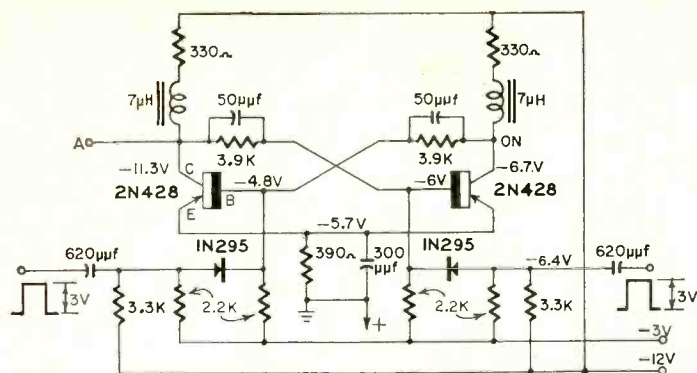


Fig. 5—Typical circuit of a nonsaturated, double-input flip-flop. A switching rate of 1 mc is possible. The diodes prevent triggering by negative impulses.

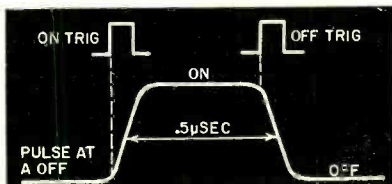

The Author

George R. Spencer was born March 18, 1927. He received a Bachelor of Science degree cum laude in electrical engineering in 1949 from Norwich University, Vt., where he had been a member of the Academic Honor Society. In 1954, he obtained a master's from Northeastern. He has done graduate work at MIT as well.

From 1949 to 1951, he was a teaching assistant at MIT. He then joined Tracer Labs in Boston for a period of about a year. Later, he became a member of the Engineering Division of Raytheon, where he is now employed in the Semiconductor Division. His previous work was as application engineer on receiving tubes for crystal diodes. His present specialty is that of transistor application engineering.

Mr. Spencer belongs to the Theta Chi fraternity.

at 50 mc; the 2N503 a minimum of 11 db, at 100 mc, and the 2N502 is controlled to have a minimum power gain of 8 db at 200 mc.

High-frequency transistors have been used to a great extent in computers and data-processing equipment where their role has been, not as a small signal amplifier, but as a switch (see Fig. 5). This equipment depends on the control of direct currents in a minimum of time. With transistors such as the 2N501 it is now possible to attain switching rates up to hundreds of megacycles.

The entertainment field has used many transistors in manufactured portable radios, not to mention the large number of radio kits that are being marketed. All-transistor car radios and broadcast receivers are now marketed and an all-transistor battery-operated TV set was shown to the public recently.

The military field has used transistors in missile guidance systems, communications, radar, power supplies and regulators as well as computer applications. The industrial and commercial field has applied transistors to all of the aforementioned applications, including also telephone systems, alarm systems and data-processing equipment.

Receiving-tube usage has been affected already to a significant extent. Transistor hearing aids and portable receivers have caused a marked reduction in subminiature and miniature tube production of types formerly used in these applications. Although considerable progress has been made in improving transistors' power-handling and temperature capabilities, voltage ratings and frequency response, it is in these abilities that the vacuum tube still has an advantage.

The transistor is essentially a high-current low-voltage device ideal for low-impedance circuitry, whereas the tube is a low-current high-voltage device suited for high-impedance applications. As a result, in those applications requiring high frequency response with either high-voltage or high-

power ratings, the tube still maintains a definite advantage. Power transistors generally have a cutoff frequency of less than 50 kc and are rated at less than 100 volts for collector-base voltage, while high-frequency types of transistors are normally rated below 30 volts.

What will the future bring?


Fig. 3 depicts probable sales for 1957, 1958 and 1959 in the three main product categories. It is expected that commercial industrial use and military use will increase at a faster rate than the home entertainment market, with the entertainment usage still multiplying rapidly. Expected new uses will be television receivers, hi-fi amplifiers, all-wave receivers, all-transistor car radios, phonograph amplifiers, tape recorders, FM tuners and controls for home appliances. The automobile is likely to use the transistor in fuel injection systems, where transistors coupled with solenoids control the amount and timing of the fuel injected into each cylinder.

Pleasure boating and aviation are potential transistor markets that are beginning to be exploited. Gasoline vapor detectors, altimeters, depth-finding equipment, receiver and direction-finding equipment (see photos) are just a few examples.

Transistor types now under development will open even greater roads to new and untried applications. Raytheon's recently announced spacistor (see "Two New Approaches to Amplification," RADIO-ELECTRONICS, November, 1957) is just one example. This device, similar in appearance to a tetrode (four-terminal) transistor shows promise of increasing the useful frequency range of transistors to 1,000 mc and higher. Furthermore, this device has a very high input and output impedance, allowing it to compete directly with vacuum tubes.

The conclusions of this article are evident; the trend to transistors is increasing at an exponential rate. Their small size, long life, and excellent reliability are the keystones of their success.

END

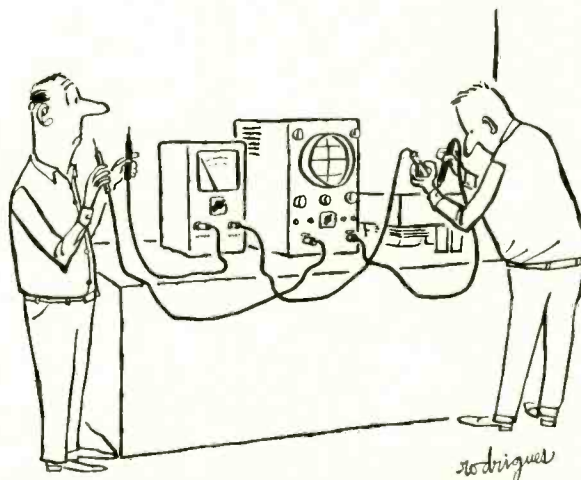

Part I—Not all semiconductors are transistors—some can be used as voltage-variable capacitors, electronic switches or to measure magnetic fields

more jobs for semiconductors

By PAUL PENFIELD, JR.

SAY "semiconductor" to most people and what do you get back? If the person knows anything about electronics you'll hear him say, "transistors." All of us know that transistors are made out of semiconductors, usually germanium or silicon. How many of us know about the many other practical applications for semiconductors?

The many peculiarities of semiconductors can be used in making all kinds of devices. To describe all the characteristics completely a knowledge of advanced physics and quantum mechanics is necessary, but this is not needed here since the practical man is more interested in the actual device than the advanced theory. In this article we have space to discuss only practical devices that work—no purely hypothetical ideas. It is assumed that the reader has some knowledge of the theory of diode and transistor action.

Semiconductor diodes have a history as old as radio itself. Remember galena crystals and catwhiskers? Galena is a semiconductor that comes with many built-in p-n junctions—by moving the catwhisker around you can locate one to use for rectifying the signal. Dry-disk rectifiers, copper-oxide instrument rectifiers and selenium rectifiers are other examples of early semiconductor diodes.

As often happens, the practical diode was used long before its theory was well understood. But with the added knowledge of the theory of conduction in semiconductors came new methods of making diodes, and many new types. Now point-contact and junction diodes are available in a wide range of current and voltage levels. Some are made

specifically for rf detection, some for high-power rectification, etc.

But there are several ways to use diodes other than as rectifiers. Many special-purpose types are available.

The Varicap

One such special-purpose diode is the Varicap. In a circuit this diode behaves like a variable capacitor in parallel with a high resistance (or in series with a low resistance). The value of the capacitor is changed by varying the voltage across the device.

Its operation is easy to understand. In a junction diode in reverse bias the electrons and holes are pulled away from the junction. That, after all, is why so little current flows. Because the electrons and holes are pulled away, a depletion layer¹ is built up at the junction

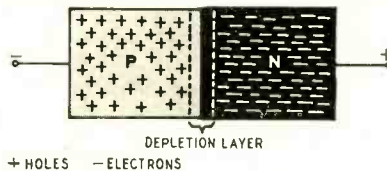


Fig. 1—With a reverse bias a region with no electrons or holes surrounds the junction.

—a layer with no current carriers in it (see Fig. 1). This acts just like a capacitor whose value depends on the thickness of this depletion (dielectric) layer, which in turn depends on the voltage applied. All junction diodes act this way, but the Varicap is designed to take advantage of this changing capacitance and gives a range of about 3 to 1 in capacitance. Therefore some obvious applications for this device, such as frequency modulation or automatic frequency control. The device as presently made is useful into the uhf range.

Another interesting special-purpose diode makes use of this same depletion layer. This is the "punch-through" diode developed at MIT in recent years.

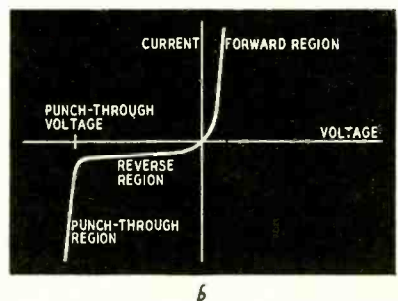


Fig. 2—The punch-through diode (a) and its volt-ampere curve (b).

In this device one of the contacts (see Fig. 2) is placed very close to the junction. At low voltages it behaves like a normal junction diode. But as soon as the depletion layer gets big enough to hit the contact (as soon as reverse voltage gets large enough) a large current can pass. The volt-ampere curve for this device is shown in Fig. 2. There are many computer applications calling

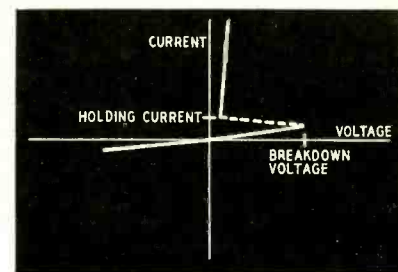
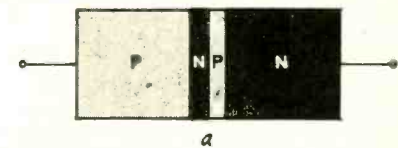


Fig. 3—The Shockley 4-layer diode: a—diode construction; b—volt-ampere curve of the bi-stable unit.

¹P. Penfield Jr., "Transistor Action," *Audio*, October, 1956, page 15.

P. Penfield Jr., "Confused About Transistor Types?," *RADIO-ELECTRONICS*, October, 1956, page 104; November 1956, page 78.

P. Penfield Jr., "More About Transistor Types," *RADIO-ELECTRONICS*, November, 1957, page 35; December, 1957, page 108.

P. Penfield Jr., "Transistors In Audio Circuits," Part I, *Audiocraft*, October, 1956, page 18.

Rufus P. Turner, *Transistors—Theory and Practice*, Gernsback Library Inc.

²Pacific Semiconductors, Inc., 10451 W. Jefferson Blvd., Culver City, Calif.

³Also called a space-charge layer.

for just such a curve. Another use is as a voltage regulator.

Essentially the same volt-ampere curve describes another type of diode—the Zener diode. The result is nearly the same but the method of getting that result is different. Instead of putting a contact close to the junction, the doping of the two sides of the diode is fixed so that the entire voltage drop is across a very small depletion layer. That way, moderate reverse voltages can be used to break down the crystal, allowing high currents to pass. The Zener diode and the punch-through diode can be used in much the same way.

The last specialized diode we'll consider here is the Shockley four-layer

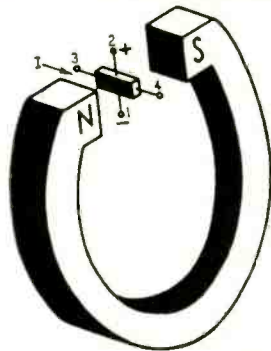


Fig. 4—Diagram of the basic Hall-effect device.

diode (Fig. 3-a). This is just like a hook transistor except that there is no base lead. As the volt-ampere curve in Fig. 3-b shows, at low currents the device is a high resistance. But as soon as the voltage reaches the breakdown point, the device becomes a low resistance. It can be turned on and off (low resistance—high resistance) at will by varying the applied voltage and current, and making it a good switching component. Multivibrators, sine-wave and sawtooth generators, ring counters, and switching circuits for computers can be made using the device.

The operation of the Shockley four-layer diode reminds one of the old "coherer." It acts in a similar fashion. As the current is brought up, the device flips from a high-resistance condition to a low-resistance state. The difference is that the coherer remains in the low-resistance state even after the current is brought down. The only way to get it back into the high-resistance state is to tap it gently with something like the end of a screwdriver. The coherer, recently marketed under the name, "semiconductor relay," is especially useful for one-shot applications, such as proximity fuses or detonation caps.

Hall-effect devices

An electron (and also a hole) is acted on not only by an electric field, caused by applying a voltage, but also by a magnetic field. The magnetic field makes the particle swerve—the force of the field is at right angles to the direction in which the particle is moving.

The Hall effect is the influence of a

magnetic field on electrons and holes in solids. A device employing the Hall effect is shown in Fig. 4. The magnetic field is produced by the permanent magnet with N and S poles as indicated. An electromagnet could also be used. If current I is made to flow through the semiconductor (terminals 3 and 4) placed in the field, both holes and the electrons will tend to be deflected upward. The vertical voltage across the semiconductor (terminals 1 and 2) depends on whether more holes or more electrons get deflected. In a p-type sample there are more holes than electrons and so the voltage has the polarity shown. For n-type material the polarity at terminals 1 and 2 would be reversed.

The action is very similar to magnetic deflection of the beam in a cathode-ray tube.

What good is such a device? Well, there are at least three ways to operate it. First, it can be run without a magnet. Then there will be no voltage at terminals 1 and 2. But if you have a magnetic field you would like to measure, simply stick the device in it and measure the output voltage. This is one of the simplest ways to measure the strength of a magnetic field and can be calibrated to give a direct-reading gauss-meter.


Second, we can use an electromagnet instead of the permanent magnet. Supplying a signal to the electromagnet, the strength of the magnetic field depends on the signal. The output at terminals 1 and 2 will then depend on the input to the electromagnet. What we have here is an amplifier, although for most purposes not a very good one. This same circuit can also be used as a computer multiplying circuit, since the output is proportional to both the electromagnet current and the current I .

Lastly, the device can be operated as a gyrator. A gyrator is a four-terminal device that is not reciprocal—the transfer impedances or transconductances are not the same in opposite directions. Draw any four-terminal network using resistors, capacitors, inductors and transformers, and you will find it is reciprocal. The Hall-effect gyrator is not.

Circuit-theory people have known about gyrators for many years and have devised circuits around them, in spite of the fact that no practical gyrator existed. Now these circuits can be used with the Hall-effect gyrator. They are useful mainly for computers.

Hall-effect elements for all three purposes are being made and sold by the Siemens Co. in West Germany. Theoretically a metal could also be used for such a device, but the effect is very, very small in metals whereas it is rather large in semiconductors.

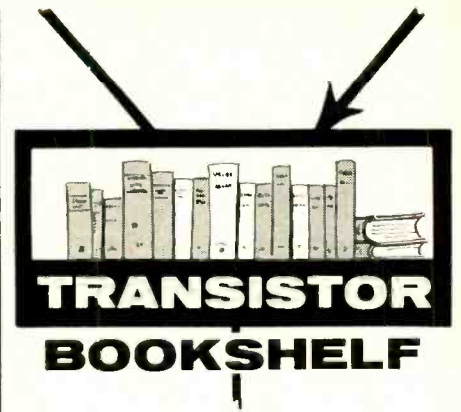Next month we will investigate some more semiconductor devices. Among them will be photoresistors, photodiodes, photocells, thermistors and thermocouples. TO BE CONTINUED



A brief rundown of some of the basic and advanced texts on transistor theory and applications

By RUFUS P. TURNER

SINCE the first public announcement of the transistor 10 years ago, an enormous amount of technical literature concerning this device has become available. In 1949, students and technicians inquired where they might find any book that might help them understand transistors. Today, the question has changed to *which* book is best for a particular reader.

After making a close inspection of many transistor books, I have selected those which appear most serviceable to the practical workers found in large numbers among the readers of RADIO-ELECTRONICS. The books listed in Group I present theory in terms not requiring a knowledge of higher mathematics. They contain numerous transistor applications of the kind so important to the practical circuit man. In most instances, no mathematical knowledge beyond simple algebra is needed.

Listed in Group II are more advanced transistor and semiconductor texts. To understand the material in this second group of books thoroughly, the reader must have a good foundation in higher mathematics (calculus and beyond), engineering and physics, including modern theory of solids.

Group I

BOOK OF THE TRANSISTOR. *J. S. Kendall* (Wehman). Contains simple explanations of transistor theory and action, how to make point-contact transistors, care of transistors, electrical characteristics of American and European transistors. 44 pp.

FUNDAMENTALS OF TRANSISTORS. *Leonard M. Krugman* (Rider). Basic semiconductor and transistor theory, circuit theory for transistor amplifiers and oscillators. Requires some easy familiarity with algebra. 140 pp.

HANDBOOK OF SEMICONDUCTOR ELECTRONICS. *Lloyd P. Hunter*, Editor

(McGraw-Hill). Complete coverage of semiconductor theory. Semiconductor devices and manufacture. Typical applications illustrated with skeleton circuit diagrams. Some sections will be better understood if the reader has a good mathematical foundation. Book is divided into 20 sections. A good reference manual.

HOW TO MAKE A TRANSISTORIZED PORTABLE RADIO, AND 20 OTHER APPLICATIONS FOR RF TRANSISTORS. (Sylvania). Collection of practical circuits for amplifiers, oscillators, broadcast receivers, ham radio, test instruments and miscellaneous devices. 34 pp.

TRANSISTOR APPLICATIONS, VOL. I. (Raytheon). Collection of 53 articles on practical applications of transistors reprinted from various magazines, 25 of them from RADIO-ELECTRONICS. Electrical characteristics of Raytheon transistors. 116 pp.

TRANSISTOR APPLICATIONS, VOL. II. (Raytheon). Simplified transistor theory; practical transistor circuit design principles; installation, care and testing of transistors; miscellaneous practical circuits and devices; reference data; electrical characteristics of Raytheon transistors. 58 pp.

TRANSISTOR CIRCUIT HANDBOOK. *Louis E. Garner, Jr.* (Sams). Simplified survey of transistor theory, numerous practical circuits, reference data and electrical characteristics of commercial transistors. 410 pp.

TRANSISTOR CIRCUITS. *Rufus P. Turner* (Gernsback). Over 150 practical circuits for transistor audio amplifiers, rf and if amplifiers, dc amplifiers, oscillators, power supplies, radio receivers, triggers and switches, control devices, test instruments, amateur and miscellaneous devices. 160 pp.

TRANSISTOR CIRCUITS AND APPLICATIONS. *John M. Carroll* (McGraw-Hill). Numerous reprints of articles previously published in *Electronics* magazine. A good cross-section of all areas of practical applications of transistors. 283 pp.

TRANSISTOR ENGINEERING REFERENCE HANDBOOK. *H. E. Marroux* (Rider). Simplified transistor theory and some practical circuit applications. Much space devoted to characteristics of commercial transistors and to circuits of commercial transistor devices. Divided into five sections. 288 pp.

TRANSISTOR MANUAL. 2nd Edition. (General-Electric). Simplified transistor theory, transistor and rectifier construction, transistor and rectifier circuit applications, physical dimensions of transistors, practical circuits for the experimenter, characteristics of General-Electric transistors and principal electrical characteristics of registered JETEC transistor types from all manufacturers. 113 pp.

TRANSISTOR TECHNIQUES. *Bohr, Braumbeck, Kampf, Knight, Padgett, Prenskey, Queen, Reed, Schenkerman, Steen and Turner* (Gernsback). Practical data on transistor care, testing,

performance, and measurements. Numerous practical circuits. 96 pp.

TRANSISTORS. *Louis E. Garner, Jr.* (Sams). Simplified introduction to transistor theory and transistor circuits, transistor circuit components and electrical characteristics of commercial transistors. 105 pp.

TRANSISTORS HANDBOOK. *William D. Beviitt* (Prentice-Hall). Theory of semiconductor and transistor action. Transistor types. Many practical circuits in all areas of application from simple amplifiers to computers. Knowledge of elementary algebra helpful to understanding of some theory sections. 410 pp.

TRANSISTORS IN RADIO AND TV. *Milton S. Kiver* (McGraw-Hill). Elementary presentation of electronic and semi-conductor theory, transistor action and applications of transistors to radio, television and related circuits. Electrical characteristics of transistors. Servicing of transistor equipment. 220 pp.

TRANSISTORS, THEORY AND PRACTICE. *Rufus P. Turner* (Gernsback). A standard textbook for the beginning transistor student and refresher for the experienced worker. Contains chapters on semiconductor theory; transistor characteristics; equivalent circuits of transistors, amplifiers, oscillators; duality in transistor circuit design; triggers and switches; practical transistor circuits; tests and measurements, and characteristics of commercial transistors. 144 pp.

28 USES FOR JUNCTION TRANSISTORS. (Sylvania). Simplified transistor theory; 28 practical circuits employing transistor types 2N34, 2N35, and 2N68 in amplifiers, oscillators, control devices and test instruments; electrical characteristics of Sylvania transistors. 47 pp.

Group II

ELECTRONS AND HOLES IN SEMICONDUCTORS. *William Shockley* (Van Nostrand).

INTRODUCTION TO JUNCTION TRANSISTOR THEORY. *R. D. Middlebrook* (Wiley).

INTRODUCTION TO TRANSISTOR CIRCUITS. *E. H. Cooke-Yarborough* (Oliver & Byrd).

PRINCIPLES OF TRANSISTOR CIRCUITS. *Richard F. Shea, Editor* (Wiley).

PROGRESS IN SEMICONDUCTORS. Vols. I and II. *Alan F. Gibson, Editor* (Wiley).

SEMICONDUCTORS: THEIR THEORY AND PRACTICE. *G. Goudet, C. Meuleau, and E. M. Deloraine* (MacDonald & Evans).

TRANSISTOR AUDIO AMPLIFIERS. *Richard F. Shea* (Wiley).

TRANSISTOR CIRCUIT ENGINEERING. *Richard F. Shea* (Wiley).

TRANSISTOR ELECTRONICS. *Lo, Endres, Zamels, Waldhauer, and Cheng* (Prentice-Hall).

TRANSISTORS I. RCA Laboratories (RCA).

TRANSISTORS AND OTHER CRYSTAL

VALVES. *T. R. Scott* (Macdonald & Evans).

TRANSISTORS: THEORY AND APPLICATIONS. *Abraham Coblenz and Harry L. Owens* (McGraw-Hill).

Publishers

Publishers or distributors listed in the foregoing text are identified below: *General Electric*. General Electric Co., Semiconductor Products Dept., Electronics Park, Syracuse 1, N. Y.

Gernsback. Gernsback Library, Inc. 154 W. 14th St., New York 11, N. Y. *Macdonald & Evans*. Macdonald & Evans, Ltd., London, England. (American distributor: Essential Books, Inc., Fair Lawn, N.J.)

McGraw-Hill. McGraw-Hill Book Co., 327 W. 41st St., New York 36, N. Y. *Oliver & Byrd*. Oliver & Byrd, Ltd., London, England.

Prentice-Hall. Prentice-Hall, Inc., Englewood Cliffs, N. J.

Raytheon. Raytheon Mfg. Co., 55 Chapel St., Newton 58, Mass.

RCA. RCA Laboratories, Inc., Princeton, N. J.

Rider. John F. Rider Publisher, 116 W. 14th St., New York 11, N. Y.

Sams. Howard W. Sams & Co., Inc. 2203 E. 46th St., Indianapolis 5, Ind.

Sylvania. Sylvania Electric Products, 1740 Broadway, New York 19, N. Y.


Van Nostrand. D. Van Nostrand Co., Inc., 250 Fourth Avenue, New York, N. Y.

Wehman. Wehman Brothers, 712 Broadway, New York 3, N. Y.

Wiley. John Wiley & Sons, 440 4th Ave., New York, N. Y.

Acknowledgement

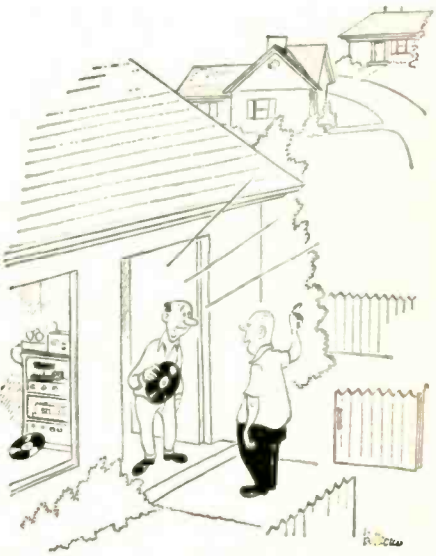The author is indebted to Technical Book Co. of Los Angeles for placing at his disposal each of the books reviewed in this article. END



"Good evening! I live about a half-mile up the road, and my wife and I have been arguing about the composer of the last symphony you played."

THE TRANSISTOR "FIFTH"


By I. QUEEN
EDITORIAL ASSOCIATE

WANTED: a light-duty amplifier with low distortion, plenty of volume. Must be compact.

That was the problem after I bought a new FM tuner. An amplifier was needed for FM listening and monitoring tape recordings being made from the FM programs. It would also be used for various utility purposes.


Tests showed that 100 mw delivered to an efficient speaker produces all the sound that is needed in an ordinary room. Therefore, I decided to build an amplifier with a 200-mw output (1/5 watt, from which unit derives its name). In this age of audio amplifiers that deliver 50 and 60 watts, you may feel that 1/5 watt is just a whisper. How-

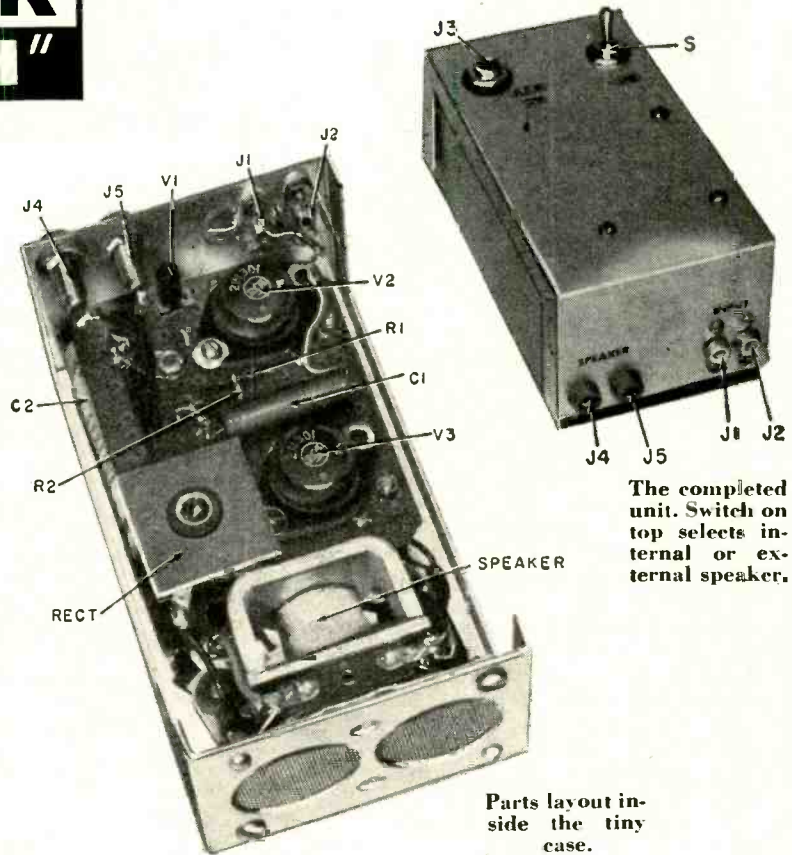Compact one-fifth watt amplifier is powered by 6.3 volts ac



Parts layout inside the tiny case.

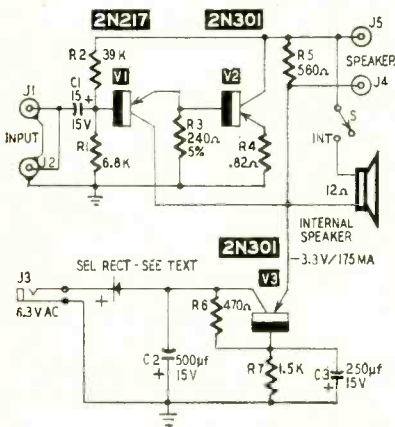The completed unit. Switch on top selects internal or external speaker.



- R1—6,800 ohms
- R2—39,000 ohms
- R3—240 ohms, 5%
- R4—0.82 ohm
- R5—560 ohms
- R6—470 ohms
- R7—1,500 ohms
- All resistors 1/2-watt 10% unless noted
- C1—15 μ f
- C2—500 μ f
- C3—250 μ f
- All capacitors 15-volt electrolytics
- J1, 2—phono jacks
- J3—phone jack
- J4, 5—pin jacks
- S—spst toggle
- V1—2N217
- V2, 3—2N301
- Selenium rectifier, see text
- Speaker, 12-ohm coil, 2 x 3 inches (RCA 21451 or equivalent)
- Socket, transistor, 3-pin, in-line, for V1
- Socket, 9-pin miniature (2) for V2 and V3
- Perforated bakelite board, cut to size
- Case, 5/4 x 3 x 2 inches
- Miscellaneous hardware

Fig. 1—Circuit of the 200-mw amplifier.

ever, this equals the power of many thousands of people talking at once. (Average individual voice power in conversation is in the order of 30 μ w.) Certainly it is far more than most neighbors will stand for!

The amplifier measures only 5 1/4 x 3 x 2 inches. This includes a self-contained small speaker. Of course, connections for a good external speaker are provided. I use a Lansing D208 in a 2 x 1-foot enclosure.

Frequency response is excellent. It is down about 2 db at 12,000 cycles and about 0.8 db at 12 cycles. *Undistorted power* output is 200 mw—about 1.3 volts across 8 ohms. Maximum input is about 0.1 volt. No volume control is included because the amplifier is used with an FM tuner which has a gain control. An interesting feature is the absence of transformers. Besides improving frequency response, this saves money and space. The two stages are direct-coupled, with the speaker fed directly by a power transistor. A 16- or 8-ohm speaker is recommended, but 4-ohm units give good results.

The circuit is in Fig. 1. V1 effectively in a grounded-collector stage is followed by a grounded emitter V2. The output transistor is an RCA 2N301. It delivers the 1/5 watt with about 3.3 volts on its collector. V1 is a 2N217,

chosen after various tests with other driver transistors. It gave maximum power with minimum distortion, at this low voltage.

The power supply

This amplifier operates from an unusual but easy-to-find power source, 6.3 volts ac. This voltage (at less than 0.3 amps) is found in many electronic instruments. It must be rectified and filtered before being applied to the amplifier. Since the voltage is so low, there is no need for an entire (117-volt) rectifier stack. I removed two elements from a 150-ma stack and connected them in parallel. See Fig. 2. This permits up to 300-ma drain (at 6.3 volts). The amplifier consumes less than 175 ma.

The rectifier elements are mounted on a long screw which holds the unit to a bakelite board and serves as the negative terminal. A cardboard sleeve insulates the screw from the elements and washers. One side of each element has a smooth metallic surface. The other side is rough-looking because it is coated with selenium. These are identified as M and S, respectively, in Fig. 2. Washers are used to make good contact with the surfaces.

After rectification, ripple is smoothed by V3, another 2N301. This is done by

AUDIO—HIGH FIDELITY

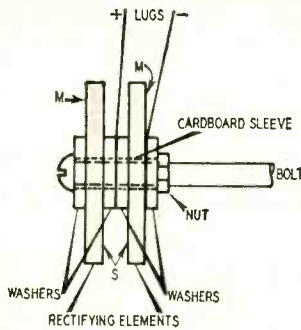


Fig. 2—Assembling the rectifier: Left washer contacts head of screw. Nut also contacts screw. Therefore, negative lug and screw contacts both M surfaces. Cardboard sleeve over screw insulates positive lug and S-surfaces.

supplying the rectified voltage to the transistor base. The output from this transistor is nearly pure dc. (For a detailed description of this action see "Transistor Low-Voltage Supply," *RADIO-ELECTRONICS*, October, 1957.) At full gain, the hum is hardly audible even if you place your ear right up against the speaker cone. Neither V2 nor V3 is provided with a heat sink since both are worked far below their maximum ratings.

The amplifier circuit is built on a perforated sheet of bakelite held in place by long screws and spacers. I used a 2 x 3-inch RCA model 214S1 speaker in one end of the aluminum box. A switch cuts this speaker in or out as desired. Resistor R5 closes the power amplifier load circuit should the internal speaker and the external unit be both disconnected at the same time.

Two input terminals (phono jacks) are connected in parallel. One may be used for the incoming signal, the other for connection to a tape recorder. In many recorders the speaker is automatically disconnected during recording (to prevent acoustical feedback into a mike). With this pair of input terminals, the FM tuner feeds the recorder while you monitor it with the amplifier. When you connect the Fifth to an FM tuner, the signal lead shield provides the common ground between tuner and amplifier. The only other lead you need

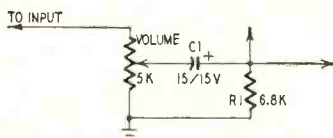


Fig. 3—Use this circuit to add a volume control to the amplifier.

is to the 6.3-volt supply, assuming the other filament lead is grounded.

To operate the Fifth from batteries instead of ac, eliminate V3 and its circuitry. Apply 3 or 4 volts to the V1, V2 circuit. A pair of flashlight D cells will last a long time and give plenty of volume when this amplifier is fed from a portable transistor tuner. A single cell supplying less than 25 ma provides ample volume for low-level listening.

If your application calls for a volume control, connect it as shown in the circuit of Fig. 3. **END**



A TAPE recorder scarcely adequate for a baby's unsteady mid-range gurgle cannot do justice to today's stereo tapes. These require steady transport past a well-aligned head of proper frequency response. Test tapes of acknowledged accuracy have been used for years to uncover any increase in equipment wow and flutter, improper head alignment and impaired frequency response. Such tapes are useful only where adjustments can be made to improve the performance of a tape machine. In the past the only test tapes commonly used by radio stations, recording companies and top-flight repair men were the two Ampex test tapes. These are individually made custom jobs—the 15-ips tape going out to 15,000 cycles, the 7½ out to 10,000 cycles. The sole difficulty for the rest of us—the price of the 7½-ips tape (5563) goes out to \$14.50. Ampex test tape 5563 contains the following: 10,000 cycles of long duration for alignment of the tape head; 250 cycles at 0 VU reading; 250 cycles at -10 db which is its standard test level, then test frequencies from 10,000 down to 50 cycles. Before recording these test frequencies on each tape, Ampex selects the center-line cuts of blank tape and then polishes it thirty times by running it against itself. This assures optimum contact with your playback head and accounts for the price of the finished tape. That was the situation in test frequency tapes until a few weeks ago when Livingston Audio Products, a pioneer in recorded tapes, announced a custom-engineered test tape at \$9.95, the LX-1E. I immediately made an appointment with John White, their chief engineer, to see how they do it. Instead of polishing the tape beforehand, they depend upon automation for uniform results while recording. In a specially designed laboratory set apart from their Caldwell, N. J., plant, I watched the operator produce each tape individually. As each test frequency from 50 to 12,000 cycles is announced, relays (audible on the finished tape) activate a compressor amplifier designed to maintain constant levels by taking into consideration any variation in the tape itself. This system does away with the need for bias readjustment ordinarily required. (Where needed they have substituted precision military components to insure stability. "Red base" tubes are in virtually every socket.) Heads and tape drive are cleaned every 10 tapes. The LX-1E test tape also contains a 3,000-cycle tone for testing wow and flutter, 5,000- and 10,000-cycles for head alignment, a 250-cycle tone at zero level followed by a section of unrecorded tape for judging signal-to-noise ratio. The handiest feature of all is the vertically striped leader tape which acts as a stroboscope for checking the speed of the transport mechanism. Service technicians will welcome this strobe when getting acquainted with an unfamiliar machine. The Livingston LX-1E fills a need in its price range. For some time now Audio Devices, Inc., has offered an excellent custom-made test tape at \$10. That tape, however, is designed solely for head alignment. Recorded at 15 ips, its test tones of 2, 10 and 15 kc jump to 1,000, 5,000 and 7,500 cycles at 7½ inches per second. Next month we'll take up test tapes made on duplicators.

Dance Hits of the 30's and 40's
New World Theatre Orchestra
Bel Canto Stereo Tape ST-30
(7-inch; playing time, 22 min. \$9.95)

Taking full advantage of the relatively uniform dynamic range in dance music compared

to that found in symphonic writing, Bel Canto offers a reel recorded at about twice the level found on classical orchestral tape recordings. Yet they manage this without introducing distortion. At this sound level, tape hiss ceases to exist as a factor in reproduction on first-grade equipment. High-level recording in commercial tapes has been tried in the past with small instrumental groups but I've never heard a taping of a dance band of this size with distortion held to this minimum. The music consists of tasteful arrangements of five old favorites including *Paper Doll*, *Dream*, *Stars Fell on Alabama*, etc. Go out of your way to hear this recording. This is tape with all the problems solved.

WILLSON: The Music Man
Original Broadway Cast Album
Capitol Stereo Tape ZF-41
(7-inch; playing time, 46 min. \$14.95)

Capitol has captured in depth the small-town flavor of Meredith Willson's musical comedy. Robert Preston as the brassy band-instrument salesman can really demonstrate his wares in stereo. Throughout the show, only stereo can distinguish with ease the close layers of harmony built up by an old-fashioned male quartet as well as the tiniest inflections of the chorus. Very live recording helps. Smart New York audio-dealers are using this tape to demonstrate wide-range stereo's benefits on expensive sound equipment.

Holiday for Trumpets
Warren Kime and his Five Trumpets
Replica Stereo Tape T-110
(7-inch; playing time, 24 min. \$8.95)

From the Iowa of *Music Man* to present-day Illinois where this Replica tape was made. Here is light, popular music featuring clever arrangements for five trumpets. Very easy to take. Sweet, untroubled highs and crisp bass set apart this well-recorded tape. Many of the individual trumpet touches would have been lost in single-channel recording.

PROKOFIEV: Lieutenant Kije
Fritz Reiner conducting Chicago Symphony Orchestra
RCA VICTOR Stereo Tape BCS-96
(7-inch; playing time, 20 min. \$8.95)

Other than the concert hall, RCA's brilliant new tape provides the ideal medium in which to hear Prokofiev's larger-than-life score. The music makes exaggerated use of bass drum, fife, brasses and cymbals in depicting the life span of the imaginary Lieutenant Kije. No record has ever conveyed the full scope of this satire of military life under the czars. The man at the controls, Lewis Layton, has drawn upon the experience gained by RCA in more than a dozen stereo recordings of the Chicago orchestra. His handling of the live acoustics matches the broad sweep of Fritz Reiner's performance.

Fiesta Flamenca
Carlos Montoya and Spanish dancers and singers
Cook Stereo Tape 1027
(7-inch; playing time, 24 min. \$12.95)

The heel-stomping of the Spanish dancers in this troupe offers ideal material for testing the

bass transient response now possible in this medium. An old favorite in the Cook catalog, *Fiesta Flamenca* is set in motion again on this stereo tape.

Deutschmeister on Parade
Julius Herrmann conducting Deutschmeister Band
Westminster Sonotape SWB 7004
(7-inch; playing time, 17 min. \$6.95)

This stereo tape is unique in one respect. In the first selection *Castaldo March*, this perky little brass band is heard far in the distance on the left microphone alone. No sound whatever issues from the right channel for the next 35 seconds. Then as the band nears the normal stereo field, the right-channel mike is slowly opened and the band parades across the room in stereo. Finally the left-channel microphone is slowly closed and we have 35 seconds of music on the right channel alone. Following this maximum illusion of directionality, the band offers a group of sprightly continental marches in typically clean Westminster sound.

Ruffles and Flourishes
Music for Field Trumpets and Drums
Frederick Fennell conducting members of Eastman Symphonic Wind Ensemble

Mercury Stereo Tape MS5-13
(7-inch; playing time, 21 min. \$8.95)

A truly rousing entry by Mercury in the heightening competition to exploit stereo's advantages. The military trumpets are carried on one channel, the drums on the other. Without a symphony orchestra in the way, the bass drum and cymbals have a surprise in store for any speaker system. A note of caution: after listening to this tape on top-notch equipment, the steep attenuation of lowest bass frequencies on discs will become most apparent.

Vic Dickenson Septet
AV-Vanguard AV-752J
It Might as Well Be Spring
Sol Yaged and Quintet
AV-Herald AV-755J

These two monaural tapes of modern jazz can demonstrate on a first-class system that single-channel hi fi is also capable of a very high degree of presence. Both have a big bass and a good sharp high highs, though not as prominent as those in *Dancing and Dreaming*.

Note: Records below are 12-inch LP and play back with RIAA curve unless otherwise indicated.

HAYDN:
Symphony No. 100 in G (Military)
Symphony No. 101 in D (The Clock)
Antal Dorati conducting London Symphony Orchestra
Mercury MG 50155

Every audiophile will want to know how the "Battle" movement of the Haydn *Military* symphony is waged in Dorati's version. The answer: musically. Many listeners today will welcome the fact that Mercury's single-mike technique doesn't permit undue emphasis on cymbals and drums found in other versions. Clean sound and brisk, well-detailed playing.

The Sounds of Holland
Capitol T-10133

A tour of Holland in sound. A year of painstaking work with very fine Dutch-made portable tape recorders went into this album. With narration by the noted actor, Hans Conried, the tour includes an airport, railroad station, the harbor, canals and traffic sounds including hundreds of bicycle bells. The best "documentary" touch is the clomp of wooden shoes on a cobbled sidewalk.

Italian Interlude
Murray Dickie, Tenor, with Gianni Monese and His Orchestra
Vox VX 25.190

A collection of Neopolitan favorites sung in pleasant native style by a tenor from Scotland.

Signor Monese and his orchestra provide authentic accompaniment. Up-to-date sound such as this may revive interest in this type of song so popular in the early days of radio.

RAVEL: Bolero
LISZT: Mephisto Waltz
Hermann Scherchen conducting Vienna State Opera Orchestra
Westminster Lab Series W-Lab 7059

Westminster's policy of holding down the maximum peak level in this deluxe series to 14 cm/sec pays off handsomely in the Ravel *Bolero*. The music builds naturally from a low-level beginning yet the climax does not contain the distortion present in virtually every other recorded version. The point of superiority is fast becoming academic, however, because many Lab Series buyers are now going over to \$6.95 stereo tapes.

STRAVINSKI: Petrushka
Firebird
Leopold Stokowski conducting Berlin Philharmonic Orchestra
Capitol PAO 8407

Uncommonly spacious sound typical of that favored by German recording engineers. The effect of a huge concert hall does not disguise the fact that Stokowski cannot persuade the Berlin players to unbend at any point in their rigidly correct performance of *Petrushka*. The *Firebird*, with less flexibility required of the orchestra, is more successful. A highly professional job of recording marred only by excessive poise in the performance.

TCHAIKOVSKY: Swan Lake
Joseph Levine conducting Ballet Theatre Orchestra

Capitol PAO 8416

TCHAIKOVSKY: Excerpts from Sleeping Beauty
Pierre Monteux conducting London Symphony Orchestra
RCA Victor LM-2177

Both ballets receive excellent treatment on these discs. The sweet sound of Tchaikovsky's strings is heard to better advantage in the Capitol performance because a flatter recording curve is employed but Monteux has the last word on the music he conducts. Very enjoyable.

HAYDN: Concerto (for harpsichord) in D
BACH: Concerto (for harpsichord) in D Minor
Sylvia Marlowe and Concert Arts Chamber Orchestra
Capitol P-8375

It still seems to me that in this series of Marlowe records Capitol is doing the best job of presenting the harpsichord in all but living presence. Those who own systems capable of presenting the high end with a minimum of coloration will be especially delighted by the purity with which the harpsichord tone in the upper register is presented, and, conversely, that same purity can do a beautiful job of showing off such a system. The small chamber orchestra contributes a rich and gutty bass and a fine contrasting solidity to the fragile harpsichord. The two works also present a contrast in style and variety and give the harpsichord plenty of opportunity to show off its own variety.

Manmoth Fair Organ
Carrousel Becquart
London LL 1644

If the range of your sense of humor matches that of your sound equipment you'll enjoy this record. Here is the most sophisticated 50-year-old mechanical organ on discs today. A feature of the Carrousel Becquart in Belgium, it romps through several items well known in this country, but most of its perforated rolls contain music familiar only to generations of visitors to Belgian fairs. Capitol Record's barrel organ production *Afternoon in Amsterdam* created a following for music of this sort by reason of the lavish care taken in recording it. Now London frr offers a mechanical organ of more lasting appeal. Your tweeters will ap-

preciate the subtle clarity of the organ bells and your friends will find humor in the optimistic approach to the intricate orchestral arrangements. A. Schollaert, the man who devised the rolls, obviously found fun in science.

Resort Favorites for Dancing
Harry Marshard and His Orchestra
Unicorn 1049

An easy way to crash a swank affair offering music by Harry Marshard, the Boston-based society dance favorite of the past 25 years. What really will catch your ear in this record is the uncanny mike work of Peter Bartok — perhaps the shrewdest of the top handful of recording engineers who have achieved fame in the LP era, a fame limited to owners of really top-notch sound systems, yet a fame nonetheless. Bartok's symphonic recordings have been models of orchestral balance and realism. Working on stage at Town Hall in New York with a well-drilled society dance band, he uses both to maximum advantage. Without an echo chamber or other studio gimmicks, he gets the full sound of each instrument while retaining the overall balance. Through placement of the instruments, he achieves the definition that others think they get by boosting the upper end of the record curve. The orchestra doesn't relax for a second because the medleys on the record include the brightest favorites of the dancing set at six East Coast resort areas.

OFFENBACH: Gaité Parisienne
Felix Slatkin conducting Hollywood Bowl Symphony
Capitol PAO-8405

Can they go much beyond this point in recording *Gaité Parisienne* on monaural discs? Not without recourse to hokum—devices such as artificial volume expansion or peaks in the frequency range at the point where cheap speakers fall off in response. We already have several "Gaités" with souped-up sound on other labels. Capitol now has the top version with a pleasing performance and wide range yet natural sound. For excitement beyond this, I refer you to stereo.

Gypsy Strings
Yoska Nemeth and his Gypsy Orchestra
Vox VX-25220

A fine change of pace both musically and sonically. This group gives fiddle, clarinets, cello and cimbalon opportunity to show off individually, and in combination to produce an opulence as colorful as gypsy costumes. The recording is fittingly spacious and very live and, despite the high average level, very clean. One of the best gypsy records in the catalogs. Most of the traditional gypsy airs and dances are included in the repertoire of some 26 or 27 selections.

SCHUBERT: Symphony No. 2
Symphony No. 6
Couraud conducting Bamberg Symphony
Vox P-10240

A sympathetic performance and excellent recording of two of the six symphonies Schubert composed between the ages of 16 and 21. No great challenge here to hi-fi capabilities but just another excellent subject for using hi fi for what it does best—reproducing music worth listening to and delightful to hear.


Vienna Midnight
Liane and Boheme Bar Trio
Vanguard VRS 9026

Paris Midnight
Liane and Boheme Bar Trio
Vanguard VRS 9018

Audiophiles discovered years ago that the velvety voice of Liane and the close-up piano, bass and alternating guitar and accordion of the Boheme Bar Trio gave them "presence" on any speaker. The early 10-inch Vanguard recordings of these cafe favorites employed the NAB recording curve. General advances in the recording art and use of the RIAA curve put these 12-inch discs near the top of the list. END

Name and address of any manufacturer of records mentioned in this column may be obtained by writing Records, RADIO-ELECTRONICS, 154 West 14 St., New York 11, N.Y.

Audio Filter has VARIABLE Bandpass

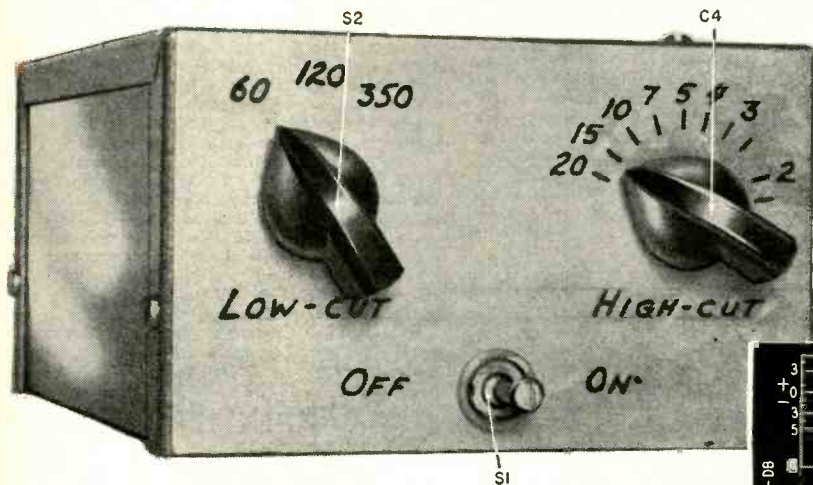

This valuable audio accessory uses three bass rolloffs and a wide-range variable treble rolloff to improve hi-fi reproduction or amateur reception and transmission

By Dr. CARL F. ROTHE

AN inexpensive audio filter with variable high- and low-frequency cutoff lets the experimenter or audiophile demonstrate the effect of high- or low-frequency losses. It also provides a way to reduce noise or rumble and a simple method of evaluating program material. By cutting back on the frequency response from either end until a reduction in response is heard, you can estimate the quality of the program or audio system. Using the treble control to reduce static or noise generally cuts the useful program material much more rapidly than does this sharp-cutoff filter.


The low-frequency cutoff selectively cuts excessive bass if the speaker is not properly loaded. It also helps to reduce switching transients and hum when experimenting with an audio system, thereby protecting the speaker.

The bandpass filter described here gives a choice of three low-frequency cutoffs (60, 120 and 350 cycles) at 12 db per octave, and a continuously variable high-frequency cut at 18 db per octave, between 1.8 and 28 kc. The filter is designed to be placed between the preamp and power amplifier of an audio system. It can also be used with the speech amplifier of ham gear to limit bandpass, or with experimental equipment.

L-C filters provide sharp cutoff, but are not easily variable and are expensive, especially if magnetically shielded inductors are used to reduce pickup of the ever-present hum. R-C networks give ultimate attenuation of 6 db per octave per section and, when three are put in series, a very comfortable 18 db per octave is obtained. However, as with the bridged-T network, the knee is far from sharp and the cutoff is slow at first.

Using R-C networks with an amplifier with 20-db gain, and applying negative feedback, the knee is sharpened and

Fig. 1 — Response curves of the variable-bandpass filter.

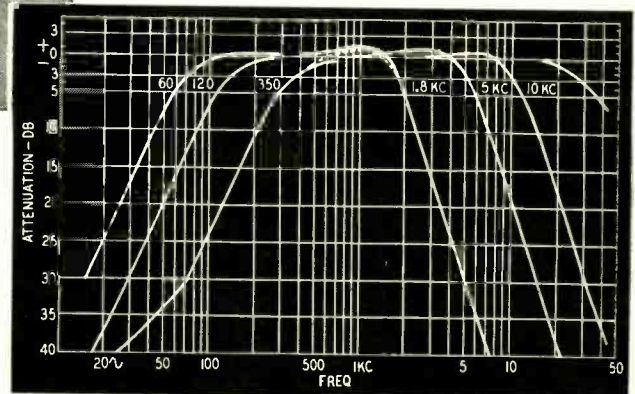

unity gain realized at the middle frequencies. The final responses are shown in Fig. 1.

The high-cut filter is similar to that described by Lawrence Fleming in *Radio & Television News*, May, 1955. Several improvements are incorporated in the present circuit. The noise output of Fleming's filter varied inversely with the cutoff-frequency setting. When using the filter with a high-gain power amplifier, such as the Heathkit W-5, the noise was objectionable at low-frequency cutoff settings. Bypassing the cathode resistor with a 15- μ f capacitor eliminated the noise (see Fig. 2).

The characteristic 3-db hump, just prior to cutoff as described by Fleming, is reduced by using less feedback around the high-cut filter. The extra gain thus available permitted the use of more feedback around the low-cut filter, resulting in a sharper knee in its response curve.

Low-cut filter

The low-cut filter presents a major design problem since, ideally, the reactive components should be in the shunt-to-ground legs of the network and thereby have little effect at the flat response part of the curve. This cannot be done without using inductors. A three-section R-C network with the capacitors in series was used with feedback. With feedback from the large 0.1- μ f output coupling capacitor C1, attenuation was sharp until the reactance of the network capacitors became so high that the signal bypassed the

filter by taking the lower impedance path offered by the feedback line. This limited attenuation to about 20 db. By using a smaller capacitor (C15) for the feedback loop the low frequencies were effectively kept from entering the output.

Maximum possible frequency response is often desired, so a switch was added to bypass the filter. Resistors R1 and R2 were added to keep the coupling capacitors of the filter, preamp and power amplifier at the same dc potential and thus reduce switching transients.

If greater selection of cutoff frequencies is desired, different values of capacitors in the filters can be used. Doubling the capacitors' size gives a cutoff at about half the previous frequency. If a fourth position were available on the LOW-CUT selector switch, three .01- μ f capacitors could be added to give flat bass response to about 40 cycles. This would effectively reduce turntable rumble with a minimum loss of bass. Using feedback extends the cutoff frequency (where the response is down 3 db) from that obtained without feedback. Theoretically, the cutoff frequency equals $\frac{1}{2}\pi RC$ (R in megohms, C in μ f, $2\pi = 6.28$). Under the conditions used here, it is approximately $1/9RC$ for the low and $2/9RC$ for the high end. For exact values, experimenting will have to be done.

Because of the large amount of feedback, the input impedance is about 300,000 ohms and so the impedance of the source should be relatively low.

The filter is highly stable since there is no overall gain.

Construction details

The filter was built into a 7 x 5 x 3-inch case. The three-gang capacitor was put in one corner, and the 12AU7 on a bracket behind it. This left half of the box for the low-cut filter capacitors and other components.


The layout is not particularly important, since the signal level is relatively high and the gain unity. However, if greater than 30-db cuts are desired at high frequencies, it is well to keep the input circuitry of the high-cut filter and the capacitors and wiring of the low-pass unit at least 1/2 inch apart. The heater leads, of course, should be twisted together, kept short and close to the chassis. Center-tap grounding of the heater transformer helps minimize hum. The heater circuit shown in Fig. 2-b can be used with power supplies with one side of the heater supply grounded to the B-minus supply or with a floating heater winding.

Resistor R3 was picked to give a stage gain for the high-pass filter of about 1.5 at 1,000 cycles. Feedback resistor R10 for the low-pass filter was then chosen to give an overall gain of 1 for the whole filter at 1,000 cycles. I used a 1-megohm pot for this resistor (see photos). A 560,000-ohm fixed resistor (see schematic) can be used.


I calibrated the filter with a Hewlett-Packard audio generator and a Heathkit vtvm. Variations in output of the generator and response of the vtvm were eliminated by comparing the indicated voltages at the various frequencies with the filter selector OFF to those with the filter ON. If equipment is not available for calibration, the standard broadcast-band trf capacitor used gives the following cutoff points: fully closed, 1.8 kc; one-quarter open, 3 kc; one-half, 5 kc; three-quarters, 10 kc; seven-eighths, 16 kc, and fully open, 28 kc.

The calibration points were marked on a separate aluminum panel, but could have been made directly on the gray hammertone panel.

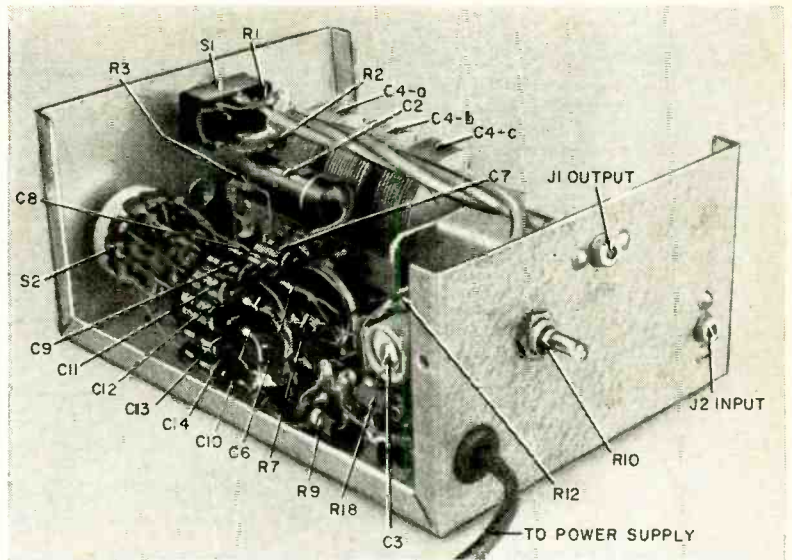The filter has greatly improved the reception of weak AM stations when static or heterodyning is present. Boomy male voices are made more intelligible, and turntable rumble, when present, is reduced. The effects of loss of bass are clearly demonstrated. END



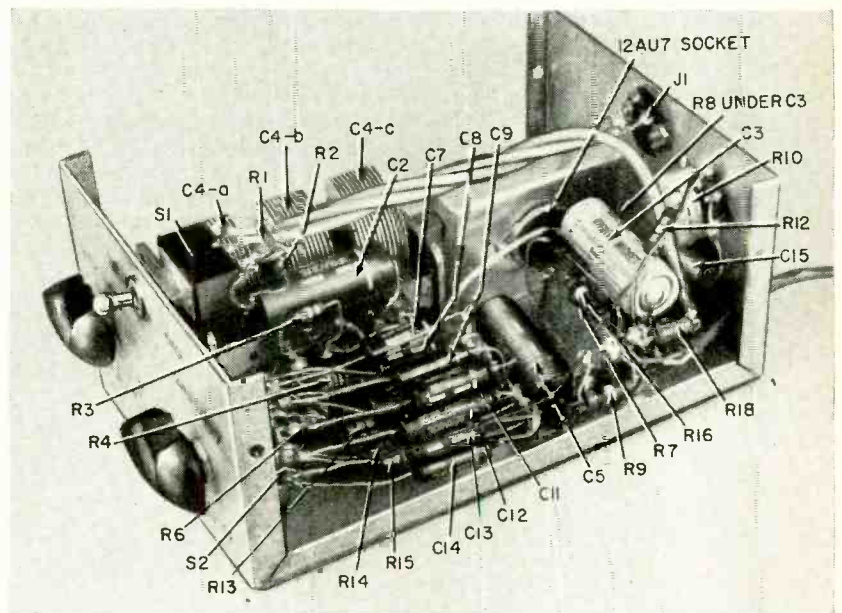Above, an inside view showing the Low-Cut switch assembly. And, below, another look at the filter's insides.



- R1, 2—4.7 megohms
- R3—820,000 ohms
- R4, 11—470,000 ohms
- R5—1 megohm
- R6, 7, 12, 13, 14, 15—270,000 ohms
- R8, 17—2,200 ohms, 1 watt
- R9, 16—100,000 ohms, 1 watt
- R10—560,000 ohms
- R18, 19—47 ohms, 1 watt
- All resistors 1/2-watt 10% unless noted
- C1—0.1 μ f, tubular
- C2, 5—.06 μ f, tubular
- C3—15 μ f, 25 volts, electrolytic
- C4—10-365 μ f per section, 3-gang trf type variable capacitor (Allied 60 H 726 or equivalent) with extender 60 H 366 for adapting 3/8-inch shaft to 1/4 inch
- C6, 9, 12—.0068 μ f, tubular
- C7, 10, 13—.0033 μ f, tubular
- C8, 11, 14—.0015 μ f, tubular
- C15—.01 μ f, tubular
- All capacitors 600 volts unless noted
- J1, 2—phono jacks
- S1—dptd toggle
- S2—3- or 4-position 3-pole rotary (single deck)
- V1—12AU7
- Chassis, 7 x 5 x 3-inch box
- Miscellaneous hardware

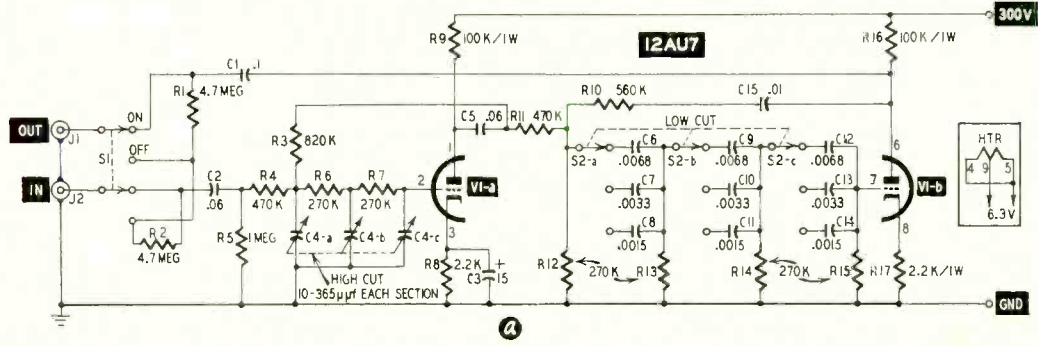


Fig. 2 — Circuit of the audio filter.

more

about

the

CATHODE

FOLLOWER

Designing a preamp output stage that uses a cathode follower isn't quite as easy as it sounds

By NORMAN H. CROWHURST

It seems that I have gone through all this before. My previous article on the subject, "Getting the Cathode Follower Straight" (RADIO-ELECTRONICS, December, 1954) elicited more correspondence from readers than any other article to date. These could be grouped under two headings: (1) the reader who appreciated the presentation (often because he had found the matter out the hard way himself) and therefore found it useful (2) the reader who felt I was doing the cathode follower an injustice!

The latter had apparently been taught in college that the cathode follower is a panacea, not only for all audio troubles, but almost all electronic troubles. Without checking up on the statements I made, he felt my article to be a slight on such a wonderful device.

Recently, however, a friend of mine approached me about designing a cathode-follower output stage for a preamplifier. He had been trying, somewhat unsuccessfully, to apply data obtained from various sources and remembering my article, he thought I might be able to help him solve his problem.

As that article treated the matter only theoretically, it will not be inappropriate to give readers the benefit of this help, so anyone who wishes can apply the correct principles himself. To highlight the possible pitfalls—and make sure some readers do not still

think I am misrepresenting their pet circuits—let's follow my friend's course, by trying first to use the available data.

Published data

Using the symbol R_s for the output source impedance, R_p for the plate resistance, R_L for the cathode load resistance and μ for the tube's amplification factor, several authorities correctly give the formula for output source impedance as

$$R_s = \frac{R_L R_p}{R_L (\mu + 1) + R_p}$$

This formula can be rearranged to find the appropriate cathode load resistance

$$R_L = \frac{R_s R_p}{R_p - R_s (\mu + 1)}$$

My friend found the second formula (written out in full) in the RCA receiving-tube manual. He first thought a feasible tube would be one half of a miniature twin triode, the 12AU7. Looking up the values, he found that, with a plate supply voltage of 250, it requires a grid bias of -8.5 volts, has an amplification factor (μ) of 17 and a plate resistance of 7,700 ohms.

Substituting these values into the formula, assuming a desired 500-ohm output source impedance, he came out with a cathode load resistor of *minus* 3,000 ohms! Not having any negative-value resistors in his junkbox, he decided that a different approach was necessary.

He went on to try a different tube—a 12AX7—but, before we follow him, let's see just what this negative value really means. Go back to the formula for source resistance and substitute successively higher values of cathode load resistance R_L , until we reach a theoretical value of infinity. At this point, the odd term R_p in the bottom of the fraction becomes negligible compared to the terms that contain R_L , as a factor in both top and bottom. This means that, for this particular condi-

tion, the source resistance reduces to the expression

$$R_s = \frac{R_p}{\mu + 1}$$

Hence, for this particular tube, with a theoretical infinite cathode load resistance, the source resistance will be 7,700 ohms divided by (17 + 1), or 430 ohms. This happens to be less than the desired 500 ohms. Using any practical value of R_L , instead of this theoretical infinite value, produces a source resistance that is *lower* than 430 ohms.

Thus, the only way, in theory, that the source resistance could be raised to 500 ohms would be to extend the cathode load resistance beyond infinity and into the negative resistance region. This is all very well in theory, but cannot be done in practice! However, there is a simple and practical way over the difficulty which we shall come to later in the article.

Meanwhile, my friend who turned to the 12AX7 found the relevant values were: grid bias -2, amplification factor (μ) 100, plate resistance 62,500 ohms. Substituting these into the formula gave a cathode load resistor of 2,600 ohms.

Plate current is given as 1.2 ma, so to get a bias of -2 volts, the resistance in this part of the circuit should be only about 1,660 ohms. Using a practical value of 1,800 ohms, with a further series value of 820 ohms to make up the cathode load, the circuit appears as shown in Fig. 1. This supplies correct bias to the tube and should land up with a 500-ohm source resistance.

So my friend went ahead and built this circuit. It came as somewhat of a shock to him to find considerable distortion when he fed the output into a 500-ohm load. Using a distortion meter he found that, with 1 volt out, he was getting up to 20% distortion. Removing the 500-ohm load, the output rose to about 4 volts. Turning the input down a little, he found he could now get 3 volts output with 5% distortion.

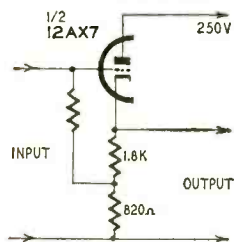


Fig. 1—Circuit—with values calculated from formula and tabulated data—for using a 12AX7 as a cathode follower to give a 500-ohm output impedance.

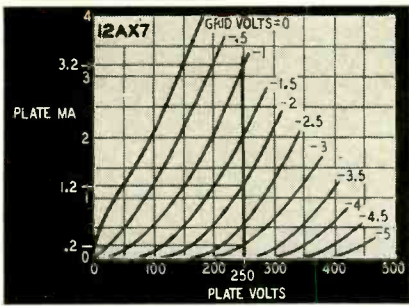


Fig. 2—Characteristics of the 12AX7 show operating condition produced by circuit of Fig. 1.

Even this, however, is rather short of high fidelity! It was at this stage that my friend came to me in desperation.

Why the distortion?

Before showing him how to get better results, it will be well to explain the distortion. Let's take the tube characteristics shown in Fig. 2. A load line representing 2,600 ohms will be so nearly vertical as to be indistinguishable from a constant voltage of 250. The well-known formula for gain of a cathode follower is

$$A = \frac{\mu R_L}{R_p + R_L (\mu + 1)}$$

Using $R_L = 2,600$ ohms, $R_p = 62,500$ ohms, $\mu = 100$ for the unloaded condition, this works out to be 0.8. In other words, the voltage swing between cathode and ground is 4 times that between grid and cathode, with the result that the cathode-to-ground swing is four-fifths of the voltage applied between grid and ground.

Assume that we can apply a grid to cathode swing of 1 volt either way from the -2-volt bias point. Going negative to -3 volts, plate current is 0.2 ma. At -2 volts, plate current is 1.2 ma while, at -1 volt, plate current rises to 3.2 ma. So, for a 1-volt sinusoidal input between grid and cathode, the output will give a fluctuation of 2 ma one way and 1 ma the other way.

This represents a second-harmonic

distortion given by $\frac{a - b}{2(a + b)} \times 100$,

or 16% under this condition. As a cathode follower, however, there would be 4-volt swing from cathode to ground, requiring 5 volts swing from grid to ground to achieve this condition. The feedback will tend to neutralize the distortion to something less than 16%. The gain reduction is 5 to 1 because without feedback 1 volt in produces 4 volts out, while with feedback it takes 5 volts in to produce 4 volts out. So we should expect to reduce the distortion 5 times, or to 3 1/3%.

But 3 1/3% of 4 volts is 133 mv. If the input is pure, there must also be 133 mv of antiphase second harmonic between grid and cathode to balance this. Referred to 1 volt, 133 mv is 13 1/3%. As the tube generates 16 2/3% from the fundamental in opposite phase, this leaves us the difference of 3 1/3% in the

output, as assumed. This is illustrated in Fig. 3.

So we land up with a peak voltage of 4 with distortion of 3 1/3%. Since 3 volts rms is about 4.5 volts peak—a little more than this—it is not surprising to find that distortion read on the meter is 5%.

Now for the loaded condition. Instead of 2,600 ohms for the cathode load resistor, we now use the combined resistance of 2,600 ohms with the 500-ohm resistor in parallel, giving us 420 ohms. From the formula this gives a voltage gain of 0.4, which means that for 3 volts in, between grid and cathode, there will be 2 volts out, between cathode and ground. It will take a 5-volt input to produce a 2-volt swing at the output.

Looking at the distortion on the tube characteristics, swinging 2 volts each way from the bias point of -2: for zero grid voltage the current is about 6 ma (this is beyond the curves given, so is estimated) and for -4 volts, it is zero. Thus the positive swing is 4.8 ma while the negative swing is 1.2 ma. This

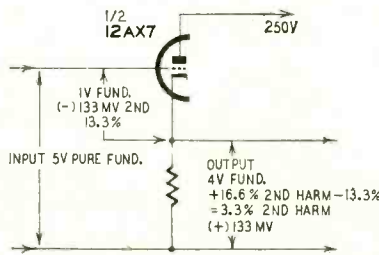


Fig. 3—Distribution of distortion components.

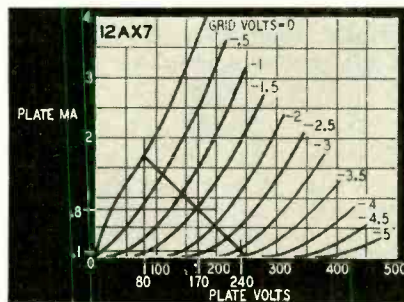


Fig. 4—Characteristic curves of a 12AX7 with a 100,000-ohm load line.

figures out to 30% second-harmonic distortion.

Feedback, however, reduces the gain by three-fifths because, without feedback, 3 volts in would give 2 volts out, while with feedback it requires 5 volts in to give 2 volts out. This means the distortion should be reduced to 18%.

A peak swing of 2 volts between grid and cathode, as just considered, will give 1 1/3 volts between cathode and ground and will require an input of 3 1/3 volts. The output of 1 1/3 volts peak is equivalent to 0.7 times this, or about 0.95 volt rms.

With a theoretical distortion of 18% for 0.95 volt it is not surprising to find that we measure 20% with 1 volt.

A good cathode follower

So theory backs the measurement.

How, then, are we to improve the performance of a cathode follower for a preamplifier output circuit? Using this example, it is evident that loading with 500 ohms produces an actual plate circuit load of 420 ohms. This not only produces excessive nonlinearity but reduces the working gain of the tube by one-third.

If we use a higher resistance in the cathode circuit, we should improve this situation somewhat because the effective cathode load would then be nearer the external value of 500 ohms. While this would reduce the distortion a little, the best solution is to operate into an open circuit, or at least a virtual open circuit. This way, the only 500 ohms present is that provided by the tube's cathode circuit. This method, using a larger value of resistor in the cathode circuit, considerably improves the output.

Reworking the characteristics, we could use a 100,000-ohm cathode load and arrange to have a bias of 1.5 volts (see Fig. 4). This gives a plate current of 0.8 ma, so the bias resistor should be about 2,000 ohms.

A 1.5-volt swing each way, measured between grid and cathode from the bias point, yields a swing from 170 volts at the bias point to 80 and 240 volts. This represents 10% distortion since there is a 60-volt excursion one way and 90 volts the other.

However, a 3-volt peak-to-peak input produces 150 volts peak-to-peak output, which means the tube is operating at a gain of 50. As a cathode follower it will require 153 volts in to give an output of 150. This means that the gain reduction is 51. Dividing the 10% distortion by the factor of 51 gives us an overall distortion of slightly less than 0.2%, which is a considerable improvement. The necessary circuit is shown in Fig. 5.

Now let's assume that the same circuit is loaded with 500 ohms. Drawing a vertical load line through the 170-volt operating point, we can consider an excursion from -0.5 to -2.5 volts on the grid. This will produce a current swing from 2.5 ma to 0.1 ma, or 2.4 ma overall across 500 ohms. This produces a swing of 1.2 volts from cathode to ground for the 2-volt swing between

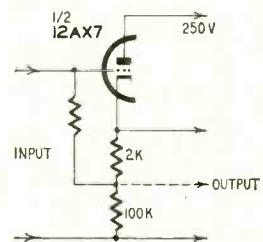


Fig. 5—Basic circuit for cathode follower represented in Fig. 4. For simplicity, coupling capacitor is not shown. The dotted line shows an alternate output, which gives 2% less voltage on open circuit and a source resistance about 2,000 ohms higher than the solid line connection.

AUDIO—HIGH FIDELITY

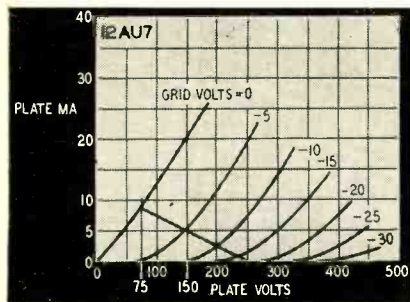


Fig. 6—Characteristics of a 12AU7, showing cathode follower operation using a 20,000-ohm load.

grid and cathode, or a total of 3.2 volts swing at the input from grid to ground.

The 2.4-ma swing is made up of 0.7 ma negative from 0.8 and 1.7 ma positive. This represents 15% distortion.

However, the feedback, which reduces gain by a ratio of 2/3.2, the difference in the input required to give 1.2 volts out, brings the distortion down to slightly less than 10%.

This is for a peak-to-peak output of 1.2 volts, or an rms of not much more than 0.4 volt. So, for working into a loaded circuit, use of a larger cathode resistance has made our position worse—we cannot get as much output for the same amount of distortion.

Back to the 12AU7

Now let's return to my friend's first choice, the 12AU7. Its characteristics are shown in Fig. 6 and a 20,000-ohm load line is drawn from a 250-volt operating point. For convenience in assessing distortion, we'll assume the bias is -5 volts. This gives an operating point of 150 volts at the plate. So the bias resistor has to be 1,000 ohms as shown in Fig. 7.

To assess operating conditions without an external load, assume a 5-volt excursion each way: the plate voltage swings from 75 to 150 to 200. This again represents 10% distortion, but the overall swing of 125 volts cathode to ground is achieved with a grid-to-cathode swing of 10 volts, or 135 volts from grid to ground. This means that the gain is reduced by a factor of 13.5, so that the resulting distortion will be 10/13.5, or about 0.75%.

This is at an output of 125 volts peak to peak or 45 volts rms. As practical levels would be a lot lower than this, we can expect less distortion than with the 12AX7.

Now consider what happens when we load the output with 500 ohms. Drawing a vertical line through the 150-volt point on the 5-volt bias curve, we find that the current excursion is now from 0 to 5 to 20 ma. This represents 25% distortion. A swing of 20 ma in 500 ohms will produce 10 volts output swing for 10 volts from grid to cathode. So feedback will just halve the distortion, reducing it to 12.5%.

But notice that here we have a swing of 10-volts peak to peak available, or about 3.5 rms with 12.5% distortion. So it should be possible to produce an output of about 1 volt rms with not

much more than 1% distortion, which is a considerable improvement on the possibility with the 12AX7.

Source resistance

But, using this method, how can we assess the output source resistance? We could, of course, use the formula again but it is simpler, as we are using tube characteristics to assess distortion, to use the same characteristics to assess source resistance produced.

Reverting to the 12AX7 with a 100,000-ohm load resistor (see Fig. 4), we observe the slope of the -1.5-volt characteristic where it intersects the load line. This we can judge by noticing the voltage change corresponding to a given

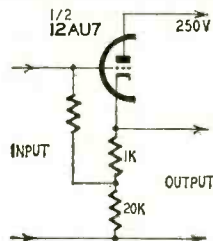


Fig. 7—Basic circuit of cathode follower represented in Fig. 6.

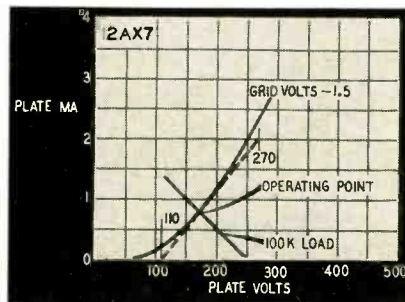


Fig. 8—Finding the working value of a tube's plate resistance—a 12AX7—at the operating point of Fig. 4.

current. Drawing a tangent to the 1.5-volt line (dashed line in Fig. 8), we get 0 ma at 110 volts and 2 ma at 270 volts, a difference of 160 volts for 2 ma or 80 volts for 1 ma. This represents a plate resistance of 80,000 ohms which is effectively in parallel with the 100,000-ohm coupling resistor, giving a source resistance, without feedback, of 45,000 ohms.

You will recall that feedback reduces gain by 51 times, so the plate resistance or source resistance is also reduced 51 times. So 45,000 ohms becomes about 880.

Using the same method with the 12AU7 tube and drawing a tangent to the curve, we find the working plate resistance to be about 10,000 ohms—there is a 100-volt change for 10 ma. The coupling resistor was 20,000 ohms, so the source resistance without feedback is about 6,700 ohms. The gain reduction was 13.5 to 1 so the source resistance is 6,700 ohms divided by 13.5, or about 500 ohms.

This is the desired figure of 500 ohms. There is no margin for adjustment. If the 500-ohm figure is important, a load resistor of less than 20,000 ohms can be used. Try, for example, 10,000 ohms.

The load line for this is shown in Fig. 9. Using a bias of -5 volts, we require a 620-ohm bias resistor.

The output swing is 100 volts for a grid swing of 10 volts. The distortion is about 5% and, with feedback reducing the gain at 11 to 1, distortion is less than 0.5%. This is probably a little more than the other load line gave for the same output level, but is a big improvement over the original values obtained. At an output of a few volts instead of 35 volts rms (at which the 0.5% is obtained), distortion should be very small.

At this point on the -5-volt curve, plate resistance is about 8,000 ohms, which in parallel with 10,000 ohms gives 4,500 ohms. This divided by 11 gives an output resistance of about 410 ohms. This result has been confirmed in practice. Lower values of plate resistance can be used, but they cause further increases in distortion. For achieving a reasonable distortion figure 10,000 ohms is about a minimum value.

If the source resistance is reduced below the design figure, it can be padded out with series resistance, as shown in Fig. 10. There is no need to go in search of a negative resistance for the load circuit!

The procedure in designing a cathode-follower output is to find a suitable load line in the same way as designing an ordinary plate-coupled output.

If the cathode follower is to be matched-loaded, distortion will be inevitably high unless the levels are kept very low. The more practical use of a cathode-follower output is to provide a low source resistance, so the connect-

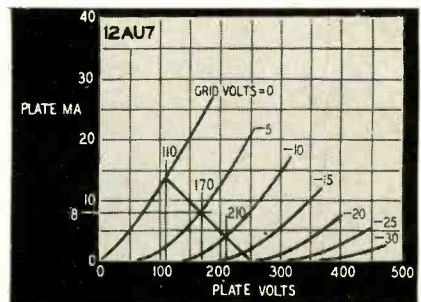


Fig. 9—Using a lower value load for the 12AU7—10,000 ohms—produces a lower source resistance, with slightly more distortion for the same output level.

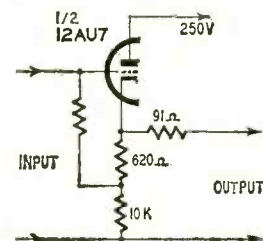


Fig. 10—Instead of looking for a negative resistor, the desired source resistance can be padded out as shown here. The values indicated give a source resistance of 410 ohms, which can be padded to 500 ohms by the 91-ohm resistor. In practice a coupling capacitor is needed.

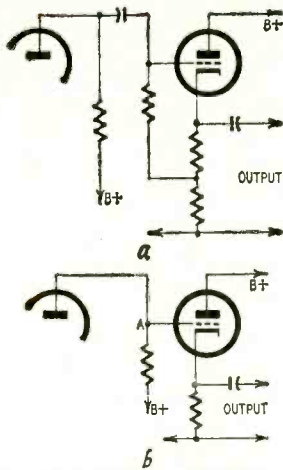


Fig. 11—Practical considerations: a—the traditional way of connecting a cathode follower to get correct operating conditions and block dc components; b—a practical method that eliminates one coupling capacitor and two resistors, but requires careful control of the dc potential at point A on the previous stage.

ing link between a preamp and power amplifier is nonsusceptible to loading effects due to cable capacitance or static pickup. The low impedance presented, looking back into the cathode follower, effectively short-circuits any

kind of static pickup that might otherwise occur. The load to which the cathode follower is connected can then be large compared to R_s with no ill effects.

While a high-slope triode, such as the 12AX7, can be used to provide a low source resistance at low signal levels, low-impedance tubes like the 12AU7 are more flexible in this application. When working into open circuit or high impedance, the coupling resistance in the cathode circuit should be more than the plate resistance of the tube—preferably at least $1\frac{1}{2}$ times. Above this value, further increase does not make much difference in performance, provided suitable operating conditions are chosen. Below it, distortion begins to increase rapidly. For working into a matched load, the best coupling resistor is, more critical and should be in the region of the tube's plate resistance.

But the ideal purpose of a cathode-follower output stage is not for matching a low resistance. It is for providing a low source resistance.

If a number of power amplifiers are connected in parallel, or fed through frequency-selective networks for separate channel amplification, a cathode follower is ideal to prevent interaction between the different inputs.

The practical circuits shown in this article use a return point for the bias obtained by calculating and employ a coupling capacitor to isolate the plate voltage from the previous stage. An alternative method of design is to work out the cathode-follower details in conjunction with the preceding stage.

If the operating voltage drop, as in this example, is 105 from cathode to ground, then the plate voltage of the preceding stage can be designed to operate around 100 volts—the cathode-to-ground voltage plus the bias voltage of 5. Then the output can be direct-coupled, as shown in Fig. 11.

This obviates the necessity for a coupling capacitor, a grid-to-bias-point resistor and a separate bias resistor. So we save a coupling capacitor and two resistors by using this method!

In this article I have gone into the question of what value capacitor to use. This will be determined, in the usual way, by low-frequency response consideration. An important point that should be mentioned, though, is that matching into a 500- or 600-ohm load necessitates a very large output coupling capacitor, about 100 times the value necessary when working from a cathode follower into a high impedance. END

NEXT MONTH

◆ Build an Electronic Compass

You can pinpoint your position in the woods or on the water with this combination magnetic compass and radio direction finder.

◆ An Electronic Boat Horn

This transistorized unit combines a horn with a low-power loud hailer.


◆ Mr. Math-Simplified Analog Computer

Learn how an analog computer works while solving easily and quickly many of the problems that turn up in servicing and design.

Final Touchup For Your Amplifier

By HAROLD REED

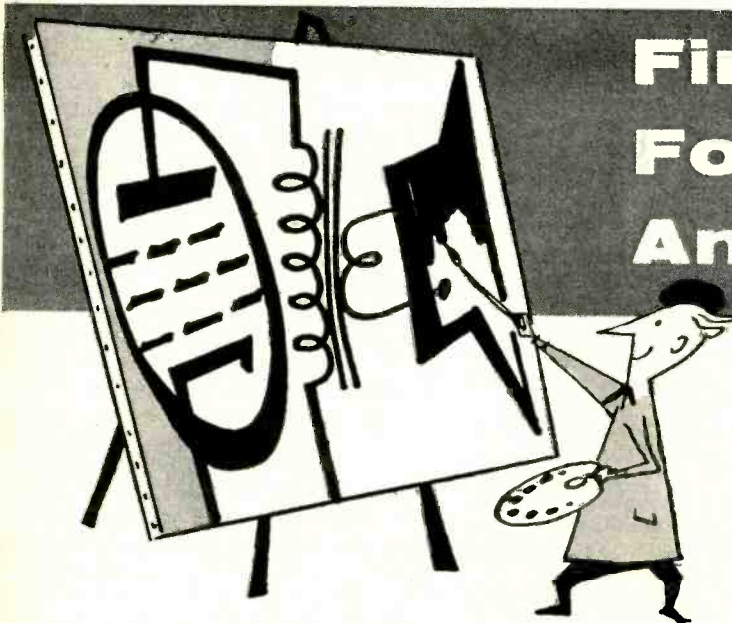Some simple methods for correcting an audio amplifier's frequency response



IN designing and building audio amplifiers, known and proven practices must be followed to obtain the best possible frequency response. This, of course, includes careful selection of resistive and capacitive components used in the amplifier's circuitry, and high-quality transformers. But, when the amplifier is complete, it may still be desirable to apply frequency correction for one reason or another. Let us first consider a simple method to provide some high-frequency boost.

The cathode resistor in a voltage-amplifier stage provides correct dc operating bias for the tube. The audio signal voltage also appears across this resistor and the voltage drop developed is in opposition to the input signal voltage. This results in inverse or negative feedback, causing a reduction in gain. It is customary, therefore, to bypass the cathode resistor with a large capacitor, presenting a low impedance to the signal current and reducing the audio voltage drop to a negligible value. However, beneficial results may often be obtained by not bypassing the cathode resistor heavily. Let us consider the voltage-amplifier stage in Fig. 1.

High-frequency boost

Without any bypass capacitor across cathode resistor, R_c , feedback voltage reduced stage gain by about 5 db. A

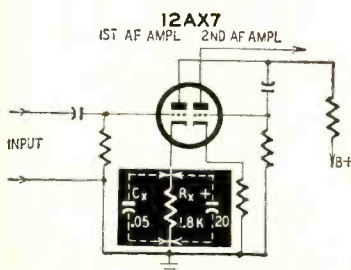


Fig. 1—Bypassing the cathode resistor resulted in high-frequency boost.

20- μ f capacitor shunted across this resistor ended this loss in gain, boosting the voltage 5 db from 20 to 15,000 cycles and 4 db at 20,000 cycles.

Suppose your amplifier is dropping off at the higher frequencies. We may be able to obtain just the desired boost with a small capacitor across the cathode resistor. As an example, the 20- μ f capacitor shown in Fig. 1 was removed and replaced by a .05- μ f unit, C_x . This results in a boost of about 2 db at 10,000 cycles, 3 db at 15,000, and 4 db at 20,000 cycles. The small value of capacitance has high reactance to the lower frequencies and causes little or no change in the feedback voltage. At the higher frequencies, the capacitor's reactance becomes relatively small, causing a reduction in the signal-voltage drop in the cathode circuit and a cor-

responding reduction in negative feedback. In the example just cited, capacitive reactance X_c equals the 1,800-ohm resistor at about 17,000 cycles. This correction may be applied to the pre-amp if a large cathode bypass is not needed to reduce hum. If a bypass is needed, the alteration should be applied to a later voltage-amplifier stage.

Another convenient method that can be used to increase gain at the higher frequencies is shown in Fig. 2. A capacitor and resistor in series are placed between cathode and ground. Feedback from the amplifier output is brought back to this cathode circuit. The reactance of the .01- μ f capacitor C_x equals the 1,000-ohm resistor R_x at 16,000 cycles.

The capacitor couples 1,000 ohms in parallel with 2,200 ohms, reducing the

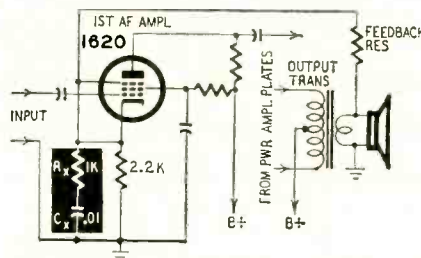


Fig. 2—Another method of increasing high-end boost.

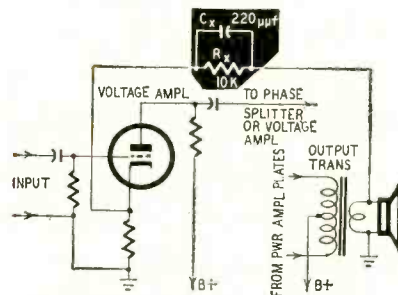


Fig. 3—High-frequency attenuation attained by shunting the feedback resistor.

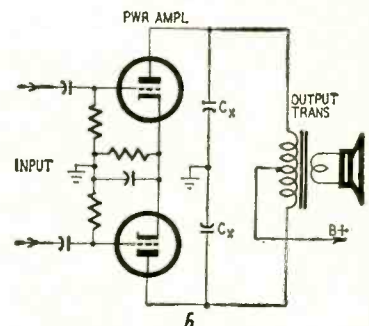
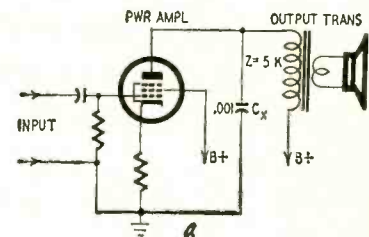


Fig. 4—Suppressing ultrasonic oscillations: a—in a single-ended output stage; b—in a push-pull output stage.

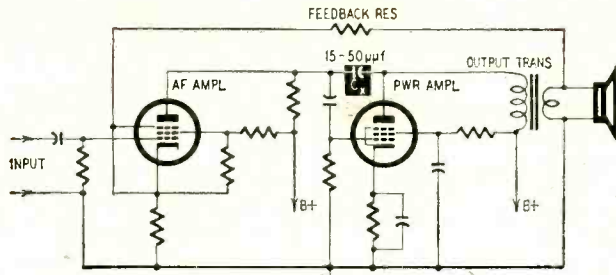


Fig. 5—A one-stage feedback loop also helps avoid ultrasonic oscillation.

combined value to about 690 ohms. A change from 2,200 to 690 ohms will give about a 10-db boost, most of which will occur by 16,000 cycles—theoretically about 7.3 db. Other factors adjust this to a 6-db overall rise in gain at 16,000 cycles with the particular values given for R_x and C_x . The reactive value of C_x increases with decreasing frequency and has negligible effect at the lower half of the audio band.

In a specific case, an amplifier was flat when designed and tested in the experimental breadboard manner. After being dressed up and packaged relatively long shielded leads in the grid circuit, including the gain control, resulted in a high-frequency drop. The simple R-C network shown provided a remedy with negligible effect on other characteristics.

Suppressing ultrasonics

It may be desirable to attenuate certain audio frequencies. One useful arrangement for high-frequency attenuation is presented in Fig. 3. The feedback resistor is shunted by a suitable capacitor. This is often helpful in suppressing ultrasonic frequencies or reducing gain at the upper limit of the audio band.

Suppose we are concerned with a parasitic oscillation above 20,000 cycles. In Fig. 3 the feedback resistor (R_x) is 10,000 ohms. Shunting it with a 220- μ f capacitor delivers an attenuation of 1 db at 20,000 cycles. The capacitive reactance X_c becomes smaller as frequency increases, introducing more feedback and reducing gain above the audio range. An even smaller capacitor, causing less than 1-db attenuation at 20,000 cycles, may be enough to suppress the parasitic, depending of course on the frequency of oscillation. Larger capacitor values can be used to reduce gain in the upper part of the audio band. However, this cannot be carried too far. Increasing the feedback beyond a certain value at the high frequencies will result in the amplifier breaking into oscillation.

There are other ways to suppress ultrasonic oscillations. A small capacitor may be connected from the plate of the output tube to ground. Its value will depend on the output load impedance and usually can be small enough to have negligible effect on the amplifier frequency response. (See Fig. 4-a.) Measurements in the circuit with indicated values of output load and C

showed 0.1-db attenuation at 20,000 cycles and 6-db attenuation at 44,000 cycles. This method may also be applied to a push-pull output stage as shown in Fig. 4-b. Larger capacitor values may be used if attenuation of the upper audio frequencies can be tolerated.

Another simple treatment often found effective is shown in Fig. 5. A small amount of feedback at high frequencies is introduced around one stage by a small capacitor, say between 15 and 50 μ f. This is inside the normal feedback loop.

Audio-frequency phase shift in a negative-feedback amplifier prevents the use of maximum feedback voltage. Neutralization of high-frequency phase shift can be obtained with an R-C network in the output stage as shown in Fig. 6-a. Resistor (R_x) and capacitor (C_x) in series are placed across the plate of each stage of the push-pull circuit; that is, across each half of the transformer winding. This is a typical output stage often found in hi-fi amplifiers and uses tubes like the 6V6 with an 8,000-ohm-to-voice-coil output transformer. The capacitive reactance X_c at 20,000 cycles is 8,000 ohms. This, in series with the 2,200-ohm resistor, places an impedance of about 8,300 ohms across each half of the transformer primary at the top of the audio band. X_c , then, increases or decreases inversely with frequency. Another circuit arrangement is given in Fig. 6-b, using a single resistor and capacitor.

Low-frequency alterations

You may want to make some minor alterations at the lower audio frequency. The reactance of the coupling capacitor between the plate of one stage and grid of the next is usually negligible at the middle and high frequencies of the audio band. At the lower frequencies its reactance can be come appreciable and some of the signal voltage will appear across it, resulting in loss of low-frequency gain. Therefore, the coupling capacitor is made relatively large. However, if you want to attenuate the lower frequencies, you may deliberately reduce the capacitive value of the coupling capacitor. Consider the circuit in Fig. 7. The frequency response was flat within 0.5 db using the .01- μ f capacitor C_x . By replacing this with a .001- μ f unit, the frequency response became -4 db at 30

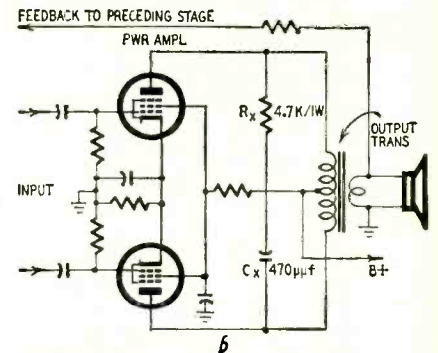
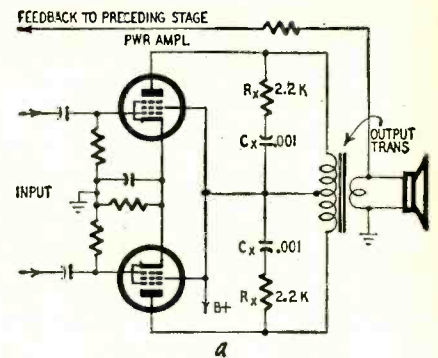


Fig. 6—Neutralizing audio-frequency phase shift.

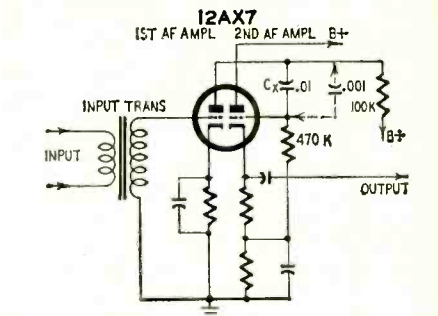


Fig. 7—Reducing the value of the coupling capacitor attenuates the lower frequencies.

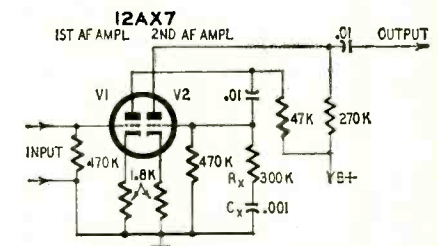


Fig. 8—Bass boost with a simple R-C network.

cycles and zero db at 1,000 cycles. This attenuation decreases with progressively larger values of the coupling capacitor. Some interesting data on bass attenuation in R-C-coupled pentode stage by variation of the screen bypass capacitor are given in the *Radiotron Designer's Handbook*.¹

Bass can be boosted with a simple R-C network as shown in Fig. 8. R_x and C_x are shunted across the plate circuit of V1. If C_x is .001 μ f, its reactance is equal to R_x , 300,000 ohms at approximately 550 cycles. As the frequency of the audio signal decreases, the reactance of C_x increases, and a

AUDIO—HIGH FIDELITY

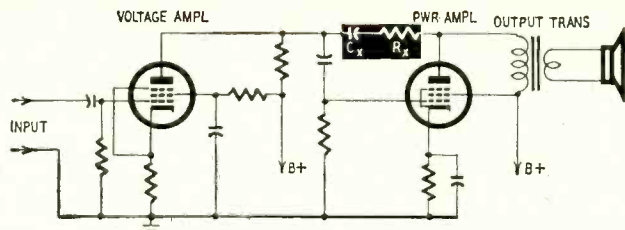


Fig. 9—Another bass-boost network.

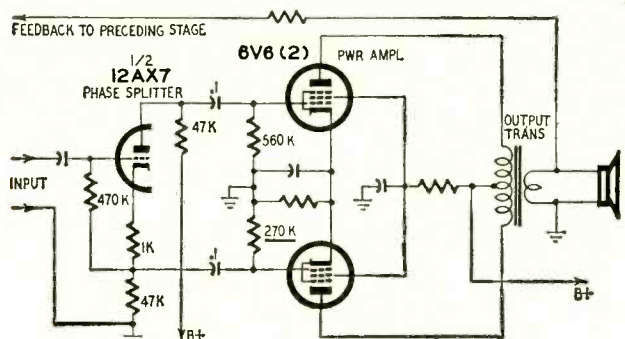


Fig. 10—Changing grid-resistor values can end high-frequency oscillation.

larger signal is available at the grid of V2. Using the circuit and values indicated, response was 5 db at 30 cycles and zero db at the reference frequency, 1,000 cycles. The response was within 1 db across the band prior to connecting the R-C network. The value of the grid resistor for the stage following the R-C network must be as high as possible with respect to R_x . Also the value of R_x should be at least twice the plate resistance of V1 to prevent plate loading of the tube.

Another handy network for bass boost is presented in Fig. 9. A capacitor is inserted in series with the feedback resistor. As frequency decreases, the reactance of C_x increases, resulting in reduced feedback and greater gain. *Caution:* Negative feedback is reduced at the low end where it is most needed to control distortion. Increasing gain in this manner may also increase distortion.

When using the phase-splitter type of phase inverter, balance at the lower frequencies is usually good. Shunt capacitances across the plate and cathode outputs of the inverter, however, are different at the high frequencies and unbalance may result. High-frequency response is better through the cathode side of the inverter than through the plate side as the grid input capacitance of the output tubes has less effect on the cathode side of the phase splitter than on the high-impedance plate side. With increased feedback, instability may be a problem.

Where very-high-frequency oscillation exists in an amplifier, varying the values of the grid resistors, lowering the resistance in the grid circuit opposite the cathode side of the inverter, is helpful. This may best be done by temporarily inserting a 500,000-ohm potentiometer in place of the fixed resistor shown in Fig 10.

This differential in the grid resistors

results in considerable attenuation at the lower frequencies if small coupling capacitors, say .01 μ f, are used. In Fig. 10 these capacitors are 0.1 μ f and there is negligible effect on the low-frequency response even when the potentiometer is reduced to 270,000 ohms, or half the value of the other grid resistor. (But, in feedback circuits, check for instability!)

Another method of obtaining balance

is to apply some negative feedback to one side of the circuit. If feedback is provided by a small capacitor on the side of the circuit with the greatest response to the higher frequencies, then balance can be effected due to the reduction in gain on this side of the circuit. Since the response is greater on the cathode side of the inverter, negative feedback should be introduced on this side of the circuit. A good arrangement for applying this method in the 50-watt amplifier circuit is given by David Hafler.² A 390- μ f capacitor is connected from the screen of the output stage, situated on the inverter cathode side of the circuit, to the cathode circuit of the amplifier input tube, thus reducing high-frequency gain on this side of the circuit.

The db loss or gain figures given in the foregoing discussion were measured values with the configurations employed. The audio amplifier constructor should use these merely as a guide and select R and C values best suited for his needs and in accordance with his particular amplifier circuitry. While these procedures worked with the particular amplifier tested, you may not get the same results with every amplifier. However, these suggestions are useful and the examples show what has been done. END

REFERENCES

- ¹Radiotron Designer's Handbook, 4th Edition, Radio Corporation of America.
- ²David Hafler, "A 50-Watt Power Amplifier," *Radio and Television News*, June, 1956.

Whadya mean you won't take my ad?



Sorry, Mr. Mail-Order-Tube Advertiser, as long as you refuse to state in your advertisement whether the tubes you sell are new or used, perfect or seconds, rejects, surplus or in any way substandard, RADIO-ELECTRONICS will not accept your advertising. That's been our policy since January, 1956. It has cost us a substantial volume of advertising, yes—but it has won us a great many friends too. So, as long as it protects our readers, we're going to stick with it.

The capacitance of this startling little semiconductor, the size of a 1/4-watt resistor, varies with the voltage applied to it

using the VARICAP

By RUFUS P. TURNER

THE capacitance of a reverse-biased semiconductor junction varies with the reverse dc voltage—capacitance decreases as voltage is increased. This effect has been noted in both diodes and power rectifiers. In selenium rectifier plates, for example, the capacitance is comparatively large, often reaching 0.25 μ f or more. Attempts to use this voltage-sensitive capacitance have been thwarted by the comparatively low reverse resistance of the junction—rather high currents are needed to effect the capacitance changes, and the Q is too low for most practical applications. Also, both the capacitance and reverse resistance are extremely temperature-sensitive in ordinary diodes and rectifiers.

An important milestone was reached with development of the silicon junction diode. This semiconductor device has capacitance in small but useful amounts readily varied by the reverse bias. And the reverse resistance of the silicon p-n junction is so high (often 10,000 megohms at -1 volt) that almost no current at all is required to do the job. Essentially a high-Q component, the silicon junction is noted for the stability of its capacitance over a wide temperature range. In research laboratories during the past 2 years, the voltage-sensitive capacitance of the

silicon p-n junction has been used in experimental voltage-operated tuning, frequency modulators, automatic frequency control, capacitor type amplifiers, tunable filters and numerous sensitive remote-control devices. Workers who had been intrigued by the earlier dielectric amplifier (using voltage-sensitive ceramic capacitors), only to be frustrated by their severe temperature drift, have had their interest restimulated by the silicon junction.

Now, a useful new semiconductor component, the Varicap (see RADIO-ELECTRONICS, January, 1958, page 45) has become commercially available. This simple, two-terminal, p-n junction device, designed for use as a voltage-variable capacitor, opens new vistas for the simplification of many electronic circuits. The number of applications to old circuits and the possibilities for new circuits will be limited only by the experimenter's imagination and ingenuity. No larger than most 1/4-watt resistors and resembling a miniature crystal diode, the Varicap will do the work of a reactance modulator tube or of a variable capacitor, both of which are many times its size.

Varicap characteristics


Fig. 1 shows the schematic symbol and equivalent circuit of the Varicap. The markings in Fig. 1-a indicate the dc bias voltage polarity. The positive end of the unit is marked with a painted black band.

Fig. 1-b shows the equivalent circuit. Capacitance C varies approximately as $1/\sqrt{V}$, where V is the reverse bias voltage, and is practically constant (for

any given value of V) from -65°C to 150°C . Both capacitance and the series resistance (R.) are substantially independent of the operating frequency. The maximum frequency at which the equivalent circuit remains as shown in Fig. 1-b is 500 mc.

Varicaps are available in six capacitances, as shown in the chart. These capacitances are obtained with a dc bias of -4 volts. Capacitance tolerance is $\pm 20\%$. A Varicap costs about \$1.50.

Fig. 2 shows the capacitance variation with reverse dc bias voltage. This curve applies to all types of Varicaps, regardless of their nominal capacitance, and shows that each has 100% of the rated capacitance when the bias is -4 volts. Only a few millimicroamperes of

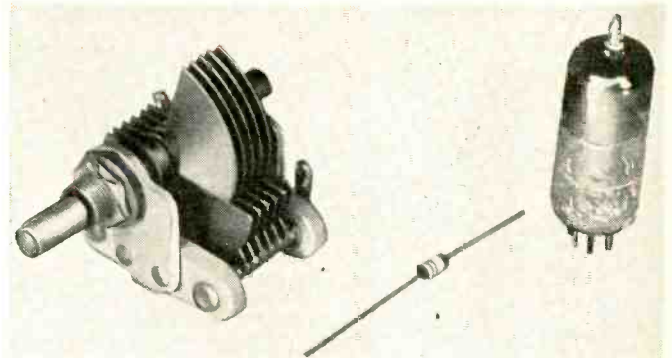

(Above) a Miniature tuning capacitor and reactance tube dwarf Varicap which may replace them. (Below) Afc circuit which you can add to FM receiver fits on 2 1/8 x 2 3/8-inch Phenolic board.

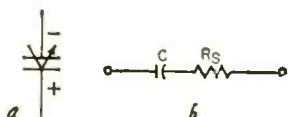
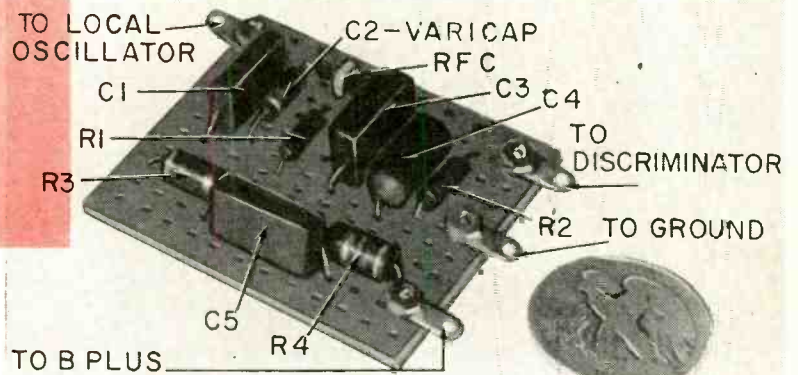


Fig. 1—Schematic symbol and equivalent circuit of the Varicap.

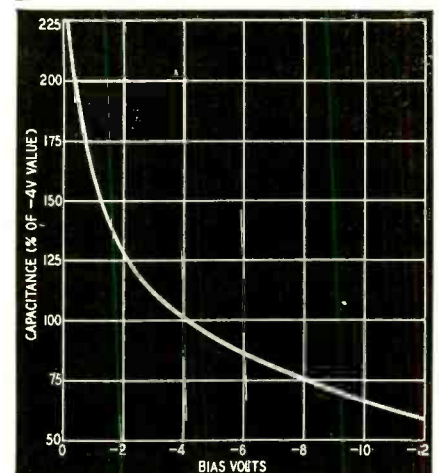


Fig. 2—How capacitance varies with bias voltage.

ELECTRICAL CHARACTERISTICS OF THE VARICAP					
Varicap Type Number	Capacitance @ -4 v ¹ (μf)	Maximum Operating Voltage ²	Series Resistance		Typical Q @ 50 mc
			Maximum (ohms)	Typical (ohms)	
V20	20	-20	18	8.5	18.7
V27	27	-20	14	7.5	15.7
V33	33	-20	12	6.6	14.6
V39	39	-20	10	5.4	15.1
V47	47	-20	7.5	4.4	15.4
V56	56	-15	7.0	4.2	13.5

¹Tolerance ±20%.
²The bias voltage plus the signal voltage peak should not exceed the maximum operating voltage. Also, the bias voltage should not be set so low that the signal voltage will swing the Varicap into the forward, or conducting, direction.

current flow when bias is applied to the Varicap. Thus, virtually no power is required to vary the capacitance of this very-high-resistance device.

Since the bias signal may be either steady or fluctuating, a variety of control signals may be employed. The frequency range extends from dc to more than 500 mc.

In any application, the total voltage applied to the Varicap (that is, the dc bias voltage plus the signal-voltage peak when there is an alternating component) must not exceed the unit's maximum operating voltage. Also, since the Varicap is a diode operated in the reverse direction, the dc bias voltage should not be set so low that the signal-voltage peak will swing operation into the forward, or conducting, region.

The Varicap actually utilizes the capacitance of the p-n junction to do its job. Why capacitance exists in the junction won't be rehashed here. Junction capacitance in semiconductor devices is familiar to the reader; collector capacitance, for example, is well known for its role in limiting the high-frequency response of transistors.^{1,2}

In a conventional capacitor, a small leakage current flows through the dielectric because it is not a perfect insulator. The higher the insulation resistance, the lower this current. In a mica capacitor in good condition, dielectric resistance may be 100,000 megohms or more, and the leakage current at low dc voltages so tiny that it can be ignored completely. In a tubular paper capacitor, the dielectric resistance may be as low as 1,000 megohms; therefore leakage current is much higher than in a mica unit. The leakage current is highest of all in an electrolytic capacitor; it may be an appreciable part of a milliampere. Because of leakage current, the equivalent circuit of a capacitor shows a leakage resistance in parallel with the capacitor plates.

The leakage resistance is so high in a mica capacitor that its shunting effect is negligible. The dielectric between the plates approaching a perfect insulator, there is (to all practical intents and purposes) no appreciable

leakage path between the plates, and the parallel resistance may be erased from the equivalent circuit. Similarly, in the Varicap, the leakage resistance is extremely high (in the order of tens of thousands of megohms) since the reverse-biased silicon p-n junction passes only a few thousandths of a microampere. As in the mica capacitor, the parallel resistance may be ignored and the junction considered a capacitance, since its reactance is many orders of magnitude lower than the shunting resistance. The situation is much the same as having a very good dielectric between the "plates" of the junction. This capacitance varies, as explained earlier, with the impressed dc reverse voltage.

A conventional capacitor also has a series resistance component R_s. At high frequencies, the magnitude of this resistance is due to the resistance of plates, leads and various in-phase components of current. The Q of the capacitor is affected by this series resistance. The Varicap also has an R_s component. It is shown in Fig. 1-b and is specified for each type in the chart. The Q of the Varicap (but not its capacitance) similarly depends upon this series component. As mentioned earlier, however, this series resistance component is independent of frequency up to 500 mc.

It is well to reflect that other semiconductor junctions, such as germanium diodes and selenium rectifiers, pass much higher reverse (leakage) currents. These leakages are not only higher than those of high-quality silicon junctions but increase markedly with increased reverse voltage. In these units, because the leakage resistance is often of the same order of magnitude or even lower than the capacitive re-

actance, the useful change produced by changing the voltage on these devices is not exclusively a capacitance change but rather a change in the impedance of the equivalent R-C circuit. In this respect, the selenium rectifier somewhat resembles the electrolytic capacitor with its high leakage. Quite to the contrary, the extremely high leakage resistance of the silicon p-n junction and its useful capacitance identify it as a high-quality capacitor.

Tuning effect

One of the first applications that comes to mind is use of the Varicap as a voltage-variable tuning capacitor in an L-C circuit. Fig. 3 shows the author's test setup to demonstrate this effect and to check the tuning range for one set of operating conditions.

In this arrangement, C2 is a type V56 Varicap which serves as the tuning capacitor of the L-C circuit, L2-C2. Capacitor C1 blocks direct current flow from the coil. This capacitance is very large with respect to C2. Adjustable dc bias is supplied by a battery through potentiometer R2. The bias level is indicated by the dc voltmeter. Isolating resistor R1 blocks rf flow into the dc circuit but introduces no appreciable dc voltage drop because of the negligible direct current flowing through the Varicap. An rf choke can be used in place of R1. The rf vtvm acts as a high-impedance resonance indicator. The test signal is supplied by a conventional rf signal generator link-coupled to the L-C circuit through coil L1. Coil L2 has been wound for resonance with C2 in the vicinity of 2 mc.

Near zero dc voltage, the Varicap has its highest capacitance (nominally greater than 100 μf) and the L-C circuit therefore is tuned to its lowest frequency. At -9 volts, the capacitance is low (approximately 39 μf) and the circuit is tuned to its highest frequency. To keep within operating ratings of the Varicap, the dc voltage should not be set to less than 1, nor the rf voltage, indicated by the vtvm, to more than 0.5 volt rms.

To demonstrate the effectiveness of the Varicap as a voltage-variable tuning capacitor: (1) Set the dc voltage to -1. (2) Tune the rf signal generator for resonance, as indicated by peak deflection of the vtvm. Set the generator output control to hold this deflection to 0.5-volt rms. (3) Record the generator frequency as f1. (4) Set the dc voltage

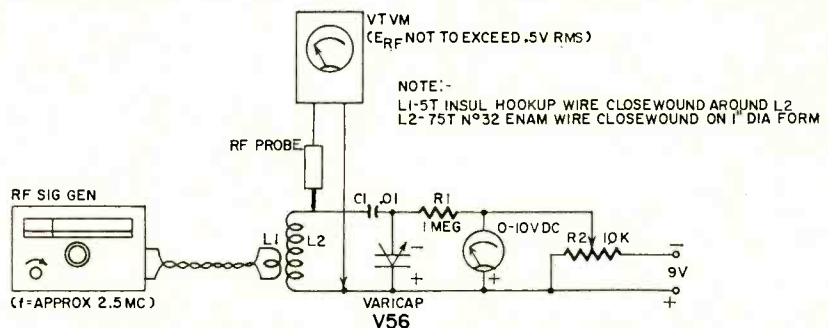


Fig. 3—Test setup to demonstrate Varicap performance.

¹William Shockley, *Electrons and Holes in Semiconductors*, D. Van Nostrand Co., 1950, page 100.

²D. C. Brown and F. Henderson, "The PN Junction as a Variable Reactance Device for FM Production," *Electronic Engineering*, (London) November, 1957, page 556.


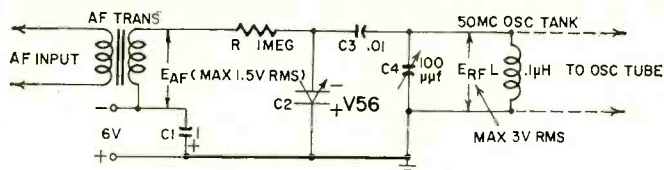


Fig. 4—Circuit of a Varicap frequency modulator circuit.

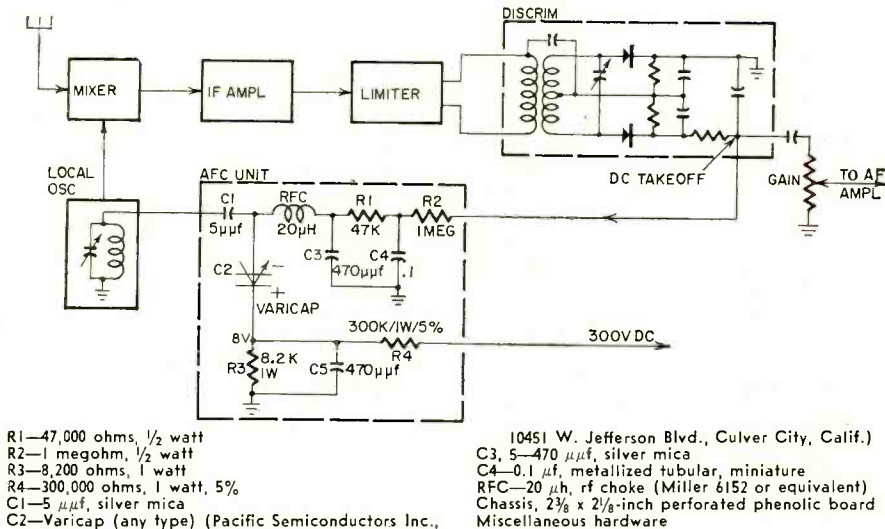

R1—47,000 ohms, 1/2 watt
R2—1 megohm, 1/2 watt
R3—8,200 ohms, 1 watt
R4—300,000 ohms, 1 watt, 5%
C1—5 μ mf, silver mica
C2—Varicap (any type) (Pacific Semiconductors Inc.,

10451 W. Jefferson Blvd., Culver City, Calif.)
C3, 5—470 μ mf, silver mica
C4—0.1 μ f, metallized tubular, miniature
RFC—20 μ h, rf choke (Miller 6152 or equivalent)
Chassis, 2 3/8 x 2 1/8-inch perforated phenolic board
Miscellaneous hardware

Fig. 5—A Varicap afc circuit for your FM receiver.

to -9 , noting that the vtvm deflection falls indicating detuning of the circuit. (5) Retune the generator to locate the new, higher resonant frequency and record this as f_2 . The tuning range afforded by the 8-volt bias change is equal to $f_2 - f_1$.

In the test setup shown in Fig. 3, the circuit was tuned from 1400 kc at -1 volt to 2250 kc at -9 volts, a tuning range of 850 kc. A wide frequency band may be covered with the same capacitance change if L_2 's inductance is made smaller to increase the operating frequency. In some applications of this principle, it will be desirable to use the Varicap as a voltage-variable trimmer in parallel with an air tuning capacitor.

Many applications of this principle suggest themselves. Examples are the voltage tuning of rf test oscillators, local oscillators in radio and TV receivers (especially in remote control operation), self-excited oscillators in transmitters and absorption wave-meters.

Frequency modulator

In the experimental circuit shown in Fig. 4, the Varicap (C2) is shunted (through .01- μ f blocking capacitor C3) across the tank circuit (L-C4) of a self-excited 50-mc oscillator. An audio-frequency voltage (E_{ar}) is applied to the Varicap in series with the 6-volt dc bias supplied by the battery. This ac fluctuates the bias at the audio-frequency rate. The capacitance of the Varicap accordingly fluctuates about its mean -6 -volt value, frequency-modulating the oscillator. The center frequency is determined by the setting of the 100- μ f air capacitor (C4) and the -6 -volt bias level.

Sweep width is proportional to the amplitude of E_{ar} and is adjusted by varying this audio voltage. In Fig. 4, the rf oscillator is tuned to the center frequency of 50 mc when C4 is set to 50 μ mf, the dc bias to -6 volts and E_{ar} to zero. A 0- to 4-mc sweep is obtained when E_{ar} is varied from 0 to 1.5 volts rms.

To prevent exceeding the Varicap voltage ratings in this kind of FM oscillator, the sum of the dc, peak ac and peak rf voltages must not exceed the maximum voltage shown in the chart. Also, the dc bias must not be set so low that the sum of E_{ar} peak and E_{rf} peak will drive the Varicap into its forward, or conducting, region. In Fig. 5, these conditions are met when $E_{dc} = -6$ volts, E_{ar} does not exceed 1.5 volts rms and E_{rf} does not exceed 3 volts. While the latter is a relatively low rf tank voltage for tube type oscillators, it is reasonable for high-frequency transistor oscillators with which the Varicap frequency modulator is a natural companion.

Although the tank circuit shown in Fig. 4 has been designed for 50-mc operation, it is not imperative that this frequency be used. The same FM scheme may be used at other center frequencies by properly proportioning the L-C circuit. The lower the center frequency, the lower the sweep width obtained with a given Varicap capacitance swing, and vice versa. The transformer shown in Fig. 4 is not critical. Any audio unit whose secondary will deliver a maximum of 1.5 volts rms audio from a given af source is usable if it has a satisfactory audio response.

Automatic frequency control

The voltage-variable capacitance of

the Varicap and its temperature stability suit it for use as a simple, highly sensitive, afc device which performs better than some reactance tube circuits. The small size of an afc unit, containing a Varicap, four small capacitors, four resistors and an rf choke, lets you tuck it into a receiver with a minimum of disturbance to the set's circuitry. This should be welcome news to hi-fi enthusiasts whose FM receivers have no automatic frequency control.

Fig. 5 shows an afc circuit developed by Pacific Semiconductor engineers, which I adapted for bias from the 300-volt dc supply of an FM receiver. The photos show the complete unit ready for wiring into the receiver. Any type of Varicap may be used. The receiver's local oscillator is simply realigned to compensate for the shunting capacitance introduced by the biased Varicap C2 which functions as a frequency-controlled trimmer across the local oscillator tank.

The Varicap is referred to a dc bias of -8 volts obtained from the receiver's 300-volt supply through the voltage divider R3, R4. The afc dc voltage is obtained from one side of the discriminator. For other than 300-volt supplies, the values of R3 and R4 will not be the same as mine but must be worked out for an output of -8 volts from the particular supply voltage of the set that you are adding this afc circuit to.

The completed afc unit is built on a perforated phenolic board 2 3/8 inches long and 2 1/8 inches wide. The pigtailed of the components are passed through the holes in the board and interconnected underneath to complete the wiring. Printed circuitry may be used. The four connections to the receiver circuit are made at solder lugs mounted along the edge of the panel. The completed unit should be mounted as close as possible to the local oscillator so that the lead from the tank to C1 will be short.

(Certain silicon diodes can also be used as variable capacitors in such applications as this. In the February-March, 1958, issue of *Rectifier News*, published by the International Rectifier Corp., El Segundo, Calif., a circuit is shown for using their 3DS1 silicon diode as an afc control device for an FM tuner.—Editor)

Other applications

Other suggested uses for the Varicap include all-electronic dc-to-dc and dc-to-ac choppers, amplitude modulators, alignment sweep generators, capacitor type amplifiers (both ac and dc), ac type flip-flops, automatic amplitude control in rf oscillators, FM telemetering and elimination of the fine-tuning control in TV receivers.

In some applications, Varicaps, like capacitors, may be operated in parallel for increased capacitance and in series back to back for increased voltage-handling capability. END

the TECNETRON

Competitor to the TRANSISTOR?

Neither spacistor nor transistor, this new semiconductor triode shows great promise for the ultra-high frequencies

By E. AISBERG*

HARDLY a month passes nowadays without the announcement of some "sensational" new amplifying device. The great majority of these startling inventions, after their brief flurry in the popular and technical press, disappear into oblivion. But we believe that the *Tecnetron*, just announced in France, has a brilliant and enduring future.

The most remarkable feature of this device is that its transconductance *increases with frequency*, unlike more common semiconductor amplifiers whose performance falls off as frequency increases and becomes very low as the cutoff frequency is approached. Up to the present, frequencies in the order of 500 mc have been attained with the Tecnetron. And, as further work and research make it possible to reduce the capacitances of the contacts and other parts of the montage, there seems to be nothing to prevent it from functioning at 1,000 mc or even higher.

It has been possible—with a Tecnetron working in class A at 500 mc—to obtain a power output of 30 mw, with a dissipation of 125 mw. Since the characteristics of individual Tecnetrons are very consistent, one can

*Publisher, *Toute la Radio, Television, Radio Constructeur et Depanneur, Electronique Industrielle* (Paris).


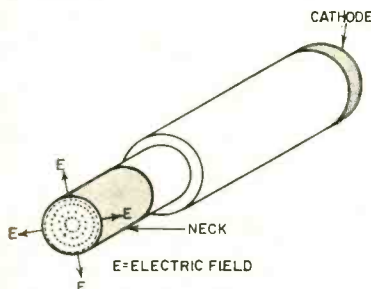
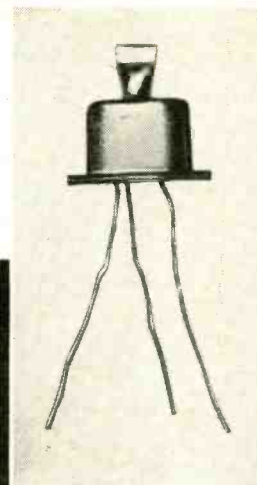


Fig. 1—Tecnetron cut to show cross-section of neck. The space charge E tends to drive the conducting area toward the center of the rod.

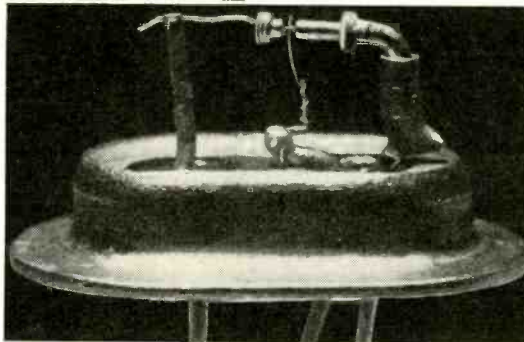

Left—Closeup of Tecnetron; above—a unit in its case.

envision the paralleling of several identical units to obtain watts—or even kilowatts—of power. This may make it possible to use Tecnetrons in applications requiring heavy currents.

In addition, the Tecnetron—though using germanium—is less sensitive to high temperatures than the transistor. It will operate at temperatures 20°C higher than will transistors. This should extend its field of applications considerably.

Neither is it a fragile experimental device that works only under laboratory conditions. Pilot production by regular industrial methods had begun on a small scale at the time of its announcement. About 700 units per month are being produced, and indications are that production could quickly be increased to the thousands.

What is the Tecnetron?

First, why is it the Tecnetron? The first syllable of the name begins as does that of its inventor, S. Tetzner. The initials CNET follow. These stand for the Centre National d'Etude des Telecommunications (National Center for the Study of Telecommunications), that great ensemble of research laboratories sponsored by France's Ministry of Posts, Telegraphs and Telephones. And of course the final syllable is the conventional one for such electronic devices.

Now, how is the Tecnetron constructed? It is a small rod of n-type germanium, 2 mm in length and 0.5 mm in diameter, provided with two contact electrodes at the ends. These must be of such material that they act solely like electrical conductors and not like transistor junctions.

The germanium rod is reduced in diameter at its center (Fig. 1) to form a "bottleneck" of very small diameter (about 30 microns). Around this neck is placed a cylinder of indium. This makes a metal-to-semiconductor bar-

rier-layer contact of excellent characteristics. The ratio of forward-to-back resistance is greater than a million to one.

A relatively high potential (50 volts or more) is applied to the electrodes at the end of the rod. These may be called the cathode and anode. The cylinder of indium might be called a grid, for it plays exactly that role. The inventor prefers to call it the "bottleneck" or simply the "neck" to indicate its method of action better. The neck is polarized negatively with respect to the cathode, and the circuit of a stage of amplification (Fig. 2) is like that of a tube triode, with the load resistance placed in the anode circuit in series with the supply voltage.

A field-effect transistor?

Is this device not essentially that which Shockley called a "field-effect transistor" which he described in the *Proceedings of the IRE* (November, 1952; Vol. 40, pp 1365-76) and with which he was not able to obtain appreciable gains above 2 mc? Like Shockley, Tetzner has turned to the field effect, discovered by Lilienfeld in 1928. Here the resemblance ends. Whereas Shockley worked with plane surfaces (or a parallelepiped), Tetzner has utilized the cylindrical configuration, transforming a linear effect to a quadratic one by applying a *radial* electric field.

What is the field effect? Our readers know of the Hall effect, due to which

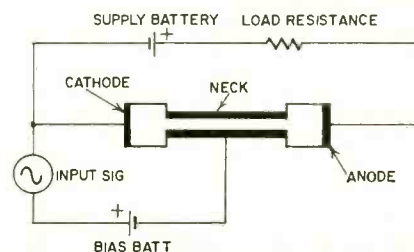


Fig. 2—Schematic of Tecnetron hookup.

charge carriers in semiconductors can be deflected from their paths under the action of a magnetic field. The Lilienfeld effect is analogous to the Hall effect, but is based on the action of the electric instead of the magnetic field. In semiconductors such as germanium, charge carriers (electrons or "holes") can be deflected from their

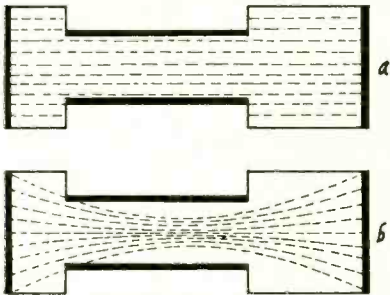


Fig. 3-a—Distribution of charge carriers (electrons) with neck unbiased; 3-b—reduction of current path caused by negative bias on neck.

paths by the action of such an electric field.

The Tecnetron action

The neck of the indium cylinder creates a concentrated electric field in the interior of the rod, depending on the charge on the cylinder. With no charge whatever, the current is propagated evenly through the whole area of the neck. As one applies a negative voltage to the cylinder, the electrons are deflected toward the center, occupying only a reduced section of the rod (Fig. 3). Thus the apparent resistance of the rod increases as the active section—through which electrons pass—decreases. This action is proportional to the square of the radius.

Note well that this is a variation in the total resistance, not in the specific resistivity which remains constant.

The voltage applied to the indium cylinder causes the neck to act as if its diameter were decreased. Thus the cathode-anode current is varied, causing the voltage across the load resistor to reproduce faithfully the changes in the voltage applied to the neck, but at a greater amplitude.

The best analogy of the Tecnetron is without doubt a flexible rubber hose through which flows a current of water. If the hose is compressed more or less by the hand, the flow decreases in the same ratio. If the hose is compressed circularly—from all sides toward the center, as by an encircling thumb and forefinger—the diminution of current will follow the square law. This centripetal constriction is an essential characteristic of the Tecnetron.

Effects of capacitance

If we analyze these actions carefully, we note that the variation in resistance is accompanied by a variation in capacitance between the part of the germanium occupied by the electrons and the indium cylinder. As the cylinder becomes more negative, it drives the electrons further from it and

toward the center of the rod, thus reducing the capacitance between the current-carrying portion of the rod and the cylinder. As the voltage becomes less negative, the electrons flow through a larger section of the germanium and the capacitance increases. The Tecnetron acts like the equivalent circuit of Fig. 4.

These variations of capacitance, which are increased by the cylindrical configuration of the device, have an effect on the current through the external circuitry similar to that which the variations of resistance have on the flow of electrons through the germanium. These two actions are synchronous and reinforce each other, thus increasing the gain. There is of course a very slight detuning effect in resonant circuits due to the instantaneous variations in capacitance produced by the signal. These are very small, since the total input capacitance is a fraction of a micromicrofarad and the detuning is proportional to the square root of the capacitance change. Practically, according to the inventor, it manifests

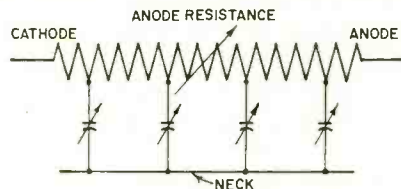


Fig. 4—The Tecnetron can be considered as a variable resistance and a distributed variable capacitance.

itself as a slight enlargement of the passband.

The capacitance effect, with its reduction of impedance as frequency increases, is one of the reasons for the high transconductance at high frequencies (Fig. 5) and the fact that the Tecnetron's figure of merit continues to increase with frequency. The figure of merit is the product of the gain by the width of the passband over which the gain is maintained at ± 3 db.

Tecnetron as amplifier

We have seen that the neck which acts as a control electrode is polarized negatively with respect to the cathode. Thus no appreciable direct current can flow in the cathode-neck circuit, because of the extension of the barrier layer into the n-type germanium.¹

Under these conditions, the input resistance is several megohms. The input capacitance is in the order of $2 \mu\text{mf}$.

The output impedance is generally higher than 1 megohm, and the load resistance thus may be chosen as high as it is practically permissible to set it; usually between 2,500 and 250,000 ohms.

If we plot the characteristics of the Tecnetron by measuring the anode current as a function of the anode-cathode voltage at various values of neck voltage, we obtain a family of curves which resemble strikingly those of a pentode

¹M. Tetzner, *Revue Générale d'Electricité*, June, 1954.

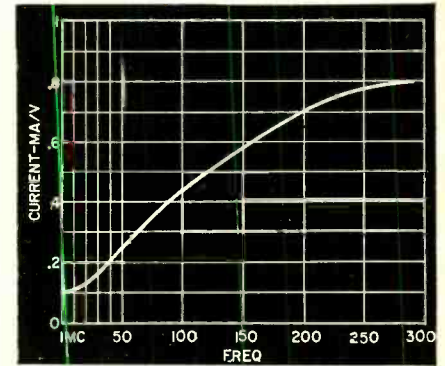


Fig. 5—Variation of the transconductance as a function of the signal frequency.

tube (Fig. 6). Which is to say, that we have here an excellent voltage amplifier. The chart shows experimental results obtained at various frequencies.

Manufacturing the Tecnetron

It was necessary to develop special technical methods to manufacture the Tecnetron. This was one of the major achievements of M. Tetzner and the CNET researchers who aided him. For part of the work, the classic procedures of transistor production could be followed. Then a whole series of new mechanical operations intervened: cutting the refined crystals into plates, then into little rods. This last operation was performed with ultrasonic cutting apparatus. The constriction for the neck was made by a procedure of electrolytic etching perfected especially for the purpose. The indium was also deposited by electrolysis, with the rod

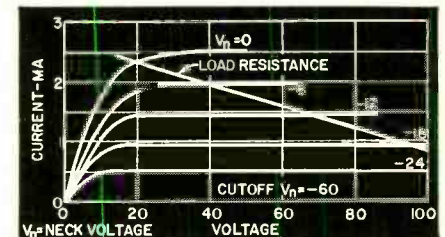



Fig. 6—These Tecnetron static characteristic curves show the variation of anode current as a function of anode voltage, for several neck voltages.

Freq. (mc)	Gain (db)	Voltage ratio	Passband (mc)	Figure of Merit
110	22	12.9	1.7	21
200	16	6.31	6	37
460	9	2.818	29	80

in continuous rotation during the process. More conventional techniques could be used in applying the terminal (cathode and anode) contacts.

Up to the present, procedures already developed permit manufacture on a large scale. Research is continuing, however, and the next step is the creation of a power Tecnetron and another model especially for ultra-high frequencies. Special arrangements which will permit continuing still further up the frequency spectrum are also under study. And, as always, as the area of actual accomplishment is increased, the greater become the prospects of future progress.


END

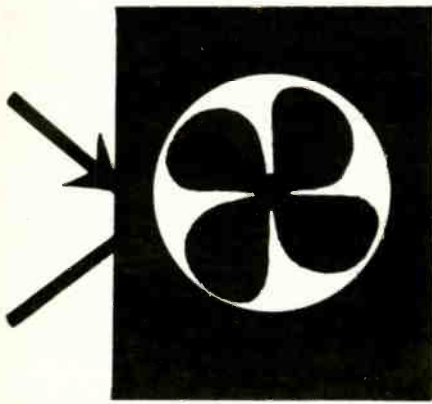


Construct a temperature-sensing unit to operate your fan or air-conditioner automatically

Train your fan with TRANSISTORS

By JAMES A. McROBERTS

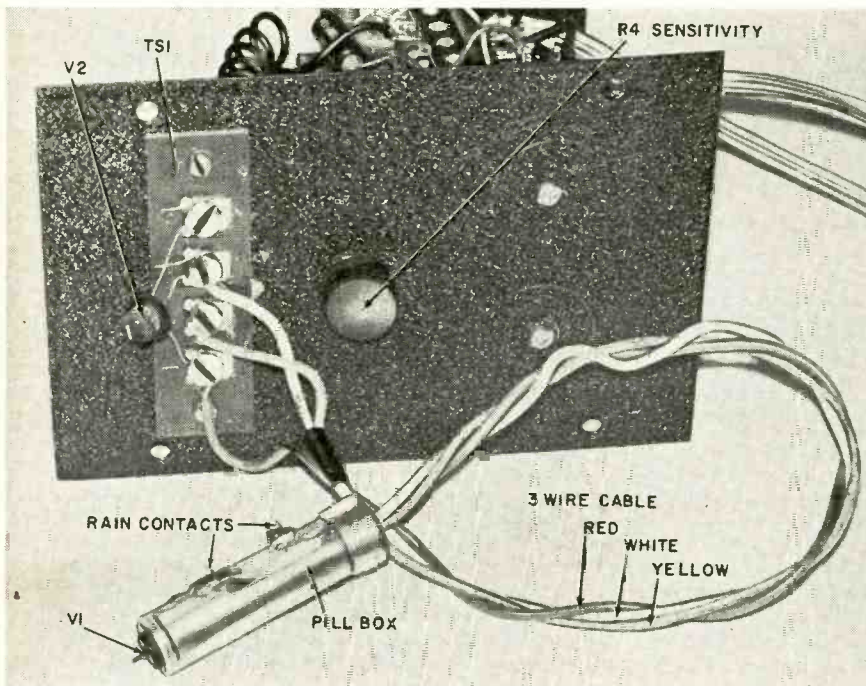

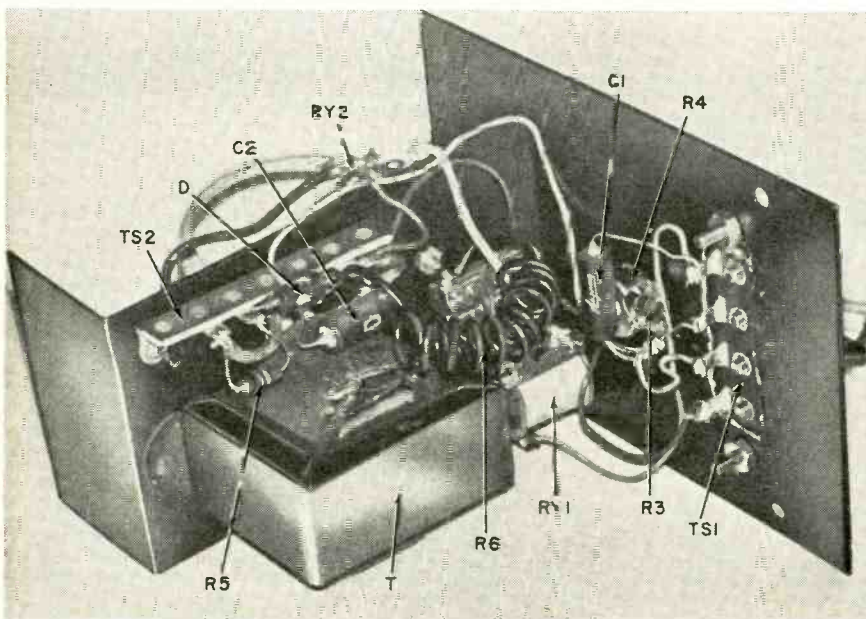The control unit with the outside sensor connected.



Inside the main control unit. Handle the chassis carefully or it may break loose from the front panel.

LOW-COST transistors can perform heat-sensing duties almost as well as their more conventional electronic jobs. Two are employed here in a device to sense very small temperature differences. It checks to see if it is cooler outdoors than inside. If so, it turns on a fan. If not, the fan stays off. If it is raining, another brain cell prevents the fan from going on, so rain will not be pulled into the house when the owner is away fishing.

The device can also be set to turn on an air conditioner whenever the difference between inside and outside temperatures exceeds a certain amount.


The device is simple and easy to construct, with the added advantage of being easy on the pocketbook.

Circuit description

Fig. 1 helps explain these sensing, memory and control functions. With proper circuit components, transistors V1 and V2 behave like thermal resistances—their collector currents increase as their temperature rises. V2 is mounted on the control-unit panel to sense inside temperature. Its collector current passes through the coil of relay RY1. As inside temperature rises, the increased current closes the relay.

Outside sensing transistor V1 counterbalances this action of V2 for similar increases or decreases of temperature. For example, as V1 becomes warmer, its collector current also rises. This current passes through R3 and R4, creating a voltage drop which makes V2's base less negative. Consequently, V2's collector current decreases. As a result, the relay's coil current remains relatively steady during even heating or cooling of both transistors.

A cooling fan is effective only when the outside temperature is lower than the inside, as at night. When the inside temperature is lower, V1 (outside sensor) draws more collector current relative to V2 (inside sensor), regardless of the actual value of the current. There is proportionately a greater voltage drop across its load, R3 and R4. V2's base voltage and collector current are lowered. Hence, current through relay RY1 is less than the

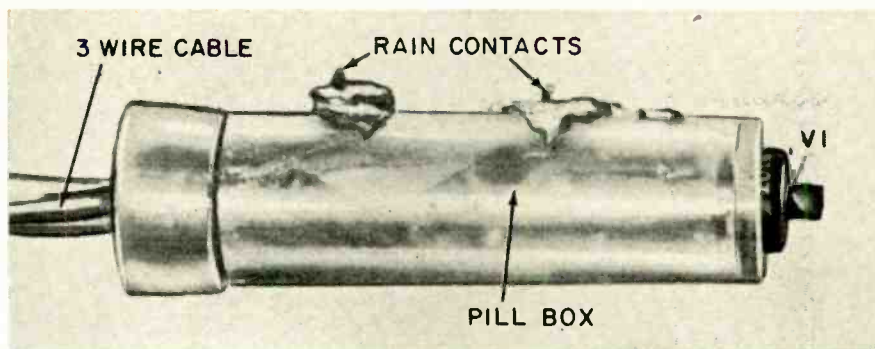

Closeup of the sensor. Keep rain contacts facing up.

even-temperature value for that particular temperature range. The fan remains off.

As outside temperature falls, V1 draws proportionately less current and relay RY1's current rises. Eventually RY1 is energized and the fan is turned on. Due to a difference in the turn-on and drop-out points of the relay, the fan remains on until the outside temperature rises above the inside. If you wish, you can install a switch in the power supply to break the circuit and release the relay. Only a momentary off-on is wanted so the transistors do not cool. This added feature may not be necessary since outside and inside temperatures are both rather low at this time, and a slight rise in outside temperature shuts off the fan. A thermostat may be included to shut off the fan at some comparatively low temperature. Install its contacts in the control unit's power supply line.

If it is raining, the fan sucks in rain unless its intake is well sheltered. A house full of water could result. An auxiliary rain lockout circuit supplies more base current to transistor V1 when water is present across the rain contacts (see photos). This decreases relay coil current. When the space between the rain contacts is wet (water, not just moisture from dew), the relay coil's voltage is about 2 volts less than otherwise. The fan cannot go on. Omit this circuit if the rain lockout feature is not wanted.

The power supply is conventional except that the center tap of the transformer supplies ac through a 2-ohm resistor to the auxiliary 6-volt relay.

Sensitivity controls

If other than even temperature is desired, the SENSITIVITY CONTROL (R4) is adjusted for the desired difference of temperature for turn-on or turn-off. However, V1's base resistor must be altered if the differential exceeds about 10° F. Less than this value does not require any change, just a new setting of R4. Fig. 2 shows the modification for a large temperature differential. R1 is split into two parts, a protective resistor R1-a and an adjustable element R1-b. R1-b is set for uniform relay coil current (RY1) or voltage across

it (monitor with high-resistance voltmeter) with ambient temperature changes. Both transistors are kept at the same temperature. Be careful in such work—the heat from a hand or a nearby lamp will upset the compensation. If either transistor is handled, allow about 3 minutes for it to cool before making any further adjustment.

Rain lockout sensitivity can be doctored too by adding a potentiometer (R3) in series with a protective resistor (R4) as shown in Fig. 2. It can be made sensitive to the slightest amount of moisture by lowering the resistance of potentiometer R2-b. Added pots may be panel-mounted or left inside the control unit as factory adjustments.

Construction hints

The control unit and its power supply are housed in a 4 x 5 x 6-inch metal utility cabinet with the built-in chassis. The photos give an idea of parts placement.

A three-wire cable in the standard fan model connects the external sensor

to screw terminals mounted on the front panel of the control unit.

In practice a long three-wire cable is employed. The tiny amount of current flow permits lengths up to 1,000 feet without appreciable voltage drops.

In this model, transistor V1 is mounted on the end of a pillbox. (You can get one at the drug store.) A hole is drilled in the end to permit the transistor to pass through. Transistor leads are clipped for mounting in a socket, thereby simplifying installation. The rain contacts are small metal tabs sealed in place with Duco cement.

This cement also makes a watertight seal between the transistor's case and the pillbox. A hole in the pillbox cover admits the cable, which is also sealed off. The entire assembly is made up prior to pushing into the pillbox for easy installation.

I mounted the pillbox with a small pipe strap on a north window. Use a shield over the outside sensor to keep sunshine off it. A soap tray makes a good shield. The rain contacts are mounted uppermost so water will run off them for quick recovery of sensitivity after a rain.

Mounting parts in the control unit is not critical and the parts themselves may be used as templates in laying out chassis holes. Cut the rectangular hole to admit TS1's lugs first. Use care and avoid breaking the built-in chassis or additional work is required to secure it to the cabinet's front panel again—this happened to me.

Observe the polarity of capacitors C1 and C2 as well as of the diode-rectifier D. When soldering these parts, use a heat sink on the lead to the component to prevent damage. Use a hot iron and solder rapidly. Allow to cool prior to removing the heat sink.

The 6-volt auxiliary relay is intended

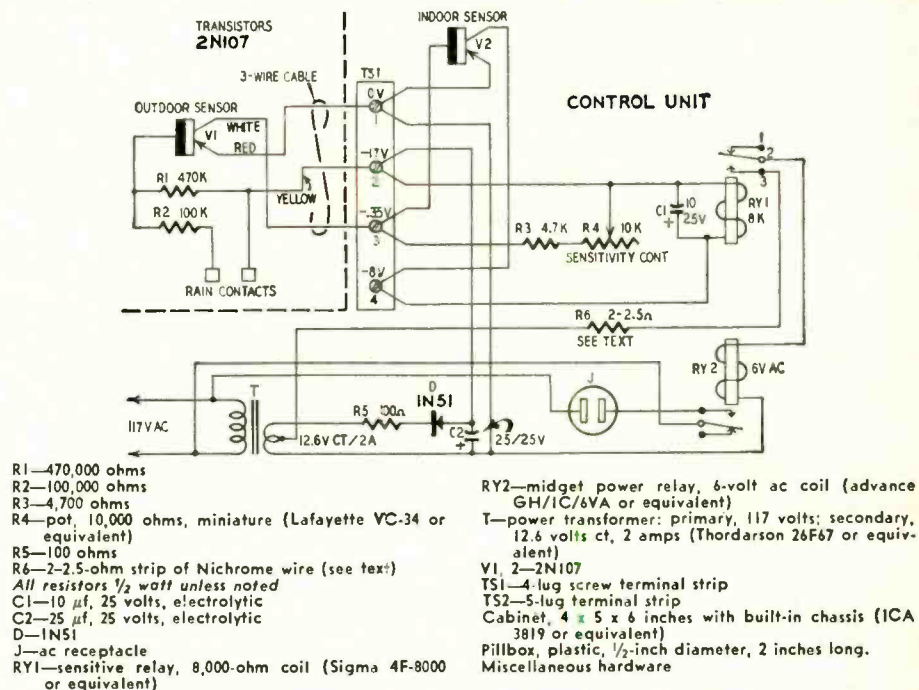


Fig. 1—Complete circuit of the sensing and control units. They are connected by a three-wire cable.

ELECTRONICS

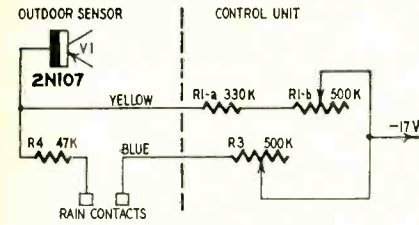


Fig. 2—Modifying the control system to handle air conditioners.

for intermittent duty only. A length of Nichrome heater wire (R6) is cut to 2 ohms (use an ohmmeter to measure). It is straightened out and slipped into a length of spaghetti (see photos). This added resistance permits continuous duty without overheating the relay. The Nichrome wire is readily obtained at neighborhood hardware stores.

Final adjustments

Test and adjust the unit on the bench before putting it into use. A lamp may be plugged into the outlet receptacle J for this check. (J is an ordinary cube tap for smaller fans. For heavy power fans leave it out and wire direct via BX cable.) The external sensor unit may be used with a short cable length for testing and later spliced at the window.

Hook up the external sensor and mount V2 as shown in the photos. Turn on the power. Rotate the SENSITIVITY CONTROL. The lamp should light and a relay click heard at some setting of this control. This is the turn-on point. A little more counterclockwise rotation will extinguish the light and the relays will click off at the same time.

Now let the transistors warm up from current passage through them. Keep the SENSITIVITY CONTROL at about the drop-out point. Leave the unit on overnight to age the transistors and the diode rectifier as well as to form capacitors C1 and C2. The relay pull-in and drop-out points will be relatively stable thereafter. The unit may now be connected for steady operation.

The sensitivity setting for even inside and outside temperature turn-on is that obtained on the bench test. A little more counterclockwise (toward turn-off) is the setting for a slightly lower outside temperature turn-on. This is the setting usually used.

Air-conditioner control

For controlling an air conditioner, the object is the opposite of fan cooling. We wish to maintain a temperature differential between inside and outside temperatures. Consequently we make a minor change in the relay contact wiring. On Fig. 1 the wire to contact 3 of relay RY1 is connected to contact 1.

Sensitivity is adjusted for the required temperature differential in this type of service.

As an alternative to the change in relay wiring, V1 and V2 may be interchanged, making V1 the inside sensor. Rain lockout, if still wanted, would be extended outside by a pair of wires. END

TRANSISTOR DICTIONARY

By H. BARR

COMPILED from several sources and presented here are over 150 terms unique to the transistor field. General radio-electronic-television terms that are not directly related to transistors are excluded, as well as specialized scientific terms we are not likely to run across. Many of the terms defined have several meanings. Only the particular meaning appropriate to the transistor field is given. Also, many of the words have various spellings and no attempt has been made to list all possible variations.

—A—

Acceptor Impurity used to produce p-type semiconductor.
Alloy-diffused transistor Transistor in which the base is diffused in, and the emitter alloyed.
Alloy process Process for making junctions by melting an acceptor or donor on the surface of the semiconductor and letting it refreeze.
Alloy transistor Transistor made by the alloy process.
Alpha Emitter-to-collector current gain. For a junction transistor alpha is less than one.
Alpha-cutoff frequency The high frequency at which the value of alpha is down to 0.7 of its low-frequency value.

—B—

Back bias See *reverse bias*.
Barrier See *junction*.
Barrier capacitance See *depletion-layer capacitance*.
Barrier layer, barrier region See *depletion layer*.
Barrier-layer capacitance See *depletion-layer capacitance*.
Base Electrode on a transistor.
Base resistance Resistance in series with the base lead in the common T equivalent circuit of a transistor.
Base ring Ohmic contact to the base region of power transistors, made in the shape of a ring.
Beta Base-to-collector current gain of a transistor.
Bonded-barrier transistor Transistor made by alloying when the alloying material is on the end of a wire.
Boundary, p-n See *p-n junction*.
Button Piece of metal for alloying onto the base wafer in making alloy transistors.

—C—

Carriers Particles which carry current, specifically either electrons or holes.
Collector Electrode on a transistor.
Collector capacitance Depletion-layer capacitance associated with the collector junction.

- Collector efficiency** Ratio of useful power output to final stage power supply power input, usually expressed in percentage.
- Collector family** Set of characteristic curves for a transistor, in which collector current and collector voltage are used as variables.
- Collector junction** On junction transistors, the junction between the collector and the base.
- Collector resistance** Resistance in series with the collector lead in the common-T equivalent circuit of a transistor.
- Common base** Configuration for amplifiers, in which the base is common to both input and output circuits.
- Common collector** Configuration for amplifiers, in which the collector is common to both input and output circuits.
- Common emitter** Configuration for amplifiers, in which the emitter is common to both input and output circuits.
- Complementary symmetry** Any of several types of circuits using both p-n-p and n-p-n transistors in a symmetrical arrangement.
- Conductivity** A property of a semiconductor expressing how easily current may flow through it; the reciprocal of resistivity.
- Configuration** Type of amplifier circuit, depending on which electrode is common to input and output; for example, common-emitter configuration.
- Coupling** Method of passing the signal from one stage to another; for example, *capacitor coupling*, *transformer coupling*.
- Crossover distortion** Harsh type of distortion produced by incorrectly biased class-B amplifiers.
- Crystal** Regular array of atoms in a solid; for example, *single-crystal germanium*.
- Current amplification, current gain** Ratio of output to input current.
- Cutoff current** Collector current with no emitter current and normal collector-to-base bias.
- Czoehralski technique** Method of growing large single crystals by pulling them from a molten state; usually used to grow germanium and silicon single crystals.
- D—
- Depletion layer** Region near a junction without current carriers, on reverse bias.
- Depletion-layer capacitance** Capacitance of the depletion layer, which is a function of reverse voltage.
- Depletion-layer transistor** Any of several types of transistors which rely directly on motion of carriers through depletion layers for their operation; for example, spacistor.
- Derating** Reducing ratings on a transistor, especially the maximum power dissipation rating at higher temperatures.
- Diamond lattice** The crystal structure of both germanium and silicon as well as diamond.
- Diffused-base transistor** Any of several types of drift transistors in which the base is diffused in.
- Diffused emitter-collector transistor, diffused E-C transistor** Transistor in which both the emitter and collector are made by the diffusion process.
- Diffusion** Movement of carriers from heavily populated regions to regions without as many carriers, similar to slow diffusion of ink through a still glass of water; also similar movement of donors and acceptors at high temperatures.
- Diffusion process** Method for making junctions by diffusing acceptors or donors into a semiconductor at a high temperature.
- Diffusion transistor** Transistor relying on diffusion for carrying current; for example, ordinary junction transistor.
- Diode** Two-terminal semiconductor device that rectifies.
- Dissipation** Loss of electrical energy into heat.
- Donor** Impurity used to produce n-type semiconductor.
- Doping** Adding impurities to change the resistivity of semiconductors and to make n-type or p-type.
- Dot** See *button*.
- Double-base diode** See *Unijunction transistor*.
- Double-diffused transistor** Junction transistor in which both the emitter and the base are diffused in.
- Drain** Electrode on a field-effect transistor.
- Drift** Movement of carriers because of applied voltage.
- Drift transistor** Transistor relying on drift for carrying current; compare diffusion transistor.
- E—
- Electroforming** Process of creating p-n junctions by passing current through point contacts.
- Electrons** Negatively charged current carriers.
- Emitter** Electrode on a transistor.
- Emitter junction** On junction transistors, the junction between the emitter and the base.
- Emitter resistance** Resistance in series with the emitter lead in the common-T equivalent circuit of a transistor.
- Equivalent circuit** A circuit which approximates the actual transistor under some conditions.
- F—
- Field-effect transistor** Type of transistor relying on movement of a depletion layer to vary the conduction between two electrodes, the source and the drain.
- Floating junction** Junction through which no net current flows.
- Forward bias** Large-current bias as applied to a diode; opposite to reverse bias.
- Fused-junction transistor** See *alloy transistor*.
- Fused transistor** See *alloy transistor*.
- G—
- Gate** Electrode on a field-effect transistor.
- Germanium** Common semiconductor material, usually used for making transistors.
- Grounded base** See *common base*.
- Grounded collector** See *common collector*.
- Grounded emitter** See *common emitter*.
- Grown-diffused transistor** Junction transistor with junctions formed by diffusion of impurities near a grown junction.
- Grown-junction transistor** Junction transistor with junctions formed by adding impurities to the melt while the crystal was being grown.
- H—
- Hall effect** Transverse voltage produced by current travelling at right angles to a magnetic field; especially prominent in semiconductors.
- Header** Part of a transistor which the leads pass through to get outside.
- Heat sink** Something that will absorb and dissipate a large amount of heat without getting hotter.
- Holes** Positively charged current carriers in semiconductors.
- Hook transistor** Four-layer transistor with a built-in hook amplifier for a collector.
- h-parameters** Four commonly used parameters for specifying the small-signal behavior of a transistor.
- Hybrid parameters** See *h-parameters*.
- I—
- Impurity** Small addition to a semiconductor, especially a donor or an acceptor.
- Injector** Electrode on a spacistor.
- Intrinsic-region transistor** Four-layer transistor with an intrinsic region between the base and the collector.
- Intrinsic semiconductor** Neither n-type nor p-type, containing roughly equal numbers of electrons and holes.
- i-type** Intrinsic semiconductor
- J—
- Junction** Region separating two different types of semiconductor, especially p-n junction.
- Junction diode** A diode which uses a junction to get a rectifying characteristic.
- Junction transistor** Most common type of transistor, using two junctions with the base region between them.
- L—
- Large-signal analysis** Consideration of large excursions from the no-signal bias, so that the nonlinear, switching properties of the transistor are important.
- Leakage current** That portion of cutoff current due to surface effects.
- M—
- MADT transistors** Micro-Alloy Diffused-base Transistors.
- Majority carriers** Whichever type is more plentiful, i.e. electrons in n-type and holes in p-type.
- Meltback process** Method of making

(Continued on page 82)


here

we

grow

again

With this issue we introduce our new building—over 140,000 sq. ft. of modern plant equipment under one roof, the largest in the nation devoted to direct mail selling of electronic kits. To you, in the field, goes the credit for the tremendous growth of the electronic industry over recent years. Your imagination, courage and resourcefulness have moved America into the electronic age at a breathtaking pace. A pioneer in "do-it-yourself" electronic kits, Heath Co. has always endeavored to stay out in front. As a result we have grown too—from one small building to a point where we occupied seven buildings in the local area. Our new plant is your assurance of more and better HEATHKITS to come!

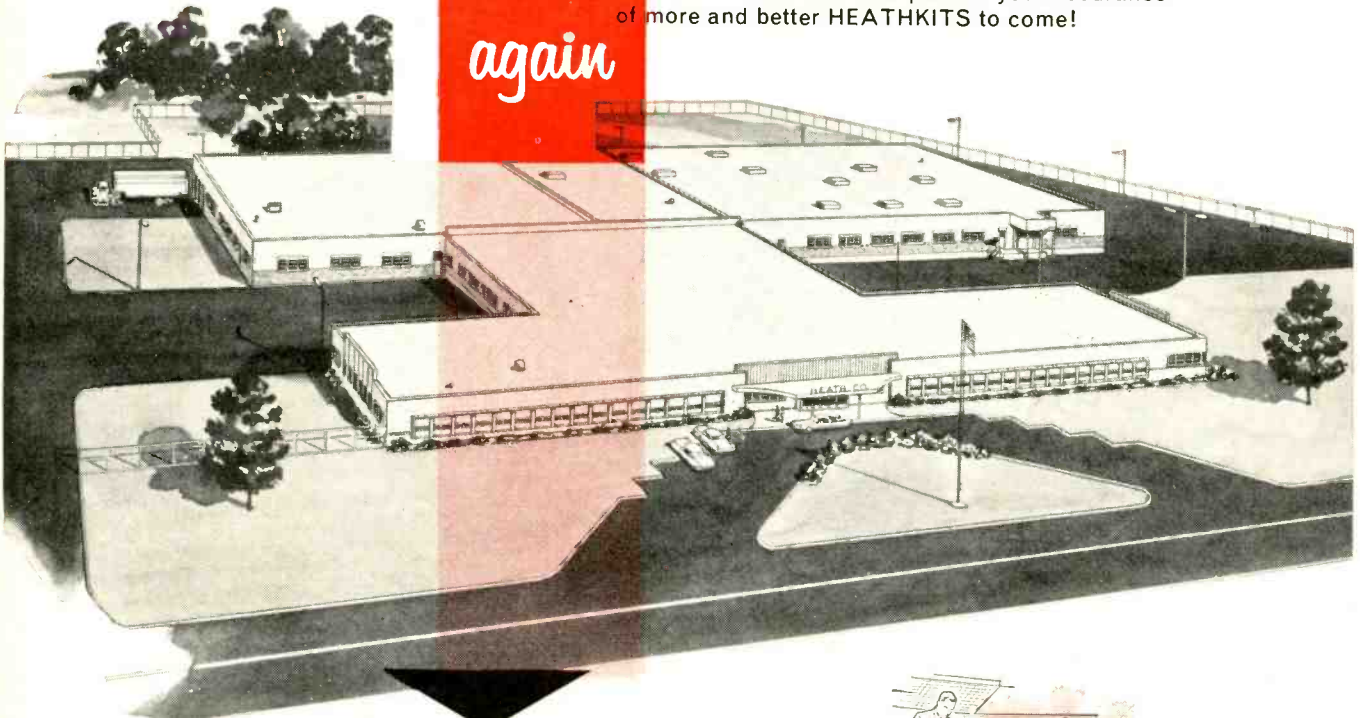

here's what it means to you



Faster, more efficient handling of orders to speed HEATHKITS to your doorstep.



More for your purchasing dollar through increased efficiency and lower handling costs.



Faster research and development projects bringing you the latest electronic equipment in step with ever-expanding fields.



Better and faster service facilities to help you with any problems and questions you may have.

 a subsidiary of Daystrom, Inc.

HEATHKIT  **HEATH COMPANY, Benton Harbor 20, Mich.**

TIME PAYMENTS . . .

The Heath Time Payment Plan was designed for your convenience. Now, you can order the kits of your choice, and pay for them in small monthly installments. Write for full details.

HEATHKIT EXTRA PERFORMANCE 70-WATT AMPLIFIER KIT

For really high performance, with plenty of reserve power, the W-6M is a natural. The full 70-watts output will seldom, if ever, be required. However, this reserve insures distortion-less sound on power peaks. The W-6M will loaf along at normal listening levels and yet is always ready to extend itself when program material demands it, without the least amount of strain. The output circuit employs 6550 tubes with a special-design Peerless output transformer for maximum stability at all power levels. A quick-change plug selects 4, 8 and 16 ohms or 70-volt output and the correct feedback resistance. A variable damping control is also provided for optimum performance with any speaker system. Extremely good power supply regulation is possible through the use of a heavy-duty transformer along with silicon-diode rectifiers, which are noted for their very long life, and yet are smaller than a house fuse. Frequency response at 1 watt is ± 1 db from 5 cps to 80 kc with controlled hf roll-off above 100 kc. At 70 watts output harmonic distortion is below 2%, 20 to 20,000 cps and IM distortion below 1%, 60 and 6,000 cps. Hum and noise 88 db below full output. In addition to high performance, its fine appearance makes it a pleasure to display in your living room. Proper layout of chassis insures ease of assembly by eliminating those cramped and difficult places to get at. Clear instructions—and top-quality components. Get started now and make this amplifier the heart of your hi-fi system. Shipped express only. Shpg. Wt. 50 lbs.

MODEL W-6: Consists of W-6M kit, plus WA-P2 preamplifier. Express only. Shpg. Wt. 59 lbs. \$129.70

MODEL W-6M

\$109⁹⁵

HEATHKIT HIGH FIDELITY FM TUNER KIT

This tuner can bring you a rich store of FM programming, your least expensive source of high fidelity material. It covers the complete FM band from 88 to 108 mc. Stabilized, temperature-compensated oscillator assures negligible drift after initial warmup. Features broadbanded circuits for full fidelity, and better than 10 uv sensitivity for 20 db of quieting, to pull in stations with clarity and full volume. Employs a high gain, cascode RF amplifier, and has AGC. A ratio detector provides high-efficiency demodulation without sacrificing hi-fi performance. IF and ratio transformers are prealigned, as is the front end tuning unit. Special alignment equipment is not necessary. Edge-lighted glass dial for easy tuning. Here is FM for your home at a price you can afford. Shpg. Wt. 8 lbs.

MODEL FM-3A

\$25⁹⁵

(with cabinet)

HEATHKIT BROADBAND AM TUNER KIT

This AM tuner was designed especially for high fidelity applications. It incorporates a special detector using crystal diodes, and the IF circuits feature broad band-width, to insure low signal distortion. Audio response is ± 1 db from 20 cps to 9 kc, with 5 db of preemphasis at 10 kc to compensate for station rolloff. Sensitivity and selectivity are excellent, and tuner covers complete broadcast band from

550 to 1600 kc. Quiet performance is assured by 6 db signal-to-noise ratio at 2.5 UV. Prealigned RF and IF coils eliminate the need for special alignment equipment. Incorporates AVC, two outputs, two antenna inputs, and built-in power supply. Edge-lighted glass slide-rule dial for easy tuning. Your "best buy" in an AM tuner. Shpg. Wt. 8 lbs.

MODEL BC-1A

\$25⁹⁵

(with cabinet)

HEATHKIT MASTER CONTROL PREAMPLIFIER KIT

Designed for use with any of the Williamson-type amplifiers, the WA-P2 has five switch-selected inputs, each having its own level control to eliminate blasting or fading while switching through the various inputs, plus a tape recorder output. A hum control allows setting for minimum hum level. Frequency response is within $\pm 1\frac{1}{2}$ db from 15 to 35,000 cps. Equalization provided for LP, RIAA, AES, and early 78's. Separate bass and treble controls. Low impedance cathode follower output circuit. All components were specially selected for their high quality. Includes many features which will eventually be desired. Shpg. Wt. 7 lbs.

MODEL WA-P2

\$19⁷⁵

(with cabinet)

An amplifier you will be proud to own

70-WATT AMPLIFIER

Selects and controls sound to your taste

AM-TUNER


FM-TUNER

PREAMPLIFIER



ADVANCED-DESIGN
25-WATT AMPLIFIER

*Top performance
in its
power class!*

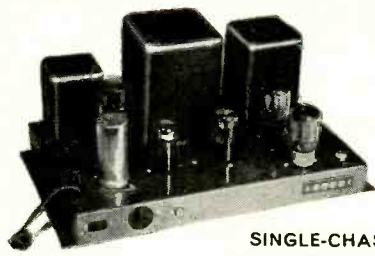

SINGLE-CHASSIS
20-WATT AMPLIFIER

*Hi-Fi equipment
for your listening
pleasure!*



DUAL-CHASSIS
20-WATT AMPLIFIER



GENERAL-PURPOSE
20-WATT AMPLIFIER

HEATHKIT ADVANCED-DESIGN 25-WATT HIGH FIDELITY AMPLIFIER KIT

Designed especially to satisfy critical audio requirements, the W-5M incorporates the extra features needed to complement the finest in program sources and speaker systems. Faithful sound reproduction is assured with a frequency response of ± 1 db from 5 to 160,000 cps at 1 watt, and harmonic distortion is less than 1% at 25 watts, with IM distortion less than 1% at 20 watts. Hum and noise are a full 99 db below rated output, assuring quiet, hum-free operation. Output taps are 4, 8 and 16 ohms. Exclusive Heathkit features include the "tweeter saver", and the "bas-bal" balancing circuit, requiring only a voltmeter for indication. Years of reliable service are guaranteed through the use of conservatively rated, high quality components. KT66 tubes and Peerless output transformer are typical. Shipped express only. Shpg. Wt. 31 lbs.

MODEL W-5: Consists of W-5M kit above plus model WA-P2 preamplifier. Express only. Shpg. Wt. 38 lbs. \$79.50

MODEL W-5M

\$59⁷⁵

HEATHKIT SINGLE-CHASSIS 20-WATT HIGH FIDELITY AMPLIFIER KIT

The model W4-AM Williamson-type amplifier will amaze you with its outstanding performance. A true Williamson circuit, featuring extended frequency response, low distortion, and low hum levels, this amplifier can provide you with many hours of listening enjoyment with only a minimum investment compared to other units on the market. 5881 tubes and a special Chicago-standard output transformer are employed to give you full fidelity at minimum cost. Frequency response extending from 10 cps to 100 kc within ± 1 db at 1 watt assures you of full coverage of the audio range, and clean clear sound amplification takes place in circuits that hold harmonic distortion at 1.5% and IM distortion below 2.7% at full 20 watt output. Hum and noise are 95 db below full output. Taps on the output transformer are at 4, 8 or 16 ohms. Shipped express only. Shpg. Wt. 28 lbs.

MODEL W-4A: Consists of W-4AM kit above, plus model WA-P2 preamplifier. Express only. Shpg. Wt. 35 lbs. \$59.50

MODEL W-4AM

\$39⁷⁵

HEATHKIT DUAL-CHASSIS 20-WATT HIGH FIDELITY AMPLIFIER KIT

The model W3-AM is a Williamson-type amplifier built on two separate chassis. The power supply is on one chassis, and the amplifier stages are on the other chassis. Using two separate chassis provides additional flexibility in installation. Features include the famous acrosound model TO-300 "ultralinear" output transformer and 5881 tubes for broad frequency response, low distortion, and low hum level. The result is exceptionally fine overall tone quality. Frequency response is ± 1 db from 6 cps to 150 kc at 1 watt. Harmonic distortion is less than 1% and IM distortion is less than 1.3% at 20 watts. Hum and noise are 88 db below 20 watts. Designed to match the speaker system of your choice, with taps for 4, 8 or 16 ohms impedance. A very popular high fidelity unit employing top quality components throughout. Shipped express only. Shpg. Wt. 29 lbs.

MODEL W-3A: Consists of W-3AM kit above plus model WA-P2 preamplifier. Express only. Shpg. Wt. 37 lbs. \$69.50

MODEL W-3AM

\$49⁷⁵

Heathkits...

By DAYSTROM

*bring you the lasting satisfaction
of personal accomplishment*

HEATHKIT GENERAL-PURPOSE 20-WATT HIGH FIDELITY AMPLIFIER KIT

The model A-9C will provide you with high quality sound at low cost. Features a built-in preamplifier with four separate inputs, and individual volume, bass and treble controls. Frequency response covers 20 to 20,000 cps within ± 1 db. Total harmonic distortion is less than 1% at 3 db below rated output. Push-pull 6L6 tubes are used, with output transformer tapped at 4, 8, 16 and 500 ohms. A true hi-fi unit using high-quality components throughout, including heavy-duty "potted" transformers.

Shpg. Wt. 23 lbs.

MODEL A-9C

\$35⁵⁰

**HEATHKIT "BASIC RANGE"
HI-FI SPEAKER SYSTEM KIT**

The extremely popular Heathkit model SS-1 Speaker System provides amazing high fidelity performance for its size. Features two high-quality Jensen speakers, an 8" mid-range woofer and compression-type tweeter with flared horn. Covers from 50 to 12,000 CPS within ± 5 db, in a special-design ducted-port, bass reflex enclosure. Impedance is 16 ohms. Cabinet measures 11½" H x 23" W x 11¼" D. Constructed of veneer-surfaced plywood, ½" thick, suitable for light or dark finish. All wood parts are precut and predrilled for easy, quick assembly. Shpg. Wt. 30 lbs.

MODEL SS-1
\$399⁹⁵

**HEATHKIT "RANGE EXTENDING"
HI-FI SPEAKER SYSTEM KIT**

Extends the range of the SS-1 to ± 5 db from 35 to 16,000 CPS. Uses 15" woofer and super-tweeter both by Jensen. Kit includes crossover circuit. Impedance is 16 ohms and power rating is 35 watts. Measures 29" H x 23" W x 17½" D. Constructed of veneer-surfaced plywood ¾" thick. Easy to build! Shpg. Wt. 80 lbs.

MODEL SS-1B
\$999⁹⁵

**HEATHKIT "LEGATO"
HIGH FIDELITY SPEAKER SYSTEM KIT**

The quality of the Legato, in terms of the engineering that went into the initial design, and in terms of the materials used in its construction, is matched in only the most expensive speaker systems available today. The listening experience it provides approaches the ultimate in esthetic satisfaction. Two 15" theater-type Altec Lansing speakers cover 25 to 500 CPS, and an Altec Lansing high-frequency driver with sectoral horn covers 500 to 20,000 CPS. A precise amount of phase shift in the crossover network brings the high frequency channel into phase with the low frequency channel to eliminate peaks or valleys at the crossover point, by equalizing the acoustical centers of the speakers. The enclosure is a modified infinite baffle type, especially designed for these speakers. Cabinet is constructed of veneer-surfaced plywood, ¾" thick, precut and predrilled for easy assembly. Frequency response 25 to 20,000 CPS. Power rating, 50 watts program material. Impedance is 16 ohms. Cabinet dimensions 41" L x 22¼" D x 34" H.

Choice of two beautiful cabinets. Model HH-1-C in imported white birch for light finishes, and HH-1-CM in African mahogany for dark finishes. Shpg. Wt. 195 lbs.

MODEL HH-1-C
MODEL HH-1-CM
\$2999⁹⁵
EACH

Heathkits...

By DAYSTROM

*let you save up to ½
or more on all types
of electronic equipment.*

HEATHKIT SINE-SQUARE GENERATOR


The new AG-10 provides high quality, sine and square waves over a wide range, for countless applications. Some of these are; radio and TV repair work, checking scope performance, as a variable trigger source for telemetering and pulse work, and checking audio, video and hi-fi amplifier response. Frequency response is ± 1.5 db from 20 CPS to 1 MC on both sine and square waves, with less than .25% sine wave distortion, 20 to 20,000 CPS. Sine wave output impedance 600 ohms, square wave output impedance 50 ohms, (except on 10v ranges). Square wave rise time less than .15 μ sec. Five-position band switch—continuously variable tuning—shielded oscillator circuit—separate step and variable output attenuators in ranges of 10, 1, and .1 volts for both sine and square wave, with extra range of .01 volt on sine wave. Both sine and square wave can be used at the same time without affecting either wave form. Power supply uses silicon-diode rectifiers. Shpg. Wt. 12 lbs.

MODEL AG-10
\$499⁹⁵

HEATHKIT AUDIO ANALYZER KIT

The AA-1 is actually three instruments in one compact package. It combines the functions of an AC VTVM, an audio wattmeter, and an intermodulation analyzer. Input and output terminals are combined, and high and low frequency oscillators are built in. VTVM ranges are 0-.01, .03, .1, .3, 1, 3, 10, 30, 100 and 300 volts (RMS). Wattmeter ranges are .15 mw, 1.5 mw, 15 mw, 150 mw, 1.5 w, 15 w and 150 w. IM scales are 1%, 3%, 10%, 30% and 100%. Provides internal load resistors of 4, 8, 16 or 600 ohms. A tremendous dollar value. Shpg. Wt. 13 lbs.

MODEL AA-1
\$499⁹⁵

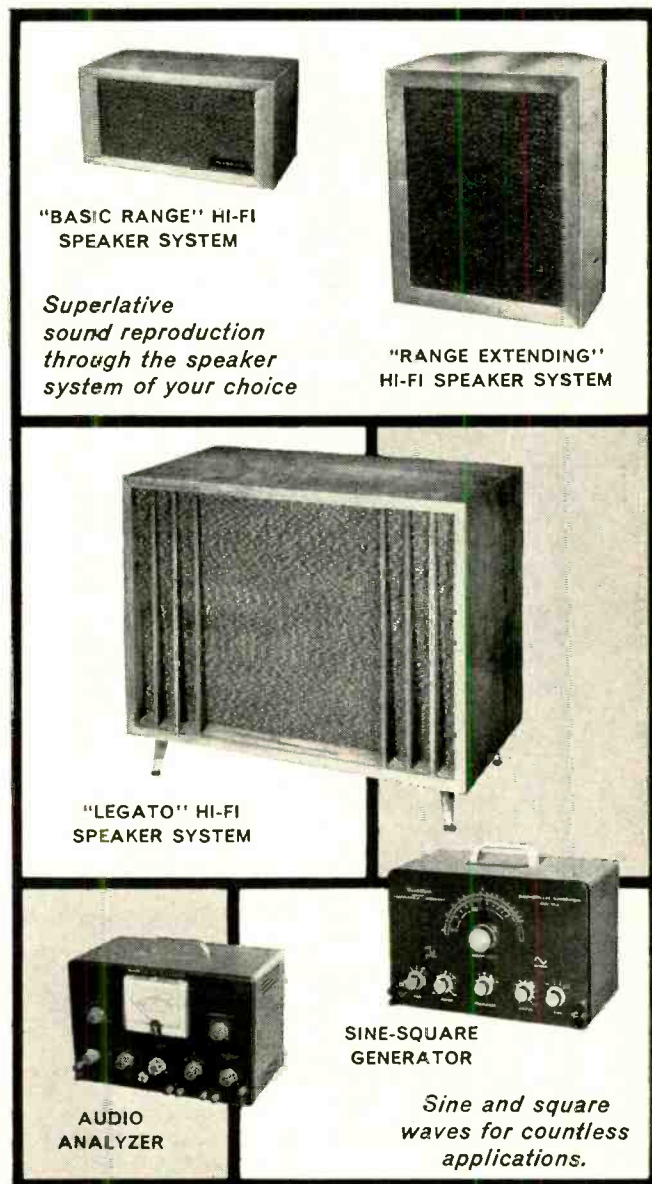

"BASIC RANGE" HI-FI
SPEAKER SYSTEM

*Superlative
sound reproduction
through the speaker
system of your choice*

"RANGE EXTENDING"
HI-FI SPEAKER SYSTEM

"LEGATO" HI-FI
SPEAKER SYSTEM

SINE-SQUARE
GENERATOR

AUDIO
ANALYZER

*Sine and square
waves for countless
applications.*

HEATH COMPANY A Subsidiary of Daystrom, Inc. BENTON HARBOR 20, MICH.



Audio equipment for your hi-fi testing

GENERAL PURPOSE" SCOPE



AUDIO WATTMETER



AUDIO GENERATOR



HARMONIC DISTORTION METER



AUDIO VTVM

HEATHKIT "GENERAL PURPOSE" 5" OSCILLOSCOPE KIT

The model OM-2 Oscilloscope is especially popular with part-time service technicians, students, and high fidelity enthusiasts. It features good vertical frequency response ± 3 db from 4 cps to over 1.2 mc. A full five-inch crt, and sweep generator operation from 20 cps to over 150 kc. Stability is excellent and calibrated grid screen allows precise signal observation. Extra features include external or internal sweep and sync, 1-volt peak-to-peak calibrating reference, 3-position step-attenuated input, adjustable spot shape control, push-pull horizontal and vertical amplifiers, and modern etched-metal circuits. Easy to build and a pleasure to use. Ideal for use with other audio equipment for checking amplifiers. Shpg. Wt. 21 lbs.

MODEL OM-2
\$39.95

HEATHKIT AUDIO WATTMETER KIT

The AW-1 Audio Wattmeter can be used in any application where audio power output is to be measured. Non-inductive LOAD resistors are built in for 4, 8, 16 or 600 ohms impedance. Five power ranges cover 0.5 mw, 50 mw, 500 mw, 5 w, and 50 w full scale. Five switch-selected db ranges cover -10 db to $+30$ db. All indications are read directly on a large $4\frac{1}{2}$ " 200 microampere meter. Frequency response is

± 1 db from 10 cps to 250 kc. Precision type multiplier resistors used for high accuracy, and crystal diode bridge for wide-range frequency response. This meter is used in many recording studios and broadcast stations as a monitor as well as servicing. A fine meter to help supply the answers to your audio operating or power output problems. Shpg. Wt. 6 lbs.

MODEL AW-1
\$29.50

HEATHKIT AUDIO SIGNAL GENERATOR KIT

The model AG-9A is "made to order" for high fidelity applications, and provides quick and accurate selection of low-distortion signals throughout the audio range. Three rotary switches select two significant figures and a multiplier to determine audio frequency. Incorporates step-type and a continuously variable output attenuator. Output indicated on large $4\frac{1}{2}$ " panel meter, calibrated in volts and db. Attenuator system operates in 10 db steps, corresponding to meter calibration, in ranges of 0-.003, .01, .03, .1, .3, 1, 3 and 10 volts RMS. "Load" switch permits use of built-in 600-ohm load, or external load of different impedance. Output and frequency indicators accurate to within $\pm 5\%$. Distortion less than .1 of 1% between 20 and 20,000 cps. Total range is 10 cps to 100 kc. Shpg. Wt. 8 lbs.

MODEL AG-9A
\$34.50

HEATHKIT HARMONIC DISTORTION METER KIT

All sounds consist of dominant tones plus harmonics (over-tones). These harmonics enrich the quality and brightness of the music. However, additional harmonics which originate in the audio equipment, represent distortion. Used with an audio signal generator, the HD-1 will accurately measure this harmonic distortion at any or all frequencies between 20 and 20,000 cps. Distortion is read directly on the panel meter in ranges of 0-1, 3, 10, 30 and 100% full scale. Voltage ranges of 0-1, 3, 10 and 30 volts are provided for the initial reference settings. Signal-to-noise ratio measurements are also permitted through the use of a separate meter scale calibrated in db. High quality components insure years of outstanding performance. Full instructions are provided. Shpg. Wt. 13 lbs.

MODEL HD-1
\$49.50

Heathkits...

By DAYSTROM

are well known for their high quality and reliability.

HEATHKIT AUDIO VTVM KIT

This new and improved AC Vacuum Tube Voltmeter is designed especially for audio measurements and low-level AC measurements in power supply filters, etc. Employs an entirely new circuit featuring a cascode amplifier with cathode-follower isolation between the input and the amplifier, and between the output stage and the preceding stages. It emphasizes stability, broad frequency response, and sensitivity. Frequency response is essentially flat from 10 cps to 200 kc. Input impedance is 1 megohm at 1000 cps. AC (RMS) voltage ranges are 0-.01, .03, .1, .3, 1, 3, 10, 30, 100 and 300 volts. Db ranges cover -52 db to $+52$ db. Features large $4\frac{1}{2}$ " 200 microampere meter, with increased damping in meter circuit for stability in low frequency tests. 1% precision resistors employed for maximum accuracy. Stable, reliable performance in all applications. Shpg. Wt. 5 lbs.

MODEL AV-3
\$29.95

HEATHKIT COLOR BAR AND DOT GENERATOR

The CD-1 combines the two basic color service instruments, a Color Bar Generator and White Dot Generator in one versatile portable unit, which has crystal-controlled accuracy and stability (no external sync lead required). Produces white-dots, cross hatch, horizontal and vertical bars, 10 vertical color bars, and a new shading bar pattern for screen and background adjustments. Variable RF output on any channel from 2 to 6. Positive or negative video output, variable from 0 to 10 volts peak-to-peak. Crystal controlled sound carrier with off-on switch. Voltage regulated power supply using long-life silicon rectifiers. Gain knowledge of a new and profitable field by constructing this kit. Shpg. Wt. 12 lbs.

MODEL CD-1
\$59⁹⁵

HEATHKIT "EXTRA DUTY" 5" OSCILLOSCOPE KIT

This fine oscilloscope compares favorably to other scopes costing twice its price. It contains the extra performance so necessary for monochrome and color-TV servicing. Features push-pull horizontal and vertical output amplifiers, a 5UPI CRT, built in peak-to-peak calibration source, a fully compensated 3-position step-type input attenuator, retrace blanking, phasing control, and provision for Z-axis modulation. Vertical amplifier frequency response is within +1.5 and -5 db from 3 CPS to 5 MC. Response at 3.58 MC down only 2.2 db. Sensitivity is 0.025 volts RMS/inch at 1 kc. Sweep generator covers 20 CPS to 500 kc in five steps, five times the usual sweep obtained in other scopes through the use of the patented Heath sweep circuit. Etched-metal circuit boards reduce assembly time and minimize errors in assembly, and more importantly, permit a level of circuit stability never before achieved in an oscilloscope of this type. Shpg. Wt. 21 lbs.

MODEL O-12
\$64⁹⁵

Heathkits...

By DAYSTROM

are guaranteed to meet or exceed advertised specifications

HEATHKIT TV ALIGNMENT GENERATOR KIT

This fine TV alignment generator offers stability and flexibility difficult to obtain even in instruments costing several times this low Heathkit price. It covers 3.6 mc to 220 mc in four bands. Sweep deviation is controllable from 0 to 42 mc. The all-electronic sweep circuit insures stability. Crystal marker and variable marker oscillators are built in. Crystal (included with kit) provides output at 4.5 mc and multiples thereof. Variable marker provides output from 19 to 60 mc on fundamentals and from 57 to 180 mc on harmonics. Effective two-way blanking to eliminate return trace. Phasing control. Kit is complete, including three output cables. Shpg. Wt. 16 lbs.

MODEL TS-4A
\$49⁵⁰

HEATHKIT ELECTRONIC SWITCH KIT

A valuable accessory for any oscilloscope owner. It allows simultaneous oscilloscope observation of two signals by producing both signals, alternately, at its output. Four switching rates. Provides gain for input signals. Frequency response ± 1 db, 0 to 100 kc. A sync output is provided to control and stabilize scope sweep. Ideal for observing input and output of amplifiers simultaneously. Shpg. Wt. 8 lbs.

MODEL S-3
\$21⁹⁵

HEATHKIT VOLTAGE CALIBRATOR KIT

This unit is an excellent companion for your oscilloscope. Used as a source of calibrating voltage, it produces near-perfect square wave signals of known amplitude. Precision 1% attenuator resistors insure accurate output amplitude, and multivibrator circuit guarantees good sharp square waves. Output frequency is approximately 1000 CPS. Fixed outputs selected by panel switches are: .03, 0.1, 0.3, 1.0, 3.0, 10, 30 and 100 volts peak-to-peak. Allows measurement of unknown signal amplitude by comparing it to the known output of the VC-3 on oscilloscope. Shpg. Wt. 4 lbs.

MODEL VC-3
\$12⁵⁰

Functional styling with clean uncluttered look



COLOR BAR AND DOT GENERATOR



"EXTRA DUTY" SCOPE



TV ALIGNMENT GENERATOR



ELECTRONIC SWITCH



VOLTAGE CALIBRATOR

HEATH COMPANY A Subsidiary of Daystrom, Inc. **BENTON HARBOR 20, MICH.**

MAY, 1958

71

HEATHKIT TUBE CHECKER KIT

Eliminate guesswork, and save time in servicing or experimenting. The TC-2 tests tubes for shorted elements, open elements, filament continuity, and operating quality on the basis of total emission. It tests all tube types encountered in radio and TV service work. Sockets are provided for 4, 5, 6 and 7-pin, octal, and loctal tubes, 7 and 9 pin miniature tubes, 5 pin hytron miniatures, and pilot lamps. Tube condition indicated on 4½" meter with multi-color "good-bad" scale. Illuminated roll chart with all test data built in. Switch selection of 14 different filament voltages from .75 to 117 volts. Color-coded cable harness allows neat professional wiring and simplifies construction. Very easy to build, even for a beginner. Shpg. Wt. 12 lbs.

MODEL TC-2

\$29⁹⁵

HEATHKIT HANDITESTER KIT

The small size and rugged construction of this tester makes it perfect for any portable application. The combination function-range switch simplifies operations. Measures AC or DC voltage at 0-10, 30, 300, 1000 and 5000 volts. Direct current ranges are 0-10 ma and 0-100 ma. Ohmmeter ranges are 0-3000 (30 ohm center scale) and 0-300,000 (3000 ohm center scale). Very popular with home experimenters, electricians, and appliance repairmen. Slips easily into your tool box, glove compartment, coat pocket, or desk drawer. Shpg. Wt. 3 lbs.

MODEL M-1

\$17⁹⁵

HEATHKIT PICTURE TUBE CHECKER KIT

The CC-1 can be taken with you on service calls so that you can clearly demonstrate the quality of a customer's picture tube in his own home. Tubes can be tested without removing them from the receiver or cartons if desired. Checks cathode emission, beam current, shorted elements, and leakage between elements in electromagnetic picture tube types. Self-contained power supply, and large 4½" meter. CRT condition indicated on "good-bad" scale. Relative condition of tubes fluorescent coating is shown in "shadow-graph" test. Permanent test cable with CRT socket and anode connector. No tubes to burn out, designed to last a lifetime. Luggage-type portable case. Shpg. Wt. 10 lbs.

MODEL CC-1

\$24⁹⁵

HEATHKIT ETCHED-CIRCUIT VTVM KIT

This multi-purpose VTVM is the world's largest selling instrument of its type—and is especially popular in laboratories, service shops, home workshops and schools. It employs a large 4½" panel meter, precision 1% resistors, etched metal circuit board, and many other "extras" to insure top quality and top performance. It's easy to build, and you may rely on its accuracy and dependability. The V7-A will measure AC (RMS) and DC voltages in ranges of 0-1.5, 5, 15, 50, 150, 500 and 1500. It measures peak-to-peak AC voltage in ranges of 0-4, 14, 40, 140, 400, 1400 and 4000. Resistance ranges provide multiplying factors of X 1, X 10, X 100, X 1000, X 10k, X 100k, and X 1 megohm. Center-scale resistance readings are 10, 100, 1000, 10k, 100k, 1 megohm and 10 megohms. A db scale is also provided. The precision and quality of this VTVM cannot be duplicated at this price. Shpg. Wt. 7-lbs.

MODEL V7-A

\$24⁵⁰

Heathkits...

BY DAYSTROM


*let you fill your exact needs
from a wide variety
of instruments*

HEATHKIT 20,000 OHMS/VOLT VOM KIT

This fine instrument provides a total of 25 meter ranges on its two-color scale. It employs a 50 ua 4½" meter, and features 1% precision multiplier resistors. Requires no external power. Ideal for portable applications. Sensitivity is 20,000 ohms-per-volt DC and 5000 ohms-per-volt AC. Measuring ranges are 0-1.5, 5, 50, 150, 500, 1500 and 5000 volts, AC and DC. Measures direct current in ranges of 0-150 ua, 15 ma, 150 ma, 500 ma and 15 a. Resistance multipliers are X 1, X 100 and X 10,000, with center-scale readings of 15, 1500 and 150,000 ohms. Covers -10 db to +65 db. Easy to build and fun to use. Attractive bakelite case with plastic carrying handle. Shpg. Wt. 6 lbs.

MODEL MM-1

\$29⁹⁵

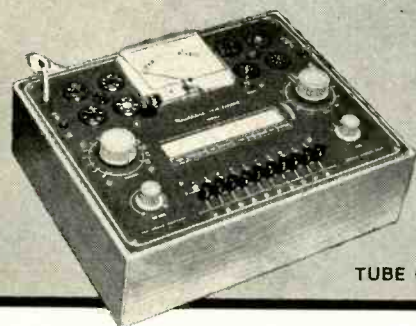

TUBE CHECKER



ETCHED
CIRCUIT VTVM

*High quality
test gear you
will be
proud to own*



HANDITESTER

*Priced low
to fit your
budget*



PICTURE TUBE
CHECKER



20,000
OHMS/VOLT VOM

HEATHKIT RF SIGNAL GENERATOR KIT

Even a beginner can build this prealigned signal generator, designed especially for use in service work. Produces RF signals from 160 kc to 110 mc on fundamentals in five bands. Covers 110 mc to 220 mc on calibrated harmonics. Low impedance RF output in excess of 100,000 microvolts, is controllable with a step-type and continuously variable attenuator. Selection of unmodulated RF, modulated RF, or audio at 400 CPS. Ideal for fast and easy alignment of radio receivers, and finds application in FM and TV work as well. Thousands of these units are in use in service shops all over the country. Easy to build and a real time saver, even for the part-time service technician or hobbyist. Shpg. Wt. 8 lbs.

MODEL SG-8

\$19⁵⁰

HEATHKIT LABORATORY RF GENERATOR KIT

Tackle all kinds of laboratory alignment jobs with confidence by employing the LG-1. It features voltage-regulated B+, double shielding of oscillator circuits, copper-plated chassis, variable modulation level, metered output, and many other "extras" for critical alignment work. Generates RF signals from 100 kc to 30 mc on fundamentals in five bands. Meter reads RF output in microvolts or modulation level in percentage. RF output available up to 100,000 microvolts, controlled by a fixed-step and a variable attenuator. Provision for external modulation where necessary. Buy and use this high-quality RF signal generator that may be depended upon for stability and accuracy. Shpg. Wt. 16 lbs.

MODEL LG-1

\$48⁹⁵

HEATHKIT DIRECT-READING CAPACITY METER KIT

Here's a fast, simple capacity meter. A capacitor to be checked is merely connected to the terminals, the proper range selected, and the value read directly on the large 4½" panel meter calibrated in mmf and mfd. Ranges are 0 to 100 mmf, 1,000 mmf, .01 mfd, .1 mfd full scale. Not affected by hand capacity. Shpg. Wt. 7 lbs.

MODEL CM-1

\$29⁵⁰

Heathkits...

By DAYSTROM


*are educational
as well as functional*

HEATHKIT "IN-CIRCUIT" CAPACI-TESTER KIT

With the CT-1 it is no longer necessary to disconnect one capacitor lead to check the part, you can check most capacitors for "open" or "short" right in the circuit. Fast and easy—to save your valuable time in the service shop or lab. Detects open capacitors from about 50 mmf up, so long as the capacitor is not shunted by excessively low resistance value. Will detect shorted capacitors up to 20 mfd (not shunted by less than 10 ohms). (Does not detect leakage.) Employs 60 cycles and 19 megacycle test frequencies. Electron beam "eye" tube used as indicator. Compact, easy-to-build, and inexpensive. Test leads included. Shpg. Wt. 5 lbs.

MODEL CT-1

\$7⁹⁵

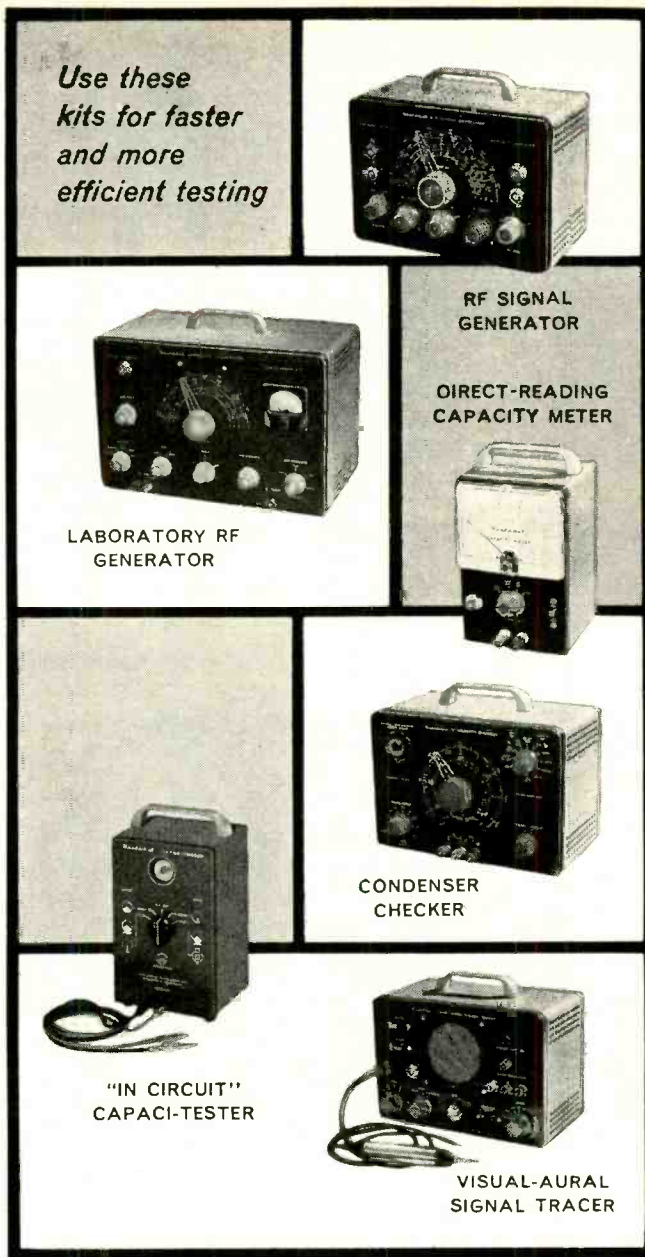

*Use these
kits for faster
and more
efficient testing*



RF SIGNAL GENERATOR



LABORATORY RF GENERATOR

DIRECT-READING CAPACITY METER



CONDENSER CHECKER



"IN CIRCUIT" CAPACI-TESTER



VISUAL-AURAL SIGNAL TRACER

HEATHKIT CONDENSER CHECKER KIT

This handy instrument uses an electron beam "eye" tube as an indicator to measure capacity in ranges of .00001 to .005 mfd, .5 mfd, 50 mfd and 1000 mfd. Also measures resistance from 100 ohms to 5 megohms in two ranges. Checks paper, mica, ceramic and electrolytic capacitors. Selection of five polarizing voltages. Shpg. Wt. 7 lbs.

MODEL C-3

\$19⁵⁰

HEATHKIT VISUAL-AURAL SIGNAL TRACER KIT

Although designed originally for radio receiver work, the T-3 finds application in FM and TV servicing as well. Features high-gain channel with demodulator probe, and low-gain channel with audio probe. Traces signals in all sections of radio receivers and in many sections of FM and TV receivers. Built-in speaker and electron beam eye tube indicate relative gain, etc. Also features built-in noise locator circuit. Provision for patching speaker and/or output transformer to external set. Shpg. Wt. 9 lbs.

MODEL T-3

\$23⁵⁰

HEATH COMPANY A Subsidiary of Daystrom, Inc. BENTON HARBOR 20, MICH.

HEATHKIT IMPEDANCE BRIDGE KIT

The model IB-2A employs a Wheatstone Bridge, a Capacity Comparison Bridge, a Maxwell Bridge, and a Hay Bridge in one compact package. Measures resistance from 0.1 ohm to 10 megohms, capacitance from 100 mmf to 100 mfd, inductance from 0.1 mh to 100 h, dissipation factor (D) from 0.002 to 1, and storage factor (Q) from 0.1 to 1000. A 100-0-100 ua meter provides for null indications. The decade resistors employed are of 1% tolerance for maximum accuracy. Completely self-contained. Has built in power supply, 1000-cycle generator, and vacuum-tube detector. Special two-section CRL dial insures convenient operation. Instruction manual has entirely new schematic that clarifies circuit functions in various switch positions. A true laboratory instrument, that will provide you with many years of fine performance. Shpg. Wt. 12 lbs.

MODEL IB-2A
\$59.50

HEATHKIT "LOW RIPPLE" BATTERY ELIMINATOR KIT

This modern battery eliminator incorporates an extra low-ripple filter circuit so that it can be used to power all the newest transistor-type circuits requiring 0 to 12 volts DC,


and the new "hybrid" automobile radios using both transistors and vacuum tubes. Its DC output, at either 6 or 12 volts, contains less than .3% AC ripple. Separate output terminals are provided for low-ripple or normal filtering. Supplies up to 15 amps on 6 volt range or up to 7 amps on 12 volt range. Output is variable from 0 to 8 or 0 to 16 volts. Two meters constantly monitor output voltage and current. Will also double as a battery charger. Shpg. Wt. 23 lbs.

MODEL BE-5
\$39.95

HEATHKIT ISOLATION TRANSFORMER KIT

The model IT-1 is one of the handiest units for the service shop, home workshop or laboratory. Provides complete isolation from the power line. AC-DC sets may be plugged directly into the IT-1 without the chassis becoming "hot". Output voltage is variable from 90 volts to 130 volts allowing checks of equipment under adverse conditions such as low line voltage. Rated for 100 volt amperes continuously or 200 volt amperes intermittently. Panel meter monitors output voltage. Shpg. Wt. 9 lbs.

MODEL IT-1
\$16.50

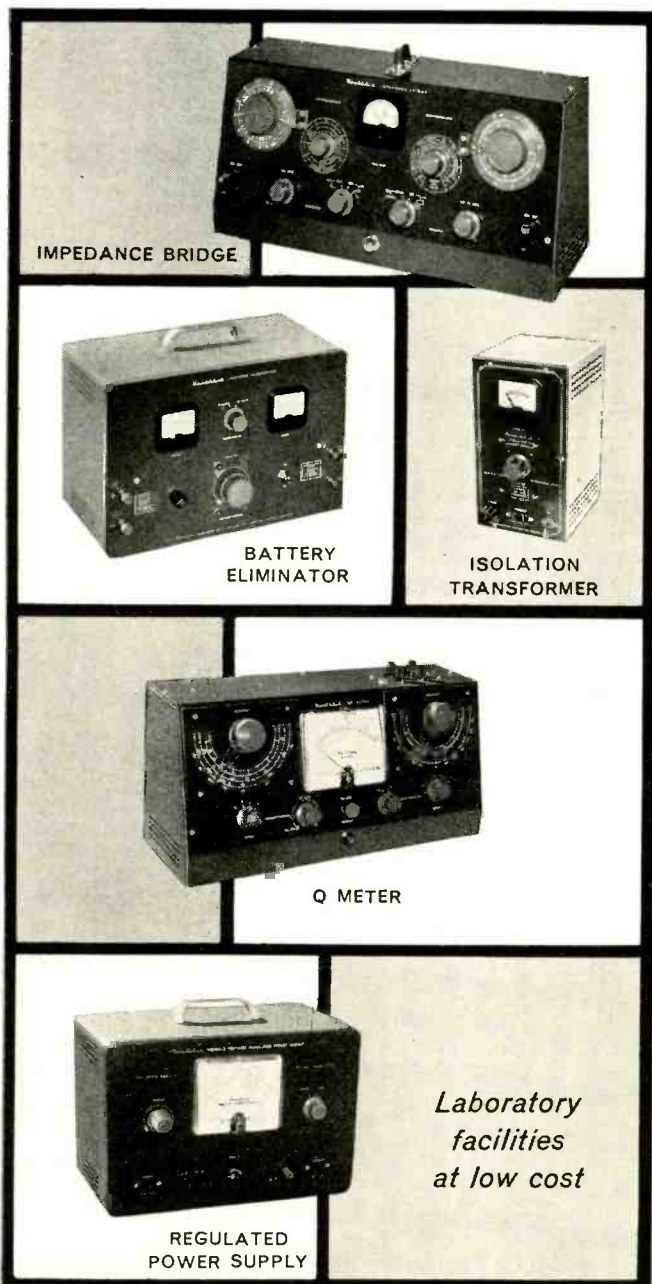

Heathkits...

By DAYSTROM

are designed with high-quality, name-brand components to insure long service life

HEATHKIT "Q" METER KIT

At this price the laboratory facilities of a Q Meter may be had by the average service technician or home experimenter. The Q Meter permits measurement of inductance from 1 microhenry to 10 milihenry, "Q" on a scale calibrated up to 250 full scale, with multipliers of 1 or 2, and capacitance from 40 mmf to 450 mmf \pm 3 mmf. Built in oscillator permits testing components from 150 kc to 18 mc. Large 4 1/2" panel meter is featured. Very handy for checking peaking coils, chokes, etc. Use to determine values of unknown condensers, both variable and fixed, compile data for coil winding purposes, or measure RF resistance. Also checks distributed capacity and Q of coils. No special equipment is required for calibration. A special test coil is furnished, along with easy-to-follow instructions. Shpg. Wt. 14 lbs.

MODEL QM-1
\$44.50

HEATHKIT REGULATED POWER SUPPLY KIT

Here is a power supply that will provide DC plate voltage and AC filament voltage for all kinds of experimental circuits. The DC supply is regulated for stability, and yet the amount of DC output voltage available from the power supply can be controlled manually from 0 up to 500 volts. At 450 volts DC output, the power supply will provide up to 10 ma of current, and provide progressively higher current as the output voltage is lowered. Current rating is 130 ma at 200 volts output. In addition to furnishing B+ the power supply also provides 6.3 volts AC at up to 4 amperes for filaments. Both the B+ output and the filament output are isolated from ground. Ideal unit for use in laboratory, home workshop, ham shack, or service shop. A large 4 1/2" meter on the front panel reads output voltage or output current, selectable with a panel switch. Shpg. Wt. 17 lbs.

MODEL PS-3
\$35.50



*Terrific values
in amateur
equipment!*



DX-20 TRANSMITTER



DX-40 TRANSMITTER



DX-100 TRANSMITTER

HEATHKIT DX-20 CW TRANSMITTER KIT

The Heathkit model DX-20 "straight-CW" transmitter features high efficiency at low cost. It uses a single 6DQ6A tube in the final amplifier stage for plate power input of 50 watts. A 6CL6 serves as crystal oscillator, with a 5U4GB rectifier. It is an ideal transmitter for the novice, as well as the advanced-class CW operator. Single-knob band switching is featured to cover 80, 40, 20, 15, 11 and 10 meters. Pi network output circuit matches various antenna impedances between 50 and 1000 ohms and reduces harmonic output. Top-quality parts are featured throughout, including "potted" transformers, etc., for long life. It has been given full "TVI" treatment. Access into the cabinet for crystal changing is provided by a removable metal pull-out plug on the left end of the cabinet. Very easy to build from the complete step-by-step instructions supplied, even if you have never built electronic equipment before. If you appreciate a good, clean signal on the CW bands, this is the transmitter for you! Shpg. Wt. 18 lbs.

MODEL DX-20

\$35⁹⁵

a most attractive appearance, and is designed for complete shielding to minimize TVI. A 4-position switch provides convenient selection of three different crystals or a jack for external VFO. The crystals are reached through access door at rear of cabinet. You can build this rig yourself and be proud to show it off to your fellow hams. Get your DX-40 now for many hours of operating enjoyment. Shpg. Wt. 25 lbs.

MODEL DX-40

\$64⁹⁵

HEATHKIT DX-100 PHONE AND CW TRANSMITTER KIT

Listen to any ham band between 160 meters and 10 meters and note how many DX-100 transmitters you hear! The number of these fine rigs now on the air testifies to the enthusiasm with which it has been accepted by the amateur fraternity. No other transmitter in this power class combines high quality and real economy so effectively. The DX-100 features a built in VFO, modulator and power supplies, complete shielding to minimize TVI, and pi network output coupling to match impedances from approximately 50 to 600 ohms. Its RF output is in excess of 100 watts on phone and 120 watts on CW, for a clean strong signal on all the ham bands from 10 to 160 meters. Single-knob band switching and illuminated VFO dial and meter face add real operating convenience. RF output stage uses a pair of 6146 tubes in parallel, modulated by a pair of 1625's. High quality components are used throughout, such as "potted" transformers, silver-plated or solid coin silver switch terminals, aluminum heat-dissipating caps on the final tubes, copper plated chassis, etc. This transmitter was designed exclusively for easy step-by-step assembly. Shpg. Wt. 107 lbs.

MODEL DX-100

\$189⁵⁰

Heathkits...

BY DAYSTROM

*are designed by
licensed ham-engineers,
especially for you*

HEATHKIT DX-40 PHONE AND CW TRANSMITTER KIT

A most remarkable power package for the price, the new DX-40 provides both phone and CW facilities for operation on 80, 40, 20, 15, 11 and 10 meters. A single 6146 tube is used in the final amplifier stage to provide full 75 watt plate power input on CW, or control carrier modulation peaks up to 60 watts for phone operation. Modulator and power supplies are built right in and single knob bandswitching is combined with a pi network output circuit for complete operating convenience. The tight fitting cabinet presents

FUNCTIONAL DESIGN . . .

The transmitters described on this page were designed for the ham, by hams who know what features are desirable and needed. This assures you of the best possible performance and convenience, and adds much to your enjoyment in the ham shack.

HEATH COMPANY A Subsidiary of Daystrom, Inc. BENTON HARBOR 20, MICH.


*Automatically turns off
transmitter and gives
visual signal*




"AUTOMATIC"
CONELRAD ALARM



GRID DIP METER

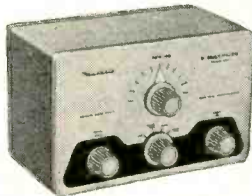

"Q" MULTIPLIER

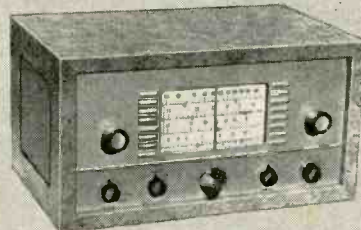

COMMUNICATIONS-TYPE
RECEIVER

*An ideal receiver
for the beginning
ham or short
wave listener*

HEATHKIT "AUTOMATIC" CONELRAD ALARM KIT

This conelrad alarm works with any radio receiver; AC-DC-transformer operated—or battery powered, so long as the receiver has AVC. Fully complies with FCC regulations for amateurs. When the monitored station goes off the air, the CA-1 automatically cuts the AC power to your transmitter, and lights a red indicator. A manual "reset" button reactivates the transmitter. Incorporates a heavy-duty six-ampere relay, a thyratron tube to activate the relay, and its own built-in power supply. A neon lamp shows that the alarm is working, by indicating the presence of B+ in the alarm circuit. Simple to install and connect. Your transmitter plugs into an AC receptacle on the CA-1, and a cable connects to the AVC circuit of a nearby receiver. A built-in sensitivity control allows adjustment to various AVC levels. Receiver volume control can be turned up or down, without affecting alarm operation. Build a Heathkit CA-1 in one evening and comply with FCC regulations now! Shpg. Wt. 4 lbs.

MODEL CA-1
\$13⁹⁵

HEATHKIT "Q" MULTIPLIER KIT

The Heathkit Q Multiplier functions with any AM receiver having an IF frequency between 450 and 460 KC, that is not "AC-DC" type. It derives its power from the receiver, and needs only 6.3 volts AC at 300 ma (or 12 VAC at 150 ma) and 150 to 250 volts DC at 2 ma. Simple to connect with cable and plugs supplied. Adds additional selectivity for separating signals, or will reject one signal and eliminate heterodyne. A tremendous help on crowded phone and CW bands. Effective Q of 4000 for sharp "peak" or "null". Tunes any signal within IF band pass without changing the main receiver tuning dial. A convenient tuning knob on the front panel with vernier reduction between the tuning knob and the tuning capacitor gives added flexibility in operation. Uses a 12AX7 tube, and special high-Q shielded coils. Instructions for connecting to the receiver and operation are provided in the construction manual. A worthwhile addition to any communications, or broadcast receiver. It may also be used with a receiver which already has a crystal filter to obtain two simultaneous functions, such as peaking the desired signal with the crystal filter and nulling an adjacent signal with the Q Multiplier. Shpg. Wt. 3 lbs.

MODEL QF-1
\$9⁹⁵

HEATHKIT GRID DIP METER KIT

A grid dip meter is basically an RF oscillator for determining the frequency of other oscillators, or of tuned circuits. Extremely useful in locating parasitics, neutralizing, identifying harmonics, coil winding, etc. Features continuous frequency coverage from 2 mc to 250 mc, with a complete set of prewound coils, and a 500 ua panel meter. Front panel has a sensitivity control for the meter, and a phone jack for listening to the "zero-beat." Will also double as an absorption-type wave meter. Shpg. Wt. 4 lbs.

Low Frequency Coil Kit: Two extra plug-in coils to extend frequency coverage down to 350 kc. Shpg. Wt. 1 lb. No. 341-A. \$3.00

MODEL GD-18
\$21⁹⁵

HEATHKIT ALL-BAND COMMUNICATIONS-TYPE RECEIVER KIT

This communications-receiver covers 550 kc to 30 mc in four bands, and provides good sensitivity, selectivity, and fine image rejection. Ham bands are clearly marked on an illuminated dial scale. Features a transformer-type power supply—electrical band spread—antenna trimmer—head-phone jack—automatic gain control and beat frequency oscillator. Accessory sockets are provided on the rear of the chassis for using the Heathkit model QF-1, Q Multiplier. Accessory socket is handy, also, for operating other devices that require plate and filament potentials. Will supply +250 VDC at 15 ma and 12.6 VAC at 300 ma. Ideal for the beginning ham or short wave listener. Shpg. Wt. 12 lbs.

Cabinet: Fabric covered cabinet with aluminum panel as shown. Part no. 91-15A. Shpg. Wt. 5 lbs. \$4.95.

MODEL AR-3
\$29⁹⁵
(Less cabinet)

Heathkits...

BY DAYSTROM

*are outstanding in performance
and dollar value*

HEATHKIT REFLECTED POWER METER KIT

The Heathkit reflected power meter, model AM-2, makes an excellent instrument for checking the match of the antenna transmission system, by measuring the forward and reflected power or standing wave ratio. The AM-2 is designed to handle a peak power of well over 1 kilowatt of energy and may be left in the antenna system feed line at all times. Band coverage is 160 meters through 2 meters. Input and output impedances for 50 or 75 ohm lines. No external power required for operation. Meter indicates percentage forward and reflected power, and standing wave ratio from 1:1 to 6:1. Another application for the AM-2 is matching impedances between excitors or R.F. sources and grounded grid amplifiers. Power losses between transmitter output and antenna tuner may be very easily computed by inserting the AM-2 in the line connecting the two. No insertion loss is introduced into the feeder system, due to the fact that the AM-2 is a portion of coaxial line in series with the feeder system and no internal connections are actually made to the line. Complete circuit description and operation instructions are provided in the manual. Cabinet size is 7-3/8" x 4-1/16" x 4-5/8". Can be conveniently located at operating position. Shpg. Wt. 3 lbs.

MODEL AM-2

\$15⁹⁵

HEATHKIT VARIABLE FREQUENCY OSCILLATOR KIT

Enjoy the convenience and flexibility of VFO operation by obtaining the Heathkit model VF-1 Variable Frequency Oscillator. Covers 160-80-40-20-15-11 and 10 meters with three basic oscillator frequencies. Better than 10 volt average RF output on fundamentals. Plenty of output to drive most modern transmitters. It features voltage regulation for frequency stability. Dial is illuminated for easy reading. Vernier reduction is used between the main tuning knob and the tuning condenser. Requires a power source of only 250 volts DC at 15 to 20 milliamperes and 6.3 volts AC at 0.45 amperes. Extra features include copper-plated chassis, ceramic coil forms, extensive shielding, etc. High quality parts throughout. VFO operation allows you to move out from under interference and select a portion of the band you want to use without having to be tied down to only two or three frequencies through use of crystals. "Zero in" on the other fellow's signal and return his CQ on his own frequency! Crystals are not cheap, and it takes quite a number of them to give anything even approaching comprehensive coverage of all bands. Why hesitate? The model VF-1 with its low price and high quality will add more operating enjoyment to your ham activities. Shpg. Wt. 7 lbs.

MODEL VF-1

\$19⁵⁰

Heathkits...

By DAYSTROM

are the answer for your electronics hobby.

HEATHKIT BALUN COIL KIT

The Heathkit Balun Coil Kit model B-1 is a convenient transmitter accessory, which has the capability of matching unbalanced coax lines, used on most modern transmitters, to balance lines of either 75 or 300 ohms impedance. Design of the bifilar wound balun coils will enable transmitters with unbalanced output to operate into balanced transmission line, such as used with dipoles, folded dipoles, or any balanced antenna system. The balun coil set can be used with transmitters and receivers without adjustment over the frequency range of 80 through 10 meters, and will easily handle power inputs up to 250 watts. Cabinet size is 9" square by 5" deep and it may be located any distance from the transmitter or from the antenna. Completely enclosed for outdoor installation. Shpg. Wt. 4 lbs.

MODEL B-1


\$8⁹⁵

HEATHKIT 6 OR 12 VOLT VIBRATOR POWER SUPPLY KITS

These little power supply kits are ideal for all portable applications with 6 volt or 12 volt batteries, when you are operating electronic equipment away from power lines. By replacing the power supplies of receivers, small public address systems, or even miniature transmitters with these units, they can be used with conventional 6 or 12 volt batteries. Use in boats, automobiles, light aircraft, or any field application. Each unit provides 260 volts DC output at up to 60 milliamperes. More than one power supply of the same model may be connected in parallel for increased current capacity at the same output voltage. Everything is provided in the kit, including a vibrator transformer, a vibrator, 6X4 or 12X4 rectifier, and the necessary buffer capacitor, hash filter, and output filter capacitor. Shpg. Wt. 4 lbs.

6 VOLT
MODEL VP-1-6
12 VOLT
MODEL VP-1-12

\$7⁹⁵ Each

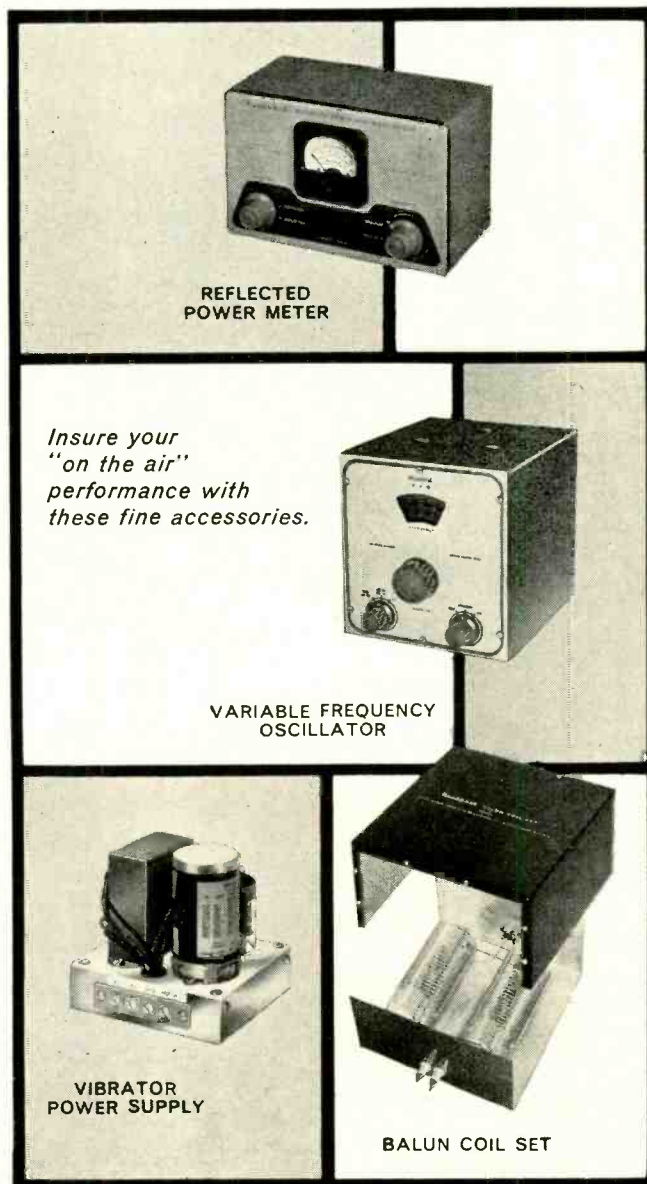

HEATH COMPANY A Subsidiary of Daystrom, Inc. BENTON HARBOR 20, MICH.

**HEATHKIT ELECTRONIC
IGNITION ANALYZER KIT**


Previous electronic experience is not necessary to build this fine ignition analyzer. The construction manual supplied has complete step-by-step instructions plus large pictorial diagrams showing the exact placement and value of each component. All parts are clearly marked so that they are easily identified. The IA-1 is an ideal tool for engine mechanics, tune-up men, and auto hobbyists, since it traces the dynamic action of voltage in an ignition system on a cathode-ray tube screen. The wave form produced is affected by the condition of the coil, condenser, points, plugs, and ignition wiring, so it can be analyzed, and used as a "sign-post" to ignition system performance. This analyzer will detect inequality of spark intensity, a poor spark plug, defective plug wiring, breaker-point bounce, an open condenser, and allow setting of dwell-time percentage for the points. An important feature of this instrument is its ability to check dynamic performance, with the engine in operation (400 to 5000 RPM). It will show the complete engine cycle, or only one complete cylinder. Can be used on all types of internal combustion engines where breaker-points are accessible. Use it on automobiles, boats, aircraft engines, etc. Shpg. Wt. 18 lbs.

MODEL IA-1
\$59⁹⁵

**HEATHKIT PROFESSIONAL
RADIATION COUNTER KIT**

This Heathkit professional-type radiation counter is simple to build successfully, even if you have never built a kit before. Complete step-by-step instructions are combined with giant-size pictorial diagrams for easy assembly. By "building it yourself" you can have a modern-design, professional radiation counter priced far below comparable units. Provides high sensitivity with ranges from 0-100, 600, 6000 and 60,000 counts-per-minute, and 0-.02, .1, 1 and 10 miliroentgens-per-hour. Employs 900-volt bismuth tube in beta/gamma sensitive probe. Probe and 8-foot expandable cable included in kit price, as is a radiation sample for calibration. Use it in medical laboratories, or as a prospecting tool, and for civil defense to detect radioactive fallout, or other unknown radiation levels. Features a selectable time constant. Meter calibrated in CPM or mR/hour in addition to "beep" or "click" from panel-mounted speaker. Prebuilt "packaged" high voltage power supply with reserve capacity above 900 volt level at which it is regulated. Merely changing regulator tube type would allow use of scintillation probe if desired. Employs five tubes (plus a transistor) to insure stable and reliable operation. Kit price includes batteries. Shpg. Wt. 8 lbs.

MODEL RC-1
\$79⁹⁵

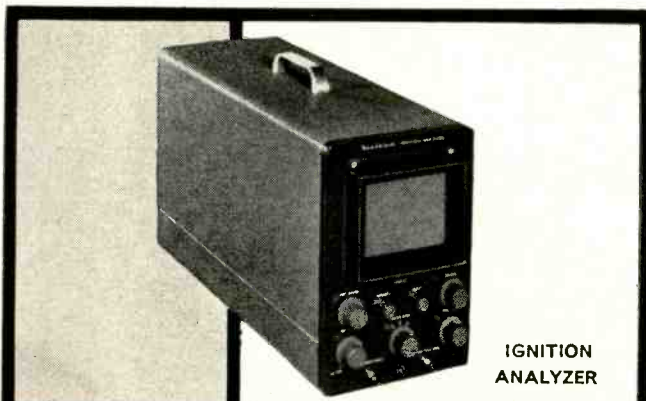

IGNITION
ANALYZER



*Kit includes everything
you need for
construction — even
batteries!*

RADIATION COUNTER

Heathkits...

By DAYSTROM

*are supplied with comprehensive
instructions that eliminate costly
mistakes and save valuable time*

HEATHKIT ENLARGER TIMER KIT


The ET-1 is an easy-to-build electronic device to be used by amateur or professional photographers in timing enlarger operations. The calibrated dial on the timer covers 0 to 1 minute, calibrated in 5-second gradations. The continuously variable control allows setting of the "on" cycle of your enlarger, which is plugged into a receptacle on the front panel of the ET-1. A "safe light" can also be plugged in so that it is automatically turned "on" when the enlarger is turned "off." Handles up to 350 watts with built-in relay. All-electronic timing cycle insures maximum accuracy. Timer does not have to be reset after each cycle, merely flip lever switch to print, to repeat time cycle. A control is provided for initial calibration. Housed in a compact plastic case that will resist attack of photographic chemicals. A fine addition to any dark room. Shpg. Wt. 3 lbs.

MODEL ET-1
\$77⁵⁰

HEATHKIT BATTERY TESTER KIT


The BT-1 is a special battery testing device that actually "loads" the battery under test (draws current from it) while it is being tested. Weak batteries often test "good" with an ordinary voltmeter but the built-in load resistance of the BT-1 automatically draws enough current from the battery to reveal its true condition. Simple to operate with "good-weak-replace" scale. Tests all kinds of dry cell batteries within ranges of 0-15 volts and 0-180 volts. Slide switch provides for either 10 ma or 100 ma load, depending on whether you're testing an A or B battery. Not only determines when battery is completely exhausted, but makes it possible to anticipate failure by noting weak condition. Ideal for testing dry cell hearing aid, flashlight, portable radio, and model airplane batteries. Test batteries in a way your customers can understand and stimulate battery sales. Shpg. Wt. 2 lbs.

MODEL BT-1
\$8⁵⁰

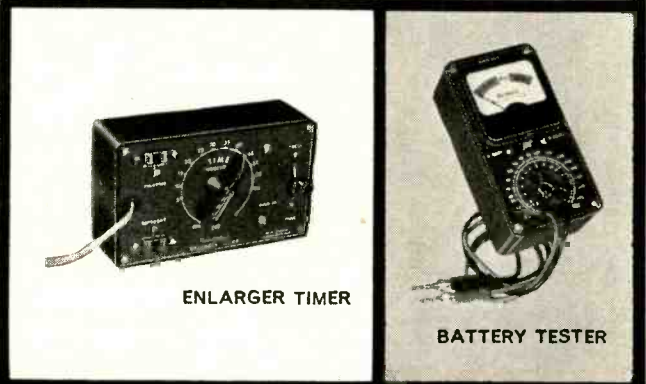

ENLARGER TIMER

BATTERY TESTER

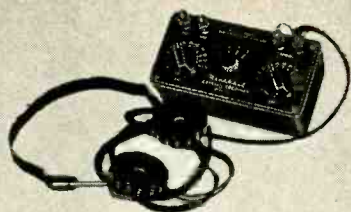

CRYSTAL RADIO



Now you can have radio
wherever you go —
with the portable
that plays anywhere!



BROADCAST BAND RADIO



TRANSISTOR PORTABLE

HEATHKIT CRYSTAL RADIO KIT

The Heathkit model CR-1 crystal radio is similar to the "crystal sets" of the early radio days except that it has been improved by the use of sealed germanium diodes and efficient "high-Q" coils. The sealed diodes eliminate the critical "cats whisker" adjustment, and the ferrite coils are much more efficient for greater signal strength. Housed in a compact plastic box, the CR-1 uses two tuned circuits, each with a variable tuning capacitor, to select the local station. It covers the broadcast band from 540 to 1600 kc. Requires no external power whatsoever. This receiver could prove valuable to emergency reception of civil defense signals should there be a power failure. The low kit price even includes headphones. Complete step-by-step instructions and large pictorial diagrams are supplied for easy assembly. The instruction manual also provides the builder with the basic fundamentals of signal reception so that he understands how the crystal receiver functions. An interesting and valuable "do-it-yourself" project for all ages. Shpg. Wt. 3 lbs.

MODEL CR-1
\$7⁹⁵

result of these efforts. Six name-brand (Texas Instrument) transistors were selected for extra good sensitivity and selectivity. A 4" by 6" PM speaker with heavy magnet was chosen to insure fine tone quality. The power supply was designed to use six standard size "D" flashlight cells because they are readily available, inexpensive, and because they afford extremely long battery life (between 500 and 1000 hours). Costs you no more to operate from batteries than what you pay for operating a small table-model radio from the power line. An unbreakable molded plastic was selected for cabinet material because of its durability and striking beauty. Circuit is compact and efficient, yet components are not excessively crowded. Transformers are prealigned so it is ready for service as soon as construction is completed. Has built in rod-type antenna for reception in all locations. Cabinet dimensions are 9" L x 8" H x 3 3/4" D. Comes in holiday gray, with gold-anodized metal speaker grille. Compare this portable, feature by feature, to all others on the market, and you'll appreciate what a tremendous dollar value it represents! Shpg. Wt. 4 lbs.

MODEL XR-1
\$34⁹⁵
(Less batteries)
(With cabinet)

Heathkits...

By DAYSTROM

are easy and fun to build,
and they let you learn
by "doing-it-yourself"

HEATHKIT TRANSISTOR PORTABLE RADIO KIT

Heath engineers set out to develop a "universal" AM radio, suitable for use anywhere. Their objective was a portable that would be as much "at home" inside as it is outside, and would feature top quality components for high performance and long service life. The model XR-1 is the

HEATHKIT BROADCAST BAND RADIO KIT

This table-model broadcast radio is fun to build, and is a fine little receiver for your home. It covers the standard broadcast band from 550 to 1600 kc with good sensitivity and selectivity. The 5 1/2" PM speaker provides surprisingly good tone quality. High-gain IF transformers, miniature tubes, and a rod-type built in antenna, assure good reception in all locations. The power supply is transformer operated, as opposed to many of the economy "AC-DC" types. It's easy to build from the step-by-step instructions, and the construction manual includes information on operational theory, for educational purposes. Your success is assured by completely detailed information which also explains resistor and capacitor color codes, soldering techniques, use of tools, etc. A signal generator is recommended for final alignment. Shpg. Wt. 10 lbs.

Cabinet: Fabric covered cabinet with aluminum panel as shown. Shpg. Wt. 5 lbs. Part no. 91-9A. \$4.95.

MODEL BR-2
\$78⁹⁵
(Less cabinet)

HEATH COMPANY A Subsidiary of Daystrom, Inc. BENTON HARBOR 20, MICH.

protects against possible explosion and fire from undetected fuel vapor

FUEL VAPOR DETECTOR




detects electrolysis currents which cause deterioration of underwater metal fittings on your boat

ELECTROLYSIS DETECTOR




indicates condition and charge of batteries for safe cruising

BATTERY CHARGE INDICATOR

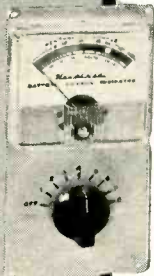

R.F. POWER METER

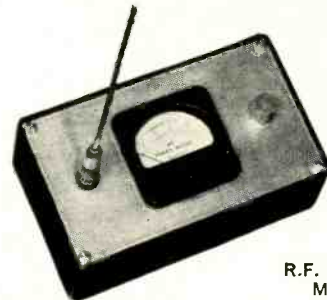

HEATHKIT FUEL VAPOR DETECTOR KIT

Protect your boat and its passengers against fire or explosion from undetected fuel vapor by building and using one of these fine units. The Heathkit Fuel Vapor Detector indicates the presence of fumes on a three-color "safe-dangerous" meter scale and immediately shows if it is safe to start the engine. A pilot light on the front panel shows when the detector is operating, and it can be left on continuously, or just used intermittently. A panel control enables initial calibration of the detector when installed. Features a hermetically-sealed meter with chrome bezel, and a chrome-plated brass panel. It is very simple to build and install, even by one not having previous experience. Models FD-1-6 (6 volts DC) and FD-1-12 (12 volts DC) operate from your boat batteries. The kit is complete in every detail, even to the inclusion of a spare detector unit. Shpg. Wt. 4 lbs.

6 volt
MODEL FD-1-6
12 volt
MODEL FD-1-12

\$35⁹⁵

EACH

HEATHKIT BATTERY CHARGE INDICATOR KIT

The Heathkit model CI-1 Marine Battery Charge Indicator has been designed especially for the boat owner, although it has found use in service stations, power stations, and radio stations where banks of batteries are kept in reserve for emergency power. It is intended to replace the hydrometer method of checking storage batteries, and to eliminate the necessity for working with acid in small, below-decks enclosures. Now it is possible to check as few as one, or as many as eight storage batteries, merely by turning the switch and watching the meter. A glance at the meter tells you instantly whether your batteries are sufficiently charged for safe cruising. Dimensions are 2-7/8" W x 5-11/16" H x 2" D. Operates on either 6 or 12 volt systems using lead-acid batteries, regardless of size. Simple installation can be accomplished by the boat owner in fifteen minutes. Shpg. Wt. 3 lbs.

MODEL CI-1

\$16⁹⁵

HEATHKIT ELECTROLYSIS DETECTOR KIT

The Heathkit model ED-1 Electrolysis Detector indicates the extent of electrolysis currents between the boat's common ground and underwater fittings, except on boats having metal hulls. These currents, undetected, could

cause gradual corrosion and deterioration of the propeller or other metal fittings below the water line. It is particularly helpful when installing electrical equipment of any kind, or to determine proper polarity when power is obtained from a shore supply. Easy-to-build, the model ED-1 consists of a hermetically-sealed, waterproof meter, special sensing plate, and sufficient wire to install, including the necessary hardware. Mounts on instrument panel where it can be easily seen. Requires no power for operation, and gives instant warning to guard your boat for a lifetime. Shpg. Wt. 2 lbs.

MODEL ED-1

\$9⁹⁵

HEATHKIT RF POWER METER KIT

The Heathkit RF Power Meter Kit is designed to sample the RF field in the vicinity of your transmitter, whether it be marine, mobile, or fixed. Output meter is merely placed in some location close to the transmitter, to pick up RF radiation from the antenna. Requires no batteries, electricity, nor direct connection to the transmitter. It provides you with a continuing indication of transmitter operation. You can easily detect if power is dropping off by comparing present meter readings with past ones. Operates with any transmitter having output frequencies between 100 kc and 250 mc, regardless of power. Sensitivity is 0.3 volts RMS full scale, and a special control on the panel allows for further adjustment of the sensitivity. Meter is a 200 ua unit, mounted on a chrome-plated brass panel. The entire PM-1 measures only 3 3/4" W x 6 1/4" L x 2" D. An easy way to put your mind at ease concerning transmitter operation. Shpg. Wt. 2 lbs.

MODEL PM-1

\$14⁹⁵

Heathkits...

By DAYSTROM

now offer you completely modern marine equipment with outstanding design features

ELECTRONICS

(Continued from Page 65)

junctions by melting a correctly doped semiconductor and allowing it to refreeze.

Meltback transistor Junction transistor made by the meltback process.

Melt-quench transistor Junction transistor made by quickly cooling a melted-back region.

Microalloy transistor Transistor using very thin alloyed collector and emitter, usually made in the same shape as a surface-barrier transistor.

Minority carriers Whichever type is less plentiful, i.e. electrons in p-type and holes in n-type.

Modulator Electrode on a spacistor.

-N-

Noise figure The ratio of actual equivalent noise input to thermal noise input, usually expressed in decibels.

n-p-i-n transistor Intrinsic-region transistor with p-type base and n-type emitter and collector.

n-p-n-p transistor Hook transistor with p-type base, n-type emitter, and hook collector.

n-p-n transistor Junction transistor with p-type base and n-type collector and emitter.

n-type Semiconductor doped with a donor so that electrons are more plentiful than holes.

-P-

Parameters Set of numbers which characterize a device, especially a transistor.

Peak inverse voltage Maximum reverse voltage rating for a diode or a transistor.

Photodiode Semiconductor diode whose reverse current increases upon illumination.

Photoresistor Semiconductor resistor whose resistance drops when illuminated.

Phototransistor Photodiode with a built-in hook amplifier; physical construction is the same as a junction transistor.

Pinch-off In a field-effect transistor, the effect of having reduced source-to-drain current as far as possible.

Pinch-off voltage The voltage at which pinch-off occurs.

p-n-i-p transistor Intrinsic-region transistor with n-type base and p-type emitter and collector.

p-n junction Junction between p-type and n-type areas of a semiconductor.

p-n-p-n transistor Hook transistor with n-type base, p-type emitter, and hook collector.

p-n-p transistor Junction transistor with n-type base, and p-type collector and emitter.

Point contact A sharp point placed on a semiconductor for making point-contact devices.

Point-contact diode A diode which uses a point contact to get a rectifying characteristic.

Point-contact transistor Old-style transistor made by forming junctions by the unpredictable process of electroforming.

Power gain Ratio of output power to signal input power, not to be confused with *collector efficiency*.

Power transistor A transistor, usually an alloy-junction type, made to handle high currents and high power.

p-type Semiconductor doped with an acceptor so holes are more plentiful than electrons.

-R-

Rate-grown transistor Junction transistor with junctions formed by varying the rate of the crystal's growth.

Recombination Simultaneous elimination of both an electron and a hole.

Rectifier Any device which has a non-symmetrical volt-ampere curve, and which therefore can be used to rectify a.c.; for example, *junction diode*.

Resistivity A property of a semiconductor directly related to the resistance to electricity; the reciprocal of conductivity.

Reverse bias Small-current, high-voltage bias as applied to a diode; opposite to forward bias.

Reverse current The small current that flows in a diode under reverse bias.

-S-

Saturation The low-resistance condition in a transistor when the collector voltage is very small.

Saturation current That portion of cutoff current not due to surface effects; do not confuse with *saturation*.

Saturation resistance The ratio of voltage to current in saturation.

Seed Special single crystal used to start the growth of large single crystals by the Czochralski technique.

Selenium Semiconductor used mainly in rectifiers.

Semiconductor Material which conducts by both electrons and holes.

Silicon Common semiconductor, used in transistors and diodes.

Small-signal analysis Consideration of only small excursions from the no-signal bias, so that the transistor can be represented by a linear equivalent circuit.

Source Electrode on a field-effect transistor.

Space-charge layer See *depletion layer*.

Spacistor Type of transistor relying on modulation of carriers injected into a depletion layer.

Stability Lack of tendency toward thermal runaway.

Stability factor A number which measures the stability of a transistor stage.

Stabilization Process of introducing stability into a circuit.

Surface barrier A barrier formed automatically at a surface due to trapped electrons held at the surface.

Surface-barrier transistor Transistor using surface barriers instead of p-n junctions.

Symmetrical transistor Transistor in which collector and emitter are made identical, so either can be used for either purpose.

-T-

Tandem transistor Two transistors in

one package, internally connected together.

Tetrode transistor Any of several types of transistors with four electrodes.

Thermal runaway Condition in which the dissipation in the transistor increases with higher temperature so fast that the temperature keeps rising.

Thermistor Temperature-sensitive resistor, usually made from a semiconductor.

Transistor Semiconductor device with three or more electrodes used for amplification.

Transistor action The physical mechanism of amplification in a junction transistor.

Transition layer, transition region See *depletion layer*.

Transition-layer capacitance See *depletion-layer capacitance*.

Transit time Average time it takes a minority carrier to diffuse from emitter to collector in a junction transistor.

Trapping Holding of electrons or holes by any of several mechanisms in a crystal, preventing the carriers from moving.

Traps Any of several imperfections in a crystal which can trap carriers.

-U-

Unijunction transistor Transistor made for switching circuits, having only one junction.

-V-

Varistor A semiconductor device with a symmetrical but nonlinear volt-ampere characteristic.

Voltage amplification, voltage gain Ratio of output voltage to input voltage.

-W-


Whisker A point contact.

-Z-

Zener diode A diode which breaks down at the Zener voltage, used for voltage regulators.

Zener voltage That reverse voltage at which a large current starts to flow, caused by breaking down the crystal.

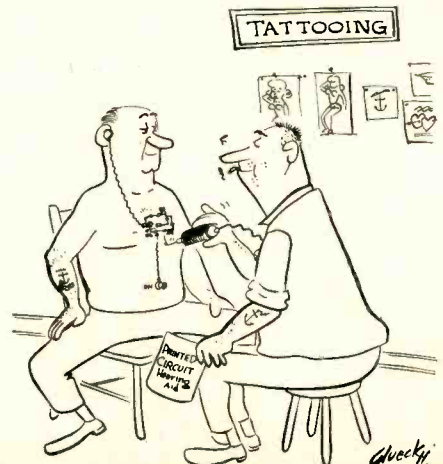Zone refining A technique for purifying crystals by passing a melted zone through the crystals, which drags the impurities with it. END



6-Band Portable TRANSISTOR



This 4-transistor trf receiver brings you the radio world between 100 kc and 20 mc

By J. E. PUGH, JR.

A TRF amplifier combined with a class-B detector and a bit of controlled regeneration makes possible a wide-range all-transistor portable receiver that is hard to beat in overall performance.

A tuning range of 100 kilocycles to 20 megacycles is broken into six steps. The lower limit of this range is determined by the physical size of the necessary coils and their Q. The upper limit is determined by the alpha-cutoff frequency of the rf transistors.

The long-wave band is a feature not ordinarily found in radios, and it will provide many hours of pleasure for anyone who enjoys getting off the conventional path occasionally.

The trf stage uses an rf transistor connected in a common-base circuit (see diagram) biased for class-A operation. Although the gain of the common base is less than that of the common-emitter circuit, it was selected because of its marked advantages in other respects. One of the most important advantages is its better frequency response compared with the common-emitter circuit—important for more uniform response over a wide range of frequencies. Also this circuit does not need neutralization while the common-emitter amplifier does. This results in a circuit that is stable, very simple and easy to align.

The common-base circuit has an additional advantage in that it has a much higher output impedance. This makes it possible to connect the collector directly to the top of rf transformer T2. In a common-emitter circuit the collector must be tapped down from the top of the coil for best results, complicating the band-switching problem.

A class-B detector is used because it is simple and has a high degree of sensitivity. A 2N112 was used in this circuit and in the photographs, and a 2N114 was in the trf stage. However the recently introduced 2N247 drift transistor was substituted when I found that it gave considerable improvement in performance at a much lower cost.

Regeneration is obtained by feeding some of the rf energy at the base of V2 back to V1's emitter through C6, a variable capacitor. This feedback reduces the rf resistance of the resonant cir-

cuits and increases their effective Q, improving the selectivity and sensitivity. Therefore, the actual circuit, so far, consists of an rf amplifier and a class-B detector having variable selectivity and sensitivity. The degree of the detector's selectivity and sensitivity above the normal point is determined by the amount of feedback. When feedback is set at minimum, the receiver can be used as a normal nonregenerative receiver with medium sensitivity and selectivity. When feedback is great enough, V1 oscillates, making CW reception possible.

The emitter voltage for V1 and V2 is set slightly above 3 volts by R13. This improves performance on the low-frequency end of the tuning range but also lowers the highest frequency at which regeneration can be obtained. Regeneration is smooth with *no dead spots up to the upper frequency limits.*

Capacitor C1 is a 9-180- μ f trimmer used to compensate for different antenna lengths. Once set, it need not be touched unless the antenna length is changed.

Band switching

Two two-pole six-position rotary switches handle the band switching. Separate switches are used so transformers T1 and T2 can be separated enough to prevent feedback. Six transformers are used at T1 and six at T2 to cover the tuning range. Each transformer at T1 and T2 has its own trimmer capacitor (C3 and C5, respectively), making a total of 12 trimmers for the two groups of transformers. Separate trimmers are used to permit best alignment for each band.

The circuit diagram shows only one transformer for T1 and one for T2. Trimmer capacitors C3 and C5 are in-

TRANSFORMER WINDING CHART

Transformer	Freq Range	Primary	Secondary*
T1-a	100 to 215 kc	Miller 6322	80 turns No. 32 either direction
T1-b	215 to 550 kc	Miller 6318	27 turns No. 32 either direction
T1-c	530 to 1400 kc	Miller 4513	9 turns No. 32 either direction
T1-d	1.4 to 4.0 mc	Miller 4508	12 turns No. 32 either direction
T1-e	4.0 to 10.0 mc	Miller 4504	5 turns No. 22 either direction
T1-f	10.0 to 20.0 mc	Miller 4501	4 turns No. 22 either direction
T2-a	100 to 215 kc	Miller 6322	145 turns No. 32 opposite T1-a secondary
T2-b	215 to 550 kc	Miller 6318	48 turns No. 32 opposite T1-b secondary
T2-c	530 to 1400 kc	Miller 4513	16 turns No. 32 opposite T1-c secondary
T2-d	1.4 to 4.0 mc	Miller 4508	16 turns No. 32 opposite T1-d secondary
T2-e	4.0 to 10.0 mc	Miller 4504	3 turns No. 22 opposite T1-e secondary
T2-f	10.0 to 20.0 mc	Miller 4501	2 turns No. 22 opposite T1-f secondary

NOTE: All secondaries except T1-d and T2-d are wound on the outer surface of the primary winding. The primaries of these two coils are wound in two sections spaced about 1/16 inch apart. The secondaries are wound in this spacing between the two sections. For further details see text.

*All secondaries enameled wire

RADIO

licated in the same manner. This is done to make the schematic easy to follow. The additional units would add no information since they are schematically identical. In the description that follows, the transformers will be called T1-a to T1-f and T2-a to T2-f, and the capacitors C3-a to C3-f and C5-a to C5-f.


The audio section of the receiver is entirely conventional and needs no explanation.

Bias stabilization is used in all stages to minimize transistor variations due to temperature changes. This is especially important in the rf circuits because a temperature change will cause a shift in the resonant response of the circuits if stabilization is not used. It also makes it possible to substitute transistors of a similar type without changing other component values.

Building the receiver



The front and back panels and the chassis are all made of XXP-26—a high-grade paper-base phenolic material—and are fastened together with 5/8-inch angle brackets. Large plastic supply houses carry this material. If you wish,

- R1, 5, 9, 12—1,000 ohms
- R2, 8, 11—3,300 ohms
- R3, 7, 10—18,000 ohms
- R4—39,000 ohms
- R6—pot, 5,000 ohms, audio taper
- R13—4,700 ohms
- All resistors 1/2-watt 10%
- BATT 1, 2, 3, 4—1.5-volt cells, penlight, flashlight
- C cell, or mercury cell (see text)
- C1—9-180 μ mf, trimmer
- C2—10-365 μ mf, 2-gang tuning capacitor
- C3-a-C3-f, C5-a-C5-f—3-35 μ mf, trimmer (El Menco type 403 or equivalent) (12 needed)
- C4, 12, 14—25 μ f, 10 volts, miniature electrolytics
- C6—10-365- μ mf tuning capacitor (Lafayette MS-215 or equivalent)
- C7, 8, 9—1 μ f, 200 volts, metallized paper, miniature
- C10—.001 μ f, tubular ceramic
- C11, 13—10 μ f, 12 volts, miniature electrolytics
- C15—2 μ f, 200 volts, metallized paper, miniature
- J—phone jack
- S1, 2—2-pole 6-position rotary, shorting type (Mallory 3126J)
- S3—spst toggle
- T1-a-T1-f, T2-a-T2-f—see transformer winding chart
- T3, 4—audio driver transformers: primary, 20,000 ohms; secondary, 1,000 ohms (Argonne AR-104 or equivalent)
- V1, 2—2N247 (RCA)
- V3, 4—CK722 (Raytheon)
- Dial, 5:1 ratio, 3-inch diameter (National Velvet Vernier or equivalent)
- Chassis—see text
- Bar knobs (2)
- Dial plates, 1-6 (2) (Mallory 376 or equivalent)
- Terminal strip, 2 screw lugs
- Battery holder
- Miscellaneous hardware

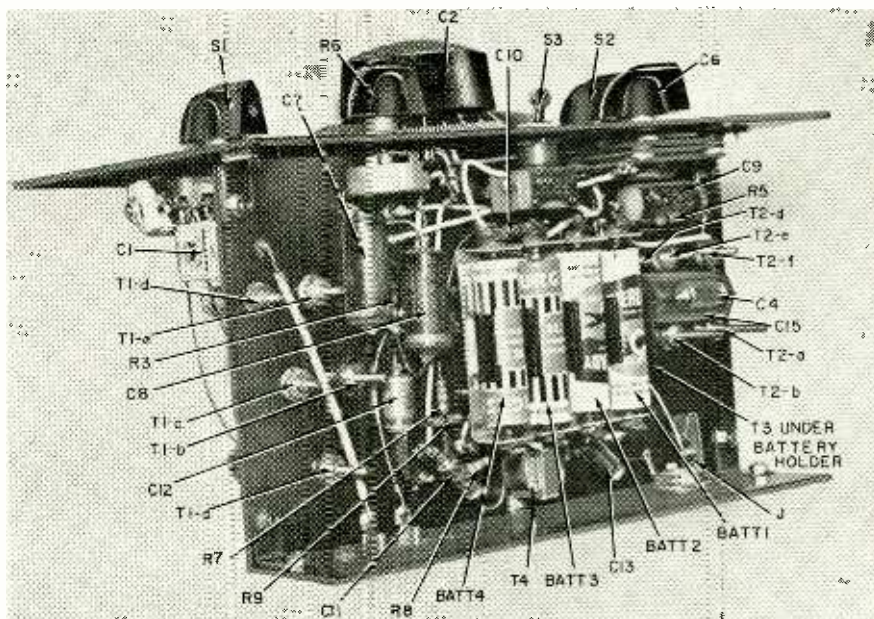

(Above) The underchassis may look crowded, but it really isn't. Don't forget, transformer T3 is mounted under the battery holder.

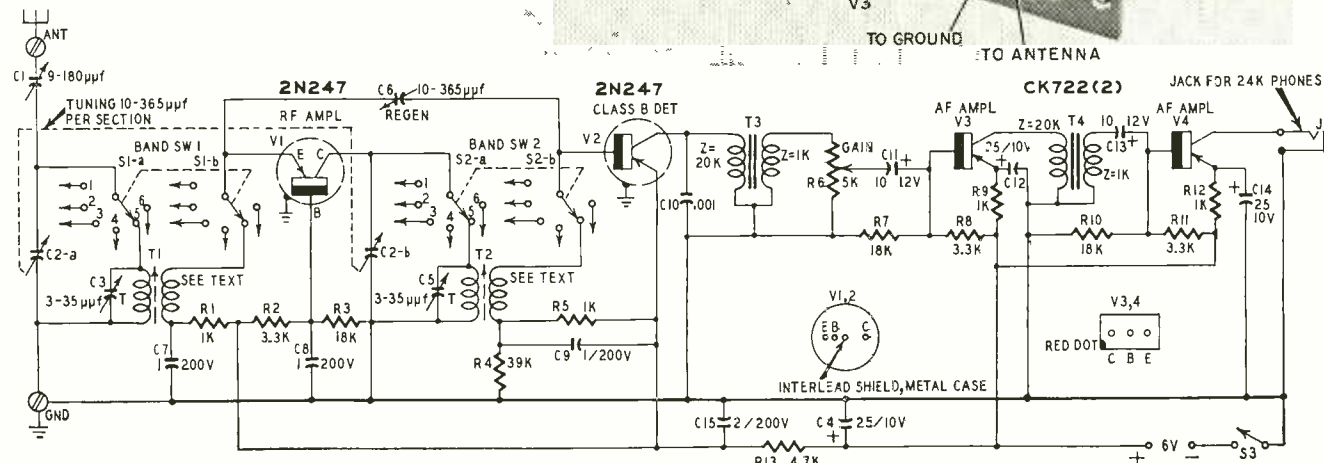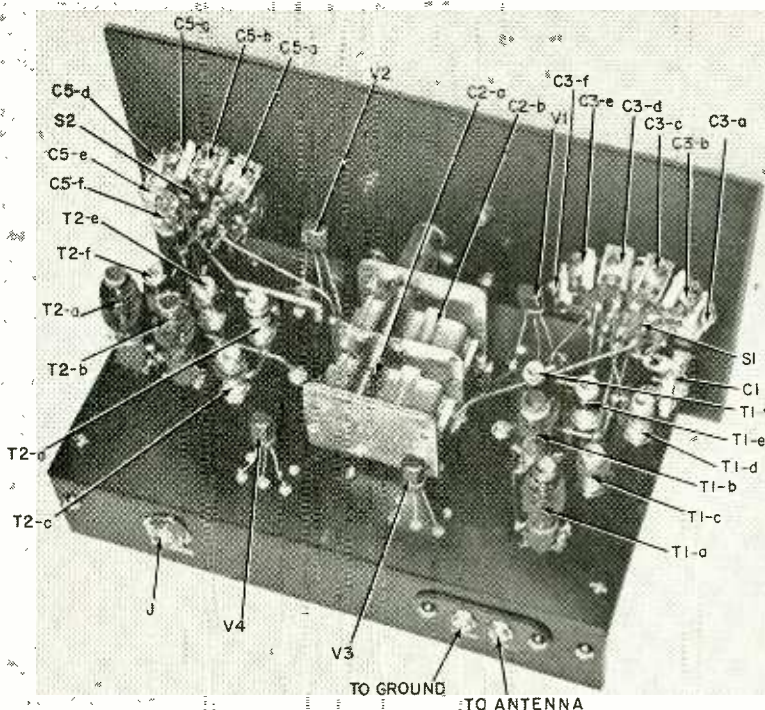(Below) Careful layout makes the set easy to wire. Headphone jack and antenna and ground connections are on the receiver's back panel.



Circuit of the four-transistor receiver.

the front and back panels can be metal, such as aluminum, and the chassis can be made of Bakelite. The front panel is about 1 inch wider than the chassis and back panel so the entire receiver can be housed in a wooden case. The front panel is $8\frac{3}{4} \times 5\frac{1}{2}$, the chassis $7\frac{3}{4} \times 4\frac{1}{2}$, and the back panel is $4\frac{1}{2} \times 1\frac{5}{8}$ inches. However, you can follow your own ideas on these dimensions and on the exact layout of parts.

Turret type terminal lugs are used for all connections on the chassis. All of these are USECO type 1290 except the two large ones used for ground terminals. These large lugs are USECO type 1320 and are located on both sides of the tuning capacitor between it and the coils (see photos). Swaging tools are needed to fasten both types of lugs and, if you want to avoid this investment, the USECO type 1300T lug, which is fastened with 4-40 nuts, can be used. These lugs and the swaging tools are available at Newark Electric Co., Chicago; Burstein-Applebee Co., Kansas City, Mo., and the Radio Shack, Boston, and others. A cheaper but not-as-neat terminal can be made from 4-40 x $\frac{1}{4}$ -inch screws, nuts and solder lugs.

A tuning dial with a drive ratio of about 5 to 1 should be used to aid in separating signals in the higher frequency range. I used a 3-inch diameter National *Velvet Vernier*. When buying the tuning capacitor, note the direction of rotation so that dial calibration (clockwise or counterclockwise) will be correct. Also note the shaft diameter as some capacitors have a $\frac{3}{8}$ -inch diameter while most dials take a $\frac{1}{4}$ -inch shaft. This problem can be solved by using a $\frac{3}{8}$ - to $\frac{1}{4}$ -inch shaft extender.

Trimmer capacitors C3-a to C3-f have their lower end (the end connected to the adjustment screw) soldered to a short length of No. 16 bus wire that circles about halfway around the bandswitch housing and connects to a shaft grounding lug. This lug is one of the type supplied with volume controls. Another length of No. 16 bus wire connects from this lug to the type 1320 ground lug next to the tuning capacitor. The other group of trimmers, C5-a to C5-f, is mounted in a similar manner on the other bandswitch. Both assemblies can be seen in the photos. These groups of trimmers replace the trimmers usually mounted on the tuning capacitor, and if the tuning capacitor is equipped with them they should be removed.

Winding the secondaries

Transformer winding data is given in the chart. As noted the secondaries can be in either direction but the T2 group must be opposite the T1 group to obtain regeneration. For example, the T1 group can spiral upward in a clockwise direction and this would make it necessary for the T2 group to spiral upward in a counterclockwise direction.

The Miller 6300 series of coils (used

for T1-a, T1-b, T2-a, T2-b) have both ends of the existing winding connected to lugs on a fiber sleeve close to the base of the winding. Carefully unsolder the outer end from its lug and remove a few turns to provide enough lead to reach the bandswitch. The unused lug is now used as a tie point for the hot end of the secondary. The lower ends of the secondaries of the T1 group all connect to a single lug located between V1 and the front panel, and the lower ends of the T2 group connect to a lug between V2 and the front panel.

When fastening the Miller 4500 series coils to the chassis, use a wrench to hold the hex nut on the top side of the coil form as the coil will not take any rough handling. After the coil is fastened to the chassis a very small triangular spring, found among the hardware supplied with each coil, is put into position to put tension on the core-adjusting screw.

An easy way to do this is first to turn the adjustment screw up until it is flush with the threaded housing. Then lay the wide side of the spring in the slot in the side of this housing and push the other sides of the spring over the end of the housing. After this, the adjustment screw can be backed out of the housing and oiled with a light oil.

Shaft grounding lugs can be used on the regeneration and gain controls where a nonmetallic front panel is used. Otherwise they will not be needed.

A convenient method for mounting the battery box is to fasten four $\frac{5}{8}$ -inch threaded posts to it, using existing holes near the corners of the box. These posts are mounted on the receiver chassis with 6-32 flat-head screws in countersunk holes so that the heads of the screws clear the underside of the tuning capacitor's frame.

Before soldering any parts into place, mark the terminal lug to which each transistor collector will be connected with a small dab of paint on both sides of the chassis. This makes wiring easier and helps prevent mistakes.

Before soldering the transistors in place check carefully to see that no mistakes have been made because the rf transistors can easily be ruined.

Alignment procedure

Connect a short antenna, about 10 feet long, and a ground to the set. Now back off capacitor C1 about $1\frac{1}{2}$ turns from full capacitance. The signal generator should be the modulated type with a frequency range covering 100 kc to 20 mc but, if one is not available, the harmonics of a low-frequency generator can be used to cover the higher frequencies.

Loosely couple the generator to the antenna by attaching a short length of wire to its hot terminal.

The output meter can be any ac voltmeter with an impedance of 1,000 ohms per volt or more and a 0-to-5- or 10-volt scale. This meter can be connected across the headphone terminals.

Now adjust the signal generator to 100 kc, set the bandswitches to position 1, set the tuning capacitor for maximum capacitance, and adjust T1-a and T2-a cores for maximum output. Next set the signal generator to the upper frequency for band 1, set the tuning capacitor for minimum capacitance and adjust the C3-a and C5-a for maximum output. Repeat these adjustments until maximum output is obtained at each end of band 1.

Switch to band 2 and adjust transformers T1-b and T2-b and trimmers C3-b and C5-b in the same manner, allowing a small frequency overlap for the two bands. In a similar manner adjust the corresponding coils and trimmer capacitors for the remaining bands.

It is not necessary to switch the battery off when changing bands. The switches are the shorting (make-before-break) type and do not open any circuits, therefore there is no chance of damaging the transistors when switching.

When aligning the receiver keep the signal generator adjusted for minimum usable signal to prevent overloading. Also keep the REGENERATION control set close to the oscillation point to obtain best alignment. This is done because this control has a slight detuning effect on the resonant circuits as it is varied.

After alignment is completed obtain the dial reading for some known station, such as one of the WWV frequencies or a broadcast station, on the high end of one of the bands. Now, if the antenna length is ever changed, simply set the dial to this predetermined reading and adjust antenna trimmer C1 until the station falls at the correct dial reading. All bands will be corrected automatically without further adjustment.

This receiver is suitable for use during a Conelrad alert. Mark the dial at 640 and 1240 kc for easy adjustment during such an alert. END

AES LECTURE NOTES

A volume containing detailed notes on the first half of the Audio Engineering Society's (AES) 1957-58 lecture series on "Principles and Practices of Tape and Disc Recordings" is now available.


The book covers the 15 autumn and winter lectures by authorities in the audio field and can be ordered from Sumner Hall, Lecture Series Chairman, Amityville, N. Y. The price of \$5 for members and applicants of AES and \$7.50 for nonmembers also includes a second volume of notes, on the present series of lectures, which will be published in June. Subscribers to the lecture series receive these notes at no charge.



This new dual-concentric control by Mallory enables a distributor to custom-build an exact replacement from selected units, rigidly locked together, in just 30 seconds. You can stop "touring the town" looking for hard-to-find "factory-built" replacements when you start using the new Mallory "Sta-Loc" controls.



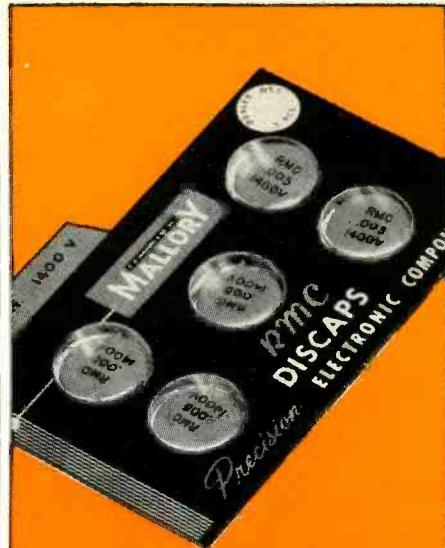Tops in capacitors for every service need . . . the Mallory FP line. Now, the new and improved design gives you even greater dependability, lighter weight, and longer life, thanks to the exclusive new internal structure that eliminates "potting". Still retains the exclusive etched cathode construction . . . hum-free performance.




Long the original equipment standard, now available for service . . . it's the Mallory-RMC Discap, a product of the world's largest maker of ceramic disc capacitors. Look for the handy 3" x 5" file-card package. It's easy to stock, and easy to use. Hangs over your bench, tells you at a glance what capacitors you have.

Look to Mallory...



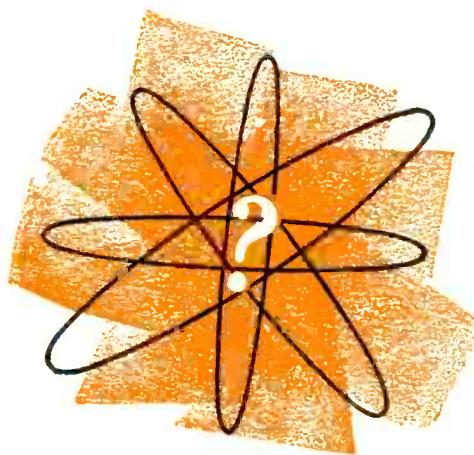The new portable car radio depends on Mallory mercury battery power, as do thousands of personal portables. Cash in on this profitable replacement market with a ready stock. Mercury batteries, pioneered by Mallory, have long shelf life, and a long, dependable service life. Mallory also offers a broad line of zinc-carbon batteries.



And in your future . . . who knows what electronic marvels will become reality, and thus become new service business for you. Mallory will continue to develop components for new circuits, and replacement parts to service these new needs. You can continue to depend on Mallory leadership, ingenuity, and your Mallory Distributor.



It's a "Gem" of a package—5 Mallory "Gem" tubular capacitors in a trim, easy-to-use dispenser. Keeps your stock clean and fresh—keeps kinks out of lead wires. Look for it on your distributor's self-service display—you can't find a better capacitor than these rugged, moisture-proofed Mallory "Gems".



You can add a modern touch to service jobs by replacing with the new Mallory "push-pull" line switch. The receiver can be turned on or off without rotating the control... warms up to the volume level in use when the set was turned off. Mallory offers a complete line of replacement controls featuring this modern touch.



For longer, more trouble-free auto radio servicing, especially on critical jobs, replace with the new Mallory Gold Label vibrator. For economy jobs, use the new Mallory Highlander in the handy ten-pack carton. Both lines feature Mallory's exclusive buttonless contact design for longer, quieter, more efficient service.

...for Leadership... and Profits

for Innovations to Meet Your Needs... Dependable Components of Precision Quality

There is evidence aplenty on these pages of dynamic growth in the Mallory line. All of these are developments of the past 12 months—continuation of years of progressive pioneering by Mallory to meet the needs of the service industry.

As you face the problems of repairing increasingly complex equipment, you can depend on Mallory for the proven quality that prevents "come-backs"—

makes your service jobs right the first time! Depend on Mallory, too, for new designs that keep pace.

Perhaps you have associated the Mallory name only with vibrators... or electrolytics... or volume controls. If so, you should meet the rest of the big Mallory family of service-engineered components. Your local Mallory distributor is prepared to introduce you.

P. R. MALLORY & CO. Inc.
MALLORY

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

- Capacitors
- Vibrators
- Resistors
- Power Supplies
- Mercury and Zinc-Carbon Batteries
- Controls
- Switches
- Rectifiers
- Filters

Transistors in the TV set

By LOUIS E. GARNER, JR.

Part I:—Been wondering what transistor TV circuitry looks like? Here are the first sections of such a receiver—the front end, video if strip, video detector and video amplifiers



SEVERAL years ago one of our leading electronic manufacturers, RCA, designed, assembled and demonstrated an all-transistor (except for the CRT) television receiver. This early set used a comparatively small picture tube and was put in a clear plastic case for demonstration and display purposes. It employed a number of specially selected types of the now nearly obsolete point-contact transistor.

RCA was (and is) not the only firm interested in transistor TV receivers. Nearly every major television receiver manufacturer, as well as most semiconductor manufacturers, has investigated transistor TV circuits, and a number of firms have assembled their own sets. A few months ago, for example, Motorola placed on display two prototypes of a fully transistorized portable TV receiver (see *What's New, RADIO-ELECTRONICS*, March, 1958). The Motorola receiver uses a 14-inch picture tube and is powered by a set of self-contained rechargeable nickel-cadmium batteries. Its performance equals that of conventional (vacuum-tube) line-operated portables.

While no major television receiver manufacturer is producing an all-transistor set today, such receivers will be manufactured in the future and transistor designs will, one day, become standard for all portable receivers. In fact, due to their low power consumption and long life, there is the real possibility that they will eventually replace vacuum-tube sets in home as well as portable applications. The 31-transistor Motorola prototype, for example, requires only 12 watts for operation, compared to a minimum of 105 watts for a conventional portable.

In addition to their low power requirements, transistors offer many advantages over vacuum tubes in TV receiver design. They are smaller, lighter, more rugged and more efficient

than tubes, and they operate at much lower temperatures. Thus, the interior of a transistor TV receiver will run *much cooler* than a comparable vacuum-tube set. This is extremely important in determining the service life of electronic components. As every service technician knows, one of the major factors contributing to component breakdown is the high temperatures developed within a set. Excessive heat causes electrolytic capacitors to dry out, certain types of insulation to melt or deteriorate, and other components to operate above their normal ratings.

Three barriers have limited the use of transistors in TV circuits in the past: the lack of suitable types for vhf and high-power applications, lack of circuit design knowledge and the high cost of transistors compared to vacuum tubes. The first two have been overcome for practical purposes. Vhf and power transistors are, today, readily available from major manufacturers in production quantities, and the design experience obtained in transistorizing military electronic equipment where

cost is not a factor (such as airborne radar equipment) can be applied directly to the design of transistor TV sets.

The remaining barrier, cost, is being whittled down rapidly. With improved production techniques, the transistor yield rate has been going up and production figures have soared. As a result, transistor prices have dropped continuously—almost on a month-to-month basis. There is good reason to believe that ultimately they will drop *below* those of vacuum tubes with corresponding characteristics. After all, as far as internal construction is concerned, a transistor is simpler than a vacuum tube.

The home experimenter and electronics hobbyist interested in new circuits, the service technician who may be called on to repair transistor TV receivers, and the technically minded consumer who may one day buy such a set, all have an interest in the circuitry and performance of transistor TV receivers.

As far as general circuitry is con-

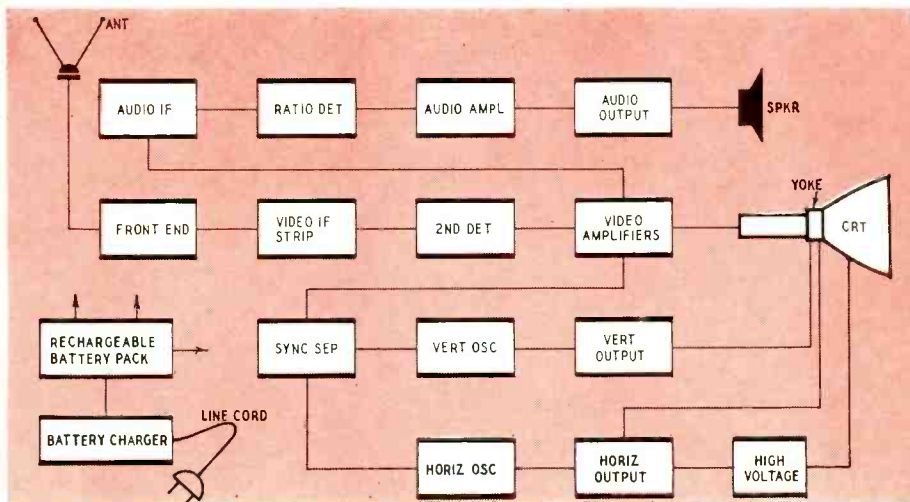


Fig. 1—Block diagram of an all-transistor TV receiver.

ROHN TOWERS cover 3 fields

Bigger Profits for You!




Rohn Manufacturing Company is the largest *exclusive* manufacturer of home television towers! Thousands of distributors, dealers and servicemen have handled, sold and installed Rohn Towers for years! They've proved to themselves that *there's more money in Rohn Towers and accessories than any other line!* Rohn Towers now *dominate the field* and profits for those handling this line are better than ever. Why? Because Rohn offers profits in all 3 major tower fields:

1

HOME TV

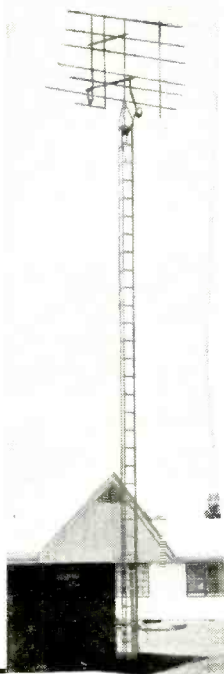By far the biggest usage of Rohn products has been and still is for home TV installations. In addition to finest of self-supporting towers, the Rohn line includes telescoping masts, tubing, roof towers and all other types of accessories for installations of all kinds. Wise dealers and servicemen rely *entirely* on the Rohn line for *all* installation requirements. This means **BIGGER PROFITS.**



2

COMMUNICATIONS


Many distributors, dealers and servicemen are making **EXTRA PROFITS** by stocking or handling the heavier type Rohn Towers that are suitable for communications purposes. There is a demand in *every area* for radio communications towers, micro-wave towers, radio telephone towers and industrial towers. You can supply this need in your area. Special new literature is available for your use.



3

AMATEUR USE

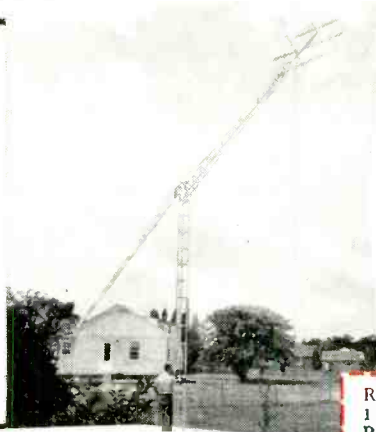Another major field of usage for Rohn Towers is in the field of amateurs and experimenters. The especially designed "fold-over" tower is the *best in the field* for the amateur because it allows working on the antenna *on the ground*. Thousands of amateurs use Rohn Towers with a tremendous demand still to be sold. You can supply this demand in your area and capture **BIG PROFITS** for yourself.



Send the coupon or write or phone today for the field that you are neglecting or those that interest you the most. ▶

ROHN Manufacturing Company

116 LIMESTONE, BELLEVUE
PEORIA, ILLINOIS Phone 4-9156

look at these ROHN exclusives

● HOT DIPPED GALVANIZED

The finest, most durable finish is available for ROHN Towers and accessories . . . all done entirely on the ROHN premises under careful ROHN supervision.

● UNEQUALLED DESIGN AND ENGINEERING

ROHN is the only design that has stood up over the years. ROHN has been first and foremost . . . and always the *leader* in new products to meet the changing demands.

● MASS PRODUCTION FOR LOW COSTS

ROHN was the first to utilize mass production techniques to build a superior tower at the most competitive prices. This means no sacrifice in quality yet far greater profits for you.

● UNIVERSAL CUSTOMER ACCEPTANCE

Thousands and thousands of installations prove the ROHN line first in customer satisfaction.

● PIONEER MANUFACTURERS

Pioneers in tower manufacturing—and today one of the world's largest manufacturers of this type equipment. The ROHN Company was built on satisfaction on the part of distributor, dealer and customer alike.

● COMPLETE LINE

Only ROHN offers a full line—*one* dependable one-stop source for all TV installation equipment. Save headaches, save shipping costs, save time . . . use ROHN unequalled service *exclusively*.

ROHN MANUFACTURING COMPANY

116 Limestone, Bellevue
Peoria, Illinois

GENTLEMEN: Please send me the catalog and information on the following:

TV Towers Amateur Towers
 Communications Towers Full line
of Rohn products


NAME _____

FIRM _____

ADDRESS _____

CITY _____ STATE _____

When a Serviceman Needs a Friend

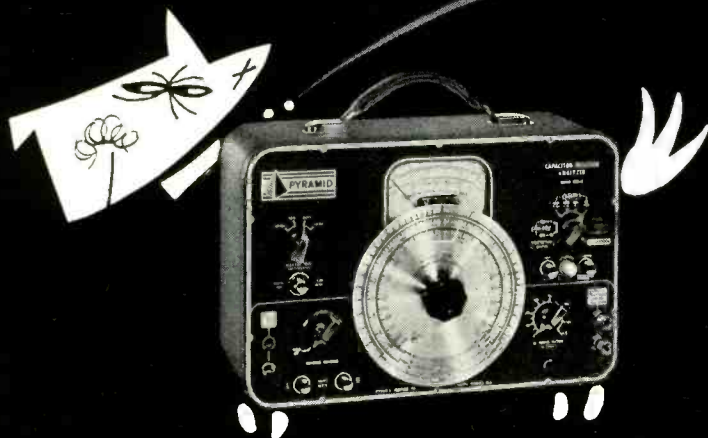

He naturally turns to Pyramid's CRA-2 Capacitor-Resistor Analyzer . . . because with this versatile, multi-purpose test instrument, all the guesswork is taken out of trouble shooting. Perfect for work in industrial and military electronics, black and white, and color television, and all other related fields. The CRA-2 incorporates the most advanced test features:

- "Quick Check" in circuit test for Open Circuits, Short Circuits, Intermittents, High RF Impedance, and High Power Factor.
- Speedy accurate checks for Capacitance, Power Factor, Resistance, Insulation-Resistance and Leakage Current.
- Precision meter for accurate readings of Leakage Current, Applied Voltage and Insulation Resistance.
- Combined Wien and Wheatstone Bridge.
- Accurate Vacuum-Tube Ohmmeter Circuit.

Write today for complete information about the Pyramid CRA-2 Capacitor-Resistor Analyzer. Remember! when a serviceman needs a friend, he can always depend on Pyramid.

CAPACITORS—RECTIFIERS
FOR ORIGINAL EQUIPMENT—AND REPLACEMENT

PYRAMID
ELECTRIC COMPANY
North Bergen, New Jersey

TELEVISION

cerned, the block diagram of a typical transistor TV receiver (Fig. 1) is not much different from that of a tube set. Nor should there be much difference in overall performance. A commercially manufactured transistor TV receiver, to compete with vacuum-tube sets, must perform as well as (if not better than) they do. Price-wise, the first transistor TV receivers will be more expensive than vacuum-tube sets but, eventually, should be competitive.

With similar block diagrams and comparable performance, the real differences between tube and transistor-operated TV receivers will be found in the actual circuitry used in each section of the sets. Let us examine some of the circuits that well may be used in future TV receivers.

The front end

The receiver's rf section (front end) receives, selects and converts the incoming TV sound and picture carriers into if signals carrying the full audio and video modulation of the original rf carriers. In addition, it *may* amplify the original signals prior to conversion to if signals.

If the receiver is designed to operate only in the vhf band (through channel 13), we know that the transistors will have to handle signals up to about 216 mc. This means that the front end will have to use vhf units. Currently, the only vhf transistors in full production are the MADT's produced by Lansdale Tube Co. (Philco), the junction tetrode transistors made by G-E and Texas Instruments and the drift transistors introduced by RCA. Any of these types might be used in the front end.

A Philco 2N502, an MADT type, can supply a power gain of about 10 db as an rf amplifier at 200 mc. Similar gain should be possible if it were used as a converter.

At present, vhf transistors are harder to manufacture and hence are much more expensive than lower-frequency units. Therefore, in an economy TV receiver, there might be a certain amount of skimping in front-end design to compensate for the comparatively higher prices of such transistors. Thus, the front end in such a set may consist of little more than a vhf local oscillator, a diode mixer and appropriate tuned circuits to select the incoming signal and to set oscillator frequency. In a more expensive receiver, and in later models, the front end might include one or more stages of rf amplification and a converter, or a mixer with a separate local oscillator. The schematic diagram for such a front end is shown in Fig. 2.

Vhf p-n-p transistors V1 and V2 are, respectively, the rf amplifier and converter. The common-emitter configuration is used for both stages. To simplify the circuit, I have assumed that the unit uses a continuous-tuning arrangement on each band. The high-low bandswitch has been omitted. In many commercial receivers, however, separate



Model TD-55 — TUBE TESTER . . . Total Price \$26.95 — Terms: \$6.95 after 10 day trial, then \$5.00 per month for 4 months.



Model TW-11 — TUBE TESTER . . . Total Price \$47.50 — Terms: \$11.50 after 10 day trial, then \$6.00 per month for 6 months.



Model TV-12 — TRANSCONDUCTANCE TUBE TESTER . . . Total Price \$72.50 — Terms: \$22.50 after 10 day trial, then \$10.00 per month for 5 months.



Model 770-A — VOLT-OHM-MILLIAMMETER . . . Total Price \$15.85 — Terms: \$3.85 after 10 day trial, then \$4.00 per month for 3 months.

SHIPPED ON APPROVAL NO MONEY WITH ORDER NO C.O.D.

Superior's New Model TD-55 EMISSION TYPE TUBE TESTER

FOR } The Experimenter or Part-time Serviceman, who has delayed purchasing a higher priced Tube Tester.
The Professional Serviceman, who needs an extra Tube Tester for outside calls.
The busy TV Service Organization, which needs extra Tube Testers for its field men.

Speedy, yet efficient operation is accomplished by: 1. Simplification of all switching and controls. 2. Elimination of old style sockets used for testing obsolete tubes (26, 27, 57, 59, etc.) and providing sockets and circuits for efficiently testing the new Noval and Sub-Minar types.

You can't insert a tube in wrong socket
It is impossible to insert the tube in the wrong socket when using the new Model TD-55. Separate sockets are used, one for each type of tube base. If the tube fits in the socket it can be tested.

"Free-point" element switching system
The Model TD-55 incorporates a newly designed element selector switch system which reduces the possibility of obsolescence to an absolute minimum. Checks for shorts and leakages between all elements

The Model TD-55 provides a supersensitive method of checking for shorts and leakages up to 5 Meg-ohms between any and all of the terminals.

Elemental switches are numbered in strict accordance with R.M.A. Specifications.

The 4 position fast-action snap switches are all numbered in exact accordance with the standard R.M.A. numbering system. Thus, if the element terminating in pin No. 7 of a tube is under test, button No. 7 is used for that test.

Complete with carrying case **\$26.95** NET

Superior's STANDARD PROFESSIONAL New Model TW-11 TUBE TESTER

- Tests all tubes, including 4, 5, 6, 7, Octal Lockin, Hearing Aid, Thyatron, Miniatures, Sub-miniatures, Novals, Sub-minars, Proximity Fuse Types, etc.

- Uses the new self-cleaning Lever Action Switches for individual element testing. All elements are numbered according to pin-number in the RMA base numbering system.

- Model TW-11 does not use combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket.

- Free-moving built-in roll chart provides complete data for all tubes. Printed in large easy-to-read type.

NOISE TEST: Phono-jack on front panel for plugging in either phones or external amplifier detects microphonic tubes or noise due to faulty elements and loose internal connections.

EXTRAORDINARY FEATURE
SEPARATE SCALE FOR LOW-CURRENT TUBES
Previously, on emission-type tube testers, it has been standard practice to use one scale for all tubes. As a result, the calibration for low-current types has been restricted to a small portion of the scale. The extra scale used here greatly simplifies testing of low-current types.
Housed in hand-rubbed oak cabinet

\$47.50 NET

Superior's New Model TV-12 TRANSCONDUCTANCE TUBE TESTER

★ Employs improved **TRANS-CONDUCTANCE** circuit.

An in-phase signal is impressed on the input section of a tube and the resultant plate current change is measured. This provides the most suitable method of simulating the manner in which tubes actually operate in Radio & TV receivers, amplifiers and other circuits. Amplification factor, plate resistance and cathode emission are all correlated in one meter reading.

★ **NEW LINE VOLTAGE ADJUSTING SYSTEM.**
A tapped transformer makes it possible to compensate for line voltage variations to a tolerance of better than 2%.

★ **SAFETY BUTTON**—protects both the tube under test and the instrument meter against damage due to overload or other form of improper switching.

EXTRA FEATURE
Model TV-12 Also Tests Transistors!

A transistor can be safely and adequately tested only under dynamic conditions. The Model TV-12 will test all transistors in that approved manner, and quality is read directly on a special "transistor only meter scale."

Housed in hand-rubbed oak cabinet

\$72.50 NET

Superior's New Model 770-A POCKET-SIZED VOLT-OHM MILLIAMMETER

USING THE NEW "FULL VIEW" METER
71% MORE SCALE AREA

Occupies exactly the same space used by the older standard 2 1/2" Meters, yet provides 71% more scale area. As a result, all calibrations are printed in large easy-to-read type.

• Housed in round-cornered, molded case. Beautiful black etched panel.

6 A.C. VOLTAGE RANGES: 0-15/30/150/300/1500/3000 Volts • 6 D.C. VOLTAGE RANGES: 0-7.5/15/75/150/750/1500 Volts • 2 RESISTANCE RANGES: 0-10,000 Ohms • 0-1 Megohm • 3 D.C. CURRENT RANGES: 0-15/150 Ma • 0-1.5 Amps. • 3 DECIBEL RANGES: -6 db to +18 db, +14 db to +38 db, +34 db to +58 db.

Complete with test leads

\$15.85 NET

USE APPROVAL FORM ON NEXT PAGE NO INTEREST OR FINANCE CHARGES ADDED!

We invite you to try before you buy any of the models described on this and the following page. If after a 10 day trial you are completely satisfied and decide to keep the Tester, you need send us only the down payment and agree to pay the balance due at the monthly indicated rate.

If not completely satisfied, you are privileged to return the Tester to us, cancelling any further obligation.

TRY FOR 10 DAYS

before you buy!
then if satisfactory pay in easy, interest free,
monthly payments. See coupon below.

Superior's New
Model 77

VACUUM TUBE VOLTMETER WITH NEW 6" FULL-VIEW METER

Compare it to any peak-to-peak V. T. V. M. made by any other manufacturer at any price!

- ✓ Model 77 completely wired and calibrated with accessories (including probe, test leads and portable carrying case) sells for only \$42.50.
- ✓ Model 77 employs a sensitive six inch meter. Extra large meter scale enables us to print all calibrations in large easy-to-read type.
- ✓ Model 77 uses new improved SICO printed circuitry.
- ✓ Model 77 employs a 12AU7 as D.C. amplifier and two 9006's as peak-to-peak voltage rectifiers to assure maximum stability.
- ✓ Model 77 uses a selenium-rectified power supply resulting in less heat and thus reducing possibility of damage or value changes of delicate components.
- ✓ Model 77 meter is virtually burn-out proof. The sensitive 400 microampere meter is isolated from the measuring circuit by a balanced push-pull amplifier.
- ✓ Model 77 uses selected 1% zero temperature coefficient resistors as multipliers. This assures unchanging accurate readings on all ranges.

AS A DC VOLTMETER: The Model 77 is indispensable in Hi-Fi Amplifier servicing and a must for Black and White and color TV Receiver servicing where circuit loading cannot be tolerated.

AS AN AC VOLTMETER: Measures RMS values if sine wave, and peak-to-peak value if complex wave. Pedestal voltages that determine the "black" level in TV receivers are easily read.

AS AN ELECTRONIC OHMMETER: Because of its wide range of measurement leaky capacitors show up glaringly. Because of its sensitivity and low loading, intermittents are easily found, isolated and repaired.

Model 77 comes complete with operating instructions, probe and test leads. Use it on the bench — use it on calls. A streamlined carrying case, included at no extra charge, accommodates the tester, instruction book, probe and leads. Operates on 110-120 volt 60 cycle. Only

\$42.50
NET



Model 77 — VACUUM TUBE VOLTMETER
... Total Price \$42.50 — Terms: \$12.50
after 10 day trial, then \$6.00 per month
for 5 months.

Superior's New
Model 76

ALL PURPOSE BRIDGE

IT'S A CONDENSER BRIDGE IT'S A RESISTANCE BRIDGE IT'S A SIGNAL TRACER IT'S A TV ANTENNA TESTER

Specifications

- ✓ **CAPACITY BRIDGE SECTION**
4 Ranges: .00001 Microfarad to .005 Microfarad; .001 Microfarad to .5 Microfarad; .1 Microfarad to 50 Microfarads; 20 Microfarads to 1000 Microfarads. Will also measure the power factor of all condensers from .1 to 1000 Microfarads.
- ✓ **RESISTANCE BRIDGE SECTION**
2 Ranges: 100 ohms to 50,000 ohms; 10,000 ohms to 5 megohms.
- ✓ **SIGNAL TRACER SECTION**
With the use of the R.F. and A.F. Probes included

with the Model 76, you can make stage gain measurements, locate signal loss in R.F. and Audio stages, localize faulty stages, locate distortion and hum, etc.

- ✓ **TV ANTENNA TESTER SECTION**
Loss of sync., snow and instability are only a few of the faults which may check the TV antenna first? Locates a break in any TV antenna and measures the location of the break in feet from the set terminals. Complete with R.F. and A.F. probes and test leads.

\$26.95
NET



Model 76 — ALL PURPOSE BRIDGE ...
Total Price \$26.95 — Terms: \$6.95 after
10 day trial, then \$5.00 per month for 4
months.

Superior's New
Model TV-50

GENOMETER

7 Signal Generators in One!

- ✓ R.F. Signal Generator for A.M.
- ✓ Audio Frequency Generator
- ✓ Color Dot Pattern Generator
- ✓ R.F. Signal Generator for F.M.
- ✓ Bar Generator
- ✓ Marker Generator
- ✓ Cross Hatch Generator

R.F. SIGNAL GENERATOR: 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 180 Megacycles on powerful harmonics.
VARIABLE AUDIO FREQUENCY GENERATOR: Provides a variable 300 cycle to 20,000 cycle peaked wave audio signal.
BAR GENERATOR: Pattern consists of 4 to 16 horizontal bars or 7 to 20 vertical bars.
CROSS HATCH GENERATOR: The pattern consists of non-shifting horizontal and vertical lines interlaced to provide a stable cross-hatch effect.

DOT PATTERN GENERATOR (FOR COLOR TV): The Dot Pattern projected on any color TV Receiver tube by the Model TV-50 will enable you to adjust for proper color convergence.
MARKER GENERATOR: The following markers are provided: 189 Kc., 262.5 Kc., 456 Kc., 600 Kc., 1000 Kc., 1400 Kc., 1600 Kc., 2000 Kc., 2500 Kc., 3579 Kc., 4.5 Mc., 5 Mc., 10.7 Mc., (3579 Kc. is the color burst frequency.)
Complete with shielded leads ...

\$47.50
NET



Model TV-50 — GENOMETER ... Total
Price \$47.50 — Terms: \$11.50 after 10
day trial, then \$6.00 per month for 6
months.

MOSS ELECTRONIC DISTRIBUTING CO., INC.
Dept. D-467 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked on approval. If completely satisfied I will pay on the terms specified with no interest or finance charges added. Otherwise, I will return after a 10 day trial positively cancelling all further obligation.

Name

Address

City Zone State

All prices net, F.O.B., N.Y.C.

- Model TD-55 Total Price \$26.95
\$6.95 within 10 days. Balance \$5.00
monthly for 4 months.
- Model TW-11 Total Price \$47.50
\$11.50 within 10 days. Balance \$6.00
monthly for 6 months.
- Model TV-12 Total Price \$72.50
\$22.50 within 10 days. Balance \$10.00
monthly for 5 months.
- Model 770-A Total Price \$15.85
\$3.85 within 10 days. Balance \$4.00
monthly for 3 months.
- Model 77 Total Price \$42.50
\$12.50 within 10 days. Balance \$6.00
monthly for 5 months.
- Model 76 Total Price \$26.95
\$6.95 within 10 days. Balance \$5.00
monthly for 4 months.
- Model TV-50 Total Price \$47.50
\$11.50 within 10 days. Balance \$6.00
monthly for 6 months.

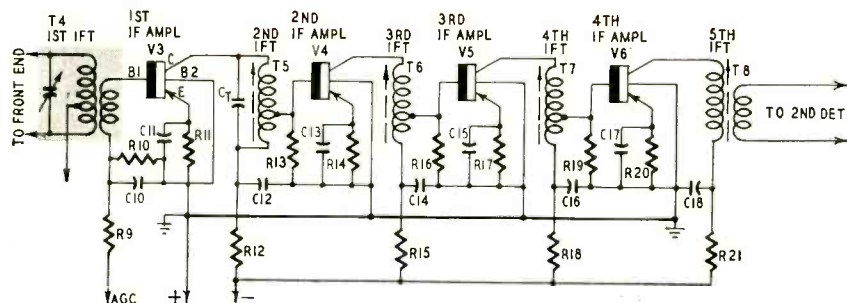


Fig. 3—Video if strip. Four stagger-tuned if amplifier stages are used.

rent due to agc action and, if C_T were not included in the circuit, this could result in circuit detuning.

Interstage if transformers T5, T6 and T7 are stepdown autotransformers. They are tapped down to provide an impedance match between the high-impedance collector circuit of one stage and the low-impedance base circuit of the succeeding one. Thus, T5 provides a match between V3's output and V4's input circuit, T6 provides an impedance match between V4 and V5, while T7 is tapped to provide a match between V5's collector and V6's base circuits.

Capacitors C12, C14, C16 and C18 operate with resistors R12, R15, R18 and R21, respectively, to form decoupling networks for their corresponding stages. Three of these decoupling resistors also have a secondary function. V4's base bias is supplied through a voltage divider made up of V3's collector decoupling resistor (R12) and V4's base resistor R1. In the same way, V4's decoupling resistor (R15) and V5's base resistor R16 supply base bias current for V5. And, finally, V6's base bias is supplied by a voltage divider made up of V5's decoupling resistor R18 and V6's base resistor R19.

In each stage, the emitter resistor and its appropriate bypass capacitor serve the dual function of stabilizing stage operation and of supplying the reverse bias for each transistor's second base connection (B2) necessary for true tetrode operation. R11 and C11 do this job for V3, R14 and C13 for V4, R17 and C15 for V5, and R20 and C17 for V6.

Individual stage gain could be controlled by varying the amount of reverse bias applied to the second base electrode in each stage. Thus, an effective overall gain control could be achieved by applying a separate controllable bias to the transistors' second base connections (B2). In some receivers, a similar arrangement also could be used for agc action. The agc control voltage could be fed to the second base connections.

The amplified if carrier signals appearing across the last if transformer (T8) are coupled to the second detector.

Video detector and amplifier

The video second detector strips the video modulation from the video if carrier and, at the same time, mixes

the audio and video if carriers to provide a new audio if carrier at 4.5 mc. Both vacuum-tube and semiconductor diodes are used as second detectors in present-day (vacuum-tube) TV receivers. A semiconductor diode could be used in a similar application in an all-transistor set. However, second-detector action also can be obtained from a transistor amplifier stage biased almost to cutoff—that is, biased for class-B operation. Such a detector might be preferred because it supplies higher gain than a simple diode detector.

The video amplifier must be reasonably flat to better than 4 mc and should provide good gain with minimum phase shift. A two-stage transistor amplifier could be expected to yield a gain comparable to (or slightly better than) that obtained from a single pentode vacuum-tube stage. Therefore, we can expect the video amplifier to be a two- or three-stage circuit.

If present-day cathode-ray tubes are used in a transistor receiver, chances are that the video amplifier output stage would have to use a high-voltage transistor—one that can safely withstand a collector-emitter voltage of 80 to 100—to supply a big enough video signal to drive the C-R tube and produce a picture of normal contrast. However, some work has been done toward developing a special picture tube for transistor TV applications. This tube requires relatively little signal drive and can be used with low-voltage transistors. There is a good chance that such tubes will be available by the time full-scale receiver production has started. Still later, we may

expect to see flat semiconductor picture "tubes."

Since the video second detector and video amplifiers must handle a fairly broad band of frequencies, good-quality rf transistors will be used in them. High-frequency junction transistors, tetrodes, surface-barrier units or drift types may be used.

The circuit of a video detector and two-stage video amplifier is given in Fig. 4. An n-p-n transistor is used as the detector (V7), while the video amplifier consists of p-n-p junction triode (V8) and tetrode (V9) transistors. The common-emitter configuration is used in all three stages.

In the detector stage, the small base bias current necessary for detector action is supplied by voltage divider R23-R24, bypassed by C20. Emitter resistor R25, bypassed by C21, insures stable operation. V7's collector load consists of peaking coil L7 and resistor R26. C22 serves as an rf bypass capacitor.

In operation, V7 is biased almost to cutoff, and only the positive half-cycles of the applied signal are effective in controlling collector current. As the amplitudes of the if carrier signals applied to V7 by T8 increase, V7's collector current increases. The pulsating dc voltage appearing on V7's collector electrode is a composite signal which includes: rf components of the amplified if carrier signals, the modulation of the video if carrier, and a new signal at 4.5 mc representing the beat between the audio and video if carriers. (This 4.5-mc signal becomes the new audio if carrier and contains both the amplitude modulation of the original video if carrier and the frequency modulation of the audio if signal.) The rf components of the detected signal are bypassed by C22. The dc component of this composite signal is fed back to the agc-controlled rf and if stages through filter R22-C19.

The bias applied to the agc-controlled stages depends on the current fed through R27 and on V7's dc collector voltage. As stronger rf signals are picked up, the amplitudes of the if

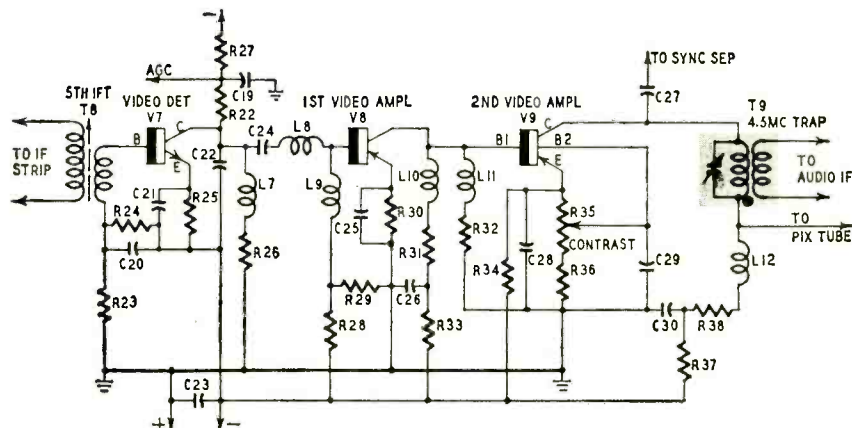


Fig. 4—Video detector and amplifier stages. In some sets a conventional diode detector might be used. Age voltage is taken from detector, sync output from first video stage, and 4.5-mc audio if signal from trap in output stage.

TELEVISION

carriers increase and V7's collector current increases. This results in a greater dc voltage drop across collector load resistor R26, reducing V7's collector voltage and allowing the bias applied through R27 to increase. This, in turn, reduces the gain of the age-controlled stages.

Both the 4.5-mc audio if carrier and the detected video signal are fed through dc blocking capacitor C24 to V8, the first video amplifier stage. L8 and L9 are peaking coils in V8's base circuit and serve to improve this stage's high-frequency response. V8's base bias current is supplied through voltage divider R28-R29, while stage stabilization is insured by emitter resistor R30, bypassed by C25. V8's collector load consists of peaking coil L10 and resistor R31. R33 and C26 form a decoupling filter for the stage.

The first and second video amplifier stages (V8 and V9) are direct-coupled to minimize low-frequency phase shift. Thus, V8's collector connects directly to V9's control base (B1). V9's base bias current is determined by a voltage divider made up of R33, R31 and R32. L11 serves as a peaking coil in the base circuit. V9's collector load consists of a 4.5-mc trap (T), peaking coil L12 and resistor R38. R33 and C30 form a decoupling filter.

Emitter resistor R36 and potentiometer R35, bypassed by C28 and C29, have a dual job. First, the dc voltage developed across these resistors helps stabilize the stage. Second, the reverse bias voltage between R35's arm and ground is fed to V9's second base connection (B2) to insure tetrode operation. B2's bias can be varied by adjusting R35 and this, in turn, varies V9's stage gain. Thus, R35 serves as a CONTRAST CONTROL. Adequate bias for gain control is assured by bleeder resistor R34, connected to the junction of resistor R35 and V9's collector electrode.

The amplified audio if and video signals appearing in V9's collector circuit are fed to different sections of the TV receiver. The 4.5-mc audio if signal is trapped by a tuned resonant circuit in T9, and coupled by the transformer's secondary to the audio if amplifier. A portion of the amplified video signal is fed through blocking capacitor C27 to the sync separator section, while the video signal itself is applied to the picture tube.

There is one remaining component in this circuit—C23. This capacitor is used as a bypass across the section's power supply connections and thus serves as a decoupling filter for these three stages.

So far we have taken a detailed look at a transistor TV receiver's front end, video if strip, and video detector and amplifier. Next month we will continue our tour of the all-transistor TV receiver and travel through the audio if strip, audio amplifier, ratio detector, sync separator and sweep and high-voltage circuits.

TO BE CONTINUED

MASTER THE BASICS OF TELEVISION

the easy RIDER "picture book" way

BASIC TELEVISION by Dr. Alexander Schure

NOW AVAILABLE

5 complete volumes

The whole world of black and white television is before you for only \$10.00. You can master the basics of television easily, rapidly and thoroughly with this 5-volume "learn by pictures" training course.

It's so easy to learn

Here's how this easy, illustrated course works. Every page covers one complete idea! There's at least one big illustration on that same page to explain it! You build a thorough, step-by-step knowledge at your own pace—as fast as you yourself want to go.

No experience, education needed

BASIC TELEVISION uses the same methods that have proven so successful in the famous Rider picture books on electricity and electronics. All that is assumed is that you have a knowledge of radio. Every phase of television is made instantly clear—explained in plain English supported by carefully prepared, large and exciting drawings that make every idea crystal clear.

More Than 700 Illustrations • 688 pp.

#198, soft cover 5 volumes. \$10.00 per set;

#198-H, cloth bound in a single binding, \$11.50

Learn at home—no correspondence

This course is so complete, so different—there's no need for the usual letter writing, question and correspondence. You learn in the comfort of your own home, in your spare time... at your own pace.

NEW BOOKS FOR GREATER ELECTRONIC KNOW-HOW

METALLIC RECTIFIERS AND CRYSTAL DIODES by Theodore Conti. Growing use of metallic rectifiers and crystal diodes in computers and guided missiles as well as in radio television and telegraph circuitry makes this book of great interest to the engineer, technician and experimenter. Covering construction, characteristics, basic design data, applications, trouble-shooting repair and replacement, this book presents the basic information enabling the reader to understand and apply these components with sure results.

— New Electronics Technology Series Releases —

IMPEDANCE MATCHING by Alexander Schure, Ph.D., Ed.D. Covering comprehensively the problems of impedance matching in electrical and electronic circuitry, this book provides detailed information on how to obtain maximum power transfer between any type of generator and load. Dealing initially with maximum power transfer in d-c circuits, the text covers inductance-capacitance relationships, vector notation and the j operator. Impedance matching devices, their application at audio and radio frequencies and in transistor circuits are covered.

#166-23, soft cover, \$2.90

ELECTROSTATICS by Alexander Schure, Ph.D., Ed.D. This volume, on one of the cornerstones in the study of electricity, considers fundamental physical units and quantities preparatory to the study of Columb's Law and Gauss' Law. The electrical field is considered both quantitatively and qualitatively making liberal use of worked out examples. Applications such as the Van de Graaf machine and such natural electrostatic phenomena as thunderstorms are discussed.

PHYSICS AND MATHEMATICS IN ELECTRICAL COMMUNICATION, by James Owen Perinne, Ph.D. — Profound and probing explanation of what happens in electrical circuits that contain resistance, inductance and capacitance. On a foundation of associated mathematics made completely understandable and replete with numerical examples, the author brilliantly ties together physical concepts and electrical communications. An entirely new approach is used in analyzing hyperbolic functions, exponential equations and related functions. Of special significance is the content of the graphical demonstrations of electrical behavior. 8½" x 11", cloth bound, 268 pp., #219, \$7.50.

STEREOPHONIC SOUND, by Norman H. Crowhurst — World-famous audio authority Norman H. Crowhurst's new book is the first true assessment of this exciting new medium for realistic sound. 128 pp., illus. #209, \$2.25.



FREE! Handsome genuine leather, gold-stamped book-mark, if you write today for FREE Catalog RE-5.



Buy these and many other RIDER BOOKS at your electronics parts jobber, book store or department store book department. Look for the Rider Bookseller.

If your favorite store does not sell the Rider books you want, order direct. Add state, city tax where applicable. Canadian prices 5% higher.

HOW TO READ SCHEMATIC DIAGRAMS, by David Mark. Teaching theory and the recognition of symbols, this book is ideal for all those people beginning a career or are starting hobbies in electronics. Covering the symbols and abbreviations used in schematic diagrams related to the electronics field, this book starts with individual components and carries through to receivers and similar equipment. Components and circuits are identified and explained. Soft cover, 160 pp., illus. #208, \$3.50.

CONDUCTANCE CURVE DESIGN MANUAL, by Keats A. Pullen, Jr., Eng. D. — An original technique for designing electronic circuits based on conductance curves. Gm, rp and μ are replotted as necessary so as to enable design using small signal parameters to predict large signal performance — greatly shortening design time and minimizing problems arising from approximation. Circuit reliability can be improved and distortion reduced at the same time by using the tables and curves in the manual. Engineers, engineering students and lab technicians can now select the proper tubes and their associated components to suit the needs of almost any type of circuit with greater reliability than ever before. #210, 8½" x 11", stiff cover, \$4.25.

INDUSTRIAL CONTROL CIRCUITS, by Sidney Platt — Control circuits are responsible for the rigid regulation and control of countless industrial processes. They constitute the core of industrial electronics. This book covers those control applications most frequently encountered in industrial electronics. The uses of industrial control circuits are discussed and described in detail, showing how basic electronics is applied to these circuits. #202, soft cover, \$3.90.

FAMOUS 'PICTURE-BOOK' COURSES
BASIC ELECTRICITY, BASIC ELECTRONICS, BASIC SYNCHROS & SERVO MECHANISMS, by Van Valkenburgh, Nooter Neville, Inc. — The fabulous picture-text books that teach faster and easier! The theory, principles, and servos are here presented in a manner that permits a rapid grasp of the fundamentals of these vitally important subjects. Over 2,000 specially prepared illustrations present, explain, and make every topic discussed picture-clear.

Basic Electricity, #169, soft cover, 5 vols., 624 pp., per set \$10.00. #169H, cloth bound in single binding \$11.50.

Basic Electronics, #170, soft cover, 5 vols., 550 pp., per set \$10.00. #170H, cloth bound in single binding \$11.50.

Basic Synchros and Servomechanisms, #180, soft cover, 2 vols., 270 pp., per set \$5.50. #180H, cloth bound in single binding \$6.95.



JOHN F. RIDER PUBLISHER, INC.

116 West 14th Street, New York 11, N.Y.


In Canada
 Charles W. Pointon, Ltd.
 6 Alcona Ave., Toronto, Ontario

TRANSFORMER NEWS FROM TRIAD



**NEW
REPLACEMENT CATALOG
& TELEVISION GUIDE
NOW AVAILABLE**

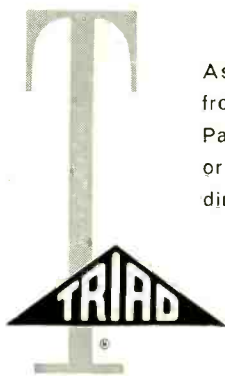The new TV-58 catalog & guide lists all of Triad's new replacement transformers...lists thousands of recommendations for television receivers...lists hundreds of recommendations not previously covered.



Ask for your copy from your Triad Parts Distributor—or write to us direct—

TRIAD TRANSFORMER CORPORATION
4055 REDWOOD AVE. | 812 E. STATE STREET
VENICE, CALIFORNIA | HUNTINGTON, INDIANA

A SUBSIDIARY OF LITTON INDUSTRIES.

TV Service CLINIC
conducted by
By ROBERT G. MIDDLETON
TELEVISION CONSULTANT

WE pick up again with receiver quick checks in this issue. These are of primary importance in preliminary work, both on the bench and in the set-owner's home.

When the complaint is *weak picture* and new tubes do not cure the trouble, we must find out where the circuit trouble is. We have either of two situations:

1. Weak (or no) picture, *with* snow.
2. Weak (or no) picture *without* snow. (This is generally age trouble.)

Consider No. 1: *Snow* and *audio noise* come from the receiver's front end. For example, there is no snow or noise when the second if stage is dead and there is only a little snow when the first if stage is dead.

Here are the points to keep in mind:

1. The mixer-oscillator stage generates the most snow in normal operation.
2. The antenna contributes the next largest amount of snow.
3. The rf amplifier contributes the next largest amount of snow.
4. The first if stage contributes just a little snow, in normal operation.

Now let us see how this helps us in quick checks. Let's tackle a receiver with snow in the picture. Where is the trouble? Maybe it's in the antenna—could be the lead-in is broken off. So we remove the lead-in from the receiver, meanwhile watching the snow in the picture and listening to the noise in the sound.

If there is practically no change in the snow level, don't waste time with the receiver. The trouble is in the antenna. To confirm this connect a pair of rabbit ears to the receiver. (Hold the ears out of the window if in a steel building.)

But, on the other hand, if there is a marked reduction of snow when the lead-in is disconnected, the trouble is in the receiver. Leave the lead-in disconnected and pull the rf amplifier tube. No change in snow level means that the trouble is in this or a nearby succeeding stage. (NOTE: In a series-string set, we have to use a dummy tube, with all but heater pins cut off.)

Trouble in the rf stage is often caused by a short in the tube, which

overheats the plate resistor and changes its value. However, make another check to see if the trouble could be in the mixer. With any kind of a picture on the screen, we know that the oscillator is working.

Unplug the oscillator-mixer tube. There must be a great reduction in snow if this stage and the first if stage are OK. This tells us whether the trouble is in the rf stage.

If the chassis is on the bench, there is a valuable quick test that you can make with a voltmeter. Connect the meter at the output of the picture detector. Then lift the shield over the mixer tube, but keep your fingers in contact. This couples stray fields to the mixer's plate. A reading on the meter shows that the mixer and all if stages are in working order. No picture in this case generally points to a dead oscillator.

The oscillator can also be quickly checked from the same floating tube shield. Use a good detector probe with your meter. Apply the probe between shield and chassis. A reading of 0.5 to 2 volts means the oscillator is running. Zero reading means a dead oscillator.

Raster blooming

I am having trouble with raster blooming in a Philco 51-T1634. Numerous checks have been made, with little success.—P. V., S. Peabody, Mass.

The trouble can be localized by dc voltage measurements. First see if the high voltage is up to par. This is very likely low. Then check the other picture-tube voltages. Normal voltages are: pins 1 and 2, 0 volt; 10, 300 volts; 11, 120 volts; 12, 6.3 volts ac. The trouble will be found in the circuit with incorrect voltage.

Circuit ghost

We have trouble with what looks like a ghost here. In a test pattern, there is a white circle showing next to the black circle. It is about the same in all locations and with various receivers. Could the trouble be in the sets?—G. McP., Renfrew, Ont.

This is not a multipath ghost which you describe, but a circuit ghost. Sometimes high video peaking is used at the TV camera, especially when old films are televised. This gives greater snap

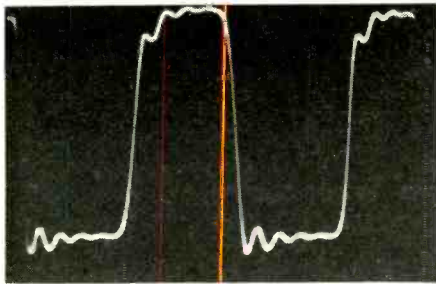


Fig. 1—High video peaking (high-frequency peaking) causes rapid signal changes to overshoot and ring. This gives rise to circuit ghosts.

to the picture, but also causes a spurious transient response (see Fig. 1), which gives the effect of close-in negative ghosts in the picture. Of course, if video peaking in the receiver is also high, the negative ghost will be intensified.

Larger screen?

I have a Wilcox-Gay chassis 439 and would like to change from the 19- to a 21-inch picture tube. What would you suggest?—M. H. W., Brooklyn, N. Y.

The most practical conversion is to a 21EP4. This tube can be swept almost as easily as the 19AP4, and will require no change in output transformers. The difficulties will all be mechanical.

21-inch conversion

I would like to use the all-glass 21CPY22 in place of a 19VP22 picture tube. Is this conversion feasible?—R. F. P., Toledo, Ohio

It is definitely easier to convert from the 19VP22 to the 21CPY22 than to a 21AXP22, for example. The lower anode voltage for the 21CPY22 is an advantage. The dynamic convergence voltages used by the 19VP22 should serve satisfactorily, also. The mechanical details will not be simple but, if you have the time available, the conversion is practical.

Horiz sync on the blink

I am having trouble with a 21-inch Philco model 22B4002, chassis R-191, code 140. It has good picture and sound but loses horizontal sync intermittently and folds over. This can be corrected with a slight touch of the hold control. The horizontal output transformer tests 69 ohms low between terminals 2 and 4. Could this cause the intermittent loss of sync?—E. H. B., West Palm Beach, Fla.

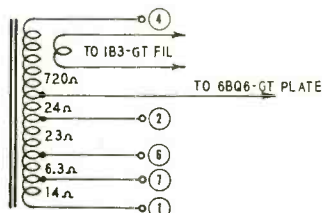


Fig. 2—The windings of a flyback transformer have a manufacturing tolerance. An error of less than 10% indicated on an ohmmeter is not evidence of trouble.

Just 2 settings on the NEW Model FC-2 FAST-CHECK TUBE TESTER



tests over 600 tube types completely, accurately... AND IN SECONDS!

SIZE:
H: 14⁵/₈"
W: 11¹/₄"
D: 4³/₈"

NEW Special compartment to accommodate line cord and CRT Test Adapter cable

CANNOT BECOME OBSOLETE

Engineered to accommodate all future tube types...new tube listings furnished periodically.

TRY THE FC-2 BEFORE YOU BUY IT!

Shipped on approval for FREE 10 day trial... No obligation to buy

EASY TO BUY IF YOU'RE SATISFIED!

Pay in small monthly payments at net cash prices... no financing charges

MODEL FC-2—housed in rugged oak carrying case complete with CRT adapter, tube listings... only **\$69.50** Net

GUARANTEED FOR 1 FULL YEAR

This extremely low price is made possible only because YOU ARE BUYING DIRECT FROM THE MANUFACTURER

- NO MULTIPLE SWITCHING
- NO ROLL CHART CHECKING

The FAST-CHECK enables you to save valuable time and eliminate unprofitable call backs. You earn extra money and win confidence by showing your customer the actual condition and life expectancy of the tube on the large meter scale of the FC-2. The extra tubes you will sell each day will pay for the FAST-CHECK in a very short time.

WIDE RANGE OF OPERATION

- Checks quality of over 600 tube types... more than 99% of all TV and radio tubes, including the newest series-string TV tubes, auto 12 plate-volt tubes, OZ4s, magic eye tubes and gas regulators.
- Checks inter-element shorts and leakage.
- Checks for gas content.
- Checks for life expectancy.

IMPORTANT FEATURES

- ✓ Checks each section of multi-section tubes and even if only one section is defective the tube will read "Bad"
- ✓ 41 long lasting phosphor-bronze tube sockets accommodate all present and future tube types—cannot become obsolete
- ✓ Less than 10 seconds required to test any tube
- ✓ Large D'Arsonval type meter is extremely sensitive yet rugged—is fully protected against accidental burn-out
- ✓ Line isolated
- ✓ 7-pin and 9-pin straighteners conveniently mounted on panel
- ✓ Quick reference tube chart lists over 600 tube types
- ✓ Line voltage compensation

NEW A specially designed PICTURE TUBE ADAPTER cable is now part of the FC-2... making it a highly efficient CRT Tester-Rejuvenator. This feature eliminates the need of carrying extra instruments and makes the FC-2 truly an all-around tube tester. The adapter enables you to check all picture tubes (including the new short-neck 110 degree picture tubes) for cathode emission, shorts and life expectancy... also to rejuvenate and restore cathode emission of weak picture tubes.

"You've really made tube testing a snap"... "I've almost got the cost of the Fast-Check paid off with the extra money I've made, and it's only 2 weeks since I received it"... "It's easier to use than you said"... "I wouldn't ever want to be without it"... "I use it in the shop and take it along on every call!"

WHAT SERVICEMEN* are SAYING ABOUT THE FC-2

*Names on request

MAIL COUPON NOW—NO MONEY REQUIRED WITH ORDER

CENTURY ELECTRONICS CO., INC. 111 Roosevelt Avenue Dept. 105, Mineola, N. Y.

Please rush the new Model FC-2 FAST-CHECK TUBE TESTER for a 10 day trial period. If I am not completely satisfied I will return the instrument within 10 days without further obligation. If fully satisfied I agree to pay the down payment within 10 days and the monthly installments as shown. No financing charges are to be added. Should I fail to make payment when due, the unpaid balance shall become due and payable at once.

- BUDGET TERMS:** Pay \$14.50 within 10 days after receipt of instrument. Balance \$11.00 monthly for 5 months, plus shipping charges.
- PREPAID TERMS:** Enclose \$69.50 with coupon as payment in full and Century will pay all shipping costs. 10 day money-back guarantee.

Name.....
Address.....
City..... State.....

ABSOLUTELY NO RISK ON YOUR PART

TELEVISION

As shown in Fig. 2, the rated resistance between the flyback terminals noted is 744 ohms. An error of 69 ohms is small (less than 10%) and within the manufacturing tolerance, plus the tolerance of a service ohmmeter. You are more likely to find this trouble in a defective ringing coil (L800), or in the time-constant circuits of the horizontal multivibrator. Check R809, R810, R811 and possibly R806, R807. If stable, then check C815-a for leakage.

Rf radiation

A Sylvania color TV receiver has been causing interference on black-and-white receivers in the same building. A bar floats back and forth on one channel only. It appeared first on channel 7 but when the 6BQ6's were changed, it moved to channel 9. I am also having difficulty converging the color dots.—W. E., Chicago, Ill.

The interference is due to rf radiation. It can come from the antenna and lead-in of the color receiver, or is sometimes conducted by the power line. If the latter, installing rf filters in the line will help. If the antenna and lead-in are radiating strongly, try to reroute the lead-in away from others. Also install the antenna as far from the other antennas as possible.

Lack of convergence is caused by misadjustment of the static and dynamic convergence controls. One or more of the beam magnets may be re-

versed. A complete step-by-step convergence will be required.

Weak blues

An RCA 21-CT-660U color receiver has weak blue hues, and snow appears in the blue parts of the picture. I have changed the (B-Y) amplifier plate-peaking coil, which reduced the snow to a certain extent. How should I adjust the new bandpass transformer?—R. W., Philadelphia, Pa.

If you get a normal black-and-white picture, the picture tube is not at fault. The trouble is caused by low gain in the (B-Y) signal channel. Hence, you will not correct the trouble by adjusting the bandpass transformer. This transformer affects the entire chroma signal. The trouble will probably be found between the demodulator driver and the picture tube. A wide-band scope and low-capacitance probe should be used to find out where the signal loss occurs. This will permit you to close in on the fault.

Fuse blowing

An RCA 24D7545, chassis KCS-104A has had repeated fuse failures. Slow-blow fuses do not help. The receiver has a 0.3-amp rating. I have tried tube substitution. In my own shop, the fuse does not blow.—J. T., East Chicago, Ill.

Since the fuse blows in the customer's home but not in your shop, it indicates that the line voltage is different.

Check to see whether the line voltage is high in the set-owner's home, and if an occasional surge occurs. A receiver usually requires higher starting current when it has been standing idle for a long period. This is because the electrolytics become partially unformed when idle. Fuse blowing caused by heavy starting current can often be eliminated by using a surgistor, which consists of a small wirewound resistor and a bimetallic relay strip. I assume you have tried replacing the horizontal output tube, an occasional offender.

Audio hum

A Westinghouse V-2311-45 2L48, model H-14T170 has a loud hum in the sound. The hum changes pitch and grows louder or weaker with changes in picture scenes.—M. N. B., Southampton, N. Y.

The hum that you report is video signal, and vertical sync pulses in particular, getting into the sound signal. There are several possible points of entry. A scope and low-capacitance probe will give a definite answer, showing the vertical sync mixed with the sound. The possible points of entry are: (1) Overload of the first video output tube. Such overload occurs because of low plate voltage, low screen voltage, leaky grid capacitor C313 (Fig. 3) or wrong value of R315. A short in C315 will cause the same trouble. A lesser possibility is leakage



For my Money
XCELITE Tools are
the Finest!

. . . Superbly made and designed for Radio, T.V. and Electronic Technicians. See your Distributor . . . only one quality . . . the finest — whether you choose individual items or the handy kits . . .

Use the Tools the Professionals use!



XCELITE, INCORPORATED

ORCHARD PARK, NEW YORK

Canada: Charles W. Pointon, Ltd., Toronto

XCELITE

Quality Hand Tools

PREFERRED BY THE EXPERTS

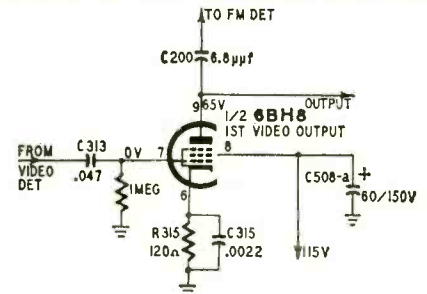


Fig. 3—Video overload and sync buzz can be caused by faulty C313, C200 or C315. Low plate or screen voltage or a change in the value of R315 can also be the fault.

in C200. (2) Poor decoupling of the video-amplifier output circuit from the audio circuits. Capacitor C508-A performs this function. It should be checked. (3) Overload in an if stage. Clamp the age to see if the sound interference disappears. If it disappears look for age trouble, such as a leaky delay capacitor. (4) Incorrect voltages on the 3BN6, intercarrier audio detector tube. Correct voltages are: pin 1, 1.5 volts; 2, 0; 5, 70; 6, 0; 7, 65. (5) Misalignment of sound if input coil (L200) or quadrature coil L201. END

The TV DX COLUMN will appear in the JUNE issue of RADIO-ELECTRONICS.

Build the Best— build ALLIED knight®-kits



the finest electronic equipment in money-saving kit form

LOWEST COST

ALLIED'S giant buying power passes biggest savings on to you—you do the easy assembly and your finished instrument equals the performance and appearance of several times the low KNIGHT-KIT cost. Your savings are BIG.

EASIEST TO BUILD

KNIGHT-KIT "Step-and-Check" instruction manuals with wall-sized picture diagrams are marvels of clarity—it's like having a good instructor at your side. No experience required—you can easily build any KNIGHT-KIT and get professional results.

LATEST DESIGN

Each ALLIED KNIGHT-KIT incorporates the very latest circuitry for top-quality performance. Tried and proved professional design and the use of premium quality parts throughout help insure your building success to bring you quality results.

COMPLETE KIT SELECTION:

- HI-FI
- HOBBY
- INSTRUMENT
- AMATEUR




MONEYBACK GUARANTEE. When properly assembled, KNIGHT-KITS fully meet published specifications or we refund your money in full.

EASY TERMS. If your KNIGHT-KIT order comes to \$45.00 or more, you can make your purchase on our attractive Easy Payment Plan.

High Fidelity Everyone Can Afford

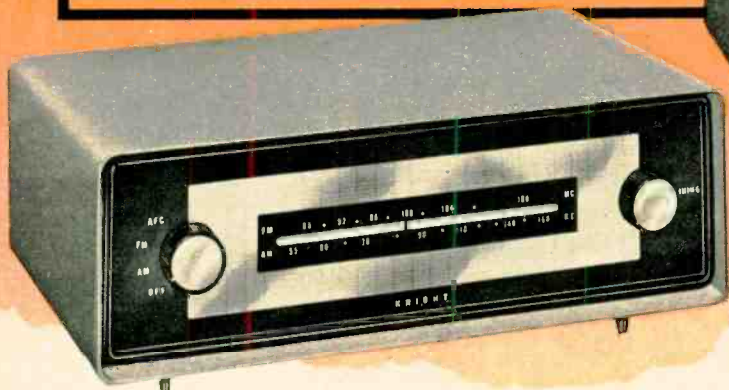- World's Finest Hi-Fi Kits
- Custom-Styled
- Easiest to Build Hi-Fi
- Money-Saving



knight-kit 18-Watt Complete Hi-Fi Amplifier Kit

Model Y-786

\$39.95

Only \$3.99 down

- The Last Word in Custom Hi-Fi Styling
- Full 18 Watts with Superb Hi-Fi Specifications
- 8 Inputs for Every Desired Signal Source
- Printed Circuit Switch and Printed Circuit Boards
- Full Equalization for All Record Types

Here is a custom-styled, easy-to-build complete Hi-Fi amplifier at a price that defies comparison. Delivers full 18 watts output with wide-range, flat frequency response for true hi-fi reproduction. Features 8 inputs for every possible signal source, including NARTB equalized tape head input. At full 18 watts output, distortion is only 0.5%; uses new RCA 6973 hi-fi output tubes. Frequency response is ± 1 db, 20-30,000 cps; tape head and magnetic cartridge sensitivity, 5 microvolts for 18 watts output; hum and noise level better than 60 db below 18 watts. Output taps for 4, 8 or 16 ohm speakers. Controls: Input and Record Equalization; Bass Boost and Attenuate; Treble Boost and Attenuate; Volume. Simplest assembly is made possible through the use of an exclusive printed circuit switch and two printed circuit boards—most of the kit wiring is already done for you. With custom-styled French-gray "space-saver" case on tapered feet finished in chrome, 4 x 13 x 8". Complete with case, tubes, all parts, and step-by-step instructions, for easy, error-free assembly. Shpg. wt., 15 lbs.

Model Y-786. 18-Watt Hi-Fi Amplifier Kit. Net only \$39.95

knight-kit High Fidelity FM-AM Tuner Kit

Model Y-787

\$49.95

Only \$4.99 down

- Latest Time-Saving Printed Circuit Design
- Flywheel Tuning
- Automatic Frequency Control
- 2.5 μ v FM Sensitivity
- True High Fidelity Response
- Beautiful Custom-Styled "Space Saver" Case

The best-looking, best-performing FM-AM tuner kit your money can buy! Carefully designed for quick, easy construction—a tuner you'll enjoy assembling and be proud to own, both for its amazing musical performance and outstanding beauty. Covers the full AM broadcast band and 88 to 108 mc FM. On FM, sensitivity is a remarkable 2.5 microvolts for 20 db of quieting; hum and noise, -60 db; IF bandwidth, 200 kc at 50% down on curve; response, ± 0.5 db, 20-20,000 cps. On AM, sensitivity is 3 microvolts for 10 db signal-to-noise ratio; IF bandwidth, 8 kc at 50% down on curve; response, 20-8000 cps. Outstanding features include: Inertia Flywheel Tuning for effortless, accurate tuning; Automatic Frequency Control (plus AFC disabling) to "lock-in" FM stations; printed circuit board (with most of the kit wiring already done for you) assures time-saving, error-free assembly; pre-aligned RF and IF coils; tuned RF stage on FM; drift-compensated oscillator; neon glow tuning pointer; cathode follower output; two output jacks—one for recorder, one for amplifier; rotatable built-in ferrite antenna for AM. Includes beautiful French-gray case with chrome-finished tapered feet, 4 x 13 x 8". Ideal for use with 18, 20 or 30 watt KNIGHT-KIT amplifiers. Ready for easy assembly. Shpg. wt., 12 lbs.

Model Y-787. FM-AM Tuner Kit. Net only \$49.95

EASY TERMS TO FIT YOUR BUDGET. ALLIED KNIGHT-KITS may be purchased under our Easy Payment Plan. Your order need total only \$45.00 or more—only 10% down, small monthly payments thereafter. No red tape—fast handling assured.

Our 37th Year



© Registered Trade-Mark of Allied Radio Corporation

ORDER FROM **ALLIED RADIO** 100 N. WESTERN AVE. • CHICAGO 80, ILL.

Now you can have Custom-Styled Hi-Fi in **ALLIED**



knight-kit 30-Watt Complete Hi-Fi Amplifier Kit

Model Y-762

\$76⁹⁵

- Full Equalization, $\pm 1/2$ db of Recommended Accuracy
- Printed Circuit Switches • Printed Circuit Boards
- 8 Inputs For Every Possible Signal Source
- Full 30 Watts Output • Custom-Styled Beauty

Only \$7.69 down

Comparable to the best in Hi-Fi—at far less cost! Deluxe features include: Linear-deluxe Williamson-type circuit for flawless response; equalization for all records within $1/2$ db of recommended accuracy; 2 exclusive new printed circuit switches in preamp section (no complex wiring to do); 3 printed circuit boards for time-saving, error-free assembly; separate, continuously variable Level and Loudness controls; use of premium 12AY7 tube for low noise and hum; DC on all filaments of preamp tubes; exclusive A-AB-B speaker selector switch (use speakers of mixed impedances without mismatch). 8 inputs: Tape Head direct; G.E. and Pickering cartridges; Ceramic cartridge; Microphone; Auxiliary; Tape Preamp; Tuner (with separate Level Set control). Power amplifier response, $\pm 1/2$ db, 15-100,000 cps at full 30 watt level; distortion—harmonic, 0.55% at 30 watts—IM, 0.74% at 20 watts. Separate Bass and Treble controls; rumble filter switch; variable damping. Output, 8 and 16 ohms. With smart French-gray cabinet, 4 x 15 x 15". Ready for easy, money-saving assembly. Shpg. wt., 32 lbs.

Model Y-762. 30-Watt Hi-Fi Amplifier Kit. Net only **\$76.95**

knight-kit High Fidelity FM Tuner Kit

Model Y-751

\$38⁹⁵

- Authentic High Fidelity FM Response
- Flywheel Tuning • Automatic Frequency Control
- Printed Circuit • Pre-Adjusted Coils and IF's
- 4 Microvolt Sensitivity Guaranteed

Only \$3.89 down

Here is top value in creative engineering, impressive hi-fi performance and distinctive design—a tuner you'll be proud to build and own. Covers the full FM band, 88 to 108 mc. Features Automatic Frequency Control (with disabling feature) to "lock-in" stations and prevent drift; Inertia Flywheel Tuning for velvet-smooth, accurate station selection; pre-adjusted RF coils; pre-aligned IF's; cascode broad-band RF amplifier; drift-compensated oscillator; neon bulb pointer. All critical wiring is already done for you in the form of a printed circuit board—assembly is simple. Sensitivity is 4 microvolts for 20 db of quieting across entire band; output, 2 volts at 1000 microvolts input; IF bandwidth, 200 kc; response, 20-20,000 cps. with only 0.6% distortion. Output jacks for amplifier and tape recorder; cathode follower output. Ideal for use with the KNIGHT-KIT amplifiers, or any amplifier with phono-tuner switch. Features custom-styled case in French-gray, with tapered chrome-finished feet, 4 x 13 x 8". Includes all parts, tubes and step-by-step instructions for easy assembly. Shpg. wt., 12 lbs.

Model Y-751. Hi-Fi FM Tuner Kit. Net only **\$38.95**

knight-kit Deluxe 3-Way Speaker System Kit

Model Y-937

\$89⁵⁰

Only \$8.95 down


- Pre-Finished "Quik-Craft" Corner Enclosure
- Klipsch Designed and Licensed
- Famous Knight 12" 3-Way Speaker
- Easy to Assemble—Top Hi-Fi Quality
- Choice of Enclosure Finishes

Deluxe quality high fidelity speaker system at a money-saving low price. Easy to assemble—all you need is a screwdriver. System includes KNIGHT "Quik-Craft" corner-type folded-horn enclosure kit, and the famous-value KNIGHT 3-Way 12-inch speaker. Just assemble the enclosure—no finishing required—all surfaces are finished in hand-rubbed Korina blonde, mahogany or walnut. The speaker is the new 3-way type: 12" woofer cone for bass (full $1 3/4$ pound woofer magnet), conical radiator for mid-frequencies, built-in compression-type tweeter (with wired

level control and calibrated dial) for highest frequencies. Unexcelled enclosure efficiency and superb speaker performance combine to cover the whole spectrum of audible sound for true hi-fi response from 35 to 15,000 cps, ± 3 db. Kit includes 12" 3-Way speaker, prefinished enclosure panels, grille cloth, hardware and instructions. Specify Korina blonde, mahogany or walnut when ordering. Shpg. wt., 44 lbs.

Model Y-937. 3-Way Speaker System Kit. Net only **\$89.50**

3-Way Speaker

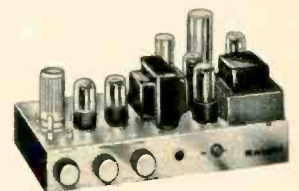

knight-kit 10-Watt Hi-Fi Amplifier Kit

Y-753


\$23⁵⁰

Low-cost, authentic hi-fi amplifier. Response, ± 1 db, 30-20,000 cps. Input for crystal phono or tuner; chrome-plated chassis is punched for preamp kit below, to permit use of magnetic phono. Only 0.5 volt drives amplifier to full output. Separate bass and treble controls. Only 1% harmonic distortion. Matches 8-ohm speaker. 7 x 13 x 6". With all parts, tubes and instructions. Shpg. wt., 13 lbs.


Model Y-753. Net only **\$23.50**
 Y-235. Preamp Kit. **\$ 3.10**
 Y-757. Metal Cover. **\$ 3.95**

knight-kits

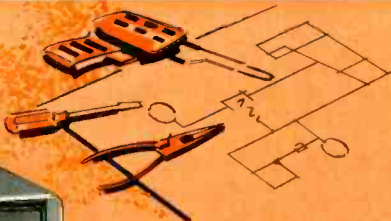THE VERY FINEST MUSICAL QUALITY—SO EASY TO BUILD
MONEY-SAVING HI-FI EVERYONE CAN AFFORD



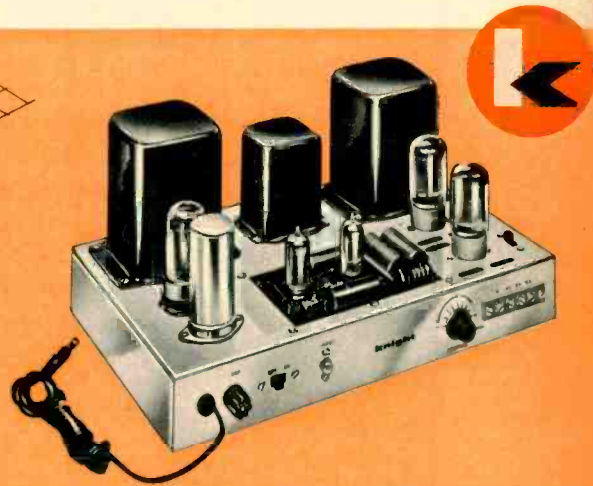So Easy To Build
Anyone can build
KNIGHT-KIT HI-FI.
No experience re-
quired to get top
results!



knight-kit High Fidelity Preamp Kit

Model Y-754

\$39.95

Only \$3.99 down

- Exclusive Printed Circuit Switches and Boards
- Equalization $\pm \frac{1}{2}$ db of Recommended Accuracy
- 8 Inputs Including Tape Head
- DC or All Tube Filaments
- Self-Powered
- Custom-Styled

Sensational Hi-Fi design at amazing low cost. Provides precise record equalization guaranteed within $\frac{1}{2}$ db of recommended accuracy!—more accurate than all but the most expensive factory-built preamps. Includes exclusive new KNIGHT-KIT printed circuit switches for easy, error-free assembly; 2 printed circuit boards eliminate all other wiring, except for power supply and control leads—so easy to build. Has built-in power supply; includes premium 12AY7 and ECC82 tubes. Frequency response, ± 0.5 db, 10-50,000 cps. Has 8 inputs: Tape Head; G.E. Phono; Pickering Phono; Ceramic; Microphone; Auxiliary; Tape Preamp; Tuner. Level adjustment for tuner input. Includes separate Bass and Treble controls; separate Level and Loudness controls; Rumble Filter switch; DC on all tube filaments; cathode follower output 2 extra AC outlets. You get every advanced hi-fi feature in this easy-to-build preamplifier at the lowest possible cost. Includes beautiful custom-styled French-gray case, with tapered chrome-finished legs, 4 x 13 x 8". With all parts, tubes, step-by-step instructions; ready for easy assembly. Shpg. wt., 12 $\frac{1}{2}$ lbs.
Model Y-754. Hi-Fi Preamp Kit. Net only **\$39.95**

knight-kit 25-Watt Hi-Fi Basic Amplifier Kit

Model Y-755

\$44.50

Only \$4.45 down

- Hi-Fi Response, ± 0.5 db, 10 to 120,000 cps
- Only 0.15% Distortion at 30 Watts Output
- Printed Circuit Wiring Board • Chrome-Plated Chassis
- Williamson-Type Circuit with Over 25 Watts Output

Here's superb Hi-Fi performance at less than half the cost of a comparable commercially-assembled unit. Williamson-type linear-deluxe circuit delivers over 25 watts of virtually undistorted reproduction. Ideal for use with the KNIGHT-KIT preamp at left. Includes printed circuit board for simplified, error-free assembly. Remarkable hi-fi response, ± 0.5 db, 10-120,000 cps at 20 watts. Harmonic distortion, 0.15% at 30 watts; IM, 0.4% at 20 watts. Hum level, 85 db below 25 watts output. Output impedances, 4, 8 and 16 ohms; output tubes, 2-5881. Includes balance control for precise matching of the output tubes; variable damping control for maximum performance with any speaker system—prevents low-frequency distortion from overdamping or underdamping. Very attractive black and chrome styling, 6 $\frac{1}{4}$ x 14 x 9". An outstanding engineering achievement in a basic hi-fi amplifier, delivering performance equal to the finest commercially assembled units. Includes all parts and tubes; with step-by-step instructions, ready for easy assembly. Shpg. wt., 25 lbs.
Model Y-755. 25-Watt Amplifier Kit. Net only **\$44.50**
Y-759. Metal Cover for above; black finish. 5 lbs. Net **\$4.25**



knight-kit 20-Watt Hi-Fi Amplifier Kit

Y-750

\$35.75

\$3.57 down

True hi-fi for less! Complete with full set of controls and built-in preamplifier. Response, ± 1 db, 20-20,000 cps; distortion 1% at 20 watts. Inputs for magnetic phono, microphone, crystal phono or recorder, and tuner. Compensation positions for 78 and LP records. Separate bass and treble controls. Output impedances, 4, 8, 16 and 500 ohms. Chrome-plated chassis. 7 x 13 x 8 $\frac{3}{4}$ ". Ready for easy assembly. Shpg. wt., 20 lbs.
Model Y-750. Net only **\$35.75**
Y-758. Metal Cover **\$4.15**

knight-kit 2-Way Hi-Fi Speaker System Kit

Model Y-789

\$49.95

Only \$4.99 down

- Easy to Assemble—Pre-Finished Enclosure
- High Fidelity Response, 45 to 14,000 cps
- 12" Woofer and Horn-Type Tweeter
- A Wonderful Money-Saving Speaker Value

BIG SAVINGS—assemble your own quality KNIGHT-KIT 2-way speaker system—it's quick and easy! The cabinet is *pre-finished* in full-grained, high luster blonde or mahogany—you just assemble 7 pieces, mount the speaker components and enjoy rich, thrilling hi-fi sound—at incomparably low cost. Special Jensen-engineered baffle features "ducted port" construction to bring out the full beauty of bass notes, perfectly matching the Jensen woofer and compression tweeter; genuine L-pad control is rear-mounted to permit adjustment of tweeter for best tonal balance. Impedance, 16 ohms. The assembled unit delivers a frequency response of 45 to 14,000 cps. Enclosure measures 26 x 19 x 14". Beautifully styled to blend in any room. Kit includes Jensen 12" woofer, Jensen compression-type tweeter, pre-finished wood parts (with grille cloth installed), acoustic material, glue, hardware and step-by-step instructions. Absolutely no furniture finishing required. *Specify blonde or mahogany finish when ordering.* Shpg. wt., 33 lbs.
Model Y-789. 2-Way Speaker System Kit.
Net only **\$49.95**




KNIGHT-KIT HI-FI IS AVAILABLE ON EASY TERMS TO FIT YOUR BUDGET

Fascinating

ALLIED **knight-kits**

FOR EXPERIMENTERS AND HOBBYISTS

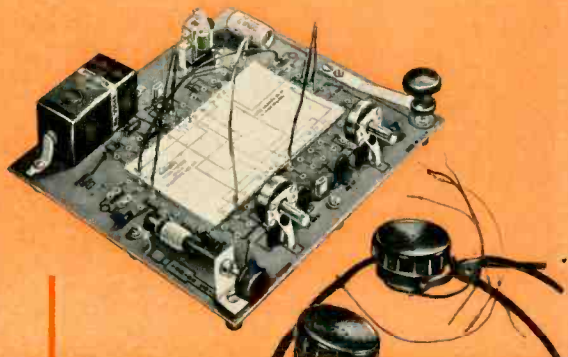

knight-kit 2-Transistor Pocket Radio Receiver Kit

- Model Y-262 • Loud, Clear Local Reception
 • Newest Printed Circuit Board
 • Built-In Loop Antenna
 • Complete Kit—Nothing Else To Buy

\$14.65

It's fun to build this pocket-size two-transistor radio—and you'll enjoy its crystal-clear local broadcast-band reception wherever you go! Fits in your pocket, or with its button-down flap, can be worn from your belt. Completely self-contained with built-in ferrite loopstick antenna—no external antenna needed. Extremely efficient reflex type 2-transistor circuit actually does the work of 3 transistors! Printed circuit board reduces building time to about one hour. Has air-dielectric variable capacitor for easy, accurate station tuning. Operates for months and months on long-life alkaline battery supplied. Sensitive miniature earpiece provides crystal-clear tone. Handsome tan carrying case, plastic-impregnated, is styled to resemble leather; only 4x3 3/4 x 1 3/4". Kit includes all parts, transistors, earpiece, battery and case. Shpg. wt., 1 1/2 lbs.

Model Y-262. Net only \$14.65

knight-kit "Trans-Midge" Transistor Receiver Kit

- Model Y-767 Tiny, cigarette-pack-size one-transistor radio kit—fascinating to build—so low-priced. This novel miniature receiver will provide endless listening pleasure the moment assembly is completed. Covers the local AM broadcast band with exceptional sensitivity and selectivity. Special features include: Efficient, slug-tuned coil for excellent station separation; external knob for easy station tuning; low-drain transistor operating for months from single penlight cell supplied; hinged-back, red plastic case. Kit includes all parts, transistor, battery, compact case and easy-to-follow instructions for quick assembly. (External antenna and headphones required.) Shpg. wt., 8 oz.

\$2.45

Model Y-767. Net only \$2.45
 J-149. 4000 Ohm Headphones. 1 lb. \$2.15
 C-100. Antenna Kit. 1 1/2 lbs. \$1.03

knight-kit 10-Circuit Transistor Lab Kit

- Model Y-299 Sensational experimenters' transistor kit—an electronic marvel! Perfect for experimenter, student or hobbyist. Assemble basic parts once, then complete project after project (10 in all), by simply plugging leads into proper jacks on printed circuit board—no wiring changes needed. You learn how transistors operate by "plugging in" to make any one of the following circuits; AM radio for strong headphone reception; 2-stage audio amplifier; wireless broadcaster; code practice oscillator; electronic timer; electronic switch; electronic flasher; photoelectric relay; voice-operated relay; capacity-operated relay. Includes all parts, 2 transistors, battery, headphones, circuit leads, relay, photocell, special guide cards for each project, explanation of each circuit. 3 lbs.

\$15.75

Model Y-299. Net only \$15.75


knight-kit 5-Transistor Superhet Personal Portable Radio Kit

- Model Y-766 • Styled to Equal the Finest
 • Push-Pull Audio Drives 3 1/2" Speaker
 • Printed Circuit for Easy Building
 • 200 Hour Battery Playing Life

\$29.95

Beautiful, easy-to-build transistorized personal portable with every ultra-modern design feature: 5 Texas Instrument Co. transistors; latest printed circuit chassis for easy, error-free assembly; bigger-than-average 3 1/2" speaker; class B push-pull audio output; built-in high-gain ferrite loopstick antenna; plus phone jack output for private listening. Provides sensitive reception of the AM broadcast band with exceptional tone quality. Ultra-smart high-impact ivory plastic case has handsome gold trim with ebony accents; includes pull-out handle; only 7 1/2 x 3 3/8 x 1 1/4". With all parts, transistors, 9 volt transistor radio battery, carrying case and instructions anyone can easily follow. Shpg. wt., 2 lbs.


Model Y-766. Net only \$29.95

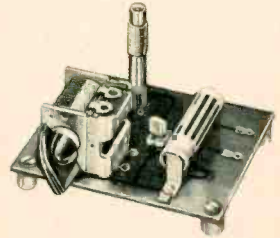

1-Transistor Radio Kit

- \$3.95** Offers excellent AM local broadcast headphone reception. Printed circuit board for easy assembly. Operates from single penlight cell for months. Complete with all parts, transistor and penlight cell. (Antenna and headphones required.) Shpg. wt., 1 lb.

Model Y-765. Net only \$3.95

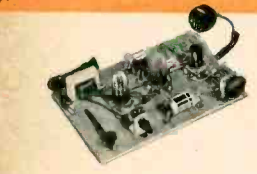

- "10-In-One" Electronic Lab Kit**
\$12.65 Famous experimenters' kit. Builds any of 10 fascinating projects, including broadcast receiver, wireless phono oscillator, code practice oscillator, signal tracer, relays, etc. Shpg. wt., 5 lbs.
 Model Y-265. Net only \$12.65



- "6-In-One" Electronic Lab Kit**
\$8.45 A favorite with beginners. After basic wiring is completed, you make circuit changes without soldering. Builds any of six favorite projects, including radio, wireless broadcaster, etc. Shpg. wt., 3 lbs.
 Model Y-770. Net only \$8.45



- Crystal Set Hobby Kit**
\$2.15 Entertaining, educational. Delivers clear headphone reception of local broadcast stations. With all parts, ready for easy assembly. (Antenna and headphones required.) Shpg. wt., 1 lb.
 Model Y-261. Net only \$2.15



- Wireless Broadcaster Kit**
\$9.50 Play music or make announcements through your radio set—no connection to set required! Loads of fun—easy to build. Works up to 50 feet from set. Shpg. wt., 3 lbs.
 Model Y-705. Net only \$9.50

ORDER FROM **ALLIED RADIO** 100 N. WESTERN AVE. • CHICAGO 80, ILL

www.americanradiohistory.com

FUN TO BUILD . . . INSTRUCTIVE . . . LATEST CIRCUITS FOR TOP PERFORMANCE

WIDEST CHOICE OF QUALITY HOBBYIST KITS



Interruption of light beam triggers relay, which in turn sounds chime or bell, turns on lights, etc.

knight-kit Photoelectronic Relay Kit

Model Y-702 Advanced-design, ultra-sensitive photoelectronic relay—build it yourself and save! Dozens of uses: for automatic control of lights, door annunciator, burglar alarm, counting devices, etc. Provides dependable operation up to 250 feet with white light, up to 125 feet with "unseen" light (red filter) from Light Source Kit listed below. Selectable operation, with "trip" for burglar alarm to provide continuous ringing of alarm; and "auto" if relay is to operate each time beam is broken (for chimes, counting devices, turning on lights at darkness). Has SPST relay operated from thyatron; 6.3 v. terminals provide power for accessories. For 105-120 v. 50-60 cy. AC use. 6 lbs.
Model Y-702. Relay Kit. Net only . . . \$13.50
Model Y-703. Light Source Kit. With bulb and red filter. Shpg. wt., 3½ lbs. Net. \$6.75



"Ranger II" Superhet Receiver Kit

\$17.25 Popular Broadcast band receiver built and enjoyed by thousands. Features built-in antenna, automatic volume control, ball-bearing tuning condenser, PM dynamic speaker. Handsome plastic cabinet. Easy to assemble. AC or DC operation. Shpg. wt., 8 lbs.
Model Y-735. Net only . . . \$17.25



knight-kit "Ocean Hopper" All-Wave Radio Kit

Model Y-740 This top-performing regenerative receiver puts a world of listening pleasure at your finger-tips. Tuning range (using coils listed below) is virtually world-wide; covers 155 kc to 35 mc, including every type of radio transmission: AM broadcast, marine, aircraft, distress channels, direction-finding, Amateur, frequency standard, foreign broadcast, and police. With band-spread tuning. For use with headphones or 3-4 ohm PM speaker. Kit is supplied with standard broadcast band coil and all tubes and parts. (Less extra coils, headphones, speaker and cabinet.) Shpg. wt., 5 lbs.
Model Y-740. Net only . . . \$11.95
Y-746. Cabinet for above. 1½ lbs. Net \$2.90
 Extra coils available: Long Wave Coil (155-470 kc), Net 79c. Short Wave (1.65—4.1 mc; 2.9—7.3 mc; 7—17.5 mc and 15.5—35 mc). Each 65c.



knight-kit "Space-Scanner" Bandswitching World-Wide Radio Kit

Model Y-243 • Broadcast or Short Wave Reception
 • Sensitive Regenerative Circuit
 • Convenient Bandsread Tuning
 • Built-In Loudspeaker
\$15.95
 Imagine the thrill of hearing overseas broadcasts on a precision receiver you've built yourself—and then, at the flip of a switch, being able to tune to your favorite local broadcast station! Bandswitch selects exciting short wave, including foreign broadcasts, amateur calls, aircraft, police and marine radio on the 6.5 to 17 mc range, as well as standard 540-1700 kc broadcasts. Features highly sensitive regenerative circuit. Includes built-in 4" PM speaker and beam-power tube for strong volume and clear tone. Headphone connectors are available for private listening; switch cuts out speaker. Controls: Bandsread, Main Tuning, Antenna Trimmer, Bandswitch, Regeneration. Volume. 7x10x6". Easy to build from step-by-step instruction manual. For 110-120 v., 50-60 cy. AC or DC. (Less cabinet.) Shpg. wt., 5 lbs.
Model Y-243. Net only . . . \$15.95
Y-247. Cabinet for above. Shpg. wt. 2 lbs. Net. \$2.90

knight-kit 2-Way Intercom System Kit

Model Y-295 • Low Cost—Easy to Assemble
 • High Gain—Clear Tone
 • Handsome Metal Cabinets
 • Includes 50-Foot Cable
\$14.75
 Easy to build at lowest cost—ideal for home, office, shop or school. Consists of Master unit and Remote unit. Remote unit may be left "open" for answering calls from a distance, for "baby sitting", etc. Remote also may be set for "private" operation—cannot be "listened-in" on, but it can be called and can originate calls. Master unit includes high-gain 2-stage amplifier, combination volume control and on-off switch, plus pilot light. Each unit has 4" PM dynamic speaker. System responds to even a whisper. Handsome Antique white cabinets, each 4¾x6½x4¾". With all parts, tubes and 50-ft. cable (up to 200-ft. may be added). For 110-120 v., AC or DC. 8 lbs.
Model Y-295. Master and one Remote. Net only . . . \$14.75
Y-296. Extra Remote Station Kit. 3 lbs. . . . \$3.75



Phono Amplifier Kit

\$9.45 Build it yourself—and save! Ideal for use in a portable phonograph—just add record player and 3-4 ohm speaker. 1½ watts output. Inverse feedback circuit. Easy to assemble. Shpg. wt., 3 lbs.
Model Y-790. Net only . . . \$9.45



Electronic Photoflash Kit

\$28.50 Ideal for color or black and white photography. 1/700th-of-a-second flash; 50 watt/second output. Synchronizes with any camera with X or O shutter. (Less battery.) Shpg. wt., 4 lbs.
Model Y-244. Net only . . . \$28.50



Code Practice Oscillator Kit

\$3.95 Ideal for beginners learning the code. Transistorized circuit. Operates for months from single penlight cell supplied. Clear, crisp 500 cycle tone. Jacks for headphones; screw terminals for key. 1 lb.
Model Y-239. Net only . . . \$3.95



Phono Oscillator Kit

\$5.85 "Broadcasts" recorded music through any standard radio set up to 50 feet away. No direct connection to set required. Easy to build—fun to use. Shpg. wt., 2 lbs.
Model Y-760. Net only . . . \$5.85

FINEST ELECTRONIC EQUIPMENT IN EASY-TO-BUILD MONEY-SAVING KIT FORM



knight-kit Low-Cost Tube Tester Kit

Model Y-143

- With 16 Filament Voltages
- 600 Latest Tube Types Listed
- Easy-to-Read 4½" Meter
- Tests Series-String TV Tubes

\$2975

Expertly designed for complete, up-to-date coverage of tube types. Tests *series-string TV tubes*; tests 4, 5, 6 and 7 pin large, regular and miniature types, octals, loctals, 9-pin miniatures and pilot lamps. Tests for open, short, leakage, heater continuity and performance (by amount of cathode emission). Big 4½" square meter has clear "GOOD?-REPLACE" scale. With line-voltage indicator and line-adjust control. Choice of 16 filament voltages from 0.63 to 117 volts to check virtually all receiving tubes; blank socket for future type tubes. Universal-type selector switches permit selection of any combination of pin connections. Single-unit, pre-assembled 10-lever function switch simplifies and speeds assembly. Up-to-date illuminated roll chart lists over 600 tube types. Counter model case, 5 x 14 x 10". Easy to build. 14 lbs.

Model Y-143. Net only **\$29.75**
Y-142. Portable Case model. 15 lbs. Net **\$34.75**
Y-141. Picture Tube Adapter. 1 lb. Net **\$ 4.25**

knight-kit RF Signal Generator Kit

Model Y-145

\$1975

Build this wide-range, extremely stable RF signal generator—save two-thirds the cost of a comparable wired instrument! Large, semi-circular dial is clearly calibrated; range is covered in 5 separate bands for close accuracy in setting individual frequencies. Ideal for aligning RF and IF stages in radio and TV sets and for troubleshooting audio equipment. Delivers output on fundamentals from 160 kc all the way out to 112 mc; useful harmonics to 224 mc. Has built-in 400-cycle sine-wave audio oscillator for modulating RF; audio is also available externally. Features high-stability Colpitts circuit. Convenient jack for external modulation. Maximum audio output 10 volts; RF output over 0.1 volt on all ranges. Step and continuous-type attenuator controls. Supplied with precision-wound coils that require no adjustment. 7 x 10 x 5". Shpg. wt., 11 lbs.

Model Y-145. Net only **\$19.75**

knight-kit 1000 Ohms/Volt VOM Kit

Model Y-128

\$1695

Exceptional accuracy and versatility at amazing low cost. Ideal for service shop, lab or Amateur use. Large 4½", 400 microamp meter with separate scales for AC and DC voltage and current, decibels and resistance. Uses 1% precision resistors; has 3-position function switch and 12-position range switch. 38 ranges include: AC, DC and output volts, 0-1-5-10-50-500-5000 (1000 ohms/volt sensitivity); Resistance, 0-100-100,000 ohms and 0-1 meg (center scale readings of 60, 150 and 1500 ohms); Current, AC or DC, 0-1-10-100 ma and 0-1 amp; Decibels, -20 to +69 in 6 ranges. Precision resistors are used as shunts and multipliers to assure exceptional accuracy of measurements. With all parts, battery, test leads and black bakelite case with convenient carrying handle, 6¾ x 5¼ x 3¾". A great value in an easy-to-build quality instrument. Shpg. wt., 2½ lbs.

Model Y-128. Net only **\$16.95**

knight-kit Vacuum Tube Voltmeter Kit

Model Y-125

- 200 µa Movement, 4½" Meter
- Includes AC, Peak-to-Peak
- Balanced-Bridge, Push-Pull Circuit
- 1% Film-Type Resistors

\$2495

Top buy in an extremely stable, highly accurate VTVM. Easy to assemble—entire chassis is printed circuit board. Perfect for radio-TV service work, lab and Amateur use. Features low-leakage type switches; 1% film-type precision resistors; balanced-bridge, push-pull circuit (switch to any range without readjusting zero set); zero center scale and direct-reading db scale; polarity reversing switch. Ranges: Input Resistance, 11 megs; DC and AC rms, 0-1.5-5-15-50-150-500-1500; AC Peak-to-Peak, 0-4-14-40-140-1400-4000; Response, 30 cycles to 3 mc; Ohms, 0-1000-10K-100K and 0-1-10-100-1000 megs; db, -10 to +5. Includes all parts, tubes, battery, test leads and portable case, 7¾ x 5¼ x 4-¾". Easy to assemble. Shpg. wt., 6 lbs.

Model Y-125. Net only **\$24.95**
Y-126. Hi Voltage Probe; extends DC to 50,000 v. **\$ 4.75**
Y-127. Hi-Frequency Probe; extends AC to 250 mc. **\$ 3.45**



6V-12V Battery Eliminator Kit

\$3295

High current rating; continuously variable filtered output; delivers 15 amps at 6 volts, 10 amps at 12 volts. May be used as battery charger. Two meters provide simultaneous current and voltage readings. Shpg. wt., 18 lbs.

Model Y-129. Net only **\$32.95**



Transistor Checker Kit

\$850

Checks gain ratio of all types of transistors; checks germanium and silicon diodes; checks for continuity and shorts. A valuable instrument at very low cost. Easy to assemble. Shpg. wt., 2½ lbs.

Model Y-149. Net only **\$8.50**



Flyback Checker Kit

\$1950

Checks condition of all types of horizontal output transformers and deflection yokes, as well as TV linearity and width coils. 4½" meter; widest range in its field. Shpg. wt., 6 lbs.

Model Y-118. Net only **\$19.50**



Sweep Generator Kit

\$4375

Extreme linearity on a par with costly lab instruments; fundamentals to 250 mc; output flat within 1 db; electronic blanking. Easy, money-saving assembly. Shpg. wt., 16 lbs.

Model Y-123. Net only **\$43.75**



Capacitor Checker Kit

\$1250

Tests capacitors while in the circuit! Has widest range—20 mmf to 2000 mfd. Exclusive circuit for cancelling lead capacity. "Magic Eye" indicator. Save 60% over factory-wired units. 5 lbs.

Model Y-119. Net only **\$12.50**

ADVANCED-DESIGN INSTRUMENTS FOR SERVICE, INDUSTRIAL AND RESEARCH USE
IN EASIEST-TO-BUILD, MONEY-SAVING KIT FORM



knight-kit 20,000 Ohms/Volt VOM Kit

Model Y-140 Outstanding quality and performance at money-saving low price. Features 1% precision multipliers; 4½" meter accurate within 2% of full scale deflection; 50 microamp sensitivity for 20,000 ohms/volt input resistance on DC; front panel "Zero adjust"; single switch to select function and range. 32 ranges: AC, DC and output volts, 0-2.5-10-50-250-1000-5000; Resistance, 0-2000-200,000 ohms and 0-20 meg.; DC ma, 0-0.1-10-100; DC amps, 0-1-10; Decibels, -30 to +63 in six ranges. Moisture-resistant film-type resistors for extreme accuracy. Carefully engineered circuit design achieves high sensitivity and extremely versatile application. Kit includes all parts, battery, test leads and black bakelite case with highly legible white markings; size 6¾ x 5¼ x 3¾". Easy to assemble. Shpg. wt., 5 lbs.

Model Y-140. Net only \$29.50

knight-kit High-Gain Signal Tracer Kit

Model Y-135 A remarkable value in an easy-to-build instrument which permits visual and aural signal tracing of RF, IF, video and audio circuits. Has *highest gain in its price class*. Traces signal from antenna to speaker. Reproduces signal at plate or grid connection of any stage. Identifies and isolates "dead" stages. Features: usable gain of 91,000; "magic eye" with calibrated attenuators for signal presence indication and stage-by-stage gain measurements; built-in 4" PM speaker; combination 2-position probe, one for RF (6 mmf. input), the other for audio. Provides noise test; built-in watt-meter calibrated from 25 to 1000 watts; provision for external scope or VTVM. Binding posts provide output transformer and speaker substitution test, plus external 280 volts B+. With all parts, tubes and probe. 7x10x5". 12 lbs.

Model Y-135. Net only \$26.50

knight-kit 5" Wide-Band Oscilloscope Kit

Model Y-144 • 5 mc Width for Color TV
• Horizontal Sweep to 600 kc
• 25 mv/inch Sensitivity
• Z-Axis Input

\$69.00
Only \$6.90 down
Printed Circuit Construction
Equals or betters the performance of commercially wired scopes costing far more. Two printed circuit boards and laced wiring harness assure wiring accuracy and cut assembly time. Ideal for lab use, color TV servicing and high frequency applications. Wide sweep range—15 to 600,000 cps. Vertical response, ± 3 db, 5 cps to 5 mc; only 1 db down at 3.58 mc color burst. High vertical sensitivity of .025 rms v/inch. Input capacity, 20 mmf. Outstanding features: cathode follower inputs; 2nd anode provides 1400 volts high-intensity trace; push-pull amplifiers; positive and negative locking; frequency-compensated attenuator; Z-axis input; one volt P-P calibrating voltage; astigmatism control; retrace blanking circuit; DC positioning control. Includes CRT. 14½ x 9½ x 16". 40 lbs.

Model Y-144. Net only \$69.00
Y-148. Demodulator Probe. Net \$ 3.45
Y-147. Low Capacity Probe. 12 mmf. Net \$ 3.45



Voltage Calibrator Kit

\$12.75 Permits use of any scope as precision peak-to-peak AC voltmeter. Puts a true square-wave voltage on scope screen. Selects any voltage between .01 and 100 volts; feeds external signal direct to scope for instant comparison. Shpg. wt., 5 lbs.

Model Y-136. Net only \$12.75

knight-kit 5" General-Purpose Scope Kit

Model Y-146 • Phantastron Linear Sweep
• 25 mv/inch Sensitivity
• Printed Circuit Board
• Retrace Blanking Circuit

\$42.00
Only \$4.20 down
Feature for feature the world's best oscilloscope kit value. A stand-out in its class with all these fine features: *Printed Circuit* wiring board and laced harness for quick, error-free assembly. *Phantastron Sweep Circuit* for high linearity of sweep from 15 to 150,000 cps. *25 Multivolts Per Inch Sensitivity*—3 times that of similarly priced scope kits. *Calibration Voltage*—1 volt peak-to-peak square wave, fully regulated. *Vertical Amplifier*—frequency response ± 3 db, 3 cps to 1.5 mc (± 6 db to 2.5 mc). Includes: Directly coupled positioning controls; retrace blanking circuit; frequency-compensated vertical input attenuator; positive and negative internal sync; high 2nd-anode voltage for high-intensity trace; input capacity, 45 mmf. Kit includes CRT. 9½ x 13¾ x 17¾". 26 lbs.

Model Y-146. Net only \$42.00



Resistance Substitution Box

\$5.95 Easily determines resistor values required in a circuit. Makes available 36 standard 1-watt resistance values in 2 ranges between 15 ohms and 10 megohms, with 10% accuracy. Slide switch selects range; 18-position switch for value selection. Shpg. wt., 2 lbs.

Model Y-139. Net only \$ 5.95



Capacitance Substitution Box

\$5.95 Makes it easy to find capacitor values needed in a circuit. Provides 18 standard values from .0001 mfd to .22 mfd, ± 20%. All values are 600 volt, except .15 and .22, which are 400 volt. 18-position selector switch. Shpg. wt., 2 lbs.

Model Y-138. Net only \$ 5.95



Audio Generator Kit

\$31.50 Excellent design; range, 20 cps to 1 mc; less than .25% distortion; 600 ohm output. Ideal for hi-fi testing; offers the flat response of a lab standard. Shpg. wt., 16 lbs.

Model Y-137. Net only \$31.50



R/C Tester Kit

\$19.50 Measures capacitance and resistance. Balanced-bridge circuit; indicates power factor; tests capacitors at rated voltage. Large, easy-to-read dial and "magic eye." Shpg. wt., 10 lbs.

Model Y-124. Net only \$19.50

EASY TERMS AVAILABLE

Take advantage of the most liberal Easy Pay plan in electronics. On Knight-Kit orders totaling \$45 or more—just 10% down, small monthly payments thereafter. Low carrying charges—no "red tape."



knight-kits FOR THE RADIO AMATEUR

knight-kit All-Band Amateur Receiver Kit

Model Y-726

\$104⁵⁰

Only \$10.45 down

- Tunes 540 kc to 31 mc
- Built-In Q-Multiplier
- Constant Running HF Oscillator
- Worthy of the Advanced Ham Operator
- Printed Circuit Bandswitch
- Printed Circuit Board • 1.5 μ v Sensitivity

A sensational communications receiver value with all the selectivity, sensitivity and features of high-priced commercial units. Uses printed circuitry throughout, including the exclusive new KNIGHT-KIT printed circuit band-switch, for remarkably easy assembly. Covers 540 kc to 31 mc in 4 ranges; calibrated, electrical bandspread on 80-10 meter Ham bands; slug-tuned Hi-Q coils; continuous, VR tube-regulated B+ applied to HF oscillator lets you switch from standby to receive with no drift; built-in Q-multiplier peaks desired signal or nulls interference; delayed AVC; provision for crystal calibrator (below). Sensitivity, 1.5 microvolts for 10 db signal-to-noise ratio. Selectivity: variable from 300 cps to 4.5 kc at 6 db down. Exalted BFO injection. Controls: Main tuning, bandspread, band selector, Q-multiplier selectivity, Q-multiplier tune, null-off-peak, BFO pitch, RF gain, AF gain, BFO-MVC-AVC-ANL, off-stby-rec-cal, antenna trimmer, and phone jack. Cold-rolled $\frac{1}{16}$ " steel chassis. Handsome metal cabinet, 10 x 10 x 16 $\frac{1}{2}$ ". (Less phones, 8-ohm loudspeaker and S-meter.) 23 lbs.

Model Y-726. Amateur Receiver Kit. Net. . . . \$104.50
Y-727. S-Meter Kit for above. 1 lb. Net. . . . \$9.50



knight-kit 50-Watt CW Transmitter Kit



Model Y-255

\$38⁹⁵

Only \$3.89 down

- Ideal for the Novice
- Pi Antenna Coupler
- Bandswitching—80 to 10 Meters

There's exceptional value in this very popular bandswitching transmitter kit. Compact and versatile, it's the perfect low-power rig for the beginning novice as well as the seasoned veteran. Has bandswitching coverage of 80, 40, 20,

15 and 10 meters. Rated at 50 watts—actually operates at up to 60 watts on 80 and 40 meters. Oscillator is efficient 6AG7; final is reliable 807. Crisp, clean, cathode keying of oscillator and final. Built-in pi coupler permits use with random length antennas. Has highly effective TVI suppression. Other features not usually found in transmitter kits at this low price include: Ceramic-insulated final tank capacitor; pre-assembled switches; pre-wound parasitic chokes; ceramic coil forms; coax connector; crystal and VFO socket on front panel; power take-off jack for accessory equipment. Meter reads either plate or grid current of final. Takes crystal or VFO without circuit changes. Cabinet interior and chassis are copper-finished. Size, 8 $\frac{1}{2}$ x 10 $\frac{1}{2}$ x 8 $\frac{1}{4}$ ". With tubes and all parts for easy assembly. (Less crystal and key.) Shpg. wt., 19 lbs.

Model Y-255. 50-Watt Transmitter Kit. Net only. . . . \$38.95

knight-kit Self-Powered VFO Kit



Model Y-725

\$28⁵⁰

Only \$2.85 down

Complete with built-in power supply! Careful design and voltage regulation assure high stability. Excellent oscillator keying characteristics for fast break-in without clicks or chirps. Full TVI suppression. Has plenty of bandspread; separate calibrated scales for 80, 40, 20, 15, 11 and 10 meters; vernier drive mechanism. 2-chassis construction keeps heat from frequency determining circuits. Output cable plugs into crystal socket of transmitter. Output: 40v on 80, 20v on 40. With Spot-Off-Transmit switch for spot frequency tuning. Extra switch contacts for operating relays and other equipment. Attractive metal cabinet, 8 $\frac{3}{4}$ x 6 x 6". Ready for easy assembly. Shpg. wt., 8 lbs.

Model Y-725. VFO Kit. Net only. . . . \$28.50

knight-kit 100 Kc Crystal Calibrator Kit

Model Y-256

\$10⁵⁰

Net only

Crystal frequency standard at very low cost. Gives marker every 100 kc up to 32 mc. A "must" for marking band edges. Mounting flanges for installation in or back of receiver cabinet. Size only 1 $\frac{1}{2}$ x 1 $\frac{1}{2}$ x 3". Requires 6.3 v. at 0.15 amp and 150-300 v. DC at 3-6 ma. Trimmer for zero-beating with WWV; On-Off switch. Complete with tube, crystal, all parts and easy-to-follow instructions. Shpg. wt., 1 lb.

Model Y-256. 100 Kc Crystal Calibrator Kit. Net only. . . . \$10.50



knight-kit Amateur RF "Z" Bridge Kit



Model Y-253

\$5⁸⁵

Measures standing wave ratio (SWR) and impedance-of antenna systems; ideal for adjusting antenna systems for optimum results. Measures impedances from 20 to 400 ohms up to 100 mc; SWR to 150 mc. Any VOM may be used for null indicator. With coax input and output connectors. Meters both input and bridge voltage. Calibrated dial gives direct impedance reading; includes 1% precision resistor for precise calibration adjustment. With all parts and handy plasticized SWR chart (less meter). 2 $\frac{1}{2}$ x 3 x 4 $\frac{1}{2}$ ". Shpg. wt., 1 $\frac{1}{2}$ lbs.

Model Y-253. "Z" Bridge Kit. Net only. . . . \$5.85

ORDER BLANK

ALLIED RADIO

100 N. WESTERN AVE., CHICAGO 80, ILL.

ALLIED RADIO, Dept. RE, 100 N. Western Ave., Chicago 80, Ill.

Ship me the following KNIGHT-KITS:

Quantity	Description	Model No.	Price

\$..... enclosed. (For parcel post, include postage — express is shipped collect).

My Down Payment in the amount of \$..... is enclosed. Send Time Payment form.

Name.....

Address.....

City..... Zone..... State.....

ALL PRICES NET F. O. B. CHICAGO



Our 37th Year




FREE 1958
404-PAGE
ALLIED
CATALOG

See the 1958 ALLIED 404-Page Catalog for complete listings of more than 50 KNIGHT-KITS, covering Hi-Fi, Hobby, Test Instrument and Amateur Kits. The 1958 ALLIED Catalog is your complete Buying Guide to the world's largest stocks of everything in Electronics.

Send FREE 404-Page 1958 ALLIED Catalog.

According to Hank, you can save a lot of work by "fixing the audio first!"

speaking of DOGS

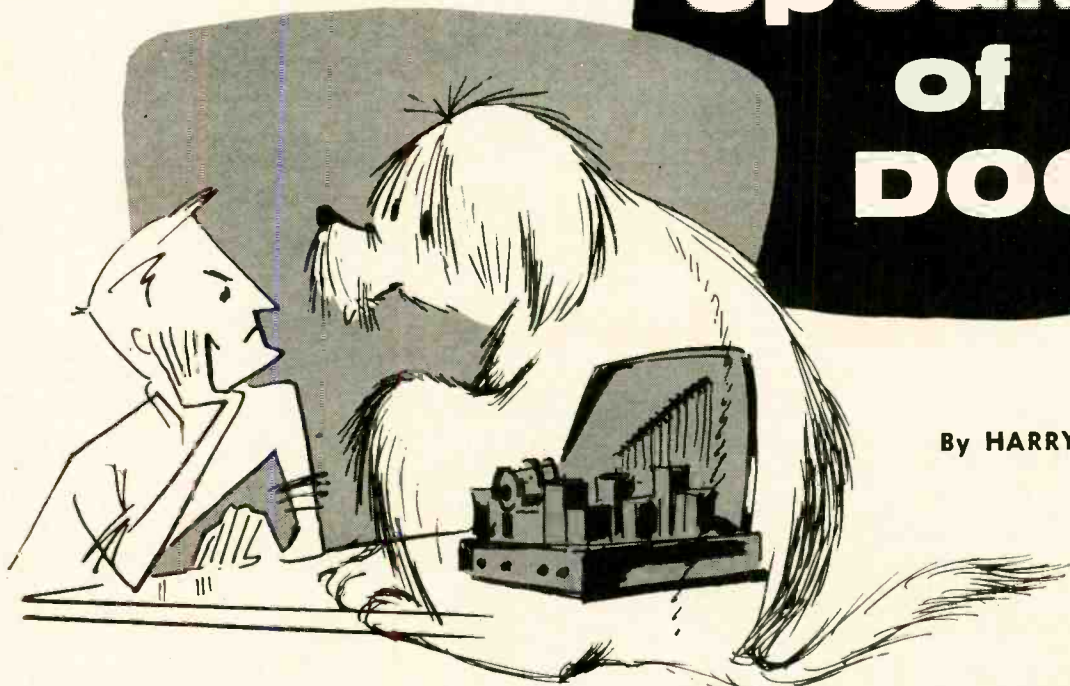

By HARRY M. LAYDEN

As usual, whenever technicians get together, the conversation took off on a single track. These two had scarcely greeted each other before the talk turned to shop. Hank, the older of the two, couldn't get a word in edgewise, as Bob, a youth of 20, yakked about a job that was giving him fits. After patiently listening to the woes of the youngster for all of 5 minutes, Hank finally got in a word.

"You may be making the job tougher than it really is. I can recall that very thing happening to me a couple of times, before I got wise to what I was doing wrong. I think you'll find out that it pays off in the long run to fix the sound first."

Bob was all ears as Hank cleared his throat to go on. "I recall a Du Mont RA-302 that was a dilly! It came in with a case of audio buzz and a picture with white lines spaced about 2 inches apart throughout the frame. Here, let me sketch the circuit so you'll be able to follow better." Hank pulled out a pencil and traced a schematic on the back of an envelope (see Fig. 1).

"Notice," the veteran continued, pointing to a network connected to the C-R tube's grid, "how retrace blanking is provided for. I sized up the problem as a defect somewhere in the vertical-retrace blanking section. The scope showed that the blanking spike was apparently OK but it certainly wasn't doing its job. I went through the circuit as carefully as a miser counts his money.

"Every part was tested, but I couldn't find anything wrong. One at a time I substituted every part, but it was no soap. By this time I was a little groggy.

Boy, was I but thoroughly pooped!"

Did you give up?

As Hank paused to get his second wind, Bob prodded him. "What happened then—did you give up?"

"You don't give up in this business, Bob! You may execute what is known in military circles as a strategic withdrawal to pull yourself together and regain your self-esteem, but you never give up.

"No, I didn't quit. But I did take a 5-minute break, off by myself, with a coke and a cigarette. That always helps.

"Then I got a bright idea. Why not, I asked myself, work on that other problem, the buzz? I'll have to fix it anyway, why not now? So, I shifted the attack and began investigating the buzz. This proved brilliant!"

"How come?" Bob wanted to know. "I don't see . . ."

"You will!" Hank cut in. "You will! I knew that buzz usually comes from either the sync pulses or the vertical sweep. It's easy to identify which is which. Simply kill the vertical oscillator. If the buzz persists it's not the source.

"In my case, the buzz disappeared the instant the vertical oscillator was pulled! Replacing the tube brought back the buzz. There couldn't be any doubt now about where the buzz was originating. Somewhere, somehow, the vertical sweep was getting into the audio."

Hank paused to light a cigarette before continuing. "It didn't take long to find the answer. The scope showed the spike at the B-plus point feeding the

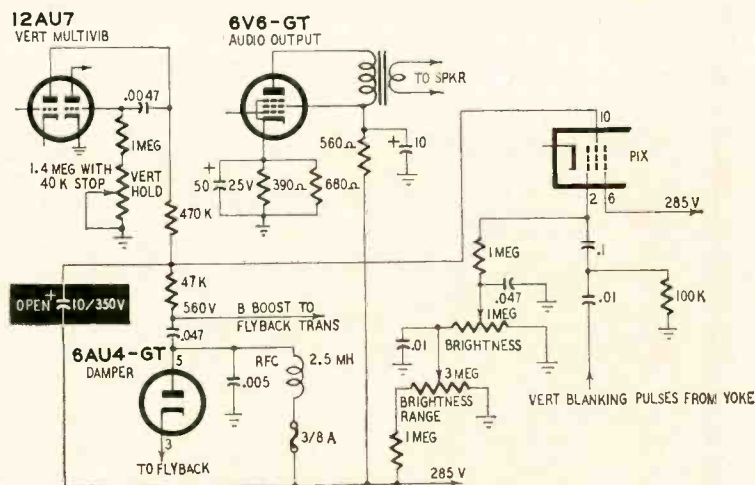


Fig. 1—Partial circuit of the Du Mont RA-302.

TELEVISION

audio output tube, even with the output tube out of its socket!

"This B-plus point is at 285 volts and is the negative return for this boost supply filter capacitor," Hank said, pointing at a 10- μ f electrolytic in the drawing.

"It's a semipolarized unit and filters and decouples the boost voltage. As long as it does its job, there's no problem. But let it develop a high power factor or lose its capacitance, then you're in trouble!

"Look here," Hank said, pointing to a spot on the schematic, "the boost voltage is the feed source for the vertical oscillator. I figured that vertical spikes would be transferred to the 280-volt B-plus if this decoupling capacitor had given up the ghost. It would then be working as a coupling device rather than the decoupler it was intended for. In less time than it takes to tell, I bridged it with a test capacitor, and both retrace lines and buzz vanished."

"The problem was licked, and was I relieved!" Hank heaved a sigh of relief, as if he had been reliving the experience all over again.

A matter of logic

"But those retrace lines," Bobby persisted, "what about them? How did they get into the picture?"

Hank smiled a bit, as he rejoined, "I was afraid you'd ask that. The answer is so ridiculously simple that I guess you'll put me down as a real boob for not realizing it sooner.

"But that's the trouble with second-guessing. The second time around, things get so simple we begin to suspect that the simplicity was in our own mental chemistry," Hank mused out loud.

"If you trace out the first anode circuit, you can't miss the answer to your question. It's connected directly to the boost voltage! See what I mean! The first anode voltage containing the unfiltered vertical spikes was intensity-modulating the C-R tube's beam at the spike repetition rate.

"It never occurred to me to check the first anode with the scope. It's rarely suspect in retrace problems and we humans are creatures of habit. I just didn't associate the two. The point that has stuck with me," Hank went on, "is that I could have spared myself a lot of grief by fixing the audio first. There's good logic behind it!"

Bob was visibly incredulous. "I don't get it. It just happened to work out that way. Why do you say fixing the sound first has logic behind it?"

"For two very good reasons," Hank replied. "First, and you'll probably agree, the sound section of a TV set is usually more straightforward and less complicated than the video section. Consequently, it's easier to troubleshoot than the more complicated picture circuits. And second, TV sets as a general rule come into the shop with one defect at a time. There may be multiple symptoms, but there is usually

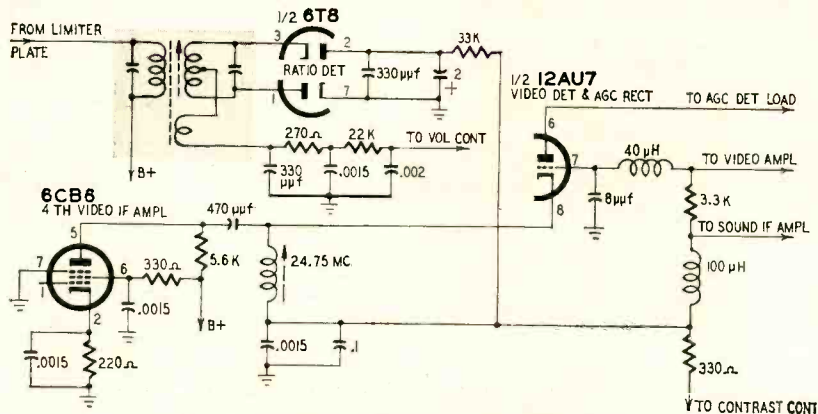


Fig. 2—Circuitry between the ratio detector and video detector in a Philco 52-T2157.

only one major defect in the cause of them all.

"Even where the symptoms stem from separate and distinct causes, it's no harder to attend to the sound first. It will have to be fixed before the job is finished anyways, and, as it may save you trouble, why not do it first?"

"I think you'll be playing the game with the odds in your favor since curing the sound symptom sometimes cures the video symptoms automatically."

Conquering a monster

"You may be right," Bob conceded. "But I don't think it will work out that way with the job I've got on the bench now." The doubt in his mind showed itself in his tone.

Hank looked at his watch, and said, "I've got a few minutes. Let's go by the shop and look at this monster."

A Philco 52-T2157 was set up on the bench for a sweep inspection of the if curve. Bob turned the equipment on, and a nice if curve was displayed on the scope.

"My trouble," Bob explained, "is that sound is getting into the picture, and the sound itself seems to have a high noise level." He manipulated the marker generator to show Hank that the clean bill of health he had given to the if circuits was justified.

Hank asked to see the service literature, and went into a huddle with it for a few moments. "Now, Bob, let's see what we can do about cleaning up the sound. As a first step, let's redraw the ratio detector circuit for quick reference (see Fig. 2).

"From what we know about the quieting action in ratio detectors (they depend on the relatively long time constant provided by the electrolytic and the load resistor), it would appear that something is wrong right here," Hank said, indicating the 2- μ f electrolytic and the 33,000-ohm resistor connected to the ratio detector.

"Remove the sweep and scope equipment and tune in a station," he requested. Bob's description of the symptoms coincided with the facts; the noise level was high and sound was definitely getting into the picture. Seeing a vtvm right at his elbow, Hank set it up for minus dc on the 10-volt range. When

the meter was applied across the electrolytic, instead of a normal steady dc reading, the pointer fluctuated in step with the sound!

"I thought so!" Hank exclaimed. "Bridging the electrolytic with a test capacitor cleared up the trouble." The noise was gone but, more amazingly, there was no sign of sound interference in the picture!

Bob stood there speechless. "I don't get it," he stammered. "How, why, this just can't be! Where's the connection? . . ."

Hank left him in the dark for a few moments, enjoying his evident discomfort. "It's like I told you before, Bob, fix the sound first," Hank pointed out. "With this electrolytic open, quieting action was lost and the sound was getting into the picture circuits by way of the video detector.

"As you can see from the diagram, the video detector's cathode returns through the coil and the 33,000-ohm resistor to the ratio detector. If this point isn't tied down to ground through the electrolytic, it floats and the unsuppressed audio modulates the video detector."

The explanation evidently rang a bell as Bob's face lit up with a giant smile. "Well, what do you know," was all he could think of. Then he was quiet for a few minutes. At last he broke the silence with, "You know, Hank, I think you have something there in that idea to fix the sound first.

"Last week I had a job in here, where there was neither picture or sound. There was a raster, but that was about all. I spent a lot of time in the video and tuner circuits and didn't find the trouble there. It was the audio output tube. It had gone dead. The cathode was the B-plus source for the if strip."

"I could have saved a lot of time if I had started the probing in the sound section. Well, we live and learn," was his sage conclusion.

Hank nodded in agreement, and added, "You'll find out, as I did, that a lot of those so-called tough dogs are really only as tough as we make them."

"I know what you mean," Bob answered, and then, with a twinkle in his eye, added, "Especially the ones that bark the loudest!"



END

Battery-powered unit
is also a voltmeter and ammeter

TRANSISTOR NULL DETECTOR and SENSITIVE INDICATOR

(Above) Completed instrument.

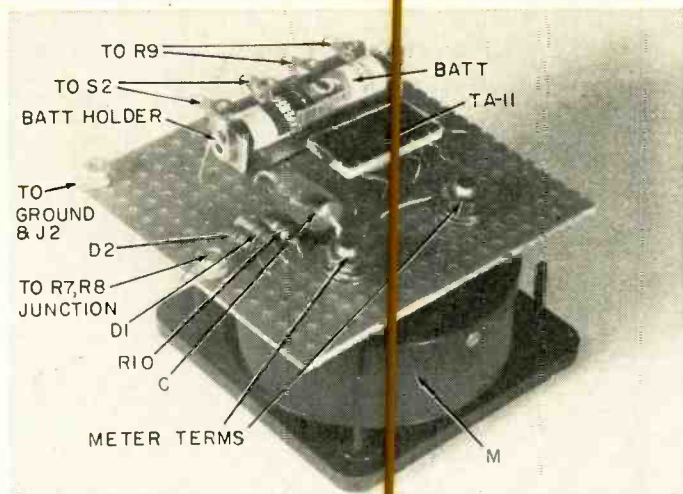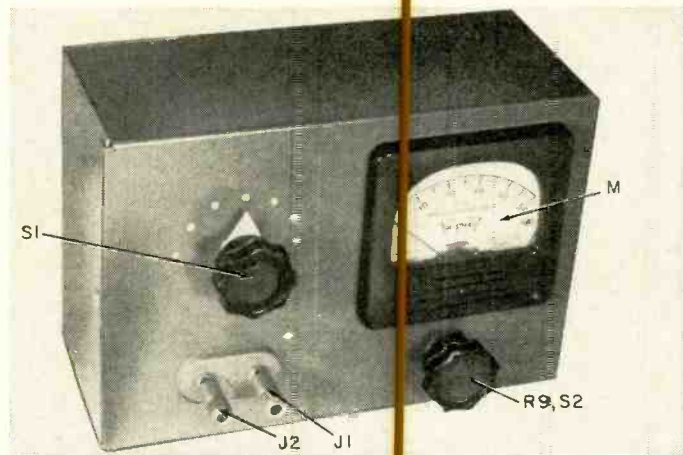(Right) Closeup of layout on phenolic board. Board is held in place by meter terminals.



By TED LADD

A BATTERY-powered null detector for ac bridges is very desirable from the standpoint of complete isolation from the power line. This type of instrument is free from the hum and interaction troubles common to line-operated devices, and requires no warmup time. However, a null detector employing battery type tubes will be microphonic unless extraordinary precautions are taken in its mechanical design. Also, such a unit is expensive to operate. Both A and B batteries are required and because of the high current drain, long life cannot be expected. The B battery type tubes will be microphonic overnight if the instrument is left running when not in use. These factors result in rather expensive upkeep. A further disadvantage is the relatively large size and weight of the batteries.

The shortcomings of the tube type null detector can be overcome by using a transistor circuit. A transistor type instrument can operate from one small, cheap 1.5-volt cell. It is nonmicrophonic, light, rugged, and requires no warmup. Its current drain is so low that no disaster results from forgetting to turn the instrument off—even if it is left on for long periods. You may accidentally leave it on overnight.

The all-transistor null detector de-

scribed here is designed for economical and reliable operation. It is self-contained, small (only 7 x 5 x 3 inches), weighs 1.5 pounds, and its dc requirements are low (4.4 ma maximum at 1.5 volts). In addition to its intended use as a balance indicator for ac bridges, it has numerous applications where sensitive ac indicators are required.

Instrument circuit

Fig. 1 is the complete circuit of the null detector. This is seen to be similar to the amplifier-rectifier type of vacuum-tube voltmeter. There are three major sections: an input-signal voltage divider (R1 to R8); a four-stage R-C-coupled, high-gain, low-noise transistor amplifier (TA-11); and an indicator circuit (C, D1, D2, M, R10). The indicating meter is a 0-50 dc microammeter.


The Centralab TA-11 is a factory-made miniature unit. It is 1.175 inches long, 0.665 inch wide and 0.250 inch thick. The complete circuit of the TA-11 can be found on page 106 of the January, 1958, issue of RADIO-ELECTRONICS. Seven pigtailed connections, numbered as in Fig. 1, are provided for external connections. This completely fabricated amplifier saves most of the assembly and wiring time required to build the null detector—46 soldered connections

are reduced to the 7 pigtail connections. All capacitors, fixed resistors and low-noise transistors that make up the four-stage amplifier are in the sealed package. Fig. 2 shows the frequency response of the TA-11.

The input voltage divider (R1 to R8 together with RANGE switch S1) provides a coarse gain control, while potentiometer R9 provides fine control. The voltage-divider resistance values specified in Fig. 1 limit the maximum input signal to 10 volts rms. A voltage-divider resistor string may be worked out for higher voltages, if desired. It needed small variations of voltage range between steps A and E of switch S1 and a large reduction between F and G. The use of 5% resistors resulted in the odd voltages shown in Fig. 1. However, you may prefer to work out a divider giving integral voltage values and even steps (such as 10 to 1), particularly if the instrument is to be used also as an ac voltmeter-millivoltmeter.

The instrument has an input resistance of approximately 81 megohms on the 10-volt range, 71 megohms for 9.1 volts, 41 megohms for 7.3 volts, 21 megohms for 4.2 volts, 1 megohm for 115 mv and 91,200 ohms for 11 mv. These high input resistances, uncommon in most transistor devices, make loading by the

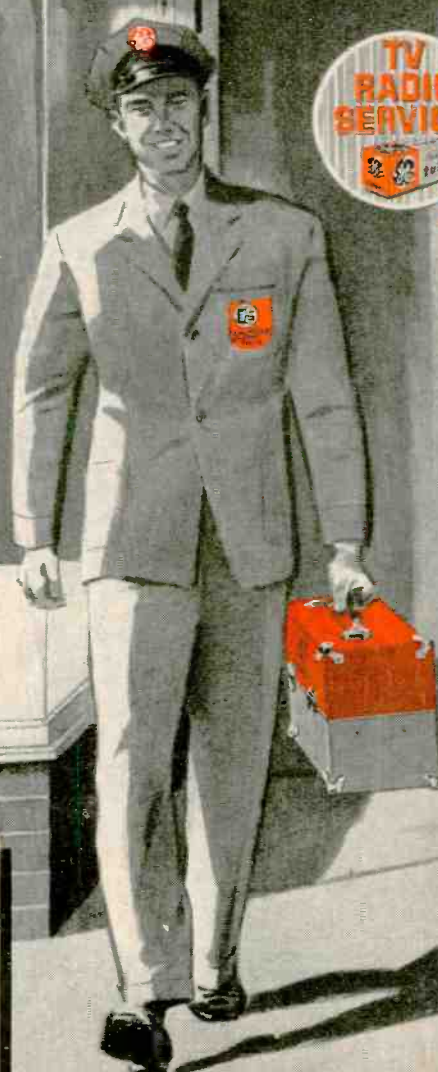*They're New...
Smart... Attract Customers..*



A. ILLUMINATED SIGN-A-RAMA. Visible for blocks. Brightly lit with six flashing lamps. Cube-faced, large—48" by 24"—gives top identification to your store or shop. Mounting hardware is included.

B. ILLUMINATED SPECIAL-MESSAGE SIGN. Carries your name, or tells any brief message you select. Ideal for windows or interiors. 37" by 14". Uses two 30-watt bulbs. Kit of letters and numerals is included.

C. DISPLAY BACKDROP. Arrange this handy rack-up display to meet your advertising needs. Material is flexible, can be curved or will mount flat. For window trim, walls, or counter-fronts. Two 36" x 24" designs per strip.

D. GIANT TUBE CARTON. Eye-arresting... indicates the quality components you install and sell.

E. DECORATIVE WINDOW DECAL. Neat attractive, new dry-apply type. 12" diameter.

GENERAL ELECTRIC'S COLOR-KEYED SHOP SIGNS!

Color-keyed to the G-E tube carton—symbol of quality!



Here is your chance to give your shop-front and windows eye-appeal with "sell". Colors of all eleven new General Electric signs and displays match handsomely the famous G-E tube carton. Quality appearance is keyed to high quality of product—a message every passerby is sure to read.

Attractive and modern, General Electric's color-keyed signs and displays also stand for leadership. They identify your shop as a source for television repairwork done to professional standards, backed by up-to-the-minute facilities.

All your display needs are met by smart new G-E designs—from an eye-catching, easy-to-apply door or window decal, to metal and illuminated outdoor and indoor signs... plus colorful utility items like the electric clock and thermometer.

These brand-new signs and displays are waiting for you now at your General Electric tube distributor's. Ask him how to obtain them! *Distributor Sales, Electronic Components Division, General Electric Company, Owensboro, Kentucky.*

- ◀ **SERVICE CLOTHING**, smartly styled, also is available. Garments are color-keyed to new G-E signs and displays—give that professional look. Durable, launder easily.
- ◀ **SERVICE CASES** in three useful sizes—small, medium, and large—match color-theme of General Electric displays. Now you can carry with you neatly, compactly, everything you need for making home service calls!

Progress Is Our Most Important Product

GENERAL ELECTRIC

11-11-102



METAL FLANGE SIGN. A display workhorse. Double-faced. Mount it anywhere! Compact—15" by 12"—handy for building corners, delivery entrances, and other side locations.



ILLUMINATED CLOCK, electric. Both useful and advertises your business. Easily read—16" diameter—with long-life bulbs. Hang on a wall, or mount on a counter (easel is provided).



HANGING METAL SIGN. For shop front or service entrance. Message both sides, plus your name-plate. Large—48" by 36"—easily seen. Hanging hardware is included; lights are available.



COUNTER-WALL-WINDOW SIGN. Illuminated. Use it anywhere in your shop! Wrap-around cover has the attractive display on both sides. 15" by 11½" by 5".




OUTDOOR-INDOOR THERMOMETER. Tells temperature accurately. Every viewer will see your advertising message. Replaceable front. 12" diameter.



METAL TACK-ON SIGN. Narrow, smart dimensions—14" by 42". Fasten against building, or mount as a free-standing display.




**TRIO®
COLORITE**

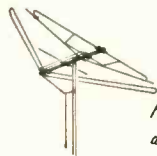

For color or black and white in areas formerly using Conicals and Conical Yagis

**TRIO®
COLOR ROYAL**

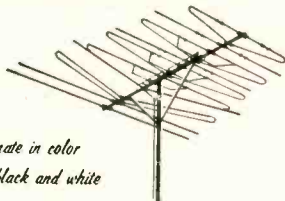

For the Ultimate in color reception or black and white

TRIO COLOR ANTENNAS FEATURE THE

magna-chrome
element system

FOR:

high forward gain

Sharper, Clearer Pictures High Signal-to-Noise Ratio

flat frequency response

Improved Contrast on Black & White

Perfect Reproduction of the Color Signal


highest front-to-back ratio

For Freedom From Co-channel Interference

TRIO® Manufacturing Company
GRIGGSVILLE, ILLINOIS

Export Sales Div., Scheel International Inc.,
5909 N. Lincoln Ave., Chicago, U.S.A.
Cable Address: HARSCHTEL

TEST INSTRUMENTS

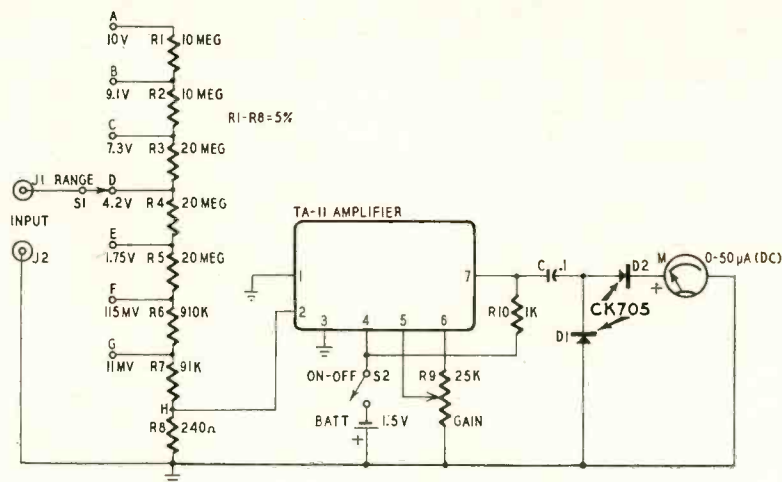

R1, 2—10 megohms
R3, 4, 5—20 megohms
R6—910,000 ohms
R7—91,000 ohms
R8—240 ohms
R9—pot, 25,000 ohms, linear taper, 10%
R10—1,000 ohms, 10%
All resistors 1/2-watt 5% unless noted
BATT—1.5 volts, penlight D-cell or mercury cell
C—0.1 μ f, metallized tubular, miniature
D1, 2—CK705 (Raytheon)

J1, 2—3-way binding posts (see text)
M—0-50 dc microammeter
S1—single-pole 11-position, nonshorting rotary switch (see text)
S2—spst switch on pot R9
TA-11—Centralab 4-stage R-C-coupled transistor amplifier
Chassis box, 7 x 5 x 3 inches
Perforated phenolic board, 3/2 x 3/2 inches
Battery holder, for battery used
Miscellaneous hardware

Fig. 1—Circuit of the handy test instrument. Use of a TA-11 printed circuit amplifier makes it easy to build.

instrument negligible.

The amplifier's output-signal voltage is developed across a 1,000-ohm resistor, R10. This voltage is coupled to the meter circuit through a 0.1- μ f capacitor, C. The meter rectifier consists of two germanium diodes, D1 and D2. In the absence of an input signal, there is no deflection of microammeter M, hence no zero-set adjustment is required and the instrument is ready for operation as soon as it is switched on. The unit's voltage response is very nearly linear.

The miniature amplifier requires connections only to the input, output, ground, battery and gain control through its seven pigtailed. The total current drain is between 3.6 and 4.4 ma dc, depending upon individual transistor parameters and resistor values within the amplifier. Since the current drain is so low and the instrument is usually used intermittently, I use a penlight cell to power it. This cell is seen in place in the photos. However, a larger, size-D flashlight cell or a 1.5-volt mercury cell might be preferable in more rugged service because of their greater milliampere-hour capacity.

With an input-signal voltage corresponding to a particular setting of RANGE switch S1, the meter will be deflected to full scale when GAIN control R9 is set for maximum resistance between its arm and ground and will be at zero when R9 is set for minimum resistance between arm and ground. Thus, by adjusting S1 and R9, the operator has excellent control of detector sensitivity during bridge-balancing adjustments.

Maximum amplifier gain, which I did not need, may be obtained by applying the input signal to point H on the voltage-divider string. Full-scale deflection of meter M then is obtained

with an input signal of only 30 mv rms.

Construction kinks

No attempt was made to subminiaturize this instrument, although you could easily make it smaller. My instrument is built into an aluminum chassis box 7 x 5 x 3 inches. It could be fitted into a meter box and, if a 1- or 1.5-inch diameter microammeter, a miniature selector switch and a dime-size potentiometer are used, it can be made pocket-size. Photos show construction.

All circuit components except the RANGE switch (S1), input voltage-divider resistors (R1 to R8), ON-OFF switch (S2), potentiometer (R9) and the input binding posts are mounted on a 3/2-inch-square panel of perforated phenolic held by the microammeter terminal screws. The leads from the TA-11 capacitor C, resistor R10 and diodes D1 and D2 are passed through nearby perforations in the board and are interconnected underneath to complete the wiring. This is a labor-saving arrangement somewhat similar to a printed circuit. Solder lugs, held by 1/4-inch 6-32 screws and nuts, are provided for connections to the external components (see photos).

The battery is held in a bracket type holder mounted on the circuit board. Select this holder for the battery you intend to use. Leads from the holder are passed through the nearest perforations and connected under the board. Leads from the meter terminal screws are also passed through perforations in the board.

The INPUT terminals are three-way binding posts on a phenolic strip (National FWH assembly). However, conventional insulated binding posts may be used. They should be spaced on 3/4-inch centers to accommodate standard plugs and patch-cord assemblies.

TEST INSTRUMENTS

The ON-OFF switch (S2) is attached to the GAIN control potentiometer (R9). This potentiometer is mounted on the front panel below the meter.

Since a 7-position selector switch is not easy to get, a standard 11-position switch is employed with a removable stop placed at the seventh position. Resistors R1 to R8 are soldered directly between the lugs of this switch.

Use the shortest practicable leads in making connections under the circuit board. Be careful when soldering the leads from the amplifier and diodes. To prevent heat damage to these components, hold the lead with long-nose pliers during the soldering operation and until the joint has cooled.

Observe battery, meter and diode polarity. Failure to do so will cause downward deflection of the meter and may damage the amplifier. Also, be sure to follow the manufacturer's number coding of the TA-11 amplifier leads.

Standard 1/2-watt carbon resistors are specified for the input voltage divider (R1 to R8). The tolerance of these resistors is entirely satisfactory when the instrument is used as a null detector and the RANGE switch serves only as an uncalibrated coarse gain control. However, precision resistors are required when the instrument is also used as an electronic ac voltmeter—millivoltmeter and a voltage divider is worked out for standard full-scale voltage ranges.

Final check

Check all wiring carefully before clipping the battery into its holder and closing the ON-OFF switch. Incorrect connections can damage the amplifier if the battery is connected.

After verifying that all wiring is correct, run a complete check on the instrument: Throw switch S2 to OFF. Set potentiometer R9 to zero-gain position. Set switch S1 to position A (10 volts). Connect an audio oscillator to the INPUT terminals. Set the oscillator to 1,000 cycles. Set the oscillator's output control to zero position. Switch on the oscillator and allow a 5-minute warm-up. Turn on switch S2. Set potentiometer R9 to maximum-gain position. Advance the oscillator output until full-scale deflection of microammeter M is obtained. Run potentiometer R9 up and down to check for smooth control of gain. Reset this control for full-scale deflection of the meter. Check operation at each of the settings of the RANGE switch, using correspondingly lower output voltages from the oscillator. A voltage calibration of the microammeter scale may be made (against an ac vtvm connected in parallel with the

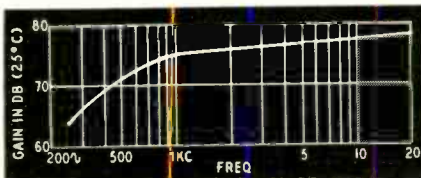


Fig. 2—Frequency response of the 4-stage amplifier.

MAY, 1958


CONTROL REPLACEMENT RECOMMENDATIONS FOR 18,000 TV MODELS!

a must
if you
service
TV!

Only \$1⁰⁰

Howard W. Sams

REPLACEMENT GUIDE FOR TV CONTROLS

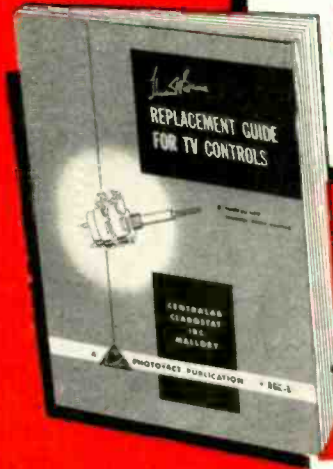

A SAMS FIRST! Lists the recommended replacement TV controls of these manufacturers:

CENTRALAB
CLAROSTAT
IRC
MALLORY

nothing
else
like
it!

IT'S EASY TO FIND THE
PROPER REPLACEMENT BY
EXCLUSIVE NEW "INDUSTRY
PART NUMBER" SYSTEM



QUICK-ACTION REFERENCE:

You'll find the original control part number (or drawing number) in the special Index Section listed either alphabetically or numerically under the TV set manufacturer's name. Opposite this listing is the exclusive "Industry Part Number" . . . such as X-400.

Simply look up the Industry Part Number (in this case, X-400), and you'll find the recommended replacement controls of your manufacturer's (Centralab, Clarostat, IRC and Mallory) listed in the columns beside it . . . takes only seconds—it's that simple!

8 1/2 x 11"

IT BELONGS
ON YOUR
BENCH!

Only \$1⁰⁰

HOWARD W. SAMS & CO., INC.

Indianapolis 5, Indiana



ORDER THIS BOOK FROM YOUR SAMS DISTRIBUTOR TODAY, OR MAIL COUPON BELOW

HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. 2-E8
2201 E. 46th St., Indianapolis 5, Indiana

Send copy(ies) of "Replacement Guide for TV Controls." My (check) money order for \$ is enclosed.

Name

Address

City Zone State

(Outside U.S.A. priced slightly higher)

You can rely on QUAM SPEAKERS in every SOUND SYSTEM installation

You get trouble-free operation and excellent sound reproduction with Quam Adjust-a-Cone Public Address Speakers. Their wide frequency response range and heavy rugged construction assure you of complete customer satisfaction.



Quam—and only Quam

Lowest possible flux loss
Accurate magnet alignment

Precise centering and
voice coil alignment

Greater heat and humidity
protection in outdoor
speakers

— gives you these important benefits:

made possible by the patented U-Shaped Pot

because of the patented Adjust-a-Cone
Suspension

with the new exclusive Humi-Gard Cone

Over 25 years of engineering "know-how" is built into every Quam speaker. EIA standards are rigidly adhered to, your assurance of top quality and performance.

Write for your free copy of Catalog S-757, describing the complete line of Quam Public Address, Outdoor and Intercom speakers.

QUAM, the quality line, for all your speaker needs

QUAM-NICHOLS COMPANY

236 EAST MARQUETTE AVENUE • CHICAGO 37, ILLINOIS

In Canada: A. T. R. Armstrong, Ltd., 700 Weston Road, Toronto 9, Ontario
D. Eldon McLennan, Ltd., 1624 W. Third Avenue, Vancouver 9, B.C.

RADIO-ELECTRONICS pays \$3.00 for good cartoon ideas
and \$15.00 and up for finished work

RADIO-ELECTRONICS • 154 W. 14 St., New York 11, N.Y.

How Many Hours Have You Used Your Stylus? (Phono Needle)

HI-FI EYE—THE RECORD PROTECTOR— can answer this honestly. CAN YOU? A worn stylus WITH ONLY ONE PLAYING can wipe all the highs from your valuable records. A simple glance at HI-FI EYE tells you the total hours your stylus has been in use. Use this simple means to protect your valuable records. Easily installed. Operation automatic. Designed to sell for \$24.95. **SPECIAL INTRODUCTORY OFFER \$14.95.** Don't delay, order today. Guaranteed. 6 months warranty. No C.O.D.'s. California add 4%.

E.I.S. Box 44739
Hancock Station
Los Angeles 44, Calif.

• NO HOOK-UPS • NO ADJUSTMENTS TO MAKE

STOP TV and RADIO TUBES from BURNING OUT!



Amazing New "Tube-Guard"
**GUARANTEED To Extend The Life
of ALL TYPES of Electronic Tubes.**
SAVE \$20 to \$100 Per Year On
Costly TV Tube Replacements.

Tried and tested and proved 100% effective for three years and longer by a well-known TV laboratory. Just plug your Television or Radio Cord into "Tube-Guard," which then plugs into your electric outlet. "Presto!"—it works like a Rheostat. Automatically controls application of electricity, eliminating current surges which causes tube burnout. **Finest Insurance You Can Buy—Works on • Television Set • Radio • Hi-Fi Equipment • Phonographs • Tape Recorder, Etc. Only \$2.00 ppd.**

Satisfaction Absolutely Guaranteed Or Money Back
Scott Mitchell House, Dept. T-RE, 611 Broadway, N.Y. 12, N.Y.

TEST INSTRUMENTS

oscillator at the INPUT terminals) at any desired setting of S1—with potentiometer R9 set for maximum gain.

Other uses

In addition to its intended use as a bridge null detector, this transformerless instrument may be employed for other purposes requiring a sensitive ac indicator with high input impedance:

Af signal tracer. With its negligible loading of a circuit under test, the instrument is well suited to signal tracing in audio amplifiers and other audio systems. For this purpose, connect a shielded probe to the high INPUT terminal and connect the low INPUT terminal to the chassis (or B-minus) of the system under test. The meter gives visual indications of signal strength and, if potentiometer R9, range switch S1, and the meter scale are voltage-calibrated, gain and loss may be determined from the deflections obtained at successive test points.

Rf signal tracer. For this application, connect a shielded, crystal type demodulator probe to the high INPUT terminal. Connect the low INPUT terminal to the chassis (or B-minus) of the system under test. As in the preceding application, the meter gives a visual indication of signal strength. Gain and loss may be determined from successive deflections if the instrument has been voltage-calibrated.

Electronic ac voltmeter—millivoltmeter. If the instrument is used as a voltmeter, precision resistors will be required for R1 to R8 (1% or better), and the input voltage divider must be worked out in the conventional manner for the desired full-scale voltage ranges. The instrument must be voltage-calibrated. Voltage calibration and voltage measurements are made with potentiometer R9 in its maximum-gain position.

Ac ammeter. Here, the instrument is first calibrated as a direct-reading voltmeter. When a precision 1-ohm resistor is connected across its INPUT terminals, it then will indicate ac amperes. Ac milliamperes will be indicated on the millivolt ranges. A battery-operated electronic current meter of this type has the advantage that both input terminals can be above ground, as they frequently must be when measuring signal currents, without introducing the disturbances that line-operated instruments do when used in this manner.

Sensitive indicator. As a sensitive, high-impedance indicator, the instrument has various applications: Tuning indicator in filter adjustment and testing. Resonance and intensity indicator in field-strength meters utilizing modulated rf input. Output indicator for repetitively operated piezoelectric devices. Hum-field locator when used with an inductive probe. Leakage current checker in small-signal ac devices. In other words an extremely useful, general-purpose instrument you'll be glad to own.

END


IF JOBS LIKE THESE ARE "ON YOUR MIND"...

... but you can't qualify because you lack

ADVANCED TECHNICAL KNOWLEDGE...

SEND NOW FOR CREI'S NEW FREE BOOKLET

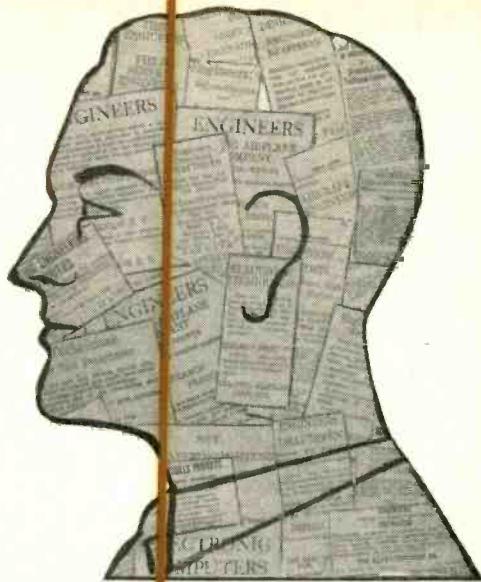It's crammed with facts and data—containing a time-proved plan to make you ready for the big jobs and a high-salaried career now being offered in



**ELECTRONICS — TELEVISION — BROADCASTING — GUIDED MISSILES — INSTRUMENTATION
RADAR — COMPUTERS — AUTOMATION — ASTRONAUTICS — SERVOMECHANISMS
AERONAUTICAL ELECTRONICS — TELEMETERING — COMMUNICATIONS — MANUFACTURING**

The want ads above are real ones . . . they appear almost daily in magazines and newspapers—all over the country. They show how desperately the electronics industry needs trained men. On the other hand, they give you a good idea of what opportunities await you—if you get advanced technical training now. And no wonder trained men are needed! Look what's happening in "astronautics," of which the earth satellite is just the most recent, but by no means the ultimate example. Computers, Radar, Aeronautical Electronics—all are booming—all need trained electronics men. Top manufacturers sold upwards of 13.5 billions of dollars worth of electronic equipment last year. By 1965 it's expected the radio-electronics industry will do about 22 billion dollars of business per year.

What do these figures mean to you? They mean that thousands of new electronic jobs have been added to the great, expanding field of electronics.

LITERALLY THOUSANDS ARE NEEDED!

You are needed—for development, research, design, production, testing, inspection, manufacture, broadcasting, telecasting, servicing. But you can qualify only if you take time to advance your knowledge . . . if you take 2 minutes right now to write for the free CREI booklet, with no obligation.

SHORTEST DISTANCE TO A GOOD CAREER IS CREI TRAINING

If you follow the plan outlined in our free booklet, you will be in line for promotion and pay increases in short order. Read what these typical CREI graduates have to say:

"In this time of less than two years, I have almost doubled my salary and have gone from wire-man to engineering assistant and now to junior engineer. I have CREI to thank."—Frank A. Eckert, 22 Clover Lane, Levittown, Pa.

"I chose CREI training upon recommendation of two top engineers. Before I completed the course, I became transmitter chief of a 5 kw station. I am now employed as a technician at a 100 kw TV station and in spare time have a good TV sales and service business."—Arlie D. Patton, 203 Burke Ave., San Antonio, Tex.

By method, experience, and personnel—CREI is equipped to teach you what

you will need when you translate your study into work. As proof that CREI knows what industry wants, many leading companies recommend CREI training for their own personnel. Among them: United Airlines, Canadian Broadcasting Corporation, Trans-Canada Airlines, Douglas Aircraft Co., The Martin Co., Columbia Broadcasting System, All-American Cables and Radio, Inc., Gates Radio Co., Canadair Ltd., Federal Electric Corporation, and U.S. Information Agency (Voice of America).

TOP FIRMS LOOK FOR CREI MEN

A CREI diploma itself is ample proof to many leading companies that a man is worth hiring. Moreover, employers contact us regularly for graduates to fill good jobs. Our placement bureau cannot keep up with the demands.

What do you want? To pass FCC exams? Start your own business? CREI has helped others reach these goals, and can help you. Or, do you want to go after good-paying electronics jobs, secure, permanent careers like those advertised above? Whatever your choice, CREI can help you as it

has helped thousands of men—provided you have the ambition to follow the plan.

CREI ALSO OFFERS RESIDENCE TRAINING

CREI Residence School in Washington, D.C. offers training at same high technical level. Classes start at regular intervals. Qualified residence school graduates earn degree: "Associate in Applied Science." Check coupon if you prefer residence study.

VETERANS

If eligible for training under the new G.I. Bill of Rights, check the coupon for full information.

What's the next step? Certainly get more information. Mail the coupon below today, or write Capitol Radio Engineering Institute, Dept. 145-Y, 3224 16th St. N.W., Washington 10, D.C.



MAIL FOR FREE BOOKLET

CAPITOL RADIO ENGINEERING INSTITUTE

ECPD Accredited Technical Institute Curricula • Founded 1927

Dept. 145-Y 3224 16th St. N.W., Washington 10, D.C.

Please send me your course outline and FREE illustrated Booklet "Your Future in the New World of Electronics" . . . describing opportunities and CREI home study courses in Practical Electronic Engineering Technology.

- CHECK FIELD OF GREATEST INTEREST
- Radar, Servo and Computer Engineering Technology
 - Electronic Engineering Technology
 - Broadcast (AM, FM, TV) Engineering Technology
 - Television Engineering Technology
 - Aeronautical Electronic Engineering Technology

Name _____ Age _____
 Street _____
 City _____ Zone _____ State _____
 Check: Home Study Residence School Korean Veteran

NOT FOR BEGINNERS.

If you have had a high school education and experience in electronics, and realize the need of high-level technical knowledge to make good in the better electronic jobs—you can qualify for CREI home study training. (Electronics experience is not required for admission to CREI Residence School.) Please fill in the following information:

Employed By _____
 Type of Present Work _____
 Education: Years High School _____
 Years College _____
 Electronics Experience _____

VTVM Calibrator

*Is the ac scale on your vtvm accurate?
Here's a simple instrument to make
and keep it so*

By J. H. SUTTON

OF the thousands of vtvm kits currently being sold and assembled, probably very few have their ac calibration control adjusted accurately. This is in contrast to the probability that most dc calibration controls are accurately set.

Assuming that the kit is a good one and properly assembled, the builder can adjust the dc calibration control to near laboratory accuracy by using a 1.55-volt dry cell. However, the voltage for adjusting the ac calibration control usually comes from the power line, either directly or through a stepdown transformer, and here is the difficulty. What precise value is the line voltage?

The instruction book may say to assume that the line voltage is 117 or that a stepdown transformer delivers 6.3 volts. Either assumption can be wide of the mark. I figured on a 117-volt line while adjusting my meter but later found out, by reference to a laboratory meter, that line voltage was actually about 122. Here was an error of 4.5%, which might be additive to the rated 5% error of the instrument.

A similar check of my meter showed that the dc calibration control adjustment had been quite accurate—the deviation being less than 1%.

What is needed is a good, secondary method of calibration (primary method is with a laboratory standard meter) the accuracy of which depends upon the known value of a standard dc source (a mercury or dry cell), the accuracy of a dc meter calibrated by such a cell and a method of equating this dc calibration to an ac source.

Equating dc and ac voltages is achieved in the ordinary vom by rectifying the alternating voltage and

indicating the direct voltage on an ac-equivalent scale. In a similar manner, most vtvm's equate ac to dc voltages derived from the same source.

If, with our vtvm connected across a given resistor, we can measure in sequence a half-wave pulsating voltage and a full-wave alternating voltage, both derived from the same source, then these voltages will be mathematically related to each other:

$$\frac{\text{rms value of alternating full wave}}{\text{average value of pulsating half wave}} =$$

$$\frac{0.71}{0.32} = 2.2$$

or as mathematicians express the relation:

$$\frac{\pi}{\sqrt{2}} = 2.221$$

This relationship is used in the vom. The basic circuit employed is seen in Fig. 1. I have added an ac tap and variable resistor R3. M is the meter, for our purposes a vtvm. RECT 1 and RECT 2 are selenium rectifiers. When RECT 1 is connected to the dc tap, pulsating dc flows through resistor R1. When RECT 1 is connected to the ac tap, alternating current will flow through R1. As R1's precision does not enter into the accuracy of the result, it can be any resistor whose value is known within 10 or 20%. The only

requirement is that its value remains constant. R3 is variable in order to adjust the voltage across R1 but it is a convenience, not a necessity.

Selection of R1 depends partly upon the calibrating voltage we wish to drop across it. This voltage should be the full amount, or nearly so, of the 12- or 15-volt ac scale since this is possibly the lowest ac scale which, around full value, is reasonably certain to have linear response. At and below 5 volts ac, the signal rectifier of most vtvm's has a nonlinear response and the more expensive meters have special scales to show this. By choosing the 12- or 15-volt scale we go above the area of signal-rectifier nonlinearity.

Building a calibrator

Since it is desirable to check the calibration of a vtvm periodically, the circuit was set up in permanent fashion as shown by Fig. 2 and the photos. The chassis is a transparent cake-slice box. This, like other plastics, can be drilled safely only with a hand drill while the plastic is backed by a wood block. Drill positions on this chassis can most easily be fixed by attaching a template with Scotch tape.

Potentiometer R3 is used to adjust the dc reading to 6.75 volts, from which the calibration voltage is 15 volts ac (6.75 × 2.22). The 6.75 volts can be easily interpolated as corresponding to


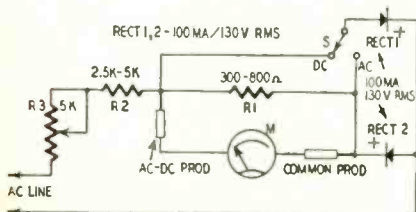


Fig. 1—Basic calibrator circuit.

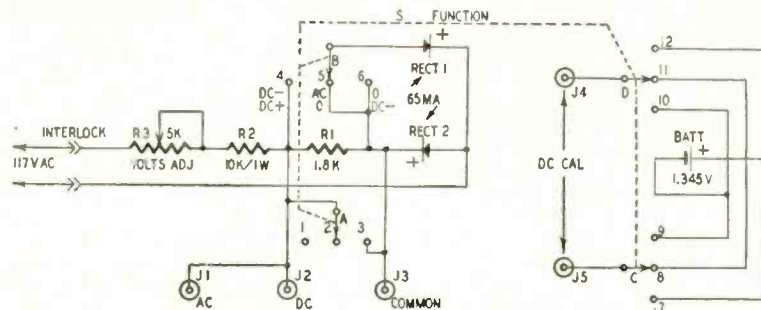


R1—1,800 ohms, 1/2 watt, 10%
R2—10,000 ohms, 1 watt, 10%
R3—pot. 5,000 ohms, carbon, 1 watt
BATT—1.345 volts, mercury (Mallory RM625R or equivalent)
J1—J5—tip jacks

RECT 1, 2—selenium rectifiers, 130 volts rms, 65 ma
S—4-pole 3-position rotary, nonshorting (Mallory 3243J or equivalent)
Interlock receptacle and line cord, TV type Case, wedge-shaped cake-slice box

Fig. 2—Calibrator for ac and dc ranges of your vtvm.

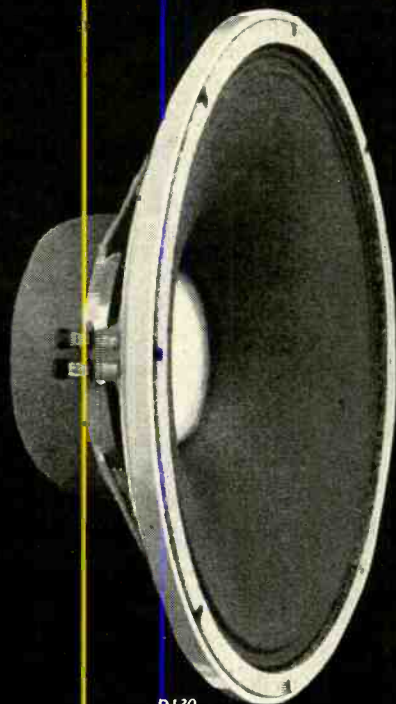**BUILD
YOUR
OWN JBL
ACOUSTICAL
ENCLOSURE
FROM
DETAILED
PRODUCTION
PRINTS**



D130




175 DLH


get the greatest thrill!

high fidelity can give you...

THE HARKNESS Model C40

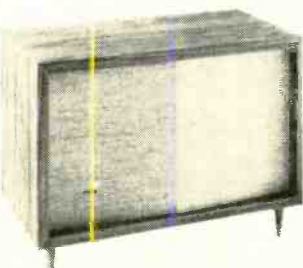

Model C34

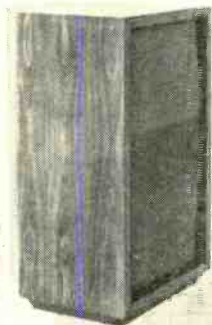


full range, rich, clean sound from precision JBL Signature loudspeakers mounted in an acoustical enclosure you make with your own hands. Reward your painstaking craftsmanship with speakers designed for the perfectionist. JBL Signature units, such as the Model D130, are acknowledged by foremost authorities to be the finest made. The D130 is the only 15" extended range speaker made with a 4" voice coil. It is unsurpassed in efficiency and transient-handling ability. The JBL Model 175DLH gives you smooth, crisp reproduction of frequencies above 1200 cps. The 175DLH is equipped with an acoustical lens, an exclusive JBL development, for even distribution of highs over a 90° solid angle. Any speaker, if it is to give you accurate bass reproduction, must be mounted in a properly engineered acoustical enclosure.

BUILD A JBL BACK-LOADED FOLDED HORN

Designed specifically for the JBL D130, the JBL back-loaded folded horn is probably the most widely-used enclosure of its type ever manufactured. The cabinet is relatively small—less than 40" in its greatest dimension—and yet, ingeniously folded within, is an exponentially tapered horn path with an effective length of six feet. The horn adds an octave of accurate, clean, deep down bass. There are two versions of the horn: Model C34 stands vertically and may be placed in a corner, although corner placement is not required. Model C40, the Harkness, is a low-boy folded horn that is independent of wall or corner for proper functioning. Prints are designed for direct, simple, clear instruction, and time-saving construction. Cost is three dollars per set.

USE THIS FORM TO ORDER YOUR PLANS

Now you can build this most popular JBL enclosure from detailed production prints which include a complete list of materials, all dimensions, and instructions for assembly.



JAMES B. LANSING SOUND, INC.
3249 Casitas Avenue, Los Angeles 39, California

Gentlemen:


Enclosed find \$ _____ for

_____ Model C34 Production Prints @ \$3.00 per set.
_____ Model C40 Production Prints @ \$3.00 per set.


Please print clearly or type your name and complete address:

Name _____
Address _____

TEST INSTRUMENTS

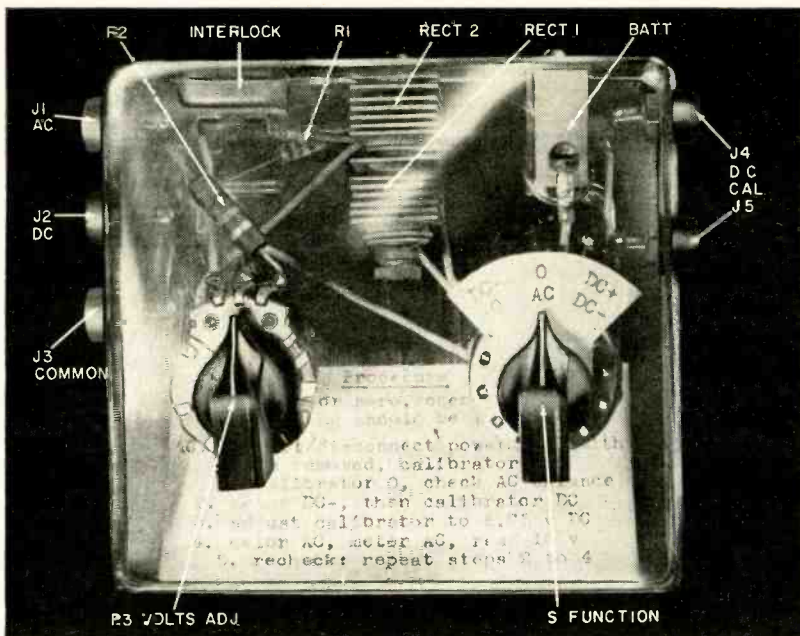

Top view of completed calibrator.

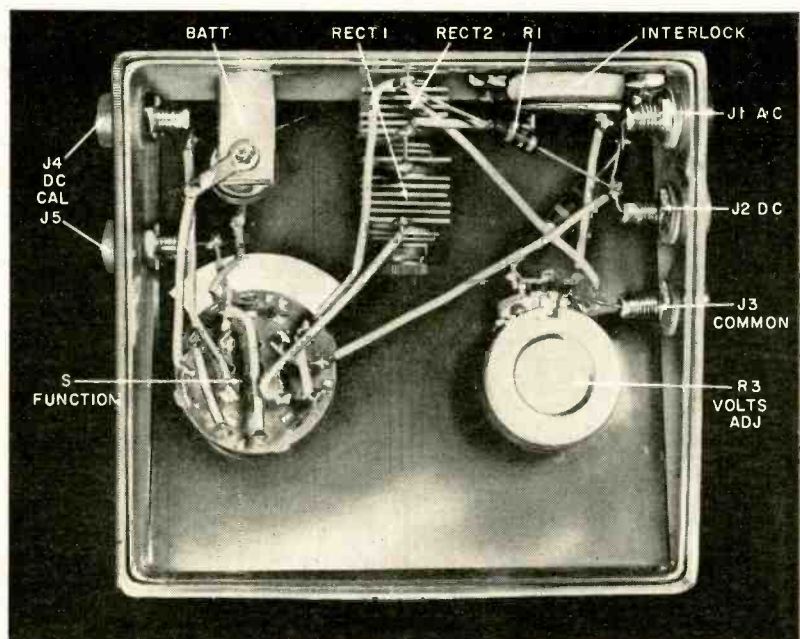

Bottom view shows simple layout of the few components.

2.25 volts on the 5-volt scale, provided your dial has 15- and 5-unit linear divisions.

The selenium rectifiers are fastened together and to the chassis with a common bolt through their center. The vtvm prods plug into tip jacks on the side. If the vtvm common prod is equipped only with a clip, a phone tip can be inserted in the common jack and the clip attached. The calibrator is connected to the ac line with a TV cheater cord and interlock receptacle.

Also incorporated in the device is a circuit for dc calibration from a 1.345-volt mercury cell, and switch S is wired so that the circuit for dc calibration is completely isolated from the circuit for ac calibration. In lieu of the mercury cell, you may wish to use an ordinary

penlight cell—there is plenty of room.

Looking at the switch from the underside (Fig. 3), contacts 1-6 are for ac calibration while contacts 7-12 are for dc calibration. The latter connections are arranged so that the cell terminals reverse for easy comparison of the dc- and dc+ calibration readings. Because of the dc circuit, a nonshorting switch must be used.

The holder for the mercury cell is home-rolled and is detailed in Fig. 4. The mercury cell fits in the cup and is held in place by the tire valve spring which also furnishes contact pressure for both electrodes. The bottom of the cup is coated with solder to provide a bright surface for electrode contact.

It is possible to buy these cells with leads attached to both terminals

(RM625RT). If you get one of these, the cell leads can be soldered directly into the circuit. In the absence of such leads, solder directly to the cell but be careful as heat may damage it.

Using the unit

To use the calibrator follow these instructions: Warm up the vtvm for an hour or more before starting and make sure that its zero adjust is properly set. Now set the vtvm for dc. Plug the meter leads into J4 and J5. Using the calibrator's top scale (DC-, 0, DC+), set at 0. The meter should read 1.345 volts dc.

Now set the vtvm on ac. Connect the calibrator to the ac line. Plug the meter leads into J1, J2 and J3. Using the calibrator's bottom scale (0, AC, DC-), set the calibrator at 0 and check ac balance. Switch the vtvm to dc-, and then the calibrator to DC-. Adjust R3 on the calibrator for a 6.75-volt dc reading on the vtvm. Next set the calibrator to AC and the meter to ac. Set the vtvm's ac calibration control to give a reading of 15 volts ac. Recheck once or twice.

With this switching system, the calibrator can be turned to zero without meter disturbance, whether the meter is in the ac or dc position. If the meter is set to dc, the momentary switching of RECT 1 out of the circuit will give the needle a minor up-scale flick which will not upset the zero adjust. Note that this adjustment may be upset if the calibrator is connected or disconnected with the vacuum-tube voltmeter's prods in and the calibrator not set at 0. END

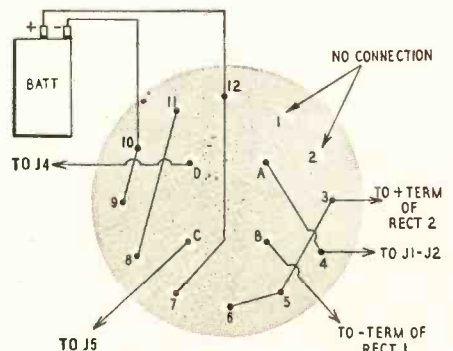


Fig. 3—Wiring the function switch.


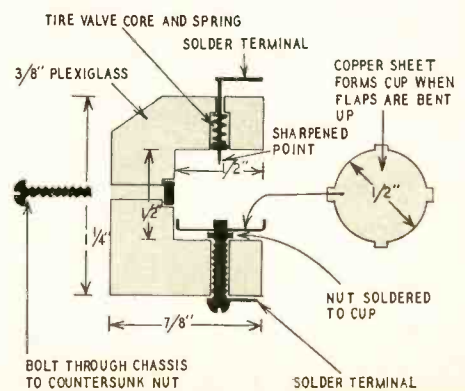


Fig. 4—Holder for the mercury cell.

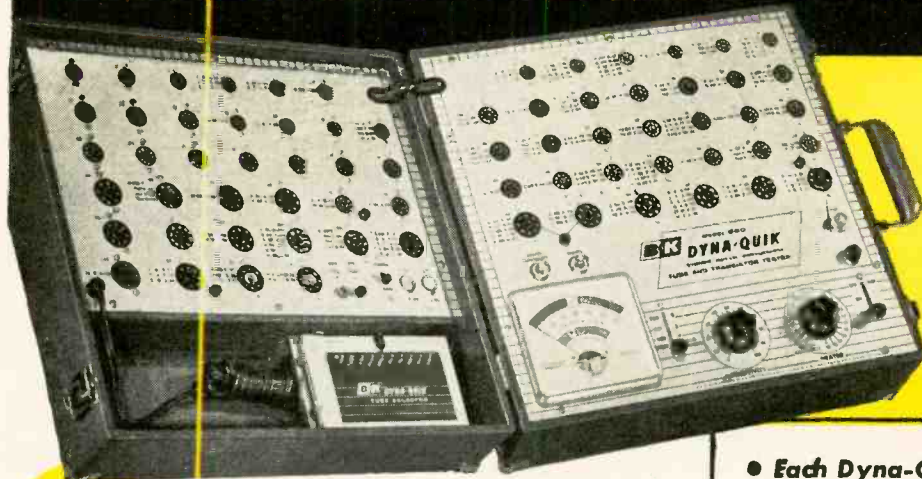Cut testing time in half— DOUBLE TUBE SALES



B&K
DYNA-QUIK
Makes Money for
Servicemen Everywhere

**NEW
MODEL
650**

Fastest, Most Complete, Portable DYNAMIC MUTUAL CONDUCTANCE TUBE & TRANSISTOR TESTER

Checks over 99% of the tubes most widely used in television receivers, plus popular home and portable radio tubes. Tests over 500 tube types. Lists over 125 tube types, with settings, on socket panels for maximum operating speed. Complete listing in fast telephone-index type selector. Includes 16 spare sockets and sufficient filament voltages for future new tube types. Tests each section of multiple tubes separately for Gm—Shorts—Grid Emission—Gas Content—and Life. Provides instantaneous Heater Continuity check. Shows tube condition on "Good-Bad" scale and in micromhos. Special bridge assures automatic line compensation. No multiple switching—No roll chart. Includes pin straighteners. Transistor Tester checks junction, point contact and barrier transistors, germanium and silicon diodes, selenium and silicon rectifiers.

Net, **\$169⁹⁵**

- Each Dyna-Quik Tube Tester completely tests each tube in seconds
- Eliminates substitution testing
- Shows customer true condition and life expectancy of tubes
- Sells more tubes right on-the-spot
- Cuts servicing time, wins customer confidence
- Saves costly call-backs, brings more profit

One extra tube sale on each of 5 calls a day pays for the Dyna-Quik in a few weeks.

NEW MODEL 500B Money-Making Portable DYNAMIC MUTUAL CONDUCTANCE TUBE TESTER

Thousands of the famous B&K Dyna-Quik are in profitable use today by service technicians everywhere. Servicemen say: "Best tube tester I've ever owned for speed and dependability!" "Makes money. Really indispensable!" "Have two...one for the shop and one for house calls!"

Now, with more tube sockets, the new Model 500B makes it easy to test more tubes faster and make more money. Accurately quick-checks most of the TV and radio tubes usually encountered in everyday service work. Tests tubes for shorts, grid emission, gas content, and leakage. Measures true dynamic mutual conductance with laboratory accuracy in the home or shop. Makes complete tube test in seconds, tests average TV set in a few minutes. Quickly detects weak or inoperative tubes. Shows tube condition on "Good-Bad" scale and in micromhos. Life Test shows customer the tube life expectancy. Makes it easy to sell more tubes right-on-the-spot.

One switch tests everything. No multiple switching. No roll chart. Automatic line voltage compensation. 7-pin and 9-pin straighteners. New tube reference charts are made available by the factory at regular intervals.

Net, **\$129⁹⁵**




2 additional tube sales per call on an average of 5 calls a day can increase your income as much as \$50.00 per week

See your B & K Distributor or write for Bulletin AP10-E



B&K MANUFACTURING CO.
3726 N. Southport Ave., Chicago 13, Illinois
Canada: Atlas Radio Corp., 50 Wingold, Toronto 10, Ont.
Export: Empire Exporters, 458 Broadway, New York 13, U.S.A.

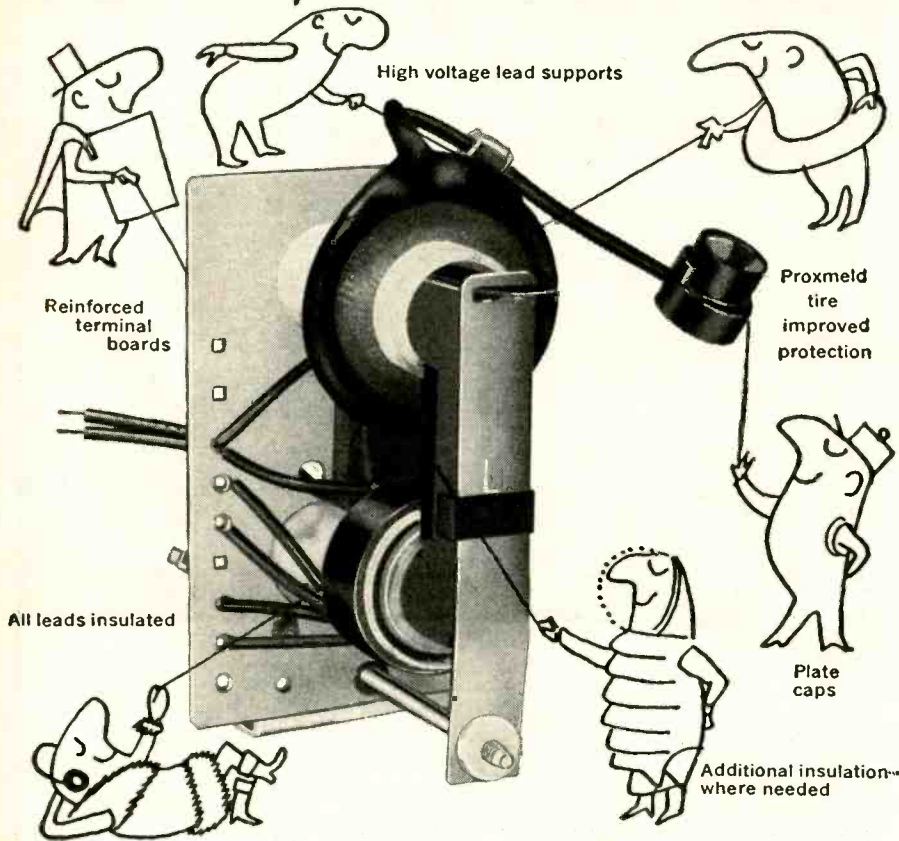You get these *plus* features with STANCOR



Stancor, the pioneer in the field of exact replacement flybacks, now goes one step further. The Stancor replacement represents an *improvement* over the original manufacturer's units. Additional features—like those above—are added when necessary to insure optimum performance. Stancor flybacks are engineered and improved replacements to help make your work more efficient and more reliable.

FREE —a new 100 page TV Replacement Guide with a brand-new format. Locates the replacement immediately—with or without the original part number. Models listed individually in numerical order. See your distributor or write us for your free copy.



CHICAGO STANDARD TRANSFORMER CORPORATION

3509 Addison Street • Chicago 18, Illinois

Export Sales: Roburn Agencies, Inc. • 431 Greenwich Street • New York 13, N. Y.

The **JUNE** issue of **RADIO-ELECTRONICS**
goes on sale **MAY 22**

Reserve Your Copy Now at Your Local Newsstand

ENGINEERING

**B. S. DEGREE
IN 27 MONTHS**



Prepare for unlimited opportunities of the Electronic Age! Earn your B.S. DEGREE IN 27 MONTHS in Aeronautical, Chemical, Civil, Electrical or Mechanical Engineering; in 36 MONTHS in Mathematics, Chemistry, Physics. Intensive, specialized courses. Comprehensive training in electronics, television, advanced radio theory and design, math, nuclear physics and elec. eng. Engineering Science preparatory courses. Low rate. Graduates in demand. Spacious campus; 20 bldgs., dorms, gym, playing field. Earn part of your expenses in Fort Wayne. G.I. approved. Enter June, Sept., Dec., March. Catalog.

INDIANA TECHNICAL COLLEGE
1758 E. Washington Blvd., Fort Wayne 2, Indiana

Please send me free information on B.S. ENGINEERING DEGREE IN 27 MONTHS as checked.

Electronics Chemical Aeronautical
 Civil Mechanical Electrical
B.S. DEGREE IN 36 MO. in: Math. Chem. Physics

Name.....
Address.....

"A Serviceman's Service"

**ALL MODEL TELEVISION
TUNERS REPAIRED**

\$8⁰⁰ plus necessary
tubes and parts

5-DAY SERVICE after receipt. 90-Day Warranty on parts and workmanship.

Send Your Tuners in Now

Television Tuner Service Co.
2534 Rusty Dr. Des Plaines, Ill.

Technicians' News



VOTES IN SAN ANTONIO

The San Antonio Radio & Television Association (SARTA), San Antonio, Tex., held an election and voted the following persons into office: C. W. Schertz, Lone Star TV Center, president; O. O. Brigman, Brigman Radio & TV, vice president; Don Van Der Brugen, Sight & Sound of San Antonio, secretary; Tom Boyd, Boyd's Radio & TV Service, treasurer. Ralph McCoy, City-Wide TV Service, and Roland Mueller, M & M TV Service, became directors.

ARTSNY HOLDS ELECTION

Officers of the Associated Radio-Television Servicemen of New York Inc. (ARTSNY) for 1958 are: Marty Boxer, president; Max Leibowitz, executive secretary; Phil Goldfarb, treasurer. In the technical chapter: Peter La Presti, vice president; Jacob Allen, recording secretary; O. Capetelli, corresponding secretary; John Bush, sergeant at arms. In the business chapter: Charles Edward, vice president; Lou Gioa, recording secretary; Jack Sperling financial secretary; Bob Mulwitz, sergeant at arms. To the board of directors: Frank Joseph, Harry Magar, Harry Temler, John Wagonny, Harold Levinson, Harold Goodman, Harold Landfield, Henry Ruscoll, Charles Anglone, Jack Spegal, John Burns.

SERVICE GROUPS COMBINE

Three Philadelphia TV Service groups have combined to form a new association called the Television Service Association of Delaware Valley. The new association is made up of 300 members from the Northeast Service Dealers Association, the Philadelphia Radio Servicemen's Association, and the Television Dealers association of Philadelphia.


Officers of the new group are: Ray Cherrill, Cherrill Radio & TV Service, president; John S. McCloy, McCloy's TV Service, vice president; Harvey Morris, Harvey's Radio & TV Service, secretary; Louis J. Smith, corresponding secretary; Jack Rubin, Delaware Valley TV Service, treasurer.

On the board of directors are: Samuel Brenner, Ray Fink, Albert M. Haas, Charles Knoell and Ralph Newby.

NEW TESA OFFICERS

At a banquet held at the Chestnut Lodge in Buffalo, N. Y., the Television & Electronics Service Association (TESA) of Greater Buffalo installed Irving Toner as their president. Other

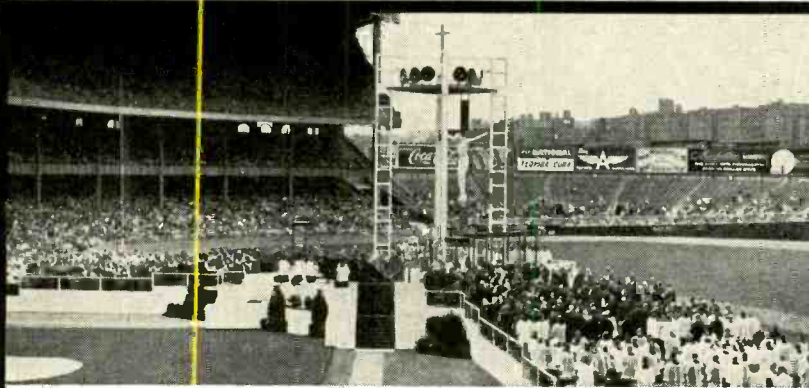When EXPERTS need quality high fidelity ...they CHOOSE *University* SPEAKERS



FOR UNUSUAL STADIUM FUNCTION The vast expanses of Yankee Stadium were converted to an open-air cathedral for the mass offered by Francis Cardinal Spellman, R.C. Archbishop of New York, to mark his 25th Anniversary as Bishop.

"The Yankee Stadium is well-known for its acoustic difficulties. The specific problem for this special event was to cover hundreds of thousands of square feet with true high fidelity reproduction of voice, organ and choir without reverberation and echo effects. With a single group of University speakers mounted over the altar, we were able to 'saturate' the stadium with highest quality sound that the N.Y. Times called 'cathedral-like' in its front page story. What's more, the high efficiency and distortion-free characteristics of the speakers enabled us to use remarkably low amplifier power."

Edward P. Casey, President
Edward P. Casey Sound Systems, Inc., New York



FOR PROFESSIONAL RECORDING STUDIO The Crew Cuts, well-known recording artists, are shown monitoring playback of the master tape to check over-all quality and fidelity of a new recording made at Universal Recording Corporation (the world's largest independent recording studio for all the leading artists and labels).

"For many years, we have used various speaker systems in our control rooms and studios. Recently, we installed the University 'Classic.' According to Mr. Mason Copping, our chief engineer, the 'Classic' has not only met the rigid power requirements of studio monitoring, but gives us a realistic picture in terms of the final reproduced balance. The favorable reaction from our clients, artists and our engineers especially, is unanimous!"

M. T. Putnam, President
Universal Recording Corporation, Chicago

A FEW OF UNIVERSITY'S MANY




WOOFERS



TWEETERS




MID-RANGE

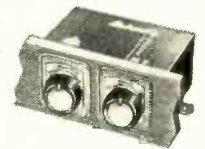

NETWORKS



DIFFAXIAL

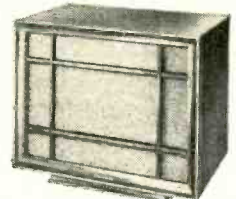

SYSTEMS



ENCLOSURES



KWIKITS

from the world's largest selection
to gratify every need and budget

MAIL COUPON TODAY FOR FREE LITERATURE

Desk J-3, University Loudspeakers, Inc.
80 So. Kensico Ave., White Plains, N.Y.

I would like to learn more about University loudspeakers and components. Please send me the free literature checked.

- Speaker Systems
 Speaker Enclosures and Kits
 Speaker Components

Name _____

Address _____

City _____ Zone _____ State _____

LISTEN

University sounds better



INFRARED SNIPERSCOPE TELESCOPE & PARTS

See in the dark—without being observed. War surplus Sniperscope M-2. Gov't cost about \$1200. Used for industrial plant security; research lab experiments; infrared photography; spectroscopy, etc. Instrument complete, ready to use. Includes Power Pack, infrared light source. Will operate from 6 V auto battery. Battery or transformer available.



Stock No. 85,053-EK..... Shipping \$150.00
weight approx. 12 lbs.

f.o.b. Barrington, N. J.

Order by stock No.—Send check or M.O.—money-back guarantee!

Save still more money! Build your own Sniperscope! We will furnish instructions—parts, including: Power Packs, 1P25A image tubes, light units, filters, etc. For details—request FREE Catalog "EK."

SPECIAL! SPECIAL!

INFRARED 1P25A IMAGE TUBE

Stock No. 70,127-EK.....\$9.95 pstd.

Send check or money order, money-back guarantee

COLOR TV TUBESCOPE

Saves time, effort in alignment of color dot pattern.

Stock No. 50,139-EK.....22 power.....\$24.50 pstd.

Send check or money order, money-back guarantee

GET FREE CATALOG "EK"

America's No. 1 source of supply for experimenters, hobbyists. World's largest variety of Optical Items. Bargains galore. War Surplus—Imported—Domestic! Microscopes, Telescopes, Satellitescopes, Color TV Tubesopes, Infrared sniperscopes and Parts, Prisms, Lenses, Reticles, Mirrors and dozens of other hard-to-get Optical Items.

WRITE FOR FREE CATALOG EK

EDMUND SCIENTIFIC CO.
BARRINGTON, NEW JERSEY

save your records!

adjust your stylus pressure
with "pRescription-accuracy"

AUDAX STYLUS BALANCE



\$395
NET

- a precision instrument with lab-calibrated weights.
- no springs — no inaccurately-printed scales.
- the only way to obtain correct stylus pressure.

Send 10c for 24-page book, "Electronic Phono Facts"

AUDAX — DIV. OF REK-O-KUT Co., Inc.

Dept. RE, 38-19 108th St., Corona 68, N. Y.

Canada: Atlas Radio, Toronto • Export: Mornan Exp., N. Y.

TECHNICIANS' NEWS (Continued)

officers installed were: Norm Telaak, J. Beitz, George Leffler, Joseph Adams, J. Opiela, Pat Pratt, Ralph D'Augustine, Nick Meltie and Edward Danna-har. NATESA president Russell Har-mon administered the oath of office.

Among the out-of-town guests were Bert Bregenzer, Philadelphia, Pa., chairman of the Federation of TV and Radio Service Associations of Pennsylvania; Dan Hurley, Syracuse, president of ESFETA; Don Roberts, Syracuse, president of TESA-Syracuse and Middle Atlantic Governor of NATESA; Bert Lewis, Rochester, eastern vice president of NATESA; Malcom Nelson, presi-dent ETA, Jamestown, N. Y.; and Frank Kurkowski, president TESA-Mohawk Valley, Utica, N. Y.

RTA-SANTA CLARA NEWS

At a dinner and dance held at Mariani's Restaurant in Santa Clara, Calif., the Radio TV Association of Santa Clara Valley installed new officers.

Richard J. Kelso is the new presi-dent; W. I. Smith, vice president; Harold L. Kelley, Jr., secretary treas-urer. Newly elected directors are: Quentin W. Muchow, James C. Davis, C. S. Dawson, Russell J. Ham, Jack Morrisroe and O. N. Timmons.

MIDWEST ELECTRONIC FORUM

A display of carefully planned educa-tional exhibits and informative speak-ers made the second annual Midwest Electronic Forum, held at the Hotel Statler in Detroit, Mich., a success.

Keynote speaker was Edward Wimmer, vice president of the Na-tional Federation of Independent Busi-ness, who noted that independent busi-nessmen will have to combine efforts to fight for their existence. He also suggested they brighten up their stores or shops with an eye to greater cus-tomer appeal.

William J. Nagey, general manager of Philco's accessory division, urged plus sales to increase profits. John Bennett, also of Philco presented a talk on Service Etiquette and stated that tools and appearance are great assets in building customer confidence.


Stanly Bartlemen, a Zenith hi-fi specialist, spoke on demonstration sell-ing of hi-fi. Stuart Greenly of Flint, Mich., told of his experiences in credit and collections.

Others on the technical program in-cluded Robert G. Middleton of Radio Electronic Television Schools and John Meagher of RCA and Robert B. Tomer of CBS.

TESA-SC (Missouri) ELECTS

The Television & Electronics Serv-ice Association of south-central Mis-souri elected E. Cattoll of Cabool as its president for 1958. Other officers elected were James Rathbun of Sparta as vice president and Bill Pryer of Mountain Grove as secretary-treasurer of the group. END

Never Before Available at this LOW PRICE

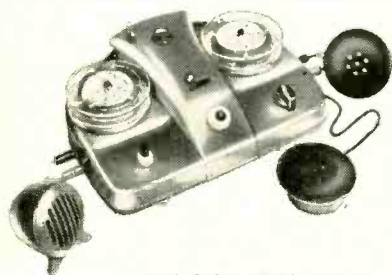

PRECISION, PORTABLE, BATTERY OPERATED, TRANSISTOR TAPE RECORDER

HI-QUALITY REPRODUCTION! \$29.95
WEIGHS ONLY 2 POUNDS!

plus \$1.25
pp. & hdlg.

PRECISION ENGINEERED—Amazing, new, battery operated, portable, fully transistorized recorder, imported from West Germany, precision engineered to render same functions as machines costing 5 times as much.

FOR HOME, STUDENTS, BUSINESS—It will be the center of attraction at home for recording family get-togethers, capturing the magic of speech and song of family and friends—records radio, record and TV shows! Educators agree that students benefit greatly from studying with a tape recorder. Business men can pack it in brief case and take on trips to record letters, speeches, instructions, ideas; faithfully records verbal agreements, discussions. Perfect for recording interviews!

PENNIES TO OPERATE—The ingenious Tel-Tape records, plays back, erases—has variable speed controls! Operates on 4 small flashlight batteries available at any store for pennies. Simply press button and record.

Unconditionally guaranteed for 90 days against mechanical defects. Comes complete with sensitive microphone, head set and tape.—\$29.95 plus \$1.25 pp. & hdlg.

AVAILABLE ACCESSORIES

PATCHCORD — Plug in attachment for playback thru radio, TV or phonograph \$2.00
STETHO HEAD-SET — Like a doctor's stethoscope. Lightweight. Leaves hands free for typing, etc. \$6.95
REEL OF TAPE (225 ft.) \$1.25
BATTERIES — Set of 4 80c

Send Check or Money Order. \$3.00 Deposit on COD orders.

10-DAY MONEY BACK GUARANTEE

FILNOR PRODUCTS, INC., Dept. M-29, 101 West 31st St., New York 1, N. Y.

NEW

DEALER

BUSINESS

SALES PROMOTION MATERIAL

BUILDERS

TECHNICAL LITERATURE


CATALOG

SERVICE TOOLS

CBS-HYTRON SALES CORPORATION
A Subsidiary of Columbia Broadcasting System, Inc.



4th Edition

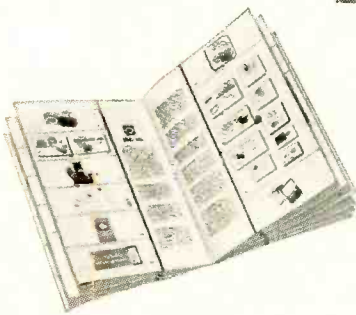

ILLUSTRATES AND DESCRIBES...

... service tools • tube caddy • drop cloth • shop coat, shirt, pants • engineer's and technician's handbooks • reference guides, charts, manuals • Tube Tips • Transistor Course • price lists • job tag • repair sticker • door-knob hanger • ad mats • radio and TV scripts • direct-mail postal cards • consumer booklet • stationery • book matches • dealer giveaways • decals • window valance • window streamers • satin banner • giant tube carton • clock • clock-sign • flange and metal hanging signs • illuminated indoor and outdoor signs.

This book can build business for you.

That's a promise! Get a free copy of this new Fourth Edition of the Business Builders Catalog and see for yourself. Check the more than 90 items ranging from new Printed-Circuit Soldering Aids to new Illuminated Outdoor Signs. You'll find that each is designed with you, the independent service-dealer, in mind. Put them to work. Prove to yourself that they can build more service and tube business, more profits for you. Ask your CBS Tube distributor (or us) for your copy of Business Builders Catalog, PA-37 . . . today!

ELECTRON TUBES



CBS-HYTRON
Danvers, Massachusetts

A Division of
Columbia Broadcasting System, Inc.

For the best in entertainment tune to CBS



NO BURGLARS need apply

...and no burglar tools need be applied to the ESL C-60 Series electrodynamic cartridge. Most pickups require a change in your preamplifier's input resistor, which usually means opening the amplifier to alter with special tools a portion of its complicated wiring. But not with the ESL! No matter what your preamplifier's present input resistor, the performance of the ESL C-60 Series is completely unaffected. No step-up transformers are needed, either.


Most important, the ESL C-60 Series is the world's most advanced cartridge—acknowledged as the finest you can buy for your record changer or arm.

Send for your free copy of "The Cartridge of Tomorrow" to discover thirty-eight reasons why the ESL C-60 Series is tops on every count. For only \$39.50, you can own the cartridge that's years ahead.

FOR LISTENING AT ITS BEST

Electro-Sonic Laboratories, Inc.

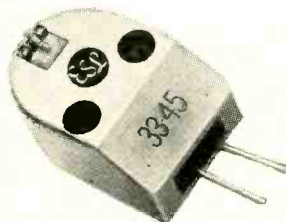Dept. E • 35-54 Thirty-sixth Street • Long Island City 6, N.Y.



GET MORE WORK OUT OF YOUR OSCILLOSCOPE!

Learn to service ANY radio or TV easier and faster!

Here, in an enlarged 2nd edition, is THE book that really shows you how to use oscilloscopes on every job! Clearly as A-B-C, MODERN OSCILLOSCOPES AND THEIR USES tells you exactly when, where and how. You learn to locate either AM or FM radio or television troubles in a jiffy. Even tough realignment jobs are made easy. No involved mathematics! Every detail is clearly explained—from making connections to adjusting circuit components and setting the oscilloscope controls. And you learn to analyze patterns fast and RIGHT!

'SCOPES IN COLOR TV!

Includes latest data on use of 'scopes in color TV, industrial electronics, teaching... even in atomic energy work. More than 400 clear pictures. Dozens of pattern photos make things doubly clear.

'SCOPES IN COLOR TV!

Includes latest data on use of 'scopes in color TV, industrial electronics, teaching... even in atomic energy work. More than 400 clear pictures. Dozens of pattern photos make things doubly clear.

PRACTICE 10 DAYS FREE!

Dept. RE-58, RINEHART & CO., Inc.
232 Madison Ave., New York 16, N.Y.

Send new 2nd edition of MODERN OSCILLOSCOPES AND THEIR USES for 10-day examination. If I like book, I will then send \$6.50 (plus postage) in full payment, or return book postpaid and owe you nothing. (SAVE! Send \$6.50 with order and we pay postage. Same return privilege with money refunded.)

Name.....
Address.....
City, Zone, State.....
OUTSIDE U.S.A.—Price \$7.00, cash with order only. Money back if you return book in 10 days.

ERSIN
Welding
FIVE CORE SOLDER

World's finest!

CONTAINS 5 CORES OF NON-CORROSIVE FLUX

Made especially for the
RADIO AND ELECTRONIC MARKET

**Guarantees your work —
FASTER! SURER! NO CALL-BACKS!**

**LOWEST POSSIBLE PRICES —
PROMPT DELIVERY**

**SOLD ONLY THROUGH
RADIO PARTS DISTRIBUTORS!**


**Dept. ME 388
MULTICORE SALES CORPORATION
PORT WASHINGTON, NEW YORK**

New Tubes & Semi-conductors

WARRANTING special attention this month is the MADT (Micro Alloy Diffused-base Transistor). Three of these types are presented, and between them they have the unusual properties (for transistors) of acting as power oscillators at 100 and 200 mc, oscillating beyond 500 mc and providing 11 db of power gain at 100 mc. Some computer switching type transistors and plug-in silicon diodes also have their interesting points.

2N581, 2N583, 2N585

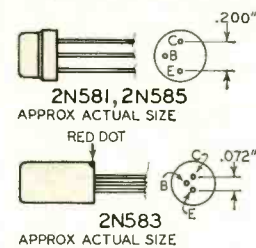The 2N581 and 2N583 are germanium p-n-p alloy junction types while the 2N585 is a n-p-n type. All are specifically designed for use in medium-speed switching circuits. Max-




imum tentative ratings of these RCA units are:

	2N581	2N583	2N585
V_{CB}	-18	-18	25
V_{CE}	-15	-15	24
V_{EB}	-10	-10	20
I_C (ma)	-100	-100	200
I_E (ma)	100	100	-200
P_c (mw) (25°C)	80	80	120
	(55°C)	35	35
	(71°C)	10	10

2N500

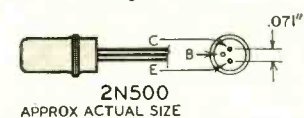A hermetically sealed germanium MADT field-flow transistor intended for use as a uhf power oscillator. A power output of over 20 mw at 200 mc and 40 mw at 100 mc can be expected. Polarities are similar to p-n-p junction transistors. For maximum performance the 2N500 should be attached to a heat sink such as a 2 x 2-inch copper fin clipped to the top shell.



Maximum ratings of the Philco 2N500 are:

V_{CB}	-20
V_{CE}	-15
V_{EB}	-0.5
P_c (mw) (25°C)	75
in free air	100
with heat sink	

BUILD 16 RADIO

CIRCUITS AT HOME

with the New Deluxe 1958
PROGRESSIVE RADIO "EDU-KIT"

only

\$22⁹⁵

A COMPLETE RADIO COURSE

Now Also Includes

★ TRANSMITTER

★ SIGNAL TRACER

★ SIGNAL INJECTOR

★ CODE OSCILLATOR

★ No Knowledge of Radio Necessary

★ No Additional Parts or Tools Needed

★ EXCELLENT BACKGROUND FOR TV

★ School Inquiries Invited

★ Attractively Gift Packed

NO NEED TO SPEND HUNDREDS OF DOLLARS FOR A RADIO COURSE

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction practice and servicing.

You will learn how to build radios, using regular schematics; how to wire and solder in a professional manner; how to service radios. You will work with the standard type of punched metal chassis as well as the latest development of Printed Circuit chassis.

You will learn the basic principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice code, using the Progressive Code Oscillator. You will learn and practice trouble-shooting, using the Progressive Signal Tracer, Progressive Signal Injector, Progressive Dynamic Radio & Electronics Tester and the accompanying instructional material.

You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur Licenses. You will build 16 Receiver, Transmitter, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for Television.

Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with a basic education in Electronics and Radio, worth many times the complete price of \$22.95. The Signal Tracer alone is worth more than the price of the entire Kit.

THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby, a well paying business or a job with a future, you will find the "Edu-Kit" a worth-while investment.

Many thousands of individuals of all ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that you cannot make a mistake. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor is necessary.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematics, study theory, practice trouble-shooting—all in a closely integrated program designed to provide an easily-learned, thorough and interesting background in radio.

You begin by examining the various radio parts of the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set you will enjoy listening to regular broadcast stations, learn theory, practice testing and trouble-shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are sixteen Receiver, Transmitter, Code Oscillator, Signal Tracer, and Signal Injector circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

A COMPLETE RADIO COURSE—NOTHING ELSE TO BUY

You will receive all parts and instructions necessary to build 16 different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, wire, solder, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio & Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book. You receive all parts, tools, instructions, etc. There is nothing else to buy. Everything is yours to keep.



Reg. U.S. Pat. Off.

FREE EXTRAS

● SET OF TOOLS

● SOLDERING IRON
● ELECTRONICS TESTER
● TESTER INSTRUCTION MANUAL
● HIGH FIDELITY GUIDE
● QUIZZES
● TELEVISION BOOK
● RADIO TROUBLE-SHOOTING BOOK
● MEMBERSHIP IN RADIO-TV CLUB
● CONSULTATION SERVICE
● FCC AMATEUR LICENSE TRAINING
● PRINTED CIRCUITRY
● PLIERS-CUTTERS
● ALIGNMENT TOOL
● CERTIFICATE OF MERIT
● VALUABLE DISCOUNT CARD
● WRENCH SET

SERVICING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms and causes of troubles in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

Stalatis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend \$240 for a Course, but I found your ad and sent for your Kit."

FROM OUR MAIL BAG

Ben Valerio, P. O. Box 21, Magna, Utah: "The Edu-Kits are wonderful. Here I am sending you the questions and also the answers for them. I have been in Radio for the last seven years, but like to work with Radio Kits, and like to build Radio Testing Equipment. I enjoyed every minute I worked with the different kits; the Signal Tracer works fine. Also like to let you know that I feel proud of becoming a member of your Radio-TV Club."

Robert L. Shuff, 1534 Monroe Ave., Huntington, W. Va.: "Thought I would drop you a few lines to say that I received my Edu-Kit, and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios and phonographs. My friends were really surprised to see me get into the swing of it so quickly. The Troubleshooting Tester that comes with the Kit is really swell, and finds the trouble, if there is any to be found."

PRINTED CIRCUITRY

At no increase in price, the "Edu-Kit" now includes Printed Circuitry. You build a Printed Circuit Signal Injector, a unique servicing instrument that can detect many Radio and TV troubles. This revolutionary new technique of radio construction is now becoming popular in commercial radio and TV sets.

A Printed Circuit is a special insulated chassis on which has been deposited a conducting material which takes the place of wiring. The various parts are merely plugged in and soldered to terminals.

Printed Circuitry forms the very basis of Automation Electronics.

UNCONDITIONAL MONEY BACK GUARANTEE

ORDER DIRECT FROM AD
RECEIVE FREE BONUS RESISTOR AND CONDENSER KITS WORTH \$7.00

- Send "Edu-Kit" Postpaid. I enclose full payment of \$22.95.
 Send "Edu-Kit" C.O.D. I will pay \$22.95 plus postage.
 Send me FREE additional information describing "Edu-Kit."

Name _____

Address _____

PROGRESSIVE "EDU-KITS" INC.

497 Union Ave., Dept. 140, Brooklyn 11, N.Y.

THE BIGGEST \$1 DOLLAR SALE IN OUR HISTORY!

SAVE \$3 to \$30 ON EVERY POLY-PAK! Exclusive with us!

FREE! PICK ANY \$1 POLY-PAK FREE WITH EACH \$10 ORDER!

\$1 POLY-PAKS®

- 20 ROTARY SWITCHES.** Ass'd. gangs, insulation, contacts. Wide variety. Wt. 3 lbs. Reg. \$18.
- 60 TUBULAR CONDENSERS.** Paper, molded, oil, porcelain. .0002 to .25 mf. to 1.000V. Wt. 2 lbs. Reg. \$12.
- 1 MINI-METER.** 1 1/4" round, 0-8 amps, A.C. Chrome face. Reg. \$3.
- 8-PC. NUTDRIVER SET.** Plastic handle. 3/16, 7/32, 1/4, 5/16, 11/32, 3/8, 7/16" steel socket wrenches in plastic case. Wt. 1 lb. Reg. \$3.
- 50 ASSORTED KNOBS** for radio, TV, appliances. Bakelite, plastic. Wt. 2 lbs. Reg. \$9.
- 100 RADIO PARTS.** Surprise assortment. Reg. value over \$15. Wt. 3 lbs.
- 2 PNP TRANSISTORS** — Scoop! Famous make, worth many dollars each! While they last!
- 65-PC. CONDENSER SPECIAL!** All types ass'd. Molded, paper, ceramic, oil, mica, variable discs. Reg. \$15. Wt. 2 lbs.
- 15-PC. TWIST DRILL SET.** 1/16 thru 1/4" x 64ths. In graduated plastic holders. Reg. \$8.
- 40 SUB-MINI RESISTORS.** Only 1/4" long. 20 values: 15 ohms to 10 meg. Color-coded. Reg. \$6.
- 10 ELECTROLYTICS.** Single & dual 1.5, triples. FP types, to 500 mf. Wt. 3 lbs. Reg. \$14.
- 70 MICA CONDENSERS.** Silver, 5% incl. 30 values: .0001 to .01 mf. to 1,000V. Wt. 1 lb. Reg. \$5.
- 75-PC. RESISTOR SPECIAL!** All types ass'd. Power, carbon, transistor, precision. 30 values. Worth \$15. Wt. 1 lb.
- 10 "POLY" BOXES.** Clear plastic, hinged, w/snap locks. Ass'd. sizes. Reg. \$3.
- TV MIRROR.** Sylvania, stainless steel, 12 x 8". See TV picture while servicing. Many home uses, too. Wt. 1 lb.
- 40 HI-Q CONDENSERS.** ERS. Finest porcelain types. Reg. \$8.
- 60 TERMINAL STRIPS & BOARDS.** Wide variety solder lug, binding, etc. Wt. 1 lb.
- 40 POWER RESISTORS.** W.W. condohm, vitreous, sand-coated. 15 values: 5 to 50 W, 35 to 11,000 ohms. Wt. 2 lbs.
- 50 PLUGS & RECEPTACLES.** Audio, power, chassis, panel & spkr. types. Wt. 2 lbs.
- 40 MOLDED CONDENSERS.** wide assortment, including oils, porcelain, plastic. Reg. \$8.
- "FLEA-POWER"** MINI-MOTOR. Permanent magnet, 1/2 to 3 VDC to operate, 3,000 rpm. Wt. 1 oz.
- 40 TUBE SOCKETS.** Wide ass't. mica, printed, shield-based incl. Reg. \$8. Wt. 2 lbs.
- 150 RESISTORS.** 30 values: 1/2 to 2 W. Reg. \$10. Wt. 2 lbs.
- CRYSTAL MIKE.** Postage-stamp size. Capd. 100 to 8,000 cps. Reg. \$5.
- 6 POPULAR DIODES.** Crystals and silicon, some worth \$10!
- 6 TRANSISTOR SOCKETS.** with mounting plate.
- 10 POWER SWITCHES.** 115 VAC. Ass'd. SPST, DPST, DPDT. Shop must!
- 60 COILS & CHOKES.** RF, IF. Ant. Large variety. Incl. slug-tuned. Wt. 2 lbs. Reg. \$13.
- 40 VOLUME CONTROLS.** Single & doubles: ass'd. values, shafts. Reg. \$15. Wt. 2 lbs.
- 3 LBS. HARDWARE.** approx. 2000 pcs. Ass'd. screws, brackets, etc. Reg. \$8.
- 2 SUB-MINI SOLENOIDS.** 1 x 5/8 x 3/8". Change elec. energy to mech. 12 VDC @ 300 ma actuates plunger. Wt. 2 oz. Reg. \$5.
- 8 GERMANIUM DIODES.** Glass-sealed, w/long leads. Reg. \$4.50.
- 40 PRINTED CIRCUIT PARTS.** Diodes: carbon, precision resistors: chokes: molded, ceramic condensers: boards. Reg. \$15.
- SEVEN 25-FT. ROLLS WIRE.** Ass'd. colors, stranding, insulation, #18 to #24. Wt. 2 lbs. Reg. \$3.75.
- 20 Raytheon KNOBS.** Precision worth \$5 ea. Instrument types, metal insert, w/set-screws. \$1 lb. Reg. \$7.
- 2 TRANSISTOR XFMRS.** UTC "pounce" type. Interstage: 1x3/4" type. Imp. Factors unknown. Color-coded leads. Reg. \$10.
- 20 PRINTED CIRCUITS** ass'd. Integrated, Reg. \$7.
- WORLD'S SMALLEST RADIO KIT.** 2 1/2 x 1 3/4 x 3/4" w/permeability tuned diode, all parts, directions. Reg. \$3.50.
- 5 DIAL-LITE ASSEMBLIES.** Ass'd. colored jewels for mini bulbs. Reg. \$3.50.
- 0-60 MINUTE TIMER.** Darkroom, shop use. Sounds alarm, w/glass, chrome bezel. Wt. 3 lbs. Reg. \$7.
- 80 CERAMIC CONDENSERS.** Tubular, popular makes. Wt. 1 lb. Reg. \$12.
- 40 DISC CONDENSERS.** For transistor & sub-mini work. Reg. \$5.
- 40 PRECISION RESISTORS.** carboloy & W.W. 1/2% ass'd. to 1 W, to 1 meg. Wt. 1 lb. Reg. \$25.
- 10 TIMING MECHANISMS.** 2 second, intricate gearing. Wt. 2 lbs. Reg. \$3 ea.
- 60 HI-Q RESISTORS.** Finest made! LAC, A-B. 30-values: 15 ohms to 10 megs: 1/2 to 2 W. 1/2% incl. Wt. 1 lb. Reg. \$15.
- 20 FERRITE TUNED COILS.** Ant. osc. IF. Wt. 2 lbs. Reg. \$15.
- 40 FT. "ZIP" CORD.** AC/DC line, speaker cable, 2 conductor. State color: BLACK, BROWN, WHITE. Wt. 2 lbs.
- 5 ROLLS "MICRO" WIRE.** 25 ft./roll, ideal for transistor & sub-mini work. Hi-temp, nylon, glass. 24 to 30. Reg. \$5.
- 250-ft. HOOKUP WIRE.** ass'd. colors, insulation, stranding, 25' lengths or longer. Wt. 3 lbs.
- MINI 0-9999 COUNTER** by Veeder-Root. Double-ended shafts. Tape recorder, motors, etc. Reg. \$5.
- MINI SIGMA SENSITIVE RELAY.** 10,000 ohms SPST with assembly. Reg. \$6.50.


HOW TO ORDER Check items wanted. Return entire ad w/check or M.O. including sufficient postage; excess returned. C.O.D. orders, 25% down. Rated net 30 days. Print name, address, amount money enclosed in margin. (Canada postage, 45¢ 1st lb., 28¢ ea. addl. lb.) EXPORT ORDERS INVITED.

LEKTRON 131 Everett Ave. CHELSEA 50, MASS.

NEW TUBES & SEMICONDUCTORS (Cont'd)

2N502, 2N503

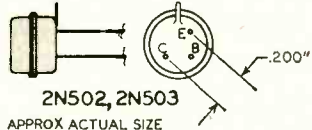The 2N502 and 2N503 are hermetically sealed germanium MADT field-flow transistors. Their maximum ratings are identical to the 2N500 in all but collector dissipation. At 25° C the 2N502 and 2N503 have a collector dissipation of 60 mw.




The 2N502 is designed for use as a vhf amplifier. Its maximum frequency of oscillation is over 500 mc and its power gain is at least 8 db at 200 mc.

The 2N503 is designed for amplifier applications at frequencies up to 100 mc. Its gain at 100 mc is at least 11 db. Polarities of these Philco transistors are similar to those found in p-n-p junction transistors.

M14 SILICON RECTIFIERS

A series of medium-power rectifiers with a rectifying junction formed by diffusion. The case is selected to provide reliable, rugged units for use in both chassis and printed-circuit construction. This series is available with either the anode or cathode connected to the case. Units with the anode connected to the case are designated M14A and units with the cathode connected to the case are designated M14C. A numerical suffix indicates the peak inverse voltage rating of these Motorola products.

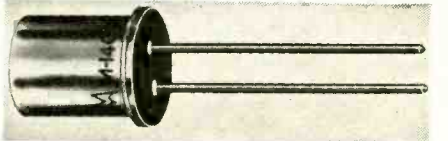


- Peak inverse ratings are:
- M14A1, M14C1—100 volts
 - M14A2, M14C2—200 volts
 - M14A3, M14C3—300 volts
 - M14A4, M14C4—400 volts
 - M14A5, M14C5—500 volts
 - M14A6, M14C6—600 volts

Other ratings that are identical for all units are:
Dc rectified current—0.5 amp
Surge current for 2-msec square wave—35 amps
Surge current, one-half 60-cycle sine wave—5 amps

2N460, 2N461

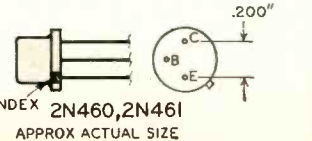Intended for general purpose industrial applications, these are p-n-p alloy-function transistors. Effective hermetic sealing, close control of leakage current at high voltage and efficient thermal design (achieved in part by connecting the transistor base to the case) insure reliable operation at normally encountered environmental conditions.



"OUTPERFORMS THEM ALL"



I. J. Saltzman, Globe Sound Service, Jamaica, N. Y., experienced commercial sound engineer, says: "On side by side comparison test, the CJ-44 outperforms them all."

NEW! ATLAS "King Cobra-Jector" CJ-44



Shown with GB-1 Universal Mounting Bracket

Complete with "Acousti-Match" Built-in Driver Unit
List \$72.50
NET \$43.50

A wide-angle, all-purpose, all-weather Public Address Speaker, complete with integral high-power super-efficient "Acousti-Matched" driver unit. "Acoustic-Matched" means "Controlled Response" within the frequency limits most useful in P. A. and high level music reproduction. "Controlled Response" offers conversion efficiency never before obtainable in high-powered speakers. "Controlled Response" results in smooth reproduction — free from peaks which so often create and sustain acoustic feedback.

The CJ-44 conserves costly amplifier output power — fewer speakers do a complete job. The speaker horn is easily rotated for horizontal or vertical dispersion patterns.

The CJ-44 is the only high-powered P. A. speaker that can be equipped with the new Atlas Universal Mounting Bracket, permitting quick and secure directional adjustment on both planes. Simple to make a horizontal or vertical adjustment as a final "touch-up" to the installation.

The CJ-44 is designed for the "tough jobs." No gimmicks, no fluffs, no wild claims — just a reliable super-efficient speaker for all applications.

- Input Power: 30 watts constant
50 watts peak
- Input Impedance: 16 ohms
- Response: 150-9,000 cps
- Dimensions: Bell 23" x 13";
Over-all length 19"
- Net Weight: 16 lbs.

Write for free Catalog 57.

ATLAS SOUND CORP.
1449-39 St., Brooklyn 18, N. Y.
Atlas Radio Ltd., Toronto, Canada

NEW TUBES & SEMICONDUCTORS (Cont'd)


In a typical class-A audio amplifier circuit the only difference between these two units is in power gain. The 2N460 delivers 34 db while the 2N461 in the same circuit produces a 37 db power gain.

Other ratings of both Tung-Sol units are:

V _{ce}	—20
I _c (ma)	5
Frequency (test) (cycles)	1,000
R _i (ohms)	4,500
R _s (ohms)	500
P _c (mw)	40
Distortion (max) (%)	5

2N425, 426, 427, 428

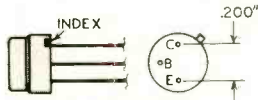These are p-n-p alloy-junction transistors designed for use in computer and switching applications. The transistors have very short "turn on" and "turn off" times. The case features a welded hermetic seal and a standard basing design.



2N425, 426, 427, 428
APPROX ACTUAL SIZE

Maximum ratings of these Tung-Sol units at 25°C are:

	2N425	426	427	428
V _{CB}	—20	—30	—30	—30
V _{EB}	—20	—20	—20	—20
V _{CE}	—20	—18	—15	—12

I _c (dc) (ma)	—400	—400	—400	—400
I _c (peak) (amps)	—1	—1	—1	—1
Turn on time (μsec)	3	2	1.5	2.5
Turn off time (μsec)	2	1.5	1	1
				END

50 Years Ago

In Gernsback Publications

HUGO GERNSBACK, Founder	
Modern Electrics	1908
Wireless Association of America	1908
Electrical Experimenter	1913
Radio News	1919
Science & Invention	1920
Television	1927
Radio-Craft	1929
Short-Wave Craft	1930
Television News	1931

Some larger libraries still have copies of Modern Electrics on file for interested readers.

In May, 1908, Modern Electrics

- A Silicon Detector, by A. C. Austin, Jr.
- Wireless Telegraph Oddities, by Signor Marconi.
- Construction of Wave Detectors. The Dynamophone (voice-operated relay) by Hugo Gernsback.
- Wireless Telephony, by Newell A. Thompson, Jr.
- Wireless Around the World.
- How to Remedy Troubles in Wireless Telegraph Instruments.

COMPLETE TRAINING FOR BETTER RADIO-TV SERVICE JOBS



Let these two world-famous Ghirardi training books teach you to handle all types of AM, FM and TV service jobs by approved professional methods—and watch your efficiency and earnings soar!

Completely modern, profusely illustrated and written so you can easily understand every word, these books have the way to fast, accurate service on any type of home radio-TV electronic equipment ever made. Each book contains the latest data on the latest methods and equipment—NOT a rehash of old, out-of-date material. Each is co-authored by A. A. Ghirardi whose famous RADIO PHYSICS COURSE and MODERN RADIO SERVICE were, for 20 years, more widely used for military, school and home study training than any other books of their type!

THE NEW Ghirardi RADIO-TV SERVICE LIBRARY

Almost 500 pages and over 800 clear illustrations show step-by-step how to handle every phase of modern troubleshooting and servicing.

1—Radio and Television Receiver TROUBLESHOOTING & REPAIR

A complete guide to profitable professional methods. For the novice, it is a comprehensive training course. For the experienced serviceman, it is a quick way to "brush up" on specific jobs, to develop improved techniques or to find fast answers to puzzling service problems. Includes invaluable "step-by-step" service charts, 820 pages, 417 illus., price \$7.50 separately. See combination offer!

2—Radio and Television Receiver CIRCUITRY AND OPERATION

This 669 page volume is the ideal guide for servicemen who realize it pays to know what really makes modern radio-TV receivers "tick" and why. Gives a complete understanding of basic circuits and circuit variations; how to recognize them at a glance; how to eliminate guesswork and useless testing in servicing them. 417 illus. Price separately \$6.75.

New low price . . . You Save \$1.25!

If broken into lesson form and sent to you as a "course," you'd regard these two great books as a bargain at \$8.00 or more! Together, they form a complete modern servicing library to help you work faster, more efficiently and more profitably.

Under this offer you buy them both for only \$13.00. You save \$1.25 on the price of the two books—and have the privilege of paying in easy installments while you use them.

10-DAY FREE TRIAL

Dept. RE-58, RINEHART & CO., Inc.
232 Madison Ave., New York 16, N.Y.

Send (books) below for 10-day FREE EXAMINATION. In 10 days, I will either remit price indicated plus postage) or return books postpaid and owe you nothing.

Radio & TV Receiver TROUBLESHOOTING & REPAIR, (Price \$7.50 separately)

Radio & TV Receiver CIRCUITRY & OPERATION (Price \$6.75 separately)

Check here for MONEY-SAVING COMBINATION OFFER . . . Save \$1.25.

Send both of above big books at special price of only \$13.00 for the two (Regular price \$14.25) if you save \$1.25. Payable at rate of \$4 (plus postage) after 10 days if you decide to keep books and \$3 a month thereafter until \$13 has been paid.

Name: _____

Address: _____

City, Zone, State: _____

Outside U.S.A.—\$8 for TROUBLESHOOTING & REPAIR; \$7.25 for CIRCUITRY & OPERATION; \$14 for both. Cash with order only, but same 10 day return privilege.

SALES MANAGER AM & FM Car Radios

Experienced in Handling Nation-Wide Distribution.

Must have a solid sales-management background and thorough knowledge in radio field. Opportunity to develop with rapidly growing concern. Not over 40. Salary and liberal bonus. Reply to: Box RE5, Radio-Electronics, 154 W. 14 St., New York 11, N.Y.

INFRARED SNOOPERSCOPIES!

OPTICS • LAMPS TUBES • PARTS

Former "Top-Secret" Infra-Red Viewers For Seeing In Total Darkness—Undetected. Now Available For Civilian Applications!

Bell & Howell—uses 1P25-A Image tube. Priced from \$50 to \$99.95.

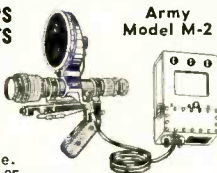


IMAGE TUBE POWER SUPPLY SNOOPERSCOPE PART #1450-A

Power-pack for 1P25-1P25-A tubes (will also supply CV-147 tubes). Input 6 volts d.c. at only 0.33 ampere. Output 4,250 volts d.c. and additional focusing voltages. Operates from single 6-volt dry cell lantern batteries. Size 4 1/2" x 3" x 8". Gov't. cost \$02.00. NEW CONDITION. Complete, ready to turn on, only \$5.95 ppd. \$7.95 ppd.

INFRARED LIGHT SOURCE SNOOPERSCOPE PART #1364-A

Input 6-volts, 5 amperes. 5 1/2" double glass filter. Projects a powerful beam of invisible radiation (free of all visible light) illuminates for infra-red viewing or photography up to distance of 400 feet. STR. #L-5459. BRAND NEW, only \$5.95 ppd.














Cash with order—merchandise guaranteed. Write today for FREE CATALOG. Contains detailed description, price list, and wide uses of units. Also large selection of other infra-red parts available at our amazing low prices.

McNEAL Electric & Equipment Co.
4736 Olive St., Dept. RE-5, St. Louis 8, Mo.

WILL YOUR REPLACEMENT Fuse Resistor BURN OUT AGAIN?

Not if you use — The NEW SENCORE "FUSE-SAFE" CIRCUIT TESTER

       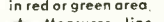   Save costly call backs by testing the circuit before replacing fuse, fuse resistor or circuit breaker.



\$8.95 DEALER NET MODEL FS-3 AC-DC or both as needed for Fuse Resistor Circuits

Individual scale for each value fuse resistor — no interpretation, just read in red or green area.

- ★ Measures line current and up to 1100 watts of power at 115 volts using line cord and socket.
- ★ Two convenient current ranges — 0 to 2 amps and 0 to 10 amps. Test leads clip in place of fuse or fuse resistor.
- ★ 5 ohm, 10 watt resistor prevents TV circuit damage and simulates operating conditions.

As Recommended by Leading Manufacturers

Mfg by SERVICE INSTRUMENTS CORP. 171 OFFICIAL RD., ADDISON, ILL.

Cut out this ad now for further information




Popular and Fast Moving . . .

"ILLINI

ELECTROMITE CONDENSERS"

Time Tested
Quality

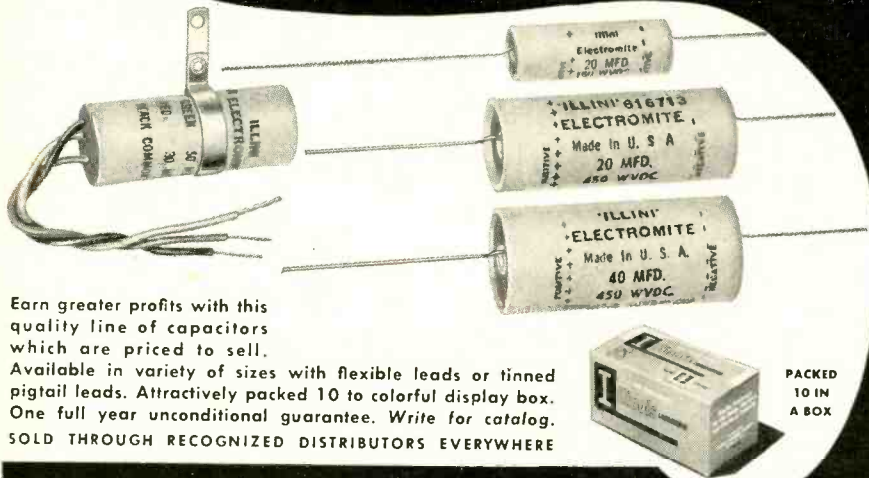


Earn greater profits with this quality line of capacitors which are priced to sell. Available in variety of sizes with flexible leads or tinned pigtail leads. Attractively packed 10 to colorful display box. One full year unconditional guarantee. Write for catalog. SOLD THROUGH RECOGNIZED DISTRIBUTORS EVERYWHERE



Telephone: Everglade 4-1300

ILLINOIS CONDENSER COMPANY

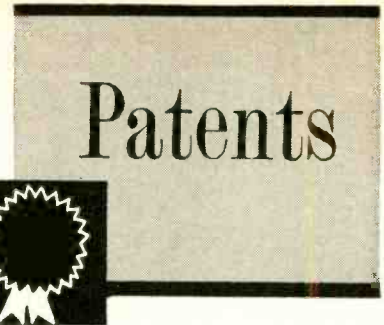1616 N. Throop Street • Chicago 22, Illinois




TUBE-TRANSISTOR AMPLIFIER

Patent No. 2,801,298

Roop Narayan Mital, Eindhoven, Netherlands
(Assigned to North American Philips Co., Inc., New York, N. Y.)

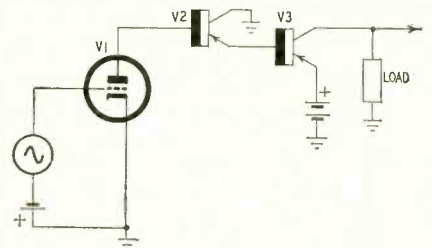One popular combination of transistors is that of a common collector followed by a common emitter. This combination results in good matching between stages so that transformers may be eliminated. Furthermore, it provides a relatively high input and low output impedance. In this



circuit the transistor pair is preceded by a tube amplifier. This gives good overall matching and, of course, very high voltage gain.

The big advantage of a tube input is its high input impedance, a value that cannot be approached by the usual transistor in any type of circuit.


TRANSISTOR SWITCH

Patent No. 2,791,760

Ian M. Ross, New Providence, N. J. (Assigned to Bell Telephone Labs., Inc., New York, N. Y.)

A specially prepared transistor becomes an efficient switch in this circuit. The body of the transistor is p-type, but there is a small n-conductive area. A battery connects across the ends of the p-type material. The battery circuit impedance remains low since there is no junction in its path.

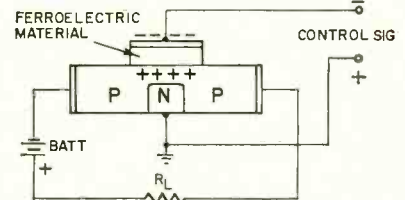Contacting the transistor is a ferroelectric capacitor. It has the unusual property of maintaining a given polarization until a rather large (about 200 volts) reverse potential is applied.



With a control signal or pulse connected with polarity shown, the bottom plate of the capacitor goes positive. Holes diffuse into the narrow channel above the n-area of the transistor. Thus the low impedance of the crystal remains. If the control signal were reversed, however (with sufficient amplitude), the ferroelectric polarization would also reverse. Now electrons would close the battery circuit above the n-area. The crystal impedance becomes very high due to the temporary n-p junction.

The device is an excellent memory unit as the capacitor's polarization is retained until a rather large reverse force is applied. Readout consists of simply testing the battery circuit for high or low impedance, so it does not weaken the polarization.

TRANSISTOR ATTENUATORS

Patent No. 2,816,238

George Elliott, Rochester, N. Y. (Assigned to General Dynamics Corp.)

Transistors are very efficient switches. They are excellent conductors when biased in the forward direction. Their resistance when blocked is high. Here a pair of transistors is used to pass or attenuate audio signals along telephone lines.

Both collectors return to the minus terminal of

RADIO-ELECTRONICS

NEW IMPROVED SENCORE LC3 Leakage Checker

Another Sencore Time-Saver

Check these outstanding New Features Now — For the first time . . .

- Checks 130 different tube types — more than any other "grid circuit" type checker. Includes UHF and latest type tubes.
- Checks picture tubes without removing tube from cabinet or chassis.
- New Roll Chart prevents obsolescence — just dial the tube type and save time. Chart is easily replaced at no extra cost.
- Dynamic Filament checks including heater to cathode leakage & shorts — no need for a second filament tester.
- Two spare preheating sockets to cut down testing time.
- Capacitor checks simplified.

The LC3 provides all these new improved features in addition to those employed in earlier leakage or "grid circuit" testers. A must for any TV service technician.

\$28.95 DEALER NET Really Whips Tough Dogs

SERVICE INSTRUMENTS CORP. In stock at your local parts distributor
171 Official Rd • Addison, Ill.

Cut out this ad now for further information

SUBSTITUTE PARTS WITH-OUT SOLDERING

Quickly with E-Z-Hook "SUB" Connectors Easily Has 1001 Uses!

Connect a speaker, or

Substitute a

- transformer
- capacitor
- resistor, or

In Seconds!!

★ Makes connections instantly!
★ Won't pull off!
★ Insures positive contact!

Saves time, money and parts in servicing, experimenting, instructing and production.

E-Z-HOOK SUB
No. 71-1... SUB... Only 69¢ ea.

Six Colors! — for Easy Lead-Identification


ORDER THROUGH YOUR PARTS DISTRIBUTOR

E-Z-HOOK TEST PRODUCTS
Dept. G-1, 1536 Woodburn Ave.
Covington, Ky.

E-Z-HOOK TEST PRODUCTS SAFE • FAST • SURE

Use Delco Radio Service Parts!

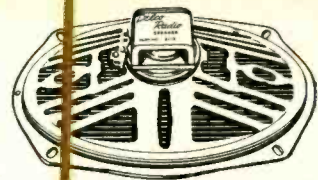2N278—Highest power transistor used in auto radios.



SPEAKERS




IRON CORES



RESISTORS



CAPACITORS

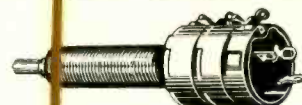

CONTROLS




TUBES




COILS



VIBRATORS

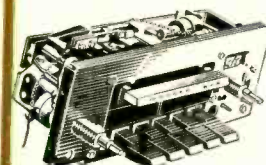

TUNER PARTS

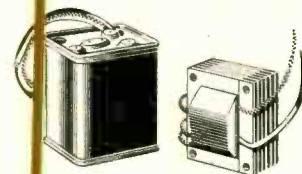

TRANSFORMERS

Your Delco Radio Electronic Parts Distributor carries the complete line, giving you fast, dependable service on the items you'll need for Delco Radio—and other radio—service work. Delco Radio also provides:

- Wide selection of special application parts
- Complete technical training program
- Effective warranty program
- Dealer identification signs

Get the facts today on this truly profitable dealer setup, and grow with General Motors!

Available everywhere through Electronic Distributors associated with . . .



DELCO RADIO

DIVISION OF GENERAL MOTORS, KOKOMO, INDIANA




STOP!

Demand the finest in Electronic Test Equipment—EMC, of course. You get the most quality per measurement dollar!

NEW! EMC Model 301 Speedi Tube Tester

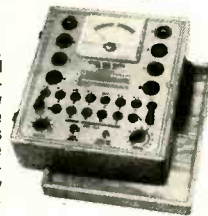Checks tubes in seconds. Checks shorts, leakages, and quality. Over 375 tubes, including 024, now listed. New listings available. Uses line voltage regulation. Checks and rejuvenates Picture Tubes with Model PTA (Picture Tube Adaptor), at only \$4.50. Model 301P (illustrated), with 4 1/2" meter & oak Carrying case \$47.50
 Kit 33.20
 Model 302C, (with 7 1/2" meter) 62.90
 Kit 47.90



NEW! EMC Model 108 Handi Tester

The only appliance and auto battery tester in its price class to use a D'Arsonval, instead of an iron vane type meter. Gives exclusive advantages of maximum accuracy and scale length, and minimum battery replacement cost... at no added charge. Complete with test leads and instruction manual.


Wired \$15.95 Kit 12.95

NEW! EMC Model 905-6A Battery Eliminator, Charger, and Vibrator Checker

A MUST for auto radio service. Features continuously variable voltage output—in either 6 or 12 volt operation. Checks all 6 or 12 volt vibrators.



Wired \$67.90 Kit 44.90

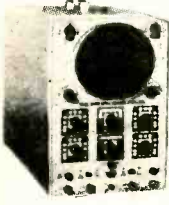


NEW! EMC Model 601, Wide Band Oscilloscope for Color & Monochrome TV

Features full 5 mc band with push-pull vertical amplifier with sensitivity .02 volts per inch, retrace blanking amplifier for clearer pictures, and multivibrator sweep from 15 cycles to over 75 kilocycles. Wired and tested \$117.90

NEW! EMC Model 206P Dynamic Mutual Conductance Tube Tester

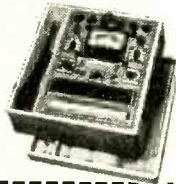The lowest priced mutual conductance tube checker on market. Checks tubes for microhm value and gas content. Completely flexible switching. Your best buy in a quality tube tester. (Hand rubbed Carrying Case) \$83.50



Yes, tell me more, send me—FREE— a detailed catalog of the complete EMC line. RE5


NAME _____

STREET _____

CITY _____ STATE _____

EMC Electronic Measurements Corp. 625 B'way • New York 12, N. Y. Ex. Dept. 370 B'way, N. Y. 13

PATENTS (Continued)

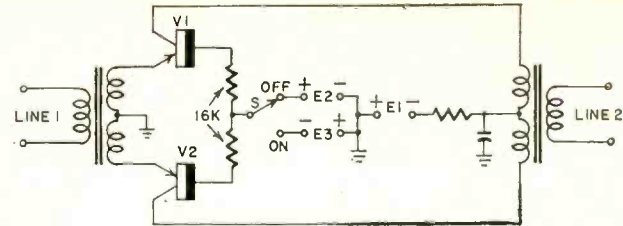

E1. The emitters return through either E2 or E3 depending upon the position of switch S. When switched to E2, both emitters return to the minus terminal and are blocked. Thus no audio can flow through V1 or V2. When S is thrown to E3, posi-

tive bias permits conduction through V1 and V2. Conventional p-n-p transistors conduct to some extent in either direction. For best results here, however, they should be processed for *bilateral* conduction.

DC TO AC CONVERTER
 Patent No. 2,804,547

Harry T. Mortimer, Los Angeles, Calif. (May be used by the US Government without payment of royalty)

There are several ways of converting dc to ac. Among the most efficient circuits is a transistor oscillator that generates a square or pulse wave. In this converter (Fig. 1), the transformer core material has a rectangular hysteresis loop. As a

L1-C, the tuned circuit, is adjusted for a low audio frequency. L2 is the feedback coil. At some instant during a cycle, V conducts fully and becomes nearly a short circuit. This prevents flow from the constant-current source I through L1. At this time nearly the entire voltage E is avail-

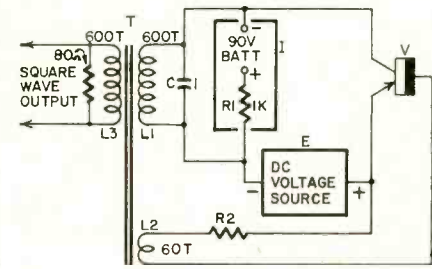


Fig. 1

result, the core can be saturated easily. Abrupt reversal of saturation (from one polarity to the other) provides maximum induced voltage with minimum power loss.

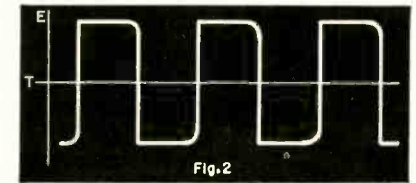


Fig. 2

able to saturate L1 with positive polarity. As V's conduction falls a smaller voltage is available from E across L1. Also, current from I now begins to flow and saturate L1 in a negative direction.

The hysteresis loop is such that magnetic switching is accomplished rapidly from one polarity to the other. Fig. 2 shows a typical waveform of the circuit's voltage output. END

LEARN

Television
RADIO-COLOR-TV

Electricity
ELECTRONICS

IN THE GREAT SHOPS OF **COYNE**

TRAIN QUICKLY! OLDEST, BEST EQUIPPED SCHOOL of ITS KIND in U.S.

Veterans and Non-Veterans—Get practical training in top opportunity fields. Prepare now for a better job and a real future. Advanced education or previous experience not needed. Employment service to graduates.

Enroll NOW—Pay Later

Finance Plan and Easy Payment Plan. Also Part Time Employment help for students. Training in Refrigeration and Electric Appliances can be included.

FREE BOOK Clip coupon for Big Free Illustrated Book. No obligation and No Salesman Will Call. Act NOW.

B. W. Cooke, Jr., President
COYNE ELECTRICAL SCHOOL
 OPERATED NOT FOR PROFIT ESTABLISHED 1899
 500 S. Paulina, Chicago Dept. 58-5C

B. W. COOKE, Jr., Pres.
COYNE Electrical School
 500 S. Paulina St., Chicago 12, Ill. Dept. 58-5C

Send FREE BOOK and full details on:

TELEVISION-RADIO
 ELECTRICITY-ELECTRONICS

NAME _____

ADDRESS _____

CITY _____ STATE _____

Make Sure

You Get Every Issue of **RADIO-ELECTRONICS**

Subscribe now and save

1 year \$4.00, 2 years \$7.00
3 years \$9.00

Canada same as the US. Extra postage per year: Pan-America, 50c; all other foreign, \$1.00

ORDER by MAIL and SAVE!

TV PICTURE TUBES

10BP4	7.95	17BP4	\$10.95	21AMP4	\$19.95
12LP4	8.95	17CP4	17.00	21ATP4	20.95
14B/CP4	9.95	17GP4	17.60	21AUP4	20.95
16DP4	14.95	17HP4	13.60	21EP4	14.95
16EP4	15.90	17LP4	13.60	21FP4	15.95
16GP4	15.90	17QP4	11.95	21WP4	17.30
16KP4	10.95	17TP4	19.30	21YP4	15.95
16LP4	10.95	19AP4	19.30	21ZP4	14.95
16RP4	10.95	20CP4	13.90	24CP4	23.95
16WP4	15.20	20HP4	17.95	24DP4	26.95
16TP4	10.95	21AP4	22.10	27EP4	39.95
17AVP4	15.20	21ALP4	20.95	27RP4	39.95

27"—6 month guarantee—all others 1 year. Aluminized Tubes \$5.00 more than above prices. These prices are determined to include the return of an acceptable similar tube under vacuum.

ALL PRICES FOB CHICAGO, ILLINOIS. Deposit required. When old tube is not returned, refundable at time of return. 25% required on COD shipments. Old tubes must be returned prepaid. We ship anywhere.

WRITE FOR COMPLETE LIST.

PICTURE TUBE OUTLET

3032 Milwaukee Ave., Chicago 18, Ill.
 Dickens 2-2048

OPPORTUNITY ADLETS

Rates—50c per word (including name, address and initials). Minimum ad 10 words. Cash must accompany all ads except those placed by accredited agencies. Discount, 10% for 12 consecutive issues. Misleading or objectionable ads not accepted. Copy for July issue must reach us before May 15, 1958.

RADIO-ELECTRONICS,
154 West 14 St., New York 11, N. Y.

WANT USED PHOTOFACT set for cash. BOX 8021, AMARILLO, TEXAS.

HIGH-FIDELITY SPEAKERS REPAIRED. AMPRITE Speaker Service, 70 Vesey St., New York 7, N.Y. BA 7-2580.

CASH PAID! Sell your surplus electronic tubes. Want unused, clean transmitting, special purpose, receiving, TV types, magnetrons, klystrons, broadcast, etc. Also want military & commercial lab test and communications gear. We swap too, for tubes or choice equipment. Send specific details in first letter. For a fair deal write, wire or telephone: BARRY, 512 Broadway, New York 12, N.Y. Walker 5-7000.

RECORDERS, Hi-Fi. Tapes. Free Wholesale Catalogue. CARSTON, 215-T East 88th St., New York 28, N.Y.

Ampex, Concertone, Crown, Ferrograph, Presto, Tandberg, Zenith, Bell, Sherwood, Rek-O-Kut, Dynakit, Orions, Trades. ROYNTON STUDIO, 1018E Pennsylvania, Yonkers, N. Y.

ANY KIT priced to \$70 assembled and tested for \$15. Work guaranteed. Ship prepaid. Returned C.O.D. GORDON COMBS, R3, Hemet, Calif.

LABORATORY QUALITY equipment and Military Surplus Electronics bought, sold. ENGINEERING ASSOCIATES, 434 Patterson Road, Dayton 9, Ohio.

DIAGRAMS FOR REPAIRING RADIOS \$1. Television \$2. Give make, Model. DIAGRAM SERVICE, Box 672-RE, Hartford 1, Conn.

EXCEPTIONAL SAVINGS on Hi-Fi, speakers, components, amplifiers & tuners, tape recorders, etc. Write for individual quotations on your specific needs; no catalogues. CLASSIFIED HI-FI EXCHANGE, RE, 2375 East 65 St., Brooklyn 34, N. Y.

ALL MAKES OF ELECTRICAL INSTRUMENTS AND TESTING equipment repaired. HAZELTON INSTRUMENT CO., 128 Liberty Street, New York, N. Y.

TELEVISION Tuner Repairs. DAN'S TELEVISION LABORATORY, 619A Sunrise Highway, Babylon, N.Y.

"WINEMAKING: Beer, Ale Brewing" Illustrated. \$2. EATON BOOKS, Box 1242-T, Santa Rosa, Calif.

PICTURE TUBES—lowest prices in country. Factory boxes. Prices quoted. GENERAL ELECTRONICS, 3131 Bailey Ave., Buffalo 15, N. Y.

WORLD RENOWNED Hartley Speakers now available to Dealers. Servicemen, custom installers lowest franchise requirements in High Fidelity industry write to HARTLEY PRODUCTS COMPANY 521 East 162nd St., New York 51, N.Y.

DISCOUNTS TO 50%, recorders, tapes, hi-fi components, consoles, photograph equipment. Request specific prices only. LONG ISLAND AUDIO & CAMERA EXCHANGE, 3 Bay 26th St., Brooklyn 14-R, N.Y.

FREE CATALOG! Hundreds of subjects! TREASURE-SITE BOOK COMPANY, 279 South Alden, Philadelphia 39, Pa.

MATHEMATICS. Universal Correspondence School of Mathematics, Box 5225, Philadelphia 26, Pa.

DIAGRAMS! Repair Information! Radios—Amplifiers—Recorders \$1 Televisions \$1.50. Give make, model, chassis. TV MILTIE, Box 161EA, Hicksville, N.Y.


CASH PAID for simple ideas. MALONE'S, Box 511-RE, Glendora, Calif.

HIGH-PAYING JOBS, opportunities; foreign. USA. All Trades. Companies pay fare. For information, write Dept. 57-U, National Employment Information, 1020 Broad, Newark, N.J.

FIX AUDIO RADIOS FAST! Valuable tips 10c. Sparks, 78 Walnut, Philadelphia 44, Pa.

SAVE MONEY! Get our price list on all types Radio and TV tubes at Mrs. prices! 100% guaranteed, all brand new and unused, no mechanical or electrical rejects, not washed or rebranded! 24 hour service! Write United Radio Company, 58 Market St., Newark, N.Y.

radio-electronic Circuits

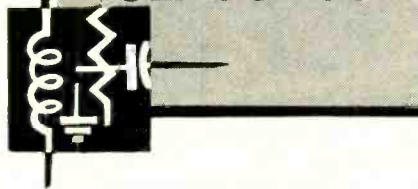


PROTECT YOUR TRANSISTORS

Most transistors and miniature electrolytics are highly sensitive to the wrong battery polarity. Few technicians or experimenters have escaped burning out at least one of these components by inserting a battery backward in some kind of transistor circuit. A fool-proof protective circuit can be added, at small cost, to the transistor set which will guarantee the right polarity no matter how the battery is connected.

The protective circuit is a bridge rectifier type consisting of four germanium diodes, such as the 1N39-A, 1N43 or 1N69. Dc voltage from the battery is applied to the bridge circuit instead

(4) 1N69, 1N43, 1N39-A

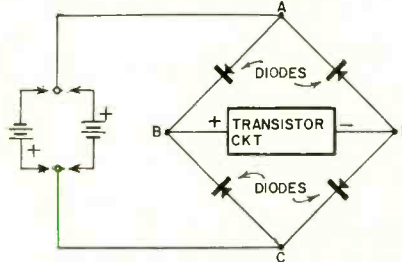

of the usual ac, but the results are the same. The bridge allows current to flow only one way through the transistor circuit load. If the battery is reversed, the polarity across the load still remains the same.

Construct the bridge shown in the schematic and connect the battery at points A and C. Using a voltmeter, measure the voltage and determine the polarity at B and D. Point B should be positive. Wire B and D permanently to the transistor circuit where the battery would normally go, with D to the negative connection and B to the positive. From then on, you can connect the battery to A and C without checking polarity or worrying about damaging the components.—Dave Stone

SEMICONDUCTOR RF NOISE

While cleaning some of the haywire out of my ARC-5 transmitter, I replaced my old selenium rectifier with four new, small-size germanium power diodes. This provided the 28 volts needed to operate the transmitter relays. The next time I turned on the equipment, I looked forward to an improved signal in keeping with the new neat arrangement. But the signal was worse. There was a good loud 50% modulation 60-cycle hum! After considerable musing, muttering and mum-

"ONE DOLLAR" buys

As much as \$15 worth — Everything Brand New and sold to you with a money back guarantee.

DEDUCT 10% ON ANY ORDER OF \$10 OR OVER
Plus a **FREE SURPRISE PACKAGE**


- 100 - ASSORTED FUSES popular sizes,\$1
- 100 - ASST. 1/2 WATT RESISTORS some 50%.....\$1
- 70 - ASSORTED 1 WATT RESISTORS.....\$1
- 35 - ASSORTED 2 WATT RESISTORS.....\$1
- 50 - ASST. TUBULAR CONDENSERS.....\$1
- 10 - 6' ELECTRIC LINE CORDS with plugs.....\$1
- 5 - TV CHEATER CORDS with both plugs.....\$1
- 4 - 50' SPOOLS HOOK-UP WIRE 4 colors.....\$1
- 50 - STRIP'S ASST. SPAGHETTI best sizes.....\$1
- 200 - ASST. RUBBER GROMMETS best sizes.....\$1
- 100' - TV IN LEAD-IN WIRE 300Ω heavy duty.....\$1
- 50' - FLA. 4-CONDUCT. WIRE many purposes.....\$1
- 25' - INSULATED SHIELDED WIRE.....\$1
- 1 - \$7 IN DOOR TV ANTENNA 11-gain 3 section.....\$1
- 20 - ASST. TV KNOBS, ESCUTCHEONS, Etc.....\$1
- 3 - ASST. TOGGLE SWITCHES spst, dpdt, etc.....\$1
- 15 - ASST. ROTARY SWITCHES \$15 worth.....\$1
- 100' - FINEST NYLON DIAL CORD best size.....\$1
- 200 - SELF TAPPING SCREWS #8 x 1/2".....\$1
- 35 - ASST. RADIO KNOBS screw and push-on.....\$1
- 100 - KNOB SPRINGS standard size 3/8" x 1/4".....\$1
- 100 - ASSORTED KNOB SET-SCREWS.....\$1
- 25 - ASSORTED CLOCK RADIO KNOBS.....\$1
- 400 - ASST. H'DWARE screws, nuts, rivets, etc.....\$1
- 50 - ASST. SOCKETS oval, novel and miniature.....\$1
- 20 - ASSORTED TUBE SHIELDS best sizes.....\$1
- 50 - ASST. MICA CONDENSERS some in 50%.....\$1
- 50 - ASST. CERAMIC CONDENSERS.....\$1
- 10 - ASST. VOLUME CONTROLS less switch.....\$1
- 5 - ASST. VOLUME CONTROLS with switch.....\$1
- 100 - VOLUME CONTROL HEX NUTS.....\$1
- 20 - ASST. PILOT LIGHTS popular types.....\$1
- 10 - PILOT LIGHT SKTS, bayonet type, wired.....\$1
- 50 - ASST. TERMINAL STRIPS 1, 2, 3, 4 lug.....\$1
- 10 - ASST. RADIO ELECTRO. CONDENSERS.....\$1
- 5 - ASST. TV ELECTROLYTIC CONDENSERS.....\$1
- 15 - ASST. TV COILS sync. peaking, width, etc.....\$1
- 25 - ASST. MICA TRIMMER CONDENSERS.....\$1
- 50 - TUBULAR CONDENSERS .02-400v.....\$1
- 50 - TUBULAR CONDENSERS .001-600v.....\$1
- 15 - TUBULAR CONDENSERS .047-600v.....\$1
- 50 - TUBULAR CONDENSERS .01-400v.....\$1
- 2 - ELECTROLYTIC COND. 40/40-450V.....\$1
- 2 - ELECTROLYTIC COND. 40/10/10-450V.....\$1
- 30 - FP CONDENSER MOUNTING WAFERS.....\$1
- 3 - ELECTROLYTIC COND. 80-450v.....\$1
- 3 - ELECTROLYTIC COND. 50/30-150v.....\$1
- 15 - TUBULAR CONDENSERS .015-1600v.....\$1
- 10 - HY TUBULAR CONDENSERS .006-1800v.....\$1
- 10 - HY TUBULAR CONDENSERS .001-6000v.....\$1
- 10 - HY TUBULAR CONDENSERS .005-6000v.....\$1
- 35 - MICA COND. 20-100 mmf & 15-270 mmf.....\$1
- 35 - MICA COND. 20-470 mmf & 15-680 mmf.....\$1
- 35 - MICA COND. 20-820 mmf & 15-1090 mmf.....\$1
- 35 - CERAMIC COND. 20-5 mmf & 15-10 mmf.....\$1
- 35 - CERAMIC COND. 20-25 mmf & 15-47 mmf.....\$1
- 35 - CERAMIC COND. 20-56 mmf & 15-82 mmf.....\$1
- 35 - CERAMIC COND. 20-100 mmf & 15-150 mmf.....\$1
- 35 - CERAMIC COND. 20-270 mmf & 15-470 mmf.....\$1
- 35 - CERAMIC COND. 20-1000 mmf & 15-1500 mmf.....\$1
- 35 - CERAMIC COND. 20-2000 mmf & 15-5000 mmf.....\$1
- 50 - 100Ω 1/2 WATT RESISTORS 5%.....\$1
- 75 - 470Ω 1/2 WATT RESISTORS 10%.....\$1
- 50 - 3.3Ω 1 WATT RESISTORS 10%.....\$1
- 50 - 150Ω 1 WATT RESISTORS 10%.....\$1
- 50 - 470Ω 1 WATT RESISTORS 10%.....\$1
- 25 - 2.2Ω 2 WATT RESISTORS 5%.....\$1
- 25 - 22Ω 2 WATT RESISTORS 10%.....\$1
- 25 - 100Ω 2 WATT RESISTORS 10%.....\$1
- 10 - ASST. WIRE'ND RES. 5, 10, 20 watts.....\$1
- 3 - AUDIO OUTPUT TRANS. 50L6 type.....\$1
- 3 - AUDIO OUTPUT TRANS. 6K6 or 6V8 type.....\$1
- 3 - I.F. COIL TRANSFORMERS 456 kc.....\$1
- 3 - I.F. COIL TRANSFORMERS 10.7 mc FM.....\$1
- 4 - OVAL LOOP ANTENNAS ass't hi-gain types.....\$1
- 3 - LOOPSTICK ANT. new ferrite adjustable.....\$1
- 12 - RADIO OSCILLATOR COILS 456 kc.....\$1
- 3 - 1/2 REG VOLUME CONTROLS with switch.....\$1
- 5 - 50K VOLUME CONTROLS less switch.....\$1
- 10 - SURE GRIP ALIGNMENT CLIPS.....\$1
- 1 - GOLD GRILLE CLOTH 14"x14" or 12"x18".....\$1
- 1 - 5" FM SPEAKER 4-ohm #5 magnet.....\$1
- 5 - SET SPEAKER PLUGS wired.....\$1
- 10 - SET'S PHONO PLUGS and PIN JACKS.....\$1
- 2 - \$2.50 SAPPHIRE NEEDLES 4000 playbacks.....\$1
- 5 - DIODE CRYSTALS 2-IN2 2-IN23 1-IN264.....\$1
- 2 - SELNIUM RECTIFIERS 1-65 ma & 1-150 ma.....\$1
- 1 - TV CRT. OUTPUT TRANS. 10 to 1 ratio.....\$1
- 5 - TV CRT. SOCKETS with 18° leads.....\$1
- 5 - HI-CRT. ANODE LEADS with 18° leads.....\$1
- 1 - TV RATIO DETECTOR TRANS. 4.3 mc.....\$1
- 5 - ASST. VHF TUNER STRIPS oscillator.....\$1
- 1 - SET TV KNOBS standard type incl. decals.....\$1
- 1 - LB POOL ROSIN CORE SOLDER 40/60.....\$1
- 6 - SPIN TIGHT SOCKET SET 3/16" to 7/16".....\$1
- 3 - TV ALIGNMENT TOOLS 5", 7", 12".....\$1

HANDY WAY TO ORDER—Simply tear out advertisement and pencil mark items wanted (dot in square is sufficient); enclose with money order or check. You will receive a new copy of this ad for reorders.

ON SMALL ORDERS—Include stamps for postage, excess will be refunded. Larger orders shipped express collect.

BROOKS RADIO & TV CORP.
84 Vesey St. Dept. A, New York 7 N.Y.


25 WORDS

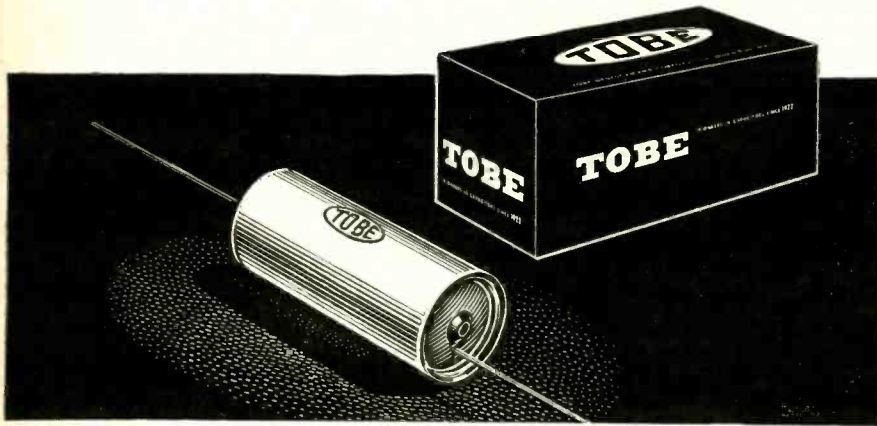

Tell Why You Like Tobe Service Capacitors

Your 25 words can win the Ford Ranch Wagon

And Here Are the TSC* Features to Help You Win • No substandard materials can possibly enter the manufacture of TOBE SERVICE CAPACITORS, because *everything* is quality-checked beforehand • Highest grade dielectric materials prevent voltage breakdown in service • TSC's are designed for high-temperature operation – will not dry out or deteriorate in service • Copperweld leads soldered directly to foil insure you against opens • Moisture-tight seals guard against shorts • Pigtail leads will not pull out or break off • No danger of hot soldering iron opening internal connection or melting sealing compound • TSC's will maintain specified capacity over entire operating temperature range • TSC's receive 100% quality-control inspection prior to shipment • Continuous production-line testing automatically rejects "duds" • Maintenance of large inventories on complete line means faster delivery to your TOBE DISTRIBUTOR and you.

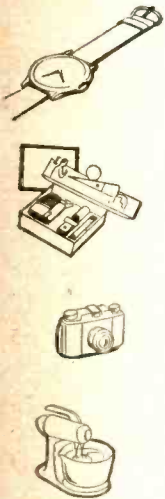

*Tobe Service Capacitors



TOBE
RADIART
CAPACITORS

**HERE'S YOUR
ENTRY BLANK**

Tobe Deutschmann Corporation, Dept. C
2900 Columbia Avenue, Indianapolis 5, Indiana

"I prefer Tobe Service Capacitors in my work because _____

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____


I enclose a Tobe boxtop

RADIO-ELECTRONIC CIRCUITS (Continued)

bling about leaving things alone once they're working, I began digging into my nice neat layout to chase the source of the 60 cycles.

As any of you fellows who are familiar with the ARC-5 transmitters know, the cathode and heater circuit of the oscillator are kept above rf ground. My first suspicion was a short in the coil or in one of its associated bypass capacitors, but no defect was found here or in any of the other logical sources in the oscillator, amplifier or modulator. Next, I thought that the common transformer for both the relay supply and the heaters was the cause, but a separate transformer for the relay supply did not eliminate the hum.

I noticed that the hum stopped when the transmitter relay was held manually closed. Further tests indicated that the hum originated in the germanium power rectifier and 100- μ f filter circuit used to provide dc for the relays. The usual .001- μ f bypass capacitors around the rectifiers to ground did not help. Two 50- μ h chokes placed in the leads to the heater transformer did the trick (see diagram) and completely eliminated the trouble.

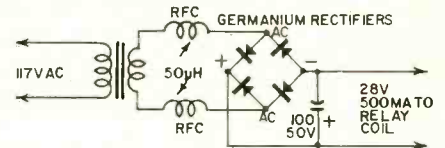

It seems that the very low forward resistance of the germanium rectifiers generated a very sharp current spike on each cycle. This showed up as a 60-cycle pulse which apparently modulated the oscillator circuit. Some TV germanium rectifier power supplies use a small bypass capacitor across the rectifier to eliminate a similar type of rf pulse. The higher-impedance 250-volt circuit used in the TV set may be the reason why the bypass worked in the TV circuit and not with 25-volt relay supply which I was using. A 50-ohm resistor would probably have eliminated the rf by rounding off the sharp spike. I did not use one because of the additional voltage drop it would cause.

In any event the point to remember is that these devices have good characteristics which may give trouble if not watched.—Fred Lingel, K1CCW.

END



"Now do you believe it has a reasonable response at 15 cycles?"

try
This
one




SOLDERING HINT

Here's a way to avoid overheating transistors or other delicate components while soldering. Fold a small piece of felt or cotton and dip it in a glass of water. Then, using an alligator clip to hold it in place, clip it to the lead between the component and the joint to be soldered. Due to the large amount of heat dissipated by the dampened cloth, this is better than holding the lead with pliers. It also leaves both hands free.—*Homer E. Hogue*

TRANSISTOR AS A DIODE

When no crystal diode is at hand for experiments, crystal radios, etc., a low-priced transistor will do the job. Don't throw away transistors which have been spoiled by incorrect battery polarity. Chances are, they can still be used as crystal diodes by using two of the three electrodes.

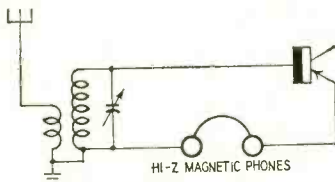The diagram shows a 99-cent CK722 used as a crystal diode in a typical crystal radio. When using a CK722, best results were obtained by using



the base and emitter connections as shown. The emitter and collector connections also gave good results, but when base and collector connections were used, the sensitivity was poor. The interelectrode capacitance of a transistor is slightly higher than that of a crystal diode. When used as a diode, the transistor's sensitivity does not quite equal that of a 1N34, but it sure comes in handy in a pinch and the experiments should be interesting.—*Arthur Trauffer*

DETECTING MICROPHONIC TUBES

The usual method of locating a microphonic tube is to tap each in turn until a "boing" is heard in the speaker. However, some tubes are so microphonic that they sound off no matter what part of the chassis is tapped. One way of locating these tubes is to connect a voltmeter across the plate, screen or cathode resistor and then tap it. Microphonism is indicated when the meter flickers as the tube is tapped. When testing power output tubes, keep the volume turned down to eliminate the effects of microphonics in earlier stages.—*Charles Erwin Cohn*

WIN THIS FORD



RANCH WAGON

Or one of 49 other valuable prizes


Here's all you do . . . In 25 words or less, tell us why you prefer TOBE SERVICE CAPACITORS.

Then, send your entry to us with the top from any TOBE capacitor carton, or the plastic box some TOBE capacitors are packed in.

That's all there is to it. Enter as many times as you wish, providing each entry is accompanied by a TOBE carton top or the plastic box. Use entry blank below. Additional entry blanks can be obtained from your TOBE DISTRIBUTOR.

Contest Closes May 30

Contest is open to all service-men over 21 years of age residing in the continental United States. Employees of the TOBE DEUTSCHMANN CORPORATION and their advertising agency are excluded. All entries become the property of TOBE DEUTSCHMANN CORPORATION. Decisions of the judges are final. In case of tie, duplicate prizes will be awarded. Contest closes May 30, 1958. Winners will be announced June 30th.

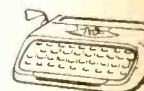

HERE'S YOUR
ENTRY BLANK



TOBE
RADIART
CAPACITORS

Tobe Deutschmann Corporation, Dept. C
2900 Columbia Avenue, Indianapolis 5, Indiana

"I prefer Tobe Service Capacitors in my work because _____


NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

I enclose a Tobe boxtop

Easy-to-Use
= STEREO

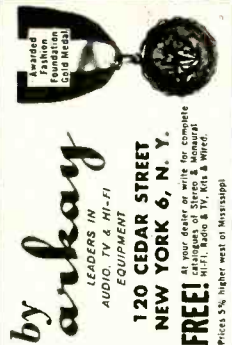

Arkay SA 25

Attached to your present power amp and preselector, you get stereo 2-2-2 Channel 1-25 watt amp recs.; sens. tape @ 20 watts, 20-20,000 cycles; tuner aux. 3my for 25 watts. Controls: volume, bass treble, to and hi filters; equal for all labels plus HARTB tape head. Channel 2—same sens. SAVE! Easy-to-build kit. \$89.95




The best and only unit of its kind. Precision components, 100% tested, guaranteed. No failure. A. S. K. 2000 20. Stereo. \$42.95. Save! Easy-to-build kit. \$59.95



Merco's an exceptional 45% increased AC 50 cycle stereo sound. Tuner of unsurpassed sensitivity and frequency of operation. May be used as either a Stereo or as a dual band broadcast or manual FM or AM. \$74.95. Save! Easy-to-build kit. \$89.95



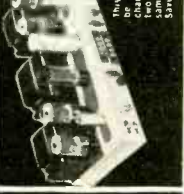This new dual channel 55 watt amplifier can be used as either a Stereo or as a dual band broadcast or manual FM or AM. \$74.95. Save! Easy-to-build kit. \$89.95




OTHER MATCHING ARKAY STEREO UNITS...

...Your Present System Logical, Inexpensive Step to STEREO...

TRY THIS ONE (Continued)

JEWELER'S SAW CUTS CONTROL SHAFTS

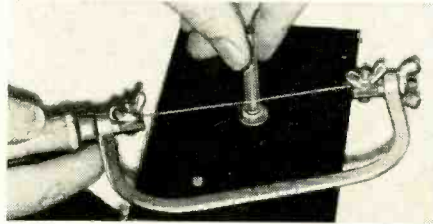The photo shows a jeweler's saw being used to cut a control shaft to length. The fine teeth of this saw make sharp, even cuts without binding and jamming to the extent experienced with a common hacksaw.



The control can be cut after it has been mounted without excessive vibration that might loosen the mounting nut. The subsequent hazard of moving the loose control and damaging wiring is also eliminated.


In sawing, hold one hand on the shaft as shown. This prevents any tendency toward binding.—James A. McRoberts

SOLDERING AID

We use modeling clay as a soldering aid in our shop. We shape it to hold small odd-shaped components and assemblies that cannot be clamped in a vise for soldering. This method of holding small parts has an added advantage. No outside metal contact dissipates the needed heat.—Henry Josephs

CLAMPS FROM BATTERY CLIPS

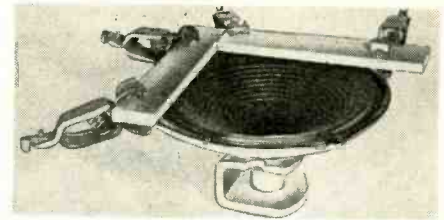Thin strips of wood and large battery clips make excellent clamps when



reconnecting a speaker cone. If not enough clips are available to hold the entire cone, reconnect a half or a quarter section at a time.—Carleton A. Phillips

STOP THAT DRILL

When I accidentally drilled through a TV chassis and on into an electrolytic capacitor on the underside, I realized that one should always use a drill stop to restrict the travel of the drill. Looking around the shop I came up with some ideal drill stops—lengths of wire-insulating spaghetti.

There are several sizes, so no matter what size drill you are using you can usually find a piece that makes a good snug fit. Since that little episode related above, I always use a length of spaghetti to stop the drill. It's considerably less expensive than a quad-section electrolytic.—Scott Mack END

Another Sencore Time-Saver

Handy "36" R-C Substitution Unit

Most Often Needed Components At YOUR Fingertips!

3 pole, 12 position switch individually selects one of the "36" components for direct substitution.

Contains:

- ★ 12—1 watt 10% resistors from 10 ohms to 5600 ohms
- ★ 12—1/2 watt 10% resistors from 10K ohms to 5.6 megohms
- ★ 10—400 volt capacitors from 100-mfd. to .5mfd.
- ★ 1—10mfd., 450V Electrolytic
- ★ 1—40mfd., 450V Electrolytic

★ For Shop, Lab., or outside service

AVAILABLE AT ALL PARTS DISTRIBUTORS!

SERVICE INSTRUMENTS CORP.
171 OFFICIAL RD., ADDISON, ILL.

ONLY \$1275 DEALER NET

Completely isolated

POPULAR SENCORE PRODUCTS

- Transistor Tester
- Leakage Checker
- Filament Tester
- Voltage Regulator
- Bias Supply

YOUR DOLLAR STILL HAS PLENTY OF CENTS at

RAD-TEL TUBE CO.

<input type="checkbox"/> INSULATED RESISTORS. Assorted values and assorted watt. Assort. of 100	<input type="checkbox"/> PRINTED CIRCUIT SOCKET KIT. 9 and 7 pin type. Kit of 25
<input type="checkbox"/> KNOB KITS. Assorted Types. Bag of 30	<input type="checkbox"/> WIRED PLUGS, SOCKET. Very useful assortment. Kit of 20
<input type="checkbox"/> SOLDER LUG KITS. Every usable assortment. Kit of 48	<input type="checkbox"/> SPEAKER SELECTOR SWITCH. For rear seat speaker. 3-position—either or both.
<input type="checkbox"/> MICA CONDENSERS. All popular sizes. Kit of 25	<input type="checkbox"/> EM FOCUS COILS. 250 ohms. 2 for
<input type="checkbox"/> BY-PASS CONDENSERS. .002 to .2MFD. 200 to 1000 VDC. Kit of 25	<input type="checkbox"/> WIRE KIT. Pre-cut, pre-trimmed. 3 lbs.
<input type="checkbox"/> ELECTROLYTIC CONDENSERS	<input type="checkbox"/> FILTER CONDENSERS
<input type="checkbox"/> 8 mfd 475v tubular. 10 for \$1	<input type="checkbox"/> 20-20 MFD. 150V. 2 for \$1
<input type="checkbox"/> 20 mfd 450 v cin 5 for \$1	<input type="checkbox"/> 40-40 MFD. 150V. 2 for \$1
<input type="checkbox"/> 80 mfd 350v can 5 for \$1	<input type="checkbox"/> 50-30 MFD. 150V. 2 for \$1
<input type="checkbox"/> 250 mfd 350v can 5 for \$1	<input type="checkbox"/> CHEATER CORD. Extra long on & off switch. 10 ft. 5 inches. 2 for \$1
<input type="checkbox"/> 10, 100, 10, 100 25v—can 3 for \$1	<input type="checkbox"/> YOKES 55", similar merit. MD 12 10 for \$1
<input type="checkbox"/> VOLUME CONTROL KITS. Assortment; some individually boxed. Kit of 10	<input type="checkbox"/> PILOT LIGHT SOCK. ET KIT. 30 bayonet base socket wire leads, brackets, clamp and snap. Extra Special! 2 Kits for \$1
<input type="checkbox"/> CERAMIC KITS. Extra special buy. 2 kits of 50	<input type="checkbox"/> BI-PASS CONDENSER KITS. Assort. values 100, 10, 1 mfd. 200, 400, 600 V. Mylar dielectric for top quality. 25 for \$1

Use This Ad As Your Order Blank

Rad Tel TUBE CO.

Not Affil. With Any Other Tube Mail Order Co.

Write Dept. RE-5 for FREE Catalog of Tubes & Parts. Subject to prior sale. NO C.O.D.'s, please, on this sale. Allow for postage.

55 Chambers Street, Newark 5, N.J.

new Devices



TRANSISTOR-LITE. Transistor-controlled neon lamp for use in computers, data processors, signal systems, keyboard equipment, and transistor automatic control devices. Housed in anodized aluminum tube 2 inches long, 1/2 inch in diameter. Requires 3.5-volt signal for control. *Echo-Lite*, pushbutton with NE-2 neon bulb enclosed.



Memo-Lite, subminiature thyatron indicator for transistor circuits.—**Transistor Electronics Co.**, 3357 Republic Ave., Minneapolis 26, Minn.

TRANSISTOR STATIC CONVERTERS. Transceiver and receiver supplies for 6- and 12-volt inputs. Typical transceiver, volts dc: 500 @ 165 ma; 270 @ 150 ma; —55 @ 10 ma. Receiver supply, 6-volt input; delivers 250 volts dc @ 80 ma or 290 @ 80 ma. 12-volt receiver supply delivers 250 volts dc @ 80 ma or 290 @ 80 ma or 250 @ 130




ma.—**UAC Electronics**, Div. of Universal Transistor Products Corp., 36 Sylvester St., Westbury, N. Y.

POWER MEGAPHONE, Power Voice. 6-transistor unit has 15-watt output. Powered by flashlight batteries. Range up to



3/4 mile. Weighs 8 pounds.—**Motorola Inc.**, Communications & Electronics Div., Technical Information Center, 4501 W. Augusta Blvd., Chicago 51, Ill.

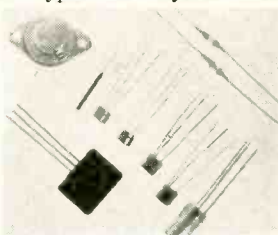SEMICONDUCTOR LINE. Power, small-signal, switching, special-purpose transistors; various types of crystal diodes



make up new *Gemco* line.—**Great Eastern Manufacturing Co.**, 165 Remson Ave., Brooklyn 12, N. Y.

SOLID-STATE CHOPPER, model 50. Encapsulated transistorized chopper or modulator alternately connects and dis-




connects load from signal source. As demodulator, converts ac signal to dc. Driving voltage square wave—1-10 volts peak to peak. Driving source resistance, 600 ohms. Driving input resistance, 600 ohms. Input voltage, dynamic range from fraction of millivolt to more than 2 volts. Output voltage equals chopped input voltage. Chopping (driving) frequency, dc-100 kc or higher.—**Solid State Electronics Co.**, 815 Orion Ave., Van Nuys, Calif.

DICTATING INSTRUMENT, Audograph Key-Noter. All-transistor unit works off 117-volt ac line only. Pushbutton operation. Record and playback. 6 1/2 x 8 1/2 x 2 5/8 inches. 5 pounds 10 ounces.



Uses 20-minute disc. Embossing process.—**Gray Manufacturing Co.**, 20 Arbor St., Hartford, Conn.

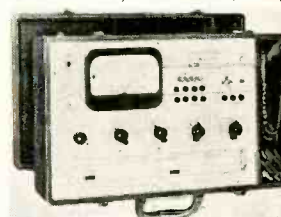
TRANSISTOR TESTER, model 960. Portable unit tests for I_{ceo} gain, leakage, shorts of both p-n-p and n-p-n transistors. Checks low-, medium-, high-



power units. Test settings on roller chart.—**Precision Apparatus Co. Inc.**, 70-31 84th St., Glendale, N. Y.

TRANSISTOR CHECKER conversion kit TCK-2. Converts the Sencore TDC22 transistor checker to later type circuit used in

Just Out

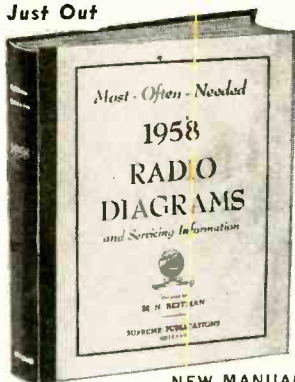

NEW MANUAL

Be prepared to repair quickly all new 1958 radio sets. In this big volume you have easy-to-use, large schematics, needed alignment data, replacement parts lists, voltage values, and information on stage gain, location of trimmers, and dial stringing, for almost every 1958 radio. Includes auto radios, transistor portables, and all types and makes of home sets. Giant in size, 8 1/2 x 11"; manual style, sturdy binding. Price, only **\$2.50**

New SUPREME 1958 Radio Manual


Now you can benefit and save money with Supreme amazing scoop of 1958. This one giant volume has all the service data you need on all recent radio sets. A full year of models of all popular makes, home and auto sets, portable radios, combinations, changers, all included. The full price for this mammoth 1958 manual is only \$2.50, nothing else to buy for a whole year. Other Supreme radio service volumes for previous years (mostly at \$2) are described below. Separate TV manuals are listed at right.

SUPREME RADIO MANUALS FOR PREVIOUS YEARS

Use Supreme manuals to repair all radios faster, easier; save time and make more money. Here is your lowest-priced service data. Covers all years, from 1926-38 to 1958 models, in 18 volumes. Used by 174,000 shrewd servicemen. Most volumes only \$2 each, see coupon. Average volume 190 large pages, 8 1/2 x 11 inches. Quality printing, easy to use, manual-style binding. Amazing values. Be wise, use these manuals to get all needed diagrams, parts lists, alignment facts, and service hints, at the smallest cost. See your jobber or send no-risk trial coupon. →

SUPREME TELEVISION SERIES

Here is your complete source of TV service data at lowest prices. Supreme manuals at only \$3 each are amazing bargains and defy competition. Each annual manual covers a whole year of models, using original factory material. Include giant double-spread circuits and blueprints, alignment procedure, waveforms, voltage charts, factory revisions, and helpful service hints. Select volumes from list below and send no-risk coupon.

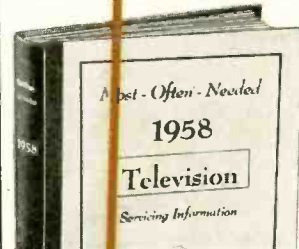

- 1958 TV Manual, \$3
- 1957 Early TV, \$3
- 1957 Late TV, \$3
- 1956 TV Manual, \$3
- 1955 Early TV, \$3
- 1955 Late TV, \$3
- 1954 TV Manual, \$3
- 1953 TV Manual, \$3
- 1952 TV Manual, \$3
- 1951 TV Manual, \$3
- 1950 TV Manual, \$3
- 1949 TV Manual, \$3
- 1948 TV Manual, \$3

NO-RISK TRIAL ORDER COUPON

SUPREME PUBLICATIONS, 1760 Balsam Rd., Highland Park, ILL.

<input type="checkbox"/> 1958 Radio Diagrams, \$2.50 <input type="checkbox"/> 1957 Radio Manual, \$2.50 <input type="checkbox"/> 1956 Radio Diagrams, \$2.50 <input type="checkbox"/> 1955 Radio Manual, only \$2 <input type="checkbox"/> 1954 <input type="checkbox"/> 1953 <input type="checkbox"/> 1952 <input type="checkbox"/> 1951 <input type="checkbox"/> 1950 <input type="checkbox"/> 1949 <input type="checkbox"/> 1948 <input type="checkbox"/> 1947 <input type="checkbox"/> 1946 <input type="checkbox"/> 1942 <input type="checkbox"/> 1941 <input type="checkbox"/> 1940 <input type="checkbox"/> 1939 <input type="checkbox"/> 1926-1938 Manual, \$2.50 <input type="checkbox"/> Radio & TV Master Index, 25¢	These annual RADIO volumes specially priced at only \$2.50 each...	Rush today TV manuals checked <input type="checkbox"/> below and Radio manuals at left. Satisfaction guaranteed. <input type="checkbox"/> New 1958 Television Servicing Manual, only... \$3. <input type="checkbox"/> Additional 1957 TV, \$3. <input type="checkbox"/> Early 1957 TV, \$3. <input type="checkbox"/> 1956 Television Manual, \$3. <input type="checkbox"/> Early 1955 TV, \$3. <input type="checkbox"/> Additional 1955 TV, \$3. <input type="checkbox"/> 1954 TV Manual, \$3. <input type="checkbox"/> 1953 Television Manual, \$3. <input type="checkbox"/> 1952 TV, \$3. <input type="checkbox"/> 1951 Television Manual, \$3. <input type="checkbox"/> 1950 TV, \$3. <input type="checkbox"/> 1949 TV Manual, \$3. <input type="checkbox"/> 1948 TV Manual, \$3. <input type="checkbox"/> New Television Servicing Course, complete... \$3. <input type="checkbox"/> I am enclosing \$..... Send postpaid. <input type="checkbox"/> Send C.O.D. I am enclosing \$..... deposit.
---	---	---

THIS GROUP
ONLY
\$2
EACH


TELEVISION SERVICING COURSE

Let this new course help you in TV servicing. Amazing bargain, complete only \$3, full price for all lessons. Giant in size, mammoth in scope, topics just like a \$200.00 correspondence course. Lessons on picture faults, circuits, adjustments, short-cuts, UHF, hints, alignment facts, antenna problems, troubleshooting, how to use test equipment, fault-finding hints, picture analysis. Special, only... **\$3**



Supreme Publications
Sold by All Leading Parts Jobbers

One
for all...

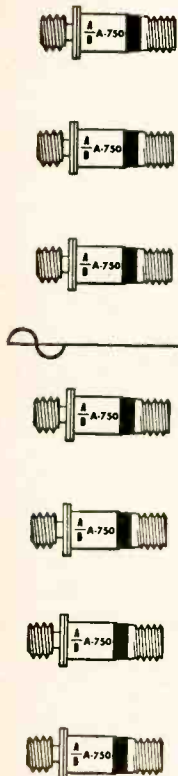

Audio's Silicon Rectifiers replace all 130 volt Selenium Rectifiers up to 750 ma in ALL repair jobs, in all radio, TV and electronic devices. See your distributor and demand the *best* reliability.

After all...

it screws and plugs in *too* for various applications

WRITE FOR YOUR COPY



68 PAGE SILICON RECTIFIER HANDBOOK \$1

Inquire Dept. RE-5/58

AUDIO DEVICES, INC.
Rectifier Division

620 E. DYER RD. • SANTA ANA • CALIFORNIA

Canadian Repr./Alex L. Clark, Ltd. • 3745 Bloor St. W., Toronto
Internatl. Repr./Rocke Internatl. Corp. • 13 E. 40th St., N.Y. 16, N.Y.

NEW DEVICES (Continued)

TRC4 tester which checks power transistors more thoroughly.—Service Instruments Corp. (Sen-core), 171 Official Rd., Addison, Ill.

POWER RESISTOR DECADE BOX, model 210-C. 6 resistance decades arranged to give any rating between 1 and 999,999




ohms in increments of 1 ohm. Maximum power capacity, 225 watts at 1,000 volts.—Clarostat Manufacturing Co., Inc., Dover, N. H.

SUB CONNECTORS, E-Z-Hook. For substituting parts in circuit. Makes connections quickly,




positive contact. Hooks over wire and will not pull off.—E-Z-Hook Test Products, 1536 Woodburn, Covington, Ky.

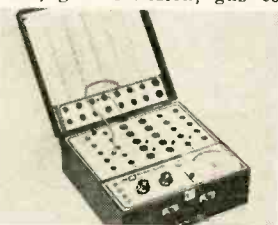TUBE TESTER, model 500B Dyna-Quik. Dynamic mutual-conductance type. Tests for shorts, grid emission, gas con-



tent, leakage and life expectancy.—B & K Manufacturing Co., 3726 N. Southport Ave., Chicago 13, Ill.

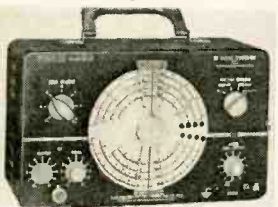RF SIGNAL GENERATOR KIT, model G-30. 8 bands cover 160 kc-240 mc. To 120 mc in fundamentals. Rf output exceeds 100-



000 μ v. 400-cycle audio output approximately 15 volts.—Paco Electronics Co., Div. Precision Apparatus Co., Inc., 70-31 84th St., Glendale, Calif.

AC VTVM, model WV-74A. Measures ac voltages from .01 to 100. Decibels from -40 to +40. Also useful as wide-range audio preamplifier with approximately 38-db maximum gain.




Frequency range on all measurement and amplifier functions is from 20-500,000 cycles.—RCA Electron Tube Division, Harrison, N. J.

EDGEWISE PANEL METERS, Model 1502. Dc voltmeters: 0-50, 0-150, 0-500. Dc ammeters: 0-5, 0-10. Dc milliammeters: 0-1, 0-10, 0-100, 0-500. Dc microammeters: 0-50, 0-100. Accurate within 2% of full-scale deflection. Model 1507 includes



VU meters and rectifier type ac voltmeters.—Simpson Electric Co., 5200-18 W. Kinzie St., Chicago 44, Ill.

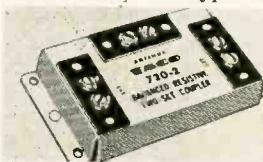MULTISET COUPLERS. Indoor model 720. Outdoor model 725. Balanced resistive type for 2




TV receivers. Provide up to 25-db isolation between sets.—Technical Appliance Corp., Sherburne, N. Y.

SCREW DRIVERS, Red Cap line. 7 models: RC-1, No. 1 Phillips, 3-inch blade. RC-2, No. 2 Phillips, 4-inch blade. RC-3, 3/16



x 4-inch blade. RC-5, 3/16 x 5-inch blade. RC-6, 3/8 x 4-inch blade. RC-8, 1/2 x 6-inch blade. RC-10, 5/16 x 6-inch blade.—Vaco Products Co., 317 E. Ontario St., Chicago 11, Ill.

UHF CONVERTER, model BTU-2R Ultraverter. Adds uhf chan-

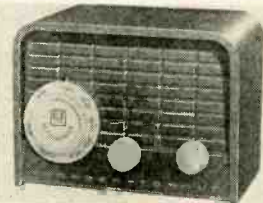

nels 14-83 to standard vhf receivers. Uses 2 tubes, matches 300-ohm line.—Blonder-Tongue Laboratories Inc., 9 Alling St., Newark 2, N. J.

LONG-NOSE PLIERS, shock-proof. Made of high-impact plastic. Designed for high-voltage work.—General Cement



Manufacturing Co., Div. of Tectron Inc., 400 S. Wyman St., Rockford, Ill.

INSULATION SPRAY, No-



NEW DEVICES (Continued)

Noise Rubber Coat Spray. Prevents arcing, shorting, corrosion due to moisture. Nonflammable and contains no plastic.—**Electronic Chemical Corp.**, 813 Communipaw Ave., Jersey City, N. J.

STEREO PHONO CARTRIDGE, for 45-45 stereo disc reproduction. Electrodynamic type uses twin D'Arsonval movements. Response from 20 to beyond 18,000 cycles. Output impedance



20 ohms at 1 kc. Crosstalk ratio 20 db. Output voltage 2 mv at 10 cm/sec. Fits standard arms.—**Electro-Sonic Laboratories Inc.**, 35-54 36th St., Long Island City 6, N. Y.


STEREO CARTRIDGE, Ceramalex. Single ceramic element. Frequency range from 50—15,000 cycles ± 5 db into 3-megohm load. Typical channel separation 20 db. Output voltage at 1,000 cycles is 0.5 minimum. 6-8 grams tracking force.—**Erie Resistor Corp.**, Electronics Div., 644 W. 12 St., Erie, Pa.

CERAMIC CARTRIDGE, Series 7. Model 7T-S: dual sapphire turnover unit. Model 7T-D: a dual diamond model. Response flat within 2 db from 20-12,000 cycles plus smooth rolloff up to




20,000 cycles.—**Sonotone Corp.**, Elmsford, N. Y.

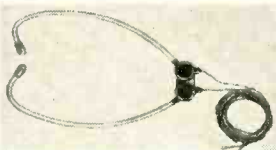BINAURAL HEADPHONES, Model MS-431, 6 ohms impedance, magnetic. **Model MS-432**, 5,000 ohms, magnetic. **MS-433**, 100,000 ohms, crystal. Response 40-16,000 cycles. — **Lafayette**



Radio, 165-08 Liberty Ave., Jamaica 33, N. Y.

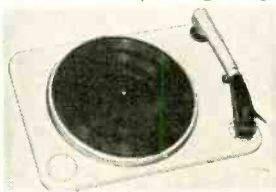
HI-FI RECORD PLAYER, Model B-21. 4 speeds, each may be varied within 5% range. 4-pole



motor. Plug-in head. Turntable covered with serrated rubber pad.—**David Bogen Co.**, Div. of **Siegler Corp.**, P. O. Box 500, Paramus, N. J.

4-SPEED RECORD CHANGER,

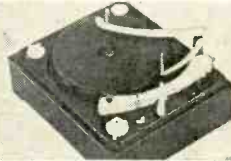Garrard model RC121/II. Plays as either an automatic-intermix changer or single-play unit with pickup arm completely free. 4-pole induction surge motor with dynamically balanced rotor. Turret drive. Cast-aluminum pickup arm with removable




head. Stylus pressure and height adjustments. — **Garrard Sales Corp.**, 80 Shore Rd., Port Washington, N. Y.

DOUBLE-PLAY TAPE, Sonoramic. Uses DuPont Tensilized



Double-Play Mylar as base. Comes in 2,400-foot 7-inch reels. — **Ferrodynamics Corp.**, Lodi, N. J.

4-CHANNEL TAPE HEAD,

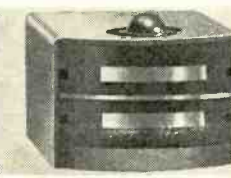

model TR-48. Record-playback type. Has 2 tracks, each .031 inch wide and 0.119 inch apart. Permits recording or playback of 4 channels on one ¼-inch tape.—**Shure Brothers Inc.**, 222 Hartrey Ave., Evanston, Ill.

FM TUNER, model LT-70. Sensitivity 4 μ v for 20-db quieting. Less than 1% distortion. Response 20-20,000 cycles within 1 db. Multiplex and tape recorder outputs as well as usual



audio output.—**Lafayette Radio**, 165-08 Liberty Ave., Jamaica 33, N. Y.


FM-AM TUNER-PREAMPLIFIER, Knight KN-200. Tuner section provides 3.5- μ v sensitivity for 20-db quieting on FM and 10 μ v for 20-db signal-to-noise ratio on AM. Tuner section has afc and EM 81 indicator tube.



Preamp has scratch filter, rumble filter; volume, loudness, bass, treble controls. Separate rolloff and turnover controls provide 12 record compensation

Get This Valuable Book

FREE

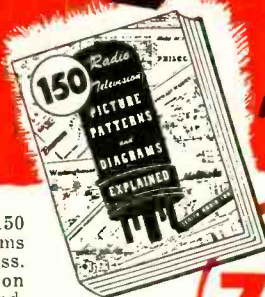

Just For Examining **COYNE'S** New Set

"Applied Practical Radio-Television"
on **7 DAY FREE TRIAL!**

Yes, you get this big, brand new book, "150 Radio-Television Picture Patterns and Diagrams Explained", absolutely FREE! Just off the press. Gives complete 11 x 22" Schematic Diagrams on leading models Radio and TV Sets. Easy-to-read, large 8 1/2 x 11" pages, with full instructions on how to use the diagrams. A "must" in every repair kit. You get this book as a FREE Gift for asking to see Coyne's new 7-book set. "Applied Practical Radio-Television"!

At Last! Money-Making "Know-How" on Transistors, Color TV and Servicing

Coyne's great 7-volume set gives you all the answers to servicing problems—quickly! For basic "know-how" that's easy to understand you'll find everything you want in Volumes 1 to 5 on over 5000 practical facts and data. Every step from fundamentals to installing, servicing and trouble-shooting all types of radio and TV sets. So up-to-date it covers COLOR TV, UHF and the latest on TRANSISTORS. All this plus Volume 7—NEW Coyne **TECHNICAL DICTIONARY** with over 4000 definitions of the latest terms, symbols and abbreviations in radio-TV, electronics and electricity.

EXTRA! 868 Page TV Cyclopedic Included!

For speedy on-the-job use, you also get Vol. 6—famous Coyne **CYCLOPEDIA**. Answers problems on servicing, alignment, installation, etc. in easy ABC order. Use this 7-volume **TV-RADIO LIBRARY FREE** for 7 days; get the Servicing Book FREE!

FREE! New Supplements

With your set you also get Coyne's annual Supplement Service FREE for 5 years. Keeps you up-to-date on latest radio and TV developments. Yours, absolutely FREE, if you act now!

NOW!
7 BIG BOOKS
IN ONE GREAT SET!



SEND NO MONEY! Just mail coupon for 7-volume set on 7 days free trial. We'll include book of 150 TV-Radio Patterns & Diagrams. If you keep the set, pay \$3 in 7 days and \$3 per month until \$24.50 plus postage is paid. (Cash price, only \$22.95). Or you can return the library at our expense in 7 days and owe nothing. **YOU BE THE JUDGE.** Either way, the book of TV-Radio Patterns is yours **FREE** to keep! Offer is limited. Act **NOW!**

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL, Dept. 58-T1
500 S. Paulina St., Chicago 12, Ill.

YES! Send 7-Volume "Applied Practical Radio-Television" for 7 days FREE TRIAL per your offer. Include TV-Radio Patterns & Diagram Book FREE.

Name.....Age.....

Address.....

City.....Zone.....State.....

Where Employed.....
 Check here if you want library service. C.O.D. You pay postman \$22.95 plus C.O.D. postage on delivery. 7-day money-back guarantee.

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL
500 S. Paulina St., Dept. 58-T1, Chicago 12, Ill.


positions. Inputs for magnetic and ceramic cartridges, mike, tape recorder, tape head or crystal phono. Two outputs—for amplifier and tape recorder.—**Allied Radio Corp.**, 100 N. Western Ave., Chicago 80, Ill.

STEREO PREAMP and control amplifier, model *SM-244*. 28 watts peak each channel, 14 watts rms continuous each channel. Harmonic distortion less than 1%. IM distortion less than 1.5% at full output. Hum and




noise 80 db below full output. Frequency response within 1 db from 20-20,000 cycles. Output impedances, 4, 8 or 16 ohms. Tape output, 500 ohms. Inputs for phono, tape head, mike, radio and auxiliary.—**Pilot Radio Corp.**, 37-06 36th St., Long Island City 1, N. Y.

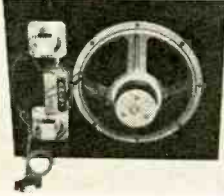HI-FI SPEAKER SYSTEM, model *W*. 12-inch woofer, two 3½-inch cone type tweeters with crossover network cover 40-15,000 cycles. Handles 24 watts. Fully wired, mounted on 16 x 20-inch plywood board. Impedance 8 ohms.—**Allied Radio**



Corp., 100 N. Western Ave., Chicago 80, Ill.

CERAMIC CAPACITORS, Ultra-Kaps. For transistor circuit applications. 0.22, 0.47, 1.0

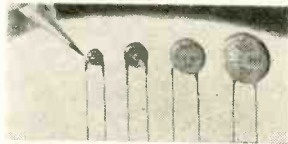


and 2.2 μ f. All rated at 3 volts dc. Size ranges from ¼-¾ inch diameter.—**Centralab, Div. of Globe-Union Inc.**, 900 E. Keefe Ave., Milwaukee 1, Wis.

TANTALUM SLUG CAPACITORS. Miniature units 15/32 inch long and 7/32 inch in




diameter. Range from 30 μ f at 6 volts to 1.75 μ f at 125 volts. Operate between -55 and 100°C without derating.—**Pyramid Research & Development Dept.**, Pyramid Electric Co., 1445 Hudson Blvd., N. Bergen, N. J.

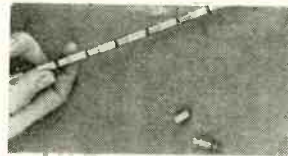EXPANDABLE RECTIFIER, model *A750*. Each silicon unit




1-inch long and rated at 400 volts inverse with maximum forward current rating of 750 ma. Threaded on each end, units screw together to form high-voltage series chain. Also in units rated up to 5 amps.—**Audio Devices Inc.**, 620 E. Dyer Rd., Santa Ana, Calif.

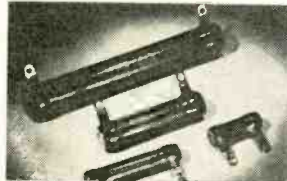VITREOUS-ENAMEL RESISTORS, Greenohm V line. Fixed and variable types. 5-200-watt ratings, resistance values 1-



900,000 ohms, tolerances of $\pm 5\%$ for 50 ohms and up or $\pm 10\%$ for 49.9 ohms and under.—**Clarostat Manufacturing Co., Inc.**, Dover, N. H.

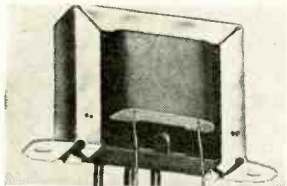REPLACEMENT TRANSFORMER, Stancor model VBO-201. Replaces vertical blocking oscillator transformer used in models of Airline, Crosley, Hallicrafters, Hoffman, Hyde Park, Motorola, Sentinel, Silvertone and Sylvia TV receivers.—**Chicago**




Standard Transformer Corp., 3501 Addison St., Chicago 18, Ill.

FM RADIO ANTENNAS, model FMY-8 (illustrated). High gain, 8-element directional Yagi. Flat response over FM band with 10.2-db gain. Model *FM3A*: an-



tenna, mast, roof mount, fasteners, lead-in and set clip. Nondirectional. Preassembled.—**Winegard Co.**, 3000 Scotten Blvd., Burlington, Iowa.

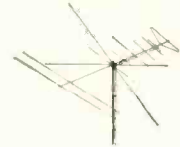CONICAL-YAGI TV ANTENNA, Winged 88. Single and two-bay



models. Improved version of the *Sharpshooter 88*.—**Trio Manufacturing Co.**, Griggsville, Ill.

AUTO RADIO ANTENNA, model JA-7 Bullet. Chrome, die-cast swivels for vertical or 45° angle mounting. 3-section telescoping mast extends to 57 inches.—**Tenna Manufacturing Co.**, 7580 Garfield Blvd., Cleveland 25, Ohio. END

All specifications given on these pages are from manufacturers' data.

Let Electronics Serve The Family

Perma-Power Garage Door Opener

RADIO CONTROLLED

Just press the dashboard button . . . the garage door opens and the light goes on. Press again to close and lock securely. It protects at night and during bad weather. Any member of your family can open or close the door, as easy as ringing a bell . . . and from the comfort of your car.



Just Press the Button

Perma-Power FEATURES:

- ★ ASSURED RELIABILITY
- ★ One year guarantee
- ★ Meets F. C. C. Requirements
- ★ Easy installation with illustrated instructions
- ★ Completely automatic safety devices
- ★ Operates from over 100 ft.
- ★ Low cost; complete package
- ★ BUY NOW!

Perma-Power COMPANY

3100 N. ELSTON AVE. CHICAGO 18, ILLINOIS
Manufacturers of Electronic Equipment Since 1928

SAVE ½ — PAY PART-BY-PART — HAVE FUN

Assembling the SCHOBER ELECTRONIC ORGAN in KIT form



NO SPECIAL SKILLS NEEDED

Now you can afford a real, full concert organ, just like those made by the foremost organ manufacturers. Because over ½ the cost is saved when you assemble it yourself. And it's REALLY EASY: only 24 separate units, all with printed circuits, and detailed-to-the-smallest-step instructions. In addition, you purchase each of the 24 kits when you are ready for it — and can afford it.

You'll get a real kick out of putting the Schober Electronic Organ* together — and then sitting down and pulling the stops for Strings, Trumpets, Clarinets, Diapasons, Flutes, etc. Electronic Percussion optional; chimes available.

Compact CONSOLE

One of the many exclusive features of this exceptional organ is the handsome console, in a wide variety of finishes. It is equally at home in a traditional or modern setting, and takes little more space than a spinet piano.

Free Literature

Complete descriptive booklet and price list are available on request. And, if you wish to hear the glorious pipe organ tone of the Schober Electronic Organ, a 10" long-playing demonstration recording is available for \$2. This is refundable when you order. Write today and see what a fine instrument you can get at such a great saving.

The SCHOBER ORGAN CORP.

2248-B Broadway, New York 24, N. Y.

*Designed by Richard H. Dorf

Technotes



MICROPHONIC JITTER

The photo illustrates an intermittent contact of a tube shield (over an oscillator tube) in a TV tuner. Jarring would cause the shield to contact the chassis, forming a new (and unwelcome) addition to the tuned-circuit



parameters of the local oscillator. The speaker vibrated the chassis, varying the fine tuning and detuning the set!

The remedy was simply to bend the chassis shield so that the tube shield would not contact it.—James A. McRoberts

RCA 21CS7815

We were called out to answer a complaint on wrong colors. Preliminary checks showed that both Y and chroma signals were coming through at satisfactory levels. However, color sync was uncertain, particularly at the counter-clockwise end of the hue control, and no adjustment of the hue control would produce the proper sequence of colors.

Changing tubes in the chroma section had no effect on the picture, except to shift the range of the hue control. The maximum shift obtained by changing tubes still did not bring the range to normal.


Because of the uncertain color sync, we then assumed that the burst amplifier might have drifted in its tuning, so that the burst was being attenuated and shifted in phase.

Noting carefully where the slug in the burst amplifier was set, we made a trial turn and lost color sync completely. Then we tried a turn in the opposite direction—the color dropped into tight lock and the correct color sequence was displayed at the center position of the hue control. Now the hue control could be turned through its complete range without loss of color sync.—Robert G. Middleton

SLOW TUNING

"It just won't select stations fast enough" was the complaint as the lady customer set the ivory table model down

TELEVISION

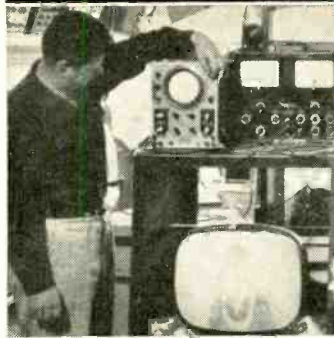

AT HEALDS YOU LEARN BY DOING IN MODERN ELECTRONICS LABORATORIES

HEALD ENGINEERING COLLEGE

Established 1863

Van Ness at Post, RE
San Francisco, Calif.

Never before in American history has the need been so great for Trained Engineers and Technicians. No other type of training can compare with actual shop practice you get at Healds under expert instructors.

Bachelor of Science Degree, 27 Months

- Television Technician including Color TV (12 Months)
- Electronics Technician (12 Months)
- Industrial Electronics Technician (12 Months)
- Electronics Engineering (B.S. Degree)
- Electrical Engineering (B.S. Degree)
- Mechanical Engineering (B.S. Degree)
- Civil Engineering (B.S. Degree)
- Architecture (B.S. Degree)

Heald College ranks FIRST West of the Mississippi in "Who's Who in America"

Approved for Veterans
DAY AND EVENING CLASSES

Write for Catalog and Registration Application.
New Term Starting Soon.

Your Name
Address
City
State


INVALUABLE!

ELEMENTS OF MAGNETIC TAPE RECORDING
by N. M. Haynes—Published by Prentice-Hall, Inc.
The book that brings you up-to-date on tape recording. Complete history, theory, design. 392 Pages, 265 Illustrations, 5 1/4" x 9". Only \$7.95 or better book stores or get your autographed copy directly from author. Remit with order please. Book mailed same day. Order from:



AMPLIFIER CORP. of AMERICA 398 Broadway, New York 13, N. Y.

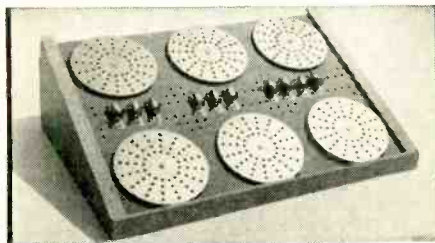Can you think . . . faster than this Machine?



Control Panel of GENIAC set up to do a problem in check valve research.

Be careful before you answer. GENIAC® the first electrical brain construction kit is equipped to play tic-tac-toe, cipher and encipher codes, convert from binary to decimal, reason (in syllogisms) as well as add, subtract, multiply and divide. Specific problems in a variety of fields—actuarial, policy claim settlement, physics, etc., can be set up and solved with the components. Connections are solderless and are completely explained with templates in the manual. This covers 125 circuits and shows how new ones can be designed.

You will find building and using GENIAC® a wonderful experience; one kit user wrote us: "This kit has opened up a new world of thinking for me." You actually see how computing, problem solving, and game play (tic-tac-toe, nim, etc.) can be analyzed with Boolean Algebra and the algebraic solutions transformed directly into circuit diagrams. You create from over 400 specially designed and manufactured components a machine that solves problems faster than you can express them.

Schools and colleges, teachers of science or math, engineering, philosophy or psychology will find these excellent demonstrations of circuitry solutions in symbolic logic, theory of numbers, cybernetics, and automation.

Note: Teachers take advantage of our 10% discount to educational institutions and for group purchases.

SEND for your GENIAC® kit now. Only \$19.95 with over four hundred components and parts, fully illustrated manual and wiring diagrams. We guarantee that if you do not want to keep GENIAC® after one week you can return it for full refund.

-----MAIL THIS COUPON-----
**SCIENCE KITS, Dept. RE-58, Oliver Garfield Co.
108 East 16th Street, New York 3, N. Y.**

Please send me:
1 GENIAC Electric Brain Construction Kit and Manual.
\$19.95 (East of Mississippi)
\$20.95 (Elsewhere in United States)
\$21.95 (Outside the United States)

Returnable in seven days for full refund if not satisfied.
I enclose \$..... in full payment.
My name and address are attached.

TAPE RECORDERS

HI F COMPONENTS

Tapes—Accessories

UNUSUAL VALUES

Send for Free Catalog

RESSNER

65-02 RE: 174 St.

Freshing 65, N. Y.



STEREO LAYS AN EGG

Stereo can be wonderful but it just doesn't come naturally by the use of two of everything in sound. Unfortunately, this is what too many are realizing after substantial investments in this glamour child of high fidelity.

Stereo actually requires still higher fidelity than single channel systems due to the highly critical timing sequences which must be maintained until the separate signals reach each of the listeners' ears. Probably the most difficult problem in this regard is in the speaker system which now must reproduce and radiate these signals in the exact sequence required.

If this requirement is not met, and we have a virtual dissection of the input signal combined with random phasing and haphazard blending topped off by highly directive radiation, "stereo will most surely lay an egg," regardless of the cost involved.

With the use of a pair of the patented Karlson Enclosures and a couple of good wide range speakers, all these complicated requirements are automatically realized and you can have the very best in stereo at the most modest prices.

These enclosures are designed for 8, 12, 15 inch speakers and are available in kit, unfinished, and finished form at prices you can afford ranging from \$18.60 to \$174.00. Special models are also available for obtaining more optimum phasing with large multiple speaker systems.

Write to Karlson Associates, Inc., Dept. RE9, 1610 Neck Road, Brooklyn 29, New York for free catalog.

do you
want a
successful
career in
AVIONICS?
(Electronics-Aeronautics)

NOW

at **NORTHROP INSTITUTE**,
you can combine
specialized education
in these two
TECHNOLOGICAL FIELDS!

You no doubt realize that there are **HIGH SALARY** opportunities available right now for young men trained in the field of **ENGINEERING TECHNOLOGY**. You also should realize that there will be even greater opportunities for trained men in the years just ahead.

Training takes only 2 years

The quickest way you can take advantage of this demand from Industry is to enroll at an Industry-approved school—Northrop Institute—in Aeronautical—Electronics Engineering Technology. Thousands of Northrop graduates have used this training to qualify for fine positions in Industry. **AND SO CAN YOU!**

Whether your present or future interest lies in the communications aspects of **Electronics**; industrial automation; automatic guidance systems, electronic computers; or control and safety equipment systems; whether you wish to specialize in piloted aircraft or missiles—you owe it to yourself to find out about **NORTHROP INSTITUTE TRAINING**. Just fill out and mail the coupon below. Do it now!

Approved for Veterans



Northrop
Aeronautical Institute

An Accredited Technical Institute
1189 W. Arbor Vitae Street
Inglewood 1, California

NORTHROP AERONAUTICAL INSTITUTE
1189 W. Arbor Vitae Street, Inglewood 1, Calif.
Please send me immediately the Northrop catalog, employment data, and schedule of class starting dates. I am interested in:

- Electronic Engineering Technology
- Aeronautical Engineering Technology
- Aircraft Maintenance Engineering Technology
- Master Aircraft and Engine Mechanic
- Jet Engine Overhaul and Maintenance

Name Age

Address

City Zone .. State


Veterans: Check here for Special Veteran Training Information.

TECHNOTES (Continued)

on the counter. "Isn't there something you can do about it?" she asked.

"Yes, ma'am, there sure is," I replied. "Come back in about a half hour and I'll have it fixed."

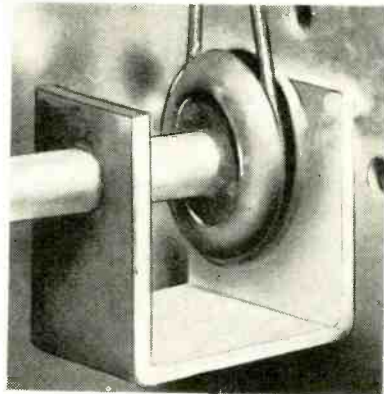I expected the set to have a slipped dial cord but it didn't. It did, however, take more than a couple dozen turns to tune from one end of the dial to the other. I knew then that I would have to step up the ratio of the tuning shaft. I did this by slipping two tight-fitting rubber grommets over the shaft—one cemented inside the other. I then re-strung the dial cord as shown in the photo.




When Mrs. Housewife came to pick up the set, I had her try the dial. "It works fine now," she said. "You see, the reason it bothered me so much, I listen to a program at 650 on the dial

and, right after it is over, Elvis Presley comes on at 1420. He's usually halfway through 'Don't Be Cruel' before I can turn from one end of the dial to the other."


The moral to the story?—Don't be cruel to housewives.—*John A. Comstock*

NO RED

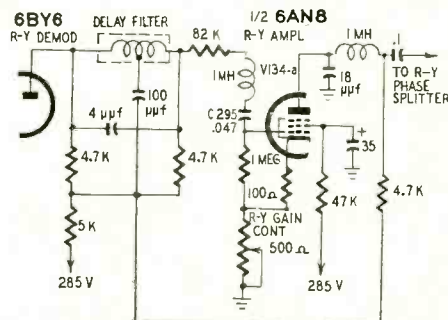Complaint: "Something wrong with the color." No red could be seen on the screen. After trying the usual tubes we pulled the chassis, an RCA CTC3. Circuit checks revealed loss of the R - Y signal. Voltage readings in the R - Y circuit disclosed a high voltage



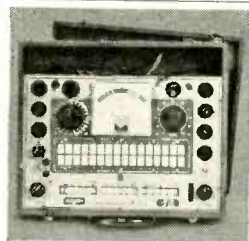on the grid of V134-a, the R - Y amplifier. Further checks showed that coupling capacitor C295 had shorted, allowing B-plus voltage to appear at the grid, paralyzing the R - Y amplifier. Capacitor and tube were replaced, set returned and everyone was satisfied. —*B. Lawrence* END



SAVE 4 WAYS
WITH A
JACKSON 648A
DYNAMIC® TUBE TESTER

SAVE ON TIME

Jackson 648A, with fingertouch sequence switching is the world's fastest fully-flexible tube tester.

SAVE ON CALL BACKS

Jackson 648A features famous Jackson Dynamic® circuit, for reliable tests on all radio, tv and most industrial tubes.

SAVE ON INVESTMENT

Jackson 648A is one of the lowest cost, fully-reliable, fully-wired testers on the market.

SAVE ON UPKEEP

Jackson 648A is fully flexible, provides for almost any new development in tube design. No cards to lose. No sea of sockets to confuse you. 23 Separate heater voltages—more than any other tester. Latest test data published monthly on page 65, PF Reporter.



Famous "Service-Engineered" Test Equipment

JACKSON ELECTRICAL INSTRUMENT COMPANY
16-18 S. Patterson Boulevard • Dayton 2, Ohio

SPRAY or DROP it



the **NEW QUIETROLE**
Spray-Pack

or the **QUIETROLE**
Bottle with the **Eye Dropper Cap**



Now **QUIETROLE** offers you both types of containers. Either way assures you of the same unfailing results that **QUIETROLE** is known for.

Make your next purchase **QUIETROLE**, get both and learn the difference between quality and poor substitutes. **QUIETROLE** is the original product of its kind, it is a **FIRST** of the industry and you can depend on it to end your noisy control and switch troubles.

manufactured by
QUIETROLE
COMPANY
Spartanburg, South Carolina


Business and People

Tobe-Deutschmann Corp., Distributor Div., Indianapolis, Ind., is promoting its service capacitors with a contest for service technicians. A Ford Ranch Wagon is the grand prize. Contest closes May 31.


CBS-Hytron, Danvers, Mass., is offering service technicians a series of



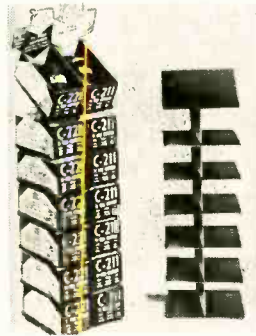four new signs, including indoor clock, outdoor, flange and electric clock signs. Perma-Power Co., Chicago, designed a new display rack to push sales of its



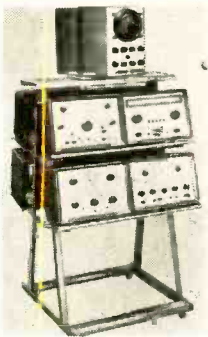Tube Briteners and color TV service aids. RCA Electron Tube Div., Harrison, N. J., introduced two new service-shop aids to service technicians as a bonus for purchases of RCA test equipment.





The Swivel-Scope provides a rotating base for the oscilloscope and the Porta-Rack will accommodate TV alignment equipment.

ORRadio Industries, Opelika, Ala., opened its new plant late in March. Sen. John Sparkman made the key address and many prominent guests including Peter L. Jensen watched a demonstration of the new Ampex TV video tape recorder.

Capitol Radio Engineering Institute,

YOUR SEMICONDUCTORS off-the-shelf!

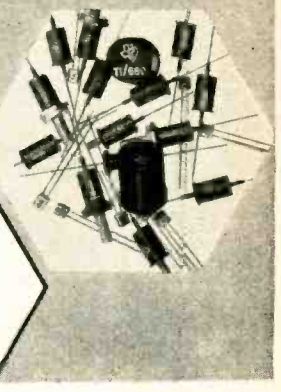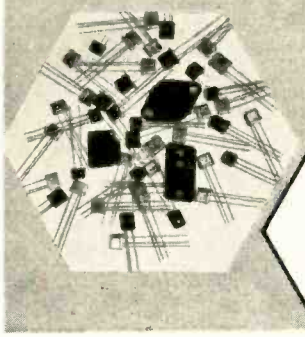

your
TI distributors
give you
off-the-shelf delivery
of all TI Semiconductors
... the industry's
widest line

GERMANIUM VHF, high frequency, radio converter and IF, audio output, general purpose, and phototransistors.
SILICON high temperature, high power, medium power, switching, high frequency, and small signal transistors. (There are more TI types of silicon transistors than the silicon types of all other manufacturers.)
SILICON DIODES with higher voltage operation plus extremely low power loss... both metal and glass case types available.
SILICON RECTIFIERS for high voltage power supplies in high temperature applications.

Check the list below for the TI distributor closest to you
... call him today for immediate off-the-shelf delivery.

- | | | |
|---|---|---|
| ALBUQUERQUE , New Mexico
MIDLAND SPECIALTY CO.
1712 Lomas Blvd. N. E.
Tel: 7-0236 | DAYTON 4 , Ohio
SREPCO, INC.
314 Leo Street
Tel: BAldwin 4-3871 | NEWARK 2 , New Jersey
RADIO WIRE TELEVISION OF N. J., INC.
24 Central Avenue
Tel: MARket 2-1661 |
| ATLANTA , Georgia
ACK RADIO SUPPLY COMPANY OF GEORGIA
331 Luckie Street N. W.
Tel: JA 4-8477 | DENVER 4 , Colorado
DENVER ELECTRONIC SUPPLY CO.
1254 Arapahoe Street
Tel: AMherst 6-1671 | NEW YORK 6 , New York
MILGRAY ELECTRONICS, INC.
136 Liberty Street
Tel: REctor 2-4400 |
| BIRMINGHAM , Alabama
ACK RADIO SUPPLY COMPANY
3101 Fourth Avenue South
Tel: FA 2-0588 | DETROIT 38 , Michigan
FERGUSON ELECTRONIC SUPPLY CO.
2306 Puritan Avenue
Tel: UN 1-6700 | NEW YORK 13 , New York
RADIO WIRE TELEVISION, INC.
100 Sixth Avenue
Tel: REctor 2-8600 |
| BOSTON 10 , Mass.
RADIO WIRE TELEVISION, INC.
110 Federal St.
Tel: HUbbard 2-7850 | EL PASO , Texas
MIDLAND SPECIALTY CO.
500 W. Paisano Drive
Tel: KEystone 3-9555 | OAKLAND 7 , California
ELMAR ELECTRONICS -
140 Eleventh Street
Tel: Hlgate 4-7011 |
| BUFFALO 16 , New York
GENESEE RADIO AND PARTS CO., INC.
2550 Delaware Avenue
Tel: DElaware 9661 | GLENDALE 1 , California
R. V. WEATHERFORD CO
6921 San Fernando Road
Tel: Victoria 9-2471 | PLAINFIELD , New Jersey
LAFAYETTE RADIO CORPORATION
139 W. 2nd Street
Tel: 6-4718 |
| CAMDEN 2 , New Jersey
GENERAL RADIO SUPPLY CO.
600 Penn Street
Tel: WOODlawn 4-8560
Tel: WALnut 2-7037 | HOUSTON 1 , Texas
HARRISON EQUIPMENT CO.
1422 San Jacinto (Box 2514)
Tel: CApitol 8-6315 | ROCHESTER 5 , New York
ROCHESTER RADIO SUPPLY COMPANY, INC.
600 E. Main Street
Tel: LOcust 2-9900 |
| CEDAR RAPIDS , Iowa
GIFFORD-BROWN, INC.
618 First Street N. W.
Tel: EMpire 4-2491 | JAMAICA 33 , New York
RADIO WIRE TELEVISION, INC.
165-08 Liberty Avenue
Tel: JAmaica 3-4600 | SALT LAKE CITY 10 , Utah
STANDARD SUPPLY CO.
225 East Sixth South Street
Tel: ELgin 5-2971 |
| CHICAGO 80 , Illinois
ALLIED RADIO CORPORATION
100 N. Western Avenue
Tel: HAymarket 1-6800 | LOS ANGELES 15 , California
RADIO PRODUCTS SALES, INC.
1501 S. Hill Street
Tel: RIchmond 9-7471 | SAN DIEGO 1 , California
RADIO PARTS CO.
2060 India Street
Tel: BElmont 9-9361 |
| CHICAGO 6 , Illinois
NEWARK ELECTRIC CO., INC.
223 W. Madison Street
Tel: STate 2-2944 | WEST LOS ANGELES 64 , California
CALIFORNIA ELECTRONIC SUPPLY, INC.
11801-11 W. Pico Blvd.
Tel: BRadshaw 2-2124 | TULSA 10 , Oklahoma
ENGINEERING SUPPLY CO.
1124 East 4th Street
Tel: DIamond 3-8121 |
| CLEVELAND 15 , Ohio
PIONEER ELECTRONIC SUPPLY CO.
2115 Prospect Ave.
Tel: SUperior 1-9410 | MELBOURNE , Florida
ELECTRONIC SUPPLY
909 Morningside Drive
Tel: 1735 | WASHINGTON 1 , D. C.
ELECTRONIC WHOLESALERS, INC.
2345 Sherman Ave. N. W.
Tel: HUdson 3-5200 |
| DALLAS 35 , Texas
ENGINEERING SUPPLY CO.
6000 Denton Drive
Tel: FLEetwood 7-2861 | MIAMI 32 , Florida
ELECTRONIC SUPPLY
61 N. E. Ninth Street
Tel: FRanklin 9-4512 | |

SEMICONDUCTOR - COMPONENTS DIVISION

TEXAS INSTRUMENTS

INCORPORATED

POST OFFICE BOX 312 DALLAS, TEXAS

Washington, D. C., established an advanced home-study course in nuclear engineering technology. It will be made available this fall by CREI Atomic, Inc., a newly formed subsidiary.

CBS Tube Div., Danvers, Mass., has expanded its display packaging pro-



gram for germanium diodes with a new dispenser card for its popular 1N34-A. It lists the types the 1N34-A replaces.

Heath Co., Benton Harbor, Mich., moved to a new and greatly enlarged plant in the same city. The entire manufacturing operation, formerly in seven buildings, has been consolidated under one roof.

Merit Coil & Transformer Corp. got operations under way at its new plant in Merit Plaza, Hollywood, Fla., a full 2 weeks ahead of schedule. The company will continue to maintain regional offices in Chicago as well as headquarters in Florida.

Astron Corp., East Newark, N. J., increased its West Coast warehouse facilities managed by I. R. Stern & Co., Burbank, Calif.

Sylvania Electric Products switched its special tube operations headquarters from Woburn, Mass., to Williamsport, Pa.

David R. Hull, vice president and general manager of Raytheon's equipment operations, Waltham, Mass., was advanced to vice president for defense programs.



Donald W. Gunn, general sales manager of the Sylvania Electronic Tubes Div. since 1953, was appointed vice president-sales for the divi-



sion. He will continue to maintain headquarters in New York. W. Herbert Lamb (left) and Walter A. Weiss, were appointed vice presidents for television picture tubes and radio tubes, respectively, for the Electronic Tubes Div. Lamb, who had been general manager of the TV Picture Tube Div.

SPECIAL INTRODUCTORY OFFER!

VACO

Red Cap


"At Your Service"

Screw Drivers

Here's your chance to get a beautiful 5-piece screw driver set at a true bargain price! All the most popular sizes (including No. 2 genuine Phillips) plus—a FREE tool hanger board complete with patented, adjustable hanger hooks for holding your most frequently used tools. Here's how:

FREE Tool Hanger Board and Patented Hanger Hooks

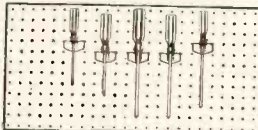Just mail in the coupon enclosed in the RC 15 Boxed Set and VACO will send you this 12" x 24" perforated masonite panel and set of hanger hooks at no charge.



A \$5.50 VALUE!

See Your Jobber, Today!



Regular price... \$3.65
Introductory Special...
\$2.98

VACO PRODUCTS CO., 317 E. Ontario St., Chicago 11, Ill.
In Canada: Atlas Radio Corp., Toronto 19, Ontario

TAPE RECORDERS

WHOLESALE PRICES

HI-FI COMPONENTS

NATIONAL BRANDS

WRITE FOR FREE CATALOGUE

CARSTON

215-TD E. 88 ST.
NEW YORK 28, N. Y.

30 Watt Hi-Fi Super Lin Kit

AMP-PREAMP with TRANSISTORIZED FRONT END

FREQUENCY RESPONSE:

+1 db 10-40,000 cps.


TUBES: uses (1) 6AU6.

(1) 12AT7, (1) 12AU7.

(2) EL34's, (1) 5V4-GB.


SHIPPING WEIGHT 26 lbs. FL-30

Sale Price... \$42.00

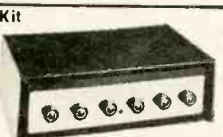

F.O.B. N.Y.

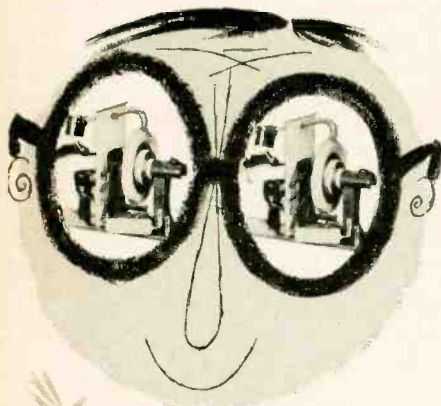Send for Free Catalogue
CUTICK ELECTRONICS HI-FI RADIO TV PARTS
171 Washington St., (Dept. R-E), New York 7, N. Y.



Seeing Double?

SURE... THEY LOOK ALIKE
BECAUSE
THEY ARE EXACTLY ALIKE

Each Merit product of the same type is exactly the same as another—both in construction and appearance.

COMPARE IT WITH MERIT

Take a Merit product off the shelf. Compare it with any other similar product on the market. You'll find Merit is superior!



COMPARE IT WITH
MERIT
MERIT COIL & TRANSFORMER CORP.

MERIT PLAZA, HOLLYWOOD, FLORIDA



SELECT-O-SWITCH

4-WAY SELECTOR SWITCH
Use as antenna switch or as a hi-fi speaker switch. Permits channeling one input to any one of 4 outputs.

model SS4 LIST \$3.25



Switch-in-Base

DUO-JUVENATOR

Parallel and Series TV tube booster. Cures 95% of all CRT failures. One-piece construction.

model RPS2 LIST \$2.95


TELE-LINK

2-SET TV & FM COUPLER

Matched transformers for peak performance on 2 TV or FM sets from one antenna.



model TL2 LIST \$2.95

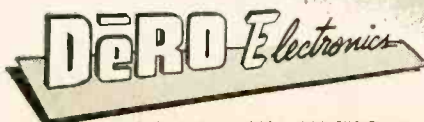

134 NASSAU ROAD, ROOSEVELT, N. Y.

in Seneca Falls, N. Y., will maintain his headquarters there. Weiss will remain at Emporium, Pa., where he had held the position of manager of the radio tube plant.

W. J. Zaun (left), former manager of quality control, was promoted to the



newly created position of manager-operations, Government service for the RCA Service Co., Camden, N. J. T. Y. Flythe, former administrator of technical products field quality succeeds him.

Arch Warden was elected a vice president of Xcelite Inc., Orchard Park, N. Y., manufacturer of hand tools. He will continue as sales manager. A. J.



(Arlie) Holmes, who joined the company last year, was named assistant sales manager.

Everett Leedom rejoined Electro-Voice, Inc., Buchanan, Mich., as advertising manager, a position he held previously for 2½ years. Jay Carver, whom he succeeds, becomes manager of the Wood Products Div. of Electro-Voice.

Edward H. Heller (left), prominent investment banker, and Jan Oostermeyer, former Shell Chemical Corp.



president, were elected to the board of directors of Siegler Corp., parent company of David Bogen Corp., Presto Recording Corp. as well as Olympic Radio & TV.

Henry G. Sellers, Jr., joined ORRadio Industries, Opelika, Ala., as assistant director of research. A chemist, he comes to the company from Newport Industries.



Robert G. Dailey, former vice president-sales, of Vokar Corp., Dexter, Mich., acquired full control of the company and moved its headquarters to Chelsea, Mich. END

"NOISE" BIG 3
Beware Of Cheap Substitutes!

NO-NOISE NEW RUBBER COAT SPRAY
6 Oz. Spray Can Net To Servicemen **\$3.25**

- Insulates where applied
- Protects indefinitely
- Prevents arcing, shorting, corrosion
- Waterproofs thoroughly
- Non-inflammable
- Contains no plastic

NO-NOISE VOLUME CONTROL and CONTACT RESTORER
• Cleans • Protects • Lubricates
NOT A CARBON TET SOLUTION
2 Oz. Bottle Net To Servicemen **\$1.00**
6 Oz. Spray Can Net To Servicemen **\$2.25**

NO-NOISE TUNER-TONIC With PERMA-FILM
• Economical—a little does a lot!
• Cleans, lubricates, restores all tuners, including wafer type.
• Non-toxic, non-inflammable.
• Use for TV, radio and FM
6 Oz. Aerosol Can Net To Servicemen **\$3.25**

ELECTRONIC CHEMICAL CORP.
813 Communipaw Avenue Jersey City 4, N. J.

COYNE TRAINS YOU IN SPARE TIME AT HOME

COYNE QUALITY TRAINING AT LOWEST COST

TELEVISION RADIO-COLOR TV

Only from famous COYNE do you get this modern up-to-the minute TV Home Training. Easy to follow instructions—fully illustrated with 2150 photos and diagrams. Not an old Radio Course with Television tacked on. Includes UHF and COLOR TV. Personal guidance by Coyne Staff. *Practical Job Guides* to help you EARN MONEY QUICKLY IN A TV-RADIO SALES AND SERVICE BUSINESS—part time or full time. COSTS MUCH LESS—pay only for training—no costly "put together kits."

SEND COUPON FOR FREE BOOK
SEND COUPON BELOW for Free Book and full details including EASY PAYMENT PLAN. NO COST OR OBLIGATION—NO SALESMAN WILL CALL.

B. W. COYNE, Jr., Pres. **COYNE ELECTRICAL SCHOOL** FOUNDED 1899

A TECHNICAL TRADE INSTITUTE OPERATED NOT FOR PROFIT
500 S. Paulina, Dept. 58-H5, Chicago 12, Illinois

COYNE ELECTRICAL SCHOOL
Television Home Training Div.
500 S. Paulina St., Chicago 12, Ill., Dept. 58-H5
Send FREE BOOK and details of your Television Home Training offer.

Name _____
Address _____
City _____ State _____

TRANSISTOR RADIO REPAIRS NOW EASY!

with this **NEW Sams BOOK "SERVICING TRANSISTOR RADIOS"**
COMPLETE ANALYSIS OF 70 POPULAR TRANSISTOR RADIO MODELS

includes new General Motors (Delco) Transistorized Auto-Portable Radio

Also Valuable Section—**"BASIC POINTERS ON SERVICING TRANSISTORIZED RADIOS"...**

COVERS LATEST MAKES AND MODELS
This book helps you earn big profits on Transistor Radio repairs—gives you complete, time-saving information—helps you become an expert on transistorized radios! Complete data on 70 latest models is based on actual lab analysis of each set. You get the famous Sams Standard Notation schematics—accurate, big, legible; full photo views of each chassis, with all components identified; complete alignment instructions; complete parts lists with full replacement data—everything you need to be successful in fast-growing transistorized radio servicing. Here's a "must" book for your bench. Order it now!
152 pages; 8½ x 11" **\$2.95**
PRICE ONLY.....

SEE THIS BOOK AT YOUR SAMS DISTRIBUTOR OR MAIL COUPON

FREE TRIAL COUPON

Howard W. Sams & Co., Inc., Dept. 2-EE8
2201 E. 46th St., Indianapolis 5, Ind.

Send me Sams "Servicing Transistor Radios" for 10 days FREE examination. In 10 days I will pay for the book, plus few cents delivery cost, or return postpaid.

We pay delivery costs if you remit with this coupon; same return privilege.

Name _____
Address _____
City _____ Zone _____ State _____
Outside U.S.A. priced slightly higher



THE FINEST AND MOST COMPLETE LINE OF
Transistor Coils & I.F. Transformers

All loops described below have a secondary which is overcoupled for maximum gain stability with a variation in output load. Designed to match an input impedance of approximately 600 ohms. These loops also make excellent antenna coils for conventional vacuum tube receivers. They offer better signal pickup and increased selectivity over ordinary air loops.

SUBMINIATURE ANTENNA LOOPS



An adjustable antenna coil with a high Q ferrite core. May be used with any variable condenser having a maximum capacity between 250 & 450 mmf. Dimensions: 1/2" x 2 1/2"

Cat. No.	Q @ 790 KC	Freq. Range	Tuning Cond. Max. Capacity	List Price
2002	250	540-1650 KC	250-450 mmf.	\$1.50

I. F. TRANSFORMERS



Catalog Nos. 2041 and 2042 are miniature I.F. transformers having a tuned primary and untuned secondary. The primary is tapped for use in circuits which require a tap. Proper impedance match between primary and secondary insures optimum performance. Dimensions: 1/2" sq. x 3/4" high.

Cat. No.	Freq.	Impedance	Use	List Price
2041	455 KC	25K—600 Ohms	Input	\$2.95
2042	455 KC	25K—1000 Ohms	Output	2.85

SUBMINIATURE



To our knowledge the 9-C1 and 9-C2 are the smallest I.F. transformers in existence. All technical specifications for the 2041 and 2042 apply respectively to the 9-C1 and 9-C2. Dimensions: 3/8" sq. x 5/8" high.

Cat. No.	Freq.	Impedance	Use	List Price
9-C1	455 KC	25K—600 Ohms	Input	\$3.50
9-C2	455 KC	25K—1000 Ohms	Output	3.50

UNSHIELDED MINIATURE OSC.



These coils are designed for use in a converter circuit using only one transistor for both the oscillator and mixer. Dimensions: 3/8" x 1" high

Cat. No.	Tuning Cond. Max. Capacity	I.F. Freq.	Use	List Price
2020	365 mmf.	455 KC	Osc.	\$2.00
2022	78-100 mmf.	455 KC	Osc.	2.00

SHIELDED SUB-MINIATURE OSC.



The 2021 oscillator coil is a sub-miniature shielded version of the #2022 described above. Identical in size to our 9-C1 and 9-C2 I.F. transformers. Designed for use with a condenser having a maximum capacity of approximately 100 mmf. (Miller #2110). 3/8" sq. x 5/8" high

Cat. No.	Tuning Cond. Max. Capacity	I.F. Freq.	Use	List Price
2021	100	455 KC	Osc.	\$2.50


STANDARD ANTENNA LOOPS



Due to its large pickup area the #2000 is one of our most popular loops. Dimensions: 3/4" x 9"

Cat. No.	Q @ 790 KC	Freq. Range	Tuning Cond. Max. Capacity	List Price
2000	450	540-1650 KC	365 mmf.	\$2.75


MINIATURE ANTENNA LOOPS

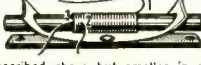

Similar to the #2000 described above but smaller in size for miniature sets. Slightly less signal pickup than the #2000, but extremely high Q. Dimensions: 3/4" x 3 3/4"

Cat. No.	Q @ 790 KC	Freq. Range	Tuning Cond. Max. Capacity	List Price
2001	550	540-1650 KC	365 mmf.	\$2.50
2003	500	540-1650 KC	125 mmf.	2.50

FLAT FERRITE LOOPS

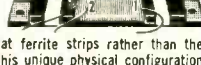

These coils are wound on flat ferrite strips rather than the normal ferrite rods. Due to this unique physical configuration they are remarkably sensitive for their small size. Dimensions: 1/4" x 3 3/4" x 3 3/4"

Cat. No.	Q @ 790 KC	Freq. Range	Tuning Cond. Max. Capacity	List Price
2004	500	540-1650 KC	365 mmf.	\$2.50
2005	450	540-1650 KC	125 mmf.	2.50

VARIABLE CONDENSERS



Catalog #2110 is a miniature 2-gang variable condenser. The antenna section has a range of 10-130 mmf. Catalog #2112 is a standard size 2-gang condenser having a range of 10-365 mmf. for both sections. Shaft is 1/4" dia. x 1 1/4" long.

Cat. No.	Sections	Dimensions	List Price
2110	2	1 1/4" x 1 3/4" x 1 1/4"	\$2.50
2112	2	2 3/4" x 1 1/4" x 1 1/4"	3.50

SOLD BY ALL LEADING RADIO AND TELEVISION PARTS DISTRIBUTORS
Write for General Catalog 37A

J. W. MILLER COMPANY
5917 South Main Street • Los Angeles 3, Calif.
Canadian Representative Atlas Radio Corp. Ltd. 50 Wingold Ave. Toronto 10, Ont. Canada

technical
Literature



Any or all of these catalogs, bulletins, or periodicals are available to you on request direct to the manufacturers, whose addresses are listed at the end of each item. Use your letterhead—do not use postcards. To facilitate identification, mention the issue and page of RADIO-ELECTRONICS on which the item appears. UNLESS OTHERWISE STATED, ALL ITEMS ARE GRATIS. ALL LITERATURE OFFERS ARE VOID AFTER SIX MONTHS.

PHYSICS AS A CAREER is a 16-page illustrated booklet describing what physics is and what the opportunities for new physicists are. Among the topics discussed are: physics—the science; physicists in industry and the training of the physicist.—American Institute of Physics, 335 E. 45 St., New York 17, N. Y.

ELECTRONICS COURSES, intended for home study, are offered in a 4-page bulletin. Radio, television and electronics are covered by the group.—Supreme Publications, 1760 Balsam Rd., Highland Park, Ill.

1958 STEREO TAPE CATALOG contains over 90 stereo titles in its 28 pages. The fields of classical, semiclassical, jazz, popular and folk music are represented. Also included are 150 monaural tapes. Stereo listings include all artists and selections on the tape. Individual sections are devoted to tape accessories and sampler and test tapes.—Livingston Audio Products Corp., Box 202, Caldwell, N. J.

TAPE IT OFF THE AIR is a how-to-do-it pamphlet which aids you in making quality recordings of radio programs. Hints on how to set the correct volume level and where to hook up your tape recorder to a radio or TV set are also included. —ORRadio Industries Inc., Shamrock Circle, Opelika, Ala.

HIGH-FIDELITY EQUIPMENT is described in several brochures and specification sheets announced by this firm.

The brochures: *EP-257*, a 3-color 10-section folder, with brief descriptions of hi-fi components and suggested home applications; *EP-243*, 12-page color booklet on diamond styli.

The specification sheets, all 4-page 4-color: *EP-235*, VR-II 4-gram cartridge and styli; *EP-234*, tone arms and replacement styli; *EP-237*, amplifier and preamps; *EP-238*, 12-inch wide-range speakers; *EP-233*, coaxial speakers; *EP-232*, woofers and tweeter, audio crossover network; *EP-239*, cabinets and enclosures.—General Electric Hi-Fi, Box 101, Liverpool, N. Y.

SYNTHETIC SAPPHIRE phono styli and an all-purpose dynamic microphone are

NOW . . . Check Vibrators In ANY Tube Checker

Another Sencore Time-Saver

“VIBRA-DAPTOR”

MODEL VB-2

2 ADAPTORS IN

Checks Both Three and Four Prong Vibrators

• Merely plug into any tube checker. Set for 6AX4 (or 6SN7) for 6 Volt Vibrators and 12AX4 (or 12SN7) for 12 Volt Vibrators.

• Two lamps viewed through top of adaptor indicate whether or not Vibrator needs replacing. • Rugged — Made of steel.

• Replaceable but unbreakable #51 indicating Lamps. • Operates easily with Sencore LC2 Leakage Checker. • Complete instructions screened on front.

At leading distributors everywhere

MANUFACTURED BY **SERVICE INSTRUMENTS CORP.**
171 OFFICIAL RD. ADDISON, ILL.

Cut out this ad for further information

ONLY \$275
DEALER NET

POPULAR SENCORE PRODUCTS

- Transistor Tester
- Leakage Checker
- Filament Tester
- Handy “36”
- Vibra-Daptor

BIGGEST BUYS OF '58!

Regency

ALL-TRANSISTOR Vest-Pocket RADIO READY TO PLAY!

\$14.95 Including 1000-hour batteries and phone!

Lektron scoops the field with the “hottest” pocket transistor radio since the advent of the transistor! Designed and built by Regency, one of America's great names in radio. Uses an exclusive circuit with RF, DET and AMF stages. SMALLER THAN A PACK OF CIGARETTES!—only 5 x 2 x 1". NO EXTERNAL ANTENNA OR GROUND—no hanging wires! Amazing sensitivity, volume and selectivity. Attractively designed two-tone styrene case. Variable tuning covers 540 to 1500 kcs. **READY TO PLAY** when you receive it! 1000-hour batteries and ultra-sensitive phone included in this fabulously low price! Gift packed. Wt. 1 oz. Postpaid.

SATISFACTION GUARANTEED!

20,000 OHMS/VOLT MULTI-TESTER

LOWEST PRICE IN U.S.A.!

\$17.99

Ready to go! 5 1/2 x 3 5/8 x 2 1/8". Test leads incl. Ranges: AC & DC V.: 0 to 1200, 600, 120, 30, 6, 20K ohms/volt; DC: 10K ohms/volt; AC: DC mts: 0 to 300, 12, 1.2; DC micro-amps: 0 to 80; DC ohms: 0 to 10K, 100K, 1 meg, 10 megs; DB: 20 to 17; CAPACITANCE: .0005 to .01; INDUCTANCE: 30 to 3,000 henrys. Ship wt. 5 lbs. Please include postage with this item; excess returned.

WRITE FOR NEW SUMMER BARGAIN FLYER!

LEKTRON

131 EVERETT AVE. CHELSEA 50, MASS.

described in catalog sheet ASC-200. The styli are intended for replacement and new equipment applications.—Argonne Electronics Mfg. Corp., 165-11 South Rd., Jamaica 33, N. Y.

FLYBACK AND YOKE replacements are presented on a hardy wall chart, listing Stancor exact-replacement parts. The chart, printed on index cardboard, lists each TV set manufacturer alphabetically. All units for which there is an exact replacement are listed in numerical order by the manufacturer's part number.—Chicago Standard Transformer Corp., 3501 W. Addison St., Chicago 18, Ill.

TWO-WAY RADIO and how it can save time and money for a service organization is the subject of an illustrated brochure *How Service Organizations Increase Efficiency With 2-way Radio*. Examples of how radio systems are used in auto emergency, ambulance, refrigeration repair, local delivery and other services are given.—RCA, Communications Equipment, Camden, N. J.

RADIO-PHONOGRAPH CATALOG contains complete information about this firm's 1958 line of high-fidelity consoles. A description of all models, including finishes and outstanding features, is offered.—Fisher Radio Corp., 21-21 44th Dr., Long Island City 1, N. Y.

TANTALUM ELECTROLYTICS are detailed in a 4-page folder. Characteristics of a full line of these units are presented along with a brief description of the theory behind them.—Texas Instruments Inc., Semiconductor Components Div., P. O. Box 312, Dallas, Tex.


TRANSFORMER CATALOG TR-58 describes and illustrates hundreds of transformers. Toroid, pulse, transistor, hermetically sealed, geophysical, power, heater and audio transformers, chokes and television components are among the listings.—Triad Transformer Corp., 4055 Redwood Ave., Venice, Calif. END

CORRECTIONS

In "Master Control Unit for Audio Tests" by Dr. L. B. Hedge, which appeared on page E4 of the March 1958 issue, reference 5 was omitted from the list at the end of the article. This should have read: L. B. Hedge, "The Long-Tailed Cascade Pair," RADIO-ELECTRONICS, October, 1956.

Mr. Wayne Lemons calls our attention to an error in his article "Taming The Horizontal Oscillator" which appeared in the April 1958 issue. The series resistor, from plate to ringing coil, should be 5.6K instead of 56K. Therefore the paragraph concerning R4 which states, "Temporarily shunt R4 with a resistor that will bring its value down to about 10,000 ohms" is also incorrect. In reality the technician will have to increase R4's value to 10,000 ohms by adding a series resistor.

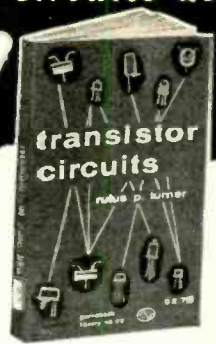Yours now—over 150 practical circuits using TRANSISTORS!



Rufus P. Turner, popular transistor authority and engineer, takes transistors out of the laboratory and puts them on the work bench. He has collected over 150 practical circuits for amplifiers, oscillators, power supplies, amateur equipment and other units. All were designed by experts—some by the author himself. All were tested in the author's laboratory—and all of them work! No watering down with transistor testing or theoretical explanation circuits! This book offers a treasure chest of building blocks which will save hours of tiresome designing. You can put these circuits to an infinite number of uses other than those originally suggested. No one who works with transistors at home or in the lab can afford to miss Turner's latest book. Order your copy now.

SOME OF THE HIGHLIGHTS

Audio Amplifiers • RF and IF Amplifiers • DC Amplifiers • Oscillators • Power Supplies • Radio Receivers • Triggers and Switches • Control Devices • Test Instruments • Amateur Devices • Miscellaneous Circuits including Geiger counter, phono oscillator, hearing aid, and intercom.

ORDER THESE COMPANION VOLUMES

Transistors—Theory & Practice—The practical man's "Bible" on transistors. Covers theory, characteristics, tests, plus a guide to commercial transistors. Written so the practical man can read, understand and learn how to work with transistors. No. 51—144 pages. \$2.00

Transistor Techniques—A handbook for the experimenter who wants to work with transistors! Gives scores of hints on how to use transistors in various types of equipment. Covers testing, performance, construction, care and measurements. A practical how-to-do-it book which keeps theory and math to a minimum. No. 61—96 pages. \$1.50

TRANSISTOR CIRCUITS—By Rufus P. Turner. 160 Pages. Gernsback Library Book No. 63. Paper cover. \$2.75

MAIL THIS COUPON TODAY

GERNSBACK LIBRARY, Inc., Dept. 58
154 West 14th St., New York 11, N.Y.

My remittance of \$..... is enclosed. Please send me the books checked below postpaid.

- No. 63 Transistor Circuits. \$2.75
 - No. 61 Transistor Techniques. \$1.50
 - No. 51 Transistors—Theory & Practice \$2.00
- Prices 15% higher in Canada.

NAME..... please print
STREET.....
CITY..... STATE.....

"OK! OK! So the Fred Astaire always comes out in you when you hear a JENSEN NEEDLE."

Dynaco Output Transformers

Featuring para-coupled windings, a new design principle (patents pending). These transformers use advanced pulse techniques to insure superior square wave performance and undistorted reproduction of transients. Dynaco transformers handle full rated power over the entire audio spectrum from 20 cps to 20 kc. without sharp rise in distortion at the ends of the band which characterizes most transformers. Conservatively rated and guaranteed to handle double nominal power from 30 cps to 15 kc without loss of performance capabilities.

Specifications:
Response: Plus or minus 1 db 6 cps to 60 kc.
Power Curve: Within 1 db 20 cps to 20 kc.
Square Wave Response: No ringing or distortion from 20 cps to 20 kc. Permissible Feedback: 30 db.


MODELS

A-41	10 watts	EL-84, 6V6, 6AQ5	14.95
A-42	25 watts	5881, EL-34, KT-66	19.95
A-43	50 watts	KT-88, EL-34	29.95
A-44	100 watts	KT-88, 6550	39.95
A-45	100 watts	PP par KT-88, EL-34	39.95

(all with tapped primaries except A-44 which has tertiary for screen or cathode feedback)

Additional data on Dynakit and Dynaco components available on request including circuit data for modernization of Williamson-type amplifiers to 50 watts of output and other applications of Dynaco transformers.

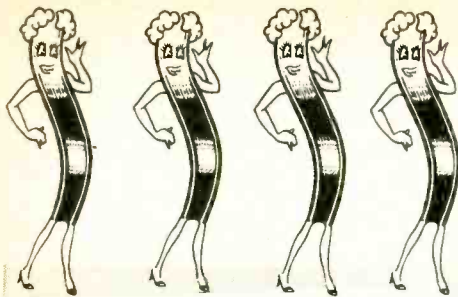DYNACO INC.
617 N. 41st, Philadelphia 4, Pa.
Export Division: 25 Warren St., New York, N.Y.



Which one can prove her **QUALITY?**

Most brands of twin lead look alike! Also, the price brands make the same claims of quality and performance as the top quality brands.

What Reason . . . What Proof

Can you give your customer that he is getting something better when he pays a little more for twin lead?

WITH *Columbia*
PERMALINE

Your Customer has the reason

So GOOD that it's
GUARANTEED up to 25 YEARS!

DISTINCTIVE APPEARANCE

HIGH MOLECULAR WT. POLYETHYLENE

DEVELOPED AFTER YEARS OF RESEARCH

See your Jobber . . .

Ask him about Permaline — and ask to see the Laboratory Report on weathering studies of Polyethylene.

Once you "Try" COLUMBIA . . . you'll want to always "Buy" Columbia . . . Because only, but only COLUMBIA gives you a complete guarantee for 25 YEARS.

AVAILABLE AT ALL LEADING DISTRIBUTORS

Columbia
WIRE & SUPPLY CO.

2850 IRVING PK. RD., CHICAGO 18

This is the
2-Set TV COUPLER

Rated No. 1

• • • by a nationally known independent product quality rating group as the result of tests made on 10 leading two-set couplers for:

- IMPEDANCE MATCH
- SIGNAL TRANSFER
- TWO-SET ISOLATION

MOSLEY 902



List Price \$3.10


Rated **FIRST** in overall quality for weak signal reception means; the MOSLEY 902 Dual Match 2-Set TV Coupler can be sold and installed in practically any TV area with full confidence that your customers will be completely satisfied!

Available at Radio and Television
Parts Distributors — coast-to-coast.

Mosley
Electronics, Inc.

8622 ST. CHARLES ROCK ROAD
ST. LOUIS 14, MISSOURI

Books

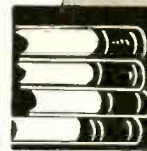

TV AND RADIO TUBE TROUBLES, by Sol Heller. Gernsback Library, Inc., 154 W. 14 St., New York 11, N. Y. 5½ x 8½ inches, 224 pages. \$2.90.

It's strange nobody thought of it before, but here at last is a book on tubes and the troubles they cause. Tubes are responsible for most service calls. Furthermore, the picture tube needs special handling and adjustments. A tester does not completely solve the tube problem, because of its limited scope.

Logically, the book begins with safety: the proper handling of a picture tube and how to minimize danger of implosion, burn, shock, X-rays. There are six chapters on common and uncommon TV defects where tubes play a leading role. Eliminating corona and arcing, adjusting a yoke, ion trap, pin-cushion magnet, are some nontube, but associated, problems also discussed. A separate chapter covers radio tube troubles, and the final one deals with tube replacement.

The book contains a wealth of time-saving information for people who are looking for trouble—in radios and TV receivers.—IQ


WIRELESS SERVICING MANUAL, 9th Edition, by W. T. Cocking. Wireless World by Iliffe & Sons Ltd., Dorset House, Stanford Street, London S.E. 1, England. 5¾ x 8¾ inches, 268 pages, 17s. 6d.

This is the latest version of a British radio servicing text that first appeared in 1936. Completely revised to take into account all the latest developments, it presents useful techniques of testing and repairing radio receivers. It is written with a definite British slant and such terms as h.t. are used instead of high voltage, a feature which makes reading a little difficult at first.—LS

HOW TO READ SCHEMATIC DIAGRAMS, by David Mark. John F. Rider Publisher, Inc., 116 W. 14 St., New York 11, N. Y. 5½ x 8½ inches, 147 pages. \$3.50.

A pictorial diagram or parts layout can help when it is desirable to change tubes or resolder broken leads and can guide the nontechnical constructor in assembling very simple equipment. For major radio repairs, construction or study, nothing takes the place of a schematic. It conveys full technical information, is easiest to interpret and, therefore, the most common type of circuit representation. However, some knowledge of basic theory is required to get maximum benefit from a schematic.

The Allsolver

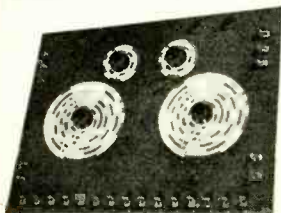

Add, subtract, divide, multiply, find roots, powers, solve trig and algebra. Learn to operate this transistorized miniature computer within hours!

Multiply as many as 10 numbers by adding a few more parts!

Special dials enable you to find the log, sin, cos, tan, etc. of numbers and read them or use for further problem solving.

Sent in kit form with meter and batteries, no soldering required. Request our FREE CATALOG in home-study courses in: COMPUTERS, AUTOMATION, ROBOTS, LOGIC, ELECTRONICS.

C14 COMPUTER MASTER (diploma issued), 50 lessons plus projects (digital voltmeter, digital ohmmeter, etc.) \$22.50 down and \$12.40 for 6 months.

EBEX School,

1015 Atkin Ave., Salt Lake City, 6,
Utah Div. of Electronic Brain Enterprises Inc.

Send the ALLSOLVER, enclosed \$38.50 (or \$14.50 and

GOD)

Send catalog on courses and kits.

Name _____

Address _____

ic. This book shows how to read wiring, pictorial and block diagrams as well as schematics. Along with the schematics the reader finds a simple discussion of the function of circuits and parts.

The author covers power supplies, amplifiers, oscillators, etc. By learning about these circuits and parts *separately*, the reader is soon able to identify them when combined in a complete schematic. The book is suitable for beginners who wish to learn the elements of radio, or workers in other fields who need to repair or adjust electronic instruments from time to time.

IDEAS, INVENTIONS, AND PATENTS, by Robert A. Buckles. John Wiley & Sons Inc., 440 4th Ave., New York 16, N. Y. 9 x 6 inches, 270 pages, \$5.95.

Have you built that better mouse-trap? Perhaps it came in the form of a new video amplifier circuit or maybe you've come up with a new type of semiconductor. If you have and are thinking of taking out a patent on your new idea, this book should make interesting reading. In simple, nonlegal language you learn who is entitled to receive a patent, what happens in the patent office, what to do with the issued patent, and about designs, copyrights and trademarks. All in all, a detailed study of how to protect your invention.

ACOUSTICS, by Joseph L. Hunter. Prentice-Hall, Inc., 70 Fifth Ave., New York 11, N. Y. 5 3/4 x 9 inches. 407 pages. \$8.50.

Modern hi-fi and public-address setups utilize principles of acoustics and electronics. This book discusses the theory and practice of acoustics. Problems are given, and many worked-out examples appear. The book presupposes knowledge of physics and math to calculus.

The first half discusses theory, including vibrating strings, oscillators and waves. Chapters on applications with speakers, microphones, recording and room acoustics as well as ultrasonics and underwater sound follow.

FREQUENCY MODULATION ENGINEERING, by Christopher E. Tibbs and G. G. Johnstone. John Wiley & Sons, 440 4th Ave., New York, N. Y. 435 pages, 5 1/2 x 8 1/2 inches, \$8.50.

This is a revised edition that speaks of receivers, transmitters, propagation, aerials and measurements. The author uses vectors, calculus and theory, but the practical side is not neglected. The book shows and describes modern commercial equipment and results of field tests. It is well illustrated with charts and circuit diagrams. References are made to both British and American works on the subject.—RF END

STAN-BURN

CATHODE RAY TUBE SPECIALS

ONE YEAR GUARANTEE

G.E.	Type	STAN BURN G.E.	Type	STAN BURN
\$15.80	12P4	\$10.00	2475	17P4 \$18.00
197.0	12PA4	13.95	37.00	19A4A 24.00
	12P4	11.50	28.35	20CP4A 18.95
20.35	12P4	15.00	33.60	20CP4B 21.95
20.75	12P4	13.75	36.00	21A4 21.15
33.75	12P4	14.50	29.75	21EP4A 20.15
33.75	12P4	18.50	34.85	21EP4B 23.25
33.75	12PA4	15.25	30.90	21EP4C 21.15
33.75	12P4	18.75	37.00	21MP4 26.25
23.50	12P4	15.75	29.75	21YP4 22.00
23.50	12PA4	18.75	34.85	21YP4A 25.00
31.50	12P4A	16.25	28.30	21ZP4 21.00
31.50	12P4	16.25	33.60	21ZP4B 24.00
28.40	12P4B	15.75	100.00	21AP4 56.00
30.75	12P4	20.51	48.40	21CP4A 38.00
33.90	12P4	21.50	50.00	21DP4A 39.00

*ALUMINIZED INQUIRE FOR ANY TUBE TYPE NOT LISTED. STAN-BURN CRT TUBES RCA LICENSED—MFD. BY LIC. COLN. All orders of 6 or more STAN-BURN CRTs subject to above discount. PRICES SUBJECT TO CHANGE WITHOUT NOTICE.

WHY PAY MORE?

Top brand nationally adv. merchandise in this and other Radio & TV mags. is yours at low, low cost. Send us your list. Give Mfr.'s name and Model No. of item. Write for '58 catalogs to Dept. RE-5 today.

GENERAL ELECTRIC RECEIVING TUBES

Brand New—1 Year Guarantee—Boxed

O24	.83	6K6GT	1.13	12SA7	1.45
1B3GT	.81	6SN7GT	1.13	12SK7	1.33
5U4GA	.95	6V6GT	1.03	12SQ7	1.18
6AG5	.25	6W4GT	1.15	35W4	.68
6AU6	.00	12AU7	1.18	125G7	.90
6BQ6A	.08	12BA6	.95	50C5	1.03
6BC6GA	.10	12BE6	1.03	50L6GT	1.15

ADDITIONAL 10% DISCOUNT IN LOTS OF 10 ASSORTED!
WRITE FOR COMPLETE PRICE LIST
SAVE UP TO \$100 A YEAR ON TV REPAIRS
 Amazing new book "How To Repair Your Own TV Set" gives you everything you have to know to spot TV trouble. Shows how to fix it "presto." Everything in easy-to-understand language and step-by-step diagrams. Latest up-to-date information on tube changes, antennas, the location charts, trouble shooting guide, etc., plus list of tube types and prices. Only \$1.00 plus 10c postage.

HI-FI DIAMOND NEEDLES—1 Yr. Guar.

Diamond needles reduce record wear and needle noise thus retaining full frequency response and tonal qualities of your records for a longer period of time.

SINGLE DIAMOND needle.....\$7.95
DIAMOND SAPP dual needle.....8.95
 Shipment PPD. (specify cartridge make)

RECORD CHANGERS

COLLARO TC-340 4 speed changer...\$36.75
COLLARO TC-440 4 speed changer... 40.67
COLLARO TC-540 4 speed changer... 45.57
GARRARD RC-88 4 speed changer... 53.41
GARRARD RC-98 4 speed changer... 66.15

FREE Wood mounting base, record wiping cloth and 45 RPM spindle with all orders for Collaro and Garrard changers, with this ad.

VM 4 SPEED HI-FI CHANGER—Model 1210 with Ronette or Astatic flip-over cartridge.....\$22.95
MONARCH Model UABU 4 SPEED AUTO. INTERMEDIATE CHANGER less cartridge.....\$19.95
WEBCOR 4 SPEED CHANGER with turn-over cartridge.....\$23.95
RONETTE (phono fluid) cartridge flip-over type.....\$2.98
SONOTONE cartridge, flip-over.....\$2.98
45 RPM SPINDLE for V.M. or Monarch.....\$1.98
WOOD MOUNTING BASE for V.M. or Monarch.....\$3.95
MOUNTING BOARD unfinished for V.M. or Monarch.....\$1.50

NEW GENERAL ELECTRIC HI-FI VARIABLE RELUCTANCE CARTRIDGE. Replaces discontinued R X050 type. Full range reproduction 20-20,000 cycles. Four gram tracking force for minimum record and stylus wear.
4G050—Dual Sapphire needles.....\$8.77
4G052—Diamond, Sapphire needles...\$18.99

KITS!

We stock the following manufacturers' complete line of kits—see reference pages.

EICO see pages 31-32
ARKAY see page 134
QUALITY see page 150
ELECTRO-VOICE
PRECISE Inside Back Cover
BOGEN see page 29
CABINART
GROMMET TECHMASTER
 All domestic orders will be shipped prepaid. Send us your list. Order by Mfr. and Model No. of item.

\$20 WORTH OF ELECTRONIC PARTS IN GRAB-BAG consisting of: certain sockets, coils, speaker transistors, resistors, etc. **ONLY \$3.98 (plus 50c postage)**

YOU NAME IT—WE HAVE IT

Complete line of T.V. & Radio receiving tubes, coils, transistors, antennas & accessories—No Minimum Order—**DEALER DISCOUNTS!** Thousands of satisfied Hi-Fi enthusiasts and dealers will vouch that **STAN-BURN GIVES THE BEST DEAL POSSIBLE!**
EXPORT INQUIRIES AND OFFERS INVITED.
 Terms: 2% with order, Balance C.O.D. All prices F.O.B. New York Warehouse.
 Write for our latest price list and Hi-Fi Catalog RE-5. All Prices Subject to Change Without Notice.

STAN-BURN

RADIO and ELECTRONICS CO.
 558 CONEY ISLAND AVE. • B'KLYN 18, N. Y.

WANT BACK ISSUES?

Back numbers of most issues of RADIO-ELECTRONICS are available upon request.

This year's issues: 35¢
Last year's issues: 40¢
Previous year: 45¢, etc.

All January Special TV issues: 50¢

RADIO-ELECTRONICS

154 W. 14 St. New York 11, N.Y.

A Theatre Organ for YOUR HOME!

The Artisan simplified step-by-step assembly system with all mechanical and wood parts fully assembled lets you build a magnificent 2 manual and full pedal organ at a saving of up to 50%! No special skill needed!

New 12" LP ALBUM
Only \$2.98

Hear the thrilling tones of the Artisan as played by prominent artists of the Theatre Organ. With explanatory notes.

PORTFOLIO of ORGAN FACTS jam-packed with vital information about organs. Only \$1.00

(LP Album and Portfolio—both for only \$3.49)

Order Direct from
ELECTRONIC ORGAN ARTS, INC.
 4878 EAGLE ROCK BLVD., DEPT. D-24, LOS ANGELES 41, CALIF.

SENCORE FILAMENT CHECKER

MODEL FC-4

Another Sencore Time-Saver

★ COMPLETELY NEW
 ★ MORE VERSATILE
 ★ LOWER COST

Quickly finds any open filament. Especially handy for servicing series filament TV sets and radios; only checker that checks all octals, loctals, 7 and 9 pin miniatures automatically.

Continuity and voltage tester—no switches, merely plug in test leads.

AT LEADING DISTRIBUTORS EVERYWHERE
 Mfg by **SENCORE SERVICE**
INSTRUMENTS CORP.
 171 OFFICIAL RD., ADDISON, ILL.

Only \$295
DEALER NET WITHOUT LEADS \$275

POPULAR SENCORE PRODUCTS

- Transistor Tester
- Leakage Checker
- Filament Tester
- Voltage Regulator
- Bias Supply

**2 YEARS
OF STUDY**
can give you these
ADVANTAGES

- Associate In Applied Science degree
- Preparation for a career as an engineering technician In

**ELECTRONICS
ELECTRICAL POWER
METALLURGY
COMPUTERS
AIR CONDITIONING**

- or you can continue without loss of credit to a 4-year Bachelor of Science degree In Mechanical or Electrical Engineering

at **MSOE**
in Milwaukee

THE
ENGINEERING
TECHNICIAN

FREE
folder answers your questions about the Engineering Technician, who he is, what he does, and how to become one.
SEND TODAY

**MILWAUKEE
SCHOOL OF ENGINEERING**
1025 N. Milwaukee St., Dept. RE-558,
Milwaukee, Wisconsin

Please send free folder
 "The Engineering Technician,"
 Booklet "Your Career in Engineering."
(please print)

I'm interested in _____
(name of course)

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

Eligible for vets. educational benefits
 yes no.

Discharge date _____

MS-94

SCHOOL DIRECTORY



**college grads get
ahead faster!**

... have higher incomes ... advance more rapidly. Grasp your chance for a better life. Share rewards awaiting college men. Important firms visit campus regularly to employ Tri-State College graduates. Start any quarter. Approved for Vets.

Bachelor of Science Degree in 27 months

Complete Radio Engineering courses (TV, UHF, FM, Electronics). Also Mechanical, Civil, Electrical, Chemical, Aeronautical Engineering in 36 months a B.S. in Business Administration (General Business, Accounting, Motor Transport Management Majors). Superior students faster. More professional class hours. Small classes. Enrollment limited. Beautiful campus. Well-equipped labs. Prep courses. Enter June, Sept., Jan., Mar. Earnest, capable students (whose time and budget require accelerated courses and modest costs) are invited to write Jean McCarthy, Director of Admissions for Catalog and "Your Career in Engineering and Commerce."



TRI-STATE COLLEGE

2458 College Avenue, Angola, Indiana

ELECTRONICS

**ENGINEERING DEGREE
IN 27 MONTHS**

Prepare for unlimited opportunities in electronics! B.S. degree in 27 months, mathematics, electrical engineering, TV, advanced radio theory and design. Modern labs. Low tuition, earn board. Also Aero., Chemical, Civil, Electrical, Mech., Engineering. B.S. degree in 36 mo. in Math., Chem., Physics. Also prep courses. G.I. appr. 20 biligs., dorms., gym. Enter June, Sept., Dec., March. Catalog. Keeping Pace With Progress.

INDIANA TECHNICAL COLLEGE

1558 E. Washington Blvd., Fort Wayne 2, Ind.

**CODE SENDING
RECEIVING SPEED**

Be a "key" man. Learn how to send and receive messages in International Morse code. Communicate with operators around the globe. Learn at home quickly through famous Candler System. Used by best operators. Qualify for Amateur or Commercial License. Write for FREE BOOK.

CANDLER SYSTEM CO.
Dpt. 3-E, Box 9226, Denver 20, Colo., USA

**GET INTO
ELECTRONICS**

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar and automation. Basic and advanced courses in theory and laboratory. Assoc. degree in electronics in 39 mos. B.S. in electronic engineering obtainable. ECPD accredited, G.I. approved. Graduates in all branches of electronics with major companies. Start September, February. Dorms, campus. High School graduate or equivalent. Catalog.

**VALPARAISO TECHNICAL
INSTITUTE**

Dept. C Valparaiso, Indiana



ENGINEERING DEGREES



E.E.
Option Electronics
or Power

**Earned through
HOME STUDY**

Residence Classes Also
Available

**PACIFIC INTERNATIONAL
UNIVERSITY**

(Operating as a College of
Engineering only at present)
5719-M, Santa Monica Blvd.,
Hollywood 38, Calif.

ELECTRONICS

**PREPARE FOR A GOOD JOB!
BROADCAST ENGINEER
RADIO SERVICING AUTOMATION**

TELEVISION SERVICING
BLACK & WHITE—COLOR

APPROVED FOR VETERANS AND SURVIVORS
OF VETERANS

BUILDING AIR CONDITIONED
SEND FOR FREE LITERATURE

BALTIMORE TECHNICAL INSTITUTE
1425 EUTAW PLACE, BALTIMORE 17, MD.

**ATTENTION: SERVICE TECHNICIANS' ASSOCIATIONS
CLUB MEMBERS
STUDENT GROUPS**

Special subscription rates to RADIO-ELECTRONICS are available to associations, clubs, schools, employe groups, etc. For information write—

G. Aliquo, RADIO-ELECTRONICS

154 W. 14 St.

New York 11, N.Y.

SUPER MAGNET SUPER SAVING!

Buy this Little Giant magnet, most powerful made, a sensational bargain! The low price of \$1.50 is less than 50% of what you'd pay for this magnet. Experimenters—hobbyists will find hundreds of uses for this powerful 1oz. Alnico permanent magnet. LIFTS 5 LBS. EASILY. Limited quantity. Order several today. Measures 1 3/4 x 1 1/2".
Item No. 86 \$1.50
Special Bargain (Shp. Chgs. 10c)



**250 POWER
TELESCOPE LENS KIT**

Make your own high powered 6 ft. telescope! Kit contains 2" diam., 75" focal length, ground and polished objective lens and necessary eye pieces. Magnifies 50x to 250x. Full instructions.

ITEM NO. 123
\$2.95
(Shp. Chgs. 10c)



AMAZING BLACK LIGHT

250-watt ultra-violet light source. Makes fluorescent articles glow in the dark. Fits any lamp socket. For experimenting, entertaining, unusual lighting effects.



Shp. wt. 2 lbs. ITEM NO. 87 **\$2.95**
(P. P. & Hdlg. Chgs. 35c)

**HUDSON SPECIALTIES CO., 160 W. 14th St.
Dept. RE-5-58, New York 7, N.Y.**

I am enclosing full remittance for items circled below. (Be sure to include shipping charges.)
87 33 86 123

Name _____ Please Print Clearly

Address _____

City _____ Zone _____ State _____

WATTHOUR METER

Leading makes—reconditioned. Ideal for trailer parks. 100-110 volts, 60 cycles. 2-wire A.C. 5 amp. Heavy metal case 8 1/2" x 6 1/4" x 5". Easy to install. Shp. wt. 14 lbs.



ITEM NO. 33 **\$4.50**
NOW ONLY
(P.P. & Hdlg. Chgs. \$1.25)

ADVERTISING INDEX

Radio-Electronics does not assume responsibility for any errors appearing in the index below.

Allied Radio Corp.....	9, 99-106
Amplifier Corporation of America.....	139
Arkay Inc.....	134
Atlas Sound Corp.....	126
Audio Devices Inc.....	136
B & K Manufacturing Co.....	119
Barjay Co.....	150
Barry Electronics Corp.....	150
Bell Telephone Labs.....	24
Benco Television Associates.....	91
Bogen (David).....	29
Bosch (Robert) Corp.....	127
British Industries Corp.....	124
Brooks Radio & Television Corp.....	131
CBS-Hytron.....	123
Capitol Radio Engineering Institute.....	15, 115
Carston Studios.....	142
Centrallab Div. of Globe-Union.....	16
Century Electronics Co. Inc.....	97
Chicago Standard Transformer Corp.....	120
Clarostat Manufacturing Co. Inc.....	30
Cleveland Institute of Radio Electronics.....	11
Columbia Wire & Supply Co.....	146
Coyne Electrical School.....	130, 137, 143
Cutick Electronics.....	142
Deleo Radio Div. of General Motors.....	129
DeRo Electronics.....	142
Deutschmann (Tobe) Corp.....	132, 133
DeVry Technical Institute.....	7
Dressner.....	139
Dynaco Inc.....	145
Ebex School.....	146
Edmund Scientific Co.....	122
E. I. S.....	114
Electro-Sonic Labs.....	124
Electro-Voice Inc.....	Inside Back Cover
Electronic Chemical Corp.....	143
Electronic Instrument Co. (EICO).....	31, 32

Electronic Measurement Corp.....	130
Electronic Organ Arts.....	147
Electronic Publishing Co.....	149
E-Z Hook Test Products Co.....	128
Filnor Products.....	122
Garfield (Oliver) Co.....	139
General Cement Manufacturing Co.....	22
General Electric Co.....	110-111
Gernsback Library Inc.....	141, 145
Grantham School of Electronics.....	17
Heald Engineering College.....	139
Heath Co.....	66-81
Hudson Specialties Co.....	148
Illinois Condenser Co.....	128
Indiana Technical College.....	120
Jackson Electrical Instrument Co.....	140
Jensen Industries.....	145
Karlson Associates Inc.....	139
Kuhn Electronic Products.....	150
Lafayette Radio.....	151-153
Lansing (James B.) Sound Inc.....	117
Lektron Inc.....	126-144
McNeal Electric & Equipment Co.....	127
Mallory (P. R.) & Co. Inc.....	86-87
Merit Coil & Transformer Co.....	142
Miller (J. W.) Co.....	144
Mosley Electronics Inc.....	146
Moss Electronic Distributing Co. Inc.....	92-93
National Radio Institute.....	3, 13
National Schools.....	5
North American Philips Co. Inc.....	Inside Front Cover
Northrop Aeronautical Institute.....	140

"TAB" Tubes Tested, Inspected, Boxed

New and used Gov't & Mfrs.
6 Mos. Guarantee! Surplus! No Rejects

Receiving	Types orders \$10 or more, ppd. 48 states
0A2	.8 6B16 .72 12AT6 .59 117Z3 .69
0B2	.7 6BK7 .99 12AT7 .89 117Z6 1.10
0C2	.8 6BL7 1.79 12AU6 .69 434A 2.00
0D3	.8 6BN6 1.08 12AU7 .69 2C51 2.65
0Z4	.5 6B06 1.19 12AX7 .79 2021 .68
1A7	1.0 6B27 1.25 12BA6 .69 3023 5.00
1B3	.7 6C15 .99 12BE7 .99 717A 5.51
1R5	.7 6C5 .69 12BD6 .59 4-125 29.00
154	.7 6CB6 .80 12BE6 .59 4-250 35.00
174	.7 6CG6 1.43 12BE7 .99 4340 7.00
1U4	.6 6M6 .59 12BH7 .99 4PR60 29.50
1U5	.6 6J5 .59 12BY7 1.00 4X150 19.00
1X2A	.6 6V6 .59 12CZ7 .99 4350 35.00
3Q4	.6 6K6 .59 12CU6 1.45 4X500 38.00
3Q5	.6 6K7 .79 12SA7 .69 58P1 3.98
354	.6 6L5 1.19 12CZ7 .99 58P4 1.98
3V4	.6 6E4 .59 12SH7 .89 35T 4.00
5R4	1.2 6SA7 .99 12SJ7 .75 100T 7.00
5U4	.6 6X4 .59 12X7 .99 35T 4.00
5V4	.6 6S7 1.19 12SQ7 .69 388A 1.00
5Y3	.5 6C7 .89 198G6 2.15 418A 14.00
6A84	.5 6C7 .79 197B .69 350T 43.00
6A87	.5 6C7 .69 25R6 1.39 850T 1.10
6AC7	.6 6J7 .69 25L6 .72 808 1.00
6AH6	.6 6SK7 .72 25W4 .77 809 3.00
6AL5	.6 6L7 .89 25Z5 .72 810 10.00
6AL5	.5 6N7 2/51 25Z6 .75 811 3.00
6AQ5	.6 6S07 .74 EL34 3.49 812 3.00
6AS7	3.49 6E7 .79 EL27 .69 813 9.00
6AT6	.4 6T8 .98 35L6 .59 814 2.45
6AU4	1.2 6U8 .98 35W4 .52 815 2.50
6AU6	1.6 6V5 1.39 35V6 .69 35B 6.00
6AX4	.6 6W6 .89 50A5 .69 866A 1.60
6BA6	1.6 6X4 .39 50B5 .69 866B 1.60
6BE6	1.6 6X5 .49 6C5 .69 5879 1.20
6BD6	.6 6Y6 .89 50L6 .69 5881 2.70
6BE6	1.2 7N7 .89 KT66 3.29 6550 3.90
6B86	1.2 7AL5 .59 75 .69 5842 11.00
6BM6	.7 12AQ5 .75 80 .59 5654 1.00

Write for Complete Tube List! Discounts to Qty. Buyers
TUBES WANTED! WE BUY! SELL & TRADE!

NEW GTD RADIO & T.V. RECTIFIERS

35MA 40¢ @ 6 for \$2;	65MA 45¢ @ 5 for \$2;
75MA 49¢ @ 5 for \$2;	100MA 59¢ @ 6 for \$3;
150MA 70¢ @ 5 for \$3;	250MA 79¢ @ 6 for \$4;
300MA 88¢ @ 5 for \$4;	350MA \$1.00 @ 6 for \$7;
400MA \$1.00 @ 5 for \$5;	500MA \$1.35 @ 4 for \$5;
650MA \$2.00 @ 5 for \$5;	100MA/260V \$1.25
@ 9/51;	100MA/156V 95¢ @ 300MA/156V

\$1.75, 3/5. Order \$10, Postpaid 48 States!

MFGS. & DISTRIBUTERS. WRITE FOR QTY. PRICES
NEW FULL WAVE BRIDGE RECTIFIER Hmt
Sealed with clip \$1.55 @ .7 for \$10

NEW "TEKSEL" SELENIUM BRIDGE RECTIFIERS. ONE YEAR GTD!

FULL WAVE BRIDGE • WRITE FOR CATALOG

CURR.	11VAC	36VAC	72VAC	144VAC
MSV	1.0DC	28VDC	56VDC	112VDC
1AMP	\$.30	\$ 2.00	\$ 4.00	\$ 9.45
2AMP	\$.15	\$ 3.00	\$ 6.25	\$ 12.30
3AMP	\$.10	\$ 4.00	\$ 16.75	\$ 30.00
6AMP	\$.15	\$ 8.00	\$ 17.50	\$ 36.15
10AMP	\$.10	\$ 12.15	\$ 26.30	\$ 48.90
15AMP	\$.10	\$ 19.00	\$ 40.00	\$ 75.00
24AMP	\$.00	\$ 29.45	\$ 57.50	\$ 108.45

HAMS NEW TRANSORIZED "TABPAK"

D.C. Power Supply!!! Kit or Assembled. Filtered. Small in size. Light Weight. 12 to 14VDC. (Low Idle Current.) Output 450 & tap @ 250 VDC at up to 150 ma/65 watts.

"TABPAK" Assembled TR39CB.....	\$35
"TABPAK" Kit TR39CK.....	\$30

KITS! "TAB" THE BEST KITS!

All Kits Contain Most Popular Values & Sizes	
Kit 35 Precision Resistors	Kit 35 Power Resistors
Kit 18 Switches	Kit 7 Mica Cond's
Kit 3 Transformer Transf.	Kit 6 Crystal Diodes
Kit 150 Carbon Resistors	Kit 8x25 ft. Hookup Wire
Kit 42 Panel Lamps	Kit 100 Ceramic Cond
Kit 12 Electrolytic Cond's	Kit 18 Rotary Switches
Kit 15 Volume Controls	Kit 6 Crystals & Holders
Kit 36 Tube Sockets	Kit 65 Inductors & Coils
Kit 50 Tubular Cond's	Kit 5 Microswitches
Kit 500 Lugs & Eyelets	Kit 10 Wheat Lamps
Kit 10 Xrnt. Mica Cond's	Kit 40 Insulators
Kit 5 Lbs. Suprise Kit	Kit 85 Insulated Resist.
Kit 10 Xrnt. Mica Cond's	Kit TV Knobs
Kit Enamiation Fluid	Kit Nylon Cement & Varnish
Kit Volume Control Fluid	Kit Varnish

BUY 10 KITS GET ONE FREE! EACH KIT 99¢

DC POWER FOR TRANSISTORS!

Transistor Filtered Power Supply Kit used to power transistor circuits, amplifiers etc. Delivers 12VDC at 2AMPS filtered less than 0.5 ripple or 28VDC at 1A. TPS-20 Kit \$18. TPS-2W assembled & wired \$24. 113VAC Supt Transformer & Full Wave Bridge Rectifier for 12VDC @ 2AMPS \$4.50. RECTRAN KIT RTK \$18. RT1W Assembled & Wired \$8.50. RT2K Kit for 18VDC at 6 AMPS \$7.00. RT2W Assembled & Wired \$14.75

FINEST HI-FI RECORDING TAPE

1200 ft. — 7" Reel — \$1.45 Lots of 3
Money Back Gfd.

Highest quality controlled plastic base tape made by new "Erin" process. Precision casted & slit. Gtd. Constant output. Price Free. Freq. 7 1/2 IPS 40-15K Hertz Wnd In. New 1st Quality "Mylar" 2400 Ft. — 7" Reel Ferro "Erin" Loss Process Recording tape...\$4.49, 3 for \$12

NEW VRII "GE" PHONO CARTRIDGES

Post paid 48 States!

4G061/1 or 4G063/78 DIAMOND	\$16
4G050/1 or 4G78 TRI-PLAY SAPPHIRE	\$8.59
4G052/1 or 4G78 TRI-PLAY DIAMOND & SAP.	\$18
4G053/1 or 4G78 TRI-PLAY DIAMONDS	\$26

DIAMOND PHONO-NEEDLES! Postpaid 48 States! REGISTERED ONE YR. GUARANTEED BY THE MFR! 25 LPT'S ONE DIAMOND \$7. TWO DIAMONDS \$4. DIAMOND & SAPPHIRE \$8. PLEASE SEND CARTRIDGE NAME & NUMBER

NEWEST IMPROVED HI-FI SPEAKERS!

With inbuilt Network Ticonal Anilco 5 Plus Magnet. 4 to 8 ohms C.

12" 3-WAY. 20 Watt/35-18,000 Cycles	\$38
MODEL F12H3X. Wgt. 10 lbs.	\$38
12" COAX. 20 Watt/45-12,000 Cys.	\$27
6" 2-WAY. 25 Watt Midrange 300-6000 Cys.	\$24

Electrostatic Tweeter & data \$3.25 @ .2/56

TERMS: Money Back Guarantee! Our 14th year. \$2 min order F.O.B. N.Y.C. Add shg. charges or for C.O.D. 25% dep. Prices shown subject to change.

1111 ING LIBERTY ST., N. Y. 6, N. Y.
PHONE: RECTOR 2-6245
Write for Catalog

all new edition
VOL. III. NO. 1

up-to-date component prices

PLUS

the quick easy way to figure service charges

Pure Rice's

OFFICIAL PRICING DIGEST

Flat rate and hourly service charges, based on and showing regional and national averages, plus up-to-date list or resale prices on over 63,000 components. Arranged alphabetically by manufacturers and products, numerically by part number. Compact, convenient size fits in tube caddy, toolbox or pocket. \$2.50 per copy from your distributor.

ELECTRONIC PUBLISHING COMPANY, INC.
180 N. WACKER DRIVE, CHICAGO 6, ILL.

NEW! IMPROVED!

SENCORE
TRC4
TRANSISTOR CHECKER

Another Sencore Time-Saver

America's newest, most popular test instruments

NOW CHECKS:

- ★ Transistors for opens, shorts, leakage and current gain. Includes new gain test on power transistors.
- ★ Crystal Diodes checks forward to reverse current ratio on all diodes.
- ★ Selenium Rectifiers checks forward and reverse currents.

Controls are accurately set for each transistor by referring to replaceable set-up chart on rear. Test leads or socket provides for fast hook-up. See your parts distributor.

ONLY \$17.95
Dealer Net
Cannot become obsolete. Approved by leading manufacturers.

Mfg by **SERVICE INSTRUMENTS CORP.**
171 OFFICIAL RD., ADDISON, ILL.

Cut out this ad now for further information

HQ for the 5 TOP NAMES in
TV & RECEIVING TYPE

TUBES

AT SENSIBLE PRICES!

Individually boxed. First quality only. Brand New

WRITE FOR LATEST TUBE CATALOG FREE!

Receiving, transmitting, special purpose tubes, diodes, transistors, etc.

- **GEIGER COUNTERS**—RCA . . . Brand New, jobber-boxed close out prices—WRITE for price—5 different models.
- **Choke-Hermet-sealed 11 Hys** @ 300MA—New—\$3.95. Specify L-102. (5" x 4" x 5")
- **Choke. Swinging to Match Above**—New—\$5.95. Specify L-102 swimming. (5" x 4" x 5")
- **Plate Xmftr**—115V/60 cy-sec: 700-0-700 @ 300 MA—Specify F107 (Tapped down also @ 600-0-600) \$11.25. (5" x 4" x 5")
- **Kotron Selenium Rectifier** 18/14/52 amps. Full-wave bridge type. Unused. Special price \$15.00.
- **Hallierafter's 3 1/2" Round Luminated (back) "S" Meter.** Basic 0-5MA movement. Reads up to 50 DR. over 80. New. Boxed—\$3.95.
- **Roller-Smith 2" Round Herm. Sealed 0-200 Microammeter.** Has -8 to +6 DB lower scale—New \$4.95.
- **Transistors**—Many types in stock @ bargain prices—What do you need?
- **Jennings UCSX Vacuum Variable**—20 to 675 micro. —10KV—\$36.95 w/mount & gears.
- **PH-522/AXT-2 Ham-TV Cameras w/1846 Tube**—Use for closed circuit uses—Unused—\$75.00. See May '57 "CQ" P. 28. (Two for \$150 Postpaid U.S.A.)
- **CL-2 Lamp**—New—\$10.00. See article Radio-Elect. Oct. '57—P. 93. (CL-2 Socket—\$1.00)
- **6 Volt Vibrapak**—New—\$9.95. (Reg. over \$30.00 net)
- **807-W Sylvania Jan Boxed 807W**—Interchangeable with 807 (Reg. \$12.85)—only \$1.25 each. 807 Jan Boxed @ \$1.10 each.
- **Prop-Pitch Motor**—55 lbs. uncrated. New or like new. \$28.00 each. F.O.B. N.Y.C. Via express or truck. (Add \$10.00 for Basic Conversion)
- **28 volt—10 amp Xmftr**—TRI: 115 vac/60 v. \$4.50.
- **Tool-Kit**—25 piece imported tool kit \$8.50.
- **New! 1 1/2" Square 0-1 Ma. Meters**—New \$3.95
- **BC 457A** (4-5.3 Mes.). \$5.95.
- **BC 458A** (5.3-7 Mes.). \$5.95.
- **Glas-Line—Non Metallic Guy-Line** @ \$2.80 per 100 feet. 100 foot roll \$17.34.
- **Bud 77" Panel Space Relay Racks.** Standard 19" Amateur width—17" deep. Deluxe grey-cerulac finish—Inlaid side panels—top and bottom—back door with double lock—brand new in original wrappings—complete with hardware—shipped knocked-down—F.O.B. N.Y. area. An excellent buy at \$35.00.
- **6 Foot Line Cords.** Extra-heavy zip-cord w/plug. 25c each5 for \$1.00
- **PTR Miniature Choke**—2 Hys. @ 130 Ma. 2 3/4" high, 1 1/2" wide, 1" deep. Hermet. Sealed. Brand new. Price: 40c ea. 10 for \$3.00. 100 for \$25.00
- **Little Gem Audio XMFR** 19,000 to 600 ohms—New—boxed49¢
- **RCA US/C3 Sniperscope**—New \$125.00
- **Barry's Green Sheet** (Jan. '58)25¢

2-COLOR TUBE CARTONS

Keeps your tube stock neat. New safety partition prevents tube breakage. Distinctive lithographed in glossy red and black. The most distinctive tube carton available today. Minimum quantity: 100 of any one size. Write for case lot prices. Packed 1000 to case. F.O.B. N.Y.C.

Size	For Tube	Per 100
Miniature	6AU6, etc.	\$1.00
GT	6SN7, etc.	1.25
Large GT	183, etc.	1.50
Large G	5U4G, etc.	2.00

WHITE GLOSSY BOXES

Completely blank. No printing or color. Otherwise same as above. Same high quality, same low prices. Specify "WHITE" when ordering. When color is not stated, 2 color cartons will be shipped.

Write for complete tube list. All shipments F.O.B. Our Warehouse. Rated firms (Dun & Brad. current F.3 or better) Net 10 Days. 10 day guar. price of mfd. only. All merchandise guaranteed.

HOW TO ORDER: Send full remittance and save C.O.D. collection fee—include sufficient money for postage.—We refund unused amount.—If you desire shipment C.O.D., include 25% deposit.—Send cash by registered mail. Subject to price variation and stock depletion. No C.O.D.'s on tube cartons.

OPEN MONDAY TO SATURDAY
We are near Prince St./BMT Station
Spring St./IRT Station

BARRY ELECTRONICS CORP.
512 Broadway, Dept. RE-4, N.Y. 12, N.Y.
Phone: WALKER 5-7000



ADVERTISING INDEX (Continued)

Opportunity Adlets	131	Supreme Publications	135
Paco Electronics Co. Inc.	14	Sylvania Electric Products Inc.	26-27
Perma-Power Co.	138	Tab	149
Philco Techrep Div.	154	Telco	22
Picture Tube Outlet	130	Television Tuner Service Co.	120
Progressive Edu-Kits Inc.	125	Tenna Manufacturing Co.	6
Pyramid Electric Co.	90	Tobe Deutschmann Corp.	132, 133
Quality Electronics	150	Triad Transformer Corp.	96
Quam-Nichols Co.	114	Trio Manufacturing Co.	112
Quietrole Co. Inc.	140	Tung-Sol Electric Co.	8
RCA Electron Tube Div	Back Cover	University Loudspeakers Inc.	121
RCA Institutes	23	Vaco Products Co.	142
Rad-Tel Tube Co.	134	Wen Products Inc.	12
Raytheon Manufacturing Co.	28	Xcelite Inc.	98
Rek-O-Kut Co.	122	Zenith Radio Corp.	18-19
Rider (John F.) Co.	95		
Rinehart Books Inc.	124, 127		
Rockbar Corp.	10		
Rohn Manufacturing Co.	89		
Sams (Howard W.) & Co.	25, 113, 143		
Schober Organ Co.	138		
Scott (Hermon Hosmer) Inc.	20		
Scott-Mitchell House Inc.	114		
Service Instruments Corp.	127, 128, 134, 144, 147, 149		
Sprayberry Academy of Radio-Television	21		
Stan-Burn Radio & Electronics	147		

SCHOOL DIRECTORY PAGE 148

Baltimore Technical Institute
Candler System Co.
Indiana Technical College
Milwaukee School of Engineering
Pacific International University
Tri-State College
Valparaiso Technical Institute

BRANCH ADVERTISING OFFICES: Chicago: 600 Waukegan Road, Glenview, Ill. (Glenview 4-6900). Los Angeles: Ralph W. Harker and Associates, 600 South New Hampshire, Tel. DUckirk 7-2328. San Francisco: Ralph W. Harker and Associates, 444 Market St. Tel. GARfield 1-2481.

FOREIGN AGENTS: Great Britain: Atlas Publishing and Distributing Co., Ltd., 18 Bride Lane, London E.C. 4. Australia: McGill's Agency, Melbourne. France: Brentano's, Paris 2e. Belgium: Agence et Messageries de la Presse, Brussels. Holland: Treflectron, Heemstede. Greece: International Book & News Agency, Athens. So. Africa: Central News Agency, Ltd., Johannesburg. Capetown, Natal: Universal Book Agency, Johannesburg. India: Broadway News Centre, Dadar, Bombay #14. Pakistan: Paradise Book Stall, Karachi 3.

BE QUALITY WISE . . . BUY QUAL-KITS!



HI-FI AMP. KIT

Complete 6 tube-10 watt amplifier Push-pull beam power output, built-in pre-amp, 5 position selector switch, 3 position record equalization, LP, RIAA, Eur. Response 1/2 db. 20-20,000 cps. Output 10 watts at less than 2% IM. Low noise level and harmonic distortion. **\$28.50**

Every kit complete with 28 page fully illustrated instruction and assembly manual. Cover and legs optional.

*Add 10 percent for new federal tax

QUALITY-ELECTRONICS

319 Church St. Dept. RE-5 New York 13, N. Y.



HI-FI AM-FM TUNER KIT

Advanced 7 tube circuit plus Rectifier for full sensitivity and selectivity. Distortion less than 1%. Sensitivity is 5 uv for 30 db quieting on FM. 25 uv AM. Armstrong FM Circuit with limiter. Foster-Seeley Discriminator. 20-20,000 cps response. Full AFC control—no drift. Easy assembly. **\$28.95***

Write for FREE catalog and name of nearest dealer carrying these remarkable units.

CRYSTAL CONTROLLED CONVERTERS

POLICE • FIRE • COMMERCIAL

- ✓ Precision—Stability
- ✓ Sensitivity
- ✓ Easy Installation

\$32.50

• A compact converter supplied with commercial tolerance crystals, self contained automatic noise limiter. Also models with switch. Ideal for mobile or home use.

TUNERS

Enjoy FM Programs While You Drive.

- FM BROADCAST
- 30-50 MC
- 108-176 MC

from **\$22.50**

WRITE FOR LITERATURE

KUHN ELECTRONICS

20 GLENWOOD CINCINNATI 17, OHIO

TEST CONDENSERS IN THE SET!

Test Selenium Rectifiers!
CHECK CAPACITORS UNDER WORKING CONDITIONS!



NOT A KIT • SATISFACTION GUARANTEED OR RETURN WITHIN TEN DAYS FOR REFUND

CAPACITEST 2,

with thousands already in use. Is an improved, compact checker that does a giant job to save you time and money. It tests Selenium Rectifiers! It will check condensers at 150 volts, which is approximately the working voltage in a radio or TV set. Meters will not give this type of check since the applied voltage is 20 volts or less. Avoid cut-backs by using CAPACITEST. Accurately, quickly shows open, shorted or intermittent capacitors and leaky electrolytics. Compact: 4" x 4" x 2" — Lightweight for bench or tool kit.

CAPACITEST

Quickly, Accurately Checks:

- PAPER, CERAMIC, MICA CAPACITORS
- ELECTROLYTICS
- SELENIUM RECTIFIERS
- CONTINUITY
- AC/DC VOLTAGES
- FLASHBULBS

\$9.95 postpaid dir. net complete, ready to operate

FREE each SET OF LEADS with each CAPACITEST 2 for limited time. Order direct from mfr. Send \$3 deposit with COD's. Save PP & COD fees. Send \$9.95 and we'll pay postage.


BAR JAY The Barjay Co. 145 West 40 Street New York 18, N.Y.

Lafayette Leaders In The Field of Transistors

Joins In The Tenth Anniversary Salute To The Transistor

NEW! 6 TRANSISTOR SUPERHET RECEIVER with LATEST NPN-PNP TRANSISTORS

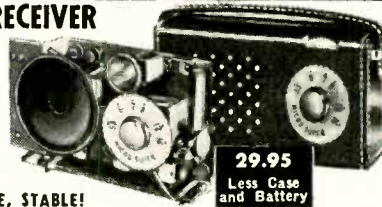- GE 2N188A AUDIO OUTPUT TRANSISTORS
- 100% SUBMINIATURE PARTS — NO COMPROMISES!
- CLASS B PUSH-PULL AMPLIFICATION—PLENTY OF POWER.
- FOR GROUP AND PRIVATE LISTENING
- LABORATORY DESIGNED — SENSITIVE, SELECTIVE, STABLE!



29.95
Less Case and Battery

Superb Performance! Incomparable Value!

Transistor-wise Lafayette proudly presents its newly revised 6 Transistor Superhet Receiver Kit KT-119A. This improved model uses the latest GE NPN-PNP Transistors in an ingeniously engineered, laboratory tested circuit providing superb performance and an amazing superior commercial quality. The circuit features a specially matched set of 3 IF transformers, Oscillator Coil, High-Q Loop, Class B Push-Pull Audio Amplification and optimum Transformer Coupling in audio and output stages. Has efficient 2 3/4" speaker for exemplary reproduction and earphone jack for private listening. Complete with all parts, transistors, pre-punched chassis, but less battery and leather case. New 28 page easy-to-follow step-by-step instruction book. Size 6 x 3 1/2 x 1 1/2. Shpg. wt., 3 lbs.

- KT-119A — Complete Kit—Less Case and battery.....Net 29.95
 BATTERY 9V BURGESS 2N6.....Net 1.30
 MS-339A — Sturdy attractive brown leather case with carrying strap for KT-119A. 6 x 3 1/2 x 1 1/2". Shpg. wt., 1 lb.....Net 2.95
 MS-366 — Sensitive matching earphone.....Net 1.29

"SUNFLEX" 2 TRANSISTOR REFLEX RADIO RECEIVER KIT

- FOR SOLAR OR FLASHLIGHT BATTERY OPERATION
- NPN-PNP CIRCUIT REFLEXED FOR 3 TRANSISTOR PERFORMANCE



An efficient miniature receiver kit for earphone operation. Works on 2 inexpensive penlight cells (3 volts) or in sunlight using solar batteries (not supplied). 1 mil current drain. Complete kit with detailed instructions. Size 4 3/4 x 3 5/8 x 1 1/8". Shpg. wt., 1 lb.
 KT-132—"SUNFLEX" KIT (less earphones).....Net 11.95
 MS-260—Super Power Dynamic Earphone.....Net 3.95



"HELIODYNE" SUBMINIATURE SOLAR SILICON BATTERY

- MOST EFFICIENT TYPE OF SUN BATTERY

Generates electrical energy from sunlight or other light source. Rated 3.2 volts at 2 millamps. Ideal for "Sunflex" receiver. 1-1/16 x 3/32".

- MS-240—"HELIODYNE" SILICON SOLAR BATTERY.....Net 6.65

4 TRANSISTOR TELEPHONE PICKUP AMPLIFIER KIT

- FOR GROUP LISTENING OF PHONE CONVERSATIONS



Extra-sensitive 4 transistor telephone pickup amplifier with "class B" push-pull output for efficient speaker operation. Merely requires pickup coil under or near phone. Also may be used as high gain amplifier for phono and mike.

- Easy-to-follow instructions. Size 4 1/2 x 4 1/4 x 4 1/4". Shpg. wt., 3 lbs.
 KT-131—Complete Kit Less Battery & Pickup Coil.....Net 17.95
 BATTERY RCA VS300 (9V).....Net 1.30
 MS-16—Telephone Pickup Coil.....Net 2.95

Dynamic Stereophonic Headphones

- True Binaural Reproduction • Frequency Response 40-16,000 cps. • Matched Magnetic and Crystal Transducers
- Exceptionally Lightweight • Six Types — Monaural and Binaural



BINAURAL



MONAURAL

Take your choice of six stethoscope type headsets. Binaural or Monaural! High impedance or low impedance! Magnetic or crystal! Only Lafayette offers a complete selection. Binaural units are equipped with two separate and individual transducers and cord sets for true dual channel reproduction. Long the most widely accepted means of stereophonic listening. Both monaural and binaural units are extremely sensitive to insure the desired response. Sound is carried through crystal clear plastic tubes (lined with removable, plastic earpieces. Ingenious hinge device permits adjustment to any desired spacing. Less than 2 ozs. total weight for the utmost in listening comfort. Binaural sets may be used for monaural listening. Shpg. wt., 6 ozs.

- | | | | |
|---|------|---|------|
| BINAURAL MAGNETIC HEADPHONES | | MONAURAL-MAGNETIC HEADPHONES | |
| MS-431 Binaural-Magnetic-6 ohms impedance..... | 2.65 | MS-429 Monaural-Magnetic-6 ohms impedance..... | 1.75 |
| MS-432 Binaural-Magnetic-5000 ohms impedance..... | 2.95 | MS-430 Monaural-Magnetic-5000 ohms impedance..... | 1.95 |
| MS-433 Binaural-Crystal-100,000 ohms impedance..... | 2.25 | MS-369 Monaural-Crystal-100,000 ohms impedance..... | 1.65 |

HIGH SENSITIVITY 20,000 OHM PER VOLT DC 10,000 OHM PER VOLT AC MULTITESTER

LOOK AT THESE FULL SCALE RANGES!



D.C. Volts: 0-6; 0-30; 0-120; 0-600; 0-1200; 0-6000 Volts—A.C. Volts: 0-6; 0-30; 0-120; 0-600; 0-1200 Volts—Resistance: 0-10K; 0-100K; 0-1 Meg; 0-10 Megohms—D.C. Current: 0.60 Microamp; 0-6; 0-60; 0-600 Milliamps—Decibel: -20 to +17 db (0db=0.774V)—Capacity: .0001-.01; 005-.15 mfd—Inductance: 20-2000 millihenry—Output Ranges: 0-6; 0-30; 0-120; 0-600; 0-1200 Volts.

The new Lafayette high sensitivity Multitester is a complete instrument (not a kit). In addition to its unusual sensitivity of 20,000 OHMS PER VOLT ON D.C. AND 10,000 OHMS PER VOLT ON A.C., and the extraordinary number and scope of its ranges, it is packed with features that would make it cost at least twice as much if made in this country. Uses 1% precision resistors, silver contacts on selector switch, 35 ua 3" meter. Dependable, rugged and accurate. Even the test leads are heavy duty with high voltage insulation. Voltage source required for low capacity range is 120V for high range capacity and inductance scale is 6V A.C. Attractive plastic front with metal bottom. Size 6 1/4" x 4 1/4" x 2 1/2". Complete with batteries and leads. Shipping weight 4 1/2 lbs.

- RW-30A In lots of 3. Each 19.25 Singly. Each 19.95

4 AND 6 TRANSISTOR SUPERHET KITS POCKET AND HOME RADIO FOR SPEAKER AND EARPHONE OPERATION



Completely self-contained, pocket size portable set which operates a miniature earpiece so only you can hear. The circuit uses 4 transistors (2 high frequency and 2 audio) plus a germanium diode, 2 IF stages and built-in high gain ferrite core and antenna. The result is a sensitive, stable and selective receiver covering the entire broadcast band. It requires no outside antenna or ground connection. The kit is supplied complete with transistors and all parts, including battery, and drilled and punched chassis. Pictorial and circuit diagrams are included with simple, easy-to-follow instructions. (Note: Earpiece and carrying case are not supplied.)


- KT-94 — Complete Kit. Shpg. wt., 2 lbs.....Net 19.95
 MS-311—Leather Carrying Case.....Net 1.95
 MS-260—Super Power Dynamic Earpiece.....Net 3.95

2-TRANSISTOR PUSH-PULL OUTPUT KIT WITH SPEAKER SELF-CONTAINED IN BEAUTIFUL PLASTIC CASE

Converts 4-Transistor Kit KT-91 into a 6-transistor home radio with speaker. Transistorized push-pull audio stage plugs into 4-transistor kit, suitable for group listening. Performance equal or superior to commercially wired sets selling at much higher prices. Kit includes 2 transistors, 2 transformers, 2 1/2" P31 speaker, pre-punched chassis, speaker case (holds all components), battery, hardware, instructions and diagrams.
 KT-96—Shpg. wt., 1 lb.....Net 11.50

3 TRANSISTOR SUPERHET POCKET RADIO KIT

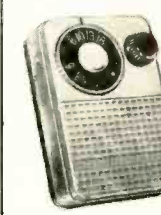- A TRUE POCKET SUPERHET RECEIVER
- NO EXTERNAL ANTENNA
- NO EXTERNAL GROUND



A remarkable sensitive, super-selective pocket superhet receiver with astonishing performance over the complete broadcast band. Uses 2 high-frequency and one audio transistor plus efficient diode detector and features 2 specially matched IF transformers for maximum power transfer. The components are housed in a professional looking beige plastic case. The receiver's appearance is enhanced by attractive maroon and silver station dial. Sensitive built-in ferrite antenna eliminates need for external antenna. A designer's dream in a true pocket superhet receiver! Complete with all parts, transistors battery, case, dial and easy to follow step-by-step instructions. 4 1/2" x 2 1/2" x 1-1/16". Shpg. wt., 1 lb.

- KT-116 — Complete Kit, less earphone.....Net 16.95
 MS-260—Super Power Dynamic Earphone.....Net 3.95

Lafayette Radio 165-08 Liberty Ave.
 JAMAICA 33; N. Y.

NEW YORK, N.Y. 100 6th Ave. RECTOR 2-8600	BOSTON, Mass. 110 Federal St. HUBBARD 2-7850	BRONX, N.Y. 542 E. Fordham Rd. FORDHAM 8-813	NEWARK, N.J. 24 Central Ave. MARKET 2-1661	PLAINFIELD, N.J. 139 W. 2nd St. PLAINFIELD 6-4718
---	--	--	--	---

FREE LAFAYETTE CATALOG

A Must For Every Hi-Fi Enthusiast

New! Years Ahead!



NEW 180 PAGE ELECTRONIC CATALOG FEATURING THE BEST BUYS IN THE BUSINESS

The newest and largest assortment of Electronic, Radio and TV parts, Hi-Fi and Public Address Components and systems, Test Equipment, tubes, Transistor Kits and miniaturized components for transistor circuitry, Ham Equipment, Builders Kits, Tools, Books, Microscopes, Binoculars, Telescopes, Cameras, and Drafting Equipment.—ALL AT LOWEST PRICES—Catering to the economy minded dealer, serviceman, engineer, technician, experimenter and hobbyist. **CRAMMED FULL OF MONEY SAVING BUYS. SEND FOR YOUR FREE COPY TODAY.**

LAFAYETTE STEREO TUNER KIT

THE MOST FLEXIBLE TUNER EVER DESIGNED

- 11 Tubes + Tuning Eye + Selenium Rectifier
- 12 Tuned Circuits
- Dual Double-Tuned Transformer Coupled Limiters
- Separately Tuned FM and AM Sections
- Dual Cathode Follower Output
- Armstrong Circuit with FM/ AFC and AFC Defeat
- Multiflex Output for New Stereo FM

More than a year of research, planning and engineering went into the making of the Lafayette Stereo Tuner. Its unique flexibility permits the reception of binaural broadcasting (simultaneous transmission on both FM and AM), the independent operation of both the FM and AM sections at the same time, and the ordinary reception of either FM or AM. The AM and FM sections are separately tuned, each with a separate 3-gang tuning condenser, separate flywheel tuning and separate volume control for proper balancing when used for binaural programs. Simplified accurate knife-edge tuning is provided by magic eye which operates independently on FM and AM. Automatic frequency control "locks in" FM signal permanently. Aside from its unique flexibility, this is, above all else, a quality high-fidelity tuner incorporating features found exclusively in the highest priced tuners.

FM specifications include grounded-grid triode low noise front end with triode mixer, double-tuned dual limiters with Foster-Seeley discriminator, less than 1% harmonic distortion, frequency response 20-20,000 cps \pm 1/2 db, full 200 kc bandwidth and sensitivity of 2 microvolts for 30 db quieting with full limiting at one microvolt. AM specifications include 3 stages of AVC, 10 kc whistle filter, built-in ferrite loop antenna, less than 1% harmonic distortion, sensitivity of 5 microvolts, 8 kc bandwidth and frequency response 20-5000 cps \pm 3 db.

The 5 controls of the KT-500 are FM Volume, AM Volume, FM Tuning, AM Tuning and 5-position Function Selector Switch. Tastefully styled with gold-brass escutcheon having dark maroon background plus matching maroon knobs with gold inserts. The Lafayette Stereo Tuner was designed with the builder in mind. Two separate printed circuit boards make construction and wiring simple, even for such a complex unit. Complete kit includes all parts and metal cover, a step-by-step instruction manual, schematic and pictorial diagrams. Size is 13 3/4" W x 10 3/8" D x 4 1/2" H. Shpg. wt., 18 lbs.

The new Lafayette Model KT-500 Stereo FM-AM Tuner is a companion piece to the Models KT-300 Audio Control Center Kit and KT-400 70-watt Basic Amplifier Kit and the "Triumvirate" of these 3 units form the heart of a top quality stereo hi-fi system.

KT-500.....Net **74.50**

LAFAYETTE MASTER AUDIO CONTROL CENTER

with BINAURAL CHANNEL AND DUAL VOLUME CONTROL.

- Self-Powered
- DC On All Filaments
- 24 Positions of Equalization
- Tape Head Input, High Impedance
- Dual Cathode Follower Output Stages

This is not only the finest hi-fi preamp characterized by unmatched features, but it has been functionally designed to keep pace with the conversion of your present hi-fi system to binaural (Stereo) sound. Incorporates an extra channel and dual volume control for binaural reproduction. Features include DC on all tube filaments, negative feedback in every stage, dual cathode follower output stages and latest printed circuit construction. Less than 0.09% IM distortion and less than 0.07 harmonic distortion at 1V. Hum and noise level better than 80 db below 3V. Uniformly flat frequency response over entire audible spectrum. 7 inputs for every type of phono, tuner or tape. Tasteful styling, brilliantly executed. Size 12 3/4" x 9 1/2" x 3 3/4". Shpg. wt., 10 1/2 lbs.

KT-300—Lafayette Master Audio Control Kit Complete with cage and detailed assembly instructions. Net **39.50**

LT-30—Same as above completely wired and tested with cage and instruction manual.

Net **59.50**

DELUXE 70 WATT BASIC AMPLIFIER

- Conservatively Rated At 70 Watts
 - Inverse Feedback
 - Variable Damping
 - Metered Balance And Bias Adjust Controls
 - Available In Kit and Wired Form
- Here's ultra-stability in a 70 watt basic power amplifier employing highest quality components conservatively rated to insure performance and long life. Features matched pair KT 88's and wire range linear Chicago output transformer, variable damping control, meter for bias and balance and gold finish chassis. Frequency response 10-100,000 cps \pm 1db. Hum and noise 90 db below full output. IM distortion less than 1 1/2% at 70 watts, less than 0.3% below 30 watts. Harmonic distortion less than 2% at 70 watts from 20 to 20,000 cps \pm 1 db. Output impedance 4, 8 and 16 ohms. Handsome decorative cage perforated for proper ventilation. Size 14 1/2" x 10" x 7 3/8" including cage and knobs. Shpg. wt., 40 lbs.

KT-400—Lafayette 70 watt Deluxe Basic Amplifier Kit complete with cage and detailed assembly instructions. Net **69.50**

LA-70—Same as above completely wired and tested with cage and instruction manual.

Net **94.50**



KT-500 IN KIT FORM **74.50**

ONLY 7.45 DOWN 7.00 MONTHLY



KT-300 IN KIT FORM **39.50**

ONLY 6.95 DOWN 7.00 MONTHLY

NEW! LAFAYETTE SCOOP!

DUAL WIDE-ANGLE TWEETER Daly **5.95**

Modernize Your Hi-Fi System

Modernize your high fidelity listening by adding this wide-angle dual-tweeter to extend treble range in a 2-way or 3-way speaker system. Mounts directly on any 12" speaker and converts it to a coaxial type. Response 2500 to 16,000 cps. Recommended crossover 2500 to 4000 cps. Heavy magnets for high efficiency. Dispersion angle approx. 125° horizontally. Impedance 16 ohms (2-8 ohm units in series). Will handle up to 20 watts program in 2 or 3-way systems. Incorporates specially designed chrome-plated steel bracket of rigid construction to prevent resonances. Measures 12" L x 2" D x 2 7/8" H overall. Shpg. wt. 2 lbs.

SK-100 Dual Tweeter Net **5.95**

Lafayette Radio DEPT JE P. O. BOX 511 JAMAICA 31, N. Y.

Send FREE LAFAYETTE Catalog 305

Name **CUT OUT AND MAIL TODAY**

Address

City..... Zone.... State.....

LAFAYETTE PROFESSIONAL TURNTABLE

with AUTHENTIC HYSTERESIS SYNCHRONOUS MOTOR

Value ~~29.50~~ Only **64.50**
SAVE OVER 50%

PROFESSIONAL TURNTABLE WITH HYSTERESIS-SYNCHRONOUS MOTOR

The Lafayette Model PK-225 is a true hysteresis-synchronous motor and is free from speed variations due to fluctuations in line voltage, load and temperature. It is the smoothest type known, completely free from "cogging" (the minute variations of speed which show up as wow and flutter)

ONLY LAFAYETTE'S HYSTERESIS-SYNCHRONOUS MOTOR, in its price class, is made to extremely fine tolerances (on the order of .00001 inches)! Only Lafayette's motor has 16 cores; a high permeability rotor magnet, ball thrust bearings, oilite sleeve bearings plus felt oil reservoir, cooling fins as an integral part of the rotor and a hollow rotor core for maximum efficiency and minimum heat. Only Lafayette's motor can be oiled from above, without disassembly, through a unique oil feed system. Only Lafayette's motor has a self-aligning armature.

Here's THE turntable—the last word in professional high-fidelity performance! A fine precision instrument in every sense. Just look at some of these **OUTSTANDING FEATURES**:- **WOW AND FLUTTER**: Less than 0.2% • **TURN-TABLE**: Heavy, diecast aluminum. Lathe-turned for perfect balance and concentricity. 12" diameter—weighs approx. 4 lbs. and provides amazingly constant speed; the extra-heavy rim acts just like a flywheel to prevent speed variations • **TRUE-HYSTERESIS-SYNCHRONOUS MOTOR**: For smooth, low-noise, wow- and flutter-free operation • **RUMBLE AND NOISE**: 50db below average recorded level • **INTEGRATED SPEED CONTROL**: For all 3 speeds—78, 45 and 33½ rpm • **2 OVERSIZE, HEAVY DUTY IDLERS**: Precision-ground; provide positive constant-speed rim drive • **SINGLE BALL THRUST BEARING**: Turntable rides smoothly over ball bearing floating on thin film of oil • **FREE FLOATING, SHOCK-MOUNTED MOTOR** • **RUBBER CUSHION SHOCKMOUNTS** • **AUTOMATIC IDLER DISENGAGEMENT** • **CORK AND RUBBER MAT** • **STAINLESS STEEL PRECISION SPINDLE** • **POWER REQUIREMENTS**: For 105-130 volts, 60 cps AC; draws 16 V.A. • **ACCESSORIES SUPPLIED**: 45 RPM adapter, Strobe disc • **SIZE**: 2½" above and 4" below motor board; 14¾" deep x 12¼" wide • **SHIPPING WEIGHT**: 16 lbs.

LAFAYETTE MODEL PK-225Net **64.50**
Deluxe Woodbase for PK-225 and 12" Tone Arm (Specify Finish). Shpg. wt., 13 lbs.....Net **14.95**
Deluxe Woodbase for PK-225 and 16" Tone Arm (Specify Finish). Shpg. wt., 15 lbs.....Net **15.95**

LAFAYETTE
MODEL
PK-225



SPECIAL MONEY-SAVER COMBINATION

PK-225 Turntable, PK-90 12" Tone Arm, New GE VMI Series Triple-Play Cartridge Model 4G-052 with Genuine GE Diamond and Sapphire Styl. **SPECIAL!**Net **81.50**

VISCIOUS DAMPED TRANSCRIPTION TONE ARMS



PK-90—11.95

VISCIOUS
DAMPED
ARM


LICENSED
UNDER CBS
U. S. PATENT
NO. 2676806



PK-170—17.95

VISCIOUS
DAMPED
ARM

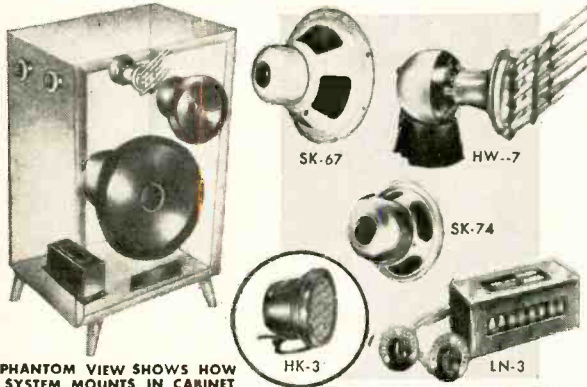3 WAY SYSTEM WITH 15" WOOFER . 8" MID-RANGE SPEAKER . . HORN TWEETER . . CROSSOVER NETWORK



PHANTOM VIEW SHOWS HOW SYSTEM MOUNTS IN CABINET

- 15-INCH WOOFER WITH 31.5 OZ. MAGNETIC (SK-67)
- 8-INCH MID-RANGE SPEAKER (SK-74)
- NEW HIGH FREQUENCY ACOUSTICAL LENS TWEETER (HW-7)
- 3-WAY CROSSOVER NETWORK (LN-3)

Lafayette presents this outstanding 3-way speaker system designed for the high fidelity enthusiast who desires performance formerly possible in multi-speaker systems costing many times this price. You won't believe your ears when you hear the superb reproduction throughout the entire audio spectrum. The SK-67 15" woofer provides phenomenal bass response, the SK-74 8" speaker delivers full bodied, mid-range frequencies, and the HW-7 high frequency acoustical lens tweeter faithfully reproduces the highest audible frequencies. Crossover points at 350 and 700 cycles are provided by the LN-3 3-way inductance-capacitance network with continuously variable presence and brilliance controls that adjust tone balance to personal taste. Shpg. wt., 25 lbs.

SY-93. Complete System as listed aboveNet **55.50**

2 WAY SPEAKER SYSTEM 40-16,000 CYCLES

- 25 WATT WOOFER
- CROSSOVER NETWORK
- IMPORTED HI-FI TWEETER
- LEVEL BRILLIANCE CONTROL

This 2-way speaker system is another excellent buy for the moderate purse. It is basically the same as the SY-85 system described at the top of the page, but incorporates the deluxe SK-68 speaker with 21.5 oz. Alnico V magnet. This results in more efficient reproduction and extension of the lower register. Complete system includes the SK-68 12" 25 watt woofer, HK-3 zone type tweeter and LN-2 crossover network with level-brilliance control. Range of system 40-16,000 cycles. Shpg. wt., 18 lbs.

SY-87—Complete SystemNet **27.50**

NEW! POWER MEGAPHONE... Portable Sound Broadcaster

- Uses 8 Flashlight Cells
- Completely Self-Contained
- Weighs only 6½ lbs. with Batteries
- High Efficiency Horn Projects Sound 1000 Ft.
- Shoulder Strap for Portability and Ease of Use
- Microphone Detachable On 10-Foot Cord
- For Construction, Auctions, Carnivals, Fire & Police Use
- Also Ideal for Marine, Railroad, Civil Defense, Sporting Events

A power megaphone with many unusual features and many applications. Basically a highly efficient sound projector horn with a built-in microphone, capable of amplifying and projecting the voice with a range of 1000 feet. The microphone is a telephone-type element, easily replaceable, and may be detached and extended up to 10 feet from the horn. The reflex-type horn is extremely light-weight, rubber-rimmed, of strong, sturdy spun aluminum construction with 2¾" air column and is supplied with a strap for carrying or placing on the shoulder. A press-to-talk switch on the microphone provides for economy of power use—power is used only when actually talking. No warm-up time required—amplification is instantaneous. A patented non-linear current limiting device restricts current flow to safe levels for longest battery life. Uses 8 size "D" flashlight cells in series with an approximate life of about 10 hrs. of use. Battery housing serves as base for entire assembly. Battery compartment opens easily by means of 2 thumbscrews for battery replacement. Size 17" long overall; horn mouth is 12" diam. Shpg. wt., 8 lbs. less batteries.

PA-12—Power Megaphone, Less batteries.....Net **29.50**

BATTERIES FOR ABOVE—Burgess No. 2 or RCA

VS036—8 RequiredNet each **.13**

Reg. Value ~~69.50~~
ONLY **29.50**



Self-Contained—
Only 6½ lbs.
THROWS VOICE
1000 FT.

SHOULDER
STRAP &
DETACHABLE
MIKE
JUST AIM
& TALK



Lafayette Radio

165-08 Liberty Ave.
JAMAICA 33; N. Y.

INCLUDE POSTAGE WITH ORDER

NEW YORK, N.Y. 100 6th Ave. REctor 2-8600	BOSTON, Mass. 110 Federal St. HUBbard 2-7850	BROOKLYN, N.Y. 542 E. Fordham Rd. FORDham 7-8813	NEWARK, N.J. 24 Central Ave. MARket 2-1661	PLAINFIELD, N.J. 139 W. 2nd St. PLAINfield 6-4718
---	--	--	--	---

LEARN SEMICONDUCTOR ELECTRONICS AT HOME

...prepare now for advancement in this growing, new technology!

GAIN VALUABLE KNOWLEDGE FOR A PROFITABLE CAREER IN ELECTRONICS WITH THIS SPECIALIZED CORRESPONDENCE COURSE ON TRANSISTORS THAT HAS BEEN SPECIALLY DEVELOPED BY THE PHILCO TECHNOLOGICAL CENTER



Learn by doing with complete training kit

Get practical experience, learn faster and easier. Conduct 18 experiments with training kit included. Build Amplifiers, Oscillators, Multivibrators, Pulse Circuits, AM Receivers, as well as Computer Circuits such as "AND," "OR" and "CARRY."



Learn theory, construction and all important applications of all major types of transistors—Junction, Point Contact, Surface Barrier and many other related types—with this advanced Correspondence Course specially developed for engineers and experienced technicians now engaged in Design, Installation, Maintenance or Manufacture of electronics equipment or systems.

ELECTRONICS SPECIALISTS ARE URGENTLY NEEDED. Even during hard times and periods of high unemployment such as we are going through now, the newspapers are full of help-wanted ads for electronics technicians and engineers. And the pay is good, too! Of course, the more you know the better your chances for better jobs and bigger pay.

GET INTO THE SEMICONDUCTOR FIELD NOW. This field is growing fast. Industry can't find enough experienced technicians and engineers. Career opportunities are unlimited. Now's the time to get in on the ground floor.

THE PHILCO TECHNOLOGICAL CENTER IS A DEPARTMENT OF PHILCO TECHREP DIVISION, THE WORLD'S LEADING ELECTRONICS FIELD ENGINEERING ORGANIZATION. You benefit from Philco's 17 years of experience in providing electronics training and technical assistance to the Armed Forces and industry all over the world ... and from advanced training methods developed through these many years. You learn from proven courses that have been developed by experienced electronics training specialists to give you a complete and practical knowledge of semiconductors.

Mail Coupon Today for Detailed Information of Course Level and Materials!

(NO OBLIGATION)

Prepare for a Career in Field Engineering with these Philco Correspondence Courses

BASIC RADAR—an introductory course.

ADVANCED RADAR—Comprehensive course on radar equipment and systems.

BASIC ANALOG COMPUTERS—an introductory course.

ADVANCED ANALOG COMPUTERS—Comprehensive coverage of systems and equipment.

PHILCO TECHNOLOGICAL CENTER
22nd and Lehigh Ave., Philadelphia 32, Pa.

TC-11

Please send free booklet and course information on subjects checked below:

- | | |
|---|--|
| <input type="checkbox"/> SEMICONDUCTORS
Transistor Principles
and Practices | <input type="checkbox"/> ADVANCED RADAR |
| <input type="checkbox"/> BASIC RADAR | <input type="checkbox"/> BASIC ANALOG COMPUTERS |
| | <input type="checkbox"/> ADVANCED ANALOG COMPUTERS |

NAME _____

ADDRESS _____

CITY _____ STATE _____

**PHILCO
TECHNOLOGICAL
CENTER**

22nd and Lehigh Ave.
Philadelphia 32, Pa.



CONVENTIONAL-
REENTRANT-HORN
SOUND COVERAGE




CDP SOUND COVERAGE

Reach More People More Clearly with *Electro-Voice* P. A. Speakers and Microphones

Electro-Voice CDP® P. A. Speakers afford dispersion through a solid 120° angle *without pin-pointing of sound*. Dispersion is all-important; power alone is never enough. CDP gives you both in two coaxially-mounted diffraction horns working from opposite sides of a single diaphragm.

CDP . . . 120° Angle Sound Dispersion • Greater Coverage with Fewer Units . . . Higher Intelligibility • 2½ Octaves More Musical Range • Peak-Free Response • Blast-Proof —Weather Proof

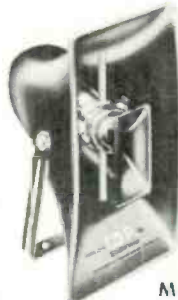Model 848 CDP handles the biggest jobs. 25 watts, 16 ohms. Response: 175-10,000 cps, crossover at 1000 cps. Sensitivity rating, 52 db. Size, 10½" x 20½" x 20". Wt., 12 lbs. List, \$75.




Model 848 CDP



Model 847 CDP

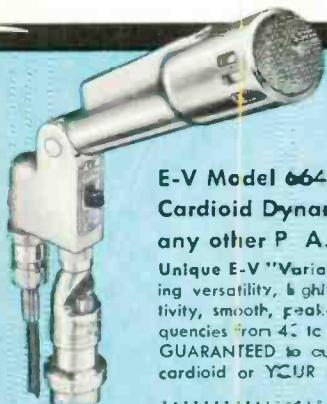Model 847 CDP for smaller areas. 12 watts, 16 ohms. Response: 250-10,000 cps, crossover at 1500 cps. Sensitivity rating, 51 db. Size, 11¾" x 7¾" x 10½". Wt., 6½ lbs. List, \$46.50.



**E-V Model 664 High-Fidelity
Cardioid Dynamic Outperforms
any other P. A. Cardioid**

Unique E-V "Variable D"® gives you amazing versatility, highly directional sound selectivity, smooth, peak-free response at all frequencies from 40 to 15,000 cps, no boominess. GUARANTEED to outperform any other P. A. cardioid or **YOUR MONEY BACK!** List price, \$85.00.



Model 423 dynamic omnidirectional microphone. 60-12,000 cps response range. List, \$57.



Model 626 slim dynamic omnidirectional microphone. 60-15,000 cps response range. List, \$72.50.



Model 927 crystal omnidirectional microphone. 60-8,000 cps response range. List \$22.50.

Send for Bulletin 195-W35. It's a 24-page handbook with a lot of answers on public address problems. Cat. No. 126-W85 will give you complete details on Electro-Voice P. A. and general-purpose microphones. Bulletin No. 246-W85, "The ABC's of Microphones," is packed with facts about the different types of microphones and how they work. Send for them today!



ELECTRO-VOICE, INC. BUCHANAN MICH.
Export: 13 East 40th Street, New York
16, U.S.A. Cables ARLAB

straight from the shoulder talk...

A TV Picture Tube Warranty is only as good as the manufacturer who issues it...

You can rely on the
**Picture Tube
Warranty**
of RCA



The manufacturer's warranty is for your protection. An RCA 12-month warranty card is assurance that your replacement picture tube is a genuine RCA Silverama—and that the reputation and integrity of RCA stand behind it. It's well worth while to insist on an RCA Silverama, the same advanced tube used in many of the new '58 TV sets. Often, it will even produce a picture more brilliant, sharper, clearer than your set gave when new! So, if your picture tube should need replacing, be sure you get what you pay for, the best picture tube made—RCA Silverama. After your service dealer installs it, ask him to complete your copy of the warranty card. One comes with every genuine RCA Silverama Picture Tube.

Super-Aluminized  Daylight Clear
RCA Silverama
PICTURE TUBES
RCA Electron Tube Division, Harrison, N. J.

“Just as good”
isn't good
enough for
your TV!



Let's face it! Nothing lasts forever. When you have to pay out good money for a replacement Picture Tube, you're entitled to the best that modern electronics can produce—that's an RCA SILVERAMA. It stands to reason that RCA, with its great laboratories, facilities, and “know-how” — produces the finest Picture Tubes money can buy. So, don't let “just as good” tempt you. Remember, RCA Silverama Picture Tubes cost no more than other brand-name aluminized tubes ... they are warranted for one full year, too.

Super-Aluminized  Daylight Clear
RCA Silverama
PICTURE TUBES
RCA Electron Tube Division, Harrison, N. J.

...that makes it easy
for you to sell the #1
picture tube... **RCA Silverama**®

Messages like these appear regularly in TV Guide and other publications, telling millions of TV viewers (many of them your customers) the facts about their all-important picture tube.



RADIO CORPORATION OF AMERICA
Electron Tube Division
Harrison, N. J.