

MARCH

Radio-Electronics


TELEVISION • SERVICING • HIGH FIDELITY

HUGO GERNSBACK, Editor

Tunnel Diode CW Transmitter

▶ **SERVICING PHOTOFASH EQUIPMENT**

Wideband AC Voltmeter

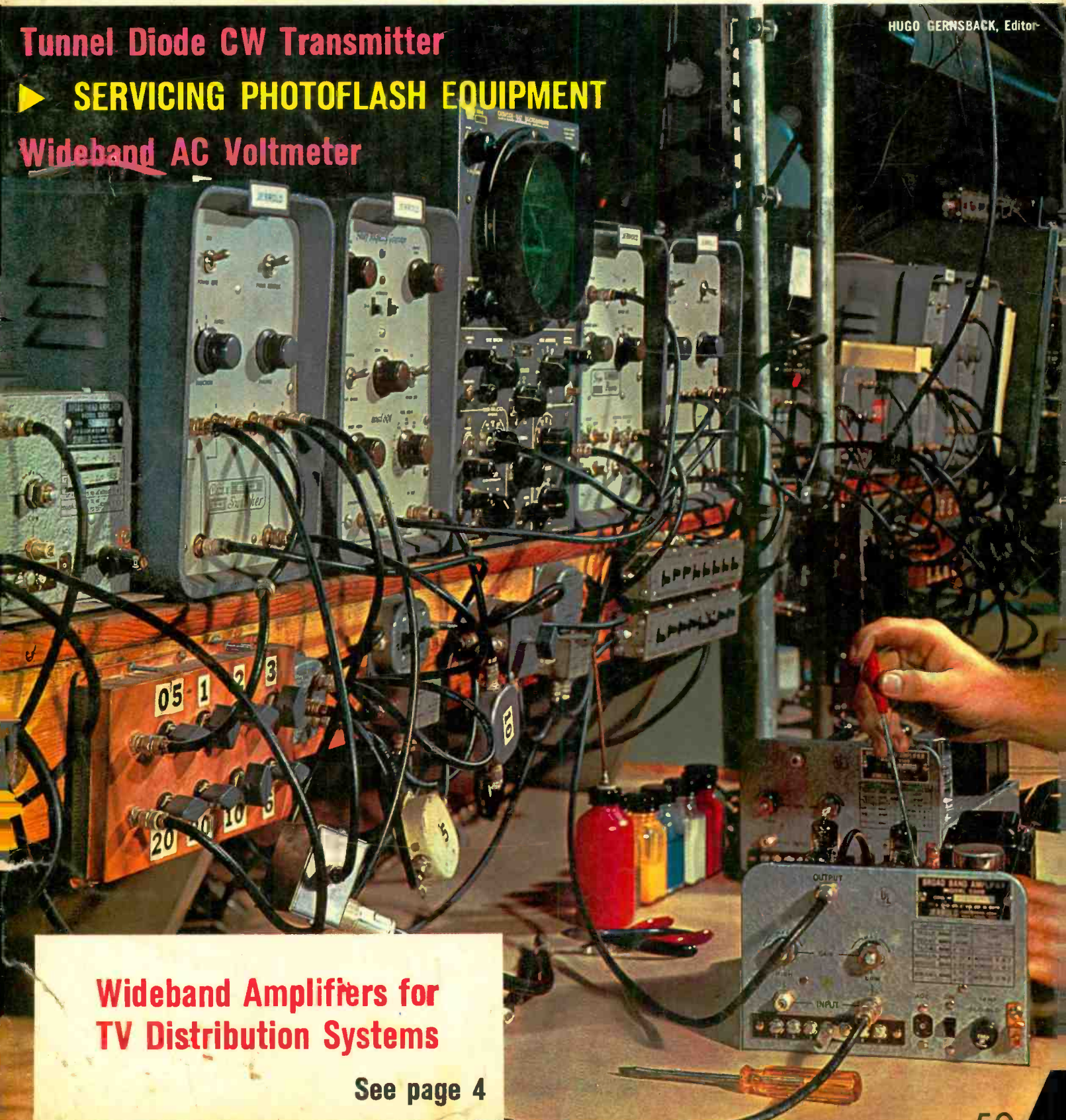

Wideband Amplifiers for TV Distribution Systems

See page 4

NOW... 4 GREAT "SALESMEN" SELLING FOR YOU!


Look at this parade of selling power! Sylvania advertising will make an average of over 9 million sales calls each week — thousands in your area — 52 weeks of the year. The top stars of radio, the largest-selling weekly magazine in the country... all selling for you in 1961.

Yes, Sylvania is going all out to help you build profits. All new streamers, in-store display and direct mail are

available from your Sylvania tube distributor. See him today. Stock up on Silver Screen 85 picture tubes and Sylvania quality receiving tubes. Do it now for a fast start to more profits in 1961.

Electronic Tubes Division,
Sylvania Electric Products Inc.,
1740 Broadway, Dept. 248.
New York 19, New York.

**IMPACT
ALL YEAR
LONG**




"ARTHUR GODFREY TIME"
52 weeks of the old redhead, telling his millions of listeners to specify Silver Screen 85 when it's time to replace their old picture tube.



**DON McNEILL'S
"BREAKFAST CLUB"**
Don McNeill, M.C. of the longest-running weekday program in radio, selling his millions of loyal listeners on the advantages of Sylvania Silver Screen 85 picture tubes.



**MONITOR
WITH NICHOLS & MAY**
Star talent like Nichols & May sell the Silver Screen 85 and you — the local independent TV service dealer — on the biggest network weekend show in radio.



**TV
GUIDE**
**FAVORITE OF
7,250,000 TV OWNERS**
TV GUIDE selling you and the Silver Screen 85 picture tube wherever TV sets are in use! Hard-hitting ads telling set owners how to make their old TV's work better than new, with a Silver Screen 85.



**SILVER
SCREEN 85**
The "pre-sold"
picture tube

**Sell the
profit leader
SYLVANIA!**

SYLVANIA

Subsidiary of **GENERAL TELEPHONE & ELECTRONICS**



SAVE OVER \$3 ON THIS BRAND-NEW EDITION

Every Essential Term in Physics and Electronics—15,000 of Them

—NOW IN ONE GIANT DICTIONARY!

BRAND-NEW 2nd EDITION — Bigger, More Useful than Ever! Famous ONE-SOURCE reference book expanded to 1,400 pages — covers major new fields; presents latest ideas, discoveries in 17 basic areas! New multi-lingual indexes.

NOW completely revised and expanded, *The International Dictionary of Physics and Electronics* is the only book available that defines and explains every important term in 16 basic and many new fields of modern physics and electronics.

More than 15,000 laws, relationships, equations, basic principles, instruments, and techniques are described in over half a million words. It takes the place of a whole library of reference books on: Electronics • Meteorology • Mechanics • Gases • Liquids • Solids • Acoustics • Optics • Units and Dimensions • General Principles • Heat and Thermodynamics • Atomic and Nuclear Physics • Mathematical Physics • Quantum Mechanics • Electricity • Relativity.


Coverage of all of these fields has been brought completely up-to-date. In addition, there is NEW MATERIAL on new developments in thermonuclear research and magnetohydrodynamics . . . space physics . . . astrophysics. IRE definitions in networks, computers, etc. New review of physics: great developments from Newton to non-conservation of parity and strange particles.

Arranged to Give You Any Information in Seconds

No more hunting from book to book — no more guesswork, wasted time or effort. Here's everything you need in one 1,400-page easy-to-use reference volume. Articles are arranged progressively — begin with concise definition and add details in later paragraphs. Unique cross-reference system lets you find any fact fast: bold-face "word signals" refer you to related articles. And newly-added 4-language index — Russian, German, French, Spanish — lists all terms with English equivalents.

Special Money-Saving Offer

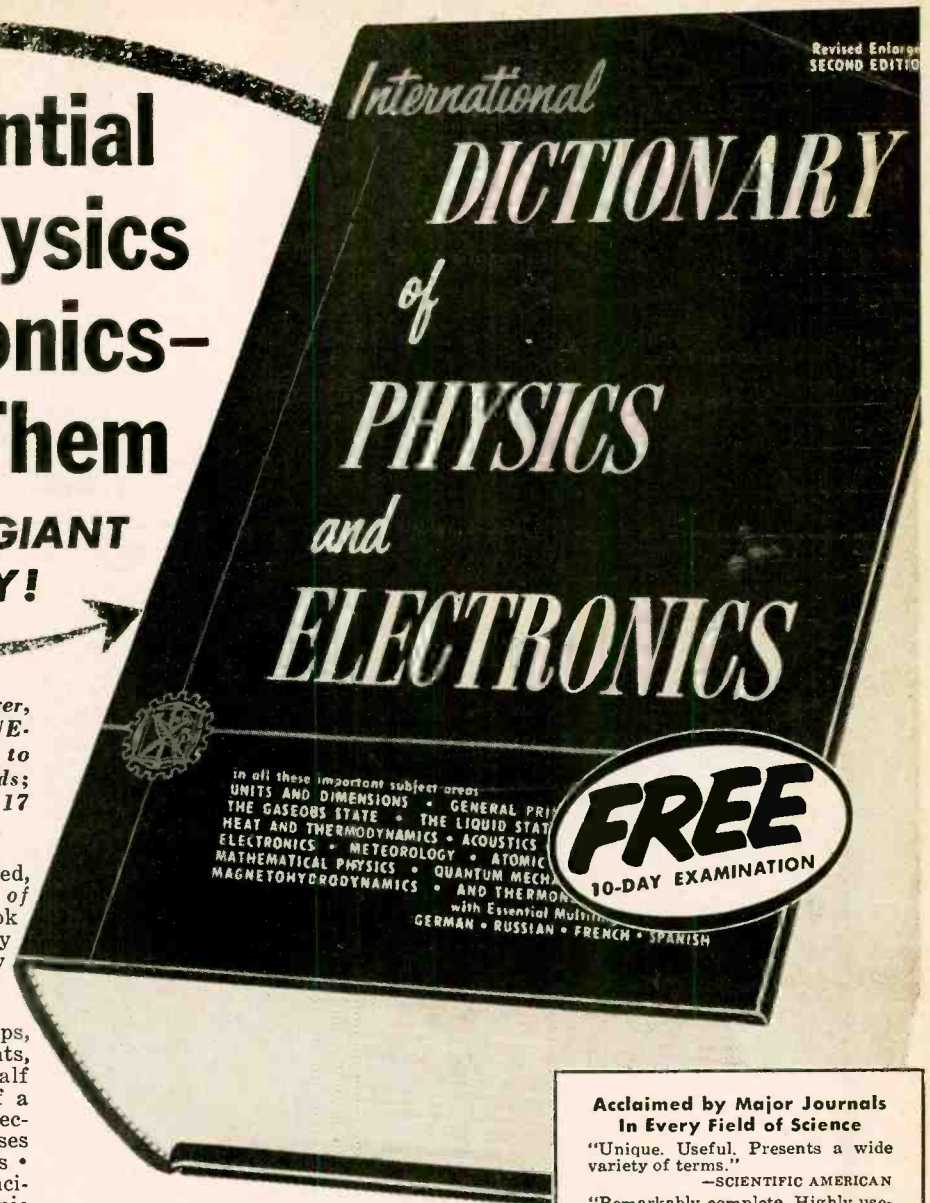This authoritative book is a monumental publishing achievement — 1,400 pages, 15,000 terms; bound and manufactured for a lifetime of use. After May 30 it will be priced at \$27.85.



Until that time, however, the publishers are making a direct-to-reader offer of only \$24.75 (payable in installments) a saving of \$3.10. To take advantage of this \$3.10 saving you need send no money now — only certificate below. Book will be sent to you for FREE 10-DAY EXAMINATION.

Use this enormous Dictionary to recheck work, clarify data, catch up with new ideas, developments. See how it can repay its cost many times over in just one avoided error. If not convinced that it will be one of your most valuable books return it and pay nothing. (Cost of book is tax deductible if used in your work.) Mail no-risk certificate now to: **D. Van Nostrand Company, Inc., Dept. 183, 120 Alexander St., Princeton, N.J. (Estab. 1848.)**

Acclaimed by Major Journals In Every Field of Science

"Unique. Useful. Presents a wide variety of terms."

—SCIENTIFIC AMERICAN

"Remarkably complete. Highly useful. Provides definite and concise answers to a myriad of questions."

—PHYSICS TODAY

"Will undoubtedly make a well-deserved place for itself."

—ELECTRONICS

"There has been a real need for such a work."

—LIBRARY JOURNAL

"Recommended for all that do any reference work in physics."

—NUCLEONICS

"Unique in its field and exceptionally clear in its typography. It should prove a most useful reference."

—TELE-TECH

"The best book of definitions available on the market today. Highly recommended."

SEND NOW — SAVE OVER \$3

**D. Van Nostrand Company, Inc.
Dept. 183, 120 Alexander St.,
Princeton, N.J.**

Name.....
(please print)

Address.....

City..... Zone..... State.....

Please send me the brand-new 2nd Edition of *The International Dictionary of Physics and Electronics*. If not delighted, I'll return it within 10 days and owe nothing. Otherwise, I'll remit \$9.75 plus small shipping cost then and \$5 a month for 3 months.

Check Here and SAVE! Enclose full payment (\$24.75) with this certificate and all shipping costs will be prepaid. Money-back guarantee. (In Canada: 25 Hollinger Rd., Toronto 16. Price slightly higher.) Foreign and A.P.O.—please enclose \$24.75 with certificate.

Radio-Electronics

MARCH, 1961

Formerly RADIO-CRAFT — Incorporating SHORT WAVE CRAFT — TELEVISION NEWS — RADIO & TELEVISION*

OVER FIFTY YEARS OF ELECTRONIC PUBLISHING

Hugo Gernsback
..... Editor and Publisher
M. Harvey Gernsback
..... Editorial Director
Fred Shunaman
..... Managing Editor
Robert F. Scott, W2PWG
..... Technical Editor
Larry Steckler
..... Associate Editor
I. Queen
..... Editorial Associate
Jack Darr
..... Service Editor
Fernando Martinez
..... Art Director
Wm. Lyon McLaughlin
..... Tech. Illustration Director
Fred Neinast
..... Art Associate
Elizabeth Stalcup
..... Production Manager
Lee Robinson
..... Director, Advertising Sales
John J. Lamson
..... Eastern Sales Manager
G. Aliquo
..... Circulation Manager
Adam J. Smith
..... Director, Newsstand Sales
Robert Fallath
..... Promotion Manager

Average Paid Circulation
Over 163,000



ON THE COVER

(Story on page 50)

Aligning amplifiers with a 50-mc passband is not simple. All the equipment on this section of a Jerrold test bench is really useful.

Color original by
Jerrold Electronics

Radio-Electronics is indexed in
Applied Science & Technology Index
(Formerly *Industrial Arts Index*)

119 Business and People
81 Correction
18 Correspondence
122 New Books
29 New Literature

editorial

33 Anti-Plane-Collision Radar—*Hugo Gernsback*

radio

34 Home-Made Tunnel-Diode CW Transmitter—
Lester A. Earnshaw, ZLIAAX
54 Consolan, What Is It?—*Elbert Robberson*

electronics

36 Inside the Electronic Photoflash—*C. L. Henry*
49 Communication by Light Wave
58 Heat to Electricity—*E. Aisberg*
80 Watch Demagnetizer
82 Emergency Alarm in Your Home

television

42 Vhf Translator TV for Your Town—*Philip Freen*
44 BBB Raps Set Manufacturers
50 Aligning Wide-Band Vhf Amplifiers (Cover Feature)—*Jack Beaver*
53 Translator Authorization Fact Sheet
60 TV Service Clinic (Signal Generators in TV Alignment)—
Conducted by Jack Darr
89 Sync Separators and Clippers, Part II—*Jack Darr*

what's new

45 Pictorial Reports of New Developments

audio-high fidelity

46 Custom Hi-Fi Preamp Design—*Mannie Horowitz*
59 Convert Your Speaker System to Stereo for \$20—
Gordon R. Lichtenwalter
96 Remote Amplifier Has Four-Transistor Circuit—
George Waslo, WKRC-TV

test instruments

40 Easy-to-Build Wide-Band Vtvm Doubles as Audio Analyzer—
Kenneth E. Walters
73 Two-Terminal Oscillator—*I. Queen*
74 Wobulating Sweep Generator Worth Building—*Gerald Wilner*
92 Case of the Missing Spot—*Paul W. Karrol*

industrial electronics

68 About These Super-Scopes—*Tom Jaski*
86 Radio-Controlled Die Protection—*Dellroye D. Darling*

the departments

115 New Patents
106 New Products
113 New Tubes and Semiconductors
6 News Briefs
117 Noteworthy Circuits
100 Technicians' News
98 Technotes
123 Try This One
116 50 Years Ago

Radio-Electronics March, 1961, Vol. XXXII, No. 3. Published monthly at Mt. Morris, Ill., by Gernsback Publications, Inc. Second-class postage paid at Mt. Morris, Ill. Copyright 1961 by Gernsback Publications, Inc. All rights reserved under Universal, International and Pan-American Copyright Conventions.

Subscription Rates: U.S., U.S. possessions and Canada, \$5.00 for one year; \$9.00 for two years; \$12.00 for three years. Pan-American countries \$6.00 for one year; \$11.00 for two years; \$15.00 for three years. All other countries \$6.50 a year; \$12.00 for two years; \$16.50 for three years.

Subscriptions: Address correspondence to Radio-Electronics, Subscriber Service, 154 West 14th St., New York 11, N.Y. When requesting a change of address, please furnish an address label from a recent issue. Allow one month for change of address.

Gernsback Publications, Inc., Executive, Editorial and Advertising Offices, 154 West 14th St., New York 11, N.Y. Telephone ALgonquin 5-7755. Hugo Gernsback, Chairman of the Board; M. Harvey Gernsback, President; G. Aliquo, Secretary.

Advertising Representatives: Los Angeles: Harker-Husted-Coughlin, 400 South Alvarado St., Tel. DUmalkirk 7-2328. San Francisco: Harker-Husted-Coughlin, 444 Market St., Tel. GARfield 1-0151. Chicago: 8631 East Prairie Road, Skokie, Ill. Tel. ORchard 5-3740. United Kingdom: Publishing & Distributing Co., Ltd., Mitre House, 177 Regent St., London, W. 1, England.


Foreign Agents: Great Britain: Atlas Publishing and Distributing Co., Ltd., 18 Bride Lane, London E.C. 4.

Postmaster: If undeliverable, send Form 3579 to: RADIO-ELECTRONICS, 154 West 14th St., New York 11, N.Y. *Trademark registered U. S. Pat. Office.

BREAK THROUGH TO HIGHER PAY

in ELECTRONICS


TV-RADIO

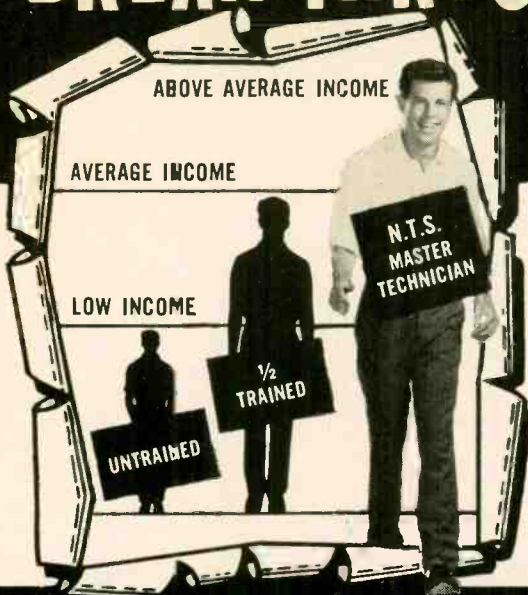

START NOW! Break through the Earning Barrier that stops half-trained men. N.T.S. "All-Phase" training prepares you — at home in spare time — for a high-paying CAREER in Electronics — TV — Radio as a MASTER TECHNICIAN. One Master Course at One Low Tuition trains you for unlimited opportunities in All Phases: Servicing, Communications, Preparation F.C.C. License, Broadcasting, Manufacturing, Automation, Radar and Micro-Waves, Missile and Rocket Projects.

A more rewarding job... a secure future... a richer, fuller life can be yours! As an **N. T. S. MASTER TECHNICIAN** you can go straight to the top in industry... or in your own profitable business.


You work on actual job projects

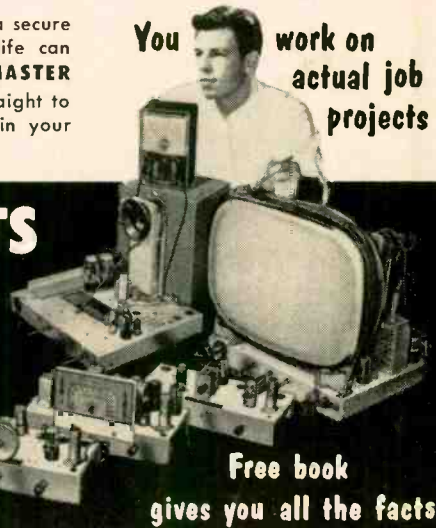

SUCCEED IN MANY HIGH-PAYING JOBS LIKE THESE...

- TV-Radio Sales, Service and Repair
- Profitable Business of Your Own
- Communications Technician — F.C.C. License
- Hi-Fi, Stereo & Sound Recording Specialist
- TV-Radio Broadcasting Operator
- Technician in Computers & Missiles
- Electronics Field Engineer
- Specialist in Microwaves & Servomechanisms
- Expert Trouble Shooter
- All-Phase Master Technician

19 BIG KITS YOURS TO KEEP

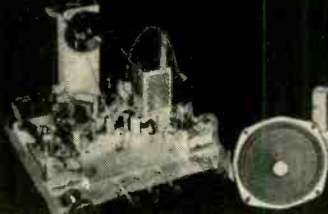

Free book gives you all the facts

NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905
4000 S. FIGUEROA ST., LOS ANGELES 37, CALIF., U. S. A.
Write Dept. RG-31



ACCREDITED MEMBER
... the only nationally recognized accrediting agency for private home study schools.

RESIDENT TRAINING AT LOS ANGELES

If you wish to take your training in our Resident School at Los Angeles, start NOW in our big, modern Shops and Labs. Work with the latest Auto and Diesel engines — all types — fuel injection, automatic transmissions, all power equipment — most complete facilities offered by any school. Expert, friendly instructors. Graduate Employment Service. Help in finding home near school — and part time job while you learn.

WRITE FOR SPECIAL RESIDENT SCHOOL CATALOG AND INFORMATION

N.T.S. Shop-Tested HOME TRAINING is **Better, More Complete, Lower Cost**... and it is your key to the most fascinating, opportunity-filled industry today!

YOU LEARN QUICKLY AND EASILY THE N.T.S. SHOP-TESTED WAY

You get lessons, manuals, job projects, unlimited consultation, graduate advisory service. You build a Short Wave-Long Wave Superhet Receiver, plus a large-screen TV set from the ground up, with parts we send you at no addi-

tional cost. You also get a Professional Multimeter for your practical, job projects.

EARN AS YOU LEARN... WE SHOW YOU HOW!

Many students pay for entire tuition — and earn much more — with spare time work they perform while training. You can do the same... we show you how.

SEND FOR INFORMATION NOW... TODAY! IT COSTS YOU NOTHING TO INVESTIGATE.

N.T.S. HOME TRAINING is

- Classroom Developed
- Lab-Studio Planned
- Shop-Tested
- Industry-Approved
- Specifically Designed for Home Study



MAIL COUPON NOW for FREE BOOK and ACTUAL LESSON

NO OBLIGATION!
NO SALESMAN WILL CALL

NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

Mail Now To
National Technical Schools, Dept. RG-31
4000 S. Figueroa St., Los Angeles 37, Calif.

Please rush FREE Electronics-TV-Radio "Opportunity" Book and Actual Lesson. No Salesman will call.

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

Check here if interested ONLY in Resident Training at Los Angeles.

VETERANS: Give date of discharge _____

News Briefs

New Color TV System May Help Small Stations

A new system of photographing and transmitting color TV signals worked out by Prof. William T. Hughes of Iowa State University offers many advantages of simplicity and low cost, according to its developer. A two-camera pickup, with one camera picking up the luminance signal and the other an alternately blue and red signal, as controlled by a color wheel, replaces the conventional three-camera setup. A delay line in parallel with the red-blue line supplies an extra delayed-chroma signal, and both chroma and luminance are fed to an NTSC encoder which puts out an NTSC signal.

The signal, it is claimed, can be sent over wire or microwave circuits of lower quality than would be necessary for conventional color transmission, can be monitored en route with simple equipment, and can be recorded on a black-and-white video recorder. Present TV stations can modify their equipment to use the Iowa State system at a much lower cost than would be necessary to install conventional color TV equipment.

Ultraviolet Now Used For Communications

An experimental system designed for long-distance communication in free space has been demonstrated by Westinghouse. Signals picked up by a standard TV camera are used to modulate the beam of a 5ZP16 cathode-ray tube, which radiates 1 watt of ultraviolet from a .011-inch spot. This is focused into a .033°



conical beam by an optical reflector. This beam is intense enough, says Dr. Paul Pan of Westinghouse, to permit communication over a 10-kc band at distances up to about 15,000,000 miles. For shorter ranges, such as the distance to the moon, video bandwidths could be transmitted.

The receiver is a phototube—an ultraviolet-sensitive photomultiplier. The output image is displayed on the screen of a regular TV receiver, as shown in the photo.

Electricity Replaces Ether

An abdominal operation performed on a woman patient at the Medical Center of the University of Michigan depended on electricity as the anesthetic. A 700-cycle signal from a signal generator was fed through an amplifier to 1-inch diameter electrodes connected to the patient's temples. In less than a minute after the unit was turned on, the patient was unconscious. The patient remained asleep as long as current was fed to the electrodes. After the operation, the current was turned off and the patient regained consciousness in less than 60 seconds. The patient said she felt no discomfort or nausea upon awakening. The entire system costs about \$150.

This anesthetic system is highly desirable, since it works directly on the nervous system and does not seem to affect blood circulation or any body organs.

The use of the electrical anesthesia was developed after 4 years of research by the university's Medical Center under an Army grant. The Army was interested because quick recovery from anesthesia is advantageous when operating under combat conditions.

New Computers Speak English

Announcements by three companies in the computer field indicate that computers may be programmed with plain English instead of coded commands in the language of binary numbers. IBM first described a new computer called *Suitcase*, which recognizes the digits from 1 to 9, spoken by a person who has been given an hour's training in enunciation.

More recently RCA and Remington Rand reported on an experiment in exchanging computer programs using plain English between data processing systems of different manufacturers. Using conventionalized English, called *Common Business*

Oriented Language (COBOL) two problems were programmed and first fed to the equipment of the manufacturer who prepared the program. Then, with minor changes, they were fed into the other manufacturer's equipment. The machines worked equally well and gave the same answers in both cases.

When using COBOL, the machine is programmed to understand nouns used in the business in which it works, such as "payroll file" or "employee number." It also knows some 20 verbs, including the arithmetic commands "add, divide," etc., and such words as "read, display," or "stop." A computer order in COBOL, for instance, might be written "SUBTRACT DEDUCTIONS FROM GROSS GIVING NET." The same command in the older numerical code would be, for the RCA 501, 72-010237--00-600000. The UNIVAC II translation would be B00549 S00623 C00942.


Low-Power Optical Maser Announced by IBM

A new optical maser (RADIO-ELECTRONICS, December, 1960, page 8) that is expected to permit continuous generation of coherent light waves is reported by Drs. Peter P. Sorokin and Mirek J. Stevenson of International Business Machines. Earlier masers, as developed by Hughes and Bell Laboratories, require so much power that they can be operated only in short pulses.

Secret of the new maser is the crystal in which the light is generated. It is calcium fluoride, a common optical material, and the ions that are stimulated into coherent light emission are of trivalent uranium or divalent samarium. The rods with trivalent (three electrons missing from the outer shell) uranium impurities emit infrared light at a wavelength of 2.5 microns; the divalent samarium (two electrons missing from the outer shell) produces light at 0.708 micron, in the deep red portion of the spectrum. The power required to stimulate the crystal is less than 1/500 that necessary for a ruby crystal with chromium atoms as the impurity.

NAA Transmits Again

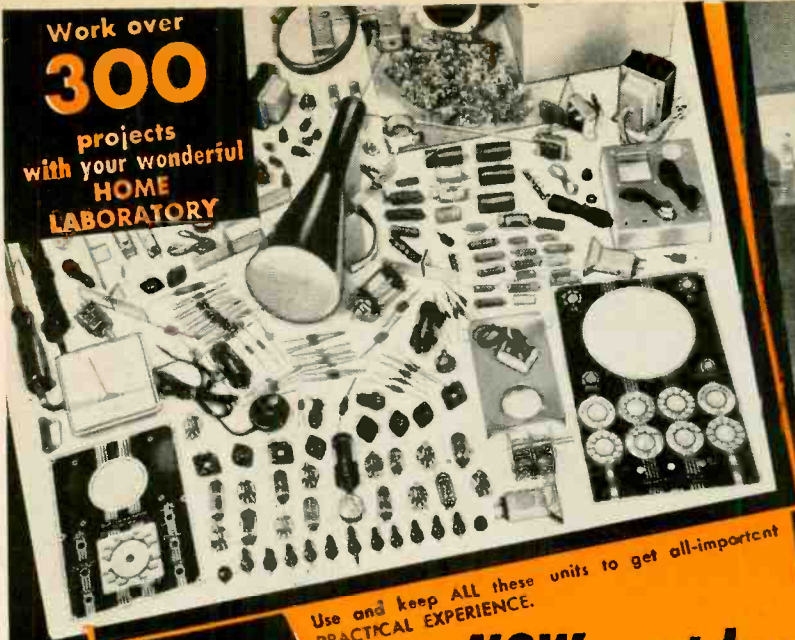The new super-power low-frequency Navy radio station at Cutler, Me., has been allotted the traditional call letters NAA. The call was made famous by the Navy's original high-power station at Arlington, Va.,




Work over
300
projects
with your wonderful
**HOME
LABORATORY**

Use and keep ALL these units to get all-important
PRACTICAL EXPERIENCE.



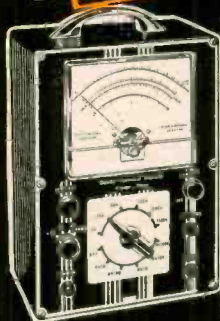A MILLION DOLLARS IN EQUIPMENT! Instruments, tools, supplies are available for DeVry Tech students in our Chicago and Toronto Laboratories. Above is shown a Closed Circuit TV station in our Chicago Laboratories.



Also!

Build and keep This DeVry Tech **VACUUM TUBE VOLTMETER** — one of the most useful of all test instruments.


NOW...at home...get DeVry Tech's amazing effective training in

ELECTRONICS

RADIO-TELEVISION! Nothing else like it for providing real LABORATORY-TYPE training at home. Get the kind of thorough, practical experience YOU NEED for the kind of progress YOU WANT in today's tremendous field of Television, Radio and Electronics. Qualify yourself for real money... interesting work... a wonderfully promising future. And when you finish, DeVry Technical Institute's active Employment Service HELPS YOU GET STARTED! Or open your own profitable Television-Radio Service Business.



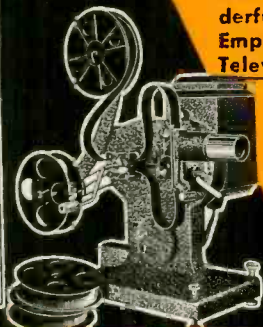ABOVE: Also build and keep this quality Oscilloscope — almost a "must" for Television servicing.



Exclusive HOME MOVIES

help you grasp important points **FASTER... EASIER... BETTER.** A tremendous advantage!

THOUSANDS OF SUCCESSFUL GRADUATES

Why has DeVry Technical Institute become one of the largest training organizations of its kind? Because it provides EVERY MAJOR HOME TRAINING AID to help make the subject EASIER to learn... EASIER to remember—the kind of training so helpful for REAL PROGRESS. Students get thorough, up-to-date, practical training that TAKES ADVANTAGE of new and improved training developments. Study the ADVANTAGES shown on this page. Think what they can mean to YOU... to YOUR FUTURE! Or come to DeVry Tech's modern Training Laboratories in Chicago or Toronto. MAIL COUPON TODAY for complete facts—including 2 valuable free booklets, "Pocket Guide to Real Earnings" and "Electronics in Space Travel". Also, valuable information for men subject to MILITARY SERVICE.

Accredited member of
National Home Study Council

**SEND FOR 2 FREE BOOKLETS
MAIL COUPON TODAY!**



DEVRY TECHNICAL INSTITUTE

4141 Belmont Avenue, Chicago 41, Ill., Dept. WE3-R

Please give me your two free booklets, "Pocket Guide to Real Earnings" and "Electronics in Space Travel"; also include details on how to prepare for a career in Electronics. I am interested in the following opportunity fields (check one or more):

- | | |
|--|--|
| <input type="checkbox"/> Space & Missile Electronics | <input type="checkbox"/> Communications |
| <input type="checkbox"/> Television and Radio | <input type="checkbox"/> Computers |
| <input type="checkbox"/> Microwaves | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Radar | <input type="checkbox"/> Industrial Electronics |
| <input type="checkbox"/> Automation Electronics | <input type="checkbox"/> Special "Short Courses" |

Name _____ Age _____
Address _____ PLEASE PRINT Apt. _____
City _____ Zone _____ State _____

Check here if you face military service.
Canadian residents: Write DeVry Tech of Canada, Ltd.,
970 Lawrence Avenue West, Toronto 19, Ontario

1001

NEW! ALL NEW!

**Now Prepare For
SPACE AND MISSILE
Electronics At Home**

DeVry Tech now also makes available their highly effective SPACE and MISSILE ELECTRONICS Program. Now a man can train at home for a job in "outer space"—and not only "keep his feet on the ground": he can keep his present job while he is training. DeVry opens a wider range of job opportunities to a wider range of men 17-55.

**DeVRY TECHNICAL
INSTITUTE**
CHICAGO • TORONTO

MATCH LIVE SOUND WITH THORENS TD-124



The turntable that adjusts for perfect pitch!

Thorens compensates for variations in house current and recording systems; gives the truest reproduction with all your records, old or new. Adjustment is so fine that records can be used to accompany *live* vocal and instrumental performances. Swiss precision engineering ensures longer record life, performance to match the finest components you will ever own. See your Thorens dealer soon for expert attention and high fidelity service.

- 4 speeds adjust while record plays
- Illuminated strobe and circular level built in
- Easy installation of 12" and 16" arms
- Only \$99.95 net. Other models from \$47.50

THORENS

FAMOUS SWISS HI-FI COMPONENTS

MUSIC BOXES • SPRING-POWERED SHAVERS • LIGHTERS

A Division of ELPA Marketing Industries, Inc. • New Hyde Park, New York

Guaranteed for one full year. Sold only through carefully selected franchised dealers.



which was the foremost of the US coast stations and whose time signals were received not only by mariners but by watchmakers, who used special "Arlington" receivers fixed-tuned to that station.

The new NAA is now being tested at frequencies as low as 14 kc and will operate on some frequency in that region. It will not send time signals since NBA, at Balboa, has a complete schedule of time signals on 18 kc.

Electronic Refrigerator Announced by Hitachi

The Consumer Goods Div. of Hitachi Ltd., Tokyo, has released specifications on an electronic refrigerator, including a freezer compartment. The capacity of the refrigerator is approximately 3 1/3 cubic



feet and the outside dimensions 20 x 46 x 23 inches. It uses 36 thermo-elements. The power consumption is given as 30 volts, 10 amps for the cooling space and 20 volts, 10 amps for the freezer. Box temperature is 40°F, freezer temperature 9°F at an ambient temperature of 86°F.

Radio Pioneer Passes

John V. L. Hogan, early pioneer in radio and high fidelity, died Dec. 29, 1960, in New York City. He was 71.


His career started while a schoolboy, when, as he said, he was the chief (and only) laboratory assistant to Dr. Lee de Forest in the winter of 1906-07. In that capacity, he was one of the three or four people who were present at the birth of the Audion. Shortly afterward, as a student in the Sheffield Scientific School at Yale (where de Forest had received his training), he invented the gang capacitor, the patent on which fortunately had a few years to run when ganged tuning devices came into general use. Later he was associated with Fessenden in some of his work at Brant Rock.

Mr. Hogan became a consulting engineer in 1921 and worked with TV, facsimile and communications radio among other projects. He founded the country's first high-fidelity broadcast station in 1928. Using the experimental call W2XR, it broadcast high-quality musical programs and signals intended to

ALLIED value-packed 1961

444-PAGE ELECTRONICS CATALOG

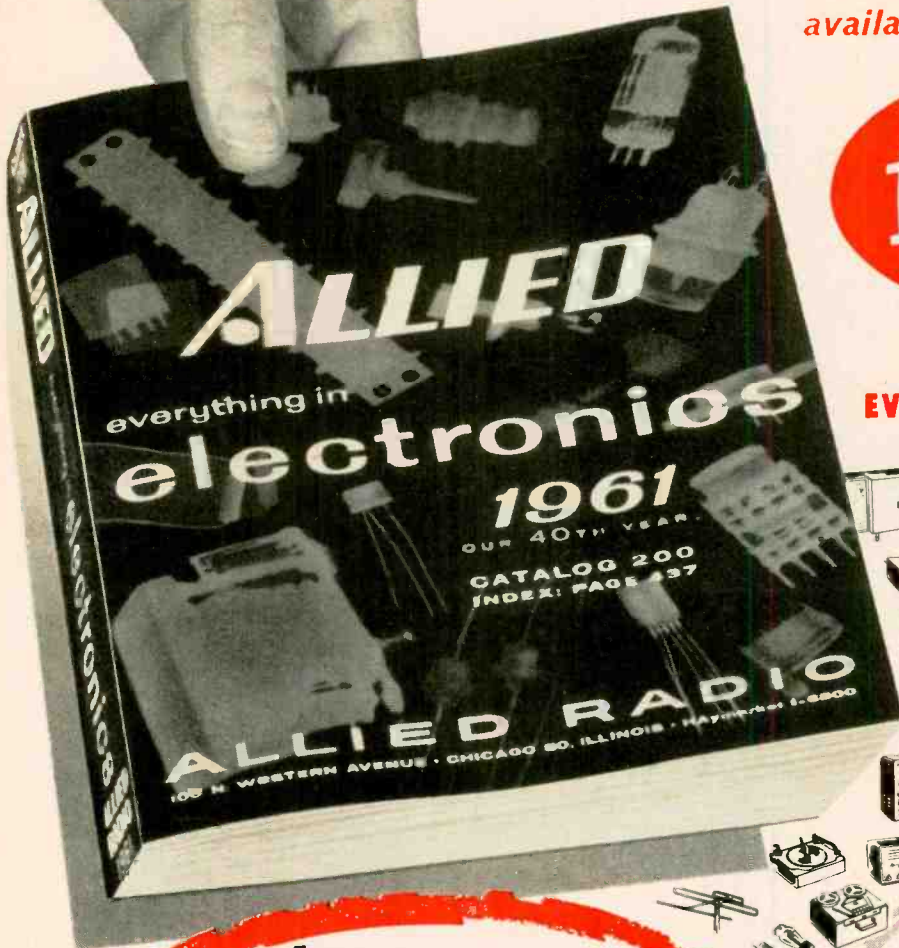including special products
available only from Allied



free

SAVE MOST ON

EVERYTHING IN ELECTRONICS

- New Stereo Hi-Fi Systems— Everything in Hi-Fi Components
- Money-Saving, Build-Your-Own KNIGHT-KITS® for Every Need
- Best Buys in Recorders & Supplies
- Newest Public Address Systems, Paging and Intercom Equipment
- Amateur Receivers, Transmitters and Station Gear
- Citizen's Band 2-Way Radio
- Test and Laboratory Instruments
- TV Tubes, Antennas, Accessories
- Huge Listings of Parts, Tubes, Transistors, Tools, Books

BUY ON EASIEST TERMS

only \$2 down on orders up to \$50;
only \$5 down on orders up to \$200;
only \$10 down over \$200.
Up to 24 months to pay.

ALLIED exclusives:

MONEY-SAVING KNIGHT-KITS®—truly the very best in build-your-own electronic equipment—lowest in cost, easiest to assemble, best for performance. Select from a complete line of Stereo hi-fi kits, Hobbyist kits, Test Instrument and Amateur kits. KNIGHT-KITS are an exclusive ALLIED product.

KNIGHT® STEREO HI-FI—Comparable to the best in quality, styling and performance, yet priced far lower. Select super-value KNIGHT components or complete systems and save most. Also see the largest selections of famous-name hi-fi components and money-saving ALLIED-recommended complete high-fidelity music systems.

Exclusive Allied products save you more

You get every buying advantage at ALLIED: Lowest, money-saving prices, fastest shipment, expert personal help, easiest-pay terms, satisfaction guaranteed or your money back.

send coupon today
for 444-page catalog

free

ALLIED RADIO

Satisfaction Guaranteed or Your Money Back

World's Largest Electronic Supply House



MARCH, 1961


ALLIED RADIO, Dept. 2-C1
100 N. Western Ave., Chicago 80, Ill.

Send FREE 1961 Allied Catalog No. 200

Name _____
PLEASE PRINT

Address _____

City _____ Zone _____ State _____

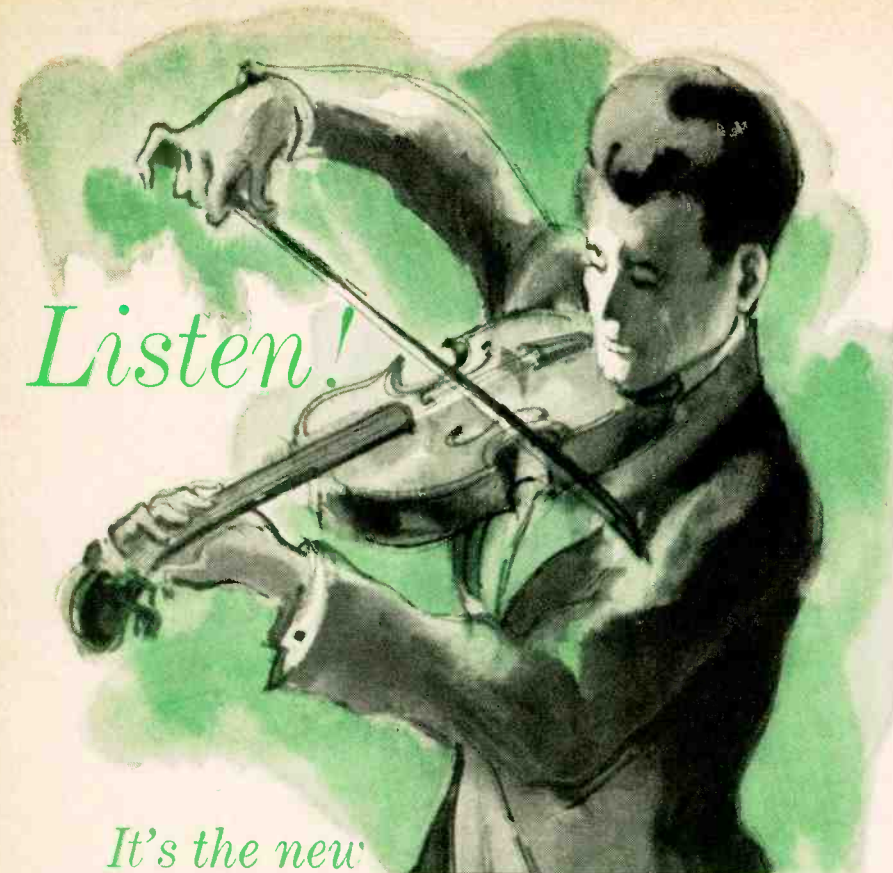

Listen!

*It's the new
Sonotone Ceramic "Velocitone"*

No stereo cartridge—not even the finest magnetic in the world—outperforms it!

Listen!... with your own magnetic... or with any magnetic you can buy today—at any price. Then replace it *directly* in your component system with Sonotone's new "VELOCITONE" STEREO CERAMIC CARTRIDGE ASSEMBLY. Listen again! We challenge you to tell the difference. Experts have tried... in dozens of A-B listening tests. And, in every single one, Sonotone's "VELOCITONE" performed as well as or better than the world's best magnetic.

Listen!... perfectly flat response in the extreme highs and lows (better than many of the largest-selling magnetics).

Listen!... excellent channel separation—sharp, crisp definition.

Listen!... highest compliance—considerably superior tracking ability.

Listen!... absolutely no magnetic hum—quick, easy, *direct* attachment to any magnetic inputs.

Listen!... remarkable performance characteristics unexcelled anywhere. (Write Sonotone Corporation for specifications.)

Now listen to the price. Only \$23.50... about one-half the price of a good stereo magnetic cartridge. Yet Sonotone's "VELOCITONE" stereo ceramic cartridge system cannot be outperformed by any magnetic—regardless of price.

Sonotone®
CORP.

ELECTRONIC APPLICATIONS DIVISION, ELMSFORD, N. Y., DEPT. C2-31
IN CANADA, CONTACT ATLAS RADIO CORP., LTD., TORONTO

LEADING MAKERS OF CARTRIDGES • SPEAKERS • TAPE HEADS • MIKES • ELECTRONIC TUBES • BATTERIES



test the response of home broadcast receivers. In 1936 it became a commercial station, WQXR, under which call it is still being operated as a broadcast station by *The New York Times*.

He developed a facsimile system (described in this magazine July, 1946) that reproduced text at the rate of 500 words per minute. Transmission at this speed, he pointed out, made a home radiofacsimile newspaper possible.

As secretary of the Society of Wireless Telegraph Engineers when it merged with the Wireless Institute to form the present organization, he was one of the founders and an active member of the Institute of Radio Engineers.

**FCC Will Construct
Experimental UHF TV**

New York's Empire State Building Corp. recently announced the signing of a contract for housing a uhf TV transmitter for the FCC and for an antenna on the Empire State Building tower. The new station will be used by the FCC to study uhf coverage and other problems as a guide to allocations policy. The new station will become the eighth to transmit from the Empire State Building.

Erwin Schrodinger Dies

Prof. Erwin Schrodinger died in his native Vienna, Jan. 4, at the age of 74. His work, in combination with that of de Broglie and Dirac, formed the foundation for the modern concept of wave mechanics. He shared with P. A. M. Dirac the Nobel prize for physics in 1933.

Professor Schrodinger conducted a seminar at the Institute for Advanced Studies in Princeton, N. J., in 1934. He left Austria at the coming of the Hitler regime in 1938 and taught at the Dublin Institute for Advanced Studies in Ireland till 1956, when he returned to Austria.

Earth, Too, Has Hum

That the earth itself gives off a subsonic radio hum at 7.8 cycles per second has been discovered by scientists of the Lincoln Laboratory,

How to Get a Commercial FCC License

do you know what an FCC license really can do for you in Electronics?

- 1 More income for you every week
- 2 A more interesting job in electronics

Chances are if you are reading this magazine, you can qualify for the really good jobs in electronics, like those shown at left. Your past training and experience in radio & TV repair, armed forces electronics, ham operator, etc. can be your foundation for a profitable career as an electronics technician. Send for the Career Information Material shown below today.

Investigate Our NEW Training Program in Computers, Servo Mechanisms, Magnetic Amplifiers and Others

Accredited by National Home Study Council

Get All 3 Valuable Booklets **Free . . .**




Just Mail The Coupon Below Today

CLEVELAND INSTITUTE OF ELECTRONICS

Desk RE-51-A
1776 E. 17th St.
Cleveland 14, Ohio

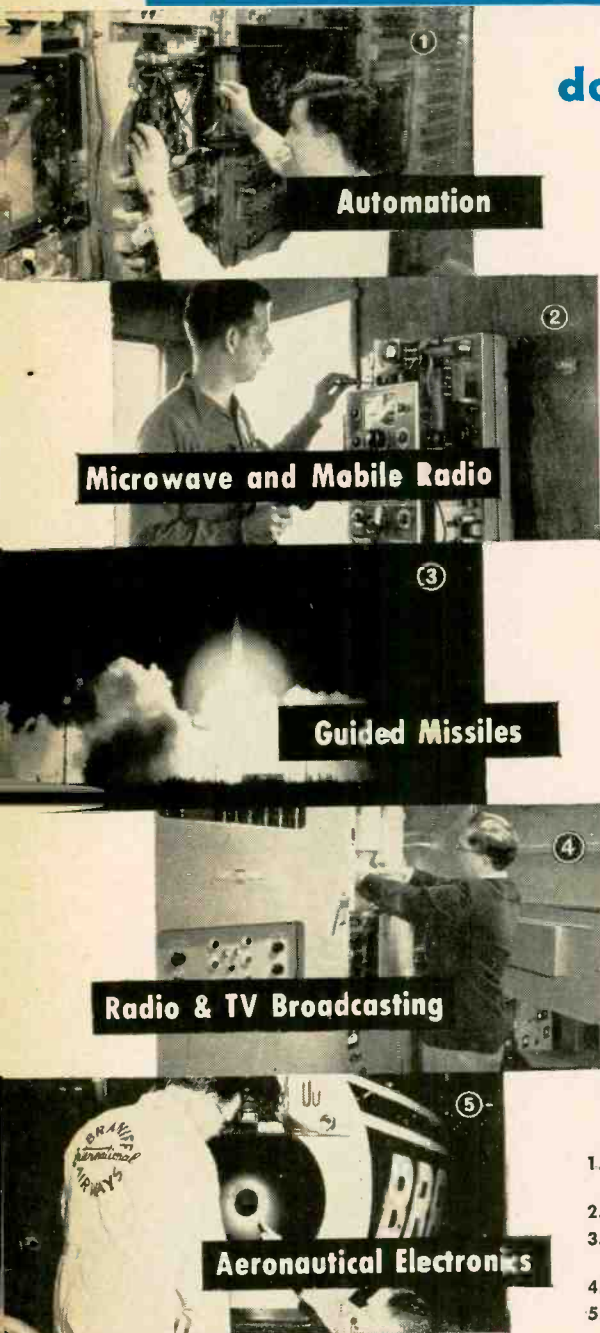1. Raytheon Manufacturing Company
2. Radio Corporation of America
3. Jupiter IRBM, Army Ordnance Missile Command
4. Collins Radio Company
5. Radio Corporation of America



Free! 

FIND OUT HOW:

1. The new electronic devices can be handled by you.
2. To solve the problems that will stump your fellow technicians.
3. Training is Job Insurance when employment is tough to find . . . and more money for you when times are good.

Successful Electronics Training

CLEVELAND INSTITUTE OF ELECTRONICS

Desk RE-51-A, 1776 E. 17th St., Cleveland 14, Ohio

Please send FREE Career Information Material prepared to help me get ahead in Electronics. I have had training or experience in Electronics as indicated below:

- | | |
|---|---|
| <input type="checkbox"/> Military | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Radio-TV Servicing | <input type="checkbox"/> Home Experimenting |
| <input type="checkbox"/> Manufacturing | <input type="checkbox"/> Telephone Company |
| <input type="checkbox"/> Amateur Radio | <input type="checkbox"/> Other |

In what kind of work are you now engaged? _____

In what branch of Electronics are you interested? _____

Name _____ Age _____


Address _____

City _____ Zone _____ State _____

RE-51-A

Latest issue of TUNG-SOL TIPS

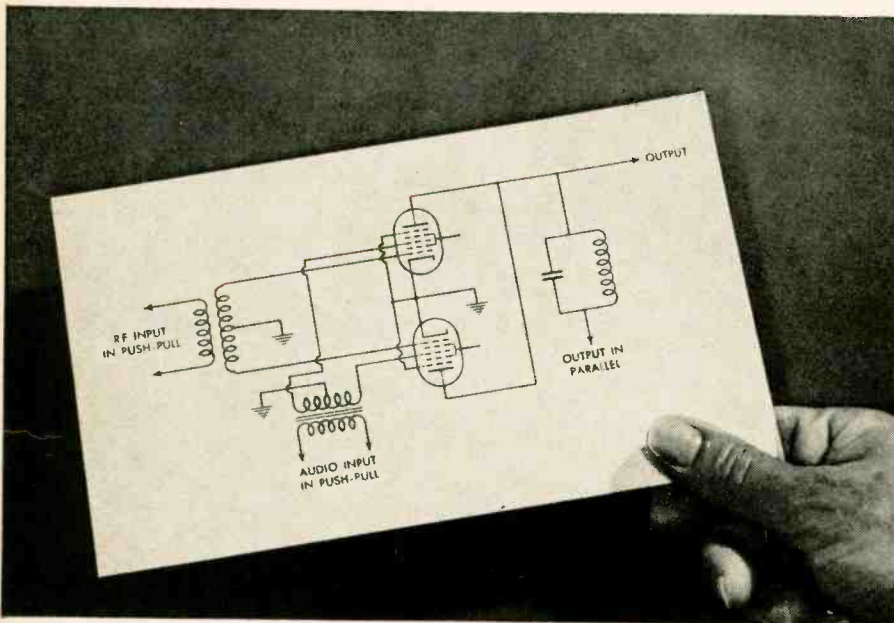tells you what you should know about
SINGLE SIDE BAND



The two-tube balance modulator circuit is an important element in single side band transmission. It's discussed in the latest issue of *Tung-Sol Tips*.

MONTH after month *Tung-Sol* has been delivering to the industrial serviceman one important issue of *Tung-Sol Tips* after another. Specially written for the service dealer who wants to devote his talents to servicing industrial equipment, every issue of *Tips* is crammed full of vital information to help him in his work. This latest issue is no exception.

Issue #14 offers in down-to-earth, on-the-job terms a full-scale treatment of single side band transmission. It discusses its advantages over conventional AM signals—and these advantages are considerable. You'll discover how the elimination of the carrier signal and one-side band are accomplished without any reduction of signal quality and intelligence. You'll be introduced to a whole series

of typical modulator circuits which are used to suppress the carrier. In addition, there's a thorough explanation of the filtering and phasing methods for eliminating sidebands.

Tips also delivers a highly detailed description of SSB reception with an excellent discussion of important receiving devices as "product detectors".

So, if you're a serviceman who still hasn't signed up to get his issues of *Tung-Sol Tips* free every month, now is the time to do it. You won't want to miss this issue and the important issues planned for the future. All you have to do is drop in to see your local *Tung-Sol* distributor and ask him to put you on the *Tung-Sol Tips* mailing list. Or write directly to: *Tung-Sol Electric Inc.*, Newark 4, N. J.

ts TUNG-SOL®

SALES OFFICES: ATLANTA, GA.; COLUMBUS, OHIO; CULVER CITY, CALIF.; DALLAS, TEXAS; DENVER, COLO.; DETROIT, MICH.; IRVINGTON, N. J.; MELROSE PARK, ILL.; NEWARK, N. J.; PHILADELPHIA, PA.; SEATTLE, WASH. IN CANADA: ABBEY ELECTRONICS, TORONTO, ONT.

Massachusetts Institute of Technology. The low-frequency waves, they say, are excited by lightning discharges in the area between the earth's surface and the ionosphere. This space forms a resonant cavity, with waves reflected from the ionosphere at one boundary and from the earth at the other.

Calendar of Events

Pacific Electronics Trade Show (PETS), Feb. 26-Mar. 1, Great Western Exhibit Center, Los Angeles, Calif.

EIA Spring Conference, Mar. 15-17, Statler Hilton Hotel, Washington, D.C.

Magnetic Recording Industry Assoc., San Francisco High Fidelity Show, Mar. 15-19, Cow Palace, San Francisco, Calif.

1961 IRE International Convention, Mar. 20-23, Waldorf-Astoria Hotel and New York Coliseum, New York, N. Y.

IHFH High Fidelity Music Show, April 4-9, Ambassador Hotel, Los Angeles, Calif.

American Society for Testing Materials Symposium on Materials and Electron Device Processing, April 5-7, Benjamin Franklin Hotel, Philadelphia, Pa.

Southwestern IRE Conference & Electronics Show, April 19-21, Baker Hotel and Dallas Memorial Coliseum, Dallas, Tex.

IRE 7th Region Technical Conference and Trade Show, April 26-28, Westward Ho Hotel, Phoenix, Ariz.

Television Classroom Takes to the Air

A flying TV school 23,000 feet above Indiana was ready to start telecasting instruction over Indiana and portions of Michigan, Illinois, Ohio, Wisconsin and Kentucky early in the year, Westinghouse Electric reports.

The Stratovision system was tested by Westinghouse some years ago. Two planes are allotted to the work, one being on the air at a time. Transmission is on uhf channels 72 and 76. Each plane is equipped with two 1-kw transmitters. The signal is a special narrow-band type—3 mc wide, and will be transmitted from video tapes.

WWV Sets Its Clock Back

The time signals from WWV, Washington, D. C., and from WWVH in Hawaii were retarded by 5 milliseconds early in January. The adjustment brought the signals of the US stations into closer agreement with the standard-frequency broadcast stations of other countries throughout the world. At the same time, the two stations resumed broadcasting a special timing code that gives the day, hour, minute and second for 1-minute intervals ten times per hour.


World-Wide Color Television At 1964 Fair, Says Sarnoff

The 1964 World's Fair at New York may well be ushered in by a world-wide color television broadcast, reported David Sarnoff, RCA chairman and chief executive officer.

"From a technical standpoint," he stated, "I am certain that it will be possible to televise the fair opening in natural color, over remote parts of the world, by a satellite communications system." **END**


THE A.E.S. Gigolo

A MIRACLE IN SOUND

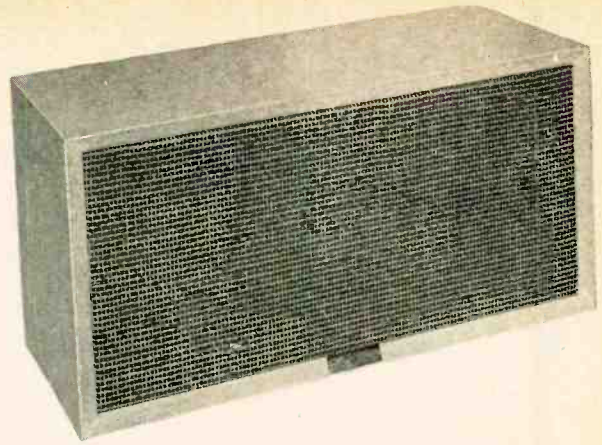

After two years of research and development a speaker system we can unconditionally guarantee to be the finest bookshelf unit ever built for home use that you have heard, REGARDLESS OF PRICE, or your money back.

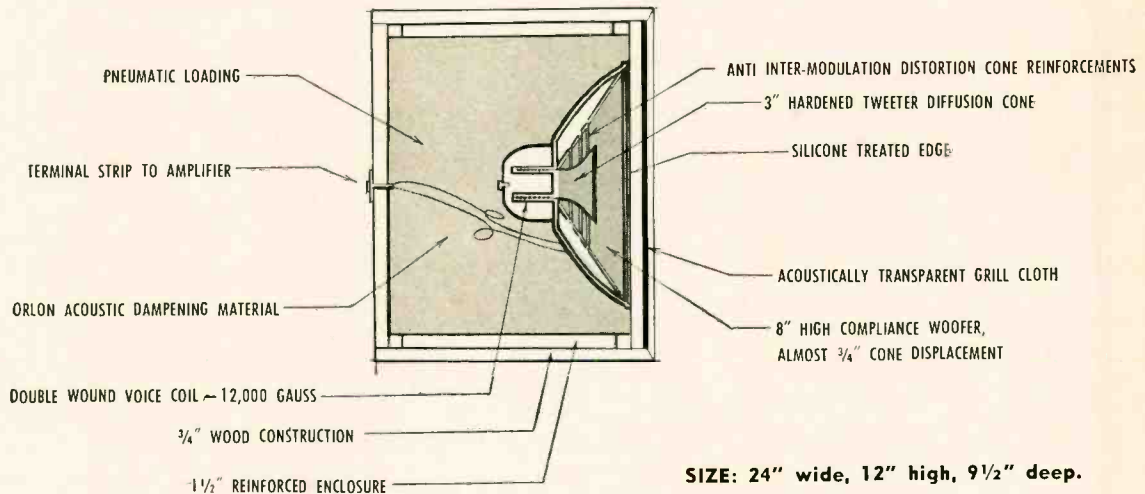Thousands of these gigolos are now in use all over the country. The acceptance has been unbelievable. Never before a sound so realistic to so many people in so many different homes! These are the facts that enable A.E.S. to make this bold offer.



SIZE: 24" wide, 12" high, 9 1/2" deep.

Response: 19-21,000 CPS

This unit will operate at maximum efficiency with amplifiers from 8 to 75 watts.

In limited quantity, and for a limited time only, \$15.00 complete, plus shipping.

PRODUCT RESEARCH & DEVELOPMENT COMPANY CONSUMER PRODUCT REPORT*

A new product recently introduced is the subject of much controversy. It has been this controversy that prompted the Product Research & Development Company to make the following tests and report.

REPORT SUBJECT: A. E. S. GIGOLO

Description: Bookshelf type speaker system. Size, 24" wide, 12" high, and 9 1/2" deep, which places the Gigolo among the few true bookshelf speakers. Cabinet construction is unusually heavy and well reinforced. Its weight is 23 lbs. Visual inspection showed care in assembly, with tightly sealed front and back. Cabinet was expertly sanded and ready for finishing. The grill material is of the plastic, acoustically transparent type, neutral in color and acceptable in style. Our first impression was that the manufacturer's efforts were directed to sound reproduction only, with little regard for furniture finish or style. But, some of the do-it-yourself finishing kits on the market will help rectify this situation. The wood product used throughout the cabinet is of a new type and differs from the usual plywood construction. The completely sealed enclosure is filled with spun orlon, which in our opinion will not only do a better job of dampening than fiberglass but also will eliminate the possibility of glass particles finding their way to the speaker voice coil. A real first—Good thinking A.E.S. The reproducing unit is an eight inch high compliance silicone treated woofer, with an exceptionally long-throw double wound voice coil. This speaker is also equipped with a hardened high frequency reproducing cone . . .

Listening Test. This was the most enlightening part of our test. To exploit the manufacturer's claim of efficiency and power handling capacity, we went to the extreme of using a six transistor

radio as a sound source. We found it had sufficient power to drive the A.E.S. Gigolo to a good listening level. What makes this simple experiment so remarkable is that the balance of this test was completed by using a Scott model 272-88 watt stereo amplifier . . .

The manufacturer's claim of frequency response from 19 cps to 21 KC cannot be disputed from the standpoint of response only. But the test indicated that this was not a flat reproduction. However, we would like to point out that in group listening tests the Gigolo was repeatedly picked out from other bookshelf speakers ranging from \$49.00 to over \$200.00, to have the liveliest and a most realistic performance. These unusual reactions (considering price) may be somewhat explained by the fact that the Gigolo seemed to be the more efficient and to have the most midrange presence of the units tested.

Summary: Without a doubt there are available speaker systems with specifications better than the A.E.S. Gigolo. But, at a selling price of fifteen dollars (\$15.00) this unit offered by A.E.S. Inc., 3338 Payne Avenue, Cleveland 14, Ohio, is, in our opinion, the best value ever offered to the audio market.

In conclusion it is the opinion of our marketing analyst that the manufacturer's cost of the Gigolo exceeds the present selling price of fifteen dollars (\$15.00). Look for a price increase in the very near future. PRD.

ORDER BLANK

A.E.S., Inc.
3338 Payne Avenue, Cleveland, Ohio

Gentlemen: please ship.....GIGOLOS.

I understand these units are guaranteed and if I am not satisfied I may return for a full refund of sales price, \$15.00 each.

Name.....


Address.....

City and State.....

Enclosed find check.....money order.....

*Reprinted with permission of Product Research & Development Co., subsidiary of A.E.S.

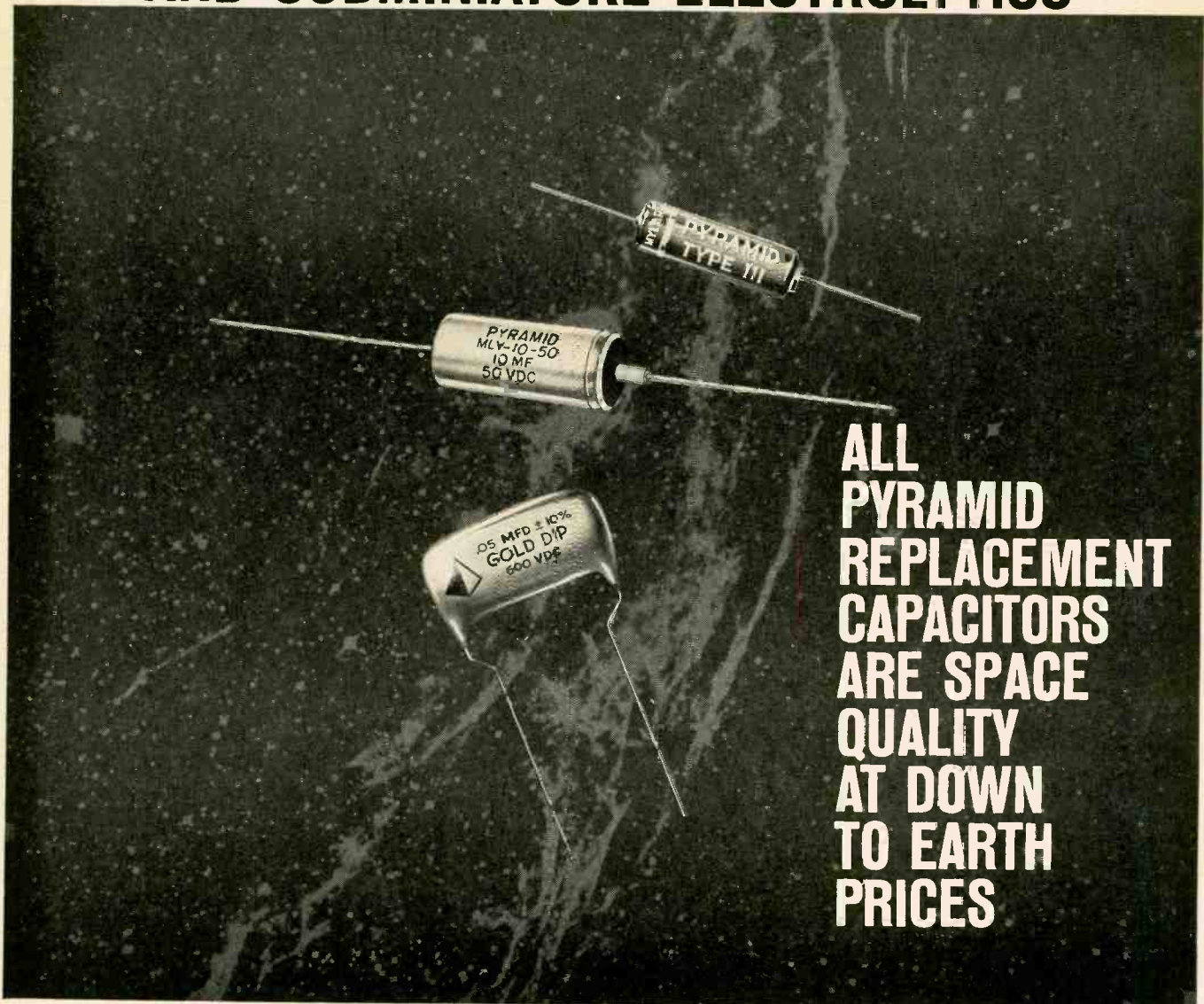DIPPED AND MOLDED MYLAR* CAPACITORS AND SUBMINIATURE ELECTROLYTICS



**ALL
PYRAMID
REPLACEMENT
CAPACITORS
ARE SPACE
QUALITY
AT DOWN
TO EARTH
PRICES**

Pyramid makes the capacitors you want for replacement. Every type of Pyramid capacitor is manufactured under the most rigid standards to insure their high reliability and long life. You can depend on them.

MOLDED MYLAR

Type 111 "Gold Standard" Molded Mylar Capacitors are now available in greatly reduced sizes. They have a noninductive polyester film extended foil section, and are molded in a nonflammable thermosetting plastic case. These capacitors have very high insulation resistance, are impervious to moisture and are extremely rugged. Operating temperature range: -55°C to $+100^{\circ}\text{C}$.

SUBMINIATURE ELECTROLYTICS

MLV Miniature Electrolytic Capacitors are ideally suited for transistorized radio receivers, hearing aids, portable TV sets, and miniaturized circuit requirements. These capacitors are noted for low leakage and a long shelf and operating life. They are designed for 85°C operation.

DIPPED MYLAR


Type 151 Gold-Dip Mylar capacitors are designed to be used for printed board circuitry as well as conventional applications. They are engineered for the highest reliability, are moisture resistant and have high insulation resistance.

Operating temperature range: -55°C to $+110^{\circ}\text{C}$. Look for them on Pyramid's new Whirl-o-mat, five to a package, in Clear-Vu paks.

*GUL POINT™

PYRAMID ELECTRIC COMPANY
DARLINGTON, SOUTH CAROLINA

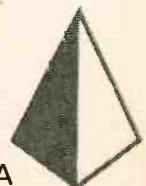Canada: Wm. Cohen, Limited, 8900 Tanguay Street, Montreal
Export: Morhan Exporting Co., 485 Broadway, New York 13, N.Y.



What Does F. C. C. Mean To You?

What is the F. C. C.?

F. C. C. stands for Federal Communications Commission. This is an agency of the Federal Government, created by Congress to regulate all wire and radio communication and radio and television broadcasting in the United States.

What is an F. C. C. Operator License?

The F. C. C. requires that only qualified persons be allowed to install, maintain, and operate electronic communications equipment, including radio and television broadcast transmitters. To determine who is qualified to take on such responsibility, the F. C. C. gives technical examinations. Operator licenses are awarded to those who pass these examinations. There are different types and classes of operator licenses, based on the type and difficulty of the examination passed.

What are the Different Types of Operator Licenses?

The F. C. C. grants three different types (or groups) of operator licenses—commercial radiotelePHONE, commercial radioteleGRAPH, and amateur.

COMMERCIAL RADIOTELEPHONE operator licenses are those required of technicians and engineers responsible for the proper operation of electronic equipment involved in the transmission of voice, music, or pictures. For example, a person who installs or maintains two-way mobile radio systems or radio and television broadcast equipment must hold a radiotelePHONE license. (A knowledge of Morse code is NOT required to obtain such a license.)

COMMERCIAL RADIOTELEGRAPH operator licenses are those required of the operators and maintenance men working with communications equipment which involves the use of Morse code. For example, a radio operator on board a merchant ship must hold a radioteleGRAPH license. (The ability to send and receive Morse is required to obtain such a license.)

AMATEUR operator licenses are those required of radio "hams"—people who are radio hobbyists and experimenters. (A knowledge of Morse code is necessary to be a "ham".)

What are the Different Classes of RadiotelePHONE licenses?

Each type (or group) of license is divided into different classes. There are three classes of radiotelePHONE licenses, as follows:

(1) Third Class RadiotelePHONE License. No previous license or on-the-job experience is required to qualify for the examination for this license. The examination consists of F. C. C. Elements I and II covering radio laws, F. C. C. regulations, and basic operating practices.

(2) Second Class RadiotelePHONE License. No on-the-job experience is required for this examination. However, the applicant must have already passed examination Elements I and II. The second class radiotelePHONE examination consists of F. C. C. Element III. It is mostly technical and covers basic radiotelePHONE theory (including electrical calculations), vacuum tubes, transistors, amplifiers, oscillators, power supplies, amplitude modulation, frequency modulation, measuring instruments, transmitters, receivers, antennas and transmission lines, etc.

(3) First Class RadiotelePHONE License. No on-the-job experience is required to qualify for this examination. However, the applicant must have already passed examination Elements I, II, and III. (If the applicant wishes, he may take all four elements at the same sitting, but this is

not the general practice.) The first class radiotelePHONE examination consists of F. C. C. Element IV. It is mostly technical covering advanced radiotelePHONE theory and basic television theory. This examination covers generally the same subject matter as the second class examination, but the questions are more difficult and involve more mathematics.

Which License Qualifies for Which Jobs?

The THIRD CLASS radiotelePHONE license is of value primarily in that it qualifies you to take the second class examination. The scope of authority covered by a third class license is extremely limited.

The SECOND CLASS radiotelePHONE license qualifies you to install, maintain, and operate most all radiotelePHONE equipment except commercial broadcast station equipment.

The FIRST CLASS radiotelePHONE license qualifies you to install, maintain, and operate every type of radiotelePHONE equipment (except amateur, of course) including all radio and television stations in the United States, and in its Territories and Possessions. This is the highest class of radiotelePHONE license available.

How Long Does it Take to Prepare for F. C. C. Exams?

The time required to prepare for FCC examinations naturally varies with the individual, depending on his background and aptitude. Grantham training prepares the student to pass FCC exams in a minimum of time.

In the Grantham correspondence course, the average beginner should prepare for his second class radiotelePHONE license after from 200 to 250 hours of study. This same student should then prepare for his first class license in approximately 75 additional hours of study.

In the Grantham resident course, the time normally required to complete the course and get your license is as follows:

In the DAY course (5 days a week) you should get your second class license at the end of the first 9 weeks of classes, and your first class license at the end of 3 additional weeks of classes. This makes a total of 12 weeks (just a little less than 3 months) required to cover the whole course, from "scratch" through first class.

In the EVENING course (3 nights a week) you should get your second class license at the end of the 15th week of classes and your first class license at the end of 5 additional weeks of classes. This makes a total of less than 5 months required to cover the whole course, from "scratch" through first class, in the evening course.

HERE'S PROOF that Grantham Students prepare for F. C. C. examinations in a minimum of time. Here is a list of a few of our recent graduates, the class of license they got, and how long it took them:

	License	Weeks
Hugh J. Stock, Box 446, Lander, Wyo.	1st	11
Orlie W. McCool, 414 W. South St., Neosho, Mo.	1st	12
Eugene R. Kraus, Moore Drive, Peru, N. Y.	1st	12
Robert E. Sullivan, 2475 E. Douglas, Des Moines, Iowa	1st	12
Jack Hughes, 101 4th Street, Sebring, Fla.	1st	22
Dennis K. Bingaman, R. D. #1, Dalmatia, Penna.	1st	14
Earl Howard Tolley, RR #3, Eaton, Ohio	1st	11
Victor B. Arroyo, 3633 Gangel Ave., Pico Rivera, Calif.	1st	20
Henry N. Wright, 160 Cedar Street, Springfield, Mass.	1st	12

Resident Classes Offered at Four Locations

To better serve our many students throughout the nation, Grantham School of Electronics maintains four separate schools—located in Hollywood, Seattle, Kansas City, and Washington, D. C.—all offering the same resident courses in F. C. C. license preparation. (Correspondence courses are conducted from Hollywood.)

The Grantham course is designed specifically to prepare you to pass FCC examinations. All the instruction is presented with the FCC examinations in mind. In every lesson test and pre-examination you are given constant practice in answering FCC-type questions, presented in the same manner as the questions you will have to answer on your FCC examinations.

Why Choose Grantham Training?

The Grantham Communications Electronics Course is planned primarily to lead to an F. C. C. license, but it does this by TEACHING electronics. This course can prepare you quickly to pass F. C. C. examinations because it presents the necessary principles of electronics in a simple "easy to grasp" manner. Each new idea is tied in with familiar ideas. Each new principle is presented first in simple, everyday language. Then after you understand the "what and why" of a certain principle, you are taught the technical language associated with that principle. You learn more electronics in less time, because we make the subject easy and interesting.

Is the Grantham Course a "Memory Course"?

No doubt you've heard rumors about "memory courses" or "cram courses" offering "all the exact FCC questions". Ask anyone who has an FCC license if the necessary material can be memorized. Even if you had the exact exam questions and answers, it would be much more difficult to memorize this "meaningless" material than to learn to understand the subject. Choose the school that teaches you to thoroughly understand—choose Grantham School of Electronics.

Is the Grantham Course Merely a "Coaching Service"?

Some schools and individuals offer a "coaching service" in FCC license preparation. The weakness of the "coaching service" method is that it presumes the student already has a knowledge of technical radio and approaches the subject on a "question and answer" basis. On the other hand, the Grantham course "begins at the beginning" and progresses in logical order from one point to another. Every subject is covered simply and in detail. The emphasis is on making the subject easy to understand. With each lesson, you receive an FCC-type test so you can discover daily just which points you do not understand and clear them up as you go along.

For further details concerning F. C. C. licenses and our training, send for our FREE booklet, "Careers in Electronics". Clip the coupon below and mail it to the School nearest you.

Get your First Class Commercial F. C. C. License Quickly by training at



GRANTHAM SCHOOL OF ELECTRONICS

1505 N. Western Ave. 408 Marion Street 3123 Gillham Road 821 - 19th Street, N.W.
Hollywood 27, Calif. Seattle 4, Wash. Kansas City 9, Mo. Washington 6, D.C.
(Phone: HO 7-7727) (Phone: MA 2-7227) (Phone: JE 1-6320) (Phone: ST 3-3614)

MAIL COUPON NOW—NO SALESMAN WILL CALL →

MAIL COUPON TO SCHOOL NEAREST YOU

(Mail in envelope or paste on postal card)

To: **GRANTHAM SCHOOL OF ELECTRONICS**
1505 N. Western 408 Marion 3123 Gillham Rd. 821-19th, NW
Hollywood Seattle Kansas City Washington

Please send me your free booklet telling how I can get my commercial F. C. C. license quickly. I understand there is no obligation and no salesman will call.

Name _____ Age _____
Address _____
City _____ State _____

I am interested in: Home Study, Seattle classes
 Hollywood classes, Kansas City classes, Washington classes

Two outstanding products by the HIDDEN

500*

who plan for your future:



DIFILM[®] BLACK BEAUTY[®] CAPACITORS
molded tubular



DIFILM[®] ORANGE DROP[®] CAPACITORS
dipped tubular

TWO GREAT TUBULARS . . . TAKE YOUR CHOICE!

(±10% Capacitance Tolerance is standard at no extra cost)

- Sprague Difilm Capacitors can't be beat! Dual-dielectric construction combines the best features of both Mylar[®] polyester film and special capacitor tissue. And for additional reliability, Difilm capacitors are impregnated with Sprague's HCX[®], a solid impregnant which produces a rock-hard capacitor section—there's no wax to drip, no oil to leak!
- **BLACK BEAUTY Molded Tubulars** are actually low-cost versions of the famous Sprague high-reliability capacitors used in modern military missiles. They're engineered to withstand 105°C (221°F) temperatures . . . even in the most humid climates! And their tough, molded phenolic cases can't be damaged in handling or soldering.
- **ORANGE DROP Dipped Tubulars** are the perfect replacement for radial-lead capacitors now used by leading manufacturers of TV sets. Leads are crimped for neat mounting on printed wiring boards. Extremely small in size, they'll fit anywhere, work anywhere. And they're double-dipped in epoxy resin for extra protection against moisture.

*The "Hidden 500" are Sprague's 500 experienced researchers who staff the **largest research organization in the electronic component industry** and who back up the efforts of some 7,000 Sprague employees working in 14 manufacturing operations—four at North Adams, Mass.; Bennington and Barre, Vt.; Concord and Nashua, N. H.; Lansing, N. C.; Grafton, Wis.; Visalia, Calif.; two at Ponce, Puerto Rico; and Milan, Italy.



WORLD'S LARGEST CAPACITOR MANUFACTURER

FREE!

LAFAYETTE'S 1961 CATALOG

324 GIANT SIZED PAGES

The Complete Catalog Featuring
"The Best Buys In The Business"

- Stereophonic Hi-Fi Equipment
- Public Address Systems
- Tape Recorders
- Radio and TV Tubes and Parts
- Citizen Band Equipment
- Amateur Equipment
- Industrial Supplies

Send for Lafayette's FREE Catalog—the most complete, up-to-the-minute electronic supply catalog crammed full of everything in electronics at our customary down-to-earth money-saving prices.

CONTAINS HUNDREDS OF EXCLUSIVE LAFAYETTE ITEMS NOT AVAILABLE IN ANY OTHER CATALOG OR FROM ANY OTHER SOURCE—SEND FOR YOUR COPY NOW!

A "must" for the economy-minded hi-fi enthusiast, experimenter, hobbyist, engineer, technician, student, serviceman and dealer.



Our 40th Year

EASY PAY PLAN—the simplest, and quickest way to get what you want when you want it. As little as \$2 down . . . up to 24 months to pay.

NEW!

29.95

2.00 Down



RK-125 Transistorized Portable
Tape Recorder with Built-In Speaker

19.95



TE-15
Tube
Checker

99.50

5.00 Down



HE-20 Deluxe Citizens
Band Transceiver

13.50



RW-60 20,000 Ohms Per Volt Multitester

KT-200, Kit

64.50

5.00
Down



HE-1G, Wired

79.95

5.00
Down

Communications Receiver

49.95

2.00 Down



Two for

96.50

5.00 Down

NEW!

"Walkie-Talkie"
HE-29
9-Transistor Portable Citizens Band

Mail the coupon today for your FREE copy of
Lafayette Radio's 1961 Catalog.

LAFAYETTE RADIO

165-08 LIBERTY AVENUE, JAMAICA 33, N. Y.

OTHER LOCATIONS

NEW YORK 13, N.Y.	BRONX 58, N.Y.	NEWARK 2, N.J.
PLAINFIELD, N.J.	PARAMUS, N.J.	BOSTON 10, MASS

FREE!




LAFAYETTE RADIO
Dept. JC-1, P.O. Box 190
Jamaica 31, N. Y.

Send me the FREE Lafayette 324 page
1961 catalog 610

Name _____

Address _____

City _____ Zone _____ State _____

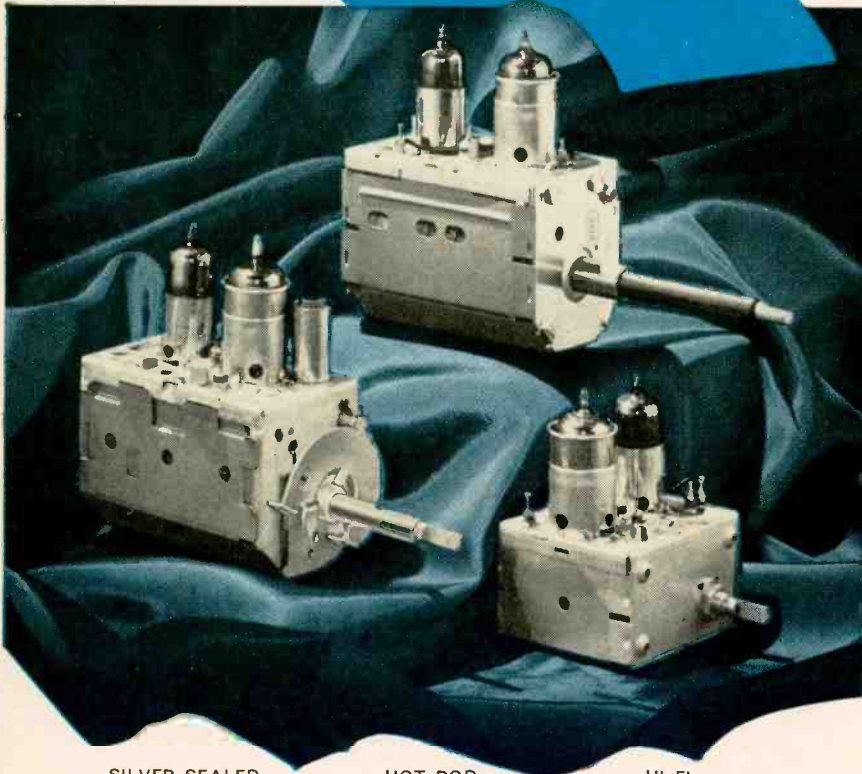

SILVER SEALED
(switch-type)

HOT ROD
(turret-type)

HI FI
(FM) Tuner

Throughout the industry, the trouble-free TARZIAN TUNERS are winning praise for meritorious achievement.

No other commercial unit possesses so many of the desirable features found in the TARZIAN TUNER which is recognized as "the world's finest tuner for the world's finest sets."

Today, TARZIAN is the only commercial manufacturer offering the HOT ROD (turret-type) and SILVER SEALED (switch-type) . . . as well as the Hi Fi FM Tuner. All with built-in HIGH QUALITY . . . DEPENDABILITY . . . and EXCELLENT PERFORMANCE at LOW COST.



For more information, write to: Sales Department, Tuner Division

SARKES TARZIAN INC

east hillside drive • bloomington, indiana

Manufacturers of TV and FM Tuners • Closed Circuit TV Systems
• Broadcast Equipment • Air Trimmers • Magnetic Tape • Semiconductors

Correspondence




LOW-VOLTAGE CAPACITORS

Dear Editor:

I note the article on Centralab's Ultra-Kap ceramic capacitors which appears on pages 60 and 61 of your January issue. These are reduced barium titanate ceramics. They are made and sold by Sprague under the trademark Hypercon.

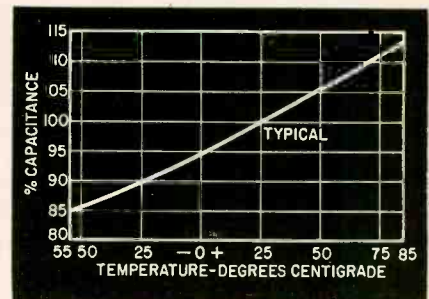Although your article states that such capacitors are not made at voltages above 10 volts, we regularly produce 12-volt capacitors for the original equipment manufacturer market. Further, we are furnishing 20-volt capacitors



consisting of two 10-volt discs stacked in series to some set manufacturers.

Our *Engineering Bulletin No. 6141A* lists our current catalog designs for the single-disc 3- and 12-volt units. The curve of capacitance with temperature might be of particular interest to your readers. The one for the 3-volt units is shown.


The new Sprague Transfarad Capacitor Analyzer, which is intended specifically for transistorized electronic equipment, does make it possible to measure quickly leakage currents in reduced barium titanate capacitors such as our Hypercon series or the Centralab Ultra-Kap series.

SIDNEY L. CHERTOK
Sprague Electric Co.
North Adams, Mass.

IT ISN'T SO!

Dear Editor:

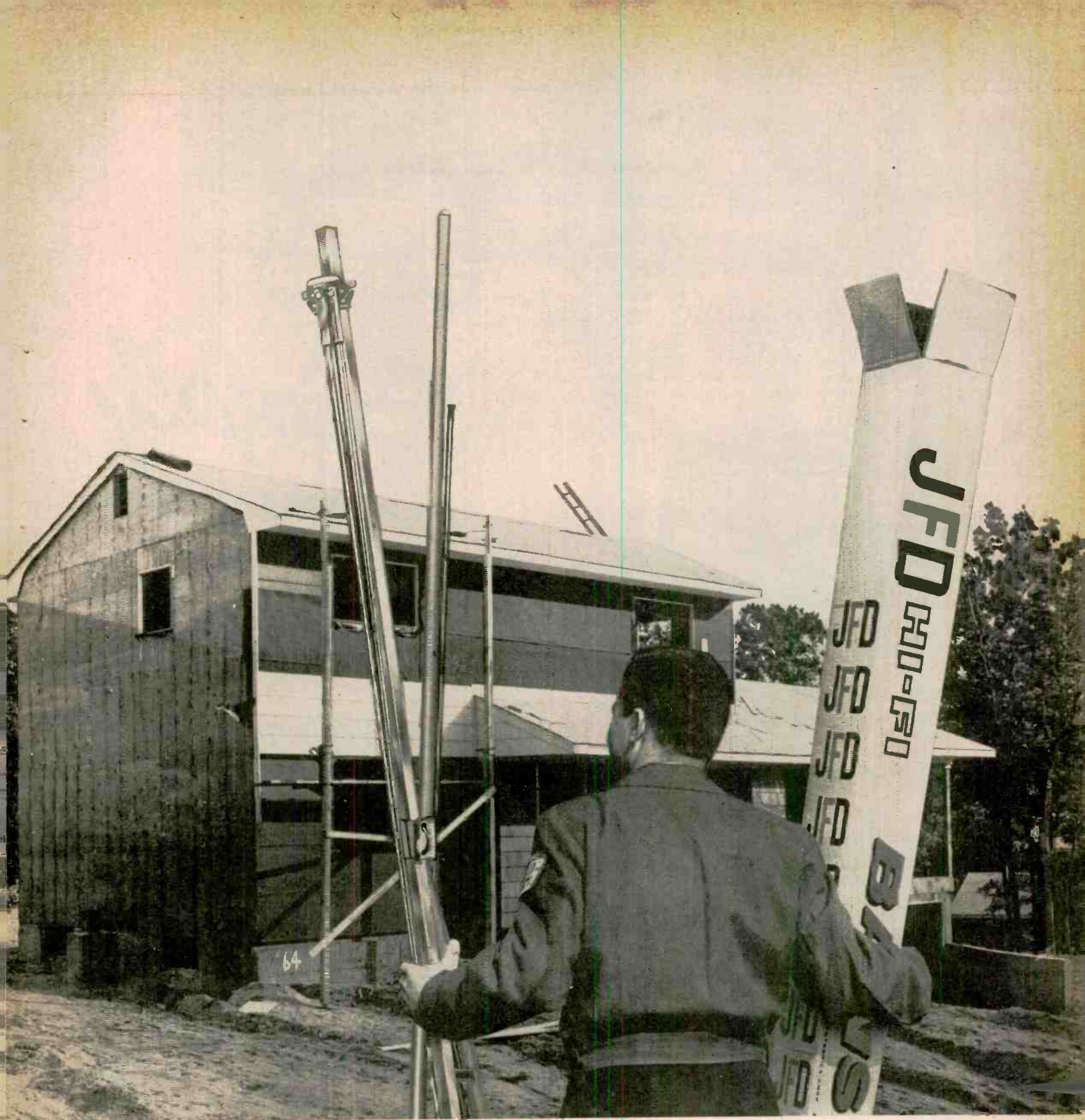I would like to take issue with Jack Darr's statement that the eight types of balun coils shown in the December, 1960, article on tuner input coils would replace 95% of the coils in modern tuners. Although the illustrated coils are fairly popular ones, I doubt that they would even replace one-third of the coils in currently used tuners. As
(Continued on page 22)




The Businessman in the Serviceman suit knows 1,400,000 new houses* mean unlimited opportunities in new antenna installations. He intends to get his share of this profitable business. His antenna brand? . . . JFD, of course—for performance that delights his customers and confirms their confidence in his technical ability.



HI-FI HELIX



HI-FI BANSHEE

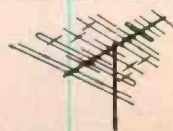

HI-FI FIREBALL

THE BRAND T-AT PUTS YOU

JFD

IN COMMAND OF THE MARKET

JFD ELECTRONICS CORPORATION
BROOKLYN 4, NEW YORK

*Source - American Builder

American Motel MAGAZINE

SURVEY on TELEVISION in MOTELS reports...



FACT: More

JERROLD

TV Master Antenna Systems Have Been Installed Than The Next 4 Makes Combined!

While the survey shows a tremendous acceptance of Master Antenna Systems—56% of the Motel operators report having one—there is still an overwhelming segment of the market yet to be sold! And construction of new Motels—new markets—is progressing at a faster-than-ever pace!

Look to Jerrold—the leader in Master TV Antenna Systems—to help you get your share of this profitable business. The top portion of this advertisement is now appearing in AMERICAN MOTEL MAGAZINE . . . doing a strong "pre-selling" job on *your* Motel prospects!

And remember—your trained Jerrold distributor is always ready to show you how to plan and install Master Antenna Systems quickly, easily, profitably.

Yes, look to Jerrold—the world's largest manufacturer of TV distribution systems and equipment. It's the profitable thing to do!

FREE! Valuable Installation Handbook . . .



A complete "How-to-do-it" manual—normally selling for \$1—that covers almost every conceivable type of installation. Included are 150 typical system layouts in detail.

Jerrold Electronics Corporation
Distributor Sales Division
Dept. Ids-124, Philadelphia 32, Pa.

Gentlemen:
Please send me the "TV Distribution Handbook." I am enclosing 25c to cover handling costs and postage.

Name _____
Firm _____
Address _____
City _____ Zone _____ State _____

JERROLD

ELECTRONICS CORPORATION, Phila. 32, Pa.

Jerrold Electronics (Canada) Ltd., Toronto

Export Representative: CBS International, New York 22, N.Y.

there be any trouble within 24 hours after delivery, there is no charge for labor or parts, *if it was the part we replaced*. For the next 10 days, if the customer calls us for service, we make the minimum service charge plus parts (no parts charge if any of the parts installed by us break down). Up to 90 days, should any part we install go bad, we make a minimum service charge. After 90 days, full rates go into effect.

All this is explained to the customer. Furthermore, we tell the customer, whenever we pull the chassis, that we have a flat rate shop charge. We *do not* give an estimate, only our labor charges.

After all of this, we ask the party to sign an Authorization Sheet so we may proceed with the repair of his set. This Authorization Sheet contains two pertinent facts according to law in this state. (1) The party shall pay *cash* for all work done upon delivery. (2) The party allows the technician to retain the right to all parts entered in the set, according to the invoice, and that, the repairman may enter his premises at any time during the day to retain possession of said parts if the bill is not paid.

When the customer calls, he is told that all services are for cash only.

We have had many instances of invoices reading: Parts \$00.35, Labor \$16.00, Total \$16.35 plus State Tax.

Our customers do not complain about this for they appreciate our honesty.

HENRY NAKAZATO


Kailua, Oahu, Hawaii

[Sounds like an interesting approach. Offers the customer a little more than just a warranty on the work done. Assures him of some protection (cost-wise) if his set should fail again within a short period of time. Any other customer relation ideas?—*Editor*]

TOPLESS JARS

Dear Editor:

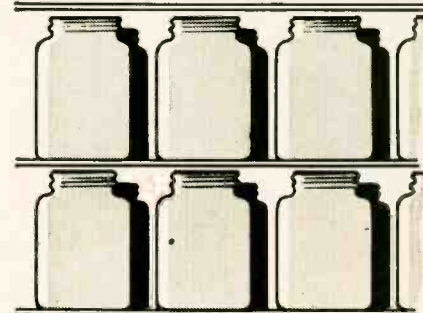I would like to offer a delayed comment on an article by Henry J. Miller in the May, 1960, issue, page 88. Mr. Miller uses a large number of screw-cap jars to store small parts. It would save him and possibly some RADIO-



ELECTRONICS readers a considerable amount of time and patience if the shelves were spaced a little closer to the jar tops (see diagram). Such a close fit would let the user keep the jar open and still dust-free, and make it a lot easier to get parts in and out when desired.

L. H. BROWN

Abingdon, Berks, England

END

RADIO-ELECTRONICS

Learn RADIO, TELEVISION AND ELECTRONICS by Practicing at Home in Your Spare Time

At No Extra Cost you get specially developed Electronic Training Kits for practical experience. Shop and laboratory practice at home make learning easier, interesting, faster. You do not need a high school diploma or previous experience.

Increasing Demand for Trained Men

This is the Electronics age. Men with Electronic know-how are in demand. They enjoy high pay and growing opportunities for advancement. Satellites, Radar, Automation in Industry, Missiles, Rockets, Planes, Stereo, TV, Radio, Two



Way Communications for transportation are a few of the fantastic developments in the fast growing Electronics industry. If you are not completely satisfied with your work; if you are doubtful about your future, investigate Electronics.

High Pay, Prestige, Bright Future

What branch of Electronics interests you? Thousands of successful NRI graduates prove that NRI's learn-by-practice method is the way to success. You start in your chosen career 'way ahead of the man who only learns from books. You do not need to give up your job. You do not need to go away to school. You learn at home, get practical knowledge from training kits NRI provides.




Train With the Leader

NRI is the world's oldest and largest home study Electronics school. You benefit from the experience NRI has gained from training men for 45 years. NRI offers you proven courses of home study in Electronics; Principles, Practices and Maintenance—Radio Television Communications—Radio Television Servicing.

Start Soon to Earn More

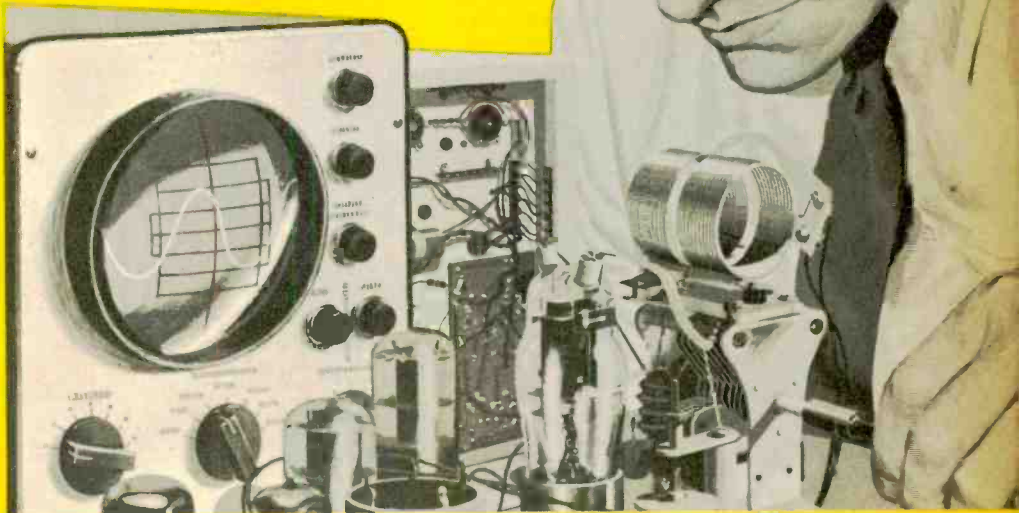Soon after enrolling NRI shows you how to apply your knowledge to earn extra money doing Electronics repairs or servicing Radio and Television sets for friends and neighbors. Take the first step toward success now. Find out what NRI offers you. Mail the postage-free card. No obligation. Cost of NRI training is low. Monthly payment plan available. NATIONAL RADIO INSTITUTE, Washington 16, D.C.



NRI Has Trained Thousands for Success



"I get over twice the salary I made before enrolling. NRI training gave me a thorough understanding." H. ATKINSON, Austin, Tex.



"I started with station CJIC, now in charge of sound effects for CBC. NRI opened doors to greater opportunity for me." F. W. TUDOR, Toronto, Ontario



"Averaged \$150 a month spare time before I graduated. Now have my own full time business and employ 2 men." F. W. COX, Hollywood, Cal.

NEW COURSE IN ELECTRONICS TURN PAGE

Cut Out and Mail—No Stamp Needed

64-PAGE CATALOG FREE


No Salesman will call. (Please PRINT) Z

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

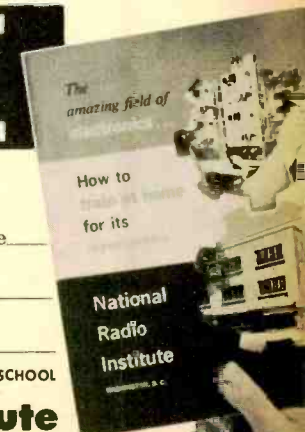OLDEST & LARGEST HOME STUDY RADIO-TV SCHOOL
National Radio Institute
WASHINGTON 16, D. C.
ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL





JOB COUNSELORS ADVISE LEARN ELECTRONICS

NEW Home Study Course in **ELECTRONICS** Principles-Practices-Maintenance **NOW READY**

This is the Electronic Age. Electronic equipment is already being used to count and control flow of liquids, solids, gases. Electronics is employed to search for oil, make surveys, control traffic, machine complex parts and in atomic installations. Military uses of Electronics are great and expanding rapidly. In business, Automation with Electronics plays an important part, prepares payrolls, calculates engineering formulas.

Learn More to Earn More

Now, to meet the growing demand for trained Electronic Technicians NRI has developed a comprehensive, complete course in Electronics Principles, Practices, Maintenance. This training stresses fundamentals. It is a course specially prepared for beginners and for Technicians. You get both theory and practical experience in an interesting, exciting way.

Ten Special Training Kits Give Practical Experience

You get practical experience with Thyatron Tube circuits, Multivibrators, build a D'Arsonval type Vacuum Tube Voltmeter (Kit 2); work and experiment with pentode tubes, selenium resistors, oscillators, transistors, magnetic amplifiers; and get practical experience in telemetry circuits as used in earth satellites, digital and analog computers (Kit 9).

NRI—Oldest and Largest School

Wishing for success won't bring success. You must act. Get FREE 64-page Catalog from America's oldest and largest home study Electronic-Radio-Television school. It gives facts, opportunities in Industrial and Military Electronics careers, also shows what you learn, tells about NRI's other courses in Radio Television Servicing and Radio Television Communications. Monthly payments plan. Mail Postage Free Card for 64-page Catalog.

NATIONAL RADIO INSTITUTE, Washington 16, D.C.



PRACTICE WITH
17" TV RECEIVER

PRACTICE WITH
LOW POWER TRANSMITTER

PRACTICE WITH ULTRA
HIGH FREQUENCY OSCILLATOR

SPECIAL TRAINING KITS NO EXTRA COST

PRACTICE WITH
D'ARSONVAL TYPE VOLTMETER

PRACTICE WITH
AC-DC RECEIVER

SEE OTHER SIDE

FIRST CLASS

Permit No. 20-R

(Sec. 34.9, P. L. & R.)

Washington, D.C.

BUSINESS REPLY CARD

No Postage Stamp Necessary if Mailed in the United States

POSTAGE WILL BE PAID BY

National Radio Institute

3939 Wisconsin Avenue

Washington 16, D.C.

**POSTAGE FREE CARD
MAIL NOW**

new LITERATURE

Any or all of these catalogs, bulletins, or periodicals are available to you on request direct to the manufacturers, whose addresses are listed at the end of each item. Use your letterhead—do not use postcards. To facilitate identification, mention the issue and page of RADIO-ELECTRONICS on which the item appears. UNLESS OTHERWISE STATED, ALL ITEMS ARE GRATIS. ALL LITERATURE OFFERS ARE VOID AFTER SIX MONTHS.

SPEAKER SYSTEM CATALOG describes systems in detail and includes specifications, enclosures and photos for each. Full page of components.—R. T. Bozak Sales Co., Box 1166, Darien, Conn.

SPEAKERS, KITS AND ACCESSORIES in 8-page catalog graphically illustrating manufacturer's line with accompanying detailed specifications for each unit.—Oxford Components, 556 W. Monroe St., Chicago 6, Ill.

COMPONENTS Catalog S600 supplements previously issued *W600*. Lists manufacturer's new product additions in complete detail.—Cambridge Thermionic Corp., 445 Concord Ave., Cambridge 38, Mass.

STANDOFF FASTENERS for supporting tubing, wire bundles, conduit, equipment and instruments are covered in new illustrated 20-page booklet, *What You Should Know About Standoff Fasteners*.—Western Sky Industries, 21301 Cloud Way, Hayward, Calif.

RADIO ELECTRONIC MASTER, 25th edition, silver anniversary number. More than 175,000 items, their specifications and prices featured in its 1,600 pages. Over 12,000 illustrations. Pinpoint index.—United Catalog Publishers, Inc., 60 Madison Ave., Hempstead, N. Y. See your distributor for price.

POTENTIOMETER FOLDER, Buyers and Engineers Guide to *Squaretrim Potentiometers*. Outlines complete details of the functions, specifications and ratings of these subminiature units in quick-reference, tabular form. 4 illustrated pages.—Schweber Electronics, 60 Herricks Rd., Mineola, N. Y.

SEMICONDUCTOR CHART lists more than 4,000 types and their 38 manufacturers. 12 new companies included. 68 pages. Write for descriptive literature.—United File-O-Matic, 60 Madison Ave., Hempstead, N. Y.

STEREO CARTRIDGE BROCHURE, on model *ADC-1*, gives background information, description and specifications of manufacturer's newest magnetic cartridge, and chart that traces its typical

BREAKTHROUGH IN KIT DESIGN!



LK-72 72-Watt stereo complete amplifier kit (left), \$149.95. LT-10 Wide-Band FM Tuner kit \$89.95.*

H. H. Scott takes totally new approach . . . makes kits easier-to-build, better performing!

BREAKTHROUGH! Here, for the first time, are kits with the performance, features and handsome good looks of H. H. Scott factory-assembled components . . . kits that are a real pleasure to build and so expertly designed that you can achieve professional results in just a few hours.

H. H. Scott assures you the performance of factory-built units with these innovations:

1. All mechanical parts such as terminal strips and tube sockets are firmly pre-riveted to the chassis thus assuring sturdy professional construction and eliminating the bother of this time-consuming operation.
2. Every wire and cable is already cut to exact length and pre-stripped. This saves you time and assures professional performance because exact lead length is automatic.
3. To take the guesswork out of assembly, electronic parts are mounted on special cards in the order in which they are used. No loose bags of parts to confuse you.
4. Full color diagrams in easy-to-follow instruction book simplify assembly and reduce errors because you match the part to the color diagram.

HERE'S WHAT ENTHUSIASTIC OWNERS SAY:

" . . . designed to professional standards; sound absolutely clean; very sensitive; instruction book of outstanding clarity." — Major B. W. Cotton, Jacksonville, Ark.
 "Looked long for the best kit — and found it . . . best instructions I ever saw, unbelievably simple to build." — M. Greenfield, White Plains, N. Y.
 " . . . I would run out of superlatives if I tried to adequately state how I feel about this tuner . . ." — Samuel R. Harover, Jacksonville, Ark.
 " . . . without a doubt the easiest kit I have ever built (out of 11) . . ." — B. P. Loman, Jr., Rochester, N. Y.
 " . . . finest kit I have ever built. And one of the finest tuners I have heard, kit or otherwise." — A. J. Zilker, Houston, Texas.

H. H. SCOTT

H. H. Scott Inc., 111 Powdermill Road
Maynard, Mass. Dept. 570-03

Rush me complete technical specifications on H. H. Scott kits. Include your new "1961 Guide to Custom Stereo."

Name _____

Address _____

City _____ Zone _____ State _____

*Prices slightly higher West of Rockies.

Export: Telesco International Corp., 171 Madison Ave., N.Y.C.

UNMATCHED FOR CONVENIENCE . . .

DUAL HEAT SOLDERING GUN

FOR ONLY
\$7.95
LIST
Model 8200K



... and best of all, it's a

Weller®

Here from Weller, long time leader in the soldering field, is the most practical convenience feature ever offered in a soldering tool.

WELLER DUAL HEAT FEATURE saves time, gives greater convenience and greatly increases tip life. A touch of your finger on the Triggermatic control switches heat to high (125 watts) or low (90 watts) as your job requires. It adapts instantly to varying needs, and you use high heat only when necessary.

HIGH EFFICIENCY WELLERTIP utilizes copper for superior heat transfer and soldering efficiency, plus iron plating for durability. Flat cross-section design gives added strength and rigidity.

MODERN DESIGN with sturdy plastic housing that resists hard knocks. Compact "feel" and comfortable balance aid precision soldering. Like all other Weller guns, this new model features instant heat, and a spotlight illuminates your work.



KIT INCLUDED

In addition to the Dual Heat Soldering Gun you get:

- Nylon Flux Brush
- Soldering Aid for opening old joints, twisting wires
- All-purpose Solder

Other dual heat models available—\$12.95 and \$16.25—up to 275 watts.

WELLER ELECTRIC CORP. • 601 Stone's Crossing Rd., Easton, Pa.

response curve.—Audio Dynamics Corp., 1677 Cody Ave., Ridgewood, N. Y.

TAPE RECORDING HEAD REFERENCE GUIDE, revised, contains information for technician and tape recordist on repair, upgrading or conversion to stereo. Features cross-reference data, specification and illustrations on record/playback and erase heads, 2- and 4-track stereo, 2-track monophonic and ¼-track record/playback units. 16 pages.—Robins Industries Corp., 36-27 Prince St., Flushing 54, N. Y. 50¢.

DEPOSITED-CARBON RESISTORS, their performance and reliability, are the subject of a study that includes data based on testing of more than 37,000 separate units. Over 20 charts and diagrams. Special section deals with resistor selection in equipment design.—International Resistance Co., PO Box 502, Burlington, Iowa.

PHOTOSENSITIVE DEVICES and Cathode-Ray Tubes, CRPD-105B. Sets related technical information up for quick reference. Contents include data for 151 special-purpose industrial tubes.—RCA, Commercial Engineering, Electron Tube Div., Harrison, N. J.

OPTICAL MASER describes theory, design and applications of the recently announced solid-state optical maser. 8-page booklet is reprint of article by Dr. A. L. Schawlow, an inventor of the maser, that appeared in his company's publication.—H. W. Mattson, Bell Telephone Laboratories, Murray Hill, N. J.

REPLACEMENT PARTS for radio, television and electronics indexed by product, type and page for easy reference. 48 pages of descriptions, specifications and illustrations.—International Resistance Co., Distributor Div., 414 N. 13th St., Philadelphia 8, Pa.


MINIATURE IF TRANSFORMER Catalog IF-60 presents more than a hundred ½-inch-square if transformers covering a range from 100 kc to 44.35 mc. Over 40 schematics.—Wells Electronic Co., 1701 S. Main St., South Bend 23, Ind.

TRANSISTOR Application Guides. RCA Silicon Power Transistors, ICE-215, deals with the special features and uses of 16 medium-power, intermediate-power and high-power silicon transistors. *RCA Silicon Vhf Transistors, ICE-228*, describes capabilities of 3 silicon vhf transistors intended for industrial and military applications at frequencies up to 300 megacycles.—RCA Semiconductor & Material Div., Commercial Engineering, Somerville, N. J. 50¢ each.

VIDEO AMPLIFIER Application Note, Video Amplifiers Using the 2N741 Mesa Transistor, makes use of circuit schematics, performance curves and photographs of a completed 10-mc amplifier to describe high-quality video amplifier circuits using low-cost 2N741 mesa transistors.—Motorola Semiconductor Products Inc., 5005 E. McDowell Rd., Phoenix, Ariz.

WIRELESS MICROPHONE SYSTEM described in brochure that also carries specifications of complete line of accessories and illustrates a number of suggested applications.—Vega Electronics Corp., Cupertino, Calif. **END**

*dedicated
to
perfection*

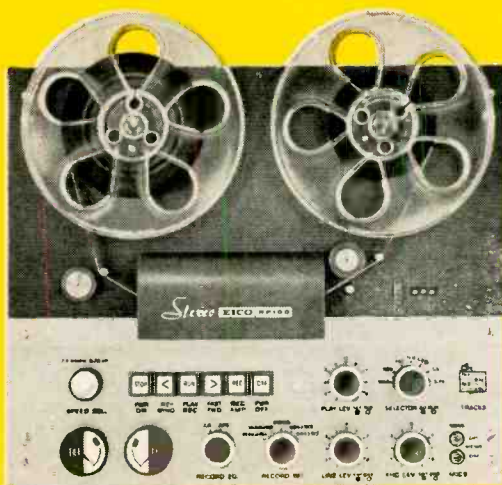

4-TRACK STEREO TAPE DECK

MODEL RP-100W

Completely assembled, wired and tested, \$395.00

MODEL RP-100K

Semi-kit includes a completely assembled and tested transport, electronics in kit form. \$289.95

Perfected 4-track stereo/mono recording, 4 & 2 track playback. True high fidelity transistor electronics, individual for record & playback, plus separate record & playback heads permitting off-the-tape monitor. 2 recording level meters, mixing, mic & level controls, switched sound-on-sound recording. Electro-dynamically braked supply & take-up reel motors; hysteresis synchronous capstan motor, individual solenoids for pinch-roller & tape lifters. All-electric, interlocked push-button transport control & interlocked safety "record" pushbutton. Precision tape guidance & sweep loading — no pressure pads. No slurring or tape bounce problems. Digital turns counter. Vertical or horizontal mounting. Modular plug-in construction. An original, exclusive EICO product designed & manufactured in U. S. A. (patents pending).

NEW MEDALIST LINE



FM-AM STEREO TUNER ST96

Kit \$89.95 Includes Metal Cover and FET Wired \$129.95

FM and AM stereo tuners on one compact chassis. Easy-to-assemble: prewired, prealigned RF and IF stages for AM and FM. Exclusive precision prewired EYE-TRONIC® tuning on both AM and FM.

FM TUNER

Switched AFC (Automatic Frequency Control). Sensitivity: 1.5uv for 20db quieting. Frequency Response: 20-15,000 cps ±1db.

AM TUNER

Switched "wide" and "narrow" bandpass. High Q filter eliminates 10 kc whistle. Sensitivity: 3uv for 1.0V output at 20db S/N ratio. Frequency Response: 20-9,000 cps ("wide"); 20-4,500 cps ("narrow").

OF EICO STEREO



70-WATT INTEGRATED STEREO AMPLIFIER ST70

Kit \$94.95 Includes Metal Cover Wired \$144.95

40-WATT INTEGRATED STEREO AMPLIFIER ST40

Kit \$79.95 Includes Metal Cover Wired \$124.95


BOTH AMPLIFIERS: Complete stereo centers plus two excellent power amplifiers. Accept, control, and amplify signals from any stereo or mono source.

ST70: Cathode-coupled phase inverter circuitry preceded by a direct-coupled voltage amplifier. Harmonic Distortion: less than 1% from 25-20,000 cps within 1db of 70 watts. Frequency Response: ±½ db 10-50,000 cps.

ST40: Highly stable Williamson-type power amplifiers. Harmonic Distortion: less than 1% from 40-20,000 cps within 1 db of 40 watts. Frequency Response: ±½ db 12-25,000 cps.

Over 2 MILLION EICO instruments in use. Most EICO Dealers offer budget terms.

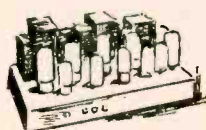There's an EICO for your every stereo/mono need. Send for FREE catalog.



Listen to the EICO Hour, WABC-FM, N. Y. 95.5 MC, Mon.-Fri., 7:15-8 P.M. © 1961 by EICO, 33-00 N. Blvd., L. I. C. 1, N. Y.

EXPORT: Roburn Agencies, Inc., 431 Greenwich St., New York 13, N.Y.



EICO, 3300 N. Blvd., L.I.C. 1, N. Y. C-3
 Send free 32-page catalog & dealer's name
 Send new 36-page Guidebook to HI-FI for which I enclose 25¢ for postage & handling.
 Name
 Address
 City Zone State


Add 5% in West. Turn Page For More EICO Values.



DESIGNED

AS YOU WOULD DESIGN IF YOU WERE AN ELECTRONICS ENGINEER...

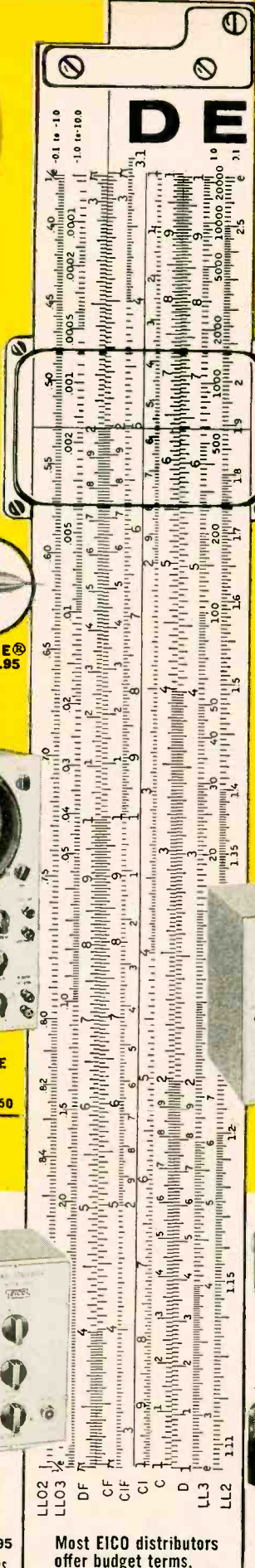Praised by the experts as Best Buys... **EICO**




(A) PEAK-TO-PEAK VTVM #232 & UNI-PROBE® KIT \$29.95 WIRED \$49.95
U. S. Pat. No. 2,790,051



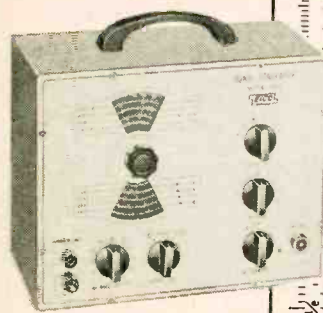(B) COLOR & MONOCHROME DC TO 5 MC LAB & TV 5" OSCILLOSCOPE #460
KIT \$79.95 WIRED \$129.50


Also available:
5" Push-Pull Oscilloscope #425
Kit \$44.95 Wired \$79.95



(C) RF SIGNAL GENERATOR #324
KIT \$26.95 WIRED \$39.95
Turn Page For More EICO Values



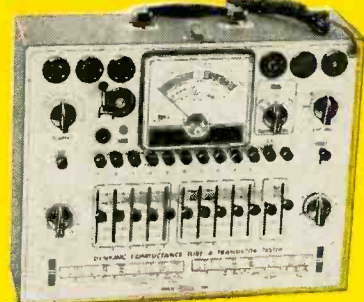(D) TV-FM SWEEP GENERATOR & MARKER #368
KIT \$69.95 WIRED \$119.95



(E) DYNAMIC CONDUCTANCE TUBE & TRANSISTOR TESTER #668
KIT \$69.95 WIRED \$109.95
Complete with steel cover and handle

(A) By far the best professional VTVM value in electronics; nobody but EICO brings you such outstanding instrument performance for so low a price! Calibration without removing from cabinet. Measure directly p-p voltage of complex & sine waves: 0-4, 14, 42, 140, 420, 1400, 4200. DC/RMS sine volts: 0-1.5, 5, 15, 50, 150, 500, 1500 (up to 30,000 volts with HVP probe, & 250 mc with PRF probe). Ohms: 0.2 ohms to 1000 megohms. 4 1/2" meter, can't-burn-out circuit. 7 non-skip ranges on every function. Zero center. Features EICO's exclusive UNI-PROBE: your terrific time-saver, performs all functions: a half turn of probe-tip selects DC or AC-Ohms!

(B) An engineering achievement unmatched in the industry! EICO-designed for laboratory precision and EICO-priced for lowest cost. Features DC amplifiers. Flat from DC to 4.5 mc, usable to 10 mc. Vert. Sens: 25 mv/in.; input 2-3 megohms; direct-coupled & push-pull throughout. 4-step frequency-compensated attenuator up to 1000:1. Sweep: perfectly linear 10 cps-100 kc (ext. cap. for range to 1 cps). Pre-set TV V & H positions. Auto sync limiter & amplifier Direct or C coupling; balanced or unbalanced inputs; edge-lit engraved lucite screen with dimmer control.

(C) More features and versatility, more range and accuracy than in generators costing three to four times as much. 150 kc to 435 mc with DNE generator in 6 fundamental bands and 1 harmonic band! ±1.5% frequency accuracy. Colpitts RF oscillator directly plate-modulated by K-follower for improved modulation. Variable

depth of internal modulation 0-50% by 400 cps Colpitts oscillator. Variable gain external modulation amplifier: only 3 volts needed for 30% mod. Turret-mounted, slug-tuned coils for max. accuracy. Fine & Coarse (3-step) RF attenuators. RF output 100,000 uv, AF output to 10 v.

(D) Provides more ranges, greater ease and accuracy, and better performance than any competitive unit. Entirely electronic sweep circuit with accurately-biased inductor for excellent linearity. Extremely flat RF output. Exceptional tuning accuracy. Hum & leakage eliminated. 5 fundamental sweep ranges: 3-216 mc. Variable marker range: 2-75 mc in 3 fund. bands, 60-225 mc on harmonic band. 4.5 mc crystal marker osc., crystal supplied. Ext. marker provision. Attenuators: Marker Size, RF Fine, RF Coarse (4-step decade). Narrow range phasing control for accurate alignment.

(E) Speedy, simple operation, unexcelled sensitivity and accuracy; superb electrical and mechanical design. Tests all receiving tubes (picture tubes with adapter), n-p-n and p-n-p transistors. Composite indication of Gm, Gp & peak emission. Simultaneous selection of any one of 4 combinations of 3 plate voltages, 3 screen voltages, 3 ranges of continuously variable grid voltage (with 5% accurate pot.). Sensitive 200 ua meter. 10 six-position lever switches: freepoint connection of each tube pin. 10 push-buttons: rapid insert of any tube element in leakage test circuit. Direct reading of inter-element leakage in ohms. New gear-driven rollchart. CRA Adapter \$4.50.



All Transistor Portable RA-6
Kit \$29.95
Wired \$49.95
less battery



Power & Bias Supply for Transistorized Eqpt. #1020
Kit \$19.95
Wired \$27.95



DeLuxe Multi-Signal Tracer #147
Kit \$24.95
Wired \$39.95



Tube Tester #625
Kit \$34.95
Wired \$49.95
Pix Tube Test Adapter \$4.50



6 & 12V Battery Eliminator & Charger #1050
Kit \$29.95
Wired \$38.95
#1060 Kit \$38.95
Wired \$47.95



V-0-M #565
Kit \$24.95
Wired \$29.95
V-0-M #536
Kit \$12.90
Wired \$14.90



R-C Bridge & R-C-L Comparator #950B
Kit \$19.95
Wired \$29.95

Most EICO distributors offer budget terms.

EICO 33-00 Northern Blvd., L. I. C. 1, N. Y. C-3
Show me HOW TO SAVE 50% on Test Instruments
 Hi-Fi Ham Gear. Send me FREE Catalog, name of neighborhood dealer. Send free Short Course for Novice License.

Name.....
Address.....
City..... Zone..... State.....

© 1961 EICO 33-00 N Blvd., L. I. C. 1, N. Y. Add 5% in the West

EXPORT: Roburn Agencies, Inc., 431 Greenwich St., New York 13, N.Y.

ANTI-PLANE-COLLISION RADAR

... *Up-to-Date Aircraft Safety Measures Are Needed Urgently* ...

THE tragic airplane disaster of Dec. 16, last, in which 134 persons were killed as a result of the collision of two airliners over New York, points up anew that present-day safety measures are fundamentally inadequate, particularly near our large metropolitan air centers.

More than 175 planes are often in the air together within a radius of 50 miles over New York City. By 1975, there will be over 350, according to a Federal study recently made.

Modern jets today fly at the rate of 550 miles an hour when cruising at full speed. Two jets on a collision course can thus approach each other at rates up to 1,100 miles per hour, *or over 3 miles in 10 seconds*. Even if the pilots see an oncoming plane, it is doubtful that they can prevent a full head-on or partial collision.

In a few years, jets now on the drawing boards will fly at 1,300 miles cruising speed. How will *they* be handled?

Today, jets approaching our airports must fly at a reduced speed of about 230 miles an hour, and are guided to the proper runway by the technicians of Federal Aviation Agency. The guiding is customarily by radio-phone from ground to plane. The tower operator literally talks the plane down. In an overcast and thick weather, the incoming plane also uses its electronic Instrument Landing System (ILS).

But last Dec. 16, when the two doomed planes were on a collision course and were fully alerted to their danger by ground personnel, one of the planes was some 11 miles off course and completely "blind" in the thick cloud overcast. Hence, even if the pilot did take evasive measures, he could not possibly have known whether he was heading out—or into—the danger course in the thick murk.

The obvious answer to this and similar situations is radar. We have commented on this over the years since 1951.*

After the 1956 two-plane collision over the Grand Canyon that took 128 lives, we said editorially, in our May 1956 issue "*Airplane Collision Control*":

But a plane flies in a three-dimensional medium. Pilots have only a comparatively small angle within which to make visual observations. They cannot look behind them, far sideways or above, or below them at a steep angle in a heavy overcast. Hence the "visual control" is wholly academic and—under certain adverse weather conditions—absurd.

We also quote from our 1951 editorial (before the practical advent of the transistor):

It should be possible in the meanwhile, however, to use a six-way modified—or sweep—radar installation, which need not weigh too much if miniature tubes and other miniature components are used. In this case, too, there would be several miniature screens which pilot or copilot could watch and see if another plane was approaching from any direction. When finally engineered, such a device will prevent many collisions. Such radar installations will be particularly advantageous during night flying and while flying in overcast weather when the visibility is extremely poor or nil.

*"Needed Electronic Inventions," RADIO-ELECTRONICS, May 1951.

What was meant here was two specialized steep angle sweep radars, one on top of the plane, one in the belly. Using two such radars, the pilots are enabled to see in six directions at once: east, west, north, south, below and above.

Weight and space requirements, once a serious handicap for commercial airplane radar, are no longer an insurmountable problem today, thanks to transistors and microminiaturization.

It is quite inexcusable to postpone the adoption of collision radars any longer—neither the cost nor technical difficulty can be given as valid reasons for delay. While radar installation on aircraft may not be a 100% solution and insurance against all collisions, it will certainly do away with a large proportion of midair crashes.

When we speak of radar, we should also mention the fact that not all radars function on radio waves. There is, for instance, the infrared or heat radar developed during the past several years by Aerojet-General Corp. It uses a rapidly rotating mirror which scans the sky for other planes. The mirror is sensitive to infrared heat rays from a distant airplane engine. It has an automatic warning instrument in the cockpit to alert the pilot that he is on a collision course. It also gives the range and bearing of the oncoming plane. Total weight of the new infrared radar is but 30 lb.

How serious the density of our aircraft in the sky is becoming was pointed out recently in a study made by scientists at the University of Michigan's Institute of Science and Technology. One of the scientists, Dr. Gustave Rabson said: "Today more than 109,000 planes use the same air space and many are flying more than 100 miles per hour. By 1975 we can expect aircraft to more than double their present air mileage. . . . We must develop a control system to handle incredibly complicated situations rapidly and safely."

Just what does this mean for the future? It means to us that, by 1975, there probably will be over 200,000 aircraft, a goodly percentage flying at more than 1,000 miles per hour. Midair collisions are bound to get worse unless we take heroic electronic measures on the ground and in the air.

As we see it, radar warnings originating in the plane and from the ground can only be a temporary makeshift—they cannot prevail for long. Man's perception and his reactions are hopelessly slow and far too sluggish for the air and space age.

The collision radar in the future must be wholly automatic—it must steer the plane out of its collision course without benefit of pilot. A warning bell or signal will sound, notifying the pilot that the plane is now under radar control. Likewise, large airliners will no longer be "talked down" by the tower during overcasts or at night. The tower operator—not the pilot—will have total electronic control over the plane during its airport approach and its touchdown. The operation will be watched by a bank of special TV cameras near the runway, via closed-circuit automated television receivers in the tower. The rest of the routine landing operation will be by the pilot.

—H.G.

home-made TUNNEL- DIODE CW transmitter

By
LESTER A. EARNSHAW,
ZL1AAX

**Crystal-controlled transmitter
operates on 3.5 mc, has verified
160-mile range**

PREVIOUS articles in RADIO-ELECTRONICS have shown that the tunnel diode makes an excellent oscillator (September 1960, page 40; October 1960, page 58, and November 1960, page 42). The device will "take off" whenever the correct operating voltage and a suitable tuned circuit are connected to its leads. The only important consideration is the power supply. Although this is usually an unlikely source of trouble, the tunnel diode supply must have a very low output impedance. If the power source impedance is *not* low, the diode is likely to slide from one end of its negative resistance slope to the other, and behave much the same as a flip-flop transistor circuit.

It is a very simple matter indeed to make the tunnel diode oscillate. It is not so easy to make the device oscillate at the correct frequency, however. Each piece of wire connecting the components together will form a tuned circuit and each of these may oscillate simultaneously. Even the rf choke may form part of the oscillatory circuit! It is essential that the undesired oscillations be suppressed.

In Fig. 1, the diode, crystal and capacitor are all in series. This configuration constitutes an oscillator circuit. However, to bias the diode with dc voltage, we need a dc path across the crystal. An rf choke will provide the necessary path but will also form an oscillatory circuit of its own. A coil and capacitor tuned to the frequency of the crystal will lock in with the crystal. The


oscillator will not take off on a spurious frequency unless the coil is badly detuned.

Part of the wirewound potentiometer (R1) is shunted across the .005- μ f ceramic capacitor. This effectively damps any tendency toward oscillation in the capacitor. The components must be connected with the shortest possible leads to keep unwanted inductance in the circuit to a minimum. The result is an oscillator circuit which will operate over a wide portion of the potentiometer range without any tendency toward parasitic operation. Parasitics are possible only when the potentiometer or coil is grossly misadjusted.

A 1.5-volt flashlight battery will power the transmitter and provide approximately 50 ma. Most of this is con-

sumed by the 50-ohm potentiometer. This apparent waste of power is necessary to hold the voltage to the tunnel diode constant, and provides the low impedance mentioned earlier.

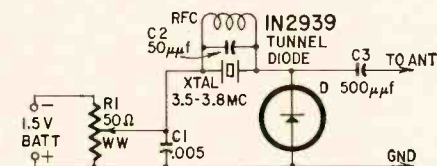An excellent source of power is a silicon solar cell. In many ways, the solar cell is ideal for this application for it is in itself a low-impedance supply. Connect the cell directly across the 50-ohm potentiometer, in place of the battery (Fig. 2). Naturally, sunlight or a bright lamp is essential.



NOTE—
RFC—50 T N° 34 ENAM ON 1/4" FORM SCRAMBLE WOUND
BATT—1.5 volts, flashlight cell
C1—.005 μ f, ceramic
C2—50 μ f, ceramic
C3—500 μ f, mica
D—IN2939 (General Electric) tunnel diode
R—pot, 50 ohms, wirewound
RFC—50 turns No. 34 enameled wire scramble-wound on a Miller No. 4300 1/4-inch diameter coil form
XTAL—3.5-3.8 mc
Chassis, to suit
Miscellaneous hardware

Fig. 1—Tunnel-diode transmitter's circuit.

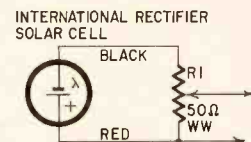


Fig. 2—International Rectifier solar cell will make an excellent substitute for the battery.

Another "stiff" supply suitable for consistent transmitter operation is the voltage developed across a silicon-rectifier junction. The rectifier is connected in series with a resistor and this combination is connected across a dc source. The dc may be a 12-volt transistor power supply, a battery charger or even an automobile battery. The resistor size is computed by Ohm's law. First determine the current to flow through the silicon rectifier and then divide the supply voltage by the current figure. The voltage drop across an average silicon

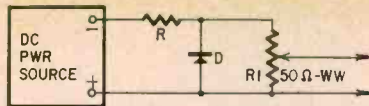


Fig. 3—Voltage drop across a silicon diode rectifier makes a good regulated power supply for the transmitter. Adjust R for 100-ma through the diode.

diode (such as the Sarkes Tarzian M500 or International Rectifier SD-94) is approximately 0.6 volt. If a battery charger is used, a filter capacitor may be required across the diode or charger output to reduce the ripple. A suitable circuit for the silicon-diode regulated power supply is shown in Fig. 3.

Adjustment and operation

Connect a few feet of wire to the antenna terminal and place this lead near the receiver. Tune the receiver to the crystal frequency and advance the potentiometer until you hear the signal beat with the receiver bfo. Just as oscillation starts, or (as the potentiometer is advanced) ceases, the note will be ragged and rough. Between these two points it will be clean and pleasant-sounding and remarkably free from chirp. If the solar cell is used to power the oscillator, a slight change in frequency will be noted as the strength of the sunlight varies, but this effect is not objectionable. Of course, if the sun goes behind a cloud (or is otherwise obscured), oscillation may cease. At these times the potentiometer may have to be readjusted.

Excessive current through the tunnel diode may ruin it and readers are warned against connecting the transmitter to a higher voltage source than that recommended unless a silicon rectifier is used to hold the voltage constant. Always turn the potentiometer to the voltage-off position before applying power to the diode. Then, depress the key and advance the potentiometer slowly until the oscillator starts. (The key is inserted in the line between C1 and the arm of R1.)

It is an excellent idea to check diode current with a 0-to-10 ma meter connected between the arm of the potentiometer and the .005- μ f capacitor (C1). As the potentiometer is turned up you will see the meter pop up to a reading of less than 1 ma. If the potentiometer is increased further, the meter will jump another step. If the voltage is increased beyond this point, the diode may be damaged! If the potentiometer is reduced, the meter will suddenly drop to the intermediate point and then to the starting current. The middle step is the correct operating point for the diode. By observing the meter and listening to the receiver, you should have no trouble getting the transmitter to work.

It was interesting to note that, with only a 3-foot length of wire connected to the antenna terminal, the oscillator was heard on a communications receiver more than 300 yards away. The strength of the signal indicated that much greater distances were possible.

To see if the tunnel diode was actually a useful communication device,

rather than a laboratory curiosity, I arranged to have a fellow New Zealand ham (ZL1AOF, some 160 airline miles distant) listen for the signals. Initial tests were very discouraging—not a peep could be heard. Next the transmitter was used to drive a 6BQ5 amplifier. Amateur radio ZL1AOF discovered he had been listening on the wrong frequency as soon as he picked up the “high-power” CW transmitter excited by the tunnel diode oscillator. Once again the tunnel diode transmitter was connected directly to the antenna. This time the signals were received with amazing clarity. A tape recording of Jack’s reception, along with a card con-

firmed the contact, attest to the performance of the transmitter.

If actual contacts are desired, rather than experiments, an 80-meter antenna must be connected to the tunnel diode, as shown in Fig. 1. A good earth ground is also absolutely essential to duplicate the author’s successful contact. [Apparently ZL1AAX has never tried a good counterpoise?—*Editor*] Some antennas may pull the diode out of oscillation and, if this happens, the value of C3 (nominally 500 μ f) should be reduced until oscillation starts. For best results adjust the potentiometer with the antenna connected to the transmitter. END


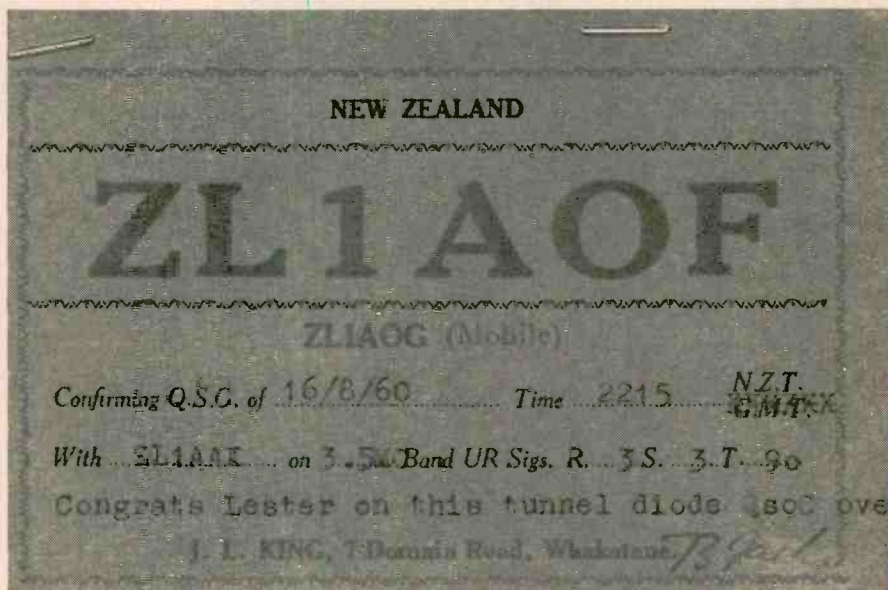


Fig. 4—Original QSL confirming 160-mile contact using tunnel-diode transmitter.

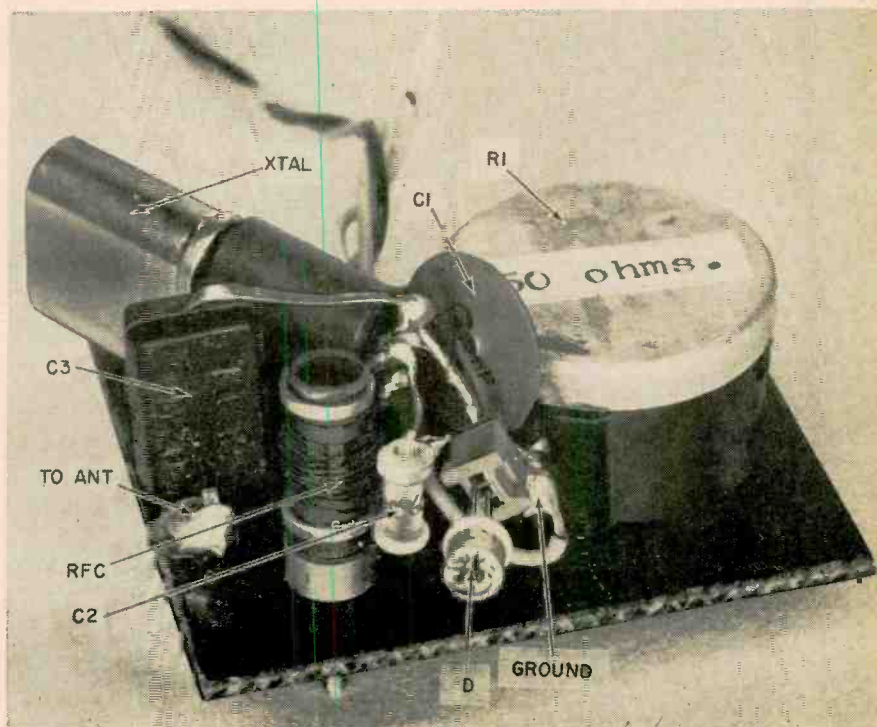

Completed transmitter requires only antenna, ground and power source.



The Braun Hobby Automatic EF-3.

E. Leitz, Inc.



The Ascortlight A423.

American Speedlight Co.

INSIDE THE ELECTRONIC PHOTOFLASH

Photoflash repairs can be business builders. Don't pass up work on these simple electronic circuits.

By C. L. HENRY

THE electronic service technician who limits his servicing to TV and radio sets is passing up a substantial amount of business. Electronics is invading new fields rapidly, and more equipment requires servicing than ever before. A good example of this is in the field of amateur and professional photography.

More than one-fifth of the amateurs and almost all professional photographers have electronic photoflash equipment. The latest photography directory lists 31 manufacturers of such equipment, each having from 2 to 16 models. All photoflash units contain at least one large electrolytic energy-storage capacitor, batteries, several resistors, a flash tube, switches, several cords and connectors. Many units are more elaborate, using dc-to-dc converters consisting of transistor oscillators, silicon rectifiers, power monitoring circuits, battery recharging and thyatron triggering circuits. As you can see, this is a fertile

field for electronic servicing. Though modern photoflash units are complex, the circuitry is usually easy to understand. Fig. 1 shows the basic circuit used in all photoflash units. C1 is charged to its rated voltage through R1. The time it takes to charge C1 to 63% of capacity is $T=RC$, the old familiar time constant formula. This is what photographers refer to when they speak of recycle time, although a slightly longer interval is usually allowed to permit the capacitor to charge to more than 80% of its rated voltage. Most photoflash units recycle in 5 to 20 seconds, depending on their power supplies.

One formula that may be unfamiliar to you is E (energy) equals $\frac{1}{2}C$ (microfarads) times V (kilovolts) squared ($E = \frac{1}{2}CV^2$). This tells us that the energy in the capacitor depends on the capacitance and the square of the voltage. For instance, in Fig. 1, with 450 volts applied to a 1,000- μ f capacitor

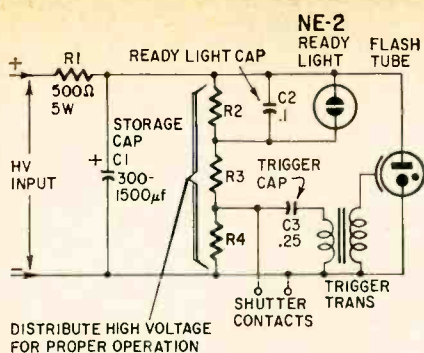


Fig. 1—Basic electronic flash circuit.

(C1), a total of 100 watt-seconds will be available when the capacitor is discharged. If this discharge takes place in .001 second through the gas tube, the circuit, in that instant, is carrying 100,000 watts. Incidentally, 100,000 watts developed in your screwdriver blade will probably melt it and will surely ruin the electrolytic capacitor. Always discharge these large capacitors through a resistor of 500 to 1,000 ohms.

Capacitor C1 is a special electrolytic, not only because of its high capacitance, but also because of its very low leakage current. Typical leakage resistance on a good capacitor will average 10 megohms. This type capacitor

must be carefully re-formed after any idle period of 2 months or more. The voltage applied should be raised slowly over a period of minutes until the rated voltage is reached. It must never be exceeded. These capacitors are also expensive (\$13.50 is typical) so be careful.

The balance of the circuit is composed of three parts: the flash tube, the ready light and the triggering circuit.

Flash tube

This is a xenon-filled tube made of either fused quartz or high-grade Pyrex. It presents a dynamic resistance, when triggered, of from 0.1 to 5 ohms depending on the type tube, and may draw an instantaneous current of 1,000 amperes. The circuit of the flash tube should be of very low resistance to prevent limiting this current. This means that all connectors must be clean and tight, and the wiring must be adequate. The spectra of these flash tubes approaches daylight, with much infrared and ultraviolet included.

The triggering circuit is composed of a trigger transformer which fires the tube by developing about 10,000 volts on its secondary, which is applied to the flash-tube trigger electrode. It should be as close to the flash tube as possible, preferably inside the envelope. C3 supplies the power for this triggering circuit by being charged to 200 volts and discharging through the primary of the trigger transformer when the shutter contacts on the camera close. An oscilloscope with a triggered sweep is very useful in checking the various instantaneous currents and voltages developed in these circuits.

Ready light

The last part of the typical flash unit is the ready light. This is an indicator that tells the photographer when the capacitor is charged to at least 80% and ready to fire. After the flash tube is fired, the neon lamp will glow steadily until the capacitor is recharged. Then it will start blinking at a rate determined by R3 and C2.

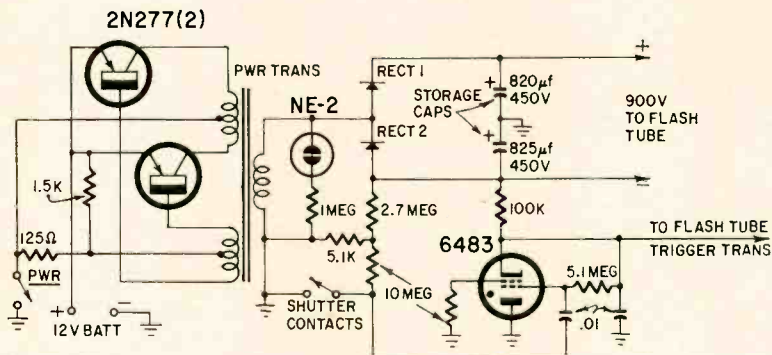


Fig. 2—Two-transistor one-tube circuit of the Ascorlight.

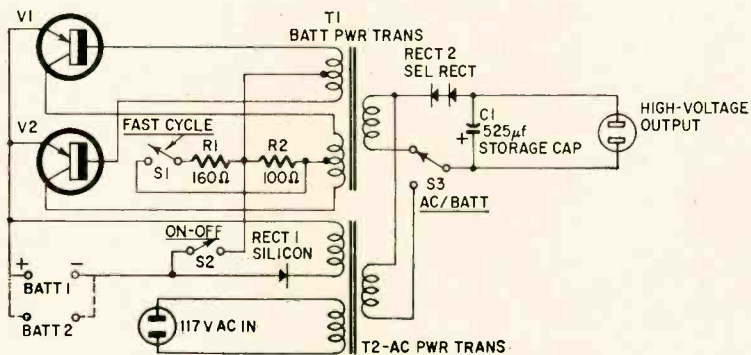


Fig. 3—Circuit of the Synctron Sixty.

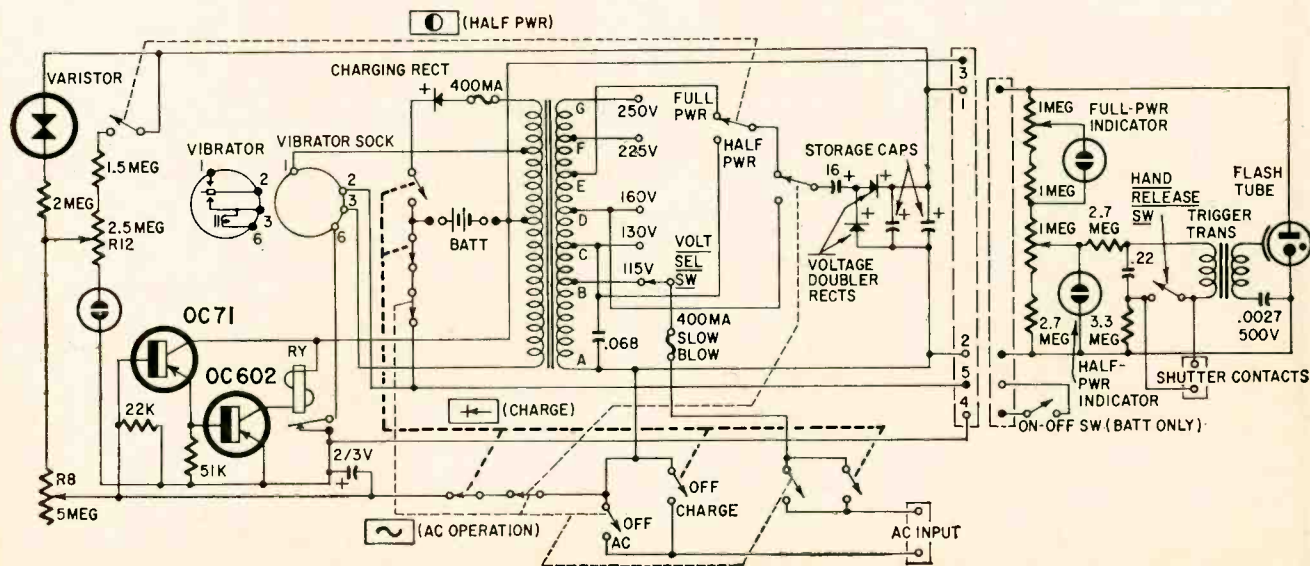


Fig. 4—The Braun Hobby EF-3.

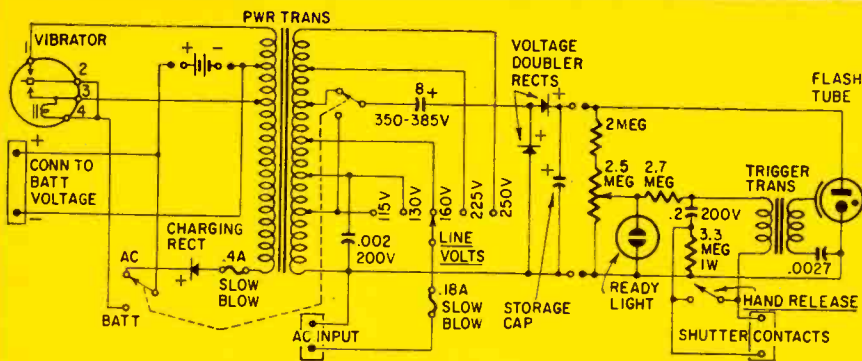


Fig. 5—Braun Hobby EF-1 electronic flash circuit.



The Multiblitz Color Cl. *Multiblitz, Inc.*

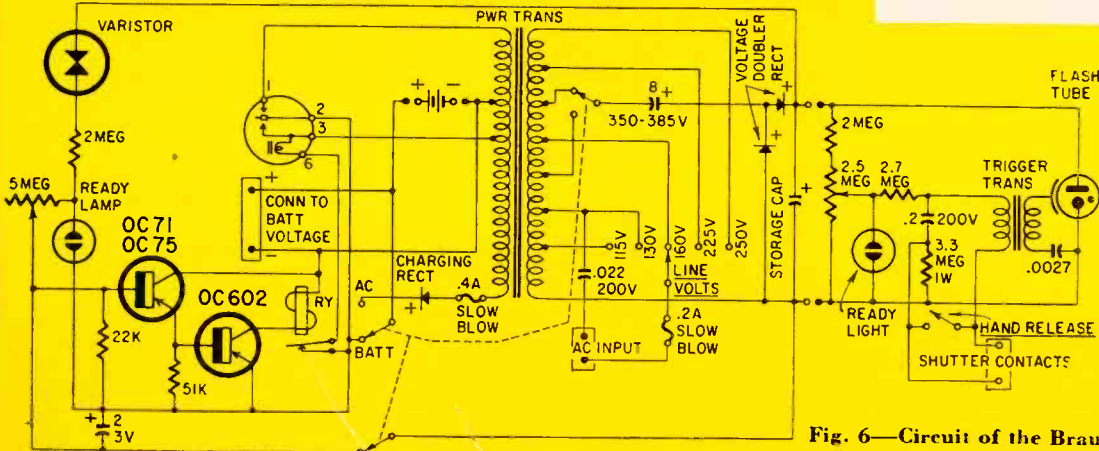


Fig. 6—Circuit of the Braun Hobby EF-2.

There are many variations of this basic circuit. Fig. 2 is the circuit of a professional photoflash unit, the Ascorlight A423, made by American Speedlight Co. A 200-watt-second unit, it will recycle in 7 seconds and has a power-conserving circuit for its nickel-cadmium battery. Drain on the battery during charging is 5 amperes, and drops to 350 ma when idling. The transistor oscillator, using two type 2N277 transistors, operates at 1,500 cycles. Waveforms from collector to collector and base to base are square, with little or no overshoot.

The transformer output is doubled by the rectifiers and supplied to the flash-tube balanced to ground, to prevent insulation troubles. The flash tube is triggered by the thyatron, a 6483. Firing the flash tube in this manner prevents excessive shutter-contact current.

Photoflash circuits

Fig. 3 is another transistor photoflash unit—the Syntron Sixty, made by Dormitzer Electric Co. Notice that ac operation is provided by T2 and RECT 2. This circuit also recharges the built-in battery through RECT 1. S1 provides a fast recycle in cases where this is desirable. As you can see, this switch raises the biasing voltage on the bases of V1 and V2, increasing the output of the circuit and also increasing the battery drain. Recycling takes 12 seconds normally and 6 seconds with S1 closed.

Figs. 4, 5 and 6 illustrate three flash units made by E. Leitz, Inc. Fig. 4 is the Braun Hobby Automatic EF-3; Fig. 5, the EF-1, and Fig. 6, the EF-2.

These flash units are transistorized (transistor power-monitor circuit) and have vibrator power supplies powered by built-in nickel-cadmium batteries. A self-charger is included in each unit. The EF-3 flash head has an adjustable reflector, to vary the beam width.

The EF-3 (see photo) has three pushbutton type multi-circuit spst and spdt switches as function selectors. When all are up, the unit operates from batteries and is controlled by a switch on the gun. The button on the left

(marked with a sine wave) is the ac on-off switch; the center button (marked with a half-shaded circle as on the diagram) is pressed for half-power operation on batteries or ac. The button marked with the rectifier symbol is pressed to charge the battery from the power line.

The transistorized power monitor cuts off the vibrator when the storage capacitors are charged to 510 volts ± 10 volts on full power or 350 volts ± 10 on half power. R8 and R12 set the

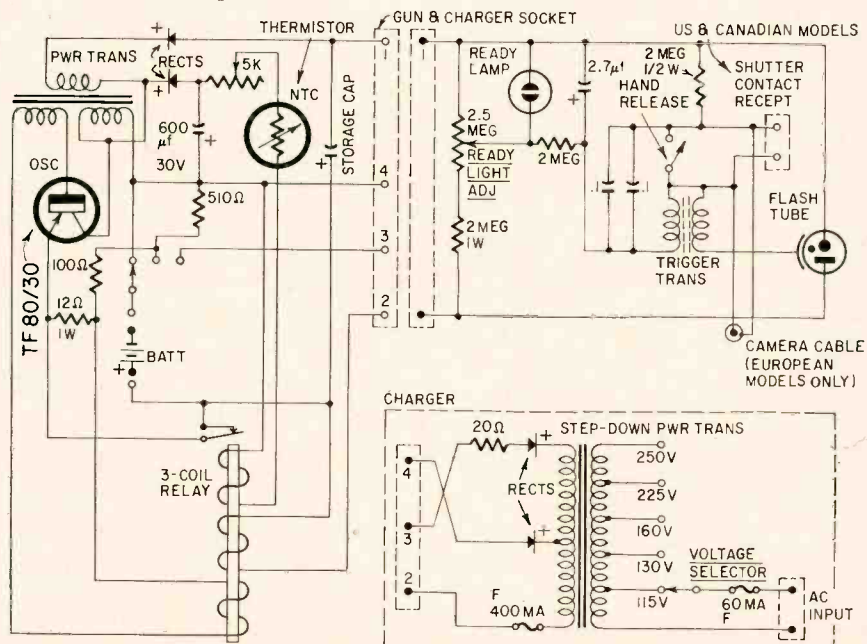


Fig. 7—F-60 power supply for the Braun flash units.

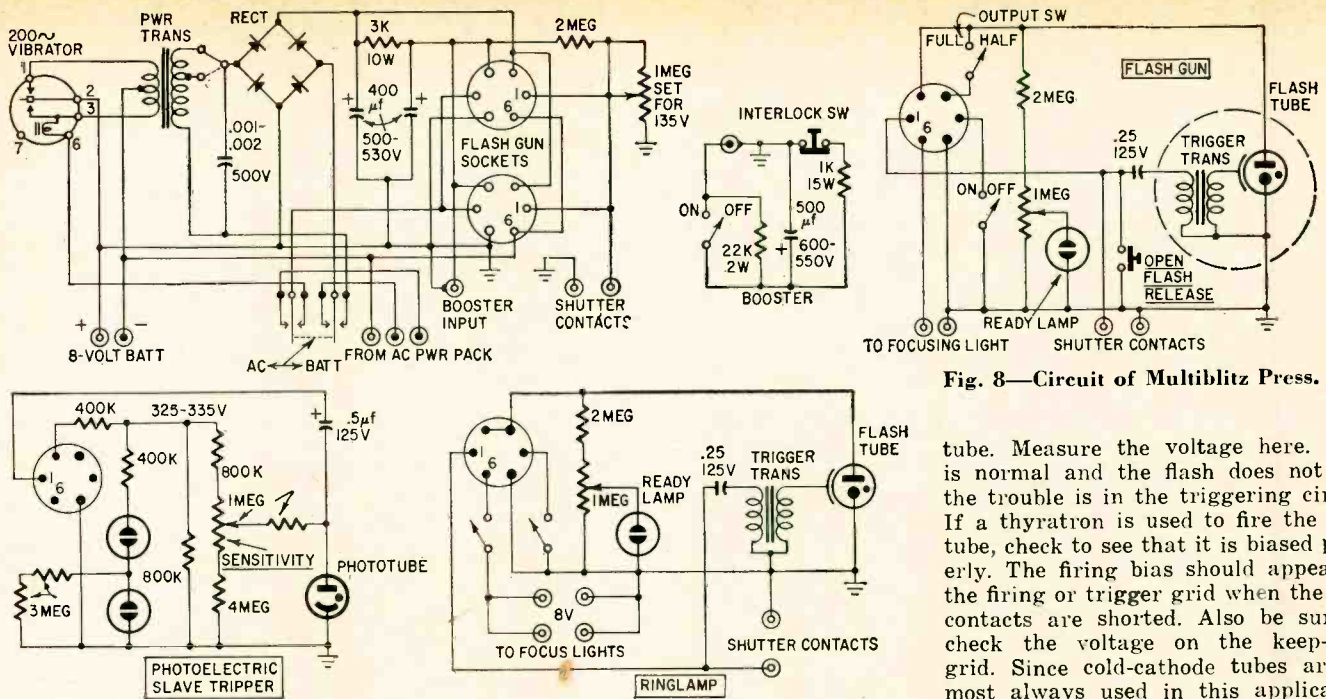


Fig. 8—Circuit of Multiblitz Press.

turnoff points for full power and half power, respectively. The vibrator comes on when the output voltage drops 10 to 30 on full power or 10 to 40 on half power.

E. Leitz advises me that they supply parts only to authorized Braun Hobby repair stations. Fig. 7 is the power supply made by E. Leitz for various flash heads, and is similar to the three just described.

The Ultrablitz Press in Fig. 8 is a versatile professional type electronic flash. It operates from an internal 8-volt storage battery, a combination ac power pack and charger or flashlight batteries. Accessories include a photoelectric slave tripper, focusing lamps, an extension flash head that can be used simultaneously with the standard head on the camera, a booster (plug-in 600-µf capacitor) to double light output and a circular or ringlight for shadowless lighting when making closeups of small objects.

Fig. 9 is another Multiblitz flash, the Color SL. A vibrator converter is also used in this unit, together with a unique transistor power-monitor circuit that allows the battery to idle between flashes. This lengthens the usable battery life before recharging is necessary. Many electronic photoflash manufac-

turners discourage local service of their flash units, even though photographers may be caused considerable inconvenience (and loss to professionals) in sending the equipment to an authorized service station in the next state, or even back to the manufacturer, for service. However, a reputable service shop should be able to obtain parts if necessary from the manufacturer, or even obtain the local service franchise! A pleasant letter here will help! In many cases substitution may be possible, even if exact replacement parts are not available. Kemlite Laboratories supply many different types of flash tubes, Sprague supplies several types of photoflash capacitors, and alternate transistors, transformers, rectifiers and vibrators are also available. All current manufacturers of photoflash units are listed in the *Popular Photography Directory*, 1960 issue.

After repairing a flash unit, test it by shooting a roll of film, following the manufacturer's guide number.

Troubleshooting

An electronic flash is easier to service than an ac-dc radio. A vom is the only piece of test equipment you must have. A scope is an additional aid.

The best place to begin is at the flash

tube. Measure the voltage here. If it is normal and the flash does not fire, the trouble is in the triggering circuit. If a thyratron is used to fire the flash tube, check to see that it is biased properly. The firing bias should appear on the firing or trigger grid when the sync contacts are shorted. Also be sure to check the voltage on the keep-alive grid. Since cold-cathode tubes are almost always used in this application, this voltage is vital to the operation. Low voltage here or a bad tube can cause the flash tube to fire too late, although this defect will be noticed only on the faster shutter speeds of the camera.

After the tube part of the trigger circuit is eliminated, check the trigger coil for proper operation. If an oscilloscope with triggered sweep is not available, replace the trigger transformer if you suspect it. A triggered scope will tell you whether the trigger transformer is functioning properly. A milliammeter in series with the trigger coil will kick slightly when the trigger capacitor is discharged through it, but experience is necessary here to judge whether the components are good.

In the event of low or no high voltage, trace the circuit further toward the battery. Also, don't forget the necessary low leakage factor of the electrolytic flash capacitor. If the capacitor's leakage current increases, a long recycle time will result. If this current is too high, the power supply may not be able to charge the capacitor to its rated voltage. The capacitor can be disconnected temporarily (**Be careful!**) and the output of the rectifier measured unloaded. In the event of high-voltage battery operation, this is, of course, unnecessary. If with the capacitor disconnected, the voltage is still low, check the rectifiers, transistors or vibrator. Remember that normal voltage with the capacitor disconnected will be only 0.7 times the voltage with it in circuit.

Some units use a power monitoring circuit. It is supposed to cut down the activity of the vibrator or transistor oscillator when the flash capacitor reaches full charge. A wrong bias here will cause the input circuits to idle all the time and will cut down the output voltage. It is best to disconnect this circuit if there is any doubt of its operation. Then if the output voltage assumes its normal value, you know where to find the trouble. **END**


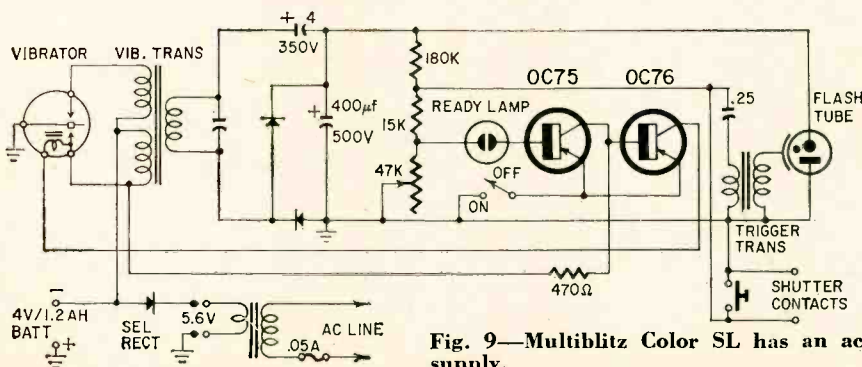


Fig. 9—Multiblitz Color SL has an ac supply.

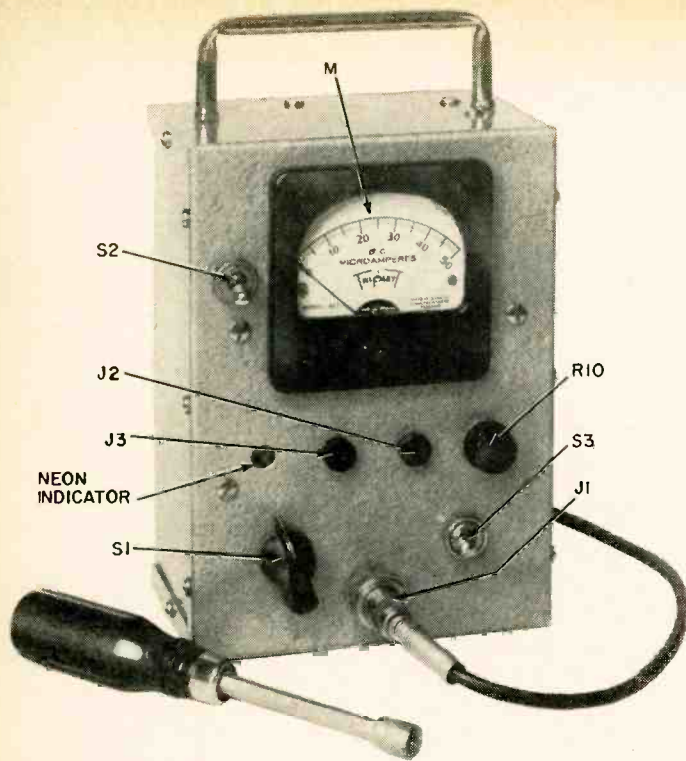EASY-TO-BUILD WIDE-BAND VTVM DOUBLES AS AUDIO ANALYZER



The completed unit in a neat crinkle-finish case.


Three-way instrument is audio vtvm, signal tracer and 1,000-cycle oscillator

By KENNETH E. WALTERS

WOULD you appreciate a wide-band voltmeter which could also be used as a preamplifier, signal tracer and, with a special probe, as a 1,000-cycle test oscillator? If so, this article was written expressly for you.

The circuit (Fig. 1) uses two dual triodes, a 12AT7 and a 12AU7, in a highly stable amplifier circuit. Response is essentially flat from 20 cycles to about 250 kc. The instrument is usable to about 1.6 mc for comparative purposes. A low-capacitance switch for S1 would improve high-frequency response.

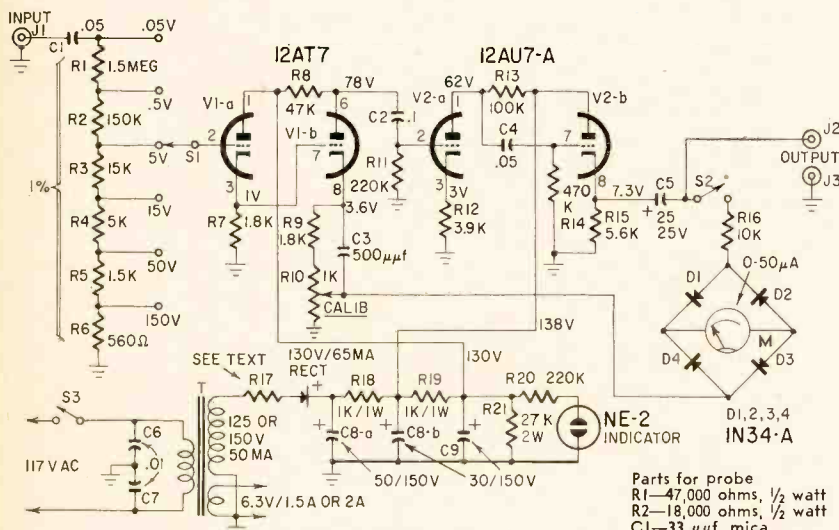V1-a is a cathode-follower input stage, direct-coupled to the grid of V1-b. This second section of the 12AT7 is an ordinary voltage amplifier that has high-frequency compensation due to the low-reactance path offered by C3. The 1,000-ohm potentiometer in the



- R1—1.5 megohms, 1%
 - R2—150,000 ohms, 1%
 - R3—15,000 ohms, 1%
 - R4—5,000 ohms, 1%
 - R5—1,500 ohms, 1%
 - R6—560 ohms, 1%
 - R7—1,800 ohms
 - R8—47,000 ohms
 - R10—pot., 1,000 ohms
 - R11—20—220,000 ohms
 - R12—3,900 ohms
 - R13—100,000 ohms
 - R14—470,000 ohms
 - R15—5,600 ohms
 - R16—10,000 ohms
 - R17—see text
 - R18, 19—1,000 ohms, 1 watt
 - R21—27,000 ohms, 2 watts
- All resistors 1/2-watt
10% unless noted
- C1—4—.05 μ f, 400 volts, paper
 - C2—0.1 μ f, 400 volts, paper
 - C3—500 μ f, mica
 - C5—25 μ f, 25 volts, electrolytic
 - C6, 7—.01 μ f, 600 volts, ceramic disc
 - C8—50—30 μ f, 150 volts, electrolytic
 - C9—30 μ f, 150 volts, electrolytic
 - D1, 2, 3, 4—IN34-A
 - J1—coaxial connector
 - J2, 3—tip jacks
 - M—0-50 μ A
 - RECT—selenium, 65 ma, 130 volts
 - S1—6-position rotary, nonshorting
 - S2, 3—sps toggle
- T—power transformer: primary 117 volts; secondary: 150 volts, 50 ma; 6.3 volts, 1.5 amp; or 125 volts, 50 ma; 6.3 volts, 2 amps (Thordarson 22R12 or Stancor PA-8421 or equivalent)
- V1—12AT7
V2—12AU7-A
Neon indicator lamp, NE-2
Sockets, 9-pin (2)
Case, 3 x 5 x 7 inches
Chassis, 4 3/4 x 2 7/8 x 1 1/2 inches
Miscellaneous hardware

- Parts for probe
- R1—47,000 ohms, 1/2 watt
 - R2—18,000 ohms, 1/2 watt
 - C1—33 μ f, mica
 - C2—.002 μ f, ceramic
 - P1—coax connector to match J1
 - P2—tip plug to match J2 on meter
 - S—dpdt slide or miniature toggle
- Probe case and tip (see text)
Alligator clip, wiring, etc.

Ac vtvm covers 0 to 150 volts in 6 ranges—lowest range, 0—.05. Audio oscillator produces square-wave output with peak-to-peak amplitude of about 12 volts. Signal-tracer function useful in all audio stages. Can be used with demodulator probe in radio if stages.

Tested by a member of RADIO-ELECTRONICS' staff, the instrument operated quite satisfactorily. Readings on low-voltage outputs from Heath, Eico, and Knight audio generators were compared to scope readings. Author's frequency range of 20—250 kc is correct within total variation of 5—10%—error increases with frequency. Unit will make measurements at higher frequencies but accuracy is impaired. However, a correction chart could be drawn up.



Fig. 1—Circuit of the handy analyzer.

cathode circuit of this stage is the calibration control. Its setting determines the amount of degenerative feedback voltage from V2-b through the metering circuit. This feedback path is broken when S2 is open and the amplifier gain increases. This is highly desirable when using the instrument as a signal tracer.

V2-a is a voltage amplifier with R-C coupling to the cathode-follower output stage. We have degenerative feedback in V2-a because of the unbypassed cathode resistor R12.

A close look at the schematic reveals that there are two phase inversions, one at the plate of V1-b and the other at the plate of V2-a. Thus the output voltage will be in phase with the input. This is one of the requirements of an oscillator, and the feedback path through C1 and the switch in the probe (Fig. 2) is the other. The circuit oscillates at about 1,000 cycles. The output is a square wave with an amplitude of about 12 volts peak-to-peak at the probe tip.

The circuit is built into a 3 x 5 x 7-inch case. The small chassis is only 4 3/4 x 2 7/8 x 1 1/2 inches. The 1 1/2-inch right-angle portion is cut to fit snugly around the meter case.

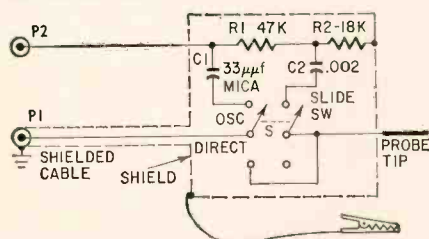


Fig. 2—Probe circuit enables operation as 1,000-cycle oscillator.

A common bus made of No. 18 copper wire is used for all B-minus connections. All leads are kept short and direct.

The combination direct and oscillator probe was built in the aluminum housing of an old can type electrolytic capacitor. The probe housing measures 1 3/8 inches in diameter and 3 3/8 inches in length. The probe tip consists of a small nail soldered into a phono plug.

Power requirements are slight. The power transformer I used had a 150-volt secondary so I added R17, a 750-ohm 1-watt resistor, to protect the 130-volt selenium rectifier. If a 125-volt transformer is used (as described in the parts list), R17 can be omitted.

Coupling capacitor C5 should be checked for leakage before closing S2. If this capacitor is leaky, excessive current may damage the meter movement. After completing the instrument, open S2 and apply power to the circuit. Check for voltage between J2 and J3 with a dc voltmeter. If voltage is found after initial warmup, it indicates leakage. An unformed, new capacitor may show leakage by the above test. Do not discard the unit—try forming it by leaving the instrument on for about an hour with a jumper across J2 and J3. This applies about 7.3 volts dc to the unit. Then make another voltage check.

To calibrate, set the range switch to the 5-volt position and touch the test

leads to a 5-volt source, preferably at 1,000 cycles, and adjust R10 for a full-scale reading.

To use the instrument as an oscillator, open the meter-circuit switch and set the range switch for .05 volt. Plug P2 (Fig. 2) into J2 and then throw the probe switch to the oscillator position. The 1,000-cycle square-wave test voltage is now available at the probe tip. After using the instrument as an oscillator meter, switch S2 should not be thrown to the meter position for about 8 seconds. This lets capacitor C5 charge through the 47,000- and 18,000-ohm resistors in the probe assembly. This prevents damage to the meter movement as the charging current of C5 is much greater than that required for full-scale deflection of the meter.

When signal-tracing, place the probe switch in the direct position and open the meter switch to increase the amplifier gain. Phones are used to monitor the output.

With a detector probe the instrument can be used to signal-trace in rf and if circuits. My vtvm detector probe works nicely with the instrument, so I did not need a special detector probe.

The 1,000-cycle square wave can be used for amplifier response testing. An amplifier with good response to 10,000 cycles or more should pass the signal

without changing the shape of the waveform.


Use the voltmeter with an audio oscillator and you have a good capacitance meter. It measures capacitance from 1 to 2,000 μf .

Set the oscillator to 1,000 cycles and adjust its output until the voltmeter reads full scale on the 0.5-volt range. Leave the ground leads of the signal generator and voltmeter connected and place the capacitor to be tested between the oscillator hot lead and the voltmeter input. The 1,000-cycle voltage divides between the reactance of the capacitor and the input impedance of the voltmeter according to the ratio of reactance to resistance.

On the 0.5-volt range, the meter reads capacitance from 20 to 2,000 μf . For capacitance below 20 μf , switch to the .05-volt range. This range reads from 1 to 11.6 μf .

I would like to point out one more possible use for the instrument. That is as a code-practice oscillator. Insert a key between P1 and J2. Then set up the circuit for oscillator operation as previously described. The code signals appearing at the output (the probe tip) may be fed to phones or to a small amplifier and speaker system.

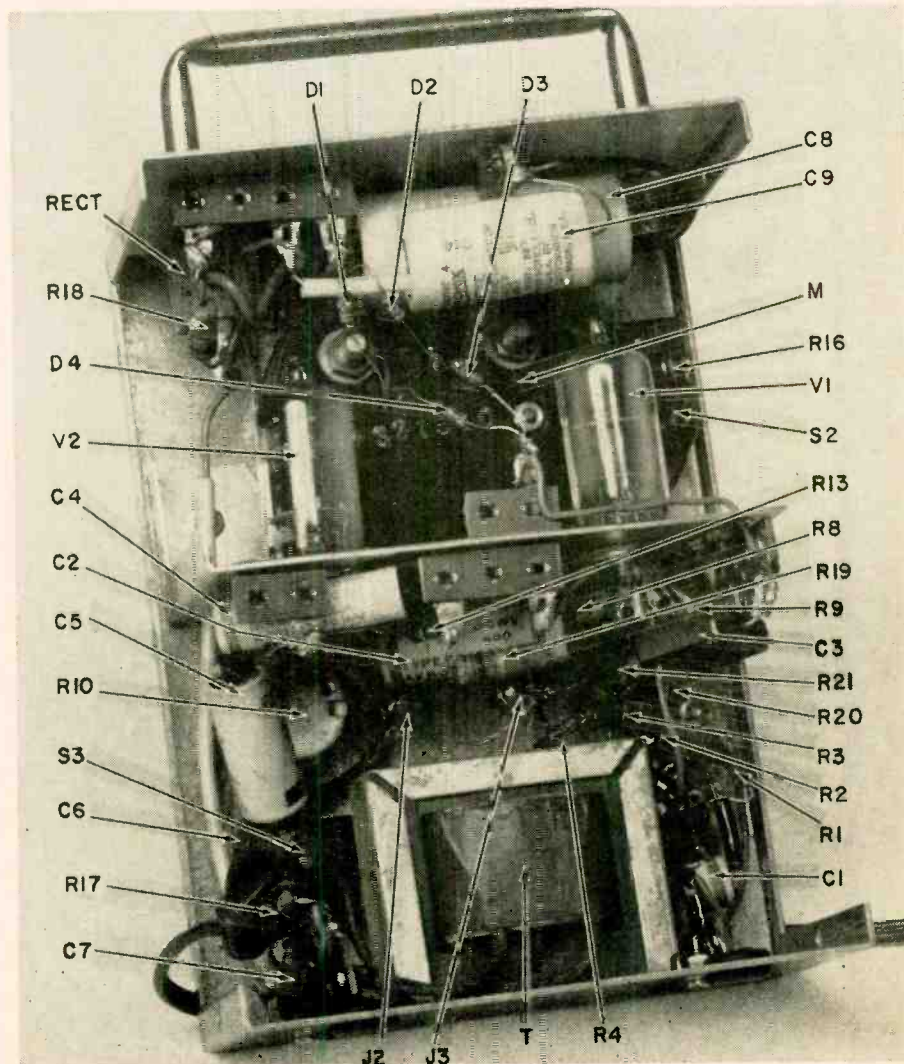
An instrument as versatile as this should find many uses. END



Parts arrangement inside the case.

VHF translator

TV for YOUR town

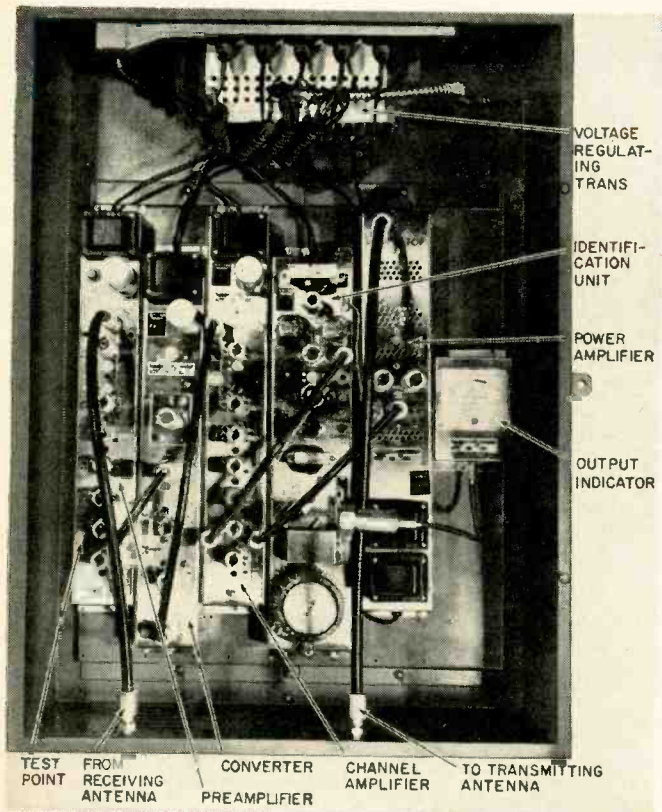

Complete vhf translator less antennas and matching transformers.

Next comes a crystal-controlled converter which changes the frequency of the incoming wanted TV channel to that of the chosen output channel.

The converted signal is further amplified by a low-distortion channel amplifier. This unit uses age to assure that maximum permissible drive is supplied to the output power amplifier tube even when the input signal fades severely. This low-distortion channel amplifier also prevents any possibility of spurious signals (harmonics of the crystal oscillator, etc.) from reaching the power amplifier.

Finally, the signal from the channel amplifier is fed to the power amplifier. This unit feeds 8.7 volts with good linearity to the 75-ohm transmitting antenna, providing 1 watt of rf power plus, of course, the antenna gain.

By using a Yagi type transmitting antenna—it can be a heavy-duty version of a standard receiving antenna—it is possible to get 10 watts of effective radiated power.

Automatic operation

The second output of the channel amplifier is fed to the identification unit. This is a programmer designed to operate the translator. It switches the transmitter off when a very weak signal, or no signal at all, is being received. It provides facilities for remote-control operation, and superimposes station identification every 1/2 hour. The unit also provides a delayed switch-off action to avoid cutoff due to momentary signal fading.

Are you ready to install a translator?

By PHILIP FREEN*

TELEVISION coverage in North America has been steadily extended in populated areas, but there are many places where a full-fledged TV station is an economic impossibility. However, with translators, the same television programming can be brought to villages of as few as 100 families.

Until recently the Federal Communications Commission allowed the use of translators on uhf only. This often required uhf converters for each home TV set. FCC docket No. 12116, September 16, 1960, legalized vhf translators. Operators of vhf translator equipment must now file applications for temporary use until October, 1961, at which time all equipment in use must be approved by the FCC.

A translator is basically an automatic television transmitter, which picks up the signal from an originating station and rebroadcasts it to an isolated community that cannot normally receive the signal from the originating station.

Vhf translators can usually be completely installed for less than \$3,000, if a suitable site with a source of 117-

volt ac is available. A typical translator can be maintained for about \$500–\$1,000 per year. The local radio technician can usually maintain the equipment, providing himself with an additional source of income while performing a service for his community.

How translators work

The photo shows the front view of the Benco T-1 translator. The callouts identify the various units contained in the transmitter housing.

The signal is received and fed through an antenna matching transformer to a preamplifier. This low-noise unit is tuned to the frequency of the distant television station. It has a gain of 65 db. The noise figure is 4 db on low-band channels and 6 db on high-band vhf channels. The circuit includes age to maintain satisfactory picture quality with input signals as low as 50 mv.

The preamplifier raises the level of the input signal so that any man-made noise in the vicinity of the translator will have little effect. In addition, any traps or filters that may be necessary to clean up the received signal can be inserted at the preamp output, where the signal is at a relatively high level.

*President, Benco Television Associates Ltd., Rexdale, Ont., Canada.

The identification unit discriminates between the TV signal and an equal amount of noise, assuring a positive action when operating with weak signals.

A power indicator is connected to the final rf output. It is factory-set to indicate maximum permissible power level with a translator output of 1 watt.

The last unit shown is the voltage-regulating transformer. It is important for constant power output since most translators are operated at the end of poor-quality power lines, and the ac input often varies between 95 to 130 volts. Tube life can be doubled by using a voltage-regulating transformer.

Site location

Site location is a task that should be undertaken very carefully. These factors must be considered:

▶ A signal of at least 100 μv should be available from the remote master TV station more than 98% of the time. To find a suitable receiving site, erect a temporary antenna, usually a Yagi type, and monitor the received signal for about 100 hours. Bear in mind that during the summer months extremely erratic conditions prevail, and it is possible to get signal-strength readings 10 times higher than those which are normal for a particular TV station.

In mountainous country, the best receiving site is often on the slope of a mountain facing the distant TV station rather than on the top of the mountain as might be expected. Try to find a fairly gentle slope rather than a precipitous one. By searching with the test antenna, both vertically (5-20 feet) and horizontally, it is usually possible to find a signal if the desired TV station is less than 150 miles away and there is no abnormally high mountain between.

In flat country, the dominating factor is usually the height of the receiving antenna which, obviously, must be as great as possible.

A good translator receiving antenna becomes especially important in low-signal areas—stacked Yagis are generally recommended. Rhombic antennas are more difficult to construct, but, judging by our experience, have superior signal-capture characteristics.

▶ Having located one or more possible receiving sites, pick out a suitable transmitting site. It should be as close to the receiving site as possible. The most desirable would place the translator transmitting antenna overlooking the town or village to be serviced and not more than 5 miles away.

The translator transmitting antenna should not have high horizontal directivity. As a general rule, when maximum radiated power is required, vertical stacking is advisable. Here again good-quality heavy-duty antennas should be used.

The polar diagram of the selected antenna should, as far as possible, cover only the populated area of the village and have a minimum of back radiation and spurious side lobes. This puts all the available power where it will do the most good and decreases the possi-

bility of interference with other translators in the vicinity.

If the best transmitting site happens to be some distance away from the best receiving site, a coaxial cable system will have to be used to bring the received signal to the translator.

▶ Whatever site is finally chosen for the transmitting antenna, there must be 117-volt power available. The source of power should be capable of delivering at least 1.5 kw with reasonably good regulation. The 1 kw over and above the electronic equipment's appetite is for soldering irons, lights and, most important of all, a 1-kw heater or hot plate. (Hot coffee and some warmth can be a life-saver after trekking up a mountain on a cold winter's day to replace a tube.)

If the receiving site is not at the same location as the transmitting site and amplification through a coaxial cable is required, it is possible to use remotely powered transistor amplifiers to eliminate the need for ac power at the receiving site.

The availability of ac power at a particular site in many cases overrides other considerations, since the cost of running ac power lines of even moderate length is rather high.

▶ After all the three factors outlined above have been considered and a site chosen, the next problem is the choice of a suitable enclosure for the equipment. While the Benco T-1 translator is completely weatherproofed and may be mounted outdoors on the antenna support, it is highly desirable, if possible, to have a small building available for tools, spares and human comfort. The translator will work quite

happily in a temperature of 20 below, but *you* will not be at peak efficiency if you have to change a tube in this temperature.

▶ The nomogram shows the signal strength available across the input terminals of the home television receiver in a village served by a translator when the TV channel and distance from translator transmitting antenna to home receiver are known. The nomogram assumes a home receiving antenna gain of 9 db and a translator transmitting antenna gain of 6 db (with reference to an isotropic antenna) and a 2-db feeder loss on both the receiving and transmitting antennas.

For example, the dotted line indicates that a signal from a channel-2 translator will arrive with 500 μv across the home TV set's 300-ohm terminals via a line-of-sight path of 30 miles provided that the first *Fresnel* zone is cleared.

In simplified terms, the *Fresnel* zone is a criterion to determine whether the earth is sufficiently far removed from the line-of-sight ray to allow free-space propagation conditions.

For those interested, the first *Fresnel*-zone clearance is given by


$$1,140 \sqrt{\frac{d}{F}}$$

where *d* is the distance in miles between the transmitting and receiving antennas and *F* is the operating frequency in megacycles.

To take the example shown, the first *Fresnel*-zone clearance for Channel 2 for 30 miles is approximately 800 feet:

$$(1,140 \sqrt{\frac{30}{60}} = 1,140 \times 0.7 \text{ approx.})$$

This means that the line-of-sight ray

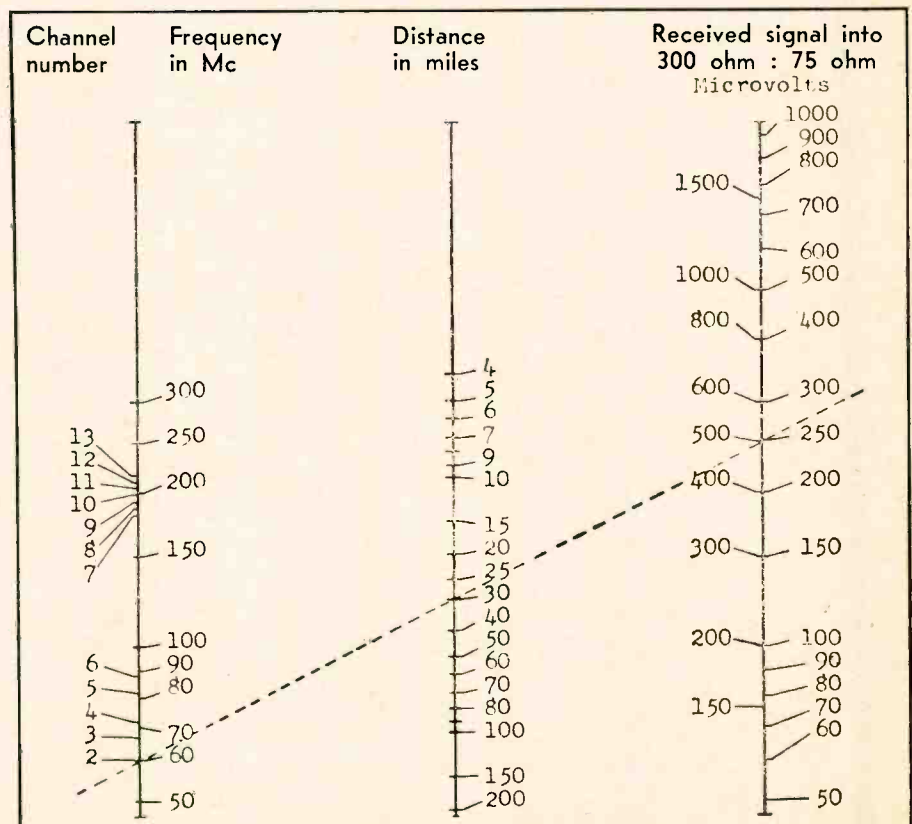

Translator signal vs distance and frequency.

from the translator transmitting antenna to the home viewing antenna should clear any obstacles in the middle of the span (15 miles) by 800 feet for the nomogram to be correct.

Installation

Installation is relatively simple since the translator package is a complete self-contained unit which, basically, needs only a receiving antenna, transmitting antenna and a connection to a 117-volt 60-cycle power source.

The unit is factory-aligned and the only control which may be set in the field without using test equipment is the power output control. The Benco unit has a power output meter. It should never read more than *maximum permissible power*. No other adjustments on the translator should be made without having a complete set of alignment data available with the necessary test equipment.

Be especially careful with coaxial cable connectors. Remember that each connection will be subjected to severe temperature variations, which tend to loosen threads and cause intermittents. Follow the manufacturer's instructions exactly.

Make power connections to the unit according to the local electrical code and make sure they are properly switched and fused.

The remote-control line, if required, should be installed from the translator to the operator's house or place of business. The line may consist of ordinary twisted-pair telephone line, but total loop resistance must not exceed the manufacturer's specifications (for the Benco T-1, 2,500 ohms).

After the translator is completely installed, use a television set to monitor the input signal at the monitor point provided. The picture obtained from the output of the translator can never be any better than the input, but, strangely enough, quite a few people expect it to be. Use a field-strength meter to check the ratio of sound to picture carrier. According to Hoyle, the sound carrier should be about half the strength of the picture ($\frac{1}{4}$ of the power). Adjustments on the T-1 translator alter this ratio if necessary.

The sound carrier should never be allowed to become greater than the picture carrier. To be safe, we have found it advisable to keep the sound carrier at only $\frac{1}{4}$ the signal strength of the picture carrier ($\frac{1}{16}$ of the power).

This still allows excellent sound reception, but assures that, if for any reason (summer conditions), the sound carrier rises in respect to the picture carrier at the input to the translator, it will never exceed it. Moreover, it allows $\frac{15}{16}$ of the output power of the translator to be put into the picture carrier.

The information in these few pages should, we trust, assist the local technician in siting and installing translators and, while this article has been slanted toward vhf translation, the same reasoning and procedure apply equally to uhf units. END

BBB Raps Set Manufacturers

NOT all those complaints against the electronic industry that we hear about from the Better Business Bureaus are customer complaints against the local service technician. More than a few are complaints from service technicians and dealers against distributors and manufacturers. This was revealed by Kenneth B. Wilson, president of the National Better Business Bureau, in a recent address to a meeting of the Service Committee of the Electronic Industries Association (EIA).

The technician did come in for his share of complaints, Wilson pointed out. But even then, the greatest volume of complaints directed at the technician was due to *misunderstanding of warranties*. It is no surprise to the service technician that the set owner is unpleasantly surprised to learn that, under the warranty setup, set owner and manufacturer are co-guarantors of the receiver and that his share—cost of the labor in replacing a defective part—may run several dollars more than that of the manufacturer—the cost of the actual component. The manufacturers may not be as aware of the situation. If such is the case, they heard of it at this meeting.

Dilatory service was another major cause of complaint, according to the BBB. Technicians may keep a set many days or even weeks. Customers are especially annoyed because "few explanations, if any, are given as to the cause of the delay in the meantime.

Overcharging, ineffective and incompetent service, and failure to live up to promises were the other main complaints against service technicians by customers.

Unavailability of replacement parts is the greatest cause of both public and service industry complaint against manufacturers (and distributors). The industry, says the BBB, may feel that it has some good alibis for this problem, but they are not good enough to satisfy either irate customers or frustrated technicians who have to wait weeks or even months for a needed part:

"The plain and inescapable fact of the matter is that they find it difficult, if not impossible, to believe that the brains and intelligence which have been able to create the fabulous new electronics miracles about which they read every day, cannot develop a system which will deliver replacement parts promptly."

Inadequate field testing and inadequate inspection formed the second complaint of the service technicians, and, they report, a frequent cause of customer complaints. Said Wilson, "Dealers report there are very few brands of TV sets they would dare take to a customer's home in an unopened carton, because so many sets require servicing *before* installation."

A group of related complaints centers

around the quality of the product. Poor quality of components, unavailability of parts for discontinued or small-run items and units badly designed from a servicing standpoint all came in for their share of criticism.

Delay in correcting manufacturing faults irked technicians especially. In many cases, they tell the BBB, the manufacturer discovers a production weakness soon after a new model starts running, but continues to distribute sets already completed.

Poor communications of this type are often the fault of the distributor, as is the dissemination of other service information. He and the manufacturer are both held responsible by the service organization for failure to supply product and service data promptly. Another form of poor communications is the distributor's failure to report whether an order is being filled immediately or will have to be ordered from the factory. This puts the service technician at a disadvantage with his customer, because he cannot report definitely and accurately as to possible delays.

Availability of replacement parts is a responsibility of the distributor whose business is supposed to distribute just such parts, as well as of the manufacturer. Some distributors are the subject of complaints on this score.

As might be expected, many complaints arise from distributor sales of parts to consumers at the same prices as to service customers, as well as the "nurturing" of spare-time service operators. Many of these, complainants point out, are presumably operating illegitimately, without filing tax reports on business done.

In concluding the report, the National Better Business Bureau presented 12 recommendations to manufacturers from among those received from the servicing industry:

- ▶ Ship only tested products.
- ▶ Do more thorough field testing to minimize "built-in" breakdowns.
- ▶ Stick to high-quality components with long-life potential.
- ▶ Create better public understanding of the true nature of your warranties.
- ▶ Keep warranties within time periods which will be profitable to service.
- ▶ Get service information to the industry.
- ▶ Limit advertising claims to demonstrable performance in the field.
- ▶ Provide more and better training facilities and clinics for the servicing of the industry's products.
- ▶ Make replacement parts promptly available to the service industry.
- ▶ Design circuits with better accessibility to parts.
- ▶ Recognize and correct manufacturing faults promptly.
- ▶ Secure distributor cooperation in expediting parts orders. END


WHAT'S NEW



SCIENCE-FICTION MONSTER substitutes for man in dangerous places. Two TV camera eyes transmit pictures of its handiwork to human operator at a remote-control console. They can be remotely adjusted to view any action of the robot. Arms of the Hughes Aircraft *Robot* are double-jointed at shoulders, elbows and wrists for extreme flexibility.




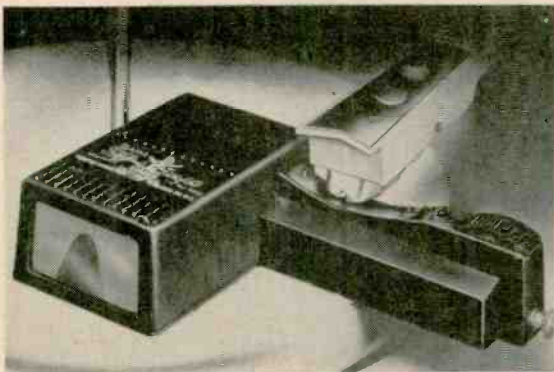3-D RADAR ANTENNA on the masthead of missile cruiser USS *Galveston* simultaneously detects range, bearing and attitude of aircraft. Single antenna replaces two or more previously required to do the same job. Unit is part of Hughes Aircraft Frescan radar system.



WORN STYLII are easy to spot with the Syl-A-Scope. This simple optical instrument, a shadowgraph, displays a detailed magnified picture of any phonograph stylus and reveals any wear or flaws. The device is made by Robins Industries, New York, N.Y.

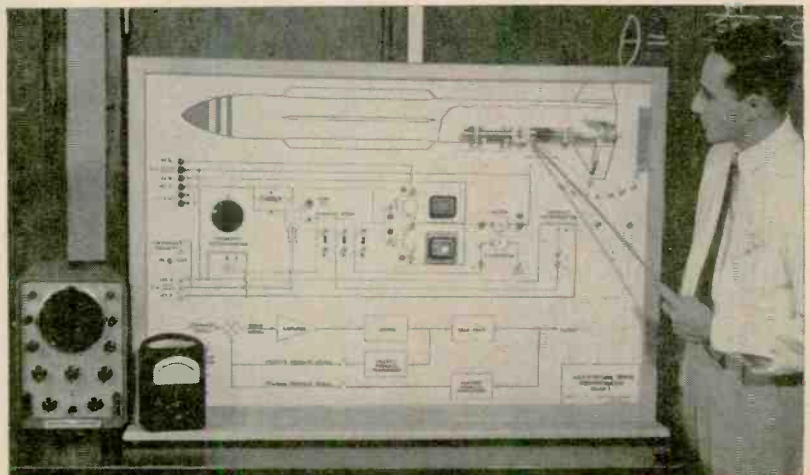DYNAMIC EDUCATOR helps teach servo theory, design and application. Developed by Advanced Research Associates, Kensington, Md., the device includes an operable velocity and position feedback servo system mounted on a 33 x 49-inch demonstration panel. It is designed for use in vocational schools.



By MANNIE HOROWITZ*

CHOOSING an amplifier to buy or to build from a kit or magazine article can be difficult. Overcomplicated units loaded with controls confuse rather than provide any worth-while benefit. On the other hand, a simplified unit which does not serve the complete purpose of the audiophile should also be avoided.

To simplify circuitry comparison, the amplifier is divided into two sections—the preamplifier and the power amplifier. Here, the preamp is discussed as an individual unit. This discussion also applies to the preamp section of a composite unit that has the preamp and power amplifier on a single chassis.

The preamplifier may consist of an amplifier stage for a magnetic cartridge, a group of rumble and scratch filters, a tone-control section and a low-impedance output stage.

Fig. 1 is the schematic of the Eico HF-61A preamp. A simple yet complete unit, it lends itself easily to analysis and circuitry comparisons.

That the unit is built for versatility is especially noticeable at the phono input, where there is a special slide switch for selecting one of two record players. This is useful for individuals who use a record changer for old 78- and 45-rpm discs and a turntable for 33's. Phono 2 has two input jacks, J2


*Electronic Instrument Co. (EICO), Long Island City, N. Y.

CUSTOM HI-FI PREAMP

and J3. J2 is compensated for high-output magnetic cartridges. Fig. 2-a shows how this section can be simplified when only one input is necessary.

The output from the phono pickup is fed to a high-gain amplifier stage for a magnetic cartridge. Not only must this stage provide a gain of about 50 at mid-frequency, but it must also incorporate the circuitry for the various record equalizations. The most common

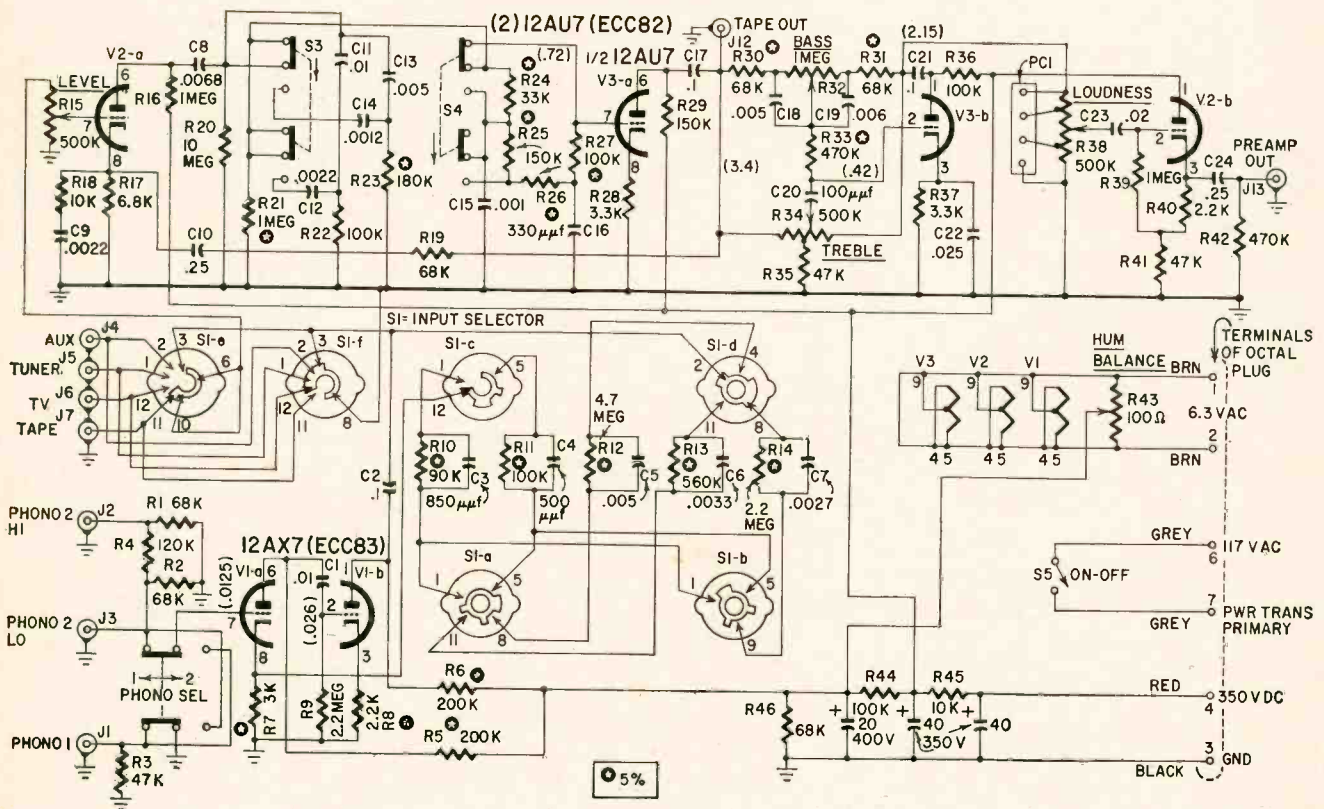Engineering considerations in amplifier design




NOTES

Selector switch S1 shown in TAPE position. Moves clockwise to TV, TUNER, AUX, COL, LON, RIAA, AM-78, EUR-78.

Rumble filter S3 shown in flat position. Moves down to 50Ω and 100Ω.

Scratch filter S4 shown in FLAT position. Moves down to 10 KC and 5 KC.

Fig. 1—The Eico HF-61A preamp.

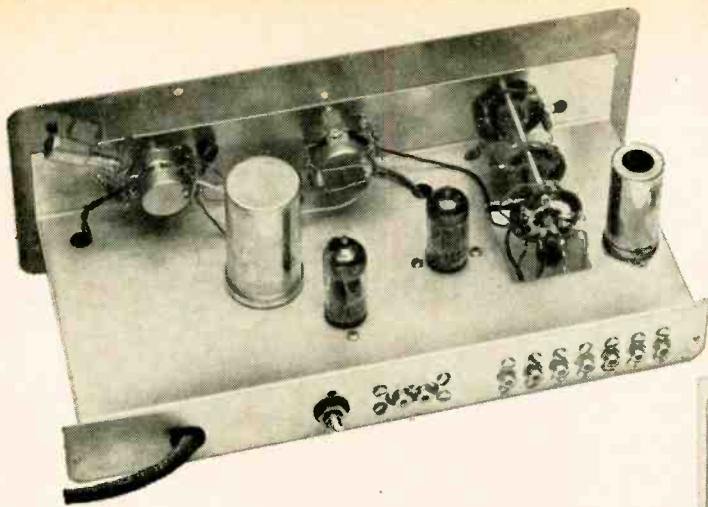

Chassis layout of the HF-61A. Input jacks and hum-balance control are on back panel.

The Eico HF-61A, a control preamp.



equalization in use today is RIAA-Ortho. Some equipment manufacturers feel that equalization for Columbia, London, American 78 and European 78 records should also be included. This is done here by switching networks with sections S1-a through S1-d on the INPUT SELECTOR. Actually, the curves for all these equalizations vary slightly from each other, and any slight compensation, although approximate, can be made by adjusting the tone controls.

Hum, noise and distortion

Fig. 2 shows the schematics of two magnetic-cartridge amplifier stages featuring RIAA equalization. Fig. 2-a is the same circuit used in Fig. 1—this time shown with only a fixed RIAA compensation. The stage must be designed for a minimum of hum and distortion. Frequently, one of these factors is sacrificed for the other. Circuits using feedback usually do both and have minimum distortion without excessive hum.

Low hum levels in a feedback circuit are possible; 50 db of hum below full output is not too difficult to get. You can get somewhat lower hum, but higher distortion, if you use a lossier, rather than a feedback circuit (Fig. 2-b).

Several manufacturers have attempted to eliminate hum entirely by using transistors in this stage. While they

got rid of the hum, the transistors sometimes introduced a more annoying factor—a high noise or hiss level. At the present state of the art, a good 12AX7 or its European low-noise equivalent, the ECC83, is probably superior to the transistor in this application.

Careful design and layout can overcome the many hum, noise and distortion problems inherent in the magnetic-cartridge preamplifier stage. However, it would be preferable to eliminate this stage entirely.

Several ceramic cartridges on the market are as good as many magnetic types and require no more gain from the preamp than does a tuner—making the extra amplifier stage unnecessary. The better ones are accurately equalized to the RIAA curve. Using these cartridges, we can get comparable results without the drawback of the hum, noise and distortion inherent in some of the amplifier stages designed for magnetic cartridges.

The phono amplifier output as well as the high-level inputs (J4, J5, J6 and J7) are all fed to a selector switch, S1-e, where the particular channel to be used is chosen. Barring the use of the selector switch for any other function, input selection can be handled by a single-pole five-position rotary switch (Fig. 3). However, switch S1 on the HF-61A accomplishes one more important function not possible with a jobber

stock item. Section S1-f shorts to ground all inputs not in use to avoid crosstalk.

S1-e leads to a level control. Although theoretically a simple attenuator, a pot has a small inherent capacitance from the sliding arm to ground. So, if its value is made too large, some settings of the control result in rolloff at the high frequencies. Values between 500,000 ohms and 1 megohm will give satisfactory results. Lower values can be too much of a load on the inputs.

The networks and switching for scratch and rumble filters are between

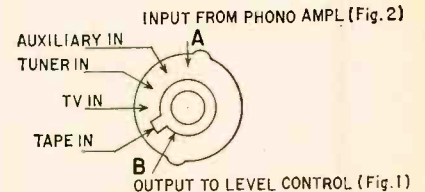


Fig. 3—Input selection can be handled by 1-pole 5-position rotary switch.

V2-a and V3-a. Rumble switch S3 moves down for 50- and 100-cycle cutoffs. Scratch filter switch S4 moves down for rolloffs at 10 kc and 5 kc. In the position shown, there is no filtering action. Sliding the switches down provides for rumble and scratch filter action. Since each switch has three positions two degrees of filtering can be provided, with the remaining position for flat output.

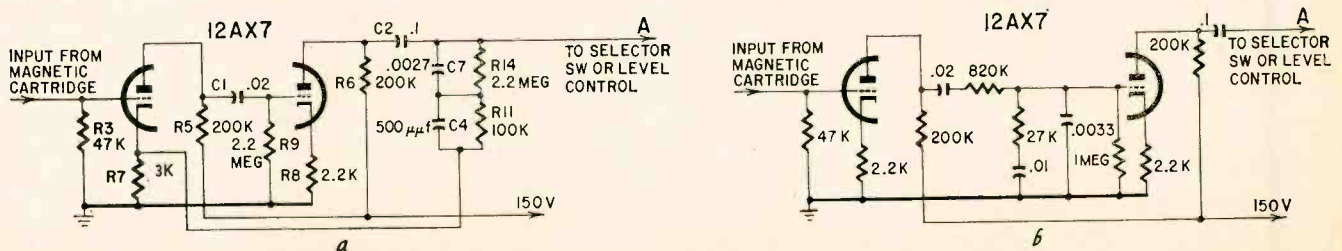


Fig. 2—Equalization circuits: a—feedback type; b—lossier type.

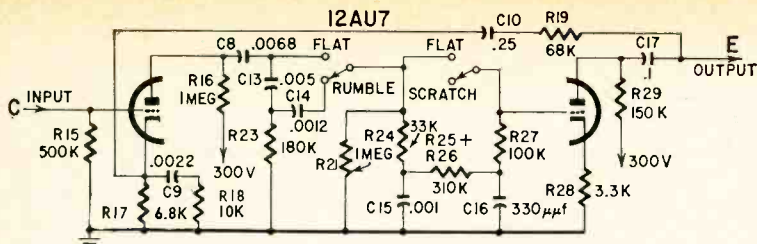


Fig. 4—Simplified feedback type scratch and rumble filters.

When good mechanical equipment is used in conjunction with a preamp, the scratch and rumble filters are not an absolute necessity. A good tone control, such as the Baxendall type, can be used for some of this filtering action. However, if these controls are desired (scratch and rumble), they should be

this point in the circuit, the LOUDNESS control can serve as a volume control for monitoring the signal being recorded, without affecting the actual recording. The LEVEL control, R15, limits the signal strength to the tape recorder to undistorted amplitudes. The preamp has a very-low-impedance out-

Feed the output from this, A, and the other inputs to a selector switch in (Fig. 3). The output from this switch, B, can go to a level control and then to the scratch and rumble filters (C in Fig. 4) when desired; or else it can go directly to the tone controls (D of Fig. 5-a or 5-b). If scratch and rumble filters are used, the output from these, E, can be connected to point F on either tone-control system, omitting the first tube and associated circuitry. The tone control output, G, can serve as the preamplifier's output. A conventional, well-filtered power supply can be added, using the rectifier circuit shown in Fig. 6 and the filtering circuit connected between the red and black leads of Fig. 1.

Many combinations are possible and

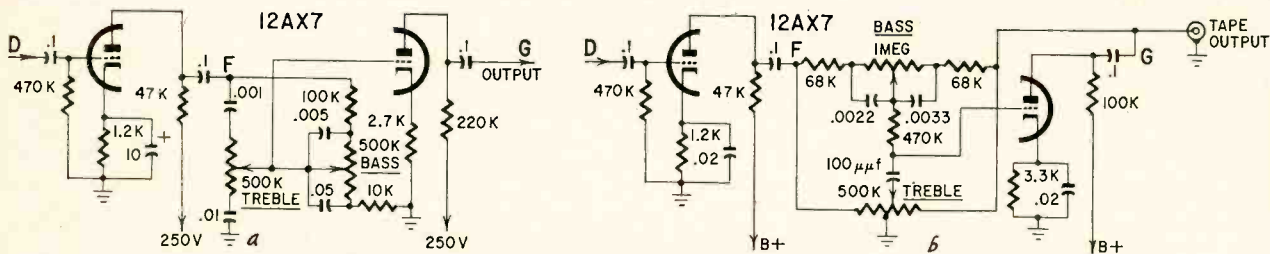


Fig. 5—Tone control circuits: a—losser type; b—Baxendall feedback type. When used with Fig. 4 circuit, eliminate everything ahead of point F.

inside a feedback network (Fig. 4). In the Eico HF-61A, this feedback network is from the plate of V3-a to the cathode of V2-a through R19 and C10 (Fig. 1).

Tone controls

For many years, the most popular type of tone control was the losser. No feedback is included in the circuit. As a result, response was seldom perfectly flat and distortion was high. An excellent system, the Baxendall gives perfectly flat response with cancellation of distortion in the tone control stage. This is done with the help of the feedback loop (from plate to grid which also provides the tone control action (Fig. 5-b).

An output to a tape recorder should come from some low-impedance point in the unit. It should not include loudness compensation, but should include rumble and scratch filters, if any. This output should come before the tone controls because of the lack of linearity in these circuits. However, when using the Baxendall type, this objection is minimized.

To do all this, a cathode-follower output should be placed before the tone controls for the tape takeoff. However, a low-impedance output can be taken directly from the feedback type Baxendall tone control, if used (Fig. 5-b). The HF-61A uses the low impedance at the plate of V3-a (the result of feedback) for this output. In this instance, there is no undesirable tone-control coloration when recording.

The LOUDNESS control, compensating for ear inefficiencies at the high and low frequencies at low output levels, follows this circuit. When located at

put because of the cathode-follower action of V2-b.

One note about the power supply is highly important for good results from any preamp.

A good, well filtered power supply is necessary. However, many separate filter capacitors are frequently provided in one metal can. This can lead to coupling within the can between the individual capacitors, resulting in excessive 120-cycle ripple being introduced into the high-gain phono amplifier section. It is thus necessary to have a physically separate decoupling capacitor for the earlier preamplifier stages.

Build your own

A simple preamp can be made by combining some of the drawings. For example, you can start with a phono equalizer stage, either Fig. 2-a or 2-b.

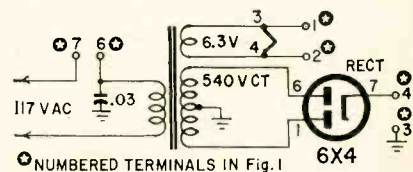



Fig. 6—Power supply used to convert Eico HF-61 into a self-power unit.

interesting results can be achieved.

A general note on wiring is important to the successful completion of any preamp. Beware of noise-causing rosin joints or rosin flux flowing into sockets. If necessary, clean the sockets with contact cleaner when the pre-amplifier construction is completed. Pay careful attention to necessary shielding and rules concerning ground loops to avoid hum and oscillation caused by electrostatic and electromagnetic fields. END



Suggested by G. Auman

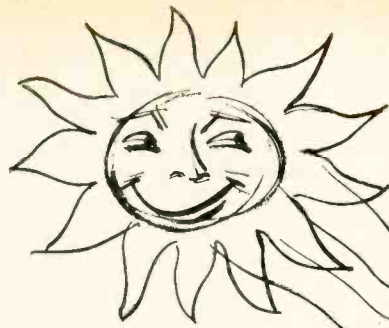

LIGHT-WAVE Communication



ORDINARY daylight and infrared light are the signal carriers of two new line-of-sight communications systems. One, the daylight version, is sold as a toy, yet works well enough to be considered much more. The infrared unit is sold as a communications device, a job which it fills effectively. Communications systems of this type would work well in space and might some day be used by a future space corps.

The toy is called a Sun-Fone. It consists of two units—a receiver and a transmitter. The transmitter is a plastic gun-shaped device with a mouthpiece on one end and a flexible mirror on the other. The mirror is adjusted so sunlight is reflected from it toward the receiver. Once aimed, the user speaks into the mouthpiece. The voice causes the mirror to vibrate at an audio rate, modulating the light-beam reflected by the mirror.

The receiver is another plastic gun-shaped device. The modulated light strikes a solar cell mounted at the rear of a trumpet-shaped light shield. It changes the modulated light into an ac voltage that is fed to a pair of headphones. They convert the ac signal back into sound and the listener can hear what his partner with the transmitter said. There is no amplifier and no batteries in the unit.

The infrared device is called an Infraphone. It is made by Infrared Industries Inc., Waltham, Mass. It is designed for commercial applications where it can fill the need for low-cost two-way communications in places where radio cannot be used or is not practical.


The unit is battery powered and can

The Infraphone. Large upper circle is receiver detector, smaller lower one, the infrared source.

be used day or night. With mirrors, it can even be used to communicate around corners.

All infraphone units are combination receivers and transmitters. Each looks a little like a reflex camera in which one lens is the infrared source and the other the detector. Both receiver and detector use a printed-circuit transistor amplifier; the transmitter to modulate the infrared output, the receiver to amplify the detected signal.

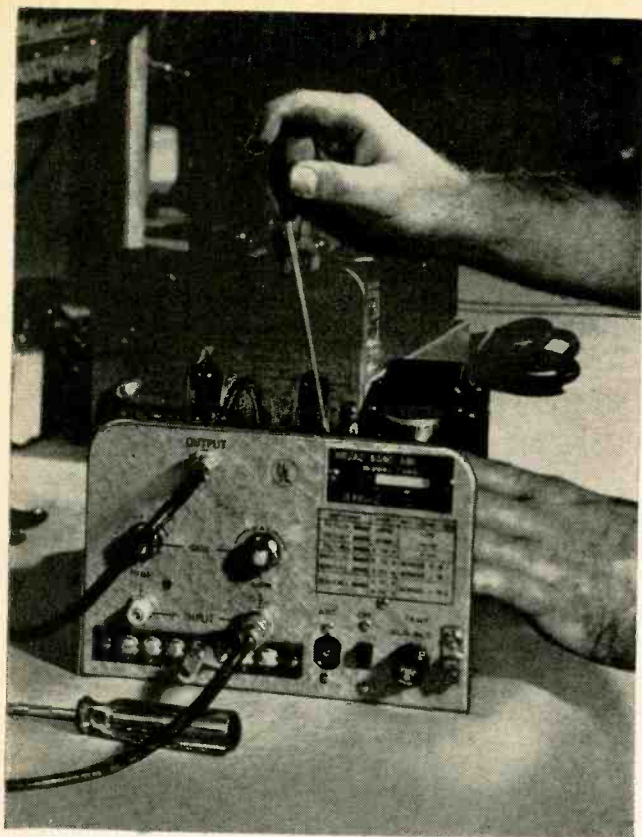Both units point the way to efficient two-way communications devices that may one day be as common as the telephone. END



ALIGNING WIDE-BAND VHF AMPLIFIERS

By JACK BEEVER*

Right equipment and techniques make it simple

ONE of the frustrating experiences in a bench technician's life is to be faced with the job of realigning a TV receiver after the customer has helpfully screwed down all the tuning slugs because he "found them all loose when the set quit, and knew they ought to be tight." When there are no alignment notes available on the receiver, even more puzzling things can occur. What technician hasn't watched the beautiful if response curve he had developed on the scope screen change to a horribly twisted affair just because he moved the alignment generator lead or turned the chassis over?

Well, TV receivers are simple! The technician is working "only" with amplifiers having 6-mc bandwidths at the most. Manufacturers of TV distribution amplifiers have had to face aligning amplifiers with vhf bandwidths of over 50 mc and to do it on a production-line basis with people who need not be artists in the alignment field.

The problems they face, and the answers they have worked out, may help the TV bench man in his struggles with misaligned TV sets because the problems only differ in degree, not in kind.

Let's look at the things that are done when a vhf broad-band amplifier comes off the assembly line. It is roughly in the condition of the TV set of the first paragraph of this article—all the alignment slugs are set at random, just as the assembler left them. Before anything else can be done, the input and

output circuits must be "matched"; that is, they must be made to show the proper impedances to the vhf signals they will receive or those they put out. In the equipment on the cover, this is 75 ohms, unbalanced, to match the standard cables (RG-59/U and RG-11/U types) used in wiring television distribution systems. If this is not done—and the next statement is important because it tells you why alignment curves can shift when leads are moved

—the sweep generator used to develop the frequency response curves will see an improper load, and reflections will be set up in the lead.

This produces standing waves on the lead and may "suck out" part of the generator's output at some frequency and enhance it at others. The technician will then try to align his curve flat when the generator's output is not flat and his curve has no relation to the actual response of the amplifier. Fig. 1

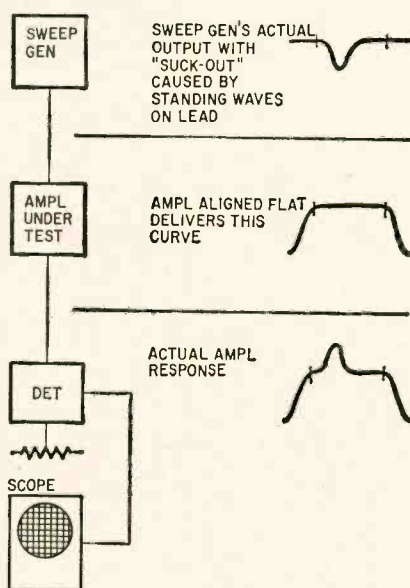


Fig. 1—Aligning an amplifier when generator output is not flat can produce strange effects.

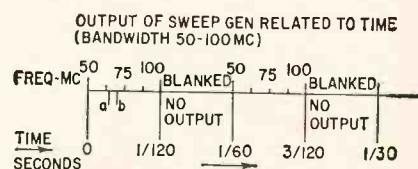


Fig. 2—Repetitive action of sweep generator.

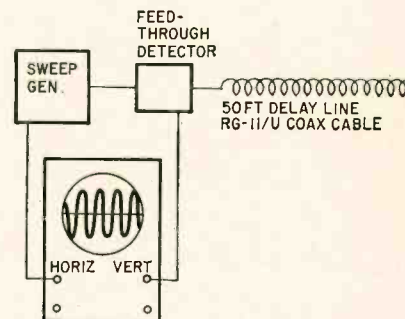


Fig. 3—Sweep generator feeding 50-foot delay line with feedthrough detector for developing scope pattern.

*Jerrold Electronics Corp.

graphically illustrates this effect.

Logically enough, the presence of standing waves on a line is used to determine the impedance match. If none exist, then the load is matched. The method of measurement is interesting and depends on the nature of sweep frequency generators.

A sweep frequency generator, at any one instant, is delivering a signal of a single frequency. A moment later, the frequency it delivers has changed, and this change goes on in one direction, say of increasing frequency until the upper band limit is reached. Then the direction of sweeping changes and the delivered signals are lowering in frequency until the lower band limit is reached. At this point the cycle starts again.

Fig. 2 illustrates this action with a generator using a 60-cycle sweep rate, and blanking. One full cycle of operation takes 1/60 second, the first half of this, 1/120 second, being occupied by the generator sweeping through all frequencies between the start (50 mc) and the finish (100 mc). The next half of the cycle is blanked—the generator output is cut off. The next cycle starts again at 50 mc and repeats the procedure.


Now examine Fig. 3. It shows a sweep generator feeding a long length of transmission line (50 feet or more at vhf), but has inserted into the input end of the line a vhf detector which does not interfere with the characteristics of the line (Jerrold D-86). The detector's output is connected to the vertical input of an oscilloscope, and the horizontal sweep is driven by a voltage from the generator which syncs it with the sweep's changing frequencies. Assume that the transmission line ends without termination—any vhf energy arriving at the end will reflect in its entirety and return down the line to the sweep generator. Let's see what happens!

Take an instant of time identified by point "a" in Fig. 2. At this instant, a signal of a given frequency starts down the transmission line. It takes a certain amount of time for it to get to the

end of the line and an equal amount for it to return (as a reflection) to the beginning. By the time this signal returns, the sweep frequency generator has changed its frequency to that indicated by point "b" in Fig. 2. Then, at the detector we now have two frequencies, that of "a" and that of "b". When they are mixed in a detector (often called a "mixer"), we get heterodyne beats, which are the sum and difference of the two frequencies. The sum will be from more than 100 mc to more than 200 mc, which cannot be reproduced by ordinary oscilloscopes. But the difference frequency will be only a few hundred cycles per second, depending on the delay caused by the line. This will appear on the scope.

We are, therefore, seeing a beat note which is the difference frequency between the outgoing generator signal and the returning reflection. We, therefore, know that a reflection exists and that the line is not terminated (or infinitely long, which is the same thing). We do not know how much is reflected. But, the amplitude of a beat note is a function only of the lower powered of the two signals which produce it. Therefore the amplitude of our scope response relates directly to the strength of the reflected wave, since it is the weaker of the two due to losses suffered in the 100 or more feet of line it traversed before returning to the detector.

If we were to terminate the end of the transmission line in its characteristic impedance, there would be no reflected wave and, therefore, no beat to make a signal on the scope. However, let's put numbers to this, as the engineers say. We need this because getting a perfect match is well nigh impossible with practical vacuum-tube circuits and we must set a specification somewhere that says how good (or poor) our match needs to be. This is usually stated in VSWR—voltage standing-wave ratio—the ratio between the maximum voltage peak found on a line and the minimum, ignoring line losses. If standing waves exist, such peaks will alternate along the line, and the ratio between the lowest voltage found and the high-

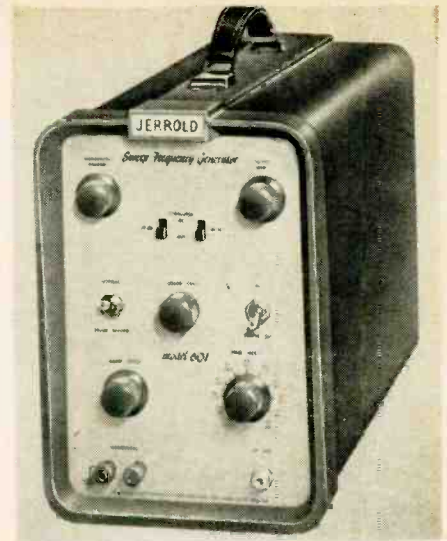

Model 601 sweep generator.

est is the VSWR. If there are no reflections, the voltage along the line will be constant, and the ratio between any two points will be 1 to 1, so a VSWR of 1 (to 1 is understood) represents a perfect match.

A measurement could be made by carefully calibrating the scope, generator, detector and line losses to determine the actual reflection, but a much better technique is one which removes all these hard-to-control variables. This is by direct comparison. If a mismatch of known and variable characteristics can be used to compare to an unknown, we can make them equal and then know the value of the unknown.

A variable attenuator can be placed in series with a delay line such as that of Fig. 3 and, by attenuating the direct wave (outgoing signal) and the reflected wave, be made to appear as though it were anything from a 100% reflection to a perfect match. Such an attenuator is shown in Fig. 4.

To make such a measurement, the equipment is set up as in Fig. 5. The attenuator is set to 0 attenuation, and the beat-note pattern on the screen of the scope to a known height. The delay


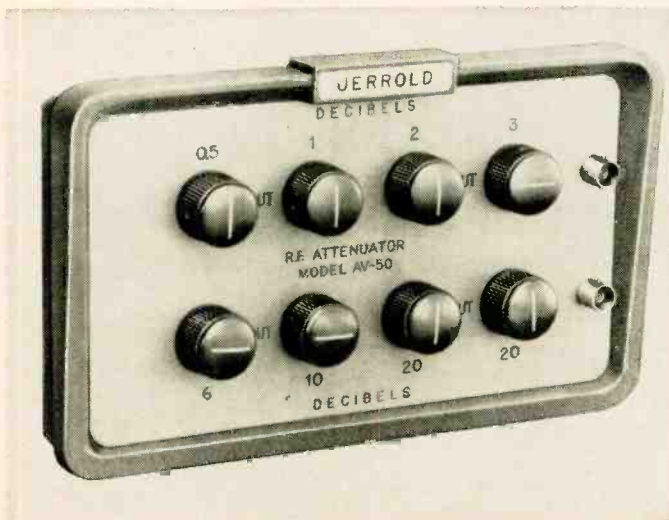


Fig. 4—Rf attenuator, model AV-50.

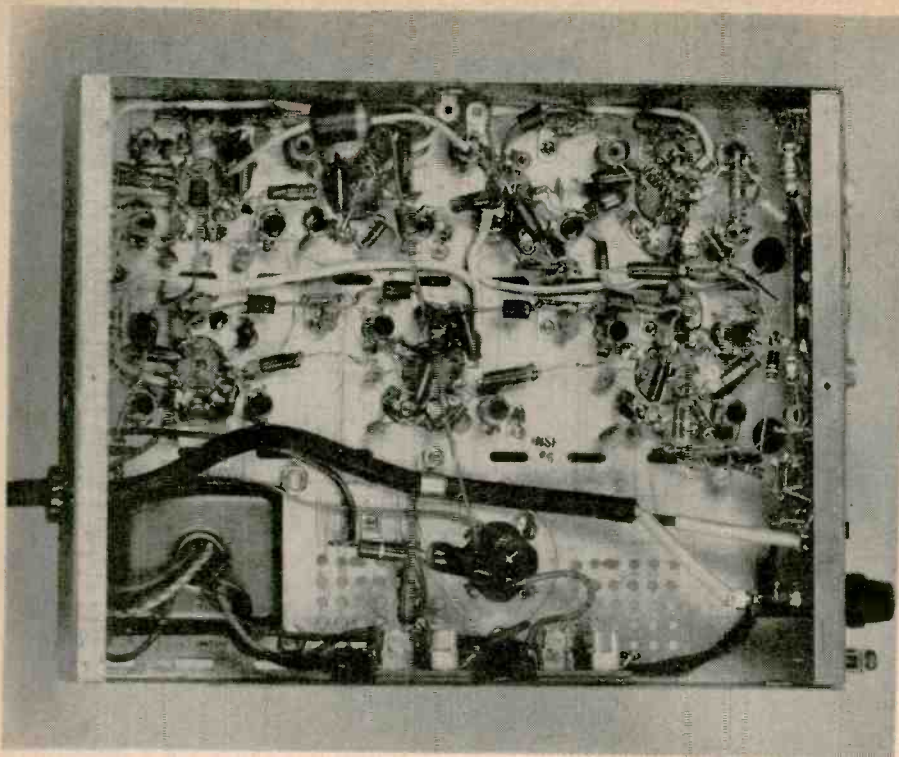

Model 2300 broad-band amplifier.



Underchassis view of the model 2300 amplifier.


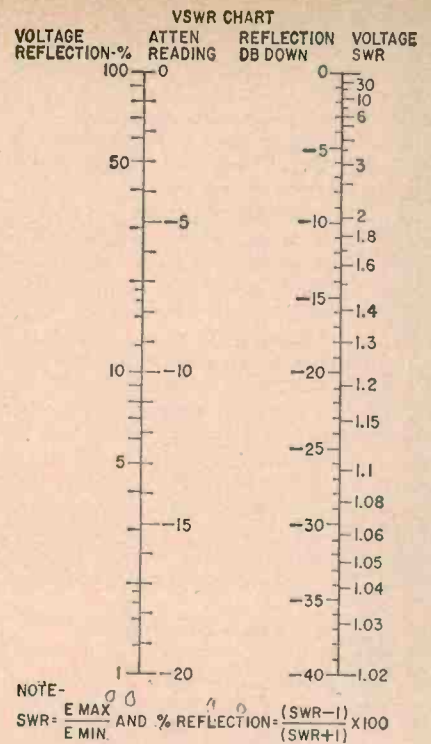


Fig. 6—VSWR nomograph.

line is then disconnected from the unknown impedance, at which time (if any degree of match is present) the beat-note pattern will increase in amplitude. The attenuator is then adjusted until the beat-note amplitude returns to the same height as before. The attenuator reading can then be compared to the nomograph of Fig. 6 to determine the VSWR. Since the attenuator acts upon the signal twice (once going and once coming back), its attenuation is actually twice that indicated. Thus, a reading of 20 db is actually 40 db of attenuation and indicates a voltage reflection of 1% or VSWR of 1.02 (a very, very good match!!).

Introducing the "flicker-dicker"

It is cumbersome to adjust two or three controls to get such a match in an amplifier input or output, so a continuous display technique was worked out in which the operator merely matches two traces on the scope screen. This is done by using a high-speed coaxial switcher which can switch these vhf currents from point to point without introducing significant mismatches in the lines involved. Such a switcher is seen on the cover. Fig. 7 is a simplified diagram of the setup.

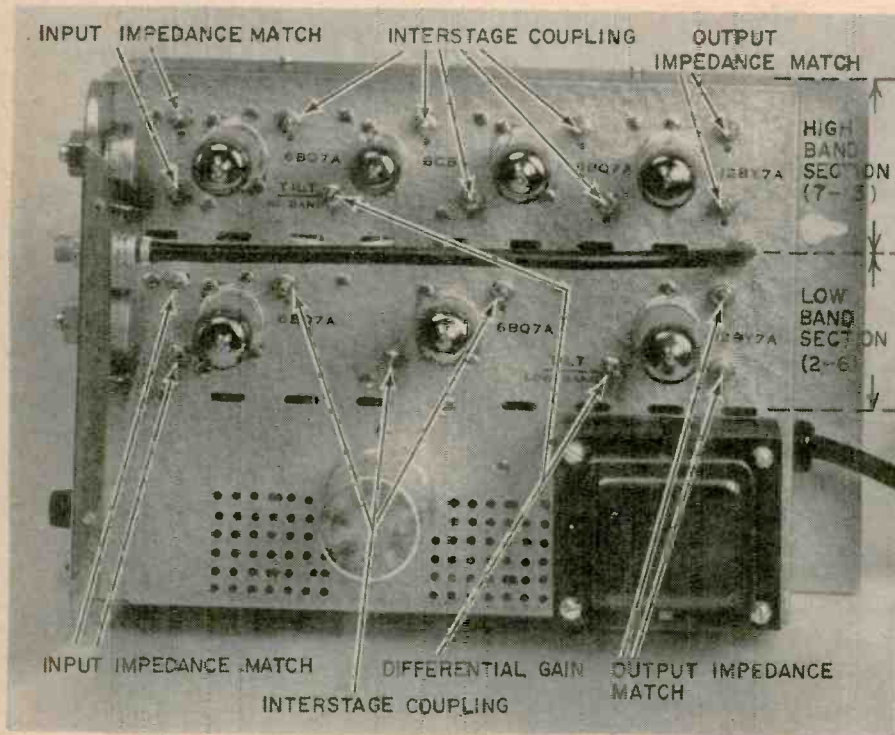

Model 2300 top-chassis view reveals number of alignment adjustments.

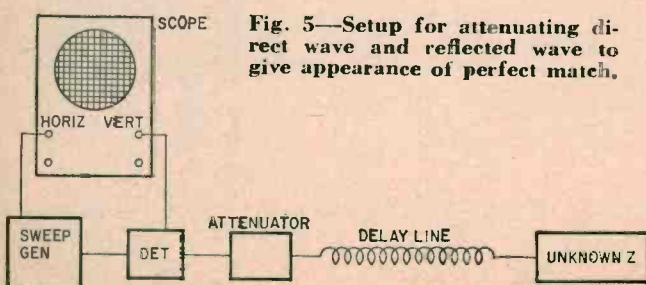


Fig. 5—Setup for attenuating direct wave and reflected wave to give appearance of perfect match.


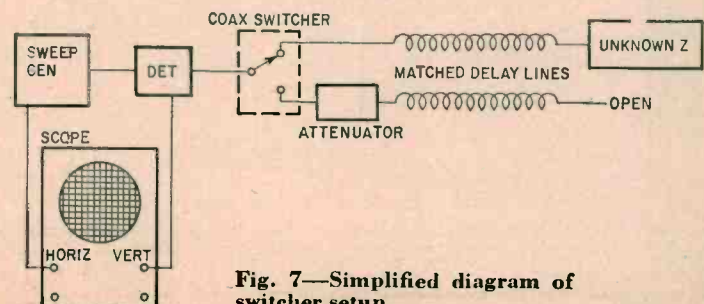


Fig. 7—Simplified diagram of switcher setup.

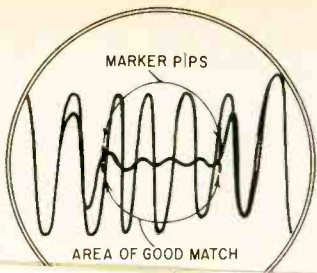

generator, it will trace line A in Fig. 10. During the second half-cycle, the blanking period (Fig. 2), there is no output and the scope presents line C in Fig. 10. This gives us a representation of the generator's output, one which will remain relatively true to other signals no matter where the scope's vertical amplitude is set.

At this point, the switcher flips to the up position and the generator out-

TRANSLATOR AUTHORIZATION FACT SHEET

ve to set up a TV rlf trans-
or your area and obtain proper
tion for the station. Or you
to legalize an existing booster.
select a vhf channel that will
ere with signals from other
ons or translators. Then pick
the translator. Instructions of
d installation can be found in
le by Philip Freen on page 42.
oration or association docu-
f the organization putting up
slator must be in order, and a
sheet showing the outfit's abil-
urchase the necessary equip-
andatory.
note-control point for shutting
he translator should it start
ig improperly must be allowed
he translator cannot be reached
han 15 minutes.

you will need permission from
inating station to rebroadcast
ansmissions.
his point you file an application
e Federal Communications Com-
Use Form 346, obtainable from
rest FCC field office or direct
e FCC, Washington 25, D.C. The
brought up so far are needed to
e this form.

you are ready to start work on
ion. A small building is prefer-
a housing for the equipment,
desired, a locked weatherproof
ounted right on the antenna mast
Notify the FCC a little ahead
of your intention to conduct on-
tests so you can conduct them
n as installation is complete.
en the station is in satisfactory
condition, file an application
Television Translator Station on
form 347. Two days after notify-
e FCC and the engineer in charge
field district you can start pro-
nning.

eral organizations manufacture
ranslator equipment that complies
all FCC requirements. They can be
l sources of information and as-
ice:

Electronics
re Ave.
chelle, N. Y.
-Tongue Laboratories Inc.
g St.
N. J.

Television Associates
an Div. of Blonder Tongue
er Rd.
e, Ontario, Canada

lectronics
H, Ariz.
onics, Missiles & Communications Inc.
Third St.
Vernon, N. Y.

tial Television
areholm Drive
geles 46, Calif.


merican Relay Systems
ain St.
Rapid City, S. D.

resistance depending upon lighting
conditions. Rarely will the failure
mechanism of a photoconductor
show up as a short; however, a
photoconductor may develop an
open circuit due to damage to the
cadmium-sulfide wafer which could
be the result of dropping the device
and cracking the wafer. The glass
envelope is quite rugged and capable
of withstanding more abuse than the
fragile wafer.

It is important that no moisture
enter the glass envelope, as radical
changes in resistance will result. This
can best be determined by measuring
the resistance of the photoconductor
in total darkness. Simply wrap the
suspected device in a dark cloth with
only the leads exposed and measure
the dark resistance. It should be
greater than 100K ohms. While all
photoconductors presently manufac-
tured by Sylvania are sealed in glass,
it is possible that some TV receiver
manufacturers are using those sealed
with epoxy resin. This material may
allow moisture to enter. For your

convenience, all Sylvania photo-
conductors contain the "Blue-Dot"
feature long found in Sylvania flash
bulbs. This is a blue colored dot
which turns pink with as little as an
8% increase in humidity. A photo-
conductor displaying the slightest
change in dot color should be dis-
carded even though it appears to have
normal characteristics; it will soon
become very unstable.

Undoubtedly, some TV receiver
owners will require education in
what should be expected of auto-
matic brightness and contrast con-
trols. There should be no apparent
change in picture quality when room
lighting is changed. This is the
purpose of the automatic feature
which may be demonstrated by
placing the hand over the photo-
conductor and observing the change
in brightness and contrast. Many
observers will be surprised that the
change is not greater than it is; but,
as mentioned earlier, only a 50%
change is required from total dark-
ness to very bright room lighting.

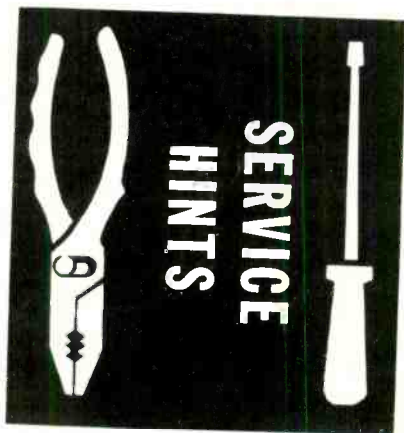


NO VERTICAL DEFLECTION

In servicing the RCA chassis KCS 94,
95 and 97, I found zero voltage on the
grid of vertical output tube VIII
(6AQ5) and about 200 volts on the
plate. I then noticed the white
horizontal line did not seem bright
enough and checked voltage on the
CRT which was too low. In tracing
from pin 10 of the CRT, I found
R182 resistor (270K ohms) open.
Replacing the resistor restored pic-
ture to normal. This same condition
and defect was identical in all three
chassis.

sweeping at the rate which
full deflection to the half-cycle of sweep
setup of Fig. 9.

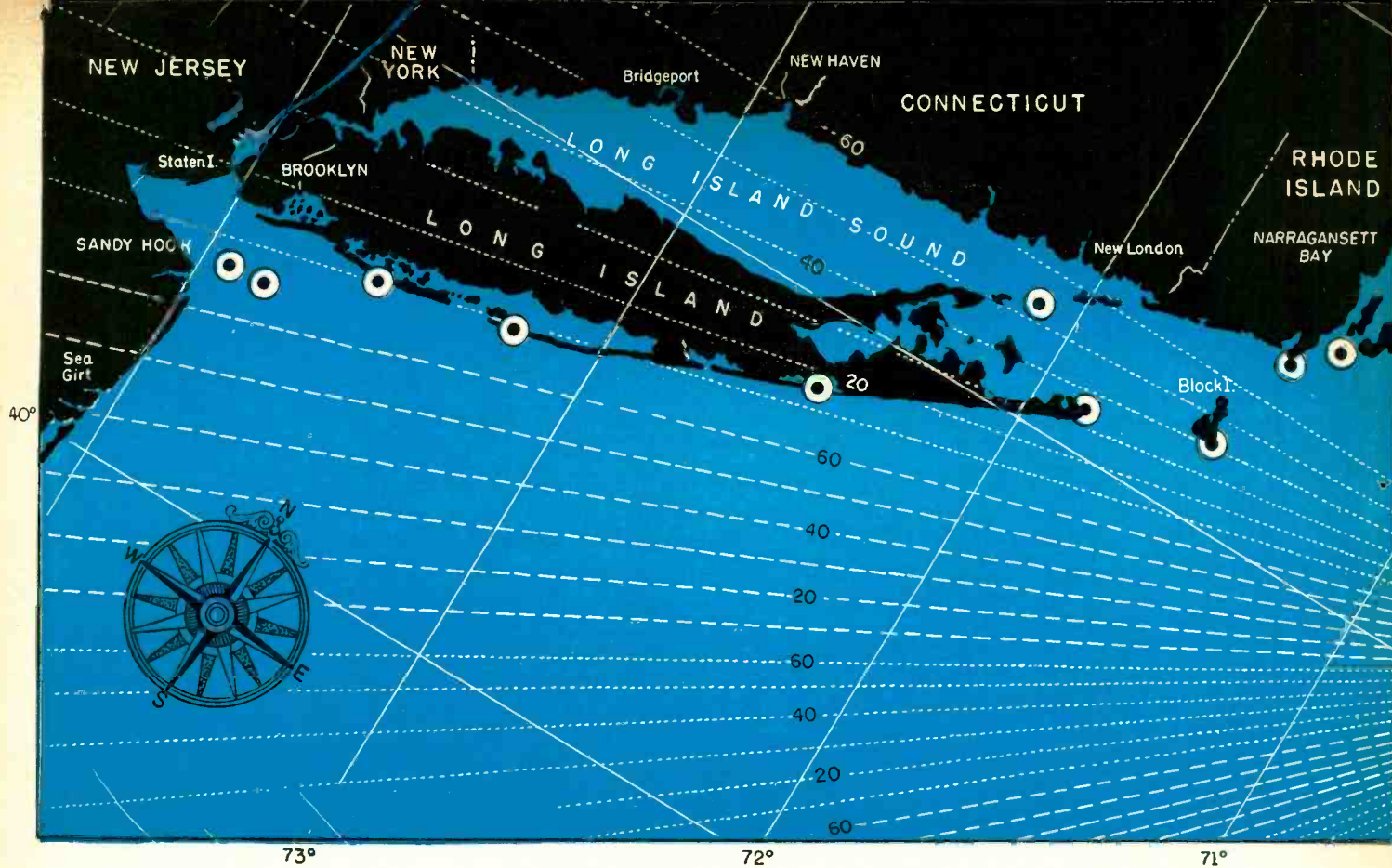Mack Kunzman
San Francisco, California
NO-KINK TEST LEADS



CONSOLAN—

New navigation aid for small boats needs only a surplus long-

By **ELBERT ROBBERSON**

AM accustomed to odd questions. Like, someone will telephone and say, "I am sailing single-handed to England next month. What kind of communications equipment can I get that doesn't cost much, and doesn't need any batteries to speak of, and that will bring help if I am dismayed in mid-Atlantic."

The answer: homing pigeons. I can handle most questions of this type with similar answers.

But last spring I began to get calls: "Tell me something about Consol. Is it good? What kind of equipment do I need to pick it up? How does it work? How accurate is it?"

It seems that hundreds of yachting laddies were planning to enter the 1960 sailing race from Newport, R. I., to Bermuda. Word had passed down the grapevine about a new radio aid to navigation that would tell a skipper his position without having to shoot the sun with a sextant, or make pips behave on an oscilloscope, or twist a DF loop. This would make small-boat navigation as easy as falling off a bar stool. The idea had the boys drooling for the dope.

All I knew was that there were Consol beacons broadcasting in Europe and that airplanes using them got around in the fog just fine. But the fact there are Consolan stations in the US that can be used by boats was apparently one of the best kept secrets in electronics.

It is likely that electronic service agencies around coastal waters will begin to hear questions about Consol and Consolan with increasing frequency. You can be the first in your neighborhood to know the answers. And there might be something in it for the shop able to set up radio receivers to pick up Consolan signals. Here is the information I have been able to dig up.


During World War II, English pilots picked up curious radio signals from Germany. It was not long before they deduced that the directional pattern was just as useful for navigating Spitfires as Messerschmidts. This was Sonne, presumably so-named by the Germans because of the resemblance of the pattern to sunrays.

When the British built their own stations, they named the system Consol. In the United States, a slightly different system is called Consolan. All of

them produce the same end result: a long-range pattern of radial sectors of dots and dashes. Simply by tuning in the signal and counting the dots and dashes heard, a vessel's line of position may be obtained from a set of tables or a Consolan chart. The only special requirements for the receiver are that it tune to frequencies between 190 and 200 kc, and that it have a bfo. No tricky circuits or adjustments are needed. All you need are ears and the ability to count dots and dashes. Consolan stations are operating at Nantucket and San Francisco, and a Consol type station in Miami is scheduled for completion in late 1960 or early 1961. There are five Consol stations in Europe, and Japan has a similar system.

How Consol works

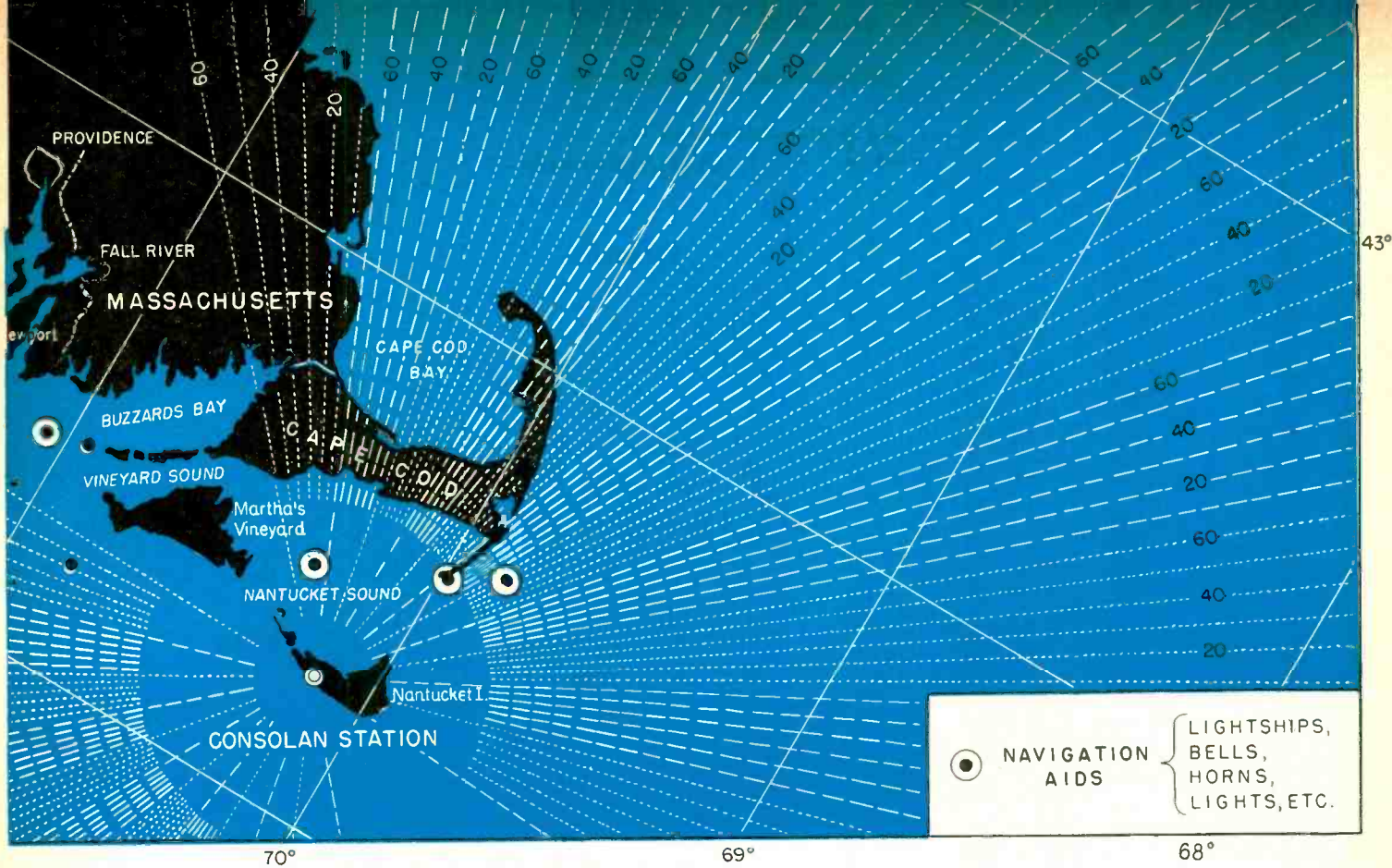Three vertical radiators in a line spaced three wavelengths apart and excited in phase with a power ratio of 1 to 6.75 to 1 produce the radiation pattern shown in Fig. 1. If the phase of the north tower is advanced 90° and the south tower retarded 90°, the pattern will be squeezed as shown in Fig. 2. And if this is reversed, so the north tower lags by 90° and the south tower



WHAT IS IT?

wave receiver, and some simple modifications you can make.

leads the same amount, the pattern is squeezed in the other direction, making a mirror image.

If we attach a keyer to the phase-shifting networks so the end towers are alternately leading and lagging, the pattern flip-flops between the solid and dotted lines of Fig. 3. With the keyer making interlocking dots and dashes for the two end towers, a receiver moved around the station would pick up dots in one sector and dashes in the next "around the clock." Between sectors the dots and dashes would merge into an "equisignal." There would be 24 equisignals, and each could be used like a radio range to "home" on the station.

To make the system useful on more than just 24 course lines, one more element is added: a rotating goniometer. The principle of the goniometer is illustrated in Fig. 4. This goniometer couples the transmitter to the towers so that, as it rotates, the excitation to the end towers undergoes a gradual change of phase from plus 90° to minus 90° (or the opposite). The effect is that the dot-and-dash lobes and the equisignal bearing lines rotate around the station.

The goniometer is driven at a constant speed of 48 revolutions per hour, taking 75 seconds to complete a revolution. Attached slip rings control the dot-dash keyers and the station-identification keyers. At the beginning of a sequence, the end towers are disconnected and the identification keyer sends out the station's identification letters for 7.5 seconds on the center (nondirectional) tower. Then for 30 seconds, as the phasing changes through 180°, the end towers are fed interlocking dots and dashes. A 7.5-second silent period or an identification follows; then another 30-second phasing sweep.

Each sweep 60 dots and dashes are sent out. The number and order of the dots and dashes you hear depends upon your geographical location with respect to the antenna lobes. Since equisignals are repeated approximately every 20° around the station, it is necessary for you first to know approximately where you are, but this ambiguity is of small importance in a boat because your position by reckoning (or guessing) will indicate in which of the sectors of the Consol pattern you are.

In effect, your count of dots or

dashes tells you how far around the circle from the starting point the goniometer has turned to bring the equisignal to you. Hence, it gives your angular relation to the transmitting station.

Thus, if you happen to be on one of the lines marked "60" on the chart, you are along the leading edge of a segment and will hear 60 dashes (or dots) before the segment passes you (minus a few as you get into the equisignal). If you are in the middle of a segment, however, it will sweep around to the equisignal halfway through the listening period, and you will hear about as many dashes as dots.

Consolan is the same as Consol except that only two towers spaced three wavelengths apart are used. Due to the fact that three wavelengths very nearly amount to 3 miles at 190 kc, this saves a lot of ground area for the farmers. The lobe nulls become zero with Consolan, whereas they are filled in by the center tower of a Consol station. As far as the use of the facilities are concerned, however, operation is the same.

Theoretically, to obtain a Consol (or Consolan) line of position, you tune the receiver to the frequency with the bearing on and the ave off. Immediately after

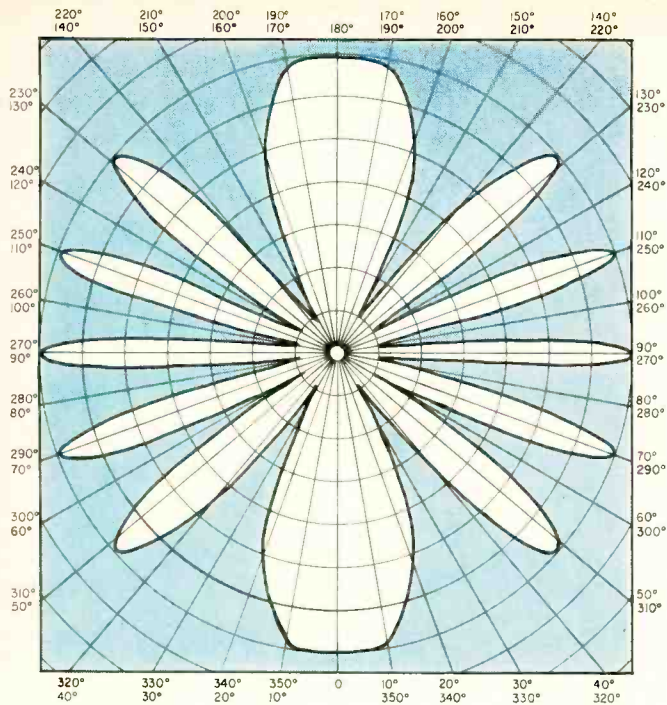


Fig. 1—Fundamental pattern from which Consolan pattern is derived.

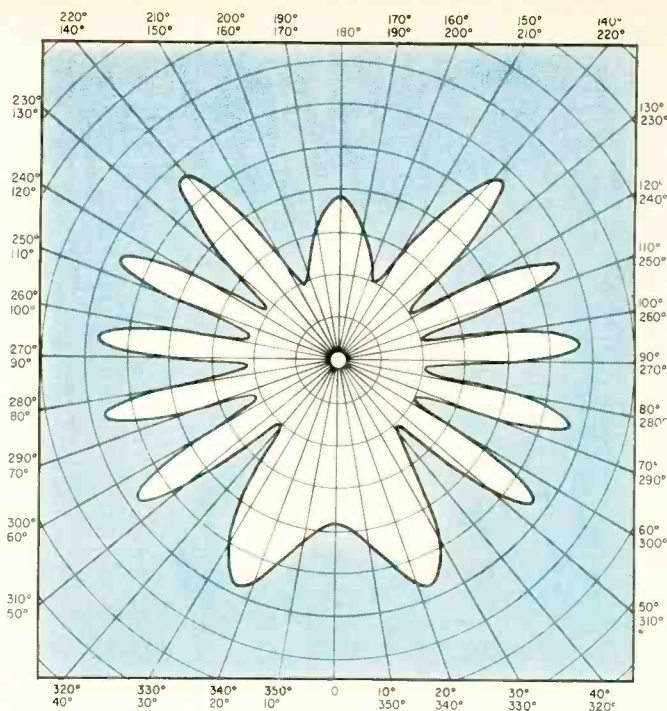


Fig. 2—Effect of 90° lead on north and 90° lag on south tower.

the identification signal is sent in code, start counting the first thing heard, dots or dashes, until they blend into the equisignal. Then, just look on the Consolan chart and find the line that corresponds to your count. For example, a Consolan line from Nantucket (TUK) for 40 dots brings you to the Kitchen Shoals buoy off the eastern tip of Bermuda. Consolan chart lines are inscribed every 10 or 20 characters; to find intermediate lines, just interpolate.

There are also Consol and Consolan tables for the various stations. These give bearing lines in degrees which can be marked on a conventional navigating chart.

In practice, the equisignal may be several characters wide or obscured by noise, so that one or more characters will be lost in the mud. To get an accurate number in spite of this, we add one refinement to our counting. It is based on the assumption that, during

the equisignal period, the same number of dots and dashes is lost. Because 60 dots and dashes are transmitted, we can tell the exact number of characters that were not recognized, by subtracting the total number of dots and dashes heard from 60. Divide this difference by 2, and you have the number of dots and dashes lost.

For example, on Long Island Sound in my own boat, the *Short Wave*, I tune in TUK at Nantucket and start count-

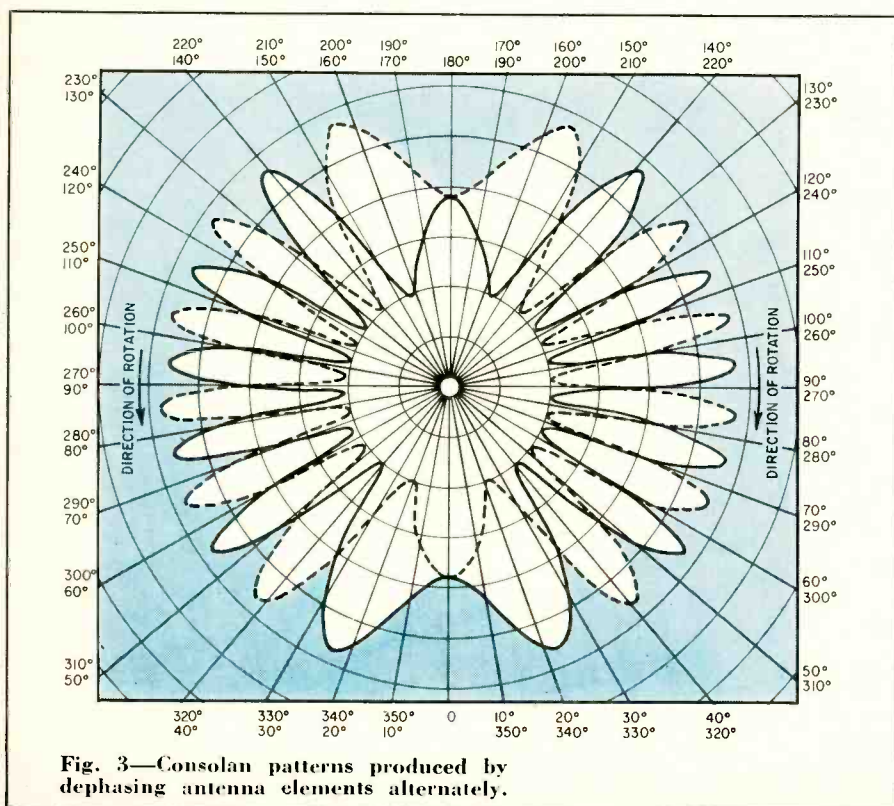


Fig. 3—Consolan patterns produced by dephasing antenna elements alternately.

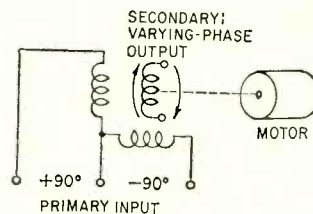


Fig. 4—Goniometer makes pattern rotate.

ing after the station identification is sent. I get 39 dots, then equisignal, then the dashes become audible and I count 17 dashes. Because 39 and 17 add up to 56, I see that I have lost four characters to make up the 60. This means that I lost two dots and two dashes. Adding the lost two dots to my count of 39 gives 41. Therefore, according to my chart, I am on the 41-dot line which extends from Mamaroneck, N. Y., eastward down Long Island Sound.

At the present time, due to the lack of additional stations from which to obtain cross bearings, it is necessary to use a course line or to take a radio direction-finder bearing on one of the numerous radio stations along coastal waters to determine a "fix." However, in the many cases for which Consolan is appropriate, this is no great disadvantage.

A simple regenerative receiver,

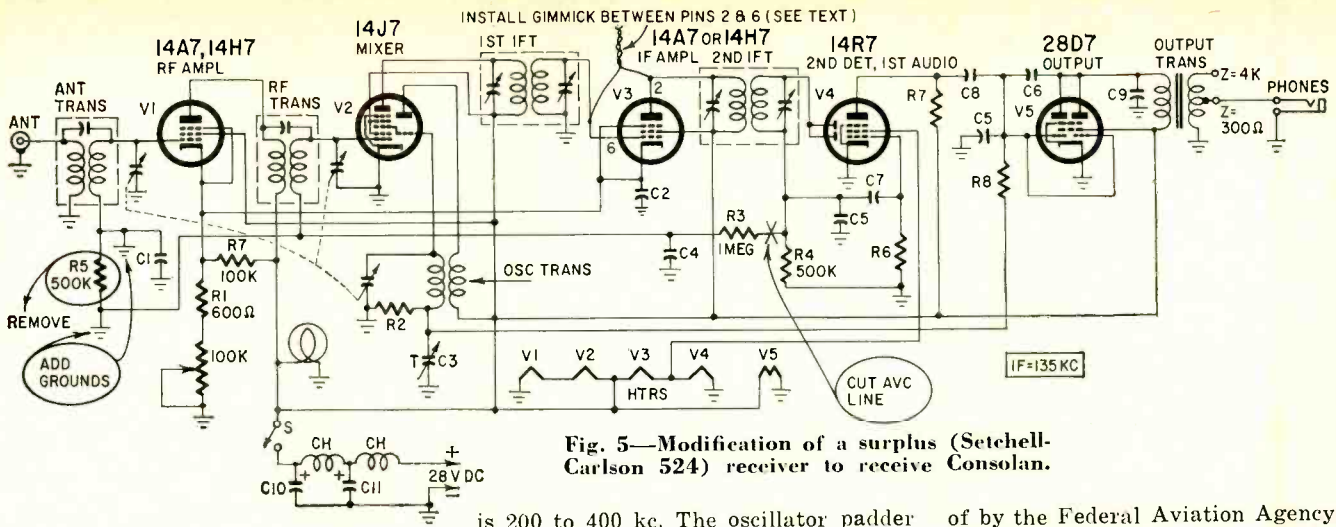


Fig. 5—Modification of a surplus (Setchell-Carlson 524) receiver to receive Consolan.

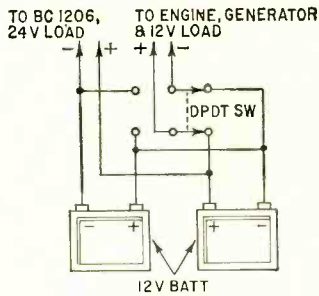


Fig. 6—Battery hookup on author's boat.

vacuum tube or transistor, is entirely suitable for Consolan reception. Too many of these have been described in the literature for me to make any further suggestions on their construction.

Another very good receiver for the purpose can be obtained from military surplus for under \$10—the Setchell-Carlson BC-1206 Radio Range receiver. This set is originally wired with avc and has no bfo. I altered one of these for the *Short Wave* by grounding the avc bus and by soldering a 1¼-inch length of insulated wire to the grid terminal of the if amplifier tube. Dressing this wire across the socket and around the plate terminal for the same tube introduces enough positive feedback, or regeneration, to cause the stage to oscillate when the sensitivity control is advanced. This self-oscillation serves the same purpose as a bfo, permitting reception of the CW Consolan signals. Fig. 5 indicates the changes made.

The BC-1206 operates on from 24 to 28 volts. On the *Short Wave*, this voltage is obtained by connecting my two 12-volt engine batteries (the one in use and the reserve battery) in series, as shown in Fig. 6. This hookup, with a double-pole double-throw 80-ampere battery switch, permits using either of the 12-volt batteries on the engine and to operate auxiliary devices while making 24 volts available at all times for the Consolan receiver.

One caution—using this hookup, it is imperative that the 24-volt receiver *not* be grounded. Otherwise, you will have serious trouble from an opposite engine ground when the switch is closed.

The frequency range of the BC-1206

is 200 to 400 kc. The oscillator padder on the main tuning capacitor can be readjusted to extend the tuning range to 190 kc at the expense of losing a few unimportant kc on the high-frequency end of the band. The same effect could be obtained by realigning the if transformer tuning to bring in 190 kc when the tuning capacitor is fully meshed.

The same kind of alterations can be made to conventional small-boat radio direction finders or low-frequency receivers not already equipped with a bfo. Another possibility is to construct a small self-contained heterodyne oscillator covering the range of from 190 to 200 kc. This should be built in a non-conductive container to give the circuit the maximum coupling to the input circuit of the receiver. To make a 194-kc CW signal audible, the external heterodyne oscillator is placed alongside the receiver and tuned to from 500 to 1,000 cycles above or below 194 kc. A compact transistorized oscillator designed for this purpose is available from R. B. Stoops, 52 Hoyt St., Stamford, Conn.

The Consolan system is an interim aeronautical aid to navigation which will be used until some future date (my guess is that this is a long way off) when an "ultimate" aeronautical aid is decided upon. The construction and operation of US stations is taken care

of by the Federal Aviation Agency.

Tables listing the location and bearing angles of US Consolan stations are printed in the US Navy Hydrographic Office and Coast Guard *Notices to Mariners* available to mariners at no cost. The US Navy Hydrographic Office, Washington, D. C., also issues a chart on which Consolan lines for TUK (Nantucket, Mass.) are inscribed: Plotting Chart (Newport to Bermuda), H.O. 16,510-A (\$1).

The following aircraft charts containing Consol and Consolan angles may be purchased from the Coast and Geodetic Survey, Washington, D. C.: Aircraft Position Chart, North Atlantic, 3071 (10¢)

Continental Entry Chart, East Coast, CEC-1 (50¢)

Caribbean Sea, GLC-9 (50¢)

Aircraft Positioning Chart, US-Honolulu, 3096 (for San Francisco, SFI)

Aircraft Positioning Chart, Caribbean Sea 3073 (for Miami, MIA)

Nothing is perfect, and Consolan is right up in there on this score, but here is a navigational aid for coastal waters that can be used to the fullest extent, requiring nothing more complicated than an ordinary "blooper" receiver. It is sure to find increasing use among boatmen as well as aviators. To be up to date, master its workings. END

NANTUCKET CONSOLAN STATION									
DOT SECTORS									
Count of Dots	True Bearing from Station								
	0	20 2	39 5	60 7	91 4	138 6	169 3	190 5	209 8
1	20 1	39 3	60 5	91 1	138 9	169 5	190 7	209 9	229 8
2	19 9	39 1	60 3	90 7	139 3	169 7	190 9	210 1	230 0
3	19 7	39 0	60 1	90 3	139 7	169 9	191 0	210 3	230 2
4	19 6	38 8	59 9	89 9	140 1	170 1	191 2	210 4	230 3
5	19 4	38 7	59 7	89 5	140 5	170 3	191 3	210 6	230 5
6	19 3	38 5	59 5	89 2	140 8	170 5	191 5	210 7	230 7
7	19 1	38 3	59 3	88 8	141 2	170 7	191 7	210 9	230 9
8	18 9	38 2	59 1	88 5	141 5	170 9	191 8	211 1	231 0
9	18 8	38 0	58 9	88 1	141 9	171 1	192 0	211 2	231 2
10	18 6	37 9	58 7	87 7	142 3	171 3	192 1	211 4	231 4
11	18 5	37 7	58 6	87 4	142 6	171 4	192 3	211 5	231 6
12	18 3	37 5	58 4	87 1	142 9	171 6	192 5	211 7	231 7
13	18 1	37 3	58 2	86 7	143 3	171 8	192 7	211 9	231 9
14	18 0	37 2	58 0	86 4	143 6	172 0	192 8	212 0	232 1

Fig. 7—Portion of table showing bearings from TUK against given dot counts.

HEAT to electricity

The Klein converter, a new device
for direct conversion of heat into electricity

By E. AISBERG*

ON July 1, 1960, the Academy of Sciences held a meeting in Paris, France, that may become historic. That day Francis Perrin, High Commissioner of Atomic Energy, read a note from Siegfried Klein entitled modestly, "Obtaining a Direct Current of Electricity from an Ionized Gas or Vapor."

Siegfried Klein is far from being unknown among electronics people. He has been known for several years as the inventor of the first loudspeaker, without a membrane, in which the sound waves are generated by vibrations of molecules of an ionized gas—the Ionophone.

One of the classic problems in the domain of energy is that of converting heat directly into electricity. The method used at present in atomic reactors appears thoroughly barbarous in the eyes of scientists. Between the calories that enter and the output watts from an atomic converter one finds several intermediary conversions. The heat boils water or heats a liquid metal. The vapor produced operates turbines that drive electrical generators. We can see how little logic there is in this and how urgent it is to find a direct method of converting heat into electricity.

In one type of heat-to-electricity converter—the MHD generator—heat ionized a gas, producing a *plasma*. At high temperatures, the extremely rapid movement of molecules produces numerous collisions between them. Some atoms are broken into two parts—a positive ion and a negative electron. By passing a jet of plasma through a magnetic field, we can separate the negative and positive charges, for the field impels them in opposite directions. They are then directed toward two electrodes which become the terminals for the electromotive force.

Siegfried Klein works with the same ionized gas. But he separates the opposite charges without using any deflecting field, magnetic or electric. And it is in this that his invention is remarkable.

Siegfried Klein's paper

We have been able to establish an important separation of positive and negative electric charges in a jet of ionized vapor, metallic or otherwise. This separation of charges is obtained without applying a magnetic or electric field in the vicinity of the collecting electrodes.

The experimental equipment shown uses mercury vapor. The setup consists of a glass vessel whose base forms a reservoir containing a certain amount

*Director, *Toute la Radio*, Paris, France.


of mercury. This reservoir has a vent (2) at its top and a tube (5) connecting the upper portion to the base. This section extends upward as a glass cylinder with metallic electrodes (3) and (4). The lower portion of the reservoir is encircled by a coil through which a 40-mc rf current flows to ionize the mercury vapor. Before being put into operation, the apparatus is evacuated to a pressure of about 10^{-3} millimeter of mercury.

Once ready, the device is placed over a Bunsen burner and the mercury brought to a temperature of several hundred degrees centigrade. Because of this heating, the mercury-vapor pressure in the reservoir rises to several centimeters of mercury and a powerful jet of vapor, ionized by the 40-mc field and carrying about 1 gram of mercury per second, traverses the vent and the electrodes. These vapors condense in the upper portion of the apparatus, where there is a vacuum in the order of 10^{-2} millimeter of mercury. The condensed mercury descends through the tube (5) into the base of the reservoir.

Experiments show that a continuous emf of approximately 10 volts appears between electrodes (3) and (4). The characteristic of output voltage vs load is that of a battery having in the most favorable case an internal resistance of about 50 ohms. The value of the emf is within large limits independent of the high-frequency power absorbed in the process of ionizing the mercury vapor. Varying the degree of ionization, on the other hand, modifies the amount of current collected between the electrodes. The current also depends on the amount of ionized fluid that traverses the equipment. For no load it starts from zero and increases rapidly. It reaches a maximum and then starts to decrease again, the flow of mercury continuing to rise. This fact is important, since it demonstrates that for a low degree of ionization of the vapor it is possible to obtain relatively strong currents. The amount of rf power absorbed increases directly with vapor flow.

It is worth noting that electrode (3) is near the vent and is always negative with respect to electrode (4). If more than two electrodes are placed in the path of the vapors, there is always 10 volts between two successive electrodes. Everything takes place as if two comparable electric generators were hooked up in series.

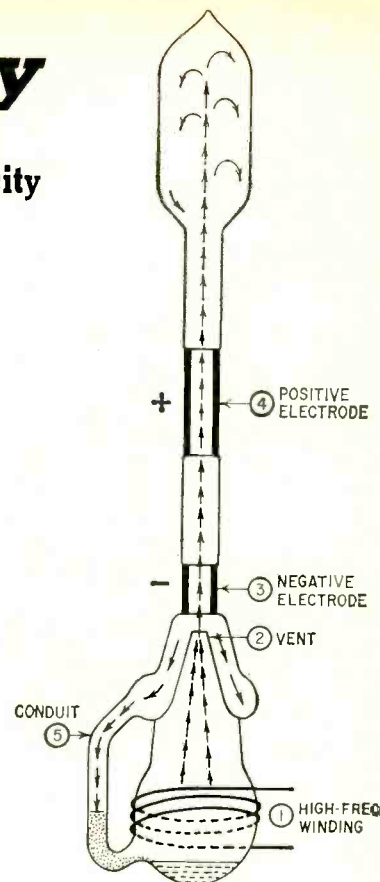A slight cooling of electrode (4) facilitates the condensation of ionized vapor and influences current strength favorably. Other things being equal, if electrode (3) is at 350°C and electrode (4) at 80° , the emf is 10 volts and the



Klein's converter.

internal resistance 15 ohms. If, on the other hand, electrode (3) is at 350° and (4) is 150°C , emf remains the same and resistance rises to 30 ohms.


Why it works?

No exact explanation of the phenomenon that causes this separation of electric charges under the conditions described can be given at present. We believe that the separation occurs because the fluid formed of molecules, ions and electrons, in traversing the equipment at a high speed and penetrating afterward into a zone of low pressure, diffuses in an unequal fashion. The more mobile electrons reach the first electrode more rapidly and the ions and droplets, because of their greater mass, travel farther and condense on the farther electrode (4).


We have repeated the same experiment using water in the place of mercury. We got 90 volts instead of 10, but the internal resistance of the source of voltage is considerably greater. It seems that there is a relation between the emf's of voltage sources of this type and their internal resistances.

We believe that such a device could convert heat to electricity, assuming that the cesium vapor or other substances could be ionized by heat, for example by contact with a surface at high temperature.

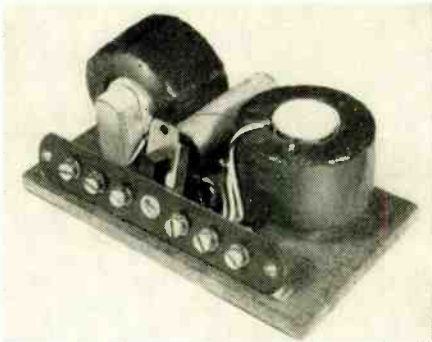To determine the yield of this kind of apparatus, we used a high-frequency source of energy that heated the mercury with eddy currents and ionized the gas and have found, up to the present, a yield up to 12%.
END



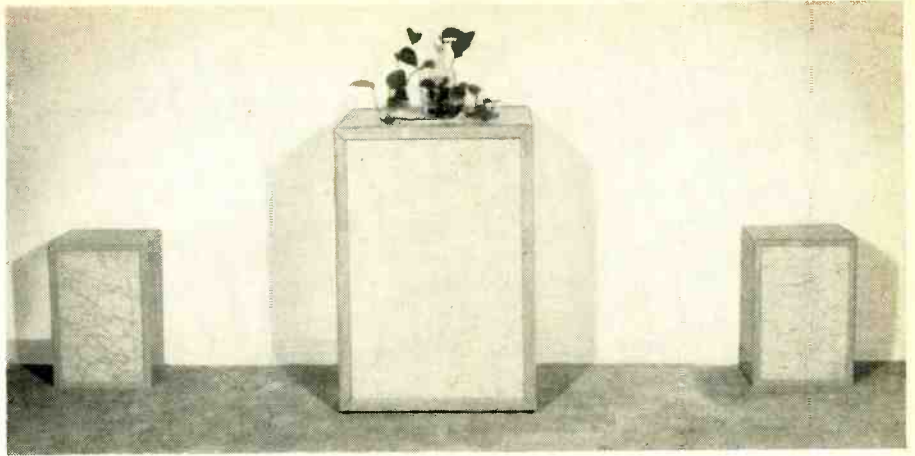Two views of the completed crossover. Note the electrolytics nestled between the coils.



Convert Your Speaker System to STEREO for \$20

Wing speakers and a simple crossover network combine with your present unit to make a satellite-type system

By **GORDON R. LICHTENWALTER**

HAVING built up what I considered a good-quality hi-fi system over the last few years, and upsetting the family budget at intervals, I was all set for fine recorded sound. Then came stereo on records! I listened here and there. No doubt about it. Stereo was very impressive, and the bug bit me bad.

My wife had been very tolerant of the "woofs" and the "tweets", the explosion of cannons and the tinkle of bells, which came after the children were in bed, the dishes done and the garbage disposal had stopped its infernal racket.

Then, once again I looked into the budget. My wife, reading my thoughts, give me one of those "Oh no you don't" looks. So the following is my inexpensive solution to stereo.

Browsing around one day I chanced to hear a stereo system using a good existing speaker system and two small wing speakers. The center speaker handled the bass end from both channels up to about 400 cycles, which, some say, is not too directional anyway, and the wing speakers took all frequencies available from the amplifiers. Just what I needed to go with the 15-inch speaker and Karlson enclosure, until I saw the price—the better part of \$200! Not for me, but why not make something similar for myself?

A glance through the catalog and a trip to the Electronic House, and I had two 8-inch speakers that could handle 10 watts each. The dealer also furnished

the plans for a small ducted-port enclosure (18 x 12 x 8½ inches) designed for the speakers.

The enclosures were sawed out and assembled in a few evenings, then checked out with a Hewlett-Packard audio oscillator, which my employer owns. The enclosure and speakers performed well, and played very nicely on the monaural system.

Next, work was started on the crossover, which consists of two inductors about 3.2 mh each, and two 50-µf 25-volt electrolytics hooked back to back to make a 25-µf ac capacitor. These electrolytics should be checked for equal capacitance and be of the same make and age, so that their power factor will be the same.


Make the coil forms of 1-inch wood dowel, 1-1/16 inches long. Cut the 2-inch diameter ends out of ¼-inch Masonite. Drill a hole through the center of

the dowel, and the Masonite ends. Assemble into a spool, using a 3/16-inch bolt and nut with large washers on each end. The bolt is removed later so, if you have no previous experience in coil winding, glue the Masonite ends to the dowel. Otherwise, when the bolt is removed, your coil may come apart. Of course, other forms may be used as long as they are not metal and have the same dimensions.


Wind 355 turns of No. 20 enameled wire on the forms. Do not scatter-wind them or your coils will come out larger than the 2-inch forms and may have more inductance than needed.

If the layers become uneven, wrap a strip of heavy paper around the previous layer and start a new even one. I inserted paper about every third layer. When your coils are finished, wrap them with plastic tape or apply motor varnish to keep them from coming apart. Tie the end down or bring it through a hole in the Masonite. Remove the bolt and mount your coils as shown in the diagram and photos, using only nonmetallic mounts. The coils are mounted at right angles to keep one from inducing current in the other, as in a transformer.

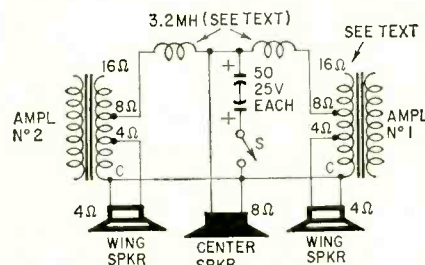The use of nonmetallic mounts keeps down eddy currents in nonmagnetic metals, and reduces the inductance and hysteresis distortion which would occur if magnetic materials were used. Hook up the coils and capacitors as shown. If you install a switch in series



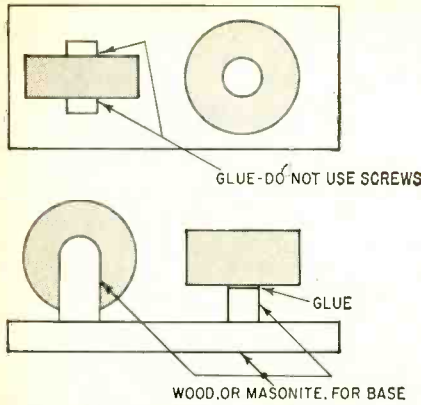Circuit of the completed crossover. Unit is connected to speakers and ready to use.



Coils are mounted at right angles to each other.

with the electrolytics, you can change the crossover frequency and db-per-octave slope. This will result in filling in the center channel more with the switch open, or less with the switch closed. Either way, the center speaker will handle the bass for either channel or the sum of both.


Phasing is a must in this system. Check all three speakers with a 1½-volt flashlight battery. Touch the speaker leads to the battery. If the speaker moves forward, mark the positive lead. If the speaker moves backward, reverse the leads and then mark the positive lead. These are your polarities. This movement can be seen through most grill-cloths with the aid of a flashlight.

Hook up the crossover as shown, and don't worry if the amplifiers are not matched. The unit has been tried with several combinations (thanks to interested friends and their stereo systems) and functions well with all types.

I use one 20-watt and one 10-watt amplifier. If you use amplifiers that are not alike, use a four-wire input system and reverse the wires on one half of the cartridge for correct phase. This is evidenced by full bass or lack of bass.

Properly hooked up and phased, the three speakers give wonderful non-directional sound on monaural, and all the stereo effect you can ask for without a hole in the middle when playing stereo.

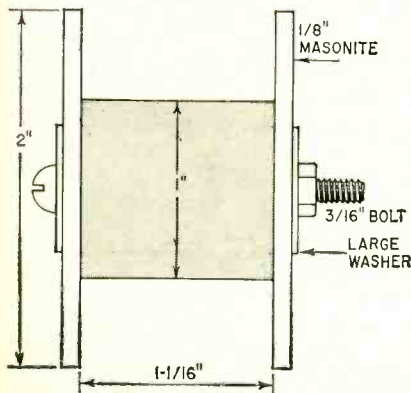This crossover was designed for an 8-ohm center speaker, but, if you now have a 16-ohm unit, you can get good results with the crossover as is, or add 80-100 turns to each coil. **END**



Details of coil construction.

TV Service CLINIC

conducted by

JACK DARR, SERVICE EDITOR

Signal Generators in TV Alignment

WE use several kinds of signal generators in TV work—rf, FM sweep, marker and so on—but in one aspect they are all alike. *For best results, we must match the impedance of the generator output to that of the load to which it is connected.*

Any kind of signal generator is a source of power. Its output is usually taken off through a coaxial cable whose characteristic impedance should match the output impedance of the generator. The cable impedance is determined by its physical characteristics: the dimensions and spacing of its conductors. The generator's output impedance is determined by the characteristics of the transformer or coupling device used.

Now, what about the *other* end of the cable? What happens there? If we simply connect a short piece of coax to a generator, we will inevitably find that it's a stub at some frequency! The generator is pumping rf power into the cable. Under certain conditions, some of this power will bounce back toward the generator, causing standing waves on the coax. If the coax were infinitely long, all of the power would be absorbed in it. If it has a finite length, there are always some conditions where we have incomplete absorption, reflection and the formation of standing waves.

In the infinite-line case, all of the power is dissipated in the line. It is shunted by the inherent capacitance and attenuated by the line inductance and resistance. With shorter lines, we can get the same desirable result by providing what we might call an artificial termination to do the same thing—absorb all the power that reaches the end of the line. To do this, we can connect a noninductive resistor across the end of the line. If it has the same resistance value as the characteristic impedance of the coaxial cable, it will absorb the power, thus preventing any of it from being reflected up the line to cause standing waves.

"But," says somebody in the back row, "if you absorb all the power, there won't be any left to put into the TV set! What do you do then?" A very good question. I was afraid you were going to ask that! Actually, I've been saying that all the power was absorbed

in the terminating resistance. This, of course, isn't quite true. If you remember your textbooks, the power relationship between a generator and a matched load looks something like Fig. 1-a. Exactly half of the power developed by the generator is delivered to the load. Why? Because this power is the product of the current flowing in the circuit and the impedance (I^2R). If the impedances

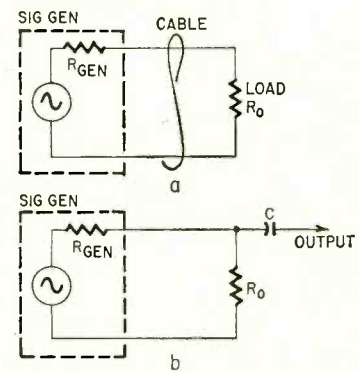


Fig. 1-a—Power developed by generator is divided equally between internal impedance of generator and impedance of load R_0 . b—Power still equally divided between impedance of generator and resistance of load. Voltage drop across load resistor is taken off through capacitor C and used for alignment work, etc.

are matched, to prevent reflections and phase shifts, the two impedances must be exactly equal. Right? Therefore, if the same current is flowing through two equal resistors, half the power is developed across each one.

Same voice from the back: "Well, you've still used up all the power. What am I going to use for alignment on my TV?" Patience, friend, we'll get there. Now, let's see, I've used up all the power that was developed, but what you're forgetting is what happens when we pass current through an impedance (or resistance).

We get a voltage drop! If our impedances are matched, we get maximum current flow; therefore we also get maximum voltage drop. This is what we use to align our TV sets, the signal voltage (Fig. 1-b)! Power in these circuits is just a handy thing to do arith-

metic with. The actual power output of the average generator is about seventh-tenths of a horsepower or thereabouts!

To terminate any signal generator output cable properly, simply look up the output impedance in the instruction book, if you can still find it. The average seems to be about 50 ohms, although some go as high as 90 and others have ready-made 300-ohm balanced terminations for use in tuner alignment. To make a termination, simply connect a plain molded carbon resistor of the right value across the end of the cable, as shown in Fig. 2, connect a small capacitor to the hot lead (the center conductor), and you're ready to go to work.

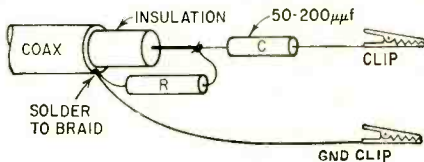


Fig. 2—Physical construction of terminating resistor and coupling capacitor.

Fig. 3 shows one of the ill effects you can run into when the cable is improperly terminated—false indications of regeneration in the video if strip or tuner. Even though the signal generator is very loosely coupled to the input (by clipping the output lead to a floating tube shield on the mixer tube), you can

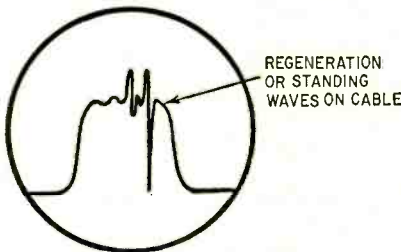


Fig. 3—How regeneration shows up in response curve during alignment.

still have trouble if the generator has standing waves on that cable!

Incidentally, if you want to check your generator's output cable to see if there is already a terminating resistor in it, disconnect it from the generator and simply take a reading across the cable conductors with an ohmmeter. If you get a 50-ohm reading, for instance, there must be a terminating resistor already in place. A completely open reading shows that there is no termination.

Herringbone on color set

In servicing an RCA 21CT660U color receiver, I found a herringbone pattern, discernible when color is tuned in. It seems to be tunable. It is particularly noticeable when a picture of little detail or a full screen of one color is present. Also, there are two vertical lines on the left side of the screen when color is being received.—J. I. H., Rededa, Calif.

This herringbone pattern on color can be caused by several things. The easiest to repair would be a misadjust-

ment of the fine tuning itself. This would push the oscillator slightly off center on your color channel, making the color burst ride too far down the slope. Center the fine-tuning adjustment, then reset the tuner oscillator on that channel while color is being received.

Another possibility is that the 13th harmonic of the 3.58-mc oscillator is beating with the 45.75-mc picture carrier. This harmonic, which is about 46.5 mc, is coupled into the picture if circuits by the shielded cable which runs from C175, at the plate of the vertical output tube, to R29, on the terminal board nearest the CRT. The shield of this cable is grounded to the chassis near the 3.58-mc oscillator socket. Cut this ground loose and ground it at the other end, near the terminal strip. The new ground is apparently not critical. The trouble is caused by ground-return currents between the shielding and the chassis.

This type of interference, as I know, can be caused by a strong channel 8 signal. The 4th harmonic of the picture carrier will be picked up by the 300-ohm ribbon going to the vhf/uhf switch. Try installing a 22- μ f capacitor between terminals B and C on the 4th video if transformer. This usually reduces this interference to the point where it isn't noticeable.

Vertical shrinkage

A short time after this G-E 21C1550 is turned on, it loses height from the bottom. It comes up to about 2 inches after about 15 minutes. How do I tackle this one?—A. D., Quezon City, R. I.

This set uses a 6BL7 for both oscillator and output. The most likely possibility is a weak tube. However, this stage is fed from the boost so check the boost voltage for dropping after 15 minutes.

Another possibility: there is a thyrite resistor in the B-plus supply, 1 megohm cold and 600,000 ohms hot. Check it for excessive change in value.

Drive line?

A G-E 21C40 developed horizontal sweep trouble and I replaced the flyback transformer. Since then, there has been a slight wrinkle in the horizontal sweep which appears as a bright line near the middle of the screen. Changing the horizontal linearity control no longer affects picture linearity to any appreciable extent.

I've replaced tubes, linearity coil and the screen resistor of the output tube with no effect. The bias voltage on the horizontal output grid is -45.—W. N. T., New York, N. Y.

It is definitely possible that the wrong flyback was used. This series is pretty critical about its flybacks and I do not know of any one outside of G-E who makes an exact duplicate. The correct part number for this chassis is an RTO-166-5. Check the flyback to see that the correct one was used.

Aside from this, the major clue would be in the action of that linearity con-

trol. All linearity controls introduce a "cancelling" or opposing voltage which lowers the power dissipated in the horizontal sweep circuit and increases the efficiency; in other words, the linearity control *must* "tune" to the flyback frequency to have the proper effect. If this isn't done, you will get a wrinkle in the raster.

From your reading of -45 volts on the grid of the horizontal output tube, it might seem that the trouble is caused by an overdrive condition; the value given in the service data for this chassis is -33. Overdriving the horizontal output tube will give you a drive line.

This chassis does not include any kind of horizontal drive control. So, if you have checked all the possible causes of overdrive (plate resistors in the horizontal oscillator, excessive B-plus to the horizontal oscillator, etc.), I suggest you try adding a drive-control trimmer capacitor to the circuit (Fig. 4). This is comparatively simple, as it can be a screwdriver-adjustable unit of about 3 to 15 μ f. It can be mounted

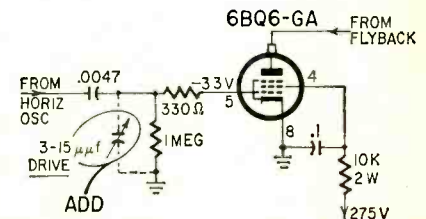


Fig. 4—Adding a horizontal-drive control to a G-E 21C40.

on the back apron of the chassis. With this, pull your drive down and see what effect this has on the line. I would recommend checking the horizontal output tube plate current both before and during these adjustments. Also, see what effect the horizontal linearity control has on plate current; it should show a dip, even though it may be a slight one. You might, as a last resort, try using a different linearity control; the correct replacement has an inductance range from 4 to 28 millihenries.

Jitter

I have an intermittent vertical jitter in a Crosley 426. It occurs about every 30 seconds, after the set has warmed up for 5 minutes. This seems to be due to only one field of the scan jittering! When I put a scope on the yoke, I can see one pulse stationary while the other jitters!

I've changed everything in the circuit including both electrolytics and the transformer and yoke. Now I've run out of possibilities!—C. F. W., Mason City, Iowa.


I notice a factory modification on this series calling for a larger electrolytic in the cathode circuit: from 30 μ f to 100 μ f. You can try this quickly by simply bridging 70 μ f across the present capacitor. However, I don't think that this is a cure.

(Continued on page 66)

50-WATT STEREO AMPLIFIER AND CONTROL CENTER

Get the most from your stereo system with this superb unit; power-packed 50 watts (25 w. per channel); complete tone, balance and stereo /mono function controls; five dual-stereo inputs plus separate monophonic mag. phono; mixed-channel center speaker output; luggage-tan vinyl clad steel cover. 31 lbs.

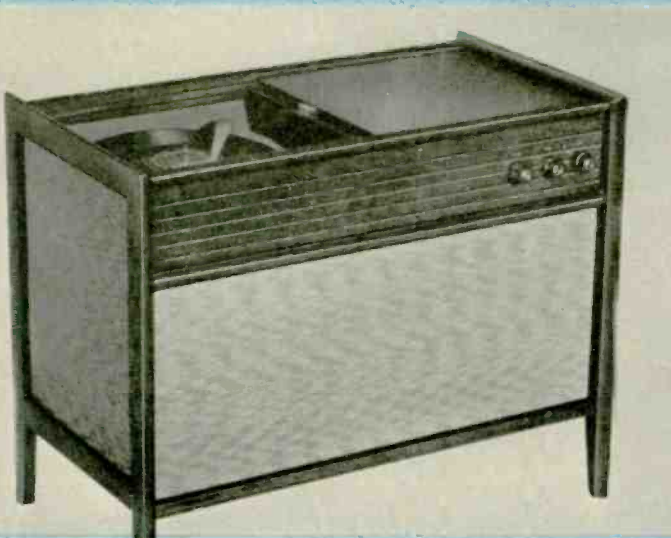Kit Model AA-100 **\$84.95**
 Assembled Model AAW-100 **144.95**



GET BIG STEREO SOUND AT LOWEST COST WITH THIS COMPLETE STEREO-PHONO CONSOLE . . . NOW IN ASSEMBLED OR KIT FORM FROM \$129.95 UP

Modest only in size and price, this new Heathkit Stereo-Phono Console amazes every listener with its room-filling, true-to-life stereo sounds. Proportioned to fit any room, it's less than three feet long and only end-table height, yet it houses a complete stereo-phono system with features usually found only in much larger consoles. There's six speakers . . . two 12" woofers for smooth "lows," two 8" speakers and two 5" cone-type tweeters for "mid-range" and "highs". The 4-speed automatic stereo /mono record changer is equipped with an "anti-skate" device and a turn-over diamond and sapphire styli cartridge. On the front panel are separate, dual bass and treble controls plus a concentric volume control. The handsome cabinet with solid genuine walnut frame, walnut veneer front panel, and matching "wood-grained" sliding top measures just 31 3/4" L x 17 3/8" D x 26 3/4" H. Whether you buy the ready-to-play or kit form, the cabinet is factory assembled and finished. 70 lbs.

Kit Model GD-31 **\$129.95**
 Assembled Model GDW-31 **149.95**

COMPLETE 28-WATT AND 50-WATT STEREO CONSOLES

Enjoy incomparable Heathkit stereo with factory wired components in beautiful preassembled, prefinished cabinets . . . ready to use! The consoles are available in both 28 and 50 watt models, with money-saving optional kit plans. The 28-watt model (HFS-26) contains the Heathkit AJ-10 stereo AM/FM tuner, SA-2 stereo amplifier, AD-50A stereo record changer and two US-3 12" coaxial hi-fi speakers. The 50-watt model (HFS-28) contains the Heathkit AJ-30 deluxe stereo AM/FM tuner; AA-100 deluxe stereo amplifier; AD-60B deluxe stereo record changer; and two Jensen H-223F coaxial 2-way 12" hi-fi speakers. Specify walnut or mahogany.

Assembled Model HFS-26 . . . 215 lbs. **\$475.00**
 Kit Model HFS-27 . . . 215 lbs. **370.00**
 Assembled Model HFS-28 . . . 264 lbs. **675.00**
 Kit Model HFS-29 . . . 264 lbs. **550.00**

(Cabinets available separately, write for information)





STEREO/MONO PORTABLE PHONOGRAPH

Now you can thrill to magnificent stereo wherever you are, wherever you go! The smartly-styled cabinet with two-tone aqua and white durable vinyl covering comes completely preassembled. In closed carrying position the speaker wing and main cabinet blend into a single handsome unit in dazzling aqua and white vinyl. In use, the detachable speaker-wing top may be spaced at any distance for maximum stereo effect. The completely preassembled automatic changer plays your favorite stereo and mono records at speeds of 16, 33 $\frac{1}{3}$, 45 and 78 rpm, while controls on the amplifier section give you complete command of volume, stereo-balance and tonal quality. 28 lbs.

Kit Model GD-10.....\$69.95

look forward to the happy months ahead
of outdoor living with Heath equipment



PORTABLE 4-TRACK STEREO TAPE RECORDER

Plays and records 4-track stereo tape for endless hours of delight! Can even be used as a hi-fi center to amplify and control tuners, record players, etc. Has "record," "play," "fast-forward" and "rewind"; 2 speeds (3 $\frac{3}{4}$ and 7 $\frac{1}{2}$ IPS); tone balance and level controls; monitoring switch for each channel to let you hear programs as they are recorded; pause button for editing; and two "eye-tube" recording level indicators. Speaker wings are detachable. Cabinet and tape mechanism are preassembled; all amplifiers and speakers included. 49 lbs.

Kit Model AD-40.....\$179.95



NEW LOW COST STEREO RECORD CHANGER KIT

Here's fine changer features at a budget price . . . oversize 11" turntable, "anti-skate" device, jam-proof mechanism and plug-in cartridge head. 4 speeds with automatic shutoff. Assembles easily, quickly with no special tools. Complete with your choice of three different, famous-name, diamond-styli stereo cartridges. 15 lbs.

Model AD-80C,
Sonotone 8TA4-SD cartridge.....\$37.95

Model AD-80A, GE VR-227 cartridge. 41.95

Model AD-80B, Shure M8D cartridge. 42.95



REVERBERATION SYSTEM

Add a thrilling new "cathedral" dimension to listening! Reverberation supplies the dimension of spaciousness to sound, as heard in concert halls, etc. where "echoes" enrich and reinforce the original sounds. The GD-61 adds reverberation acoustically, not by electronic mixing, thus it doesn't disrupt your present system and it may be placed anywhere for best listening effect. Can be connected to speaker terminals of hi-fi systems, radios, TV sets, etc. Control lets you add just the right amount of reverberation. The GD-61 consists of Hammond type IV reverberation unit, amplifier with power supply and 8" speaker. Pre-assembled birch cabinets in mahogany or walnut finishes. Measures 11 $\frac{1}{2}$ " H x 23" W x 11 $\frac{3}{4}$ " D. 30 lbs.

Kit Model GD-61M (mahogany) or
GD-61W (walnut) each.....\$69.95

NOW ONLY
HEATH
BRINGS YOU
ALL 3!

1. HEATHKIT
for
do-it-yourself
hobbyists.

2. HEATHKIT
factory-built,
ready to use.

3. HEATHKIT
learn-by-doing
Science Series
for youngsters.

HEATH COMPANY / Benton Harbor, Michigan

TWO AND SIX METER TRANSCEIVERS

The "ham on the go" will find the new Heathkit "Shawnee" 6-meter and "Pawnee" 2-meter transceiver kits irresistible! Both of the handsome units offer complete AM and CW facilities with: single knob tuning . . . tracked VFO and exciter stages; 10 watt output; built-in low pass filter; three-way power supply built-in for 117 VAC, 6 VDC or 12 VDC with separate DC and AC plugs and cables included; dual-purpose modulator . . . 10 watts for high level plate modulation or 15 watts for PA operation; double conversion receiver . . . crystal controlled first oscillator; tuning meter . . . auto-switched for received signal strength or relative power output; VFO or crystals . . . front panel switch of VFO or four crystals for novice, CAP, MARS or net operation; "spotting" switch; complete shielding of power supply, final and receiver front end; ceramic microphone . . . push-to-talk with coiled cord. And many more outstanding features . . . write for information. 34 lbs.

Kit Models HW-10 (6 meter) and HW-20 (2 meter) each **\$199.95**



look forward to the happy months ahead of outdoor living with Heath equipment



6-TRANSISTOR PORTABLE RADIOS

These award-winning, smartly-styled portables are ready to go anywhere! Both feature vernier tuning; 6-transistor circuit; 4" x 6" speaker for big set tone; prealigned transformers. 6 flashlight cells furnish power. (less batteries).

Kit Model XR-2P (plastic) . . . 6 lbs. **\$29.95**

Kit Model XR-2L (sim. leather & plastic) . . . 7 lbs. **\$34.95**



**"WALKIE-TALKIE"
CITIZEN'S BAND TRANSCEIVER**

Ideal companion for the outdoorsman . . . talk to friends up to a mile away. No license required . . . anyone can use it . . . Features 4-transistor circuit, superregenerative receiver, crystal controlled transmitter. Powered by single long-life battery. Case included. 3 lbs. (less battery)

Kit Model GW-30 each **\$32.95**

Assembled Model GWW-30 each **\$50.95**

**"WARRIOR" GROUNDED-GRID
KILOWATT LINEAR**

Attention Amateurs! Compare its feature for feature, the Warrior paces KW rigs at double this low price! Completely self-contained, the amplifier, HV, filament and bias supplies are built-in. Drives with 50 to 75 watts, no matching or swamping network required. Stable g-g circuit with up to 70% efficiency. Oil-filled capacitor and 5-50 henry swinging choke. Bands: 80 through 10. Max. power input; SSB—1,000 watts PEP; CW—1,000 watts; AM—400 watts (500 using controlled carrier mod.); RTTY—650 watts. Write for information.

Kit Model HA-10 . . . 100 lbs. **\$229.95**


TRANSISTOR DEPTH SOUNDER

For summer boating fun and safety, the MI-10 is your best buy by far in a dependable depth sounder . . . and you can buy it in kit form or factory wired and tested, ready to use. Gives reliable depth indications to 100' or more over "hard" bottoms; somewhat less over "soft" bottoms. Rotating neon light gives clear indications on hooded dial face. Six long-life flashlight batteries are used for power. Transducer may be mounted through hull, or temporarily outboard. 10 lbs. (less batteries).

Kit Model MI-10 **\$ 69.95**

Assembled Model MIW-10 **107.95**



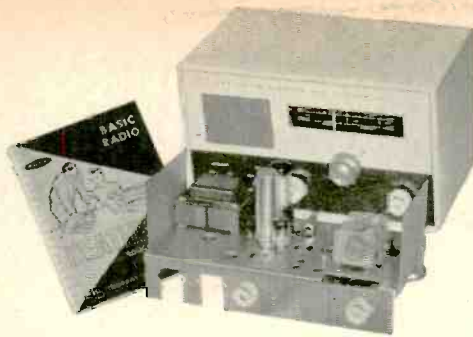

HEATHKIT BASIC RADIO COURSE

Here's a new 2-part series in basic radio for youngsters and adults. "Basic Radio—Part I" teaches radio theory in everyday language, common analogies, and no difficult mathematics. Experiments performed with radio parts supplied result in a regenerative radio receiver. "Part II" of the series advances your knowledge of radio theory and supplies additional parts to extend your Part I receiver to a 2-band superheterodyne.

- Model EK-2A . . . "Part I" . . . 8 lbs. **\$19.95**
- Model EK-2B . . . "Part II" . . . 4 lbs. **\$19.95**
Available March 24
- Model AK-8 . . . Cabinet for Part II Receiver . . . 4 lbs. **\$3.95**
Available March 24



DELUXE CITIZENS BAND TRANSCEIVER

Get the GW-10 for superior 2-way communication: superheterodyne receiver with switch selection of crystal control of any one channel or continuous vernier tuning of all 23 channels; automatic "series gate noise limiter"; adjustable squelch control; press-to-talk mike with coil cord; illuminated dial. Crystal controlled transmitter has switch selection of 3 crystals (one furnished). Hardware supplied for under dash mounting. Built-in power supply, 117 V. AC and 6 or 12 V. DC models 11 lbs.

- Kit Model GW-10 **\$62.95**
- Assembled Model GWW-10 . . . **99.95**



3-BAND RADIO DIRECTION FINDER

Now, at big savings, a deluxe completely transistorized portable RDF in your choice of kit or assembled models. The DF-3 operates on marine beacon, standard broadcast and ship-to-shore bands to offer you both portable radio entertainment and reliable direction finding facilities. Featured are: 9-transistor circuit; 6 flashlight battery power supply; preassembled prealigned tuning section; new sense antenna for non-ambiguous bearings; lighted dial and tuning meter. 13 lbs.

- Kit Model DF-3 **\$ 99.95**
- Assembled Model DFW-3 . . . **169.95**



SEND MY FREE COPY OF YOUR COMPLETE CATALOG



HEATH COMPANY / Benton Harbor 20, Michigan

ORDERING INSTRUCTIONS: Fill out the order blank. Include charges for parcel post according to weights shown. Express orders shipped delivery charges collect. All prices F.O.B. Benton Harbor, Mich. A 20% deposit is required on all C.O.D. orders. Prices subject to change without notice. Dealer and export prices slightly higher.

Please send the following items:

ITEM	MODEL NO.	PRICE

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

Order direct by mail or see your Heathkit dealer.
Ship via Parcel Post Express C.O.D. Best Way

Columbia

SUPER-FLEX

Ultra Flexible Coaxial Cable

- EXTRA FLEXIBLE CONDUCTOR
- EXTRA FLEXIBLE JACKET
- EXTRA LOW COST

NEW! Super-flexible 52 ohm and 72 ohm Coaxial Cable for Citizens' Band and Multiple Television Systems, etc. Cable jackets are high gloss super-smooth, non-contaminating FLEXLIFE Vinyl that will not become rigid in cold weather. Another First from COLUMBIA.

SUPER-FLEX RG 58A/U

Center Conductor: 19/0068 Tinned Copper. Jacket: Columbia Black Flexlife Insulation. Dielectric: Low loss Foam Polyethylene.



SUPER-FLEX RG 8/U

Center Conductor: 19/24 Soft Copper. Jacket: Columbia Black Flexlife Insulation. Dielectric: Low loss Foam Polyethylene.



SUPER-FLEX RG 59/U

Center Conductor: 7/31 Soft Copper. Jacket: Columbia Silver Grey Flexlife Insulation. Dielectric: Low loss Foam Polyethylene.



Available thru your local distributor

Columbia
WIRE & SUPPLY CO.
 2850 IRVING PARK ROAD
 CHICAGO 18, ILLINOIS

"America's Most Complete Wire Line"

(Continued from page 61)

Check the coupling capacitors and plate resistors in the sync circuits, especially around the 6AN8 and 6U8. As a good test, disconnect the vertical sync by lifting one end of the vertical integrator, free-wheeling the picture and watching for any sign of the jitter. It might also be wise to check the vertical circuit's B-plus line with a scope for traces of ripple.

There is one more possibility in some of these sets. Add a 33,000-ohm resistor in series with a 0.005 μ f ceramic capacitor (1,000 volts or so) from the back picture-tube support to the nearest chassis ground. This network bypasses any pulses which could disturb the interlace and conceivably be causing this trouble.

Markers meet in the middle!

I'm aligning an RCA TV. I get two markers on the response curve, instead of only one. They start from the center of the first hump and second hump, and move together until they meet in the middle. Then they disappear! If you keep on turning the dial of the sweep, they reappear in the middle and go back out to their original positions at the side!

Why do I get two markers when I am only feeding in one signal? After aligning at what I think is the right place, the result is no better than when I started. I get sound without picture or picture without sound, and a lot of swishing noises when I turn the fine tuning—J. B., Philadelphia.

Your trouble with the dual markers is caused by an incorrect setting of

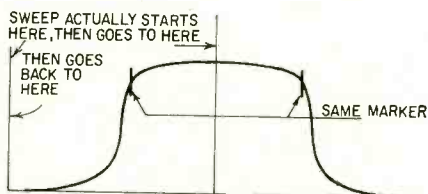


Fig. 5—Improperly adjusted sweep generator can give this pattern.

the sweep generator. Instead of getting the whole response curve, you get only half of it (Fig. 5). In other words, instead of displaying the entire response curve of the tuner, you're actually seeing only half of it. The extra marker is the mirror image of the first.

To set up a sweep generator properly, tune it to approximately the center of the band being swept. In your case this would be channel 13 (210-216 mc), so set it to about 213 mc. Now run a marker into the curve. If you get

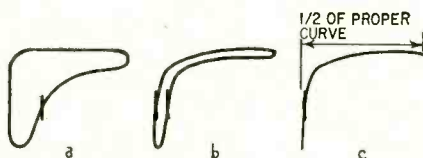


Fig. 6—*a*—possible proper scope pattern; *b*—this pattern can be changed to *c* by turning on scope's retrace blanking.

the dual-marker effect you mention, your sweep is improperly set. Try feeding the horizontal sweep from the sweep generator into the scope. Now, set your phasing control until you get a curve with only a single marker. You may wind up with something that looks like Fig. 6, but that's the right curve! You can also get rid of mirror images by adjusting the horizontal blanking (return-trace blanking) on your generator. This will (or should) take out half of the curve, and one of the markers.

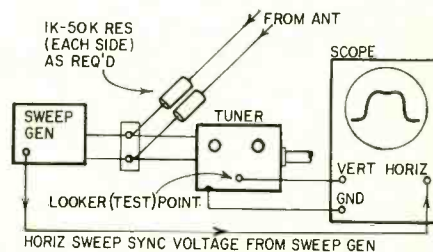


Fig. 7—How to use TV station signals as sweep generator markers.

The simplest way to adjust a curve like this is the use of strong TV station signals as markers (Fig. 7).

Picture-tube change

We want to convert an RCA KCS-47-A chassis to use a 21-inch picture tube. How about a 21AMP4 or a 21ALP4 for this? If the normal 12,000 volts is not sufficient, what changes in the existing components are needed to boost the high voltage? Are there any other changes that you would recommend—yoke, flyback, etc.—J. O. D., Williamsburg, Va.

I doubt the advisability of trying to convert this chassis to use the picture tubes you mention. This is mainly due to their high-voltage requirements—16,000 volts for each type. Several other types would be much more applicable. Look in your picture-tube book and you'll find ones which require less high voltage. My first choice would be Bob Middleton's favorite, the 21EP4. It requires only 12,000 volts and is a 70° tube.

Fada flyback replacement

We are servicing a Fada S-1060 which has an open winding on the primary of the flyback transformer. Our distributor tells us that Fada has gone out of business.

Can you give us the name of a source which might supply the required replacement part, or the necessary information to alter the high-voltage circuit to use a standard replacement part?—G. E. S., Whippany, N. J.

A Triad flyback No. D-112 will be suitable. This is listed as a direct replacement for Fada part Nos. 37.255 and 37.255B. It should be available from any parts supply house.

Antenna coupling

Can you tell me if there is a company making transformers to couple bays of TV antennas together? These are supposed to be superior to stacking bars

in terms of impedance matching.

I'm now using an Amperex ECC88/6DJ8 tube in the lower section of my Jerrold De-Snower. Is there any better tube, for low-noise, at 100 volts plate? —F. E., Port Orford, Ore.

I'm a little confused here as to your meaning. Actually, the so-called stacking bars used to couple two bays of a TV antenna together are transformers. Their principal function is to match the two impedances and to couple the antennas together. They are generally used as quarter-wave transformers to match the 600-ohm impedance of the stacked antennas to the 300-ohm impedance of the transmission line. I have never heard of anyone manufacturing transformers specifically for this purpose.

The ECC88 is probably the latest of a long series of low-noise tubes, to the best of my knowledge at the moment. It is a twin-triode of the new frame-grid construction and is being widely used in community-antenna system amplifiers, where its tremendous mutual conductance is a big help: 12,500 micromhos! It is interchangeable base-wise with the popular twin-triode types (6BQ7, etc.).

Incidentally, this tube is also made with the numbers 6922 and E88CC. This last numerical arrangement denotes a special type of construction for hard service such as in computers. But as long as the same numbers are there, it is the same tube. This is the European numbering system: the E stands for 6.3 volts filament, the C means triode (CC means twin-triode) and the 88 is the series number.

Add a dc restorer

I would like to install a dc restorer on my Hotpoint 21S505 TV, preferably a silicon or germanium diode. Will I need a retrace eliminator?—A. G. K., Oak Park, Ill.

You can use the dc restorer shown in Fig. 8. It is for a cathode-driven picture


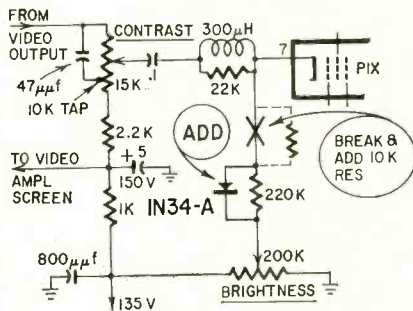


Fig. 8—Dc restorer that can be added to a Hotpoint 21S505.

tube like the one your Hotpoint uses. Several diodes would be suitable, either silicon or germanium. Be sure to check the one you have to see that it has a very high back resistance—at least 100,000 ohms. Otherwise your results won't be too good. You won't need a retrace eliminator. If you get retrace lines after the dc restorer is installed, the diode is reversed!

END

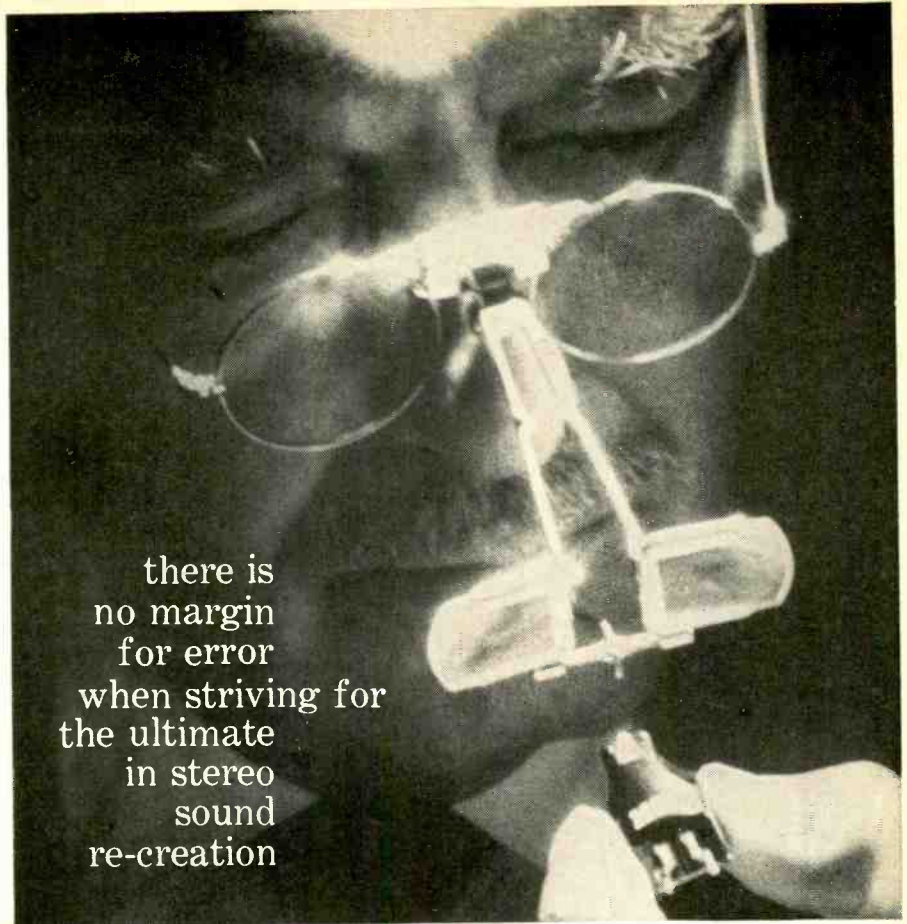

there is
no margin
for error
when striving for
the ultimate
in stereo
sound
re-creation

SHURE

Stereo Dynamic

HI-FI PHONO CARTRIDGES

Tiny though it is, the cartridge can make or break a stereo system. For this breathtakingly precise miniaturized electric generator (that's really what it is) carries the full burden of translating the miles-long undulating stereo record groove into usable

electrical impulses... without adding or subtracting a whit from what the recording engineer created. Knowing this keeps Shure quality standards inflexible. Shure Brothers, Inc., 222 Hartrey Avenue, Evanston, Illinois.

CARTRIDGES

- Standard M8D. A superb blend of quality and economy... \$16.50
- Custom M7/N22D. Widely acclaimed; moderately priced... \$36.75
- Professional M3/N21D. Overwhelming choice of the critics... \$47.25
- Laboratory Standard Model M3LS. Individually calibrated, limited quantity... \$75.00

TONE ARMS

- Studio Dynamic. Integrated arm and cartridge. Cannot scratch records... \$89.50
- Professional Independent Tone Arm. For any quality cartridge... \$29.95



CUT OUT AND MAIL TODAY



8 FREE
BIG ISSUES

OLSON
CATALOGS

TYPICAL VALUE

DIAL TELEPHONE

\$7.93

No. PH-31
Standard phone
company model.



We will send you a new issue every 6 weeks for a full year—NO CHARGE! Compare our World Famous Values.

MAIL TO: OLSON ELECTRONICS
(Formerly Olson Radio)

717 S. Forge St., Akron 8, Ohio

SEND FREE CATALOGS

Send Dial Telephone @ \$7.93, plus postage

NAME _____ ADDRESS _____

CITY _____ ZONE _____ STATE _____

ABOUT THESE SUPER- SCOPES

Special circuitry and CR tubes speed up scanning in some new industrial scopes as high as 100 megacycles.

By TOM JASKI

IN this age of moon rockets, message repeating satellites and supertelemetry from space platforms, and particularly in the industrial fields where electronics is rapidly becoming the workhorse for the control of machines too fast and complex for human control, electronic development has demanded higher performance standards from the instruments used. Particularly in oscilloscopes, where the problem of bandwidth vs sensitivity has always dominated the design scene, the new demands have forced radical approaches to deflection-amplifier design. The technology of these new amplifiers is not based on new discoveries. Primarily it is the application, for commercially produced oscilloscopes, of cir-

cuitry already familiar but used only rarely in special laboratory situations.

Two main approaches have been taken. The first is an improvement of the amplifiers themselves to the limits of tube capabilities, and the improvement of cathode-ray tubes to match the strides in amplifier progress. The second approach is to divide the incoming signal into a number of equal portions which are easily amplified and to reconstitute it from the amplified "samples". Both methods have their problems and limitations. Let us briefly examine what they are and how we can solve them.


In cathode-ray tubes, the electron beam that writes the image on the screen is deflected in its brief passage

between the deflection plates in proportion to the signal applied to these plates. For greater writing speed, we must—to obtain sufficient image brilliance—speed up the electrons so they will collide with the fluorescent particles on the back of the screen with greater intensity, thus giving a normal trace despite the faster scanning time. This is relatively easy to do. We can simply apply a higher potential to the accelerating anode.


Another method is to develop new fluorescent materials for the face. This too has been done successfully. But by "intensifying" the beam we have created a new problem. The beam is now "harder", more difficult to deflect, putting greater demands on the deflection amplifiers.

Another way to improve the deflection system is to mount in the tube a series of deflection plates so shaped and spaced that an electron traveling between them will receive from each additional plate another bit of deflecting force in the proper time sequence. This is illustrated in Fig. 1, which is, in effect, a type of traveling-wave deflection structure. Electron speed must be very closely controlled to avoid distortion in the trace.

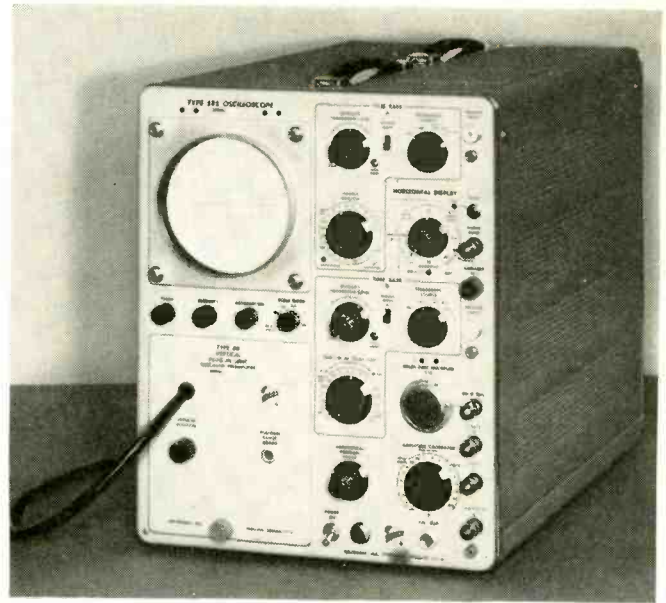After we have pulled all these tricks with the CRT, we must look elsewhere



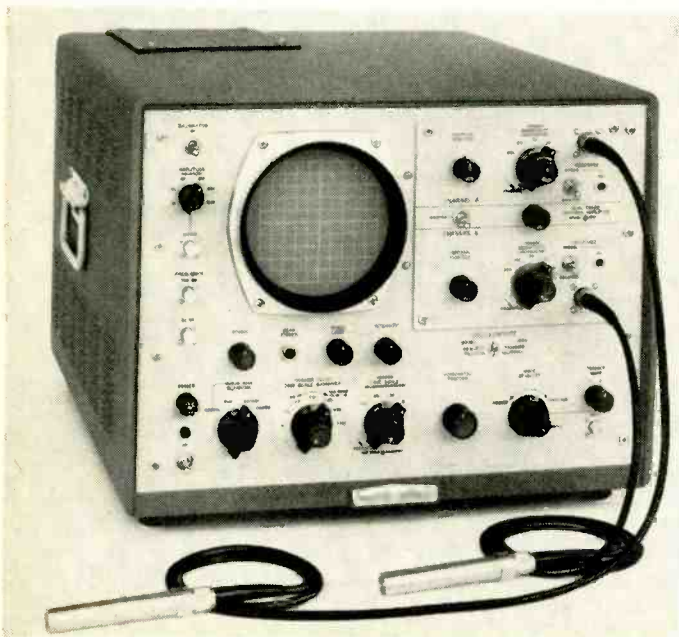Tektronix 585 oscilloscope uses distributed amplifiers for 100-mc bandwidth.



Hewlett Packard 185A oscilloscope uses sampling system to display fast pulses.


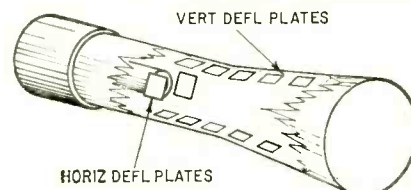


Fig. 1—Special cathode-ray tube with a series of deflection plates. (Deflection plate supports and connections are not shown.)

Fig. 2—Partial circuit of main vertical amplifier in Hewlett Packard model 160 scope illustrates the use of parallel amplifiers to get sufficient deflection with high bandpass.

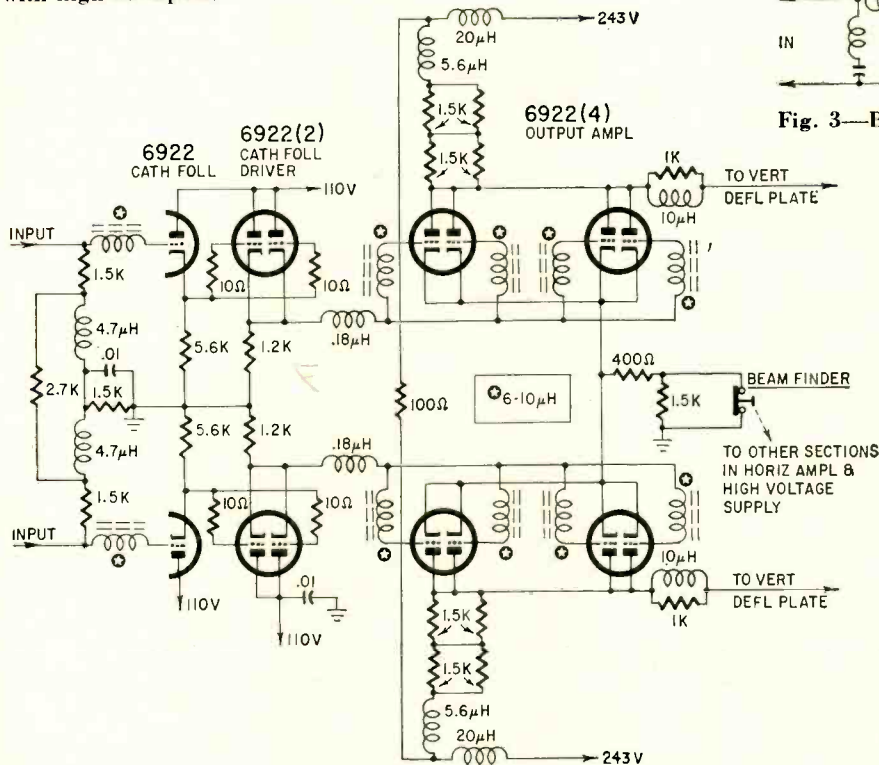

for further improvements, keeping in mind that in spite of our special structure, we still need greater deflection voltages.

Now what about the deflection amplifiers? In a conventional amplifier, the gain of a deflection stage is proportional to the transconductance of the tube. Thus, with high-transconductance tubes, we can reach a certain level of sensitivity for the final stage. But there is a limit to this simply because of the tube's structural requirements—high transconductance requires close element spacing. By increasing the plate load resistance we can get more deflection voltage for the same voltage applied to the grid, but this increases the time constant of our deflection amplifier circuits, since it is proportional to a product of circuit capacitance and resistance. And if we increase the time constant, we limit the amplifier's upper frequency response severely.

So we must keep the plate load resistor as small as practicable. To do this we can increase the size of the tube and thus the total current through the plate load. A modern approach to this is the parallel output tubes used in some high-performance scopes such as the Hewlett Packard 160 (Fig. 2). Here several tubes have a common plate load and provide adequate deflection up to about 15 mc.

Beyond this, or at least beyond about 30 mc, we have to turn to a special kind of an amplifier to reduce the time constant further. More parallel tubes

or larger tubes would now begin to increase the total capacitance, the other factor involved. Because of this capacitance, amplifiers have had to be developed in which the advantages can be tapped, without the burdens. These turned out to be *distributed amplifiers*, in which the transconductance of the tubes work together and their outputs can be added, without being particularly affected by the input and output capacitances. Successful distributed amplifiers have been built for several thousands of megacycles, but in oscilloscopes the best deflection amplifiers, within practical commercial limits, have an upper frequency limit of about 600 mc.

Fig. 3 shows a basic distributed amplifier. Here we see what look like two conventional delay lines of lumped capacitances and inductances, and that is what they are. The input signal travels down the grid delay line, and the output of each tube down the plate delay line. The lines are so designed that when a signal, amplified by the first tube, leaves its plate, it will arrive at the plate of the second tube precisely at the same time that the input signal, now also amplified by the second tube, is being reproduced on the plate of that tube. Thus the two amplified signals add. This process continues all the way down the line until a signal is obtained strong enough to deflect the beam in the cathode-ray tube.

The signal on the plates will, of course, tend to travel in both direc-

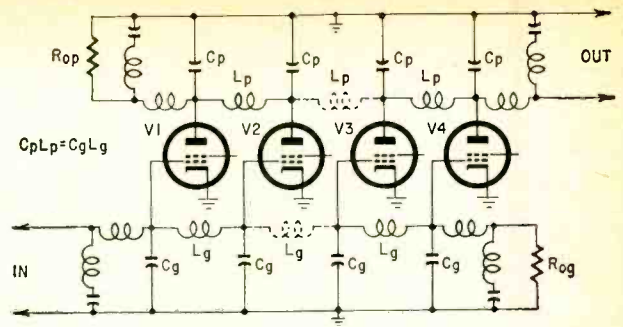


Fig. 3—Basic distributed amplifier circuit.

tions along the delay line but we are interested only in the forward-traveling one. So we absorb the backward-traveling signal (which must not reflect into the line) in terminating resistance R_{og} . Since now the principle of amplification is entirely different and we no longer depend on certain values of plate load resistances, the tube capacitances can now be used as part of the delay line capacitances and no longer contribute in the same way to the time constant of the circuit. You can see that we have neatly licked the time-constant problem.

This does not mean that we can build these amplifiers for *any* frequency, for we now have other problems, such as the upper cutoff frequency of the delay line. This is primarily determined by losses in connecting leads, capacitors, and through grid loading. Insulation also behaves differently at very high frequencies, and insulation losses increase. But the picture is more favorable with a conventional unit.


At low frequencies, when a signal would virtually not be delayed by the line (the delay is the same, but the relative significance of the delay compared to the signal frequency is insignificant), how does the distributed amplifier work? Well, here we have the situation that all these tubes are virtually in parallel, and we need only a very small load resistor to get ample deflection, as discussed previously. Thus the distributed amplifier has a very great bandwidth. We do encounter some problems at low frequencies, but none as serious as time delay or losses.

Distributed amplifiers, of course, also have disadvantages, the most serious of which is noise. With so many tubes, thermal noise becomes a real problem. Another obvious disadvantage is cost. We need more tubes and larger heater and power supplies which must be carefully regulated for stability.

Fig. 4 is a practical version of a distributed amplifier for deflection. It is used in the Tektronix type 585 100-mc scope. The series of deflection plates is also shown. Notice that this main deflection amplifier uses 10 triode sections and a dual pentode. The delay line driver is built along the same principles, and uses another 14 triodes. Sensitivity is 0.25 volt per inch, band-pass dc to 100 mc and rise time .0035 μ sec. Additional amplification can be obtained wherever bandwidth can be sacrificed for greater sensitivity. Notice

(Continued on page 72)

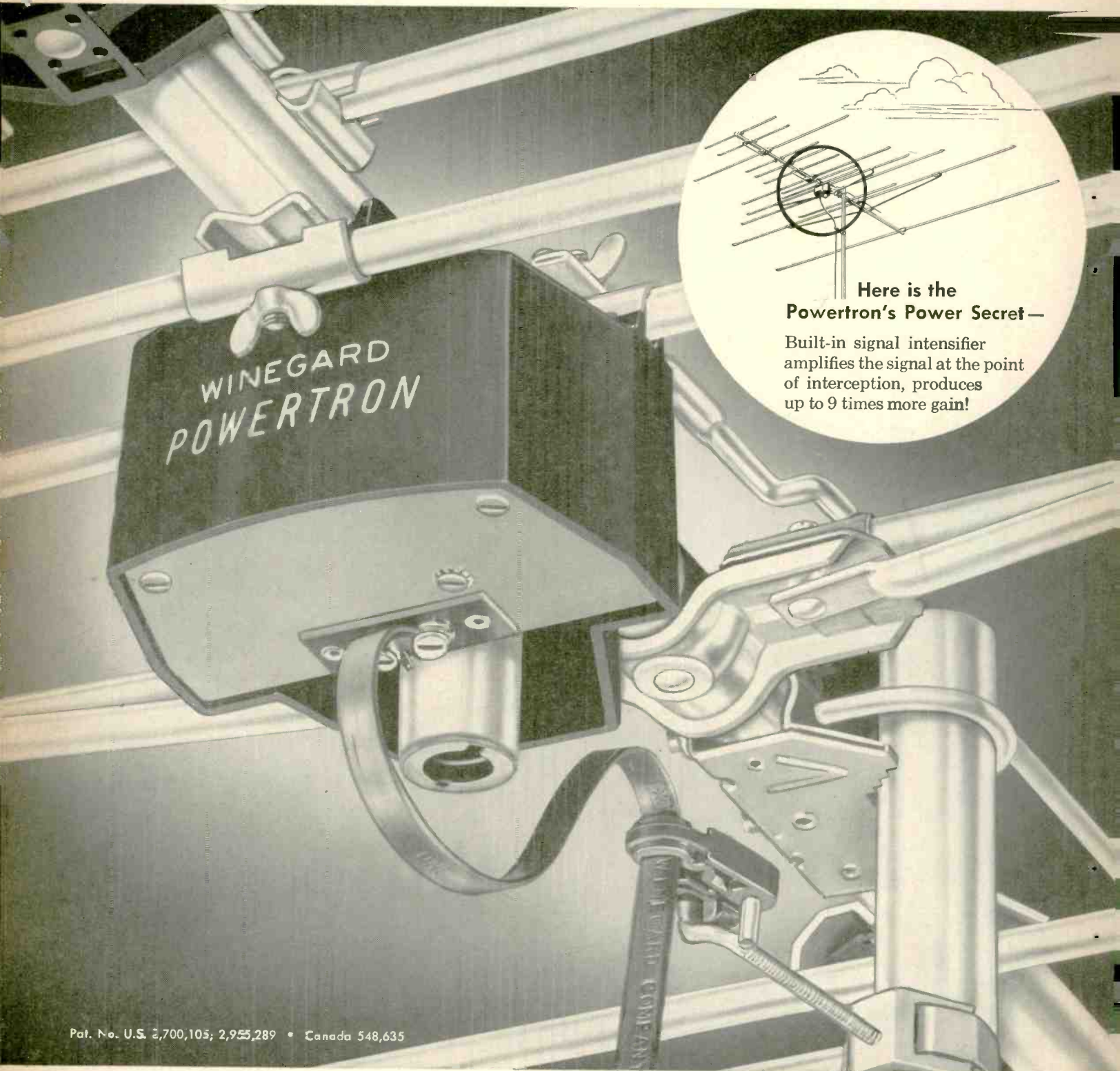World's first Electronic TV Antenna . . .



Here is the
Powertron's Power Secret —

Built-in signal intensifier
amplifies the signal at the point
of interception, produces
up to 9 times more gain!

Pat. No. U.S. 2,700,105; 2,955,289 • Canada 548,635

NOW AN ANTENNA WITH 5-9 TIMES MORE GAIN THAN ANY TV ANTENNA EVER MADE!

Here's the antenna that will obsolete tens of thousands of old-style antennas, will give new life to old TV sets, will build new profits for TV Service Technicians.

WINEGARD POWERTRON

POWERTRON AMPLIFIES TV SIGNALS AT THE POINT OF INTERCEPTION

Now Winegard engineers have designed a new high gain, all-channel yagi antenna incorporating a low noise, high gain RF amplifier in one integral unit! Because the input circuit of this amplifier *exactly matches* the characteristics of the new "Tapered T" driven elements to which it is *directly coupled*, every last particle of signal is amplified. The results are amazing.

We call this new electronic antenna the POWERTRON. The Powertron amplifier uses the frame grid 6DJ8 dual triode (12,500 MHOS) transconductance, in a radical new RF circuit, that allows this one tube to amplify all signals in the VHF TV band, 54 to 216 MC, with a gain of 5 times (14 DB). This gain is added to the gain of the antenna which is a high gain yagi design, quite superior to other all channel antennas.



The Powertron power supply lowers 117 VAC to a safe 24 volts which is fed up the lead-in to the Powertron antenna. Completely fused, the power supply is made shock-proof by an AC isolation transformer.

Imagine what this super-powerful electronic antenna can do! Weak signals become strong and clear—dim pictures bright and contrasty. Old-style tuners pull in snow-free pictures better than 1961 models on ordinary antennas.

You can do many things with this new antenna that are impossible with any other. You can drive up to 6 TV sets in deep fringe, 10 TV sets in normal areas without an additional amplifier. You can put TV outlets in every room of the house and all sets will have better pictures than any single set with a regular antenna.

Because of its extreme sensitivity, Powertron can be installed lower than other antennas. For instance, where 40-ft. masts are normally used, a Powertron can usually be installed at 25 ft., yet give better results!

Where desirable, the Powertron can be remotod up to 1/4 of a mile and still deliver a perfect signal.

In large distribution systems (motels, apartments, etc.), Powertron makes the perfect antenna to use in conjunction with Winegard's 4-tube A-400 or 7-tube A-700 distribution amplifiers.

For critical color, Powertron's extremely linear frequency response makes it the ideal antenna for your "color" installations.



P-44



P-44X



SP-44X

To sum it up, Powertron makes weak TV pictures good, and good TV pictures even better. It *works equally well* for color or black and white reception. It is the world's first all channel (VHF) *electronic* TV antenna, and is a tremendous step forward in the search for improved TV reception.

3 Gold Anodized Powertron Models —

Powertron Model P-44, 14 elements \$74.95 list.

Powertron with Power Pack Model P-44X, 21 elements, \$91.90 list.

Super Powertron Model SP-44X, 30 elements, \$104.95 list.

NEW TELETRONS, TOO! NON-ELECTRONIC, BUT 26% TO 484% MORE POWER INCREASE THAN COLOR'CEPTOR

Similar to the Powertron, but without the RF amplifier, Teletron embodies the same new WINEGARD "TAPERED T" DRIVEN ELEMENTS for proven performance superior to any other non-electronic TV antenna. Teletron is gold anodized, has the same fine quality construction and mechanical features as the Powertron.

3 Gold Anodized Teletron Models —

Teletron Model T4, 14 elements, \$34.95 list.

Teletron Model T-4X, 21 elements, \$51.90 list.

Super Teletron Model ST-4X, 30 elements, \$64.95 list.


COMPARISON OF POWERTRON AND TELETRON MODELS TO WINEGARD COLOR'CEPTOR

Chart shows Gain and Power Increase over Color'Ceptor (CL-4) Antenna

Model	DB Gain Over CL-4	Power Increase Over CL-4	Voltage Gain Over CL-4
P-44 Powertron	14 DB	25.1 Times (2500%)	5.01 Times
P-44X Powertron with Pack	15.8 DB	38.4 Times (3800%)	6.20 Times
SP-44X Super Powertron	19.1 DB	81 Times (8100%)	9.0 Times
T-4 Teletron	1.0 DB	1.26 Times (26%)	1.12 Times
T-4X Teletron with Pack	2.8 DB	1.9 Times (90%)	1.38 Times
ST-4X Super Teletron	6.1 DB	4.84 Times (484%)	2.2 Times

GET IN ON THE POWERTRON — TELETRON PROFIT BANDWAGON!

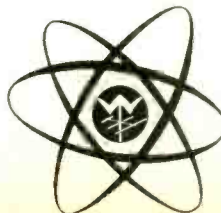Be first in your area to offer the superb Powertron performance to your customers. Take advantage of many new sales aids now available through your Winegard distributor . . . and watch for sales-making consumer ads in **LIFE**



Winegard

Winegard Co., 3013-3 Scotten, Burlington, Iowa

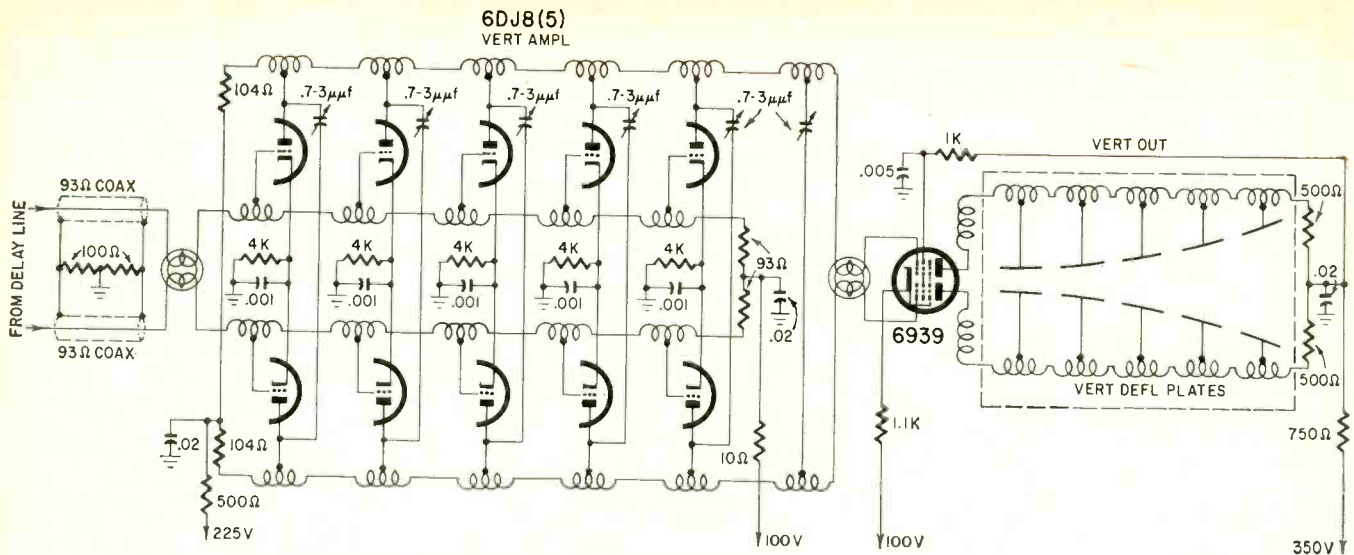


Fig. 4—Distributed amplifier used in the Tektronix type 585 scope.

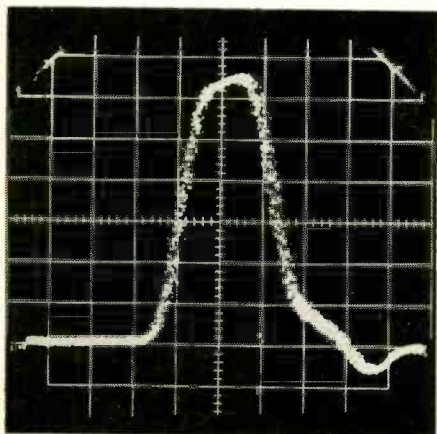


Fig. 5—Scope pattern of 2- μ sec pulse displayed by using sampling technique.

as low as one-fiftieth of the input signal frequency. If the bandwidth required for the input signal were 500 mc, then the bandwidth demanded of the amplifier would be only 10 mc, a much more reasonable figure.

After amplification, the signal samples are put together again to display a true image of the input pulse signal. Fig. 5 shows such a trace of a 2- μ sec pulse which is displayed with a sweep speed of 1 μ sec per cm, and with a vertical sensitivity of 5 mv per cm.

Fig. 6 shows how this is done. The signal, which must be of a repetitive type, is applied to a sampling gate which samples the signal periodically, the rate being determined by the setting of the time scale. Since the sampling must be synchronized with the signal to obtain a stationary image, the signal is delayed in the amplifier, allowing the triggering of the sweep system by the signal. Since the signal is so much shorter than the total time it takes to sample a number of times, each sample taken successively in time will be of a different portion of the input signal. If we were to sweep continuously, the signal displayed would be a series of small dots (if they were visible) for, in between samples, the

input would be zero (closed gate). Thus the scope employs a special sweep circuit which advances the spot horizontally only a small distance on the screen per sample. When a trigger is received, the avalanche blocking oscillator (so called because it uses avalanche transistors) starts a ramp (rising) voltage which increases precisely in time, depending on the time-scale setting.

The ramp voltage is fed to the voltage comparator where it is compared with one from the staircase generator. If this voltage equals the one fed back from the staircase generator the sampling gate is opened and the staircase generator is advanced one step. By sweeping the spot horizontally across the tube face this way, all the "dead" spots are eliminated from the trace, and it appears to the viewer as a continuous line. The resolution of the picture is determined by the size of the steps of the staircase generator. The larger these steps, the greater the distance between the spots that make up the trace. The trace can be magnified by reducing the feedback voltage to the comparator. This lets the comparator fire sooner, reducing the time between spots and the distance per spot.

Obviously, only repetitive signals can be viewed this way. The signal must last long enough in approximately the same form for the number of scanning operations required to reconstitute the signal.

These then, are the two principal methods used for very-high-frequency oscilloscopes. Other methods have been used, such as the Japanese oscilloscope capable of displaying sine waves of 30,000 mc. But in this case the special cathode-ray tube had to be viewed with a microscope, since no practical deflection amplification was possible at the time. Before long, someone will join the two methods and put the advantages of both in one instrument.

● Since this article was written, Tektronix has come out with a distributed type oscilloscope, similar to the 100-mc unit described here, which has a bandwidth from dc to 1,000 mc. Principles of operation are the same as those for the 100-mc scope. END

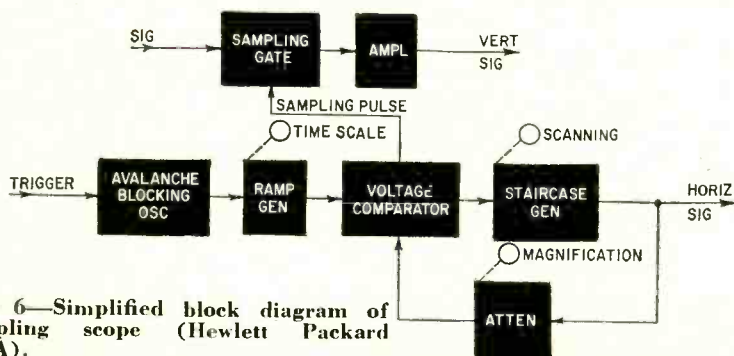


Fig. 6—Simplified block diagram of sampling scope (Hewlett Packard 185A).

2-Terminal Oscillator

By I. QUEEN

THIS negative-resistance oscillator covers a wide frequency band and can generate a pure sine wave. It functions without a transformer, center-tapped coil or even a capacitor. It uses a pair of transistors, which may be low-gain types. The circuit is a modification of patent No. 2,943,282, issued recently to Harold J. Pfiffner of Venice, Calif.

The diagram shows a practical version of the oscillator. Its tank coil is simply a high-impedance (about 1,500 ohms resistance) earpiece shunted by .002 μ f. Output is a pure sine wave.

Actually a wide variety of two-terminal inductors can serve as tank (instead of the earpiece). I have tried choke coils, transformer windings, large rf chokes and ferrite antennas. The smaller the inductor the higher the output frequency and, in general, the smaller the capacitor required across it. An antenna loopstick shunted by a 365 μ f capacitor at C will generate frequencies up to about 1 mc. By removing turns you can go higher.


To adjust the circuit, begin with R at minimum. Increase it until oscillations occur (observe a scope or voltmeter, or listen in on a nearby receiver). The waveform is purer (lowest distortion) when R is as large as possible before oscillations die out. With the earpiece, the output is about 0.3 volt at about 1,500 cycles.

Among other tanks tried was a small surplus transformer currently found in many radio stores. It has three center-tapped windings specified as 22,000, 5,200 and 600 ohms. The following results were noted:

Winding	Voltage	Frequency
high	0.6	350
medium	0.3	2,000
low	0.05	3,500

In each case, the full winding was used and the other two were left open. The capacitor value for C was .022 μ f.

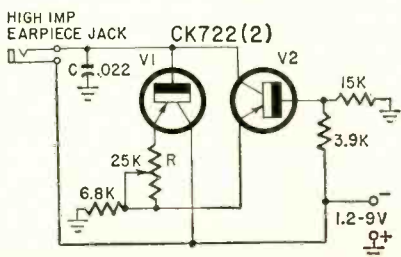
In the audio range, low-cost low-gain transistors are suitable. In fact, some that tested poorly in other equipment gave good results here. For if and higher-frequency bands, use high-frequency types like 2N484. END



NOW! Advanced concept...integrated design...

The EMCEE VHF TRANSLATOR

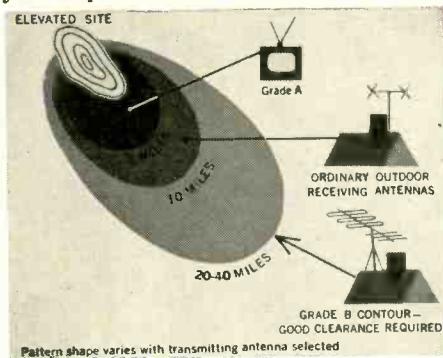for simplest installation and maximum performance! FCC TYPE ACCEPTED!



Here's the new VHF Translator with outstanding advantages for all installations. EMCEE Translators are the result of long experience in quality design and trouble-free construction by some of America's leading experts. Now fill in troublesome areas with the advanced EMCEE VHF Translator.

ELECTRONICS,
MISSILES AND
COMMUNICATIONS, INC.

264 E. Third Street • Mount Vernon, New York
GET FULL FACTS ON ADVANCED DESIGN AND LOW COST TODAY!

ELECTRONICS, MISSILES & COMMUNICATIONS, INC.
264 E. Third Street • Mount Vernon, New York
Gentlemen:

—Please rush free planning package including data sheet, complete installation check list, coverage calculation form.

—Please send free reprint of FCC rules covering translators.

NAME _____
ADDRESS _____
CITY _____ STATE _____



STEREO SYSTEM FOR A MILLION-AIRE: 4 SELECTIONS

Gentlemen's Quarterly magazine asked James Lyons, editor of *The American Record Guide* (the oldest record review magazine in the United States), to poll hi-fi authorities on which audio components they would choose for the best possible stereo system, without any regard for price.

Three writers in the audio field and one audio consultant made up independent lists. The ideal systems they projected in the April, 1960 issue of *Gentlemen's Quarterly* are suitable for discriminating millionaires—one of the systems, using a professional tape machine, would cost about \$4000.

ACOUSTIC RESEARCH AR-3 loudspeakers are included in three of the lists,* and these are moderate in price. (There are many speaker systems that currently sell for more than three times the AR-3's \$216.) AR speakers were chosen entirely on account of their musically natural quality.

Literature on Acoustic Research speaker systems is available for the asking.

*In two cases alternates are also listed. For the complete component lists see the April, 1960 *Gentlemen's Quarterly*, or write us.

ACOUSTIC RESEARCH, INC. 24 Thorndike Street Cambridge 41, Massachusetts


WOBBULATING SWEEP GENERATOR

By GERALD WILNER

Accurate narrow-band sweep generator for checking crystal filters, aligning if strips, aligning AM receivers, etc.

WHEN designing and building crystal filters for single-side-band activities, I found it almost impossible to take response curves with the standard variety of signal generators. A good part of the difficulty was caused by the small bandwidths of the crystal filters, coupled with the fact that they provide extremely sharp skirts on either side of the passband. Unless an ultra-stable signal generator with a vernier dial is available, it becomes almost impossible to set the generator so the resulting output can be measured. If it can be done, many readings are needed to evaluate the filter's response properly. Moreover, each time the filter is adjusted, the procedure must be repeated. Since bandwidths are small, I decided to build a simple narrow-band sweep generator, commonly known as a wobulator.

It uses an all-electronic transducer, such as a common reactance tube, to sweep the desired frequencies. Changing the tube's gain (Fig. 1) changes its input capacitance. The tube used has its suppressor grid brought out to a base pin and not internally connected to the cathode. The gain is changed by applying a changing voltage (Δe) as shown. A sinusoidal voltage could be used, but it would give a scope trace bunched up in some places and spread out in others. A more sophisticated method is to use a sawtooth, so it can be used as both the deviation voltage and sweep or sync for the scope.

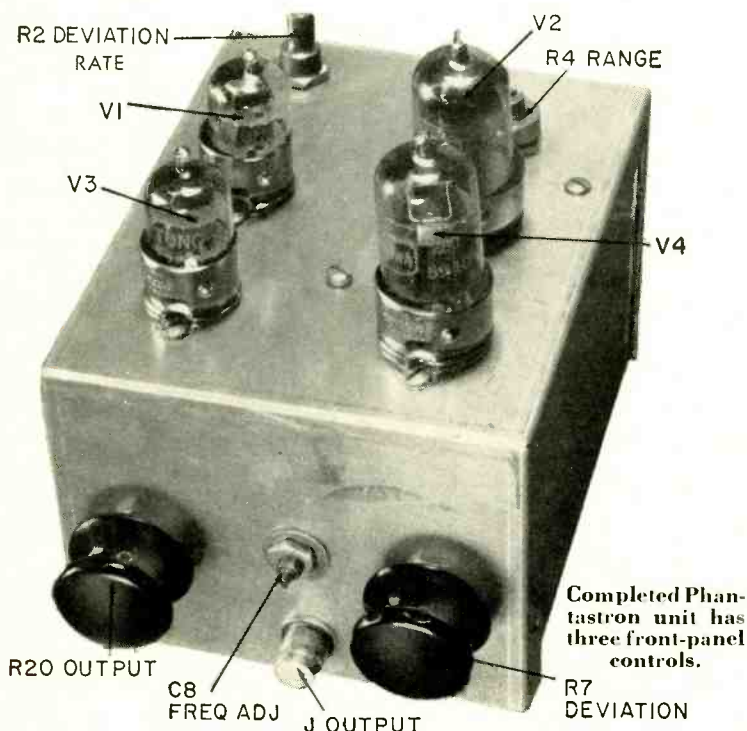

Completed Phantatron unit has three front-panel controls.


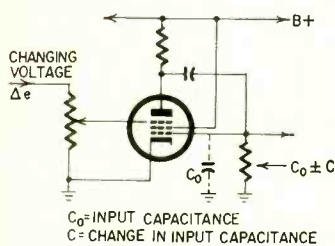


Fig. 1—Basic wobulator is built around a reactance tube.

- R1—pot, 500,000 ohms
- R2—470,000 ohms
- R3—pot, 1 megohm
- R4, 6—1,000 ohms
- R5—pot, 2.2 megohms
- R7—10,000 ohms
- R8—1 megohm
- R9—470 ohms
- R10—pot, 1,000 ohms
- R11, 12—47,000 ohms
- All resistors 1/2-watt 10%
- C1—4 μ f, 250 volts, electrolytic
- C2—0.47 μ f, paper
- C3—0.1 μ f, paper
- C4—25 μ f, 25 volts, electrolytic
- C5—15 μ f, mica
- C6, 8—.01 μ f, ceramic
- C7—65–340 μ f, trimmer (El-Menco 303 or equivalent)
- J—coaxial connector
- L—1 mh (Miller 952 or equivalent)
- V1—NE-51
- V2—6AS6
- V3—12AU7
- Chassis, to suit
- Miscellaneous hardware

Fig. 2—Circuit of neon wobulator.

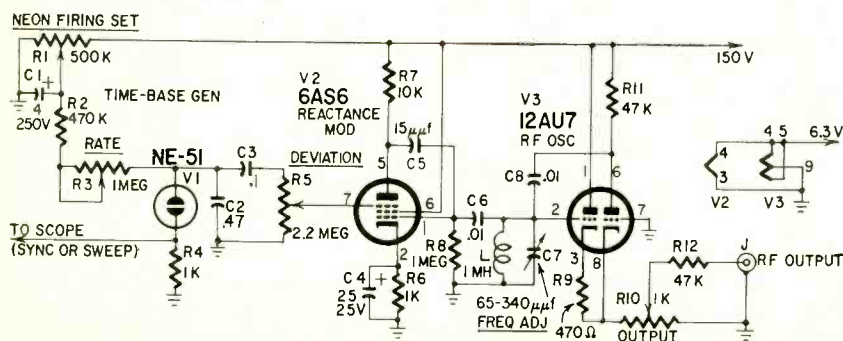

Two wobulators—a simple two-tube neon lamp type and a four-tube reactance-wobbled instrument—are described. The more practical four-tube wobulator is designed for a center frequency of 455 kc, but may be adapted to other ranges. Maximum deviation is about 80 kc—sweep rate 2-15 cycles per second.

Instrument performs exactly as specified by the author. It would also be ideal as a sweep generator for AM radios and especially useful for hi-fi AM tuners where flat, broadband response is important. The electronic sweep is both interesting and practical. Do not confuse this instrument with trick gadgets and gimmicks.



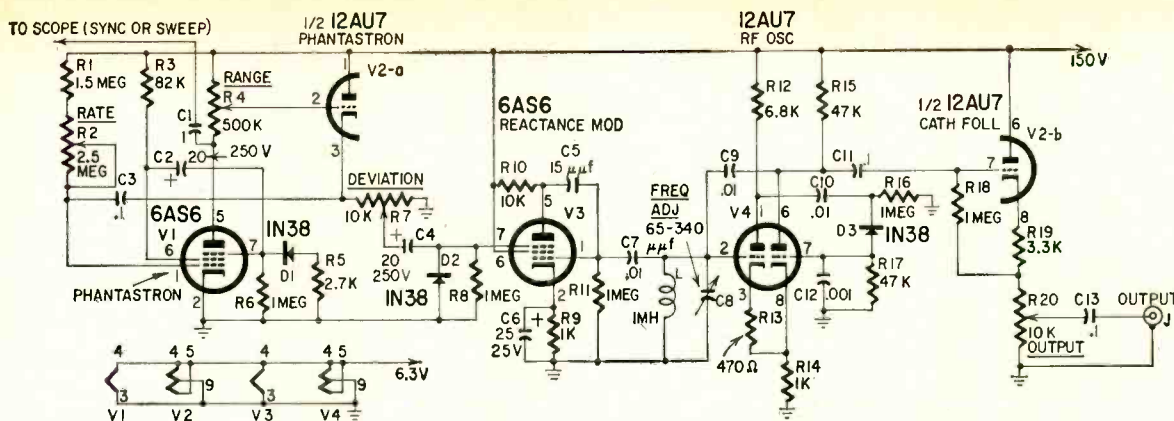


Fig. 3—Four-tube phantastron wobblator is an extremely accurate instrument.

- R1—1.5 megohms
- R2—pot, 2.5 megohms
- R3—82,000 ohms
- R4—pot, 500,000 ohms
- R5—2,700 ohms
- R6, 8, 11, 16, 18—1 megohm
- R7, 20—pot, 10,000 ohms
- R9, 14—1,000 ohms
- R10—10,000 ohms
- R12—6,800 ohms
- R13—470 ohms
- R15, 17—47,000 ohms
- R19—3,300 ohms
- All resistors 1/2-watt 10%
- C1—1 μ f, paper
- C2—20 μ f, 250 volts, electrolytic
- C3—0.1 μ f, ceramic
- C4—20 μ f, 250 volts, electrolytic
- C5—15 μ f, mica
- C6—25 μ f, 25 volts, electrolytic
- C7, 9, 10—.01 μ f, ceramic
- C8—65-340 μ f, trimmer (El-Menco 303 or equivalent)
- C11, 13—.01 μ f, paper
- C12—.001 μ f, ceramic
- D1, 2, 3—IN38
- J—coaxial connector
- L—1 mh (Miller 952 or equivalent)
- V1, 3—6AS6
- V2, 4—12AU7
- Chassis, to suit
- Miscellaneous hardware

Two 455-ke wobblator designs are detailed. The first, a neon wobblator, is a simple two-tube affair with a neon-lamp relaxation oscillator that is easy to build, but lacks certain refinements. Nevertheless, it will give a good account of itself. The second, called a phantastron wobblator, is a four-tube affair giving complete versatility.

Neon wobblator

The neon wobblator is composed of a neon-lamp time-base generator (Fig. 2) which supplies a sawtooth voltage, set by R3, between 1 and 10 cycles. Resistor R4 is inserted to extract a spike to sync the scope. The sawtooth amplitude is controlled by R5, the DEVIATION control. This sawtooth is then fed to V2's suppressor and varies V2's gain, hence controlling part of the capacitance in shunt with coil L. The oscillator itself is a two-terminal Crosby. Its output is developed across R10, the cathode resistor in the cathode-follower output stage.

Resistor R12 isolates the output from the oscillator to minimize oscillator pull, and at the same time presents a high impedance to the external load. Maximum deviation is approximately 80 kc.

This circuit has several drawbacks but functions satisfactorily. The sawtooth is not linear, but exponential, leading to distortion. Also, the sawtooth is a rising function that puts the low-frequency end of the pattern on the

right side of the scope screen and the high-frequency end on the left. This is not serious, but could cause misinterpretation of results. The final difficulty is that anything connected to the output circuit could pull the oscillator since the load is in the cathode circuit.


Phantastron wobblator

The circuit shown in Fig. 3 has none of the neon-wobblator drawbacks. It develops a linear sweep that has a negative slope—decreases with time. Thus, the presentation on the face of the scope has the low-frequency end at the left and the high-frequency end on the right. V1 and V2-a comprise a linear phantastron. Potentiometer R2 controls the rate, which has a range of about 2 to 15 cycles. The output is taken off V2-a's cathode and fed into V3. From here on, the operation of the circuit is identical to the neon wobblator. The

only exception is that the output is taken from V4's plate instead of V2-b, a cathode follower. Thus, a load hung on the cathode follower's output cannot disturb the oscillator.

To set up this circuit:

- ▶ Turn the DEVIATION control full on.
 - ▶ Connect a scope to the output and adjust for a screen pattern similar to Fig. 4.
 - ▶ Distance A represents one excursion through the frequency range desired. Now connect a signal generator with approximately 10,000 to 20,000 ohms in series across the wobblator output. A "glitch" or beat marker will be seen.
 - ▶ Alternately adjust RANGE control (R4) and the signal generator until the maximum excursion is around 50 kc or any range desired. Once R4 is
- (Continued on page 80)*

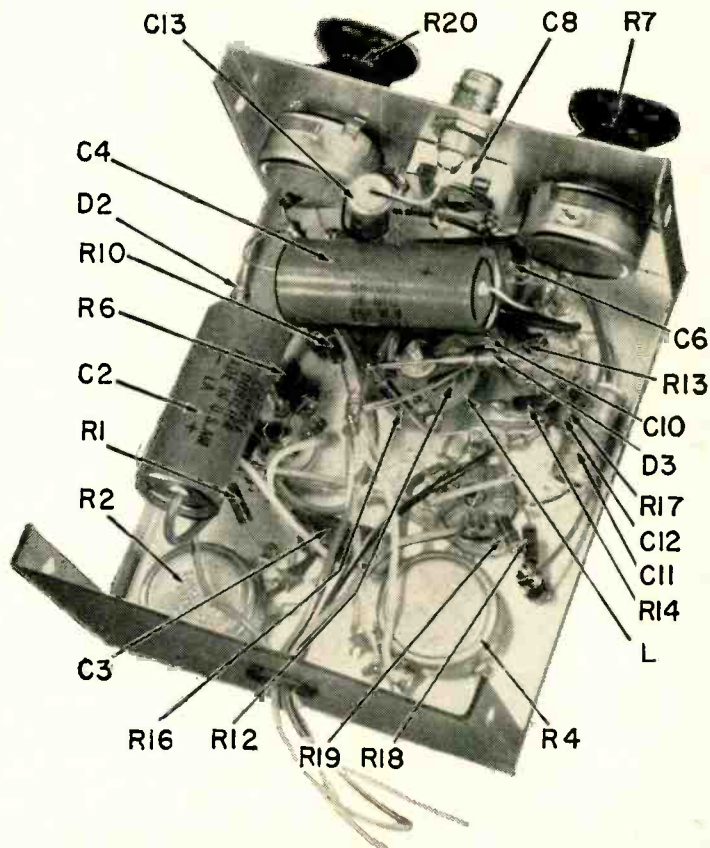

Bird's eye view of the insides of a phantastron wobblator.

A PROPHECY

For men and women with a sincere desire to succeed



"In the years that have passed since my days on the faculty of RCA Institutes, I have become even more firmly convinced that the individual who continues his education . . . particularly his technical education . . . is the individual who profits both as a thinking man and as a working man. Science and industry will reward you for your talents and energy. Out of your efforts may come inventions, new products, processes and services. There is everything good yet to be accomplished in our lives and in our work. What man has done, man can do better."

David Sarnoff

Chairman of the Board,
Radio Corporation of America

RCA Institutes Offers the Finest of Home Study and Resident Training for Your Career in the Rapidly Expanding World of Electronics

RCA Institutes, founded in 1909, is one of the largest technical institutes in the United States devoted exclusively to electronics. A service of Radio Corporation of America, RCA Institutes offers unparalleled facilities for technical instruction . . . tailored to your needs. The very name "RCA"

means dependability, integrity, and scientific advance.

RCA Institutes Home Study School, licensed by the New York State Department of Education, offers a complete program of integrated courses for beginners and advanced students rang-

ing from electronic fundamentals to automation. All courses are designed to prepare you for a rewarding career in the rapidly expanding world of electronics. *The caliber of the training you receive is the finest!* And you get top recognition as an RCA Institutes graduate!

START YOUR CAREER TRAINING IN THE RAPIDLY EXPANDING WORLD OF ELECTRONICS

RCA INSTITUTES
offers
HOME STUDY COURSES
and
**RESIDENT SCHOOL
COURSES**
in New York City
and Los Angeles



**SEND
THIS
POSTCARD
FOR
FREE
BOOK**

**FILL OUT,
DETACH, AND
MAIL TODAY**



RCA INSTITUTES, INC., Dept. ZRE-31
Schools of Television and Electronic Technology
A Service of Radio Corporation of America
350 West Fourth Street, New York 14, N. Y.
610 South Main Street, Los Angeles 14, Calif.

Please rush me the FREE illustrated book checked below. I understand that I am under no obligation and that no salesman will call.

Home Study School Resident School New York
Resident School Los Angeles

Name _____
(Please Print)

Address _____

City _____ Zone _____ State _____

Korean Vets: Enter Discharge Date _____

CANADIANS: Take advantage of these same RCA Institutes Home Study Courses at no additional cost. No postage, no customs, no delay. Fill out this card and send in envelope to: RCA Victor Limited, 5581 Royalmount Ave., Montreal 9, Que.



RCA Institutes offers the finest of training for your career in Electronics

*Learn how you can take advantage
of this opportunity*

SEND POSTAGE-FREE CARD FOR FREE BOOK TODAY.


BUSINESS REPLY MAIL

No Postage Stamp Necessary if mailed in U. S.

Postage will be paid by —


RCA INSTITUTES, INC., Dept. ZRE-31
350 West Fourth Street
New York 14, N. Y.

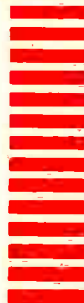FIRST CLASS
PERMIT NO.
10662
NEW YORK, N. Y.



HOME STUDY COURSES *in* *Electronic Fundamentals • TV Servicing* *Color TV • Electronics for* *Automation • Transistors*

Voluntary Tuition Plan. The important thing to remember about RCA Institutes Training is the convenient, *no-obligation payment plan*. This plan affords you the most economical possible method of home study training because you pay for each study group only when you order it. If you interrupt your course *at any time, for any reason*, you owe nothing more. You *never* have to pay for the whole course if you don't complete it. No other obligations. No monthly installment payments!

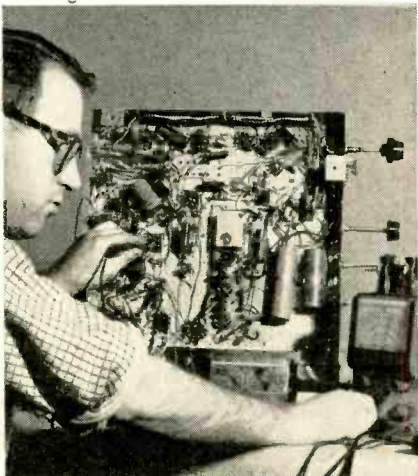

RCA Instruction is Personal. With RCA Home Study training you set *your own pace* in keeping with *your own ability*, finances, and time. The Institutes allows you ample time to complete the course. Your lesson assignments are individually graded by

technically trained personnel, and helpful comments are added where required. You get theory, experiment, and service practice beginning with the very first lesson. All lessons are profusely illustrated. You get a *complete training package* throughout the entire course.

You Get Prime Quality Equipment. All kits furnished with the course are complete in every respect, and the equipment is top grade. You keep all the equipment furnished to you for actual use on the job... *and you never have to take apart one piece to build another!*

* * *

RESIDENT SCHOOLS *in* *Los Angeles and* *New York City* train you for any field of *Electronics* you may choose!


No Previous Technical Training Required For Admission. RCA Institutes Resident Schools in Los Angeles and New York City offer training that will prepare you to work in re-

warding positions on research and production projects in fields such as automation, communications, technical writing, television, computers, and other industrial and advanced electronics applications. Even if you did not complete high school, RCA will prepare you for such training with courses specially designed to provide the basic math and physics required for a career in electronics.

Free Placement Service. RCA Institutes graduates are now employed in important jobs at military installations such as Cape Canaveral, with important companies such as IBM, Bell Telephone Labs, General Electric, RCA, and in radio and TV stations all over the country. Many other graduates have opened their own businesses. A recent New York Resident School class had 92.06% of the graduates who used the Free Placement Service accepted by important electronics companies... *and had their jobs waiting for them on the day they graduated!*



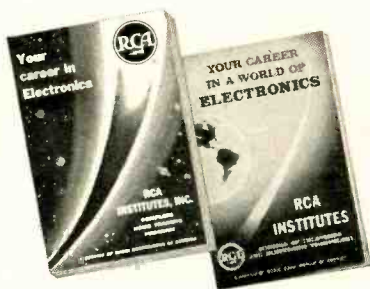Coeducational Day and Evening Courses. Day and Evening Courses are available at Resident Schools in New York City and Los Angeles. You can prepare for your career in electronics while continuing your normal full-time or part-time employment. Regular classes start four times each year.



**SEND POSTCARD FOR FREE
 ILLUSTRATED BOOK TODAY!
 SPECIFY HOME STUDY OR
 RESIDENT SCHOOL**

RCA INSTITUTES, INC. A SERVICE OF RADIO CORPORATION OF AMERICA, 350 W. 4th St., New York 14, N. Y., 610 S. Main St., Los Angeles 14, Calif.



The Most Trusted Name in Electronics

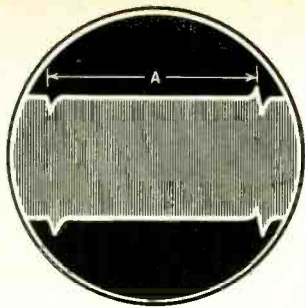


Fig. 4—Scope trace produced by the wobulator.


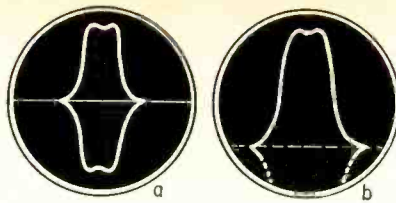


Fig. 6—Filter check waveforms; a—starting waveform; b—only top half is kept on scope screen.

Fig. 5—Setup for checking filter response with the wobulator.

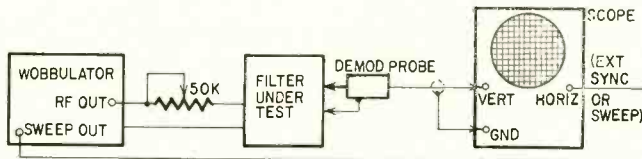

(Continued from page 75)

set, do not disturb. Use the DEVIATION control for all adjustments.

Power supplies are not shown. Any voltage around 150 will suffice. It is advisable to use a regulated supply.

Construction procedure

No part of the layout or construction should be difficult; there is nothing critical about the wiring.

The phantatron wobulator is built into a 5 x 4 x 3-inch case. The photos show the position of the parts. If a self-contained power supply is desired, a larger chassis is needed.

One final word in passing. This par-

ticular wobulator was designed for 455 kc for crystal filter investigations. However, it may be used for other applications such as aligning if strips, fm receivers, etc. For these jobs the center frequency may have to be raised by using a smaller coil and tuning capacitor. It was not the scope of this article to include such designs, but those who are enterprising enough will find the following hints helpful:

- ▶ It might be desirable to increase the repetition rate by decreasing C3 to say .01 μ f.
- ▶ Decrease R15 and include about 200 μ h in shunt with it.


Knowing that V3 supplies a capacitance change of approximately 50 μ f, one can determine the value for L necessary for the required frequency.

Using the wobulator


Let's assume we have built a filter and want to know what its response looks like. First, we set up the pattern as in Fig. 4, and connect a signal generator. Set the signal generator at the desired frequency and adjust the wobulator frequency control so a glitch appears approximately in the center of the trace. The wobulator is now ready for use.

Since the wobulator presents a low-impedance output, we run it through a high resistance into the filter as in Fig. 5. If the filter is fed through a buffer tube, connect the wobulator directly into the grid. Connect a scope as shown. Adjust the wobulator's output for as little drive as possible so as not to overload, if going through a buffer tube. Adjust the scope's gain and the wobulator's deviation control until you get a pattern like the one in Fig. 6-a. The pattern should be symmetrical about the axis. If it is not, decrease the wobulator's output. Now, since we are interested only in the top half of the figure, adjust the vertical position and gain of the scope to display only the top half. The pattern in Fig. 6-b should result.

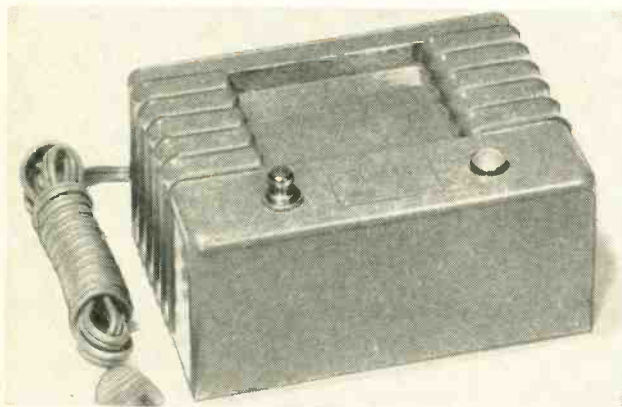With this pattern on the scope, effects of adjustments, additions and touch ups are readily apparent. END



Watch is placed in recessed section.

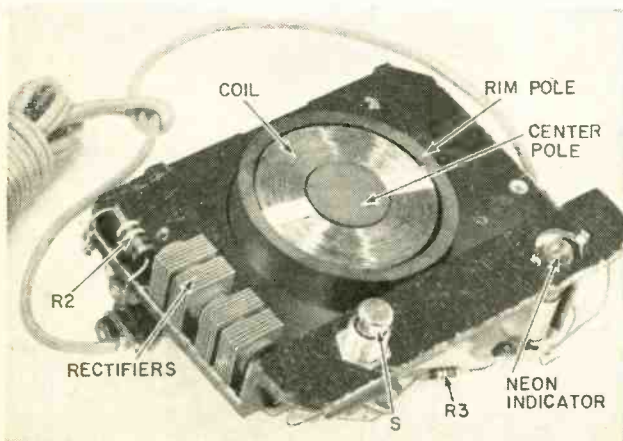


Inside view of watch demagnetizer.

WATCH DEMAGNETIZER

THIS simple compact unit demagnetizes watches quickly and safely. The entire process takes only 1/20 second and the unit operates at a frequency that cannot damage any part of the watch.

The demagnetizer is shown in the photos. To use it, the watch is placed in the recess on its top. The recess is aligned with a coil of enameled wire wound on a powdered-iron core. This, of course, is the demagnetizing coil. Then, with the unit connected to the ac line, the pushbutton is depressed. A few moments' wait and the watch is demagnetized. A neon lamp flashes to show the device is working.

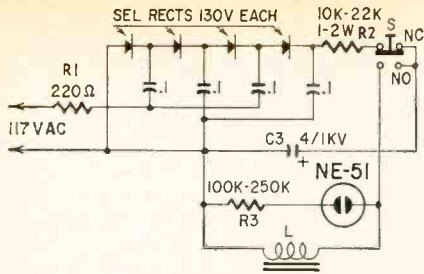The unit's operation is simple (see schematic). The demagnetizing coil (L) is connected to the normally open



switch contact. When not in use, the pushbutton's normally closed terminals complete a charging circuit to charge capacitor C3. A voltage quadrupler supplies 440 to 600 volts charging voltage. When the pushbutton is depressed, the charging circuit is opened and the discharge circuit, through L, is closed. When the capacitor's discharge current flows through L, a *ringing circuit* composed of L and C3 produces the damped ac wave (one that dies down quickly from its maximum value to zero) that does the demagnetizing. The frequency of the damped wave is determined by circuit values—about 500 cycles in the arrangement shown.


The damped oscillations give the same effect as using a standard demagnetizing device and moving its coil away from the watch—the amplitude of the ac field decays to zero.

The core and rim of the demagnetizing coil form opposite poles of an electromagnet with the polarity of each reversing at the ringing frequency. When a watch is placed in the demagnetizer, magnetic lines of force pass through the watch movement from the center post to the rim in rapidly reversing directions and decaying intensity to demagnetize the watch. The demagnetizer is the invention of Frank Dostal, chief engineer of American Time Products, Inc., which manufactures it.

CORRECTION


The symbol for pi (π) was inadvertently left out of the two reactance formulas in the second line of the second paragraph of the article "L-C Reactance Nomo Saves Calculation" on page 52 of the February issue. The nomo itself is correct. The formulas for capacitive and inductive reactance are $X_C = \frac{1}{2\pi fC}$ and $X_L = 2\pi fL$, respectively.

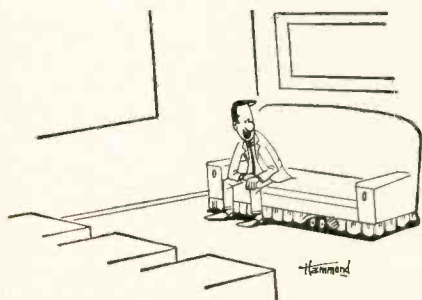We thank Mr. Lewis F. Garber, of Pasadena, Calif., for bringing this to our attention.



"See the difference in 3-channel stereo?"

MARCH, 1961

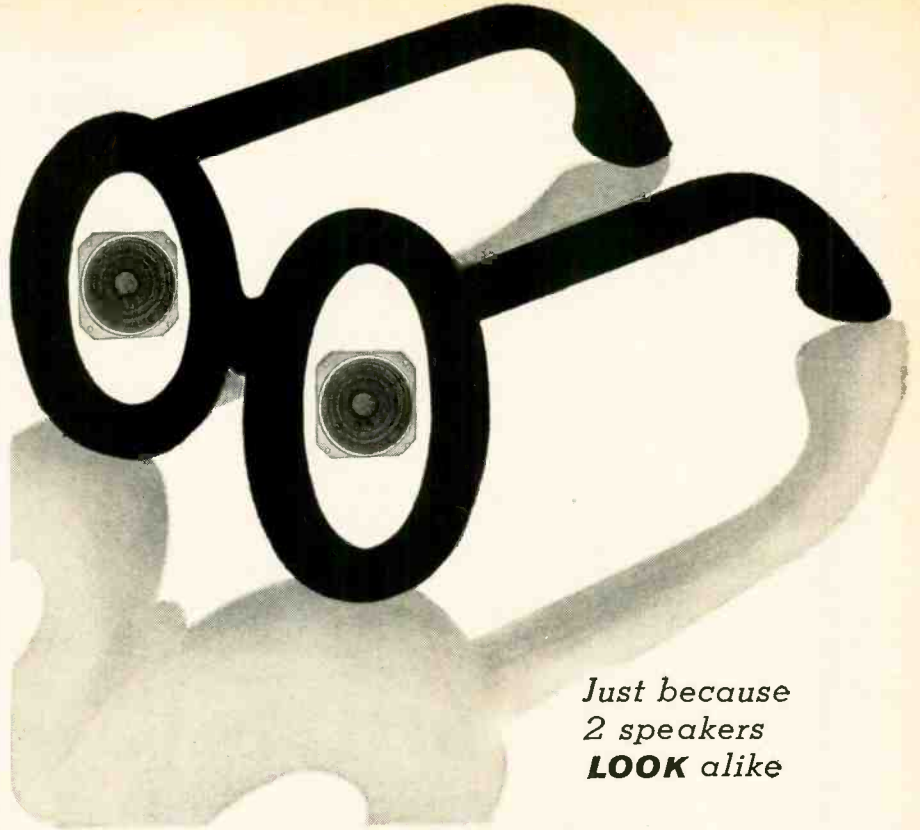

Just because
2 speakers
LOOK alike

doesn't mean they'll **SOUND** alike...

or that they'll give the same
trouble-free performance.

ask for **QUAM**

The NO CALL-BACK speaker with the exclusive Adjust-a-Cone Suspension
Completely manufactured in the United States of America

QUAM-NICHOLS COMPANY

238 East Marquette Road • Chicago 37, Illinois



SEND
NOW FOR
BIG FREE
CATALOG!

FREE Catalog Of The WORLD'S FINEST GOV'T SURPLUS ELECTRONIC BARGAINS

AUDIO AMPLIFIER & ALARM SYSTEM

AM-1415/UNS-1 AUDIO AMPLIFIER, printed circuit type using 5 Tubes: 3/12AX7, 1/12AT7, & 1/6AQ5 on a board 5 1/2 x 7 1/2". The 115 V., 60 cyc. power supply uses a 5Y3 Tube. Input impedance is 500 ohm and can be used for Phono pickup, carbon or crystal microphone. Output is conservatively rated 5 Watts (Tests indicate 10-15 Watts with good response). Front panel is finished in new Air Force blue, size is 7 3/4 x 9 3/4", has volume control, on/off switch, also two switches and sensitivity control for operation of the automatic alarm system (when desired). The alarm system is operated by adjusting the sensitivity control to the noise or sound level and when this is exceeded it operates the relay which closes the contacts that are wired to a 2 contact connector at the back of the chassis. This was used to operate an alarm bell warning of approaching aircraft (has unlimited uses).

Price—Brand New: \$14.95

Address Dept. RE • Prices F.O.B. Lima, O. • 25% Deposit on C.O.D. Orders




FAIR RADIO SALES
2133 ELIDA RD. • P.O. Box 1105 • LIMA, OHIO



STOP!...
Demand the finest in Electronic Test Equipment—EMC, of course. You get the most quality per measurement dollar!

NEW! EMC Model 301 Speedi Tube Tester

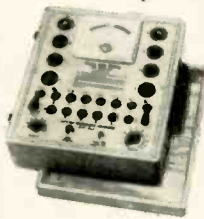Checks tubes in seconds. Checks shorts, leakages, and quality. Over 375 tubes, including 024, now listed. New listings available. Uses line voltage regulation. Checks and rejuvenates Picture Tubes with Model PTA (Picture Tube Adaptor), at only \$4.50. Model 301P (illustrated),



with 4½" meter & oak Carrying case \$47.50
Kit 33.20
Model 302C, (with 7½" meter) 62.90
Kit 47.90

NEW! EMC Model 108 Handi Tester

The only appliance and auto battery tester in its price class to use a D'Arsonval, instead of an iron vane type meter. Gives exclusive advantages of maximum accuracy and scale length, and minimum battery replacement cost . . . at no added charge. Complete with test leads and instruction manual.



Wired \$15.95 Kit 12.95

NEW! EMC Model 905-6A Battery Eliminator, Charger, and Vibrator Checker


A MUST for auto radio service. Features continuously variable voltage output—in either 6 or 12 volt operation. Checks all 6 or 12 volt vibrators.



Wired \$67.90 Kit 44.90


NEW! EMC Model 601, Wide Band Oscilloscope for Color & Monochrome TV

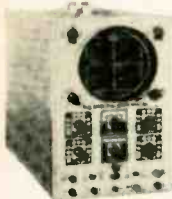Features full 5 mc band with push-pull vertical amplifier with sensitivity .02 volts per inch, retrace blanking amplifier for clearer pictures, and multivibrator sweep from 15 cycles to over 75 kilocycles. Wired and tested \$117.90



NEW! EMC Model 206P Dynamic Mutual Conductance Tube Tester

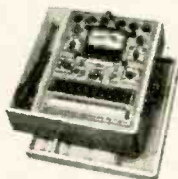The lowest priced mutual conductance tube checker on market. Checks tubes for microhm value and gas content. Completely flexible switching. Your best buy in a quality tube tester. (Hand rubbed Carrying Case) \$83.50




Yes, tell me more, send me FREE—a detailed catalog of the complete EMC line. RE-361

NAME _____

STREET _____

CITY _____ STATE _____

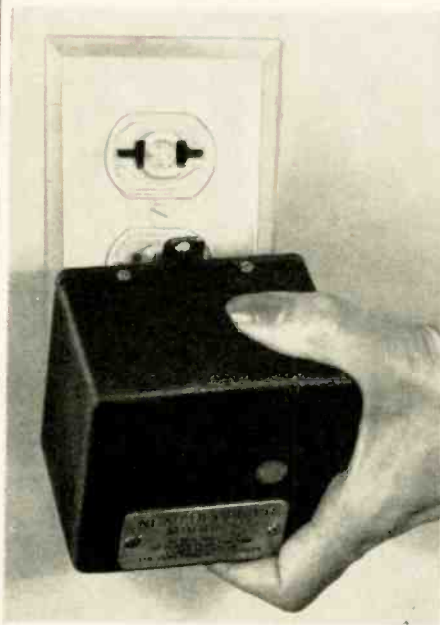EMC Electronic Measurements Corp.
625 B'way, New York 12, N. Y.
Ex. Dept., Pan-Mar Corp., 1270 B'way, N.Y. 1, N.Y.



Alarm receiver simply plugs into convenient wall receptacle.

Proposed new system for Civil Defense emergency warnings would use simple warning device that can be plugged into the nearest ac electric outlet and forgotten

AS intercontinental ballistic missiles approach perfection, our Office of Civil and Defense Mobilization is intensifying its efforts to produce an emergency warning system that will be immediate, universal and economically practical.

Sirens have been depended on in the past. Though effective for outdoor use in urban areas, they cannot always be heard indoors and, as population thins out, their effectiveness drops, reaching practically zero in rural areas.

Three routes for reaching the indoor population were considered: the telephone, the radio and the power line. The cost of modifying the telephone system to give an instant warning was found prohibitive. Besides, not all people have telephones. Radios are almost universal, but only a small percentage of them may be turned on at any given moment (a very small percentage at such hours as 3 AM, for example).

But 96% of the population has electricity, and the power line is "on" 24

emergency alarm in your home



With cover removed, internal construction is revealed.

hours a day. An alarm device that would operate from the power lines would approach the ideal.

Such a system has been developed and, after passing intensive field tests at Charlotte, Mich., last fall, appears to be the coming warning method. Called the National Emergency Alarm Repeater (NEAR), it is simply a small box (see photo) that plugs into any convenient outlet. It sends a raucous buzz—or series of irregular buzzes—for 50 seconds when a warning signal is put on the line.


Details of NEAR device

The basic units of the device are a series coil-capacitor circuit tuned to 240 cycles, across the line; a vibrating reed that closes a circuit intermittently when a 240-cycle is received; a time-delay device and a 120-cycle clapper to sound the alarm.

The time delay is a very important feature. A useful receiver must operate every time a warning signal is received,

but must not be triggered by a 240-cycle transients or the coded signals often used on power lines. If the homeowner is awakened a few times by false alarms, he will unplug the device and its usefulness will have ended.

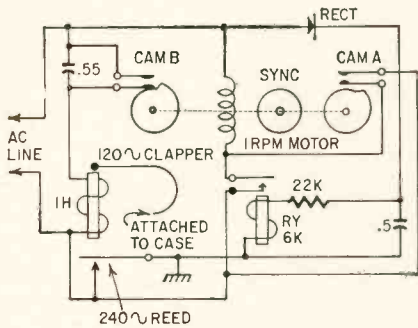The resonant circuit across the line is a 0.55- μ f capacitor in series with a 1-henry coil (see diagram). Both the 240-cycle reed and 120-cycle clapper are actuated by the core of this coil. With only 60-cycle current in the line, not enough current can pass through the coil to attract either reed or clapper.



Circuit of the NEAR receiver.

When a 240-cycle signal is received, more current flows in the resonant circuit and the reed buzzes at a 240-cycle rate. This passes current through the rectifier every time the reed makes contact when the line current is in the right direction. The dc passing through the 6,000-ohm relay pulls down its armature and starts the 1-rpm motor.

The motor, which is the time-delay device, starts to rotate. If the signal lasts less than 10 seconds, the relay opens and the motor returns to its starting point. But if the signal continues for 10 seconds, two cams attached to the motor shaft close contacts. One set shorts out the 0.55- μ f capacitor across the line, putting the full 117 volts on the coil. The current is now great enough to operate the 120-cycle tuned-reed clapper, and it sounds the alarm, using the case of the receiver as its "bell." The cam may be so shaped as to close the contacts for 50 seconds, or to open and close them irregularly during that period, heightening the alarm effect.

The other cam shorts the relay contacts, permitting the alarm to continue after the signal is shut off. After 1 minute, the first cam reaches the end of its cycle and shuts the motor off, awaiting another signal.

The 240-cycle warning signal is obtained from the 60-cycle power frequency with saturable reactors which act as frequency multipliers. These are installed at power stations or substations and supply a signal of approximately 1 volt to the receivers. The NEAR plan would link them up into a series of repeaters, so that a signal from the key station would actuate the adjacent ring of signal generators, which would in turn actuate another ring. Between 400 and 600 generators, properly placed, could cover the whole United States. END

FREE GIANT 1961 204 PAGE CATALOG

B-A 1961

ANNUAL CATALOG #11

SINCE 1927

A Complete Buying Guide for Everything in

RADIO TV ELECTRONICS

for DEALERS, SERVICE MEN, SCHOOLS, BROADCASTERS, INDUSTRIALS, THEATRE, MANUFACTURERS, CHURCHES, HOMES, PUBLIC UTILITIES, LABORATORIES, ENGINEERS, EXPERIMENTERS, ADVENTURERS

INDEX PAGE 201-202 PHONE Baltimore 7-1193

Guarantee

We guarantee every item in our catalog to be exactly described and guaranteed to be the actual item represented. No portion of the money described will be given the service contracted by the maker or your money back!

BURSTEIN-APPLEBEE 1012-14 McGEE ST., KANSAS CITY 6, MO.

BURSTEIN-APPLEBEE CO. Dept. RE
1012-14 McGEE St., Kansas City 6, Mo.

Send Free 1961 B-A Catalog No. 611

SAVE UP TO 50% ON B-A SELECTED KITS

TOP VALUES IN POWER AND HAND TOOLS

HI-FI AND STEREO SYSTEMS & COMPONENTS

30 PAGES OF BARGAINS NOT IN ANY OTHER CATALOG

100'S OF NEW ITEMS LISTED HERE FOR 1ST TIME

RUSH COUPON TODAY!

NAME _____

ADDRESS _____

CITY _____ STATE _____

NEW MAGNIFYING LAMP FOR PRECISION WORK!

Swing-O-Lite INSPECTOR

the best lamp you can use for miniature assembly work, bench work, blueprints and schematics, etc.

DEALER & DISTRIBUTOR INQUIRIES INVITED
REPS WANTED—CHOICE TERRITORIES OPEN

Write for FREE CATALOG of complete line. Dept. RE-361

NAME _____

STREET _____

CITY _____ STATE _____

13 MOONBARK ROAD, HACKENSACK, N. J.

\$36⁰⁰

LIST LESS BULB

MODEL M1
(45" arm reach)

- 5" diameter precision polished magnifying glass
- 22 watt shadow-free fluorescent light
- Complete arm mobility for exact spot location
- Exclusive convenience electric outlet in base (optional extra)
- Choice of colors and mounts

OTHER MODELS AVAILABLE

EXAMINE ANY OF THESE TESTERS BEFORE YOU BUY!!

Yes, we offer to ship at our risk
one or more of the testers
described on these pages.

SUPERIOR'S NEW MODEL 770-A

VOLT-OHM MILLIAMMETER



FEATURES:

- Compact—measures 3 1/8" x 5 7/8" x 2 1/4".
- Uses "Full View" 2% accurate 850 Microampere D'Arsonval type meter
- Housed in round-cornered, molded case.

SPECIFICATIONS:

- 6 A.C. VOLTAGE RANGES: 0-15/30/150/300/1500/3000 Volts.
- 6 D.C. VOLTAGE RANGES: 0-7.5/15/75/150/750/1500 Volts.
- 2 RESISTANCE RANGES: 0-10,000 Ohms, 0-1 Megohm.
- 3 D.C. CURRENT RANGES: 0-15/150 Ma., 0-1.5 Amps.
- 3 DECIBEL RANGES: -6 db to +18 db, +14 db to +38 db, +34 db to +58 db.

The Model 770-A comes complete with test leads and operating instructions. Price is \$15.85. Terms: \$3.85 after 10 day trial then \$4.00 monthly for 3 months.

SUPERIOR'S NEW MODEL 79

SUPER-METER

WITH NEW 6" FULL VIEW METER



SPECIFICATIONS:

- D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500.
- A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000.
- D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes.
- RESISTANCE: 0 to 1,000/100,000 Ohms. 0 to 10 Megohms.
- CAPACITY: .001 to 1 Mfd. 1 to 50 Mfd.
- REACTANCE: 50 to 2,500 Ohms, 2,500 Ohms to 2.5 Megohms.
- INDUCTANCE: 15 to 7 Henries, 7 to 7,000 Henries.
- DECIBELS: -6 to +18, +14 to +38, +34 to +58.

The following components are all tested for QUALITY at appropriate test potentials. Two separate BAD-GOOD scales on the meter are used for direct readings.

All Electrolytic Condensers from 1 MFD to 1000 MFD.
All Selenium Rectifiers. All Germanium Diodes.
All Silicon Rectifiers. All Silicon Diodes.

Model 79 comes complete with operating instructions, test leads and carrying case. Price is \$38.50. Terms: \$8.50 after 10 day trial then \$6.00 monthly for 5 months.

SUPERIOR'S NEW MODEL 77

VACUUM TUBE VOLTMETER

WITH NEW 6" FULL VIEW METER



Compare it to any peak-to-peak V.T.V.M. made by any other manufacturer at any price!

SPECIFICATIONS:

- DC VOLTS—0 to 3/15/75/150/300/750/1500 volts at 11 megohms input resistance.
- AC VOLTS (RMS)—0 to 3/15/75/150/300/750/1500 volts.
- AC VOLTS (Peak to Peak)—0 to 8/40/200/400/800/2000 volts.
- ELECTRONIC OHMMETER—0 to 1000 ohms/10,000 ohms/100,000 ohms/1 megohm/10 megohms/100 megohms/1,000 megohms.
- DECIBELS—10 db to +18 db, +10 db to +38 db, +30 db to +58 db. All based on 0 db = .006 watts (6 mw) into a 500 ohm line (1.73v).
- ZERO CENTER METER—For discriminator alignment with full scale range of 0 to 1.5/7.5/37.5/75/150/375/750 volts at 11 megohms input resistance.

Model 77 comes complete with operating instructions, probe and test leads and carrying case. Price is \$42.50. Terms: \$12.50 after 10 day trial then \$6.00 monthly for 5 months.

SUPERIOR'S NEW MODEL 80

20,000 OHMS PER VOLT ALLMETER



6 INCH FULL-VIEW METER provides large easy-to-read calibrations. No squinting or guessing when you use Model 80.

MIRRORED SCALE permits fine accurate measurements where fractional readings are important.

SPECIFICATIONS:


- 7 D.C. VOLTAGE RANGES: (At a sensitivity of 20,000 Ohms per Volt) 0 to 15/75/150/300/750/1500/7500 Volts.
- 6 A.C. VOLTAGE RANGES: (At a sensitivity of 5,000 Ohms per Volt) 0 to 15/75/150/300/750/1500 Volts.
- 3 RESISTANCE RANGES: 0 to 2,000/200,000 Ohms, 0-20 Megohms.
- 2 CAPACITY RANGES: .00025 Mfd. to .3 Mfd., .05 Mfd. to 30 Mfd.
- 5 D.C. CURRENT RANGES: 0-75 Microamperes, 0 to 7.5/75/750 Milli-amperes, 0 to 15 Amperes.
- 3 DECIBEL RANGES: -6 db to +18 db, +14 db to +38 db, +34 db to +58 db.

NOTE: The line cord is used only for capacity measurements. Resistance ranges operate on self-contained batteries.

Model 80 Allmeter comes complete with operating instructions, test leads and portable carrying case. Price is \$42.50. Terms: \$12.50 after 10 day trial then \$6.00 monthly for 5 months.

SUPERIOR'S NEW MODEL 70 UTILITY TESTER

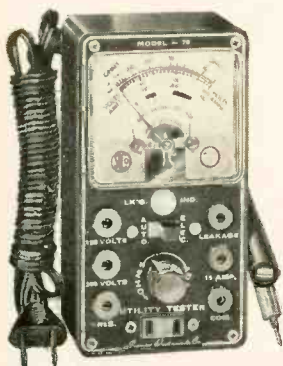FOR REPAIRING ALL ELECTRICAL APPLIANCES MOTORS ★ AUTOMOBILES



Written in simple, easy-to-understand style.

INCLUDED FREE

64 page condensed course in electricity. Profusely illustrated.

As an electrical trouble shooter the Model 70:

• Will test Toasters, Irons, Broilers, Heating Pads, Clocks, Fans, Vacuum Cleaners, Refrigerators, Lamps, Fluorescents, Switches, Thermostats, etc. • Measures A.C. and D.C. Voltages, A.C. and D.C. Current, Resistances, Leakage, etc. • Incorporates a sensitive direct-reading resistance range which will measure all resistances commonly used in electrical appliances, motors, etc. • Leakage detecting circuit will indicate continuity from zero ohms to 5 megohms (5,000,000 ohms).

As an Automotive Tester the Model 70 will test:

• Both 6 Volt and 12 Volt Storage Batteries • Generators • Starters • Distributors • Ignition Coils • Regulators • Relays • Circuit Breakers • Cigarette Lighters • Stop Lights • Condensers • Directional Signal Systems • All Lamps and Bulbs • Fuses • Heating Systems • Horns • Also will locate poor grounds, breaks in wiring, poor connections, etc.

Model 70 comes complete with 64 page book and test leads. Price is \$15.85. Terms: \$3.85 after 10 day trial then \$4.00 monthly for 3 months.

DID YOU EVER?

- ▶ Order merchandise by mail, including deposit or payment in full, then wait and write...wait and write?
- ▶ Purchase anything on time and sign a lengthy complex contract written in small difficult-to-read type?
- ▶ Purchase an item by mail or in a retail store then experience frustrating delay and red tape when you applied for a refund?

Obviously prompt shipment and attention to orders is an essential requirement in our business... We ship at our risk!

NO

**CONTRACT TO SIGN
CO-MAKERS
EMPLOYER
NOTIFICATION**

The simple order authorization included in this offer is all you sign. We ask only that you promise to pay for or return the goods we ship in good faith.

**EXAMINE ANY ITEM YOU SELECT
IN THE PRIVACY OF YOUR OWN HOME**

Then if completely satisfied pay on the interest-free terms plainly specified. When we say interest-free we mean not one penny added for "interest" for "finance" for "credit-checking" or for "carrying charges." The net price of each tester is plainly marked in our ads—that is all you pay except for parcel post or other transportation charges we may prepay.

SUPERIOR'S NEW MODEL 82A
MULTI-SOCKET TYPE

TUBE TESTER



- SPECIFICATIONS:**
- Tests over 1000 tube types.
 - Tests OZ4 and other gas-filled tubes.
 - Employs new 4" meter with sealed air-damping chamber resulting in accurate vibrationless readings.
 - Use of 22 sockets permits testing all popular tube types and prevents possible obsolescence.
 - Dual Scale meter permits testing of low current tubes.
 - 7 and 9 pin straighteners mounted on panel.
 - All sections of multi-element tubes tested simultaneously.
 - Ultra-sensitive leakage test circuit will indicate leakage up to 5 megohms.

Model 82A comes housed in handsome, portable, saddle-stitched Texon case. Price is \$36.50. Terms: \$6.50 after 10 day trial then \$6.00 monthly for 5 months.

SUPERIOR'S NEW MODEL TW-11
STANDARD PROFESSIONAL

TUBE TESTER



- Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin-number in the RMA base numbering system, the user can instantly identify which element is under test.
- Free-moving built-in roll chart provides complete data for all tubes. All tube listings printed in large-easy-to-read type.
- **NOISE TEST:** Phono-jack on front panel for plugging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.
- **SEPARATE SCALE FOR LOW-CURRENT TUBES**—Previously, on emission type tube testers, it has been standard practice to use one scale for all tubes. As a result, the calibration for low-current types has been restricted to a small portion of the scale. The extra scale used here greatly simplifies testing of low-current types.

The Model TW-11 comes housed in a handsome, portable, saddle-stitched Texon case. Price is \$47.50. Terms: \$11.50 after 10 day trial then \$6.00 monthly for 6 months.

SUPERIOR'S NEW MODEL 83A

C.R.T. TESTER

**Tests and Rejuvenates
ALL PICTURE TUBES**

- ALL BLACK AND WHITE TUBES**
From 50 degree to 110 degree types—from 8" to 30" types.
- ALL COLOR TUBES**
Test ALL picture tubes—in the carton—out of the carton—in the set!




Model 83A provides separate filament operating voltages for the older 6.3 types and the newer 8.4 types. Model 83A properly tests the red, green and blue sections of color tubes individually—for each section of a color tube contains its own filament, plate, grid and cathode. Model 83A will detect tubes which are apparently good but require rejuvenation. Such tubes will provide a picture seemingly good but lacking in proper definition, contrast and focus. Rejuvenation of picture tubes is not simply a matter of applying a high voltage to the filament. Such voltages improperly applied can strip the cathode of the oxide coating essential for proper emission. The Model 83A applies a selective low voltage uniformly to assure increased life with no danger of cathode damage.

Model 83-A comes housed in handsome portable Saddle-stitched Texon case—complete with socket for all black and white tubes and all color tubes. Price is \$38.50. Terms: \$8.50 after 10 day trial then \$6.00 monthly for 5 months.

SUPERIOR'S NEW MODEL 85

TRANS-CONDUCTANCE TYPE TUBE TESTER

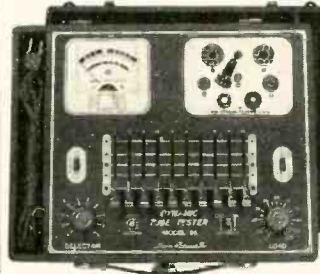

- Employs latest improved TRANS-CONDUCTANCE circuit. Test tubes under "dynamic" (simulated) operating conditions. An in-phase signal is impressed on the input section of a tube and the resultant plate current change is measured as a function of tube quality. This provides the most suitable method of simulating the manner in which tubes actually operate in radio, TV receivers, amplifiers and other circuits. Amplification factor, plate resistance and cathode emission are all correlated in one meter reading.
- **SYMBOL REFERENCES:** Model 85 employs time-saving symbols (*, +, ●, ▲, ■) in place of difficult-to-remember letters previously used. Repeated time-studies proved to us that use of these scientifically selected symbols speeded up the element switching step. As the tube manufacturers increase the release of new tube types, this time-saving feature becomes necessary and advantageous.

• **"FREE-POINT" LEVER TYPE ELEMENT SWITCH ASSEMBLY** marked according to RETMA basing, permits application of test voltages to any of the elements of a tube.

• **FREE FIVE (5) YEAR CHART DATA SERVICE.** Revised up-to-date subsequent charts will be mailed to all Model 85 purchasers at no charge for a period of five years after date of purchase.

Model 85 comes complete, housed in a handsome portable cabinet with slip-on cover. Price is \$52.50. Terms: \$12.50 after 10 day trial then \$8.00 monthly for 5 months.

SUPERIOR'S NEW MODEL TV-50A

GENOMETER 7 Signal Generators in One!



- ✓ R.F. Signal Generator for A.M.
- ✓ R.F. Signal Generator for F.M.
- ✓ Audio Frequency Generator
- ✓ Bar Generator
- ✓ Cross Hatch Generator
- ✓ Color Dot Pattern Generator
- ✓ Marker Generator


A versatile all-inclusive GENERATOR which provides ALL the outputs for servicing:

- A.M. Radio • F.M. Radio • Amplifiers
- Black and White TV • Color TV

The Model TV-50A comes absolutely complete with shielded leads and operating instructions. Price is \$47.50. Terms: \$11.50 after 10 day trial then \$6.00 monthly for 6 months.

SUPERIOR'S NEW MODEL 88

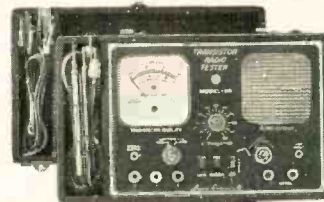TESTS ALL TRANSISTORS AND TRANSISTOR RADIOS



AS A TRANSISTOR RADIO TESTER

An R.F. Signal source, modulated by an audio tone is injected into the transistor receiver from the antenna through the R.F. stage, past the mixer into the I.F. Amplifier and detector stages and on to the audio amplifier. This injected signal is then followed and traced through the receiver by means of a built-in High Gain Transistorized Signal Tracer until the cause of trouble is located and pinpointed.

AS A TRANSISTOR TESTER

The Model 88 will test all transistors including NPN and PNP, silicon, germanium and the new gallium arsenide types, without referring to characteristic data sheets. The time-saving advantage of this technique is self-evident. A further benefit of this service is that it will enable you to test new transistors as they are released!

Model 88 comes housed in a handsome portable case. Complete with a set of Clip-on Cables for Transistor Testing; an R.F. Diode Probe for R.F. & I.F. Tracing; an Audio Probe for Amplifier Tracing and a Signal Injector Cable. Complete—nothing else to buy! Price is \$38.50. Terms: \$8.50 after 10 day trial then \$6.00 monthly for 5 months.

Try any of the instruments on this or the facing page for 10 days before you buy. If completely satisfied then send down payment and pay balance as indicated on coupon. No interest or Finance Charges Added! If not completely satisfied return unit to us, no explanation necessary.

MOSS ELECTRONIC, INC., Dept. D-865, 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked on approval. If completely satisfied I will pay on the terms specified with no interest or finance charges added. Otherwise, I will return after a 10 day trial positively cancelling all further obligations.

- Model 770-A Total Price \$15.85 \$3.85 within 10 days. Balance \$4.00 monthly for 3 months.
- Model 75 Total Price \$38.50 \$8.50 within 10 days. Balance \$6.00 monthly for 5 months.
- Model 77 Total Price \$42.50 \$12.50 within 10 days. Balance \$6.00 monthly for 5 months.
- Model 80 Total Price \$42.50 \$12.50 within 10 days. Balance \$6.00 monthly for 5 months.

- Model TW-11 Total Price \$47.50 \$11.50 within 10 days. Balance \$6.00 monthly for 6 months.
- Model 83-A Total Price \$38.50 \$8.50 within 10 days. Balance \$6.00 monthly for 5 months.
- Model 70 Total Price \$15.85 \$3.85 within 10 days. Balance \$4.00 monthly for 3 months.
- Model 82-A Total Price \$36.50 \$6.50 within 10 days. Balance \$6.00 monthly for 5 months.

- Model 85 Total Price \$52.50 \$12.50 within 10 days. Balance \$8.00 monthly for 5 months.
- Model TV-50A Total Price \$47.50 \$11.50 within 10 days. Balance \$6.00 monthly for 6 months.
- Model 88 Total Price \$38.50 \$8.50 within 10 days. Balance \$6.00 monthly for 5 months.


Name

Address

City Zone State

All prices net, F.O.B. N.Y.C.

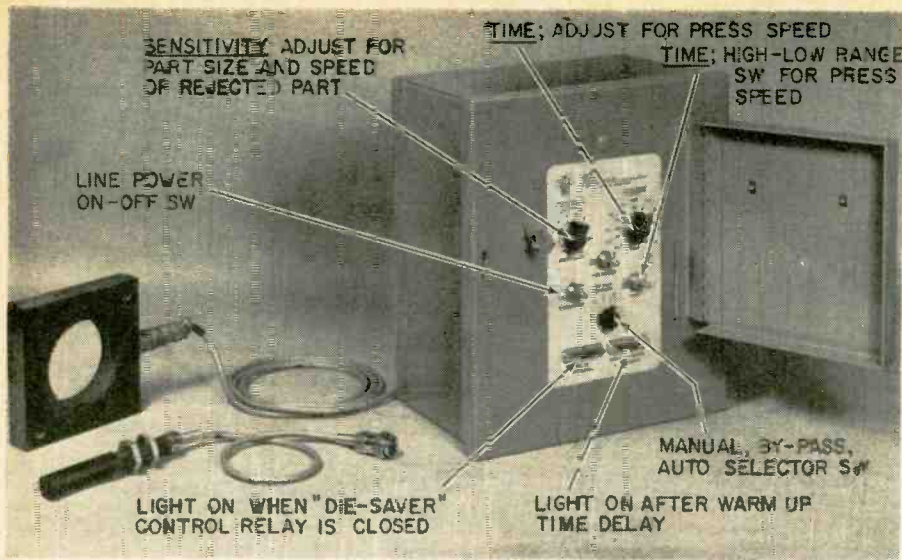Export Division: Roeca International Corp.,
13 East 40th St., New York 16, N. Y.



Robotron die saver with two of the many types of sensing coils.

By DELLROYE D. DARLING*

MOST high-production metal assemblies are made up mainly of die-stamped parts. The dies used to make these parts are very expensive; a set to produce some small item like a hubcap often costs several thousand dollars. Protecting these dies from damage is an important item in the cost of production, and anything that will increase the production rate will help also to reduce the price of the finished product.

A common cause of die damage is the insertion of two or more blanks into the die at the same time. This is called "multiple heading." Clearances between the male and female sections of a die are carefully calculated, and there is no room for more than one blank at a time. When a press is operated at a slow speed by a human operator, he can make sure the stamped part is removed before inserting a fresh blank. At high production rates, though, and especially on automatic presses, there is always a chance of multiple heading.

The rf proximity control offers one good means for checking to make sure the stamped part has been ejected before reloading. The Proximity Die Saver manufactured by the Robotron Corp. is especially designed for the job. When a human operator is running the press, it allows him to work faster without the chance of die damage. With suitable transfer equipment, this control can produce completely automatic production stamping.

One of the chief differences between this die saver and a standard rf proximity device is its ability to sense the movement of a piece of metal, yet be able to ignore large stationary masses of metal at a comparatively close range.


Circuit operation

The heart of this die saver is an electron-coupled rf oscillator, operating at about 300 kc. It is basic theory that a tuned circuit will oscillate when excited by an electrical pulse, but the resistance of the circuit gradually damps the oscillation. The tube in an oscillator circuit makes up for these losses and keeps the tuned circuit oscillating.

Usually, a well-designed oscillator is arranged so the tube is able to make up the losses even when some energy is being taken out of the tuned circuit. For use as a proximity control, the opposite

RADIO-CONTROLLED DIE PROTECTION

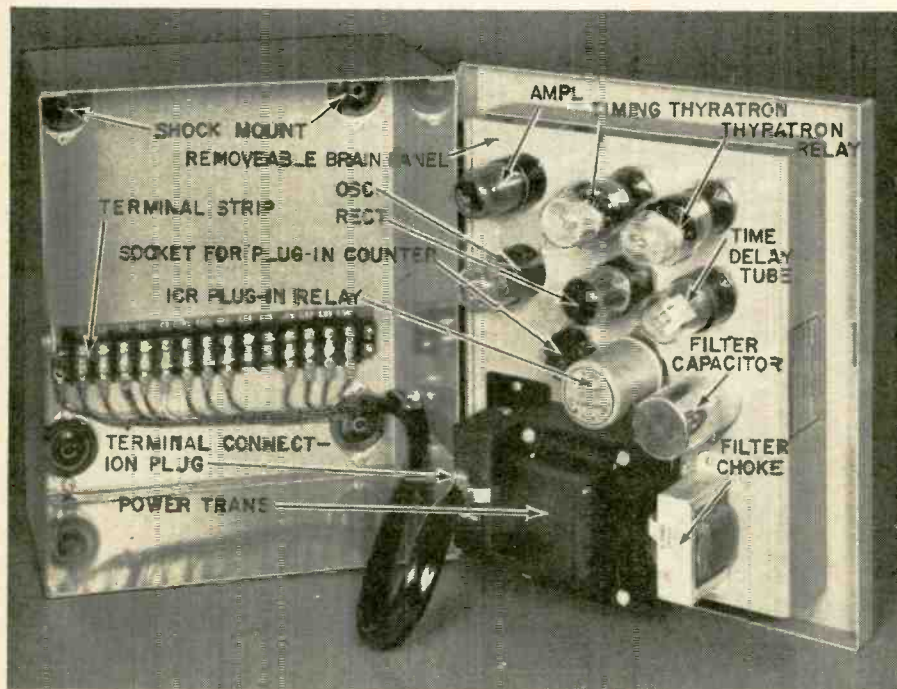Electronics increases production and lowers costs



At look at the components inside the control box.

*Director, Industrial Electronics Radio Electronic Television Schools.

is true. The oscillator is designed to be very weak, and even a small amount of additional loss will stop it altogether. A piece of metal coming close to the coil acts like a shorted secondary, and the oscillator will reduce its output or stop completely. (This is something like the action of some military mine detectors.)

Fig. 1 shows how the pickup coil (detector ring) is mounted on the press so the stamped parts will pass through it as they are ejected from the die.

This control's secret of success lies in the fact that it senses *movement* of a piece of metal near the coil, but ignores the large, stationary mass of the press itself. This is done by using coupling capacitors in the control amplifier so that only a change in oscillator output will trip the control.

The circuit diagram (Fig. 2) shows how the rf output of the oscillator, taken from the cathode, is rectified and used to charge capacitor 9C. Any change in this charge is coupled to the grid of amplifier 1V-a through capacitor 6C. The amplifiers then feed a large positive pulse to the control grid of thyatron 2V, forcing it to fire.

Although 2V has a dc anode supply, it fires only long enough to charge timing capacitors 1C and 13C. When these capacitors are fully charged, the impedance of the anode circuit becomes so high that 2V can't pass enough current to keep firing, so it goes out automatically.

Relay tube 3V has a negative bias on its shield (grid 2), which keeps it blocked. When a positive bias from 2V's anode circuit, it is forced to fire and keeps firing until the charge on 1C and 13C drops to a certain level. This provides a timing action to keep relay 1CR pulled in as long as there is enough charge on the timing capacitors. The contacts of 1CR are in series with the press initiation circuit in such a way that the press can start only when 1CR is energized.

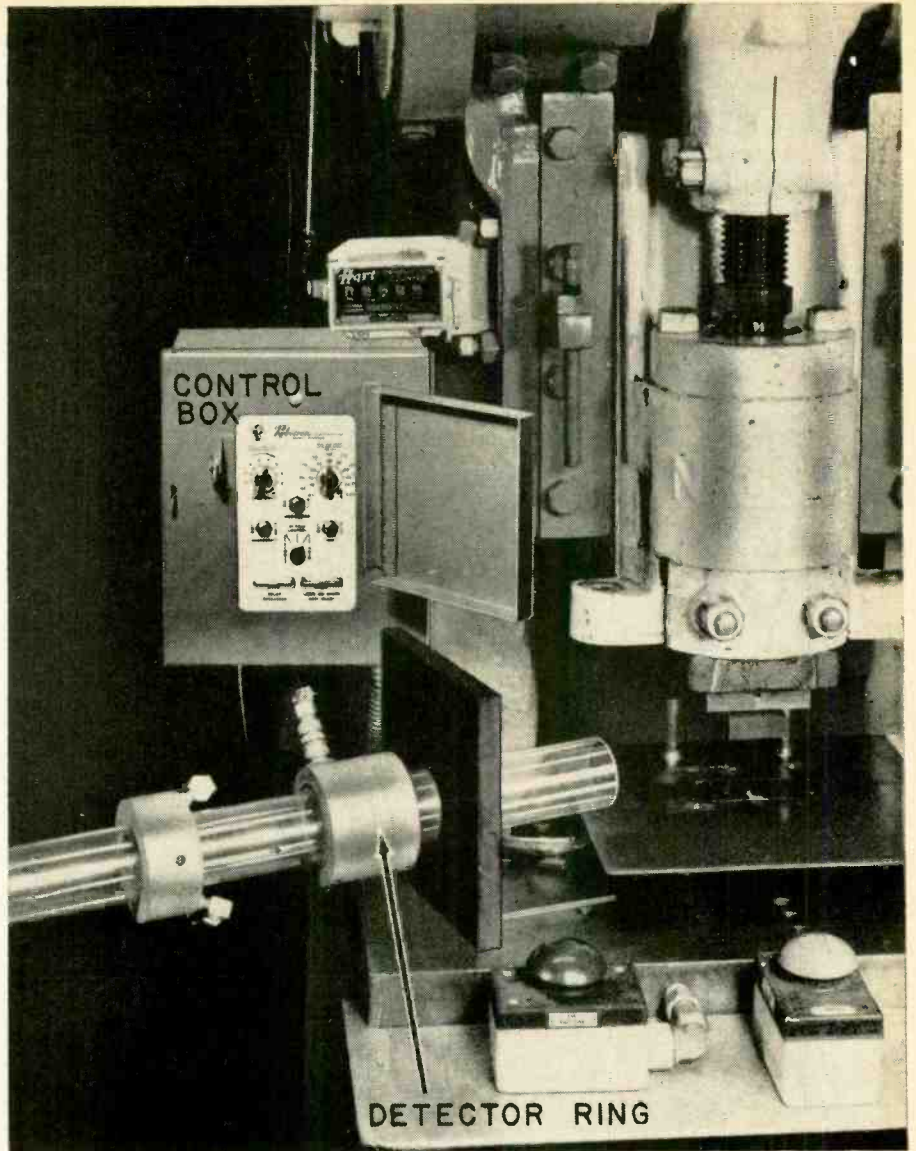


Fig. 1—The die protector set up for use.

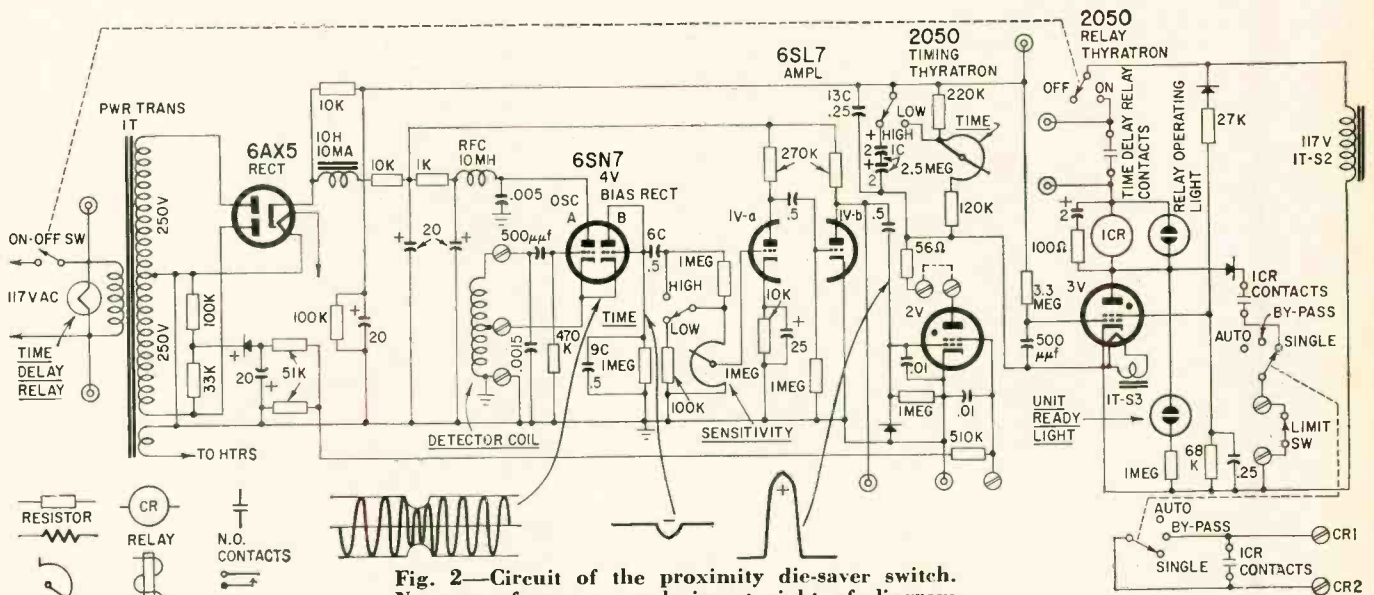


Fig. 2—Circuit of the proximity die-saver switch. Note transformer secondaries at right of diagram marked 1T-S2 and 1T-S3. These are physically parts of 1T but for convenience are shown in another part of the schematic.

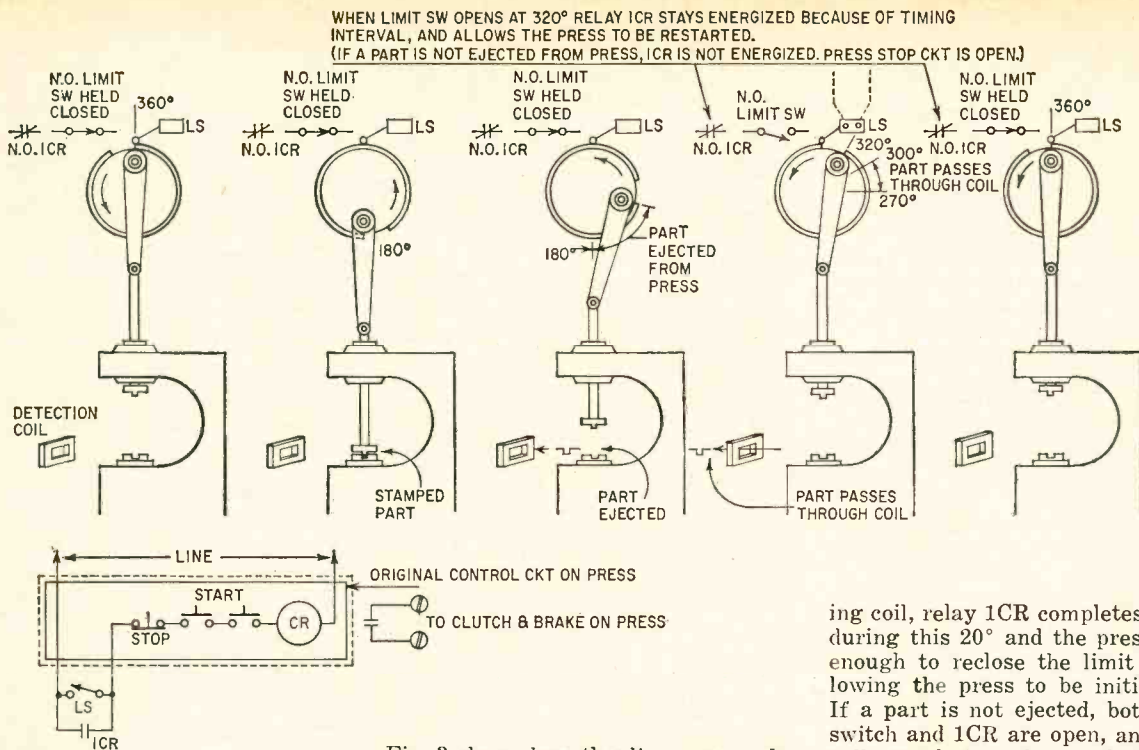



Fig. 3—Typical installation and operating cycle of die saver on a hand-fed press.

Fig. 3 shows how the die saver works in conjunction with the press. The setup shown here as an example is for a hand-fed press with a pin-and-dog clutch and brake.

A limit switch and cam is used to complete the press initiation circuit during all but 20° of press rotation. If a part has been ejected through the sens-

ing coil, relay 1CR completes the circuit during this 20° and the press turns far enough to reclose the limit switch, allowing the press to be initiated again. If a part is not ejected, both the limit switch and 1CR are open, and the press will stop before the revolution is completed. The part must then be removed from the die and the press restarted with a bypass switch on the control unit.

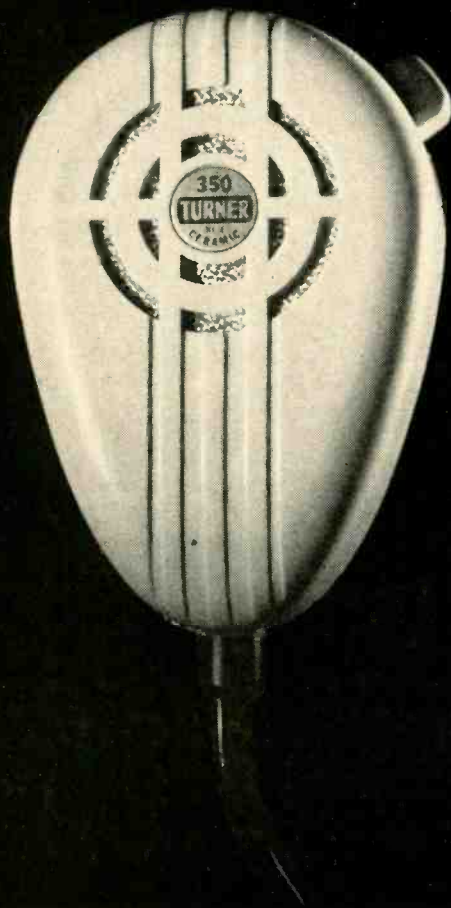Troubleshooting this control is relatively simple, but like anything else, the secret of fixing it is in knowing how it works. END




THIS is the microphone for mobile use

THE TURNER 350C

Good performance on mobile operations — citizen's band, 2-way commercial radio and amateur radio — requires a microphone designed for mobile use. Tape recorder type mikes can't do the job. The Turner 350C is a reasonably priced, ceramic microphone especially designed for quality voice reproduction. DPST switch is wired for relay operation with easily reversible terminals to allow modification (if necessary). A wiring diagram is enclosed with each microphone. Hanger button and standard dash bracket are included for mobile rig mounting. Microphone furnished with 11" retracted (five foot extended) Coiled Kord. Response: 80 to 7000 cps. Output: -54 db. List price: \$16.80 complete. See your electronic parts distributor. He has the Turner 350C in stock.

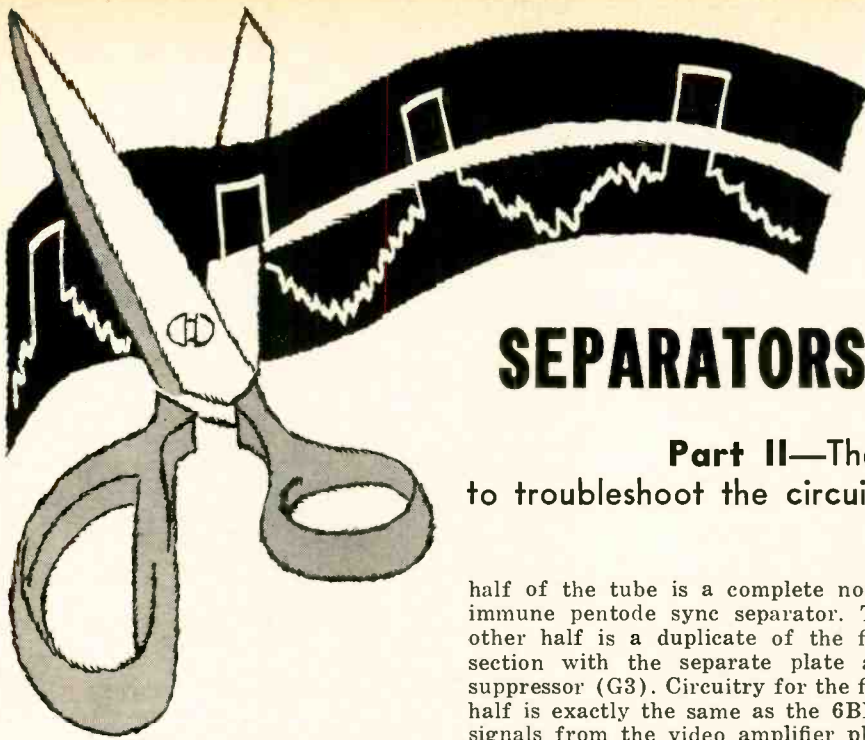THE  MICROPHONE COMPANY
933 17th Street NE
Cedar Rapids, Iowa



SYNC

SEPARATORS AND CLIPPERS

Part II—The 'BU8—how it works and how to troubleshoot the circuits it's used in

By **JACK DARR**
SERVICE EDITOR

LAST time we covered a combination tube with three functions (sync separator, sync clipper and noise gate). Here is another tube that handles these three functions plus a fourth—it provides agc action too! This is the 'BU8 series (3BU8, 6BU8, etc.). For simplicity, we'll refer to it as the 6BU8.

The internal construction of this tube is what makes it unique. Fig. 1 shows the base connections. While it seems to be an ordinary twin-pentode at first glance, a closer look shows that the cathode, screen grid and control grid are common to both sections. There are separate suppressor grids and plates for each section.

Now let's see how it works. Each section of the tube is the equivalent of the dual-control pentodes we discussed last month, and the sync-separator action is exactly the same. So in Fig. 1

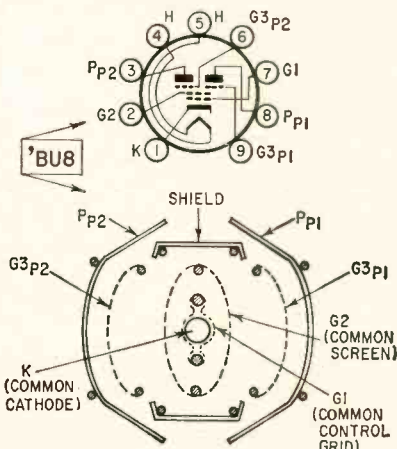


Fig. 1—Basing diagram and physical layout of the 'BU8.

half of the tube is a complete noise-immune pentode sync separator. The other half is a duplicate of the first section with the separate plate and suppressor (G3). Circuitry for the first half is exactly the same as the 6BE6: signals from the video amplifier plate are applied to G3. Since G1 is common to both sections, the signal from the video amplifier grid is fed to both sections. Conduction periods of both sections are the same and the sync is

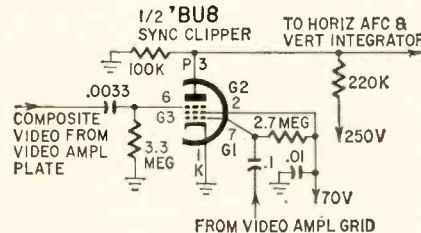


Fig. 2—Sync circuit using the 'BU8.

clipped and amplified and noise is removed (Fig. 2).

The agc

For the extra application—agc—we have a slightly different process. Video amplifier plate signals are applied to G3 (second section) at about 15 volts peak to peak. The tube is so biased that G3 is never driven to zero bias. This level may be set with the agc control.

The set's agc should hold receiver gain at as nearly a constant level as possible. For this reason, we must use some part of the signal with a constant amplitude. Obviously, we cannot use the video signal as this is constantly changing with brightness and contrast levels in the televised scene. So, we fall back on our old friends, the sync tips. They always correspond to 100% of the rf input level. By setting the bias of the agc section of the tube and applying a video signal to the agc section, we can develop a dc voltage which is always proportional to the amplitude of the incoming signal.

As the plate must be about 35 volts positive to conduct at all, it obviously

can't be used directly as an agc voltage source. So we set up a voltage divider (Fig. 3). One end is connected to a source of positive voltage, the other to a source of negative voltage. (In many sets, the negative voltage is obtained from the grid of the horizontal oscillator or horizontal output stages!)

Now, we've about 40 volts positive at one end (the voltage at the plate of the agc tube with zero signal input) and 75 volts negative at the other. High-value resistors are used here to limit current flow.

The tube's plate is connected near the center of the circuit. Here it acts as a sort of variable resistor or a source of variable voltage, whichever way you want to consider it. (If the grid voltage of a vacuum tube is changed, the plate voltage changes correspondingly if the plate load resistance is fixed.) We connect the tuner and video-if agc lines to points along this

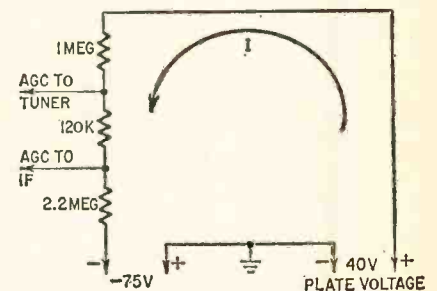


Fig. 3—Agc voltage divider.

voltage divider, so we can apply to them any value of "fixed bias."

If we vary the plate voltage of the tube, we vary the agc bias. If the plate voltage of the tube varies in accordance with average signal strength, we have practical agc action. Assume the tuner and if agc are about 3 and 4 volts negative, respectively. If the signal strength rises, the tube's grid bias goes more positive and the tube conducts more heavily. This lowers the plate voltage, increasing the negative bias on the tuner and if agc (reducing the gain


Pinpoint in Seconds...

HORIZONTAL & VERTICAL SWEEP TROUBLES

NEW

SENCORE

Time Saver

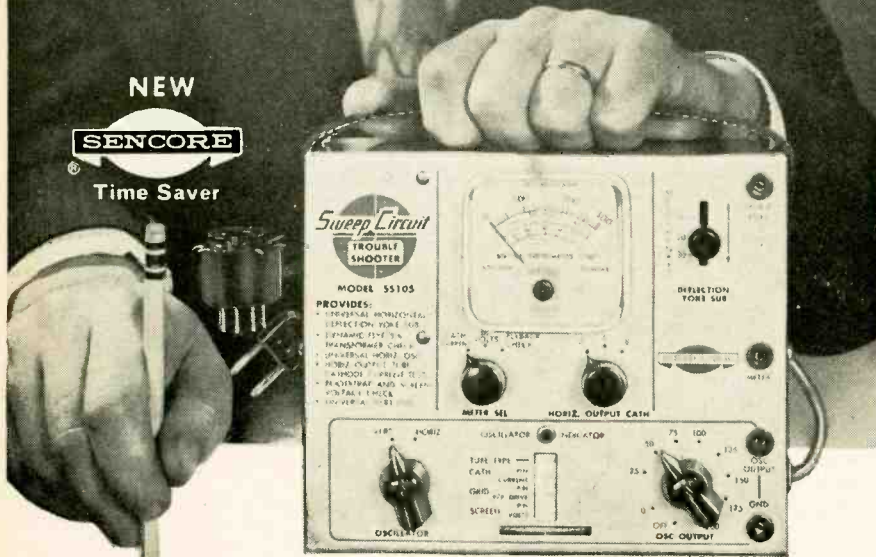

The missing link in TV service ...

SENCORE SS105 SWEEP CIRCUIT TROUBLE SHOOTER



HORIZ. OSC.	VERT. OSC.
HORIZ. O.P. STAGE	VERT. O.P. STAGE
HORIZ. FLYBACK XFORMER	VERT. O.P. XFORMER
HORIZ. DEFLEC. YOKE	VERT. DEFLEC. YOKE

IT'S A ... UNIVERSAL HORIZONTAL OSCILLATOR. For direct substitution. No wires to disconnect in most cases. Traces trouble right down to the defective component. Variable output from 0-200 volts, peak-to-peak. Oscillator will sync to TV sync signal giving check on sync circuits.

HORIZONTAL OUTPUT CATHODE CURRENT CHECKER. A proven method that quickly checks the condition of the horizontal output tube and associated components. Adaptor socket prevents breaking wires. Easily replaceable Roll Chart gives all necessary pin, current and voltage data. New Roll Charts are Free.

UNIVERSAL DEFLECTION YOKE. A new, simple way to determine yoke failure accurately—without removing yoke from picture tube. Merely disconnect one yoke lead and substitute. If high voltage (also bright vertical line) is restored, TV yoke is defective.

DYNAMIC FLYBACK TRANSFORMER CHECKER. Merely flip switch to "Flyback Check" and meter will indicate condition of flyback transformer, in degrees of horizontal deflection. Extremely sensitive and accurate; even shows up one shorted turn on flyback.

VOLTMETER. For testing bootstrap, screen and other voltages. Direct-reading voltmeter, 0-1000 volts.

UNIVERSAL VERTICAL OSCILLATOR. Checks oscillator, output transformer and yoke. Merely touch lead to component and check picture on screen.

SS105 is completely self-contained, nothing else is needed. New Improved Circuit... DEALER NET 42⁹⁵

ALL PARTS

SENCORE

MADE IN AMERICA

SENCORE

ADDISON 2, ILLINOIS

LOOKING? You stand a better chance of finding what you want if you advertise in RADIO-ELECTRONICS classified ads. See details on page 128.

NOW READY!

NEW NRI HOME STUDY COURSE IN ELECTRONICS

- Principles
- Practices
- Maintenance

CASH IN ON THE AGE OF ELECTRONICS. For every graduate engineer, Electronics needs 4 to 7 trained technicians. New, comprehensive NRI course prepares you for high pay, interesting jobs, exciting future. Big demand for trained Electronic technicians. Advance great. Train quickly at home in spare time. Special training equipment included at no extra cost. Write for FREE catalog. National Radio Institute, Dept. ICF, Washington 16, D.C.

A NOTE TO THE HI-FI BUYER
AIR MAIL us your requirements for an IMMEDIATE LOWEST PRICE QUOTATION Components, Tapes and Records SHIPPED PROMPTLY AT LOWEST PRICES
WRITE TODAY FOR FREE CATALOG
AUDIO UNLIMITED 190-R Lexington Ave. New York 16, N. Y.



OUT OF SPACE?

You bet we'd be... if we were to tell you all about AUDION's 'Out of this World Hi-Fi Values'!

Write for free Catalog

audion
25-E Oxford Road
Massapequa, New York

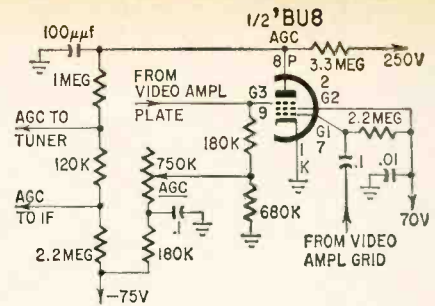


Fig. 4—The 'BU8 agc circuit.

of those stages). The gain is held constant and there's your agc action.

Fig. 4 shows a complete circuit of this agc section used in many sets. In addition to its agc action, the tube has the same immunity to noise that the sync separator has because it is connected in basically the same way. Since the video amplifier grid signal is applied to the common control grid, noise pulses are not only clipped out of the sync, but kept from affecting the agc. Filter component time constants in the agc network are low enough so that the agc bias will not drop during the very small chopped-out portion of the noise pulse.

Servicing sync circuits

Servicing a sync circuit isn't difficult, if you understand what they're supposed to be doing! There is always one good positive symptom of sync trouble: the picture will be *very* unstable, in one or both directions!

It's usually easy to find out which section is causing the trouble. For example, if both horizontal and vertical sync are weak, the trouble would be most likely found in some stage which handles both sync signals: clippers, separators, etc. Of course, the very first step in sync-circuit testing should be tube replacement with *known good* tubes. It is a good idea to check even new tubes before installing them in any sync circuit. Many tubes have been pulled from sync separators and installed in tuners where they performed perfectly, although they would not work at all in the sync section.

Video in the sync will cause the most trouble in horizontal oscillators. Horizontal sync depends more upon the phase than the amplitude of the sync pulse. If the horizontal sync is contaminated by video signals, it will cause pulling of the picture, usually near dark objects. (Dark places are the points where the video signals are strongest.) The trouble is due to erroneous correction voltages developed by the horizontal afc.

Vertical sync performance depends mainly upon pulse amplitude: the sync signals are passed through an integrator circuit and fed to the vertical oscillator in the form of sharp spikes. Weak vertical sync action with good horizontal sync, therefore, points toward trouble somewhere in the sync separator: a weak tube, incorrect operating voltages, etc.

Loss of both horizontal and vertical

sync can also be caused by sync clipping in an overloaded video if stage. This can be checked quickly by adjusting the agc control or, better still, by applying an override bias to the if age line. If the picture straightens up, the trouble is *not* in the sync stages. Gassy if tubes or heater-cathode leakage in age controlled stages can cause this. (For some reason, second video if tubes seem to be the major cause of this trouble.)

'BU8 circuit troubles

A few peculiar troubles turn up in circuits using 'BU8 tubes. They are the result of the slightly unusual circuitry involved. For example, loss of both horizontal and vertical sync would indicate that either the G3 signal was missing in the sync section or that the tube was defective. Unstable sync in the presence of noise would indicate loss of the G1 signal or too low a setting of the noise control.

A white-out (snowless white raster, no picture, usually no sound either) often indicates age trouble. The if amplifiers are blocked if trouble hits the voltage divider. An opened (or increased) 3.3-megohm 'BU8 plate resistor (Fig. 4) would apply -70 volts to the tuner and if age. This would block both stages completely!

If the 2.2-megohm resistor to the -75-volt source should increase or open, the controlled grids would go positive causing a severe overload condition: negative picture or complete picture loss (blank screen). To check this circuit, measure all voltages, especially the two source voltages with a vtvm to see that they are within the tolerance. They will vary from set to set, as do all other voltages, but should agree closely with those shown on the schematic.

Check the high-value resistors in the divider as they must be quite close to their nominal value to prevent troubles. (One unusual trouble was found in this circuit recently: the age voltages were off and the trouble turned out to be lack of drive voltage on the horizontal output tube! This reduced the -75 volts and upset the whole circuit even though there was apparently plenty of brightness. Always check those source voltages!)

One last horrible example before we quit. After much checking of parts in a vertical sync circuit, a pair of the little diodes used in the horizontal phase comparator was unsoldered to check another part. The diodes were found to be badly unbalanced when checked with an ohmmeter "while they were out." These were replaced as a matter of course. Lo and behold, when the set was turned on, the vertical sync trouble was gone! Apparently the leaky diode was shunting the vertical sync signals enough to affect the operation of the vertical sync circuits which depend upon amplitude, remember? Apparently there was sufficient horizontal signal left to operate the phase comparator which depends on phase and not amplitude!



A complete range of capacitors and resistors at your command.


SENCORE HANDY 36 SUBSTITUTION UNIT

Serviceman . . . Engineer . . . Experimentor . . . here's a unit that really saves you time. The Handy 36 provides the 36 most often needed capacitors and resistors for fast, on the spot substitution. The 12 position, 3 wafer switch individually selects one of the 36 components. You simply dial the value you want to the exact or closest reading. Substitution is still the only time tested method for determining whether or not a component is faulty while operating in circuit.

Eliminate time wasted in hunting for parts to use in testing. Say goodby to the soldering mess created by substituting individual components. Put an end to the twisted wires and messy parts you've tossed in parts drawers.

The Handy 36 is simple to use. If a component is suspected of being shorted, open one end and substitute the Handy 36. Or, merely parallel any capacitor or resistor you think is open.

Model H36 DEALER NET 1275

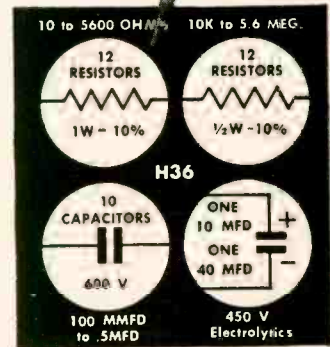

The Handy 36, with new improved circuitry, pays for itself in the first month by saving you those valuable minutes. The parts alone in the H36 would cost you more than the completed unit.

Ask any parts distributor for the "Handy 36", accept no substitute.

ALL PARTS
SENCORE
 MADE IN AMERICA

SENCORE
 ADDISON 2, ILLINOIS

SERVICEMAN'S "CADDY"
20,000 ohms per volt **MULTI TESTER**
FREE LEATHER CASE

Reg. \$39.95 Value
\$16.95 Postpaid

- High sensitivity — 20,000Ω/V
- New design; wide scale arc
- Compares with 4 1/2" meters
- Measures 3 1/4" W x 4 1/2" x 1 1/4"
- Compact black bakelite case

MODEL TS-60H ALCO
 DC V. ranges: 5-25-250-500-2500 @ 20,000Ω per V.
 AC V. ranges: 10-50-100-500-1000 @ 10,000Ω per V.
 DC current: 50 μa, 2.5 ma.

SEND FOR FREE CATALOG
 Send TS-60H Multi-tester — \$16.95 enclosed

Order direct or thru local distributor

ALCO ELECTRONIC PRODUCTS 3 Walcott Ave., Lawrence, Mass.

4" Meter Scales!

the CASE of the missing spot

Introducing a chart that will indicate
what stages to check when your scope is out of order

By PAUL W. KARROL

WHEN Phil (my young ham friend) brought his scope over to my shop for repair, little did I think that I would spend the rest of the morning on it; but that is what happened.

"This scope never gave me any trouble before," Phil began, "but finding the gremlin in it is harder than I thought it would be."

"What are the symptoms?" I asked, while leafing the instruction book to the page with the diagram.

"Well, I've been using it to monitor my final linear amplifier. Right in the middle of a QSO it just stopped operating—no spot—no nothing."

"Did you check the fuse and tubes?"

"Oh, sure," he answered quickly. "I checked most of the voltages too."

"How about point-to-point resistance tests according to the chart in the book?"

"I did some of them, but my ohmmeter only goes up to 100,000 ohms. That's one of the reasons I brought it over here—I know you have proper test instruments."

"How about the tubes? How did you check them?"

"I checked them on my emission checker. Why?"

"Well, I think we had better test them on my dynamic checker. We'll also check out the cathode-ray tube. Let's take the set out of its case now."

Phil carefully removed the scope.

"Before we do anything else, I'll short out all the capacitors in the high-voltage circuits with this long screwdriver," I told him. "You can't tell if one is charged or not—bleeders do open up you know. Whenever you work on a scope or any electronic equipment for that matter, always short out the high-voltage capacitors. When you begin the live test, be doubly careful—4,000 volts or more is nothing to fool with."

"Yeah, I know," Phil smiled. "Even a small charge can bite."

We tested and put back all tubes but one.

"This one is a little weak, Phil," I

said, handing it to him. "I have a replacement, but I'm sure that is not the trouble."

After we had plugged in the new tube, I began to remove the fuse-holder screw.

"I checked the fuse," Phil said, "and it looked OK. In fact, the pilot lit and all the tubes warmed up fine on my last test."

I placed the ohmmeter test prods across the fuse—the needle didn't move. "A fuse may look OK but sometimes it isn't. What were you saying about a 'good' fuse?" I laughed.

"Well, as I said, it was fine about an hour ago. Maybe that's our trouble, huh?"

"I hardly think so," I answered. "Reach into that top bench drawer on your right and give me a 3AG 2-ampere fuse."

Before plugging in the power cord, I turned to Phil.

"Now we'll examine the set very carefully and look for burned resistors or anything else that looks abnormal."

Phil watched closely as I probed various connections and examined all visible parts.

"Everything looks OK," I said, "but that doesn't mean we don't have a bad part or two. So far, we have looked for the simplest causes of trouble first. Now we begin detailed testing."

I examined the power-cord plug connections. "The plug looks in order," I said, plugging it into the nearest receptacle. I turned on the scope.

In a few seconds, all tubes (including the CRT) were glowing.

I turned up the intensity control to

get a spot on the CRT screen—but it remained blank.

"Before we go any further, let's take a look at the scope troubleshooting chart I prepared for one of my radio classes," I said. "It's on the wall above my desk." [See page 94—*Editor*.]

"As you can see, Phil, it is so laid out that all you have to do is to go to the left side, pick out the symptom, then go to the center for the scope section or stage action involved. The right-hand column gives possible causes. For example, let's take your scope's symptoms—no spot on the screen. We find this information on the second and third lines of the chart.


"A number of possible causes are listed in the end column. Let's check the high-voltage supply first. Before we do, let me draw a sketch of the sections we are interested in."

I copied the circuit from the instruction book (see diagram). "There's nothing complicated about this. First, let's check the voltage on both sides of the 470,000-ohm filter resistor."

With my voltmeter set to the proper high scale (and using a voltage-multiplier probe), I measured the voltage on the resistor.

"Looks OK. Now let's check at pin 3

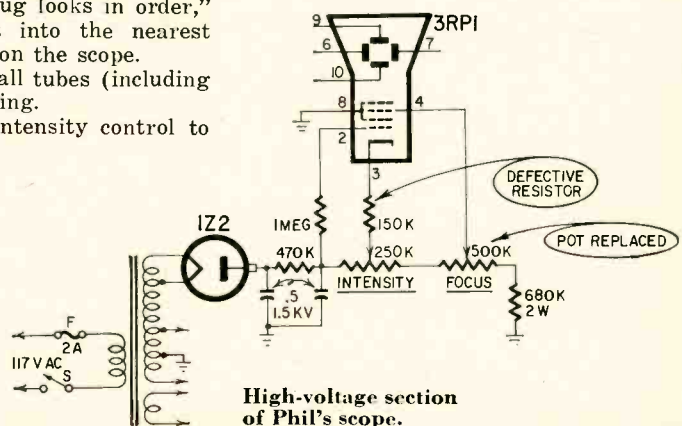(text continued on page 95, chart on page 94)



High-voltage section
of Phil's scope.

NEW

TESTS All TV and Radio Tubes
—both old and new

TESTS the Nuvistors

TESTS the new 10-pin tubes

TESTS the new 12-pin Compactrons

TESTS voltage regulators, thyratrons,
auto radio hybrid tubes,
European hi-fi tubes, and
most industrial types.



Model **600**
DYNA-QUIK

only **\$69⁹⁵**
NET

8½" x 11" x 4½"
Handsome, sturdy
leatherette-covered
carrying case

NEW TUBE
INFORMATION
SERVICE

available every 3
months for all B&K
Dyna-Quik Tube Testers



for the first time, a
B & K QUALITY
TUBE TESTER
at this
amazing low cost!

Checks for all shorts, grid
emission, leakage, and gas

Checks each section of multi-
section tubes separately

Checks tube capability under
simulated load conditions

Rejects bad tubes
—not good tubes

For the man who wants the performance and reliability of a B&K professional-quality tester at minimum cost . . . there's nothing like the new "600". No other tube tester in this price range is so complete and up-to-date. Tests the newest tube types, as well as the old. It's fast . . . it's accurate . . . it's easy to use. Quickly reveals tube condition. Saves customers. Sells more tube replacements. Stops call-backs. Steps up servicing profit . . . day after day. Pays for itself over and over again.

Exclusive adjustable grid emission test. Sensitivity to over 100 megohms. Phosphor bronze socket contacts. Complete tube listing in handy reference index. Extremely compact.

B & K MANUFACTURING CO.
1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.
Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

SCOPE TROUBLE CHART

SYMPTOM	SECTION OR ACTION	TROUBLE SOURCE
No tubes lit	Heater and pilot power supply	Fuse, transformer, line cord or plug
No spot Irregular spot due to CRT hum modulation	Cathode-ray-tube spot	High-voltage supply, open feed resistors, shorted bypass capacitors, horizontal or vertical plate-load resistor open, defective positioning circuits causing beam to go off screen, bad cathode-ray tube Check CRT shield position
No spot or no focus or control	Intensity and focus	Focus or intensity controls, cathode-ray tube, bleeder open, cathode-ray-tube pin contacts, broken leads to cathode-ray tube
No vertical positioning or no amplifier action	Vertical positioning Vertical amplifier	Vertical amplifier tubes, low-voltage supply (including tubes), resistors, coupling and bypass capacitors, position control, attenuator switch
No horizontal positioning or no amplifier action	Horizontal positioning Horizontal amplifier	Horizontal amplifier tubes, low-voltage supply, resistors, coupling and bypass capacitors, position control
No sweep (some or all ranges), no frequency control	Sweep (horizontal amplifier)	Sweep or horizontal amplifier tubes, sweep-circuit switch, capacitors, resistors, low-voltage supply
No sync (drifting patterns)	Sync amplifier and switch	Sync amplifier tubes, switch, resistors, capacitors, low-voltage supply
No intensity modulation	Z-axis amplifier	Z-axis amplifier tubes, resistors, capacitors, low-voltage supply

on the CRT," I suggested.

No reading!

"Hmmm—looks like a bad intensity control," Phil said, his eyes still on the meter.

"Don't be too hasty." I switched the probe to the 250,000-ohm intensity potentiometer.

The meter needle went up the scale.

"I think we've found it," I said, placing the probe first on the pot arm and then at the other end of the resistor connected to it.

No reading again.

I turned the scope off and shorted out the high-voltage capacitors again.

After cutting out the offending part, we checked it on the high-range ohmmeter.

"She's open," Phil said. "But it doesn't look cooked."

I took another 150,000-ohm resistor from the box. "It doesn't have to look cooked to be bad. Remember the worm with an apple wrapped around it?"

"I can see what you mean," he replied with a grin.

After the new resistor had been soldered in place, we again turned on the scope.

As the faint green glow began showing on the CRT, Phil exclaimed, "Boy, it sure is good to see that missing spot again!"

I turned down the intensity control and tried to focus the spot—but there was no action.

"We may have a bad focus pot," I said, reaching for a bottle of contact cleaner.

"Oh, that control has always been a little erratic," Phil declared, reaching for the focus knob and pulling it a little. "See, you have to pull on it to make it work."

I put down the bottle of cleaner. "Seems to me we ought to replace that control. No use having a control that doesn't work properly."

Phil agreed.

As soon as the pot was installed, the scope was again tested and worked beautifully.

I told Phil to put the scope back in the case and then come over to my desk.

"I don't know how to thank you, Paul," he began, "not only for the work on the scope but also for the troubleshooting hints. I'd certainly appreciate a copy of the chart for future reference."

I pulled a mimeographed copy of the chart out of a desk drawer and handed it to him.


"This will help you think, if it does nothing else," I told him. "But, remember, locating the fault is only part of the job. You still have to look for the simplest causes of trouble first and then make resistance and voltage checks according to the book."

Glancing down at the scope by his side, Phil said with a wide grin, "I hope I don't have to bring it back soon—thanks again."

"No, I don't think you will have to," I replied, looking over my shoulder at the chart on the wall and then toward the departing ham." END

ALL AMERICAN MADE! ALL AMERICAN MADE!

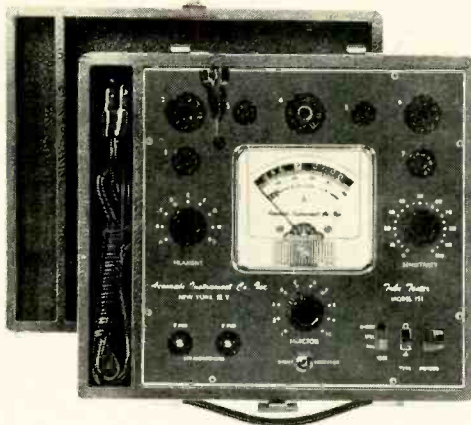ACCURATE INSTRUMENTS' New Model 151 — a Modern, Streamlined TUBE TESTER



Only \$21.95

COMPLETE!

Not a Kit...

The 151 is a completely wired and calibrated tester...

Ready to use!

Don't let the low price mislead you!

The Model 151 was designed and produced with the knowledge that the only way to meet "imported" tester competition is to turn out a better product at a lower price.

Compare the Model 151 features and specifications below with any tube tester, domestic or foreign, in the \$30.00 to \$50.00 price range.

Model 151 Features and Specifications:

- ✓ Tests over 1,000 Tube Types
- ✓ Makes all necessary tests. Checks for shorts and leakages between all elements; tests for filament continuity; indicates the quality (emission) of all tubes.
- ✓ Checks all modern tubes including 7-pin miniatures; octals; lock-in's; 9-pin noval miniatures and new T-9 types.
- ✓ Five (5) Year Free Tube Data.
- ✓ Speedy Operation assured by use of a new improved circuit which enables us to use a single rotary switch in place of the one-at-a-time slide switches previously used.
- ✓ 7 and 9 pin tube straighteners permanently mounted on front panel.
- ✓ Employs a rugged, accurate, highly damped meter movement with sealed air-damping chamber.
- ✓ Comes housed in a beautiful portable carrying case with slip-on cover.

\$21⁹⁵

Model 151 comes complete—
absolutely no extras. Only...

Order direct from Metropolitan Electronics. Shipped C.O.D. or send cash with order. Use the convenient order form at the right.

Metropolitan Electronics
106 Fifth Ave., Dept. RE-3, New York 11, N. Y.

Please send me Model 151 Tube Tester.

\$21.95 enclosed.


Ship C.O.D.

Name _____

Address _____


City _____ Zone _____ State _____

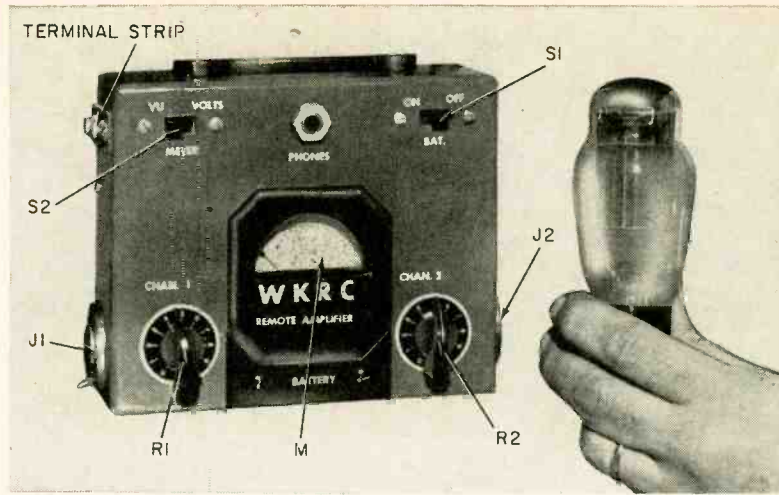Remote Amplifier has Transistor Circuit...



Careful construction gives the remote amplifier a professional appearance.

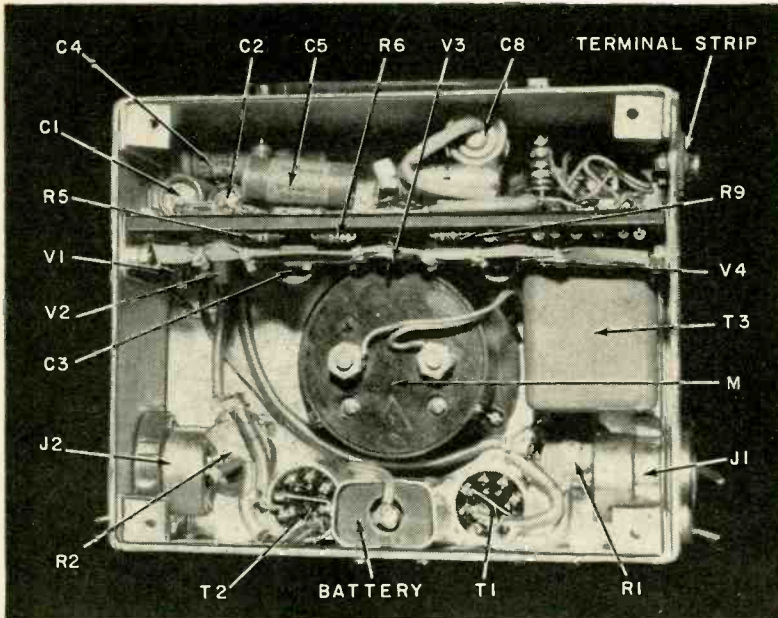2-microphone 4-transistor unit is completely portable and low in cost



By **GEORGE WASLO, WKRC-TV**

REMOTE broadcast amplifiers are important to any radio station, no matter how small or large the station may be.

The usual problems with all these units is their high cost, high battery drain (or dependence on ac line voltage) and bulky size and weight. To get around these problems, I came up with the two-microphone four-transistor unit described in this article.

This transistorized unit does the same job as larger, more expensive commercial units and thanks to the transistors, battery life is much better. The

Rubberband holds transistors in place. V1 and V2 were originally CK727's. As this transistor is no longer available, 2N207-B's are now used.

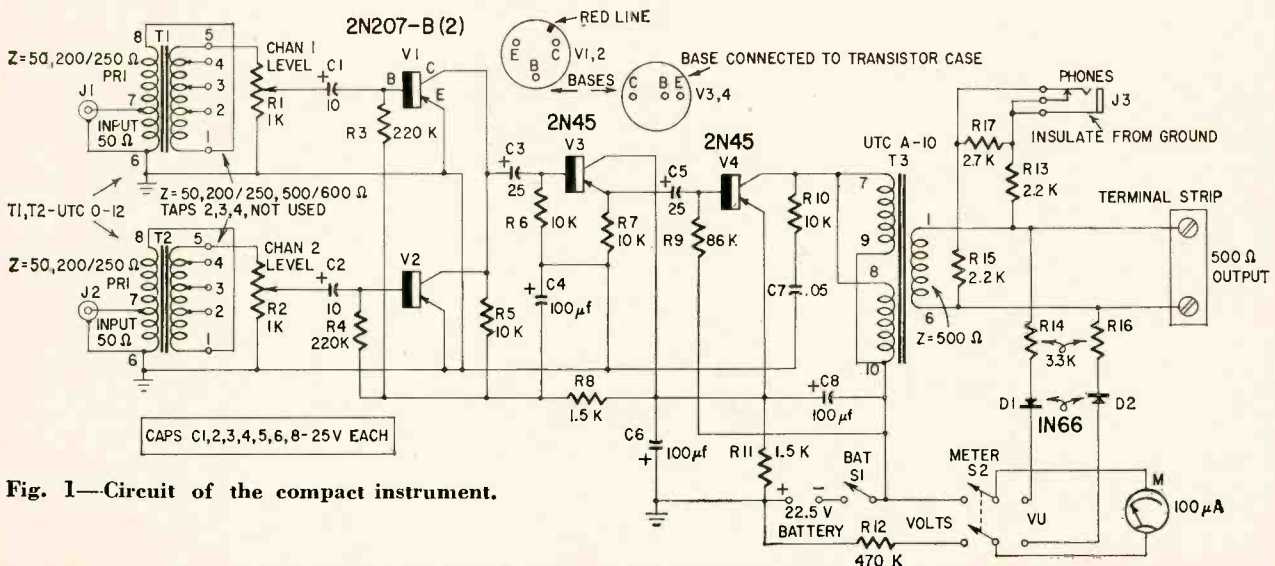


Fig. 1—Circuit of the compact instrument.

unit is still used at WKRC (AM radio), primarily as a standby amplifier at Cincinnati Redlegs home baseball games.

Fig. 1 shows the circuit of the remote pickup. The two input channels are identical. Designed for use with 50-ohm microphones, each one feeds through a matching transformer to the base of a 2N207-B low-level, low-noise, common-emitter amplifier stage. The outputs of these transistors are tied together and R-C-coupled to two medium-power transistor stages. The first, V3, is a common-emitter circuit using a 2N45. V3's output is fed to V4, a common-collector stage. The voltage developed for this stage is used to supply operating potential for the preceding low-level stages. Audio is bypassed and the effective supply impedance for V1 and V2 is lowered by a large shunt capacitor across R11.

The output of V4 is now fed to the primary of an output transformer selected to match the transistor output to a 500-ohm line. Isolation resistors for phones and diode rectifiers are connected to the secondary of this transformer. The meter (0-100 μ a) can be used as an audio-level indicator or to check battery voltage. The function is



Fig. 2—Curve shows excellent frequency response of the portable, low-cost amplifier.

selected with switch S2. The device's frequency response is shown in Fig. 2.

The unit is built into a 5 x 6 x 2 1/2-inch case. Rubber feet are mounted on the bottom and back so it can be used in either position. The battery lasts 25 hours or more (total current drain is only 5 ma). Of course, with a larger battery, life would be longer. The unit was built three years ago and is still in use, a sure indication of its practicality and dependability. END

- R1, 2—pot, 1,000 ohms, audio taper
- R3, 4—220,000 ohms
- R5, 6, 7, 10—10,000 ohms
- R8, 11—1,500 ohms
- R9—86,000 ohms
- R12—470,000 ohms
- R13, 15—2,200 ohms
- R14, 16—3,300 ohms
- R17—2,700 ohms
- All resistors 1/2-watt 10%
- C1, 2—10 μ f, 25 volts, electrolytic
- C3, 5—25 μ f, 25 volts, electrolytic
- C4, 6, 8—100 μ f, 25 volts, electrolytic
- C7—05 μ f
- D1, 2—1N66
- J1, 2—microphone jacks
- J3—phone jack (Switchcraft 12-A, ICA 1871, or equivalent)
- M—0-100- μ a meter
- S1—spst slide
- S2—dpdt slide
- T1, 2—miniature input transformers: primary, 50, 200/250 ohms; secondary, 50, 200/250, 500/600 ohms (UTC 0-12 or equivalent)
- T3—hi-fi audio transformer: primary, 50, 125/150, 200/250, 333, 500/600 ohms; secondary, 50,000 ohms (UTC A-10 or equivalent)
- V1, 2—2N207-B
- V3, 4—2N45
- Battery 22.5 volts (RCA VS084 or equivalent)
- Case, 5 x 6 x 2 1/2 inches
- Sockets, transistor (4)
- Lug terminal strip, screw type (2)
- Miscellaneous hardware

Everything on TRANSISTORS and COMPUTERS You Need To Know To Get Ahead In Electronics

BASIC TRANSISTORS ('Pictured-Text' Course), by Alex Schure, Ph.D. An ideal introduction to the entire field of semiconductors and transistors for the person approaching the transistor for the first time. In order that the reader get full appreciation of the operation and potentialities of transistor circuits, a thorough coverage is made of the characteristics of semiconductor materials, including what they are, how they operate and how they are made. Fundamental operation of a wide variety of transistor circuits in radio and general electronic equipment are analyzed and their actions described. The methods of biasing and coupling in transistor circuits are described. Coverage includes conventional voltage amplifier transistors, the power type, and tetrode units. Specially conceived illustrations make every phase of the subject of transistors completely understandable. #262, soft cover, \$3.95; #262-H, cloth, \$5.50.

SEMICONDUCTORS & TRANSISTORS by Alexander Schure, Ph.D. (25th in Electronic Technology Series). This book is a design oriented text on transistors. It provides the mathematical approach to semiconductors and transistors in the design of circuitry. It discusses and evaluates from the mathematical viewpoint, the theory and characteristics of these materials and devices including fabrication. The mathematical treatment is sufficiently extensive to make absolutely clear the pertinent ideas relating to circuit design. The reader, through presentation and practical situations and problems, is given an opportunity to apply the principles he has learned. Questions and problems are given at the end of each chapter. #166-25, \$2.90.

FUNDAMENTALS OF TRANSISTORS (2nd Ed. revised & enlarged) by Leonard M. Krugman, P.E. Attacks the study of transistors from the viewpoint of transistors and transistor circuit parameters. The book emphasizes theory. It makes theory understandable through mathematical derivations and many numerical examples and solutions. Theoretical operation of various transistor circuits is made clear by step-by-step mathematical analysis. Problems are given at the end of each chapter. A highlight of this book is a very extensive bibliography. #160, \$3.50.

FUNDAMENTALS OF TRANSISTOR PHYSICS by Irving Gottlieb, P.E. A thorough analysis of the action of semiconductors from the physics viewpoint. Semiconductor physics is presented beginning with the theoretical aspects and culminating in the practical transistor and its fundamental circuit. Transistor circuit operations are dealt with only as they amplify the theory. Having reached the fundamental transistor, the author presents analogues to similar fundamental vacuum tube circuits. Related semiconductor devices such as the double base or tetrode transistor, the double-base diode, the unipolar field control transistor, and the silicon control rectifier are covered. Recent developments in transistor physics are discussed including the new tunnel diode. #267, \$3.90.

PRINCIPLES OF TRANSISTOR CIRCUITS by S. W. Amos, B.Sc. Penetrates deeply into the 'why' and 'how' of transistor operation and explains the three basic circuit configurations which form the foundation for all transistor circuits. #241, \$3.90.

BASIC ELECTRONICS VOLUME 6 by Van Valkenburgh, Nooger & Neville, Inc. A companion volume to the existing Rider 5-volume series on Basic Electronics by the same authors. It expands the original 5-volume course into the areas of semiconductors, transistors and frequency modulation, using the 'picture-book' technique. The presentation at the elementary level without using mathematics. #170-6, soft cover, \$2.90; #170-6H, cloth, \$3.95.

BASICS OF ANALOG COMPUTERS ('Pictured-Text' Course) by Thos. D. Truitt (dir. of Advanced Study Group, Electronic Assoc. Inc.) & A. E. Rogers, (senior consultant, Electronic Assoc. Inc.) Anyone having a basic knowledge of electronics engineering will derive great benefit from this remarkable "pictured-text" course on analog computers. If you are an engineer, you will be made familiar with the analog computer—its suitability for your design needs—and the programming requirements. If you are a teacher in a college or a technical institute, you will find this an effective course. If you are a computer maintenance technician, you can gain a familiarity with this important computing technology. If you are an engineering college student, you can easily acquire a thorough understanding of the analog computer. More than 400 illustrations reinforce the ideas discussed in the text. Beginning with the simple ideas of analog devices, the book slowly introduces the mathematical concepts involved, explains in detail the workings of modern general-purpose electronic analog computers and rounds out the course with practical applications. #256-H, 3 vols. in one cloth binding, \$12.50.

BASICS OF DIGITAL COMPUTERS ('Pictured-Text' Course) by John S. Murphy. This widely acclaimed text has proven itself to be the finest available at the basic level. Provides basic theory of computer arithmetic, circuitry, logical building blocks and memory. Vol. I provides the background; Vol. II introduces the basic building blocks of logical systems; Vol. III discusses the operation of the digital computer. #196, 3 vols., soft covers, \$8.40; #196-H, all 3 vols. in one cloth binding, \$9.50.

DESIGN OF TRANSISTORIZED CIRCUITS FOR DIGITAL COMPUTERS by Abraham I. Pressman, M.S. This book has been acclaimed by engineers for its improved miniaturized circuit design for digital computers. Using "worst case" design, this book explains how switching time and drive capabilities and requirements of all the essential digital computer building blocks may be calculated, and how these blocks may be assembled in chains to perform computer-type logical operations. "Worst case" design assures successful operation under all conditions! It saves maintenance time! The author provides practical design problems that work! #215, cloth, \$9.95.

These and many other Rider titles are available at bookstores, electronic parts distributors, dept. stores or direct. Send for new catalog. Dept. RE-3

JOHN F. RIDER PUBLISHER, INC., 116 West 14th Street, New York 11, N. Y.
Canada: Chas. W. Pointon, Ltd., 66 Racine Rd., Rexdale, Ont.
Export: Acme Code Company, Inc., 630 9th Ave., N. Y. C.

LOWEST PRICED ELECTRONIC ASSORTMENTS IN AMERICA!

RADIO-TV PARTS BY THE POUND IN NEW ... JUMBO PAKS!

SPECIAL TRUCK-LOADS of manufacturers' over-runs at a fraction of their original cost!	ONE POUND PRECISION RESISTORS WORTH \$100	ONE POUND DISC CONDENSERS WORTH \$50	ONE POUND CERAMIC CONDENSERS WORTH \$85	<div style="font-size: 2em; font-weight: bold;">\$3⁰⁰</div> per pound
	ONE POUND DISCS & CERAMICS WORTH \$75	ONE POUND DISCS, CERAMICS PRECISIONS WORTH \$70	BUY 4 GET THE 5TH PAK FREE!	

Clip out & mail
Average count 400-1000 pcs per pak

FREE GIANT BARGAIN CATALOG WRITE FOR YOURS!

HOW TO ORDER: Include check or M.O. with sufficient postage; excess returned. C.O.D. orders, 25% down; rest, net 30 days. INCLUDE POSTAL ZONE in address.

LEKTRON

241 Everett Ave.
CHELSEA 50, MASS.

BECOME A RADIO TECHNICIAN
for only \$15.95 up

BUILD 10-25 RADIO

CIRCUITS AT HOME

with the New Progressive

RADIO "EDU-KIT"®

All Guaranteed to Work!

PRACTICAL only
HOME RADIO COURSE **\$15.95** UP

NOW INCLUDES

- ★ RECEIVERS
- ★ TRANSMITTERS
- ★ SQ. WAVE GENERATOR
- ★ AMPLIFIER
- ★ SIGNAL TRACER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR



TRAINING ELECTRONICS
TECHNICIANS SINCE 1946

- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools needed
- ★ Excellent Background for TV
- ★ School Inquiries Invited
- ★ Attractively Gift Packed

FREE EXTRAS

- SET OF TOOLS ● RADIO & ELECTRONICS TESTER ● ELECTRIC SOLDERING IRON ● TESTER INSTRUCTION MANUAL ● MEMBERSHIP IN RADIO-TV CLUB; CONSULTATION SERVICE ● HI-FI GUIDE ● QUIZZES ● TV BOOK ● FCC AMATEUR LICENSE TRAINING ● RADIO BOOK ● PRINTED CIRCUITRY ● PLIERS-CUTTERS ● ALIGNMENT TOOL ● WRENCH SET ● CERTIFICATE OF MERIT ● VALUABLE DISCOUNT CARD

WHAT THE "EDU-KIT" OFFERS YOU

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction, servicing, basic Hi-Fi and TV repairs, code, FCC amateur license requirements.

You will learn how to identify radio symbols, how to read and interpret schematics, how to mount and lay out radio parts, how to wire and solder, how to operate electronic equipment, how to build radios. Today it is no longer necessary to spend hundreds of dollars for a radio course. You will receive a basic education in radio, worth many times the small price you pay.

THE KIT FOR EVERYONE

The Progressive Radio "Edu-Kit" was specifically prepared for any person who has a desire to learn Radio. The "Edu-Kit" has been used successfully by young and old in all parts of the world, by many Radio Schools and Clubs in this country and abroad. It is used for training and rehabilitation of Armed Forces Personnel and Veterans throughout the world.

The Progressive Radio "Edu-Kit" requires no instructor. All instructions are included. Every step is explained. You cannot make a mistake.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore, you will construct radio circuits, perform jobs and conduct experiments to illustrate the principles which you learn.

You begin by examining the various radio parts included in the "Edu-Kit." You then learn the function of these parts. Then you build a simple radio. With this first set, you will enjoy listening to regular broadcast stations, learn theory, practice testing and troubleshooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are Receiver, Transmitter, Code Oscillator, Signal Tracer, Signal Injector, Square Wave Generator and Amplifier circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

In order to provide a thorough, well-integrated and easily-learned radio course, the "Edu-Kit" includes practical work as well as theory; troubleshooting in addition to construction; training for all, whether your purpose in learning radio be for hobby, business or job; professionally-arranged material, ranging from simple circuits to well-advanced topics in Hi-Fi and TV. Your studies will be further aided by Quiz materials and our well-known FREE Consultation Service.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build several different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, hookup wire, solder, selenium rectifiers, volume controls, switches, knobs, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio & Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to the F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, and a High Fidelity Guide and Quiz Book. Everything is yours to keep.

Statistics, of 25 Popular Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend \$240 for a course, but I found your ad and sent for your Kit."

CHOOSE FROM THESE POPULAR "EDU-KIT" MODELS

- 10A: 10 Circuits \$15.95
- 15A: 15 Circuits \$19.95
- 16A: 16 Circuits (Includes Printed Circuitry) \$22.95
- 20A: 20 Circuits (Includes Printed Circuitry and 4 Advanced Circuits) \$26.95
- 25A: 25 Circuits (includes Printed Circuitry and 9 Advanced Circuits) \$30.95

UNCONDITIONAL MONEY-BACK GUARANTEE

Please RUSH my Progressive Radio "Edu-Kit" to me. BE SURE TO INCLUDE all the FREE EXTRAS and BONUS RESISTOR and CONDENSER KITS WORTH \$7.00.

MODEL desired..... Price.....

Send "Edu-Kit" postpaid. I enclose remittance in full.

Send "Edu-Kit" C.O.D. I will pay postage.


Send me FREE additional information describing "Edu-Kits."

Name.....

Address.....

Progressive "EDU-KITS" Inc.

1186 Broadway, Dept. 174G
Hewlett, N. Y.

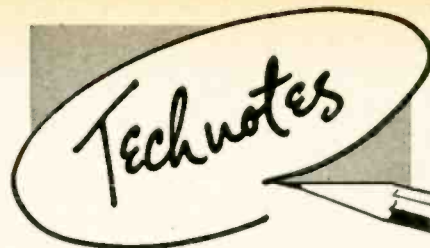


HIGH-VOLTAGE HINT

An interesting troubleshooting procedure is possible when you have high-voltage troubles in sets using the 3A3. Quite often, when trouble develops in the horizontal sweep system, there will still be some sweep energy, but not enough to light the filament of the 3A3. By substituting a 1B3 you can frequently get light on the screen. This will help you identify the circuit fault. For instance, when a yoke shorts, there may be no light on the screen but, by substituting the 1B3 for the 3A3, the familiar keystone raster can be seen and the trouble diagnosed.—Wayne Lemons

ZENITH 23H22

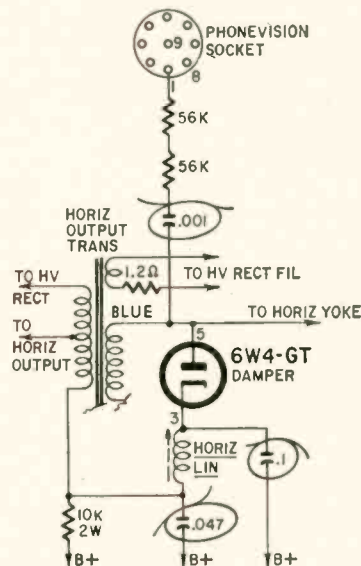Complaints of horizontal wiggle and loss of horizontal sync have been caused by a leaky .001- μ f capacitor connected between the blue lead of the horizontal output transformer and two 56,000-ohm resistors that go to pin 1 of the Phonevision socket. Also check the 0.1- μ f and .047- μ f capacitors off the damper cathode for leakage or arcing. Replace with 600-volt units if bad.



Piecrust oscillations giving a watery picture after the set has warmed up can be cured by lowering the setting of the horizontal grid drive and adjusting the horizontal linearity coil. For stubborn cases, insert a 47-ohm 1-watt resistor in the plate and cathode leads of the 6W4.

Poor width and low voltage or no raster at all can be caused by a decrease in value or an open in the 10,000-ohm 2-watt carbon resistor connected from B-plus to the horizontal output transformer primary and horizontal linearity coil. Replace this resistor with a 4-watt unit.—George P. Oberto

CRT CHECKER

Obtain a 90-550-volt neon test lamp. Solder two 12-inch lengths of No. 2, rubber-covered wire to the neon-lamp wires. Tape the soldered connections carefully. Bare the free ends of No. 2 wire and solder heavy-duty alligator clips to one of them. On the other one, build up solder on it and file into a test-probe point. Now wrap many layers of electrician's rubber tape above the clip and fashioned point. This protects you against shock and it also acts as a convenient hand grip.

To use this neon lamp to test for brightness and contrast on a picture tube, proceed as follows: Clip one end lead to the TV chassis. Turn the set on and touch the other probe to the control grid of the picture tube (generally pin 2 of the 12-pin socket). Now, turn the brightness control. If everything is normal, the neon-light brightness should vary with the setting of the brightness control. To test the contrast control, do the same, only this time touch the probe to pin 11 of the picture tube, the cathode. For another test connect the lamp between pins 2 and 11. Turn the set on, rotate both contrast and brightness controls. Either control should vary the neon-lamp brightness. If this is so, everything is OK in the contrast and brightness circuits.—*A. von Zook*

MOTOROLA TS53

The complaint was too frequent replacement of the 1B3. The tube would have an open filament each time it went bad. I found that the filament winding of the flyback transformer had two turns around the core. I had believed that once around the core was standard practice. Since the 1B3 filament seemed to burn rather brightly, I removed one turn and eliminated the existing 3.3-ohm resistor. Now the filament glowed normally. The lighter load on the flyback increased horizontal sweep and high-voltage too.—*Charles Andrews*

LAB SCOPE ACTS UP


We were called to troubleshoot a \$3,000 lab scope—its horizontal sweep refused to work. The operator had already replaced tubes to no avail. This scope was a trigger-sweep instrument with a calibrated sweep circuit. The spot rested contentedly at the left-hand edge of the screen and refused to move horizontally, although there was plenty of vertical deflection when signal was applied to the scope.

The first question that came to mind was whether the electronic trigger was working or a defect in the preamp was keeping the trigger circuit from working. So we took a conventional service scope with low-capacitance probe and checked the output of the trigger circuit. Each time the operator applied an input signal, the trigger circuit kicked. Evidently, the trouble was between the trigger and the CRT. So we proceeded to trace the trigger signal down to the sweep circuit (sawtooth maker).

Following the signal down a harness and into a printed-wiring board, we lost the signal upon entering the board. The sawtooth maker was dead. When we checked the connection of the harness conductor to the printed board, the trouble was apparent. The insulation had been carelessly removed from the conductor and the lead had been cut almost in two. It took only normal vibration and jarring of the instrument to open the connection.

We cleaned the terminal, skinned the end of the conductor properly and soldered it in place. Now we were back in business and the beam swept horizontally as it was supposed to.

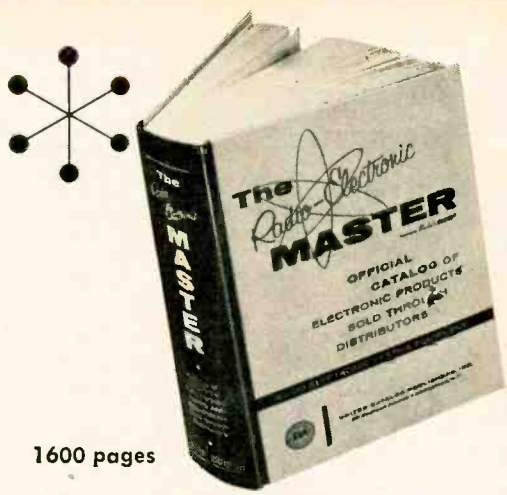This was an interesting job, because this is the last kind of trouble that you expect to find in very expensive test equipment.—*Robert G. Middleton* END



1600 pages



- ✱ **IT'S NEW.** Covers all the latest products: • miniature and sub-miniature components • printed circuit components • silicon rectifiers • new transistor types • citizens band, SSB and new mobile ham gear • microwave and telemetering components and equipment • stereo equipment... every new electronic product for servicing, experimenting, design, industrial and military applications.
- ✱ **IT'S THE WORLD'S BIGGEST ELECTRONIC CATALOG.** 1600 pages—more than 175,000 items—with specifications, illustrations and prices. Contains hundreds of items not found in smaller catalogs.
- ✱ **IT'S THE EASIEST TO USE.** Quickest way to get current catalog data on the products of more than 330 manufacturers. Systematically organized in 32 product sections for rapid reference.
- ✱ **IT'S INDISPENSABLE TO SERVICE MEN, ENGINEERS, HOBBYISTS.** If you're a service technician, The MASTER means more profitable operation because it covers all items necessary for radio, TV, audio and industrial servicing. If you're an engineer or buyer, you'll save design and purchasing time. If you're a ham, hobbyist or experimenter, you'll get the right product to do the job best, because you're shopping in the electronic supermarket.

AND IT'S NOW AVAILABLE AT
YOUR LOCAL DISTRIBUTOR

1961 MASTER

\$3.95 at parts distributors
\$4.95 in Canada

FREE from your distributor: New Foreign Tube Interchangeability Guide, or write direct, enclosing 25c.

RADIO-ELECTRONIC MASTER — 60 MADISON AVE., HEMPSTEAD, N. Y.

"My Photofact Library is the most important tool in my daily servicing. With my Photofacts I am able to complete a job in just half the time it would take without them . . . Membership in the PEET program is the best thing that could happen to any Electronic Technician. I believe I speak from experience as this is my 19th year of full-time servicing."

—A. Kish, Jr.
Al's Radio & Television
Carteret, N. J.



Service Technicians! YOU EARN MORE... YOU RATE with the public when you own the PHOTOFACT® service data library!

You enjoy maximum earnings as the owner of a complete PHOTOFACT Service Data Library! It's inevitable, because no matter how expert you are, you can always *save more time on any job, get more jobs done daily*—EARN MORE, DAY IN AND DAY OUT...

What's more—as the owner of a complete PHOTOFACT Library, you know your customers' sets *best*. You can actually show each customer you have the PHOTOFACT Folder covering his very own set. Result: You command public respect and acceptance which paves the way to more business and earnings for you.

HOW TO STAY AHEAD...

Yes, the truly successful Service Technicians are those who own the complete PHOTOFACT Library, who can meet and solve any repair problem—faster and more profitably. And these men *keep ahead* because they're on a Standing Order Subscription with their Distributors to receive all new PHOTOFACTS as they are released monthly. (They're eligible for the benefits of membership in PEET, too—see below!)

ONLY \$10 DOWN puts the complete PHOTOFACT Library in your shop—and you have up to 30 months to pay. See your Sams Distributor today, or write to Howard W. Sams

NOW IS THE TIME TO JOIN

"PEET"

THE POWERFUL NEW PROGRAM FOR QUALIFIED TECHNICIANS

If you now own a PHOTOFACT Library or plan to own one, you can apply for membership in "PEET." It's the first industry program really designed to build powerful public acceptance for the Service Technician who qualifies. Builds enviable prestige and business for its members. Benefits cost you absolutely nothing if you qualify. Ask your Sams Distributor for the "PEET" details, or mail coupon today.

HOWARD W. SAMS & CO., INC.
1726 E. 38th St., Indianapolis 6, Ind.

- Send me full details on the new "PEET" Program.
- Send full information on the Easy-Buy Plan and Free File Cabinet deal.
- I'm interested in a Standing Order Subscription.
 - I'm a Service Technician full-time; part-time

My distributor is _____

Shop Name _____

Attn: _____

Address _____

City _____ Zone _____ State _____

TECHNICIANS'

NEWS



TV SERVICE LICENSE IN D.C.?

The District of Columbia Business Licensing Committee is pushing a move to introduce legislation in the next session of Congress to require licensing of local TV shops. This would affect only shops in the District of Columbia and is not intended as a nation-wide licensing law.

Tests run by the committee from time to time have indicated that some TV shops have made unreasonable charges for repairs.

FRAUD IN CALIFORNIA

Los Angeles, Calif.—Two local TV technicians, Herman and Oscar Singer, were arrested on charges of petty theft. They were called to repair sets placed in the homes of policemen. Each set had either one bad tube or one bad capacitor with an anticipated repair cost of about \$2 plus labor.

Three sets were repaired. The bills ran \$41.46, \$41.76 and \$42. Police also reported that five new tubes in one of the sets had been replaced with used ones. Another unfortunate black eye for the honest service technician.

The California State Electronics Association supports the fight against fraud. The association's president, Robert Whitmore has stated, according to *Home Furnishings Daily*, "Public exposure of the sundowners provides strong support for our campaign for state licensing of TV technicians.

"Actually, the sundowners represent only a small fraction of our industry, but account for more than \$60,000,000 of the \$168,000,000 total volume of TV service in this state. However, this small group has continually blackened the public image of TV technicians, causing serious problems for conventional operators."

WARNA-GRAM

Alameda County, Calif.—This technique is used by the Alameda County TV & Radio Association to give its members immediate notice of crooked operators preying on their business:

This setup informs members at once of bad or fraudulent checks, stopped checks for service payment, fake or questionable "charity" solicitations, thefts and burglaries, questionable or worthless advertising promotions, just plain gyps of any kind.

The plan is simple. A member, say, has a check for service "stopped." He immediately phones ACTRA executive secretary Phil Fisher, detailing the situation. Five key members are imme-

diately called. Each of these phones the two members on his list; each of the latter passes the word to two more, and so on.

It has been checked out, and the entire membership can be covered in half an hour.

If any dealer doesn't answer the call, the dealer responsible is urged to call again later in the afternoon or earlier the next morning, or at noon when most one-man shop owners are in. If a break in the chain shows up, Phil is phoned at once. He bypasses the break, calling lower in the chain to keep the warning moving.

ESFETA-PROPOSED LICENSE BILL

At a recent meeting of the Empire State Federation of Electronic Technician Associations, the proposed New York State license bill was reviewed with legal counsel.

Important extracts from the proposed bill are:

Any TV technician now engaged in television repair work will be eligible for a license under the "Grandfather Clause" (necessary on all new license legislation).

Tube changers, those who know nothing about circuit repairs, will not be eligible for a license.

No part-timer will be denied a license, provided he is qualified. (This will help good part-timers to become good full-timers.)

The license board will be composed of seven members: four licensed technicians (from different geographical areas of the state); one service manager for a manufacturer of TV receivers; one electronics teacher appointed by the State Board of Education; and one individual who shall have had no previous and no present interest in the television service industry, to be representative of the consumer.

The license board will protect the public from unscrupulous service shops and will protect the TV technician from unscrupulous customers.

In addition, once the license bill is in effect, courses of instruction will be set up which will allow licensed technicians to take voluntary courses to keep them up to date with technical advances in the field. It will also allow apprentices to get first-class schooling instead of the present "90-day wonder" courses.

ASSOCIATION PROTECTS SET OWNER

Fort Worth, Tex.—The local branch of the Texas Service Association gives its members a solid backing and protects its members' customers at the same time.

If a customer has a complaint, he sends it to association headquarters. It is then referred to a committee to investigate immediately. If the complaint is justified, it is settled to the customer's satisfaction and the service shop that did the original work is billed for the cost. If the bill is refused,

the firm is dropped from the association, and the Texas Electronics Association of Fort Worth assumes the cost.

During the 3 years the plan has been in operation, only one member has been dropped.

PHILCO LABOR WARRANTY

The new line of Philco TV receivers will carry a 90-day warranty that covers labor as well as parts. The customer must bring the set to the shop.

Servicing will be handled by some 30,000 independent Philco service technicians, dealers with qualified service shops and technicians who repair sets for non-servicing retailers, according to Henry T. Paiste, Philco consumer relations and service director.

There is a certain cost to the customer, although it is included in the price of the TV set. The new sets cost between \$1.75 and \$4 more than before.

ARTS OFFICERS FOR '61

St. Joseph Valley, Ind.—The Association of Radio & Television Service of St. Joseph Valley elected the following officers for 1961:

President: Cas Molenda, Avenue Radio Shop. First vice president: Ed Barant, Marquette TV-Radio. Second vice president: Harold Rhodes, The Electric Co. Secretary: Jack Cook, Electronic Service Co. Treasurer: Dick Tepe, Tepe Television Service. Sergeant at Arms: Dan Walker, Walker's TV & Radio Service. Chairman of the board: Buss Bills of Bills' TV Service.

CABLE SYSTEM DEFEATED

Lompoc, Calif.—A vote of the people of Lompoc defeated an attempt by Cablevision to get a franchise for their cable TV system in that area, reports the *CSEA Countdown*. The decision was 3 to 2 against the franchise. *Countdown* says that "as a service group we are not against cables, if an area cannot be served by free TV; but where a promotion to capture an audience with only promises is offered then we must, for the preservation of independent service, fight with all the facilities we have at our disposal."

TESA SPRINGFIELD MEETS

Springfield, Ohio—At a recent meeting held at the local Credit Bureau, Mr. James Merrill spoke on effective credit management. Methods of gathering and filing credit information were described. A question-and-answer period followed. END

HAM "AUCTION-FEST"

Broward Amateur Radio Club is holding its fifth annual Auction-fest March 11, 1961 in Fort Lauderdale, Fla., at the Armory, SW 4th Ave. and 24th St. Doors open 8 am; auctioning from 10 am to 5 pm, with a lunch break at noon. Attendance has placed this event as tops in Florida ham radio auctions.

IMPORTANT NEW SAMS BOOKS

BECOME A COMMUNICATIONS EXPERT!

Second-Class Radiotelephone License Handbook

by Edward M. Noll



You must have a second-class radiotelephone license to repair (and in some cases to operate) various communications equipment, including two-way mobile radio. Here's all the information you need to pass the 2nd class exam, and to successfully maintain and operate 2-way and other communications units on the job. 6 chapters contain questions and answers based on the FCC exam. 6 more chapters of text give you the thorough background and full knowledge of communications theory and practices you will need. Gives vital data on fundamental systems, rules and regulations, operating practices and procedures, communications test equipment, transmitter tuning and adjustment, etc. Elements I, II, and III of the 2nd class exam are explored in detail. Extensive Appendix provides much useful reference data. 240 pages; 5½" x 8½". Only **\$3.95**

HELPS YOU SOLVE THE "TOUGH DOGS"!

Radio and TV Trouble Clues



A collection of unusual "tough dog" troubles, based on actual field experiences with specific radio and TV receivers. Compiled by the Sams engineering staff from material featured in the "Quicker Fixing" column of *PF REPORTER* magazine, the book shows you in detail how to avoid time-consuming errors. Three sections cover troubles in TV and radio receivers, plus "oddball" problems; illustrated with dozens of photographs and schematics of the set or circuits being analyzed. Here's a guide that will help you get those "tough dogs" off your bench faster and easier. 96 pages; 5½" x 8½". Only **\$1.50**

NEW Tube Substitution Handbook

NEW VOL. 2. Revised to include over 4,450 direct substitutions. Lists 1,644 receiving tubes with over 2,500 substitutions; shows 186 Industrial and 494 European substitutes for American receiving tubes; 453 American receiving tube substitutes for European types, with 725 direct substitutions. 17% more substitutions than in previous volume! Handy 5½" x 8½" size. Only **\$1.50**



1960-1961 TV Circuit Handbook



Shows you what's new in TV circuits for 1960-61. Describes circuits of all major manufacturers, from remote tuner controls to picture tubes, including color TV. The best "briefing" you can get on the new, unfamiliar TV circuits. **\$3.95** 136 pages; 8½" x 11". Only **\$3.95**

HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. C-21 1720 E. 38th St., Indianapolis 6, Ind.

- Send me the following books:
- Second-Class Radiotel. License Hdbk. (QAN-1)
 - Radio and TV Trouble Clues (RTQ-1)
 - Tube Substitution Handbook, Vol. 2 (TUB-2)
 - 1960-1961 TV Circuit Handbook (CHM-1)
- \$.....enclosed. Send Free Book List

Name _____
 Address _____
 City _____ Zone _____ State _____

..... (Outside U.S.A. priced slightly higher)

A CREI college-level extension program in advanced electronic engineering technology that offers you ...

high professional status and better income



DYNAMIC EXPANSION OF ELECTRONICS INDUSTRY CREATES OUTSTANDING JOB OPPORTUNITIES. No other major field of engineering has enjoyed a more rapid growth or promises a more brilliant future than electronics. New developments in space exploration, guided missiles, automation, computers, and many other fields create new jobs daily, jobs which have to be filled by men with a modern advanced education in electronics. The shortage of competent electronic personnel will grow more acute over the next decade, and salaries and professional stature of technical men are expected to reach new highs.


The fact that new positions must be filled by men with an up-to-date education is evidenced by the experience of the CREI Placement Bureau, where the demand for graduates and advanced students has far exceeded the supply for several years. It is of interest to note that

many leading companies regularly visit CREI strictly for the purpose of recruiting CREI graduates and students.

Many CREI students have learned that they do not have to complete the program to realize considerable increases in their status and income. Their own employers realize that if you are ambitious enough to pursue this college-level program, you are a better candidate for rapid promotion. Professional people in supervisory positions recognize the value of CREI education.


HOME STUDY IS CONVENIENT AND TIME SAVING. You will find more than 20,500 CREI students working in most every phase of electronics in all 50 states and in most foreign countries of the free world. Just like them, you can pursue the CREI

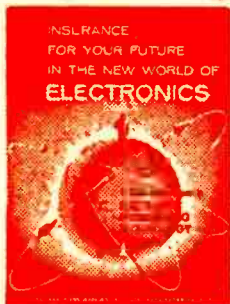**Free 44-page book about
Electronics and CREI pro-
gram of study . . . gives you
facts on advancing your
career status—improving
your income**



**This is a Postage-Free POST CARD . . . Fill out . . .
detach . . . and mail today for YOUR FREE COPY'**

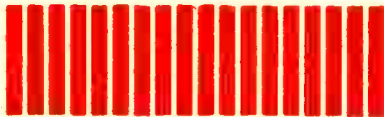**FIRST CLASS
PERMIT NO. 288-R
Washington, D. C.**



BUSINESS REPLY MAIL

No Postage Stamp Necessary if Mailed in United States

Postage Will Be Paid By



3224 Sixteenth Street, N.W.

WASHINGTON 10, D. C.

1403H

Learn how the CREI program of home study can advance your career and income

Please provide all requested
data to help us evaluate
your qualifications
and your needs



SEND THIS POSTAGE-PAID CARD
FOR FREE 44-PAGE BOOK

THE CAPITOL RADIO ENGINEERING INSTITUTE

ECPD Accredited Technical Institute Curricula • Founded 1927

Dept. 3224 Sixteenth St., N. W., Washington 10, D. C.

Please send me your FREE BOOK "Insurance for Your Future
in the New World of Electronics" . . . describing oppor-
tunities and the CREI extension programs in Advanced
Electronic Engineering Technology.

- CHECK Servo and Computer Engineering Technology
FIELD OF Electronic Engineering Technology
GREATEST Communications Engineering Technology
INTEREST Aero and Navigational Engineering Technology
 Automation and Industrial Electronics Eng. Tech.
NEW Nuclear Engineering Technology

Name _____ Age _____

Street _____

City _____ Zone _____ State _____

Check: Home Study Residence Program GI Bill

TO OBTAIN FAST, IMMEDIATE SERVICE AND TO AVOID
DELAY, IT IS NECESSARY THAT THE FOLLOWING IN-
FORMATION BE FILLED IN:

EMPLOYED BY _____

TYPE OF PRESENT WORK _____

EDUCATION: YEARS HIGH SCHOOL _____ OTHER _____

ELECTRONICS EXPERIENCE _____

CREI's Extension Division now offers you a college-level program in electronics comparable in technological content to advanced residence courses.

CREI offers college-level opportunity to the man who wisely realizes that the recognition and rewards in electronics are now going to other men—especially the man with modern advanced education.

Within two to four years, depending on the courses you select and amount of stick-to-itiveness brought to bear, you can complete the CREI program in advanced electronic engineering technology. The program was developed hand-in-hand with leading private companies and government agencies contributing to the Nation's efforts in electronics, communications, missiles and space exploration.

OFFICIALS OF PRIVATE COMPANIES AND GOVERNMENT AGENCIES APPROVE CREI FOR THEIR OWN PERSONNEL.

The quality and advanced standing of the CREI educational program is readily seen in the appreciation expressed for it by both industry and government. At present there are 5,240 U. S. Navy electronics personnel enrolled in CREI extension programs. More than fifty leading electronics organizations in this country and in foreign nations actually pay all or part of the tuition for employees taking CREI courses. The list below comprises a few of these organizations:

National Broadcasting Company • Jerrold Electronics Corporation • Pan American Airways • Radio Corporation of America • Canadian Aviation and Electronics • Federal Electric Corporation • The Martin Company • Voice of America • Canadian Broadcasting Corporation • Northwest Telephone Company • Commercial Cable, Incorporated • Canadair Limited • Columbia Broadcasting System • All America Cable and Radio • Canadian Marconi • Mackay Radio • United Air Lines • Gates Radio Company • Mohawk Airlines • Florida Power and Light Company • British Air Force, Army, Navy

program while you continue your regular full-time job. You study at home during hours chosen by you, and you are not rushed. Also, you do not have to waste valuable time traveling to and fro but can concentrate on your studying at the hours most convenient to you.

The courses are prepared in easy-to-understand format, and your progress is guided all along the way by the CREI staff of experienced instructors. These instructors always stand ready to give you personal assistance and help whenever you may need it.

ECPD Accredited Technical Institute Curricula • Founded in 1927

The Capitol Radio Engineering Institute

3224 16th Street, N.W., Washington 10, D. C., Dept. 1403-H

TO THE SERIOUS-MINDED MAN, CREI OFFERS THESE IMPORTANT BENEFITS:

- * You gain a solid college-level education in electronics; you keep abreast of continuous new developments and sophistications in the field of electronics.
- * You can gain higher status and enjoy the increased respect of your associates.
- * You facilitate more rapid professional advancement and corresponding increases in pay.
- * You gain the personal satisfaction that comes from working and communicating intelligently with technical colleagues and superiors.

The accredited program is designed to meet your present and future employment requirements and to increase your professional status and earning power.

PROFESSIONAL STANDING

CREI was founded in 1927 and is one of the oldest technical institutes in America. We co-founded the National Council of Technical Schools, and we were among the first three technical institutes whose curricula were accredited by the Engineers' Council for Professional Development. The U. S. Office of Education lists CREI as "an institution of higher education."

QUALIFICATIONS FOR CREI

You qualify for CREI study if you have a high school diploma or equivalent, and if you have had basic electronic training and practical experience in some phase of electronics. Tuition is reasonable and may be paid monthly, if you wish. Veterans qualify for this program under the GI Bill.

CREI RESIDENCE SCHOOL

CREI conducts a residence school in Washington, D.C. for those who can attend classes. Day and evening classes start at regular intervals. Graduates earn AAS Degree in 27 months of study. Electronics experience or training is not required for admission.

SEND FOR THIS FREE 48-PAGE BOOK TODAY. . . USE POSTAGE-PAID CARD ATTACHED.

Write for the detailed and informative book "Insurance for Your Future in the New World of Electronics." It is yours for the asking without cost or obligation. The book gives details about curricula and CREI and answers several searching questions about the future in electronics. The book is of vital interest to every man employed in electronics.





The Beautiful *Schober* CONSOLETTA
—only small organ with two full 61-note keyboards and 22 stops. Requires only 2'x3'2" floor space! Commercial value approximately \$1600 or more.

BUILD THIS SUPERB *Schober* ORGAN FROM SIMPLE KITS and save over 50%

Give Your Family A Lifetime of Musical Joy With A Magnificent Schober Electronic Organ!

Now you can build the brilliant, full-range Schober CONSOLETTA or the larger CONCERT MODEL with simple hand tools! No skills are needed; no wood-working necessary. Just assemble clearly marked electronic parts guided by step-by-step instructions. You build from kits, as fast or as slowly as you please . . . at home, in your spare time — with a small table serving as your entire work shop.

Pay As You Build!

Start building your organ at once, investing just \$18.94! The superb instrument you assemble is as fine, and technically perfect, as a commercial organ . . . yet you save over 50% on quality electronic parts, high-priced labor, usual store mark-up!

Free Booklet

Send for 16-page booklet in full color describing Schober organs you may build for home, church or school — plus articles on how easy it is to build your own organ and how pleasant it is to learn to play. Also available is 10" LP demonstration record (price \$2.00 — refundable on first order). Send for literature. No obligation and no salesman will call.

THE GREAT CONCERT MODEL meets specifications of American Guild of Organists

Mail This Coupon For FREE Schober Literature And Hi-Fi Demonstration Record TODAY!

The Schober Organ Corp., Dept. RE-10
43 West 61st St., New York 23, N.Y.


- Please send me the 10" hi-fi Schober and other literature on the Schober organs.
- Please send me the 10" hi-fi Schober demonstration record. I enclose \$2.00 (refundable on receipt of my first kit order).

Name.....
Address.....
City..... Zone..... State.....

new PRODUCTS




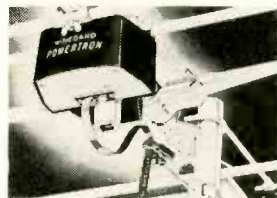ELECTRONIC TV RECEIVING ANTENNA, Pioneertron. Booster at antenna amplifies TV signals up to 9 times normal signal voltage. All-channel



Yagi. 14-, 21- and 30-element models suitable for color and black-and-white. Power transformer plugged into house outlet supplies 24 volts to booster via lead-in.—Winegard Co., 3000 Scotten Blvd., Burlington, Iowa.

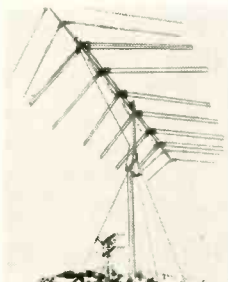TRAVELING-WAVE ANTENNAS, Super 10 T-W 10-element antenna combines 6 hairpin-driven



dipoles with 4 parasitic low-band and co-linear high-band elements. Super 8 T-W, 4 driven and 4 parasitic elements.—Channel Master Corp., Ellenville, N. Y.

TV/FM SYSTEM KIT, model HK-1, feeds up to 4 TV or FM sets from single indoor antenna.



4-set coupler, 300-ohm ribbon line and installation hardware.—Blonder-Tongue Labs, 9-25 Alling St., Newark 2, N. J.

OSCILLOSCOPE KIT, Dual Trace. Simultaneous observation of 2 signals. Flat 10 cycles to 5 mc, useful to 9 mc. Push-pull vertical and horizontal



amplifiers. Cathode-follower inputs. 5-inch screen. 13 1/4 x 8 3/4 x 18 1/2.—Radio Shack Corp., 730 Commonwealth Ave., Boston 17, Mass.

VACUUM-TUBE VOLTMETER KIT, KT-174. 200-ma meter movement with balanced-bridge push-pull circuitry. 2-color scale incorporates direct decibel scale plus zero-center scale. Rear scope terminals for simultaneous waveform observation and ac measurement. Dc and ac volts 1.5 to



1,500 full scale in 7 ranges each; resistance 1,000 ohms to 1,000 megohms full scale. Special low ac ranges (0-50, -150, -500 mv rms, 0-140, -420, -1,400 mv peak to peak) for audio and hi-fi applications. Printed circuit. 9 1/2 x 6 x 5 in.—Lafayette Radio Corp., 165-08 Liberty Ave., Jamaica 33, N. Y.

TRANSISTOR TESTER, Model 700. Checks existing, (and future) transistors without need for data chart reference. Also diodes for forward-



reverse ratio. Hammertone-finish steel case. Handle folds back to rest instrument in tilted position. Instruction manual—Mercury Electronics Corp., 77 Searing Ave., Mineola, N. Y.

TEST INSTRUMENT for color TV installing and servicing in home and on bench, IR-64A.



Color bar/dot/crosshatch generator combines functions of both. Rf output cable, cable-carrying bracket attachment. Instruction booklet. Heavy-duty metal case. 13 lb. 13 1/2 x 10 x 8 inches—RCA Electron Tube Div., Harrison, N. J.

CB POWER OUTPUT AND MODULATION METER, Model LS for insertion in transmission




line between antenna and set. *Model TS* test set, with a 50-ohm dummy antenna for testing transmitter with antenna disconnected. Black crackle case. 2 x 4 x 4 in.—Crown Electric Products Co., P.O. Box 171, Orange, N. J.

TRANSMITTER-RECEIVER COMBINATION, Pawnee. Complete AM and CW facilities on 2-meter amateur band. Built-in 3-way power supply. 117-vac fixed station or 6- or 12-vdc mobile operation. Built-in speaker, ac and dc



power cables, primary fused relay for mobile installation, mounting bracket and push-to-talk ceramic-element microphone with coil cord and mounting clip. 6 x 12 x 10 in. 34 lb.—Heath Co., Benton Harbor, Mich.

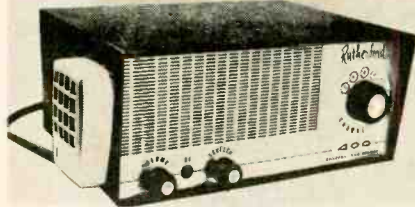CITIZENS-BAND RADIOPHONE, 400. Meets FCC requirements. Universal power supply operating from 6 or 12 volts dc or 117 vac. Automatic




noise limiter. Adjustable squelch. 6 crystal-controlled receive and transmit channels. Black splashproof case.—Rutherford Electronics, 8930 Lindblade St., Culver City, Calif.

AUTO RADIO SPEAKER, model SP410E, for '61 Buick, Cadillac, Chevrolet (except Corvair), Studebaker (except Lark), Pontiac and Olds-



mobile 2.15-ounce Alnico V magnet. Handles 8 watts power. 4 x 10 in.—Utah Radio Products Co., Inc., 1124 E. Franklin St., Huntington, Ind.

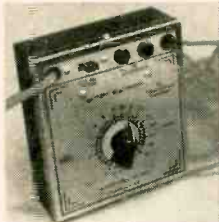BATTERY ELIMINATOR, Professional model 2. For transistorized equipment. Supplies clean,



filtered dc fully variable from 0 to 15 volts.—National Radio Institute, 3939 Wisconsin Ave., Washington 16, D. C.

SUBSTITUTION UNIT, Big 20, model PR111. For all power resistors encountered in radio and

For Fun and Profit... Latch on to the Latest GERNSBACK LIBRARY BOOKS

Here's a great book for getting youngsters (of any age) off the ground toward a career in science. Gives easy-to-understand step-by-step illustrated instructions on how to build scores of electric devices—a simple electric motor, an electrical jitterbug, a solenoid, a spark coil, the famous Tesla coil, and a variety of electrical meters. And you can build them with simple tools and materials you can buy at any 5 and 10 cent store. Includes the theory of electricity and tips on tools, soldering and construction techniques. An ideal gift for the youngster you want to get started in a career.

FUN WITH ELECTRICITY
By Tom Kennedy, Jr.

Gernsback Library Book
No. 83—128 pages.
Paper bound edition.
\$2.65



The Story of Stereo: 1881—
John Sunier
No. 98—160
pages. **\$2.95**

For the first time—the whole fascinating history of stereo from its earliest beginnings in the last century right up to today. Stereo applications on tape, film, discs and broadcasting—plus a consideration of stereo techniques in the home, in business, industry and medicine.




Practical Auto Radio Service & Installation
By
Jack Greenfield
No. 87—160
pages. **\$2.95**

Shows you how to install and remove auto sets, rear seat speakers, troubleshoot and repair speakers, tuners, power supplies. Covers FM, hybrids, all-transistor sets, auto phonographs. This one will help you build your business, increase your earnings.



Practical TV Troubleshooting
No. 102—128
pages. **\$2.35**

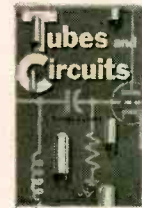Some of the best technician-writers in the business tell you how to handle intermittents, ghosts, horizontal oscillator troubles, foldover, jitter and many other common and uncommon tough ones. A compilation of the best on TV servicing from *Radio-Electronics Magazine*.



Tubes and Circuits
By George Christ
No. 82—192
pages. **\$3.45**

Considers basic electron theory, characteristics of simple and multiple element tubes, various tube types, gas tubes, photoelectric emission, and industrial applications. This book enables the technician to analyze circuit troubles intelligently and correct them quickly and efficiently through an understanding of fundamentals.

OTHER POPULAR GERNSBACK LIBRARY BOOKS

SERVICING

- No. 85—How to Get the Most Out of Your VOM \$2.90
- No. 81—Printed Circuits. \$2.90
- No. 78—Rapid Radio Repair. \$2.90
- No. 76—Servicing Transistor Radios. \$2.90
- No. 72—Oscilloscope Techniques. \$2.90
- No. 68—TV and Radio Tube Troubles. \$2.90
- No. 65—Servicing Color TV— \$2.90
- No. 60—Rapid TV Repair. \$2.90
- No. 59—Servicing Record Changers. \$2.90
- No. 57—The VTVM. \$2.50
- No. 55—Sweep and Marker Generators for TV and Radio— \$2.50
- No. 54—Probes. \$2.50
- No. 52—The Oscilloscope. \$2.25
- No. 49—Radio & TV Test Instruments. \$1.50
- SEMICONDUCTORS**
- No. 92—Fundamentals of Semiconductors— \$2.95
- No. 89—Transistor Projects. \$2.90
- No. 63—Transistor Circuits. \$2.75
- No. 61—Transistor Techniques. \$1.50
- No. 75—Transistors Theory & Practice. \$2.95
- HIGH FIDELITY**
- No. 90—Hi-Fi Made Easy. \$2.90
- No. 86—Installing Hi-Fi Systems. \$3.20
- No. 80—Stereo—How it Works. \$2.90
- No. 79—Designing and Building Hi-Fi Furniture. \$2.90
- No. 73—Audio Measurements. \$2.90
- No. 71—Audio Design Handbook. \$2.90
- No. 67—Elements of Tape Recorder Circuits. \$2.90
- No. 66—Basic Audio Course. \$2.75
- No. 64—Understanding Hi-Fi Circuits. \$2.90
- No. 58—Maintaining Hi-Fi Equipment. \$2.90
- No. 56—High-Fidelity Circuit Design. (Cloth Bound.) \$5.95
- No. 48—High Fidelity—Design, Construction, Measurements. \$1.50
- HOBBIES**
- No. 74—Model Radio-Control. \$2.65
- No. 70—Electronic Puzzles and Games. \$1.95
- No. 69—Electronic Hobbyists' Handbook. \$2.50

No. 53—Radio-Control Handbook. \$2.25

No. 45—Radio Tube Fundamentals. \$1.00
Books paper bound unless otherwise noted.

FUNDAMENTALS—MISCELLANEOUS

- No. 84—Marine Radio for Pleasure Craft. \$2.95
- No. 77—Guide to Mobile Radio. \$2.85
- No. 62—TV—It's a Cinch. \$2.90
- No. 47—Radio & TV Hints. \$1.00

Books purchased for professional use are tax deductible

SEE YOUR DISTRIBUTOR or ORDER DIRECT


Gernsback Library, Inc. Dept. 31
154 West 14th St., New York 11, N. Y.

Please send me postpaid the books listed below. My remittance of \$..... is enclosed.

Please list books by number

Name.....
Street.....
City..... Zone..... State.....

For that

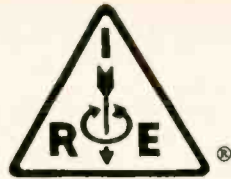

NEW IDEA

visit the

IRE SHOW

March 20-23, 1961

New York

Coliseum and Waldorf-Astoria Hotel

Members \$1.00, Non-members \$3.00

Age limit—over 18

EFFICIENT!

SAFE!

FAST!



ARROW'S T-25 Low Voltage Wire STAPLE GUN

For Fastening Any
Inside or Outside
Wire Up to 1/4" in Diameter



- Telephone wire
 - Intercom wire
 - Bell wire
 - Thermostat wire
 - Radiant heating wire
 - Hi-Fi, Radio & TV wires
- Tapered striking edge gets into close corners!

Available in: Brown, Ivory, Beige, Monel, Bronze, Natural



TAPE RECORDERS



**HI-FI COMPONENTS
SLEEP LEARN KITS**

Unusual Values
Free 1961
Catalog
DRESSNER,
1523RE Jericho Tpke, New Hyde Park, N.Y.

MERITAPE
Low cost, high
quality recording
tape, in boxes or cans.

"New 1961
Catalog"



★ A complete catalog of specialized industrial Electronic TUBES and COMPONENTS... featuring Barry Electronics savings to Industry, Servicemen and Experimenters.


We have thousands of tube types in stock. First Quality at Sensible Prices. Buy with confidence.

Prove these values to yourself! Complete and mail the coupon below for your copy of the "Greensheet."

We'll also purchase your equipment and unused tubes. Send details: **BARRY ELECTRONICS CORP.** 512 Broadway, New York 12, N.Y. Dept. RE-3.


Please send me a copy of the new 1961 "Greensheet" and add my name to your mailing list.

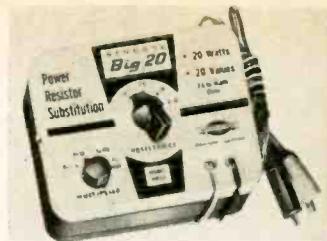(RE-3)
Name..... Title
Company.....
Address.....
City..... State



TV work. Each power resistor can be substituted in circuits that dissipate up to 20 watts—Service Instruments Co., Addison, Ill.

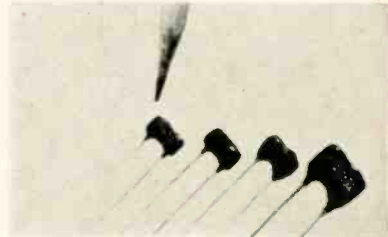DIPPED SILVERED MICA CAPACITORS, Royal Blue. Phenolic-coated. Capacitance range from 1 μ f to .04 μ f. Delay line, computer, missile, high-grade equipment and commercial/industrial general-purpose applications. Multi- and single-coated. Standard voltage ratings 500, 300, 100 vdc; capacitance tolerances \pm 10%, 5%, 2%, 1%



and 1/2%.—Cornell-Dubilier Electronics Div., Federal Pacific Electric Co., 55 Cromwell St., Providence, R. I.

VIBRATOR, type 1619. Molded polyethylene case. 1.2 ounces. 3-, 6-, 12-, 24-, or 32-volt ratings.



115 \pm 7-cycle frequency. Developed for photoflash applications. Maximum load 3 amperes.—Mallory Electromagnetic Co., Div. of P. R. Mallory & Co. Inc., 3029 E. Washington St., Indianapolis 6, Ind.

AUDIO INPUT TRANSFORMERS. Primary impedance 600/500 ohms et. A-4773, line-to-grid transformer with turns ratio of 1:20 and secondary impedance 240,000 ohms. A-4779, line-to-



single or push-pull grid applications with turns ratio of 1:10 and secondary impedance 60,000 ohms et. A-4780, line to push-pull applications with turns ratio of 1:20 and secondary impedance 240,000 ohms et.—Chicago Standard Transformer Corp., 3501 W. Addison St., Chicago 18, Ill.

PACKAGED ELECTRONIC CIRCUITS. Compensator network, PC-405; audio, PC-406; integrators,



PC-407 and PC-408; phase detector, PC-409.—Centralab, Div. of Globe-Union, 900 E. Keefe Ave., Milwaukee 1, Wis.

ULTRA-MINIATURE PHONE PLUG. Micro, Plug. 1/26th standard phone-plug size, for use with miniaturized jacks in transistor radios, miniature electronic equipment, computing de-



in **Radio-Electronics** next month...

COVER STORY:

ALL AUTOMATIC ELECTRONIC LAWN MOWER—Look—no hands! A homeowner's dream come true. Goes one step beyond the remote-controlled unit. Built by an ingenious experimenter who hates to mow the lawn.

TUNNEL-DIODE GRID DIP METER—The tunnel diode makes the grid dip meter easier to build and use. This versatile meter will also inject a signal for test purposes.

MINI-PACK AMPLIFIER YOU CAN MAKE—Here's a three-transistor audio amplifier no bigger than a peanut! A natural for hearing aids, miniature radios and portable instruments.

NEW TRANSISTOR TV TUNERS—At least three companies are making them. This article tells you what they are and what they can do. Outlines some of the problems they may present.


APRIL ISSUE ON SALE MARCH 16

50¢ at newsstands and parts distributors

Subscription rates 3 years \$12 2 years \$9 1 year \$5

154 West 14th Street, New York 11, N. Y.

ATLAS "Job Rated" P. A. SPEAKERS

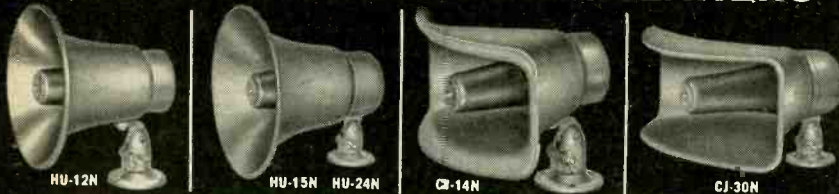

There is an Atlas Speaker Ideally Suited for Every Job

All Atlas P. A. speakers are highly efficient, especially in the voice frequency range, providing the extra "punch" needed to override high level background noise. Most are 100% weatherproof; aluminum and diecast parts are treated with corrosion inhibitors, then finished in "stone hard" baked enamel. The CJ Cobra-Jector horns are constructed of nonresonant, indestructible fiberglass, and HU and TP speaker horns of aluminum, finished in gun-metal grey. The HU and TP speakers are particularly designed for efficient talkback operations. The peaked characteristics within the voice frequencies increase the sensitivity of these speakers as pickup devices.

All HU and CJ speakers are equipped with versatile "Versalock" . . . This rugged, reliable mounting bracket, completely adjustable both horizontally and vertically, provides positive locking in any position.

The DU-12 and DC-5, Atlas' renowned Ecor projectors, are styled to harmonize with any decor, modern or traditional. Send for free catalog to Dept. RE-3

Model	HU-12N	HU-15N	HU-24N	CJ-14N	CJ-30N	CJ-44	TP-15N	TP-24N	DU-12	DC-5
POWER*	7.5 w	25 w	25 w	7.5 w	25 w	60 w	25 w	25 w	7.5 w	6 w
IMPEDANCE**	8 ohm	8 ohm	8 ohm	8 ohm	8 ohm	16 ohms	8 ohm	8 ohm	8 ohm	8 ohm
FREQUENCY C.P.S.	350-10,000	250-10,000	200-10,000	400-10,000	250-10,000	150-9000	250-10,000	200-10,000	400-10,000	120-7000
LENGTH OVERALL	7 1/4 in.	8 3/4 in.	12 in.	8 in.	1 1/4 in.	23" x 13"	16 1/2 in.	23 in.	14 in.	14 in.
BELL DIAMETER	7 1/2 in.	9 3/4 in.	11 1/4 in.	9 1/2" x 5 1/2"	14" x 6"	19 in.	9 3/4 in.	11 1/4 in.	7 in.	7 in.
NET PRICE	\$16.20	\$20.10	\$22.35	\$18.00	\$24.60	\$43.50	\$31.20	\$34.50	\$19.80	\$13.20

*Input range limited to frequencies above horn cutoff **All models available in 45 ohms at slightly higher prices



TP-15N TP-24N




DC-5
DU-12



CJ-44

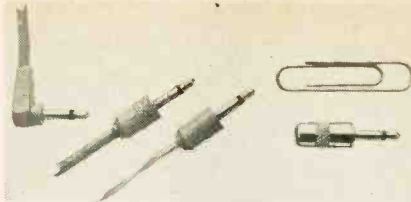ATLAS SOUND CORP.
1449 39th Street
Brooklyn 18, N. Y.
In Canada:
Atlas Radio Corp., Ltd.,
Toronto, Ontario




vices, tape recorders—Switchcraft Inc., 5555 N. Elston Ave., Chicago 30, Ill.

TOOL, Piggy-Back. Plastic handle with 1/4-inch hexagon socket. Reversible blade with one end



3/16-inch regular blade and other end No. 1 Phillips bit. Midget instrument type screwdriver fits into 1/4-inch hexagon socket.—Vaco Products Co., 317 E. Ontario St., Chicago 11, Ill.

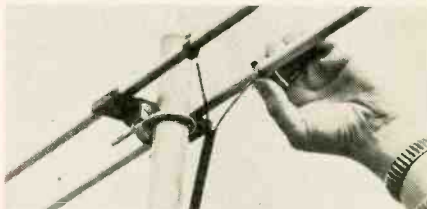CONNECTOR, Kwik-Klip. For antenna lead replacement. One-hand, clip-on operation eliminates



need to remove rusted or corroded nuts and bolts.—CBS Electronics, Div. of Columbia Broadcasting System Inc., Danvers, Mass.

STEREO HI-FI AMPLIFIER KIT. 2 fully integrated preamps. Rated power output of 16 watts




per channel. Total IHFM music power rating 39 watts. For bookshelf placement, measures 4 1/4 x 14 1/4 x 11 3/4 inches. Cordovan gray finish—Allied Radio Corp., 100 N. Western Ave., Chicago 80, Ill.

STEREO RECEIVER, Fisher 500-S. 0.9 μv sensitivity for 72-ohm antenna. Microray tuning indicators on FM and AM. 45-watt stereo power



amplifier. Master audio control with 20 controls and switches for every application.—Fisher Radio Corp., 21-21 44th Drive, Long Island City 1, N. Y.

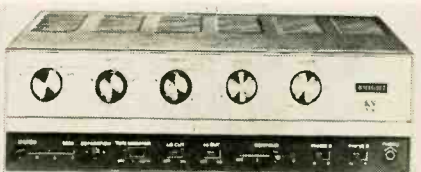STEREO AMPLIFIER, KN-775. 37.5 watts per channel. Minimum IHFM music power rating of 96 watts. 4 EL34 audio output tubes. Frequency response ±0.5 db, 25 to 20,000 cycles; IHFM



power bandwidth 15 to 85,000 cycles. Has 16-ohm center-channel output, front-panel phone jack. Solid aluminum front panel. Gold and charcoal brown finish. 4 1/4 x 15 3/4 x 15 1/4 inches. Beige case.—Allied Radio Corp., 100 N. Western Ave., Chicago 80, Ill.

RADIO-ELECTRONICS

SAVE 20% BUY DIRECT

OFFICIAL COMMUNICATIONS CONVERTER



For state, local police and fire networks between 30 and 50 MC AM/FM

- Uses 12V hybrid tubes — requires no B+ supply
- Has built-in squelch
- Stable drift free operation regardless of input operation
- Easy installation—plugs into cigarette lighter

~~\$59.95~~ Buy direct for only **\$47.96** plus \$3.75 xtal

TRANSCON DIVISION
NORTHEAST TELECOMMUNICATIONS INC.
Danbury, Conn.

CATALOG ON REQUEST


Available from franchised distributors at slightly higher cost.

BUILD YOUR OWN THEREMIN!



Now you can enjoy the ethereal, mysterious, fascinating sound of the THEREMIN. You play this most modern of musical instruments without touching it—simply by moving your hands about it. The THEREMIN has no keys, buttons or strings.

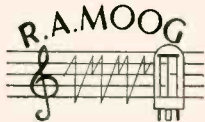For the first time, a transistorized THEREMIN is available in kit form. This easy-to-build musical instrument is featured in the January, 1961, issue of *Electronics World* magazine. For a free reprint of this article and complete information on this exciting new kit, mail this coupon today.




R. A. MOOG CO.
Department C, P.O. Box 263
Ithaca, New York

Please send me complete information on the build-it-yourself THEREMIN.


Name _____
Address _____
City _____ Zone _____ State _____
Please Print

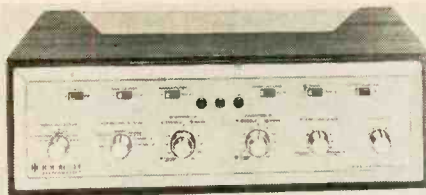STEREO AMPLIFIER, New 299B. Tape monitoring provisions for recording. Extra high level



input for connection of electronic organ. Increased power to 50 watts.—H. H. Scott Inc., Dept. P, 111 Powdermill Rd., Maynard, Mass.

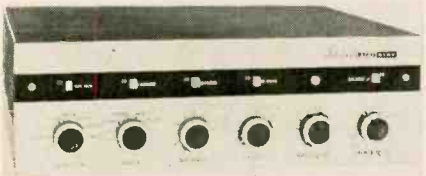STEREO INTEGRATED AMPLIFIERS, 70-watt ST70 and 40-watt ST40. Kit and factory-wired. For any stereo program source. Williamson type



circuits employing voltage amplifiers and split-load phase inverters driving output stage. $\pm 1/2$ db 12-25,000-cycle frequency response. Harmonic distortion less than 1% 40-20,000 cycles.—EICO (Electronic Instrument Co. Inc.) 33-00 Northern Blvd., Long Island City 1, N. Y.

STEREO PHONOGRAPH CARTRIDGES, M7-N21D and M3-N21D. M7 and M3 cartridges



equipped with high-compliance N-21D stylus originally designed for M212 Studio Dynetic pickup. For independent tone arms at tracking force of 2 grams. Stylus compliance 9.0×10^{-6} cms/dyne, frequency response 20 to 20,000 cycles, $\pm 2 1/2$ db.—Shure Brothers Inc., 222 Hartrey Ave., Evanston, Ill.

READY-BUILT HI-FI CABINETS, Model AE-20 Series. Center cabinet holds all components but



speakers for which speaker-wing cabinets models AE-30 and AE-40 series, available.—Heath Co., Benton Harbor, Mich.


RECORD CABINET, model 106. Matches manufacturer's hi-fi equipment cabinets and speaker



enclosures. Walnut, hand-rubbed mahogany, blond or ebony. Removable base or legs. $20 \times 32 1/2 \times 18$ in.—Rockford Special Furniture Co., 1803 W. Belle Plaine, Chicago 13, Ill.

TAPE RECORDER, Magnematic. Bookshelf, 3 1/2 x 10 x 11 1/2 in., for home (illustrated); *Broadcaster*, fitting standard 3 1/2-inch rack panel, for professionals. Tape handling eliminated by plastic cartridge that inserts into player. Cartridges

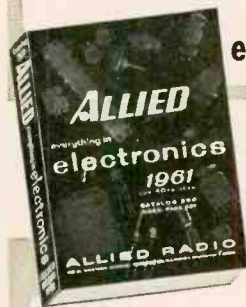SAVE on everything in stereo hi-fi and electronics



send for the 1961

ALLIED CATALOG free

444-PAGES • VALUE PACKED. Write today for the leading Electronics Catalog. World's largest selection, including products and values available only from ALLIED.SAVE ON:

- Everything in Hi-Fi Music Systems & Components • Biggest Selection of Hi-Fi Ceterelry
- Exclusive Knight® Super-value Stereo • Knight-Kits®—Best in Build-Your-Own Hi-Fi • Tape Recorders and Phono Equipment
- Everything in Electronic Parts, Tubes, Transistors, Test Equipment, Amateur Gear, P.A. Systems, TV Accessories, Tools, Books.

only \$2 down on orders up to \$50

Save most at ALLIED. Write for FREE 1961 Catalog today!

ALLIED RADIO

ALLIED RADIO, Dept. 103-C1
100 N. Western Ave., Chicago 80, Ill.

Send FREE 1961 ALLIED Catalog.

Name _____

Address _____

City _____ Zone _____ State _____

free catalog

TV-RADIO Servicemen or Beginners...

Send for *Coyne's* 7-Volume Job-Training Set on 7-Day **FREE TRIAL!**



The First Practical TV-RADIO-ELECTRONICS Shop Library!

Answers ALL Servicing Problems QUICKLY... Makes You Worth More On The Job!

Put money-making, time-saving TV-RADIO-ELECTRONICS know-how at your fingertips—examine Coyne's all-new 7-Volume TV-RADIO-ELECTRONICS Reference Set for 7 days at our expense! Shows you the way to easier TV-Radio repair—time saving, practical working knowledge that helps you get the BIG money! How to install, service and align ALL radio and TV sets, even color-TV, UHF, FM and transistorized equipment. New photo-instruction shows you what makes equipment "tick". No complicated math or theory—just practical facts you can put to use immediately right in the shop, or for ready reference at home. Over 3000 pages; 1200 diagrams; 10,000 facts!

SEND NO MONEY! Just mail coupon for 7-Volume TV-Radio Set on 7-Day FREE TRIAL! We'll include the FREE BOOK below. If you keep the set, pay only \$3 in 7 days and \$3 per month until \$27.25 plus postage is paid. Cash price only \$24.95. Or return set at our expense in 7 days and owe nothing. Either way, the FREE BOOK is yours to keep. Offer limited, so act NOW!

"LEARNED MORE FROM THEM THAN FROM 6 YEARS WORK!"

"Learned more from your first two volumes than from 5 years work."
—Guy Bliss, New York

"Swell set for either the serviceman or the beginner. Every service bench should have one."
—Melvin Masbruch, Iowa.

FREE DIAGRAM BOOK!

We'll send you this big book, "150 Radio-Television Picture Patterns and Diagrams Explained" ABSOLUTELY FREE just for examining Coyne's 7-Volume Shop Library on 7-Day FREE TRIAL! Shows how to cut servicing time by reading picture-patterns, plus schematic diagrams for many TV and radio sets. Yours FREE whether you keep the 7-Volume Set or not! Mail coupon TODAY!

Like Having An Electronics Expert Right At Your Side!

VOL. 1—EVERYTHING ON TV-RADIO PRINCIPLES! 300 pages of practical explanations; hundreds of illustrations.

VOL. 2—EVERYTHING ON TV-RADIO-FM RECEIVERS; 403 pages; fully illustrated.

VOL. 3—EVERYTHING ON TV-RADIO CIRCUITS! 336 pages; hundreds of illustrations, circuit diagrams.

VOL. 4—EVERYTHING ON SERVICING INSTRUMENTS! How they work, how to use them. 368 pages; illustrated.

VOL. 5—EVERYTHING ON TV TROUBLESHOOTING! Covers all types of sets. 437 pages; illustrations, diagrams.

VOL. 6—TV CYCLOPEDIA! Quick and concise answers to TV problems in alphabetical order, including UHF, Color TV and Transistors; 868 pages.

VOL. 7—TRANSISTOR CIRCUIT HANDBOOK! Practical Reference covering Transistor Applications; over 200 Circuit Diagrams; 410 pages.

ALL 7 BOOKS HAVE BRIGHT, MODERN, VINYL CLOTH WASHABLE COVERS

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL
1455 W. Congress Parkway, Dept. 31-T1, Chicago 7, Illinois

Yes! Send me COYNE'S 7-Volume Applied Practical TV-RADIO-ELECTRONICS Set for 7-Days FREE TRIAL per your offer. Include "Patterns & Diagrams" book FREE!

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

Check here if you want Set sent C.O.D. Coyne pays postage on C.O.D. and cash orders. 7-Day Money-Back Guarantee.

Coyne

ELECTRICAL SCHOOL 1455 W. Congress Parkway
Dept. 31-T1, Chicago 7, Illinois





RADIO HANDBOOK

-gives comprehensive, up-to-the-minute data for designing and building radio equipment

Extensive theory—the Radio Handbook covers practically every phase of radio theory, in simplified, easy-to-grasp form.

Latest design data—all original material—enables you to design any standard type of transmitting and receiving equipment, from medium to ultra-high frequencies.

Latest construction data—broadest coverage in the field. You get complete original information on how to build and operate advanced high performance equipment. Plans include details on attractive styling. All data clearly indexed. 800 pages—all editorial—with hard cover. The largest RADIO HANDBOOK ever published.

at your dealer, plus any tax **\$8.50**

Buy from your favorite distributor at \$8.50, or add 10% on direct orders to:



EDITORS and ENGINEERS, Ltd.

Summerland 5, California

Bookstores: Order from Baker & Taylor Co., Hillside, N.J.



handle up to 1200 feet. 20 models available for 1 $\frac{1}{2}$, 3 $\frac{1}{4}$, 7 $\frac{1}{2}$ and 15 ips, mono play only, mono play and record, stereo play only, stereo play and mono record, and stereo play and record.—Magnetomatic Div., Amplifier Corp. of America, 398 Broadway, New York 13, N. Y.

TAPE RECORDER HEAD DEMAGNETIZER, type 516C1. Reduces noise and distortion. Unit is plugged into 117-volt ac outlet, tip brought



into contact with record-playback head and withdrawn.—Dist. Prod. Dept., RCA Tube Div., 415 South Fifth Street, Harrison, N. J.

TURNTABLE CHANGER, Dual-1006 Custom. Fully automatic and manual turntable and automatic record changer. Roller-feeler indexing action measures record for lead-in groove. Ele-



vator-action spindle operates without pusher arms or offset spindles. One-piece free-floating tone arm tracks and trips down to 1 $\frac{1}{2}$ grams.—United Audio Products, 202-4 E. 19th St., New York 3, N. Y.

4-SPEED TURNTABLE AND TONE ARM, PK-449. 3-lb., rim-weighted 12-inch aluminum table with permanently lubricated oilite bronze bearing. Precision spindle turns on single ball bear-



ing. Speed control allowing for $\pm 7\%$ variation of each speed. Supplied with stroboscopic disc, 45-rpm adapter, shielded hookup cables and ac line cord.—Lafayette Radio Corp., 165-08 Liberty Ave., Jamaica 33, N. Y.

PREAMPLIFIER, model 122 Dynaural Stereo Control Center. Dynaural rumble and scratch suppressors. Center-channel level control on front



panel. 5 separate stereo inputs, each with own level control.—H. H. Scott Inc., Dept. P, 111 Powdermill Rd., Maynard, Mass.

All data are from manufacturers' specifications.

Unbelievable LOW PRICES! NOT KITS . . . But Factory Wired and Guaranteed HIGH QUALITY INSTRUMENTS



New! Model 999 Radio & TV SIGNAL GENERATOR

Provides highly stable signal. Generates R. F. frequencies from 150 Kilocycles to 50 Megacycles. (150 Kc. to 12.5 Mc. on Fundamentals and from 11 Mc. to 50 Mc. on Harmonics). R.F. is obtainable separately or modulated by the Audio Frequency. Measures 7 $\frac{3}{4}$ " x 7 $\frac{3}{4}$ " x 5". Weight 8 Lbs.

Complete—only \$14.95



New! TC-75 Univ. Combination TEST SPEAKER & SIGNAL TRACER

Plus resistor tester
Plus condenser tester
Plus output indicator
Plus speaker substitution. Plus resistor substitutor
Plus substitute 100 V D.C. power supply
Plus field substitutor. Plus condenser substitutor
Plus voice coil substitutor
Plus signal tracer
Plus universal output transformer
Plus experimental one stage audio amplifier
Measures 7" x 11" x 5". Weight, 8 Lbs.

Complete—only \$19.95


Order directly from METROPOLITAN ELECTRONICS • 106 Fifth Ave., New York 11, N.Y.

NEW TUBES and SEMI-CONDUCTORS

A TRIPLE-TRIODE 12-pin Compactron leads off this month. It is followed up by a series of switching transistors, a conduction-cooled uhf beam power tube, a 9-pin triode-pentode for TV and other recent releases.

6D10

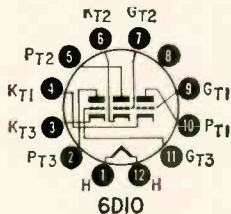Compactron containing three high-mu triodes with separate pin connec-



tions for all three cathodes, grids and plates. It is designed for use as an oscillator, mixer, grounded-grid amplifier, and automatic frequency control service.

Maximum ratings of this Tung-Sol tube are:

	(each section)	
V_p	330	
V_G (max pos)	0	
V_G (max neg)	50	
P_p (watts)	2	

Characteristics with 125 volts on the plate and -1 volt on the grid are:


	(each section)	
μ	57	
R_p (ohms)	13,600	
g_m (μ mhos)	4,200	
I_p (ma)	4.2	

2N1136, -A, -B

A series of very high gain p-n-p transistors designed as high-current switching devices for dc-dc converter and dc-ac inverter circuits. The series has three voltage breakdown ratings for use in both 12- and 28-volt supplies without danger of burnout. Current gain is controlled to eliminate need for matching. The transistors can switch up to 400 watts.

NOW! A down-to-earth guide to MODERN TEST PROCEDURES

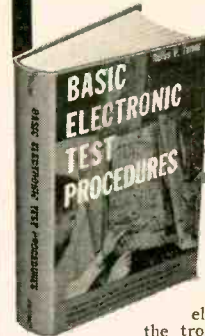- Alternate Test Methods • Cautions • Correct Instrument Usage • Readings • Connections and Control Settings • Test Techniques • Time-Saving Methods ... and all the rest!



Almost anyone can repair TV's, radios and other electronic equipment AFTER the trouble has been located. The trick is to know how to spot troubles in the first place—and that means knowing how to use instruments fast and accurately. Actually, it's amazing what you can do with only a few instruments—providing you know how to use different kinds for the same job; how to select the right ones; where to use them; how to connect them into circuits; how to set controls; how to read them; and how to follow professional test procedures every step of the way. And that's exactly what this new 316-page book with its more than 190 how-to-do-it pictures and procedure sketches teaches you.

IT'S WHAT YOU KNOW ABOUT USING INSTRUMENTS THAT COUNTS!

BASIC ELECTRONIC TEST PROCEDURES by Rufus Turner helps you learn to troubleshoot any circuit, equipment or component in half the usual time. Covers different methods for doing specific jobs. For instance, you learn to check distortion by the 'scope, rejection filter, harmonic-distortion meter, wave analyzer or audio oscillator methods. You learn to make resistance measurements with a current-meter, a volt-ammeter, a volt-meter, an ohmmeter, or via the bridge method. Subjects include current checks; power, capacitance, resistance, AF, RF, phase, distortion, and modulation measurements; tube and semi-conductor testing; audio amplifier tests; sensitivity, RF gain, fidelity, AVC voltage, operating voltage checks, etc.; visual alignment techniques—even transmitter and industrial electronic test procedures. Price only \$8.00.

CONSIDER OSCILLOSCOPES for instance!

Simplified explanations of modern oscilloscope techniques show how to use your 'scope as a volt-meter, current meter, variable frequency oscillator, etc., or for making RF, phase or AM measurements; for distortion and deflection checking; square wave testing; visual AM and FM alignment, and for many other jobs. Every detail is explained—from making connections to analyzing patterns.

INDUSTRIAL ELECTRONICS, TOO!

STILL ANOTHER BIG FEATURE is the book's usefulness in acquainting you with industrial electronic test techniques—including testing non-electronic phenomena such as strain, pressure, etc.

PRACTICE 10 DAYS . . . FREE!

Dept. RE-31, Technical Division,
HOLT RINEHART and WINSTON, Inc.
383 Madison Ave., New York 17, N.Y.

Send **BASIC ELECTRONIC TEST PROCEDURES** for 10-day **FREE EXAMINATION**. If I decide to keep book, I will then send you \$8.00 plus postage in full payment. If not, I will return book postpaid and owe you nothing. (SAVE! Send \$8.00 with your order and Rinehart pays the postage. Same 10-day guarantee with your money promptly refunded if you're not more than satisfied with book.)

NAME.....

ADDRESS.....

CITY, ZONE, STATE.....

OUTSIDE U.S.A.—Cash with order only. Price \$8.50. Money back if book is returned in 10 days.

For that  **NEW IDEA**
visit the
IRE SHOW

March 20-23, 1961 New York
Coliseum and Waldorf-Astoria Hotel
Members \$1.00, Non-members \$3.00 Age limit—over 18

CUSTOMER SERVICE ENGINEERS



OUTSTANDING CAREER OPPORTUNITIES

Continued expansion of the PHILCO COMPUTER DIVISION has created a number of positions for persons with a minimum of 2 years of data processing equipment maintenance and/or installation experience.

Successful candidates will undergo advanced computer training in the PHILCO 2000 System at our Willow Grove, Pa. plant.

ASSIGNMENTS AVAILABLE IN MAJOR CITIES THROUGHOUT U.S.A.


Contact

Mr. John Felos

Professional Employment Manager

**COMPUTER DIVISION
WILLOW GROVE, PA.**

PHILCO
Famous for Quality the World Over

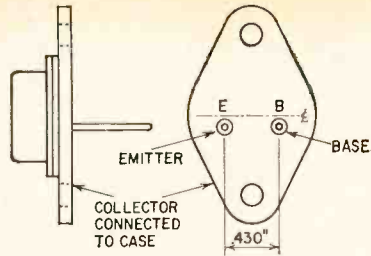

2N1136, -A, -B


Maximum ratings of these Bendix transistors are:

	2N1136	-36-A	-36-B
V_{CE}	40	70	80
V_{CE0}	30	55	65
V_{CB}	60	90	100
I_C (amps)	6	6	6
P_C (watts)	60	60	60

(P_C is the maximum average power dissipation. It can be exceeded during switching time.)

7842

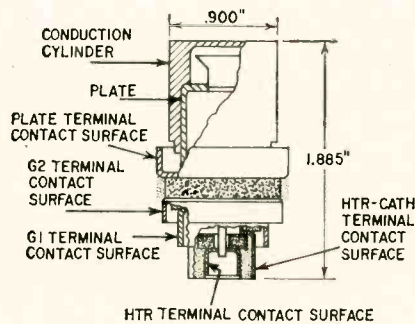A very small conduction-cooled uhf beam power tube for missiles, satellites or mobile equipment where air cooling may not be practical. It is intended for use as an rf power amplifier, oscillator, frequency multiplier, af power amplifier or modulator.




7842

Typical ratings of the RCA 7842 as an rf power amplifier in class-C FM telephony service are:

	at 400 mc		at 1215 mc
V_P	400	900	900
V_{G2}	200	300	300
V_{G1}	-35	-30	-22
I_P (ma)	150	170	170
I_{G2} (ma)	5	1	1
I_{G1} (ma)	3	10	4
Useful power output (watts)	23	80	40

2N1572, -73, -74

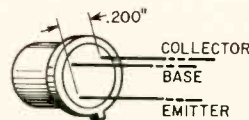A group of general-purpose n-p-n double-diffused silicon mesa transistors that cover a beta range of 20 to 200. They are well suited to use in cascaded audio amplifiers where they produce current gains between 80 and 92 db for 1-ke signals.



2N1572, 2N1573, 2N1574

Maximum ratings of these Texas Instruments transistors are:


V_{CE}	80
V_{EB}	5
P_{total} (at 25°C ambient) (watts)	0.6

Electrical characteristics at 25°C ambient are:

	2N1572	-73	-74	
h_{re}	15	30	80	($V_{CE}=5$, $I_E=-1$ ma, $f=1$ kc)
h_{oe}	25	65	95	($V_{CE}=5$, $I_E=-5$ ma, $f=1$ kc)

6DX8

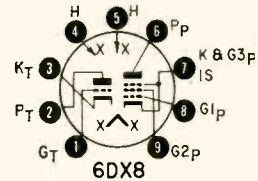A triode-pentode in a 9-pin miniature envelope. The triode is for use in keyed agc, sync separator, sync amplifier and noise suppressor circuits; the pentode for use as a video amplifier.




Typical operating conditions and characteristics for the Tung-Sol 6DX8 are:

	Triode	Pentode		
V_P	200	170	200	220
V_{G2}	—	170	200	220
V_{G1} (bias)	-1.7	-2.1	-2.9	-3.4
I_P (ma)	3	18	18	18
I_{G2} (ma)	—	3	3	3
g_m (μ mhos)	4,000	11,000	10,400	10,000
R_p (kohms)	—	100	130	150
μ	65	—	—	—
μ (G2 with respect to G1)	—	36	36	36

2N1516/OC170

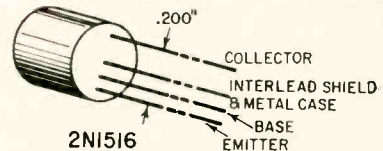A p-n-p germanium PADT (post alloy diffused transistor) designed for use as an if or rf amplifier and for oscillator-converter applications in the medium- and high-frequency ranges. Power gain at 10.7 mc is 20 db min-



imum and conversion gain at 26 mc averages 18 db.

Maximum ratings of this Amperex transistor are:


V_{CB}	20
I_C (ma)	10
I_E (ma)	10
I_E (reverse) (ma)	1
P_C (mw)	83

END

TENTH ANNUAL SSB DINNER

The SSB Amateur Radio Association will sponsor the Tenth Annual SSB Dinner and Hamfest on Tuesday, March 21 at the Hotel Statler-Hilton, 33rd St. and 7th Avenue, New York, N.Y. All amateurs and their friends are invited. There will be no formal speeches.

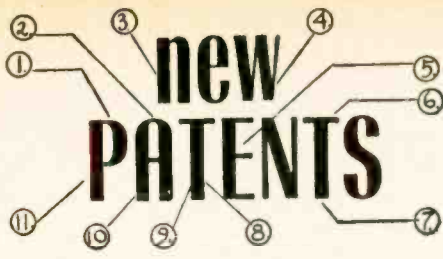Equipment displays open at 10 a.m. and the dinner starts at 7:30 p.m. Tickets purchased in advance are \$10 each and \$11 at the door.



RECTIFIER

Patent No. 2,953,738

Richard L. Bright, Adamsburg, Pa. (assigned to Westinghouse Electric Corp.)

A transistor makes an efficient rectifier. Here it is alternately biased to full conduction and to complete cutoff. In the first case, the voltage



across the transistor is nearly zero, and in the second its current is nearly zero. Therefore the power dissipation is negligible.

For highest efficiency, the bias source should supply a square-wave signal.

SENSITIVE DC AMPLIFIER

Patent No. 2,952,815

Stuart C. Rockafellow, Plymouth, Mich. (assigned to Robotron Corp., Detroit, Mich.)

Hams and others are familiar with the dip in plate current when an oscillator is tuned to resonance (Fig. 1). This principle is used here.

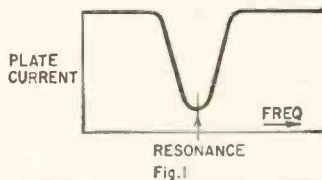


Fig. 1

In Fig. 2, the dc signal to be amplified is fed into the primary of saturable reactor T. Its secondary is the plate tank of a crystal oscillator. The secondary inductance is higher than needed

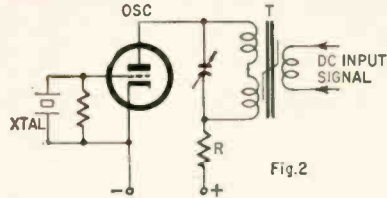


Fig. 2

for resonance. The dc tends to saturate T's core and lower the coil inductance. This causes a dip in plate current as resonance is approached.

The inventor finds that a signal of a few mv can produce a large change in the voltage drop across R. The voltage gain may be as high as 200.


BRIDGE THERMOSTAT

Patent No. 2,945,133

Balthasar Hubert Pinckaers, Hopkins, Minn. (assigned to Minneapolis-Honeywell Regulator Co., Minneapolis, Minn.)

This device is a sensitive thermostat, requiring only a single power supply. When the bridge is balanced, there is no bias between emitter and base of V1. Little current flows through R2, so V2's base is at the potential of the negative power terminal. The transistor conducts fully and energizes RY.

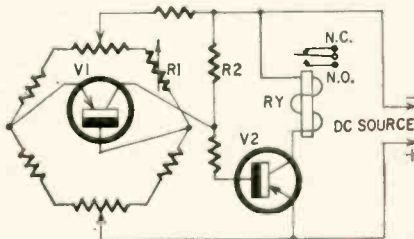R1 is a temperature-sensitive resistor whose resistance balances the bridge at some critical temperature. Below this value, R1's resistance



MAD?
... because of cold solder joints?

World's Finest
ERSIN Multicore
FIVE-CORE SOLDER

Sold only by Radio Parts Distributors.


MAKE MONEY IN SPARE TIME Learn at Home to Fix **ELECTRIC APPLIANCES**

Tester Furnished—No Extra Charge. Fix toasters, irons, fans, other electric appliances for friends and neighbors. Make money in spare time or build your own full time business. SAVE cash by repairing your own appliances. Enjoy the security of a skill to fall back on during slack periods, seasonal layoffs, when you retire. NRI will train you at home. **MAIL COUPON NOW. Sample Lesson and Catalog FREE.**

National Radio Institute, Dept. FC1, Wash. 16, D. C.
Please send me Electrical Appliance sample lesson and catalog FREE (No Salesman Will Call).

Name..... Age.....
Address.....
City..... Zone..... State.....

Just Out

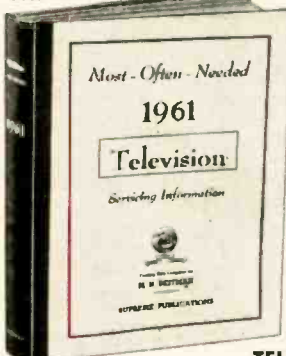

New SUPREME 1961 TV Manual

AMAZING BARGAIN

The new 1961 TV manual is the bargain of the year. Covers all important sets of every make in one giant volume. Your price for this mammoth manual is only \$3. This super-value defies all competition. Other annual volumes at only \$3 each. Factory service material simplifies repairs. Includes all data required for quicker TV servicing. Practically tells you how to find each fault and make needed repair. More pages, more diagrams, more service data per dollar of cost.

TELEVISION SERVICING COURSE

Let this new course help you in TV servicing. Amazing bargain, complete, only \$3, full price for all lessons. Giant in size, mammoth in scope, topics just like a \$200.00 correspondence course. Lessons on picture faults, circuits, adjustments, short-cuts, UHF, alignment facts, hints, antenna problems, trouble-shooting, test equipment, picture analysis. Special, only **\$3**

SIMPLIFIED RADIO SERVICING (Introduction to TV)

Explains how to use comparison method to find most radio faults in minutes. Many practical tests without any equipment. Also several sections on use of instruments. Introduction to TV. Schematics, charts, service hints. Job sheets cover all sets. New edition. Only **\$1.50**

RADIO VOLUMES



RADIO DIAGRAMS


SUPREME is your best source for all needed RADIO diagrams and service data. Covers everything from the most recent 1960 radios to pre-war old-timers; home radios, stereo combinations, transistors for portables, FM, and auto sets. Sensational values. Only \$2 for many volumes. Every manual has extra large schematics, all needed alignment facts, printed boards, voltage values, trimmers, dial stringing, and helpful hints. Volumes are large in size, 8 1/2 x 11 inches, about 190 pages. See coupon at right for a complete list of these popular radio service manuals. →

COVERS ALL POPULAR SETS

Here is your service data for faster, easier TV repairs. Lowest priced. Best by comparison. Supreme TV manuals have all needed service material on every popular TV set. Helpful, practical, factory-prepared data that will really make TV servicing easy for you. Benefit and save with these amazing values in service manuals. Only \$3 per large, yearly volume.

SIMPLIFIES TV REPAIRS

These giant TV manuals have complete circuits, needed alignment facts, printed boards, servicing hints, production changes, voltage charts, waveforms, and double-page schematics. Here are your authentic service instructions to help you do expert work quicker; and priced at only \$3 per large annual manual. Repair any TV model ever made by having in your shop all 15 volumes as listed in coupon. Your special price for all, only \$40. Or try the new 1961 TV manual to see what an amazing bargain you get for \$3. Send no-risk trial coupon today.

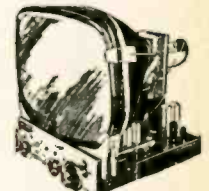

The repair of any television set is really simple with Supreme TV service manuals. Every set is covered in a practical manner that will simplify trouble-shooting and repair. This is the help you need to find toughest faults in a jiffy. Most \$3 TV volumes cover a whole year of service material. New Television Servicing Course will aid you in learning TV. Be wise, buy Supreme Manuals only once each year instead of spending dollars every week.

NO-RISK TRIAL ORDER COUPON

SUPREME PUBLICATIONS, 1760 Balsam Rd., Highland Park, ILL.

1960
 1959
 1958
 1957
 1956
 1955
 1954
 1953
 1952
 1951
 1950
 1949
 1948
 1947
 1946
 1942
 1941
 1940
 1926-1938 Manual, \$2.50
 Simplified Servicing, \$1.50

Popular RADIO Diagram Manuals at only **\$2.50** each.....
 Radio Manual, only \$2
 These annual RADIO volumes specially priced at only **\$2.50** each.....

THIS GROUP ONLY
\$2 EACH

Rush today TV manuals checked below and Radio manuals at left. Satisfaction guaranteed.

New 1961 TV Manual, \$3. 1960 TV, \$3.
 Additional 1959 TV, \$3. Early 1959 TV, \$3.
 1958 TV Manual, \$3. Additional 1957 TV, \$3.
 Early 1957 TV, \$3. 1956 TV Manual, \$3.
 Additional 1955 TV, \$3. Early 1955 TV, \$3.
 1954 TV, \$3. 1953 TV, \$3. 1952 TV, \$3.
 1951 TV, \$3. 1957-58 RCA TV Manual, \$1.50
 New Television Servicing Course, complete... \$3.

I am enclosing \$..... Send postpaid.
 Send C.O.D. I am enclosing \$.... deposit.

Name:

Address:

Supreme Publications
 Sold by All Leading Parts Jobbers

MARCH, 1961



NEW STEREO SONY STEREO TAPE DECK

Now, for less than the cost of a good record changer, you can add a versatile new dimension to your hi fi system. ■ The Sony 262-D tape deck has a 4 track stereo erase head and 4 track stereo record/playback head. Heads are wired to six output and input facilities for connection of external electronics to play and record four track stereo. This is the same quality mechanism used in the most expensive Sony Superscope tape recorders.

\$89⁵⁰

Other tape recorders in the remarkable Sony line include the dual track bantam at \$99.50, the Stereorecorder 300, a complete portable stereo portable stereo system at only \$399.50, and the 262-SL parallel and sound-on-sound recorder at \$199.50. ■ For literature or nearest dealer, write: Superscope, Inc., Dept. T, Sun Valley, Calif.

SONY SUPERSCOPE The tapeway to Stereo

drops, biasing V1 to conduction. Due to the drop across R2, V2 conducts less and RY releases its armature and the contacts close.


If desired, the relay contacts may close a circuit (not shown) to supply heat to R1. Its resistance will rise until bridge balance is restored, at which time the relay contacts will open again.

TIMING DEVICE

Patent No. 2,942,123

Niles F. Schuh, Jr., Lima, Ohio. (Assigned to Westinghouse Electric Corp., E. Pittsburgh, Pa.)

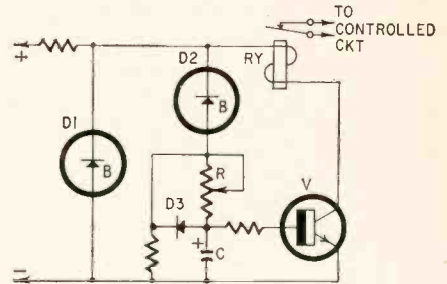This is an adjustable voltage-sensitive time-delay device. For example, it operates the relay rapidly on high overvoltages and less rapidly on



lower voltages. Thus it is insensitive to line transients.

D1, D2 are Zener diodes. D1 holds the input constant and is rated at higher voltage than D2.

Below its breakdown value, D2 is blocked. Little current flows through R into C, and any charge is wiped off by D3. After breakdown, D3 is blocked by flow through R, and C begins to charge. This biases V to conduction. Eventually, the bias will be sufficient to energize RY and end the time interval.

END

50 Years Ago

In Gernsback Publications


HUGO GERNSBACK, Founder

Modern Electrics	1908
Wireless Association of America	1908
Electrical Experimenter	1913
Radio News	1919
Science & Invention	1920
Television	1927
Radio-Craft	1929
Short-Wave Craft	1930
Television News	1931

Some larger libraries still have copies of Modern Electrics on file for interested readers.

In March, 1911, Modern Electrics

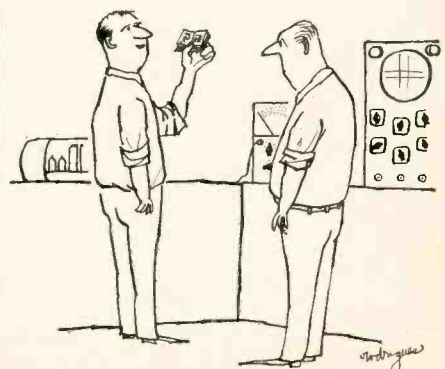- An English Thermo-Electric Generator, by Frank C. Perkins.
- Bela Gati (Radio) Experiments, by A. C. Marlowe.
- Cathode Ray Tele-Photography, by Dr. Alfred Gradenwitz (Berlin).
- A New Photophone.
- Mercury Interrupter.
- A Liquid Transmitter.
- A Handy Detector, by E. S. Stull, Jr.
- Wireless Key, by Clarence J. Carney.
- A Unique Receiving Outfit, by Stanley C. Battles.



"It's a hearing-aid service manual."

the business-like approach

to SERVICE CHARGES and RECORD KEEPING



For customer's prices on every replacement part, plus flat rate and hourly service charge data, regional and national. Dave Rice's OFFICIAL PRICING DIGEST, listing over 63,000 items. \$2.50.

AVAILABLE FROM YOUR DISTRIBUTOR

If you want to operate on a professional level, Dave Rice's OFFICIAL ORDER BOOKS give you triplicate forms for order, invoice, and office records...spaces for tubes, parts, serial numbers, labor and tax charges, signatures, etc. 75c per book, \$6.50 for dust-proof box of 10.



Dave Rice's

ELECTRONIC PUBLISHING COMPANY, INC. 180 N. WACKER DRIVE • CHICAGO 6, ILL.

Ask By Name For GENUINE your assurance of brand name quality

"NO NOISE" PRODUCTS



NO-NOISE VOLUME CONTROL and CONTACT RESTORER

- Cleans • Lubricates
- Protects • Not a Carbon Tet Solution

2 oz. Bottle \$1.00
6 oz. Spray Can \$2.25
Net to Servicemen

NO-NOISE TUNER-TONIC with PERMA-FILM

- Cleans, lubricates, restores all tuners, including water type.
- Non-toxic, non-inflammable.
- For TV, radio and FM use.
- Ecc - n - o - m - i - c - a little does a lot.



6 oz. Aerosol Can \$3.25
Net to Servicemen

FREE at your jobbers 5" PLASTIC EXTENDER

- Included With Each Can
- Push Button Assembly
- For Pin-Point Applications
- Does Not Cause Shorts




ELECTRONIC CHEMICAL CORP. 813 Communipaw Avenue Jersey City 4, N. J.

NOTEWORTHY CIRCUITS

MULTIVIBRATOR FROM SINGLE PULSER

The "Single Pulse Generator" by J. H. Thomas on page 79 of the April, 1960, issue of RADIO-ELECTRONICS was just the thing we needed in the test lab. The pulses provided by our standard pulse generators and chopper equipment were either too narrow or too wide, consequently the pulser met our requirements. However, we realized that the unit could be made more versatile by developing it into a free-running multivibrator, without resorting to additional equipment, should the necessity arise.

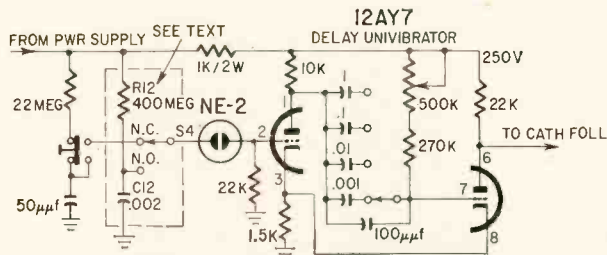

Jacks J1-J2 are specifically shown for this purpose in the original issue.

We required a repetitive pulse spaced every 100 milliseconds over the entire pulse-width scale. By trial and error we developed the circuit shown. The only additions were a two-way switch (S4), 400-megohm resistor (R12, several 22-meg units in series) and a .002- μ f capacitor, C12.

With switch S4 in the NC position, the circuit behaves as designed. In the NO position, the neon lamp oscillates at a low-frequency rate sufficient to drive the 12AY7 tube.

Before making this modification, we had difficulty trying to trigger the unit pulses to determine the pulse widths. All that is now required is to synchronize the scope to the input with the

PACKAGE HI FI or SINGLE COMPONENTS

You'll find our prices low
and service fast.

Write for our quotation
CENTER INDUSTRIAL ELECTRONICS, Inc.
74-R Cortlandt Street, New York 7, N.Y.

ENGINEERING DEGREE IN SCIENCE 27 or 36 MOS. MATH

B.S. degree—36 mos. • B.E. degree—27 mos.
Accelerated year-round program prepares for early employment in fields of Science and Engineering. Regular 4-year program for B.S. Degree completed in 36 months, special engineering degree program in 27. Classes start March, June, July, September, January. Quality education. Graduates employed from coast to coast. Government approved for veteran training. Students from 50 states, 40 countries. 20 buildings; dorms, gym. Campus. Save time and money. Earn board. Write for catalog, 1731 E. Washington Boulevard, Fort Wayne 2, Indiana

INDIANA TECHNICAL COLLEGE

HI-FI RECORDING TAPE

Splice Free (except 2400")
15 day money-back guarantee

	3	12+	24+
1200' 7" Acetate	\$1.29	\$1.17	99c
1800' 7" acetate	1.79	1.59	1.45
1800' 7" mylar	2.09	1.99	1.85
2400' 7" mylar	3.29	2.99	2.75
2400' 7" tensilized mylar	4.25	3.95	3.75

Can Be Assorted. Add 15c Postage Per Reel.
10c For 24c Lot Orders.

HI-FI COMPONENTS TAPE RECORDERS available from wide variety of stock and shipped within 24 hours. Write for free wholesale catalogue. "WE WILL NOT BE UNDERSOLD." Write us and see why.

CARSTON

125-RD East 88 St.
New York, 28, N. Y.



YOU'LL BE AMAZED...

at our low, low hi-fi prices.
Write for FREE discount catalog
A-12, or send for our special quotations on your component needs.

KEY ELECTRONICS COMPANY
120 Liberty St., New York 6, N.Y.

TV PICTURE TUBES AT LOWEST PRICES

ALL ALUMINIZED GLASS TYPES

Tube Type	Price With Old Tube	Tube Type	Price With Old Tube	Tube Type	Price With Old Tube
108P4	7.95	178JP4	11.50	21CEP4	21.00
12LP4	8.95	17CP4	11.50	21CXP4	15.75
14AJP4	14.00	17CK/CA/BZ/	21DEP4	21.00	
14ATP4	14.00	BRP4	17.00	21DFP4	21.00
14BY/CP4	10.00	17DLP4	17.00	21DLP4	21.00
14HP4	11.00	17H/RP4	12.50	21DSP4	21.00
14QP4	11.00	17L/VP4	12.50	21EP4	14.25
14RP4	11.00	17QP4	11.50	21FP4	14.50
14W/ZP4	11.00	20C/DP4	13.50	21WP4	16.00
14XK4	11.60	20H/MP4	14.50	21XP4	16.50
16DP4	12.00	21AC/B5/	21YP4	16.00	
16K/RP4	9.95	AMP4	15.75	21ZP4	15.50
16LP4	12.50	21AL/ATP4	24C/VP4	23.50	
16TP4	9.95	21ALP4	16.75	24EP4	24.50
16WP4	12.00	21AU/AVP4	24HP4	26.50	
17AT/AVP4	12.50	21AWP4	15.75	24DP4	24.50
17BP4	9.95	21BTP4	16.75	27EP4	39.95
		21CBP4	16.75	27RP4	39.95
				27SP4	40.95

METAL TYPES

12UP4	12.00	16GP4	14.50	19AP4	16.00
16AP4	13.50	17CP4	17.00	21AP4	19.75
16EP4	14.00	17GP4	17.60	21MP4	20.75
		17TP4	17.60		

TEST TUBES

8XP4	16.07	8YP4	16.07
------	-------	------	-------

1 year warranty

Prices include the return of an acceptable similar tube under vacuum. These tubes are manufactured from

reprocessed used glass bulbs. All parts and materials including the electron gun are brand new.

ALL PRICES FOR CHICAGO, ILLINOIS. Deposit required when old tube is not returned, refundable at time of return. 25% deposit required on COD shipments. Old tubes must be returned prepaid. Tubes shipped Rail Express. Shipped only to Continental U.S. and Canada.

WRITE FOR COMPLETE LIST

—PICTURE TUBE OUTLET—
2922 MILWAUKEE AVE., CHICAGO 18, ILLINOIS
Dickens 2-2048

NEW 4-WAY POCKET TOOL

a real "working partner"
for removing backs of TV sets
and installing antennas



1 It's a 1/4" nut driver!
Fits Parker-Kalon screws.


Genuine Xcelite
plastic handle —
shaped and
balanced for
working ease.
Equipped with
pocket clip.

2 It's a 7/16"
nut driver!
Ideal for
antenna
installations.

3 It's a No. 1
Phillips
screwdriver!

Double-end blade
inserts in 7/16" hex
opening. Just push
it in or pull it out!
Patented spring
holds it firm.

4 It's a 3/16"
slotted screwdriver!

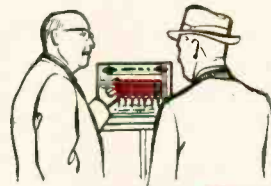

Ask to see
"No. 600"
next time you
pick up parts...

XCELITE

XCELITE, INC. • ORCHARD PARK, N.Y.
Canada: Charles W. Pointon, Ltd., Toronto, Ont.



For that
NEW IDEA
 visit the
IRE SHOW

March 20-23, 1961 New York
 Coliseum and Waldorf-Astoria Hotel
 Members \$1.00, Non-members \$3.00 Age limit—over 18



**DON'T
 THROW
 OLD RADIOS
 AWAY!**

Here's the data
 you need to fix
 them **FAST ...** and
 good as new!

Just look up the how-to-do-it data on that old radio you want to fix!

Four times out of 5, this giant, 3½-pound, 744-page Ghirdard **RADIO TROUBLESHOOTER'S HANDBOOK** gives exactly the information you need to fix it in a jiffy. Tells what is likely to be causing the trouble ... shows how to fix it. No useless test-tune. No wasted time. Handbook covers practically every radio receiver model made by 202 manufacturers between 1925 and 1942. Using it, even beginners can easily fix old sets which might otherwise be thrown away because service information is lacking. With a few simple repairs, most of these old sets can be made to operate perfectly for years to come.

THE ONLY GUIDE OF ITS KIND
Cuts service time in half!

Included are common trouble symptoms and their remedies for over 4,800 models of old home, auto radios and record changers; Airline, Apex, Arvin, Atwater Kent, Belmont, Bosen, Brunswick, Clarion, Crosley, Emerson, Fada, G. E., Kolster, Majestic, Motorola, Philco, Pilot, RCA, Silvertone, Sparton, Stromberg and dozens more. Includes hundreds of pages of invaluable tube and component data, service short cuts, etc.

TRY IT 10 DAYS ... see for yourself!

Dept. RE-31, Technical Division
HOLT, RINEHART and WINSTON, Inc.
 383 Madison Ave., New York 17, N.Y.

Send Ghirdard's **RADIO TROUBLESHOOTER'S HANDBOOK** for 10-day free examination. If I decide to keep book, I will remit the full price of only \$10 plus postage. Otherwise, I will return book postpaid and owe you nothing. (SAVE! Send \$10 with order and we pay postage. Same return privilege with money refunded.)

NAME.....
 ADDRESS.....
 CITY, ZONE, STATE.....
 OUTSIDE U.S.A.—Price \$10.50 cash with order only.
 Money back if book is returned in 10 days.



the first, the quality, the proved silencing "Lubri-Cleaner" for noisy controls and switches on TV, radio and electronic instruments. **SPRAY IT OR DROP IT ... it's easy—efficient—effective.** Make **QUIETROLE** your silent partner in providing satisfactory service.


manufactured by
QUIETROLE Company
 SPARTANBURG, South Carolina
 In Canada: **CROSS CANADA ELECTRONICS**
 12 Laurel St., Waterloo, Ont.

switch in the NO position, examine the pulse, then flip the switch back to NC position.—M. A. Suntop

**100-MC TRANSISTOR
 OSCILLATOR**

It wasn't too many years ago that special techniques were required to get an ordinary receiving tube to oscillate above 100 mc. Now, we have a number of transistors that operate readily at frequencies exceeding 200 mc. The Philco data sheet on the 2N1158-A MADT type transistor shows several power oscillator circuits for 70, 100 and 200 mc. The circuits feature high efficiency and good temperature stability.

The circuit of the 100-mc oscillator

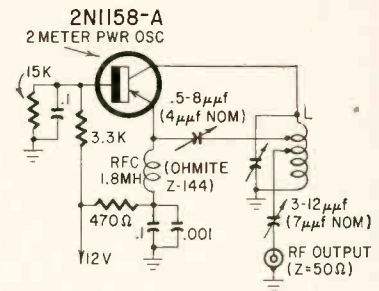


shown can be used on the 2-meter amateur band. With collector current of 9 ma, power output is 16, 24 and 32 milliwatts when V_{CE} equals 6, 8 and 10 volts, respectively. Coil L consists of 5 turns of No. 608T Air Dux with the emitter feedback tap at 4 turns and the output tap at 3½ turns from ground. The feedback capacitor should be adjusted for maximum power output at the supply voltage used.

At 100 mc, the frequency drift (negative) does not exceed 250 kc over a temperature range of 20 to 60° C. With supply voltage variations between 4 and 17 volts, the oscillator does not drift more than 1 mc.

REGENERATIVE SUPERHET

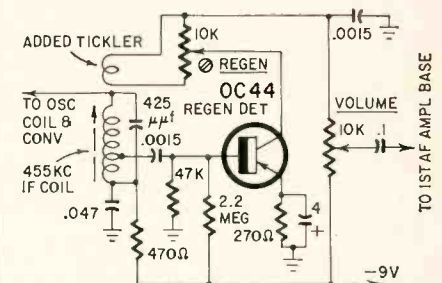
In the 1930's regenerative second detectors were sometimes used in simple superhets for increased sensitivity and selectivity. When adjusted close to the point of oscillation, the regenerative detector may provide as much gain and selectivity as two or three stages of if amplification.



A similar trick was used in a four-transistor superhet described in *Radio, Television & Hobbies* (Australia). The circuit is shown. Regenerative feedback for the OC44 detector was provided by adding a tickler winding to the if coil. Performance is optimum with the regeneration control set just short of the point of oscillation. END


BUSINESS and PEOPLE

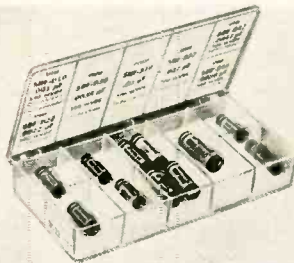Sprague Products Co., North Adams, Mass., is now packaging two specially selected assortments of its Isofarad capacitors for electronic service tech-




nicians in hinged, compartmented clear plastic cases. Specially selected assortments of its Difilm Orange Drop radial-lead dipped tubular capacitors are being packaged in metal file-drawer cabinets.

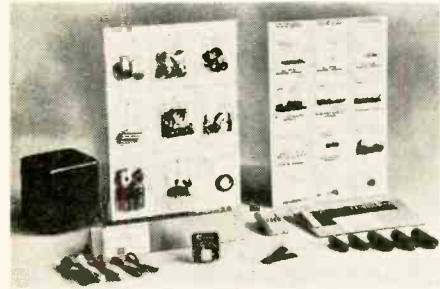Harman-Kardon, Plainview, N. Y., has been cited by the editors of the Seventh Annual Design Review of *Industrial*



Design Magazine for its Citation II 120-watt stereo high-fidelity power amplifier kit which was designed by Stewart Hegeman.

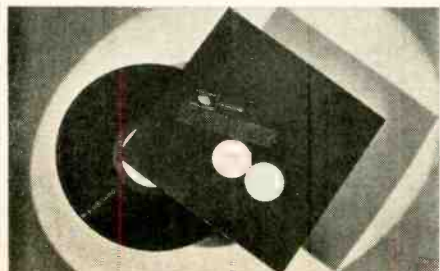Shure Bros., Evanston, Ill., produced a privately commissioned stereo record, "The Orchestra . . . The Instruments," which shows the spatial relationships of



BRAND NEW UNITED'S FIRST QUALITY TUBES DISCOUNTS up to 80% OFF GUARANTEED ONE FULL YEAR! NOT USED! NO PULLS! WHY PAY MORE?

Qty.	Tube	Price	Qty.	Tube	Price	Qty.	Tube	Price	Qty.	Tube	Price	Qty.	Tube	Price	Qty.	Tube	Price	Qty.	Tube	Price
024	044	.69	30T6	.49	6AL7	1.35	6CB6	.53	7AD7	.80	12CN5	.55	25B06	1.00						
1A5	.61	30A	.58	6AM8	.77	6CDDG	1.20	7A7	.70	12CR6	.53	17DQ6	1.00							
1A7	.61	30S	.79	6AN8	.84	6CDDG	1.20	7A7	.60	12CT8	.90	17L6	.57							
1AX2	.61	354	.60	6AQ5	.49	6CF6	.63	7C5	.80	12CX6	.90	17H3	.50							
1B3	.74	3V4	.57	6AQ6	.60	6CG7	.59	7EY6	.75	12DB8	.68	18A5	.90							
1C5	1.02	4AU6	.54	6AR5	.54	6G08	.76	7F7	.75	12DE8	.74	18FW6	.49							
1C3	.70	4BA6	.54	6AS5	.59	6CM7	.65	8AU8	.82	12DL8	.74	18FV6	.40							
1H5	.75	4BC8	.95	6AS6	2.25	6CN7	.64	8AW8	.92	12DQ6	1.00	18U4	.80							
1J3	.72	4BN6	.75	6AS8	.85	6CR6	.50	8C7	.61	12DT5	.72	19B6	1.30							
1K3	.70	4BQ7	.95	6AT6	.42	6CS6	.56	8M7	.67	12DZ6	.55	19T8	.78							
1L4	.60	4BS8	.97	6AU4	.81	6CY5	.70	8N7	.65	12EG6	.53	21EX6	1.40							
1LA4	.99	4BU8	.70	6AU5	1.05	6CU5	.57	8CX8	.90	12EK6	.57	25A4	.71							
1LA6	.99	4BZ6	.57	6AU6	.49	6CX8	.90	8E88	.93	12EL6	.49	25B06	1.00							
1L84	.99	4BZ7	.57	6AU7	.60	6CY5	.70	8L8	.75	12EZ6	.52	25C06	.70							
1LC6	.99	4C86	.57	6AU8	.86	6CY7	.70	10C8	.99	12F5	.49	GB	1.20							
1LD5	.99	4C56	.60	6AV5	.97	6DE6	.57	10DE7	.72	12F8	.65	25C06	.70							
1LE3	.99	4E27	.57	6AU7	.60	6E7	.50	11C7	.74	12FA6	.49	GB	1.40							
1LG5	.99	4DE6	.61	6AW8	.88	6DN6	1.40	12A6	.69	12FA6	.44	25D6	1.35							
1LH4	.99	4DT6	.54	6AX4	.64	6DN7	.85	12ABG	.85	12FB8	.44	25L6	.56							
1LN5	.57	5AT8	.79	6AX5	.75	6E8	1.00	12AB5	.54	12FX8	.85	25W4	.67							
1NS	.90	5AN8	.85	6BA6	.48	6D55	.65	12AC6	.68	12G6	1.05	25Z6	.65							
1SA6	1.10	5AQ5	.51	6BA7	.92	6DT6	.52	12AD6	.56	12H6	.61	32E75	.52							
1RS	.61	5AT8	.79	6BA8	.91	6EA8	.78	12AE6	.42	12I6	.61	32L7	.89							
1S4	.75	5AV8	1.00	6BC5	.54	6EA8	.90	12AF3	.72	12JA7	.75	35B5	.65							
1S5	.50	5B8	.96	6BC7	.93	6E08	.78	12AF6	.48	12K5	.64	35C5	.50							
1T3	.57	5BK7	.81	6BC8	.96	6E6W	.55	12AG6	.45	12K5	.75	35L6G	.65							
1U4	.57	5BQ7	.96	6BD6	.50	6F6	.85	12AL5	.44	12K5	.75	35LGT	.59							
1U5	.49	5BR8	.78	6BE6	.54	6H6	.55	12AL8	.94	12S7	.75	35W4	.49							
1V2	.99	5CG8	.75	6BF5	.88	6J5G	.35	12AT6	.42	12S7	.75	35Z7	.59							
1X2	.75	5EA8	.77	6BF6	.43	6J5GT	1.00	12AT7	.75	12S7	.66	36AM3	.49							
2AF4	.95	5EU8	.79	6BG6G	1.00	6J6	.66	12AT7	.75	12S7	.66	40B2	1.50							
2B3	1.00	5J6	.67	6BG6G	1.00	6J7	.85	12A7	.59	12U7	.61	50C5	.52							
2B4	.63	5T8	.80	6BH6	.64	6K6	.58	12AV6	.40	12V6	.52	50E5	.54							
2CY5	.70	5U4	.59	6BH8	.96	6L6	1.10	12AV6	.40	12W6	.68	50L6	.60							
2D21	1.15	5U8	.80	6BJ6	.61	6S4	.47	12AV7	.74	12X4	.37	70L6	.75							
3A3	.84	5V4	.82	6BK5	.85	6S47	.75	12AV7	.66	14H7	.80	70L7	.85							
3A4	.55	5V6	.55	6BK7	.84	6SC7	.75	12AX4	.74	14N7	.80	17L3	.60							
3AF4	1.02	5W4	.95	6BL7	.99	6SF5-GT	.43	12AX7	.62	17AQ6	1.00	807	.69							
3AL5	.41	5X4	.78	6BN4	.56	6SG7-GT	.40	12AY7	1.44	17BQ6	1.00	807	.69							
3A06	.50	5X8	.77	6BN6	.73	6SH7-GT	.47	12AZ7	.62	17BQ6	1.00	807	.69							
3A76	.40	5Y3	.45	6BQ5	.59	6SJ7	.75	12B4	.62	17BQ6	1.00	807	.69							
3B2	1.50	5Y4	.77	6BQ6	1.00	6SK7	1.00	12BA6	.49	17BQ6	1.00	807	.69							
3B6	.50	6A7	1.10	6CUE	1.00	6T	3/1.00	12BA7	.95	17BQ6	1.00	807	.69							
3BC5	.53	6A8	1.15	6CUE	1.00	6T	3/1.00	12BA7	.95	17BQ6	1.00	807	.69							
3BE6	.51	6A84	.45	6BR8	.77	6S17	.79	12BE5	.52	17BQ6	1.00	807	.69							
3BN4	.63	6AC7	.92	6BS8	.93	6S7	.84	12BF6	.43	17BQ6	1.00	807	.69							
3BN6	.75	6AF3	.96	6B8	.69	6S7	.84	12BH7	.72	17BQ6	1.00	807	.69							
3BU8	.70	6AF4	.96	6BX7	1.02	6U8	.77	12BQ6	1.00	17BQ6	1.00	807	.69							
3B6	.54	6AF4A	.96	6BY6	.56	6V6	.53	12CUE	1.00	17BQ6	1.00	807	.69							
3CB6	.53	6AG7	.75	6BZ6	.54	6W6	.60	12DR7	.70	17BQ6	1.00	807	.69							
3CF6	.59	6AH4	.82	6BZ8	1.05	6X4	.38	12BY7	.73	17BQ6	1.00	807	.69							
3C56	.51	6AH6	.98	6C4	.42	6X5	.51	12BZ7	.74	17BQ6	1.00	807	.69							
3CY5	.70	6AK5	3/51	6CS-GT	.75	6X8	.75	12C5	.55	17BQ6	1.00	807	.69							
3DK6	.59	6AL5	.46	6CS-M	.90	7A7	.68	12C5	.55	17BQ6	1.00	807	.69							

UNITED RADIO CO.

ESTABLISHED 1920

Send for complete parts catalog, FREE. Use ad as your order blank. TERMS: remit full price plus postage with order. No COD. Excess postage will be refunded.

Subject to Prior Sale \$5 MINIMUM ORDER

What articles would you like to see published in RADIO-ELECTRONICS? Maybe you're the man to write them. Ask for an author's guide.

RADIO-ELECTRONICS

154 West 14th St. New York 11, N. Y.

ELECTRONICS

Engineering-Technicians

Bachelor of Science Degree, 30 Months
Save Two Years' Time

- Radio-Television Plus Color Technician (12 Months)
- Electronics Technician (12 Months)
- Industrial Electronics Technician (12 Months)
- Electronics Engineering (B.S. Degree)
- Electrical Engineering (B.S. Degree)
- Mechanical Engineering (B.S. Degree)
- Civil Engineering (B.S. Degree)
- Architecture (B.S. Degree)

Missile headed for outer space. Courtesy of Space Technology Laboratories, Inc.


U.S. Air Force Photo

Heald College ranks FIRST West of the Mississippi in "Who's Who in America"

Approved for Veterans
DAY AND EVENING CLASSES
Write for Catalog and Registration Application.
New Term Starting Soon.

Your Name _____
Address _____
City _____
State _____

Now—24-Hour Tuner Service

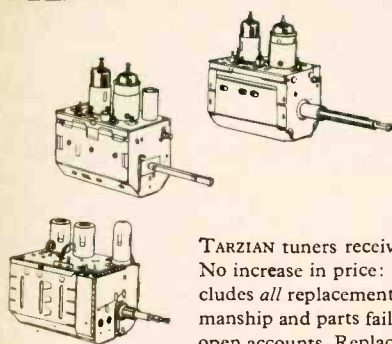

**Tarzian Offers 24-hour
Direct Factory Service
on TUNER REPAIRS
... \$8.50**

TARZIAN tuners received one day will be repaired and shipped out the next. No increase in price: \$8.50 per unit and \$15 for UV combinations. That includes all replacement parts, and a 6-month warranty against defective workmanship and parts failure due to normal usage. Tuners repaired on approved, open accounts. Replacements available at low cost on tuners beyond practical repair.

Tarzian-made tuners easily identified by this stamping. When inquiring about service on other than Tarzian-made tuners, always give tube complement . . . shaft length . . . filament voltage . . . series or shunt heater . . . IF frequency . . . chassis identification. And, allow a little more time for service on these tuners. Use this address for fast, factory repair service:

SERVICE MANAGER • TUNER DIVISION Dept. C



SARKES TARZIAN INC

east hillside drive
bloomington, indiana
edison 2-7251

Mfgs. of Tuners, Semiconductors, Air Trimmers, FM Radios, Audio Tape, and Broadcast Equipment

FREE! CATALOG OF
HI-FI, RADIO, TV
PARTS & ACCESSORIES —
yours for the asking!

Vidaire ELECTRONICS MFG. CORP.
365 BABYLON TPKE. — ROOSEVELT, N. Y.

VHF & UHF TV TRANSLATORS
Closed Circuit TV Cameras
Micro Wave Relays for
Broadcast & Business
Amateur TV Equipment

INDUSTRIAL TELEVISION CO.
7270 Beverly Blvd. Los Angeles 36, Calif.

IT'S NEW
IT'S COMPLETE
IT'S YOURS

PRECISION PACE CATALOG
of Electronic
Test Equipment
and Panel Meters for
INDUSTRY
COMMUNICATIONS
SERVICE

Write on your company letterhead to:
PRECISION Apparatus Company, Inc.
(A subsidiary of Pacotronics, Inc.)
70-31 84th Street, Glendale 27, L. I., N. Y.

**Purchasing
A HI-FI
SYSTEM?**

TIME PAYMENTS AVAILABLE
Up to 2 years to pay!

Send Us
Your
List Of
Components
For A
Package
Quotation

You Can Buy
With Confidence
AT AIREX

All merchandise is
brand new, factory
fresh & guaranteed.

Free Hi-Fi Catalog

**AIREX
RADIO
CORPORATION**

85-RE Cortlandt St., N.Y. 7, CO 7-2137


Jim Lansing*
Altec Lansing
Electrovoice
Superscope
Hartley • Viking
University • Jensen
Acoustic Research
Janszen
Wharfedale
USL Citizen Band
Gonset • Hallicrafter
Texas Crystals
Concertone
Bell • G.E.
Weathers
Harman-Kardon
Eico • Pilot
ESL
Superscope
Dual Changer
Bogen • Leak
Dynakit • Fisher
H. H. Scott
Thorens* Sherwood*
TEC • Roberts
DeWald
Sony • Tandberg*
Challenger
Wollensak
Garrard
Miracord
Glaser-Steers
Rek-O-Kut
Components
Norelco • Conrac
Fairchild
Pickering • Gray
Audio Tape
Magnecord*
Artizan Cabinets
Rockford Cabinets
*Fair Traded

the instruments in the orchestra. The recording, by Westminster Recording Co., is available only to purchasers of Shure's M3D and M7D cartridge, Stereo Studio Dynetic integrated tone arm and cartridge or Professional tone arm.

Cornell-Dubilier Electronics Div., Federal Pacific Electric Co., Newark, N. J., designed a Pik-A-Pak display rack for distributors who purchase a selection of its most popular capacitors. It holds 5,000 capacitors in less than 3 square feet of floor space.



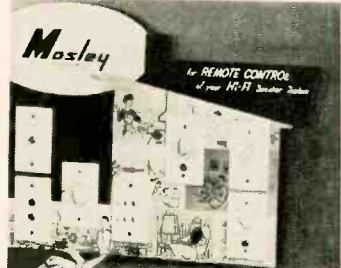Mosley Electronics, Bridgeton (St. Louis), Mo., developed a colorful new point-of-purchase display showing its



complete line of audio control plates, including speaker switches, attenuator plates and speaker wall outlets.

William E. Wilson (below left) has been named vice president and general manager of the Chicago Standard



Transformer Div. of the Essex Wire Corp., Chicago. Jack D. Hall (above right) becomes vice president, sales and marketing, and Karl F. Crease (right), vice president in charge of manufacturing. All three have extensive experience in the transformer industry.



Frank M. Hickey was promoted to manager, industrial products sales, for CBS Electronics, Danvers, Mass. In his previous assignment he was merchandising manager, industrial products.



Donald Jonson has been named distributor sales manager of the Columbia Wire & Supply Co., Chicago. He has had wide experience in sales to radio and



TV parts distributors and was previously with General Cement and with Erie Resistor.

George C. Isham, manager of marketing services for Sylvania's Electronic Tube Div., was presented with a gold watch marking his 25th anniversary



with the company. Robert E. Lewis (right), president of Sylvania, is shown making the presentation at the company's distributor sales meeting in Bal Harbour, Florida.

Seymour S. Sadowsky was appointed to a newly created position in the General Electric Cathode-Ray Tube Dept., Syracuse, N. Y. He will provide technical liaison between field requirements for replacement picture tubes and development engineering, concentrating on distribution and installation of replacement tubes.




	1960	1959
TV Retail Sales	5,176,905	5,046,971
Radio Retail Sales*	8,326,275	7,142,424
TV Production	5,302,877	5,756,210
Radio Production	15,604,784	14,069,049
Picture-Tube		
Factory Sales	8,481,924	8,705,759
Receiving-Tube		
Factory Sales	365,989,000	395,688,000

*Excluding auto.

Irwin K. Paul was promoted to assistant sales manager of Arco Electronics Inc., New York. He joined the company last June and was formerly with Sprague Products Co. and Aerovox Corp.



END

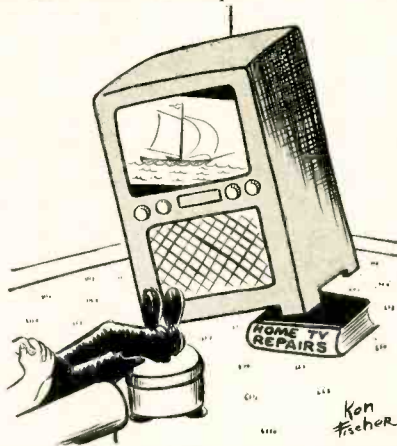

MAIL COUPON TODAY!

Find out how you can get this book *free!*

the V.T.V.M. by Rhys Samuel published at \$2.50—contains a wealth of information on how the V.T.V.M. works... how to use it. Send for particulars on how to get this valuable book.

Mail to Dept. RE3
General Techniques, Inc.
Manufacturers of Quality Electronic Kits
1270 Broadway, New York City 1, N. Y.

Name.....
Address.....
City..... Zone..... State.....

LOOKING?—you stand a better chance of finding what you want if you advertise in RADIO-ELECTRONICS Opportunity Adlets. See details on page 128.

"ONE DOLLAR BUYS"

As Much as \$15 worth—Everything Brand New and sold to you with a money back guarantee
Pick — ANY 1 DOLLAR BUY FREE with every 10 you buy.
FREE GIFT — with every Order of \$5.00 or over.

HANDY WAY TO ORDER—Simply tear out advertisement and pencil mark items wanted. (Dot in square is sufficient). Enclose with money order or check. You will receive a new copy of this ad for re-orders. ON SMALL ORDERS—Include stamps for postage, excess will be refunded. Larger orders shipped express collect.

- | | | |
|---|--|--|
| <ul style="list-style-type: none"> <input type="checkbox"/> 10 — DIODE CRYSTALS 1N34A.....\$1 <input type="checkbox"/> 5 — DIODE CRYSTALS 1N60.....\$1 <input type="checkbox"/> 100 — ASST. CERAMIC CONDENSERS.....\$1 <input type="checkbox"/> 100 — ASST. 1/2 WATT RESISTORS some 5%.....\$1 <input type="checkbox"/> 70 — ASSORTED 1 WATT RESISTORS.....\$1 <input type="checkbox"/> 35 — ASSORTED 2 WATT RESISTORS.....\$1 <input type="checkbox"/> 50 — ASST. TUBULAR CONDENSERS.....\$1 <input type="checkbox"/> 50 — CONDENSERS .01-500v.....\$1 <input type="checkbox"/> 50 — ASSORTED FUSES popular sizes.....\$1 <input type="checkbox"/> 75 — 100Ω 1/2 WATT RESISTORS 10%.....\$1 <input type="checkbox"/> 50 — 470KΩ 1/2 WATT RESISTORS 10%.....\$1 <input type="checkbox"/> 100 — 5AG FUSES 2 amp 1 1/2"x3/4".....\$1 <input type="checkbox"/> 100 — 5AG FUSES 20 amp 1 1/2"x3/4".....\$1 <input type="checkbox"/> 100 — 5AG FUSES (50 2 amp & 50 20 amp).....\$1 <input type="checkbox"/> 5 — DIODE CRYSTALS 1N84.....\$1 <input type="checkbox"/> 5 — DIODE CRYSTALS 1N69.....\$1 <input type="checkbox"/> 10 — ASST. WIRE'ND RES. 5, 10, 20 watt.....\$1 <input type="checkbox"/> 10 — HY TUBULAR CONDENSERS 006-1000v.....\$1 <input type="checkbox"/> 35 — ASST. DISC CERAMICS best numbers.....\$1 <input type="checkbox"/> 50 — ASST. MICA CONDENSERS some in 5%.....\$1 <input type="checkbox"/> 6 — ASST. SLIDE SWITCHES ass't. dpdt, etc.....\$1 <input type="checkbox"/> 3 — ASST. TOGGLE SWITCHES spst, dpdt, etc.....\$1 <input type="checkbox"/> 15 — ASST. ROTARY SWITCHES \$15 worth.....\$1 <input type="checkbox"/> 100 — FINEST NYLON DIAL CORD best size.....\$1 <input type="checkbox"/> 200 — SELF TAPPING SCREWS #8 x 1/2".....\$1 <input type="checkbox"/> 35 — ASST. RADIO KNOBS screw and push-on.....\$1 <input type="checkbox"/> 100 — ASSORTED KNOB SET-SCREWS.....\$1 <input type="checkbox"/> 25 — ASSORTED CLOCK RADIO KNOBS.....\$1 <input type="checkbox"/> 35 — ASST. SOCKETS octal, novak and miniature.....\$1 <input type="checkbox"/> 25 — ASST. PRINTED CIRCUIT SOCKETS.....\$1 <input type="checkbox"/> 10 — ASST. VOLUME CONTROLS less switch.....\$1 <input type="checkbox"/> 5 — ASST. VOLUME CONTROLS with switch.....\$1 <input type="checkbox"/> 10 — 50K VOLUME CONTROLS less switch.....\$1 <input type="checkbox"/> 20 — ASST. PILOT LIGHTS popular types.....\$1 <input type="checkbox"/> 10 — PILOT LIGHT SKTS bayonet type, wired.....\$1 <input type="checkbox"/> 50 — ASST. TERMINAL STRIPS 1, 2, 3, 4 lug.....\$1 <input type="checkbox"/> 10 — ASST. RADIO ELECTRO. CONDENSERS.....\$1 <input type="checkbox"/> 5 — ASST. TV ELECTROLYTIC CONDENSERS.....\$1 <input type="checkbox"/> 15 — TUBULAR CONDENSERS 1-600v.....\$1 <input type="checkbox"/> 15 — TUBULAR CONDENSERS .047-600v.....\$1 <input type="checkbox"/> 15 — TUBULAR CONDENSERS .47-400v.....\$1 <input type="checkbox"/> 2 — ELECTROLYTIC COND. 40,40-450v.....\$1 <input type="checkbox"/> 3 — ELECTROLYTIC COND. 50,30-150v.....\$1 <input type="checkbox"/> 35 — DISC CERAMIC CONDENSERS 5000mmf.....\$1 <input type="checkbox"/> 25 — ASST. RADIO DIAL POINTERS.....\$1 <input type="checkbox"/> 600 — ASST. H'DWARE screws, nuts, rivets, etc.....\$1 <input type="checkbox"/> 8 — ASST. LUCITE CASES handy for parts.....\$1 | <ul style="list-style-type: none"> <input type="checkbox"/> 2 — MICROPHONES 200 ohms, hi-gain.....\$1 <input type="checkbox"/> 4 — AUDIO OUTPUT TRANS. 50L8 type.....\$1 <input type="checkbox"/> 1 — 5" PM SPEAKER alnico #5 magnet.....\$1 <input type="checkbox"/> 1 — 4" PM SPEAKER alnico #5 magnet.....\$1 <input type="checkbox"/> 1 — 3" PM SPEAKER alnico #5 magnet.....\$1 <input type="checkbox"/> 1 — 3 1/2" TWEETER SPEAKER for HI-FI.....\$1 <input type="checkbox"/> 5 — SETS SPEAKER PLUGS wired.....\$1 <input type="checkbox"/> 3 — AUDIO OUTPUT TRANS. 6K6 or 6V8 type.....\$1 <input type="checkbox"/> 3 — I.F. COIL TRANSFORMERS 456 kc.....\$1 <input type="checkbox"/> 3 — I.F. COIL TRANSFORMERS 10.7 mc. FM.....\$1 <input type="checkbox"/> 3 — I.F. COIL TRANSFORMERS 282 kc (auto).....\$1 <input type="checkbox"/> 40 — ASST. PRECISION RESISTORS best sizes.....\$1 <input type="checkbox"/> 100 — MICA CONDENSERS 820 mmf.....\$1 <input type="checkbox"/> 5 — SELENIUM RECTIFIERS 65ma list \$1.50 ea.....\$1 <input type="checkbox"/> 4 — SELENIUM RECTIFIERS 75ma.....\$1 <input type="checkbox"/> 3 — SELENIUM RECTIFIERS 100ma.....\$1 <input type="checkbox"/> 2 — SELENIUM RECTIFIERS 300ma.....\$1 <input type="checkbox"/> 2 — SELENIUM RECTIFIERS 1-350ma 1-75ma.....\$1 <input type="checkbox"/> 1 — SELENIUM RECTIFIER 500 ma.....\$1 <input type="checkbox"/> 3 — ASST. SIZES RADIO CHASSIS PANS.....\$1 <input type="checkbox"/> 3 — VARIABLE CONDENSERS super 420/102mmf.....\$1 <input type="checkbox"/> 50 — STRIPS ASST. SPAGHETTI best sizes.....\$1 <input type="checkbox"/> 100 — ASST. RUBBER GROMMETS best sizes.....\$1 <input type="checkbox"/> 4 — OVAL LOOP ANTENNAS ass't hi-gain types.....\$1 <input type="checkbox"/> 3 — LOOPSTICK ANT. new ferrite adjustable.....\$1 <input type="checkbox"/> 3 — 1/2 MEG VOLUME CONTROLS with switch.....\$1 <input type="checkbox"/> 5 — ASST. 4 WATT WIREWOUND CONTROLS.....\$1 <input type="checkbox"/> 5 — 1/2 MEG VOLUME CONTROLS less switch.....\$1 <input type="checkbox"/> 5 — 1 or 2 MEG VOLUME CONTROLS 1/switch.....\$1 <input type="checkbox"/> 10 — SURE GRIP ALLIGATOR CLIPS.....\$1 <input type="checkbox"/> 1 — GOLD GRILLE CLOTH 14"x14" or 12"x18".....\$1 <input type="checkbox"/> 10 — SETS PHONO PLUGS and PIN JACKS.....\$1 <input type="checkbox"/> 2 — \$2.50 SAPPHIRE NEEDLES 4000 playings.....\$1 <input type="checkbox"/> 3 — ELECTROLYTIC CONDENSERS 80-400v.....\$1 <input type="checkbox"/> 35 — MICA COND. 20-50 mmf & 15-68 mmf.....\$1 <input type="checkbox"/> 35 — MICA COND. 20-100 mmf & 15-270 mmf.....\$1 <input type="checkbox"/> 35 — MICA COND. 20-470 mmf & 15-680 mmf.....\$1 <input type="checkbox"/> 35 — MICA COND. 20-820 mmf & 15-1000 mmf.....\$1 <input type="checkbox"/> 35 — MICA COND. 20-2200 mmf & 15-2400 mmf.....\$1 <input type="checkbox"/> 35 — MICA COND. 20-6800 mmf & 15-10000 mmf.....\$1 <input type="checkbox"/> 35 — CERAMIC COND. 20-5 mmf & 15-10 mmf.....\$1 <input type="checkbox"/> 35 — CERAMIC COND. 20-25 mmf & 15-47 mmf.....\$1 <input type="checkbox"/> 35 — CERAMIC COND. 20-56 mmf & 15-82 mmf.....\$1 <input type="checkbox"/> 35 — CERAMIC COND. 20-100 mmf & 15-150 mmf.....\$1 <input type="checkbox"/> 35 — CERAMIC COND. 20-270 mmf & 15-470 mmf.....\$1 <input type="checkbox"/> 35 — CERAMIC COND. 20-1000 mmf & 15-1500 mmf.....\$1 <input type="checkbox"/> 35 — CERAMIC COND. 20-2000 mmf & 15-5000 mmf.....\$1 | <ul style="list-style-type: none"> <input type="checkbox"/> \$15 — "JACKPOT" TELEVISION PARTS.....\$1 <input type="checkbox"/> 10 — TOP NAME 1U4 TUBES also serves as 1T4.....\$1 <input type="checkbox"/> 4 — KENRAD 6SH7 TUBES.....\$1 <input type="checkbox"/> 3 — 6AL5 unbranded, perfect.....\$1 <input type="checkbox"/> 2 — TOP NAME 6SQ7 TUBES.....\$1 <input type="checkbox"/> 2 — GENERAL ELECTRIC TUBES #35W4.....\$1 TOP NAME TUBES OZ4, 1B3, 1X2B, 5U4, 6AC7, 6AX4, 6CB6, 6J6, 6K6, 6U8, 6V6, 6SN7, 6X8, 12AU7, 12AX7, 50L6.....Each \$1 <input type="checkbox"/> 1 — ELECTRIC PHONO MOTOR 78rpm. comp.....\$1 <input type="checkbox"/> 12 — RADIO OSCILLATOR COILS 456 kc.....\$1 <input type="checkbox"/> 1 — LB. SPOOL ROSIN CORE SOLDER.....\$1 <input type="checkbox"/> 4 — 50' SPOOLS HOOK-UP WIRE 4 colors.....\$1 <input type="checkbox"/> 10 — 6' ELECTRIC LINE CORDS with plugs.....\$1 <input type="checkbox"/> 5 — TV CHEATER CORDS with both plugs.....\$1 <input type="checkbox"/> 5 — TV CRT. SOCKETS with 18" leads.....\$1 <input type="checkbox"/> 5 — HI-VOLT. ANODE LEADS with 18" leads.....\$1 <input type="checkbox"/> 100' — TWIN LEAD-IN WIRE 300Ω heavy duty.....\$1 <input type="checkbox"/> 50' — FLAT 4-CONDUCT. WIRE many purposes.....\$1 <input type="checkbox"/> 25' — INSULATED SHIELDED WIRE.....\$1 <input type="checkbox"/> 32' — TEST PROD WIRE deluxe (red or black).....\$1 <input type="checkbox"/> 1 — S7 INDOOR TV ANTENNA hi-gain 3 section.....\$1 <input type="checkbox"/> 20 — ASST. TV KNOBS, ESCUTCHEONS, Etc.....\$1 <input type="checkbox"/> 1 — RCA 70' FLYBACK TRANS. #75240.....\$1 <input type="checkbox"/> 3 — TODD 60° DEFLECTION YOKES.....\$1 <input type="checkbox"/> 1 — FLYBACK TRANS. 90° w/schematic.....\$1 <input type="checkbox"/> 1 — TV VERT. OUTPUT TRANS. 10 to 1 ratio.....\$1 <input type="checkbox"/> 1 — TV VERT. BLOCKING TRANS. standard.....\$1 <input type="checkbox"/> 15 — ASST. TV COILS sync. peaking, width, etc.....\$1 <input type="checkbox"/> 15 — ASST. STANDARD TUNER VHF STRIPS.....\$1 <input type="checkbox"/> 2 — SILICON RECTIFIERS 500ma.....\$1 <input type="checkbox"/> 1 — SILICON RECTIFIER 750ma.....\$1 <input type="checkbox"/> 25 — ASST. PEAKING COILS popular types.....\$1 <input type="checkbox"/> 10 — TV CARTWHEEL CONDENSERS 10kv.....\$1 <input type="checkbox"/> 3 — TV CARTWHEEL CONDENSERS 20kv.....\$1 <input type="checkbox"/> 2 — TV CARTWHEEL CONDENSERS 80kv.....\$1 <input type="checkbox"/> 1 — TV RATIO DETECTOR COIL 4.5mc.....\$1 <input type="checkbox"/> 1 — TV RATIO DETECTOR COIL 10.7mc.....\$1 <input type="checkbox"/> 1 — TV SOUND I.F. COIL 4.5mc.....\$1 <input type="checkbox"/> 3 — HV RECTIFIER SOCKETS 1B3 mnted.....\$1 <input type="checkbox"/> 3 — HV RECTIFIER SOCKETS 1X2 mnted.....\$1 <input type="checkbox"/> 1 — TV SYNCHROGUIDE COIL #205R1.....\$1 <input type="checkbox"/> 3 — TV ALIGNMENT TOOLS assortment #1.....\$1 <input type="checkbox"/> 3 — TV ALIGNMENT TOOLS assortment #2.....\$1 <input type="checkbox"/> 3 — TV ALIGNMENT TOOLS assortment #3.....\$1 <input type="checkbox"/> 3 — TV ALIGNMENT TOOLS assortment #4.....\$1 <input type="checkbox"/> 3 — TV ALIGNMENT TOOLS assortment #5.....\$1 |
|---|--|--|
- EACH ALIGNMENT TOOL is different and valued at over \$1

BROOKS RADIO & TV CORP., 84 Vesey St., Dept. A, New York 7, N. Y. TELEPHONE
CORland 7-2359

"TAB" Tubes Tested, Inspected, Boxed
Six Months Guarantee!! No Rejects!
NEW & Used Gov't & Mfgs. Surplus!

Orders \$10 or more. Receiving tubes only ppd, 48 states

0A2	.80	6B16	.69	12AT6	.59	1851	1.00
0B2	.85	6BK7	.99	12AT7	.84	11726	1.10
0C3	.69	6BL7	1.25	12AU6	.69	4-65A	16.00
0D3	.35	6BN6	.98	12L7	.69	267	2.75
0Z4	.59	6BQ6	1.19	12AX7	.79	3D23	3.85
1A7	.89	6BZ7	1.25	12BA6	.65	717A	5/81
1B3	.78	6C4	.43	12B7	.89	1225	29.00
1R5	.78	6C5	.69	12BD6	.59	4-250	35.00
1S4	.78	6CB6	.80	12BE6	.59	4E27	7.00
1T4	.78	6CD6	1.49	12BF6	.59	4PR60	29.50

Send 25c for Catalog!

1U4	3/\$1	6H6	3/\$1	12BH7	.99	4X150G	\$15
1U5	.73	6I5	.89	198Q6	2.15	4X250	35.00
1X2A	1.99	6J6	.48	12BZ7	.98	4X250	35.00
3Q4	.68	6K6	.99	12CU6	1.45	5BP1	8.00
3Q5	.86	6KF	1.65	12SA7	.84	5BP4	7.50
3S4	.68	6L6	.69	12SB7	.89	5T	4.00
3V4	.83	6S4	.59	12SH7	.89	100T	7.00
3R4	.98	6S8	.98	12SJ7	.75	316A	5/81
5U4	.75	6SA7	.69	12SK7	.89	35T	4.00
5V4	.89	6SB7	1.19	12SQ7	.84	4168	4.00

Wanted Surplus Electronics from schools & U
5Y3 .59 6SC7 .89 198Q6 2.15 450T 42.00
6AB4 .59 6SG7 .79 1978 .19 807 1.00
6AC7 .70 6SH7 .69 25BQ6 1.39 809 3.00
6AC7 .69 6SJ7 .69 25L6 .89 811 4.40
6AH6 .60 6SK7 .69 25W4 .77 812 3.90
6AK5 .69 6SL7 .89 25Z5 .63 813 9.00
6AL5 2/8 6SL7 2/8 1 25Z6 .75 814 3.45
6AG5 .63 6SQ7 .74 3L34 3.49 826 3.75
6AS7 3.00 6SR7 .79 EL37 2.40 826 1.00
6AT6 .49 6T8 .98 35L6 .69 828 8.00

Wanted 304 TL tubes! Pay \$ 5.00

6AU4	1.10	6U8	.98	35W4	.49	832A	7.00
6AU5	1.19	6V6GT	.70	35Y4	.69	872A	3.50
6AU6	.69	6W4	.79	5Z5	.63	1625	2/81
6AX4	.70	6W6	.59	5Z5	.63	1625	4.00
6BA6	.59	6X4	2/8 1	50B5	.69	5879	.98
6BA7	1.06	6X5	.49	50C5	.69	5883	2.70
6BD6	.69	6Y6	.69	50L6	.69	6550	3.90
6BE6	.59	7N7	.89	KT66	3.29	5654	1.00
6BG6	1.50	12AL5	.59	75	.89	5894	12.00
6BH6	.78	12AQ5	.78	80	.59	7193	10.81

TUBES WANTED! WE BUY! SELL & TRADE!

"VACDAC"® SILICON TUBE RECTIFIER
WITH BUILT IN RF SURGE & SERIES
BALANCING PROTECTION

TYPE	VRMS/PIV	AMPS	PRICE
ST866	5000/10400	0.3	\$20.00
ST816	5000/7000	0.3	\$18.00
ST814	1200/2K00	0.5	\$15.00
ST714	1200/1600	0.6	\$ 8.00

"TAB" KITS! "TAB" THE BEST KITS! "TAB"

- All Kits Contain Most Popular Values & Sizes
- | | |
|----------------------------|----------------------------|
| Kit 2 Eng. Parallel Rules | Kit 40 Sub-Min Tubes |
| Kit 35 Precision Resistors | Kit 40 Standoff Insulators |
| Kit 10 Switches | Kit 35 Power Resistors |
| Kit 75 Resistors 1/2, 1/2W | Kit 75 Mica Condens. |
| Kit 150 Carbon Resistors | Kit 5 Crystal Diodes |
| Kit 25 Panel Lamps | Kit 100 Fuses, Assorted |
| Kit 12 Electrolytic Cond's | Kit 10 Germanium Diodes |
| Kit 56 Tube Sockets | Kit 5 FT243 Xtal Holders |
| Kit 85 Tubular Cond's | Kit 8 Silicon Diodes |
| Kit 500 Lups & Eyelets | Kit 4 Ass'd Rectifiers |
| Kit 10 Bathub Oil Cond's | Kit 2 MP Transistors |
| Kit 5 lbs. Surprise Pckg. | Kit 4X50 Fld Cond's |
| Kit 10 Xmttr Mica Cond's | Kit 2 Veeder Counters |
| Kit 3 Phone/Patch Xfms | Kit 2 Computer Toroids |
| Kit 3 Searchlights | Kit High Gain XTAL Mike |
| Kit Circular Slide Rule | |
| Kit 12 Algir Clip Ass'd. | |

BUY 10 KITS—GET ONE FREE! EACH KIT 99c

NEW BATTERY CHARGER BC6-12V

For 6 or 12 Volt Batteries.
Trickle & Full Charge up to 4 amps
Charges 6 & 12 volt batteries.
Built BC6-12VB \$10.00
BC6-12VK Preassembled Kit \$ 7.50



TRANSISTORS & ACCESSORIES

- | | | | |
|--|---|--------------|---|
| 2N341 \$2.80 | 2N442 \$4.50 | 2N277 \$4 | 2N278 \$5 |
| 2N155 \$1.39 | 2N176 \$1.80 | 2N177 \$1 | 2N178 \$1.75 |
| 2N292 \$1.50 | 2N295 \$1.20 | 2N270 \$3.95 | 2N274 \$1.25 |
| 2N408 \$3.80 | 2N541 \$1.20 | 2N582 \$2.10 | \$1.80 |
| 2N570 \$2.20 | 2N581 \$1.25 | 2N582 \$2.10 | 2N174 \$8.50 |
| 2N143 \$6.50 | 2N870 \$1.60 | 2N871 \$2 | DIAMOND BASE MICA MOUNTING KIT \$ 30 |
| DELCO ROUND BASE MICA MOUNTING KIT \$ 30 | DELCO POWER HEAT SINK WITH FINS 805Q \$1.00 | | (\$10 or more this item we pay P.P./U.S.A.) |

NEW SILICON 750MA* DIODES TOP HATS

GENERAL PURPOSE 400 PIV at 300 MA
SPECIAL 2 FOR \$1 20 for \$7

rms/piv 17/25 14c	rms/piv 35/50 19c	rms/piv 70/100 29c	rms/piv 140/200 34c
rms/piv 210/300 43c	rms/piv 280/400 55c	rms/piv 350/500 70c	rms/piv 420/600 \$1.00
rms/piv 490/700 \$1.25	rms/piv 560/800	rms/piv 630/900 \$2.00	rms/piv 700/1000 \$2.00

* CAPACITOR INPUT DERATE 20%:
(\$5 or more this item we pay P.P./U.S.A.)

TOP HAT SILICON DIODE EXPERIMENTERS KIT.
USE AS STABILIZERS, ZENER DIODES & METER PROTECTION DIODES. CLIPPER & RECTIFIER DIODES! A \$10 VALUE. 8 for \$1.

SILICON POWER DIODE STUDS * OPERATION UP TO 125°C CASE TEMP

DC AMP	17.5RMS 25 PIV	35 RMS 50 PIV	70 RMS 100 PIV	105 RMS 150 PIV
1.5	.20	.35	.45	.55
2	.30	.45	.60	.80
3	.40	.60	.80	1.15
4	.50	.80	1.15	1.75
6	.75	1.15	1.75	2.90
12	1.45	2.15	2.90	3.85
18	2.15	3.15	4.40	5.60
135	2.75	3.75	5.10	6.90
70	2.99	5.45	7.60	8.75
240	5.90	9.45	12.60	15.75

LOW PRICES TO VOLUME BUYERS!
*Derate 20% for battery or capacitive load or D.C. blocking.

"TAB" TERMS: Money Back Guarantee!
Our 15th year. \$2 min. order
F.O.B. N.Y.C. Add ship charges
or for C.O.D. 25¢ per. Prices
shown subject to change.

111-GC LIBERTY ST., N. Y. 6, N. Y.
Send 25c PHONE: RECTOR 2-6245 for Catalog



FUN WITH ELECTRICITY, by Tom Kennedy, Jr. Gernsback Library, Inc., 154 W. 14th St., New York 11, N. Y. 5 1/2 x 8 1/2 in. 128 pp. \$2.65.

All the old experiments and equipment adult readers remember in the electricity books for boys which may have started them on their electronic careers are found here—the galvanometer, motor, generator, solenoid, Tesla coil and D'Arsonval meter are all present. Drawings are carefully worked out, the author having built each piece of equipment before describing it. The language of the book is aimed at the adolescent.

His first two chapters deal with principles and throughout the book there are interesting sidelights and references—for example, few people know that the Roget dancing spiral was invented by the author of Roget's Thesaurus.

The author—who was for 25 years radio reporter for the *New York Times* and a well known experimenter in the fields of electronics and hi-fi—writes with the style of a person who feels that his material is important, making the book far different from the usual work intended for a juvenile audience.

NOISE IN ELECTRON DEVICES. Edited by Louis D. Sulin and Hermann A. Haus. John Wiley & Sons, Inc., 440 Fourth Ave., New York 16, N. Y. 6 x 9 in. 413 pp. \$12.

This text, based on a MIT course, is prepared by seven authorities on the subject. Using higher math, it analyzes tube and semiconductor noise, noise propagation and other topics. Masers and parametric amplifiers are studied. It is a comprehensive book for students and specialists.—IQ

INFRARED RADIATION, by Henry L. Hackforth. McGraw-Hill Book Co., 330 W. 42 St., New York 36, N.Y. 6 x 9 in. 303 pp. \$10.

A complete guide that starts right at the beginning, this book covers the basic physical laws which govern IR, using a minimum of math. IR sources, optical systems and detectors are described in Part I. The second part describes, illustrates and discusses applications to science and industry. A final chapter shows how IR is helping space technology. The book is clearly written, well illustrated.—IQ

FROM TIN FOIL TO STEREO, by Oliver Read and Walter L. Welch. Howard W. Sams & Co. Inc., 1720 E. 38 St., Indianapolis 6, Ind. 6 x 9 in. 524 pp. \$9.95.

This will presumably become the authoritative work in its field. Chapter 1 starts *Before the Phonograph* and Chapter 29 is entitled *Tape Versus Discs, a Look Into the Future*. Between is the whole history of phonography.

Due to the interests of the authors, the book covers in depth both technical

and commercial angles, so we have chapters on the early local phonograph companies and the modern automatic phonograph industry as well as discussions of discs vs cylinders and a complete chapter on the theory of matched impedance.

An appendix covering subjects that range from Edison's early sketches to a piece of sheet music, the "Song of Mr. Phonograph," and an extensive bibliography and index conclude the book.

The photographic illustration is extensive, covering models from the earliest tinfoil devices to juke boxes of the 1958 period. A large number of the photographs are from the collection of Oliver Read, probably the leading American collector of old phonographs.

MARINE RADIO AND ELECTRONICS, by Allan Lytel. Cornell Maritime Press, Cambridge, Md. 6 x 9 in., 242 pp. \$7.

This book explains FCC rules, lists marine frequencies and tells how to make and receive calls. Radar, depth sounders, electron beacons, fishfinders, foghorns and compasses are among the devices discussed. It is clearly written and well illustrated.

Vhf, medium and high frequencies and the Citizens band are covered. Equipment maintenance, antennas, maps and schedules are among the useful information for the boatman. The book will add to safety and convenience at sea.—IQ

LET'S EXPLORE WITH THE ELECTRON, by Alfred Bender. Sentinel Books Publishers Inc., 112 E. 19th St., New York 3, N. Y. 5 1/2 x 8 in. 128 pp. \$1.

Beginning with a chapter on electricity in the making, experiments with simple batteries, electroplating, magnetism and electromagnetism, resistors and thermistors, thermoelectricity and photoelectricity are described. The book is well illustrated.

INDUSTRIAL ELECTRONICS LABORATORY MANUAL FOR ELECTRONICS TECHNICIANS, by Paul B. Zbar. McGraw-Hill Book Co. Inc., 330 W. 42 St., New York 36, N. Y. 8 1/2 x 11 in. 201 pp. \$5.

The latest in the series sponsored by the Electronic Industries Association and the New York Trade School, this manual is devoted to industrial electronics. It is divided into 39 jobs, beginning with the characteristics of a gaseous rectifier and running through thyratrons, phototubes, timing circuits and time-delay relays, three-phase rectifiers, motor control and other types of controls to computers. Six jobs deal with computers and counters. The last three cover synchros and servomechanisms.

The book fills a gap in the literature. Far too little has been written on industrial electronics. END



TRY THIS ONE

SOLAR-CELL PRECAUTION

Be careful when handling small, unmounted, "single-shingle" silicon photo-cells (such as International Rectifier type 1020). These little cells break and chip like thin glass. They will stand no bending, very little pressure and little dropping.—*Rufus P. Turner*

HEAT-SINK INSULATOR

When commonly recommended materials are not readily available for insulating a transistor from a heat sink, an excellent substitute is varnished cambric.

It can be found around most service shops, particularly in the high-voltage cages of discarded TV sets. It has excellent insulation qualities, can be cut to any shape with a pair of scissors and has fine heat-conducting ability. Be sure to coat the cambric with silicone grease before using it.—*Domenic Ripani*

CONVERT TO COLOR TV



COLORDAPTOR—A simple 10-tube circuit and rotating color wheel converts any size B & W TV to receive compatible color TV.

COLORDAPTOR — Easily attached to any TV set, does not affect normal operation, often built from parts experimenters have on hand. **BRILLIANT COLOR!**

Complete booklet—gives theory of operation, all construction details, schematic, and sample color filters. **ONLY \$1.95**


Essential Parts Kit—All Special Parts—Coils, Delay Line, Crystal, Color Filters

Up to 16" Sets— **\$19.95** 17" and Larger **\$20.95**

Other Kits, Wired Chassis, Motors Available

COLORDAPTOR 1798 Santa Cruz, Menlo Park, Calif.

RECORDING TAPE

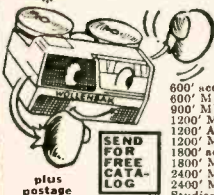

*Oxide guaranteed not to rub off or squeak—or money back. Compare ours with other "Bargain" tape. You'll find it's more than just "price" when you deal with us. We are original pioneers in the tape recorder business and our reputation means everything to us.

600' acetate (plastic), 5"	.75
600' MYLAR 5" reel	.95
900' MYLAR (Polyester), 5"	1.15
1200' MYLAR, 1/4 mil., 8" reel	1.25
1200' Acetate (plastic), 7"	1.25
1800' MYLAR, 1 1/2 mil., (astron), 7"	1.95
1800' acetate (plastic), 7"	1.75
2400' MYLAR 1 mil thick, 7"	2.25
2400' MYLAR, tensitized, 7"	2.65
2400' MYLAR, tensitized, 7"	3.45

SEND FOR FREE CATALOG plus postage

Studios, Large Users Even Lower.

NORELCO SPEAKERS

Famous 9777—successor to 9710M twin-cone speaker—original list \$9.95, usual NET 23.97. NOW while they last 1/2 off net, i.e. 11.98 plus postage. (discontinued model). Frequency 40-20,000 cy. Other SENSATIONAL Speaker reductions on a first come, first served basis.




SEND FOR SPEAKER SPECIFICATION SHEET.

COMMISSIONED ELECTRONICS CO. 1776 COLUMBIA ROAD WASHINGTON, D. C.

TOP-OF-TOOLBOX VISE

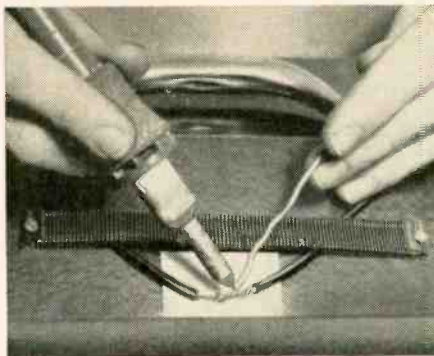Instead of tossing an old wristwatch expansion band away after it becomes



worn, fasten it down to the lid of your toolbox. This little gadget comes in mighty handy for holding small parts that are being soldered or tested.—*John A. Comstock*

INEXPENSIVE PANEL BEARINGS

Quite often, while building a piece of electronic gear, the home constructor needs a panel bearing to support the (Continued on page 126)

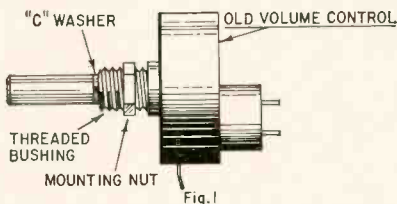


Fig. 1

MOST SENSITIVE MOST POWERFUL BEST SELLING



THE FISHER 800 STEREO FM-AM RECEIVER

■ Twice as sensitive as any competitive stereo receiver—and easily the most powerful, with a conservative rating of 70 watts distortion-free music power! The FISHER 800 incorporates the famous Golden Cascade Front-End for the outstanding FM sensitivity of 0.7 microvolts (20 db of quieting with 72-ohm antenna!) The AM signal is of FM calibre, for perfect FM-AM Stereo. The 800 offers unlimited flexibility for every application, including Center Channel, Tape Monitoring and Multiplex Stereo! Truly, here is an instrument you'll be proud to own and recommend to your friends! **\$429.50**

Write Today For Complete Specifications

FISHER RADIO CORPORATION

21-51 44th Drive • Long Island City 1, N. Y.

Television RADIO-ELECTRONICS Electricity ELECTRONICS

IN NEW SHOP-LABS OF **COYNE**

TRAIN QUICKLY! OLDEST, BEST EQUIPPED SCHOOL of ITS KIND in U.S.

Get practical training in New Shop-Labs of Coyne. Prepare for a better job and a successful future in a top opportunity field. Advanced education or previous experience not needed. Employment service to graduates.

Enroll NOW—Pay Later

Finance Plan and Easy Payment Plan. Also Part Time Employment help for students.

FREE BOOK Clip coupon or write to address below for Free Illustrated Book. "Guide to Careers"—Describes all training offered. No obligation and No Salesman Will Call. Act NOW.

B. W. Cooke, Jr., President **CHARTERED NOT FOR PROFIT ESTABLISHED 1899**
COYNE ELECTRICAL SCHOOL 1501 W. Congress Pkwy. Chicago, Dept. 61-D

Use this coupon to get our free book "GUIDE TO CAREERS"

COYNE ELECTRICAL SCHOOL training at Coyne
1501 W. Congress Pkwy.
Chicago 7, Ill. Dept. of Electronics 61-D training at home

NAME _____
ADDRESS _____
CITY _____ STATE _____

Unlike most other schools, we do not employ salesmen.

FREE!

**ELECTRONICS
CAREER KIT**

If you're interested in breaking into a good-paying job in Radio-TV-Electronics, I.C.S. will send you absolutely free a famous Career Kit with 3 famous booklets that have helped thousands of others—just like yourself—on the road to real success. Includes:

- 1 "HOW TO SUCCEED" Career Guide — 36-page gold mine of career tips and information.
- 2 "JOB CATALOG" of opportunities in your field of interest.
- 3 "SAMPLE LESSON" (math) to demonstrate the famous I.C.S. method.

Send today for your free I.C.S. Career Kit with these 3 famous booklets. There's no obligation. This may be the big break you've been waiting for. Mark and mail the coupon today.

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 37087B Scranton 15, Penna.

Please send free Career Kit with 3 famous booklets

- | | | |
|---|--|---|
| <input type="checkbox"/> General Electronics | <input type="checkbox"/> Radio-TV Serv'g | <input type="checkbox"/> Practical Electrician |
| <input type="checkbox"/> Industrial Electronics | <input type="checkbox"/> Sound Equip't. Serv'g | <input type="checkbox"/> Profess'l Eng. (Elec.) |
| <input type="checkbox"/> Radio-TV Eng'r'g | <input type="checkbox"/> Electrical Eng'r'g | <input type="checkbox"/> Electrical Drafting |
| <input type="checkbox"/> Electronic Servicing | <input type="checkbox"/> Electrical Tech. | <input type="checkbox"/> Other _____ |

Name _____ Age _____

Address _____

City _____ State _____

**Study in the "Valley of the Sun"
ELECTRONIC ENGINEERING
TECHNOLOGY**



College-level resident schooling
Veteran-approved. Catalog on request
Middleton Institute of Electronics
2937 E. McDowell Rd.
PHOENIX
ARIZONA

**ENGINEERING
HOME STUDY COURSES**

Courses written by world authorities in all branches of engineering and science and proved successful by thousands of our graduates. One hour each day in your spare time will start you off to higher pay, security and prestige. Personalized instruction methods ensure rapid progress. Fill in the coupon and indicate the course of interest. We will send you a complete outline of the course and a booklet describing the Institute and our advanced teaching methods.

- RADIO ELECTRONICS
- TELEVISION CIRCUIT
- MATHEMATICS
- ELECTRICAL ENG.
- TELEPHONY
- CIVIL ENG.
- SURVEYING
- ARCHITECTURE
- FORESTRY
- MINING
- STRUCTURAL MECHANICAL ENG.
- INDUSTRIAL ENG. & MANAGEMENT
- REFRIGERATION
- DRAFTING
- PLASTICS
- AERONAUTICAL ENG.
- HIGH SCHOOL CHEMICAL
- MATHEMATICS
- JOURNALISM
- ACCOUNTING

MAIL THIS COUPON TODAY

CANADIAN INSTITUTE OF SCIENCE & TECHNOLOGY LIMITED
767 Century Bldg., 412, 5th St. N.W., Wash., D.C.

NAME _____

ADDRESS _____

CITY _____ STATE _____

COURSE OF INTEREST _____

Canadians: Send to C.I.S.T., 767 Garden Bldg., 263 Adelaide St. West, Toronto, Ontario.



C. I. S. T.

**SCHOOL
DIRECTORY**

TV—FCC
ELECTRONICS

TRAIN AT SCHOOL RECOGNIZED BY
ELECTRONICS INDUSTRY

Specialize by choosing the residence training best suited to your needs—from 3 streamlined courses.

Non-essential math omitted.

Train for

- 1) Radio-TV Service
- 2) Electronic Technician
- 3) Communications Technician (FCC License)

Classes now starting.

Write for free booklets—no salesmen.

WESTERN ELECTRONICS INSTITUTE

5119 Sunset Blvd., Los Angeles 15, California

**ELECTRONIC
TECHNICIANS!**

Raise your professional standing and prepare for promotion!

Win your diploma in
**ENGINEERING
MATHEMATICS**

from the

Indiana Home Study Institute

We are proud to announce two great new courses in Engineering Mathematics for the electronics industry.

These unusual courses are the result of many years of study and thought by the President of Indiana Home Study, who has personally lectured in the classroom to thousands of men, from all walks of life, on mathematics, and electrical and electronic engineering.

You will have to see the lessons to appreciate them!

NOW you can master engineering mathematics, and actually enjoy doing it!

WE ARE THIS SURE: you sign no contracts—you pay only AFTER you have completed each Unit of your course.

In plain language, if you aren't satisfied you don't pay, and there are no strings attached.

Write today (a postcard will be fine), for more information and your outline of courses.

You have nothing to lose, and everything to gain!

The INDIANA Home Study Institute

924 E. Columbia Ave., Fort Wayne, Indiana

**ENGINEERING EDUCATION
for the Space Age**

NORTHROP INSTITUTE of Technology is a privately endowed, nonprofit college of engineering offering a complete Bachelor of Science Degree Program and TWO-YEAR accredited technical institute curricula. Students from 50 states, many foreign countries. Outstandingly successful graduates employed in aeronautics, electronics, and space technology. Write today for catalog—no obligation.

NORTHROP INSTITUTE OF TECHNOLOGY
1181 West Arbor Vitae Street, Inglewood 1, California

**GET INTO
ELECTRONICS**

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar and automation. Basic and advanced courses in theory and laboratory. Assoc. degree in electronics in 20 mos. B.S. in electronic engineering obtainable. ECED accredited. G.I. approved. Graduates in all branches of electronics with major companies. Start September, February, Dorms, campus. High School graduate or equivalent. Catalog.

**VALPARAISO TECHNICAL
INSTITUTE**

Dept. C Valparaiso, Indiana



ELECTRONICS

**PREPARE FOR A GOOD JOB!
BROADCAST ENGINEER
RADIO SERVICING AUTOMATION**

TELEVISION SERVICING
BLACK & WHITE—COLOR

APPROVED FOR VETERANS AND SURVIVORS
OF VETERANS

BUILDING AIR CONDITIONED
SEND FOR FREE LITERATURE

BALTIMORE TECHNICAL INSTITUTE
1425 EUTAW PLACE, BALTIMORE 17, MD.

LEARN

**RADAR MICROWAVES
COMPUTERS—TRANSMITTERS**

CODE • TV • RADIO

Phila. Wireless Technical Inst.
1533 Pine St., Philadelphia 2, Pa.
A Non-Profit Corp.
Founded in 1908

Write for Free Catalog to Dept. RE3
Classes now forming

ENGINEERING COURSES



E.E.
Option Electronics or Power
Mechanical, Civil & Physics
Also in Liberal Arts
presented through

HOME STUDY

Resident Classes Also
Available if Desired
**PACIFIC INTERNATIONAL
COLLEGE OF ARTS
& SCIENCES**

Primarily a correspondence school

5719-M Santa Monica Blvd. Hollywood 38, Calif.

MATHEMATICS MADE EASY

by new step-by-step home study method. Courses from elementary to advanced level. Fees as low as \$10. Diploma awarded. Free booklet by Prof. Allcut, P. Eng., gives complete detail. Write today to **CANADIAN INSTITUTE OF SCIENCE & TECHNOLOGY LTD.**, 412 5th St. N.W., Washington, D.C.

SCIENCE ENGINEERING

B.S. Degree—36 mos. • B.E. Degree—27 mos. Accelerated year-round program: Aero., Chem., Civil, Elec., Mech., Metal., Math., Chem., Physics. Modest rate. Earn board. New classes start Mar., June, July, Sept., Jan. Catalog, 1531 E. Washington Blvd., Fort Wayne 2, Ind.

INDIANA TECHNICAL COLLEGE

twenty to one dividend . . .

that's the return you can receive from your investment in your college education in engineering or business. Faster advancement. too. Important firms like Tri-State College graduates . . . return regularly to our campus to interview seniors. Become an Electronics Engineer. Quality faster here.

Bachelor of Science Degree in 27 Months

In Electrical (Electronics or Power major), Mechanical, Chemical, Aeronautical, Civil Engineering. IN 36 MONTHS B.S. in Business Administration (General Business, Accounting, Motor Transport Management majors). For earnest, capable, mature students. Small classes. Store professional class hours. Beautiful campus. Well-equipped labs, modernized buildings, new dorms. Year-round operation. Enter June, Sept., Jan., Mar. Founded 1881. Write J. G. McCarthy, Director Admissions, for Catalog and "Your Career in Engineering and Commerce" Book.

TRI-STATE COLLEGE 2431 College Ave. Angola, Indiana

Learn Transistor Electronics At Home!

■ Prepare now for a profitable career in this growing field. Learn theory, construction and applications of all types of transistors with this proven home-study course from the Philco Technological Center.

FOR FREE INFORMATION
PLEASE WRITE TO:

PHILCO
TECHNOLOGICAL CENTER
"C" and Ontario Sts., Philadelphia 34, Pa.

• TV - FCC • ELECTRONICS

TRAIN AT SCHOOL RECOGNIZED BY ELECTRONICS INDUSTRY. Specialize by choosing the training best suited to your needs—from three streamlined courses . . . non-essential math omitted; Train for (1) Radio-TV Servicing; (2) Electronic Technician; or (3) Communication Technician (FCC License). Classes now starting. Write for free booklets. No salesmen.

WESTERN ELECTRONICS INSTITUTE
5119 SUNSET BLVD., LOS ANGELES 15, CALIF.



Prepare for your career in

ELECTRONICS ELECTRICAL ENGINEERING RADIO-TV COMPUTERS

Through study at the Milwaukee School of Engineering, you can gain a sound technical education — and open the door to a rewarding career in the space age as an engineer or engineering technician.

At MSOE, new classes begin quarterly. Previous educational, military, and practical experience evaluated for advanced credit. Veteran approved. Write for more information today.

Associate in Applied Science
degrees — 2 years

Electronics Communications
Technology
Electrical Power Technology
Computer Technology
Air Conditioning Technology
Industrial Technology
Metallurgical Technology

Bachelor of Science degrees—4 years

Electrical Engineering
— Communications option
— Electrical Power option
Mechanical Engineering

Pre-technology program, scholarships,
financial aid, and placement service
available.



NEW!
FREE
"Your Career"
booklet.
•
MAIL
coupon today!

MILWAUKEE SCHOOL OF ENGINEERING
Dept. RE-361, 1025 N. Milwaukee St., Milwaukee 1, Wis.
(Please Print)

Name..... Age.....
Address.....
City..... State.....
Course interest.....

MILWAUKEE SCHOOL OF ENGINEERING

1025 NORTH MILWAUKEE STREET • MILWAUKEE 1, WISCONSIN

AT LAST! A home study course covering all phases of electric and electronic organ servicing.

A NEW COURSE An extensive course covering every make of organ—repair, regulating, and troubleshooting.

Electronic ORGAN SERVICING

Your Opportunity To Get Into A New, Rapidly Expanding Field At The Start. Don't Miss It!!

WRITE NOW
FOR FREE
BOOKLET

NILES BRYANT SCHOOL
Dept. E., 3731 Stockton Blvd.
Sacramento 20, California


NHSC Approved • The Pioneer School
Established 1898

FREE ELECTRONICS TEST

Prove to yourself that you are qualified to learn 2-way FM radio servicing. All you need to know is basic electronics to begin studying for a rewarding career in this rapidly growing field. Two-way radio technicians are desperately needed to fill many full and part time job opportunities in service shops throughout the country. The 38 lesson Motorola Training Institute home study course trains you to be a qualified 2-way FM radio technician in as little as 6 to 8 months. Step ahead to greater earnings, a better future by learning 2-way FM radio servicing. Send for FREE Motorola Training Institute electronics test today. No obligation and no salesman will call.

MOTOROLA TRAINING INSTITUTE Dept. A-163
4501 W. Augusta Blvd., Chicago 51, Ill.
Send FREE electronics test and details on MTI home study course.
NAME.....
ADDRESS.....
CITY..... STATE.....

TIME TO CLEAN UP YOUR SYSTEM . . .

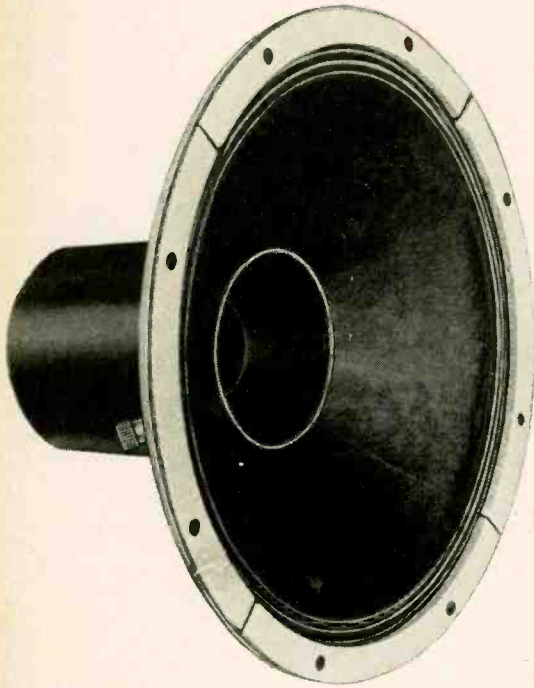

Norelco® T-7 LOUDSPEAKERS

with voice coil magnets of Ticonal-7 steel (30% more efficient* than Alnico V)

* . . . 30% more efficient response to the full signal range of your amplifier . . . WHETHER ITS RATED OUTPUT is 10 WATTS or a HUNDRED . . . at any listening level from a whisper to a shout!

Guild-crafted by Philips of the Netherlands to give you

THE CLEANEST SOUND AROUND

Ask for a demonstration wherever good sound is sold or write to:

**NORTH
AMERICAN
PHILIPS
CO., INC.**

High Fidelity Products Division,
230 Duffy Avenue,
Hicksville, L. I., N. Y.

Write for complete details about the Gernsback Technicians' and Hi-Fi Book Club Plans.

Gernsback Library, Inc.

154 West 14th St.

New York 11, N.Y.

new "LEADER" test instrument

LAG-55 AUDIO GENERATOR SINE SQUARE

A multi-purpose generator for measurements on audio equipment -amplifiers, speakers, networks. Three waveforms: sine, square and complex for all types of measurements including response, distortion, transient and I-M distortion checks. Full range is from 20 to 200,000 cps, output 5 volts with minimum amplitude variation throughout whole range.



The LEADER test instruments are being used in the more than 36 countries, attesting their excellence in design, performance and usefulness.

OHMATSU ELECTRIC CO. LTD.

850 TSUASHIMA-CHO KOHOKU-KU YOKOHAMA, JAPAN

(Continued from page 123)

long shaft of a switch or potentiometer located deep within the chassis. A suitable bearing can be made from the threaded mounting bushing of a discarded volume control (Fig. 1).

Take the back off the old control and remove the C-washer that holds the shaft in place. Slide the shaft and wiper

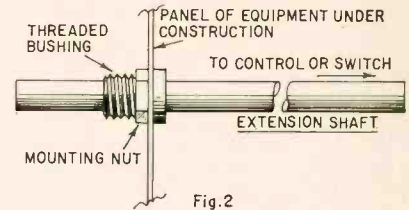



Fig. 2

arm out of the control. If the case is plastic, break it away from the threaded bushing with a pair of pliers. Tin snips or a hacksaw may be required to extricate the bushing if the case is made of metal.

Use the old volume-control nut to mount the bushing on the panel of the unit being constructed (Fig. 2). Carefully position the bushing so that the shaft which passes through it will work freely without binding.—Hartland B. Smith

CLOTHESPIN EASES PROD HANDLING

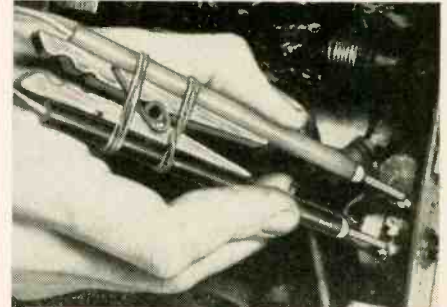By attaching your test prods to the legs of a wooden spring type clothespin with rubber bands as shown, you will be able to handle them much more



easily. Since both prods are attached to each other, you can handle them single-handed. Just a squeeze puts the tips closer together to touch test points only a short distance apart. You will find this clothespin-and-prod arrangement a real convenience once you get used to working with it.—John A. Comstock

BONDING STRAPS

One day while I was preparing to align a TV set I discovered that I needed some bonding straps right away but none could be found in the shop. I noticed some coaxial cable lying in a corner and an idea struck me. Why not use the shield of the coax?

First I measured off the desired length of coax cable. Next, with a razor blade, I slit the coax lengthwise and removed the outer covering. Then I pulled the inner conductor out of the shield and stored it for future use. Next I attached alligator clips to both ends and pulled the copper shield through my fingers to flatten it out and my inexpensive bonding strap was complete.—Paul Mitnaul

END

THE SIGN OF RAD-TEL'S QUALITY PERFORMANCE

**BUY DIRECT FROM
RAD-TEL!!
ORDER RAD-TEL'S
FIRST QUALITY TUBES TODAY!
NOT USED!! NOT PULLED OUT OF SETS!!**

**SERVICEMEN: HUGE SAVINGS!! COMPARE!!
FAST ONE DAY SERVICE.**



GUARANTEED ONE FULL YEAR UP TO 75% OFF ON BRAND NEW TUBES

**SEND FOR FREE TROUBLE SHOOTER
GUIDE AND NEW TUBE & PARTS CATALOG**

TRANSISTORS — AT FABULOUS DISCOUNTS

	PRICE	TYPE	RATING	ELECTRICAL CHARACTERISTICS		hfe
<input type="checkbox"/>	RF 49¢ ea.	GE PNP ALLOY JUNCTION GENERAL PURPOSE RF/AF	200 MW	1CBO max. 20 μ a VCB = -3V	1EBO max. 20 μ a VEB = -3V	VCE = -1.5 lb = 5 ma 20 min
<input type="checkbox"/>	AF 39¢ ea.	Power AF Mgd. Freq. to 3		20 ma VCB = -16V	20 ma VEB = -16V	VCE = -1.5 lb = 1 ma 40 min
<input type="checkbox"/>	80¢ ea.	Hi Power 15 AMP to 36	MIN. POWER OUTPUT 2.25 W	40 ma VCB = -100	40 ma VEB = -100	VCE = -1.5 lb = 1 ma 30 min

SILICON RECTIFIER

35 AMP
50 PIV
(max. 20 ma)
\$2.50 ea.

Lots of 10
\$2.25 ea.
(No Hardware)



NOT AFFILIATED WITH ANY OTHER MAIL ORDER TUBE COMPANY

RAD-TEL TUBE CO.

55 CHAMBERS STREET, NEWARK 5, N. J. DEPT. RE-361

TERMS: 25% deposit must accompany all orders, balance COD. Orders under \$5: add \$1 handling charge plus postage. Orders over \$5: plus postage. Approx. 8 tubes per 1 lb. Subject to prior sale. No C.O.D.'s outside continental USA.

EACH TUBE INDIVIDUALLY & ATTRACTIVELY BOXED

Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price
—	0Z4M	.79	—	6AW8	.89	—	12AF6	.49
—	1AX2	.62	—	6AX4	.65	—	12AJ6	.46
—	1B3GT	.79	—	5AX7	.64	—	12AL5	.45
—	1DN5	.55	—	6BA6	.49	—	12AL8	.95
—	1G3	.73	—	6BC5	.54	—	12AQ5	.52
—	1J3	.73	—	6BC7	.94	—	12AT6	.43
—	1K3	.73	—	6BC8	.97	—	12AT7	.76
—	1L6	1.05	—	6BD6	.51	—	12AU6	.50
—	1LN5	.59	—	6BE6	.55	—	12AU7	.60
—	1R5	.62	—	6BF6	.44	—	12AV5	.97
—	1S5	.51	—	6BG6	1.66	—	12AV6	.41
—	1T4	.58	—	6BH6	.65	—	12AV7	.75
—	1U4	.57	—	6BH8	.87	—	12AX4	.67
—	1U5	.50	—	6BJ6	.62	—	12AX7	.63
—	1X2B	.82	—	6BK7	.85	—	12AZ7	.86
—	2AF4	.96	—	6BL7	1.00	—	12B4	.63
—	3AL5	.42	—	6BN4	.57	—	12BA6	.50
—	3AU6	.51	—	6BN6	.74	—	12BD6	.50
—	3AV6	.41	—	6BQ5	.65	—	12BE6	.53
—	3BA6	.51	—	6BQ6GT	1.05	—	12BF6	.44
—	3BC5	.54	—	6BQ7	.95	—	12BH7	.73
—	3BE6	.52	—	6BR8	.78	—	12BL6	.56
—	3BN6	.76	—	6BU8	.70	—	12BQ6	1.06
—	3BU8	.78	—	6BY6	.54	—	12BY7	.74
—	3BY6	.55	—	6BZ6	.54	—	12BZ7	.75
—	3BZ6	.55	—	6BZ7	.97	—	12C5	.56
—	3CB6	.54	—	6C4	.43	—	12CA5	.59
—	3CF6	.60	—	6CB6	.54	—	12CN5	.56
—	3CS6	.52	—	6CD6	1.42	—	12CR6	.54
—	3CY5	.71	—	6CF6	.64	—	12CU5	.58
—	3DK6	.60	—	6CG7	.60	—	12CU6	1.06
—	3DT6	.50	—	6CG8	.77	—	12CX6	.54
—	3Q5	.80	—	6CM7	.66	—	12OB5	.69
—	3S4	.61	—	6CN7	.65	—	12OE8	.75
—	3V4	.58	—	6CR6	.51	—	12OL8	.85
—	4BC5	.56	—	6CS6	.57	—	12OM7	.67
—	4BC8	.96	—	6CU5	.58	—	12OQ6	1.04
—	4BN6	.75	—	6CU6	1.08	—	12OS7	.79
—	4BQ7	.96	—	6CY5	.70	—	12OZ6	.56
—	4BS8	.98	—	6CY7	.71	—	12EL6	.50
—	4BU8	.71	—	6DA4	.68	—	12EG6	.54
—	4BZ6	.58	—	6DB5	.69	—	12EZ6	.53
—	4BZ7	.96	—	6DE6	.58	—	12F5	.66
—	4CS6	.61	—	6DG6	.59	—	12F8	.66
—	4DE6	.62	—	6DQ6	1.10	—	12FM6	.45
—	4DK6	.60	—	6DT5	.76	—	12K5	.65
—	4DT6	.55	—	6DT6	.53	—	12SA7M	.86
—	5AM8	.79	—	6EU8	.79	—	12SK7GT	.74
—	5AN8	.86	—	6EA8	.79	—	12SN7	.67
—	5AQ5	.52	—	6HG6T	.58	—	12SQ7M	.73
—	5AT8	.80	—	6J5GT	.51	—	12U7	.62
—	5BK7A	.82	—	6J6	.67	—	12V6GT	.53
—	5BQ7	.97	—	6K6	.63	—	12W6	.69
—	5BR8	.79	—	6S4	.48	—	12X4	.38
—	5CG8	.76	—	6SA7GT	.76	—	17AX4	.67
—	5CL8	.76	—	6SK7	.74	—	17BQ6	1.09
—	5EA8	.80	—	6SL7	.80	—	17C5	.58
—	5EU8	.80	—	6SN7	.65	—	17CA5	.62
—	5J6	.68	—	6SQ7	.73	—	17D4	.69
—	5T8	.81	—	6T4	.99	—	17DQ6	1.06
—	5U4	.60	—	6UB	.78	—	17L6	.58
—	5U8	.81	—	6V6GT	.54	—	17W6	.70
—	5V6	.56	—	6W4	.54	—	19AU4	.83
—	5X8	.78	—	6W6	.69	—	19BG6	1.39
—	5Y3	.46	—	6X4	.39	—	19T8	.80
—	6AB4	.46	—	6X5GT	.53	—	21EX6	1.49
—	6AC7	.96	—	6X8	.77	—	25BQ6	1.11
—	6AF3	.73	—	7AU7	.61	—	25C5	.53
—	6AF4	.97	—	7A8	.68	—	25CA5	.59
—	6AG5	.65	—	7B6	.69	—	25C06	1.44
—	6AH6	.99	—	7Y4	.69	—	25C06	1.11
—	6AK5	.95	—	8AU8	.83	—	25DN6	1.42
—	6AL5	.47	—	8AW8	.93	—	25EH5	.55
—	6AM8	.78	—	8BQ5	.60	—	25L6	.57
—	6AN4	.95	—	8CG7	.62	—	25W4	.68
—	6AN8	.85	—	8CM7	.68	—	25Z6	.66
—	6AQ5	.50	—	8CN7	.97	—	35C5	.51
—	6AR5	.55	—	8CX8	.93	—	35L6	.57
—	6AS5	.60	—	8EB8	.94	—	35W4	.52
—	6AT6	.43	—	11CY7	.75	—	35Z5GT	.60
—	6AT8	.79	—	12A4	.60	—	50B5	.60
—	6AU4	.82	—	12AB5	.55	—	50C5	.53
—	6AU6	.50	—	12AC6	.49	—	50DC4	.37
—	6AU7	.61	—	12AD6	.57	—	50EH5	.55
—	6AU8	.87	—	12AE6	.43	—	50L6	.61
—	6AV6	.40	—	12AF3	.73	—	117Z3	.61



TV TUNER OVERHAUL

ALL MAKES
ONE PRICE
\$9.95

VHF TUNERS • UHF TUNERS • UV Combinations*

Castle overhaul charge includes all labor and minor parts and written 90 day warranty. Tubes and major parts are extra at net prices. Tuner to be overhauled should be shipped complete; include tubes, shield cover and any damaged parts. Write down model number and state complaint. Pack well and insure.

Castle, pioneers of TV Tuner overhauling, assure the best service available. Remember, Castle has a decade of experience and overhauling tuners is our only business.

*UV combination tuner must be of one piece construction. Separate UHF and VHF tuners must be dismantled and the defective unit only sent in.

SAME DAY SERVICE!

On Popular Types
48 Hours most others

Castle

TV TUNER SERVICE, INC.

5710 N. Western Ave. • Chicago 45, Illinois

In Canada: 136 Main Street • Toronto 13, Ontario

R-E

Classified

ADS

Rates—50¢ per word (including name, address and initials. Minimum ad 10 words. Cash must accompany all ads except those placed by accredited agencies. Discount, 10% for 12 consecutive issues. Misleading or objectionable ads not accepted. Copy for May issue must reach us before March 10, 1961.

RADIO-ELECTRONICS, 154 West 14 St., New York 11, N. Y.

PROMPT DELIVERY, we will not be undersold. Amplifiers, Tape Recorders, Tuners, etc. No. Catalogs, Air Mail Quotes. Compare. L. M. BROWN SALES CORP. Dept. R-239, East 24th St., New York 10, N.Y.

GARAGE DOOR OPERATORS \$59.95. Rugged chain drive automatic unit. Highest Quality. Free Literature. DEMSCO, INC., Sebring 18, Ohio.

HI-FI PROBLEMS SOLVED on-the-spot by "The Hi-Fi Doctor". Audio, Acoustic, Radio Engineer. Professional visits, day, evening, New York area. WILLIAM BOHN, Plaza 7-8569.

I'M SEEKING AN RCA PORTABLE TV SET, The 8½-inch, metal-cased receiver made in the middle 1950's. Must be working or repairable. State condition and price. R. H. Dorf, SCHOBER ORGAN CORP., 43 West 61st St., New York 23, N.Y.

TELEVISION REMOTE CONTROL—\$7.00. Free Literature—234 Monroe St., Passaic, N. J.

PROFESSIONAL ELECTRONIC PROJECTS—Organs, Timers, Computers, etc.—\$1 each. List Free. PARKS, Box 1665, Lake City Station, Seattle 55, Wash.

DISCOUNTS UP TO 50% on Hi-Fi amplifiers, tuners, speakers, tape recorders, individual quotations only, no catalogs. **CLASSIFIED HI-FI EXCHANGE**, 2375 East 65th Street, Brooklyn 34, N.Y.

NEW TWIN LINE SOLDERLESS CONNECTOR (Patent pending) insures permanent all weather TV-FM antenna connection. \$.80 each. \$8 doz. Jobbers and Distributors wanted. Write: RAMCON, 45432 Kingtree Ave., Lancaster, Calif.

COMPONENTS, Recorders, Tapes. FREE Wholesale Catalogue. CARSTON, 125-T East 88th St., New York 28, N.Y.

LEARN WHILE ASLEEP, Hypnotize with your recorder, phonograph or amazing new Electronic Educator endless tape recorder. Catalog, details free. **SLEEP-LEARNING ASSOCIATION**, Box 24-RD, Olympia, Wash.

BUSINESS CARDS. \$3.95 Thousand, Post-paid! (Raised Letters) Samples. JOHN H. TAYLOR, R. D. 2, Box 215, West Middlesex, Pa.

DON'T BUY HI-FI COMPONENTS, Kits, Tape, Tape Recorders until you get our low, low return mail quotes. "We Guarantee Not To Be Undersold." Wholesale Catalog Free. **HI-FIDELITY CENTER**, 1797C First Avenue, New York 28, N.Y.

DIAGRAMS FOR REPAIRING RADIOS, television \$2. Give make and Model. **DIAGRAM SERVICE**, Box 672 RE, Hartford 1, Conn.

START YOUR FIRE ALARM BUSINESS with our fire alarm 4"x4"x2", \$66 per doz., and micro thermal switches \$18 per dozen; maximum profit, minimum investment, fully guaranteed. **KAMCO-ELECTRO-CHEM CO.**, 2712 N. Magnolia Ave., Chicago 14, Ill.

CASH PAID! Sell your surplus electronic tubes. Want unused, clean radio and TV receiving, transmitting, special purpose, Magnetrons, Klystrons, broadcast types, etc. Want military & commercial lab/test and communications equipment such as G.R., H.P., AN/UPM prefix. Also want commercial receivers and transmitters. For a fair deal write **BARRY**, 512 Broadway, New York 12, N. Y. Walker 5-7000.

AMPEX, Concertone, Crown, Magnecord, Presto, Norelco, Bogen, Tandberg, Sherwood, Rek-O-Kut, Scott, Shure, Dynakit, others . . . Trades. **BOYNTON STUDIO**, Dept. RE, 10 Pennsylvania Ave., Tuckahoe, N.Y.

C-B Intercom operates from remote location. **FRONTIER ELECTRONICS**, Orr 3, Minn.

ALL MAKES OF ELECTRICAL INSTRUMENTS AND TESTING equipment repaired. New and used instruments bought, sold, exchanged. **HAZELTON INSTRUMENT CO.**, 128 Liberty Street, New York, N.Y.

BOOKS—ALL 10c, 2000 titles, all subjects, catalog free. **COSMAO**, Clayton 2, Ga.

FOR SALE — INFRA-RED SNOOPERSCOPIES!! Optics, Lamps, Parts. World's largest stock Infra-red components. Write for **FREE Infra-red Catalog.** **McNEAL ELECTRIC & EQUIPMENT**, Dept. RE-3, 4736 Olive, St. Louis 8, Mo.

NEW CONCEPT OF LEARNING SELF-HYPNOSIS! Now on tape or record! Free Literature. **McKINLEY-SMITH CO.**, Dept. T5, Box 3038, San Bernardino, Calif.

ADVERTISING INDEX

Radio-Electronics does not assume responsibility for any errors appearing in the index below.

Advertiser	Page No.
A. E. S. INC.	13
Acoustic Research, Inc.	73
Airex Radio Corp.	120
Alco Electronic Mfg. Co.	91
Allied Radio Corp.	B. 20, 21, 111
Arrow Fastener Company, Inc.	108
Atlas Sound Corp.	110
Audio Unlimited Inc.	90
Audion	90
B. & K. Mfg. Co.	93
Barry Electronics Corp.	108
British Industries Corp.	115
Brooks Radio & TV Corp.	121
Burstein-Applebee Co.	83
Capitol Radio Engineering Institute.	102-105
Carston Studios	117
Castle TV Tuner Service Inc.	128
Center Industrial Electronics Inc.	117
Centralab Div. of Globe Union	24
CLASSIFIED ADS.	128
Cleveland Institute of Electronics	11
Columbia Wire & Supply Co.	66
Commissioned Electronics Co.	123
Coloridator	123
Coyne Electrical School	111, 123
DeVry Technical Institute.	7
Dressner	108
Editors & Engineers.	112
Electro-Voice, Inc.	25
Electronic Chemical Corp.	116
Electronic Instrument Co. (EICO)	31, 32
Electronic Measurement Corp. (EMC)	82
Electronics Missiles & Communications, Inc.	73
Electronic Publishing Co., Inc.	116
Fair Radio Sales.	81
Fisher Radio Corp.	123
General Techniques, Inc.	121
Gernsback Library, Inc.	107
Grantham School of Electronics.	15
Heald Engineering College.	119
Heath Company.	62-65
Holt, Rinehart & Winston, Inc.	113, 118
Indiana Technical College	120
Industrial TV Co.	120
Institute of Radio Engineers.	108, 113, 118
JFD Electronics Corp.	19
Jensen Mfg. Company.	3rd Cover
Jerrold Electronics Co.	26
Key Electronics Co.	117
Lafayette Radio Electronics Corp.	17
Lektron Inc.	97
Metropolitan Electronics	95, 112
(H. A.) Moog Co.	110
Moss Electronics	84, 85
Multicore Sales Div.	115
National Radio Institute.	27-28, 90, 115
National Technical Schools.	5
North American Philips Co., Inc. (Norelco)	126
Northeast Telecommunications, Inc.	110
Ohmatsu Electric Co. Ltd.	126
Olson Radio Corp.	67
PACO Electronics Co., Inc.	120
Philco Computer Div.	114
Picture Tube Outlet	117
Progressive "Edu-Kits" Inc.	98
Pyramid Electric Co.	14
Quam-Nichols Company	81
Quietrol Co., Inc.	118
RCA Tube Div.	Back Cover
RCA Institutes	76-78
Rad-Tel Tube Co.	127
Radio Electronics Master	99
Radio TV Training School.	27
Rider, (John F.) Publisher Inc.	97
Rinehart & Co.	113, 118
Sams, (Howard W.) & Co., Inc.	100-101
Schober Organ Co.	106
Scott, (H. H.) Inc.	29
Service Instruments Corp. (Sencore)	90-91
Shure Brothers, Inc.	67
Sonotone Corp.	16
Sprague Products Co.	116
Superscope, Inc. (Sony)	116
Supreme Publications	115
Swing-O-Lite Co.	83
Sylvania Electric Products Inc.	2nd Cover
TAB	122
Tarzian, (Sarkis) Inc.	18, 120
Thorens Company	8
Tung-Sol Electric Co.	12
The Turner Microphone Company.	88
United Carbon Consumer Products Co.	99
United Radio Company	116
University Loudspeakers, Inc.	22
D. Van Nostrand Co., Inc.	3
Vidair Electronics Mfg., Corp.	120
Weller Electric Corp.	30
Winegard Company	70-71
Xcelite, Inc.	117

SCHOOL DIRECTORY PAGES 124, 125

Baltimore Technical Institute
Niles Bryant School
Canadian Institute of Science Technology
The Indiana Home Study Inst.
Indiana Technical College
International Correspondence School
Middleton Institute of Electronics
Milwaukee School of Engineering
Motorola Training Institute
Northrop Institute of Technology
Pacific International College of Arts & Sciences
Phila. Wireless Technical Institute
Philco Technological Center
Tri-State College
Valparaiso Technical Institute
Western Electronics Institute


TF-3

YOUR
"BEST BUY"
 IN
 HI-FI
 SPEAKERS

JENSEN'S THRIFTY 4-SPEAKER
 SYSTEM... CHOICE OF ECONOMICAL
 UNFINISHED OR GENUINE
 OILED WALNUT CABINETRY



When you consider the purchase of a high fidelity speaker system be sure to look into the tremendous value of the Jensen TF-3. You can pay much more for some other recommended compact speakers . . . we honestly think you'll like the new Jensen TF-3 better. Hear it and compare it to your own judge and decide which is the best buy for you. Compare this 4-speaker 3-way system with its low distortion FLEXAIR* woofer . . . its two midrange units so smooth and free from coloration . . . and the sensational new SONO-DOME* Ultra-Tweeter which goes into action only above 10,000 cycles! There's a choice of genuine oiled Walnut cabinetry or the unfinished gum hardwood for painting, staining or building-in. Use a pair for an amazingly economical outstanding stereo speaker system.

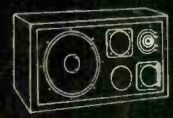

4-SPEAKER
 3-Way system

In Genuine Oiled Walnut \$99.50
 Unfinished Gum Hardwood \$79.50

Jensen MANUFACTURING COMPANY
 6601 S. Laramie Avenue, Chicago 38, Illinois

Division of The Muter Co.

In Canada: Renew Electric Co., Ltd., Toronto
 In Mexico: Universal De Mexico, S. A., Mexico D.F.

How do your customers rate you?



Your reputation is based largely on what happens *after* you leave the scene of each service call. For this reason the name on the tubes you install makes a world of difference. RCA tubes are designed and manufactured to assure customer confidence in you as well as in RCA.

RCA tube quality is your best insurance against call-backs due to premature tube failure.

RCA tube performance puts your workmanship in the best light and protects it through rigid quality control.

RCA's trademark symbolizes a name and reputation customers have respected for decades.

Your customers know that those red-white-and-black RCA tube cartons in your tube caddy represent the most trusted name in electronics. Remember, customer confidence is the cornerstone of your business.

To protect your service reputation before, during and after every service call, make sure your next tube order specifies... **RCA TUBES.**

RCA ELECTRON TUBE DIVISION, HARRISON, N. J.



SIGN OF A SERVICE JOB WELL DONE



The Most Trusted Name in Electronics
RADIO CORPORATION OF AMERICA