

ELECTRONIC SERVICING



JUNE
1958 • 50¢

ELECTRONIC SERVICING

ELECTRONIC SERVICING

Television SCHEMATICS and SERVICE GUIDE

Including: Alignment Data, Waveforms, Tube Location Guide, Operating Voltages, Essential Parts Numbers, etc.

Alignment Data, Waveforms, Tube Location Guide, Operating Voltages, Essential Parts Numbers, etc.


ANSWERMAN

VSSS

SCHEMATICS


ABSORPTION ANALYZER

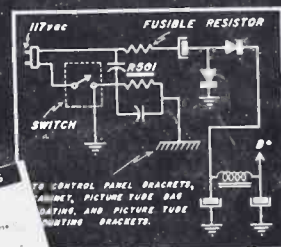ADMIRAL Video Speed Servicing Systems DATA SHEETS



Mfr: Admiral Chassis No. 14UYPSB, C
Card No. AD-14UYPSB, C-4
Section Affected: Chassis, cabinet and picture tube brackets.
Symptoms: Static discharge.
Cause: Resistor between control panel brackets and chassis is broken or disconnected.
What To Do: Replace or reconnect R301 (470K).

REAR VIEW OF PICTURE TUBE

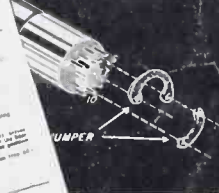

Mfr: Admiral Chassis No. 14UYPSB, C
Card No. AD-14UYPSB, C-5
Section Affected: Raster.
Symptoms: Poor focus.
Cause: Picture tube requires better focusing.
What To Do: Put a jumper strip (part 518A134) across pins 4 and 2, or pins 9 and 10 on the base of the picture tube, leave it in the position which provides the best focus. Caution: Focus also varies with ion trap adjustment.

6867 HORIZ. OSC.

Mfr: Admiral Chassis No. 14UYPSB, C

IAP 7C-3-17 OCT 58BX
CRAIG RAD SV
H CRAIG JR-PROP
SHULTSBURG WISC

NEW, IMPROVED



1B3GT

Made possible by

RUGGED, RAYTHEON FLY-BACK LIFE TESTS

At Raytheon, we test tubes to find out how *good* they are, not how bad. Accepted methods of testing tubes like the 1B3GT often resulted in subpar tubes. To improve and maintain the quality of Raytheon 1B3GT Tubes, Raytheon developed an expensive but super-accurate method of life testing these tubes.

Tests on the improved Raytheon 1B3GT far exceeded our expectations. Receiver life tests of the Raytheon 1B3GT showed not a single failure at 600 hours. (No worries about early life tube failure here.) At 1850 hours a sensational 93% of these tubes were still operating at rated efficiency in spite of the fact that *these sets were operated at 10% above their rated line input and cycled on and off every two hours.*

These torturous Raytheon Tube tests not only prove the quality of Raytheon Tubes, they help maintain

that quality. Tubes are constantly checked and tested and any variance in quality is instantly noted and quickly corrected.

That's why you can use Raytheon TV and Radio Tubes with complete confidence in their quality — with full knowledge that you are giving your customers tubes that are **RIGHT . . . for Sound and Sight.**

New Raytheon 1G3GT, 1J3GT and 1K3GT

are also subjected to the Raytheon Fly-Back Tests — and as a result meet Raytheon's highest standards of quality. Ask your Raytheon Tube Distributor for them.



RAYTHEON MANUFACTURING COMPANY

Receiving Tube and Semiconductor Operations

NEWTON 58, MASS. 55 Chapel Street CHICAGO, ILL. 9501 Grand Ave. (Franklin Park) ATLANTA 6, GA. 1202 Zonolite Rd., N.E. LOS ANGELES 7, CALIF. 2419 So. Grand Ave.

Raytheon makes all these } Receiving and Picture Tubes, Reliable Subminiature and Miniature Tubes, Semiconductor Diodes and Transistors, Nucleonic Tubes, Microwave Tubes.



Excellence in Electronics

Sprague Service-Aids for servicemen:

SPRAGUE
.02

.02 MF ± 20%
1000 WVDC
5GA-S2


... versatile **CERA-MITE*** CERAMIC CAPACITORS
with handy identification tags

Sprague's complete ceramic capacitor line is now individually tagged for quick, *complete* identification—capacitance, tolerance, voltage, and type. No fumbling, no guessing about ratings ... you're always sure with Sprague *tagged* disc capacitors. Use them all the time. You'll find that they also make excellent replacements for molded mica, ceramic tubular, and paper tubular capacitors in many applications

Stock up today! Ask your distributor about Sprague CERAMIKITS ... they contain the ceramic disc capacitors you need most ... they keep them in order ... ready to use.

*Trademark

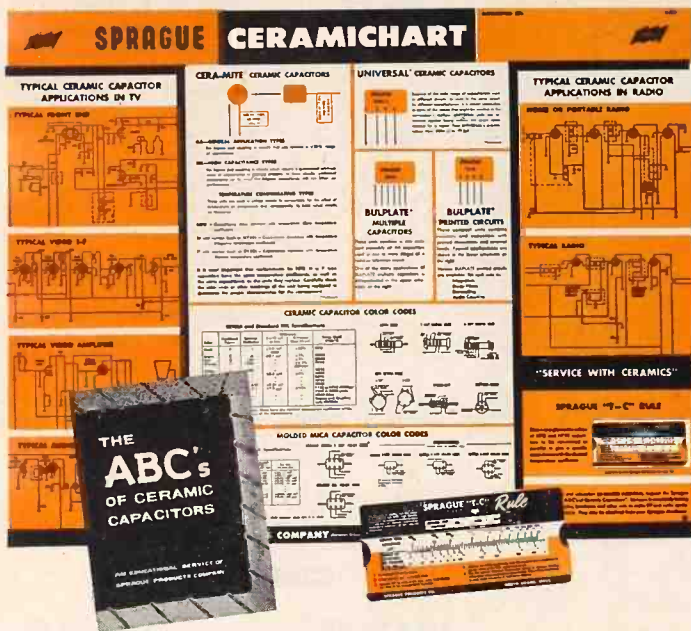... helpful **INFORMATION** on what, when, and how
of ceramic capacitors



Sprague offers you plenty of service information ... the kind you need and use everyday:

Sprague CERAMICHART: illustrates various types of ceramic capacitors and shows where to use them; details color codes.—FREE

Sprague "ABC's of Ceramic Capacitors": a compact booklet containing basic facts on all types of ceramic capacitors.—FREE

Sprague "T-C" Slide Rule: shows at a glance the values of the N750 and NP0 type ceramic capacitors to connect in parallel to equal a capacitor of desired intermediate temperature coefficient of the required capacitance; available from your distributor for only 15c.

Be sure you get this useful and valuable information from your Sprague distributor, today! Or write Sprague Products Co., Distributors' Division of Sprague Electric Company, 71 Marshall Street, North Adams, Mass.

Pioneer in ceramic capacitors ... First in ceramic capacitor information


don't be vague ... insist on

SPRAGUE®

world's largest capacitor manufacturer


SPRAGUE RESEARCH IS CONSTANTLY PRODUCING NEW AND BETTER CAPACITORS FOR YOU.

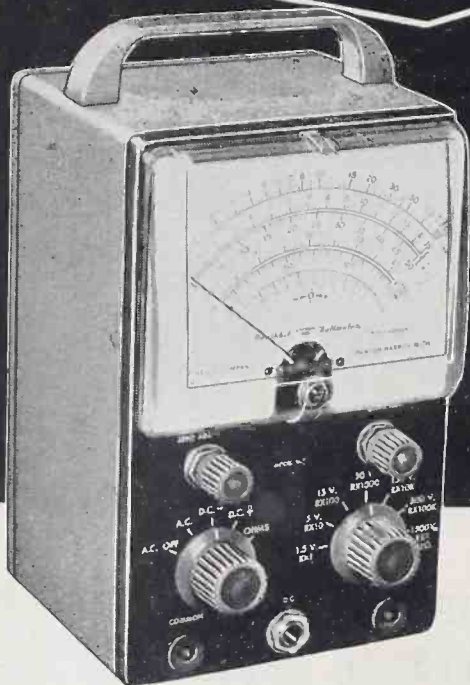look what **\$24⁵⁰** buys
in test equipment!



**HEATHKITS
GIVE YOU
TWICE AS MUCH
equipment for
every dollar
invested**

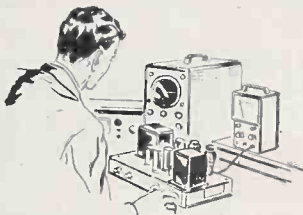The famous model V-7A Vacuum-Tube-Voltmeter is a perfect example of the high-quality Instruments available from Heath at 1/2 the price you would expect to pay! Complete, only **\$24⁵⁰**



Get the most out of your test equipment budget by utilizing HEATHKIT instruments in your laboratory or on your production line. Get high quality equipment, without paying the usual premium price, by dealing directly with the manufacturer, and by letting engineers or technicians assemble Heathkits between rush periods. Comprehensive instructions insure minimum construction time. You'll get more equipment for the same investment, and be able to fill your needs by choosing from the more than 100 different electronic kits by Heath. These are the most popular "do-it-yourself" kits in the world, so why not investigate their possibilities in your particular area of activity! Write for the free Heathkit catalog now!



Contains detailed descriptions of Heathkit models available, including VTVM's, scopes, generators, testers, bridges, power supplies, etc.



Also describes Heathkit ham gear and hi-fi equipment in kit form. 100 interesting and profitable "do-it-yourself" projects!

FREE catalog

Mail coupon below for your copy—Now!

HEATH COMPANY
A SUBSIDIARY OF DAYSTROM, INC.,
BENTON HARBOR 29, MICHIGAN

Name _____
Address _____
City & Zone _____
State _____

EDITORIAL STAFF

- Sanford R. Cowan Publisher
Oscar Fisch Editor
Irving Tepper Associate Editor
Robert T. Dargan Technical Editor
San D'Arcy Contributing Editor
Paul Goldberg Contributing Editor
Elbert Robberson Marine Communications Editor
Lawrence Fielding Hi-Fi & PA Editor
David Fish Art Director
Selma Uslaner Research

BUSINESS STAFF

Advertising Sales

- New York and East** Richard A. Cowan
Jack N. Schneider
300 West 43rd Street
New York 36, N. Y.
JUdson 2-4460
- Chicago and Midwest** Jim Summers
Suite 556
Pure Oil Building
35 E. Wacker Drive
Chicago 1, Ill.
ANdover 3-1154
- West Coast** Ted E. Schell
2700 West 3rd Street
Los Angeles 57, Calif.
DUUnkirk 2-4889
- Charles W. Hoefler
1664 Emerson Street
Palo Alto, Calif.
DAvenport 4-2661

Charles W. Gardner, Jr. Production Mgr.

CIRCULATION

- Harold Weisner Circulation Mgr.
Carol J. Binderman Ass't Circulation Mgr.
Rose Mercurlo Circulation Dept.

ELECTRONIC SERVICING (formerly Radio-TV Service Dealer) is published monthly by Cowan Publishing Corp., 300 West 43rd Street, New York 36, New York, JUdson 2-4460. Subscription Price: \$3.00 one year, \$5.00 two years in the United States, U. S. Possessions, Canada and Mexico. Elsewhere \$1.00 per year additional. Single copies 50¢. Second Class Mail privileges authorized at New York, N. Y. Copyright 1958 by Cowan Publishing Corp.

POSTMASTER: SEND FORM 3579 TO
ELECTRONIC SERVICING, 300 WEST
43rd STREET, NEW YORK 36, N. Y.

ELECTRONIC SERVICING

VOL. 19, NO. 6

JUNE, 1958

Member




Servicing With An Absorption Analyzer by M. Tepper	4
Answerman	6
Complete Manufacturer's Schematics	
Westinghouse Transistor Radio Model V2278-4	9, 10
Oldsmobile-Delco Auto Radio Model 989129	11, 12
Hoffman TV Model 332-332U	13, 20
Hoffman TV Model 334-334U	14, 19
Travler TV Model 631-56	15, 18
Travler TV Model 72916	16, 17
Zenith Transistor Radio Model 500D	21, 22
Video Speed Servicing Systems	23-26
Admiral 14YP3B Motorola TS423	
Workbench by Paul Goldberg	28
Trade Literature	29
Shop Hints and Short Cuts ..	32

Entire Contents, Copyright 1958,
Cowan Publishing Corp.

COWAN PUBLISHING CORP.,
300 West 43rd Street,
New York 36, N. Y.

CDR ROTORS

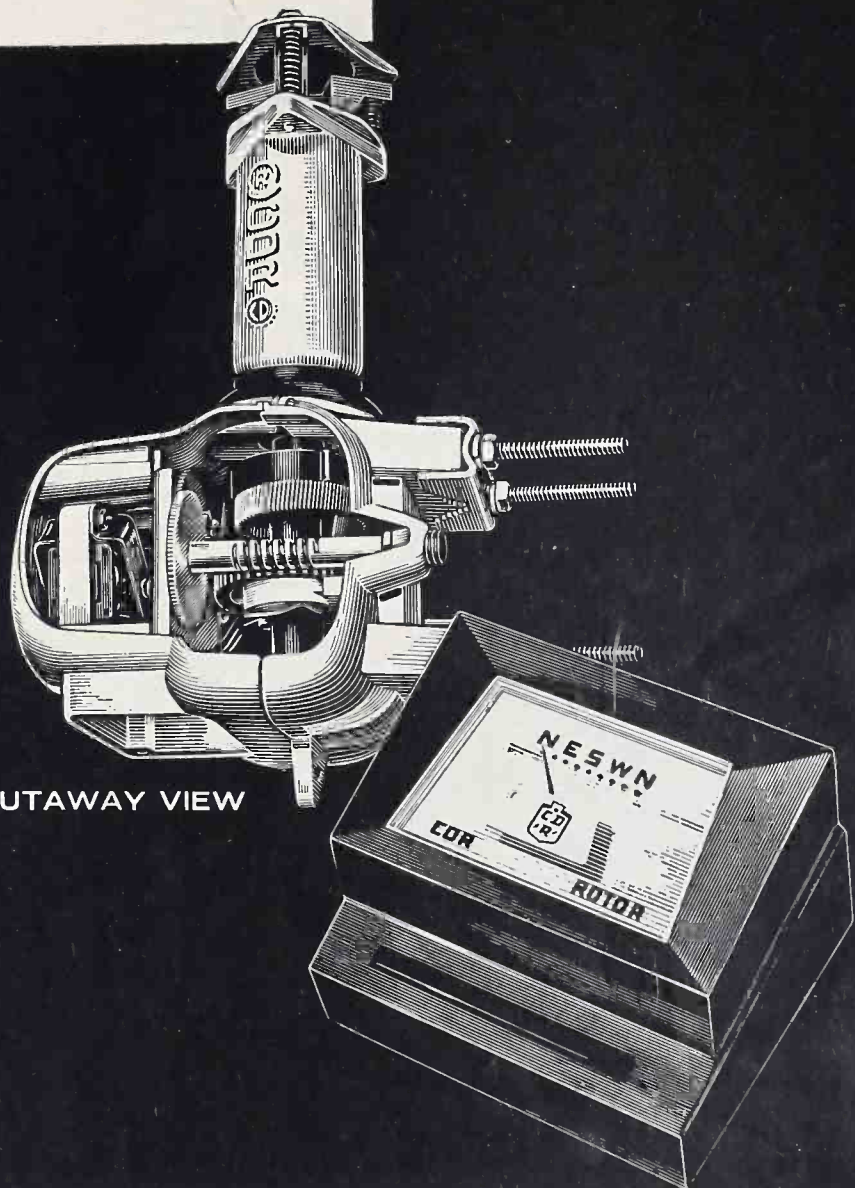

CUTAWAY VIEW

All new features

Completely designed from the ground up, CDR Model TR-15 and TR-16 Rotors have features never before available in the popular price range. Check these refinements and you'll see why: Quick mounting mast collet... speedy installation (no loose parts to assemble)... self-centering sawtooth clamps take masts up to 1½" O.D.... instant locking prevents drift... mechanical brake releases magnetically... instantly reversible... makes complete revolution in 45 seconds... meets JAN salt water test... great strength thrust bearing support... low weight... completely weather-sealed... fits standard towers... streamlined to reduce wind resistance... mahogany or blonde finish control box. Get full details today from your local CDR distributor.

CORNELL-DUBILIER ELECTRIC CORP.
South Plainfield, New Jersey

THE RADIART CORPORATION
Indianapolis, Indiana



CDR Antenna Rotors

Old Hands at Dependability

Servicing With An Absorption Analyzer

by M. Tepper

An absorption analyzer is a useful piece of test equipment. The techniques for using this device are discussed in this article.

TIME is money. Any device that will enable a service technician to cut the length of time required to service a receiver is a money-saver.

A typical absorption analyzer,* (Fig. 1) is a dynamic test equipment unit capable of extremely fast and



Fig. 1—Absorption analyzer and probe. Note the few controls.

probe, by its special shape and design, is capable of being capacity coupled to the signal in the plate circuit of a tube. Since the plate of a vacuum tube is the outermost electrode, placing a circular metal conductor about the tube envelope per-

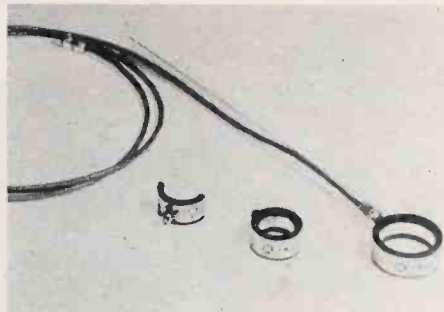


Fig. 2 — Several probe tips are supplied for different tubes.



Fig. 3—This probe permits the analyzer to be used as a scope.

mits capacitive coupling to the circuit.

Picking up the plate signal in this manner has two great advantages. First, there is no direct connection to the circuit and therefore no loading of the circuit under test. Second, the ease and speed with which it can be accomplished. As shown in Fig. 2, the probes are constructed for the various size tube envelopes. A half ring or crescent probe is for use with dual-type tubes such as the 6SN7, where each half of the tube may have a different signal. In addition to the electrostatic pick-up probe, a direct probe, (Fig. 3) with a built-in attenuator is available for conventional oscilloscope servicing with the analyzer.

Analyzer Input

The signal picked up by the probe is applied to the analyzer. The analyzer block diagram (Fig. 4) shows the basic circuits to consist of a front end, (tuner), detector and a specially designed oscilloscope. The input, if already detected, may be switched directly to the vertical amplifier of the oscilloscope. When applying an *rf*, or *if* signal, the input is switched to the appropriate position and applied to

accurate checks of circuit operation, without the necessity of removing the equipment from its cabinet. Although this article will deal mainly with the use of the instrument for service of black and white, and color TV receivers, the uses are wide and varied. Essentially the instrument can be used wherever a waveform is present in a vacuum tube circuit. This covers a lot of territory, and a lot of equipment. Some of the additional uses are in repair of radios, communication receivers, transmitters, radar, etc.

Pickup Probes

The heart of the analyzer is an electrostatic pick-up probe. The

*Kingston Electronic Corp.
Medfield, Mass.

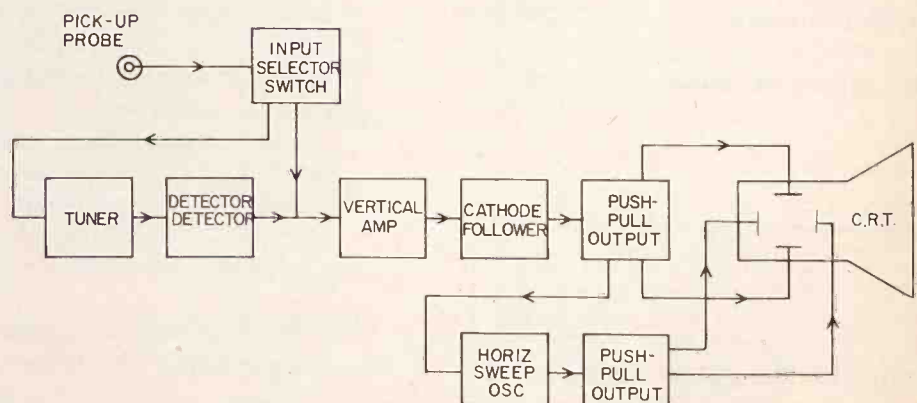


Fig. 4—The block diagram of the absorption analyzer is much the same as that of a scope except for the special input circuit.

the tuner.

The tuner is the well known Standard Coil rotary drum type, which comes complete with all 12 *vhf* channel strips. In addition, special tuner coil strips are supplied for 3.58, 4.5, 20 and 40 *mc* bands. These are inserted in place of the unused channels in the local area in which the service technician is located. These special tuner coil strips are for use with color TV circuits, intercarrier sound *if* circuits, and both 20 and 40 *mc if* circuits.

Sweep Amplifiers

The oscilloscope sweep amplifiers differ slightly with the two other analyzer models available. The analyzer model illustrated has been designed exclusively for the radio and television service technician. A quick snap of the switch will set the oscilloscope sweep circuits to the correct frequency for use with either a vertical circuit signal, or a horizontal circuit signal. Another model analyzer designed for general purpose use contains a variable frequency stepping switch permitting the selection of any desired oscilloscope sweep frequency.

Operation

Operation of the instrument in actual use is rapid and it takes more time to discuss than to do. All operations can be carried out without removal of the receiver chassis from its cabinet. The entire instrument has been designed for portable field use as well as bench use.

The use of the instrument is simple since the number of controls having been kept to a minimum. When checking an *rf* or *if* signal the input selector is set to the appropriate setting, the band selector switch, (tuner), is set for the desired channel or *if* frequency, and the oscilloscope sweep switch set to V or H for vertical or horizontal signal viewing. The probe is then used to follow the signal throughout the circuits for quick location of weak, distorted, noisy, or missing signals. The use of the electrostatic probe, permitting top-side operation, alleviates the time consuming job of disassembling a receiver. Probing about the underside of a chassis with its accompanying tedious, frustrating location of the correct tube socket, and tube socket terminal, is also reduced. The accompanying trouble shooting chart will best illustrate the ease and rapid use of the analyzer in following the signal waveforms from antenna to *crt* and speaker.

ANALYZER TROUBLE SHOOTING CHART

Circuit under test.	Test for the following:
Antenna	Test for the input <i>rf</i> signal. An open or intermittent lead-in. Use for antenna orientation. Check for incoming noise signals. Feed the lead-in through the probe, run the probe up and down the lead-in to check for standing waves.
RF Amplifier	Check for cathode to heater 60 cycle leakage. Test for weak <i>rf</i> input signal. Check for overloading and sync clipping due to wrong setting or defective <i>agc</i> , gassy tube, etc.
Oscillator and Mixer	An <i>if</i> output indicates the oscillator and mixer are operating correctly. To localize the difficulty with no <i>if</i> output, set the analyzer tuner for the correct channel. An <i>rf</i> output indicates the mixer is operating, and the difficulty is in the oscillator.
IF Amplifier	Test for increasing gain with each succeeding stage. Check for cathode to heater 60 cycle leakage. Examine the waveform for 120 cycle power supply hum. Check for overloading and sync clipping due to wrong setting or defective <i>agc</i> , gassy tube, etc. Test for noise pickup at the same frequency as that used for the <i>if</i> circuits.
Detector and Video Amplifier	Check for detected output signal. Test for gain from detector to output signal applied to the <i>crt</i> . Check for proper contrast action by examining the variation in gain while varying the contrast control.
Sync Separator	Check for the presence of sync pulses. Examine the waveform for the absence of video information. Test for the correct amplitude of the sync pulses.
AGC	To check for <i>agc</i> action, check the waveform of the <i>rf</i> amplifier, remove an <i>if</i> amplifier tube. The <i>agc</i> applied to the <i>rf</i> amplifier will increase the gain of the <i>rf</i> amplifier, increasing the amplitude of the waveform present. Replacing the <i>if</i> amplifier tube, the increased <i>agc</i> voltage will return the gain of the <i>rf</i> amplifier to normal. For series string tube circuits, varying the AGC control will indicate variation in gain in the <i>rf</i> amplifier.
Keyed <i>agc</i>	Check for the presence of horizontal pulses in the keyed <i>agc</i> tube.
Vertical Oscillator and Amplifier	Check the oscillator for sweep signal output. Test the vertical amplifier for the presence and proper amplitude of the vertical sweep voltage waveform. In receivers using the vertical pulse for vertical retrace blanking, check for the presence of the vertical blanking pulse at the signal lead of the <i>crt</i> .
Horizontal Oscillator and Amplifier	Test for the presence of the horizontal oscillator signal waveform. The shape of the horizontal oscillator waveform will vary with the type of horizontal circuit used. Test the horizontal amplifier for the presence and proper amplitude of the horizontal sweep voltage waveform. Check the damper tube operation by the presence of the horizontal output pulse waveform.
Sound <i>if</i> Amplifier	For audible signal testing plug earphones into the front panel jack labelled Sound. Test for the presence of sound at the video amplifier. Where the sound take-off is at video detector, the presence of audio will have to be tested at the sound <i>if</i> tube.

[Continued on page 28]

LEADING
SET
MAKERS
SPECIFY
TUNG-SOL

HIGH
IN PERFORMANCE

BLUE CHIP
QUALITY



TUNG-SOL[®]
Magic Mirror Aluminized
PICTURE TUBES

ELECTRON TUBE DIVISION  TUNG-SOL ELECTRIC INC.
NEWARK 4, NEW JERSEY

ANSW

Dear Mr. Answerman:

I have a condition of vertical bars appearing in the left portion of the picture on an Emerson chassis 120381-M that I don't seem to be able to eliminate. I have checked the circuits thoroughly and nothing appears to be defective. The only possible reason I can find for the deflection circuit ringing is the fact that the customer has just moved into a new home where the line voltage is abnormally high. The high B plus voltage may be causing the trouble. If this is the case what can you suggest I do?

L. G.
Dallas, Texas

Horizontal deflection coil ringing produces a fluctuation in the horizontal deflection magnetic field. This causes the electron beam to slow down or speed up according to the nonlinearity or ripple developed in the deflection current sawtooth for each horizontal line. Thus, vertical bars result, generally on the left side of the picture. This condition is different from that of each line being displaced vertically due to a defect in the vertical deflection system. It is therefore most important to determine which type of trouble is being experienced. In other words, defects in the picture on the left side can be due to ringing in the horizontal deflection coils, an unbalance between the two deflection coils or an excessive coupling between the horizontal and vertical deflection coils. To be able to correct the condition requires that the nature of the problem be known.

If examination reveals that the vertical bars are the result of ringing in the horizontal deflection system, it is quite possible, as you mention, that the high line voltage has brought about the nonlinearity or ringing in the horizontal deflection circuit. Since you have most probably checked

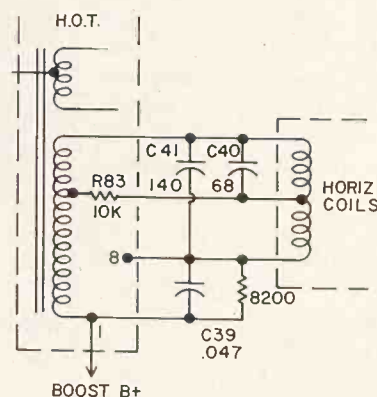


Fig. 1—Flyback transformer for the Emerson 120381M.

the condensers shown in Fig. 1, the next step that can be taken is to make several changes that will possibly clear up the condition. Resistor R83 can be reduced from 10K ohms to 2.2K ohms adding to the damping affect of this resistor. Capacitor C39, .047 mf, can be removed from its connection at terminal #1 of the horizontal output transformer and connected directly to the 255 volt source which will also decrease the possibility of deflection circuit

ERMAN

resonance.

Of course, the possibility exists that at some previous time the yoke may have been replaced by a supposed equivalent substitution and now with the higher B plus the ringing is more pronounced. It may very well be that more capacity is required to lower the resonant frequency of the horizontal windings and thereby reduce the susceptibility to ringing. Therefore if the condition persists vary the capacitances of C40 and C41 to see if the condition can be corrected. Another 68 mmf might be added in parallel with the existing condenser C40.

If the inspection of the picture has revealed that the vertical bars are the result of the electron beam being displaced vertically it is most likely occurring because of a large amount of capacitive coupling between the horizontal and vertical windings of the yoke. This allows a horizontal deflection on pulse to be coupled into the vertical deflection coil.

This latter type of picture distortion is frequently reduced or eliminated by adding a condenser of about 270 mmf between the horizontal and vertical windings of the yoke. Connect the condenser between the center of the vertical winding and the rf ground side of the horizontal winding thereby bypassing the high frequency pulses to rf ground potential. If the addition of a condenser does not correct the condition it is suggested that the yoke be replaced with a replacement recommended by the receiver manufacturer.

Dear Mr. Answerman:

We have a problem with a 27 series Magnavox TV receiver which you may be able to help us with. There is a hum or horizontal bright bar across the center of the picture which I have been unable to eliminate. I have checked by substitution all tubes in the receiver which might cause such a hum in the picture, and tested all the electrolytic condensers, etc. We would appreciate any thoughts you may have that might permit us to correct this trouble.

E. C.
St. Louis, Mo.

The Magnavox Service News Letter made available through their general service manager mentions in the

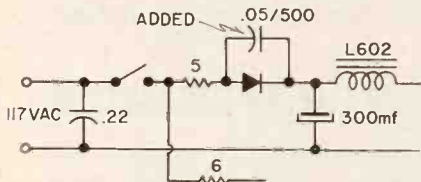


Fig. 2—Power supply change to eliminate hum bar.

April 3, 1958 issue a correction for this possible trouble. The letter states that a .05 mf, 500 volt ceramic capacitor should be shunted across the power rectifier as shown in Fig. 2 to eliminate the hum bar. Evidently the power rectifier is radiating a pulse which is being picked up somewhere along the video signal path and applied to the picture tube.

[Continued on page 30]


LEADING INDEPENDENT SERVICE DEALERS CHOOSE TUNG-SOL

LOW IN CALLBACKS



BLUE CHIP
QUALITY

TUNG-SOL® RECEIVING TUBES

ELECTRON TUBE DIVISION  TUNG-SOL ELECTRIC INC.
NEWARK 4, NEW JERSEY

AVAILABLE AT YOUR ELECTRONIC PARTS DISTRIBUTORS



1584
PAGES

only \$3⁵⁰

1958 RADIO-ELECTRONIC MASTER

(22nd edition)

FOR PURCHASING STANDARD STOCK
PRODUCTS FROM DISTRIBUTORS

TV - RADIO - AUDIO - ELECTRONICS

Completely catalogs over 150,000 standard electronic parts and equipment necessary to radio-TV-audio and industrial servicing. It places the entire electronic industry at your fingertips!

World's largest and most referred to electronic buying guide contains • complete product descriptions • specifications • 11,500 illustrations • prices

when you BUY AND SELL

You can immediately find out...What product best fills your needs? How does it compare with other makes? What does it look like? What does it cost?...because the MASTER is systematically arranged in 18 product sections with all similar products grouped together.


YOU OPERATE MORE EFFICIENTLY, MORE PROFITABLY WITH THE MASTER

The MASTER describes, illustrates, lists specs of all items necessary to radio-TV servicing. What's more — it offers thousands of additional products that can lead to extra income in Hi-Fi, sound and industrial servicing. You can buy, sell and bill direct from The MASTER. It shows list prices! It's invaluable at the bench, over-the-counter or in the field. Remember, no matter what product or component you require...YOU FIND IT FASTER IN THE MASTER!

Get your 1958 MASTER today at local electronic parts distributors or write for list. Act now — the supply is limited.

THE RADIO-ELECTRONIC MASTER

60 Madison Avenue • Hempstead, New York

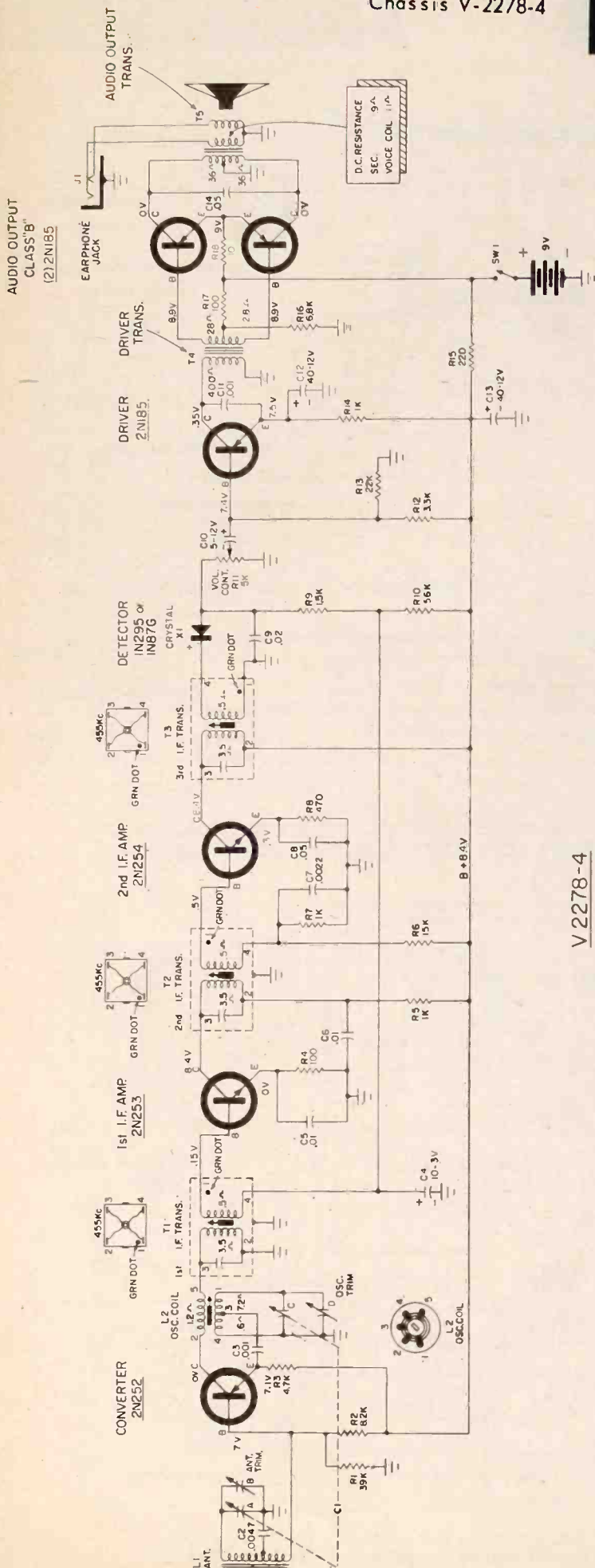

JUNCTION TRANSISTOR	
NO.	TYPE
2N252	PNP CONVERTER
2N253	NPN 1st I.F. AMPLIFIER
2N254	NPN 2nd I.F. AMPLIFIER
2N185	PNP AUDIO DRIVER
2N185	PNP AUDIO OUTPUT

V 2278-4

- NOTES:
1. DURING SERVICING, TOTAL CURRENT SHOULD BE METERED. WITH NO SIGNAL, AND VOLUME CONTROL AT MINIMUM, TOTAL BATTERY SHOULD BE APPROX. 6 MA.
 2. VOLTAGE MEASUREMENTS MADE WITH A VTVM, FROM POINTS INDICATED TO GND, WITH TUNING CAPACITOR AT MAXIMUM, VOLUME CONTROL AT MINIMUM, BATTERY SOURCE AT 9 VOLTS.
 3. AUDIO OUTPUT TRANSISTORS 2N185 MUST BE MATCHED PAIRS.
 4. ALL CAPACITORS ARE IN MICROFARADS AND RESISTORS ARE IN OHMS.

ALIGNMENT REQUIREMENTS

Signal Generator — Use generator providing modulated 455KC and AM broadcast frequencies. Connect a 4 or 5 turn loop of wire across output cable. Keep output of generator low enough to just give an indication on VTVM or output meter. Keep volume control at maximum to avoid AVC action.



Indicator — Connect VTVM or output meter across voice coil.

Receiver — Set volume control to maximum. Be sure during RF alignment that the hand or any objects on the bench do not come in close contact with the antenna loop or detuning will occur and alignment will be incorrect.

Alignment Tool — Use a fiber aligning tool that snugly fits the slot in the ferrite core to prevent chipping of the slot.

ALIGNMENT PROCEDURE


Loosely couple modulated signal to:	Generator frequency	C1 setting	Adjust for maximum:
Loop L1	455KC	maximum	T3, T2 and T1 in order. Reduce generator output if necessary for T2 and T1 adjustments
Loop L1	1625KC	minimum	Oscillator trimmer "D"
Loop L1	1400KC	1400KC	RF trimmer "B"
Loop L1	600KC	600KC	Oscillator coil, L2, if necessary

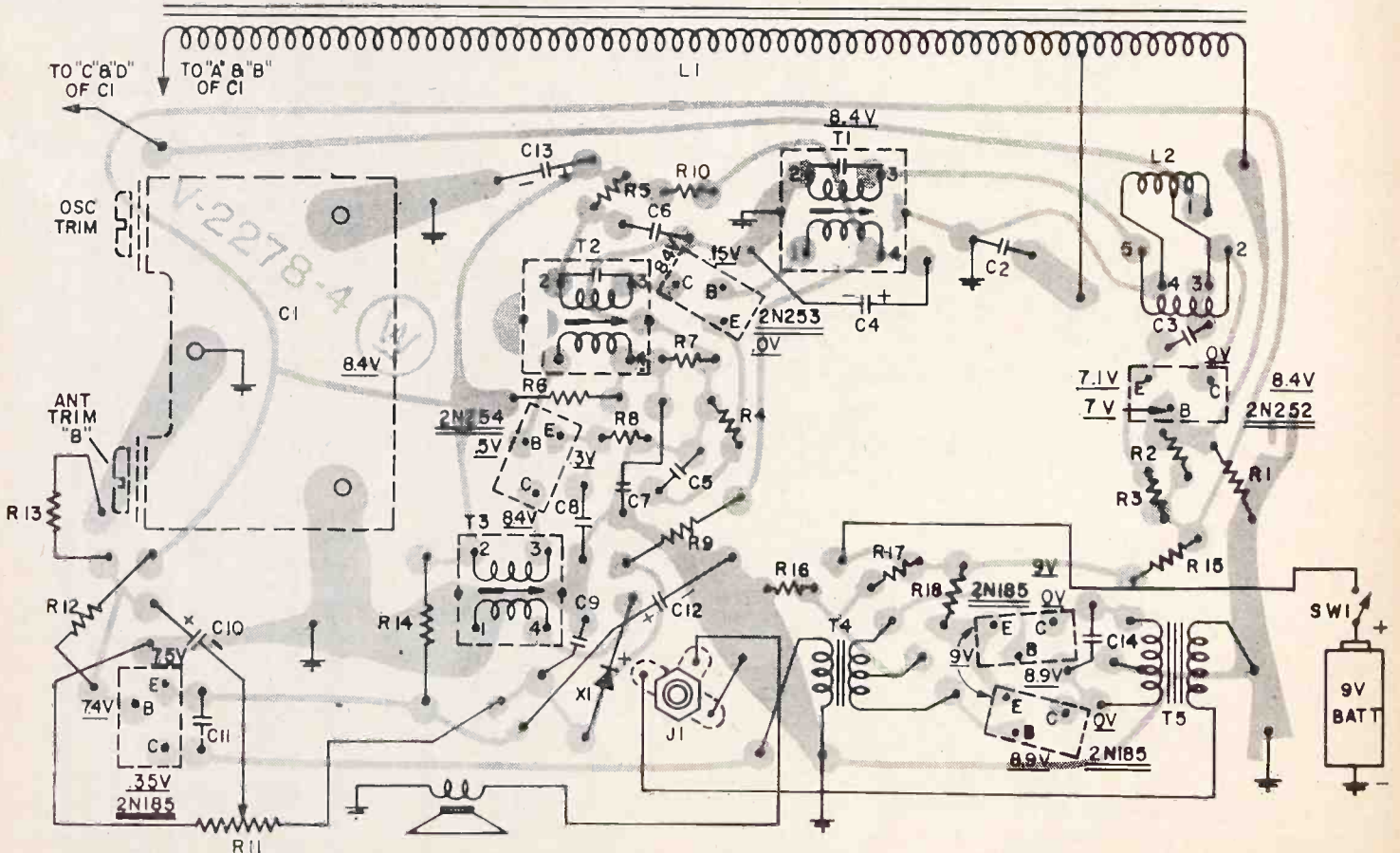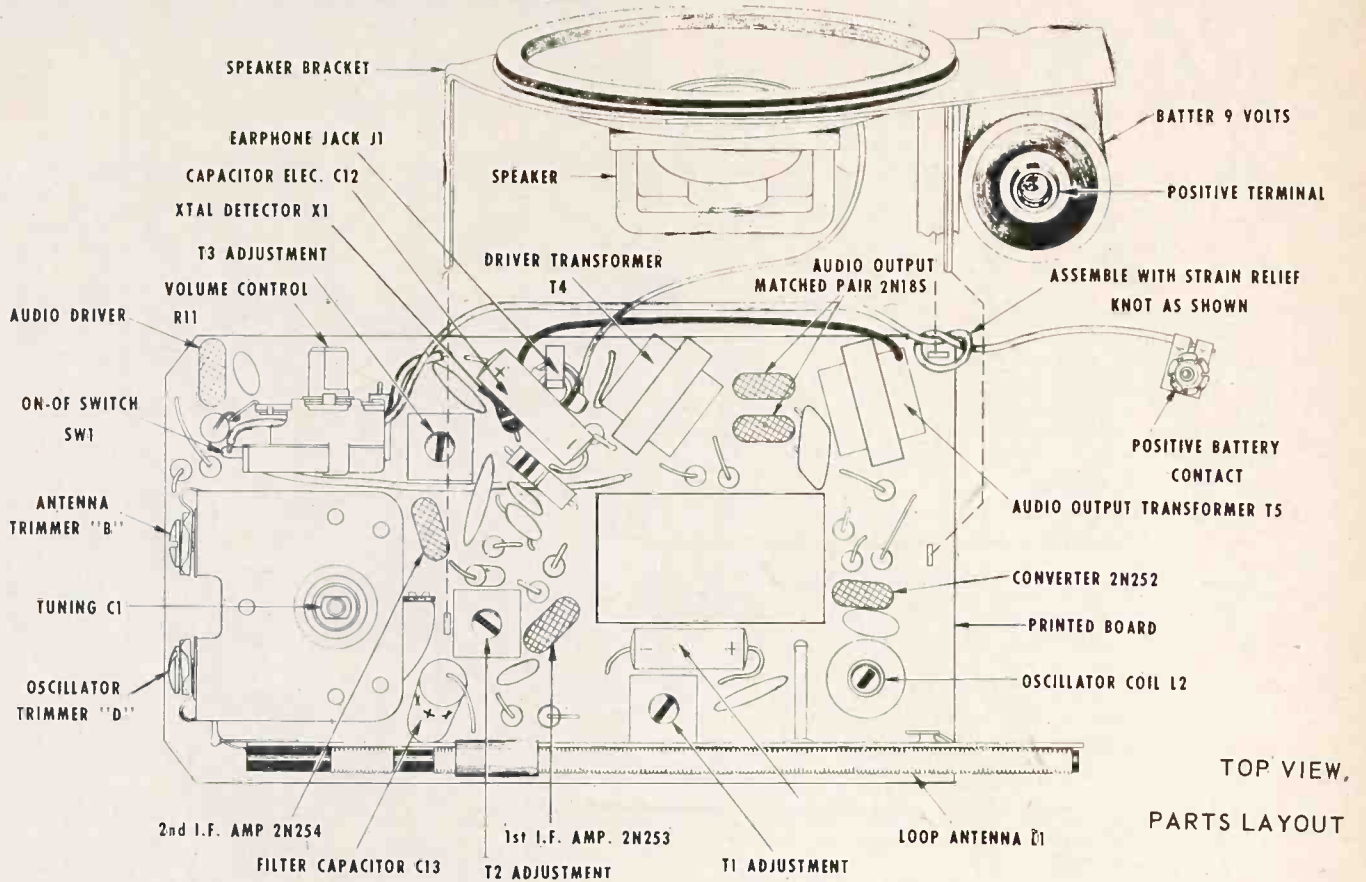

IMPORTANT!

When radio is operated on battery eliminator, the tuner may stop seeking every time a solenoid energizes, due to voltage regulation.

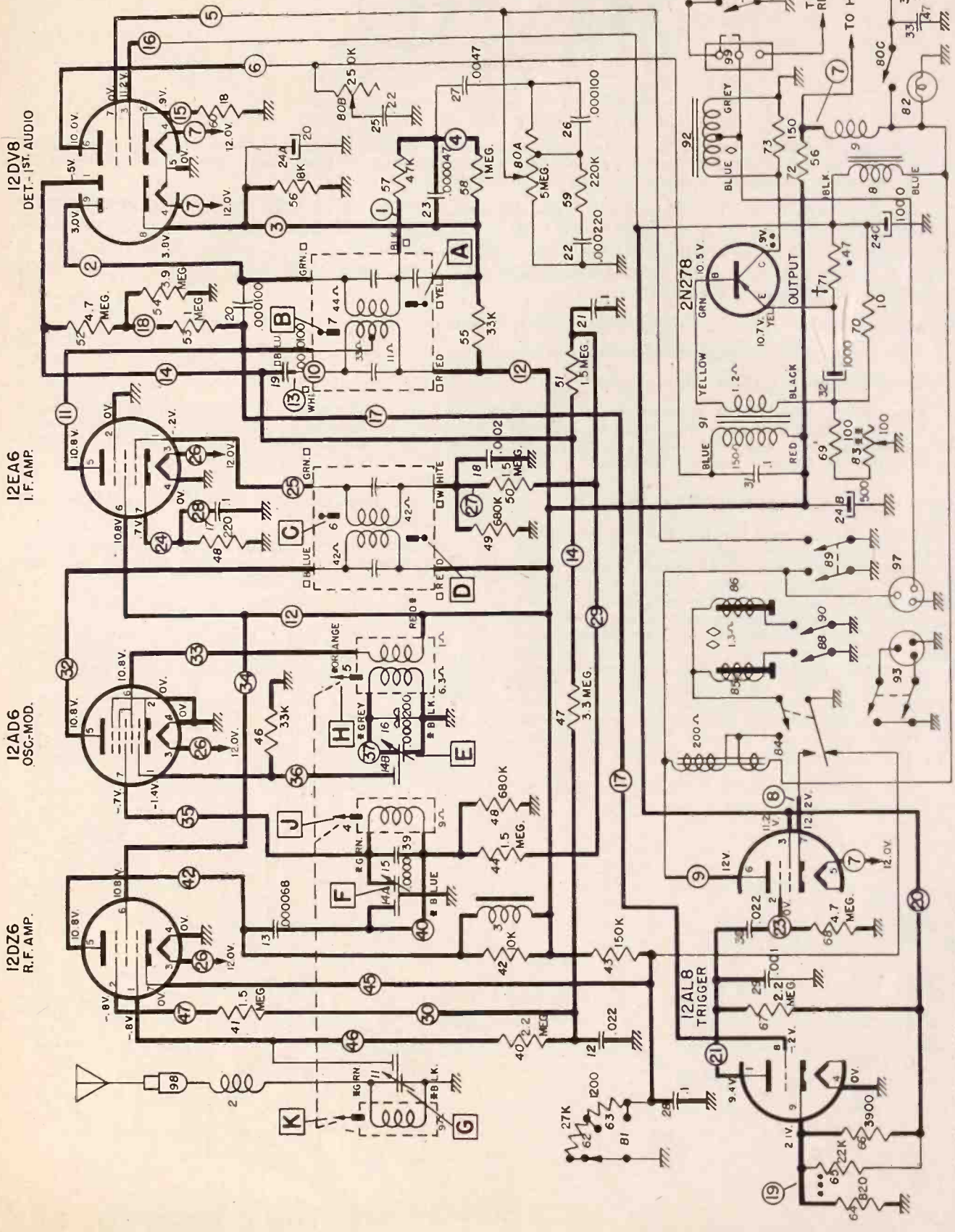
Speaker socket, Illus. 96, is a shorting-type to prevent transistor damage if speaker is disconnected. If not opened, radio will be very weak or dead.



OLDSMOBILE MODEL 989129
PRINTED CIRCUIT SHOWN IN HEAVY LINES

—TUNER CIRCUIT COMPONENTS

RECOMMENDED TROUBLESHOOTING PROCEDURE

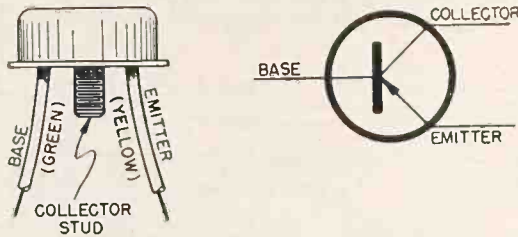

The tube stages in this receiver may be checked in the same manner as similar stages in high voltage tube circuit radios. **CAUTION:** Do not ground any point in the transistor base circuit, including the input transformer secondary, Illustration 91 as this will either damage the transistor or open the emitter resistor.

THE TRANSISTOR IS FUSED BY A FUSE TYPE RESISTOR (Illus. 71) IN THE EMITTER CIRCUIT. THIS RESISTOR OPENS QUICKLY IF A SHORT OCCURS IN THE 2N278 CIRCUIT. CHECK ACROSS THIS RESISTOR (SEE PAGE 4) USING OHMMETER ON RX1 SCALE. IF OVER 1 OHM, MOUNT A NEW RESISTOR AT THIS POINT. **CAUTION:** THIS SPECIAL RESISTOR PREVENTS FIRE, AND MUST BE REPLACED WITH EXACT PART OR WARRANTY IS VOID.

The recommended procedure for checking this radio is as follows:

1. Make certain the antenna is good, and the "A" supply voltage normal.
2. Check the tubes by substituting new ones.
3. Signal trace, using isolated (capacitor in lead) signal generator or "signal tracer." A strong audio signal injected at the 12DV8 tube plate, pin #6, should be heard in the case of a dead radio. (A quick check of the audio stage can be made with the radio warmed up by pulling out the 12DV8 tube and listening for a "click." If the "click" is heard, the transistor stage is working.)

TROUBLE SHOOTING THE OUTPUT STAGE

A quick way to determine that the 2N278 is conducting can be made by checking the collector voltage, from transistor case to the radio case. If no voltage is present, the transistor is not conducting or the transistor heat radiator is grounded to the radio case. If the voltage at the collector is higher than listed, the transistor is conducting too heavily (check with milliammeter) or the output transformer is open. The amount of current the transistor conducts is determined by the voltages at each element, the resistor in the base and emitter circuits, the input transformer secondary resistance, and the transistor itself. The most common defect in the transistor is an internal short between emitter and collector. To check for this, use the following procedure.


1. Unsolder base and emitter leads from the circuit.

2. Set ohmmeter on the "R x 1" scale (no other scale should be used.)
3. Place negative lead of ohmmeter (polarity refers to internal ohmmeter battery) on collector, and positive lead on the emitter.
4. The transistor is shorted if reading is "O."


If a transistor is replaced, the "bias" adjustment should be made for the new transistor. Adjust bias potentiometer (Illus. 83) to obtain proper collector voltage with 12 volt input to radio.

RADIO BLOWS FUSES

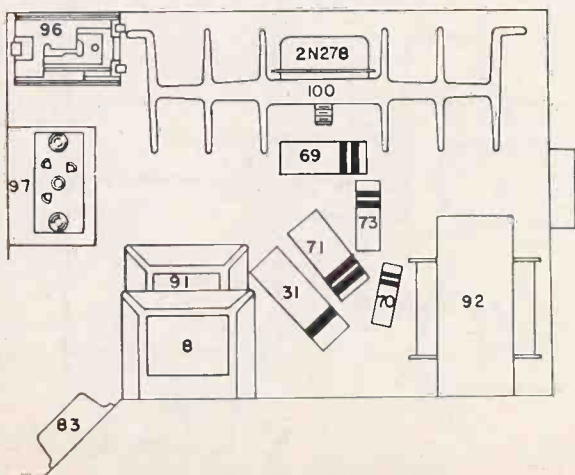If the radio blows fuses, check for a shorted transistor. If the transistor is okay, check for a short in the radio "A" supply circuit.




PARTS LAYOUT—TOP VIEW

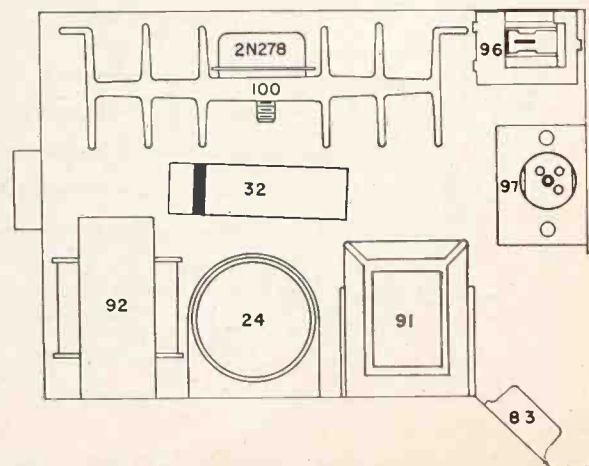


PARTS LAYOUT—BOTTOM VIEW

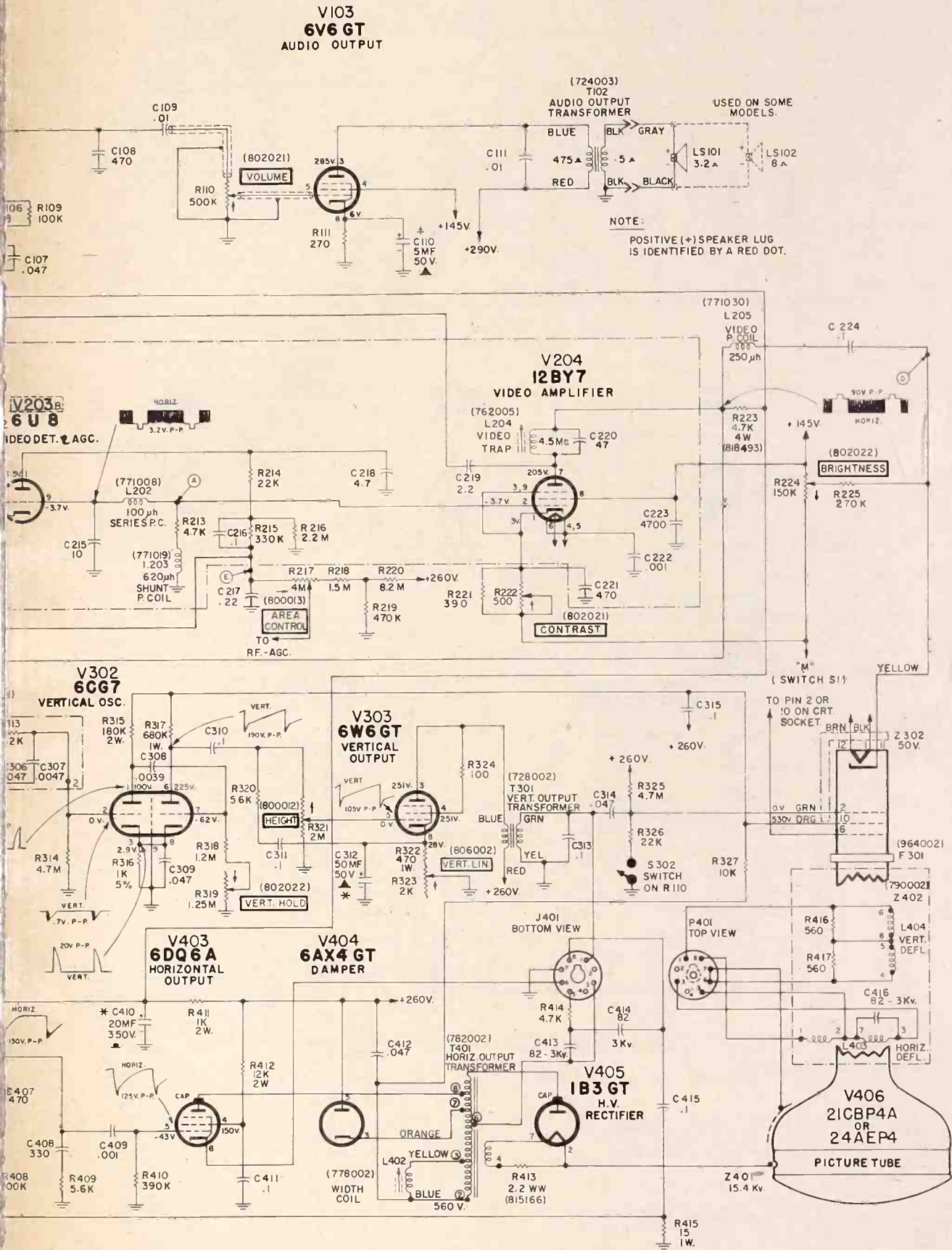Television Receiver Chassis 332, 332U, 333



MARK 10 CHASSIS 332, 332U, 333

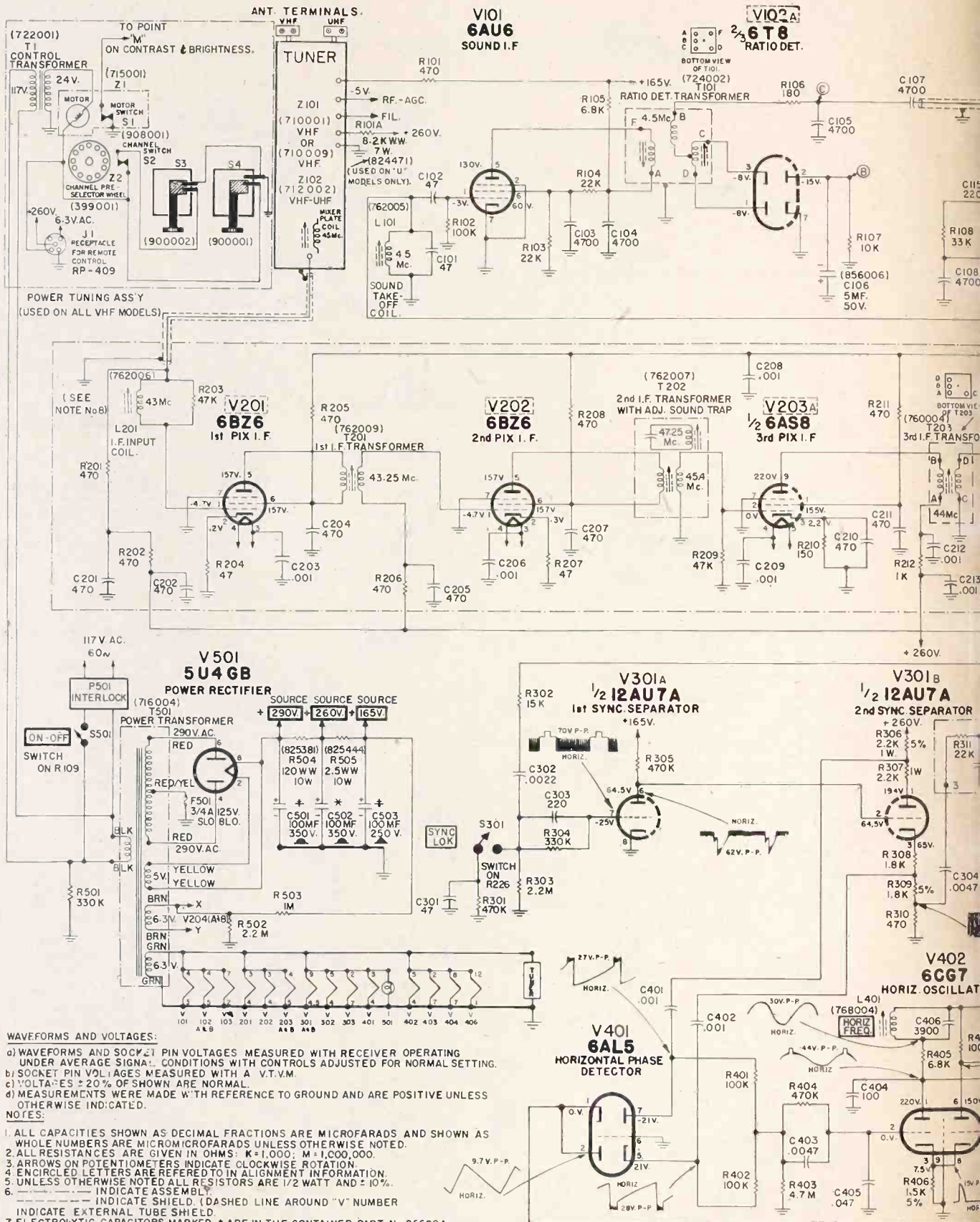

WAVEFORMS AND VOLTAGES:



- WAVEFORMS AND SOCKET PIN VOLTAGES MEASURED WITH RECEIVER OPERATING UNDER AVERAGE SIGNAL. CONDITIONS WITH CONTROLS ADJUSTED FOR NORMAL SETTING.
- SOCKET PIN VOLTAGES MEASURED WITH A V.T.V.M.
- VOLTAGES ± 20% OF SHOWN ARE NORMAL.
- MEASUREMENTS WERE MADE WITH REFERENCE TO GROUND AND ARE POSITIVE UNLESS OTHERWISE INDICATED.

NOTES:


- ALL CAPACITIES SHOWN AS DECIMAL FRACTIONS ARE MICROFARADS AND SHOWN AS WHOLE NUMBERS ARE MICROMICROFARADS UNLESS OTHERWISE NOTED.
- ALL RESISTANCES ARE GIVEN IN OHMS: K=1,000; M=1,000,000.
- ARROWS ON POTENTIOMETERS INDICATE CLOCKWISE ROTATION.
- ENCIRCLED LETTERS ARE REFERRED TO IN ALIGNMENT INFORMATION.
- UNLESS OTHERWISE NOTED ALL RESISTORS ARE 1/2 WATT AND ± 10%.
- INDICATE ASSEMBLY.
- INDICATE SHIELD (DASHED LINE AROUND "V" NUMBER INDICATE EXTERNAL TUBE SHIELD).
- ELECTROLYTIC CAPACITORS MARKED * ARE IN THE CONTAINER PART No. 856904, AND MARKED * ARE IN THE CONTAINER PART No. 856903.
- ON MODELS DENOTED CODE "AJ" THERE WILL BE AN ADDITION 47.25 Mc. ADJ. CHANNEL SOUND TRAP ON I.F. INPUT COIL L201.
- NUMERALS SHOWN IN PARENTHESIS (XXXXXX) INDICATE HOFFMAN PART No.

SCHEMATIC DIAGRAM FOR HOFFMANN

TRAVLER

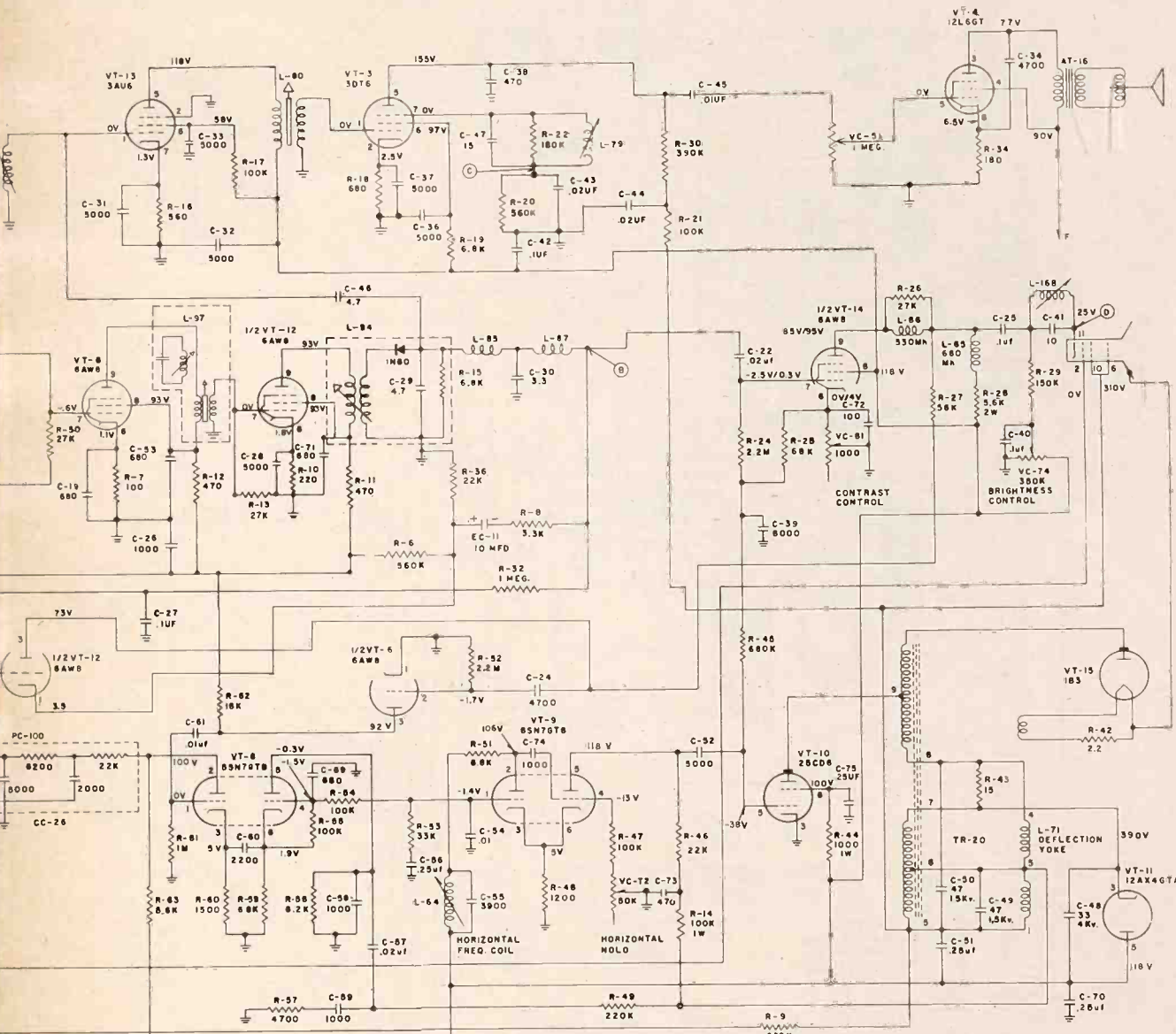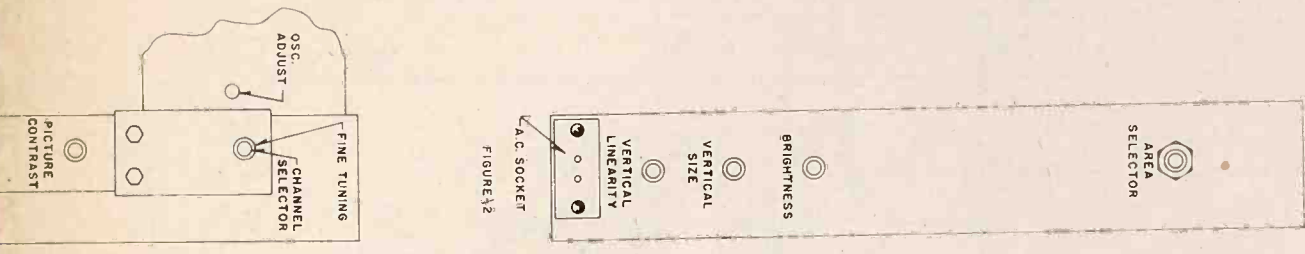

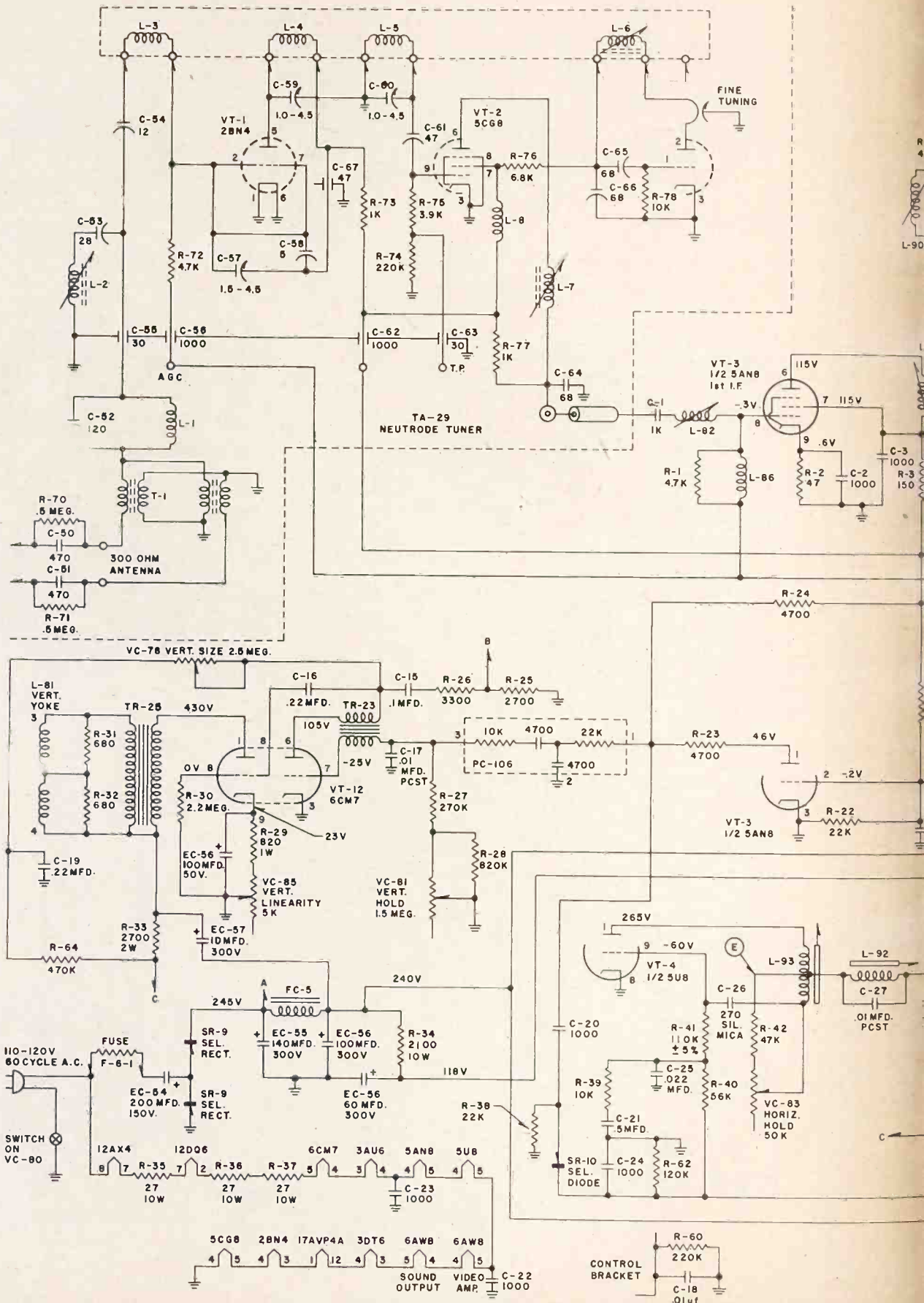
NOTE
 1- LINE VOLTAGE 117V A.C. THROUGH ISOLATION TRANSFORMER.
 2- ALL VOLTAGES SHOWN ON SCHEMATIC ARE D.C. READINGS.
 3- VOLTAGE READINGS TAKEN WITH ZERO SIGNAL INPUT USING ELECTRONIC VOLTMETER.
 4- 6AW6 VIDEO AMPLIFIER VOLTAGES ARE SHOWN AT MAXIMUM & MINIMUM SETTINGS OF CONTRAST CONTROL. ALL OTHER CONTROLS SET FOR NORMAL OPERATION.





Television Receiver Chassis 72916


TRAVLER

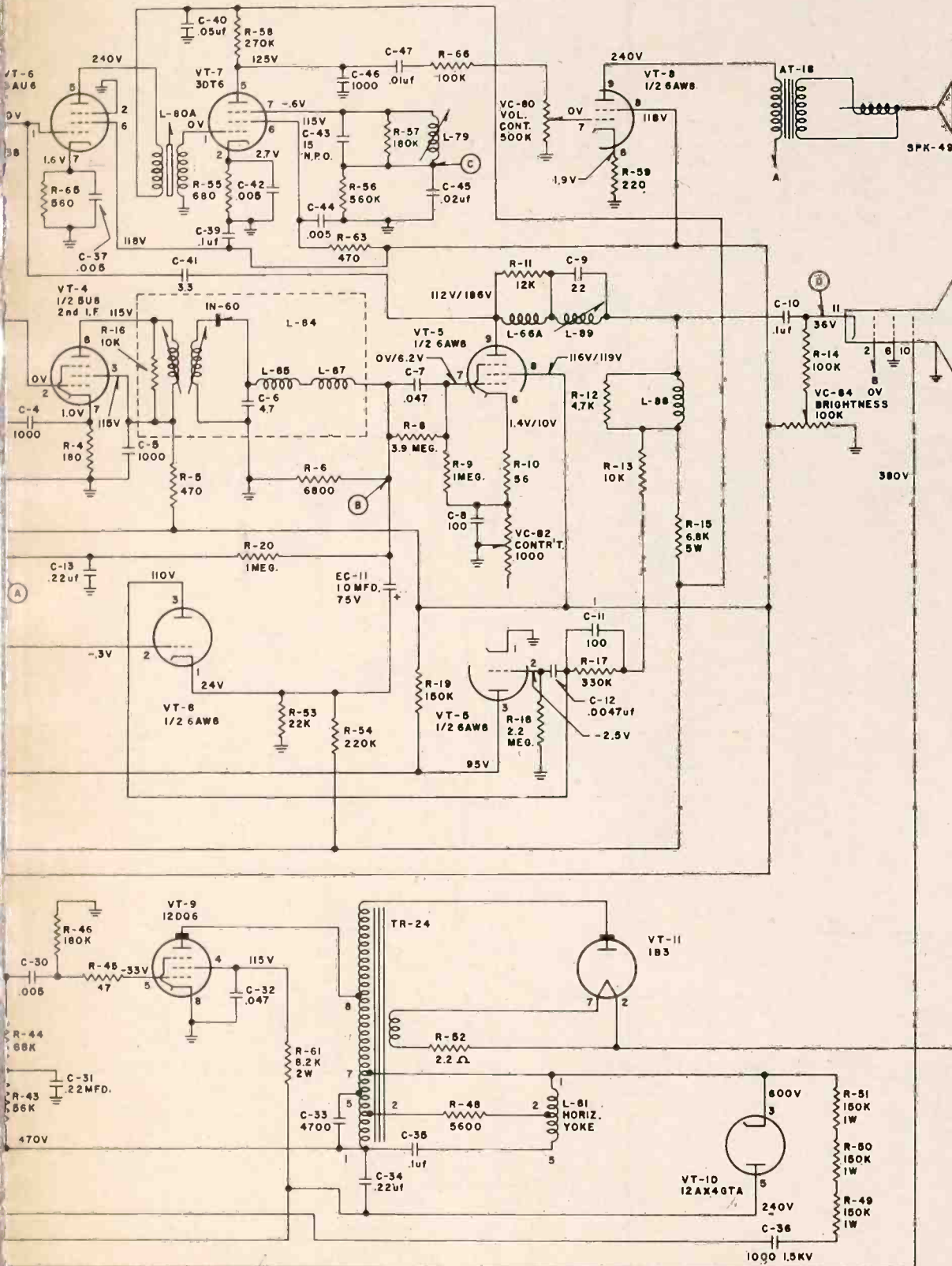- NOTE —
- 1- LINE VOLTAGE 117 V.A.C. THROUGH ISOLATION TRANSFORMER.
 - 2- ALL VOLTAGES SHOWN ON SCHEMATIC ARE D.C. READINGS.
 - 3- VOLTAGE READINGS TAKEN WITH ZERO SIGNAL INPUT USING ELECTRONIC VOLTMETER.
 - 4- 6AW6 VIDEO AMPLIFIER VOLTAGES ARE SHOWN AT MAXIMUM & MINIMUM SETTINGS OF CONTRAST CONTROL. ALL OTHER CONTROLS SET FOR NORMAL OPERATION.



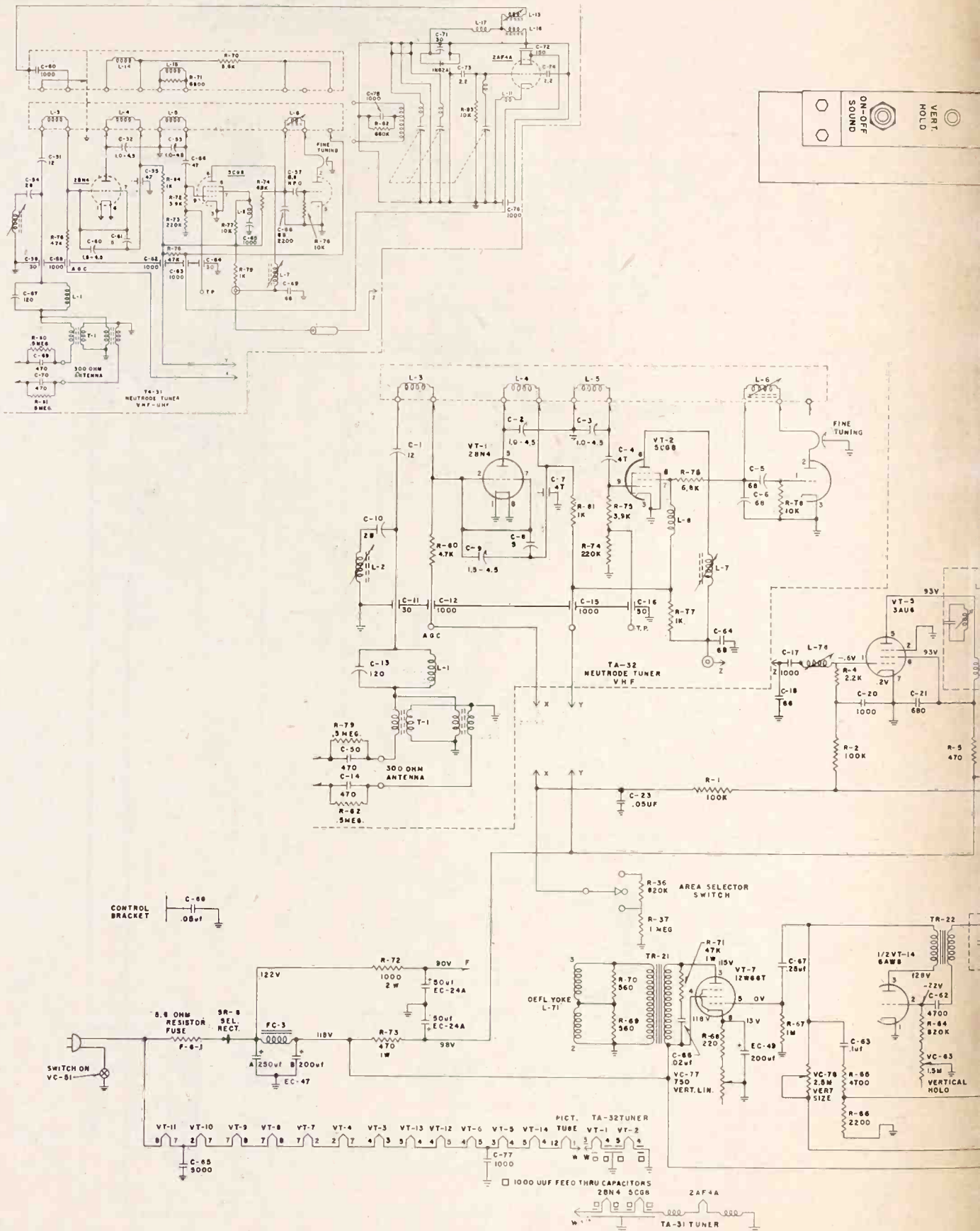

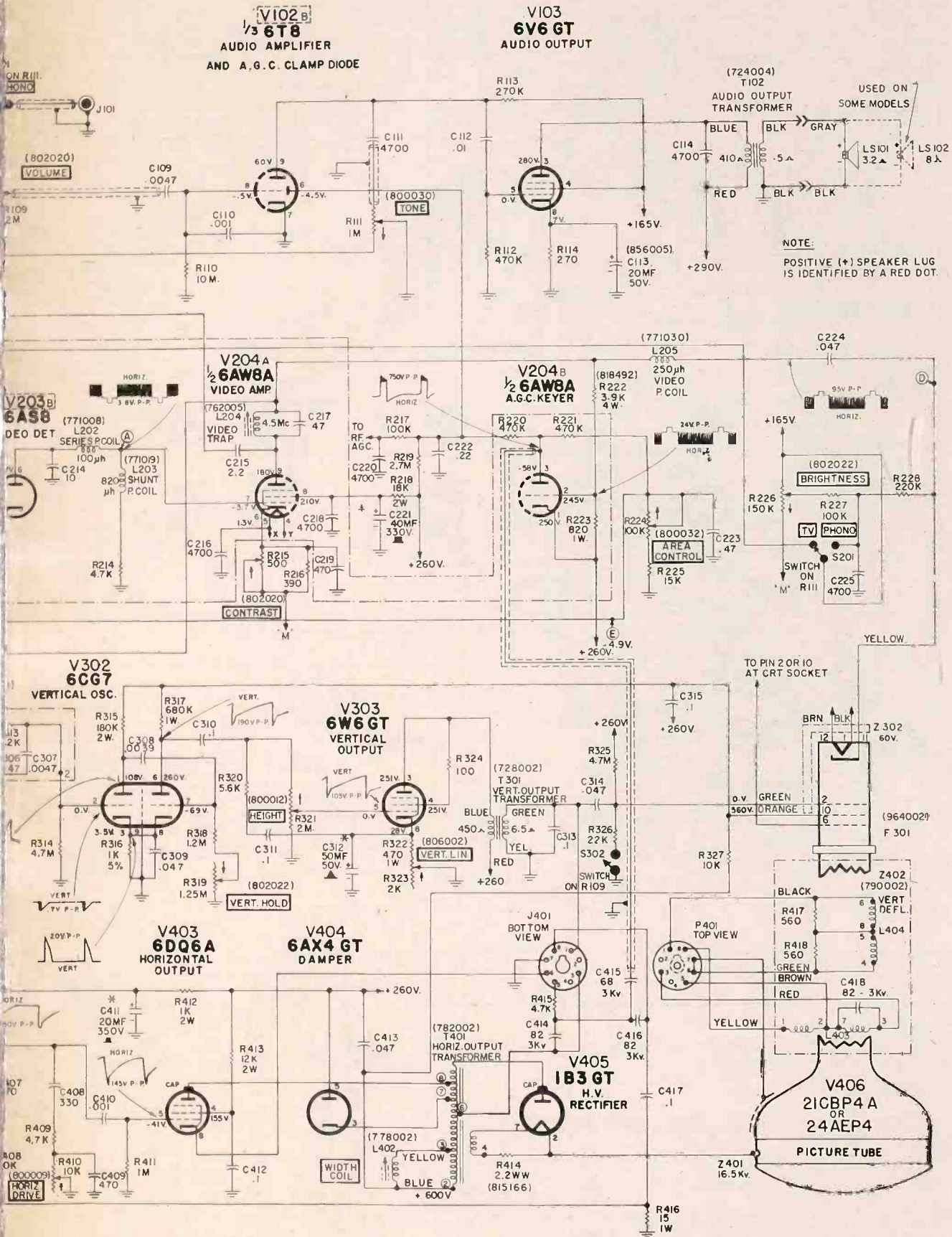



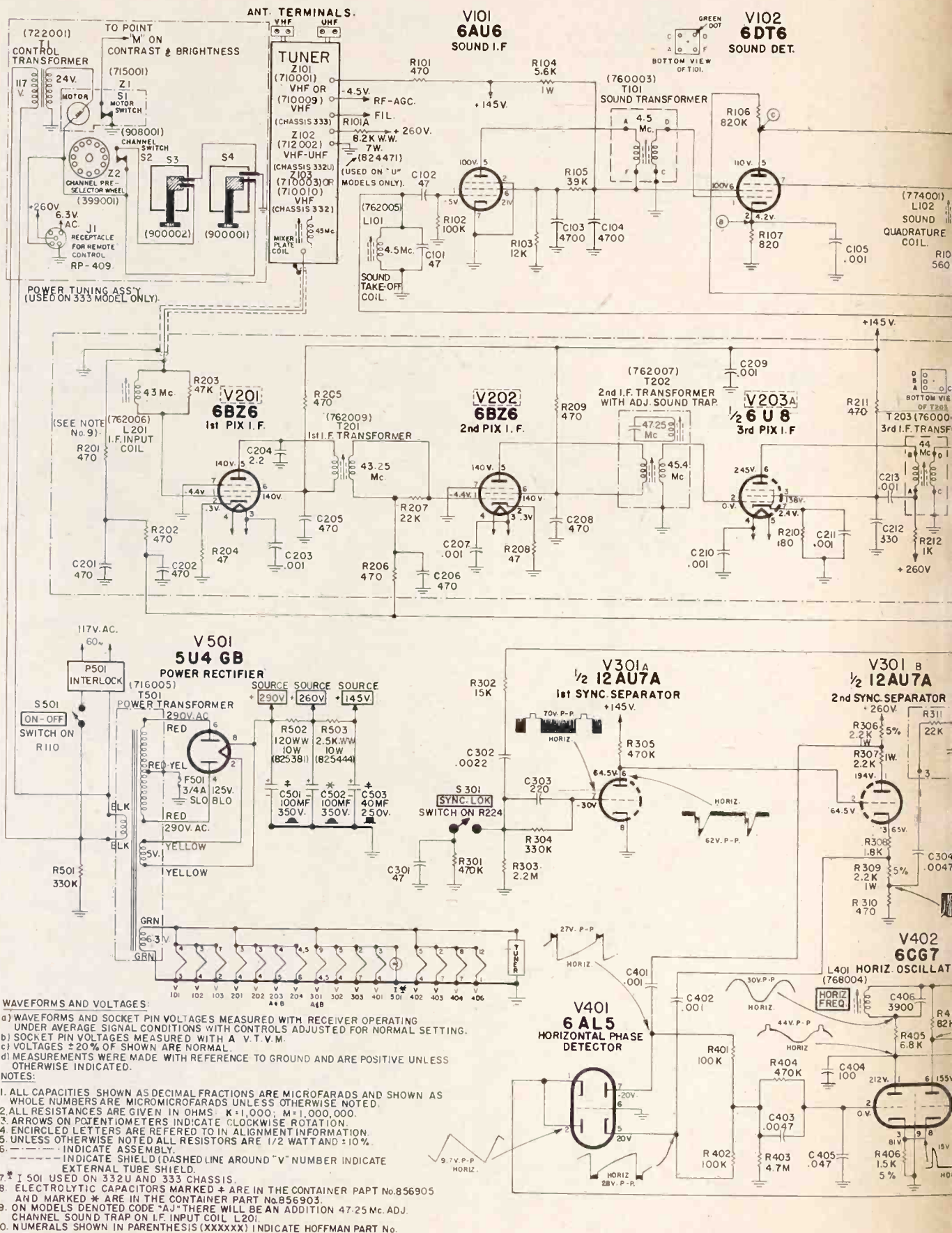


SCHMATIC DIAGRAM FOR HOFFMAN

MODEL "ROYAL 500D"

ZENITH

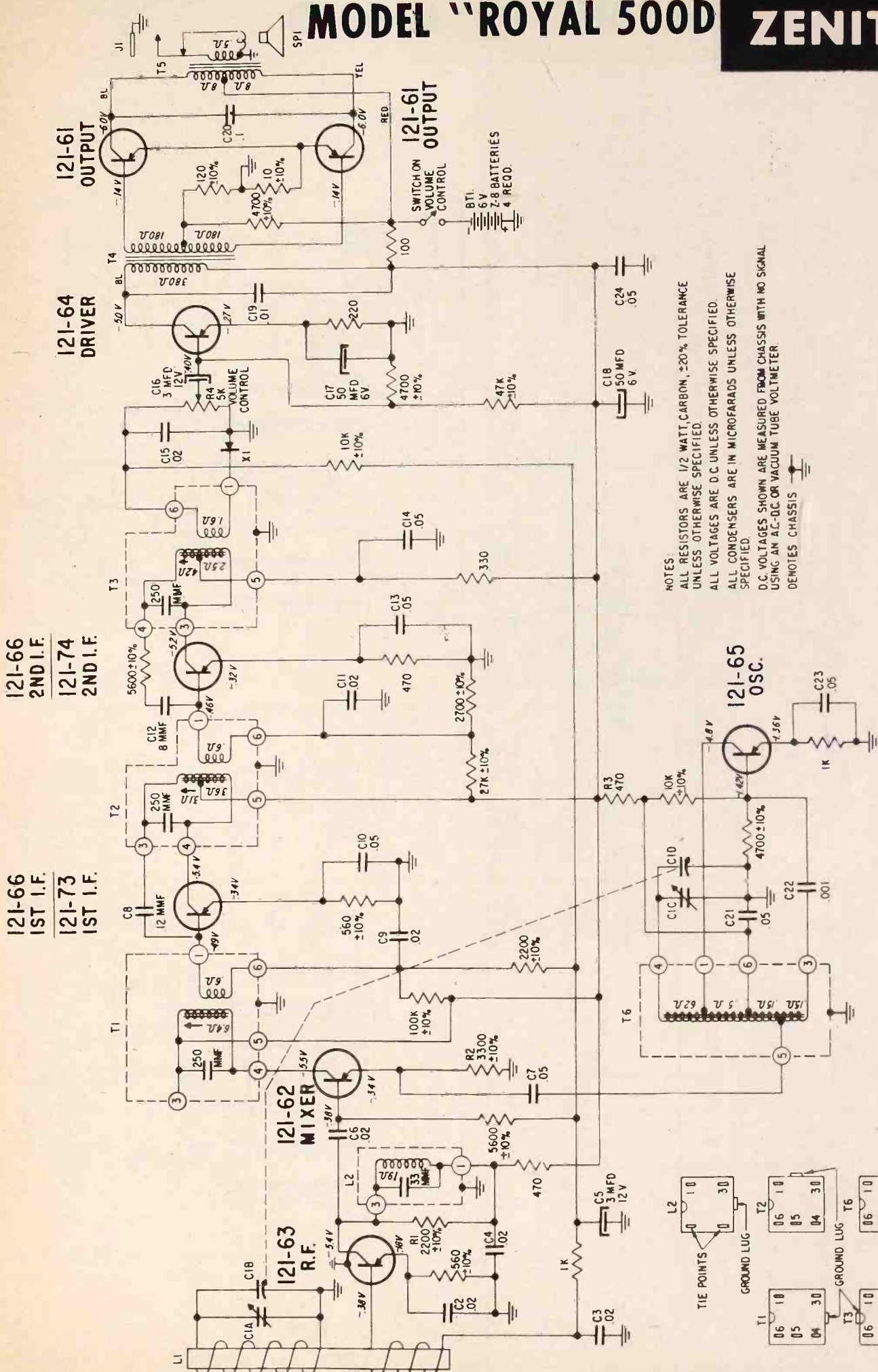

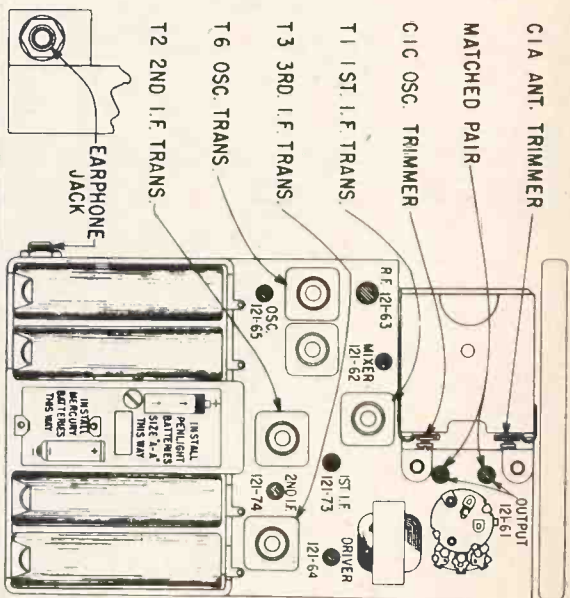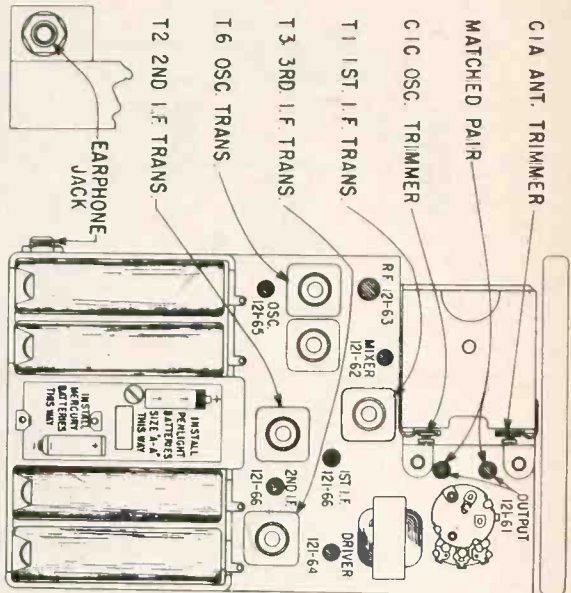

Chassis	Chassis Color Dot	Transistor Layout Label Color	Part No.	R.F.	Mixer	Osc.	1st I.F.	2nd I.F.	Crystal Diode Detector	Driver	Output-Output	Supplier
8AT40Z2	Red	Red	Zenith 121-63	PNP	121-62	121-65	121-73	121-74	103-19 IN87G	121-64	121-61	R.C.A.
8AT40Z2	Black	Black	Zenith 102-3488	PNP	121-62	121-65	121-66	121-66	103-19 IN87G	121-64	121-61	R.C.A.

ALIGNMENT PROCEDURE

Operation	Input Signal Frequency	Connect Inner Conductor From Oscillator To	Connect Outer Shield Conductor From Oscillator To	Set Dial At	Trimmers	Purpose		
1	455 KC	ONE TURN LOOSELY COUPLED TO WAVEMAGNET	Chassis	600 KC	Adj. T1, T2, T3 for maximum output.	For I.F. Alignment		
2	1620 KC			—	Gang wide open.	C1C	Set Oscillator to dial scale.	
3	535 KC			—	Gang	Adjust slug in T6	Set Oscillator to dial scale.	
4	REPEAT STEPS 2 & 3			—	—	—	—	—
5	1260 KC			—	—	1260 KC	C1A	Align loop ant.

Mfr: Admiral Chassis No. 14YP3B


Card No: AD-14YP-1

Section Affected: Sound.

Symptoms: Poor sound on very weak signals.

Reason For Change: To improve sound on weak signals by lowering Q of L202.

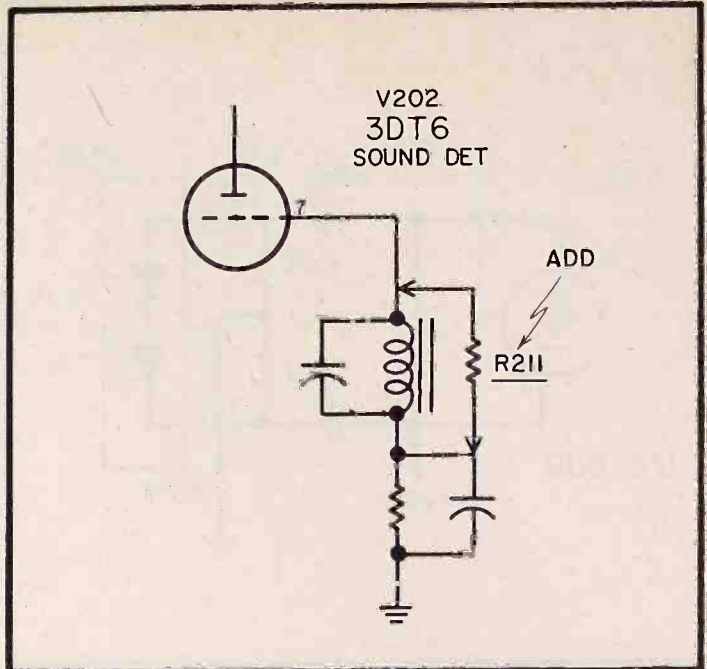What To Do: Add R211, 100K in parallel with L202.



Mfr: Admiral Chassis No. 14YP3B


Card No: AD-14YP-2

Section Affected: Raster

Symptoms: Drive lines appearing with different 12DQ6 output tubes.

Reason For Change: To reduce the possibility of drive lines with different output tubes.

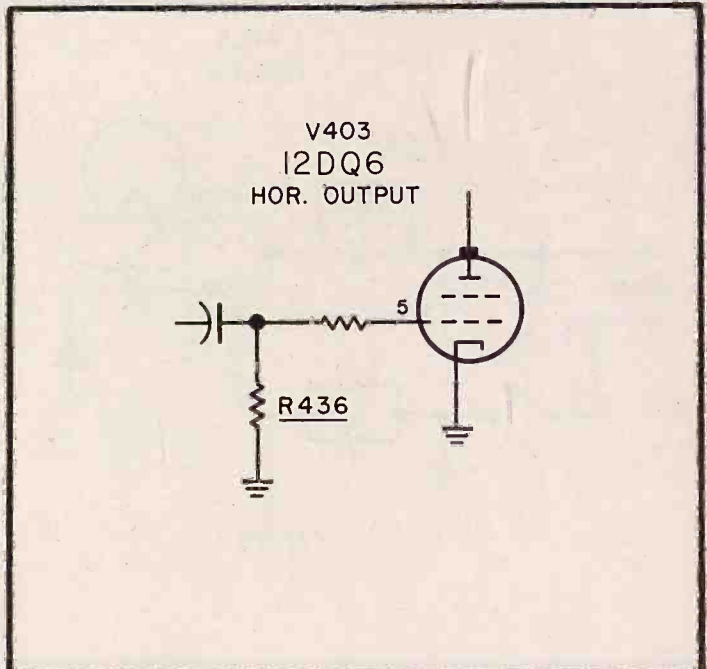What To Do: Reduce R436 from 470K to 330K.



Mfr: Admiral Chassis No. 14YP3B


Card No: AD-14YP-3


Section Affected: Raster

Symptoms: Excessive brightness. Little or no brightness control action.

Cause: Leakage or short in C410, part of printed circuit M401.

What To Do: Replace M401.

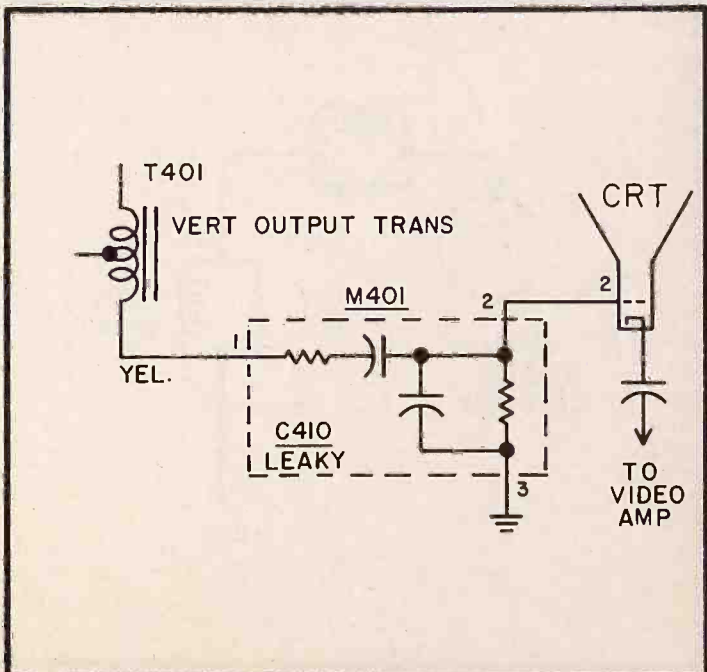

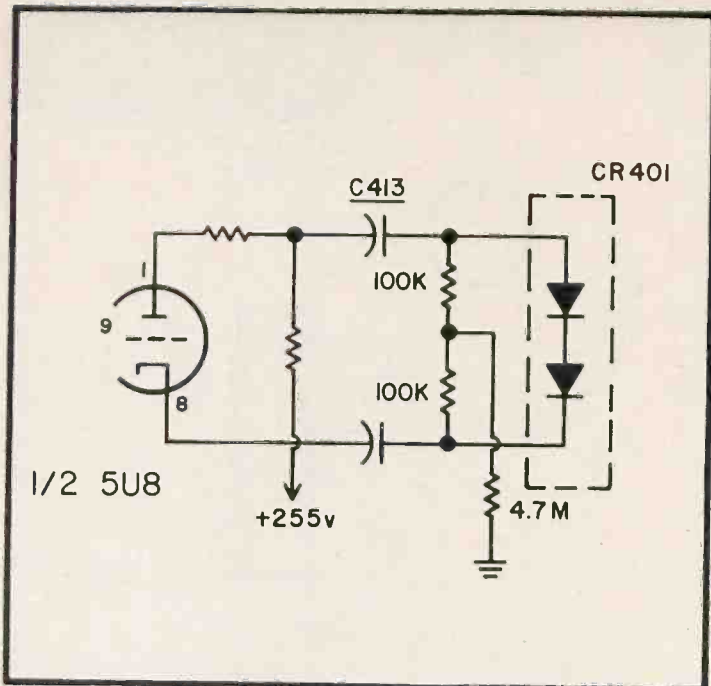

Mfr: Admiral

Chassis No. 14YP3B


Card No: AD-14YP-4

Section Affected: Raster

Symptoms: No raster.

Cause: Shorted C413.

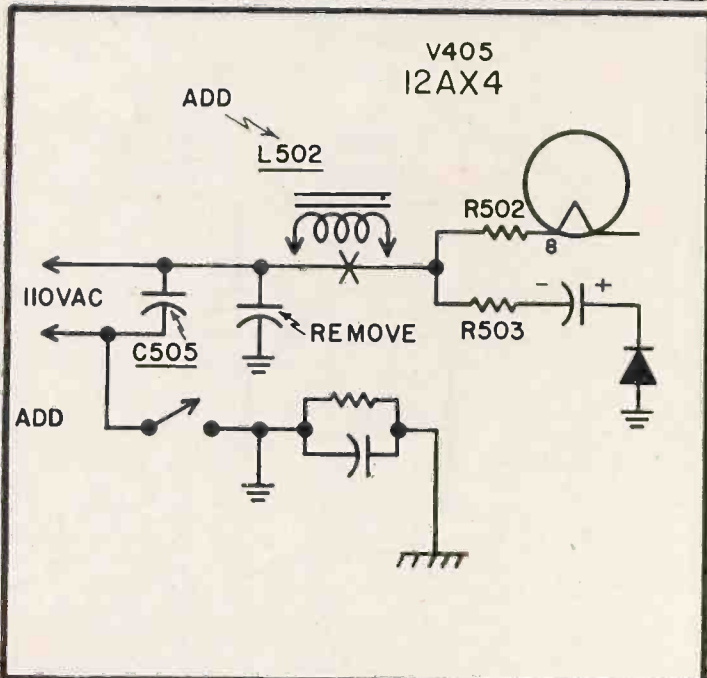What To Do: Replace C413, .001 mfd. It is also possible that the excessive positive voltage applied to the diodes CR401 may damage them and require their being replaced.



Mfr: Admiral

Chassis No. 14YP3B


Card No: AD14YP-5

Section Affected: AC Line

Symptoms: Horizontal radiation interference through ac line.

Reason For Change: To suppress horizontal sweep radiation reducing beat interference on am radios.

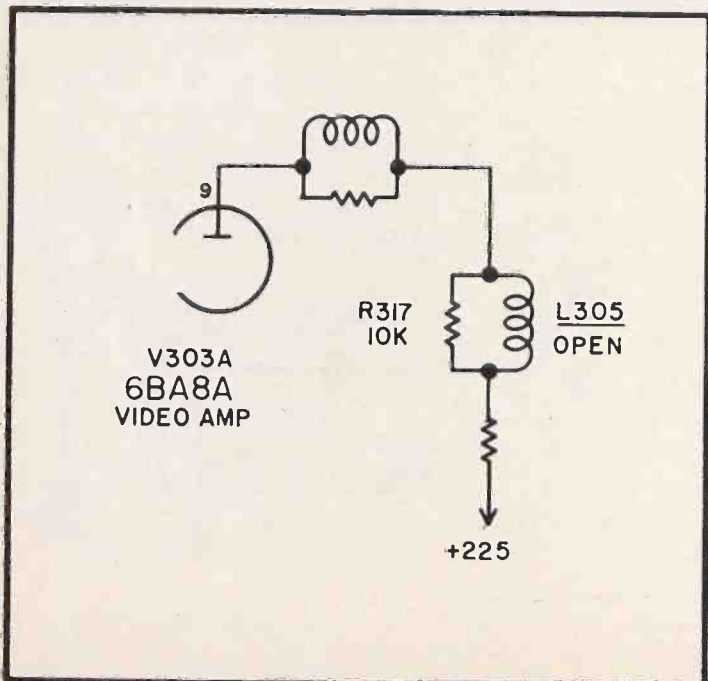What To Do: Remove C501 between ac line and ground. Add C505, .047 1KV, across the line at the terminals of the ac interlock. Insert rf choke L502, part #73B31-1 between one side of the ac line and the junction of resistors R502 and R503.



Mfr: Admiral

Chassis No. 14YP3B

Card No: AD-14YP-6

Section Affected: Pix

Symptoms: Excessive contrast, poor pix detail, (focus good).

Cause: Open L305 causing R317 to act as part of video amp plate load resistance.

What To Do: Repair or replace L305 (L305 is wound on R317).

Mfr: Motorola Chassis No. TS423


Card No: MO-TS423-1

Section Affected: Raster

Symptoms: Excessive brightness. Brightness control inoperative.

Cause: Leaky or shorted C201 in vertical blanking circuit.

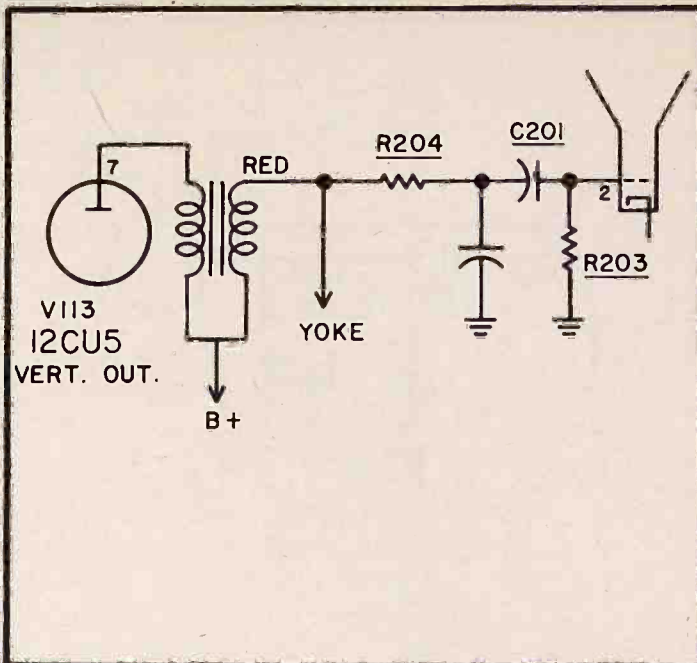What To Do: Replace C201, .01 mfd., check R204, 3.3k and R203, 47K and replace if they have changed value.



Mfr: Motorola Chassis No. TS423


Card No: MO-TS423-2

Section Affected: Sync

Symptoms: No vertical hold.

Cause: Shorted C602.

What To Do: Replace C602, .001 mfd.

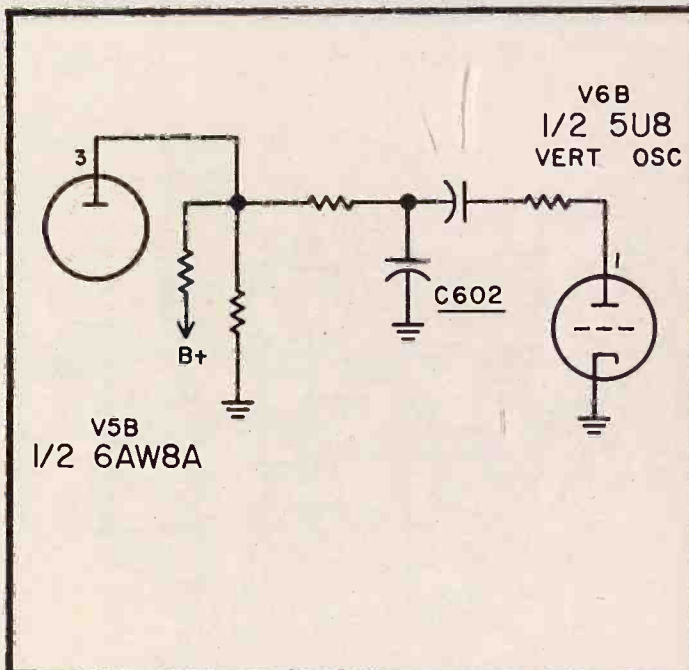

Mfr: Motorola Chassis No. TS423


Card No: MO-TS423-3


Section Affected: Vertical sweep.

Symptoms: Poor vertical linearity. Linearity control at extreme end.

Reason For Change: To center the vertical linearity action.

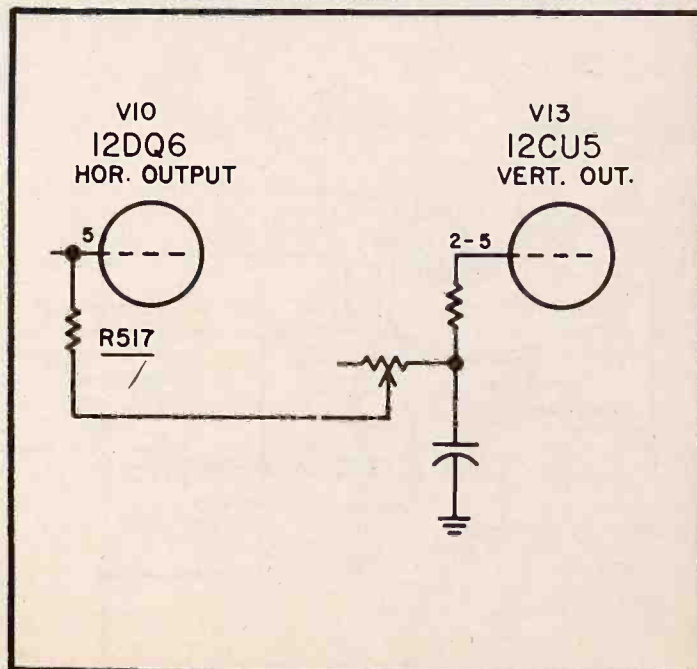What To Do: Change R517 from 1 meg to 470K.



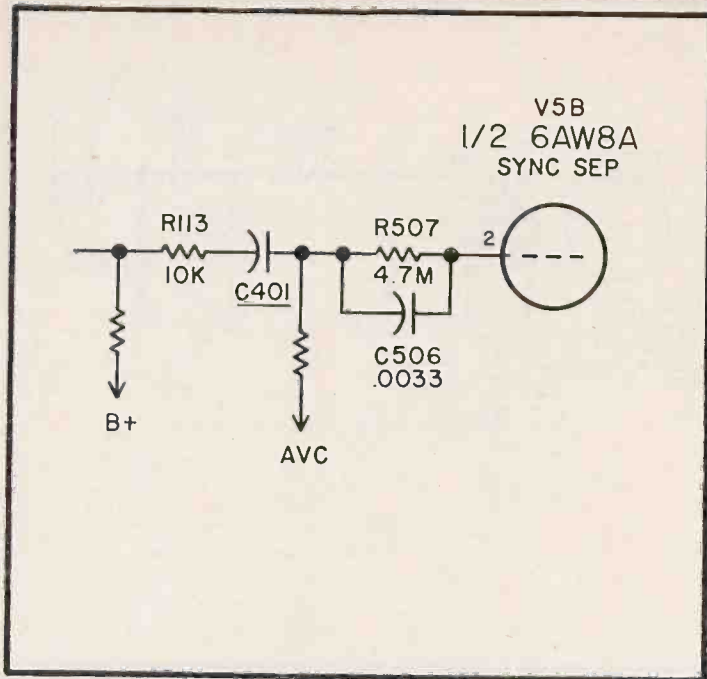

Mfr: Motorola

Chassis No. TS423


Card No: MO-TS423-4

Section Affected: Pix—Sync. Sound

Symptoms: Video overload and sync instability.
Buzz in sound.

Cause: Leaky or shorted C401.

What To Do: Replace C401, .01 mfd.

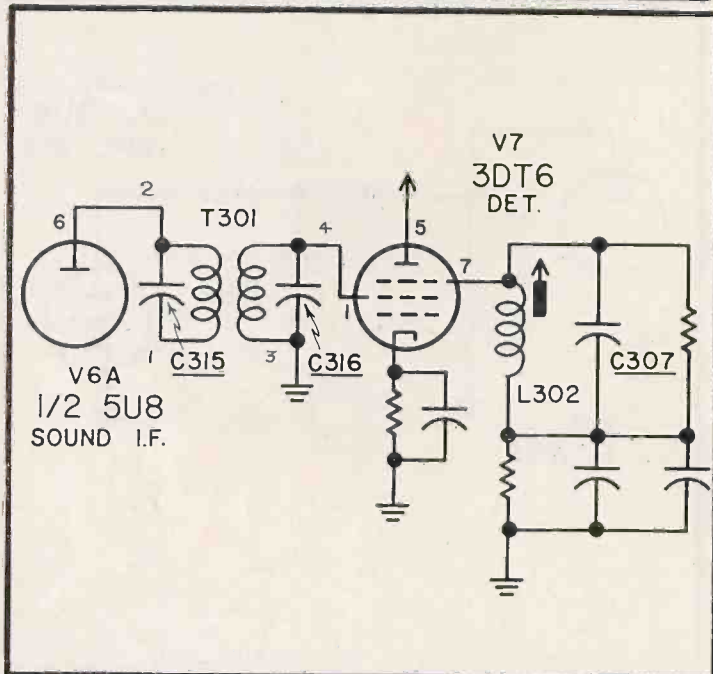

Mfr: Motorola

Chassis No. TS423


Card No: MO-TS423-5

Section Affected: Sound

Symptoms: Drift. Frequent fine tuning necessary.

Reason For Change: To reduce drift in sound detector circuit.

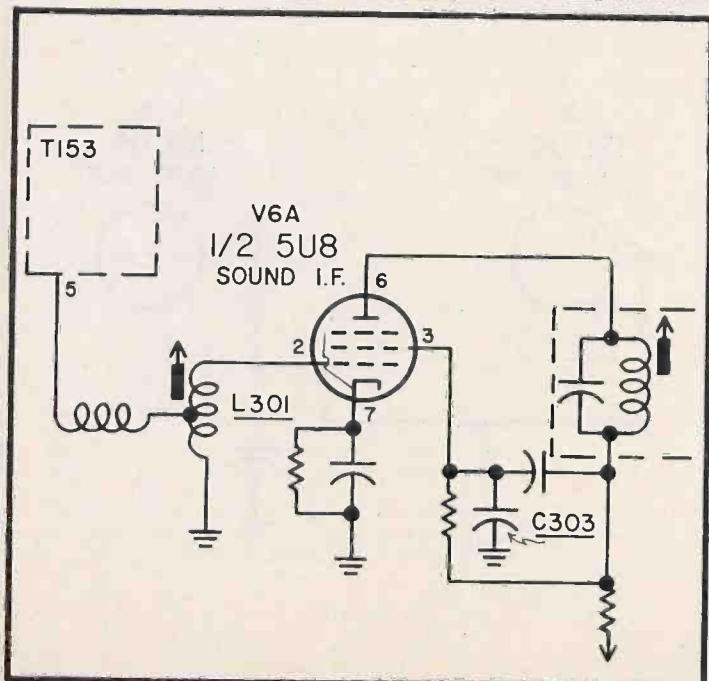What To Do: Change C315 from 4.7 mmf to 5.6 mmf. Replace C307, 18 mmf with Motorola part #21K125707 and C316, 10 mmf, with part #21R121114. These are special condensers chosen for minimum drift.



Mfr: Motorola

Chassis No. TS423

Card No: MO-TS423-6

Section Affected: Sound

Symptoms: Insufficient sound volume.

Reason For Change: To increase sound volume.

What To Do: Increase the value of C303 from .0015 mfd. to .0033 mfd. Replace L301 (sound take-off coil) with Motorola part #24K746552.

Workbench

By Paul Goldberg

Sylvania 1-508-1 Reduced Raster

The receiver was turned on and it was observed that there was insufficient high voltage and width. About one inch was lacking on each side. The vertical sweep moreover, just managed to fill the screen. Reference to the diagram indicated that the 560 volt positive boost voltage was supplied to the vertical oscillator, 6C4, V116, but was not supplied to V20, 12AU7, the horizontal oscillator and discharge tube. The first check was a voltage measurement at the high voltage fuse where the B+ supply voltage was located. The meter measured correctly at about 330 volts positive. This eliminated the low voltage supply as a possible cause of the trouble. The 1B3 high voltage rectifiers V24 and V25 were replaced individually, because if they have a plate to filament leak they could affect the width, boost and high voltage. The damper, 6V3, V23 and the horizontal output tube 6BQ6, V22 were replaced individually, but had no effect.

A scope was set up and a waveform check was made at the grid of the 6BQ6. The waveform checked correctly with the manufacturers service data. Therefore, the horizontal oscillator was supplying the correct drive.

The boost voltage was next measured at the cathode (cap) of the 6V3, damper. Here, instead of measuring the correct 560 volts positive, the measurement was 450 volts positive. This low boost voltage we assumed was the reason for the insufficient vertical sweep and horizontal width. The screen pin #4 of the 6BQ6, was next measured correctly at about 160 volts.

Because there was not the slightest sign of a trapezoidal effect, which would accuse the yoke, I suspected T63, the horizontal output transformer. Before doing anything so rash as replacing it, a voltage leakage check was made of the following condensers in the high voltage section; C2667A, C267B, C264, R270, but all showed no leakage. No check was made of C268 and C269 across the horizontal linearity coil as the horizontal linearity seemed o.k.

It was noticed at this point after glancing at the diagram, that the bleeder resistor, R270, 39K, could most assuredly cause a trouble of this kind.

[Continued on page 28]

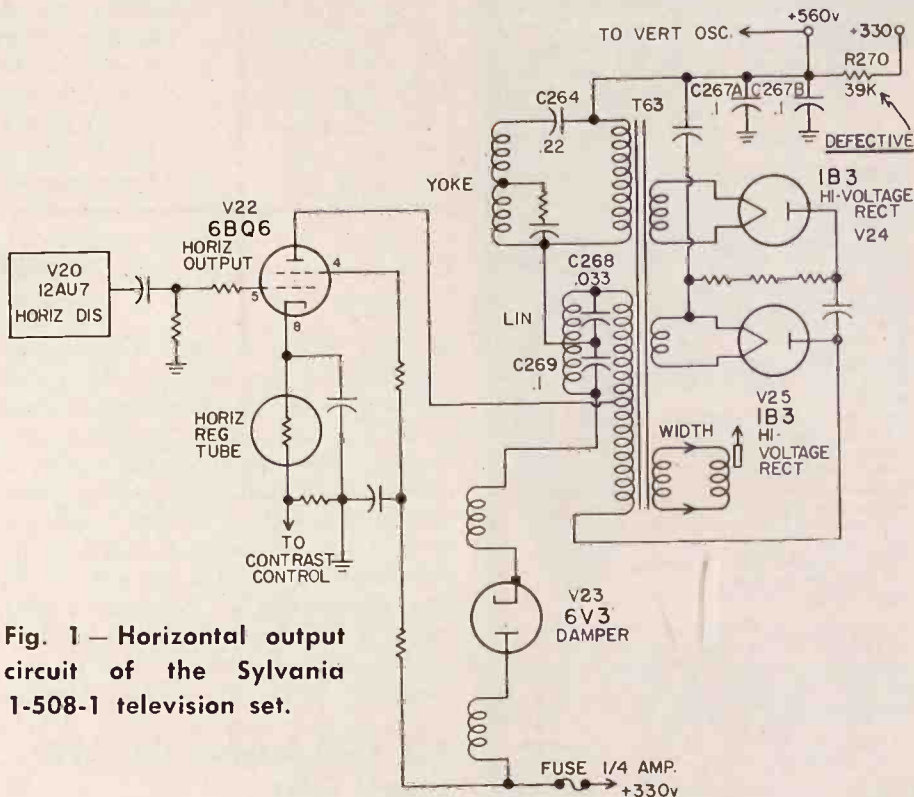


Fig. 1 — Horizontal output circuit of the Sylvania 1-508-1 television set.

THESE
TUBE SALES
CAN BE YOURS!

A self-service tube testing route is a natural for servicemen. It's just like having branches of your shop in drug stores, luncheonettes, super-markets and other retail locations in your area, testing and selling tubes for you 12 hours a day — 7 days a week. Each Century self-service tube tester you place can net up to \$1000 a year . . . and there is no limit to how many you can handle.

Century's low manufacturer-to-you prices enable you to place more units with less investment . . . yet you are assured of the most versatile, accurate and durable testers available. Century backs you up with a proven plan of operation, sales literature, window streamers, etc. Learn how you can make money automatically and keep your income growing, without giving up your present source of revenue. Write today for FREE booklet that tells all about this booming business.

MAIL THIS COUPON TODAY FOR FREE BOOKLET!

CENTURY ELECTRONICS CO., INC.
Dept. 706, 111 Roosevelt Avenue, Mineola, N. Y.

Please send me without obligation, FREE booklet and particulars about setting-up a self-service tube tester route. I understand no salesman will call.

Name

Address

City State

Please print clearly

NEW
IMPROVED
SENCORE
LC3
Leakage Checker

Another Sencore Time-Saver

Check these outstanding New Features

Now — For the first time . . .

Checks 130 different tube types — more than any other "grid circuit" type checker. Includes UHF and latest type tubes.

Checks picture tubes without removing tube from cabinet or chassis.

New Roll Chart prevents obsolescence — just dial the tube type and save time. Chart is easily replaced at no extra cost.

Dynamic Filament checks including heater to cathode leakage & shorts — no need for a second filament tester.

Two spare preheating sockets to cut down testing time.

Capacitor checks simplified.

The LC3 provides all these new improved features in addition to those employed in earlier leakage or "grid circuit" testers. A must for any TV service technician.

SENCORE SERVICE
INSTRUMENTS CORP.
 171 Official Rd. • Addison, Ill.

In stock at your local parts distributor

\$28.95
 DEALER NET
Really Whips Tough Dogs

Cut out this ad now for further information

ask the
"Man-on-the-Roof"
 why he prefers

South River



TWO TO A SET

RATCHET TYPE CHIMNEY MOUNT

Model RT (Galv. Banding)
 Model RT-ST (Stainless Banding)

FASTEST, SIMPLEST, MOST CONVENIENT EVER MANUFACTURED — Mounts in 2 simple steps. Completely factory assembled with no eye-bolts, banding clips, nuts, etc., to handle. Furnished with flat-lay, non-coiling banding, heavy gauge embossed, welded steel construction. Forged, heat treated Alum. ratchets.

WRITE FOR NEW 1958 CATALOG

SOUTH RIVER pioneer & outstanding producer of finest line of antenna mounts
METAL PRODUCTS CO., INC.
 South River, New Jersey

ABSORPTION ANALYZER

[from page 5]

Audio Amplifier

With gated beam type detector circuits check for sound at the gated beam detector tube. Test for increased audio output at the power output stage. With discriminator type detector circuits test for audio at the triode first audio amplifier. Test for increased output at the power output stage. Distortion may be checked at any of the above test points. To check the speaker, test for the presence of an audio in the leads carrying the signal to the speaker voice coil. ■■

WORKBENCH

[from page 27]

Resistor $R270$ was then checked and was found to measure $3K$. What was amazing, was that this resistor didn't show any signs of having been overheated. After replacing $R270$ with a new $39K$, 2 watt, the receiver functioned properly. The boost voltage which was obviously diminished by the defective $R270$ is the plate voltage for the $6BQ6$, horizontal output tube. If it is lowered due to a defect of this kind, it would cause the insufficient width and high voltage.

RCA Color Receiver 21-CD-8725 Loss of Color

It was noted that the picture was seen in black and white on both color and black and white channels. A defect in practically any of the tubes in the color section of this receiver may cause this problem.

Referring to Fig. 2, the first and 2nd bandpass amplifiers, $V701B$ and $V702A$ amplify the chroma. During color reception the burst signal is amplified by $V702B$, and is processed by the phase detector, killer detector and killer stages in such a way that the 2nd bandpass amplifier, $V702A$ is

biased to allow conduction. The color signals therefore can pass through to the circuits which are necessary for color reproduction.

During black and white reception, no burst signal is present, and the stages mentioned above operate in such a way as to drive $V702A$ into cutoff, thus rendering the following color stages inoperative, and producing a black and white picture.

The 3.58 mc oscillator and reactance tube $V707A-B$, feeds an important voltage to the killer detector, and in addition supplies the input for the demodulators. The X and Z demodulators, $V703A-B$ remove the chroma information from the 3.58 mc carrier.

Each one of these tubes was replaced individually, but had no effect. A voltage check was next made at pin 1 of the $6U8A$ color killer tube. The voltage measured about 23 volts negative. This voltage was enough to cut off the 2nd bandpass amplifier, $V702A$. This indicated that the killer tube was conducting. A voltage check was next made at pin 7 of the $6BN8$ killer detector. Here the meter read 8 volts positive. For normal

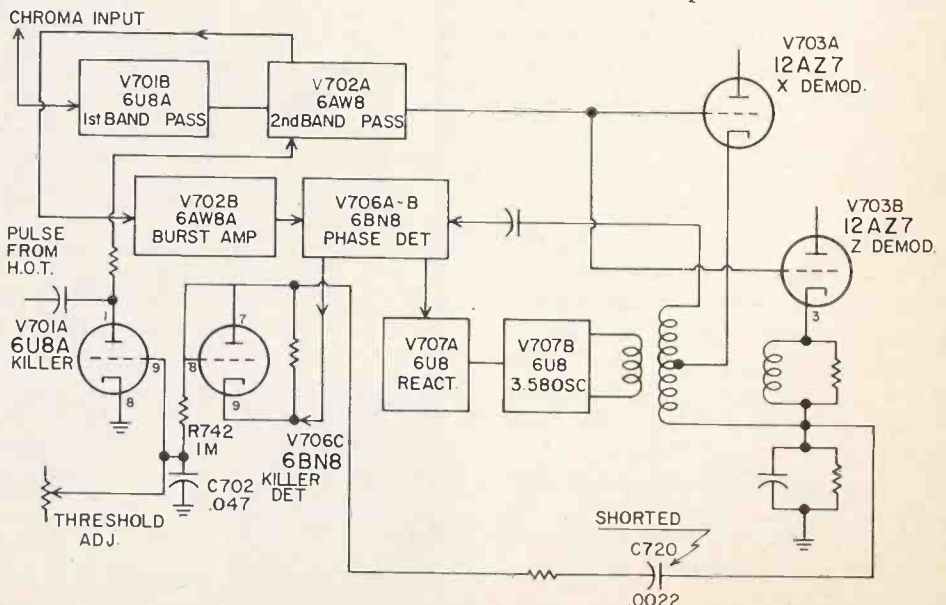


Fig. 2—Diagram of color circuits in the RCA 21CD8725.

TRADE LITERATURE

A new data bulletin, recently published by Sprague Products Company, 71 Marshall St., North Adams, Mass., is entitled "The ABC's of Ceramic Capacitors." Prepared as part of Sprague's continuing educational service program, this bulletin treats in easy-to-understand language all the major ceramic capacitor types—high-k, general application, the three temperature compensating types, multiple, universal, buttonhead, high voltage "doorknob," and printed circuits. The bulletin covers the history of capacitors, the construction of modern capacitors, descriptions of basic terms and many photos, charts and application data.

A new pocket-size folder, "TV Service Safety Hints," just printed by P. R. Mallory & Co. Inc. is designed for use by television service engineers to give customers a better understanding of the job that the service profession is doing. Based on the series of cartoon advertisements which Mallory has been using for several years in TV Guide, this folder tells television set owners "don't do it yourself—call on us!" It dramatizes the dangers and pitfalls of amateur "doctoring" of television ailments, in humorous and informative style.

The folder is an effective and inexpensive promotional piece which the service technician can mail to his customers, leave at neighboring homes after completing a service call, or present when delivering a new set. Space is provided for imprinting of the individual dealer's name. Service dealers and associations can obtain quantities of these folders at \$1.00 per 100 from their nearest Mallory distributor, or by writing to Distributor Division, P. R. Mallory & Co. Inc., Indianapolis 6, Indiana.

The Chicago Standard Transformer Corporation, 3501 West Addison St., Chicago 18, Illinois, has published a handy wall chart, listing Stancor exact replacement flybacks and yokes, by original manufacturers part numbers. The chart, printed on index cardboard, lists each TV set manufacturer alphabetically. All units for

[Continued from page 30]


WORKBENCH

[from page 28]

color operation this voltage should be about 1 volt negative. This was the clue. A voltage from the output circuit of the 3.58 mc oscillator, V707B, is sent back through capacitor C720 to the plate of the killer detector. When the negative burst is fed to the killer detector cathode, and the feedback voltage goes positive at the plate, current flows causing C702 to charge up negatively and cut off the killer tube, V701A. Since the voltage at the plate of the killer detector read 8 volts positive instead of about 1 volt negative, C720 was clipped open and voltage leakage checked. It was found to have a dead short. Capacitor C720 was replaced with a new .0222 mf and the color picture now came in properly. The threshold adjustment was made, and then checked for operation on a color channel. With C270 shorted, the positive 8 volt from the demodulator cathode was now directly fed to the plate of the killer detector through the 1 meg resistor R742 to the grid of the killer tube. The positive 8 volts on the killer caused it to conduct heavily cutting off the 2nd chroma bandpass amplifier, thus killing the color.

GL SLIDE SWITCHES

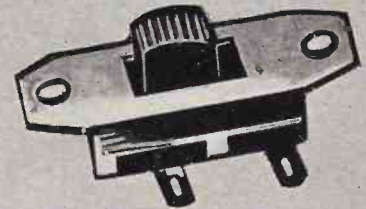A complete line to meet every modern engineering need. You get convenience in low cost switches constructed for long trouble-free service.



Single-Pole, Single-Throw with or without spring returns

Single-Pole, Double-Throw

Printed Wiring Terminal Types

Double-Pole, Double-Throw with or without spring returns

Triple-Pole, Double-Throw

3-Position, 4-Position

Special Purpose Types

FREE Switch Catalog . . . write today

GENERAL CEMENT MFG. CO.

Division of TEXTRON INC.

Western Plant: Los Angeles 18, Calif.

Main Plant: ROCKFORD, ILLINOIS, U.S.A.

VSSS*

*A compilation of specific receiver service repairs, "bugs," chronic troubles, field circuit changes, manufacturers' production revisions, etc. The compilation enables the service technician to pinpoint what is wrong with any given TV set and to correct the fault in the shortest possible time.

Video Speed Service Systems is guaranteed to simplify servicing all TV sets. Contains over 600 service items representing over 2500 of the most serviced TV models now in use. Over 25 different manufacturers' lines are covered.

—CUT OUT AND MAIL—

COWAN PUBLISHING CORP., 300 WEST 43rd STREET, NEW YORK 36, N. Y.

Please send me postpaid Video Speed Servicing Systems

Vol. 1 in Hard Cover Ring-Binder Edition for \$4.95

Vol. 2 in Paper Bound Edition for \$2.95

My Check for \$..... is enclosed.

New York City residents add 3% sales tax

Name.....

Address.....

City..... Zone..... State.....

oped leakage, placing a positive voltage on the picture tube grid. If you remove condenser C115 from the circuit the brightness control will probably function normally but retrace lines will be evident.

The following letter is another example of the type of problem that can result from a failure in the vertical retrace circuitry.

Dear Sir:

I have a receiver in which I haven't been able to obtain a raster or picture even though there is sufficient high voltage, I believe. I don't have a high voltage meter so that I can't be certain on this point but I can draw a high voltage arc that appears about normal. I have changed and checked those components I suspected might be the cause of the trouble. I have even replaced the picture tube thinking the electron gun was defective but the tube was good as I found out by using it with another TV receiver. The voltages are normal at either side of the brightness control and at the variable arm.

The receiver is the Motorola TS-533 chassis.

H. T.
Boston, Mass.

The above problem is probably another condition where a component in the vertical retrace circuitry failed and caused an opposite condition to the case previously given. An interesting point about these two cases is that it

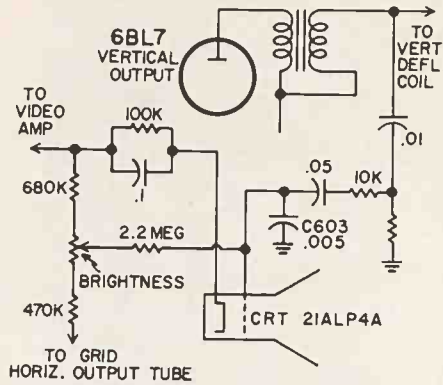


Fig. 5—Retrace blanking with a positive control grid voltage.

was a condenser that failed in both instances. Here, condenser C603 (Fig. 5) has undoubtedly shorted bringing the grid down to ground potential. The positive voltage applied to the grid cancelled some of the positive voltage applied to the cathode. When C603 shorts it causes the picture tube to be biased beyond cutoff so that it would not be possible to obtain a raster or picture. ■■

Advertiser's Index


Belden Mfg. Co.	Cover 3
Century Electronics Co., Inc.	27
Cornell-Dubilier Elec. Corp.	3
General Cement Mfg. Co.	29
Heath Company	2
RCA Electron Tube Division	Cover 4
Raytheon Mfg. Co.	Cover 2
Service Instruments Co.	28
South River Metal Prods. Co.	28
Sprague Electric Co.	1
Tung-Sol Electric, Inc.	6, 7
United Catalog Pub.	8
Vis-U-All Prods. Co.	32

Shop Hints and Short Cuts

We would welcome hints and short cuts from our readers. ES will pay \$5 for each hint used. Sorry, but we cannot be responsible for unaccepted material. In case of duplication, first received will be accepted.

When the ejector spring in the spindle post snaps, a piece of rubber band stuffed in the opening of the spindle (as shown above) will serve as well. We have done it many times and never had a call back.

R. M.
Fairlawn, N.J.

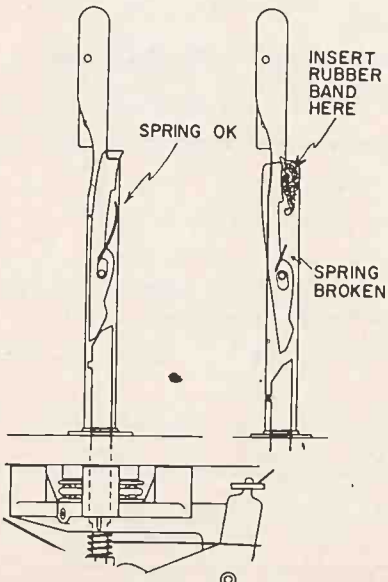

A few transistor portables which we've had in the shop squealed and motorboated quite badly. Immediately the filter and decoupling capacitors were suspected, but they all proved to be OK. The trouble was finally traced to dirty battery contacts. We cleaned them and applied a very thin coat of solder and the sets played like new again. (Be careful not to apply too much heat otherwise the temper will be taken out of the contacts.) Many manufacturers are now cad plating the battery contacts so as to avoid this difficulty.

R. G.
Houston, Texas

FREE Information About This

BUSINESS OPPORTUNITY



key to car radio service market

How many car radios have you serviced lately? Most service operators are missing this tremendous market because they have no regular contact with car owners!

This VIS-U-ALL Auto-Radio Service Merchandiser literally moves your shop into the gas stations and garages where car owners must go. It multiplies your sales of parts—booms your repair volume, too. And without increasing your overhead!

Let us tell you how easy it is to increase your net profit by \$50 a week. See distributor or write us.

VIS-U-ALL products company
305 Fuller N.E., Grand Rapids 3, Mich.



If it's worth Engineers' time . . .



. . . It's worth Engineered Cable




Belden

**INTERCOMMUNICATING
AND
SOUND SYSTEM CABLES**

Indoor-outdoor, phones
or speakers—there is a
Belden engineered cable
to meet your needs for
a permanent, trouble-
free installation.

"Items from the
Complete Belden Line"

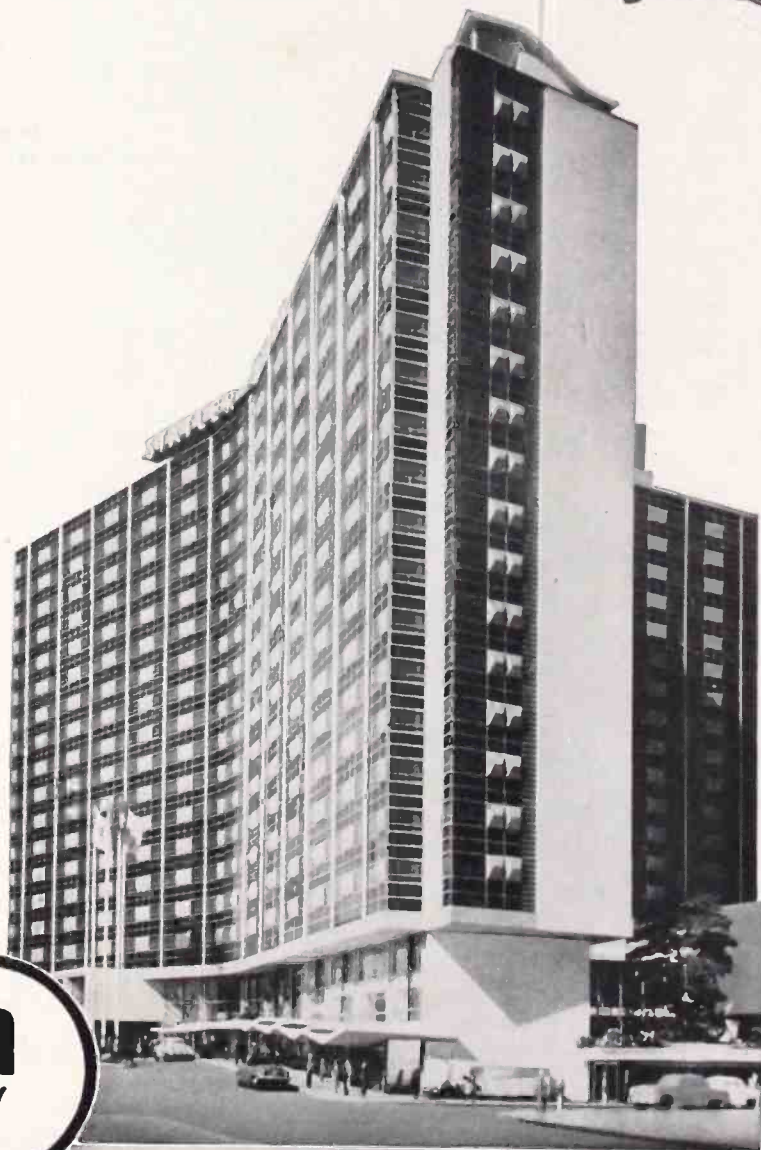*Intercommunications systems in
the Statler Hilton in Dallas,
and other leading hotels
with intercommunications
systems, are wired by Belden.*



Belden

**WIREFORMER FOR INDUSTRY
SINCE 1902
CHICAGO**

10-8

Magnet Wire • Lead and Fixture Wire • Power Supply Cords, Cord Sets and Portable Cord • Aircraft Wires
Welding Cable • Electrical Household Cords • Electronic Wires • Automotive Wire and Cable



FREE!

RCA MAGNETIC TOOL/RAK

REPLACE WITH  Silverama PICTURE TUBES


with each purchase of an RCA Silverama Picture Tube

The new RCA Magnetic TOOL/RAK is a workbench "must" for every TV Service Technician. Smartly designed in appearance and functionally sound in use...this magnetic "grip" TOOL/RAK facilitates easy, orderly placement of your tools when they are not in use. Just place tools on the RCA Magnetic TOOL/RAK—they stay put! Installed close at hand, the TOOL/RAK saves valuable time and eliminates fussing and fumbling for misplaced tools on crowded workbenches.

Now, for a limited time only, you can obtain one RCA TOOL/RAK FREE, with each and every RCA Silverama Picture Tube you purchase from your Authorized RCA Tube Distributor.

Get your TOOL/RAKS while they last—place your order today!

DOZENS OF PRACTICAL USES!

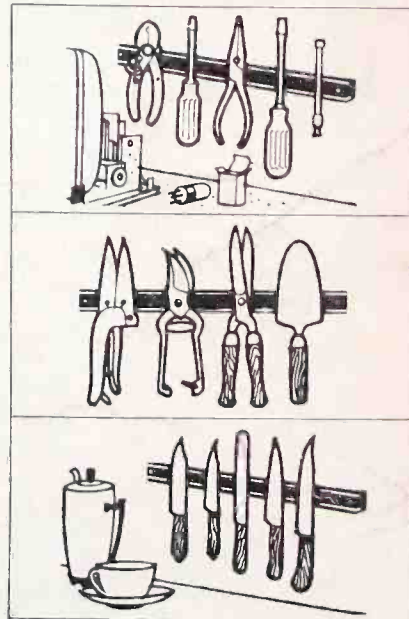

RADIO CORPORATION OF AMERICA
Electron Tube Division

Harrison, N. J.