

OCTOBER, 1954

# Radio-Television SERVICE DEALER

TV - AM - FM - SOUND

Includes

3

Sections

1. VIDEO SPEED SERVICING SYSTEMS
2. TV FIELD SERVICE DATA SHEETS
3. COMPLETE TV SERVICE INFORMATION SHEETS



**The Professional Radio-TVman's Magazine**  
Reaching Every Radio TV Service Firm Owner in the U.S.A.





**Snyder**  
PHILADELPHIA

**Long  
Ranger**  
WITH  
**RadarFlector**

**\$39<sup>75</sup>**  
LIST  
MODEL  
AX-674

ABOLISHES REAR PICKUP • INTER-CHANNEL INTERFERENCE

**VHF EXTRA HIGH GAIN**

VHF/UHF COMBINATION CONICAL-YAGI

**TV ANTENNA**

**SNYDER**

SNYDER MFG. CO., PHILADELPHIA 40, U.S.A. • BELLEVUE TUBE MILL,  
INC., PHILADELPHIA • SNYDER ANTENN-GINEERS LTD., TORONTO 14,  
CANADA • WORLD EXPORT: ROBURN AGENCIES, INC., N. Y.



# Every Service Firm Owner in the U.S.A. Receives SERVICE DEALER Monthly DISTRIBUTION THIS ISSUE OVER 65,000

COWAN PUBLISHING CORP., 67 West 44th Street, New York 36, N. Y.

VOL. 15, NO. 10

OCTOBER, 1954

## EDITORIAL STAFF

*Publisher*

**SANFORD R. COWAN**

*Editor*

**SAMUEL L. MARSHALL**

*Editorial Production*

**ROBERT CAMPBELL**

*Contributing Editors*

**LEONARD LIEBERMAN**

**ROBERT T. DARGAN**

**PAUL GOLDBERG**

**MARVIN KLEIN**

**SAN D'ARCY**

## BUSINESS STAFF

*Advertising Director*

**SANFORD L. CAHN**

*Advertising Manager*

**HARRY W. REIZES**

*Advertising Sales*

**LAWRENCE STEINER**

*Production Manager*

**DAVID SALTMAN**

*Circulation Manager*

**HAROLD WEISNER**

*Ass't Circ. Mgr.*

**C. J. BINDERMAN**

## BRANCH OFFICES

**LOS ANGELES**

**TED E. SCHELL**

2700 West Third Street

Dunkirk 2-4889

**CLEVELAND**

**RICHARD E. CLEARY**

Commercial Bank Bldg.

Berea, Ohio

BE:ea 4-7719

## FEATURE ARTICLES

- Servicing Vertical Instability, by Steve Travis** ..... 10  
The technique of pinpointing causes of vertical instability that originate in pre-oscillator stages.
- Block Diagram Analysis of Color Transmission and Reception, Part 2, by Bob Dargan and Sam Marshall** ..... 14  
Comprehensive mathematical analysis of the composition and formation of luminance and color-difference signals, simplified by block diagrams.
- Community Antenna System, by Edward M. Noll** ..... 22  
The development of an efficient community service by wise investors and a skilled engineering staff.
- Key Test Points, by Steve Travis** ..... 28  
Systematized troubleshooting of TV deflection, vertical and horizontal oscillator systems.
- RC Circuits, Part 5, by Cyrus Glickstein** ..... 30  
Functional characteristics of Complex RC circuits with series-parallel elements, and their application to TV sync circuits.
- Sync Amplifier Problems, by Paul Goldberg (A Workbench Feature)** 34  
The use of an oscilloscope in conjunction with manufacturer's service data in correcting three sync amplifier problems.
- TV Service Information Sheets** ..... 65-72  
Complete data on CBS-Columbia Models 17M06, 22C06, 22C38, Chassis 750-3, 751-3.

## CIRCUIT AND SERVICE FORUM

- Answer Man**
- CBS-Columbia Ch. 750-3—Height Shrinks ..... 27
- Increasing Scope Gain ..... 52
- The Workbench—Sync Amplifier Problems**
- RCA KCS82—Horizontal Pull ..... 34
- Emerson Chassis 120162A—Horizontal Pull and Vertical Roll ..... 34
- Motorola TS114—Intermittent Horizontal Pulling and Vertical Jitter ..... 35
- Rider TV Field Manual Service Data Sheets**
- Firestone Models 13-G-128, -129, -130, etc., Codes 334-3-MS39A, 334-3-MS39B 37
- Pacific Mercury Ch. 200-1, 2, 3, 4, etc. .... 39
- Western Auto Model 2D-1315A, 2D1325A, etc., Ch. 21T1A, 17T1B, 21T2A .... 41
- Video Speed Servicing Systems**
- Philco Chassis R181, D181 ..... 43
- Zenith Chassis 21L21 ..... 45
- DuMont Chassis RA306/307 ..... 47

## DEPARTMENTS


- |                               |           |                                |           |
|-------------------------------|-----------|--------------------------------|-----------|
| <b>Editorial</b> .....        | <b>5</b>  | <b>New Products</b> .....      | <b>50</b> |
| <b>Association News</b> ..... | <b>18</b> | <b>Trade Flashes</b> .....     | <b>54</b> |
| <b>Answer Man</b> .....       | <b>27</b> | <b>Trade Literature</b> .....  | <b>58</b> |
| <b>Workbench</b> .....        | <b>34</b> | <b>Advertising Index</b> ..... | <b>64</b> |

RADIO-TELEVISION SERVICE DEALER is published monthly by Cowan Pub. Corp., 67 West 44th St., New York 36, N. Y. Subscription price: \$1 for 2 years in the United States, & U.S. Poss. Elsewhere \$1 per year additional. Single Copies 25c. Reentered as second class matter Sept. 25, 1950 at the Post Office at New York, N. Y. under the Act of Mar. 3, 1879. Copyright 1954, Cowan Publishing Corp.

POSTMASTER: SEND FORM 3579 TO RADIO-TELEVISION SERVICE DEALER, 67 WEST 44TH ST., NEW YORK 36, N. Y.



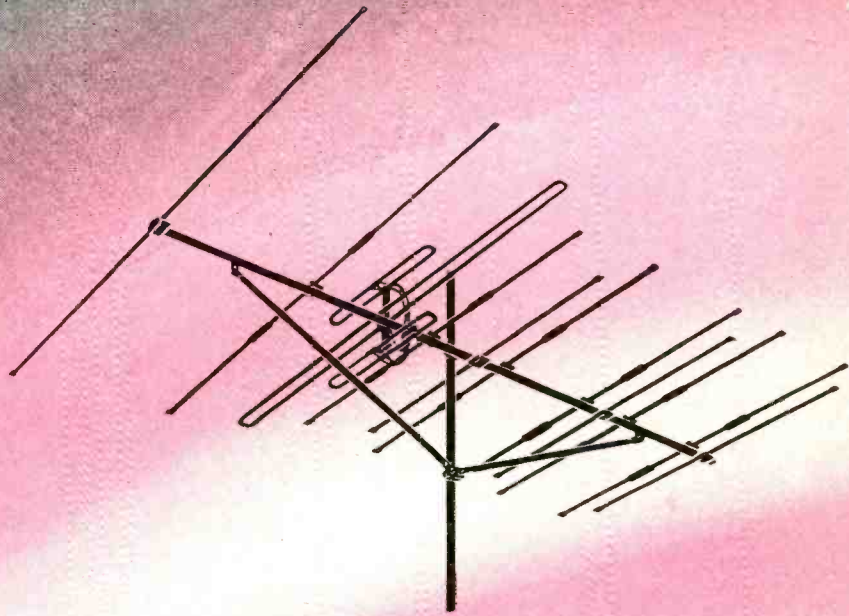*This*  
*is*  
**CHANNEL  
MASTER'S**  
*greatest*  
*antenna*  
*discovery!*




the  
**RAINBOW\***

**the most important antenna  
development since the  
introduction of the basic Yagi!**

**The World's First  
Triple-Powered Yagi...**

**Brilliant all-channel  
VHF performance —  
and really ready for **COLOR!****

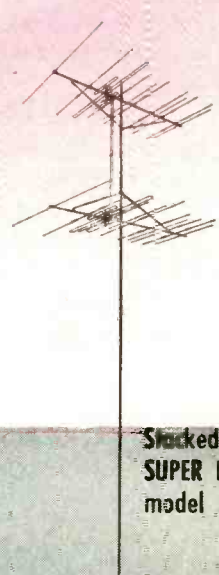- No other antenna provides such outstanding long distance reception in black and white.
- No other antenna is so well prepared to meet the exacting requirements of color television: Uniform high gain, flat frequency response, extremely narrow polar patterns, highest front-to-back ratios.



**Stacked  
SUPER RAINBOW  
model no. 331-2**

**Single bay  
SUPER RAINBOW  
model no. 331**

\*Pat Pending




# these 3 basic engineering advances

make the RAINBOW the most powerful all-channel VHF antenna science has yet produced.

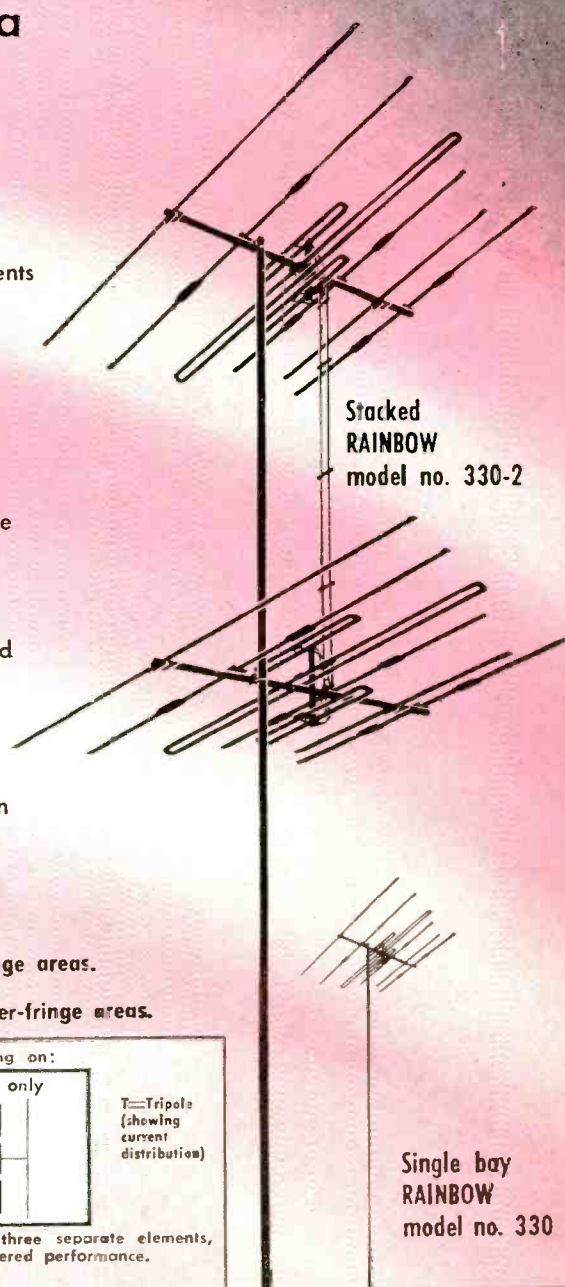- 1. New spacing formula:** Channel Master research has now established new, more efficient relationships between the Yagi's parasitic elements (directors and reflectors) — far greater efficiency than a screen. The radical new spacing arrangement between these elements has, for the first time, extended the full efficiency and high gain of the basic narrow band Yagi over the full width of an entire VHF band.
- 2. New "triple power" High Band directors and reflector:** Three-segment directors and reflectors, with each segment insulated from its adjacent segment, provide the combined power of three High Band Yagis, operating side by side, in perfect phase. This is the first time an entire antenna has been made to operate on the same high gain principle as the fabulous Tri-Pole.
- 3. New "intermix" design:** Combines — into one single antenna — two separate, independent sets of directors and reflectors, one for High Band, one for Low Band. Each parasitic system operates only on its own band. No compromise design. No interaction. No signal loss.

**PLUS** Channel Master's original, super-gain TRI-POLE . . . the unique triple-powered dipole that made the Champion the most wanted antenna in America.



Stacked RAINBOW model no. 330-2

Single bay RAINBOW model no. 330

## 2 great models available:

**RAINBOW, Model No. 330** — for secondary and near-fringe areas.

**SUPER RAINBOW, Model No. 331** — for fringe and super-fringe areas.

Full band width — highest gain — of any all-channel antenna.

Diagram illustrates independent operation of the RAINBOW's High Band and Low Band parasitic elements. Note unique new spacing arrangement between elements.

Heavier lines indicate elements operating on:

Low Band only

High Band only

Legend: Tripole (showing current distribution)

Note that each High Band element is actually three separate elements, each insulated from the others, for triple-powered performance.

## Here's how the RAINBOW out-performs the famous Champion.

|                            |                       | CHANNEL | 2       | 3       | 4       | 5       | 6       | 7     | 8     | 9       | 10      | 11      | 12      | 13 |
|----------------------------|-----------------------|---------|---------|---------|---------|---------|---------|-------|-------|---------|---------|---------|---------|----|
| Gain Over 1-Bay Champion   | 1 Bay RAINBOW         | 0 DB    | 0 DB    | 0 DB    | +2 DB   | +3 DB   | +2.5 DB | +1 DB | +5 DB | +5 DB   | +1.5 DB | +2.5 DB |         |    |
|                            | 1-Bay SUPER RAINBOW   | +1 DB   | +1 DB   | -1.5 DB | +2.5 DB | -3.5 DB | +3.5 DB | +2 DB | +2 DB | +1.5 DB | +2 DB   | +3.5 DB | +4.5 DB |    |
| Gain Over Stacked Champion | Stacked RAINBOW       | +1.5 DB | +2 DB   | +1.5 DB | +1.5 DB | +2 DB   | +5 DB   | +5 DB | +0 DB | +0 DB   | +0 DB   | +1 DB   | +1.5 DB |    |
|                            | Stacked SUPER RAINBOW | +2 DB   | +2.5 DB | -3 DB   | +3 DB   | +4 DB   | +5 DB   | +5 DB | +1 DB | +2 DB   | +2 DB   | +2.5 DB | +3.5 DB |    |



Seen in October



**CHANNEL MASTER CORP.**  
ELLENVILLE, N. Y.



THE WORLD'S LARGEST MANUFACTURER OF TV ANTENNAS

Write for complete technical literature



# MERIT

HVO-23

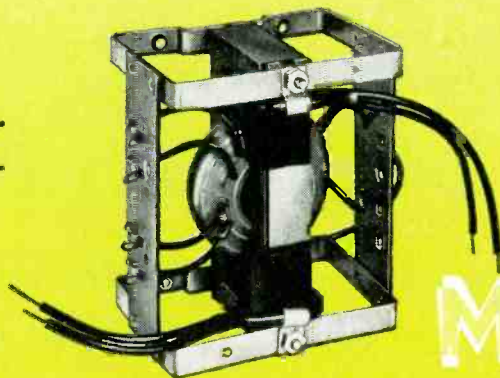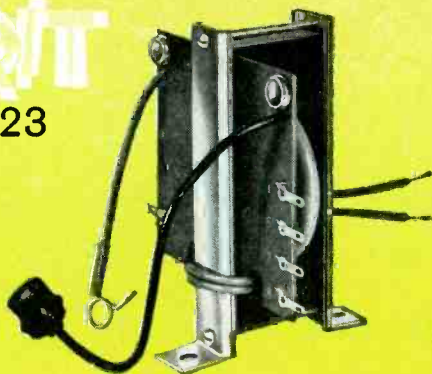


# MERIT

HVO-16

Burton Browne Advertising

# MERIT

HVO-13

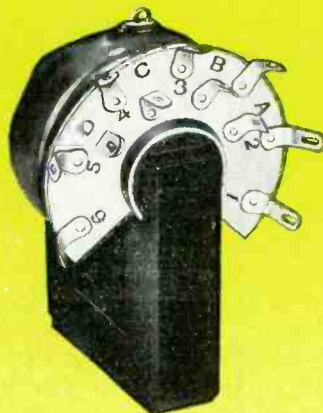

**MERIT**—the only transformer line designed exclusively for service—  
will be on the spot with exact replacements for color television.

Since 1947 Merit has made available to you a complete line of replacement transformers including such exact replacement requirements as Merit Model HVO-13 for Sylvania, Model HVO-16 for Philco and Model HVO-23 for Admiral.

Merit's three plants are geared to supply your replacement transformer needs when you need them wherever you are.

*Ask your jobber, or write for, your copy of Merit 1955 Replacement Guide #407 listing up-to-date replacement components for all models and chassis of TV receivers.*

## WATCH

# MERIT

## FOR EXACT REPLACEMENT IN COLOR TV

AS IT HAS BEEN IN BLACK & WHITE TV SINCE 1947

MERIT COIL & TRANSFORMER CORP.

4427 N. Clark Street, Chicago 40, Illinois





# EDITORIAL...

by S. R. COWAN  
PUBLISHER

## A Publisher Hurts Servicemen

In yesteryear it was common practice and considered good business for competing publications, particularly newspapers, to blast away at one another at the slightest excuse. Of late this practice has not been indulged in because modern publishers are supposed to be more polite than their forebears. Well—because we are both old fashioned and because we have the interests and welfare of the radio-TV servicing profession at heart, we now find it necessary to blast away, with all the power we command, at a contemporary publishing firm whom we sincerely believe is doing professional radio-TV servicemen a rank inexcusable injustice. We refer to Ziff-Davis Pub. Co. (who for years has published "*Radio News*"—which is supposed to be published for the benefit of radio-TV servicemen). Ziff-Davis has just launched another monthly magazine titled "*Popular Electronics*." Both "*Popular Electronics*" and "*Radio News*" have the same Editor, a fine fellow personally, by name of Oliver (Ollie) Read.

Scanning "*Popular Electronics*" first issue we find in it articles titled: "How To Test and Replace Radio & Television Controls"—"How To Align Receivers"—"How To Fix Home Radios"—"Adjusting Your TV Height Control"—and others of passing interest.

As "*Popular Electronics*" like "*Radio News*" is sold on newsstands, copies can get into the hands of laymen, set owners and others besides professional servicemen. These laymen, then, are being advised and told how to do their own radio-TV repair jobs—jobs that, under normal circumstances, without "*Popular Electronics*" interference, might be relegated to professional servicemen.

Isn't this a ludicrous and intolerable situation? Here we find that a magazine publisher who *claims* to be the serviceman's friend is actually taking jobs away from those servicemen, worsening their already too-competitive position. Ziff-Davis, in this age of free and unrestricted enterprise, has, by launching "*Popular Electronics*" with its "service-your-own-set" type of articles, bitten the hands that feed them. The companion magazine "*Radio News*" with the same Editor as "*Popular Electronics*" will probably find itself loved much less henceforth by professional servicemen who naturally do not want their income or profession undermined.

## Our Prediction Is Upheld

Just five years ago RCA introduced the first 45 rpm record. We then predicted that "45's" along with 33 1/3 rpm recordings, would revitalize the phonograph business and eventually force 78 rpm records into obsolescence. That prediction is being borne out. In 1949 record industry sales totalled 160 million dollars. This year the total may exceed 225 million. And this despite the tremendous impact and competition of TV, which was in its infancy in 1949. Think of it! In the past five years 200 million "45" records and 13 million "45" turntables have been sold. Think of all the needles and cartridges that can be sold in the years ahead!

Mr. Frank Folsom, President of RCA, is now of the opinion that in another five years the "45" will account for more than 75% of the total record volume. We don't care about that—but we do hope that with each coming year more and more electronically actuated phonograph record players will be sold and used. They can be and are a wonderful influence upon the nation's adolescents who in time may be taught to appreciate good music and truer fidelity of phono reproduction.

In this connection may we voice our objection to the rampant and frequently misused term "High Fidelity." When the writer founded and became the first publisher of the magazine "Audio Engineering" in 1944 it was his thought, and that of his associates, that the term "High Fidelity" meant truly faithful wide frequency-range reproduction of the better class music or artistic rendition. Today some manufacturers put one or two tiny speakers, each having a 300 to 3000 cps range, into an oblong cabinet and call that sort of garbage "Hi-Fi." Something in the way of standards is needed to differentiate between genuine and quasi High Fidelity. Possibly the Audio Engineering Society and the Institute of Radio Engineers could get together on a standards project of that kind.

Being close to the matter, we realize that for various reasons, some valid, others selfish, many manufacturers would not wish to have such "standards" established. This group might stymie any action that IRE or AES might undertake. At least, an attempt to define High Fidelity minimums should be made, otherwise many avoidable misunderstandings between the public and the sellers of audio reproducers are bound to arise.



ACHIEVEMENT OF A

# Quarter Century

For those who pursue the ultimate—the rediscovery of perspective in music...

## Imperial

**PR-100**




The stimulation and pleasure gained by listening to a live performance is the result of much more than frequency range considerations.

Here is a revolution—the use of true proportions of sound in authentic reproduction including smooth coverage of the complete useful frequency range and thus recreating the fine performance with the greatest possible degree of accuracy.

Voices come to life and there's a new almost geometrical separation of instruments. A three-way system with 1-f unit loaded by a new-design reactance-annuling trilateral-mouth horn for bass; selected compression-driver horn-loaded mid channel with intrarange equalizer for a final touch to precise balance and coloration elimination; and superlatively smooth, space-blended supertweeter top. Each instrument is individually serial numbered and accompanied with a signed certificate certifying that the reproducer fully meets the exacting performance standards set for it. (Components and performance are the same as for RS-100 Laboratory Reference Standard Reproducer.)
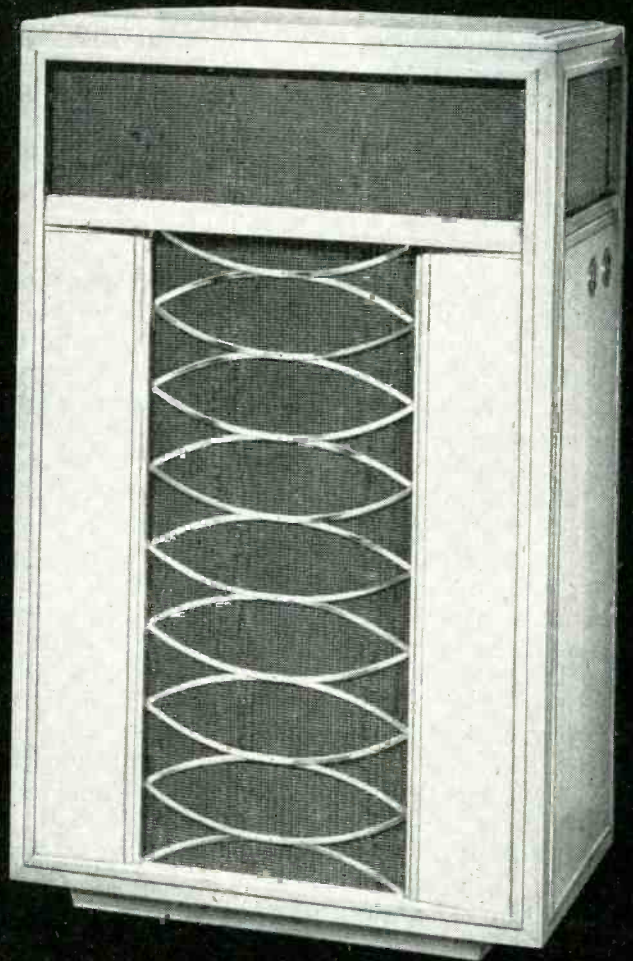
### PR-100 "IMPERIAL" REPRODUCER

ST-919. Selected Mahogany. Net Price ..... \$525.00  
ST-918. Satin Korina. Net Price ..... 535.00



## LABORATORY STANDARD

**RS-100**




Built for research comparison

The Imperial was designed by the Jensen engineering staff for their own use as a reference standard of the highest quality of high-fidelity reproduction. In this original laboratory version the RS-100 Laboratory Reference Standard Reproducer is a new and important tool for sound, recording and broadcast engineers, workers in psychoacoustics and music critics who require an unusually high quality of reproduction. Some music lovers and audiophiles will undoubtedly want to own an RS-100. Cabinet is plywood attractively two-toned in blue gray.

### RS-100 LABORATORY REFERENCE STANDARD REPRODUCER

ST-920. Net Price ..... \$468.00

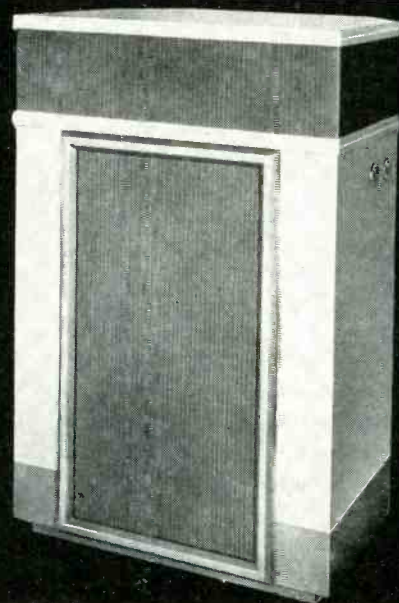

Burton Browne Advertising

Jensen—world's quality standard for more than a quarter century.

# Jensen

MANUFACTURING COMPANY

Division of the Muter Co.  
6601 S. Laramie, Chicago 38, Illinois





# A NEW CONCEPT IN ROTATOR ENGINEERING!

Built-In Thrust Bearing—3200:1 Reduction Gear Train—Dynamic Braking!




## ROTO KING

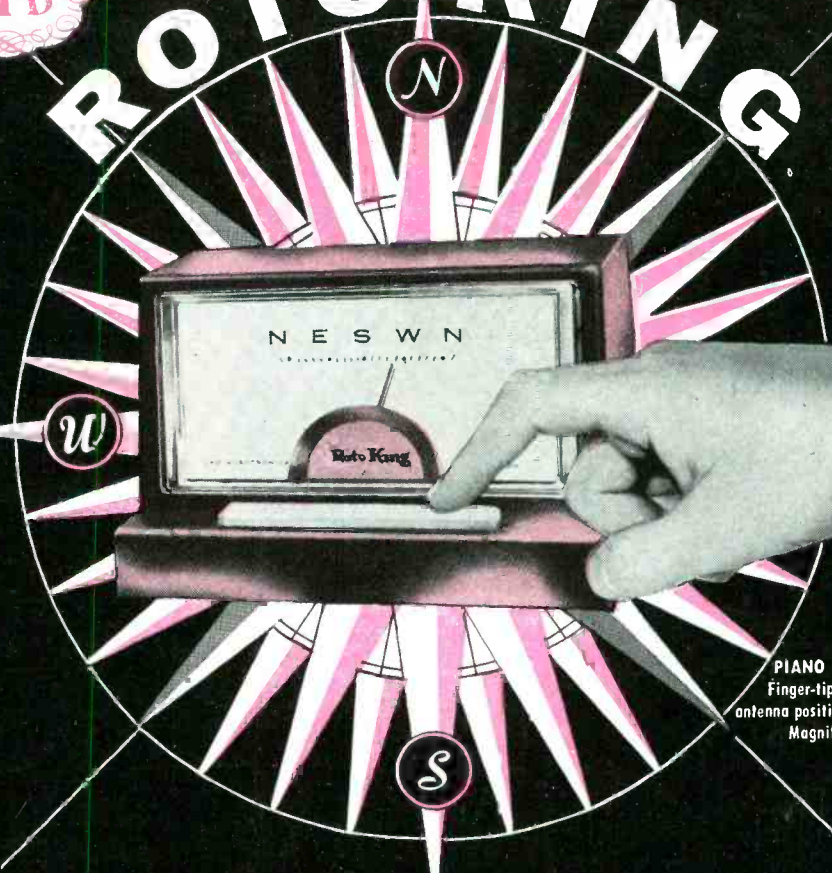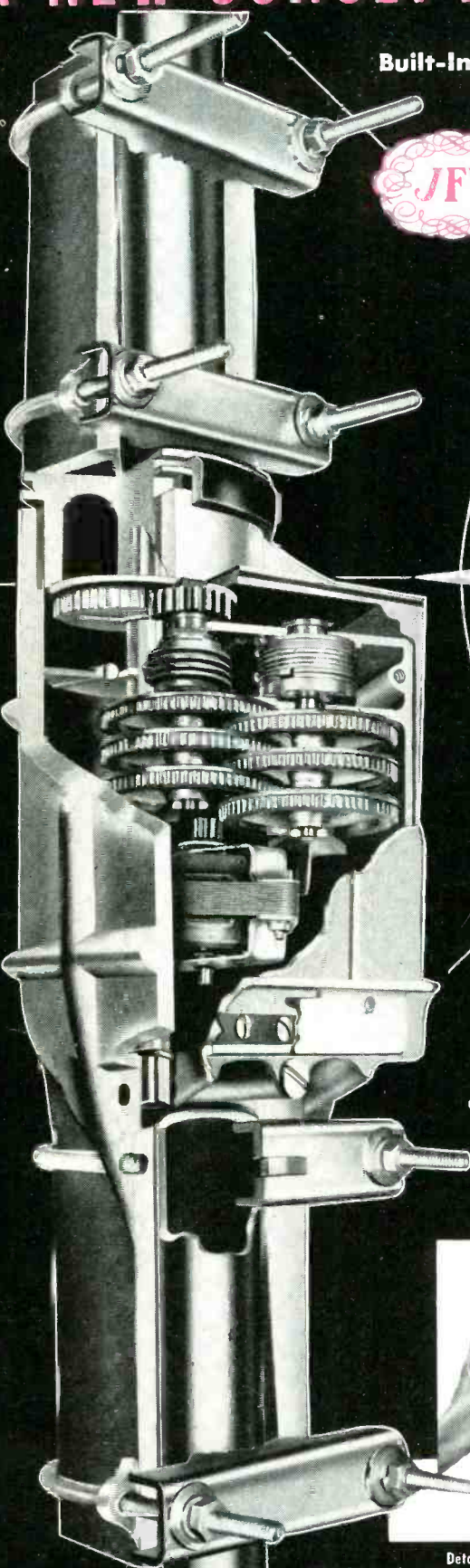

**PIANO KEYBOARD TUNING!**  
Finger-tip control tuning. Precise antenna position indicated at all times. Magnificently styled console is a joy to behold.

Especially designed for fidelity reception of sharply directional color transmission. The JFD Roto King is the first ever engineered to overcome shortcomings of conventional rotator design which seriously affect the accuracy of antenna position and indication: ambiguity (error) and voltage fluctuation. The result is stop-watch tuning of antenna for fidelity reception of critically directional VHF, UHF and color signals especially.

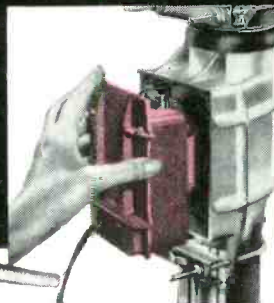


**CARTRIDGE SERVICING!**

Detachable power drive unit can be removed in seconds. No laborious dismantling of antenna.



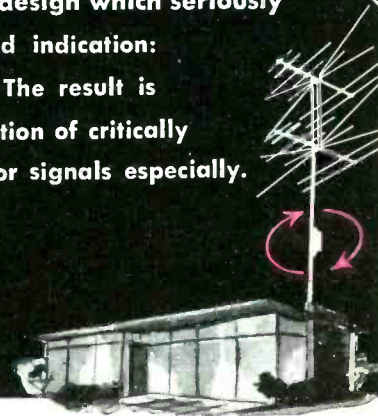**STOP WATCH TUNING ACCURACY!**

Ultra-sensitive control system accurate within 1/2 degree of desired position. Instant stop. No ambiguity. No drift or error.



**390 DEGREE ROTATION IN EITHER DIRECTION**

Complete 390 degree revolution permits station selection beyond end of normal 360 degree traverse.

Copyright 1954 by JFD Mfg. Co., Inc.




**JFD MANUFACTURING CO., INC., BROOKLYN 4, NEW YORK**

LOOK TO JFD FOR ENGINEERING LEADERSHIP  
Export Division: 15 Moore St., N.Y.C.  
WRITE FOR FORM NO. 288

**Model RT100-M Mahogany \$44.95 List**  
**Model RT100-IV Ivory 44.95 List**



# ANOTHER RAYTHEON FIRST!

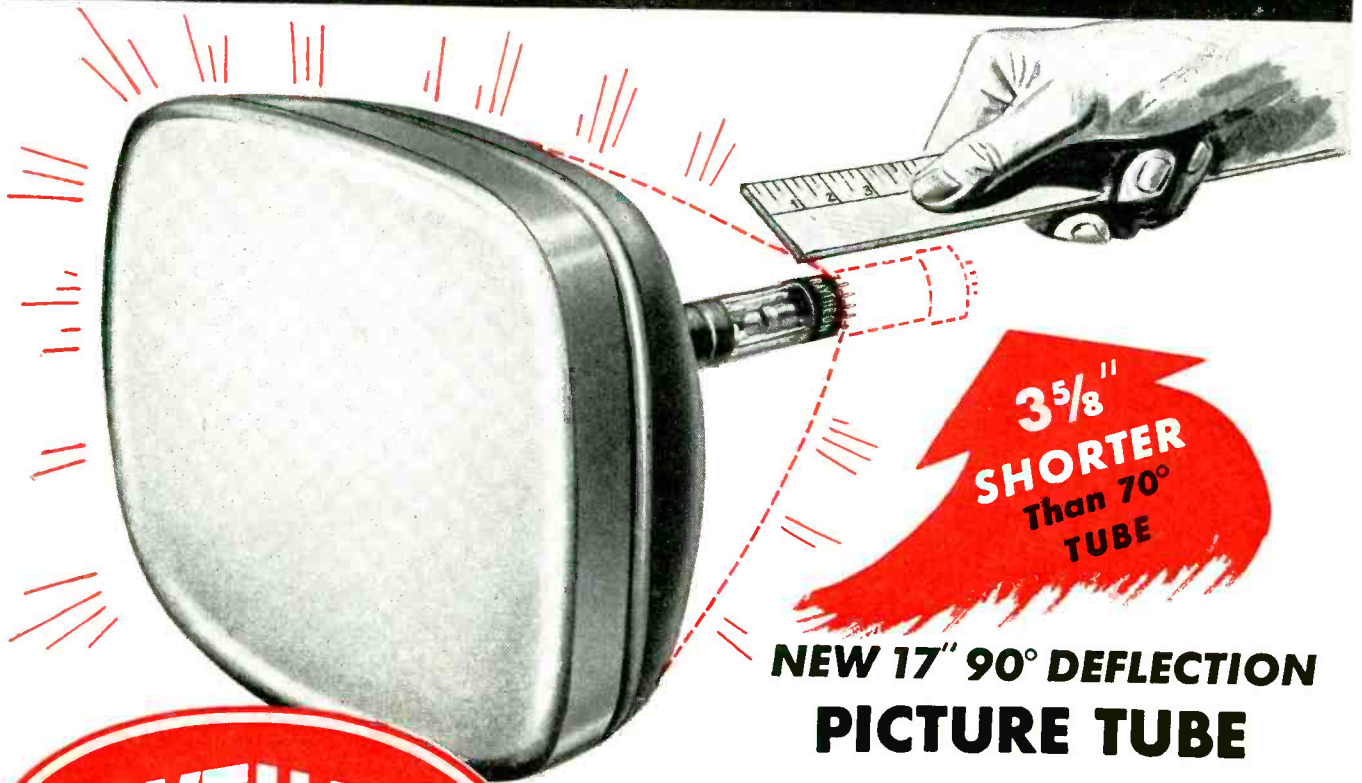


## RAYTHEON 17AVP4

Raytheon leads the way to smaller, light weight, more compact, television receivers with the amazing new 17AVP4 monochrome picture tube. It is  $3\frac{5}{8}$  inches shorter in overall length and approximately 4 pounds lighter than present 17 inch tubes. The type 17AVP4 incorporates a new  $90^\circ$  deflection angle bulb, a 1 inch shorter neck length and achieves maximum compactness with conventional viewing area. The 17AVP4 has electrostatic focus, magnetic deflection and features the same crisp, clean picture that makes all Raytheon Picture Tubes outstanding for quality.

This important new Raytheon tube, developed and produced at Raytheon's new modern picture tube plant at Quincy, Massachusetts is one more reason why you can standardize on Raytheon Picture Tubes with complete confidence that you are giving your customers the very latest and best.

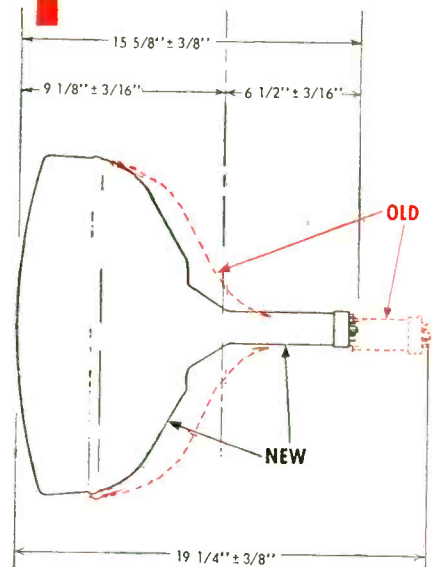*Remember, Raytheon Picture Tubes are Right for Sight, Right for You, and always New. Buy them through your nearest Raytheon Tube Distributor.*



*Excellence in Electronics*

### RAYTHEON MANUFACTURING COMPANY

Receiving and Cathode Ray Tube Operations  
 Newton, Mass., Chicago, Ill., Atlanta, Ga., Los Angeles, Calif.

RAYTHEON MAKES ALL THESE:

RECEIVING AND PICTURE TUBES • RELIABLE SUBMINIATURE AND MINIATURE TUBES • SEMICONDUCTOR DIODES AND TRANSISTORS • NUCLEONIC TUBES • MICROWAVE TUBES



# "Compatible"

LABORATORY  
PERFORMANCE

PRICED  
FOR THE  
SERVICEMAN

\$**189**<sup>50</sup>  
net


For Black and  
White and Color  
Television . . .  
plus FM and AM  
Radio . . .

Unexcelled in performance and versatility, the RCP model 780 is engineered as a completely electronic sweep circuit without motor or moving parts. Unique electronic unidirectional coupling provides for sweep in one direction only at a uniform output level (AGC). For use with any marker generator and oscilloscope, model 780 is the first laboratory type all electronic sweep generator priced reasonably enough for service use.

#### Service Designed for Ease of Operation:

- Built-in Detector/Comparator Permits
  - (1) Visual observation and accurate settings of marker signals and sweep width of alignment of TV IF's and Wave Traps.
  - (2) Laboratory and service technicians to check their test equipment.
  - (3) Check of test set-up for improper grounding or long leads.
- Push button attenuator for rapid, precise alignment and measurements.
- Automatic internal blanking with straight line base generation for scope picture—eliminates return trace.
- 180° 60 cycle phasing voltage for use on all oscilloscopes available on front panel.
- Jack provided for modulation by external signal such as color generators (bar or dot) and is automatically mixed in the sweep circuit.

# All Electronic SWEEP GENERATOR by RCP

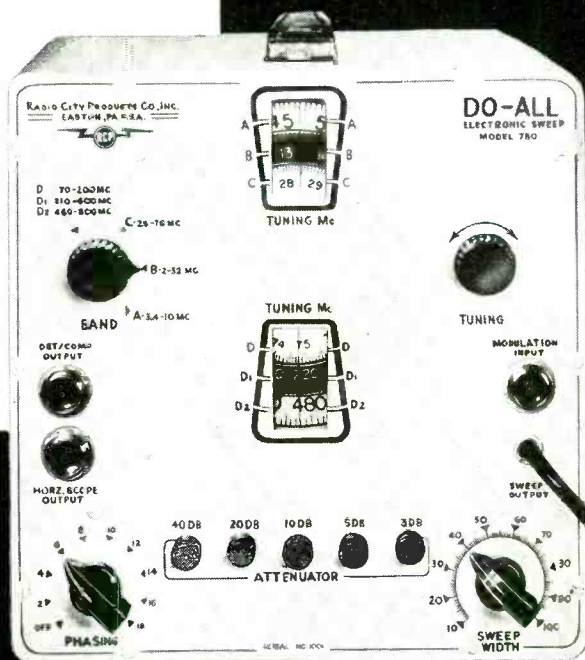

#### Features:

Anti-backlash dial—Electronically regulated power supply—Highly linear sweep to close tolerances of manufacturer's specifications—Range 3.2 megacycles to 800 megacycles—Wide sweep width control 0 to 30 megacycles—Automatic gain control—Precision, triple shielded attenuator.

## SPECIFICATIONS

Sweep Linearity: Exceptional high degree of linearity not possibly obtainable in mechanical sweeps.


| Band | Linearity Sweep Width Within 2 DB   | Linearity Sweep Width Within 4 DB |
|------|-------------------------------------|-----------------------------------|
| A    | 0- 8 mc                             | Max. 15 mc                        |
| B    | 0-10 mc                             | Max. 25 mc                        |
| C    | 0-10 mc                             | Max. 22 mc                        |
| D    | 0- 8 mc @ 70 mc<br>0-20 mc @ 200 mc | Max. 25 mc<br>Max. 30 mc          |



**RADIO CITY PRODUCTS CO.**  
EASTON, PENNSYLVANIA



# Servicing

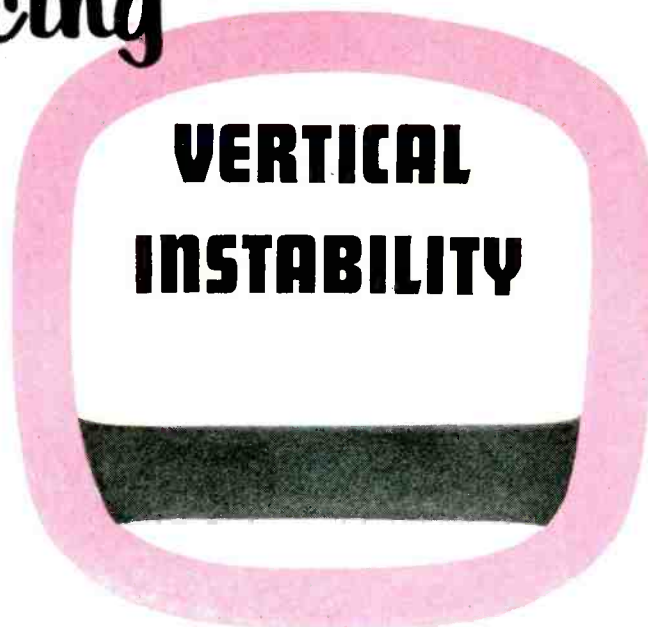

by **Steve Travis**

ONE of the compensations of television servicing is that the symptom shown in the picture tube most often reveals the defective circuit. However this premise may be a faulty one if followed blindly. This is particularly true in the case of vertical instability which generally takes on the following forms:

- 1—Picture locks but is very touchy
- 2—Picture locks but is out of frame
- 3—Vertical jitter
- 4—Any of the above plus excessive contrast

It is very tempting to interpret the above symptoms as being caused by a defect in the vertical oscillator circuit. However, it will be generally found that most vertical sync troubles do not originate in the vertical oscillator circuit proper, but rather in the many circuits that precede the oscillator.

## Sync Compression

The most common cause of vertical instability is sync compression which may be better understood from the following discussion. When the composite video signal is formed at the transmitter, the sync pulses occupy 25% of the upper portion of the signal as shown in Fig. 1.

When the composite video signal is reproduced at the receiver it must be a complete duplicate, in every way, of the signal formed at the transmitter. In certain types of troubles that may occur in the receiver, the amplitude of the



Fig. 1 — Normal signal

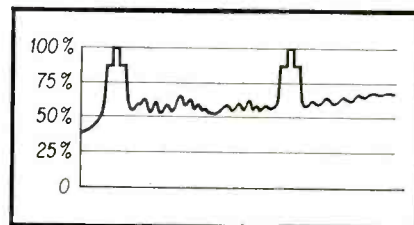


Fig. 2 — Sync. compressed.

sync pulse will be reduced while the video signal amplitude will remain constant or may even become greater. A reduced sync pulse is shown in Fig. 2. From this figure it can be seen that the video signal now occupies 90% of the amplitude and the sync only 10%. The lowered sync level is referred to as sync compression.

Sync compression can occur in any stage through which the composite video signal passes. This includes the:

- 1—RF stage
- 2—IF stage
- 3—Video detector
- 4—Video amplifier

Sync compression in these stages may be caused by any of the following:

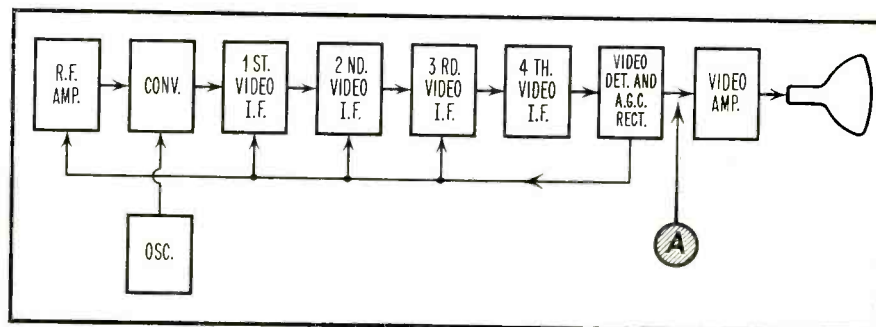


Fig. 3 — Block diagram of sync check at video detector output.



- 1—Defective tubes
- 2—Defective *agc* system
- 3—Defective components causing non-linear amplification

Except for excessive contrast the same symptoms indicated in the first paragraph may develop from defects in the sync circuits themselves. Although not referred to in the category of sync compression we will cover service procedures for these conditions as well.

Since the sync pulses affected are both horizontal and vertical it may be asked why sync compression does not generally result in severe horizontal instability. This is because of the stabilizing effect of the horizontal *afc* circuit. In most cases, if horizontal instability does occur due to sync compression, it may appear as a horizontal pull.

### Service Procedure

The prime objective in trouble shooting is first to isolate the defective stage and then to isolate the defective part within that stage. The first component that should be checked is the tube, and that by substitution only. Care must be taken in this procedure to change *all* the tubes of the complete section suspected. If, for example, more than one *if* amplifier tube is gassy it may be overlooked in a substitution process in which only *one* tube at a time is replaced. When the tubes of a particular section have been eliminated as the possible source of trouble, we can then proceed to eliminate other components in the suspected stage.

### Key Test Points

A key test point for checking sync operation is the video detector output designated as point A in Figs. 3 and 5. By using an oscilloscope we can observe the composite video signal at this point. If there is no sign of sync compression at this point we may then proceed to

check the video amplifier and sync circuits. Proper and improper wave forms are shown in Fig. 4A and B, Fig. 4B indicating compression. The oscilloscope should be adjusted to show at least two vertical fields. If there is any indication of sync compression shown on the scope then the cause must be located somewhere between point A and the *rf* amplifier.

Faults may be isolated by two methods. If the serviceman owns a crystal detector probe, he should connect it to the vertical input terminals of the oscilloscope. This now enables him to check the composite video waveform at any point on the *if* strip. The test procedure is from the last *if* amplifier back to the *rf* stage. If the waveform at the plate of any stage shows compression, and the input does not, the stage being checked is defective. A voltage or resistance analysis will most often show up the offending part.

If the equipment mentioned in the previous paragraph is not available a

second method of attack may be employed. This is a straight voltage analysis from the last *if* amplifier to the antenna. When making this voltage analysis special attention should be paid to the control grid readings. The actual value of voltage to be read at the control grid is determined by the strength of the incoming signal and the condition of the *agc* circuit. Therefore the value of control grid voltage obtained may vary somewhat from published figures. A rule of the thumb range is between -2 to -6 volts.

### Grid Current

Voltage is not the only quantity to be checked. Of equal importance is the absence or presence of grid current. If grid current flows in the *rf* or *if* tubes an inevitable result will be sync compression. This can be checked by measuring the output voltage of the *agc* rectifier at point B in Fig. 5.

This voltage will normally be pro-  
[Continued on page 61]

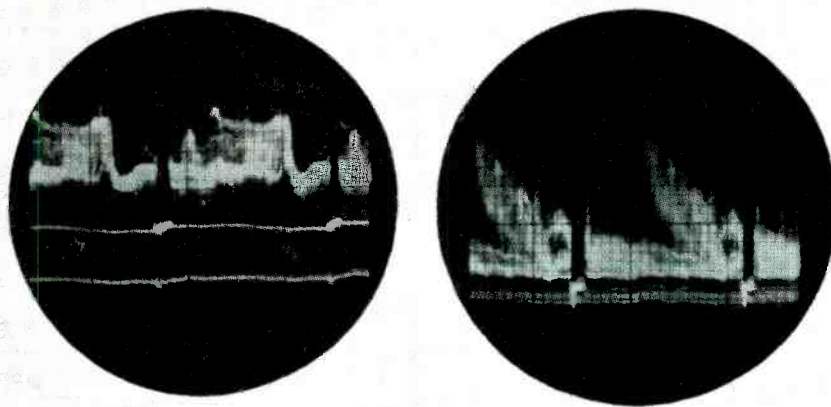


Fig. 4 — (A) Proper and (B) Improper waveforms at video detector output. (B) indicates sync compression in video signal.

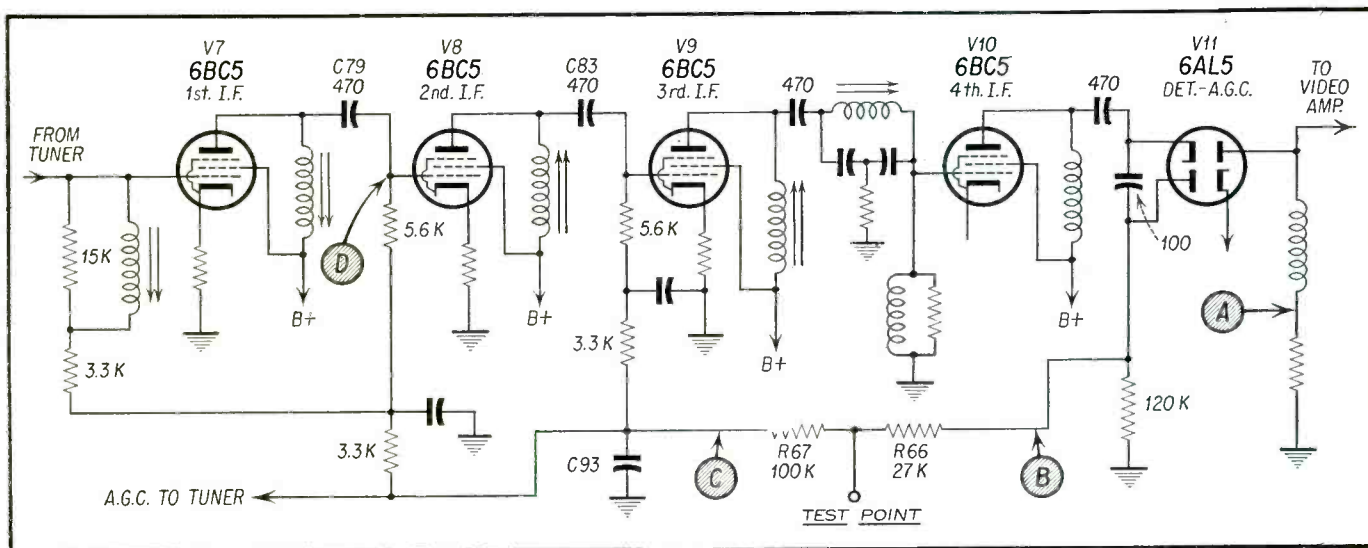



Fig. 5 — Typical video detector, *agc* rectifier and vertical instability distribution circuit.



# HEAR THE DIFFERENCE !

Based on the famous University model WLC Theater System used so successfully and extensively in deluxe stadium and outdoor theater installations . . . auditoriums, expositions, concert halls and other important applications where only the highest quality equipment is acceptable—University engineers now bring you a smaller, compact version—the BLC—for general application in public address work. The BLC is the New standard for both voice and music, indoors and outdoors. The BLC is now yours, at the low low price of

ONLY  
\$75  
LIST

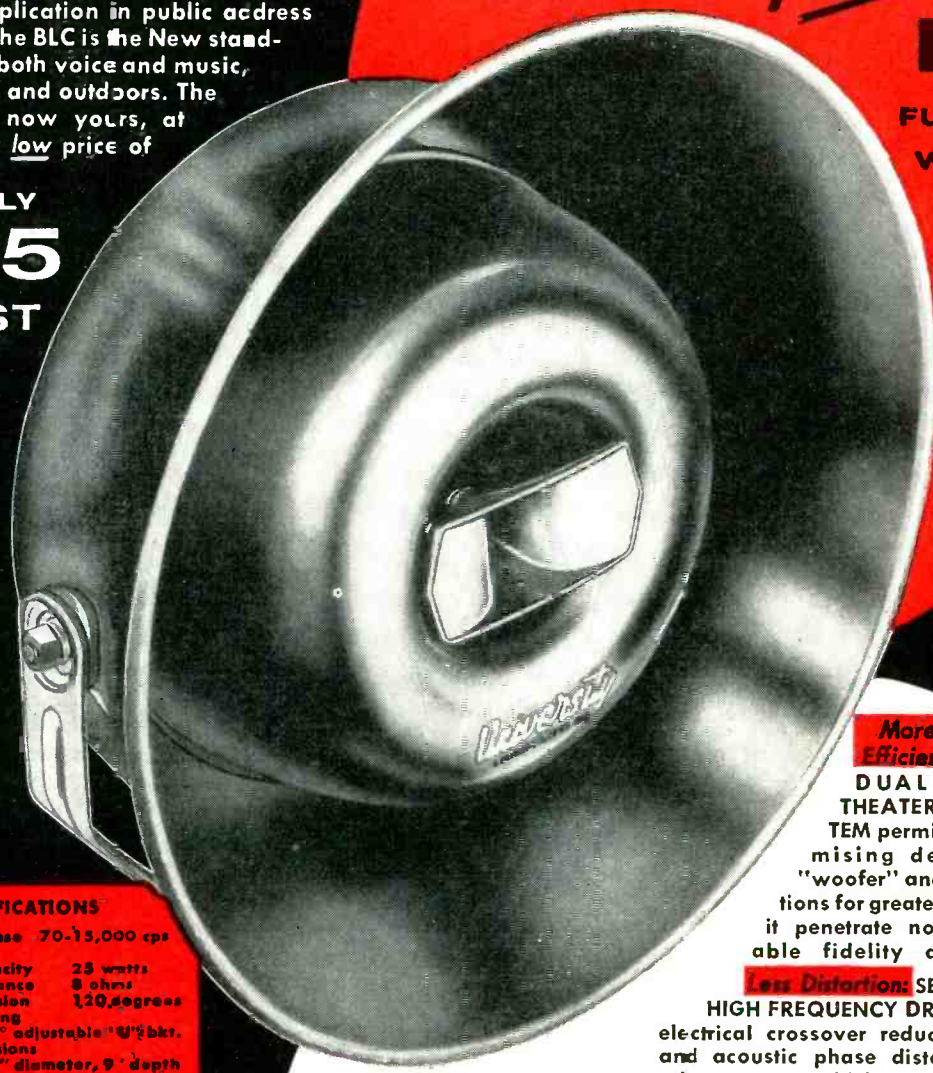


MAKE *Every* P.A.  
A HI-FI INSTALLATION  
WITH THE *New* MODEL  
**BLC**

FULL RANGE  
WEATHERPROOF  
COAXIAL  
SPEAKER


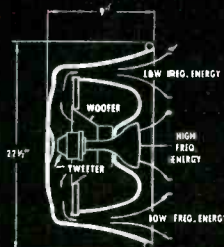
### SPECIFICATIONS

Response 70-15,000 cps  
Power Capacity 25 watts  
Impedance 8 ohms  
Dispersion 120 degrees  
Mounting 180° adjustable U-bkt.  
Dimensions 22½" diameter, 9" depth



Ask your distributor for a convincing demonstration, and HEAR THE DIFFERENCE !

### More Efficient:

DUAL RANGE THEATER TYPE SYSTEM permits uncompromising design of the "woofer" and "tweeter" sections for greatest efficiency. Hear it penetrate noise with remarkable fidelity and intelligibility.

### Less Distortion:

SEPARATE LOW AND HIGH FREQUENCY DRIVER SYSTEMS with electrical crossover reduces intermodulation and acoustic phase distortions common to other systems which attempt to use two different horns on a single diaphragm.

### More Compact:

EXCLUSIVE WEATHERPROOF DUAL RANGE COAXIAL DESIGN eliminates wasted space. Depth of BLC is only 9"; can be mounted anywhere, even flush with wall or ceiling.

### More Dependable:

EXPERIENCED MECHANICAL ENGINEERING AND CAREFUL ELECTRICAL DESIGN meet the challenge of diversified application and environmental hazards. Rugged, and conservatively rated—you can rely on the BLC.

**Better Lows:** BALANCED "COMPRESSION" TYPE FOLDED HORN, starting with eight inch throat and energized by top quality low frequency "woofer" driver provides more lows than other bulky designs.

**Better Highs:** DRIVER UNIT TWEETER with exclusive patented "reciprocating flares" wide angle horn transmits more highs with greater uniformity . . . high frequency response that you can hear!

**University** LOUDSPEAKERS INC.

80 SOUTH KENSICO AVENUE

WHITE PLAINS, N. Y.



A service record unmatched  
in the history of television!

# CROSLEY SUPER-V

*is a service man's dream!*

"No more groping and twisting"

"Entire chassis accessible for service"

*Just look at what  
service men say!*


"By removing the cabinet back, every tube is right in front of one's eyes. No more groping and twisting to relocate tube-socket pins. The separate diagram showing the actual filament wiring makes the search for an open filament a matter of seconds."

L. B. Hallberg, Hardware Products Co., Sterling, Ill.

"The Crosley Super-V is a service man's dream; the new vertical chassis allows the changing of tubes in a few minutes. When service of a more complicated nature is required, the cabinet can be removed by loosening 6 screws; this leaves the entire chassis accessible for service."

Roy R. Thompson, Saginaw Distributors, Inc., Saginaw, Mich.

*Just look inside  
a Super-V!*

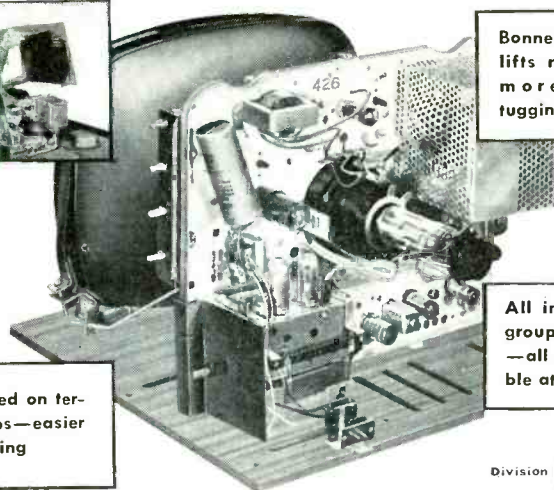

Bonnet-type cabinet lifts right off—no more chassis tugging

All important parts grouped in one plane—all tubes accessible at rear

Points wired on terminal strips—easier circuit tracing

Division  Cincinnati 25, Ohio

**Crosley gives you more for your money!**

# Block Diagram Analysis

of

## COLOR TRANSMISSION

and

## RECEPTION

by **BOB DARGAN**  
and **SAM MARSHALL**

From a forthcoming book entitled  
"Fundamentals of Color Television."

### Part 2

AT this point it would be advisable to discuss the luminance signal,  $E_V$  in somewhat greater detail. The maximum luminance signal of a television scene corresponds to the brightest white area in the field of vision of an observer. The minimum luminance signal corresponds to black.

As indicated in Chapter I, the luminance signal is made up of definite proportions or percentages of the red, green, and blue signals, these being:  
 $E_V = .3 E_R + .59 E_G + .11 E_B$  (II-1)  
These percentages describe the manner in which the individual colors give rise to the sensation of brightness. Thus, green contributes 59%, to the brightness sensation, red 30%, and blue 11%. Mixing these colors in the percentages stated above results in the sensation of colorless light ranging from a bright white to dark gray depending on, how much light is present.

As an example, let us consider the case where a color camera is scanning a peak white scene. According to NTSC specifications equal and maximum primary color signal values appear at the outputs of the three color camera tubes. For a black and white tube to reproduce this sensation of white, the signals would have to be connected to a signal mixing network, called a "matrix," so that the final color signal outputs are produced in the following ratio:

30% red, 59% green, 11% blue.

This is illustrated in Fig. 8A where a maximum white signal produces amplitude as well as percentage ratios of 30, 59 and 11.

Now, if a darker scene is scanned, such as 50% gray, as in Fig. 8B, the

camera voltage outputs will be reduced in each case to  $\frac{1}{2}$  the original value; but the same ratio of color signals will appear at the output of the matrix, that is:

30% red, 59% green, 11% blue.

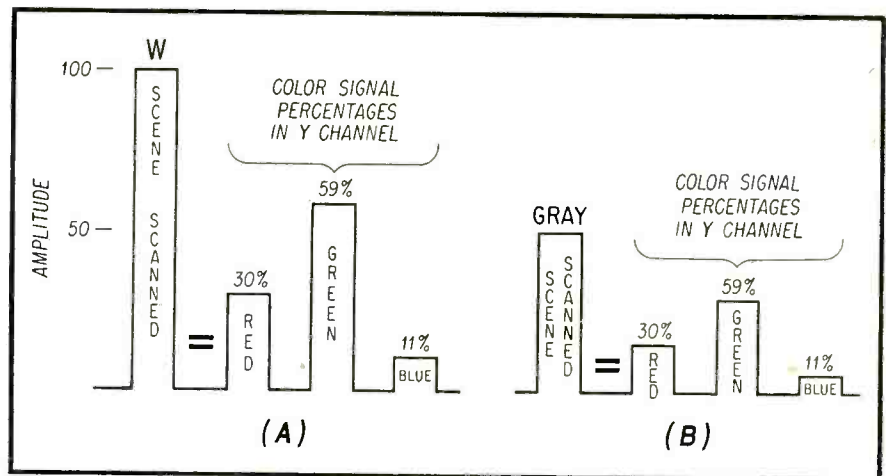


Fig. 8—In (A) 100% white signal scene produces following color signal amplitudes and percentages in Y channel:

Amplitudes: Red-30, Green-59, Blue-11.

Percentages: Red-30%, Green-59%, Blue-11%.

In (B) 50% luminance or gray signal produces following color signal amplitudes and percentages in Y channel:

Amplitudes: Red-15, Green-29.5, Blue-5.05.

Percentages: Red-30%, Green-59%, Blue-11%.

Thus it should be evident that the color signal percentages in a monochrome (white or gray) scene remain constant; what differentiates one monochrome scene from another, that is, white from gray, are the relative amplitudes of the component colors in both scenes.



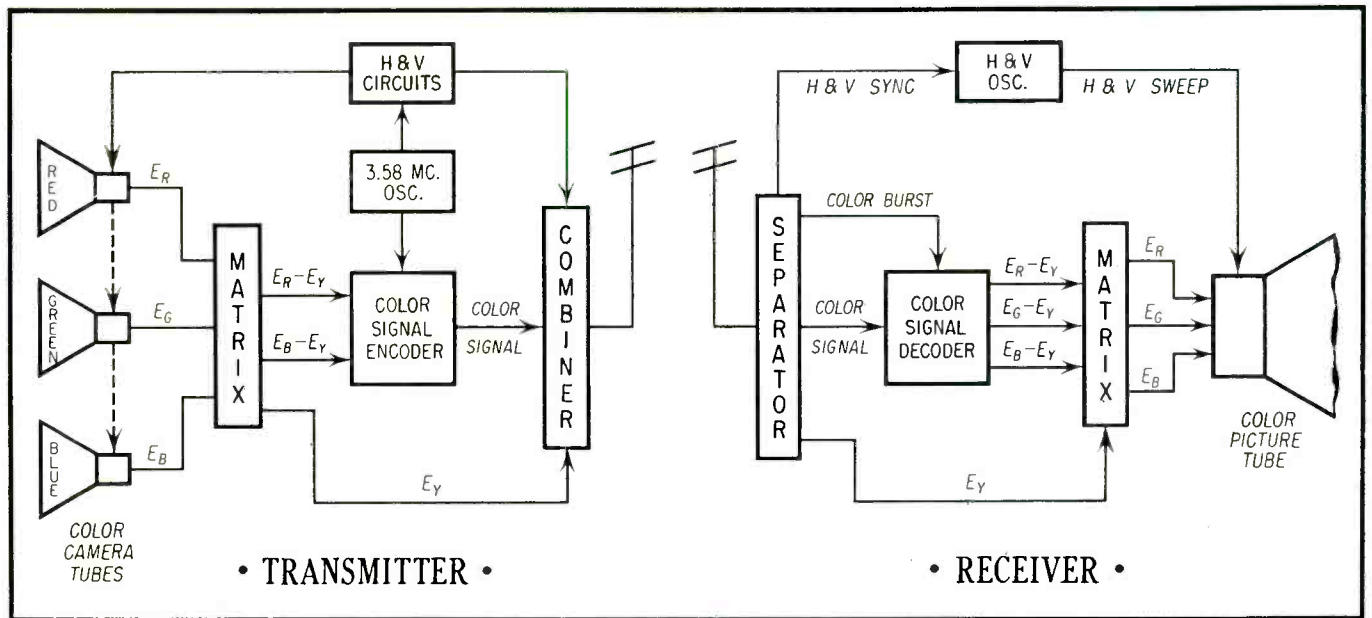


Fig. 9—Block diagram of color TV system with color-difference signals added.

### Color-Difference Signals

We are now ready to find out how the primary color signals leaving the outputs of the color camera tubes are processed so that ultimately two signals are made available for transmission. These are a brightness signal containing the luminance information; and a color signal containing information relative to the hue and saturation of the spot being scanned.

Referring to Fig. 9 we will observe that the three color voltage outputs of the camera tubes are fed into a matrix in the first color signal processing operation we are concerned with. This signal processing involves subtracting  $E_Y$  or the luminance signal from the red color signal and the blue color signal.

Symbolically, by subtracting the  $Y$  signal from the red color signal, we obtain:

$$E_{RED} - E_Y \text{ or } E_R - E_Y$$

This expression is referred to as the red "color-difference" signal. Similarly, the blue color-difference signal can be represented as:

$$E_B - E_Y$$

Notice that  $E_Y$  is brought out as a separate signal from one point on the matrix,  $E_R - E_Y$  from another point, and  $E_B - E_Y$  from a third point. By properly proportioning the matrix values, the  $E_Y$  signal may be made to have the percentages shown in equation II-1.

The red color-difference signal,  $E_R - E_Y$ , therefore is made up as follows:

$$E_R - E_Y = E_R - (.3E_R + .59E_G + .11E_B)$$

$$= .7E_R - .59E_G - .11E_B \quad \text{(II-2)}$$

Notice that negative signal values are indicated in equation II-2. These negative values simply mean that the polarity of the color signal referred to is inverted. Negative signals may be ob-

tained by suitable phase inverting circuits about which additional details will be given in another chapter.

The blue color-difference signal developed at the output of the matrix is shown as  $E_B - E_Y$ , and has the following color signal makeup:

$$E_B - E_Y = E_B - (.3E_R + .59E_G + .11E_B)$$

$$= .89E_B - .3E_R - .59E_G \quad \text{(II-3)}$$

Thus, by proper matrixing we convert the three primary color signals into a luminance signal  $E_Y$ , and two color-difference signals  $E_R - E_Y$  and  $E_B - E_Y$ .

A question that might be asked at this point is why isn't a green color-difference signal also developed. The answer is that it is not necessary to do so in the transmitter inasmuch as this signal may be derived at the receiver by

suitable matrixing of the  $E_R - E_Y$  and  $E_B - E_Y$  signals. Since the latter signals already contain values of  $E_G$  as shown in equations II-1, II-2, and II-3 by suitable additions and subtractions the  $E_G - E_Y$  signal is obtained. This operation will shortly be illustrated.

The real significance of these new color signals is that we have reduced the color information to be transmitted from three primary color signals to a  $Y$  signal and two color-difference signals. Exactly how the color-difference signals are transmitted will shortly be explained. First let us see how the color-difference signals are processed at the transmitter, then at the receiver; and then how eventually the original red, green, and blue color signals are reestablished.

A comparison between the transmitter sections of Figs. 6 and 9 will reveal that except for the creation of the color-difference signals, Fig. 9 is the same as Fig. 6. Observe that  $E_R$ ,  $E_G$ , and  $E_B$  enter a matrix where  $E_Y$  and the color-difference signals are formed.  $E_Y$ , the complete luminance signal enters the combiner preparatory to becoming part of the composite video signal.  $E_R - E_Y$  and  $E_B - E_Y$  enter a new color encoder where in combination with the 3.58 mc subcarrier a single color signal is formed. As in Fig. 6, this color signal combines with the  $Y$  signal and the sync signal to form the composite video signal.

At the receiver, (Fig. 9), the color-difference signals may be used to recover the original  $E_R$ ,  $E_G$  and  $E_B$  signals. For instance, to recover  $E_R$  we simply add  $E_Y$  to the red color-difference signal in a suitable matrix and obtain:

$$(E_R - E_Y) + E_Y = E_R \quad \text{(II-4)}$$

To recover  $E_B$  we simply add  $E_Y$  to

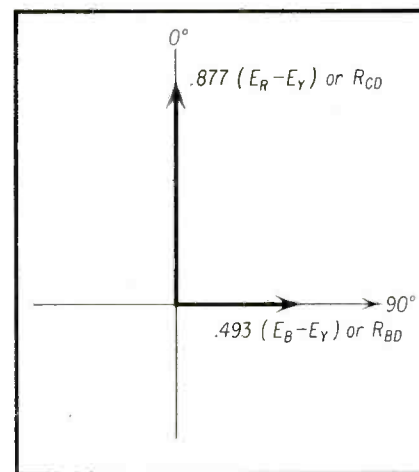


Fig. 10A—Phase relations between color difference signals after modulation of sub-carriers. Assume the  $E_R - E_Y$  axis to be the zero degree reference axis.

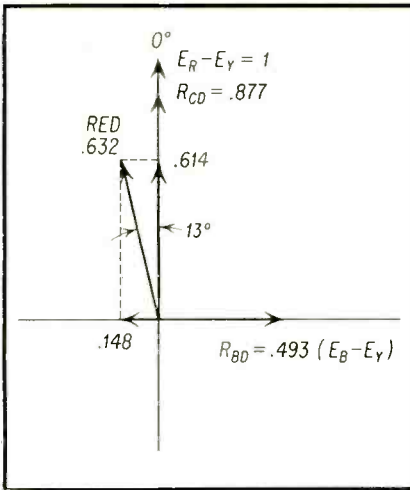


Fig. 10B—Relative values of color difference signals developed as a result of pure red signal. Phase displacement of red signal is 13°. Relative amplitude is .632.

the blue color-difference signal and obtain:

$$(E_B - E_Y) + E_Y = E_B \quad (\text{II-5})$$

To recover  $E_G$  we add  $E_Y$  to the green color difference signal and obtain:

$$(E_G - E_Y) + E_Y = E_G \quad (\text{II-6})$$

It was originally stated that  $E_G$  is

obtained at the receiver, by combining  $E_R - E_Y$  and  $E_B - E_Y$ . We will now see how this is done. It can be shown (See proof of Equation II-7 below) that:

$$E_G - E_Y = \frac{-30}{59}(E_R - E_Y) - \frac{11}{59}(E_B - E_Y) \quad (\text{II-7})$$

Thus, if in the decoder we adjust our circuit components to obtain the above negative signals in the fractions or percentages shown,  $E_G - E_Y$  may be obtained.

To summarize this section up to this point, we have shown how the original color signals are converted at the transmitter matrix into a Y or luminance signal and two color-difference signals. At the receiver the color-difference signals are mixed in a matrix to reproduce the original  $E_R$ ,  $E_G$ , and  $E_B$  color signals. Although the green color difference signal is not developed as a separate signal in the transmitter, in the receiver it may be obtained by proper matrixing of the  $E_R - E_Y$  and  $E_B - E_Y$  signals.

Comparing Fig. 9 with Fig. 6, no change was made in the block diagram other than to remove the color-difference signals from the encoder and decoder and to treat them in separate sections.

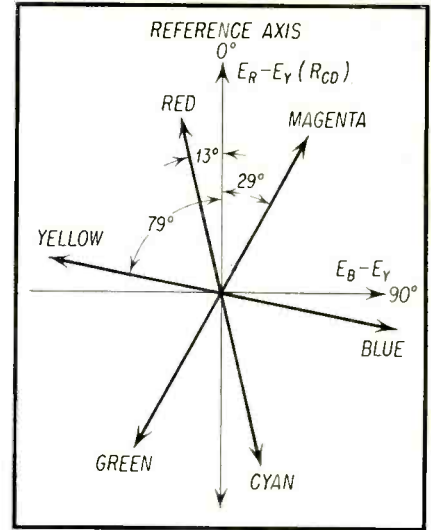


Fig. 11—Phase displacements of various color signals with respect to  $E_R - E_Y$  axis.

### Reduced Color Difference Signals

We are now ready to go one step further in our analysis of the color system, that is, the development of a new set of color signals directly related to the previous color-difference signals. These new color signals are necessary to the operation of the NTSC color system.

Ordinarily the original color-difference signals as developed could be used to modulate the color subcarrier. However, it has been found that the color portion of the composite signal may cause overmodulation at certain color signals on maximum signal amplitudes. To prevent this overmodulation the color-difference signals are attenuated so that the new value of the red color difference signal which we shall call  $R_{CD}$  is:

$$R_{CD} = .877 (E_R - E_Y) \quad (\text{II-8})$$

In like fashion the new value of the blue color difference signal which we shall call  $B_{CD}$  is:

$$B_{CD} = .493 (E_B - E_Y) \quad (\text{II-9})$$

It might be pointed out that even with the above reduced color-difference signal values a certain amount of overmodulation could be produced if the scene scanned contains highly-saturated colors. This possibility is so unlikely that it can safely be assumed that no trouble will arise from over-modulation of this type. Of course the color-difference signal could be further compressed to eliminate the possibility of any overmodulation. However, doing this would result in a serious reduction of the signal to noise performance of the color channel.

### Color Signal Phase Relations

The new color-difference signals  $R_{CD}$   
[Continued on page 62]

Equation II-7 may be proved by expanding the right side as follows:

$$E_G - E_Y = \frac{-30}{59} (E_R - E_Y) - \frac{11}{59} (E_B - E_Y) \quad (2)$$

$$= -.51 (E_R - E_Y) - .19 (E_B - E_Y) \quad (3)$$

Collecting terms  $= -.51 E_R + .51 E_Y - .19 E_B + .19 E_Y \quad (4)$

Expanding  $E_Y = -.51 E_R - .19 E_B + .7 (3 E_R + .59 E_G + .11 E_B) \quad (5)$

$$= -.51 E_R - .19 E_B + .21 E_R + .413 E_G + .077 E_B \quad (6)$$

Collecting terms  $= -.3 E_R - .11 E_B + .41 E_G \quad (7)$

.41  $E_G$  may be written as:  $.41 E_G = -.59 E_G + E_G \quad (8)$

Substituting: (8) in (7)  $= -.3 E_R - .11 E_B - .59 E_G + E_G \quad (9)$


(The first three terms above are equal to  $-Y$ , therefore)

$$E_G - E_Y = E_G - E_Y$$

Thus, the right side of equation II-7 is identical with the left side, and equation II-7 is proved correct.


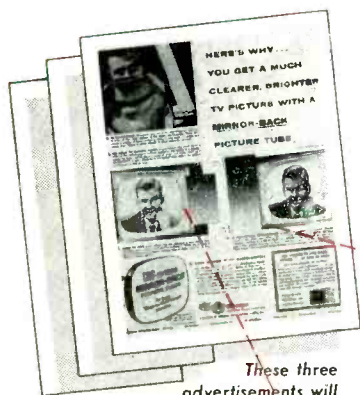
# Now, TV set owners can understand benefits of Aluminized Tubes!



These three advertisements will appear in **Post** this fall.

## THESE ADVERTISEMENTS IN **Post** EXPLAIN THAT:

1. **IN MAGAZINES**, the pictures you see (when magnified) are made by a series of tiny dots applied to the paper *mechanically*.

**ON YOUR TV SCREEN**, the pictures are also made by a series of dots (which appear as lines) applied *electronically*. These dots, in both cases, create a variety of tones including black, a range of grays, and white. **BUT**, it is the **LENGTH** of this "Black-to-White Range" (the gray scale) that makes the picture excellent, good, fair, or poor.




ARTHUR GODFREY famous CBS star



TRUE BLACK

SHORT  
"BLACK-TO-WHITE RANGE"

TRUE WHITE

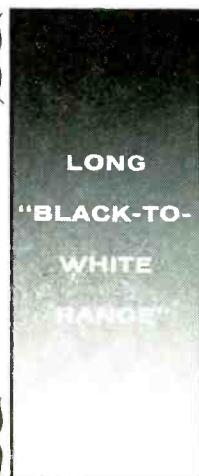

LONG  
"BLACK-TO-WHITE RANGE"



2. **ORDINARY PICTURE TUBES** used in most TV sets made before 1953 produce a *short* "Black-to-White Range." While the picture is good, the picture tube cannot develop enough *light output* for a *long* "Black-to-White Range."

3. **CBS-HYTRON MIRROR-BACK TUBES** produce up to *twice the light output* of ordinary picture tubes. Like the silver backing on a mirror, the *shiny* aluminum backing on a Mirror-Back tube reflects to the viewer *all the light* on the screen. The resulting increased brightness and reduced halation (unwanted spreading of light from one dot to another) is *essential* to give you a *long* "Black-to-White Range." The full range you *must* have for the clearest, sharpest, brightest pictures that are a joy to watch.

**TALK LONG "BLACK-TO-WHITE RANGE" PICTURES**  
**...SELL BIGGER-PROFIT**

## CBS-HYTRON MIRROR-BACK PICTURE TUBES

Talk . . . demonstrate . . . and sell "Long-Black-to-White-Range" clearer, sharper, brighter pictures. It's easier to sell premium-grade, brand-new CBS-Hytron Mirror-Backs . . . with their controlled quality and dependable full-year guarantee. Profit more. Tie in with **POST**. Get this Mirror-Back Promotion Kit . . . from your CBS-Hytron distributor, or mail coupon.



CBS-HYTRON Main Office: Danvers, Massachusetts

A Division of Columbia Broadcasting System, Inc.

A member of the CBS family: CBS Radio  
CBS Television • Columbia Records, Inc.

CBS Laboratories • CBS-Columbia • CBS International • and CBS-Hytron



CBS-HYTRON, Danvers, Mass.

I want all the material to identify me as a *Certified Quality Service* dealer who sells Mirror-Back tubes. Please rush me CBS-Hytron Mirror-Back Promotion Kit containing:

1. 22 x 28-inch Advertised-in-POST window poster.
2. 25 consumer self-mailers, "How You Can Have Clearer, Sharper, Brighter TV Pictures."
3. *Certified Quality Service* decalomania.

I enclose 25¢ for postage and handling. I want . . . more consumer self-mailers at 1¢ each, for which I enclose an additional \$ . . .

Name . . . . . (please print)

Street . . . . .

City . . . . . State . . . . .



# ASSOCIATION NEWS

## NETSDA—New York

Activity for the fall season was initiated by delegates representing Radio and TV Service Dealers and Technicians Associations from Pennsylvania, New Jersey and New York, at a meeting Aug. 29 of the National Electronic Technicians and Service Dealers Associations, in New York. Provisions were made for incorporation as a non profit Corporation and officers were elected to hold office until the annual meeting in January. Committees were appointed to work on and develop the scope and activity of NETSDA. A definite program toward exchange of ideas and liaison between all associations was an important committee activity.

## ARTS—Chicago

A series of nine talks on Color Television to be given by experts in the field of TV manufacturing and servicing is to be sponsored by the Associated Radio and TV Servicemen. The schedule, from October through January, will cover Color transmission, construction and development of tube, the CBS planar mask tube, and colorimetry. The second phase of lecture will begin at the end of January, 1955, and will involve circuitry, design problems, repair problems, and color vs. B&W operation.


## TEA—Fort Worth, Texas

The Radio and Television Service Clinic and Electronics Fair, held annually under the sponsorship of the Texas Electronics Assn., Inc., was presented at the Adolphus hotel in Dallas, during August 27-29, and featured clinical discussions of all facets of the servicing industry—B&W and color servicing techniques, service cost analysis, collections, small claims courts, TVI, public relations, merchandising, service-management relations, and a special comprehensive lecture on color theory. Factories, representatives, and distributors were well represented.


## SORRY—Wrong Association

We offer our sincere apologies for the confusion caused by our unfortunate reference in last month's "Association News" to the LIETA "Guild" News. The "Guild" News is not published by LIETA, but by the Radio Television Guild of Long Island, the group which has taken an exemplary step by instituting their effective Public Relations Program.

# FULL VIEW FULL VALUE

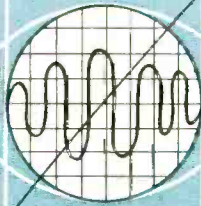

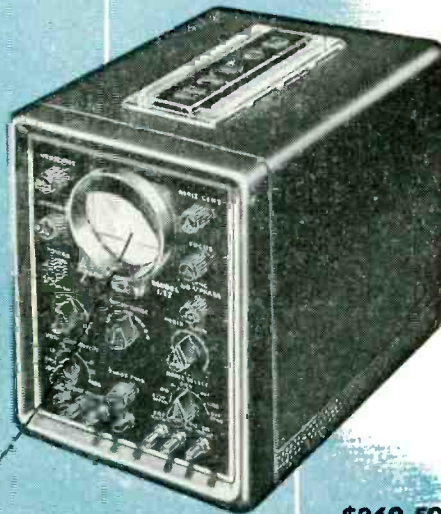WITH A  
**HYCON**  
**OSCILLOSCOPE**  
**MODEL 617**



**\$269.50**

SHARP UNDISTORTED TRACE EDGE TO EDGE

You get *more* for your scope dollar in a Model 617 Oscilloscope, because Hycon's special flat face 3-inch tube eliminates fringe distortion. You pay for a 3-inch scope—you get 3 inches of sharp, usable trace.

And this precision scope meets all requirements for color TV servicing. So before you buy any scope, compare it to the Model 617 feature by feature. For full view—full value you'll buy Hycon... setting the standards "where accuracy counts."

- 4.5 MC BANDPASS WITHIN  $\pm 1$  DB (VERTICAL AMPLIFIER)
- HIGH DEFLECTION SENSITIVITY (.01 V/RMS PER INCH)
- INTERNAL CALIBRATING VOLTAGES
- EDGE LIGHTED BEZEL
- STURDY, LIGHTWEIGHT CONSTRUCTION



See Hycon's line of matched, bench-stacking test instruments at your Electronic Parts Jobber's.



Service facilities in your area.

# Hycon Mfg. Company

2961 EAST COLORADO STREET PASADENA 8, CALIFORNIA

"Where Accuracy Counts"



*New*  
**UHF & VHF  
 LEAD-IN**

Thousands of separately sealed tiny cells, filled with inert gas, make this waterproof cable stable and efficient electrically.

**ADVANTAGES:**

- 1 Lowest losses at UHF and VHF frequencies.
- 2 Great abrasion resistance and mechanical strength.
- 3 No time-consuming end seal required; easy to install.
- 4 No internal moisture to cause signal loss.
- 5 No kinking when used with antenna rotors.
- 6 Resistant to snow, ice, rain, and wind.
- 7 Resistant to ultraviolet rays from the sun.
- 8 Uses Belden Weldo™ conductor for long conductor life.
- 9 Can be clamped tightly in stand-off insulators without crushing. No special fittings required.
- 10 Conductor spacing is constant even when the lead-in is transposed.
- 11 No stripping problem for attaching the conductor.

This heavy wall of brown virgin polyethylene protects the cable against mechanical abuse and damage from ultraviolet sun rays.

*...Cuts*  
**SIGNAL LOSS**

This completely new 300-ohm line results from the development of a new cellular plastic core where each separate cell is filled with an inert gas to make an efficient cable with the lowest possible losses at both UHF and VHF frequencies. With this absolutely waterproof cable, no sealing of the ends is necessary. Celluline cable can be fixed in stand-off insulators without crushing. The thick outer wall of polyethylene serves to protect the cable from abrasion and sun damage.

By fusing *only* virgin polyethylene, the wall can be made smooth—absolutely free from rough spots—to prevent the adherence of dust and other impurities which would increase the losses.

The copper-covered steel strands, which make up the conductors, assure 49% greater resistance to breaking from flexing or stretching than any all-copper conductor.

**8275 CELLULINE<sup>®</sup>**  
 TRANSMISSION LINE

by **Belden**  
 WIREMAKER FOR INDUSTRY



# Hot Off The Press!

**NEW**  
**SANGAMO**  
*twist-tab*  
**DRY ELECTROLYTIC**  
**CAPACITOR**  
**REPLACEMENT**  
**GUIDE**

FILL IN AND  
MAIL THIS COUPON  
TO DEPT. SP

**the little Indian says: SEND FOR YOUR FREE COPY TODAY**



PLEASE SEND ME A FREE COPY OF YOUR NEW TWIST-TAB  
REPLACEMENT GUIDE

NAME \_\_\_\_\_

FIRM \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_

SC54-15

**SANGAMO ELECTRIC COMPANY • MARION, ILL.**

**NOW SERVING**  
**Successful**  
**MASTER**  
**TV SYSTEMS**  
**FROM COAST TO COAST**



**B-T LABS** 'Add-A-Unit'  
MODEL CA-1

**AUTOMATIC ALL-CHANNEL**  
**COMMERCIAL ANTENSIFIER**

The Model CA-1 is probably the most popular VHF signal amplifier in the field. In use since 1951, it has weathered every conceivable test of performance and endurance.

The fact is that there are more B-T CA-1 line amplifiers in use today, than any other single make. The reasons are clear. The Model CA-1 performs effectively and reliably. It is economical, and is amazingly simple to install.

*These are the important features:*

**GAIN** — 27db (22x)

**IMPEDANCE** — 75 ohms and 300 ohms at input and output terminals.

**CONTROLS** — Screw-driver gain control.

**TUNING** — None . . . automatic all-channel transmission.

**INSTALLATION** — Ordinary screw terminals. No special tools required.

**TUBES** — (2) 6J6 and (2) 6BQ7 in cascaded, push-pull circuit.

**CABINET** — Hammertone gray metal. 8 x 4½ x 5". Weighs 5 lbs.

List Price **\$7750**

. . . and for no-loss distribution of amplified TV signals in multi-set installations, see the



**Models DA-2 and DA-8**  
**Distribution Amplifiers.**

For Complete Data on VHF-UHF  
Distribution, write to Dept. YK-7

**BLONDER-TONGUE LABORATORIES, INC.**

Westfield, New Jersey




**BUY  
QUALITY...**

**BUY *TRIO***

Uses Famous New "INSTA-LOK" Clamp


**THE  
*TRIO*  
VARI-CON**

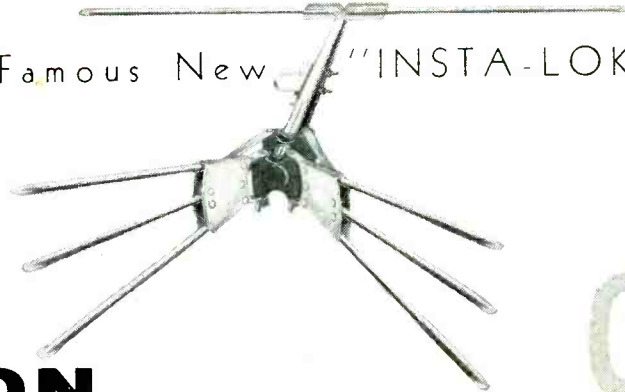

CHANNELS  
2 thru 83


ADJUSTABLE For Higher Gain On The Channels Of Your Choice

- 10 seconds assembly and peaking time
- Only antenna with spring dampeners—lessens element breakage
- "Insta-Lok" Clamp, revolutionary new parasitic element support for instant, permanent alignment. Locking strength exceeds element strength.
- New Mycastyrene insulators.
- Available in 1, 2, 3 & 4 bay models for ultra-fringe or all-channel reception.

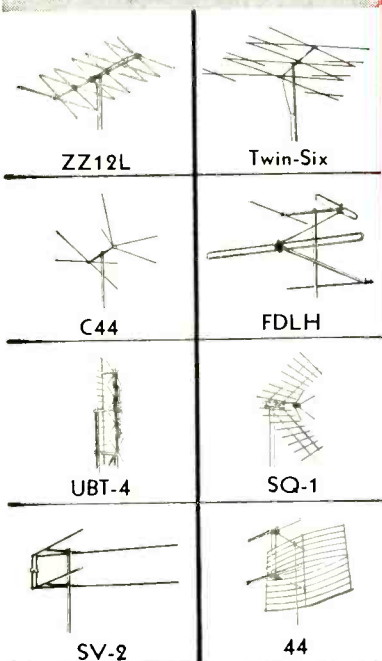


***TRIO* 88**

Far superior construction. Rugged, foolproof—easily installed. Parasitic elements supported by TRIO's revolutionary new "Insta-Lok" clamps. Low channel dipoles supported by the strongest conical head made. No vibration—No element shedding. Completely pre-assembled. Available in single or two bay models.

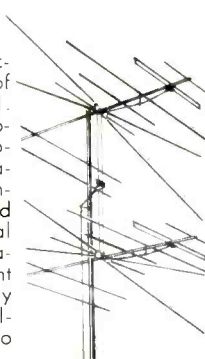


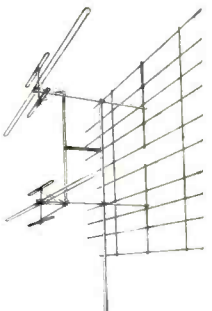***TRIO* 66**

Three dipoles provide exceptionally high gain on all VHF channels. Exclusive TRIO grid reflector gives improved performance. Extremely rugged yet lightweight. Pre-assembled—simply unfold and tighten reflector and dipole assemblies. Three vertical braces on reflector screen for increased strength. Available in single or two bay models.



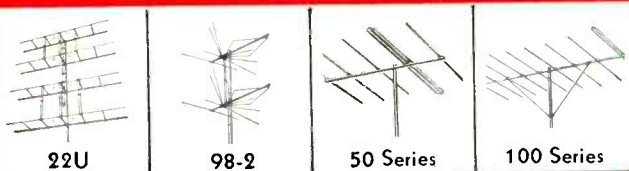Ask To See America's Most Dependable And Beautiful Rotator:



The New TRIO  
**"ARISTOCRAT"**

**TRIO** Leader in Antenna Development

# Community



**T**ELEVISION is no longer a stranger in Casper, Wyoming. It will not remain a stranger in many other cities if they follow the example of Casper. How pictures were brought to this prairie city from Denver, Colorado is a study of free-enterprise in operation. The clear, stable picture enjoyed here (almost 300 miles from Denver) is a result of well-planned local investment plus engineering skill and cooperation. Through the enthusiasm and efforts of Bill Daniels, president of the Community Television Systems of Wyoming, Inc. the citizens can receive entertainment from the four major networks carried by Denver television stations.

Mr. Daniels conceived the idea, and with the guidance of T. G. Morrissey, a Denver consultant engineer, presented the plan that was accepted by some thirty local investors. Approximately one year, and a half-million dollars later Casper had television (beginning December 1953). In less than a year there have been 900 subscribers and an anticipated 3000 by January 1955. Equipment and line installations have been made to serve a potential 9000 subscribers.

Management and engineering for Community Television Systems of Wyoming (C.T.S.) are under the capable directions of two brothers, Gene and Richard Schneider. Gene takes care of the business administration and enrollment of new subscribers while Dick supervises the installations and maintains the equipment in peak operating condition. They also were responsible for the installation of the distribution

system that carries the signal to all parts of the city.

The Casper signal originates at a mountain location, Crow Creek Hill in Wyoming, some 100 miles from Denver. Here each station (Channels 2, 4, 7, and 9) are picked up and prepared for transmission via microwave link to Casper. An operator is on duty at this location at all times that the Casper viewers are receiving signal. One of his duties is to make the change-over from one station to another in accordance with a program schedule distributed to

Casper viewers. Only a single-channel link is employed, consequently, Casper viewers receive a program from only one of the Denver stations. The station to be chosen at Crow Creek Hill for each quarter-hour period is determined by local popularity polls. Viewers set their receivers to Channel 4 while the actual program choice is made at Crow Creek Hill. A typical day's program would be as follows:

Channel numbers indicate the Denver station distributed during time period indicated. Casper receivers are set to Channel 4 for all programs.

The composite video signal from the chosen station at Crow Creek is next supplied to the A.T.&T. Co. This signal (approximately 6000 megacycles) is microwaved over a 200-mile path from Crow Creek to Casper. Actually the line of sight distance is only 122 miles but relay link follows an arc path because of terrain conditions (mountains north of Laramie), Fig. 1. Five intermediate booster links are required with the signal finally terminating at the telephone building in Casper. From here the composite video signal is sent via coaxial cable to the control room and offices of the C.T.S. of Wyoming.

Here the signal is amplified and prepared for modulation of a low-powered transmitter (tuned to Channel 4) which feeds the signal to a Jerrold community television distribution system. Program sound is also conveyed over the link and modulates another carrier displaced by 4.5 megacycles from the Channel 4 picture carrier.

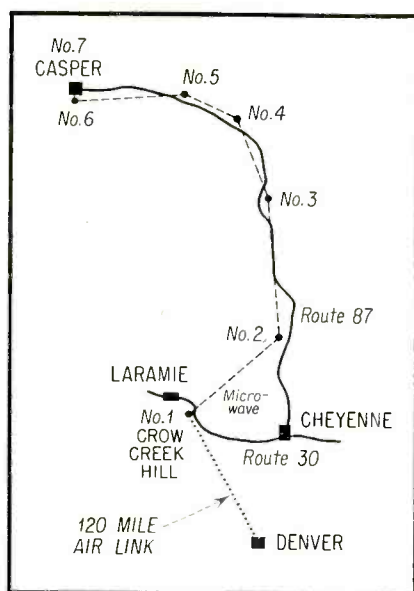


Fig. 1—Air and microwave link from Denver to Casper.



# TV System

by Edward M. Noll

A well-planned local investment plus engineering skill and cooperation yield a clear, stable, community-wide reception. The complete story of the organization and operation of this service.



## Master Receiver and Control Locations

The functional plan of the CTS equipment required at Crow Creek and at Casper is shown in Fig. 2. The Denver stations are picked up on individual Yagi antennas and applied to four quality receivers (individual receiver for each station). Each receiver can be switched to other channels in case of failures or desire to pick up additional channels as they come on the air.

The sound and picture outputs of

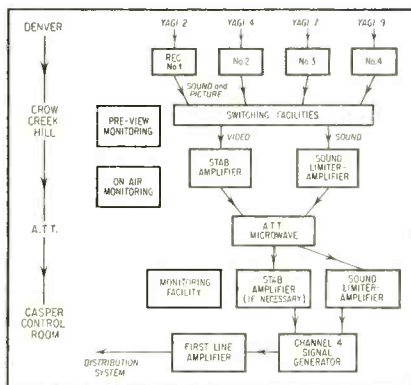


Fig. 2—Community Television system equipment at Crow Creek Hill and Casper.

each receiver are supplied to a switching system that permits a choice of the station signal to be sent to Casper. The video channel through which the signal passes contains a stabilizing amplifier for proper cleaning and shaping of the synchronizing information while the audio channel has gain and limiter circuits for proper setting of program sound levels and peaks.

Elaborate dual monitoring facilities are provided for checking sound levels, picture quality, and waveform fidelity for both the station now "on air" up in

Casper as well as to preview the next station to be switched over to the link. An operator is on duty at this location during the 12-hour program period for each day.

At the Casper control center of CTS, video and audio are monitored again before application to Channel 4 signal generator. Sound is passed through another limiter-amplifier and level indicator. A second stabilizing amplifier can also be switched into the video channel when necessary. Picture and sound signals are used to modulate the Channel 4 signal generator that has facilities for proper adjustment of contrast, brightness, and white level of the composite video modulation.

## Distribution System

The Casper distribution system has been installed over the entire city. Main feeder lines fan out from the central location of CTI offices with secondary lines running down the front or back of most every street. Thus, this system can already serve 9000 potential users. Only the drop-offs into individual houses need to be made as new subscribers are obtained.

The central location of the control point permits an efficient arrangement of the main feeder lines so that no single line has more than 11 amplifiers in cascade. When the signal enters the edge of a city (as it does with many community antenna systems) it is more difficult to obtain an ideal feeder arrangement. All lines in the Casper installation are double-shielded, minimizing greatly the radiation problems encountered with the earlier community antenna systems. In fact there has been only one known case of "signal stealing" in the area and that was via a needle pierced through the line.

The Casper subscriber pays \$150 to be attached to the line and a rental of

\$7.50 per month (plus 8% federal tax) to receive his television. We who receive so much television for so little should take note. We are too prone to forget that television affords so much entertainment for so little. Our bouquets should go to the subscribers of Casper who pay more for television, appreciate it more, and realize they still are obtaining an entertainment bargain.

Distribution amplifiers are spaced along the main feeder lines to compensate for cable attenuation, permitting the development of a constant amplitude signal at all points along the distribu-

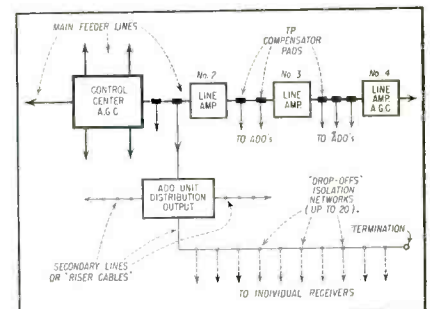


Fig. 3—Basic plan of community distribution system.

tion system. In fact every third amplifier along each main feeder is a Jerrold automatic gain control amplifier—this type of amplifier retains a constant output despite signal variations, voltage changes, and changes in loading conditions along the feeders. It is the operation of these units that ensures uniformity of performance throughout the system.

At various points along the main feeder lines distribution outlets can be attached via special compensator pads. These compensating pads, Fig. 3, prevent interaction between tap-off points along the main feeder and permit application of a constant amplitude signal

[Continued on page 56]

See For Yourself!



*New!*

**PHILCO**

**SUPER PERFORMANCE**

**TV**


**ANTENNAS**




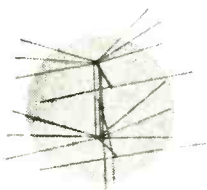
# GUARANTEED TO OUTPERFORM ANY EQUIVALENT TYPE ANTENNA OR YOUR MONEY and LABOR COSTS BACK!


There's been enough words written about TV antenna performance. Now . . . *see the facts for yourself!* Compare any of the new PHILCO Super-Performance TV Antennas with any equivalent type on the market. If the new PHILCO does not give you the finest picture possible, your money back for the antenna *plus* your labor costs up to \$10.00. Ask your PHILCO Distributor for complete details on this amazing offer!



**PHILCO VHF  
SUPER CONICAL**
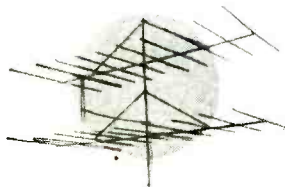
## **PHILCO TWO-BAY SUPER CONICAL ALL-CHANNEL ANTENNA**

Strong signal pickup on VHF channels 2 through 13 . . . UHF channels 14 through 83 . . . ideal for fringe area reception . . . all-aluminum construction with dowelled elements: Part No. 45-3096-2. Rugged single bay design: Part No. 45-3096.




**PHILCO VHF  
LOW BAND YAGI**

## **PHILCO TWO-BAY VHF LOW BAND YAGI ANTENNA**

10 elements . . . all-aluminum . . . factory pre-assembled. Top performance on channels 2 through 6 . . . 13 db to 15 db gain on various channels. Single bay Part No. 45-3112-2 through 6. Stacked version harness Part No. 45-3267.
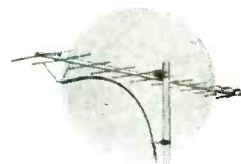
## **PHILCO GOLDEN YAGI UHF ANTENNA**

Designed for 300 ohm operation . . . all metal construction . . . 11 db to 12 db gain on various channels. "Cronak" coated components resist salt air . . . humidity. Six models cover entire UHF spectrum: Basic Part No. 45-1996.



**PHILCO UHF  
GOLDEN YAGI**

## **PHILCO PARAFLECTOR ALL-CHANNEL UHF ANTENNA**

Pre-assembled, all-aluminum . . . 8 to 10 db gain . . . outstanding fringe area performance . . . immediate mounting on existing masts. Part No. 45-3071. Bow Tie, Part No. 45-3069 and Bow Tie with reflector, Part No. 45-3070 give top quality pictures in many UHF areas.



**PHILCO UHF  
PARAFLECTOR**


**PHILCO CORPORATION ACCESSORY DIVISION**

"A" AND ALLEGHENY AVE. • PHILADELPHIA 34, PA.

A new standard in  
 electrical and mechanical  
 perfection in all **32**  
 new YAGI antennas





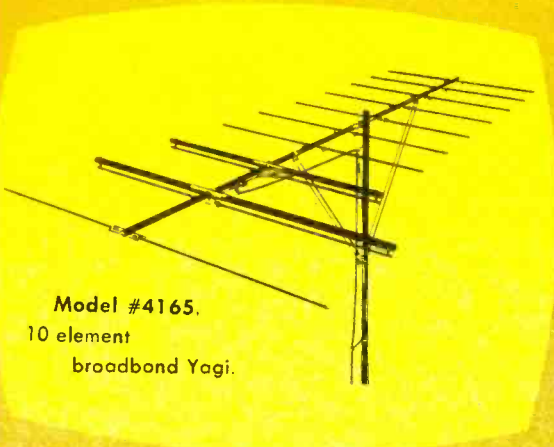Featuring the new  
**WALSCO "Octopus"**  
**Model #4110.**  
 A combination  
 Yagi-conical for  
 superlative all-channel  
 reception.



**Model #4165.**  
 10 element  
 broadband Yagi.

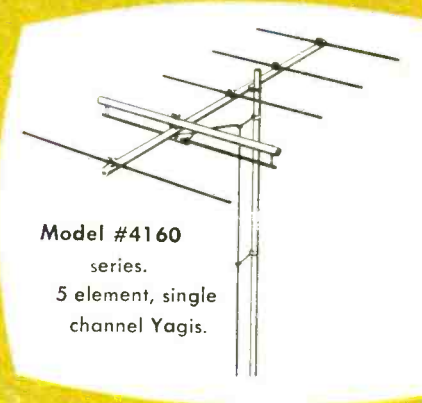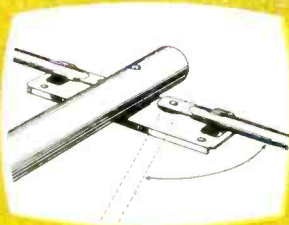Walsco's exclusive  
 "umbrella" snap-out  
 design provides perfect  
 element alignment  
 instantly.



**Model #4160**  
 series.  
 5 element, single  
 channel Yagis.


# WALSCO

## "futurized"

### YAGIS

### reach

### everywhere

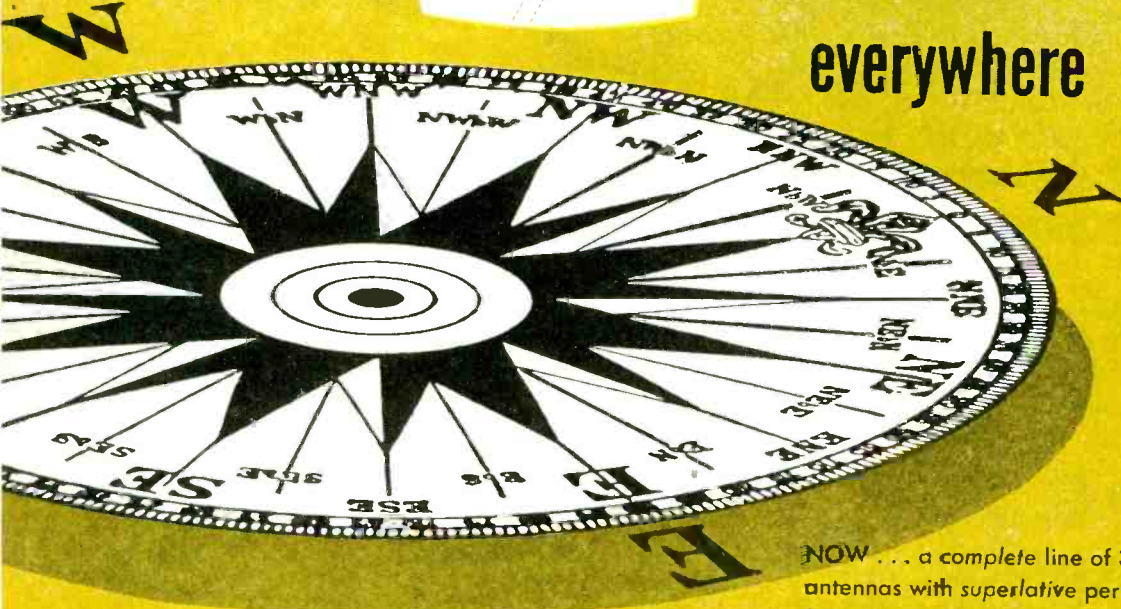

NOW . . . a complete line of 32 "futurized" Yagi antennas with superlative performance . . . for fringe and ultra-fringe areas; for black and white and color on all present and future channels. No loose hardware . . . completely pre-assembled using Walsco's exclusive "umbrella" snap-out design. Nothing compares at any price!

Write for complete information  
 on all 32 "futurized" Yagi models




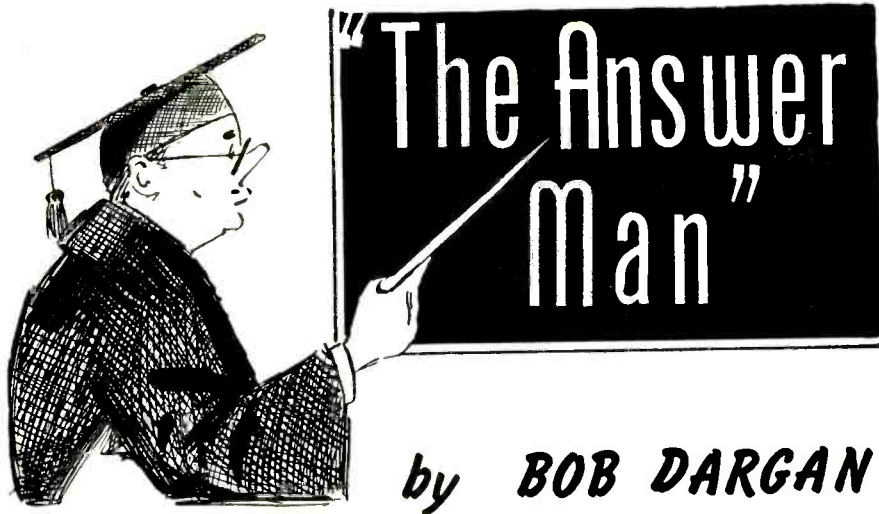**ELECTRONICS CORPORATION**

3602 Crenshaw Blvd. • Los Angeles 16, California

Overseas Distributor:  
 AG Auriema, Inc. • 89 Broad St., New York 4, N.Y.





Do you have a vexing problem on the repair of some radio or TV set? If so, send it in to the Answer Man, care of this magazine. All inquiries acknowledged and answered.

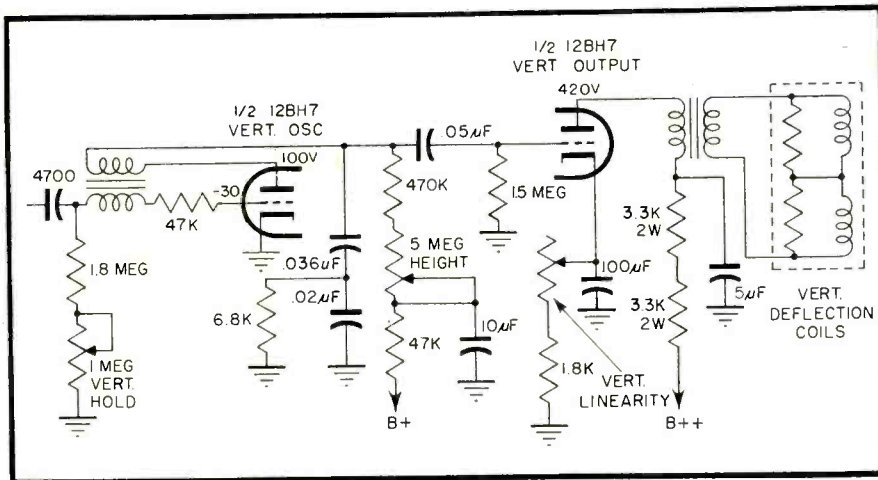


Fig. 1 — Vertical deflection section of the CBS-Columbia Chassis 750-3.

### CBS Columbia Ch. 750-3— Height Shrinks

Dear Mr. Answerman:

I have encountered on several occasions vertical deflection troubles that have caused me considerable difficulty in locating. The present case I have in mind, a CBS-Columbia chassis 750-3, is a problem where the height shrinks after a period of about ten to fifteen minutes. The shrinkage amounts to about one inch on the top and bottom and occurs very slowly.

What do you suggest as a recommended procedure in servicing this type of deflection trouble?

N.E.  
New Haven, Conn.

Naturally the first step is to substitute the tubes concerned, the vertical oscillator and output tubes. In this receiver

these functions are combined into one envelope and the tube is the 12BH7 dual triode. The circuit for the CBS-Colum-

bia 750-3 chassis is shown in Fig. 1. After checking the tubes a record should be made of the vertical oscillator grid and plate voltages as well as the vertical output grid and plate voltages. These should be taken under the two conditions, normal operation and when the picture shrinks. If a marked change occurs it usually is an indication of which stage the trouble will be located in.

At the same time a scope can be placed at the grid of the vertical output tube and the peak to peak voltage measured when the deflection is normal. After the height shrinks any change in waveform shape or amplitude can be noted for this input grid circuit.

If the waveform changes at the grid of the output tube it is fair to assume that the trouble is in the vertical oscillator circuit. Since there is no change in the vertical oscillator frequency, the change in waveform is probably due to a change in B voltage supplied to the circuit. The 470K resistor, the height control and the 47K resistor feeding the B voltage should be checked while hot after the shrinkage occurs. With the receiver switched off the resistors can be measured immediately to see if they have increased from their normal value.

There are other components that can cause this type of trouble in the circuit. If the .036 μf charging condenser develops a leak as the circuit warms up the waveform at the grid will be reduced in amplitude and the shrinkage will result.

Consider now that the grid waveform remains constant when the shrinkage occurs. If the scope is connected to the plate of the vertical output stage the waveform at this point will probably shrink in amplitude along with the height of the picture. Another check that can be made at this point is the peak to peak voltage at the plate of the

[Continued on page 52]

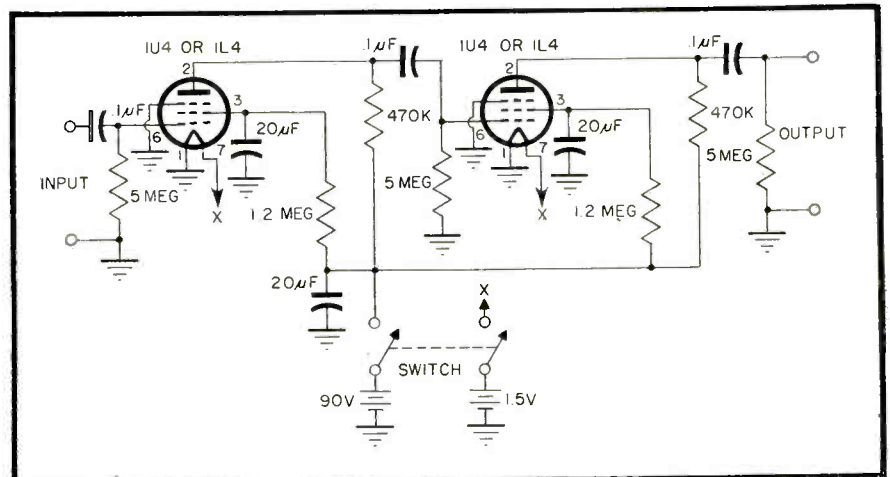


Fig. 2—Schematic for battery operated scope pre-amplifier.

# Key Test Points

by **Steve Travis**

*Methods of systematic stage isolation and defective component pinpointing as applied to TV deflection, vertical and horizontal oscillator systems.*

## The Deflection System

The picture and raster is impressed on the tube by deflecting the beam from the electron gun both vertically and horizontally. It therefore requires two deflection systems to accomplish this. The vertical deflection system uses a 60 cycle oscillator which moves the electron beam slowly down the picture tube face at this frequency rate. The horizontal oscillator develops a sawtooth of voltage which causes the beam to be deflected horizontally at 15,750 cycles per second. Both oscillators are locked in with the station sync signals.

The deflection system is the section in a TV receiver that generally requires more servicing than any other section. This is due primarily to the high voltages and circuit complexities found in

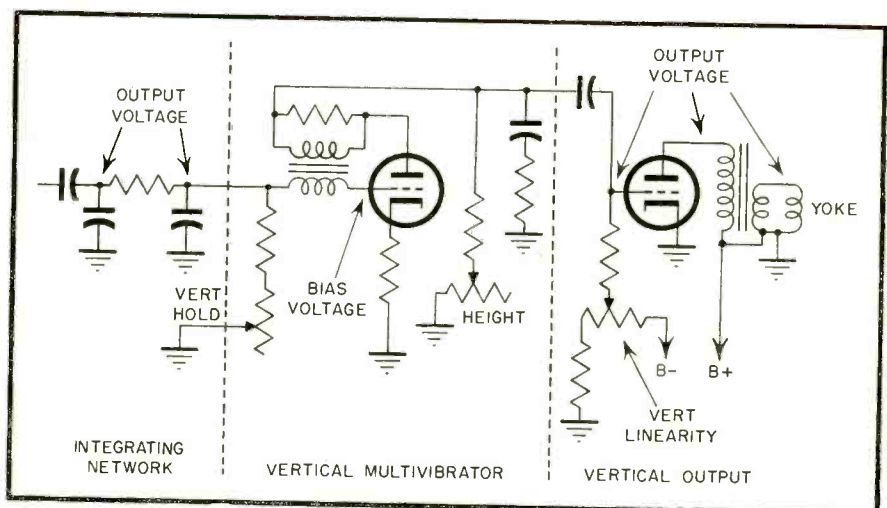


Fig. 1—Vertical blocking oscillator and conventional output stages.

the deflection system. However, it is only necessary to observe ordinary troubleshooting procedures to properly service the deflection section, as for that

matter any other sections. The difficulty is isolated first in its section, then to a particular stage of that section, and finally to the defective component.

## The Vertical Oscillator

In troubleshooting the vertical oscillator the technician is concerned with the same approach as servicing other oscillator circuits. The key test point is the grid of the oscillator tube. Here the negative grid voltage is the key test point. As explained previously, whether the oscillator circuit is of the multivibrator or blocking type, if the stage is operating as it should a negative voltage will be generated at the grid circuit a negative voltage. See Fig. 1. If the oscillator is operating, a negative grid voltage will be present. The important point is that the negative voltage is generated in the normal development of the oscillator frequency, and therefore indicates that is the oscillator operating whether of the blocking or multivibrator type. These two generally


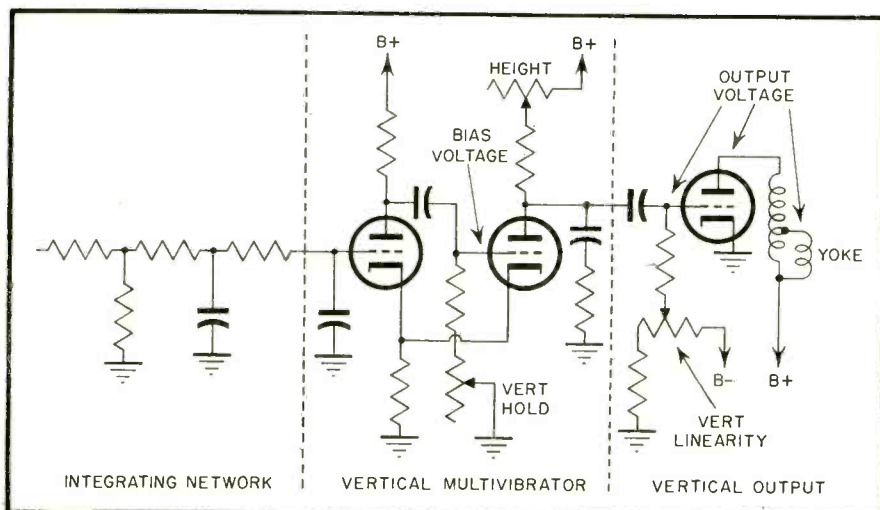


Fig. 2—Vertical multivibrator and autotransformer output stage.

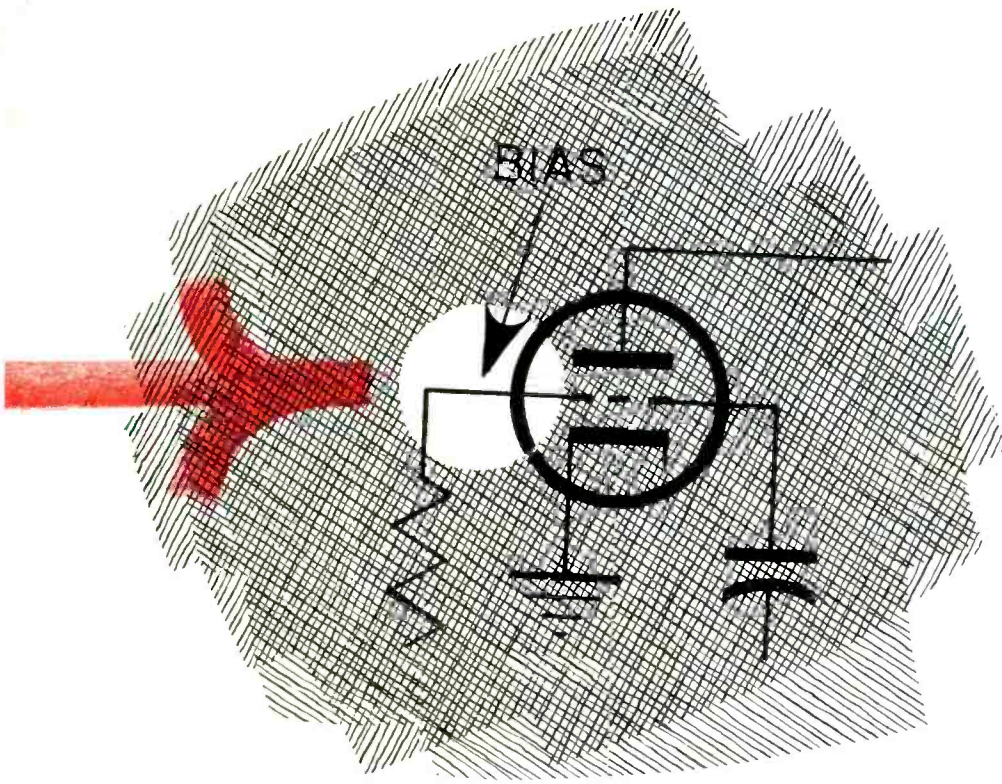



used vertical deflection systems are shown in Figs. 1 and 2.

A method of trouble shooting the vertical deflection system is to connect the vertical stages through a .1 uf condenser to the top of the volume control and use the speaker as an indication of whether the oscillator signal is being developed and being passed through the different stages to the vertical deflection yoke. The vertical buzz will be heard from the speaker as the condenser is connected to the different stages of the Vertical system indicating that the signal is present at those locations. In this manner the signal can be traced from the oscillator to the deflection yoke. Varying the vertical hold

control should change the pitch of the buzz from the speaker confirming that vertical deflection pulses are being heard. Of course, the voltage observed on an output meter can be used as an indication of the presence of vertical oscillator pulses in the vertical oscillator or output sections, as in Fig. 1 and 2.

### The Horizontal Deflection System

The horizontal section can also use either a multivibrator or blocking type of oscillator to produce horizontal deflection. The developed sawtooth of voltage from the oscillator is coupled to the horizontal output section where it is changed to a current sawtooth and applied to the horizontal deflection yoke to magnetically deflect the electron beam.

In each stage of the horizontal deflection system check points exist which can be quickly used to isolate the difficulty to a particular stage. Once the stage has been isolated, voltage and resistance checks will locate the defective component.

### The Horizontal Oscillator

The grid bias at the horizontal block-

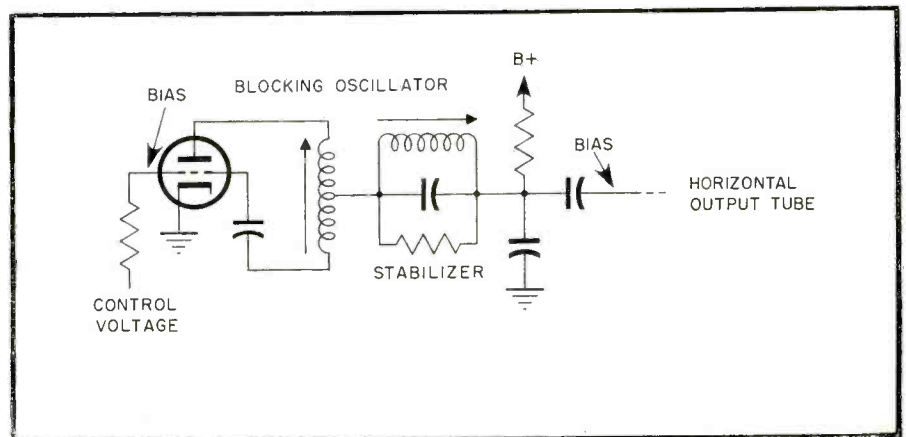


Fig. 3—Horizontal blocking oscillator circuit indicating key test points.

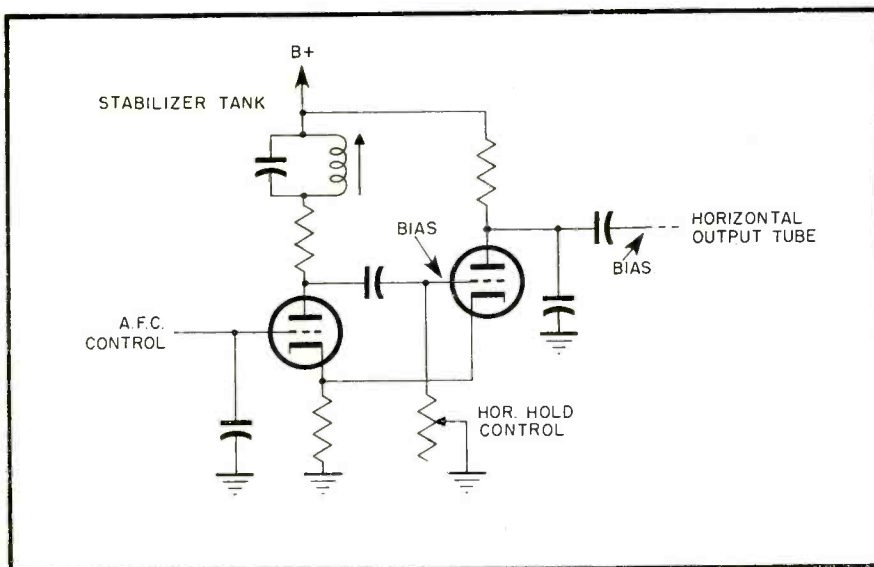


Fig. 4—Horizontal multivibrator circuit indicating key test points.

ing oscillator or multivibrator is a definite check as to whether the horizontal oscillator is functioning. At the grid of the oscillator a negative bias of 30 volts or more indicates that the oscillator is working. This voltage depends upon the type of circuit and can be as high as 70 volts in a horizontal blocking oscillator. As with other types of oscillator circuits the only way the negative voltage can appear at the grid of the oscillator tube is for the circuit to be developing oscillations. Therefore this test point is an excellent, quick check on the circuit. The numerical value of the negative voltage is not important. It is the presence of the negative voltage that indicates that the circuit is functioning. Two generally used horizontal oscillator circuit are shown in Fig. 3 and 4.

[To be continued]

# RC CIRCUITS

by Cyrus Glickstein

This fifth installment discusses the functional characteristics of complex RC circuits with series parallel elements, and their application to TV sync circuits.

**W**E have previously analyzed complex RC circuits with one condenser and two resistors. We will now find that complex RC circuits with two condensers, one series and one parallel, have some unsuspected behavior quirks.

## Basic Action of Series Condensers

As an introduction to these circuits, let's review the action of two condensers in series across a battery, Fig. 23. When the switch is closed, current flows only for an instant. The condensers charge up immediately and current flow stops. The voltages across the condensers add up to the battery voltage, since the battery voltage divides across the two condensers in *inverse* proportion to capacity. That is, there is less voltage across the larger condenser. For example, if  $C_1$  is  $.1 \mu f$  and  $C_2$  is half the size— $.05 \mu f$ —in Fig. 23, then the battery voltage (180V) divides inversely across the two condensers—60V across  $C_1$  ( $.1 \mu f$ ) and double the voltage, or 120 V across  $C_2$  ( $.05 \mu f$ ).

## Series-Parallel Circuit Action

When the switch is closed in the series-parallel circuit with two condensers shown in Fig. 24a, the battery voltage instantaneously divides across the two condensers in inverse ratio to their capacity, just as in the previous case. At this first instant,  $R_1$  has no effect on the action. However, immediately after this first surge,  $R_1$  provides a *discharge* path for parallel condenser  $C_1$  while series condenser  $C_2$  continues to *charge*.  $C_1$  discharges to zero through  $R_1$  while  $C_2$ , the series condenser, charges to battery voltage through  $R_1$ . Arrowheads show the direction of current flow in Fig. 24a. The curves illustrating the voltages across each condenser are shown in Fig. 24b and c.

Time constant for  $C_2$  is defined as the time it takes this condenser to charge to 63% of the *exponential portion* of the curve (Fig. 24c), disregarding the initial surge. That is, after the first instantaneous charge,  $C_2$  then charges in the usual exponential way

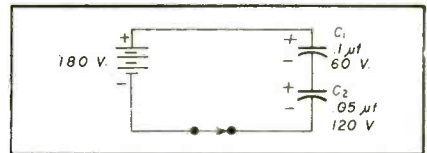


Fig. 23 — Two condensers across a battery divide the voltage in inverse ratio to capacity.

from 120 v to 180 v. For  $C_1$ , time constant is the time it takes  $C_1$  to discharge to 37% of the initial surge voltage. Since the circuit has one overall time constant, both events take place at the same instant.

Whether a condenser charges or discharges, the *current* through the circuit decreases. The current curve in either case is an exponential curve of decay. Therefore, the decreasing current through  $R_1$  divides—part goes to  $C_1$  which is discharging and part goes to  $C_2$  which is charging, Fig. 24a. This has exactly the same effect on the time constant of the circuit as if both condensers are in parallel and charging through  $R_1$ , as shown in the equivalent circuit, Fig. 24d. In the equivalent circuit, the decreasing current through  $R_1$  also divides between the two condensers.

Effectively, the two condensers are in *parallel* and the time constant of the entire circuit of Fig. 24a (or 24d) is:

$$T = (C_1 + C_2) \times R$$

$$= (.05 \mu f + .1 \mu f) \times 20,000$$

$$= .15 \times 10^{-6} \times 20,000 = 3,000 \text{ usec}$$

The fact that the two condensers in Fig. 24a divide the battery voltage during the first surge may seem at first glance to reduce the time constant of the circuit. This however is not the case. A simple example will clarify the situation. Assume we have a simple series RC circuit across a battery. This circuit has a certain time constant based on the value of  $R$  and  $C$ . Now before the switch is closed, another condenser of *equal* value is placed across the resistor—a circuit similar to Fig. 24a. When the switch is closed, the series condenser  $C_2$  instantaneously charges to *half* the voltage, then more slowly charges to the other half of the voltage. Current for the initial, instantaneous charge of the two condensers does not flow through the resistor at all, but through the condensers only. Therefore, series condenser  $C_2$  has to charge slowly *through the resistor* to only one-half the amount of voltage as compared to a simple series circuit. However, in this series-parallel circuit, initial current through the resistor, after the first surge, is also one-half compared to the initial current in a simple series circuit. This is true since only one-half the source voltage appears across  $C_1$ , which is in parallel with  $R_1$ . Note that

[Continued on page 57]

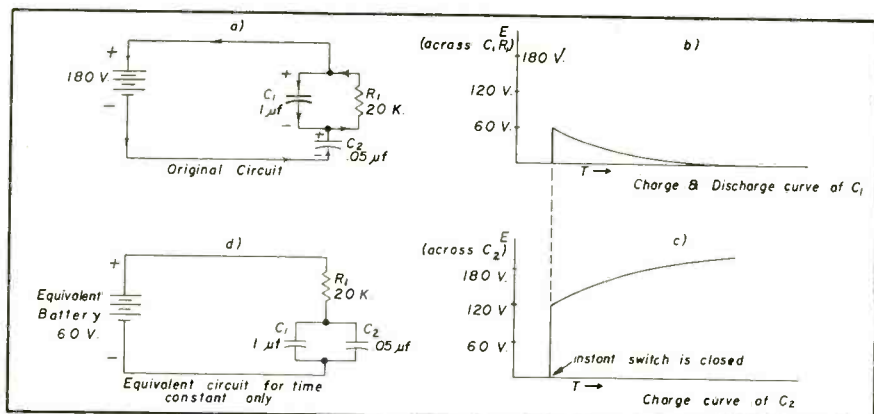


Fig. 24—Charging action which takes place in series parallel circuits. Parallel RC in series with C.



# Simpson


MODEL

## 260

MULTI-TESTER

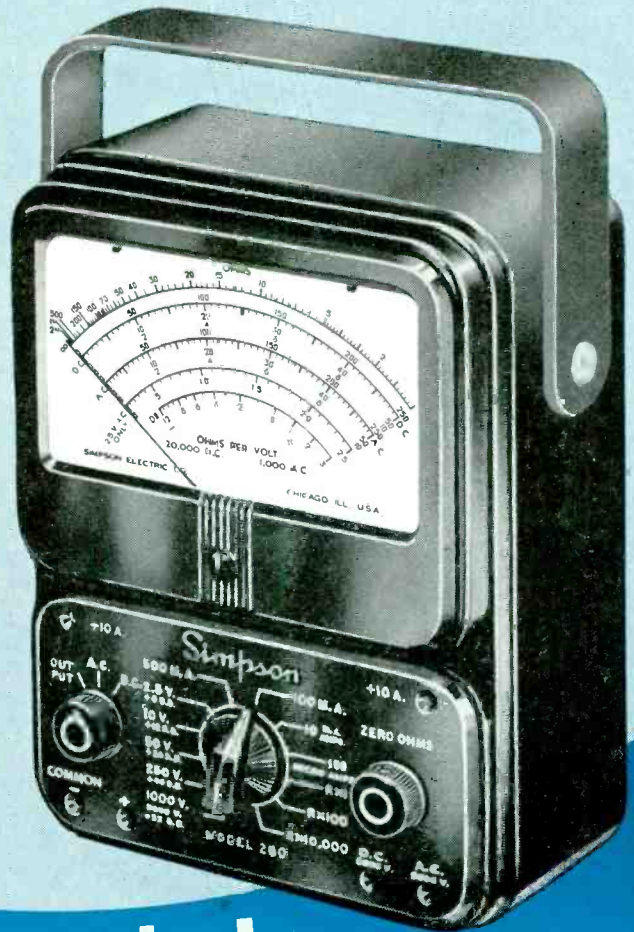**outsells all others combined!**

More technicians are using the Model 260 than any other high-sensitivity VOM. Over half a million Model 260's have been sold to date! 20,000 Ohms per volt. You'll find it wherever quick, accurate, electrical checks are needed. It's so handy, so dependable, so sensibly priced. Ask your jobber to show you the Simpson Model 260. Only **\$38.95**, including Adjust-A-Vue Handle. Carrying cases from **\$6.75**.



**world's most popular!**

MODEL

## 262

**the new vom with a 7" meter**

20,000 Ohms per volt DC. 5,000 Ohms per volt AC. 33 RANGES

DC VOLTAGE: 0-1.6, 0-8, 0-40, 0-160, 0-400, 0-1600, 0-4000 volts (20,000 ohms per volt sensitivity)

AC VOLTAGE: 0-3, 0-8, 0-40, 0-160, 0-800 volts (5,000 ohms per volt sensitivity)

AF OUTPUT VOLTAGE: 0-3, 0-8, 0-40, 0-160 volts (0.1 microfarad internal series capacitor)

VOLUME LEVEL IN DECIBELS: -12 to +45.5 DB in 4 ranges.

Zero DB Power Level, .001 watt in 600 ohms.

DC RESISTANCE: 0-500 ohms (4.5 ohms center); 0-5,000 ohms (45 ohms center);

0-50,000 ohms (450 ohms center); 0-500,000 ohms (4,500 ohms center);

0-5 megohms (45,000 ohms center); 0-50 megohms (450,000 ohms center)

DC CURRENT: 0-80, 0-160 microamperes, 0-1.6, 0-16, 0-160 milliamperes,

0-1.6, 0-16 amperes (267 millivolts maximum drop)

MODEL 262 complete with 2 test leads with removable alligator clips, 4,000 v. DC multiplier

Dealer's Net Price, including Adjust-A-Vue Handle. **..\$9.95**

Accessory High Voltage Probe for 16,000 volts DC. **..\$11.50,**

40,000 volts DC. **..\$12.50**



*Deluxe!*

SEE THEM AT YOUR JOBBER, OR WRITE . . .


**Simpson** ELECTRIC COMPANY

WORLD'S LARGEST MANUFACTURER OF ELECTRONIC TEST EQUIPMENT

5204 W. Kinzie St., Chicago 44, Illinois, Phone: ESTbrook 9-1121

In Canada: Bach-Simpson, Ltd., London, Ontario

# FOR GREATER PROFITS

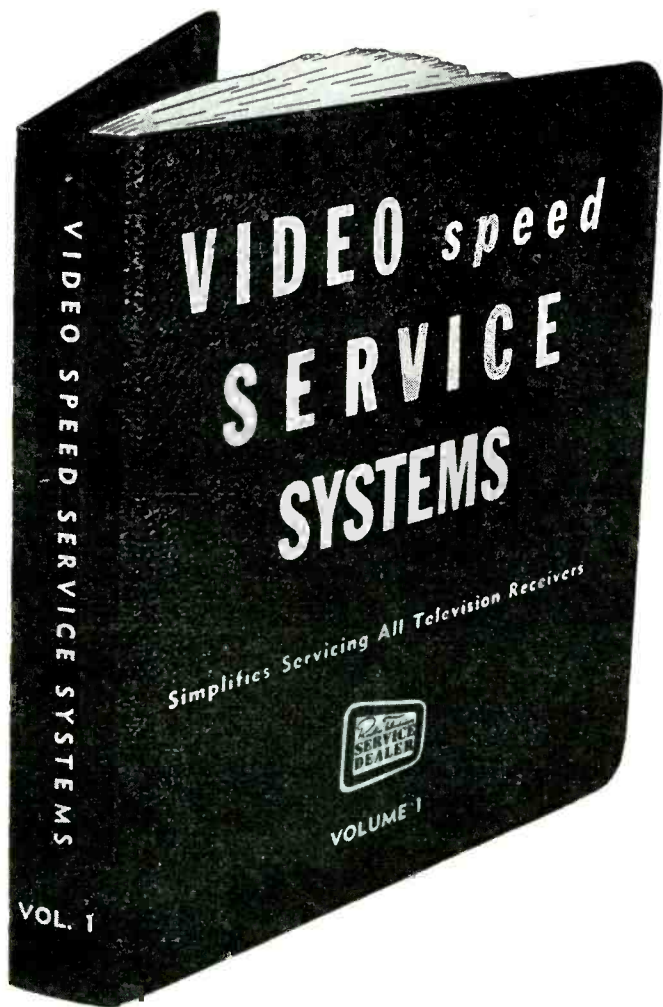

## **SPEED UP YOUR SERVICING with THIS NEW BOOK**

which shows you how to take care of and repair in the quickest possible time:

- Common troubles characteristic of certain receivers
- "Bugs" which might take you hours to find
- Factory and field service changes

**SET UP SO THAT YOU CAN MAKE THESE REPAIRS IN THE SHOP OR IN THE FIELD WITHOUT REFERENCE TO ANY OTHER SOURCE**

Contains over 600 Service Items representing over 1000 of the most-serviced Television models now in use. Over 25 different manufacturers' lines are covered.

**\$4.95**

postpaid  
(Add 3% Sales Tax in New York City)

**DISTRIBUTORS—ORDER YOUR SUPPLY NOW!**

Service Dealers—get your copy of VSSS from your Distributor. If he can't supply you, order direct by mail from us.

Video Speed Servicing Systems IS **GUARANTEED** to Simplify Servicing All TV sets. A number of new Data Items are published in every issue of "Radio-Television Service Dealer" as a regular monthly feature.

**TEAR OFF AND MAIL NOW**

**RADIO-TELEVISION SERVICE DEALER**

67 West 44th Street, New York 36, N. Y.

Please send me post-paid VIDEO SPEED SERVICING SYSTEMS Volume 1. Enclosed herewith is

my  check  money order for \$\_\_\_\_\_ for \_\_\_\_\_ copies at \$4.95 each. (Add 3% Sales Tax in New York City)

Name .....

Address .....

City ..... Zone ..... State .....



# WAR DECLARED ON DEALER CALL-BACKS!



## NEW TUBE TYPES FROM SYLVANIA SPEARHEAD ATTACK!

The most important step in a concentrated campaign to eliminate dealer call-backs has been taken by Sylvania with the release of a group of new tube types. Sylvania's new 5U4GB leads the group.

The 5U4GB attacks the call-back enemy on many different fronts:

1. The tube has been re-designed. Now, plates are longer and heavier with twin wings for better heat dissipation, Sylvania's 5U4GB carries increased ratings of 275 ma at 44 volts drop with 1.0 amp peak plate current.
2. Wafer Stem Construction—originally developed by Sylvania for the lock-in tube—has been adapted to the 5U4GB. The wafer stem eliminates electrolysis, provides stronger mount construction, permits better spacing.
3. A new T-12 bulb provides greater heat dissipation, gives added strength, more rigidity because of its straight construction.
4. Bottom mica has been added to make the tube stronger, improve filament alignment and eliminate arcing.

Other Sylvania types are vastly improved, too! All have Sylvania's famous wafer stem construction, plus these additional design features:

- Better Lead Spacing
- Stronger Mount Supports
- Stronger Micas
- Firmer Filament and Plates
- Greater Protection Against Shock and Vibration
- Better Heat Dissipation
- Low Glass Electrolysis
- Fewer Burnouts
- Stronger, More Rugged Overall Construction

### NO MINOR SKIRMISH

The Sylvania war on dealer call-backs is not a minor skirmish. It will continue until dealer call-backs on these and other receiving tube types are completely eliminated. The dealer's

biggest profit-robbing enemy can look forward only to an incessant, continuing effort on the part of Sylvania to make his existence a thing of the past. These quality tubes are now at your Sylvania distributor's.

**TO IDENTIFY SYLVANIA'S NEW RECEIVING TUBES LOOK FOR THE NEW CARTON!**



# SYLVANIA

Sylvania Electric Products Inc. 1740 Broadway, New York 19, N. Y.

In Canada: Sylvania Electric (Canada) Ltd., University Tower Bldg., St. Catherine Street, Montreal, P. Q.

**LIGHTING • RADIO • ELECTRONICS • TELEVISION**

This new tube carton identifies Sylvania's new high quality, improved receiving tubes. It's assurance to dealers everywhere that inside is one of the finest receiving tubes made—unsurpassed for quality and performance. For further information write to Dept. 4R-3910 at Sylvania.

THIS installment is devoted to three sync amplifier problems. The use of the oscilloscope is extremely important in hunting down these faults. Equally important is the manufacturer's service data which usually contains the correct waveforms at the important places.

### RCA KCS82—Horizontal Pull

The receiver was turned on and immediately it was noticed that a horizontal pulling condition took place at the top of the raster. The picture could not be straightened out. The top of the picture would either pull to the right or the left.

A check was then made to see if there was any hum in the picture. Hum in the picture is a well known cause of horizontal pulling. Two black bars in the picture is indicative of 120 cycle hum. This is caused by a bad filtering condition in the "B" supply. One black bar in the picture is the result of 60 cycle hum. This is caused usually by cathode to filament leakage in one of the video or rf tubes. If the cathode of a tube is grounded the hum leakage is also grounded. Thus, a cathode-grounded tube usually will not be the cause of this type of trouble.

In this case there was no hum in the picture; however, another symptom was observed: The contrast could not be lowered to a point that could be considered normal. It was therefore supposed that a slight case of age trouble was also present.

Checking the tubes, all the video *if* and *rf* amplifiers were replaced individually but with no effect. Next, all sync tubes (V109, V111, V112) were replaced individually but with no effect. The horizontal oscillator (V114) was also replaced but also without effect.

At this point the manufacturer's service notes were consulted. Immediately it was seen that the cathode voltage of the horizontal sync separator, V111B, was being fed to the *agc* amplifier, V111A. Here was a possible trouble spot.

The scope was next set up to view horizontal pulses, and a waveform check was made at pin #7, grid of V111B. This waveform checked okay against the service data. (Ref. to Fig. 1A.) Next, a waveform check was made at pin #6 of V111B. (Ref. to Fig. 1B.) Here it was obvious that there was something wrong. The horizontal sync pulse was not being amplified. The purpose of V111B is to amplify the horizontal sync pulse and also separate this pulse from the video and blanking information. This is accomplished by biasing the cathode at 70 volts positive with respect to grid. This tube will then only conduct on the horizontal sync pulses.

# The Work Bench

by PAUL GOLDBERG

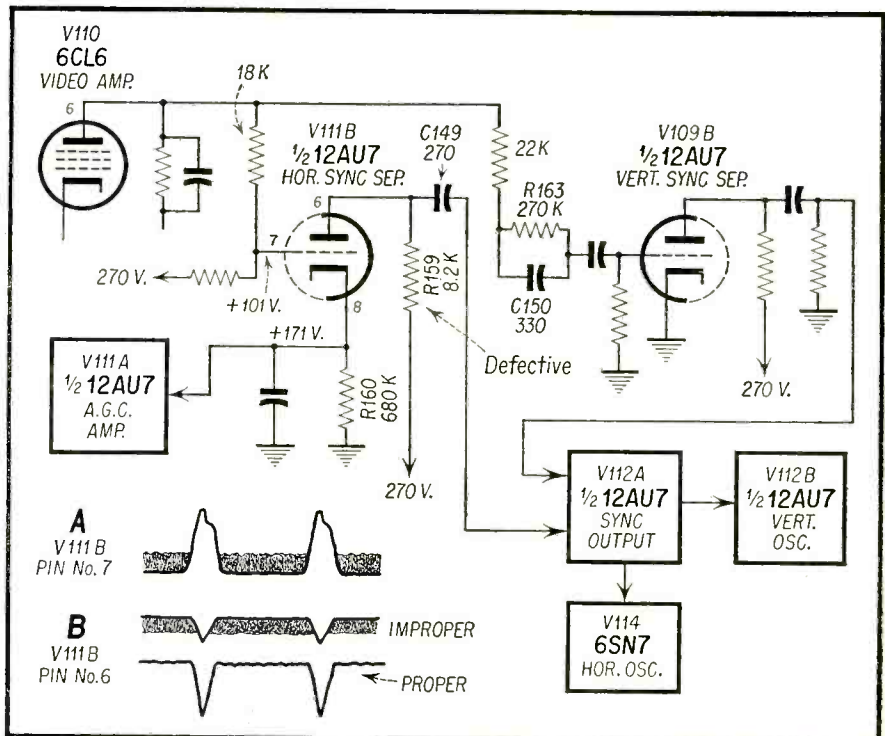


Fig. 1 — Partial schematic, RCA KCS82.


Knowing these facts, a voltage check was attempted at pin #6 of V111B. But before doing so, it was noticed that R159, 8.2K, the plate load resistor, was severely burned. Seeing this, a resistance measurement was taken and it was found to measure only 125 ohms. The resistor was then replaced. Because no reason could be found for R159 burning up, V111, 12AU7 was replaced as the only possible cause. The receiver now functioned properly.

### Emerson Chassis 120162A—Horizontal Pull and Vertical Roll

The receiver was turned on and it immediately started to pull horizontally and roll vertically. This was evidently both a horizontal and vertical sync

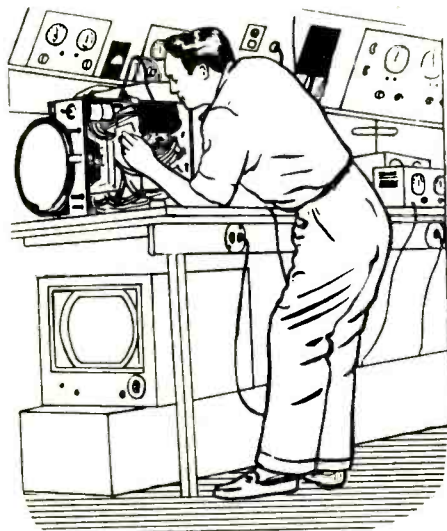problem. V11B, 1/2 12AU7, was the only composite sync amplifier. Thus V11 was immediately replaced but without effect. A search was then made for hum in the picture but there was none. V12 was next replaced but without effect. The oscilloscope was then set up and a waveform was taken at pin #7 of V11B. This waveform checked correctly with the manufacturer's data. (Fig. 2A). A waveform was then taken at pin #2 of V12A. This waveform seemed also to check correctly. (Ref. to Fig. 3B). A waveform was then taken at pin #7 of V12B and here was the trouble. (Ref. to Fig. 2C). A study of the sync circuitry was made. The composite sync pulses enter V11B and are amplified. After being amplified the





This Month:

# SYNC AMPLIFIER PROBLEMS

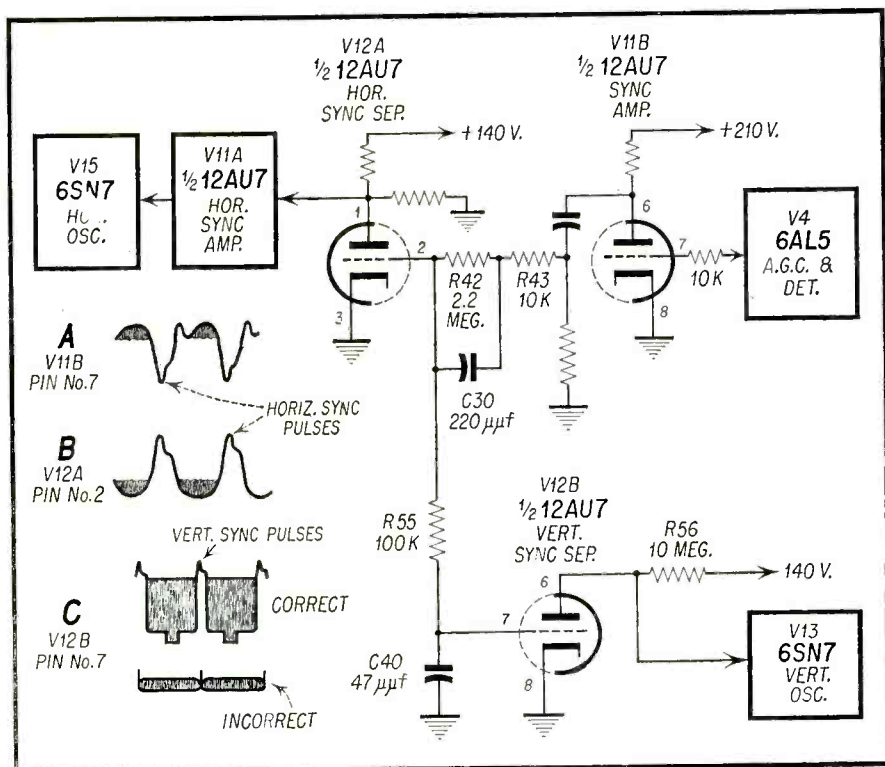


Fig 2. — Partial schematic, Emerson 120162-A.

composite sync signal enters a network (R42, 2.2 meg and C30, 220 mmf) at pin #2 of V12A. This network has an excellent horizontal sync pulse to noise ratio. However, it attenuates the vertical sync pulses. To improve on this situation a low pass filter (R55, 100K and C40, 47 mmf) is employed which increases the vertical sync pulse to noise ratio at pin #7 of V12B. Thus, due to these networks, only the horizontal sync pulses will be amplified by V12A, and only the vertical sync pulses will be amplified by V12B. To get back to the trouble now and referring to the incorrect waveform in Fig. 2C, it is evident that very little vertical sync pulse was getting to the grid of V12B. A resistance measurement was then made from

Pin #7 of V12B to ground. The meter read about 500K. C40, 47 mmf, was next clipped from the grid, pin #7, and measured. It measured about 750K ohms leakage. C40 was then replaced with a new condenser and the receiver functioned properly.

Because C40 was leaking, horizontal as well as vertical sync pulses were being amplified by both V12A and V12B. C40, normally would kill all horizontal sync pulses arriving at pin #7 of V12B. Moreover, the vertical sync pulses no longer had the easy path of R55 and C40 and so they divided themselves between the grids of V12A and V12B. Thus, the diminished vertical sync pulse caused the intermittent vertical roll and the vertical sync pulse being

allowed to trigger the horizontal oscillator caused the horizontal pulling.

## Motorola TS114—Intermittent Horizontal Pulling and Vertical Jitter

The receiver was turned on and it was observed after a time that the horizontal began to pull intermittently and that the vertical had a bad jitter. Inasmuch as there was no sign of age trouble, we decided to check the clipper circuits. V12, the clipper, was replaced but had no effect. Next the scope was set up and a waveform check was made at Pin #1 of V12A, the first clipper. The waveform however checked correctly with the manufacturer's service data. (Ref. to Fig. 3A.) A waveform check was next taken at Pin #2 of V12A. Here the waveform was not correct. (Ref. to Fig. 3B.) The purpose of V12A, the first clipper is to remove the blanking end video information and

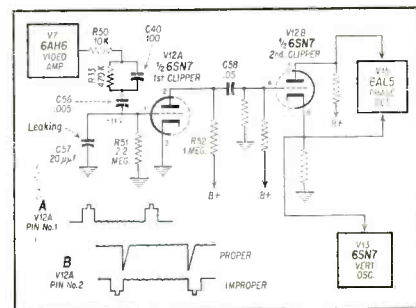



Fig. 3 — Partial schematic, Motorola TS114.

amplify only the sync pulses. C57 and R51 form the cutoff grid leak bias for V12A. Because of this grid leak action, V12A will only conduct on the sync pulses thus eliminating the blanking and video information. Now the waveform taken at Pin #2 of V12A, you will notice, contains all the video and blanking information. This should not be. Refer to Fig. 3B and the correct and incorrect waveforms can be seen.

[Continued on page 56]

# BUSS..
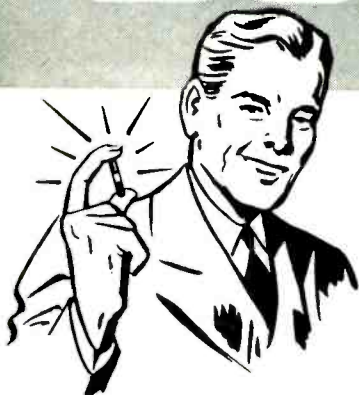
## ONE SOURCE TO MEET ALL YOUR FUSE NEEDS!...



Constant research and engineering over the past 39 years have resulted in a most complete line of BUSS fuses: dual-element (slow blowing), renewable and one time types . . . in any size from 1/500 amperes up — plus a companion line of fuse clips, blocks and holders.



To make sure that BUSS fuses meet the highest standards of dependability . . . every BUSS fuse normally used by the Electronic Industries is tested in a sensitive electronic device that automatically rejects faulty fuses.

Many manufacturers and service organizations have standardized on BUSS fuses to simplify their buying, stock handling and records — and to safeguard their good-will and reputation. You too, will find it good business to let BUSS meet all your fuse needs.

**BUSS is the PROFIT brand  
because it is the KNOWN brand.**

BUSS fuses have ready customer acceptance. The millions and millions of fuse installations for home, farm and industry have firmly established the dependability and unquestioned high quality of BUSS fuses. And BUSS fuses stay sold because your customers stay satisfied.

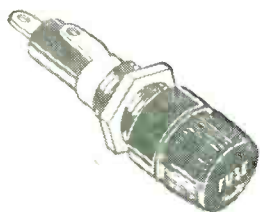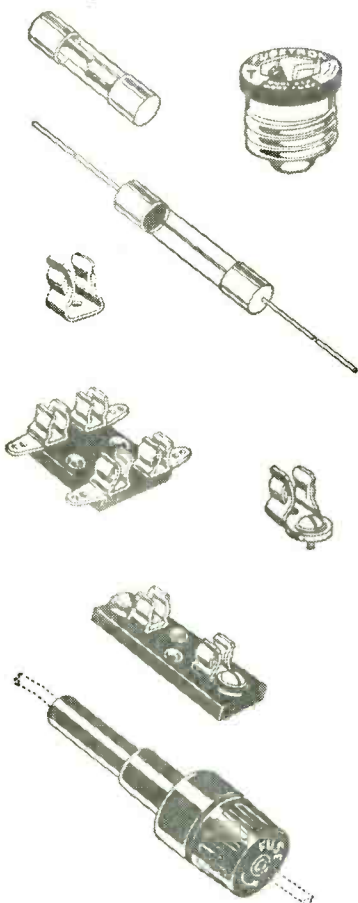*Makers of a complete line of fuses for home, farm, commercial, electronic and industrial use.*



**FOR MORE INFORMATION  
MAIL THIS COUPON**

BUSSMANN Mfg. Co. (Div. McGraw Electric Co.)  
University at Jefferson, St. Louis 7, Mo. SD-1054  
Please send me bulletin SFB containing facts on BUSS  
small dimension fuses and fuse holders.

Name.....Title.....  
Company.....  
Address.....  
City & Zone.....State..... 1054



# FIRESTONE

Models 13-G-128, -129, -130, -132, -145, -146,  
Codes 334-3-MS39A, 334-3-M39B

## TUBE LIST

| SYMBOL     | TYPE         | CIRCUIT FUNCTION                         |
|------------|--------------|--|
| VHF Tuner  | 6J6          | R-F Osc., Mixer                          |
| *VHF Tuner | 6BQ7         | R-F Amp.                                 |
| UHF Tuner  | 6AF4         | R-F Osc.                                 |
| Tuner      | 1N72 or 1N82 | Crystal Mixer                            |
| V-1        | 6CB6         | 1st I-F Amp.                             |
| V-2        | 6CB6         | 2nd I-F Amp.                             |
| V-3        | 6CB6         | 3rd I-F Amp.                             |
| V-4        | 6AL5         | Det., DC Restorer                        |
| A & B      |              |  |
| V-5        | 12AT7        | 1st Video Amp., Phase Splitter           |
| A & B      |              |  |
| V-6        | 6AH6         | Video Output                             |
| V-7        | 6BE6         | Sync. Separator                          |
| V-8        | 6SN7-GTA     | Vert. Osc. & Vert. Output                |
| V-9        | 6AU6         | Automatic Gain Cont.                     |
| V-10       | 6AU6         | 1st Audio I-F                            |
| V-11       | 6AU6         | 2nd Audio I-F                            |
| V-12       | 6AL5         | Ratio Detector                           |
| V-13       | 6AV6         | 1st Audio Amp.                           |
| V-14       | 6AQ5         | Audio Output                             |
| V-15       | 6AL5         | Phase Detector                           |
| V-16       | 6SN7-GTA     | Hor. Oscillator                          |
| V-17       | 6BQ6-GT      | Hor. Output                              |
| V-18       | 6AX4-GT      | Damper                                   |
| V-19       | 1B3-GT       | H.V. Rect.                               |
| V-20       | 5U4-G        | L.V. Rect.                               |
| & V-22     |              |  |
| V-21       | 21MP4        | Pix Tube 21" Metal Rect. (Electrostatic) |



\* For replacement purposes a 6BZ7 tube may be used in place of a 6BQ7.

## KEY VOLTAGES


|  |               |
|--|---------------|
| B+, plate of damper, V18 pin 5         | 300 VDC       |
| Boosted B+, cath. of damper, V18 pin 3 | 520 "         |
| Plate of Vert. Osc., V8 pin 2          | 75 to 200* "  |
| Plate of Vert. Out., V8 pin 5          | 500 "         |
| Plates of Hor. Osc., V16 pin 2         | 175 to 200* " |
| pin 5                                  | 260 "         |
| Grid of Hor. Out., V17 pin 5           | -26 to -35 "  |

\* Voltage is a function of control settings.

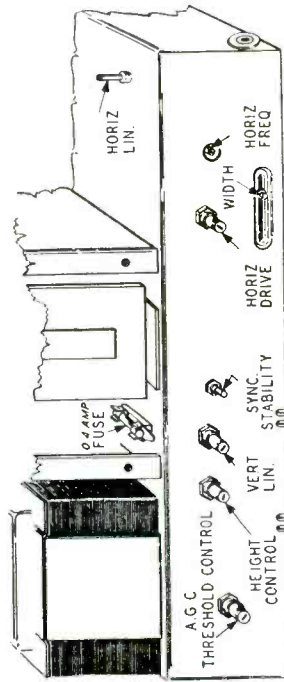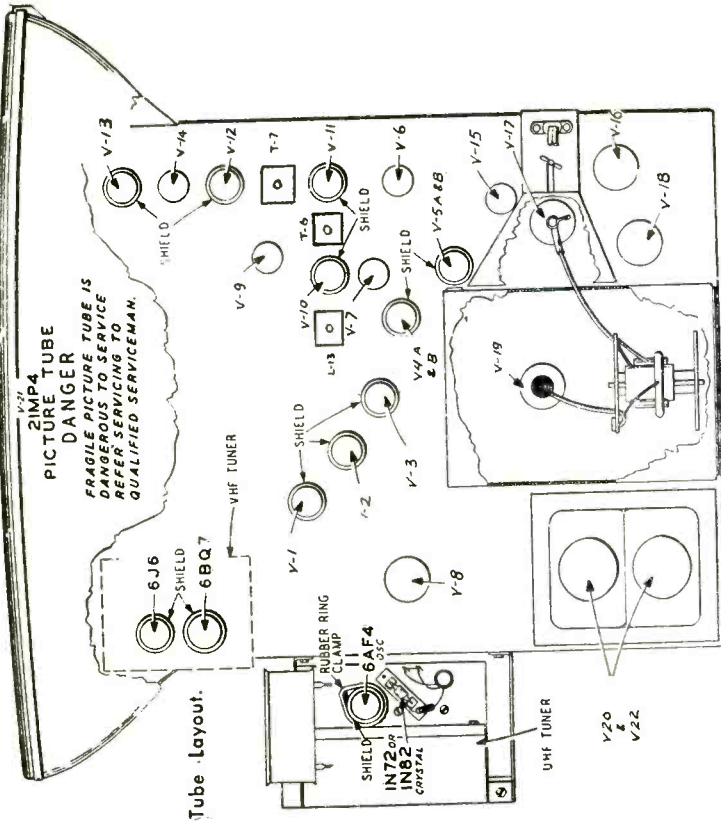All voltages are measured with a VTVM connected between the tube pins and chassis.



## Adjustments Rear of Chassis

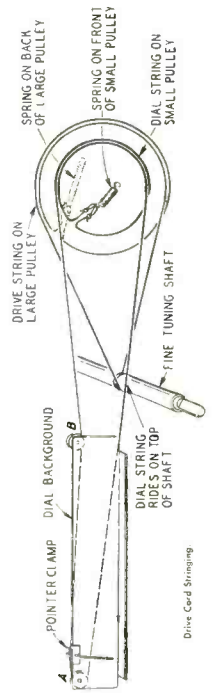

Dial Stringing

## ADJUSTMENTS

**WIDTH, DRIVE AND LINEARITY ADJUSTMENTS**

While receiving a signal from a station (with picture locked in sync) turn contrast control fully counter-clockwise, turn the brightness control up so that the picture appears washed out. Adjust width control until the picture fills the mask. Turn the horizontal drive control clockwise until white bars appear in the left center portion of the raster, then turn counter-clockwise until the white bars just disappear. This adjustment will allow the horizontal system to operate at maximum efficiency. Adjust horizontal linearity control for best linearity. If adjustment of the horizontal drive or horizontal linearity is required, it usually will be necessary to recheck the horizontal oscillator alignment. If adjustment of the horizontal linearity control is required, readjustment of the horizontal drive control will be necessary. Adjust the picture centering device to align the picture with the mask.

**CENTERING ADJUSTMENT**

If horizontal or vertical centering is required, adjust each ring in the centering device until proper centering is obtained. If a clamp type centering device is used, rotate the device to the left or right and turn the knob located at the top of the device until the picture is centered correctly.

**ADJUSTMENT OF AGC THRESHOLD CONTROL**

Tune the receiver to the strongest station in the area in which the receiver will be used. While observing the picture and listening to the sound, turn the control clockwise until signs of overloading (buzz in sound, washed-out picture) appear. Then turn the control a few degrees counter-clockwise from the point at which overloading occurs. (The stronger the signal input, the more counter-clockwise this setting will be.) In areas where the strongest signal does not exceed 10,000 uv the setting will usually be maximum clockwise. With the control set correctly, the AGC will automatically adjust the bias on the R.F. and I.F. amplifiers so that the best possible signal to noise ratio (Minimum snow) will be obtained for any signal input to the receiver.

**ADJUSTMENT OF SYNC STABILITY CONTROL**

When receiving strong (500 MV or more) signals, set hold controls so that the picture is locked in. Turn the sync control slowly clockwise until bending occurs at top of picture. Then turn the control a few degrees counter-clockwise until bending disappears. If the control is set incorrectly bending, tearing, etc., will be present and when switching from channel to channel the picture will not lock in quickly. In weak signal areas the control should be set for maximum picture stability. In general the weaker the signal the more clockwise the control should be turned.

When the sync stability control is correctly adjusted the receiver will hold sync without tearing or rolling under even the most adverse noise conditions.

**CHECK OF HORIZONTAL OSCILLATOR ALIGNMENT**

Tune in a station and adjust the horizontal hold control until the picture falls into sync. Momentarily remove the signal by switching off channel and then back. The picture should pull into sync over a range of 90° rotation of the horizontal hold control. If in the above check the receiver fails to hold sync or the pull-in range is at the extreme end of the control, it will be necessary to make the following adjustment.

**HORIZONTAL FREQUENCY ADJUSTMENT**

With the horizontal hold control set to the center of its range of rotation, adjust the horizontal frequency control until the picture pulls into sync.

**ION TRAP MAGNET ADJUSTMENT**

The ion trap magnet should be positioned close to the base of the tube with the magnet of the ion trap on the side where the electron gun is nearest the glass neck of the picture tube. From this position adjust the magnet by moving it back and forth and at the same time rotating it slightly around the neck of the picture tube until the brightest raster is obtained on the picture screen. Reduce the brightness control setting until the raster is slightly above average brilliance. Readjust the ion trap magnet for maximum raster brilliance and best focus. **MAXIMUM RASTER BRILLIANCE AND BEST FOCUS OCCUR AT THE SAME POINT.** Do not sacrifice brilliance for best focus. The ion trap magnet adjustment is a very critical one especially with the electrostatic type zero focus picture tube. Consequently, great care should be taken to make sure that the ion trap magnet is correctly adjusted.

**PICTURE TUBE SAFETY GLASS**

It will be necessary to clean the picture tube safety glass and the face of the picture tube occasionally. Remove the screws and cleat. Insert your fingers into the opening at the center of the frame and carefully lift up and pull out the safety glass. Clean the safety glass and the face of the picture tube with a soft lint-free cloth dampened with water or mild soap-suds.

For models that have the cleat and screws at the top of the cabinet the following caution must be observed:  
**CAUTION—UPON REMOVAL OF THE LAST SCREW AND THE CLEAT THE GLASS MAY FALL FORWARD. SUPPORT THE GLASS WITH ONE HAND AS YOU LIFT IT GENTLY FROM THE CABINET.**

## FIRESTONE TROUBLE SHOOTING CHART

|   |   |
|---|---|
| <b>No Sound—No Raster</b><br>Power input circuit<br>V20, V22<br>Check B+ fuse F-1 (0.4 Amps)  | <b>Snow in Pix</b><br>Check Tuner tubes<br>V1, V2, V3, V4<br>AGC Threshold control<br>Antenna and transmission line   |
| <b>No Raster—Sound OK</b><br>Brightness control<br>V4, V16, V17, V18, V19, V21<br>Ion trap<br>HV xformer Hor. yoke CRT connections  | <b>Engraved Effect in Pix</b><br>Tuner fine tuning<br>Contrast and AGC Threshold controls<br>Check Tuner tubes<br>V1, V2, V3, V4, V5, V6, V21<br>Check Vid. Det. and Amp. peaking coils<br>Check 0.047 mf cap. connected to pin 1 of V6                 |
| <b>Weak Pix—Sound and Raster OK</b><br>Tuner fine tuning<br>Contrast and AGC Threshold controls<br>Check Tuner tubes<br>V1, V2, V3, V4, V5, V6  | <b>Vert. Bars</b><br>Hor. Drive control<br>V17, V18<br>Check 66 mmf cap. connected to terminals of defl. yoke<br>Defl. yoke ringing   |
| <b>Poor Hor. Lin.</b><br>Hor. Lin and Hor. Drive controls<br>V17, V18<br>Check 0.047 and 0.1 mf caps. connected to Hor. Lin. coil<br>Hor. Out. Trans.   | <b>Pix Jitter Up and Down</b><br>Vert. Hold and Sync. Stability controls<br>AGC Threshold and Contrast controls<br>V4, V5, V7, V8   |
| <b>Poor Vert. Lin.</b><br>Vert. Lin. and Height controls<br>V8<br>Check 0.1 mf cap. connected to Vert. Out. Trans.<br>Check 100 mf cap. connected to pin 6 of V8<br>Check 0.1 mf cap. connected to pin 4 of V8<br>Vert. Out. Trans.             | <b>Pix Bending</b><br>Hor. Hold and Freq. controls<br>AGC Threshold and Sync Stability controls<br>V5, V7, V9, V15, V16, V17<br>Check 0.047 mf cap. connected to pin 4 of V16   |
| <b>Pix Jitter Sideways</b><br>Hor. Hold and Freq. controls<br>AGC Threshold control<br>V9, V15, V16, V17<br>Check 0.01 mf cap. and 27K and 6.8K res. connected to pin 5 of V15<br>Sync Stability control  | <b>Distorted Sound</b><br>Tuner fine tuning<br>AGC Threshold and Tone controls<br>Check Tuner tubes<br>V10, V11, V12, V13, V14<br>Check audio coupling network connected to pin 7 of V14<br>Sound and Vid. IF alignment L-13, T-6<br>Det. alignment T-7 |
| <b>Smear Pix</b><br>Tuner fine tuning<br>Contrast and AGC Threshold control<br>V1, V2, V3, V4, V5, V6, V9<br>Check Tuner tubes<br>Check Vid. Det. and Amp. peaking coils<br>Check 0.047 mf cap. connected to pin 1 of V6<br>IF and RF alignment | <b>Weak Sound—Pix OK</b><br>Tuner fine tuning<br>Volume and AGC Threshold controls<br>Check Tuner tubes<br>V10, V11, V12, V13, V14<br>Sound and Vid. IF alignment L-13, T-6<br>Det. alignment T-7   |
| <b>Poor Pix Detail</b><br>Tuner fine tuning<br>V1, V2, V3, V4, V21<br>AGC Threshold control<br>IF and RF alignment  | <b>Noisy Sound—Pix OK</b><br>Volume and Tone controls<br>V10, V11, V12, V13, V14<br>Check sound system of loose connections<br>Speaker<br>Sound IF and Det. alignment L-13, T-6 and T-7   |
| <b>Sound Bars in Pix</b><br>Tuner fine tuning<br>Check Tuner tubes<br>V1, V2, V3, V4, V9<br>AGC Threshold control<br>Check alignment of L-7<br>IF and RF alignment  | <b>Sync. Buzz in Sound</b><br>Tuner fine tuning<br>V4, V10, V11, V12<br>Sound IF and Det. alignment L-13, T-6, T-7  |



# PACIFIC MERCURY

Chassis 200—1, 2, 3, 4, 5, 11, 12, 13, 14, 15

## TUBE LIST


| SYMBOL | TUBE   | CIRCUIT FUNCTION         |
|--------|--------|--------------------------|
| V1     | 6CB6   | 1st Vid. IF Amp.         |
| V2     | 6CB6   | 2nd Vid. IF Amp.         |
| V3     | 6CB6   | 3rd Vid. IF Amp.         |
| V4     | 12AX7  | Vid. Det. Noise Balance  |
| V5     | 6CB6   | Vid. Amp.                |
| V6     | 6AU6   | Sound IF Amp.            |
| V7     | 6AL5   | Rat. Det.                |
| V8     | 6AV6   | Audio Out.               |
| V9     | 6AQ5   | Audio Out.               |
| V10    | 12AU7  | Sync. Sep.               |
| V11    | 6AU6   | AGC Amp.                 |
| V12    | 6AV6   | Vert. Osc.—Noise Balance |
| V13    | 12BH7  | Vert. Out.               |
| V14    | 6SN7GT | Hor. Osc.                |
| V15    | 6AU5   | Hor. Out.                |
| V16    | 6W4    | Damper                   |
| V17    | 1B3GT  | HV Rect.                 |
| V18    | 5U4C   | LV Rect.                 |
| V19    | 17HP4  | Picture Tube             |
| V20    | 6X8    | Osc.—Mixer               |
| V21    | 6BZ7   | RF Amp.                  |
| V22    | 6J6    | UHF Osc.                 |

## KEY VOLTAGES

- B+, plate of damper, V16 pin 5 290 vdc
  - Boosted B+, cath. of damper, V16 pin 3 450 vdc
  - Plate of VERT. OSC., V12 pin 7 240 vdc
  - Plate of Vert. Out., V13 pin 1 450 vdc
  - Plate(s) of Hor. Osc., V14 pin 2 180 vdc
  - pin 5 180 vdc
  - Grid of Hor. Out., V15 pin 1—12.5 vdc
- (All voltages are measured with a VTVM connected between the tube pins and chassis.)

## CHASSIS IDENTIFICATION CHART


| CHASSIS NUMBER | PICTURE TUBE TYPE | TUNERS    | UHF       |
|----------------|-------------------|-----------|-----------|
| 200-1          | 17HP4             | PMC-57006 | PMC-57007 |
| 200-2          | 17HP4             | PMC-57006 | PMC-57008 |
| 200-3          | 17HP4             | PMC-57006 | PMC-57009 |
| 200-4          | 17HP4             | PMC-57006 | None      |
| 200-5          | 17HP4             | PMC-57011 | None      |
| 200-11         | 21MP4             | PMC-57006 | PMC-57007 |
| 200-12         | 21MP4             | PMC-57006 | PMC-57008 |
| 200-13         | 21MP4             | PMC-57006 | PMC-57009 |
| 200-14         | 21MP4             | PMC-57006 | None      |
| 200-15         | 21MP4             | PMC-57011 | None      |

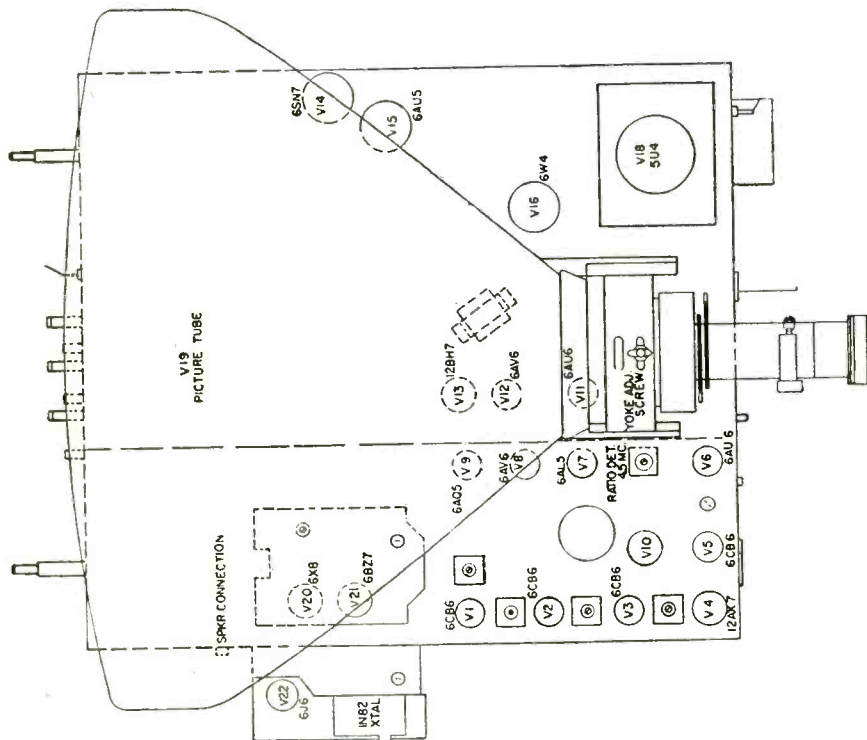

TUBE LOCATION CHART



REAR CONTROLS

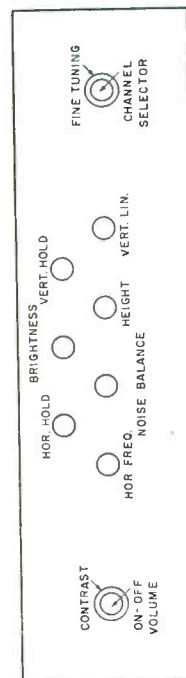

FRONT CONTROLS

**Warning**—Operation of the receiver chassis outside of the cabinet involves the danger of working with high voltages. Extreme caution should be exercised at all times.

Occasional minor adjustments will be needed if any circuit work or tube replacement is required. A test pattern, generated locally or from a broadcast station, is recommended for best results. The operating and auxiliary controls, located on the front panel and rear apron, should be set for as good a pattern as possible before making the following adjustments:

#### CENTERING

Rotate each of the Centering Rings separately until the picture is properly centered.

#### HEIGHT AND WIDTH

Adjust the Height and Width Controls, so that the picture fills out the dimensions of the screen. A slight re-adjustment of the centering control may be necessary.

#### HORIZONTAL DRIVE CONTROL

The Horizontal Drive Control is adjusted by backing off the control until a vertical white bar appears in the middle of the picture, and then going in one full turn from this point. This adjustment may be reached from the underside of the chassis mounting board. See below for detailed description of Horizontal Oscillator Sync Adjustment.

#### VERTICAL LINEARITY CONTROL

Set the Vertical Linearity Adjustments for a symmetrical pattern. A slight re-adjustment of the Height and Width Controls may then be necessary.

**Note:** The sequence of adjustments outlined above is suggested as a convenient method of approach and not an arbitrary procedure. The procedure used to obtain the final results may be varied to fit the circumstances.

#### NOISE BALANCE CONTROL

Turn the Channel Selector to the strongest station signal on the air. Slowly turn the Noise Balance Control, from full clockwise position counterclockwise until the picture just starts to show a distorted shape. Then turn the control slightly in the opposite direction so that the picture shape is normal. Check all channels. If the picture shape is distorted on any channel, advance the control slightly clockwise to restore normal shape. (Note: Whenever the picture is distorted, or slanting bars are encountered which cannot be adjusted correctly with the horizontal lock or fine tuning controls, always set the noise balance control fully clockwise before making any other adjustment.)

#### PICTURE TUBE ADJUSTMENTS

**Warning:** The picture tube envelope encloses a high vacuum. Any accidental blow or rough handling may cause the tube to implode with dangerous and destructive force. The wearing of heavy gloves and shatter-proof goggles is advised when handling the picture tube.

1. Turn the Brightness Control to maximum (clockwise) and the Picture Control to minimum (Counterclockwise).
2. Rotate the Ion Trap Magnet and at the same time move it backward and forward to obtain the brightest raster.
3. Reduce the Brightness Control so that the raster is slightly over normal brilliance and re-adjust the Ion Trap Magnet for maximum brightness.
4. Loosen the Deflection Yoke adjusting screws and rotate the Deflection Yoke so that the top and bottom edges of the raster are parallel to the top of the chassis. When this adjustment is made, tighten screws.
5. Adjust the Centering Control until the entire raster is visible, centered within the opening of the mask, with no shadowed corners.
6. Move the Ion Trap Magnet as in step 2 for final adjustment.

## PACIFIC MERCURY TROUBLE SHOOTING CHART

#### NO RASTER—SOUND OK

Brightness con.  
Check HV Fuse F1 (0.25 Amps)  
Ion trap  
V14, V15, V16, V17, V19  
HV trans. Hor. yoke CRT connections

#### WEAK PIX—SOUND AND RASTER OK

Tuner fine tuning  
Contrast con.  
V1, V2, V3, V4, V5, V11, V20

#### POOR HOR. LIN.

Hor. Drive con.  
V15, V16  
Check 0.05  $\mu$ f cap. connected to pin 5 of V16  
Hor. Out trans.

#### POOR VERT. LIN.

Vert. Size and Lin. con.  
V12, V13  
Check 0.05 and 0.1  $\mu$ f caps. connected to red lead of Vert. Osc. trans.  
Check 100  $\mu$ f Elec. cap. connected to pin 3 of V13  
Vert. Out. trans.

#### PIX JITTER SIDEWAYS

Hor. Hold, req. Locking-Range and Waveform con.  
V14, V15  
Check 2200  $\mu$ f cap. connected to pin 1 of V14

#### PIX JITTER UP & DOWN

Vert. Hold and Contrast con.  
Noise Balance con.  
V10, V11, V12, V13  
Check 4700  $\mu$ f cap. connected to yellow lead of Vert. Osc. trans.

#### ENGRAVED EFFECT IN PIX

Tuner fine tuning  
Contrast con.  
V1, V2, V3, V4, V5, V11, V19, V20  
Check 0.1  $\mu$ f cap. connected to cath. of V19 (No. 11)  
Check Vid. Det. and Amp. peaking coils

#### VERT. BARS

Hor. Drive con.  
V15, V16  
Check 47  $\mu$ f cap. connected to yoke terminals  
Defl. yoke ringing

#### PIX BENDING

Hor. Hold, req. Locking-Range and Waveform con.  
V10, V11, V14, V15  
Check 0.02  $\mu$ f cap. connected to pin 3 of V14  
Noise Balance con.

#### EXCESSIVE RASTER (PIX SIZE)

Hor. Drive con.  
Check HV Fuse F1 (0.25 Amps)  
V15, V17, V19  
Check 0.025  $\mu$ f cap. connected to pin 8 of V15

#### RASTER BLOOMING

Hor. Drive con.  
V15, V16, V17, V18, V19  
Check HV Filter cap.  
Check 470k  $\Omega$  Res. connected to HV Filter cap.

#### INSUFFICIENT RASTER WIDTH

Hor. Drive and Size con.  
V15, V16, V18  
Check 2-1000  $\mu$ f caps. connected to terminal "D" of Hor. Osc. trans.  
Hor. Out. trans.  
Low line voltage

#### INSUFFICIENT RASTER HEIGHT

Vert. Size and Lin. con.  
V12, V13, V18  
Check 0.05 and 0.1  $\mu$ f caps. connected to red lead of Vert. Osc. trans.  
Vert. Out. trans.  
Low line voltage

#### NO VERT. DEFL.

V12, V13  
Check 0.05 and 0.1  $\mu$ f caps. connected to red lead of Vert. Osc. trans.  
Vert. Defl. coils (yoke)  
Vert. Out. and Osc. trans.

#### NO VERT. SYNC.—HOR. SYNC. OK

Vert. Hold con.  
Vert. Int. network  
V11, V12, V13  
Check 4700  $\mu$ f cap. connected to yellow lead of Vert. Osc. trans.

#### NO HOR. OR VERT. SYNC.—PIX SIGNAL OK

V10, V11  
Noise Balance con.

#### NO HOR. SYNC.—VERT. SYNC. OK

Hor. Hold, Freq., Locking-Range and Waveform con.  
V10, V14, V15  
Check 330  $\mu$ f cap. connected to pin 4 of V14

#### NO SOUND—PIX OK

Tuner fine tuning  
Vol. con.  
V6, V7, V8, V9  
Speaker (open voice coil or defective connection)  
Sound and Vid. IF alignment I9  
Det. alignment T3





**VERTICAL SIZE AND VERTICAL LINEARITY CONTROL**

The vertical size and linearity controls should both be adjusted at the same time while a test pattern is being transmitted. The linearity control affects the upper portion of the picture especially the lower portion of the picture. Adjust both controls simultaneously until the test pattern is symmetrical and fills the entire screen vertically. Readjust the vertical hold control if necessary.

**CAUTION:**

The vertical linearity control is on the top chassis plate, therefore, severe shock may result from contact. If an isolation transformer is unavailable, use an insulated screwdriver for the adjustment to reduce shock hazards. The adjustment can be made from either the top or bottom of the chassis.

**FRINGE-SUBURBAN-LOCAL SWITCH**

The three position switch selects the proper operational characteristics of the receiver for the signal strength area in which located. The position of the switch is governed by the signal strength available.

In the Fringe position the A.G.C. voltage is reduced to a bare minimum and the sync stabilizer adjust control affects the sync clipping level to reduce noise affects.

In the Suburban position full A.G.C. is applied and the sync stabilizer adjust control functions as in the fringe position.

In the Local position full A.G.C. is applied and sync stabilizer adjust control disabled.

**SYNC STABILIZER ADJUST CONTROL**

The control varies the operational characteristics of the sync clipper stage to obtain the optimum operation point for the least effect of noise interrupting synchronization. The control should be adjusted for a steady picture.

**ION TRAP MAGNET**

The position of the ion trap magnet MUST be over the grid of the picture tube (second cylinder from the base identified by a flared forward lip). If the adjustment is necessary, loosen the wing nut and rotate until the position which gives maximum illumination is found. Adjust the screw for maximum illumination. Repeat the above two steps. Rotate and slide magnet until the best focus position is found. Tighten wing nut. Adjustment should be made with brightness and picture controls set for normal viewing.

**HORIZONTAL SIZE CONTROL**

The horizontal size control should be adjusted until the picture fills the entire screen horizontally. A clockwise rotation will decrease size. To some extent the vertical size control setting may be affected by a major horizontal size adjustment.

**HORIZONTAL HOLD CONTROL**

The horizontal hold control is located on the rear flange of the chassis and should be adjusted in the following manner.

Set the picture control to its normal operating position. Turn the thumb screw clockwise until it reaches its stop. Turn two complete turns counter-clockwise. The thumb screw is a vernier adjustment and will then be in the center of its range.

Turn the iron core with a small screwdriver or adjusting tool until the picture is steady (no horizontal movement). Set the core to the middle of its range.

After the iron core has been properly adjusted the thumb screw should then be used as a vernier adjustment to control synchronization when necessary.

**CENTERING MAGNET**

The centering magnet should be rotated and the control adjusted until the picture is properly framed keeping in mind that the effect of the control is governed by the position of rotation. If the control is above or below the neck of the picture tube, the picture will be moved up or down. To the left or right of the neck of the picture tube, the picture will be moved either to the left or right.

**DEFLECTION YOKE**

The correct position for the deflection yoke is as far forward on the neck of the picture tube as the shape of the tube will allow. Tube shadow or a tilted raster may result from an incorrectly positioned yoke. If a positioning adjustment is necessary, loosen the yoke nut located at the top of the picture tube assembly.

**HORIZONTAL LINEARITY MAGNET—17" ONLY**

The horizontal linearity magnet affects the linearity of the right side of the picture only. The magnet pulls or stretches the right side and has a greater effect closer to the picture tube.

**ANTI-PIN CUSHION MAGNET—21" ONLY**

Adjust centering until an edge of the raster is visible. Loosen the positioning screws and slide the magnet backward or forward until the edge of the raster is vertically straight. If keystoning is noticed adjust magnets in vertical plane.

**NO VERT. SYNC.—HOR. SYNC. OK**

Vert. Hold con.  
V12, V13  
Sync. stabilizer con.  
Check 0.0047 and 0.022  $\mu$ f caps. connected to pin 3 of V13

**VERT. BARS**

V16, V17  
Check 47  $\mu$ f cap. connected to yoke terminals  
Defl. yoke ringing

**PIX BENDING**

Hor. Hold con.  
Sync. Stabilizer con.  
V12, V14, V15  
Check 0.017  $\mu$ f cap. connected to pin 4 of V15

**WEAK OR NO PIX—SOUND WEAK—RASTER OK**

Tuner fine tuning  
V1, V2, V3, V4, V5, V6  
RF and IF alignment

**EXCESSIVE RASTER (PIX SIZE)**

Hor. Drive con.  
Hor. and Vert. Size con.  
V7, V16, V18  
Check 8.2K  $\Omega$  res. and 0.047  $\mu$ f cap. to pin 4 of V16

**INSUFFICIENT RASTER WIDTH (23)**

Hor. Size con.  
V16, V17  
Check 560  $\mu$ f and 0.01 uf caps. connected to pin 2 of V15  
Hor. Out. trans.  
Low line voltage

**INSUFFICIENT RASTER HEIGHT**

Vert. Size and Lin. con.  
V13  
Check 0.47  $\mu$ f cap. connected to pin 4 of V13  
Check B+ supply voltage  
Vert. Out. trans.  
Low line voltage

**NO VERT. DEFL.**

V13  
Check 0.01 and 0.017  $\mu$ f caps. connected to red Lead of Vert. Osc. trans.  
Check 0.47  $\mu$ f cap. connected to pin 4 of V13  
Vert. Defl. coils (yoke)  
V.O.T. and Vert. Osc. trans.

**POOR VERT. LIN.**

Vert. Size and Lin. con.  
V13  
Check 0.47  $\mu$ f cap. connected to pin 4 of V13  
Check 100  $\mu$ f Elec. cap. connected to pin 6 of V13  
Vert. Out. trans.

**NO HOR. OR VERT. SYNC.—PIX SIGNAL OK**

V12  
Check 0.0022  $\mu$ f cap. connected to pin 7 of V12  
Sync. Stabilizer con.  
Fringe switch

**NO HOR. SYNC.—VERT. SYNC. OK**

Hor. Hold con.  
V14, V15, V16  
Check 330  $\mu$ f cap. connected to pin 5 of V15

**DISTORTED SOUND**

Tuner fine tuning  
V2, V8, V9, V10, V11  
Check Vid. Det. xtal. CK706 (Part of T2)  
Check 0.01  $\mu$ f cap. connected to pin 5 of V11  
Sound and Vid. IF alignment  
Det. alignment

**WEAK SOUND—PIX OK (8C)**

Tuner fine tuning  
Vol. con.  
V2, V8, V9, V10, V11, V12  
Sound and Vid. IF alignment  
Det. alignment

**SYNC. BUZZ IN SOUND**

Tuner fine tuning  
V2, V6, V8, V9  
Check Vid. Det. xtal CK 706 (Part of T2)  
Sound IF and Det. alignment

**WEAK PIX—SOUND AND RASTER OK**

Tuner fine tuning  
Contrast con.  
V2, V3, V4, V5, V6, V12  
Fringe switch

**POOR HOR. LIN.**

V16, V17  
Check 50  $\mu$ f El. cap. connected to terminal 1 of Hor. Out. trans.  
Hor. Out. trans.


**ENGRAVED EFFECT IN PIX**

Tuner fine tuning  
Contrast con.  
V2, V3, V4, V5, V6  
Check 0.1  $\mu$ f cap. connected to pin 1 of V6  
Check Vid. Det. and App. peaking coils



# 40% Sharper Tuning

than any other AUTOMATIC ROTOR

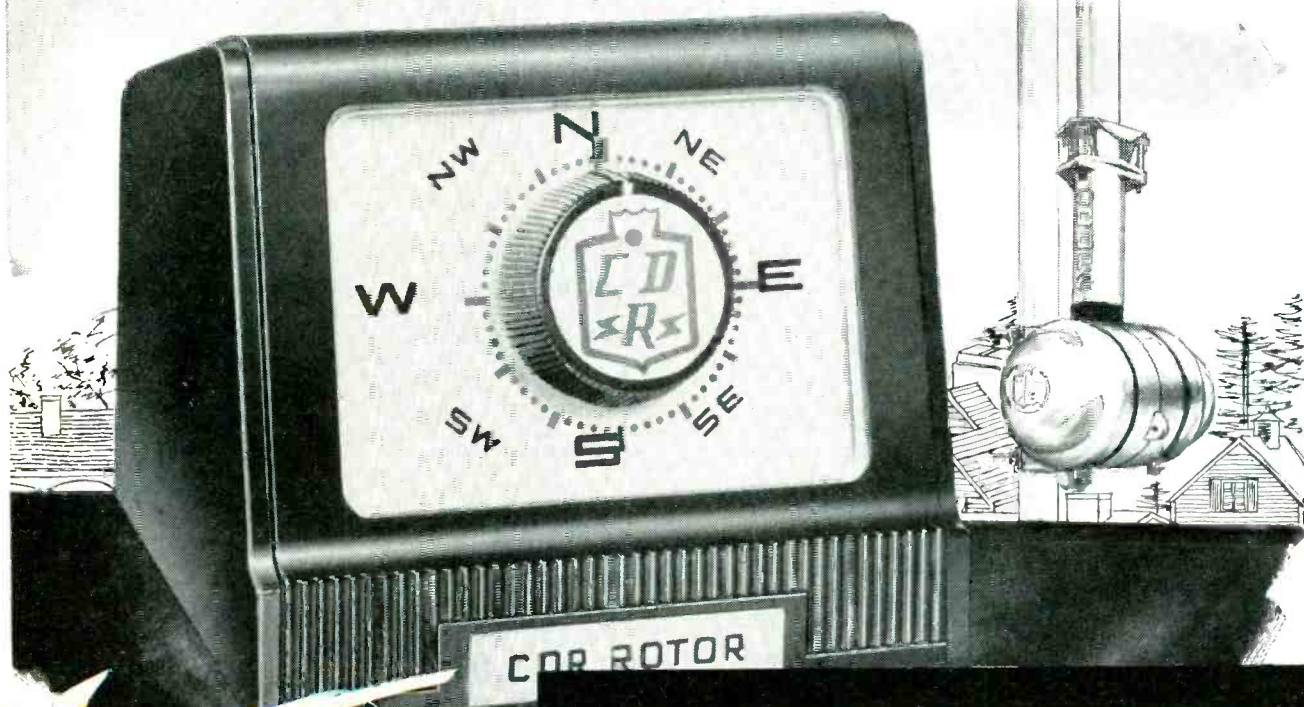

## Model AR-1 and AR-2 C·D·R automatic ROTOR

Here is EVERYTHING that ANYONE could ask for in a rotor! Powerful enough to turn any TV antenna... sturdy construction... and a handsome modern design plastic cabinet that AUTOMATICALLY turns the antenna to any position... AND ACCURACY that presents 40% SHARPER TUNING than any other automatic rotor!

...AND THEY ARE PRE-SOLD to consumers in every leading rotor market area with saturation TV SPOT ANNOUNCEMENTS!

Model AR-2... complete AUTOMATIC rotor with thrust bearing... and handsome modern design cabinet, uses 4 wire cable

Model AR-1... same as AR-2 without thrust bearing

Field Tested  
For Years

*& Tried  
& Tested  
& Proven*



**CORNELL-DUBILIER**  
SOUTH PLAINFIELD, N. J.




**THE RADIART CORP.**  
CLEVELAND 13, OHIO

RADIO-TELEVISION SERVICE DEALER • OCTOBER, 1954

# New



# Products


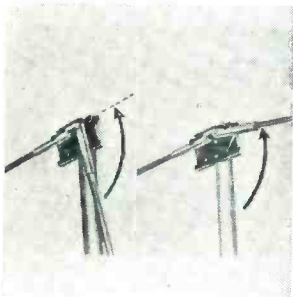


### Snap-Lock Antennas

Channel Master Corporation, Ellenville, N. Y., has announced that its complete line of preassembled antennas will incorporate "Snap-Lock" action. This new design eliminates the need for wing nuts and all other hardware requiring manual tightening. At the same time it provides for a stronger, more rigid assembly than has heretofore been possible for dipoles, directors, and reflectors.
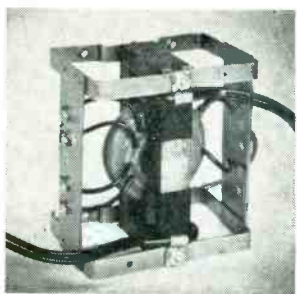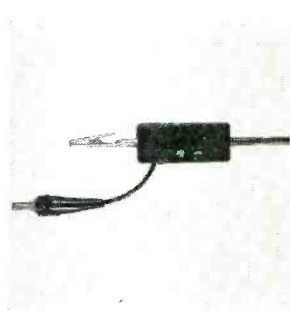
### Simpson HF Probe

Many of the service scopes now in use have relatively low sensitivity, which may place the technician at a disadvantage in checking certain low-gain circuits in the color TV chassis; however, by use of a suitable video voltage-doubler probe, it is observed that a scope having a sensitivity of 0.05 volt-per-inch, e.g., provides an effective sensitivity of 0.025 volt-per-inch.




### Merit Replacement Transformers

Seven high voltage, horizontal deflection transformers, models HVO-15 through HVO-21, designed as exact replacements for Philco units are now being manufactured by the Merit Coil and Transformer Corp., 4427 North Clark Street, Chicago. According to the manufacturer, these seven transformers cover 90 per cent of all Philco chassis and models produced prior to and during 1953.
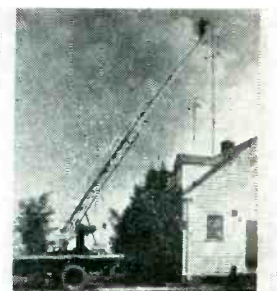
### Memco Aerial Ladders

Aerial ladders such as these, manufactured by Memco, of Oklahoma City, have become very popular with the fringe-area serviceman, who simplifies his antenna service and installation technique, saves a great deal of time, and perhaps his life, because of the ladder's safety features. For info, write: Memco, 1007 NW 36 St., Oklahoma City 3, Okla.





### Vokar Vibrator Line

A specially built line of replacement vibrators has been made available by Vokar Corporation, Dexter, Michigan. The new vibrator, known as the Imperial, is reported to have unlimited shelf-life, and quiet, unexcelled performance. Packaged in a distinctive golden can, the Imperial carries an unconditional full-year warranty. Contact points are coated with anti-oxidizing agent and each point carefully cleaned by hand rather than mechanically.
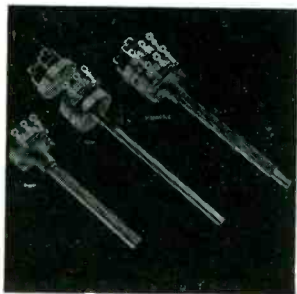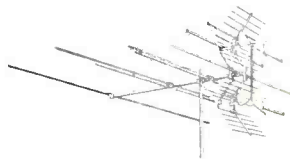
### Vee-D-X Antenna

The new "Chief Series" of antennas by LaPointe Electronics is designed around the phasing technique known as "Dyna-phase" which effects unity coupling of all three TV bands for a perfect impedance match through a single lead in line to the set. Dispensing with filters, auxiliary stubs and couplers, this antenna has an average gain for uhf that closely approximates stacked arrays with a high front-to-back rejection ratio.




### Centralab Dual Control Replacements

Centralab's "Fastatch" system of dual-concentric control replacements eliminates the problem of finding a "Special" control. Centralab has separated the rear unit, complete with inner shaft from the front unit, complete with outer shaft, so that shafts can be cut to the proper length and then the units "snapped" together in one motion. The Fastatch switch, if required, is "snapped" on to the rear unit.
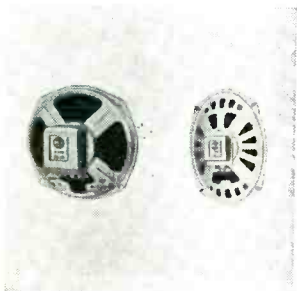
### Picture Clear UHF Antenna

The uhf section of the antenna consists of two stacked dipoles together with a reflector. These are designed to be broad-banded and to cover the entire uhf spectrum with minimum standing wave ratio when matched to the standard 300-ohm load. The reflector of the uhf section has been designed in such a manner that it also served as a good antenna for vhf reception in primary service areas. Address inquiries to RTSD.




### RCA Loudspeakers

Two new RCA loudspeakers which feature larger-than-usual Alnico V magnets are now available to radio-television service dealers for replacement applications. The speakers are a 6½-inch permanent-magnet type (RCA-220S1), for replacement service in table model radio and television receivers and in centralized sound systems; and a 6-by-9-inch permanent-magnet type (RCA-218S1), for use in automobile radios and home music systems.
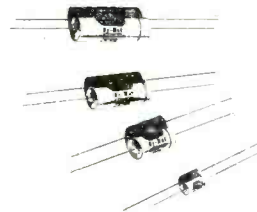
### Astron Paper Capacitors

Astron "Hy-Met," high temperature "Metalite" metallized paper capacitors, are the smallest paper capacitors available for their given ratings and operating temperatures according to Astron Corporation, East Newark, New Jersey. Hy-Met is designed for operation over a wide temperature range of -55° C to +125° C. It features the unique self-healing characteristics of metallized paper capacitors, and has good capacitance vs. temperature stability.





# THE 980 LINE



Model 985 Calibrator—\$199.50



Model 983 Oscilloscope—\$329.50



Model 984 Sweep Generator—\$199.50



Model 982 Vacuum Tube Voltmeter—\$69.50

Representing an entirely new approach in test equipment design and operation, the 980 Line instruments have brought new *simplicity* and new *time-saving facility* to TV receiver alignment and servicing. Now available to TV technicians through leading distributors. Literature giving complete information on request. WESTON Electrical Instrument Corporation, 614 Frelinghuysen Avenue, Newark 5, N. J.

8420



TEST EQUIPMENT



Model 981 Tubechecker—\$199.50



Model 980 Analyzer—\$52.50


INSURE CUSTOMER SATISFACTION . . .
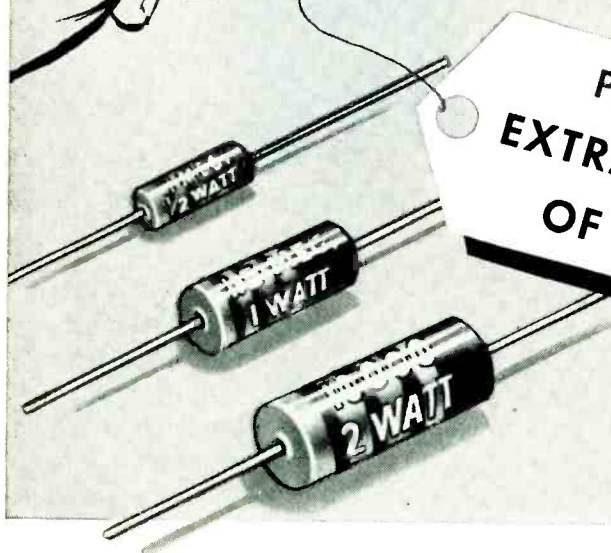
# OHMITE®




*Little Devil*®  
**COMPOSITION  
RESISTORS**

Provide an  
**EXTRA MARGIN  
OF SAFETY**



● You can eliminate "call-backs" and insure customer satisfaction by standardizing on Ohmite "Little Devil" composition resistors. These tiny units provide an *extra margin of safety* on your repair jobs. For example, they are rated at 70C instead of the usual 40C . . . and they meet all test requirements of MIL-R-11A, including salt water immersion and high humidity tests without wax impregnation. Ohmite "Little Devil" resistors are available in 1/2, 1, and 2-watt sizes ( $\pm 5\%$  or  $\pm 10\%$  tolerance) in all RETMA values. Order from your distributor, today.

Other Dependable  
OHMITE Products

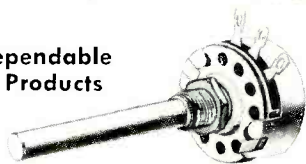

Type AB Noise-Free Potentiometers



BROWN DEVIL Wire-Wound Resistors

## ANSWERMAN

[from page 27]

vertical output tube which should be 1600 volts.

Shrinkage can be caused by an increase in the resistor values in the cathode or plate circuit of the vertical output tube. The 3000 ohm vertical linearity control and the series 1800 ohm resistor should be checked to determine if they are increasing in resistance.

If the cathode resistor checks good, the next point to examine is the two 3.3K resistors feeding B plus to the vertical output transformer. These resistors may be increasing in value reducing the plate voltage. This should also show in the *dc* plate voltage reading as a voltage change.

If the plate voltage does not change appreciably and the series resistors are found to be good the next step is to substitute a new vertical output transformer. Of course the vertical deflection coils can be at fault but this is not as likely as the transformer.

If the core material of the deflection coils should separate or is badly cracked so that a space develops when the current flows through the deflection coils the yoke can be responsible for this type of trouble.

### Increasing Scope Gain

Dear Sir:

I have an oscilloscope that doesn't have enough vertical gain for certain TV troubleshooting purposes. Could you furnish me with a wiring diagram of a battery operated pre-amplifier that will permit me to use my scope with smaller voltages such as those present in the *if* stages of a television receiver.

J.K.D.

Greencastle, Ind.

Many technicians are finally getting to know their test equipment. An oscilloscope is no longer a piece of equipment that gathers dust on a shelf above the service bench, but in many shops is employed to quickly locate troubles. Along with the scope there are two pieces of auxiliary equipment that are very useful. These two attachments are the voltage calibrator and the pre-amplifier.

Older scopes and even some newer ones may have sufficient bandpass but the gain may not be as high as desired. Also some scope kits can be greatly improved with the addition of a pre-amplifier.

[Continued on page 56]

Be Right with  
**OHMITE®**

DEPENDABLE RESISTANCE UNITS



Write for  
Stock  
Catalog

OHMITE MANUFACTURING CO.  
3640 Howard Street, Skokie, Illinois  
(Suburb of Chicago)



# SPECIAL OFFER TO OUR READERS!

By special arrangement with John F. Rider Publisher, Inc., RADIO-TV SERVICE DEALER now brings you a COMPLETE diagram service to help you do a faster, easier servicing job!

**ALL COMPLETE!**

**ALL FACTORY PREPARED!**

**ALL FACTORY AUTHORIZED!**

- ✓ Just 70¢ for COMPLETE SERVICING INFORMATION on any TV receiver . . . any year, any make, any model . . . from 1946 on!
- ✓ Just 50¢ for COMPLETE SERVICING INFORMATION on any radio . . . any year, any make, any model . . . from 1941 on!

**TAKE ADVANTAGE OF THIS SPECIAL OFFER . . . MAIL THE COUPON TODAY!**

Radio-TV Service Dealer, 67 W. 44 Street, New York 36, N. Y.

Please RUSH me the following diagrams:

| RADIO DIAGRAMS @ 50¢ EACH |      |         |
|---------------------------|------|---------|
| YEAR                      | MAKE | MODEL # |
|                           |      |         |
|                           |      |         |
|                           |      |         |
|                           |      |         |
|                           |      |         |
|                           |      |         |
|                           |      |         |
|                           |      |         |

| TV DIAGRAMS @ 70¢ EACH |      |         |
|------------------------|------|---------|
| YEAR                   | MAKE | MODEL # |
|                        |      |         |
|                        |      |         |
|                        |      |         |
|                        |      |         |
|                        |      |         |
|                        |      |         |
|                        |      |         |
|                        |      |         |
|                        |      |         |

MAKE ALL CHECKS & MONEY ORDERS PAYABLE TO Radio-TV Service Dealer  
(For all New York City orders, please submit additional 3% sales tax.)

Name .....

Address .....

City ..... State .....

I'D RATHER USE TUNG-SOL TUBES



There's every reason why servicemen feel this way. Tubes they need they can get. Quality is always uniform—always up to set manufacturers' specs. Callbacks are rare. It's more profitable for servicemen to use Tung-Sol Tubes.


# TUNG-SOL<sup>®</sup>

dependable
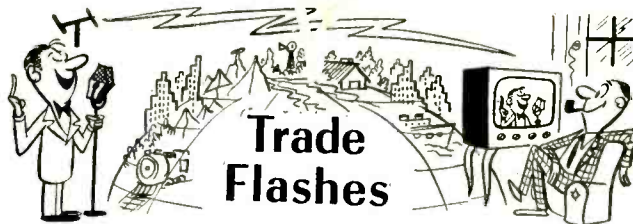
## PICTURE TUBES



TUNG-SOL ELECTRIC INC., Newark 4, N. J.  
Sales Offices: Atlanta, Chicago, Columbus,  
Culver City (Los Angeles), Dallas, Denver,  
Detroit, Newark, Seattle.



The largest assembly of high-fidelity enthusiasts ever to gather for a single event will attend the 1954 Audio Fair, according to Harry N. Reizes, Fair manager. Scheduled for four days beginning October 14 at the Hotel New Yorker, the Fair will play host to an estimated 30,000 visitors.

A retail sales contest, open to its thousands of dealers throughout the country, has been announced by the General Electric radio and television department. The contest will be of twenty weeks duration ending on Dec. 31 with the award of a 17-day all-expense paid cruise of the Caribbean to winning dealers and their wives. Every G-E radio and TV dealer in the country will have an opportunity to come out on top in the contest, regardless of the size of his business. Standing in the contest will be based on a point system and all dealers will be classified according to average volume of sales during a predetermined period.

Dallas, Texas, is getting ready a "Texas-style" welcome for the Electronic Parts Distributors' 3rd Regional seminar to be held at the Baker Hotel, October 22 and 23, 1954. This educational program, financed jointly by National Electronic Distributors Association and Radio Parts & Electronic Equipment Shows, Inc., will present Elmer Wheeler, Dallas' "super salesman" who will give visiting distributors tips on effective selling. There will also be two panels composed of distributors. One will discuss "Inventory Control," a subject shown to be at the top of jobbers' problems lists; the other will cover a variety of subjects, including methods of checking freight rates; how to help a dealer be a better businessman; ways to cut down on paper work, etc., Insurance, Business Management and possibly the new tax law. A movie on Credit & Collections, entitled "Of Time and Salesmen" produced by Dun & Bradstreet will also be shown as part of this broad program. Entertainment will include refreshments, a cocktail party and a prize award.

More than two million dollars will be spent in all media this fall to advertise CBS-Columbia color and black-and-white television receivers and radio sets. Advertising and promotion of CBS-Columbia's new color receivers will be highlighted by a two-page four color insertion in Life Magazine, to be followed up by an extensive factory saturation newspaper schedule in key cities, and expanded radio and television spots, plus full dealer cooperative schedules.

Blonder-Tongue Laboratories, Inc. of Westfield, N. J., manufacturer of master TV systems and uhf converters has expanded production capacity with the opening of a second plant nearby. This provides a total of over 50,000 square feet. Supplementing the remodeled assembly lines are a modern machine shop, enlarged service department and excellent shipping and receiving facilities. Additional floor space is available for the production of new Blonder-Tongue products, as soon as designs are released.



The Vokar Corporation, of Dexter, Michigan, manufacturers of Imperial vibrators, has announced recently that they plan to merchandise their Imperial line through their nationwide distribution setup of jobbers.

An attractive point of sale display is being offered to all distributors free of charge by Radio City Products Company, Inc., Easton, Pennsylvania. This impressive display is in four colors and acts as a silent salesman and at the same time it practically displays their new Model 480 Universal Multitester. Any distributor who orders four or more units automatically receives one of these displays without requesting it. The display features the "world's best multitester value."

The Battery Committee of National Electronic Distributors Association met with manufacturers of batteries on September 28, in Chicago. A letter to manufacturers explaining the purpose of the session, stated: "The NEDA Battery Index is serving an excellent cross-reference purpose as it now stands. However, there are a number of dry batteries that are not directly interchangeable, and on which electrical specifications and size are not exact. To start work on a clarification project, we invite you to send one of your engineers to attend a meeting in Chicago for the purpose of determining insofar as is possible, directly replaceable numbers in competitive lines."

Manufacturing companies represented include General Dry Batteries, Inc., Cleveland, Ohio; Burgess Battery Company, Freeport, Ill.; National Carbon Company, New York City; Olin Industrieis, Inc., New Haven, Conn.; Ray-O-Vac Company, Madison, Wis.; Radio Corporation of America, Harrison, New Jersey; Marathon Battery Company, Wausau, Wisconsin, and Bright Star Industries, Clifton, New Jersey.

Quam-Nichols Company has announced that effective September 1, 1954, the Wes Alderson Co., 10430 National Blvd., Los Angeles 34, California, will represent our company in the sales of its products to jobbers and manufacturers in Southern California.

Sylvania Electric Products, Inc. announced the availability to electronics distributors in the west of a new promotional program intended to help service dealers to drastically cut callbacks. Essentially, the program involves the construction and development of new tube types which will help the serviceman at the point of chassis, when he is being harassed by having to return to a customer's home after barely having left there to service a set.



Mr. Julius Finkel, president and founder of JFD Manufacturing Company, 6101-16th Avenue, Brooklyn, New York, accepts the 5-Millionth Indoor Antenna from Miss Joan Adler, who presents it to him on behalf of the JFD Production Department. This special gold-plated model is offered to Mr. Finkel, who is approaching his 25th year in business, in recognition of his high principles, and successful products.

I'D RATHER YOU WOULD



Customer confidence in local servicemen is due in large measure to the dependability of the products they use. Tung-Sol maintains quality standards that build up the local serviceman in his community.

## TUNG-SOL<sup>®</sup>

dependable

## TUBES-DIAL LAMPS

TUNG-SOL makes All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Picture Tubes, Radio, TV and Special Purpose Electron Tubes and Semiconductor Products.



## ANSWERMAN

[from page 52]

Examples of where the scope pre-amplifier is desirable is in the alignment of *vhf* tuners. In this case the pre-amplifier permits aligning without overdriving the tuner to obtain an output waveform that can be observed on the scope tube.

This is even more important in *uhf* tuner trouble shooting and alignment where the input and output levels are so small that the average scope will reveal nothing.

The scope pre-amplifier presented in Fig. 2 is a voltage amplifier employing conventional tubes, either the 1U4 or the 1L4, and is built with standard parts that service shops may easily obtain. The circuit is straightforward and can easily be assembled.

The pre-amplifier employs a 90-volt battery for the B plus and a 1.5-volt battery to provide the filament voltage. A battery operated unit is less apt to develop hum and bounce problems that would be possible with other types of power supplies. To further eliminate hum it is desirable to use coax cable for the input and output signals and the outside shield of the cable should


be fastened to the metal container rather than to terminals protruding from the metal container. Best results can be obtained if the batteries are also enclosed in the case.

The 1U4 or 1L4 tube is employed because of the low filament current drain. The 1U4 tube is preferable because of its high gain and low B plus current drain.

In the chassis layout, maintain the input and output leads and circuit resistors and condensers as far as possible from each other so that feedback possibilities are reduced.

The use of a scope pre-amplifier with an *rf* probe will permit the serviceman to go right up to the front end of a TV receiver and view the signals that otherwise would not be discernible. Also he can more easily perform stage by stage alignment in high gain, low level equipment.
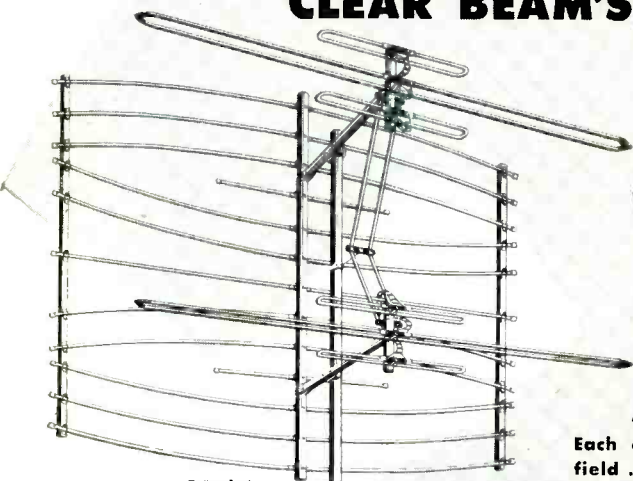
## HOTTEST IN THE FRINGES..NATION-WIDE! CLEAR BEAM'S BIG



Model  
TK1500


**TRI-KING**

## ALL-BAND FRINGE ANTENNAS

Each a peak performer in its field . . . a triple threat to any fringe problem . . . with more dollar-for-dollar construction value!

The Tri-King TK1500 offers super fringe performance through better design features. Half wave electrical spacing between dipoles for higher gain on every channel. Positive "back up action" through the use of a full radar screen . . . acclaimed industry-wide as the finest reflector ever designed for ghost rejection and elimination of co-channel

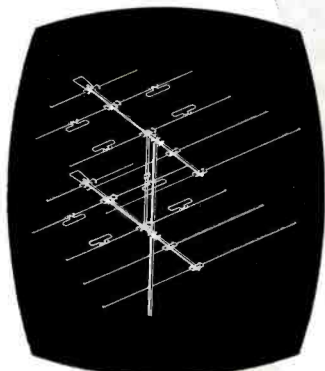
interference! Fully wind tunnel tested. Available in single bay (Model TK1000) and Super, wide spaced array (Model TK1800).



Clear Beam  
**HUNTER**

2 Bay Model MYH 50-2

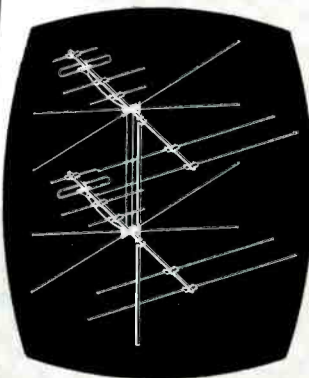New wave trap principle gives extremely high gain, sharp directivity, in-phase tuning on all channels. New, flat design for low wind resistance!



Clear Beam  
**BIG CHIEF**  
2 Bay Model BC 12-2

An advanced conical-Yagi with element diameters varied for precision tuning, matched sensitivity and peak performance on high and low band!

**B CLEAR ANTENNA CORP.**  
**BEAM**

Canoga Park, Calif. • Chicago, Ill.  
affiliated with TEMPO TV products

Warehouses in Seattle, Portland, San Francisco, Honolulu, Dallas, Kansas City, Chicago, Detroit, Baltimore

## WORKBENCH

[from page 35]

A voltage check was then taken at Pin #1 of V12A. Instead of the meter reading 11 volts negative, it read about one volt negative. A resistance check was next made from Pin #1, grid of V12A, to ground. The reading was about 200K instead of 2.2 meg. ohms. C57 (20 *uif*) was then clipped from the circuit and on checking its resistance it read 300K ohms. We replaced C57 and the receiver now functioned properly. The point to remember here is that because there was no bias on V12A due to a defective C57, the video and blanking information was not eliminated and was therefore allowed to trigger the vertical and horizontal oscillators.

## COMMUNITY TV SYSTEM

[from page 23]

to each distribution outlet or ADO unit regardless of its separation from the line amplifiers.

The distribution outlets or ADO units are used to feed three separate secondary lines or riser cables. Individual receivers are connected to the riser cables, each cable handling 20 receivers. The ADO units are minimum loss bridging amplifiers that provide a high degree of decoupling between amplifiers and the individual riser cables. They have a minimum forward loss and a very high backward attenuation.

From the secondary lines the individual drop-offs are made to receivers



via isolation networks. As many as 60 receivers can be supplied with signal from the three riser cables attached to an ADO unit. Other ADO units are available that permit feeding of 200 receivers.

The special drop-off isolation networks link the cable that runs into an individual receiver with the riser cable. These drop-off networks must be positioned along the riser cable according to a color code. They have varying degrees of attenuation according to their separation from the ADO unit. With this arrangement the same amplitude signal is applied to each receiver along the riser whether the drop-off is made near the ADO unit or at the far end of the line. At the same time they permit optimum isolation between all receivers along the cable.

According to Gene Schneider, performance reliability of the system depends on a rigid preventive maintenance schedule. A chief technician and two assistants handle the maintenance and installation chores. Each amplifier location is seen once each five weeks and its signal level measured. Every ten weeks a replacement amplifier is substituted at each location. The removed amplifier is taken to the shop to be inspected, adjusted, and aligned. It then can be inserted at another location along the system.

The maintenance schedule is arranged so that level checks are being taken in one part of the city while amplifier substitutions are made in another part. Such a schedule affords a good indication of the overall system almost each week because of the interlocking arrangements with the main feeders.

The technical crew also makes the individual drop-offs to new subscribers and many other chores such as re-routing lines when pole changes are made, for building construction and, yes, even for house movings.

The story of television in Casper is an inspiring one because it is a direct result of local community activity—hopes, pioneering spirit, effort, and results. No dole or grants are involved. This is the answer for obtaining first rate television in many cities of comparable size and location.

## RC CIRCUITS

[from page 30]

in a simple series circuit, full source voltage appears across the resistor at the first instant. The effect on time constant so far is zero—since a modified RC circuit where the condenser effectively charges up to one-half the battery voltage, starting with one-half the

original initial current, would have the same time constant as before if no other factor is involved. The third factor which makes the difference is the fact that the current for both condensers goes through  $R1$ , even though one condenser is discharging and the other is charging. Effectively, this is the same as if both were charging or both discharging through  $R1$ .

Immediately after the first surge, the voltage across parallel condenser  $C1$  can be considered the battery voltage in an equivalent circuit, Fig. 24d-60v. The parallel condenser  $C1$  discharges by

this amount of voltage and the series condenser charges by exactly the same amount. The current for both condensers flows through  $R1$ . The time constant of a simple series RC circuit is changed in exactly the same degree by placing a second condenser across either the resistor or the original condenser. However, the effect on circuit operation and on the output waveform will be different, as shown in the voltage curves of Fig. 24, when the condenser is across the resistor.

One important characteristic of this  
[Continued on page 59]

FLYBACKS • YOKES • WIDTH  
CONTROLS • VERTICAL OUTPUTS

# STANCOR

YOUR MOST COMPLETE SOURCE OF  
EXACT REPLACEMENT  
TV TRANSFORMERS

● Designed from original manufacturers specifications, STANCOR exact replacement transformers faithfully duplicate the ratings and mounting styles of the original unit.

There is no skimping on wire, insulation or laminations. They will equal or better the performance and quality of the original and every STANCOR transformer is individually tested before packaging.

LINEARITY CONTROLS • POWERS

BLOCKING-OSCILLATORS



NEW... and typical of STANCOR exact replacements is the DY-13A Deflection Yoke, exact replacement for all Muntz 24" and 27" sets. There are no leads to solder—the DY-13A plugs into the set. Bulletin 495 listing models using this yoke is available from your distributor or from STANCOR.

Stancor transformers are listed in:  
Photofact Folders  
Counterfacts  
Radio's Master  
File-O-Matic



## CHICAGO STANDARD TRANSFORMER CORPORATION

3586 ELSTON AVENUE • CHICAGO 18, ILLINOIS  
EXPORT SALES: Roburn Agencies, Inc., 431 Greenwich Street, New York 13, N. Y.

# 2 RIDER BOOKS PUBLISHED IN SEPTEMBER

## PICTURE BOOK OF TV TROUBLES, Vol. 1

(Horizontal AFC-Oscillator Circuits)

by the RIDER LABORATORY STAFF

The first of a new "TV Case History" series, designed to provide the technician with a better understanding of how to diagnose TV receiver troubles by means of picture and waveform observation. All material in this book is the result of actual troubleshooting done in the Rider labs! Over 65 "faulty" picture tube pattern illustrations . . . over 150 waveform illustrations (normal and abnormal!) A MUST for every service technician!

**CHAPTERS:** Pulse-width Type (Synchroguide); Phase Detector—Stabilized Multivibrator; Phase Discriminator—sine wave oscillator (Synchrolok); Phase Detector—sine wave oscillator.

Cat. #168 . . . . . 80 (5½x8½") pages . . . . . only \$1.35

## HOW TO USE TEST PROBES

by A. A. Ghiradri and R. G. Middleton

The only book of its kind! Written by two of the country's leading electronics experts, this book covers all types of test probes used with VOM's, VTVM's, and scopes. The one book that tells you what to use, where to use it, how to use it! Complete, step-by-step explanations, with practical examples of results and effects.

**CHAPTERS:** Resistive High Voltage D-C Probe; Capacitance-Divider High Voltage A-C Probe; Test Cable Shielding and Test Circuit Loading Fundamentals; Resistive Circuit-Isolation Probe ("D-C Probe"); Compensated R-C ("Low Capacitance") and Cathode Follower Circuit-Isolation Probes; Rectifying Probes for the VTVM; Demodulator Probes; Index.

Cat. #165 . . . . . 176 (5½x8½") pages . . . . . only \$2.90

Buy these books from your jobber or bookstore today! If unavailable, write to:  
John F. Rider Publisher, Inc.

### SPECIAL OFFER!

"ELECTRICITY FOR BOYS & GIRLS"  
ONLY 25¢

Answers ALL the questions your youngsters ask about electricity! In simple, "boys-and-girls" language, this book clearly explains electricity, electrons, atoms, batteries, generators, currents, conductors, electrical terms, how to build a simple electric motor, and much more! Profusely illustrated! Perfect for every boy and girl! 64 (5½x8½") pages, only 25¢!

### MAIL THIS COUPON TODAY!

JOHN F. RIDER PUBLISHER, INC. (SD)  
480 Canal St., New York 13, N. Y.

Please send me . . . . . copies of **ELECTRICITY FOR BOYS AND GIRLS**, @ 25¢ each.  
Payment enclosed.

NAME . . . . .

ADDRESS . . . . .

CITY . . . . . STATE . . . . .

# Trade Literature ✓ Check List

**Catalog:** installation practices, and types of accessories available for a multiplicity of installations, including splicers, HV probes, custom TV, outlet wall plates, combination and polarized connectors, terminals, etc.

Javex  
P.O. Box 646  
Redlands, Calif.

150,000 cross-reference listings of TV sweep components for every TV set mfd. to date, plus servicing data and theory of sweep circuits.

Ram Electronics Sales Co.  
Irvington, N. Y.

1954 Catalog of stock transformers for Radio, TV, amateur, communications, etc. applications. Electrical and physical specs for over 500 units. Also write for bulletin #469, for Flyback replacements.

Chicago Standard Transformer Co.  
Addison and Elston,  
Chicago 18, Ill.

New Tung-Sol Tube Characteristics Manual, 200 pages listing data on 600 receiving tubes, 110 premium types, 170 CRT's, 85 diodes plus tube base diagrams, color codes, dial lamps and numbering codes.

Tung-Sol Electric Co.  
95 8th Ave.,  
Newark 4, N. J.

Jensen Catalog #1040, covers their line of general purpose and commercial loudspeakers, projectors, cabinets, volume controls and transformers.

Jensen Manufacturing Co.  
6601 South Laramie Ave.,  
Chicago 38, Ill.

Electro-Voice Catalog #119 illustrates and describes mikes, HI FI speakers, components, enclosures, phono cartridges, PA components, FM and TV boosters, and RME products.

Electro-Voice, Inc.  
Buchanan, Mich.

Complete products catalog featuring the Astatic line of phono pickups, needles, recording heads, mike stands, TV uhf converters and boosters.

Astatic Corporation  
Conneaut, Ohio

Allied Catalog #140 listing a highly comprehensive line of electronic equipment for domestic consumption. You name it. It's here.

Allied Radio Corporation  
100 N. Western Ave.,  
Chicago 80, Ill.

The CBS-Hytron Reference Guide for Miniature Electron Tubes, containing all miniature tubes, regardless of make. 329 types.

CBS-Hytron  
Danvers, Mass.

A Catalog of Chester Wires and Cables for every electronic purpose, and for every installation technique.

Chester Cable Corp.  
Chester, New York

JFD's Brochure with charts, diagrams, and photos of development of their new Jet-Helix antenna.

JFD Manufacturing Co.  
6101 16th Ave.  
Brooklyn 4, N. Y.

GE's Brochure, illustrating in diagrams the fundamentals of the GE Chromacoder TV B'casting system.

General Electric  
Electronics Park  
Syracuse, N. Y.

Aside from the books reviewed in our Trade Literature columns, many valuable bulletins, catalogs, guides, etc. are made available by manufacturers, etc. at no cost, or in some cases, nominal cost, to the servicing profession. As an aid to the busy technician, RTSD publishes this Check List. To the best of our ability, the items are listed in the order in which we learned about them. This, we feel, is the fairest and most sensible way to help the serviceman keep up with things. Items that couldn't make the list this month because of space limitations will ride at the head next issue. Unless otherwise specified, all literature pieces in the Check List are free for the asking. Simply write to the organization listed in the Source column, and mention you saw it in *Service Dealer*.



## RC CIRCUITS

[from page 57]

circuit should be noted and remembered. After the first surge, the parallel condenser discharges while the series condenser continues to charge. With some modifications, we will find the same thing happening in many other types of complex RC circuits.

The basic action of any of the RC networks we have discussed may be modified to some extent in a radio or TV stage because of the way the circuit is connected. For example, connecting the grid of a tube to a certain point in the RC circuit may effectively short out one resistor when the grid draws current on positive signal peaks. However, during the rest of the signal cycle, the resistor functions as part of the network.

### Sync Circuit Application

This happens in a common circuit in current TV receivers, Fig. 25. The RC network is used between the output video amplifier and the first sync clipper stage. Our previous analysis makes it simple to understand the general action of the RC circuit. Before that is discussed, it will be helpful to review briefly how this type of clipper stage operates.

Grid leak bias and low plate voltage are used in the sync clipper stage, V1. The amount of grid leak bias is determined by the positive peak voltage of the incoming signal—the sync pulses. As a result of the low plate voltage and the bias, the tube cuts off at a comparatively small negative signal. Therefore, only the most positive part of the incoming composite video signal—the sync pulses—appears in the output at the plate. All the rest of the video signal is negative enough to cause the tube to cut off.

The combination C1R1 in Fig. 25 acts as a "noise filter" to reduce the harmful effect of short-duration, high-amplitude noise pulses on the sync clipper stage. Without C1R1, the grid leak condenser C2 would charge up instantaneously to the peak amplitude of the noise pulse. On the peaks of the positive signals the time constant is short, since the grid draws current. At this instant, the effective grid-to-cathode resistance of V1 is very much smaller than R2 which is in parallel, and acts to short out R2. After the noise pulse passes, C2 discharges through R2, a long time constant path. This causes a large increase in grid leak bias. When sync pulses come in for the next few lines, the clipper stage will remain cut off because of the heavy bias and no sync pulses appear in the output. This

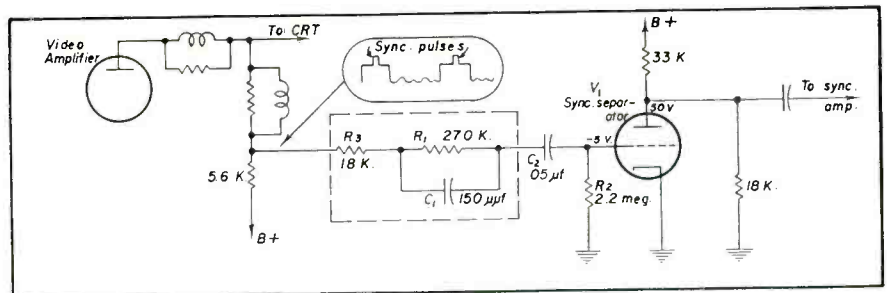


Fig. 25—Series parallel RC input circuit to sync separator stage.

can easily upset synchronization.

However, with C1R1 in the circuit, a large noise pulse as before causes the


grid of the clipper to draw current, just as an incoming sync pulse does. However, the voltage divides instan-

## INADEQUATE WIRING A MAJOR PROBLEM AFFECTING TV PERFORMANCE

One of the greatest problems of the electrical industry is that of inadequate distribution and insufficient wiring. Systems that are planned to standards that existed years ago when the average residential load was only 25% or less of today's demand are inadequate to main-

tain the capacity and maintain the voltage necessary for the proper performance of all the usual appliances and equipment available in the average American home. The extreme sensitivity of a TV receiver is instantly effected in performance by a low voltage condition. This problem
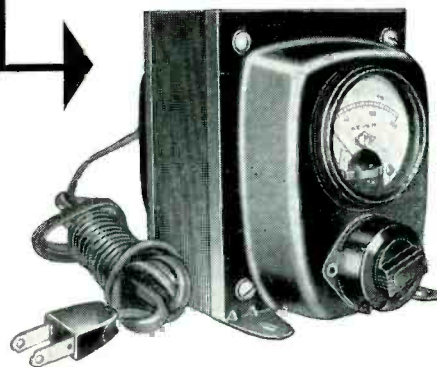
## CAN BE SOLVED WITH THE ACME ELECTRIC T-8394M VOLTAGE ADJUSTOR



The T-8394M Voltage Adjustor can be used by the service man to reproduce the operating condition about which the customer complains by turning tap switch to the voltage which simulates such condition. For example, customer complains that evening program pictures flicker and shrink. When service man calls next day all operation appears normal — voltage tests out properly. But, by adjusting voltage to 97 volts the condition about which the complaint was made is reproduced. This indicates low voltage condition during evening that can be corrected with a T-8394M Voltage Adjustor.

ORDER FROM YOUR JOBBER

**ACME ELECTRIC CORPORATION**  
MAIN PLANT: 4610 Water Street • Cuba, N. Y.  
West Coast Engineering Laboratories: 1375 W. Jefferson Blvd. • Los Angeles, Calif.  
In Canada: ACME ELECTRIC CORP. LTD. • 50 Northline Road • Toronto, Ont.


**Acme ACME Electric**  
TRANSFORMERS

# TV SERVICEMEN: here's the help you need

**NEW**

## "TV SERVICE DATA BOOK"

by MILTON S. KIVER

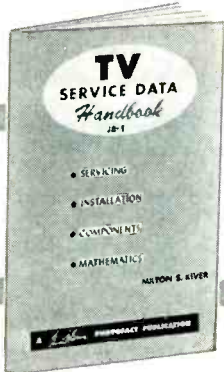

Packed with  
facts you'll  
use every  
single day

**GET IT  
TODAY**

**all the data you need  
in one handy guide—**

- saves valuable time
- helps you earn more

**Instant TV Servicing and Installation Reference:** Have at your finger-tips all of the most frequently needed charts, tables and formulas you require in Television servicing and installation. Includes charts on fuses, color codes, attenuator pads, monochrome signal specifications, guy wire lengths, etc.—all the data you'll ever want in your daily work. Save valuable time on calculations by quick reference to the tables of mathematical constants and electrical formulas. Speeds your work for greater earnings.

**Trouble-Shooting Guide:** Includes section on TV trouble-shooting. Lists common trouble symptoms and tells how to locate defective components. Recommends most effective methods for use of test probes and other accessory equipment. You'll want to keep it handy in your tube caddy for quick reference at the bench or in the field. It pays for itself in a single day's work. Over 100 pages. 5½ x 8½".

ORDER JB-1. \$1.50  
Only

**ORDER  
TODAY**

**HOWARD W. SAMS & CO., INC.**

Order from your Parts Jobber today, or write to Howard W. Sams & Co., Inc., 2209 East 46th St., Indianapolis 5, Ind.

My (check) (money order) for \$..... enclosed. Send.....copy (ies) of "TV Service Data Book" (JB-1, \$1.50).

Name.....

Address.....

City.....Zone.....State.....  
(outside U.S.A. priced slightly higher)

taneously between  $C1$  and  $C2$  in inverse proportion to the capacity. Practically all of the voltage therefore appears across  $C1$ . This is similar to the first surge when the switch is closed in Fig. 24a. As a result, there is practically no increase of voltage across grid leak condenser  $C2$  and no change of bias. Since the time constant for the discharge of  $C1$  through  $R1$  is short,  $C1$  can discharge rapidly.

When signals with a longer duration come in—such as vertical sync pulses—the initial voltage is also practically all across  $C1$ . However, these sync pulses last long enough for grid leak condenser  $C2$  to charge to a substantial portion of the applied signal voltage, while at the same time  $C1$  discharges. When the transmission of these sync pulses is completed,  $C2$  then discharges through  $R2$  to provide grid leak bias.  $C1R1$  act to keep the grid leak bias level fixed by the sync pulse amplitude rather than by random noise pulses. Obviously, this noise filter is not a complete solution to all noise problems since large noise bursts may duplicate the effect of vertical sync pulses. Most current models use in addition noise cancellation stages.

$R3$ , 18K, is added in series with the network to act as a decoupling resistor.  $R3$  prevents  $V1$  from loading down the video amplifier stage, especially when the grid of  $V1$  draws current,  $R3$  is large enough to decouple  $V1$  from the video amplifier stage output circuit but still small enough to allow  $C1$  to charge up quickly to the positive peaks of applied signals.

A drop in the value of  $R3$  can cause picture fuzziness and/or sync instability. Strictly speaking, the RC circuit of Fig. 25 falls in the category of a more complex network which will be discussed in the next installment. However, the small value of  $R3$  compared to  $R1$  makes the circuit function substantially as described above.

[To Be Continued]

## VERTICAL INSTABILITY

[from page 11]

portional to the strength of the incoming signal. However, the presence of grid current alters the situation considerably. Thus, referring to the diagram, we observe that resistors  $R66$ ,  $R67$  and condenser  $C93$  form the filter network for the *age* line. Since the grid circuit should draw no current there should be no voltage drop across  $R66$  and  $R67$ . The voltage at point  $C$  in Fig. 5 should equal the voltage at point  $B$  if no current flows.

[Continued on next page]



TRY THE

**Walco**  
Packaged  
**SERVICE PLAN**

**8 Ways Better!**

Service men go for Walco's packaged phonograph needle replacement plan because it's so easy to understand and put to work. No headaches trying to figure out which needle for which cartridge—two easy guides figure for you. And you don't have to be a salesman to sell replacement—even to sell profitable diamond needles—Walco sells 'em for you, by proven methods learned in our long experience as leaders in the replacement needle industry—and as originators of the modern jewel tip needle. See how the Walco plan stacks up 8 ways better to help you service and sell:

- 1 **WALCO SERVICE PAKS**—for VM, Webcor, RCA, Philco, Magnovox and other leaders. Take the right Pak on a service call and you're ready for instant replacement anywhere.
- 2 **EASY REPLACEMENT GUIDE**—3-page center spread in Walco's Catalog 600 gives instant identification of osmium, sapphire and diamond needles. Includes illustrations and prices. You can put it on your wall.
- 3 **10-SECOND GUIDE**—to most popular replacements. Name of phono is all you need!
- 4 **CROSS-REFERENCE INDEX**—gives you the right Walco Needle Number to replace any replacement needle.
- 5 **LISTING IN SAM'S PHOTOFACTS**—convenient help when you need it.
- 6 **REPLACEMENT REMINDER STICKERS**—Peel protective back, stick on customer's phonograph. Tells him when needle was replaced by you—reminds him to replace periodically.
- 7 **RECORD SPINDLE CARDS**—They tell the customer you've replaced a needle and how long it will wear—then urge him to re-order.
- 8 **NATIONAL ADVERTISING**—building your customer's confidence in Walco and in you for replacing with Walco. Ads in High Fidelity, Saturday Review and other record-minded magazines.

Get all the information—see how much easier it is to sell and service with Walco!

SEND FOR WALCO'S CATALOG 600

**Walco** TRADE NAME OF  
ELECTROVOX CO., INC.  
Leaders in Replacement Needles

60 Franklin Street, East Orange, N. J.



Under normal conditions the control grids connected to the *agc* line will measure the same as at point C of Fig. 5. If a grid is drawing current the grid voltage will measure less negative than the *agc* line (point C). For example, in Fig. 5, if point C in the *agc* line measures  $-5V$  and a check at point D reveals a potential of  $-2.9V$  we can conclude that current flows in the grid circuit of V8.

This could come from two sources only: One is V8 itself, and the other is a defective C79. If V8 is gassy the grid will develop a positive potential permitting current to flow in the circuit. This may be checked by removing V8 from the socket and rechecking the voltage. Since the removal of V8 kills the signal, the *agc* line voltage will drop to a very low value, probably less than  $-1$  volt. If the grid pin at the socket of V8, with V8 removed now measures the same value as the *agc* line, V8 is defective. If the grid pin of V8 still reads some positive value, the second possibility, that is, a leaky or shorted 470 *mf* C79 is the cause of the trouble.


If the scope test at point A of Fig. 3 does not show sync compression, the video amplifier should be checked. Wave form checks should be made at the input and output points of each stage in the video circuit. Tube voltages and resistance checks should be made at any stage that shows incorrect waveforms.

#### Sync Circuit Check

If the video amplifier stages check OK the sync circuit is checked next. Again two methods may be employed, waveform analysis or voltage analysis. Waveforms of the sync stages may be made with a scope. Unfortunately, unless the exact waveforms are known, it is very difficult to determine whether or not an observed waveform is correct. It is therefore best to supplement the scope test with a voltage analysis.

One invaluable test that can be made with the scope is a check for the presence of undesired signals. The writer has frequently found unstable sync in receivers resulting from spurious signals in the sync circuit with no channel tuned in. These spurious signals, tracked down with the scope invariably show up an open filter somewhere. It is almost impossible to pin point this type of trouble by voltage measurements.

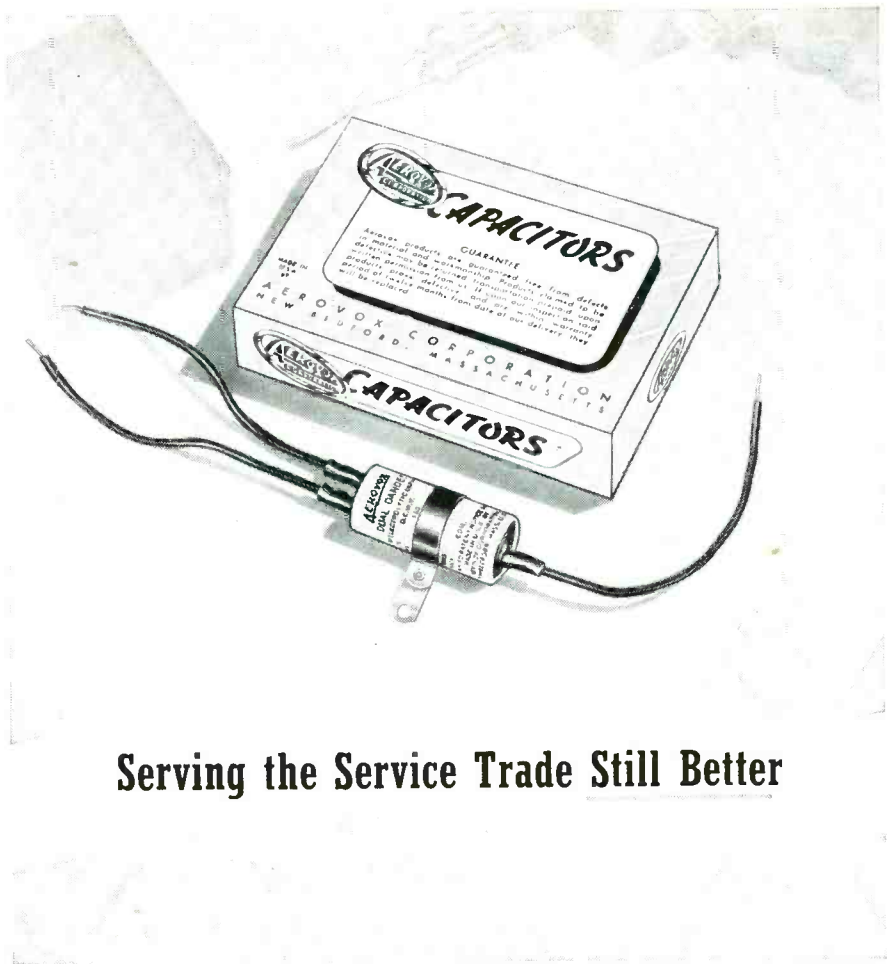When making a voltage analysis of the sync circuit, receiver check points are invaluable as points of reference. Fig. 6 shows a typical sync circuit. It must be kept in mind that the sync signals will affect the voltage readings to some extent. Under normal operating conditions the presence of sync pulses will produce a negative voltage at the



Serving the Service Trade Still Better



*The*  
**ASD**  
**TELEVISION**  
Tube Tester

**MODEL TV-20**

**NET \$124.50**

**HERE IT IS**

- NO ROLL CHART
- PRACTICALLY NO SET-UP
- 20 CONNECTED SOCKETS
- LARGE 4½" METER
- HIGH GAS SENSITIVITY

The tube tester designed especially for the television serviceman. With this tester you can test an entire set of TV tubes in a few minutes. This means less time spent per job, more profit, more tube sales and fewer call-backs.

*Write for Details or See Your Distributor.*

**Developed and Manufactured by**  
**AMERICAN SCIENTIFIC DEVELOPEMENT CO.**  
334-336 S. Main St., Ft. Atkinson, Wisc.

**STOP TV TUNER NOISE...**  
**QUICKLY—SAFELY! with**

**SPRA-KLEEN**

**Pressure-Applied CLEANER-LUBRICANT**



**WRITE TODAY** for your free copy of the big new G-C Catalog 156.



**DEALER'S NET \$1.00**  
**LIST \$1.67 (6 full ounces)**

**A NEW MUST FOR EVERY SERVICEMAN**

- No Harmful Ingredients
- Exclusive X-79 Formula
- Reaches Everywhere — No Need To Pull a TV Chassis!

G-C's new SPRA-KLEEN Electrical Contact Cleaner and Lubricant is just what you need for fast, easy, safe servicing of TV tuners and other parts like relays, switches and controls. No need to pull that chassis; just "poof" and SPRA-KLEEN's directional nozzle reaches any remote corner. See your favorite jobber today!

**GENERAL CEMENT MANUFACTURING CO.**

914 Taylor Avenue Rockford, Illinois

STATEMENT REQUIRED BY THE ACT OF AUGUST 24, 1912, AS AMENDED BY THE ACTS OF MARCH 3, 1933, AND JULY 2, 1946 (Title 39 United States Code, Section 233) SHOWING THE OWNERSHIP, MANAGEMENT, AND CIRCULATION OF RADIO-TELEVISION SERVICE DEALER, published monthly at New York, N. Y. for October 1, 1954.

1. The names and addresses of the publisher, editor, and business managers are: Publisher, Sanford R. Cowan, 6 Embassy Court, Great Neck, N. Y.; Editor, Samuel L. Marshall, 262 Sullivan Place, Brooklyn, N. Y.; Business Manager, Sanford R. Cowan, 6 Embassy Court, Great Neck, N. Y.

2. The owner is: (if owned by a corporation, its name and address must be stated and also immediately thereunder the names and addresses of stockholders owning or holding 1 per cent or more of total amount of stock. If not owned by a corporation, the names and addresses of the individual owners must be given. If owned by a partnership or other unincorporated firm, its name and address, as well as that of each individual member, must be given.) COWAN PUBLISHING CORP., 67 West 44th Street, New York 36, N. Y.; Sanford R. Cowan, 6 Embassy Court, Great Neck, N. Y.

3. The known bondholders, mortgagees, and other security holders owning or holding 1 per cent or more of total amount of bonds, mortgages, or other securities are: None.

4. Paragraphs 2 and 3 include, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting; also the statements in the two paragraphs show the affiant's full knowledge and beliefs as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock and securities in a capacity other than that of a bona fide owner.

(Signed) S. R. COWAN, Publisher

Sworn to and subscribed before me, this 20th day of August, 1954.

HARRY N. REIZES, Notary Public

grids of the stages that are grid leak biased.

Referring to Fig. 6 we find our check points are A at V1, B at V2, and C at V3. At points A and B the voltage should read negative if a sync pulse is present. If C1 or C2 are leaky the reading may change to a lower value or may even go positive. In order to check this, it is necessary to switch off the channel and recheck the grid voltages.

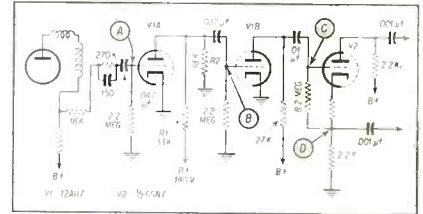


Fig. 6 — Typical sync circuit.

In the event of positive grid voltage the sync pulse shape and amplitude will be materially changed. The extent of the waveshape change determines how badly the sync is upset. Sometimes loss of both horizontal and vertical hold are observed. Reference to Fig. 6 will indicate that point D is normally positive with respect to ground. Therefore, the grid of V2 will read positive. However, its positive value should never exceed the reading from point D to ground.

Careful plate voltage readings should be made in sync circuits. V1 should have a low plate voltage due to the voltage divider action of R1 and R2. Should the plate voltage rise the separating action of this stage will alter and video information will enter the sync, causing instability. In comparison, V2 has a higher plate voltage. Sync instability will occur if the 27K plate resistor should rise in value, thereby lowering the plate voltage; or should the source voltage drop.

The foregoing, in general, outlines the underlying principles of vertical sync instability. Of course, certain peculiar circuit designs will give rise to concomittant peculiar effects. However, if the serviceman understands the basic causes and symptoms relating to these troubles, the overall servicing operation becomes quicker and that much more profitable.

**COLOR TV**

[from page 16]

and B<sub>CD</sub> could now be utilized to modulate the color subcarrier to produce the single color signal shown in Fig. 9. The manner in which this would be done is explained in detail in the next

**Give the United Way**



**wanted:** Your Endorsement!  
On the NEW  
AUTHORIZED CRT Tester


**why:** Because we at AUTHORIZED feel that our statements regarding this amazingly efficient new CRT Tester may sound prejudiced to the serviceman who hears and reads many claims every day. We say that the AUTHORIZED CRT Tester does the following:

- Outperforms any other tester on the market.
- Tests all electromagnetic and electrostatic duodecal socket based tubes.
- Reveals the condition of a picture tube quickly and accurately. No time lost in unnecessary computation. One switch position gives ALL continuity tests! Simultaneously tests all elements for opens, shorts and leakage. The split neon bulbs indicate condition of the tube . . . a meter gives the emission reading.
- Serves as an absolutely invaluable point-of-sale tool. This compact and portable tester will enable you to let your customer sell himself in his own home.

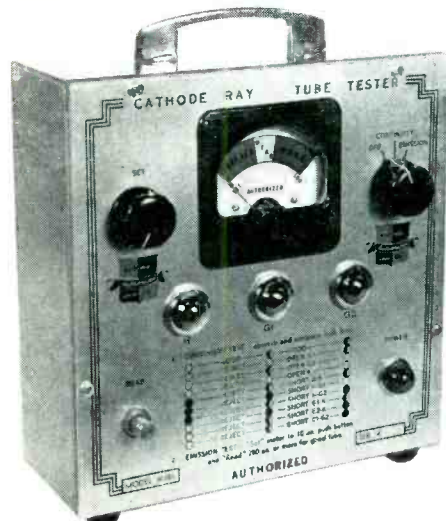**we want you to back us up!**

**therefore:** We have allocated a certain number of AUTHORIZED CRT Testers to be sent to servicemen on a ten day try-out basis. Send us your request on company letterhead, with your distributor's name. At no cost to you, we want you to use it, test it, and appraise it, under actual service conditions. The billing will be on memo, and we will pre-pay the shipping cost. At the end of the ten days we would like you to return the instrument to us, plus your appraisal, so that another serviceman can have the same opportunity.

**if,** after using one, you would like to purchase an AUTHORIZED CRT Tester, you will find it available at your local jobber-distributor.



**Authorized Manufacturing Company**  
919 Wyckoff Ave., Brooklyn 27, N. Y.

section; at this point all that we must know about the process is that two artificially produced carriers of the same frequency (3.58 mc) but displaced in phase by 90° may be modulated by the color-difference signals. This process permits two separate and distinct sets of AM sidebands to be transmitted on the same carrier frequency without interfering with each other.

Since the individual color-difference signals modulate two carriers displaced in phase by 90° the phase relations between the resulting signals are as shown in Fig. 10A. Observe that the new red and blue color-difference signals now take up definite right angle positions with respect to each other. Just as the red and blue color difference signals take up a definite angle with respect to each other, it can be shown that all color signals assume certain phase angles with respect to each other depending on the color or hue of the signal. In this manner, any color may be identified by the phase it has compared to a reference color signal to which we may arbitrarily assign zero reference phase. In Fig. 10A zero phase corresponds to  $E_R - E_Y$ .

As an example of the above let us assume that a saturated red bar is being scanned. Then,  $E_G$  and  $E_B = 0$ ; and assuming relative values,  $E_R$  and  $E_Y$  become:

$$E_R = 1$$

$$E_Y = .3 \text{ (recalling that the matrix is set so that } E_Y = .3E_R + .59E_G + .11E_B\text{).}$$

Under these conditions the relative color-difference signal amplitudes become equal to:

$$E_R - E_Y = -.3$$

$$E_R - E_Y = .7$$

For these values (referring to Fig. 10A and 10B) the new color-difference signal amplitudes are:

$$R_{CD} = .877 (E_R - E_Y)$$

$$= .877 \times .7 = .614$$

$$B_{CD} = .493 (E_R - E_Y)$$

$$= .493 \times -.3 = -.148$$

The resultant of these two values shown in Fig. 10B corresponds to a pure red signal of maximum brightness. Notice that the phase displacement of the red signal is 13° to the left of the red color-difference signal zero phase position.

By a similar analysis all of the other colors may be shown to have definite positions with reference to  $E_R - E_Y$ . This is illustrated in Fig. 11 for some of the major colors. Thus, a red signal is displaced 13° from the reference axis; a green signal  $180^\circ - 29^\circ = 151^\circ$ ; and a blue signal  $180^\circ - 79^\circ = 101^\circ$ . Notice that the colors red, blue and green and magenta are displaced 180° from their complementary colors, cyan, yellow and magenta.

[To be continued]

**SAVE!**  
with  
*Columbia*  
**PLASTIC INSULATED HOOKUP WIRE**



**SAVE!**

Save time by conveniently having the hookup wire you need on service calls. Buy this hookup wire at one cost per spool no matter what gauge or type.

**SAVE!**

Obtain attractive, re-usable, durable metal spools at no cost. Spools can be utilized after wire on spool is used up.

**SAVE!**

Minimize service problems by carrying the hookup wire with ten different colors for each gauge . . . easier to find, easier to use, better to work with.

**ORDER FROM YOUR JOBBER TODAY!** Illustrated catalog is available. Write today.

Watch for Columbia's new packaging of Television Cable!

*Columbia*

**WIRE & SUPPLY CO.**

2850 Irving Park Road • Chicago 18, Ill.  
"America's Most Complete Wire Line"

**NEW! EICO**  
**FLYBACK & YOKE**  
**TESTER KIT**



MODEL  
 944


LOWEST  
 PRICED  
 KIT  
 \$23.95  
 Wired  
 \$34.95

Checks all flybacks & yokes  
 instantly—in or out of set!

- Detects even 1 shorted turn!
- Exclusive separate calibration for air & iron-core flybacks for accurate testing of all types.
- Tests continuity of coils, speakers, switches, etc.
- Large 4½" meter, 3 colored scales.
- Complete with easy Instructions.
- Compact, rugged, smartly styled.

See it at your jobber today. Write for FREE Catalog D-10 describing EICO's 38 Kits and 42 Wired Instruments. Prices 5% higher on West Coast.

**EICO** ELECTRONIC INSTRUMENT CO., Inc.  
 84 Withers Street, Brooklyn, N. Y.  
 © 54

**FREE** 

**1955**  
**308-PAGE**  
**ALLIED**  
**ELECTRONIC**  
**SUPPLY**  
**CATALOG**

Send for it

Everything in Electronics  
 For Service Technicians and Engineers

Get the complete, up-to-date 1955 ALLIED Catalog. It's packed with the world's largest selection of TV and radio parts and accessories, test instruments, Hi-Fi systems and components. P. A. systems, tubes, tools—everything for service work and industrial electronic application. Depend on ALLIED for fast shipment from the world's largest stocks—save time and money. Send today for your FREE 308-page ALLIED Catalog.

ALLIED RADIO CORP., Dept. 26-K-4  
 100 N. Western Ave., Chicago 80, Ill.

Send FREE 1955 ALLIED Catalog

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

**Advertising  
 Index**


|   |         |
|---|---------|
| Acme Electric Corp.....                         | 59      |
| Aerovox Corporation.....                        | 61      |
| Allied Radio Corp.....                          | 64      |
| American Scientific Development Co..            | 61      |
| Authorized Manufacturing Co.....                | 63      |
| Belden Manufacturing Co.....                    | 19      |
| Blonder-Tongue Laboratories, Inc.....           | 20      |
| Bussmann Manufacturing Co.....                  | 36      |
| CBS-Hytron .....                                | 17      |
| Channel Master Corp.....                        | 2, 3    |
| Chicago Standard Transformer Corp..             | 57      |
| Clear Beam Antenna Corp.....                    | 56      |
| Columbia Wire & Supply Co.....                  | 63      |
| Crosley Div., Avco Mfg. Co.....                 | 13      |
| Electronic Instrument Co., Inc.<br>(EICO) ..... | 64      |
| General Cement Mfg. Co.....                     | 62      |
| Hycon Mfg. Co.....                              | 18      |
| Jensen Industries.....                          | 64      |
| Jensen Manufacturing Co.....                    | 6       |
| JFD Manufacturing Co., Inc.....                 | 7       |
| Merit Coil & Transformer Corp.....              | 4       |
| Ohmite Manufacturing Co.....                    | 52      |
| Oxford Electric Corp.....                       | 64      |
| Philco Corporation .....                        | 24, 25  |
| Precision Apparatus Co., Inc.....               | Cover 3 |
| Radiart Corporation .....                       | 49      |
| Radio City Products Co., Inc.....               | 9       |
| Raytheon Manufacturing Co.....                  | 8       |
| RCA Batteries.....                              | Cover 4 |
| Rider, John F. Publisher.....                   | 53, 58  |
| Sams, Howard W. & Co.....                       | 60      |
| Sangamo Electric Company.....                   | 20      |
| Simpson Electric Company .....                  | 31      |
| Snyder Manufacturing Co.....                    | Cover 2 |
| Sylvania Electric Products Inc.....             | 33      |
| Trio Manufacturing Co.....                      | 21      |
| Tung-Sol Electric, Inc.....                     | 54, 55  |
| University Loudspeakers, Inc.....               | 12      |
| Walco .....                                     | 60      |
| Walsco Electronics Corp.....                    | 26      |
| Weston Elec. Instrument Corp.....               | 51      |



*"Since I got this Hi-Fi rig  
 with a JENSEN NEEDLE,  
 business is jumping."*

**Preferred for  
 Original Equipment  
 Proven for  
 Replacement**

**OXFORD**

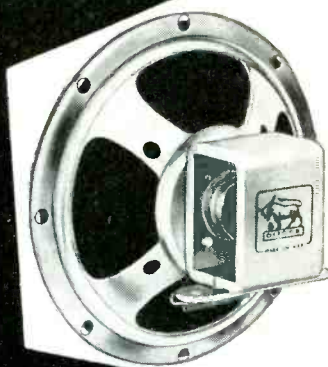

**Speakers**

Available from leading jobbers!

**OXFORD ELECTRIC CORP.**

3911 S. Michigan Ave., Chicago 15, Ill.

EXPORT: ROBURN AGENCIES, N.Y.C., N.Y.

In Canada: Atlas Radio Corp., Ltd., Toronto




**RADIO-TELEVISION SERVICE DEALER  
COMPLETE TV SERVICE INFORMATION SHEETS**

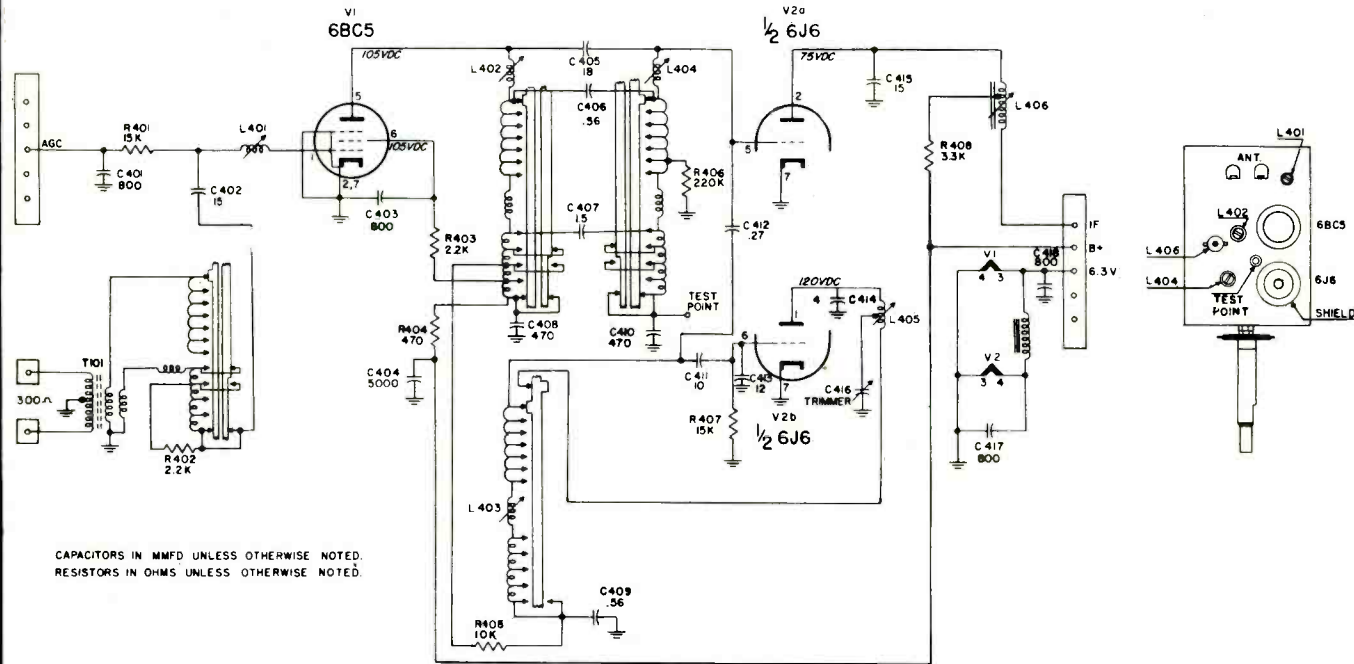**CBS-COLUMBIA**


Models 17M06, 22C06, 22C38  
Chassis 750-3, 751-3

An exclusive service of Cowan Publishing Corp. by special arrangement with John F. Rider, Publisher




CAPACITORS IN MMFD UNLESS OTHERWISE NOTED.  
RESISTORS IN OHMS UNLESS OTHERWISE NOTED.


TUNER SCHEMATIC & TUBE LOCATION

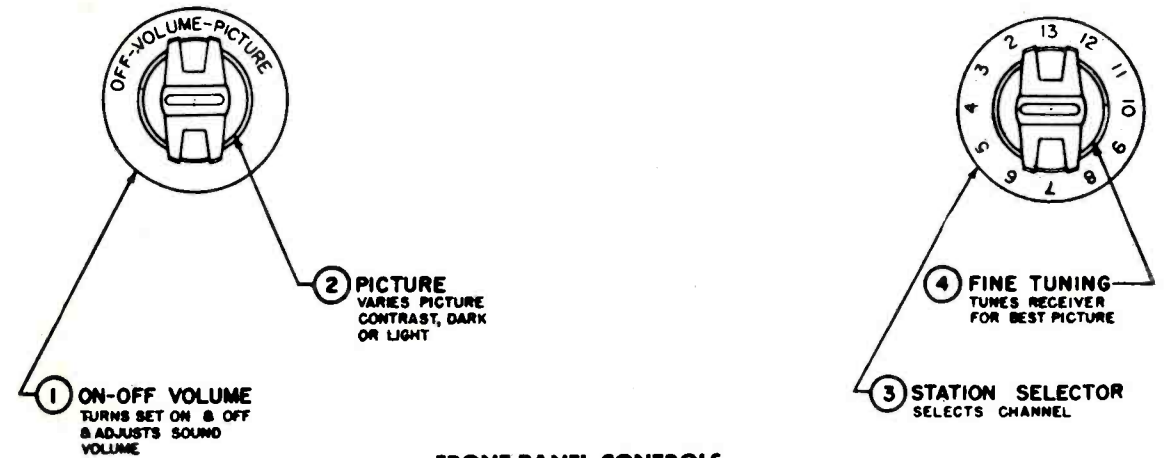


FRONT PANEL CONTROLS

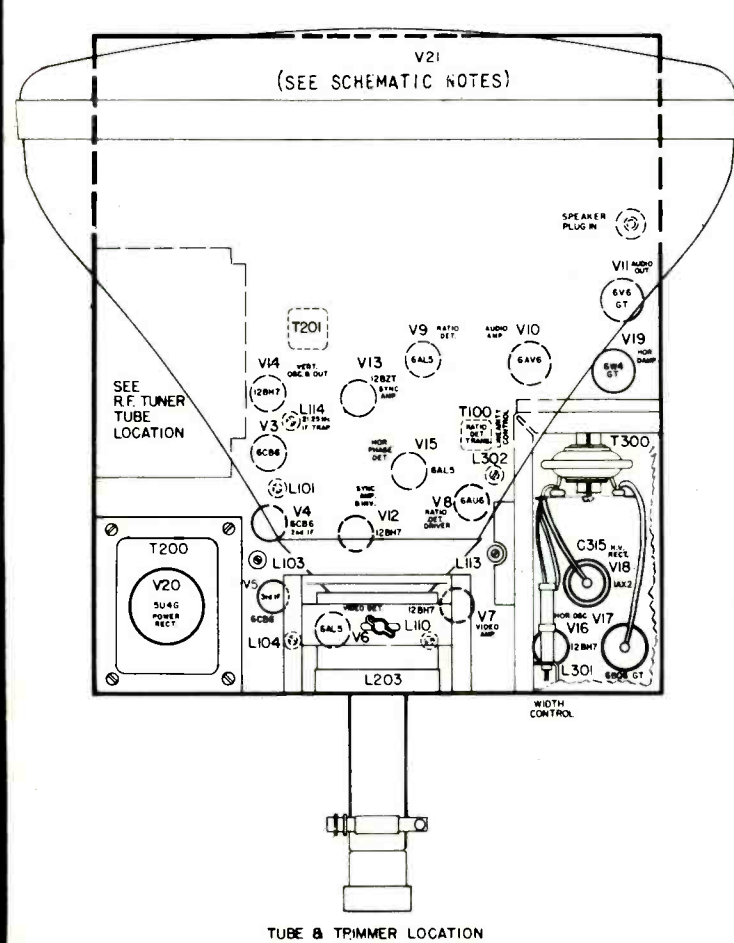

TUBE & TRIMMER LOCATION

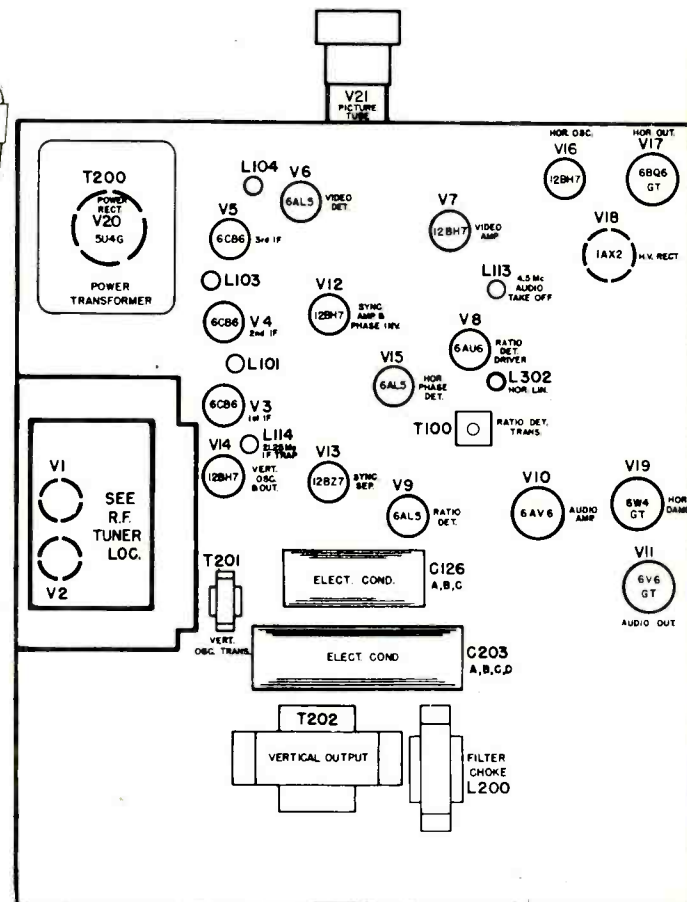

BOTTOM VIEW

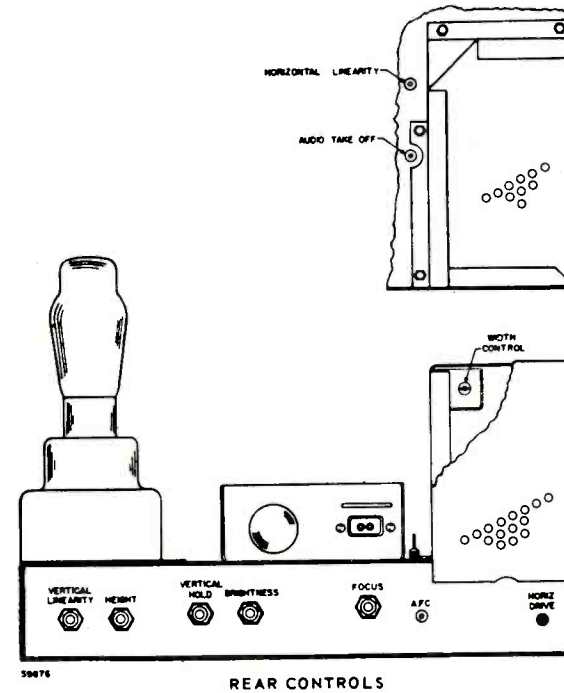

REAR CONTROLS

- CABINET  
SAFETY GLASS  
GLASS-RET. CLIP  
RET. CLIP LOCKING SPRING  
MASK  
BACK COVER  
SPEAKER  
KNOB, CHANNEL SELECTOR (VHF)  
KNOB, CHANNEL SELECTOR (VHF & UHF)  
KNOB, ON-OFF-VOLUME  
KNOB, PIX CONTROL  
KNOB VERNIER  
INDICATOR DISC (UHF)

| MODEL 17M06          | MODEL 22C06   | MODEL 22C38    |
|----------------------|---------------|----------------|
| A60215               | A60201        | A60201         |
| A62457-23            | A62457-25     | A62457-25      |
| A62466 or A6205      | A -           | -              |
| A541440 or w/ A62466 | -             | -              |
| A62470               | A62481        | A62481         |
| A62329               | A62483-2      | A62495         |
| A5866 - 5" PM        | A5124 - 8" PM | A58124 - 8" PM |
| A39281-2             | A39281-2      | A39281-2       |
| A39277-2             | A39277-2      | A39277-2       |
| A39280-2             | A39280-2      | A39280-2       |
| A39279               | A39279        | A39279         |
| A39278               | A39278        | A39278         |
| A40152               | A40152        | A40152         |

**TELEVISION ALIGNMENT PROCEDURE**

Aligning a television receiver is an exacting procedure and involves the use of bench space, test equipment and skilled personnel at the service shop, as well as the cost of making two trips to the customer's home. Before deciding that the chassis must be pulled and aligned at the shop, the serviceman should check these very common sources of trouble:

- 1 - The antenna and installation.
- 2 - Front panel and rear chassis controls, including picture tube adjustments.
- 3 - Reception on all available channels.
- 4 - Tube failures. Substitute from your kit of known good replacements.
- 5 - Visual inspection of underside of chassis for obvious faults, such as loose connections, etc.

**TEST EQUIPMENT REQUIRED FOR ALIGNMENT**

The equipment specified below is desirable, but in cases where this equipment is not available, it is possible to align the receiver by use of a 20 to 30 mc. modulated r-f signal generator, using the picture and speaker as indication of alignment.

- 1 - Signal Generator with an output variable between 100 and 100,000 microvolts, and crystal controlled or crystal-calibrated at the following frequencies:
  - a- 4.5 megacycles
  - b- 22.8 megacycles
  - c- 25.4 megacycles
  - d- 21.25 megacycles

- 2 - DC Vacuum Tube Voltmeter with 5 volt and 10 volt scales.
- 3 - A pair of balanced ( $\pm 1\%$ ) 100K carbon resistors.

**TEST EQUIPMENT**

**REQUIRED FOR SWEEP ALIGNMENT CHECK**

- 1 - R-F sweep generator with frequencies ranging from 40 to 220 megacycles, having sweep width of approximately 10 megacycles, and having adjustable output to approximately 0.1 volt.
- 2 - Crystal-controlled or crystal-calibrated markers for the picture and sound carriers of each channel.
- 3 - Cathode Ray Oscilloscope with good low frequency response.

**CAUTION: THE SECOND ANODE LEAD TO THE PICTURE TUBE HAS A HIGH POTENTIAL. DURING THIS ALIGNMENT IT IS ADVISABLE TO REMOVE THE HORIZONTAL OUTPUT TUBE FROM ITS SOCKET, THUS ELIMINATING THIS HIGH VOLTAGE HAZARD.**

**I.F. ALIGNMENT PROCEDURE**

- 1 - Connect "high" lead of signal generator to the test point located on the top of the RF tuner unit (Refer to the R-F tuner location diagram located on inside of cabinet). Connect ground to chassis.

- 2 - Connect DC VTVM lead (through 10K isolating resistor) to 4.7K diode load resistor (R113); ground to chassis. Set VTVM to 5 volt scale, negative polarity.
- 3 - Set I.F. generator to 25.4 megacycles with sufficient output to read approximately 3 volts on the VTVM.
- 4 - Carefully adjust L101 and L104 (see tube and tuner location) for maximum deflection on VTVM. Adjust sweep generator output to keep meter reading approximately 3 volts.
- 5 - Set I.F.-signal generator to 22.8 megacycles with sufficient output to read approximately 3 volts on the VTVM.
- 6 - Carefully adjust L406, L103 (see tube and tuner location) for maximum deflection on VTVM. Adjust signal generator output to keep meter reading approximately 3 volts.
- 7 - Set I.F. signal generator to 21.25 megacycles, set VTVM to 10 volt scale (negative polarity), and adjust signal generator output for convenient deflection on VTVM.
- 8 - Adjust L114 for minimum deflection on VTVM.

**SWEEP ALIGNMENT CHECK**

Although not essential, a sweep alignment check is a desirable verification of good R-F and I.F. response. Proceed as follows:

- 1 - Connect R-F sweep generator to antenna terminals (antenna impedance 300 ohms.)
- 2 - Calibrate oscilloscope for convenient 5 volts peak-to-peak vertical deflection (5 volts peak-to-peak is approximately 1/4 of the peak-to-peak voltage of the 6.3V A.C. filament).
- 3 - Connect vertical input of oscilloscope (through 10K isolating resistor) to 4.7 diode load resistor (R113); ground to chassis. Connect horizontal input of oscilloscope to "scope" terminals of R-F generator; adjust for convenient horizontal sweep.
- 4 - Set R-F sweep generator to channel 3, television receiver to channel 3, and if necessary, adjust sweep generator output, sweep width, and scope horizontal setting for convenient band-pass display having 5 volts vertical deflection as previously calibrated. (If you must touch scope vertical settings during these adjustments recalibrate scope for 5 volts peak-to-peak as in step 2 above).
- 5 - Couple crystal-controlled R-F carrier markers very loosely to antenna terminals, adjust receiver FINE TUNING control till video carrier marker is 1/2 down on curve. Turn up marker output till R-f sound carrier is visible on bandpass and adjust sound trap (L114) to minimize effect of sound carrier marker.
- 6 - Check all channels as above.

**SOUND ALIGNMENT**

- 1 - Connect 4.5 megacycle signal generator to pin 2 of 12BH7 (V7) video amplifier.

- 2 - Connect DC V.T.V.M. lead to pin 7 of 6AL5 (V9) ratio detector, negative polarity.
- 3 - Adjust signal generator to precisely 4.5 megacycles; adjust output to read approximately 5 volts on V.T.V.M.
- 4 - Adjust L113 and bottom of T100 for maximum deflection on V.T.V.M. Keep V.T.V.M. reading below 10 volts at all times.
- 5 - Attach two series-connected 100K ( $\pm 1\%$ ) resistors across R126 (Ratio Detector Load Resistor). Connect DC V.T.V.M. to center-tap of 100K resistors, and connect ground wire of V.T.V.M. to junction of C119 and C120 (Audio Take-Off of T100).
- 6 - Adjust top of T100 for zero reading on V.T.V.M. between a plus and a minus peak.

**VIDEO AMPLIFIER TRAP**

When necessary, the video amplifier 4.5 mc trap (L110) should be adjusted as follows:


- 1 - Connect 4.5 mc signal generator "high" lead to picture tube grid; ground to chassis.
- 2 - Connect DC V.T.V.M. to pin 7 of 6AL5 (V9) ratio detector, 10 volt scale, negative polarity.
- 3 - Adjust L110 for minimum deflection on V.T.V.M.

**R-F OSCILLATOR**

If all channels are not within range of FINE TUNING control, adjust two screws located in front of r-f tuner unit for adjustment of either low or high band. **CAUTION:** Do not touch adjustments on top of r-f tuner unit, other than converter plate coil, L404, during IF Alignment.

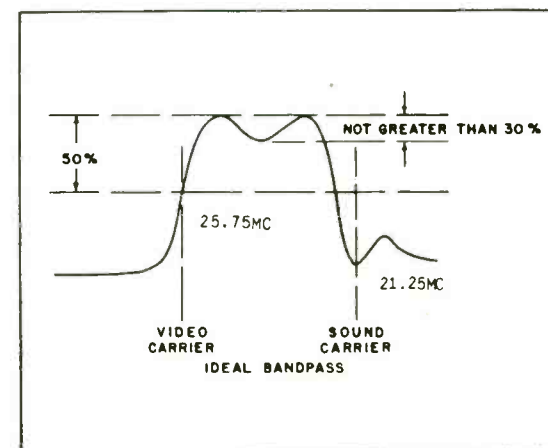**HORIZONTAL OSCILLATOR ALIGNMENT**

If the Horizontal Hold control fails to maintain sync, the horizontal oscillator should be reset. To reset this screwdriver adjustment, set the horizontal hold control in the center of its range and sync the picture with the horizontal A.F.C. adjustment screw. Check the hold control action on various channels and alter the screw adjustment as required to provide sync on all channels.



**DEFLECTION YOKE, ION TRAP AND FOCUS ADJUSTMENT**

Following is the proper procedure for adjusting the Deflection Yoke, Ion Trap and Focus.

The receiver should be turned on but not connected to an antenna. These steps should then be taken in the following order:

- 1 - The Deflection Yoke should be moved as far forward as possible on the neck of the CRT.
- 2 - The Brightness control should be turned to maximum (clockwise) and the Contrast control should be turned to minimum (counterclockwise).
- 3 - The Ion Trap should be rotated and at the same time moved forward and backward to find the position which produces the brightest raster on screen.
- 4 - The Deflection Yoke should be rotated so that the top and bottom edges of the raster are parallel to the top of the chassis.
- 5 - The Brightness control should now be reduced (ccw) to a point where the raster is slightly above normal brilliance.
- 6 - With Brightness and Contrast controls at normal positions, adjust the Focus control (rear of chassis) for well-defined scanning lines.

**HEIGHT, WIDTH AND LINEARITY**

To adjust the overall size and linearity of the picture it is almost mandatory that a test pattern transmitted from a local station be used. It should also be remembered that in areas where more than one station is being received, that pictures transmitted from different stations will vary slightly in size. The smallest transmitted picture should be made to fill the area outlined by the mask.

The Width control (rear of H.V. cage) should be adjusted to give a picture that will fill the mask horizontally.

The Height and Vertical Linearity controls (both rear of chassis) should then be adjusted for a linear picture that will fill the mask vertically.

**PICTURE TUBE HANDLING PRECAUTIONS**

The picture tube encloses a high vacuum and with the large surface area of glass involved, the stresses set up, particularly at the front rim of the tube, are considerable. An abnormal handling stress, accidental blow at a highly stressed surface, or even a scratch on the surface of the tube could cause it to implode or collapse with destructive violence.

**HIGH VOLTAGE WARNING**

Operation of this receiver outside the cabinet or with covers removed involves a shock hazard from the receiver power supplies. Work on the receiver should not be attempted by anyone who is not thoroughly familiar with the precautions necessary when working on high voltage equipment.



**RADIO-TELEVISION SERVICE DEALER  
COMPLETE TV SERVICE INFORMATION SHEETS**

**CBS - COLUMBIA**

Models 17M06, 22C06, 22C38  
Chassis 750-3, 751-3

An exclusive service of Cowan Publishing Corp. by special arrangement with John F. Rider, Publisher

Set No. 2 - Page 3 CBS-Columbia

| RESISTORS   |                   |  |
|-------------|-------------------|--|
| SCHEM. LOC. | CHASSIS* PART NO. | DESCRIPTION                                |
| R100        | PE231-1163        | Carbon, 3900 Ohm 1/2W ±10%                 |
| R101        | PE231-1113        | Carbon, 33 Ohm 1/2W ±10%                   |
| R102        | PE231-1137        | Carbon, 330 Ohm 1/2W ±10%                  |
| R103        | PE231-1179        | Carbon, 18K ohm 1/2w ±10%                  |
| R104        | PE231-1117        | Carbon, 47 Ohm 1/2W ±10%                   |
| R105        | PE231-1123        | Carbon, 82 Ohm 1/2W ±10%                   |
| R106        | PE231-1167        | Carbon, 5600 ohm 1/2w ±10%                 |
| R107        | PE231-1133        | Carbon, 220 Ohm 1/2W ±10%                  |
| R108        | PE231-1133        | Carbon, 220 Ohm 1/2W ±10%                  |
| R109        | PE231-1129        | Carbon, 150 Ohm 1/2W ±10%                  |
| R110        | PE231-1197        | Carbon, 100k Ohm 1/2W ±10%                 |
| R111        | PE231-1177        | Carbon, 15k Ohm 1/2W ±10%                  |
| R112        |                   |  |
| R113        | PE231-1165        | Carbon, 4700 Ohm 1/2W ±10%                 |
| R114        | PE231-1133        | Carbon, 220 Ohm 1/2W ±10%                  |
| R115        | PE231-1165        | Carbon, 4700 Ohm 1/2W ±10%                 |
| R116        | PE232-1161        | Carbon, 3300 Ohm 1W ±10%                   |
| R117        | PE231-1221        | Carbon, 1.0 Megohm 1/2W ±10%               |
| R118        | PE231-1131        | Carbon, 180 Ohm 1/2W ±10%                  |
| R119        |                   |  |
| R120        | PE233-74          | Carbon, 11k Ohm 2W ±5%                     |
| R121        | PE233-1179        | Carbon, 18k Ohm 2W ±10%                    |
| R122        | PE231-1173        | Carbon, 10k Ohm 1/2W ±10%                  |
| R123        | PE231-1197        | Carbon, 100k Ohm 1/2W ±10%                 |
| R124        | PE231-1197        | Carbon, 100k Ohm 1/2W ±10%                 |
| R125        | PE231-1155        | Carbon, 1800 Ohm 1/2W ±10%                 |
| R126        | PE231-1189        | Carbon, 47k Ohm 1/2W ±10%                  |
| R127        | PE231-1245        | Carbon, 10 Megohm 1/2W ±10%                |
| R128        | PE231-1213        | Carbon, 470k Ohm 1/2W ±10%                 |
| R129        | PE231-1213        | Carbon, 470k Ohm 1/2W ±10%                 |
| R130        | PE232-1137        | Carbon, 330 Ohm 1W ±10%                    |
| R131        | PC21134-4         | Wirewound, 3250 Ohm 7W ±10%                |
| R136        | PE231-1173        | Carbon, 10k Ohm 1/2W ±10%                  |
| R139        | PE231-1215        | Carbon, 560K ohm 1/2w ±10%                 |
| R140        | PE231-1187        | Carbon, 39K ohm 1/2w ±10%                  |
| R200        | PE23151           | Wirewound, 1.2 Ohm 1W ±10%                 |
| R201        | PC21134-2         | Wirewound, 60 Ohm 10W ±10%                 |
| R202        | PE231-1183        | Carbon, 27k Ohm 1/2W ±10%                  |
| R203        | PE231-1175        | Carbon, 12k Ohm 1/2W ±10%                  |
| R204        | PE231-1193        | Carbon, 68k Ohm 1/2W ±10%                  |
| R205        | PE231-1213        | Carbon, 470k Ohm 1/2W ±10%                 |
| R206        | PE231-1229        | Carbon, 2.2 Megohm 1/2W ±10%               |
| R207        | PE231-1229        | Carbon, 2.2 Megohm 1/2W ±10%               |
| R208        | PE232-1181        | Carbon, 22k Ohm 1W ±10%                    |
| R209        | PE231-1221        | Carbon, 1.0 Megohm 1/2W ±10%               |
| R210        | PE231-1171        | Carbon, 8200 Ohm 1/2W ±10%                 |
| R211        | PE231-1181        | Carbon, 22k Ohm 1/2W ±10%                  |
| R212        | PE231-1221        | Carbon, 1.0 Megohm 1/2W ±10%               |
| R213        | PE231-1159        | Carbon, 2700 Ohm 1/2W ±10%                 |
| R214        | PE231-1163        | Carbon, 3900 Ohm 1/2W ±10%                 |
| R215        | PE231-1163        | Carbon, 3900 Ohm 1/2W ±10%                 |
| R217        | PE231-1169        | Carbon, 6800 Ohm 1/2W ±10%                 |
| R218        | PE232-127         | Carbon, 1.8 Megohm 1W ±5%                  |
| R219        | PE231-1189        | Carbon, 47k Ohm 1/2W ±10%                  |
| R220        | PE231-1213        | Carbon, 470k Ohm 1/2W ±10%                 |
| R221        | PE231-1225        | Carbon, 1.5 Megohm 1/2W ±10%               |
| R222        | PE231-1155        | Carbon, 1800 Ohm 1/2W ±10%                 |
| R225        | PE233-1161        | Carbon, 3300 Ohm 2W ±10%                   |
| R226        | PE233-1161        | Carbon, 3300 Ohm 2W ±10%                   |
| R227        | PE231-1229        | Carbon, 2.2 Megohm 1/2W ±10%               |
| R228        | PE231-1185        | Carbon, 33k Ohm 1/2W ±10%                  |
| R229        | PE231-1207        | Carbon, 270k Ohm 1/2W ±10%                 |
| R230        | PE231-1221        | Carbon, 1.0 Megohm 1/2W ±10%               |
| R231        | PE231-1181        | Carbon, 22k Ohm 1/2W ±10%                  |
| R232        | PE231-1181        | Carbon, 22k Ohm 1/2W ±10%                  |
| R233        | PE231-1171        | Carbon, 8200 Ohm 1/2W ±10%                 |
| R234        | PE231-1189        | Carbon, 47k Ohm 1/2W ±10%                  |
| R236        | PE232-1205        | Carbon, 220K ohm 1w ±10%                   |
| R300        | PC21134-16        | Wirewound, 2250 Ohm 15W ±10%               |
| R301        | PE233-1165        | Carbon, 4700 Ohm 2W ±10%                   |
| R302        | PE233-1169        | Carbon, 6800 Ohm 2W ±10%                   |
| R303        | PE231-1197        | Carbon, 100k Ohm 1/2W ±10%                 |
| R304        | PE231-1197        | Carbon, 100k Ohm 1/2W ±10%                 |
| R305        | PE231-1213        | Carbon, 470k Ohm 1/2W ±10%                 |
| R306        | PE231-1233        | Carbon, 3.3 Megohm 1/2W ±10%               |
| R307        | PE232-1181        | Carbon, 22k Ohm 1W ±10%                    |
| R308        | PE231-1167        | Carbon, 5600 Ohm 1/2W ±10%                 |
| R309        | PE231-1155        | Carbon, 1800 Ohm 1/2W ±10%                 |
| R310        | PE231-1205        | Carbon, 220k Ohm 1/2W ±10%                 |
| R311        | PE231-1213        | Carbon, 470k Ohm 1/2W ±10%                 |
| R312        | PE231-1197        | Carbon, 100k Ohm 1/2W ±10%                 |
| R313        | PE231-1123        | Carbon, 82 Ohm 1/2W ±10%                   |
| R314        | PE233-1133        | Carbon, 220 Ohm 2W ±10%                    |
| R315        | PE23163           | Carbon, 0.56 Ohm 1/2W ±10%                 |
| R316        | 751-3 PE233-2321  | Carbon, 1.0 Megohm 2W ±20% (Allen Bradley) |
| R317        | 750-3 PE231-1171  | Carbon, 8200 Ohm 1/2W ±10%                 |
| R318        | PE232-1177        | Carbon, 15k Ohm 1W ±10%                    |
| R319        | 750-3 PE231-1109  | Carbon, 22 Ohm 1/2W ±10%                   |
| R319        | 751-3 PE231-1117  | Carbon, 47 Ohm 1/2W ±10%                   |
| R320        | 751-3 PE233-1165  | Carbon, 4700 Ohm 2W ±10%                   |

| CAPACITORS  |                   |   |
|-------------|-------------------|---|
| SCHEM. LOC. | CHASSIS* PART NO. | DESCRIPTION                                 |
| C100        | PE190-133         | Mica, 270mmf 500V ±10%                      |
| C101        | PA19147           | Ceramic, Shielded Dual Disc, 1500mmf GMV    |
| C102        | PE556-234         | Ceramic Tubular, 680mmf 350V ±10% (Insul.)  |
| C103        | PE190-133         | Mica, 270mmf 500V ±10%                      |
| C104        | PE190-133         | Mica, 270mmf 500V ±10%                      |
| C105        | PA19148           | Ceramic, Single Disc 1500mmf GMV            |
| C106        | PA20138           | Electrolytic, 1mfd 50V                      |
| C107        | PP19163           | Ceramic, Shielded Dual Disc 5000mmf GMV     |
| C108        | PE190-140         | Mica, 510mmf 500V ±10%                      |
| C109        | PE190-107         | Mica, 22mmf 500V ±10%                       |
| C110        | PE555-101         | Ceramic Tubular 10mmf. 500V ±20% (Unins.)   |
| C111        | PE555-136         | Ceramic Tubular 1000mmf 350V ±20% (Unins.)  |
| C112        | PE194-160         | Paper, .05mfd 600V ±20%                     |
| C113        | PP19201           | Ceramic Tubular, 820mmf 350V ±10% (Unins.)  |
| C114        | PE555-100         | Ceramic Tubular, 5mmf 500V ±10% (Unins.)    |
| C115        | PE555-113-2       | Ceramic Tubular, 47mmf 500V ±20% NPO        |
| C116        | PE197-160         | Molded Tubular .05mfd 600V ±20%             |
| C117        | PE194-151         | Paper, .005mfd 600V ±20%                    |
| C118        | PA19148           | Ceramic Single Disc 1500mmf GMV             |
| C119        | PE556-236         | Ceramic Tubular, 1000mmf 350V ±10% (Insul.) |
| C120        | PE194-160         | Paper, .05mfd 600V ±20%                     |
| C121        | PA620181          | Electrolytic, 1mfd 100V                     |
| C122        | PE194-156         | Paper, .02mfd 600V ±20%                     |
| C123        | PE194-160         | Paper, .05mfd 600V ±20%                     |
| C124        | PE194-145         | Paper, .001mfd 600V ±20%                    |
| C125        | PE194-151         | Paper, .005mfd 600V ±20%                    |
| C126        | PA20135           | Electrolytic, 10-10-10 mfd 450V             |
| C127        | PE194-145         | Paper, .001mfd 600V ±20%                    |
| C128        | PE555-100         | Ceramic, 5.0mmf 500V ±10% (Uninsul.)        |
| C129        | PA20182           | Electrolytic, 50mfd 25V                     |
| C132        | PE194-145         | Paper, .001mfd 600V ±20%                    |
| C133        | PE556-136         | Ceramic Tubular, 1500mmf 350V ±20% (Insul.) |
| C201        |                   |   |
| C202        | PA19109           | Ceramic, Single Disc 5000mmf GMV            |
| C203        | PA20144           | Electrolytic, 40-40-20-20-mfd 450V          |
| C204        | PA19109           | Ceramic, Single Disc 5000mmf GMV            |
| C205        | PA19109           | Ceramic, Single Disc 5000mmf GMV            |
| C206        | PA19109           | Ceramic, Single Disc 5000mmf GMV            |
| C207        | PE194-156         | Paper, .02mfd 600V ±20%                     |
| C208        | PE190-137         | Mica, 390mmf 500V ±10%                      |
| C209        | PE190-133         | Mica, 270mmf 500V ±10%                      |
| C210        | PE194-155         | Paper, .01mfd 600V ±20%                     |
| C211        | PE194-155         | Paper, .01mfd 600V ±20%                     |
| C212        | PE192-163         | Mica, 4700mmf 500V ±10%                     |
| C213        | PE194-159         | Paper, .035mfd 600V ±20%                    |
| C214        | PE194-156         | Paper, .02mfd 600V ±20%                     |
| C215        | PE194-160         | Paper, .05mfd 600V ±20%                     |
| C216        | PA20174           | Electrolytic, 5mfd 350V (Non-Polarized)     |
| C218        | PE194-160         | Paper, .05mfd 600V ±20%                     |
| C219        | PE194-160         | Paper, .05mfd 600V ±20%                     |
| C220        | PE194-155         | Paper, .01mfd 600V ±20%                     |
| C221        | PE194-151         | Paper, .005mfd 600V ±20%                    |
| C222        | PE194-151         | Paper, .005mfd 600V ±20%                    |
| C223        | PE194-155         | Paper, .01mfd 600V ±20%                     |
| C227        | PA19109           | Ceramic, Single Disc 5000mmf GMV            |
| C300        | PE194-145         | Paper, .001mfd 600V ±20%                    |
| C301        | PE194-145         | Paper, .001mfd 600V ±20%                    |
| C302        | PE197-151         | Molded Tubular .005mfd 600V ±20%            |
| C303        | PE197-151         | Molded Tubular .005mfd 600V ±20%            |
| C304        | PE194-160         | Paper, .05mfd 600V ±20%                     |
| C305        | PE195-261         | Mica, Silver, 3900mmf 500V ±5%              |

| CAPACITORS  |          |           |                                 |
|-------------|----------|-----------|---------------------------------|
| SCHEM. LOC. | CHASSIS* | PART NO.  | DESCRIPTION                     |
| C306        |          | PE190-137 | Mica, 390mmf 500V ±10%          |
| C307        |          | PE190-133 | Mica, 270mmf 500V ±10%          |
| C308        | 750-3    | PE190-125 | Mica, 120mmf 500V ±10%          |
| C308        | 751-3    | PE190-137 | Mica, 390mmf 500V ±10%          |
| C309        |          | PA1772    | Trimmer, 25-280mmf              |
| C310        |          | PA20137   | Electrolytic, 10mfd 25V         |
| C311        | 751-3    | PP19145   | Mica, 5mmf 2500V GMV            |
| C312        |          | PE197-160 | Molded Tubular .05mfd 600V ±20% |
| C313        | 751-3    | PP19146   | Mica, 10mmf 2500V GMV           |
| C314        |          | PE197-160 | Molded Tubular .05mfd 600V ±20% |
| C315        | 751-3    | PA1998-3  | Ceramic, 500mmf 20kv            |
| C316        |          | PE197-162 | Molded Tubular .1mfd 600V ±20%  |
| C317        |          | PA20147   | Electrolytic 25mfd 12V          |
| C318        |          | PP19180   | Mica, 220mmf 1000V ±10%         |
| C320        | 750-3    | PE190-133 | Mica, 270mmf 500V ±10%          |

| CHOKES & COILS |          |          |  |
|----------------|----------|----------|--|
| SCHEM. LOC.    | CHASSIS* | PART NO. | DESCRIPTION                              |
| L101           |          | A3392    | Coil, Pix IF                             |
| L102           |          | A28253   | Choke, RF                                |
| L103           |          | A3392    | Coil, Pix IF                             |
| L104           |          | A3392    | Coil, Pix IF                             |
| L105           |          | A28253   | Choke, RF                                |
| L106           |          | A28255-2 | Coil, Peaking (White)                    |
| L107           |          | A28255-1 | Coil, Peaking (Red)                      |
| L108           |          | A28255-2 | Coil, Peaking (White)                    |
| L109           |          | A28255-1 | Coil, Peaking (Red)                      |
| L110           |          | A28286   | Coil, 4.5 MC. Trap                       |
| L111           |          | A28255-1 | Coil, Peaking (Red)                      |
| L112           |          | A28255-4 | Coil, Peaking (Green)                    |
| L113           |          | A28286   | Coil, 4.5 MC Audio Takeoff               |
| L114           |          | A28314   | Coil, 21.25 MC IF Trap                   |
| L200           |          | A1406    | Coil, Filter Choke                       |
| L201           |          | A28276   | Choke, Filament                          |
| L202           |          | A28276   | Choke, Filament                          |
| L203           | 750-3    | A28328   | Coil, Deflection Yoke                    |
| L203           | 751-3    | A28330   | Coil, Deflection Yoke                    |
| L300           |          | A28263   | Coil, Horiz. Freq. Control               |
| L301           | 750-3    | A28279-1 | Coil, Width Control                      |
| L301           | 751-3    | A28318-1 | Coil, Width Control                      |
| L302           |          | A28292   | Coil, Horiz. Linearity                   |
|                |          | A28331   | Deflection Yoke Cover w/Centering Device |

| TRANSFORMERS |          |               |                     |
|--------------|----------|---------------|---------------------|
| SCHEM. LOC.  | CHASSIS* | PART NO.      | DESCRIPTION         |
| T100         |          | A1201 or 1202 | Ratio Detector      |
| T200         |          | A10109        | Power               |
| T201         |          | A10106        | Vertical Oscillator |
| T202         |          | A10152-1      | Vertical Output     |
|              |          | A10136 or     |                     |
| T300         |          | A10137        | Horizontal Output   |

| CONTROLS    |          |          |                                      |
|-------------|----------|----------|--------------------------------------|
| SCHEM. LOC. | CHASSIS* | PART NO. | DESCRIPTION                          |
| P100        |          | A24142   | Contrast-Volume, 5K-250K ohm         |
| P200        |          | A24112   | Vertical Hold, 1.0 Megohm            |
| P201        |          | A24111   | Vertical Size, 5.0 Megohm            |
| P202        |          | A24114   | Vertical Linearity, 3K ohm Wirewound |
| P204        |          | A24110   | Brightness, 100K ohm                 |
| P206        |          | A24112   | Focus Control, 1.0 Megohm            |

| MISC. CHASSIS ACCESS. & PARTS - ALL CHASSIS |                                       |
|---|---------------------------------------|
| PART NO.                                    | DESCRIPTION                           |
| A65100K                                     | Chassis                               |
| A5355                                       | Shield, H.V. Supply                   |
| A5356                                       | Cover, H.V. Supply Shield             |
| A54609                                      | Bracket, Horiz. Freq. Control Coil    |
| A541059                                     | Bracket, Interlock                    |
| A541242                                     | Grounding Spring CRT Coating          |
| A540-62                                     | Terminal Strip, AAEEAAEAA             |
| A540-67                                     | Terminal Strip, AAEEAA                |
| A540-44                                     | Terminal Strip, AAEEAA                |
| A540-19                                     | Terminal Strip, AEA                   |
| A540-34                                     | Terminal Strip, AEA                   |
| A18155                                      | Socket, Octal Moulded                 |
| A18210                                      | Socket, Octal Moulded Bakelite Saddle |
| A18173                                      | Socket, 9 Pin Moulded                 |
| A18171                                      | Socket, 9 Pin Moulded No Saddle       |
| A18157                                      | Socket, 9 Pin Wafer                   |
| A18147                                      | Socket, 7 Pin Wafer                   |
| A18101                                      | Socket, Speaker-Plug                  |
| A541131                                     | Socket, H.V. Cond.                    |
| A562-6                                      | Capacitor Clips; 1-3/8                |
| A562-3                                      | Capacitor Clips; 3/4                  |
| A54618-1                                    | Tube Shield                           |
| A3206                                       | Ion Trap                              |
| A541341                                     | Anode Lead Holder                     |

| MISC. CHASSIS ACCESS. & PARTS - 17" TUBE |  |
|--|--|
| PART NO.                                 | DESCRIPTION                              |
| A54851                                   | Bracket, Yoke Hood & Support             |
| A541084-1                                | Channel, CRT Front Support; Left         |
| A541084-2                                | Channel, CRT Front Support; Right        |
| A54827                                   | Strap, CRT; Right                        |
| A54828                                   | Strap, CRT; Left                         |
| A541086                                  | Bracket, CRT Stop                        |
| A55141-1                                 | Anode Connector Assembly                 |
| A541085                                  | Cushion, Rubber; CRT Channel             |
| A541110-2                                | Cushion, Sponge Rubber; CRT Strap, Right |
| A541110-1                                | Cushion, Sponge Rubber; CRT Strap, Left  |
| A54971-18                                | Cushion, Cork; CRT Stop Bkt.             |
| A18197-3                                 | Socket, Kinescope                        |

| MISC. CHASSIS ACCESS. & PARTS - 21" CHASSIS |  |
|---|--|
| PART NO.                                    | DESCRIPTION                                      |
| A541251                                     | Bracket, Interlock                               |
| A541248-1                                   | Bracket, CRT Rear Support (Left)                 |
| A541248-2                                   | Bracket, CRT Rear Support (Right)                |
| A541000                                     | CRT Rubber Grommet                               |
| A541246                                     | Bracket, Yoke Hood and CRT Grommet               |
| A541250-1                                   | Bracket, Yoke Hood Support (Left)                |
| A541250-2                                   | Bracket, Yoke Hood Support (Right)               |
| A541383                                     | Bracket, CRT Front Support and Stop              |
| A541249                                     | Bracket, Tie Rod                                 |
| A541254                                     | CRT Strap Assembly                               |
| A541261-1                                   | Rubber Cushion (CRT Front Support and Stop Bkt.) |
| A541261-2                                   | Rubber Cushion (CRT Front Support and Stop Bkt.) |
| A541102-6                                   | Rubber Cushion (CRT Strap)                       |

\*Used on all chassis unless otherwise specified in this column. If specified, the part is used only on the chassis indicated.

John F. Rider








# NOW AT LAST...

## A Reliable, General-Purpose 5" OSCILLOSCOPE

Priced  
at Only **\$127.50**

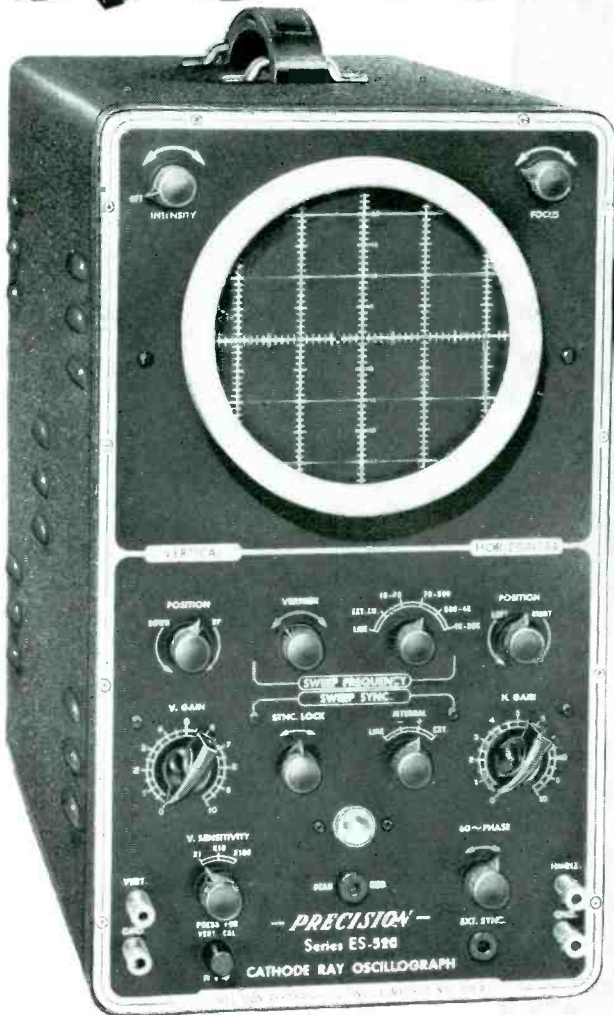

### The NEW **PRECISION** MODEL **ES-520**

The new ES-520 is *PRECISION*-engineered in response to long and growing demand for a reliable, factory-made, general purpose 'scope at a price within reach of all to whom initial investment is of extreme importance.

The ES-520 conforms to every *PRECISION* standard of quality, workmanship and performance. It is a completely factory-engineered, factory-wired and factory-calibrated instrument . . . ready to go to work for you the moment you take it out of its carton!

#### SPECIFICATIONS

- ★ Push-Pull vertical drive. 20 millivolts per inch sensitivity.
- ★ 3-Step, frequency-compensated, vertical input attenuator.
- ★ Vertical frequency response 20 cycles to 500 KC within 2 DB
- ★ 1 volt, peak-to-peak, built-in vertical voltage calibrator.
- ★ Excellent vertical square wave response from 20 cycles to 50 KC.
- ★ Push-pull horizontal drive. 50 millivolts per inch sensitivity.
- ★ 'H' frequency response 20 cps to 200 KC within 3 DB (at full gain).
- ★ Internal linear sweep 10 cycles to 30 KC. Neg. and pos. sweep synch.
- ★ Tube Complement: 12AU7 'V' cathode follower and amplifier, 6C4 phase-splitter, 12AZ7 push-pull 'V' drive. 6AB4 'H' amplifier, 12AZ7 push-pull 'H' drive. 12AU7 sweep oscillator. 6X4 rectifier, 1V2 high potential rectifier, NE-51 calibration regulator, 5U1 CR tube.
- ★ Built-in 60 cycle sine-sweep phasing control.
- ★ Beam modulation input terminal at front of panel.
- ★ All 4 deflection plates directly accessible at rear.
- ★ Filter-type, removable, calibrated graph-screen.
- ★ Etched, anodized, heavy gauge aluminum panel.

**SERIES ES-520:** In black ripple finished, rugged steel cabinet, 8¼ x 14½ x 16½". Complete with all tubes, including 5U1 CR tube. Comprehensive instruction manual. Code: Quest. Shipping weight: 30 lbs. Net Price: \$127.50.

...and STILL THE LEADER IN ITS FIELD  
for performance, versatility and value—  
the popular **PRECISION**



### **ES-500A** HIGH SENSITIVITY WIDE-RANGE 5" OSCILLOSCOPE

The famous ES-500A incorporates advanced engineering features and refinements so necessary to meet the more critical needs of modern electronic circuit analysis, AM, FM and TV.

**SERIES ES-50CA:** in louvered, black ripple-finished, heavy gauge steel case, 8¼ x 14½ x 18". Complete with removable light shield, calibrating mask and detailed instruction manual. Net Price: \$173.70



**PRECISION Apparatus Company, Inc.**  
92-27 HORACE HARDING BLVD., ELMHURST 6, N. Y.

Export Division: 458 Broadway, New York 13, U.S.A. Cables: Morhanex  
Canada: Atlas Radio Corp., Ltd., 560 King Street W., Toronto 2B

**"Strong demand for the RCA brand built my radio battery business**

**227%!"**



**says—CLIFFORD E. PORTER of Arrow Radio Laboratory  
 399 Dorchester Street, South Boston, Massachusetts**

**"BEEN SELLING** batteries for years but when I started to stock and promote the RCA brand, my radio battery business soared. That's a real tribute to RCA Batteries' popularity with portable radio owners," he added.

Pictured with Mr. Porter is Miss Phyllis Brown of Dorchester, Mass. who uses RCA Batteries in her RCA Victor "Super Personal" portable radio.

WITH RCA Batteries as a working partner in your portable radio sales and service business, you'll find profit opportunities you never before enjoyed. Active promotion of your stock of RCA Radio Batteries will establish your store as the portable radio service and battery replacement headquarters in your neighborhood. Once that fact is well known your radio battery business will balloon UPWARD.

To get started today, order a repre-

sentative stock of the ten top-selling RCA Batteries from your RCA Battery Distributor Salesman. When aggressive RCA merchandising techniques are applied to your battery department, you will enjoy a turnover and profit rate greater than ever before.

**Want to read more particulars?** Ask your RCA Distributor for a copy of the new RCA Battery merchandising booklet, "1954 Sales Planner." You'll be glad you did.

**Here's how RCA helps you sell more Radio Batteries**



● NATIONAL TV and RADIO ADVERTISING



● POWERFUL SALES PROMOTION



● COMPLETE LINE



● GREATEST NAME IN RADIO



● RADIO TRADE DISTRIBUTION



**RADIO CORPORATION of AMERICA**  
**RADIO BATTERIES**  
**HARRISON, N. J.**