

Radio-Television SERVICE DEALER

TV - AM - FM - SOUND

Includes

3


Sections

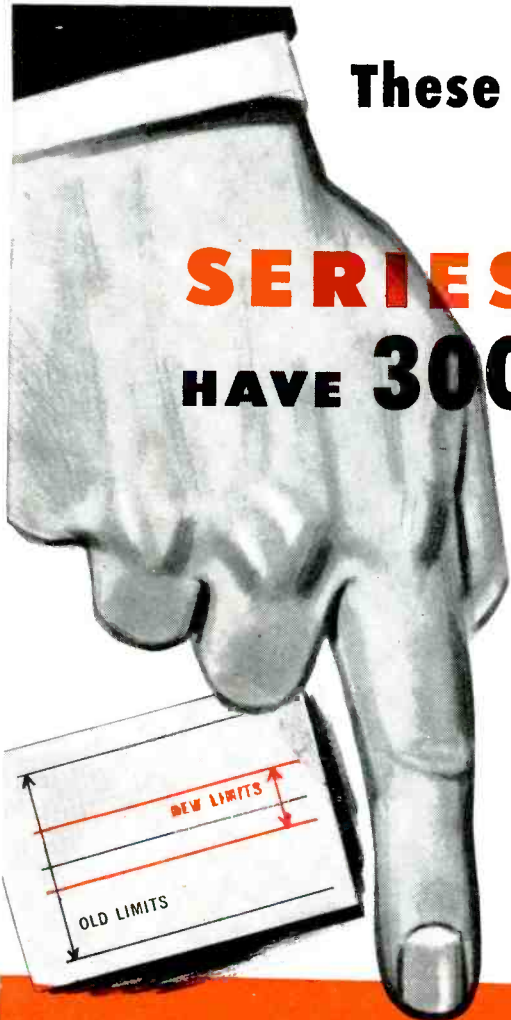1. VIDEO SPEED SERVICING SYSTEMS
2. TV FIELD SERVICE DATA SHEETS
3. COMPLETE TV SERVICE INFORMATION SHEETS



The Professional Radio-TVman's Magazine
Reaching Every Radio TV Service Firm Owner in the U.S.A.





These



SERIES STRING TUBES HAVE 300% GREATER RELIABILITY

High voltage surges due to inequalities of heater warmup time previously have limited the most effective use of "series connections" of tube heaters in TV receivers. The new Raytheon "Series String" Tubes — now used by many leading set manufacturers — virtually eliminate heater burnouts, permitting the use of this type of circuitry which results in lighter, more compact receivers.

Raytheon helped set manufacturers solve this warmup problem, by designing a new line of "Series String" Tubes which feature tightened controls on heater warmup, identical current value and a heater stability so improved that heater burnouts from warmup surges are rare. By narrowing the tolerances on heater wire to one-third of the former specifications and improving heater coating techniques this has been achieved. This important advance plus Raytheon's thorough knowledge of every aspect of tube construction guarantees the superior quality of Raytheon "Series String" Tubes.

<p>RAYTHEON 3AL5 is a heater-cathode type double diode of miniature construction. Its principal application is as a diode detector, automatic volume control rectifier, or as a low current power rectifier.</p>	<p>RAYTHEON 3AU6 is a heater-cathode type, sharp cutoff pentode of miniature construction designed for service as a high-frequency amplifier in radio and television receivers.</p>	<p>RAYTHEON 3BC5 is a heater-cathode type, sharp cutoff pentode, of miniature construction. Used as an RF amplifier and as a high-frequency, intermediate amplifier.</p>	<p>RAYTHEON 3BN6 is a 7-pin miniature, heater-cathode type, sharp cutoff pentode. Designed to perform the combined functions of limiting and frequency discrimination in FM and TV receivers.</p>	<p>RAYTHEON 3CB6 is a heater-cathode type sharp cutoff pentode of miniature construction designed for use as an intermediate frequency amplifier, operating at frequencies in the order of 40 megacycles, or as an RF amplifier in VHF Television Tuners.</p>
<p>RAYTHEON 5AM8 is a diode pentode of miniature construction designed for use as a video detector and IF amplifier in television receivers.</p>	<p>RAYTHEON 5AN8 is a medium-mu triode and a sharp cutoff pentode of miniature construction designed to perform combined functions of a video detector or IF amplifier and sync separator.</p>	<p>RAYTHEON 5J6 is a heater-cathode type, double triode of miniature construction designed for mixer applications.</p>	<p>RAYTHEON 5U8 is a heater-cathode type triode-pentode of miniature construction designed for use as an oscillator mixer.</p>	<p>RAYTHEON 6S4A is a heater-cathode type medium-mu, high-perveance triode of miniature construction for use as a vertical deflection amplifier in TV receivers.</p>
<p>RAYTHEON 6SN7GTB is a dual triode designed for use as a combined vertical oscillator and vertical deflection amplifier in television receivers.</p>	<p>RAYTHEON 7AU7 is a heater-cathode type double triode of miniature construction designed for use as a resistance coupled voltage amplifier, phase inverter, horizontal deflection oscillator or vertical deflection oscillator-amplifier in television receivers.</p>	<p>RAYTHEON 12AX4GTA is a heater-cathode type diode designed for use in Horizontal frequency damper service in television receivers.</p>	<p>RAYTHEON 12BH7A is a heater-cathode type medium-mu double triode of miniature construction designed for use as a vertical deflection amplifier in television receivers employing "Series String" heater designs.</p>	<p>RAYTHEON 12BK5 is a miniature beam power pentode designed for use as a power output tube in radio and TV receivers.</p>
<p>RAYTHEON 12BY7A is a heater-cathode type pentode of miniature construction designed for use as a video amplifier.</p>	<p>RAYTHEON 12L6GT is a heater-cathode type beam pentode power amplifier. Generally used as an output tube in ac-dc receivers.</p>	<p>RAYTHEON 12W6GT is a heater-cathode type beam pentode designed for service as a vertical deflection amplifier in TV receivers having a relatively low B supply voltage.</p>	<p>Ask your Raytheon Tube Distributor about these and other new Raytheon "Series String" Tubes.</p>	



Excellence in Electronics

RAYTHEON MANUFACTURING COMPANY


Receiving and Cathode Ray Tube Operations
Newton, Mass., Chicago, Ill., Atlanta, Ga., Los Angeles, Calif.

RAYTHEON MAKES ALL THESE:

RECEIVING AND PICTURE TUBES • RELIABLE SUBMINIATURE AND MINIATURE TUBES • SEMICONDUCTOR DIODES AND TRANSISTORS • NUCLEONIC TUBES • MICROWAVE TUBES



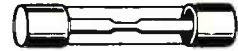Why it's Good Business to Standardize on BUSS FUSES



Manufacturers and service organizations in increasing numbers are standardizing on BUSS fuses because . . . they know, from their own experience, that BUSS fuses give dependable electrical protection under all service conditions.

In fuses, unfailing dependability is so necessary — for the fuse alone protects when there is trouble on the circuit. And just as important, a fuse should never give a "false alarm" by blowing needlessly.

To make sure that BUSS fuses maintain their 40 year old reputation for highest quality, every BUSS fuse normally used by the Electronic Industries is tested in a sensitive electronic device that automatically rejects any fuse not correctly calibrated, properly constructed and right in all physical dimensions.

BUSS fuses sell and stay sold

Buyers readily accept BUSS fuses. The millions and millions of BUSS fuses used in home, farm and industry over the past 40 years have established their reliability and unquestioned high quality. And, of course, the trouble-free service of BUSS fuses means fewer "kicks" and call-backs to cut away profits . . . Your goodwill, reputation and profits are safeguarded when you standardize on genuine BUSS fuses.

Makers of a complete line of fuses for home, farm, commercial electronic and industrial uses.



***For More Information
Mail this Coupon***

BUSSMANN Mfg. Co. (Div. McGraw Electric Co.)
University at Jefferson, St. Louis 7, Mo. S13-1254


Please send me bulletin SFB containing facts on BUSS small dimension fuses and fuse holders.

Name.....Title.....

Company.....

Address.....

City & Zone.....State..... 1254

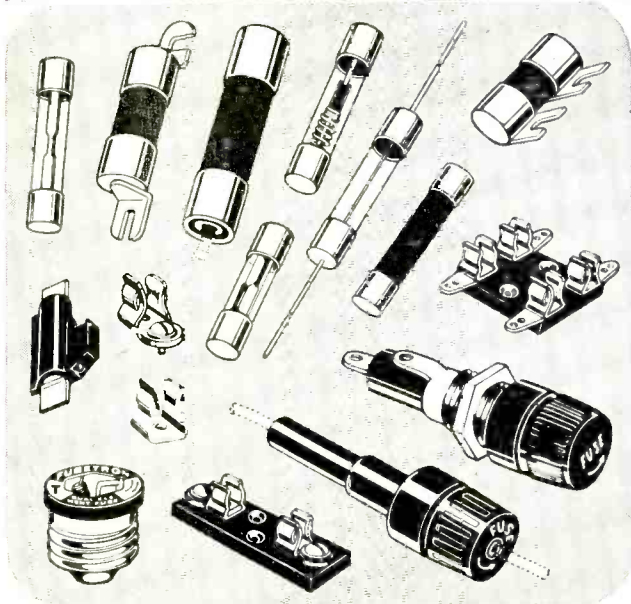




**YOUR ELECTRONIC
EQUIPMENT**
Demands Highly Specialized
WIRE

**THE MANUFACTURERS
AND SERVICE MEN
WHO SERVE BEST**

Specify

Belden

WIREMAKER FOR INDUSTRY

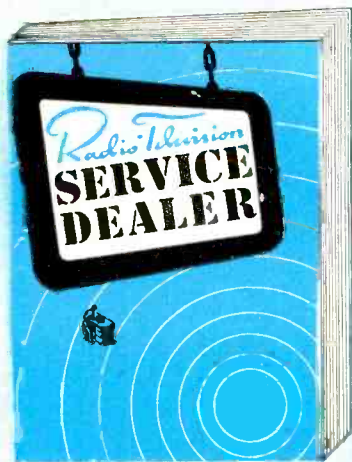

EVERY SERVICE FIRM OWNER IN THE U.S.A. Receives **SERVICE DEALER** Monthly Distribution of this Issue over **67,500**

Member **EPA** —Circulation Statement sent on request

COWAN PUBLISHING CORP., 67 West 44th Street, New York 36, N. Y.

VOL. 15, NO. 12

DECEMBER, 1954

EDITORIAL STAFF

Publisher

SANFORD R. COWAN

Editor

SAMUEL L. MARSHALL

Editorial Production

ROBERT CAMPRELL

Contributing Editors

ROBERT T. DARGAN

PAUL GOLDBERG

SAN D'ARCY

BUSINESS STAFF

Advertising Director

SANFORD L. CAHN

Advertising Manager

HARRY N. REIZES

Advertising Sales

LAWRENCE STEINER

Production Manager

DAVID SALTMAN

Circulation Manager

HAROLD WEISNER

Ass't Circ. Mgr.

C. J. BINDERMAN

BRANCH OFFICES

LOS ANGELES

TED E. SCHELL

2700 West Third Street
Dunkirk 2-4889

CLEVELAND

RICHARD E. CLEARY

Commercial Bank Bldg.

Berea, Ohio

BErea 4-7719

MID-WEST

ED DAMER

333 N. Michigan Avenue

Chicago 1, Illinois

FRanklin 2-7100

FEATURE ARTICLES

- Chrominance Systems in Color TV Receivers, Part 1**
by *Bob Dargan and Sam Marshall* 11
Discussion of signal processing of chrominance signal in Q and I receiver.
- Understanding and Servicing Horizontal Output Transformer Circuits, Part 2**, by *Oscar Fisch* 16
The structure and function of the H.O.T. and trouble-shooting procedures.
- Sectionalized Printed Circuit TV Receiver**,
by *Walsco Electronics Corp.* 19
A unique TV receiver utilizing sectionalized printed circuit units.
- TV Instrument Clinic, Part 6**, by *Robert G. Middleton* 23
Servicing techniques involving identification of complex scope patterns.
- Transistor Portable**, by *Regency* 25
Commercial applications of new components and circuitry continue.
- A New TV Remote Control Unit**, by *Irvin R. Gwitz* 28
Description of a versatile TV remote control unit.
- Applications of Resistive Networks**, by *J. C. Geist* 31
Applications of resistive networks in TV.
- Audio Adaptations for Profitable Servicing**, by *Gil Tint* 32
Practical and profitable suggestions for increasing utility of Hi-Fi systems.
- Sync Amplifier Problems**, by *Paul Goldberg (a Workbench Feature)* 34
The use of the Oscilloscope in troubleshooting these problems.
- Detroit Servicemen's Show**, by *H. Hirt* 36
Distributors stage an unprecedented show for the serviceman.
- TV Service Information Sheets** 65-72
Complete preliminary service data for CBS-Columbia Color TV Receiver, Model 205.

CIRCUIT AND SERVICE FORUM

Answer Man

- G.E. Model 24C101—Ripples in Pattern 27
- Sylvania Chassis I-510-1—Horizontal Drifts 27

The Workbench

- Admiral 21C1—Lack of horizontal and vertical hold 34
- DuMont RA 103C—Vertical roll and horizontal wobble 35
- RCA 630 TS—Pulling at top of pix and vertical slipping 35

Video Speed Servicing Systems

- Majestic 121B 37
- Philco 50-T1600, 51-T1600, etc., Code 121 and 122 39
- RCA KCS 81 41

Rider TV Field Manual Service Data Sheets

- Philco, Code 140, Ch. R191, D191 43
- Stewart Warner, Mod 9132A 45

DEPARTMENTS

Editorial	4	New Products	48
Association News	8	Trade Flashes	50
Answer Man	27	RTSD Annual Index	62
Workbench	34	Advertising Index	64

RADIO-TELEVISION SERVICE DEALER is published monthly by Cowan Pub. Corp., 67 West 44th St., New York 36, N. Y. Subscription price: \$1 for 2 years in the United States, & U.S. Poss. Elsewhere \$1 per year additional. Single Copies 25c. Reentered as second class matter Sept. 26, 1950 at the Post Office at New York, N. Y. under the Act of Mar. 3, 1879. Copyright 1954, Cowan Publishing Corp.

POSTMASTER: SEND FORM 3579 TO RADIO-TELEVISION SERVICE DEALER,
67 WEST 44th ST., NEW YORK 36, N. Y.



EDITORIAL...

by S. R. COWAN
PUBLISHER

Lost Opportunities—Lost Dollars

Having been associated with professional servicemen for over 25 years I fully realize that most are much more service than sales-minded. By that I mean that the average serviceman will tackle with glee any repair job regardless of the difficulty involved whereas only "exceptional" servicemen make it their standard practice to *try* to sell something more than mere service—things like antenna rotators, long-play needles, portable battery sets, or that second TV set for the customer's bedroom.

For example, all servicemen will repair faulty record-players or they will replace defective cartridges whenever a customer *asks* to have such jobs attended to. But, does the *average* serviceman, having finished repairing a receiver, make it his *standard practice* to ask his customer leading, sales-pointed questions such as: "How is your record-player working?" — or: "How about letting me install a new, more efficient TV antenna or rotator so you'll get better reception?" Sorry to say, and practically all of you will concur, the answer is an emphatic NO! The average serviceman simply allows hundreds of potential sales opportunities — and fabulous additional earnings — to slide by him month after month. Let's review this sad condition more fully!

We all know that at present the country is what one could call "phonograph record crazy." With that in mind, during the past two months I have made a thorough market study of the record-player business and its attendant effect upon the earnings of the service profession. My findings will undoubtedly interest all independent servicemen, and particularly service dealers and service firm owners who have one or several technicians on their payrolls. Analyze the following facts carefully:

There are more than 67½ million record players of all types (from radio-phono combinations to portables) *now in general use* in this country. (As there are only 45 million homes, every other home has 2 record-players). Of the 67½ million record-players in use, 40 million are single-speed 78 RPM; 12 million are 2-speed 33 1/3 — 78; 2 million are 2-speed 33 1/3 — 45; 2 million are single-speed 45; and 1½ million are 3-speed 33 1/3 — 45 — 78.

During this year cartridge manufacturers sold to servicemen through parts distributors for replacement use almost 1½ million cartridges. This may not sound like an impressive figure if only

given casual thought, but believe me, it is "peanuts" compared to what sales *might have been* had servicemen *tried* to get more replacement cartridge sales. Over 90% of the cartridges sold by servicemen this year were sold because the record-player owners gave their servicemen instructions to make the replacements. Less than 10% of the cartridges were bought by customers at the instigation of repairmen, or because servicemen "suggested" that they would get more enjoyment from their phonographs thereby.

As the public is record-player conscious, I urge *all* servicemen to get "sales-minded" immediately and from now on "go after" replacement cartridge sales at every opportunity — meaning whenever you have a conversation with any customer. Also, when possible, ascertain if the customer wouldn't like to have his old (and probably obsolete single-play), unit replaced with a modern multi-speed turntable—a new tone arm—new long-play stylus, etc. Try this sales-minded policy in earnest for a while (and have your employed technicians do it too), and within a short time you will increase your earnings by hundreds of dollars, and probably you'll increase your technicians' earnings too, on a profit-sharing basis.

In like manner, it will pay handsomely to "go after" replacement antenna sales, remote-tuning device sales, rotator sales, and the like. If only 1 out of every 10 customers that you and your technicians have contact with becomes a buyer of some supplemental service or accessory, you will not only profit therefrom, but more important, you'll increase the customers' respect and Good Will for you as they will recognize in most cases that you acted as you did with their best interests in mind.

TV Receiver and Station Count

As of Oct. 1st, 1954 in 251 major markets there were 402 TV stations on the air, 112 of them being UHF and 286 VHF. By January 1955 an additional 29 VHF and 28 UHF stations expect to be in operation to give us a grand total of 463.


At this writing statisticians estimate that slightly over 32 million TV sets are in use of which slightly less than 1 million are UHF. An additional 3 million TV sets are on dealers' floors or are in distributors' stocks ready for delivery. There is a normal production-to-sales ratio at present, which is a good sign.



Burton Browne Advertising

THINGS ARE **NOT** AS THEY SEEM...

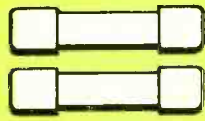Things are not as they seem
These two fuses look alike . . .
Until you look inside.



This is not a spiral. It is a series of concentric circles that do not join.

This fuse has a straight element—cannot be made more delicate than 1/16 amp. with normal blowing characteristics.



This fuse has a bridge construction (note short filament between electrodes). This type fuse may be rated as low as 1/500 amp. with precision blowing characteristics required for protection of extremely fine instruments. Without this construction pioneered by Littelfuse—the microscopically fine filament would break in shipment, in normal operating vibration or even from nearby footsteps.




LITTELFUSE
DES PLAINES, ILLINOIS

Littelfuse leads all other fuse manufacturers in design patents on fuses.

**this great all-channel antenna discovery
is smashing sales and performance records
in every TV area!**

Single bay
SUPER RAINBOW
model no. 331

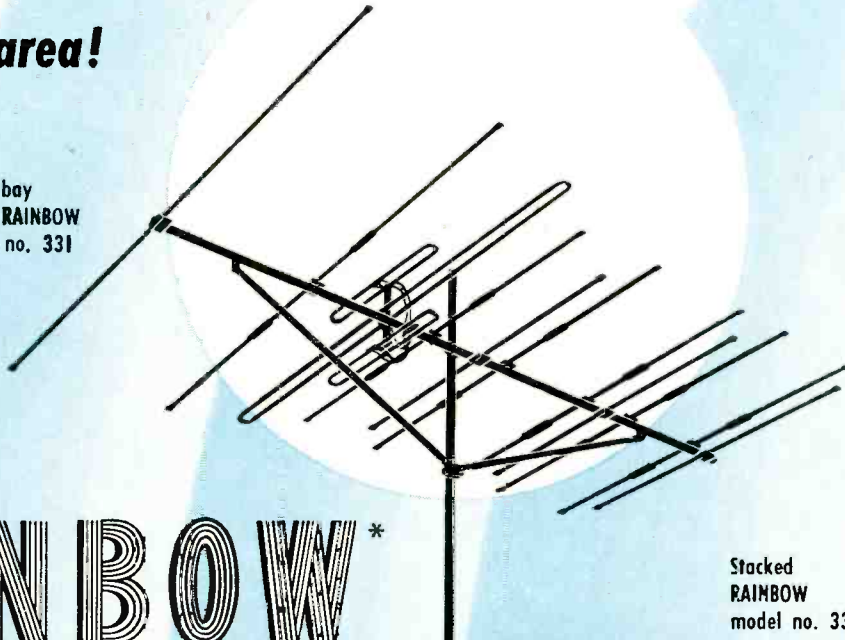

Stacked
RAINBOW
model no. 330-2

the
CHAMPION

RAINBOW*

brilliant black-and-white performance —
and really ready for COLOR!

these 3 revolutionary, power-packed
design features — found in no
other antenna today!


- 1. New spacing formula:** Radical new spacing arrangements between the directors and reflectors has, for the first time, extended the full efficiency and high gain of the basic narrow band Yagi over the *full width* of an entire VHF band.
- 2. New "triple power" High Band directors and reflectors:** Three-section directors and reflectors, with insulated segments, provide combined power of three High Band Yagis, operating side by side, in phase.
- 3. New "inter-mix" design:** Combines — into one single antenna — two separate, *independent* sets of directors and reflectors, one for High Band, one for Low Band. Each parasitic system operates *only* on its own band. Fullest efficiency — no compromise design.
PLUS Channel Master's patented, super-gain TRI-POLE . . . the unique triple-power dipole that made the Champion America's most wanted antenna.

CHANNEL MASTER
*creative
engineering*

Here's how the RAINBOW out-performs the famous Champion:

		CHANNEL	2	3	4	5	6	7	8	9	10	11	12	13
Gain Over 1-Bay Champion	1-Bay RAINBOW	0	0	0	+1	+2	+3	+2.5	+1	+0.5	+0.5	+1.5	+2.5	
	1-Bay SUPER RAINBOW	+1	+1	+1.5	+2.5	+3.5	+3.5	+3	+2	+1.5	+2	+3.5	+4.5	
Gain Over Stacked Champion	Stacked RAINBOW	+1.5	+2	+1.5	+1.5	+2	+1.5	+0.5	+0	+0	+1	+1.5		
	Stacked SUPER RAINBOW	+2	+2.5	+3	+3	+4	+5	+1	+1	+2	+2	+2.5	+3.5	

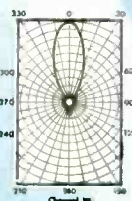horizontal
polar pattern
(relative
voltage)



for fringe and super-fringe areas:

Super Rainbow, model no. 331

\$37⁵⁰ list

stacked Super Rainbow,

model no. 331-2

\$75⁷⁰ list

for suburban and near-fringe areas:

Rainbow, model no. 330


\$23⁶⁰ list

stacked Rainbow, model no. 330-2

\$48⁶⁰ list

Write for complete technical literature

something new in indoor antennas

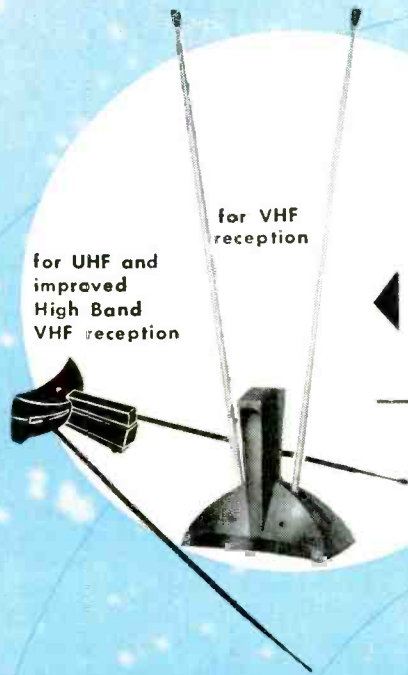

for UHF and improved High Band VHF reception

for VHF reception

- features 3 telescoping sections.
- tilt-proof polystyrene base — cannot tip over.
- handsomely packaged for display.

the ALL-VU*

*all VHF . . . all UHF
the only indoor antenna with this "2-Way" feature.

model no. 381 \$6⁹⁵ list

the PRE-VU

for all-channel VHF reception only.

model no. 380
\$5⁹⁵ list

ALUMast

Aluminum Masting.
The new idea in antenna masting—

can never rust!

- in telescoping sections
- in swaged 5, 10, and 14 foot sections

Lightweight ALUMast is 1/3 the weight of steel, making it so easy to install — it swings right up! Stronger than steel, ALUMast is easier to stock and actually more economical.



brings you today's **5**
newest installation ideas

for . . . more effective installations
. . . greater customer satisfaction
. . . higher profits for you!

SELECTENNA COUPLING SYSTEM

permits unlimited antenna combinations with only one transmission line!


- for the first time, you can tie together an unlimited combination of antennas, including separate antennas operating on the same band.
- ideal for areas currently using rotators, manually-operated selector switches, and "omni-directional" antennas.

list price—

\$542

each including hardware and wire for joining couplers.

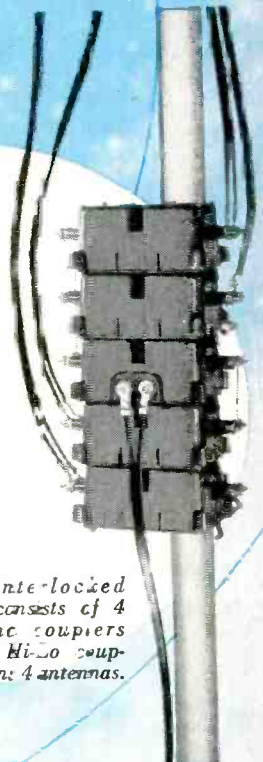This inter-locked stack consists of 4 antenna couplers and 1 Hi-Lo coupler; join 4 antennas.



TV ROTATOR

with features found in no other rotator today:

- flexible worm gear, built-in thrust bearing.
- removable motor, electrical and mechanical stops.
- weatherproof, lightweight, strong.
- straight-thru mast mounting, built-in chimney mount.
- extremely high torque.



model no. 9521, \$49⁹⁵ list

model no. 9520, without directional indicator, \$44⁹⁵ list



Beautifully-styled cabinet has great consumer appeal — is smallest on market (2 3/4" x 4").
Finger-tip control bar.



CHANNEL MASTER CORP. ELLENVILLE, N. Y.

WORLD'S LARGEST MANUFACTURER OF TELEVISION ANTENNAS

INSURE CUSTOMER SATISFACTION . . .

OHMITE®

WIRE-WOUND RESISTORS

Provide an
**EXTRA MARGIN
OF SAFETY**



One replacement resistor that doesn't hold up can cause a faulty repair job . . . and one faulty repair job can cost you one good customer. For your higher wattage replacement needs, the most dependable resistors you can buy are OHMITE wire-wound resistors. They provide an *extra margin of safety* that puts your mind at ease, and helps you build confidence among your customers. OHMITE vitreous-enameled resistors have all-welded construction for greater reliability. Brown Devil resistors are available in 5, 10, and 20-watt sizes, 0.4 to 100,000 ohms. Other fixed resistors to 200 watts. Dividohm adjustable resistors, useful as voltage dividers, available in sizes from 10 to 200 watts, and 1 to 100,000 ohms. Order a supply, today.

**OHMITE
MANUFACTURING COMPANY**

3640 Howard St., Skokie, Illinois
(Suburb of Chicago)

Write for
Stock
Catalog



Be Right With

OHMITE

DEPENDABLE RESISTANCE UNITS

ASSOCIATION NEWS

NETSDA

A meeting of NETSDA was held in the Hotel Diplomat in New York, Sunday, November 14, and attended by delegates representing associations in New York State, Pennsylvania and New Jersey. The main topic of discussion was the license bills pending in various places. Association Counsel, Mr. Joseph Forman gave an excellent review of the New York City bill with some of the problems that had to be taken care of in the formation of the bill. The necessity of having a board established which would be as impartial as possible, composed of various segments of the industry, government and the public was made apparent, and it was generally agreed by delegates present that such an impartial board to examine applicants, issue licenses and take care of future discussions between licensees and the public, would be a primary prerequisite for a good license bill.

The next meeting will be in January, exact time and place to be determined at a later date.

PRMSA—Phila.

At the October 12, 1954, open meeting, P.R.S.M.A. presented Winston Electronics, Inc., manufacturers of Win-Tronix test equipment. The meeting was held in the Gold Room at the Broadwood Hotel, Broad and Wood Streets, here in Phila. Winston presented three speakers—Winston H. Starks—Ralph Weinger and Daniel Kursman who spoke on color television test equipment.

Because of a change in Color Telecast, the show that was to be presented that night at 7:30 to 8:00 P.M., was not put on the air and was not seen at the meeting. P.R.S.M.A. will try again to arrange a meeting when a color telecast can be seen.

NATESA

The receipt you issue is of extreme importance. It can bind you to many things of which you may be entirely unaware and can cause you untold trouble and cost. Legally, you are bound by common law to exercise certain care over any goods in your charge.

Because of this, every service shop is the grave-yard of many junks whose owners decide they don't want to spend money on to revive. One other aspect is

[Continued on page 63]

Field Tested and Proven

by Hundreds of Thousands of Satisfied Users



model AR-2... complete AUTOMATIC rotor with thrust bearing... and handsome modern design cabinet, uses 4 wire cable


model AR-1... same as AR-2 without thrust bearing

model TR-12

A special combination value consisting of complete rotor including thrust bearing. Handsome modern cabinet with meter control dial, uses 4 wire cable.

model TR-11

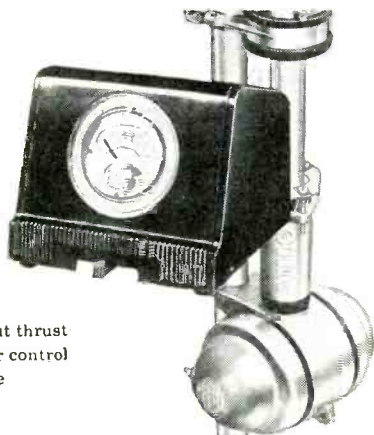The same as the TR-12 without thrust bearing, complete with meter control dial cabinet, uses 4 wire cable




model TR-2

The heavy-duty rotor with plastic cabinet featuring "Compass Control", illuminated "perfect pattern" dial, uses 8 wire cable

model TR-4

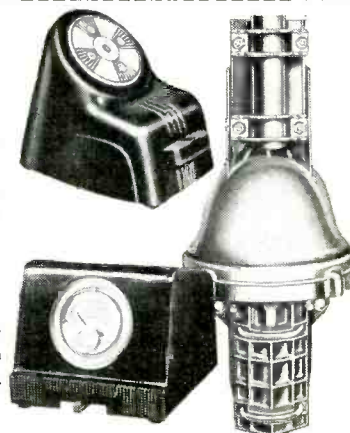The heavy-duty rotor complete with handsome, modern design cabinet with meter control dial, uses 4 wire cable.



CORNELL-DUBILIER
SOUTH PLAINFIELD, N. J.



THE RADIART CORP.
CLEVELAND 13, OHIO

ACHIEVEMENT OF A *Quarter Century*

For those who pursue the ultimate—the rediscovery of perspective in music...



Imperial

PR-100


The stimulation and pleasure gained by listening to a live performance is the result of much more than frequency range considerations.

Here is a revolution—the use of true proportions of sound in authentic reproduction including smooth coverage of the complete useful frequency range and thus recreating the fine performance with the greatest possible degree of accuracy.

Voices come to life and there's a new almost geometrical separation of instruments. A three-way system with 1-f unit loaded by a new-design reactance-annuling trilateral-mouth horn for bass; selected compression-driver horn-loaded mid channel with intrarange equalizer for a final touch to precise balance and coloration elimination; and superlatively smooth, space-blended supertweeter top. Each instrument is individually serial numbered and accompanied with a signed certificate certifying that the reproducer fully meets the exacting performance standards set for it. (Components and performance are the same as for RS-100 Laboratory Reference Standard Reproducer.)

PR-100 "IMPERIAL" REPRODUCER

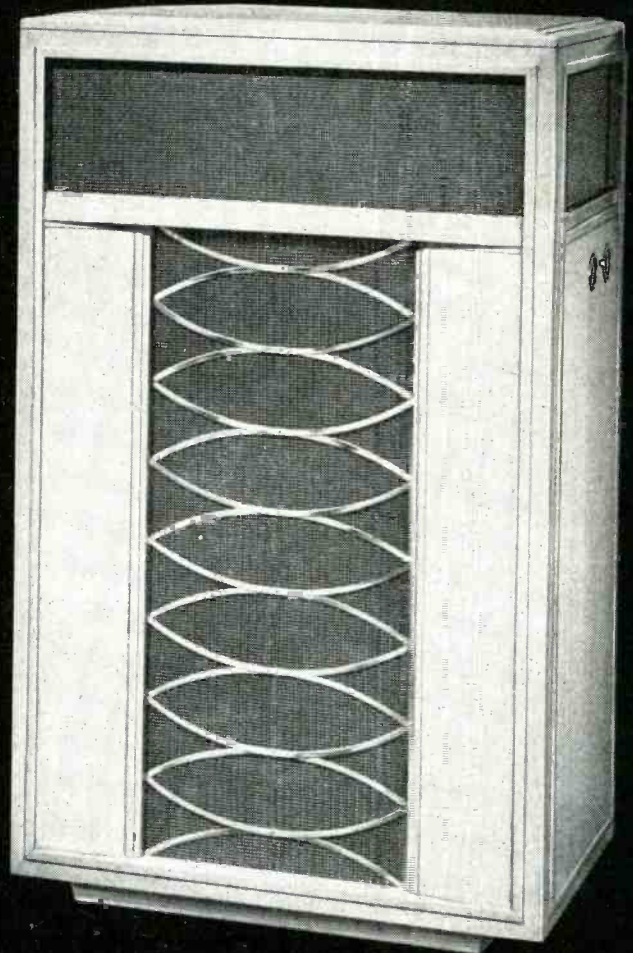ST-919. Selected Mahogany. Net Price..... \$525.00
 ST-918. Satin Korina. Net Price..... 535.00



LABORATORY STANDARD


RS-100

Built for research comparison

The Imperial was designed by the Jensen engineering staff for their own use as a reference standard of the highest quality of high-fidelity reproduction. In this original laboratory version the RS-100 Laboratory Reference Standard Reproducer is a new and important tool for sound, recording and broadcast engineers, workers in psychoacoustics and music critics who require an unusually high quality of reproduction. Some music lovers and audiophiles will undoubtedly want to own an RS-100. Cabinet is plywood attractively two-toned in blue gray.

RS-100 LABORATORY REFERENCE STANDARD REPRODUCER

ST-920. Net Price..... \$468.00

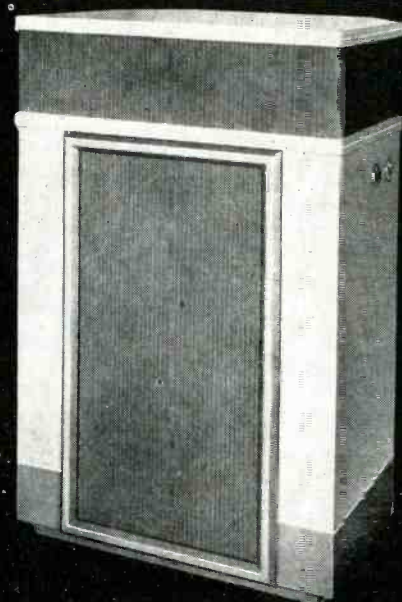

Barton Browne Advertising

Jensen
 MANUFACTURING COMPANY

Jensen—world's quality standard for more than a quarter century.

Division of the Muter Co.
 6601 S. Laramie, Chicago 38, Illinois

CHROMINANCE Systems

in Color TV Receivers

by **BOB DARGAN**
and **SAM MARSHALL**

Discussion of signal processing of chrominance signal in Q and I receiver.

Part 1

THE chrominance section of a color TV receiver is used to recover and process color signals from the composite video signal. There are two types of chrominance systems used. These are the I & Q or "Ceiling Performance" and the R-Y and B-Y or "Economy" systems. The manner in which these two systems operate will now be considered from a general descriptive point of view. A more detailed analysis will follow subsequently.

Ceiling Performance and Economy Systems

In a previous chapter entitled, "Block Diagram Analysis of Color Transmission and Reception," the entire discussion was based on the I and Q system which provides for a 1.5 mc video frequency generation of certain colors which the eye can differentiate in fine detail and a 0.5 mc video frequency generation of other colors which the eye cannot differentiate in fine detail. Such a system provides the finest available in color reception, and a receiver designed around this system is commonly referred to as a "Ceiling Performance" receiver.

It is entirely possible to extract the color difference signals without making use of the individual I and Q signals. By doing this we lose the high definition color video frequencies from zero to 0.5 mc. Such a receiver, because of the fewer circuits required is called an "Economy Receiver".

A discussion of a general block diagram encompassing both systems now follows. It must be borne in mind that the diagram shown is typical of receivers in general and does not refer to any specific type.

On examining this block diagram, shown in Fig. 1, it will be observed that the video detector feeds the demodulat-

ed video if composite signal into the section marked composite video amplifier. Here the various signal components making up the composite video signal are extracted by means of traps and filters and fed to their respective sections for further processing. These signal components are the luminance signal, the horizontal and vertical sync

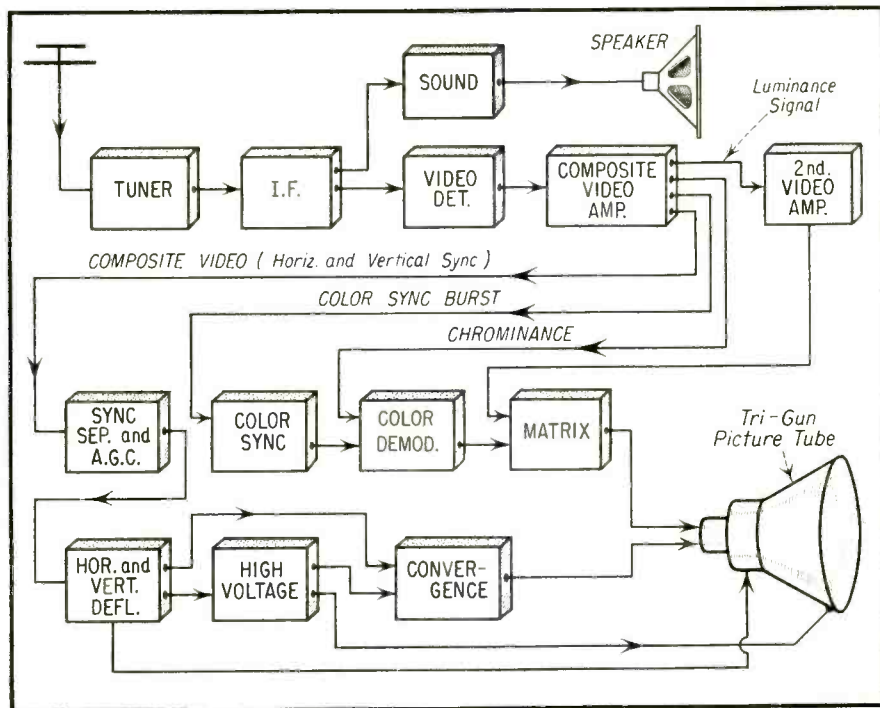


Fig. 1—A simplified block diagram of a general color TV receiver

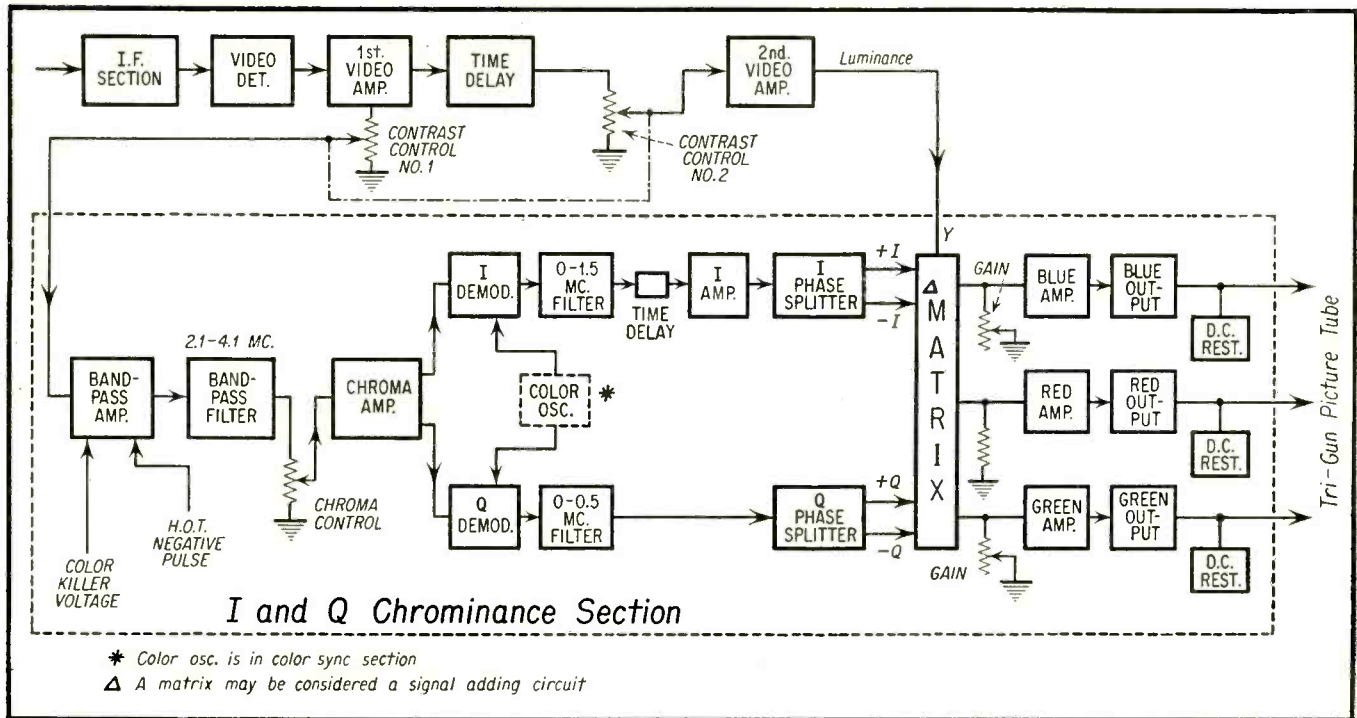


Fig. 2—The stages comprising the I and Q chrominance section.

pulses, the color sync burst and the chrominance signal.

Notice that the Y or luminance signal, which is equivalent to the black and white brightness information of the scene, is processed in a conventional manner through a 2nd video amplifier. From this point it is applied to the picture tube through the signal mixing network called the matrix. For a B & W transmission the signal in the luminance channel consists only of the black and white video signal and the standard B & W horizontal and vertical sync pulses. For a color transmission the luminance channel contains the Y signal and the horizontal and vertical color sync pulses.

It can be seen that many of the sections are common to black and white (B & W) receivers. In general, there are four sections that actually have been added with the color picture tube to bring about a change to color television. These are a Color Sync section, a Chrominance section, a Matrix section and a Convergence section.

Briefly explained, the Color Sync section processes the color burst signal so that correctly phased 3.58 mc signals are developed and fed into the color demodulators.

The demodulators into which are fed the chrominance suppressed carrier color sideband signals, extract the I and Q or R-Y and B-Y signals from the chrominance signal and apply them to the Matrix section. The Matrix section mixes the luminance and I and Q (or R-Y and B-Y) signals so that the original primary colors are presented

to the corresponding guns of the picture tube. The convergence section provides a means of producing color registration in the 3-gun shadow mask type of color picture tube.

In a conventional ceiling performance receiver, the color demodulators extract the I and Q signals from the chrominance signal. Following this the I and Q signals are fed into the matrix network where they are mixed with the Y signal to produce the primary red, green and blue signals.

In comparison, the economy receiver extracts the R-Y and B-Y signals from the chrominance signal. Following this, the R-Y and B-Y signals are mixed to produce the G-Y signal. Then all three color-difference signals are mixed or matrixed with the Y signal in a separate matrix, or directly in the picture tube via the grid and cathode terminals. The net result is the reproduction of the original primary red, green and blue signals. In the economy receiver it must be borne in mind that the processing of the chrominance signal to produce the R-Y and B-Y signals involves losing the 0.5 mc to 1.5 mc color sidebands signals. This will be explained in greater detail subsequently.

The I & Q Chrominance Section

Let us examine the stages that comprise the Chrominance section of a ceiling performance (I & Q) receiver. These are shown in Fig. 2. The color sideband signals applied to the chrominance section is obtained at the contrast potentiometer in the cathode of the video amplifier circuit. In certain re-

ceiver designs this contrast control may be located in a cathode follower stage so as to provide a low impedance source, thereby insuring less interference as the signal is coupled into the following stage.

To refresh the reader's memory it will be recalled (Fig. 3) that the detected video output contains luminance signals from zero to 4.1 mc, and a chrominance signal which extends from 2.1 to 4.1 mc around a 3.58 mc suppressed sub-carrier. This chrominance signal contains the double sideband information (from 0 to 0.5 mc) of both the "I" and "Q" signals and the single sideband information (from 0.5 mc to 1.5 mc) of the "I" signal.

The Bandpass Amplifier

Since signal information other than these chrominance signal frequencies might give rise to spurious circuit operation, that is noise signals at frequencies below 2.1 mc and crosstalk between the luminance and chrominance signals, it is desirable to suppress all other frequencies than those between 2.1 mc and 4.1 mc. For this reason the signal obtained at the contrast control #1 is coupled to a frequency limiting bandpass amplifier as shown in Fig. 2. In the plate circuit of this amplifier a filter is employed which restricts the output to a bandwidth of from 2.1 mc to 4.1 mc. See Fig. 4.

The bandpass amplifier is used to perform another function, which is the removal of the eight cycles of color burst. This is accomplished by blocking the bandpass amplifier tube for the pe-

riod corresponding to the color burst. Blocking takes place by feeding a negative spike of the horizontal sweep frequency from the horizontal output transformer. This voltage spike cuts off the bandpass amplifier during the period of the color burst, thus preventing these pulses from being present in the bandpass amplifier. If the color burst signal were to pass through this stage the overall background of the color picture would be disturbed because of the presence of the recovered burst envelope in the blue output signal. This recovered burst has an amplitude equal to or greater than the horizontal sync signal and could easily cause the blue *dc* restorer to set up an excessive *dc* component.

Another signal fed to the bandpass amplifier is a color killer voltage which is derived from the color sync section. (See Fig. 2). This killer voltage causes the bandpass amplifier tube to be cut off when black and white signals are being received, thus preventing signals of any sort being present at the input of the demodulator during black and white programs. If the amplifier were not made inoperative at this time it would be possible for high frequency luminance and noise signals to pass through and eventually be applied as signals to the color grids thereby causing the appearance of "confetti" on the pix tube screen. Incidentally, some receivers apply the color killer voltage to the demodulator stages.

Chroma Control

Following the bandpass filter is a chroma control which permits adjustment of the intensity of the color signals entering the I and Q demodulators. This, in turn, results in an increase or decrease of the color signal voltages applied at the input to the matrix.

Also fed into the input of the matrix is the Y or luminance signal which adds luminance information to the above mentioned color signal. The amount of this added luminance may be controlled by the contrast control #2, Fig. 2.

It will be noted in Fig. 2 that contrast

controls #1 and #2, which are the luminance and chrominance contrast controls respectively, are ganged together to provide for a single master contrast control action. This insures "tracking of the chrominance and luminance signals so that for any setting of the "Chroma" control the ganged arrangement of #1 and #2 will retain the correct ratio (relative amounts) of luminance and chrominance signals.

In the actual adjustment of a color TV receiver, for proper color and luminance, the sequence is as follows:

1. The chroma control is turned off.
2. The contrast control is turned off.
3. The brightness control is adjusted so that the screen is just below the point of illumination.
4. The contrast control is now turned up for the most pleasing black and white picture. Also the brightness control is readjusted to give a proper *black*.
5. The chroma control is now turned up until correct color saturation is obtained.
6. The Phase control is adjusted for proper hue by adjusting the phase control against known colors (such as skin-tones) until these colors appear as they should on the screen.

An analysis of these six steps points up the fact that the contrast control increases or decreases both the color and luminance signal at the same time. To increase the ratio of color signal to luminance, the chroma signal must be turned up. Conversely to decrease the ratio of color signal to luminance, the chroma signal must be turned down. Thus, the chroma control provides a means of controlling the color tints or saturation.

If the pre-set controls are properly adjusted in the chrominance section (particularly in the matrix and color amplifier gain circuits) then, varying the chroma control (see Fig. 2) should produce a variation of only the relative saturation of the color voltages applied to the picture tube and not the colors themselves. In fact, a check on the proper adjustment of the matrix and individual color gain controls is to vary the chroma

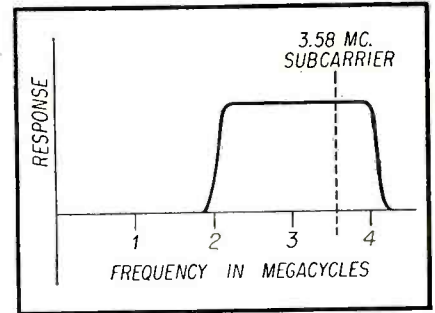


Fig. 4—Bandpass response of bandpass filter in output of bandpass amplifier.

control carefully and to observe the effect on the color picture tube screen. If these variations result in a change in color or hue the previously mentioned matrix and gain control adjustments are at fault. On the other hand, if varying the chroma control as outlined produces a change in color saturation only, the matrix and gain control adjustments are correct.

Chroma Amplifier

Following the bandpass amplifier and its filter network we usually find an additional stage known as the chroma amplifier. This stage increases the peak to peak amplitude of the color signal at the output of the chroma control and provides equal chrominance signal voltages to both the I and Q demodulators.

I & Q Demodulators

Before analyzing the action taking place in a demodulator it would be well to recall the original make-up of the chrominance signal. It will be recalled that the Q signal is made up of low video frequencies (0 to 0.5 *mc*) corresponding to the low acuity colors around purple and green and the I signal is made up of the high video frequencies (0 to 1.5 *mc*) corresponding to the high acuity colors around orange and cyan. It will also be recalled that the I and Q signals modulate a set of 3.58 *mc* quadrature carriers and are transmitted on a single suppressed carrier frequency as a pair of signals displaced by a phase angle of 90 degrees. The suppressed carrier Q signal is double sidebanded and the suppressed carrier I signal is double sidebanded up to 0.5 *mc* on each side of the carrier and single sidebanded from 0.5 *mc* to 1.5 *mc* on one side of the carrier. These two signals comprise the chrominance signal.

The primary purpose of the demodulator is to separate the I and Q suppressed carrier sidebands combined in the chrominance signal, and to reconvert them back into video frequencies identical to the original I and Q signals. To do this the input of each demodulator is fed the chrominance signal and

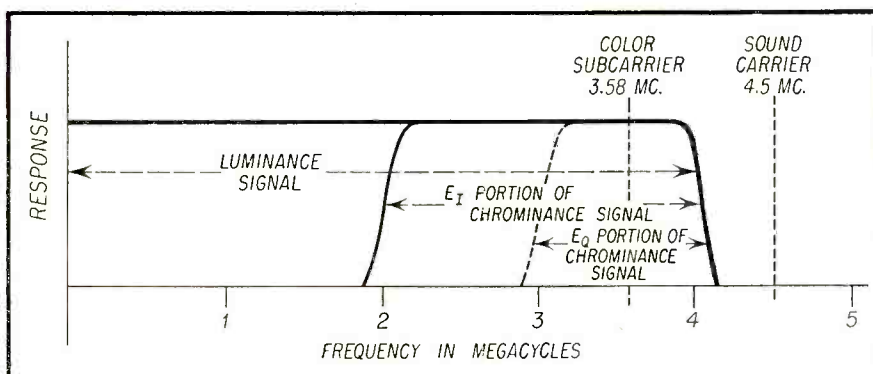


Fig. 3—Complete color picture signal pass band.

AT LAST!

REMOTE CONTROL FOR TV SETS



**EASIEST
INSTALLATION!
LOWEST RETAIL
PRICE!**

**THIS NEW
MOTOR-DRIVEN
REMOTE
CONTROL
UNIT FITS
ALMOST EVERY
TELEVISION
SET**

REMOT-O-MATIC HAS ARRIVED!

Here is the unit which is making history in the television industry. But more important . . . it is making money for dealers and servicemen all over the nation. REMOT-O-MATIC is priced so low that it is within the means of every TV set owner.

NATIONALLY ADVERTISED

REMOT-O-MATIC advertising is now nation-wide . . . on television, in newspapers and in magazines. Point of sale dealer helps, brochures, mailing stuffers, window and counter displays and filmed commercials are available.

REMOT-O-MATIC DeLuxe gives you these controls: On-and-off control; Sound control; Brightness control; Fine Tuning control and a motor-driven Channel Changer that is absolutely silent. In addition, REMOT-O-MATIC gives you the convenience of taking the sound control away from the set so that the sound is controlled from the remote unit only . . . or at the set as you choose.

DE LUXE

\$39⁹⁵



Your discounts, installation profits and the public demand for REMOT-O-MATIC provide the best reasons why you should immediately write us for jobber and dealer discounts.

REMOT-O-MATIC SALES, INC.

8747 Sunset Boulevard • Los Angeles 46, California

a separate 3.58 mc oscillator signal, the latter being applied as follows: The phase of the first 3.58 mc signal fed to the I demodulator is in phase with the I component of the suppressed carrier chrominance signal, and the phase of the second 3.58 mc fed to the Q demodulator is in phase with the Q component of the suppressed carrier chrominance signal.

The plate circuits of these demodulators, under the above mentioned conditions contain signal products, which, in the case of the I demodulator is the I signal in its original video frequency form. The manner in which these transitions take place will be described in greater detail subsequently.

It might be pointed out that the action described above is strictly true for the I demodulator but not for the Q demodulator. The reason for this is as follows:

In the I demodulator the complete I signal is passed by the circuit because it is in phase with the first 3.58 mc oscillator signal applied. The Q signal being 90 degrees out of phase with the first 3.58 mc signal develops equal and opposite voltages in the plate circuit which cancel out because it is double sidebanded; so that the Q signal is rejected.

In the Q demodulator the complete Q signal is passed by the circuit because it is in phase with the second or quadrature 3.58 mc signal applied. The I signal, however, is rejected only for that portion of its spectrum where it is double sidebanded (0 to 0.5 mc) for the same reason that the double sidebanded Q signal is rejected in the I demodulator. From 0.5 mc to 1.5 mc the I signal is single sidebanded, and that portion of the I signal is not rejected in the Q demodulator. This component of I signal is referred to as "Quadrature Crosstalk," and must be eliminated. This is done by the insertion of a 0 to 0.5 mc filter in the output of the Q demodulator which effectively rejects the 0.5 to 1.5 mc quadrature crosstalk components previously referred to.

Referring to the block diagram of Fig. 2 it will be observed that the I demodulator contains a 0 to 1.5 mc filter. This filter in the I channel is primarily designed to provide attenuation of signals other than the 0 to 1.5 mc video color signals which may find their way through the demodulators. Such signals are derived from the luminance channel.

Time Delay Networks

The passage of the Q signal through the zero to 0.5 mc filter introduces a time delay which is somewhat greater

[Continued on page 54]



Weston Model 981
Proportional Mutual Conductance Tubechecker

FILTERED D-C POTENTIALS

for accurate
 G_m
measurements

OUTSTANDING FEATURES:

G_m MEASUREMENTS— G_m measurements are made more accurately by using filtered d-c plate, screen grid and control grid potentials. A precision voltage divider network and selector switch allows a proportionate value of signal voltage to be chosen for testing tubes having transconductances up to 30,000 micromhos. Signal voltages of 5.2, 2.6, 1.3, and 0.65 volts peak-to-peak having a frequency of 5000 cycles are provided.

GRID BIAS, SCREEN GRID AND PLATE VOLTAGE: Filtered d-c potentials of 90, 130, and 220 volts are available for plate and screen potentials. A variable filtered d-c voltage in two ranges of 0-5 and 0-20 volts are used to obtain better resolution of Grid Bias settings. *Far greater accuracy is obtainable with filtered d-c potentials than previously possible in portable tubecheckers.*

METER MEASUREMENT OF HIGH LEAKAGE RESISTANCE—Since tube leakage as high as several megohms can cause poor performance in TV Receivers, this tubechecker is designed to provide an accurate meter measurement of leakage resistance as high as 5 megohms between tube elements, thus being particularly useful for TV servicing and TV line production assembly.

TWIN SECTION TUBES—Three toggle switches make it possible to rapidly check and compare the respective sections of twin section tubes at only one setting of the selector switches.

WESTON 980 LINE
TEST EQUIPMENT

THE
980
LINE

PROPORTIONAL
MUTUAL
CONDUCTANCE
TUBECHECKER

SEND COUPON TODAY FOR
COMPLETE DESCRIPTION AND PRICES

Weston Electrical Instrument Corporation
614 Frelinghuysen Avenue
Newark 5, New Jersey

Please send literature on the new 981 Tubechecker.

NAME _____

ADDRESS _____

understanding and servicing Horizontal Output Transformer circuits

by Oscar Fisch

PART 2

A discussion of the operating principles of horizontal output transformers, together with procedures designed to facilitate rapid servicing and replacement.

IN the previous installment the impedance matching function of the horizontal output transformer was discussed in some detail. It was pointed out that the matching of the impedance of the horizontal deflection coils (the load) to that of the horizontal output tube (the generator), is a necessary requirement if maximum power transfer is to be obtained.

This may all be interesting from a theoretical point of view, but it might be worth while at this point to examine the practical implications of impedance matching. Once again, a very close comparison can be made between the corresponding parts of a radio receiver and a TV receiver. In the radio receiver, the action taking place from the audio

output tube to the speaker may be summarized as follows:

1. The audio output tube (see Fig. 1A) delivers power to the output transformer in the form of an audio signal current.

2. The output transformer delivers this power to the voice coil of the speaker.

3. The audio signal current through the voice coil produces a magnetic field, the strength of which varies in step with the strength of the current.

4. This varying magnetic field reacts with the steady field of the permanent magnet (or the electromagnet of an electro magnetic speaker). The reaction between these two fields results in a movement of the speaker cone and the consequent production of sound.

5. The greater the variations in the magnetic field through the voice coil, the louder will be the sound issuing from the speaker.

6. Thus, to get the loudest sound from the speaker, requires the delivery maximum power to the voice coil from the output tube. The output transformer provides this maximum possible power to that of the output tube.

A step by step comparison with the action in a TV receiver shows a very close correspondence, as follows, and as illustrated by Fig. 1B.

1. The horizontal output tube delivers power to the horizontal output transformer in the form of a sawtooth horizontal sweep current.

2. The output transformer delivers this power to the horizontal deflection coils in the deflection yoke.

3. The sweep signal current, flowing through the horizontal deflection coils, produces a magnetic field through the neck of the picture tube. The strength

of this field varies in step with the strength of the current.

4. This magnetic field is directly across the path of the electron beam within the cathode ray tube. As the beam passes through the field, it is deflected to the left or to the right, depending on the polarity of the field. The amount of deflection depends on strength of the magnetic field.

5. The greater the variation in magnetic field strength, the greater will be the deflection of the electron beam.

6. Thus, to produce the maximum deflection of the electron beam requires the delivery of a maximum current swing to the deflection coils. This in turn produces a maximum overall change in magnetic field strength. The horizontal output transformer provides for the delivery of maximum available power by matching the impedance of

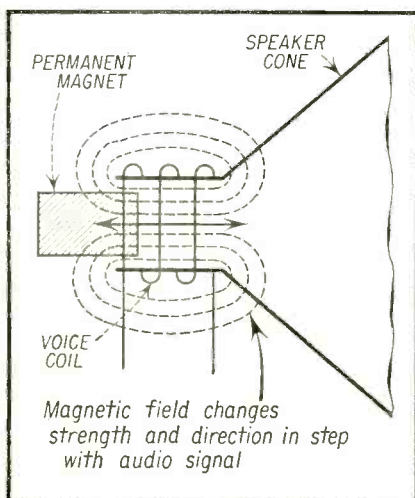


Fig. 1A—Action of magnetic field in speaker.

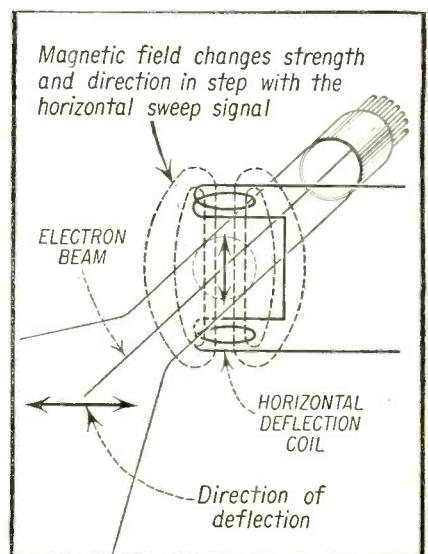


Fig. 1B—Action of magnetic field in horizontal defl. coils of CRT.

the deflection coil to that of the horizontal output tube.

How does all this bear on the problem a service technician faces when the horizontal output transformer must be replaced? Actually, it must be admitted that what nearly always happens is that the technician hies himself to his favorite distributor and says "Hiya Jerry! I need a flyback for an Admiral 121 M 12A." Jerry then thumbs through the pages of a replacement catalog and comes up with a Stancor A-8134 or other make replacement flyback transformer. Another common procedure would be to get an exact replacement from the manufacturer. Neither of these procedures requires any extensive knowledge on the part of the technician, so why bother with all this business of impedance matching, deflection angles, etc., etc. Our answer is that when a serviceman understands these basic principles, he becomes more proficient in diagnosing and remedying troubles. This increased proficiency can be translated directly into dollars and cents by cutting down substantially on the time required for repairs.

In the light of the previous discussion, we might summarize the deflection power requirements as follows. Suppose a receiver uses a 19GP4 picture tube. Examining the characteristics of this tube shows that the deflection angle is 66°. This is the starting point for which the other components in the deflection circuit are designed. In Fig. 2, the line OA represents the electron beam of the left end of the raster, while OB is its position at the right hand end. The deflection angle of a CRT, in this case 66°, is the angle formed by these two extreme positions of the beam.

The force which is used to deflect the beam over this angle is derived from the saw tooth wave of current flowing through the deflection coils, as mentioned previously. Fig. 3 is a graph of this current. A and B on the solid line graph are the maximum negative and positive values of the current through the coils, and at these current values the magnetic field deflects the beam to OA and OB respectively, in Fig. 2.

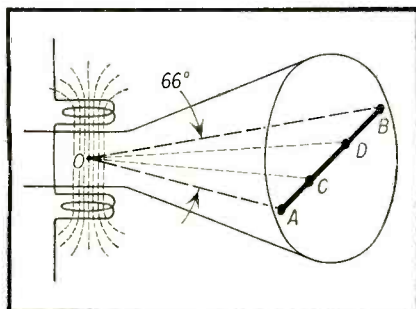


Fig. 2—Deflection angle of a CRT (19GP4).

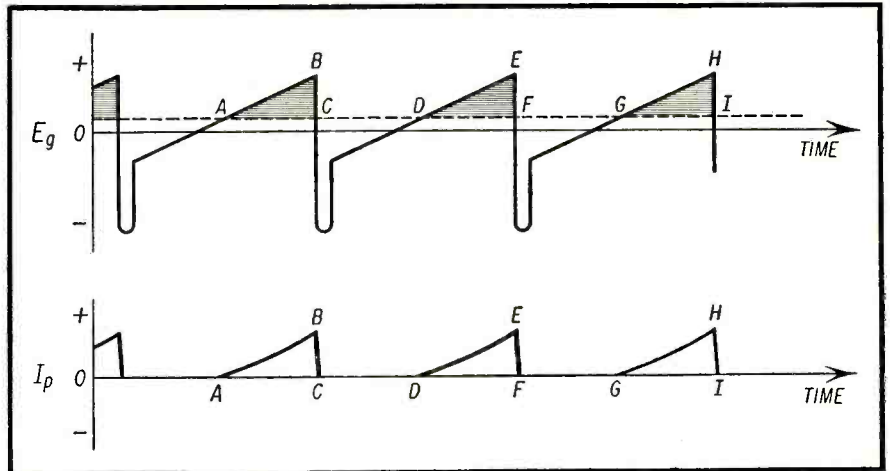


Fig. 4B—Signal voltage at grid of horizontal output tube. Current flows only during shaded portion of signal. Fig. 4C—Current flow in the plate circuit of the horizontal output tube.

The next step is to design the deflection coils so that the desired deflection may be produced with the available power from the output stage. Thus we have 70° yokes, 57° yokes, etc. If, for any reason, the current through the deflection coils is reduced, as shown by the dotted line of Fig. 3, the beam will be swept through a smaller angle. This would be the angle formed by CO and DO of Fig. 2, and of course indicates reduced width of the picture.

Obviously, an improper match could be responsible for such a reduction in sweep width. The properly designed horizontal output transformer, then forms the final connecting link in the chain between the horizontal output tube and the electron beam in the CRT.

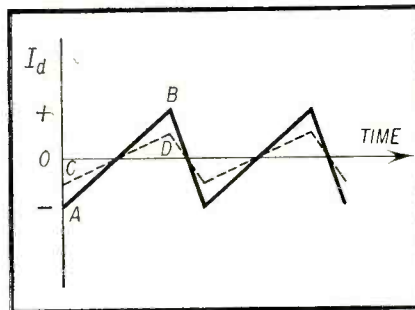


Fig. 3—Current through horizontal deflection coils, corresponding to deflections in Fig. 2.

This is why for example, flyback transformer and deflection yokes are frequently sold as matched sets for larger tube conversion jobs. This is also why the technician, when replacing either the flyback transformer or the deflection yoke must always consider whether the replacement part will provide proper matching.

Replacement transformers of the "universal" type are designed for angular deflections of from 50° to 70°. Any deflection angle within this range may be

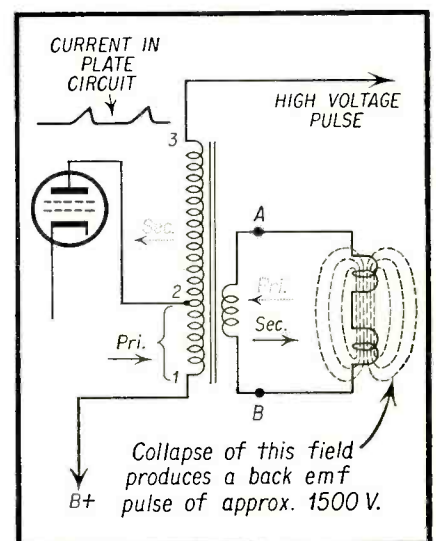


Fig. 4A—Production of H.V. pulse for 2nd anode.

handled by selecting the proper taps. For 24 inch picture tubes and larger, 90° deflection angles are used. The universal replacement transformer, therefore cannot be used in this application. Flyback transformers specifically designed for a 90° deflection must be used.

High Voltage Production

It was pointed out in the previous installment that the production of a high voltage for the picture tube second anode is another major function of the horizontal output transformer. This must be taken with a very slight grain of salt. There are a few receivers (very few) which use an rf power supply for high voltage production. These receivers use the basic horizontal output transformer, which is not concerned with high voltage production. For clarity, this is the only type we might truly call a horizontal output transformer.

The much more common type which
[Continued on page 56]

Worried about callbacks?



...relieve your mind
install Astron BLUE·POINTS[®]
for unsurpassed dependability


Service technicians, set owners—in fact everyone worries about set failures that require a callback. Set owners rely on you as an authority, to install only the finest quality replacement parts. Your reputation rides on the performance of every part you install. Both your reputation and profits suffer should a costly callback be necessary. That's why more and more smart service technicians are installing fabulous Astron BLUE·POINT molded plastic tubulars... their unsurpassed dependability guarantees **NO CALLBACK!** Developed after exhaustive testing, Astron BLUE·POINT gives you • new bonded seal and shell impervious to heat and moisture • continuous 85°C operation **WITHOUT DERATING** • solid thermo-setting impregnant for high capacitance stability • positive protection against vibration • low power factor • high insulation resistance • individually tested and guaranteed • clearly marked shell for easy identification.

Astron also manufactures a complete line of advance-design, exact replacement capacitors (including Safety Margin[®] electrolytics in twist prong and other popular case styles) for superior performance in every radio and television servicing requirement.

New Astron Bulletin AB-20B showing complete physical and electrical characteristics of Astron BLUE·POINT capacitors now available... for your free copy write today!

*TRADEMARK

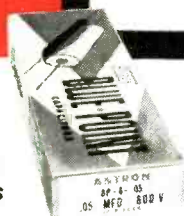available nationally
through
authorized distributors



ASTRON

C O R P O R A T I O N

255 GRANT AVENUE, E. NEWARK, N. J.



Export Division: Rocke International Corp. 13 E. 40 St., New York, N. Y. In Canada: Charles W. Pointon 6 Alcina Ave., Toronto 10, Ontario

sectionalized

PRINTED CIRCUIT

TV receiver

by **Walsco Electronics Corp.**
*A unique TV receiver utilizing
 sectionalized printed circuit units in
 a vertical chassis of new design.*

A NEW innovation in chassis design and construction which is entirely different than the conventional has just been announced by the Walsco Electronics Corporation. Its primary features are:

1. Nine printed-circuit plug-in assemblies (see Fig. 1), each quickly removable.
2. A vertical chassis with components and wiring visible from front or rear.
3. Remote control operation.

From the point of view of maintenance this receiver is almost a serviceman's dream. Upon removal of the rear panel (see Fig. 2) all parts and tube socket terminal are accessible for immediate checking. Also, because of the sectionalized feature of this receiver as is evident in the schematic (Fig. 3), im-

portant test points are at the technician's fingertips for quick testing and diagnosis. Finally, in cases where alignment adjustments are necessary, they too are immediately accessible.

Of even greater significance than the above, from the point of view of servicing, is the possible technique of stocking replacement strips and providing quick and immediate service by installing a complete strip for one in which any of the components is defective or misaligned. In this manner the customer

receives a "factory-rebuilt" replacement, a technique which is used today in many fields for quicker service and greater profits.

The chassis design, especially with the remote control feature, lends itself to custom installations and cabinet design, with a flexibility that should satisfy the wildest-eyed interior decorator. Here again is an item the dealer or technician can sell with considerable latitude for the inclusion of accessories and installation charges.

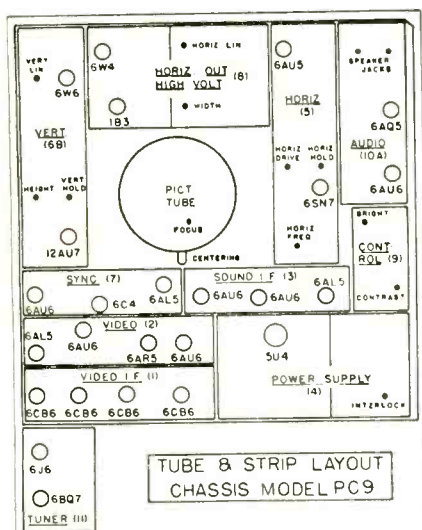


Fig. 1—Tube and printed circuit strip layout of Walsco Model PC9 TV receiver. Shown also are the various adjustment controls available for immediate adjustment.


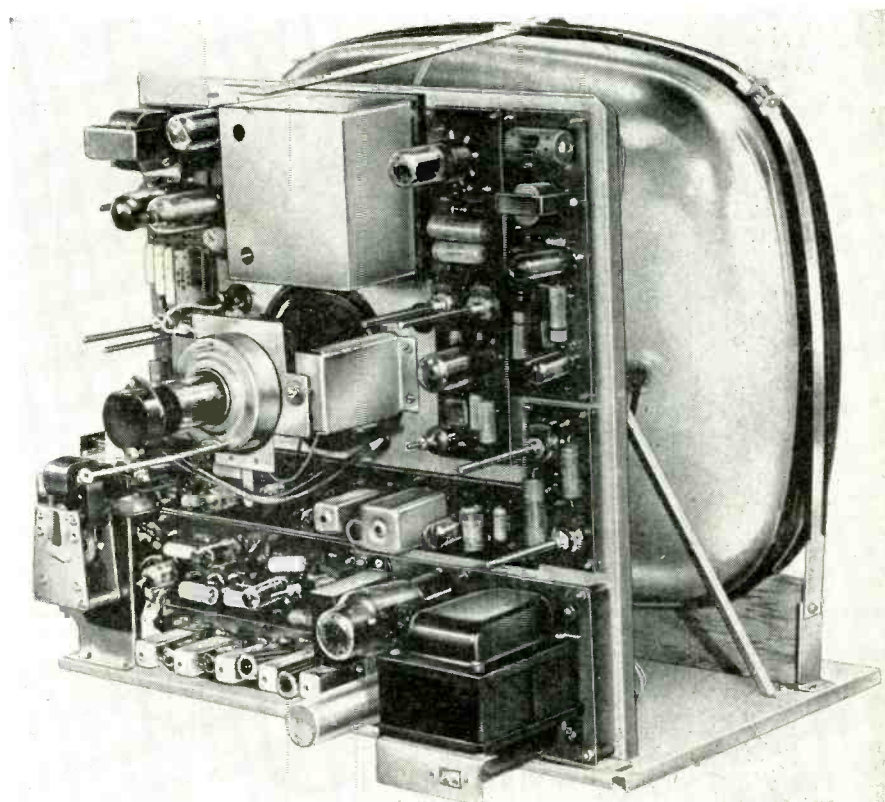


Fig. 2—Appearance of receiver on removal of rear panel.

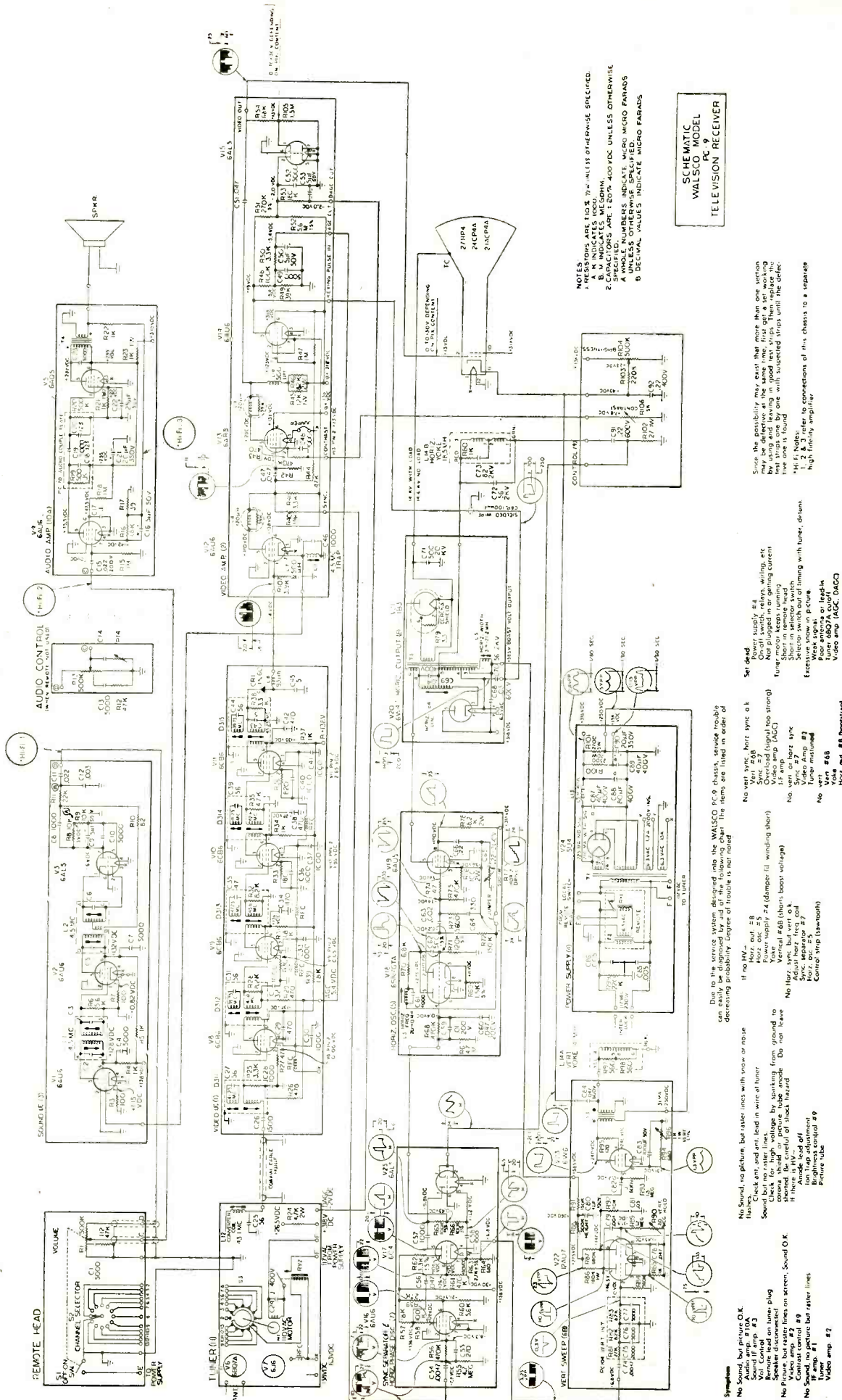

**SCHEMATIC MODEL
WALSOCO MODEL
PC 9
TELEVISION RECEIVER**

NOTES:
 1. RESISTORS ARE 1/2W. 2W UNLESS OTHERWISE SPECIFIED.
 2. CAPACITORS ARE 50V UNLESS OTHERWISE SPECIFIED.
 3. ALL VALUES ARE IN OHMS UNLESS OTHERWISE SPECIFIED.
 4. ALL VALUES ARE IN MICRO MICRO FARADS UNLESS OTHERWISE SPECIFIED.
 5. ALL VALUES ARE IN MICRO MICRO FARADS UNLESS OTHERWISE SPECIFIED.


Check the probability that they may be defective at the same time first set up one section by using and leaving in good test strips. Then replace the defective one with suspected strips until the defective one is found.
 *If F Notes:
 1. High frequency connections of this chassis to a separate high frequency amplifier.

Set dead
 No vert. sync. horiz. sync. ok
 Sync. #1 (too strong)
 Sync. #2 (too weak)
 Sync. #3 (too strong)
 Sync. #4 (too weak)
 Sync. #5 (too strong)
 Sync. #6 (too weak)
 Sync. #7 (too strong)
 Sync. #8 (too weak)
 Sync. #9 (too strong)
 Sync. #10 (too weak)
 Sync. #11 (too strong)
 Sync. #12 (too weak)
 Sync. #13 (too strong)
 Sync. #14 (too weak)
 Sync. #15 (too strong)
 Sync. #16 (too weak)
 Sync. #17 (too strong)
 Sync. #18 (too weak)
 Sync. #19 (too strong)
 Sync. #20 (too weak)
 Sync. #21 (too strong)
 Sync. #22 (too weak)
 Sync. #23 (too strong)
 Sync. #24 (too weak)
 Sync. #25 (too strong)
 Sync. #26 (too weak)
 Sync. #27 (too strong)
 Sync. #28 (too weak)
 Sync. #29 (too strong)
 Sync. #30 (too weak)
 Sync. #31 (too strong)
 Sync. #32 (too weak)
 Sync. #33 (too strong)
 Sync. #34 (too weak)
 Sync. #35 (too strong)
 Sync. #36 (too weak)
 Sync. #37 (too strong)
 Sync. #38 (too weak)
 Sync. #39 (too strong)
 Sync. #40 (too weak)
 Sync. #41 (too strong)
 Sync. #42 (too weak)
 Sync. #43 (too strong)
 Sync. #44 (too weak)
 Sync. #45 (too strong)
 Sync. #46 (too weak)
 Sync. #47 (too strong)
 Sync. #48 (too weak)
 Sync. #49 (too strong)
 Sync. #50 (too weak)
 Sync. #51 (too strong)
 Sync. #52 (too weak)
 Sync. #53 (too strong)
 Sync. #54 (too weak)
 Sync. #55 (too strong)
 Sync. #56 (too weak)
 Sync. #57 (too strong)
 Sync. #58 (too weak)
 Sync. #59 (too strong)
 Sync. #60 (too weak)
 Sync. #61 (too strong)
 Sync. #62 (too weak)
 Sync. #63 (too strong)
 Sync. #64 (too weak)
 Sync. #65 (too strong)
 Sync. #66 (too weak)
 Sync. #67 (too strong)
 Sync. #68 (too weak)
 Sync. #69 (too strong)
 Sync. #70 (too weak)
 Sync. #71 (too strong)
 Sync. #72 (too weak)
 Sync. #73 (too strong)
 Sync. #74 (too weak)
 Sync. #75 (too strong)
 Sync. #76 (too weak)
 Sync. #77 (too strong)
 Sync. #78 (too weak)
 Sync. #79 (too strong)
 Sync. #80 (too weak)
 Sync. #81 (too strong)
 Sync. #82 (too weak)
 Sync. #83 (too strong)
 Sync. #84 (too weak)
 Sync. #85 (too strong)
 Sync. #86 (too weak)
 Sync. #87 (too strong)
 Sync. #88 (too weak)
 Sync. #89 (too strong)
 Sync. #90 (too weak)
 Sync. #91 (too strong)
 Sync. #92 (too weak)
 Sync. #93 (too strong)
 Sync. #94 (too weak)
 Sync. #95 (too strong)
 Sync. #96 (too weak)
 Sync. #97 (too strong)
 Sync. #98 (too weak)
 Sync. #99 (too strong)
 Sync. #100 (too weak)

Fig. 3—Circuit diagram of Walsco, Model PC9 printed circuits receiver.



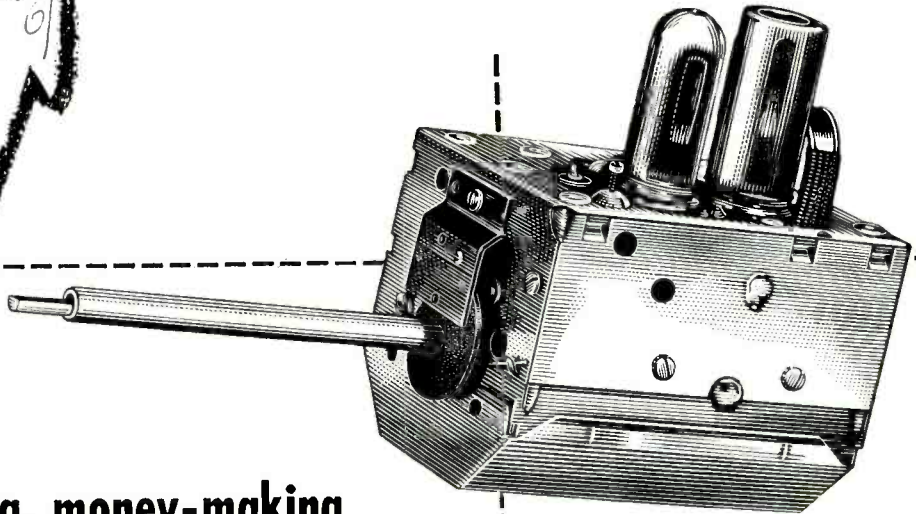**NOW! Any TV serviceman may
ADD \$60, \$100 OR MORE A
WEEK TO GROSS PROFITS!**



Share in the big, money-making tuner replacement market!

Hundreds of TV set owners in your community will welcome the sharper, stronger pictures afforded by newer, more powerful Standard cascode and pentode tuners. And a completely new Standard replacement tuner often costs your customer *less* than the parts and labor required for a major repair to the original tuner.

Approved Standard Tuners Install Faster, Easier!

Standard replacement tuners have shafts and leads easily cut to fit any set. In most jobs the tuner mounts into the space occupied by the original tuner with no alteration of the cabinet front.

Get Extra Profits Through Easy Conversion to UHF!

Set owners demand adaptability to UHF—and get it when you install Standard replacement tuners. Standard UHF conversion strips are priced to sell, permit easy, perfect tuning, and require no outside cabinet, adjustments, wires or extra parts of any sort.

Sell Approved

STANDARD TV REPLACEMENT TUNERS TV-2232—TV-1532

**Super cascode and pentode models
designed and built especially for the
replacement market**

STOP COSTLY CALLBACKS!

Install only APPROVED Standard TV replacement tuners. Non-approved tuners often *can not* be adapted to a particular set with satisfactory results. Each approved Standard tuner comes individually boxed, complete with circuit diagrams and installation data. Accept no substitutes!

Standard
COIL PRODUCTS CO., INC.

CHICAGO • LOS ANGELES • BANGOR, MICH. • NO. DIGHTON, MASS.

Export Agent: Rocke International Corporation, 13 E. 40th Street, New York City

Get set for bigger profits with Standard Coil's line of TV replacement tuners. Call your jobber today or write Standard Coil Products Co., Inc., 2085 North Hawthorne Avenue, Melrose Park, Illinois.

In TV it's Standard

SNYDER

5-D PUSH BUTTON

Directronic®
INDOOR TV ANTENNA

for BLACK and WHITE or COLOR



SNYDER Manufacturing Company

TWENTY-SECOND AND ONTARIO STREETS
PHILADELPHIA 40, P.A.

TV INSTRUMENT CLINIC

PART 5

Based on CHALLENGE CLINIC demonstrations, this new series discusses many measurement and test problems raised by service technicians.

By ROBERT G. MIDDLETON

Field Engineer,
Simpson Electric Co.

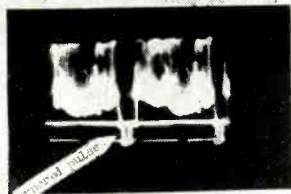


Fig. 1—Scopes with wide band vertical amplifiers display square corners on pulses.

Q. I have two scopes in the shop, but they do not show the same waveforms when testing horizontal sync pulses; also, when testing vertical sync pulses, the horizontal lines in the pattern appear much brighter than the vertical lines in the pattern. What is the reason for these troubles?

A. Scopes with wide-band vertical amplifiers display the square corners of pulses, as shown in Fig. 1. However, scopes with narrow-band vertical



Fig. 2—Rounded pulse display.

amplifiers round off the corners of pulses, as illustrated in Fig. 2. Waveform displays often exhibit considerable difference in the brightness of horizontal and vertical excursions in the pattern (Fig. 3) because of velocity modulation; i.e., the beam may

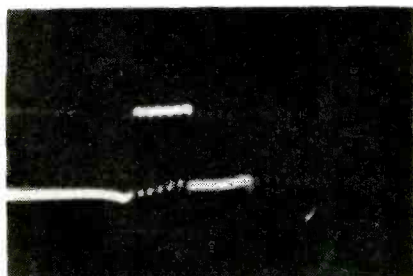


Fig. 3 — Difference in brightness caused by velocity modulation.

be traveling faster in the vertical direction than in the horizontal direction; this difference in the speed of beam travel results in velocity modulation of the pattern brightness. Velocity modulation becomes less apparent when the vertical-gain control

is reduced in setting, and the horizontal-gain control is advanced in setting. To avoid distortion of high-frequency waveforms such as horizontal sync pulses, make direct connection of the video-amplifier output to the vertical-deflection plates to the CRT in the scope.

Q. When checking the video signal in some receivers, the vertical sync pulse appears to fall below the level of the horizontal pulses. Then, after the vertical pulse passes, the response rises again. What causes this trouble?

A. The situation noted above is illustrated in the photo of Fig. 4B. The vertical sync pulse falls in the display because of differentiating action in the video amplifier. For example, the coupling capacitor C shown in Fig. 4A may be found to be too small, or the grid-leak resistor R may be found to be too small. As a result, the theoretical signal shown in the diagram becomes distorted in practice as seen in the photo. (Note that the scope display is "upside down" with respect to the diagram.)

Q. My scope does not sync tightly on some of the waveforms encountered in the TV chassis. What can be done to improve the sync lock?

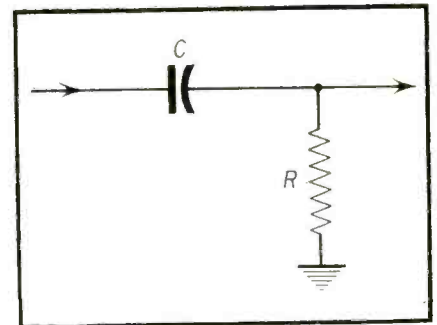


Fig 4A—An RC coupling arrangement such as used in a typical video amplifier stage.

A. A sync-sharpener may be used, as shown in Fig. 5. The sync-sharpener differentiates the waveform, and converts it into spikes which are usually more effective in locking the horizontal sweep circuit of the scope. Video signals are often difficult to lock because the camera signal is a random changing voltage; in such case, the

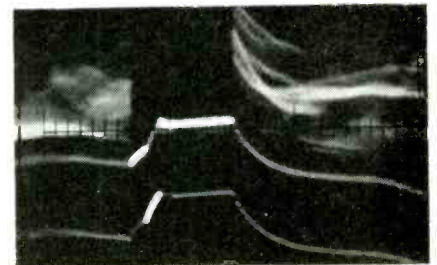


Fig. 4B—When the time constant RC is too small to accommodate the vertical blanking pedestal, the pedestal becomes differentiated (low frequencies are lost and shifted in phase).

operator will often find it advantageous to utilize the external sync facility of the scope. Switch the scope


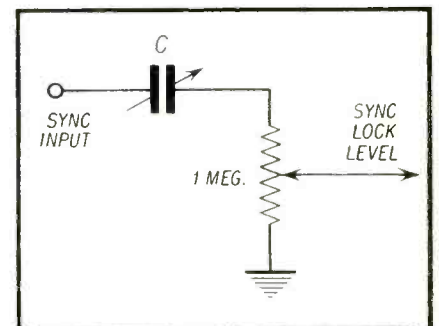


Fig. 5—A sync-sharpener arrangement for obtaining better sync lock of the pattern on the scope screen, under difficult circumstances. The value of C must be determined experimentally.

to external sync, and run a test lead from the external sync post to a point within a few inches of the picture tube screen. The pulse radiation from the picture tube will provide a clean tight locking voltage.

TRANSISTOR

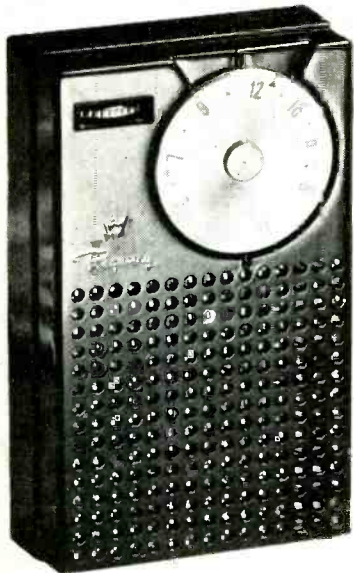

PORTABLE

The commercial applications of new components and circuitry continues without a letup as is evidenced by this revolutionary portable radio

Full view of transistor portable radio. Relative size compared to that of a teacup is shown in the upper right corner.

THE revolutionary pocket radio described below is the first in the history of the electronics industry to use transistors instead of tubes, and is now in production by Regency of Indianapolis.


According to Mr. Edward C. Tudor, I.D.E.A. prexy, the Regency pocket radio represents the first commercial adaptation of the transistor to a radio. "We were able to achieve this—and the accompanying miniaturization—through close cooperation with Texas Instruments Incorporated of Dallas, who effectively engineered and produced the essential high performance transistors that made our radio possible," he said.

"The development of the transistor itself marks a significant milestone in the history of electronics," he said. "Just as its perfection and adaptation enabled us to manufacture the Regency pocket radio, so does its development promise to change the size, appearance and nature of hundreds of other items in our daily life—possibly even our way of life itself," he added. "We are pleased to have worked with Texas Instruments, a company so prominent in this important revolution in our industry. This transistor development, in our opinion, rivals their important exclusive production of silicon transistors and assures the industry of more developments to come," he added.


Technical Features

Some of the interesting technical features of this receiver are as follows:

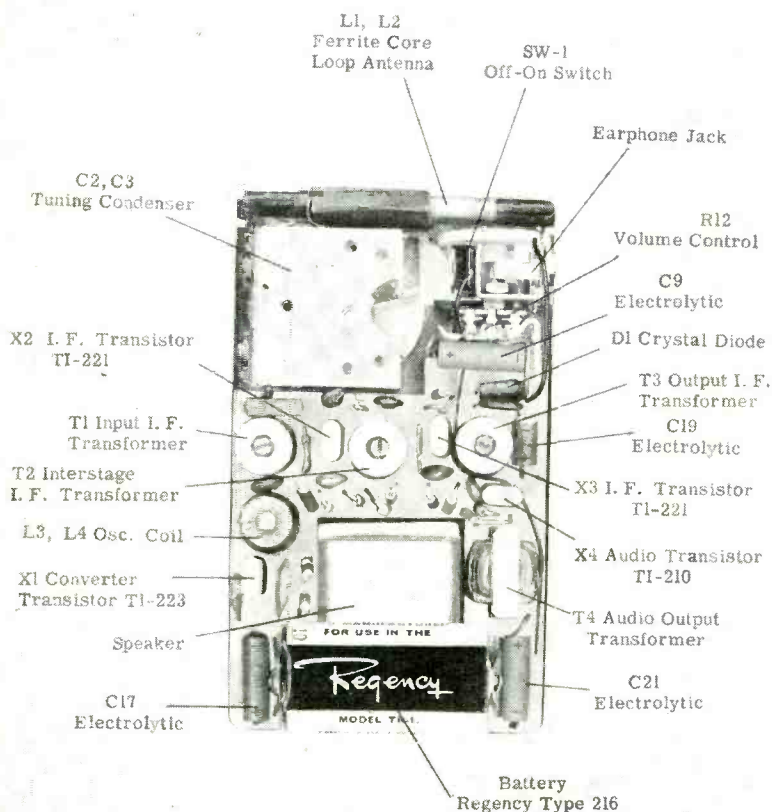The power supply is a single $22\frac{1}{2}$ volt hearing aid battery. The power drain is approximately 4.3 ma with no signal, reducing to about 4 ma with *ave*



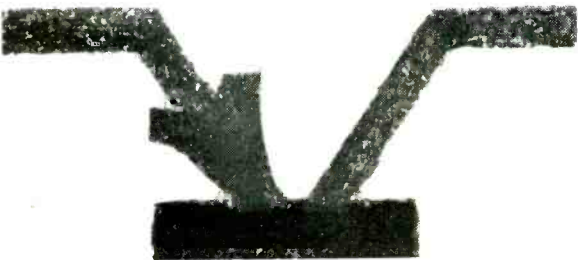Exposed view of chassis shows various components corresponding to circuit diagram notations. Observe use of miniature components.



action on a local station. Battery life varies between 20 and 30 hours, depending on use.

New high performance NPN, grown junction germanium type transistors are used, developed by Texas Instruments Incorporated, for this receiver application. These are as follows (see schematic):


- X1. Converter Oscillator—Texas Instruments No. TI-223
- X2. First Intermediate Frequency Amplifier—Texas Instruments No. TI-221

X3. Second Intermediate Frequency Amplifier—Texas Instruments No. TI-221

X4. Output Audio Amplifier—Texas Instruments No. TI-210

D1. Is a germanium diode with a selected characteristic for low forward impedance at low signal levels

Raytheon—CK706A or
Tungsol—TS117

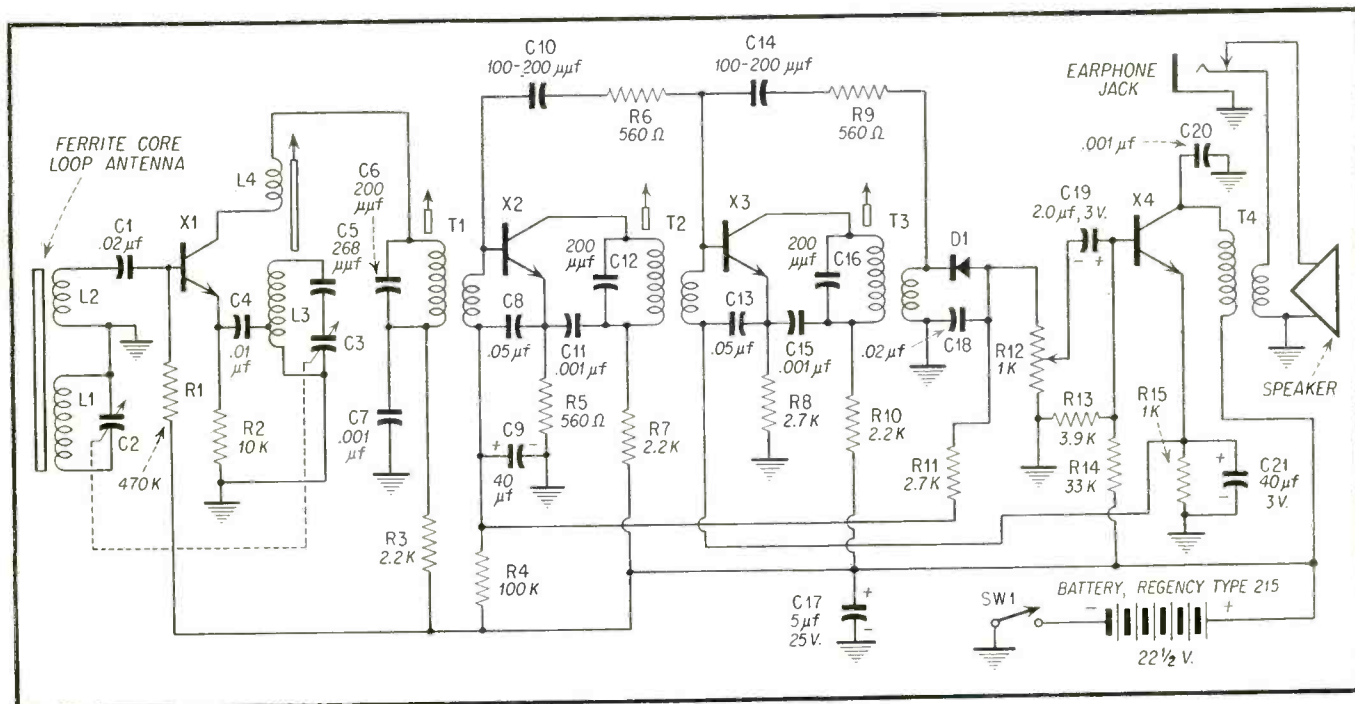


Circuit diagram of Regency Model TR-I transistor pocket radio receiver.

A new standard in
electrical and mechanical
perfection in all **32**
new YAGI antennas





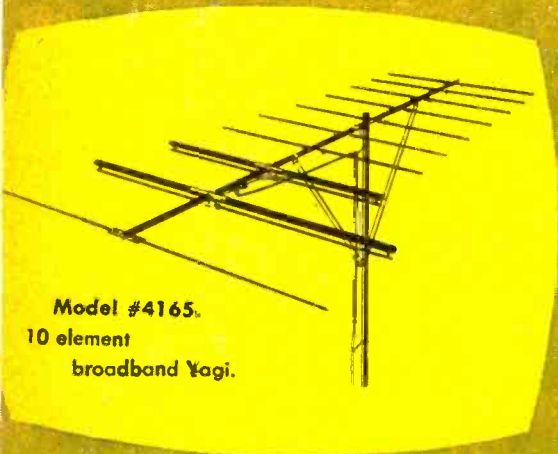Featuring the new
WALSCO "Odopus"
Model #4110.
A combination
Yagi-conical for
superlative all-channel
reception.




Model #4165.
10 element
broadband Yagi.

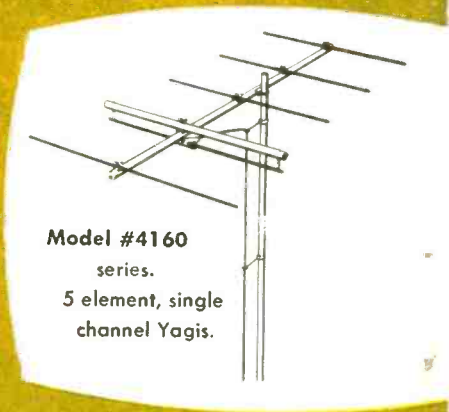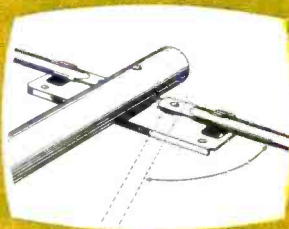Walsco's exclusive
"umbrella" snap-out
design provides perfect
element alignment
instantly.




Model #4160
series.
5 element, single
channel Yagis.

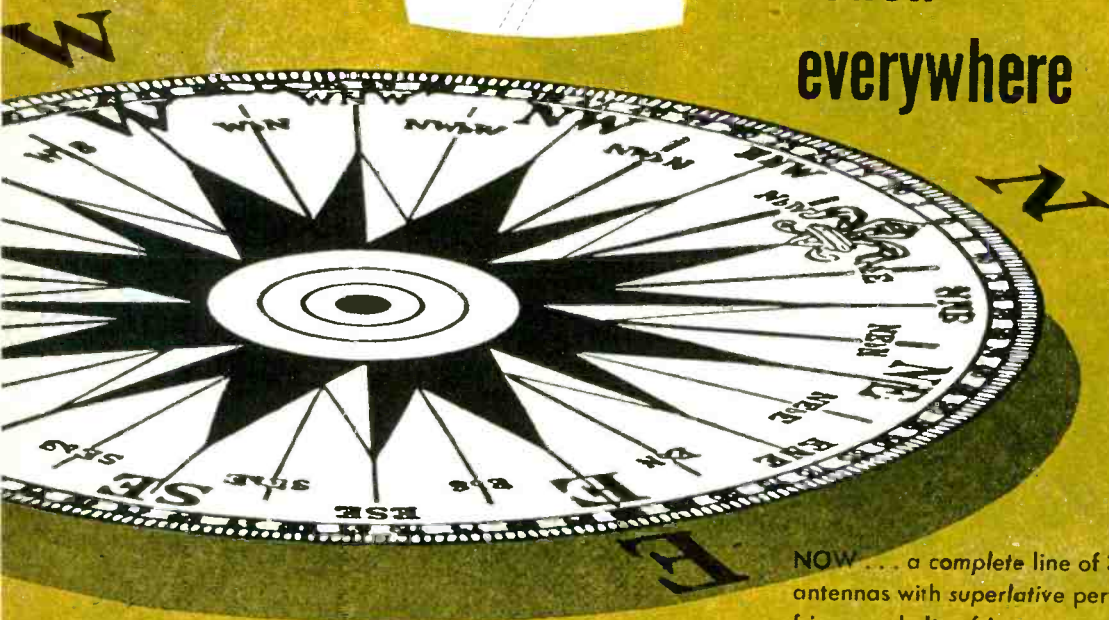WALSCO "futurized" YAGIS reach everywhere



NOW . . . a complete line of 32 "futurized" Yagi antennas with superlative performance . . . for fringe and ultra-fringe areas; for black and white and color or all present and future channels. No loose hardware . . . completely pre-assembled using Walsco's exclusive "umbrella" snap-out design. Nothing compares at any price!

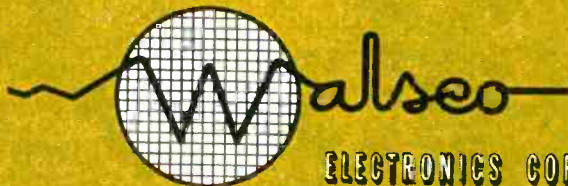
Write for complete information
on all 32 "futurized" Yagi models



ELECTRONICS CORPORATION

3602 Crenshaw Blvd. • Los Angeles 16, California

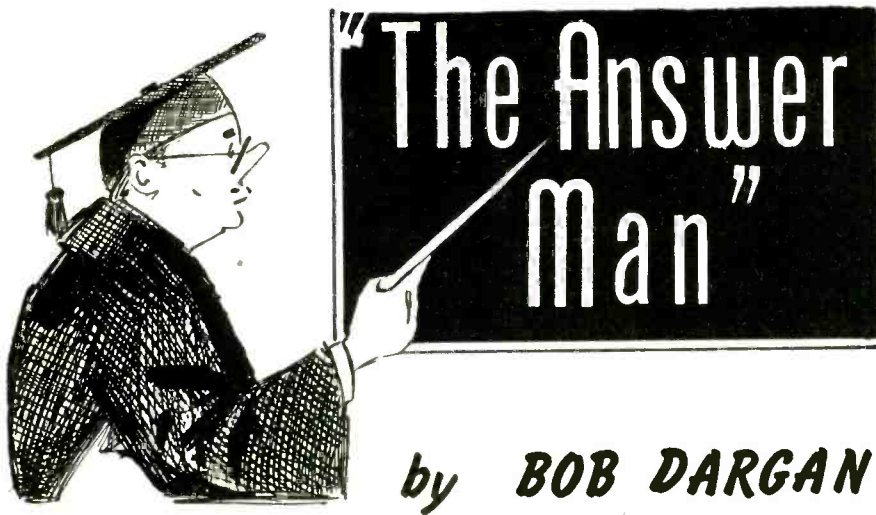Overseas Distributor:
Ad Auriema, inc. • 89 Broad St., New York 4, N.Y.



Do you have a vexing problem on the repair of some radio or TV set? If so, send it in to the Answer Man, care of this magazine. All inquiries acknowledged and answered.

Note: Only communications with Radio-TV Service Firm letterheads will be considered and answered. Please indicate make, model, and chassis number of receiver.

G.E. Model 24C101— Ripples in Pattern

Dear Answer Man:

I have a G.E. receiver Model 24C101 that has a peculiar condition in it. There are ripples in the picture but they are not horizontal or vertical ripples as far as I can determine. In examining the condition on a test pattern they seem to be more pronounced in the outer circle of the pattern. These waves seem more noticeable at the top of the test pattern circle and are present with any channel selected.

I have checked the usual parts such as tubes, voltages, resistors, etc. The tubes have all been replaced and all voltages are correct as indicated in the

service literature. The only thing that might be of help is the fact that this ripple can be affected a little with the horizontal hold control adjustments. At a certain point the waviness is reduced to a minimum but still is noticeable. What can be causing this trouble?

E. V.
Philadelphia, Pa.

The condition you have described is usually termed "Piecrusting" and is due to an open condenser in the automatic frequency control circuit of the horizontal oscillator.

The horizontal *afc* circuits provide a correction voltage to be applied to the horizontal oscillator circuit; and in this case to the reactance tube. This correc-

tion voltage should bring the oscillator to the proper operating frequency. However, if there is something wrong in the *afc* circuit so that an incorrect voltage is applied to the oscillator or its reactance tube the circuit will hunt for the correct frequency where the sync pulse is locked in with the deflection system. With this hunting process will be a slight shift in phase of certain portions of the picture. A group of horizontal lines will be shifted first to the right and then to the left as the horizontal oscillator hunts for the correct frequency and phase. The effect is a ripple on the outer circles of a test pattern or what can easily be recognized as "Piecrusting".

The *afc* circuit, because of a defective component, will over-correct in one direction by applying too much voltage to the horizontal oscillator circuit. This over-correction then causes the horizontal oscillator to shift in phase a slight amount. Then it will over-correct in the opposite direction. This results in a slight shift in certain portions of the picture, each horizontal sweep line not being directly below the previous line.

Varying the horizontal hold control will change the amount of ripple in the picture because this alters the horizontal oscillator voltage in phase. Therefore, varying the horizontal hold control will permit varying degrees of oscillator hunting and different amounts of ripple.

As shown in Fig. 1 three filter condensers should be checked to determine which condenser is open. The most likely condenser to suspect is the .015 μ f condenser in series with 68K resistor.

Sylvania Chassis 1-510-1— Horizontal Drifts

Dear Answer Man:

In servicing a Sylvania Chassis 1-510-1 the reason for the receiver being taken to the shop was for poor vertical lock-in action. The integrator network was checked and found to be open. Another one was obtained and installed. Then I found that I also had horizontal sync trouble. The integrating network corrected the vertical sync trouble but the horizontal oscillator drifts as though there were no sync pulses to lock it in. I have gone over the circuits a number of times and I haven't been able to locate the trouble. Do you have any ideas on this one? Could there be something wrong in the new integrator network?

D. S.
St. Louis, Mo.

Undoubtedly what has happened is that in the installation of the integrating network the terminals were reversed.

These small printed circuits are good and have been used in quite a number

[Continued on page 54]

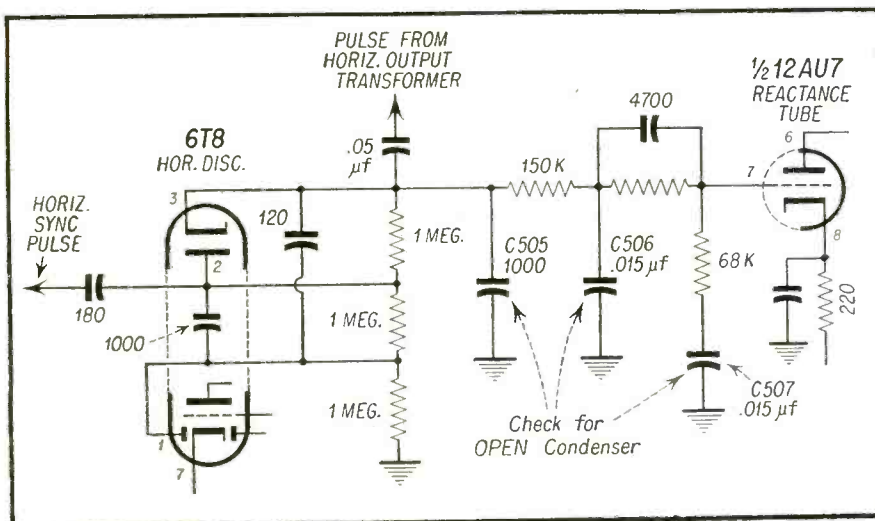


Fig. 1—G.E. Model 24C101 Horizontal Phase Comparer circuit and reactance tube.

A New

TV Remote Control Tuner



by **Irvin R. Gwartz**
Remot-O-Matic
Los Angeles, Calif.

*Description of a versatile
TV remote control unit, a good source
of income for the enterprising
and sales-minded dealer or serviceman.*

THE advent of remote control units for television receivers has opened another profit door for the TV dealer and technician. These accessories are now priced so that all owners of TV receivers can afford them. A little enterprise on the part of the dealer in making his customers aware of the advantages of this device should net him handsome returns in the way of sales and installation fees.

The De Luxe model of the Remot-O-Matic provides a remote unit which gives the user control of six functions, these being:

1. On-and-off control
2. Sound control
3. Brightness control
4. Contrast control
5. Channel switching
6. The convenience of taking the sound control away from the set so that the sound is controlled from the remote unit or at the set itself . . . as desired.

Described below are the installation instructions for the Remot-O-Matic remote control unit. These instructions are presented in order to give the technician an idea of the relative ease with which these units can be installed. Detailed wiring instructions have been omitted inasmuch as the wiring diagram

shown on the next page is self-explanatory. However, detailed wiring instructions do come with every unit.

Installation Instructions:

1. Remove chassis from the cabinet and place it on working area so that the tuner is easily accessible.
2. The Motor Assembly is to be mounted directly behind the tuner with the shaft of the Motor Assembly lined with the shaft of the tuner as follows:

[There must be room for it . . . or the Remot-O-Matic Adapter kit must be used for interior installation.]

Select the location to be used for mounting the brackets (Figure 1). Various designs of chassis allow for different locations for the mounting brackets. In Figures 2, 3 and 4 you will see three different locations and methods for mounting the brackets. These three locations and methods cover nearly all possibilities, however, the brackets are so constructed that they allow for wide range of positioning in increments of 1/16".

3. Where the methods in Figure 2 or Figure 3 apply, take the following steps:

- A. Decide on the surface where you intend to mount the bracket whether it be on the side of the chassis or the main base of the chassis.
 - B. Place brackets of Figure 1 together to form complete mounting brackets as shown in Figure 5.
4. Mount the Motor Assembly to bracket B (Figure 1) and secure with two #8 screws and lock washers . . . into the mounting studs of the Motor Assembly.
 5. We have a 6" shaft on the Motor Assembly which may be cut to any length. Place the Motor Assembly in the approximate position you have in the chassis and thus determine the length of shaft needed. It is important that a gap of from 1/32" to 1/8" be maintained between the shaft of the tuner and the shaft of the motor.
- Note: If the tuner shaft does not protrude through the rear wall of the tuner, it will be necessary to drill a hole in the rear wall of tuner so that the coupler can slide onto the tuner shaft without binding.

[Continued on page 55]

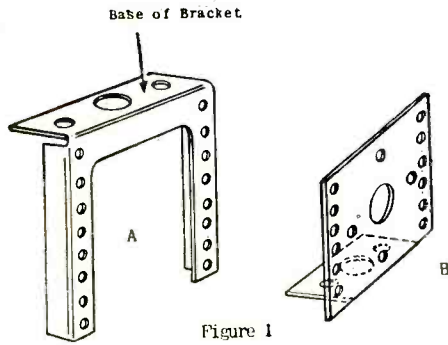


Figure 1

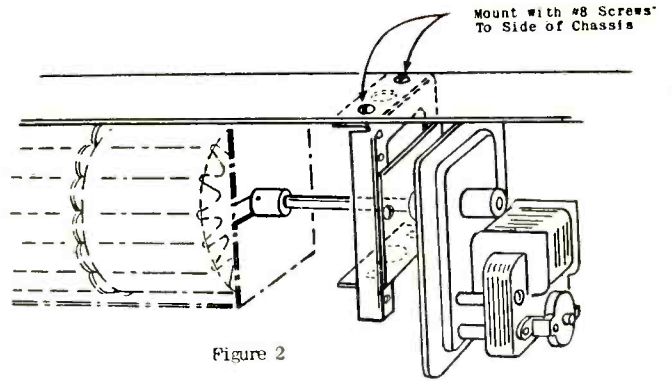


Figure 2

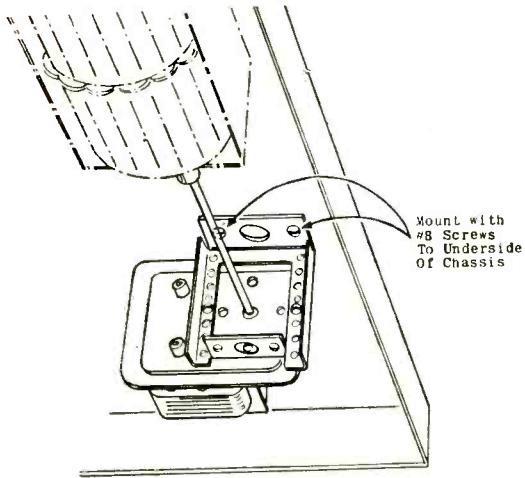


Figure 3

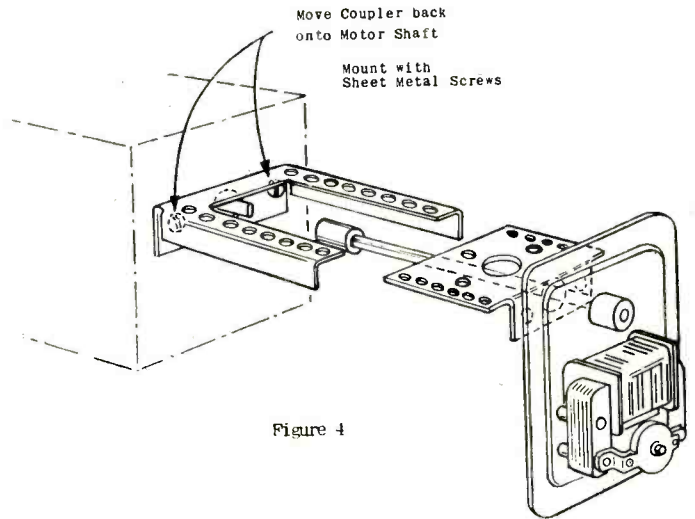


Figure 4

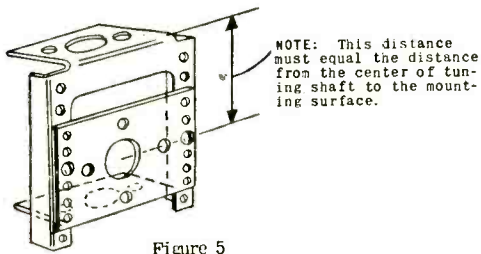


Figure 5



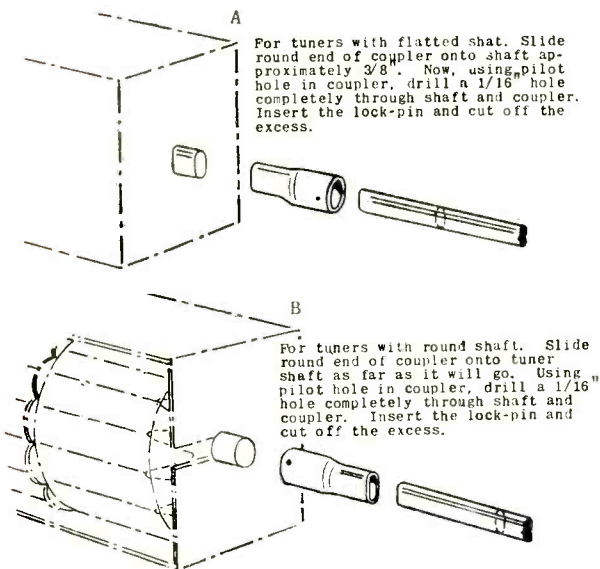


Figure 6

WIRING DIAGRAM

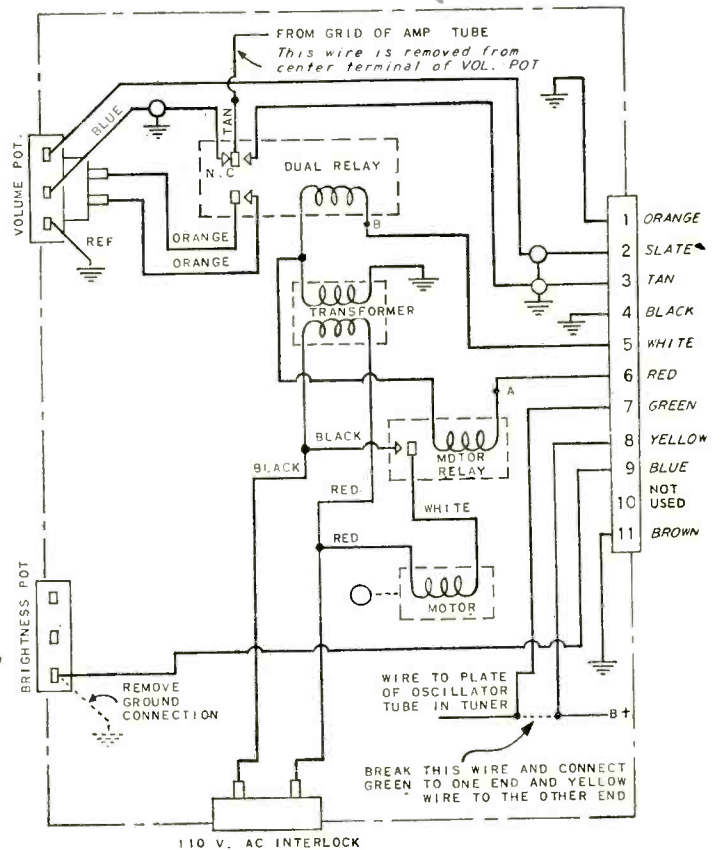

FOR GREATER PROFITS

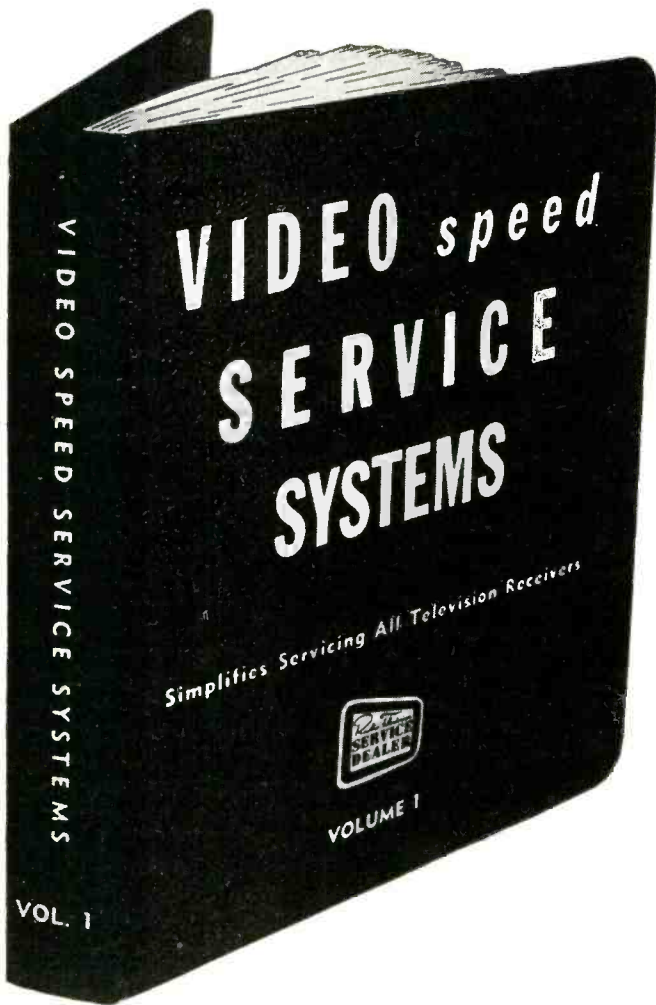

SPEED UP YOUR SERVICING with THIS NEW BOOK

which shows you how to take care of and repair in the quickest possible time:

- Common troubles characteristic of certain receivers
- "Bugs" which might take you hours to find
- Factory and field service changes

SET UP SO THAT YOU CAN MAKE THESE REPAIRS IN THE SHOP OR IN THE FIELD WITHOUT REFERENCE TO ANY OTHER SOURCE

Contains over 600 Service Items representing over 1000 of the most-serviced Television models now in use. Over 25 different manufacturers' lines are covered.

\$4.95

(Add 3% Sales Tax in New York City)

DISTRIBUTORS—ORDER YOUR SUPPLY NOW!

Service Dealers—get your copy of VSSS from your Distributor. If he can't supply you, order direct by mail from us.

Video Speed Servicing Systems IS GUARANTEED to Simplify Servicing All TV sets. A number of new Data Items are published in every issue of "Radio-Television Service Dealer" as a regular monthly feature.

TEAR OFF AND MAIL NOW

RADIO-TELEVISION SERVICE DEALER

67 West 44th Street, New York 36, N. Y.

Please send me post-paid VIDEO SPEED SERVICING SYSTEMS Volume 1. Enclosed herewith is


my check money order for \$ _____ for _____ copies at \$4.95 each. (Add 3% Sales Tax in New York City)

Name

Address

CityZone State

applications of

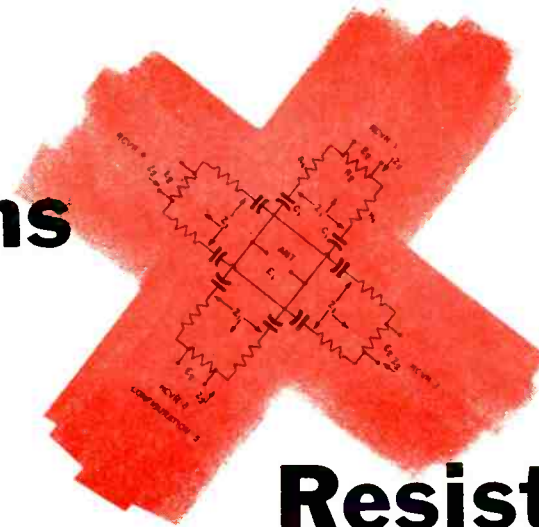

Resistive Networks

by J. C. Geist

Comprehensive design data and applications of resistive networks in TV measurements and antenna signal termination and distribution.

MOST technicians have used resistive networks in some phase of TV service work. However, there does not seem to be a general recognition of the wide variety of uses these simple devices can serve as auxiliary service aids. Table 1 lists a number of different types of resistive networks and the pertinent characteristics of each type. The table in turn refers to the applicable circuit configurations which are shown in the attached drawings. While it is true that for most of the applications listed, there are other devices available with less signal losses and more refined characteristics, the resistive network generally represents the simplest, least expensive and most convenient answer when the losses can be tolerated. Furthermore, when arranged compactly, using short lead lengths, the resistive network will be useful over extremely wide frequency ranges. Simple networks made up of standard composition resistors will give

Network	Configuration	Resistor Values in Ohms	Nominal Z1 in Ohms	Nominal Z2 in Ohms	E2/E1	Insertion Loss in db
A	1	R1=110 R2=62 R3=150	72	300	.54	5.3
B	1	R1=130 R2=56 R3=150	50	300	.52	5.7
C	2	R1=82 R2=220	300	300	.47	10
D	2	R1=120 R2=68	300	300	.10	20
E	3	R1=78 R2=160 R3=220	300	300	.10	20
F	4	R1=100 R2=140	72	72	.36	10
G	4	R1=360 R2=88	72	72	.10	20

Table 1—Characteristics of configurations discussed in the text.

good performance over the entire range covered by the high and low television vhf channels. With sufficient care in construction using the smallest resistors and very short lead lengths this range can even be extended into the uhf tele-

vision band. Some of the ways in which these networks can be advantageously put to use are discussed below.

Sweep Generator/Receiver Impedance Matching

When a sweep-frequency signal generator is used for TV tuner alignment the transmission line from the generator must be terminated in its characteristic impedance. If the termination is not of the correct value the transmission line will act as a frequency sensitive tuning element (VSWR varying with frequency) and thus cause an erroneous indication of the bandwidth characteristic of the tuner. Most sweep generators utilize a low-impedance unbalanced (one side grounded) coax output to simplify output attenuator construction and to reduce leakage. Since the tuner has a balanced (neither side grounded) antenna input with an impedance of 300 ohms it is necessary for the generator coax to be terminated by a device which will match the high receiver impedance to the low coax impedance and at the same time convert from a balanced to an unbalanced circuit. Networks A or B, depending on the generator coax impedance, are designed to do this job. The resistive network does not provide a completely balanced output as do other devices such as *rf* transformers or "balun" transmission line networks and it introduces greater losses than these latter devices. However, the resistive network provides an output sufficiently close to perfect balance to accomplish a satisfactory termination, and at the same time offers the advantages of extreme simplicity and usefulness over a wide frequency range. The relatively low

[Continued on page 57]

Configuration	Receiver Outlets	Resistor Values in Ohms	Nominal Z1 in Ohms	Antenna Line Termination in Ohms	Z2 in Ohms	E2/E1	Insertion Loss in db	Receiver Isolation in db
5	2	R ₁ = 200 R ₂ = 580	600	$\frac{600}{2} = 300$	300	.75	9	19
5	3	R ₁ = 350 R ₂ = 610	900	$\frac{900}{3} = 300$	300	.21	14	29
5	4	R ₁ = 550 R ₂ = 390	1200	$\frac{1200}{4} = 300$	300	.13	19	36
6	2	R ₁ = 240 R ₂ = 130 R ₃ = 32	600	$\frac{600}{2} = 300$	300	.14	17	34

Table 2—Resistor values and characteristics for different combinations of impedance and number of receivers in the system.

AUDIO ADAPTATIONS for Profitable Servicing

AES COL RCA COL FFrr NAB TAPE AUX

by **Gil Tint**
Practical and profitable suggestions for increasing the utility of Hi-Fi systems

THIS article provides a number of adaptations that may be made to obtain more versatile performance of audio equipment where a hi-fi installation has already been made. The modifications outlined herein do not require chassis pulling or alteration. All work is done primarily by means of adapters and external mountings.

An effective way to satisfy the hi-fi customer is to provide him with "extras"—features which make his installation more than just an interconnected group of ready-made components. What is nice about these modifications is that, while they not only make an audio system more attractive, they are also simple to install and add very little to the audio man's costs. Here are a few such additions which the writer has found quite useful.

Feeding TV Sound Through the HI-FI System

Almost every TV ad one sees stresses the advantages of FM sound. The average consumer is led to believe that his set is capable of wide range audio reproduction. Unhappily, this is not the case. After the sound information passes (relatively unscathed) through the tuner, if stages, and FM detector, it is squeezed through one single-ended audio stage and fed to a speaker just about up to reproducing a telephone conversation faithfully. Why waste this hi-fi potential? This is a good question to ask the customer—from a sales point of view. Invariably, he will welcome the chance to improve his TV sound by

utilizing his audio system. The necessary circuit changes could be made by pulling the chassis, drilling the required holes, mounting a terminal strip and making the electrical changes. As every technician knows, however, chassis-pulling involves extra time and labor and should be avoided where possible. The advantages of the methods described here are that all work takes place on the top side of the chassis, and the adapters can be prepared during free time and merely plugged in when needed.

First an "S" type of socket (Fig. 1, item A) is fitted into the shell of a tube base (B). The #5 pin of the "S" socket is grounded, thereby grounding out the grid of the audio output tube. The #5 pin of the tube base (B) connects internally to the output connection of the first audio tube so that a lead connected to this point may be brought out to the hi-fi power amplifier.

The diagram in the lower right hand corner of Fig. 1 shows how this modification renders the output stage of the TV receiver inoperative. The incoming signal, on the other hand, is transferred through the connecting cable to the desired hi-fi audio amplifier and speaker combination.

A shielded cable length of no more than 5 feet is practical in this case because of the high impedance circuit involved. Excessive hum pick-up and high-frequency attenuation would result if a longer cable were used. Aside from the cable, the only materials needed are the tube base of an old octal tube, a suitable phono-input connector and an Amphenol "S" type octal socket, 78-S8. This socket is perfect for this application since it exactly fits the tube base. A hole should be drilled in the side of the base near pin 5 for bringing out the audio lead. After making the electrical connections, some speaker cement

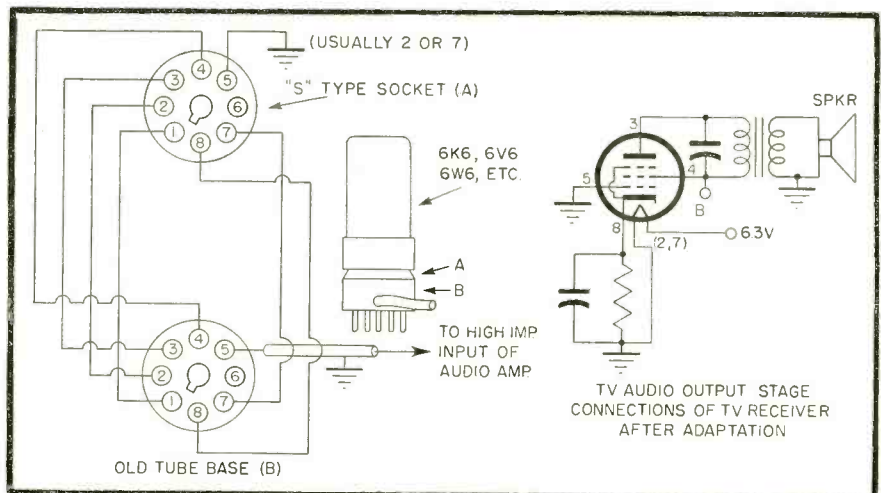


Fig. 1—Recommended when amplifier is close to TV receiver.


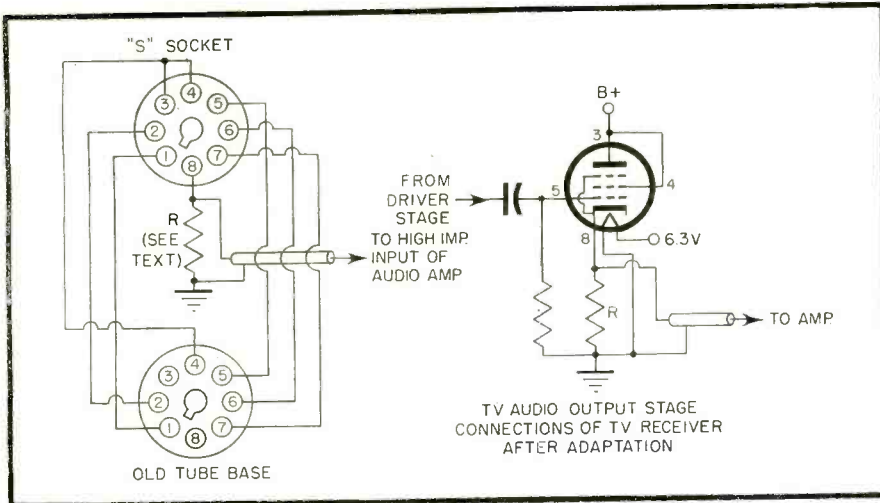


Fig. 2—Cathode follower for remote connections.

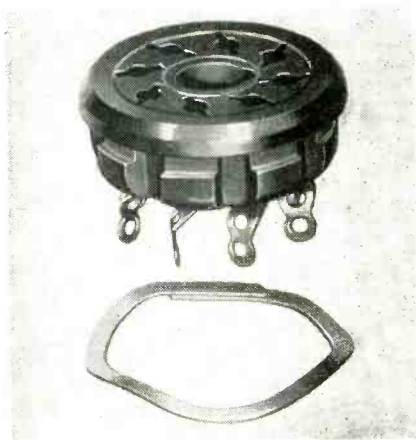

An "S" type Octal Socket.

should be applied where the socket and base meet. When the joint has dried, the original tube can be replugged into the adapter, and the adapter plugged into the power output stage of the TV set. It is important that the audio output then be connected to the high imped-

ance input of the audio amplifier. Overloading and distortion will result if the pre-amplifier input is used.

A metal tube of the same type can be adapted by the above method if precautions are taken to see that pin 1 on the tube socket has not been used as a *dc* tie-point by the manufacturer. This condition would render the tube shell hot to ground and create a shock hazard.

Adapter for More Remote Locations

Figure 2 illustrates a variation of the above which can be used when the TV receiver is remotely located from the audio amplifier. Before trying this one, however, the customer should be warned that having the sound come from a different point in the room from the picture might seem peculiar at first. Adjusting to it isn't difficult, though, and the improved quality will be worth the effort. As above, only octal tubes

[Continued on page 49]

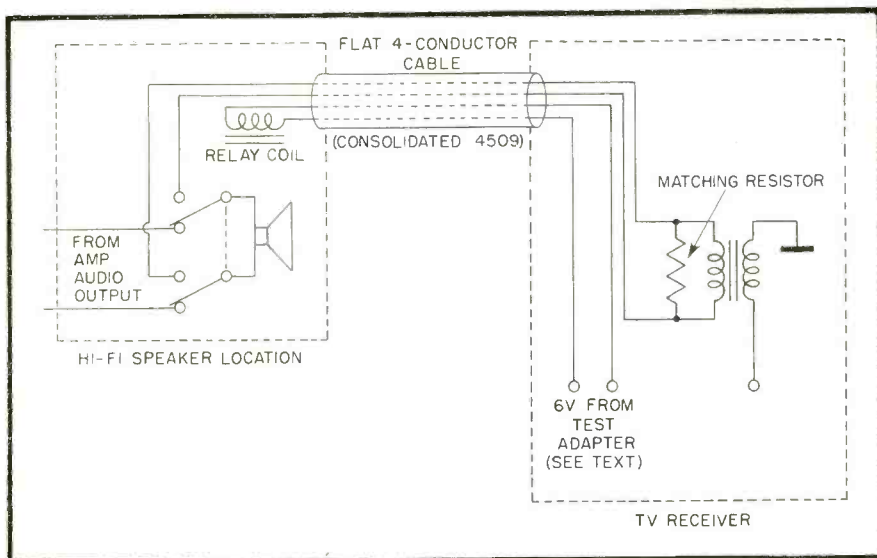


Fig. 3—Automatic switching of Hi-Fi speaker to TV output.

NEW Columbia PACKAGING

- For easier selling
- For quicker inventory
- To save time and money



VHF-UHF FOAM POLYETHYLENE TV TRANSMISSION LINE

100 ft. of high quality VHF-UHF cable in an attractive multi-colored box for easy handling. Takes little space and is quickly identified. Installs as easy as flat T/V line.



NEW 300 OHM TELEVISION LINE PACKAGE

100 ft. of wire in printed, clear polyethylene package with the television line neatly coiled, banded, identified. Price lower than comparable packages.

EXCLUSIVE!

NEW "PERMALINE" 300 OHM POLYETHYLENE TV TRANSMISSION LINE

- Will outlast any 300 ohm line in use today
- Far superior... resists practically anything
- NO DETERIORATION

Write for your FREE SAMPLE TODAY!

"Columbia" products are available at recognized distributors.

Columbia WIRE & SUPPLY CO.

2850 Irving Park Road, Chicago 18, Ill.
"America's Most Complete Wire Line"

THIS installment is devoted to three sync amplifier problems. The use of the oscilloscope is extremely important in hunting down these faults. Equally important is the manufacturer's service data which usually contains the correct waveforms at the important places.

Admiral 21C1—Lack of horizontal and vertical hold

The receiver was turned on and it was observed that the horizontal and vertical hold would break as the contrast was lowered; however, at maximum contrast, the picture would hold properly. As this seemed to be a composite sync problem, V403, 12AU7, the sync separator and clipper, and V401B, 1/2 6SN7, sync inverter were individually replaced but without effect.

Before going any further, the diagram was consulted. The composite sync, video and blanking voltage is fed through a coupling network consisting of R323, R329, C315, C308, to V403A. The low plate voltage (32 volts) on V403A, Sync Separator, developed by R418, and R417, and the cut-off grid leak bias provided by R414 and C308 allow only the most positive peaks (sync pulses) to cause plate current flow. In this manner the blanking and video voltage is eliminated and only the sync pulses are amplified. V403B is the sync clipper, and because of the low plate voltage caused by R420 and the grid leak bias caused by C409, and R416, the negative sync and noise pulses drive the tube to cut-off; thus achieving the desired clipping

The Work Bench

by PAUL GOLDBERG

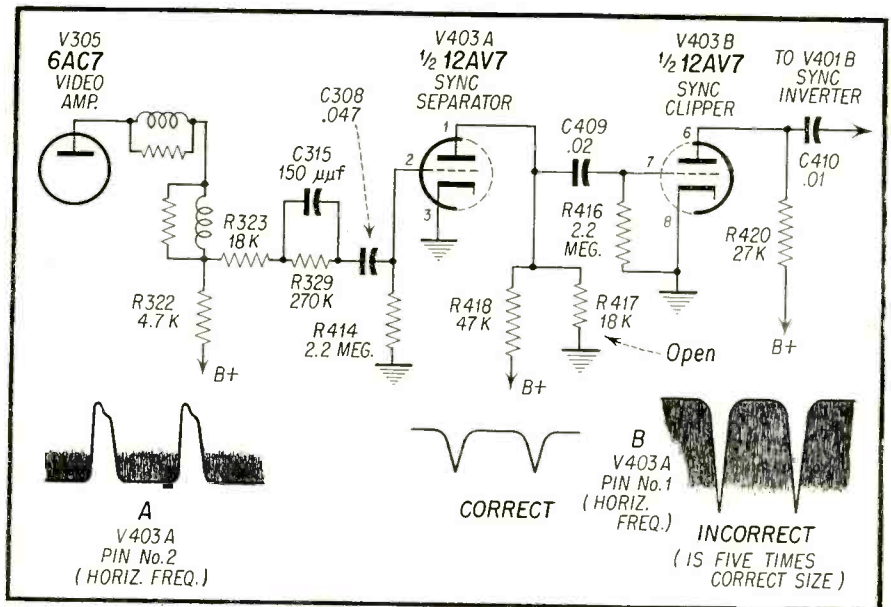


Fig. 1—Partial schematic of Admiral 21C1 sync section.

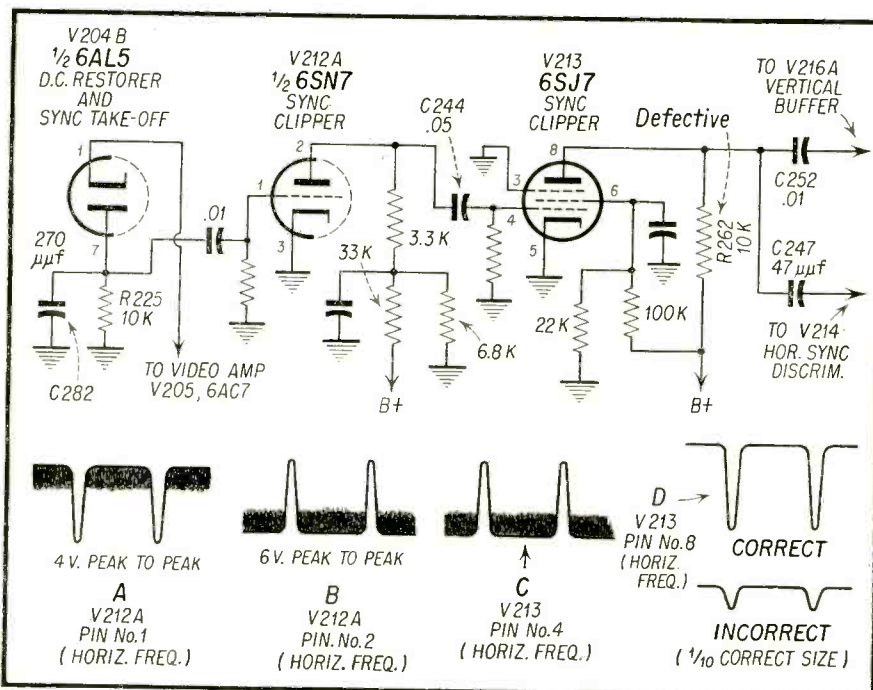



Fig. 2—Partial schematic of DuMont RA 103C sync section.

and limiting of the noise and sync pulses.

To get back now, the scope was set up to check a few wave forms. A wave form check was made at pin #2 of V403A, but it was found to check correctly with the manufacturer's service data. (Ref. to Fig. 1A). Next, a wave-form check was made at pin #1 of V403A. However, here the waveform did not check correctly with the manufacturer's data. (Ref. to Fig. 1B). In fact, the waveform measured about five times its correct size.

Now that the locality of the trouble had been placed, a voltage check was made at pin #1 of V403A. The voltage measured 130 volts positive. The diagram called for 32 volts positive. Next, R417 and R418 were resistance checked. R418 measured correctly but R417, 18K, was found to be open. It was immediately replaced and the receiver now functioned properly.

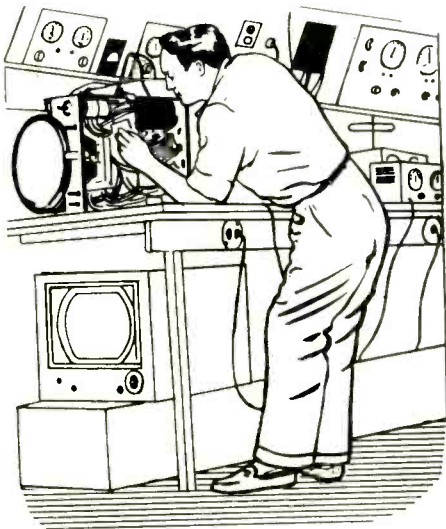Because R417 opened, the plate voltage jumped from 32 volts to 130 volts. With this plate voltage the negative grid leak bias developed was not



This Month:

SYNC AMPLIFIER PROBLEMS

enough to cut off V403A. Thus, the complete signal at the grid, pin #2, of V403A, appeared at the plate, pin #1. Therefore, because no elimination of the video and blanking pulses could take place in V403A, the video and blanking pulses triggered the horizontal and vertical oscillators, causing poor vertical and horizontal hold condition.

Du Mont RA 103C—Vertical roll and horizontal wobble

In this receiver it was observed that when the contrast was increased or decreased, even slightly, the picture would roll vertically. The picture also had a bad horizontal wobble. In fact, tapping any component in the horizontal sync or oscillator section caused the picture to wobble horizontally.

This was definitely a composite sync problem, so V212A, V213, and V204B,

the composite sync clippers and the *dc* restorer were replaced individually, but with no effect. The oscilloscope was next set up to make a few waveform checks and the diagram referred to.

Since negative composite sync pulses appear across R225, V204B, the diode rectifier, acts not only as a *dc* restorer, but as a sync separator. V212A, and V213 are the sync clippers. They manage to clip the signal at both ends. V212A, accomplishes this by virtue of a low plate voltage (+ 19 volts) and V213, 6SJ7, accomplishes this by virtue of a low screen voltage (+ 50 volts). In other words, the composite sync signal at both control grids drives the tubes into saturation and into cut off. Thus, the composite sync level is kept rather constant at the output of V213 because of the limiting action of these tubes.

A waveform check was made first,

at pin #1 of V212A. Here the waveform checked correctly with the service data (refer to Fig. 2A). Next, a waveform check was made at pin #2 of V212A and here again the waveform was correct. (Ref. to Fig. 2B). A waveform check was now made at pin #4, the grid of V213. This was also correct (Ref. to Fig. 2C). At pin #8 the plate of V213, however, the waveform was found to be one tenth its proper size (Ref. to Fig. 2D).

Voltage measurements were next taken at the plate and screen of V213. The screen voltage checked correctly at around 50 volts positive, but the plate voltage measured about 300 volts positive. It seemed that R262, 10K, was not dropping any voltage because the B+ side of this resistor also measured about 300 volts positive. R262 was then resistance checked and was found to measure about 200 ohms. C244, C252, and C247 were next measured for voltage leakage because of the possibility of their causing the defective R262. But all these condensers checked satisfactorily. The 6SJ7, V213 also checked okay. Thus, it was assumed that the low wattage rating of this resistor was the cause of its failure. This half watt resistor was now replaced with a new 2 watt 10K resistor (to be safe), and now the receiver functioned properly.

It is easy to understand that if R262, 10K, the load resistor across which is developed the composite sync pulse voltage, drops in resistance to 200 ohms, the load voltage will not be large enough to cause the vertical and horizontal oscillators to be triggered properly.

RCA 630 TS—Pulling at top of pix and vertical slipping

The receiver was turned on and it was observed that there was a quivering and pulling at the top of the picture. It

[Continued on page 49]

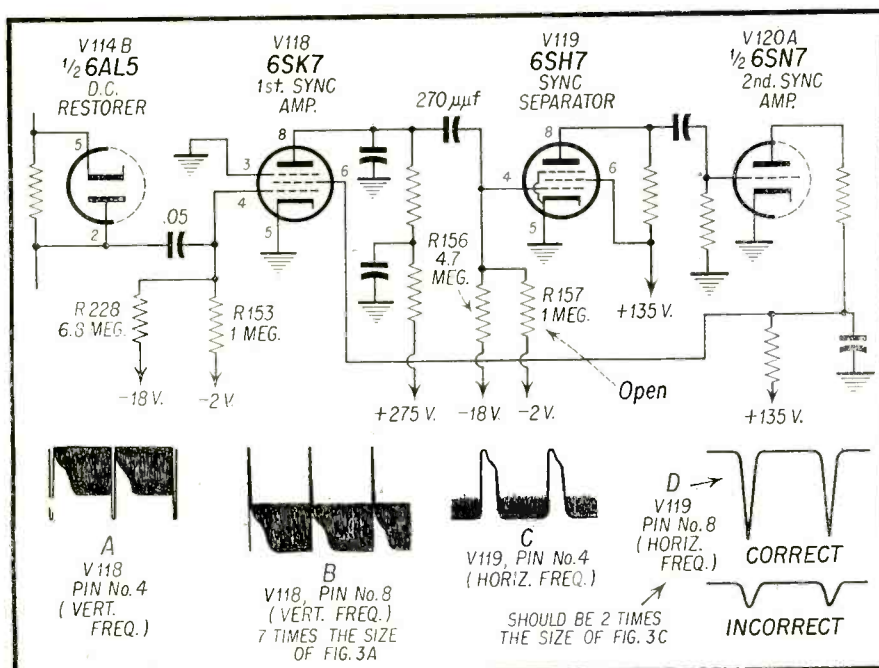


Fig. 3—Partial schematic of RCA 630TS sync section.

THE DETROIT SERVICEMEN'S SHOW



Photos courtesy of Michigan Press Photo Service

A number of distributors get together to put on a show for servicemen primarily with unparalleled results.

THE First Detroit Electronic Parts Show, staged at the Whitehall Bldg., State Fairgrounds, Detroit, Michigan on November 2nd and 3rd, 1954, attracted 6100 Radio and TV Dealers and Servicemen from the Greater Detroit area. The show was a great success.

The twelve independent electronic parts jobbers in Greater Detroit who sponsored the show in co-operation with manufacturers and members of the Wolverine Chapter of Representatives feel highly satisfied to have been of service to the Radio TV Service-Industry.

The show was opened by Lt. Governor Clarence A. Reid and Peggy Lee, well known recording artist. Mr. H. Hirt, Secy.-Treasury of Radio Specialties Co. was chairman of the event. Governor Williams sent his best wishes by telegram.

Following are some of the comments from a cross-section of the industry:

(1) *H. H. Rainier, Mgr. Electronic Product Sales, Sylvania Electric Products, Inc.*

Sylvania wishes to congratulate the Greater Detroit Distributors on their first undertaking of a show directed to dealers. This kind of effort demonstrates genuine sincerity on the part of the electronic distributors to bring the servicemen into direct contact with manufacturers and their products. Sylvania as a manufacturer who has always felt a close alliance with the service industry, feels that this initial venture by the Detroit Distributors was an outstanding success. We at Sylvania have attended many similar shows and we feel the Detroit Show is one of the best we have attended. Best wishes for continued success.

(2) *H. Kalker, General Sales Manager, Sprague Products Co.*

Let me congratulate you and your

committee for a very fine job in presenting the first Dealer Servicemen Show in Detroit, sponsored by the Distributors and the Representatives. Despite the inclement weather, I was pleasantly surprised at the thousands of Dealers, Shop Owners and Servicemen who came to the show, their hungry desire for information was well proven by the fact that by late evening most Manufacturers ran out of thousands of their pieces of literature. It is my hope that you will continue this program on an annual basis and that you have the Distributors, with the help of the Manufacturer, man the booths as these people are really your customers and not direct customers of the Manufacturers.

I am sure that in the next few months, you will have found that this Show has helped considerably in cementing a more personal and friendly relationship in addition to a business relationship between the Distributors, Representatives and Manufacturers. I was very happy to have had the privilege and opportunity to see the show in person.

(3) *John T. Thompson, Sales Mgr., General Electric Co.*

You and your committee are certainly



Mr. H. Hirt, chairman of the show.

to be congratulated on the complete success of the first dealer parts show conducted in the Detroit area. As far as I know, this is the first cooperative show of this type ever held for dealers and their technicians in the electronics service industry. Its complete success reflects the hunger of the dealer and his television and radio service technicians for more product information and guidance from his distribution suppliers and their manufacturing sources. We in the Tube Dept. of the General Electric Co. felt it a real privilege to participate with you in this progressive industry step and wish to assure you of our complete support in future activities of this type.

(4) *E. D. Powers, Exec. Vice President of Thordarson-Meissner*

I am truly amazed at the tremendous outpouring of TV & Radio Technicians who attended the 2 day show. I have been to components expositions all over the United States and have never seen the equal of the attendance at the State Fairgrounds. This is especially phenomenal when you consider that this is the first show exclusively for servicemen and technicians of its type ever attempted in the entire country. It is indeed a tribute to the imagination, planning and splendid organization of the electronic parts distributors of Greater Detroit, under the very capable chairmanship of H. Hirt of Radio Specialties Co., 456 Charlotte. The Radio & TV parts distributors of the U. S. can well take example from this excellent and inspired type of good merchandising in bringing the manufacturers of complex equipment in direct contact with the ultimate users of their products. It cannot help but generate good will, trust and greater cooperation among maker, distributor and servicemen.

Mfr: Majestic Model No. 121B

Card No. MAJ 121-1


Section Affected: Raster

Symptom: No high voltage

Cause: Defective component

What to Do:

Replace: R94 (5K, 5 watt)—open

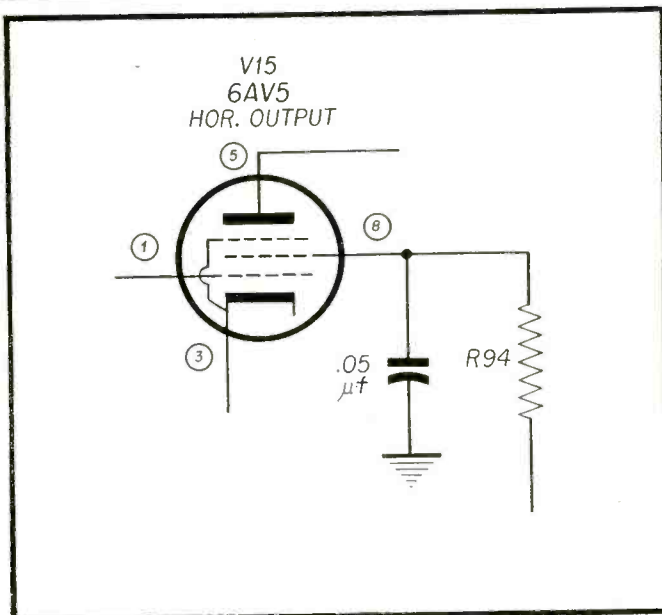

Mfr: Majestic Model No. 121B

Card No. MAJ 121-2


Section Affected: Sound

Symptom: No sound

Cause: Defective component

What to Do:

Replace: C18 (.005 μf)—shorted

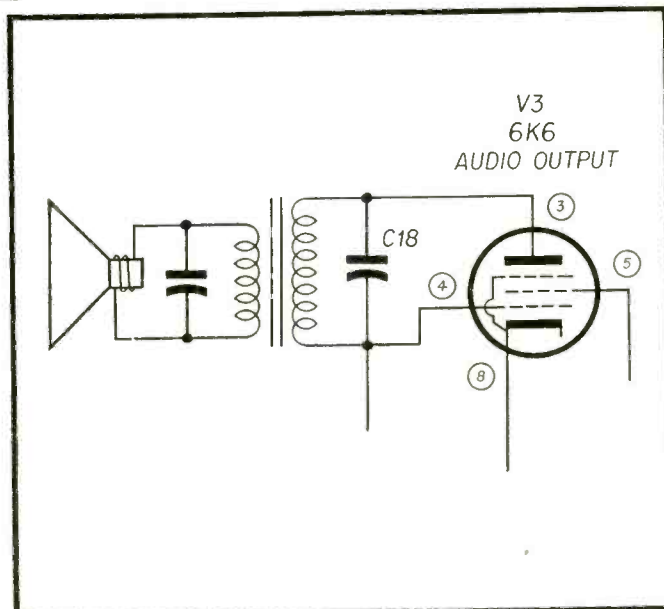

Mfr: Majestic Model No. 121B

Card No. MAJ 121-3


Section Affected: Pix


Symptom: Video overload

Cause: Defective component

What to Do:

Replace: C33 (100 μμf)—leaking

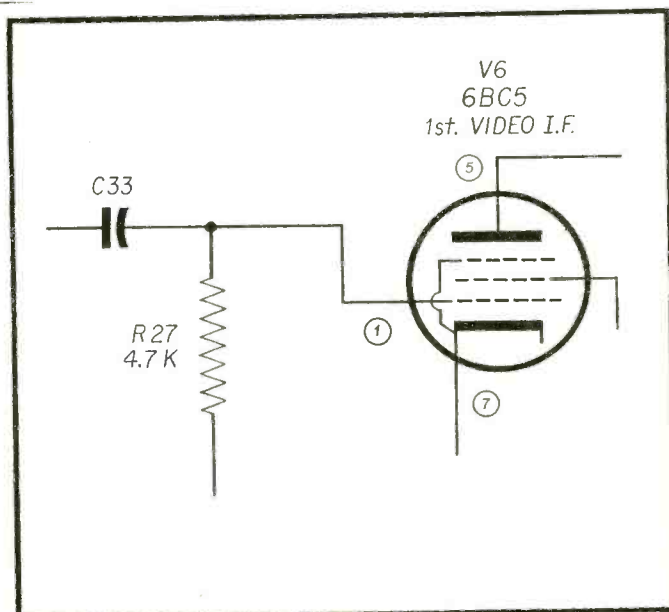

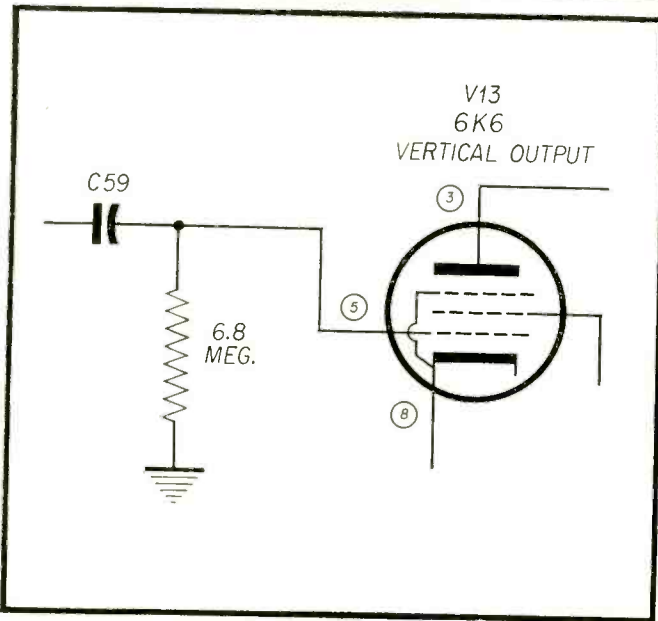

Mfr: Majestic Model No. 121B

Card No. MAJ 121-4


Section Affected: Raster

Symptom: Vertical foldover at bottom

Cause: Defective component

What to Do:

Replace: C59 (0.1 μ f)—leaky

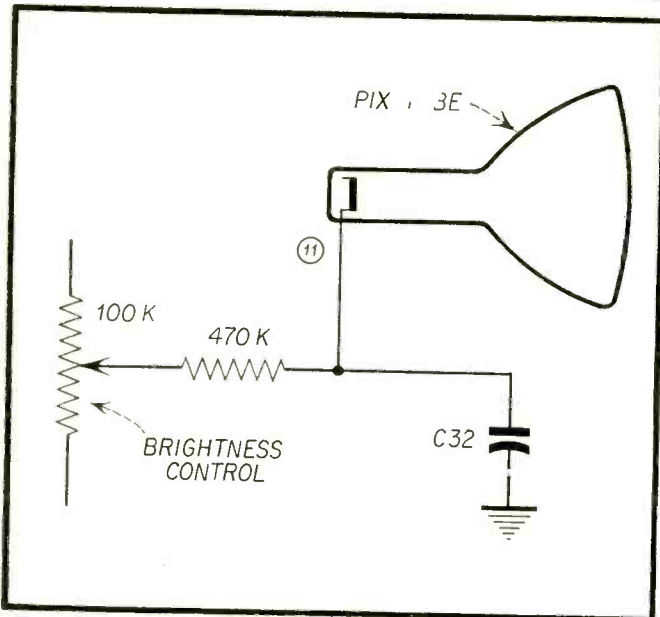

Mfr: Majestic

Model No. 121B

Card No. MAJ 121-5


Section Affected: Raster

Symptom: No control of brightness

Cause: Defective component

What to Do:

Replace: C32 (.05 μ f)—shorted

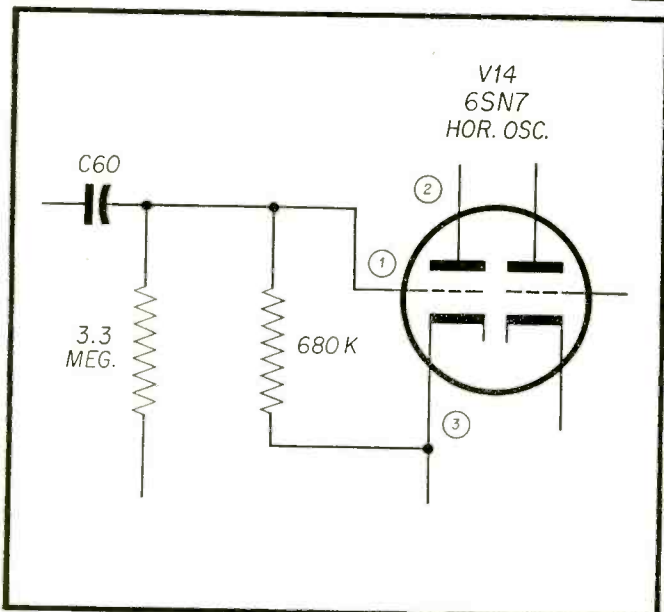

Mfr: Majestic

Model No. 121B

Card No. MAJ 121-6

Section Affected: Sync

Symptom: Horizontal frequency drift

Cause: Defective component

What to Do:

Replace: C60 (.002 μ f)—leaky

Mfr: Philco Model No. 50-T1600,
51-T1600, etc.

Card No: PH1600-1 Code No. 121 and 122

Section Affected: Sync

Symptom: Critical sync action under difficult reception conditions


Reason for Change: Circuit improvement

What to Do:

Remove: 6.8K, 1.2 meg resistors as shown also 100 μf , .047 μf and 330 μf condensers as shown

Install: Parts and rewire as shown in Card No. PH1600-2

(continued on Card No. PH 1600-2)

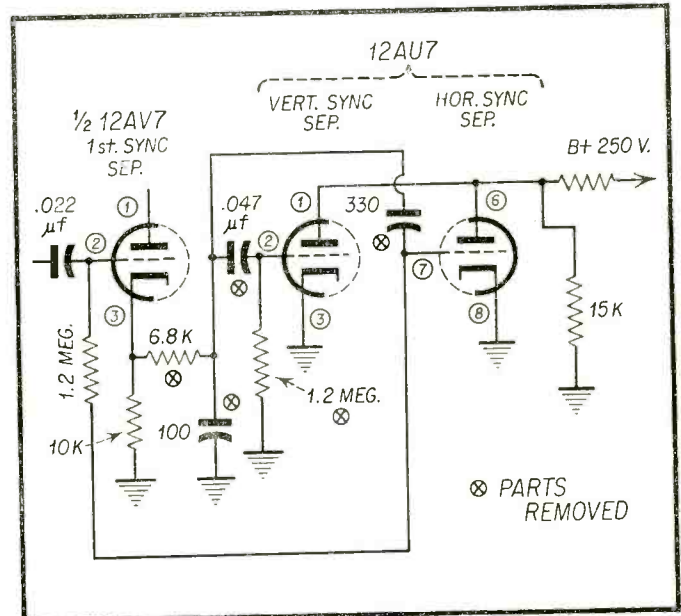

(continued from Card No. Ph 1600-1)

Mfr: Philco Model No. 50-T1600,
51-T1600, etc.

Card No: PH1600-2 Code No. 121 and 122

Section Affected: Sync

Symptom: Critical sync under difficult reception conditions


Reason for Change: Circuit improvement

What to Do:

Install: 39K, 180K, 270K, 6.8K, 100K, resistors as shown

Also, .015 μf , 120 μf condensers as shown

Rewire: As shown

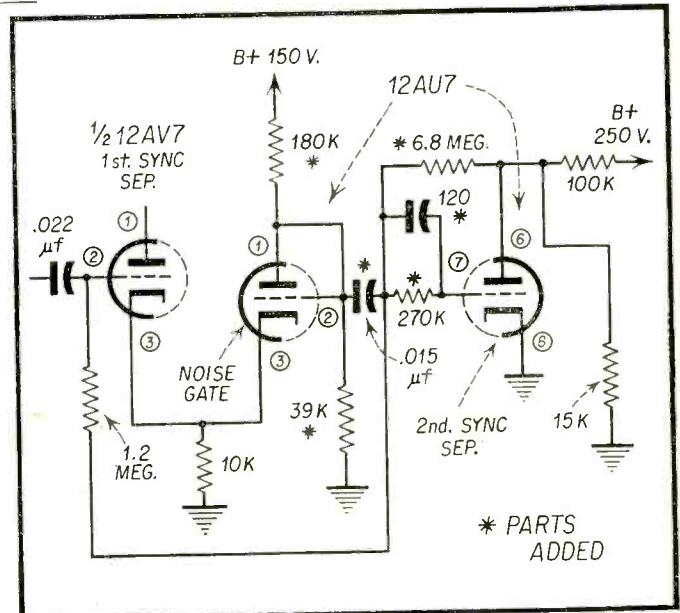

Mfr: Philco Model No. 50-T1600,
51-T1600, etc.

Card No: PH1600-3 Code No. 121 and 122


Section Affected: Raster


Symptom: No raster; no high voltage; R104 (4.7K) resistor burns

Cause: C86 (40 μf) is open, causing horizontal rf energy to flow completely through R104 (4.7K) which burns up.

What to Do:

Replace: C86 (40 μf)
Also R104 (4.7K)

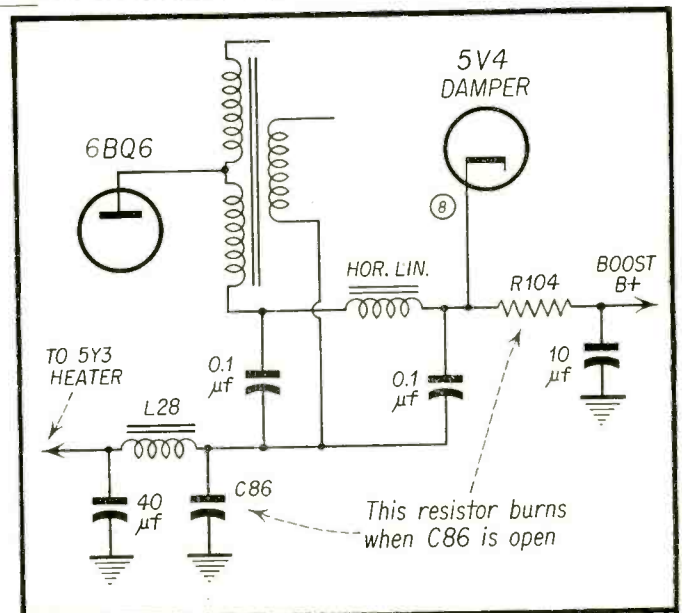

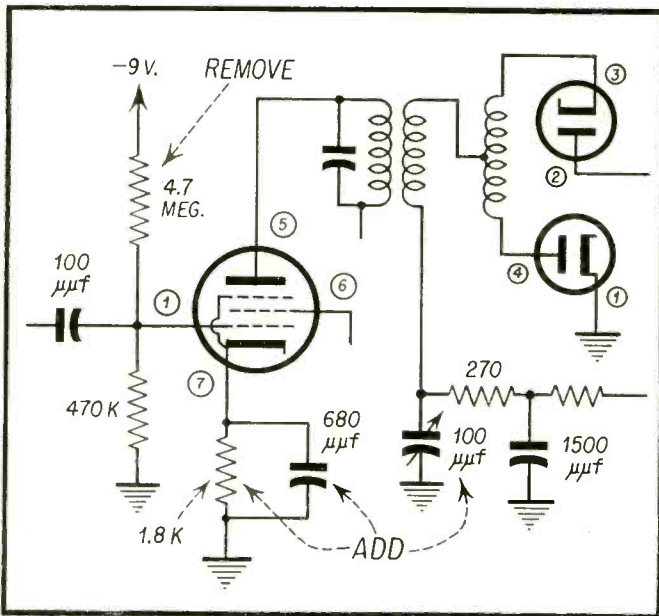

Mfr: Philco **Model No.** 50-T1600, 51-T1600, etc.

Card No: 50T-1600-4 **Code No.** 121 and 122

Section Affected: Audio

Symptom: Intercarrier buzz


Cause: Insufficient AM rejection

What to Do:

Remove: 4.7 meg resistor

Add: 680 μmf condenser

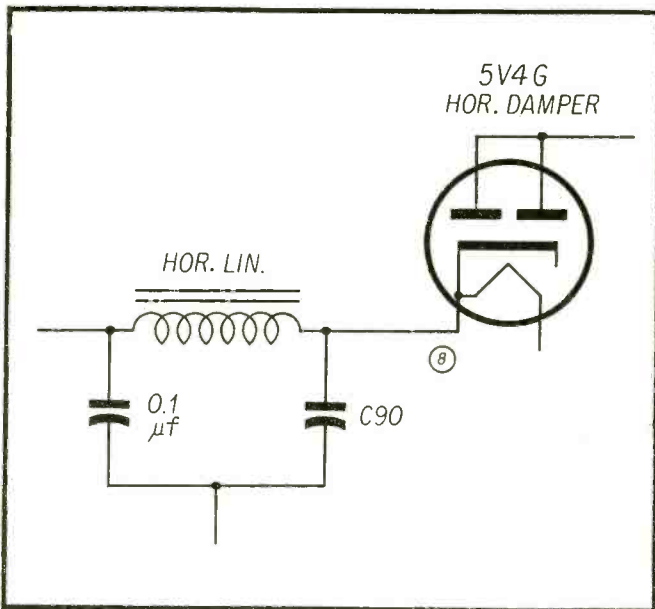Also, 100 μmf adjustable condenser and 1.8K resistor



Mfr: Philco **Model No.** 50-T1600, 51-T1600, etc.

Card No: PH50T1600-5 **Code No.** 121 and 122


Section Affected: Pix

Symptom: Poor Horizontal linearity

Cause: Open condenser

What to Do:

Replace: C90 (.1 μf)

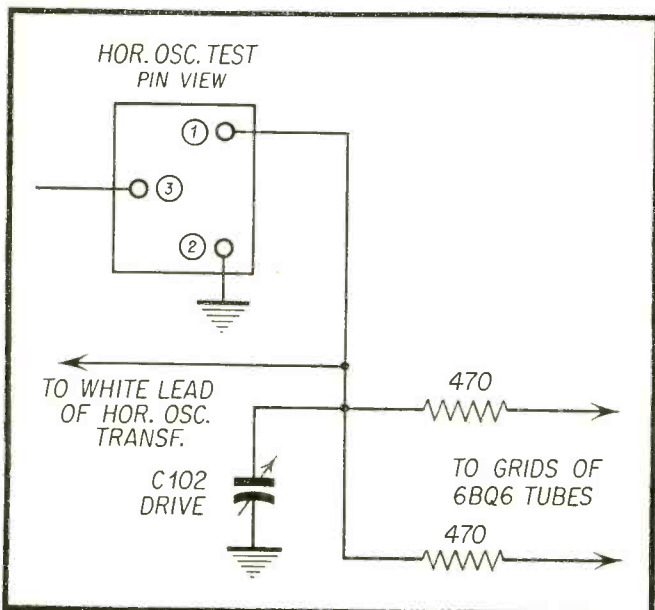

Mfr: Philco **Model No.** 50-T1600, 51-T1600, etc.

Card No: PH1600-6

Section Affected: Raster

Symptom: Intermittent raster, bias on 6BQ6GT intermittent

Cause: Defective drive capacitor (mica cracked)

What to Do:

Check: C102 (horizontal drive control), note condition of mica and replace

Mfr: RCA Chassis No. KCS 81

Card No: RC81-1


Section Affected: Sound

Symptom: Raspy sound

Cause: Leaky Condenser

What to Do:

Replace: C117 (.01 μ f)

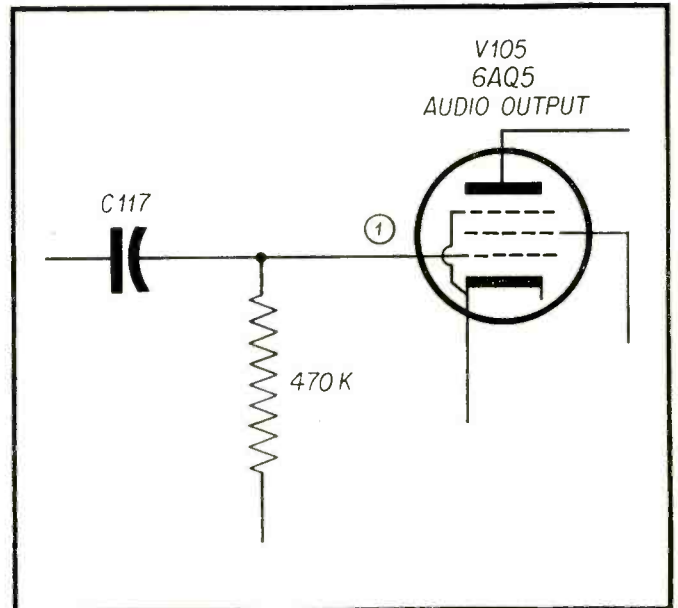

Mfr: RCA Chassis No. KCS 81

Card No: RC81-2


Section Affected: Raster

Symptom: No control of brightness

Cause: Shorted condenser

What to Do:

Replace: C183 (.1 μ f)

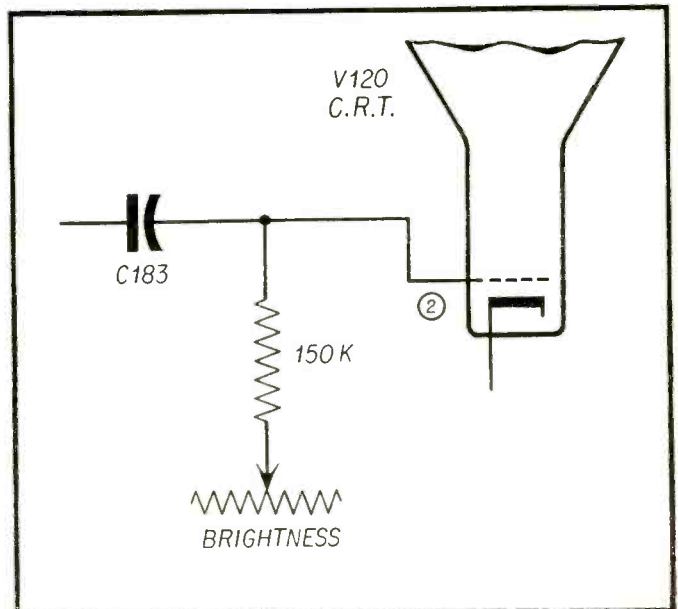

Mfr: RCA Chassis No. KCS 81

Card No: RC81-3


Section Affected: Sync


Symptom: Critical horizontal and vertical sync

Cause: Shorted condenser


What to Do:

Replace: C170 (.01 μ f)

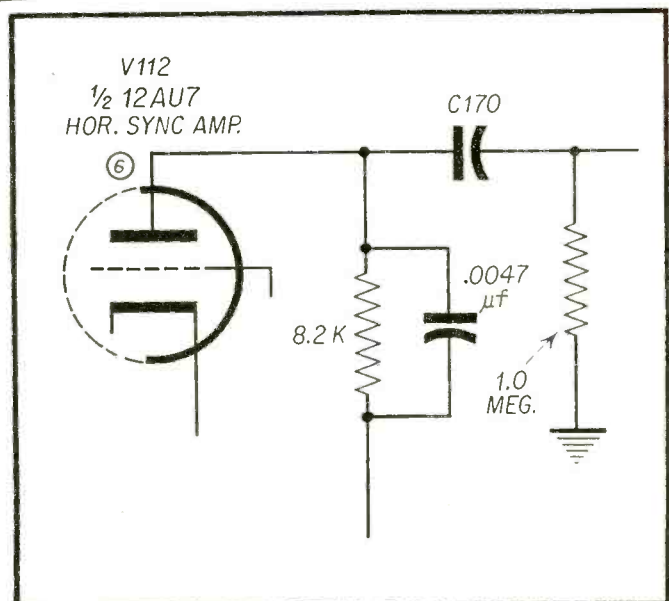


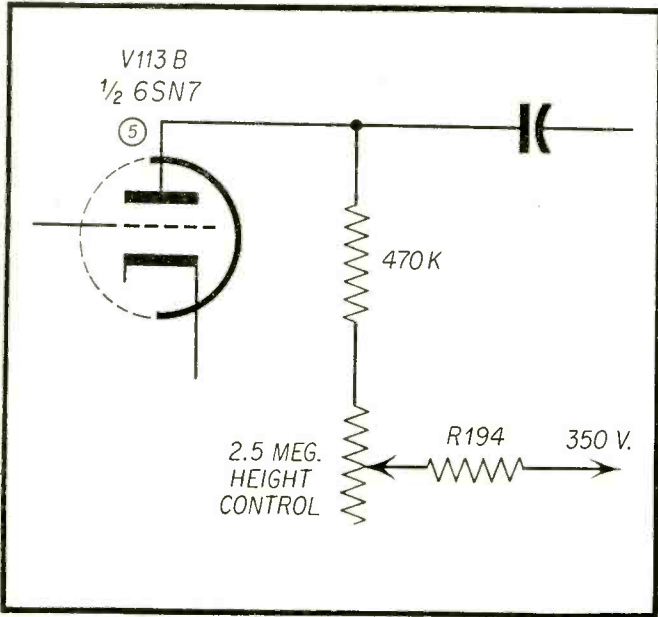

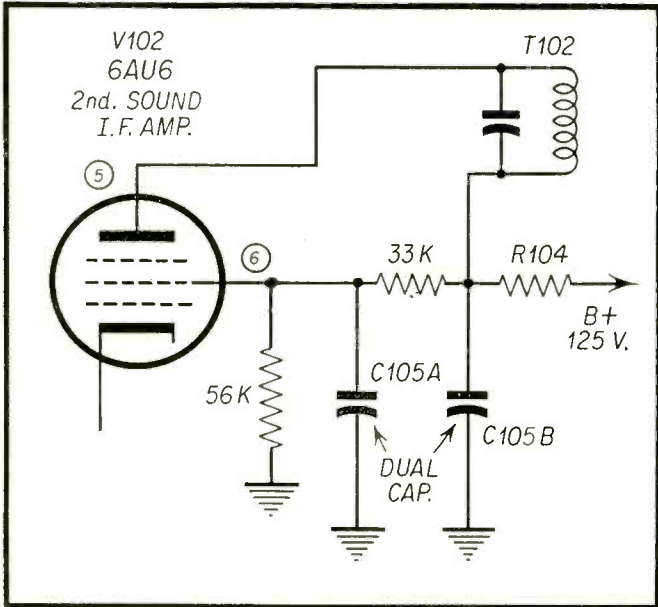Mfr: RCA **Chassis No.** KCS 81
Card No: RC81-4
Section Affected: Raster
Symptom: Insufficient height
Cause: Resistor increases in value
What to Do:
 Replace: R194 (220K)



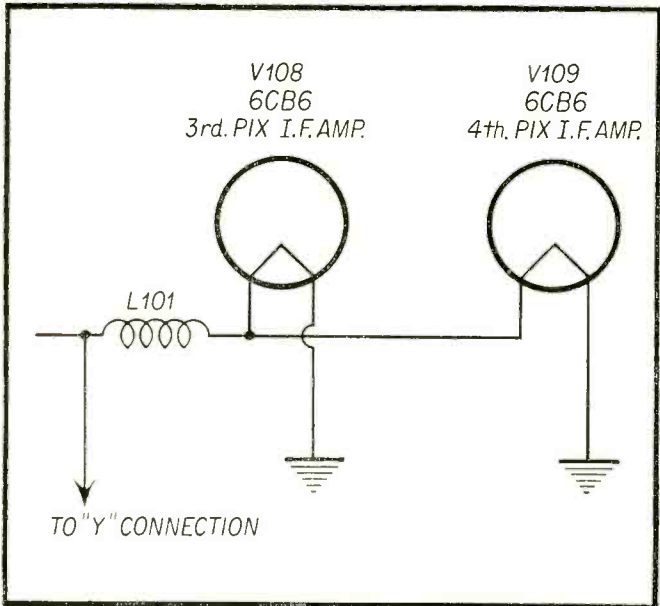Mfr: RCA **Chassis No.** KCS 81
Card No: RC81-5
Section Affected: Audio
Symptom: No Audio
Cause: Shorted condenser; and resistor changed in value caused by shorted condenser
What to Do:
 Replace: C105B (.01 μ f)
 Also, R104 (1K)



Mfr: RCA
Card No: RC81-6
Section Affected: Sound & pix; V108, V109
Symptom: No sound, no pix
Cause: Open filament choke
What to Do:
 Replace: L101 (filament choke)

PHILCO

Code 140, Chassis R-191, D-191

TUBE LIST

RF CHASSIS R-191

SYMBOL	TYPE	CIRCUIT FUNCTION
V1	6BZ7	R-F Amp
V2	6X8	Oscillator-Mixer
V3, V4, V5	6CB6	Video I-F Amp
V6	6AU6	Video Amp
V7	6AQ5	Video Output Amp
V8	6AU6	Sound I-F Amp
V9	6T8	Ratio Detector, First Audio, and Tuner A-G-C Clamp
V10	6V6G	Audio Output
V11	6CS6	Sync Separator
V19	17Y14 or 21ZP4A	Picture Tube


DEFLECTION CHASSIS D-191

SYMBOL	TYPE	CIRCUIT FUNCTION
V12	12AU7	Phase Splitter, Vert. Oscillator
V13	12B4	Vert. Output
V14	6AL5	Hor. Phase Com- parer
V15	12AU7	Hor. Osc.
V16	6BQ6GT	Hor. Output
V17	6AX4GT	Hor. Damper
V18	1B3GT	H. V. Rectifier


KEY VOLTAGES

B+, plate of damper, V17 pin 5	260 vdc
Boosted B+, cath. of damper, V17 pin 3	420 vdc
Plate(s) of VERT. OSC., V12 pin 6	149 to 202 vdc
Plate of Vert. Out., V13 pin 9	205 vdc
Plate(s) of Hor. Osc., V15 pin 1	165 vdc
Grid of Hor. Out., V16 pin 5	170 vdc
	-88 vdc

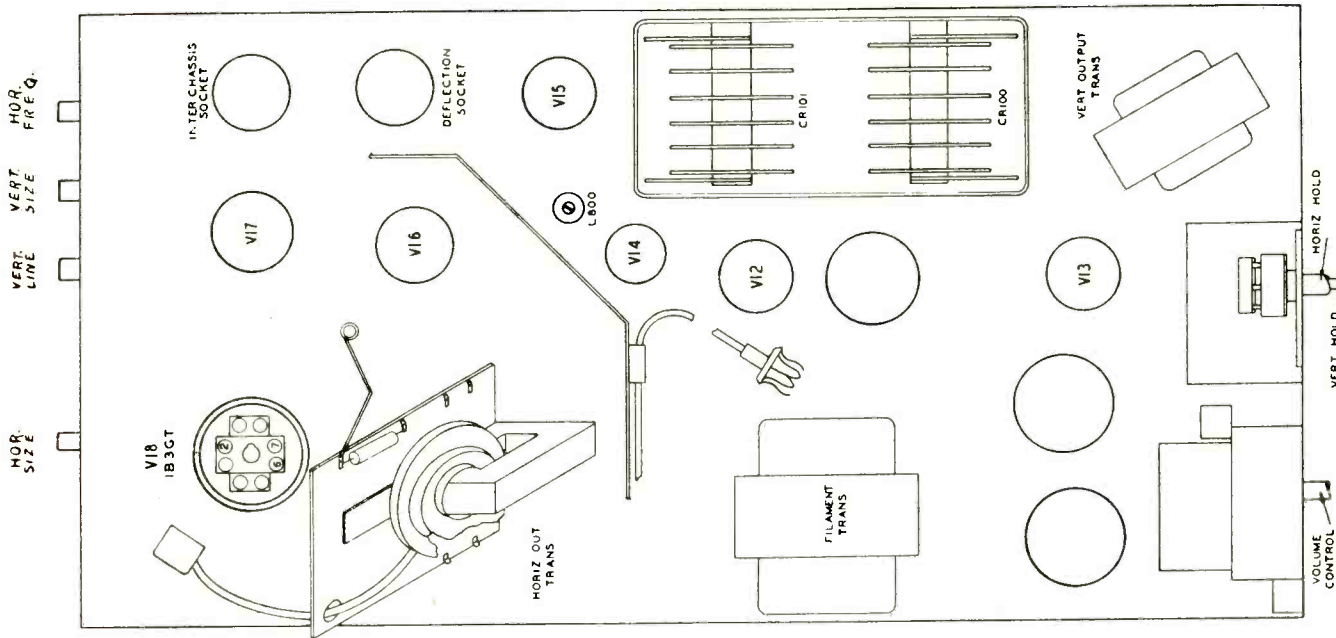All voltages are measured with a VTVM connected between the tube pins and chassis.



Deflection Chassis D-191, Base Layout

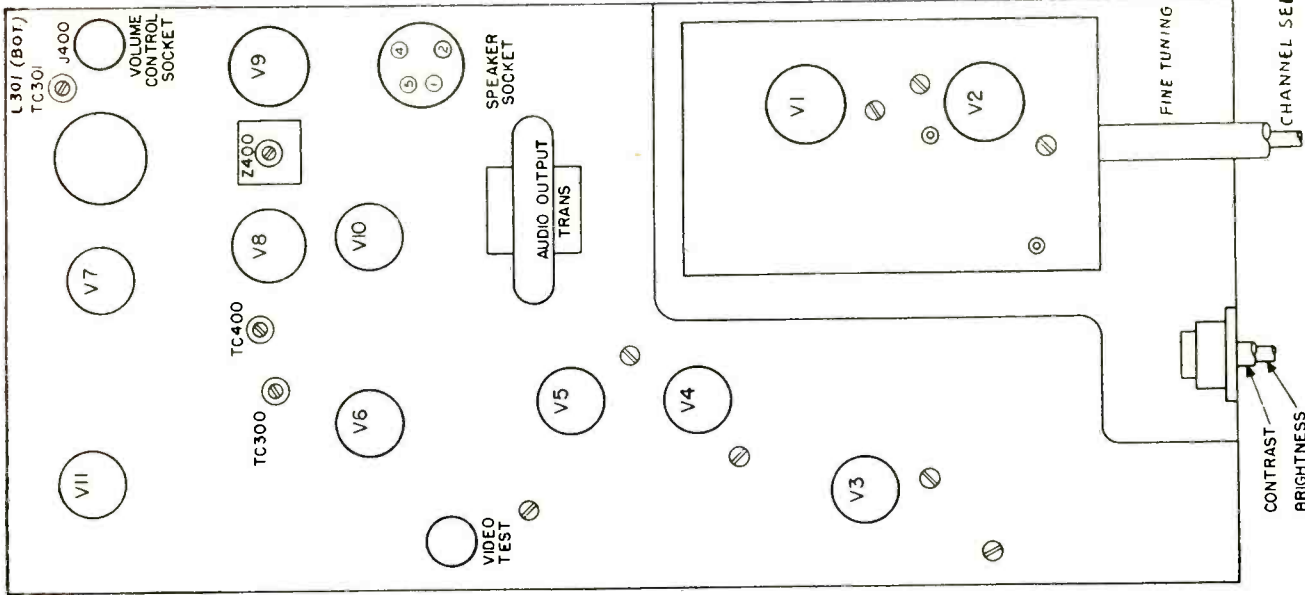

R-F CHASSIS R-191, TOP VIEW, SHOWING LOCATIONS OF ADJUSTMENTS

B SUPPLY FUSE REPLACEMENT

The B supply protective fuse, F100, is wired into the low-voltage section, and is in series with the selenium rectifiers. For replacement, use a 1.6-ampere delay-action type fuse, Philco Part No. 45-2656-23.
CAUTION: Discharge the circuit before replacing the fuse.

HORIZONTAL-OSCILLATOR ADJUSTMENT

To adjust the horizontal-oscillator circuit, tune in a station and proceed as follows:

1. Reduce the width of the picture until approximately 1 inch of blank screen appears at the right-hand and left-hand sides of the picture.
2. Increase the BRIGHTNESS control setting until the blanking becomes visible. This will appear as a dark vertical bar on each side of the picture.
3. Connect a .1 μ f. condenser from the test point, adjacent to TC800, to ground. (The plate side of the horizontal ringing coil, L800, is connected to the test point.)
4. Set the HORIZONTAL HOLD control to the approximate center of its mechanical rotation.
5. Adjust the HORIZ HOLD CENTERING control unit equal portions of the blanking bar appear on both sides of the picture.
6. Remove the .1- μ f. condenser from the test point.
7. Adjust the horizontal ringing coil, L800, until equal portions of the blanking bar again appear on both sides of the picture.
8. Rotate the HORIZONTAL HOLD control through its range. The picture should fall out of sync on both sides of the center of its rotation. If the picture does not fall out of sync on both sides, readjust the HORIZ HOLD CENTERING control.
9. Rotate the HORIZONTAL HOLD control through its range, and observe the number of diagonal blanking bars that appear just before the picture pulls into sync. The pull-in should occur with from 1 to 2 diagonal bars when the sync position is approached from either direction. If proper pull-in is not obtained, repeat the above procedure.

VIDEO PEAKING-COIL ADJUSTMENT

The video peaking coil, L303, is adjusted at the factory for proper transient response of the video circuits. Ordinarily, this coil will require no further adjustment by the serviceman. On any station where excessive overshoot or excessive smear is present, a slight adjustment of L303 may improve the picture quality on that station; however, this adjustment may sacrifice the quality on other channels. If L303 is replaced in servicing, adjustment will be required.

Before adjusting L303, check the tuner alignment and i-f alignment. (Never adjust

L303 until the alignment of the receiver is correct.) Then tune in a station and adjust L303 until there are no trailing whites or smear in the picture. Turning TC301 clockwise reduces trailing whites and overshoot; turning TC301 counterclockwise reduces picture smear and increases trailing whites. The proper position is the point where no smear or trailing whites appear in the picture.

The above procedure for adjustment of TC301 applies to a particular station exhibiting smear or overshoot. After TC301 is adjusted, reception on all the other stations should be checked, to make certain that the adjustment has not impaired the picture quality.

OSCILLATOR ALIGNMENT**General**

Tuning cores are provided in the oscillator coils at channels 13, 11, 9, 7, 6, and 4. By adjusting these tuning cores, all channels may be placed on frequency. This procedure should be carried out with the highest frequency channel first, since the alignment of each channel affects the alignment of all the channels below it in frequency. The channel adjustments are so arranged that, with one exception, each adjustment corrects the tuning of more than one channel. The coverage of the various adjustments is as follows:

CHANNEL ADJUSTMENT	CHANNELS CORRECTED BY ADJUSTMENT
13	13 and 12
11	11 and 10
9	9 and 8
7	7 only
6	6 and 5
4	4, 3, and 2

The FINE TUNING cam should be preset for all adjustments by placing the stop on the FINE TUNING cam between the Channel 7 and 8 holes on the front plate of the tuner.

PROCEDURE USING STATION SIGNAL

The following simplified procedure may be used to align the oscillator when the television i-f alignment is satisfactory and a station signal is available:

1. Mechanically preset the FINE TUNING cam to the center of its range (see figure 4).
2. Tune in the highest-frequency channel to be received.
3. Adjust the tuning core for that channel, or the next higher channel, for the best picture; that is, starting with sound in the picture, turn the tuning core until the sound disappears. Repeat for each channel received in the area.

NO RASTER—NO SOUND

Power input circuit
Check B+ Fuse F100 (1.6 Amps.)
Check selenium rectifiers CR100 and CR101

WEAK PIX—SOUND AND RASTER OK

Tuner fine tuning
Contrast con.
V3, V4, V5, V6, V7
Check Vid. Det. xstal CD200 (1N64)

POOR HOR. LIN.

Width con.
V16, V17
Check 0.047 μ f cap. connected to terminal T1 of hor. out. trans.
Hor. Out trans.

PIX JITTER SIDEWAYS

Hor. Hold and Freq. con.
Check adjustment of TC300
Check 0.01 μ f cap. connected to pin 7 of V15
Check 1000 μ af cap. connected to pin 7 of V15

PIX JITTER UP & DOWN

Vert. Hold and Contrast con.
V11, V12
Check Vid. Det. xstal CD200 (1N64)

SMEARED PIX

Tuner fine tuning
Contrast con.
V3, V4, V5, V6, V7
Check Vid. Det. and Amp. peaking coils
Check Vid. Det. xstal CD200 (1N64)
IF and RF alignment
Check adjustment of TC301

POOR PIX DETAIL

Tuner fine tuning
Focus con.
V3, V4, V5
Check Vid. Det. and Amp. peaking coils
IF and RF alignment

SOUND BARS IN PIX

Tuner fine tuning
V1, V2, V3, V4, V5, V6
Check adjustment of TC300
IF and RF alignment

ENGRAVED EFFECT IN PIX

Tuner fine tuning
Contrast con.
V1, V2, V3, V4, V5, V6, V7, V19
Check adjustment of TC301
Check Vid. Det. xstal CD200 (1N64)
Check Vid. Det. and Amp. peaking coils

VERT. BARS

V16, V17
Check 68 μ af cap. connected to yoke terminals Y1 and Y2
Defl. yoke ringing

PIX BENDING

Hor. Hold and Freq. con.
Check adjustment of TC800
V11, V12, V14, V15, V16
Check 2000 μ af and 0.01 μ f caps. connected to pin 7 of V14

INSUFFICIENT BRIGHTNESS

Ion trap
Brightness con.
V16, V17, V18, V19
Low line voltage

EXCESSIVE RASTER (PIX SIZE)

Size
Hor. and Vert. con.
V16, V17, V18, V19

INSUFFICIENT RASTER WIDTH

Width con.
V16, V17
Check selenium rectifiers CR100 and CR101
Check 390 and 5000 μ af caps. connected to pin 1 of V15
Hor. Out trans.
Low line voltage

INSUFFICIENT RASTER HEIGHT

Vert. Size and Lin. con.
V12, V13
Check 0.1 μ f cap. connected to pin 2 of V13
Check B+ voltage
Check 0.015 μ f cap. connected to red lead of Vert. Osc. trans.
Vert. Out trans.
Low line voltage

NO VERT. DEFL.

V12, V13
Check 0.1 μ f cap. connected to pin 2 of V13
Check 0.015 μ f cap. connected to red lead of Vert. osc. trans.
Vert. Defl. coils (yoke)
V. O. T. and Vert. Osc. trans.

NO HOR. OR VERT. SYNC.—PIX SIGNAL OK

V11, V12
Check 0.017 μ f cap. connected to pin 2 of V12

NO HOR. SYNC.—VERT. SYNC. OK

Hor. Hold and Freq. con.
Check adjustment of TC800
V12, V14, V15, V16
Check 390 μ af cap. connected to pin 2 of V15

DISTORTED SOUND

Tuner fine tuning
V2, V8, V9, V10
Check Vid. Det. xstal CD200 (1N64)
Check 0.0068 μ f cap. connected to pin 5 of V10
Sound and Vid. IF alignment TC400, Det. alignment Z400

STEWART WARNER

Model 9132-A

TUBE LIST


SYMBOL TYPE CIRCUIT FUNCTION

V1	6AU6	1st Sound IF Amp.
V2	6AU6	2nd Sound IF Amp.
V3	6T8	Sound Discr.-Sound Amp.
V4	6U6GT	Sound Out.
V5	6J6	Mixer-Osc.
V6	6BQ7 or 6BZ7	RF Amp.
V7	6AU6	1st Vid. IF Amp.
V8	6AU6	2nd Vid. IF Amp.
V9	6AU6	3rd Vid. IF Amp.
V10	6CB6	4th Vid. IF Amp.
V11	6AL5	Vid. Det., DC Re-storer
V12	6AU6	Vid. Amp.
V13	6BE6	Gated Sync. Sep.
V14	6K6GT	Vid. Out.
V15	21AP4	Picture tube
V16	6AU6	AGC Amp.
V17	12AT7	Sync Slipper, Phase Splitter
V18	6AL5	Hor. AFC Phase Det.
V19	6SN7GT	Hor. Osc.
V20	6CD6G	Hor. Out.
V21	1B3GT	HV Rect.
V22	6W4CT	Damper
V23	6X5GT	Rect.
V24	5U4G	Rect.
V25	6J5GT	Vert. Osc.
V26	6S4	Vert. Out.


KEY VOLTAGES

B+	plate of damper, V22 pin 5	330 vdc
Boosted B+	cath. of damper, V22 pin 3	480 vdc
Plate(s) of VERT. OSC.,	V25 pin 3	75 vdc
Plate of Vert. Out.,	V26 pin 9	420 vdc
Plate(s) of Hor. Osc.,	V10 pin 2	310 vdc
	pin 5	110 vdc
Grid of Hor. Out.,	V20 pin 5	—13 vdc

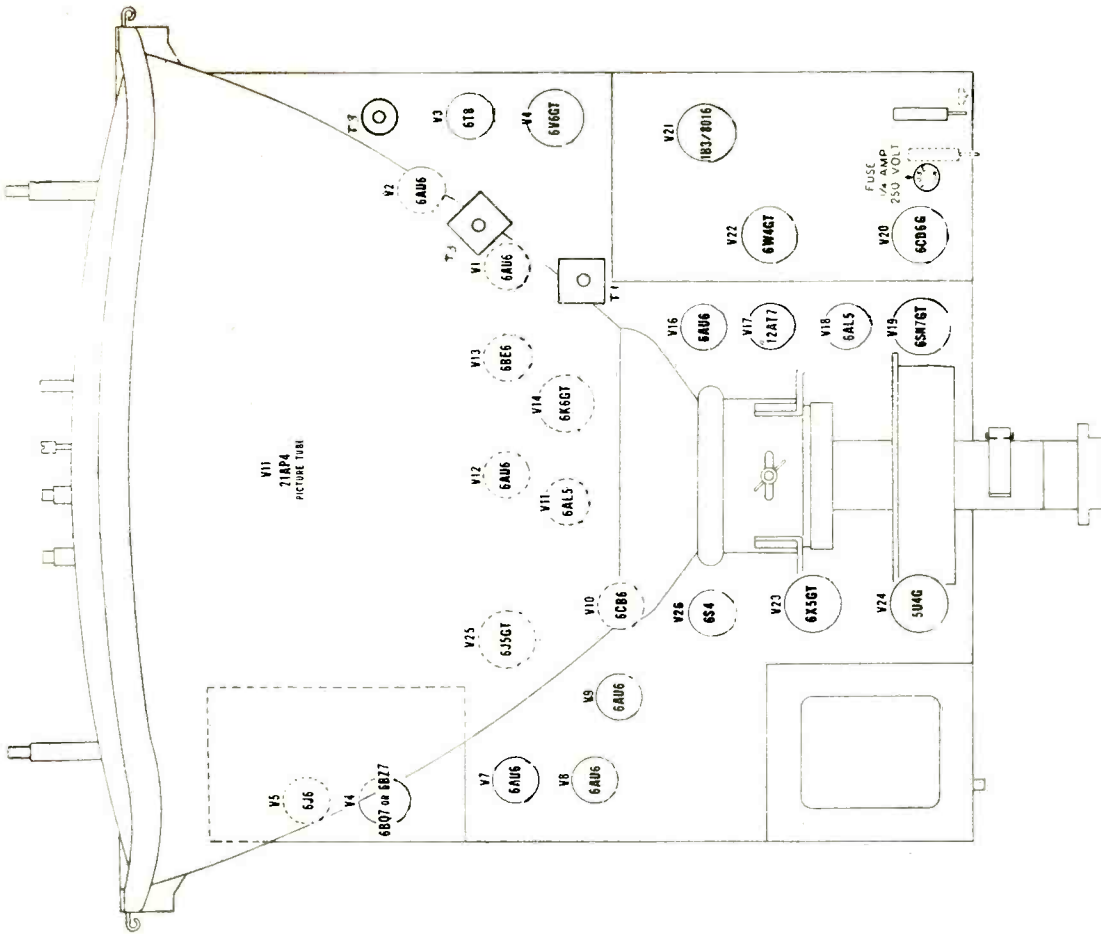
All voltages are measured with a VTVM connected between the tube pins and chassis.



TOP VIEW

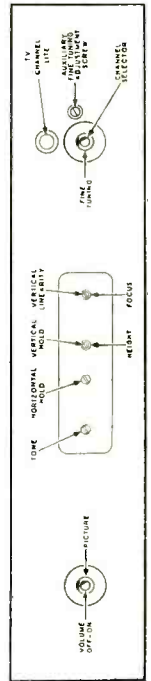

FRONT CONTROLS

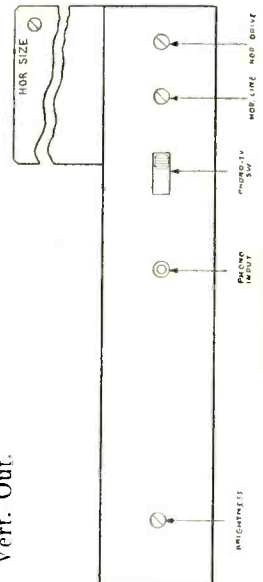

REAR CONTROLS

ADJUST ION TRAP

If screen remains dark or is only dimly illuminated when "Brightness" control is turned clockwise, the ion trap may require adjustment.

The ion trap is located on the neck of the picture tube and consists of a magnet held in position by metal bands.

With "Brightness" control (located at rear of receiver) set approximately $\frac{1}{2}$ turn clockwise, rotate the entire ion trap assembly while sliding it back and forth until picture tube screen is illuminated to maximum brilliance. Reduce "Brightness" control setting and repeat this operation to assure accurate positioning of ion trap.

Do not turn "Brightness" control to its maximum clockwise position until ion trap is correctly adjusted—failure to observe this precaution may result in damage to the picture tube.

CAUTION: There is only ONE correct setting of the ion trap. This position is attained when maximum brilliance occurs on the picture tube screen. If defocusing of picture or neck shadow results, DO NOT adjust position of ion trap. Failure to observe this precaution will result in an ion burn (brown spot) on the face of the picture tube. Since this condition is brought about by lack of proper ion trap adjustment at time of receiver installation, the picture tube will not be eligible for warranty adjustment.

AUXILIARY FINE TUNING ADJUSTMENT

It is found that the tuning range of the "Fine Tuning" control is inadequate to permit correct tuning of a station in its assigned channel, then adjustment of the "Auxiliary Fine Tuning" screw will be necessary. This special screw is accessible after removal of the "Channel Selector" and "Fine Tuning" knobs. They may be removed by merely pulling them forward.

Adjustment of the "Auxiliary Fine Tuning" screw may be undertaken in accordance with the following procedure.

- Set "Channel Selector" to desired channels; then remove this knob.
- Set "Fine Tuning" knob to the center of its range; then remove this knob. The flat portion of the main tuning shaft (outer shaft) should now be in the uppermost position. Note the location of the "Auxiliary Fine Tuning" adjustment screw on receiver chassis.
- Using a thin screwdriver (preferably non-metallic), adjust the setting of "Auxiliary Fine Tuning" screw for correct tuning of the desired television station. **CAUTION:** Do not attempt to rotate this screw more than two full turns in either direction, as further rotation may release it from the thread clip within the tuning mechanism and the coil for that channel (located in R.F. Tuner Unit) would then have to be removed in order to restore the screw to

the correct position. If a metal screwdriver is used, detuning occurs when the screwdriver is removed but it will be noted that this degree of detuning can now be compensated by resetting the "Television Fine Tuning" control (outer shaft). Thus the range of the "Television Fine Tuning" control (after knob is replaced on the shaft) will be adequate to tune in the station.

This completes the adjustment of the "Auxiliary Fine Tuning" screw for one channel. Identical screws are provided on each channel and they are all accessible thru the same opening in the tuning mechanism as each successively moves into position when the "Channel Selector" knob is rotated.

HORIZONTAL LINEARITY

Inproper horizontal linearity causes the circular test pattern to appear condensed on the right edge of the screen and extended on the left edge or vice versa. Adjust for proper linearity by using "Horizontal Linearity" control located at rear of chassis. In event that proper horizontal linearity cannot be obtained by adjusting this control, then check the setting of the "Horizontal Drive" control to be sure it has been correctly adjusted.

HORIZONTAL DRIVE

The "Horizontal Drive" control located at rear of chassis should be rotated clockwise to a point just prior to where the picture tube brilliancy and size decrease. Then adjust this control $\frac{1}{2}$ turn counter-clockwise.

ELIMINATING SEMI-CIRCULAR SHADOW

This shadow is caused by the electron stream striking the neck of the tube and it can generally be corrected by applying one or a combination of the following procedures:

Make sure deflection yoke is symmetrically positioned with respect to the neck of the picture tube by loosening the three wing nuts and adjusting yoke position. Should a change in height of the deflection yoke be required to obtain symmetry of yoke around neck of picture tube, it will be necessary to loosen the four wing nuts (two nuts located on each leg of mounting frame) and raise or lower yoke as required. After adjustment has been completed be sure to retighten nuts securely.

BRIGHTNESS

The "Brightness" control (located at rear of receiver chassis) should be initially adjusted in conjunction with the "Contrast" control for the brightness level desired by set owner—check all active station channels. Too much brightness will have the same effect as too little contrast, and vice versa, therefore, it is necessary to strike a proper balance between contrast and brilliance.

STEWART-WARNER TROUBLE SHOOTING CHART

VERT. BARS

Hor. Drive con.
V20, V22
Check 56 μf cap. connected to yoke socket terminal 6
Def. yoke ringing

PIX BENDING

Hor. Hold. con.
V16, V18, V19, V20
Check 0.05 μf and 5000 μf caps. connected to pin 1 of V19

EXCESSIVE RASTER (PIX SIZE)

Hor. Drive con.
Hor. and Size Sync. con.
V15, V20, V21

RASTER BLOOMING

Hor. Drive con.
V15, V20, V21, V22, V23, V24
Check HV Filter cap.
Check 1 Meg Ω Res. connected to HV Filter cap.

INSUFFICIENT RASTER WIDTH

Hor. Drive and Size con.
V20, V22, V23, V24
Check 270 and 390 μf caps. connected to pin 5 of V19
Hor. Out. trans.
Low line voltage

INSUFFICIENT RASTER HEIGHT

Vert. Size and Lin. con.
V23, V24, V25, V26
Check 0.1 μf cap. connected to pin 6 of V26
Check 0.05 μf cap. connected to pin 6 of V26 through a 6.8k Ω res.
Vert. Out. trans.
Low line voltage

NO VERT. DEFL.

V25, V26
Check 0.1 μf cap. connected to pin 6 of V26
Check 0.05 μf cap. connected to pin 6 of V26 through a 6.8k Ω res.
Vert. Defl. coils (yoke)
V. O. T. and Vert. Osc. trans.

NO VERT. SYNC.—HOR. SYNC. OK

Vert. Hold con.
Vert. Int. network
V13, V16, V17
Check 4700 μf cap. connected to pin 5 of V25

NO HOR. OR VERT. SYNC.—PIX SIGNAL OK

V13, V16, V17
Check 0.05 μf cap. connected to pin 7 of V13
Check 0.05 μf cap. connected to pin 2 of V17

NO HOR. SYNC.—VERT. SYNC. OK

Hor. Hold con.
V17, V18, V19
Check 330 μf cap. connected to pin 2 of V19

DISTORTED SOUND

Tuner fine tuning
V1, V2, V3, V4, V6
Check 0.005 μf cap. connected to pin 5 of V1
Sound and Vid. IF alignment T1, T2
Det. alignment T3

NO SOUND—PIX OK

Tuner fine tuning
Vol. con.
V1, V2, V3, V4
Speaker (open voice coil or defective connection)
Sound and Vid. IF alignment T1, T2
Det. alignment

SYNC. BUZZ IN SOUND

Tuner fine tuning
V1, V2, V3, V11, V16
Sound IF and Det. alignment T1, T2, T3

NO RASTER—NO SOUND

Power input circuit
Check B+ fuse (1 Amp.)

NO RASTER—SOUND OK

Brightness con.
Check HV Fuse (0.25 Amps.)
Ion trap
V15, V19, V20, V21, V22
HV trans. Hor. yoke CRT connections

WEAK PIX—SOUND AND RASTER OK

Tuner fine tuning
Contrast con.
V5, V6, V7, V8, V9, V10, V11, V12, V14, V16

POOR HOR. LIN.

Hor. Lin. and Drive con.
V20, V22
Check 0.05 μf caps. connected to Hor. Lin. Coil
Hor. Out. trans.

POOR VERT. LIN.

Vert. Size and Lin. con.
V25, V26
Check 0.1 μf caps. connected to pin 6 of V26
Check 100 μf Elec. cap. connected to pin 2 of V26
Vert. Out. trans.

PIX JITTER SIDWAYS

Hor. Hold Con.
V18, V19, V20
Check 0.01 and 0.05 μf caps. connected to pin 1 of V18

SMEARED PIX

Tuner fine tuning
Contrast con.
V7, V8, V9, V10, V11, V12, V14, V16
Check Vid. Det. and Amp. peaking coils
Check 0.05 μf cap. connected to pin 5 of V11
IF and Rf alignment

SPECIAL OFFER TO OUR READERS!

By special arrangement with John F. Rider Publisher, Inc., RADIO-TV SERVICE DEALER now brings you a COMPLETE diagram service to help you do a faster, easier servicing job!

ALL COMPLETE!

ALL FACTORY PREPARED!

ALL FACTORY AUTHORIZED!

- ✓ Just 70¢ for COMPLETE SERVICING INFORMATION on any TV receiver . . . any year, any make, any model . . . from 1946 on!
- ✓ Just 50¢ for COMPLETE SERVICING INFORMATION on any radio . . . any year, any make, any model . . . from 1941 on!

TAKE ADVANTAGE OF THIS SPECIAL OFFER . . . MAIL THE COUPON TODAY!

Radio-TV Service Dealer, 67 W. 44 Street, New York 36, N. Y.

Please RUSH me the following diagrams:

RADIO DIAGRAMS @ 50¢ EACH		
YEAR	MAKE	MODEL #

TV DIAGRAMS @ 70¢ EACH		
YEAR	MAKE	MODEL #


MAKE ALL CHECKS & MONEY ORDERS PAYABLE TO Radio-TV Service Dealer
(For all New York City orders, please submit additional 3% sales tax.)

Name


Address

City State

New

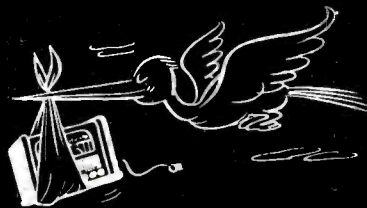

Products


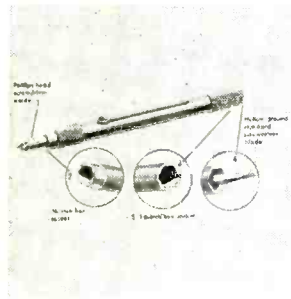


CBS-Hytron 4-Way Tool

CBS-Hytron, Danvers, Mass., has announced a 4-Way Tool consisting of: a slotted steel barrel with hex sockets, $\frac{1}{4}$ -inch at one end, $\frac{5}{16}$ -inch at the other; a double-ended screwdriver blade... one end with Phillips head, the other standard... which slides inside the barrel; and a knurled setscrew to lock the sliding blade into any one of three recessed positions within the slotted barrel. When the sliding blade is centered within the barrel, either hex socket can be used.

JFD Jet-Helix

The combination of the special flat plane conical, which proved exceptionally successful in the JFD Super-Jet, and the microwave helix, makes this a revolutionary antenna design for real dynamic performance. The Jet-Helix is completely constructed from Alcoa Aluminum, and highly engineered for the best reception ever achieved. The helix exhibits unusually high gain and directivity. For info, write JFD Mfg. Co., 6101 16 Ave., Brooklyn 4, N.Y.

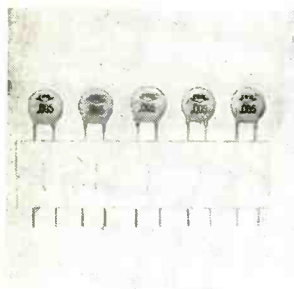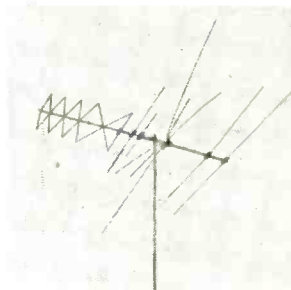


Erie "Pallet-Pak"

Erie Resistor Corporation, Distributor Division, 50 E. Wynnewood Rd., Wynnewood, Pa., announces a new method of bulk packaging ERIF Disc Ceramicons at no extra cost, which it has named "Pallet-Pak." Five discs are inserted between two strips of cardboard and stapled in position between the leads, eliminating tangled leads and providing an easily identified, easily handled, and quickly inventoried item.

"Corridor" Speech Master

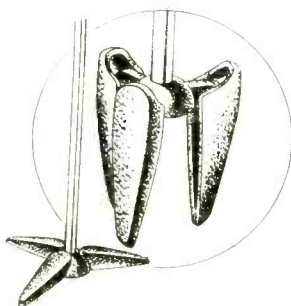The Jensen Manufacturing Company of this city is now producing a reproducer specially designed for two-direction sound coverage in corridors or offices. The new unit, Model RK-61, has a heavy drawn steel case with extended perforations on both sides to permit high quality speech coverage in both directions while offering complete protection to the heavy duty six-inch loudspeaker driver unit.




Snyder Mike Stand

A new floor stand has been introduced by Snyder Manufacturing Company of Philadelphia. The stand is a floor model and is coded the MS-2. $32\frac{1}{2}$ inches collapsed, its chrome plated 2-section telescopic staffs extend to $61\frac{1}{2}$ inches and are held securely by the Snyder Sure-Grip Lock with Velvet Action. The Base, of gray crackle finish cast iron, is light in weight. Additional information may be obtained by writing to Dick Morris at Snyder Mfg. Co., Philadelphia 40, Pa.

Clear Beam Antenna

Clear Beam Antenna Corp. announces availability of the "Big Chief," an all new high gain antenna combining the principles of the giant conical with a Yagi. This antenna provides servicemen with a functional type high gain all-band unit designed to cover all channels 2 to 13. Snap-open construction and special die-formed hardware provide easy assembly. The use of wider diameter tubing on the low band section of the antenna affords improved sensitivity.

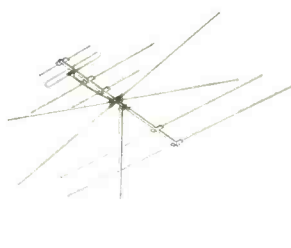


Raytheon Set Jackets

"Make your TV set match your room decor" is the theme of a new display featuring the "jacket wardrobe" of Raytheon's 17-inch and 21-inch Challenger sets. The full-color display measures 2 by 3 feet, stands securely on top of the 17-inch set through a combination of die-cut design and easel back, and contains swatches of the fabrics used for the ten slip-on jackets. For details, write Raytheon Mfg. Co., 801 N. Michigan Ave., Chicago 11, Ill.

Regency FM-AM Tuner

A new FM-AM professional tuner, Model AF-250, is now being manufactured by Regency which utilizes a genuine Armstrong circuit with two limiters, and has separate FM and AM circuits from antenna to output. AFC on FM provide maximum fidelity at all times. The unit is of cast polystyrene over black wrinkle steel. For information, write Regency, a division of I.D.E.A., Inc., 7900 Pendleton Pike, Indianapolis 26, Ind.

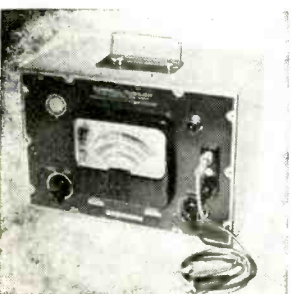


Cornell-Dubilier Flyback Checker

The CD "Flyback Transformer and Yoke Checker" is extremely sensitive and can detect even a single short circuited turn in the windings by indicating inductance change. The instrument, called the CD model BF-80, employs an oscillator circuit, a 6V6 vacuum tube and a $4\frac{1}{2}$ " microammeter with separate indicator scales for short tests, continuity tests, and yoke tests. For further information write: Cornell-Dubilier Electric Corporation, South Plainfield, N. J.

Channel Master Roto-King

Development of the Roto-King new antenna rotator has been announced by Channel Master Corporation, Ellenville, N.Y. The rotator is designed to provide the set-owner with hair-line accuracy in pin-pointing TV stations. Its many features include a flexible worm gear which eliminates the danger of gear-slipping, back-lash, and binding, assuring a longer life and positive control, and its midget control cabinet, the smallest cabinet on the market, measuring just $2\frac{3}{4}$ " x 4".

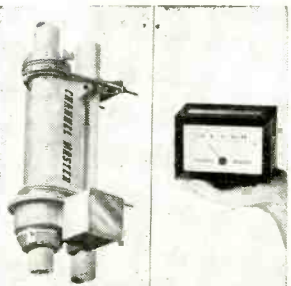

WORK BENCH

[from page 35]

was also noted that when the contrast was decreased slightly, the picture would slip vertically. Evidently, this was a composite sync problem. Therefore, V118, 6SK7, the first sync amplifier, V119, 6SH7, the sync separator, and V120A, the second sync clipper were replaced individually but did not solve the problem. Just as a slight possibility, V114B, 6AI5, the *de* restorer was also replaced.

The oscilloscope was next set up to check a few waveforms, and the diagram consulted. The 6SK7, V118, is a remote cut off type tube which is grid biased by the bleeder network, R228 and R153. The signal arriving at the grid of V118 is in a negative direction.

Knowing these facts, a waveform check was made at pin #4 of V118 but the waveform checked correctly with the manufacturer's service data (Ref. to Fig. 3A). Next a waveform check was made at pin #8 of V118 and this waveform also checked correctly with the manufacturer's notes (Ref. to Fig. 3B).

V119, the sync separator was then considered. This tube is grid biased by the bleeder network R156 and R157. The operating voltages applied to the grid, screen and plate are such that the negative or bottom portion of the applied positive going signal is cut off. Thus, the video and blanking pulses are removed and only the sync pulses appear at the plate of V119. Knowing this, a waveform check was now made at pin #4 of V119. This waveform checked correctly, yet it seemed to quiver a bit too much (Ref. to Fig. 3C). However, on checking pin #8, the plate of V119 we found trouble. Instead of being twice the size of that at pin #4 of V119 the waveform was about the same size. Moreover, it appeared to quiver entirely too much (Ref. to Fig. 3D).

A voltage measurement was then taken at the grid of V119, pin #4. Instead of measuring about -5 volts, it measured about -18 volts. The receiver was then turned off and a resistance check was made of R156 and R157. R156 checked properly but R157 measured infinite. R157, 1 megohm, was then replaced with a new 1 meg resistor and the receiver now functioned properly.

With R157 open and -18 volts applied to the grid only the uppermost positive tips of the sync pulses would cause V119, 6SH7, to conduct. Thus, because of the small sync pulse voltage applied to the horizontal and vertical oscillators, the picture would slip vertically and pull horizontally.

AUDIO ADAPTATIONS

[from page 33]

such as the 6K6, 6V6, 6W6 etc. can be adapted.

Again an "S" type socket and an old tube base are connected together, but this time as shown in Fig. 2. This results in the plate and screen of the output tube of the TV receiver being connected together so that the tube performs as a triode. Observe also that the

plate of the tube is connected to B+, and that the signal output is taken off the cathode. Thus, this stage becomes a cathode follower with a low impedance output which may be connected into a low impedance load. Systems between signal sources and loads using low impedance circuits produce a minimum of noise and interference voltage pickup in the lines, so that long lengths of wire may be connected between the cathode output terminals and the distant power amplifier input without excessive noise or hum pickup.

[Continued on page 52]

Just what the TV Doctor ordered...

R STANCOR
EXACT REPLACEMENT FLYBACKS

Whether the "patient" is a Crosley, a Muntz, an RCA, or any other brand, you can be sure of a prompt recovery when the prescription reads "STANCOR"


Patient: *Muntz*

Stancor A-8242
New Exact Replacement Flyback for Muntz TO-0028 and TO-0029
List Price \$9.00




Patient: *Crosley Super V, Hallicrafters*

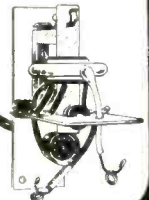Stancor A-8241
New Exact Replacement Flyback for Crosley 157820 and Hallicrafters 550251
List Price \$8.10



Patient: *RCA*

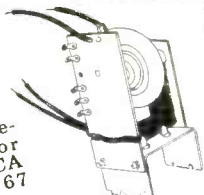Stancor A-8244
New Exact Replacement Flyback for RCA 78201 and RCA 78810. Used in 67 models and chassis.
List Price \$10.00



FREE—HIGH FIDELITY, Ultra-Linear Amplifier Bulletin 479 describing performance and construction of the 24 watt Stancor-Williamson Amplifier, using Stancor Ultra-Linear Output Transformer A-8072 (\$15.00 net). Available from your distributor.



CHICAGO STANDARD TRANSFORMER CORPORATION
3586 ELSTON AVENUE • CHICAGO 18, ILLINOIS

EXPORT SALES: Roburn Agencies, Inc. • 431 Greenwich Street • New York 13, N. Y.

Stancor transformers are listed in Photo-fact Folders, Counter-facts, Radio's Master, and File-O-Matic.

**I NEVER LOSE A WINK OF SLEEP
WORRYING ABOUT TUNG-SOL TUBES**



Tung-Sol Tube quality is the best insurance a dealer can have against service call-backs. You safeguard your service work and protect your profit when you use dependable Tung-Sol Tubes for replacement.

TUNG-SOL®

dependable
PICTURE TUBES



TUNG-SOL ELECTRIC INC., Newark 4, N. J.
Sales Offices: Atlanta, Chicago, Columbus,
Culver City (Los Angeles), Dallas, Denver,
Detroit, Newark, Seattle.



Television CRT manufacturers' sales of cathode ray tubes in September topped the 1.1 million mark to establish a new high in monthly unit sales, as reported by the Radio-Electronics-Television Manufacturers Association. Receiving tube sales in September gained by over 16 percent from August and were at the highest level since June of last year. Nearly 1 million television receivers were sold at retail during September, bringing sales for the first nine months of this year to the highest point on record. TV set sales in September more than doubled the August rate and radio sales were at the highest level this year, the Association added.

The Sprague Electric Company has started construction of a 13,000 square foot, one-story building in the Venice section of Los Angeles, Calif. to house all its Southern California operations. The building, in contemporary modern California architectural style of stone, glass, and cinder block, is expected to be completed in the spring of 1955. The Sprague company will then move from its present rented quarters in Culver City.

One-year warranties on TV picture tubes appear to be on the way out. On December 1, GE and DuMont will switch to six-month warranties on all sales of replacement CR tubes. A change to 12-month pro-rata warranty systems has already been made by RCA and Sylvania. The industry policy in regard to tubes sold to set manufacturers, but it is possible that these warranties may be reduced to a period of six months, early next year.

A new record care kit, ready in time for Christmas business, has been announced by Walco Products, Inc., East Orange, N. J. Designed to appeal to anyone with a record collector or hi-fi fan on his (or her) Christmas list, the kit contains a 6 oz. can of Walco Stati-Clean, popular anti-static spray cleaner for records; 2 packages of Walco Discovers—protective record sleeves made of the soft plastic, polyethylene; a book on record care by a leading audio expert, and a small camel's hair brush for cleaning dust from phonograph needle tips.


Latest developments in the Color TV field: Initial quantities of a pre-production run of RCA Victor's new 21-inch color television receiver, for demonstration purposes only, have been shipped to distributors in key color TV Markets. . . . Muntz TV, Inc., hopes to have a color set on the market in February, Earl W. Muntz, president, said recently. The color tube used will probably be CBS-Columbia's. . . . Magnavox will venture into color television for the first time next year with a 21-inch console incorporating a 21-inch round shadow mask color tube. . . . The U. S. Patent Office has granted Dr. Ernest O. Lawrence, a Nobel Prize physicist, a patent covering a basic invention for better and less expensive color television picture tubes. All Lawrence tubes embody the basic principle of post-deflection focusing and electronic color registration which makes it possible to build color stability in the tube itself. . . .

The "Dragnet" TV show, about the first of next year, will feature an exposé of a television service "racketeer." A. W. Bernsohn, managing director of the National Appliance and Radio-TV Dealers Association, announced that the script has been prepared by Dragnet Productions, Inc., with the cooperation of the Los Angeles Electric League and NARDA. Frank J. Moch, NATESA president, voiced apprehension at the announcement of the project, recalling that one of the earlier "Dragnet" scripts on the same subject proved quite derogatory to the industry; however, he expressed the hope that "anything controversial" may have been avoided this time by virtue of NARDA's editing of the script.

As of late, a great number of radio and television set manufacturers have been striving to build more compact units. As a result of this, the speaker must, of course, also be reduced. Since the dimension most important in this respect is the depth, there is an ever increasing number of shallow speakers being used. So as to offer the serviceman a suitable replacement speaker for these sets, Oxford electric has developed a series of shallow speakers which is identified as the "H" Series. These units have all the characteristics of the conventional replacement speakers. The "H" Series is limited to five sizes, which will be sufficient for almost all replacements.

A turn-out of some 250 service people attended the first 1954 meeting of the Service Managers' Organization of New York held at the New York Trade School on Wednesday, September 29th, according to Donald Packer, Service Manager of Olympic Radio & Television Inc., who sponsored the meeting.

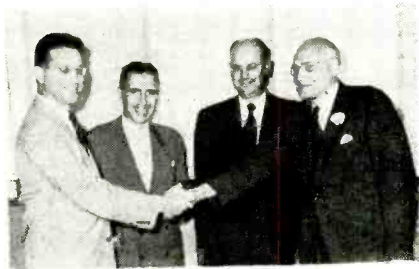OLYMPIC'S Chief Engineer, Lee Seigmund, spoke about service considerations of OLYMPIC'S new vertical chassis.



Norman B. Krim, Vice-President and General Manager Raytheon's Receiving and Cathode Ray Tube Operations, congratulates F. Edward Anderson, Distributor Tube Sales Manager, on completion of 25 years of continuous service. Mr. Anderson directs the replacement sales of Receiving, Picture and Industrial Tubes, including Semi-conductor Diodes and Transistors to over 600 distributor accounts. Mr. Anderson is a member of the Radio Oldtimers Club and is well known throughout the radio and television industry.

An agreement by GE field TV-radio service executives has been reached by which GE radio repair work will be channelled through independent service shops throughout Pennsylvania. A ninety-day free-labor policy has been inaugurated by GE for its radio line, by which all sets will be serviced by their distributors during the length of the guarantee period. GE, during a recent meeting with the Federation of Radio Service Men's Associations of Pennsylvania, declared that it did not want to exploit the service business and compete with service and appliance dealers.

IT'S FUN TO STAY UP WHEN YOU HAVE SUCH GOOD, CLEAR RECEPTION



The Tung-Sol Tubes you get from your wholesaler are the same high quality tubes used by leading radio and TV set manufacturers. You'll be giving customers like me the best possible service when you replace with Tung-Sol Tubes.

TUNG-SOL[®] dependable TUBES-DIAL LAMPS

TUNG-SOL makes All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Picture Tubes, Radio, TV and Special Purpose Electron Tubes and Semiconductor Products.



now you can really
understand
COLOR TV!

get the new SAMS book

**"Fundamentals of
Color Television"**
by
BOYCE



written so
you can
UNDERSTAND IT
ONLY
\$2.00

all you want to know
in five great chapters:

CHAPT. 1: "What You Need to Know About Color."
A simple description of color, its relationship to the eye, its application in Color TV; explains terms: hue, saturation, mixtures, purity, chromatic, achromatic, luminosity, etc.

CHAPT. 2: "Color Picture Reproduction." Covers physical aspect of color reproduction in the picture tube; tube structures and exact physical functioning in all major color tube types.

CHAPT. 3: "Principles of NTSC Color System." Complete description of Color TV signal; compatibility requirements; integration of color and sound; methods of transmission and reception.

CHAPT. 4: "Color Receivers." Covers theory of operation of various receiver systems using any of the color picture tubes, in block diagram analysis form.

CHAPT. 5: "Circuit Analysis of Color Receivers." Covers every circuit in detail; gives practical information on special components associated with color; all text supported by photos, block diagrams and schematics.

Prepare for Color TV with the help of this complete, easy-to-understand up-to-date book. 224 pages. 5½ x 8½".

ORDER BA-1 **\$2.00**
Only

**ORDER
TODAY**

HOWARD W. SAMS & CO., INC.

Order from your Parts Jobber today, or write to Howard W. Sams & Co., Inc., 2209 East 46th St., Indianapolis 5, Ind.

My (check) (money order) for \$..... enclosed. Send.....copy(ies) of "Fundamentals of Color Television" (BA-1, \$2.00)

Name.....

Address.....

City.....Zone.....State.....
(outside U.S.A. priced slightly higher)

AUDIO ADAPTATIONS

[from page 49]

The TV receiver schematic must be referred to for two reasons. The first is to make sure that the cathode resistor of the output stage is returned to ground—not B minus. Those circuits employing an ungrounded B minus supply do not lend themselves to this adaptation due to the high voltage difference between the two chassis. The second is to note the value of the cathode bias resistor. Since there is negligible *dc* drop in the TV audio output transformer, the B plus screen voltage can be applied to the plate without disturbing the rest of the circuit—thereby allowing the use of the cathode load resistor, *R_k*, of the same value as the old one.

The same materials are used as described in the previous section with the addition of the load resistor. Notice that the cable is connected to the socket this time, instead of the base. The cathode follower's inherent degeneration also makes it desirable from the point of view of reduced amplitude distortion. This increase in fidelity, however, is obtained at the expense of a loss in gain. With the rather low value of load resistor used here, the stage gain is somewhere between 0.35 and 0.50—low even for a cathode follower. This should not prove a serious drawback in most cases, however, since the audio amplifier has ample reserve gain to make up for this loss.

Although most amplifiers contain an input grid coupling condenser, it pays to check the schematic for its presence. If there isn't any, a .01 *uf* paper condenser should be inserted at the amplifier end of the cable. Without this condenser, the grid would be driven several volts positive, causing excessive plate dissipation and distortion.

If, as is probable, these changes result in a duplication of volume controls, the amplifier control should be set at some high level and the volume varied at the TV set. This prevents the possibility of overdriving the earlier voltage in the receiver to make up for the loss in the cathode follower.

Speaker Switching by Means of Relays

If the customer's TV set uses a miniature audio output tube, such as a 6AQ5 (in which case the above adapters cannot be used because of the glass-to-metal seal) or his is one of those rare sets with a fairly good push-pull audio section, a great improvement in performance can be obtained by substituting the hi-fi speaker of his hi-fi system for the small commercial one used in most receivers. Fig. 3 indicates a method by which this

You Can Solve
Your Problems
in Handling

VHF and UHF

**TV SIGNAL
AMPLIFICATION**

**CHANNEL
CONVERSION**

**TV SIGNAL
DISTRIBUTION**

Easily...
Effectively...
Economically!

USE THIS HANDY COUPON

BLONDER-TONGUE LABORATORIES, INC.
Dept. VM-7, Westfield, New Jersey

Please send me the following FREE Literature:

- The B-T 'Add-A-Unit' Master TV System
- 'Add-A-Unit' Installation Manual
- TV Calculator
- UHF Converters

Name.....

Address.....

City.....Zone.....State.....

can be done without the addition of any switches or controls. Here a relay automatically throws in the hi-fi speaker only when the TV set is turned on. A double-pole-double throw, 6 volt *ac* relay is mounted on the rear of the hi-fi speaker enclosure and connected as shown.

It is not advisable to mount the relay at the TV set since this might lengthen the speaker cable considerably, possibly causing high frequency oscillations in feedback type amplifiers. Four conductor flat cable is practical for this job since it can be laid under the carpet.

Voltage for energizing the relay coil is obtained from the filament terminals of any 6 volt tube in the receiver. These terminals are made accessible by the use of a Vector test adapter, type "T", which is plugged between the tube socket and the tube.

This will not work with a set with either series or series-parallel filament strings, since the filament current would be changed. It is also a good idea to choose a tube whose filaments are returned to ground rather than some positive *dc* voltage. High *dc* voltages can cause trouble if the relay frame is grounded to the chassis by its mounting stud.

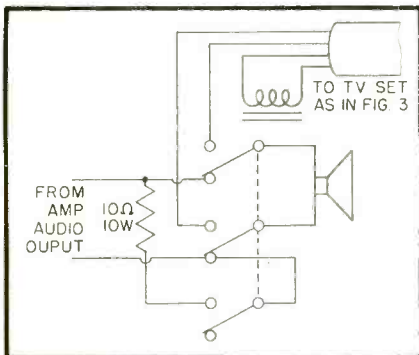



Fig. 4—Use of 3-pole relay to maintain permanent loading of audio output transformer.

Constant Loading on Output Transformer

With the above arrangement, it is possible to damage the hi-fi audio output transformer if the hi-fi audio system is turned on while the TV set is on. Fig. 4 shows how this hazard can be avoided at a slightly greater expense. By using a three-pole, double-throw relay, the transformer is loaded with a 10 ohm, 10 watt resistor when the TV set is in use, thereby maintaining a load on the hi-fi output stage under all switching conditions.

The matching resistor of Fig. 3 will be necessary when the speaker has a different impedance from the TV output transformer. A 10 ohm, 5 watt resistor is a good compromise for most cases.

HOTTEST IN THE FRINGES.. NATION-WIDE! CLEAR BEAM'S

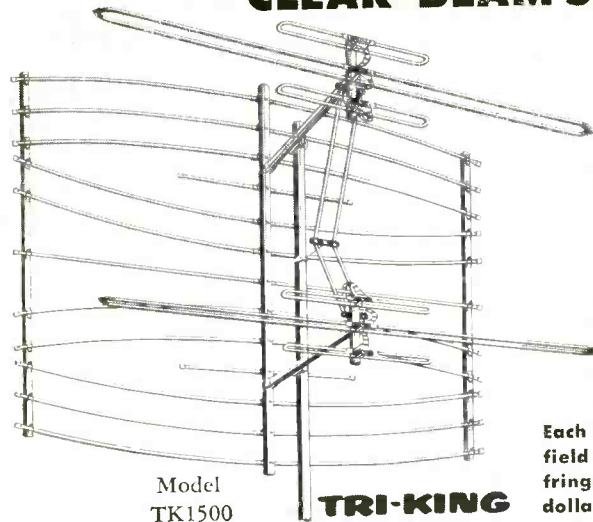

BIG 3

ALL-BAND FRINGE ANTENNAS


Each a peak performer in its field . . . a triple threat to any fringe problem . . . with more dollar-for-dollar construction value!

The Tri-King TK1500 offers super fringe performance through better design features. Half wave electrical spacing between dipoles for higher gain on every channel. Positive "back up action" through the use of a full radar screen . . . acclaimed industry-wide as the finest reflector ever designed for ghost rejection and elimination of co-channel interference! Fully wind tunnel tested.

Available in single bay (Model TK1000) and Super, wide spaced array (Model TK1800).

Clear Beam
BIG CHIEF
2 Bay Model BC 12-2

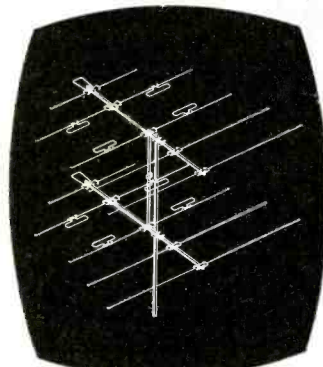
An advanced conical-Yagi with element diameters varied for precision tuning, matched sensitivity and peak performance on high and low band!



Clear Beam
HUNTER

2 Bay Model MYH 50-2

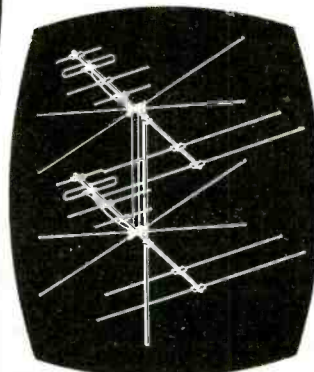New wave trap principle gives extremely high gain, sharp directivity, in-phase tuning on all channels. New, flat design for low wind resistance!



B CLEAR ANTENNA CORP. **BEAM**

Canoga Park, Calif. • Chicago, Ill.
affiliated with TEMPO TV products

Warehouses in Seattle, Portland, San Francisco, Honolulu, Dallas, Kansas City, Chicago, Detroit, Baltimore

1440 pgs.

Fully catalogs
Radio-TV-
Electronic
parts &
equipment:
Tubes,
Trans-
mitters,
Test Equip-
ment, Comm.
Receivers,
Transformers,
Capacitors,
Antennas,
Resistors,
Coils & Relays,
Recording &
PA Systems,
Hardware,
Tools, etc., etc.
**OFFICIAL BUYING
GUIDE OF THE
INDUSTRY**

1440 page MASTER for everything in Electronics

Make rapid selections from one industry-wide MASTER CATALOG complete with SPECIFICATIONS, ILLUSTRATIONS, DESCRIPTIONS, DIAGRAMS, PRICES on thousands of Radio-TV-Electronic parts and equipment.


NEW! 1955 BUYING GUIDE

List \$6.50

As low as **\$1.95** • Over 85,000 items • Fully indexed • 8½" x 11" • Over 8,500 illus. • Weighs 6 lbs.

From leading parts distributors or write to:

UNITED CATALOG PUBLISHERS, INC.
110 Lafayette Street, New York 13, N. Y.

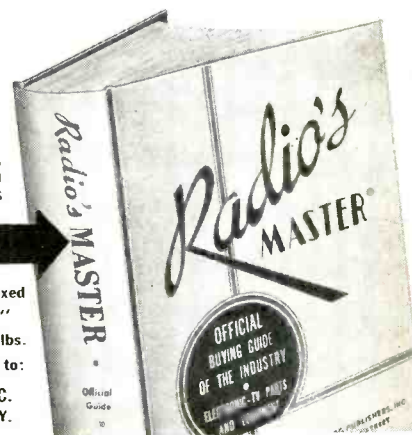

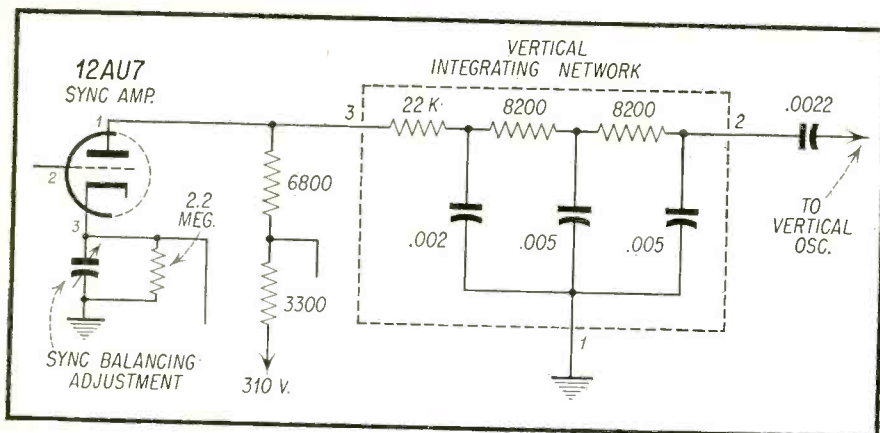


Fig. 2—Correct integrator wiring circuit.

ANSWERMEN

[from page 27]

of manufacturers TV receivers. But they do fail occasionally. What happens is that they open up inside at one of the leads. In the installation of the replacement integrating network several technicians have wired the new part in backwards.

Consider what would happen in Fig. 2 if the point 3 were connected to the .0022 μf condenser and point 2 were connected to the 6800 ohm resistor. The .005 μf condenser of the integrator network would short most of the horizontal pulse to ground leaving very little pulse to be used by the horizontal oscillator for lock-in purposes. However, the reactance of the .005 μf condenser to the vertical 60 cycle pulses would not be too low and there would be enough signal available at the output to hold the vertical oscillator in sync.

COLOR

[from page 14]

than that introduced by the filter in the I demodulator. To make both the I and Q signals arrive simultaneously at the matrix network a slight additional delay network is introduced in the I demodulator. Still on the subject of time delay it would be appropriate at this time to point out that the luminance channel which has negligible time delay is also provided with a time delay network. The latter brings the luminance signal into the matrix network at the exact same time as the I and Q signals.

Phase Splitter

In the I channel the I voltage is amplified and passed on to the phase splitter, whereas in the Q channel no amplification is necessary so that the output from the Q demodulator is coupled directly to its phase splitter. The purpose of the two phase splitters is to obtain both positive and negative polarity I and Q signal voltages. The positive and negative I and Q signals now enter a matrix network into which the Y signal is also fed.

Five signals are now available at the input of the matrix network. These are +I, -I, +Q, -Q, and Y. These five signals combine with each other in the matrix to produce the original red, green and blue color signals. The mathematical relationships are as follows:

$$R = .96I + .62Q + Y$$

$$B = -1.10I + 1.7Q + Y$$

$$G = -0.28I - .64Q + Y$$

These primary color voltages are then fed to the color signal amplifiers which are controlled by potentiometers, except for the red amplifier stage which em-



The Miller K-Tran I.F. Transformers are available for the following frequencies: 262 KC, 455 KC, 1500 KC, 4.5 MC and 10.7 MC.

4.5 MC transformers are for use in television receivers having an intercarrier sound channel. 10.7 MC transformers find their main application in FM receivers and tuners.

All transformers are shell core permeability tuned, thus providing a magnetic shielding of the windings and reducing the influence of the aluminum can. Stable silver mica fixed capacitors are enclosed in the low-loss terminal base.

CAT. NO.	Frequency	Use	NET PRICE
12-H1	262 KC	Input Transformer	1.50
12-H2	262 KC	Output Transformer	1.50
12-H6	262 KC	Output Transformer diode filter	1.59
12-C1	455 KC	Input Transformer	1.32
12-C2	455 KC	Output Transformer	1.32
12-C6	455 KC	Output Transformer diode filter	1.41
12-C7	455 KC	Input Transformer for Battery Radios	1.32
12-C8	455 KC	Output Transformer for Battery Radios	1.32
12-C9	455 KC	Input Transformer for AC-DC Radios	1.32
12-C10	455 KC	Output Transformer for AC-DC Radios	1.32
13-W1	1500 KC	Input Transformer	1.44
13-W2	1500 KC	Output Transformer	1.44
13-PC1	455 KC	Input I.F. Transformer For Printed Circuits	1.44
13-PC2	455 KC	Output I.F. Transformer For Printed Circuits	1.44
6203	4.5 MC	Input or Interstage Transformer	1.65
6204	4.5 MC	Discriminator Transformer	1.98
6205	4.5 MC	Ratio Detector Transformer	1.98
1463	10.7 MC	Input or Interstage Transformer	1.65
1464	10.7 MC	Discriminator Transformer	1.98
1465	10.7 MC	Ratio Detector Transformer	1.98
SUB-MINIATURE K-TRAN - Only 1/2" Square by 1 1/2" High			
10-C1	455 KC	Input Transformer	1.50
10-C2	455 KC	Output Transformer	1.50

(Available through your local distributor.)

*Manufactured under "K-TRAN" patents of Automatic Mfg. Co. *K-TRAN is registered trademark.

J. W. MILLER COMPANY
5917 South Main Street • Los Angeles 3, California

Canadian Representative: Atlas Radio Corporation, Ltd. 560 King Street, W. Toronto 2B, Canada

ploy a fixed gain network. These potentiometers are set entirely by the requirements of the phosphor efficiency of the color picture tube and their adjustments will be discussed in detail in a later chapter.

Following each individual color amplifier a color output stage may be found depending on the receiver design. The red, blue and green voltages are then applied to the respective electron guns of the tri-gun picture tube.

DC restoration is incorporated at this point. The use of *dc* restorers is essential to the proper presentation of color pictures. Whereas the omission of the *dc* component in a monochrome receiver is not serious because a turn of the "Brightness" knob can compensate for this loss, such a simple correction is not available to the operator of the color receiver. Although the "brightness or background" control of the color receiver does control all three guns simultaneously it does not affect them equally. The ratio of the different gun effects are dictated by the relative phosphor efficiencies and cannot be used to correct for defective video presentation, as would occur in the absence of the three *dc* components.

REMOTE CONTROL


[from page 29]

6. Now place the unit back in the chassis and pick up location of mounting holes from the mounting bracket making sure that the shafts are perfectly aligned and the gap above-mentioned is maintained. Then drill two holes with a ± 19 drill.
7. Before making units secure to chassis, determine the proper method of coupling the tuner shaft (Figure 6).
8. Placing the Motor Assembly back in chassis, slide it forward so that coupler engages both shafts and secure brackets in position, #8 screw assemblies.
9. Where the method in Figure 4 applies, take the following steps: Place the base of mounting bracket A against rear wall of tuner so that large hole in the base centers around the tuner shaft. (NOTE: If the tuner shaft does not protrude through rear wall of tuner, it will be necessary to drill a hole in rear wall of the tuner so that the coupler can slide onto the tuner shaft without binding.)
10. Pick up mounting hole locations from mounting bracket and drill two ± 29 holes in the tuner case. Mount with two #8 sheet metal screws and lock washers.
11. Mount the Motor Assembly to

bracket B as shown in Figure 4 and secure with two #8 screws and lock washers into the mounting studs of the Motor Assembly. (Motor Assembly in Figure 4 can be rotated 180° and then mounted if space so demands.)

12. Bracket B may now be mounted onto Bracket A dependent upon space limitations. The motor shaft should be cut at whatever length is desirable so that Bracket B can be bolted to Bracket A as space allows. It is important that a gap of from 1/32" to 1/8" be maintained between the shaft of the tuner and the shaft of the motor.

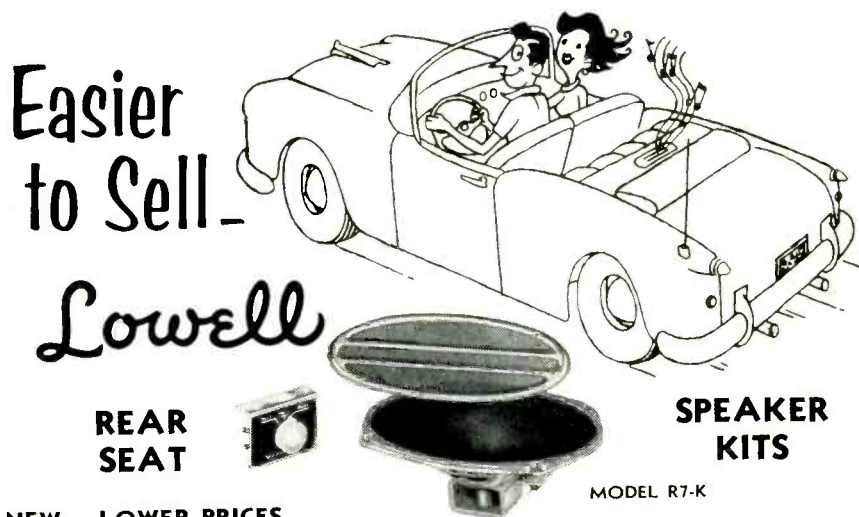13. Now attach the coupler as shown in Figure 6A.
14. Slide the coupler onto the tuner shaft and bolt the brackets in place. Use #8 screw assemblies.
15. Mount the Relay Assembly in any convenient location preferably on the rear of the chassis using #8 screws. (Bear in mind that the female disconnect plug will require a corresponding hole in the cabinet-back.)
16. The unit is now ready for wiring. Follow the wiring diagram, using tag attached to the Relay Assembly for sequence of wiring. **PAY STRICT ATTENTION TO**



NEW — LOWER PRICES

Greatly increased demand for the popular LOWELL rear seat speaker kits enable a substantial reduction in price. NOW — more than ever, LOWELL is your best buy — Sells itself on sight because it's *quality thru and thru!*

NOTE THESE LOWELL FEATURES!

- ♣ Finishes to harmonize with any car interior. Standard colors include grey, light blue or light bronze. Chrome at slight additional cost.
- ♣ Perforated metal grille protects speaker cone from damage, is fade-proof, tamper-proof. Edges of all metal parts nicely turned and finished. LOWELL REAR SEAT SPEAKER KITS are QUALITY THRU AND THRU!
- ♣ Available as a complete kit, with or without speaker.
- ♣ Two popular sizes. MODEL R7-K with 6" x 9" oval speaker. MODEL R5-K with 5" x 7" oval speaker.
- ♣ Highest quality permanent magnet speakers for finest reproduction of speech and music.
- ♣ Kit includes easy to mount 3 position switch to permit use of car radio speaker alone, rear seat speaker alone or both simultaneously. All hardware, instructions and 15' cable furnished.



MODEL R5-K

All the way around, LOWELL rear seat speaker kits offer smarter styling, higher quality, improved fidelity and easier installation. You can see the difference; hear the difference, yet LOWELL costs you less!

WRITE FOR ILLUSTRATED FOLDER WHICH GIVES COMPLETE DETAILS

IN CANADA:
ATLAS RADIO CORP., LTD.,
560 KING STREET, WEST,
TORONTO 28, CANADA

Lowell MANUFACTURING CO.
3030 LACLEDE STATION RD., ST. LOUIS 17, MO.

FIX EVERY TV RECEIVER!

TV FIELD SERVICE MANUALS

Edited by Harold Alsborg

JUST PUBLISHED: VOLUME 3

A complete TV tube location handbook PLUS all these other valuable features: for each model, a table of more than 30 trouble symptoms, showing tubes to check, parts to check, adjustments to make . . . field (and shop) adjustments on horizontal oscillators, tuner oscillators, AGC controls, picture tubes . . . explanations of 40 most-commonly-found troubles, with picture tube patterns to illustrate each one—drawings of front & rear preset controls and tuner dial stringing, tube complement, key voltages, series filament wiring. 7 years (1947-1953) of TV receiver production in each volume! Spiral bound—open the book and it stays open! Why wait? Order all 3 volumes today!

VOL. 3 (JUST PUBLISHED) (Cat. #155-3) covers: Emerson, Fada . . . only \$2.10

VOL. 2 (Cat. #155-2) covers: Bendix, Caphart, CBS-Columbia, Crosley, DuMont . . . only \$2.40

VOL. 1 (Cat. #155) covers: Admiral, Affiliated Retailers (Artone), Aimcee (AMC) Air King, Air Marshall, Allied Purchasing, Andrea, Arvin, Automatic . . . only \$2.10

SIZE OF ALL 3 BOOKS: 5 1/2" x 8 1/2"

OTHER VOLUMES COMING SOON!

These books tell you how!

TV MANUFACTURERS' RECEIVER TROUBLE CURES

JUST PUBLISHED: VOLUME 6

QUESTION: Who's the one man who can tell you—better than anybody else—how to cure a specific fault in a specific receiver?

ANSWER: THE MANUFACTURER!

Nobody knows his own set like the manufacturer! And here—in one compact, inexpensive series—64 different TV receiver manufacturers give you the facts on specific "bugs" that have come up in their models! In our new Volume 6, for instance (all new—coverage up through 1954—no duplication—new manufacturers), 12 makers list 249 precise, "how-to—" answers about specific troubles and improvements in their sets! Volumes 1 to 5 give you similar coverage! Every volume gives you important information on such typical problems as picture bending . . . intercarrier buzz . . . fringe area operation . . . sync instability . . . interference . . . jitter . . . retrace blanking . . . poor picture quality . . . and much, much more! Not theory or "perhaps" information—actually tells you how to cure existing faults! Lists step-by-step procedures to follow, parts needed, etc.—also shows you how to improve performance of the set! One service call pays for all 6 volumes! Order your set today!

VOL. 6 (JUST PUBLISHED) (Cat. #143-6) covers: Admiral, Aimcee (AMC), Arvin, Bendix, Cadillac TV, Caphart, CBS-Columbia, Conrac, Crosley, DuMont, Emerson, Firestone.

Vols. 1-5 cover 61 manufacturers from A to Z!

EACH VOLUME 128 (5 1/2" x 8 1/2") PAGES

ONLY \$1.80 EACH

OTHER VOLUMES COMING SOON

Rider books are sold by parts jobbers and book stores throughout the country. If YOUR dealer doesn't have these books, mail this coupon to us!

JOHN F. RIDER PUBLISHER, INC.
Dept. SD-12, 480 Canal St., N.Y.C.

Please RUSH me:

TV FIELD SERVICE MANUALS

- Vol. 1 . . . \$2.10
 Vol. 2 . . . \$2.40
 Vol. 3 . . . \$2.10

TV RECEIVER TROUBLE CURES

- Vol. 1 . . . \$1.80 all 6 volumes at \$1.80 ea.

Name

Address

City & State

THE COLOR CODE. Be sure to recheck your wiring. Then plug REMOT-O-MATIC male plug into female plug on the Relay Assembly. On the remote unit, set the fine tuning knob up to its maximum (clockwise). Turn the set on at the set itself and align all operating channels to the center of the fine tuning range. Now shut the set off at the set and turn the brightness control on the set itself to its maximum position (clockwise).

From the remote unit, turn the set on and operate each control on REMOT-O-MATIC to prove your wiring. Then turn off the set.

17. Re-install the chassis into the cabinet. Make a hole in the cabinet-back where male plug is to engage female plug. Replace cabinet-back. Turn Remot-O-Matic over to your customers so that they may now really enjoy television.

HORIZONTAL OUTPUT TRANSFORMERS

[from page 17]

is the subject of our discussion is termed, as previously mentioned, a "horizontal output and high voltage" transformer, or simply a "flyback" transformer.

Figure 4 is a simplified schematic for the purpose of explaining the production of the high voltage to be used for the 2nd anode of the picture tube. A logical starting point in this explanation is at the grid of the horizontal output tube. The driving voltage at this point is the modified sawtooth or trapezoidal wave of voltage shown in Fig. 4B. The horizontal output tube is biased with a voltage sufficiently negative so that current will flow through the tube only when the signal rises above the dotted line of Fig. 4B. The output tube therefore conducts between A and C, D and E, and G and I. It is cut off between B and C and also between D and E. It can be seen then, that the current in plate circuit will have the form shown in Fig. 4C. This is the current flowing through the section of the autotransformer winding from top #2 to top #1 in Fig. 4A.

As the plate current rises from A to B, a similar current is induced in the secondary circuit; similar that is, in wave form. Actually, the current in the secondary circuit is larger than that in the primary because of the step down ratio in the transformer. If this sounds strange, just recall that when the voltage is stepped down, the current is stepped up. As this current flows through the horizontal deflection coils, it builds up

Color's bigger than ever! AND THE NEW 2ND EDITION OF



IS MORE THAN EVER A MUST

Color television receivers at much better prices are due to hit dealers' floors any time now. And when color television starts moving in volume . . . every technician must be ready for this new, different, profitable field. There's not a day to lose. Get your copy of the brand new 2nd edition of *PRACTICAL COLOR TELEVISION* . . . and get it right away!

Here is the latest practical color service information you can get from any source. Included in its 86 pages are: Principles of Color Television . . . Detailed Circuit Diagrams . . . Operating Instructions . . . Antenna Requirements . . . Test Recommendations . . . and much, much more. Time-tested information . . . brought up to the minute by RCA, pioneer in compatible color television.

\$2.00 a copy . . . and worth far more in future color television profits for you! See your RCA Parts and Tube Distributor, or mail the coupon . . . today.

RCA SERVICE COMPANY, INC.

A Radio Corporation of America Subsidiary
CAMDEN, NEW JERSEY

RCA Service Co., Inc.
Commercial Service Section
Camden, N. J.



Please send me _____ copies of "Practical Color Television" at \$2.00 each.

Check or Money Order for \$. . . enclosed.

NAME

COMPANY

STREET

CITY ZONE STATE

a steadily increasing magnetic field around these coils. This of course is the field which is responsible for the deflection of the electron beam. At points corresponding to B, E, and H of Fig. 4C, the magnetic field reaches its maximum value and then suddenly drops to zero. (Note. Actually, a shock excited oscillation begins at points B, E, and H. In the interest of simplicity and clarity, this action of the circuit will be omitted now and discussed in detail when the damping circuit is taken up.) Since the collapse of the field is very rapid, and since one of the factors which determines the size of the induced or back *e.m.f.* is the speed with which the lines of force cut the turns of wire in the yoke, there results across the yoke a high pulse of back *e.m.f.* This pulse reaches a value of approximately 1500 volts.

Notice, from Fig. 4A, that since this pulse appears across the terminals of the deflection coil, it must also appear across the terminals of the secondary winding of transformer, since these points are electrically the same. Now it is important to note that when the signal was being traced through from left to right, the transformer was a step down transformer, that is, fewer turns on the secondary than on the primary. However, in following the pulse of back *e.m.f.* from right to left, starting at the yoke, the transformer, working in reverse, steps up this rule of voltage. Terminals A and B, in Fig. 4A for example may be considered as the primary for the pulse, and terminals 1 and 3 the secondary. Depending on the design of the transformer, the pulse may be stepped up to a value of from approximately 9 KV for some of the 10 inch receivers to as high as 20 KV for some present day receivers.

[To Be Continued]

RESISTIVE NETWORKS

[from page 31]

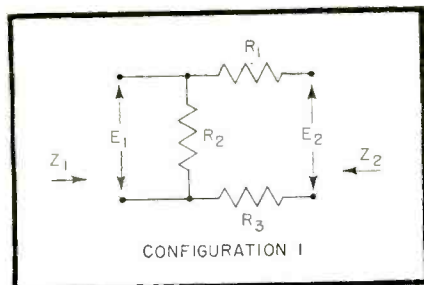


Fig. 1—Unbalanced to balanced load network.

value of loss encountered can normally be compensated for by merely advancing the signal generator output.

An impedance match is not con-

sidered essential when a fixed-frequency generator is being used since the mismatch would normally only introduce errors in the indicated microvolt output, a measurement which is not accurate anyway with inexpensive signal generators. It follows of course that when accurate signal strength measurements are being made a proper generator-to-receiver impedance match should be provided. The loss introduced by the matching network must of course be taken into account in determining absolute values of receiver input.

This simple little device may take on considerable importance in *uhf* work. While tuner alignment has not consti-


tuted a major problem in *vlf* receivers it seems possible that it will in *uhf* equipment. If so, a matching device effective over a wide frequency range will be necessary for satisfactory results. It may also be necessary in recovering sufficient signal voltage to adjust antenna coupling in *uhf* tuners to provide proper antenna transmission line impedance matching, in which case it will be absolutely essential to have the test line properly terminated.

Transmission Line Termination


The antenna input impedance of a TV tuner may vary widely (as much as 10 to 1) for different channels. Hence

9 OUT OF 10 Fringe Area Installations Need ACME ELECTRIC VOLTAGE ADJUSTORS

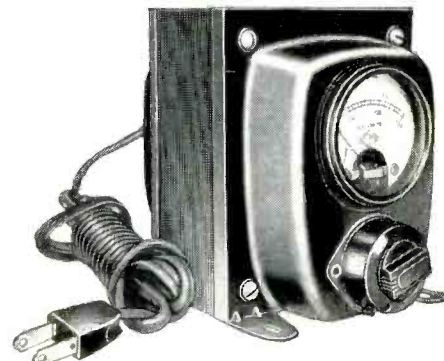Overloaded distribution lines and low voltage service are prevalent conditions in TV fringe areas according to a recent "spot check". As a result complaints on picture shrinking, fluttering and dimming plague the service man. Usually this condition can be readily corrected with an Acme Electric Voltage Adjustor, either the inexpensive manual type or the deluxe automatic design.




The T-8394M Voltage Adjustor can be used by the service man to reproduce the operating condition about which the customer complains by turning tap switch to the voltage which simulates such condition. For example, customer complains that evening program pictures flicker and shrink. When service man calls next day all operation appears normal — voltage tests out properly. But, by adjusting voltage to 97 volts the condition about which the complaint was made is reproduced. This indicates low voltage condition during evening that can be corrected with a T-8394M Voltage Adjustor.

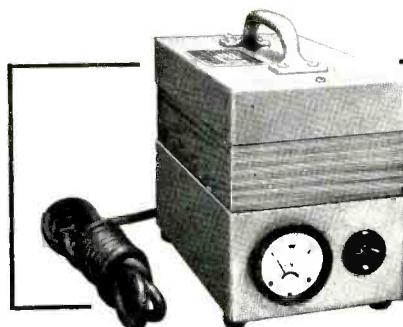

Regardless of line voltage supply, the Automatic Voltrol corrects voltage fluctuation over a range from 95 to 130 volts. The voltmeter supplied indicates secondary voltage while unit is in operation. A built-in relay automatically disconnects circuit when set is turned off.

Acme Electric
TRANSFORMERS

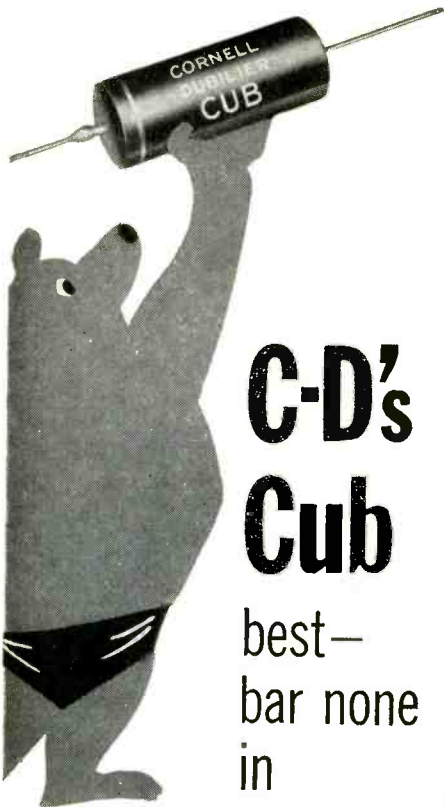ACME ELECTRIC CORPORATION
MAIN PLANT: 4612 WATER STREET • CUBA, N. Y.
West Coast Engineering Laboratories:
1375 West Jefferson Boulevard. • Los Angeles, California
In Canada: Acme Electric Corp. Ltd.
50 Northline Road • Toronto, Ontario



C-D's Cub

best—
bar none
in

molded tubular capacitors

The C-D "Cub" capacitor has proven itself the best on the market today—by out-lasting, out-performing, out-selling any other replacement capacitor for radio or TV. For consistent high quality—always rely on C-D, the only tubulars with the built-in extras required in servicing sets today. That's why distributors *who know*, carry the complete C-D line.

Special! "Cub-Kit" with bonus plastic service dispenser. IT'S FREE!

Ask your C-D Distributor. He's listed in your local Classified Telephone Directory.

CONSISTENTLY
**CORNELL-
DUBILIER**
DEPENDABLE



THERE ARE MORE C-D
CAPACITORS IN USE TODAY
THAN ANY OTHER MAKE.

PLANTS IN SO. PLAINFIELD, N. J.; NEW BEDFORD, WORCESTER AND
CAMBRIDGE, MASS.; PROVIDENCE AND HOPE VALLEY, R. I.; INDIANAPOLIS,
IND.; SANFORD AND FUGUAY SPRINGS, N. C.; SUBSIDIARY, RADIART
CORP., CLEVELAND, OHIO.

any signal generator-to-receiver impedance matching device which depends on the reflected impedance of the tuner input will be subject to considerable mismatch. For instance, with either a transformer match or a generator with a direct 300 ohms output a tuner input impedance of 3000 ohms would reflect a 10 to 1 mismatch to the transmission line. Under these conditions, alignment procedures could not be expected to give satisfactory results. It is therefore necessary to use an isolation termination such as Network C with direct output, transformer-matched or "balun"-matched sweep generators.

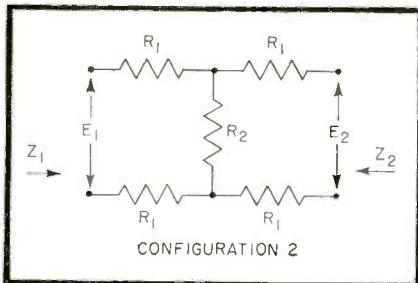


Fig. 2—Isolation network for regulating impedance across generator as load impedance varies.


With this isolating network designed for input and output impedances of 300 ohms the input impedance will vary only from 267 ohms to 370 ohms as the tuner input impedance varies from 30 to 3000 ohms. It is interesting to note that with Network A, designed for 72 ohms, a like change of tuner input impedance would cause the transmission line termination to vary only from 64 to 80 ohms, a variation small enough so as not to require an additional isolation network.

The isolation terminating network should also be found useful in reducing ghosts in troublesome installations using unusually long transmission lines. If the antenna transmission line is sufficiently mismatched at the receiver end a portion of the received signal will be reflected back toward the antenna and if the line and the antenna are sufficiently mismatched, as they are sure to be at some frequencies, the reflected signal will be re-reflected back to the receiver. These reflected signals if sufficiently strong will cause multiple ghosts on the picture. Proper termination of the line at either end will eliminate these reflections and the resulting ghosts; a job made to order for Network C since it will maintain proper impedance match at the receiver end of the line for all channels regardless of variations in the receiver input impedance. Of course the signal will have to be sufficiently strong to provide a satisfactory picture after suffering the network loss. Note that



**WHY
LOOK
HIGH
AND
LOW?**

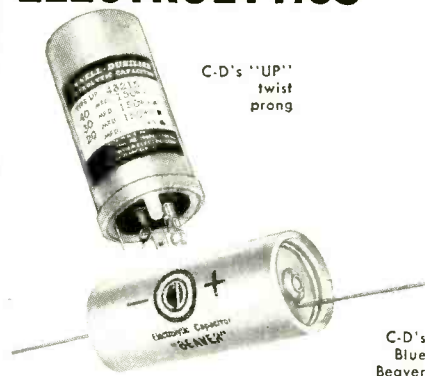**C-D IS THE ONLY
COMPLETE LINE OF
ELECTROLYTICS**



No matter what you need in electrolytic capacitors—C-D has it. Every type, shape and rating... all of consistent high quality proven by outstanding field performance. C-D capacitors are always reliable... and readily available—because Distributors *who know*, carry the complete Cornell-Dubilier line.

Free! TV Capacitor "Replacement Guide"—and C-D Twist Prong Cross Index from your C-D Distributor. He's listed in your local Telephone Directory.

CONSISTENTLY
**CORNELL-
DUBILIER**
DEPENDABLE



THERE ARE MORE C-D
CAPACITORS IN USE TODAY
THAN ANY OTHER MAKE.

PLANTS IN SO. PLAINFIELD, N. J.; NEW BEDFORD, WORCESTER AND
CAMBRIDGE, MASS.; PROVIDENCE AND HOPE VALLEY, R. I.; INDIANAPOLIS,
IND.; SANFORD AND FUGUAY SPRINGS, N. C.; SUBSIDIARY, RADIART
CORP., CLEVELAND, OHIO.

the losses given in Table 1 are for networks terminated with the rated output (Z_2) impedance. This loss will vary with the actual value of antenna input impedance. For instance the loss in Network C will vary from 2.4 to 5.6 db as the antenna input impedance is varied from 30 to 3000 ohms.

Signal Attenuation Applications

Resistor networks may also be used to reduce the signal strength by a required amount while maintaining the proper transmission line impedance termination. Two examples of such applications are discussed below.

In cases of excessive signal strength it is desirable to reduce the signal with an attenuator rather than by rotating the antenna away from the station direction. The attenuator will help to provide a good transmission line termination and will also reduce the susceptibility to

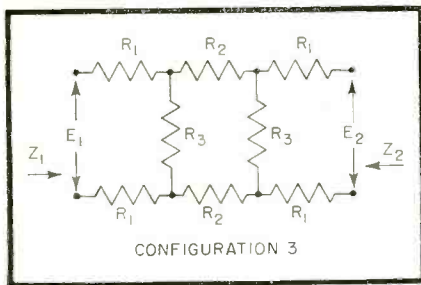


Fig. 3—Attenuation sections in cascade.

ghosts from reflected signals. Station location relative to the receiving location may in some cases dictate the use of a network of suitable attenuation to reduce the signal level from a close signal to within the *age* range of the receiver while at the same time allowing sufficient signal level from more distant stations.

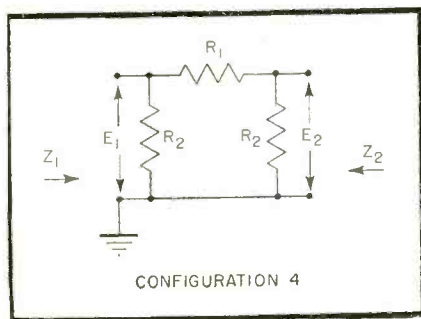


Fig. 4—Attenuation network for use with 72-ohm lines.

Another use for the attenuation network is in service testing. To insure proper operation of sync circuits a test should be made to insure picture sync under weak signal conditions. Resistor networks provide a convenient means for reducing the signal level for such

checks. The amount of attenuation may be varied by selection of the proper resistor values to reduce the signal while still maintaining the desired input and output impedances. Network C and D for 300 ohm balanced line provide 10 db and 20 db attenuation respectively. For values greater than 20 db it is desirable to use two attenuation sections in cascade as in Network E. in this arrangement individual resistor valued remain small thus reducing leakage so that the network will provide attenuation at higher frequencies.

Networks F and G provide 10 and 20 db attenuation respectively for use

with 72 ohm coax transmission line. Note that with these networks the terminal which is common to the input and output must be connected to the shield side of the transmission line.

Antenna Distribution

When sufficient signal strength is available a resistor network may be used as a convenient means of feeding several receivers from a single antenna. This simple device has the advantages of requiring no power and of operating uniformly over a wide frequency range. Furthermore the inherent insertion loss provides a good degree of isolation be-

Unequaled Performance and Appearance Achieved with New RCP Design.

Universal MULTITESTER—MODEL 480
Only \$14.85 Net

Based on the world famous RCP model 447 Multitester, the model 480 sets an all-time high in value for an economical, rugged, universal tester that is a must for every laboratory, shop and serviceman's kit.

3" meter 800 microampere D'Arsonval movement gives 1,000 ohms per volt sensitivity. Battery for ohmmeter readily removable—no soldering necessary. Flush molded in jacks.

Only because of enormous production is this unusually low price possible. Here is a better, yet lower cost, instrument than any similar unit on the market.

Tube Tester Meets All Today's Needs, Plus Tomorrow's Color Television.

PORTABLE TUBE TESTER—MODEL—327P
Only \$51.95

Greatest testing performance ever built into a compact instrument. Tests all tubes in current radio and television receivers, as well as in color TV receivers: checks transmitting, hearing aids, ballasts, gaseous rectifiers, and tuning indicators.

A stream-line approach to the tube test charts gives simple and speedy operation and permits easy, rapid addition of new tube test data. Data is also given on current color TV tubes.

Checks CRT picture tubes both black and white and color with CR adapter cable (available at slight additional cost). Black and white picture tubes can readily be reactivated with this tester.

An unusually compact, lightweight instrument for bench and on-the-job use. Solid oak carrying case with slip-hinge cover.

See your local parts distributor or WRITE SD-12 FOR LATEST RCP CATALOG

RADIO CITY PRODUCTS CO., Inc.

152 WEST 25th STREET • NEW YORK 1, N. Y.



Replacement
Needling You?

TRY THE

Walco
Packaged
SERVICE PLAN

8 Ways Better!

Service men go for Walco's packaged phonograph needle replacement plan because it's so easy to understand and put to work. No headaches trying to figure out which needle for which cartridge—two easy guides figure for you. And you don't have to be a salesman to sell replacement—even to sell profitable diamond needles—Walco sells 'em for you, by proven methods learned in our long experience as leaders in the replacement needle industry—and as originators of the modern jewel tip needle. See how the Walco plan stacks up 8 ways better to help you service and sell:

1 WALCO SERVICE PAKS—for VM, Webcor, RCA, Philco, Magnovox and other leaders. Take the right Pak on a service call and you're ready for instant replacement anywhere.

2 EASY REPLACEMENT GUIDE—3-page center spread in Walco's Catalog 600 gives instant identification of osmium, sapphire and diamond needles. Includes illustrations and prices. You can put it on your wall.

3 10-SECOND GUIDE—to most popular replacements. Name of phono is all you need!

4 CROSS-REFERENCE INDEX—gives you the right Walco Needle Number to replace any replacement needle.

5 LISTING IN SAM'S PHOTOFACTS—convenient help when you need it.

6 REPLACEMENT REMINDER STICKERS—Peel protective back, stick on customer's phonograph. Tells him when needle was replaced by you—reminds him to replace periodically.

7 RECORD SPINDLE CARDS—They tell the customer you've replaced a needle and how long it will wear—then urge him to re-order.

8 NATIONAL ADVERTISING—building your customer's confidence in Walco and in you for replacing with Walco. Ads in High Fidelity, Saturday Review and other record-minded magazines.

Get all the information—see how much easier it is to sell and service with Walco!

SEND FOR WALCO'S CATALOG 600

Walco TRADE NAME OF
ELECTROVOX CO., INC.
Leaders in Replacement Needles
60 Franklin Street, East Orange, N. J.

tween receivers so as to minimize the possibility of the different receivers on the same antenna system interfering with each other.

A network arrangement for this application is Configuration 5. Table 2 lists the resistor values and pertinent characteristics for different combinations of impedance and number of receivers in the system. Resistor values have been selected to provide the minimum insertion loss while maintaining proper impedance values. For less than

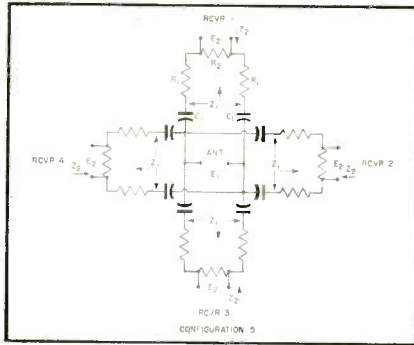


Fig. 5—Network arrangement for feeding several receivers from a single antenna system.

four receiver outlets only the appropriate number of outlet networks of the values shown in Table 2 would be connected. The isolating capacitors, C, are included to prevent power current from flowing between two receivers which have the power and antenna circuits connected to the chassis.

Note that in the Configuration 5 network the isolation between receivers is increased as the network loss is increased so that, providing sufficient signal

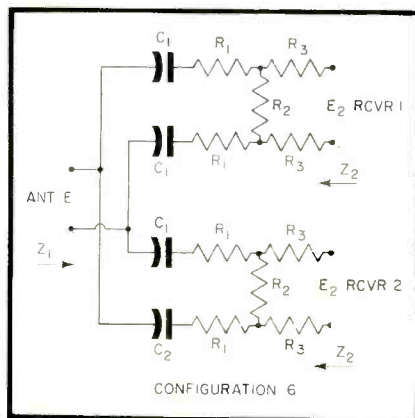



Fig. 6—Two-outlet network with increased attenuation.

strength is available, the increased loss is an advantage in increasing receiver isolation. A two-outlet network with increased receiver isolation is shown as Configuration 6. The values for this arrangement are also shown in Table 2.

The Secret Is In The Lips

JFD "LITTLE GIANT"
LIGHTNING ARRESTER

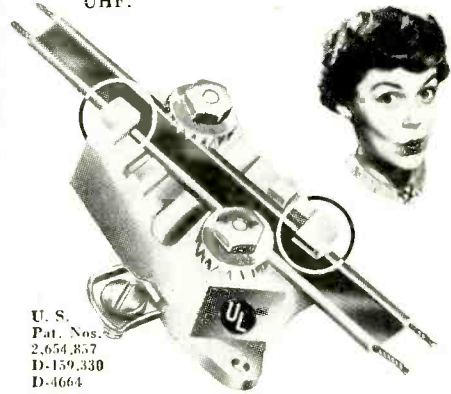Look for the exclusive strain-relief patented retaining lips that protect your lead-in—VHF or UHF.



U. S.
Pat. Nos.
2,654,857
D-159,330
D-4664

You see positive contact made.

No. **AT105** (for wall or window sill mounting) **\$1.25** list


No. **AT105S** (with stainless steel strap for universal mounting) **\$1.50** list

Look to JFD for Engineering Leadership

JFD MFG. CO., Inc., Brooklyn 4, N. Y.
INTERNATIONAL DIVISION
15 MOORE ST. N. Y. C.

**SELL MORE TUBES!
SAVE SERVICE TIME!**

INDISPENSABLE
ON EVERY
SERVICE
CALL

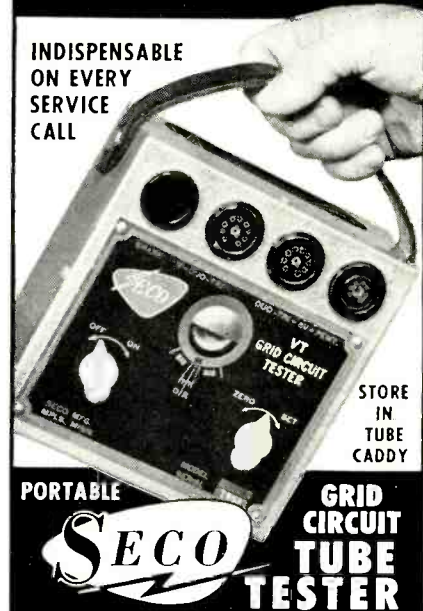

PORTABLE

SECO

GRID
CIRCUIT
TUBE
TESTER

STORE
IN
TUBE
CADDY

MAKE THIS 4 WAY CHECK:

1. Control grid emission (Exclusive Feature!)
2. Grid to cathode shorts.
3. Gaseous condition in tube.
4. Cathode to heater shorts.

See your Jobber or write for literature and prices.

SECO MFG. CO. 5013 PENN. AVE. S.
MINNEAPOLIS, MINN.

Availability

A number of the networks described herein are available commercially either in printed circuit form or as assemblies of carbon composition resistors in small plastic boxes. Those that are not readily available can be easily assembled in the shop. The accompanying photograph shows one of the 300/300 ohm, 20 db attenuators listed in Table 1 which has been assembled into a small plastic Walsco hardware box.



One of the 300/300 ohm, 20 db attenuators listed in Table 1 assembled in small plastic container.

A four-receiver antenna network, Configuration 5, consisting of parts mounted on a lucite panel in a physical arrangement similar to that shown in the schematic has been found by the author to give good performance. The isolation in this network is sufficient so that disconnecting any number of receivers does not appreciably affect the performance of those remaining connected.

While the networks described herein are basically quite simple devices as evident from the accompanying photograph, care must be used in their assembly to insure best performance. Particularly for use in the *uhf* TV band, small resistors with very short lead lengths must be used. The very small 1/10-watt carbon composition resistors are well suited to this application since they allow closer spacing and smaller overall size. Extreme care must be taken in the soldering operation to prevent excessive heat from causing damage to or changing the value of the resistors. The heat from the soldering iron applied close to the resistor body can easily cause a permanent increase in resistance of over 10%. Probably the best soldering technique for this application consists of first scraping or sanding the resistor leads and then generously but quickly tinning both the terminals and the resistor leads. Then, after securing the leads to the terminals, and while holding the resistor lead with long nose pliers close to the body, quickly solder each terminal without the addition of any more solder. In this manner the time of heat application is held to a minimum and the pliers help to soak up some heat and keep down the temperature of the resistor body.

SHOP-AIDS


by Authorized

A New Approach to Test Instruments . . . Stressing . . . Portability—
Compact Design—Ease of Operation—Clear, Positive Results in
Understandable Form

Authorized CRT TESTER—

Reveals the condition of a picture tube quickly and accurately. No time lost in unnecessary computation. The split neon bulbs indicate the continuity of the tube. A meter gives the emission reading.

Only **\$49.95**
dealer net

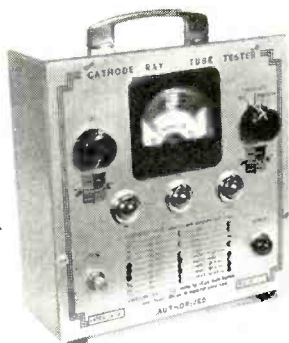

Authorized MULTIVOLTER—

A portable power supply with a variable voltage source. Takes the place of dry cells. A convenient source of voltage substitution without complicated switching. —135-0-+135 v d-c; 0-135 v a-c; 6.32 @ 1a.

Only **\$14.95** dealer net
Write for complete Technical Data



Authorized MANUFACTURING COMPANY
919 Wyckoff Avenue, Brooklyn 27, N. Y.

WAIT!

**DON'T BUY ANY
SOLDERING IRON
UNTIL YOU SEE**

**THE
New ESICO
SOLDERING IRON**

Makes all other irons
obsolete!

*The shape of
soldering irons to come!*

UNVEILING EARLY IN 1955

ESICO

ELECTRIC SOLDERING IRON CO., INC.
DEPT. F DEEP RIVER, CONN.



"Our stock of
JENSEN NEEDLES"

Radio-Television Service Dealer Annual Index for 1954

ANSWERMAN

44 mc band for TV receivers.....	June p. 29
AC voltage on antennas.....	Aug. p. 27
Adjacent channel interference.....	June p. 29
Admiral Ch. 21J1—width.....	Jan. p. 32
Bias Box (troubleshooting <i>agg</i>).....	May p. 12
Capehart—weak pix.....	Nov. p. 34
CBS-Columbia Ch. 750-3—height.....	Oct. p. 27
Condenser checker.....	July p. 13
Crosley Model 10-416—audio modulation of pix.....	Sept. p. 36
Crosley Model DU-21, Ch. 357-1—focus.....	Jan. p. 31
Difference between tuner and converter.....	Apr. p. 16
Du Mont RA-306—Intermittent pix shrinkage.....	Sept. p. 36
Emerson 600TV—retrace suppression.....	May p. 12
G.E. 17T103—vertical hold.....	May p. 15
G.E. 24C101—ripples in patterns.....	Dec. p. 27
H.O.T. whistle.....	July p. 13
Increasing scope gain.....	Oct. p. 52
Montgomery Ward 2WA—weak.....	Aug. p. 47
Muntz 21" TV—excessive arcing.....	Nov. p. 34
Philco 51-T1606—pix pulls.....	Mar. p. 53
Philco Model 1600—no boost dc, insufficient hor. deflection.....	Jan. p. 32
Philco Ch. 71RF—vert. deflection.....	Jan. p. 32
Philco Model 48-1001—brightness.....	Apr. p. 11
Philco field strength meter.....	Mar. p. 54
Proper service techniques.....	May p. 18
RCA Model 2T51—width.....	Jan. p. 31
Replacing 10BP4 with 10RP4.....	Aug. p. 27
Replacing tuners with Standard Cascade tuners.....	Feb. p. 51
Rhombic Antennas.....	Mar. p. 53
Selenium Rectifiers.....	July p. 43
Sylvania Ch. 1-500-1—Horizontal drifts.....	Dec. p. 27
Traveler Model 64R50—Intermittent Channel 7 and 13 reception.....	Sept. p. 36
Yagi Antennas on new channels.....	Apr. p. 11

ASSOCIATION NEWS

Associated Radio & TV Servicemen of Chicago.....	June p. 53
Associated Radio-TV Service Dealers of Columbus, Ohio.....	Mar. p. 58 Apr. p. 45 Sept. p. 27
Associated Radio-TV Servicemen of New York.....	Mar. p. 17
Certified Electronic Technicians Assn., New York.....	Nov. p. 16
Council of Radio & TV Service Associations, Penna.....	Feb. p. 56 Mar. p. 58 Apr. p. 8 July p. 41
Electronic Service Association Detroit, Mich.....	July p. 41
Empire State Federation of Electronic Technicians Assns., N. Y.....	Nov. p. 16
Eastern TV Conference.....	Mar. p. 17 June p. 53 July p. 41 Sept. p. 27
Federation of Radio Servicemen's Associations, Penna.....	Jan. p. 50 Sept. p. 27
Long Branch Radio Technicians Association, Long Branch, Cal.....	Apr. p. 30
Long Island Electronic Technicians Association, L.I., New York.....	Jan. p. 48 Feb. p. 56 Mar. p. 14 Apr. p. 8
Long Island TV & Radio Technicians Guild.....	Feb. p. 14 Apr. p. 45 June p. 53 Sept. p. 27 Oct. p. 18
National Alliance of Television and Electronic Service Associations.....	Feb. p. 14 Mar. p. 58 Sept. p. 27
National Electronic Technicians & Service Dealers Assns.....	Feb. p. 14 Oct. p. 18
Philadelphia Radio Servicemen's Association, Inc.....	Feb. p. 16 Apr. p. 8 Nov. p. 16
Radio & TV Association of Springfield, Ohio.....	Mar. p. 17
Radio & TV Technicians' Guild, Gadsden, Alabama.....	June p. 53
San Antonio Radio & TV Association, Texas.....	Mar. p. 14
Southern Pennsylvania Radio & TV Technicians Association.....	Apr. p. 45

Television Installation Service Assn., Chicago, Ill.....	July p. 41
Television Service Dealers Assn., Phila., Pa.....	July p. 41
Texas Electronics Assn.....	Oct. p. 18
Ulster Electronic Technicians Association, Kingston, N. Y.....	June p. 53

CIRCUIT COURT

Capehart CX36—Sync System.....	Mar. p. 52
DuMont RA160—Vertical Amplifier.....	Mar. p. 52
Sylvania 1-518—Video Amp., Sync, Keyed AGC.....	Jan. p. 39

EDITORIAL

A Publisher Hurts Servicemen.....	Oct. p. 5
Beware of Fake Subscription Salesmen.....	Mar. p. 6
Changing Service Dealer Trends.....	Sept. p. 4
Color TV Merchandising.....	Jan. p. 10
Color TV Set Prices.....	Feb. p. 10
Color TV Status.....	July p. 4
Current Production and Sales Figures.....	Sept. p. 4
Instruments and Progress.....	July p. 4
Legal Verdicts of Interest.....	Aug. p. 4
Lost Opportunities—Lost Dollars.....	Dec. p. 4
New Discounts open to Hi-Fi Servicemen.....	June p. 5
New Type Manufacturers Service Policy.....	Nov. p. 5
Opinions Pro and Con.....	Jan. p. 10
Optimists are Wel.....	Mar. p. 6
Our Prediction is Upheld.....	Oct. p. 5
Our New Departments.....	May p. 5
Our New Regular TV Service Information Section.....	Sept. p. 4
Picture Tube Prices.....	Feb. p. 10
Price Cutting is Rampant.....	Feb. p. 10
Please Answer Our Questionnaire Promptly.....	Apr. p. 5
Printed Circuit Servicing.....	Nov. p. 5
Published Price Schedules.....	Nov. p. 5
Random Notes.....	Feb. p. 10
Scarce Metal Shortage.....	Aug. p. 4
Servicing Color TV Sets.....	Feb. p. 10
Shop Efficiency.....	May p. 5
Starting Our Fifteenth Year.....	Apr. p. 5
The Customers Write.....	Jan. p. 10
The Readers Write.....	June p. 5
TV Channel Changes.....	Feb. p. 10
TV Receiver and Station Count.....	Dec. p. 4
We Apologize.....	Mar. p. 6
We Caused a Furor.....	Sept. p. 4
Wholesale Servicing.....	Nov. p. 5
Worthwhile Income Booster Ideas.....	May p. 5
You Ask For It.....	May p. 5

FEATURE ARTICLES

A.G.C. Problems, by Paul Goldberg.....	July p. 20
A.G.C. Systems, by Phil Maucher.....	Apr. p. 48
A New Cathode Ray Tube Tester by Morton Greenberg.....	Nov. p. 49
A New License Bill by Abraham Frankel.....	July p. 24
A New Deal For Hi-Fi by Noel Namro.....	Aug. p. 17
A New TV Remote Control Unit by Irving R. Gwartz.....	Dec. p. 28
Antenna Check, by Fred Voorhaar.....	Aug. p. 14
A New All-Channel VHF-UHF Antenna by Harris and Greenberg.....	Apr. p. 53
Applications of Resistive Networks by J. C. Geist.....	Dec. p. 31
A Revolutionary Method of Antenna Coupling by Harold Harris.....	Sept. p. 24
A Special Purpose Tube Tester by Jacob Anthes.....	July p. 22
A Versatile VTVM, by R. Blitzer.....	June p. 44
Audio Adaptations for Profitable Servicing, by Gil Tint.....	Dec. p. 32
Auto Inverters, by San D'Arcy.....	June p. 23
Block Diagram Analysis of Color Transmission and Reception by Bob Dargan and Sam Marshall.....	Sept. p. 9 Part 1..... Part 2..... Part 3.....
CBS Color Tube.....	Sept. p. 31
Chrominance Systems in Color TV Receivers by Bob Dargan and Sam Marshall.....	Dec. p. 11
Color Oscillator and Central Circuits by Bob Dargan and Sam Marshall.....	Mar. p. 19
Color Stripe Signal.....	May p. 29
Color TV, by Leonard Lieberman.....	Jan. p. 23 Part 3..... Part 4.....

Community Antenna System by Edward M. Noll.....	Oct. p. 22
Curing TVI in AM Radios by Steve Travis.....	Sept. p. 21
Detroit Servicemen's Show.....	Dec. p. 36
Du Mont Chroma Sync Teletron.....	June p. 51
Entering Hi-Fi, by Gil Tint.....	May p. 22
Enterprising TV Serviceman Brings Shop to Customer.....	Mar. p. 30
Fifth Annual NATESA Convention Get Started in P.A., by Gene Hessel.....	Apr. p. 47 Part 1..... Part 2.....
High Voltage Problems by Paul Goldberg.....	July p. 20
Horizontal Frequency Troubles by Paul Goldberg.....	Aug. p. 36
Horizontal and High Voltage Color Set Circuitry by Bob Dargan and Sam Marshall.....	May p. 9 Part 1..... Part 2..... Part 3..... Part 4.....
Jetonic Antenna by Douglas H. Carpenter.....	May p. 20
Key Test Points, by Bob Dargan.....	Jan. p. 26 Part 2..... Part 3..... Part 4.....
Key Test Points, by Steve Travis.....	Oct. p. 38 Part 1..... Part 2.....
Lead Dress Problems by Paul Goldberg.....	Sept. p. 32
Oscilloscope Y-Axis Pre-Amplification, by Harry Casey.....	June p. 10
Performance and Market Analysis of Rotators, by Arne Benson and Bernard Nussbaum.....	Nov. p. 24
RC Circuits, by Cyrus Glickstein.....	May p. 34 Part 3..... Part 4..... Part 5.....
Remote Tuners, by San D'Arcy.....	Apr. p. 28
Replacing Printed Circuit Components, by Admiral Corp.....	Nov. p. 7
Sectionalized Printed Circuit TV Receiver by Walco Electronics Corp.....	Dec. p. 19
Sell and Service Radio-Controlled Garage Door Openers by San D'Arcy.....	July p. 33
Servicing Marine Radio, Part 1 by Marvin Klein.....	June p. 24
Servicing Video I-F Systems (Symposium Series No. 10) by Matthew Mandl.....	Feb. p. 21
Servicing Vertical Instability by Steve Travis.....	Oct. p. 10
Sniello-Vision, by Oscar Fisch.....	Apr. p. 52
Solving Sweep-Alignment Problems by Robert G. Middleton.....	Mar. p. 27 Part 1..... Part 2..... Part 3.....
Sound Problems, by Paul Goldberg.....	May p. 30
Servicing Remote Tuners by Woodrow W. Smith.....	Aug. p. 18
Stand-off Insulators and UHF by Carpenter and Tolins.....	Jan. p. 40
Sync Amplifier Problems by Paul Goldberg.....	Oct. p. 34
Sync Amplifier Problems by Paul Goldberg.....	Dec. p. 34
Tape Recorder Servicing Series by Robin Blanchard.....	July p. 14 Part 1.....
Torture Test for TV Rotators by Herbert G. Koenig.....	Mar. p. 41
Transistor Portable, by Regency.....	Dec. p. 24
True and False Color Concepts by Matthew Mandl.....	July p. 18
Tuner Problems, by Paul Goldberg.....	Nov. p. 50
TV Service Information Sheets CBS Columbia Ch 750-3, 751-3.....	Oct. p. 65
Raytheon Ch. 17T18, 21T19.....	Nov. p. 65
CBS Columbia Color TV Receiver Model 205.....	Dec. p. 65
TV Colorimetry by Bob Dargan and Sam Marshall.....	Apr. p. 21
TV Instrument Clinic by Robert G. Middleton.....	Apr. p. 12 Part 1..... Part 2..... Part 3..... Part 4..... Part 5..... Part 6.....
Understanding and Servicing Horizontal Output Transformer Circuits, by Oscar Fisch.....	Nov. p. 32 Part 1..... Part 2.....
Universal Test Bench Connectors by Irving Tepper.....	Mar. p. 31

Video Amplifier Servicing Hints by Robert G. Middleton	Mar. p. 27
Waveform Analysis in Sync Circuits, by George Holmes	Jan. p. 45

GUEST EDITORIAL

Edward F. Morgan, CBS-Columbia	Jan. p. 16
H. J. Schulman, Du Mont	Feb. p. 12

NEW PRODUCTS

Jan. p. 46, Feb. p. 54, Mar. p. 56, Apr. p. 54,
May p. 51, June p. 42, July p. 34, Aug. p. 31,
Sept. p. 52, Oct. p. 50, Nov. p. 52-54, Dec.
p. 48.

RIDER TV FIELD MANUAL SERVICE DATA SHEETS

Admiral TV Chassis 22C2: 22E2	Mar. p. 43
Aimcee Model 1C23, Ch. T.D.	Sept. p. 45
Arvin 1900 Series	May p. 43
Capehart Model 12F272M, Ch. CT-74	Mar. p. 47
Dumont RA-166, -167, -170, -171	Nov. p. 41
Emerson Models 711F, 712F, 720D, 732B, 734B, 733F	Feb. p. 43
Fada Models 17C2, 17C4, 17C6, 17T9	May p. 47
Firestone Models 13-G-128, -129, -130, etc.	
Codes 334-3-MS39A, 334-3-MS39B	Oct. p. 37
Firestone Model 13-G-135	Nov. p. 43
General Electric Models 17C125, 20C107, 20C201, etc.	Sept. p. 47
Hallcrafters Models 1067, 1068, Chassis L1100D, runs 1 & 2	June p. 33
Hoffman, Chassis 400, Models 21M721, -B723, -M722 and Chassis 401, Models 21M146, -B147, -P148, -M320, -B321, -P322	July p. 25
Magnavox Chassis CT, Series 331 through 357	Apr. p. 41
Majestic, Series 112-17", 113-21"	July p. 27
Motorola, Models 17F13C etc.	June p. 37
Olympic, TM-TN Chassis	Nov. p. 45
Pacific Mercury Chassis 200-1, 2, 3, 4, etc.	Oct. p. 39
Philco Ch. R-191, D-191, Code 140	Dec. p. 43
RCA KCS74 and KCS74M1	Jan. p. 41
RCA KCS81, Models 305, 305U, 317, 317U, etc.	Aug. p. 31
Sentinel, Mods. LU500, 510, 511, etc.	Aug. p. 29
Stewart-Warner, Model 9132A	Dec. p. 45
Sylvania Chassis 1-508-1, 1-508-2	Feb. p. 47
Western Auto Model 2D-1315A, 2D1325A, etc., Ch. 21T1A, -2A, 17T1B	Oct. p. 41
Westinghouse, Ch. V-2233-1, Models H740T21, H742K21, H743K21	Sept. p. 49

TRADE FLASHES

Jan. p. 6, Feb. p. 6, Mar. p. 8, Apr. p. 6,
May p. 52, June p. 50, July p. 42, Aug. p. 42,
Sept. p. 16, Oct. p. 54, Nov. p. 20, Dec. p. 50.

TRADE LITERATURE

Feb. p. 16, May p. 63, June p. 56, July p. 45,
Oct. p. 58.

VIDEO SPEED SERVICING SYSTEMS

Admiral 21B1	Nov. p. 35
Crosley Model 10-419MU	Sept. p. 37
Capehart CX-33DX	June p. 45
Du Mont chassis RA109	Feb. p. 35
Du Mont chassis RA105	Apr. p. 37
Du Mont chassis RA164	June p. 47
Du Mont chassis RA166	July p. 29
Du Mont chassis RA306	Aug. p. 23
Emerson chassis 120066-B, Mod. 571	Mar. p. 35
General Electric 830 "R" Version	Jan. p. 35
Hallcrafters, Mod. 805, ch. M800S	Apr. p. 39
Hallcrafters, Mod. HA-861-1	Sept. p. 39
Kaye Halbert Model 231	July p. 31
Majestic Model 121B	Dec. p. 37
Motorola, ch. TS32B, Mod. 12VT13	Mar. p. 37
Muntz 2053A, chassis 17B1	Nov. p. 37
Philco Mod. 50-T1600, 51-T1600, etc.	Dec. p. 39
Philco chassis R181, D181	Oct. p. 43
Philco chassis R191, D191	Aug. p. 25
Philco RP41, 42, 43	Feb. p. 37
RCA KCS47A	May p. 37
RCA KCS68C	Nov. p. 39
RCA KCS81	Dec. p. 41
Sentinel Model 1U425	Sept. p. 41
Sylvania 1-504-1	May p. 39
TeleKing 812	Jan. p. 37
Westinghouse chassis V2150-101	Mar. p. 39
Zenith 23G22	Feb. p. 39
Zenith Chassis 21L21	Oct. p. 48

WORKBENCH

Admiral 19B1— Shift in Oscillator Frequency	Nov. p. 50
Admiral 20V1—Buzz	May p. 30
Admiral 21B1—No Brightness	July p. 20
Admiral 21C1—Lack of Horizontal and Vertical Hold	Dec. p. 34
Admiral 22A2—Video Overload	June p. 41
Admiral 22M1—Horizontal Drift	Aug. p. 36
Admiral 22M1—Smearred Pix	Sept. p. 33
Capehart CX-33— Horizontal Wiggle	Feb. p. 33
Capehart CX-33— Intermittent Blooming	July p. 20
Crosley Mod. 10-423MX— Short in Front End	Nov. p. 51
Du Mont RA-103C—Horizontal Frequency Out of Range	Aug. p. 36
Du Mont RA-103C—Vertical Roll and Horizontal Wobble	Dec. p. 35
Du Mont RA-103D— Insufficient Height	Jan. p. 33
Du Mont RA105— Pix and Sound Fades Out	Sept. p. 32
Du Mont RA164— Critical Vertical Hold	Mar. p. 34
Emerson Mod. 654B, ch. 12011B— Video Overload	June p. 41
Emerson Ch. 120162A—Horizontal Pull and Vertical Roll	Oct. p. 34
Freed Model 55—Hum	Sept. p. 33
General Electric 10T1— Critical Vertical Hold	Mar. p. 34
General Electric 12T1— Horizontal Tearing	Feb. p. 34
Motorola TS-60—Loss of Channels	Jan. p. 34
Motorola TS-60— Poor Horizontal Hold	Feb. p. 33
Motorola TS95—Sound Distorted at High Volume Setting	May p. 31
Motorola TS114— Intermittent Horizontal Pull and Vertical Jitter	Oct. p. 35
Philco Model 52-1882-121, RF chassis 44, Defl. ch. D4— Vertical Roll	Mar. p. 33
Philco 1954 "B" TV181— 183's Burn Out	July p. 21
RCA KCS 47A— Intermittent H.V.	Jan. p. 34
RCA KCS82—Horizontal Pull	Oct. p. 34
RCA 630TS—Pulling at Top of Pix and Vertical Slipping	Dec. p. 35
Tele-King 812—Distortion	May p. 30
Westinghouse chassis 21050-01— No Raster	July p. 21
Zenith, Ch. 24G26— Low γ Gain	Nov. p. 50

ASSOCIATION NEWS

[from page 8]

the problem of handling sets through an intermediary who later claims the set was not his so he wants the set returned without charge. Storage of these "orphans" and protection against losses pose serious and costly problems.


To overcome this situation, a new form of receipt, shown below, has been developed and proved very efficient.

RECEIPT	
In consenting to the removal of or acceptance for service of the unit described on this receipt, the undersigned states that it is his/her property and that service is being assumed by the company with the understanding that the set will be stored for a period of not more than 30 days following notice of completion of service, phone or post card notice is deemed sufficient. After 30 days, it is agreed that a storage and protection fee of 25c per day will be added to the billing. It is further agreed that should the goods not be claimed after 60 days from date of this receipt and should no other previous arrangement in writing be agreed upon, the company has the authority to junk, sell or in any other way dispose of the goods and be completely released of any and all claims against it arising from the transaction covered by this receipt.	
Signed _____	Set Owner
Signed _____	Company
Date _____	

RTSA—Pittsburgh

The RTSA of Pittsburgh, Inc., is in the process of setting up a course in TV Training to upgrade the qualified technician. This subject was brought up the last regular meeting, and quite some enthusiasm was shown by the show of hands.

COMING JAN. 15!

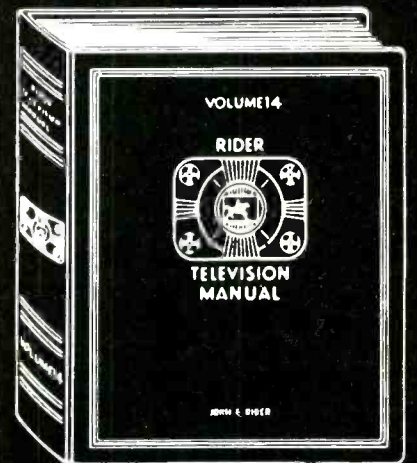

RIDER'S TV 14


LIMITED PRINTING—

*tell your jobber to
reserve your copy now!*

only \$24.

**Preferred for
Original Equipment
Proven for
Replacement**

**O
X
F
O
R
D**

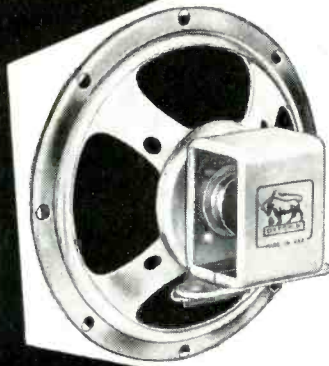

Speakers

Available from leading jobbers!

OXFORD ELECTRIC CORP.


3911 S. Michigan Ave., Chicago 15, Ill.

EXPORT: ROBURN AGENCIES, N.Y.C., N.Y.

In Canada: Atlas Radio Corp., Ltd., Toronto

AUDEL'S TV-RADIO SERVICE LIBRARY

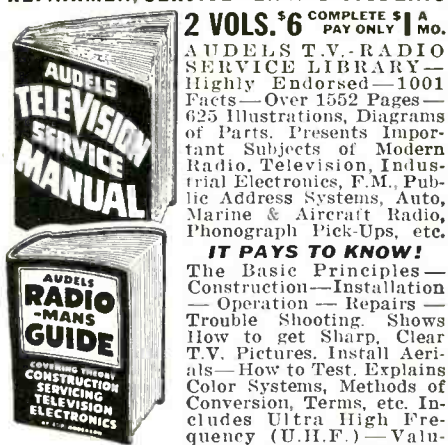HERE IS LATE INFORMATION IN A HANDY FORM FOR RADIO AND TELEVISION REPAIRMEN, SERVICEMEN AND STUDENTS



2 VOLS. 6 COMPLETE \$1 A MONTH PAY ONLY \$1 MO.

AUDEL'S T.V. RADIO SERVICE LIBRARY—Highly Endorsed—1001 Facts—Over 1552 Pages—625 Illustrations, Diagrams of Parts. Presents Important Subjects of Modern Radio, Television, Industrial Electronics, F.M., Public Address Systems, Auto, Marine & Aircraft Radio, Phonograph Pick-Ups, etc.

IT PAYS TO KNOW!

The Basic Principles—Construction—Installation—Operation—Repairs—Trouble Shooting. Shows How to get Sharp, Clear T.V. Pictures. Install Aerials—How to Test. Explains Color Systems, Methods of Conversion, Terms, etc. Includes Ultra High Frequency (U.H.F.)—Valuable for Quick Ready Reference & Home Study. Tells How to Solve T.V. & Radio Troubles—Answers Your Questions.

Get this Information for Yourself. 7 DAY TEST—ASK TO SEE IT!

MAIL ORDER

AUDEL Publishers, 49 W. 23 St., N.Y. 10, N.Y. Mail AUDEL'S T.V. RADIO SERVICE LIBRARY 2 Vols. \$6 on 7 days free trial. If O. K. I will remit \$1 in 7 days and \$1 monthly until \$6 is paid. Otherwise I will return them.

Name _____
Address _____
Occupation _____
Employed by _____ SD

Advertising Index

Acme Electric Corp.	57
Astron Corporation	18
Audel Publishers	64
Authorized Manufacturing Co.	61
Belden Manufacturing Co.	2
Blonder-Tongue Laboratories, Inc.	52
Bussmann Manufacturing Co.	1
Channel Master Corp.	6, 7
Chicago Standard Transformer Corp.	49
Clear Beam Antenna Corp.	53
Columbia Wire & Supply Co.	33
Cornell-Dubilier Electric Corp.	9, 58
Electric Soldering Iron Co., Inc.	61
Jensen Industries	61
Jensen Manufacturing Co.	10
JFD Manufacturing Co., Inc.	60
Lowell Manufacturing Co.	55
Miller, J. W. Co.	54
Ohmite Manufacturing Co.	8
Oxford Electric Corp.	64
Precision Apparatus Co., Inc.	Cover 3
Radiart Corporation	9
Radio City Products Co., Inc.	59
Raytheon Manufacturing Co.	Cover 2
RCA Tube Dept.	Cover 4
RCA Service Co., Inc.	56
Remot-O-Matic Sales, Inc.	14
Rider, John F. Publisher	56, 63
Sams, Howard W. & Co.	52
Seco Manufacturing Co.	60
Snyder Manufacturing Co.	22
Sprague Products Co.	64
Standard Coil Products Co., Inc.	21
Transvision	64
Tung-Sol Electric, Inc.	50, 51
United Catalog Publishers	53
Walco	60
Walsco Electronics Corp.	26
Weston Elec. Instrument Corp.	5

**GET THIS NEW
SPRAGUE T-C RULE**



Save time . . . avoid mistakes . . . in finding the values of stock N750 and NPO type ceramic capacitors to connect in parallel to equal a capacitor of desired intermediate temperature coefficient of the required capacitance. Just slide this handy, pocket-size rule to the proper values and you'll come up with the right answer quick as a wink every time. On back are complete color codes on all types of ceramic capacitors. Ask your Sprague Distributor for one, or write to Sprague Products Co., 71 Marshall Street, North Adams, Mass. It's only 15c.

SPRAGUE PRODUCTS COMPANY

Distributors' Division of the Sprague Electric Co.
NORTH ADAMS, MASS.

FOR
The Finest
**MASTER
AMPLIFIED
AND COMMUNITY TV
ANTENNA SYSTEMS-**

— Send Us Your Problem for
FREE Engineering Advice.

FREE: Important Technical Manual for Community and Master TV Systems

FIELD STRENGTH METER, operates both on Battery and AC . . . \$89.

Write today to:
TRANSVISION, INC. NEW ROCHELLE, N. Y.

MOVING?



Please Mail Us Your Change of Address Today

Also include old address and code line, if possible. Thanks.


RADIO-TELEVISION SERVICE DEALER

67 West 44 St., New York 36, N. Y.

PLAY IT SAFE!



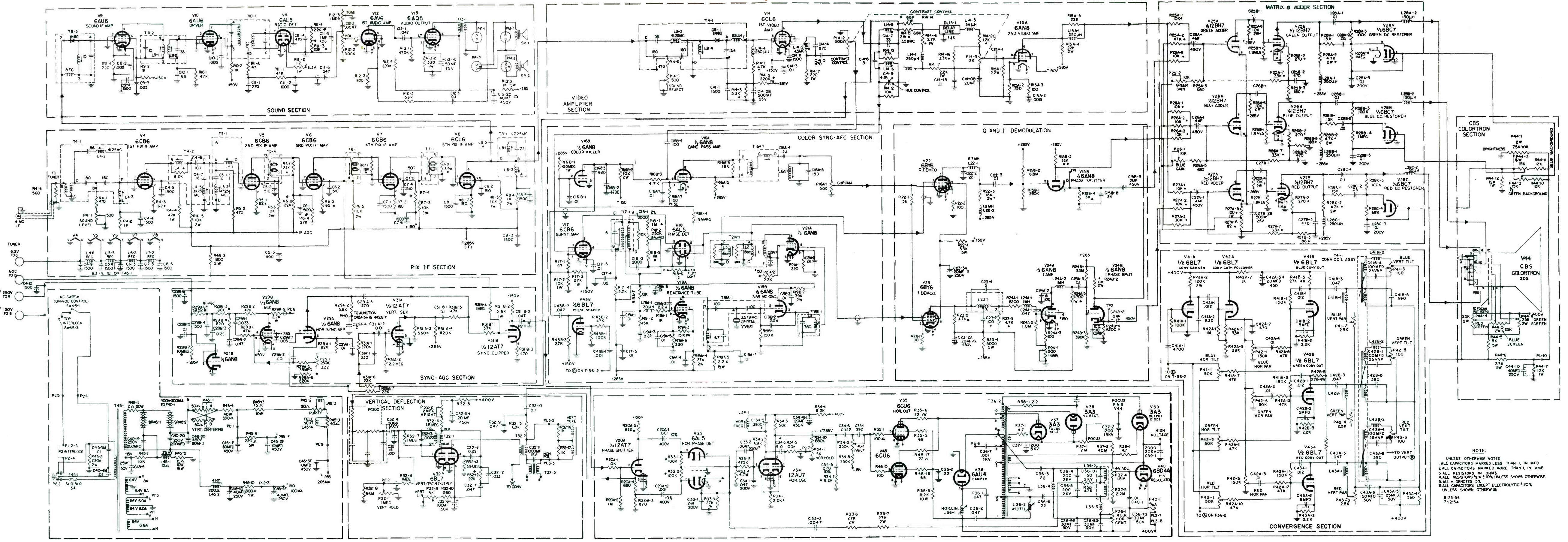Support—
THE ARTHRITIS
AND RHEUMATISM
FOUNDATION



NOTE
 1. ALL CAPACITORS MARKED LESS THAN 1 IN MFD.
 2. ALL CAPACITORS MARKED MORE THAN 1 IN MFD.
 3. ALL RESISTORS $\frac{1}{2}$ W. 5% UNLESS SHOWN OTHERWISE.
 4. ALL RESISTORS $\frac{1}{4}$ W. 10% UNLESS SHOWN OTHERWISE.
 5. ALL * DENOTES 5% UNLESS SHOWN OTHERWISE.
 6. ALL CAPACITORS EXCEPT ELECTROLYTIC $\pm 20\%$ UNLESS SHOWN OTHERWISE.


8-23-54
 7-12-54

CBS-COLUMBIA

COLOR TELEVISION RECEIVER

PRELIMINARY SERVICE DATA

MODEL 205

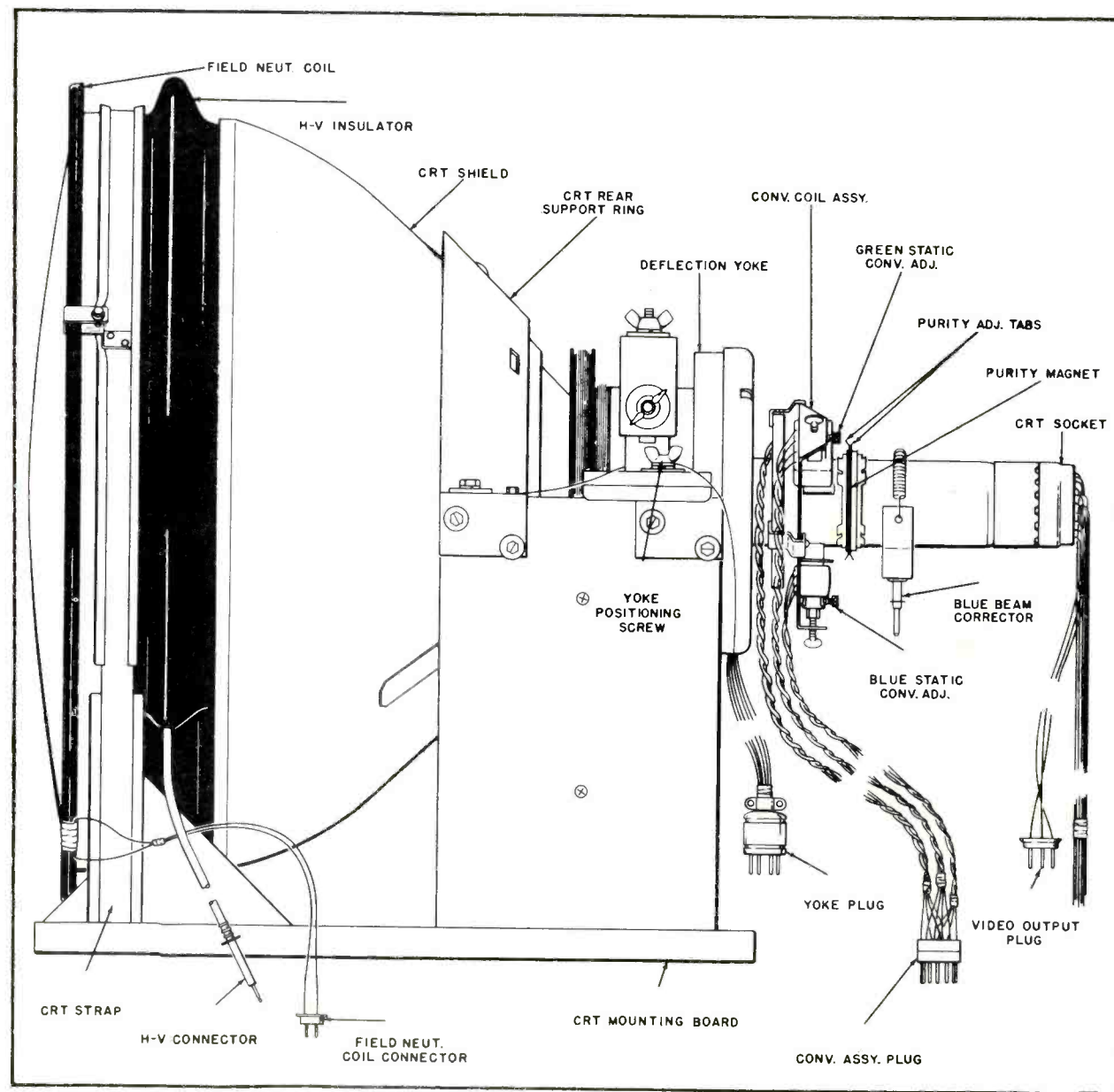

Picture tube assembly.

Picture Tube
Type CBS Hytron 19VP22
Dimensions 19-inch round, all glass. Viewing area 205 square inches

Operating Controls
Station Selector, Fine and UHF Tuning, Vertical and Horizontal, Hold, Contrast, Volume, Tone, Chroma and Hue

Power Rating
Source 105-120 volts 60-cycle AC
Consumption 500 Watts

Number of Tubes
41 tubes plus 3 rectifiers, 2 selenium rectifiers and 3 crystal diodes

Ant. Input Impedance
VHF 300 ohms balanced
UHF 300 ohms balanced

Frequency Range
Channels 2 through 82

Intermediate Frequencies
Video IF 45.75 mc
Sound IF 41.25 mc
Sound Inter-carrier Freq. 4.5 mc
Color Subcarrier Freq. 42.17 mc
Adjacent Channel Sound 39.75 mc
Trap Freq. 47.25 mc
Adjacent Channel Video 47.25 mc
Trap Freq. 41.25 mc
Accompanying Channel Sound for less than 10% distortion 41.25 mc

Crt High Voltage
26 kv adjusted

Loudspeakers
Size Two, 6½ in x 9¼ in. speakers
Voice Coil 3.2 ohms at 400 cycles

Focus
Electrostatic

Deflection
Electromagnetic

Convergence
Static PM Magnetic
Dynamic Electromagnetic

Cabinet Dimensions

Model	Width	Height	Depth
205C1 Console	34¼	42-11/16	26-1/16
205C2 Console w/Doors	34¼	42-11/16	26-15/16






Warning - High Voltage

POTENTIALS AS HIGH AS 26,000 VOLTS ARE PRESENT WHEN THIS RECEIVER IS OPERATING. OPERATION OF THE RECEIVER OUTSIDE THE CABINET OR WITH COVERS REMOVED INVOLVES A SHOCK HAZARD FROM THE RECEIVER POWER SUPPLIES. WORK ON THE RECEIVER SHOULD NOT BE ATTEMPTED BY ANYONE WHO IS NOT THOROUGHLY FAMILIAR WITH THE PRECAUTIONS NECESSARY WHEN WORKING ON HIGH-VOLTAGE EQUIPMENT.

Tube Complement


Symbol	Type	Function
V1	6BZ7	RF Amplifier
V2	6N8	Mixer and Oscillator
V3	6AF4	UHF Oscillator
V4	6CB6	1st IF
V5	6BC6	2nd IF
V6	6BC6	3rd IF
V7	6CB6	4th IF
V8	6CL6	5th IF
V9	6AU6	Sound IF Amplifier
V10	6AU6	Driver
V11	6AL5	Ratio Detector
V12	6AU6	Audio Amplifier
V13	6AQ5	Audio Output
V14	6CL5	1st Video Amplifier
V15	6AN8	2nd Video Amplifier—Q Phase Splitter
V16	6AN8	Band Pass Amp.—Color Killer
V17	6CB6	Burst Amplifier
V18	6AL5	Phase Det.
V19	6AN8	Reactance Tube—3.58 mc Oscillator
V20	12AT7	Horizontal Phase Splitter
V21	6AN8	1 Amplifier—AGC Clamp
V22	6BY6	Q Demodulator
V23	6BY6	I Demodulator
V24	6AN8	I Amplifier—I Phase Splitter
V25	12BH7	Green Adder—Green Output
V26	12BH7	Blue Adder—Blue Output
V27	12BH7	Red Adder—Red Output
V28	6BC7	Green Red Blue DC Restorers
V29	6AN8	AGC Amp—Horiz. Sync Separator
V31	12AT7	Vert. Sync Separator—Sync Clipper
V32	6BL7	Vert. Oscillator—Vert. Output
V33	6AL5	Horizontal Phase Det.
V34	12AU7	Horizontal Oscillator
V35	6CU6	Horizontal Output
V36	6AU4	Damper
V37	3A3	HV Rectifier
V38	3A3	HV Rectifier
V39	3A3	HV Rectifier
V40	6BD4	HV Regulator
V41	6BL7	Convergence sawtooth Gen-Blue conv. Output
V42	6BL7	Green conv. Output—Conv. Cathode Follower
V43	6BL7	Pulse Shaper—Red. Conv. Output
V44	19VP22	Colorton CRT
V46	6CU6	Horizontal Output

Specifications

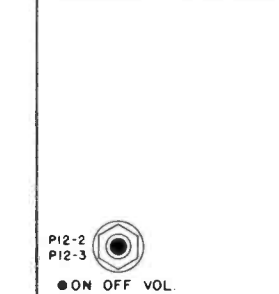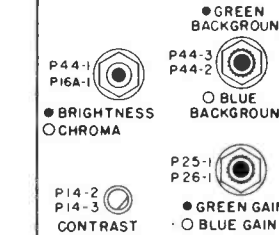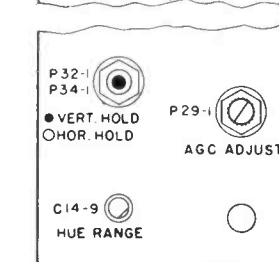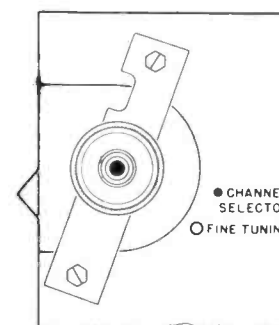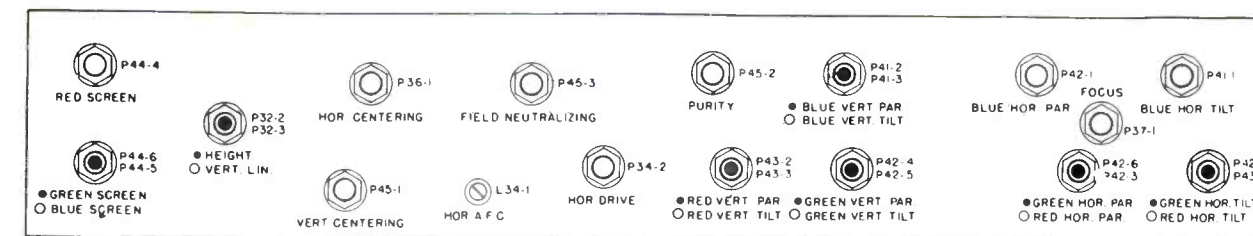

Signal chass front controls.

Deflection chass front controls.

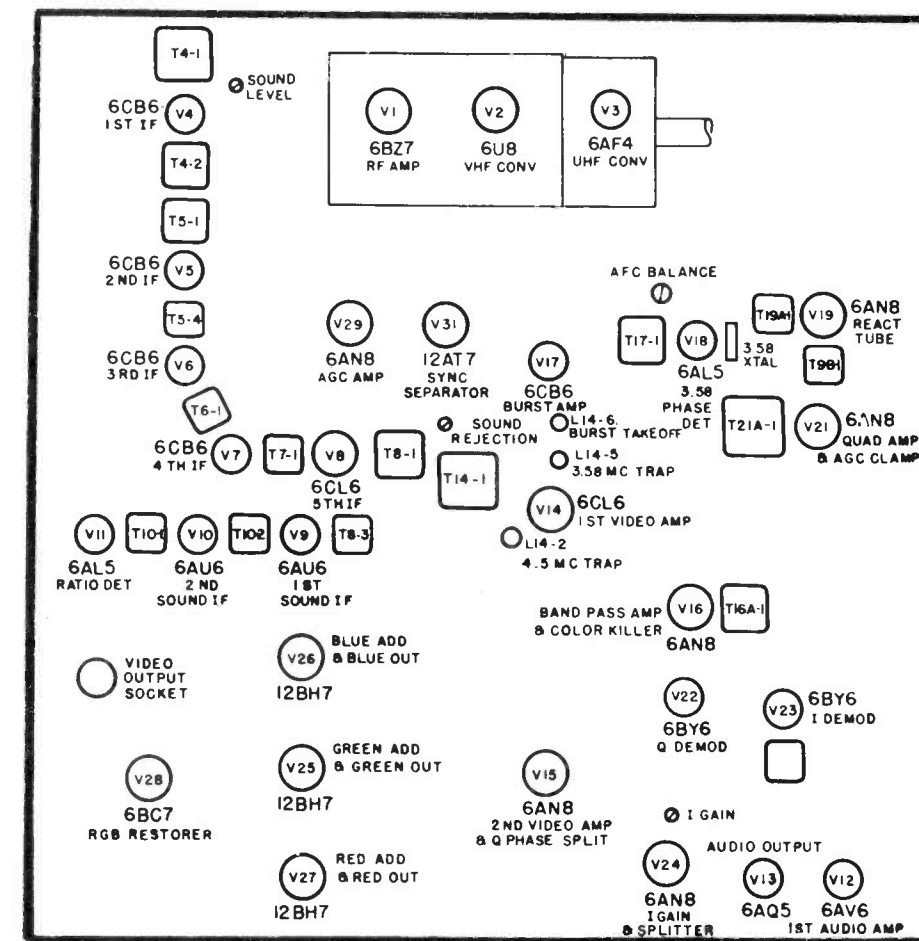

Top view of signal chass



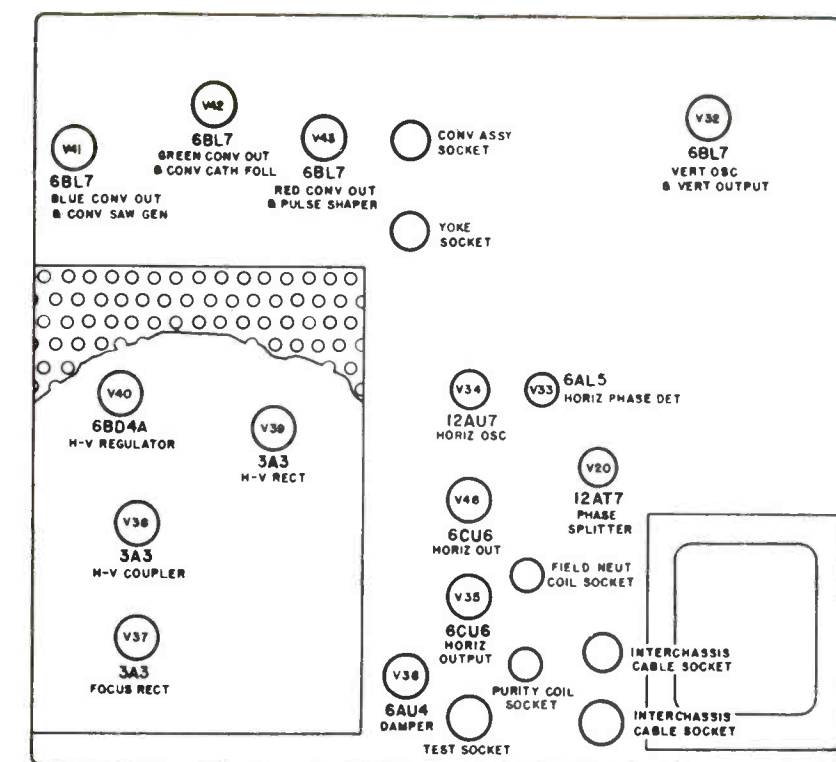


Fig. 9—Top view of deflection chass

UHF Tuner

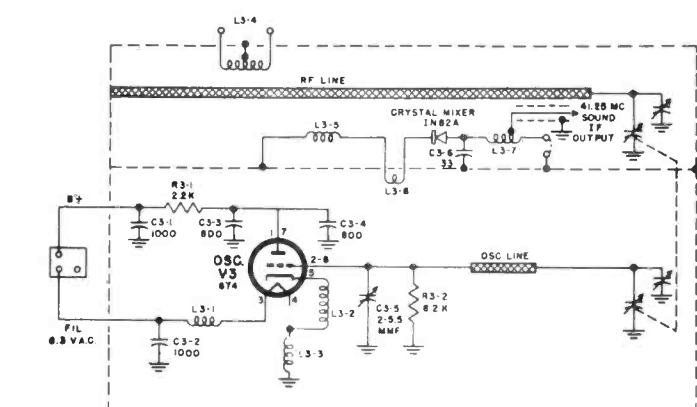

VHF Tuner

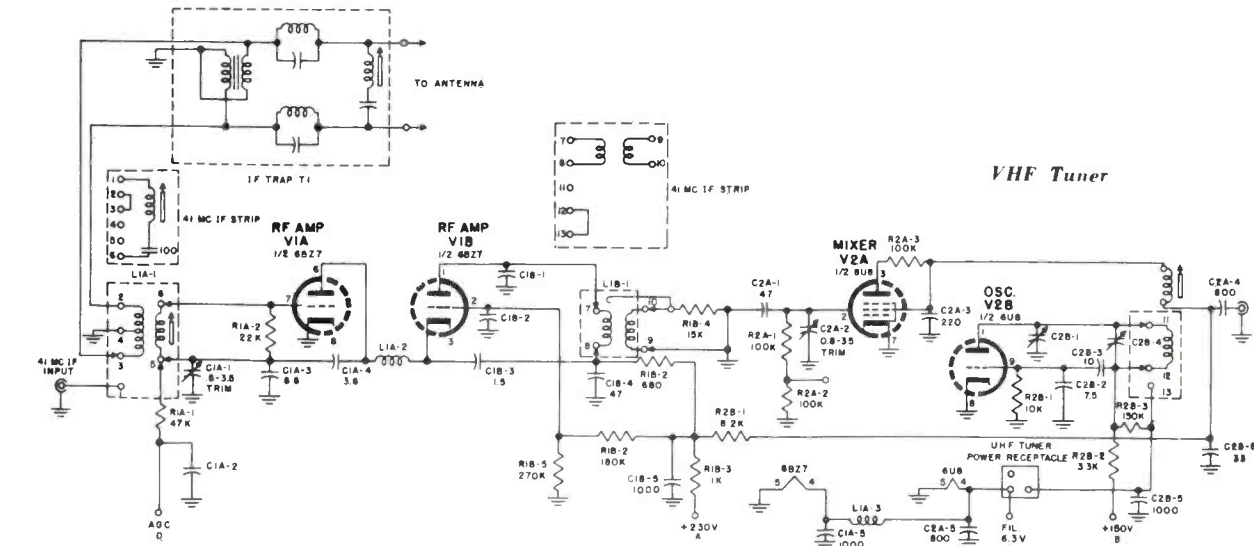

PRECISION



Announces a **NEW**
BASIC TEST INSTRUMENT

...for Laboratory and Test Bench
...for Engineer and Technician

THE MODEL

E-300

SINE-SQUARE WAVE SIGNAL GENERATOR

(AUDIO-VIDEO RANGE)

GENERAL SPECIFICATIONS:

- ★ **VARIABLE-FREQUENCY SINE-WAVE RANGES:**
for testing audio amplifiers, low frequency RF amplifiers, etc.:
Continuous Coverage from 20 Cycles to 200 Kilocycles in Four Bands.
- ★ **VARIABLE FREQUENCY SQUARE-WAVE RANGES:**
for analyzing audio amplifiers, wide-range amplifiers, etc.:
20 Cycles through 20,000 Cycles in Three Bands.
- ★ **FOUR FIXED, HIGH-FREQUENCY SQUARE WAVES:**
for analysis of video and other wide-band amplifiers up to 20MC band-width:
50 KC — 100 KC — 250 KC — 500 KC steps.
- ★ **OUTPUT CHARACTERISTICS:**
Variable Frequency Ranges: 0-2000 ohms, 0-10 volts RMS, flat within ± 1 db.
Accuracy: $\pm 2\%$ from 50 cps. to 200 KC. ± 1 cps. from 20 cps. to 50 cps.
Distortion: Less than 1% from 20 cycles through 200 KC.
20 KC Square-Wave Rise Time: .5 microseconds.
Fixed High Frequency Square-Waves: 0-250 ohms, 0-5 volts P-P
Rise Time: .05 microsecond • Overshoot: Negligible
- ★ **TUBE COMPLEMENT:** 1-5879, 1-6CL6, 1-6J6, 2-6AU6, 1-6BL7, 1-6AH6, 1-6X4.
- ★ **SEPARATE OUTPUT CIRCUITS:** for the variable and fixed frequency ranges. Dual pilot lamps automatically indicate the active output jacks.
- ★ **TERMINATED, LOW-LOSS, HIGH FREQUENCY COAXIAL OUTPUT CABLE:**
transmits the H.F. square waves to circuits under test, without distortion.
- ★ **EXTERNAL 'SYNC' TERMINAL POST:**
for synchronizing oscillograph horizontal sweep to H.F. square-wave.
- ★ **ETCHED-ANODIZED TUNING DIAL and PANEL:** NO-glare, engine-turned dial finish and soft-black panel field afford utmost visibility and ease of reading.

MODEL E-300: in black, ripple finished, portable steel case — 10½x12x6".
Complete with tubes, coaxial output cable and operating manual.

Net Price \$175⁰⁰

THE NEW SERIES E-300 has been especially developed to answer many modern electronic amplifier testing problems which cannot be handled with just the usual complement of test instruments.

The Series E-300 provides accurate sine and square wave signals for direct performance testing of:

High Fidelity Audio Amplifiers

TV Video Amplifiers

Carrier Current Systems

... and other wide range devices, etc.

Sine-Square Wave Analysis, with the Series E-300, streamlines amplifier test procedure and assures more uniformly high standards of apparatus performance, because sine-square wave testing is a most reliable indicator of:

Frequency Response

Phase Shift

Amplitude Distortion, etc.

The operating Manual for the Series E-300 has been especially prepared to describe the basic techniques of sine-square wave testing. The information establishes a foundation that will permit the operator to interpret sine-square wave-forms in terms of frequency response, distortion, etc.


You may obtain this comprehensive Manual, at only 25¢ per copy, to cover cost of printing and handling. Write directly to factory.

EXPORT DIVISION: MORHAN EXPORTING CORP.
458 Broadway, New York 13, U.S.A.
IN CANADA: ATLAS RADIO CORP.
560 King Street W., Toronto 2B



PRECISION Apparatus Company, Inc.

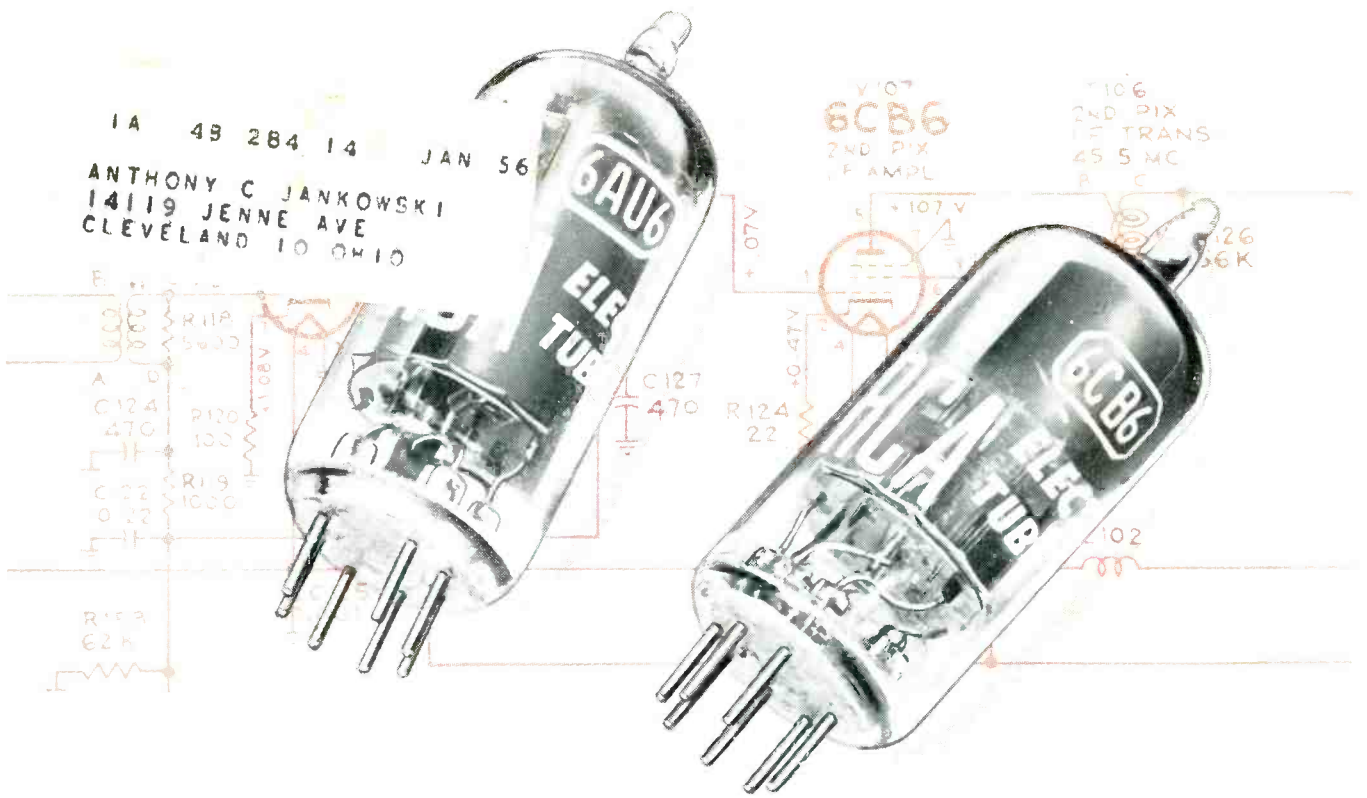70-31 84th Street, Glendale 27, L. I., N. Y.



SAVE TIME IN REPAIRING TV IF CIRCUITS!

Use RCA Tubes with built-in quality!



HERE'S WHY . . . Strict quality control in manufacturing RCA Tubes assures consistent uniformity of characteristics. For example, careful control of transconductance, plate-current cutoff, and tube capacitances in RCA Tubes for TV IF Circuits is your assurance of quick servicing without quality difficulties.

In circuits so vital to the production of sharp pictures and strong signals—be sure, use RCA Tubes!



RADIO CORPORATION of AMERICA
ELECTRON TUBES
HARRISON, N. J.

Your First Choice for TV circuits . . . dependable RCA Tubes.