

Over 40 Electronics Projects You Can Make

RADIO-TV Experimenter

Published by
SCIENCE and
MECHANICS
Magazine

75c

No. 555



Sun-Powered
Receiver


**WHITE'S
RADIO
LOG**



2000 Changes · New, Up-to-Date
Directory of North American
AM-FM-TV STATIONS
WORLD-WIDE SHORT WAVE



Radio
Remote Controls

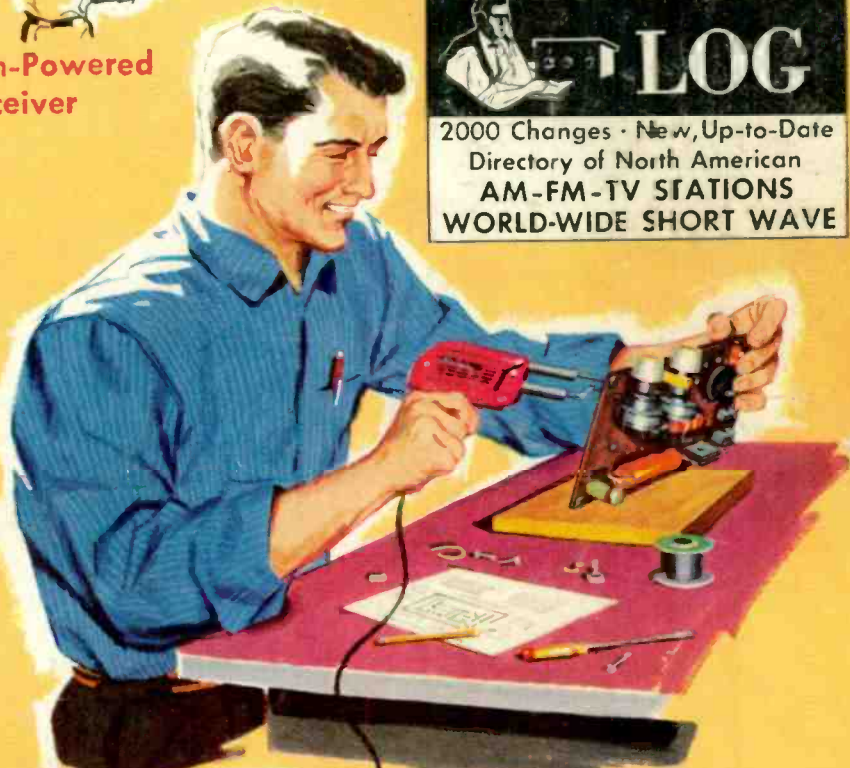

LOCHER



Mystery
Capacity Control

Plans for
Hi-Fi Cabinet
Plus How to Add
Stereo Sound



Printed Circuit Phono Amp


New, Ultra-Small Wrist Radio
6-Meter Radiotelephone Station
Applause Meter · Hi-Fi Mixer
Red Hot Transistor Receiver
Bull's Eye Game · Global DX
Capacitor Checker · Reflex Radio

WE'RE MAKING IT EASIER THAN EVER TO BECOME A WELL PAID
RADIO-TELEVISION SERVICE TECHNICIAN

NOW - Just \$6 Starts You Training in
RADIO-TELEVISION

the **SPRAYBERRY** "Learn-by-Doing" Way . . .

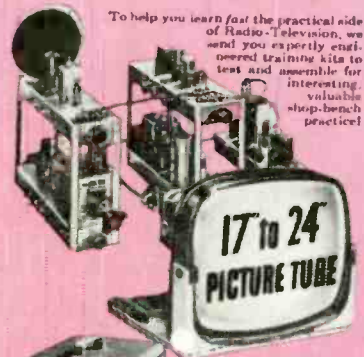
25 BIG, COMPLETE KITS
of PARTS & EQUIPMENT



To help you learn fast the practical side of Radio-Television, we send you expertly engineered training kits to test and assemble for interesting, valuable shop-bench practice.



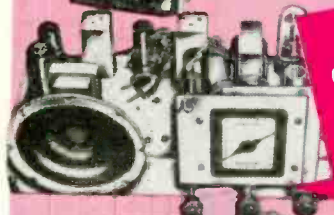- The new Sprayberry Training Television Receiver, built and tested in 5 sections.
- Now offered... this fine modern oscilloscope.
- You build this powerful two-band superheterodyne radio receiver.



Big New CATALOG AND Sample Lesson FREE!



You build the new Sprayberry tester—a complete 18 range Volt-Ohm-Milli amp meter test meter.



*** This great industry is begging for trained men . . . to step into good paying jobs or a profitable business of their own! Our new plan opens the doors of Radio-Television wide to every ambitious man who is ready to act at once!

Men by the thousands . . . trained Radio-Television Service Technicians . . . are needed at once! Perhaps you've thought about entering this interesting, top paying field, but lack of ready money held you back. Now — just \$6 enrolls you for America's finest, most up to date home study training in Radio-Television! Unbelievable? No, the explanation is simple! We believe Radio-Television *must* have the additional men it needs as quickly as possible. We are willing to do our part by making Sprayberry Training available for less money down and on easier terms than ever before. This is your big opportunity to get the training you need . . . to step into a fine job or your own Radio-Television Service Business.

Complete Facts Free — Act Now; Offer Limited

Only a limited number of students may be accepted on this liberal and unusual basis. We urge you to act at once . . . mail the coupon below and get complete details plus our big new catalog and an actual sample lesson—all free. No obligation . . . no salesman will bother you.

HOME STUDY TRAINING IN SPARE TIME

Under world-famous 27-year old Sprayberry Plan, you learn entirely at home in spare time. You keep on with your present job and income. You train as fast or as slowly as you wish. You get valuable kits of parts and equipment for priceless shop-bench practice. And everything you receive, lessons and equipment alike, is all yours to keep.

LET US PROVE HOW EASILY YOU CAN LEARN!

Radio-Television needs YOU! And Sprayberry is ready to train you on better, easier terms, than any ambitious man can afford. *Just \$6 starts you!* Mail coupon today . . . let the facts speak for themselves. You have everything to gain. Let us prove the kind of opportunity in store for you!

SPRAYBERRY Academy of Radio-Television
 1512 Jarvis Avenue, Dept. 212-L, Chicago 26, Illinois

Mail This Coupon Now—No Salesman Will Call

Sprayberry Academy of Radio-Television
 Dept. 212-L, 1512 W. Jarvis Ave., Chicago 26, Ill.

Please rush all information on your ALL-NEW Radio-Television Training Plan. I understand this does not obligate me and that no salesman will call upon me. Include New Catalog and Sample Lesson FREE.

NAME _____ Age _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

RADIO-TV Experimenter.....VOLUME SIX

CONTENTS

Red Hot Transistorized Receiver.....	25	Components Cabinet	119
Component Color Code Standards.....	29	How to Add Stereo to Hi-Fi for \$35.....	120
Transistorized Fire Alarms.....	30	Magic-Eye Capacitor Checker.....	123
Listening with a Transducer.....	33	Dressing Up Old Radios.....	128
Transistorized Amplifiers.....	34	What Stereophonic Sound Is All About.....	130
Tele-Tenna Beamer.....	37	Mazda Lamp Resistors.....	135
Pocket Reflex Superhet.....	39	Tie-Rack Radio.....	137
Two-Channel Mixer.....	44	Electric Etcher.....	140
Potentiometer for the Electronics Lab.....	48	Battery Eliminator for Transistor Radios.....	141
Tracking American Satellites.....	50	Applause Meter.....	146
Workbench Chassis Turntable.....	71	Phone Jack for Radio or TV.....	150
Testing Coils for Shorts.....	77	Electronic Bull's Eye Game.....	152
Telephone Conversation Amplifier.....	78	Heavy-Duty Soldering Pot.....	156
Economy Record Player.....	80	World-Wide DX.....	159
Transistorized Hi-Fi Preamplifier.....	83		
Armchair Speaker Control.....	87		
Air-Powered Tuner.....	89		
Adjustable Stand for Bedside TV.....	91		
Shelf Amplifier Systems.....	92		
Automatic Tape Recorder Stop.....	95		
Six-Meter Radiotelephone Station.....	98		
Ultra-Small Wrist Radio.....	108		
Student's Special SW Receiver.....	111		
Electronic Timer.....	115		
Simple Phono Amps.....	117		

ILLUSTRATED ON COVER

Printed Circuit Phono Amplifier..	21
Radio Remote Controls.....	54
Silicon Solar Cell Radio.....	67
Hi-Fi Speaker Cabinet.....	72
Mystery Capacity Control.....	143
WHITE'S RADIO LOG	161

Cover by Dick Locher

Curt Johnson, Handbook Editor
Herb Siegel, Assistant Editor, Handbooks
Bill Wadkins, Assistant Art Director, for Handbooks
Thomas A. Blanchard, Radio-TV Editor

Published and Copyrighted 1958 by

SCIENCE AND MECHANICS PUBLISHING COMPANY

450 East Ohio Street

Chicago 11, Illinois


The Radio-TV Experimenter contains a selection of the most popular electronics projects and radio and TV maintenance articles that have appeared in *Science and Mechanics Magazine*, plus a number of projects and helpful articles on the same subjects appearing for the first time.

Science and Mechanics Handbook Annual No. 5, 1958—No. 555

Editorial Board

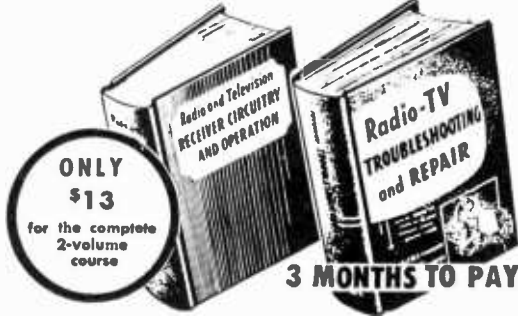V. D. ANGERMAN
Editor and Publisher
DON DINWIDDIE
Managing Editor
ART YOUNGQUIST
Home Workshop Editor
RAY WHITMAN
Feature Editor
P. D. URBAIN
Associate Editor
LILLIAN ANDERSEN
Associate Editor
RAY S. LINDENMEYER
Technical Editor
F. M. EISENZOPH
Art Director
CHUCK BACHTELL
Assistant Art Director

Complete Training FOR BETTER RADIO-TV SERVICE JOBS



Let these two great Ghirardi training books teach you to handle all types of AM, FM and TV service jobs by approved professional methods—and watch your efficiency and earnings soar!

Each book is a complete service training guide. Each contains complete data on modern methods and equipment—not a re-hash of old, out-of-date material. Each is co-authored by A. A. Ghirardi whose famous RADIO PHYSICS COURSE and MODERN RADIO SERVICING were, for 20 years, more widely used for military, school and home study training than any other books of their type!

THE NEW Ghirardi RADIO-TV SERVICE LIBRARY

Almost 1500 pages and over 800 clear illustrations show step-by-step how to handle every phase of troubleshooting and servicing.

1—Radio and Television Receiver TROUBLESHOOTING AND REPAIR

A complete guide to profitable professional methods. For the beginner, it is a comprehensive training course. For the experienced serviceman, it is a quick way to "brush up" on specific jobs, to develop improved techniques or to find fast answers to puzzling service problems. Includes invaluable "step-by-step" service charts, 820 pages, 417 illus., price \$7.50 separately.

2—Radio and Television Receiver CIRCUITRY AND OPERATION

This 680-page volume is the ideal guide for servicemen who realize it pays to know what really makes modern radio-TV receivers "tick" and why. Gives a complete understanding of basic circuits and circuit variations; how to recognize them at a glance; how to eliminate guesswork and useless testing in servicing them. 417 illus. Price separately \$6.75.

Special low price . . . you save \$1.25

If broken into lesson form and sent to you as a "course," you'd regard these two great books as a bargain at \$50 or more! Under this new offer, you save \$1.25 on the price of the two books—and have the privilege of paying in easy installments while you use them! No lessons to wait for. You learn fast—and right!

STUDY 10 DAYS FREE!

Dept. MM-6, RINEHART & CO., Inc.
232 Madison Ave., New York 16, N. Y.

Send books below for 10-day FREE EXAMINATION. In 10 days I will either remit price indicated (plus postage) or return books postpaid and owe you nothing.

Radio & TV Receiver TROUBLESHOOTING & REPAIR (Price \$7.50 separately)

Radio & TV CIRCUITRY & OPERATION (Price \$6.75)

Check here for MONEY-SAVING COMBINATION OFFER . . . Save \$1.25. Send both of above big books at special price of only \$13.00 for the two. (Regular price \$14.25 . . . you save \$1.25.) Payable at rate of \$4 plus postage after 10 days if you decide to keep books and \$3 a month for 3 months until the total of \$13.00 has been paid.

Name

Address

City, Zone, State

Outside U.S.A.—\$8.00 for TROUBLESHOOTING & REPAIR; \$7.25 for CIRCUITRY & OPERATION; \$14.00 for both. Cash only, but money refunded if you return books in 10 days.

TEST AND DESIGN TRANSISTORIZED CIRCUITS . . . EASIER . . . FASTER!

WITH THE SECO PS-2 BATTERY ELIMINATOR

Perfect for testing and servicing any low power transistorized equipment—takes place of battery! Supplies clean, filtered DC. Output is continuously variable from 0 to 15 volts. Ideal for designing transistorized circuits to select optimum performance with least current drain! Can't be damaged by a short circuit.

MODEL PS-2 Complete with jacks, leads, clips. \$13.95

Write for free literature today



SECO MANUFACTURING CO.
5015 Peim Ave. So., Minneapolis, Minn.

Prepare for a

SECURE FUTURE

as a technician with Guided
Missiles, Computers, Aircraft, Radar

Complete training requires just
a little over a year

Course approved by Board of
Education and Veterans Administration

Write for full information

BROWN INSTITUTE OF ELECTRONICS

3127 East Lake Street
MINNEAPOLIS 6, MINNESOTA

Lafayette Radio

1959 CATALOG

The Complete Catalog Featuring
"The Best Buys In The Business"

Send for Lafayette's 1959 Catalog—the most complete, up-to-the-minute electronic supply catalog crammed full of everything in electronics at our customary down-to-earth money-saving prices.

Depend on LAFAYETTE for all of your needs . . . complete stocks—immediate shipment—personal technical assistance—proven dependability.



DEPT
EX-6

P. O. BOX 511
JAMAICA 31, N. Y.

Send FREE LAFAYETTE Catalog 590

Name

Address

City..... Zone.... State.....


These men are getting practical training in . . .

ELECTRICITY

ELECTRONICS

ON REAL

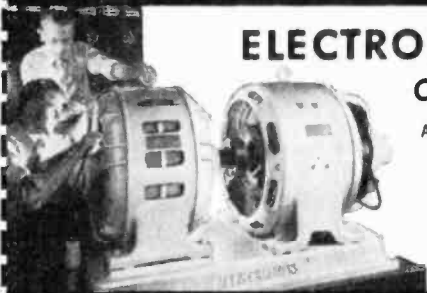A.C. and D.C. Motors
Generators
Switchboards
Controllers
Appliances
Electronic Units




TELEVISION

COLOR-TV

ON REAL

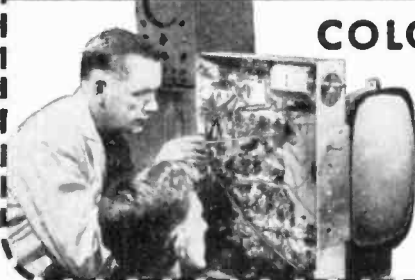Television
Receivers
Including Color TV
AM and FM Radios
Auto Radios
Test Equipment



Train in Great Shops of COYNE

in Chicago—Prepare for a better job and a real future in **TOP OPPORTUNITY FIELDS**. Train on real full-size equipment at **COYNE** where thousands of successful men have trained for nearly 60 years—*largest, oldest, best equipped school of its kind*—est. 1899. Trained instructors show you how, then do practical jobs yourself. No previous experience or advanced education needed. **Employment Service to Graduates**. **START NOW—PAY LATER**—Liberal Finance and Payment Plans. Part-time employment help for students. **GET FREE BOOK**—"Guideto Careers in **ELECTRICITY -ELECTRONICS and TELEVISION-RADIO**"—no obligation; no salesman will call. Vets and Non-Vets get vital facts now.

Coyne Electrical School 500 So. Paulina Street
Chartered Not For Profit Chicago 12, Dept. 78-9C



MAIL COUPON TODAY!

COYNE ELECTRICAL SCHOOL
500 S. Paulina St., Chicago 12, Ill., Dept. 78-9C

Send **BIG FREE** book and details of your training offer by return mail. I am interested in:

Electricity-Electronics Television-Radio

Name _____


Address _____

City _____ State _____

COYNE offers
LOW COST

TELEVISION RADIO - COLOR TV

Training in
Spare Time **AT HOME**

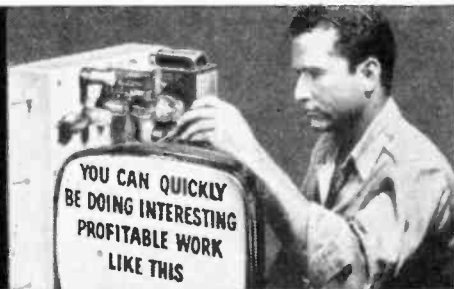

The future is **YOURS** in **TELEVISION!**
A fabulous field—good pay—fascinating work—a prosperous future in a good job, or independence in your own business!

Coyne brings you **MODERN-QUALITY** Television Home Training; training designed to meet Coyne standards at truly lowest cost —you pay for training only—*no costly "put together kits."* Not an old Radio Course with Television "tacked on." Here is **MODERN TELEVISION TRAINING** including **Radio, UHF and Color TV**. No Radio background or previous experience needed. Personal guidance by Coyne Staff. **Practical Job Guides** to show you how to do actual servicing jobs—*make money early in course*. Free Lifetime Employment Service to Graduates.

COYNE
ELECTRICAL SCHOOL
A TECHNICAL TRADE INSTITUTE OPERATED
NOT FOR PROFIT
500 S. Paulina Street, Chicago 12, Dept. 78-H9

B. W. COOKE, JR.
President



Coyne—the Institution behind this training . . . the largest, oldest, best equipped residential school of its kind. Founded 1899.

Send Coupon for Free Book

and full details,
including easy
Payment Plan.
**No obligation, no
salesman will call.**



COYNE Television
Home Training Division
500 S. Paulina St., Chicago 12, Ill.
Dept. 78-H9

Send Free Book and details on how I can get Coyne Quality Television Home Training at low cost and easy terms.

Name _____


Address _____

City _____ State _____

Shipped on... approval

**SEND NO MONEY —
NO C.O.D.**

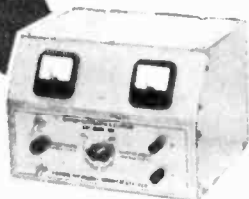
Try them for 10 days at no risk!
Examine first, and then only if completely
satisfied, pay lowest prices for
highest quality units, in easy
monthly installments.



MODEL 905 BATTERY ELIMINATOR and CHARGER

Continuously variable voltage output. Automatic overload relay self-resetting. Either 6 or 12 volt operation. Heavy duty rectifier. Continuous operation 6V. at 10A. or 12V. at 6A. Intermittent operation 6V. at 20A. or 12V. at 12A.

Model 905 (Wired) \$37.50

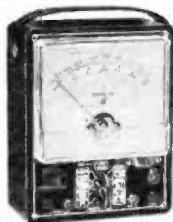

VOLOMETER, Model 104.

This 20,000 Ohms per volt instrument is the lowest priced, domestic made, unit of its kind in today's market. Uses large 4½" D'Arsonval, 50 mi-

croampere meter, accurate to 2%. Housed in polished, high impact, bakelite case . . . uses a durable, etched aluminum panel. 3 AC Current Ranges. Checks resistance accurately in 3 ranges to 20 megohms. 5 DC and AC Ranges to 3000 volts. 5 DB Ranges. Model 104 (wired) \$26.95 Net



MODEL 204 P TUBE-BATTERY-OHM CAPACITY TESTER

An Emission Tube Tester, with a completely flexible switching arrangement. Test all tubes. Checks batteries under rated load on "reject-good" scale. Uses 25W line voltage control. Checks condenser leakage to 1 meg. Checks resistance up to 4 megs. Checks capacity from .01 to 1 mfd.

Model 204P (illustrated) \$55.90

Cathode Ray Tube Adaptor available..... \$ 4.50

**MAIL THIS
COUPON
TODAY! NO
OBLIGATION
TO BUY—YOU
MUST BE
SATISFIED!**

TESTMASTER, INC.

Dept.
EX-8

192 Mercer Street, New York 12, N. Y.

Please send me for approval the units checked.
If completely satisfied, I will pay on terms specified,
with no interest or finance charges. Otherwise,
I will return after a 10 day trial, positively
cancelling all obligations.

Name _____

Address _____

City _____ Zone _____ State _____

All prices net, F.O.B. N. Y. C.

MODEL 905
Total Price \$37.50
\$11.50 within 10 days.
Balance \$6.50 for 4 mos.

MODEL 204 P
Total Price \$55.90
\$15.90 within 10 days.
Balance \$8.00 for 5 mos.

MODEL 104
Total Price \$26.95
\$6.95 within 10 days.
Balance \$5.00 for 4 mos.

Men 17 to 55 - GET FREE FACTS!

See How **DeVry Tech** Can Prepare You For A Profitable Future In Many Fields


from **Communications** to **Guided Missiles, etc.**



No Previous Technical Experience Or Advanced Education Needed!

Laborers and bookkeepers, store clerks, shop men, farmers, salesmen - men of nearly every calling - have taken the DeVry Tech program and today have good jobs or service shops of their own in Electronics. You don't have to quit your present job. If you are 17 to 55, see how you may get yourself ready for a future in the fast-growing Electronics field.

Whether you prepare at home or in our well-equipped Chicago or Toronto Laboratories, you get sound, basic training in both principles and practice. At home, you use educational movies. You build actual circuits and test equipment. You read simple directions, follow clear illustrations. When you finish, you are prepared to step into a good job in this excitingly different field. You may even start a service shop of your own. Mail coupon for free facts today.

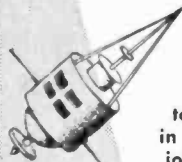

FREE EMPLOYMENT SERVICE

Puts you in touch with job opportunities - or helps you forward a better position in the plant where you are now employed.


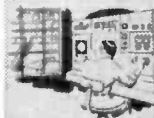
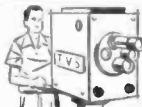




Draft Age?

We have valuable information for every man of draft age; so if you are subject to military service, be sure to check the coupon.

Get **FREE** Booklet!

We'll give you a free copy of an interesting booklet, "Electronics and YOU." See for yourself how you may take advantage of the opportunities in this fast-growing field.



	Radar
	Automation Electronics
	Television
	Micro-Waves
	Computers
	Broadcasting
	Your Own Service Shop

DeVry Technical INSTITUTE

Chicago 41, Illinois
Formerly DeFOREST'S TRAINING, INC.

"One of North America's Foremost Electronics Training Centers"
Accredited Member of National Home Study Council



DeVry Technical Institute
4141 Belmont Ave., Chicago 41, Ill., Dept. TV-X-0
Please give me your FREE booklet, "Electronics and YOU," and tell me how I may prepare to enter one or more branches of Electronics as listed above.

Name _____ Age _____
Street _____ Please Print _____ Apt. _____
City _____ Zone _____ State _____

Check here if subject to Military Training.

DeVry Tech's Canadian Training Center is located at 626 Roselawn Avenue, Toronto 12, Ontario


2040

NOW **2** ASSEMBLE-IT-YOURSELF


Schober ELECTRONIC ORGANS

**SAVE HALF
NO SPECIAL SKILLS
PAY KIT-BY-KIT**

Now you can afford an electronic organ. Whether you choose the full Concert model or the smaller Consolette, you have an organ equal to any made by the foremost manufacturers. In addition, you save over 1/2 the cost because you assemble it yourself...and you enjoy the thrill of achievement. Too, you purchase each kit only when you are ready for it.



2 different MODELS
2 different SIZES
2 different PRICES



**CONCERT
MODEL**

- ☆ TWO FULL SIZE PIPE-ORGAN MANUALS, 122 KEYS
- ☆ OCCUPIES 3'5" x 4'7" FLOOR SPACE
- ☆ 26 STOPS AND COUPLERS
- ☆ 32 BASS PEDALS
- ☆ ASSEMBLED CONSOLE
- ☆ CONFORMS TO AMERICAN GUILD OF ORGANISTS SPECIFICATIONS FOR PIPE ORGANS
- ☆ COMPLETE STEP-BY-STEP INSTRUCTIONS

**CONSOLETTE
MODEL**

- ☆ OCCUPIES ONLY 2' x 3'2" FLOOR SPACE
- ☆ TWO FULL SIZE PIPE-ORGAN MANUALS, 122 KEYS
- ☆ 22 STOPS — ABOVE-KEYBOARD TABS
- ☆ 13 HEEL-AND-TOE BASS PEDALS
- ☆ 7 FULL OCTAVES OF TONE (DOWN TO 32 CPS)
- ☆ BUILT-IN SPEAKERS OPTIONAL
- ☆ ASSEMBLED CONSOLE
- ☆ COMPLETE STEP-BY-STEP INSTRUCTIONS

**10" LP RECORD DEMONSTRATING BOTH MODELS
AVAILABLE FOR \$2, REFUNDABLE UPON PURCHASE**

FREE NEW 1959 EDITION OF 16 PAGE ILLUSTRATED BOOKLET ON REQUEST

Write Now — See What Fine Instruments You Get At Such Great Savings

The SCHOBER ORGAN Corporation • 2248-U BROADWAY • NEW YORK 24, N. Y.

SCHOBER KITS ALL OVER THE WORLD

☆ Designed by Richard H. Dorf.

DIAMONDS • PEARLS • RUBIES • JADE • EMERALDS • SAPPHIRES

ROCKHOUNDS! It's finally available again! A comprehensive guide to North American gem locations—Plus 81 detailed maps pinpointing rich and secluded native gemstone sites—plus full-color, natural-size photos of 53 different gem varieties shown as they occur in nature—Plus a detailed text explaining hunting methods, field testing and identification techniques and special chapters devoted to the most valuable gems—ALL in Russell P. MacFall's completely revised, newly printed **GEM HUNTER'S GUIDE**. To get your copy, send \$3.95 to Science and Mechanics, Dept. 5555, 450 East Ohio Street, Chicago 11, Illinois. Money-back guarantee. *No C.O.D.'s or stamps, please.*

OPALS • AMETHYST • TOPAZ • LAPIS LAZULI • ONYX • BERYL



ELECTRONICS-TV SCHOOL

Midwest's First & Foremost

(Our 28th Year Exclusively Electronics)

10-MONTH RESIDENT SHORT-COURSE

Special 10 in 1 training embraces Electronics; Radio, TV & Color TV Servicing; Communications; Radar; Microwave; Synchros, Servomechanisms & Industrial Electronics. Wide job opportunities & placement. Small school with big reputation. Personalized training; competent instructors. Not Approved.

UNIVERSAL TV-ELECTRONICS SCHOOL

318-A East 10th St. Kansas City 6, Mo.

Name..... Age.....

Address.....

City..... State.....

Veterans give discharge date.....

RADIO CONTROL Headquarters

For Models. FREE, Send for FCC Form 505 & Catalog "X"

R/C RECEIVER 27 1/4 Mc. Compl. w. Relay, **\$8.61**

R/C XMITTER Hi-Power HAND-HELD, compl., 17.95; KIT 11.95

R/C TRANSMITTER & RECEIVER KIT: 27 1/4 Mc. 5 watt 2-Tube

Simple Transm. & 2-Tube Rec. incl. drilled Bases, **9.95**

Wound Coil, Res., Cond., SIGMA Relay, Instruct. **9.95**

HANDIE-TALKIE Transmitter & Rec., Chassis, New, **6.65**

Wired, w. Tube, 2 Triodes **6.65**

SIGMA 4F RELAY: 8,000 ohm, \$4.25; 6 Reed Relay 14.95

2-6V Battery Charger Kit \$4.95; Wired **6.95**

Storage Battery: 8B54-A, 3Volt, 27 Amp/hr **4.25**

Crystals: 27.255 Mc. \$2.85; Holder **.15**

2" Meters D-1Ma \$3.65; 500 MicroA \$3.95; 3Ma **2.95**

DYNAMOTORS: 12V/235V @ 75Ma **2.95**

6V 150V @ 100Ma \$6.95; 5V 300V, 100Ma **9.95**

R/C BOOKS: Model Con. \$1; Radio Con. \$1; Handbook **2.25**

RELAY CONTROL UNIT incl. Sensitive 10,000 ohm Sig-

ma Relay (2 1/2Ma) Thermal Bi-

Metal Strip. Heating Element, Hi-Z Audio Choke, Mini Air-

nico V Magnet, Neon Lamp, Resistors, Capacitors, only **99c**

TUBES: XFG1, RK61, 3A4, 3A5, 1AG4, 6K4...Transistors **.99**

Relays: 10K ohm, 2Ma DC or 110V AS SPDT 95c; SPST .85

Flashing STROBOSCOPE "Stops" or "Slows" motion of

any machine, adj. 900 to 14,000 per min., alum. **\$19.85**

GYRO ELECTRONICS CO. 325-X CANAL ST. NEW YORK 13, N. Y.

NOW READY! McGraw-Hill's New Train-Yourself Course

TELEVISION AND
RADIO REPAIRING

REPAIRING
RECORD CHANGERS

PROFITABLE RADIO
TROUBLESHOOTING

PRACTICAL RADIO
SERVICING

PROFITABLE
TELEVISION
TROUBLESHOOTING

6 BIG VOLUMES
Including
Home Course
Outline!
Shows how
to Get
Ahead Fast.

FIX TV RADIO and RIGHT AWAY RECORD CHANGERS

— even if you've never looked inside a set before!



BE YOUR OWN BOSS!

AT LAST — at Amazing LOW COST — The Most Complete TV-Radio Repair Course Ever Published. TELLS and SHOWS How to Do Every Job Quickly and Easily — Make GOOD MONEY, Full or Spare Time in the BOOMING Repair Business

AFTER 10 YEARS OF PREPARATION — McGraw-Hill's new 6-Volume Course brings you everything you need to know to "cash in" on the TV-RADIO boom. Over 2,350 pages of money-making "know-how" by top factory engineers and electronic experts. **THREE** giant REPAIR MANUALS tell and show how to FIX every trouble the easy way. **TWO** huge TROUBLESHOOTERS tell exactly WHERE to begin, WHAT tools to use, HOW to "polish off" every job. Complete Home Study Volume guides you every step of the way, tells how to get ahead fast as a repairman — build up your own business, full or spare time, for **BIG PROFITS!**

EARN While You Learn

Tested — and now used in top schools, and repair shops — Course volumes are simple enough for green beginners, amazed "pros" with new easy methods. Starts you doing simple repairs — and earning money — from very first chapter. ABC pictures and directions make tougher jobs a "snap." Before you finish you can earn many times its cost.

NO previous training needed. NO complicated formulas. **PLAIN ENGLISH**

pictures and directions cover ANY job on EVERY set — tubes, circuits, speakers, new a-c/d-c portables, Color TV, even what to charge for every job!

BIG MONEY — Spare or Full Time

Forget lack of experience. Forget your age. Over 40 MILLION TV sets, 130 MILLION radios — and the shortage of repairmen — mean big money for you. Course makes it easy to "cash in," spare time or full, start your own business, enjoy your work and a big bank account!

SEND NO MONEY

Try Course 10 days FREE. (We pay shipping!) If you don't agree it can get

you started in a money-making repair business — return it, pay nothing. Otherwise keep it. Earn while you learn; and pay the low cost on easy terms. Mail coupon NOW.

McGraw-Hill Book Co., Dept. S&M-E-A
327 West 41st St.,
New York 36, N. Y.

Examine
Entire Course
FREE
for 10 Days!

PARTIAL CONTENTS

- 1 Television and Radio Repairing — Testing, repairing, replacing parts, 566 pages. 700 "This Is How" pictures, diagrams. By John Markus. Feature Ed., Electronics Magazine.
- 2 Practical Radio Servicing — Easy-to-follow directions, diagrams, drawings — with job sheet for every repair job. 569 pages. 473 illus. By William Marcus, Alex Levy. Electronic Training Experts.
- 3 Profitable Radio Troubleshooting — WHERE to look and WHAT to do for every trouble. How to avoid costly mistakes, handle customers profitably. 330 pages. 153 "how-to" illus. By William Marcus, Alex Levy.
- 4 Profitable TV Troubleshooting — Short-cuts to SPOT and FIX every trouble — fast, for big profits. By Eugene A. Anthony, Service Consultant. General Elec. Co.
- 5 Repairing Record Changers — Step-by-step pictures and directions — how to set up service bench, etc. 278 pages. 202 A-B-C pictures. By Eugene Ecklund, Eng. DuMont Lab., Inc.
- 6 Complete Home Course Outline — Getting started in television and radio servicing. How to get the most out of your Course. How to get ahead FAST. By John Markus.

THIS AMAZING
OFFER SAVES
YOU \$11.85!

THIS COUPON SAVES YOU \$11.85

McGraw-Hill Book Co., Dept. S&M-E-A
327 West 41st St., New York 36, N. Y.

Send me — postpaid — for 10 days' FREE TRIAL the 6-Vol. McGraw-Hill TV, Radio and Changer Servicing Course. If okay, I'll remit only \$4.95 in 10 days; then \$5.00 monthly for 5 months. (A total savings of \$11.85 on the regular price of the Course and Detect-O-Scopes.) Otherwise, I'll return Course in 10 days; pay nothing.

ALSO SEND FREE (to keep whether or not I keep the Course) the 3 TV, RADIO, and CIRCUIT DETECT-O-SCOPE CHARTS. — total value \$3.00.

Name _____ (Please Print Clearly)


Address _____

City _____ Zone No. _____ (if any) State _____

CHECK HERE if you prefer to enclose first payment of \$4.95 with coupon. Same easy pay plan; same 10-day return privilege for full refund.

S&M-E-A

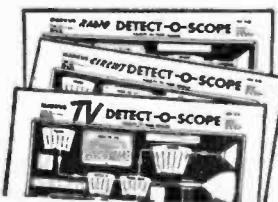Free ALL THREE Valuable Repair Aids: TV, RADIO, and CIRCUIT Detect-O-Scopes (Total Retail Value \$3.00)



FREE — whether you keep the Course or not — THREE amazing DETECT-O-SCOPE Charts. TV and RADIO Scopes enable you to spot all tube troubles in a jiffy. CIRCUIT Scope spots all circuit troubles. Make fix-it jobs easier, faster. 16 x 21 inches. ALL THREE (worth \$3.00) yours FREE while they last on this introductory offer.

TRANSISTORIZED POCKET FM RADIO AND CONVERTOR KIT



Fun for the youngster or the veteran in the electronic field . . . A 3-way transistorized pocket FM radio and tuner which tunes the complete FM band from 88 to 108.6 megacycles plus aircraft band from 109 to 145 megacycles. This fantastic set can be used in your car, home, or pocket, and needs no antenna or ground wires. Completely non-directional, this compact FM radio and tuner will play where all other radios have failed. Set has been demonstrated under an X-ray beam and near other electrical devices without any static or distortion. Featuring a two-stage circuit, this FM radio and tuner will produce music of top quality from stations located many miles from the receiver. Kit comes complete with easy-to-build instructions.

Kit, Complete with
Special Hi-Fi Earpiece with earmold, cord, and plug, \$29.95 postpaid.
(less Earpiece, \$26.95)

RADIO-TV SERVICING AID



Powerful 7-power magnifying glass mounted on 3" tweezers. Excellent tool for

getting into difficult and hard-to-see places. Ideal for radio kit builders, model craftsmen and for the Radio-TV service technician. Special low price, \$2.25 postpaid . . . A REAL SERVICE AID BARGAIN!

TWO-STAGE TRANSISTOR AMPLIFIER OR PRE-AMP KIT



You can build a powerful two-stage amplifier or pre-amp which can be used as a phonograph amplifier or amplifier for a crystal set, and as a pre-amp for crystal or magnetic pick-up. Kit comes complete with two transistors, volume control with switch, attractive plastic case with a snap bottom, and is powered with a single penlight cell with an output of nearly 1/2 of a watt. Complete with easy-to-follow instructions. \$6.95 postpaid.

SPECIAL SECTION for RADIO BEGINNERS

Crystal-Set Kit \$1.25 p p

Headphones (double) \$2.25 p p

Ball Bearing Tuning Condenser with Metal Dial and Knob \$1.50 p p

(Free Crystal with each \$10.00 order)

Beginners all Wave Kit Two Stage Circuit with Transistor, High Frequency Tube, Drilled Chassis and all Clips and Wire—\$7.95 less batteries. Many users report up to 12,500 miles on short wave plus the Broadcast Band. Tunes from 16 meters to 160 meters.

WORLD'S SMALLEST TWO BAND RADIO




Size 2 1/2" x 3 1/2" x 1 1/2"

It's ready now . . . The 2-band 8-oz. battery, transistorized Ekeradio, the world's smallest radio with short wave band. The radio needed in every home and office for any emergency such as earthquake, floods, hurricanes, snow storms or an enemy attack when electricity falls. Uses a powerful subminiature tube and transistor. Operates on its self contained batteries (can be changed without tools). Features: switch for short wave, ball bearing tuning condenser, has metal calibrated dial, uses the latest type earpiece, same as used in the best hearing aids, and comes in wrinkled gold finish. Plays instantly at anytime, anywhere, without disturbing anyone. You can tune in on exciting police calls . . . listen to airplanes and ground stations . . . hear the fishing boats and ship to shore broadcasts . . . get the radio amateurs on the 75 meter (ham) band. All this and the complete broadcast band. Yes, it's all at your finger tips, and is crystal clear, high fidelity, static free reception . . . send for your Ekeradio today. Show it to your friends and they, too, will be proud to own one. Wired and air tested . . . batteries, button receiver and 8 feet receiving wire antenna. This is not a kit. Comes all ready to play. Price \$29.95. P.P.

EKERADIO ELECTRONIC DEVELOPMENTS

Dept. E • 650 North Fair Oaks Avenue
In Calif. add State Tax—No C.O.D.

• Pasadena, California
U. S. Orders Only

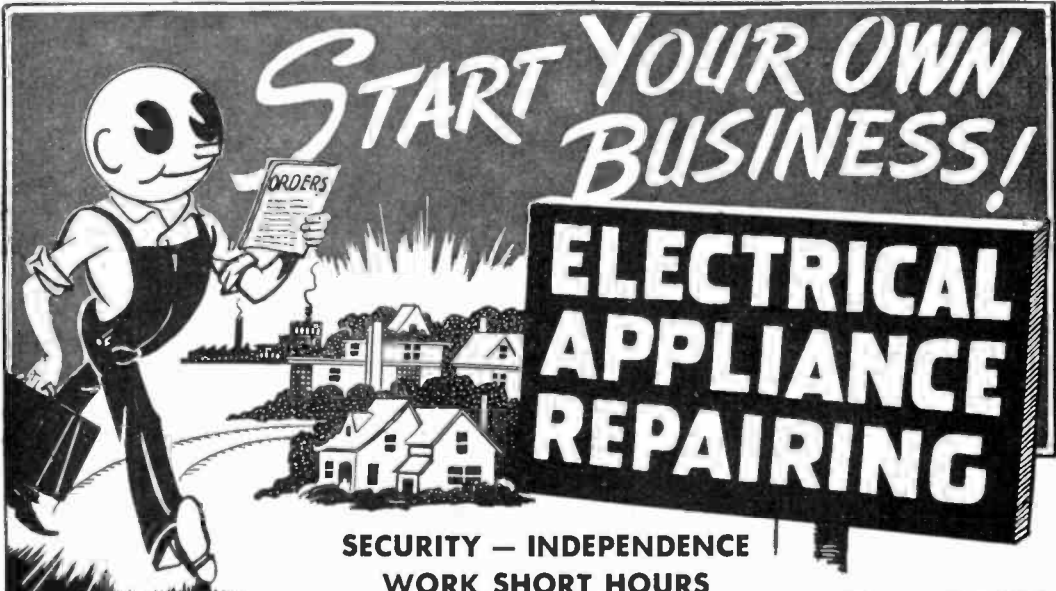

EARN WHILE YOU LEARN!

Only had your course a few short weeks and have already made \$800.00. Going to quit my job paying \$250.00 straight salary to operate my own business.—J. D. S., St. Louis, Mo.
I work day times at the shipyard and after 4:00 P. M. I operate from my cellar and garage. I average \$10.00 to \$15.00 clear every day.—Walter Hanhy, Brockton, Mass.

**SECURITY — INDEPENDENCE
WORK SHORT HOURS**

There are millions of electrical equipment units in daily use . . . in factories, homes, office buildings and on farms. Skilled electrical technicians are needed to keep this equipment in good running condition. Learn at home in spare time.

You can now **BE TRAINED** to fill this **BIG NEED** . . . a need that grows day by day because of new electrical inventions for home and factory.

If you are mechanically inclined, can hold and use tools, we can give you the training and time-saving kits that will enable you to . . . Command More Money at Work . . . A Better Paying Job Elsewhere . . . Or A Business Of Your Own!

The **ELECTRONIC KIT**, a multi-purpose trouble detector, and other valuable Shop Method Training is sent to you! All instruction material is written in simple, easy-to-understand language, chock full of hundreds of detailed photos and drawings. Used by servicemen the country over.

We show you how to quickly locate the trouble, how to fix it and what to charge. **ALSO**, how to solicit business and keep business coming to you.

Get Full Facts on how you can get this training at home in your spare time and pay for it out of your earnings while learning!

IN YOUR OWN KITCHEN, BASEMENT, OR GARAGE

You don't need elaborate fixtures or expensive equipment to be a successful repairman. Work as many hours as you wish. The Electrical Appliance Technician is his own boss!

**\$5.00 - \$6.00
HOUR**

often charged for making ordinary repairs. We show you how to repair refrigerators, vacuum cleaners, washing machines, motors, etc., etc.

AGE IS NO BARRIER

Nor is a minor physical handicap. Work is light, pleasant and **PROFITABLE**.

FREE BOOK

On America's fastest growing industry
CHRISTY TRADES SCHOOL, Dept. D-411, 3214-16 W. Lawrence Ave., Chicago 25

**CHRISTY TRADES SCHOOL, Dept. D-411
3214-16 W. Lawrence Ave., Chicago 25, Ill.**

Gentlemen:

Please rush me your **FREE ILLUSTRATED BOOK** about Electrical Appliance Servicing, facts on your Electronic Kit and Special form for paying later from earnings while learning.

NAME _____ Age _____

ADDRESS _____

CITY _____ Zone _____ State _____

SEND COUPON TODAY

WORKING KIT FURNISHED



BUILD THE BEST!
 build ALLIED'S own amazing
knight®-kits



see them all in
ALLIED'S 1959
ELECTRONIC SUPPLY CATALOG

free

BUILD YOUR OWN!
IT'S EASY—IT'S FUN—
SAVE UP TO 50%



452
 value-packed
 pages



HAM KITS



HOBBY KITS



INSTRUMENT KITS



HI-FI KITS

SAVE on Everything in Electronics



WORLD'S LARGEST STOCKS: Everything for Experimenters, Builders, Amateurs, Servicemen, Engineers, Hi-Fi enthusiasts. Get more for your money in Hi-Fi systems and components, including latest Stereo; save on build-your-own KNIGHT-KITS; recorders and tape, Amateur station equipment; TV tubes, antennas, accessories; test instruments; industrial electronic equipment—plus the world's largest stocks of parts, tubes, transistors, tools and books. Send today for your FREE 1959 ALLIED Catalog!

EASY TERMS AVAILABLE

ALLIED RADIO

Everything in Electronics at Lowest Prices

our 38th year

send for
FREE
 Catalog

ALLIED RADIO CORP., Dept. 64-9
 100 N. Western Ave., Chicago 80, Ill.

Rush FREE 1959 ALLIED 452-Page Catalog.

Name _____

Address _____

City _____ Zone _____ State _____

CAR BUYER'S CHECKLIST

DATE _____ SALE _____

DEALER _____

MAKE _____ Get price in letters

MODEL _____ Insured later and borrow building charges

YEAR _____ Subtotal price of motor

WARRANTY _____ Transportation charges


EXTRA EQUIPMENT _____ Dealer's extra and handling charges

DEALER'S SALES TAX _____ Dealer's base rate on new standard equipment

OPTIONAL EQUIPMENT AND ACCESSORIES

Standard	Optional	Price
Automatic	<input type="checkbox"/>	
Power windows	<input type="checkbox"/>	
Power door locks	<input type="checkbox"/>	
Power seats	<input type="checkbox"/>	
Power steering	<input type="checkbox"/>	
Power brakes	<input type="checkbox"/>	
Power windows	<input type="checkbox"/>	
Power door locks	<input type="checkbox"/>	
Power seats	<input type="checkbox"/>	
Power steering	<input type="checkbox"/>	
Power brakes	<input type="checkbox"/>	
Power windows	<input type="checkbox"/>	
Power door locks	<input type="checkbox"/>	
Power seats	<input type="checkbox"/>	
Power steering	<input type="checkbox"/>	
Power brakes	<input type="checkbox"/>	
Power windows	<input type="checkbox"/>	
Power door locks	<input type="checkbox"/>	
Power seats	<input type="checkbox"/>	
Power steering	<input type="checkbox"/>	
Power brakes	<input type="checkbox"/>	
Power windows	<input type="checkbox"/>	
Power door locks	<input type="checkbox"/>	
Power seats	<input type="checkbox"/>	
Power steering		

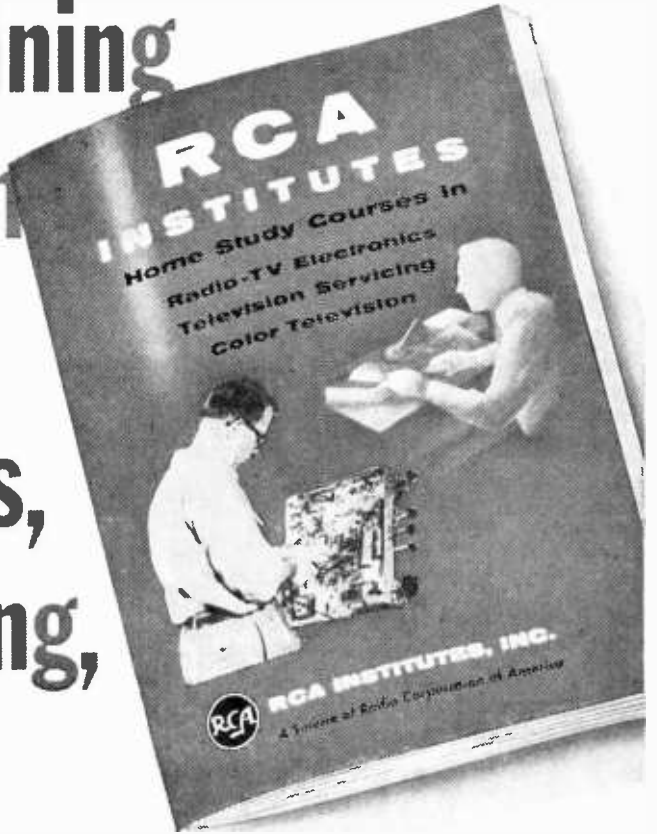RCA offers you the finest training at home in Radio-TV electronics, TV servicing, Color TV



SEND FOR THIS FREE

BOOK NOW!



RCA INSTITUTES

A SERVICE OF RADIO CORPORATION OF AMERICA
350 WEST FOURTH STREET, NEW YORK 14, N. Y.

In Canada — RCA Victor Company, Ltd.
5001 Cote de Liesse Rd., Montreal 9, Que.

RESIDENT SCHOOL courses in New York City offer comprehensive training in Television and Electronics. Day and evening classes start four times each year.

Detailed information on request.

Pay-as-you-learn. You need pay for only one study group at a time. Practical work with very first lesson. All text material and equipment is yours to keep. Courses for the beginner and advanced student.

RCA Institutes, Inc., Home Study Dept. RTVE-58
350 West Fourth Street, New York 14, N. Y.
Without obligation, send me FREE 52 page CATALOG on Home Study Courses in Radio, Television and Color TV. No Salesman will call.

Name.....
Please Print

Address.....

City.....Zone... State.....

KOREAN VETS! Enter discharge date.....

To save time, paste coupon on postcard

Abraham Marcus, co-author of famous best-seller "Elements of Radio" makes amazing offer!



TRY MY TV and RADIO REPAIR COURSE FREE FOR 1 MONTH

"If you haven't earned at least \$100 in spare time during that period you pay not a cent."

Here it is! The most amazing guarantee ever offered on any radio-TV course anywhere! We'll send you Abraham Marcus' course to use FREE for one full month! If in that time you haven't actually made \$100 fixing radios and TV sets, just return the books to us and pay not a penny!

Why do we make this sensational offer? First, because these books are so easy to use. They are written in the same clear, easy-to-understand language that made the author's "Elements of Radio," a 1,000,000-copy best-seller. Second, because these books get right to the point—tell you what to do in 1-2-3 fashion. For example, once you master the first few chapters of the TV book you are ready for business—ready to do service jobs in the field—jobs that account for over 80% of all service calls. **DON'T WAIT!** You risk nothing when you send the coupon below. You don't have to keep the books and pay for them unless you actually make extra money fixing radios and TV sets. Even when you decide to keep them, you pay on easy terms. Mail the coupon now.



WHAT YOU GET IN THESE 3 GIANT VOLUMES

ELEMENTS OF TELEVISION SERVICING. Analyzes and illustrates more TV defects than any other book, and provides complete step-by-step procedure for correcting each. You can actually SEE what to do by looking at the pictures. Reveals for the first time all details, theory and servicing procedures for the RCA 28-tube color television receiver, the CBS-Columbia Model 205 color set, and the Motorola 19-inch color receiver.

RADIO PROJECTS. Build your own receivers! Gives you 10 easy-to-follow projects, including crystal detector receiver—diode detector receiver—regenerative receiver—audio-frequency amplifier—tuned radio-frequency tuner—AC-DC superheterodyne receiver—etc.

RADIO SERVICING Theory and Practice. Here is everything you need to know about radio repair, replacement, and re-adjustment. Easy-to-understand, step-by-step self-training handbook shows you how to locate and remedy defects quickly. Covers TRF receivers; superheterodyne receivers, short-wave, portable, automobile receivers, etc. Explains how to use testing instruments, such as meter, vacuum-tube voltmeters, tube checkers, etc., etc.

MAIL THIS COUPON

Prentice-Hall, Inc., Dept. 5747-L1
Englewood Cliffs, New Jersey

Please send me Abraham Marcus' TV & RADIO REPAIR COURSE (3 volumes) for 10 days FREE examination. Within 10 days I will either return it and owe nothing, or send my first payment of \$3.60, plus a few cents postage. Then, after I have used the course for a FULL MONTH, if I am not satisfied I may return it and you will refund my first payment. Or I will keep the course and send you two more payments of \$5.00 a month for two months.

Name _____
Address _____
City _____ Zone _____ State _____

ENGINEERING

American Industry needs more Trained Engineers to meet present day shortage. We are now receiving more requests for our Electronic Technicians than we can supply. Train Now at Heald's.

BACHELOR OF SCIENCE DEGREE, 27 MONTHS

- Degree Courses:
- Electronic Engineering
 - Electrical Engineering
 - Highway Engineering
 - Mechanical Engineering
 - Structural Engineering
 - Civil Engineering
 - Architectural

- Diploma Courses:
- TELEVISION Color TV
 - Electronic Technician
 - Industrial Electronic Tech.
 - Tool & Die Design
 - Architectural Drafting
 - Mechanical Drafting
 - Structural Drafting

Approved for Veterans

Pictured above Heald Student in Electrical Laboratory

Enroll Now for New Term
Heald College Ranks FIRST West of the Mississippi in "Who's Who" in America
Mail Coupon for FREE Catalog

Heald Engineering College
Est. 1863

Van Ness at Post, Dept. RTV-1
San Francisco, California

NAME _____
STREET _____
CITY _____
STATE _____




AMAZING TRANSISTOR RING RADIO

Here is the smallest and most novel transistor radio ever! Easily assembled circuit employs PNP transistor amplifier and micro-diode detector. Ferrite inductor tunes standard broadcast band. Power supplied by novel, self-contained dry charge galvanic cell for which materials are included. This unique kit available only from us. Ideal for school projects, experimenters, and all interested in novel devices. EVERYTHING needed to assemble the Ring Radio (plastic case, diode, transistor, etc., etc.) sent postpaid

for ONLY \$3.65. Use your own earphone or order below our specially priced precision midjet phone.

WRIST RADIO-\$3.95

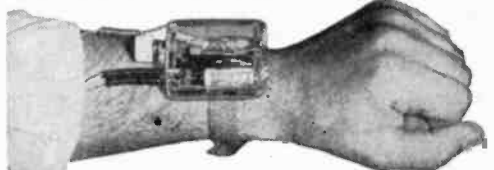

Hundreds of radio experimenters have assembled this combination Wrist. Pendant & Pocket Clip TRANSISTOR RADIO with great success. Complete set of parts includes PNP Transistor, micro-glass diode, plastic case, bakelite chassis plate, ferrite inductor tuner, knob, ceramic capacitor, pocket clip, hardware, hookup wire, etc.—ALL for \$3.95 postpaid. Set works on a 1 1/2 V., 124 battery sold by hearing aid dealers in your town. Uses any standard magnetic earphone or we'll furnish precision 8000 ohm hearing aid phone (retail price: \$8; not a cheap import) for only \$3.49. Illustrated instructions. All orders shipped 1st Class Mail U.S. & Canada. Sorry, no COD's.

ELECTRO-MITE Reg. U. S. Pat. Off. Springdale 636-X, Conn.

Build Your Own 16 RADIO

CIRCUITS AT HOME

with the New Deluxe 1959

PROGRESSIVE RADIO "EDU-KIT"

A Practical Home Radio Course

Now Includes

- ★ TRANSMITTER
- ★ SIGNAL TRACER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR
- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools Needed
- ★ EXCELLENT BACKGROUND FOR TV
- ★ School Inquiries Invited
- ★ Sold in 19 Countries

YOU DON'T HAVE TO SPEND HUNDREDS OF DOLLARS FOR A RADIO COURSE

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction practice and servicing. THIS IS A COMPLETE RADIO COURSE IN EVERY DETAIL. You will learn how to build radios, using regular schematics; how to wire and solder in a professional manner; how to service radios. You will work with the standard type of punched metal chassis as well as the latest development of Printed Circuit chassis. You will learn the basic principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice code using the Progressive Code Oscillator. You will learn and practice trouble-shooting, using the Progressive Signal Tracer, Progressive Signal Injector, Progressive Dynamic Radio & Electronics Tester and the accompanying instructional material. You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur Licenses. You will build 16 Receiver, Transmitter, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for television, Hi-Fi and Electronics.

Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with a basic education in Electronics and Radio, worth many times the complete price of \$22.95. The Signal Tracer alone is worth more than the price of the entire kit.

THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby, a well paying business or a job with a future, you will find the "Edu-Kit" a worth-while investment. Many thousands of individuals of all

ages and backgrounds have successfully used the "Edu-Kit" in more than 70 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that you cannot make a mistake. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor is necessary.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematics, study theory, practice trouble-shooting—all in a closely integrated program designed to provide an easily-learned, thorough and interesting background in radio. You begin by examining the various radio circuits of the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set you will enjoy listening to regular broadcast stations. Then, practice testing and trouble-shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are sixteen Receiver, Transmitter, Code Oscillator, Signal Tracer, and Signal Injector circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 16 different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, instruction manuals, hook-up wire, solder, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio and Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for working with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book. You receive Membership in Radio-TV Club, Free Consultation Service, Certificate of Merit and Discount Privileges. You receive all parts, tools, instructions, etc. Everything is yours to keep.

Unconditional Money-Back Guarantee

The Progressive Radio "Edu-Kit" has been sold to many thousands of individuals, schools and organizations, public and private, throughout the world. It is recognized internationally as the ideal radio course.

By popular demand the Progressive Radio "Edu-Kit" is now available in Spanish as well as English.

It is understood and agreed that should the Progressive Radio "Edu-Kit" be returned to Progressive "Edu-Kits" Inc. for any reason whatever, the purchase price will be refunded in full, without quibble or question, and without delay.

The high recognition which Progressive "Edu-Kits" Inc. has earned through its many years of service to the public is due to its unconditional insistence upon the maintenance of the highest engineering and instructional standards, and 100% adherence to its Unconditional Money-Back Guarantee. As a result we do not have a single dissatisfied customer throughout the entire world.

ONLY \$22.95



Reg. U.S. Pat. Off.

FREE EXTRAS

• SET OF TOOLS

- SOLDERING IRON
- ELECTRONICS TESTER
- PLIERS-CUTTERS
- ALIGNMENT TOOL
- WRENCH SET
- VALUABLE DISCOUNT CARD
- CERTIFICATE OF MERIT
- TESTING INSTRUCTION MANUAL
- HIGH FIDELITY GUIDE & QUIZZES
- TELEVISION BOOK & RADIO TROUBLE-SHOOTING BOOK
- MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE & FCC AMATEUR LICENSE TRAINING
- PRINTED CIRCUITRY

SERVICING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms and causes of troubles in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

J. Statistic, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend \$240 for a Course, but I found your ad and sent for your Kit."

FROM OUR MAIL BAG

Ben Valerio, P. O. Box 21, Magna, Utah: "The Edu-Kits are wonderful. Here I am sending you the questions and also the answers for them. I have been a radio fan for the last seven years, but I like to work with Radio Kits, and like to build Radio Testing Equipment. I enjoyed every minute I worked with the Edu-Kit kits; the Signal Tracer works fine. Also like to let you know that I feel proud of becoming a member of your Radio-TV Club."

Robert L. Shuff, 1334 Monroe Ave., Huntington, W. Va.: "Thought I would drop you a few lines to say that I received my Edu-Kit, and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios and phonographs. My friends were really surprised to see me get into the swing of it so quickly. The Troubleshooting Tester that comes with the Kit is really swell, and finds 'n' trouble, if there is any to be found."

ORDER DIRECT FROM AD—RECEIVE FREE BONUS RESISTOR AND CONDENSER KITS WORTH \$7

- Send "Edu-Kit" postpaid. I enclose full payment of \$22.95.
- Send "Edu-Kit" C.O.D. I will pay \$22.95 plus postage.
- Send me FREE additional information describing "Edu-Kit."

Name
Address

PROGRESSIVE "EDU-KITS" INC.
1186 Broadway (Progressive Building, Dept. 503NN), Hewlett, N. Y.

SHOOT TV TROUBLE FAST

With H. G. Cisin's Copyrighted RAPID "TV TROUBLE SHOOTING METHOD"

Without experience or knowledge, this guaranteed new method of servicing TV sets enables you to **DIAGNOSE TV** troubles as rapidly as an expert. **NO THEORY—NO MATH**—you can locate all faults in record-breaking time regardless of make or model. "TV TROUBLE SHOOTING METHOD" is the most valuable aid to TV servicing ever written. Be a TV Trouble Diagnostician. Increase your present earnings. Open your own Profitable Business or get a high-paying skilled job.

It's all in this book . . . Nothing more to Pay—Nothing else to Buy

Alphabetically listed are 85 picture troubles, over 58 raster and 17 sound troubles. By this unique copyrighted method you know **EXACTLY WHERE** the trouble is; plus step-by-step instructions, including 69 **RAPID CHECKS**, help to find faulty part.

13 IMPORTANT PRELIMINARY CHECKS NEED NO INSTRUMENTS! Of the 69 Rapid Checks, **OVER 65 ALSO REQUIRE NO INSTRUMENTS!** Rapid checks include emergency checks for distorted pictures; defective tubes including PIX tube, plus 57 others. **ALL EXPLAINED IN SIMPLE LANGUAGE, PERFORMED WITHOUT INSTRUMENTS. MANY CHECKS USE THE PICTURE TUBE AS A GUIDE.**

H. G. Cisin, the author, is the inventor of the AC/DC midket radio. He licenses RCA, AT&T, etc. He has also trained thousands of technicians now owning their own prosperous TV service organizations or holding highly paid TV positions. His years of experience are embodied in this remarkable new book.

Guaranteed Money Back in 5 Days if Not Satisfied!

ABSOLUTELY FREE with each order: Your choice of Cisin's newest books: **BASIC ELECTRICITY—Vol. 1 of TV-RADIO TUBE SUBSTITUTION GUIDE.** These sell for 50c ea. **ACT NOW—get 2 books postpaid at cost of only one!**

\$1 Post-paid

RUSH COUPON NOW!

H. G. CISIN, Consulting Engineer—Dept. SM-19
Amagansett, N. Y.

Enclosed find \$1. Rush Trouble Shooting Method and free book marked above (if not marked Basic Elec. will be sent).
 Send all 3 books. Enclosed find \$1.50.

Name _____
Address _____
City _____ Zone _____ State _____



LEARN CODE the fast, easy way. Get maximum speed and efficiency to qualify as an operator in the quickest, easiest way. Picture yourself at your own transmitter, sending out radio code, messages that will be received around the globe. For 47 years the **CANDLER** system has trained beginners for all telegraphing requirements, operator licenses, highest ratings, and FCC specifications, both amateur and commercial.

4 CANDLER COURSES AVAILABLE:—Beginning Code Course; Amateur Code Course; Simplified Code Course; Type It Right Course. Send for Free details today.

CANDLER SYSTEM

P. O. Box 9226 Dept. 108 Denver 20, Colo.

Develop 380,000 Volts

With This Van de Graaff Generator



Every electrical experimenter will want to build an operating model of the full-size electrostatic generator that aided in the development of the atomic bomb. This model will perform a variety of fascinating experiments and develop up to 380,000 volts. Complete bill of materials and step-by-step construction details make it easy to build the generator. Two large illustrated plans, size 22x34 inches. Order Craft Print No. 197—Price \$1.50. Also, "Souped-Up" Tesla Coil, Craft Print No. 191—Price \$1.00. Both plans, \$2.00.


SCIENCE AND MECHANICS

450 East Ohio St., Dept. 5556
Chicago 11, Ill.



Here's the Hobby
As New as Earth Satellites!

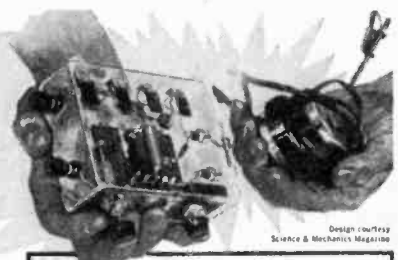NOW YOU CAN BUILD RADIOS—MOTORS—RELAYS Powered by the Sun!



Design courtesy Science & Mechanics Magazine

YOU'VE READ ABOUT SOLAR BATTERIES ON EARTH SATELLITES!...and now solar batteries can power devices of all types for you! Beginners, hobbyists, engineers, everyone with a basic knowledge of electronics can have hours of fun and gain first-hand experience in the new science of harnessing solar energy... the power source of the future! Leading electronic parts distributors carry a complete line of precision-made photovoltaic instruments that directly convert light into electrical energy. Best of all—they are not expensive, and with proper care will last indefinitely. Start this new hobby—today. It's easier than you think—and fun—to put the sun to work for you! It's the newest hobby under the sun!

THIS 84 PAGE BOOK TELLS HOW SUN BATTERIES AND PHOTOCELLS WORK—GIVES PLANS FOR MANY PROJECTS \$1.50

Packed with information, this book gives basic theory and applications. Completely illustrated, it contains wiring diagrams and plans—every detail necessary to build many interesting devices.

FREE PLANS!

for the radio shown and other interesting devices will help you get started. Ask for the

"PROJECT OF THE MONTH"

At your electronic parts distributor!

INTERNATIONAL RECTIFIER CORP. B2M SUN BATTERY

This is the famous B2M you've read about in leading popular magazines in bright sunlight (10,000 ft. candles) this battery will deliver 2 milliamperes at 250 millivolts under optimum conditions.

A \$2.50 value for only **\$1.50**



BUY THE B2M, THE BOOK AND ALL OTHER COMPONENTS REQUIRED AT YOUR FAVORITE ELECTRONICS PARTS DISTRIBUTOR.

If you are unable to locate them in your area, send check or money order to **INTERNATIONAL RECTIFIER CORPORATION, EL SEGUNDO, CALIFORNIA.**

SPECIAL OFFER, The book and the B2M Sun Battery for only \$2.85 at your distributor

NOW!
at a price
you can afford!

MAKE MORE MONEY in TELEVISION RADIO-ELECTRONICS

**BETTER...MORE COMPLETE...LOWER COST...
WITH NATIONAL SCHOOLS SHOP-METHOD
HOME TRAINING!**

BETTER...Training that is proved and tested in Resident School shops and laboratories, by a School that is the **OLDEST** and **LARGEST** of its kind in the world.

MORE COMPLETE...You learn **ALL PHASES** of Television-Radio-Electronics.

LOWER COST...Other schools make several courses out of the material in our **ONE MASTER COURSE**... and you pay more for less training than you get in our course at **ONE LOW TUITION!**



These
two FREE books will
show you how!

You get all information
by mail... You make
your own decision... at
home! **NO SALESMAN
WILL CALL**

TOP PAY... UNLIMITED OPPORTUNITIES LIFETIME SECURITY CAN BE YOURS!

You are needed in the Television, Radio, and Electronics industry! Trained technicians are in growing demand at excellent pay—in **ALL PHASES**, including Servicing, Manufacturing, Broadcasting and Communications, Automation, Radar, Government Missile Projects.

NATIONAL SCHOOLS SHOP-METHOD HOME TRAINING, with newly added lessons and equipment, trains you in your spare time at home, for these unlimited opportunities, including many technical jobs leading to supervisory positions.

YOU LEARN BY BUILDING EQUIPMENT WITH KITS AND PARTS WE SEND YOU. Your National Schools course includes thorough *Practical* training—**YOU LEARN BY DOING!** We send you complete standard equipment of professional quality for building various experimental and test units. You advance step by step, perform more than 100 experiments, and you build a complete TV set from the ground up, that is yours to keep! A big, new TV picture tube is included at no extra charge.

EARN AS YOU LEARN. We'll show you how to earn extra money right from the start. Many of our students pay for their course—and more—while studying. So can you!

RESIDENT TRAINING AT LOS ANGELES


If you wish to take your training in our Resident School at Los Angeles, the world's TV capital, start **NOW** in our big, modern Shops, Labs and Radio-TV Studios. Here you work with latest Electronic equipment... professionally installed... finest, most complete facilities offered by any school. Expert, friendly instructors. Personal attention. Graduate Employment Service. Help in finding home near school... and part time job while you learn. Check box in coupon for full information.

LESSONS AND INSTRUCTION MATERIAL ARE UP-TO-DATE, PRACTICAL, INTERESTING. Every National Schools Shop-Method lesson is made easy to understand by numerous illustrations and diagrams. All instruction material has been developed and tested in our own Resident School Shops, Laboratories and Studios.

SEND FOR INFORMATION TODAY... it can mean the difference between **SUCCESS** and failure for you! Send for your **FREE BOOK** "Your Future in Television-Radio-Electronics" and **FREE Sample Lesson.** Do it **TODAY**, while you are thinking about your future. It doesn't cost you anything to investigate!

GET THE BENEFITS OF OUR OVER 50 YEARS EXPERIENCE

Approved for
GI Training

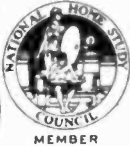

NATIONAL SCHOOLS

Los Angeles 37, Calif.

YOU GET...

- 19 Big Kits—**YOURS TO KEEP!**
- Friendly Instruction and Guidance
- Job Placement Service
- Unlimited Consultation
- Diploma—Recognized by Industry
- **EVERYTHING YOU NEED FOR SUCCESS!**

SHOP-METHOD HOME TRAINING COVERS ALL PHASES OF INDUSTRY

1. Television, Including Color TV
2. Radio AM & FM
3. Electronics for Guided Missiles
4. Sound Recording and Hi-Fidelity
5. FCC License
6. Automation and Computers
7. Radar & Micro-Waves
8. Broadcasting and Communications

NATIONAL TECHNICAL SCHOOLS



WORLD-WIDE TRAINING SINCE 1905

MAIL NOW TO
NATIONAL SCHOOLS, Dept RKK-88
4000 S. FIGUEROA ST. LOS ANGELES 37, CALIF.
Rush free TV-Radio "Opportunity" Book and sample lesson. No salesman will call.

NAME _____ AGE _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____

Check if interested **ONLY** in Resident School training at Los Angeles **VETERANS'** Give date of discharge.

Interesting, Pictorial FREE BOOKLET

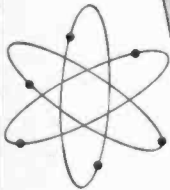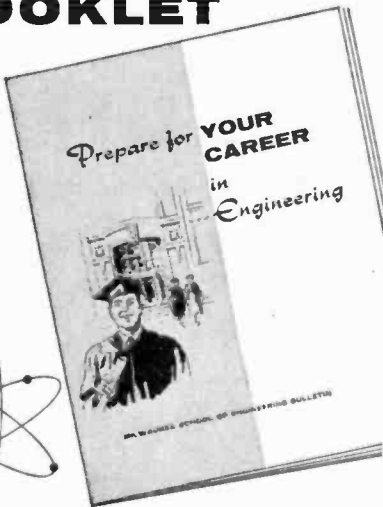

to help you decide on your career in **ELECTRONICS RADIO-TV COMPUTERS**

Here is a graphic story about preparing for your career as an engineer or engineering technician in electronics, radio, television, computers, etc. Booklet tells about:

- Wide variety of job opportunities
- Courses offered, degrees you can earn
- Pictures of the Milwaukee School of Engineering and its facilities
- Recreation and fraternities
- Scholarships; part-time work

—plus other interesting and informative facts to help you make a sound decision on your career.

MS-90

Milwaukee School of Engineering
— dedicated to serving young men and industry

SEND COUPON TODAY!

Milwaukee School of Engineering
Dept. RTX 58, 1025 N. Milwaukee St., Milwaukee, Wis.

Please send me free new booklet
"Prepare for Your Career in Engineering"
I'm interested in Radio-TV Electronics
 Computers

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

I am I am not eligible for veterans educational benefits. (discharge date)

New Isotronic Training Method!

LEARN TV REPAIR IN ONE SHORT WEEK

Now, after 5 years research—a dynamic TV training technique that makes others obsolete! If you've waited for a chance to have your own prosperous business, here's an opportunity to make up to \$150 weekly, almost immediately!

NO EXPENSIVE TRAINING - NO LONG STUDY!

You want to get started servicing TV sets - not building them! So, why pay up to \$250 for high-priced lessons and equipment... study long months? Our revolutionary ISOTRONIC method qualifies you to handle any make TV set right away! All the complicated technical theory is already taken care of by our Scientists! This new technique - hailed the most practical in the field - was developed by two of the industry's most respected scientists, in cooperation with every major American TV manufacturer!

PUT YOUR "KNOW HOW" TO WORK FOR PROFIT!

In addition to the most streamlined training program of its type, you also benefit from a complete Business Plan that explains fully how to start, conduct, and expand your own TV Service business. Written by expert business consultants. Packed solid with practical know-how instead of theory! Yes, a complete "Business Package" designed to quickly bring you the good things in life that come with your own successful business.

FREE LESSON PROVES ISOTRONIC METHOD WORKS!

For conclusive proof, send now for full details and **FREE SAMPLE LESSON**. Apply it to your own ailing set or a friend's - repair it without a single tool or testing device - convince yourself that the amazing Isotronic method can put you in a profitable TV business of your own, in one short week! Write today - free lesson supply limited! (No obligation, no salesman will call.)
ELECTRONIC ENGINEERING CO., Dept. B-878
1038 So. La Brea, Los Angeles 19, California



Looking for a Science Project?

Then get the Science Experimenter, a collection of science project articles for the experimenter of every age, but especially valuable to younger adults—in school or out—now engaged in the study of some phase of modern science. The scope of the projects for which detailed, show-how plans and step-by-step text are given in this book embraces the entire field of physical science. And in addition to the two-score projects included—projects which can be used as points of departure for Science Fair entries—there are also authoritative, informative general articles on varied aspects of scientific research and knowledge. If you cannot obtain a copy of the SCIENCE EXPERIMENTER (Handbook No. 557) from your newsdealer after October 30th, let us know and we will see that he is supplied. Or send 75c direct to Science and Mechanics, Dept. 5557, 450 East Ohio Street, Chicago 11, Illinois and we will fill your order. Look for it—

The SCIENCE EXPERIMENTER

Goes On Sale October 30th

How to Build Your Own Photo Equipment

It's Easy! It's Fun! And you can save lots of money, too! Our 160-page "Photo Craftsman" Handbook explains H-U-W to build 90 different pieces of photographic equipment. Hundreds of photos, drawings, diagrams, tables, bills of materials and step-by-step instructions make it as easy as ABC to build precision photo equipment. Send 50c for this big handbook of plans now!

90 "Do It Yourself" Plans 50¢



How to Build—

- Photo Enlarger
- Home Movie Titrer
- LowCost Speedlight
- Boom Light
- Copying Stand
- Tray Rocker
- LowCost Flashgun
- Rotary Washer
- Processing Tanks
- Flash Synchronizer
- Film Viewer
- Electronic Timer
- and 78 other useful projects,

SCIENCE AND MECHANICS MAGAZINE

5558 Dunham Building - Chicago 11, Illinois

FOR REPAIRING RADIO AND TV

Superior's New Model 79

SUPER-METER

The Most Versatile All-Purpose Multi-Range Tester Ever Designed



WITH NEW 6" FULL-VIEW METER

A Combination VOLT-OHM MILLIAMMETER. Plus CAPACITY, REACTANCE, INDUCTANCE AND DECIBEL MEASUREMENTS.

Also Tests SELENIUM AND SILICON RECTIFIERS, SILICON AND GERMANIUM DIODES.

- ✓ D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500.
- ✓ A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000.
- ✓ D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes.
- ✓ RESISTANCE: 0 to 1,000/100,000 Ohms. 0 to 10 Megohms.
- ✓ CAPACITY: .001 to 1 Mfd. 1 to 50 Mfd.
- ✓ REACTANCE: 50 to 2,500 Ohms, 2,500 Ohms to 2.5 Megohms.
- ✓ INDUCTANCE: .15 to 7 Henries, 7 to 7,000 Henries.
- ✓ DECIBELS: -6 to +18, +14 to +38, +34 to +58.

The following components are all tested for QUALITY at appropriate test potentials. Two separate BAD-GOOD scales on the meter are used for direct readings.

- ✓ All Electrolytic Condensers from 1 Mfd. to 1000 Mfd.
- ✓ All Selenium Rectifiers.
- ✓ All Silicon Rectifiers.
- ✓ All Germanium Diodes.
- ✓ All Silicon Diodes.

Comes complete with operating instructions and test leads. Use it on the bench—use it on calls. Carrying case included at no extra charge accommodates the tester, instruction book and test leads. Only

38⁵⁰

Superior's New Streamlined Model TD-55

TUBE TESTER



Quickly and Efficiently Tests Radio and TV Tubes Including: Seven Pin Miniatures; Eight Pin Subminors, Octals and Loctals; Nine Pin Novals.

YOU CAN'T INSERT A TUBE IN THE WRONG SOCKET.

It is impossible to insert the tube in the wrong socket when using the new Model TD-55. Separate sockets are used, one for each type of tube base. If the tube fits in the socket it can be tested.

"FREE-POINT" ELEMENT SWITCHING SYSTEM.

The Model TD-55 incorporates a newly designed element selector switch system which reduces the possibility of obsolescence to an absolute minimum. Any pin may be used as a filament pin and the voltage applied between that pin and any other pin, or even the "top-cap."

CHECKS FOR SHORTS AND LEAKAGES BETWEEN ALL ELEMENTS. The Model TD-55 provides a super sensitive method of checking for shorts and leakages up to 5 Megohms between any and all of the terminals.

ELEMENTAL SWITCHES ARE NUMBERED IN STRICT ACCORDANCE WITH R.M.A. SPECIFICATION.


One of the most important improvements, we believe, is the fact that the 4 position fast-action snap switches are all numbered in exact accordance with the standard R.M.A. numbering system. Thus, if the element terminating in pin No.7 of a tube is under test, button No. 7 is used for that test.

The Model TD-55 comes complete with operating instructions and charts. Use it on the bench—use it for field calls. A streamlined carrying case, included at no extra charge, accommodates the tester and book of instructions.

26⁹⁵

FOR REPAIRING ALL ELECTRICAL APPLIANCES MOTORS AND AUTOMOBILES

Superior's New Model 70 UTILITY TESTER

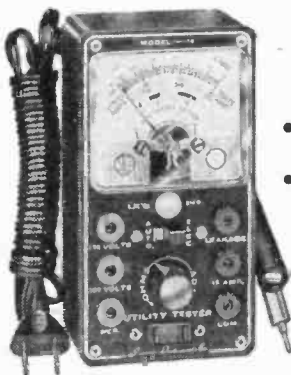

As an electrical trouble shooter the Model-70:

- Will test Toasters, Irons, Brailers, Heating Pads, Clocks, Fans, Vacuum Cleaners, Refrigerators, Lamps, Fluorescents, Fans, Switches, Thermostats, etc.
- Measures A.C. and D.C. Voltages, A.C. and D.C. Current, Resistances, Leakage, etc.
- Will measure current consumption, while the appliance under test is in operation.
- Incorporates a sensitive direct-reading commonly used in electrical appliances, motors, etc.
- Leakage detecting circuit will indicate continuity from zero ohms to 5 megohms (5,000,000 ohms).

As an Automotive Tester the Model 70 will test:

- Both 6 Volt and 12 Volt Storage Batteries
- Generators
- Starters
- Distributors
- Ignition Coils
- Regulators
- Relays
- Circuit Breakers
- Cigarette Lighters
- Stop Lights
- Condensers
- Directional Signal Systems
- All Lamps and Bulbs
- Fuses
- Heating Systems
- Horns
- Also will locate poor grounds, breaks in wiring, poor connections, etc.

Handsome round-cornered molded bakelite case, 3 1/4" x 5 1/4" x 2 1/4". Complete with all test leads. Also included is a 64 page book giving detailed instructions for testing all electrical appliances, automotive equipment, etc. Only

15⁸⁵

SHIPPED ON APPROVAL NO MONEY WITH ORDER — NO C.O.D.

Try any of the above instruments for 10 days before you buy. If completely satisfied then send down payment and pay balance as indicated on coupon. No Interest or Finance Charges Added! If not completely satisfied return unit to us, no explanation necessary.

MOSS ELECTRONIC DISTRIBUTING CO., INC. Dept. D-495, 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked on approval. If completely satisfied I will pay on the terms specified with no interest or finance charges added. Otherwise, I will return after a 10 day trial positively cancelling all further obligation.

Name

Address


City..... Zone..... State.....

F. O. B., N. Y. C.

Model 70..... Total \$15.85 \$3.85 within 10 days; Balance \$4.00 monthly for 3 months.

Model 79..... Total \$38.50 \$8.50 within 10 days; Balance \$6.00 monthly for 5 months.

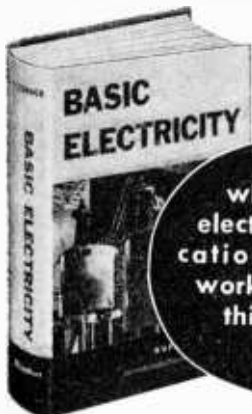Model TD-55: Total \$26.95 \$6.95 within 10 days; Balance \$5.00 monthly for 4 months.



Brand New!

No matter what kind of radio, electronic, communications or electrical work you plan to do, this is the most important training of all!

BASIC ELECTRICITY

Your key to Success in Radio-Electronics

Trying to learn radio-electronics without first studying Basic Electricity is like trying to row a boat without oars!

Actually, a radio-electronic system uses almost every form of electric current and electromagnetic reaction known. That's why the training supplied by this big new BASIC ELECTRICITY home training manual is so vitally important to beginners and "old timers" alike.

GOODBYE TO GUESSWORK!

Think how often you've been "stumped" by a technical talk, text book or by some complicated equipment . . . simply because you're not too clear about the principles involved. Think of the troubles you may have had with basic electrical factors such as reactance, phase relations, impedance, etc. for the same reason.

And think of the future too! BASIC ELECTRICITY by Rufus Turner brings you truly top notch training for profitable industrial work where it's impossible to say just where electricity ends and electronics begins.

Starting with a clear explanation of fundamentals, the book progresses to every phase of electrical and electromagnetic theory and operation. Included are dozens of typical electrical problems and their solutions. Each chapter ends with a Self-Test review of all the main points. Essential elements such as motors, generators, batteries, polyphase, etc., often neglected by ordinary electronic books, are fully covered. Everything is explained clearly as A-B-C by text and over 300 clear illustrations.

COMPLETE ELECTRICAL KNOW HOW plus BASIC ELECTRONICS

In one big, easily understood home training guide

Includes Basic Circuits and Direct Currents; Switches and Controls; Current Flow in Liquids and Gases; Magnetism and Electromagnetism; A.C.; Capacitors and Capacitance; Inductors and Inductance; Phase Relations and Impedance; Transformers; Generators and Motors; Polyphase Systems; Rectifiers; Wiring; Illumination; Telegraph and Telephone Fundamentals; Instruments.

10 DAY FREE EXAMINATION!

Dept. MH-7, RINEHART & CO., INC.,
232 Madison Ave., New York 16, N. Y.

Send Turner's 396-page BASIC ELECTRICITY manual for 10-day FREE EXAMINATION. If book is satisfactory, I will then send you \$6.50 (plus postage) promptly in full payment. If not, I will return book within 10 days and owe nothing. (SAVE! Save \$6.50 with order and we pay postage. Same return privilege with money refunded.)

Name.....
Address.....
City, Zone, State.....
OUTSIDE U.S.A.—Price \$7.00 cash with order. Money back if you return book within 10 days.

CUT COSTS ON CAR UPKEEP

get a copy of the

CAR OWNER'S HANDBOOK

If you want to save money on your car's running costs and upkeep, you'll want Volume 4 of this handbook, a comprehensive guide to the use, performance, and care of your automobile. Over 20 of the articles in it are devoted to troubleshooting and maintenance jobs you can do yourself to get top engine efficiency and more miles to the gallon, articles that tell you how to save on oil; remedy road stalls; stormproof your car; repair its muffler; silence body noises; service carburetors; overhaul brakes; and much more.

In addition, there are performance test reports on six of the leading imported economy cars, plus the lowdown on gas additives and station wagons and many other topics of interest and value to the car owner.

For a copy of the CAR OWNER'S HANDBOOK, send 75¢ (no C.O.D.'s or stamps, please) for Handbook No. 552 to Dept. 5553.

SCIENCE AND MECHANICS
450 EAST OHIO STREET
CHICAGO 11, ILLINOIS

Free Trial Guarantees you can

FIX ANY TV FAST!

..or pay not one cent!

NO EXPERIENCE OR HIGHER MATH NECESSARY

Let 10 days' FREE use of this book prove —at our expense—you can install and repair any TV set like an expert. You'll be amazed how easy it is to spot most troubles by eye and ear alone—how the clear, step-by-step instructions and illustrations reduce even the most complicated problems to simple a-b-c's. Quickly and easily, with this manual to guide you, you can turn your up-to-the-minute knowledge into plenty of spare-time cash or be your own boss in a profitable business.

In this new edition you get: The latest circuits—Troubleshooting techniques—Transistorized TV sets—Remote control tuning—Troubleshooting printed wiring—Module type construction—Packaged circuits—Newest servicing hints—Latest information on color TV and test equipment . . . every new advancement plus the basic know-how you need to put any set back in perfect working order.

Mr. C. W. Morris of Charleston, W. Va., says: "I have paid as much as \$200.00 for courses that haven't given me the clear understanding this book has."

10-DAY TRIAL COUPON—MAIL TODAY

PRENTICE-HALL, INC., Dept. 5747-L2
Englewood Cliffs, New Jersey
Send me TELEVISION SERVICING for 10 days' FREE TRIAL. In that time I'll either return it and owe nothing, or keep it and pay \$2.75 down (plus postage) and \$2 monthly for 2 months.
Name.....
Address.....
City..... Zone..... State.....
SAVE! Send \$6.75 now and we'll pay postage. Refund and same return privilege guaranteed.



All New! 3rd Revised Edition

- TRANSISTORS
- COLOR SETS
- TUBE CIRCUITS
- DEFLECTION METHODS
- DC RESTORATION
- ANTENNAS
- POWER SUPPLIES
- SYNCHRONIZATION

NOW YOU CAN SECURE A HIGH SALARIED • TOP PRESTIGE CAREER IN ELECTRONICS IN ONLY ONE YEAR!

ELECTRONICS is the fastest growing industry in America today, creating unlimited opportunities for high salaries, with rapid advancement in **INDUSTRY AND THE ARMED FORCES** for Bailey Trained electronic engineering technicians.

LARGE CORPORATIONS from coast to coast, and **BRANCHES OF THE ARMED FORCES** send recruiters to visit each graduating class at Bailey Tech, offering unusually high starting salaries.

BAILEY GRADUATES ARE BEING HIRED for such fascinating and interesting work as technical salesmen, research and development of guided missiles, electronic business machines and automatically controlled manufacturing plants, etc., also good **RATINGS IN THE ARMED FORCES.**

UP TO SEVEN TECHNICIANS are needed for every engineer... this, plus superior training is why Bailey Graduates are being paid more to start, and are advancing more rapidly than many men who have spent four years in training.

Resident training is easier and costs less than you may think! We provide housing and part-time jobs while in school, plus free nationwide employment service for graduates. If you want to quickly enter America's fastest growing and most exciting industry, write for free booklet... no obligation.

**VETERAN APPROVED
BAILEY TECHNICAL SCHOOLS**
1635 S. Grand • St. Louis 4, Mo.



This Minneapolis-Honeywell system controls hundreds of automatic manufacturing operations. Experience on live equipment is emphasized at Bailey and is another reason for the tremendous backlog of high pay positions waiting **BAILEY GRADUATES.**

MAIL TODAY

Please mail immediately this free booklet without obligation

Name _____
Address _____
City _____ State _____



Get This Valuable Book

FREE



Yes, you get our big Diagrams book, FREE! It's like a road-map that shows you the way to easier Radio-TV repair. Needed by every serviceman. Complete 11x22" Schematic Diagrams on many radio and TV sets help cut servicing time. Includes simple instructions on how to use diagrams and picture patterns. This book is yours FREE for asking to see Coyne's great new 7-book set, "Applied Practical Radio-Television!"

AT LAST! MONEY-MAKING "KNOW-HOW" ON TRANSISTORS, COLOR TV AND SERVICING

Coyne's new 7-volume set gives you all the answers to servicing problems—quickly! For basic "know-how," you'll find everything you want in Volumes 1 to 5 on over 5000 practical facts and data. Every step is completely explained from fundamentals to installing, servicing and trouble-shooting all types of radio and TV sets. So up-to-date it covers **COLOR TV, UHF** and latest on **TRANSISTORS.**

EXTRA! NEW TV CYCLOPEDIA For speedy on-the-job use, you get Vol. 6—the 868 page **TV CYCLOPEDIA.** Answers problems on servicing, alignment, installation, etc. in ABC order. All this plus **Volume 7—NEW Coyne TECHNICAL DICTIONARY** with over 4000 definitions of the latest terms, symbols and abbreviations. Use all 7 books FREE for 7 days; get the Servicing Book FREE!

Just For Examining COYNE'S New Set

"Applied Practical Radio-Television"

on 7 DAY FREE TRIAL!

**NOW!
7 BIG BOOKS
IN ONE GREAT SET!**



SEND NO MONEY!

Just mail coupon for 7-volume set on 7 days free trial. We'll include book of 150 TV-Radio Patterns and Diagrams. If you keep the set, pay \$3 in 7 days and \$3 per month until \$24.50 plus postage is paid. (Cash price, only \$22.95.) Or you can return the library at our expense in 7 days and owe nothing. **YOU BE THE JUDGE.** Either way, book of TV-Radio Patterns is yours FREE to keep! Offer limited. **ACT NOW!**

**FREE!
5 YEARS
OF VALUABLE
SUPPLEMENTS**



Coyne's FREE Annual Supplement Service keeps your set up-to-date on everything that will be new the next 5 years in Radio-TV, electronics and electricity.

FREE BOOK — FREE TRIAL COUPON!

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL, Dept. 97-RE
500 S. Paulina St., Chicago 12, Ill.

YES! Send 7-Volume "Applied Practical Radio-Television" for 7 days FREE TRIAL per your offer. Include TV-Radio Patterns & Diagram Book FREE.

Name _____ Age _____
Address _____
City _____ Zone _____ State _____

Where Employed _____
 Check here if you want library sent C.O.D. You pay postman \$22.95 plus C.O.D. postage on delivery, 7-day money-back guarantee.

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL
500 S. Paulina St., Dept. 97-RE Chicago 12, Ill.

The Mechanism of Mind



WHY YOU ARE AS YOU ARE— and *What You Can Do About It!*

DID you ever stop to think *why* you do the things you do? Have you often—when alone—censured yourself for impulsive urges, for things said or done that did not truly represent *your real thoughts*, and which placed you at a disadvantage? Most persons are *creatures of sensation*—they react to instinctive, impelling influences which surge up within them and which they do not understand—or *know how to control*. Just as simple living things involuntarily withdraw from irritations, so likewise thousands of men and women are content to be motivated by their undirected thoughts which haphazardly rise up in their consciousness. *Today you must sell yourself* to others—bring forth your best abilities, manifest your personality, if you wish to hold

a position, make friends, or impress others with your capabilities. You must learn how to draw upon your latent talents and powers, not be bent like a reed in the wind. There are simple, natural laws and principles which—if you understand them—make all this possible.

For centuries the Rosicrucians (not a religious organization) a world-wide movement of men and women devoted to the study of life and its hidden processes, have shown thousands how to probe these mysteries of self. Renowned philosophers and scientists have been Rosicrucians—today men and women in every walk of life owe their confidence and ability to solve personal problems to the Rosicrucian private, *sensible* method of self-development. To learn what the Rosicrucians can do for you regardless of your present position in life, send **TODAY** for your free copy of the book, "The Mastery of Life." There is no obligation. Please address your request to Scribe A.J.D.

The ROSICRUCIANS (AMORC) SAN JOSE, CALIFORNIA, U.S.A.

Printed circuit amplifier has reserve power for driving a big speaker. Unit (inset) is so compact, it can be installed inside much smaller speaker cabinets than that shown if desired. Total weight is only 6 oz.



Printed Circuit Phono Amplifier

Smaller, cheaper, neater than conventional units
—and it can drive a 12-inch speaker!

By THOMAS BLANCHARD


MASS producers of electronic equipment have found printed circuitry ideal for their operations. The experimenter, too, will find it worthwhile to utilize printed circuitry—as this project demonstrates. A two-tube, inverse feedback, phono amplifier, it can be assembled on a ready-made #PC-360 copper etched wiring board (available from Photocircuits Corp., see Table A), or etched on a blank board using readily available materials (see Materials List and Table A).

Generally speaking, there are two ways to make a printed circuit: the additive and the subtractive. In the additive, or plating process, a sheet of plain phenolic (Bakelite) is sketched

with a conductive ink. The phenolic is then placed in a copper plating tank until a sufficient deposit of copper affixes itself to the inked circuit paths. This method, however, is strictly a commercial process.

In the subtractive, or etched process, a sheet of phenolic to which is bonded on one side a thin layer of copper foil, is used. The techniques employed to etch the circuit are simple enough for the experimenter to handle them in his kitchen or basement, and they are the ones we'll use for this phono amplifier's circuit.

First, remove any traces of grease or dirt from the copper side of the plastic laminate board and then trace the circuit design on the copper (free-hand, if desired, but the wiring board shown in Fig. 2 can be transferred to the plastic sheet with ordinary carbon paper). After tracing, ink in the lines with either a commercial acid-resisting varnish (resist) or with ordinary shellac. A small amount of ordinary fountain ink can be added to the shellac to tint it so that the wiring will be clearly visible. Use a camel's hair brush to apply the shellac. (A special type of self-stick tape is also available for forming the wiring pattern, as are self-stick dots for making socket lug and terminal points.)

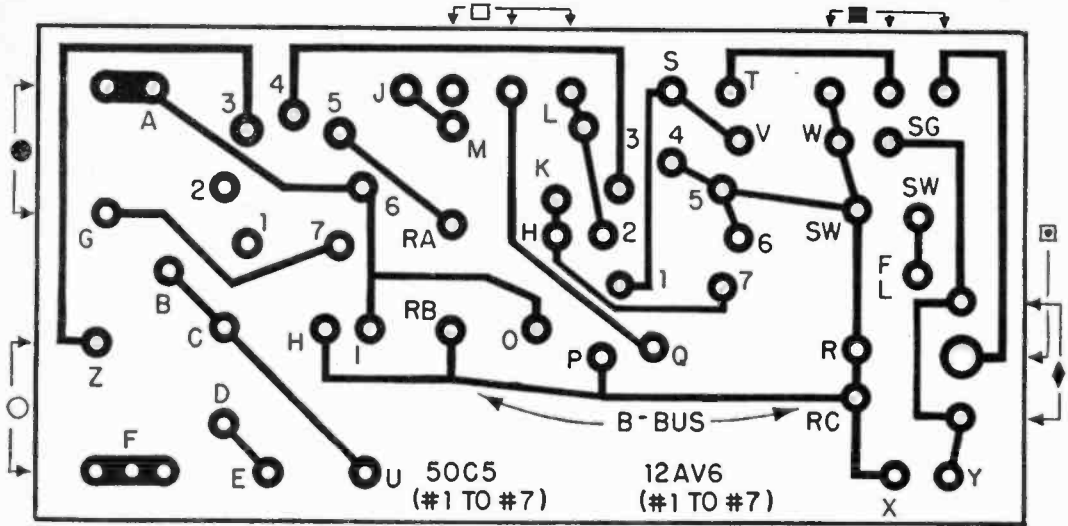

○ - TO 400 OHM, 10W. RESISTOR ● - TO OUTPUT TRANSFORMER AND SPEAKER
 □ - 10K TREBLE TONE CONTROL ■ - 500 K VOLUME CONTROL
 SWITCH ◻ - PHONO JACK CENTER PIN ◆ - PHONO JACK OUTER SHELL
 AND EXTERNAL GROUND


2

ETCHED COPPER-PHENOLIC WIRING BOARD

SHOWN ACTUAL SIZE

KEY TO WIRING BOARD COMPONENTS INSERTION

A to B —	390 ohm, 1-watt Resistor
C —	Rectifier Plus
D —	Rectifier Anode
E to F —	22 ohms, 1/2-watt Resistor
H to 50C5	Pin #1—150 ohms, 1/2-watt
A to G —	Output Transformer
I —	80 mfd. Plus
J to 50C5	Pin #7—470K ohms, 1/2-watt
K to 50C5	Pin #5—.1 mfd. Midjet
L to M —	.0015 Ceramic Disc Cap.
N to O —	220K ohm, 1/2-watt Resistor
P to 12AV6	Pin #2—3300 ohms, 1/2-watt
Q to R —	.1 mfd. Ceramic Tubular
S to T —	.05 mfd. Ceramic Tubular
U —	80 mfd. Plus (2nd section)
RC —	80-80 mfd. Common Negative
V and W —	5.6 megohms, 1/2-watt
X to Y —	.1 mfd. Tubular Capacitor
Z to F —	400 ohm, 10-watt Wirewound Res.
F to FL —	120v. Line Cord
SW to SW —	Line Switch on Volume Control
SG —	Ground to shell of Switch
RA to RB —	470K, 1/2 watt resistor

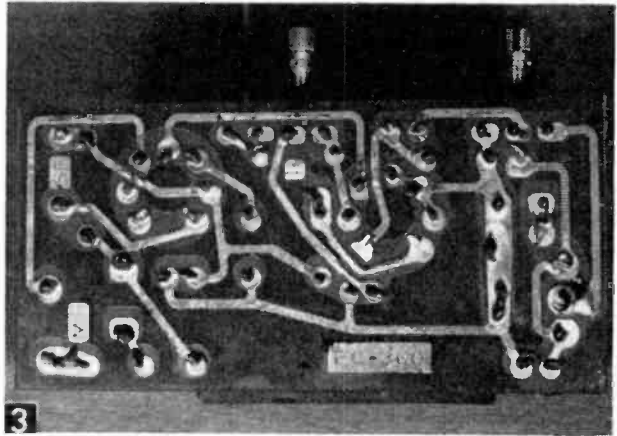

Electrical paths are unetched copper protected in acid bath by special masking tape or painted-on 'resist' such as shellac.

With the wiring layout completed, the next step is to etch the plate. Again, commercial printed circuit etchants are available, but the experimenter can "roll his own." The etchant is nothing more than ferric chloride (also known as perchloride of iron), a chemical you can get at any local photo engraving shop, professional pharmacy, or industrial chemical supply house. Dilute one part of ferric chloride with two parts water and pour just enough of this solution into a glass or plain china dish to cover the wiring board (copper side up). Allow the board to remain in the acid bath until all the unprotected copper has been etched (eaten) away. This process can be hastened by brushing the plate

gently while in the solution, and by using warm water.

When the plate is completely etched, remove it from the acid bath and thoroughly wash with household detergent. If tape resist has been used, peeling it off will reveal the bright copper "printed" circuit (see Fig. 3). If shellac resist is used, wash it off with denatured alcohol.

In the case of commercial wiring boards, component insertion holes are die-punched into the board after etching. The experimenter, however, drills the necessary holes, either before or after the etching operation. Holes into which resistor and capacitor pigtail leads are inserted are made with a 1/32-in. drill. Holes into which socket, po-

TABLE A—WHO AND WHERE TO WRITE FOR INFORMATION ON PRINTED CIRCUITS

- Centralab
A Division of Globe-Union, Inc.
900 E. Keefe
Milwaukee 1, Wisc.
- Cornell-Dubilier Electric Corp.
333 Hamilton Blvd.
South Plainfield, N. J.
- Erie Resistor Corp.
Erie, Penna.
- Sprague Products Co.
Marshall St.
North Adams, Mass.
- Photocircuits Corp.
Glen Cove, L. I., N. Y.

sary are silk-screen printed with an epoxy masking varnish. The sole purpose of this operation is that it saves a lot of solder. The experimenter's hand soldering, therefore, will not look unlike a factory job, because solder appears only at tie points.

You may have read that printed circuits should be soldered only with tiny, low-heat irons. Our own experience has been only with quick, high-heat soldering guns. We get sure, quick bonding of components to printed wiring and have never experienced any problems of foil loosening from the laminate. Good printed circuit solder is Kester "Resin Five" with a ratio of 60 parts tin to 40 parts lead. This solder (in the orange, not the red or green, box) is available in 25c packages at most hardware and radio shops.

Generally, components used in printed circuitry are the same as those used in conventional chassis designs with the exception of sockets and potentiometers. Even these items can be of the more conventional type, but those designed expressly for printed circuit boards mount more readily.

This phono amplifier has an output of about 2½ watts. A 12AV6 dual diode-triode detector is used as input amplifier with a 50C5 pentode serving as the power amplifier. These tubes are wired with a 400-ohm, 10-watt, voltage dropping resistor, external from the printed circuit. Instead of the resistor, you can connect a 95v. phono motor in the circuit and use it as the voltage drop. (See "Economy Record Player," page 80, for details of how this is done.)


When you test the completed amplifier, don't place it on a metal topped table or on a workbench strewn with small tools or bits of wire. The circuitry of this amplifier is exposed and prone to short-circuits from stray articles.

Complete, the amplifier is so light and compact that it will mount directly inside a speaker enclosure simply by drilling two ⅜-in. holes for the volume and tone controls. Space these holes 2½ in. apart.

Since the chassis is completely unshielded, solder a length of hookup wire from the line-switch shell to the isolated ground connection to prevent stray hum pickup. This external grounding point may also be used to deter possible hum if you connect the phono pickup arm and the frame of the phono motor to it.

ELECTRONIC CROSSWORD PUZZLE

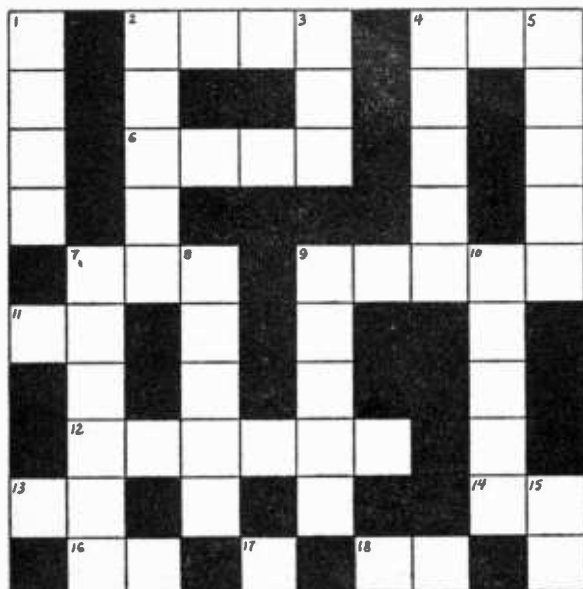Good at crossword puzzles? Here's one in which all of the words and abbreviations used are common in the field of electronics. On the right are the clues, see how well you do:



DOWN:

- 1) An element in a vacuum tube.
- 2) Unit of inductance.
- 3) An atom or molecule that has fewer or more electrons than normal.
- 4) A common term denoting a radio receiver.
- 5) A two-element vacuum tube.
- 7) The first man to demonstrate that electric current could be passed from a heated filament to a cold plate in a vacuum.
- 8) That which hypothetically fills space and serves as a medium for the transmission and reception of radio waves.
- 9) A positive element in a vacuum tube.
- 10) Radio interference.
- 15) A system used to address a large group of people.

ACROSS:

- 2) Abbreviation meaning the faithful reproduction of sound.
- 4) One of the three primary colors used in color television.
- 6) An inert gas that glows bright orange-red when ionized.
- 7) An organ of the body used when viewing television.
- 9) A common expression meaning telephone.
- 11) An abbreviation meaning long-distance, spelled backwards.
- 12) The outside covering of a shielded transmission line.
- 13) With the addition of one letter, the abbreviation of logarithm.
- 16) An abbreviation meaning wires are not connected.
- 17) The letter symbol for current flow.
- 18) Abbreviation for a type of phonograph record.

For solution, see page 97.

The RED HOT

A simple economical portable that packs a BIG wallop

By FORREST H. FRANTZ, SR.



Small enough to slip into your coat pocket, the Red Hot has excellent sensitivity and selectivity and plenty of power.

Here's that economical, power-packed pocket portable you've been looking for. Measuring only 1¼ x 3¼ x 4 in., this set has loudspeaker power and is extremely sensitive and selective. What's more, no pick-up lead of any kind dangles from the set and its design is simplicity itself.

If you're wondering how a two-transistor set can pack the kind of wallop the Red Hot does, here are the reasons. In the first place, it uses entertainment grade transistors. Though better in quality than experimenter grade transistors, entertainment grade transistors cost only a little more. The GE 2N168A transistor, for example, has a much higher cut-off frequency than the experimenter types of the AF and RF varieties, an important consideration when the transistor is to be used as an RF amplifier. And the GE 2N192 transistor, used in the output stage, has a higher beta (current gain or amplifying capacity) than the experimenter grades.


With good transistors as basic ingredients, the design determines how well a piece of transistorized electronic gear will perform. To get plenty of gain in the Red Hot, T1 (see Fig. 2) is used to amplify the signal twice. With this "reflex" technique, T1 amplifies the received signal while it is still in the radio frequency form, and then again when it is in the audio frequency form after detection

by diode D. The audio output of T1 is introduced to the base of transistor T2 through the audio driver transformer L4. The better impedance match between T1 and T2 given by L4 provides considerably more gain than you can expect from resistance-capacitance coupling.

Another feature contributing to the gain is that there's positive feedback in the RF stage. It's not apparent from the circuit, and it's not enough feedback to make the set oscillate, but there is feedback, resulting from the relative placement of the components in the case. This feedback feature and the high Q of the antenna coil (L1) make the set quite selective in spite of the fact that it has only one tuned circuit.

Cost of the Red Hot is about \$15 (and the four penlite cells used last a long, long time). You can construct the set in six to 20 hours, depending upon your experience. An expert might even do it in less than six hours. To make the construction go smoothly and quickly, obtain all of the parts in advance (see the Materials List), have the required tools handy, and go over the instructions a time or two before you actually begin work.

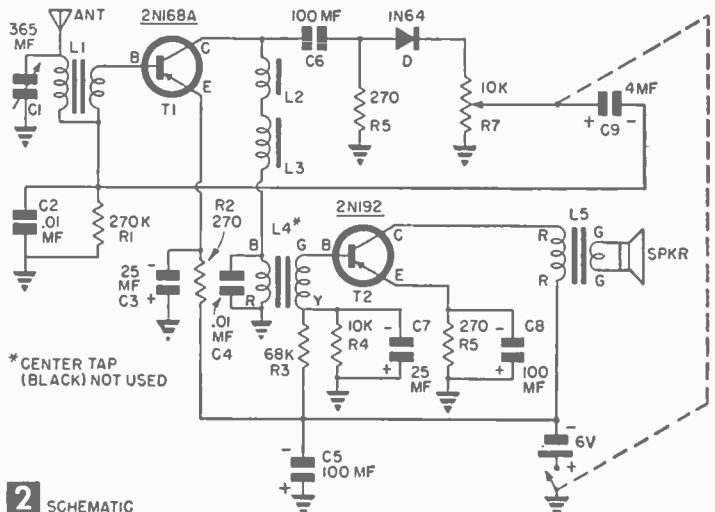Construction. You'll need 1) an ice pick; 2) a hand drill; 3) a ⅛ in. dia. drill bit; 4) a hand taper reamer; 5) a measuring scale or tape; 6) a hack saw; 7) needle nose pliers; 8) diagonal (cutting) pliers; 9) small screwdriver



*CENTER TAP (BLACK) NOT USED

2 SCHEMATIC

(blade about $\frac{1}{16}$ in. wide); 10) medium size screwdriver (blade about $\frac{3}{16}$ in. wide); 11) small soldering iron; 12) tin snips.


Mounting holes are required in the plastic case for 1) the antenna coil, L1; 2) the output transformer, L5; 3) the tuning capacitor, C1; 4) the volume control, R9; 5) the battery holder; 6) the loudspeaker (Spkr.). Sound holes are also required for the loudspeaker. Figure 3 shows the positions and the dimensions of these holes in the plastic case.

Mark off the hole positions on the case, then heat the ice pick and use it to make holes in the case on the marked centers. Don't get the ice pick red hot or it will melt the plastic too fast and make the work difficult. Make the holes just big enough so that the hand taper reamer can be made to bite in without difficulty. When all pilot holes have been made with the hot ice pick, allow the melted plastic around the holes to harden. To assure yourself that the holes are properly located, place the components over the appropriate holes. If necessary, use the hot ice pick to relocate centers. After you're sure of the hole center locations, enlarge all the holes to size with the taper reamer with the exception of the loudspeaker sound holes. These are closely spaced and you might get into difficulty trying to ream them out smooth, so leave them rough.

When you've completed this work, wash the case with soap and cold water to remove dirt and finger prints. Rinse in clear cold water and dry.


If you want to paint the interior of the case, do it now. Spraying will be more effective than brushing since the paint may run—particularly around the speaker sound hole openings—if you brush paint.

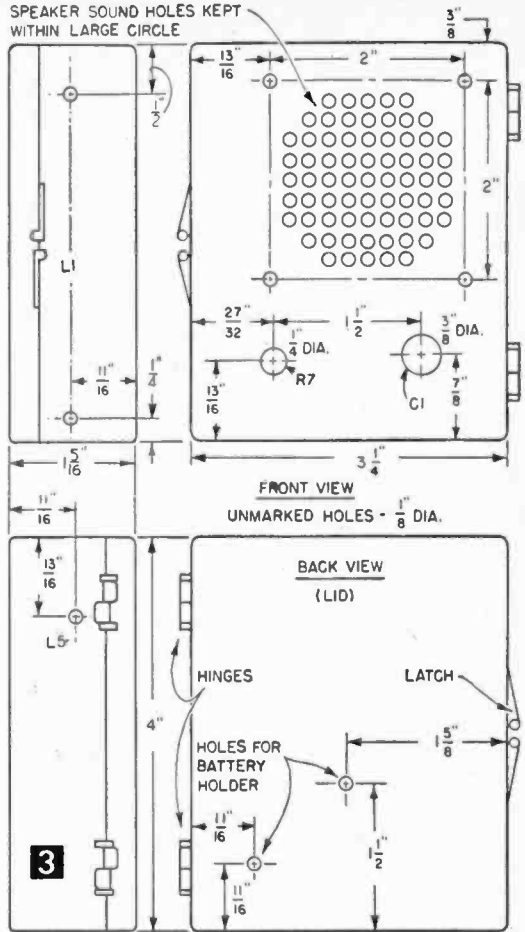Now, cut the volume control (R7) shaft to a length of $\frac{1}{4}$ in. and the shaft of the tuning capacitor (C1) to a length of $\frac{3}{8}$ in. Remove five turns from the tuning coil (the end of L1 with many turns), and one turn from the transistor input



coil (the end of L1 with few turns). Remove the coil from the Masonite mounting base to do this. (Simply take off the tape which is wrapped around each end of the coil). When

4 PICTORIAL

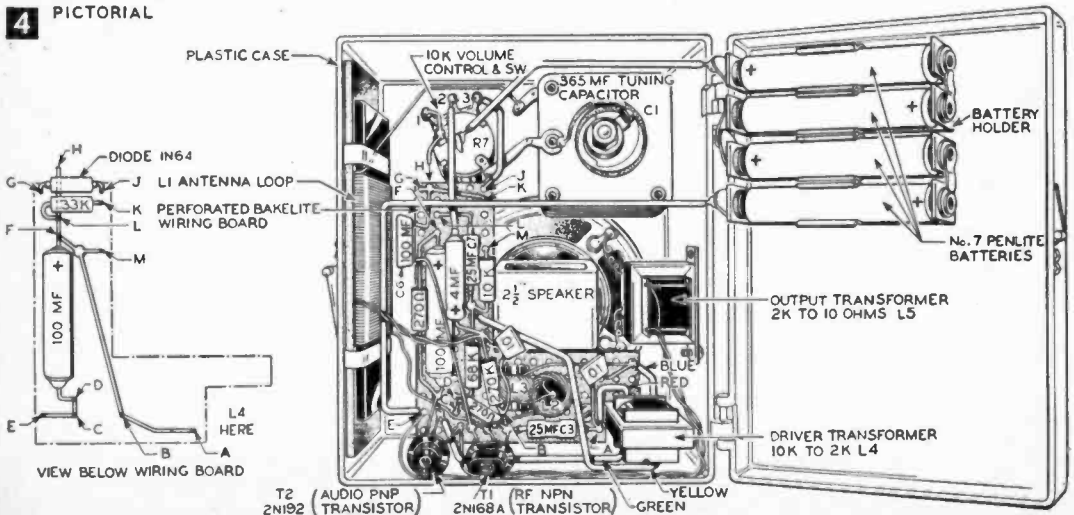


MATERIALS LIST—THE RED HOT

R2, R5	270 ohms	} 1/2 watt, carbon resistors, 10% tolerance
R4	10K ohms	
R6	33K ohms	
R3	68K ohms	
R1	270K ohms	
R7	10K miniature volume control with switch (Lafayette VC-28)	
C1	365 mmfd tuning capacitor (Lafayette MS-215)	
C6	100 mmfd miniature ceramic capacitor (Centralab DM-101)	
C2, C4	.01 mfd 75v miniature ceramic capacitor (Lafayette C-612)	
C9	4 mfd 6v miniature electrolytic capacitor (Lafayette CF-101)	
C3, C7	25 mfd 6v miniature electrolytic capacitor (Lafayette P6-25)	
C5, C8	100 mfd. 6v miniature electrolytic capacitor (Lafayette CF-106)	
D	diode (GE 1N64)	
T1	RF NPN transistor (GE 2N168A)	
T2	audio PNP transistor (GE 2N192)	
L1	flat ferrite antenna loop (Miller 2004)	
L4	driver transformer 10K to 2K (Lafayette TR-96)	
L5	output transformer 2K to 10 ohms (Lafayette TR-93)	
SPKR	2 1/2" loudspeaker (Lafayette SK-66)	
1	battery holder (Lafayette MS-170)	
4	batteries (#7 penlite cells)	
1	miniature knob (Lafayette MS-185)	
1	small pointer knob (Smith 2220)	
1	plastic case 1/4 x 3/4 x 4" (Lafayette MS-298)	
1	perforated Bakelite wiring board (Lafayette MS-304)	
L2	25' 7/41 litz wire* jumble-wound on 3/4" length, 1/4" diameter ferrite core	
L3	15' 7/41 litz wire* jumble-wound on 1/2" length, 1/4" diameter ferrite core	

(Apply a coat of Duco Cement to hold windings of L2 and L3 in place.)

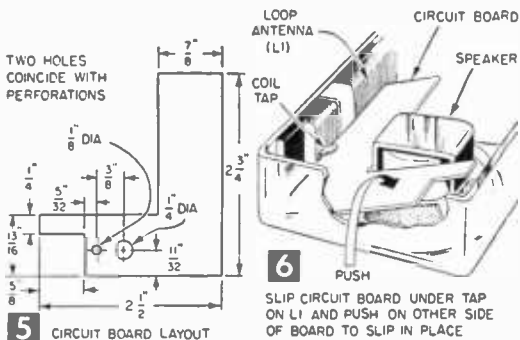* A 7 1/2" long core (MS-331) and 100' of litz wire (Belden 8817), more than enough for these coils, may be obtained from Lafayette Radio, 165-08 Liberty Avenue, Jamaica 33, N. Y., source for all of the components in this radio.



you've removed the turns, leave about 3 in. lead lengths on each end, providing connections at the lead ends by stripping off about 1/2 in. of the cotton insulation. Rub the lead ends gently with very fine sandpaper to partially remove the enamel insulation from the individual strands, being careful not to break any of the strands. Then, using a hot iron and rosin core solder, heat up the lead ends and apply solder while rubbing the iron back and forth along the ends. Continue until you've burned off the enamel and the coil ends look shiny and well tinned. Replace the coil on the Masonite mounting strip and fasten in place with the original tape.

Next, make L2 and L3. Both of these coils are wound on short lengths of ferrite core. Dimensions, type of wire and winding data are given in the Materials List. Cut the lengths of ferrite core from the 7 1/2-in. length by notching the core material with a hacksaw or file and then breaking it off. Or you can try to saw it off all the way.

Mounting Coil Components. Fasten the loudspeaker in the case with 4-36 x 1/4-in. machine screws and nuts. Terminals should be along the hinge side of the case (see Fig. 4). Then mount the volume control (R7), the tuning capacitor (C1), output transformer (L5), antenna coil (L1), and the battery holder. Place two thicknesses of electrical tape along the edge of C1 that will be behind the edge of the loudspeaker and be sure to slip a lockwasher on the bushing of C1 before you mount it. Otherwise it may short-circuit through the loudspeaker frame.

When you fasten the battery holder to the back of the case, stick the screws through from the battery holder side and fasten the nuts on the outside of the case. If the nuts are fastened against the battery holder, they may puncture the insulating paper cover on the batteries and short circuit them through the holder's frame. The connecting lugs on the holder should be bent down to allow clearance to close the case.

Mount L5 with the 10-ohm winding connections toward the loudspeaker terminals. Don't uncoil these leads; connect them to the terminals of the loudspeaker before you fasten the transformer in place.

Finally, wire these components in the case. Note that the connection between the switch and volume control lugs is also soldered to the volume control frame, too.

Wiring the Circuit Board. Cut and drill the perforated circuit board according to the layout of Figure 5. Use a hacksaw to do the cutting, smoothing the edges with a file. Drill the holes with a 1/8-in. drill, and use a taper reamer to enlarge to the 1/4-in. hole. Try the board in the case for fit. It should fit between the upper edge of the case and the speaker, and the antenna coil and the speaker with the antenna coil tap above the circuit board. Insert the board as shown in Fig. 6 to check the fit. If it doesn't fit, file the edges of the board as required. The fit should be tight. When you're sure you have a good fit, remove board and mount components.

When you mount the driver transformer (L4) be sure to place the mounting flange of the transformer on the underside of the circuit board or you'll find it impossible to close the lid on the receiver after assembly. The other transformer mounting flange is bent down to allow the circuit board to fit in the case.

Connections are made by pushing lead pigtails through the perforations in the board. The long lead on the bottom of the board that runs around most of the board is the common return and it is formed from the extra length of lead pigtails

that remain after the parts are mounted on the board. The short straight lead on the bottom of the circuit board to which the negative end of C5 is connected is the battery negative bus. All parts except the transistors and C6 and C9 are mounted tight against the circuit board. A $\frac{1}{8}$ in. space is left between the transistor bottoms and the circuit board to prevent straining the leads and to keep heat transfer to the transistors during the soldering process within reason.

Mount L2 by applying a small amount of Duco cement to the core and inserting it in the $\frac{1}{4}$ -in. hole on the circuit board. Apply a very small amount of Duco cement to L3 and fasten it perpendicular to L2. Don't use too much Duco for this because you'll have to loosen L3 later. Be sure that L2 and the other components do not extend more than $\frac{5}{8}$ in. above the top of the circuit board. If they do, you may have trouble closing the lid of the case after assembly. None of the components, with the exception of the output transformer (L5), should protrude beyond the edges of the circuit board because the circuit board will be held in place by the tight fit between it, the loudspeaker, the edge of the case, and the antenna coil.

Final Assembly. There are eight connections which will have to be made from the circuit board to components in the case. They are, in order of connection: 1) collector of T2 to primary of L5; 2) negative bus to primary of L5; 3) base of T1 to end of short winding on L1; 4) junction of C2, R1 and C9 to tap on L1; 5) common return to switch; 6) plus terminal of C9 to center terminal of R7; 7) K terminal of D to upper terminal of R7; 8) negative line to negative terminal of battery.

The first three connections must be made before the circuit board is mounted in the case. After they're made, place the edge of the circuit board against L1 but below the coil tap as shown in Fig. 6, and push the board into place in the case. Then, make the other five connections.


Now close the lid, and move parts and leads as required to allow easy closing. You may find that the back of the loudspeaker interferes with complete closure of the lid. If it does, trace the outline of the speaker magnet frame on the lid of the case and make a tool from a piece of sheet metal (which can be cut out of a tin can) as shown in Fig. 7. Grip the hold flange of this tool with a pair of needle nose pliers, heat the tool slightly, and apply it to the inside of the case lid along the magnet frame tracing using a small amount of pressure. This will dent the lid slightly to allow it to close over the speaker magnet frame without interference. It's wise to do this several times if necessary, starting with low temperatures. Otherwise, you may get the tool too hot and damage the case.

Now you're ready to insert the batteries. Do this cautiously with the switch in Off position and be sure to position the plus and minus terminals properly. Do not let the clips on the

holder cut through the insulating paper cover on the batteries.

If you have a milliammeter, connect it across the switch terminals (plus meter terminal to battery side of switch) with the meter on a range of 100 *ma* or more. The meter deflection should be less than 10 *ma*. If it's more than 10 *ma*, start looking for trouble, perhaps an error in wiring, an incorrect resistor, reversal of capacitor polarity, short circuits, or similar mistakes. (Occasionally, you may run into trouble due to bad components; this occurs so rarely if all new components are used, however, that this possibility

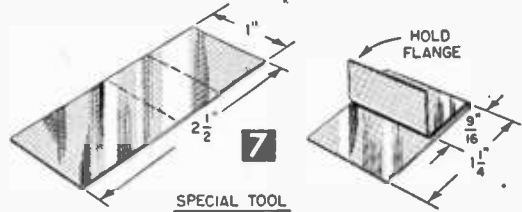CUT STRIP OF SHEET METAL AND BEND AS SHOWN



should be dismissed till the circuit has been checked several times). If the meter reads less than 10 *ma*, switch to the range nearest 10 *ma* (but not less than 10 *ma* on your meter). You should get a reading of 6 *ma* or less. On my set the reading was 4 *ma*, but tolerance variations in transistors and other components might allow variations in current from about 3 to 6 *ma*. You can expect long battery life with such a small current demand.

Next, turn the set on and try it out. If it squeals at the high frequency end of the dial, move C6 away from L1 a small amount at a time till the squeal is eliminated. Some feedback between C6 and L1 is desirable for maximum sensitivity, but if there's too much feedback, squealing may occur. The feedback is increased by moving C6 closer to L1, decreased by moving C6 away from L1.

The orientation of L3 also affects feedback. The contribution is most noticeable at the low frequency end of the dial. The axis of L3 should be parallel to L1. To find the correct orientation for this coil, tune in a station on the low frequency end of the dial and note the volume level. Then break the Duco cement bond between L2 and L3 and reverse the positions of the ends of L3. Retune the set to the station for maximum volume. If the station comes in louder, fasten L3 in this position with Duco. If the volume decreases, however, return the coil ends to their original positions and re-cement.


Although this little set is one of the hottest performers I've seen with such a simple circuit configuration, a little additional experimenting with the orientation and positions of L2 and L3, can make it even more sensitive and selective. Since no external pick-up lead is used, this set is highly directional. The antenna coil must be horizontal; rotate the set in a horizontal plane for best pick-up.

Component Color Codes


Color	1st Digit 2nd Digit	Multiplier	Res. Tol.	Cap. Tol.	Cap. Volts
Black	0	None
Brown	1	0	1%	100
Red	2	00	2%	200
Orange	3	,000	3%	300
Yellow	4	0,000	4%	400
Green	5	00,000	5%	500
Blue	6	,000,000	6%	600
Violet	7	0,000,000	7%	700
Grey	8	00,000,000	8%	800
White	9	,000,000,000	9%	900
Silver	10%	10%	...
Gold	5%

RETMA COLOR CODE STANDARD


POWER TRANSFORMERS

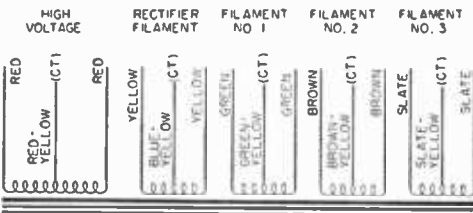


A.F. TRANSFORMERS

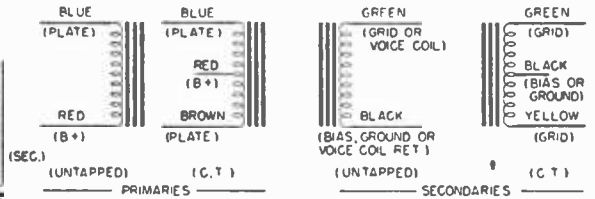


RESISTORS

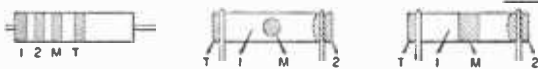


I.F. TRANSFORMERS

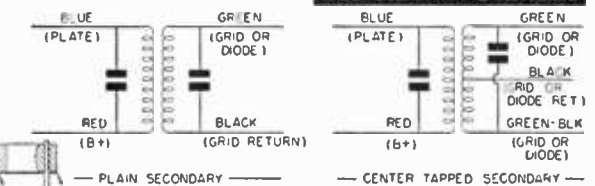

MOLDED PAPER CAPACITORS

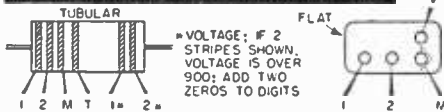


MOLDED MICA CAPACITORS

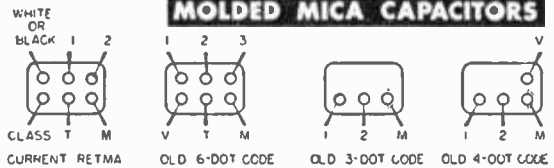


TRANSISTORS

E - EMITTER
B - BASE
C - COLLECTOR

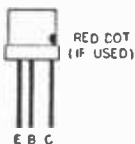


CODES

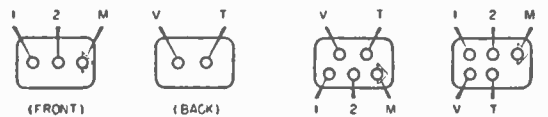- 1 - 1ST DIGIT
- 2 - 2ND DIGIT
- 3 - 3RD DIGIT
- M - MULTIPLIER
- V - VOLTAGE
- T - TOLERANCE



VARIATIONS IN OLD 5-DOT CODES

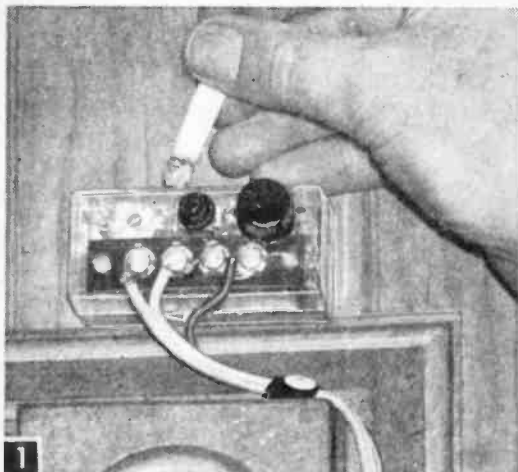

Midget bell system powered transistorized alarm unit can be set with aid of cigaret to trigger alarm the instant room temperature rises above normal.

Transistorized Fire Alarms

IF YOUR family members are worth more to you than \$10 and a little spare time, you'll be interested in these transistorized fire alarms.


The transistor sensing elements in these alarms are more reliable than fusible or link type elements—even with wide fluctuations of line voltage. Moreover, they can be set to react at any range from 68° to 170° F.

In the alarm shown in Fig. 1, the house bell system is used both for power and for the alarm itself. In the other version (Fig. 2), a bell and bell transformer are made part of a self-powered design. The fire alarm sensitive elements in both types of units should be mounted near the ceiling as in Fig. 2 or at the top of an open staircase.

Self-Powered Unit. Since the self-powered unit is a complete system, we'll describe its circuit construction and operation first. In Fig. 3B, plug P1 supplies 110-volt a-c to bell transformer TR1; secondary voltage is rectified by diode D1 to furnish d-c of about 15 to 18 volts filtered by capacitor C1.

Power supplied to the collector (C) of the transistor passes through the coil of a sensitive relay, factory-adjusted to pull in at a current of about 1.5 ma. When the relay pulls in (dotted line position of relay arm, Fig. 3), the circuit is closed to the bell and the bell rings.

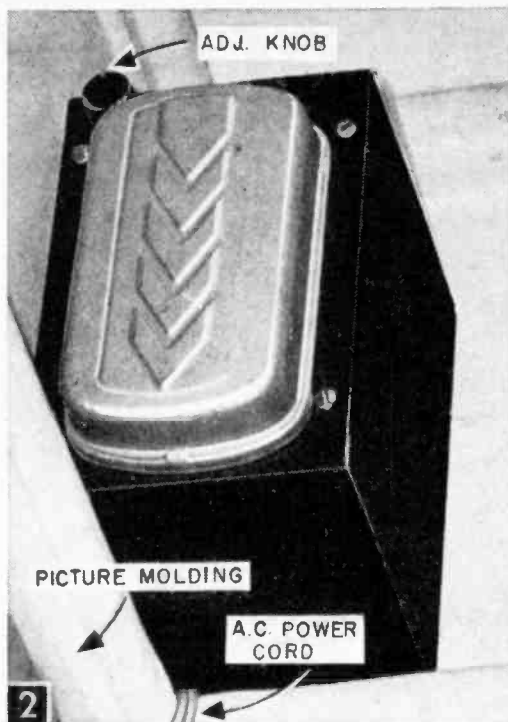In contrast to the transistor, the bell draws considerable current. This reduces the amount available for the relay, causing it to drop out and remove the bell from the circuit, thereby pulling the relay back in. A pulsating alarm sig-



Self-powered alarm unit is independent of house bell system, can be wired to operate auxiliary devices such as fire gong or extinguisher.

nal results then, when the alarm is actuated by heat in excess of its setting.

The current drawn by the transistor collector through its collector-base-emitter circuit is controlled primarily by the resistance in its base circuit and by the room temperature. Base current is limited by resistor R1 and potentiometer R2. Potentiometer R2 is set so that current to the relay has it ready to pull in if room temperature exceeds normal, as in case of fire, when the collector current to the relay would increase; the relay energizes; the alarm bell rings.

Capacitor C2 helps to hold the relay in longer, once in, and also to prevent premature pull-in. Resistor R1 prevents transistor damage should potentiometer R2 accidentally be turned all out.

The self-powered unit is housed in a standard metal utility cabinet with built-in chassis. Wire as in Figs. 3 and 4. For parts layout simply use the components as templates. Do *not* solder to the transistor socket with the transistor in place. Before pushing the transistor into its socket, cut the long leads to a length of about $\frac{3}{8}$ in. and make sure that these are straight.

Bell System Powered Unit. As shown in Fig. 6, only three wires are needed to connect this system to a typical house doorbell and door opener circuit. Two line wires (L1 and L2) furnish input power; S1 and S2 terminals are wired across the pushbutton (one side of the line is also one side of the pushbutton connection). The alarm connections themselves are the same as those for the

self-powered system as shown in the boxed area, Fig. 3. Closing of the relay contacts is the same as pushing the doorbell pushbutton. Use heavy wiring (not less than the standard #18 bell wire) to prevent excessive voltage drop in the wiring from the unit to the bell system.

Wire as shown in Figs. 6 and 7. Mount the terminal strip first, close to the edge of the case, then position the relay, and scribe and drill a center for it.


Don't mount the relay at this time, but position and drill holes for the transistor socket, finishing the cutout with a file, and mount the socket with retaining ring. Next drill the hole for potentiometer R2 and mount it, mount a terminal lug under one of the Bakelite terminal mounting screws to serve as a tiepoint for the power supply negative potential.

First, wire in resistor R1 and the lead from R2 to the negative tiepoint, then wire the lead from the emitter terminal of the transistor socket to the line terminal L2 and solder in place along with capacitor C1's positive lead. Note that the polarity is marked on the case.

Next, install the germanium diode, once again observing polarity; soldering the + end (also la-

3



SCHEMATIC SELF-POWERED UNIT

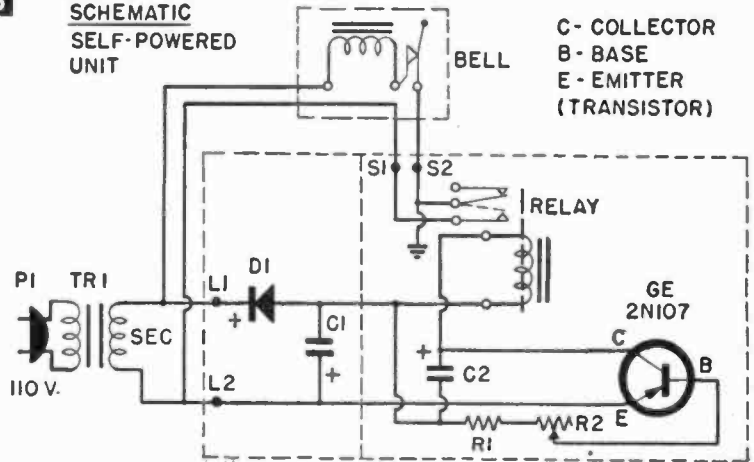

beled "K" or indicated by a symbol) to the L1 terminal on the Bakelite strip. Run an insulated lead from the nearest relay coil terminal to the minus tiepoint and solder it in place. Use a pencil type iron and make all connections to the capacitors and to diode D1 rapidly. Mount the relay with its screw, and solder the + end lead of capacitor C2 to the remaining relay coil terminal and the collector lug of the transistor socket.

Now insert all leads going to the negative (-) tiepoint into the lug hole and solder them. Run a wire from the normally open contact of the relay to the S1 terminal post and solder both of these points. Then connect a wire from the lug on the frame of the relay (near the retractile spring) to the S2 lug on the terminal strip. Take care to insure that the motion of the spring is not altered and that solder does not get into the armature hinge.

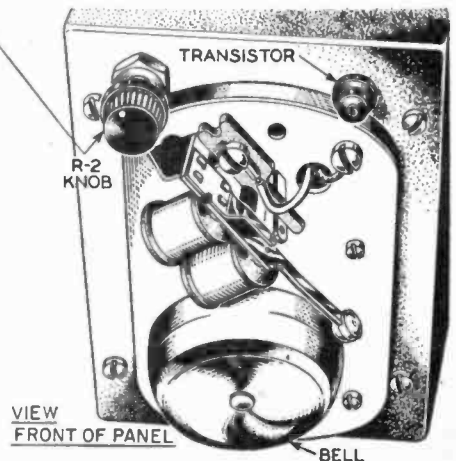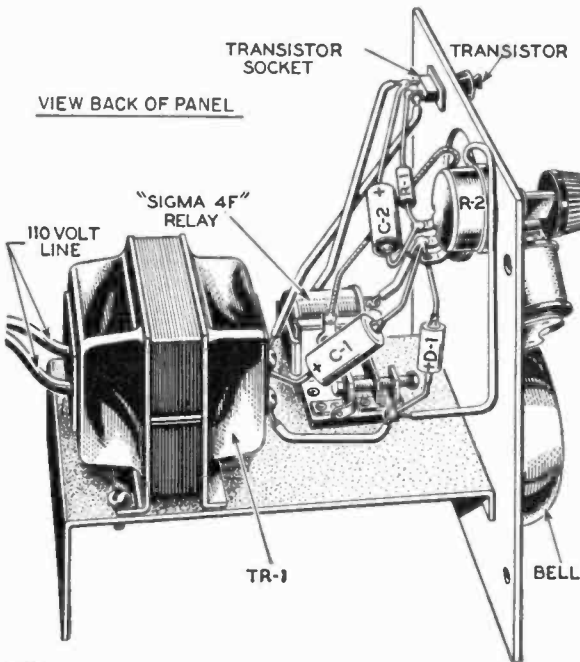Adjustment of Units: After construction is completed, mount unit as shown in either Fig. 1 or Fig. 2 (depending upon which type you have made) and screwfasten in place. Plug in the self-contained unit or make connections to the bell sys-



4 SELF-POWERED UNIT PICTORIAL

tem for the bell system powered unit and test for operation by turning the adjustment knob clockwise to the point where the bell rings. Then turn it back. The distance you turn it back will depend upon the room temperature; the adjustment knob must be backed off to prevent false alarms.

Hold a cigaret for one minute about 1 in. from the transistor of the unit (Fig. 1). Adjust the knob so that the alarm will just turn on about 15 seconds after the cigaret is removed if you're using a 2N107 transistor, or a full minute for the CK722 type transistor. Manipulate adjustment knob in this test interval for a fine setting.


A more exact method of adjustment employs a strip of iron to which a thermometer has been strapped. Heat the iron to the desired turn-on temperature plus 10°. Then touch it to the transistor case and adjust the knob to turn on at that temperature.

Auxiliary devices such as a fire gong or fire extinguisher can be operated by a power relay actuated by the sensitive relay of the alarm unit. Connections are made as shown in Fig. 5. The power source is appropriate to the device used.

Both types of alarm units may be paralleled to operate at different locations. Standby current drain of bell-powered units is so low (about .025 watt from bell transformer) that 20 units draw less than an electric clock. Each alarm unit has the low voltage a-c power supplied to its L1, L2 terminals and its relay terminals paralleled across the pushbutton.

Self-powered units can have their relay contacts paralleled in the same manner to ring a single bell (bell on each unit is then omitted), or, they too can control another, heavier duty relay as in Fig. 7. As another alternative, several system units can be supplied with input power from one self-powered unit, taking a-c low voltage directly from bell transformer secondary.

—JAMES A. McROBERTS.

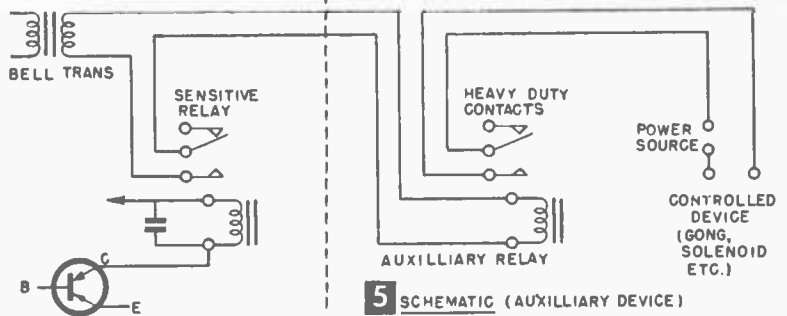


MATERIALS LIST—TRANSISTORIZED FIRE ALARM SYSTEMS


- Relay Jewel or Argonne R/C AR-21 (Lafayette F 260)
- D1 1N64 germanium diode (1N34 can be used)
- C1 electrolytic capacitor, 50 mfd., 25 v.
- C2 electrolytic capacitor, 10 mfd., 15 v.
- R1 resistor, 10,000 ohms, 1/2 watt
- R2 potentiometer, miniature, 1 megohm with knob (Lafayette VC-38; MS 185 knob)
- 2N107 transistor, G. E.; (or CK722) transistor with socket
- 4-terminal mounting strip (Lafayette MS 229)
- Plastic case, 1 x 1 3/16 x 2 7/8" (Lafayette MS 167)

- Additional parts for Self-powered Unit**
- Bell transformer, (Snapit Cat. #2302)
 - Edwards doorbell
 - Sigma 4F relay (instead of Argonne)
 - ICA #3819 metal utility cabinet, 4 x 5 x 6", with built-in chassis (instead of plastic case)
 - electric light cord and plug

6 BELL SYSTEM POWERED UNIT SCHEMATIC

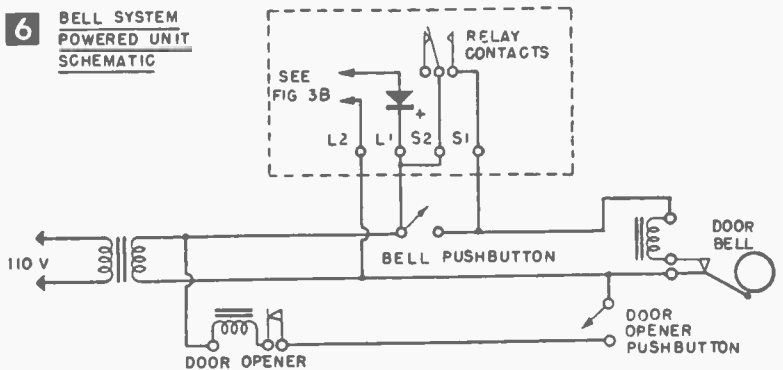

7 BELL POWERED UNIT PICTORIAL

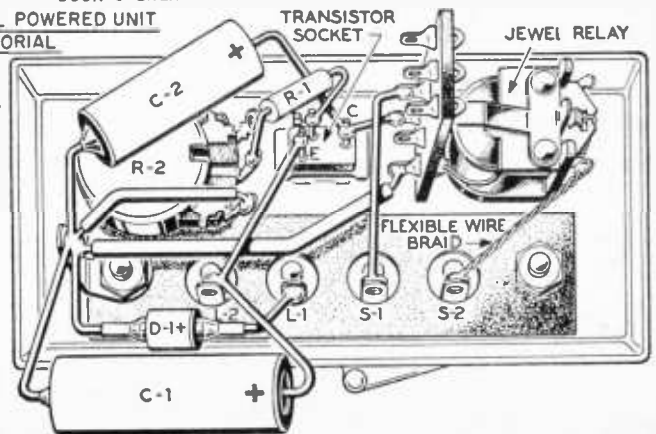

Listen with a Transducer

By T. A. BLANCHARD

HERE is a neat little transducer that can be applied to any type of headphone, or headset. You will hear everything—even a faint whisper—bell clear, without any earphone over the ear. Moreover, the system can be practically invisible, if for example, you might presently use a hearing aid.

The phone attachments shown here are generally known as *transducers*, coined from transmitter and *reproducer*. The sound waves generated by the moving diaphragm of a headphone, instead of going directly into the ear canal, travel through a light and very flexible vinyl plastic tube. This tubing is nothing more than a wire insulation known and sold as *radio spaghetti*. All radio suppliers have it in various diameters and colors including transparent types. Single headphones of all-plastic construction make excellent *transducers*. Remove the phone cap, and diaphragm. Drill a $\frac{3}{32}$ in. hole in the back of phone (B). Into this hole insert a suitable length of $\frac{3}{32}$ in. vinyl tubing; allow to project inside the receiver about $\frac{1}{8}$ in. Secure with several drops of Duco cement. Do not plug up the tube opening.

Replace diaphragm and cap on receiver, attaching a piece of Scotch electrical tape over the cap to seal the sound perforations or hole. Sound waves are generated both from the front and back by an earphone diaphragm. The vinyl tubing coming out of the back of the case provides the most convenient method of installation.

The molded eyelet in earphone case (C) provides for attaching the phone to your person. Solder a small safety clasp to a bead key chain




so the *transducer* may be pinned to lapel or shirt. Or, thread a shoestring through the eyelet, and wear the reproducer around your neck. Insert end of vinyl tubing just inside the ear, then loop behind the ear where it will remain without falling out. If you prefer an earpiece, make one as shown (D).

A universal *transducer* may be constructed to fit any type headset without altering phones. Cut off a suitable length of radio spaghetti, and obtain 2 eyelet type rivets about $\frac{1}{2}$ in. long and with a dia. that will allow tubing to make a tight fit either inside or over the eyelet. In the center of a $1\frac{1}{8}$ sq. in. tire patch, pierce a hole, leaving the starched cloth backing in place. Next step in construction is to force an eye-

let into the hole, and then slip on tubing.

Slip a rubber radio grommet designed for a $\frac{1}{4}$ in. hole on the longer earpiece eyelet. Wind a narrow strip of Scotch tape over the flanged end of eyelet so grommet makes a tight fit. Finally attach the remaining end of tubing.


To attach to headphone, apply rubber cement to phone cap and allow it to set. Strip off cloth backing on tire patch and position over opening in earphone. It will remain attached indefinitely. Headphone set may be laid on a table, or hung around neck by headband spring. Rubber grommet makes a perfect little earpiece. A double set of transducers can be made, one for each phone, but volume is usually so good that a single unit is ample. Rubber grommet, eyelets, and vinyl tubing are stocked by all radio suppliers. Eyelets usually come in packages of assorted sizes. Leathercraft supply shops, harness shops

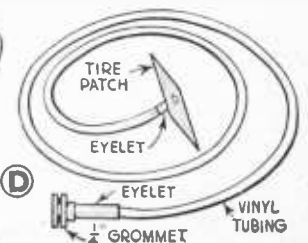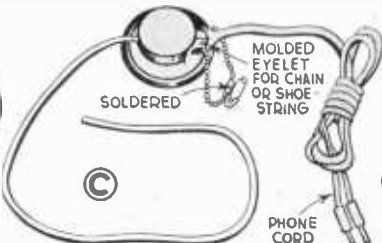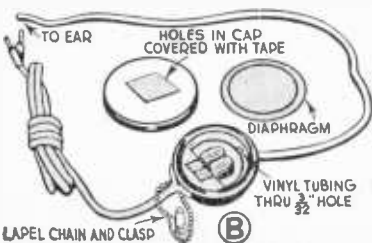

(if you can find one these days) and hardware stores also have them.

Users of hearing aids may adopt this system with ease. Check the diameter of the opening in

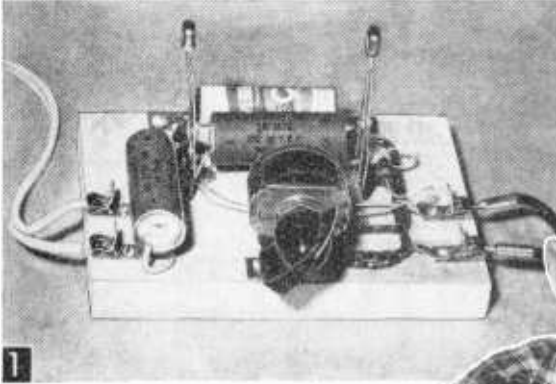earpiece. Obtain a piece of clear tubing that will provide a snug fit inside the earpiece. Tubing may be worn with or without rubber earbutton; place earphone in the shirt pocket.



Left, closeup showing transistors in place. Amplifier may be used with single or double headphones of 2,000 ohms or more, and it will serve as detectophone or a stationary hearing aid. Below, a 4-in. PM speaker and output transformer mounted in cabinet at left makes a wide range dynamic mike for this tiny but powerful 2-stage transistor amplifier.

THIS simple breadboard layout will show you how you can adapt transistors to audio frequency amplifiers. In fact, the completed setup shown in Fig. 1 will serve you as a very sensitive detectophone and will pick up voice and music with surprising clarity and volume.

While transistor hearing aids use transformer-coupled amplifiers which provide somewhat greater gain and less distortion, we have found that the simple, inexpensive resistance-coupled circuit is excellent for experimental purposes. Moreover, its components are available at all radio parts suppliers, whereas few dealers stock the expensive sub-miniature components employed in hearing aids.

Vacuum tubes have high impedance inputs allowing crystal mikes or pickups to provide the grid signal. Transistors, on the other hand, have low impedance inputs making crystal mikes impractical. Transistor hearing aids, therefore, use a miniature moving coil magnetic mike known as the dynamic type, which is not easy for you to obtain at this writing. But your mike problem is easily solved by using an ordinary 4 or 5-in.



Transistor Amplifier

Powered with just a penlite battery, this 2-stage amplifier demonstrates how to use transistors in a sensitive detectophone

By THOMAS A. BLANCHARD

PM speaker and a regular 2500-ohm output transformer. In this case, the output transformer is used as a "mike-to-grid" input transformer.

Although this amplifier can be reduced to less than half the size shown in Fig. 3, the 3½ x 5-in. baseboard mounting allows the parts to be 100% salvaged for re-use in other experiments. The two three-lug solder tie strips, mounted on the baseboard with ½-in. rh wood screws, serve to tie down resistors and capacitors as well as pro-

vide three lug points for terminating the transistor pigtail leads. Input and output amplifier connections are simple Fahnestock clips also secured to the base with 1/2-in. rh (round-head) wood screws. For the volume control mounting, use a window shade bracket with the 1/8-in. pin hole drilled out to 3/8 in. to take the threaded control bushing. Two small tin or copper brackets screwed to the base provide a mounting clip for the penlite battery which powers the amplifier.


When wiring up the amplifier (Figs. 2 through 4), the transistors are not installed until the unit has been completed. When installing the transistors, hold a tiny wad of damp cotton on each pigtail lead to block transmission of soldering heat up into the transistor elements. Never apply heat to or near the transistor's metal jacket.

The transistor pin arrangement shown applies to units in current production. Some transistors may differ physically, so follow the instruction sheet furnished for the location of C (collector), B (base) and E (emitter). The RR-38 transistors shown here have dual purpose leads allowing direct pigtail connections. Or, with the leads cut short, transistors may be plugged


MATERIALS LIST—TRANSISTOR AMPLIFIER

- 1 pc. wood about 5 by 3 1/2 by 5/8 in. for breadboard base
- 1 4 or 5-in. PM speaker
- 1 2500-ohm output transformer (commonly called 50L6 type)
- 2 RR-38 or CK-722 transistors or other P-N-P junction type
- 1 pair magnetic headphones, 2,000 to 4,000-ohms impedance
- 2 C-D (or equivalent) electrolytic capacitors, 20 mfd. 25 d-c w.v.
- 2 220K (220,000-ohm) 1/2-watt composition resistors
- 1 10K (10,000-ohm) 1/2-watt composition resistor (see note below)*
- 1 10K Mallory or IRC linear potentiometer (volume control)
- 1 bar pointer knob for above
- 4 Fahnestock clips
- 1 window shade, brackets, wood screws and hook-up wire

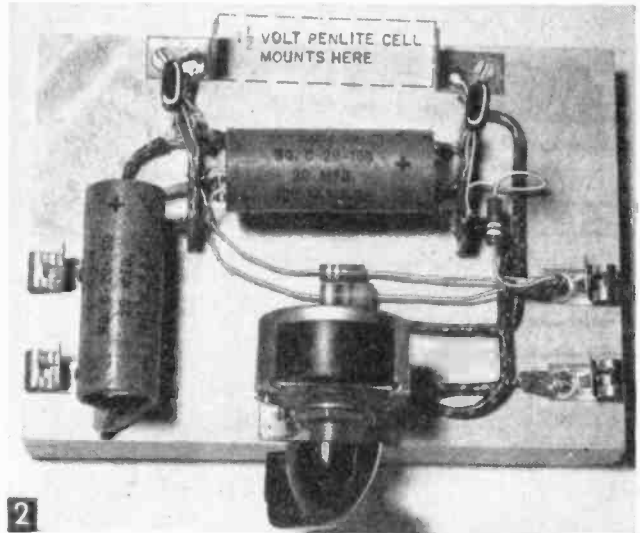*Some transistors may require more collector current. If amplifier fails to work, switch transistors, or change 10K resistor to 3.9 or 4K.



Transistor amplifier assembled on 5 x 3 1/2-in. breadboard base. For greater output, extend battery clips and insert two penlite cells in series.

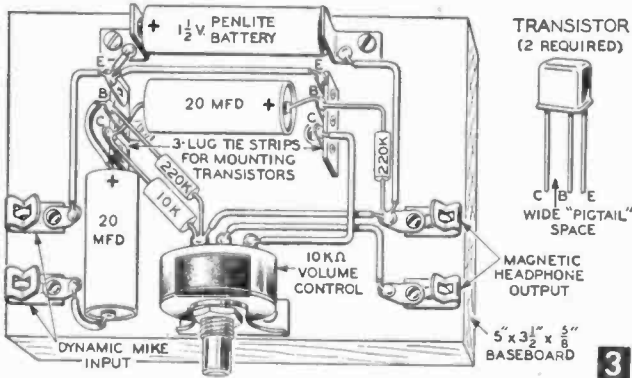


into 4-pin miniature sockets.

Note that the values of the coupling capacitors are two thousand times as great as those used in vacuum tube amplifiers; this is necessary because of the low impedance characteristics of the transistor.

Also note that the capacitors used in the model are of higher voltage rating than required only because we had them handy. Since the maximum voltage applied to this circuit will never exceed 3 volts, any working voltage above six will be sufficient, and the capacity may be as high as 40 mfd.

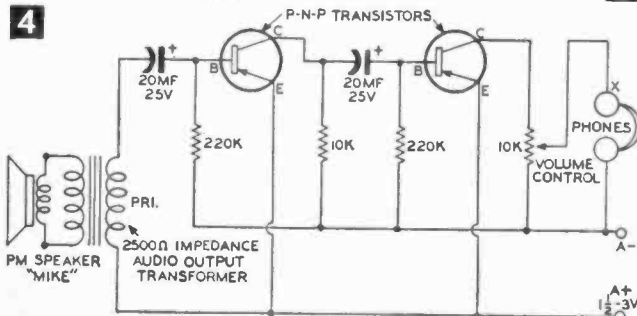Having attached a pair of magnetic headphones to the output clips, advance the volume control. If all the wiring is okay, the pickup of minute sounds will surprise you. Remember to use headphones of 2,000 to 4,000-ohms resistance for best results; crystal headphones will not work!




The 10,000-ohm volume control in the output circuit will slightly reduce the maximum amplifier output. If you prefer to build the unit and leave the volume control out, then connect headphone lead mark X in Fig. 4 directly to C (the collector of the output transistor).

Some magnetic headphones may produce slight distortion when the volume control is retarded. To correct this, insert a 20 mfd. capacitor between the arm of the potentiometer (volume control) and the X phone lead.

A 50% gain in signal output is possible simply by increasing the voltage from 1½ to 3 volts. Two penlite batteries can be inserted between wide-spaced clips, with two strips of wood attached to the baseboard to form holding-cleats for these additional batteries.


Two-Band,

Two-Transistor Receiver

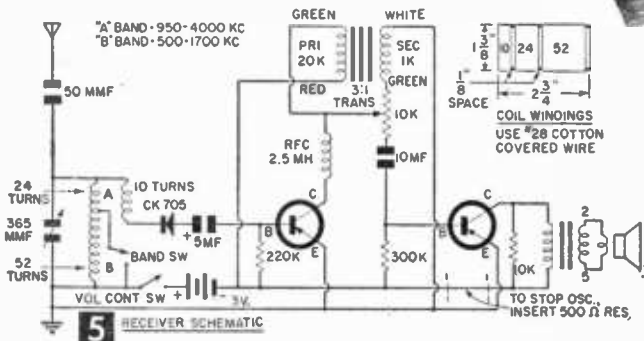

Using the transistor amplifier as a starting point, and taking a cue from the last hint given above, Robert B. Rich of Springfield, Mass., designed a compact receiver that will please the most discriminating experimenter. Constructed on a ¼-in. plywood chassis, it will pull in stations over a radius of 1000 miles with loudspeaker performance.

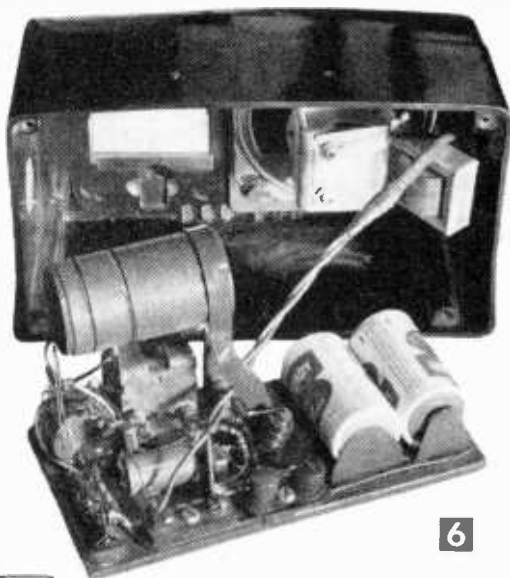And, although selectivity of the set is not



Robert Rich's two-band, two-transistor receiver. Actual life of the batteries used is about 1000 hours. For roughly 30¢, that's not bad.

equal to that of a superhet, Mr. Rich reports that his unit separates seven local stations within a radius of five miles, tunes from 500 to 4000 kc.

The completed unit is shown in Fig. 6; its schematic, in Fig. 5. The antenna coil is tuned to a 25-ft. inside antenna against a good ground. The winding of the coil is the critical factor in reception: spacing must not exceed 2½ times the dia. of the coil. If you use a 1-in. coil form, for instance, then you would use No. 30 cotton-covered wire, the insulation spacing the turns for greater selectivity yet still keeping within the scale dimensions of the coil.

A note to the impatient: Don't build this set. Mr. Rich wound 26 coils before arriving at the correct band coverage.

TWO-BAND RECEIVER-MATERIALS LIST

- 1 coil, see text and Fig. 5
 - 1 365 mmf. variable capacitor, miniature or regular
 - 1 Raytheon CK705 diode
 - 1 Raytheon CK722 transistor
 - 1 Raytheon 2N138 transistor
 - 1 driver transformer: 20K primary; 1K secondary
 - 1 volume control; audio taper, 10K with switch
 - 1 2.5 mh choke coil
 - 1 5 mf electrolytic, 25 v. capacitor
 - 1 10 mf electrolytic, 25 v. capacitor
 - 2 large flashlight batteries
 - 1 300,000-ohm resistor, ½ watt
 - 1 220,000-ohm resistor, ½ watt
 - 1 10,000-ohm resistor, ½ watt
 - 1 output transformer (Stancor No. A3856; use secondary taps 2 & 5 to speaker terminals)
 - 1 Quam 4-A15 PM speaker or equivalent
 - 1 volume control knob
 - 1 variable capacitor knob with pointer
 - 1 plywood base ¼ x 4 x 8"
 - 1 small radio cabinet 4½ x 5 (high) x 9"
- Wire, solder, wood screws, phone and speaker jacks, 2 battery holders.




D. Vletor

"Dinner is ready. Do you read me? Dinner is ready."

Tele-Tenna Beamer


By THOMAS A. BLANCHARD

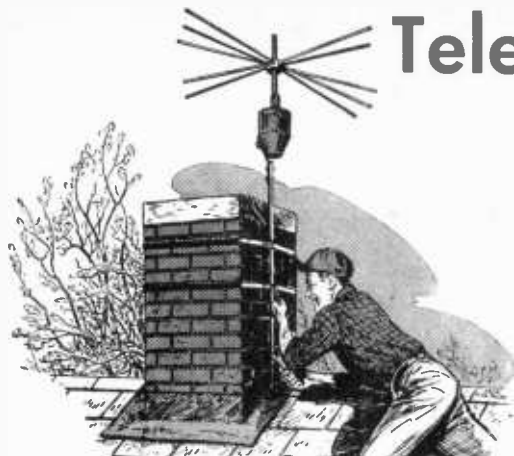

made to its frame in order for it to run, plus the fact that a television mast and reflectors should be grounded anyway for lightning protection, the solution is simple and practical.

Find "hot" side of your power line by connecting a fixture plug to a single wire *only!* Connect this single lead to one terminal on a light socket. Now connect another wire to the remaining light socket terminal and secure the end of this wire to a water pipe or steam radiator. Insert any 100 watt size Mazda lamp in the socket. If lamp


FOR best TV reception, your antenna must be oriented toward the point of transmission. Where reception is received from several compass points, a series of individual antennae may be required for best reception; this is not only unsightly, but makes a difficult installation problem on the average rooftop. The ideal system is to drive a single television antenna with a low-speed Barber-Colman Aircraft Controller motor, operated from a toggle switch convenient to the television set. Several commercial outfits are on the market, but here is one you can assemble for a couple of dollars.

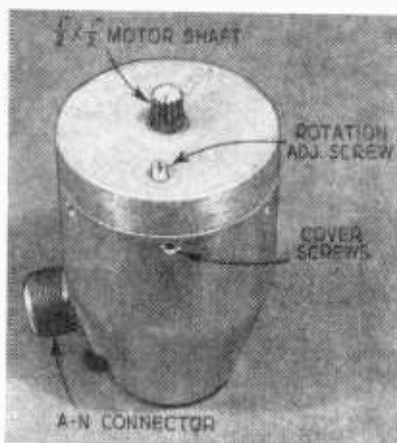

This 2½ Barber-Colman Aircraft Controller Motor has a precision gear drive and makes an ideal antenna beamer. It rotates ¼ around horizon in ¾ minute. Rotation adjustment screw permits less rotation.


operated from a toggle switch convenient to the television set. Several commercial outfits are on the market, but here is one you can assemble for a couple of dollars.

Although the motor used was intended for 24 volt dc operation, being a series type it operates equally well on 24 volts ac. Like the commercial antenna rotors, this motor requires a 12 to 24 v. step-down transformer for operating on 110 volt house current. Lacking a transformer, you may operate with a 100 watt Mazda lamp bulb, or a resistor in series with the hot side of the power line. This system can be quite practical if a few precautions are observed: One side of your power line is grounded; one side is hot! The grounded side is common with water and sanitary piping that runs through the home. Now, since aluminum housing containing controller motor is grounded and a connection must be

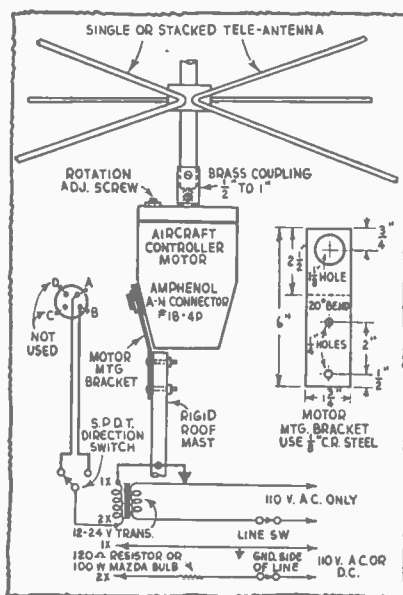

doesn't light, reverse plug. The plug-pin to which wire is connected when bulb lights is the "hot" side. Mark outlet and plug with white paint to indicate correct plug position, or replace outlet with a polarized receptacle which will prevent incorrect plug-in. Having established "hot" side of the line, connect this single wire, through the Mazda lamp or ballast resistor to the arm of the single pole-double throw switch. By grounding the antenna mast on the roof to the sewage vent pipe, the return lead of the motor is automatically established.

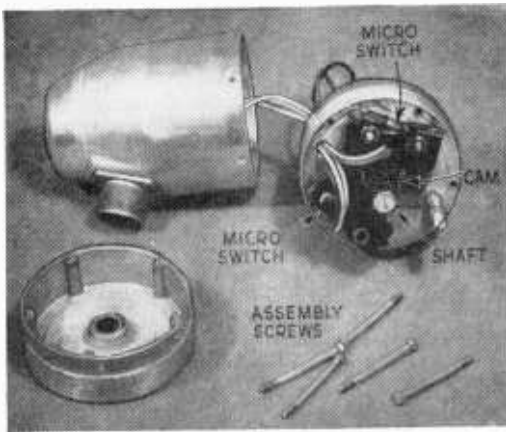When the transformer system is used, one side of the transformer 12 or 24 volt secondary winding should be grounded to a convenient water pipe. Thus when television mast is grounded on the roof to the sewage vent pipe, the return circuit is completed without need for a third wire. Where the home lacks this convenient ground, a third wire will be required, for the TV-mast



Motor is easily knocked-down for removal of Formica cam which lifts off drive shaft. Removed, motor runs in clockwise or counter-clockwise direction for other heavy-duty jobs.

should be grounded for lightning protection. Use a piece of iron, copper, or aluminum wire #8 gauge or heavier for the ground.

The aircraft controller motor is housed in a combination drawn and die-cast aluminum housing. An Amphenol A-N 4-prong fitting projects out the side. The pins inside fitting are marked A, B, C, D, but only A and B are used. From your radio supply house obtain the female cable connector to fit the Amphenol #18-4P. Connect a length of heavy-duty SJ round rubber fixture cord from pins A and B to toggle switch near your TV receiver. You can make a wooden box containing the direction switch, line switch and transformer (or lamp bulb).

Should the #18-4P connector be unavailable, solder ends of SJ cord directly to pins A and B. Fill up hole with pitch or calking compound for weather protection. Use a $1\frac{1}{8}$ x 18 BX nut to mount motor to bracket, which is formed from a $1\frac{3}{4}$ x 6 in. strip of $\frac{1}{8}$ in. cold-rolled steel. Every town boasts at least one general machine and blacksmith shop that can make this bracket if home facilities are not available. Don't attempt to cut the $1\frac{1}{8}$ in. bracket hole with a radio socket punch. Drill a $\frac{1}{4}$ in. pilot hole, then clamp bracket in a vise and ream to size with a pipe reamer inserted in a bit brace.

We show the aircraft motor opened, but it is not necessary to disturb the unit unless you want to use it for continuous rotation as in operating winches, light hoists, etc. In this case, first remove the 6 fl screws securing cover. Pry off shell from gear box using, first, jack-knife blade, then a screwdriver. Burrs from the counter-sinking make removal of shell difficult but if you pry at the cover screw points, the shell will come off nicely. With die-cast section free from shell, cut copper wire loop which secures 5 screws holding the gear-train and limit switch assembly. Also remove locking nut on the "increase" screw. Now lift off motor cover and you'll see

the 2 Micro limit switches.

This motor rotates about $\frac{3}{4}$ revolution in about $\frac{3}{4}$ minute. If you wish continuous rotation, lift off Formica cam located on motor shaft, being sure tiny metal key is removed with it. Removal of cam prevents actuation of Micro-switches and motor will run continuously either clockwise or counter-clockwise simply by throwing toggle switch in desired direction.

In most cases, the $\frac{3}{4}$ revolution is ample for beaming your tele-antenna. After a few practice runs, you'll know just when you see the "peak" signal of a given station on your television screen. The built-in Micro-switches make

MATERIALS LIST—TELE-TENNA BEAMER

- 1 Barber-Colman Aircraft Controller Motor (available from Instrument Associates, Dept. SM, 351 Great Neck Rd., Great Neck, N. Y.)
 - 1 Single pole-double throw toggle switch (S.P.D.T.) (all radio and electrical supply houses)
 - 1 Single pole toggle switch (above source & dime stores)
 - 1 12 to 24 v. to 110 v. transformer such as used in military battery chargers (available from many radio and surplus dealers). Or use alternate system with a series 100 watt Mazda lamp or 120 ohm-50 watt wire-wound radio type resistor
 - 1 Suitable length type SJ heavy-duty rubber fixture cord to extend from rooftop to control box near television set
 - 1 Amphenol A-N connector (female) #18-4P
 - 1 Mounting bracket (homemade per diagram)
 - 1 Shaft coupler (commercial or homemade $\frac{1}{2}$ " to 1")
-

the motor stop automatically at the end of either clockwise or counter-clockwise rotation. Then a mere flip of the D.P.D.T. toggle switch starts the motor travel in the opposite direction of last completed cycle. The small adjustment screw marked "increase" permits as little as $\frac{1}{4}$ revolution if turned to extreme left, or the maximum of $\frac{3}{4}$ revolution at extreme right. This is accomplished by one of the Micro-switches being mounted on a gear driven eccentric plate.


Mount the motor as near to the antenna array as possible. Also use as rigid a roof mast as possible. The aircraft controller has a $\frac{1}{2}$ -in. dia. splined shaft. Couple this to the stub length of antenna mast with a brass or steel motor coupling or have a local shop make up a suitable coupling if you can't buy one. Drill and tap 2 holes in coupling for 10-32 set screws so antenna may be locked securely to motor shaft.

To protect motor shaft from the elements, a rubber suction cup (often called a "plumber's helper") may be forced over antenna mast. This forms an umbrella keeping water away from the motor shaft. However, since shaft rides in a bronze bearing, there is little chance of corrosion especially if a ribbon of silicone grease is applied around the shaft and bearing junction. If antenna is mounted on the chimney, clean soot from the area near the insulators occasionally.

The HYBRO-HET

A Four-Transistor Pocket Reflex-Superhet

By FORREST H. FRANTZ, SR.

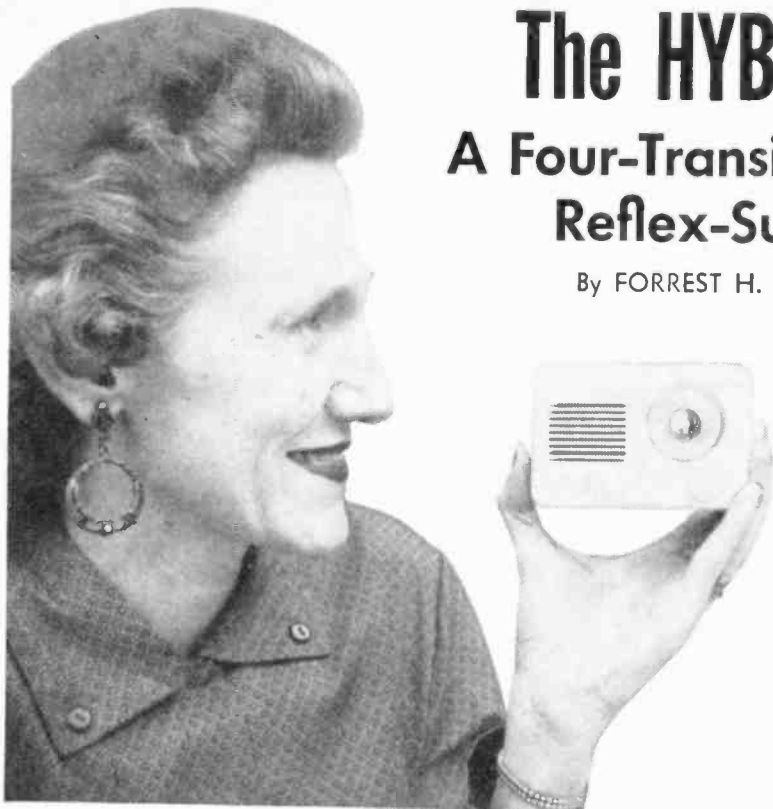

Its small size and superior performance make the Hybro-Het rank high as a gift.

WANT a pocket portable radio with loudspeaker volume—one that performs well without antenna? If you do, the Hybro-Het will meet your requirements. Housed in a 1 5/16 x 2 3/8 x 4 1/4 in. cabinet (without protruding knobs), the Hybro-Het utilizes several circuit innovations that pay off in high performance and have the additional pay-off features of low cost, about \$20, and construction and tuning simplicity.

Construction is simple because a commercially available cabinet, tuning dial, and coils are used and because the entire circuit is constructed on a miniature, perforated Bakelite board. The cabinet and tuning dial do not require any drilling or modifications, they are ready to use; the Bakelite board requires minimum drilling and cutting. Perforations in the board are anchor and connection points for leads. Component leads that are to connect are pushed through a hole, twisted together and soldered; excess lead length is clipped off. The insulating properties of the Bakelite are exploited to the utmost by mounting parts and wiring on both sides of the board.

Figure 2B shows the functional arrangement of the circuit. The signal



from the antenna coil-tuning capacitor combination is fed into transistor T1 which amplifies it—and does three other jobs. Two of these other jobs are to generate a signal 455 kc above the received signal and to mix this signal with the received signal.

The T2 circuit is a 455 kc regenerative detector. (The regenerative detector is noted for its sensitivity and selectivity.) The output signal from T2 is, of course, an audio signal. Thus, this versatile circuit does a multiple job.

The output of T2 is fed back to T1. Since the frequencies of the received and the internally-generated oscillator signal in the T1 circuit are much higher than the audio frequency from T2, the audio frequency can be amplified by the same transistor (T1). This little trick of "reflexing" is one that old timers will recall in connection with

Materials List—HYBRO-HET

R1	27 K, 1/2 watt
R2	100 K, 1/2 watt
R3	390 ohms, 1/2 watt
R4	6.8 K, 1/2 watt
R5	1 K, 1/2 watt
R6	270 K, 1/2 watt
R7	10 K, 1/2 watt
R8	68 K, 1/2 watt
R9	47 ohms, 1/2 watt
R10-S1	5 K Volume Control with Switch (Lafayette VC-48)
C13	500 mmfd, 75 v. capacitor (Lafayette C-608)
C5	.005 mfd, 75 v. capacitor (Lafayette C-611)
C2, C7, C8, C9	.01 mfd, 75 v. capacitor (Lafayette C-612)
C4	.05 mfd, 75 v. capacitor (Lafayette C-614)
C3	6 mfd, 12 v. electrolytic capacitor (Lafayette CF-102)
C6, C10, C11	8 mfd, 6 v. electrolytic capacitor (Lafayette CF-121)
C12	100 mfd, 15 v. electrolytic capacitor (Lafayette CF-126)
C1a	tuning capacitor (Lafayette MS-270)
C1b	tuning capacitor (Lafayette MS-270)
L1	antenna coil (Lafayette MS-272)
L2	oscillator coil (Lafayette MS-265)
L3	IF transformer (Lafayette MS-268)
T1	2N136 transistor (General Electric)
T2	CK768 transistor (Raytheon)
T3, T4	CK722 transistor (Raytheon)
TR & SPKR	1 1/2" loudspeaker & matching transformer (Lafayette SK-62)
B	Battery (See text)
1	Miniature perforated bakelite board 2 3/8 x 3 1/16" cut from Lafayette MS-305
1	Dial knob for tuning capacitor (Lafayette KN-24)
1	Plastic case & volume control knob, ivory (Lafayette AR-190)

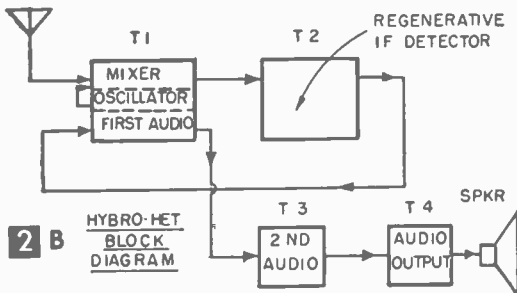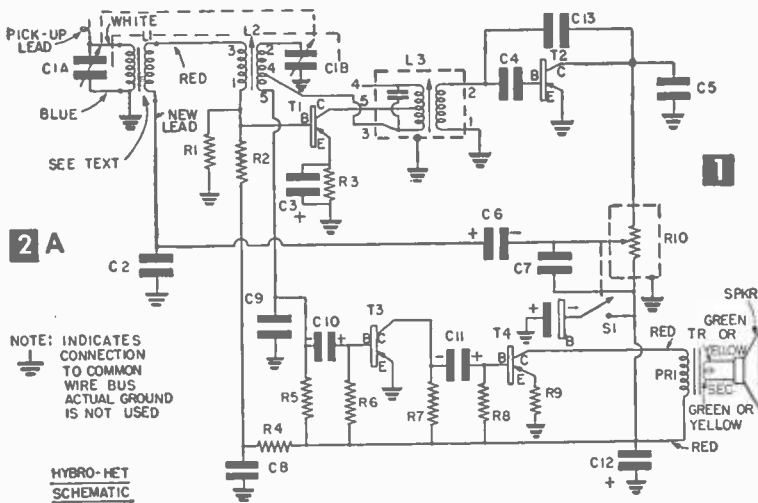

early vacuum-tube circuits.

The audio signal from the output of T1 is fed into transistor audio amplifier T3, and thence to the output stage T4.

Construction. Tools required are: hacksaw, pocket knife, file, 1/2-in. taper reamer, hand drill, needle-nose pliers, diagonal pliers, screwdriver and soldering iron or soldering gun. (When you begin to solder connections, remember that the small components and the transistors you're working with can't stand a whole lot of heat. Use rosin core solder only and leave 3/8-in. leads on the transistors, and you won't have any trouble.)

A single cut across the Lafayette MS-305 piece of perforated Bakelite 2 3/8 in. from one end will give you the required 2 3/8 x 3 1/16 in. blank for the chassis board. Smooth the edge with a file. Whenever you place the board in a vise for cutting or drilling, clamp it between two pieces of wood to minimize the possibility of breakage.

The lay-out for cutting and drilling the perforated bakelite board is shown in Fig. 3. Drill the 1/8-in. holes and 1/8-in. pilot holes for all other holes. Enlarge the pilot holes to size with taper reamer. All holes except D, K and I are centered on perforations.

Opening A is started by sawing with a hacksaw blade held nearly parallel to the surface of the board. After you've cut through the board near the corners, push the blade through and saw in the usual manner with the blade nearly perpen-

dicular to the surface of the board. (Smooth edges with a file.) Opening G is made by drilling the end holes to 1/8 in. and cutting a joining slot with a hacksaw.

The output transformer (TR) mounting hole on your left as you look at the side of the transformer labeled "2K" must be enlarged to 3/4 in. to permit mounting with a #6-32 x 1/4-in. machine screw and nut. (The transformer frame is held together with rivets through the mounting holes; don't enlarge the second

mounting hole, or you may have trouble handling the transformer.) A single screw and nut at the enlarged mounting hole with a drop of Duco cement at the other hole will hold the transformer in place on the chassis board.

The oscillator coil (L2) terminal lugs should be cut with diagonal pliers, bent up and trimmed as shown in Figure 4A. This operation reduces the mounting space required for the oscillator coil.

Shorten the shaft of the tuning capacitor (C1) to 1/2 in. with a hacksaw and dress the end of the shaft with a file until the shaft is 1 5/8 in. long. The capacitor's shaft should be fastened in the vise for this operation so that no side stresses are placed on the plastic bearings of the capacitor.

The antenna coil (L1) is manufactured with its two windings fastened together. They must be separated. Remove the tape at the ends of the coil, leave the blue lead on the end of the long winding, but cut the end of the short winding from the blue lead as shown in Fig. 5. Provide a lead for this end of the short winding, insulate with tape and refasten the tape around the end of the coil.

Mount the components TR, R10, L2, L3, C1, C4, C12, T1, T2, T3 and T4 on the back of the chassis board (See Fig. 6A). Transistors and fixed capacitors are mounted simply by pushing their leads through the perforations on the board. The mounting lugs on the L2 shield are bent up and back against the shield. (A short length of #20 wire, about 2 in., should be soldered to each of these lugs before mounting the transformer.)

Mount the IF transformer by passing terminal lugs 2, 3 and 5 through slot G on the terminal board, and bending them over. Terminal lug 1 is bent up over the edge of the board, and lug 4 is cut off to a length of 1/8 in. (no connection will be made to it). Make the bottom of L3 hug the chassis board; file the two plastic protrusions at the top of the shield even with the shield. Oscillator coil (L2) fits in hole H on the chassis board and is held in place with a drop of Duco cement.

Now, place the partially assembled radio in the cabinet to check shaft and cabinet hole alignment. If the shafts don't center in the holes, do some reamer work on the chassis board before you proceed with the wiring.

Most of the wiring is completed with component leads. The common ground bus and shield connections are made with #20 wire. Other connections requiring extra wire may be made with #22. The best sequence is to complete the wiring associated with the oscillator coil (L2), transistor T1 and the IF transformer (L3) primary first. (Soldering of most connections can be done after the set has been completed and tested.)




Next, complete the wiring associated with the secondary of the IF transformer, transistor T2, and the volume control (R10). Solder the lead that has been soldered to the bent-back mounting lug of L3 to R10. A lead returns from this point to terminal 1 of L3. The other L3 shield lead goes to the ground bus.

The speaker need not be fastened to the chassis board since it will be held firmly in place by pressure when the chassis board is mounted in the cabinet. However, transparent tape or a rubber band holding it in place will protect it during testing and alignment.

The antenna loop coil (L1) and a short antenna pick-up lead (about a foot of #20 plastic insulated hook-up wire) is connected next. When this is completed, you're ready to hook the Hybro-Het to its batteries and try it out. Two Ray-O-Vac No. 716 miniature batteries (1½ v. each) connected in series with a Mallory TR-145R (7.5 v.) constituted my power supply. I insulated the terminals with transparent tape. As an alternative power supply, two Mallory T-114R batteries connected in series will supply 10 v. and fit nicely, one battery on each side of the loudspeaker.

The Hybro-Het will work with a battery voltage between 7.5 and 12 v. The lower voltage should be avoided because operation becomes unsatisfactory when the batteries go down the least bit.


Alignment. The Hybro-Het can be aligned without expensive instruments, using a superhet broadcast radio as the IF signal source. Remove the regular broadcast radio from its case and connect the common ground return in the broadcast set to the common ground return on the Hybro-Het (see Fig. 7). You can readily find this point since the negative terminal of the power supply electrolytic filter capacitor in the regular broadcast radio is tied to common ground. Connect a second lead from the plate of the first IF stage in the regular broadcast radio through a 100-

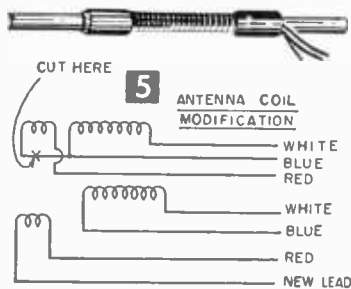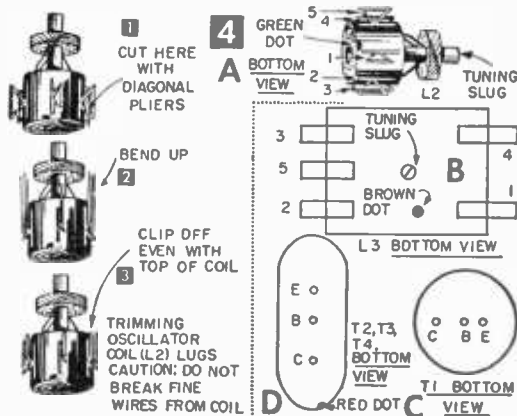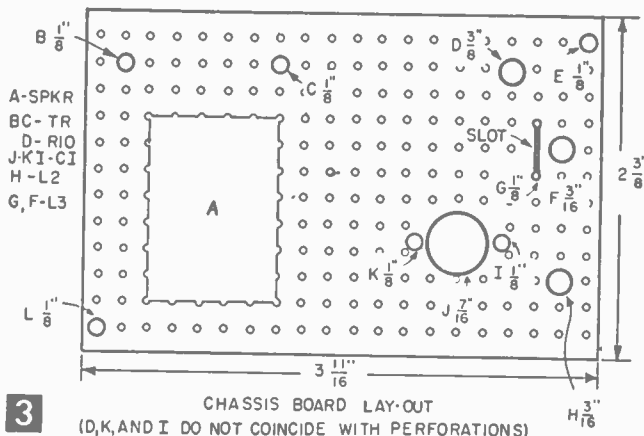


mmfd mica capacitor to the base of T1 (junction of R1 and R2) and turn the Hybro-Het tuning dial capacitor fully closed (530 kc), the broadcast radio to a station between 1200 and 1500 kilocycles.

Turn the volume on the regular broadcast set down, and tune the IF transformer (L3) slug with a screwdriver through hole F in the chassis board for maximum output. You'll probably have to reduce the Hybro-Het volume control setting since this control also serves as a regeneration control. When this adjustment is completed, the IF stage is tuned.

Now, disconnect the leads from the regular broadcast set. Set the slug in the oscillator coil (L2) of the Hybro-Het so that the top of it is flush with the upper edge of the L2 coil form as you look at the front of the chassis board. Turn the oscillator trimmer capacitor on C1 three-fourths closed and leave the antenna trimmer on C1 fully open. With the set in the case, tune the C1 dial to a local broadcast station between 1300

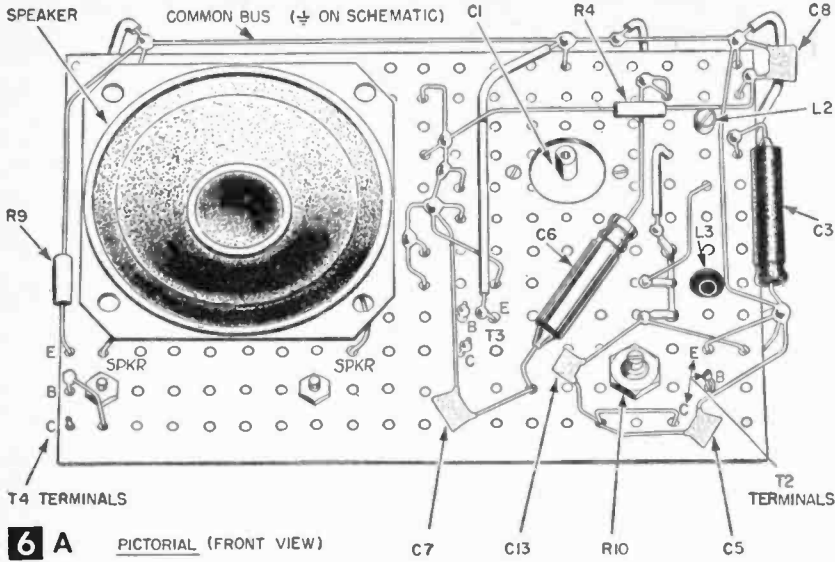

6 A PICTORIAL (FRONT VIEW)

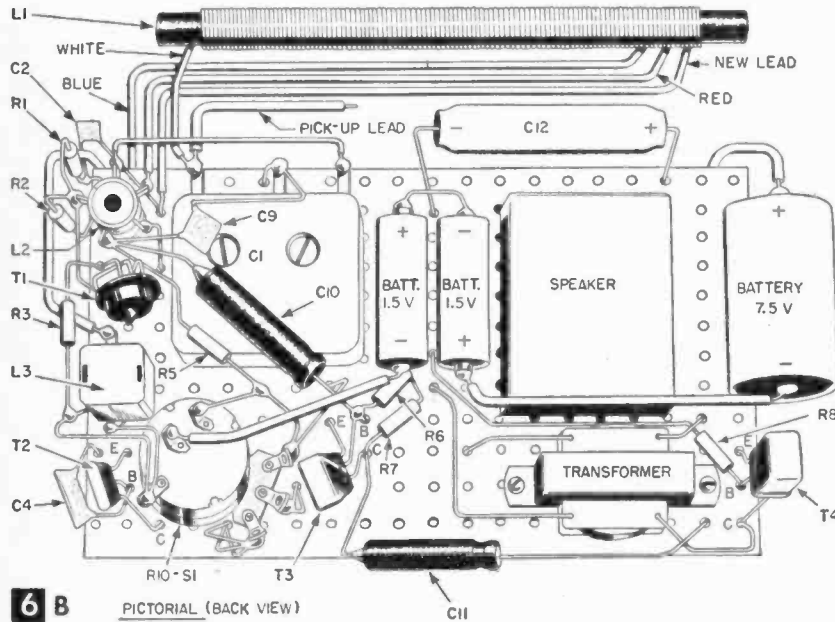

6 B PICTORIAL (BACK VIEW)

and 1500 kc. Adjust the antenna trimmer for maximum output. Again, you may have to reduce the volume control setting until "squealing" stops. Then tune to a station on the low end of the C1 dial (around 600 kc). Move the C1 dial slightly to one side of the station and tune the L2 slug until the station comes in. If it's louder than it was, continue the process until you have maximum output. If you get a weaker output, work in the other direction on the dial.

After you complete this procedure, go back to the high frequency end of the dial and re-trim the antenna. If the loudest signal results with the antenna trimmer (C1A) fully closed, you may have to open the oscillator trimmer (C1B) slightly

in order to tune the set. If you get the loudest results with the antenna trimmer full open, you'll have to close the oscillator trimmer slightly. The oscillator coil slug may again require slight adjustment at 600 kc, followed by a re-trim of the antenna at the high frequency end of the broadcast band to complete alignment. Place a drop of Duco cement on the L2 slug when alignment is completed.

If you have trouble, bear in mind that this is a regenerative radio and it may squeal with the volume control full on. Reduce this setting until the squeal stops; you should not have to reduce it much. At lower volume settings, the control performs as a conventional volume control.


If you can't eliminate squealing by reducing the volume control setting, check to be sure that you've connected the volume control case and IF trans-

former shields to ground. Check to be sure that you've dressed leads so that they can't short a circuit.

If the set motorboats on you, check the battery voltage. Motorboating will occur when the batteries become weak.

If the set is inoperative, check the audio by touching the junction of C2 and C6 with your finger. If the audio is working, you'll get a faint hum and your trouble is probably associated with the oscillator and IF portions of the circuit. If you don't get a faint hum, check the audio and output stage first, and then the T1 stage.

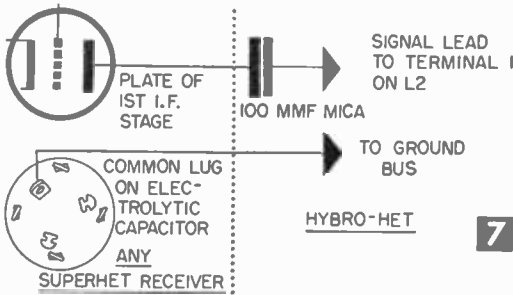A 1/8-in. hole should be drilled in the side of the cabinet to permit passage of the pick-up



ARRANGEMENT FOR ALIGNING I.F. STAGE: WITH TOO STRONG A SIGNAL, DISCONNECT LEAD FROM TERMINAL 1 ON L2 AND WRAP INSULATED PORTION OF SIGNAL LEAD AROUND TERMINAL 1 OF L2

lead. A knot in the lead will relieve strain on the tuning capacitor to which it connects. You may wish to drill another hole on the other side of the cabinet through which you can pass the other end of this lead. The end of the lead would then be knotted inside of the cabinet. Thus, the pick-up lead can serve as a handle. This would reduce pick-up length to about 5 in., adequate for most localities.


Placing your finger on the metal knurled tuning capacitor screw will increase pick-up in most instances. The set has adequate pick-up for local stations without resorting to this, however.

**What's Your
Radio-TV Theory Quotient?**
By JOHN A. COMSTOCK

Think you know your radio and television theory fairly well? Or are you a bit rusty on some points? Here's a test designed to reveal how much you really do know of the theory behind radio and TV. If you score 18 or more correct, your TQ is excellent; 15 to 18 correct it's good; 12 to 15, fair; 12 or less—you need to brush up on theory! (See page 158 for answers to the test.)

1. A _____ and _____ make up a resonant circuit (fill in the blanks).
2. A resonant circuit is said to be tuned when:
 - a) The inductive reactance equals the capacitive reactance
 - b) The inductive reactance is greater than the capacitive reactance
 - c) When total resistance is zero
 - d) None of the answers given above
3. When a resistor of 10 ohms is placed in parallel with another resistance of _____ ohms, the total resistance in such a circuit is 5 ohms.
4. A resistor of 10 ohms, 10 watts, is in parallel with another of the same resistance and wattage rating. What amount of power can be dissipated by the two?

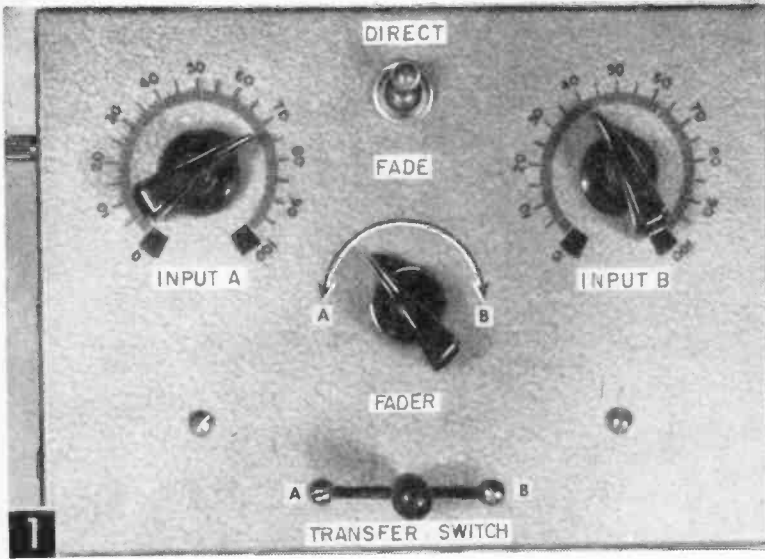5. The unit of measurement of impedance is the:
 - a) Farad
 - b) Ohm
 - c) Rel
 - d) Henry
6. Disregarding losses, the amount of power in the secondary of a transformer is the same as that in the primary winding.
 - a) True
 - b) False
7. When a _____ of 15 microfarads is placed in parallel with one of the 10 microfarads, the total _____ equals:
 - a) 25 microfarads
 - b) 15 microfarads
 - c) 30 microhenries
 - d) 25 microhenries
8. The device used to convert sound energy into electrical energy is a:
 - a) Loudspeaker
 - b) Microphone
 - c) Antenna
 - d) Picture tube
9. A transducer is a:
 - a) Microphone
 - b) Loudspeaker
 - c) Light bulb
 - d) All of these devices
10. The _____ element in a transistor serves the same purpose as a cathode in a vacuum tube.
11. The n-p-n and p-n-p transistors are:
 - a) Junction type
 - b) Point-contact type
12. In television, interlaced scanning is used to:
 - a) Widen channel
 - b) Reduce flicker
 - c) Increase frame rate
 - d) _____
13. At what frequency does the horizontal scanning generator operate in a TV speaker?
 - a) 30 cps
 - b) 60 cps
 - c) 6 Mc
 - d) 15,750 cps
14. The sound transmitter at a TV station employs _____ modulation.
15. S _____ signals are sent in the composite video signal to maintain the correct beam scanning pattern on the receiver screen as at the camera pick-up tube.
16. In the United States, a) negative, b) positive, picture tube phase transmission is used.
17. What is an intercarrier type TV receiver?
18. The blanking signals are transmitted to _____ the electron beam in the picture tube during _____.
19. In color TV, what signal corresponds to the video signal in a black and white system?
20. The video transmitter at a color TV station employs amplitude modulation.
 - a) True
 - b) False



Front-panel view of two-channel mixer well-suited for use with high-fidelity equipment—and inexpensive!

phones, phono pick-ups, tuners, etc. The two inputs are fed into separate jacks (J1 and J2), through separate "Level" controls (R1 and R2) and into separate amplifiers (V1A and V1B).

Amplified, the signals are then fed through separate sides of the Transfer Switch (SW1), through separate sides of the Function Switch (SW2), and into separate sides of the Fader Control (R7). The signals, still separated, each go to a grid of a dual cathode-follower stage (V2), whose plates and cathodes are common. Here, mixing occurs. The output is fairly low impedance, permitting up to 100 ft. of microphone cable between the mixer and main amplifier.

HIGH-EFFICIENCY Two-Channel Mixer

By W. F. GEPHART

A MIXER to superimpose voice on recorded music, operate one amplifier from two microphones, etc., should have the following characteristics:

- 1) The input impedance should match the impedances of the devices feeding it and the output should be suitable for high-gain amplifier inputs.
- 2) The input and output impedance should not vary as the mixer's controls are varied.
- 3) The variation in gain for each channel should be smooth from zero to maximum.
- 4) There should be no interaction between controls.
- 5) The mixer should not affect frequency response of the input signals and should not introduce any hum or noise into the signal being fed into the amplifier.
- 6) The mixer should be versatile enough to permit either fading or direct switching or a combination of both.

Many mixers do not have all of these characteristics and when used with high-fidelity equipment the results are disappointing. Those that do work well usually have expensive, balanced, pad-type controls—too expensive for most non-professionals. The mixer described in this article, however, can be assembled of inexpensive parts, possesses all of the characteristics mentioned as necessary, and is well-suited for high-fidelity use.

Figure 2, a schematic diagram of the mixer's circuit, shows that the input circuits are designed for high-impedance inputs such as crystal micro-

The function of the Level controls (R1 and R2) is to equalize the levels of the two incoming signals, so that no gain adjustment will be required when switching from one signal to another.

The Transfer Switch (SW1) is used to switch directly from one signal to another without fading. When in the center position, both signals are passed. Moving the switch to either side permits only the signal selected to go through, grounds out the other.


The Function Switch (SW2) determines whether the signals are to be switched directly by the Transfer Switch or faded into each other by the Fader Control (R7). When in the "Direct" position (as in Fig. 2), the signals go directly to the grids of V2, bypassing the Fader Control.

The Fader Control (R7) is a dual potentiometer, wired so that the gain of one signal is increased as the other is decreased. It must be a linear taper potentiometer connected so that as the shaft turns, resistance increases in one element as it decreases in the other. As shown in Fig. 2 (ignoring the small dotted lines), a standard dual potentiometer may be used and, at midpoint, an equal amount of each signal will pass. The fading action is therefore (turning clockwise) from full signal A to half signal A plus half signal B to full signal B. If it is desired to have no signal at midpoint (with fading action from full signal A to zero to full signal B), the potentiometer must be modified. This modification will be explained later.

Figure 2 assumes that external power for the mixer can be secured from the main amplifier. Power requirements are 6.3 volts ac at 7 amps and between 150 and 250 v. dc at 5 ma. This power may be brought in by a four-conductor cord wired directly into the mixer or through a power plug.

If power from the main amplifier is not available, a built-in power supply, such as that shown in Fig. 6, can be included. Note that the power line is isolated from the chassis and ground by the two filament transformers. This is necessary not only from a standpoint of safety, but also to prevent interaction between the mixer and main amplifier.

To minimize ac hum, a filament balancing control (R11 in Figs. 2 and 6) is provided. If power is secured from a main amplifier with either side of its filament circuit grounded to the chassis, however, this control should not be included. This control should be set after the mixer is connected to the main amplifier and the inputs are plugged in. With no signal (this may require holding your hand over microphone), both Level controls at full gain, and the main amplifier gain turned up until a hum is heard, adjust the Hum

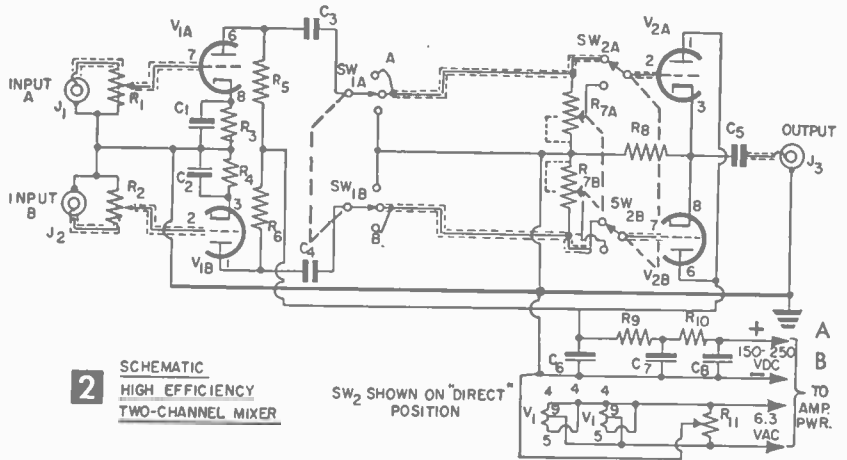

Control for minimum hum in the speaker.


Figure 4 gives the panel and chassis layout for the unit without the power supply. No dimensions are indicated for the mounting of the two Input jacks and Hum Control in one end of the case and the Output jack and power plug at the other end; these can be placed where most convenient. If a power supply is to be built in, a larger box (3½ x 6 x 10 in.) should be used. The same size chassis piece can be used, but it should be mounted to one side, leaving clearance at one end of the box for the two transformers and selenium rectifier. The pilot light and power switch could be placed symmetrically on either side of the Fader Control, on the panel under the Level controls. The Hum Control and both Input and Output jacks would then be on the other end of the case.




3 Back of panel view of mixer with cover removed. Note Input jacks and Hum Control on end panel at right.

Figure 3, a back view of the mixer, and Figs. 7 and 8 show wiring arrangements. Notice that SW1 (shown in Fig. 8), is mounted with ¾-in. spacers. This particular switch (Mallory 6243) has a very long arm which tends to protrude too far from the mixer's front panel unless mounted in this manner. Also notice that shielded sockets and tube shields are used to reduce hum and interference.


Run the filament leads first, twisting the wires together and keeping them close to the chassis (chassis is made of scrap aluminum, with a ½-in. bend along one side; a convenient source is the side panel of an old 3-in. deep chassis). Be sure to use shielded wire where shown in the schematic and elsewhere if long (over 2 in.) signal leads are used. Generally, it will be best to use plastic-covered shielded wire to prevent the grounded shielding from shorting out against other wiring. Within reason, the larger the diameter of the shielding, the better, since small-diameter shielding has a higher

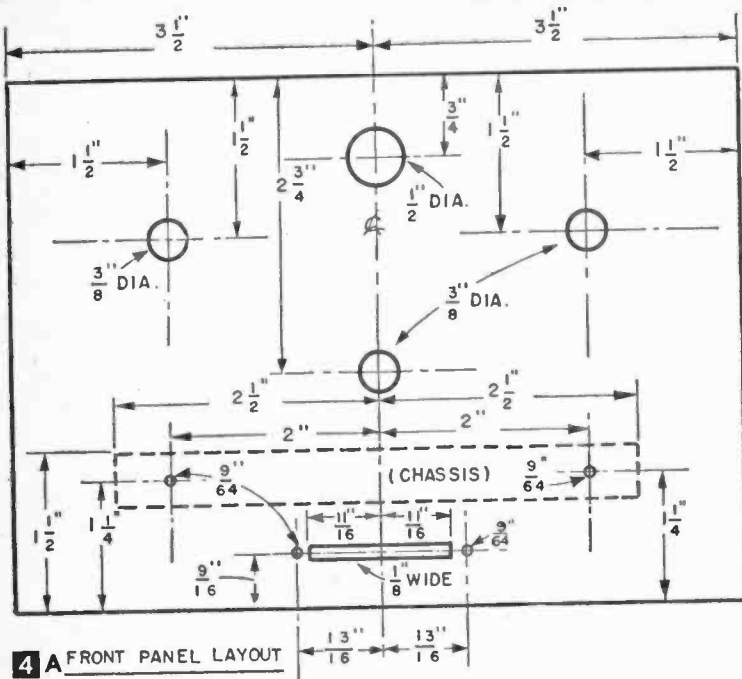

4 A FRONT PANEL LAYOUT

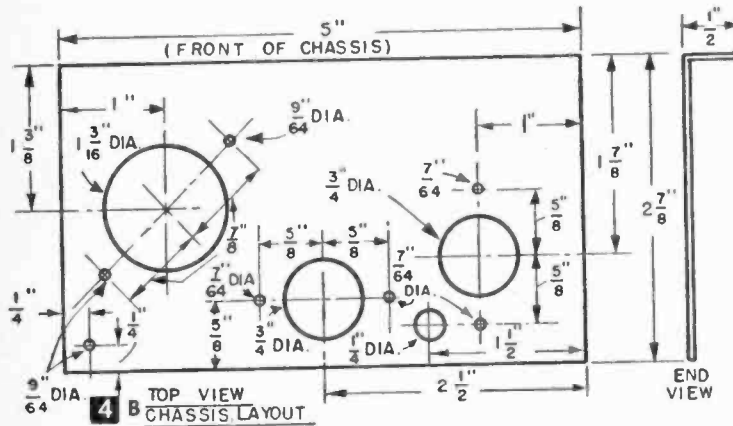

4 B TOP VIEW CHASSIS LAYOUT

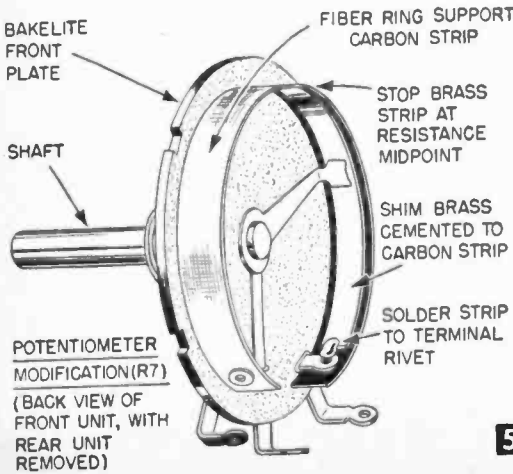

5

capacity which reduces high-frequency response. In some cases, as can be seen in Figs. 7 and 8, two-conductor shielded wire can be used to good advantage. To minimize stray chassis currents, a common ground bus is used and all ground connections are made to it. This bus is grounded to the chassis at the Input and Output jacks.

Modification of Fader Control.

The ideal way to provide zero gain on both signals (instead of half-gain) at midpoint would be to have a dual, linear-taper, center-tapped potentiometer of 1 or 2 megohms. But such pots are not normally available. An untapped potentiometer can be "shorted out" as shown in Fig. 5 if it has a removable back, and if the front and rear sections can be separated. The clockwise half of one potentiometer and the counter-clockwise half of the other is shorted out with a small piece of shim brass which results in the potentiometer arms being shorted to ground (see small dotted lines on R7 in Fig. 2) at midpoint. Turning the shaft one way moves one arm toward the grid (with decreasing resistance and therefore increasing signal), while the other arm stays on the shorted-to-ground section. This results in fading action from full signal A to zero to full signal B.

To modify the potentiometer (use a 2-meg. pot.), cut a strip of shim brass (as thin as is available) the width of the potentiometer carbon strip. Using an accurate ohmmeter, adjust pot's arm to the exact midpoint, and mark it carefully. Cut the brass strip to a length slightly in excess of the circumferential distance from the midpoint of the carbon strip to the end terminal, and cement it (using contact cement) to the inner side of the strip (as shown in Fig. 5). Solder one end to the lug rivet at the end of the strip. Do the same to the other half of the dual potentiometer, using the opposite segment of the carbon strip. While every effort should be made to have the unsoldered end of the brass strips at the same point when the potentiometer is re-assembled, a little variation won't hurt since the midpoint is the point of lowest gain.

MATERIALS LIST—TWO-CHANNEL MIXER

R1, R2—.5 meg. potentiometers*
 R3, R4—1500 ohm, 1/2 watt
 R5, R6—.1 meg. 1/2 watt
 R7—Dual 1 meg. potentiometers* (See text)
 R8—47000 ohm, 1/2 watt
 R9—15000 ohm, 1 watt, wire-wound
 R10—10000 ohm, 1 watt, wire-wound
 R11—200 ohm, 2 watt potentiometer (Mallory C200P or M200PK)
 C1, C2—10mfd, 25 volt
 C3, C4—.05 mfd, 300 volt
 C5—.2 mfd, 300 volt
 C6, C7—20 mfd, 250 volt }
 electrolytic } Mallory FP-320, Sprague TVL 3540
 C8—40 mfd, 250 volt }
 electrolytic }
 SW1—DP 3 pos. Lever Switch (Mallory 6243 or Switchcraft 3036L)
 SW2—DPDT toggle switch
 J1, J2, J3—Phono Jacks #
 V1—12AX7
 V2—12AU7

Case—Bud "Minibox 3 x 5 x 7"

Tube sockets and shields, knobs, shielded wire, etc.

Additional and Substitute Parts Required If
 Power Supply Is To Be Included.

(See Fig. 6)

T1—Filament Transformer: Secondary 6.3 volts @ 1 amp

T2—Filament Transformer: Secondary 6.3 volts @ .5 amp

SR1—20 ma. selenium rectifier

R12—5000-ohm, 1-watt, wire-wound

C9—40 mfd, 150-volt, electrolytic

SW3—SPST toggle switch

PL—6.3-volt pilot light and jeweled socket


If power supply is used, larger, low-voltage quadruple condenser unit can be used to act as C6, C7, C8 & C9; such as Mallory FP 312 (100-80-60-40 mfd @ 150 volts).

* All potentiometers must be linear taper

Jacks may be varied to suit needs; however, adapters made by Switchcraft can be used to adapt various microphone plugs to phono jacks.

Control toward the center position, fading out the signal. The other signal will not fade in since it is grounded out at the Transfer Switch. The

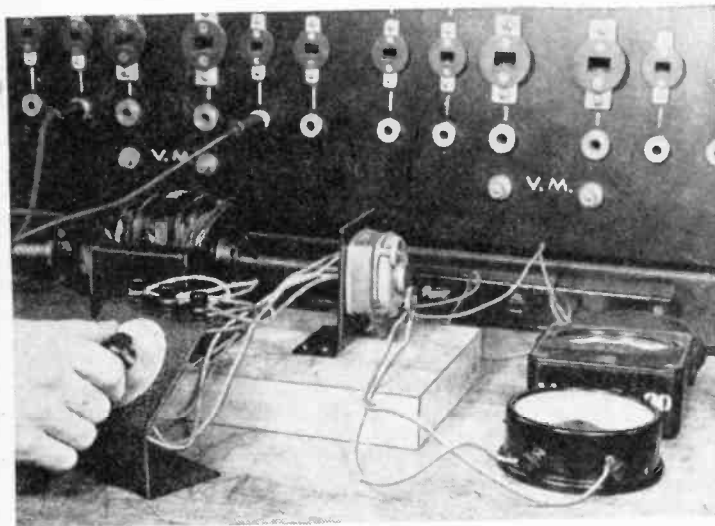same operation could be performed with the Level controls but this would unbalance the input levels.



A setup in a special laboratory experiment in which the potentiometer described in this article is being used in the circuit of a small Alnico type generator to vary the generator's output.

POTENTIOMETER for the Electronics Lab

Here's just the thing for your radio and electrical testing work

By HAROLD P. STRAND

ELECTRICAL experimenters and radio technicians have constant need of variable resistors for many purposes. These should be in such form that they are handy to use on the bench and

are easily adjusted. One type of home built adjustable slide wire resistor, described in detail on page 153 of *Experimenter*, Vol. 5, was built around a resistance tube commonly sold in radio stores. Another and more versatile type can be built from a power rheostat, a piece of 1/16 in. aluminum sheet, a knob, a dial and three binding posts. This device is shown in use in a circuit of a special piece of electrical apparatus under test, where a certain resistance value is necessary. The handy stand takes but little space on the bench and offers suitable support. The pointer type knob is easily adjusted to give any value within the range of the unit.

Insulated binding posts at the back permit easy connections. Several of these units should be made up, using various rheostats, both in respect to resistance and wattage, so as to be able to cover any reasonable condition.



Begin building by bending up the stand from some 1/16 in. sheet aluminum (thinner gage steel can be used). Dimensions given will accommodate 50 watt Ohmite power rheostats, which have three terminals so they can be used as potentiometers or as straight series resistance if desired. These 2 3/16 in. dia. rheostats can be obtained in values ranging from .5 ohm 10 amperes up to 10,000 ohms .070 ampere.

In the center of inclined surface of the stand, drill a hole to clear threaded end of rheostat, so it can be locked in place with the nut provided. Before securing it in place, however, make up a dial from some .015 or .020 thick sheet brass. Cut this out in the form of a 2 3/4 in. dia. circle. Then scribe a 2 3/16 in. dia. circle on the disc and lay out your scale on this line. The figures 0 and 10 should be extreme stop positions of the pointer knob, which should be marked first by testing knob for its two positions. Between these two points, lay out 10 even divisions on the circular line. Divide each division into 5 equal parts, which will be the subdivisions. With a set of number stamping dies, stamp numbers from 0 to 10 on the main divisions just above the line. Use a prick punch to make markers for each sub-division. Should stamping the numbers result in warping the disc as it often does, anneal metal by heating over a flame and when cool it can be flattened easily. When completed, clean and polish dial and finish it with a coat of clear lacquer.

Now place dial in position over hole in stand, and push rheostat stud through; locknut holds the assembly in place. Keep numbers 0 and 10 in a level position at the bottom and terminals of rheostat at the top. In addition to hole for rheostat mentioned, drill three additional 1/4 in. dia. holes at the back level surface for the Bakelite binding posts. Since metal stand would short-circuit posts if they were placed directly in the holes, provide insulating sleeves and washers in position, to insulate the posts from the stand. Bakelite tubing, 1/4 in. O.D. (with a hole to clear the 6-32 threaded studs of the posts) and 1/16 in. long, serves to insulate studs in the holes. A fi-

ber washer, together with a brass washer and a nut complete assembly of the posts. At the back side solder three short pieces of No. 18 lead wire to the three rheostat terminals and connect these to binding posts. If you have the facilities, apply a black crackle finish; put this durable, attractive finish on before any assembly work is done but after all four holes had been drilled. If crackle finish is not available, paint metal with dull black lacquer or any other finish selected.

Potentiometers are used in many ways in electrical circuits. They are often connected with the outside terminals across the line, (provided resistance value is suitable) and load is taken from center terminal and one side of the line. Thus a method is provided for getting reduced voltage control. Another use is for voltage dividers in circuits. They can also be used as simple series resistance by using one outside terminal and the center one. When using any form of resistance in circuits make sure that both resistance value and capacity of resistor in amperes are suitable. Otherwise, it is easy to burn out a resistor quickly.

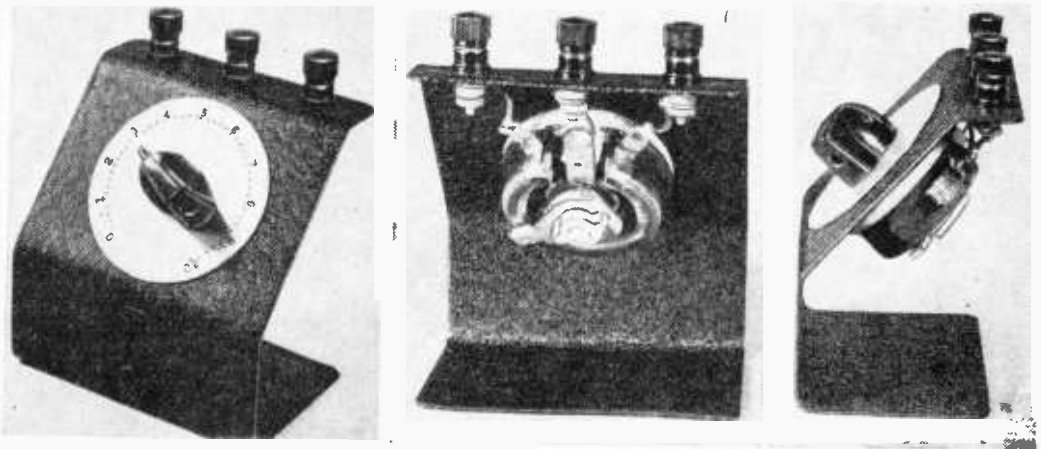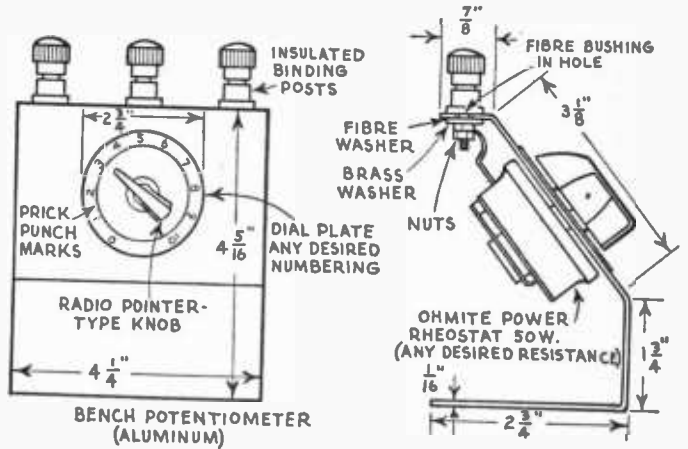

From left to right, front, rear and side views of the versatile potentiometer, which was built from a power rheostat, a knob, a dial, and three binding posts. Note connections on rear view.



Radio Tracking AMERICAN SATELLITES

By JEROME TANNENBAUM

SO many new sounds have been coming from space recently that the amateur listener feels almost as if he were tuning in on a satellite "orchestra."


First, there were the familiar "beep-beep" signals from the Russian Sputniks. Then the fainter, varied musical tones of the American Explorer I. Not long after that came the signals from Vanguard I satellite, sounding very much like those from Explorer I (and later Explorer III), but with a little more of a "thrumming" tone.

Compared to the Sputniks the signals from the first American Explorer I and Vanguard I satellites were weaker and more difficult to receive. In Chicago, the 108.030 megacycle signals from Explorer I at their strongest sounded to us like a continuous carrier with a very shallow (about 15%) superimposed modulation. The four telemetering tones we heard were fairly short, none longer than one-third second. These tones followed each other in such rapid succession that

they sounded almost like a continuous chord. Explorer I signals came in sharply, were in briefly, only about four minutes, and then went out sharply. We could easily hear a slow, two-second fade resulting from the slow rotation of the satellite.

No Job for Amateurs?

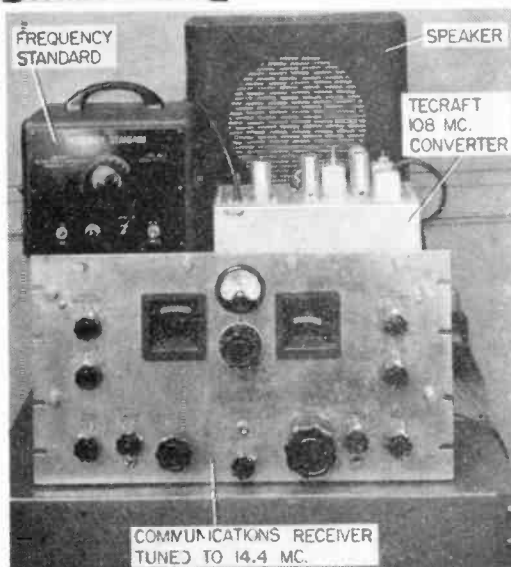Not long ago, many experts were saying that picking up the 108 megacycle signals from the American satellites



At top of page, electronic consultant Tannenbaum seated in front of equipment he has used for tuning in on American satellite signals. Photo directly above identifies equipment which was used.

would be beyond the reach of most amateurs. Receiving equipment, they said, would be in the \$1,500 class, and thus even the casual listener would have to be in a high tax bracket!

These experts had a point. The power used by the American satellites, 10 to 50 thousandths of a watt, was but a small fraction of the 1-watt transmitters used in the earliest Sputniks. And such low power imposes a very hard task for receiving tubes and circuits. Also, because the operating frequency of 108 megacycles provides only for line-of-sight reception, there is very little bending of the waves by the ionosphere. Thus reception will occur only when the satellite is near or above the horizon for the receiving station, it will be in only for brief periods, and for many parts of the world it will be in only when its orbit is highest (apogee) near the longitude of the receiving station.

It is also more difficult to get maximum effi-

ciency from receiving tubes and circuits at 108 megacycles than at the 20 megacycles the Russians used. American scientists chose this high frequency and short wave length (each wave is only about 3 meters long) because the lack of bending would permit the more accurate use of radio to fix the orbit and track the satellite's position accurately.

To receive the 108 megacycle satellite channel, a very good antenna, cut to this channel, is required in most locations. The "front end" of the receiving system must be able to handle very weak signals without masking them with internally generated noise.

As the experts knew, these requirements would have called for quite expensive equipment a few months ago. Now, thanks to the ingenuity and energy of three manufacturers, moderately-priced equipment is available which the amateur can use for American satellite tracking. It is detailed for you in Table A.

Hookup. Figure 2 shows the system for receiving weak signals using the Tecraft converter. You may already have a communications receiver which can receive signals at 14.4 megacycles; most communications receivers cover this frequency. The Tecraft converter converts the 108 megacycle satellite frequency to the more easily received intermediate frequency of 14.4 megacycles, where it can be amplified and detected in the normal way by the communications receiver.

Use Beat Oscillator. The beat oscillator on your communications receiver not only converts the carrier of the satellite into an easily heard tone, but is also useful in measuring the Doppler Shift in frequency due to the satellite's tremendous velocity. You can turn it off when you wish to listen to or tape record the tone modulation which conveys the information from the satellite's instruments.

Don't set the selectivity on your communications receiver too sharp, since there is a consider-

How Cold Are You, Van?

ANYONE who can tune in on the broadcasts from the 6 inch test Vanguard satellite (and perhaps some of the later satellites) could learn the temperature where the sphere was at the time.

The test satellite carries two transmitters, each with its own antenna, broadcasting at 108.00 and 108.03 megacycles, or within four kilocycles of these frequencies. The crystal controlling the mercury cell powered broadcasts at the even 108 megacycles is mounted at the satellite's center so its temperature will be as nearly constant as possible.

The crystal controlling the solar-powered broadcasts at 108.03 megacycles is temperature-sensitive, however, and mounted on the satellite's surface.

The difference between the two frequencies thus indicates the skin temperature, each degree centigrade changing the frequency by about 100 cycles. Temperature so measured is expected to be accurate to within 5°.


able Doppler Shift in frequency. Further, the Lyman-alpha satellite uses tone modulation of between 2.5 and 15 kilocycles. To record such information, you'll have to use the receiver in its broadest selectivity position and employ a high fidelity tape recorder, capable of recording 15,000 cycles.

Power Requirements. Power to run the Tecraft converter comes from the communications receiver itself, if its power supply is more than minimal, or from a high fi-


delity amplifier or separate power supply. The Tecraft converter requires 6.3 volts ac at 2 amps and 150 to 250 volts dc at 50 ma.

If you are serious about trying to catch those satellite signals, you will find (as we did) that it is wise to run receiver, converter, and frequency standard continuously, day and night, to minimize the warm-up drift and various thermal drifts. We used a 250-watt Sola constant voltage transformer to run all units; this minimizes drifts due to changes in line voltage. While you don't have to have a constant voltage transformer, it will reduce the amount of recalibration.

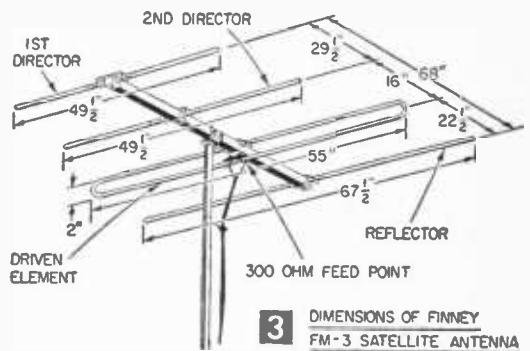Use Frequency Standard. A frequency standard helps to spot the exact frequency with a minimum amount of tuning and retuning. For the Tecraft converter setup (Fig. 2), use a frequency standard to set the communications receiver at the exact intermediate frequency of



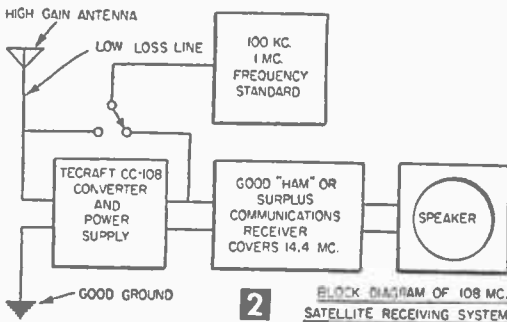3 DIMENSIONS OF FINNEY FM-3 SATELLITE ANTENNA



2 BLOCK DIAGRAM OF 108 MC. SATELLITE RECEIVING SYSTEM

14.400 mc to receive satellite signals on 108.000 mc, or 14.430 mc to receive satellite signals on 108.030 mc.

Although the older model frequency standard which we used would set the exact frequency of the communications receiver, its harmonic output at 108 megacycles was too low to be useful as a double check on the receiving system. Most newer frequency standards do not have this fault.

To put a strong harmonic on 108 megacycles we

TABLE A—EQUIPMENT LIST

To receive the 108 megacycle American satellite signals you will want to use:

1. One of the following weak-signal, low-noise, high stability converters:
 Tecraft CC-108 Converter.....\$44.95
 Tapetone Model TC-108 Converter..... 95.00
2. Finney FM-3 Yagi, 4-element, high gain antenna (with satellite modification) cut to 108 megacycles.....\$7.35
 RG11U, RG59U, or tubular twin lead.
3. Almost any good communications receiver designed for amateur or military use that can tune to 14.4 megacycles.
4. A frequency standard.

(The above converters and the antenna may be ordered from Allied Radio Corporation, Dept. S, 100 North Western Avenue, Chicago 80, Illinois.)

tried using the 24th harmonic of a 4.5 megacycle crystal normally used for alignment of TV sound channels. These crystals and generators for them are widely used by TV servicemen and labs, and are stock items with most jobbers. A simple circuit sets them into oscillation and their exact frequency can be determined by use of the low frequency standard. The 27th harmonic of a 4 megacycle crystal might also be used. We found that a little ingenuity would put a marker right on 108.000 megacycles to further confirm the receiver calibration.

You'll save a great deal of time and improve your chances of hearing if you can obtain the latest timetable for the satellites' orbit from a local newspaper, press service, or IGY facility.

High-Gain Antenna. The difference between hearing and not hearing the American satellites


may well be the difference between a superior and a fair antenna. The antenna used should be cut to 108 megacycles. Figure 3 shows the dimensions of the Finney Model FM-3 antenna as supplied modified to receive 108 megacycle signals; the dimensions of this antenna are critical. For listeners who want to cut down channel 6 TV antennas, all dimensions should be scaled in proportion to the frequency difference.

Use Balun. To prevent losses in signal amplitude, your antenna must be very well matched to the converter input. But both the Tecraft and Tapetone converters have a 52 or 72 ohm unbalanced input, while the impedance at the Finney antenna terminals is 300 ohms balanced. Therefore, you'll need to use an impedance changing and balancing device called a "balun," which is made and hooked up as shown in Fig. 4.


Minimize Line Loss. Signal strengths in the northern portion of the U. S. and Canada will be considerably lower than those in the very southernmost states. In weaker signal areas, and if the antenna and the converter are to be separated by more than 100 ft. of transmission lines, to minimize line loss, use tubular (not the ordinary flat type) twin lead for the longest span between receiver and antenna. Also, install the balun close to the converter and run a short length of 75 ohm coax to the converter.

In higher signal areas or where the transmission line will be under 100 feet, you can install the balun right at the antenna terminals and use coaxial cable (RG11U or RG59U) for the long span down to the receiver.

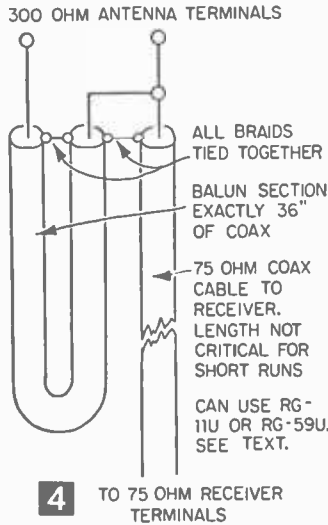In some city locations where electrical noise is very high there may be a gain in overall signal-to-noise ratio if coaxial cable is used for the longer span since extraneous noise pickup by the



4 TO 75 OHM RECEIVER TERMINALS

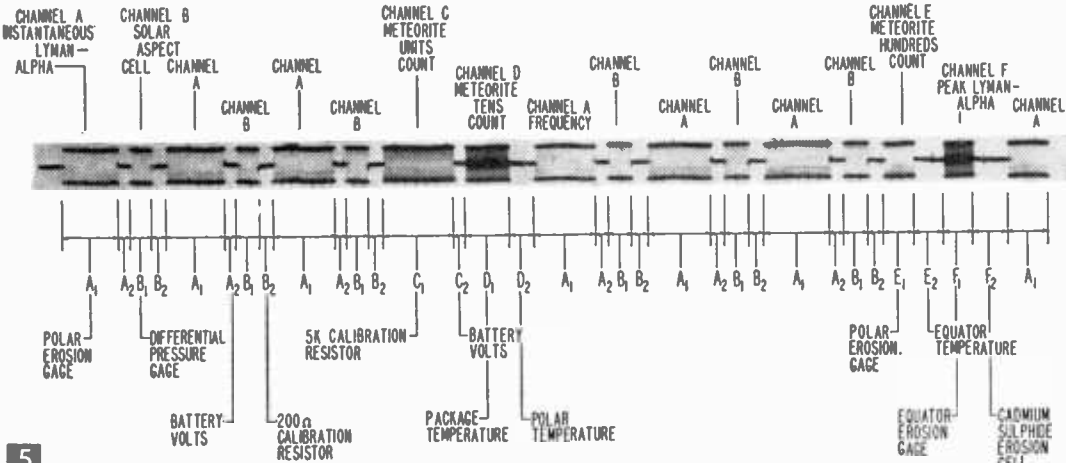

5

Components of typical Layman-alpha satellite telemetry signal. Diagram courtesy U. S. Naval Research Laboratory.

transmission line will be reduced.

The higher the antenna installation the better. Height gives a better chance of receiving the satellite when it is not so high above the listener's horizon. Mount the antenna in the clear, above surrounding objects that would interfere with its directivity and gain.

Antenna Orientation. For observers nearer the equator and up to about 35° North and South latitude, the antenna may point West or West S.W. For more northern or more southern latitudes (up to about 50° latitude) turn the main directivity of the antenna more to the equator. For very northern and very southern latitudes, (in excess of 50°) use a due South direction for the American satellite signals.


Some experimenters prefer to use their arrays mounted vertically since this gives a broader directivity pattern. Others mount their antenna horizontally and use TV type beam rotators, to follow the changing direction of the satellite with respect to the observer.

Coded Messages from Space. The newer American satellites will send back to earth tones which can be decoded as information on the skin temperature, meteorite count and short ultra violet (Lyman-Alpha) radiation from the sun—all these are secrets of space that are now being unlocked for the first time. If you want to be in on discovering what those secrets are, be sure to beg, borrow or buy a hi-fi tape recorder.

Figure 5 shows the telemetering code for the Lyman-Alpha satellite. Note that the information is coded either as a burst frequency, burst duration or spacing between adjacent bursts. The start of each telemetering frame may be recognized by the fact that channel A (instantaneous Lyman-Alpha), a long burst; and channel B (solar aspect), a short burst alternate 3 times. Their sequence is A B A B A B, a long short long short long short sequence.

Cracking the Code. Perhaps the best way for an amateur to crack the code is to use, in conjunction with a hi fi tape recorder, an audio generator and oscilloscope. Run a loop of tape containing the signal continuously through the recorder at its very slowest speed. Mix the recorder output and audio generator output through 100 k resistors at the oscilloscope input. The audio generator may then be varied in frequency to "beat" with a given tone burst frequency and the burst frequency read off the audio generator dial. Be sure to allow for the difference in recording speed and playback speed. Each burst may then be cracked individually.

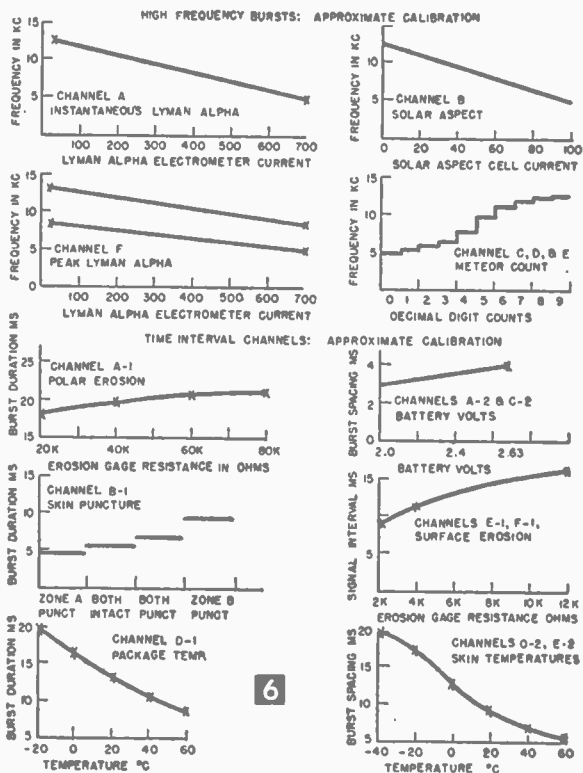You can approximate burst and interval durations in milli-seconds by setting the audio generator to 1,000 cycles per second and counting the number of generator cycles visible during an interval or burst duration. Once again, be mindful of recording and playback tape speed. If the



6

Here are some typical Lyman-alpha satellite calibration curves, as supplied by the U. S. Naval Research Laboratory.

ratio between these two speeds is, say, 4:1, use a 250 cycle timing signal from the audio generator to give a duration of 1 milli-second per cycle on the oscilloscope.

Reporting. Your tape recordings may actually help the American satellite tracking program. For one thing, when a new satellite is launched, amateur observers can aid in plotting its orbit in the first two days of its flight. Your reports, giving your latitude and longitude and the exact time and date and other details on the observation, should be wired to Project Vanguard, Naval Research Laboratory, Washington 25, D. C.

The amateur observer who is able to make good tape recordings can help in another way. While official observing stations will make their own tape recordings, there may be times and locations where an official recording cannot be made, perhaps during a very short solar disturbance.

When such recordings are needed they will be asked for within two days after the event has occurred. So save your recordings for at least two days, and if you are lucky enough to have a recording for one of the periods that will be requested, send this recording, or a copy of it, to the Naval Research Laboratory. Include with it data on the tape speed and type of tape recorder you used, the exact time and date of observation, and the latitude and longitude of the observer.

Radio Remote Controls

Weighing less than 4 lbs. complete with batteries and antenna, this compact radio control transmitter, when used with its companion receiver, will operate models, open doors or perform other tasks you designate.



Operate this ultra-simple crystal-controlled unit in the license-free 27.255 megacycle Citizens' Band to open your garage doors or guide a model plane

By THOMAS A. BLANCHARD

Pulse-Type Transmitter. A remote radio control outfit need not be complicated or expensive in order to perform a number of useful, entertaining functions such as operating garage doors or controlling model power boats, wheeled models or model planes in flight. While there are four Citizens' Bands provided by the FCC in which remote radio control transmitters may be operated without a license (the only requirements are that the apparatus be a crystal-controlled device and FCC Form #505 be filed by a U.S. citizen who is at least 18 years of age), the control shown here operates on the lower 27.255 megacycle band rather than in the UHF 460 megacycle range. Ultra-high frequency controls pose exacting mechanical and electrical design requirements not always accomplished with standard components. Other than the use of a piezoelectric crystal ground to 27.255 mc., the parts used here are conventional. Both the trans-

mitter (Fig. 1) and its receiver mate (see page 57), can be built for less than the cost of a frequency-type relay alone.

The circuit employed here is a basic crystal-controlled oscillator of the continuous wave type. When the control is energized by depressing the push switch, an RF signal is picked up by the receiving unit in the model. The signal to receiver circuit sends a flow of current through the plate circuit, causing the coil of a sensitive relay to become energized. The relay armature carrying the switch contacts is pulled down to close some particular operating circuit in the model.

Make chassis for transmitter of aluminum or steel (Fig. 2A), bending to form a shelf arrangement inside box. Also cut and bend an aluminum or steel strap to serve as a clamp to secure A and B batteries in lower part of utility box.

Transfer switch and tuner holes to front of utility box from chassis, locating them $3\frac{3}{8}$ in. from top of box, and cut or drill. Center $2\frac{5}{16}$ in. dia. meter hole $1\frac{1}{2}$ in. from top of box. Drill battery clamp mounting holes to pass a $\frac{1}{2}$ in. #8



machine screw; space $4\frac{3}{4}$ in. apart, $1\frac{3}{4}$ in. from bottom of utility box.

Connecting all ground leads to the chassis will keep the number of leads on the underside of the control chassis at a minimum (Fig. 3B). Terminate one side of toggle switch on a soldering lug under the same nut used to secure one end of the 6-lug tie strip located on top of chassis (Fig. 3A).


Back up the opposite end of the 6-lug tie strip with the 2-lug tie strip on the chassis underside (Fig. 3B). Attach one end of the $3.3 \mu\text{H}$ RF choke and one terminal of the crystal socket to the grounded lug of the 2-lug tie strip, then solder the remaining end of the choke and one end of the 47K resistor to the tie-strip's remaining insulated lug (Fig. 4). Place a soldering lug under one of the tube socket's mounting nuts, nearest tube pins 1 and 7. A short piece of wire connects pins 1 and 7 to the ground lugs (Fig. 3B).

The switches and variable 35 mmf capacitor are permanently mounted to the chassis. Mount toggle and push-button switches so as to allow enough shank to pass through the aluminum box, and tighten in place with an open-end wrench. Purchase an extra nut with each switch for neatly and firmly securing the chassis later in the cabinet by the threaded switch shanks.


While ordinarily variable capacitors have their rotor shafts grounded, not so here as the capacitor is used to tune the tank coil in the B-plus plate circuit. Both rotor and stator plates must be insulated. Before mounting the 35 mmf capacitor, check to be sure the rotor lug was not grounded at the factory to one of the 4-36 or 4-40 threaded mounting studs. If it was, unsolder and rotate the spring lug so that it rests on the ceramic portion of the capacitor. Mount the unit so that its $\frac{3}{4}$ -in. shaft will be centered in its $\frac{3}{8}$ -in. chassis hole (see Figs. 2 and 3A).

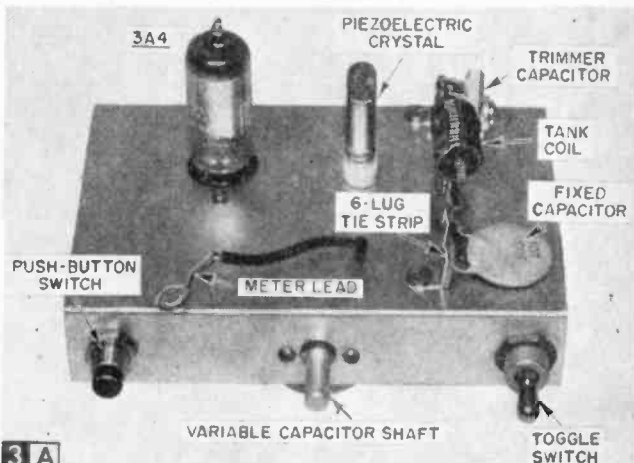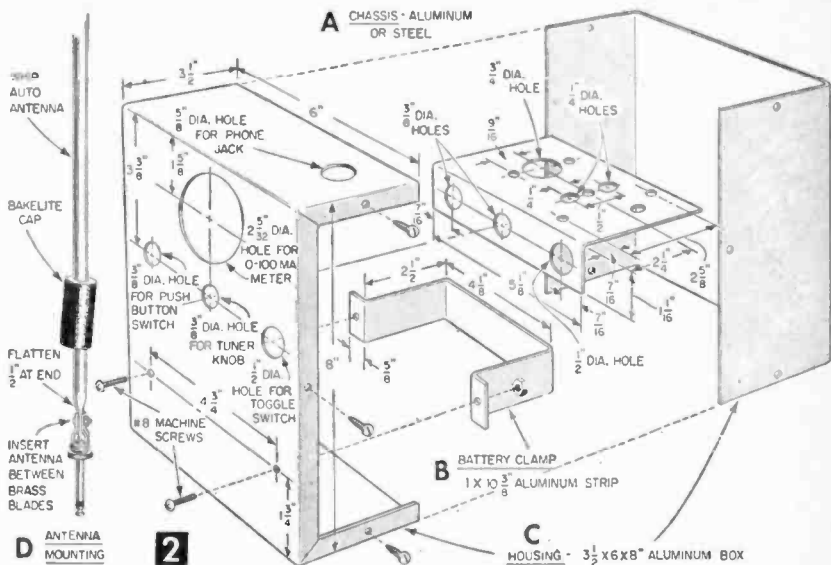

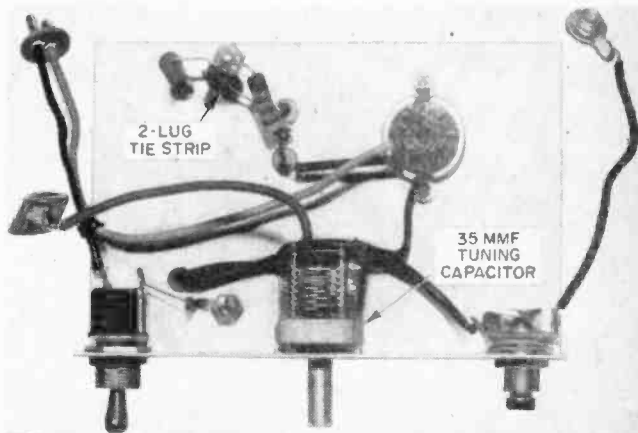
Top view of chassis. The two 4-36 mounting screws for 35 mmf tuner shaft are on $11/16$ -in. centers. Tuner shaft, push-button switch and toggle switch serve as means of mounting chassis in box.



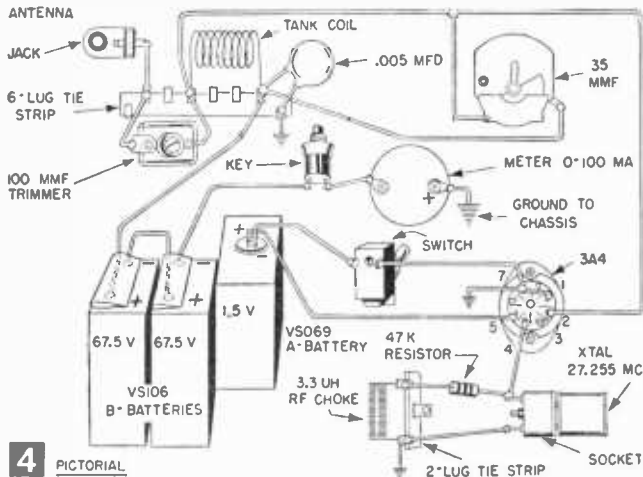Underside of chassis. Grounding lugs keep wiring at a minimum.



4 PICTORIAL

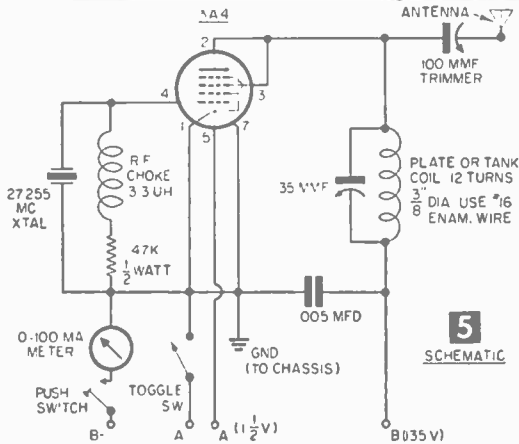

5 SCHEMATIC

The top side of the chassis (Fig. 3A) requires only wiring in tank coil, screwdriver-adjusted trimmer capacitor and the .005 mfd fixed ceramic capacitor. These components are terminated on the first, third and sixth lugs of the 6-lug tie strip. To make a plate coil that will tune 27.255 mc., wind an 18-in. length of #16 enameled magnet wire in a tight spiral around a piece of 3/8-in. dia. wood dowel or metal tubing. When you remove the form, you will have a self-supporting coil. With flat-nose pliers, bend about 3/4 in. at one end of coil wire at right angles. Calling the next turn of wire "one," count off 12 spirals and unwind any excess turns, making another right-angle bend at the 12th turn. Scrape off the enamel insulation from both ends of the coil and mount to tie strip as shown in Figs. 3A and 4.


The trimmer lugs may be soldered directly to the tie-strip lugs without use of hook-up wire which is shown in Fig. 4 for convenience of illustration. Solder the .005 mfd ceramic capacitor from the hot side of the tank coil to the grounded mounting ear of the tie strip. Bring a single lead up from the underside of the chassis and fit the end to a soldering lug which attaches to the minus terminal of the 0-100 ma. panel

meter. Ground the meter's plus terminal by placing a soldering lug under one of the meter mounting screws. Thus only one meter wire is involved when removing chassis from cabinet. Install batteries, securing with aluminum clamp (Figs. 4 and 6).

The plug-in whip antenna can be obtained at the nearest auto junk yard, since none of the original mounting hardware is required. Cut off with a hacksaw near the body mount. Be sure antenna is extended before sawing, or you will saw through one of the telescoped sections, making antenna inoperative.

Place about 1/2-in. of the sawed-off end of the antenna tubing in a vise and compress until nearly flat. Remove the screw-on Bakelite cap from the phone plug and take out the terminal screws intended to secure the phone cord tips. Place the flattened whip antenna between the brass blades of the plug and drill a hole through blades and antenna (Fig. 2). Insert a short 3/32 machine screw (after first sliding Bakelite cap on whip antenna) and tighten securely. Then screw cap back to metal plug.

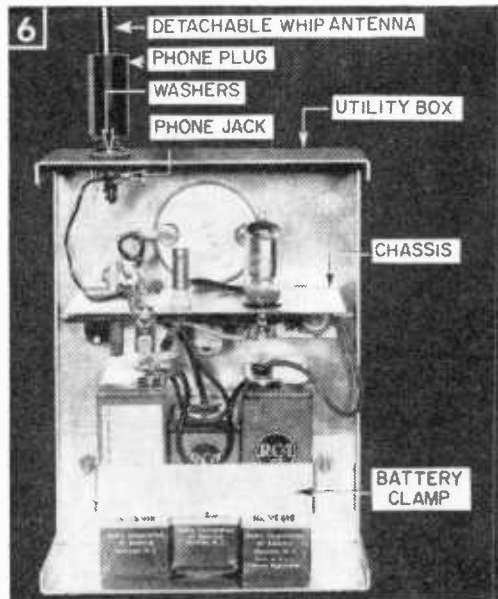Mount a matching phone jack on top of utility box, centering it over the toggle switch. The jack has a 3/8-in. shank, but should be centered in a 5/8-in. hole and backed on each side with a fiber or Bakelite washer so as to be completely insulated from the cabinet (Figs. 2 and 6). Connect a short length of hook-up wire to both soldering lugs on the jack. Terminate the other



Inside view of utility box shows chassis, batteries and antenna installed, and wiring completed. Shelf-like chassis and plug-in antenna can be easily removed from box.

MATERIALS LIST—TRANSMITTER FOR RADIO CONTROL

All parts available from Lafayette Radio, Dept. SM, 165-08 Liberty Ave., Jamaica 33, N. Y.

- 1 3½ x 6 x 8" aluminum radio utility box
hammer-tone gray enamel (housing)
 - 1 Shurite #950 panel meter. Range: 0-100 d-c milliamperes
 - 1 27.255 megacycle piezoelectric crystal in mount
 - 1 ceramic crystal holder
 - 1 miniature pentode tube Type 3A4
 - 1 7-pin miniature molded tube socket
 - 1 S.P.S.T. toggle switch
 - 1 momentary push-button switch (key switch)
 - 1 standard-size phone plug
 - 1 standard-size phone jack
(single or closed-circuit type)
 - 1 2-pin A-battery plug
 - 2 male B-battery Dot snap-fastener type connectors
 - 2 female B-battery Dot snap-fastener type connectors
 - 1 6-lug tie strip with end mounting ears
 - 1 2-lug tie strip with center mounting ear
 - 1 pc #14-gage aluminum ¼ x 5½" (chassis)
 - 1 pc #14-gage aluminum battery clamp 1 x 10¾"
 - 1 1½ volt A-battery, RCA Type VS069 or equiv.
 - 2 67½ volt B-battery, RCA Type VS016 or equiv.
(connected in series for 135v.)
 - 1 18-in. length #16 enameled magnet wire for tank coil
 - 1 IRC 3.3 microhenry RF choke, Type CLA
 - 1 47K ohm (47,000) ½-watt composition resistor
 - 1 35 mmf. miniature tuning capacitor
 - 1 4-80 or 100 mmf. trimmer capacitor
 - 1 .005 mfd. ceramic capacitor
 - 1 auto whip-type antenna, extending to 6 ft.
- Misc. hardware, chrome handle, hook-up wire,
⅝" knurled knob.

end of the lead to lug #1 of the 6-lug tie strip where the trimmer capacitor is located (Figs. 4 and 6.) For carrying convenience, attach a chrome metal handle to side of the utility box.

Your radio control transmitter is now ready for testing. Because it includes a built-in meter, you always know if the signal is getting out by

Occupying only a 2x 3½-in. area this tiny receiver easily fits on underside of model boat decking.

the extent of the needle swing. With batteries connected, toggle switch at on and push switch depressed, rotate the 35 mmf capacitor knob until the meter dips to the lowest reading (about 20 ma. without antenna). The circuit is then in resonance and sending out a signal.

To transmit the maximum signal possible with this control, the 80 or 100 mmf trimmer allows the antenna coupling to be adjusted for maximum loading. Plug-in the fully-extended whip antenna; then, with a plastic-blade screwdriver close the plates of the trimmer by turning the screw clockwise. Watch the meter for any sudden swing of the needle. If the needle shoots up to 60 ma., try to bring the circuit back into resonance by turning the front control knob. If this proves ineffective, loosen the trimmer screw until the meter can again be dropped by rotation of the 35 mmf knob to about 20 ma. The trimmer screw need

be adjusted only once. Thereafter, whether the antenna is used partially telescoped or fully extended, you only need rotate the knurled knob until the lowest reading is obtained with push switch closed.



Because the rise of current is quite sudden when circuit resonance ceases, the sharp needle swing provides the operator with a continuous check on the control. Should there be any influence on the circuit through body capacitance, making it difficult to maintain the lowest meter reading, change the value of the 47K grid leak resistor to a lower value such as 39K.

Exposing set-screw of ⅝-in. knurled tuner knob to body contact may affect meter reading during circuit adjustment. In this case, coat head with nail polish, or cover with tape.


Receiver. The circuit board on which the receiver is constructed is available in panels of various sizes, or larger pieces may be cut to size. Holes, ⅜ in. dia. are located ¼ in. apart. The holes are arranged geometrically.

Small phosphor bronze connectors known as "Flea" clips may be inserted into the ⅜ in. holes. Flatten spade end of clip with pliers, allowing transistor or tube leads to clip firmly in place. Pigtailed components such as capacitors and resistors may have their leads threaded through the holes, thus providing a secure mounting.

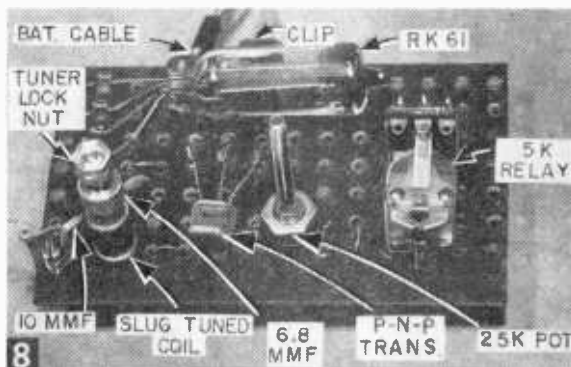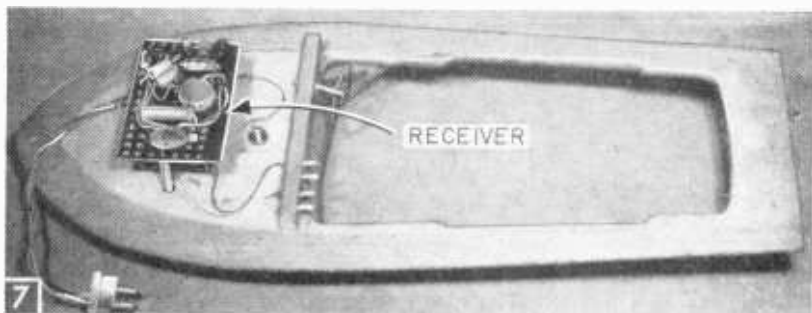The relay is a minute s.p.d.t. type with a 5K ohm coil. Either the Lafayette 5K "Gem" or "Jewel" types may be used. The function of the



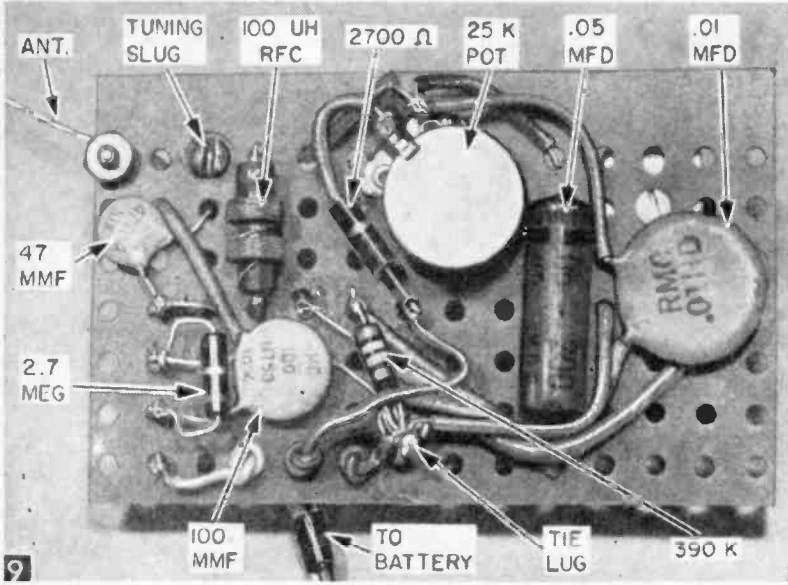Top side of receiver showing how parts are mounted on panel of perforated Bakelite. Geometric arrangement of holes provides a versatile wiring board.



Underside of receiver. Wiring board holes allow set to be mounted with two or more small metal studs in whatever position best fits the particular model.

relay is similar to that of a speaker. A relay, however, converts the signal into motion, whereas the speaker converts the signal into sound. Motion in this case is to cause the relay contacts to open or close and control other circuits which in turn provide the necessary animation—banking, looping, starting, stopping, forward, reverse or turning.

Tuning the receiver to the 27.255 mc. signal sent out by the transmitter is accomplished by a special slug-tuned coil. Lafayette Radio will provide a 1/4-in. coil form, 3/4 in. long fitted with aluminum threaded ferrule and slug. Two silver rings are pressed over the coil form to provide termination for each end of the coil winding. The winding consists of 22 turns of #30 enameled magnet wire close wound in the center of the form. Each end of the winding is scraped clean of enamel, then soldered to the silver terminals. A thin coat of Duco cement may be flowed on the finished coil to give it some rigidity.

While the cement is drying, the parts may be installed on the wiring board as in Fig. 12. Dimensions are not needed because the board holes will automatically provide for suitable parts locations. Mount the relay with a single jeweler's type screw (provided) and the antenna lug and tube clip with 4-40 x 1/4-in. binding head machine screws and nuts. When mounting the tube clip, place another soldering lug on the underside of the same screw. This lug serves as a tie point for all the leads and components in the A/B-circuit.


The tube clip can be either of two things: A catch as used to secure the doors on kitchen cabinets, or the type

of clip used to mount electrical cartridge fuses in many home and factory wiring systems. Both clips must be "sprung" because too much clip tension may break the tube. The clip gap should be about 1/2 in. which is the diameter of the RK61 triode.

While the CTC-LSM coil form is provided with a threaded ferrule for panel or chassis mounting, it is mounted in the lower right hand corner of the wiring board (Fig. 12) in reverse fashion by enlarging one of the 3/32-in. holes to 1/4 in. Cement the Bakelite tube, not the ferrule, into this hole with

Duco or Pliobond cement. Both the .05 mfd tubular paper capacitor and the 100 uH R. F. choke are threaded to the panel board to make them secure. One end of the choke and one end of the .05 mfd terminate on Lug #1 of the 25K potentiometer. This is a subminiature type mounted in a 1/4 in. hole. Opposite ends of choke and capacitor terminate on tube and transistor "Flea" clips as shown in Fig. 11.

With all wiring completed, the receiver is ready for testing and adjusting to 27.255 mc. Install tube in clip and attach pigtail leads to respective "Flea" clips. Cut off excess pigtail leads on tube. Observe that tube lead #1 is identified by a red dot on the glass with other leads following in sequence (Fig. 10). The transistor (C) collector pigtail lead (Figs. 10 and 11) is identified by a red dot on the side of the unit, or by the fact that a wide space separates it from Base (B), the center lead, and Emitter (E), the remaining outside pigtail lead.

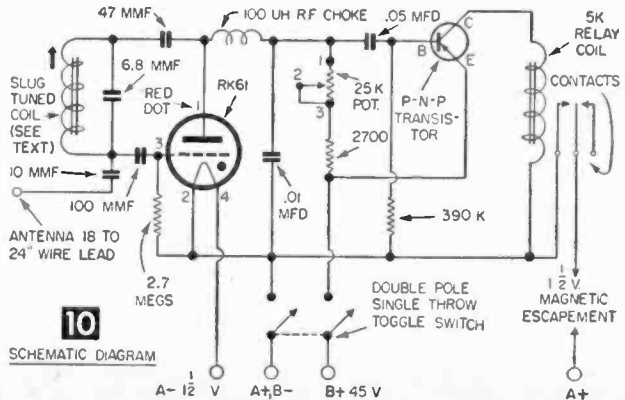

10 SCHEMATIC DIAGRAM

matic plan, however, shows relay wired into 1½-volt filament circuit for triggering rubber-band powered escapements used to control flight of model planes. To test your receiver at distances,



14

Model boat can be maneuvered remotely in a tight loop, sweeping circle, zig-zag course or follow a straight line. Insert photo shows close-up of factory-built model boat which comes equipped with battery-powered, electric motor propeller drive.

insert a 1½-volt penlight bulb at arrows. Then after dark, you can determine just how effective your little radio control transmitter-receiver rig is. For receiver antenna any sort of insulated wire may be used. Length may vary from 18 to 24 inches.

In tests following the construction and installation of the receiver in the model boat (Fig. 7), we found that the receiver acted in an erratic fashion at times. The probable cause for this is due to the circuit employing a gas-filled triode (thyatron) as detector. At the same time, the circuit employed is a super-regenerative type. This circuit is oscillating all the time and may well be creating a feedback effect so as to keep the relay energized unless the antenna is loaded up excessively.

After trying loading coils in the antenna circuit as well as varying grid bias, the solution to



View of hull with deck removed to show location of parts and deck screw holes.

erratic operation and *really* stable receiver performance was obtained with a capacitor-resistor by-pass connected from the input (grid) end of the R. F. tuning coil to ground (A, B), Fig. 13.

Model Boat Control. Use an inexpensive, ready-made 16-in. model boat (see Fig. 1 and materials list), which may be purchased at your local toy store.

The boat is propelled by a single screw propeller driven by a miniature PM motor. Power is supplied by four standard D-size flashlight cells. Two hand-thrown switches turn on motor and/or running lights. Hull is plastic.

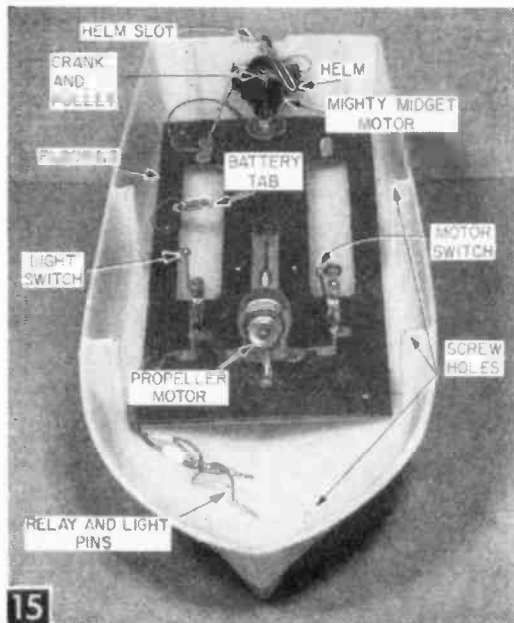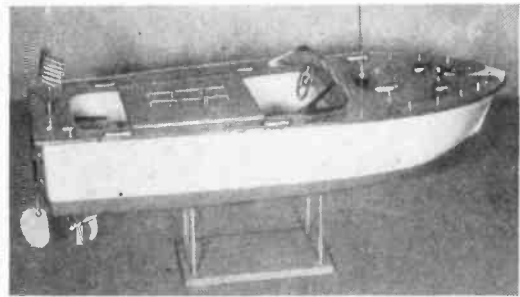To install your radio control system, first remove the wooden deck. The hull is molded of an acetate that melts at about 350° F, and will release the drive screws if they are heated sufficiently. Place the tip of a soldering gun or heavy-duty iron on the head of each screw, and at the same time, lift up on the deck; each drive screw will spring loose from the bulkhead as it is



15


heated. Repeat the operation for all eight screws and the deck is off!

Then with a $\frac{5}{64}$ in. twist drill inserted in a pin vise (hand chuck) clean out the bulkhead screw holes (Fig. 15), turning the pin vise by hand—do not use a power drill. The drill will go down about $\frac{3}{8}$ in.—drill no deeper than original holes. With holes thus reamed out, the deck can be replaced with conventional #2 x $\frac{3}{8}$ in. rh brass wood screws. The screws will cut their own threads into the plastic and may be inserted or removed as often as necessary. The boat flooring which carries the battery holders, and the PM motor (Fig. 15) are also secured with drive screws. Replace them with #2 rh wood screws in the same manner.


Now mount the radio control receiver on two 1 in. spacers with 4-40 x $1\frac{1}{8}$ in. rh machine screws to the underside of the bow deck (Fig. 16). Drill a $\frac{1}{4}$ in. hole in the deck to clear the tuning coil adjustment screw and a $\frac{1}{8}$ in. hole to pass the shaft of the potentiometer sensitivity control. Then drill another $\frac{1}{4}$ in. hole just forward of the windshield for the antenna jack connector.

Connect the receiver battery leads (shown in Fig. 13) to the male side of a 3-pin, Amphenol miniature connector. A minus connects to Pin 1. A plus B minus connects to Pin 3 and B plus to Pin 2. Connect the female socket to the batteries which are located on the underside of the boat hatch cover (Fig. 17). The receiver A battery is the medium C size flash cell which snaps into a battery holder as used in transistor radios. The B battery is a 45 v. Burgess U-30 hearing-aid type cell. A simple clip was fashioned from a strip of aluminum to hold the B battery to the hatch cover.

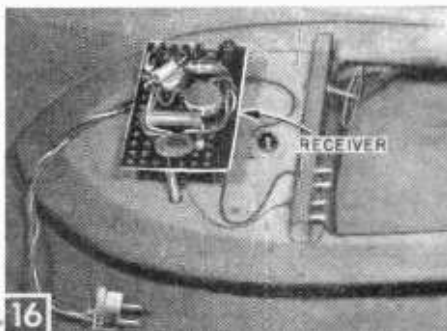The original wiring for the boat running lights was cleaned up, covered with strips of Scotch masking tape, and the leads terminated to clips mounted on the dash. The two normally open relay contacts were then connected to another pair of clips on the dash. The connectors used here were contacts salvaged from an old octal wafer tube socket. By drilling four $\frac{1}{8}$ in. holes



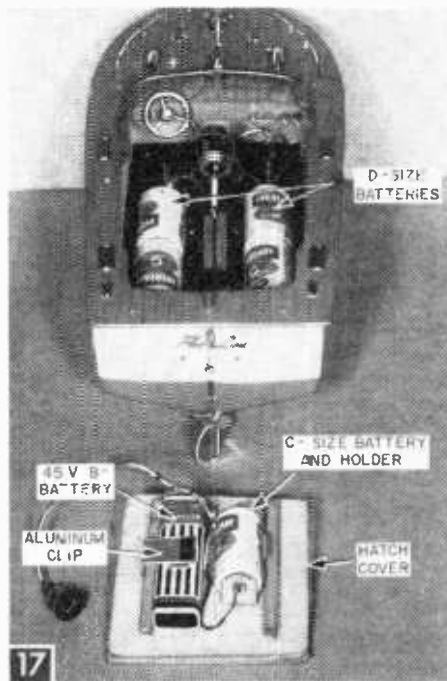Remote-control radio-receiver is mounted to underside of forward deck.



Stern view of boat with inverted hatch cover in foreground to show location of batteries.

in the dash, the contacts make a press fit. Contact pins are nothing more than brass shade bracket nails to which leads are soldered. If the builder desires, the separate dash connectors may be eliminated by using a 7-pin miniature male and female connector in place of the 3-pin type shown.


Pilot Control. While we have limited the radio control here to steer the boat, the same mechanism may be expanded to stop the motor mid-stream, turn on the lights. These no-cost additions can be made by the experimenter.

A conventional escapement would (if space permitted) allow the boat to be operated forward, 90° right, and 90° left. With the system used here, the turn is not fixed. The boat can operate in a tight loop, or sweeping circle, it will respond to zig-zag course, or follow a straight line. All this is accomplished by a miniature geared-down PM motor with a simple homemade eccentric helm drive.

The *Mighty Midget* motor is a British import selling for under \$3. It includes a 6:1 gear reduction with a small brass pulley for normal power take-off. First loosen the set-screw securing the large gear, so that the drive shaft carrying the swaged-on pulley can be removed. Then fashion a small crank from a piece of solid bare copper wire and solder to the pulley as in Fig. 18B. Place a 2-56 machine nut on the motor shaft before reassembly so that the nut acts as a bearing and allows the pulley to clear the motor housing when operated in a vertical position.

Mount the *Mighty Midget* to the hull transom (Fig. 15) with two 2-56 x $\frac{3}{8}$ in. brass rh machine screws. Drill mounting holes $1\frac{1}{16}$ in. apart and $1\frac{1}{16}$ in. from the top edge of the hull. With a file, make a slot in the transom, $\frac{1}{8}$ in. deep and 1 in. wide to clear the helm. Before permanently mounting the motor to the transom, however, make up the helm.

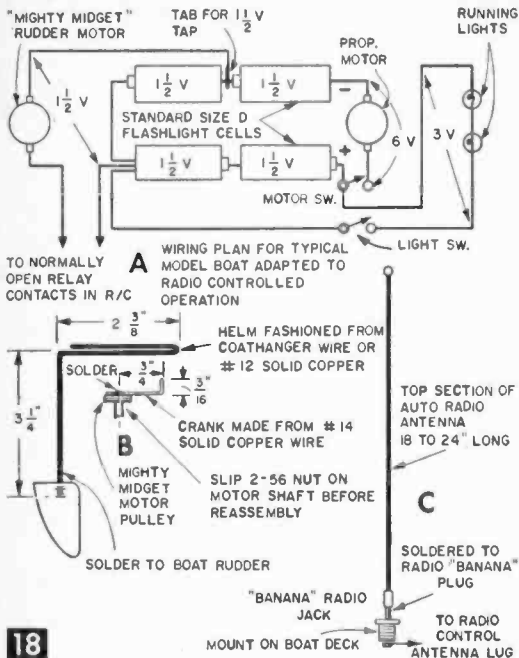
The rudder on the original boat, made a snap



18

fit into a socket-hole in the keel. The rudder was set to the desired angle by hand and remained so fixed until changed. For our remote control boat, the original rudder still is used but altered slightly.

First remove it by pulling it out of the keel socket, then unsolder the short brass pin. Make the helm from a length of solid copper wire, or light coathanger wire approx. #12 gage or the diameter of a #46 twist drill. Bend the wire to the shape shown in Fig. 18B with special care given to the hairpin bend. Attach the helm to the stern with a pair of radio lugs of the type used on tie-strips. Bend the lugs at right angles so that the eyelet portion forms a bearing for the wire helm. Fasten the lugs to the stern with #2-56 x 1/4 in. rh machine screws. Drop the helm through the bearings, fit the rudder in place and resolder. When soldering the rudder, apply a wad of wet cleansing tissue to the helm and lower bearing to act as a heat sink so that no harm comes to the plastic hull.

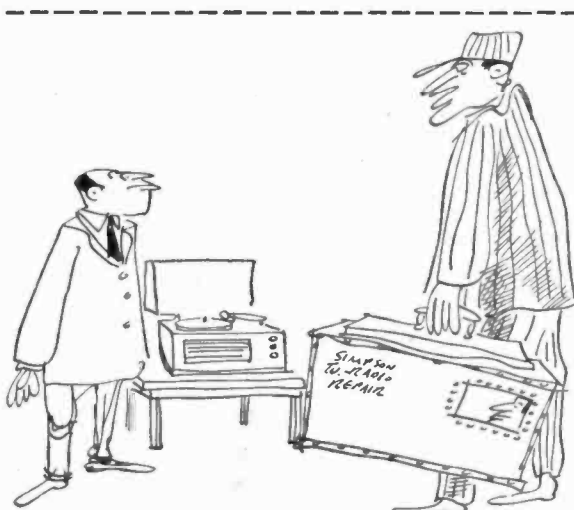

D. Vietor

"I brought Harry along—he's our expert on portables."

MATERIALS LIST—REMOTE CONTROL MODEL BOAT

- 1—Pre-built model Sports Cruiser, the "Sea Wolf" by K & O Models, Inc., 14720 Keswick St., Van Nuys, Calif. Sold by dept. and toy stores. Boat is 16" long with 7" beam. Price \$9.95.
- 1—"Mighty Midget" 6:1 gear drive motor by Victory Industries (Surrey) Ltd., Guildford, England. Sold by Lafayette Radio, Jamaica 22, L. I., N. Y. Price \$2.95.
- 1—45 V. hearing aid battery (Burgess U-30), B-battery connectors, 3-pin plug set, "C" flashlight battery holder also from Lafayette Radio.
- 2—doz. #2 x 3/8" rh brass wood screws.
Misc. electronic items as needed available from either Lafayette Radio, or Allied Radio Corp., Chicago.

The helm motor operates on voltages from 1 1/2 to 6. However, since it is desired to have it rotate slowly, only 1 1/2 volts are applied to it as against the full 6 volts applied to the screw motor. To accomplish this, make up a battery tap from a bit of thin brass or tin-can stock. With a 1/4 in. bolt dimple one end of the strip of metal by placing it on a block of soft wood and striking the bolt a sharp blow with a hammer. Then, with a tinsnips, cut the strip to the shape of a large soldering lug or tab. Insert it between two of the flashlight cells as shown in Fig. 18A, fitting the dimple over the brass battery cap where it will not be dislodged.

Before replacing the deck, check to see that the brass flag holder does not extend below deck and thus foul the helm action. If this little boat fitting isn't flush with the underside, file or grind off any excess. Then fasten the deck.

With the radio control receiver adjusted as explained earlier, and all wiring in place, your boat is ready for a dry run. Press down the operating key on the transmitter and note that the rudder runs back and forth. With a little practice, you'll be able to key the transmitter so as

to swing the rudder to any position you desire. Rotate the receiver control left to right. This will allow the helm motor to run. Slowly turn the control to the point where the helm motor just stops. The receiver is now adjusted at maximum sensitivity.

Do not operate the screw motor out of water and expect the radio controlled helm motor to act normally. The full 6 volts is applied to the screw motor because of the resistance offered when



This dime-store toy truck was converted into a remote controlled robot that responds to "push button" commands of— forward, back-up, turn or stop.

the propeller is submerged in water. Out of water, the screw motor runs wild, and sets up so much vibration that it jars closed the sensitive relay contacts which start and stop the helm motor. These false pulses can make it appear that the radio control is "on the blink" when it actually is working perfectly.

To make the boat tamper-proof, no toggle switch was included in the wiring circuit. To shut off power to the receiver, disconnect the 3-pin plug. To increase the range, the A plus B minus lead from batteries may be grounded to the metal motor housing. This takes the connection directly to the water via the prop shaft.

The antenna for the radio remote controlled model boat can be any piece of stiff wire 18 to 24 in. long. Solder the end of the wire to a "banana" plug which fits the jack mounted on the deck (Fig. 18C). An excellent antenna will be found in the top wire section of an au' radio antenna which can be picked up at any junk yard.

The radio control does not affect manual operation of the boat as it can always be operated manually without alterations. Set helm by turning the large helm motor gear with the fingers to whatever fixed course is desired.

Motorized Robot Truck. While we do not claim that this little radio controlled truck shown in Fig. 19 can do everything a real car can do, it comes darn close to it.

The foundation of the project is a pressed-steel toy moving van made by Louis Marx & Co., and sells for \$2.95. The same chassis with a stake body is \$1.95, and although we used the moving van model, we would advise the latter be used since it is lighter, thus requiring a smaller traction motor. The various mechanical motions are home-made from #16 gage aluminum or brass, while the "tricky" drive gear problem is

solved by A. C. Gilbert Co., makers of *Erector*.


After obtaining the truck, remove the body and cab from the chassis (Fig. 20). As with most metal toys, these parts are secured with bent-over tabs which must be straightened out to

19



disengage the parts. After removing the parts, press the tabs flat in a vise so that they will serve to register the location of the cab and body on the chassis for reassembly. The tabs will not be used for fastening since the cab and body will be secured with 6-32 machine screws so the parts can be removed as often as necessary.

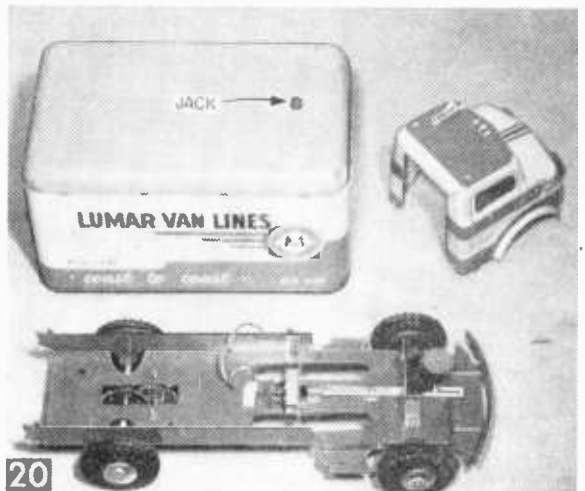Next, remove the wheels and axles from the



20

Cab and body of toy truck are removed to permit installation of steering and drive unit on truck chassis. Radio receiver, remote controls and batteries are located in truck body.

truck by filing down the burr on the swaged end of each axle. Then lay out and cut a $2\frac{5}{8} \times \frac{3}{4}$ opening in the chassis (Fig. 21) over the rear axle to clear the 9:1 ratio gear train. Cut the opening by drilling a series of holes along the layout and cutting between the holes with a chisel.

One of the truck wheels must be rigidly secured to the rear axle. Fasten by applying Pliobond all-purpose cement to the "headed" end of the axle for a distance of $\frac{3}{4}$ in. Also coat the inside of the wheel "bearing" with cement using a pipe cleaner for an applicator. Allow both parts to set for an hour. Then apply a second coat of Pliobond to the axle and slip the wheel in place. Now set axle and wheel aside and allow 24 hours for drying. The remaining rear wheel is allowed to turn freely for differential action as on a real car.

Fortunately, the truck axles are the same size as the bore in the Erector gears. Slip the #CJ 36-tooth, 1-9/16 in. dia. gear on the rear truck axle and lock in position with the set screw. Place the other wheel on the axle and apply a drop of solder to the hub cap. Next make the

two gear brackets (Figs. 21 and 22) to support another #CJ gear and a #P-13, 12-tooth, pinion gear. Use the original front truck axle, which is to be replaced with a modified Erector steering mechanism, for the 2 in. length of shafting that is needed to support the CJ and P-13 gears on the brass brackets.


The power take-off gear (Fig. 21) is another P-13 pinion type. However, since the gear is drilled for a $\frac{5}{32}$ in. shaft, and as all miniature PM motors come with a $\frac{3}{32}$ in. shaft, an adaptor is required. A simple solution was found for this problem by drilling a $\frac{5}{32}$ dia. $\times \frac{3}{8}$ in. long aluminum rivet, through the center. File one end of the rivet half way through as in Fig. 22, and slip it into the hole in the gear with the filed portion under the set screw. When tightened, the set screw will then lock up against the $\frac{3}{32}$ in. motor shaft.


Of the several sizes of PM motors available from model supply houses, select a *heavy duty* or *super* type which will provide the necessary torque. A smaller, less powerful motor can only be used by adding an additional CJ and P-13 gear supported on brackets ahead of those that are shown in Fig. 21.

Locate mounting holes on chassis for gear-shaft bracket and motor by trial set up. Do not mesh gears too tightly or they will not turn freely. The distance from center of rear axle to the shaft supporting CJ and P-13 is 1 in. as is the distance from shaft to center of motor shaft. With gear train properly lined up, apply petroleum jelly, a light lubricant, to the gear teeth and shaft bearings. After hooking up the motor to several flashlight batteries a quick check on how your transmission functions should spur you on to the next step — the radio-controlled steering and switching system.

The front wheels of the toy truck, when purchased, do not steer. They are attached to a fixed axle the same as the rear wheels. Your first step is to cut off the fixed axle hangers from the chassis and install a functional steering mechanism. For this purpose, we were able to adapt Erector's #MI Front Axle Unit as included with their #9½ Automotive Set. It can be purchased separately for 25¢.

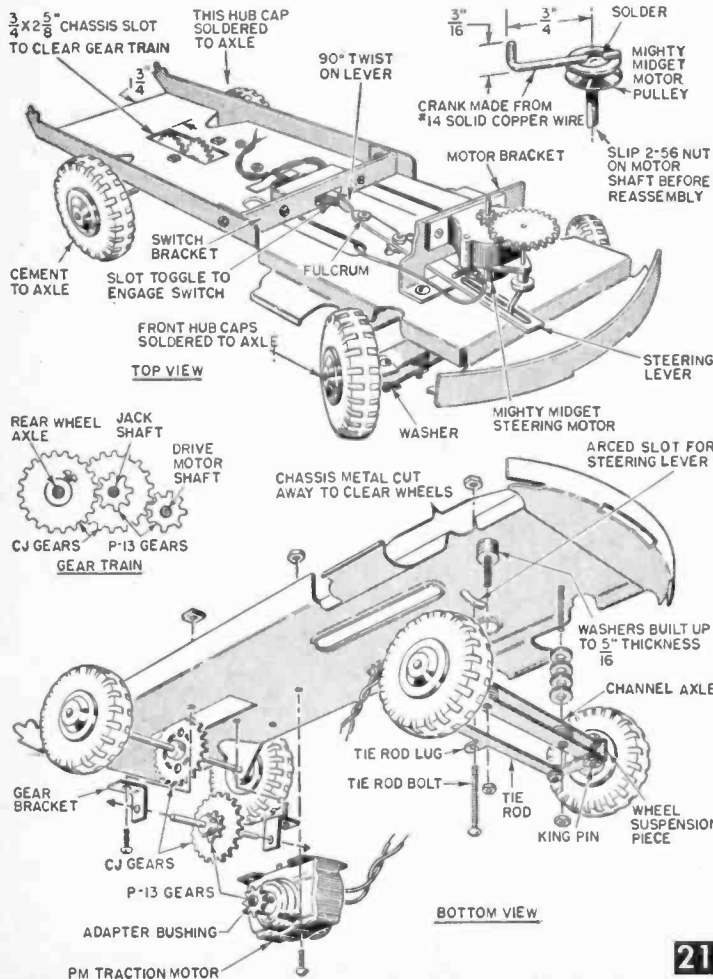The axle unit measures 6 in. wide and must be cut down to $4\frac{1}{4}$ in. to fit the truck chassis used. Because this assembly



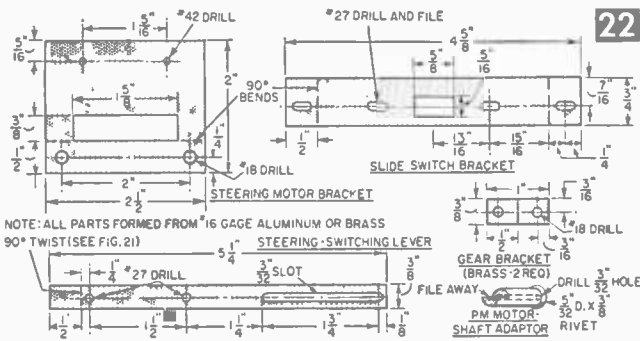

is loosely fitted with rivets, the latter are ground off and later reassembled with machine screws (Fig. 21). As received, the steering gear lug on the tie rod is off center to the left. The distance from the lug to the nearest tie rod end hole is 2 in. By cutting off the longer end of the tie rod and drilling a new hole, we have now placed the tie-rod lug in the exact center of the shortened tie rod. Now cut off the channel-like axle member to which kingpins and wheel suspension are mounted and drill a new kingpin hole $3\frac{5}{8}$ in. from the outside hole at the opposite end of the axle. Finally drill a new #18 axle mounting hole $\frac{3}{4}$ in. from the kingpin hole and 2 in. from the original axle mounting hole. To provide steering clearance for the front wheels, snip off part of the chassis at the front and rear of the wheels as in Fig. 21.

The steering mechanism is now reassembled. Because the axle channel piece makes a very loose fit with the wheel suspension, shim each end with 1/16-in. thick washers to remove excess play. The kingpin screws are 8-32 x $\frac{5}{8}$ " rh brass. Draw up the nuts as tight as they will go without binding. The tie rod pins are 8-32 x $\frac{3}{8}$ " rh brass machine screws. After all nuts have been properly adjusted, secure them with a drop of solder so that there is no chance of their working loose from vibration.

To mount the axle assembly on the chassis, drill two #18 holes 2 in. on centers as in Fig. 21. These holes also serve for mounting the steering motor bracket (Fig. 22) which should be made at this time and assembled together with the front axle to the chassis with

6-32 x $\frac{3}{4}$ in. machine screws. Place washers or spacers on the screws under the axle to support it $\frac{5}{16}$ in. away from the chassis. Insert washers or spacers $\frac{1}{4}$ in. thick inside the channel so that when the screws are tightened, the channel is not compressed.


To bring the steering action to the top of the chassis cut a $\frac{1}{4}$ x $\frac{7}{8}$ in. arc slot through the chassis centered with the hole in the tie-rod lug (Fig. 21). Then secure a 6-32 x $1\frac{1}{2}$ -in. machine screw to the tie-rod lug with

a nut. With wheels pointed straight ahead, drill a #18 hole $1\frac{1}{2}$ in. behind the steering screw in the chassis and insert a 6-32 x $\frac{1}{2}$ in. screw secured with a nut. This rigid screw will serve as fulcrum for the steering lever made from a strip of aluminum as in Fig. 22. To cut the slot, first drill a series of $\frac{3}{32}$ in. holes, then file to shape. When assembling the steering lever to the chassis, place washers on both the steering and fulcrum screws so as to support the lever $\frac{1}{4}$ in. above the chassis. Note in Fig. 21 that the portion of the lever behind the fulcrum screw is twisted 90° so as to engage a slot filed into the Bakelite switch toggle. Make the steering-motor crank as in Fig. 21 and solder to the motor pulley. Place a 2-56 nut on the motor shaft before reassembly so that the nut acts as a bearing and allows the pulley to clear the motor housing when operated in a vertical position. Mount the motor on its bracket so that the crank engages the slot in the steering lever.

When the steering motor is energized, the crank actuates the lever causing two functions to be performed: (1) The lever moves the screw from the steering mechanism back and forth to

MATERIALS LIST—RADIO CONTROLLED TRUCK

- 1 Pressed-steel toy truck with 10" wheelbase (17" overall). Made by: Louis Marx & Bro. Co., Toy Center Bldg., 200 5th Ave., New York, N. Y. Sold by toy, variety, and dept. stores everywhere.
- 1 Steering motor. "Mighty Midget" sold by Lafayette Radio, Jamaica 33, N. Y.
- 1 Traction motor. Any PM heavy duty shunt type. Sold by local model shops. Also from L. Barnett, IMP Products, 33 Union Sq., New York 3, N. Y., or Polk Models, Crafts & Hobbies, Inc., 314 5th Ave. (at 32nd St.), New York, N. Y.
- 1 Erector #M1 "Front Axle Unit" price 25¢.
- 2 Erector #CJ "36-tooth Gears" price 20¢ each.
- 2 Erector #P-13 12-tooth pinion gears, price 10¢ each.
- Erector axle rod/shafting also available in following lengths at 1¢ per inch: 1", 2 $\frac{7}{8}$ ", 4", 5", 7", 10" and 19 $\frac{3}{4}$ ".
- Order Erector Parts from: Mrs. M. M. Wool, Consumer Dept. A. C. Gilbert Co., P. O. Box 1610, New Haven, Conn.
- 2" x 8" x 16 ga. sheet aluminum used for brackets can be obtained from local sheet metal shop. Brass available from local auto parts dealers or hardware store.
- 1 Double Pole—Double Throw Slide Switch from Radio Parts Suppliers. Made by: Stackpole Carbon Co., St. Marys, Penna.
- 1 $\frac{5}{32}$ " dia. x $\frac{3}{8}$ " long aluminum rivet
- 2 $\frac{5}{32}$ x $\frac{1}{4}$ " rh brass machine screws for gear bracket
- 2 $\frac{5}{32}$ x $\frac{3}{8}$ " rh brass machine screws for axle king pins
- 2 $\frac{5}{32}$ x $\frac{3}{8}$ " rh brass machine screws for axle tie rod
- 2 $\frac{5}{32}$ x $\frac{3}{8}$ " rh machine screws for axle mounting
- 1 $\frac{5}{32}$ x $1\frac{1}{2}$ " rh machine screw for tie-rod lug
- 2 $\frac{5}{32}$ x $1\frac{1}{8}$ " rh machine screws for mounting body
- 4 $\frac{5}{32}$ x $\frac{1}{4}$ " rh machine screws for switch bracket
- 1 $\frac{1}{4}$ " x $\frac{1}{4}$ " rh machine screw for lever fulcrum
- 4 $\frac{5}{16}$ x $\frac{1}{2}$ " rh machine screws for mounting motors
- 2 $\frac{5}{32}$ General Cement Co. spade screws for mounting cab

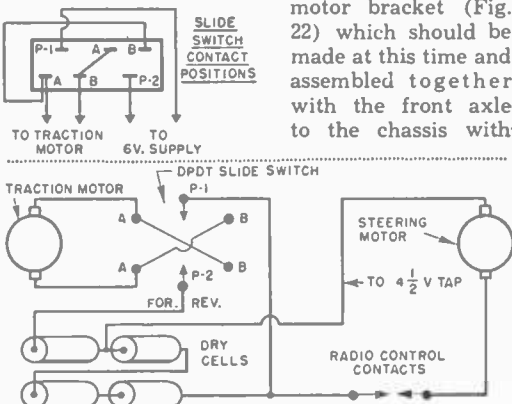

23 SCHEMATIC

turn the wheels. This is a 2nd class lever function. (2) At the same time the lever provides 1st class duty by moving a D.P.D.T. slide switch back and forth. This switch causes the traction motor to run forward, stop, and reverse.


There are several makes of slide switches available, all of which require modification. Since some sort of snap action is provided internally, the switch must be made to slide easily. The Stackpole switch shown is probably most simple to convert. However two switches must be purchased. Lift up the tabs on the switch frame so that the contact strip may be removed. Cup your hands while doing this to hold the spring.

As shown in Fig. 24, the Bakelite toggle contains two $\frac{5}{32}$ in. dia. holes into which the pole tension springs are inserted. The countersunk hole accepts a button-type silver slide contact. The plain hole accepts a silver ball contact. The ball is both contact and detent causing the switch to snap into position. To remove this friction, the ball contact is replaced with another button contact and its spring taken from a similar switch. Countersink the plain hole in the Bakelite toggle, or throw, to match the other hole before replacing with button contact. With springs and button contacts positioned, reposition the contact strip on the frame, and bend down the lugs. Apply petroleum jelly to the inside surface of the switch frame before reassembling so that toggle slides easily.

Make the slide-switch bracket (Fig. 22), mount the switch on it and assemble the bracket to the chassis as in Fig. 21. Note that all bracket holes are elongated with a $\frac{1}{8}$ in. dia. file so that when the lever engages the slot filed in the Bakelite toggle, the switch can be positioned correctly both for forward-back, and side-to-side alignment.

The hole in the end of the lever which slips over the fulcrum screw should be a close fit. The hole in which the steering screw is engaged, however, should be elongated slightly. Both the $\frac{1}{8}$ in. round file and $\frac{1}{16} \times 7/16$ in. flat file are most useful in dressing down any points in the mechanical linkage where binding may occur. Turn the gear on top of the Mighty Midget motor by hand and make necessary adjustments before applying power to the motor. PM motors should never be operated in a stalled or jammed condition as some parts may be ruined.

Once smooth mechanical action is obtained, turn down the 6-32 nuts so they just touch the lever. Now apply a drop of model airplane cement to the threads to lock the nuts in position. Two flashlight cells attached to the steering motor, with front wheels propped up, will allow you to see just what happens. The 6:1 geared down steering motor turns the crank which is soldered to the pulley. As the crank rotates, the lever swings the wheels and the toggle on the switch back and forth. When the wheels are turned partially or completely to the right, the auto runs forward. When the steering motor carries the

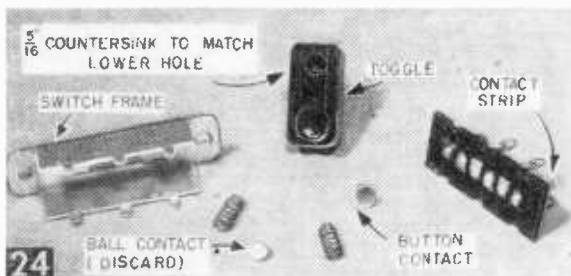

Performance of radio controlled truck is accomplished, in part, by modified slide switch. Stackpole D.P.D.T. has been disassembled to show parts.

wheels left, the switch reverses the traction motor causing the car to back up. At a point just off a straight wheel position, the switch disengages power to the traction motor and car stops.

Because of the rapid action of the relay contacts in the receiver, the switch can be made to pass through an undesired function simply by holding down the transmitter key until the desired sequence is reached. After a little practice, the operator can tell by noting the position of the wheels if a long or short pulse from the transmitter is needed.


Because the reverse-forward actions take place when the wheels are in a turning position, the effect is most realistic especially when backing up the truck for a turnaround. Anything reduced to the simple workable system employed here just can't have everything. You must be content to have the car steer in tight to sweeping circles in a clock or counterclockwise direction only. The opposite turns being reserved for reverse travel. However, by eliminating the slide switch, and connecting the traction motor directly to the 6v. battery supply, the radio will then control only steering allowing the truck to move in all forward directions.

The radio receiver is installed along with battery clips inside the truck's van body with radio control receiver mounted on spacers as described for the remote controlled model boat. Drill two #18 holes in the van body and chassis (Fig. 21) for 6-32 x $1\frac{1}{2}$ -in. machine screws. Position the body over the chassis lugs and fasten in place with the 6-32 screws.

Two 6-32 General Cement Co. "spade screws" are attached to each side of the cab. Position the cab over the chassis so tabs engage the slots, draw up the nuts on the spade screws and the steering motor is concealed but readily accessible for service. If the tires rub against the fender skirts, file or snip away the slight amount of metal at points where tire strikes fender.

The steering-switching designs described in the article can also be used on a model car of your own choosing. Lighter cars will require less power at the steering motor. The right voltage is best determined by experiment. For example, if steering is too rapid at the $4\frac{1}{2}$ v. tap, move the lead down to 3v. Or if action is too slow, advance tap lead to full 6v. as used for the traction motor.

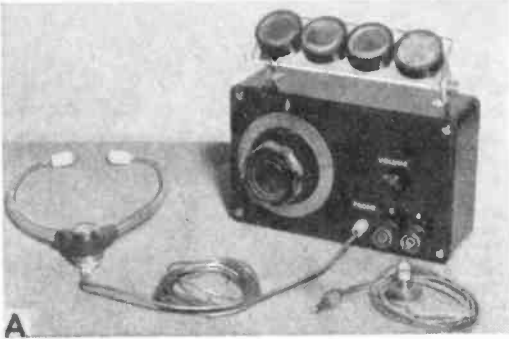This solar powered radio, using four silicon cells, produces about as good a volume as a similar circuit powered by 10 selenium cells. Inset A shows radio with two of the different types of magnetic, 2000 ohm earphones you can use with it. Or you can power radio with a mercury cell and convert it to loud-speaker operation.



Silicon Solar Cells Power Transistorized Radio



Silicon solar cells are now available at a price many experimenters can afford. And here's a first-class project using them


THE solar-powered 108.03 megacycle transmitter in our orbiting Vanguard satellite is expected to operate long after a companion transmitter, powered by mercury cells, has quit.

That's the nice thing about tapping the sun's power—not only will your equipment operate cheaply for a long time but you also minimize maintenance and replacement problems.




The solar battery cells used in the Vanguard's 108.03 megacycle transmitter are silicon cells, and this transistorized radio (Fig. 4) uses four silicon cells. As you probably know, these silicon cells are much more efficient than selenium cells. Silicon cells keep their voltage up under load and generally provide greater electrical energy from a given number of cells, so that fewer cells are required to perform a given task. Up until recently, however, the cost of the more efficient silicon cells was so high relatively few experimenters could afford to use them to power small radios or motors. Now they can.

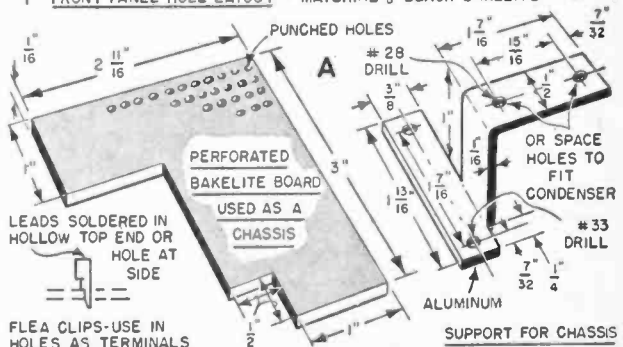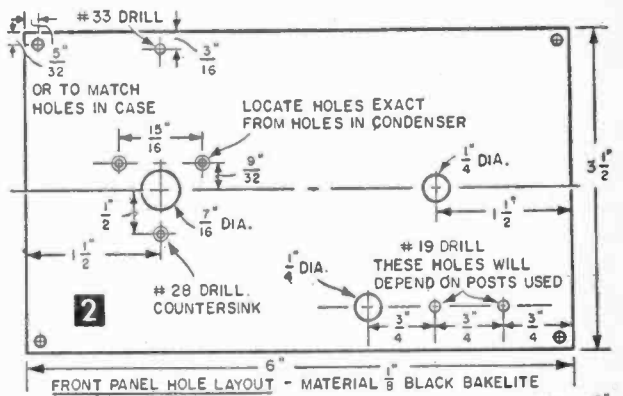For this sun-power radio project, four silicon cells are utilized, connected in series to obtain the maximum voltage. Since the current requirement for tran-



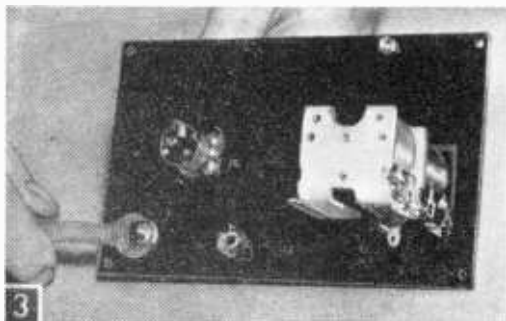

Parts attached to front Bakelite panel.

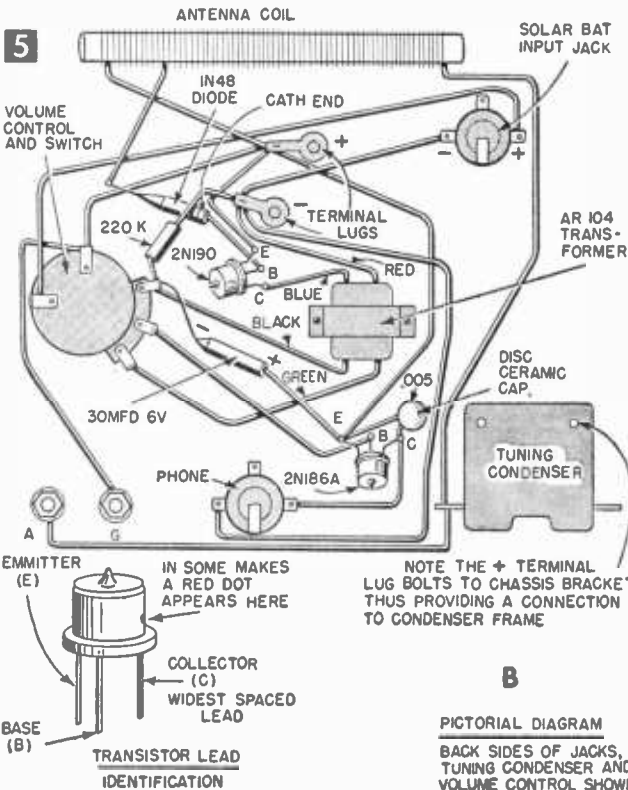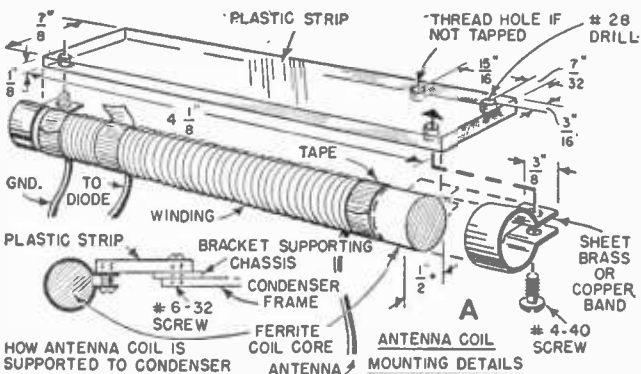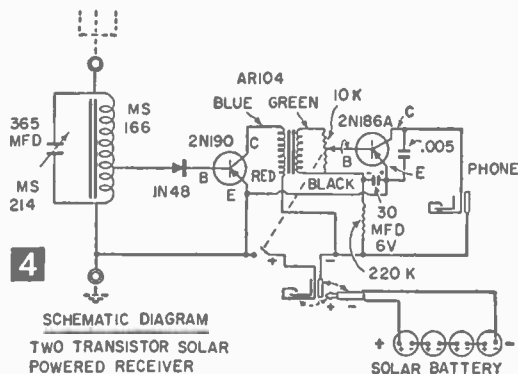

sistors is small, the current delivered from such a series circuit will be more than enough. Bright sunlight will produce 50 milliamperes or more current, and 1.5 or slightly more volts.

Using sunlight, we obtained good reception from four local (Boston area) stations, with satisfactory selectivity. Playing a 100-150 watt lamp bulb on the solar cells will also operate this radio, though with reduced volume, of course.


The radio (Figs. 5 and 6) uses two transistors, which is about the maximum number that can be powered with 1.5 volts and still get acceptable earphone volume. The circuit is of the common emitter type and if you do not want to use solar cells, you can use a dry cell (1.5 to 3 volts) and have yourself a useful little earphone radio. For earphones you can use a regular headset of 2,000 ohms or higher rating or single ear or binaural magnetic type of same rating.

You can also use a 4-volt mercury battery and get strong local stations to come in with sufficient volume to operate a loudspeaker. To do this, use an output transformer, plugged into the phone jack with short leads and a speaker with 3-4 ohms voice coil. You can mount the transformer to the speaker frame and house it in a small baffle or enclosure with the speaker. Use a miniature type output transformer which matches the impedances of the output transistor and the voice coil.

A short antenna or perhaps 15 to 25 ft. of wire from the antenna post, with a ground to a radiator or water pipe, gives the best results. But just connecting the antenna post to the finger stop on a dial phone provides excellent reception. You can also connect a clip lead from the antenna post, with no ground, to the wire

MATERIALS LIST—SILICON CELL SOLAR RADIO

- | | |
|------|--|
| No. | Description |
| 1 | Bakelite meter case, 6 1/2 x 3 3/4 x 2" (MS-216) |
| 1 | miniature single-gang 365 mmfd. tuning condenser (MS-214) |
| 1 | volume control with switch, miniature type, 10,000 ohms (VC-28) |
| 1 | miniature knob for 1/8" shaft (MS-185) |
| 2 | subminiature jacks (MS-282) |
| 2 | subminiature plugs (MS-281) |
| 2 | binding posts for bared wires or banana plugs, Black, Smith PJ21 |
| 1 | antenna coil with 1/2" ferrite core (MS-166) |
| 1 | transformer for transistor circuits (AR-104) |
| 1 | electrolytic capacitor 30 mfd. 6 volt, miniature type (CF-104) |
| 1 | G.E. diode 1N48. Can use other types such as 1N34 |
| 1 | G.E. 2N190 transistor (or try 2N107, CK721, CK722) |
| 1 | G.E. transistor 2N186A |
| 1 | package of flea clips (MS-263) |
| 2 | small solder lugs for #6 screw |
| 1 pc | perforated Bakelite board (MS-304) |
| 1 | 1/2 watt resistor, 220,000 ohm |
| 1 | ceramic capacitor, .005 disc type |
- The above material can be purchased from Lafayette Radio, 165-08 Liberty Avenue, Jamaica 33, N. Y.
- 1 tuning knob with dial 180 degrees 0-100. ICA 2 3/4" dia. Type 2171. Could also use at lower cost a pointer knob 1 1/4" #55H 074 and a Croname dial plate Type 569 0-100 #55H 140.
- 4 International Rectifier silicon cells Type SA5-M. Could also use lower cost Type SA5-PL (unmounted) and cement (Pliobond) them to plastic mounting strip and make lead connections. The above materials can be purchased from Allied Radio, 100 N. Western Avenue, Chicago 80, Ill.
- Miscellaneous
- 1 pc clear plastic or Bakelite 1/8 x 4 1/8 x 7/8" (antenna coil mounting strip)
- 1 pc aluminum about 1/16 thick x 2 x 3" (chassis support bracket)
- 1 pc black Bakelite 1/8 x 6 x 3 1/2" (front panel)
- 1 pc soft brass or copper about .025 x 3/8 x 4" (antenna coil clamps)
- 1 pc clear plastic or Bakelite 1/8 x 1 1/2 x 5" (solar cell strip)
- 1 pc aluminum about 1/16 thick x 7/16 x 4" (solar battery brackets)
- Miscellaneous screws, nuts, hook-up wire, solder, etc.

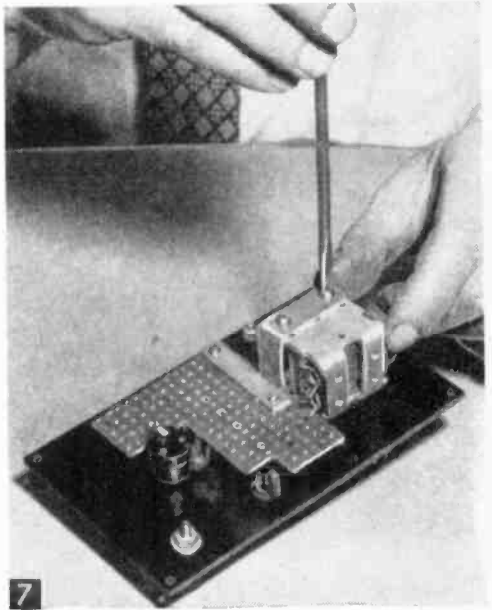


7 Attaching bracket to condenser. Note perforated sheet in foreground, to which bracket has already been attached.


frame of a lampshade, or with about three or four turns of insulated wire around several metal slats of a venetian blind; the radio signals will be picked up inductively from the blind slats. Connecting the antenna post of the radio to a ground sometimes works quite well in picking up signals.

Start construction by drilling holes (Fig. 2) and fitting the components to the front panel (Figs. 3 and 6) which has been cut from 1/8-in.


black Bakelite to neatly fit in the recess of the meter case. Attach the tuning condenser with short 6-32 flathead screws, making sure these screws are not so long that they project through the condenser frame and strike the movable plates.

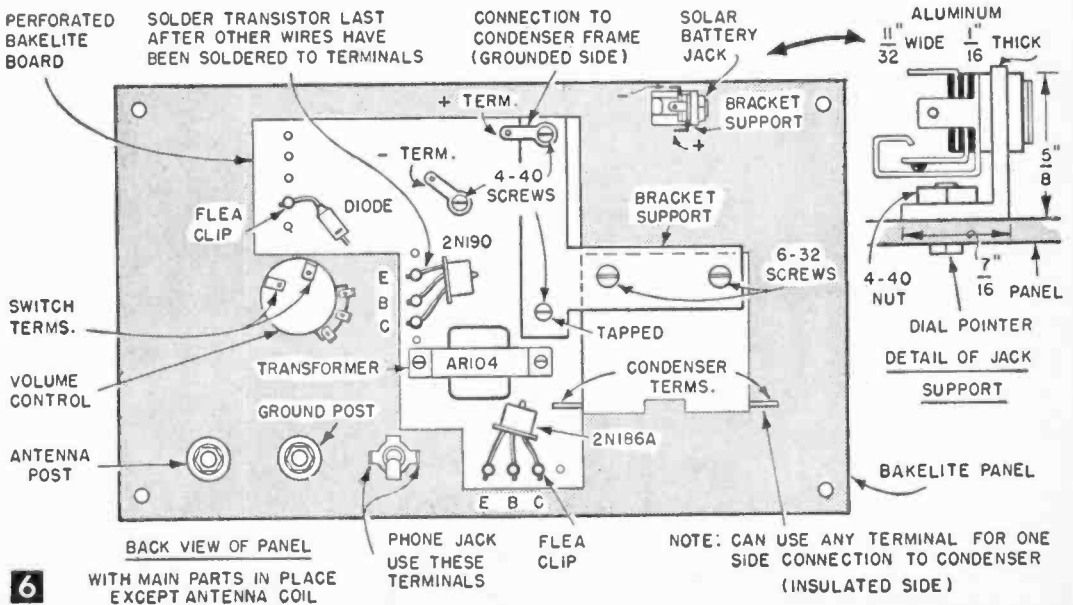Note in Fig. 2A the bracket which is bent up from 1/16-in. or 3/32-in. aluminum; this bracket supports a piece of perforated Bakelite (Fig. 2A) which serves as a "chassis," to the frame of the



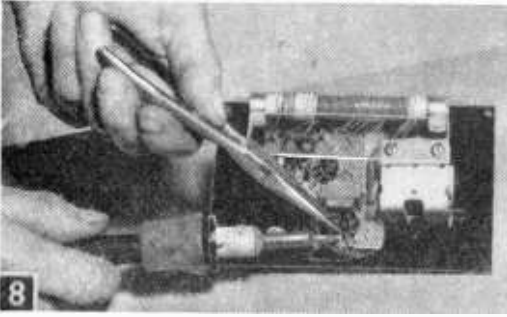

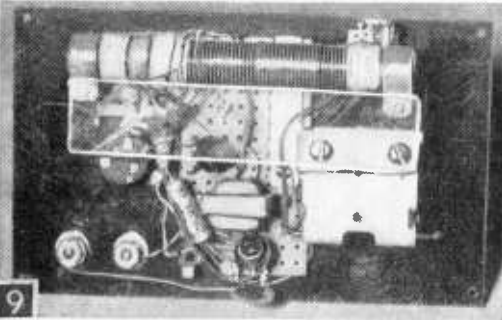Note mounting of antenna coil at top. At bottom, how to hold transistor leads with long-nose pliers to conduct heat away from transistors when soldering.




Note ground binding post added at lower left and solar battery jack added just above antenna coil (also see Fig. 6).

condenser. Attach the bracket to the perforated Bakelite with two screws in tapped holes. The other end of the bracket has drilled holes that match up with holes in the condenser (Fig. 7). You can tap the condenser holes for machine screws if they do not come already tapped. Make sure that all screws turning into a condenser frame do not protrude through enough to touch the rotating section.

The antenna coil (Fig. 5) has a large (about 1/2-in.) diameter ferrite rod, over which the coil comes wound. Of three leads provided, the center one, near one end, is the *tap* and the other two are the *start* and *finish*. To mount the coil, bend up two clamps from thin sheet brass which go around the ends of the core tightly when the ends of the clamp come together (Fig. 5A). Cut a strip of 1/8-in. thick plastic for a base and attach the coil with the clamps to this piece using 4-40 screws and nuts. The coil should come along one edge of the strip as in Fig. 5. Next, secure strip, together with chassis bracket, to the condenser frame with the same screws (Fig. 9). Although this simple method of supporting the perforated Bakelite is rigid enough for use, when applying pressure as you would when you press in the flea clips, place a thin piece of wood under it as a support.

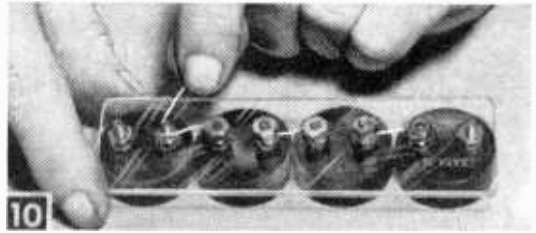Mount the inter-stage transformer to the Bakelite perforated with two 4-40 screws in tapped holes. Then press the tiny flea clips in the holes at the points indicated in Fig. 6 as wire terminals.



Four silicon cells are mounted to a strip of plastic and connected in series (plus to minus) with bare tinned copper wire.

Also at the two other points shown, flea clips are used for the connection of the transistor leads. Connect a solder terminal under one of the screws in the condenser bracket as a common plus terminal for a group of wires and attach a second solder terminal to the perforated board with a 4-40 screw for the common minus terminal.

Connect the switch on the end of the volume control in series with the plus side going to the solar battery jack. Use #28 plastic insulated Alpha sub-miniature wire (obtainable in electronic parts stores in a small 30 foot spool) and solder all terminals with rosen-core solder. Cut off the transistor leads to about 1/2-in. length for convenient connections, and then use long-nosed pliers (Fig. 8) when soldering the connecting wires to the terminals to help conduct damaging heat away from the transistor. Be sure you identify the collector lead at the transistor; this is the one widest spaced from the others (Fig. 5B). Also examine the jacks carefully to locate the two out of the three provided which you will actually use.


While doing the wiring, remove one screw in the antenna strip and swing the strip away a bit to allow better access to the parts underneath. Note in Fig. 4 that a wire runs from the negative common terminal to the jack where the solar battery connects. A second wire runs from one side of the switch to the jack and a wire connects the other side of the switch to the positive common terminal. Take care to get this polarity correct all the way through to the solar battery.

The jack connecting the solar battery is supported in a small aluminum angle bracket attached under the nut holding the pointer at the top of the tuning dial (Figs. 6 and 9).

Because the drilled and tapped holes provided at the corners of the Bakelite meter case are rather large for good appearance in attaching the panel, I drilled them deeper with a 43 drill and tapped for 4-40 screws.


Testing the Circuit. With a 1 1/2 volt penlight cell plugged into the solar battery jack (take care to get the correct polarity), connect a short antenna to the antenna post and a ground wire to the post which has been added (Fig. 9). Plug in the earphone. You should be able to pick up some stations by rotating the tuning dial and adjusting the volume.

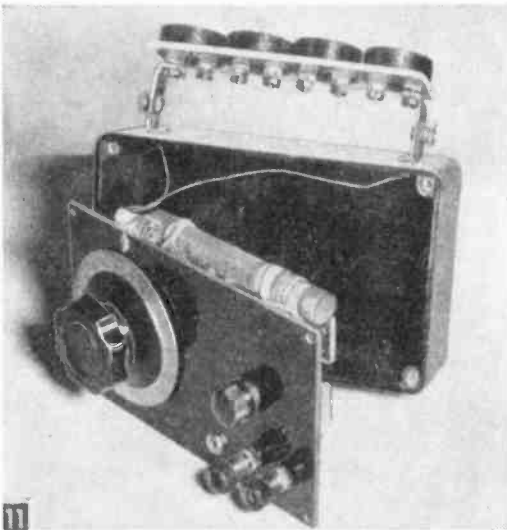Assembling the Solar Battery. Arrange the four silicon solar cells along a strip of 1/8-in. plas-



Solar battery mounted to case with brackets shown in detail A. Short wires connect from bracket attaching nuts to plug which fits into miniature jack shown in Fig. 6. Brackets carry current from solar cells down to circuit.

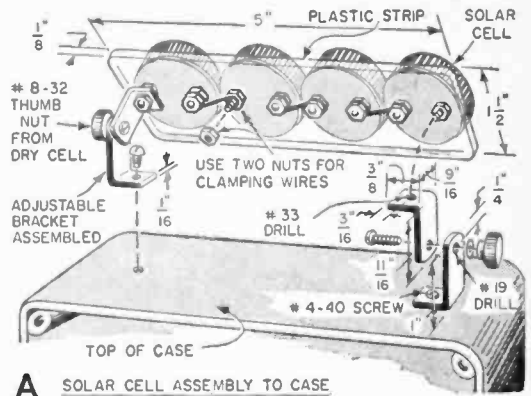
tic, drilling holes as required to clear the mounting studs (Fig. 10). Connect the plus and minus posts as in Fig. 4 to form a series group, using bare, tinned #24 copper wire. There will be a plus and a minus post left over; attach to the bracket pieces shown in Fig. 11. Then attach the



A SOLAR CELL ASSEMBLY TO CASE

shorter pieces of the brackets to the top of the case with 4-40 screws. Use 8-32 screws and thumb nuts (from an old dry cell) at the brackets for adjusting them. Make sure the plus (positive) side of the battery is connected through the proper jack terminal to the plus side of the circuit or to one of the switch terminals and the minus (negative) side goes to the common negative terminal strip. Once properly connected, the plug will go in the jack and make these connections correctly at all times.

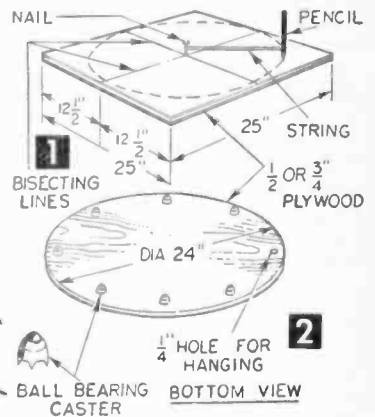Finally, add some neat lettering to the panel (Fig. 1A) using decals sold by electronic supply houses. Coat lettering with thin lacquer or transparent plastic for protection.—HAROLD P. STRAND.



Workbench Chassis Turntable

YOU can save time when working on radio-TV or electrical appliances by building a turntable that will rotate to keep the work always within easy reach without having to lift and move it. To make such a turntable, take a piece of 1/2 in. or 3/4 in. plywood about 25 in. square and locate the exact center by scribing two bi-

secting lines in from the edges. With center located, drive a small nail partly in where the lines cross (see Fig. 1), and attach a string to a pencil, tying the opposite end to the nail. Then, holding the string tight, scribe a circle.

Jigsaw out the disk and drive eight ballbearing casters into the bottom of the disk about 2 in. in from the edge, spaced approximately equidistant from each other (see Fig. 2). Drill a 1/4 in. hole near one edge of the turntable so that it can be hung on a nail driven in the shop wall when not in use.—J. A. C.

IN THEIR search for the ultimate in sound reproduction—a laboratory reference standard reproducer—the Jensen engineering staff designed this speaker cabinet (Fig. 1) to house their own KT-31 Imperial 3-way, speaker system kit. Although the KT-31 kit and the speaker cabinet are a perfect match for true high fidelity that will delight the most exacting audiophile, design of the cabinet is such that any good quality 15-inch co-axial speaker may be installed.

It is well to point out right now, so you'll know before beginning construction, that the cabinet should be inverted if a G-610 Tri-axial or a 15-inch co-axial speaker is to be installed. This places the systems closer to ear level. In this case it is recommended that part No. 2 which is now the top of the cabinet, be doubled in thickness to add strength when it is used as a base. This addition will not change the dimensions of other parts except those three trim pieces which border the front and side edges.

Construction is not difficult although it is not as easy to build as a simple bass-reflex. To simplify things we've eliminated confusing dimensions from the drawings and numbered the parts so that you can cut them exactly as called for in the materials list. With a few exceptions, where trimming to fit will mean tighter joints and therefore better appear-

ance, the dimensions called for are exact.

Use $\frac{3}{4}$ in. thick fir plywood throughout except where solid material is called for. Remember that the prime requisite of any speaker enclosure is rigidity, so all joints must be tight and firm. Use screws where called for but be sure to drill shank and lead holes. Joints should also be airtight so don't spare the glue and don't wipe off excess as you normally would except where such "squeezeings out" would show on the outside of the cabinet. Use a non-drying caulking compound on the inside of the structure to further seal the joints. It's best to do this as you go along before some joints become inaccessible due to added parts.

Coat all inside parts with shellac to prevent moisture absorption which could lead to warping and splitting of the wood. No absorption material (specified in some plans) is necessary or desirable in a horn-type enclosure such as this.

Cabinet Construction. Start by laying out



1 Speaker cabinet is of the free-standing type. It can be used in a corner or against a wall.

Hi-Fi Speaker Cabinet

Engineered to Please the Ear

By R. J. DeCRISTOFORO



2 Balance controls on side of cabinet permits adjustment of speaker to room in which it is placed.

and cutting the bottom and top pieces (#1 and #2, Fig. 4) to size and shape. Then cut the front panel (#3) to size and lay out the 13 1/4 in. dia. speaker opening in the center of the panel 11 3/4 in. up from the bottom edge.

Since the panel is too large to saw the circular opening for the speaker on a jigsaw, use a compass saw, or portable jigsaw. File the edges evenly and sand smoothly.


Your next step is to make the two posts (#4) from solid material such as a clear piece of 2 x 4 in. stock. Cut grooves in each post on two adjacent sides 1/4 in. deep x 3/4 in. wide at a point 8 in. down from the top end (A in Fig. 3). The grooves could be cut by hand with saw and chisel but a dado assembly on a table saw will assure uniformity of cuts and go faster. Be sure the 8 in. dimension is exact, because the top of the groove must line up with the top edge of the front panel.

Attach the posts to the back of the front panel with glue and #8 x 1 1/2 in. fh screws spaced 5 in. apart. Set each post in 3/4 in. from the sides of the panel and 3/4 in. up from the bottom edge, so that the sides and bottom of the speaker will be flush with the edges of the front panel.

Add the bottom (#1) to the front panel (#3) next, bracing it temporarily so it will be at right angles to the front. Fasten with glue and 8d finishing nails spaced 4 in. apart. Also drive one nail up through the bottom into each post. The base, made up of parts #21 and #22 is optional and may be added at this time if desired. After cutting the compartment top (#5 in Fig. 3), make a 1 1/4 in. square notch at each front corner (A in Fig. 3), so the board will fit in the grooves cut in the posts, and bevel the rear edge 20°. Apply glue to the grooves in both posts and along the front edge of compartment top and put it in position. Use 8d nails to draw it up tight.

At this point apply caulking compound to the inside corners of the cabinet along each post, in the corner made by the base and front and in the corner formed by the front and compartment top. Follow this procedure as you go along to be sure of air tight construction.

Cut the center shelf (#6), and notch the two front corners as you did for #5. Like #5, the rear edge is also beveled 20°. A cleat (#8, Fig. 4) is cut to size and attached to the front edge of the center shelf with glue and #8 x 1 1/2 fh screws. Then drive screws through the cleat into the front panel (Fig. 5) to hold the center shelf in position. The distance between #5 and the center shelf (#6) should be 20 3/4 in. Use temporary braces to keep the center shelf square to the front. Cut the upper compartment back and bevel both top

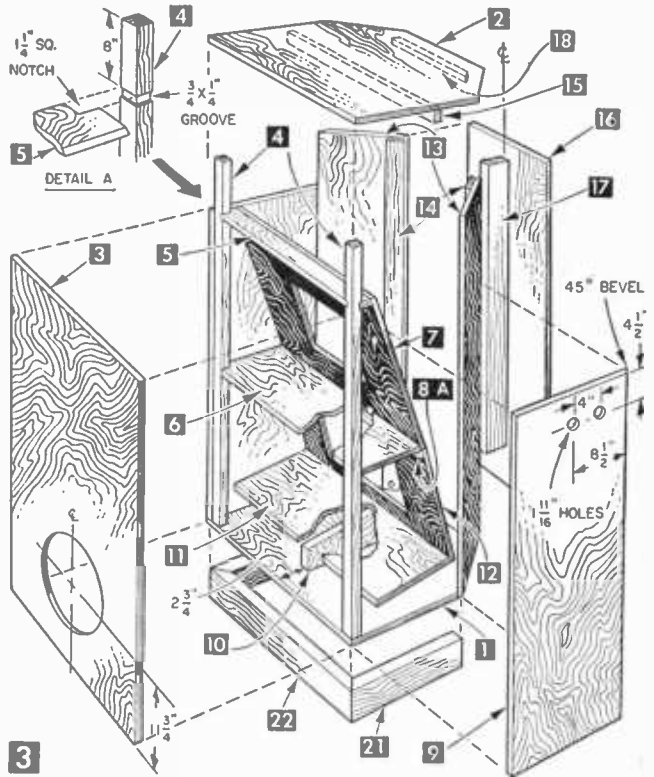

and bottom edges so it will mate exactly with the bevel cuts on the parts it will attach to. Before adding this to the assembly, cut a 12 in. square opening exactly in its center. Then fasten #7 to the cabinet with glue and 6d finishing nails.

Start assembling the lower speaker compartment by cutting #10 to size. This is 12 7/16 in. long, 4 in. wide at one end and tapers to 2 3/4 in. wide at the other. Attach to the bottom as in Figs. 3 and 4, centered and 2 3/4 in. in from the front panel. Use glue and four #6 x 1 1/2 in. fh screws, driven up through the bottom. Part #10 supports the bottom shelf (#11) at the proper angle. Cut a 6° bevel along the back edge of #11 and attach it to the support using glue and three #6 x 1 1/2 in. fh screws. Cut the cleat #8A with a 12° bevel along one edge and attach along the rear bottom edge of the center shelf as in Fig. 4.

To add rigidity to the structure at this stage of the assembly, it's best to add the left side. Bevel the back edges of each side (#9) 45° so they will be flush with #13, Fig. 4, which will be added later.

To add the side (#9), lay the cabinet on its side and coat all contacting edges with glue. Then put the side in place and secure with 8d finishing nails spaced 4 in. apart (Fig. 7).

Make the lower compartment back #12 next and cut a 12 x 17 in. access opening in its center. Glue and nail to the back edge of the bottom shelf and to the cleat on the underside of the center shelf.

Now lay the cabinet on the installed side and

MATERIALS LIST—HI-FI SPEAKER CABINET

All dimensions in inches

No.	Part	No. Req.	Size	Material
1	bottom	1	3/4 x 22 1/2 x 31	fir plywood
2	top	1	3/4 x 24 x 32 1/2	fir plywood
3	front	1	3/4 x 32 1/2 x 41 1/4	fir plywood
4	post	2	1 1/2 x 1 1/2 x 48 1/2	straight grain fir
5	compartment top	1	3/4 x 43 1/4 x 31	fir plywood
6	center shelf	1	3/4 x 11 3/4 x 31	fir plywood
7	compartment back	1	3/4 x 23 1/8 x 31	fir plywood
8	cleat	1	1 x 1 x 28	straight grain fir
8A	cleat	1	1 x 1 x 31	straight grain fir
9	side	2	3/4 x 16 3/4 x 41 1/4	fir plywood
10	support	1	3/4 x 4 x 12 3/16	fir plywood
11	lower shelf	1	3/4 x 12 3/16 x 31	fir plywood
12	lower compartment back	1	3/4 x 15 1/2 x 31	fir plywood
13	corner side panels	2	3/4 x 11 3/4 x 49 1/4	fir plywood
14	cleats	2	1 x 3 x 48 1/2	straight grain fir
15	stiffener	1	1 1/2 x 2 1/2 x 29	straight grain fir
16	back	1	3/4 x 17 1/2 x 49 1/4	fir plywood
17	stiffener	1	1 1/2 x 2 1/2 x 40	straight grain fir
18	cleat	1	1 x 1 x 19	straight grain fir
19	upper compartment door	1	3/4 x 14 x 14	fir plywood
20	lower compartment door	1	3/4 x 14 x 19	fir plywood




upper and lower compartment doors are not shown on construction drawings

21	base side	2	2 x 4 x 16 3/4	straight grain fir
22	base front	1	2 x 4 x 31	straight grain fir

parts #21 and #22 are optional and required only if base is desired

23	filler	2	3/4 x 2 1/4 x 8	fir plywood
24	filler	2	3/4 x 1 1/2 x 8	fir plywood
25	filler	2	3/4 x 1 x 8	fir plywood
26	front trim	2	3/4 x 2 1/4 x 50	clear pine
27	front trim	2	3/4 x 2 1/4 x 33	clear pine
28	front trim	1	3/4 x 3/4 x 33	clear pine
29	side trim	4	1/4 x 3/4 x 9 1/2	clear pine
30	side trim	4	1/4 x 3/4 x 17	clear pine

- 2 #10 x 2" fh screws
- 63 #8 x 1 1/2" fh screws
- 24 #8 x 1 1/2" rh screws
- 3 #6 x 1 1/2" fh screws
- 2 yds grille cloth (36" wide)
- 1 pt polyvinyl resin glue (white glue)
- small tube caulking compound (M-D is good brand and available in most hardware stores)
- 1 lb. 8d finishing nails (2 1/2")
- 1 lb. 6d finishing nails (2")
- small box 3/8" x 18 brads
- 1/4" tacks or staples for grille cloth

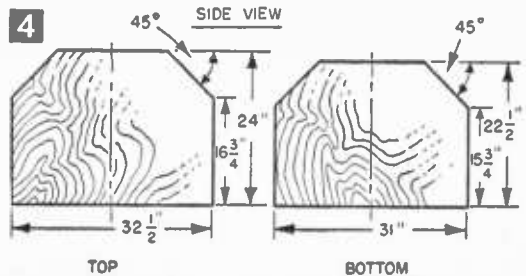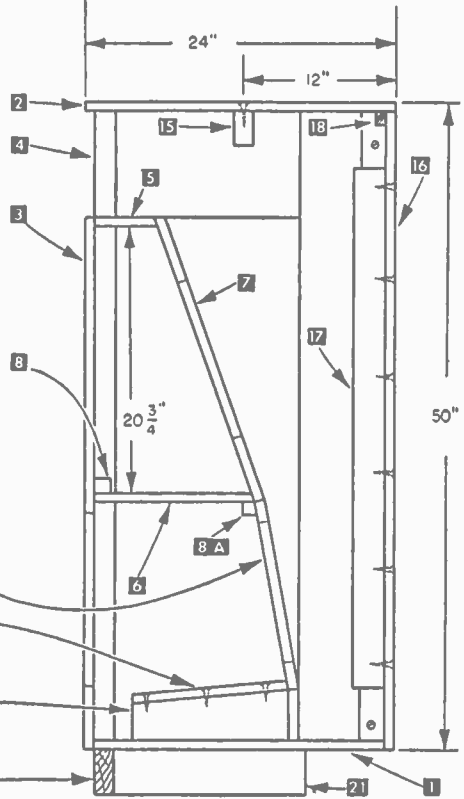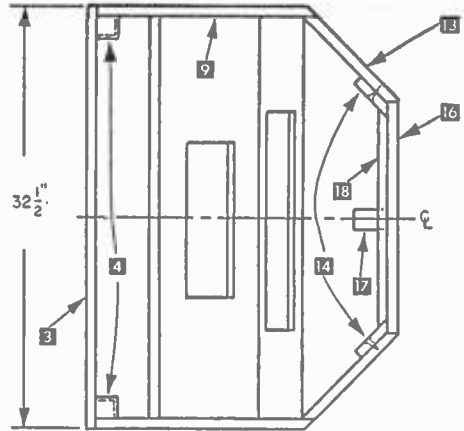

add the second side following the same procedure outlined for the first. If speaker used has H-F and M-F balance controls (Fig. 2), bore the two holes shown in Fig. 3 for H-F and M-F balance controls. Make parts #19 and #20, which cover the access opening in both upper and lower compartments and temporarily attach with #8 x 1 1/4 in. long screws spaced 4 in. apart (Fig. 6).

Both corner side panels (#13) can be added now. Bevel each one along both vertical edges 45° (Fig. 4), and attach with glue and 8d nails driven through into the base and edge of the sides. Make cleats #14 and #18 and attach parts #14 to the side panels as in Fig. 4 using glue and #8 x 1 1/4 in. fh screws. These cleats form a rabbit into which the back of the cabinet can be recessed.

Before adding the top (#2) attach the stiffening member (#15 in Fig. 3) using five #8 x 1 1/2 in. fh screws. Then attach the top by using plenty of glue on all mating surfaces and driving in 8d finishing nails spaced 3 to 4 in. apart. Use one #10 x 2 in. fh screw through the top down into each post. Add cleat #18 and the cabinet is ready for the back (#16). After cutting the back to

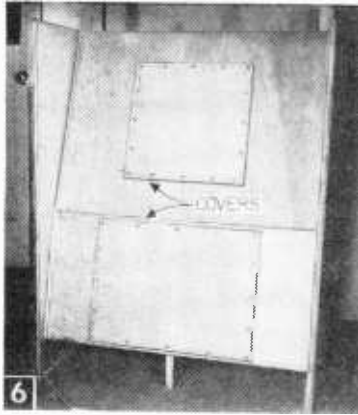
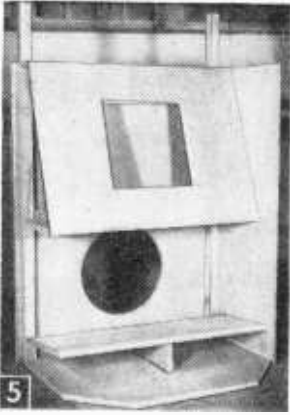


Fig. 5. Rear view of cabinet showing left side in place. Fig. 6. Access openings in upper and lower compartments are covered with pieces of $\frac{3}{4}$ in. plywood. Fig. 7. Rear view of cabinet with back removed to show stiffener fastened to center of back.

size, stiffen it by fastening part #17 to the center of the back (Fig. 3) with glue and six #8 x 1½ in. *fh* screws. Attach the back, which must be removable, with 24 #8 x 1½ in. *rh* screws and washers.

At this point, basic construction is complete and all permanent nail and screw heads should be sunk below the surface of the wood and puttied over. Examine exposed plywood edges carefully and if any holes show, fill with putty. You can sand now to make the surfaces smooth, but contrary to usual procedure (if you desire the an-


tique white finish shown on the original), you don't have to be extremely careful with sanding because some slight imperfections will actually add to the appearance of the finish.


Before attaching the grille cloth to the front panel, add the filler blocks (parts #23, #24, and #25—B in Fig. 8), to bring these recessed areas flush with the surfaces of the cabinet. Attach blocks with glue and 6d finishing nails. Staple the grille cloth so that about 1 in. of bare wood shows around all edges. (Fig. 10) so the molding can be attached. The grille cloth, on the front, runs from top to bottom of the cabinet. Cut smaller pieces to cover the openings on the sides.

Figure 8 shows how the molding is applied. These can be decorative moldings that you can purchase from your lumber dealer or you can make your own with a molding head or shaper. Another method, and one which we used, is to attach blank strips to the cabinet and add the shapes with a portable router. In any case, attach the molding strips on the front with glue and 6d finishing nails, and the strips on the sides with small brads. Sink all nails under the surface of the wood and fill the holes with wood putty.

Finishing. If you prefer the antique finish shown apply a clear resin sealer to all wood surfaces and let dry. Then brush on a full application of flat-finish, white undercoat. After the undercoat dries, make an antique glaze by mixing equal parts of turpentine and glazing liquid and tinting it to the tone desired. Umbers (colors in oil) may be used to tint or you can use a stain. We found that walnut stain gave a good tone. Wipe the glaze on with a cloth, being sure that it piles up in the corners. How you apply the glaze has much to do with the final appearance.

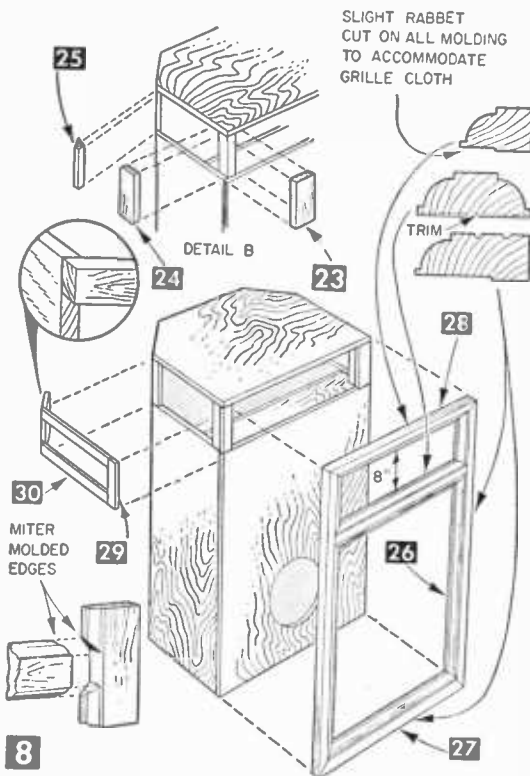It's best to practice on scrap wood both to establish the best wiping stroke and the most appealing tint. Some leeway is possible by letting the glaze set awhile and then wiping again with a cloth that has been dampened with turpentine. Let the glaze dry thoroughly, then finish with two coats of satin-finish varnish, then wax.



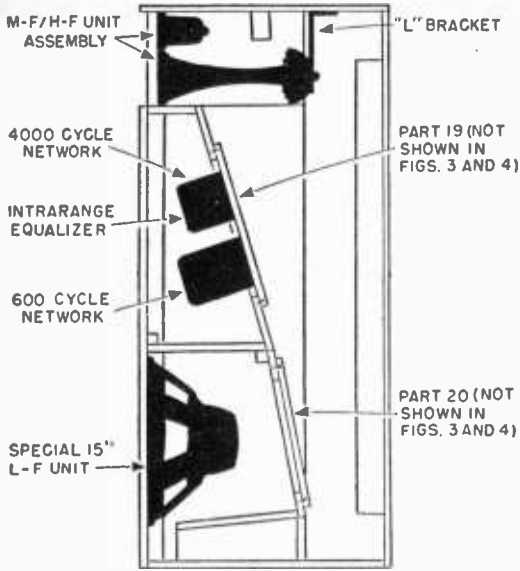


9 INSTALLATION OF JENSEN KT-31 IMPERIAL 3-WAY SPEAKER-SYSTEM KIT

Installing Units. Any speaker you buy will contain specific instructions relating to installation of that particular unit. You'll find the back opening and access openings in the cabinet are ample for installation of any 15 in. speaker. When divided systems such as the Jensen KT-31 Imperial (Fig. 9) are installed, the woofer is placed in the lower compartment, the cross-over networks in the upper compartment and the tweeters behind the opening at the top of the cabinet.

Balance controls (Fig. 2), are set in the holes provided for them and are adjusted following the instructions provided with the speaker system. In general, follow these instructions. Pencil an outlining circle around the speaker cut-out which will be visible after the speaker is put in position. This will make centering the speaker a simple matter. When tightening the screws that attach the speaker, take up on each an equal amount to prevent distortion of the speaker frame. When drilling holes in the compartment backs for connecting wires (wires that go from cross-over networks to controls, etc.) make them only as large as needed and caulk all these holes with strips of felt after the wires have been passed through. Connect the speaker to your Hi-Fi amplifier and you're ready for the ultimate in sound reproduction.

Marking Your Radio for CD Bands

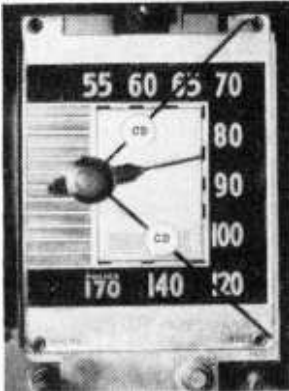● In the event of an enemy attack on the U. S., the only radio broadcasts will be made by Civil Defense on a frequency of 640 or 1240 kc. To mark your radio now for pinpoint emergency tuning, first remove the knobs and chassis-holding screws and slide chassis out of cabinet, being careful not




to ground an ac-dc chassis. Using a signal generator, mark the 640 and 1240 kc spots on the dial with a sharp-pointed pencil. Pull the line plug for safety, and draw the lines across the face of the dial with black India ink, or white ink if dial is black, or you can stretch threads secured at each end with Duco cement across dial. Type the letters "CD" on white paper, cut out and cement on lines.—A. T.

Components Held by Spring

● If you're tired of digging through boxes and drawers of assorted parts looking for the right value of resistance or capacitance, try this method for easy selection. Hang a long spring about

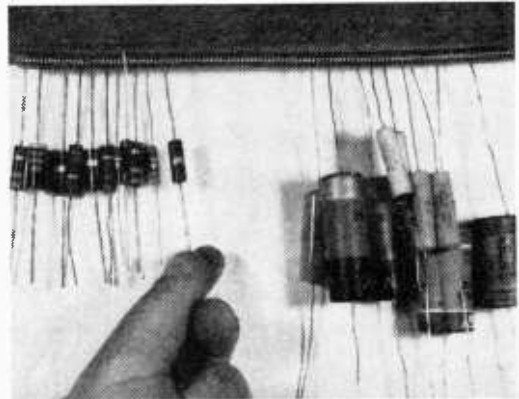the size of a screen-door spring from a handy place on your test bench, or somewhere handy



to your work area, and insert all your resistors and capacitors between the coils.—PHIL MCCAFERTY.

Clay Solves Radio Problems

● Modeling clay is the answer to many radio-TV problems. (1) It can be used to hold a dial string on a pulley when restringing an elaborate dial mechanism; (2) It will hold small parts to be soldered or tested on the bench; (3) It is especially handy for removing metal filings from the magnetic pole pieces of speakers or recording heads.—JOHN A. COMSTOCK.

Testing Those Coils for Shorts

By HAROLD P. STRAND

IN THE winding of coils for motors, generators, transformers and similar equipment, one of the problems is that of avoiding short circuits between turns in the finished coil. The tester shown will detect a short among as few as 4 turns in about 500 total turns in a coil, a feat that is not quite possible to duplicate with a wheatstone bridge, due to slightly varying resistance between normal coils anyhow.

This device works in a similar manner to a transformer. A laminated iron core is made up from transformer E laminations (Fig. 1). The stack, corresponding in width to the particular coils to be tested, is riveted together through drilled holes in the E. The straight pieces are likewise riveted to form a separate bar, which can be laid on top.

A coil is then wound, which forms the primary of the transformer and which is connected to a 115 volt 60 cycle line, through a Variac or variable voltage power transformer. The coil to be tested is placed on the same leg, on top of the primary. This is in effect the secondary of the special transformer. A voltmeter should be used across the leads of the primary and an ammeter and a wattmeter are connected in the circuit, as shown in the diagram, so as to be able to read amperes and watts input to the primary.

The way the tester works is this. A transformer with no load on the secondary draws but very little current and watts, the amount indicated, being the excitation of the core or the iron losses. Now, if the coil on the core leg has no shorted turns, the watts registered on the meter will be the same as when the coil is removed; since the coil leads are open, the secondary is therefore at open circuit or no load. On the other hand, if a coil with some shorted turns is placed on the core, current will flow in the coil through the shorted turns. This will be reflected in higher primary watts and current, as the primary always supplies added current to meet the demands of the secondary. Therefore, by getting increased readings on the meter, we can quickly detect shorted turns in a coil, the value of the increase being in relation to the number of


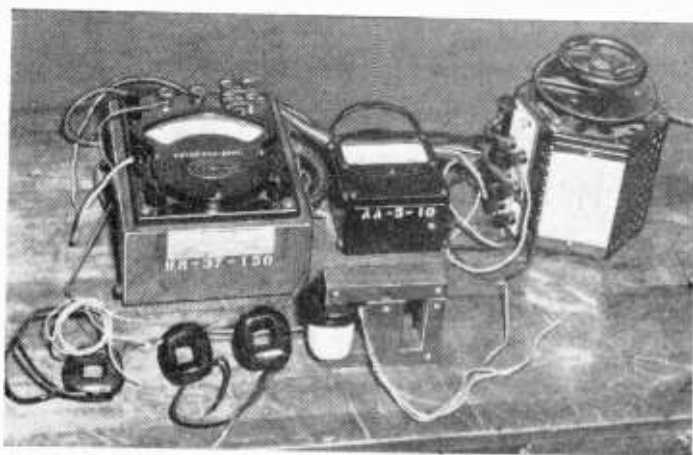


Fig. 1. Using coil tester to test a group of 4 field coils for shorts. One coil in this finished group was found shorted and therefore useless. A considerable saving in time was made by learning of this defect before installing in generator frame.

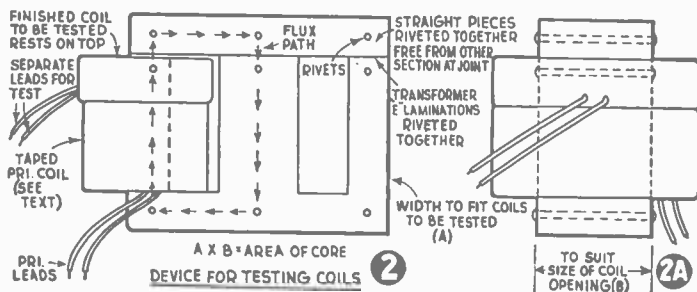


turns and degree of contact at the shorts. To build the tester, select some transformer laminations on which coils to be tested will fit over one of the outside legs, when stacked to a thickness that will fill the coil space. Clamping the E pieces tightly between clamps, drill holes to pass iron rivets (Figs. 1 and 2). Stack straight pieces to the same thickness, then drill and rivet. To figure the right number of turns to use for the primary coil, use the transformer formula:

$$E \times 10^8 \\ 4.44 \times f \times A \times B_M$$

in which E=primary voltage, $10^8=10$ raised to the eighth power, f=frequency of the supply, A=area of the core, B_M =maximum flux density in lines per sq. in., 4.44 a factor=4 times the form factor (1.11).

For this job it is well to make the flux density quite high, so as to get close to saturation. A figure of 100,000 lines was found satisfactory. For example, suppose your core outside leg, which the coil surrounds, measures $\frac{3}{4}$ in. wide and you are going to stack the core $1\frac{1}{2}$ in. Then, $.75 \times 1.5 = 1.125$ or 1.13 is close enough. This is the area. Substituting figures for symbols in the

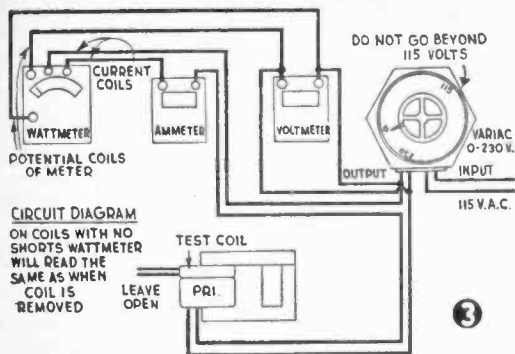

formula, we get:

$$\text{Turns} = \frac{115 \times 100,000,000}{4.44 \times 60 \times 1.13 \times 100,000} = 382.$$

Wind the coil on a suitable wooden form, using

about 20 Formex wire. The wire size is not critical, since with good coils, there will be but little current flowing in the primary and, if a shorted coil is on the leg, the increased current will last only long enough to get a meter reading. Make the form size such as to leave room on the core leg for the coil to be tested.

A wattmeter should be used with a scale of about 0-75 or 100 watts, in order to be able to read the exciting current easily. Close the switch supplying the 115 volts ac to the Variac, having the dial of the latter at 0. Then gradually bring up the voltage to 115 volts, watching the wattmeter carefully. A sudden jump in current to a high value, indicating a shorted coil, calls for quickly bringing the Variac dial back to 0, to protect the meter. In this manner, coils can be quickly tested. Those showing no increase over the primary watts, from the value when no coil is on the leg, can be passed as good.

"Wireless" Pickup Amplifies Phone Talks

A standard earphone, with cap and metal diaphragm removed, is taped over telephone receiver. Voice comes over the loudspeaker.



A radio earphone makes a simple inductor pickup to send a phone call through your radio speaker

Amplifying a telephone conversation so that the caller's voice can be heard by any number of people is simple. There are several methods of obtaining "wireless" connection to any phone. The two methods described in this article are inductive pick-up systems.

The easiest method requires only a radio receiver provided with a phonograph pickup jack. Many sets have such a connection on the back of the chassis. Otherwise, such a jack may be provided. Plans and instructions for installing such a pickup jack are given in detail in the article, "A Phone Jack for Radio or TV," found on pages 150-151 of this volume.

The telephone pickup consists of a single radio earphone with a resistance of 1000 ohms or more. While even an ancient earphone may be used, much better results will be obtained from one of the newer receivers having an Alnico magnet. Many war surplus headsets are of the Alnico type. Unscrew the plastic earphone cap, lift off the metal diaphragm and disconnect the cord (if earphone is obtained from a double headset). Now connect a new pair of wires, using rubber-covered fixture wire, to the earphone lugs and connect a radio-phonograph plug to the opposite end of the fixture wires.

Leave earphone cap and diaphragm just as they are and attach the open unit over the telephone's receiver with Scotch tape or heavy elastic band. To obtain proper polarity between telephone receiver and earphone pickup, turn or rotate earphone slowly until loudest dial tone comes in. A drop of red nail polish on phone receiver and earphone edge will identify the proper position


for future use.

In some instances, the pickup is more sensitive when phone receiver cap is unscrewed and earphone placed against phone receiver's diaphragm. However, very modern phones have a cartridge type receiver which disconnects when cap is removed. For all practical purposes—unless you know exactly what you are doing—do not remove the receiver cap on telephones as the pickup will work in most cases as first described.

Another pickup which connects to the amplifier or phono-pickup jack in the same manner as the earphone pickup, is a homemade induction coil consisting of several hundred turns of No. 40 gage enameled magnet wire.


Form a cylinder 3 in. in diameter from light cardboard, holding it in shape with Scotch tape. The tube should be long enough to handle since it is removed after coil has been wound. Wind 400 or more turns of magnet wire onto the tube, keeping the turns within a 3/4 in. space. Scramble-winding is adequate for our purpose. When finished, secure coil around its circumference with adhesive tape.

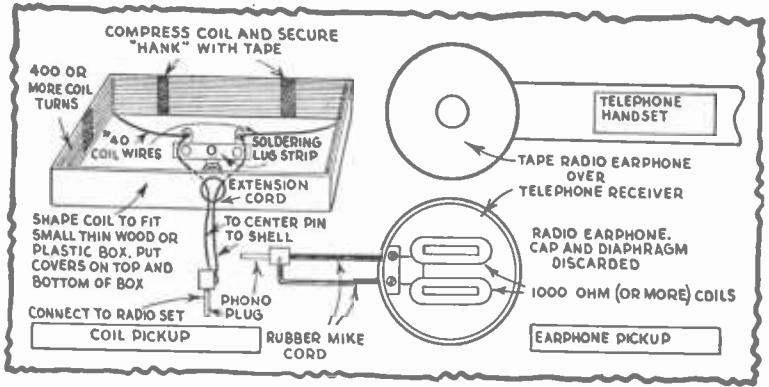The completed coil is too delicate to withstand rough handling and should be placed inside a



shallow plastic or wooden box. A two terminal soldering lug fastened inside box permits fine magnet wires to be joined to fixture cord extension connecting to jack on radio or amplifier. Be sure enamel insulation is removed from ends of magnet wire before soldering to lug strip or an open circuit will result. Wireless pickup is obtained by laying telephone receiver on coil box, or by placing box under phone base, depending on type of telephone.

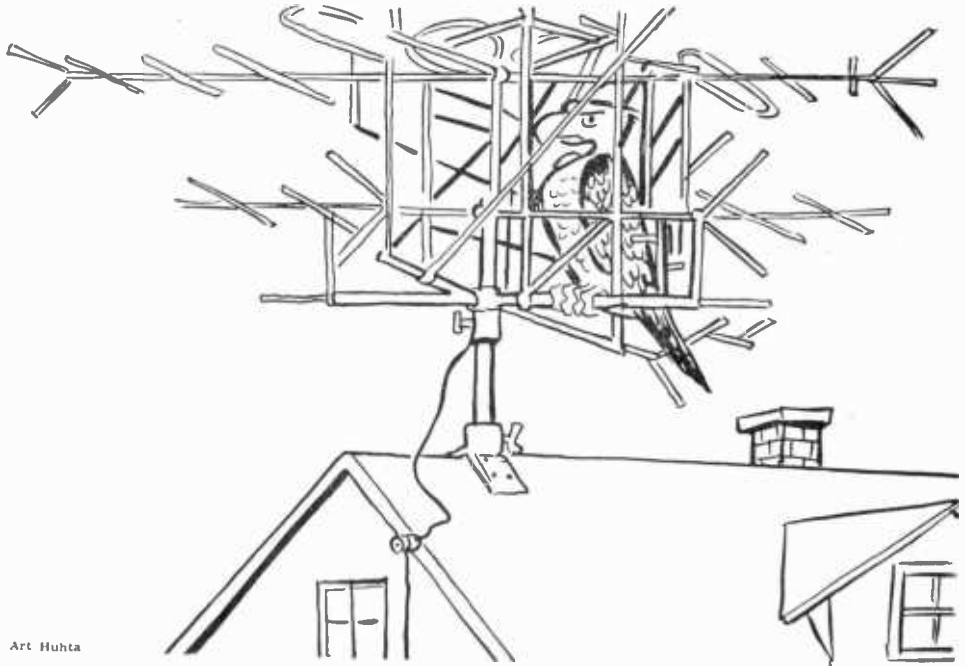Of the two pickup methods described, induction coil method is best for all around purposes. There are some instances where the simple earphone method may not work to complete satisfaction. For a very sensitive induction pickup, use the secondary winding from an old Model-T Ford spark coil. This eliminates the necessity of winding your own coil.



Record player built largely from spare parts found in the author's workshop. The white disc around turntable spindle is a built-in "spider" for playing 45 rpm records. Disc retracts for 33 and 78 rpm records.



Economy Record Player

Powered with a single tube amplifier, this portable phonograph plays 78, 45 and 33 rpm records. It's got reserve power to fill a big room with music, yet takes no more current than a 15-watt light bulb

HERE is a 3-speed record player that can save you money both in construction and in operation. First, before purchasing any parts, check through your own and your friends' stockpiles for all available parts. For the original record player we salvaged an amplifier, components and speaker from a discarded radio; the cabinet was a beat-up relic pock-marked with odd holes. If you have an old 78 crystal pickup in working order, just replace the .003 needle with a .001 sapphire designed for 45 and 33-rpm long-play microgroove records. If you want to play old 78-rpm records as well, a .002 all-purpose needle can be used, but we don't advise it. We purchased a new turnover phono pickup for playing 78, 45, or 33-rpm records and the 3-speed motor and turntable used here.

Economy of operation can be traced to the motor. The conventional motor is designed with a coil for operating on 120-volt 60 cycle current. The motor used here, however, is wound with a 95-volt coil. Connecting the motor in series with the heater of the 25L6GT pentode tube adds up to 120 volts. Thus the tube provides the series voltage drop for the motor, or the motor provides the voltage drop for the tube—however you wish to look at it. A step-down heater transformer or a current-wasting voltage-drop resistor, usually required with single pentode amplifiers, is not needed.


The circuit is extremely efficient and simple. Although the amplifier uses a single tube, it supplies sufficient output to fill a 20 x 20-ft. room. Operated directly off the 120-volt a-c line, the player is completely shockproof even if installed in a metal cabinet.

Any discarded record player cabinet, or one made from scrap wood, may be used. It may be as small as 3 1/4 x 8 x 10 in. I.D., which will leave a turntable overhang (Fig. 2). This, how-


MATERIALS LIST—ECONOMY RECORD PLAYER

No. Req.	Description
1	3 x 5" pc. #14 or #16 aluminum (chassis)
1	.01 mfd. capacitor, 150 w.v. or higher
1	.05 mfd. capacitor, 150 w.v. or higher
1	.1 mfd. capacitor, 150 w.v. or higher
1	50-50 mfd., 150 w.v. electrolytic strap-type capacitor
1	150 ohm, 1/2-watt composition resistor
1	47 ohm, 1-watt composition resistor
1	10K (10,000) 1-watt composition resistor
1	1 megohm potentiometer, audio taper (volume)
1	500K (1/2 meg.) potentiometer with S.P.S.T. switch attached
1	50 ma. selenium 1/2-wave rectifier
1	4-in. PM speaker with 2000 to 2500 ohm audio output transformer
1	3-speed phono motor with 95 v. coil and turntable. Alliance, General Industries, or German import

No. Req.	Description
1	turnover crystal pickup, Astatic Model TMS with #7-CAC-D arm. (Rose Electronics, Inc.—see above)
1	25L6GT pentode output tube
1	octal wafer-type socket
1	4 x 4" plastic or aluminum screening (speaker grille)
2	1/4 x 3/4" spacers
3	6-32 fh screws and nuts, 1" long
3	6-32 fh screws and nuts, 1/4" long
1	6-32 machine screw and nut, 3/4" long
1	1-lug tie-strip
1	2-lug tie strip
1	TV "cheater" cord and male interlock receptor
2	knobs

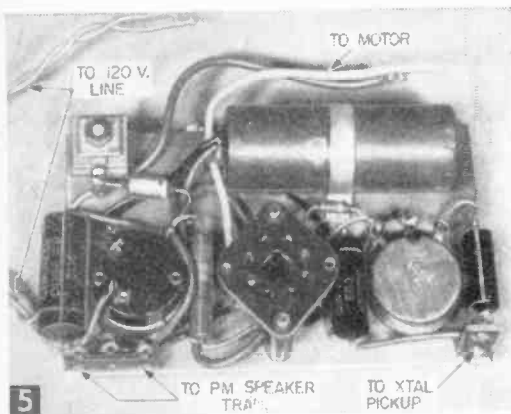

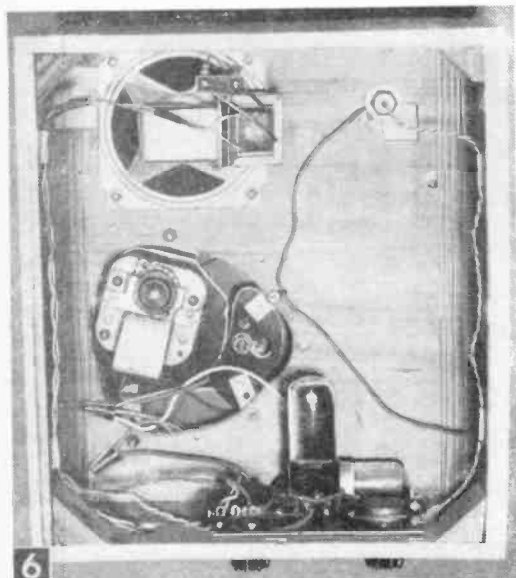5 Amplifier chassis is flat aluminum plate smaller than a 2¢ postcard. Note excess metal of 6-32 socket mounting screws has been filed off flush with nuts.




6 View of underside of record player. Amplifier bolts to side of cabinet with single 6-32 screw. Loose leads are affixed to cabinet with masking tape.

$\frac{3}{4}$ -in. 6-32 machine screw which secures chassis to cabinet (see Fig. 1). Control holes in the cabinet are $\frac{5}{8}$ in. dia. to allow clearance of potentiometer nuts. Use plastic or aluminum fly screening, loose-woven plastic fabric or a 4 x 4-in. piece of perforated sheet aluminum as speaker grille. Mount pickup clip under lower righthand speaker mounting screw.

Fit cabinet with a TV male interlock and "cheater" cord rather than a plain cord, so cord can be removed from the record player when not in use. To avoid hum pickup, the line switch is not part of the volume control, but is attached to the tone control which is removed from the grid input. Another source of hum pickup can be avoided by connecting wire from amplifier chassis to motor frame to pickup washer on underside of cabinet (Fig. 6).—T. A. BLANCHARD.


Chassis Punching

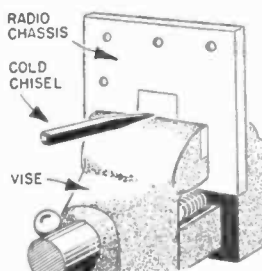

When you need to punch square holes neatly in a metal radio chassis, yet don't have a square punch, a cold chisel and bench vise can be used to punch holes of almost any size. As cutting proceeds, rotate the chassis so that the outline mark is always flush with the vise jaws. You will find that this method is faster and gives an outline almost as smooth as that obtained with a chassis punch.—JOHN A. COMSTOCK.

Radio Shaft Coupler

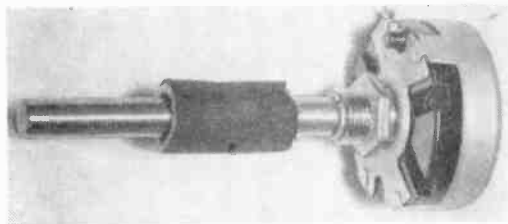
A 1-in. length of automobile windshield-wiper hose can be used as a quick, inexpensive $\frac{1}{4}$ in.-to- $\frac{1}{4}$ in. shaft coupler for radio and other electronic components. While not intended to replace conventional couplers which employ setscrews, the hose does grip the shafts with surprising tenacity, making it handy in an emergency or in



an experimental lashup. A 3- to 4-in. length of the hose makes a good flexible coupler for connecting the shaft of a variable component to a knob shaft when the two are out of line with each other. Offset drive up to at least 45 degrees is easily accomplished. Other uses for the hose include couplers for small electric motors, Veeder-Root counters; in fact, anywhere $\frac{1}{4}$ in. shafts are used and the load requirements are moderate.—FRANK H. TOOKER.

Tooth Brush Becomes Radio Tool

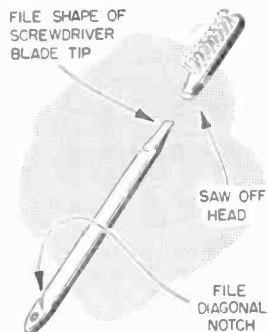The plastic handle of that worn toothbrush you're about to throw away will make a useful radio tool. Saw off the bristly head, file the neck thin in the shape of a screwdriver blade tip and use it as an alignment tool. The opposite end makes a handy probe and, with a notch filed in one edge, the tool also can be used for dial stringing.—JOHN A. COMSTOCK.




puts and also a microphone input, bass and treble control, as well as a volume control with switch. Since a small self-contained battery is used with this unit, no outside power connections are required and the unit can be placed up to 175 ft. away from its associated equipment if desired.

The transistorized preamplifier can be built from a kit supplied by Lafayette Radio or you can build it entirely from the group of standard parts given in the Materials List. The chassis, however, is not a standard size, so it is bent up from sheet aluminum to the dimensions given in Fig.

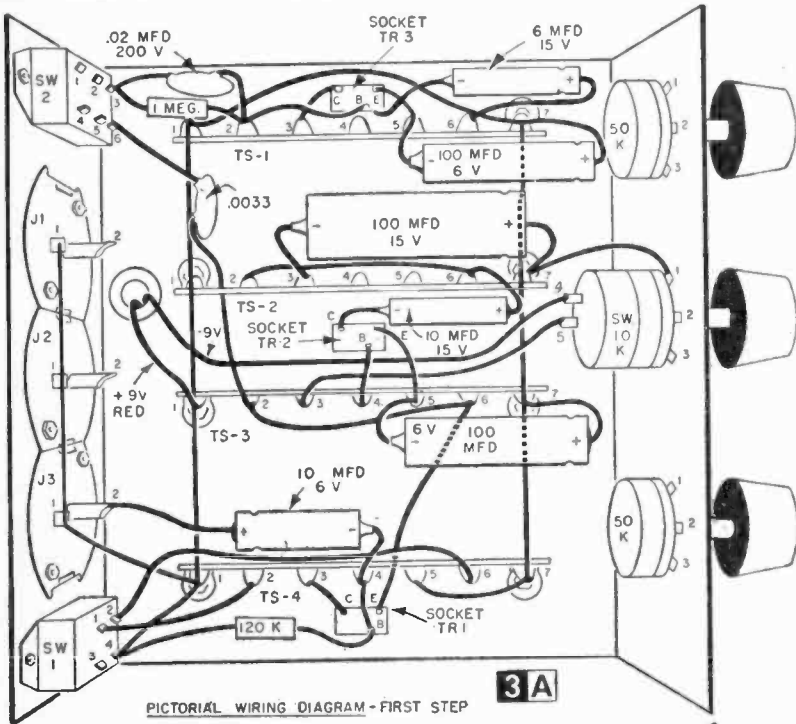
1. It can be bent up in a vise over a hardwood block, but a bending brake will make a better job of it. If you don't have a brake, perhaps your local sheet metal shop will do this for you on their.

Lay out the rectangular socket holes on the metal and then drill a number of holes within the rectangular area. Break out the metal between the drilled holes and dress to size and shape with a file. Fix the sockets in their openings on the chassis, positioning them so that the terminal with the widest spacing (collector) will be located with respect to the other components as shown in Fig. 3. (A locking ring is forced down on the lower end of each socket, securing them in place.) Now install the jacks and controls, as well as the long terminal strips. Be sure to place as indicated, with the volume control and On-Off switch in the center. Secure the slide switches in their openings, attach the battery holder to the top of the chassis—using for this purpose one of the bolts securing a terminal





PICTORIAL WIRING DIAGRAM - FIRST STEP

3A

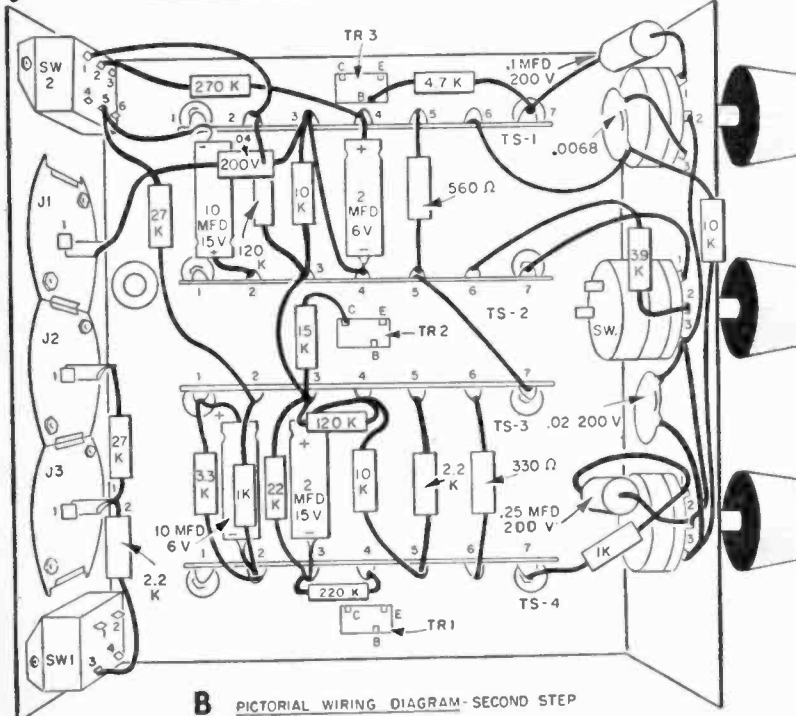


B PICTORIAL WIRING DIAGRAM - SECOND STEP

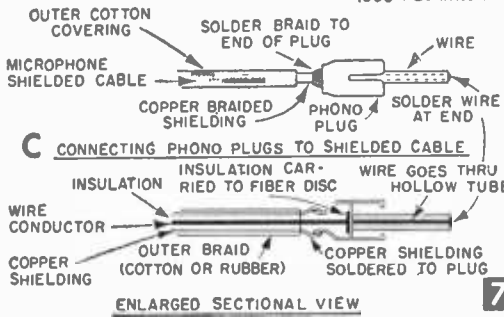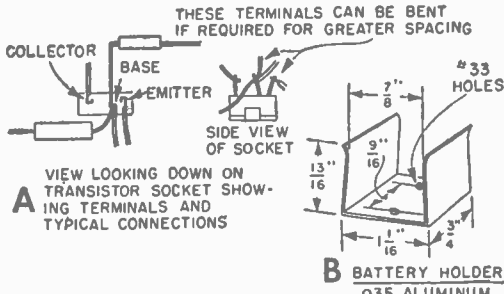

A good first test can be made with a microphone and amplifier, together with a speaker. The unit shows excellent gain over results obtained by plugging the mike directly into the amplifier. For phonograph use, simply plug a magnetic cartridge into the input jack instead of the mike. A selection of either high or low impedance jacks with a high-low switch allows the best matching conditions. Connections between the mike or phono cartridge as well as between the preamplifier and the power amplifier should be made with shielded cable to avoid picking up hum. The method of installing these phono plugs to cable is shown in Fig. 7C.

Buttoning Up Earphones

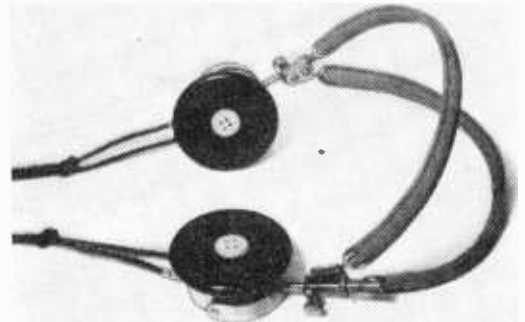
• In order to protect the thin metal diaphragm inside an earphone which has a single large opening in the cap, cement a button over the opening with *Duco* cement. Sound waves readily pass through the small openings in the button but



the diaphragm is protected from damage by sharp objects when phones are stored or transported. The button also provides a better ear seal between the cap opening and the eardrum.—A. TRAUFFER.

Knobs for Compression Capacitors

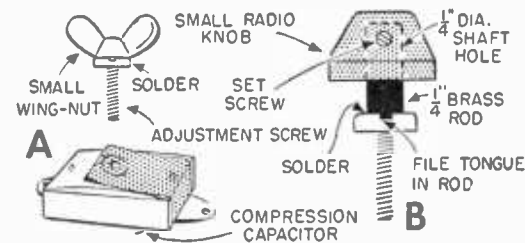
• Small economical compression-type capacitors up to 380 mmf capacity used as tuning capacitors in crystal sets or small tube sets can be adjusted without a screwdriver if you solder a small wing-



nut to the head of the screw (see A). If hand-contact effects are troublesome when using a wing-nut, solder a short length of 1/4 in. dia. brass rod securely to the head of the screw to take a small radio knob (see B). File a tongue in other end of rod to fit slot in screw head.—A. TRAUFFER.

MATERIALS LIST—TRANSISTORIZED HI-FI PREAMPLIFIER

No. Reqd.	Description
3	transistor sockets MS-275
3	G.E. 2N190 transistors
1	9 volt Burgess 2U6 battery
1	male and 1 female battery snap-on clip or snap-on, two-terminal insert
1	D.P.D.T. slide switch (SW17)
1	D.P.S.T. slide switch (SW16)
3	RCA type phono jacks and plugs
1	10-K ohm volume control with switch (K = 1000), miniature type VC-28
2	50-K ohm controls (no switch), miniature type VC-36
3	miniature knobs for 1/8" shaft MS-185
4	solder lug terminal strips each with 2 ground lugs, 5 insulated lugs
(7 total)	Cinch-Jones 55-A
2	27-K ohm 1/2 watt resistors
2	2200 ohm 1/2 watt resistors
3	120-K ohm 1/2 watt resistors
1	220-K ohm 1/2 watt resistor
1	330 ohm 1/2 watt resistor
1	3300 ohm 1/2 watt resistor
2	1000 ohm 1/2 watt resistors
2	10 mfd. 6 volt Argonne capacitors (electrolytic)
1	2 mfd. 25 volt Argonne capacitor (electrolytic)
2	100 mfd. 6 volt Argonne capacitors (electrolytic)
2	10 mfd. 15 volt Argonne capacitors (electrolytic)
1	100 mfd. 15 volt Argonne capacitor (electrolytic)
1	6 mfd. 15 volt Argonne capacitor (electrolytic)
1	2 mfd. 6 volt Argonne capacitor (electrolytic)
2	.02 mfd. disc ceramic capacitors
1	.25 mfd. 200 volt capacitor (Aerovax Aerolite PB2Z)
1	.0033 mfd. disc ceramic capacitor
1	.1 mfd. 200 volt capacitor
1	.0068 mfd. disc ceramic capacitor
1	.04 mfd. 200 volt capacitor (Aerovax micro-miniature PB3Z)
1	rubber grommet for 1/4" hole.
1	pc half-hard alloy sheet aluminum about .040" x 7" x 4 1/2" (bend to make chassis)
1	pc half-hard alloy sheet aluminum about .030-.035 x 3" x 3/4" (bend to make battery clip)
18	round head 4-40 machine screws 1/4" long
18	4-40 hex nuts
	plastic covered hook-up wire about 24 gage (stranded); small spaghetti tubing
	Kit #KT117 for building the Hi-Fi Preamplifier can be obtained from Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N. Y., for \$18.45.

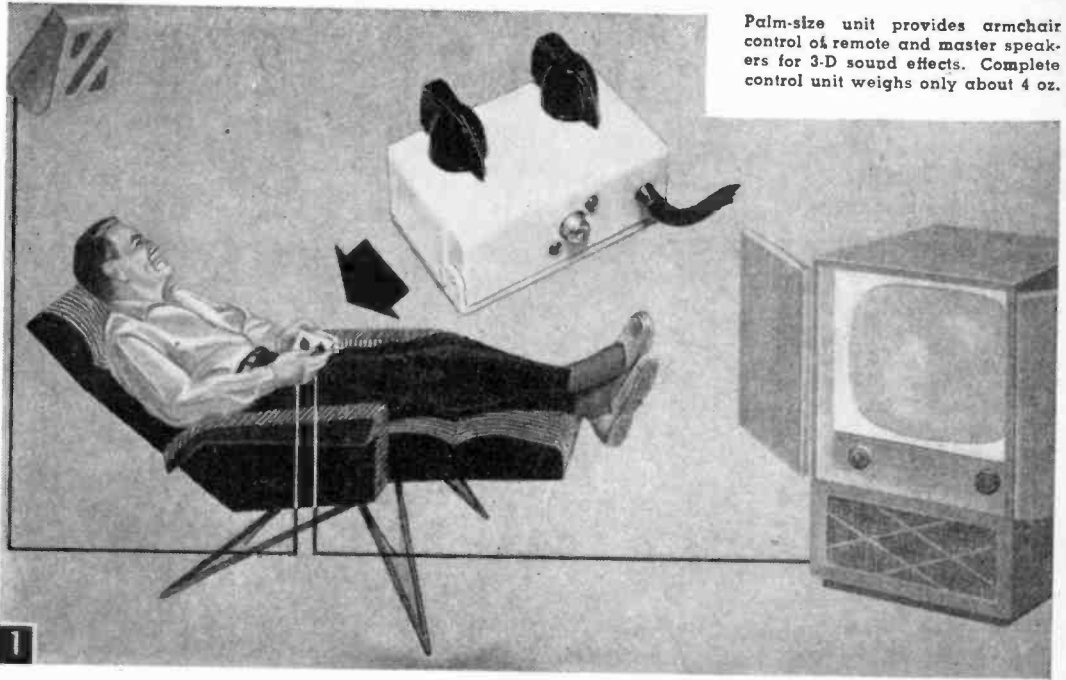

Palm-size unit provides armchair control of remote and master speakers for 3-D sound effects. Complete control unit weighs only about 4 oz.

Armchair Speaker Control

FOR a surprisingly small investment, plus a few simple and safe alterations, your radio, TV or phono amplifier can be given a new sound dimension. From the comfort of an armchair, you can control—separately—the volume of the console speaker and that of an extension speaker located in an opposite corner of the room. Music, adjustable from a whisper to a roar without leaving your seat, literally surrounds you.


An 8-in. PM speaker is the ideal size for the remote unit. It can be mounted in a homemade cabinet, or your parts dealer can furnish inexpensive wall cabinets in a variety of sizes to fit speakers from the 4 to the 12-in. size. Speakers are graded and priced by the ounce-weight of the magnet.

Whatever size of speaker you may select, it is wise to pay a little more—the best speakers are relatively inexpensive—for the model with a heavy Alnico magnet.

Decide where you wish to locate the remote speaker, measure the distance between it and the spot where you want to

place the control box, and purchase a suitable length of regular lamp "zip" type plastic fixture cord at any hardware or dime store. Connect one end of the fixture cord to the speaker's two voice coil soldering terminals. To the opposite end of the cord, solder an ICA type phono plug. This completes the work on the remote speaker.

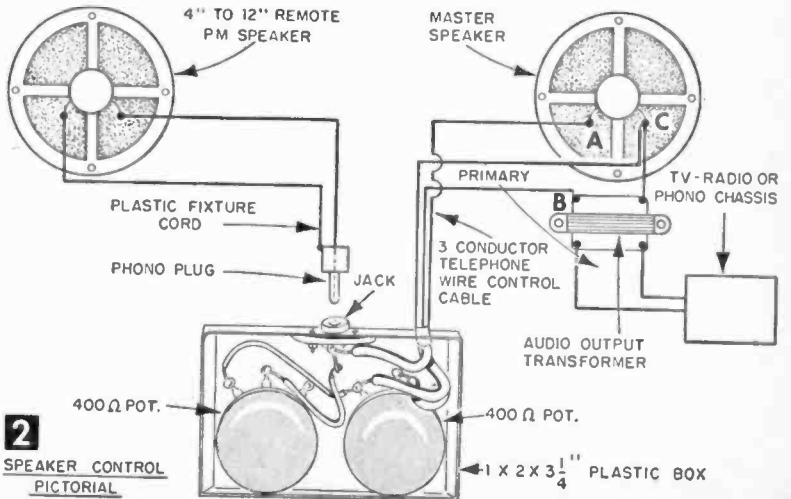The armchair, dual volume control is a palm-sized plastic box (it can be as small as 1 x 2 x 3 1/4 in.) in which are mounted the volume controls, two 400 ohm, wire-wound potentiometers. Four 3/8



2
SPEAKER CONTROL
PICTORIAL


MATERIALS LIST—ARMCHAIR SPEAKER CONTROL

No.	Description
1	plastic or homemade box, 1 x 2 x 3/4" or larger
1	phono plug and jack (ICA)
2	wire-wound potentiometers (IRC #W-400)
1	6 or 8' 3-conductor telephone wire
1	length plastic "zip" fixture cord
1	PM speaker with heavy Alnico magnet, any size from 4" to 12"
1	homemade or commercial cabinet for speaker
2	knobs

in. holes are drilled in the box: two on the top for mounting the potentiometers, and two on the side, one for the ICA type phono jack, and one for a clearance hole for the three-wire control cable to the master console speaker.

Using three-conductor telephone wire, connect the components as shown in Figs. 2 and 3 (note that the potentiometers are wired as rheostats, with no connections to their righthand terminals). The control cable should be long enough to reach from the master speaker to your armchair, coffee table, etc. You can, of course, leave the control on top of the console cabinet if desired. With circuit components connected to the leads of one end of the three-conductor wire, the control box is complete.

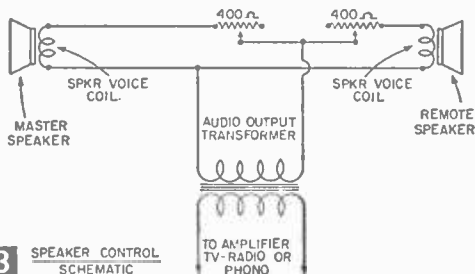The final step is to make connections to the console master speaker. Some receivers and amplifiers have the audio output transformer mounted directly on the speaker frame. Others



have the output transformer mounted on the chassis. In either case, do not disturb any wires on the primary side of this transformer. Instead, connect cable wire C to voice coil lug C on speaker (see Fig. 2; do not remove the wire already connected to C). Next, unsolder the lead on speaker lug A, connect this disconnected wire to cable lead B and tape up the connection. Finally, connect cable lead A to the now vacant speaker lug A and the installation is complete.

Turn on the TV, radio or phono player, advance its volume control all the way, and turn both control knobs on your armchair control to the extreme left. Now, plug the remote speaker into the phono jack and you're ready to go; advancing one knob on the armchair control will bring up the volume of the remote speaker, advancing the other will bring the console speaker into play. A multi-dimensional sound effect re-


sults when you place yourself between the two speakers. Adjusting the individual volume controls to different levels furthers the effect, making it seem that the music is coming from all parts of the room. When desired, the master speaker operates *without* the remote cable being plugged in.—T. A. B.



"GOT A CALL HERE TO REPAIR A RADIO. THINK YOU REMEMBER HOW?"

Quick Volume Control Cleanup

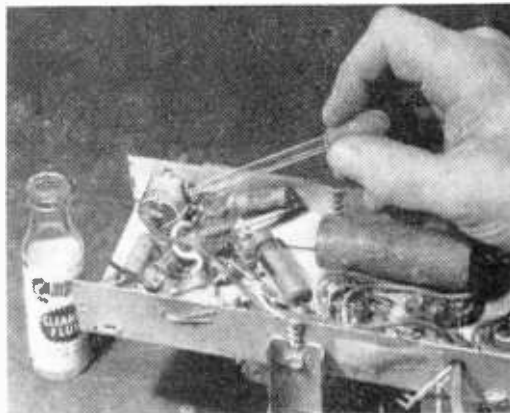• When the volume or tone control on a radio becomes scratchy and spotty, the reason is usually hardened grease on the contact ring, or glaze on the resistance element. Instead of unsoldering wires and dismantling the control in order to



clean the parts, squirt a small amount of carbon tetrachloride from a medicine dropper onto the control surfaces through the lug openings, and work the shaft back and forth until it dries. This may be done while the set is in operation, so that the results can be judged on the spot.—HERBERT Y. MOON.

Air-Powered Tuner

Adds Hi-Fi to Your
TV Set or Record Player



This little tuner brings hi-fi radio reception to TV when plugged into the set's "phono jack." Photo above shows how an old alarm clock case provided a neat cabinet for the tuner.

local stations as well as high-powered transmitters within a 50 mile radius. We have, however, used it to receive distant stations late at night using an outdoor antenna. Ordinarily, no elaborate antenna is needed. Crystal detectors are not highly selective and the shorter the antenna, the greater the selectivity (and the lower the sensitivity). In this respect, attaching the antenna lead to one of the antenna terminals on the TV set, or to some non-grounded metal object, provides more than ample signal pick-up.

You'll also find that this "air powered" tuner is virtually static free. Clicks, and buzzes common to conventional radios, do not exist. Only severe electrical storms will create static and to a much lesser degree than they do on electric powered sets.

Because of the few parts required for this tuner (Fig. 3), we were able to build the unit on a Masonite or plywood panel which fits into a plastic case which once contained an alarm clock (Fig. 2). You can easily make a case for the tuner if you don't have a defunct clock handy. Our clock case had a round flanged opening for the $3\frac{3}{4}$ in. diameter clock face and bezel. A $3\frac{3}{4}$ in. diameter Masonite disc was cut to fit this opening and the radio components were mounted on this disc.

Two holes drilled close to the disc edge allow it to be rigidly clamped in the clock case, using two 6-32 x $\frac{1}{2}$ in. *rh* machine screws, washers and nuts. A $\frac{3}{8}$ -in. hole drilled in the center of the panel will clear the capacitor shaft and its ball bearing rotor. The 6-32 tuning capacitor mounting holes are located and drilled after the capacitor has been obtained, since mounting hole


MATERIALS LIST—AIR-POWERED TUNER

- 1 plastic alarm clock case about $4\frac{1}{2}$ x $4\frac{1}{2}$ x 2" (or homemade cabinet)
- 1 364 or 374 *muf* variable tuning capacitor (midget or small size)
- 1 50 *muf* fixed mica or ceramic capacitor
- 1 1N60 or other general purpose crystal (germanium) diode
- 1 Ferrite slug-tuned antenna coil
- 1 3-lug soldering tie-strip
- 1 antenna clip (Mueller Alligator clip #60 or #85)
- 1 phono pin plug
- 1 length (3 to 5 ft.) shielded phono cable
- 1 length insulated hook-up wire for antenna lead
- 1 small piece Masonite for panel
- 1 strip #16 copper, aluminum, etc., for coil mtg. bracket ($1\frac{1}{4}$ x $1\frac{1}{2}$ in.)

SINCE radio's early days the high fidelity virtues of the crystal detector have been well known. The modern counterpart of the old catwhisker "tickled" galena, silicon, or iron pyrite detector is the germanium diode . . . a tiny fixed crystal unit that never requires delicate adjustments. So dependable is this little crystal diode that many TV sets use it, instead of a tube, as the Video Detector.

Since many TV receivers have a plug-in connection for record players, a suitable tuner will allow reception of local AM radio stations when connected into the TV set's *phono jack*. For that matter, this "air-powered" tuner may be connected into any amplifier with two or more stages. Why do we call it "air-powered"? Well, the tuner itself costs nothing to operate since power is taken right out of the ether.

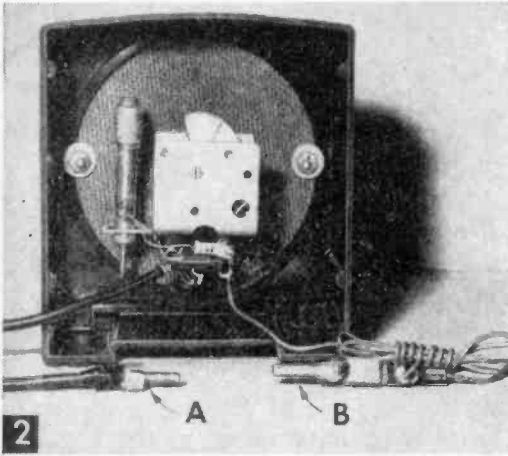This tuner of course is limited to reception of



2
Masonite panel fits opening in clock case, and is securely clamped by two 6-32 machine screws on each side of flanged retainer. Note phono pin plug connector at A and antenna clip lead at B.

locations vary widely from one make to another.

The variable tuning capacitor is a small broadcast type of either 364 or 374 mmf. The antenna coil is a high-Q ferrite slug-tuned type. Make a small bracket for the coil as in Fig. 3. Then snap the coil into the 5/16 in. bracket hole, and mount the bracket into one of the various 6-32 holes found on the capacitor frame. Also screwed down with the coil bracket a 3-lug soldering tie-strip, to which various components are eventually terminated for a neat and rigid assembly.


Wire up components as in Figs. 3 and 4. When soldering the germanium diode detector into the circuit, hold a small wad of damp cotton or cleansing tissue around the pigtail lead being soldered, so that heat is not conducted up into the little unit. Excessive heat can ruin the diode's internal adjustment.

Not shown in Figs. 3 and 4, though *theoretical* necessary, is a dc load resistance across the output jack. You can use a 1/2-watt unit of from 39,000 to 50,000 ohms. You will need to add it, however, only if the output signal is distorted.


When connecting up the antenna coil, note that the inside or "start" lead of the winding connects to the stator (stationary plate) lug of tuning capacitor along with one side of the 50 mmf coupling capacitor and the anode or unmarked end of the crystal detector (Figs. 3 and 4). Remaining coil lug, and capacitor and diode pigtails terminate on the tie-strip as in Fig. 3.

The output cable is ordinary shielded phono wire which consists of a light copper outer braid and center insulated lead. Connect the braid to the lefthand tie-strip lug, and connect the inner lead to the center lug (Fig. 3). Connect the remaining end of the phono cable to a phono pin plug—braid to plug shell, and inner wire to plug pin.

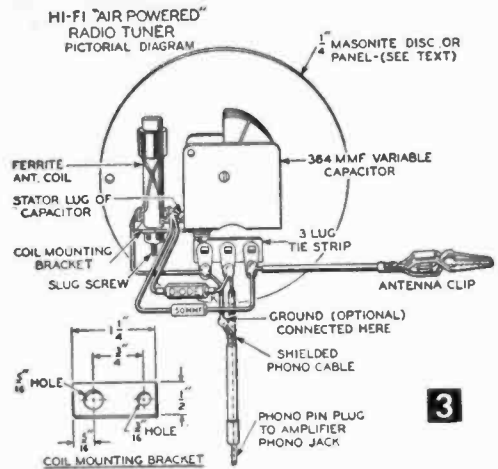Cut about 6 foot of insulated wire for antenna lead. Solder one end to the righthand tie-lug, and attach a small battery or test clip to the



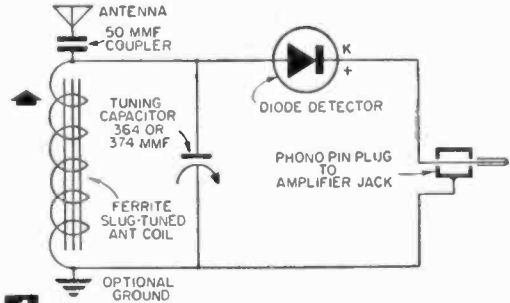3
Tuning capacitor carries all components which are wired before assembly is secured to Masonite panel. Single 6-32 screw fastens coil bracket and soldering tie-strip to the frame of tuner.




4
SCHEMATIC DIAGRAM

remaining end of the wire. Your "air-powered" tuner is now ready for testing.

Testing. If the tuning capacitor does not tune high enough with plates open, turn the slug screw on the antenna coil out until a station at the 1500 kc end of the dial comes in (assuming you have a local station at this point on the dial). On the other hand, if a local station is around 550 kc on the dial, turn the coil screw in until it can be picked up with the variable capacitor's plates in meshed position.

Assuming that your wiring is correct, and that your amplifier is a 2- or 3-stage job that provides ample volume when used to play LP records with a low voltage output crystal, your "air-powered" tuner should provide excellent results.

But remember, in areas where there are a number of local stations, the tuner may lack selectivity if too much antenna pick-up is used. We found a 6 ft. length of wire ample for local reception with volume control 50% retarded. Therefore, if you have a selection of local stations, a good antenna isn't necessary. Where more signal pick-up is needed (since local stations are non-existent) the use of a more efficient antenna will not pose any problem since distant station selectivity will be as good as with a TRF type electric receiver.—T. A. BLANCHARD.

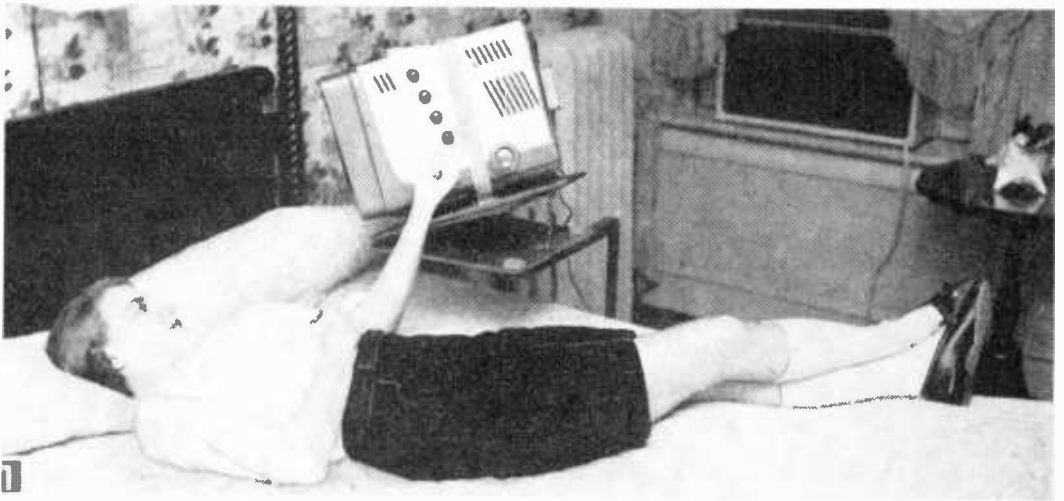

Relax while enjoying the program with a portable television set carried on a bedside stand. Simply roll it into position, swivel the set to face you, then tilt it to a good viewing angle.


Bedside TV

AT TACH a portable television set to this adjustable bedside stand and you can watch your favorite TV programs while resting or convalescing in bed. The swivel top allows set to be turned in any direction; hinges permit tilting for best viewing (Fig. 1). Wheels on the base of the stand make it easy to position set at any distance from the bed. Designed to hold a 14-in. GE set, table can be altered to accommodate your portable TV.

Make the top or platform of three pieces of $\frac{3}{8}$ x 12 x 13-in. plywood (Fig. 2). At the exact center of two of the pieces, drill a $\frac{1}{4}$ -in. hole and insert a $\frac{1}{4}$ -in. dia. x 1-in. long machine screw which serves as a pivot. Pull up the screw fingertight into the nut and, with a center punch, upset the end of the screw slightly so that the nut cannot come off. Hinge the lower piece of plywood to the third piece at what will be the front of the platform.

Equidistant from each edge, drill a row of matching $\frac{1}{8}$ x $\frac{1}{8}$ -in. deep holes 1 in. apart in bottom of center piece and in top of bottom piece. Cut a 2½-in. length of stiff coat-hanger wire to use for tilting platform to desired angle. Attach a length of safety chain with screw eyes to center and lower parts of the platform to protect TV set from toppling forward if tilted too far. Two spacer blocks of scrap wood glued to bottom piece of platform will keep TV set level when wire tilt-top brace is removed.

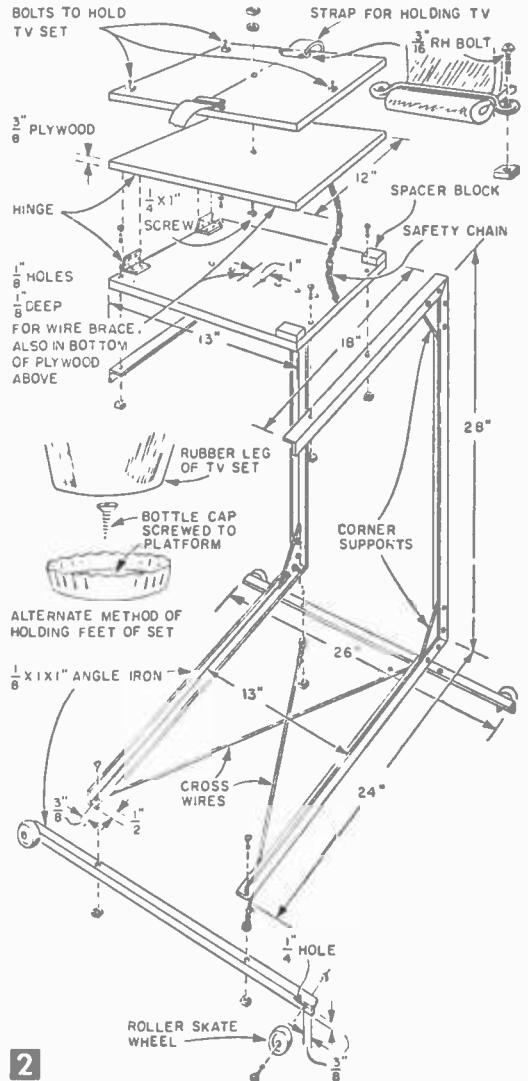Cut a web-type army belt in two so that it can be buckled at top center of the set when attached to platform. Fold cut belt ends under and hold down with section of coat-hanger wire



2

MATERIALS LIST—ADJUSTABLE TV STAND

No.	Size and Description	Use
3 pcs	$\frac{3}{8}$ x12x13" plywood	platform
2 pcs	$\frac{1}{8}$ x1x1"x8" angle iron	stand
1	web-type army belt	holding strap
1	$\frac{1}{8}$ dia. x1" long machine screw	pivot
4	$\frac{1}{8}$ x3x3" right-angle triangles	corner supports
2 doz.	$\frac{1}{4}$ x1" rh stove bolts	stand
4	ball-bearing roller-skate wheels	wheels
8	$\frac{1}{4}$ dia. x1" fh stove bolts	wheels, platform
8	$\frac{1}{8}$ " fh or rh stove bolts	crosswires, belt hold-down
3	$\frac{1}{4}$ x $\frac{3}{4}$ " fh bolts	feet
coat-hanger wire, 2 hinges, length of small chain, 2 small screw eyes, spacer blocks, enamel		

bent as shown (Fig. 2) and secured to plywood platform top with $\frac{3}{16}$ -in. rh stove bolts. To prevent interference with movement of swivel top, countersink nuts into the plywood and file off any rough projections, or use fh stove bolts countersunk with nut on top toward strap.

The three rubber bumpers used as feet on the TV set can be placed in bottle caps screwed to swivel top of platform or, if the feet are hollow, bolt them directly to plywood. Run countersunk fh bolts upward through top plywood piece only so they project about $\frac{1}{4}$ in. above nut, but don't attach TV set just yet. Never set the feet down into holes bored in the platform, or you will cut off the movement of air and the set may overheat.

To make the steel stand (Fig. 2), cut two 70-in. lengths from the $\frac{1}{8}$ x 1 x 1-in. angle iron stock and mark off 24 in. from one end and 18 in. from the other end of both pieces. At each mark saw

out a 90° wedge from one side of the angle iron, then make a right-angle bend at each notch using a vise (see Fig. 2).

Now file round the corners of the remaining two 26-in. lengths of the angle iron stock. Measure $\frac{3}{8}$ in. from one edge and $\frac{3}{8}$ in. from each end of each piece. Drill a $\frac{1}{4}$ -in. hole at this point and bolt a ball-bearing roller skate wheel in place.

Using small C-clamps to clamp the two 26-in. lengths onto the 24-in. portion of the angle-iron stand, drill through the two thicknesses of angle iron with a $\frac{1}{4}$ -in. drill. Assemble with $\frac{1}{4}$ x 1-in. rh stove bolts. To give rigidity to the assembly, add a right-angle triangle at each corner.

Now clamp the bottom plywood board of top assembly to the 18-in. horizontal brackets of the stand. Drill $\frac{1}{4}$ -in. holes through the board and, using $\frac{1}{4}$ x 1-in. fh stove bolts, attach stand to board. Saw off any extra length of bolt and file.

While crosswires at the base are not absolutely necessary, they will make the assembly more rigid. Stretch coat-hanger wire from corner to corner, fastening each end around a bolt. With assembly completed, give it two coats of black iron enamel or choose a color to match or contrast with the furniture in the room. Then slide hollow legs of set down over bolt threads projecting from top of platform. With the TV set secured in position, pull the strap over the top of the set and draw up moderately tight, and you're ready for that late, late show—E. P.

Shelf Amplifier Systems




A

Amplifier cabinet is shown next to record player on corner table. Speaker is open-ended enclosure (Fig. 2) beneath table.



B





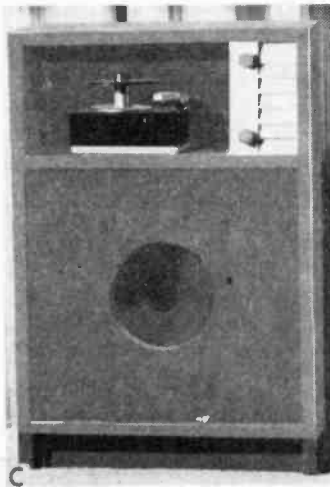


C


B Corner bookcase installation of speaker (detailed in Fig. 4).

C Diaphragm enclosure system (diagrammed in Fig. 3) with amplifier at top right of shelf.

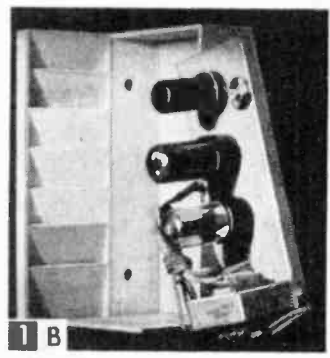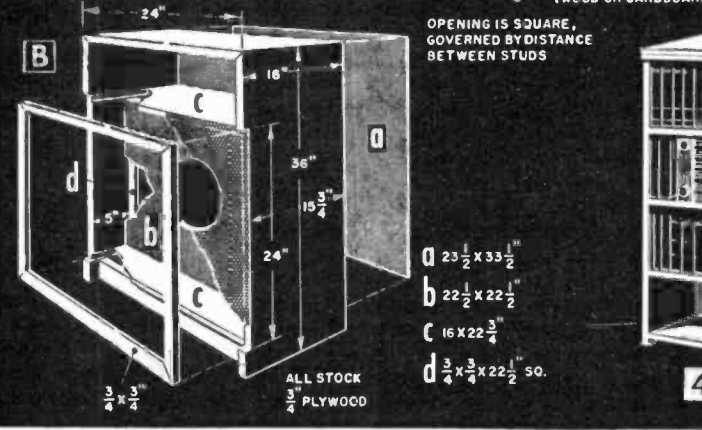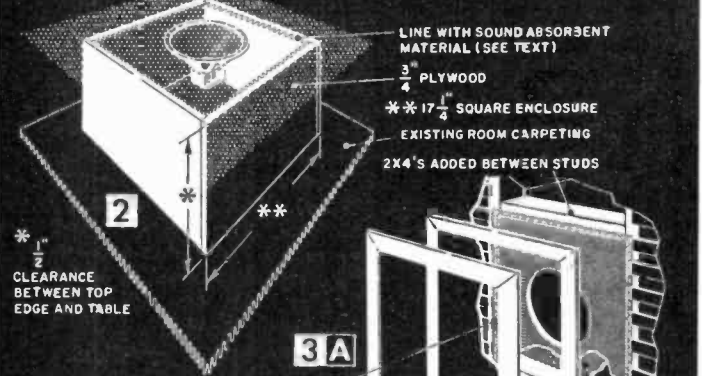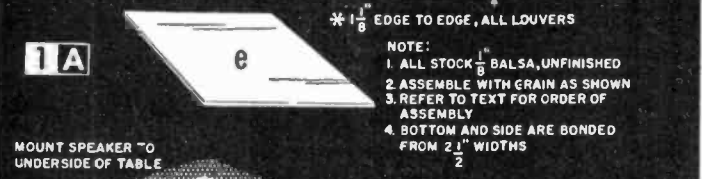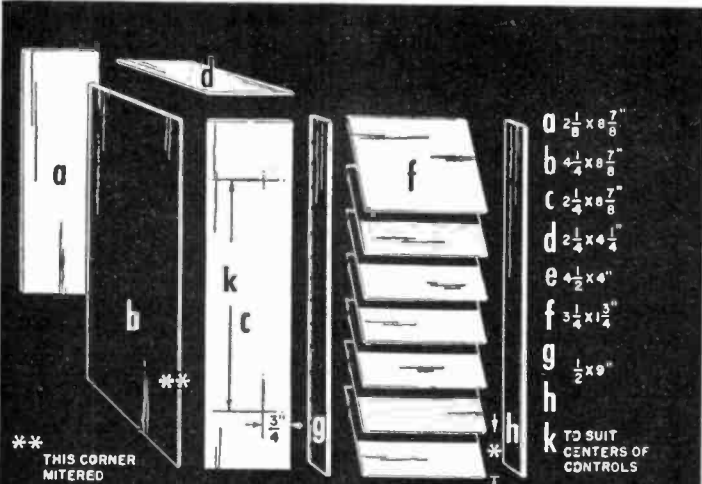DESIGNED for installation in bookcases or similar pieces of furniture, and producing good reproduction for cost, these auxiliary amplifier cabinet and speaker systems feature simplicity and flexibility. The materials are all easily obtained with the possible exception of the balsa wood; this should have a brown or



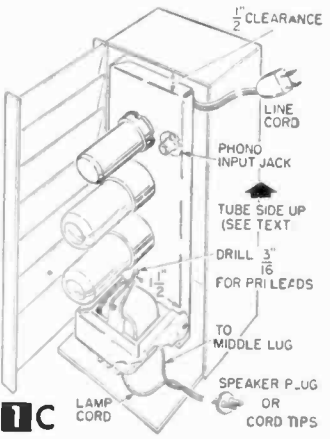
Amplifier and cabinet in which it is placed.




reddish color, (stronger than the good-looking white) and should be well dried.


The amplifier cabinet can be waxed, but left unfinished it has a soft, attractive quality—and is easy to clean.

To construct the amplifier

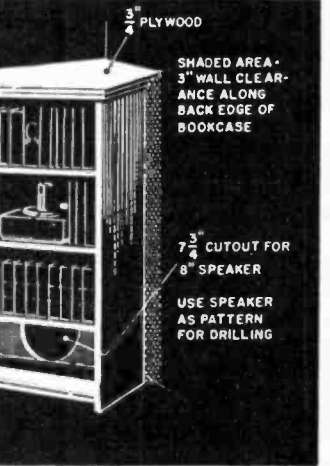

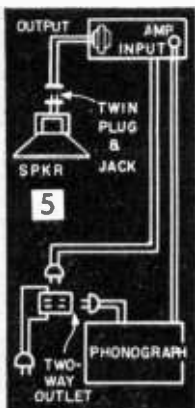

CORNER INSTALLATION OF OUTLET AND JACK

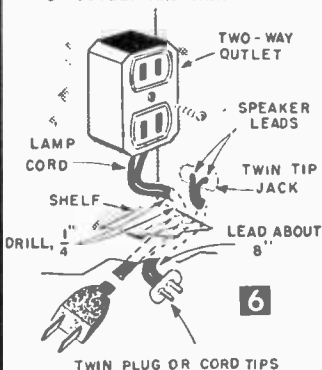

cabinet, cut all parts to the dimensions indicated in Fig. 1A and sand lightly with fine sandpaper to produce a satin-like finish. Assemble the louvered unit first, then cut the control holes in the front panel. Although the overall dimensions will remain similar no matter what type of two or three tube amplifier you use, control locations will vary from one unit to another and for that reason the center to center distances of the control holes should be taken from the chassis of the amplifier you're housing. Be sure, however, to leave the required $\frac{1}{2}$ -in. ventilation space all around as in Fig. 1C. (The amplifier shown in Fig. 1 is a three-tube amplifier. The Knight-Kit "Low-Cost Phono Amplifier Kit" listed in the Materials List is a two-tube amplifier that also fits well in the cabinet. Kits, usually, are less expensive than pre-built units.)

Build the remainder of the cabinet, starting with the front panel, adding the side panel of two cement-bonded pieces, then the rear panel, top, and bottom panel of two bonded pieces. Sand square and add the louvered section, finish with #00 sandpaper. Use a sanding block; the sanding must be even.

Mount the amplifier with the hottest, or tube side upward to assure optimum heat dispersal (Fig. 1C).

You can control the record player from the amplifier switch, or, as shown in Figs. 5 and 6, you can plug it into a two-way outlet (more flexible) and control it with its own switch.

Three extremely simple adaptations of well-known speaker enclosures can be used in conjunction with the amplifier unit.

The first enclosure, suitable for corner table installation, consists of four pieces of plywood (Fig. 2) lined with a sound absorbent material, such as 1 in. of felt, or deep pile carpeting, fiberglass or cotton batting. Make the interior as "dead" as possible, allowing $\frac{1}{2}$ -in. clearance between the top edge of the enclosure and the table top. Screw-fasten the speaker snug against the underside of the table using #3 x $\frac{1}{2}$ -in. fh screws, but be careful not to warp the frame of the speaker.

The second enclosure (Fig. 4), for use with a

MATERIALS LIST—SHELF AMPLIFIER SYSTEMS

No. Req.	Description
1	amplifier kit Cat. #83Y790
2	knobs Cat. #71H208
1	twin-tip jack Cat. #43H261
1	twin-tip plug Cat. #43H260
1	two-way outlet
12'	lamp cord
1	line plug
1 tube	Comet cement
2 1/2 sheets	Balsa wood 1/8 x 3 x 36" (see text)
1	8" speaker Cat. #81D144
4 pcs.	3/4" plywood 12 1/2 x 17 1/4" corner table installation
1 pc.	3/4" plywood 26 x 26" bookcase installation
2 doz.	#7 x 1 1/2" fh screws
1 doz.	#3 x 1/2" rh screws
1 doz.	#6-1" fh screws
	Diaphragm Enclosure
1 pc.	22 1/2 x 22 1/2" Plywood, 3/4"
2 pcs.	16 x 36" Plywood, 3/4"
2 pcs.	16 x 22 3/4" Plywood, 3/4"
1 pc.	16 x 24" Plywood, 3/4"
9'	1 x 2 stock
1 yd.	100 count muslin
1 pc.	hardboard 23 1/2 x 32 1/2"

(Catalog #'s are those of Allied Radio Corp.
100 N. Western Ave., Chicago 80)

corner-located bookcase, gives slightly better results with the same speaker and is even easier to construct than the open-ended enclosure.

Make a cut-out in the back-board of a corner-located bookcase centered between the two bottom shelves and fasten your speaker to the rear of the bookcase with machine screws. Again, be careful not to warp the frame of the speaker. Locate the bookcase at equal angles to two intersecting walls, allowing 3-in. clearance along the back edges (Fig. 4). Then cut a 3/4-in. plywood wedge top to fit snug with the walls and flush with the front and side edges of the bookcase.

In the third system the speaker is installed in a wall (Fig. 3A) or in an entirely portable enclosure providing for the installation of both amplifier and record player with speaker (Fig. 3B). (Since the size of the enclosed shelf space is not critical, the dimensions given in Fig. 3B for the portable enclosure can be altered to suit your record player.)

Cut out pieces to size and dado the sides and miter the top and top side edges as indicated. Then assemble the sides, top and bottom, and secure the shelf into place, using finishing nails and glue. Add the kick plate, fasten the supports in place with #6 x 1-in. screws, and fasten the baffle to the supports.


Next, cut a hole 8 in. in dia. in the center of a yard of 100-count muslin. Draw the 1-in. lap of material through the baffle hole and staple in place, then pull the material taut to the outer edge of the enclosure and staple in even tension. (The surface must be smooth.)

Now nail and glue the face in place, spray the muslin with three or four heavy coats of lacquer—sufficient to make this diaphragm resonant, but not stiff enough to make response difficult—and finally fasten the speaker in place, again being careful not to warp its frame.—W. R. WADKINS

Automatic Stop for Tape Recorders

By W. F. GEPHART

THE better record changers provide for automatic shut-off following the last record, but few tape recorders are so equipped. Lack of this feature means that the recorder must be shut off promptly near the end of the tape to prevent the tape from coming loose. If the tape does come loose, it may be damaged; in any case, re-threading for re-winding purposes is always necessary. It is particularly annoying to have to be alert to stop the mechanism when listening to music on tape.

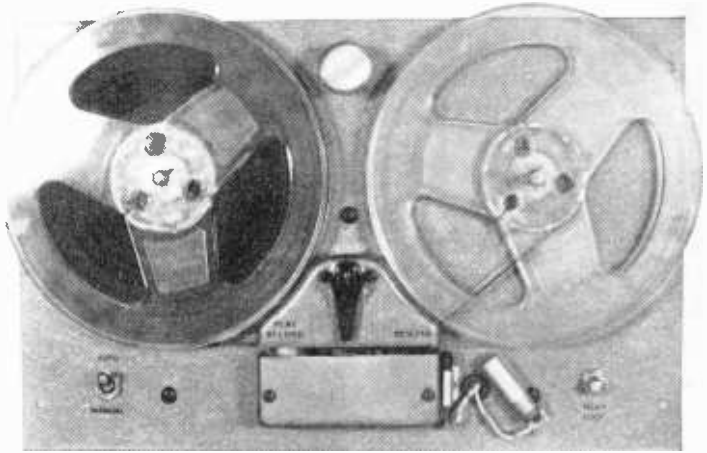

1 Lamp, photocell and Relay Lock switch of automatic tape recorder stop are located lower right. This arrangement of stopper is that shown in Fig. 2B.

The circuit shown in Fig. 4 will automatically stop the mechanism at any desired point on the tape. It can also be used at the start of the tape to prevent the tape coming off the take-up reel during re-winding as well as at the end of the recorded material on the tape. It can be adapted to any recorder.

The circuit is complete with power supply, but power can be secured from the recording amplifier if desired. The power supply is shown within the dotted lines on the schematic and, if external voltages are available, the parts within the dotted lines and half of the "Auto-Manual" switch (S1a) can be eliminated. Power requirements are 6.3 v. at .45 amp. (connected to points "C" and "D" on Fig. 1) and 130 volts at 10 ma (positive connected to point "A" and negative connected to point "B").

When the recorder is to be used on "automatic stop," S1 is put in the "Auto" position, connecting the motor circuit through the upper contacts of RY1 (and turning on the power to the control unit). The motor circuit is not complete until


the relay (RY1) is closed and the regular recorder starting switch is closed. The relay is closed by pressing the "Relay Lock" button (S2). It is held closed by the lower set of its own contacts, connected in a locking circuit. The recorder is then started (either "Forward" or "Rewind") in the usual manner.


Due to adjustment of the sensitivity control (R3) as explained below, tube V1 is not conducting and RY2 is not energized. When light strikes the photocell, however, the tube conducts, energizing RY2, which breaks the circuit to the coil of RY1, which opens and stops the motor.

Figure 2 shows two means of lamp-cell placement. In most recorders, the arrangement shown in Fig. 2A will be required, particularly when large reels are used. In this case, a strip of aluminum foil is cemented to the outside of the tape at the point where the mechanism is to stop. As this reflective coating passes the lamp-cell area, light is reflected into the cell which starts the tube conducting and stops the motor.


If sufficient room is available, the arrangement in Fig. 2B can be used. In this case, a section of clear cellophane is spliced in the tape at the desired point, and the light goes through the tape to stop the motor.

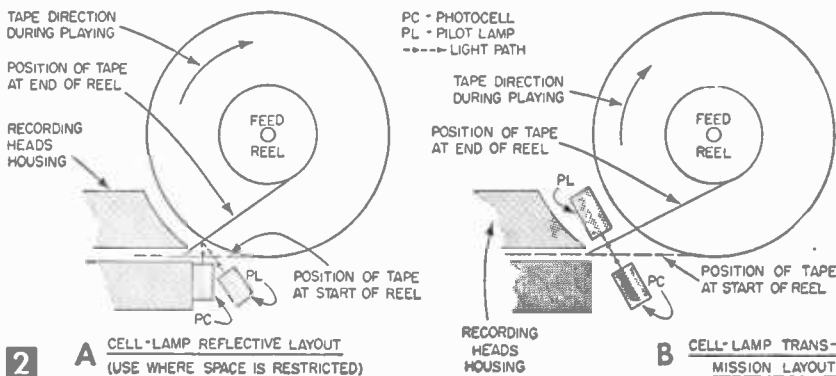In either case, the sensitivity of the circuit must be set at a level



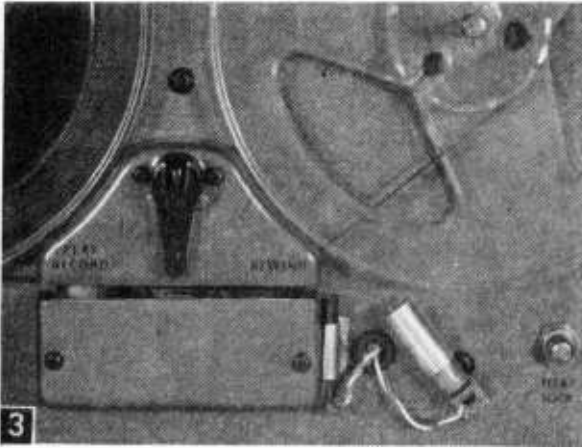

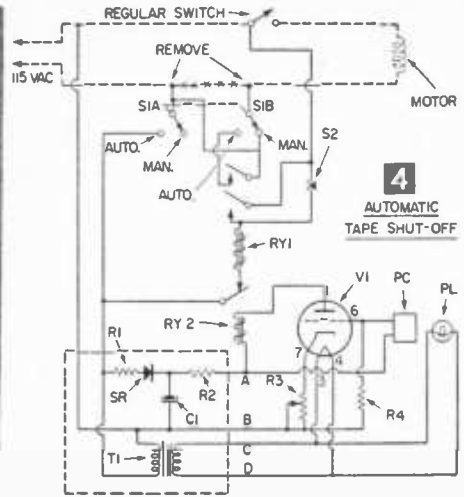Closeup of photocell housing (left), lamp (center), and Relay Lock switch on top of tape recorder case.



which will prevent the circuit from operating at normal room light. This is best done by placing the regular tape in front of the light, and adjusting the sensitivity control (R3) until the "stop relay" (RY2) closes, and then backing off the control until the relay just opens. Check adjustment by moving the transparent or reflective tape in the path and seeing if the relay closes. The adjustment should be right on the edge of sensitivity, that is, the relay should just barely close when the transparent or reflective coating is in line. It needn't close firmly, just enough to break the circuit to RY1 for an instant. The most sensitive adjustment may mean that RY2 will chatter slightly when the transparent or reflective coating is in line, but it guarantees that random room light will not actuate the circuit.

To further minimize the chance of room light affecting the cell, it is housed well back in a large diameter piece of "spaghetti" which acts as a hood (see Fig. 3). The lamp is also enclosed in an aluminum clip-on hood (bent around a 3/8-in. rod) to concentrate the light.

These hoods and mounting details (using the reflective system) are shown in Fig. 3. Both units must be placed in back of the line of the tape when feeding from a full reel of maximum size, but as close to the tape as possible. The actual location of each unit will depend on the recorder used; it must be determined by trial and error. Mount one of the units (preferably the cell), set the reflective or transparent section of tape in the area, and move the lamp around to the point that gives best results. Then fasten the lamp in place.

Due to the locking feature of RY1, only a

MATERIALS LIST—AUTOMATIC STOP

R1	39 ohms, 1 watt*
R2	250 ohms, 5 watt*
R3	5000 ohm potentiometer
R4	1.5 megohm, 1/2 watt
C1	50 mfd., 150 volt*
SR	65 ma. selenium rectifier*
T1	6.3 volt @ 1 amp. filament transformers*
S1	DPDT toggle switch ("Auto-Manual")#
S2	SPST push button ("Relay Lock")
Ry1	DPST relay with 110-volt coil
Ry2	SPST (normally closed) relay with 5000-ohm coil (Potter & Blumfield LM5 or equivalent)
V1	6AB4
PC	Crystal photocell, Clairex CL-2
PL	6.3 volt (.3 amp.) pilot light

* Not required if power supply is not to be included.
A SPDT switch can be used if power supply is not to be included.

small piece of "trigger tape" (reflective or transparent) need be used. As long as the trigger tape is in the lamp-cell area, the motor cannot be started with S1 on "Auto," since RY2 is closed and RY1 cannot be closed. If the trigger tape stays in the light-cell area after the mechanism has stopped, it must be moved manually out of the light-cell area to start the motor (or S1 can be thrown to "Manual"). After the trigger tape is out of the area, the motor can be started again by pressing the "Relay Lock" button (S2) and using the regular motor starting switch. Whenever the mechanism has stopped automatically, turn the regular motor switch "Off," thus disengaging the mechanism, before restarting the motor.

If a section of trigger tape is placed near the beginning of the reel of tape, the automatic stop feature can be used when re-winding to prevent the tape from coming loose from the take-up reel and to insure starting over at the same point. Due to tape speed of re-winding, the trigger tape should be several inches long for this purpose.

The location of the "Auto-Manual" switch (S1) and the "Relay Lock" button (S2) is not important, but must necessarily be clear of mechanism beneath the panel and clear of the largest size reels to be used.


All under-panel wiring must be carefully routed and fastened in place to prevent fouling any part of the mechanism. Also, adequate shielding must be used to prevent any ac hum from being induced into the heads and to prevent any demagnetization of tape from taking place. For that reason, particularly if a power supply is to be used, the components should be mounted as far from the heads as possible. The

Under-case view of tape recorder showing mounting of control components and wiring of automatic stop (top center).

chassis for mounting parts should be of heavy gage steel for additional shielding.


Figure 5 shows the under-panel view of the circuit used with a recording mechanism, with the power supply included. The placement of parts is not critical, although an effort was made to put the filament transformer as far from the heads as possible. The tube has a shield only to act as a hold-down to prevent it from working loose in the socket. The sensitivity control is locked at the proper setting with a dab of nail polish on shaft and its housing.

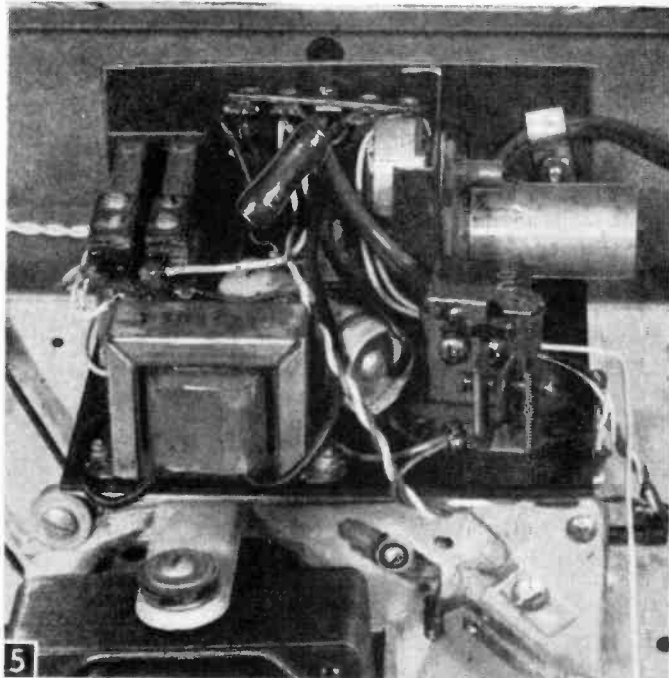So, load her up, set S1 on "Auto," press the "Relay Lock" button momentarily, start the mechanism with the regular switch, and forget it. It will stop automatically wherever you put the trigger tape.



Parts Substitution Block

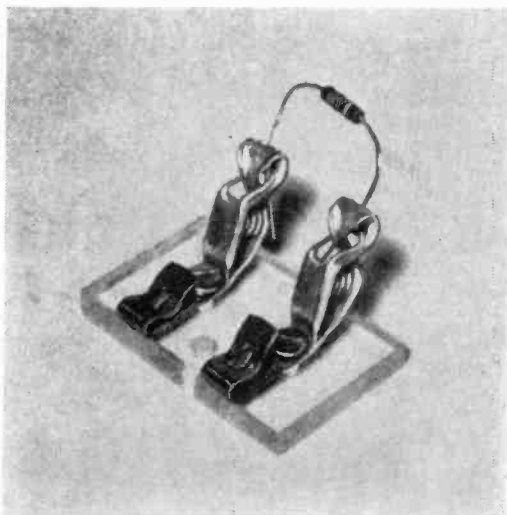
• Experimenters will find this parts substitution block a convenient timesaver when working with experimental circuits. Make the block from two test clips (Muller #45), two single ended Fahnestock clips, and a piece of plastic or other suitable insulator (for the base). Cut off the wire supports at the rear of the test clips, remove the



screws and drill the holes slightly larger. Secure the clips with longer screws to the base as shown. Place the part to be substituted in the jaws of the clips and connect test leads from the circuit to the Fahnestock clips.—JOHN A. COMSTOCK.

Test Clip Strips Wire

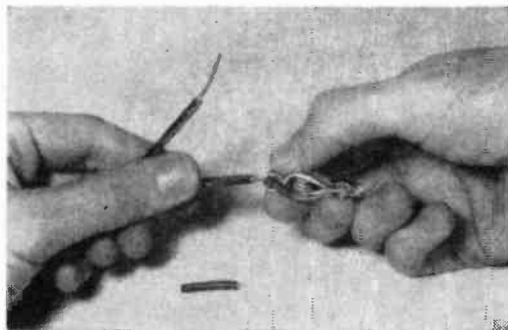• Have you ever tried to strip insulation from stranded wire with a knife or nail clipper only to find several of the wire strands accidentally cut?



Next time you have some wire to strip, place it in the jaws of a test clip, grasp the clip by the outside of the jaws and pull. This will peel off the insulation without appreciably harming the conductors.—JOHN A. COMSTOCK.

ANSWER TO
ELECTRONIC
CROSSWORD
PUZZLE
Page 24

G	H	I	F	I	R	E	D
R	E	O	A				
I	N	E	O	N	D	O	
D	R			I	D		
E	Y	E		P	H	O	N
X	D	T		L	O		
	I	H	A		I		
	S	H	E	A	T	H	S
L	O	R	E		E	P	
	N	C	I		L	P	A



Six-Meter Radiotelephone Station

By C. F. ROCKEY
W9SCH

To quote from a recent issue of a leading national magazine, "Ham' radio makes plenty of sense as a hobby. . . . It's practical; it's a lot of fun and a lot more sociable than you might think; it can be surprisingly inexpensive; it even has a community service side that gives the hobby a solid, worthwhile purpose. . . . On the social side, you get to know fellow hams both in person and over the air—and it's astonishing how airwave friendships last. . . . As for service, you can take part in one of the ham 'nets' that handle communications for the civil authorities in times of emergency or disaster."

If you're a ham already, you know all this. If you're not, the information may prompt you to become a ham. In either case, the six-meter station described in this article would make an ideal set for you. Why? well, for one thing, the six-meter band for which it is engineered is characterized by consistent and reliable communication over a 20- to 30-mile range. For another, the band is remarkably free from interference in most localities. It is, therefore, ideal for low-power operation. And when multi-element, high-gain, directive antenna systems

As an amateur radio "ham" you can join local and national radio clubs (such as the American Radio Relay League headquartered in West Hartford, Conn.) and make a host of airwave friends.

are used, communication ranges of thousands of miles are possible.


It is the consistency and reliability of relatively short-range communication, however, that especially recommends the six-meter band to the more serious amateur. And civil-defense authorities have especially recommended the six-meter band for emergency communication work!

Most commercially-built equipment for this band is expensive; the most widely-known unit sells for over \$200. The set described in this article, however, can be built for only a little more than one-third of this sum, even when new parts are used. If you use second-hand parts, the cost will be greatly reduced even over this.

The transmitter section of this amateur radiotelephone station is crystal-controlled. With crystal control, it is virtually impossible to emit an illegal off-frequency signal. The receiver section combines the sensitivity and reliability of the superheterodyne circuit with the simplicity and inexpensiveness of the super-regenerative. It is easy to "get-going," free from radiation, and sensitive enough to receive from any distance that the transmitter can reach.

No "overtone oscillators" or other trick circuits are used in this unit; all tubes are ordinary types, available everywhere. We feel that this unit will provide the absolute per-dollar maximum in Very High Frequency communication for the low-power or Technician class amateur.

Begin construction by cutting the large opening for the power transformer in the 4 x 10 x 17-in. chassis (Fig. 2). Exact dimensions for this opening are best obtained by measurement directly from the transformer you will use. Such openings are usually cut by drilling a series of closely spaced 1/8-in. holes along the outline and breaking away the strips of metal left between these holes with a screwdriver. After making the cut-out for the power transformer, cut the

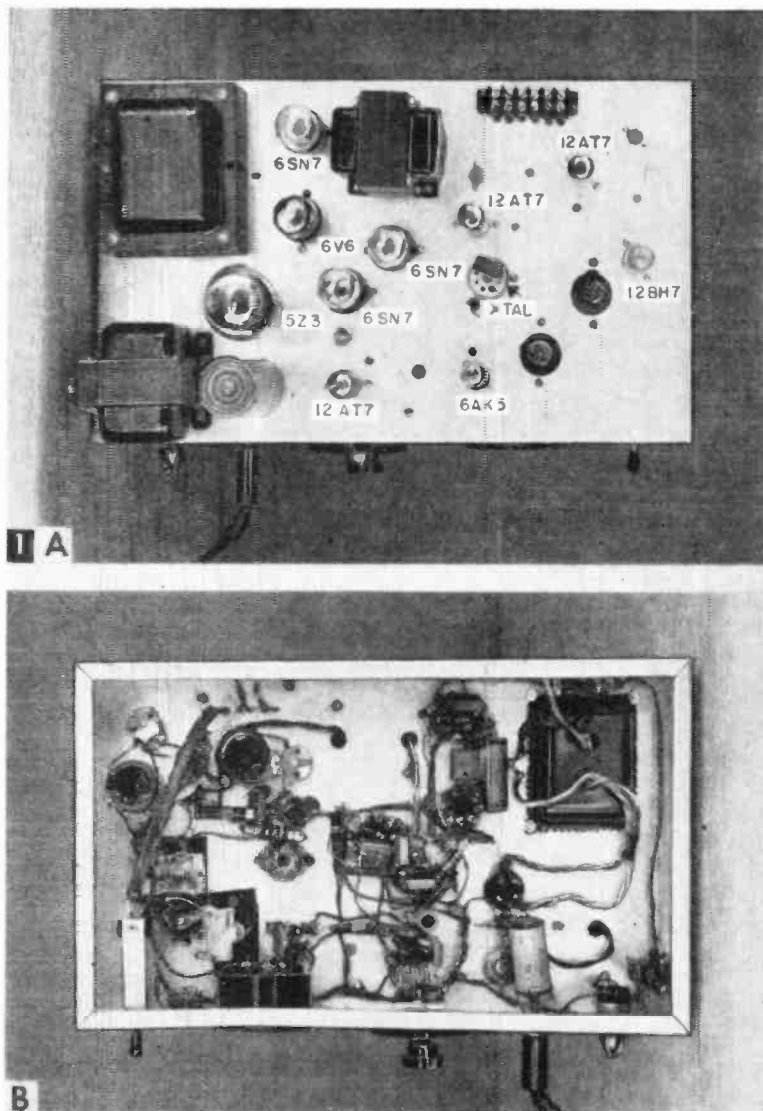

Top (A) and bottom (B) views of the completed six-meter station.

large, round opening for the tuning meter by transferring the hole dimensions from the manufacturer's template (usually supplied in carton with the milliammeter) and drilling $\frac{1}{8}$ -in. holes and breaking away with a screwdriver as with the transformer opening. Punch the tube socket holes with Greenlee or other make chassis punches, and drill and cut away opening for the Send-Receive switch, following the template supplied by the manufacturer.

With large holes cut, drill small holes, using each socket or small part as its own template. Mount the power transformer, the filter choke, the can-type electrolytic capacitor, the combination volume control and Off-On switch, the 5Z3 rectifier tube socket and other tube sockets (large sockets with $6\text{-}32 \times \frac{3}{8}$ -in. rh machine

screws, small with $4\text{-}35 \times \frac{1}{4}$ -in.), the terminal strip, and the Send-Receive switch on the chassis.

Wiring for the power supply is shown in the schematic, Fig. 3. (Figure 5 gives a pictorial wiring diagram for the power supply, receiver section, and transmitter section.) Most of the wiring for the entire unit can be done with #20 plastic-insulated hookup wire; connections should be soldered with rosin-core solder.

Wire placement in the power supply is not critical; leads may be as long as necessary. The 20 mfd electrolytic capacitor and other, similar, small parts are mounted by their leads, using insulated tie-points screwed to the chassis at convenient locations. Be sure to observe polarity when connecting electrolytic capacitors, since they would be permanently damaged by wrong connections. (Other types of capacitors are not critical as to polarity of connection.) All grounds in unit are made to chassis.

When the power supply wiring has been completed, check it carefully. With the 5Z3 rectifier tube in its socket and operating, the power

supply should deliver from 350 to 500 volts dc measured across the 20 mfd output filter capacitor with a radio service-type dc voltmeter. When full transmitter load is applied, the voltage will drop to the correct operating value of about 350 volts.

Begin receiver wiring by first connecting heater circuits of all tubes (see Fig. 4). One side of each tube's heater is connected to a common heater supply wire which is then connected to point "H" in the power supply (Fig. 3). The other side goes to ground. Insert receiver tubes in sockets (do not insert the 5Z3 rectifier) and apply power. If wiring is correct, all heaters will light.



With heater circuit checked, wire the audio amplifier circuits of the receiver. Mount the

phone jack on the front of the chassis and work forward from the last stage of audio amplification. Mount mica capacitors and resistors by their leads, using insulated tie-points as necessary. When you have wired the last amplifier stage, insert the audio amplifier 6SN7 GTB into its socket and plug headphones into jack. With power supplied and Send-Receive switch in "Receive" position, touching pin #4 grid terminal of the tube with the tip of a screwdriver should produce a noticeable click or buzz in the headphones. If this, or any other stage does not operate, the difficulty is incorrect wiring, a solder-spot short, or a defective component or tube.

Wire the next stage of audio amplification and test similarly. A screwdriver on pin #1 grid of the 6SN7 GTB should now produce a very much stronger buzz in the headphones.

The first connections for the second-detector stage are to the volume control potentiometer, with its associated 100 K ohm (100,000 ohms) resistor and 5 mfd bypass capacitor. The second detector coil is wound on a National XR-50 variable-slug coil form as shown in Fig. 6E. The position of the cathode-tap on this coil is particularly critical. Make sure that it is closest to the grounded end of the coil.

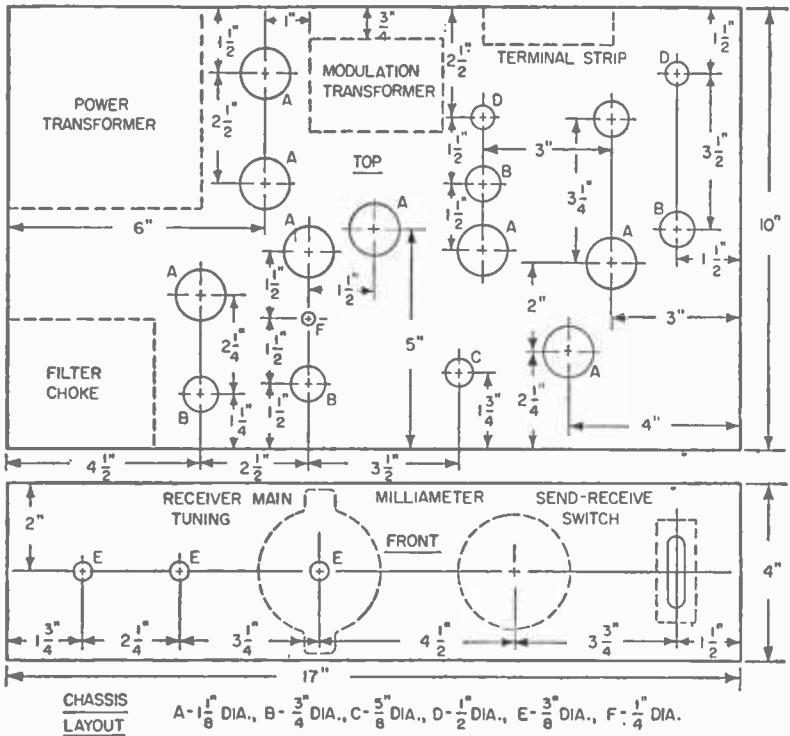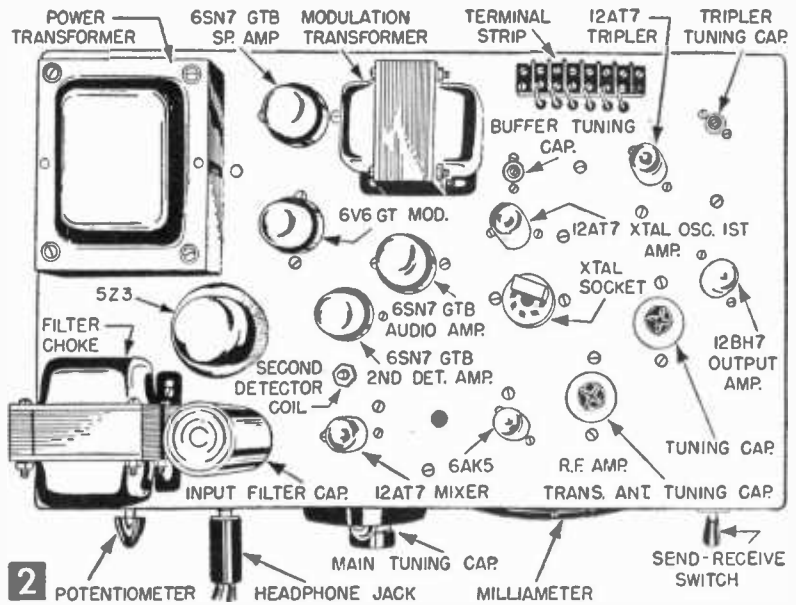Fasten turns in place by coating with polystyrene cement. Since the second detector is the heart of the receiver, check and recheck its wiring, then insert tubes and plug in phones and apply power with Send-Receive switch in "Receive" position. When the tubes have warmed, gradually advance the volume control clockwise. A loud, clean hiss



should be heard in the phones and it should be possible to control the strength of this hiss from inaudible to very strong with the volume control.

When wiring the R. F. amplifier and oscillator-mixer circuits, keep leads as short as possible. Although zero-length leads are not as essential in a 50-megacycle unit as they would be in higher-frequency units, short lead-length will pay

dividends in operating effectiveness. It is also good construction technique in any VHF circuit to establish a single ground point for each tube, and bring all high-frequency grounds to that point.


And, when wiring circuits using miniature tubes, it is important to avoid excess solder on the tube socket connections. Use a hot iron and do a quick but thorough job on each connection.

Keeping these construction principles in mind, wire the R.F. amplifier, mixer and oscillator circuits as shown in Fig. 4. The grid (A and B) and plate (C) coils for the R.F. amplifier are each wound on high-resistance 1-watt carbon resistors (see Fig. 6A, B and C). Any 1-watt carbon resistor larger than 100 K ohms will do.


Where possible, solder the coil connections directly to the resistor leads.

The oscillator coil (D) is formed by winding 9 turns of #14 tinned copper wire around a 1/2-in. diameter drill shank. Remove drill and mount coil by soldering its ends directly to the receiver tuning capacitor terminals. This coil should have

3 POWER SUPPLY SCHEMATIC

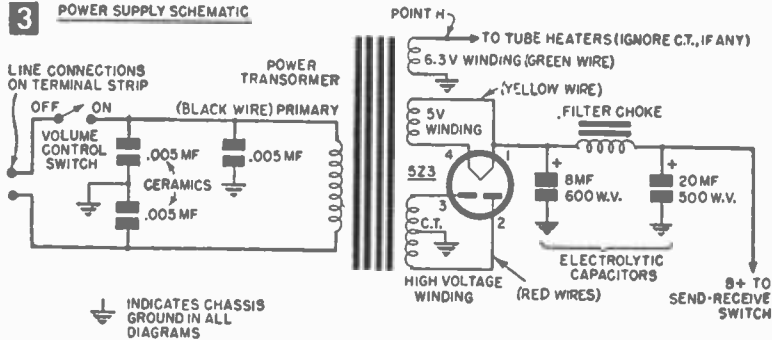


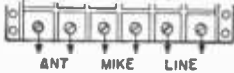TOP VIEW OF TERMINAL STRIP SHOWING CONNECTIONS AS VIEWED FROM BACK OF CHASSIS



4

RECEIVER SCHEMATIC

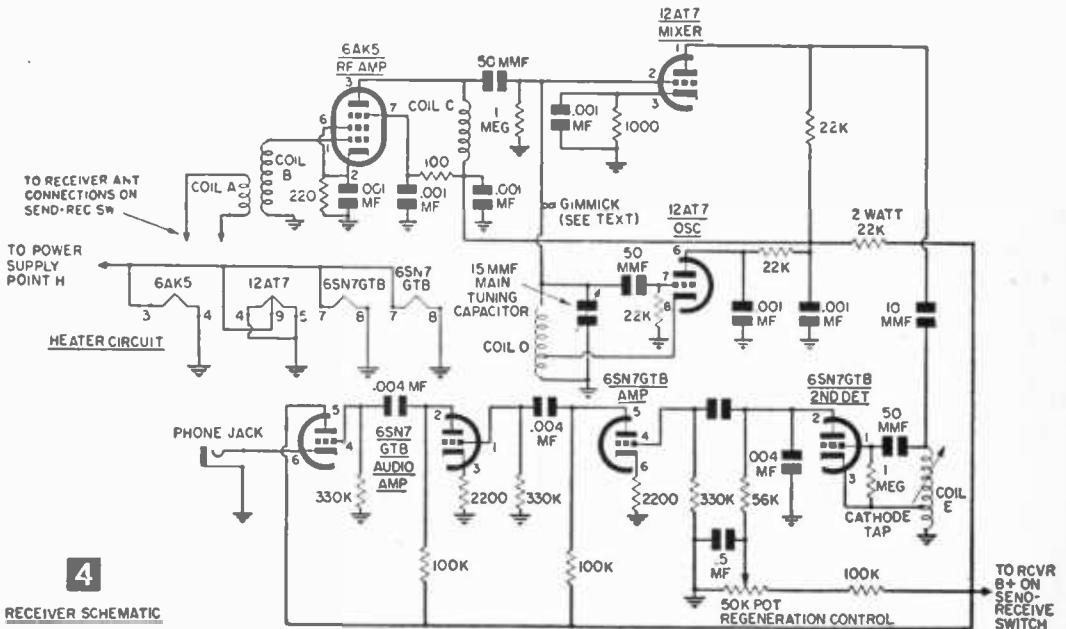

Enjoy Thrilling High Fidelity **Super Hi-Fi FM Record Player**

Build this high-fidelity, frequency modulated phono oscillator and bring your wax-works to life, enjoy all the sound you pay for from your recordings. Full-size pictorial and schematic wiring diagrams, complete materials list, illustrated step-by-step assembling instructions. Order Craft Print No. 264 now. Price, \$1.00



SCIENCE AND MECHANICS, 450 East Ohio St., Dept. 5551, Chicago 11, Ill.

its turns uniformly spaced so that the total length of the coil is about 1 1/4 inches. The ground end of this coil is the end which connects to the capacitor rotor plate terminal. The cathode tap should be two full turns from the ground end.

The circuit component labelled "Gimmick" in Fig. 4 capacitively couples signal energy from the 12AT7 oscillator section into the mixer section. It consists of two pieces of ordinary hookup


wire (insulation left on) twisted together 5 times.


To adjust the coils for proper resonant frequency, a grid-dip meter will be needed. Usually, such a meter can be borrowed from another ham. Instructions for its use are supplied by the manufacturer.

With power Off, plug tubes into their respective sockets and adjust the slug in the second-detector coil (coil E) until the grid-dip meter indicates

NOTE: .001 = 1000MMF CERAMIC
50 = 50MMF CERAMIC

POTENTIOMETER AND SWITCH

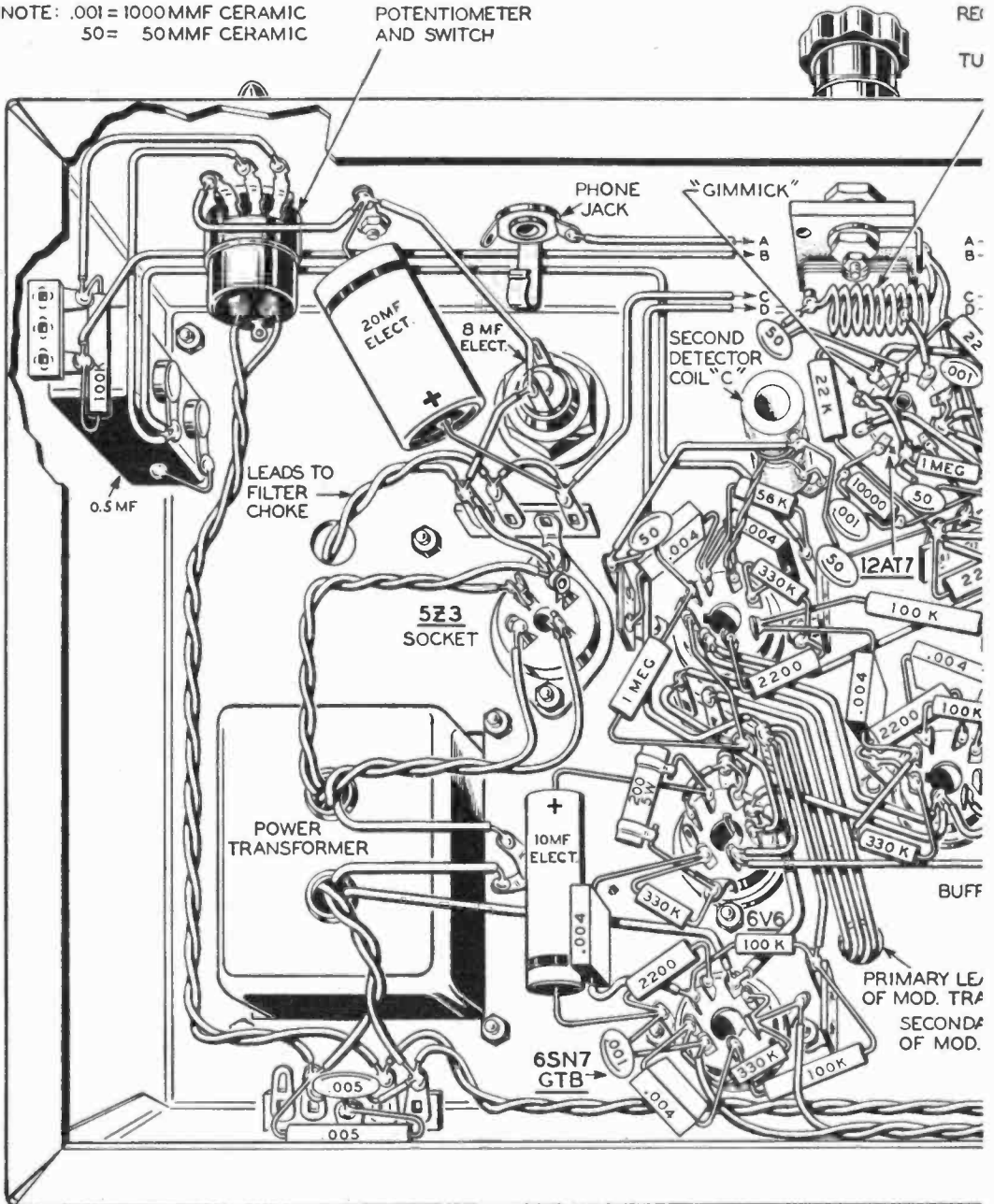

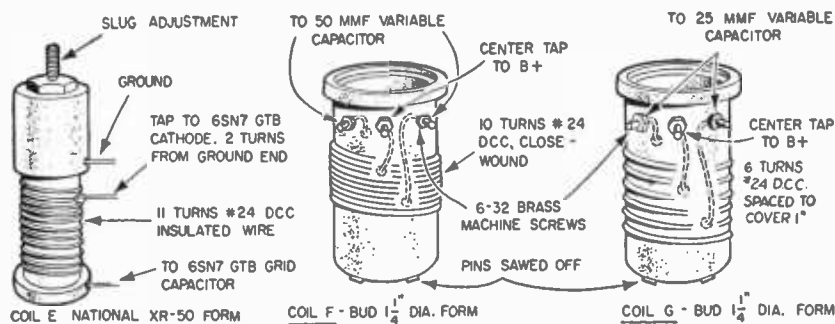

COILS

(TO WIND COIL D, SEE TEXT. COIL E IS ADJUSTED TO CORRECT VALUE BY ADJUSTING SLUG POSITION; OTHER COILS MAY HAVE TO BE INDIVIDUALLY "PRUNED," AFTER INSTALLATION, FOR BEST RESULTS)

6

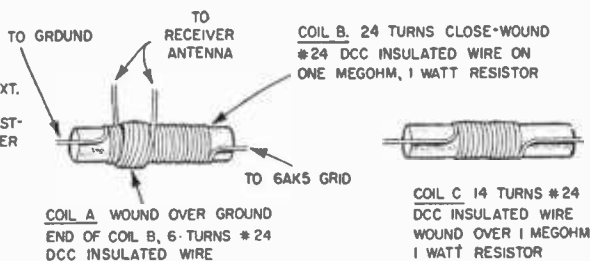


TABLE A—RESONANT FREQUENCIES

Coil	Tuning Capacitor	Resonant Frequency, MC approximate (8.33 MC XTAL)
A	none	not significant (antenna coil)
B	tube-circuit capacitance	51 MC
C	tube-circuit capacitance	51 MC
D	tuned by main receiver tuning capacitor, 15 mmf	tuning range must include 80 to 84 MC (for 30 MC I.F.) may be wider without harm
E	tube-circuit capacitance	adjust slug for resonance at 30 MC
F	50 mmf max.	8.33 MC
G	15 mmf	25 MC
H	15 mmf	50 MC
I & J	none	not significant (coupling links)
K	50 mmf	50 MC

With coils adjusted, plug in headphones and apply power. Connect a simple VHF antenna such as that used with TV receivers, or that shown in Fig. 12, to the receiver input, or to the antenna terminals of the terminal strip, and throw the Send-Receive switch to the "Receive" position. Adjust the volume control until you hear a slight hiss in the phones and if there are 50-megacycle amateurs operating in your vicinity you should be able to tune them in. As a signal is tuned in, the hiss will tend to disappear and the voice will ride in strongly above it. A slight readjustment of the regeneration control will clarify and strengthen weaker signals.

Building the Transmitter. First of all, do not build this or any other transmitter unless you have a General or Technician class amateur license from the FCC. (See *Do You Need A License?*, bottom of page 107, for further information on this subject.)

Begin construction of the transmitter section by making heater circuit connections (see Fig. 8). Next, wire the crystal oscillator circuit, using


an octal (8-pin) tube socket for the crystal socket. You may use any two alternate pins for the crystal connections. (We used pins 1 and 3). The crystal oscillator circuit is the simple and reliable Pierce type and will oscillate with any 8-megacycle crystal. (None of the other circuit component values are critical, either). Any modern crystal having a fundamental frequency between 8.334 megacycles and 9.000 megacycles will enable you to operate in

the six-meter band, but since most amateurs prefer to operate below 52 megacycles, the highest preferred crystal frequency will be 8.666 megacycles. Be sure that as you wire the transmitter you obtain B+ for all stages at the proper terminal of the Send-Receive switch (see Fig. 7).

When wiring for the oscillator stage is completed and has been checked, apply power with 12AT7 and crystal plugged in and Send-Receive switch in "Send" position. Now, holding a 2-watt neon lamp bulb by its glass envelope, touch the base of the bulb to pin #1 of the 12AT7 oscillator section. A bluish-pink glow in the bulb indicates proper oscillation.

Next, disconnect power and wire the buffer amplifier stage of the transmitter. Coil F (see Fig. 6F) is wound on a Bud 1/4-in. dia. plug-in coil form. It consists of 10 closely-wound turns of #24 double cotton-covered, center-tapped. Three 6-32 brass screws of about 1/4 in. dia. can be used as coil terminals. Saw the pins of the coil form off flush with the bottom of the form, and mount it on the chassis with a 6-32 machine screw up through the bottom. When mounting the 50 mmf tuning capacitor, drill a hole in the chassis large enough to give ample shaft clearance, since you must insulate both rotary and stationary plates from the chassis. Mount capacitor with 4-40 x 1/4-in. rh machine screws.

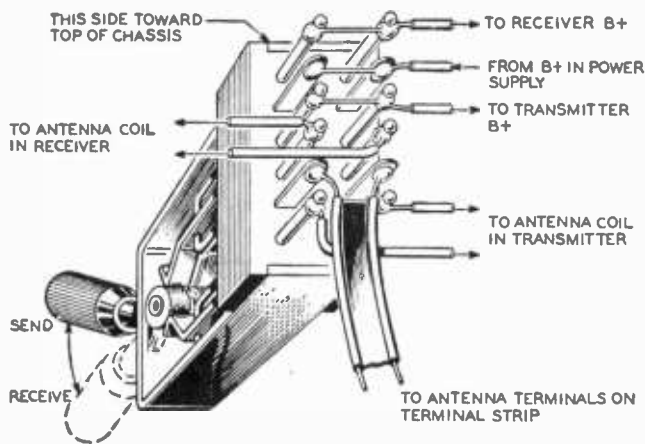When wiring of this stage is completed, apply power as before and check for output. Coil F should tune to the correct frequency with the 50 mmf capacitor nearly completely meshed. Check



7 SEND-RECEIVE SWITCH (END VIEW)

for this by inserting the tuning lamp and loop shown in Fig. 9 into the coil; sufficient energy should be present to light the lamp dimly but definitely. *Remember*—the shafts of the tuning capacitors in the plate circuits of the transmitter tubes have 350 volts of B+ on them when the transmitter is On. Do not touch these shafts. The buffer's output should be on 8 megacycles.

With the buffer amplifier completed, disconnect power and proceed to the construction of the push-pull 12AT7 tripler stage. Mount the 25 *mmf* variable capacitor in the same manner as the 50 *mmf* capacitor for the buffer stage was mounted. Wind coil G as shown in Fig. 6G and mount it as you did coil F.

When the tripler stage is completely wired, insert tubes and crystal and apply power. Using the grid-dip meter, retune the first amplifier to the crystal frequency to compensate for the added grid capacitance of the tripler. Then set the grid-dip meter to 25 megacycles and adjust the 25 *mmf* tripler tuning capacitor for maximum output as indicated by a brightly glowing tuning lamp when loop is inserted into coil G. Avoid accidental contact with the coil or the tuning capacitors.

When the tripler stage is functioning properly, disconnect power, and wire the doubler final amplifier. The grid circuit of this amplifier is identical with that of a push-pull stage, but the plates of the two triode elements are in parallel. This circuit arrangement, called "push-push" amplification, provides strong, efficient output on twice the frequency of the input, while strongly suppressing output on other frequencies. It is an ideal circuit for applications of this nature and provides good output on 50 megacycles.

Punch a 1½-in. socket hole in the chassis for the 15 *mmf* tuning capacitor and make an insulating strip as shown in Fig. 11. Mount it under the 1½-in. hole with 6-32 x ¼-in. rh machine screws. Coil H consists of 10 turns of #14 tinned copper wire wound on a ½-in. drill shank. Space the turns uniformly until the winding is about

1¼-in. long, remove drill and solder the ends of this coil directly to the 15 *mmf* tuning capacitor.

An important temporary change in the wiring of the final amplifier stage is made at point P (see Fig. 8). When transmitter is completed, the lead to the left of this point will go through the modulation transformer secondary to B+. Since the modulation transformer is not yet installed, however, a length of hookup wire should be temporarily connected from point P to a transmitter B+ terminal of the Send-Receive switch so that you can conveniently test this stage.

To test the push-push final amplifier stage, insert tubes and crystal, apply power and throw Send-Receive switch to "Send." With the grid-dip meter set to 50 megacycles, couple


it to the final tank coil and adjust the 15 *mmf* tank capacitor for maximum output as indicated by the tuning lamp. A slight readjustment of the tripler tuning capacitor will also increase the 50 megacycle output. When the tuning-lamp loop is brought near the push-push amplifier tank coil it should glow very brightly—perhaps even burn out. For a further check, you can connect a similar tuning loop to a standard 15 v. series-string Christmas-tree lamp. With the loop inserted in the final tank coil and everything tuned on-the-nose, the Christmas-tree lamp should glow brilliantly.

If R.F. power output of the strength indicated is not obtained, first recheck the tuning of the buffer amplifier and tripler, using a completely insulated alignment screwdriver to avoid introducing hand capacity. Also make sure that the tuning-lamp loop is pushed completely into the coil, and the final tuning capacitor is precisely set for maximum possible output. If output is still low, measure the B+ dc supply voltage with a radio-TV service type voltmeter. This supply voltage should be between 350 and 400 v. for maximum power output. Finally, make sure that all the tubes you are using are in top shape.

When the final amplifier gives satisfactory output, punch a 1½-in. hole in the chassis for the antenna tuning capacitor, and make and mount a second plastic insulating strip (Fig. 11). Then fasten the 50 *mmf* antenna tuning capacitor securely to the insulating strip.

The antenna coil (Coil K) is wound with #14 tinned copper wire in the same manner as was the final tank coil. It consists of 7 turns on a ½-in. dia. form (drill shank) spaced to roughly 1 in. It is soldered directly to the terminals of the 50 *mmf* antenna tuning capacitor. The "twin-lead" from coil K to the Send-Receive switch is tapped-off two turns from the end of the coil.

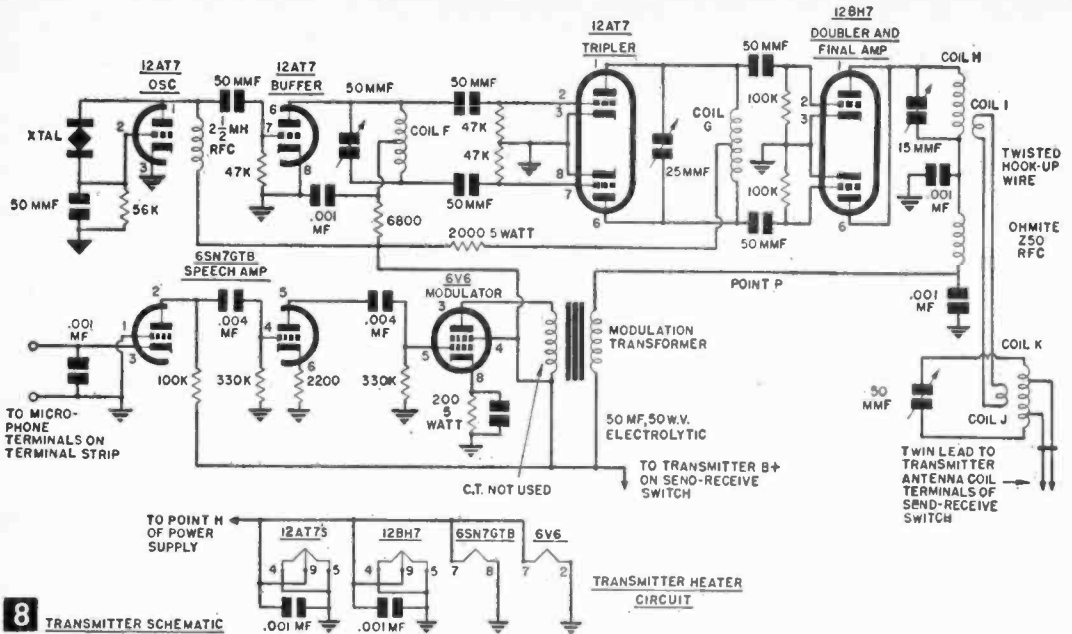
The antenna coil is coupled to the tank coil by means of a twisted hookup wire link. A one-turn loop inserted all the way into the tank coil at the B+ end couples the tank to the link. At the other



8 TRANSMITTER SCHEMATIC

end, a one-turn loop pushed between the center turns of the antenna coil transfers the power. Make sure the insulation on these coupling loops is in good condition, the link is continuous, and the loops are pushed tightly into the respective coils. When the loops are in position fasten them there with polystyrene cement.


The Ohmite R.F. choke, 1N34 crystal diode, and the bypass capacitor of the R.F. tuning meter (Fig. 10) can all be neatly fastened by their leads to a two-lug insulated tie-point. The pickup wire for this meter is a length of hookup wire brought near the antenna tuning coil. RFC1 is an Ohmite Z-50 R.F. choke. A twisted pair of hookup wires run to the 0-1 milliammeter terminals. Mount this meter in the hole on the front of the chassis and connect to read up-scale when the transmitter is energized. (If it reads backwards, reverse its leads.)

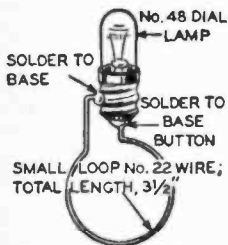


9 TRANSMITTER TUNING LAMP

With the radio-frequency portion of the transmitter completed, wire the speech amplifier and modulator stages. To test these stages, use a loudspeaker output transformer, speaker connected, temporarily wired in place of the still uninstalled modulation transformer. With tubes in place and microphone connected at the back of chassis terminal strip, the system should function as a good low-power PA system when the Send-Receive switch is thrown to "Send."

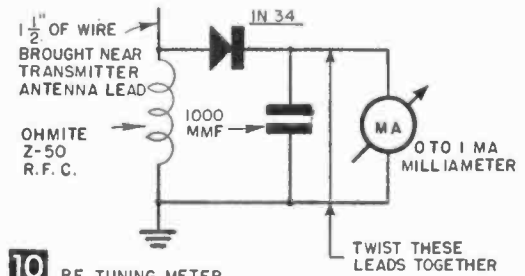
After testing, remove the loudspeaker transformer and the temporary connection from point P to B+ and install and connect the modulation



10 RF TUNING METER

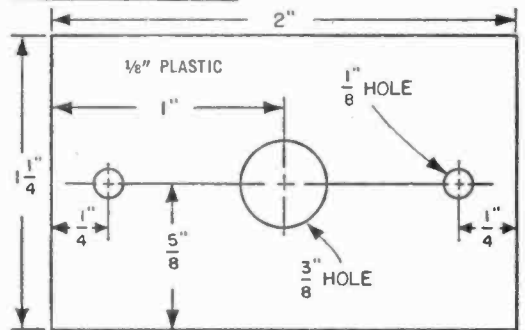

11 INSULATING STRIPS (MAKE TWO)

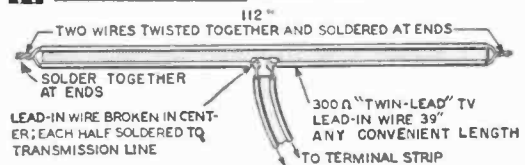

- 12** RULES FOR ERECTING ANTENNA
- (1) KEEP IT HORIZONTAL.
 - (2) KEEP IT BROADSIDE TO THE DIRECTIONS YOU WISH MOST TO WORK.
 - (3) ERECT IT AS HIGH ABOVE GROUND AS POSSIBLE.

MATERIALS LIST—SIX-METER RADIOTELEPHONE STATION

Req'd.	General	Transmitter
1	Bud aluminum chassis 4 x 10 x 17"	3 9-prong, high-frequency plastic sockets, Amphenol ("miniature")
1	Federal type 1424 4PDT anti-capacity switch	3 8-prong sockets, Amphenol "MIP"
1	6-terminal Jones barrier terminal strip	1 Hammarlund 15 mmf type HF-15 variable capacitor
1	line cord and plug	1 Bud 50 mmf type MC variable capacitor
3	1/4"-shaft knobs	1 25 mmf Hammarlund "APC-25" variable capacitor
	assorted screws, nuts, wire, solder, insulated tie-points.	1 50 mmf Hammarlund "APC-25" variable capacitor
	1/8" plastic sheet	2 Bud 1 1/4" dia. plug-in coil forms
	Power Supply	1 National R-100 R.F. choke coil, 2 1/2 millihenries
1	power transformer, Thordarson No. 22R07	1 Ohmite Z-50 R.F. choke
1	filter choke, Thordarson #20C55	1 modulation transformer, Thordarson type 21M54
1	8 mfd filter capacitor, Cornell-Dubilier #608C	1 James-Knights type H73 crystal or equivalent (see text)
1	20 mfd 500 w.v. filter capacitor, Sprague "Atom"	2 .004 mfd postage-stamp mica capacitors
1	four prong socket, Amphenol "MIP"	1 10 mfd, 50 volt electrolytic capacitor
1	.01 mfd 400 w.v. paper capacitor	7 .001 mfd disc ceramic capacitors
2	.005 mfd ceramic capacitors	6 50 mmf disc ceramic capacitors
1	5Z3 rectifier tube	3 47K (47,000 ohms) 1/2 watt, carbon resistors
	Receiver	2 100K (100,000 ohms) 1 watt, carbon resistors
1	National type BM vernier dial	2 100K (100,000 ohms) 1/2 watt, carbon resistors
1	single-circuit phone jack	2 330K (330,000 ohms) 1 watt, carbon resistors
1	100K (100,000 ohms) linear-taper potentiometer, with Off-On switch	1 2200 ohm, 1 watt carbon resistor
2	8-prong sockets, Amphenol "MIP"	1 6800 ohm, 1 watt, carbon resistor
1	9-prong, high-frequency plastic socket, Amphenol ("miniature")	1 200 ohm, 5 watt, wire-wound resistor
1	7-prong, high-frequency plastic socket, Amphenol ("miniature")	1 2000 ohm, 5 watt, wire-wound resistor
1	15 mmf variable capacitor, Hammarlund HF-15	Tuning Meter
1	0.5 mf, 600 w.v. Aerovox "bathtub" capacitor	1 Ohmite Z-50 R.F. choke
1	National type XR-50 coil form	1 .001 mf ceramic disc capacitor
3	1 megohm (1,000,000 ohms) 1 watt, carbon resistors	1 IN34 crystal diode
1	1 megohm, 1/2 watt, carbon resistor	1 0-to-1 ma D.C. milliammeter Triplett model 321
1	220 ohm, 1/2 watt, carbon resistor	Tubes for receiver and transmitter
1	100 ohm, 1/2 watt, carbon resistor	3 6SN7GTB
3	22K, (22,000 ohms) 1 watt, carbon resistors	1 6V6GT
1	22K, (22,000 ohms) 2 watt, carbon resistor	3 12A17
1	56K, (56,000 ohms) 1 watt, carbon resistor	1 6AK5
3	100K, (100,000 ohms) 1 watt, carbon resistors	1 12BH7
3	330K, (330,000 ohms) 1 watt, carbon resistors	External Equipment
1	1000 ohm, 1/2 watt, carbon resistor	1 single-button, telephone-type carbon microphone
1	2200 ohm, 1 watt, carbon resistor	1 pair 2000 ohm headphones, magnetic
4	.004 mfd postage-stamp mica capacitors	several No. 48 dial lamp bulbs, one 2-watt neon lamp bulb,
6	.001 mfd, disc, ceramic capacitors	15 v. "series" Christmas lamp bulb
3	50 mmf, disc, ceramic capacitors	1 headphone plug, single circuit
1	10 mmf, disc, ceramic capacitors	1 roll "twin-lead" TV lead-in, 300 ohm, and other antenna supplies as necessary

transformer. As a final test, connect the Christmas-tree lamp to the antenna terminals on the terminal strip and with tubes and crystal in place energize and throw Send-Receive switch to "Send" position. Adjust all transmitter controls for maximum light emission from the Christmas-tree lamp. Speaking into the microphone should cause the lamp to fluctuate noticeably in brilliance and the tuning-meter needle to flutter (indicating sufficient modulation.)

The last step in construction of this amateur radiotelephone station is to make and connect a dipole antenna as shown in Fig. 12. With antenna connected, tune the transmitter for maximum indication on the tuning meter (with the pickup wire set for half-scale meter reading) and you're ready to communicate.

The transmitter has been designed to avoid interfering with the operation of properly in-

stalled TV receivers. Any six-meter transmitter—including expensive commercially built models—can occasionally cause interference in nearby TV sets, however. Such interference can be eliminated if the TV set owner will install a Drake No. TV-300-HP high-pass filter on his set. (This unit is designed to suppress 50 MC feed-through).

Such interference as may be caused by ham equipment is not the fault of the ham transmitter but is an inherent property of wide-band TV apparatus. A filter, such as the Drake high-pass, will stop the interference. If a set owner will not install such a filter, or wishes to become obstreperous, invite him to write to the Federal Communications Commission. They will deal fairly with the case. To date, no licensed amateur who cooperates with the Commission has lost his operating privileges because his equipment is suspected of being the source of TV interference.

Do You Need a License?

Yes! Although anyone may use the receiver section of this station, the transmitter cannot be used without an amateur's license issued by the Federal Communications Commission. Failure to obtain a valid license from the FCC exposes the offender to a penalty of \$10,000 and/or two years' imprisonment.

The Technician class of amateur operator license is available to any U.S. citizen who can pass a five words per minute code test and a simple examination in radio theory and law. (Write to your nearest FCC office for complete details on this examination.)

The Technician class license, unlike that for the Novice class, is renewable by application every five years if you have been operating actively during that time. However, like that for the Novice class, it does carry limited privileges as to the frequency bands you may use.

Ultra-Small Wrist Radio

By HOMER L. DAVIDSON

ONLY three-quarters of an inch high by $1\frac{1}{2}$ inches square, this receiver can be worn on the wrist and has plenty of volume, even on weak stations. To get a satisfactorily performing set down to such a small size, a printed circuit is used not only as a functional part of the wiring, but also an On-Off switch.

The circuit (Fig. 2) is simple and standard. A short, flexible length of wire with a small alligator clip attached to its loose end (clip to a bed spring, a metal window frame, a screen, etc.) brings the signal to the antenna coil—a small, ferrite type modified by removing its metal mounting clip and cutting the cardboard form with a razor blade back as close as possible to the coil winding itself while still permitting replacement of the clip by bending its terminals down close to the form and slipping it back on. The clip mounts the screw by means of which the powdered iron slug core is turned in and out of the coil. Cut the form back at the opposite end of the coil close to the windings also (to enable the coil assembly to fit the case) and turn the core all the way in, mark the length which extends from the form (about $\frac{1}{4}$ -in.), unscrew the core from the coil and with a power grinder, grind it off to length. If you don't have a power grinder, an ordinary file will also do the trick.

A small fixed capacitor (C1), together with the ferrite-type coil, tunes the entire broadcast band. The first transistor (TR1) acts as a rectifier (detector) and also as the first amplifier stage, while C2 capacity couples the two stages of amplification, and a second CK722 transistor feeds the signal into a small magnetic earphone. Output is amazingly strong on local stations. On one of our locals, the phone can be laid down and the station can still be heard. Batteries are the size of small buttons. They were purchased at a Sonotone hearing aid store for 30¢ each.


Printed Circuit Assembly. Figure 3 shows the four small pieces that go to make up the PC assembly. Piece A is nothing more than a $1\frac{1}{2}$ -in. square of clear plastic $\frac{1}{8}$ in. thick. Piece B is another piece of the same with two $\frac{3}{16}$ in. holes and a $\frac{1}{8}$ -in. hole drilled into it as shown. (The hearing-aid, button-size batteries locate in the $\frac{3}{16}$ -in. holes; the $\frac{1}{8}$ -in. hole is for the bolt that goes to switch SW1, piece D). Views C-1 and C-2 are top and bottom of the actual printed circuit







Super small (the toy watch placed on top of its case gives you the scale), this wrist radio provides a terrific amount of volume.

board, copper-clad both sides. View C-1 is the top side, the numbers on it key to those in the pictorial diagram, Fig. 5. Number 2, for instance, ties the collector side of TR1 to the small coupling capacitor C2. Number 3 is the point to which the metal clip lug of the tuning coil is soldered; it is actually the grounded side of the circuit.

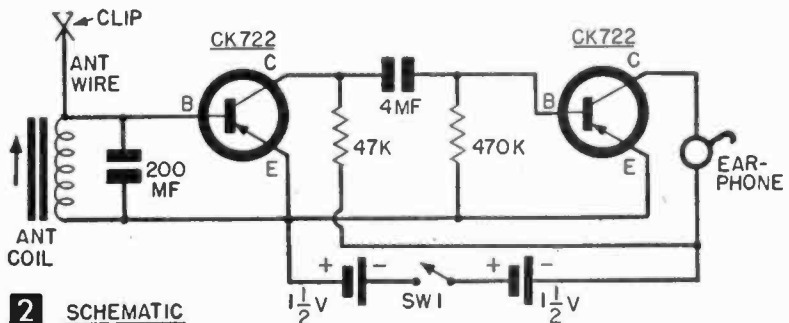On the bottom side of the printed board, view C-2, numbers 6 and 7 are the battery rests. Number 7 is the positive side of one battery; number 6, the negative side of the other. Insert a wire in the small hole indicated in number 7, it will come through the hole in the middle of number



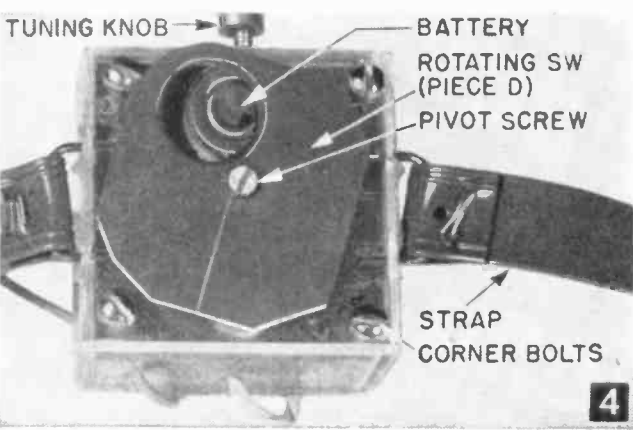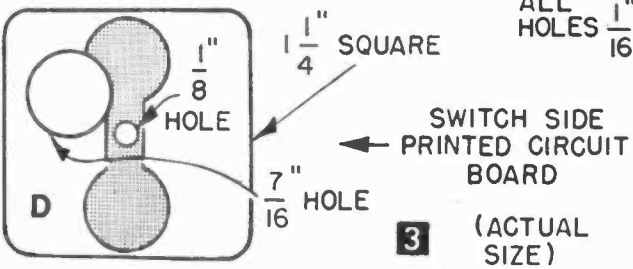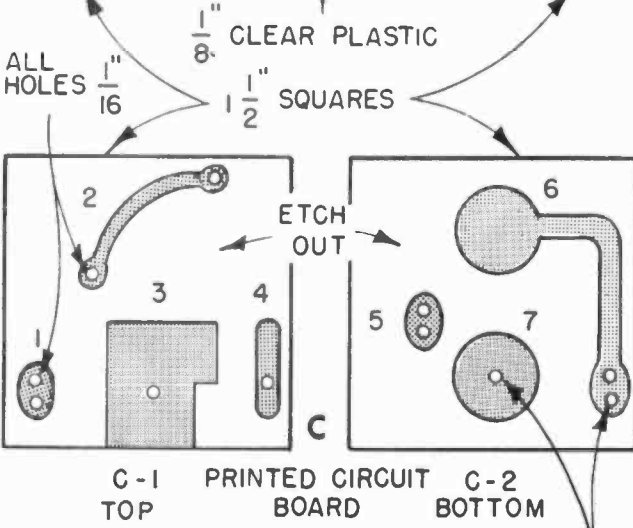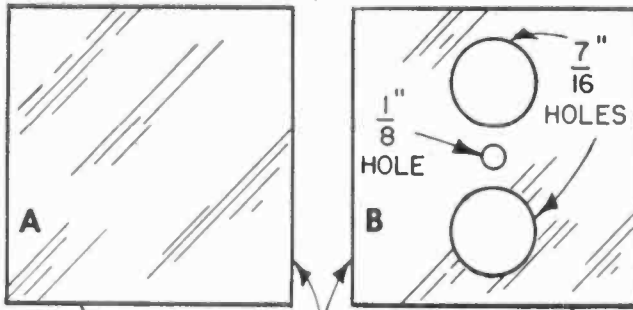

3, and solder both ends to the copper strips.

The switch board, piece D, is a single-side printed circuit board, smaller than the others since it must turn without hitting the small bolts that secure the assembly. When turned to the On position, it shorts against a battery terminal. (Drill a 7/16-in. hole through piece D so that the batteries can be inserted and removed.)


First cut out, sand and drill pieces A and B. Then print circuit pieces C-1 and C-2 and D. To print, trace with carbon paper directly from Fig. 3, onto the printed circuit boards (see Materials List). I used a ball-point liquid resist pen (see Materials List) to draw the circuits. Simply push down on the ball of the pen and the liquid resist will flow. Stay inside the traced lines of the circuit. (For a detailed discussion of PC techniques, see "Printed Circuit Phono Amplifier," page 21.)

After the circuit has been drawn on the copper clad laminate and is dry, place pieces in etch solution. Turn piece C-1 and C-2 over so that both sides are etched evenly. Rock or agitate the solution so that the pieces move, thus quickening the etching process. To check the etching process, lift the boards from the solution with a pencil. A clear brown color indicates that all of the copper has been etched away.

Wash the etched board in running water (and pour the remaining etch solution back into its container; it can be used again), and remove the resist paint with the sharp point of a pocket knife. Now, drill all the holes indicated in Fig. 3. The small holes indicated in the printed circuitry should be about 1/16 in., no larger than necessary to pass conventional wiring.

Fasten pieces B and D together with a small bolt and nut. Counter-sink the head of the bolt into the plastic of piece B. The nut should be turned tightly enough to secure piece D firmly, then solder it to the bolt. (The printed side of piece D faces piece B). Mount and solder all parts including transistors into place on piece C-1. Align pieces as

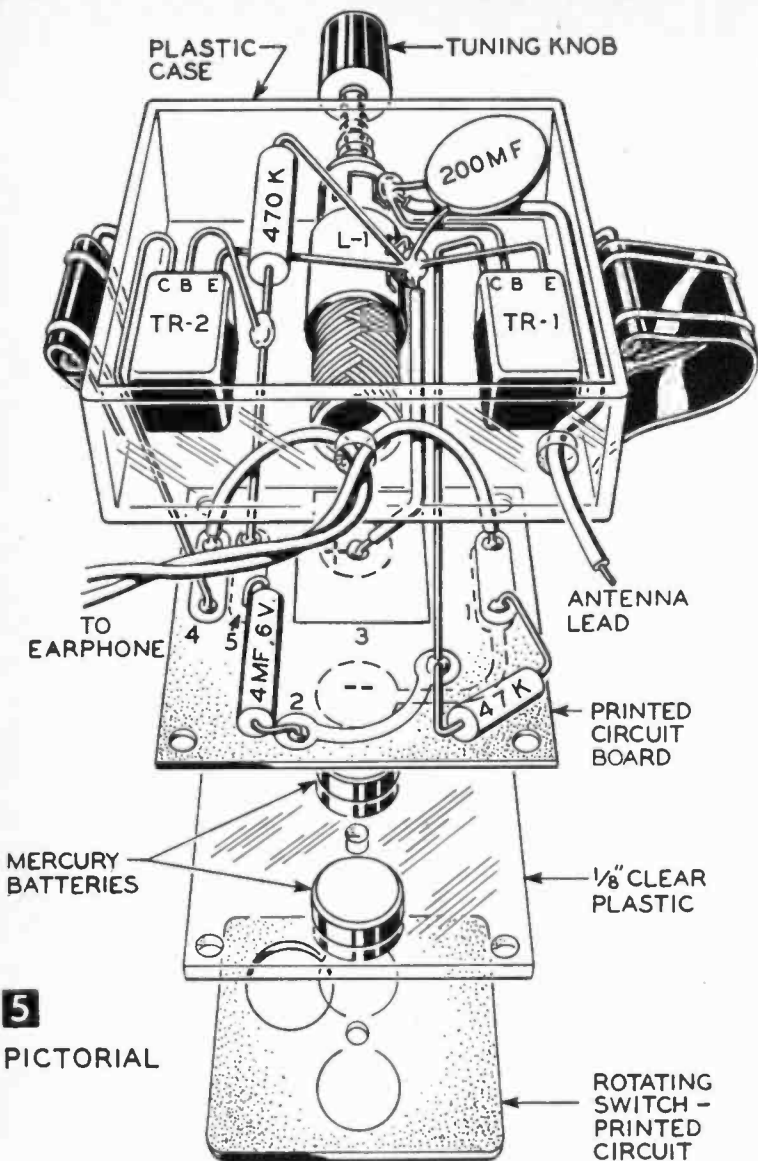Back view of receiver showing laminate switch (piece D). Here, the Wrist Radio is shown in all its ultra-smallness, just slightly less than full-size.



5
PICTORIAL


MATERIALS LIST—WRIST RADIO

- C1 200 mfd ceramic disc capacitor (Centralab DD201)
- C2 4 mfd 6-v. transistor midjet electric capacitor
- R1 47,000 ohms, 1/4-watt carbon resistor
- R2 470,000 ohms, 1/4-watt carbon resistor
- L1 high-gain loopstick (Lafayette MS-11; see text for physical modification)
- B1, B2 Sonotone miniature hearing aid batteries (M-40A) see text
- SW1 Raytheon CK722 transistors
- Earphone Dynamic (Lafayette MS-260)

Printed Circuit Material*

- ball point pen (PRLT)
- Piece D—copper laminate XXXP (PC-D)
- Piece C—copper laminate XXXP (PC-DD)
- liquid etchant (PE-5)

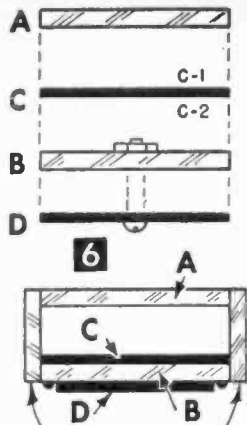*All PC materials obtainable from Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N. Y.



PLASTIC SIDES GLUED TO ASSEMBLY
BOLT PIECES C AND B AT ALL FOUR CORNERS. B AND D THROUGH CENTER

shown in Fig. 6 and drill a 1/8-in. hole at each corner. Then bolt pieces B and C together at the corners, pieces B and D through the center. (The unit must be tested before piece A is secured in position.)

When the unit has been assembled, insert the batteries. Place a dot of red paint on number 7, piece C-2, to identify this as the positive terminal of one of the batteries. The other battery, of course, is turned to its negative side on number 6.

Now turn the switch (piece D) to its On position (you'll hear a click in the earphone) and tune for a station.

When you are sure you have reception, glue small pieces of 1/16-in. plastic around the sides of the assembly, filing down corners and sides for neatness. Drill 1/8-in. holes in the side opposite the tuning knob for the antenna and phone wires. Then buy a toy dime-store watch and remove its band and fasten the band to the sides (see Fig. 4) by pressing holding clips into the plastic case with a hot soldering iron.

Crayons Mark Terminals

- When removing defective parts such as transformers from a radio or TV, use wax crayons to mark the terminals from which leads have been unsoldered, for identification when installing a new part.



Designed primarily for use by the student ham who wants to keep up his code speed, the Student's Special can be modified to receive the standard broadcast band.

Student's Special

By C. F. ROCKEY

Here's a project for the radio-minded high school or college student, or for the man whose son is such a student—an inexpensive short-wave receiver for the study desk

THIS receiver employs an untuned radio frequency amplifier, a regenerative detector, and an audio amplifier. In addition to increasing the unit's sensitivity, the RF amplifier isolates the detector from the antenna, thus minimizing hand-capacity effects. A voltage regulator tube also makes a big contribution to overall stability. This circuit thus offers the maximum in short-wave receiving satisfaction at minimum cost. And, since a large resistance unit is required to drop the heater voltage, a lamp bulb is used for this purpose, a lamp that normally burns only slightly less brightly than normal and does double duty as a close-in reading lamp. In addition, a sturdy book trough, capable of holding half a dozen textbooks, is included.

Build the receiver unit itself first; then, the book trough and lamp assembly. Begin by lay-

ing out the chassis as shown in Fig. 2. Set the tubes and coil in position in order to assure proper clearance, then drill all small holes with a No. 27 drill, large enough to clear the body of a 6-32 screw. Punch socket holes with a 1 $\frac{3}{16}$ -in. Greenlee socket punch (available from any large radio supply house).

Next, take the 7 x 10-in. front panel (see Materials List) to your neighborhood sheet-metal shop and have the tinsmith cut exactly 1 in. from it, making it 7 x 9 in. He can do this on his foot-powered shear much more neatly than you can with a hacksaw. If no such facilities are available, however, you'll have to use the saw; this metal is too tough for hand tin shears. Finish the raw edge of the panel with black automobile "touch-up" enamel.

Now lay out and drill holes for the front-panel mountings (Fig. 3). Consult the instructions and template enclosed with the tuning dial when drilling mounting holes for it. Then fasten the sockets, terminal strip and selenium rectifier to the chassis, using 6-32 steel machine screws and hex nuts (buy 1-in. screws, cutting them shorter where too long with diagonal cutters and pliers) and secure to the chassis the insulated tie points for holding the electrolytic filter capacitors. Insert other tie points as the wiring progresses.

Figure 4 gives the schematic for the wiring; Fig. 5, the pictorial. Heater and plate-supply leads can be as long as convenient; you can even group these together cable-like if you wish. Keep these wires close to the chassis, however, in order to avoid hum troubles later.


Keep plate, grid and other signal-carrying leads as short and direct as possible. Except for the electrolytic and large paper capacitors (which should be hung between tie points) the resistors and capacitors can be wired-in directly without other mounting precautions.

Care is the only preventer of wiring errors. Mark over the schematic as wires are inserted; check each stage or circuit as it is completed. Carefully observe polarity on electrolytic capacitor and selenium rectifier connections. Finally, have one of your radio-minded friends recheck the wiring for you, before plugging-in

to eliminate those annoying mistakes a person misses when checking his own work.

When you are sure that the under-chassis wiring is complete and correct, mount the variable capacitors, dial, potentiometer and phone jack securely on the panel. Then fasten the chassis and panel together, and complete the wiring.

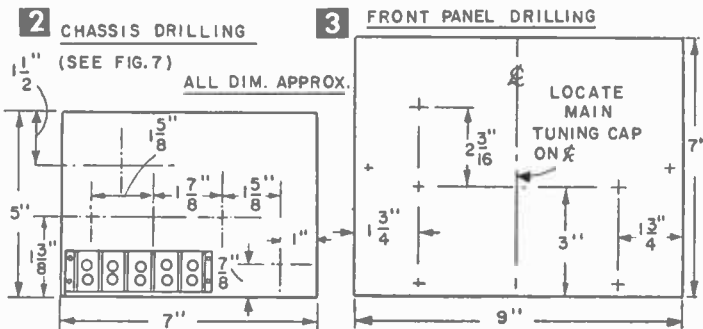
When all wiring has been completed and checked, insert



MATERIALS LIST—SHORT-WAVE RECEIVER

- | No. | Description |
|-----|---|
| 1 | 7 x 10" steel panel (Bud Radio Corp.) |
| 1 | chassis, steel, 1 1/2 x 5 x 7" (Bud Radio Corp.) |
| 1 | terminal strip, 5-terminal barrier type (Allied Radio Corp., catalog no. 41-H-673) |
| 1 | vernier tuning dial, national type BM |
| 2 | knobs, 1/4" shaft |
| 1 | 100 mmf variable band-set capacitor (Bud Radio Corp., type #1855) |
| 1 | 33 mmf variable main tuning capacitor (Bud Radio Corp., type #1852) |
| 1 | 100K linear taper potentiometer, with S.P.S.T. switch |
| 4 | 8-prong (octal) socket, amphenol, type "MIP" |
| 1 | 4-prong socket, amphenol, type "MIP" |
| 1 | single circuit headphone jack (Mallory type 701) |
| 1 | phone plug (Mallory type 75) |
| 1 | selenium rectifier, half-wave, 65 ma (Selectron) |
| 6 | insulated tie-points, 2 insulated lugs coil forms, 4-prong (I.C.A. type 2158) one for each coil desired |
| 2 | 6SK7 tubes (metal type preferable; "GT" type may be used) 6SG7 tubes may be used instead of 6SK7's if available |
| 1 | 6J5 tube (a 6L5 may be used; metal type preferred) |
| 1 | VR 90 tube (sometimes called 0B-3) wire, screws and solder as required |

- | No. | Description |
|---|---|
| Capacitors Required | |
| Mica ("postage stamp" type) | |
| 3 | 100 mmf |
| 5 | 6000 mmf |
| 1 | 25 mfd |
| Paper (200 v. working voltage) | |
| 2 | 0.25 mf tubular |
| 1 | 1.0 mf tubular |
| Electrolytic (150 v. working voltage, tubular type) | |
| 2 | 30 mfd |
| Resistors Required | |
| Carbon type (all 1-watt size unless otherwise stated) All values in ohms (K-1000 ohms) | |
| 2 | 22K |
| 1 | 8.2 megohm |
| 2 | 100K |
| 1 | 270K |
| 1 | 47K |
| 1 | 100 |
| 1 | 5K, 2-watt |
| Wire-wound type: | |
| 1 | 2K, 10 watt |
| 1 | 40-watt, Mazda lamp, 110 volt, with socket. |
| Headphones required: Trimm "dependable," or any other good high-impedance double headset. Crystal phones may be used, but are expensive and not necessary here. | |
| 1 | line cord and plug |

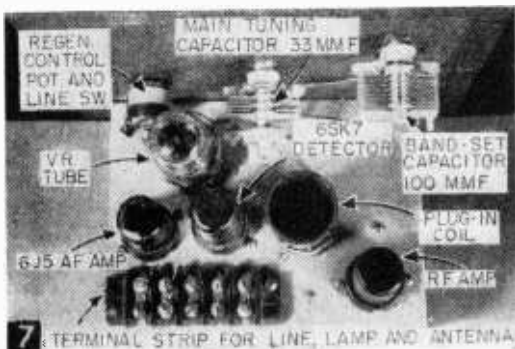

Top of chassis view.

post on the terminal strip. With the potentiometer set just above the oscillation point (slightly on the "hiss" side), rotate the band-set capacitor. Whistling, indicating the presence of signals, should be heard. For best reception of code signals, the potentiometer should be set just on the oscillating point; for voice signals, just below the oscillating point.

The correct technique for tuning in a voice signal is first to tune for the steady whistle, indicating the presence of the "carrier wave,"


then gradually back down the potentiometer until the whistle just stops. Finally, carefully and slowly readjust the tuning control until the voice or music comes in the best. Much as with playing the violin, a little practice is prerequisite to good results.

The band-set, band-spread tuning system used in this receiver enables you to spread a narrow section of the spectrum, such as an amateur or a short-wave broadcasting band, over the whole dial. When used properly, this vastly improves tuning, and enables you to hear many stations which otherwise would be missed completely.

As designed, this receiver is for use with headphones. This is to avoid barraging a non-radiotic roommate with irritating "noise." However, many strong amateur and short-wave broadcasting stations (the Voice of America, the British Broadcasting stations, and occasionally Russia) come in strong enough to work a small PM speaker when coupled through a plate-to-voice coil output transformer. Stick to the 'phones for regular work, however. You'll hear many more stations with them.

Oh yes, the set is automatically grounded through the power line. Do not use an outside ground (you may blow a line fuse). And, if the hum-level seems high, reverse the plug. If you want to use a doublet antenna instead of the straight wire, connect one side to the antenna terminal and the other to the chassis.

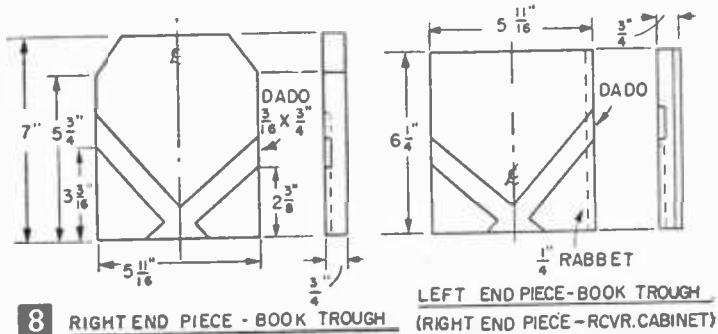Building the Book Trough Unit. Make this unit from clear white pine unless you are equipped for and experienced in working with hard woods. Begin by cutting and dadoing the book trough end pieces (see Fig. 8). Then make



8

MATERIALS LIST—BOOK TROUGH

No.	Description
7 linear ft.	$\frac{3}{4}$ x 5 and $1\frac{1}{8}$ " white pine stock, clear
11"	1 x 1" white pine
3'	rubber covered lamp cord
12 $\frac{1}{4}$ "	lamp tubing, threaded
1	nut to fit lamp tubing
1	keyless lamp socket
1	clip-on-bulb lamp shade, 8" dia. at bottom
Nails, insulated staples, finishing materials	

the front and back pieces for the book trough (Fig. 9A). If you don't have dadoing equipment, nail the book trough directly to the ends, shortening the back and front pieces by about $\frac{1}{2}$ in. in order to keep the overall proportions correct and omit the panel recess shown in Fig. 9A in the book trough front piece. Sand these parts and assemble, using 3d finishing nails.

Next, make the left-hand receiver cabinet end pieces, and the top piece for the receiver cabinet (Fig. 9B). You can simplify this part of the project by not recessing the cabinet back or by omitting the back entirely if you don't need its dust-proofing protection.

Now cut off 25 in. of the $5\frac{1}{8}$ -in. stock for the base (Fig. 10A), drill the $\frac{1}{2}$ -in. and $\frac{1}{4}$ -in. holes, and groove the bottom for the lamp cord.


Begin the general assembly (Fig. 11) by first nailing the left-hand cabinet end to the baseboard, with its outside edge $\frac{3}{4}$ -in. from the left end of the baseboard. Then nail the left-hand end of the book trough (right-hand end of the cabinet) to the base with its right-hand edge exactly 9 in. from the outside edge of the previously nailed end piece. Then nail down the right-hand end of the book trough.

After the cabinet top has been nailed on, make the lamp stand (Fig. 10B) from an 11-in. piece of 1x1 stock. Carefully drill a $\frac{1}{2}$ -in. hole (lengthwise) through this piece, using a long, electrician's auger bit, or drill halfway from each end with a regular auger bit. Round the corners at the upper end.

From your local electrical supply store get 12 $\frac{1}{4}$ -in. of lamp tubing (long, threaded steel pipe through which the cord is passed in nearly every table lamp), and a nut to fit. Pass this lamp tubing through the lampstand and through the $\frac{1}{2}$ -in. hole at the right-hand end of the base. Screw the nut on to the bottom of the lamp tubing, thus fastening the lampstand on to the base. Next, screw the shank of a lamp socket on to the upper end of the lamp tubing until it presses firmly on the upper end of the wooden lampstand. Now nail the lampstand to the right-hand end of the book trough. Remove the lamp socket to facilitate finishing the woodworking. Cutting, drilling and installing the back of the cabinet completes the woodworking.

This unit may be finished either by painting or by staining and varnishing.

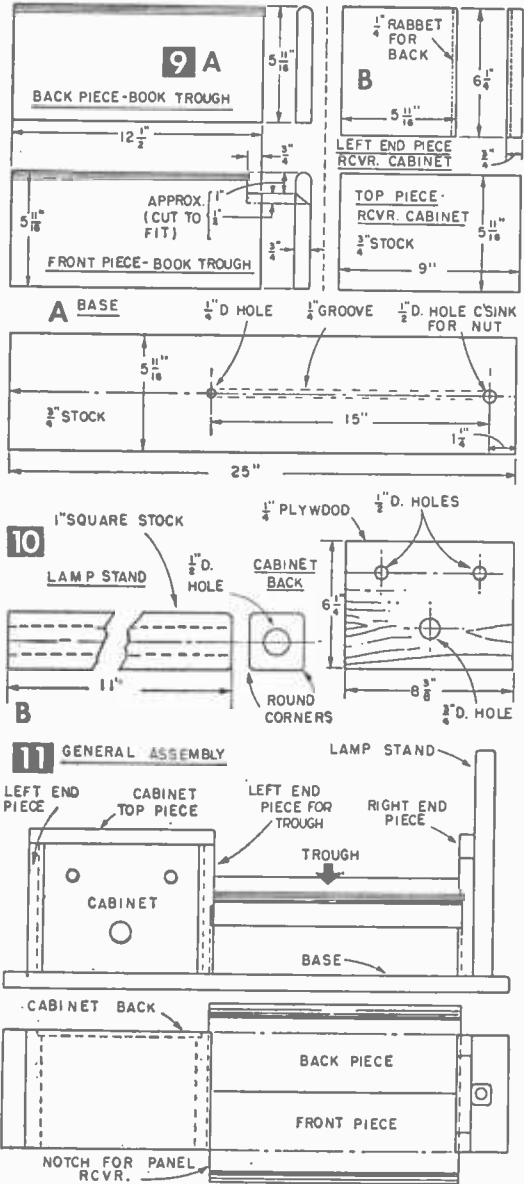When the finish is dry, screw the lamp socket back on the upper end of the lamp tubing, con-



nect about 3 ft. of rubber-covered lamp cord to the socket and assemble after passing the cord down through the lamp tubing to the bottom of the base. Run the lamp cord through the groove and pass it up through the $\frac{1}{4}$ -in. hole into the cabinet.

Fasten the cord into the groove with small insulated staples, at several places, being careful not to pierce the insulation on the lamp cord.

Now make lamp, power line, and antenna connections to the terminal strip on the back of the receiver chassis and fasten the receiver panel to the front of the cabinet. Screw a 40-watt lamp bulb into the lamp socket, put an appropriate shade on this bulb, and your *Student's Special* is complete.

ELECTRONIC TIMER

Now You Can Split Seconds

By THOMAS A. BLANCHARD

FEW projects in the field of electronics have the general appeal to all experimenters as do timing devices which operate without benefit of moving parts. In industry, electronic timers are already widely used in the control of precision operations where a motor-driven timer would be much too sluggish to time short interval operations.

Unlike mechanical timers, which depend upon various gear escapements, the electronic timer depends merely upon a vacuum tube and the charging or discharging of a condenser in the grid bias system to control the time cycle. Without question, the timer described here is simple enough for beginning radio experimenters to duplicate with success. More important, few parts are required in construction—all generally available, including tubes, since any one of several low current-low voltage tubes may be employed. However, the constructor is not limited to one of the pentodes suggested in the schematic. Actually the pentode is connected to function as a triode, therefore, any triode such as a 30, 1E4G, 1H4G, 1LE3, 1G4G, etc., may be substituted simply by changing the filament resistors from 600 to 1000 ohms each.


The timer is housed in a 3x4x5 metal box such as stocked by all radio supply houses. The chassis is a simple metal bracket consisting of a 1½ in. diameter hole for mounting an octal wafer socket, and two ½ in. diameter holes; one for mounting the timing condenser and the other for passing wires.

It can be stated here that these physical specifications may be ignored if the constructor has other materials on hand for housing the timer.

As shown in the drawings, the box panel is drilled to accommodate a 10-meg potentiometer, and terminal strip. Also, a suitable hole is drilled in the side of the box, toward the rear, to receive a double pole-single throw toggle switch.

To assemble the chassis:

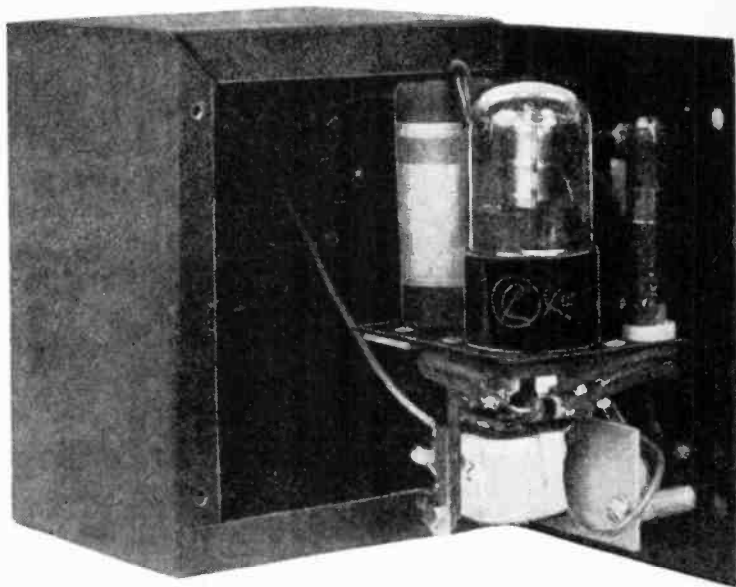Attach the wafer socket first; then put a strip of bakelite over the adjoining ½-in. hole for mounting the 0.5 mfd. paper condenser. A brass eyelet or lug in the center of this strip provides a convenient mounting for the condenser. One of condenser leads



is passed through eyelet and soldered securely.


The filament voltage drop resistors are mounted vertically in each corner of the chassis by means of long 6-32 machine screws. A fiber washer should be placed over each end of the resistor if

ELECTRONIC TIMER—Materials List

- 1 3x4x5 Metal Box
- 1 Metal chassis (homemade)
- 1 10 meg (or more) potentiometer
- 1 30,000 ohm, 1/2 watt resistor
- 1 50,000 ohm, 1/2 watt resistor
- 2 600 ohm, 10 watt resistors for .1 amp. tubes ohmite (1000 ohm, 10 watt resistors for .06 amp. tubes)
- 1 octal wafer socket
- 1 potentiometer dial plate
- 1 bar knob
- 1 terminal strip
- 1 0.5 mfd. or larger paper condenser
- 1 4 mfd., 150 volt electrolytic condenser
- 1 Pentode or triode tube of the low current type
 - Pentodes: (.1 amp. filaments) 1Q5GT, 1C5GT, 3Q5GT*, etc.
 - Pentodes: (.05 amp. filaments) 1T5GT, 1A5GT, 1LA4*, 1LB4*, 30*, 1E4G, 1LE3*, 1G4GT, 1H4G, 1E4G, etc.

Tubes marked with asterisk (*) require socket wiring changes. All others interchangeable in circuit.

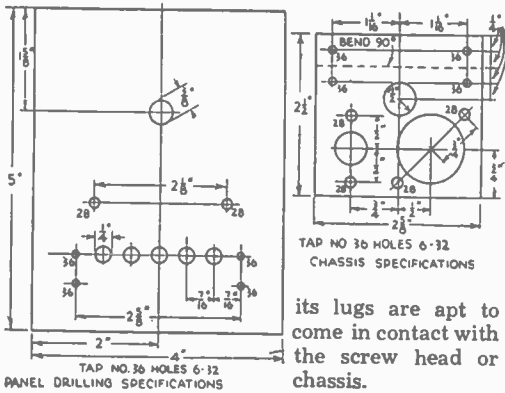NOTE: For simplification, pentode in schematic is drawn as a triode. The sup. grid, (prong 4) is tied to plate (prong 3) in all instances. Thus pentodes and triodes may be interchanged without altering wiring.



its lugs are apt to come in contact with the screw head or chassis.

The chassis is attached to the panel at this stage. Since the panel carries the terminal strip and potentiometer, the control now stands ready for wiring. Because of the timer's simplicity, no special comments are needed because the drawings show all details. The relay and toggle switch are installed after all other work has been completed.

In the original model, two studs were threaded and screwed directly onto two of the screws projecting from the terminal strip to provide a mounting for the relay. The spacing of these studs is identical to the mountings of several popular relays sold by radio suppliers. However, in the original model, it was necessary to mount the relay on a bakelite strip since its design did not include a mounting bracket.


A D.C. relay of the single pole-double throw type, and having a coil resistance of 2,000 ohms or more, controls the load circuit. A 4 mfd., 150 volt electrolytic condenser is shunted across the coil to eliminate the A.C. in the half-wave recti-

fied current delivered to the relay.

The control is completed by wiring in the relay contacts and d.p.s.t. toggle switch. One half of the toggle switch serves to put positive bias, through a 30,000 ohm resistor, on the grid. The two remaining poles on the toggle switch are wired in series with the normally closed contact of the relay.

When the toggle switch is open, the grid of the tube is negatively biased and the relay does not close. Tripping the toggle switch does two things: First, negative bias is applied, but is retarded in reaching the grid because of the high resistance potentiometer and condenser in the grid circuit. At the instant positive bias is applied, we complete the circuit through the normally closed contact of the relay. This causes the device being timed (photo enlarger, etc.) to come on. After an elapse of time, depending upon the position of the potentiometer adjustment, the grid becomes positive. At that instant, the relay becomes energized, and the timer circuit opens, shutting off the device being timed.

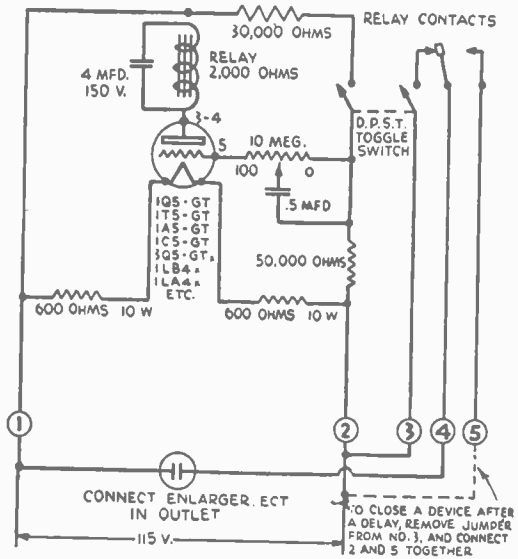This same timer may be employed to perform the reverse operation simply by changing the terminal connections shown in the schematic.



Now when the toggle switch is closed, the controlled circuit will remain open, and not close until a predetermined elapse of seconds. The circuit will then remain closed until the timer is reset. Tripping the toggle switch back to its "off" position automatically resets the timer.

The timer, using the 10 meg potentiometer and 0.5 mfd. paper condenser specified, will time from 0 to 35 seconds, approximately. However, the timing range can be increased by increasing the grid capacitance to 1 mfd. or more. A 20 meg potentiometer will still further extend the time delay to minutes.

There are no bugs prevalent in this circuit, but

if the timer is wired properly and does not function, look to the relay for the source of the trouble. Some relays may have the fixed contacts spaced too far from the moving arm, or the spring tension on the arm may be too stiff. The

solution is to carefully bend the arms with flat-nose pliers, or weaken the coil spring by removing it from the relay and stretching it slightly. The latter measure should be employed before bending the fixed contacts.


Simple Phono Amps for Earphone Listening

By ARTHUR TRAUFFER

THEY don't come any simpler than these phono amplifiers. Both models (Figs. 2 and 3) are built around a low-priced transistor and a small battery, using the same basic circuit as shown in Fig. 4.

Either model will boost the output of any crystal or ceramic phono cartridge so you can hear the music loud and clear in a pair of magnetic earphones—where it won't disturb the household!

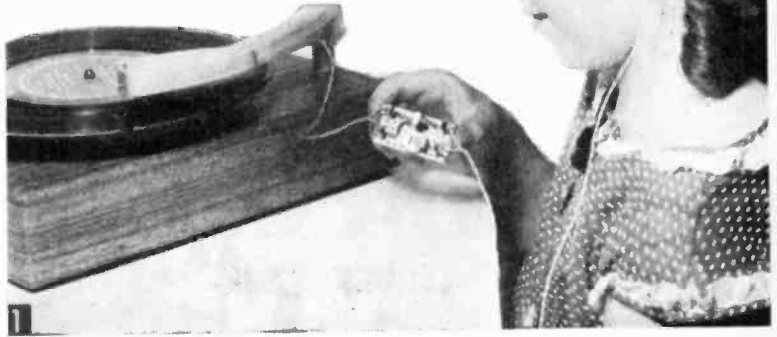Note in Fig. 4 that the collector is connected to the "ground" side of the circuit, instead of the emitter to the ground as in most transistor audio amplifier circuits. With this common-collector configuration, you'll have high input impedance and low output impedance. And, although this circuit has little actual gain, it serves as an efficient impedance-matching device which matches



Youngsters can listen to records without disturbing the rest of the family (and you can play your favorite discs late at night) with this simple phono amplifier.

the impedance of common magnetic earphones to the comparatively high impedance of crystal and ceramic phono cartridges. This results in more efficient coupling between cartridge and phones.

Breadboard Model. In the "breadboard" model of this phono amp (Figs. 1 and 2), four #15 Fahnestock clips, and the two parts of the mercury cell clip, are mounted with four 2-56x $\frac{1}{4}$ -in. roundhead machine-screws in #44-drill holes in a $\frac{1}{16}$ x1x2-in. piece of perforated Bakelite. You can screw-fasten the clips on a small block of hardwood if no Bakelite is handy.

The two parts of the battery clip are cut, bent, and drilled as in Fig. 2 from lightweight tin or brass sheet. Place the two Fahnestock clips that hold the battery clip so their mounting holes are about $1\frac{1}{8}$ in. apart.

Cover the three leads of a low-priced general-purpose p-n-p junction transistor with small diameter spaghetti tubing to prevent shorts. But cut this tubing short enough so you can pinch the leads, close to the soldering ends with the nose of a pair of pliers to absorb some of the heat while soldering the leads to the clips.

As shown in Figs. 1 and 4 solder the base (B) lead of the transistor to the upper-left clip, the collector (C) lead to the lower-left clip, and the emitter (E) lead to the upper-right clip. When inserting the Mallory RM-625 mercury cell into the clip, be sure that the bottom or negative side


MATERIALS LIST—SIMPLE PHONO AMP

"Breadboard" Model:

- 1 low-priced general-purpose p-n-p junction transistor
- 1 Mallory RM-625 mercury cell (1.3 volt)
- 1 pc $\frac{1}{16}$ x 1 x 2" Bakelite (or hardwood will do) thin tin or brass sheet, $\frac{1}{4}$ " wide by $2\frac{1}{4}$ " long
- 4 #15 Fahnestock clips
- 4 round-head 2-56 x $\frac{1}{4}$ " machine-screws with hex nuts 6" length small diameter spaghetti tubing


Plastic Box Model:

- 1 low-priced general-purpose p-n-p junction transistor
- 1 battery-holder for single penlite cell (Lafayette Radio, MS-137)
- 1 Ray-O-Vac #400 or Eveready #912 penlite cell
- 1 standard phono jack
- 2 standard phone tip jacks
- 1 plastic hinged-cover box $1\frac{1}{4}$ x 2 x 3" (dime store) 6" small diameter spaghetti tubing
- 2 round-head 4-36 x $\frac{1}{4}$ in. machine-screws, with hex nuts
- 1 pair sensitive high-impedance magnetic earphones, or one Lafayette Radio, No. MS-260 magnetic earpiece. Do not use crystal phones with this amplifier

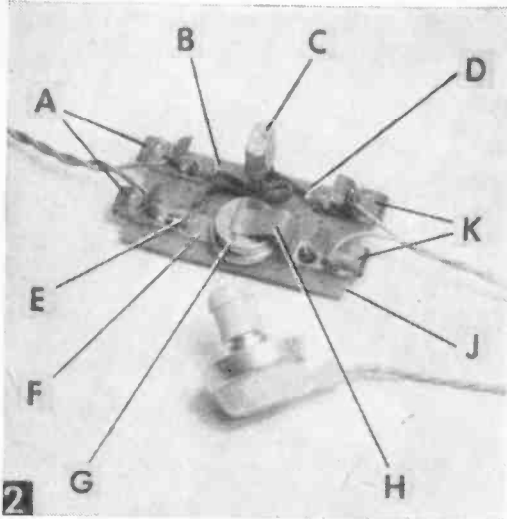

Closeup of "breadboard" model.

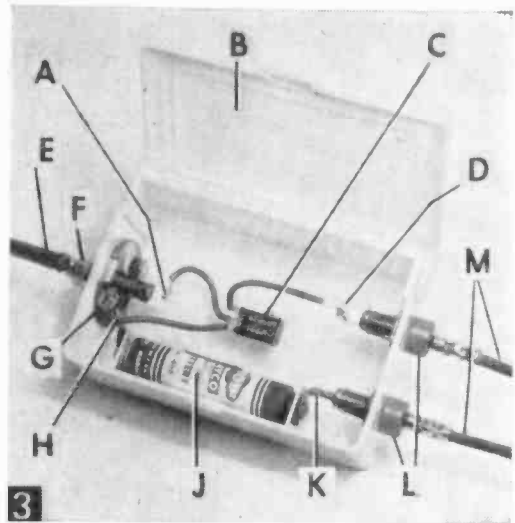(A) input (#15 Fahnestock clips); (B) solder "base" lead of transistor to upper-left Fahnestock clip; (C) low-priced p-n-p junction transistor; (D) solder "emitter" lead of transistor to lug of upper-right Fahnestock clip; (E) solder "collector" lead of transistor to lower-left Fahnestock clip; (F) battery clip, 1/4" by 1" thin metal strip. Bore hole in left end and fasten under Fahnestock clip; (G) Mallory RM-625 mercury cell; (H) battery clip, 1/4 x 1 1/4" thin metal strip bent to hold battery. Bore hole in right end and fasten under Fahnestock clip; (J) 1/16 x 1 x 2" perforated Bakelite strip; (K) output (#15 Fahnestock clips).



Closeup of plastic case model.

(A) solder "base" lead of transistor to center lug of phono jack; (B) dime store plastic box with hinged cover, 1 1/4 x 2 x 3"; (C) any low-priced p-n-p junction transistor. (The writer used a Raytheon CK721 because he happened to have it on hand; (D) solder "emitter" lead to lug of phone tip jack; (E) cable from phono pickup; (F) standard phono plug; (G) input (standard phono jack); (H) solder together: outer lug of phono jack, lug of battery-holder, "collector" lead of transistor; (J) 1 1/2 volt penlite cell held in an Acme battery holder; (K) solder battery-holder lug directly to lug on phone tip jack; (L) output (standard phone tip jacks); and (M) phone cords and tips.


Input and output jacks are used for convenience.

of the cell goes to the collector of the transistor. If you happen to have an n-p-n transistor and want to use it, then turn the mercury cell upside-down so the positive side goes to the collector, being careful not to short the cell while slipping it into the clip. Stick a piece of tape over the bottom of the "breadboard" model amplifier so the mercury cell cannot short out if the amplifier is placed on a bare metal surface.

Plastic Box Model. Figure 3 shows this fancier model. The dime store hinged-cover plastic box measures 1 1/4x2x3-in., but you can use most any plastic box of similar size. This model has a standard phono jack input to take the phono plug found on the cords of many record-players. Two phone tip jacks are used in the output so the tips on the earphone cords can be plugged-in quickly. A 1 1/2 volt penlite cell is held in an Acme battery-holder.

Mark the locations for the three phono jack mounting holes on the left side of the plastic box (Fig. 3). Then use a 5/16 in. drill for the center hole, and a #34 drill for the two screw holes. Secure the phono jack to the case using two 4-36x 1/4 in. roundhead machine screws. Mount the two phone tip jacks in two 1/4 in. diameter holes drilled in the right side of the box.

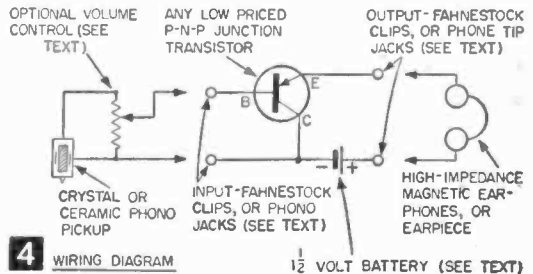Cover the three transistor leads with small spaghetti tubing; then solder the base (B) lead to the center lug on the phono jack, the collector (C) lead and one battery-holder lug to the outside lug on the phono jack, and the emitter (E) lead to the upper-right phone tip jack (Fig. 3).



Solder the remaining battery-holder lug to the lower-right phone tip jack.

When inserting the penlite cell, be sure that the negative end goes to the collector of the transistor. If you want to use a n-p-n transistor, simply reverse the battery in the holder so the positive end goes to the collector.

Using a low-output crystal phono cartridge and a pair of good high-impedance magnetic ear-phones, I get surprisingly good volume and tone quality with the simple amplifier. If you use a high-output crystal or ceramic cartridge, you may find it necessary to use a volume control connected as in Fig. 4. Or, it may be that your record-player is already equipped with a volume control.

If you hear too much treble and not enough bass, connect a .01 mfd (or smaller) fixed capacitor across the earphone. Experiment to find the size capacitor which works best.

Small Parts Cabinet

By HAROLD JACKSON


Test bench housekeeping is easier for the experimenter if he has a small parts and component cabinet like this one made from dime-store muffin pans. Rims of the pans slide in grooves dadoed into the sides of the cabinet. If you use a pan of different size than the 1¼ x 7½ x 10⅝-in. ones I used, change the dimensions accordingly, allowing ⅛ in. extra at sides and ends to keep trays from binding. Simply glue and brad the box parts together.

Since most muffin pans have slanting sides, make up the end blocks to grip the rim and bear against the slanted cup side. Top of the pans should be perpendicular to front block. Screw through the sides of two end cups into end block. Attach pulls or handles ½ x 3 in. A colorful decorative scheme is to paint cabinet gray and end blocks red.



MATERIALS LIST—SMALL PARTS CABINET

- | | |
|---|-----------|
| 1—1/4" plywood x 7¼ x 11¼" | bottom |
| 1—1/4" plywood x 8 x 11⅝" | top |
| 2—3/4" plywood x 4¾ x 11¼" | sides |
| 1—3/4" plywood x 4¾ x 8" | back end |
| 3—1⅜ plywood x 1½ x 7¼" | end block |
| 3—6-cup muffin pans; 3—tray pulls, screws | |

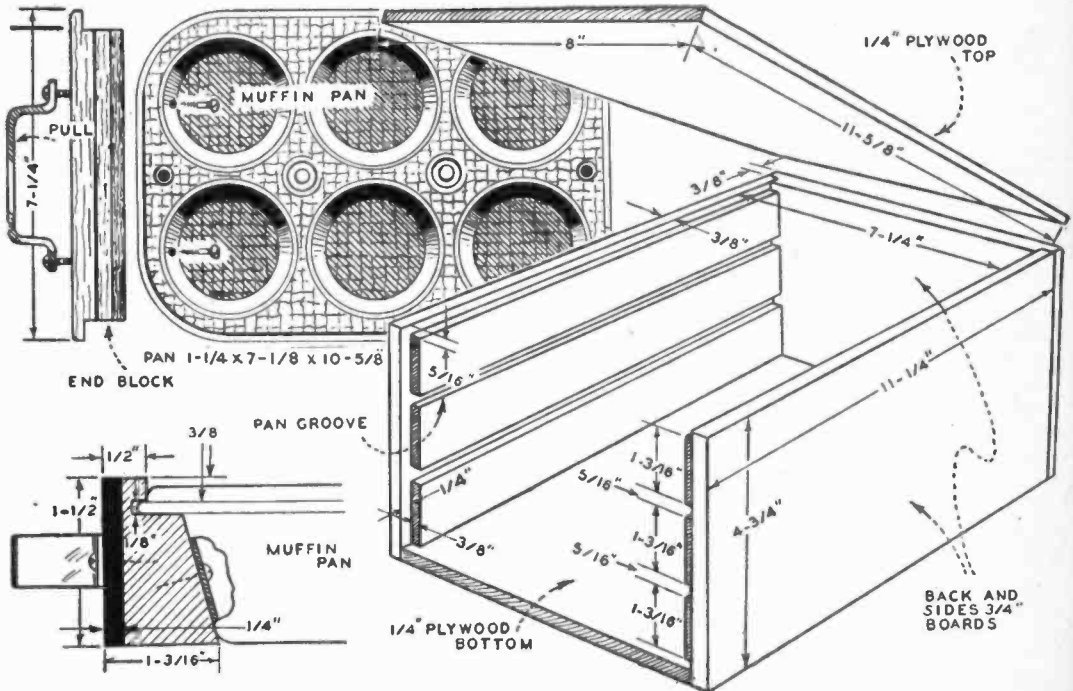



For demonstration purposes, this is all you need for stereophonic sound. Here a record changer with stereo pickup (center) simultaneously feeds the small amplifier on bench next to it and in turn the temporary speaker assembly at right from one channel of the stereo disc, and feeds the amplifier and speaker unit in the TV set at left from the other channel. Distances are about right for stereo listening in the average living room.

How to Add Stereo to Hi-Fi

By CLIFF HALL

UNTIL recently, stereophonic sound systems for the home have been financially out of the reach of most people.

Today, if you already have a reasonably good high-fidelity record playing system plus a reasonably good television set, the likelihood is that you can convert these units for stereophonic sound reproduction at a cost as low as \$35, or in some cases as low as \$20.

The reason for this abrupt revolution in stereo costs lies in the development by the industry of a new animal in the field—the stereophonic disc record.

What Is Stereo? In case we lost you on the first turn, stereophonic (or binaural—"two-eared") sound reproduction means the same thing to music as stereoscopic photography means to pictures. Because we have two eyes, we look at any object from two angles and in this way can perceive depth and the relative positions of more than one object. Thus the stereoscopic camera, with two lenses ("eyes"), makes two pictures which we can view at the same time and see the scene in proper perspective, just as though we were viewing it in person with our own two eyes.

Similarly, with two ears, we actually hear any sound from two "listening points" separated by the width of our head (see pages 130 through

134). If the sound is coming from the right, its vibration gets to our right ear first and to our left ear a fraction of a second later. Automatically, our mental system translates this fraction-of-a-second of time lag and tells us that the source of the sound is to the right. Thus, even with our eyes closed, we can tell with considerable accuracy the direction from which sounds around us come.


Just like a conventional camera with its single lens (eye), a conventional sound system with its single microphone (ear) picks up the sound from only one point; you might say that it is listening with one ear closed.

To solve this problem and re-create as realistically as possible the illusion that you are actually on the scene—listening with both ears and hence able to tell the direction the various sounds are coming from—technicians have been working for years to develop stereophonic sound systems. To do this requires what actually amounts to two complete and separate sound recording and reproducing systems; two microphones placed a distance apart (the two "ears" of the sound system); two recording machines each to record what its own microphone is hearing, and what amounts in actuality to two records. On the reproducing end, in turn, you'll need a device which will play these two records simultaneously, two amplifiers, and two sets of speakers on opposite sides of the room.

Until this year, the only method available to the public to do this job has been through the use of a stereophonic tape reproducer. In this method, the two sound channels are recorded on opposite edges of a magnetic tape; they are then played back simultaneously through two separate amplifiers (or one two-channel amplifier, which is substantially the same thing) and two sets of speakers.

Costs of such a system have generally run to a minimum of about \$400, while adding tape stereo to your present hi-fi would involve an outlay generally in the \$200 and up vicinity. Even at these prices, popularity of the system has been growing by leaps and bounds because of the extreme realism—the feeling of actually being present in the concert hall—which stereophonic sound systems give you.

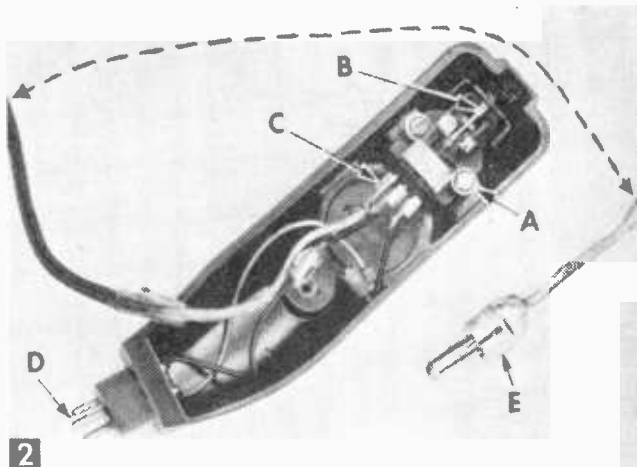Meanwhile, manufacturers of disc records have been hard at work de-



2

The Electro-Voice stereo cartridge (here installed in a Garrard plug-in head) has a mounting flange with standard centers for two bolts (A). The 45° diamond stylus (B) feeds three output terminals (C)—a common ground in the center and one channel through each outside terminal. Here one channel is fed through the standard Garrard plug-in leads (D), while the second feeds a secondary shielded cable, equipped with standard phono jack plug (E), to attach to TV amplifier.

for \$35

vising a new method to do the same job—on discs instead of tape—to combat this threat to their business.

Out of a welter of varying technical approaches industry leaders late in 1957 agreed upon the basis for a new stereo disc system. At the time this is written you can actually buy the equipment to play the new records, and by the time this reaches print, you should be able to buy the records themselves.

Viewed through a microscope, the groove in a conventional high-fidelity disc record consists of a series of side-to-side wiggles (Fig. 4). As the stylus of your record player passes through the groove, this side-to-side motion or vibration at varying speeds (frequencies) is translated into electrical impulses which your amplifier boosts so that your speaker can reproduce the original sound or something close to it.

In the new stereo discs, the microscopic picture is different (C in Fig. 4). Here, both sides of the groove are cut to a 45° angle, and each side carries its own independent set of wiggles which is in fact a separate recording (coming from a separate microphone). When a specially designed stylus passes through this new groove, it picks up side-to-side vibrations from one of the channels and up-and-down vibrations from the other; it then passes these two sets of impulses into two sets of wires and in turn into two amplifiers and two sets of speakers.


The result, reproduced as described above, is true stereophonic sound. But the new records have an additional gimmick: They are designed to be totally compatible, as well, with former high-fidelity pickups and systems. In other words, it is possible to play the new stereo disc through your present hi-fi system and get (it is claimed) approximately the same result as you would with a conventional hi-fi disc.

When the new system was agreed upon, manufacturers throughout the industry followed through with announcements that they would have pickups to play the new records on the market "in the near future," while record companies announced that the discs themselves would be forthcoming—likewise in the near future. Opinions as to costs varied widely.

After these original announcements, little further was heard until one firm, Electro-Voice of Buchanan, Mich., jumped the competitive gun by actually placing on the market a diamond-stylus stereo pickup cartridge (Fig. 2)—and not at the over \$50 price many had anticipated, but at a modest \$19.50.


SCIENCE and MECHANICS secured one of the first of these for evaluation.

Installation of the cartridge is a simple matter (Fig. 3). Flanges on the cartridge are spaced the conventional half-inch apart and simply by removing two screws, in most cases, the new stereo pickup can be dropped into the head of your pickup arm in place of your old hi-fi cartridge. Instead of the conventional pair of leads coming from the old cartridge, you now have three—one on each side for the two channels and a common ground in the center. Wiring simply involves connecting two terminals to your two old pickup leads and attaching a new shielded lead

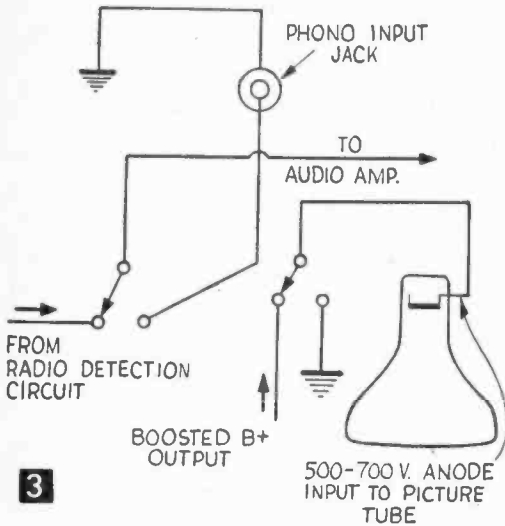

3

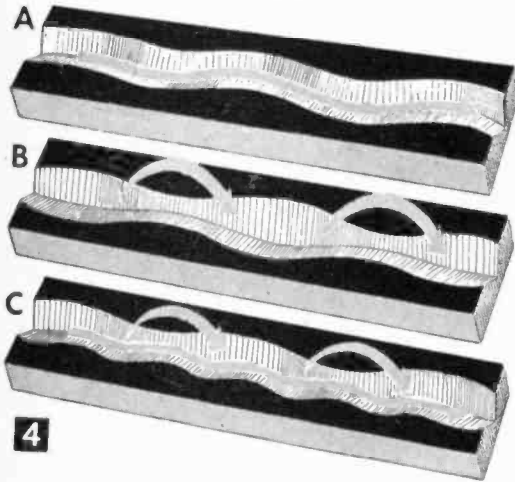One of the common methods of converting a TV set for phono use is by installing a phono input jack and a switch which cuts out radio detector output and grounds one of the control anode inputs to the picture tube. A number of other methods are used, too; if you don't understand TV circuitry, better call a service man.



4

- A** Opposite sides of the groove in a conventional disc recording are exact mirror images of each other. Where one side of the groove has a bulge, the opposite side has an exactly matching indentation. Thus the stylus (needle) moves only from side to side.
- B** If a groove were made in which bulges on one side were matched by bulges on the other, rather than indentations, then the stylus would be squeezed up and down, rather than moved from side to side.
- C** In a stereophonic disc, the above two methods are combined. Some of the bulges on one side are matched by indentations on the other, causing side-to-side movement which records one of the sound channels. Meanwhile, some of these same bulges on one side are opposed by bulges on the other side, causing up and down movement which records the other sound channel. The in-phase and out-of-phase variations are so finely spaced that manufacturers claim up to 25,000 cycles per second can be recorded on both channels.

(available at any radio shop) of suitable length.

In such record players as the Garrard (which we used), which has a plug-in pickup head, it is possible to get a spare head in which to install the stereo cartridge, so that you can change back to your hi-fi cartridge at any time simply by unplugging one and plugging in the other. You will, of course, have to adjust the tracking weight (11 grams is recommended for the stereo cartridge). The new lead can be taped to the pickup arm out of the way.

Now that you have your stereo pickup installed, next comes the problem of two amplifiers and two sets of speakers. You already have one—your regular hi-fi setup through which your record player played in the first place. But don't rush right out and buy another amplifier and speaker setup unless you have money to burn. Instead, take a good look around the living room. See that TV set over in the corner (Fig. 1). Let's look at it more closely.

If it's a good TV, especially if it's a console model of good manufacture, the chances are that it has a sound system almost as good as most of the lower-priced so-called hi-fi assemblies. And that sound system—that amplifier and speaker unit—can supply the "other side" of your stereo setup, at least to start.

Several models of console sets have for some years been manufactured with a phonograph input and selector switch already installed. If yours is one of these, you're in. (We used a five-year-old RCA 21-in. console already so equipped.) The TV, you see, is designed to do a job of reproducing the frequency modulated sound signal that accompanies the picture signal; most of them have amplifier units far superior to those of low-priced radios, and many have coaxial speakers of good size.

If your TV is not so equipped, you have two options: Install an input and selector yourself, or call your local radio-TV repairman, who will make the installation for you, in most cases for about \$15.

In this connection, we strenuously recommend that unless you have some little specific knowledge about TV innards, you call the repairman. High voltages, high enough to knock you flat, are involved here, with dangers too complex to discuss in this article. If, on the other hand, you know what you are doing inside that back panel, the problem is simply one of installing a switch to cut out the radio detector output and ground one of the central anode inputs to the picture tube. It is best to install a jack socket on the back panel to accept the lead from your stereo pickup. The schematic diagram (Fig. 3) presents such a typical installation; a number of other methods are used, however, and your service man may suggest one more suitable for your set.

Long enough leads between components should be left at the outset to permit moving the speaker units about the room to find the locations that will give the best result. (You'd better get the wife in the act here.)

Many leaders in the field suggest a separation between speakers of about six feet. In our installation, we found a wider spread—10 to 12 feet—provided a clearer separation of sound sources, perhaps because of room acoustics or because we are simply not accustomed enough to listening to stereo.

You will have to do some twiddling, too, to achieve a balance between the two dissimilar amp and speaker units. You will probably have to cut back the highs a bit on the hi-fi side to get its quality of reproduction closer to that of the TV.

As for fidelity, as in the case of any kind of a hi-fi or so-called hi-fi installation, the "finished product" will be no better than the quality of your weakest component—in this case, likely the amplifier of your TV set. But you will have stereo sound's startling realism at low cost.

With our test setup, the first stereo disc we could get was the Audio-Fidelity waxing of the Dukes of Dixieland, Vol. III. We also obtained the identical recording in a conventional, monaural LP version. We asked several trained musicians to listen.


All were impressed with the clarity with which you could place the relative physical location

of the instruments in the combo. But all had reservations, too. The comparison monaural disc without question yielded higher fidelity—wider frequency range—when played through the hi-fi unit alone with conventional pickup than did any of the other possible combinations. Playing the stereo disc with conventional pickup yielded a good sound; so did playing the stereo disc with the stereo pickup through two amplifiers; so did playing the stereo disc with both channels fed to the hi-fi amplifier alone, and so also did playing the conventional disc with the stereo pickup fed to one amplifier—but none were up to the straight conventional setup in our opinion, although the systems are adequately compatible in all directions.

Certainly, both equipment and disc quality will improve. Late in May, Electro-Voice announced a second pickup equalized to a velocity curve and capable of being interchanged with a magnetic rather than a ceramic cartridge. Other manufacturers will have equipment on the market this summer, they say, and platters will soon be plentiful.

If you dig this new sound, you can go as far as you wish in equipment. But you can also get in the act now for as little as \$35.

Magic-Eye Capacitor Checker

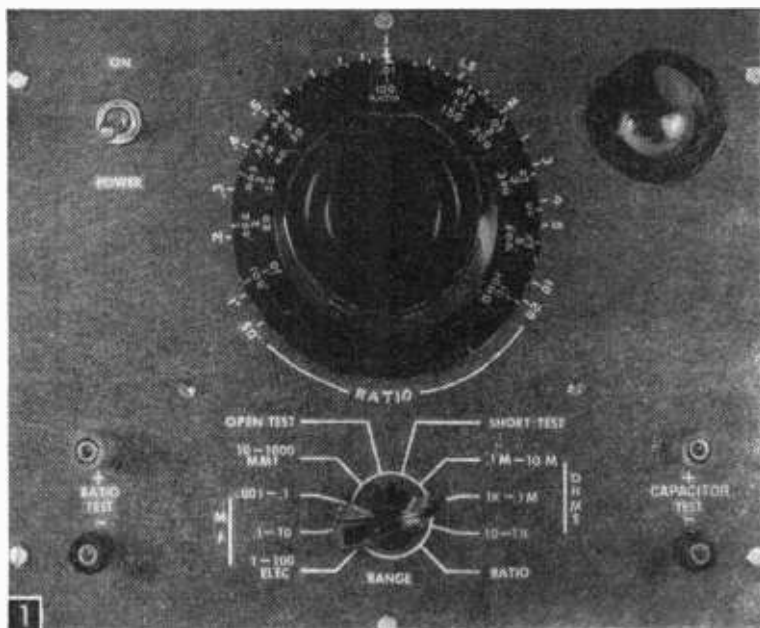


Front-panel view of checker. Not only can capacitance values be checked with it, but also resistance values and capacitance and resistance ratios.

trouble cannot be found by ohmmeter tests, substitution is usually resorted to. With a capacitance checker, however, a supply of substitution capacitors is not needed for checking; and the checker, if of the bridge type, can also be used for circuit design work.

Two types of capacitor checkers are normally available: the bridge, which measures capacitance value and also indicates shorted and open capacitors *when out of the circuit*; and a second instrument which does not measure capacitance, but does check for short-

NEXT to tubes, capacitors probably give more trouble in electronic circuits than any other single component. Sometimes, in critical applications, capacitors change value and upset circuit operation. Since this kind of

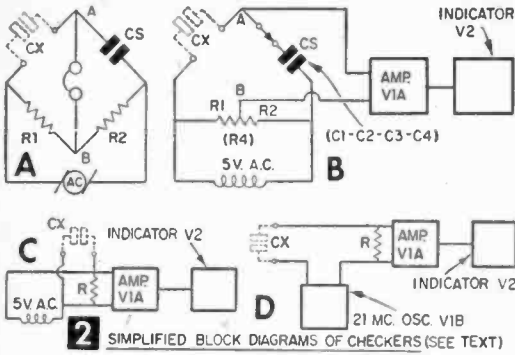and open capacitors *while they are still wired in the circuit*. The checker described in this article performs *both* of these functions as well as checking electrolytic capacitors, measuring resistance, and comparing R and C ratios.




Since three different basic circuits are used, let's first look at them in simplified form. Figure 2A shows an ordinary capacitance bridge; C_x is a capacitor of unknown value and C_s is a capacitor of known, or "standard" value. When the ratio of the resistance of R_1 to R_2 is the same as the ratio of the reactance of C_x to C_s , the voltage drop at point A and point B will be equal and there will be no voltage drop across the headphones.


In other words, a null indication. If the voltage used is sufficient, null indicators other than headphones, such as meters or tuning eye tubes, can be used. When other indicators are used, however, you normally cannot test electrolytic condensers, since appreciable ac voltage will damage them.

In the checker described in this article, a low test voltage is used, permitting a check of electrolytic condensers; this voltage is then amplified, enabling the use of a tuning eye as an indicator. The simplified circuit diagram for this checker is shown in Figure 2B, with a single potentiometer used as a two-ratio resistance divided by the arm. The voltage between points A and B appears across the grid resistor of the amplifier V1A. When a null is reached by moving the arm, no voltage appears and the tuning eye opens.


On the "Short Test," as shown in Figure 2C, the capacitor under test is connected in parallel with the grid resistor, which is connected across a 5 v ac source. The voltage drop across the resistor closes the tuning eye. If a shorted capacitor is connected across the resistor, the voltage drop is shorted out and the eye opens. This test can be made with the questionable capacitor wired in its regular circuit. External resistances as low as, roughly, 50 ohms in parallel with the capacitor will not materially affect the test.

Figure 2D shows the "Open Test" circuit. In this case, the output of a 21-megacycle oscillator (V1B) is connected to the grid resistor in series with the capacitor under test. If the capacitor is good, it will pass virtually all of the oscillator output, which will cause a voltage drop across the grid resistor and close the eye. If the capacitor is open, it will not pass the oscillator output and the lack of voltage drop across the resistor permits the eye to open, an "in circuit" test.

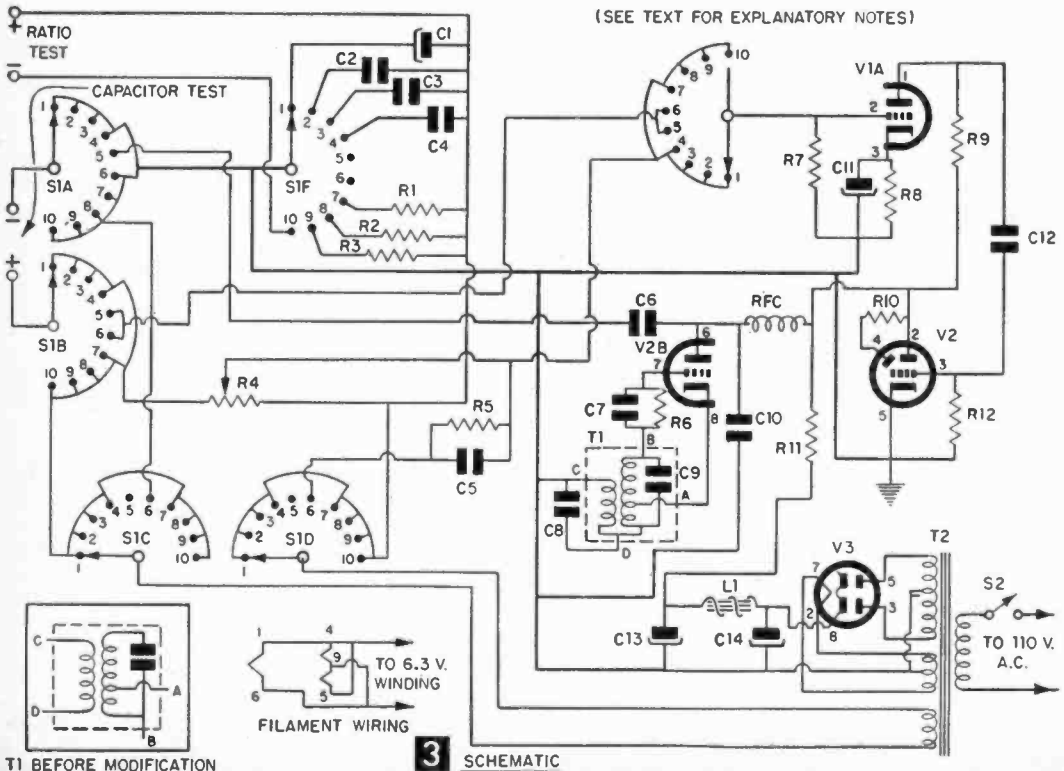

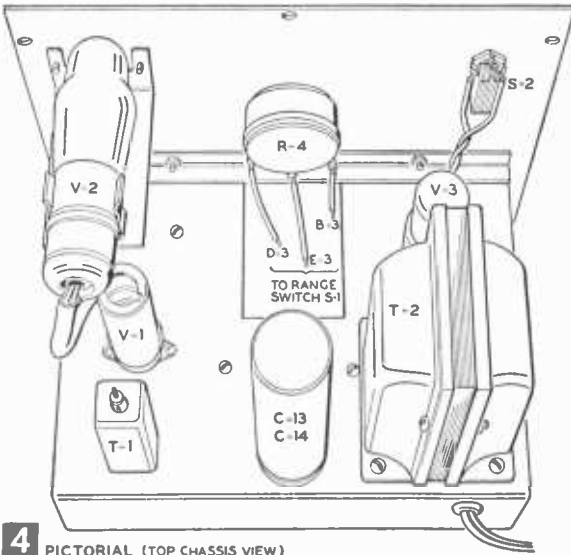

4 PICTORIAL (TOP CHASSIS VIEW)

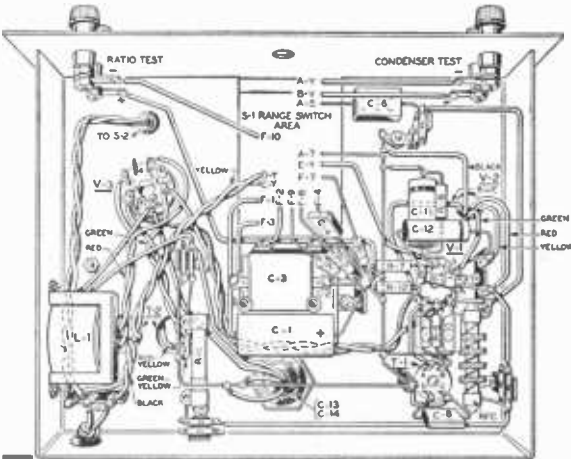

5 PICTORIAL (UNDER CHASSIS VIEW)

tions of the Range Switch (S₁) on Figure 3 correspond to the ranges as shown in the photo, Fig. 1, as follows:

- Position 1—Electrolytic capacitor, 1 to 100 mfd.
- Position 2—Capacitance, .1 to 10 mfd.
- Position 3—Capacitance, .001 to .1 mfd.
- Position 4—Capacitance, 10 to 1000 mmfd.
- Position 5—"Open" Test
- Position 6—"Short" Test
- Position 7—Resistance, .1 to 10 megohm
- Position 8—resistance, 1000 to 100,000 ohms
- Position 9—Resistance, 10 to 1000 ohms
- Position 10—Ratio Bridge

Since the bridge operates on *ac*, it is important to follow good shielding practice, and isolate the power transformer, choke and rectifier tube from the oscillator-amplifier tube V1. Figure 7 shows the chassis layout, giving the dimensions for the specific parts listed in the Materials List. If alternate parts are used, there may be slight deviations in mounting holes, but the general layout should be the same.

Since the unit itself will have some internal capacitance which will be added to the measured value, and will determine the minimum value that can be measured, every effort should be made to keep this internal capacitance to a minimum. The use of a single ground bus tends to reduce such internal capacitance and also reduces chassis currents which are detrimental to *ac* instruments.

The overall accuracy of the unit will depend on the accuracy of the "standard" capacitors, C1, C2, C3 and C4, the "standard" resistors, R1, R2, and R3, and the accuracy of calibration. (Spend a little additional to secure precision components unless a laboratory-type bridge is available to test lower-priced components to secure accurate values). In the case of C₁, the electrolytic capacitor, low-tolerance units are generally not available and it is suggested that stock units be tested to get as nearly as possible the correct value. Most stock units have a value in excess of their rated value, and a 5 mfd. or 8 mfd capacitor will be closer to the required 10 mfd. than one rated at 10 mfd.


If a laboratory bridge is not available to select C1, build your checker without connecting C1. When the bridge is functioning and the ratio scale has been calibrated (as explained later), set the Range on ".1-10", connect various stock units across the "Capacitor Test" terminals, and, using the ratio scale, attempt to find one that gives a ratio reading of 10:1. This will provide a reasonably accurate measurement, although balancing an electrolytic unit against non-electrolytic units causes some error.

In wiring the checker, run the filament circuits first, twisting the wires and running them next to the chassis. Then wire the power supply

By referring to Figure 2A, it can be seen that resistances could be substituted for C_x and C_y, and a null obtained. Three resistances (R₁, R₂, and R₃) have been included in the Range Switch (S₁) circuits of our checker to allow resistance measurements of anywhere from 10 ohms to 10 megohms.

Often there is a need for matched capacitors or resistors that have identical values, or have an exact relationship in values. In Figure 2B it can be seen that R₁ could be calibrated to read the ratio of resistance, and, if a second unknown value were substituted for C_y, the ratio of two external values could be determined. A position on the Range switch of our checker provides for this arrangement, using a second set of binding posts.

Figure 3 gives the detailed schematic diagram of this checker; Figure 4, a back view of the unit, showing parts placement. The numbered posi-

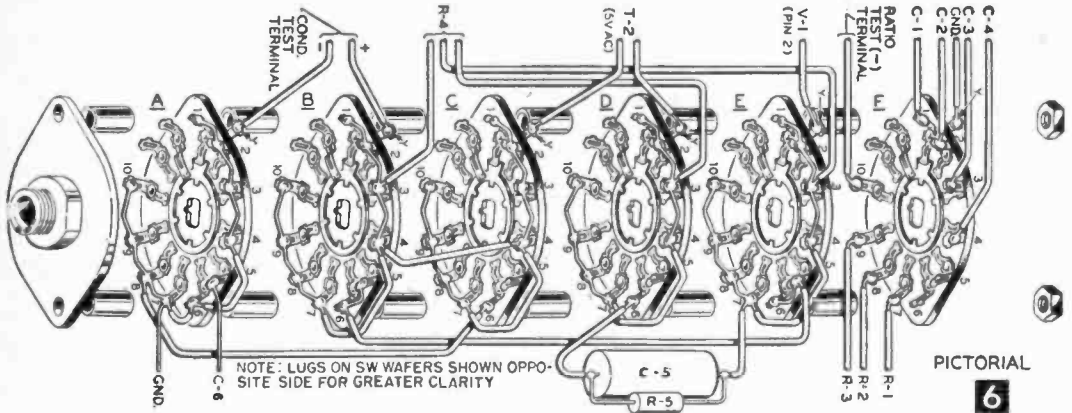

completely, with all wires carrying *ac* twisted and flat against the chassis. If a dropping resistor (R_{11}) is to be used, do not select its value or solder it in place until the rest of the unit is built. This resistor is necessary only when the power supply voltage *under load* exceeds 250 v, and its value is selected by trial-and-error in final testing, to reduce the supply voltage to 250 v.

After the power supply is wired, connect the ground bus wire in place and complete the remainder of the wiring (see Figs. 5 and 6). Many of the Range Switch (S_1) wafers have jumpers between terminals, and it simplifies wiring if these are wired before the switch is mounted. The switch wiring is also simplified if a section of the chassis above the switch is cut out, as shown in Fig. 7.

In the unit pictured, the cabinet used was smaller than specified, which required cutting the front of the chassis off and attaching it to the panel with an angle. Normally, the chassis would be attached to the panel by the binding

posts and the range switch. However, part of the underedge chassis lip should be cut away (as shown in Fig. 8) to give clearance for the Range Switch.


To minimize lead length and internal capacitance, the switch wafers must be designated in the order shown in Figs. 3 and 6. Wafer "A" (S_{1A}) is at the front of the switch, wafer "F" (S_{1F}) at the back, etc.


The coil (T_1) must be modified before mounting. The inset in Figure 3 shows the coil wiring as purchased and the letter designations on the terminals in the main diagram show the modified connections. This change is made by removing the coil from the shield can and unsoldering the coil and capacitor connections that go to terminal "B" and moving them to the terminal marked "D" along with the other coil connection. Then run a lead from the upper end of the coil and capacitor to terminal "B."

When the oscillator is wired, some adjustments may have to be made to secure optimum oscillation. Using a VTVM (or oscilloscope, if available), adjust the coil cores for

maximum output. Adjust the upper screw first (coil "A"- "B"), and then the lower. After adjustment, short the "Capacitor Test" terminals together (with Range Switch on "Open Test") to make sure that oscillation doesn't stop when a load is connected. If so, back off the coil adjustments.

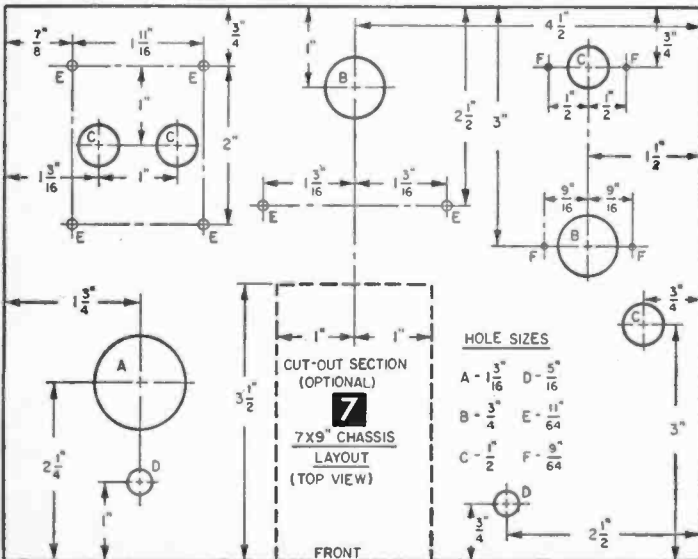Calibration. Before attempting to calibrate the unit, initial tests should be made. Test the bridge in each capacitance and resistance range (using capacitors and resistors of values within the range) to see if a null is obtained, opening the eye, in each range. Turn the potentiometer (R_4) slowly, as the nulls are usually quite sharp. Test the "Short"



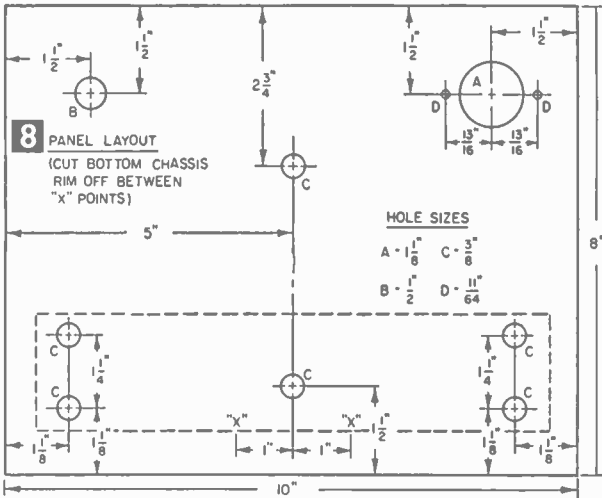

and "Open" ranges by seeing if the eye opens and closes as the "Capacitor Test" terminals are shorted out.

The Ratio range should be calibrated first. This can be done with an accurate ohmmeter, a Wheatstone bridge or a series of 1% tolerance resistors. If an ohmmeter or bridge is used, make a series of measurements of the resistance on either side of the potentiometer arm at various positions and calibrate the scale according to the ratio of these measurements. For this scale, the center point (where the resistance on either side of the arm is equal) is calibrated "1" and points on one side reduced to .05, and those on the

other side increased to 20. If 1% resistors are used to calibrate this range, various ratio combinations are connected across the two sets of terminals and spot calibrations made.

The most accurate means of calibrating the bridge scale is to use a series of precision capacitors or resistors. Since the resistance scales follow the same calibrations as the capacitance, use precision resistors to calibrate both scales, since precision resistors are cheaper than good capacitors. Only the center range (1000 to 100,000 ohms) need be calibrated; the other ranges are direct multiples. By using seven precision resistors (1000, 2000, 3000, 4000, 20,000, 30,000 and 40,000 ohms), each 1000-ohm point on the range can be calibrated.

A cheaper means of calibration would be to use a series of regular stock resistors, if a Wheatstone bridge can be borrowed from the local high school or a junior college or university physics lab or from some other source. When you have it, the exact value of the stock resistor is checked on the bridge, and then spot calibrations are made.

Since this main control has no "zero" point where the potentiometer is fully clockwise or counter-clockwise, it is necessary to make a reference mark in case the knob has to be removed. Turn the knob to either extreme and mark a reference point.

In the unit pictured in Fig. 1, part of the calibrations are on the skirt of the knob, referring to an arrow on the panel, and a mark can be seen on the knob skirt beyond the "1000" mark. When the potentiometer is fully counter-clockwise, the knob is placed on the shaft so that this mark aligns with the top arrow on the panel itself.

If a skirted knob is used as shown, part of the scales can be on the skirt, referring to an arrow on the panel, and part on the panel, referring to an arrow on the knob skirt. Another means would be to paste a piece of paper on the panel and use a knob with a clear plastic pointer (with a hairline scribed on it) to indicate the scale. If it is desired to maintain the black face of the panel and yet make scales on it, the figures can be lettered directly on the panel using Johnston's "Snow White" ink.







Because of the single range-function switch (S₁), the unit is simple to use. With the exception of the Ratio range, all connections are made to the "Capacitor Test" terminals. In bridge tests, the main knob (R₁) is turned slowly for a null, and in the "Short" and "Open" tests, no manipulation is required. When checking capacitance values, attach the capacitor directly to the terminals instead of using leads which might have some inherent capacitance. For "Open" and "Short" tests, leads may be used. The binding posts on the front panel of this unit will take plugs as well as wires.

MATERIALS LIST—CAPACITANCE CHECKER

- R1 1 meg., 1%
- R2 10,000 ohm, 1%
- R3 100 ohms, 1%
- R4 15,000 ohms, 4 watt (Mallory M15MKP or equiv.)
- R5 4000 ohm, 1 watt
- R6 1 meg., 1/2 watt
- R7 2.2 meg., 1/2 watt
- R8 2500 ohm, 1/2 watt
- R9 50,000 ohm, 1 watt
- R10 1 meg., 1/2 watt (included in Amphenol Eye Assembly—see below)
- R11 See text
- R12 5 meg., 1/2 watt
- C1 10 mfd., 300-volt electrolytic (see text)
- C2 1 mfd., 5% (Cornell-Dubilier Type 6100)
- C3 .01 mfd., 5% (Cornell-Dubilier Type 1DR or 1AD)
- C4 .0001 mfd., 5% (Aerovox Type 1469)
- C5 .5 mfd., 200 volt
- C6 270 mmfd., 400 volt mica
- C7 200 mmfd., mica
- C8 75 mmfd., mica, 300 volt
- C9 Included in T₁
- C10 .01 mfd., mica, 300 volt
- C11 10 mfd., 25 volt
- C12 .05 mfd., 300 volt
- C13-C14 8-8 mfd., 450-volt electrolytic (Sprague PLS-88, Mallory SR638)
- S1 6 pole, 10-position rotary switch (Mallory 1361L)
- S2 SPST toggle
- T1 21 mc. TV converter transformer (Miller #6185)
- T2 480 v. C.T. @ 55 ma., 5v & 6.3v. Fil. (Stancor PC-8402)
- V1 12AU7
- V2 6E5
- V3 6X5
- L1 6 hy. 50 ma. choke (Stancor C-1707)

Amphenol MEAG Tuning eye assembly
 2 x 7 x 9" chassis
 8 x 8 1/4 x 10" cabinet (Bud C-1789)
 Binding Posts, Knobs, AC cord, tube sockets & shields, etc.

Giving Old Radios a New Look

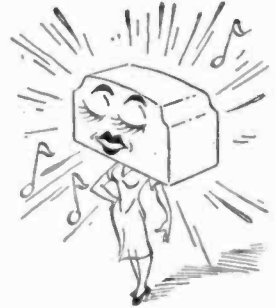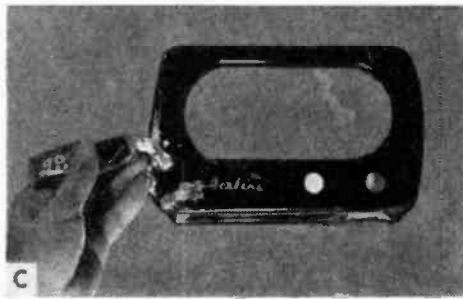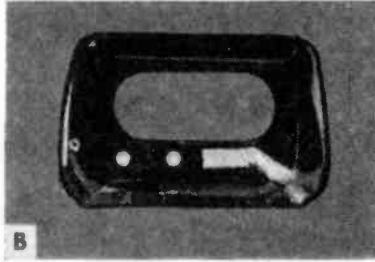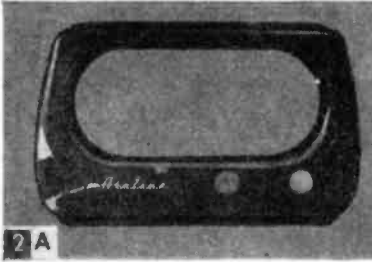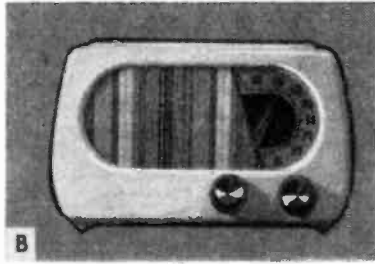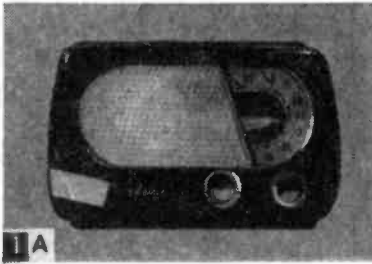

MOST families have an old table model radio around the house that looks terrible. Chances are that it has had a fall or two and that the plastic cabinet has some cracks in it, possibly even some holes where lost pieces were not retrieved. Quite often, a radio which has been dropped once or twice is abandoned in the garage or the attic—although it may still perform satisfactorily as a receiver. If you have a set that has met this fate, dig it out and devote a few hours to fixing it up. The finished product can look better than the original. (If you don't have such a set, table model radios with broken cabinets can be obtained for \$2 to \$5 at many used furniture or second-hand stores. Add a little of your time and less than a dollar's worth of materials to them and you have an extra radio for the kitchen, a child's bedroom, or a summer bungalow).

The radio shown in Fig. 1A cost \$2. It wasn't working, but I didn't mind since I knew I could repair it myself. If it had been working, it would have cost \$3 or \$4. The cabinet was a drab brown; the grill cloth, tan.

I removed the radio from the cabinet by loosening

two screws at the rear. Most radios have three or four additional screws which can be loosened at the bottom of the cabinet. Tuning knobs usually just pull off their shafts, but in some of the older radios, they're held by small set screws.

Next I removed the celluloid dial face which was fastened with snap fasteners, and the cardboard speaker baffle and grill cloth assembly, which was also fastened with snaps, and set them aside.

The stripped plastic cabinet was then soaked in lukewarm detergent water, scrubbed, rinsed and allowed to dry. The cracks were filled with cement (Duco or Pliobond) forced together, held with twine, and allowed to dry. When the cement had dried I reinforced the cracks with masking tape on the inside, bottom and other less obvious points on the cabinet as shown in Fig. 2B. I used a piece of masking tape along a back edge of one of the sides where a piece of the cabinet had been cracked out and lost. This broken edge could have been built up on a wire screen base, but I didn't feel that it was worth the effort. This portion of the cabinet is rarely noticed and the masking tape patch was later concealed by paint.

Next, I filled in gouges, places where chips had been lost from the cabinet, and glue seams with plastic wood (Fig. 2C). I built the plastic wood up well above the remainder of the cabinet surface so I could sand it down smooth with the surface. Since plastic wood shrinks when it hardens, I had to make several applications. (On the first application I used too much plastic wood and the surface hardened and sealed the sub-surface so it couldn't dry and harden. If this happens to you, pin-prick the surface of the plastic wood.

When the plastic wood hardened, I sanded it down smooth with the cabinet surface. If, after you've finished sanding, you have some doubts about any of the surface being smooth, refill again with plastic wood and repeat the sanding process. Next, clean the cabinet with a damp cloth first, then a dry one to remove dust left by the sanding. The repaired cabinet is shown in Fig. 2A ready for painting. Paint can be sprayed on or applied by brush. If you did a good job of filling and sanding, one coat will do. Choose color to suit the surrounding in which the radio will be placed.

During one of the waiting periods in the cabinet repair and refinishing procedure, I removed the old grill cloth from the speaker cardboard baffle and replaced it with a new, many-colored, striped cloth, that would blend with almost any

surrounding. (The cabinet was painted light gray for the same reason). The new cloth was cut using the old one as a pattern, and was fastened to the cardboard with mucilage. The mucilage was applied sparingly to prevent it from soaking through the cloth and spotting the front side of the new grill.

I cleaned the old tuning dial face and knobs with a damp cloth. Refinishing the dial is undesirable from the standpoint of the difficulty in doing a good job and the time involved. Refinishing the knobs is undesirable because painted knobs may eventually become tacky and unattractive.

Finally, I reassembled the radio. The finished product shown in Fig. 1B leads me to believe that my time (about an hour) was well spent.—F. H. FRANTZ, SR.



Circuit Substitution Board

WHEN working on a radio or TV set, it is often necessary to temporarily substitute a replacement capacitor or resistor in a circuit. Usu-

ally this means bending the leads *just* so and substituting the part directly, an awkward process that often results in shorting out the circuit with the bare leads.


Substitution is greatly facilitated by mounting a pair of alligator clips and pin jacks (red and black for polarity) on a piece of hardboard. Then a new component can be tested in the circuit simply by placing it in the clips and running test leads to its connections.

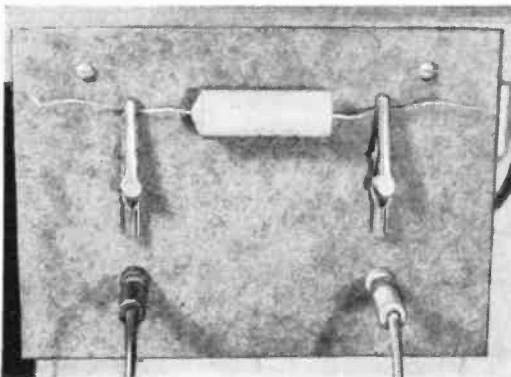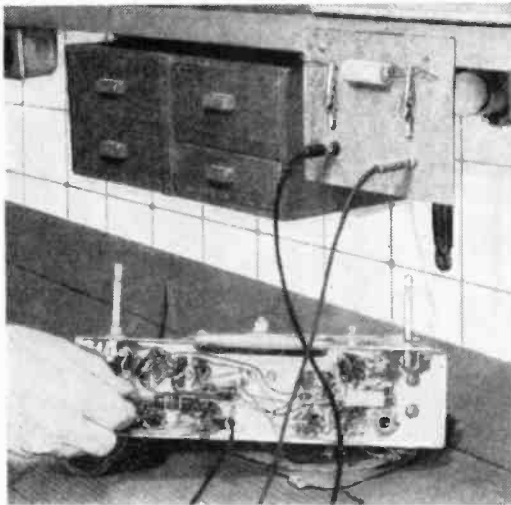Mount clips with moveable jaw up using small machine screws set about 3½ in. apart. Mount board over bench within easy reach.—H. Y. M.




Paper Clips Grip Test Wires

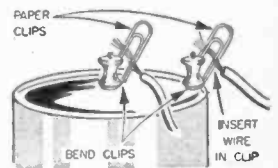● Bend paper clips at right angles and attach to the posts of a dry battery as illustrated, for quickly attaching wires used in low-voltage testing jobs.—G. E. H.




Transistor Soldering

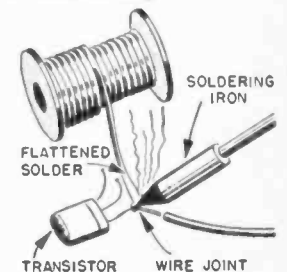● When soldering a transistor into a circuit, there is always the hazard of overheating the component through heat conduction. To eliminate this possibility, hammer the end of the solder flat. This will allow it to melt almost instantly at



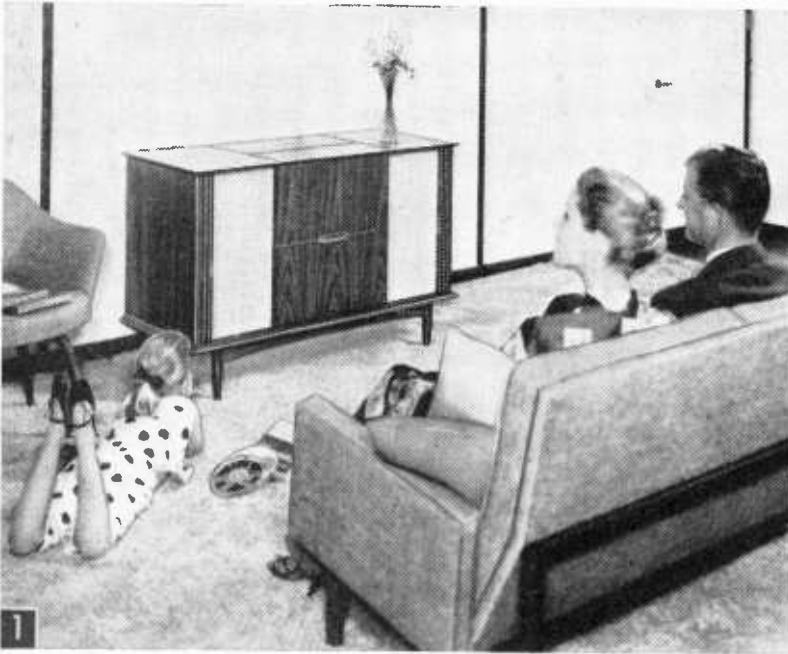the touch of the iron, reducing the amount of heat needed to solder the joint.—J. A. C.



A complete stereophonic home music system, the Ampex Crescendo Console has a tape recorder-stereophonic reproducer, two separate speaker-amplifier systems, an AM-FM tuner, a four-speed record changer and a microphone.

STEREOPHONIC SOUND

By TOM JASKI

STEREOPHONIC sound has been called the "ultimate" that modern technology offers to the discriminating music listener; it has added dimension and depth to music and given a living, moving quality to sound available otherwise only at a live concert performance.

Bell Telephone Laboratories demonstrated stereophonic sound more than 25 years ago, picking up a live program with two microphones and conveying it over two separate telephone circuits to a concert hall where the two signals were amplified and fed into two specially designed speaker systems. (Leopold Stokowski, conducted the Philadelphia Symphony Orchestra for this experiment.)

A more recent event in the evolution of stereophonic sound took place in 1956 in San Francisco's War Memorial Opera House, the San Francisco Symphony Orchestra performing. At least so far as the audience could tell, the orchestra was playing, but in the middle of the performance the musicians laid down their instruments, the music went on, and the


audience learned that they had been listening to a previously recorded stereo tape, the musicians faking their instrumental efforts.

Stereophonic—or binaural sound has been in use commercially for several years in movie theaters where it adds to the lifelike quality of Cinemascope and other wide-screen film techniques. It has been only very recently, however, that equipment and tape manufacturers began to focus attention on consumer markets. But they have now entered the field with such enthusiasm, and are offering such a wide variety of equipment, that the pleasures of stereo sound are presently within the budget of almost everyone.


What Is Stereophonic Sound? Although we



2 SOUND REACHES THE LEFT EAR SOONER

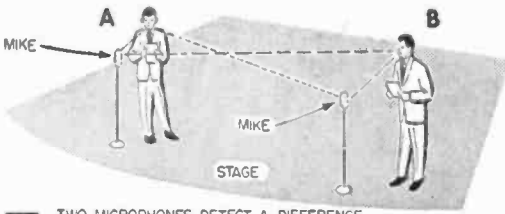

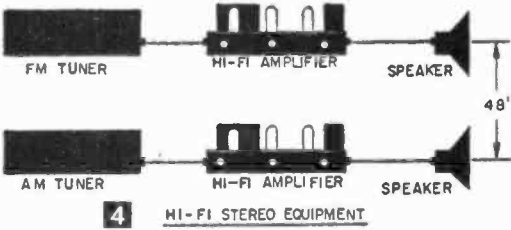3 TWO MICROPHONES DETECT A DIFFERENCE IN SOUND COMING FROM A AND B



4 HI-FI STEREO EQUIPMENT

normally pay little attention to the phenomenon, practically all of us can determine with fair accuracy the direction from which a sound comes. Sound has to travel a different distance to reach each of our ears and thus it differs slightly in loudness and phase at each ear (see Fig. 2). As infants, we learned to interpret this difference so that we could determine the point of origin of sound; if a sound moves from one place to another, we are capable of detecting this motion.

In Fig. 2 the sound from the speaker source has to travel a slightly greater distance to reach the right ear of the listener than it does to reach the left ear. The distance from the source to the left ear in portions equal to the wavelength of the sound at a specific frequency is three wavelengths; the distance to the right ear is three and one-half wavelengths. Thus, there is not only

a difference in the loudness of the sound reaching the two ears, but also a phase shift of 180 degrees. The faculty that enables the human brain to use these differences in phase and loudness to determine full direction is called binaural hearing.


When recording with a single microphone (which is reasonably directional) the microphone may detect a slight difference in loudness, but it is incapable of providing any significant indication of phase difference. When making a recording with a single microphone, the sense of direction and the sense of motion are almost completely lost except that we can still tell whether or not the source of sound is approaching or receding from the microphone.

If we reproduce the sound recorded with a single microphone through a single amplifier channel and speaker, we compound the difficulty. Some of the dynamic range caused by the variation in distance from the microphone to the sound source will be lost in the recording and the reproducing system and the reproduced sound will have even more of the characteristics of a single point source of sound.

If two microphones are mounted on a stage at a considerable distance from each other, however, and we record individually what each microphone picks up, we have a different story, (see Fig. 3). There will be a difference in the loudness and the phase of the sound reaching each microphone and if we make two separate recordings, each fed by one of the microphones, and then play the two recordings back through two amplifiers and two physically separated speakers, any sound from a moving source will appear to be moving in the room in which we are listening. In the dual recording of an orchestral performance, for example, the reproduction will pro-



5

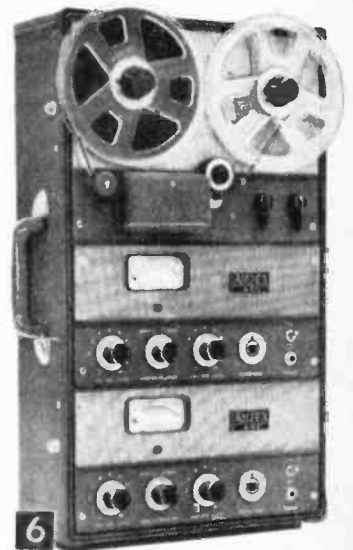

6

Fig. 5. This stereophonic system, the Ampex A121, includes a tape recorder-stereophonic reproducer and two matched speaker-amplifier systems. Fig. 6. The Ampex 601 for the professional audio engineer and the semi-professional who takes his stereo recording seriously and is willing to pay the price for high quality.

TABLE A—STEREO EQUIPMENT

The following list gives a sampling of equipment of interest to the audiophile:

Ampex Corp., 934 Charter Street, Redwood City, Calif.
 Viking, 9600 Aldrich Ave. S., Minneapolis 20, Minn.
 VM Corp.,* Benton Harbor, Michigan
 Berlant Concertone, 9449 W. Jefferson Blvd., Culver City, Calif.
 David Bogen Co. Inc.,* P.O. Box 500, Paramus, N. J. (pre-amplifiers)

E.M.C. Corp., St. Paul 6, Minnesota
 Wolfensak,* 320 East 21st Street, Chicago 16, Ill.
 Pentron Corp.,* 777 S. Tripp Ave., Chicago 24, Ill.
 RCA (Victor), Camden 2, New Jersey
 * adapters
 (The Harrison Publishing Company prints a catalog of available tapes, listing over 50 recording companies. The catalog can be obtained from your hi-fi dealer or from the Harrison Co., 274 Madison Ave., New York 16. Here are some of the companies listed:

RCA VICTOR	PENTRON
EMC	NATIONAL
WESTMINSTER SONOTAPE	MERCURY
HIFITAPES	OMEGATAPES
BEL CANTO	STEREOPHONY INCORP.
CELESTIAL	WEBCOR)

vide us with the same sense of direction we would have if we were in the concert hall, hearing one instrument from one place on the stage and another from the other side, and some from the middle. This is stereophonic sound reproduction.

We need not limit ourselves to orchestral music to enjoy the benefits of stereo reproduction. Even a recording of a group conversation will give us the feeling of audio perspective when it is played back. We might, for example, hear conversations from one corner of the room; or steps moving down the hall; or the sound of cars passing by.

Program Sources. Obviously, most of us will not have the opportunity to set up stereophonic recording equipment at a concert. But fortunately there are several companies which make two-channel stereo tape recordings. They offer thousands of selections of every type of music, from Brahms to Beethoven to Dixieland jazz. (Most stores that sell phonograph records are beginning to stock stereophonic tape.) In addition, a number of radio broadcasting stations have inaugurated the practice of weekly stereophonic concerts. This is done by stations which transmit the same program, but over two separate broadcast channels, simultaneously on AM and FM. The listener picks up the program on both channels simultaneously with separate radio sets, and thus obtains the benefit of stereophonic sound. (Programs may be taped or live, or both.)


The minimum amount of equipment that can be used to listen to such programs is two radios, one an FM receiver and the other a standard AM broadcast receiver, each picking up one channel of the dual-channel program. Set them about four feet apart in the same room. Even with inexpensive table model receivers, the results are thrilling.

Figure 4 shows a somewhat more elaborate set-up, one that will appeal to high-fidelity enthusiasts: two tuners, one an FM tuner and the other an AM tuner, two high-fidelity amplifiers



and two speakers (again placed about four feet apart in the same room). By adding a suitable tape reproducer to the equipment shown in Fig. 4 you can enjoy taped stereophonic programs.

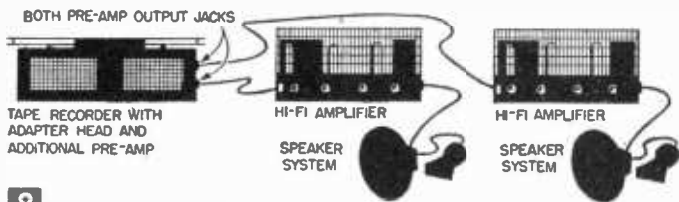Stereophonic tapes have two sound tracks, each recorded through an individual recording channel. Each half of the tape carries one-half of the recorded program. Standard stereo tapes sold today for home use are recorded at a speed of $7\frac{1}{2}$ inches per second. Almost all home tape re-



orders are dual speed types, providing tape speeds of $7\frac{1}{2}$ ips and $3\frac{3}{4}$ ips. For reproduction of commercial stereo tapes, a special dual head which will pick up the program from both tracks of the tape simultaneously, or in some cases, two heads, one for each of the two sound tracks on the tape, plus a separate pre-amplifier for the second channel, are required.


This may sound like an expensive proposition; sometimes it is. The Ampex Crescendo Console, shown in Fig. 1, for example, costs almost \$1500; the Ampex A121 system (Fig. 5), and the portable Ampex 601 (Fig. 6) for the professional and semi-pro, \$995.

Similar systems at slightly lower prices, are produced by RCA, by the Berlant Concertone Audio Division of American Electronics, Inc. and by Viking. For most of us, however, these are likely to be astronomical outlays.

But let's see what can be done with much slimmer budgets. To begin with, if we own any late model tape recorder providing $7\frac{1}{2}$ ips tape speed that can satisfactorily reproduce music, we already have half of a stereophonic system. Today, several manufacturers of inexpensive and medium priced home recorders are producing adapter kits to convert their recorders for stereophonic tape. Pentron, for instance, offers a conversion kit for \$16.95 consisting of a pre-amplifier, extra head, cable and mounting hardware, complete with instructions, for converting your present tape recorder to stereo.

There are two basic kinds of stereo tape recordings, one type for use with separate heads, the other for use with dual heads. For tape players with a single dual-track head, the re-

ording companies are producing tapes with "stacked" program channels. This means that the two tracks on the tape are perfectly aligned, one above the other, so that there is no displacement in time. When an extra head is used in addition to the existing head, we need a "staggered" type of recording in which the program tracks are displaced by the distance between the centers of the two heads, so that they still reproduce the program with no displacement in time. Any discrepancy in the timing of the two tracks would of course cause very unpleasant results. It would give the same effect as if the musicians in the orchestra failed to keep in time with each other. Tapes for both "stacked" and "staggered" heads are commonly available.

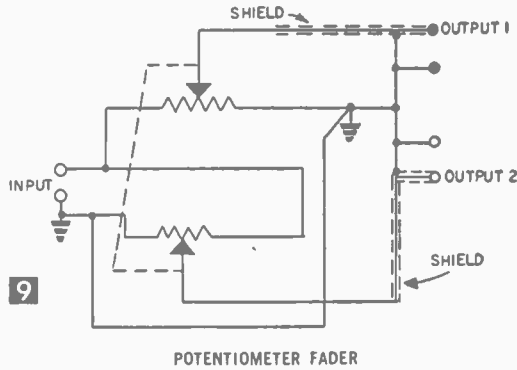

POTENTIOMETER FADER

Suppose then, that we have an existing tape recorder of satisfactory quality for which we can get a conversion kit. The kit will generally include a pre-amplifier for boosting the signal from the second track. The output of this pre-amplifier is fed to the second power amplifier which has its own speaker system (see Fig. 7). Here one-half of the program is reproduced through the tape recorder directly and the other half through the power amplifier and speaker. The quality of this set-up is limited by the quality of the speaker and amplifier in the tape recorder. Most home type tape recorders use only small speakers in the interests of portability.

A more elaborate and undoubtedly a more satisfactory arrangement is shown in Fig. 8, where the signal from both tape recorder pre-amplifiers is applied to two identical power amplifiers. This, within limits set by the amplifiers and speaker systems, and, of course, by the quality of the heads in the tape recorder, provides the next best thing to a completely engineered stereophonic sound system.

Speaker Placement. Considering the size and the acoustics of the concert hall or the broadcast studio where musical programs are recorded on tape, it is not difficult to understand that it is almost impossible to duplicate the same acoustical conditions in a living room. The placement of the speakers of a stereophonic system in a room cannot be considered as an exact science; in the final analysis it will be the listener who has to determine his preference between the several possible speaker placements.

If you want to provide a dramatic demonstration of stereophonic sound effects, place the loudspeakers as far apart as possible along one wall of the room, facing into the room at a slight angle. The apparent motion of the sound from

one corner of the room to the other will then be very obvious. This type of speaker placement in rooms with hard acoustical surfaces may, however, allow enough diffusion of sound from reflection of wall to ceiling to cause loss of a great deal of the stereophonic effect.

At the other extreme, with the speakers placed close together, no matter at

what angle we set the speakers most of the effect of the stereophonic reproduction will be lost. In general it has been found that a spacing of four feet between the speakers tends to give the most satisfactory results. For best results, of course, you should experiment with the actual equipment and judge for yourself what spacing and arrangement of speakers produces the most desirable results.

Stereophonic sound system speakers may be built into a home as in conventional hi-fi systems, but careful experimentation should be conducted before cutting holes in the wall to house the speakers. In built-in installations, care must be given to the problem of possible acoustical feedback from one speaker to the other inside the structure of the wall. There is also the unpleasant possibility that the two speakers might produce sufficient acoustical power to cause resonance in the wall at the lower frequencies.

The importance of the quality of the speakers and the speaker housing for true high fidelity reproduction is, if anything, more important in stereo sound than in conventional systems. Any spurious resonance or natural frequency in the speaker or baffle will obviously emphasize undesirable characteristics. You might find that such a simple thing as throw rugs on the floor or drawn draperies, produce a noticeable effect on the quality of reproduction. Arrangement of furniture and variations in the number of people in any room may also contribute one way or another to the result.

About the only specific thing that can be said about speaker arrangements is that the best results can only be determined by actual experimentation with the equipment in the room in which it is to be used and with the furniture arranged as you expect it to be.

Operation. Careful adjustment of amplifier volume and tone controls will always be necessary, no matter what equipment you use. If the equipment is to be used for monaural reproduction as well as binaural, keep a record of the control settings for stereo reproduction, so that the adjustments will not have to be experimented with each time.


You can test your stereo system with a test

tape. Such a tape is similar in content and function to hi-fi test records. Sono tape #SWB-AL101 is typical; recorded on it are the tests necessary to check the tape player with stacked heads as well as the other components of the system. With the tape comes an instruction manual explaining these various tests in detail. The tape contains such things as single-frequency tones on each track alternately, a 3000-cycle tone for wow and flutter checks, and a 440-cycle tone for checking left and right speaker connection; equalization and loudness; correct speaker placement; transient response; distortion; and very high volume. The test tape was produced for standard NARTB playback equalization characteristics and contains spoken instructions to let the listener know whether the sound should come from the left or right. (For recording purposes it should be remembered that the microphone placement should correspond with this arrangement.)

Making Your Own Recordings. Careful attention must be given to microphone placement. Too wide a separation between microphones will produce a dead area when the sound moves from the range of one microphone to the other; too close a spacing between microphones will reduce the effects you are aiming for. Correct microphone placement depends upon the type of recording you are making; a ping-pong game requires a different set-up than an orchestral performance.

Always remember that you are dealing with two recording tracks. It is possible to make up to a certain extent for the deficiencies in the recording of one track or another by adjustment in the reproduction system, but this is doing it the hard way. The more nearly you achieve equality in the level and tone range on the two tracks, the easier it will be to properly reproduce them.

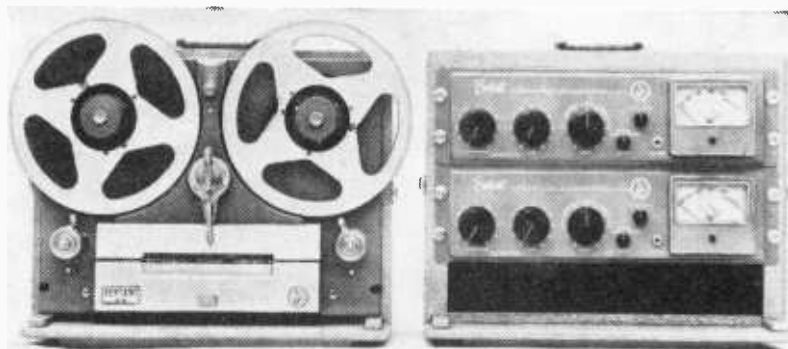If your favorite music is not available on stereo tape, you might be interested in making simulated stereophonic recordings from phonograph



10

Above, the portable stereo unit made by Berlant Concertone; on the left, Viking's portable unit.

records or other single-channel sources. In order to do this you can use the right-left-middle fader shown in Fig. 9. This consists of two ganged potentiometers with linear taper and the necessary jacks. For low-impedance sources, such as the output of some tuners, or the voice coil of terminals of existing amplifiers, the potentiometers should be about 10,000 ohms each. For high-impedance sources, such as pre-amplifiers, the potentiometers should be one-half megohm. If


high-impedance potentiometers are used, all leads must be carefully shielded. When you re-record the music, adjust the potentiometer to make the music come either from the left or the right or the apparent middle.

Another way to accomplish a similar, pseudo-stereophonic effect is to feed the single channel signal to two amplifiers, one of which has the treble turned up and the bass control down while the other favors the basses. The result will be an apparent separation between the bass instruments and the treble instruments.

A stereo set-up, in addition to providing stereo reproduction, can also be a lot of fun in other experiments. For example, while recording one channel, it is possible to dub in comment on the second track which, when played back, will be heard simultaneously with the music. This can be useful in some types of instruction or educational work. If you have a recorder with staggered heads you can feed part of the signal from the second head into the same final amplifier as the first head to produce an artificial echo. When you do this, remember that each pre-amplifier has a bias oscillator and that if improperly adjusted, the bias oscillators may produce a beat or whistle in your recorder when you use them for special effects (such as the special echo).

Mazda Lamp Resistors

By T. A. BLANCHARD

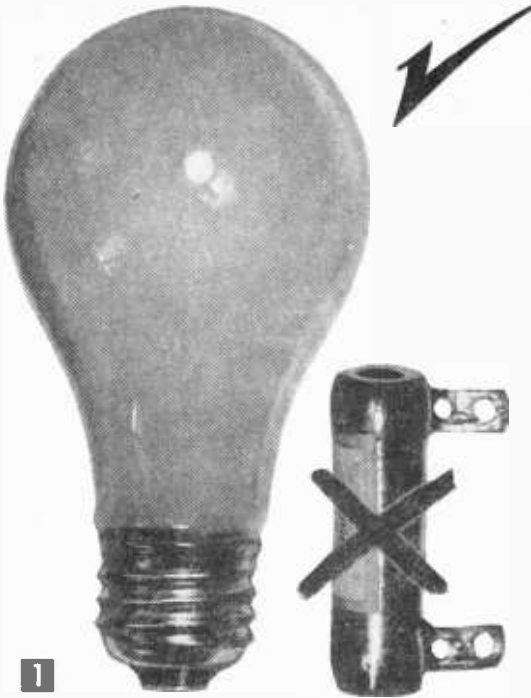

1

While larger than wire-wound resistors, Mazda lamps provide voltage-drop resistance and yield useful illumination at the same time. This 60-watt lamp can handle almost three times the load of the ex'd-out 75-ohm resistor.

LIGHT BULB resistors eliminate stepdown power transformers when building and experimenting with small sets. Ten lamps provide ten useful resistance values.

You may have noticed how carefully tube manufacturers work out the filament operating voltages of tubes employed in compact ac-dc type receivers. In a standard five-tube receiver, there are three 12-v. tubes, a 35-v. tube, and a 50-v. tube. Adding up these filament voltages you will find the total is 121. Simply by wiring each tube in a series string (just like many older Christmas tree light strings) the tubes can be operated directly off the domestic power line (105-125-v.) without need for a bulky step-down transformer.

Some compact sets employ only 4 tubes. In these sets, the manufacturer must lose 12-v., otherwise tubes would burn out. To lose the 12-v., a voltage-drop resistor is inserted in series with the tubes. In a modern four-tube set, a 75-ohm,

5-watt resistor will breach the gap caused by the absence of a fifth 12-v. tube.

Where the required voltage-drop is small, a resistor is not objectionable, and many manufacturers use ordinary carbon 2-watt resistors in series with the tubes for satisfactory results. Instead of the large 75-ohm wire-wound unit, a 33- and 39-ohm carbon resistor (total: 72 ohms, 4 watts) is employed.


Experimenters can apply this method to small sets—even one-tubers! However, as the voltage drop increases, the wattage rating of the resistor often increases so much that a very bulky unit is required. In addition to the size, a high-voltage dropping resistor becomes quite hot, affecting other components.

Since any voltage-dropping resistor is a total loss from standpoint of efficiency, the experimenter might as well get something for his money—that something is light! For practically any experimental application, ordinary Mazda light bulbs make excellent voltage-dropping resistors. Moreover, where a particular resistance and wattage rating isn't immediately available, you needn't kill time shopping for the necessary unit.

Table A lists all standard Mazda lamps from 150 down to 6 watts and the approximate resistance rating of each lamp size (when hot). After computing the required voltage-drop required for a particular circuit, select a lamp having a resistance as close to the computed drop as possible. The lamp can be within 10% plus or minus.

TABLE A
MAZDA LAMP RESISTANCES

Mazda Lamp WATTAGE	Resistance in OHMS
150	88
100	132
75	177
60	221
50	240
40	329
25	518
15	802
10	1321
6	2210

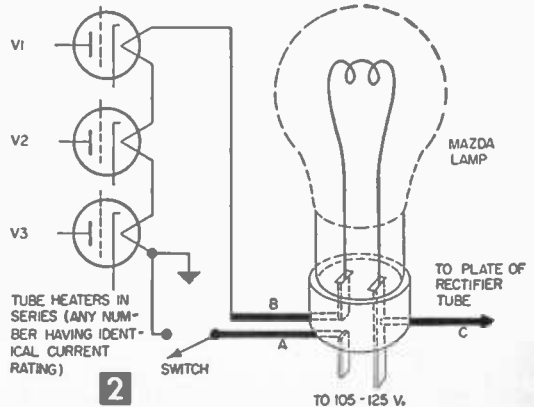

Unlike a carbon or wire-wound resistor, the Mazda lamp exerts a unique "shock absorber" action in the tube string. The lamp takes the initial inrush of current when the set is turned on, rather than letting it fall upon the more costly tube heaters. You'll note that the Mazda lamp comes on at full brightness, then dims off as much as 50% as the radio tubes reach operating temperature. Thus, you have a built-in surge absorber.

A Mazda lamp is more bulky than a resistor, of course, but it gives off useful light rather than damaging heat, and it is a cheap, quick solution for resistance problems in addition to its versatility. A small bedside radio with two or three tubes may be designed to fit in the base or housing of a table or bed lamp. You'll have a radio that costs almost nothing to operate, since the radio circuit consumes barely 10% more current than the lamp alone!


Figure 3 shows a novel cord plug known as a "series tap." This plug resembles any ordinary plug, except that it has a female outlet in the cap. One side of the power line supplies both the receiver itself, its rectifier tube and the lamp, plugged into the top of the series tap (Fig. 2); the other side connects to B-minus in the radio and the end of the string of tube heaters operating in series with the lamp plugged into the series tap.

A separate On-Off switch for small radios operated in this manner is unnecessary. Merely turning off the table or bed lamp switch shuts off the radio. Very little current, if any, is drawn by the set with "cold" tube heaters (radio off).

When constructing or converting a set (not already designed with series filaments) the experimenter must observe this precaution—all tube heaters must have the same amperage rating. Check the ratings in a tube manual. If you find that two tubes are .15 amp and one is .3 amp, you cannot wire these tubes in series without a complicated shunt system. Select a similar tube in the manual with a .15 amp heater to match the other tubes. Or, if two tubes are listed as .3 amp, change the remaining .15 amp tube to a type with .3-amp heater. Any set already designed with series heater tubes does not pose this problem; simply select a Mazda lamp with a resistance near that of the wire or carbon resistor unit indicated in the set's schematic diagram.

To compute the voltage drop required for a particular set, follow these three steps:

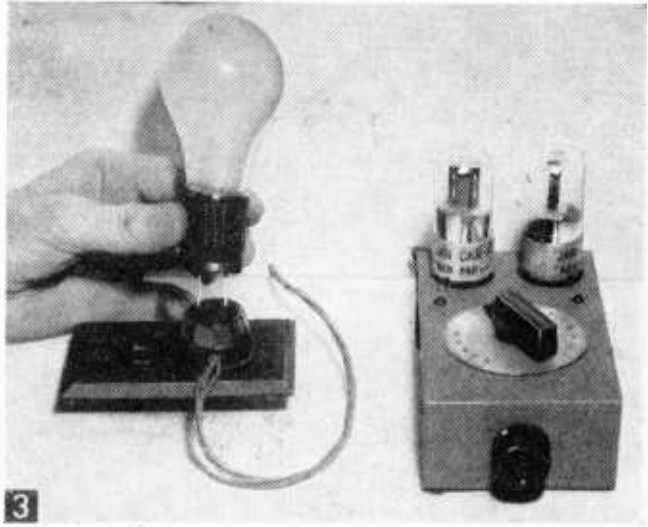- 1) Determine from the local power company, the peak line voltage in your locality.
- 2) Add up the operating voltages of each tube in your circuit. Subtract the total from the line voltage.



Small radio or other electronic devices can be fitted with 3-wire cord and series tap. Tap is plugged into outlet, then Mazda voltage-dropping lamp plugs into series tap for operating tube heaters.

- 3) Divide the current rating of the tubes used into the remaining voltage after subtracting total of tube voltages in step 2. Answer: resistance in ohms required for line-drop.


For example, let us assume that your power company delivers 120 volts into your home. You have constructed a set with just two 6.3-v. tubes. Each tube draws .3 amperes. Adding up the tube filament voltages totals 12.6 v. Subtracting 12.6 v. from 120 leaves 107.4 v. Now, divide .3 into 107.4, giving the required voltage dropping resistance of 358 ohms.


Checking the lamp resistances in Table A shows that a 40-watt bulb has a resistance of 329 ohms. Since this value is within the 10% tolerance, it is the right size to use.

You can use lamps for resistors when operating motors, buzzers, low-voltage bulbs, or when testing electrical circuits. If you don't know the current rating of such apparatus, start with a 10-watt Mazda lamp, working up to higher wattage lamps until the device functions at proper speed or intensity. With their almost unlimited versatility, you'll find that an assortment of ten Mazda lamps is one of the best buys you can make.

Quick Wire Connections

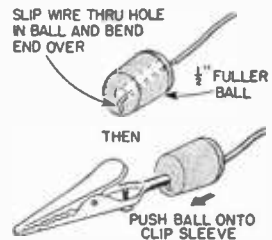- To make a quick and secure wire connection to an alligator clip without soldering, use a ½-in. rubber Fuller ball, which has a hole just the right size for this purpose. This also saves the threads on clips with terminal screws, which tend to strip threads.—A. TRAUFFER.



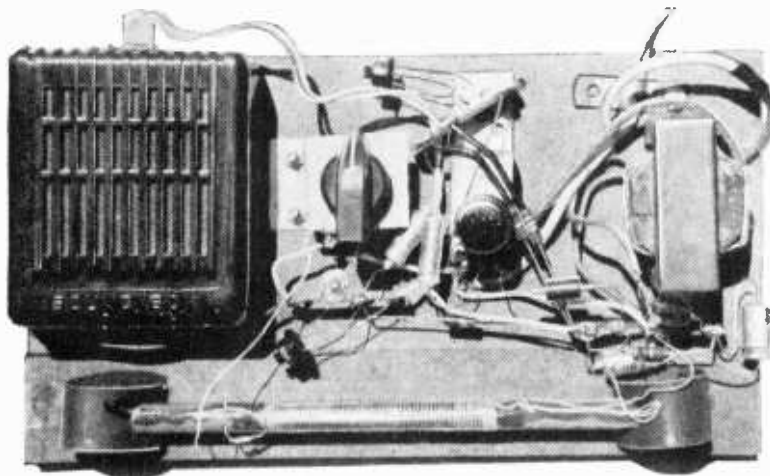

The two transistors used in this powerful little set use, together, less than 1/4 watt of power.

as a power supply rectifier. It can perform in this infrequently seen application because the current and voltage demands of the two transistors used are small.

Construction. The tie-rack radio can be built in two or three hours. And it was designed to be safe because my youngsters will be using it.

The base for the set is a piece of Masonite 4 3/4 x 9 in. Figure 2 gives the hole placement for the components designated in the Materials List.

Tie-Rack Radio

By FORREST H. FRANTZ, SR.

"IT LOOKS like a tie rack," was my first thought when I saw the high-Q transistor loop antenna used here. You may get your ties slightly snarled up in circuit components if you try to make this radio double as a tie rack, but you'll never get a snarl up on set performance. Room-filling loudspeaker volume without an outside antenna, good selectivity, short construction time, and low cost are the outstanding features of this two-transistor radio.



The outstanding performance of this simple set results from utilizing some basic knowledge, the "tie-rack" antenna, and some novel construction techniques. The basic knowledge referred to is something any experimenter who's ever built a battery receiver has learned. Namely: a battery radio which performs poorly with a short antenna will perform well against ground. The tie-rack radio has a return to ground through the 6.3 v transformer and the ac line which provides operating power.

The tie-rack antenna, a transistor loop antenna with a Q of 450, is as essential to this receiver's outstanding performance as the indirect ground. The high Q (quality factor) of this antenna assures sensitivity and selectivity far in excess of that possible from a simple crystal diode circuit with a more ordinary antenna coil. A short length of wire—about 12 in. long in metropolitan areas, to 36 in. in areas more remote from radio stations—is all the antenna that's required.

Note also the use of a crystal diode

The most rapid construction sequence to follow is:

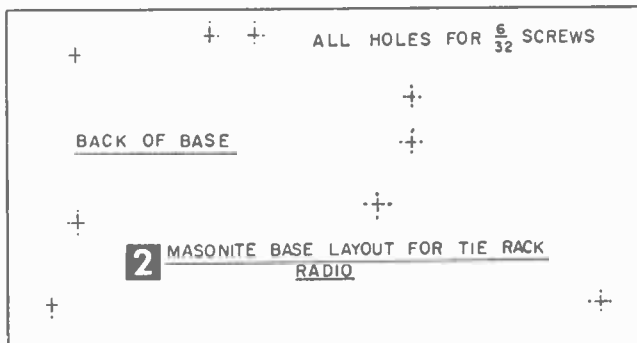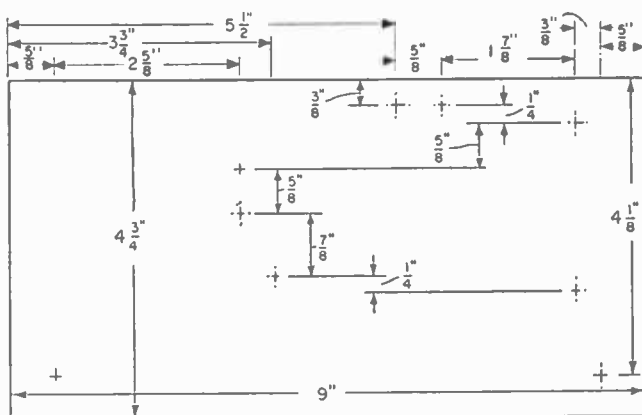- 1) Cut and drill the Masonite panel.
- 2) Mount tuning capacitor C1 and volume control R1 on their brackets.
- 3) Solder one lead from the ac line cord to one lead from the transformer TR2. Tape the splice. The other lead from the line cord and



transformer TR2 primary lead connect to the switch SW terminals on R1. (In soldering connections to miniature components, diodes and transistors, apply heat for shortest possible amount of time and use pliers between soldering iron and component as heat sink.)

4) Mount transformer TR2, volume control R1, and tuning capacitor C1 on the base. A metal clamp under the upper transformer mounting screw holds the line cord in place. The four-terminal connection (tie-down) strip is fastened under the other transformer mounting screw. A three-terminal tie-down strip is fastened with the volume control bracket mounting screw.



5) Mount the loop antenna L1 and the remaining three-connection tie-down strip on the board as shown in Fig. 3.

6) Wire the power supply (secondary of TR2, D2, R5, C4, and C5) being careful to connect D1, C4 and C5 for correct polarity. To avoid mistakes in wiring, go over each connection on the circuit diagram (Fig. 4) with a red pencil as you make the connections.

7) Wire the detector circuit (L1, C1, D1 and R1).

8) Wire the audio amplifier (C2, R2, R3, R4, C3, T1, T2). The leads to the speaker are brought out to a plug furnished with the speaker case.

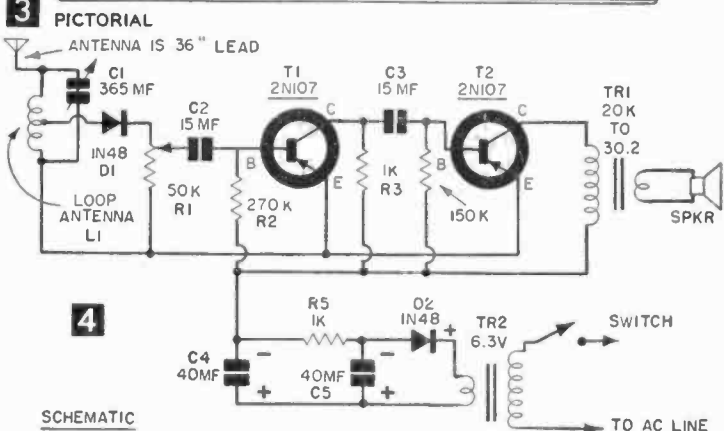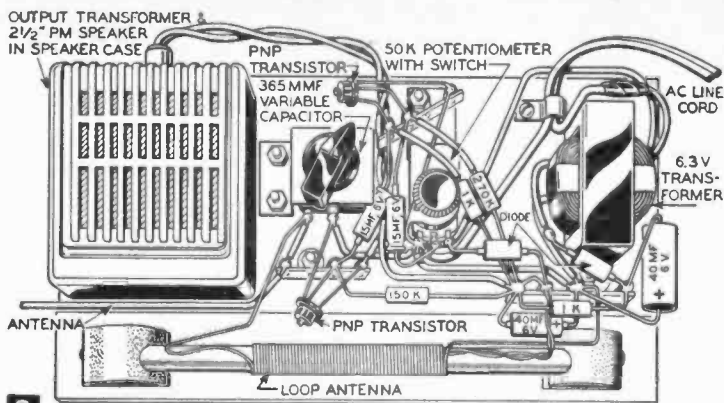9) Wire the output transformer TR1 to the speaker and the terminals in the speaker case. Bend the output transformer mounting lugs out to the side so that a grommet or piece of rubber



3 PICTORIAL

4

SCHMATIC


tape can be wedged between the side of the speaker case and the top of the transformer to hold it in place against the speaker frame (see Fig. 5). Fasten the back of the speaker case to the set out, fasten the speaker case to the Masonite with Duco cement.

Tie-Rack Radio Check Out. Check the wiring and examine connections. If everything looks good, connect a voltmeter (set to 5 v or higher dc range) across C4 with voltmeter connection polarity the same as that of C4. Plug the set's line cord into an ac outlet and turn the switch On. If the voltmeter reads between 3 and 6 v, advance volume control R1 to full volume and touch the center terminal with your finger. A hum indicates the audio amplifier is working, and you're ready to tune in stations. If any of the tests do not give the desired indication, unplug the set and recheck the wiring. Be especially careful that the cases of the miniature electrolytic capacitors do not touch other wiring.

If you can hear a small hum in the loudspeaker when you're tuned off a station with the volume all the way up, connect the volume control mounting bracket to the common emitter return.

The critical component is the antenna coil. But even this may be changed if you use a tapped transistor coil of equally high Q. All other components can readily be replaced by their less ex-

MATERIALS LIST—TIE RACK RADIO	
C1	365 mfd variable capacitor (Lafayette MS-274)
C2, C3	15 mfd, 6v capacitor
C4, C5	40 mfd, 6v capacitor
R1	50K potentiometer w/sw (Lafayette NC-31)
R2	270K, 1/2 watt resistor
R3, R5	1K, 1/2 watt resistor
R4	150K, 1/2 watt resistor
L1	loop antenna (Miller 2000)
TR1	output transformer, 20K to 3.2 (Lafayette AR131)
TR2	6.3v filament transformer (Lafayette 106-01)
SPKR	2 1/2" PM speaker (SK-65)
D1, D2	crystal diode (CBS—Hytron 1N48)
T1, T2	PNP transistor (GE 2N76 or 2N107, or Raytheon CK722)
1	speaker baffle (Lafayette MS-315)
1	line cord
2	knobs
1	Masonite board 4 3/4 x 9"
2	brackets
2	3-terminal connection strips
1	4-terminal connection strip

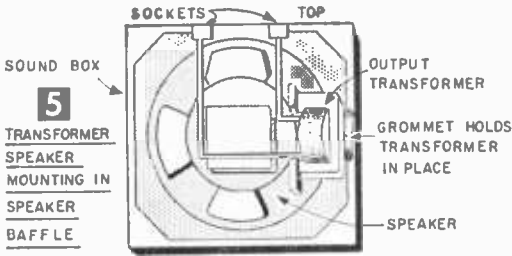

pensive equivalents without appreciable sacrifice in performance. The transistors T1 and T2, for example, can be the inexpensive CK722's. And the output transformer, speaker, volume control, and capacitors can be standard-size components. Figures 1 and 3, for example, show a standard size component in place of the C5 called out on the parts list. If you push economy to the hilt, I believe your Tie Rack radio will materialize for less than \$8!

How It Works. The tie-rack radio employs a crystal diode detector (D1) followed by a two-transistor audio amplifier (T1 and T2). It derives its power from the ac half-wave power supply consisting of TR2 which steps the 110-v line voltage down to 6.3 v, diode D2 which rectifies this voltage to provide pulsating dc, and capacitors C4 and C5 and resistor R5 which filter the pulsations out to provide pure dc for the transistor operating biases.

The short antenna lead and loop antenna L1

pick up RF signals. The setting of C1 determines the frequency to which L1-C1 are resonant. A signal at the resonant frequency is in essence amplified by the combination while signals at other frequencies are rejected.


A tap on the "tie-rack" loop antenna L1 provides a low impedance match to the crystal diode detector D1 which would reduce the circuit Q if connected to the upper end of L1. The diode D1 is non-linear (that is, it allows current to flow more readily in one direction than the other), and rectifies the received signal.

The high-frequency pulsations remaining in the signal after such rectification are filtered by the capacitance of the succeeding circuitry, and an audio signal appears across the volume control R1. The fraction of this signal to be amplified is determined by the volume control setting.

The audio signal is then passed through C2, but dc cannot and the bias established for the base of transistor T1 by R2 is not disturbed. Transistor T1 amplifies the signal. Resistor R3 provides collector operating bias for T1. The signal feeds in turn through C3 into T2 where further amplification occurs. Because the ac primary impedance of TR1 is high, small changes in T2 collector current result in large output signals. The output transformer matches the high-impedance collector circuit to the low-impedance loudspeaker, thus assuring the high voltage gain necessary if this set is to have the high speaker volume it has.

Pointed-End for Radio Ground Pipe

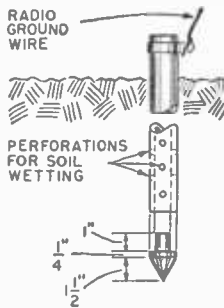- A simple pointed end makes it easier to drive a radio ground pipe. Insert the lathe-turned point into the bottom end of the pipe to keep dirt from plugging the pipe. Holes drilled through the pipe for soil wetting reduce electrical resistance between ground pipe and soil.—ARTHUR TRAUFFER.



For Better TV Reception

- If the voltage on a house wiring circuit drops below 108 volts due to inadequate wiring, the results in terms of TV viewing may be a greyed picture, smaller picture, no picture at all, distorted image, inability of the set to receive weak signals or less satisfactory reception in fringe areas. To get the best reception from your TV set, connect it to a circuit used for lights primarily, rather than to a circuit which serves motor-driven appliances—especially such equipment as the refrigerator, automatic washer and dishwasher. If you still have trouble from low voltage, install a branch circuit for TV use alone.


Plug-in Alligator Clip

- Prods on the ends of test leads may be easily converted to alligator clips. Obtain an insulated alligator clip and one insulated 'phone jack. Then bore clip so 'phone jack will screw snugly into it. With this setup test leads may be used with both prods or with clip and prod.



Plastic Tweezers

- With this plastic tweezers, you can probe for loose connections in a radio or TV receiver. If you make it 8 in. long, it will also prove handy for handling prints in photo solutions. Cut clear plastic (polystyrene, Plexiglas or Lucite) to length, and shape ends as shown. Heat across center with match and bend strip double, allowing 1/4 in. space between halves. Hold until plastic sets, then bevel tips of tweezers with sandpaper or file and smooth all sharp edges.

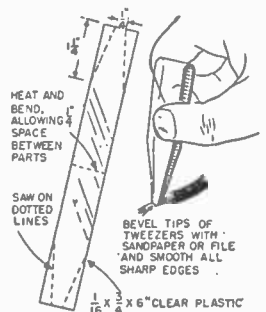

ELECTRIC ETCHER for Marking Tools

By NATHAN BOGOCH

AN ELECTRIC etcher is an exceedingly simple device, and any amateur workman should be able to make one. It enables one to etch permanently upon the metal parts of his tools, not only his name, but also the sizes and numbers of such tools as drills, taps, dies and wrenches. Progressive steps of construction for making the etcher are shown in the drawings below.

First obtain a penholder with a cork or rubber end. Remove this cork or rubber and also the springy piece of metal which originally was intended to hold the pen point in place.

To form a core for what will be an electro-magnet, fill the metal tube with thin iron nails, cut to protrude slightly from the end of the cylinder. Insert enough so that they will be wedged permanently in place.

Now obtain a piece of light spring steel (a watch spring will do) about an eighth of an inch wide and carefully bend it into a "U" shape so that the ends are about half an inch apart. Heat one of the ends and drill with a 1/16-inch drill. Then solder about half an inch of No. 14 copper wire in this hole and file the end to a point. Solder the other end to the end of the nail core.

To make the magnet winding first solder one end of a piece of No. 20 insulated copper wire to the lower end of the metal tube. Then wrap a strip of paper around the tube for insulation and wind 100 turns of the wire upon it. Terminate the other end under a machine screw located just above the metal tube. This completes construction of the metal etcher.



In operation, one of the wires coming from a toy transformer (dry cells or a storage battery),


which should supply about 10 volts, is connected to the machine screw on the etcher and the other is connected to the object to be etched by means of an ordinary clip.

The current flowing through the coil forms an electromagnet which attracts the steel spring, breaking the circuit. When the circuit is broken the spring is released and, the copper point again coming in contact with the metal object, the circuit is again completed and the operation is once more repeated.

This occurs so rapidly that the electric spark formed at the contact of the object to be etched and the copper point is practically constant. It is this spark that melts enough of the surface metal of the object to produce a clear and permanent "etching" you'll be proud of.

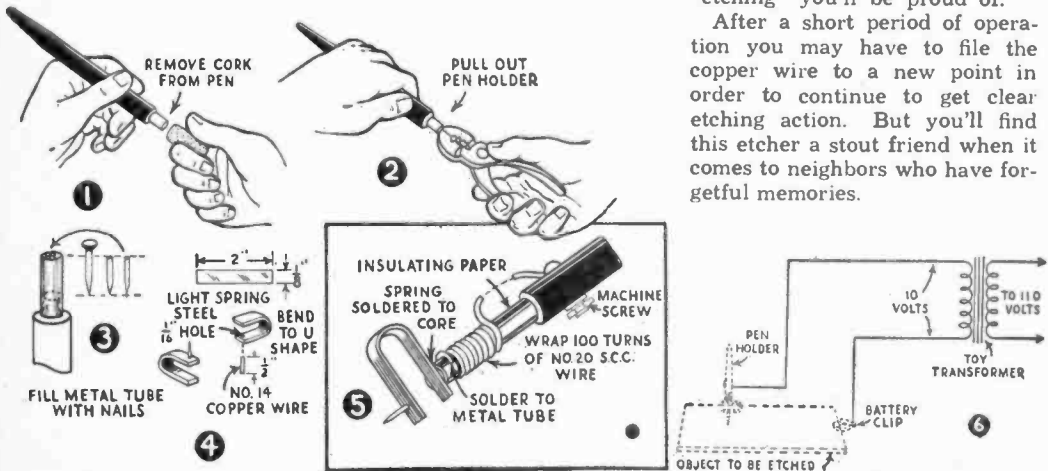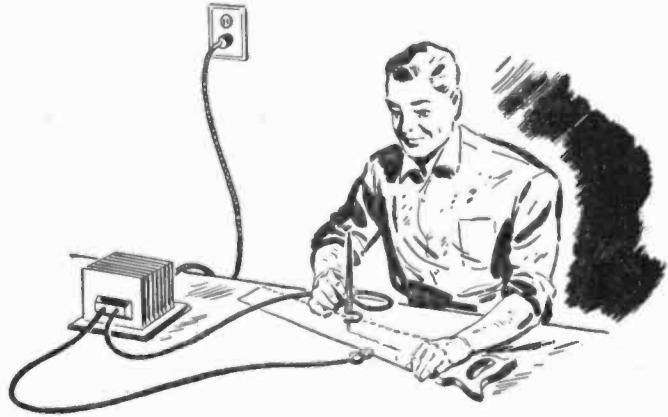After a short period of operation you may have to file the copper wire to a new point in order to continue to get clear etching action. But you'll find this etcher a stout friend when it comes to neighbors who have forgetful memories.



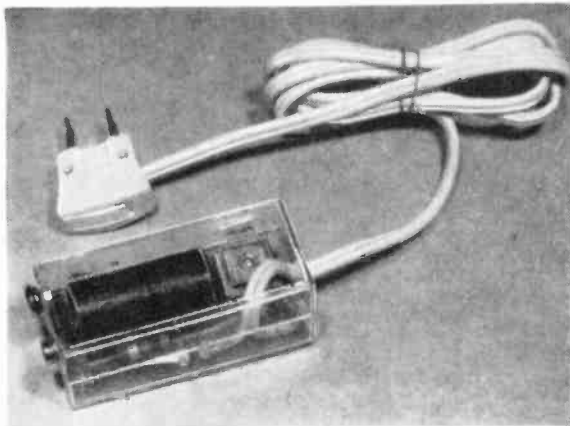

Battery eliminator (above) built into hinged plastic box delivers 9-volts to this six-transistor set.

Battery Eliminator for Transistor Radios

Tiny power pack provides low-voltage d-c for operating transistor sets from 117-volt lines

By THOMAS A. BLANCHARD

WHILE most transistor battery packs commercially available are priced under \$1, their special type does not always make them readily available when needed. Too, there are many instances where a transistorized set could be operated indefinitely—and with results superior to battery operation—if house current could be substituted for the expendable dry cells.


Well, sir, this tiny battery eliminator (Fig. 1) does just that. Operating off any 117-120-v. power line, it provides approximately 9 v. d-c for portables with five to seven transistors, and—because the radio circuit is provided with an earth return via the powerline—the range of any transistor

radio using it will be greatly improved over battery operation.


Because the unit must fit inside the radio, the power pack is built on a chassis that fits inside a transparent plastic box measuring $1 \times 1\frac{1}{4} \times 3$ in. In those cases where this size may still be too large, the builder can always operate the set with the battery eliminator outside the radio case. It is also possible to choose a plastic box of another shape and arrange the parts accordingly; because the chassis is a piece of perforated Bakelite, a great variety of layouts is possible.

With the exception of a $4-40 \times \frac{5}{8}$ -in. fh machine screw and nut (used to mount the $\frac{1}{2}$ -wave selenium rectifier), the component leads serve as mountings and tie-lugs. Pigtail leads of capacitor and resistor are threaded through the holes in the Bakelite. Lead ends are brought to the top of the panel, and small loops formed with needle-nose pliers or a wire tool. The loops make excellent soldering lugs for the line cord and flexible output leads and there is no chance for parts to shift or tear loose from their moorings. No hook-up wire is required between the input a-c and output d-c; since components pigtails are more than adequate in length for this purpose.

As the schematic (Fig. 2) shows, this power supply differs in certain respects from those used in conventional ac-dc power supplies. First, instead of the two or three filter capacitor sections required in vacuum-tube circuits, only a single 30-mfd., 150-v. electrolytic unit is used. Unlike tubes, transistors are not so susceptible to a-c hum, making additional filtering unnecessary. In tests using a conventional highly filtered and smoothed d-c supply, no improvement in set performance was obtained over pack use.

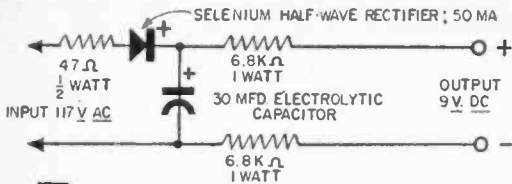

2 SCHEMATIC

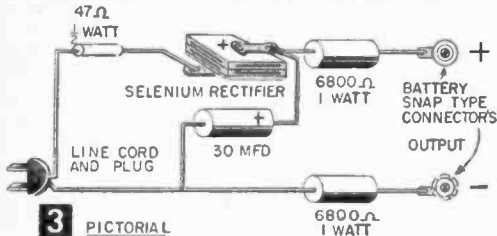

3 PICTORIAL

Note—Battery eliminator should be assembled in non-metallic container ONLY. Size and shape may be varied to suit individual requirements.


MATERIALS LIST—BATTERY ELIMINATOR

- 1 transparent plastic box; 1 x 1 1/4 x 3" (size optional)
- 1 piece perforated 1/16" Bakelite (size optional)
- 1 half-wave selenium dry disc rectifier. If available, 30 ma. size (1 1/16" sq.) may be used; otherwise, use 50 ma. (1 3/16" sq.)
- 2 6.8K (6800) ohm 1-watt, IRC composition resistors
- 1 30 mfd., 150v., electrolytic capacitor (C-D Blue Beaver)
- 1 47 ohm, 1/2-watt, IRC composition resistor
- 1 line cord plug
- 2 suitable battery connectors
- 1 4-40 x 3/16" fl machine screw and nut

Another advantage offered by transistor circuits is that voltage-drop resistors may be inserted in both sides of the power line. There is about 90-v. d-c at the selenium rectifier. This means a voltage drop of 81 v. is required for a typical 9-v., 9 ma (no signal) transistor radio. Ordinarily, these 81 v. would be dropped with a single dropping-smoothing resistor. We found that by splitting the drop on both sides of the line using two 6.8 K, 1-watt resistors, less heat had to be dissipated less space was necessary, and a safety feature was added. With a voltage-drop resistor on both sides of the line, shock hazard was greatly reduced. Also, with the unit plugged into an outlet that was not of the polarized type, the resistor in the grounded lead would "blow" on external shorts.

Of course, precautions should be taken to avoid careless handling of ac-dc-power supplies. First, the battery eliminator should never be built into anything except a plastic box—battery connections should be made before the cord is connected to the power line—and, if the battery connectors are apt to contact any metal inside the radio, connectors should be carefully insulated against shorts with plastic electrical tape. Finally, when the eliminator is not being used, disconnect it from the wall receptacle.

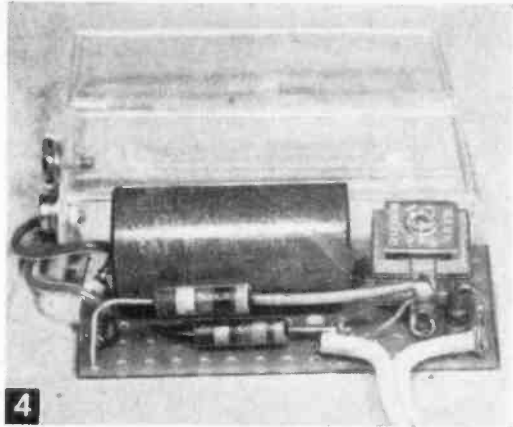Wire the unit as shown in Figs. 2 and 3. With the chassis wiring completed, solder fixture cord and short leads to battery snap connectors. (Battery connectors may be salvaged from a dead cell.) Connectors are attached to the lid of the



4


Components are self-supported by threading leads through holes in perforated Bakelite panel. Bare threaded component leads are insulated by box. Pig-tail ends of component leads are bent into loop-lugs for soldering line cord and connector wires. Chassis is held secure by a 2-56 self-tapping screw from outside of plastic case.

box with 4-40x1/4-in. machine screws. Soldering lugs should be attached to the ends of the output leads before connectors are mounted on the box, or heat will damage the container.

File a slot in the end of the box lid opposite from the connectors just wide enough to pass the fixture cord. Make this slot tight enough so that when the box lid is closed it will hold the cord secure. Use a strip of transparent tape to seal the box unit.

When the eliminator is to be used for lengthy sessions, provide a few vent holes in the case to release heat generated in the two 6.8 K-ohm resistors. The eliminator as described in this article is designed for circuits operating on 6 to 9-v. batteries. For circuits requiring lesser operating voltages, increase the values of the 6.8 K voltage-dropping resistors.

Basin Prevents TV Tube from Rolling

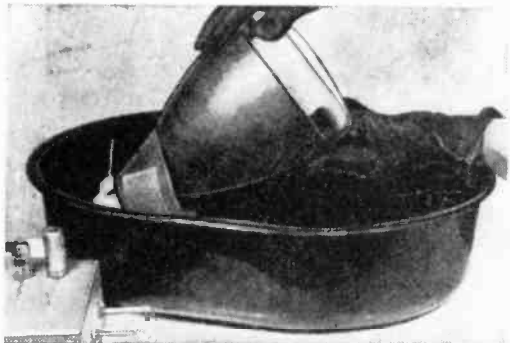

- Place TV tubes in hard rubber basins, available at surplus stores, for safe keeping while trying another tube or handling other repairs on the set. The hard rubber is less likely to damage the tube than metal containers.—H. LEEPER.




Hand approaching metal plate causes the lamp plugged into control receptacle to light up. Bells, motors, etc. may be plugged into the 110-120 v outlet.

Experimenting With a Capacity Control

No phototubes or light beams are required with this simple electronic unit which turns lights on or off with a mere wave of the hand

By THOMAS A. BLANCHARD

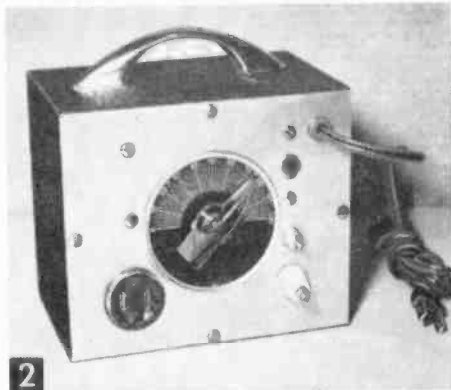THIS capacity control is simply another application of the versatile oscillator. In respect to the jobs it can do, it is similar to the photo-electric control. No light beams or phototubes are required to trigger it, however, only the presence of a human being near it.



Capacity control is housed in a stock radio chassis cabinet. Outlet is at left, insulated control terminal is at right of dial on front panel of control unit.

The circuit can be wired for sensitive or for ultra-stable operation. For sensitive operation, for example, a metal plate could be attached inside a store window. A shopper standing outside, then, placing his hand near or on the window glass would cause a display in the window to light up. When he moved away from the "sensitive" area, the lights would go out. (By substituting a length of insulated wire for the metal plate, a larger area of the window could be made sensitive to the approach of a shopper. There would never be actual contact between the window-shopper and the control because of the plate-glass barrier.)

It works like this: A small R.F. choke and tuning capacitor is inserted in series with the circuit's oscillator coil's cathode lead (see Fig. 3). Varying the capacity across the R.F. choke provides the sensitivity control so that the point at which the plate current relay picks up can be accurately determined.

Omitting the choke and tuning capacitor, gives a much more stable effect. The control then requires actual physical contact for triggering. Thus, if the control wire is attached to a metal door knob, for instance, you have to touch the knob before the circuit will operate. The control lead can be attached to any ungrounded metal object. When touched at any point it will cause the control relay to close. There is no danger of shock.

Suppose you have water seepage in the basement of your home. Mount the control lead $\frac{1}{4}$ in. off the basement floor and if the water rises $\frac{1}{4}$ in. it contacts the control lead, causing an alarm to ring. Applications of a capacity control are almost limitless—not to mention its amusement (and educational) value. For example, you can cut a piece of aluminum foil

the R.F. choke will eventually be located. (In fact, even the capacitor itself isn't needed at this point.) With power applied, the relay should close when the insulated terminal screw is touched. The control can be used for non-sensitive applications in this form.

For sensitive control, the variable capacitor can be any midget type between 60 and 100 mmf. A less expensive compression-type trimmer can be substituted here if more readily available. The R.F. choke may require some experimental work in order to obtain maximum sensitivity from the circuit. For the choke, we used a TV "peaking coil" of approximately 100 microhenries. Both peaking coils and R.F. chokes of the miniature type are wound on Bakelite pigtail forms that resemble 1-watt resistors. When connected across the stator and rotor lugs of the tuning capacitor with plates wide open, the control relay should pull in. Now, slowly closing the plates, you should reach a point where the relay drops out.


When this action is obtained, the choke will be of suitable inductance. However, if the relay remains energized with the plates of the tuner fully meshed, the inductance is excessive, and turns will have to be taken off.

You may find it more convenient to make your own choke. All you will need is fine enameled magnet wire (size #34 to #40). Measure off about 12 ft. and scramble-wind the wire on a 1-watt insulated resistor having a high resistance (22 megohms or more.) Carefully scrape off insulation from the leads and solder one to each pigtail.

Add or subtract turns until the relay will release when the variable capacitor plates are about at the half-closed position. Install in the chassis cabinet with a suitable dial plate and bar knob to adjust the tuning capacitor and attach a short lead and metal plate to the control's insulated terminal. Plug a light bulb into the receptacle and rotate the capacitor knob until the light comes on.

Now back off the sensitivity control until the light just goes out. Leave the control alone now, and bring your hand toward the metal plate. At a point ranging from 6 inches to one foot, body capacity will cause the control to turn on the light. Withdrawing your hand will turn off the light.

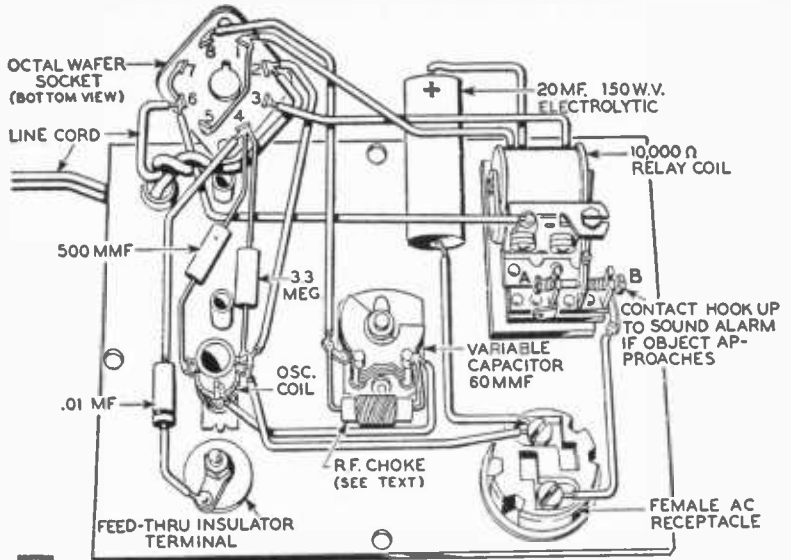If the length of the lead and/or size of the metal plate is changed, the control must be



5 PICTORIAL



Looking into rear of control box with cover removed. Front panel and chassis are one, making for simplified construction.

readjusted. Note, too, that if too much fixed capacity is attached to the control, the relay will remain locked-in. If this happens, use a smaller metal object, or shorter connecting line from control to plate.

Since the capacity control employs the popular ac-dc hook-up, you will find that it operates best when its ground circuit plugs into the ground side of the power line. (Reverse the line plug to determine the best operating position.)

Attach a metal drawer pull to the chassis cabinet for carrying convenience. To provide ventilation for the tube, punch two rows of holes in the back panel of chassis cabinet or use perforated Reynolds do-it-yourself aluminum for the box cover. (You can cut this material with a kitchen shears.)

Applause Meter




This inexpensive and compact applause and sound level meter has plenty of reserve gain and a headphone output. It can double as a hearing aid or remote "listener"

By FORREST H. FRANTZ, SR.




Small, inexpensive and tops in performance for price, that's this sound-level, applause meter.

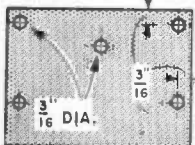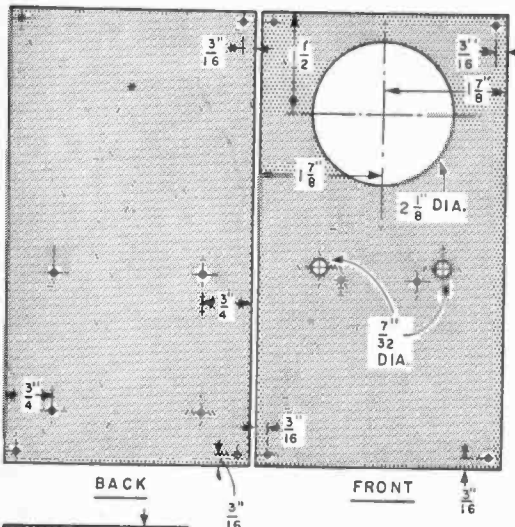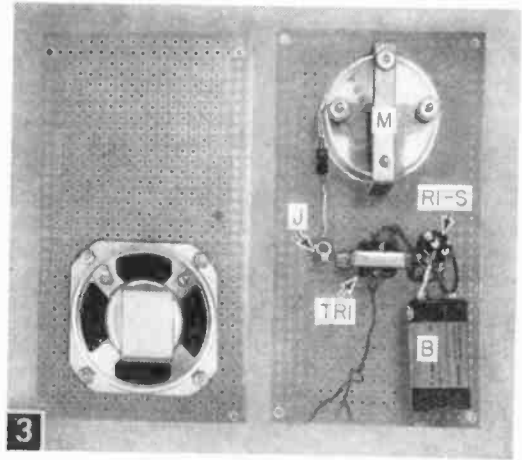A COMBINATION applause and sound level meter is a device that is both useful and entertaining. If you should be looking for a nice quiet location for your new home, for instance, this instrument will help you do the job scientifically. More probable jobs would be locating rattles in cars, vibrations in machinery, and even termites in woodwork.



ALL UNMARKED HOLES ARE $\frac{1}{8}$ " DIA

AMPLIFIER BOARD **2**

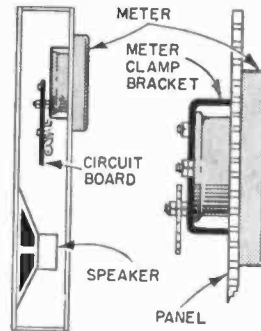

THE METER IS HELD IN PLACE ON THE PANEL BY THE METER CLAMP BRACKET

4

And when those amateur contests are held, here's your scoring device. We'll say no more about what it can do; as soon as you've constructed it, you'll start to find uses to which to put it.

High-precision sound level meters cost several hundred dollars. They're made out of the highest quality components and they have high caliber circuitry wired into them. As

an experimenter, you don't need—and probably can't afford—such precision. This meter can be built for about \$14 less headphones and battery.

To achieve a slim package you'll need wood strips of the type used for garden trellises. These strips are $\frac{3}{16}$ x $1\frac{1}{8}$ in. You need two of them $6\frac{3}{4}$ in. long, and two 3 in. long. Glue and brad them together to form a frame on which the $3\frac{1}{16}$ x $6\frac{3}{4}$ in. perforated Bakelite front and back panels will


fit. I enameled my frame gray, but almost any color goes nicely with the perforated boards.

Drill the front and back panels as shown in Fig. 2. I used a fly cutter to cut the 2 1/8-in. meter hole. A coping saw will do just as well if you take some time to trim your work with a file. When you drill or saw the boards, back them with wood to prevent splitting. The holes at the corners are used to fasten the boards to the wooden frame.

The small perforated board is the wiring board. It's cut with a hack saw from the small sheet of perforated Bakelite board listed in the Materials List and is mounted on the meter in the final assembly. The only work required on the back panel is the mounting of the loudspeaker, which will serve as a microphone. (A loudspeaker is used in preference to a microphone

because it is less directional and more sensitive.) When it is mounted, saw off the long meter mounting screws (not its terminal screws) to a length of 1/2 in. from the back of the meter. Fasten the end of the screw to be discarded in a vise to do the sawing, and support the meter gently with your hand. Then shorten the volume control (R1-S) shaft to a length of 5/8 in. from the front of the bushing. Again, the end to be discarded is the end you should fasten in the vise.

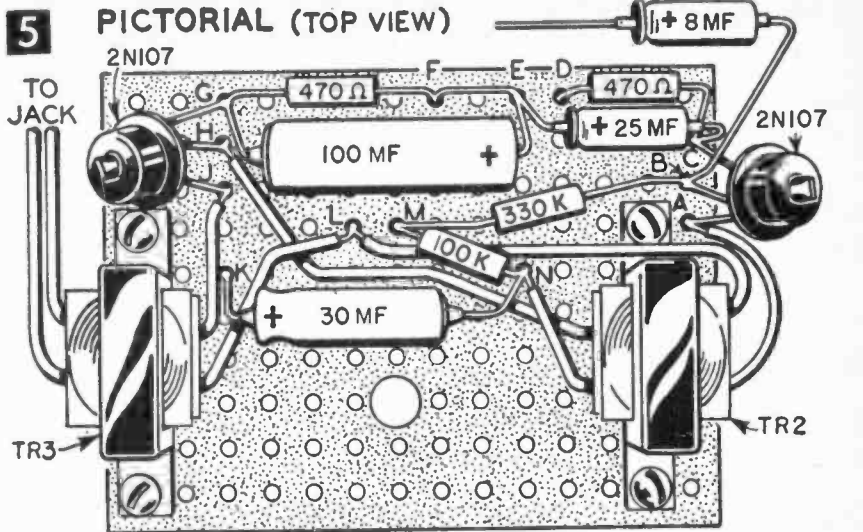Now, secure the meter M, the jack J, the transformer TR-1, and the 10K volume control to the front panel. The meter is fastened to the panel as shown in Fig. 4. Connect the diode D and the battery as shown in Fig. 3 and complete the wiring for the transformer winding marked




LETTERS DESIGNATE HOLE INSERTIONS


PICTORIAL (BOTTOM VIEW)

"P." You can use six penlite cells (#7) in series to obtain 9 v., three cells in the location occupied by the battery in my model, three on the other side of the board. If you place the front and back panels on the frame, you'll be able to place these batteries more easily. Be sure that they don't short-circuit. You'll want to do some insulating with tape after you complete the entire construction job.



Now you're ready to wire the circuit board. Figures 5 and 6 will help you in mounting the components, the circuit itself is shown in Fig. 7. Connections are made by forcing the component pigtail leads through the perforations and soldering. Excess lead length is clipped off on the side of the board shown in Fig. 6. Note that the plus lead of C3 is used to form a common return, or

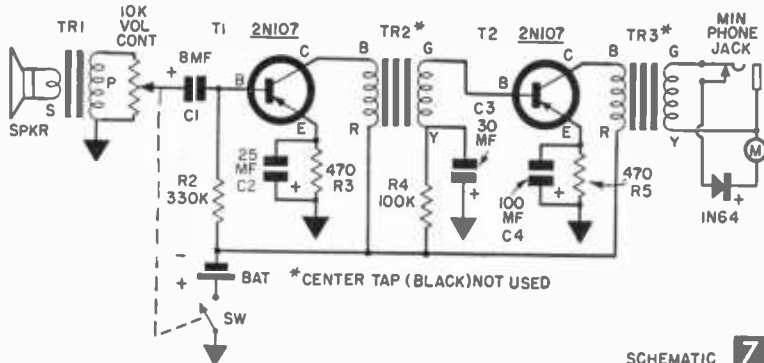

SCHEMATIC 7

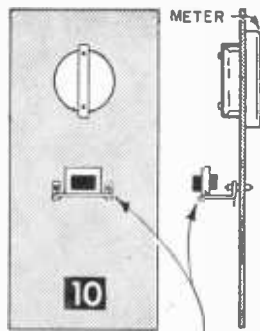

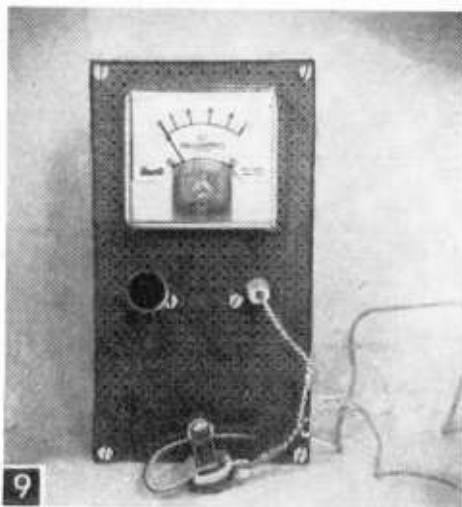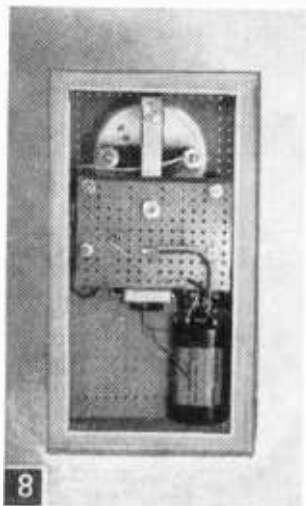IF YOU EXPERIENCE FEEDBACK, MOUNT TRANSFORMER (TR1) PARALLEL TO THE PANEL, ON BRACKETS, INSTEAD OF DIRECTLY ON THE PANEL



and fasten the back to the wooden frame with wood screws.

The front of the completed instrument is shown in Fig. 9. To test it, turn the switch *On* and advance the volume control. Whistle or make some other noise. You should get deflection before you turn the gain all the way up because this is a very sensitive instrument. Listening with the earphone will be helpful. Note that the meter is disconnected

"ground," for the battery through the switch.

Use rosin-core solder for all connections and use a hot, clean soldering iron. Grasp the pigtails of the transistors between the transistor body and the point at which heat is applied, thus shunting heat away from the transistor during soldering. Tape up (or clip off) the center taps leads on TR2 and TR3; you won't be using them.


After you've completed the construction of the amplifier, you're ready to assemble the three sub-assemblies you've prepared. First, fasten the front panel to the wooden frame with wood-screws. Then place the amplifier within the case and solder the leads from the secondary of TR3 to the phone jack. Connect a lead from the phone jack to the negative terminal of M, connect C1 to the center lead of the volume control, and fasten a lead from the ground bus on the amplifier to the switch.

Now place the amplifier on the back of the meter and fasten the lower nut (which holds the meter clamp bracket against the meter panel) to hold the circuit board in place. Finally, fasten the negative return from the amplifier to the battery. The back of the completed instrument, with the exception of the speaker-mike, is shown in Fig. 8. Solder the leads on the side of the transformer marked "S" to the loudspeaker terminals,

MATERIALS LIST—APPLAUSE METER

	$\frac{1}{2}$ watt carbon resistors, 10% tolerance
R3, R5	470 ohms
R4	100K
R2	330K
R1-S	10K miniature volume control & switch (Lafayette VC-28)
C1	8 mfd, 6v ultra-miniature electrolytic capacitor (Lafayette P6-8)
C3	30 mfd, 6v miniature electrolytic capacitor (Lafayette CF-104)
C2	25 mfd, 6v ultra-miniature electrolytic capacitor (Lafayette P6-25)
C4	100 mfd, 6v miniature electrolytic capacitor (Lafayette CF-106)
MIKE	$2\frac{1}{2}$ " PM loudspeaker, 10-ohm voice coil (Lafayette TR-93)
TR2, TR3	10K/2K driver transformer (Lafayette TR-96)
T1, T2	2N107 transistor (General Electric)
D	1N64 diode (General Electric)
J	subminiature phone jack (Lafayette MS-282)
M	0-1 ma meter (Shurite 8300Z)
B	battery (Mallory TR146F) (See text for less expensive alternates)
1	sheet of miniature perforated Bakelite board (Lafayette MS-304)
2	$3\frac{1}{8} \times 6\frac{3}{4}$ " miniature perforated Bakelite boards (Lafayette MS-305)
1	3K headphone (Lafayette AR-46; the Jack is supplied with the headphone and does not have to be obtained separately if the headphone is obtained from Lafayette)
1	miniature knob (Lafayette MS-185)

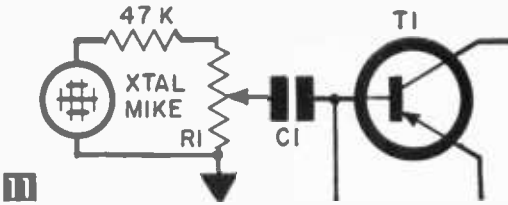All circuit components can be obtained from Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N. Y.



when the earphone is plugged in. If you don't hear anything, or if you don't get a deflection of the meter when the earphone is disconnected, turn the amplifier off and check your wiring.

If you get a squeal on the phone, or a constant full-scale deflection of the meter without having an input noise, you're having feedback trouble and you may have to shorten some of the input and output leads or turn TR-1 sideways and mount it on a bracket as shown in Fig. 10 to eliminate magnetic coupling.

Since both sides of the instrument case are perforated, the speaker-mike is sensitive to sound from front or back, a decided advantage. In order to be able to make comparisons of readings, provide the volume control with a scale marked in India ink on the front panel or fasten a paper scale on the panel with Carter's Rubber Cement. Place an index mark on the knob with a triangular file and fill it with white India ink to make it stand out. My model doesn't have this feature, but it's worth adding. Then, if the sound level or applause hits peaks that require a reduction in the volume control setting, you can readily interpret levels without loss of reference by using the control setting in conjunction with the meter reading.

There are some modifications to the sound level-applause meter that you may wish to incorporate. One, meter response is fast; if you want to slow it down so that it will tend to hold peaks, connect an electrolytic capacitor across the terminals of the meter. Use from 10 to 100 *mfd* depending on how "slow" you want to make the meter; a 6 v capacitor is adequate.

If you want to use a crystal microphone instead of the loudspeaker, eliminate TR1 and connect the mike as in Fig. 11. You won't have as much sensitivity with this arrangement, but you'll have enough.


There it is—an inexpensive sound level meter that can be used for many measurements. It has a microphone to convert sound to electrical energy; an attenuator (the volume control) to choose a range; an amplifier to get the signal up to strength to drive a meter through the rectifier; and a phone jack to listen in if you wish. These are the features that you find on an expensive instrument. If you're wondering how a two-transistor instrument can be so sensitive, the answer lies in the transformer coupling which provides better match between the transistors and enables us to work them more efficiently. But this costs us something in frequency response. Bear this in mind, and don't use to measure frequency response of hi-fi systems.

First Aid for Speakers

- Speakers on inexpensive small radios can often be given a new lease on life with a little fingernail polish applied around the center of the cone. The fuzziness of sound may be cut down by stuffing a bit of Kleenex or tissue paper between the cone and the speaker arms. If sparking contacts on door bells and buzzers are causing noise and interference in the speakers of nearby radio receivers, much of this interference can be prevented by bridging a one or two *mfd* capacitor directly across the contacts of the bell or buzzer. The capacitor will absorb most of the spark produced.—RALPH R. DOISTER

Improved Radio Dial Illumination

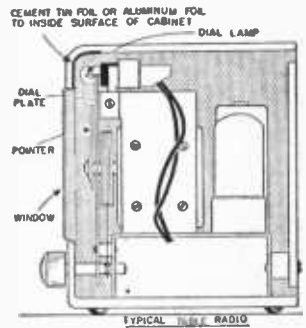- To increase the dial illumination in a radio having a lamp projecting over the top edge of the dial as shown below, cement a strip of tin-foil or aluminum foil to the inside surface of the cabinet directly over the bulb to serve as a reflector.



Do this also where the lamp is located to the side or on the bottom of the dial, if the wall of the cabinet is close enough to the lamp to allow the foil to act as an effective reflector. Otherwise, bend a reflector from a piece of tin cut from a can and solder or cement it onto the dial plate.—A. TRAUFFER.

Radio Locates Right Fuse

- Instead of using the trial-and-error or up-and-down-the-stairs method to find the right fuse in the cellar fuse box to an outlet on an upper floor, simply plug a radio into the outlet and turn the volume up high. The blaring radio will let you know when you screw a new fuse into the right socket.—R. M. WOODBURY.

Wire Soldering Technique


- When joining electrical wires or wires in electronic circuits, it is frequently difficult to hold two wires and the soldering iron or gun in position for a good solder joint. This problem can be considerably eased by tinning both wires before placing in contact. This then becomes a sweating rather than a soldering technique, which takes less heat for less time because the work does not have to be brought up to soldering temperature. Touch the wires lightly and apply the iron for just an instant to melt the solder and complete the joint. The joint will have sufficient mechanical strength and, if the resin core type of solder is used, it will carry current efficiently.—ROBERT A. WASON.

Junior witnesses and privately listens to the adventures of his favorite TV character while other members of the family enjoy their activities in peace. The phone jack is mounted on a bracket fastened to the cabinet with wood screws (below). Removal of the phone jack automatically restores loudspeaker operation.



Phone Jack for Radio or TV

By FORREST H. FRANTZ

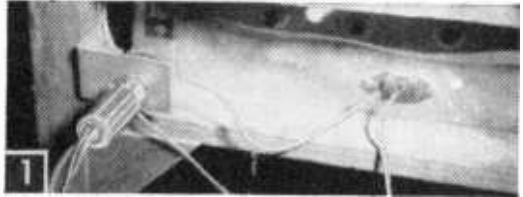


AT TIMES—at many times—a blaring loudspeaker is incompatible with the other activities going on in a room, at our house, the family den. Our den, in addition to housing the highly revered television receiver, contains my desk and technical books, my writing workshop, and the usual assortment of magazines and books that other members of the family prefer to “The Mickey Mouse Club,” the present TV favorite of our eight-year-old.


The obvious solution to the problem was the installation of a headphone jack. This solution proved to be most welcome to the eight-year-old and also to his eleven-year-old brother, both of whom find wearing headphones fascinating. (They occasionally model in them before a mirror!) The headphones are popular too when one member of the family wants to see a late movie on TV.

The installation of a headphone jack is simple, and inexpensive. There are several possible schemes that may be employed. No wiring changes are required in the radio or TV chassis wiring. And no connections are made in high-voltage circuits.

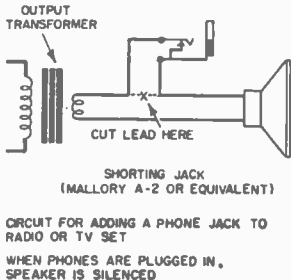First, cut one of the leads from the output transformer secondary to the loudspeaker and connect a shorting phone jack to the two wire ends (see Fig. 2). This type of jack closes the circuit and keeps the speaker oper-



2

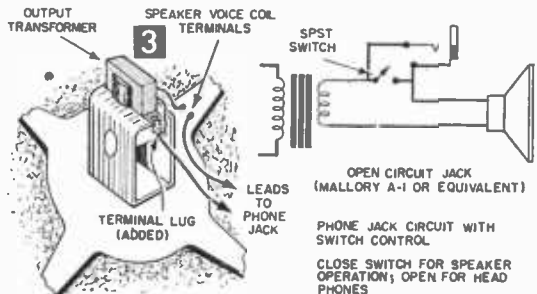


CONNECTIONS AT SPEAKER WHEN OUTPUT TRANSFORMER IS MOUNTED ON SPEAKER

4

ating until the phones are plugged in. When the phones are plugged in, they receive the major portion of the output signal while the loudspeaker receives so little that it is silent. (Headphones should have an impedance of 1000 to 3000 ohms.)

Our TV set (a small console) has an off-chassis speaker. The output transformer is mounted on the chassis and the speaker plugs into the rear of the chassis (see Fig. 1). The leads are long enough to allow them to be connected directly to the jack. The jack is mounted on a small bracket fastened to the side of the cabinet with woodscrews.

If your receiver has its output transformer mounted on the loudspeaker, connect leads out to the phone jack mounting location by removing one of the output transformer leads from the speaker connection terminals with soldering iron and pliers. Fasten a one- or two-terminal strip to the loudspeaker frame and connect the loose output transformer lead to a lug on the terminal strip (see Fig. 3). One of the phone jack leads is connected to this lug, the other to the loud-

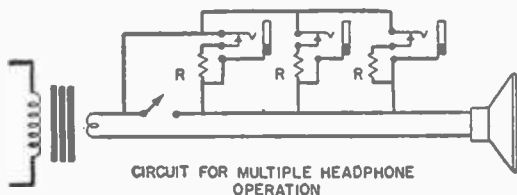

CIRCUIT FOR MULTIPLE HEADPHONE OPERATION

5

CLOSED CIRCUIT JACKS (MALLORY A2-A OR EQUIVALENT) ARE USED

THE RESISTOR "R" IS A $\frac{1}{2}$ WATT CARBON WITH RESISTANCE EQUAL TO THE HEADPHONE IMPEDANCE (APPROXIMATELY)

speaker's voice coil lug. If you want to keep the headphone jack plugged in and control it with a switch, the circuit of Fig. 4 on the opposite page, employing an open circuit jack, should be used.

For multiple headphone use, wire as shown

in Fig. 5. A switch on the receiver controls the speaker-headphone choice. Phone jacks are the closed circuit type. They can be mounted in wall outlets for permanent installation or run to portable outlet boxes wired to the set through parallel lamp cord. The resistor "R" wired into each jack should be equal to the headphone impedance. When a set of headphones is removed from a jack, this resistance is then automatically switched into the circuit, keeping the load on the headphone line constant and preventing the volume from changing abruptly on the other phones.

With all of these arrangements, the receiver volume control also controls the headphones. The volume control setting for comfortable headphone listening is the same as for comfortable loudspeaker listening when a single jack is used. Even with several pairs of phones, there's not enough difference to expose you to "loudspeaker blaring" when you switch from the headphones.

Electronic Circuits Puzzle

By JOHN A. COMSTOCK

How extensive is your knowledge of electronic circuits? Can you fill in all of the blocks in the diagram correctly and complete the circuits? (Solution to puzzle is on page 158.)

CLUES


ACROSS

- 1) Demodulator circuit.
- 6) A full-wave rectifier utilizes a transformer with a center _____.
- 9) The circuits in a TV set that synchronizes the received image with transmitted image.
- 10) A circuit sometimes used in an amplifier to secure greater gain.
- 11) A type of coupling between circuits (abbreviation).
- 13) The terminals of a circuit to which an incoming signal is applied.
- 14) A tube and its associated components within an amplifier.
- 17) The circuit in an FM receiver which "clips" amplitude peaks from the FM signal.
- 19) The circuit between the grid and cathode of a vacuum tube.
- 21) A network used in a hi-fi speaker system.
- 22) A circuit used to prevent interstage feedback.
- 23) A tuned radio frequency stage or receiver (abbreviation).

DOWN

- 1) The unfaithful amplification of a signal through an amplifier.
- 2) Parallel resonant circuit.
- 3) A "flip-flop" oscillator circuit.
- 4) An oscillatory circuit.
- 5) The "front-end" of a TV set.

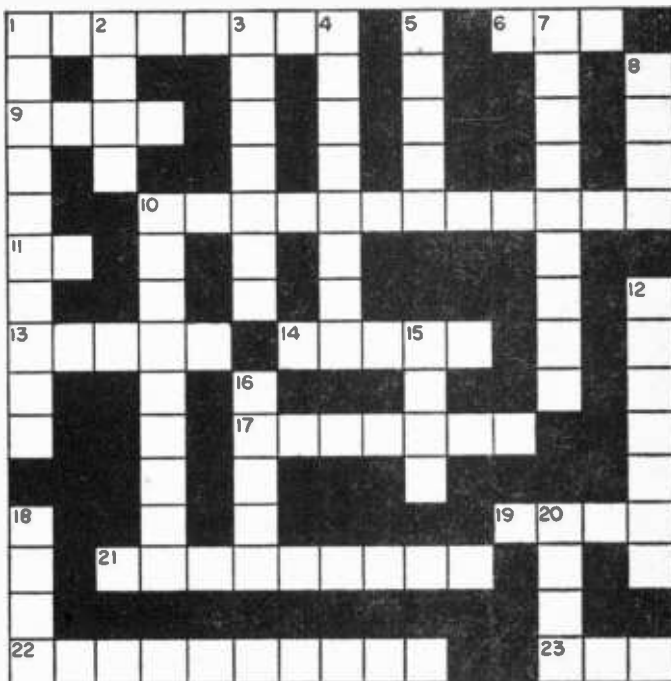- 7) Circuit that increases voltage, power, or current.
- 8) The ratio of output signal to input signal of an amplifier.
- 12) Meaning the output of one stage connected to the input of the next.
- 15) A trigger circuit.
- 16) A _____ "A" amplifier is a linear amplifier.
- 18) Device placed in a circuit to absorb or convert power.
- 20) Power supply circuit that converts a-c to pulsating d-c (abbreviation).



Answer to Electronic Circuits Puzzle, Page 158

Electronic Bull's Eye GAME



A beam of light, not bullets, scores bull's eyes in this game

By T. A. BLANCHARD


THIS electro-ray target game is a gift that not one-in-a-million kids will get and yet you can build it for just a couple of dollars. Many so-called electronic target ranges use a dummy rifle whose trigger works a *stepper switch*, causing certain lights to flash on as the trigger is pulled. (With these, I have actually aimed at the ceiling and scored a "Bull's Eye.") But you'll find nothing phoney about this Electro-Ray Target game. To ring the bell and flash the "HIT" lights depends upon your *aim*, not luck! Because your ammunition is a beam of light, this game is ideal for every member of the family as electronics eliminates the danger that goes with the use of darts, slugs, BB shot, etc. The nucleus of this game is a compact photo-electric amplifier mounted behind a plywood or Masonite target. A small aperture in "dead center" of bull's eye allows a beam of light to strike a photo-electric cell. This beam is provided by a plastic pistol which you can purchase in 5-10c stores for about 20c.


Let's start construction with the simplest unit—the *target*. First lay out the *bull's eye* as shown, using either $\frac{1}{8}$ in. plywood or Masonite. Outside diameter of bull's eye is 14 in. and each ring and space is 1 in. wide. Cut 2 x 5 in. windows below bull's eye for the *hit register*. Then enamel Masonite panel brilliant red, using silver

for the Bull's Eye. Make the circles using a draftsman's compass filled with silver bronze instead of the ordinary India ink. Then fill in the space with silver paint applied with a camel's hair brush. After paint has dried, bore a $\frac{3}{4}$ in. hole in dead-center of target with a brace and wood bit. This will allow light-beam from gun to hit light-sensitive photo-tube, sound *bull's eye* alarm, and light up the register.

Scroll work at top and bottom of target is optional. Two triangular brackets, cut from a 12 x 14 in. piece of $\frac{1}{2}$ in. box-grade pine, support the target. A diagonal line drawn through 12 x 14 panel and a single saw cut produced these two triangles. To make brackets rigid, nail and glue a piece of $\frac{1}{8}$ in. stock, 18 x 5 in., across the bottom (see rear view of completed target). Use any 5 and 10c store variety doorbell or buzzer which will operate on 6 to 8 volts ac for alarm. Bell shown here is the *one stroke* type, but a "repeater" type (Edwards, Monowatt, Bryant, etc.) would make the game more dramatic.

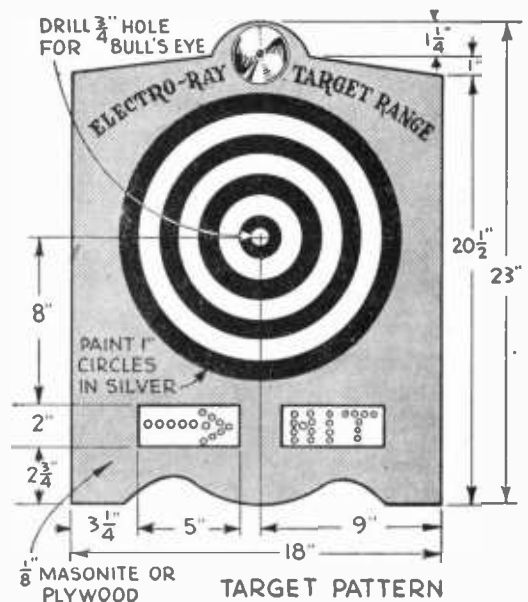Ordinarily, you would need a step-down transformer to operate the bell alarm from 115-120 volts ac. But here the visual alarm is provided




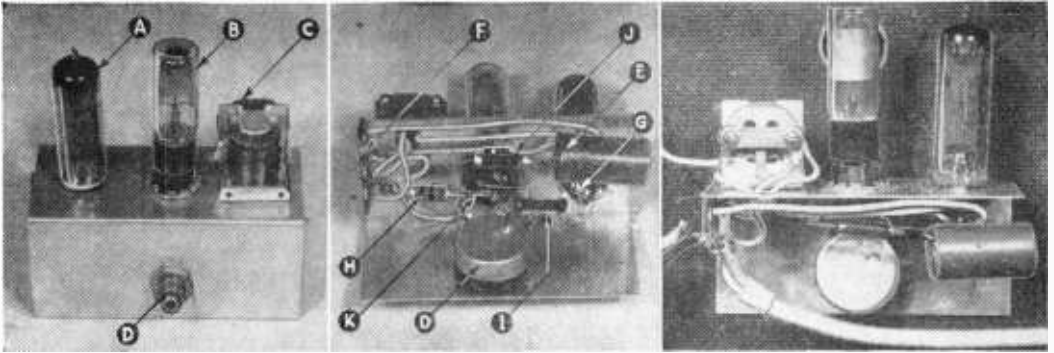

Electronic control on L-shaped chassis. (A) type 50B5 tube; (B) phototube; (C) relay; (D) potentiometer; (E) electrolytic condenser; (F) terminal strip; (G) 7 pin tube socket; (H) 5100 ohm resistor; (I) 10 megohm resistor; (J) 3900 ohm resistor; (K) phototube socket. Photo at right shows electronic control in position behind target, attached to target with projecting bushing of 1000 ohm potentiometer.

by two window openings each lit by a 100 watt Mazda lamp, under the target. This bulb also acts as a voltage drop resistor to ring the bell, and both bell and light respond together. When a perfect aim is made on target, the electronic control causes relay to close. Contacts of this relay close a 115-120 volt circuit through doorbell and 100 watt bulb. Thus bell rings and light comes on.

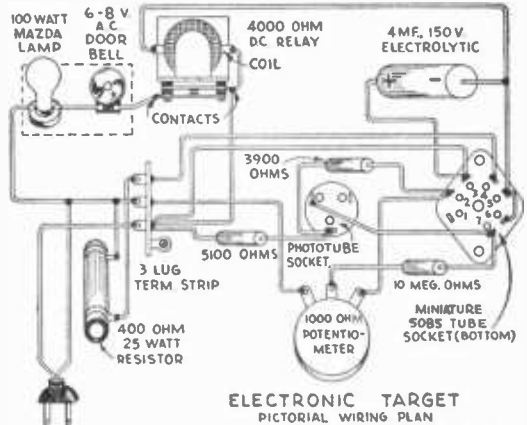Using black photo album paper, punch out an arrow and the word *hit* with ordinary paper punch. Now cut strips of colored cellophane and cover back of paper with these strips, placing over punched openings. Use Scotch tape to se-



sure cellophane strips. The results will be similar to movie exit signs. Vari-colored cellophane strips can be affixed over letter-holes for more sparkling effects. The black paper mask is sandwiched between an 11½ x 2¼ in. glass panel (rear) and a 11½ x 2¼ in. plastic sheet (front). Three wooden cleats hold assembly rigid behind target.

The electronic control is assembled on an "L" shaped aluminum chassis. First cut a 4 x 3½ in. metal piece and then bend this panel to form a 1¾ x 4 in. chassis. Drill or cut ⅝ in. holes for socket, plus a ⅜ in. hole in center of lower apron for potentiometer. Then wire up according to the pictorial plan. For convenience, a 3-lug terminal strip is mounted to chassis so that power cord, light socket, bell, and 400-ohm resistor may be mounted on target brackets easily. A wooden sub-panel may replace the aluminum chassis if desired.

The gun, a replica of a regular automatic pistol, is available in many models and sold in all Woolworth and many other 5 and 10c stores from 20c. The pistol is molded in two halves and cemented together. Using a razor knife or an Exacto-type tool, separate the pistol to reveal the "works." Note that it has a dimpled spring "clicker" or "cricket" which operates when trigger is pulled. When the trigger is pulled, the spring "cricket" comes in contact with battery holder mounted in grip of pistol. This completes the circuit and throws a beam of light

MATERIALS LIST—ELECTRONIC BULL'S EYE

Mechanical Parts:



- About 4 sq. ft. ½" plywood or Masonite
- Misc. white pine scrap
- Piece window glass, 11½ by 2¼"
- Piece clear plastic, 11½ by 2¼"
- 8 RH Wood Screws & Washers, #8, 1" long
- 8 RH 4-40 Machine Screws and Nuts, 1" long

Electrical Parts:

- 1 100 watt Mazda bulb
- 1 Porcelain cleat socket for Mazda bulb
- 1 Penlite bulb (1½ or 2.5)
- 1 Xmas tree socket for Penlite bulb
- 1 6 to 8 v. a.c./d.c. doorbell or buzzer
- 1 6 ft. extension cord and plug

Electronic Parts:

- L-shaped aluminum-steel chassis (see text)
- 1000 ohm potentiometer (screw adj. type)
- 5100 ohm, ½ watt resistor
- 3900 ohm, ½ watt resistor
- 10 megohm resistor, ½ watt
- 400 ohm, 20 watt resistor
- 3-lug terminal strip
- Misc. nuts, bolts & hookup wire
- Sensitive 4000 ohm SPST (plate type)
- 4 mid., 150 v. electrolytic
- Type 50B5 electronic tube
- Type 927 phototube
- 7-pin miniature socket
- 3-pin miniature phototube socket

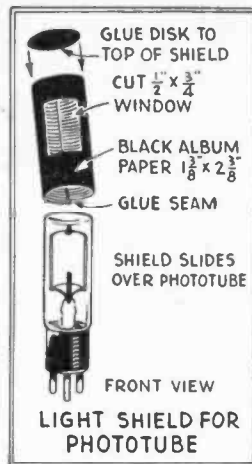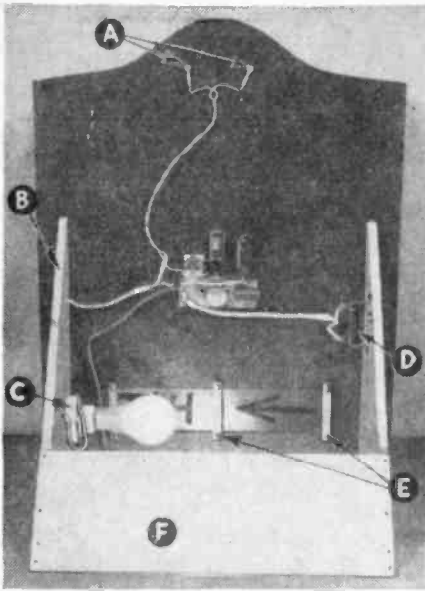

Rear view. (A) bell connections; (B) target brackets (1/2x12x14" pine); (C) 100 watt bulb and socket; (D) 400 ohm 25 watt resistor; (E) wood cleats; (F) 1/8x5x18" brace.

from pistol barrel (see photo of gun assembly).

The battery holder is a simple clip arrangement fashioned from a small strip of fiber of thin Bakelite, and fitted with tin brackets into which a penlight battery may be inserted. When trigger is pulled, circuit is closed through a flashlight bulb mounted in gun barrel. Beam is concentrated to a powerful pin-point of light by a small lens cemented in front of barrel. Lens is available from Edmund Salvage Co. for a few cents. It has a diameter of 14mm (about 9/16 in.) and a focal length of approximately 40mm (about 1 1/2 in.). Mount lens in gun barrel by first coating edge with Ambroid or Duco cement and allowing it to dry. The flashlight bulb mounts in a Christmas tree decoration socket, discarding the Bakelite shell and making use only of the brass screw shell. A good coating of cement is used to secure the socket to the plastic gun. Make an adjustment of socket with a lighted bulb before socket is put in place to insure sharpest focus.

When gun is operated with a single penlight cell, be sure to use the proper size bulb, identified by a pink bead. For longer service, make an adapter to clip into the penlight battery holder. By means of a flexible cord, power is supplied from a flashlight case. If a two cell case is used, insert a 2.5 volt bulb, (of the focussing type, identified by a blue bead), or a 2.5 magnifying penlight bulb (with white bead). To wire up gun, solder one socket wire to bottom of battery clip. Then solder remaining socket wire to top edge of spring "cricket." Remember to *remove parts from gun while soldering as heat will melt the plastic.*


Two halves of pistol are assembled with a single 1 in. by 4-40 binding head machine

screw and nut. If screw projects a little beyond nut, file off surplus. Locate hole for this screw somewhere near center of pistol grips (see drawing). To insure alignment, assemble gun and drill right through pistol grip with 1/8 in. twist drill. For a neater looking assembly, you may use a rosette-head 6-32 screw and ferrule, secured from any hardware store, or—also—a leather Key Kaddy with a screw and ferrule arrangement to support keys, can be used. Either way, a single screw is all you need as registration pins molded in the plastic prevent sections from getting out of alignment.




For those who want a more impressive type of gun, try the Tommy Gun shown in drawing on next page. Here a 5

and 10c store reading glass lens provides the optical system and you can remove this lens from the plastic holder by placing in very hot water for several minutes, then snapping it out of softened plastic frame. Lens shown in drawing is similar physically to the reading glass lens, but of superior quality. It is a chipped edge type stocked by Edmund Salvage Co. and has a 39 mm (about 1 1/2 in.) diameter and a 152 mm (about 6 in.) focal length.

Tommy Gun barrel is a 12 in. length of sturdy cardboard mailing tube having a 1 1/2 in. inside diameter. Mount lens in one end of tube, using two rings of 1 1/2 in. o.d. tubing to support it. Now cut a 1 1/2 in. dia. wood disc of 1/4 in. pine, and in its center, bore a hole just large enough to permit brass shell from Christmas tree socket to be forced-threaded in the opening. Solder length of wire to brass shell as shown. Insert socket and disc in tube so that filament of penlite bulb will be 6 in. from the Edmund lens. Small escutcheon wood screws hold disc rigid. Cut gun grips from

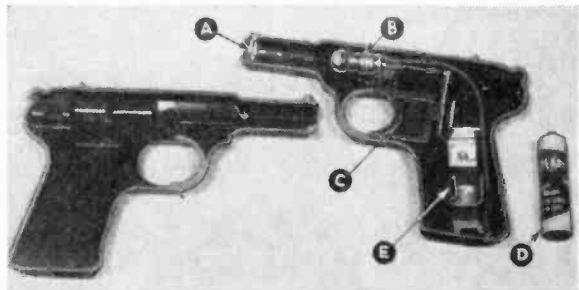

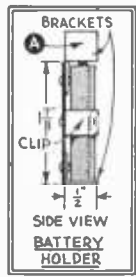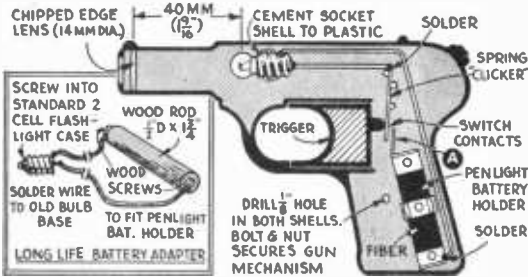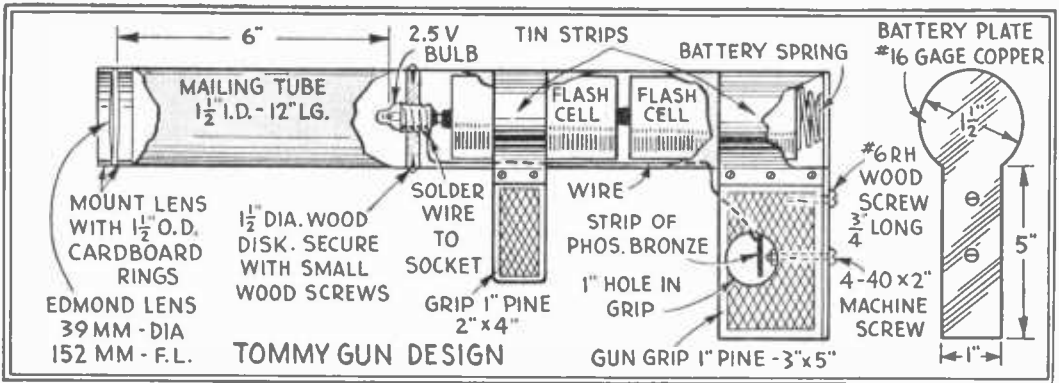Toy plastic pistol separated at seams with razor blade. (A) salvage lens; (B) flashlight bulb and socket; (C) trigger; (D) Penlite cell; (E) battery holder.



sunlight won't strike it. Now place your hand over bull's eye opening to completely shut off frontal light. Slowly adjust potentiometer until bell and light operate. At this point, turn back potentiometer screw just enough to silence bell. Target is now adjusted to the most sensitive point, so remove your hand from bull's eye. Aim ray gun at target, pull the trigger, and if your aim was good, the bell will ring and **HIT** will flash from the illuminated scoreboard.

Bushing for TV Line

● To bring TV twin-leads into the house with low-loss and without letting cold air in, make sealed feed-through bushings from polystyrene tubing. For 300-ohm line, bore a 1/2 in. dia. hole through window frame and push a length of 1/2 in. O.D. polystyrene tubing through the hole, allowing about 1 1/2 in. of tubing to project on each side of frame. Push line through tubing. Seal tube ends by heating with matches or a cigarette lighter, and, wearing a glove to protect the fingers, pinch the tube ends firmly together. Hold until plastic sets. For 150-ohm and 75-ohm twin-leads use smaller diameter tubing.—A. TRAUFFER.

Toys and Games You Can Make

■ If the high cost of giving is getting you down, you'll want a copy of *Toys and Games You Can Make*, a book containing detailed plans and building instructions for over 80 different toys and games. Ideal for gifts to children—children from two to twenty—on any occasion, and especially suitable of course for Christmas or birthday giving, toys included in this book cover the range from pull toys for infants to powercycles for young adults. You'll find just the toy for that son, daughter, nephew, niece or grandchild and you'll save money and enjoy yourself making it "just for him." *Toys and Games You Can Make* is available wherever magazines are sold. If you cannot obtain a copy from your newsdealer now, let us know and we will see that he is supplied. Or send 75¢ for Handbook No. 556 to Dept. 5552, SCIENCE AND MECHANICS, 450 East Ohio Street, Chicago 11, Illinois, and we will fill your order. A special hardbound edition of this handbook, priced at \$1.95, is available from us for your shop reference library if you order now. Supply is limited. Order from SCIENCE AND MECHANICS.



1 in. white pine to a design and size which suits your need. Cut trigger grip to dimensions shown, then bore a 1 in. hole through stock for trigger switch. With a fine scroll or fret saw, cut a slot and force a strip of phosphor bronze or spring steel in position for the trigger.

Next cut metal bands from #20 gage tinplate, etc., and form them into clamps. Gun grips are secured to bands with 4-40 rh machine screws, 1 1/4 in. long. Then bring wire previously attached to socket shell out through a small hole in tubing, down the gun stock, and solder it to the spring trigger. Insert standard flashlight cells into rear of tube under tension of a coil spring salvaged from a discarded flashlight. A copper or aluminum retainer plate screws into back of pistol grip as shown. Upper screw is a #6 rh wood type 1 in. long. Lower screw is a 4-40 rh machine screw, 2 in. long, which passes through a 1/8 in. hole in the grip to the finger opening. This bolt completes trigger switch mechanism. Thus when spring trigger is pulled, circuit to lamp is completed since spring contacts end of retainer plate screw. Should 4-40, 2 in. screw project too far, cut off surplus and file smooth.

With gun complete, Electronic Bull's Eye Game is ready for a trial. First, however, as photocell is sensitive to all light, make a hood for it to protect it from extraneous illumination, covering phototube with a tight-fitting black paper tube made of photo album paper. Cut a 1/2 x 3/4 in. window in front of cover to admit light through bull's eye. Also glue a disc of paper to top of paper tube. With phototube shield in place, set up target in a position where brilliant

Heavy-Duty Soldering Pot

By W. McCORMICK

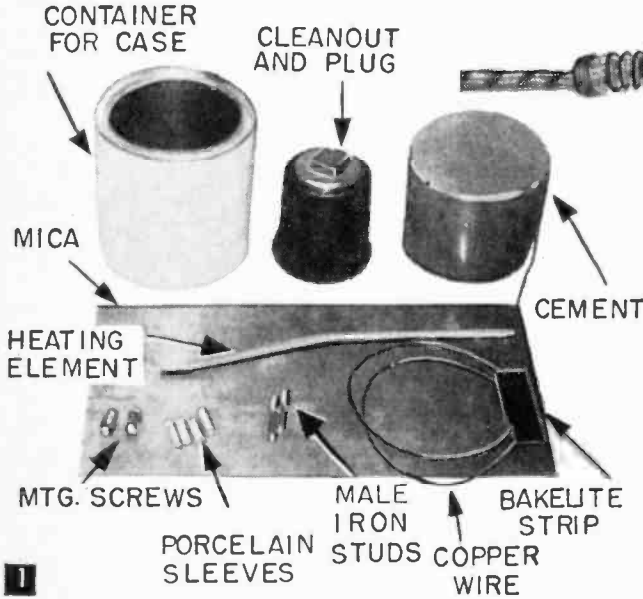
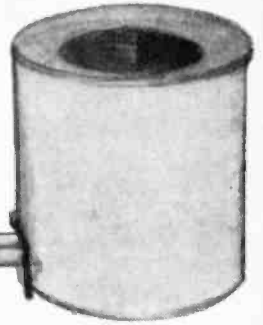



Assemble the materials needed (see Materials List; parts are available at plumbing and heating and electrical supply houses as well as from mail-order firms such as Sears, Roebuck & Co.) and begin construction by screwing the brass plug into the bottom of the cast-iron cleanout of the unit, leaving two complete threads outside the cleanout body (Fig. 2). Use refractory (furnace) cement to hold the heating element assembly in the case. Since this cement shrinks very little, it will hold.

1 Soldering pot operates on house power (115 v. ac or dc), at 5.5 amps, 600 watts. Solder capacity is 3 lbs. Materials needed are shown at left below pot.

THE experimenter will find a heavy-duty soldering pot a valuable piece of shop equipment. It tins wires and makes perfect solder joints on brass and copper as quick as a wink, preheats parts too large to be soldered with an iron alone so that they can be soldered with ease, even makes possible the soldering of aluminum if an aluminum flux is used. (Stainless steel, the most stubborn member of the metals family, will also yield if a little acid flux is first applied.) The pot described in this article is ultra-simple, rugged, efficient, and can be built for about \$2.50.

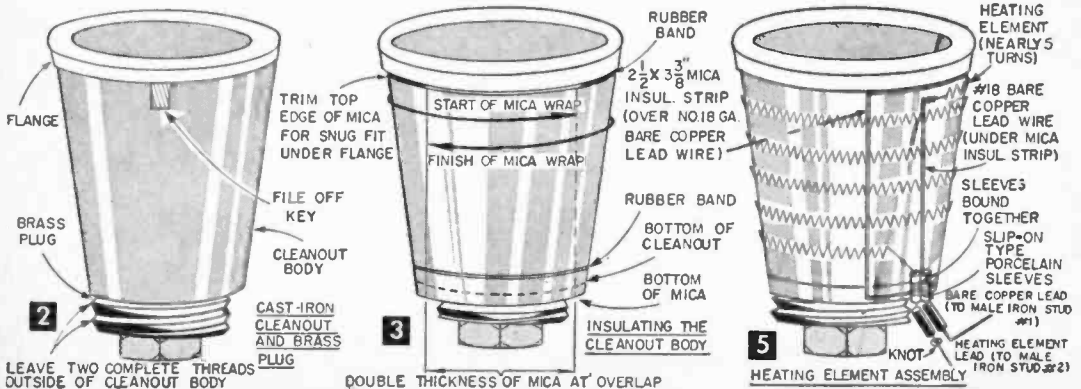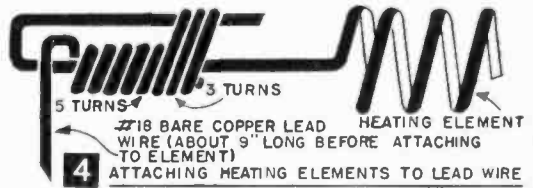File off the key under the cleanout's flange, and then cut a strip of reinforced mica $3\frac{3}{8}$ in. wide by 12 in. long. Crimp this along its length with long-nosed pliers until it forms a circle. It will snap, crackle and pop as it's crimped, but the woven reinforcing between plies will not allow it to split and peel as ordinary mica would.



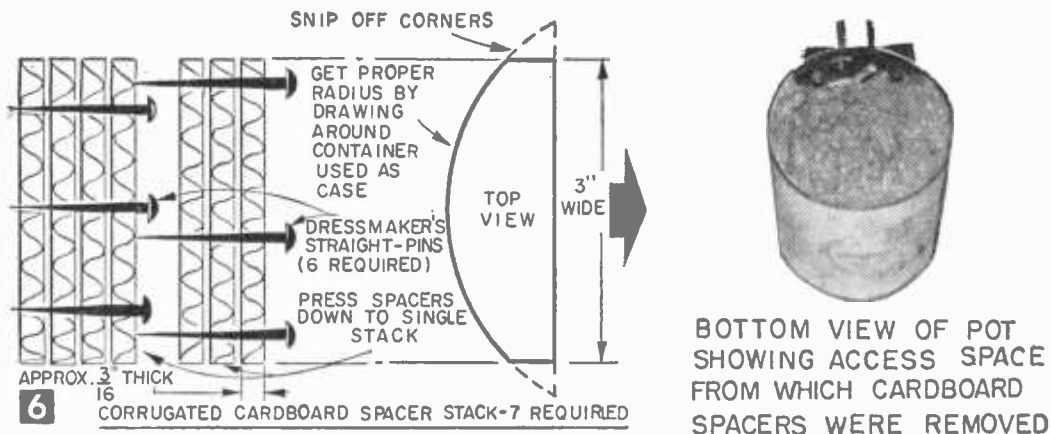

Wrap the mica around the body of the clean-out, trimming its top edge to fit snugly up under the flange, and fasten with rubber bands—one just beneath the lower edge of the flange, the other near the bottom of the cleanout body (see Fig. 3). Next, make a mica insulator strip $2\frac{1}{2}$ in. wide by $3\frac{3}{8}$ in. long (high) and slip one end of it under the top rubber band. Slide it around until it is over the first piece of mica's overlap.

Now, stretch the coiled heating element out to about 34 in. and attach it to the copper lead wire as shown in Fig. 4. Then slip the lead wire, with element attached, up under the mica insulator-strip and work the lower rubber band up over the bottom end of the mica. Position the "start" of the element winding about $\frac{3}{8}$ in. down from the underside of the flange by working the copper lead wire up or down. Straighten out the last three in. of the element wire.

Next, wind the element in a spiral down the mica. When you reach the bottom you should have slightly less than five turns (as shown in Fig. 5). If not, compress or stretch the coils until you do.

This done, unwind the element and slip two porcelain insulating sleeves on its free end. Tie a loose knot in the element wire protruding through the sleeve, work the knot up against the end of the sleeve and tighten it snug.

Slip a second pair of porcelain sleeves over the end of the copper lead wire, bending the wire that protrudes at a sharp angle to the end of the sleeve. The sleeves should now be jammed between the bend and the cleanout body.

Rewind the element, spiraling it down the mica as before. When the "finish" has been reached, bind the upper sleeve on the element wire to the upper sleeve on the copper lead wire, twisting the ends of this wire wrap with pliers.

Inspect the element for shorted turns. Make an ohmmeter check to guarantee that the copper lead wire is not in contact with the cleanout body.

Mix a cup of refractory cement with water and cover the element, rubber bands and all, with a thin coat, taking care not to disturb the element windings. Put the element assembly,

plug end up, aside to dry.

To make the case for the solder pot, take a can opener and cut the bottom and top lips out of the metal container you have selected (I used an empty tobacco can). Then make a stack of cardboard spacers to keep the cement out of the access space in the bottom of the case (as shown in Fig. 6).

A cardboard cement retainer is needed, so stand the case on a sheet of corrugated cardboard and scribe around both its inside and outside edges. Cut down between these two circles with a knife, but do not cut all the way through. Place the edge of the case on the circular channel in the cardboard and force it down into the cut.

Reach inside the case from the top and tape the stack of cardboard spacers to the inside of the case, away from the seam, at the very bottom. The spacers should rest on the cardboard cement retainer.

Now mix enough cement to fill the inside of the case level with the top of the spacers, fill, and allow four hours for this to partially set. While waiting, make the bakelite terminal board.


Returning to the case, dig the spacers out of the access space and lower the element assembly into the case, guiding the element leads into the

MATERIALS LIST—SOLDER POT

- 1 600 watt, coiled heating element
- 1 2" cast-iron cleanout with brass plug
- 1 sheet reinforced mica, $3\frac{1}{2} \times 15"$
- 2 electric iron studs (male)
- 4 porcelain insulating sleeves
- 3 lbs. refractory cement
- 2 rubber bands
- 2 sq. ft. corrugated cardboard
- 6 dressmaker's straight pins
- 1 wad of cotton or 3 Kleenex tissues
- 1 metal container, approx. $4\frac{1}{2} \times 4\frac{1}{2}"$ (empty $\frac{1}{2}$ lb. tobacco can)
- 1 strip Bakelite, $\frac{3}{16} \times 1 \times 22$
- 1 12" length #18 or heavier bare copper wire
- 2 #6 x 32 machine screws, $\frac{5}{8}"$ long
- 2 #6 x 32 hex. nuts
- 2 #6 internal tooth lock washers
- 1 asbestos shingle for base (optional)
- 1 12" length transparent tape, $\frac{1}{2}"$ wide

World-Wide Reception on the

Medium-Wave Broadcast Band

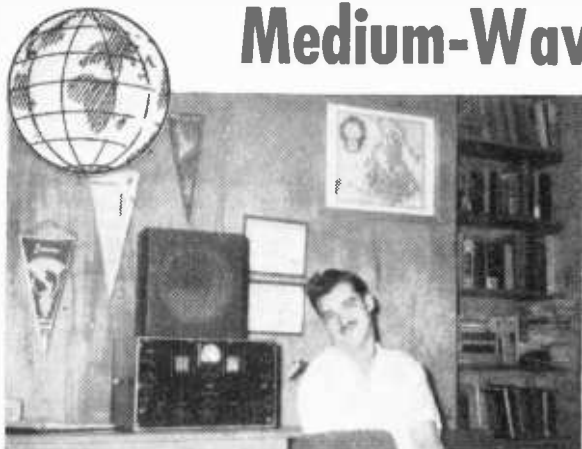

By C. M. STANBURY II

OCCASIONALLY someone mentions distant reception (DX) on the standard, medium-wave broadcast band (535 to 1605 kc, the band you tune in on with your home AM radio set). What do you think of? A 50-kilowatt station in the next state that carries the baseball games? Or maybe you're an old timer and you think of KDKA in Pittsburgh or WWJ in Detroit. Well, my friend, you're selling the broadcast band short! From wherever you're sitting you can reach out and tune in on, say, Hawaii, or New Zealand, and many another far-off spot.

During the minimum sunspot activity from 1953-1955, DX on the broadcast band reached a recent peak. Christmas Mass from Bordeaux, France, was heard in the state of Washington on 1205 kc. (East Coast listeners will be familiar with this spot on the dial—it is just 5 kc below powerful WCAU in Philadelphia.) And on a spring morning in May, 1954, Khabarovsk, Siberia, was heard near Buffalo, N. Y., on 629 kc. In addition, medium-wave hot shots logged and verified the following: VQO, 1030 kc, British Solomon Islands (from Vermont); Voice of America, 1140 kc, Philippines (from Illinois and eastern Canada); and CB106, 1060 kc, Santiago, Chile (from New Mexico).

"Yes," you may say, "but those conditions won't prevail again for another six or seven years." Well, you're still selling the band short. During the season that began in the fall of 1956 and ended in the spring of 1957—a period of very high sunspot activity—the following were heard and confirmed: 4VA, 1080 kc, Port au Prince, Haiti (from the state of Wash-

ington); JOKD, 1370 kc, Japan (from Illinois); JOTR and JOJR, two 500-watters on 940 kc, Japan (logged simultaneously by a DX'er in California); and Radio Omdurman, 572 kc, Anglo-Egyptian Sudan (from Vermont).

Convinced? Good. Here's how you can do it:

Tools. The antenna is important, but the receiver is probably considerably more important. Any fairly good outdoor antenna will provide consistently good results if your radio is suitable. Remember, unlike antennas used for short wave reception, a receiving antenna for the broadcast band is—in most cases—not tuned.

(It's usually impractical to try to do so.)

Some DX'ers get by with a very good standard set. However, the communications type receivers are always preferable to standard sets. Their sensitivity is greater, and, even more important, since the broadcast band is undoubtedly the most crowded portion of the radio spectrum, they have *selectivity*. Tops of all sets for BCB DXing are those with crystal selectivity. A crystal is a must for logging those stations operating between the 10 kc FCC allocations (split-frequency stations). When the crystal is turned on and the phasing control adjusted, stations only 4, 3 and even 2 kc apart can be separated.

The majority of American communications re-

TABLE A—WHEN TO LISTEN FOR WHAT			
LISTENER'S AREA	STATION'S AREA	SEASON	LISTENER'S TIME
	(NORTH AMERICA)	(OUTSIDE U. S. & CANADA)	1 1 1 1 2 2 2 2 0 0 0 0 0 0 0 0 6 7 8 9 0 1 2 3 4 1 2 3 4 5 6 7 0
East	N. & S. America	Fall	
East	N. & S. America	Winter	
East	N. & S. America	Spring	
East	Europe & Africa	Fall	
East	Europe & Africa	Winter	
East	Asia & Pac.	Fall	
East	Asia & Pac.	Winter	
East	Pacific	Spring	
East	Asia	Spring	
Central	N. & S. America	Fall	
Central	N. & S. America	Winter	
Central	N. & S. America	Spring	
Central	Europe	Fall	
Central	Europe	Winter	
Central	Africa	Fall	
Central	Africa	Winter	
Central	Pacific	ALL	
West	N. & S. America	Fall	
West	N. & S. America	Spr-Wtr	
West	Europe & Africa	Winter	
West	Pacific	Fall	
West	Pacific	Winter	
West	Pacific	Spring	
West	Asia	Fall	
West	Asia	Winter	
West	Asia	Spring	

TABLE B—STATIONS TO START WITH

STATION	KC	LOCATION	LISTENER'S AREA	WHEN	ADDRESS
XEWA	540	San Luis Potosi, Mexico	Everywhere except N.W.	Before 0200 EST	Cadena Radiodifusora Mexicana, Ayuntamiento 54, Mexico City
CMHQ	640	Santa Clara, Cuba	East & Central	Before 0030 EST	Circuito CMQ, Radio-centrom. Vedado, Habana
TGW	640	Guatemala, Guatemala	East & Central	0030-0130 EST	Radio Nacional. Calle "18 de Septiembre" y 7a Av., Z1
YSS	655	San Salvador, El Salvador	Everywhere except N.Y.C. & Dixie	Before 2400 EST	Radio Nacional, Teatro Nacional
Radio Nacional	655	Lisbon, Portugal	East except N.Y.C.	1700-1900 EST	Rua de Quelhas 2
YNDS, Union Radio	665	Managua, Nicaragua	Everywhere except N.Y.C. & Chicago	Before 0200 EST	
JOBK	670	Osaka, Japan	West	Early AM	N.H.K.
KULA	690	Honolulu, T. H.	Everywhere	0300 EST Mon AM	
1YZ	800	Rotorua, New Zealand	Everywhere	0300-0500 EST	P. O. Box 298
JOBK	830	Osaka, Japan	West	Early AM	N.H.K.
CMBZ	830	Habana, Cuba	East	Before 2400 EST	Radio Salas, San Rafael 108, Segundo Piso
HJKC	840	Bogota, Colombia	East & West	Before 2400 EST	CARACOL, Calle 19, No. 9-48
TGJ	880	Guatemala, Guatemala	West	Early Evening	Radio Nuevo Mundo, 6a Av., 10-45, Z1
Radio Africa	935	Tangier, Morocco	East	0200 EST (Winter)	9 rue de Russie
YVMF	1120	Maracaibo, Venezuela	East	1800-2000 EST	Ondas del Lago, Apartado 261
Voice of America	1140	Okinawa	West	Early AM	Washington 25, D. C.
N.W.D.R.	1586	West Germany	East	2255-0100	Nordduetscher, Rundfunk, Hamburg 13

TIME CONVERSIONS

CST equals EST minus 1 hour
MST equals EST minus 2 hours
PST equals EST minus 3 hours

ceivers are manufactured by: 1) Hallicrafters Company, 4401 W. 5th Ave., Chicago 24, Illinois; 2) Hammarlund Manufacturing Co., 460 W. 34th St., New York 1, N. Y.; 3) National Company, Malden 48, Massachusetts. Write these companies for information on their receivers, then study it carefully.

When you have your receiver, get a good reference log. For the U. S., and its territories, and for Canada, *White's Radio Log* (see pages 161-191) is a very complete and excellent reference. For Europe, most stations in Asia and the Pacific, and many stations in North and South America, the *World Radio Handbook* is very good. It is available from Gilfer Associates, P. O. Box 239, Grand Central Station, New York 17, for \$2.20. It gives addresses, although usually a station's call letters or slogan can be used in lieu of a street address. (Incidentally, many foreign stations identify by their slogan, not their call letters.)

Finally the U. S. Government Printing Office, Washington 25, D. C., issues the following:

Lists All Foreign Stations by Country and City . . . \$1.50
Catalogue No. Pr. 34.659:957/pt.1
Stations by Frequency . . . \$1.50
Pr. 34.659:957/pt.2
Station Name or Slogan. \$1.25
Pr. 34.659:957/pt.3

The best way to know what is being heard, and thus what to try for, is to belong to a radio club. The National Radio Club, R. D. 1, Lake City, Pennsylvania, devotes about 99% of its activities to the broadcast band. The Newark News Radio Club, 215 Market St., Newark 1, N. J., also has a good broadcast band section in its bulletin. The best times to look, and what to look for first, are given in Tables A and B of this article.

Reporting. The payoff for most DX hunters is the verification card or letter. In this connection, the method of reporting is obviously very important: the program data you give must establish the validity of your report to the satisfaction of the station.

As an absolute minimum, there must be a complete general description of the program or programs heard. Much better than the general description is the definite item system. Commercials, program name, announcer's name, etc., would all be definite items. A minimum of two items is usually required, three is preferable. Song titles generally will not do because many stations keep no record of them. (Major exceptions are programs or tests transmitted especially for DX'er and those few European and Asiatic stations which keep extremely complete records.)

When you are logging the rare station, very often the above orthodox methods must be adapted to fit conditions. Say that the station is heard very poorly. The DX'er must take what program data he can get because he probably won't get another chance at the station. So he combines the description and definite item methods. And he accurately describes the announcer's voice, or notes an unusually long period of dead air. The possibilities are endless; 90% of the occasions when a rare station is logged but impossible to report, the reason is that the DX'er was not alert enough.

When you write a station for verification, always enclose return postage. If you cannot obtain foreign stamps from a dealer, get International Reply Coupons from the post office. You can expect just about anything from medium-wave broadcast band DX. Unlike short-wave, DX, it is *always* difficult. But like short wave, everything is possible. Because of this, it represents the greatest DX challenge a listener can take on.



WHITE'S RADIO LOG

An up-to-date broadcasting directory
AM, FM, TV and Short-Wave Stations

Vol. 35 No. 2

Every effort has been made to ensure accuracy of the information listed in this publication, but absolute accuracy is not guaranteed and of course, only information available up to press-time could be included. Copyright 1958 by Science and Mechanics Publishing Co., 450 East Ohio St., Chicago 11, Ill.

QUICK REFERENCE INDEX

U.S. AM Broadcasting Stations

Listed Alphabetically by Call Letters.....162

Canadian AM Broadcasting Stations

Listed Alphabetically by Call Letters.....169

U.S. and Canadian AM Stations

Grouped According to Frequency.....169

Mexican AM Stations

Listed Alphabetically by Location within States...177

U.S. and Canadian AM Stations

Listed Alphabetically by Location.....178

World-Wide Short-Wave Stations

Listed by Frequency.....185

Canadian Short-Wave Stations

Listed by Frequency.....187

U.S. FM Broadcasting Stations

Listed Alphabetically by Location within States.....187

Canadian FM Broadcasting Stations

Listed Alphabetically by Location.....189

U.S. Television Stations

Listed Alphabetically by Location.....189

Canadian Television Stations

Listed Alphabetically by Location.....191

History of White's Radio Log

White's Radio Log was founded in Providence, R. I., by Charles DeWitt White as an extension of his earlier publishing activities which, in turn, were a continuation of the business established by his father: the publication of city directories, street guides and municipal tax guides.

In the early days of broadcasting, the compilation of a list of operating stations and their frequencies was no simple task. Prior to the Dill-White Radio Act of 1927, if a feed merchant, auto dealer, barber or undertaker wanted to advertise his wares or services, he had only to select a frequency and go on the air.

Nevertheless, Mr. White's directory publishing experience had convinced him that he could successfully assemble a radio log, and in 1924 he justified this conviction with *The Rhode Island Radio Call Book*, following this shortly after with *White's Triple List of Radio Broadcasting Stations*.

In 1927 the two publications were merged, nation-wide distribution was established and in ensuing years related publications, such as *Sponsored Radio Programs*, *Radio Announcer's Guide*, *Short-Wave Schedule Guide* and a special Canadian edition of *White's Radio Log* (which had had its title shortened to the one it bears today), were also issued. The Log reached a combined circulation of well over 1,000,000 copies at one time.

The Fall-Winter number of the 1927 Log listed 701 U.S. Stations. Most powerful were WEAJ (now WRCA), N.Y., with 50,000 watts, KDKA, Pittsburgh, WGY, Schenectady, and WJZ (now WABC), N. Y., each with 30,000 watts; WGN-WLIB, Chicago, with 15,000 watts; and Boston's WBZ, also with 15,000. Five stations listed (one a Junior

High School in Norfolk, Va.) operated on a mighty 5 watts.

In 1957, Mr. White, who was then 76 years old, died in his sleep. His heirs sold all rights in and to the Log to Science and Mechanics Publishing Company and in January of this year the first edition of *White's Radio Log* released under our auspices—Vol. 35, No. 1—was published as a special supplement to the *Radio-TV Experimenter* (Vol. 6).

This current edition of the Log—Vol. 35, No. 2—cross-indexes over 3100 U.S. standard broadcast (AM) stations, separately lists U.S. frequency modulation (FM) and television stations, has a complete compilation of Canadian broadcasters and, in addition, has a greatly expanded list of world-wide short-wave stations that identifies those stations beaming regular evening broadcasts to the United States. Completely new to the Log with this edition is a list grouped by state and city of Mexican stations that can be heard in the United States. Finally, over 2000 changes (2438 precisely) have been made in this edition to bring the listings up-to-date, and to make them as complete, as is humanly possible.

White's Radio Log is under continuous revision as new stations came on the air and others go off. Wark an revision to make the next edition even more complete and useful has already begun. To this end, any changes that you, as a user of the Log, have to suggest will be greatly appreciated.

W.D. Engeman
Publisher

Science and Mechanics

United States

Standard Broadcast (AM) Broadcasting Stations Listed Alphabetically by Call Letters
 C.L., call letters; Kc., frequency in kilocycles (for watt power of station, see list arranged by frequency, p. 169)

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
DYBU	Cebu, P.I.	1260	KBLF	Red Bluff, Calif.	1490	KCRV	Caruthersville, Mo.	1370	KFBI	Wichita, Kans.	1070
DZPI	Manila, P.I.	800	KBLI	Blackfoot, Idaho	690	KCSB	San Bernardino, Calif.	1350	KFBK	Sacramento, Calif.	1530
DZRH	Manila, P.I.	710	KBLO	Hot Springs, Ark.	1410	KCSJ	Pueblo, Colo.	590	KFDA	Amarillo, Tex.	1440
KAAA	Kingman, Ariz.	1230	KBMI	Henderson, Nev.	1400	KCSR	Chadron, Nebr.	1450	KFDM	Seaumont, Tex.	560
KABC	Los Angeles, Calif.	790	KBMM	Alhambra, Mont.	1270	KCTI	Gonzales, Tex.	1450	KBR	Grand Rapids, Wash.	1010
KABI	Ketchikan, Alaska	580	KBMD	Benson, Minn.	1290	KCTX	Childress, Tex.	1510	KFEL	Pueblo, Colo.	970
KABR	Aberdeen, S. Dak.	1220	KBMW	Breckinridge, Minn.	1450	KCUW	Red Wing, Minn.	1250	KFEQ	St. Joseph, Mo.	680
KACT	Andrews, Tex.	1360	KBMX	Coalinga, Calif.	1470	KCVL	Fort Worth, Tex.	1540	KFFA	Helena, Ark.	1360
KADA	Ada, Okla.	1230	KBMY	Billings, Mont.	1240	KCVL	Colville, Wash.	1270	KFGO	Fargo, N.Dak.	790
KADO	Marshall, Tex.	1410	KBND	Bend, Oreg.	1110	KCVR	Lodi, Calif.	1570	KFGQ	Boone, Iowa	1260
KAFP	Petaluma, Calif.	1490	KBNZ	Lajunta, Colo.	1480	KCVL	Lampasas, Tex.	1450	KFGT	Freemont, Nebr.	1340
KAFY	Bakersfield, Calif.	550	KBNO	Kennett, Mo.	830	KDAC	Fort Bragg, Calif.	1230	KFH	Wichita, Kans.	1380
KAGE	Winona, Minn.	1570	KBDE	Dakalooma, Iowa	740	KDAD	Duluth, Minn.	610	KFI	Los Angeles, Calif.	840
KAGH	Crossett, Ark.	800	KBOA	Boise, Idaho	950	KDAN	Eureka, Calif.	790	KFIR	North Bend, Oreg.	1340
KAGT	Anacortes, Wash.	1340	KBOB	Bolander, Ark.	1310	KDAY	Lubbock, Tex.	580	KFIV	Modesto, Calif.	1360
KAGR	Yuba City, Calif.	1450	KBDL	Malvern, Colo.	1490	KDAY	Santa Monica, Calif.	1580	KFIZ	Fond du Lac, Wis.	1450
KAHU	Auburn, Calif.	950	KBOM	Mandan, N.Dak.	1270	KDB	Santa Barbara, Calif.	1490	KFJB	Marshalltown, Iowa	1230
KAHU	Waipahu, Hawaii	820	KBDN	Omaha, Nebr.	1480	KDBC	Mansfield, La.	1360	KFJ	Klamath Falls, Oreg.	1150
KAIM	Kaimuki, Hawaii	870	KBOP	Pleasanton, Tex.	1380	KBDL	Dillon, Mont.	800	KFJM	Grand Forks, N.Dak	1370
KAIU	Tucson, Ariz.	1490	KBOR	Brownsville, Tex.	1600	KDBS	Alexandria, La.	1410	KFJZ	Fort Worth, Tex.	1270
KALD	Grants Pass, Oreg.	1270	KBSB	Butte, Mont.	1490	KDD	Dumas, Tex.	800	KFK	Alameda, Calif.	1910
KAKC	Tulsa, Okla.	970	KBOY	Medford, Oreg.	730	KDEC	Desorah, Iowa	1240	KFKF	Bellevue, Wash.	1330
KAKD	Wichita, Kan.	1240	KBPS	Portland, Oreg.	1450	KDEF	Albuquerque, N.Mex.	1150	KFKU	Lawrence, Kans.	1250
KALB	Alexandria, La.	580	KBRC	Mt. Vernon, Wash.	1430	KDEN	Denver, Colo.	1340	KFLD	Floydada, Tex.	900
KALC	Richland, Wash.	960	KBRK	Brookings, S.Dak.	1430	KDES	Palm Spgs., Calif.	920	KFLJ	Walsenburg, Colo.	1380
KALG	Alamogordo, N.Mex.	1230	KBRM	McCook, Nebr.	1300	KDET	Center, Tex.	930	KFLY	Klamath Falls, Oreg.	1450
KALI	Pasadena, Calif.	1430	KBRD	Bremerton, Wash.	1490	KDEX	Dexter, Mo.	1590	KFLV	Corvallis, Oreg.	1240
KALL	Salt Lake City, Utah	910	KBRS	Springdale, Ark.	1340	KDFW	Denton, Tex.	1440	KFLW	Davenport, Iowa	1500
KALM	Thayer, Mo.	1290	KBSV	Soda Springs, Ida.	540	KDHL	Faribault, Minn.	920	KFMB	San Diego, Calif.	540
KALT	Atlanta, Tex.	900	KBRZ	Freeport, Texas	1460	KDIO	Ortonville, Minn.	1350	KFMJ	Tulsa, Okla.	1050
KALV	Alva, Okla.	1430	KBSF	Springhill, La.	1460	KDIX	Hickinson, N.Dak.	1230	KFML	Denver, Colo.	1390
KAMD	Camden, Ark.	910	KBST	Big Spring, Tex.	1490	KDJJ	Holbrook, Ariz.	1270	KFMD	Fair River, Mo.	1200
KAML	Kenedy, Tex.	990	KBTA	Batesville, Ark.	1340	KDKA	Pittsburgh, Pa.	1020	KFNV	Shenandoah, Iowa	920
KAMO	Rogers, Ark.	1390	KBTK	Missoula, Mont.	1340	KKDK	Clinton, Mo.	1280	KFN	Ferrydale, La.	1600
KAMP	El Centro, Calif.	1410	KBTM	Jonesboro, Ark.	1230	KKLA	De River, La.	1010	KFNW	Fargo, N.Dak.	990
KAMQ	Amarillo, Tex.	1010	KBTN	Nashboro, Mo.	1420	KKLM	Salt River, Tex.	1230	KFDR	Lindsay, Nebr.	1240
KAMA	Aspen, Mont.	1010	KBTQ	El Estero, Kans.	1360	KKLD	Detroit Lakes, Minn.	1340	KFLO	Long Beach, Calif.	1280
KAND	Corsicana, Tex.	1340	KBUC	Corona, Calif.	1370	KKLR	Devils Lake, N.Dak.	1240	KFPW	Fort Smith, Ark.	1230
KANE	New Iberia, La.	1240	KBUD	Athens, Tex.	1410	KKMA	Montevideo, Minn.	1450	KFQD	Anchorage, Alaska	790
KANI	Oahu, Hawaii	1150	KBUH	Bridgman City, Utah	800	KKMG	Carthage, Mo.	1490	KFRB	Fairbanks, Alaska	900
KANN	Sinton, Tex.	1590	KBUN	Bemidji, Minn.	1450	KKMS	El Dorado, Ark.	1280	KFRS	San Francisco, Calif.	610
KANO	Anoka, Minn.	1470	KBUR	Burlington, Iowa	1490	KKNT	Denton, Tex.	1440	KFRD	Rosenberg, Tex.	980
KANS	Wichita, Kan.	1480	KBUS	Mexia, Tex.	1480	KKOK	Tyler, Tex.	1330	KFRE	Fresno, Calif.	990
KADK	Lake Charles, La.	1400	KBUJ	Jack, Tex.	1590	KKON	Salinas, Calif.	1480	KFRM	Newark City, Mo.	550
KAPA	Raymond, Wash.	1340	KBVM	Lancaster, Calif.	1380	KKOT	Reno, Nev.	1230	KFRQ	Longview, Tex.	1370
KAPB	Marksville, La.	1370	KBWD	Brownwood, Tex.	1380	KKQN	DeQueen, Ark.	1390	KFRU	Columbia, Mo.	1400
KAPK	Minden, La.	1240	KBYE	Okla. City, Okla.	880	KKRD	Sedalia, Mo.	1490	KFSA	Fort Smith, Ark.	950
KAPR	Douglas, Ariz.	930	KBYE	Anchorage, Alaska	1270	KKRS	Paragould, Ark.	1480	KFSB	Joplin, Mo.	1310
KARE	Atchison, Kan.	1470	KBZY	Salem, Oreg.	1490	KKSD	Deadwood, S.Dak.	980	KFSC	Denver, Colo.	1220
KARK	Little Rock, Ark.	920	KCAL	Redlands, Calif.	1410	KKSN	Denison, Iowa	1580	KFSD	San Diego, Calif.	600
KARM	Fresno, Calif.	1430	KCAP	Helena, Mont.	1340	KKTA	Delta, Colo.	1400	KFSG	Los Angeles, Calif.	1150
KARJ	Jerome, Idaho	1400	KCAR	Carlsbad, Tex.	1340	KKTB	Denison, Tex.	1350	KFTM	Ft. Morgan, Colo.	1400
KARY	Proctor, Mont.	1310	KCBC	Des Moines, Iowa	1390	KKTD	Dubuque, Iowa	1370	KFTV	Paris, Tex.	1250
KASA	Elk City, Okla.	1240	KCBQ	Lubbock, Tex.	1590	KKUB	Hutchinson, Minn.	1260	KFVN	Las Vegas, N.Mex.	1230
KASH	Eugene, Ore.	1600	KCBQ	San Diego, Calif.	1170	KKWT	Stamford, Tex.	1400	KFUD	St. Louis, Mo.	850
KASI	Ames, Iowa	1430	KCBS	San Fran., Calif.	740	KKXU	St. George, Utah	1450	KFVS	Cape Girardeau, Mo.	960
KASL	Newcastle, Wyo.	1240	KCCO	Lawton, Okla.	1050	KKZA	Pueblo, Colo.	1230	KFWB	Los Angeles, Calif.	980
KASM	Albany, Minn.	1350	KCCP	Corpus Christi, Tex.	1150	KEAN	Brownwood, Tex.	1240	KFXD	Nampa, Idaho	590
KAST	Astoria, Ore.	1570	KCEE	Tucson, Ariz.	790	KEAP	Fresno, Calif.	980	KFYN	Bonham, Tex.	1420
KATE	Albert Lea, Minn.	1450	KCFH	Chicago, Ill.	1120	KEBE	Jacksonville, Tex.	1400	KFYU	Lubbock, Tex.	790
KATP	Casper, Wyo.	1400	KCHA	Charleston City, Iowa	1580	KECK	Odesa, Tex.	920	KFYR	Bismarck, N.Dak.	550
KATL	Miles City, Mont.	1340	KCHE	Cherokee, Iowa	1440	KEED	Springfield, Oreg.	1050	KGA	Spokane, Wash.	1510
KATO	Reno, Nev.	1340	KCHI	Chillicothe, Mo.	1010	KEEL	Shreveport, La.	710	KGAF	Gainesville, Tex.	1580
KATR	Corpus Christi, Tex.	1030	KCHJ	Delano, Calif.	1010	KEEN	San Jose, Calif.	1370	KGAK	Gallup, N.Mex.	1330
KATT	Pittsburgh, Calif.	990	KCHR	Charleston, Mo.	1350	KEEP	Twin Falls, Idaho	1450	KGAL	Lebanon, Oreg.	1340
KATY	San Luis Obispo, Cal.	1340	KCHS	Truth or Consequences, N.Mex.	1400	KELA	Centralia, Wash.	1470	KGAN	Grand Rapids, Mich.	1290
KATZ	St. Louis, Mo.	870	KCHV	Coevelite, Calif.	1400	KELD	El Dorado, Ark.	1400	KGAS	Carthage, Tex.	1590
KAUS	Austin, Minn.	1480	KCID	Caldwell, Idaho	1490	KELO	Sioux Falls, S.Dak.	1320	KGAY	Salem, Oreg.	1430
KAVI	Rocky Ford, Colo.	1320	KCIL	Houma, La.	1490	KELK	Elko, Nev.	1240	KGB	San Diego, Calif.	1360
KAVL	Lancaster, Calif.	610	KCIM	Corroll, Iowa	1380	KELP	El Paso, Tex.	920	KGBT	Hartlingen, Tex.	1530
KAVR	Apple Valley, Calif.	960	KCJB	Minot, N.Dak.	910	KENA	Wana, Ark.	1450	KGBX	Springfield, Mo.	1260
KAWL	York, Neb.	1370	KCKN	Kansas City, Kans.	1340	KENA	Toppenish, Wash.	1490	KGCX	Sidney, Mont.	1480
KAWT	Douglas, Ariz.	1450	KCKY	Cooldige, Ariz.	1150	KENI	Anchorage, Alaska	550	KGD	Fergus Falls, Minn.	1250
KAYE	Puyallup, Wash.	1450	KCLA	Pine Bluff, Ark.	1400	KENL	Arcata, Calif.	1340	KGEE	Bakersfield, Calif.	1230
KAYL	Storm Lake, Iowa	990	KCLE	Cleburne, Tex.	1120	KENM	Portales, N.Mex.	1460	KGK	Stirling, Colo.	1230
KAYO	Seattle, Wash.	1150	KCFI	Clifton, Iowa	1490	KENO	Las Vegas, Nev.	1450	KGEM	Boise, Idaho	1340
KAYS	Hays, Mo.	1400	KCLN	Clinton, Iowa	1390	KENS	San Antonio, Tex.	680	KGFL	Tulare, Calif.	1170
KAYT	Rupert, Idaho	970	KCLO	Leavenworth, Kans.	1410	KENS	Shreveport, La.	1550	KGER	Long Beach, Calif.	1390
KBAB	El Cajon, Calif.	910	KCLP	Rayville, La.	980	KEP	Kennewick, Wash.	610	KGEZ	Kalispell, Mont.	600
KBAL	San Saba, Tex.	1410	KCLS	Flagstaff, Ariz.	600	KERP	Eagle Pass, Tex.	1420	KGF	Lawrence, Kans.	1230
KBAM	Longview, Wash.	1220	KCLV	Clavis, N.Mex.	1240	KERS	Kermit, Tex.	600	KGFL	Roswell, N.Mex.	1400
KBAR	Burley, Idaho	1290	KCLW	Hamilton, Tex.	900	KERC	Eastland, Tex.	1590	KGFV	Kearney, Nebr.	1340
KBBA	Benton, Ark.	630	KCLX	Colfax, Wash.	1450	KERG	Eugene, Oreg.	1280	KGFY	Pierre, S.Dak.	630
KBBC	Centerville, Utah	1600	KCMC	Texarkana, Tex.	1230	KERN	Bakersfield, Calif.	1410	KGG	Coffeyville, Kans.	690
KBSB	Buffalo, Wyo.	1450	KCMJ	Palm Spgs., Calif.	1010	KERV	Kerrville, Tex.	1230	KGGM	Albuquerque, N.Mex.	610
KBCB	Oceanlake, Oreg.	1400	KCMD	Kansas City, Mo.	810	KETA	Livingston, Tex.	1440	KGHF	Pueblo, Colo.	1390
KBCL	Bossier City, La.	1220	KCMS	McCombs, Tex.	1450	KEVA	Shamrock, Tex.	1490	KGHI	Grand Rapids, Mich.	1290
KBCS	Grand Prairie, Tex.	730	KCMS	Manitou Spgs., Colo.	1490	KEVA	Minneapolis, Minn.	1440	KGHL	Billings, Mont.	730
KBCC	Waxahachie, Tex.	1390	KCNA	Tucson, Ariz.	580	KEVL	White Castle, La.	1590	KGHM	Brookfield, Mo.	1470
KBEE	Modesto, Calif.	970	KCNI	Broken Bow, Nebr.	1280	KEVE	White Castle, La.	1590	KGIL	San Fernando, Calif.	1260
KBEI	Idabel, Okla.	1240	KCNO	Altuza, Calif.	570	KEVT	Tucson, Ariz.	690	KGIW	Alamosa, Colo.	1490
KBEK	Cartersville, Ga.	1450	KCNY	San Mar, Tex.	1470	KEVU	Portland, Oreg.	1190	KGKB	Tyler, Tex.	1480
KBNM	Branson, Mo.	1280	KCOB	Newton, Iowa	1280	KFAB	Omaha, Nebr.	1110	KGKL	San Angelo, Tex.	960
KBNS	Hot Springs, Ark.	590	KCOG	Centerville, Iowa	1400	KFAM	San Antonio, Tex.	1230	KGKO	Dallas, Tex.	980
KBIA	Columbia, Mo.	1580	KCOH	Houston, Tex.	1430	KEYE	Perryton, Tex.	1400	KGLC	Little Rock, Ark.	1450
KBIF	Fresno, Calif.	900	KCOK	Tulare, Calif.	1270	KEYJ	Jamestown, N.Dak.	1400	KGLN	Glenwood Spgs., Colo.	980
KBIG	Avalon, Calif.	740	KCOL	Fort Collins, Colo.	1410	KEYY	Corpus Christi, Tex.	1440	KGLM	Mason City, Iowa	1300
KBIM	Roswell, N.Mex.	910	KCDN	Conway, Ark.	1250	KEYZ	Provo, Utah	1450	KGLU	Safford, Ariz.	1480
KBIS	Bakersfield, Calif.	970	KCDR	San Antonio, Tex.	1300	KEYZ	Williston, N.Dak.	1450	KGMB	Honolulu, Hawaii	590
KBIX	Missoula, Okla.	1490	KCOA	Allamore, Nebr.	1400	KFB	Omaha, Nebr.	1130	KGMC	Glenwood, Colo.	1120
KBIZ	Olmito, Wyo.	1240	KCOY	Santa Maria, Calif.	1400	KFAC	Los Angeles, Calif.	1310	KGMD	Cape Girardeau, Mo.	1250
KBKC	Mission, Kans.	1480	KCRA	Sacramento, Calif.	1320	KFAL	Fulton, Mo.	1480	KGMS	Sacramento, Calif.	1420
KBKR	Baker, Oreg.	1490	KCRB	Chanute, Kans.	1460	KFAM	St. Cloud, Minn.	1450	KGNB	New Braunfels, Tex.	1420
KBKW	Aberdeen, Wash.	1450	KCRC	Enid, Okla.	1390	KFAR	Fairbanks, Alaska	660	KGNC	Amarillo, Tex.	710
KBLA	Burbank, Calif.	1490	KCRE	Crescent City, Calif.	1240	KFAY	Fayetteville, Ark.	1250	KGND	Dodge City, Kans.	1370
			KCRG	Cedar Rapids, Iowa	1600	KFB	Great Falls, Mont.	1310			
			KCRS	Midland, Tex.	590	KFCB	Cheyenne, Wyo.	1240			
			KCRT	Trinidad, Colo.	1240						

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
KGO	San Francisco, Calif.	810	KKOG	Ogden, Utah	730	KNCK	Concordia, Kans.	1390	KPAM	Portland, Ore.	1410
KGOL	Golden, Colo.	1250	KLAC	Los Angeles, Calif.	570	KNCM	Moberly, Mo.	570	KPAN	Hereford, Tex.	860
KGON	Oregon City, Ore.	1520	KLAD	Klamath Falls, Ore.	900	KNCO	Garden City, Kans.	1050	KPBY	Banning, Calif.	1490
KGOS	Torrington, Wyo.	1490	KLAK	Lakewood, Colo.	1600	KNDC	Hettinger, N.Dak.	1490	KPAC	Chico, Calif.	1060
KGRH	Henderson, Tex.	1000	KLAM	Cordova, Alaska	1430	KNDY	Marysville, Kans.	1570	KPBA	Pine Bluff, Ark.	1590
KGRN	Grinnell, Iowa	1410	KLAM	Madison, Wash.	910	KNEF	Wesboro, Ark.	970	KPBB	Carlsbad, N.Mex.	1410
KGRO	Gresham, Ore.	1230	KLAS	Las Vegas, Nev.	1230	KNEB	Shelbyville, Nebr.	960	KPDN	Pampa, Tex.	1340
KGRT	Las Cruces, N.Mex.	570	KLBN	La Grande, Ore.	1450	KNEC	McAlester, Okla.	1150	KPDQ	Portland, Ore.	800
KGST	Fresno, Calif.	1600	KLCB	Libby, Mont.	1230	KNEL	Brady, Tex.	1490	KPEG	Spokane, Wash.	1380
KGU	Honolulu, Hawaii	760	KLCN	Blytheville, Ark.	910	KNEM	Nevada, Mo.	1240	KPEL	Lafayette, La.	1420
KGVL	Greenville, Tex.	1400	KLCO	Poteau, Okla.	1280	KNET	Palestine, Tex.	1450	KPEP	San Angelo, Tex.	1420
KGVO	Missoula, Mont.	1290	KLEC	Lovington, N.Mex.	630	KNEU	Provo, Utah	1450	KPER	Gilroy, Calif.	1290
KGW	Portland, Ore.	620	KLEA	Jonesville, La.	1490	KNEW	Spokane, Wash.	790	KPET	Lamesa, Tex.	690
KGWA	Enid, Okla.	960	KLEF	El Paso, Tex.	1490	KNEK	Meridian, Kans.	1340	KPFC	Pocatambo, Idaho	910
KGY	Olympia, Wash.	1240	KLM	Los Mochis, Iowa	1410	KNMS	Hanford, Calif.	620	KPIO	Payette, Idaho	1450
KGYN	Gayton, Okla.	1220	KLEN	Killeen, Tex.	1050	KNIM	Maryland, Mo.	1580	KPIP	Cedar Rapids, Iowa	1450
KGYW	Vallejo, Calif.	1190	KLEX	Lexington, Mo.	1570	KNIT	Abilene, Tex.	1280	KPIN	Casa Grande, Ariz.	1260
KHAM	Albuquerque, N.Mex.	1580	KLFT	Golden Meadow, La.	1600	KNLR	N. Little Rock, Ark.	1310	KPKW	Pasco, Wash.	1340
KHAS	Hastings, Nebr.	1230	KLGA	Alгона, Iowa	1600	KNOC	Natchitoches, La.	1450	KPLC	Lake Charles, La.	1470
KHBC	Hilo, Hawaii	970	KLGN	Logan, Utah	1390	KNOE	Monroe, La.	1390	KPLK	Dallas, Ore.	1460
KHBB	Oklmulee, Okla.	1240	KLGR	Redwood Falls, Minn.	1490	KNOG	Nogales, Ariz.	1340	KPMC	Hankensfield, Calif.	1560
KHBM	Monticello, Ark.	1430	KLIC	Monroe, La.	1230	KNOK	Ft. Worth, Tex.	970	KPOA	Bonolulu, T.H.	630
KHBR	Hillsboro, Tex.	1560	KLIF	Fort Worth, Tex.	1190	KNOR	Norman, Okla.	1190	KPOB	Pocatambo, Idaho	1420
KHCV	Clifton, Ark.	1270	KLIJ	Jefferson City, Mo.	950	KNOT	Prescott, Ariz.	1450	KPOF	Denver, Colo.	910
KHEM	Big Springs, Tex.	1470	KLIK	Estherville, Iowa	1340	KNOW	Austin, Tex.	1490	KPOJ	Portland, Ore.	1330
KHEN	Henryetta, Okla.	1590	KLIN	Lincoln, Nebr.	1400	KNOX	Grand Forks, N.Dak.	1310	KPOL	Scottsdale, Ariz.	1440
KHEP	Phoenix, Ariz.	1280	KLIQ	Portland, Ore.	1290	KNPT	Newport, Ore.	1310	KPOL	Los Angeles, Calif.	1540
KHEY	El Paso, Tex.	690	KLIR	Denver, Colo.	990	KNUN	New Ulm, Minn.	860	KPOP	Los Angeles, Calif.	1020
KHFH	Sierra Vista, Ariz.	1230	KLIX	Twin Falls, Idaho	1310	KNUZ	Houston, Tex.	1230	KPOR	Quincy, Wash.	1370
KHHH	Pampa, Tex.	1230	KLIZ	Brainerd, Minn.	1370	KNWS	Waterloo, Iowa	1090	KPOW	Powell, Wyo.	1260
KHIL	Brighton-Cor. Lupton, Colorado	800	KLKC	Parsons, Kans.	1540	KXJ	Los Angeles, Calif.	1070	KPPC	Passaic, Calif.	1240
KHIT	Walla Walla, Wash.	1320	KLLA	Leesville, La.	1350	KOA	Denver, Colo.	850	KPPQ	Wenatche, Wash.	560
KHJ	Los Angeles, Calif.	930	KLLB	Lubbock, Tex.	1450	KOAC	Corvallis, Ore.	550	KPRB	Redmond, Ore.	1240
KHMO	Hannibal, Mo.	1070	KLMO	Longmont, Colo.	1050	KOAL	Price, Utah	1230	KPRC	Houston, Tex.	1340
KHOB	Hobbs, N.Mex.	1280	KLMR	Lamar, Colo.	920	KOAM	Pittsburgh, Kans.	860	KPRK	Livingston, Mont.	1340
KHOG	Fayetteville, Ark.	1450	KLMS	Lincoln, Nebr.	1480	KOB	Albuquerque, N.Mex.	1030	KPRL	Paso Robles, Calif.	1230
KHON	Honolulu, T.H.	1380	KLMX	Clayton, N.Mex.	1450	KOBE	Las Cruces, N.Mex.	1450	KPRS	Riverside, Calif.	1440
KHOT	Madera, Calif.	1250	KLOG	Ogden, Utah	1430	KOBY	San Francisco, Calif.	1550	KPRT	Kansas City, Mo.	1590
KHOZ	Harrison, Ark.	900	KLOH	Osaka, Wash.	1490	KOC	Alton, Tex.	1240	KPST	Prentiss, Miss.	1340
KHO	Spokane, Wash.	590	KLOI	Pinetop, Minn.	1050	KOCS	Ontario, Calif.	1510	KPST	Preston, Idaho	1400
KHSL	Chico, Calif.	1290	KLOK	San Jose, Calif.	1170	KOCY	Oklahoma City, Okla.	1340	KPUL	Carlson City, Nev.	1340
KHUZ	Borger, Tex.	1490	KLOS	Corvallis, Ore.	1340	KODE	Joplin, Mo.	1230	KPUG	Bellingham, Wash.	1170
KHVV	Honolulu, Hawaii	1040	KLOO	Albuquerque, N.Mex.	1450	KODI	Cody, Wyo.	1480	KPVA	Camas, Wash.	1480
KIBE	Palo Alto, Calif.	1220	KLOU	Lake Charles, La.	1580	KODL	The Dalles, Ore.	1440	KQDY	Minot, N.Dak.	1320
KIBH	Seward, Alaska	1340	KLOV	Loveland, Colo.	1570	KODY	North Platte, Nebr.	1240	KQIK	Lakeview, Ore.	1230
KIBL	Beaville, Tex.	1490	KLPL	Lake Providence, La.	1050	KOEL	Delwaco, Wash.	950	KQJ	Everett, Wash.	1230
KIBS	Bishop, Ark.	1230	KLP	Minot, N.Dak.	1350	KOEA	Uma, Ariz.	1240	KQKA	Paducah, N.Mex.	1410
KICA	Clifton, N.Mex.	980	KLPB	Okemah, Okla.	1140	KOEF	Palmdale, Wash.	1500	KQV	Pittsburgh, Pa.	1410
KICD	Spencer, Iowa	1240	KLPW	Union, Mo.	1020	KOFI	Kalispell, Mont.	980	KRAK	Alamogordo, N.M.	1270
KICK	Springfield, Mo.	1340	KLRA	Little Rock, Ark.	1010	KOFO	Ottawa, Kans.	1220	KRAC	Craig, Colo.	550
KICG	Calexico, Calif.	1490	KLRS	Mountain Grove, Mo.	1360	KOFY	San Mateo, Calif.	1050	KRAK	Stockton, Calif.	1140
KID	Idaho Falls, Idaho	590	KLTF	Little Falls, Minn.	960	KOGA	Ogallala, Nebr.	920	KRAL	Rawlins, Wyo.	1420
KIDD	Monterey, Calif.	630	KLTI	Longview, Tex.	1280	KOGT	Orange, Tex.	1600	KRAM	Las Vegas, Nev.	920
KIDO	Boise, Idaho	630	KLTV	Blackwell, Okla.	1580	KOH	Reno, Nev.	630	KRAY	Maricao, Tex.	1360
KIEM	Eureka, Calif.	1480	KLW	Glasgow, Mont.	1240	KOHU	Hermiston, Ore.	1290	KRBA	Lufkin, Tex.	1340
KIEV	Glendale, Calif.	870	KLW	Salt Lake City, Utah	570	KOIM	Omaha, Nebr.	1290	KRBC	Abilene, Tex.	1470
KIFI	Idaho Falls, Idaho	1400	KLUE	Shreveport, La.	1300	KOIN	Portland, Ore.	970	KRBI	St. Peter, Minn.	1310
KIFN	Phoenix, Ariz.	860	KLUV	Evansville, Wyo.	1240	KOJM	Havre, Mont.	610	KRBO	Las Vegas, Nev.	1050
KIFW	Sitka, Alaska	1230	KLUX	Haynesville, La.	1580	KOKA	Shreveport, La.	1050	KRCO	Ridgecrest, Calif.	1360
KIHN	Hugo, Okla.	1340	KLVC	Ladwell, Colo.	1230	KOKO	Warrensburg, Mo.	1450	KRCO	Prineville, Ore.	890
KIHO	Sioux Falls, S.Dak.	1270	KLV	Vivian, La.	1600	KOKX	Keokuk, Iowa	1810	KRCO	Baytown, Tex.	650
KIHR	Hood River, Ore.	1340	KLV	Lasake, Mont.	1490	KOL	Seattle, Wash.	1480	KRDG	Redding, Calif.	1300
KIJV	Huron, S.Dak.	1340	KLVL	Pasadena, Tex.	1480	KOLD	Tucson, Ariz.	1450	KRDD	Colorado Springs, Colo.	1240
KIKS	Sulphur, La.	1310	KLWN	Lawrence, Kans.	1320	KOLE	Port Arthur, Tex.	1340	KRDU	Dinuba, Calif.	1240
KIKI	Honolulu, Hawaii	830	KLWT	Lebanon, Mo.	1230	KOLJ	Quannah, Tex.	1150	KRE	Berkeley, Calif.	1400
KILE	Galveston, Tex.	1400	KLOX	Oakland, Calif.	910	KOLO	Reno, Nev.	920	KREH	Oakdale, La.	900
KILO	Grand Forks, S.Dak.	1440	KLYD	Bakersfield, Calif.	1350	KOLR	Sterling, Colo.	1490	KREI	Farmington, Mo.	800
KILT	Houston, Tex.	610	KLYK	Spokane, Wash.	1230	KOLS	Pryor, Okla.	1570	KREI	Baytown, Tex.	1360
KIMA	Yakima, Wash.	1460	KLYN	Amario, Tex.	940	KOLT	Scottsbluff, Nebr.	1320	KREI	Spokane, Wash.	870
KIML	Gillette, Wyo.	1490	KLYR	Clarksville, Ark.	1360	KOLP	Yucridge, S.Dak.	1490	KRES	Indio, Calif.	1500
KIMO	Independence, Mo.	1510	KLZ	Osaka, Okla.	580	KOMA	Okla. City, Okla.	1520	KRES	St. Joseph, Mo.	1450
KIMN	Denver, Colo.	950	KMA	Shenandoah, Iowa	960	KOMB	Cottage Grove, Ore.	1400	KREW	Sunnyside, Wash.	1330
KIMP	Mt. Pleasant, Tex.	960	KMAA	San Antonio, Tex.	1600	KOME	Tulsa, Okla.	1300	KREX	Grand Junction, Colo.	920
KIND	Independence, Kans.	1010	KMAE	McKinney, Tex.	1600	KOMO	Seattle, Wash.	1000	KRFI	Owatonna, Minn.	1390
KINE	Kingsville, Tex.	1330	KMAK	Fresno, Calif.	1340	KONW	Omak, Wash.	680	KRFI	Grand Island, Nebr.	1430
KING	Seattle, Wash.	1090	KMAU	Tulosa, N.Mex.	1550	KOMY	Watsonville, Calif.	1340	KRGV	Weslaco, Tex.	1290
KINS	Eureka, Calif.	1330	KMAN	Manhattan, Kans.	1350	KONE	Reno, Nev.	1450	KRHG	Duncan, Okla.	870
KINY	Juneau, Alaska	800	KM	Bakersfield, Calif.	1490	KONG	Visalia, Calif.	1490	KRI	Mason City, Iowa	1490
KIOA	Des Moines, Iowa	940	KMAR	Ark. Windy, Ark.	1570	KONI	Phoenix, Ariz.	1400	KRIC	Beaumont, Tex.	1450
KIOX	Bay City, Tex.	1270	KMBC	Kansas City, Mo.	1570	KONO	San Antonio, Tex.	860	KRIE	Odesa, Tex.	1410
KIPA	Hilo, Hawaii	1110	KMBL	Junction, Tex.	1450	KONP	Port Angeles, Wash.	1450	KRIO	McAllen, Tex.	910
KIRP	Seattle, Wash.	710	KMBY	Monterey, Calif.	1280	KOOK	Billings, Mont.	970	KRIP	Phoenix, Ariz.	1230
KIRT	Mission, Tex.	1580	KMCD	Fairfield, Iowa	1570	KOOL	Phoenix, Ariz.	960	KRPF	Miles City, Mont.	1340
KIRX	Kirksville, Mo.	1450	KMCM	McMinville, Ore.	1260	KOO	Omaha, Nebr.	1420	KRKD	Los Angeles, Calif.	1150
KIRH	Sioux Falls, S.Dak.	1230	KMCO	Conroe, Tex.	900	KOOS	Cody, Wyo.	1230	KRKO	Everett, Wash.	870
KIST	Santa Barbara, Calif.	1340	KMFI	Fort Scott, Kans.	1600	KOPR	Billings, Mont.	1600	KRKS	Ridgecrest, Calif.	1240
KIT	Yakima, Wash.	1280	KMFR	Marion, Ore.	1440	KOPY	Allice, Tex.	1070	KRKL	Lawiston, Idaho	1350
KITE	San Antonio, Tex.	930	KMEL	Wenatche, Wash.	1340	KORA	Bryan, Tex.	1240	KRLD	Dallas, Tex.	1080
KITI	Chehalis, Wash.	1420	KMHL	Marshall, Minn.	1400	KORC	Mineral Wells, Tex.	1140	KRLN	Canon City, Colo.	1400
KITN	Olympia, Wash.	1440	KMHT	Marshall, Tex.	1450	KORD	Paduca, Wash.	910	KRLW	Walnut Ridge, Ark.	1320
KITO	San Bernardino, Calif.	1290	KMIL	Carson, Tex.	1330	KORE	Eugene, Ore.	1450	KRMD	Shreveport, La.	1540
KIUL	Garden City, Kans.	1240	KMJJ	Grants, N.M.	980	KORK	Las Vegas, Nev.	1340	KRMG	Tulsa, Okla.	910
KIUN	Pecos, Tex.	1400	KMJK	Fresno, Calif.	580	KORN	Mitchell, S.Dak.	1490	KRMS	Spokane, Wash.	740
KIUP	Ourango, Colo.	930	KMLB	Blaine, Tex.	1440	KORV	Grangeville, Idaho	1490	KRNS	Orange Beach, Mo.	1150
KIYV	Crockett, Tex.	1290	KMLW	Marion, La.	1010	KOSA	Odesa, Tex.	1230	KRNV	The Dalles, Ore.	1300
KIYW	San Antonio, Tex.	1540	KMMJ	Grand Island, Nebr.	750	KOSE	Deerola, Ark.	860	KRNO	San Bernardino, Calif.	1240
KIXL	Dallas, Tex.	1040	KMNO	Marshall, Mo.	1300	KOSF	Nacogdoches, Tex.	1230	KRNR	Roseburg, Ore.	1490
KIXY	Provo, Utah	1400	KMNS	Sioux City, Iowa	620	KOSI	Aurora, Colo.	1430	KRNS	Burns, Ore.	1230
KIYI	Shelby, Mont.	1150	KMOC	Tacoma, Wash.	1560	KOSY	Tarkenton, Ark.	790	KRNT	Oes Moines, Iowa	1350
KJAN	Atlanta, Iowa	1220	KMND	Great Falls, Mont.	360	KOTA	Rapid City, S.Dak.	1380	KRNY	Carney, Nebr.	1460
KJAT	Tomball, Tex.	1440	KMOP	Tucson, Ariz.	1320	KOTN	Fine Bluff, Ark.	1480	KRO	Rice, Minn.	1340
KJBC	Midland, Tex.	1150	KMOR	Orlando, Calif.	1130	KOTS	Del Rio, Tex.	1230	KROD	El Paso, Tex.	600
KJBS	San Francisco, Calif.	1100	KMOX	St. Louis, Mo.	1020	KOV	Valley City, N.Dak.	1490	KROF	Abbeville, La.	960
KJCS	Festus, Mo.	1010	KMPC	Los Angeles, Calif.	710	KOVE	Lander, Wyo.	1330	KROG	Sonora, Calif.	1450
KJKJ	Junction City, Kans.	1420	KMRC	Morgan City, La.	1430	KOVO	Provo, Utah	960	KROP	Brawley, Calif.	1300
KJEF	Jennings, La.	1290	KMRS	Morris, Minn.	1570	KOWB	Laramie, Wyo.	1340	KROS	Clifton, Iowa	1340
KJET	Beaumont, Tex.	1380	KMUL	Muldoon, Tex.	1380	KOWH	Omaha, Nebr.	660	KROW	Oakland, Iowa	1460
KJFJ	Webster City, Iowa	1570	KMUR	Murray, Utah	1230	KOWL	Blind, Calif.	1490	KROV	Crookston, Minn.	1260
KJIM	St. Louis, Mo.	870	KMUS	Muskogee, Okla.	1380	KOXR	Bjornud, Calif.	1490	KROY	Sacramento, Calif.	1240
KJLT	North Platte, Nebr.	970	KMVB	Victoria, B.C.	1440	KOYL	Little Rock, Ark.	1440	KRPL	Moscow, Idaho	1400
KJNO	Juneau, Alaska	830	KMYC	Marysville, Calif.	1410	KOY	Phoenix, Ariz.	550	KRRV	Sherman, Wash.	910
KJOE	Shreveport, La.	1480	KMYR	Denver, Colo.	710	KOYL	Odesa, Tex.	1310	KRTH	Othello, Wash.	1450
KJOY	Stockton, Calif.	1280	KNAF	Fredericksburg, Tex.	1340	KOYN	Billings, Mont.	910	KRSD	Rapid City, S.Dak.	1340
KJR	Seattle, Wash.	950	KNAK	Salt Lake City, Utah	1280	KOZE	Lawiston, Idaho	1300	KRSL	Russell, Kans.	990
KJRG	Newton, Kans.	950	KNAL	Victoria, Tex.	1410	KOZI	Cheban, Wash.	1220	KRSN	Los Alamos, N.Mex.	1490
KJSK	Columbus, Nebr.	900	KNBC	San Francisco, Calif.	680	KOZY	Grand Rapids, Minn.	1490			
KKEY	Yancouver, Wash.	1150	KNBX	Kirkland, Wash.	1540	KPAC	Port Arthur, Tex.	1250			
			KNBY	Newport, Ark.	1						

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
KRTN	Raton, N. Mex.	1490	KTIB	Thibodaux, La.	630	KVNU	Logan, Utah	610	KXL	Portland, Ore.	750
KRTR	Thermopolis, Wyo.	1490	KTIL	Tillamook, Oreg.	1590	KVOA	Tucson, Ariz.	1290	KXLA	Pasadena, Calif.	1110
KRUN	Ballinger, Tex.	1400	KTIP	San Rafael, Calif.	1510	KVOC	Casper, Wyo.	1230	KXLE	Elliensburg, Wash.	1240
KRUS	Ruston, La.	1490	KTJM	Porterville, Calif.	1450	KVOD	Denver, Colo.	630	KXLF	Butte, Mont.	1370
KRUX	Glendale, Ariz.	1360	KTJS	Minneapolis, Minn.	900	KVOE	Emporia, Kans.	1400	KXLG	Helena, Mont.	1240
KRVN	Lexington, Nebr.	1010	KTKE	Seattle, Wash.	1590	KVOG	Ogden, Utah	1490	KXLK	Great Falls, Mont.	1400
KRWC	Forest Grove, Oreg.	1570	KTKE	Hebart, Calif.	1420	KVOL	Lafayette, La.	1330	KXLL	Missoula, Mont.	1450
KRWS	Fort, Tex.	1010	KTLM	Kenai, Alaska	1320	KVOT	Merrittville, Ark.	930	KXLM	Fort, Mont.	1230
KRXK	Rexburg, Idaho	1250	KTNR	Taft, Calif.	1310	KVON	Napa, Calif.	1440	KXLO	Bozeman, Mont.	1450
KRXL	Roseburg, Oreg.	1240	KTNT	Tucson, Ariz.	990	KVOT	Tulsa, Okla.	1170	KXLR	Little Rock, Ark.	1150
KRYS	Corpus Christi, Tex.	1360	KTNU	Tullulah, La.	1380	KVOP	Plainview, Tex.	1400	KXLW	Clayton, Mo.	1320
KSAC	Manhattan, Kans.	580	KTLN	Denver, Colo.	1280	KVOR	Colo. Springs, Colo.	1300	KXLY	Spokane, Wash.	920
KSAL	Salina, Kans.	1150	KTLQ	Mtn. Home, Ark.	1490	KVOS	Bellingham, Wash.	790	KXO	El Centro, Calif.	1230
KSAM	Huntsville, Tex.	1490	KTLQ	Tahlequah, Okla.	1350	KVOU	Uvalde, Tex.	1490	KXOA	Sacramento, Calif.	1470
KSAN	San Francisco, Calif.	1450	KTLR	Rush, Tex.	1580	KVOW	Littletield, Tex.	1490	KXOK	St. Louis, Mo.	630
KSAY	San Francisco, Calif.	1010	KTLL	Texas City, Tex.	920	KVWX	Worshed, Minn.	1290	KXOL	Fort Worth, Tex.	1240
KSBB	Salinas, Calif.	1380	KTML	McAlester, Okla.	1400	KVWY	Yuma, Ariz.	1400	KXOX	Sweetwater, Tex.	1360
KSBC	Liberal, Kans.	1270	KTMC	Marked Tree, Ark.	1580	KVYD	Laredo, Tex.	1490	KXRA	Alexandria, Minn.	1490
KSCJ	Sioux City, Iowa	1360	KTMS	Santa Barbara, Calif.	1250	KVPI	Ville Platte, La.	1050	KXRJ	Russellville, Ark.	1490
KSCO	Santa Cruz, Calif.	1080	KTNC	Falls City, Nebr.	1280	KVRC	Arkadelphia, Ark.	1240	KXRD	Aberdeen, Wash.	1320
KSD	St. Louis, Mo.	550	KTNM	Tucumcari, N. Mex.	1400	KVRS	Salida, Colo.	1340	KXRX	San Jose, Calif.	1500
KSDA	Redding, Calif.	1400	KTNT	Tacoma, Wash.	1400	KVRS	Rock Springs, Wyo.	1360	KXXX	Colby, Kans.	790
KSDN	Aberdeen, S. Dak.	930	KTOE	Mankato, Minn.	1420	KVSA	McGehee, Ark.	1220	KXYZ	Houston, Tex.	1320
KSDO	San Diego, Calif.	1130	KTOH	Lihue, Hawaii	490	KVSB	San Antonio, Tex.	1240	KZMN	Prescott, Calif.	1490
KSEJ	Pocatello, Idaho	930	KTOI	Okla. City, Okla.	1000	KVSC	Admore, Okla.	1200	KYCA	Prescott, Ariz.	1480
KSEK	Pittsburg, Kans.	1340	KTOP	Henderson, Nev.	1280	KVWC	Vernon, Tex.	1490	KYJC	Medford, Oreg.	1230
KSEL	Lubbock, Tex.	950	KTOD	Topeka, Kans.	1490	KVWM	Show Low, Ariz.	1050	KYME	Boise, Idaho	740
KSEM	Moses Lake, Wash.	1470	KTDW	Oklahoma City, Okla.	800	KVWO	Cheney, Wyo.	1370	KYND	Freese, Calif.	1300
KSED	Durant, Okla.	750	KTRB	Modesto, Calif.	860	KWAD	Wadena, Minn.	920	KYNG	Cosby, Oreg.	1420
KSET	El Paso, Tex.	1340	KTRC	Santa Fe, N. Mex.	1400	KWAK	Stuttgart, Ark.	1240	KYNT	Yankton, S. Dak.	1450
KSEW	Sitka, Alaska	1400	KTRF	Lufkin, Tex.	1420	KWAL	Wallace, Idaho	620	KYDK	Houston, Tex.	1590
KSEY	Seymour, Tex.	1230	KTRF	Thief River Falls, Minn.	1230	KWAT	Waterbury, S. Dak.	950	KYDR	Blythe, Calif.	1450
KSFA	Naegedoes, Tex.	860	KTRH	Houston, Tex.	740	KWBE	Beatrice, Nebr.	1410	KYOS	Mered, Calif.	1480
KSFE	Needles, Calif.	1340	KTRI	Sioux City, Iowa	1470	KWBG	Boone, Iowa	1510	KYUO	Greeley, Colo.	1450
KSFD	San Francisco, Calif.	560	KTRM	Beaumont, Tex.	990	KWBR	Oakland, Calif.	1300	KYSM	Mankato, Minn.	1230
KSGM	Ste. Genevieve, Mo.	980	KTRN	Wichita Falls, Tex.	1290	KWBV	Colo. Sprgs., Colo.	740	KYSN	Colorado Sprgs., Colo.	1460
KSIB	Creston, Iowa	1520	KTRV	Bastrop, La.	730	KWBW	Hutchinson, Kans.	1450	KYTE	Pocatello, Idaho	1290
KSID	Sidney, Nebr.	1340	KTRB	San Antonio, Tex.	550	KWCB	Wichita, Ark.	1300	KYUM	Muleshoe, Ariz.	560
KSIG	Crowley, La.	1450	KTSA	San Antonio, Tex.	550	KWCO	Chickasha, Okla.	1590	KYWV	Cleveland, Ohio	1050
KSII	Clatskanie, Ore.	1490	KTSM	Okla. City, Okla.	1600	KWDM	Des Moines, Iowa	1150	KZEA	Shreveport, La.	980
KSIL	Silver City, N. Mex.	1340	KTTN	Tranton, Mo.	1600	KWEB	Rochester, Minn.	1270	KZEE	Weatherford, Tex.	1220
KSIM	Sikeston, Mo.	1400	KTTR	Rolla, Mo.	1490	KWED	Seguin, Tex.	1580	KZEY	Tyler, Tex.	690
KSIN	Sedalia, Mo.	1050	KTTS	Springfield, Mo.	1400	KWEI	Weiser, Idaho	1200	KZIN	Coeur d'Alene, Idaho	1050
KSIV	Woodward, Okla.	1450	KTUC	Tucson, Ariz.	1400	KWEL	Midland, Tex.	1580	KZIP	Amarillo, Tex.	1310
KSIX	Corpus Christi, Tex.	600	KTUL	Tulla, Tex.	1260	KWEM	Memphis, Tenn.	990	KZOU	Prescott, Ariz.	1340
KSJB	Jamestown, N. Dak.	600	KTLU	Lookout Mountain, Okla.	1430	KWFC	Hobart, N. Mex.	1350	KZUA	Winston-Salem, Wash.	630
KSJO	San Jose, Calif.	1590	KTUR	Turlock, Calif.	1490	KWFG	Hot Springs, Ark.	1390	KZUB	Winston-Salem, N.C.	980
KSJY	Dallas, Tex.	1490	KTUT	Tooele, Utah	990	KWFR	San Angelo, Tex.	1260	WAAB	Worcester, Mass.	1440
KSL	Salt Lake City, Utah	1160	KTVJ	Seattle, Wash.	1250	KWFT	Wichita Falls, Tex.	620	WAAC	Chicago, Ill.	950
KSLM	Salem, Oreg.	1390	KTXC	Big Spring, Tex.	1400	KWGG	Stockton, Calif.	1230	WAAG	Adel, Ga.	1470
KSLQ	Opelousas, La.	1230	KTXJ	Jasper, Tex.	1350	KWGB	Goodland, Kans.	730	WAAY	Huntsville, Ala.	1550
KSLR	Oceanside, Calif.	1320	KTXL	San Angelo, Tex.	1340	KWHK	Brenham, Tex.	1280	WABA	Agua Dulce, P. Rico	850
KSLV	Monte Vista, Colo.	1240	KTKX	Austin, Tex.	1370	KWHK	Hutchinson, Kans.	1260	WABB	Mobile, Ala.	1480
KSMA	Santa Maria, Calif.	1240	KTKN	Inglewood, Calif.	1450	KWHO	Waterbury, S. Dak.	950	WABC	New York, N.Y.	770
KSM	Seminole, Tex.	1250	KTKM	Yuba City, Calif.	1600	KWHO	Salt Lake City, Utah	860	WABG	Grandwood, Miss.	860
KSMN	Mason City, Iowa	1400	KUBA	Yuba City, Calif.	1600	KWHS	Altus, Okla.	1450	WABI	Banner, Maine	1190
KSMO	Salem, Mo.	1340	KUBC	Montross, Colo.	580	KWIC	Salt Lake City, Utah	1570	WABJ	Adrian, Mich.	1490
KSN	Dens Snyder, Tex.	1450	KUBE	Pendleton, Oreg.	1050	KWIK	Pocatello, Idaho	1240	WABL	Amite, La.	1590
KSO	Des Moines, Iowa	1460	KUDI	Great Falls, Mont.	1450	KWL	Albany, Oreg.	790	WABM	Houlton, Maine	1340
KSOA	Arkansas City, Kans.	1280	KUDL	Kansas City, Mo.	1380	KWIN	Ashland, Oreg.	1400	WABO	Waynesboro, Miss.	990
KSON	San Diego, Calif.	1240	KUDV	Ventura, Calif.	1590	KWJ	Douglas, Wyo.	1050	WABR	Winter Park, Fla.	1440
KSD	Sioux Falls, S. Dak.	1140	KUDY	Littleton, Colo.	1510	KWJ	San Antonio, Calif.	1220	WABY	Albany, N.C.	1590
KSDP	Salt Lake City, Utah	1370	KUEA	Wenatche, Wash.	1410	KWJB	Globe, Ariz.	740	WABZ	Albemarle, N.C.	1010
KSDX	Raymondville, Tex.	1240	KUEQ	El Paso, Tex.	1390	KWJC	Natchitoches, La.	1450	WACA	Camden, S.C.	1590
KSPA	Santa Paula, Calif.	1400	KUGN	Eugene, Oreg.	950	KWJJ	Portland, Oreg.	1080	WACB	Kittanning, Pa.	1380
KSPI	Stillwater, Okla.	780	KUIK	Hillsboro, Oreg.	1360	KWJQ	Moses Lake, Wash.	1260	WACE	Chicopee, Mass.	730
KSP	Diboll, Tex.	1260	KUIN	Grants Pass, Oreg.	1340	KWK	St. Louis, Mo.	1380	WACK	Newark, N.J.	1420
KSPR	Casper, Wyo.	1470	KUJ	Walla Walla, Wash.	1420	KWKC	Abilene, Tex.	1360	WACL	Waycross, Ga.	570
KSPT	Sandpoint, Idaho	1400	KUKI	Ukiah, Calif.	1400	KWKC	Pasadena, Calif.	1300	WACR	Columbus, Miss.	1050
KSRO	Santa Rosa, Calif.	1350	KUKU	Willow Springs, Mo.	1380	KWLC	Longview, Wash.	1400	WADC	Akron, Ohio	1350
KSRV	Ontario, Calif.	1980	KUL	San Luis, T.H.	690	KWLM	Willmar, Minn.	1340	WAD	Wadesboro, N.C.	1210
KSST	Sulphur Springs, Tex.	1290	KUL	Ephrata, Pa.	730	KWMT	Ft. Dodge, Iowa	540	WADK	Newport, R.I.	1510
KSTA	Coleman, Tex.	1000	KULP	El Campo, Tex.	1390	KWNA	Winnemucca, Nev.	1400	WADP	Kans. Pa.	960
KSTB	Breckenridge, Tex.	1430	KUMA	Pendleton, Oreg.	1290	KWNO	Winona, Minn.	1230	WADS	Ansonia, Conn.	690
KSTL	St. Louis, Mo.	690	KUND	Corpus Christi, Tex.	1400	KWOD	Wadena, Minn.	730	WABE	Allentown, Pa.	790
KSTN	Stockton, Calif.	1420	KUOA	Siloam Springs, Ark.	1290	KWOC	Poplar Bluff, Mo.	830	WABF	Albemarle, P. Rico	950
KSTP	St. Paul, Minn.	1500	KUOM	Minneapolis, Minn.	770	KWOD	Clinton, Okla.	1020	WAEW	Crossville, Tenn.	1330
KSTR	Grand Junction, Colo.	620	KUPI	Idaho Falls, Idaho	980	KWON	Bartlesville, Okla.	1400	WAF	Stanton, Tenn.	990
KSTT	Davenport, Iowa	1170	KUR	Idaho Falls, Idaho	980	KWOR	Worland, Wyo.	1340	WAGA	Atlanta, Ga.	590
KSTV	Stephenville, Tex.	1510	KURV	Edinburg, Tex.	710	KWOS	Jefferson City, Mo.	1240	WAGC	Chattanooga, Tenn.	1450
KSUB	Cedar City, Utah	590	KUS	Vermillion, S. Dak.	690	KWOW	Pemona, Calif.	1600	WAGE	Leetsburg, Va.	1290
KSUE	Sausalville, Calif.	1240	KUSH	Cushing, Okla.	1600	KWPC	Muscatine, Iowa	860	WAGF	Dothan, Ala.	1320
KSUM	Fairmont, Minn.	1370	KUSN	St. Joseph, Mo.	1270	KWPR	Warrens, Mo.	1490	WAGM	Presque Isle, Maine	1450
KSUN	Bisbee, Ariz.	1230	KUTI	Yakima, Wash.	980	KWRC	Clairemont, Okla.	1270	WAGN	Menominee, Mich.	1340
KSV	Richfield, Utah	980	KUTV	Palmdale, Calif.	1470	KWRD	Henderson, Tex.	1420	WAGS	Bishopville, S.C.	1380
KSVF	Artes, N. Mex.	990	KUYR	Holdrege, Nebr.	1380	KWR	Warren, Ark.	860	WAHL	Hastings, Mich.	1220
KSVA	Graham, N. Mex.	1380	KUZ	Holdrege, Nebr.	1380	KWR	Riverton, Wyo.	1450	WAIL	Baton Rouge, La.	1460
KSVC	Council Bluffs, Iowa	1360	KVAN	Vancouver, Wash.	910	KWRT	Boonville, Mo.	1370	WAIB	Alexandria, N.Y.	1230
KSVO	Lawton, Okla.	1580	KVAS	Astoria, Oreg.	1230	KWRW	Guthrie, Okla.	1490	WAIP	Richard, Ark.	1270
KSWS	Roswell, N. Mex.	1230	KVBC	Farmington, N. Mex.	1390	KWSC	Pulman, Wash.	1250	WAIR	Winston-Salem, N.C.	1340
KSXC	Yreka, Calif.	1490	KVCK	Wolf Point, Nebr.	1490	KWSD	Mt. Shasta, Calif.	1340	WAIT	Chicago, Ill.	820
KSXD	Wichita Falls, Tex.	990	KVCL	Winnfield, La.	1270	KWSH	Wewaka-Seminole, Okla.	1050	WAJF	Deatur, Ala.	1490
KSXL	Alexandria, La.	870	KVCR	Redding, Calif.	600	KWSK	Pratt, Kans.	1070	WAJR	Morgantown, W. Va.	1440
KTAC	Tacoma, Wash.	850	KVCE	San Luis, Calif.	920	KWSO	Waco, Calif.	1260	WAKE	Atlanta, Ga.	1340
KTAE	Taylor, Tex.	1260	KVCF	Vernon, Utah	1250	KWTC	Barstow, Calif.	1290	WAK	Waco, Ga.	950
KTAN	Sherman, Tex.	1500	KVEN	Ventura, Calif.	1450	KWTO	Springfield, Mo.	560	WAKR	Akron, Ohio	1590
KTAR	Phoenix, Ariz.	620	KVET	Austin, Tex.	1300	KWTT	Springfield, Mo.	560	WAKU	Latrobe, Pa.	1570
KTAT	Fredonia, Okla.	1570	KVFC	Cortez, Colo.	740	KWTL	Waco, Tex.	1230	WAL	Mobile, Ala.	1410
KTBB	Tyler, Tex.	600	KVFD	Ft. Dodge, Iowa	1400	KWWL	Waterloo, Iowa	1330	WALB	Albany, Ga.	1590
KTBC	Austin, Tex.	590	KVFG	Great Bend, Kans.	1590	KWYN	Farmington, N. Mex.	960	WALD	Waterboro, S.C.	1220
KTBN	Malden, Mo.	1470	KVHC	O'Neill, Nebr.	1400	KWY	Wynne, Ark.	1400	WALE	Fall River, Mass.	1400
KTCB	Berryville, Ark.	1480	KVHL	Home, Ia.	570	KWYR	Sheridan, Wyo.	1470	WALK	Patehogue, N.Y.	1370
KTCS	Fort Smith, Ark.	1410	KVHM	Seattle, Wash.	570	KWYR	Idaho Falls, Idaho	1260	WALM	Midland, N.Y.	1440
KTEE	Carmel, Calif.	1410	KVIM	Victoria, Tex.	1340	KXAR	Hope, Ark.	1490	WALM	Albion, Mich.	1260
KTEL	Walla Walla, Wash.	1490	KVIN	New Iberia, La.	1360	KXEL	Waterloo, Iowa	1540	WALD	Humaca, P.R.	1240
KTEM	Tempe, Tex.	1400	KVJ	Redding, Calif.	540	KXGI	Ft. Madison, Iowa	1360	WALT	Tampa, Fla.	1110
KTER	Terrill, Tex.	1570	KVKM	Monahans, Tex.	1340	KXGN	Glendive, Mont.	1400	WALY	Herkimer, N.Y.	1420
KTEJ	Livingston, Tex.	1220	KVLC	Cleveland, Tex.	1410	KXIC	Iowa City, Iowa	800	WAM	Aberdeen, Md.	970
KTFI	Twin Falls, Idaho	1270	KVLT	Little Rock, Ark.	1350	KXIG	Glendive, Mont.	1400	WAMI	Opp, Ala.	860
KTFK	Texarkana, Ark.	1400	KVLA	Albion, N.Y.	1400	KXIK	Iowa City, Iowa	800	WAML	Laurel, Miss.	1340
KTFY	Brownfield, Tex.	1400	KVLH	Pauls Valley, Okla.	1490	KXIT	Dalhart, Tex.	1410	WAMH	Hint, Mich.	1400
KTHE	Thermopolis, Wyo.	1240	KVLM	Fallon, Nev.	1250	KXJK	Forrest City, Ark.	950	WAMM	Homestead, Pa.	860
KTHS	Little Rock, Ark.	1090	KVMA	Magnolia, Ark.	630						
KTHT	Houston, Tex.	790	KVNC	Colorado City, Tex.	1320						
			KVNA	Flagstaff, Ariz.	690						
			KVNI	Winstow, Ariz.	1010						
			KVNT	Coeur d'Alene, Idaho	1240						

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
WAMP	Pittsburg, Pa.	1320	WBHB	Fitzgerald, Ga.	1240	WCGA	Calhoun, Ga.	900	WBDB	Dubuque, Iowa	1490
WAMS	Wilmington, Del.	1380	WBHC	Hampden, S.C.	1270	WCGC	Belmont, N.C.	1270	WDFC	Dade City, Fla.	1350
WAMV	E. St. Louis, Ill.	1490	WBHF	Cartersville, Ga.	1450	WCHA	Chambersburg, Pa.	800	WDFI	Tarzon Sprng., Fla.	1470
WAMW	Washington, Ind.	1580	WBHP	Huntsville, Ala.	1230	WCHB	Inksburg, Mich.	1440	WDDR	Hanover, W. Va.	1340
WAMY	Amory, Miss.	1580	WBIA	Augusta, Ga.	1050	WCHF	Chippewa Falls, Wis.	1150	WDDT	Greenville, Miss.	900
WANA	Annisston, Ala.	1490	WBIE	Marletta, Ga.	1050	WCHI	Chillicothe, Ohio	1350	WDDY	Gloucester, Va.	1420
WANB	Waynesburg, Pa.	1490	WBIG	Genesboro, N.C.	1470	WCHJ	Brookhaven, Miss.	1470	WDEC	Americus, Ga.	1290
WAND	Canton, Ohio	900	WBIL	Leesburg, Fla.	1410	WCHK	Canton, Ga.	1290	WDEF	Chattanooga, Tenn.	1370
WANE	Ft. Worth, Tex.	1450	WBIP	Booneville, Miss.	1400	WCHO	Washington Court House, Ohio	1250	WDEH	Sweetwater, Tenn.	800
WANN	Annapolis, Md.	1190	WBIR	Knoxville, Tenn.	1240	WCHL	Chapel Hill, N.C.	1360	WDEL	Wilmington, Del.	1150
WANS	Anderson, S.C.	1280	WBIS	Bristol, Conn.	1440	WCHS	Charlottesville, Va.	950	WDFW	Waterbury, Vt.	550
WANT	Richmond, Va.	990	WBIV	Bedford, Ind.	1340	WCHV	Charlottesville, Va.	1280	WDEW	Westfield, Mass.	1570
WAOK	Atlanta, Ga.	1380	WBIZ	Eau Claire, Wis.	1400	WCIL	Carbondale, Ill.	1020	WDGI	Minneapolis, Minn.	1130
WAOV	Vincennes, Ind.	1450	WBKH	Hattiesburg, Miss.	1400	WCIN	Cincinnati, Ohio	1480	WDIA	Memphis, Tenn.	1070
WAPA	San Juan, P.R.	980	WBKN	Newton, Miss.	1410	WCJL	Columbia, Miss.	1450	WDIX	Dothan, Ala.	1450
WAPF	McComb, Miss.	980	WBKV	West Bend, Wis.	1470	WCJB	Dunn, N.C.	780	WDKJ	Kingstree, S.C.	1310
WAPC	Arcadia, Fla.	1480	WBLA	Elizabethtown, N.C.	1290	WCGR	Greer, S.C.	1300	WDLA	Walton, N.Y.	1270
WAPI	Birmingham, Ala.	1070	WBLE	Batesville, Miss.	1450	WCKR	Miami, Fla.	1530	WDLB	Marshfield, Wis.	1450
WAPL	Appleton, Wis.	1570	WBLG	Lexington, Ky.	1300	WCLT	Newark, Ohio	1430	WDLR	Port Jervis, N.Y.	1490
WAPT	Chattanooga, Tenn.	1150	WBLJ	Dalton, Ga.	1440	WCLB	Camilla, Ga.	1220	WDMF	Panama City, Fla.	590
WAPX	Montgomery, Ala.	1600	WBLO	Evergreen, Ala.	1470	WCLC	Jamestown, Tenn.	1260	WDMG	Douglas, Ga.	860
WAQW	Towson, Md.	1570	WBLS	Batesburg, S.C.	1430	WCLD	Cleveland, Miss.	1490	WDMJ	Marquette, Mich.	1320
WARA	Attleboro, Mass.	1320	WBLS	Batesburg, S.C.	1430	WCLE	Cleveland, Tenn.	1570	WDNC	Durham, N.C.	1400
WARB	Covington, La.	1490	WBLU	Salem, Va.	1480	WCLG	Morgantown, W.Va.	1300	WDNE	Elkins, W. Va.	1240
WARD	Johnstown, Pa.	730	WBLY	Springfield, Ohio	1600	WCLI	Corning, N.Y.	1450	WDNB	Anniston, Ala.	1240
WARE	Ware, Mass.	1250	WBMA	Beaufort, N.C.	1400	WCLD	Janesville, Wis.	1230	WDOB	Canton, Miss.	1370
WARF	Jasper, Ala.	1240	WBMC	McIntinnville, Tenn.	960	WCLS	Columbus, Ga.	1580	WDOC	Prestonsburg, Ky.	1310
WARK	Hagerstown, Md.	1490	WBMD	Baltimore, Md.	750	WCLM	Mansfield, Ohio	1570	WDDC	Chattanooga, Tenn.	1310
WARL	Arlington, Va.	780	WBML	Macon, Ga.	1240	WCLN	Newark, Ohio	1430	WDDK	Dunkirk, N.Y.	1410
WARM	Seranton, Pa.	590	WBNC	Conway, N.H.	1050	WCLW	Ward, Ohio	1460	WDDG	Marine City, Mich.	1590
WARN	Watertown, N.Y.	1240	WBNO	Booneville, Ind.	1540	WCLX	Ward, Ohio	1460	WDDK	Cleveland, Ohio	1260
WARN	Pt. Pierce, Fla.	1600	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDDL	Elkins, Ga.	1470
WARU	Peru, Ind.	1600	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDDO	Wheaton, Md.	1540
WASA	Harve de Grace, Md.	1330	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDOO	Sturgeon Bay, Wis.	910
WASK	Lafayette, Ind.	1450	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDOO	Oreanta, N.Y.	730
WATA	Boone, N.C.	1450	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDOT	Burlington, Va.	1400
WATC	Gaylord, Mich.	900	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDOV	Dover, Del.	1410
WATD	Cheraw, S.C.	1420	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDQN	DeQuoin, Ill.	1580
WATE	Knoxville, Tenn.	620	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDRK	Hartford, Conn.	1360
WATG	Ashland, Ohio	1340	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDSI	Dallas, Ga.	1580
WATH	Athens, Wis.	970	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDSL	Wilmington, S.C.	800
WATK	Antigo, Wis.	900	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDSG	Dyersburg, Tenn.	1410
WATM	Altmore, Ala.	1590	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDSM	Superior, Wis.	750
WATO	Oak Ridge, Tenn.	1490	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDSP	DeFuniak Springs, Fla.	1280
WATP	Marion, S.C.	1430	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDSR	Lake City, Fla.	1340
WATR	Waterbury, Conn.	1320	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDSR	New Orleans, La.	1900
WATS	Says, Pa.	960	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDUN	Gainesville, Ga.	820
WATT	Cadillac, Mich.	1240	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDUX	Waupaca, Wis.	2400
WATW	Ashland, Wis.	1450	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDVZ	Green Bay, Wis.	1400
WATZ	Alpena, Mich.	1450	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDVA	Danville, Va.	1250
WAUC	Wauchula, Fla.	1310	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDVH	Gainesville, Fla.	980
WAUD	Auburn, Ala.	1230	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDVM	Pocomoke City, Md.	540
WAUG	Augusta, Ga.	1050	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDWS	Champaign, Ill.	1400
WAUX	Waukesha, Wis.	1510	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDXB	Chattanooga, Tenn.	1490
WAVE	Louisville, Ky.	970	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDXE	Larewareburg, Tenn.	1370
WAVL	Dayton, Ohio	1210	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDXI	Jackson, Tenn.	1310
WAVL	Appleton, Wis.	910	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDXL	Lexington, Tenn.	1490
WAVP	Avon Park, Fla.	1390	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDKN	Clarksville, Tenn.	540
WAVU	Albertville, Ala.	630	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WDZ	Dallas, Ga.	1050
WAVY	Portsmouth, Va.	1350	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEAB	Greer, S.C.	800
WAVZ	New Haven, Conn.	1300	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEAG	Aloa, Tenn.	1470
WAWK	Kendallville, Ind.	1570	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEAM	Arlington, Va.	1390
WAWZ	Zarephth, N.J.	1350	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEAN	Providence, R.I.	790
WAXE	Yreka Beach, Fla.	1370	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEAS	Decatur, Ga.	1010
WAXB	Waynesboro, Va.	1490	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEAT	W. Palm Beach, Fla.	850
WAYE	Dundalk, Md.	860	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEAU	Waukegan, Wis.	990
WAYN	Rockingham, N.C.	900	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEAW	Plattsburgh, N.Y.	960
WAYS	Charlotte, N.C.	610	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEAW	Evanson, Ill.	1830
WAYX	Waycross, Ga.	1230	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEBB	Dundalk, Md.	1360
WAYZ	Waynesboro, Pa.	1360	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEBD	Wabuc, Minn.	560
WAZA	Bainbridge, Ga.	1360	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEBJ	Brewton, Ala.	1240
WAZF	Yazoo City, Miss.	1230	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEBD	Owego, N.Y.	1240
WAZL	Hazleton, Pa.	1490	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEBQ	Rocky Mount, Ill.	1240
WBAA	West Lafayette, Ind.	920	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEBU	Buffalo, Va.	930
WBAB	Babylon, N.Y.	1440	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEBY	Milton, Fla.	1270
WBAC	Cleveland, Tenn.	1340	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WECL	Eau Claire, Wis.	1050
WBAL	Baltimore, Md.	1090	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEDC	Chicago, Ill.	1240
WBAM	Montgomery, Ala.	1460	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEDR	McKeesport, Pa.	810
WBAP	Ft. Worth, Tex.	570, 820	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEDW	Birmingham, Ala.	1220
WBAR	Bartow, Fla.	1460	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEEB	Southern Pines, N.C.	990
WBAT	Marion, Ind.	1400	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEI	Boston, Mass.	590
WBAX	Wilkes-Barre, Pa.	1240	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEK	Peoria, Ill.	1350
WBAB	Barnwell, S.C.	740	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEPP	Pittsburgh, Pa.	1080
WBAY	Green Bay, Wis.	1360	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEER	Warrenton, Va.	1570
WBBA	Pittsfield, Ill.	1580	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEU	Reading, Pa.	850
WBBC	Burlington, N.C.	920	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEX	Easton, Pa.	1230
WBBC	Filint, Mich.	1330	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEGO	Concord, N.C.	1410
WBFB	Rocheater, N.Y.	950	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEHH	Elmira Heights, N.Y.	1590
WBBI	Abingdon, Va.	1230	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEIC	Charleston, Ill.	1270
WBBL	Richmond, Va.	1480	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEIM	Fitchburg, Mass.	1280
WBBS	Chicago, Ill.	1480	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEIR	Wrlton, W.Va.	1430
WBBS	Perry, Ga.	780	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEJL	Scranton, Pa.	630
WBBO	Forest City, N.C.	980	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEKR	Fayetteville, Tenn.	1340
WBQ	Augusta, Ga.	1340	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEK	Richmond, Ky.	1240
WBW	Youngstown, Ohio	1240	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WEKZ	Monroe, Wis.	1260
WBZ	Ponca City, Okla.	1130	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WELC	Welch, W. Va.	1150
WBCA	Bay Minette, Ala.	1150	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WELD	Fisher, W. Va.	1490
WBCC	Levittown, Pa.	1490	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WELI	New Haven, Conn.	960
WBCK	Battle Creek, Mich.	930	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WELK	Charlottesville, Va.	1010
WBCC	Bay City, Mich.	1440	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WELL	Battle Creek, Mich.	1400
WBCC	Besser, Mo.	1450	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WELM	Elmira, N.Y.	1400
WBCC	Christiansburg, Va.	1450	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WELP	Esley, S.C.	1360
WBCC	Union, S.C.	1420	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WELR	Roanoke, Ala.	1360
WBEC	Pittsfield, Mass.	1460	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460	WELK	Kinston, N.C.	1010
WBEE	Harvey, Ill.	1570	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460			
WBEJ	Elizabethtown, Tenn.	1240	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460			
WBEL	Beloit, Wis.	1380	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460			
WBEN	Buffalo, N.Y.	930	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460			
WBET	Brookton, Mass.	1460	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460			
WBEU	Beaufort, S.C.	960	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460			
WBEV	Beaver Dam, Wis.	1430	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460			
WBEX	Chillicothe, Ohio	1490	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460			
WBFD	Fremont, Mich.	1490	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460			
WBFD	Bedford, Pa.	1310	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460			
WBGC	Chilpey, Fla.	1240	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1460			
WBGR	Jesup, Ga.	1370	WBNS	Columbus, Ohio	1540	WCLM	Ward, Ohio	1			

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
WELY	Ely, Minn.	1450	WFUN	Huntsville, Ala.	1450	WHDF	Houghton, Mich.	1400	WILD	Boston, Mass.	1070
WEMB	Erwin, Tenn.	1420	WFUR	Grand Rapids, Mich.	1570	WHDL	Boston, Mass.	1450	WILE	Cambridge, Ohio	1290
WEMP	Milwaukee, Wis.	1250	WFVA	Fredericksburg, Va.	1230	WHDL	Olean, N.Y.	1450	WILK	Hammant, Conn.	1480
WENA	Bayamon, P.R.	1560	WVFG	Fuquay Sprgs., N.C.	1420	WHDM	McKenzie, Tenn.	1440	WILK	Wilkes-Barre, Pa.	850
WENC	Whiteville, N.C.	1220	WFWL	Cadman, Tenn.	1260	WHEB	Portsmouth, N.H.	750	WILL	Urbana, Ill.	580
WEND	Baton Rouge, La.	1380	WFYC	Alma, Mich.	1280	WHEC	Rochester, N.Y.	1460	WILM	Wilmington, Del.	1450
WENE	Endicott, N.Y.	1430	WGAA	Cedartown, Ga.	1340	WHEE	Martinsville, Va.	1370	WILM	Frankfort, Ind.	1570
WENK	Union City, Tenn.	1240	WGAC	Augusta, Ga.	580	WHEN	Syracuse, N.Y.	620	WILS	Lansing, Mich.	1320
WENS	Washington, Tenn.	1430	WGAD	Gadsden, Ala.	1350	WHER	Memphis, Tenn.	1430	WILZ	St. Petersburg Beach, Florida	1150
WENT	Groversville, N.Y.	1340	WGAF	Adelphi, Ga.	1100	WHFB	Benton Harbor, Mich.	1080	WIMA	Lima, Ohio	1580
WENY	Elmira, N.Y.	1230	WGAI	Elizabeth City, N.C.	560	WHFC	Cicero, Ill.	1450	WIMO	Wino, Ga.	1300
WEOA	Evanston, Ind.	1400	WGAL	Lancaster, Pa.	1490	WHGB	Harrisburg, Pa.	1400	WIMS	Michigan City, Ind.	1420
WEOK	Poughkeepsie, N.Y.	1390	WGAN	Portland, Maine	580	WHGR	Houghton L., Mich.	1290	WINA	Charlotteville, Va.	1400
WEOL	Elyria, Ohio	930	WGAP	Mayville, Tenn.	1400	WHHH	Warren, Ohio	1440	WINC	Winchester, Va.	1400
WEPG	S. Pittsburgh, Tenn.	810	WGAV	Cleveland, Ohio	1340	WHHY	Montgomery, Ala.	1440	WIND	Chicago, Ill.	580
WEPM	Martinsburg, W.Va.	1340	WGAU	Athens, Ga.	1340	WHHM	Memphis, Tenn.	1340	WINE	Kenmore, N.Y.	1080
WFCB	Erie, Pa.	1260	WGAW	Gardner, Mass.	1340	WHIE	Griffin, Ga.	1320	WINT	Dayton, Ohio	1410
WERD	Atlanta, Ga.	860	WGAY	Silver Springs, Md.	1050	WHIM	E. Providence, R.I.	1110	WINT	Murphysboro, Ill.	1420
WERE	Cleveland, Ohio	1300	WGBA	Columbus, Ga.	1270	WHIN	Gallatin, Tenn.	1010	WINK	Fort Myers, Fla.	1240
WERH	Hamilton, Ala.	970	WGBB	Freeport, N.Y.	1240	WHIO	Dayton, Ohio	1290	WINN	Louisville, Ky.	1240
WERI	Westerly, R.I.	1230	WGBE	Evanville, Ind.	1280	WHIP	Mooreville, N.C.	1350	WINR	Binghamton, N.Y.	680
WESA	Charleroi, Pa.	1490	WGBG	Greensboro, N.C.	1400	WHIR	Danville, Ky.	1230	WINS	New York, N.Y.	1010
WESS	Bradford, Pa.	1490	WGBI	Seranton, Pa.	910	WHIS	Bluefield, W.Va.	1440	WINX	Rockville, Md.	1600
WESB	Greenville, S.C.	660	WGBR	Goldboro, N.C.	1150	WHIT	New Bern, N.C.	1450	WINZ	Miami, Fla.	940
WESC	Southton, Mass.	870	WGBS	Miami, Fla.	1310	WHIY	Orlando, Fla.	1270	WIOD	Sanford, Fla.	1360
WESR	Tasley, Va.	1350	WGBL	Re. Lion, Pa.	1440	WHIZ	Zanesville, Ohio	1240	WION	Ionla, Mich.	1430
WEST	Easton, Pa.	1400	WGCD	Chester, S.C.	1490	WHJB	Greensboro, Pa.	820	WIOW	Kokomo, Ind.	1350
WESX	Salem, Mass.	1230	WGCM	Gulfport, Miss.	1240	WHJC	Matawan, W.Va.	1360	WIPI	Philadelphia, Pa.	610
WETB	Johnson City, Tenn.	790	WGEE	Geneva, Ala.	1150	WHJK	Cleveland, Ohio	1420	WIPA	Annapolis, Md.	810
WETO	Gadsden, Ala.	930	WGEN	Indianapolis, Ind.	1590	WHKK	Akron, Ohio	640	WIPC	Lake Wales, Fla.	1280
WETU	Wetumpka, Ala.	1250	WGES	Georgetown, S.C.	1390	WHKM	Hendersonville, N.C.	1450	WIPR	San Juan, P.R.	940
WETZ	New Martinsville, W. Virginia	1330	WGET	Beloit, Wis.	1490	WHKY	Hickory, N.C.	1290	WIPS	Ticonderoga, N.Y.	1250
WEUC	Ponce, P.R.	1420	WGFZ	Covington, Ga.	1430	WHLB	Virginia, Minn.	1400	WIRA	Fort Pierce, Fla.	1400
WEVA	Emporia, Va.	860	WGFA	Gainesville, Ga.	550	WHLD	Albany, N.Y.	1270	WIRE	Enterprise, Ala.	1230
WEVD	New York, N.Y.	1330	WGGA	Gainesville, Fla.	1230	WHLF	South Boston, Va.	1400	WIRC	Hickory, N.C.	1430
WEVE	Eveleth, Minn.	770	WGGB	Gainesville, Fla.	1230	WHLI	Hempstead, N.Y.	1100	WIRE	Indianapolis, Ind.	1430
WEW	St. Louis, Mo.	770	WGHC	Marion, Ill.	1150	WHLL	Wheeling, W.Va.	1600	WIRK	W. Palm Beach, Fla.	1290
WEWO	Laurinburg, N.C.	1080	WGHD	Salamanca, N.Y.	1590	WHLM	Bluffsburg, Pa.	550	WIRL	Peoria, Ill.	1290
WEWL	Royal, Mich.	1340	WGH	Newburg, Va.	1450	WHLN	Harlan, Ky.	1410	WIRU	Ironton, Ohio	1230
WEYE	Sanford, N.C.	1290	WGHM	Skewegan, Maine	1150	WHLS	Port Huron, Mich.	1450	WIRU	Humboldt, Tenn.	740
WEZB	Homewood, Ala.	1320	WGHN	Grd. Haven, Mich.	1370	WHLS	Port Huron, Mich.	1450	WIRY	Plattsburg, N.Y.	1340
WEZE	Boston, Mass.	1260	WGIB	Brunswick, Ga.	1440	WHMA	Albany, Ala.	1380	WIS	Columbia, S.C.	560
WEZL	Richmond, Va.	1590	WGIL	Galesburg, Ill.	1400	WHMI	Howell, Mich.	350	WISC	Clinton, Wis.	1490
WEZY	Cocoa, Fla.	1480	WGIR	Manchester, N.H.	610	WHMP	Northampton, Mass.	1400	WISL	Asheville, N.C.	1310
WFAA	Dallas, Tex.	570, 820	WGIV	Charlotte, N.C.	1600	WHMS	Charleston, W.Va.	1490	WISH	Indianapolis, Ind.	1310
WFAB	Allison, Ohio	1310	WGKA	Atlanta, Ga.	1600	WHNC	Henderson, N.C.	890	WISK	St. Paul, Minn.	1590
WFAR	Farell, Pa.	1470	WGK	Charleston, W.Va.	1300	WHNY	McComb, Miss.	1250	WISL	Shamokin, Pa.	1480
WFAS	White Plains, N.Y.	1230	WGL	Fort Wayne, Ind.	1580	WHOA	Des Moines, Iowa	1040	WISN	Milwaukee, Wis.	1160
WFAU	Augusta, Me.	1420	WGLC	Centerville, Miss.	1320	WHOS	San Juan, P.R.	1480	WISN	Ponce, P.R.	1280
WFAZ	Falls Church, Va.	1220	WGMA	Hollywood, Fla.	570	WHOC	Chillicothe, Miss.	1490	WISN	Clinton, N.C.	1230
WFB	Greenville, S.C.	1330	WGMS	Washington, D.C.	720	WHOK	Lancaster, Ohio	620	WISR	Butler, Pa.	630
WFB	Fernandina Beach, Fla.	1570	WGN	Chicago, Ill.	1450	WHOL	Allentown, Pa.	1300	WISV	Charlottesville, N.C.	930
WFB	Altoona, Pa.	1340	WGNU	Wilmington, N.C.	1450	WHOM	New York, N.Y.	1480	WISV	Viroqua, Wis.	1360
WFB	Syracuse, N.Y.	1260	WGNW	Newburgh, N.Y.	1220	WHOO	Orlando, Fla.	990	WITA	San Juan, P.R.	1140
WFBM	Indianapolis, Ind.	1300	WGOL	Goldboro, N.C.	1300	WHOP	Hopkinsville, Ky.	1280	WITB	Baltimore, Md.	1230
WFB	Baltimore, Md.	1300	WGOR	Georgetown, Ky.	1580	WHOS	Decatur, Ala.	800	WITT	Lewisburg, Pa.	1010
WFB	St. Walton Beh., Fla.	930	WGVA	Valdosta, Ga.	950	WHOT	Campbell, Ohio	1570	WITY	Danville, Ill.	980
WFCR	Fairfax, Va.	1310	WGPA	Bethlehem, Pa.	1100	WHOW	Custer, Ind.	1020	WITZ	Asheville, N.C.	990
WFD	Flint, Mich.	910	WGPC	Albany, Ga.	1450	WHPR	Harrisburg, Pa.	1400	WIV	Christiansburg, V.I.	1040
WFD	Manecheater, Ga.	1370	WGRI	Buffalo, N.Y.	790	WHPS	Belton, S.C.	1390	WIVK	Knoxville, Tenn.	860
WFEA	Manecheater, N.Y.	1340	WGRA	Cairo, Ga.	790	WHPE	High Point, N.C.	1070	WIVV	Vloques, P.R.	1370
WFE	Sylvauga, N.Y.	1220	WGR	Louisville, Ky.	790	WHRT	Hartselle, Ala.	880	WIVY	Jacksonville, Fla.	1050
WFEC	Miami, Fla.	1220	WGRD	Grand Rapids, Mich.	1410	WHRV	Ann Arbor, Mich.	1410	WIZE	Springfield, Ohio	1410
WFGM	Fitchburg, Mass.	1570	WGRF	Aguadella, P.R.	1340	WHSC	Hartsville, S.C.	1450	WIZZ	Streator, Ill.	1250
WFGN	Gaffney, S.C.	980	WGRM	Greenwood, Miss.	1240	WHSM	Hayward, Wis.	910	WJAC	Johnstown, Pa.	1400
WFHG	Bristol, Va.	1430	WGRV	Greeneville, Tenn.	1340	WHST <td>Clinton, Miss.</td> <td>1450</td> <td>WJBS</td> <td>Wilmington, N.C.</td> <td>780</td>	Clinton, Miss.	1450	WJBS	Wilmington, N.C.	780
WFHK	Pell City, Ala.	1430	WGRY	Gary, Ind.	1370	WHTB	Tallega, Ala.	1230	WJAK	Jackson, Tenn.	810
WFHR	Wis. Rapids, Wis.	1290	WGSA	St. Albans, Ga.	1400	WHTC	Holland, Mich.	1450	WJAM	Marion, Ala.	1400
WFH	Sumter, S.C.	560	WGSM	Huntington, N.Y.	740	WHTG	Eatontown, N.J.	1410	WJAR	Providence, R.I.	920
WFIL	Philadelphia, Pa.	1310	WGST	Atlanta, Ga.	920	WHTN	Huntington, W.Va.	800	WJAS	Pittsburgh, Pa.	1320
WFIN	Findlay, Ohio	1600	WGSV	Guntersville, Ala.	1220	WHUB	Cookeville, Tenn.	1400	WJAT	Swainsboro, Ga.	800
WFIS	Fountain Inn, S.C.	1390	WGSW	Greenwood, S.C.	1350	WHUC	Hudson, N.Y.	1230	WJAX	Jacksonville, Fla.	930
WFIV	Fairfield, Ill.	1220	WGTA	Summerville, Ga.	850	WHUM	Reading, Pa.	1240	WJAY	Hillins, S.C.	1280
WFK	Franklin, Ky.	1490	WGTC	Greenville, N.C.	1590	WHUN	Huntzberg, Pa.	1500	WJBB	Haleyville, Ala.	1230
WFKY	Frankfort, Ky.	1270	WGTM	Wilson, N.C.	590	WHVF	Vauxau, Wis.	1230	WJBC	Bloomington, Ill.	1230
WFLA	Tampa, Fla.	1490	WGTV	Georgetown, S.C.	1400	WHVH	Henderson, N.C.	1450	WJBD	Bloomington, Ill.	1230
WFLB	Fayetteville, N.C.	1490	WGUY	Bangor, Maine	1230	WHVR	Hanover, Pa.	1280	WJBE	Salem, Ill.	1350
WFL	Farmville, Va.	1570	WGVA	Geneva, N.Y.	1240	WHWB	Rutland, Vt.	700	WJBK	Detroit, Mich.	1500
WFLR	Dundee, N.Y.	1360	WGV	Greenville, Miss.	1260	WHWL	Nanticoke, Pa.	1030	WJBL	Holland, Mich.	1260
WFLW	Monticello, Ky.	930	WGW	Greenville, N.Y.	1340	WHXY	Bogalusa, La.	920	WJBO	Baton Rouge, La.	1150
WFM	Goldboro, N.C.	730	WGWG	Seima, Ala.	1240	WHYE	Roanoke, Va.	910	WJBS	Dallas, Fla.	1490
WFM	Frederick, Md.	1480	WGW	Asheboro, N.C.	1280	WHYN	Carlisle, Pa.	1430	WJBW	New Orleans, La.	1430
WFMH	Cullman, Ala.	1480	WGY	Schenectady, N.Y.	810	WHYN	Springfield, Mass.	560	WJCD	Seymour, Ind.	1390
WFMJ	Youngstown, Ohio	1390	WGYV	Greenville, Ala.	1380	WHYS	Ocala, Fla.	1370	WJCM	Sebring, Fla.	960
WFM	Mountaintop, N.C.	860	WHM	Madison, Wis.	970	WIAC	San Juan, P.R.	580	WJDA	Quincy, Mass.	1300
WFMW	Madisonville, Ky.	730	WHAB	Baxley, Ga.	1260	WIAM	Williamston, N.C.	900	WJDB	Thomasville, Ala.	630
WFNC	Fayetteville, N.C.	1390	WHAI	Greenfield, Mass.	1240	WIBA	Madison, Wis.	1310	WJDX	Jackson, Miss.	620
WFNN	DeFuniak Springs, Florida	1480	WHAK	Rogers City, Mich.	980	WIBB	Macon, Ga.	1280	WJEF	Grand Rapids, Mich.	1230
WFNS	Burlington, N.C.	1150	WHAL	Shelbyville, Tenn.	1400	WIBC	Indianapolis, Ind.	1070	WJEG	Salisbury, Ohio	980
WFOB	Fosteria, Ohio	1430	WHAM	Rochester, N.Y.	1180	WIBD	Jackson, Miss.	1450	WJEM	Hesperston, Ohio	1240
WFO	Marietta, Ga.	1230	WHAN	Cheriton, S.C.	1340	WIBM	Jackson, Miss.	1450	WJEA	Valdosta, Ga.	1150
WFOR	Hattiesburg, Miss.	1400	WHAP	Hopewell, Va.	1340	WIBR	Baton Rouge, La.	1300	WJED	Dover, Ohio	1450
WFOX	Milwaukee, Wis.	860	WHAR	Clarksburg, W.Va.	1340	WIBS	Poynette, Wis.	1240	WJER	Erie, Pa.	1400
WFOY	St. Augustine, Fla.	1240	WHAS	Louisville, Ky.	840	WIBV	Belleville, Ill.	1260	WJGD	Columbia, Tenn.	1280
WFP	Fort Payne, Ala.	1400	WHAT	Philadelphia, Pa.	1340	WIBW	Topeka, Kans.	580	WJHB	Tallega, Ala.	1580
WFP	Atlantic City, N.J.	1450	WHAW	Haverhill, Mass.	1490	WIBX	Utica, N.Y.	850	WJHL	Johnson City, Tenn.	910
WFP	Fort Valley, Ga.	1450	WHAY	Weston, W.Va.	1450	WID	Richard, Ohio	960	WJOP	Opelika, Ala.	1400
WFR	Hammond, La.	1400	WHAY	New Britain, Conn.	910	WIDB	Bridgeport, Conn.	600	WJIG	Tulahoma, Tenn.	740
WFR	Reidsville, N.C.	1600	WHAZ	Troy, N.Y.	1330	WICE	Providence, R.I.	1290	WJIM	Lansing, Mich.	1240
WFR	Freeport, Ill.	1570	WHB	Kansas City, Mo.	710	WICF	Norwich, Conn.	930	WJIV	Savannah, Ga.	900
WFR	Coudersport, Pa.	600	WHBB	Selma, Ala.	1490	WICK	Seranton, Pa.	1400	WJJC	Commerce, Ga.	1270
WFR	Fremont, Ohio	900	WHBC	Canton, Ohio	1480	WICG	Salisbury, Md.	1320	WJJD	Chicago, Ill.	1600
WFR	Savannah, Ga.	1230	WHBF	Rock Island, Ill.	1270	WICU	Erie, Pa.	1330	WJLL	Niagara Falls, N.Y.	1440
WFRP	West Frankfort, Ill.	1300	WHBG	Harrisburg, Va.	1360	WICV	Malone, N.Y.	1490	WJLM	Lewisburg, Tenn.	1400
WFSC	Franklin, N.C.	1050	WHBI	Newark, N.J.	1280	WIDU	Elizabeth, Maine	1400	WJLD	Springfield, Ala.	1490
WFST	Caribou, Maine	600	WHBL	Sheboygan, Wis.	1330	WIDU	Fayetteville, N.C.	1600	WJLB	Detroit, Mich.	1400
WFT	Kinston, N.C.	960	WHBN	Harrodsburg, Ky.	1400	WIE	Elizabethtown, Ky.	1400	WJLD	Homewood, Ala.	1400
WFT	London, Ky.	1400	WHBD	Tampa, Fla.	1050	WIFM	Elkin, N.C.	1490	WJLK	Asbury Park, N.J.	1310
WFTL	Ft. Lauderdale, Fla.	1240	WHBT	Memphis, Tenn.	560	WIG	Medford, Wis.	1490	WJLS	Beeckley, W.Va.	560
WFTM	Mayfield, Ky.	1400	WHBT	Harriman, Tenn.	1230	WIK	Deatur, Ga.	870	WJMA	Orange, Va.	1340
WFT	Front Royal, Va.	1450	WHBU	Anderson, Ind.	1240	WIKB	Iron River, Mich.	1230	WJMB	Brockhaven, Miss.	1340
WFTW	Ft. Walton, Fla.	1260	WHBY	Appleton, Wis.	1230	WIKC	Bogalusa, La.	1490	WJMC	Rice Lake, Wis.	1240
WFUL	Fulton, Ky.	1270	WHCC	Waynesville, N.C.	1400	WIKD	Newport, Vt.	1490	WJMJ	Philadelphia, Pa.	1540
			WHCO	Sparta, Ill.	1230	WIKY	Evansville, Ind.	820	WJMO	Cleveland, Ohio	1540
			WHCU	Ithaca, N.Y.	870	WILA	St. Louis, Mo.	1430	WJMR		

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
WJMW	Athens, Ala.	730	WKTF	Warrenton, Va.	1420	WMBC	Macon, Miss.	1400	WNAE	Warren, Pa.	1310
WJMX	Florence, S.C.	970	WKTG	Thomasville, Ga.	730	WMBD	Peoria, Ill.	1470	WNAG	Granada, Miss.	1400
WJNC	Jacksonville, N.C.	1240	WKTM	Mayfield, Ky.	1050	WMBG	Richmond, Va.	1380	WNAH	Nashville, Tenn.	1380
WJNO	W. Palm Beach, Fla.	1230	WKTH	South Paris, Maine	1450	WMBH	Joplin, Mo.	1450	WNAW	Nearah, Wis.	1260
WJOB	Hammond, Ind.	1230	WKTS	Brookville, Fla.	1450	WMBI	Chicago, Ill.	1110	WNAS	Norristown, Pa.	1110
WJOC	Jamestown, N.Y.	1340	WKTX	Atlantic Beach, Fla.	1600	WMBL	Morehead City, N.C.	740	WNAT	Natchez, Miss.	1450
WJOE	Ward Ridge, Fla.	1570	WKTY	LaCrosse, Wis.	980	WMBM	Miami Beach, Fla.	1340	WNBH	New Bedford, Mass.	1340
WJOF	Florence, Ala.	1570	WKUL	Cullman, Ala.	520	WMBN	Patuxent, N.Y.	1340	WNBK	Annapolis, Md.	1430
WJOL	Joliet, Ill.	1340	WKVA	W. Va.	1340	WMBQ	Auburn, N.Y.	1340	WNBX	Yankton, S.Dak.	570
WJON	St. Cloud, Minn.	1240	WKVM	San Juan, P.R.	810	WMBR	Jacksonville, Fla.	1460	WNBG	Binghamton, N.Y.	1290
WJOT	Lake City, S.C.	1260	WKWF	Key West, Fla.	1600	WMBU	Uniontown, Pa.	590	WNBH	New Bedford, Mass.	1340
WJPD	Burlington, Vt.	1230	WKWG	Wheeling, W.Va.	1400	WMC	Memphis, Tenn.	790	WNBW	Newburyport, Mass.	1470
WJPA	Washington, Pa.	1450	WKXL	Concord, N.H.	1450	WMC	New York, N.Y.	570	WNBW	Murray, Ky.	1340
WJPF	Ishpeming, Mich.	1240	WKXY	Knoxville, Tenn.	900	WMC	Welch, W.Va.	1340	WNBW	Wellsboro, Pa.	1490
WJPH	Herrin, Ill.	1340	WKXX	Sarasota, Fla.	1540	WMC	Church Hill, Tenn.	1260	WNBW	Saratoga Lake, N.Y.	1240
WJPI	Green Bay, Wis.	1330	WKY	Oklahoma City, Okla.	930	WMC	McKeesport, Pa.	1360	WNBW	Siler City, N.C.	1570
WJPS	Greenville, Miss.	1330	WKYR	Keahoga, Ky.	1270	WMC	Harvard, Ill.	1600	WNBW	Barnesboro, Pa.	950
WJPS	Evansville, Ind.	1330	WKYR	W.Va.	970	WMD	Hazlehurst, Miss.	1220	WNBW	Daytona Beach, Fla.	1150
WJQS	Jackson, Miss.	1400	WKYV	Louisville, Ky.	900	WMD	Fajardo, P.R.	1490	WNBW	Syracuse, N.Y.	1260
WJR	Detroit, Mich.	760	WKZO	Kalamazoo, Mich.	590	WMDN	Midland, Mich.	1490	WNBW	South Bend, Ind.	1490
WJRD	Tuscaloosa, Ala.	1150	WLAC	Nashville, Tenn.	1510	WME	Eau Gallie, Fla.	920	WNBW	Worcester, Mass.	1230
WJRI	Lenoir, N.C.	1340	WLAD	Danbury, Conn.	800	WMEG	Tallahassee, Fla.	1330	WNBW	Toccoa, Ga.	1370
WJSB	Crestview, Fla.	1050	WLAF	LaFollette, Tenn.	1450	WMEI	Miami Beach, Fla.	1450	WNBW	Waco, Tex.	1250
WJSM	Jamestown, N.Y.	1240	WLAG	La Grande, Ga.	1240	WMEJ	Marion, Va.	1010	WNBW	Central City, Ky.	1600
WJUN	Union, Pa.	1220	WLAW	Lakeland, Fla.	1430	WMEK	Boston, Mass.	510	WNBW	New York, N.Y.	1130
WJVA	South Bend, Ind.	1580	WLAM	Lewiston, Maine	1470	WMEF	Monroeville, Ala.	1360	WNBW	Macon, Ga.	1400
WJW	Cleveland, Ohio	850	WLAN	Lancaster, Pa.	1390	WMEF	Wilmingon, N.C.	630	WNBW	Mayfield, Ky.	1320
WJWL	Georgetown, Del.	900	WLAP	Lexington, Ky.	630	WMEG	Hibbing, Minn.	1240	WNBW	New Haven, Conn.	1340
WJWS	South Hill, Va.	1370	WLAQ	Rome, Ga.	1410	WMEJ	Daytona Beach, Fla.	1450	WNBW	Cheektowaga, N.Y.	1230
WJXN	Jackson, Miss.	1450	WLAR	Athens, Tenn.	1450	WMEF	High Point, N.C.	1230	WNBW	Hills, Mich.	1240
WJZN	Clarksville, Tenn.	1400	WLAT	Conway, S.C.	1330	WMEF	Chattanooga, Tenn.	1440	WNBW	Warner, Va.	1430
WKAB	Molite, Ala.	840	WLAU	Laurel, Miss.	1340	WMEF	Terre Haute, Ind.	1300	WNBW	Neon, Ky.	1450
WKAC	Macomb, Ill.	1510	WLAU	Grand Rapids, Mich.	1340	WMEG	Moultrie, Ga.	1400	WNBW	Indianola, Miss.	1380
WKAL	Rome, N.Y.	1450	WLAW	Muscle Shoals, Ala.	1450	WMEG	Madison, Ga.	1250	WNBW	New London, Conn.	1490
WKAN	Goshen, Ind.	1460	WLBA	Gainesville, Ga.	1580	WMEG	New York, N.Y.	1050	WNBW	Norwalk, Conn.	1350
WKAN	Kankakee, Ill.	1320	WLBB	Carrollton, Ga.	1100	WMEG	Bainbridge, Ga.	930	WNBW	Evansville, Ill.	1590
WKAP	Allentown, Pa.	1320	WLBC	Muncie, Ind.	1340	WMEG	Meadville, Pa.	1490	WNBW	Newton, N.C.	1420
WKAQ	San Juan, P.R.	580	WLBG	Laurens, S.C.	860	WMEG	Montgomery, Ala.	800	WNBW	Newton, N.C.	1360
WKAR	East Lansing, Mich.	870	WLBI	Mattoon, Ill.	1170	WMEI	Monroe, La.	1440	WNBW	Warsaw, Va.	690
WKAT	Lami Beach, Fla.	1490	WLBJ	Bowling Green, Ky.	1130	WMEI	Atlantic City, N.J.	1340	WNBW	New Orleans, La.	1060
WKAY	Glasgow, Ky.	1490	WLAK	Lakeland, Fla.	1360	WMEI	Miami, Fla.	1140	WNBW	Naples, Fla.	1270
WKAZ	Charleston, W.Va.	950	WLAL	Auburndale, Wis.	930	WMEI	Middlesboro, Ky.	560	WNBW	Columbia, S.C.	1230
WKBC	N. Wilkesboro, N.C.	810	WLBN	Lebanon, Ky.	1590	WMEI	Milwaukee, Wis.	1290	WNBW	Newport, Ky.	740
WKBB	La Crosse, Wis.	1410	WLBR	Lebanon, Pa.	1270	WMEI	Mpls.-St. Paul, Minn.	1400	WNBW	Norfolk, Va.	1250
WKBI	St. Mary's, Pa.	1400	WLBS	Birmingham, Ala.	900	WMEI	Natchez, Miss.	1240	WNBW	High Point, N.C.	1590
WKBJ	Milan, Tenn.	1600	WLBT	Bangor, Maine	620	WMEI	Iron Mountain, Mich.	940	WNBW	New York, Pa.	1250
WKBN	Covington, Tenn.	1250	WLBU	Lancaster, S.C.	1350	WMEI	Jerome, N.J.	1490	WNBW	Knoxville, Tenn.	990
WKBY	Yonkers, N.Y.	840	WLBU	Cecil, S.C.	1450	WMEI	Monroe, La.	1450	WNBW	New Orleans, La.	1240
WKBO	Harrisburg, Pa.	1230	WLBU	Clinton, N.C.	910	WMEI	Cordele, Ga.	1230	WNBW	Tuscaloosa, Ala.	1280
WKBR	Manchester, N.H.	1240	WLBU	Clinton, N.C.	910	WMEI	Pineville, Ky.	1230	WNBW	New Rochelle, N.Y.	1480
WKBS	Richmond, Ind.	1490	WLBU	Atlantic City, N.J.	1490	WMEI	Milton, Pa.	1570	WNBW	Grundy, Va.	1250
WKBW	Buffalo, N.Y.	1520	WLBU	Jacksonville, Ill.	1180	WMEI	Dublin, Ga.	1330	WNBW	Waco, Tex.	1240
WKCB	Muskegon, Mich.	850	WLBU	Ladysmith, Wis.	1340	WMEI	Millville, N.J.	1440	WNBW	Narrowfork, Pa.	900
WKCB	Berlin, N.H.	1230	WLEA	Hornell, N.Y.	1480	WMEI	Millville, N.J.	1260	WNBW	Laurel, Miss.	920
WKCT	Bowling Green, Ky.	930	WLEC	Sandusky, Ohio	1450	WMEI	Milbourne, Fla.	1240	WNBW	Newark, N.J.	1270
WKDA	Nashville, Tenn.	1240	WLEC	Richmond, Va.	1480	WMEI	Marshall, N.C.	1460	WNBW	Norton, Va.	1350
WKDD	Newberry, S.C.	1240	WLEM	Emporium, Pa.	1250	WMEI	Fairmont, W.Va.	920	WNBW	Pensacola, Fla.	1230
WKDL	Clarksdale, Miss.	1600	WLED	Ponca, P.R.	1170	WMEI	Bath, Maine	730	WNBW	New York, N.Y.	830
WKDN	Camden, N.J.	800	WLET	Toccoa, Ga.	1420	WMEI	McMinville, Tenn.	1230	WNBW	Salamanca, N.Y.	1290
WKDX	Hamlet, N.C.	1400	WLEU	Eric, Pa.	1450	WMEI	Meriden, Conn.	1470	WNBW	Portsmouth, Ohio	1260
WKDE	Kewanee, Ill.	1450	WLEW	Bad Axe, Mich.	1340	WMEI	Meriden, Conn.	1470	WNBW	San Antonio, Tex.	1200
WKEN	Dover, Del.	1050	WLFA	LaFayette, Ga.	590	WMEI	Meriden, Conn.	1470	WNBW	Owosso, Mich.	1080
WKEM	Wm. Ga.	1450	WLFG	Little Falls, N.Y.	1190	WMEI	Meriden, Conn.	1470	WNBW	Oak Hill, W.Va.	860
WKEX	Covington, Va.	1340	WLHB	New York, N.Y.	1190	WMEI	Meriden, Conn.	1470	WNBW	Jacksonville, Fla.	1360
WKGN	Knoxville, Tenn.	1340	WLHK	Newport, Tenn.	1270	WMEI	Meriden, Conn.	1470	WNBW	Rhineclander, Wis.	1240
WKHM	Jackson, Mich.	970	WLIL	Lenoir, Tenn.	730	WMEI	Meriden, Conn.	1470	WNBW	Davenport, Iowa	1240
WKIC	Hazard, Ky.	1430	WLIP	Kenosha, Wis.	1050	WMEI	Meriden, Conn.	1470	WNBW	Portsmouth, Mass.	1240
WKID	Urbana, Ill.	1580	WLIS	Old Saybrook, Conn.	1420	WMEI	Meriden, Conn.	1470	WNBW	North Vernon, Ind.	1460
WKIK	Leonardtown, Md.	1370	WLIV	Livingston, Tenn.	920	WMEI	Meriden, Conn.	1470	WNBW	OHIO E. Liverpool, Ohio	1490
WKIN	Kingsport, Tenn.	1370	WLJH	Lowell, Mass.	1420	WMEI	Meriden, Conn.	1470	WNBW	OHIO Toledo, Ohio	1470
WKIP	Poughkeepsie, N.Y.	1450	WLJL	Lincoln, Pa.	1320	WMEI	Meriden, Conn.	1470	WNBW	OHIO Bellefontaine, Ohio	1390
WKIS	Orlando, Fla.	740	WLJM	Jackson, Ohio	1280	WMEI	Meriden, Conn.	1470	WNBW	OHIO Shelby, N.C.	730
WKIT	Mineola, N.Y.	1520	WLJN	Peekskill, N.Y.	1420	WMEI	Meriden, Conn.	1470	WNBW	OHIO Ames, Iowa	840
WKIX	Raleigh, N.C.	750	WLNA	Laconia, N.H.	1350	WMEI	Meriden, Conn.	1470	WNBW	OHIO Sine, Mich.	1290
WKJB	Mayaguez, P.R.	810	WLNB	Bradock, Pa.	1550	WMEI	Meriden, Conn.	1470	WNBW	OHIO Columbia, S.C.	1470
WKJG	Fort Wayne, Ind.	1360	WLBP	Portland, Maine	1310	WMEI	Meriden, Conn.	1470	WNBW	OHIO Oak Ridge, Tenn.	1290
WKKD	Conroe, Fla.	860	WLDE	Leaksville, N.C.	1490	WMEI	Meriden, Conn.	1470	WNBW	OHIO Meridian, Miss.	1450
WKLE	Ludington, Mich.	1480	WLDF	Franklin, Va.	950	WMEI	Meriden, Conn.	1470	WNBW	OHIO Jackson, Miss.	1590
WKLK	St. Albans, W.Va.	1300	WLDO	Logan, W.Va.	1230	WMEI	Meriden, Conn.	1470	WNBW	OHIO Albany, N.Y.	1460
WKLW	Washington, Ga.	1370	WLDP	Princeton, W.Va.	1490	WMEI	Meriden, Conn.	1470	WNBW	OHIO Milwaukee, Wis.	1470
WKLX	Clanton, Ala.	980	WLDP	LaPorte, Ind.	1540	WMEI	Meriden, Conn.	1470	WNBW	OHIO Atton, Ill.	1470
WKLK	Cloquet, Minn.	1230	WLDP	Memphis, Tenn.	1480	WMEI	Meriden, Conn.	1470	WNBW	OHIO Washington, D.C.	1450
WKLK	Wilmington, N.C.	790	WLDP	Minneapolis, Minn.	1350	WMEI	Meriden, Conn.	1470	WNBW	OHIO Syracuse, N.Y.	1490
WKLK	Louisville, Ky.	1080	WLDP	Lincolnton, N.C.	1030	WMEI	Meriden, Conn.	1470	WNBW	OHIO Florence, S.C.	1230
WKLK	Blackstone, Va.	1440	WLDP	Washburn, N.C.	1430	WMEI	Meriden, Conn.	1470	WNBW	OHIO Owensboro, Ky.	1490
WKLK	Paris, Ky.	1440	WLDP	Louisville, Ky.	1350	WMEI	Meriden, Conn.	1470	WNBW	OHIO Maniwac, Wis.	1240
WKLK	Hartwell, Ga.	980	WLDP	Portsmouth, Va.	1400	WMEI	Meriden, Conn.	1470	WNBW	OHIO Pleasantville, N.J.	1400
WKLZ	Kalamazoo, Mich.	1470	WLDP	Bloix, Miss.	1490	WMEI	Meriden, Conn.	1470	WNBW	OHIO Dayton, Ohio	980
WKMC	Roaring Spgs., Pa.	1370	WLPM	Suflon, Va.	1490	WMEI	Meriden, Conn.	1470	WNBW	OHIO Oneida, N.Y.	1600
WKMF	Flint, Mich.	1470	WLPO	LaSalle, Ill.	1220	WMEI	Meriden, Conn.	1470	WNBW	OHIO Lakeland, Fla.	1230
WKMH	Dearborn, Mich.	1310	WLPR	New Albany, Ind.	1570	WMEI	Meriden, Conn.	1470	WNBW	OHIO Defiance, Ohio	1280
WKMI	Kalamazoo, Mich.	1350	WLS	Chicago, Ill.	890	WMEI	Meriden, Conn.	1470	WNBW	OHIO Grand Rapids, Mich.	1300
WKMT	Kingsport, Tenn.	1220	WLS	Woodstock Gap, Va.	1220	WMEI	Meriden, Conn.	1470	WNBW	OHIO Dothan, Ala.	560
WKNB	New Britain, Conn.	840	WLS	Wallaes, N.C.	1400	WMEI	Meriden, Conn.	1470	WNBW	OHIO Washington, D.C.	1310
WKNE	Keene, N.H.	1290	WLS	Lansford, Pa.	1410	WMEI	Meriden, Conn.	1470	WNBW	OHIO Wood Washington, N.C.	1340
WKNX	Saginaw, Mich.	1210	WLS	Pikeville, Ky.	900	WMEI	Meriden, Conn.	1470	WNBW	OHIO WPA Oak Park, Ill.	1490
WKNY	Kingsport, N.Y.	1490	WLS	Louisville, Miss.	1270	WMEI	Meriden, Conn.	1470	WNBW	OHIO Bristol, Tenn.	1490
WKOA	Hopkinsville, Ky.	1480	WLS	Wellsville, N.Y.	1370	WMEI	Meriden, Conn.	1470	WNBW	OHIO Wor New York, N.Y.	710
WKOK	Sunbury, Pa.	1240	WLS	Gastonia, N.C.	1370	WMEI	Meriden, Conn.	1470	WNBW	OHIO WORA Mayaguez, P.R.	1150
WKOP	Binghamton, N.Y.	1360	WLS	Lynchburg, Va.	590	WMEI	Meriden, Conn.	1470	WNBW	OHIO WORC Worcester, Mass.	1310
WKOV	Weldon, Ohio	1330	WLS	Clinton, Ohio	700	WMEI	Meriden, Conn.	1470	WNBW	OHIO WORD Spartanburg, S.C.	910
WKOW	Madison, Wis.	1070	WLS	Williamsport, Pa.	1050	WMEI	Meriden, Conn.	1470	WNBW	OHIO WOSA Wausau, Wis.	550
WKDX	Framingham, Mass.	1190	WLS	Lynn, Mass.	1360	WMEI	Meriden, Conn.	1470	WNBW	OHIO WOSU Fulton, N.Y.	1300
WKDY	Bluefield, W.Va.	1240	WMA	Munising, Mich.	1400	WMEI	Meriden, Conn.	1470	WNBW	OHIO WOSH Oshkosh, Wis.	1490
WKDZ	Kosciusko, Miss.	1350	WMAF	Madison, Fla.	1230	WMEI	Meriden, Conn.	1470	WNBW	OHIO WOSU Columbus, Ohio	820
WKPA	New Kensington, Pa.	1150	WMAF	Forest, Miss.	860	WMEI	Meriden, Conn.	1470	WNBW	OHIO WOTR Corry, Pa.	1370
WKPT	Kingsport, Tenn.	1400	WMAJ	State College, Pa.	550	WMEI	Meriden, Conn.	1470	WNBW	OHIO WOTW Nashua, N.H.	900
WKRC	Cincinnati, Ohio	530	WMAK	Clinton, Pa.	1300	WMEI	Meriden, Conn.	1470	WNBW	OHIO WOUB Athens, Ohio	1340
WKRG	Mobile, Ala.	710	WMAK	Washington, D.C.	630	WMEI	Meriden, Conn.	1470	WNBW	OHIO WOV New York, N.Y.	1280
WKRM	Columbia, Tenn.	1340	WMAK	Marinette, Wis.	570	WMEI	Meriden, Conn.	1470	WNBW	OHIO WOW Omaha, Nebr.	590
WKRO	Cairo, Ill.	1340	WMAK	Manfield, Ohio	1400	WMEI	Meriden, Conn.	1470	WNBW	OHIO WNAE Warren, Pa.	1310
WKRS	Waukegan, Ill.	1220	WMAK	Monroe, N.C.	1060	WMEI	Meriden, Conn.	1470	WNBW	OHIO WNAG Granada, Miss.	1400
WKRT	Cortland, N.Y.	920	WMAK	Chicago,							

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
WOWL	Florence, Ala.	1240	WREL	Lexington, Va.	1450	WSPA	Spartanburg, S.C.	950	WTTT	Port Huron, Mich.	1380
WOWO	Ft. Wayne, Ind.	1190	WREN	Topeka, Kans.	1250	WSPB	Sarasota, Fla.	1450	WTTM	Madisonville, Ky.	1310
WOXF	Oxford, N.C.	1340	WREY	Reidsville, N.C.	1220	WSPD	Toledo, Ohio	1370	WTTN	Trenton, N.J.	920
WOZK	Ozark, Ark.	900	WRFC	Athens, Ga.	960	WSPN	Saratoga Sprgs., N.Y.	900	WTTT	Waterstown, Wis.	1580
WPAB	Ponce, P.R.	550	WRFD	Worthington, Ohio	880	WSPR	Springfield, Mass.	1270	WTR	Westminster, Md.	1470
WPAC	Pathego, N.Y.	1580	WRFS	Alexander City, Ala.	1050	WSPY	Stevens Pt., Wis.	1010	WTTU	Bloomington, Ind.	1370
WPAD	Paducah, Ky.	1450	WRGA	Rome, Ga.	1470	WSBC	Durham, N.C.	1410	WTUC	Union City, Tenn.	1580
WPAG	Ann Arbor, Mich.	1490	WRGR	Starkville, Miss.	1370	WSBS	Cleveland Hgts., Ohio	1490	WTUP	Tupelo, Miss.	1380
WPAL	Charleston, S.C.	730	WRGS	Rogersville, Tenn.	1470	WSBU	Durham, Ohio	1590	WTUS	Tuskegee, Ala.	580
WPAM	Pottsville, Pa.	1450	WRHC	Jacksonville, Fla.	1400	WSSB	Cleveland, Ohio	1490	WTUN	Wilmington, Del.	1290
WPAQ	Mount Airy, N.C.	740	WRHI	Rick Hill, S.C.	1340	WSSC	Sumter, S.C.	1340	WTVB	Coldwater, Mich.	1590
WPAR	Parkersburg, W.Va.	1450	WRIB	Providence, R.I.	1220	WSSO	Starkville, Miss.	1230	WTVL	Waterville, Maine	1490
WPAT	Paterson, N.J.	930	WRIC	Richlands, Va.	540	WSSV	Petersburg, Va.	1240	WTVN	Columbus, Ohio	610
WPAW	Pawtucket, R.I.	550	WRIO	Rio Piedras, P.R.	1410	WSTA	Charlotte Amalie, Virgin Islands	1340	WTWA	Thomson, Ga.	1240
WPAZ	Thomasville, Ga.	1240	WRIS	Roanoke, Va.	1410	WSTC	Stamford, Conn.	1400	WTWB	Auburndale, Fla.	1570
WPA4	Portsmouth, Ohio	1470	WRIT	Milwaukee, Wis.	1340	WSTK	Stoughton, Va.	1230	WTWN	St. Johnsbury, Vt.	1340
WPAZ	Pottstown, Pa.	1370	WRIV	Riverhead, N.Y.	1400	WSTL	Eminence, Mo.	1420	WTXW	Rk. Spgfd., Mass.	1490
WPBB	Jackson, Ala.	1290	WRJN	Racine, Wis.	1400	WSTN	St. Augustine, Fla.	1230	WTYM	East Longmeadow, Mass.	1600
WPBC	Minneapolis, Minn.	980	WRJW	Picayune, Miss.	1320	WSTP	Salisbury, N.C.	1490	WTYN	Tryon, N.C.	1580
WPCC	Panama City, Fla.	1400	WRKD	Rockland, Maine	1450	WSTU	Spartanburg, S.C.	1490	WTTY	Marianna, Fla.	1340
WPCO	Mt. Vernon, Ind.	1590	WRKH	Rockwood, Tenn.	580	WSTV	Sturgis, Mich.	1230	WULA	Eufaula, Ala.	1240
WPCT	Putnam, Conn.	1350	WRLD	Laniti, Ala.	1490	WSTW	Suart, Fla.	1450	WULJ	Lakeport, N.Y.	1340
WPCM	Potsdam, N.Y.	1470	WRMA	Montgomery, Ala.	950	WSTX	Steubenville, Ohio	1340	WUSL	Bethesda, Maine	1120
WPDJ	Jackson, W.Va.	600	WRMF	Fort Mill, Fla.	1050	WSUH	Oxford, Miss.	910	WUCL	Wiscasset, Me.	1400
WPDH	Portage, W.Va.	1350	WRMG	Greenville, S.C.	1490	WSUN	St. Petersburg, Fla.	620	WVCG	Coral Gables, Fla.	1070
WPDX	Clarksburg, W.Va.	750	WRMN	Elgin, Ill.	910	WSUX	Seaford, Del.	800	WVCH	Chester, Pa.	740
WPEG	Arlington, Fla.	1220	WRNB	New Bern, N.C.	1490	WSVA	Harrisonburg, Va.	550	WVEC	Hampton, Va.	1490
WPEL	Montrose, Pa.	1250	WRNL	Richmond, Va.	910	WSVZ	Palatka, Fla.	1200	WVET	Rochester, N.Y.	1280
WPEN	Philadelphia, Pa.	950	WROA	Gulport, Miss.	1390	WSVA	Harrisonburg, Va.	550	WVIM	Vicksburg, Miss.	1490
WPEO	Peoria, Ill.	1020	WROB	West Point, Miss.	1450	WSVS	Crewe, Va.	800	WVIC	Mt. Kisco, N.Y.	1310
WPEP	Peoria, Ill.	1020	WROD	Daytona Beach, Fla.	1340	WSVN	Belle Glade, Fla.	900	WVPC	Greensboro, N.C.	1440
WPEP	Taunton, Mass.	1570	WROK	Rockford, Ill.	1440	WSWJ	Wilmington, N.C.	1490	WVJS	Owensboro, Ky.	1420
WPEP	Greensboro, N.C.	950	WROL	Rockford, Ill.	1440	WSYL	Sylvania, Ga.	1490	WVLC	Columbus, Ohio	1580
WPFA	Panaca, Fla.	790	WRON	Roanoke, Va.	710	WSYR	Syracuse, N.Y.	570	WVLY	Lexington, Ky.	590
WPFB	Middletown, Ohio	910	WROV	Roanoke, Va.	1330	WTAB	Tabor City, N.C.	1370	WVNL	Oiney, Ill.	740
WPDF	Darlington, S.C.	1350	WROW	Albany, N.Y.	590	WTAC	Quincy, Mich.	600	WVNM	Mt. Carmel, Ill.	1360
WPFF	Park Falls, Wis.	1450	WRWX	Clarkdale, Miss.	1460	WTAD	Quincy, Mich.	600	WVNI	Biloxi, Miss.	1570
WPGC	Bradbury Hgts., Md.	1580	WRXK	Carmi, Ill.	1350	WTAG	Worcester, Mass.	580	WVNL	Barnstable, Mass.	1440
WPGW	Portland, Ind.	1440	WRXC	Rockford, Ill.	1330	WTAL	Tallahassee, Fla.	1270	WVNW	Newark, N.J.	620
WPGB	Phillipsburg, Pa.	1260	WRXD	Clarkdale, Miss.	1460	WTAN	Clearwater, Fla.	1340	WVOK	Birmingham, Ala.	690
WPGB	Phillipsburg, Pa.	1260	WRXE	Clarkdale, Miss.	1460	WTAP	Cambridge, Mass.	740	WVOL	Nashville, Tenn.	1470
WPID	Piedmont, Ala.	1280	WRXF	Clarkdale, Miss.	1460	WTAQ	LaGrange, Ill.	1300	WVOP	Vidalia, Ga.	970
WPIK	Alexandria, Va.	730	WRXG	Clarkdale, Miss.	1460	WTAR	Norfolk, Va.	790	WVOS	Liberty, N.Y.	1240
WPIN	St. Petersburg, Fla.	680	WRXH	Clarkdale, Miss.	1460	WTAW	College Sta., Tex.	1150	WVDT	Wilson, N.C.	1420
WPIT	Pittsburgh, Pa.	730	WRXI	Clarkdale, Miss.	1460	WTAX	Spring City, Ill.	1490	WVDR	Indian, W.Va.	1290
WPKE	Pikeville, Ky.	1240	WRXJ	Clarkdale, Miss.	1460	WTAY	Robinson, Ill.	1570	WVPO	Stromberg, Pa.	1440
WPKO	Waverly, Ohio	1380	WRXK	Clarkdale, Miss.	1460	WTBC	Tuscaloosa, Ala.	1230	WVSC	Somers Pt., Pa.	990
WPKY	Princeton, Ky.	1580	WRXL	Clarkdale, Miss.	1460	WTBF	Troy, Ala.	970	WVVW	Grafton, W.Va.	1260
WPA4	Plant City, Fla.	910	WRXM	Clarkdale, Miss.	1460	WTBO	Cumberland, Md.	1450	WVWB	Bay City, Mich.	1250
WPLH	Huntington, W.Va.	1470	WRXN	Clarkdale, Miss.	1460	WTCH	Flomaton, Wis.	990	WVBD	Bamberg, S.C.	790
WPLM	Plymouth, Mass.	1390	WRXP	Clarkdale, Miss.	1460	WTCL	Shawano, Wis.	960	WVBE	Vineland, N.J.	1360
WPLY	Plymouth, Wis.	1420	WRXQ	Clarkdale, Miss.	1460	WTCT	Tell City, Ind.	1270	WVCA	Gary, Ind.	1270
WPME	Punxsutawney, Pa.	1540	WRXR	Clarkdale, Miss.	1460	WTDM	Traverse City, Mich.	1400	WVCO	Waterbury, Conn.	1240
WPMP	Pasadenoula, Miss.	1580	WRXS	Clarkdale, Miss.	1460	WTEN	Minneapolis, Minn.	280	WVCD	Washington, D.C.	1260
WPMP	Plymouth, N.C.	1470	WRXT	Clarkdale, Miss.	1460	WTFC	Campbellsville, Ky.	1450	WVGP	Sanford, N.C.	1050
WPNF	Brward, N.C.	1420	WSA1	Cincinnati, Ohio	1360	WTCR	Ashland, Ky.	1420	WVGS	Tifton, Ga.	1430
WPNX	Phenix City, Ala.	1460	WSA2	Cincinnati, Ohio	1360	WTCS	Fairmont, W.Va.	1490	WVHG	Hornell, N.Y.	1320
WPON	Pontiac, Mich.	1460	WSA3	Cincinnati, Ohio	1360	WTCT	Whitesburg, Ky.	920	WVIL	Ft. Lauderdale, Fla.	1580
WPOP	Hartford, Conn.	1410	WSA4	Cincinnati, Ohio	1360	WTCL	Philadelphia, Pa.	860	WVIM	Bucara, Md.	1400
WPOR	Portland, Maine	1440	WSA5	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVIT	Canton, N.C.	1480
WPOW	Brooklyn, N.Y.	1330	WSA6	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVJ	Detroit, Mich.	950
WPPA	Pottsville, Pa.	1360	WSA7	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVKY	Winchester, Ky.	1380
WPPA	Pottsville, Pa.	1360	WSA8	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVWL	New Orleans, La.	870
WPPA	Pottsville, Pa.	1360	WSA9	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVNC	Asheville, N.C.	570
WPPA	Pottsville, Pa.	1360	WSA10	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVNR	Rochester, N.H.	930
WPPA	Pottsville, Pa.	1360	WSA11	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVNN	Beckley, W.Va.	620
WPPA	Pottsville, Pa.	1360	WSA12	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVNL	Wilmington, N.C.	1420
WPPA	Pottsville, Pa.	1360	WSA13	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVNY	Waterbury, Conn.	790
WPPA	Pottsville, Pa.	1360	WSA14	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVOD	Lynchburg, Va.	1390
WPPA	Pottsville, Pa.	1360	WSA15	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVOK	Charlotte, N.C.	1480
WPPA	Pottsville, Pa.	1360	WSA16	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVOL	Buffalo, N.Y.	1120
WPPA	Pottsville, Pa.	1360	WSA17	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVON	Woonssocket, R.I.	1240
WPPA	Pottsville, Pa.	1360	WSA18	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVPA	Williamsport, Pa.	1340
WPPA	Pottsville, Pa.	1360	WSA19	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVWF	Palatka, Fla.	1260
WPPA	Pottsville, Pa.	1360	WSA20	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVWR	W. Warck, N.Y.	1490
WPPA	Pottsville, Pa.	1360	WSA21	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVRL	Woodside, N.J.	1600
WPPA	Pottsville, Pa.	1360	WSA22	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVSC	Glens Falls, N.Y.	1450
WPPA	Pottsville, Pa.	1360	WSA23	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVSR	St. Albans, Vt.	1420
WPPA	Pottsville, Pa.	1360	WSA24	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVST	Waoster, Ohio	960
WPPA	Pottsville, Pa.	1360	WSA25	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVSW	Pittsburgh, Pa.	970
WPPA	Pottsville, Pa.	1360	WSA26	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVTT	Tampa, Fla.	1300
WPPA	Pottsville, Pa.	1360	WSA27	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVVA	Wheeling, W.Va.	1170
WPPA	Pottsville, Pa.	1360	WSA28	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVWB	Jasper, Ala.	1360
WPPA	Pottsville, Pa.	1360	WSA29	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVWF	Fayette, Ala.	990
WPPA	Pottsville, Pa.	1360	WSA30	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVWR	Russellville, Ala.	920
WPPA	Pottsville, Pa.	1360	WSA31	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVWW	Rio Piedras, P.R.	1520
WPPA	Pottsville, Pa.	1360	WSA32	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVXL	Manchester, Ky.	1580
WPPA	Pottsville, Pa.	1360	WSA33	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVYO	Pineville, W.Va.	970
WPPA	Pottsville, Pa.	1360	WSA34	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVXL	Demopolis, Ala.	1400
WPPA	Pottsville, Pa.	1360	WSA35	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVXI	Ridgmont, Va.	950
WPPA	Pottsville, Pa.	1360	WSA36	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVXL	Dublin, Ga.	1440
WPPA	Pottsville, Pa.	1360	WSA37	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVXL	Indianapolis, Ind.	950
WPPA	Pottsville, Pa.	1360	WSA38	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVXK	Baton Rouge, La.	1260
WPPA	Pottsville, Pa.	1360	WSA39	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVXR	Guayama, P.R.	1590
WPPA	Pottsville, Pa.	1360	WSA40	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVXX	Hattiesburg, Miss.	1510
WPPA	Pottsville, Pa.	1360	WSA41	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVY	Detroit, Mich.	1570
WPPA	Pottsville, Pa.	1360	WSA42	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVYL	York, Pa.	1580
WPPA	Pottsville, Pa.	1360	WSA43	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVDE	Birmingham, Ala.	850
WPPA	Pottsville, Pa.	1360	WSA44	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVLD	New Orleans, La.	610
WPPA	Pottsville, Pa.	1360	WSA45	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVMB	Manning, S.C.	1400
WPPA	Pottsville, Pa.	1360	WSA46	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVSE	Lakeland, Fla.	1350
WPPA	Pottsville, Pa.	1360	WSA47	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVSR	Franklin, Va.	1230
WPPA	Pottsville, Pa.	1360	WSA48	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVYI	Rocky Mount, Va.	1570
WPPA	Pottsville, Pa.	1360	WSA49	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVYO	Newport News, Va.	1270
WPPA	Pottsville, Pa.	1360	WSA50	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVYE	Wytheville, Va.	1280
WPPA	Pottsville, Pa.	1360	WSA51	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVZE	Atlanta, Ga.	1480
WPPA	Pottsville, Pa.	1360	WSA52	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVZP	Covington, Ky.	1050
WPPA	Pottsville, Pa.	1360	WSA53	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WVZY	Albemarle, N.Dak.	1580
WPPA	Pottsville, Pa.	1360	WSA54	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WZOB	Ft. Payne, Ala.	1250
WPPA	Pottsville, Pa.	1360	WSA55	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WZOK	Jacksonville, Fla.	1320
WPPA	Pottsville, Pa.	1360	WSA56	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WZRO	Jacksonville Beach, Fla.	1010
WPPA	Pottsville, Pa.	1360	WSA57	Cincinnati, Ohio	1360	WTCS	Spartanburg, S.C.	1400	WZXX	Cowan, Tenn.	1440

Canadian

Amplitude-Modulation (AM) Broadcasting Stations Listed Alphabetically by Call Letters
C.L., call letters; Kc., frequency in kilocycles (for watt power of station, see list arranged by frequency, below).

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
CBA	Sackville, N.B.	1070	CFRG	Gravelbourg, Sask.	710	CJFX	Antigonish, N.S.	580	CKLG	N. Vancouver, B.C.	730
CBAF	Moncton, N.B.	1300	CFRN	Edmonton, Alta.	1250	CJGK	Yorkton, Sask.	940	CKLN	Nelson, B.C.	1240
CBE	Windsor, N.B.	1550	CFRS	Simons, Ont.	1560	CJJB	Vernon, B.C.	940	CKLS	LaSarre, Que.	1240
CBF	Montreal, Que.	690	CFRY	Portage la Prairie, Man.	1570	CJJC	Sault Ste. Marie, Ont.	1050	CKLW	Windsor, Ont.	800
CBG	Gander, Nfld.	1450	CFSL	Weyburn, Sask.	1340	CJJK	Kirkland Lake, Ont.	560	CKLY	Lindsay, Ont.	910
CBH	Halifax, N.S.	1330	CFUN	Vancouver, B.C.	1410	CJLS	Yarmouth, N.S.	1340	CKMR	Newcastle, N.B.	790
CBJ	Sydney, N.S.	1140	CFVJ	Meese Jaw, Sask.	800	CJMS	Montreal, Que.	1280	CKMX	Gorse Crown, Nfld.	600
CBJ	Chicoutimi, Que.	1580	CHAD	Amos, Que.	1440	CJMT	Chicoutimi, Que.	1420	CKNB	Campbellton, N.B.	950
CBK	Regina, Sask.	540	CHAE	Medicine Hat, Alta.	1270	CJNB	N. Battleford, Sask.	1460	CKNW	New Westminster, B.C.	1320
CBL	Toronto, Ont.	740	CHAT	Edmonton, Alta.	1080	CJNR	Blind River, Ont.	730			
CBM	Montreal, Que.	940	CHED	Edmonton, Alta.	1400	CJOB	Winnipeg, Man.	680	CKNX	Wingham, Ont.	920
CBN	St. John's, Nfld.	640	CHEF	Granby, Que.	1450	CJOC	Lethbridge, Alta.	1220	CKOC	Hamilton, Ont.	1150
CBO	Ottawa, Ont.	910	CHEX	Peterborough, Ont.	980	CJON	St. John's, Nfld.	930	CKOK	Penticton, B.C.	1340
CBT	Grand Falls, Nfld.	990	CHFA	Edmonton, Alta.	680	CJOR	Vancouver, B.C.	600	CKOT	Saskatoon, Sask.	1420
CBU	Vancouver, B.C.	690	CHGB	St. Anne de la Pocatiere, Que.	1350	CJOY	Guelph, Ont.	1450	CKOT	Tillsonburg, Ont.	1510
CBV	Quebec, Que.	980	CHLN	Three Rivers, Que.	550	CJQC	Quebec, Que.	1340	CKOY	Kelowna, B.C.	630
CBW	Winnipeg, Man.	990	CHLO	St. Thomas, Ont.	680	CJRH	Richmond Hill, Ont.	1300	CKOX	Woodstock, Ont.	1340
CBX	Edmonton, Alta.	1010	CHLT	Montreal, Que.	1410	CJRL	Kenora, Ont.	1220	CKOY	Ottawa, Ont.	1310
CBXA	Edmonton, Alta.	740	CHLNT	Sherbrooke, Que.	900	CJRW	Summerside, P.E.I.	1240	CKPC	Brantford, Ont.	1380
CBY	Corner Brook, Nfld.	790	CHML	Hamilton, Ont.	900	CJSO	Sorel, Que.	1320	CKPR	Prince George, B.C.	550
CFAB	Windsor, N.S.	1450	CHNC	New Carlisle, Que.	610	CJSP	Leamington, Ont.	710	CKPR	Fort William, Ont.	580
CFAC	Calgary, Alta.	960	CHND	Sudbury, Ont.	900	CJVI	Victoria, B.C.	900	CKRB	Ville St. Georges, Que.	1400
CFAM	Altona, Man.	1050	CHNS	Halifax, N.S.	960	CKAC	Montreal, Que.	730	CKRC	Winnipeg, Man.	630
CFAR	Flin Flon, Man.	590	CHOC	Toronto, Ont.	1070	CKBB	Barrie, Ont.	1230	CKRD	Red Deer, Alta.	850
CFBC	Saint John, N.B.	930	CHOV	Pembroke, Ont.	800	CKBC	Kathurst, N.B.	1160	CKRM	Regina, Sask.	950
CFB	Montreal, Que.	600	CHRC	Quebec, Que.	800	CKBI	Prince Albert, Sask.	900	CKRN	Rouyn, Que.	1490
CFCH	North Bay, Ont.	600	CHRD	Drummondville, Que.	1340	CKBL	Matane, Que.	1250	CKRS	Jonquiere, Que.	590
CFCL	Timmins, Ont.	580	CHRS	Roberval, Que.	910	CKBM	Montmagny, Que.	1490	CKSA	Lloydminster, Alta.	1150
CFCN	Calgary, Alta.	1060	CHSJ	Saint John, N.B.	1150	CKBW	Bridgewater, N.S.	1000	CKSB	St. Boniface, Man.	1250
CFCO	Chatham, Ont.	630	CHUB	Nanaimo, B.C.	1570	CKCH	Hull, Que.	970	CKSF	Corwall, Ont.	1220
FCFW	Camrose, Alta.	1230	CHUC	Port Hope, Ont.	1500	CKCK	Regina, Sask.	820	CKSL	London, Ont.	1290
CFCY	Charlottetown, P.E.I.	630	CHUM	Toronto, Ont.	1300	CKCL	Truro, N.S.	860	CKSM	Shawinigan Falls, Quebec	1220
CFDA	Victoria, B.C.	1380	CHVC	Niagara Falls, Ont.	1600	CKCO	Regina, Sask.	570	CKSU	Sudbury, Ont.	790
CFDG	Grande Prairie, Alta.	1050	CHWK	Kitchikawik, B.C.	1270	CKCW	Moncton, N.B.	1220	CKSW	Swift Current, Sask.	1400
CFDR	Gravelbourg, Sask.	1230	CHWO	Oakville, Ont.	1250	CKCX	Sault Ste. Marie, Ont.	1400	CKTB	St. Catharines, Ont.	610
CFGT	St. Joseph d'Alma, Que.	1270	CJAD	Montreal, Que.	800	CKDA	Victoria, B.C.	1220	CKTR	Three Rivers, Que.	1350
CFBJ	Brampton, Ont.	1090	CJAT	Trail, B.C.	1160	CKDH	Amherst, N.S.	1400	CKTS	Sherbrooke, Que.	1240
CFJC	Kamloops, B.C.	910	CJAY	Port Alberni, B.C.	1240	CKDM	Dauphin, Man.	1050	CKUA	Edmonton, Alta.	580
CFJR	Brockville, Ont.	1450	CJBQ	Belleville, Ont.	800	CKDN	New Glasgow, N.S.	850	CKVD	Val d'Or, Que.	1230
CFNB	Fredericton, N.B.	550	CJBR	Rimouski, Que.	900	CKEK	Cranbrook, B.C.	570	CKVM	Ville Marie, Que.	710
CFNS	Saskatoon, Sask.	1170	CJCA	Edmonton, Alta.	930	CKEN	Kentville, N.S.	1350	CKWG	Kingston, Ont.	980
CFOB	Fort Frances, Ont.	800	CJCB	Sydney, N.S.	1270	CKEY	Toronto, Ont.	580	CKWX	Vancouver, B.C.	1130
CFOR	Orrilla, Ont.	1570	CJCH	Halifax, N.S.	920	CKFH	Toronto, Ont.	1400	CKX	Brandon, Man.	1150
CFOS	Owen Sound, Ont.	1470	CJCS	Stratford, Ont.	1240	CKGB	Timmins, Ont.	680	CKXL	Calgary, Alta.	1140
CFPA	Port Arthur, Ont.	1230	CJCT	Dawson Creek, B.C.	1350	CKGR	Gait, Ont.	110	CKY	Winnipeg, Man.	580
CFPL	London, Ont.	980	CJED	Edmundston, N.B.	570	CKJL	St. Jerome, Que.	900	CKYL	Peace River, Alta.	630
CFPR	Prince Rupert, B.C.	1240	CJEM	Edmundston, N.B.	570	CKLC	Kingston, Ont.	1350	VOCM	St. John's, Nfld.	1230
CFQC	Saskatoon, Sask.	600	CJFP	Riviere du Loup, Que.	1400	CKLD	Thetford Mines, Que.	1230	VOWR	St. John's, Nfld.	800
CFRA	Ottawa, Ont.	1010									
CFRB	Toronto, Ont.	1010									
CFRC	Kingston, Ont.	1490									

United States and Canadian

Amplitude-Modulation (AM) Broadcasting Stations Grouped by Frequency; U.S. stations listed alphabetically by location within groups, Canadian stations precede U.S.

Abbreviations: Kc., frequency in kilocycles; W.P., watt power—Wave length is given in meters (all AM stations broadcasting at a higher frequency than 1600 Kc. are listed under Short-Wave Stations, see p. 185 and 187)

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
540—555.5			560—535.4			580—516.9			600—499.7		
CBK	Wesiga, Sask.	5000	CFRA	Ottawa, Ont.	5000	WNAX	Yankton, S.Dak.	5000	KFXM	San Bernardino, Cal.	1000
CBP	Redding, Calif.	1000	CJKL	Kirkland Lake, Ont.	5000	WFAA	Dallas, Tex.	5000	KCFJ	Pueblo, Colo.	1000
KFMB	San Diego, Calif.	5000	WOOF	Dothan, Ala.	5000	WFAP	Ft. Worth, Tex.	5000	WDFP	Panama City, Fla.	1000
WGTO	Cypress Gardens, Florida	10000	KYUM	Yuma, Ariz.	1000	WJLB	Jackson, City, Utah	5000	KGMB	Honolulu, Hawaii	5000
KBRV	Soda Springs, Idaho	500	KSFO	San Fran., Calif.	5000	WMAM	Marinette, Wis.	250	KID	Idaho Falls, Idaho	5000
KWMT	Ft. Dodge, Iowa	500	KLZD	Denver, Colo.	5000				WLK	Lexington, Ky.	1000
WFO	Peemoke City, Mo.	1000	WQAM	Miami, Fla.	5000	580—516.9			WEI	Boston, Mass.	5000
WCNG	Canonsburg, Pa.	250	WIND	Chicago, Ill.	5000	CFCL	Timmins, Ont.	1000	WKZ	Kalamazoo, Mich.	5000
WDKN	Clarksville, Tenn.	250	WMIK	Midland, Mo., Ky.	5000	CFGL	Timmins, Ont.	1000	WOB	Dmah, Nebr.	5000
WRIC	Richlands, Va.	1000	WGAN	Portland, Maine	5000	CFGL	Timmins, Ont.	1000	WOW	Albany, N.Y.	5000
			WHYN	Springfield, Mass.	5000	CKEY	Toronto, Ont.	5000	WGTM	Wilson, N.C.	5000
550—545.1			WMIC	Monroe, Mich.	500	CKPR	Ft. William, Ont.	5000	WGTN	Eugene, Oreg.	5000
CFNB	Fredericton, N.B.	5000	WBCB	Duluth, Minn.	5000	CKUA	Edmonton, Alta.	1000	WARM	Scranton, Pa.	5000
CHLN	Three Rivers, Que.	550	KWTO	Springfield, Mo.	5000	CKY	Winnipeg, Man.	5000	WBSB	Uniontown, Pa.	1000
WCN	Anchorage, Alaska	250	KMON	Great Falls, Mont.	5000	WTUS	Tuskegee, Ala.	500	KTBC	Austin, Tex.	5000
KENI	Phoenix, Ariz.	5000	KJED	Dawson City, N.C.	5000	KABI	Ketchikan, Alaska	5000	KSUB	Cedar City, Utah	1000
KOY	Phoenix, Ariz.	5000	WFLB	Philadelphia, Pa.	5000	KDA	Lawson, N.D.	5000	VQAR	St. John's, Nfld.	1000
KAFY	Bakersfield, Calif.	1000	WIS	Columbia, S.C.	5000	KMI	Fresno, Calif.	5000	KHQ	Spokane, Wash.	5000
KRAI	Craig, Colo.	5000	WHBQ	Memphis, Tenn.	5000	KUBC	Montrose, Colo.	5000			
WGGA	Gainesville, Ga.	5000	WFBM	Beaumont, Tex.	5000	WDBO	Orlando, Fla.	5000			
KFRM	Concordia, Kansas	5000	KPQ	Wenatchee, Wash.	5000	WAGS	Augusta, Ga.	5000			
WHYN	Springfield, Miss.	1000	WJLS	Beekley, W.Va.	5000	KFXD	Nampa, Idaho	5000			
WCBJ	Columbus, Miss.	1000				WILL	Urbana, Ill.	5000			
KSD	St. Louis, Mo.	5000	570—526.0			KSA	Manhattan, Kans.	5000			
KOPR	Butte, Mont.	1000	CKEK	Cranbrook, B.C.	1000	WIBW	Topeka, Kans.	5000			
WGR	Buffalo, N.Y.	5000	CKCQ	Queens, B.C.	1000	KALB	Alexandria, La.	5000			
WDBM	Statesville, N.C.	500	CJEM	Edmundston, N.B.	1000	WTAG	Worcester, Mass.	5000			
KFYR	Bismarck, N.Dak.	5000	WCAS	Gadsden, Ala.	1000	WELO	Tupelo, Miss.	5000			
KWRO	Cincinnati, Ohio	5000	KCNO	Alturas, Calif.	1000	WHP	Harrisburg, Pa.	5000			
KOAC	Corvallis, Oreg.	5000	KJAC	Los Angeles, Calif.	5000	WRKH	Richwood, Tenn.	5000			
WHLM	Bloomsburg, Pa.	500	WGMS	Washington, D.C.	5000	WVLS	Lubbock, Tex.	5000			
WPAB	Ponce, P.R.	5000	WACL	Waycross, Ga.	5000	WCHS	Charleston, W.Va.	5000			
WPAW	Pawtucket, R.I.	1000	WKBY	Paducah, Ky.	1000	WKTY	LaCrosse, Wis.	1000			
KMWI	Wailuku, T.H.	1000	WYMI	Biloxi, Miss.	1000						
KGRS	Midland, Tex.	5000	KGRT	Las Cruces, N.Mex.	1000						
KTSA	San Antonio, Tex.	5000	WMCN	New York, N.Y.	5000						
WDEV	Waterbury, Vt.	1000	WSYR	Syracuse, N.Y.	5000	CFAR	Flin Flon, Man.	1000			
WSVA	Harrisburg, Va.	3000	WVNC	Asheville, N.C.	5000	CKRS	Jonquiere, Que.	1000			
WOSA	Wausau, Wis.	5000	WMSN	Raleigh, N.C.	5000	CJON	St. John's, Nfld.	1000			
			WKBN	Youngstown, Ohio	5000	WRAG	Carrollton, Ala.	1000			
						KBHS	Hot Springs, Ark.	8000			

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
(1050-285.5)			KWKH Shreveport, La.	5000	5000	WKNX Saginaw, Mich.	1000	WHIR Danville, Ky.	250		
WBIE Marietta, Ga.	500		WDCR Detroit, Mich.	5000	5000	WADE Wadesboro, N.C.	1000	WHOP Hopkinsville, Ky.	250		
KZIN Coeur d'Alene, Idaho	250		WDGY Minneapolis, Minn.	5000	5000	WAVI Dayton, Ohio	250	WMLF Pineville, Ky.	250		
WDZ Decatur, Ill.	1000		WNEW New York, N.Y.	5000	5000	WCAU Philadelphia, Pa.	5000	KLIC Monroe, La.	250		
KNCO Garden City, Kans.	1000							WJBW New Orleans, La.	250		
WZIP Covington, Ky.	250		1140-263.0			1220-245.8		KSLD Delousas, La.	250		
WKTM Mayfield, Ky.	1000		CKXL Calgary, Alta.	1000	1000	CJOC Lethbridge, Alta.	1000	WGUJ Bangor, Maine	250		
KLPL Lake Providence, La.	250		KRAK Stockton, Calif.	5000	5000	CIDA Victoria, B.C.	1000	WBYT Baltimore, Md.	250		
KOKA Shreveport, La.	250		WMIE Miami, Fla.	1000	1000	CJRL Kenora, Ont.	1000	WCUM Cumberland, Md.	250		
WGAY Silver Sprng., Md.	1000		KGEN Boise, Idaho	1000	1000	CCEK New Glasgow, N.S.	250	WMNB No. Adams, Mass.	250		
WFG Ann Arbor, Mich.	1000		KPSV Peoria, Ill.	1000	1000	KCGW Bloncton, N.B.	1000	WESX Salem, Mass.	250		
KLOH Winston, Minn.	1000		KLPR Oklahoma City, Okla.	500	500	CKF Cornwall, Ont.	1000	WNEB Worcester, Mass.	250		
WACR Columbus, Miss.	1000		WITA San Juan, P.R.	500	500	CKSM Shawinigan Falls,		WJEB Grand Rapids, Mich.	250		
KSIS Sedalia, Mo.	1000		KSOD Sioux Falls, S.Dak.	1000	1000			WIKB Iron River, Mich.	250		
KRBO Las Vegas, Nev.	500		KORC Mineral Wells, Tex.	250	250			WLAGr Lapeer, Mich.	250		
WBNC Conway, N.H.	1000		WRVA Richmond, Va.	5000	5000			WSOO St. Ste. Marie, Mich.	250		
WNGM New York, N.Y.	5000							WSTR Surgis, Mich.	250		
WFSC Franklin, N.C.	500		1150-260.7					WKLK Cloquet, Minn.	250		
WLDN Lincoln, N.C.	1000		CKSA Lloydminster, Alta.	1000	1000	KFSC Denver, Colo.	1000	KYSM Mankato, Minn.	250		
WWGP Sanford, N.C.	1000		CHSJ Saint John, N.B.	5000	5000	WRWB Sarnia, Ont.	250	KTRF Thief Riv. Fil., Minn.	250		
KCCO Lawton, Okla.	250		CKOC Hamilton, Ont.	5000	5000	WRWB Sarnia, Ont.	250	KWNO Winona, Minn.	250		
KFMJ Tulsa, Okla.	1000		CKX Brandon, Man.	5000	5000	WREC Miami, Fla.	250	KWA Grant, Miss.	250		
KUBE Pendleton, Oreg.	1000		WBCA Bay Minette, Ala.	1000	1000	WCLB Camilla, Ga.	1000	WHSY Hattiesburg, Miss.	250		
KEED Springfield, Oreg.	1000		WGEA Geneva, Ala.	1000	1000	WSFT Thomaston, Ga.	5000	WSSO Starkville, Miss.	250		
WBUT Butler, Pa.	250		WGFA Tallahassee, Fla.	1000	1000	KWEI Weiser, Idaho	1000	WAZF Yazoo City, Miss.	250		
WJL Williamsport, Pa.	1000		KCLR Little Rock, Ark.	5000	5000	WLPO LaSalle, Ill.	1000	KODE Joplin, Mo.	250		
WSMT Sparta, Tenn.	250		KFSG Los Angeles, Calif.	2500	2500	KCRS Waukegan, Ill.	1000	KLWT Lebanon, Mo.	250		
KLEN Killeen, Tex.	1000		KRKD Los Angeles, Calif.	5000	5000	WSLN Salem, Ind.	1000	KNCM Moberly, Mo.	250		
WBRG Lynchburg, Va.	1000		KGMC Englewood, Colo.	1000	1000	KOFD Ottawa, Kans.	250	KANA Anacanda, Mont.	250		
WCMS Norfolk, Va.	1000		WCNX Middletown, Conn.	500	500	WFKN Franklin, Ky.	1000	KBML Bozeman, Mont.	250		
KNBX Kirkland, Wash.	1000		WDBD Dayton, Del.	5000	5000	KBCI Bossier City, La.	250	KXLO Lewiston, Mont.	250		
WCEF Parkersburg, W.Va.	1000		WTPM Tampa, Fla.	1000	1000	WSME Sanford, Maine	1000	KLCB Libby, Mont.	250		
WECL Eau Claire, Wis.	1000		WJEM Valdosta, Ga.	1000	1000	WAHL Hastings, Mich.	1000	KTNC Falls City, Nebr.	100		
WLIF Kenosha, Wis.	250		KANI Oahu, Hawaii	1000	1000	WADC Hazelhurst, Miss.	1000	KHAS Hastings, Nebr.	250		
KWIV Douglas, Wis.	250		WGHG Marlon, Ill.	5000	5000	KBHM Branson, Mo.	250	KELY Ely, Nev.	250		
			WDM Des Moines, Iowa	1000	1000	KGMO Cape Girardeau, Mo.	5000	KDOT Carson, Nev.	250		
1060-282.8			KSAI Salt Lake City, Utah	5000	5000	KLPW Union, Mo.	250	WKCB Berlin, N.H.	250		
CFNC Calgary, Alta.	1000		WMST Mt. Sterling, Ky.	500	500	WGNV Newburgh, N.Y.	1000	WTSV Claremont, N.H.	250		
KPAY Chico, Calif.	1000		WLOC Mumfordsville, Ky.	1000	1000	WKMT Kings Mtn., N.C.	1000	WCWC Wildwood, N.J.	100		
WNOE New Orleans, La.	5000		WBO Baton Rouge, La.	5000	5000	WENC Whitesville, N.C.	250	KALG Alamogordo, N.Mex.	250		
WHFB Benton Harbor, Mich.	1000		WGHM Skowhegan, Maine	1000	1000	WGAR Cleveland, Ohio	5000	KOTS Deling, N.Mex.	250		
WMAP Monroe, N.C.	250		WGOP Boston, Mass.	5000	5000	WJUN Mexico, Pa.	250	KFUN Las Vegas, N.Mex.	250		
WCMW Canton, Ohio	1000		WCEN Mt. Pleasant, Mich.	1000	1000	WRIB Providence, R.I.	1000	KSWB Wichita, Kan.	250		
WRCV Philadelphia, Pa.	5000		KRMS Osage Beach, Mo.	1000	1000	WALD Waterboro, S.Dak.	1000	WENIA Cheektowick, N.Y.	250		
			KIYI Shelby, Mont.	1000	1000	KABE Aberdeen, S.Dak.	250	WENY Elmira, N.Y.	250		
1070-280.2			KDEF Albuquerque, N.Mex.	1000	1000	WQWL Camden, Minn.	250	WHUC Hudson, N.Y.	250		
CBA Sackville, N.B.	5000		WRUN Utica, N.Y.	5000	5000	WCPC Etowah, Tenn.	1000	WLFF Little Falls, N.Y.	250		
WQDK Sanita, Ont.	5000		WBRU Burlington, N.C.	1000	1000	KTET Livingston, Tex.	250	WFAS White Plains, N.Y.	250		
WAPI Birmingham, Ala.	1000		WGBR Goldsboro, N.C.	5000	5000	KZEE Weatherford, Tex.	250	WSKY Asheville, N.C.	250		
KNX Los Angeles, Calif.	5000		WCU Akron, Ohio	1000	1000	WLSB Big Stone Gap, Va.	1000	WFAL Fayetteville, N.C.	250		
WVCG Coral Gables, Fla.	1000		WIMA Lima, Ohio	1000	1000	WFXA Falls Church, Va.	1000	WFRF High Point, N.C.	250		
WIBC Indianapolis, Ind.	5000		KNED McAlester, Okla.	1000	1000	KBAM Longview, Wash.	1000	WISP Kingston, N.C.	250		
KFBI Wichita, Kans.	1000		KFJI Klamath Falls, Oreg.	5000	5000			WNNC Newton, N.C.	250		
KHMO Hannibal, Mo.	5000		WHUN Huntington, Pa.	1000	1000			WCBT Roanoke Rap., N.C.	250		
WHPE High Point, N.C.	1000		WKPA New Kensington, Pa.	250	250			KDIX Dickinson, N.Dak.	250		
WLDL Laurinburg, N.C.	1000		WORA Mayaguez, P.R.	1000	1000			WCPO Cincinnati, Ohio	250		
WDIA Memphis, Tenn.	5000		WRNO Orangeburg, S.C.	1000	1000			WCOL Columbus, Ohio	250		
KOPY Alice, Tex.	1000		WTYC Rock Hill, S.C.	1000	1000			WIRL Fronton, Ohio	250		
WKOW Madison, Wis.	1000		WSNW Seneca Township, South Carolina	1000	1000			WTOL Toledo, Ohio	250		
			WAPD Chattanooga, Tenn.	5000	5000			KADA N. of Ada, Okla.	250		
1080-277.6			WCRK Morristown, Tenn.	1000	1000			WBBZ Ponca City, Okla.	250		
CHED Edmonton, Alta.	1000		WTAW College Station, Tex.	1000	1000			KVAS Astoria, Oreg.	250		
KSCO Santa Cruz, Calif.	1000		KJBC Midland, Tex.	500	500			KRNS Burns, Oreg.	250		
WTIC Hartford, Conn.	5000		KOLJ Quanah, Tex.	500	500			KCOS Coos Bay, Oreg.	250		
WKLO Louisville, Ky.	5000		KOFE Pullman, Wash.	1000	1000			KGRH Graham, Oreg.	100		
WVAP Owosso, Mich.	250		KAYO Seattle, Wash.	5000	5000			KYJC Medford, Oreg.	250		
WINE Kenosha, Wis.	1000		KKEY Vancouver, Wash.	1000	1000			KQIK Lakeview, Oreg.	250		
KWJJ Portland, Oreg.	1000		WELC Welch, W.Va.	1000	1000			WBVP Beaver Falls, Pa.	250		
WEPP Pittsburgh, Pa.	1000		WCHF Chipewaga Falls, Wis.	5000	5000			WEXX Easton, Pa.	250		
KRLD Dallas, Tex.	5000		WISN Milwaukee, Wis.	5000	5000			WKBO Harrisburg, Pa.	250		
								WCRO Johnstown, Pa.	250		
1090-275.1			1160-258.5			1230-243.8		WBZ Locust Haven, Pa.	250		
CFJB Brampton, Ont.	250		WJGD Chicago, Ill.	5000	5000	CFW Camrose, Alta.	250	WEIR Westport, R.I.	250		
CHRS St. Jean, Que.	1000		KSL Salt Lake City, Utah	5000	5000	CFGR Gravelbourg, Sask.	250	WAIM Anderson, S.C.	250		
KTHS Little Rock, Ark.	5000					CFYT Dawson City, Yukon T.	250	WNOK Columbia, S.C.	250		
WCRA Effingham, Ill.	250		1170-256.3			KBBE Belleville, Ont.	250	WOLS Florence, S.C.	250		
WVAF Waterloo, Iowa	1000		CFNS Saskatoon, Sask.	1000	1000	CFPA Port Arthur, Ont.	250	KISD Sioux Falls, S.Dak.	250		
WBAL Baltimore, Md.	5000		WCBO Montgomery, Ala.	1000	1000	CKEC New Glasgow, N.S.	250	WHBT Harriman, Tenn.	250		
WILD Boston, Mass.	1000		KCBQ San Diego, Calif.	5000	5000	CKLD Thetford Mines, Que.	250	WMMT McMinnville, Tenn.	250		
WMUS Muskegon, Mich.	5000		KLCK San Jose, Calif.	5000	5000	VOAR St. John's, Nfld.	100	KSKX Carson, Calif.	250		
KING Seattle, Wash.	5000		WLBH Mattson, Ill.	250	250	CKVD Val D'Or, Que.	250	DLK Del Rio, Tex.	250		
			KSTT Davenport, Iowa	1000	1000	WRB Auburn, Ala.	250	KNUZ Houston, Tex.	250		
1100-272.6			KVOD Tulsa, Okla.	5000	5000	WJBW Haleyville, Ala.	250	KERV Kerrville, Tex.	250		
CFTJ Galt, Ont.	250		WLEO Ponca, P.R.	2500	2500	WBHP Huntsville, Ala.	250	KLVT Leaveland, Tex.	250		
KXLA Pasadena, Calif.	1000		KPUG Bellingham, Wash.	5000	5000	WHTB Talledega, Ala.	250	KQSF Nacogdoches, Tex.	250		
WLT Tampa, Fla.	1000		WVVA Wheeling, W.Va.	5000	5000	WTBC Tuscaloosa, Ala.	250	KOSA Odessa, Tex.	250		
WMBI Chicago, Ill.	5000					KIFW Sitka, Alaska	250	KHHH Houston, Tex.	250		
KFAB Omaha, Nebr.	5000		1180-254.1			KSUN Bisbee, Ariz.	250	KSEY Seymour, Tex.	250		
WBT Charlotte, N.C.	5000		WLDJ Jacksonville, Ill.	1000	1000	KAWA Kingman, Ariz.	250	KCMC Texarkana, Tex.	250		
KEND Bend, Oreg.	5000		WHAM Rochester, N.Y.	5000	5000	KCON Conway, Ark.	250	KSUP Sulphur Sprng., Tex.	250		
WVAR Morristown, Pa.	500					KFPW Ft. Smith, Ark.	250	KWTX Waxo, Tex.	250		
WJP Casper, Wyo.	500		1190-252.0			KBTM Jonesboro, Ark.	250	KMUR Murray, Utah	250		
WHIM Providence, R.I.	1000		KGYY Vallejo, Calif.	250	250	KGEE Bakersfield, Calif.	250	KDAL Price, Utah	250		
KIPA Hilo, T.Hawaii	1000		WOWO Ft. Wayne, Ind.	5000	5000	KWTC Barstow, Calif.	250	WJBY Appleton, Wis.	250		
			WANN Annapolis, Md.	1000	1000	KBS Bishop, Calif.	250	WCLO Jansville, Wis.	250		
1120-267.7			WKOK Framingham, Mass.	1000	1000	KBS El Centro, Calif.	250	WHF Wausau, Wis.	250		
WUST Bethesda, Md.	250		WLIB New York, N.Y.	1000	1000	KDAC Ft. Bragg, Calif.	250	KVOC Casper, Wyo.	250		
KNOX St. Louis, Mo.	5000		KEX Portland, Oreg.	5000	5000	KGFJ Los Angeles, Calif.	250				
WWOL Buffalo, N.Y.	1000		WDTV St. John, V.I.	1000	1000	KPRL Paso Robles, Calif.	250				
KCLE Cleburne, Tex.	250		KLIF Dallas, Tex.	5000	5000	KRG Redding, Calif.	250				
						KWG Stockton, Calif.	250				
1130-265.3			1200-249.9			KXGO Grand Junc., Colo.	250				
CKWX Vancouver, B.C.	5000		WOAI San Antonio, Tex.	5000	5000	KLYC Leadville, Colo.	250				
KSDO San Diego, Calif.	5000					KDZA Pueblo, Colo.	250				
			1210-247.8			KGEG Sterling, Colo.	250				
			WCNT Centalla, Ill.	1000	1000	WGGG Gainesville, Fla.	250				
						WONN Lakeland, Fla.	250				
						WNAF Madison, Fla.	250				
						WSBB New Smyrna Bch., Fla.	250	</			

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
CJRW	Wamsutter, P.E.I.	250	WBAX	Wilkes-Barre, Pa.	250	WCMN	Arecibo, P.R.	1000
CKLN	Nelson, B.C.	250	WALO	Humacao, P.R.	250	WANS	Anderson, S.C.	1000
CKLS	LaSarre, Que.	250	WVON	Woonsocket, R.I.	250	WJAY	Mullins, S.C.	1000
CKTS	Sherbrooke, Que.	250	WKDK	Newberry, S.C.	250	WJGD	Columbia, Tenn.	1000
WEBJ	Brewton, Ala.	250	WEJZ	Elizabethton, Tenn.	250	KNIT	North Texas	500
WULA	Eufaula, Ala.	250	WEKR	Fayetteville, Tenn.	250	KWHI	Brenham, Tex.	1000
WOWL	Florence, Ala.	250	WEFR	Knoxville, Tenn.	250	KLTI	Longview, Tex.	1000
WARF	Jasper, Ala.	250	WKDA	Northwest, Tenn.	250	KNKX	Salt Lake City, Utah	5000
KWJB	So. of Globe, Ariz.	250	WENK	Union City, Tenn.	250	WYVE	Wytheville, Va.	1000
KOFA	Yuma, Ariz.	250	KANI	Kailua, T. Hawaii	250	KIT	Yakima, Wash.	5000
KVRC	Arkadelphia, Ark.	250	KVLF	Alpine, Tex.	250	WMNF	Richwood, W.Va.	1000
KAGH	Crossett, Ark.	250	KEAN	Brownwood, Tex.	100	WVAM	Newman, Wis.	1000
KHOZ	Harrison, Ark.	250	KORA	Bryan, Tex.	250			
KWAK	Stuttgart, Ark.	250	KOCA	Kilgore, Tex.	250	1290—232.4		
KRCR	Greent City, Calif.	250	KSOX	Raymondville, Tex.	250	CKSL	London, Ont.	5000
KROU	Diablo, Calif.	250	KXOX	Sweetwater, Tex.	250	WPBB	Jackson, Ala.	1000
KMBY	Monterey, Calif.	250	WSKI	Montpelier, Vt.	250	WVLS	Spencer, Ala.	1000
KPPC	Pasadena, Calif.	100	WSSV	Petersburg, Va.	250	KVOA	Tucson, Ariz.	1000
KRKS	Ridgecrest, Calif.	250	WRDV	Roanoke, Va.	250	KDMS	El Dorado, Ark.	5000
KROY	Sacramento, Calif.	250	WXTN	Staunton, Va.	250	KUOA	Siloam Sprgs., Ark.	5000
KRNO	San Bernardino, Calif.	250	KLEL	Ellensburg, Wash.	250	KHSL	Chico, Calif.	5000
KSON	San Diego, Calif.	250	KGY	Olympia, Wash.	250	KPER	Gilroy, Calif.	500
KSMA	Santa Maria, Calif.	250	WKDY	Waco, W.Va.	250	KITO	San Bernardino, Calif.	5000
KSUS	Susana, Calif.	250	WTIP	Charleston, W.Va.	250	WCLY	Spokane, Wash.	5000
KRDO	Colo. Sprgs., Colo.	250	WDNE	Elkins, W.Va.	250	WTUX	Wilmington, Del.	1000
KDGO	Durango, Colo.	250	WOMT	Manitowish, Wis.	250	WTMC	Ocala, Fla.	5000
KSLV	Monte Vista, Colo.	250	WIBU	Poyntelle, Wis.	250	WIRK	W. Palm Beh., Fla.	5000
KCRT	Trinidad, Colo.	250	WOBT	Rhineland, Wis.	250	WDEC	Americus, Ga.	1000
WBCO	Waterbury, Conn.	250	WJMC	Rice Lake, Wis.	250	WCHK	Canton, Ga.	1000
WWGO	Chipsy, Fla.	250	KFCB	Cheynno, Wis.	250	WTOC	Savannah, Ga.	5000
WLCO	Eustis, Fla.	250	KXOK	Swanton, Wis.	250	WPKS	Payson, Idaho	5000
WINK	Fort Myers, Fla.	250	KASL	Newcastle, Wyo.	250	WIRL	Pearis, Ill.	1000
WMMB	Melbourne, Fla.	250	KRAL	Rawlins, Wyo.	250	WCBL	Tenn, Ky.	1000
WFOY	St. Augustine, Fla.	250	KTHE	Thermopolis, Wyo.	250	KJEF	Jennings, La.	1000
WBHB	Fitzgerald, Ga.	250				WHGR	Houghton Lake, Michigan	5000
WDUN	Gainesville, Ga.	250	1250—239.9			WNIL	Niles, Mich.	500
WLAG	LaGrange, Ga.	250	CHWO	Dakville, Ont.	1000	WJIA	Saline, Mich.	1250
WBML	Macon, Ga.	250	CKBL	Matane, Que.	5000	WJBC	Wichita Falls, Tex.	500
WVNS	Statesboro, Ga.	250	CKSB	St. Boniface, Man.	1000	WBLE	Batesville, Miss.	1000
WPAX	Thomasville, Ga.	250	WZOB	ft. Payne, Ala.	1000	KALM	Thayer, Mo.	1000
WTWA	Thomson, Ga.	250	WETU	Wetumpka, Ala.	1000	KGYO	Missoula, Mont.	5000
KVNI	Coeur d'Alene, Idaho	250	KFAY	Fayetteville, Ark.	500	KOIL	Omaha, Neb.	5000
KWIK	Pocatello, Idaho	100	KGHI	Little Rock, Ark.	1000	WKNE	Keene, N.H.	5000
WCRW	Chicago, Ill.	100	KHUK	Hayward, Calif.	500	WNBF	Binghamton, N.Y.	5000
WEDC	Chicago, Ill.	250	KTMS	Santa Barbara, Calif.	1000	WPKY	Waynesboro, N.C.	5000
WSBC	Chicago, Ill.	250	KGOL	Golden, Colo.	1000	WYEF	Sandwich, N.C.	1000
WEBO	Harrisburg, Ill.	250	WNER	Live Oak, Fla.	1000	WTRX	Bellaire, Ohio	1000
WTAX	Springfield, Ill.	100	WDAE	Tampa, Fla.	5000	WHIO	Dayton, Ohio	5000
WDSR	Stirling, Ill.	100	WMGE	Madison, Ga.	1000	KUMA	Pendleton, Oreg.	1000
WHBU	Anderson, Ind.	250	WJZZ	Streator, Ill.	500	KLIT	Portland, Oreg.	5000
KDEC	Decorah, Iowa	250	WGLL	W. Wayne, Ind.	1000	WTRN	Lyrene, Pa.	1000
KWLC	Decorah, Iowa	250	WRAY	Wilmington, Ind.	5000	WICE	Paris, Pa.	1000
KBIZ	Ottumwa, Iowa	250	WFKU	Lawrence, Kans.	5000	WJG	Sumter, S.C.	500
KKD	Spencer, Iowa	250	WREN	Topeka, Kans.	5000	WQKE	Aok Ridge, Tenn.	1000
KIUL	Garden City, Kans.	250	WARE	Ware, Mass.	1000	KIVY	Crockett, Tex.	500
KACE	Wichita, Kans.	250	WWBC	Bay City, Mich.	1000	KRGV	Weslaco, Tex.	5000
WINN	Louisville, Ky.	250	KGDE	Fergus Falls, Minn.	1000	KTRN	Wichita Falls, Tex.	5000
WFTM	Maysville, Ky.	250	KQUC	Red Wing, Minn.	5000	WPVA	Logan Hpts., Va.	5000
WPKE	Pikeville, Ky.	250	WHNY	Macomb, Minn.	5000	WAGE	Logan, W.Va.	1000
WSFC	Somersett, Ky.	250	KVLY	Fallon, Nev.	1000	WYOW	Columb., W.Va.	5000
KAPK	London, La.	250	WMTR	Morristown, N.J.	1000	WMIL	Milwaukee, Wis.	1000
KANE	New Iberia, La.	250	WIPR	Ticonderoga, N.Y.	1000	WCOW	Sparta, Wis.	1000
COU	Lewiston, Maine	250	WBRM	Marion, N.C.	1000			
WCEM	Cambridge, Md.	250	WCHO	Washington Court House, Ohio	500	1300—230.6		
WJEJ	Hagerstown, Md.	250	WPEL	Pittsburgh, Pa.	5000	CBAF	Moncton, N.B.	5000
WHAI	Greenfield, Mass.	250	WCAE	Pittsburgh, Pa.	1000	CJRH	Richmond Hill, Ont.	500
WOCB	W. Yarmouth, Mass.	250	WNOW	York, Pa.	5000	WTLS	Tallassee, Ala.	1000
WATT	Cadillac, Mich.	250	WTMA	Charleston, S.C.	5000	KWBC	Searcy, Ark.	1000
WCBY	Chesogan, Mich.	250	WKBL	Covington, Tenn.	1000	KROF	Brawley, Calif.	1000
WIPD	Ishpeming, Mich.	250	KFTX	Paris, Tex.	500	KYD	Leiston, Idaho	1000
WJIM	Lansing, Mich.	250	KPAC	Port Arthur, Tex.	500	KWKW	Pasadena, Calif.	1000
WMFG	Hibbing, Minn.	250	KEXX	San Antonio, Tex.	500	KVOR	Colo. Sprgs., Colo.	1000
WJON	St. Cloud, Minn.	250	KSMI	Seminole, Tex.	1000	WAVZ	New Haven, Conn.	1000
WMFA	Aberdeen, Miss.	250	KVEL	Vernal, Utah	1000	WWTB	Tampa, Fla.	1000
WGRM	Greenwood, Miss.	250	WDVA	Danville, Va.	5000	WMTM	Moultrie, Ga.	5000
WGCM	Gulfport, Miss.	250	WYSR	Franklin, Va.	1000	WIMB	Windsor, Ga.	1000
WMDX	Meridian, Miss.	250	KWSS	Pullman, Wash.	5000	KOZE	Leiston, Idaho	5000
WMIS	Natchez, Miss.	250	WEMP	Milwaukee, Wis.	5000	WTAQ	LaGrange, Ill.	5000
KFMO	Flat River, Mo.	250				WFRX	W. Frankfort, Ill.	1000
KWOS	Jefferson City, Mo.	250	1260—238.0			WHLT	Huntington, Ind.	500
KNEM	Nevada, Mo.	250	CFRN	Edmonton, Alta.	5000	WMFT	Terre Haute, Ind.	500
KBMV	Billings, Mont.	250	DYBU	Cebu, P.I.	1000	KGLO	Mason City, Iowa	5000
KLTX	Glasgow, Mont.	250	KPRT	Birmingham, Ala.	1000	WBLS	Lexington, Ky.	1000
KFOR	Lincoln, Nebr.	250	KPIN	Casa Grande, Ariz.	1000	WBR	Baton Rouge, La.	1000
KODY	North Platte, Nebr.	250	KGIL	San Fernando, Calif.	1000	KLUE	Shreveport, La.	1000
KELK	Elko, Nev.	250	KYA	San Francisco, Calif.	5000	WFRB	Baltimore, Md.	5000
WKBR	Manchester, N.H.	250	WWOC	Washington, D.C.	250	WJDA	Quincy, Mass.	1000
WSNJ	Bridgeton, N.J.	250	WMTW	Washington, D.C.	1000	WOOD	Grand Rap., Mich.	5000
KAVE	Carrisbad, N.Mex.	250	WMNI	Miami, Fla.	5000	WRBC	Jackson, Miss.	5000
KLTV	Clifton, N.Mex.	250	WWPF	Palatka, Fla.	1000	KMMO	Morsharth, Mo.	1000
WGBB	Frederick, N.Y.	250	WHAB	Baxley, Ga.	5000	WYET	Austin, Tex.	1000
WGVA	Geneva, N.Y.	250	WTJH	East Point, Ga.	5000	WTRJ	Trenton, N.J.	250
WJTN	Jamestown, N.Y.	250	WIBV	Belleville, Ill.	1000	WOSL	Fulton, N.Y.	1000
WVOS	Liberty, N.Y.	250	WFBM	Indianapolis, Ind.	5000	WGOL	Goldboro, N.C.	1000
WNBZ	Saranac Lake, N.Y.	250	KDZG	Boone, Minn.	1000	WSDY	Mt. Airy, N.C.	5000
WSNY	Schenectady, N.Y.	250	KWHK	Hutchinson, Kans.	1000	WERE	Cleveland, Ohio	5000
WATN	Watsonville, Calif.	250	WXOK	Baton Rouge, La.	1000	WRMVO	Mt. Vernon, Ohio	5000
WBTV	Brevard, N.C.	250	WEZE	Boston, Mass.	1000	WRTV	Austin, Tex.	5000
WDOC	Charlotte, N.C.	250	WALB	Albion, Mich.	1000	KTFY	Brownfield, Tex.	1000
WJNC	Elizabeth City, N.C.	250	KRDX	Crookston, Minn.	1000	KOL	Seattle, Wash.	5000
WRAL	Raleigh, N.C.	250	KDZG	Hutchinson, Minn.	1000	WCLG	Morgantown, W.Va.	1000
KDLR	Devils Lake, N.Dak.	250	WJBL	Holland, Mich.	500	WKLC	St. Albans, W.Va.	1000
WBWB	Youngstown, Ohio	250	KRDX	Crookston, Minn.	1000			
WHIZ	Zanesville, Ohio	250	KDZG	Hutchinson, Minn.	1000	1310—228.9		
KVSD	Admore, Okla.	250	WGMV	Greenville, Miss.	1000	CKOY	Ottawa, Ont.	5000
KASA	Elk City, Okla.	250	WNSL	Laurel, Miss.	1000	WHEP	Foley, Ala.	1000
KBEL	Idabel, Okla.	250	KGBX	Springfield, Mo.	5000			
KHBB	Okmulgee, Okla.	250	WBUD	Trenton, N.J.	5000			
KFLY	Corvallis, Oreg.	250	KVSF	Santa Fe, N.Mex.	1000			
KWCC	Pendleton, Oreg.	250	WDRS	Syracuse, N.Y.	5000			
KPRB	Redmond, Oreg.	250	KFWP	Fort Worth, N.C.	1000			
KRXL	Roseburg, Oreg.	250	WCD	Edenton, N.C.	1000			
WRTA	Altoona, Pa.	250	WDDK	Cleveland, Ohio	5000			
WLEM	Emporium, Pa.	1000	WNXT	Portsmouth, Ohio	5000			
WHUM	Reading, Pa.	250	KWSH	Wewoka-Seminole, Oklahoma	1000			
WKOK	Sunbury, Pa.	250						
1270—236.1			1270—236.1			1270—236.1		
CHAT	Medicine Hat, Alta.	1000	CHAT	Medicine Hat, Alta.	1000	CHAT	Medicine Hat, Alta.	1000
CHWK	Chilliwalk, B.C.	1000	CHWK	Chilliwalk, B.C.	1000	CHWK	Chilliwalk, B.C.	1000
CJCB	Sydney, N.S.	5000	CJCB	Sydney, N.S.	5000	CJCB	Sydney, N.S.	5000
CFGT	St. Joseph d'Alma, Quebec	1000	CFGT	St. Joseph d'Alma, Quebec	1000	CFGT	St. Joseph d'Alma, Quebec	1000
GVSV	Guntersville, Ala.	1000	GVSV	Guntersville, Ala.	1000	GVSV	Guntersville, Ala.	1000
WAIP	Priehard, Ala.	250	WAIP	Priehard, Ala.	250	WAIP	Priehard, Ala.	250
KBYR	Anchorage, Alaska	1000	KBYR	Anchorage, Alaska	1000	KBYR	Anchorage, Alaska	1000
KDJI	Holbrook, Ariz.	1000	KDJI	Holbrook, Ariz.	1000	KDJI	Holbrook, Ariz.	1000
KCKK	Tulare, Calif.	5000	KCKK	Tulare, Calif.	5000	KCKK	Tulare, Calif.	5000
WNOG	Napa, Fla.	5000	WNOG	Napa, Fla.	5000	WNOG	Napa, Fla.	5000
WHLY	Orlando, Fla.	5000	WHLY	Orlando, Fla.	5000	WHLY	Orlando, Fla.	5000
WTAL	Tallahassee, Fla.	5000	WTAL	Tallahassee, Fla.	5000	WTAL	Tallahassee, Fla.	5000
WGBA	Columbus, Ga.	5000	WGBA	Columbus, Ga.	5000	WGBA	Columbus, Ga.	5000
WJJC	Commerce, Ga.	1000	WJJC	Commerce, Ga.	1000	WJJC	Commerce, Ga.	1000
KTFI	Twin Falls, Idaho	5000	KTFI	Twin Falls, Idaho	5000	KTFI	Twin Falls, Idaho	5000
WEIC	Charleston, Ill.	1000	WEIC	Charleston, Ill.	1000	WEIC	Charleston, Ill.	1000
WHBF	Rock Island, Ill.	5000	WHBF	Rock Island, Ill.	5000	WHBF	Rock Island, Ill.	5000
WCMR	Elkhart, Ind.	500	WCMR	Elkhart, Ind.	500	WCMR	Elkhart, Ind.	500
WACA	Gary, Ind.	500	WACA	Gary, Ind.	500	WACA	Gary, Ind.	500
WORX	Madison, Ind.	1000	WORX					

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
WCCN	Naillville, Wis.	1000	KRE	Berkeley, Calif.	250	KGVL	Greenville, Tex.	250	WEUC	Ponce, P.R.	1000
KVVO	Cheyenne, Wyo.	1000	KREO	Indio, Calif.	250	KEBE	Jacksonville, Tex.	250	WATD	Cheraw, S.C.	1000
1380—217.3											
CFDA	Victoriaville, Que.	1000	KSDA	Redding, Calif.	250	KIUN	Peecos, Tex.	250	WEMB	Erwin, Tenn.	1000
CKPC	Brantford, Ont.	1000	KCOY	Santa Maria, Calif.	250	KEYE	Perryton, Tex.	250	WKSJ	Paducah, Tenn.	1000
CKLK	Kingston, Ont.	5000	KUKA	Ukiah, Calif.	250	KVOP	Plainville, Tex.	250	KFYB	Bonham, Tex.	250
WGYY	Greenville, Ala.	1000	KKUN	Vision City, Colo.	250	KDWT	Stamford, Tex.	250	KTRF	Lufkin, Tex.	1000
KNLR	N. Little Rock, Ark.	1000	KDIA	Delta, Colo.	250	KTEM	Temple, Tex.	250	KGNB	New Braunfels, Tex.	1000
KBVM	Lancaster, Calif.	1000	KFTM	Ft. Morgan, Colo.	250	KFTS	Texarkana, Tex.	250	KPEP	San Angelo, Tex.	1000
KGMS	Sacramento, Calif.	1000	KBZJ	La Junta, Colo.	250	KVOU	Uvalde, Tex.	250	WWSR	St. Albans, Vt.	1000
KSBJ	Sallinas, Calif.	1000	WSTC	Stamford, Conn.	250	KIXX	Provo, Utah	250	WDDY	Gloucester, Va.	1000
KFWL	Walsenburg, Colo.	1000	WILL	Williamstown, Conn.	250	WDOT	Burlington, Vt.	250	WKTJ	Warrenton, Va.	5000
WAMS	Wilmington, Del.	1000	FTL	Ft. Lauderdale, Fla.	250	WINA	Charlottesville, Va.	250	KFTC	Charlottesville, Va.	5000
WQXQ	Ormond Beach, Fla.	1000	WIRA	Fl. Pierce, Fla.	250	WHLF	So. Boston, Va.	250	KUJ	Wallia Wallia, Wash.	5000
WTSJ	St. Petersburg, Fla.	1000	WRHC	Jacksonville, Fla.	250	WINC	Winchester, Va.	250	WPLY	Plymouth, Wis.	500
WAKO	Atlanta, Ga.	5000	WPCF	Panama City, Fla.	250	KFRD	Grand Coulee, Wash.	250	1430—209.7		
WKIG	Ft. Wayne, Ind.	5000	WPRY	Perry, Fla.	250	KWLK	Longview, Wash.	250	WFHK	Pell City, Ala.	1000
KCMJ	Carroll, Iowa	1000	WTRR	Sanford, Fla.	250	KTNT	Tacoma, Wash.	250	KHEM	Hemlock, Ark.	1000
WMTA	Central City, Ky.	1000	WCOS	Alma, Ga.	250	WBOY	Clarksburg, W.Va.	250	KAMP	El Centro, Calif.	1000
WKWK	Winchester, Ky.	1000	WSGC	Elberton, Ga.	250	WRON	Rosemeade, W.Va.	250	KARM	Fresno, Calif.	5000
WEND	Bata Rouge, La.	500	WMAQ	Macon, Ga.	250	WTKA	Thomas, Va.	250	KAL1	Pasadena, Calif.	5000
WTHH	Port Huron, Mich.	1000	WMGA	Moultrie, Ga.	250	WBTM	Williamsport, W.Va.	250	KOSI	Aurora, Colo.	5000
KLIZ	Brainerd, Minn.	1000	WCOH	Newnan, Ga.	250	WATW	Ashland, Wis.	250	WDSB	Homestead, Fla.	5000
WNLA	Indianola, Miss.	500	WGSJ	Savannah, Ga.	250	WBIZ	Eau Claire, Wis.	250	WLAK	Lakeland, Fla.	5000
WTUP	Tupelo, Miss.	1000	KIFI	Idaho Falls, Idaho	250	WDUZ	Green Bay, Wis.	250	WGSF	Covington, Ga.	1000
KUDI	Kansas City, Mo.	1000	KART	Jerome, Idaho	250	WRIN	Racine, Wis.	250	WWSG	Tifton, Ga.	5000
KWK	St. Louis, Mo.	5000	KRPL	Moscow, Idaho	250	WRDB	Reedsburg, Wis.	250	WCMY	Ottawa, Ill.	5000
KUYR	Holdrege, Neb.	500	WRPL	Portland, Idaho	250	WWSL	Wausau, Wis.	250	WIRE	Indianapolis, Ind.	1000
WAWZ	Zarephath, N.J.	5000	WDWS	Champaign, Ill.	250	WTTI	Casper, Wyo.	250	KASI	AMES, Iowa	5000
WBNX	New York, N.C.	5000	WGIL	Galesburg, Ill.	250	KODI	Cody, Wyo.	250	KMIC	Hazard, Ky.	1000
WLOS	Ashville, N.C.	5000	WEOA	Evansville, Ind.	250	1410—212.6			KMRC	Morgan City, La.	5000
WTOB	Winston-Salem, N.C.	5000	WBAT	Marion, Ind.	250	CFUN	Vancouver, B.C.	1000	WNAY	Annapolis, Md.	1000
WPKO	Waverly, Ohio	5000	KCOG	Centerville, Iowa	100	CHLP	Montreal, Que.	1000	WHLS	Wichita, Kan.	5000
KSWO	Lawson, Ohio	5000	KVFD	Fort Dodge, Iowa	100	WOLA	Walla Walla, Wash.	250	WION	Ionia, Mich.	500
KWON	Honolulu, Okla.	1000	KAYS	Hays, Kans.	250	KCTC	Ft. Smith, Ark.	500	WBRB	Mt. Clemens, Mich.	5000
KSRV	Ontario, Ore.	1000	KAYS	Hays, Kans.	250	KERN	Bakersfield, Calif.	500	WIL	St. Louis, Mo.	5000
WACB	Kittanning, Pa.	1000	KWYN	Cynthiana, Ky.	100	KTEE	Carmel, Calif.	500	KRGI	Grand Island, Nebr.	1000
WAYZ	Waynesboro, Pa.	1000	WIEL	Elizabethtown, Ky.	250	KMYC	Marysville, Calif.	5000	WNJR	Newark, N.J.	5000
WNRI	Woonsocket, R.I.	1000	WFTG	London, Ky.	250	KCAL	Redlands, Calif.	1000	WENE	Endicott, N.Y.	5000
WAGS	Bishopville, S.C.	1000	WFRP	Hammond, La.	250	KCOL	Ft. Collins, Colo.	5000	WMNC	Morgantown, N.C.	1000
KOTA	Rapid City, S.Dak.	5000	KAOK	Lake Charles, La.	250	WDOV	Dover, Del.	5000	WFOB	Fostoria, Ohio	1000
KJON	Honolulu, Okla.	5000	WRDQ	Wagoner, Maine	250	WMYR	Ft. Myers, Fla.	5000	WCLT	Newark, Ohio	500
KJET	Beaumont, Tex.	1000	WIDE	Biddeford, Maine	250	WBIL	Leesburg, Fla.	1000	KALV	Alva, Okla.	5000
KBWD	Brownwood, Tex.	1000	WWIN	Baltimore, Md.	250	WDAX	McRae, Ga.	250	KTLV	Lookout Mountain, Okla.	5000
KTSM	El Paso, Tex.	1000	WALE	Fall River, Mass.	250	WLAQ	Rome, Ga.	1000	KGAY	Salem, Ore.	5000
KMUL	Muleshoe, Tex.	500	WLLH	Lowell, Mass.	250	WRMN	Elgin, Ill.	500	WWM	Wilmington, Pa.	5000
KBOP	Pleasanton, Tex.	5000	WHMP	Northampton, Mass.	250	WTIM	Taylorville, Ill.	500	WBLR	Batesburg, S.C.	5000
WSYB	Rutland, Vt.	5000	WELL	Battle Creek, Mich.	250	WTLN	Waynesville, N.C.	1000	WATP	Marion, S.C.	1000
WNBG	Richmond, Va.	1000	WDET	Detroit, Mich.	250	WTKM	Wichita, Kan.	5000	KBRK	Brookings, S.Dak.	5000
KRKO	Everett, Wash.	1000	WMLB	Wilmington, Mich.	250	KWBB	Wichita, Kan.	1000	WENO	Madison, Tenn.	5000
WBEL	Beloit, Wis.	5000	WSAM	Saginaw, Mich.	250	WLBJ	Bowling Green, Ky.	5000	KSTB	Brockenridge, Tex.	1000
1390—215.7											
WHMA	Anniston, Ala.	5000	WSJM	St. Joseph, Mich.	250	WHLN	Harlan, Ky.	5000	KSHJ	Gladeview, Tex.	1000
KDQN	DeQuette, Ark.	500	WTCM	Traverse City, Mich.	250	KDBS	Alexandria, La.	1000	KCOH	Houston, Tex.	1000
KAMO	Rogers, Ark.	1000	KMHL	Marshall, Minn.	250	WHPB	Houston, Tex.	1000	KBCR	Mt. Vernon, Wash.	1000
KGER	Long Beach, Calif.	5000	WMIN	Mpls.-St. Paul, Minn.	250	WKBK	Newton, Mass.	500	WEIR	Weirton, W.Va.	1000
KTUR	Turlock, Calif.	1000	WBLP	Birmingham, Minn.	250	WHTG	Eatonville, N.J.	500	WBEV	Beaver Dam, Wis.	1000
KFML	Denver, Colo.	1000	WBOE	Boonville, Mo.	250	WDOE	Dunkirk, N.Y.	500	WEGO	Concord, N.C.	1000
WAVP	Avon Park, Fla.	1000	WNAG	Grenada, Miss.	250	WEGC	Concord, N.C.	1000	WSRC	Durham, N.C.	1000
WECS	Chicago, Ill.	5000	WFOR	Hattiesburg, Miss.	250	WING	Dayton, Ohio	1000	WING	Dayton, Ohio	1000
WFIW	Fairfield, Ill.	1000	WJQS	Jackson, Miss.	250	KRAM	Rockford, Ore.	1000	WLSH	Lansford, Pa.	5000
WJCD	Seymour, Ind.	1000	WMBC	Macon, Miss.	250	KQV	Pittsburgh, Pa.	5000	WYMB	Manning, S.C.	1000
KCLN	Clinton, Iowa	1000	KFRU	Columbia, Mo.	250	WCMT	Martin, Tenn.	250	KPRO	Riverside, Calif.	1000
KCBC	Des Moines, Iowa	1000	KSTM	St. Joseph, Mo.	250	KBUS	Athens, Tex.	250	WBIS	Bristol, Conn.	500
KNCK	Concordia, Kans.	500	KTTS	Springfield, Mo.	250	KVLB	Cleveland, Tex.	500	WABC	Birmingham, Ala.	1000
KNDE	Monroe, La.	5000	KXGN	Glendive, Mont.	250	KWYD	Wichita, Kan.	500	WGGC	Greenville, S.C.	5000
WCAT	Orange, Mass.	1000	KXKL	Great Falls, Mont.	250	KRIG	Odessa, Tex.	1000	WXL1	Dublin, Ga.	1000
WFLM	Plymouth, Mass.	1000	KCOW	Alliance, Nebr.	250	KBAL	San Saba, Tex.	500	WRAJ	Anna, Ill.	500
WCER	Charlottesville, Va.	1000	KLIN	Lincoln, Nebr.	250	KNAL	Victoria, Tex.	500	WPRS	Paris, Ill.	1000
KRFO	Owatonna, Minn.	500	KVCH	O'Neill, Nebr.	250	KUEN	Wenatchee, Wash.	5000	WRCK	Rockford, Ill.	1000
WROA	Gulfport, Miss.	1000	KPTL	Carson City, Nev.	250	KWBH	Laurens, W.Va.	500	KCHE	Cherokee, Iowa	500
WQBC	Meridian, Miss.	5000	KBMJ	Bozeman, Nev.	250	KWYO	Sherridan, Wyo.	1000	KJAY	Topeka, Kans.	5000
KVBC	Farmington, N.Mex.	5000	KWNA	Winnebec, Nev.	250	CJMT	Chicoutimi, Que.	1000	WKXJ	Paris, Ky.	1000
WEOK	Poughkeepsie, N.Y.	1000	WTSJ	Hanover, N.H.	250	CKOM	Saskatoon, Sask.	5000	KMLB	Monroe, La.	5000
WFL	Riverhead, N.Y.	1000	KGFL	Roswell, N.Mex.	250	KHFB	Sierra Vista, Ariz.	1000	WAAB	Warencaster, Mass.	5000
WFB1	Syracuse, N.Y.	5000	KTRC	Santa Fe, N.Mex.	250	KPOC	Pochontas, Ariz.	1000	WECM	Bay City, Mich.	1000
WFNC	Fayetteville, N.C.	5000	KCHS	Truth or Consequences, N.Mex.	250	KSTN	Stockton, Calif.	1000	WCHB	Inkster, Mich.	500
WEED	Rocky Mt. N.C.	5000	KTNN	Tucumcari, N.Mex.	250	WLIS	Old Saybrook, Conn.	500	KEVE	Minneapolis, Minn.	5000
KLPM	Minot, N.Dak.	5000	WOND	Pleasantville, N.J.	250	WDBF	Delray Beach, Fla.	500	WMVB	Millville, N.J.	1000
WOHP	Bellefontaine, Ohio	5000	WABY	Albany, N.Y.	250	WSTN	St. Augustine, Fla.	1000	WBAJ	Babylon, N.Y.	500
WFNJ	Youngstown, Ohio	5000	WBNY	Buffalo, N.Y.	250	WRBL	Columbus, Ga.	5000	WJLJ	Niagara Falls, N.Y.	1000
KCRC	Enid, Okla.	1000	WELM	Elmira, N.Y.	250	WRET	Wentworth, N.H.	5000	WBLA	Elizabethtown, N.C.	1000
KSLM	Salem, Ore.	1000	WSLB	Ogdensburg, N.Y.	250	WINI	Murphysboro, Ill.	5000	WVOT	Vermont, N.C.	1000
WLAN	Laneaster, Pa.	1000	WGBA	Greensboro, N.C.	250	WIMS	Michigan City, Ind.	5000	KITX	Kitfox, N.D.	1000
WHBP	Belton, S.C.	500	WKDX	Hamlet, N.C.	250	WVCN	Vancouver, B.C.	1000	WHH	Warren, Ohio	5000
WCSJ	Charleston, S.C.	5000	WSIC	Statesville, N.C.	250	WDAV	Davenport, Iowa	5000	KMED	Medford, Ore.	5000
WTJ3	Jackson, Tenn.	1000	WLSA	Wallace, N.C.	250	KJCK	Junction City, Kans.	1000	KODL	The Dalles, Ore.	1000
KULP	El Campo, Tex.	500	WHCC	Waynesville, N.C.	250	WTRG	Ashtand, Ky.	5000	WCDL	Carbondale, Pa.	5000
KBEC	Waxahatchie, Tex.	1000	KEYJ	Jamestown, N.Dak.	250	WHBN	Harradburg, Ky.	1000	WGBB	Red Lion, Pa.	1000
KLGN	Logan, Utah	500	KWON	Wagoner, Okla.	250	WVPS	Waverly, Pa.	5000	WQOK	Greenville, S.C.	1000
WEAM	Arlington, Va.	5000	KTMK	McAister, Okla.	250	WVLS	Waverly, Pa.	5000	KYCX	Cowan, Tenn.	1000
WWOOD	Lynchburg, Va.	5000	KNOR	Norman, Okla.	250	WVLA	Waynesville, N.C.	1000	WHDM	McKenzie, Tenn.	5000
KLOQ	Yakima, Wash.	1000	KWIN	Ashland, Ore.	250	WVLY	Waynesville, N.C.	1000	KFDA	Amariillo, Tex.	5000
1400—214.2											
CKBC	Bathurst, N.B.	250	KDMB	Cottage Grove, Ore.	250	WVOT	Vermont, N.C.	1000	KEYS	Corpus Christi, Tex.	1000
CKCY	Sault Ste. Marie, Ont.	250	KBCH	Oceanlake, Ore.	250	WVPS	Waverly, Pa.	5000	KDNT	Denton, Tex.	1000
CKFH	Toronto, Ont.	250	WEST	Easton, Pa.	250	WVBC	Pittsfield, Mass.	1000	KETX	Livingston, Tex.	1000
CKRB	Ville St. George, Que.	250	WHGB	Harrisburg, Pa.	250	WVAM	Flint, Mich.	500	WVLC	Wilmington, Vt.	5000
CKRN	Rouye, Que.	250	WJAC	Johnstown, Pa.	250	KTOE	Mankato, Minn.	500	KITX	Olympia, Wash.	500
CKSW	Swift Current, Sask.	250	WKBI	St. Marys, Pa.	250	WSUH	Oxford, Miss.	250	WHIS	Bluefield, W.Va.	500
WMSL	Decatur, Ala.	250	WICK	Seranton, Pa.	250	WQBC	Wicksburg, Miss.	500	WJPG	Green Bay, Wis.	5000
WXAL	Demopolis, Ala.	250	WRAK	Williamsport, Pa.	250	KBTN	Neeshe, Mo.	1000	1450—206.8		
WFLA	Ft. Payne, Ala.	250	WHOA	San Juan, P.R.	250	KOOO	Omaha, Nebr.	500	CBG	Gander, Nfld.	250
WJLD	Homewood, Ala.	250	WCOY	Columbia, S.C.	250	WACK	Newark, N.J.	500	CFAB	Windsor, N.S.	250
WJHO	Opekika, Ala.	250	WGTN								

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
CJOY	Guelph, Ont.	250	KFLW	Klamath Falls, Oreg.	250	WKMF	Flint, Mich.	1000	WCSL	Sylvania, Ga.	250
WDNG	Annisston, Ala.	250	KFLM	La Grande, Oreg.	250	WKLD	Kalamazoo, Mich.	1000	KTOH	Lihue, Hawaii	250
WBGO	Bessemer, Ala.	250	KBPS	Portland, Oreg.	250	KANO	Anoka, Minn.	1000	KCID	Caldwell, Idaho	250
WDIG	Dothan, Ala.	250	WLEU	Eric, Pa.	250	WCHI	Brookhaven, Miss.	500	WKRO	Cairo, Ill.	250
WFUN	Huntsville, Ala.	250	WGET	Gettysburg, Pa.	250	WNAU	New Albany, Miss.	500	WLAN	Topeka, Kans.	250
WLYA	Muscle Shoals City, Ala.	250	WDAO	Indiana, Pa.	250	KGHM	Brookfield, Mo.	1000	WAMV	Sac St. Louis, Ill.	250
KLAM	Cordova, Alaska	250	WPAM	Pottsville, Pa.	250	KTCB	Malden, Mo.	1000	WOPA	Oak Park, Ill.	250
KHCD	Clifton, Ariz.	250	WMAJ	State College, Pa.	250	WTKO	Ithaca, N.Y.	1000	WKBY	Richmond, Ind.	250
KWTT	Douglas, Ariz.	250	WJPA	Washington, Pa.	250	WPDM	Potsdam, N.Y.	1000	WNDU	South Bend, Ind.	250
KNOT	Prescott, Ariz.	250	WNEL	Caguas, P.R.	250	WBG	Greensboro, N.C.	5000	KBUR	Burlington, Iowa	250
KOLD	Tucson, Ariz.	250	WWRV	W. Warwick, R.I.	250	WPHC	Plymouth, N.C.	1000	WDBQ	Dubuque, Iowa	250
KHOG	Fayetteville, Ark.	250	WQSN	Charleston, S.C.	250	WHD	Spring Pine, N.C.	1000	KRIB	Mason City, Iowa	250
KENA	Mena, Ark.	250	WCRS	Greenwood, S.C.	250	WHO	Toledo, Ohio	1000	KTOP	Keosauqua, Iowa	250
KYOR	Blythe, Calif.	250	WMYB	Myrtle Beach, S.C.	250	KVLH	Pauls Valley, Okla.	250	WCPM	Cumberland, Ky.	250
KPAL	Port Springs, Calif.	250	WHSC	Hartsville, S.C.	250	WFIN	Vinita, Okla.	5000	WKY	Frankfort, Ky.	250
KSAT	San Francisco, Calif.	250	KYNT	Yankton, S.Dak.	250	WSAN	Allentown, Pa.	5000	WKAY	Glasgow, Ky.	250
KROG	Sonora, Calif.	250	WLAR	Athens, Tenn.	250	WJAR	Farrall, Pa.	1000	WMOJ	Dwainsboro, Ky.	250
KVEN	Ventura, Calif.	250	WAGC	Chattanooga, Tenn.	250	WDCI	Columbia, S.C.	5000	WSPC	Painville, Ky.	250
KAGR	Yuba City, Calif.	100	WDSB	Dyersburg, Tenn.	100	WEAG	Aleca, Tenn.	1000	KULN	Union, La.	250
KGIW	Alamosa, Colo.	250	WOLF	LaFollette, Tenn.	100	WVOL	Nashville, Tenn.	1000	KRUS	Ruston, La.	250
KYOU	Greely, Colo.	250	WGNS	Murfreesboro, Tenn.	250	KRBC	Ablene, Tex.	5000	WFOR	Portland, Maine	250
WLAB	Bridgeport, Conn.	250	KRIC	Beaumont, Tex.	250	KWRD	Henderson, Tex.	500	WTVL	Waterville, Maine	250
WNOB	Wilington, Conn.	250	KBEN	Carrizo Sprgs., Tex.	250	KCNV	San Marcos, Tex.	250	WARK	Hagerstown, Md.	250
WOL	Washington, D.C.	250	KCTI	Gonzales, Tex.	250	KELA	Centralia, Wash.	5000	WAVH	Haverhill, Mass.	250
WTKS	Brooksville, Fla.	250	KMBL	Junction, Tex.	250	KSEM	Moses Lake, Wash.	5000	WMRC	Milford, Mass.	100
WMFJ	Daytona Beach, Fla.	250	KCYL	Lampasas, Tex.	250	WPLH	Huntington, W.Va.	5000	WTKL	W. Springfield, Mass.	250
WSPK	Miami, Fla.	250	KMFT	Marshall, Tex.	250	WBRV	Way Bend, Wis.	5000	WABT	Adrian, Mich.	250
WBSR	Pensacola, Fla.	250	KCMR	McCamery, Tex.	250	KSPR	Casper, Wyo.	5000	WBFC	Fremont, Mich.	250
WSPB	Sarasota, Fla.	250	KNET	Palestine, Tex.	250				WMDN	Midland, Mich.	250
WSTP	Stuart, Fla.	100	KSNY	Snyder, Tex.	250				KXRA	Alexandria, Minn.	250
WNT	Tallahassee, Fla.	250	KURA	Moab, Utah	250				KOZY	Grand Rapids, Minn.	250
WBFC	Albany, La.	250	KEYY	Provo, Utah	250				KLGR	Redw. Falls, Minn.	100
WGHC	Cartersville, Ga.	250	KDXU	St. George, Utah	250				WLOX	Biloxi, Miss.	250
WCON	Cornelia, Ga.	250	WTSB	Dyersburg, Vt.	250				WCLD	Cleveland, Miss.	250
WKEU	Griffin, Ga.	250	WFRF	Front Royal, Va.	250				WLAU	Laurel, Miss.	250
WNYG	Milledgeville, Ga.	250	WREL	Lexington, Va.	250				WHOC	Philadelphia, Miss.	250
KPID	Savannah, Ga.	250	WMVA	Martinsville, Va.	250				WELT	Tupelo, Miss.	250
KWPC	Payette, Idaho	250	WLPM	Suffolk, Va.	250				WVIV	Vicksburg, Miss.	250
KEEP	Twin Falls, Idaho	250	KBIKW	Aberdeen, Wash.	250				KDMO	Carthage, Mo.	250
WHFC	Cicero, Ill.	250	KCLX	Collax, Wash.	250				KTRR	Rolla, Mo.	250
WKEL	Kewanee, Ill.	100	KRSC	Othello, Wash.	100				WADR	Adrian, Mich.	250
WCVS	Springfield, Ill.	250	KONP	Port Angeles, Wash.	250				KBOV	Keosauqua, Mo.	250
WFNE	Ft. Wayne, Ind.	250	KAYE	Puyallup, Wash.	250				KVOT	Wolf Point, Mont.	250
WAOV	Lafayette, Ind.	250	WPAP	Parkersburg, W.Va.	250				KBON	Omaha, Nebr.	250
WVAV	Vincennes, Ind.	250	WHAW	Weston, W.Va.	250				WLDB	Atlantic City, N.J.	250
KPIG	Cedar Rapids, Iowa	250	KFIZ	Fond du Lac, Wis.	250				KRSN	Los Alamos, N.Mex.	250
KWBW	Hutchinson, Kans.	250	WDLB	Marshfield, Wis.	250				KRTN	Raton, N.Mex.	250
WTKO	Campbellsville, Ky.	250	WFPF	Park Falls, Wis.	250				WGSS	Amsterdam, N.Y.	250
WNKY	Neon, Ky.	250	WRCO	Richmond Center, Wis.	250				WATV	Watkinsville, N.Y.	250
WPAD	Paduach, Ky.	250	KBBS	Buffalo, Wyo.	250				WKNY	Kingston, N.Y.	250
KSIG	Crowley, La.	250	KWRL	Riverton, Wyo.	250				WICY	Malone, N.Y.	250
KNLC	Natchitoches, La.	250							WDLF	Port Jervis, N.Y.	250
WNPS	New Orleans, La.	250							WOLF	Syracuse, N.Y.	250
WAGM	Presque Isle, Maine	250							WSSB	Durham, N.C.	250
WRKD	Rockland, Maine	250							WFLB	Fayetteville, N.C.	250
WTKD	South Paris, Maine	250							WFLB	Waxhite, N.C.	250
WTBO	Cumberland, Md.	250							WRNB	Norfolk, N.C.	250
WVAS	Springfield, Mass.	250							WSTP	Salisbury, N.C.	250
WVAP	Apex, Mich.	250							KNDC	Hettinger, N.Dak.	250
WHTC	Holland, Mich.	250							KOVC	Valley City, N.Dak.	250
WMIQ	Iron Mtn., Mich.	250							WBEX	Chillicothe, Ohio	250
WIBM	Jackson, Mich.	250							WSCR	Cleveland Hghts., Ohio	250
WKLA	Ludington, Mich.	250							WLOT	Liverpool, Ohio	250
WHLS	Port Huron, Mich.	250							WMOA	Marion, Ohio	250
KATE	Albert Lea, Minn.	250							WWRN	Marion, Ohio	250
WVLA	Belvidere, Minn.	250							KWRV	Guthrie, Okla.	100
KBMW	Breckenridge, Minn.	250							KBIX	Muskogee, Okla.	250
WELY	Ely, Minn.	250							KBKR	Baker, Oreg.	250
KDMA	Montevideo, Minn.	250							KRNR	Roseburg, Oreg.	250
KFAM	St. Cloud, Minn.	250							KBYZ	Salem, Oreg.	250
WROX	Clarksdale, Miss.	250							WOSB	Waco, Pa.	250
WCJA	Columbia, Miss.	250							WAZL	Hazleton, Pa.	250
WJKK	Jackson, Miss.	250							WARD	Johnstown, Pa.	250
WOKK	Meridian, Miss.	250							WGAL	Lancaster, Pa.	250
WNAT	Natchez, Miss.	250							WBCB	Levittown, Pa.	250
WROB	West Point, Miss.	250							WMRF	Levittown, Pa.	250
WMBH	Joplin, Mo.	250							WGWG	Meadville, Pa.	250
KJRX	Kirksville, Mo.	250							WNBK	New Bedford, Pa.	250
KOKO	Warrensburg, Mo.	250							WMDD	Fajardo, P.R.	250
KWPK	West Plains, Mo.	250							WGCD	Chester, S.C.	250
KXLL	Bozeman, Mont.	250							WMRB	Greenville, S.C.	250
KUDI	Great Falls, Mont.	250							KORN	Mitchell, S.Dak.	250
KXLL	Missoula, Mont.	250							WOPI	Bristol, Tenn.	250
KWBE	Beatrice, Nebr.	250							WDXB	Chattanooga, Tenn.	250
KCSR	Chadron, Nebr.	250							WDXL	Lewisburg, Tenn.	250
KONE	Reno, Nev.	250							WDTN	Denton, Tenn.	250
WKXL	Concord, N.H.	250							WATD	Dak Ridge, Tenn.	250
WCTC	West Brunswick, N.J.	250							KNOW	Austin, Tex.	250
KLOS	Albuquerque, N.Mex.	250							KIBL	Beville, Tex.	250
KLMX	Clayton, N.Mex.	250							KBST	Big Spring, Tex.	250
KOBE	Las Cruces, N.Mex.	250							KHUZ	Borger, Tex.	250
KENM	Portales, N.Mex.	250							WNEB	Brady, Tex.	250
WHDL	Allegany, N.Y.	250							KSAM	Huntsville, Tex.	250
WCLI	Corning, N.Y.	250							KVOZ	Laredo, Tex.	250
WWSC	Glen Falls, N.Y.	250							KVOV	Littletield, Tex.	250
WHDL	Olean, N.Y.	250							KPLT	Paris, Tex.	250
WKIP	Poughkeepsie, N.Y.	250							KGBK	Tyler, Tex.	250
WKAL	Rome, N.Y.	250							KVWG	Vernon, Tex.	250
WATL	Boone, N.C.	250							KVOG	Oden, Utah	250
WGPC	Gastonia, N.C.	250							WKIE	Nashville, Va.	250
WHVH	Henderson, N.C.	250							WVCA	Cupecper, Va.	250
WHKP	Hendersonville, N.C.	250							WVEC	Hampton, Va.	250
WHIT	West Bern, N.C.	250							WAYB	Waynesboro, Va.	250
KEYZ	Williston, N.Dak.	250							KBRD	Bremerton, Wash.	250
WJER	Dover, Ohio	250							KLOG	Kelso, Wash.	250
WMOH	Hamilton, Ohio	250							KENE	Torpenish, Wash.	250
WLEC	Sandusky, Ohio	250							WDEL	Delaware, Wash.	250
KWRW	Altus, Okla.	250							WHMS	Charleston, W.Va.	250
KGFF	Shawnee, Okla.	250							WTCS	Fairmont, W.Va.	250
KSIW	Woodward, Okla.	250							WLOH	Princeton, W.Va.	250
KWRO	Coquille, Oreg.	250							WGEZ	Beloit, Wis.	250
KORE	Eugene, Oreg.	250							WLXG	LaCrosse, Wis.	250
									WGMN	Nedford, Wis.	250
									WDSH	Onawa, Wis.	250
									KIMJ	Gillette, Wyo.	250
									KRTR	Thermopolis, Wyo.	250
									KGOS	Torrington, Wyo.	250

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	
1500—199.9												
CHUC	Port Hope, Ont.	1000	WBYS	Canton, Ill.	250	KPKI	Colorado Sprgs., Colo.	5000	WEHH	Elmira Hghts., Horseheads, N.Y.	500	
KXRX	San Jose, Calif.	1000	KSWI	Council Bluffs, Iowa	500	WWLF	Ft. Lauderdale, Fla.	1000	WNYS	Salamanea, N.C.	1000	
WTOP	Washington, D.C.	50000	WQXR	New York, N.Y.	50000	WCLS	Columbus, Ga.	1000	WGTC	Greenville, N.C.	5000	
WJBK	Detroit, Mich.	10000	WTNS	Coshocton, Ohio	1000	WDBA	DuQuoin, Ill.	250	WNOS	High Point, N.C.	1000	
KSTP	St. Paul, Minn.	50000	WTO	Toledo, Ohio	1000	WQBN	Pittsfield, Ill.	250	WAKR	Akron, Ohio	5000	
KTAN	Sherman, Tex.	250	KWCO	Chickasha, Okla.	1000	WKID	Urbana, Ill.	250	WSRW	Hillsboro, Ohio	500	
1510—199.1												
CKOT	Tillsonburg, Ont.	1000	WENA	Bayamon, P.R.	250	WCNB	Connersville, Ind.	1000	WHEN	Henryetta, Okla.	250	
KOCB	Ontario, Calif.	250	KHBR	Hillsboro, Tex.	250	WJVA	South Bend, Ind.	1000	KTIL	Tillamook, Oreg.	1000	
KTIN	San Rafael, Calif.	1000	1570—191.1			1000	WAMW	Washington, Ind.	1000	WYRF	Guayama, P.R.	5000
KUDY	Littletion, Colo.	1000	CHUB	Nanaimo, B.C.	1000	KCHA	Chardon, Ohio	1000	WCBG	Chambersburg, Pa.	1000	
WKAI	Macomb, Ill.	5000	CFRY	Portage la Prairie, Manitoba	250	WFGM	Davenport, Iowa	500	WDRF	Chester, Pa.	1000	
WMEX	Boston, Mass.	2500	CBI	Sidney, N.S.	1000	KDSN	Denison, Iowa	500	WABV	Abbeville, S.C.	1000	
KIMO	Independence, Mo.	5000	CFOR	Orillia, Ont.	1000	WGOR	Georgetown, Ky.	250	WACA	Camden, S.C.	1000	
WLAC	Nashville, Tenn.	50000	WCRJ	Onsetta, Ala.	250	WXXL	Manchester, Ky.	250	WDBL	Springfield, Tenn.	1000	
KCTV	Chicago, Ill.	250	WRWJ	Selma, Ala.	1000	WPKY	Princeton, Ky.	250	KGAS	Carthage, Tex.	1000	
KSTV	Stephensville, Tex.	250	KCVR	Lodi, Calif.	1000	KLUV	Haysville, La.	1000	KERC	Corpus Christi, Tex.	500	
KGA	Spokane, Wash.	50000	KLOV	Loveland, Colo.	250	KLOU	Lake Charles, La.	1000	KYOK	Houston, Tex.	5000	
WAUX	Waukesha, Wis.	250	WTWB	Auburndale, Fla.	1000	WRNC	Brabury Hghts., Md.	1000	KCBD	Lubbock, Tex.	1000	
1520—197.4												
WHOW	Clinton, Ill.	1000	WFBF	Fernandina Beh., Fla.	1000	WGLC	Centerville, Miss.	250	KANN	Sinton, Tex.	1000	
KSIB	Creston, Iowa	1000	WJOE	Ward Ridge, Fla.	250	WPMP	Paseo, Miss.	1000	WEZL	Richmond, Va.	5000	
WKBW	Buffalo, N.Y.	50000	WOKZ	Alton, Ill.	250	KBIA	Columbia, Mo.	250	WSSW	Platteville, Wis.	1000	
WKIT	Minneapolis, Minn.	250	WFRL	Freeport, Ill.	1000	KNIM	Marville, Mo.	250	WTRW	Two Rivers, Wis.	1000	
KOMA	Okla. City, Okla.	50000	WBBE	Harvey, Ill.	1000	WCRM	Washington, N.J.	500	1600—187.5			
KGON	Oregon City, Oreg.	10000	WTAY	Robinson, Ill.	250	KHAM	Albuquerque, N.Mex.	1000	CHVC	Niagara Falls, Ont.	5000	
WWWV	Rio Piedras, P.R.	250	WILF	Frankfort, Ind.	250	WPAC	Patuxent, N.C.	250	WAPX	Montgomery, Ala.	1000	
1530—196.1												
KFBK	Sacramento, Calif.	50000	WLAW	Kendallville, Ind.	250	ZKYK	Albemarle, N.C.	250	KGST	Fresno, Calif.	1000	
WCKY	Cincinnati, Ohio	50000	WLRP	New Albany, Ind.	1000	WTKN	Tryon, N.C.	250	KWOW	Pomona, Calif.	1000	
KGBT	Harlingen, Tex.	50000	KMCD	Fairfield, Iowa	250	WKVO	Columbus, Ohio	1000	KUBA	Yuba City, Calif.	1000	
1540—195.0												
ZNS	Nassau, B.W.I.	5000	KJFJ	Wester City, Iowa	250	KLTR	Blackwell, Okla.	500	KAK	Lakewood, Colo.	1000	
KPOL	Los Angeles, Calif.	10000	KWSK	Pratt, Kans.	250	WCOY	Columbia, Pa.	250	WKEN	Dover, Del.	500	
WSMI	Litchfield, Ill.	1000	WABL	Amita, La.	500	WYCL	York, S.C.	1000	KXTN	Atlantic Beach, Fla.	1000	
WBNI	Boonville, Ind.	250	KLLA	Leesville, La.	250	WWSR	Manchester, Tenn.	250	WKWF	Key West, Fla.	500	
WLOI	LaPorte, Ind.	250	KMAR	Winnsboro, La.	500	TUC	Union City, Tenn.	250	WGKA	Atlanta, Ga.	1000	
KXEL	Waterloo, Iowa	50000	WAQE	Towson, Md.	1000	KGAF	Gainesville, Tex.	250	WMCW	Harvard, Ill.	500	
KXEX	McPherson, Kans.	250	WFPE	Taunton, Mass.	1000	KWEL	Midland, Tex.	1000	WBTO	Linton, Ind.	1000	
KLKC	Parsons, Kans.	250	WDEW	Wasson, Mass.	1000	KIRT	Mission, Tex.	500	WARU	Peru, Ind.	1000	
WDON	Wheaton, Md.	250	WRRP	Flint, Mich.	1000	KTLU	Rusk, Tex.	1000	KLGA	Algonia, Iowa	5000	
WPTA	Albany, N.Y.	50000	WFUR	Grand Rap., Mich.	1000	KWED	Seguin, Tex.	1000	KCRG	Cedar Rapids, Iowa	5000	
WFM	Elkin, N.C.	1000	KMRS	Morris, Minn.	1000	KEVA	Shamrock, Tex.	500	KMDO	Ft. Scott, Kans.	500	
WIMO	Cleveland, Ohio	1000	KAGE	Winona, Minn.	1000	WLD	Danville, Va.	5000	WNES	Central City, Ky.	500	
WIMJ	Philadelphia, Pa.	1000	KLEX	Lexington, Mo.	250	WPUV	Pulaski, Va.	5000	WSTL	Eminence, Ky.	500	
WPTS	Pittston, Pa.	1000	WFLR	Dundee, N.Y.	250	WTTN	Watertown, Wis.	250	KFNV	Ferriday, La.	1000	
WFMC	Punxsutawney, Pa.	1000	WBUZ	Fredonia, N.Y.	250	1590—188.7			KLFT	Golden Meadow, La.	1000	
WADK	Newport, R.I.	1000	WNCJ	Silar City, N.C.	1000	WATM	Altmore, Ala.	1000	KLVI	Vivian, La.	1000	
KULF	Ft. Worth, Tex.	10000	WHOT	Campbell, Ohio	250	KPBA	Pine Bluff, Ark.	1000	WBOB	Brookline, Md.	1000	
KGBC	Galveston, Tex.	1000	WCLW	Mansfield, Ohio	250	KSJO	San Jose, Calif.	1000	WTYM	E. Longmeadow, Mass.	5000	
KIWW	San Antonio, Tex.	1000	WPTW	Piqua, Ohio	250	KUOJ	Ventura, Calif.	1000	WHRU	Ann Arbor, Mich.	1000	
WTKM	Hartford, Wis.	500	KTAT	Frederick, Okla.	1000	KWUJ	Wentworth, Conn.	5000	WTRV	Muskogee, Mich.	5000	
1550—193.5												
CBE	Windsor, Ont.	10000	KOLS	Pryor, Okla.	1000	WBRV	Waterbury, Conn.	5000	WKDL	Clarksdale, Miss.	1000	
WAAY	Huntsville, Ala.	5000	KRWK	Forest Grove, Oreg.	1000	WILZ	St. Petersburg Beach, Fla.	1000	KATZ	St. Louis, Mo.	5000	
KOBY	San Fran., Calif.	10000	KOHU	Hermiston, Oreg.	250	WALB	Albany, Ga.	1000	KTTN	Trantam, Mo.	500	
KRENT	Shreveport, La.	1000	WBUJ	Doylstown, Pa.	250	WLFV	Lafayette, Ga.	1000	WONG	Owensboro, Ky.	1000	
KES	St. Joseph, Mo.	1000	WAKU	Latrobe, Pa.	1000	WNMP	Evansville, Ill.	5000	WWRW	Woodside, N.Y.	5000	
WLOA	Bradock, Pa.	1000	WMLP	Milton, Pa.	1000	WQUB	Gainesburg, Ill.	5000	WVFC	Charlotte, N.C.	1000	
WBSC	Bonnetsville, S.C.	10000	WFGN	Gaffney, S.C.	1000	WGEI	Indianapolis, Ind.	5000	WIDU	Fayetteville, N.C.	1000	
1560—192.3												
CFRS	Simco, Ont.	250	WHLF	Centerville, Tenn.	1000	WGPC	Mt. Vernon, Ind.	1000	WFRB	Reidsville, N.C.	1000	
KPMC	Bakersfield, Calif.	10000	WCLE	Cleveland, Tenn.	1000	WKBG	Boone, Iowa	5000	WFLC	Springfield, Ohio	1000	
1570—191.1												
1580—189.2												
1590—188.7												
1600—187.5												

Mexico

Amplitude-Modulation (AM) Stations Reported Heard in Parts of the Southwestern U. S.
Listed Alphabetically by Location

Abbreviations: C.L., call letters; Kc., frequency in kilocycles; W.P., watt power

Location	C.L.	Kc.	W.P.	Location	C.L.	Kc.	W.P.	Location	C.L.	Kc.	W.P.	Location	C.L.	Kc.	W.P.	
BAJA CALIFORNIA																
Ensenada	XEPF	1400	250		XEP	1300	500					Cananea	XEFQ	980	500	
Mexicali	XED	1050	5000		XEFV	1240	250		XEOY	1000	10000	Ciudad Dregon				
	XEAA	1340	250		XELO	800	150000		XEPH	590	5000	Hermosillo	XEOX	1340	1000	
	XEAD	910	250		XEWG	1490	250		XEQB	1110	5000		XEBJ	920	5000	
	XEGL	990	5000	Hidalgo	XEYC	1460	1000		XEQK	1350	1000		XEDL	1250	500	
	XEC	1310	250	N. Casas Grandes	XEJS	1550	500		XEQR	1030	2000		XEDM	1580	50000	
	XEAC	690	5000		XETX	1400	250		XEQS	790	1000		XEHQ	590	500	
	XEAU	1470	5000	COAHUILA					XERH	1500	5000	Magdal	XEDJ	1450	100	
	XEAZ	1270	500	Monselva	XEMF	1260	250		XESM	1470	5000	Naco	XETM	1350	1000	
	XEBG	1550	1000	Piedras Negras	XEMJ	920	1000		XEUN	960	5000	Nobales	XEHF	1370	1000	
	XEGM	950	2500		XEMK	580	5000		DURANGO				San Luis	XECB	1450	250
	XEMO	850	5000	Sabinas	XEBK	1340	1000		XEDU	860	1000	Santa Ana	XEAB	1400	250	
	XEXX	1420	2000	Saltillo	XESJ	1250	500		NEW LEO							
CHIHUAHUA																
Chihuahua	XEM	1390	500	Valita Acuna	XEDH	1340	250		XER	1280	250	TAMAULIPAS				
	XEBU	620	1000		XERF	1570	50000		XEG	1050	1000000	Matamoros	XEO	970	1000	
	XEBW	1280	1000	DISTRITO FEDERAL					XEH	1420	1000		XEAM	1450	250	
	XEFI	1440	1000	Mexico City	XEL	1260	5000		XET	990	5000		XEMT	1340	250	
	XERA	1490	250		XEN	690	5000		XEAR	1080	1000	Nuevo Laredo	XEAS	1410	250	
CIUDAD CAMARGO																
Ciudad Camargo	XEHA	580	500		XEQ	940	50000		XEAH	1370	500		XEBK	1340	1000	
CIUDAD DELICIAS																
Ciudad Delicias	XEBN	1240	250		XEW	900	100000		XEDR	920	500		XEDF	790	1000	
	XEJK	1340	250		XEX	730	250000		XEF	830	5000		XEFE	960	1000	
CIUDAD JUAREZ																
Ciudad Juarez	XEF	1420	250		XEJR	1180	1000		XEGD	820	500		XERG	1090	250	
	XEJ	970	5000		XEJP	1150	1000		XEWA	540	150000		XEQO	1550	50000	
					XELA	830	1000		XEFH	1310	1000		XEOR	1390	1000	
					XELZ	1440	5000		SONORA					XERT	590	5000
					XEMX	1390	1000		Agua Prieta	XEAQ	1490	250				
										XEFH	1310	1000				

United States and Canadian

Amplitude-Modulation (AM) Broadcasting Stations Listed Alphabetically by Location
 Abbreviations: C.L., call letters; Kc., frequency in kilocycles; N.A., network affiliation—A: American Broadcasting Co., C: Columbia Broadcasting System, Inc.; M: Mutual Broadcasting System; N: National Broadcasting Co., Inc. (For watt power of station, see list arranged by Frequency, p. 169)

Location	C.L.	Kc.	N.A.	Location	C.L.	Kc.	N.A.	Location	C.L.	Kc.	N.A.	Location	C.L.	Kc.	N.A.
Abbeville, La.	KROF	960		Ann Arbor, Mich.	WHRY	1600	A	Bamberg, S.C.	WWIN	1400	A-M	Bisbee, Ariz.	KSUN	1230	M
Abbeville, S.C.	WABV	1590			WPAG	1050		Bangor, Maine	WBBD	790		Bishop, Calif.	KBS	1230	
Aberdeen, Md.	WAMD	970		Anna, Ill.	WRAJ	1440			WBDR	910	A-M	Bishopville, S.C.	WAGS	1380	
Aberdeen, Miss.	WMPA	1240		Anniston, Ala.	WANA	1490			WGUU	1230	M	Bismarck, N.Dak.	KFYR	950	N
Aberdeen, S.Dak.	KABR	1220			WDNG	1450	A	Banning, Calif.	WPBS	620	N	Bismarck-Mandan, N.Dak.	KNDK	1570	N
Aberdeen, Wash.	KSDN	930	A	Anoka, Minn.	WHMA	1390		Barboursville, Ky.	KPAS	1490		Blackfoot, Idaho	KBLI	690	
Abilene, Tex.	KXRO	1320	M	Ansonia, Conn.	KANO	1470		Bardestown, Ky.	WBVL	950		Blackstone, Va.	WKLY	1440	
	KRBC	1470	A	Antigo, Wis.	WATG	900		Barnesboro, Pa.	WNCC	950		Blackwell, Okla.	KLTR	1580	
	KNIT	1280		Artesia, N.M.	KSPV	990	M	Barrie, Ont.	WBWA	740		Blind River, Ont.	CJNR	730	
Abingdon, Va.	KWKC	1340	M	Antigonish, N.S.	CJFX	580		Barstow, Calif.	KWTC	1230	A	Bloomington, Ill.	WJBC	1230	A
Ada, Okla.	KADA	1230	A	Apple, Pa.	WAVL	910		Bartlesville, Okla.	KWON	1400	M	Bloomington, Ind.	WTTS	1370	A
Adel, Ga.	WAAG	1470		Apple Valley, Cal.	KAYR	960		Bartow, Fla.	WBAR	1460		Bloomsburg, Pa.	WHLM	1550	
Adrian, Mich.	WABJ	1490	A	Appleton, Wis.	WAPL	1570		Bastrop, La.	KTRY	730		Bluefield, W.Va.	WHIS	1440	N
Agana, Guam	KUAM	610	N	Areadia, Fla.	WHBY	1250	M	Batavia, N.Y.	KBAN	1340		Blythe, Calif.	KYOR	1240	M
Aguadilla, P.R.	WABA	850		Areadia, Calif.	KENL	1480		Batesburg, S.C.	WBAT	1430		Blytheville, Ark.	KLCN	910	N
	WGRF	1340		Ardenmore, Okla.	KVSO	1240	A	Batesville, Ark.	KBTA	1340		Bogalusa, La.	WKIC	940	N
Ahoskie, N.C.	WRCS	970		Arecibo, P.R.	WCMN	1280		Bath, Maine	WMMS	730		Boise, Idaho	KBDI	920	M
Aiken, S.C.	WAKN	990			WMIA	1070		Bathurst, N.B.	CKBC	1400			KGEM	1140	M
Akron, Ohio	WAKR	1590	A	Arkadelphia, Ark.	KVRC	1240	M	Baton Rouge, La.	WAIL	1460	M		KJDD	630	N
	WADK	1350	C	Arkansas City, Kans.	KSDK	1280			WEND	1390		Bonham, Tex.	KFYN	1420	
	WCUE	1150	C	Arlington, Va.	WARL	780			WELR	1300		Boone, Iowa	KFGQ	1260	
	WHKC	640	M		WEAM	730			WJBO	1150			WBG	590	
Alamogordo, N.M.	KALG	1230	M	Artesia, N.M.	KSPV	990	M		WJCS	910		Boone, N.C.	WATA	1450	
	KRAC	1270		Asbury Park, N.J.	WLJK	1310		Battle Creek, Mich.	WXOK	1260		Boonville, Ind.	WBNL	1540	
Alamosa, Colo.	KGIW	1450	M	Asheboro, N.C.	WGWV	1260			WBCK	930	A	Boonville, Mo.	KWRT	1370	
Albany, Ga.	WALB	1590	A	Asheville, N.C.	WISE	1150	M-A	Baxley, Ga.	WELL	1400	A	Booneville, Miss.	WBIP	1400	
	WGPC	1450	C		WLOS	1380	N-M	Bay City, Mich.	WBGM	1440	A	Boonville, N.Y.	WBRY	900	
	WJAZ	1050		Ashland, Ky.	WWSKY	1230		Bay City, Tex.	WBCB	1250	A	Borger, Tex.	KHJZ	490	M
Albany, Minn.	KASM	1150			WCMJ	1340	C	Bay Minette, Ala.	KIOX	1270	M	Bossier City, La.	WBZ	1050	
Albany, N.Y.	WABY	1400		Ashland, Ohio	WTRC	1420		Baytown, Tex.	WBKA	1150		Boston, Mass.	WCOP	1150	
	WKOK	1460	M	Ashland, Ohio	WATG	1340		Beatrice, Neb.	KWBE	1450			WILD	1090	
	WPTR	1540	A	Ashland, Ohio	KWIN	1400	M	Beaufort, N.C.	WBMA	1400			WNAK	680	N
Albany, N.Y.	WRDW	590	C	Ashland, Ohio	WATN	1400	M	Beaufort, N.C.	WBMA	1400			WEZE	1260	N
Albany, N.Y.	WKWL	790	M	Ashland, Ohio	WATN	1400	M	Beaufort, S.C.	WBEU	960			WHDH	590	C
Albemarle, N.C.	WABZ	1010	M	Ashland, Ohio	WATN	1400	M	Beaufort, S.C.	WBEU	960			WMEX	1510	
	WZKY	1580		Ashland, Ohio	WATN	1400	M	Beaumont, Tex.	KJED	1380			WORI	950	
Albert Lea, Minn.	KATE	1450	A	Ashland, Ohio	WATN	1400	M		KRIC	1450		Boulder, Colo.	KBOL	1490	
Albertville, Ala.	WAYU	630		Ashland, Ohio	WATN	1400	M		KTRM	990		Bowling Green, Ky.	WKCT	930	A
Albion, Mich.	WALM	1260		Ashland, Ohio	WATN	1400	M	Beaver Dam, Wis.	WBVE	1430			WBLJ	1430	M
Albuquerque, N.M.	KABQ	1340		Ashland, Ohio	WATN	1400	M	Beaver Falls, Pa.	WBVP	1230		Bowl Green, Ohio	WTLG	730	
	KDEF	1150	C	Ashland, Ohio	WATN	1400	M	Beckley, W. Va.	WJLS	560	C	Bozeman, Mont.	KXKL	1450	N
	KGGM	610	C	Ashland, Ohio	WATN	1400	M		WWRN	620			KBML	1230	
	KOB	1030	N	Ashland, Ohio	WATN	1400	M	Bedford, Ind.	WBW	1340		Bradbury Hgts., Md.	WPGC	1580	
	KQUE	920	M	Ashland, Ohio	WATN	1400	M	Bedford, Pa.	WBZ	1310		Braddock, Pa.	WLDA	1550	
	KLOS	1450		Ashland, Ohio	WATN	1400	M	Bedford, Va.	WBET	1350		Bradenton, Fla.	WTRJ	1490	M
	KHAM	1580	A	Ashland, Ohio	WATN	1400	M	Beville, Tex.	KIBL	1490		Bradford, Pa.	WBES	1490	M
	WEAG	1470		Ashland, Ohio	WATN	1400	M	Bellefontaine, Ohio	WTRX	1290	M	Brady, Tex.	KNEL	1490	
Alcoa, Tenn.	WRFS	1050		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WDHP	1390		Brainerd, Minn.	KLIZ	1390	
Alexander City, Ala.	WKALB	580	A	Ashland, Ohio	WATN	1400	M	Belle Glade, Fla.	WSWN	900		Brampton, Ont.	CFJB	1090	
	KDBS	1410		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	KJCB	900		Brandon, Man.	CKX	1150	
	KSYL	970	N	Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Branson, Mo.	KBHM	1220	
Alexandria, La.	KXRA	1490	A	Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Brattleboro, Vt.	CKPC	1380	
Alexandria, Minn.	KXRA	1490	A	Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Brawley, Calif.	KROP	1300	A
Alexandria, Va.	KLGA	1600		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Breckenridge, Minn.	KBMW	1450	
Alfalfa, Tex.	KOPY	1070		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Breckenridge, Tex.	KSTB	1430	
Allentown, Pa.	WHOL	600		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Bremen, Ga.	WWCC	1440	
	WAEB	790		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Bremerton, Wash.	KBRD	1490	
	WKAP	1320		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Brenham, Tex.	WBH	1490	M
Alliance, Nebr.	WSAN	1470	C	Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Brevard, N.C.	WPNF	1240	M-N
Alliance, Ohio	WFAH	1310		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Brewton, Ala.	WEBJ	1240	M
Alma, Ga.	WCOS	1400		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Bridgeport, Conn.	WICC	600	M
Alma, Mich.	WFCY	1280		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Bridgeport, N.J.	WNAH	1450	A
Alpena Township, Mich.	WATZ	1450		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Bridgewater, N.S.	CKBW	1200	
Alpine, Tex.	KVLF	1450	M	Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Brighton, Colo.	KHIL	800	
Alton, Ill.	WDKZ	1570		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Bristol, Conn.	WBIS	1440	
Altona, Man.	CFAM	1050		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Bristol, Tenn.	WQPI	1490	N
Altoona, Pa.	WFBG	1340	N	Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Bristol, Va.	WCYB	690	A
	WRTA	1240	A	Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Brockton, Mass.	WFHG	980	M
	WVAM	1430	C	Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Brockville, Ont.	WBET	1460	
Alturas, Calif.	KCND	570		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Broken Bow, Nebr.	KCNJ	1280	
Altus, Okla.	KWHW	1450		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Brookfield, Mo.	KGHM	1470	
Alva, Okla.	KALY	1430		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Brookhaven, Miss.	WCHJ	1470	
Amarillo, Tex.	KAMQ	1010	M	Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Brookline, Mass.	WBRS	1490	M
	KFDA	1440	A	Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Brooklyn, N.Y.	WPDU	1330	
	KGNC	710	N	Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Brooksville, Fla.	WFTS	1450	
	KLYN	940	C	Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Brownfield, Tex.	KTY	1350	
	KRAY	1360		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Brownsville, Tex.	KBOR	1600	A
Americus, Ga.	KZIP	1310		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Brownwood, Tex.	KBWD	1380	M
Ames, Iowa	WDCS	1290		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260			KEAN	1240	
	KSAL	1430		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Brunswick, Ga.	WGIG	1440	A
	WDI	640		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Brunswick, Maine	WCME	900	
Amherst, N.S.	CKDH	1400		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Bryan, Tex.	KORA	1240	M
Amite, La.	WABL	1570		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260			WTAW	1150	
Amory, Miss.	WAMY	1580		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260		Buffalo, N.Y.	WBEN	930	C
Amos, Que.	CHAD	1340		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260			WBNY	1400	
Amsterdam, N.Y.	WCSS	1490		Ashland, Ohio	WATN	1400	M	Bellefonte, Pa.	WJLS	1260			WEBR	970	M
Anaconda, Mont.	KANA	1230		Ashland, Ohio	WATN	1400	M	B							

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.
Du Bois, Pa.	WXLI 1440	Lucas, Mo.	KIEM 1490 M	Fosteria, Ohio	WBAP 820 N	Grand Rapids, Mich.	WJEF 1230 C
Dubuque, Iowa	WCED 1420 C	Eustin, Fla.	WLCO 1240	Fountain Inn, S.C.	WXOL 1360		WFUR 1570
Duluth, Minn.	KOTH 1430 A	Evanson, Ill.	WEAW 1330	Framingham, Mass.	WFOB 1430		WGLR 1410
	WBQO 1490 M		WNMP 1580	Frankfort, Ind.	WFOJ 1190		WLAG 1340 A
	KDAL 810 C	Evansville, Ind.	WKLU 1240	Frankfort, Ky.	WFKY 1490 M		WMOX 1480
	WEBC 560 N		WEOA 1400 C	Franklin, Ky.	WFKN 1220	Grand Rapids, Minn.	WMAA 1300 N
Dumas, Tex.	WREX 1080		WGBF 1280 N	Franklin, N.C.	WF5G 1050		KOZY 1490 M
Ouncan, Okla.	KODD 800	Eveleth, Minn.	WIKY 820	Franklin, Tenn.	WAGG 950	Grangeville, Idaho	KORT 1230
Dundaik, Md.	KRHO 1350 M	Everett, Wash.	WJPS 1330 A	Franklin, Va.	WYSR 1250	Grants, N.Mex.	KMIN 980
	WAYE 860	Evergreen, Ala.	WEVE 1340 M	Frederick, Md.	WFMD 930 C	Grants Pass, Oreg.	KUIN 1340 M
Dundee, N.Y.	WEBS 1350	Fairbanks, Alaska	KRKO 1380	Frederick, Okla.	KTAT 1570		KAJO 1270
Dunkirk, N.Y.	WFCB 870		WBLO 1470	Fredericksburg, Tex.		Gravelbourg, Sask.	CFGR 1230
Dunn, N.C.	WDOE 1410		KFAR 660 A-M-N		KNAF 1340 M		CFRR 710
Du Quoin, Ill.	WCKB 780	Fairfax, Va.	KFRB 900 C-A	Fredericksburg, Va.	WVFA 1230	Gt. Barrington, Mass.	WSBS 860
Durango, Colo.	WDQN 1580	Fairfield, Ill.	WFCR 1310	Fredericton, N.B.	CFNB 550	Gt. Bend, Kans.	KVGB 1590 N
	KIUP 930	Fairfield, Iowa	WF1W 1390	Fredonia, N.Y.	WBLZ 1570	Gt. Falls, Mont.	KFBB 1310 C
	KOGO 1240	Fairfield, Minn.	KMCD 1370	Freeport, Ill.	WFUR 1570		KYGB 1590 N
Durant, Okla.	KSE0 720	Fairmont, N.C.	WFMO 860	Freeport, N.Y.	WGBB 1240		KFBB 1310 C
Ourham, N.C.	WONC 650	Fairmont, W.Va.	WMNN 920 C	Freeport, Tex.	KBRZ 1460		KUDI 1450
	WSRC 820	Fajardo, P.R.	WTCS 1490 A	Freeport, N.Y.	WFBC 1490		KMON 560 M
	WSSB 1410	Falfurrias, Tex.	WMDO 1430	Freeport, N.Y.	KFBF 950		KXK 1400 N
Dyersburg, Tenn.	WTIK 1310 A	Fallon, Nev.	WKUL 1260	Fremont, Mich.	KFR 1340	Greeley, Colo.	KFKA 1310
	WDSG 1450	Fall River, Mass.	WSAR 480	Fremont, Ohio	WFRO 900		KYOU 1450
	WTRO 1330	Falls Church, Va.	WFAX 1220	Fresno, Calif.	KJRM 1430 A	Green Bay, Wis.	WBYA 1360 C
Eagle Pass, Tex.	KEPS 1270	Falls City, Nebr.	KTNC 1230		KBFJ 900		WJPG 1440
Eastley, S.C.	WEPS 1360	Fargo, N.Dak.	WOAY 970 N		KEAP 980		WDUJ 1400 A
Eastland, Tex.	KERC 1390		KFNW 900		KFRE 940 C	Greensboro, N.C.	WGTG 1590 M
E. Lansing, Mich.	WKAR 870	Faribault, Minn.	KFGO 790 A		KGST 1800		WBIG 1470 C
E. Liverpool, Ohio	WOHI 1490 A	Farmington, Mo.	KOHL 920		KMAK 1340		WCOG 1320 A
East Longmeadow, Mass.		Farmington, N.M.	KVBC 1350		KMY 980 N		WGBG 1400 M
	WTYM 1600	Farmville, Va.	KWYK 960		KYNO 1450 M		WPET 950
	WTJH 1260	Farrell, Pa.	WFLO 870		KYTR 1300	Greensburg, Pa.	WHJB 620
E. St. Louis, Ill.	WAMV 1490 M	Fayette, Ala.	WVWF 970		KWOC 1300	Greenville, Ala.	WGYV 1380
Easton, Pa.	WEX 1230	Fayetteville, Ark.	KHOG 1450		KWOC 1300	Greenville, Miss.	WDDY 900
	WEEX 1230	Fayetteville, N.C.	WFAI 1230 C		KWOC 1300		WDDY 900
Eastontown, N.J.	WHTG 1410		WFNC 1390 M		KWOC 1300	Greenville, N.C.	WGTG 1590 M
Eau Claire, Wis.	WEAU 790 N		WFLB 1480 A		KWOC 1300	Greenville, S.C.	WESC 660
	WBIZ 1400 M	Fayetteville, Tenn.	WEKR 1240 M		KWOC 1300		WMBR 1490 A-M
	WECL 1050				KWOC 1300		WMLU 1260
Eau Gallie, Fla.	WMEG 820	Fergus Falls, Minn.	KGDE 1250 M		KWOC 1300		WMLU 1260
Easton, N.C.	WC0J 1260	Fernandina Beach, Fla.	KGDE 1250 M		KWOC 1300		WMLU 1260
Edinburg, Tex.	KURV 710		KFBF 1570		KWOC 1300		WMLU 1260
Edmonds, Wash.	KGDN 630	Ferriday, La.	KFNV 1600		KWOC 1300		WMLU 1260
Edmonton, Alta.	CBX 1010	Festus, Mo.	KJCF 1010		KWOC 1300		WMLU 1260
	CBXA 740	Findlay, Ohio	WF1N 1330		KWOC 1300		WMLU 1260
	CFRN 1280	Fisher, W.Va.	WE1M 1280		KWOC 1300		WMLU 1260
	CHEO 1080	Fitchburg, Mass.	WFGM 1580		KWOC 1300		WMLU 1260
	CHEA 860	Fitzgerald, Ga.	WBHB 1240 M		KWOC 1300		WMLU 1260
	CHEB 930	Flagstaff, Ariz.	KCLS 600 N		KWOC 1300		WMLU 1260
	CKUA 580	Flat River, Mo.	KFMO 1240 M		KWOC 1300		WMLU 1260
Edmundston, N.C.	CJEM 570	Flint, Mich.	WBBB 1330 M		KWOC 1300		WMLU 1260
Emmhamg, Ill.	WCRA 1090		WAMM 1420		KWOC 1300		WMLU 1260
Elberton, Ga.	WSGC 1400		WMRP 1570		KWOC 1300		WMLU 1260
El Cajon, Calif.	KBAB 910 A		WKMF 1470		KWOC 1300		WMLU 1260
El Campo, Tex.	KULP 1390	Flomata, Ala.	WTCB 900		KWOC 1300		WMLU 1260
El Centro, Calif.	KULP 1390	Florence, Ala.	WJBR 1340 M		KWOC 1300		WMLU 1260
El Dorado, Ark.	KOMS 1290	Florence, S.C.	WJMX 970 A		KWOC 1300		WMLU 1260
	KELD 1400 A		WOLS 1230		KWOC 1300		WMLU 1260
Eldorado, Kans.	KBTO 1360	Floydada, Tex.	WFLD 900		KWOC 1300		WMLU 1260
Elgin, Ill.	WRMN 1410	Foley, Ala.	WHEP 1310		KWOC 1300		WMLU 1260
Elizabeth City, N.C.	WCNC 1240	Fond du Lac, Wis.	KF1Z 1450 M		KWOC 1300		WMLU 1260
	WGA1 560	Forest, Wis.	WMM 880		KWOC 1300		WMLU 1260
Elizabethton, Tenn.	WBEJ 1240	Forest City, N.C.	WRBO 780		KWOC 1300		WMLU 1260
Elizabethtown, Ky.	WIEL 1400	Forest Grove, Oreg.	KBBG 1570		KWOC 1300		WMLU 1260
Elizabethton, N.C.		Forest City, Ark.	KXJK 950		KWOC 1300		WMLU 1260
	WBLA 1450 M	Ft. Bragg, Calif.	KDAC 1230		KWOC 1300		WMLU 1260
	KASA 1240 A	Ft. Collins, Colo.	KCOL 1410		KWOC 1300		WMLU 1260
	WTR 1340 N	Ft. Dodge, Iowa	KVFD 1400 M		KWOC 1300		WMLU 1260
	WCMR 1430 N	Ft. Frances, Ont.	KWMT 540 A		KWOC 1300		WMLU 1260
Elkin, N.C.	W1FM 1540	Ft. Lauderdale, Fla.	CF0B 800		KWOC 1300		WMLU 1260
Elkins, W.Va.	WDNE 1240		WFTL 1400		KWOC 1300		WMLU 1260
Elko, Nev.	KELK 1240 M		WW1L 1580		KWOC 1300		WMLU 1260
Ellensburg, Wash.	KXLE 1240	Ft. Lupton, Colo.	KH1L 900		KWOC 1300		WMLU 1260
Elmira, N.Y.	WELM 1400 A-C	Ft. Madison, Iowa	KXGI 1380		KWOC 1300		WMLU 1260
Elmira Heights, Horseheads, N.Y.	WENY 1230 N	Ft. Morgan, Colo.	KFTM 1400		KWOC 1300		WMLU 1260
	WEHH 1590 A	Ft. Myers, Fla.	WMYR 1410		KWOC 1300		WMLU 1260
El Paso, Tex.	KROD 600 C	Ft. Payne, Ala.	WVPA 1400		KWOC 1300		WMLU 1260
	KELP 920		WZOB 1250		KWOC 1300		WMLU 1260
	KHEY 690	Ft. Pierce, Fla.	WARR 1330		KWOC 1300		WMLU 1260
	KST 1340 M		W1RA 1400		KWOC 1300		WMLU 1260
	KTSN 1380 N	Ft. Scott, Idaho	KMDD 1600		KWOC 1300		WMLU 1260
Ely, Minn.	WELY 1450	Ft. Smith, Ark.	KFPW 1230 C		KWOC 1300		WMLU 1260
Ely, Nev.	KELY 1230		KFS 950		KWOC 1300		WMLU 1260
Elyria, Ohio	WEOL 930		KTCS 1410 M		KWOC 1300		WMLU 1260
Eminece, Ky.	WSTL 1600	Ft. Stockton, Tex.	KFTS 860		KWOC 1300		WMLU 1260
Emporia, Kans.	KV0E 1400	Ft. Valley, Ga.	WFPM 1150		KWOC 1300		WMLU 1260
Emporia, Mo.	WCLV 860	Ft. Walton, Fla.	WFTW 1260		KWOC 1300		WMLU 1260
Emporium, Pa.	WLEM 2500	Ft. Walton Beach, Fla.	WFTW 1260		KWOC 1300		WMLU 1260
Endicott, N.Y.	WENE 1430		WFB5 950		KWOC 1300		WMLU 1260
Englewood, Colo.	KGMC 1150	Ft. Wayne, Ind.	WGL 1250 A		KWOC 1300		WMLU 1260
Enid, Okla.	KCRC 1390 A		WOWO 1190		KWOC 1300		WMLU 1260
	KGWA 980 M		WANE 1450 C		KWOC 1300		WMLU 1260
Enterprise, Ala.	W1RB 1230		WKJG 1390 N		KWOC 1300		WMLU 1260
Ephrata, Pa.	W5GA 1310	Ft. William, Ont.	CKPR 580		KWOC 1300		WMLU 1260
Ephrata, Wash.	W5FA 730	Ft. Worth, Tex.	KJ1M 870		KWOC 1300		WMLU 1260
Erie, Pa.	WERC 1260		KCUL 1540		KWOC 1300		WMLU 1260
	W1CU 1330 N		KFJZ 1270		KWOC 1300		WMLU 1260
	WJET 1400		KN0K 970		KWOC 1300		WMLU 1260
	WLEU 1450		WBAP 570 A		KWOC 1300		WMLU 1260
Erwin, Tenn.	WEMB 1420				KWOC 1300		WMLU 1260
Escanaba, Mich.	WDBC 680 M				KWOC 1300		WMLU 1260
Estherville, Iowa	KL1L 1340				KWOC 1300		WMLU 1260
Etowah, Tenn.	WCPH 1220				KWOC 1300		WMLU 1260
Eufaula, Ala.	WULA 1240 M				KWOC 1300		WMLU 1260
Eugene, Oreg.	KDRE 1450 M				KWOC 1300		WMLU 1260
	KASH 1600 A				KWOC 1300		WMLU 1260
	KERG 1280 C				KWOC 1300		WMLU 1260
	KUGN 590 N				KWOC 1300		WMLU 1260
Eunice, La.	KEUN 1490 M				KWOC 1300		WMLU 1260
Eureka, Calif.	KINS 980 C				KWOC 1300		WMLU 1260
	KDAN 790				KWOC 1300		WMLU 1260

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.
Havre, Mont.	KOJM 610 M	Indianola, Miss.	WIRE 1430 N	Killeen, Tex.	KLEN 1050 M	LaMars, Iowa	KLEM 1410
Havre de Grace, Md.	WASA 1330	Indio, Calif.	WISH 1310 C	Kingsman, Ariz.	KAAA 1230	Lenoir, N.C.	WJRI 1340 M
Hawkinsville, Ga.	WCEH 610	Inglwood, Calif.	WXLW 950	Kings Mountain, N.C.	WKMT 1220	Leoardtown, Md.	WKIK 1370
Haynesville, La.	KLUV 1580	Inkster, Mich.	WCHB 1440	Kingsport, Tenn.	WKIN 1230	Lehrbach, Alta.	CJOC 1220
Hayes, Kans.	KAYS 1400	Ionia, Mich.	WION 1430	Kingston, N.Y.	WKPT 1400 N	Levelland, Tex.	KLVT 1230
Hayward, Wis.	WHSM 910	Iowa City, Iowa	WKIC 800	Kingston, Ont.	WKNY 1490 M	Levittown, Pa.	WBCB 1490
Hazard, Ky.	WKIC 1430 M	Iron Min., Mich.	WMIQ 1450 A	Kingstree, S.C.	CFRC 490	Levittown, Pa.	WITF 110
Hazlehurst, Miss.	WMDC 1220	Iron River, Mich.	WIKB 1230 M	Kingston, N.C.	CKRS 1380	Levittown, Pa.	WJLM 1490 M
Helena, Ark.	AZL 490 N-M	Ironton, Ohio	WIRO 1230 M	Kingston, N.C.	CKWS 960	Lewiston, Idaho	KRLC 1350 M
Helena, Mont.	KCAP 1340 M	Iroquois, Mich.	WJMS 630 M	Kirkland, Wash.	WKD 1310	Lewiston, Maine	KOZE 1300
Hempstead, N.Y.	WHLI 1100	Ishpeming, Mich.	WJPD 1240	Kirkland Lake, Ont.	WSPF 1230 M	Lewiston, Mont.	WCOU 1240 M
Hempstead, Ky.	KBMI 1400	Ithaca, N.Y.	WHCU 1470	Kirksville, Mo.	KNBX 1050	Lewistown, Pa.	WKXA 920
Henderson, Nev.	KTDO 890 M	Jackson, Ala.	WPBB 1290 M	Kittanning, Pa.	KJLK 560	Lexington, Ky.	WLAP 630 A
Henderson, N.C.	WHVH 1450	Jackson, Mich.	WIBM 1450 A	Kittanning, Pa.	KIRX 1450 A		WVLY 1300
Henderson, Tex.	KGRI 1000	Jackson, Miss.	WKHM 970 M	Kittanning, Pa.	KCRK 1490	Lexington, Mo.	KLEX 590 M
Hendersonville, N.C.	KWRD 1470	Jackson, Miss.	WJDS 620 N	Kittanning, Pa.	WRWB 1220	Lexington, Nebr.	KRVN 1010
	WHPK 1450 A	Jackson, Miss.	WJQS 1400 C	Kittanning, Pa.	WACB 1380	Lexington, N.C.	WBUY 1440
Henryetta, Okla.	KHEN 1590	Jackson, Miss.	WJNS 1450	Klamath Falls, Ore.	WACB 1380	Lexington, Tenn.	WDXL 1490
Hereford, Tex.	KFRN 860	Jackson, Miss.	WJKI 1590		KFLJ 1150 M	Lexington, Va.	WREL 1450
Herkimer, N.Y.	WALY 1420	Jackson, Miss.	WRBC 1300 M		KFLW 1450 A-C	Lexington Park, Md.	WPTX 920
Hermiston, Ore.	KOHU 1570	Jackson, Miss.	WLSI 980		KLAD 900	Libby, Mont.	KLCC 1230 M
Herrin, Ill.	WJPF 1340 M	Jackson, Miss.	WLMJ 1280		WBIR 2140 A	Liberal, Kans.	KSCB 1270
Hettinger, N.Dak.	KNDC 1490	Jackson, Miss.	WDXI 1310		WIVK 860	Liberty, N.Y.	WYOS 1240
Hibbing, Minn.	WMFG 1240 N	Jackson, Miss.	WJAK 1460		WATE 620 N	Lihue, T.H.	KTOH 1490
Hickory, N.C.	WHKY 1290 A	Jacksonville, Fla.	WTIS 1390 A		WKGK 1340 M	Lima, Ohio	WIMA 1150 A
	WIRC 630	Jacksonville, Fla.	WZOK 1320 A		WKXY 900	Lincoln, Ill.	WPRC 1370
High Point, N.C.	WNOS 1590	Jacksonville, Fla.	WVIV 1050		WWSR 950 C	Lincoln, Nebr.	KFOR 1240 A
	WHPE 1070	Jacksonville, Fla.	WMBR 1460 C		WIOU 1350 C		KLIN 1400
Hillsboro, Ohio	WSRW 1590	Jacksonville, Fla.	WOBBS 1360		WKOS 1350	Lincolnton, N.C.	KLWS 1490
Hillsboro, Ore.	KUIK 1360	Jacksonville, Fla.	WPDQ 600		WLNH 1410	Lindsay, Ont.	WLOW 1050
Hillsboro, Tex.	KHBR 1560	Jacksonville, Fla.	WQIK 1280		WKBH 1350 N	Linton, Ind.	WBTO 1600
Hillsdale, Mich.	WBSE 1340	Jacksonville, Ill.	WLDI 1180		WLXC 1490 A	Litchfield, Ill.	WSMI 1540
Hilo, Hawaii	KIPA 1110 C	Jacksonville, N.C.	WJNC 1240 M		WKTY 580 A	Little Falls, Minn.	KLTF 960
	KILA 850 M	Jacksonville, N.C.	WLAS 910		WWSR 900	Little Falls, N.Y.	WLFF 1280
Hobart, Okla.	KTJS 1420	Jacksonville, Tex.	KEBE 1400		WBAA 920 A	Littlefield, Tex.	KYOW 1490
Hobbs, N.Mex.	KWEW 1480 M	Jacksonville Beh., Fla.	WZRO 1010		KPEL 1420 A	Little Rock, Ark.	KARK 920 N
	KHDB 1280	Jamestown, N.Dak.	KEYJ 1400 M		KVOL 1330 N		KGHI 910 M
Holbrook, Ariz.	KDJI 1270	Jamestown, N.Dak.	KKJB 690 A		WFLA 1430		KLR 1010 A
Holdrege, Nebr.	KFAN 1380	Jamestown, N.Y.	WJTN 1240 A		KLBM 1460		KOXY 1440
Holland, Mich.	WHTC 1450	Jamestown, N.Y.	WJOC 1340 M		WLAG 1240 M		KTHS 1090 C
	WJBL 1260	Jamestown, Tenn.	WCCL 1260		WTRP 620		KVLC 1050
Hollywood, Fla.	WGMA 1320	Jamestown, Tenn.	WCLO 1230 M		WTAQ 1300 M	Littleton, Colo.	KUDY 1510
Holyoke, Mass.	WREB 930	Jasper, Ala.	WWVB 1360		KBNZ 1400 M	Live Oak, Fla.	WNER 1250
Homel, La.	KVHL 1320	Jasper, Ala.	WARF 1240		KLOU 1580	Livingston, Mont.	KPRK 1340 M
Homestead, Fla.	WSDB 1430	Jasper, Ind.	WJIS 990		KADK 1400 N	Livingston, Tenn.	WLIV 920
Homestead, Pa.	WAMG 960	Jasper, Ind.	WLTK 1350		WWSR 1340 M	Livingston, Tex.	KXG 1440
Homewood, Ala.	WEZB 1820 M	Jefferson City, Mo.	KLIZ 950		WJOT 1260		KTET 1220
	WJLD 1400	Jennings, La.	KWOS 1240 M		WLAK 1430 M	Lloydminster, Alta.	CKSA 1150
Honolulu, Hawaii	KGMB 590 C	Jerome, Idaho	KJEF 1290		WONN 1230 M	Lock Haven, Pa.	WBZP 1230 M
	KHON 1380	Jerome, Idaho	KART 1400		WYSE 1350	Lockport, N.Y.	WUSJ 1340
	KIKI 850	Jesup, Ga.	WBGR 1370			Lodi, Calif.	KCVR 1570
	KGU 760 N	Johnson City, Tenn.	WIHL 910 C		KLPI 1030	Logan, Utah	KYNU 610 M
	KHYH 1040	Johnstown, Pa.	WETB 790 M		KQIK 1230	Logan, W.Va.	KLGN 1390
	KPOA 830 M	Johnstown, Pa.	WJAC 1400 N		WIPB 280		WVOW 1290
	KULA 890 A	Johnstown, Pa.	WARD 1490 C		KLAK 1400 M	Logansport, Ind.	WSAL 1230 M
Hood River, Oreg.	KIHR 1340	Joliet, Ill.	WCRO 1230 M		KLMR 920 M	London, Ky.	WFTG 1400
Hope, Ark.	KXAR 1490	Jonesboro, Ark.	KBTM 1250 C		KPES 690	London, Ont.	CFPL 980
Hopewell, Va.	WHAP 1340	Jonesville, La.	WJOL 1340		KCYL 1450		CKSL 1290
Hopkinsville, Ky.	WHOP 1280	Jonquiere, Que.	CKRS 590		KAVL 610	Long Beach, Calif.	KFOX 1280
	KQA 1480	Joplin, Mo.	WMBH 1450 M		KBYV 1380		KGER 1360
Hornell, N.Y.	WWHG 1320	Junction, Tex.	KODE 1230		WYHO 1320	Longmont, Colo.	KCI 1050
	WLEA 1480 M	Juneau, Alaska	KJNO 650 A-M-N		WLAN 1390 A-M	Longview, Tex.	KFRO 1370
Hot Springs, Ark.	KWFC 1350 A	Kailua, Hawaii	KANI 1240		WLCM 1360		KLTI 1280 A
	KBHS 590	Kaimuki, Hawaii	KAIM 870		KOVE 1330 M	Longview, Wash.	KWLK 1400 M
	KBLO 1470 M	Kalamazoo, Mich.	WKZO 590 C		WRLD 1490 A		KBAM 1220
Houghton, Mich.	WHDF 1400	KalisPELL, Mont.	KGEZ 600 M		WLSH 1430 A	Los Alamos, N.Mex.	KRSN 1490 A
Houghton Lake, Mich.	WHGR 1290	Kamloops, B.C.	KOFI 980		WLRD 1490 A	Los Angeles, Calif.	KABC 790 A
	WABM 1340	Kane, Pa.	CFJC 910		WLAN 1390 A-M		KFI 840 N
Houma, La.	KCIL 1490 N	Kankakee, Ill.	WKAN 1320		WLMC 1240 N		KHI 980 M
Houston, Miss.	WCPC 1320	Kannapolis, N.C.	WGTL 870		WMPC 1230 A		KFSG 1150
Houston, Tex.	KCOH 1430	Kans. City, Kans.	KCKN 810 C		WLOI 1540		KFWB 980
	KILT 910	Kansas City, Mo.	KCMO 810 C		KOWB 1340 M		KGFJ 1230
	KIUZ 1400	Kentville, N.S.	CKEN 1350		KYOZ 1490 M		KFCF 1330
	KPRC 950 N	Kermitt, Tex.	KERB 800		WLP0 1220		KLAC 570
	KTHT 790 M	Kerrville, Tex.	KERV 1230		WLSR 1430		KMPC 710
	KTRH 740 C	Ketchikan, Alaska	KABI 580 A-M-N		WYSE 1350		KHX 1070 C
	KXYZ 1320 A		KTKN 930 C-A		KBRT 450		KIP 1540
	KYOK 1590				KEN0 1460 A		KPOP 1020
Howell, Mich.	WHMI 1350				KLAS 1230 C		KRKO 1150
Hudson, N.Y.	WHUD 1250				KORX 1340 M	Louisville, Ky.	WAYE 970 N
Hugo, Okla.	KIHN 1340				KRAM 920		WGRG 790 M
Hull, Que.	CKCH 970				KRBY 1050		WHAS 840 C
Humacao, P.R.	WALO 1240				KWUN 1230 A		WKLO 1080 A
Humboldt, Tenn.	WIRU 740				WTRA 1480		WINN 1240
Huntingdon, Pa.	WHUN 1150				WVAM 1340 N		WKYV 900
Huntington, N.Y.	WGSW 740				WLAU 1490 A		WLOU 1350
	WPLH 1470 M				WNSL 1260	Louisville, Miss.	WLSM 1270
	WHTN 800 M-A				WLBG 850	Loveland, Colo.	KLOY 1570
	WSAZ 930 N				WLVG 1230	Lovington, N.Mex.	KLEA 630
Huntsville, Ala.	WBHP 1230 M				WKU 1250	Lowell, Mass.	WCAP 980
	WFUN 1450				WLBW 1320		WLH 1440 M
	WAAY 1350 A				WCCM 800	Lubbock, Tex.	KCBD 1590 M-N
Huntsville, Tex.	KSAW 1490				WDXE 1370		KD 580
Huron, S.Dak.	KIIV 1340				KSVO 1580 A		KDUB 1340
Hutchinson, Kan.	KWBW 1450 N				WNSL 1260		KFYO 790 C
	KWHK 1280				KCCO 1050		KLLL 1460 M
Hutchinson, Minn.	KDUZ 1260				KLVC 1230	Ludington, Mich.	WKLA 1450 A
Idabel, Okla.	KBEL 1240				WLOE 1490 M	Lufkin, Tex.	KRBA 1340 A
Idaho Falls, Idaho	KID 590 C				CJSP 710		KTRB 1420 M
	KIFI 1400 A-M				WLNW 1590	Lumberton, N.C.	WTSB 1340 M
	KUPI 980				KLWT 1230	Lynchburg, Va.	WLVA 590 A
Independence, Kans.	KIND 1010 M				KGAL 920		WVOD 1390 M-N
Independence, Mo.	KIMO 1510				WCBR 1270		WBRG 1050
Indiana, Pa.	WDAD 1450 C				WLB0 900	Lynn, Mass.	WLYN 1360
Indianapolis, Ind.	WFBM 1260 A-M				WLBE 790 M	Macomb, Ill.	WKAI 1510
	WGEE 1590				WBIL 1410		
	WIBC 1070				WAGE 1290		
					WLLA 1570		

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.
Macon, Ga.	WBML 1240 WCRC 900 WIBB 1280 WMAZ 940 C WNEX 1400 A-M	Medford, Wis.	KBOY 730 KYJC 1230 A-C WIGM 490 M	Medicine Hat, Alta.	CHAT 1270 WMBB 1240 M	Newark, Ohio	WCLT 1430
Macon, Miss.	WKBC 1070 C	Medford, Wis.	WHBO 560 M	Medicine Hat, Alta.	WHBO 560 M	New Bedford, Mass.	WBSM 1420
Madera, Calif.	KHOT 1250	Memphis, Tenn.	WHER 1430	Medicine Hat, Alta.	WHER 1430	New Bern, N.C.	WHIT 1450 M WRNB 1490 M
Madison, Fla.	WMAF 1230		WMC 790 N		WMC 790 N	Newbury, S.C.	WKDK 1420
Madison, Ga.	WMGE 1250		WDLA 1070 M		WDLA 1070 M	New Braunfels, Tex.	KGNB 1240
Madison, Ind.	WORX 1270		WMPS 680		WMPS 680	New Britain, Conn.	WHAN 910
Madison, Wis.	WHA 970 WIBA 1310 N WISC 1480-A-M WKOW 1070 C	Mesa, Ark.	WMMW 1340 WLDK 1480 WREC 690 C	Montgomery, W.Va.	WMON 1340 M WMBN 1430 M	New Brunswick, N.J.	WCTO 1450 WGNV 1220
Madison, Tenn.	WEND 1430	Menominee, Mich.	WAGN 1340 A	Monticello, Ark.	WMBN 1340 M	Newburyport, Mass.	WNBP 1470
Madisonville, Ky.	WFMW 1310 WTTL 1310	Menomonie, Wis.	WMC 790 N	Monticello, Ky.	WFLW 1360	New Carlisle, Que.	CHNC 610
Magee, Miss.	WHNY 1250 A	Merced, Calif.	WYOS 1480 M	Montmagny, Que.	CKBM 1490	Newcastle, N.B.	CKMR 790
Magnolia, Ark.	KVMA 630 M	Meriden, Conn.	WMP 1580	Montpelier-Barre, Vt.	WVTR 1250	Newcastle, Wyo.	WAST 1280 M KASL 1240 A
Malden, Me.	KTCB 1470	Meridian, Miss.	WMOX 1240	Montrose, Colo.	CKAC 730 C	New Glasgow, N.S.	CKEK 1230
Malden, N.Y.	WICY 1490 M	Meridian, Miss.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Malden, Ark.	KBOK 1310	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Manassas, Va.	WDFR 1370	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Manchester, Ga.	WDFR 1370	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Manchester, Ky.	WWXL 1580	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Manchester, N.H.	WFEA 1370 WGR 610 C WKBZ 1240	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Manchester, Tenn.	WMSR 1580	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Manhattan, Kans.	KSAC 580 KMAN 1350	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Manila, P.I.	DZPI 1800 M-C DZRH 710 N	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Manistee, Mich.	WMTE 1340	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Manitou Springs, Colo.	KCMS 1490 KCUR 980	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Manitowac, Wis.	WDR 1240 M	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Mankato, Minn.	KYSM 1230 N KTOE 1420 A	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Manning, S.C.	WYMB 1410	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Mansfield, La.	KDBC 1360	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Mansfield, Ohio	WMAN 1400 A	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marianna, Fla.	WCLW 1570	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marietta, Ga.	WFO 1230 M WBE 1050	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marietta, Ohio	WMOA 1490 M	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marine City, Mich.	WDDG 1580	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marionette, Wis.	WJAM 570 N	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marion, Ala.	WJAM 1310	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marion, Ill.	WJAM 1150	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marion, Ind.	WBAT 1400 WMRI 800	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marion, N.C.	WBRN 1250	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marion, Ohio	WBRN 1490 A	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marion, S.C.	WATP 1430	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marion, Va.	WMEY 1010	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marked Tree, Ark.	KAPB 1370	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marksville, La.	KMLW 1010	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marlin, Tex.	WOMJ 1320 M	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marquette, Mich.	KMHL 420 A	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marshall, Minn.	KMMH 1300	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marshall, Mo.	KMMH 1300	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marshall, N.C.	KMMH 1480	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marshall, Tex.	KMMH 1480 KADD 410 D	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marshalltown, Iowa	KFBZ 1230	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marshallfield, Wis.	WDLB 1450	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Martin, Tenn.	WCMT 1410	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Martinsburg, W.Va.	WEPM 1340 WHEE 1370 WVMA 1450 N	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Martinsville, Va.	WHEE 1370 WVMA 1450 N	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marysville, Calif.	KMYC 1410 M	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marysville, Kans.	KNDY 1570	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marysville, Mo.	KNIM 1580	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Marysville, Tenn.	WGAP 1400	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Mason City, Iowa	KRIB 1490 KSMN 1010	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Massena, N.Y.	WMSA 1340 A	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Massillon, Ohio	WTBG 990	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Matane, Que.	CKBL 1250	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Matawan, W.Va.	WHJC 1380	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Mattoon, Ill.	WLBH 1170	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Matvaguez, P.R.	WAEI 600 WKJL 710 WORA 1150 WPRA 990 WTTL 1300	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Mayfield, Ky.	WKTM 1050 WNGD 1320	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Mayfield, N.C.	WYNY 1420	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Mayfield, Ky.	WYNY 1420	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
McAlester, Okla.	KTMC 1400 KNED 1150	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
McAllen, Tex.	KRID 910 M	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
McCamey, Tex.	KCMR 1450	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
McComb, Miss.	WHNY 1250 A WAFP 980 KJBL 1300 M	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
McCook, Neb.	KVSA 1220	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
McGehee, Ark.	WEDD 810 C	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
McKeesport, Pa.	WCKK 1360	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
McKenzie, Tenn.	WHDM 1440	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
McKinney, Tex.	KMAE 1600	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
McMinnville, Oreg.	KMCM 1260	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
McMinnville, Tenn.	WBMC 960	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
McPherson, Kans.	WNMT 1230 M	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
McRae, Ga.	WDAX 1410 WGW 1490	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Meadville, Pa.	WHIL 1430	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medford, Mass.	WHIL 1430	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medford, Oreg.	KMED 1440 N	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medford, Wis.	KBOY 730 KYJC 1230 A-C WIGM 490 M	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	CHAT 1270 WMBB 1240 M	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WHBO 560 M	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WHER 1430	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WMC 790 N	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WDLA 1070 M	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WMPS 680	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WMMW 1340 WLDK 1480 WREC 690 C	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WHER 1430	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WMC 790 N	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WDLA 1070 M	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WMPS 680	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WMMW 1340 WLDK 1480 WREC 690 C	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WHER 1430	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WMC 790 N	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WDLA 1070 M	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WMPS 680	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WMMW 1340 WLDK 1480 WREC 690 C	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WHER 1430	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WMC 790 N	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WDLA 1070 M	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WMPS 680	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WMMW 1340 WLDK 1480 WREC 690 C	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WHER 1430	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WMC 790 N	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WDLA 1070 M	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WMPS 680	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WMMW 1340 WLDK 1480 WREC 690 C	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WHER 1430	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WMC 790 N	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WDLA 1070 M	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WMPS 680	Mesa, Ariz.	WMOX 1240	Montrose, Pa.	WPEL 1250	New Haven, Conn.	WVYZ 1300
Medicine Hat, Alta.	WMMW 1340 WLDK 1480 WREC 690 C</						

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.
Sackville, N.B.	WSYB 1380 M	Sanford, Me.	WSME 1220	Sherbrooke, Que.	KMA 960 A	Stuttgart, Ark.	KWAK 1240 M
Sacramento, Calif.	CBA 1070 N KCHA 1320 N KFBC 1530 A KGM 1350 M KROY 1240 C KXOA 1470 N KGLU 1480 N	San Francisco, California	WWEY 1290 WWGP 1050 KFRG 610 M KCBS 740 C KJBS 1100 KNBC 690 N KOBV 1550 KSAV 1010 KSNAN 1450 KSF 580 KVA 1280 KLOK 1170 KJSJ 1590 KEEN 1370 KRRX 1500	Sheridan, Wyo.	CHLT 900 CKTB 1240 KWYO 1410 M KRRV 910 M KLAN 1500 KJBU 1400	Suffolk, Va.	WLP 1450 M KIKS 1310 A KSST 1230
Safford, Ariz.	WKNX 1210	San Jose, Calif.	KNBB 690 N KOBV 1550 KSAV 1010 KSNAN 1450 KSF 580 KVA 1280 KLOK 1170 KJSJ 1590 KEEN 1370 KRRX 1500	Shirley, Mont.	KOKA 1050 KENT 1550 M KZEA 980 KJOE 1480 KLU 1300 KEL 710 KWK 130 C	Sulphur, La.	WLSM 1480 WJCH 1390 C WSSC 1340 A WKOK 1240 C
Saginaw, Mich.	WSAM 1400 N WSGW 790 M WWSR 1420 M WKLC 1300	San Juan, P.R.	WAPA 680 M WHA 400 M WIPR 940 WKAQ 580 WKVM 1290 WITA 1140	Shreveport, La.	KGKC 1480 M KHFB 1420 KSIM 1400 WNCA 1570 KUDA 1290 M KJL 1340 C WYAG 1050 CFRS 1560 KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Summerside, P.E.I.	CJRW 1240 WGA 850 WJCH 1390 C WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Albans, Vt.	CHGB 1350	San Luis Obispo, Calif.	WAPA 680 M WHA 400 M WIPR 940 WKAQ 580 WKVM 1290 WITA 1140	Sioux City, Iowa	KWYO 1410 M KRRV 910 M KLAN 1500 KJBU 1400 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Sumter, S.C.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Albans, W.Va.	CHGB 1350	San Mateo, Calif.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Sunbury, Pa.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Anne de la Poutiere, Que.	CHGB 1350	San Rafael, Calif.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sitka, Alaska	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Sunnyside, Wash.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Augustine, Fla.	WFOY 1240 C	San Saba, Tex.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sitka, Alaska	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Superior, Wis.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Boniface, Man.	WSTN 1420	Santa Ana, Calif.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Skowhegan, Maine	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Swainsboro, Ga.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Catharine, Ont.	CKTB 610	Santa Barbara, Cal.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux City, Iowa	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Sweetwater, Tenn.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Cloud, Minn.	KFAM 1450 N	Santa Cruz, Calif.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Sweetwater, Tex.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. George, Utah	WJON 1240	Santa Fe, N.Mex.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Swift Current, Sask.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Helen, Mich.	KDXU 1450	Santa Maria, Cal.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Sydney, N.S.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Jean, Que.	WCBQ 1590	Santa Monica, Cal.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Sylfauga, Ala.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Jerome, Que.	CHRS 1090	Santa Paula, Calif.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Sylvania, Ga.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. John's, Nfld.	CKJL 900 CFBC 930 CHSI 1150 CJBN 640 CJON 930 VOAR 1230 VOCM 590 VOWR 800	Santa Rosa, Calif.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Syracuse, N.Y.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Johnsbury, Vt.	WVTR 1340	Santurce, P.R.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Tabor City, N.C.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Joseph, Mich.	WVTR 1340	Saranac Lake, N.Y.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Tacoma, Wash.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Joseph, Mo.	KFEQ 680 KRES 1550 M KUSN 1270	Sarasota, Fla.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Taft, Calif.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Joseph d'Alma, Que.	CFGT 1270	Saratoga Springs, N.Y.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Tahoe Valley, Calif.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Louis, Mo.	KATZ 1600 KCHD 1100 KMOX 1120 C KSD 590 KSTL 690 KWK 1380 KXOK 630 WEW 770 WLL 1430 A	Sault Ste. Marie, Michigan	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Talladega, Ala.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Mary's, Pa.	WKBI 1400 N	Sault Ste. Marie, Ontario	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Tallahassee, Fla.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Paul, Minn.	KSTP 1500 N	Sault Ste. Marie, Ontario	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Tallahassee, Fla.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Peter, Minn.	WISK 1590 M	Savannah, Ga.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Tallahassee, Fla.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Peter, Minn.	KRBI 1310	Savannah, Tenn.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Tallahassee, Fla.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Petersburg, Fla.	WSPN 680	Sayra, Pa.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Tallahassee, Fla.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Petersburg Beach, Fla.	WTSP 1380 M	Schenectady, N.Y.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Tallahassee, Fla.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Thomas, Ont.	CHLO 680	Scottsbluff, Nebr.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Tallahassee, Fla.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
St. Genevieve, Mo.	KSGM 980	Scottsboro, Ala.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Tallahassee, Fla.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
Salamanca, N.Y.	WNY 1590	Scottsdale, Ariz.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Tallahassee, Fla.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
Salem, Ill.	WJBD 1350	Scranton, Pa.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Tallahassee, Fla.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
Salem, Ind.	WSLM 1220	Seafood, Del.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Tallahassee, Fla.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
Salem, Mass.	WESX 1230	Seattle, Wash.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Tallahassee, Fla.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
Salem, Mo.	KSMO 1340	Sebring, Fla.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Tallahassee, Fla.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
Salem, Oreg.	KSLM 1390 M KBZY 1490 N KGAY 1430 WBLU 1480	Sedalia, Mo.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Tallahassee, Fla.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
Salem, Va.	KVRH 1340 M	Seguin, Tex.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Tallahassee, Fla.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
Salina, Kans.	KSAI 1150 M	Selma, Ala.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KESL 1230 KE 1320 KIHO 1270 KSOD 1140 A	Tallahassee, Fla.	WSSC 1340 A WKOK 1240 C KREW 1230 C WDSM 710 M KSUE 1240 WJAT 800 WJCH 1390 C KXOX 1240
Salinas, Calif.	KDON 1460	Seminole, Fla.	KATY 1340 KNVC 920 M KNCN 1400 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 1490 KIST 1340 N KMTS 1250 M	Sioux Falls, S.Dak.	KANN 1590 KSCJ 1360 A KMNS 6		

Location	C.L.	Kc.	N.A.	Location	C.L.	Kc.	N.A.	Location	C.L.	Kc.	N.A.	Location	C.L.	Kc.	N.A.
Traverse City, Mich.				Vernon, B.C.	CJIB	940		Watertown, Wis.	WTTN	1580		Willow Springs, Mo.			
Trenton, Mo.	WTCM	1400		Vernon, Tex.	KVWG	1490		Waterville, Me.	WTVL	1490	A	Wilmington, Del.	KUKU	1330	
Trenton, N.J.	KTTN	1600		Vero Beach, Fla.	WAXE	1370		Watsonville, Calif.	KOMY	1340			WAMS	1380	M
	WTNJ	1300			WTTB	1490	A	Wauchula, Fla.	WUAC	1310			WDL	1150	N
	WBUD	1260		Vicksburg, Miss.	WQBC	1420	M	Waukegan, Ill.	WIKS	1220			WILM	1450	A
	WTFM	920	N		WVIM	1490		Waukesha, Wis.	WAXU	1510			WTUX	1290	A
Trinidad, Colo.	KCRT	1240	M	Victoria, B.C.	CJVI	900		Wausapa, Wis.	WUDX	800		Wilmington, N.C.	WMFD	630	A
Troy, Ala.	WTBF	970	M		CKDA	1220		Wausau, Wis.	WDSU	1400	N		WKLW	730	
Troy, N.Y.	WVAZ	1330	M	Victoria, Tex.	KNAL	1410		Waycross, Ga.	WHVZ	1230			WFNB	1340	M
	WTRY	980			KVIC	1340	M	Waverly, Ohio	WPKO	1380		Wilson, N.C.	WGTM	590	C
Truro, N.S.	CKCL	600		Victoriaville, Que.	CFDA	1380		Waxahachie, Tex.	KBEC	1390			WVOT	1420	M
Truth or Consequences, N. Mex.	KCHS	1400		Vidalia, Ga.	WVOP	970		Waycross, Ga.	WACL	570		Winchester, Ky.	WWKY	1380	
Tryon, N.C.	WTYN	1580		Vieques, P.R.	WIVV	1370		Waycross, Ga.	WAYX	1230	M	Winchester, Tenn.	WCDT	1340	
Tucson, Ariz.	KTUC	1400	M	Ville Marie, Que.	CKVM	710		Waynesboro, Ga.	WBRO	1310		Windsor, N.S.	WIMO	1300	A
	KCEE	790		Ville St. Georges, Que.	KVPI	1050		Waynesboro, Miss.	WABO	990		Windsor, N.C.	CFB	830	
	KNCA	580	A	Vincennes, Ind.	WAQV	1450	M	Waynesboro, Pa.	WAYB	1490	M	Windsor, Ont.	CBE	1550	
	KEVT	690		Vineand, N.J.	WWBZ	1360		Waynesville, Pa.	WANB	1580			CKLW	800	M
	KMOP	1330		Vinita, Okla.	KVIN	1470		Waynesville, N.C.	WHSC	1400		Wingham, Ont.	CKNX	920	
	KTKT	950		Virginia, Minn.	WHLB	1400	N	Weatherford, Tex.	KZEE	1220		Winnechua, Nev.	WKNA	1400	
	KOLD	1490	C	Virginia Beh., Va.	WBQF	1600		Webster City, Iowa	KJFJ	1570		Winfield, La.	KVCL	1270	
	KVOA	1290	N	Virouqua, Wis.	WISY	1360		Weirton, W.Va.	WEIR	1430		Winner, S.Dak.	KWYR	1260	
Tucumcari, N. Mex.	KTRK	1300	M	Visalia, Calif.	WONG	1400		Weiser, Idaho	WEIS	1400		Winnipeg, Man.	CBW	930	
Tulare, Calif.	KCKK	1270	M	Vivian, La.	KLVI	1600		Welch, W.Va.	WELC	1150			CKY	580	
	KGEN	1370		Waco, Tex.	WACO	1460	M		WEMD	1340	M		CJOB	680	
Tularosa, N.M.	KMAM	1590		Wadena, Minn.	KWAX	1230	M	Wellabro, Pa.	WBNT	1490	M	Winnboro, La.	KMAR	1570	
Tulia, Tex.	KTUE	1260		Wadsworth, N.C.	WADE	1210		Wellston, Ohio	WKOV	1330		Winona, Minn.	KWNO	1230	A
Tullahoma, Tenn.	WJIG	740		Wailuku, O.H.	KMVI	550	N	Wellsville, N.Y.	WLSV	790			KAGE	1570	
Tulsa, Okla.	KAKC	970		Waipahu, Oahu, Hawaii	KAHU	920		Wenatchee, Wash.	KEM	560	A	Winslow, Ariz.	KVNC	1010	M
	KTRR	1300			KWAL	620	M		WENI	1100		Winston-Salem, N.C.	WAAA	980	
	KRMG	790		Wallace, Idaho	KWAL	620	M	Weslaco, Tex.	KRGV	1290	N		WAIR	1340	
	KTUL	1430	C	Wallace, N.C.	WLSE	1400		W. Bend, Wis.	WBKV	1470			WSJS	600	N
	KVOO	1170	N	Walla Walla, Wash.				W. Frankfort, Ill.	WFRX	1300			WTBO	1380	M-C
	KFMJ	1050	M		KHIT	1320		W. Monroe, La.	KUZN	1310			WSIR	1490	M
Tupelo, Miss.	WELO	1490	M		KUJ	1420	M	W. Palm Beach, Fla.	WEAT	850	N	Winter Haven, Fla.	WSIR	1490	M
	WTUP	1580			KTEL	1490	A		WEAT	850	N	Winter Park, Fla.	WABR	1440	
Turlock, Calif.	WTRJ	1490	M	Walnut Ridge, Ark.					WEAT	850	N	Wisconsin Rapids, Wis.	WHR	1340	
Tuscaloosa, Ala.	WJRD	1150			KRLW	1320			WEAT	850	N		WAAA	980	
	WNPT	1280	A	Walsenburg, Colo.	KFLJ	1380		West Plains, Mo.	KWPM	1290	M	Wolf Pt., Nebr.	KVCK	1490	M
	WRBS	790		Walterboro, S.C.	WALD	1220	M	West Point, Miss.	WROB	1450	M	Woodside, N.Y.	WWRL	1600	
	WTBC	1230	M	Waltham, Mass.	WCRB	1330		West Springfield, Mass.	WTXL	1490	A	Woodstock, Ont.	CKOX	1340	
Tuscumbia, Ala.	WVNA	1590	M	Walton, N.Y.	WDLA	1270						Woodward, Okla.	KSIW	1450	
Tuskegee, Ala.	WTUS	580		Ward Ridge, Fla.	WJDE	1250		W. Yarmouth, Mass.	WCOB	1240	M	Woonsocket, R.I.	WNRI	1380	
Twin Falls, Idaho	KTJ	1270	N	Ware, Mass.	WARE	1250	M		WERI	1230	M		WWON	1240	
	KLIX	1490	M	Warner Robbins, Ga.	WRPB	1350		Westerly, R.I.	WERI	1230	M	Wooster, Ohio	WWST	960	
	KEEP	1450			WRPB	1350		Westfield, Mass.	WDEF	1570	M	Worcester, Mass.	WAAB	1440	M-N-A
Two Rivers, Wis.	WTRW	1590		Warren, Ark.	KWHF	860		Westminster, Md.	WTTR	1470			WNEB	1230	
Tyler, Tex.	KDOK	1390	M	Warren, Ohio	WHHH	1440		Weston, W.Va.	WHAW	1450	M		WORC	1310	
	KGJB	1490	M	Warren, Pa.	WNAE	1310		W. Warwick, R.I.	WWRI	1450			WTAG	580	C
	KTBE	600	A	Warrensburg, Mo.	KOKO	1450		Wetumpka, Ala.	WETU	1250			KWOR	1340	M
	KZEY	690	A	Warrenton, Mo.	KWRE	790		Wewoka-Seminole, Okla.	KWHB	1260	A	Worland, Wyo.	KWAO	730	
Tyrone, Pa.	KUKI	1490	M	Warrenton, Va.	WKTf	1420			CFSL	1340		Worthington, Minn.	WRFD	780	
Ukiah, Calif.	KUKI	1490	M	Warsaw, Ind.	WRSW	1480		Weyburn, Sask.	CFSL	1340		Worthington, Ohio	WRFD	780	
Union, Mo.	KLPW	1220		Warsaw, Va.	WNNT	690		Wheaton, Md.	WDOO	1540		Wynne, Ark.	KWYN	1400	
Union, S.C.	WBCU	1460		Wasco, Calif.	KWSO	1050		Wheeling, W.Va.	WHLL	1600		Wytheville, Va.	WYVE	1280	
Union City, Tenn.	WENK	1240		Washington, D.C.	WGMS	570	M		WKWK	1400	A	Yakima, Wash.	KIT	1280	
	WTUC	1580			WGMS	570	M	White Castle, La.	WVVA	1470	C		KIMA	1460	C
Uniontown, Pa.	WBMS	1590	C	Washington, Ga.	WKLE	1370		White Plains, N.Y.	WVAS	1230			KUYI	980	
Urbana, Ill.	WILL	580	M	Washington, Ind.	WAMW	1380		White Plains, N.Y.	WVAS	1230			KYAK	1390	M
	WKID	1580		Washington, N.J.	WCRV	1580		Whitesburg, Ky.	WTCW	920		Yankton, S.D.	KYNT	1450	M
	WIBX	950	C	Washington, N.C.	WOOV	1340		Whiteville, N.C.	WENC	1220			WNAX	370	C
	WRUN	1150		Washington, Pa.	WRRF	930	A	Wichita, Kans.	KAKE	1240	M	Yarmouth, N.S.	CJLS	1340	
	WTLB	1310	A	Washington, P.C.	WJPA	1450	M		KANS	1480	N	Yazoo City, Miss.	WAZF	1230	
	KVOU	1400		Washington Court House, Ohio	WCHO	1250		White Castle, La.	KFBI	1070		York, Nebr.	KAWL	1370	
Uvalde, Tex.	CKVD	1230		Waterbury, Conn.	WATR	1320	A	White Plains, N.Y.	WVAS	1230		York, Pa.	WNOW	1250	
Val D'Or, Que.	CKVD	1230			WATR	1320	A	White Plains, N.Y.	WVAS	1230			WYAC	1350	N
Valdosta, Ga.	WGAF	910	A	Waterbury, Conn.	WATR	1320	A	Whitesburg, Ky.	WTCW	920			WSBA	910	A-M
	WJEM	1150		Waterbury, Conn.	WATR	1320	A	Whiteville, N.C.	WENC	1220		York, S.C.	WYJL	1580	
Vallejo, Calif.	KGWY	1190		Waterbury, Conn.	WATR	1320	A	Whiteville, N.C.	WENC	1220		Yorkton, Sask.	CJGX	940	
Valley City, N. Dak.	KOVC	1490	M	Waterbury, Conn.	WATR	1320	A	Wichita Falls, Tex.	KSYD	910	M	Youngstown, Ohio	WBBW	1240	A
Vanceville, Ky.	WMTC	730		Waterbury, Conn.	WATR	1320	A		KTRN	1290			WFMJ	1390	N
Vancouver, B.C.	CBU	690		Waterbury, Conn.	WATR	1320	A	Widkes-Barre, Pa.	WBAX	1240	M		WKBN	570	C
	CFM	1410		Waterbury, Conn.	WATR	1320	A		WRE	1340	N	Yreka, Calif.	KSYC	1490	
	CJOB	600		Waterbury, Conn.	WATR	1320	A	Williamson, W.Va.	WBTH	1400	M	Yuba City, Calif.	KUBA	1600	
	CKWX	1130	M	Waterbury, Conn.	WATR	1320	A	Williamsport, Pa.	WLYC	1050			KAGR	1450	
Vancouver, Wash.	KKEY	1150		Waterbury, Conn.	WATR	1320	A		WRAC	1400	N		KOF	1240	
	KVAN	910		Waterbury, Conn.	WATR	1320	A	Williamsport, Pa.	WLYC	1050			KYUO	1400	M
Ventura, Calif.	KUDN	1450	M	Waterbury, Conn.	WATR	1320	A	Williamston, N.C.	WIAM	900			KYUM	560	N
	KVUD	1590		Waterbury, Conn.	WATR	1320	A	Williamston, N.C.	WIAM	900		Zanesville, Ohio	WHIZ	1240	N
Verdun, Que.	WVNY	850		Watertown, N.Y.	WATN	1240		Williamston, N.C.	WIAM	900		Zarephath, N.J.	WAWZ	1380	N
Vermillion, S.Dak.	KUSD	690			WATN	1240		Williamston, N.C.	WIAM	900					
Vernal, Utah	KVEL	1250		Watertown, S.Dak.	KWAT	950	M	Willmar, Minn.	KWLM	1340	A				

World-Wide Short-Wave Stations

Active and Most Commonly Heard in U. S. Listed by Frequency

(For Canadian Short-Wave Stations, see separate listing, p. 187) Abbreviations: Kc., frequency in kilocycles (to change to megacycles, divide by 1000); C.L. call letters. Due to malfunction of transmitter, interference by other stations, jamming, variance in propagational conditions, or reallocation of frequencies, stations may use other frequencies than those given.

The abbreviation (VOA) denotes Voice of America.

The symbol * denotes stations beaming regular evening broadcasts to the United States.

Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location
3275	VP4RD	Port-of-Spain.	3450	YVQI	Barcelona, Venez.	4820	XEJG	Guadalajara, Mex.	4895	PRF6	Manaos, Brazil
			3460	YVLI	Valencia, Venez.	4820	YVNB	Coro, Venez.	4897	VL4	Perth, Venez.
3300		Belize, Brit. Honduras	3480	YVLE	Puerto Cabello, Vz.	4830	YVOA	San Cristobal, Vez.	4900	YVQE	Ciudad Bolivar, Vz.
3310	YVOG	Trujillo, Venez.	3490	YVRA	Maturin, Venez.	4835	HJKE	Bogota, Colombia	4903	HJAG	Barranquilla, Col.
3320	YVQG	Barcelona, Venez.	3620	YVLG	Maracay, Venez.	4840	YVOI	Valera, Venez.	4907	YVMM	Coro, Venez.
3330	YVQL	El Tigre, Venez.	3980		Suva, Fiji Islands	4845	CSA93	Ponta Delgada, Az.	4910	JKI	Nazaki, Japan
3340	YVMY	Carora, Venez.	4650	H2CAJ	Guayaquil, Ecua.	4848	HJGF	Bucaramanga, Col.	4910	YDB2	Djakarta, Indon.
3350	YVKT	Caracas, Venez.	4752	YVNA	Maracaibo, Venez.	4850	YVMS	Barquisimeto, Vz.	4915	Accra,	Ghana
3360	YVOC	San Cristobal, Vz.	4768	HJEF	Cartagena, Col.	4855	HJFN	Neiva, Colombia	4915	YVKB	Caracas, Venez.
3360	ZQI	Kingston, Jamaica	4775	HJBG	Bucaramanga, Col.	4860	JKL	Tokyo, Japan	4917	H19B	Santiago, Dom. Rep.
3370	YVMI	Maracaibo, Venez.	4783	HJAB	Barranquilla, Col.	4860	YVPA	San Felipe, Venez.	4917	VLM4	Brisbane, Aus.
3380	YVQN	Puerto La Cruz, Vz.	4790	YVQC	Ciudad Bolivar, Vz.	4865	PRCS	Belem, Para, Brazil	4930	HJAP	Cartagena, Col.
3390	YVKK	Caracas, Venez.	4797	HJFU	Armenia, Colombia	4865	HJFA	Pereira, Colombia	4940	KJM	Kawachi, Japan
3400	YVKP	Caracas, Venez.	4800	YVME	Maracaibo, Venez.	4871	HJBG	Cucuta, Colombia	4940	YVMQ	Barquisimeto, Vz.
3410	YVMM	Caracas, Venez.	4805	YVKB	Manaos, Brazil	4880	YVKF	Caracas, Venez.			
3420	YVDE	Merida, Venez.	4810	YVMB	Maracaibo, Venez.	4892	YVKB	Caracas, Venez.			
3440	YVLI	Maracay, Venez.	4815	HJBB	Cucuta, Col.	4895	HJCH	Bogota, Col.			

Kc. C.L. Location

4945 HJCV Bogota, Col.
 4950 ZQI Kingston, Jamaica
 4951 Dakar, Senegal
 4960 YVQZ Caracas, Venez.
 4967 HJAE Cartagena, Col.
 4970 YVVK Caracas, Venez.
 4985 YVMO Barquisimeto, Vz.
 4993 H1IA Santiago, D. Rep.
 5014 PJC3 Willmitz, Curac.
 5020 HJFW Manizales, Col.
 5023 H16Z Santiago, D. Rep.
 5028 YVKB Caracas, Venez.
 5045 ZYP23 Petropolis, Brazil
 5050 YVVK Caracas, Venez.
 5053 H12L Ciudad Trujillo, D.R.
 5055 HJDW Medellin, Col.
 3075 HJKH Sutanegara, Colom.
 5758 PZH5 Paramaribo, Surinam
 5800 HRN Tegucigalpa, Hond.
 5920 HRA Tegucigalpa, Hond.
 5940 Khabarovsk, U.S.S.R.
 5940 Moscow, U.S.S.R.
 5952 TGNA Guatemala, Guat.
 5960 HJCF Bogota, Colombia
 5965 Shanghai, China
 5969 HVJ Vtelean City
 5970 H1AT Ciudad Trujillo, D.R.
 5981 ZFY Georgetown, Br. Gui.
 5985 Radio Free Europe, Munich, Germany
 5990 TGJA Guatemala, Guat.
 5995 H050 Panama, Panama
 6005 Berlin, Germany
 6005 HPSK Panama, Panama
 6009 HJFC Bogota, Colombia
 6010 GRB London, England
 6010 OLR2A Prague, Czech.
 6010 XE01 Mexico, Mex.
 6015 PRA8 Recife, Brazil
 6018 HJCX Bogota, Col.
 6020 Kiev, U.S.S.R.
 6020 Radio Free Europe, Munich, Germany
 6020 KNBH(VOA) Dixon, Calif.
 6020 XEUV Vera Cruz, Mex.
 6024 Brazzaville, Fr. Eq. Africa
 6025 Radio Nederland
 6025 H1J San Pedro, D.R.
 6030 Stuttgart, Germany
 6030 DZH6 Manila, P.I.
 6030 XEKW Morelia, Mex.
 6030 HPSB Panama, Pan.
 6035 GWS London, England
 6035 Monte Carlo, Monaco
 6035 XYZ Rangoon, Burma
 6037 San Jose, Costa Rica
 6040 GY London, England
 6040 KCBR Delano, Calif.
 6040 Tangier, Tangier
 6040 WLVO Cincinnati, U.S.A.
 6045 YDF Djakarta, Indonesia
 6050 H1YN Ciudad Trujillo, D.R.
 6050 GSA London, England
 6054 JEXX Cali, Colombia
 6055 HER2 Bern, Switzerland
 6060 GSX London, England
 6060 KNBH(VOA) Dixon, Calif.
 6060 Tangier I, Tangier
 6060 WDSI New York, U.S.A.
 6065 SBO Malmö, Sweden
 6065 XEXE Mexico City, Mex.
 6069 JOB Tokyo, Japan
 6070 GRB London, England
 6075 KGEI San Fran., U.S.A.
 6080 Munich II, Germany
 6081 OAX42 Lima, Peru
 6085 ORU Brussels, Belgium
 6085 VPARD Port-of-Spain, Trinidad
 6085 ZYK2 Recife, Brazil
 6090 GWM London, England
 6090 VL16 Sydney, Australia
 6092 Radio Luxemburg
 6095 Horby, Sweden
 6095 Radio Free Europe, Munich, Germany
 6095 ZYB7 Sao Paulo, Brazil
 6095 HJFK Pereira, Colombia
 6100 Belgrade, Yugoslavia
 6100 WRCA New York, U.S.A.
 6110 GSL London, England
 6112 H12Z Ciudad Trujillo, D.R.
 6115 Berlin, Germany
 6120 HC2FB Guayaquil, Ecu.
 6120 Z114 Limassol, Cyprus
 6120 Tangier, Tangier
 6120 WRCA New York, U.S.A.
 6122 HPSJ Panama, Pan.
 6124 HRQ Santiago, Hond.
 6125 GWA London, England
 6130 XEUZ Mexico, Mex.
 6130 Radio Spain
 6130 COCD Havana, Cuba
 6130 Port Moresby, New Guinea
 6135 H1ED Cali, Colombia
 6140 Munich, Germany
 6145 H1E Medellin, Col.
 6147 PRL9 Rio de Janeiro, Br.
 6150 GRW London, England
 6150 TGAZ Guatemala, Guat.
 6160 HJKJ Bogota, Colombia
 6160 Honolulu, Hawaii
 6160 Munich, Germany
 6165 GWK London, England
 6165 HER3 Bern, Switzerland
 6167 4VCM Port-au-Prince, H.

Kc. C.L. Location

6170 Munich, Germany
 6170 GS2 London, England
 6170 KCBR Delano, U.S.A.
 6170 YVVK Caracas, Venez.
 6172 Z1M5 Limassol, Cyprus
 6175 XEXA Mexico, Mex.
 6180 LRM Mendoza, Argentina
 6180 Ashkabad, U.S.S.R.
 6180 GRO London, England
 6182 TGWE Guatemala, Guat.
 6185 KCBR Delano, Calif.
 6185 HJCT Bogota, Colombia
 6190 Frankfurt, Germany
 6190 H19T Puerto Plata, D.R.
 6190 WLVO Cincinnati, U.S.A.
 6190 WRCA New York, U.S.A.
 6195 GRN London, England
 6195 Honolulu, Hawaii
 6200 Paris, France
 6215 SP13 Warsaw, Poland
 6235 HRD2 La Ceiba, Hond.
 6235 Karachi, Pakistan
 6248 Budapest, Hungary
 6285 TGTQ Guatemala, Guat.
 6295 OTM1 Leopoldville, Belgian Congo
 6295 TGLA Leopoldville, Belgian Congo
 6320 Baden-Baden, Germany
 6322 COCV Havana, Cuba
 6335 TGT4 Guatemala, Guat.
 6351 HRP1 San Pedro Sula, Hond.
 6374 CSA21 Lisbon, Port.
 6375 KGAQ Guatemala, Guat.
 6632 HC2RL Guayaquil, Ecu.
 6650 COCY Santa Clara, Cuba
 6660 HROW Tegucigalpa, Hond.
 6758 YNPM Managua, Nic.
 6790 Z1M6 Limassol, Cyprus
 6830 AXB21 Tel Aviv, Israel
 6870 HCAE Quito, Ecuador
 7105 Paris, France
 7112 CRAA4 Praia, Cape V. Isls.
 7120 GRM London, England
 7135 BED7 Taipei, Formosa
 7135 MCM London, England
 7145 Radio Free Europe, Lisbon, Portugal
 7150 GRT London, England
 7165 Moscow, U.S.S.R.
 7175 VUD Delhi, India
 7180 JOA Tokyo, Japan
 7185 GRK London, England
 7200 GWL London, England
 7205 Warsaw, Poland
 7210 GWL London, England
 7210 HE13 Bern, Switzerland
 7222 Budapest, Hungary
 7230 GSW London, England
 7240 Moscow, U.S.S.R.
 7240 Paris, France
 7250 GVL London, England
 7255 Pradub, Czechoslovakia
 7257 JKH Tokyo, Japan
 7260 GSU London, England
 7260 Moscow, U.S.S.R.
 7280 GWN London, England
 7285 JAK Tokyo, Japan
 7315 TKS Ankara, Turkey
 7290 Hambury, Germany
 7290 VUD Delhi, India
 7295 Moscow, U.S.S.R.
 7300 Radio Free Europe, Munich, Germany
 7300 SVD2 Athens, Greece
 7315 SSO San Salvador, Salv.
 7320 GRJ London, England
 7335 BEC36 Taipei, Formosa
 7360 Moscow, U.S.S.R.
 7670 Sofia, Bulgaria
 7850 ZAA Tirana, Albania
 7863 SUX Cairo, Egypt
 7893 H1KA Pusan, S. Korea
 7951 Illice, Argentina
 8036 FXE Beirut, Lebanon
 8664 COJK Camaguey, Cuba
 8825 COCQ Havana, Cuba
 8955 COKG Santiago, Cuba
 9007 Voice of Zion, Tel Aviv, Israel
 9026 COBZ Havana, Cuba
 9236 COBQ Havana, Cuba
 9252 Bucharest, Rumania
 9290 PRN9 Rio de Janeiro, Brazil
 9316 LRS Buenos Aires, Arg.
 9340 OAXJ Lima, Peru
 9363 COBC Havana, Cuba
 9369 Madrid, Spain
 9380 Khabarovsk, U.S.S.R.
 9400 OTM2 Leopoldville, Belgian Congo
 9410 GRJ London, England
 9440 Brazzaville, Fr. Eq. Africa
 9452 HRJ Buenos Aires, Arg.
 9463 TAP Ankara, Turkey
 9480 Moscow, U.S.S.R.
 9490 KUJ39 Agaña, Guam
 9500 XEWW Mexico, Mex.
 9504 OLR3B Prague, Czech.
 9505 HOL4 Colon, Panama
 9505 H1BD Karachi, Pakistan
 9510 YVHJ Barquisimeto, Ven.
 9510 GSB London, England
 9515 KNBH(VOA) Dixon, Calif.
 9515 TAT Ankara, Turkey
 9520 Colombo, Ceylon
 9520 HJKB Bogota, Colombia
 9520 OZF Skamlebak, Denmark
 9520 VLT9 Port Moresby,

Kc. C.L. Location

British New Guinea
 9520 WLWO Cincinnati, U.S.A.
 9525 GWJ London, England
 9525 ZB73 Victoria, Hong Kong
 9527 Warsaw, Poland
 9530 Honolulu, Hawaii
 9530 Manila, Philippines
 9530 KCBR Delano, Cal., U.S.A.
 9530 WABC New York, U.S.A.
 9531 COCD Havana, Cuba
 9535 HER4 Bern, Switzerland
 9535 SBU Stockholm, Sweden
 9540 Munich, Germany
 9540 VLG9 Melbourne, Aus.
 9540 ZL2 Wellington, N. Zeal.
 9543 KYZ Rangoon, Burma
 9548 KEFT Vera Cruz, Mex.
 9550 VJ Vtelean City
 9550 Paris, France
 9550 OLR3A Prague, Czech.
 9555 OIX2 Pori, Finland
 9555 XETT Mexico, Mex.
 9560 JBD2 Kawaichi, Japan
 9560 London, England
 9560 Paris, France
 9560 Tangier, Tangier
 9560 WLVO Cincinnati, U.S.A.
 9560 WRCA New York, U.S.A.
 9565 Komsomolsk, U.S.S.R.
 9565 ZYK3 Recife, Brazil
 9570 Algiers, Algeria
 9570 GVL London, England
 9570 KCBR(VOA) Delano, Calif.
 9570 Warsaw, Poland
 9570 Bucharest, Rumania
 9570 Rome, Italy
 9580 GSC London, England
 9580 VLB9 Shepparton, Aus.
 9585 Madrid, Spain
 9590 PDI Hilversum, Neth.
 9590 WABC New York, U.S.A.
 9600 GRY London, England
 9600 KCBR Delano, Cal., U.S.A.
 9600 KRCA San Fran., U.S.A.
 9600 Lenjograd, U.S.S.R.
 9605 HPSJ Panama, Pan.
 9605 JKL Tokyo, Japan
 9605 Radio Free Europe, Lisbon, Portugal
 9607 Athens, Greece
 9610 VLV9 Perth, Australia
 9610 ZYCB Rio de Janeiro, Brazil
 9610 LLG Oslo, Norway
 9610 XERQ London, Mex.
 9615 Voice of Amer., Tangier
 9615 VLB9 Shepparton, Aus.
 9615 WRCA New York, U.S.A.
 9618 TIDCR San Jose, C.Rica
 9620 Horby, Sweden (Nov. to Feb. only)
 9620 Paris, France
 9620 ZL8 Wellington, N.Z.
 9625 XEBT Mexico, Mex.
 9625 GWO London, England
 9625 VP4RD Port-au-Spain, Trinidad
 9630 HJKC Bogota, Colombia
 9630 VUD/10 Delhi, India
 9630 Rome, Italy
 9635 Munich, Germany
 9635 Voice of Amer., Tangier
 9640 Accra, Ghana
 9640 West Germany Radio, Cologne
 9640 DZH2 Manila, P.I.
 9640 GVZ London, England
 9645 Karachi, Pakistan
 9645 LLH Oslo, Norway
 9645 TIFC San Jose, C.Rica
 9648 HVJ9 Vtelean City
 9650 Honolulu, Hawaii
 9650 Moscow, U.S.S.R.
 9650 Tangier, Tangier
 9650 WDSI(VOA) Brentwood, N. Y.
 9652 Z1M8 Limassol, Cyprus
 9654 OTC2 Leopoldville, Belgian Congo
 9655 JK12 Nazaki, Belgium
 9656 4VEH Cap-Haitien, Haiti
 9660 EQC Teheran, Iran
 9660 GWP London, England
 9660 VLQ9 Brisbane, Aus.
 9665 HEU3 Bern, Switzerland
 9668 TGNB Guatemala, Guat.
 9670 Munich, Germany
 9670 Voice of Amer., Tangier
 9670 Moscow, U.S.S.R.
 9675 GWL London, England
 9675 JOB3 Tokyo, Japan
 9680 Paris, France
 9680 XEQQ Mexico, Mex.
 9680 VUD Delhi, India
 9680 Moscow, U.S.S.R.
 9680 Voice of America, Tangier
 9680 VLR9/VLH9 Melbourne, Australia
 9685 Paris, France
 9685 WLVO Cincinnati, U.S.A.
 9685 LRA Buenos Aires, Arg.
 9690 GRX London, England
 9690 Moscow, U.S.S.R.
 9690 Singapore, Malaya
 9695 JKM2 Kawaichi, Japan
 9700 GWY London, England
 9700 WDSI New York, U.S.A.
 9700 Sofia, Bulgaria
 9700 Voice of America, Tangier
 9700 WLVO Cincinnati, U.S.A.

Kc. C.L. Location

3700 KCBR Delano, Cal., U.S.A.
 3700 ZYF6 Ft. de France, Mart.
 3700 Moscow, U.S.S.R.
 3710 Dakar, Fr. W. Africa
 3710 YDF6 Djakarta, Indonesia
 3710 Rome, Italy
 3715 Cairo, Egypt
 3716 Moscow, U.S.S.R.
 3717 Radio Free Europe, Ger.
 3720 PRL9 Brussels, Belgium
 3730 French Equatorial Africa
 3730 Nanking, China
 3730 DZH7 Manila, P.I.
 3730 Leipzig, Germany
 3735 H12Z Ciudad Trujillo, D.R.
 3741 CSA27 Lisbon, Portugal
 3743 HC1B Quito, Ecuador
 3745 HC1B (Missionary Station), Quito, Ecuador
 3745 ORU Brussels, Belgium
 3760 CR7BE Lourenco Marques, Moz.
 3764 TGWA Guatemala, Guat.
 3770 London, England
 3770 PRL9 Brussels, Belgium
 3770 PRL4 Rio de Jan., Brazil
 3780 Rome, Italy
 3785 Monte Carlo, Monaco
 3785 GRM London, England
 3833 Budapest, Hungary
 3833 COBL Havana, Cuba
 3835 PRL9 Brussels, Portugal
 3915 GRU London, England
 3966 Brazzaville, Fr. Eq. Africa
 10058 SUV Cairo, Egypt
 10220 PSH Rio de Janeiro, Brazil
 10258 XRR4 Peiping, China
 10700 SDB2 Motala, Sweden
 10727 CSA22 Ponta Delgas, Azores
 10728 Lenjograd, U.S.S.R.
 11650 Peking, China
 11670 Bangkok, Thailand
 11680 HJQC Bogota, Colombia
 11680 GRQ London, England
 11685 Peking, China
 11690 GP5A Panama, Panama
 11700 GVL London, England
 11702 Paris, France
 11705 JOA4 Tokyo, Japan
 11705 SBP Motala, Sweden
 11710 Moscow, U.S.S.R.
 11710 Voice of America, Tangier
 11710 VUD5/7 Delhi, India
 11710 WLVO Cincinnati, U.S.A.
 11714 Z1M7 Limassol, Cyprus
 11715 HE15 Bern, Switzerland
 11718 Athens, Greece
 11720 PRL9 Rio de Janeiro, Brazil
 11720 Radio Portugal
 11720 OTM4 Leopoldville, Belgian Congo
 11720 ORY2 Brussels, Belgium
 11724 HNG Baghdad, Iraq
 11725 COCY Havana, Cuba
 11730 GVV London, England
 11730 KGEI San Fran., U.S.A.
 11730 PH Hanoi, North Viet.
 11730 CEI173 Santiago, Chile
 11735 BE6 Taipei, Formosa
 11735 LK0 Frederikstad, Nor.
 11735 Radio Free Europe, Ger.
 11740 Moscow, U.S.S.R.
 11740 Warsaw, Poland
 11740 WRCA New York, U.S.A.
 11742 CEI174 Santiago, Chile
 11750 GSD London, England
 11755 Radio Portugal
 11755 Moscow, U.S.S.R.
 11760 OLR4B Prague, Czech.
 11760 Voice of America, Tangier
 11760 VLA11/VL12 Shepparton, Aus.
 11760 VUD7/11 Delhi, India
 11764 CR27B Lourenco Marques, Mozambique
 11770 GVV London, England
 11770 YDE/YDF7 Djakarta, Indonesia
 11775 Radio Poland
 11780 BBC London, England
 11780 Moscow, U.S.S.R.
 11780 XEQH Mexico, D.F.
 11780 ZL3 Wellington, N.Z.
 11790 WDSI(VOA) New York
 11790 GVL London, England
 11790 VUD Delhi, India
 11790 WRUL Boston, U.S.A.
 11790 Voice of America, Tangier
 11795 West Germany Radio, Cologne
 11795 YDF3 Djakarta, Indonesia
 11795 WRUL Boston, U.S.A.
 11800 GWH London, England
 11800 Brussels, Belgium
 11810 Moscow, U.S.S.R.
 11810 Radio Sweden (except—Nov. to Febr.)
 11810 Rome, Italy
 11810 VLA11 Shepparton, Aus. (Morning program)
 11815 Warsaw, Poland
 11820 GSN London, England
 11820 XEBR Hermsillo, Mex.
 11825 JK16 Tokyo, Japan
 11825 Moscow, U.S.S.R.
 11825 ZYK3 Recife, Brazil
 11830 FZ54 Saigon, Fr. Indoch.
 11830 Moscow, U.S.S.R.

Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location
11830		Voice of America, Tangier	12175		TFJ Reykjavik, Iceland	15240		VLH15 Melbourne, Aus.	17270		KCBR Delano, Cal., U.S.A.
11830		WBOU(VOA) New York, U.S.A.	14492		Radio Moscow	15240		WLW0 Cincinnati, U.S.A.	17270		Rome, Italy
11830		WDSI(VOA) New York, U.S.A.	14690		PSF Rio de Janeiro, Brazil	15250		Bucharest, Rumania	17270		Voice of America, Tangier
11835		CXA19 Montevideo, Uru.	15050		ETAA Addis Ababa, Eth. U.S.A.	15250		Voice of Amer., Manila, P.I.	17275		Hilversum, Netherlands
11835		Prague, Czechoslovakia	15050		V3USE Forest Side, Mauritius	15250		WLW0 Cincinnati, U.S.A.	17280		VUD/10/11 Delhi, India
11840		VLW11 Perth, Australia	15060		Peking, China	15250		Voice of Amer., Tangier	17280		WBOU New York, U.S.A.
11840		OLRAA Praha, Czechoslovakia	15070		GWC London, England	15260		GS1 London, England	17280		Voice of Amer., Manila, P.I.
11840		LRT Tucuman, Argentina	15085		HVJ Vatican City	15260		Karachi, Pakistan	17284		HER7 Bern, Switzerland
11845		Karachi, Pakistan	15100		CSA39 Lisbon, Portugal	15270		KCBR Delano, Cal., U.S.A.	17290		GSG London, England
11847		Paris, France	15100		Moscow, U.S.S.R.	15270		Munich, Germany	17295		WLW0 Cincinnati, U.S.A.
11850		VLB11 Shepparton, Aus.	15100		EPB Teheran, Iran	15270		WBOU(VOA) New York, U.S.A.	17800		KNBH San Fran., U.S.A.
11850		ORU Brussels, Belgium	15105		KGEI San Fran., U.S.A.	15270		Sverdlovsk, U.S.S.R.	17800		WLW0 Cincinnati, U.S.A.
11850		TGNC Guatemala, Guat.	15105		OAX4X Lima, Peru	15280		Munich, Germany	17800		KRHO Honolulu, Hawaii
11850		VUD11 Delhi, India	15110		GWX London, England	15280		ZL4 Wellington, N.Z.	17800		Stockholm, Sweden
11850		LLK Oslo, Norway	15110		Moscow, U.S.S.R.	15280		Moscow, U.S.S.R.	17800		O1X5 Pori, Finland
11855		DZH9 Manila, Philippines	15120		YCJB Quito, Ecuador	15285		Voice of Amer., Tangier	17804		Rome, Italy
11855		Radio Free Europe, Lisbon, Portugal	15120		Colombo, Ceylon	15285		CRB6 Lourenco Marques, Mozambique	17805		DZ17 Manila, P.I.
11860		GSE London, England	15120		Moscow, U.S.S.R.	15285		WBOU(VOA) New York, U.S.A.	17815		Formosa Radio
11860		KWID San Fran., U.S.A.	15120		Rome, Italy	15285		WRUL Boston, U.S.A.	17815		GSV London, England
11865		CRGRA Luanda, Angola	15120		Warsaw, Poland	15285		LRU Buenos Aires, Arg.	17820		Moscow, U.S.S.R.
11865		HER5 Bern, Switzerland	15125		CSA36 Lisbon, Portugal	15290		VUD5/9 Delhi, India	17825		LLN Oslo, Norway
11870		Munich, Germany	15130		Voice of America, Tangier	15290		Voice of Amer., Tangier	17825		Radio Japan, Tokyo
11870		KNBH San Fran., U.S.A.	15130		WLW0 Cincinnati, U.S.A.	15300		DZH8 Manila, P.I.	17830		WLW0 Cincinnati, U.S.A.
11870		Voice of America, Tangier	15130		KCBR(VOA) Delano, Calif.	15300		GWR London, England	17830		WDSI(VOA) New York, U.S.A.
11870		WRUL Boston, U.S.A.	15130		WBOU Bound Brook, N. J., U.S.A.	15300		Singapore, Malaysia	17835		Karachi, Pakistan
11875		OLRA4C Prague, Czechoslovakia	15135		Radio Japan, Tokyo	15305		HER6 Bern, Switzerland	17840		Radio Sweden
11875		Radio Portugal	15135		PRB23 Sao Paulo, Brazil	15305		RV97 Novosibirsk, U.S.S.R.	17840		Brazzaville, Fr.Eq.Africa
11880		Moscow, U.S.S.R.	15140		GSF London, England	15310		KCBR Delano, Calif.	17840		Moscow, U.S.S.R.
11880		RSB Buenos Aires, Arg.	15140		YDC Jakarta, Indonesia	15310		GSP London, England	17840		VLC12 Shepparton, Aus.
11880		VLG11/VLH11 Melbourne, Aus.	15145		ZYK2 Recife, Brazil	15320		Moscow, U.S.S.R.	17840		HVJ Vatican City
11880		Horby, Sweden	15150		OAX4R Lima, Peru	15320		OLR5B Prague, Czechoslovakia	17850		Paris, France
11880		EHH Mexico, Mex.	15155		CE1515 Santiago, Chile	15325		Rome, Italy	17865		Damascus, Syria
11880		GRE London, England	15155		SBT Motala, Sweden	15330		KGEI San Fran., U.S.A.	17870		CSAA4 Lisbon, Portugal
11880		SBP Stockholm, Sweden	15156		ZYB9 Sao Paulo, Brazil	15330		Sofia, Bulgaria	17890		HCBJ (Missionary Station)
11885		APK5 Bern, Pakistan	15156		VUD5/7 Delhi, India	15330		WLW0 Cincinnati, U.S.A.	21460		KNBH(VOA) Quito, Ecuador
11890		Moscow, U.S.S.R.	15160		VLB15 Shepparton, Aus.	15335		Brussels, Belgium	21470		GSH London, England
11890		GWW London, England	15165		WLW0 Cincinnati, U.S.A.	15335		Karachi, Pakistan	21480		Hilversum, Netherlands
11890		KZFJ Manila, P.I.	15165		ZYN7 Fortaleza, Brazil	15340		Moscow, U.S.S.R.	21490		Paris, France
11890		WBOU New York, U.S.A.	15170		LKY Oslo, Norway	15340		KCBR Delano, Cal., U.S.A.	21500		WRCA New York, U.S.A.
11895		FHE3 Dakar, Fr.W.Af.	15170		TGWA Guatemala, Guat.	15340		Voice of Amer., Tangier	21510		VUD5 Delhi, India
11895		Radio Portugal	15175		Moscow, U.S.S.R.	15345		Athens, Greece	21520		HER8 Bern, Switzerland
11895		Manila, Philippines	15180		GO London, England	15347		LRA Buenos Aires, Arg.	21520		WLW0 Cincinnati, U.S.A.
11900		CE118 Vatarisco, Chile	15180		Moscow, U.S.S.R.	15345		Voice of Amer., Tangier	21530		London, England
11900		CXA10 Montevideo, Uru.	15180		OZH2 Sharmelak, Den.	15350		WRUL Boston, U.S.A.	21540		VLB2 Shepparton, Aus.
11900		HCBJ Calvary Radio Ministry	15190		VUD5/11 Delhi, India	15350		WLW0 Cincinnati, U.S.A.	21550		GST London, England
11900		XEXE Mexico City, Mex.	15190		O1X4 Pori, Finland	15350		VUD8 Delhi, India	21560		Moscow, U.S.S.R.
11900		Rome, Italy	15195		TAK Ankara, Turkey	15352		Radio Luxembourg	21560		Rome, Italy
11910		Budapest, Hungary	15200		Moscow, U.S.S.R.	15360		London, England	21570		VSDI(VOA) New York, U.S.A.
11910		Karachi, Pakistan	15200		VLA15/VLC15 Shepparton, Aus.	15360		Moscow, U.S.S.R.	21580		Horby, Sweden
11915		Radio Netherlands	15205		XESC Mexico, Mexico	15365		ZYC9 Rio de Jan., Brazil	21590		WGEO Schenectady, N.Y.
11915		Damascus, Syria	15205		Voice of America, Tangier	15390		Moscow, U.S.S.R.	21610		WLW0(VOA) Cincinnati, U.S.A.
11915		HCBJ Quito, Ecuador	15210		Munich, Germany	15390		Radio China (Canton)	21620		Colombo, Ceylon
11915		Radio Portugal	15210		GWU London, England	15400		Paris, France	21640		GRZ London, England
11918		BED4 Taipei, Formosa	15210		WBOU(VOA) New York, U.S.A.	15400		Rome, Italy	21650		WLW0 Cincinnati, U.S.A.
11924		ZFS4 Saigon, Vietnam	15210		VLG15 Melbourne, Aus.	15405		PZC Paramaribo, Surinam	21670		LLP Oslo, Norway
11924		GVX London, England	15220		PCJ Hilversum, Neth.	15410		Moscow, U.S.S.R.	21675		GWR London, England
11935		Warsaw, Poland	15220		ZL10 Wellington, N.Z.	15425		Radio Netherlands	21680		VLC21 Shepparton, Aus.
11937		Bucharest, Rumania	15225		JBD3 Kawachi, Japan	15440		Moscow, U.S.S.R.	21690		Voice of America, Tangier
11950		Radio Netherlands	15228		Kemsemsk, U.S.S.R.	15445		Radio Netherlands	21700		VUD10 Delhi, India
11950		YSAX San Salvador, Salv.	15230		GWD London, England	15450		GRD London, England	21710		GSH London, England
11955		GYV London, England	15230		Moscow, U.S.S.R.	15455		Brazzaville, Fr.Eq.Africa	21730		WBOU(VOA) New York, U.S.A.
11960		Moscow, U.S.S.R.	15230		OLRA4 Praha, Czechoslovakia	15460		Madrid, Spain	21730		WBOU(VOA) New York, U.S.A.
11964		Lisbon, Portugal	15230		VLH15 Melbourne, Aus.	17700		GPV London, England	21740		KCBR Delano, Cal., U.S.A.
11970		Brazzaville, Fr.Eq.Africa	15235		WRUL Boston, U.S.A.	17715		GRA London, England	21740		KGEI San Fran., U.S.A.
11972		TIHH San Jose, C.Rica	15235		BED3 Taipei, Formosa	17720		LRA5 Buenos Aires, Arg.	21740		Paris, France
11975		Colombo, Ceylon	15235		JOBS Tokyo, Japan	17730		GVQ London, England	21750		GYT London, England
11980		Moscow, U.S.S.R.	15240		Radio China (Canton)	17750		WRUL Boston, U.S.A.	21750		GSK London, England
11985		CSA32 Lisbon, Portugal	15240		Belgrade, Yugoslavia	17760		WGEO Schenectady, U.S.A.	26080		GSK London, England
11998		CE1180 Santiago, Chile	15240		KRCA San Fran., U.S.A.	17760		VUD Delhi, India			
12040		GRV London, England	15240		Paris, France						
12095		GRV London, England									

Canadian Short-Wave Stations

Listed by Frequency

Abbreviations: Kc., frequency in kilocycles (to change to megacycles, divide by 1000), C.L., call letters

Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location
5970		CBNX St. John's, Nfld.	6130		CHNX Halifax, N.S.	11705		CBFY Montreal, Que.*	15190		CKCX Montreal, Que.*
5970		CKNA Montreal, Que.*	6150		CKRX Winnipeg, Man.	11705		CKXA Montreal, Que.*	15255		CKSR Montreal, Que.*
5990		CHAY Montreal, Que.*	6160		CBUX Vancouver, B.C.	11720		CBFL Montreal, Que.*	15275		CKBR Montreal, Que.*
6005		CFCX Montreal, Que.*	6160		CHAO Montreal, Que.*	11720		CHOL Montreal, Que.*	15320		CKCS Montreal, Que.*
6010		CJCX Sydney, N.S.	6160		CBFR Montreal, Que.*	11720		CHRX Winnipeg, Man.	17710		CHSB Montreal, Que.*
6030		CFVP Calgary, Alta.	6160		CBFP Montreal, Que.*	11760		CBFA Montreal, Que.*	17735		CHRX Montreal, Que.*
6070		CFRR Toronto, Ont.	6160		CBFX Montreal, Que.*	11760		CKRA Montreal, Que.*	17820		CKNC Montreal, Que.*
6080		CKFX Vancouver, B.C.	6160		CHLS Montreal, Que.*	11900		CKEX Montreal, Que.*	17865		CHYS Montreal, Que.*
6090		CBFW Montreal, Que.*	6160		CBFO Montreal, Que.*	11945		CKEX Montreal, Que.*	21600		CKRP Montreal, Que.*
6090		CKOB Montreal, Que.*	6160		CHLD Montreal, Que.*	15090		CKLX Montreal, Que.*	21710		CHLA Montreal, Que.*
			6160		CHLR Montreal, Que.*	15105		CKUS Montreal, Que.*			*Transmitter at Sackville, New Brunswick.
			6160		CHFO Montreal, Que.*	15190		CBFZ Montreal, Que.*			

United States

Frequency-Modulation (FM) Stations

(Territories and possessions follow states) Abbreviations; C.L., call letters, Mc., megacycles (for frequency in kilocycles change decimal point to comma and add two zeros); asterisk (*) indicates educational station

Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.
ALABAMA											
Albertville	WAVU-FM	105.1	Cullman	WFNH-FM	101.1	ARIZONA					
Alexander City	WRFS-FM	106.1	Decatur	WHOS-FM	92.5	Globe	KWJB-FM	100.3	Blytheville	KLCN-FM	96.1
Andalusia	WCTA-FM	98.1	Homewood	WJLN	104.7	Mesa	KTYL-FM	104.7	Ft. Smith	KFPW-FM	94.9
Anniston	WHMA-FM	100.5	Langlet	WRLD-FM	102.9	Phoenix	KELE	95.5	Jonesboro	KBTM-FM	101.9
Birmingham	WAFM	99.3	Mobile	WKRC-FM	99.9		KFCA	88.5		KASU	91.9
Clanton	WKLF-FM	100.9	Talladega	WHTB-FM	97.7						
			Tuscaloosa	WTRC-FM	99.7						
			Tuscaloosa	WUOA	91.7						

Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.	
Raleigh	WKIX-FM	96.1	Stillwater	KAMC-FM	*91.7	Woonsocket	WXCN	101.5	Harrisonburg	WEMC	*91.7	
	WPTF-FM	94.7		KSPI-FM	93.9		WVON-FM	106.3		WSVA-FM	100.7	
	WRAL-FM	101.5	Tulsa	KWGS	*90.5	SOUTH CAROLINA						
Reidsville	WREV-FM	102.1	OREGON						Lynchburg	WWOD-FM	100.1	
Rocky Mount	WEED-FM	92.1	Eugene	KRVM	*91.9	Anderson	WCAC	101.1	Martinsville	WVVA-FM	96.3	
	WFMA	100.7		KULN	96.1	Charleston	WCSC-FM	96.9	Newport News	WGH-FM	97.3	
Salisbury	WSTP-FM	106.3		KWAX	96.1	Columbia	WCOS-FM	97.9	Norfolk	WMTI	*91.5	
Sanford	WWGP-FM	105.5	Grants Pass	KGPO	91.9		WUSC-FM	*89.9	Richmond	WRFC	91.1	
Shelby	WOHS-FM	96.1	Ortech, Oregon	KTEC	98.3	Dillon	WDFC-FM	92.9		WRVA-FM	94.5	
Statesville	WSIC-FM	105.7	Portland	KEX-FM	92.1	Greenville	WDFC-FM	92.5	Roanoke	WRNL-FM	102.1	
Tarboro	WCPS-FM	104.3		KOIN-FM	101.1		WDFC-FM	92.5		WRDY-FM	94.9	
Thomasville	WTNC-FM	98.3		KPFM	97.1	Orangeburg	WDRG-FM	103.7		WROV-FM	103.7	
Winston-Salem	WAIR-FM	93.1		KPOJ-FM	98.7	Rock Hill	WDRG-FM	98.3		WVLS-FM	89.1	
	WSJS-FM	104.1		KQFM	100.3	Seneca	WSNW-FM	98.1	South Norfolk	WFSS	*90.5	
						Spartanburg	WSPA-FM	98.9	Winchester	WRFL	92.5	
OHIO												
Akron	WAKR-FM	97.5	PENNSYLVANIA						TENNESSEE			
	WAPS	*89.1	Allentown	WFMZ	100.7	Bristol	WJPI-FM	96.9	WASHINGTON			
Alliance	WFAH-FM	101.7	Altoona	WVAM-FM	100.1	Greenville	WGRV-FM	94.9	Cheney	KEWC-FM	*89.9	
Ashland	WATG-FM	101.3	Bethlehem	WGPA-FM	95.1	Johnson City	WJHL-FM	100.7	Seattle	KING-FM	98.1	
Ashtabula	WICA-FM	103.7	Bloomsburg	WHLN-FM	106.5	Kingsport	WKPT-FM	98.5		KIRO-FM	100.9	
Athens	WOU1	*91.5	Chambersburg	WCHA-FM	95.9	Knoxville	WBIR-FM	93.3		KISW	99.9	
Balfaire	WTRX-FM	100.5	Du Bois	WCED-FM	102.1		WKCS	*91.1	Spokane	KUOQ	*94.9	
Berea	WBWC	88.3	Easton	WEST-FM	107.9	Memphis	WUOT	*91.9	Tacoma	KREM-FM	92.9	
Bowling Green	WBWB	*88.7	Erie	WEEX-FM	99.9	Nashville	WMCF	99.7		KPCS	90.9	
Canton	WHBC-FM	94.1	Harrisburg	WERC-FM	99.9		WFMB	105.9		KTNT	97.3	
Cincinnati	WCPO-FM	105.1	Hazletown	WHP-FM	97.3					KTOY	*91.7	
	WKRC-FM	101.9	Hazletown	WHFS	*89.3	TEXAS						
	WSAI-FM	102.7	Johnstown	WAZL-FM	97.9	Abilene	KACC-FM	*91.1	WEST VIRGINIA			
Cleveland	KYW-FM	105.7	Lancaster	WARD-FM	92.1	Austin	KHFI	98.3	Beekley	WBKW	99.5	
	WBOE	90.3		WJAC-FM	95.5	Beaumont	KAZZ	95.5	Charleston	WKAZ-FM	97.5	
	WDOCK-FM	102.1		WGAL-FM	101.3	Cedar Hills	KRIC-FM	97.5	Huntington	WHTN-FM	100.5	
	WERE-FM	98.5		WLAN-FM	96.9	Cleburne	KDFW	107.9	Logan	WLOG-FM	103.3	
	WGAR-FM	99.5		WLBR-FM	100.1	Corpus Christi	KDMC	95.5	Martinsburg	WEPN-FM	94.3	
	WJK-FM	100.7		WMBG-FM	99.7	Dallas	KIXL-FM	104.5	Morgantown	WAJR-FM	99.3	
	WJW-FM	104.1	Madisonville	WCAU-FM	98.1		KNER	*88.1	Oak Hill	WOAY-FM	94.1	
Cleveland Hts.	WSRS-FM	95.3	Philadelphia	WFIL-FM	102.1		KRLD-FM	92.5	Parkersburg	WAAM-FM	106.5	
Columbus	WCBE	*90.5		WFLN	95.7		WR-FM	101.3	Wheeling	WKWK-FM	97.3	
	WBNS-FM	97.1		WHAT-FM	96.5	Denton	WR-FM	101.3		WVVA-FM	98.7	
	WCOL-FM	92.3		WHYY	*90.9	El Paso	KVTT	*91.7	WISCONSIN			
	WOSU-FM	94.7		WIBG-FM	94.1	Et. Worth	KDNT-FM	106.3	Appleton	WLFM	*91.1	
	WVCO	94.7		WIP-FM	93.3	Houston	KVOF-FM	88.5	Chilton	WKWV	*89.3	
Dayton	WHIO-FM	99.1		WPEN-FM	102.9		WPBF-FM	96.3	Colfax	WHWC	*88.3	
Delaware	WLSN	*91.1	Pittsburgh	WPWT	*91.7		KPRC-FM	102.9	Delaware	WHAD	*90.7	
Elyria	WEOL-FM	107.3		WRTI-FM	*90.1		KFMK	97.9	Eau Claire	WEAU-FM	94.1	
Findlay	WFIN-FM	100.5		WXPN	*88.9		KTRH-FM	101.1	Greenfield Twp.	WWCF	94.9	
Fostoria	WFOB	90.3		WDXU	91.5		KUHF	91.3	Highland	WHHI	91.3	
Fremont	WFRO-FM	99.3		WFMP	99.7	Lubbock	KSEL-FM	93.7	Highland Twp.	WHSA	*89.9	
Kent	WKSU-FM	*88.1		WKJF	93.7	Nacogdoches	KELS	100.1	Jacksonville	WCLD-FM	99.9	
Lima	WIMA-FM	102.1		WWSW-FM	94.5	Plainview	KHBL	*88.1	Lafayette	WHLA	*90.3	
Marion	WMRN-FM	106.9		WPPA-FM	101.9	San Antonio	KISS	99.5	Madison	WHA-FM	*88.7	
MT. Vernon	WVVO-FM	93.7	Pottsville	WGBI-FM	101.3		KITE-FM	97.3		WISC-FM	98.1	
Newark	WCLT-FM	100.3	Scranton	WUSV	*88.9		KONO-FM	92.9		WFMF	104.1	
Oxford	WMUB	*88.5	Sharon	WPC-FM	102.9		KCMC-FM	98.1	Merrill	WLIN	100.7	
Portsmouth	WPAY-FM	104.1	State College	WDFM	91.1				Milwaukee	WFRM	96.5	
Staubenville	WSTP-FM	103.5	Sunbury	WKOK-FM	91.1	Ephraim	KEPH	*88.9	Racine	WRJN-FM	100.7	
Toledo	WSPD-FM	101.5	Warren	WRRN	92.3	Logan	KVSC	*88.1	Rice Lake	WJMC-FM	96.3	
	WHHE	92.5	Washington	WJPA-FM	104.3	Salt Lake City	KDYL-FM	98.7	Wausau	WHRM	*91.9	
	WTDS	*91.3	Wilkes-Barre	WBRE-FM	98.5		KSL-FM	100.3	Wisc. Rapids	WFHR-FM	103.3	
	WTOD-FM	104.7	Williamsport	WLYC-FM	105.1	UTAH						
Wooster	WVST-FM	104.5	York	WRAK-FM	100.3	Arlington	WARL-FM	105.1	HAWAII			
Youngstown	WKBN-FM	98.9	Providence	WNDW-FM	105.7	Charlottesville	WINA-FM	95.3	Honolulu	KAIM-FM	95.5	
						Crews	WTJU	91.3		KUOH	*90.5	
OKLAHOMA												
Norman	WNAD-FM	*90.9	RHODE ISLAND								KVOK	*88.1
Oklahoma City	KOKH	*88.9	Providence	WPJB-FM	105.1							
Shawnee	KBGC	*89.9		WPFM	95.5							
				WPRO-FM	92.3							

Canadian

Frequency-Modulation (FM) Stations

C.L., call letters, Mc., megacycles (For frequency in Kilocycles, change decimal point to comma and add two zeros)

Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.
Brantford, Ont.	CKPC-FM	92.1		CKLC-FM	99.5		CFRA-FM	93.9		CFRB-FM	99.9
Cornwall, Ont.	CKSF-FM	104.5		CKWS-FM	96.3	Quebec, Que.	CHRC-FM	98.1		CHFI-FM	98.1
Edmonton, Alta.	CFRN-FM	100.3	Kitchener, Ont.	CKCR-FM	96.7	Rimouski, Que.	CJBR-FM	101.5		CJRT-FM	91.1
	CJCA-FM	99.5	London, Ont.	CFPL-FM	95.9	St. Catharines.			Vancouver, B.C.	CBU-FM	105.7
	CKUA-FM	98.1	Montreal, Que.	CBF-FM	95.1	Timmins, N.S.	CKTB-FM	97.7	Verdun, Que.	CKVL-FM	96.9
Ft. William, Ont.	CKPR-FM	94.3		CBM-FM	100.7		CJCF-FM	94.5	Victoria, B.C.	CKDA-FM	98.5
Halifax, N.S.	CHNS-FM	95.1	Oshawa, Ont.	CKLB-FM	93.5		CKGB-FM	94.5	Windsor, Ont.	CKLW-FM	93.9
Kingston, Ont.	CFRC-FM	91.9	Ottawa, Ont.	CBO-FM	103.3	Toronto, Ont.	CBC-FM	99.1	Winnipeg, Man.	CJOB-FM	103.1

United States Television Stations

Listed Alphabetically by Location

(Territories and possessions follow states). C.L., call letters; Chan., channel number; asterisk (*) indicates educational station.

Location	C.L.	Chan.	Location	C.L.	Chan.	Location	C.L.	Chan.	Location	C.L.	Chan.	
ALABAMA												
Andalusia	WAIQ	*2	Tucson	KGUN-TV	9	Eureka	KIEM-TV	3	(Tijuana, Mex.)	XETV	6	
Birmingham	WABT	13		KOLD-TV	13		KVIQ-TV	6	San Francisco	KGO-TV	7	
	WBIQ	*10	Yuma	KVOA-TV	11	Fresno	KFRE-TV	12		KPIX	5	
	WBRC-TV	6		KIVA	11		KJEO	47		KQED	*9	
Decatur	WMSL-TV	23	ARKANSAS							KMNJ-TV	24	
Dothan	WTVY	9	Arkadelphia	KRBB	10	Los Angeles	KABC-TV	7	San Jose	KNTV	11	
Florence	WOWL	15	El Dorado	KFSA-TV	22		KOP	13	San Luis Obispo	KSBY-TV	6	
Mobile	WALA-TV	10	Ft. Smith	KNAC-TV	5		KHJ-TV	9	Santa Barbara	KEY-TV	3	
	WKRG-TV	10	Little Rock	KARK-TV	4		KXNT	2	Stockton	KOVR	13	
Montgomery	WCOV-TV	20		KATH	11		KRCA	4	COLORADO			
	WSFA-TV	12	Pine Bluff	KATV	7	Oakland	KTUU	2	Colorado Springs	KKTV	11	
Murford	WTIQ	*7	Texarkana	KCMC-TV	6	Redding	KVIP-TV	7	Denver	KRDO-TV	13	
ARIZONA												
Phoenix	KOOL-TV	10	Bakersfield	KBAK-TV	29	Sacramento	KBET-TV	10		KBTU	9	
	KPHO-TV	5		KERO-TV	10		KCRA-TV	3		KLZ-TV	7	
	KTVK	3		KHSL-TV	12	Salinas	KSBB-TV	8		KOA-TV	4	
	KVAR	12		XEM-TV	3	San Diego	KFMB-TV	8				
							KFSD-TV	10	WHITE'S RADIO LOG 189			

Location	C.L.	Chan.	Location	C.L.	Chan.	Location	C.L.	Chan.	Location	C.L.	Chan.
Grand Junction	KRMA-TV	*6	Waterloo	KVTV	9	Butte	KXLF-TV	4	Oklahoma City	KETA	*13
Montrose	KTVR	2		KWWL-TV	7	Glendive	KXGN-TV	5		KWTV	9
Pueblo	KREX-TV	5	KANSAS			Great Falls	KFBF-TV	5		WKY-TV	4
CONNECTICUT			Ensign	KTVC	6	Helen	KRTV	3	Tulsa	KOTV	6
Bridgeport	WICC-TV	43	Great Bend	CKCT	2	Missoula	KXLI-TV	12		KTUL-TV	8
Hartford	WHCT	18	Hutchinson	KTVH	12		KMSO-TV	13		KV00-TV	2
	WTIC-TV	3	Pittsburg	KOAM-TV	10	NEBRASKA			Corvallis	KOAC-TV	*7
New Britain	WNBC	8	Topeka	WBW-TV	13	Hastings	KHAS-TV	5	Eugene	KVAL-TV	13
New Haven	WNHC-TV	5	Wichita	KAKE-TV	10	Hay Springs	KOUH-TV	4	Klamath	KOTI	2
Waterbury	WATR-TV	53		KARO-TV	3	Hayes Center	KHPL-TV	6	Medford	KBES-TV	5
DELAWARE			KENTUCKY			Kearney	KHOL-TV	13	Portland	KGW-TV	8
Wilmington	WVUE	12	Lexington	WLEX-TV	18	Lincoln	KOLN-TV	10		KOIN-TV	5
DIST. OF COLUMBIA			Louisville	WAVE-TV	27	Omaha	KUON-TV	*12		KPTV	12
Washington	WMAL-TV	7		WAVE-TV	3		KWTZ	3	Roseburg	KPIC	4
	WRC-TV	4		WHAS-TV	1	Scottsbluff	WOW-TV	6	PENNSYLVANIA		
	WTOP-TV	5		WXL-TV	41		KSTF	10	Altoona	WFBG-TV	10
	WTTG	9		WPSO-TV	6	NEVADA			Erie	WVICU	12
FLORIDA			LOUISIANA			Henderson	KLRI-TV	2	Harrisburg	WSEE-TV	35
Daytona Beach	WESH-TV	2	Alexandria	KALB-TV	5	Las Vegas	KLAS-TV	8		WHP-TV	55
Fort Myers	WINK-TV	*17	Baton Rouge	WAFB-TV	28	Reno	KSHO-TV	13		WTPA	27
Jacksonville	WJCT	11		WBZZ	2		KOLO-TV	8	Johnstown	WARD-TV	56
	WFLA-TV	12	Lafayette	KLFY-TV	10	NEW HAMPSHIRE				WJAC-TV	6
	WMBR-TV	4	Lake Charles	KPLC-TV	7	Manchester	WMUR-TV	9	Lancaster	WGAL-TV	8
Miami	WCKT	4	Monroe	KTAG-TV	25	NEW JERSEY			Lebanon	WLBZ-TV	15
	WPST-TV	10	New Orleans	KNOE-TV	8	NEW MEXICO			Lockhaven	WBZZ-TV	32
	WTHS-TV	*2		KLSE	*13	Albuquerque	KGGM-TV	13	New Castle	WKS-TV	45
	WTVJ	4		WOSU-TV	6		KNME-TV	*5	Philadelphia	WCAU-TV	10
Orlando	WBOB-TV	6		WJMR-TV	20		KOAT-TV	7		WFIL-TV	6
	WLOP-TV	5		WWL-TV	4		KOB-TV	4		WHYY-TV	*35
	WPTV	9		WYES	8		KAYE-TV	6	Pittsburgh	WRCV-TV	3
Palm Beach	WJDM-TV	7	Shreveport	WYES	8		KICA-TV	12		KOKA-TV	2
Panama City	WEAR-TV	3		KTBS-TV	3		KSWB-TV	8		WIII	11
Pensacola	WSUN-TV	38	MAINE			Carlsbad	KWTV	10		WQED	*13
St. Petersburg	WFLA-TV	8	Bangor	WABI-TV	5	Ciovis	KWTV	12	Scranton	WNEP-TV	18
Tampa	WTVT	13	Poland Spring	W-TWO	2	Roswell	KWSV-TV	8		WDAU-TV	22
W. Palm Beach	WEAT-TV	12	Portland	W-TWO	2	NEW YORK			Wilkes-Barre	WBRE-TV	28
GEORGIA			Portland	WCSH-TV	6	Albany	WTEN	10		WLK-TV	34
Albany	WALB-TV	10	Presque Isle	WAGN-TV	8		WTRI	35	York	WNOV-TV	49
Atlanta	WAGA-TV	5	MARYLAND			Binghamton	WINR-TV	40		WSBA-TV	43
	WSB-TV	2	Baltimore	WJZ-TV	13	Buffalo	WNBF-TV	12	RHODE ISLAND		
	WETV	*30		WBAL-TV	11	Carthage	WBEN-TV	4	Providence	WJAR-TV	10
Augusta	WJBF	6		WMAR-TV	2	New York	WBUF	17		WPRO-TV	12
	WRDW-TV	11	Salisbury	WBCT-TV	16		WGR-TV	2	SOUTH CAROLINA		
Columbus	WRBL-TV	4	MASSACHUSETTS			Carthage	WCNY-TV	7	Anderson	WAIM-TV	40
	WTVM	28	Adams	WCOC	19	Elmira	WSEY-TV	18	Charleston	WCSC-TV	5
Macon	WMAZ-TV	13	Boston	WBZ-TV	4		WABC-TV	7		WUSN-TV	2
Savannah	WSAV-TV	3		WGBH-TV	*2		WABD	5	Columbia	WIS-TV	10
Thomasville	WTQC-TV	6		WHDH-TV	5		WCBST-TV	2		WNOK-TV	67
	WCTV	6		WNAO-TV	3		WOR-TV	9	Florence	WBTB	8
IDAHO				WRP	32		WPIX	11	Greenville	WFBZ-TV	4
Boise	KBOI	2	Greenfield	WHY-TV	40		WRCA-TV	4	Spartanburg	WSPA-TV	7
	KIDQ-TV	7	Springfield	WWLP	22	Plattsburg	WPTZ-TV	5	SOUTH DAKOTA		
Idaho Falls	KID-TV	3	MICHIGAN			Rochester	WHYC-TV	10	Florence	KOLO-TV	3
Lawton	KLEW-TV	3	Bay City	WNEM-TV	5		WROC-TV	5	Rapid City	KOTA-TV	3
Twin Falls	KLIX-TV	11	Cadillac	WJIB-TV	13	Schenectady	WVTV	10		KPLO-TV	7
ILLINOIS			Detroit	WTVS	*56	Syracuse	WWRG	6	Reliance	WPCO-TV	4
Bloomington	WBLN	15		WJL-TV	4	Utica	WYSR-TV	3	Sioux Falls	KELO-TV	11
Champaign	WCIA	3	(Windsor, Ont.)	WXVZ-TV	7	NORTH CAROLINA			Chattanooga	WDEF-TV	12
Chicago	WBMM-TV	2	East Lansing	CKLW-TV	9	Asheville	WISE-TV	62		WRGP-TV	3
	WBKB	7	Grand Rapids	WKAR-TV	*60	Charlotte	WLOS-TV	5	Jackson	WTOI-TV	7
	WGN-TV	9	Kalamazoo	W000-TV	8		WUNC-TV	*4	Johnson City	WJHL-TV	11
	WQBO	5	Lansing	WKZO-TV	3		WSDC-TV	9	Knoxville	WATE-TV	6
	WTTW	*11	Marquette	WJIM-TV	6		WTVD	11		WBIR-TV	10
Danville	WDAN-TV	24	Saginaw	WDMJ-TV	8	Durham	WFMY-TV	2	Memphis	WTVK	28
Deatur	WTVP	17	Traverse City	WKNX-TV	57	Greensboro	WNCN-TV	9		WHBQ-TV	13
Harrisburg	WSIL-TV	3		WPBN-TV	7	Greenville	WRAL-TV	5		WNO	*10
Harrisburg	WEEQ-TV	35	MINNESOTA			Raleigh	WRIT-TV	7		WNCN	5
La Salle	WEEK-TV	35	Austin	KMMT	6	Wilmington	WECT	6		WREC-TV	3
Peoria	WEEK-TV	35	Duluth	KDAL-TV	6	Winston-Salem	WSJS-TV	12	Nashville	WLAC-TV	5
	WMBD	31	Duluth	WOSM-TV	6	NORTH DAKOTA				WSIX-TV	6
	WTVH	19	Minneapolis	KMSP	9	Bismarck	KBMB-TV	12		WSM-TV	4
Quincy	WGM-TV	10		WCCO-TV	4		KFYR-TV	2	TEXAS		
Rockford	WRFX-TV	13		WTGN-TV	11	Dickinson	KDIX-TV	2	Abilene	KRBC-TV	9
	WTVQ	39	Rochester	KROC-TV	10	Fargo	WDAY-TV	6	Amarillo	KFDA-TV	10
Rock Island	WHBF-TV	4	St. Paul	KSTP-TV	*2	Grand Forks	KNOX-TV	10		KGNC-TV	4
Springfield	WIGS	20	MISSISSIPPI			Minot	KCJB-TV	13		KVII	7
Urbana	WILL-TV	*12	Columbus	WCBI-TV	4	Valley City	KMOT	10	Austin	KTBC-TV	7
INDIANA			Jacksonburg	WOAM-TV	12	Williston	KXJB-TV	4	Beaumont	KFDM-TV	6
Bloomington	WTTV	4	Jackson	WJTV	9	OHIO			Big Spring	KUMV-TV	4
Elkhart	WSJV-TV	28	Meridian	WLBTV	3	Akron	WAKR-TV	49	Corpus Christi	KRIS-TV	8
Evansville	WFIE-TV	14	Tupelo	WTOK-TV	11	Cincinnati	WCET	*48		KZTV	10
	WEHT	30		WCOG-TV	30		WCPO-TV	9	Dallas	KRLD-TV	4
	WTVW	7	MISSOURI				WKRC-TV	12	El Paso	WFAA-TV	8
Ft. Wayne	WANE-TV	15	Cape Girardeau	KFVS-TV	12		WLVN-TV	12		KELP-TV	13
	WKJG-TV	33	Columbia	KOMA-TV	8		WSOK-TV	54		KTSM-TV	9
	WPAT	21	Hannibal	KHQA-TV	7	Cleveland	KYW-TV	3	(Ciudad Juarez, Mex.)	XEJ-TV	5
Indianapolis	WFBM-TV	6	Jefferson City	KRCG-TV	13		WEWS	5	Ft. Worth	KFJZ-TV	11
	WLWI	13	Joplin	KOC-TV	12		WJW-TV	8		WBAP-TV	5
	WISH-TV	8	Kansas City	KCMO-TV	5	Columbus	WBNS-TV	10		KBGT-TV	4
	WFAM-TV	59		KMBC-TV	9		WLWC-TV	4	Harlingen	KPRC-TV	2
	WLBC-TV	49		WDFW-TV	4		WOSU-TV	*34	Houston	KGUU-TV	11
	WNDU-TV	16		WDTN-TV	10	Dayton	WHIO-TV	7		KTRK-TV	13
	WSBT-TV	22		WLVN-TV	10		WLW-D	2		KUHT	*8
Terre Haute	WTHI-TV	10		WMA-TV	35	Lima	WIMA-TV	35	Laredo	KHAD-TV	8
IOWA				WSTV-TV	9	Stuebenville	WSTV-TV	9	Lubbock	KCBD-TV	11
Ames	WOI-TV	5		WSPD-TV	13	Toledo	WSPD-TV	13		KDUB-TV	13
Cedar Rapids	KCRG-TV	9		WTVN-TV	6	Youngstown	WFMJ-TV	21	Lufkin	KPRE-TV	2
	WMT-TV	2		WVTV-TV	6		WKBN-TV	21	Midland	KMID-TV	2
Davenport	WOC-TV	6		WVTV-TV	6		WKST-TV	45	Odessa	KOSA-TV	7
Des Moines	KRNT-TV	8		WVTV-TV	6		WHIZ-TV	18	Port Arthur-Beaumont	KPAC-TV	4
	KRNT-TV	8		WVTV-TV	6	OKLAHOMA			San Angelo	KCTV	8
	WHO-TV	13		WVTV-TV	6	Ada	KTEN	10	San Antonio	KCOR-TV	41
Fort Dodge	KQT-TV	21		WVTV-TV	6	Ardmore	KVSD-TV	12		KRNT-TV	5
Mason City	KGLO-TV	3		WVTV-TV	6		KOCO-TV	5		KONO-TV	12
Ottumwa	KTVQ	3		WVTV-TV	6	Lawton	KSWO-TV	7		WOAI-TV	4
Sioux City	KTIV	4		WVTV-TV	6						

Location	C.L.	Chan.	Location	C.L.	Chan.	Location	C.L.	Chan.	Location	C.L.	Chan.
Sweetwater	KPAR-TV	12	Roanoke	WTVR	6	Oak Hill	WOAY-TV	4	U. S. TERRITORIES AND POSSESSIONS		
Temple	KCEN-TV	6		WDBJ-TV	7	Parkersburg	WTAP	15	ALASKA		
Texarkana	KCMC-TV	6		WLSL-TV	10	Wheeling	WTRF-TV	7	Anchorage	KENI-TV	2
Waco	KLTV	7	WASHINGTON						Fairbanks	KFAR-TV	2
Weslaco	KRGV-TV	5	Bellingham	KVOS-TV	12	WISCONSIN			Juneau	KTVF	11
Wichita Falls	KFDX-TV	3	Ephrata	KBAS-TV	16	Eau Claire	WEAU-TV	13		KINY-TV	8
	KSVD-TV	8	Kennewick	KTRX-TV	25	Green Bay	WBAY-TV	2	GUAM		
			Pasco	KEPR-TV	19	La Crosse	WKBT	5	Agana	KUAM-TV	8
UTAH			Seattle	KCTS	9	Madison	WHA-TV	21	HAWAII		
Salt Lake City	KSL-TV	5		KING-TV	5		WISC-TV	3	Hilo	KHBC-TV	9
	KTVT	4		KIRO-TV	7		WKOW-TV	27	Honolulu	KGMB-TV	9
	KUED	7		KOMO-TV	4		WMTV	33		KHVV-TV	13
	KUTV	2	Spokane	KHQ-TV	6	Marinette	WMBV-TV	11		KMIA-TV	2
VERMONT				KREM-TV	2	Milwaukee	WISN-TV	12		KULA-TV	4
Burlington	WCAX-TV	3		KXLY-TV	4		WMVJ-TV	4		KMAU	3
VIRGINIA			Tacoma	KTNT-TV	11		WTMJ-TV	19		KMAU	3
Bristol	WCYB-TV	5	Yakima	KTVW	13	Wausau	WSAU-TV	7	Wailuku	KMVI-TV	12
Hampton	WVEC-TV	15		KIMA-TV	29	Whitefish Bay	WITI-TV	6	PUERTO RICO		
Harrisonburg	WSVA-TV	3	WEST VIRGINIA						Mayaguez	WORA-TV	5
Lynchburg	WVLA-TV	13	Bluefield	WHIS-TV	6				Ponce	WSPR-TV	7
Norfolk	WTAP-TV	3	Charleston	WCHS-TV	8	Casper	KTWO-TV	2	San Juan	WAPA-TV	4
	WAVY-TV	10	Clarksburg	WBOY-TV	12	Cheyenne	KSPR-TV	6		WIPR-TV	6
	WTOV-TV	27	Huntington	WHTN-TV	13	Riverton	KFBC-TV	5		WKAQ-TV	2
Petersburg	WXEX-TV	8		WSAZ-TV	3		KWRB-TV	10			
Richmond	WRVA-TV	12									



Canadian Television Stations

Listed Alphabetically by Location

Abbreviations: C.L., call letters; Chan., channel number.

Location	C.L.	Chan.	Location	C.L.	Chan.	Location	C.L.	Chan.	Location	C.L.	Chan.
ALBERTA			LABRADOR			ONTARIO			PRINCE EDWARD ISLAND		
Calgary	CHCT-TV	2	Goose Bay	CFLA-TV	8	Barrie	CKVR-TV	3	Charlottetown	CFCY-TV	13
Edmonton	CFRN-TV	3				Elliot Lake	CKSO-TV-I	3			
Lethbridge	CJLH-TV	7	NEW BRUNSWICK			Hamilton	CHCH-TV	11	QUEBEC		
Medicine Hat	CHAT-TV	6	Moncton	CKCW-TV	2	Kapuskasing	CFCL-TV-I	3	Estouart	CJES-TV-I	70
Red Deer	CHCA-TV	6	Saint John	CHSJ-TV	4	Kingston	CKWS-TV	11	Jonquiere	CKRS-TV	12
BRITISH COLUMBIA			NEWFOUNDLAND			Kitchener	CKCO-TV	13	Montreal	CBFT	2
Kamloops	CFCR-TV	4	Argentia	CJOX-TV	10	London	CFPL-TV	10		CBMT	6
Kelowna	CHBC-TV	2	St. John's	CJON-TV	6	North Bay	CKGN-TV	10	Quebec	CFQM-TV	4
Penticton	CHBC-TV	13	Stephenville	CFSN-TV	8	Peterborough	CHEX-TV	12		CKMI-TV	5
Vancouver	CBUT	2				Ottawa	CBOFT	9		CJBR-TV	3
Vernon	CHBC-TV	7	NOVA SCOTIA			Port Arthur	CFOT	2	Rimouski	CKRN-TV	4
Victoria	CHEK-TV	6	Halifax	CBHT	3	Sault Ste. Marie	CJIC-TV	2	Rouyn	CHLT-TV	7
MANITOBA			Sydney	CJCB-TV	4	Sudbury	CKSO-TV	5	Three Rivers	CKTM-TV	13
Brandon	CKX-TV	5				Timmins	CKFL-TV	6	SASKATCHEWAN		
Winnipeg	CBWT	3				Toronto	CBLT	6	Prince Albert	CKBI-TV	5
						Windsor	CKLW-TV	9	Regina	CKCK-TV	2
						Wingham	CKNX-TV	8	Saskatoon	CFQC-TV	8
									Swift Current	CFJB-TV	5

Watch for the SCIENCE EXPERIMENTER—

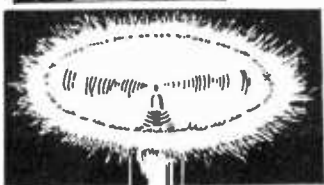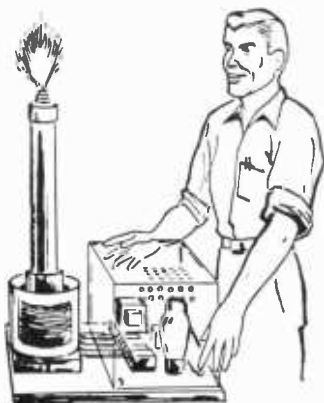

HERE it is, a collection of science project articles for amateur scientists, hobbyists, educators and experimenters of every age—but especially valuable to younger adults, in school or out, now engaged in the study of some phase of modern science. The scope of the projects in this book for which detailed, show-how plans and step-by-step text are given embraces the entire area of the physical sciences . . . And in addition to the two-score projects included in this book—projects which can be used as points of departure for Science Fair entries—there are also authoritative, informative general articles on varied aspects of scientific research and on practical application and demonstration of scientific theory. If you cannot obtain a copy of the SCIENCE EXPERIMENTER (Handbook No. 557) from your newsdealer after October 30th, let us know and we will see that he is supplied. Or send 75¢ direct to Science and Mechanics, Dept. 5559, 450 East Ohio Street, Chicago 11, Illinois, and we will fill your order.

➔ **On Sale October 30th**

GET YOUR First Class Commercial F.C.C. LICENSE IN 12 WEEKS!

Our FREE booklet, *Careers in Electronics*, gives complete details of our training—either home study or resident classes. This booklet tells how we prepare you, quickly, to pass F.C.C. examinations. For your free copy of this booklet, clip the coupon below and mail it to the Grantham School nearest you.

**WASHINGTON
D.C.**

Grantham School of Electronics
821-19th Street, N.W.
Washington 6, D.C.

**HOLLYWOOD
CALIF.**

Grantham School of Electronics
1505 N. Western Avenue
Hollywood 27, California

**SEATTLE
WASH.**

Grantham School of Electronics
408 Marion Street
Seattle 4, Washington

MAIL TO SCHOOL NEAREST YOU

(Mail in envelope or paste on postal card)

To: **GRANTHAM SCHOOL OF ELECTRONICS**

Desk E-8 • Washington • Hollywood • Seattle

Gentlemen

Please send me your free booklet telling how I can get my commercial F.C.C. license quickly. I understand there is no obligation and no sales-man will call.

Name _____ Age _____

Address _____

City _____ State _____

I am interested in Home Study, Resident Classes

F.C.C. LICENSE—THE KEY TO BETTER JOBS

An F.C.C. *commercial* (not amateur) license is your ticket to higher pay and more interesting employment. This license is Federal Government evidence of your qualifications in electronics. Employers are eager to hire *licensed* technicians.

WHICH LICENSE FOR WHICH JOB?

The **THIRD CLASS** radiotelephone license is of value primarily in that it qualifies you to take the second class examination. The scope of authority covered by a third class license is extremely limited.

The **SECOND CLASS** radiotelephone license qualifies you to install, maintain and operate most all radiotelephone equipment except commercial broadcast station equipment.

The **FIRST CLASS** radiotelephone license qualifies you to install, maintain and operate every type of radiotelephone equipment (except amateur) including all radio and television stations in the United States, its territories and possessions. This is the highest class of radiotelephone license available.

GRANTHAM TRAINING PREPARES YOU

The Grantham Communications Electronics Course prepares you for a **FIRST CLASS** F.C.C. license, and it does this by **TEACHING** you electronics. Each point is covered simply and in detail, with emphasis on making the subject easy to understand. The organization of the subject matter is such that you progress, step-by-step, to your specific objective—a first class F.C.C. license.

CORRESPONDENCE OR RESIDENCE CLASSES

Grantham training is available by correspondence or in resident classes. Either way (residence or correspondence), we train you quickly and well—NO previous training required. A beginner may qualify for his first class license in as little as 12 weeks.

HERE'S PROOF...

that Grantham students prepare for F.C.C. examinations in a minimum of time. Here is a list of a few of our recent graduates, the class of license they got, and how long it took them:

	License	Weeks
Henry M. Best, 1003 Vermont St., Fremont, N.C.	1st	11
Harold V. Jones, P.O. Box 705, Alamogordo, N. Mex.	1st	13
Michael F. Aperio, 916 Townsend St., Chester, Pa.	1st	12
Norman R. Cook, 130 Olive St., Neodeska, Kan.	1st	12
Antone Mello, 68 Union Street, Nantucket, Mass.	1st	10
John Ward, 407 E. Cowden Ave., Midland, Texas	1st	10
F. T. Verga, 538-7th Street, Buffalo, N.Y.	1st	12
Philip J. Hooks, 4825 N. Capitol, N.W., Washington, D.C.	1st	12

THREE COMPLETE SCHOOLS: To better serve our many students throughout the entire country, Grantham School of Electronics maintains three complete schools—one in Washington, D.C., one in Hollywood, Calif., and one in Seattle, Wash. All schools offer the same rapid courses in F.C.C. license preparation, either home study or resident classes.

Get your First Class Commercial F.C.C. License in 12 weeks by training at



GRANTHAM SCHOOL OF ELECTRONICS

Hollywood Division
1505 N. Western Ave.
Hollywood 27, Calif.

Washington Division
821-19th Street, N.W.
Washington 6, D.C.

Seattle Division
408 Marion Street
Seattle 4, Wash.

CHRISTY'S *Complete* ELECTRONIC COURSE

Learn TELEVISION, RADIO, RADAR, SONAR, ELECTRONICS

Only CTS offers you *COMPLETE* training in all phases of Electronics. Why be satisfied with less? The new Christy Shop-Method Home Training makes learning interesting and easy. You learn Radar, Sonar, Electronics, Radio, Television. No previous experience needed. You learn by working with actual equipment. Makes learning fun. Speeds your progress. Helps you understand quicker and remember longer.

You get comprehensive training starting with your first CTS lesson! The complete knowledge CTS provides you with, gives you a broader knowledge, a greater understanding which will mean more jobs and a higher income for you for the rest of your life.

HOME LABORATORY SENT! 19 TRAINING INSTRUMENTS INCLUDED

With CTS *COMPLETE* Home Training Course, you receive a Home Laboratory to assemble, use and keep for years of peak performance. You receive a Multi-Tester, Oscillator, Signal Tracer, Oscilloscope, Signal Generator, Electronic Timer, Regenerative Radio, Giant-size Television Receiver (optional) as well as many other valuable electronic devices. With these you will be able to make hundreds upon hundreds of exciting experiments.

EARN WHILE YOU LEARN! EARN \$5.00—\$6.00 PER HOUR

Or *MORE* while still studying! Almost from the very first you receive training that enables you to repair radios and television sets for friends and neighbors. To install and service electronic computers, communication equipment, protective equipment for police and fire departments, etc., etc.

FREE BOOK—SAMPLE LESSONS SENT

Get all there is to know about the Christy *COMPLETE* Electronic Course in Radio-Television-Radar-Sonar, etc. A complete, colorful, illustrated book on Electronics sent without obligation.

Also, we will send you Two sample lessons showing how the new CTS Shop-Method Home Training Course will train you for making big money in your spare time and for building a bright future for yourself.

CHRISTY TRADES SCHOOL, Dept. T-409, 3214-16 W. Lawrence Ave., Chicago 25

SIGN, MAIL FOR THREE BOOKS

Christy Trades School, Dept. T-409, 3214-16 W. Lawrence Ave., Chicago 25, Ill.




Gentlemen:

Please send me, without cost or obligation, two *FREE* lessons and the new 24-Page illustrated book telling all about the CTS Master Shop Method Home Training Course in Radar, Sonar, Television, Radio and Electronics, and the many opportunities this new field offers.

Name..... Age.....

Address

City..... Zone... State.....

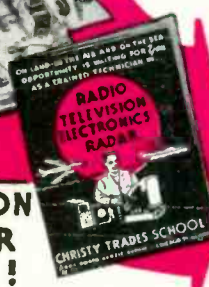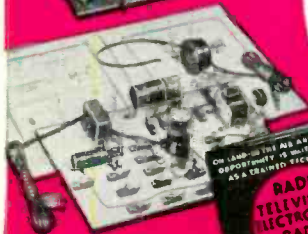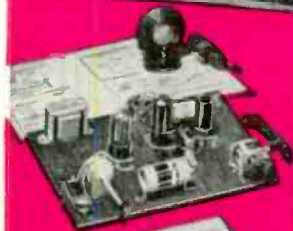


**MAIL COUPON
TODAY FOR
CATALOG !**

Learn Radio-Television

Servicing or Communications by Practicing at Home in Spare Time

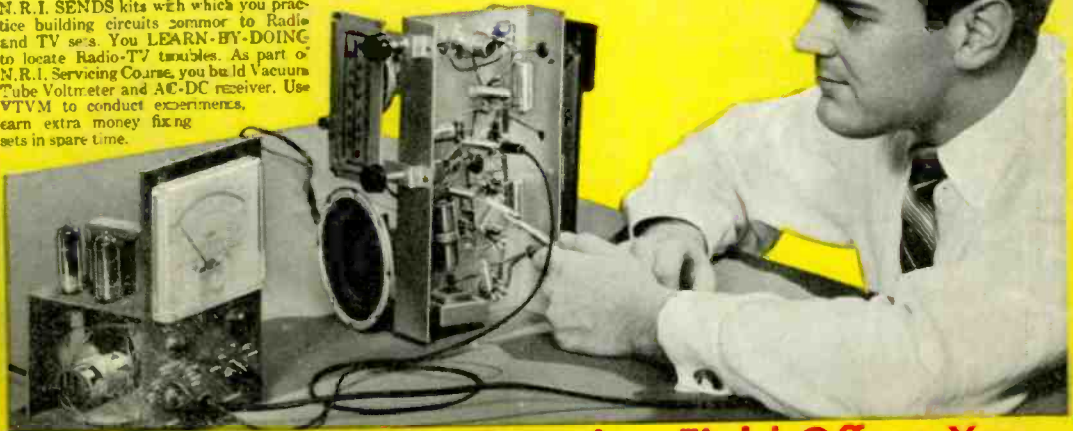N.R.I. SENDS kits with which you practice building circuits common to Radio and TV sets. You LEARN-BY-DOING to locate Radio-TV troubles. As part of N.R.I. Servicing Course, you build Vacuum Tube Voltmeter and AC-DC receiver. Use VTVM to conduct experiments. Earn extra money fixing sets in spare time.



RADIO-TV BROADCASTING (see above) offers important positions as Operators and Technicians. **RADIO-TV SERVICING Technicians** (see below) needed in every community. Their services are respected, their skill appreciated.



Fast Growing Field Offers You Good Pay, Success, Bright Future



J. E. SMITH
founder

Bigger than ever and still growing fast. That's why Radio-TV has special appeal to ambitious men not satisfied with their job and earnings. More than 4,000 Radio and TV stations. More than 150 million home and auto Radios, 40 million TV sets. Color TV promises added opportunities. For the trained man, there are good jobs, bright futures in Radio-TV Servicing or Broadcasting. Training PLUS opportunity is the ideal combination for success. So plan now to get into Radio-TV. The technical man is looked up to. He does important work, gets good pay for it. Radio-Television offers that kind of work. NRI can supply training quickly, without expense of going away to school. Keep your job while training. You learn at home in your spare time. NRI is the **OLDEST** and **LARGEST** home study Radio-TV school. Its methods have proved successful for more than 40 years.

Added Income Soon - \$10, \$15 a Week in Spare Time

Soon after enrolling, many NRI students start to earn \$10, \$15 a week in spare time fixing sets. Some pay for their training and enjoy extra luxuries this way. Some make enough to start their own Radio-TV shops. NRI training is *practical*—gets quick results. Easy to understand, well illustrated lessons teach you basic principles. And you LEARN-BY-DOING by practicing with kits of equipment which "bring to life" things you study.

Find Out What NRI Offers

NRI has trained thousands for successful careers in Radio-TV. Study fast or slow—as you like. Diploma when you graduate. Mail coupon now. Paste it on a postcard or mail in envelope. **ACTUAL LESSON FREE.** Also 64 page catalog that shows opportunities, shows equipment you get. Cost of NRI courses low. Easy terms. **NATIONAL RADIO INSTITUTE, Dept. 8HB3, Washington 16, D. C.**

N.R.I. TRAINED THESE MEN FOR SUCCESS



"I was repairing Radios by 10th Eason. Now have good TV job." **M. R. LINDEMUTH,** Fort Wayne, Ind.



"Doing spare time repairs on Radio and TV. Soon servicing full time." **CLYDE HIGGINS,** Waltham, Mass.

"I had a successful Radio repair shop. Now I'm Engineer for WHPE." **V. W. WORKMAN,** High Point, N.C.



"There are a number of NRI graduates here. I can thank NRI for this job." **JACK WAGNER,** Lexington, N. C.



VETERANS Approved Under G. I. Bills

SEND FOR BOTH FREE

National Radio Institute
Dept. 8HB3, Washington 16, D. C.

Mail me Sample Lesson and 64-Page Catalog FREE. (No salesman will call. Please write plainly.)

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

Accredited Member National Home Study Council

