


RADIO-TV EXPERIMENTER

OCTOBER-NOVEMBER 75c

**WHITE'S
RADIO
LOG** 
AM-FM STATIONS
WORLD-WIDE
SHORT-WAVE LISTINGS!

2 GREAT NOVICE PROJECTS:


The step-up
transmitter 
that starts you
toward your
general ticket!

T-R electronic
switch allows
listening 
as you send!
Page 47



*ANTENNA
TUNER
PAGE 45*

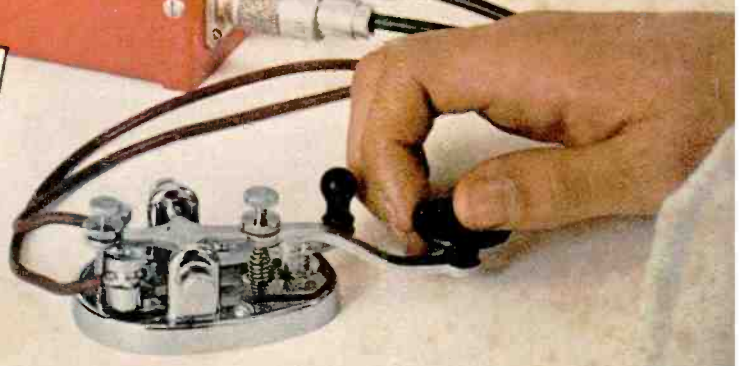BUILD
\$7.50 AUDIO
DISTORTION METER
LOUDSPEAKER
FROM A SHOE BOX



More electronics value for your money!

Save up to 50% with EICO Kits and Wired Equipment.


Whether you're looking for the fun and economy of building quality kits or you want ready-to-use factory-wired equipment — before you buy, examine carefully.

Whatever your interest — hi-fi, CB, ham, test instruments or

automotive electronics — compare EICO with anybody else.

The more critical you are, the more you'll see for yourself that your best buy is EICO. See EICO at your local dealer.

EICO
KITS & WIRED

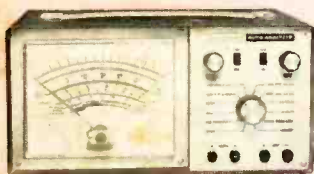

NEW EICO 888 Solid State Engine Analyzer Kit \$44.95 Only!

Now you can tune-up, troubleshoot and test your own car or boat.

Keep your car or boat engine in tip-top shape with this completely portable, self-contained, self-powered universal engine analyzer. Completely tests your total ignition/electrical system. The first time you use it — just to tune for peak performance — it'll have paid for itself. (No tune-up charges, better gas consumption, longer wear) 7 instruments in one, the EICO 888 does all these for 6V and 12V systems; 4, 6 & 8 cylinder engines:

- Checks starter
- Sets engine idle and automatic transmission shift points
- Detects dwell angle variations and distributor wear
- Checks voltage regulator
- Checks alternator and generator's current and voltage outputs
- Finds open or shorted condensers

- Detects condition of point surfaces
- Checks ignition coil and distributor
- Finds poor or open ground connections
- Checks alternator diodes
- Checks headlights, pilot lamps, horns, starter relays, fuses, accessories
- Substitutes ignition capacitor
- Determines battery charge/discharge rate

- Measures spark output & leakage
- Checks engine timing and power balance

Now you can always know your engine's efficiency — keep it in top shape yourself! The EICO 888 comes complete with a comprehensive Tune-up and Trouble-shooting Manual including RPM and Dwell angle for over 40 models of American and Foreign cars. The Model 888 is an outstanding value factory-wired at \$59.95.



Model 460 Wideband Direct-Coupled 5" Oscilloscope. DC-4.5mc for color and B&W TV service and lab use. Push-pull DC vertical amp., bal. or unbal. input. Automatic sync limiter and amp. \$89.95 kit, \$129.50 wired.



New Model 712 Sentinel 12. Dual Conversion 5-watt CB Transceiver. Permits 12-channel crystal-controlled transmit and receive, plus 23-channel tunable receive. Incorporates adjustable squelch & noise limiter, & switches for 3.5 watt P.A. use, spotting, & Part 15 operation. Transistorized 12VDC & 117VAC dual power supply. \$99.95 wired only.



Model ST70 70-Watt Integrated Stereo Amplifier. Best buy of highest ranked stereo amplifiers according to independent testing. \$99.95 kit, \$149.95 wired. ST40 40-Watt Integrated Stereo Amplifier. \$79.95 kit, \$129.95 wired. ST97 Matching FM MPX Stereo Tuner. \$89.95 kit; \$139.95 wired.



Model 232 Peak-to-Peak VTVM. A must for color or B&W TV and industrial use. 7-non-skip ranges on all 4 functions. With Uni-Probe. © \$29.95 kit, \$49.95 wired.



New Model 753 The one and only SSB/AM/CW Tri-Band Transceiver Kit. "The best ham transceiver buy for 1966" — Radio TV Experimenter Magazine. 200 watts PEP on 80, 40 and 20 meters. Receiver offset tuning, built-in VOX, high level dynamic ALC, solid state VFO. Unequaled performance, features and appearance. Sationally priced at \$189.95 kit, \$299.95 wired.

FREE 1966 CATALOG

EICO Electronic Instrument Co., Inc. RTVE-3
131-01 39th Ave., Flushing, N.Y. 11352

Send me FREE catalog describing the full EICO line of 200 best buys, and name of nearest dealer. I'm interested in:

- test equipment ham radio
 stereo/hi-fi Citizens Band radio
 automotive electronics

Name _____

Address _____

City _____

State _____ Zip _____

Over 3,000,000 EICO instruments now in use! Preferred by engineers, scientists, technicians and students.

Let I.C.S. equip you for success in radio-TV-electronics—

with professional equipment!



Brand-new "Electronic Laboratory," now being offered for the first time, can help you land in this big money-making field—FAST!

Here's an opportunity for you to turn spare time into cold cash, or begin a whole new career—in a field where the rewards have never been greater.

And you *don't* need previous experience to do it!

International Correspondence Schools has just developed a new I.C.S. Electronic Laboratory you can construct in your own home. Includes series of training kits, plus the new I.C.S. VTVM—the professional quality vacuum tube voltmeter shown here. With it comes complete course instruction combining all the fundamentals with practical knowledge you can apply at once. And best of all, you build your own professional test instrument!

I.C.S. instruction gets you going with equipment you can really use!

A famous manufacturer of nationally known electronic testing equipment worked closely with I.C.S. to develop the Electronic Laboratory and the VTVM itself. Everything you get is geared to increase your skill and knowledge step by step. Until finally, you've completed a precision testing

unit you can use for practically any kind of experimentation, design or servicing work.

Here's how I.C.S. instruction works. You begin with basic study lessons. Texts are clearly worded and easy to follow. At the same time, you "act out" what you learn with simple experiments. Then, in 3 easy stages, you assemble your own precision testing unit. Throughout, your instructor gives you expert, professional help. You learn at home, in spare time, as fast as ability permits.

Coupon brings full details on your future in this fast-growing field!

Make up your mind right now to find out how I.C.S. training in Radio-TV-Electronics can pay off for *you*. See how it can help you cash in on the tremendous demand for men skilled in installation, maintenance and servicing of radios, TV sets, hi-fis, computers, automation systems and a host of other space-age devices. Clip and mail the coupon below. You'll receive 3 valuable *free* booklets—including sample lesson. They'll show how you can land in this big-money field *fast!*

Coupon brings 3 valuable FREE booklets. MAIL IT TODAY!

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 3049, Scranton, Penna. 18515

(In Hawaii: P.O. Box 418, Honolulu. In Canada: I.C.S. Canadian, Ltd. In other countries: I.C.S. World, Ltd.)

Please rush me your new 64-page booklet "ElectronICS" which answers the most often-asked questions about preparing for an electronics career. Also send me "How to Succeed," and a sample I.C.S. lesson. I have indicated my field of interest below.

- | | | | | |
|---|---|---|---|---|
| <input type="checkbox"/> Electronic Fundamentals | <input type="checkbox"/> Hi-Fi/Stereo & Sound Systems | <input type="checkbox"/> Electronic Principles for Automation | <input type="checkbox"/> Industrial Electronics Engineering | <input type="checkbox"/> Industrial Electronics Telephony |
| <input type="checkbox"/> Electronic Instrumentation | <input type="checkbox"/> General Electronics | <input type="checkbox"/> Semiconductor-Transistor Circuits | <input type="checkbox"/> FCC Radiotelephone Licenses | <input type="checkbox"/> Other (please specify) _____ |
| <input type="checkbox"/> Computer Fundamentals | <input type="checkbox"/> Electronics Technician | | | |
| <input type="checkbox"/> Radio-TV Servicing | | | | |

Name _____ Age _____

Address _____

City _____ State _____ Zip Code _____

Occupation _____ Employed by _____

Working Hours _____ A.M. to _____ P.M. Convenient payment plan _____ Training Programs for Industry _____

I am a member of U.S. Armed Forces. Send me facts about special low rates.

RADIO-TV EXPERIMENTER

Cover Photo
by Leonard Heicklen

**NOW THERE ARE 90 RADIO
SHACKS COAST TO COAST!**

Oct.-Nov. 1966 CONTENTS/INDEX ☆Cover Highlights	Feature	Theory	Construction	Ham/CB/SWL	Audio/Hi-Fi	AM/FM/TV	Test Bench	Related Subjects
Workbench Tips.....	37	•	•	•			•	
Antenna Antics.....	38	•		•				•
☆Instant Hamming Transmitter... 39			•	•				
IC in Table Radio.....	44	•				•		
Antenna Tuner for Receivers.....	45		•	•	•		•	
☆Transmit/Receive Switch.....	47		•	•				
Case of the Broadcasting Tooth... 51		•	•					•
TV Commercial Killer.....	53		•	•			•	
House Wiring to Add Fixtures.....	57	•		•				•
☆The THD Tester.....	62		•	•	•		•	
☆Talking Shoe Box Speaker.....	65				•			
Electronic Space Puppets.....	67	•						•
Lab Check—RCA Stereo Simulator.	71	•	•	•		•		
Lab Check—Heathkit Color TV.....	73							
Erecting a TV Tower.....	75		•	•				
One Too Many (BCB) Pirates.....	81	•					•	•
Shotgun TV Repairman.....	83						•	
13-Meters, the Coming Band.....	87	•	•	•				
Digital Circuit Tracer.....	89		•	•				•
Propagation Forecast.....	92	•	•					
Electronic Roulette.....	95		•	•				•

WHITE'S RADIO LOG, Vol. 46, No. 3—Page 101

Departments • Positive Feedback 6 • CB Column 10 • Bookmark 14
• New Products 18 • Ask Me Another 27 • Literature Library 120

ARIZONA
PHOENIX — 3005 East Thomas Rd.

CALIFORNIA
ANAHEIM — 507 East Kotella Ave.
BAKERSFIELD — 1308 19th St.
LA HABRA — 1511 West Whittier Blvd.
LONG BEACH — 5676 Atlantic Ave.
LOS ANGELES:
Downey — Stonewood Shop. Ctr.
Ladera Shop. Ctr. — 3305 Cantinela Ave.
Mission Hills — 1919 Sepulveda Blvd.
Reseda — 19368 Victory at Tampa
Torrance — 22518 Hawthorne Blvd.
West Covina — 2516 East Workman Ave.
West L. A. — Pico Blvd. at Overland
DACLAND (San Leandro) — Bay Fair Shop. Ctr.
SACRAMENTO — 500 Fulton Ave.
SAN BRUNO — 481 El Camino Real
SAN DIEGO (La Mesa) — Grosmont Shop. Ctr.
SANTA ANA — Bristol Plaza Shop. Ctr.

COLORADO
DENVER:
799 South Santa Fe Dr.
Westland Shopping Center

CONNECTICUT
HAMDEN — Hamden Mart. Shop. Ctr.
MANCHESTER — Manchester Shop. Parkade
NEW HAVEN — 230 Crown St.
NEW LONDON — New London Shop. Ctr.
STAMFORD — 28 Highland Plaza Rd.
WEST HARTFORD — 38 So. Main St.

GEORGIA
ATLANTA:
Greenbriar Shopping Center
No. DeKalb Shopping Center

ILLINOIS
CHICAGO — Evergreen Plaza at 95th St.

KANSAS
WICHITA — Parklane Shopping Center

MAINE
PORTLAND — Pine Tree Shop. Ctr.

MARYLAND
LANGLEY PARK — Hampshtr.-Langley Ctr.

MASSACHUSETTS
BOSTON:
187 Washington St.
594 Washington St.
110 Federal St.
GRAINTREE — South Shore Plaza
BROCKTON — Westgate Mall
BROOKLINE — 736 Commonwealth Ave.
CAMBRIDGE — Fresh Pond Shop. Ctr.
FRAMINGHAM — Shoppers' World
LOWELL — Central Shop. Plaza
SAUELIS — N. E. Shop. Ctr.
WEST SPRINGFIELD — Century Shop. Ctr.
WORCESTER — Lincoln Plaza

MINNESOTA
MINNEAPOLIS — 1121 Nicollet Ave.
ST. PAUL — 473 North Snelling

MISSOURI
ST. LOUIS:
1123 Pine St. (Walter Ashe Div.)
South County Shopping Center.
Northland Shopping Center

NEW HAMPSHIRE
MANCHESTER — 1247 Elm St.

NEW MEXICO
ALBUQUERQUE — 8318 Lomas, N. E.

NEW YORK
BINGHAMTON (Vestal) — Vestal Shop. Plaza
BUFFALO (Cheerale) — Transtown Shop. Ctr.
NEW YORK — 1128 Ave. of the Americas
SCHENECTADY (Retteriam) — Shoppers Ctr.
SYRACUSE:
507 Erie Blvd. East.
Fairmont Fair Shop. Ctr.

OHIO
CINCINNATI — 852 Salfiton Ctr.

OKLAHOMA
OKLAHOMA CITY — Mayfair Shop. Ctr.
TULSA — 2730 South Harvard

OREGON
PORTLAND — 1928 N.E. 42nd St.

PENNSYLVANIA
PHILADELPHIA:
2327 G. Cotten Ave., Roosevelt Mall
1159 Walnut St.
PITTSBURGH — 309 So. Hills Village

RHODE ISLAND
PROVIDENCE — 355 Reservoir Ave.
EAST PROVIDENCE — Shoppers' Town

TENNESSEE
MEMPHIS — Southland Mall

TEXAS
ABILENE — 2910 North First St.
ARLINGTON — Collins at Park Row
AUSTIN — Hancock Shopping Center
BROWNSVILLE — 847 S. E. Elizabeth St.
DALLAS:
Madallion Center
125 Wynwood Village
Plymouth Park Shop. Ctr.
FORT WORTH:
1515 So. University Dr.
960 East Berry St.
3524 Denton Highway
2615 West 7th St.

HOUSTON:
7900 Katy Rd.
8438 Gulf Freeway
322 Northline Mall
Bellaire — 4759 Bissonnet

MIDLAND — South "99" Meta Drive

SAN ANTONIO:
150 Wonderland Shop. Ctr.
504 S.W. Military Drive
SHERMAN — 1620 Highway 75 North
WACO — 1016 Austin Ave.

UTAH
SALT LAKE CITY — Cottonwood Mall

VIRGINIA
ARLINGTON — Parkington Shop. Ctr.
VIRGINIA BEACH — Pembroke Mall Shop. Ctr.

WASHINGTON
SEATTLE:
2028 Third Ave.
837 N. E. 110th St.
Burien Plaza

UNUSUAL BARGAINS — AT 90 RADIO SHACK STORES!

PILOTS! GI's! VHF FANS!



**Aircraft/AM
RADIO**

Exclusive at
Radio Shack!

21⁹⁵

Our famous "Jetstream" tunes VHF 108-135
MC, AM 535-1605 KC. 10 transistors. #12-626

**'REALISTIC' SWITCHABLE
STEREO/MONO HEADSET**

- For Audio, CB,
Language Labs!
- It's Ours Alone!

6⁹⁵

Feather-light 1 1/2 oz. under-chin
8Ω dynamic. Stereo-mono switch.




33-196

**WE'RE FAMOUS FOR
STOP WATCHES!**

- Swiss Accuracy!
- 7 J. Sports Model!

9⁹⁹

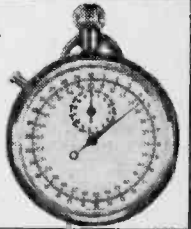Outer—1/10 sec. to 30 secs.
Inner—15 min. Start/stop crown.
Zero reset. 63-636



**FE-103 4" ACOUSTIC
SUSPENSION SPEAKER**

*This Is The Best
Little One Yet!*

7⁹⁵

30-17,000 cps, 8 ohms, FREE
system plans. 40-1197.



**NEW SUPERHET-6
WALKIE TALKIE**

Receive-Transmit 1 Mile or More!

2 FOR 29⁹⁵

21-1139

Chromed die-cast case! The
Realistic TRC-1A is a rugged
2-way CB radio with Ch. 11
crystals, batteries, earphone.



**5 "DUKES OF
DIXIELAND" STEREO
LP SPECIAL!**

ALL
5 **\$8**
FOR

We bought 5 different "Dukes"
stereo records by Audio Fidel-
ity and packaged them as a
set. Compare at \$15 to \$20!
Minstrel Time; On Campus;
Mardi Gras; Circus Time; Up
The Mississippi. 16-25,000 cps
demo quality stereo! 50-5893.

Check Coupon Below for Your

**FREE 1967
RADIO SHACK
CATALOGS!**

One full year of catalogs and bargain
bulletins! Special purchases, closeouts and
audio, CB, electronic parts exclusives!



CLIP... FILL IN and MAIL TODAY!

Send to: Radio Shack Corporation
730 Commonwealth Ave., Boston, Mass. (Eastern Customers)
1515 So. University Dr., Ft. Worth, Tex. (Western Customers)

R/TV-1066

- | | | |
|---|---------------------------------------|-------------------------------------|
| <input type="checkbox"/> Aircraft Radio | <input type="checkbox"/> 5 LP Records | <input type="checkbox"/> Stop Watch |
| <input type="checkbox"/> Walkie Talkie | <input type="checkbox"/> Headphones | <input type="checkbox"/> Speaker |
| <input type="checkbox"/> Send me FREE 1967 Radio Shack Catalogs | | |

(Add \$1 to merchandise order to cover postage and handling.)


Name

Street

City


State

Zip

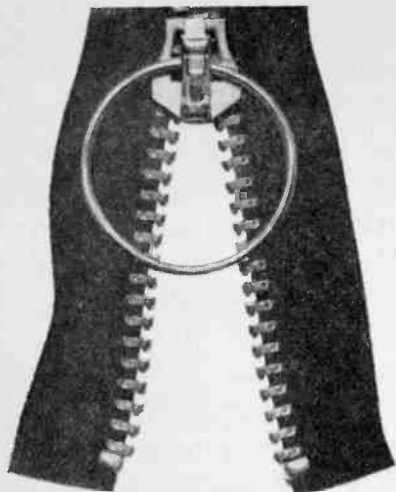

Zip through Scott's new solid state FM stereo tuner kit in one afternoon

Four to six hours! That's all you need to zip through Scott's new LT-112 FM stereo tuner kit. Start after lunch . . . enjoy superb stereo at dinner. ■ Scott solid state circuitry is the key to the LT-112's superior performance. Costly silicon transistors give performance unapproached by any other kit on the market. The LT-112 is kit-brother to Scott's best-selling 312 solid state stereo tuner, of which Audio said, ". . . one of the finest tuners anywhere." ■ Your LT-112 arrives with all critical circuitry pre-wired, pre-tested, pre-aligned, and mounted on heavy-duty printed circuit boards. Scott's exclusive life-size, full-color construction book details every step . . . makes perfect wiring almost automatic. ■ You'd never believe a kit so easy to build could be so packed with features. Built into the LT-112 is a new Scott invention . . . the Tri-modulation meter, used for a Signal Strength Indicator, Zero Center Indicator, and Alignment Meter. ■ See your Scott dealer today, and pick up an LT-112 tuner kit . . . \$179.95 plus one enjoyable afternoon will net you a lifetime of listening pleasure.

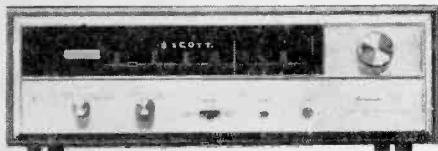

SCOTT®

For complete information on Scott's kits & components write:
H. H. Scott, Inc., 111 Powdermill Road,
Maynard, Mass. Dept. 565-10

Export: Scott International, Maynard, Mass. Cable HIFI.
Prices slightly higher west of Rockies. Prices and specifications subject to change without notice.

OCT.-NOV. 1966



RADIO-TV EXPERIMENTER

Dedicated to America's Electronics Experimenters

JULIAN M. SIENKIEWICZ WA2CQL/KMD4313	<i>Editor</i>
RICHARD A. FLANAGAN	<i>Managing Editor</i>
ELMER C. CARLSON KOD1752	<i>Technical Editor</i>
EUGENE F. LANDINO	<i>Art Editor</i>
ANTHONY MACCARRONE	<i>Art Director</i>
IRVING BERNSTEIN	<i>Cover Art Director</i>
BARBARA GABRIEL	<i>Art Associate</i>
JUDITH ANDERSON	<i>Art Associate</i>
JIM CAPPELLO	<i>Advertising Manager</i>
LEONARD F. PINTO	<i>Production Director</i>
CARL BARTEE	<i>Production Manager</i>
HELEN GOODSTEIN	<i>Assistant Production Manager</i>
CLIFF SHEARER	<i>Promotion Director</i>
JOSEPH DAFFRON	<i>Group Executive Editor</i>

President and Publisher

B. G. DAVIS

Executive Vice-President and Assistant Publisher

JOEL DAVIS

Vice-President and Editorial Director

HERB LEAVY, KMD4529

RADIO-TV EXPERIMENTER, Vol. 21, No. 2 (#806), is published bi-monthly by SCIENCE & MECHANICS PUBLISHING CO., a subsidiary of Davis Publications, Inc. Editorial, business and subscription offices: 505 Park Ave., New York, N.Y. 10022. One-year subscription (six issues)—\$4.00; two-year subscription (12 issues)—\$7.00; and three-year subscription (18 issues)—\$10.00. Add \$1.00 per year for postage outside the U.S.A. and Canada. Advertising offices: New York, 505 Park Ave., PL 2-6200; Chicago, 520 N. Michigan Ave., 527-0330; Los Angeles, 1709 W. 8th St., 213-483-5317; Atlanta, Pirnie & Brown, 3108 Piedmont Rd., N.E., 404-233-6729; Long Island, Len Osten, 9 Garden Street, Great Neck, N.Y., 516-487-3305. Southwestern advertising representative: Jim Wright, 4 N. Eighth St., St. Louis, CH 1-1965.

EDITORIAL CONTRIBUTIONS must be accompanied by return postage and will be handled with reasonable care; however, publisher assumes no responsibility for return or safety of manuscripts, art work, or photographs. All contributions should be addressed to the Editor, Radio-TV Experimenter, 505 Park Avenue, New York, New York 10022

Second class postage paid at New York, New York and at additional mailing office. Copyright 1966 by Science and Mechanics Publishing Co.

KEEP PACE WITH SPACE AGE! SEE MANNED MOON SHOTS, SPACE FLIGHTS, CLOSE-UP!

AMAZING SCIENCE BUYS

for FUN, STUDY or PROFIT

FREE! FREE!
SEND FOR GIANT 148
PAGE CATALOG "HP"
SEE BELOW!

ATTENTION, JUNIOR SPACEMEN!

NEW PARACHUTE—EQUIPPED ROCKET & SPACE CAPSULE SOAR TO 600 FEET



Blast off and watch this amazing space-age toy soar with a tremendous surge of power up to 600 ft. At top of flight rocket and capsule disengage and float fully to earth each supported by its own parachute. Fully controlled—11 time delays to choose from. You launch again and again with straight up or slanting launches. Safe to use too—no chemicals, explosives. Extra strong rubber sling provides power. You just set the controls and release rocket from its launching pad with your foot. Capsule and parachute, rocket body and parachute, launching pad, sling and instructions.

Stock No. 70,845-HP \$3.50 Postpaid

Handymen, Hobbyists, Homeowners! INGENIOUS NEW VACUUM BASE Makes Tools and Appliances Portable

Now move all kinds of normally bolted-down devices from place to place. Machined top surface of Vacuum Base drilled to securely hold vice, miller boxes, drills, reflectors, gages, measuring devices, food choppers and other home appliances. Base also handily adapted for mounting camera, binocular or telescope to car window. Bottom plate of heavy neoprene attaches securely (by vacuum) vertically, horizontally, even upside down to linoleum, metal, porcelain, formica, glass, etc. Unit resists 50 to 75-lb. force parallel to base, 200-lb. force perpendicular to base. Ruggedly constructed of cast aluminum. Gray baked enamel finish. Top surface measures 2 3/4" x 3 3/4". Overall size 5" x 4 1/4" x 2" high.



Stock No. 60,567-HP \$3.00 Postpaid

BARGAIN PRICE—WAR SURPLUS

COLLIMATOR AND INFINITE LIGHT SOURCE

Expensive surplus gun sight orig. cost Gov't. about \$100. Was essentially a collimator or source of infinite light. Many uses for experimenters—research labs. Contains ring and dot reticle, 2 1/2" achromatic lens, silvered reflector bulb, 3 3/4" x 2 1/2" reflector glass plate. Bulb operates on 14V, can be converted to 110V or inexpensive transformers are available. Convenient holes for easy mounting. Sturdily built unit meas. 3 3/4" x 5 3/4" x 2 3/4".

Stock No. 70,774-HP \$9.95 Postpaid

160V Transformer for Light Source.

Stock No. 60,521-HP \$3.75 Postpaid

BATTERIES GUARANTEED RECHARGEABLE FOR 5 YEARS

Use these remarkable space-age Nickel-Cadmium batteries in flashlights, portable radios, toy or flash guns. Obsolete all others! Low-cost kit includes compact, highly efficient battery charger and 2 "D" size Ni-Cd batteries guaranteed rechargeable to full power for 5 yrs. Power output remains constant—doesn't fade away as with lead-acid cells. Durable, black plastic charger 5 3/4" x 3" x 1 3/4" dp. plugs into standard wall outlet. 3" x 1 3/4" "D" or "C" size cells. Completely charges 1 "D" or "C" size batteries in 1 1/2 hrs. Light shows when unit is charging—will not overcharge.

Stock No. 60,591-HP \$9.95 Postpaid

Stock No. 60,592-HP—(Charger only) \$5.98 Postpaid

Stock No. 60,593-HP—(Two "D" Cells only) \$5.98 Postpaid

BINOCULAR-TO-CAMERA HOLDER

Will Fit Any Camera

For Exciting Telephoto Pictures

Bring distant objects 7 times nearer with a 35-mm camera. Create neighborhood sensation. Great backyard fun. Exciting beach attraction. Blow up with vacuum cleaners or auto air hose. Sturdy enough for play; all other uses with reasonable care (can be punctured by sharp objects). Filled with helium (available locally) use balloons high in the sky to attract crowds, advertise store sale, announce fair openings, etc. Amateur meteorologists use balloons to measure cloud heights, wind speed, temperature, pressure, humidity at various heights. Photographers can utilize for low-cost aerial photos. Recent Gov't surplus of heavy, black, neoprene rubber.

Stock No. 70,223-HP \$11.50 Postpaid

"Balls of Fun" for Kids . . . Traffic Stoppers for Stores . . . Terrific for Amateur Meteorologists . . .

SURPLUS GIANT WEATHER BALLOONS


At last . . . available again in big 8-ft. diameter. Create neighborhood sensation. Great backyard fun. Exciting beach attraction. Blow up with vacuum cleaners or auto air hose. Sturdy enough for play; all other uses with reasonable care (can be punctured by sharp objects). Filled with helium (available locally) use balloons high in the sky to attract crowds, advertise store sale, announce fair openings, etc. Amateur meteorologists use balloons to measure cloud heights, wind speed, temperature, pressure, humidity at various heights. Photographers can utilize for low-cost aerial photos. Recent Gov't surplus of heavy, black, neoprene rubber.

Stock No. 60,568-HP \$2.00 Postpaid

ORDER BY STOCK NUMBER—OPEN A/C. TO BARRINGTON—MONEY BACK GUARANTEE

EDMUND SCIENTIFIC CO., BARRINGTON, NEW JERSEY 08007

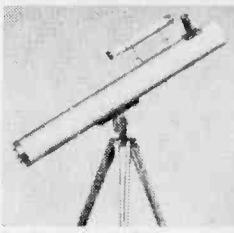See the Stars, Moon, Planets Close Up! 3" ASTRONOMICAL REFLECTING TELESCOPE



60 to 180 Power—Famous Mt. Palomar Type! An Unusual Buy! Assembled—Ready to use! You'll see the Rings of Saturn, the fascinating planet, Mars, huge craters on the Moon. Phases of Venus. Star Clusters. Moons of Jupiter in detail. Galaxies! Equatorial mount with lock on both axes. Aluminized and overcoated 3" diameter high-speed f/10 mirror. Telescope comes equipped with a 60X eyepiece and a mounted Barlow Lens, giving you 60 to 180 power. Low-cost accessory eyepiece available for higher powers. An Optical Finder Telescope, always an essential, is also included. Sturdy, hardwood, portable tripod. FREE with Scope:

—Valuable STAR CHART plus 272 page "HANDBOOK OF HEAVEN" plus "HOW TO USE YOUR TELESCOPE" BOOK.

Stock No. 85,050-HP \$29.95 Postpaid

4 1/4" Reflecting Telescope—up to 270 Power
Stock No. 85,105-HP \$84.50 F.O.B.

SUPERB 6" REFLECTOR TELESCOPE
Up to 576 Power. Equatorial mount and Pedestal Base
Stock No. 85,086-HP \$199.50 F.O.B.

MAKE YOUR OWN POWERFUL ASTRONOMICAL TELESCOPE



Kit contains fine annealed pyrex mirror blank, abrasives, diagonal mirror and eyepiece lenses. You build instruments ranging in value from \$75.00 to hundreds of dollars.

Stock No.	Diam.	Mirror Thickness	Price
70,003-HP	4 1/4"	3/4"	\$ 7.50 ppd.
70,004-HP	6"	1"	11.95 ppd.
70,005-HP	8"	1 1/2"	19.50 ppd.
70,006-HP	10"	1 3/4"	30.75 ppd.
70,007-HP	12 1/2"	2 1/2"	59.95 ppd. f.o.b. Barrington

Fascinating Toy Adaptation of Binary Digital Computer BEAT "DR. NIM" IN ANCIENT GAME:

Not easy, but fun for all! Thrilling for youngsters. Challenging for adults. Teaches computer fundamentals without need for mathematical ability. To play, release 1 to 3 marbles to roll down plastic game board through series of flip-top channels. How you SET flip-tops to begin and path of travel for each marble determines path of succeeding marbles. All plays predictable. Now DR. NIM automatically plays 1, 2, or 3 marbles. If you can make the last marble you win! Game great for playroom and parties, year-round fun. Durable red and white plastic 11 1/4" x 12 1/2" x 1 1/2". 24-p. instruction booklet.

Stock No. 70,816-HP \$2.98 Postpaid

Brand New, Quick-Charge, Industrial Surplus NICKEL-CADMIUM BATTERY

Unparalleled Value

For the first time a 6-volt, light-weight nickel-cadmium battery in stainless steel, strap type casing. 4-amp hour capacity. Almost unlimited life—thousands of discharge cycles with minute deterioration—charges fully in approx. 1 hr. with Edmund charger kit. Just a few drops of water per year provide full maintenance. Hundreds of uses for hobbyists, amateur photographers, campers, model builders, etc. Unequaled for rechargeable lanterns; cycle scooters, and boat lights; portable fluorescent and ultra-violet lights; electronic flash units. Battery requires minimum of electrolyte; is sealed to prevent loss; delivers nearly 100% of output at below freezing temperatures compared to 50% by lead-acid batteries. No corrosive fumes under any stage of recharge. Can't be damaged by accidental charge in reverse (but not recommended). Stud type terminals on top 1 3/4" apart marked for polarity; 6/32 thread, nuts and lock-washers. 6 1/2" x 4 1/4". Wt. 2 lbs. 12 ounces.

Stock No. 70,776-HP \$15.00 Postpaid

CHARGER KIT FOR 6-VOLT BATTERY. Charges in approx. 1 hr. Shuts off automatically, attaches to Stock No. 70,776 battery case. Includes transformer, ballast resistors, charger circuit board, mounting hardware, 8-ft. cord, plug switch, assembly instructions.

Stock No. 70,807-HP \$8.00 Postpaid

ONE 1.2 VOLT NICKEL-CADMIUM CELL
Stock No. 40,798-HP \$3.95 Postpaid

MAIL COUPON for FREE CATALOG "HP"

Edmund Scientific Co., Barrington, N. J. 08007
Completely New 1966 Edition. 148 pages.
Nearly 4500 Unusual Bargains.
Please rush Free Giant Catalog-HP.

Name

Address

City


State

Zip



the **Mercury** Model 501
COMPONENT SUBSTITUTOR
 the instrument acclaimed by
 servicemen, engineers and
 school shops now available in a
wire-it-yourself KIT!

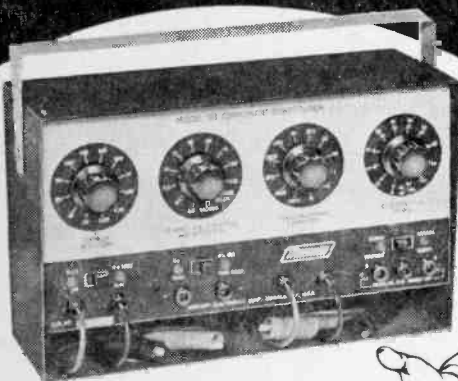step-by-step illustrated instructions
 make the Model 501 easy-to-build



Substitutes for
 any one of
 over 80
 component values

Will substitute
 up to 4 different
 components at
 the same time

A surge protector
 switch prevents arc-
 ing, sparking, or heat-
 ing of electrolytics

Electrolytics
 are
 discharged
 automatically

places a
 complete
 range of components
 at your fingertips
 for fast substitution

No longer do you have to handle crumpled parts... solder and unsolder components as you troubleshoot a set. With a twist of a knob you can set the 501 to any electronic components you want and need... Substitutes for Carbon Resistors — Power Resistors — Capacitors — Electrolytics — Crystal Diodes — Selenium Power and Silicon Power Rectifiers.

Model 501K Kit **\$25.95** Net
 Model 501 Wired **\$39.95** Net

Write for complete catalog of kits and
 wired instruments — and name of
 nearest distributor.

Mercury ELECTRONICS CORP

315 Roslyn Road, Mineola, N.Y. 11501
 Export: Morhan Exporting, 458 Broadway, N.Y.C. 10013
 Canada: William Cohen Corp.



POSITIVE FEEDBACK

JULIAN M. SIENKIEWICZ, EDITOR
 WA2CQL/KMD4313

■ Nine-foot flames shooting forth from the oxygen mask of a seriously ill hospital patient illuminated a "bizarre" accident caused by a simple short circuit. At Peter Bent Brigham Hospital in Boston, two patients with "life-endangering illness" were breathing through respirator devices when a nurse moved a floor lamp for a better look.

Faulty insulation in the lamp allowed current to flow into the lamp's metal base. Poor design of the respirator created an all-metal pathway running from a caster in the base up to the body of the instrument, along a spring inside one of the air hoses, through a valve and along a set-screw to the wire that connected the unit to the electrical ground. When the lamp base came into contact with the caster, the current in the lamp flowed through the respirator and heated the spring to "glowing red." The oxygen-rich atmosphere in the hose ignited instantly.

The result—a flame shot about three to nine feet from the face of the respirator. The room was dark and filled with sparks, smoke and fumes.

The patients were wheeled safely out the room. The investigation that followed revealed that the lamp had not one but three breaks in its insulation. In addition, it turned out that several polarized sockets had been improperly wired, which would have created "an intolerable shock hazard" for any patient on whom more than one instrument were being used.


Can It Happen in Your Home? Hospitals buy the very best of equipment and employ maintenance men to keep their electrical equipment in top shape. Yet, disasters do happen endangering the very lives doctors are trying to save. Hospitals have their problems but, remember, they are safer than your home. Don't take our word for it, check it out yourself.

Start today! Check all electrical appliances for defective power cords. Inspect lamps for loose fitting sockets. Are you using too many

(Continued on page 8)

Why solve electronics problems the old-fashioned pencil and paper way?

This free booklet shows a faster way.

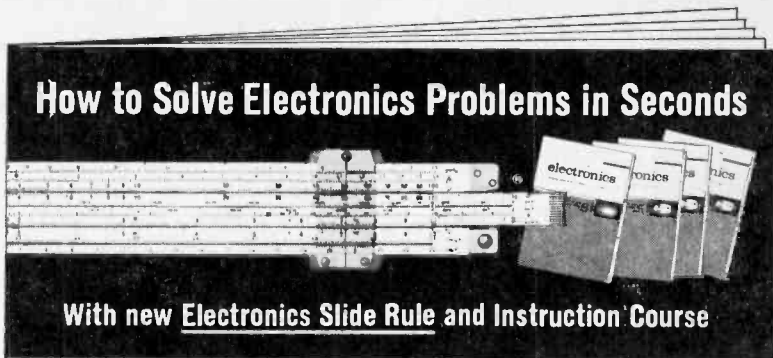

IT JUST DOESN'T MAKE SENSE! A complicated calculation can be solved by a computer in milliseconds. But a relatively simple problem in reactance is usually worked out the old-fashioned pencil-and-paper way...and takes one or two minutes.

Now there is a better way. You can solve many electronics problems in 20 seconds or less without doing any figuring at all. Our exclusive new, specially-designed electronics slide rule does the figuring for you.

If you would like to learn more about this remarkable slide rule, we will send you without cost or obligation the 12-page illustrated booklet shown above. You will see close-ups of the new inverse "H" scale that solves resonant frequency problems... the special 2π scale you'll use for inductive or capacitive reactance problems... and the amazing Decimal Locator Scales that show *exactly* where to place the decimal point in your answers.

You'll also learn about the special 4-lesson home study course which accompanies the slide rule. This course teaches you to use the special scales so you can "whiz" through the toughest problems.

Worth \$50 -

Costs Less Than \$25

People in electronics tell us that our Slide Rule and Course is worth at least \$50. Yet we offer it for less than \$25. Why? Our reason is simple: we are looking for people in

electronics who are ambitious to improve their skills... and who know that this will require more training. If we can *attract* you with the low price of our slide rule and course—and *impress* you with its quality—you are more likely to consider Cleveland Institute of Electronics when you decide you could use more electronics training.

Meanwhile, we can help you right now, especially if your work involves reactance, resonance or inductance problems. Send today for the booklet about our Electronics Slide Rule and Course. It costs you nothing. And it can open your eyes to what *Radio-Electronics* called "a whole new era in quick calculations."

JUST MAIL COUPON for this free booklet. Or just send your name and address on a postcard to the address below.

Acclaimed by Editors, Educators

"It opens a whole new era of quick calculations. Even if you never had a slide rule in your hands before, the four-lesson AUTO-PROGRAMMED™ instruction course leads you from simple calculations right through resonance and reactance problems with hardly a hitch."

WAYNE LEMONS,
Radio-Electronics

"Why didn't someone think of this before? ... the slide rule saved me time the very first day. The 'refresher' course is a marvel of clarity. I couldn't help being amazed at how many standard formula functions I was performing the hard way."

OLIVER P. FERRELL, Editor,
Popular Electronics

"I was intrigued by the 'quickie' electronics problem solutions. The special scales should be of decided value to any technician or engineer. Your slide rule is a natural."

JOSEPH J. DeFRANCE,
Head of Electrical Technology Dept.,
New York City Community College

CIE Cleveland Institute of Electronics
1776 E. 17th St., Dept EX-102, Cleveland, Ohio 44114

Cleveland Institute of Electronics

1776 East 17th Street, Cleveland, Ohio 44114

Please send me without charge or obligation your booklet describing the CIE Electronics Slide Rule and Instruction Course. **ALSO FREE** if I act at once: a handy pocket-size Electronics Data Guide.

Name _____ (please print)

Address _____

City _____ State _____ Zip _____



Accredited Member National Home Study Council
A Leader in Electronics Training... Since 1934

EX-102

POSITIVE FEEDBACK

extension cords and are these cords in good condition? Peep into the fuse box—make sure no overated fuse or penny is being used. Check that AC outlets do not overheat and make a positive grab when plugs are inserted.

There is much you can do to make your home safe from an electrical disaster. Start now. the lights just went out. . . .

Keeping an Eye on Us. Tiros VII, the world's most traveled shutterbug, has celebrated its third birthday doing what comes naturally. Launched June 19, 1963, from Cape Kennedy, Tiros VII has traveled more than one-half-billion miles. has made more than 16,500 trips around the earth and has returned more than 125,000 television pictures of the earth's cloud formations, storms, hurricanes and typhoons from its 500-mile orbit. Its cameras still are fully operational. Tiros VII, like all its predecessors and successors, was built by RCA's Astro-Electronics Division, Princeton, N. J., under the technical direction of the NASA Goddard Space Flight Center located at Greenbelt, Maryland.

The other five orbiting Tiros/Essa weather satellites are Tiros VIII launched 36 months ago; Tiros IX, the first polar orbiting, wheel-oriented weather satellite launched January 22,

1964, and Tiros X launched July 1, 1965. The first Tiros Operational Satellite, Essa 1, launched February 3, 1966, and Essa 2, launched February 28, 1966, now provide daily global weather observation.


Twelve Tiros satellites in a row have been orbited successfully and have operated well beyond their mission requirements in what has been termed as "the nation's most successful unmanned space program." They have returned more 750,000 weather photos in more than six years of operation and have traveled about 6 billion miles. Four of the spacecraft have had a useful life of more than one year, with a fifth, Tiros X, approaching that mark.

In addition, the U. S. Weather Bureau, as principal user of Tiros information, has been able to depend upon the satellites for the advanced report of major storms brewing in remote parts of the globe. Since 1962, not a day has passed without the Weather Bureau being able to obtain Tiros pictures. As a result Tiros is the first spacecraft used daily on an operational basis in the performance of a public service by the U. S. Government. We will now devote the remainder of this column to a discussion on Russian successes in the space-weather arena. . . . ■

TELEX

FOR QUALITY

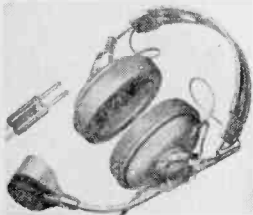The quality of Telex headsets has become well known to hams over the last twenty-five years. Here are three Telex headsets that deliver the kind of top grade performance that hams expect from Telex—




MAGNA-TWIN

For absolute maximum intelligibility under difficult QRM conditions. . . Super-comfort foam cushions. . . Rugged, moisture-proof magnetic drivers give broad response, excellent sensitivity. . . Sturdy construction of high impact plastic.



TELESET

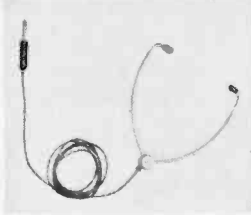Lightweight, economy version of the famous Magna-Twin. . . High performance, shock-proof Magna-Twin drivers. . . Designed especially for ham requirements.



MONOSET


Feather-light at 1.2 oz. . . Eliminates headset fatigue. . . Sound from replaceable driver is fed directly into your ears through adjustable tone arms. . . Telex quality construction assures reliability.

Write for descriptive literature today.



TELEX/Acoustic Products
COMMUNICATIONS ACCESSORIES

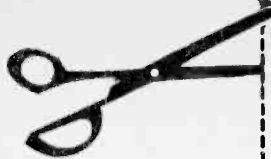Dept. 9F 3054 Excelsior Blvd. • Minneapolis 16, Minn.



SPECIAL OFFER from the famous Gernsback Electronics Book Club, an affiliate of **RADIO-ELECTRONICS Magazine**. For 10 years the Club has helped men in electronics get ahead and stay ahead in this fast-changing field. See how it can help you . . .

Gernsback Library Inc., Electronics Book Club
Dept. X, 154 West 14th Street, New York, N.Y. 10011

Enroll me in the Electronics Book Club and send me the **TWO-HANDBOOK SET: How to Fix Transistor Radios and Printed Circuits**. Bill me only 99¢ plus shipping. If not pleased, I may return both books in 10 days and forget the matter.

As a member, I need accept as few as 4 additional books a year—and may resign any time after purchasing them. All books will be described to me in advance, every other month, in the Club Bulletin, and a convenient form will always be provided for my use if I do not wish to receive a forthcoming book. You will bill me the special Club price for each book I take. This will often be as much as 30% off retail prices, plus a few cents postage.

Name.....
(please print)

Address.....

City..... State..... Zip Code.....


SAVE POSTAGE COSTS—enclose 99¢ now and we will pay postage. Same return privilege.

THIS VALUABLE COUPON BRINGS YOU the \$9.90 ELECTRONICS GUIDE below for only 99¢ with trial membership in the famous Gernsback Electronics Book Club!

You are invited to accept—at a mere fraction of the original price—an electronics guide that answers every question you've ever had on fixing transistor radios and printed circuits. We make this extraordinary offer to demonstrate just one of the many advantages you will enjoy as a member of the famous Gernsback Electronics Book Club.

Here is a complete, self-training course by expert Leonard C. Lane. It tells you *all* you want to know, including specific servicing methods and techniques. You get practical, down-to-earth guidance you can use at once to *spot trouble* in the audio section, pinpoint speaker and earphone circuit defects, *check* distortion in the audio amplifier, *locate* front-end troubles, *eliminate* printed-circuit board pitfalls, and work more effectively with the signal generator vtvm, scope and isolation probe.

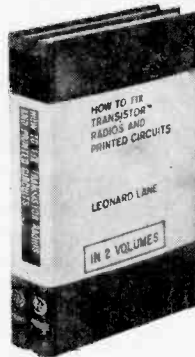NOTHING IS LEFT OUT. This giant 2-volume guide treats every area—much of it original, unavailable anywhere else in book form. Hundreds of illustrations and schematics practically turn equipment inside out for you to examine. You get practical tips to save shop time, to lessen servicing trial and error, to find and fix any trouble with professional know-how.



SEND NO MONEY NOW mail coupon for free trial

You risk nothing, now or ever, by mailing the coupon above. You will receive these 2 skill-building handbooks for free examination. If not pleased, return books in 10 days and forget the matter. Otherwise, start your membership and discover how the Club will help you *build* your know-how, *boost* your income, and *get more fun* out of electronics!

Gernsback Library, Electronics Book Club
Dept. X, 154 West 14th Street
New York, N. Y. 10011

Learn more, earn more!

Every other month the Club's News Bulletin will tell you about a significant new self-teaching book on color TV or radio servicing, test instruments, transistors, hobby projects, stereo, tape recording, industrial electronics, appliance repair, communications, or on some other area of vital interest to you. Each is a *working tool* designed to help you learn the subject quickly and easily.

Big cash savings!

As a member, *you alone* decide whether you want a particular book or not. You get 2 books now for 99¢ and need take only 4 more within a year. And the Club *saves you up to 30%* off retail prices on the books you take!


FREE reference service!

What's more, our staff agrees to answer for you personally, *any specific electronics questions* of your choice. You're entitled to 3 questions for every book purchased—an extraordinary membership benefit!

Mail coupon and enjoy these benefits at once!

- ★ Get two books immediately for 99¢.
- ★ Free 10-day examination privilege.
- ★ Continuous cash savings.
- ★ Free reference service.
- ★ Free charts given with many books.
- ★ You alone decide which books you want. Books are always returnable.
- ★ Club books are practical tools.
- ★ Choose only 4 more books in a year.

CB RIGS & RIGMAROLE

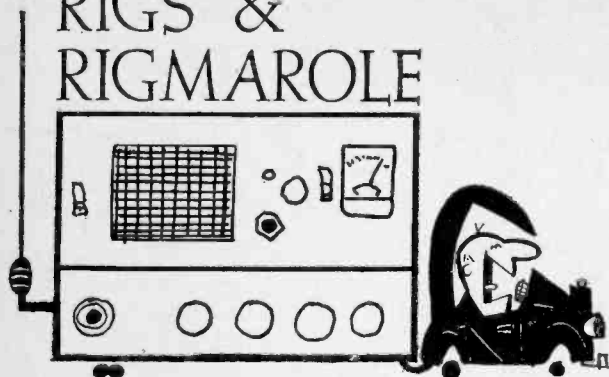

a
what's
new
product
column
that's
fun
to
read

■ *G. Whiz, it's a G. E.!* It's always a warm feeling when one of the really big manufacturers of electronic products jumps into the CB field. Insiders have long known that General Electric has been doing quiet research on the CB field—so it seems that the sales experts at GE feel that CB is worth bothering with.

GE has made their entry into CB with two new hand held transceivers, for Part 15 (unlicensed) operation.

Externally, both models are similar—each is about seven inches high, weighs slightly more than one pound, has similar styling. Operation is on any single channel and powered with penlight batteries.

Here are the main differences. The model



General Electric's Walkie-Talkie at work

Y-7000 operates with about a two mile maximum range. It sells for \$59.95 per pair.


The Y-7010 is the deluxe model, it goes over the counter and on the air for \$75.00, but it flips out a signal over a three mile range and may be operated from an operational AC power supply. Using two Y-7010 sets with the AC power supplies, you can have a CB intercom in your home, even in your home and a friend's home anywhere within the three-mile maximum range of the units.

By the way, with these unlicensed units, you don't have to tow the mark with the FCC's strict Part 95 (licensed 5-watt station) rules. You can gab for hours, work "skip," even play music! The only things to remember are that you can't cause interference to the 5-watt CB stations, as they have priority use of the channels. Here's a hint: don't operate on any of the 5 watt channels, use the so-called "radio control" channels which lie *between* the regular CB channels. The radio-control people seldom use the channels (they seem to favor CB channel 23, and will shortly be moving to 75 MHz (mc.), at least most of them). See if you can get crystals for: 26.965, 27.045, 27.145, 27.195, 27.235, 27.245 MHz.

Hooked on a New Sky Hook. Here's a nice looking piece of hardware from the people at New-Tronics Corporation, 3455 Vega Avenue, Cleveland, Ohio 44113. Thing is called the RTG-27 *Hustler* and it's "little, it's lovely, it's light," to adapt an old quote from AT&T.

Little means it's a CB antenna with a total
(Continued on page 12)

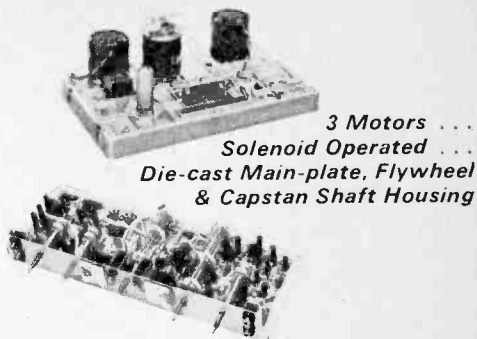How To Get A \$570 Stereo Recorder For \$400



3 Motors . . .
Solenoid Operated . . .
Die-cast Main-plate, Flywheel
& Capstan Shaft Housing

All-Solid-State Electronics . . . Record
4-Track, Stereo-Mono, Sound-On-
Sound, Sound-With-Sound & Echo

Build The New Heathkit®/Magnecord® 1020!

You Save \$170!

Thanks to Heath, you can now save \$170 on the new Magnecord 1020 professional 4-Track Transistor Stereo Tape Recorder by building it yourself. And the only difference between this Heathkit version and the original is the \$170 you save (think of all the tape you can buy with that!)

Professional Recording Facilities

You can record "live" from microphones, or from auxiliary sources like tuners, phonographs, TV's, etc., and playback . . . in 4-track stereo or mono at either 7½ or 3¾ ips. And you can make sound-on-sound, and sound-with-sound (mixing) recordings, or create interesting echo effects.

Professional Tape Transport

The tape transport is powered by 3 separate motors . . . a hysteresis synchronous capstan motor for constant, accurate speed, and two split-capacitor types to drive the reels. And with the push button controls, you can change operation instantly with just a touch of a button. Compliance arms insure correct tape tension. The fail-safe brakes, tape gate and pressure roller are solenoid operated for instant, gentle stops. And when the tape runs out, an automatic switch shuts off all motors and retracts the pressure roller.

3 Professional Tape Heads

Selectable ¼ track erase, record and play. Removable shields afford double protection against external magnetic fields. Snap-mounted head covers provide easy access for cleaning and de-magnetizing. And for quick, accurate editing, there are center-line marks.

Other Professional Features

All parts mount on a thick, die-cast mainplate that won't warp, reduces wear, provides rigid support and alignment. Two V. U. meters for visual monitoring of signal levels from tape or source. Front panel inputs and outputs for microphones and headphones. Digital counter with push-button reset. Low impedance emitter-follower outputs deliver 500 millivolts or more to amplifier inputs. Individual gain controls for each channel. And a 2N1 transistor, 4 diode circuit for cool, instant operation, and long life.

Famous Heathkit Know-How Speeds Assembly

Simple step-by-step instructions and giant pictorials guide you every step of the way. And to make construction even easier, the connecting wires and shielded cables are pre-cut, stripped and marked . . . even the connectors are installed where necessary; just plug them in! You just wire two circuit boards and mount the transport components. Total assembly time is around 25 hours!

Order yours now!

Kit AD-16, deck & electronics, 45 lbs.	\$399.50
ADA-16-1, walnut base, 8 lbs.	\$19.95
ADA-16-2, adapter ring for cabinet or wall mount, 21 lbs.	\$4.75
ADA-16-3, slides (combine with walnut base for tape drawer), 7 lbs.	\$9.95

FREE!

World's Largest Kit Catalog!

108 pages! Describe this and over 250 kits in stereo/hi-fi, color TV, organs, ham, test, CB, marine, home & hobby. Mail coupon, or write Heath Company, Benton Harbor, Michigan 49022.



HEATH COMPANY, Dept. 19-10,
Benton Harbor, Michigan 49022

Enclosed is \$ _____, plus shipping.

Please send model (s) _____

Please send FREE Heathkit Catalog.

Name _____

Address _____

City _____ State _____ Zip _____

Prices & Specifications subject to change without notice.

HF-193

CB Rigs & Rigmarole

Continued from page 10



Good starting point for any performance worth recording...

Sonotone full fidelity microphones

Wondering why your "live" home recorded tapes sound dead, lack professional quality? Stop wondering.

That accommodation mike given with your tape recorder just isn't in the same league with your recorder's pick-up capabilities.

Want results you'll be proud of? Plug a full fidelity Sonotone microphone into your tape recorder. The improvement will delight you! Because Sonotone microphones capture all the richness and vibrancy of live sound to take full advantage of your tape recorder's output capabilities.

For fine dynamic, as well as ceramic microphones... ask for a Sonotone microphone at your hi-fi dealer. Or write to

SONOTONE
audio products



SONOTONE CORPORATION, ELMSFORD, N. Y. 10523
ELECTRONIC APPLICATIONS DIVISION
EXPORT: SINGER PRODS. CO., INC., N. Y. C.,
CABLE: EXREGNIS; N. Y.



New-Tronics
Model RTG-27
Hustler Antenna

height of only 25 inches, and just in case you don't do well in the cipherin' department, that's two feet (give or take an inch). This means that your Hustler equipped car will now be able to get into the family garage, into automatic car washes, and cease being a menace to low flying planes or high flying butterflies.

The antenna comes complete with a chrome plated split-ball at its base, which in turn is mounted on a heavy gauge chrome plated steel gutter clamp. This means that if your car has a rain gutter, all it takes is a screw driver and 5 minutes between unpacking and yakking—almost "instant CB," mobile style.

You can peak the Hustler for maximum efficiency on your favorite channel, and then lock it into the peaked position. A spring at the base of the antenna is given as extra protection—just in case you *should* hit something, despite the shortened length of the antenna. It even comes complete with 12 feet of 52-ohm coax, tipped off with a soldered on connector. Everything you need for mobile operation, except the rig itself. Price is \$12.95!

Push Me Daddy, 9 to the Bar! That's what you'll be singing with the new Raytel TWR-9 base station super-fantastic dream rig. This transceiver has so many new things (new to the CB world, that is) incorporated, that we hardly know where to begin.

For one thing, it has a walnut veneer trim on the front panel. It *does not* have a microphone, because the mike is built into the set itself, and aimed in the direction of the

(Continued on page 123)

DEVRY TECH NOT ONLY TRAINS
YOU... BUT HELPS YOU GET
STARTED AT NO EXTRA COST IN
THE **BIG-MONEY FIELD OF**

ELECTRONICS!

✓ PREPARE AT HOME

Whether you want to prepare for a good-paying new job or for advancement in Electronics with your present employer, DeVry Tech offers specialized educational programs designed to meet your needs. You set up your own HOME LABORATORY and work over 300 construction and test procedures to develop on-the-job type skills. You build a quality Transistorized Meter, a 5-inch Oscilloscope and a special Design Console. DeVry also includes modern "programmed" texts, instructive motion pictures, Consultation Service. Effective? Yes!

✓ RESIDENT SCHOOL

If you prefer you may get all of your training in DeVry's U.S. or Canadian resident schools under the close guidance of friendly, experienced instructors. You work with a wide variety of commercial equipment similar to that actually used in industry as you prepare in our laboratories for a technician's job in Communications, Microwaves, Radio-Television, Automation, Radar, Computers, or other branch of Electronics. DeVry even provides part-time job placement service to those who wish to earn extra money while attending day or evening classes.

✓ PLACEMENT SERVICE

Meet W. E. Bartz, who has helped thousands of DeVry men toward exciting, profitable careers in Electronics. When YOU complete your program, he will help you too. As Placement Manager in touch with business and industry across the nation, Bartz knows the employer demand for DeVry-trained men. He has cooperated in placing our graduates with thousands of firms!

Men 18-45, start preparing NOW for this vast opportunity field. Soon you should be ready for DeVry's valuable employment help!



HOME LABORATORY EQUIPMENT
— YOURS TO KEEP!



EXPERIENCED
INSTRUCTORS



MAIL COUPON TODAY!

No Advanced
Education or
Previous Technical
Experience Needed
to Get Started

Your ambition and desire to succeed are more important! DeVry guides you every step of the way toward success.

Free

Send coupon
for these two
factual book-
lets NOW!



DEVRY TECHNICAL INSTITUTE
4141 Belmont Avenue, Chicago, Ill., 60641 Dept. RTE-8-W

Please give me your two free booklets, "Pocket Guide to Real Earnings," and "Electronics in Space Travel"; also include details on how to prepare for a career in Electronics. I am interested in the following opportunity fields (check one or more):

- | | |
|--|---|
| <input type="checkbox"/> Space & Missile Electronics | <input type="checkbox"/> Communications |
| <input type="checkbox"/> Television and Radio | <input type="checkbox"/> Computers |
| <input type="checkbox"/> Microwaves | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Radar | <input type="checkbox"/> Industrial Electronics |
| <input type="checkbox"/> Automation Electronics | <input type="checkbox"/> Electronic Control |

Name _____ Age _____

Address _____ Apt. _____

City _____ State _____ Zip Code _____

Check here if you are under 16 years of age.

2103 HOME STUDY AND RESIDENT SCHOOL TRAINING
AVAILABLE IN CANADA

DEVRY TECHNICAL INSTITUTE

4141 Belmont Avenue • Chicago, Illinois 60641

Accredited Member of National Home Study Council




BOOKMARK BY BOOKWORM

□ □ The ol' Bookworm has to take up a bit more space in this issue of RADIO-TV EXPERIMENTER because he has so many goodies to chat about. So, thanks for the space, Editor, and away we go. . . .

□ □ **Great Text.** *Basic Electronics for Scientists* has been written to provide the scientist and engineer, particularly the non-electrical, with a basic understanding of electronic devices and circuits. The volume is authored by James J. Brophy, Vice President, IIT Research Institute

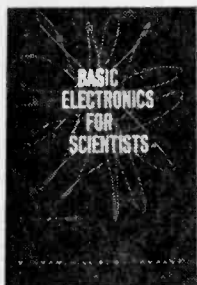The book begins with basic *dc* circuit theory, so that the treatment is completely self-contained. Topics covered include *ac* circuit theories, vacuum tubes and transistors, and other semiconductor devices.



Hard cover
471 pages
\$12.75

Also included is a chapter on digital circuits, and both analog and digital computers are discussed. Wherever appropriate, electronic instrument circuits are used as examples, and all modern instrumental approaches are presented. Emphasis is on electronic instruments rather than communications as commonly found in electrical engineering books.

Basic Electronics for Scientists is an excellent review book for the skilled technician who has learned his electronics in dribs and drabs through the years as well as those who have learned much but need some of the gaps filled in. Published by the McGraw-Hill Book Company, this text is obtainable at most book stores or by writing directly to the publisher at 330 West 42nd Street, New York, New York.

□ □ **Color TV De-Pooping.** The advent of color TV has resulted in receivers employing more vacuum tubes than the black and white sets and it has also meant the introduction of more sophisticated circuits requiring special test equip-

ment to locate and cure color troubles.

One factor has not changed. The tubes used in color TV are subject to the same troubles as those in the black and white sets and tube troubles amount to over 80 per cent of the faults which occur in any television set. In the case of the color TV set, tube troubles have been greatly increased due merely to the increase in the number of tubes in the color TV receiver.

Up to the present time, very little has been done to help the serviceman in locating faulty tubes in color sets. As a matter of fact, color set manufacturers added to the difficulty by introducing new names to describe tube functions and in too many instances have not standardized the use of these names although the circuits of all the leading color TV sets bear a very close resemblance to each other. As a result a tube having an identical function, may have different names.



A new booklet, *Color TV-Magic Fault Finder* by H. G. Cisin, has devised a novel system of standardizing the designation of tube functions whereby the tubes in all color TV sets regardless of make or model can be coded according to tube functions. As a result, the locating of defective tubes is speeded up and becomes almost automatic. Actually, the new system outlined in this book is so simplified, that a faulty tube can be located without knowledge of color TV theory, thus making it easier for TV servicemen to get started in color set servicing. A table of troubles due to misadjustments has been included and this should be of help where tube troubles are not indicated. *Color-TV-Magic Fault Finder* is published by Harry G. Cisin, Publisher, Amagansett, L. I., New York.



Soft cover
69 pages
\$2.00

(Continued on page 16)

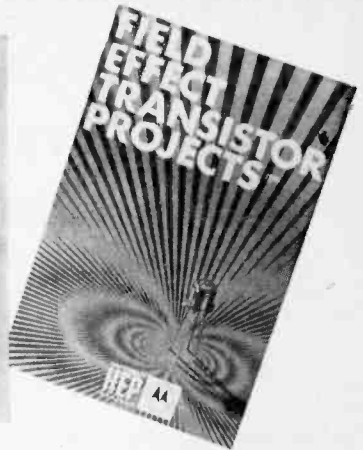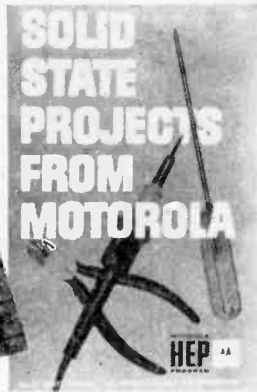NOW FIELD EFFECT TRANSISTOR and INTEGRATED CIRCUIT PROJECTS



IN 3 HEP SOLID-STATE PROJECT BOOKS FROM MOTOROLA

Motorola's HEP program provides you with the latest in quality semiconductors and offers proven projects incorporating these new devices. These project books, prepared for beginner and expert, contain easy-to-follow text and illustrations that make construction as easy as "electronics by the numbers." These books open new vistas for using semiconductors in test equipment, computers, musical instruments and fun circuits.

The first Integrated Circuit Project Book for hobbyist and experimenters contains eight chapters, 96 pages, including a basic introduction to integrated circuits. Build your own completely portable square wave generator featuring a 10 nanosecond rise time, and frequency response from 6 Hz to 60 kHz in four ranges. For fun you can build an I/C 4-octave organ with separate voicing controls. Other projects include a glidetone, binary computer, oscillator, electronic string guitar etc. Price **\$1.00**

Ten chapters, including a basic description on semiconductor fundamentals. Projects include a regulated power supply, intercom, motor speed control, 6-meter converter, minifi amplifier, signal generator and other circuits. Price **\$.50**

Another HEP first—a project book full of circuits utilizing the field effect transistor (FET), 96 pages. Projects include a high impedance DC Voltmeter (22 mega-ohms) with a scale of accuracy of $\pm 2\%$ that requires no zeroing when changing ranges; a four-input audio-mixer with a flat frequency response of 20 Hz to over 100 kHz, as well as such projects as a timer, crystal calibrator, vibrato preamp etc. Price **\$1.00**

On sale at all Motorola HEP franchised outlets, the books are also available by sending the coupon below, with the appropriate amount, plus 10 cents for handling, to HEP, Box 955, Phoenix, Arizona 85001.

HEP

DEPT. TVE106
BOX 955,
PHOENIX, ARIZ.
85001

Gentlemen:

Please send the following HEP project books:

- Integrated Circuit Projects From Motorola \$1.10
- Field Effect Transistor Projects \$1.10
- Solid-State Projects From Motorola \$.60

Enclosed is _____



MOTOROLA
Semiconductor
Products Inc.

Name _____
Address _____
City _____
State _____ Zip code _____

Olson

* **FREE**

*
Fill in coupon for a **FREE** One Year Subscription to **OLSON ELECTRONICS'** Fantastic Value Packed Catalog—Unheard of **LOW, LOW PRICES** on Brand Name Speakers, Changers, Tubes, Tools, Stereo Amps, Tuners, CB, and other Values. Credit plan available.

NAME _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____

If you have a friend interested in electronics send his name and address for a **FREE** subscription also.

OLSON ELECTRONICS
INCORPORATED

481 S. Forge Street Akron, Ohio 44308

WORLD'S FINEST

ERSIN MULTICORE 5-CORE SOLDER

NEW EASY DISPENSER


PAK only 69¢

BUY IT AT RADIO-TV
PARTS STORES

MULTICORE SALES CORP., WESTBURY, N.Y. 11591

Bookmark

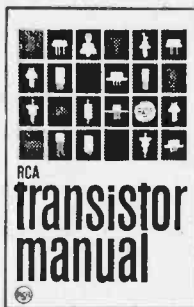Q. Guide. The new *RCA Transistor Manual* (SC-12) is expanded by more than 20 per cent to a total of 480 information-packed pages as compared to its previous edition. The man-



Soft cover
480 pages
\$1.50

ual contains new easy-to-read text on semiconductor devices and applications not covered in previous editions, a "streamlined" data section with more extensive data on active transistors, up-to-date transistor selection charts, information on military-specification types and on mounting hardware, and a revised circuits section including descriptive writeups of circuit functions and operation. The manual is intended for use by designers, students, hobbyists, and others interested in the dynamic field of semiconductor devices.

A new feature of the manual is the inclusion of a descriptive writeup for each circuit to explain the over-all operation and the functions of the individual stages. This expanded and revised section contains more than 40 circuits, complete with parts lists. Included are portable, automobile, and ac/dc radio receivers; AM/FM radio receivers; a three-band radio receiver; an FM tuner and an FM stereo multiplex adapter; a preamplifier for phono, FM, or tape pickup; audio power amplifiers with power outputs from 10 to 70 watts; stereo amplifiers with outputs from 1 to 15 watts per channel; CB and CW transmitters; crystal and power oscillators; a grid-dip meter; a code-practice oscillator; an electronic keyer; a power supply for amateur transmitters; series-and-shunt-type voltage regulators; a "light minder" for automobiles; battery chargers; a universal motor speed control (which can also be used as a light dimmer); a speed control for model trains and race cars; an electronic timer; an electronic heat control with a "ready" light; an integral-cycle ratio power control; a servo amplifier; an ac voltmeter; a shift register or ring counter; astable and bistable multivibrators; and a light flasher.

Copies of the *RCA Transistor Manual* (SC-12) may be obtained from RCA Distributors, or by sending \$1.50 to Commercial Engineer-

ing, Dept. RTV, RCA Electronic Components and Devices, Harrison, New Jersey 07029.

□ □ For the Beginner. Learning by doing is one of the best ways to study any subject. Audel's *Practical Science Projects in Electricity-Electronics*, by Edward M. Noll, enables the reader to do just that while learning about the wonderful science of electronics. The purpose of this book is twofold: to show basic electrical and electronics principles through simple projects and demonstrations, and to help the reader develop practical construction and testing skills. Information is given on the step-by-step construction of a radio-frequency amplifier, which along with higher-powered audio amplifier, permits the reader to use signals derived from various types of tuners and detectors. The book teaches feedback, oscillation, modulation, detection, and the reception of code signals. Every chapter contains sufficient text material to explain what happens in each of the demonstrations.

All of the projects are designed to be both useful and educational; and they can be constructed from inexpensive, readily available parts. For those interested in pursuing amateur radio as a hobby, material has been included on the construction and use of a code practice oscillator. This book will not only permit you to perform interesting experiments, it will also help you learn electrical and electronic fundamentals in the easiest and most enjoyable way. *Practical Science Projects in Electricity-Electronics* is available from bookstores throughout the country or from Theo. Audel & Company, Dept. RT, Indianapolis, Indiana 46206. This 480 page text costs only \$4.95.



"It is weather like this that makes me glad I have my gear well grounded!"

BECOME A RADIO TECHNICIAN For ONLY \$26.95

BUILD 20 RADIO CIRCUITS AT HOME

with the New
Progressive Radio "Edu-Kit"®
ALL Guaranteed to Work!

only
\$26.95
Reg. U.S.
Pat. Off.



A COMPLETE HOME RADIO COURSE

- BUILD**
- 12 RECEIVERS
 - 3 TRANSMITTERS
 - SIGNAL TRACER
 - SIGNAL INJECTOR
 - CODE OSCILLATOR
 - 50-WATT GENERATOR
 - AMPLIFIER

- No Knowledge of Radio Necessary
 - No Additional Parts or Tools Needed
 - Excellent Background for TV
- Training Electronics
Technicians Since 1946

FREE SET OF TOOLS, PLIERS-CUTTERS, TESTER, SOLDERING IRON.

WHAT THE "EDU-KIT" OFFERS YOU

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. You will learn radio theory, construction and servicing. You will learn how to build radios, using regular schematics; how to solder and wire in a professional manner; how to service and trouble-shoot radios. You will learn how to work with punched metal chassis as well as the new Printed Circuit chassis. You will learn the principles of RF and AF amplifiers and oscillators. You will learn the principles of Code Oscillator, Signal Tracer, Square Wave Generator, Amplifier and Signal Injector circuit and learn how to operate them. You will receive an excellent background for TV. In brief, you will receive a basic education in Electronics and Radio, worth many times the small price you pay, only \$26.95 complete.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." You begin by building a simple radio. Gradually, in a progressive manner and at your own rate, you construct more advanced multi-tube radio circuits, learn more advanced theory and techniques, and do work like a professional radio technician. These circuits operate on your regular AC or DC house current.

THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. The "Edu-Kit" is used by young and old, schools, business, Armed Forces Personnel and Veterans Administration for training and rehabilitation. One of the most important aspects of the "Edu-Kit" is the Consultation Service which we provide. We welcome students to send us their problems, whether related to any of the material covered in the "Edu-Kit" course, or encountered in other experiences in the field of electronics.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 20 different radio and electronic circuits, each guaranteed to operate. Our kits contain tubes, tube sockets, variable electrolytic capacitors, ceramic and paper dielectric condensers, resistors, the strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, hook-up wire, solder, selenium rectifier, volume controls, switches, etc. In addition, you receive Printed Circuit materials, including Printed Circuit Chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, pliers, cutters, professional electric soldering iron and a self-powered, dynamic Radio and Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide, FCC Amateur License Training, and a Quiz Book.

All parts, components, etc. of the "Edu-Kit" are 100% unconditionally guaranteed, brand new, carefully selected, tested and matched. Everything is yours to keep. The complete price of this practical home Radio and Electronics course is only \$26.95.

TROUBLE-SHOOTING LESSONS

You will learn to trouble-shoot and service radios, using the professional Signal Tracer, the unique Signal Injector, and the dynamic Radio and Electronics Tester. Our Consultation Service will help you with any technical problems.

FREE EXTRAS

- Set of Tools • Radio Book • Radio and Electronics Tester
- Electric Soldering Iron • Pliers-Cutters • Tester Instruction Book • Hi-Fi Book • TV Book • Quiz Book • Membership in Radio-TV Club: Consultation Service • FCC Amateur License Training • Printed Circuitry • Certificate of Merit • Valuable Discount Card

UNCONDITIONAL MONEY-BACK GUARANTEE

ORDER FROM AD—RECEIVE FREE BONUS RADIO & TV PARTS JACKPOT WORTH \$15

- "Edu-Kit" Postpaid, Enclosed full payment of \$26.95.
- "Edu-Kit" C.O.D., will pay \$26.95 plus postage.
- Send me FREE additional information describing "Edu-Kit."

Name
Address

PROGRESSIVE "EDU-KITS" INC.

1186 Broadway Dept. 538NN Hewlett, N. Y. 11557

**NEW! SCR CAPACITIVE DISCHARGE
FURY XII
ELECTRONIC AUTO IGNITION SYSTEM**



**Kit or Assembled!
SATISFACTION
GUARANTEED!**

You've read all the ads - Heard all the claims - Now buy the VERY BEST. FURY XII costs a little more but we ADD QUALITY rather than CUT COST !!!!
FURY XII Kit..... \$ 39.95
FURY XII Assembled..... \$ 59.95

MICRO-KITS, INC.
1900 Crest Drive, Eugene, Ore.
 I ENCLOSE \$39.95 for kit.
 I ENCLOSE \$59.95 ASSBLD
NAME ADDRESS
CITY STATE

**Get Your
F. C. C. LICENSE
and
A. S. E. E. DEGREE**

Move up. Make more money. Enjoy greater security. How? By having the knowledge, skills, and documents that industry needs and pays for. Grantham can train you—can prepare you for a successful career in electronics. Among the courses we offer are:

- (1) F.C.C. License Preparation (for first class Government license in communications electronics).
- (2) Electronics Engineering Technology (leading to the Associate in Science in Electronics Engineering degree).
- (3) Radio & Television Servicing (training you to be an expert radio-TV serviceman).

All of our courses are available in resident classes, and some of them are available also by correspondence. We are approved to offer training under the new G.I. Bill—both in resident classes and by correspondence.

Write or phone any one of our locations listed below for free details. Specify the course you are interested in.

**Grantham School of Electronics
Dept. R-6**

1505 N. Western Ave., Hollywood, Cal. 90027
(Phone: HO 9-7878)

408 Marion Street, Seattle, Wash. 98104
(Phone: MA 2-7227)

818-18th St., NW, Washington, D.C. 20006
(Phone: 298-7460)

NEW PRODUCTS

**HIGH-FIDELITY
AMATEUR RADIO
SHORT WAVE
RECORDERS
GIMMICKS
GADGETS
TOOLS
ETC.**



In-Line Preamps

Two, new, high-gain audio preamplifiers, designed for internal DC power operation, have been introduced by Switchcraft. Called "Mix-Amps," these miniature transistorized devices provide uniform gain across the audio frequency range and are particularly suited for increasing output of low level microphones and reducing high frequency response loss in long microphone cable runs. These devices are also valuable for impedance matching and fixed gain applications, and, particularly, for boosting low level outputs of attenuating networks and pads.

Both "Mix-Amps," Model 503 and 504 have uniform response (± 1 db) across the audio frequency spectrum from 20 to 20,000 Hz (cps). An impedance switch allows selection of "LOW" impedance output (2000 ohms) with 25 db gain and a "HI" impedance output (35,000 ohms) with 6 db gain. The "Mix-Amp" has a separate on-off switch, and a standard AA penlite cell provides up to 1000 hours or more of operating time.

A high signal-to-noise (S/N) ratio may be assured for long wiring and cabling runs when "Mix-Amps" are used. Connecting "Mix-Amps" close to electrical sources (microphones, signal generators, audio transducers, etc.) provides immediate amplification so that interference (induced hum and noise) will have greatly reduced effect on the audio signals. For laboratory applications, test equipment, experimental circuits, attenuating networks such as T-pads and L-pads and other low level signal devices, "Mix-Amps" offer the immediate solution to the

need for a well-shielded, linear, audio amplification device.

Model 503 "Mix-Amp" accepts standard 1/4" phone plug. Amplified output is connected through a molded 12" 2-conductor cable to a "Tini-Plug." A Model 364A adapter plug is included to convert the output connector to a standard, 2-conductor phone plug, and a size




Switchcraft Mix-Amps 503 (left) & 504 (right)

AA dry cell is also included. The metal pre-amp housing is finished in attractive metallic color and provides complete electrical shielding for all internal circuits. Model 504 has the same design features except the output plug is a long-shouldered, standard phone plug which may be used for all normal connections and for equipment with recessed jacks.

List price for Model 503 is \$16.50 and for the Model 504, \$14.50. For complete specification details write to Switchcraft, Inc., Dept. RTV, 5555 North Elston Avenue, Chicago, Illinois 60630 and ask for free New Product Bulletin No. 159.

Background Music-Paging System

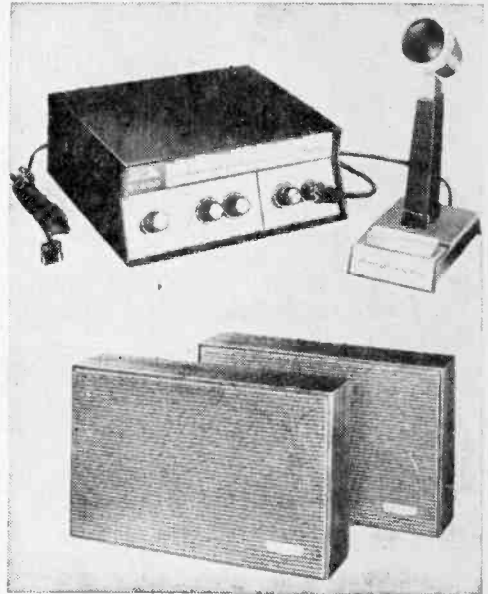An easy-to-install, easy-to-operate Ampli-Vox system makes it possible for even the smallest plants, stores, and offices to enjoy the many benefits of pleasant background music. Perma-Power's new Ampli-Vox Model S-410 provides



Perma Power's Ampli-Vox Model S-410

YOUR NEW COPY IS WAITING



FREE! For fun and pride in assembly, for long years of pleasure and performance, for new adventures in creative electronics mail the coupon below and get Conar's brand new catalog of quality do-it-yourself and assembled kits and equipment. Read about items from TV set kits to transistor radios . . . from VTVM's to scopes . . . from tube testers to tools. And *every* item in the Conar catalog is backed by a no-nonsense, no-loopholes, money-back guarantee! See for yourself why Conar, a division of National Radio Institute, is about the fastest growing entry in the quality kit and equipment business.

CONAR

MAIL THIS COUPON NOW

CONAR

KP6C

3939 Wisconsin Ave., Washington, D.C. 20016

Please send me your new catalog.

Name _____

Address _____

City _____ State _____ Zip _____ Code _____

FIX COLOR TV FAST

With H. G. Cisin's New "COLOR TV MAGIC FAULT FINDER"

Without experience, this guaranteed new method of servicing Color TV sets enables you to locate faulty tubes as rapidly as an expert. **NO THEORY—NO MATH—NO CONFUSING TECHNICAL TERMS.** The most valuable aid to color TV servicing ever written. 80% of Color TV troubles are due to defective tubes. This copyrighted new method pin-points faulty tubes in minutes.

Over 100 "bad tube" symptoms actually direct you to the cause of the trouble. In addition a special section lists over 90 trouble symptoms due to misadjustments. Copyrighted **TROUBLE INDICATING TUBE LOCATION GUIDES** for hundreds of TV models, show the exact location of each tube in the set, as well as the commercial tube type to simplify replacement **PLUS** the trouble symptoms to expect when any tube goes "bad." Tube guides include leading makes of color TV sets from Admiral to Zenith.

Get started in this rapidly expanding, profitable field of Color TV servicing. Be a color TV diagnostician. Increase your present earnings. Open your own profitable business.

H. G. Cisin, the author is the inventor of the ac-de midjet radio. He licensed RCA, AT&T, etc. He has also trained thousands of technicians, now owning their own prosperous TV service organizations or holding responsible TV positions. His years of experience are embodied in this remarkable new book.

Guaranteed Money Back in 5 days if not satisfied!

ABSOLUTELY FREE with each order. Cisin's "TV PIX GUIDE & TV TERMS," which sells separately for \$1.00. **ACT NOW**—get two books post-paid at cost of only one! **\$2** Post-paid

RUSH COUPON NOW!

H. G. CISIN, Consulting Engineer—Dept. RT-7
Amagansett, N. Y. 11930

Enclosed find \$2.00. Rush Color TV Magic Fault Finder and Free TV Pix Guide & TV Terms.

Name
Address
City State Zip

7 x 50 BINOCULARS

A magnificent hand-held binocular—the Navy's finest—made by Bausch & Lomb. UNUSED, coated. 7x magnification, 50-mm. objectives, 7.1-mm.-diameter exit pupil, relative brightness 50.4. Unexcelled for sea and shore use. You own the finest


when you own one of these! Current B&L price, \$274.50. Complete with case, straps, snap-on filter. Our price, **\$95.00**

SEQUENCE CAMERA

Perfect for many applications around the laboratory or observatory! Use for time-lapse photography or for monitoring meters or other devices. We offer the complete camera body

with lens and film magazine. Wide-angle lens, 1 3/8-inch focus, f/2.3, with stops to f/16. 24-volt operation, takes sequence shots on 35-mm. 100-foot roll film. Recording chamber permits identification of each frame with sequence number and data on card insert. The applications of this unit are limited only by your imagination. Originally made for recording the display on an oscilloscope, this camera will give you a permanent record of any changing phenomenon. Condition excellent. Shipping wt. approx. 23 lbs. **\$75.00**

MESHNA - ALLERTON ST. - LYNN MASS. 01904

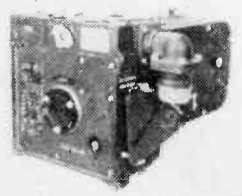

New Products

fine music reproduction; and, of utmost importance for commercial and industrial usage, does not interfere with paging. The amplifier of the Model S-410 permits the convenient adjustment of background music volume level and paging volume level *separately*. The message comes through clearly, with no loss of music program continuity.

The Ampli-Vox Model S-410 is a complete package, including an all-transistor amplifier, two loudspeakers, and a paging microphone. Any music source—tape recorder, phonograph, FM or AM tuner or radio—can be used with the Ampli-Vox system. The system is easy to install (without any tools), and any receptionist or switchboard operator can use it without special training. The transistor design provides much greater dependability than can be achieved with tube-type units, as well as instant performance with no wait while tubes warm up. Transistors also result in an amplifier compact enough to fit in a desk drawer! The audio amplifier is rated at 35 watts, E.I.A. music power, 50 watts peak. For paging convenience, the desk microphone has a push-to-talk button and a plug-in cable. Manufacturers suggested *net* price is \$189.95.

Detailed literature on the new system is available from the manufacturer, Perma-Power Company, 5740 North Tripp Avenue, Chicago, Illinois 60646. Ampli-Vox products are available everywhere in the United States and Canada, through electronic parts distributors, sound specialists, and similar outlets.

Furniture Styled Communications Consoles & Desks

A handsome and practical line of walnut communications consoles and desks have been offered by Design Industries, Inc., to house amateur radio equipment. Both console and desk feature fine furniture styling and are especially designed to bring amateur radio equipment out of attics, garages and basements and into the living room. When not in use, the console looks like a small organ or attractive desk. Its walnut finish and simple design complement any decor. Although originally designed for the ham, CB'ers and SWL's will find the units equally attractive.

Equipment is neatly flush-mounted in a durable white formica panel for easy operation. The door folds down to provide a roomy, scratch-proof formica work surface. The usual tangle of wires amid an assortment of boxes is gone. All the communications equipment fits neatly into the console. Precision cut-outs are available for most manufacturer's equipment and the front panel is easily removable for future equipment changes. Each console door has a piano



Ambassador Communications Console, Walnut—
\$395.00



Diplomat Communications Desk, Walnut—\$139.95

hinge for durability and a lock to protect equipment when not in use. The console moves easily on heavy-duty casters.

A natural chimney is provided to pass air through all equipment and there is easy access to tubes and body of each piece of equipment for adjustments and maintenance.

In addition to consoles, Design Industries offers a budget-priced walnut communications desk that groups all amateur equipment neatly on its top. It features a tilted work surface to hold equipment at just the proper operating angle. A cable trough along the rear of the desk leaves the top uncluttered for easy operating. *Collins, R. L. Drake, Galaxy, Hallcrafters*, and most other modern equipment fits the desk. Three drawers provide ample storage room. The desk's simple styling and beautiful walnut finish fit right in any room setting.

Additional information on either custom communications consoles or communications desks is available from Design Industries, Inc., Dept. RTV, P.O. Box 19406, Dallas, Texas 75219.

Sine-Square Wave Generator

A new, professional quality AF sine-square wave generator, the Model 636, has been added to the "Green Line" of electronic test instruments manufactured by Precise Electronics. The Model 636 provides a complete source of sine and square wave signals from 20 Hz (cps) to 200 kHz (kc.), for a wide range of audio and

now there are 3 time & tool-saving double duty sets

New PS88 all-screwdriver set rounds out Xcelite's popular, compact convertible tool set line. Handy midgets do double duty when slipped into remarkable hollow "piggyback" torque amplifier handle which provides the grip, reach and power of standard drivers. Each set in a slim, trim, see-thru plastic pocket case, also usable as bench stand.



PS88
5 slot tip,
3 Phillips
screwdrivers

PS7
2 slot tip,
2 Phillips
screwdrivers,
2 nutdrivers



PS120
10 color
coded nutdrivers




XCELITE

XCELITE INC. • 64 BANK ST., ORCHARD PARK, N. Y. 14127
Please send free literature N563.

name _____
address _____
city _____ state & zone _____

In Canada contact Charles W. Pointon, Ltd.

New Products

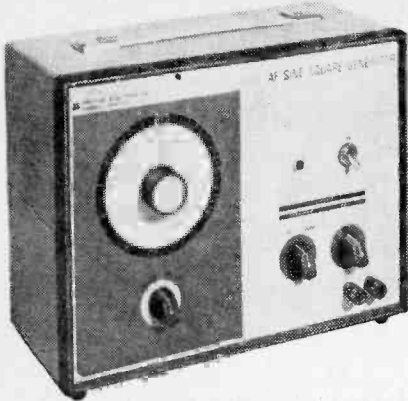

Precise Electronics Model 636
Sine-Square Wave Signal Generator

video testing, servicing, and experimental work. The instrument is designed with one scale frequency dial to simplify readings for both sine and square wave outputs, and a smooth, dual-function output control. Other notable features of the Model 636 include: negligible distortion and high stability of sine wave output; "Schmitt Trigger" multivibrator and buffer provides isolated optimum waveform square wave output;

negligible square wave tilt and fast rise time at all square wave frequencies; extensive shielding for minimum radiation pickup. For more information and specifications on the Model 636 as well as other Precise test equipment, write to Precise Electronics, Division of Designatronics Inc., 76 East Second St., Mineola, New York.

Auto Analyzer for the Saturday Mechanic

A new solid-state universal self-powered engine analyzer, the EICO Model 888, permits the layman to electronically tune up and troubleshoot all automotive and boat engines exactly as do professional automotive technicians. No technical knowledge or background is necessary. EICO's exclusive "how to" manual lists the idle speeds and the dwell angles for many manual and automatic transmissions in use today. Makes no-never-mind whether the battery voltage is 6 or 12 or the engine has 4, 6 or 8 cylinders with negative or positive ground—the 888 engine analyzer can do the job. It exactly tests and checks the total electrical/ignition system including: storage battery; generator; alternator; voltage regulator; alternator diodes; starter; starter solenoid; distributor; points; condenser; ignition coil; spark plugs; dwell angle; carburetor; fuses; bulbs; switches, accessories; all electrical wiring—sorry, no electric cigarette lighters.

If you could avoid the expense of calling your repair man each time your TV set "acted-up" you could save a great deal of money. You'll find, in easy to understand language, just how to align your color TV set; how to replace a picture tube; how to install a new antenna, or even a TV tower. These are just some of the features in the new Fall/Winter TV-REPAIR. And the editors haven't forgotten



radio and hi-fi repairing. You'll find TV-REPAIR full of dollar-saving tips. Pick up your copy at your newsstand, or use the coupon.

TV-REPAIR RTV-806
505 Park Avenue/New York, N. Y., 10022
I am enclosing \$1, which includes postage & handling charges. Please mail me my personal copy of the new TV-REPAIR.

Name _____ (please print)
Address _____
City _____ State _____ Zip _____

YOU CAN SAVE MONEY

<p>FREE POLY PAK WORTH \$25</p> <p>Includes: • Transistors • Diodes • Rectifiers • Knobs • Condensers • Coils • Etc. etc.</p> <p>Add 25¢ for handling</p> <p>BONUS #2 FREE</p> <p>\$1 FREE: YOUR CHOICE OF ANY \$1 POLY PAK LISTED BELOW FREE</p> <p>BOTH FREE WITH \$10 ORDERS</p>	<p><input type="checkbox"/> 3 INFRA-RED DETECTORS \$1 with leads, 100's of projects.</p> <p><input type="checkbox"/> 50 COILS & CHOKES \$1 rf, if, osc, peaking, etc...</p> <p><input type="checkbox"/> 10 ELECTROLYTICS \$1 can & tubulars, to 500mf..</p> <p><input type="checkbox"/> 30 HOBBY TRANS'TRS \$1 rf, if, audio, handy shop asst.</p> <p><input type="checkbox"/> 60 CERAMIC COND'RS \$1 Discs, hi-Q too; to .01mf..</p> <p><input type="checkbox"/> 25 "EPOXY" SILICON \$1 RECT 750 mil, silicon untest'd</p> <p><input type="checkbox"/> 40 INSUL'TD RESTR'S \$1 1/2, 1, 2W. Carbons, 5% too</p> <p><input type="checkbox"/> 16 TRANSISTOR RADIO SETS \$1 one-6-6-6-6-6, B-P,</p> <p><input type="checkbox"/> 10 LITTLE 'LYTICS \$1 For transr cks. 10-100mf</p> <p><input type="checkbox"/> 25 GERMANIUM DIODES \$1 DN34, 1N48, 1N60 no test</p>	<p><input type="checkbox"/> 50 ONE-WATTERS \$1 resistors, asst. values, 5% too</p> <p><input type="checkbox"/> 40 WORLD'S SMALLEST \$1 -resistors, 1/4W. to 3 meg...</p> <p><input type="checkbox"/> 5 2N107 TRANS'TRS \$1 G.E., pnp. A shop must.</p> <p><input type="checkbox"/> 40 DISC CONDENSERS \$1 25mm to .01mf, to 5KV...</p> <p><input type="checkbox"/> 25 TOP HAT RECTIFIERS \$1 silicon, .750ma, no test</p> <p><input type="checkbox"/> 75 HALF WATTERS \$1 resistors, asst, 5% too...</p> <p><input type="checkbox"/> 10 CK722 TRANS'TRS \$1 Raytheon, pnp, no test...</p> <p><input type="checkbox"/> 15 NPN TRANSISTORS \$1 2N170, 2N35, untested...</p> <p><input type="checkbox"/> 4 TRANSFORMERS \$1 Tiny, for transistor projects</p> <p><input type="checkbox"/> 100 PRINTED CIRCUIT \$1 parts, Hobby & mini work.</p>	<p><input type="checkbox"/> CLAIREX PHOTO \$2 ELECTRIC CELL for CL505 100's of light prof</p> <p><input type="checkbox"/> 4 2N170 TRANSISTORS \$1 by GE., npn for gen'l rf.</p> <p><input type="checkbox"/> \$25 SURPRISE PAK \$1 Pop. assortment radio parts</p> <p><input type="checkbox"/> 60 TUBULAR COND'RS \$1 20 values .0001 to .5 mfd</p> <p><input type="checkbox"/> 10 VOLUME CONTROLS \$1 9 types, duals too, to 1 meg</p> <p><input type="checkbox"/> 10 POWER RECTIF'RS \$1 2 amp, 400V, 30 to 500V</p> <p><input type="checkbox"/> 10 TRANSISTOR SOCKETS \$1 PNP's, NPN's & submini projects.</p> <p><input type="checkbox"/> 15 PNP TRANSISTORS \$1 CK722, 2N107, asst cases.</p>
<p>1 Amp 400 PIV for \$1</p> <p>100 TRANSISTORS 2 95¢ RF, IF, Audio Power, Untested</p> <p>3-TRANSISTOR AMPLIFIER: Printed \$1 Wired.</p> <p>INCLUDE POSTAGE, Avg. Wt, per pak 1 lb.</p>			
<p>POLY PAKS P.O. BOX 947 X SO. LYNNFIELD, MASS.</p>			



EICO Model 888 Auto Analyzer

Not a "compromise" design but rather an *all-professional* unit, the 888's solid-state circuitry includes a transistorized Schmitt trigger pulse counter, and calibration and adjust controls for "RPM" and "Ohms" tests. Its 6-inch D'Arsonval meter reads out: Volts, Engine RPM, Dwell Angle, Amperes, Ohms, Spark Output, Diode/Leakage. Compact (5 $\frac{3}{4}$ "H, 11 $\frac{1}{2}$ "W, 5"D), portable (6 lbs.), self-powered (4 "D" batteries supplied), the user may take it into car or boat for actual car-running, boat-running tests—no line cord to tie you down to an outlet. In kit form, cost is only \$44.95—wired, it's \$59.95. Want more specs? Write to EICO Electronic Instrument Co., Inc., Dept. RTV, 131-01 39th Avenue, Flushing, N. Y. 11352.

VOM-Pro Model

Triplett's new portable volt-ohm-milliammeter, Model 530-APLK, has a transistorized switching circuit that guards against accidental burn-outs, provides comprehensive overload protection and virtually eliminates bent pointers, burned out resistors, shunts and coils, and changes in accuracy due to overheating. Great for the hobbyist who is most likely to fritz a meter.

Featuring high sensitivity of 20,000-ohms-



Triplett Model 630-APLK VOM

NEW FROM ALLIED

knight-kit[®]

Taut-Band VOM

- Highly Dependable, Rugged Taut-Band Meter Movement Assures Repeat-ability of Readings
- Total of 55 Ranges . . . Starts as low as .8 VDC Full Scale for Accurate Transistor Work
- Burnout Proof Movement—No Damage to Movement Possible, Even with 1000 Times Overload



- Mirrored Scale and Knife-Edged Pointer Eliminate Parallax Errors—Assures Accurate Readings

With Test Leads and Batteries

\$39⁹⁵

Here in an easy-to-build kit, at a surprisingly-low price, is a 20,000 ohms-per-volt VOM with a burnout-proof movement.

Covers 55 ranges for reading AC and DC volts, resistance, DC current, decibels—with a switch that virtually doubles the ranges. The perfect instrument for testing radio and TV sets, hi-fi components, appliances, motors, house wiring, etc. Compact 6 $\frac{3}{4}$ x 5 $\frac{1}{4}$ x 3 $\frac{3}{4}$ " unit. Complete with batteries, test leads, assembly manual for only \$39.95. And backed by this unique money-back guarantee . . . exclusive in the industry:

KNIGHT-KIT GUARANTEE

Build a Knight-Kit in accordance with our easy-to-follow instructions. When you have completely assembled the kit, you must be satisfied or we will return your money, less transportation charges, under the Allied guarantee of satisfaction. **ALLIED RADIO**

Rush coupon today for full details and Special Introductory Offer.

ALLIED RADIO, Knight-Kit Div.

Dept. 20-KK, P.O. Box 4398, Chicago, Ill. 60680

Please rush full details and Special Introductory Offer on the new Knight-Kit Taut-Band VOM.

Name _____
 PLEASE PRINT
 Address _____
 City _____ State _____ Zip _____

ELECTRONIC TECHNICIANS!

Raise your professional standing and prepare for promotion! Win your diploma in

ENGINEERING MATHEMATICS

from the Indiana Home Study Institute

We are proud to announce two great new courses in Engineering Mathematics for the electronics industry.

These unusual courses are the result of many years of study and thought by the President of Indiana Home Study, who has *personally* lectured in the classroom to *thousands* of men, from all walks of life, on mathematics, and electrical and electronic engineering.

You will have to see the lessons to appreciate them!

NOW you can master engineering mathematics, and actually *enjoy* doing it!

WE ARE THIS SURE: you sign no contracts—you order your lessons on a money-back guarantee.

In plain language, *if you aren't satisfied you don't pay*, and there are no strings attached.

Write today for more information and your outline of courses.

You have nothing to lose, and everything to gain!


The INDIANA Home Study Institute

Dept. RT-10, P.O. Box 1189, Panama City, Fla. 32401

Tape this ad to the back of your TV or Radio Set

ALL TV-RADIO RECEIVING TUBES \$1 ea.

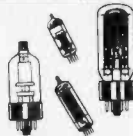• ALL BRAND-NEW, First Quality. All Types Available. • Orders Shipped First Class Same Day Rec'd. • Unconditionally Guaranteed. • 24 Month Warranty. Send \$1 for ea. tube + 50c. postage & handling of entire order. FREE: Write for "do-it-yourself" TV Test Chart and Tube List to Dept. RTVE-1066



UNIVERSAL TUBE CO. Ozone Park, N. Y. 11417

FRANCHISE OPPORTUNITY: Universal Tube Co. can set you up in your own highly-profitable business as an Electron Tube Distributor, with an exclusive territory, selling to appliance dealers and/or servicemen. For full details write immediately to Franchise Manager, address above.

BIG CATALOG

World's "BEST BUYS" in GOV'T. SURPLUS Electronic Equipment

FULL OF TOP QUALITY ITEMS—

Transmitters, Receivers, Power Supplies, Inverters, Microphones, Filters, Meters, Cable, Keyers, Phones, Antennas, Chokes, Dynamotors, Blowers, Switches, Test Equipment, Headsets, Amplifiers, Converters, Control Boxes, Indicators, Handsets, etc., etc. SEND 25¢ (stamps or coin) for CATALOG and receive 50¢ CREDIT on your order. Address Dept. 32.

FAIR RADIO SALES
P.O. Box 1105 • LIMA, OHIO • 45802

New Products

per-volt DC and 5,000-ohms-per-volt AC, the VOM has an accuracy of $\pm 1\frac{1}{2}\%$ DC and $\pm 3\%$ AC with the unit on its back. The VOM is usable with frequencies through 500 kHz (kc.). A single, easy-to-read selector switch minimizes chances of error when changing ranges, and a mirror-backed scale insures accuracy by eliminating parallax.

Weighing 5 pounds, the meter is encased in durable black molded plastic with a clear, unbreakable plastic scale window and is $31\frac{1}{32}$ " by $5\frac{1}{2}$ " by $7\frac{1}{2}$ " in size. The 630-APLK comes with batteries, leather carrying handle, 50 inch banana type leads and test prods with removable alligator clips. A variety of leather carrying cases and an accessory AC ammeter adapter with long lead attachment are available for the unit. Priced at \$95 (user net). Write to Marketing Department, Triplet Electrical Instrument Company, Bluffton, Ohio 45817.

Power Tool for the Microminiature Workshop

Let's face it, you need a miniature power tool for precision fine finishing jobs that pop up in your home workshop, hobby bench or on the job. A tool designed for such jobs is the Micro Miniature Workshop by Howard Industries. This new miniature powerhouse tool (actually kit) features streamlined design with a rugged heavy duty plastic case that's shaped for easier handling and built for longer wear, cooler operation. It is fully guaranteed for 2 years. Included with the new tool is a complete set of micro accessories including sanding discs, bristle brushes, cut-off discs, mandrel, grinding stones, buff, file, and drills. There are 24 attachments in all. An instant action Wrenchless Chuck allows quick, easy changing from one tool accessory to another.

Called "The Tool Of A 1001 Uses," the versatile new Micro Miniature Workshop cuts, grinds, sands, polishes, burnishes, cleans, carves, saws, drills and engraves. For the home craftsman or hobbyist it handles precision jobs faster, more efficiently than hand tools . . . gives fingertip ease in fine engraving, carving, cutting, drilling, etc., with smooth, cool, vibration-free operation. Also ideal for industrial applications, it speeds through jobs like production debur-




Howard Industries Micro Miniature Workshop

ring, industrial model building, pattern making, grinding of dies and molds. In the professions, its convenient shaped-to-the-hand-design and easy operation make it ideal for jewelry polishing, fine carving on dental plates and a variety of other precision jobs.

It is packaged in its own storage case, with all accessories, but also includes a convenient hanger hook for tool-rack placement. List price is \$34.50. Available nationally through hardware and appliance dealers, or write to Howard Industries, Dept. DP-1, Division of MSL Industries, Inc., Racine, Wisconsin 53404.

Push-to-Talk Mike

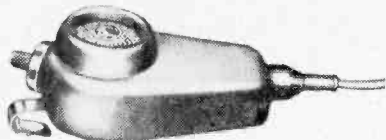Push-to-talk microphones for use with two-way mobile, ship-to-shore, ham radio and similar applications are now available from Geloso. Highly sensitive (1.2 mV/microbar) with a frequency response of 80 to 12,000 Hz (cps), the microphone has a positive-lock-action switch to hold the circuit closed. A high impact rubber case assures protection against shock and dam-



Geloso Push-to-Talk Microphone
(Models M-2, M-3 and M-40)

age. Two impedance models are available—low, 250 ohms (No. M-2) and high, 45,000 ohms (No. M-3). Also available is a crystal high-impedance push-to-talk microphone (No. M-40). Descriptive literature and prices are available from Audio Division, American Geloso Electronics, Inc., 251 Park Avenue South, New York, N. Y. 10010.


Educational Kits for Everyone

In a move to meet the needs of all age levels, *Trans-Tek Manufacturing Co.* has expanded its series of educational electronic kits. Two new kits have been added to the company's *SCHEMAT-A-KIT* series, bringing the total of kits in this series to eight. Four of the kits constitute the "basic" kits for the beginner and the other four kits belong to the "advanced" group for the more experienced experimenter.

Trans-Tek's ability to add new kits to the *SCHEMAT-A-KIT* series is an innovation which is described as the "library" approach. This concept also has proven useful in the educational field, where the *SCHEMAT-A-KIT* series can be adapted to training courses in public, private and vocational schools and colleges, and in special training courses conducted by companies and organizations.

One of the latest additions to the *SCHEMAT-A-KIT* series is a solid-state (transistorized)

You can train to be an announcer or D.J.

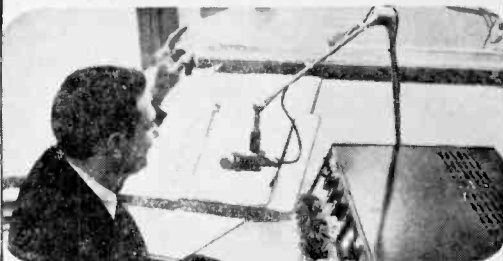

FREE VOICE ANALYSIS

Exciting new way to find out if you have the hidden talent to train for a career in radio and TV broadcasting. Urgent demand for qualified graduates. Unique, nationally recognized course supervised by John Cameron Swayze, Fran Allison, and five other broadcasting "greats" opens new horizons of high pay and fame in your life. Train in our fully equipped studios or at home in your spare time. Career Academy "reinforced learning" technique based on principles developed at Harvard and Columbia speeds training. Mail coupon today. No obligation. Training studios located in major cities.

CAREER ACADEMY

825 North Jefferson Street, Milwaukee, Wis. 53202

Please rush free, colorful 32-page brochure and arrange for Voice Analysis in my community.

Name _____ Age _____

Address _____

City _____ State _____

N32:10-66

THOUSANDS OF BARGAINS TOP VALUES IN ELECTRONIC PARTS

Transistors, Modules, Speakers, Stereo, HI-FI, Photo Cells and thousands of other Electronic Parts.

Send for FREE Catalogue

ELECTRONIC DISTRIBUTORS INC.



EDI
Dept. TA-2, 4900 Elston
Chicago, Ill. 60630

RUSH CATALOGUE

Name _____
Address _____
City _____
State _____ Zip Code _____

ASSEMBLE THIS ALL-BAND BATTERY SHORT-WAVE RADIO FOR \$9.95!




LISTEN AROUND THE WORLD—UP TO 12,000 MILES AWAY! Ships, Aircraft, Voice of America, Russia, London, Australia, Amateur Citizens, Police—Also USA Broadcast. 5 WAVE BANDS: 1/2 to 40 MC. Calibrated tuning dial. Wt. only 3 lbs.—NOW HEAR THE WHOLE WORLD TALKING DAY OR NIGHT! SEND ONLY \$2.00 (cash, ck, mo.) and pay postman \$7.95 COD postage or send \$9.95 for P.P. delivery. Complete Basic Kit as shown. Free Broadcast Coil and Plastic Case if you order now! Available only from Midway Radio, Dept. SRE 10, Kearney, Neb.

BUY U. S. SAVINGS BONDS

New Products

metronome which provides a "true metered beat for music and other uses." The kit is priced at \$2.25. Also added to the series is a code practice oscillator, designed for the beginner hobbyist and priced at \$1.79.

Trans-Tek has been granted a patent on its method of mounting its educational kits. This technique consists of mounting all components directly onto a drawn circuit schematic by means of skin-packing. Each component therefore is displayed in its actual position in the circuit. In each kit, circuit and pictorial diagrams, theory of operation and step-by-step instructions are included so as to assist the hobbyist, experimenter or educator to construct useful products with ease.

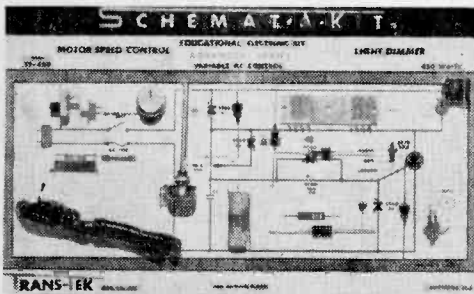

Trans-Tek Schemat-A-Kit

Other kits in the SCHEMAT-A-KIT series include: *ST-125W—Hi-Lo Switch*. This unit can dim house lights and dark rooms, and control electrical drills and small electrical tools up to 125 watts. Price \$1.79.

ST-500W—Hi-Lo Switch. This can dim house lamps and other lights and control drills and other small electrical tools up to 500 watts. Price \$2.49.

ST-612RS—Regulated Power Supply 6-12 volts. This kit breaks the power supply down into four basic parts—power transformer, full-wave bridge, filter and voltage regulator. When completed, the unit yields between 6 and 12 volts of regulated voltage at currents up to 200 milliamps. Price \$5.75.

ST-210—Intercom Amplifier. This circuit was designed as a simple amplifier employing a speaker as input. It also can be used as an intercom if the input and output connections are reversed. As an amplifier, a 3.2-ohm speaker is used and a 16-ohm speaker is recommended for output load. When completed, the amplifier will yield good room volume. Price \$5.95.

ST-313—Ultra-Hi Gain Amplifier. This three-transistor direct-coupled amplifier has a gain of more than 100,000 times. It can be used as a low-cost hearing aid or for eavesdropping. Price \$5.95.

ST-450—Variable AC Control. Using a Silicon Controlled Rectifier, this can be used as a light dimmer or motor speed control, permitting 0 to 100 per cent variations. Price \$7.50.

To get more information and specifications on the *Trans-Tek* line write to *Trans-Tek Manufacturing Co., Inc.*, Dept. RTV, Garwood, New Jersey.

SWR

The new Heath HM-15 Reflected Power Meter shows *standing wave ratios* (SWR) from 1:1 to over 3:1 on 50 or 75-ohm transmission lines. It can be used with transmitters with peak power outputs as high as one kilowatt and can be used throughout the wavelength range of 160 through 6 meters. The HM-15 is calibrated in both SWR and per cent reflected power. Styled to match the Heath SB-Series equipment,



Heath Model HM-15 Reflected Power Meter

the HM-15 is an ideal instrument for use in designing and matching new antenna systems. It can be used for matching impedances between exciters and final amplifiers. The HM-15 enables the ham radio operator to obtain peak efficiency from his transmitting equipment. Costs only \$14.95. Complete specifications and details on this valuable ham radio accessory may be obtained by writing *Heath Company*, Dept. RTV, Benton Harbor, Michigan 49022.



"Have a nice trip, Hon.
Phone me when you get there!"




Appliance Static

We have interference on our television and FM radio, all the time, from an electrical appliance—on all channels! It is quite bad. What should I do about it?

—J. C., Grimsley, Ontario, Canada

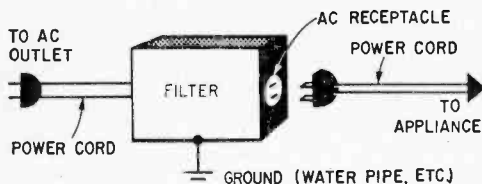Install a line filter between the appliance and the power line as shown in the diagram. Cornell-Dubilier and others make filters for this purpose.




Time Plods on!

Can you give me the circuit of an Atwater-Kent Model 20 and an AC power supply for it?

—D. E. H., Mt. Orab, Ohio

Atwater Kent, a very great man, operated a huge factory in Philadelphia where outstanding radios were produced. One day, long ago, Mr. Kent closed up his place and moved to California. Now, Philco has his plant which is so huge that employees easily get lost in it. But, even Philco can't find diagrams of its own radios, of which Philco built more than anybody else. All there is left to remind one of Atwater Kent is a fireplace in his former office, now occupied by a Philco vice-president. History was made within those brick walls (now owned by Ford), but no schematics of yesteryear are

You earn your FCC First Class License

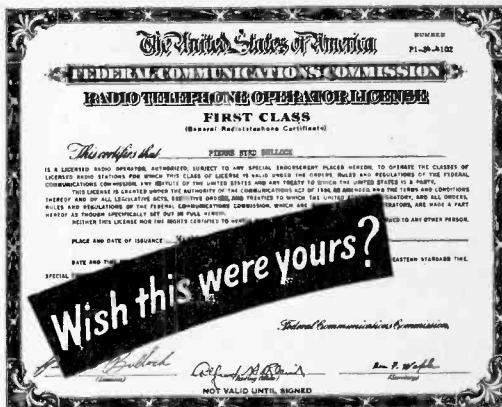

or your money back!

THERE'S A WORLD OF OPPORTUNITY FOR THE MAN WITH AN FCC LICENSE

All it takes is a few spare hours a week and NRI's FCC License Course to open the way to increased opportunities in Communications. With an FCC License, you're ready to operate, service and install transmitting equipment used in aviation, broadcasting, marine, mobile and Citizens-Band communications.

What does it take? Men with absolutely no training or experience in Electronics complete the course in 10 months. A Technician or man with some background can easily cut that time in half. And because NRI has a greater enrollment than any other school of its type, training costs you less than comparable courses offered by other schools. Further, YOU MUST PASS your FCC exams or NRI refunds your tuition in full.

Get full details about NRI FCC License Course plus other home-study plans offered by NRI, oldest and largest school of its kind. Mail coupon. No obligation. No salesman will call. NATIONAL RADIO INSTITUTE, Washington, D. C.

Available Under NEW GI BILL. If you served since January 31, 1955, or are in service, check GI line in coupon.

MAIL for FREE CATALOG



NATIONAL RADIO INSTITUTE
Electronics Division
Washington, D. C. 20016

31-106

Please send me complete information on FCC License Training and other NRI courses, as checked below. (No salesman will call.)

- | | |
|--|---|
| <input type="checkbox"/> FCC License | <input type="checkbox"/> Radio-TV Servicing |
| <input type="checkbox"/> Complete Communications | <input type="checkbox"/> Industrial Electronics |
| <input type="checkbox"/> Aviation Communications | <input type="checkbox"/> Electronics for Automation |
| <input type="checkbox"/> Marine Communications | <input type="checkbox"/> Basic Electronics |
| <input type="checkbox"/> Mobile Communications | <input type="checkbox"/> Math for Electronics |

Check for facts on new GI Bill.

Name _____ Age _____
PLEASE PRINT

Address _____

City _____ State _____ Zip _____

ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL

Ask Me Another

to be found. Don't bother with a power supply for your Model 20. Give it to a museum. It is worthy of that honor.


FM Deviation Makes Audio

I have a 152-174 mc band FM monitor receiver. I have to have the volume wide open to hear the local police. How can I improve my reception?

—J. P. H., St. Cloud, Minn.

Your receiver is undoubtedly designed to receive wideband FM (± 15 kc deviation). Nearly all stations in that band, except marine, employ narrowband FM (± 5 -kc deviation). You can hear them but not as loudly as wideband FM stations. Volume depends upon the frequency deviation, not on signal strength. Unless you want to go to the expense of installing a gated-beam FM detector, as shown in the diagram, just leave the volume control set full on.

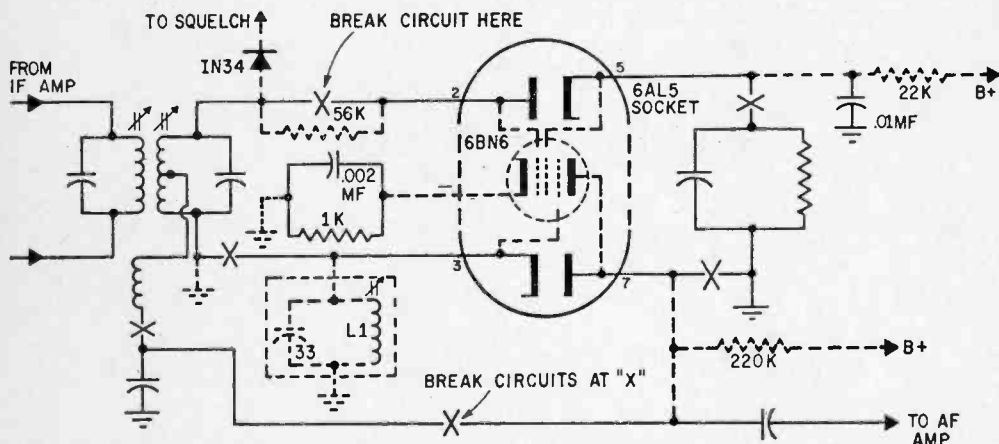Coil L1 is a 10.7-mc quadrature coil such as Sonar 22-130-003 (\$3.00). Add circuits and components shown in heavy lines. The 6BN6



RUSSIA'S SPACE HOAX

A Special Science & Mechanics Newsbook

EXCLUSIVE!

By LLOYD MALLAN

DOCUMENTED PROOF THAT THE SOVIET SPACE PROGRAM HAS BEEN FAKED!

OVER 14 MONTHS OF RESEARCH UNCOVERS EVIDENCE FROM 56 AUTHORITIES

THIS PROVOCATIVE NEW BOOK WILL BE AT YOUR NEWSSTAND SEPTEMBER 27th

For the first time we have assembled, in one book, all of the documented proof that the Soviet space program has been faked!

Science expert Lloyd Mallan's articles, including much new and never before published information on the Soviet's continuous plot to fool the world with regard to their professed space achievements and technological accomplishments, will be released in book form.

Here's provocative reading that should become part of your library, as it is certain to become a collector's item.

Don't miss RUSSIA'S SPACE HOAX, which will be at your newsstand September 27th—\$1.00. If you wish, we'll reserve a copy for you. Just use the coupon.

For quantity price, write to the publisher.

SPACE HOAX/Science & Mechanics RTV-80J
505 Park Avenue, New York, N. Y. 10022

I am enclosing \$1, which includes postage & handling. As soon as it is off the press, rush me my copy of RUSSIA'S SPACE HOAX (outside USA & Canada, add 25¢).

Name _____ (please print)

Address _____

City _____ State _____ Zip _____


tube is shown superimposed on 6AL5 tube to show both "old" and "new" circuitry.

VHF Wave Traps

On my FM receiver, I get interference from a Channel-11 TV station just above one of our local FM stations. Is there a filter I can add to remove the TVI?

—J. A. B., Kingston, Ontario

Your trouble could be due to intermodulation of strong local signals. The picture carrier of Channel 11 is at 199.25 MHz (mc) and the sound carrier is at 203.75 MHz. When your receiver is tuned to 96.525 MHz, the local oscillator operates 107.225 MHz, if your set has a 10.7-MHz IF. Now, if the receiver mixer picks up the second harmonic of the local oscillator signal, this harmonic at 214.45 MHz heterodyned with the 203.75 MHz signal apparently gets through the RF circuits of your receiver.

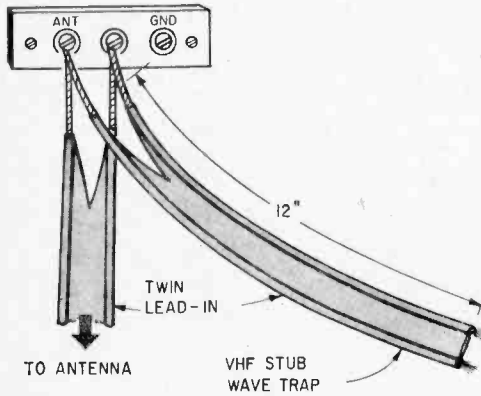

Try a series-resonant filter or wave trap across your receiver's antenna terminals as shown in the diagram. The wave trap is a one-foot length of twin lead. Snip off its free end an eighth of an inch at a time until the interference is minimized.

Output-Transformer Problem

Where can I get an output transformer for an all-transistor Vico amplifier built in about 1958?


—L.C.F., Ardmore, Pa.

The manufacturer, Video Instruments, Inc., no longer makes Vico amplifiers. The design and manufacturing rights were sold to another company some years ago. It is doubtful that identical replacement output transformers are still available. You can rewind the transformer yourself using wire of identical size and type as the original. Or, you can have it rewound at a motor or transformer repair shop. This output transformer (an autotransformer) usually burns out because of a transistor puncture or accidental

TUNAVERTER

TUNABILITY — USABILITY — QUALITY

Marine
Police
Short-
wave

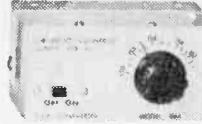

Amateur
160 M
to
2 Meters

TUMBLE, CALIBRATED solid state converters to change your auto and home radios into excellent, sensitive, selective, calibrated Amateur and VHF receivers!

- Plug into auto radio!
- No wires, no soldering!
- 6-1 reduction tuning!
- 2 WEEK MONEY BACK OFFER!
- Shipped from Stock!
- FREE 24" conn. coax!
- 100% American Made.
- 9 volt btry powered!
- Mute terminals!
- Size 2 1/4"x3 1/4"x4 1/2"

BAND	MODEL	COVERS	OUTPUT	PRICE
Marine	Marine	2.0-3.0 mc	550 kc	\$19.95 ppd
Shortwave & SWL		9.3-10 mc	800 kc	\$19.95 ppd
WWV time SW		14-18 mc	550 kc	\$19.95 ppd
160 meters	160	1.8-2.0 mc	1500 kc	\$19.95 ppd
75 meters	75	3.8-4.0 mc	800 kc	\$19.95 ppd
CB-10 M	273	26.9-30 mc	1500 kc	\$29.95 ppd
6 meters	504	49.5-54.5 mc	1500 kc	\$29.95 ppd
2 meters	1450	144-150 mc	1500 kc	\$29.95 ppd
Police, fire, etc.	{ 308, 375, 1564	{ 30-38, 37-50, 150-164 mc	{ 1500, 1500, 1500 kc	{ \$29.95, \$29.95, \$29.95 ppd
Aircraft	1828	118-128 mc	1500 kc	\$29.95 ppd

Models with Tunable BFO for SSB—CW—AM—FM!
 160 M 1600 1.8-2.0 mc 550 kc \$24.95 ppd
 80 M 800 3.4-4.1 mc 550 kc \$24.95 ppd
 75 M 750 3.8-4.0 mc 550 kc \$24.95 ppd
 40 M 400 6.97-7.325 mc 830 kc \$24.95 ppd
 20 M 200 14.0-14.35 mc 830 kc \$24.95 ppd
 15 M 150 20.975-22 mc 1500 kc \$24.95 ppd

Output kits for use with home radios state output \$1.25 ppd
 Watch For New Models!! Special Outputs On Request!
 HERBERT SALCH & CO., Dept. R, Woodsboro, Tex. 78393

Testing?



The Sept/Oct issue of **ELEMENTARY ELECTRONICS**, at your newsstand, should be basic reading for anyone who takes his electronics seriously. It features Basic Test Equipment, and goes on editorially to tell how it works and how to use it.

Also Audio Analysis with Square Waves advises how to check out your hi-fi system's amplifier . . . tells you how high the fi is.

Begin your subscription now to **ELEMENTARY ELECTRONICS** with this special offer—5 issues for \$2.00 (a 46% savings from the newsstand price).

ELEMENTARY ELECTRONICS RTV-806
 505 Park Avenue/New York, N. Y./10022

Begin my subscription to **ELEMENTARY ELECTRONICS** with the September/October issue. I am enclosing \$2.00 for 5 issues. (Outside USA & Canada, add 75¢ for postage)

Name _____
 Address _____ (please print)
 City _____ State _____ Zip _____

Ask Me Another


grounding of the speaker terminals to the chassis. Similar transformers are used in some hybrid (12-volt tube/transistor) automobile radios.

A Big Job!

Where can I get a replacement for a burned out power transformer for an old radio using two type 35, one type 24A, one type 45 and one type 80 tubes?

—J.L., New York, N.Y.

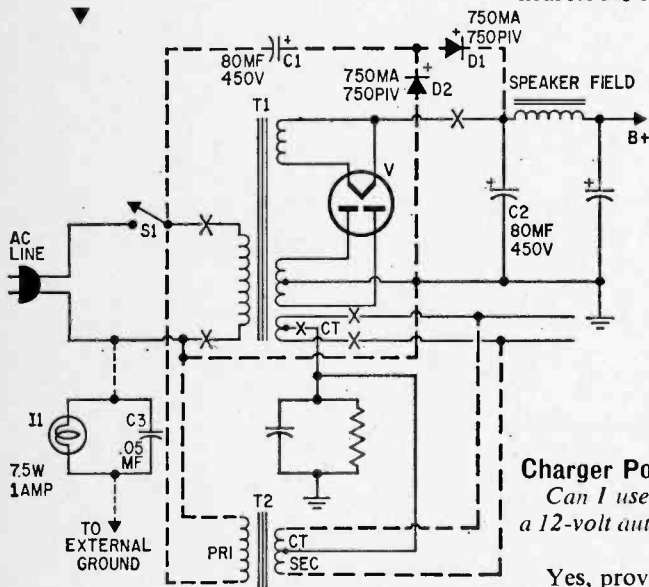Possibly at what is left of Radio Row. Or, you can get it rewound at a transformer or motor shop, but at considerable expense. Instead, you can install a 2.5-volt filament transformer (T2), two diodes (D1, D2) and two capacitors (C1, C2), connected as shown in dotted lines in the diagram. Cut the original circuits at the points marked with an X. You will then have a half-wave volt-



age doubler rectifier. But, the chassis will be hot electrically and the fuse might blow when the set is connected to a ground if the AC line plug is inserted into the electric outlet so that the ungrounded side of the power line is connected to the chassis. To avoid this problem, don't connect a ground to the radio's ground binding post. Instead, add a 7.5-watt, 120-volt lamp and an 0.05 mf capacitor, connected to one side of the line (inside the set) and an external ground (water pipe or radiator) as shown by the dotted lines. If the lamp lights when the

plug is inserted into an electric outlet, reverse its position. This time the lamp should not light.

All Around the Whip

Why is it that I can pick up so many stations on my car radio, even though the antenna is very small?

—J. D., Livingston, N. J.


Auto radios are very sensitive. The omnidirection whip antenna has a lot more pick up than the built-in bidirectional loop of most home radios.

You Can Always Tell One!

How can I tell which end of a diode is the cathode and which end is the anode?

—C. E., New York, N. Y.

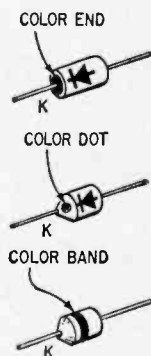Some diodes are marked with its schematic symbol, as shown in the diagram. The straight line is the cathode; the arrow is the anode. The cathode end is often identified by color at that end or a color dot or color band nearest the cathode lead.




Charger Powers Auto Radio

Can I use a 12-volt battery charger to run a 12-volt auto radio on house current?

—D. F., Scranton, Pa.

Yes, provided the charger's output voltage doesn't rise too high without a battery as a load and stabilizer. The charger must be able to supply several amperes and probably will need a very good filter circuit added to reduce hum to a tolerable level.

Best bet is to use a 12-volt battery for

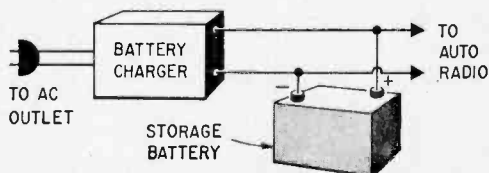

filtering, as shown in the diagram. But, why spend all that money when you can buy a transistor radio for less than \$10 and an AC job for not much more?

Improves Audio

How can I add feedback to the audio section of an AC-DC radio?

—J. N. L., New York, N. Y.

Break the first audio amplifier (V1) cathode circuit as indicated by X in the simplified diagram and insert R1 (10-ohm, 1/2-watt resistor) in the circuit. Disconnect the lead which grounds one side of the speaker voice coil to the chassis, also as noted by


an "X". Connect R2 (47-ohm, 1/2-watt resistor) from one side of the speaker voice coil to the cathode of V1. Connect the other side of the speaker voice coil to the common ground buss. If the set squeals or sounds distorted (positive feedback), reverse leads A and B to obtain negative feedback.

Crystals for RF Generator

How can an inexpensive RF Signal generator such as the Eico 324 be modified for crystal controlled accuracy?

—C.J.O., Duquesne, Pa

A different crystal would be required for each frequency and its harmonics, or a frequency synthesizer would be needed, and you would not have continuous frequency coverage. An easier way is to get a 100-kc calibrator (Hammarlund XC100 etc.) which contains a 100-kc crystal and use it to check the accuracy of your signal generator at every 100-kc point throughout the generator's tuning range. Simply feed the output of the calibrator into a radio receiver and tune in on one of its 100-kc harmonics. Also feed the signal generator output into the receiver and tune it to get a beat note with the 100-kc harmonic. Readjust the signal

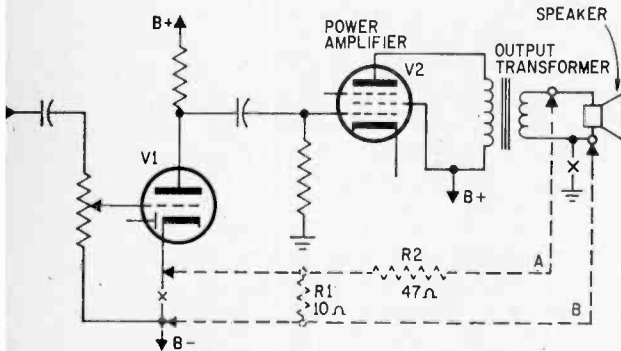

DOZENS OF SCIENCE FAIR PROJECTS

- BUNNELL VAN DE GRAFF GENERATOR
- LIGHT-BEAM TELEPHONE
- MOIRE PATTERNS
- GOLD-LEAF ELECTROSCOPE
- SCHUBERT'S OPTICS TO SEE THE INVISIBLE

SPECIAL YOUNG EXPERIMENTER SECTION!
Magnificent Experiments Right at Your Fingertips! Includes Special Recipes and Materials

NO LONGER AVAILABLE

Although the new 1966 edition of **SCIENCE EXPERIMENTER** is no longer available on a newsstand, you can still get your copy directly from the publisher.

SCIENCE EXPERIMENTER is the one magazine dedicated to the youth who is interested in experimentation, construction and "blue-ribbon" Science Fair projects. Some of the projects in this issue include a midget Van de Graff generator; light-beam telephone; moire patterns and much more.

Remember, you can only get your copy directly from the publisher. So use the coupon and we'll rush you the new 1966 **SCIENCE EXPERIMENTER**.

SCIENCE EXPERIMENTER

505 Park Avenue/New York, N. Y. 10022

RTV806

Rush me my copy of **SCIENCE EXPERIMENTER**. I am enclosing \$1 which includes postage and handling.

Name (please print)

Address

City State Zip

Please include your Zip Code

YOU CAN BUILD IT

Here's a 9 ft., 10 in. step hydro that is eligible for racing in sanctioned Class B regattas. She has a beam of 51 in. and weighs 100 lbs. without steering gear. A nifty competitor that can be constructed from Craft Print Plan #242.



RADIO-TV EXPERIMENTER

RTV806

Craft Print Division/505 Park Avenue, N. Y., N. Y. 10022

Enclosed is \$3.00. Please send me Craft Print #242. Splitfire. I understand that if I am not completely satisfied, I may return the Craft Print within 10 days for a complete refund. (Allow 3-4 weeks for 4th class delivery. 1st class, add 50c.) Add 10% for Canadian & foreign orders. N.Y.C. residents, add 5% for sales tax.

Name (PLEASE PRINT)

Address

City State Zip

Ask Me Another


generator to get zero beat (whistle on both sides) and it will be at some multiple of 100 kc. Note the difference between its dial reading at zero beat and the nearest 100-kc multiple marker.

Variable Battery Eliminator

Can you give me a circuit for an AC to DC power supply which delivers from 0 to around 12 volts at 6 milliamperes?

—L. D., Bradenton, Fla.

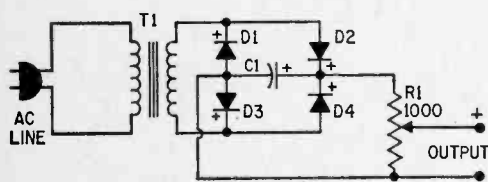In the diagram T1 is a 12-volt filament transformer, C1 is a 500-mf, 15-volt electrolytic capacitor, R1 is a 1000-ohm linear-taper potentiometer. The diodes may be of the garden variety.




AC/DC-Radio Does All

How can I use an ordinary AC-DC radio as a power supply, oscillator and intercom amplifier?

—N. G., New Carlisle, Ind.

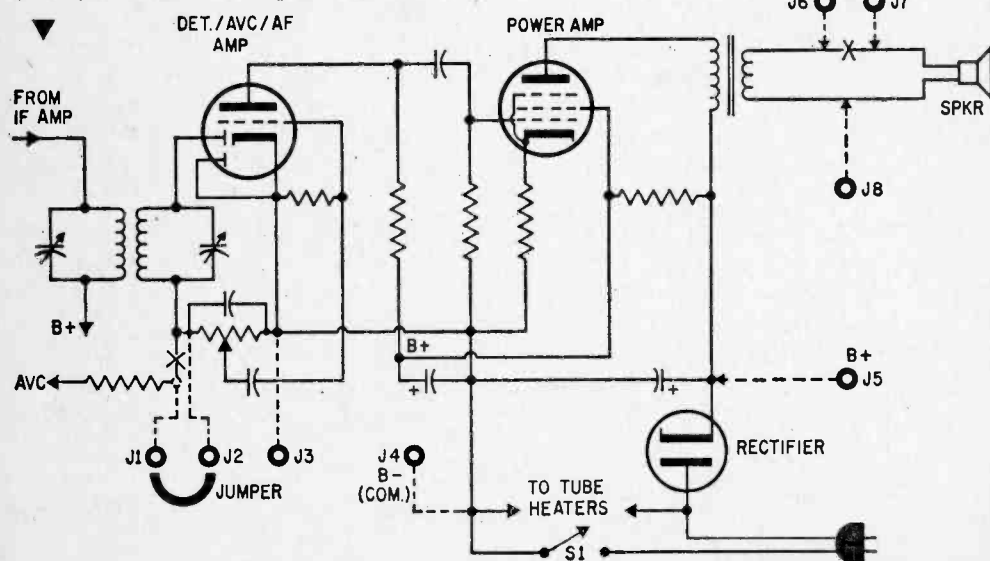Install jacks on the chassis (with proper insulating washers) or on a strip near the chassis connected as shown by dotted lines, and break the circuits at the X's. For radio reception, connect a jumper across jacks J1 and J2, and another across J6 and J7. For intercom use, remove the jumpers and connect the audio input (through an impedance step-up transformer) to



J2 and J3, and the output to J6 and J8. To obtain about 100 volts DC, connect leads to J4 (-) and J5 (+). To use the local oscillator as a test oscillator (tunes from about 1000 kc to 2060 kc), use an alligator clip to connect to the stator terminal of the oscillator section of the tuning capacitor (not shown). Use a small capacitor in series with the clip (about 22 pf) and jack J3 or J4 as the ground side. Be very careful. The whole thing can be hot—electrically, above ground—and a shock hazard exists. An isolation transformer will be a big safety factor that should not be ignored.

CRT and Then Some!


I have had a G.E. TV set for five years. Last year, I had the picture tube replaced because of loss of brightness. But now, the picture is not as bright and clear as it should be. If there is any writing, it comes out blurry. Also, whenever there is high contrast in the picture, the set produces a loud hum and the picture loses its horizontal stability. Can you please tell me what the trouble is?

—I. S., Bronx, N. Y.

After five years of use, other tubes and parts can also wear out and change in characteristics. If you want to try to do it yourself, go to a parts jobber and get a Photofacts Set on your particular set. Or, if you don't have the time, call the GE service operation (see Yellow Pages). They'll dispatch an expert—via two-way radio. Another alternative is to give it to your local ham club and buy a new set.

(Continued on page 36)

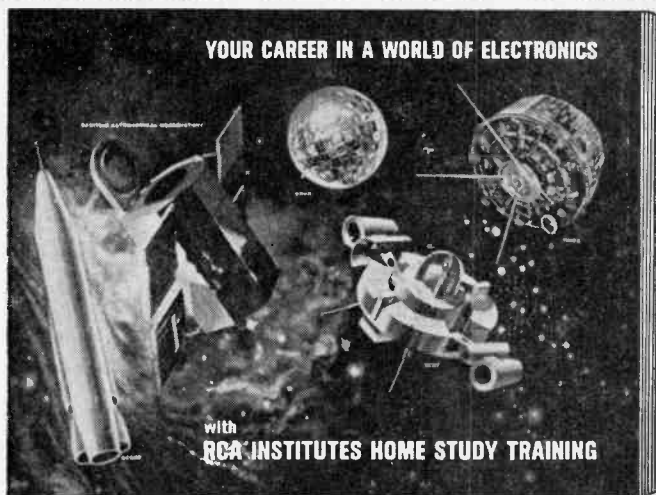SEND CARD FOR RCA'S NEW 1966 HOME STUDY CAREER BOOK TODAY



CUT THE TIME BETWEEN NOW AND SUCCESS

- Find out about RCA Institutes Career Programs.
- Learn about the amazing "Autotext" programmed instruction method—the easier way to learn.
- Get the facts about the prime quality kits you get at no extra cost.
- Read about RCA Institutes' Liberal Tuition Plan—the most economical way for you to learn electronics now.
- Discover how RCA Institutes Home Training has helped its students enter profitable electronic careers.

Lots more helpful and interesting facts too! Send postage-paid card for your FREE copy now. No obligation. No salesman will call.

RCA Institutes also offers
Classroom Training.
Catalog free on request.
(Courses also available in Spanish)



RCA INSTITUTES, Inc. Dep't. RX-06
350 West 4th Street, New York, N. Y. 10014

The Most Trusted Name in Electronics

Ask Me Another


(Continued from page 32)

Longwave Up-Verter

Can I use a frequency doubler ahead of my BCB receiver so I can receive from 275 to 700 kc (kHz)?

—J. L. D., New Orleans, La.

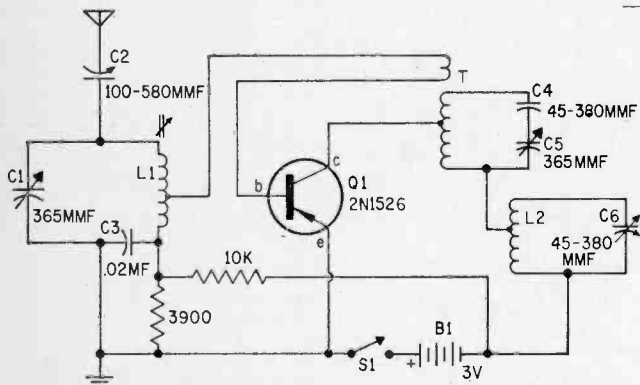Don't try to double the frequency ahead of the BCB receiver. Instead, try an up-converter using a circuit like the one shown in the diagram. Coil L1 (a tapped coil adjustable up to 3 mh) is tuned to the signal frequency (by C1; a 365 pf (mmf) tuning capacitor)—from about 170 to 500 kHz.



Transformer T is a BCB oscillator coil for 455 kHz IF which, when tuned with C5, covers from about 970 to 1300 kHz. C4 is a trimmer for limiting the tuning range of C5. Coil L2 is a BCB loopstick tuned to about 800 kHz with trimmer C6. To use it, place L2 close to the loop antenna of a BCB radio set to about 800 kHz. Tune in longwave stations with C5 and adjust C1 for best reception.

Not Legal!

On what frequency band can I operate a wireless microphone installed in the men's room in my gas station so I can listen to young punks planning trouble?

—D. K., Forest Hills, N. Y.

You can't do so lawfully any more. The FCC recently outlawed electronic eavesdropping devices except for police use. Install an electric lock on the men's room door and push the unlocking button only to let in those you trust.


9-Volts to 6-Volts DC

How can I use my AC power supply, which delivers 9-volts DC, with my 6-volt radio?

W. A., Des Moines, Iowa

Put a voltage divider (potentiometer R) and storage capacitor (C) across it as shown in the diagram. Adjust R for 6-volts output with the radio turned on while measuring the voltage

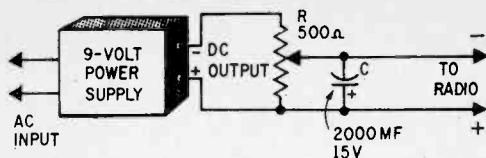across C with a DC voltmeter. It had better be a transistor radio. Automobile radios often draw as much as 9 amperes.



Another Orphan

I have Sun Ace Model PD-401 4-transistor portable tape recorder. The pushbutton system is not working. Could you tell me where it came from so I can send it back to the manufacturer for repair?

—J. G., Shawinigan South, Quebec

Never heard of that make.

Where did you buy it? It's probably an import. Why don't you take it to a local radio repair shop?

Time to Retire It

How can I make an AC converter for a radio? It uses 2 size "G" batteries wired in parallel and a 67½ volt battery.

—R. K., Morton Grove, Ill.


Don't waste your money. I just bought a 12-transistor ultra-portable radio for \$4.50 which performs rings around an old tube-type set. You ought to be able to find similar bargains in "Chicagoland."

Anti-Noise Listener

How can I hook a phone jack to my radio so that I could listen to it privately with headphones?

—W. N., Mattituck, N. Y.

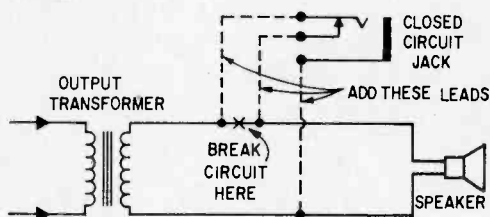Connect a phone jack to the speaker circuit as shown in the diagram and use a low-impedance (4- to 16-ohm) headset (Superex, etc.).




Never the Twain Shall Meet

I would like to change my 200-400 kHz (kc), 550 kHz-30 MHz (mc), 5-band re-


(Continued on page 123)

Workbench Tips

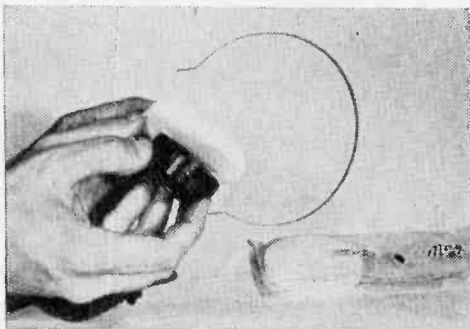■ If your SW ear phones weigh heavy on your head, take a tip from the makers of hi-fi headsets and pad them with foam rubber. Foam rubber powder puffs are ideal for the purpose and are available at most cosmetic counters. To install, simply cut a $\frac{1}{4}$ " hole in the puff's center, and cement in place as shown in photo below. Install puffs wherever headband meets top of your head.



■ Ordinary paper clips (thousands are discarded hourly) make handy, quick detachable, connectors for electrical wire ends with only slight alteration. Simply straighten out one end of the clip and attach the wire. The wire end may be spot soldered or inserted in a loop, then the loop is squeezed together in a vise or with pliers. The remaining portion of the paper clip may be used as a washer with the tab end under a terminal nut or as a simple hookup as shown in photo below.

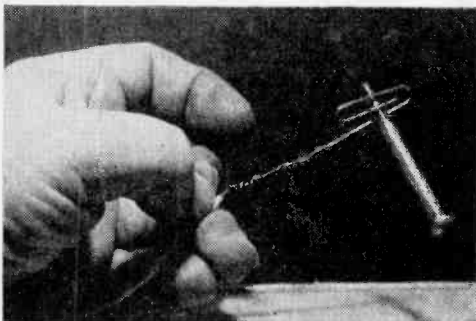

■ A frequent cause of hum (and sometimes even whistles from radios) is an improperly grounded can-type filter capacitor. Most can installations rely on their twist lock for connection to ground. In time an oxide forms—a high resistance circuit occurs. To prevent trouble, always solder at least one lug to ground in kits and when replacing.

WHAT MAKES RADIO-TV EXPERIMENTER SUCH FASCINATING READING?

It's just that in this period of time, electronics has progressed to such a fine art, that it appears in almost every phase of our existence. Subtle at times, overpowering at other times, but certainly we are living in an era where a knowledge of electronics is basic.

And that's what makes RADIO-TV EXPERIMENTER so interesting. It covers the field, whether it be theory, construction; hi-fi or audio; ham, CB, SWL; AM, FM, TV, or so many of the other related electronics subjects. It covers them, reports them, describes them, illustrates them; RADIO-TV EXPERIMENTER is certain to contain that subject of electronics which is most important to you... that's why it's so fascinating. Try a subscription and see!

RADIO-TV EXPERIMENTER RTV-806

505 Park Avenue / New York, N. Y. / 10022

I'm convinced that RADIO-TV EXPERIMENTER is for me. Begin my subscription immediately. I am enclosing \$4.00 for 1 yr.; \$7.00 for 2 yrs.; \$10.00 for 3 yrs. Bill me. (Outside USA and Canada, add 75¢ a yr.)

Name _____ (please print)
 Address _____
 City _____ State _____ Zip _____

LEARN Electronics Engineering AT HOME

Fix TV, design automation systems, learn transistors, complete electronics. College level Home Study courses taught so you can understand them. Earn more in the highly paid electronics industry. Computers, Missiles, theory and practical. Kits furnished. Over 30,000 graduates now employed. Resident classes at our Chicago campus if desired. Founded 1934. Catalog.

AMERICAN INSTITUTE OF ENGINEERING & TECHNOLOGY
 1139E West Fullerton Parkway Chicago, Illinois 60614

TRANSISTORIZED CONVERTER KITS \$5.00 EACH

Three kits available. Marine 2-3 mc, police & fire, high band 100-200 mc, low band 26-60 mc. 1 mc tuning on car radio. Full instructions.

ANY KIT \$5.00 pp. WIRED \$15.00 pp.
 MESHNA 198 ALLERTON LYNN, MASS. 01904

ALL BAND TRAP ANTENNA!

Reduces Interference and Noise on All Makes Short Wave Receivers. Makes World-Wide Reception Stronger. Complete with 95 ft. 72 ohm feedline. Sealed resonant traps. For noise and all class radio amateurs! Eliminate 5 separate antennas with better performance guaranteed. 80-40-20-15-10 meter bands. Complete 102 ft. \$17.95. 40-20-15-10 meter bands, 54 ft. (best for world-wide short wave reception) \$18.95. Send only \$3.00 (cash, o.k., m.o.) and pay postman balance COD plus postage on arrival or send full price for postpaid delivery. Complete instructions included!


Midway Antenna • Dept. ARE-10 • Kearney, Nebraska

ELLERY QUEEN'S ANTHOLOGY On Sale September 15


If you're a devotee of the best in mystery, detective, suspense and crime stories, don't miss the new ELLERY QUEEN'S ANTHOLOGY—\$1.25 at your newsstand. Or write, Ellery Queen's Anthology, 505 Park Avenue, New York, N. Y. 10022 and add 25¢ for postage and handling.

ANTENNA ANTICS


By Jack Schmidt

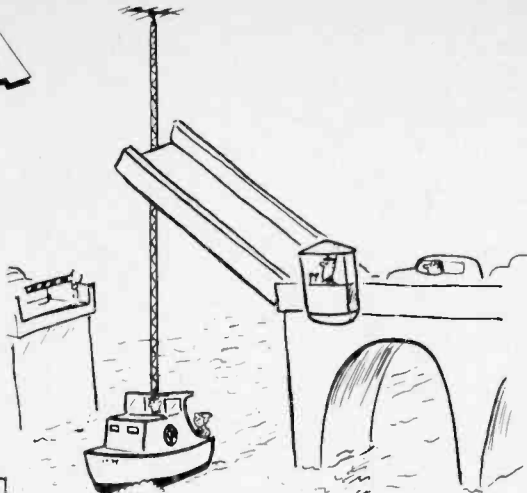

They finally got here to trim the trees!

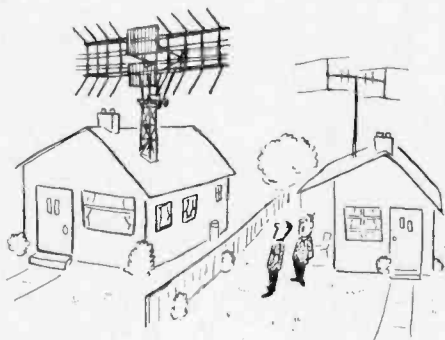

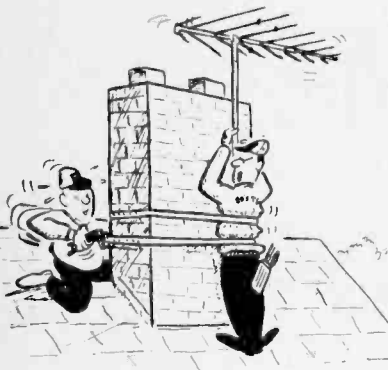It's a fake!
He doesn't even have a TV set.




Hold it—hold it—hold it!!!



Relax Bud, this isn't mine! It's part of the instrument system for a new airport here!

INSTANT

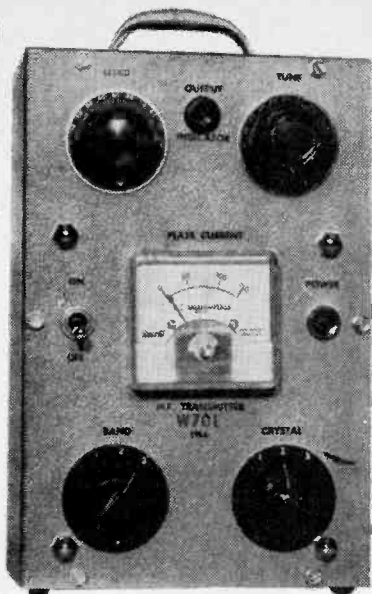

An ideal first transmitter for the Novice ham, this little rig requires but a single tube and a handful of junk-box components.

by Howard S. Pyle, W70E


HAMMING

■ This project started out as a low-power transmitter specifically for Novice-class use. As the design progressed, however, it became increasingly evident that a few simple changes would produce a versatile and flexible transmitter well suited to a variety of applications. Construction of the prototype then proceeded on this basis; the final outcome is this compact little rig which is not only ideal for Novice operation but could well be carried on to other Ham activities through many years.

Band-switching offers instantaneous shifting to the three VHF bands permitted the Novice. Complementary to this is choice of an appropriate crystal in each of the three bands or, if so desired, any one of three crystal frequencies in a chosen band. This is accomplished through a rotary selector switch.

After the Novice has secured the additional privileges of a General-class amateur, it will be found that proportioning of the LC tuning circuit is such that the 20-meter band may also be tuned with the band switch in the 15-meter position. Additionally, if VFO rather than crystal-controlled operation is later desired, an external VFO may be plugged into one of the crystal positions and used on any of the bands within the limits of the transmitter.


This rig can serve the Novice well dur-

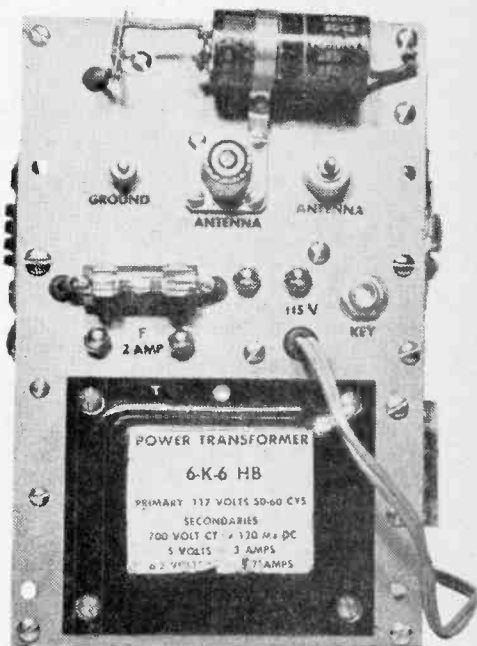

Rear view of the compact rig (above) shows both antenna connections, jack for key and fuse. Watch out for positive connection on electrolytic capacitor—it's hot! Front panel of rig is shown at top of page.

HAMMING

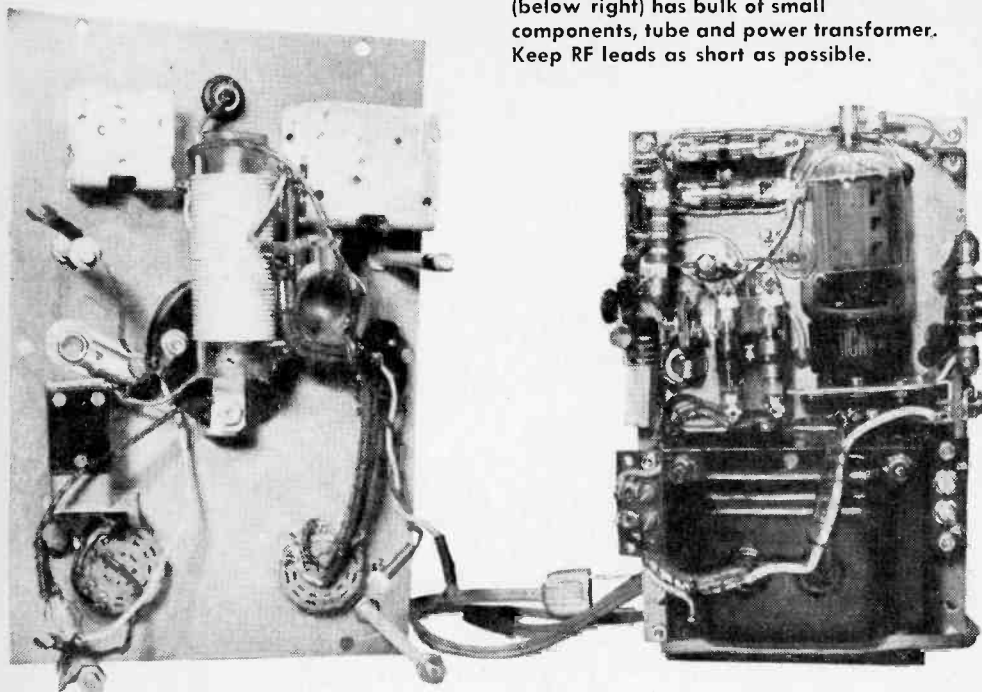Rear of front panel (below left) has relatively few components mounted on it—just tuning capacitors and coils, and the switches. Rear panel (below right) has bulk of small components, tube and power transformer. Keep RF leads as short as possible.





PARTS LIST FOR LOW-POWER, GENERAL PURPOSE TRANSMITTER

- C1, C2—.001-mf, 600-volt, ceramic-disc capacitor
 C3—409-mmf, (pf) variable capacitor (Allied 13U524 or equiv.)
 C4—365-mmf, dual variable capacitor (Allied 13U521 or equiv.)
 C5—10-mmf, ceramic capacitor
 C6—100-mmf, mica capacitor
 C7, C8, C9, C10—.001-mf, 600-volt ceramic capacitor
 C11—16-, 16-mf, 450-volt dual tubular electrolytic capacitor (or single section equiv.—approx. 40-mf. minimum)
 C12—1000-mmf, mica capacitor
 D1, D2, D3, D4—150-ma, 400-piv (prv) silicon rectifier (see text)
 F1—2-amp. 3AG fuse
 FT—Feedthrough insulator (Birnbach 458 or equiv.)
 I1—6-8 volt, 150-ma pilot lamp (Type 40, 47, 50, 51—to fit assembly)
 I2—Neon lamp, 5C. miniature bayonet base (NE-51 or equiv.)
 J1—Phone jack (for key)
 J2—Coaxial panel receptacle (Amphenol 83-1R or equiv.)
 L1—15-meter coil (6 turns on 1-inch form—see text)
 L2—40-/80-meter coil (34 turns on 1-inch form—see text)
 L3—Parasitic choke (6-turns AWG-20 enameled wire wound on R2)
 L4, L5—2.5-millihenry RF choke
 M1—0-150 ma DC milliammeter (Shurite 850 or equiv.)
 R1—47,000-ohm, 1/2-watt resistor
 R2—100-ohm, 1-watt resistor
 R3—47,000-ohm, 2-watt resistor
 R4—10,000-ohm, 10-watt resistor
 R5—126-ohm, 5-watt resistor (IRC PW5 or equiv.)
 S1, S2—5-p. 3-p rotary selector switch (Centralab 1401 or equiv.)
 S3—5-p.s.t. toggle switch
 T1—Power transformer, 117-volt pri.; 700-volt CT at 120-ma., 6.3-volt CT at 4.7-amp., 5-volt at 3-amp. sec. (Knight 62Z044 or equiv.)
 V1—6DQ6B type vacuum tube
 X1, X2, X3—Fundamental-frequency quartz crystals—select for frequency of operation.
 1—Portable aluminum carrying case, 9x6x5-inch (Bud ACC2095 or equiv.)
 Misc.—Tube socket, fuse holder, diode holder(s), terminal strips, plate cap, threaded rod, tie strips, coil forms, pilot-lamp assemblies, grommets, line cord, cable lacing cord, hookup wire, solder, machine screws, nuts, washers, etc.
- Estimated cost: \$30.00 (crystals not included)
 Estimated construction time: 9 hours.

HAMMING

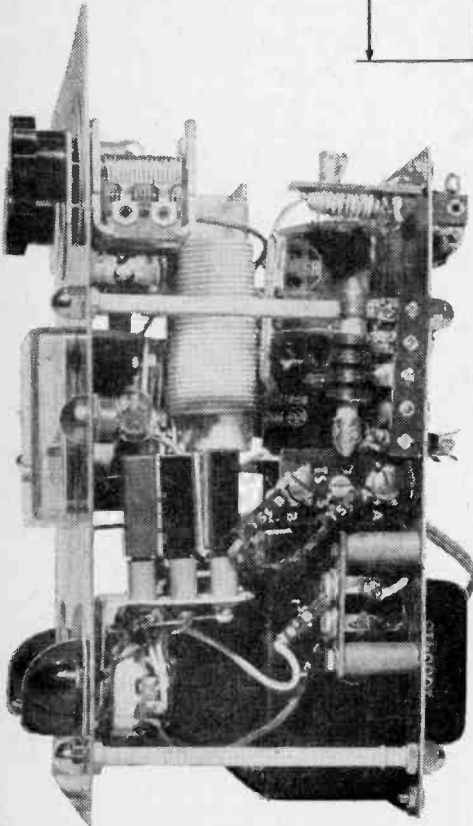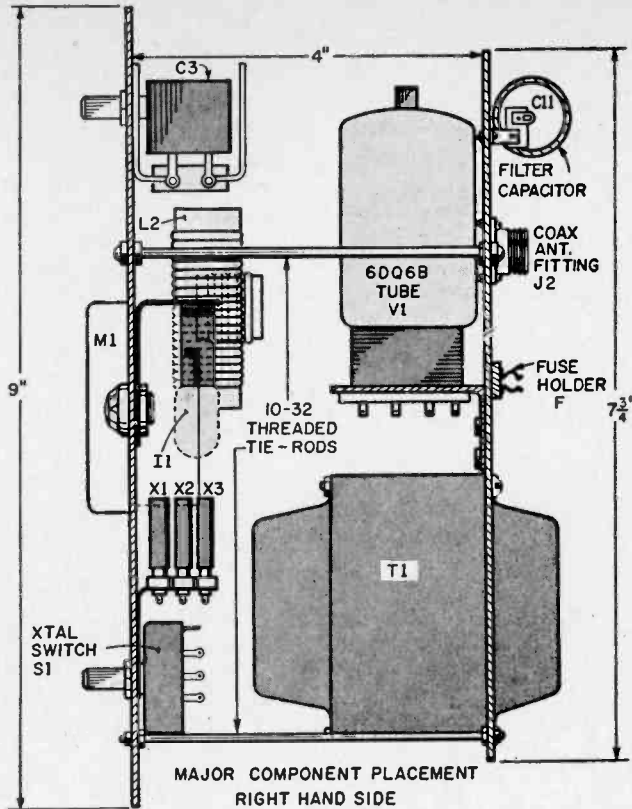Right-side view of rig has major components called out on drawing at right. Some components are partly obscured in photo below. If you're buying components select small-size versions where you have a choice. Make sure pilot lamp I1 matches filament-to-jewel for maximum brightness. You might want to mount crystals for removal without opening metal cabinet.




side of this panel, shown in another photo, is the main section of the power transformer with the bracket for the 6DQ6B tube mounted above and to the right of the transformer shell.

The balance of this side of the panel accommodates a number of tie-points mounting a number of smaller components such as resistors, capacitors, RF chokes, etc. The silicon rectifiers were also mounted here in the fuse-clip type of holder. Two 400 PIV diodes are used in series in each leg of the high-voltage secondary windings; however, if you use diodes of 750 PIV rating or higher, you can get by nicely with two.


Small screw-type terminal strips were variously placed where they would be conveniently accessible with a screwdriver after the panels were sandwiched. The few wires from front-panel components were soldered in their positions on the rear of the front panel with spade-type solder lugs at the loose ends to permit easy connection to the rear-panel terminal strips.

Winding Coils. The two variable (tuning) capacitors appear at the top rear of the front panel with the 40/80/meter coil be-

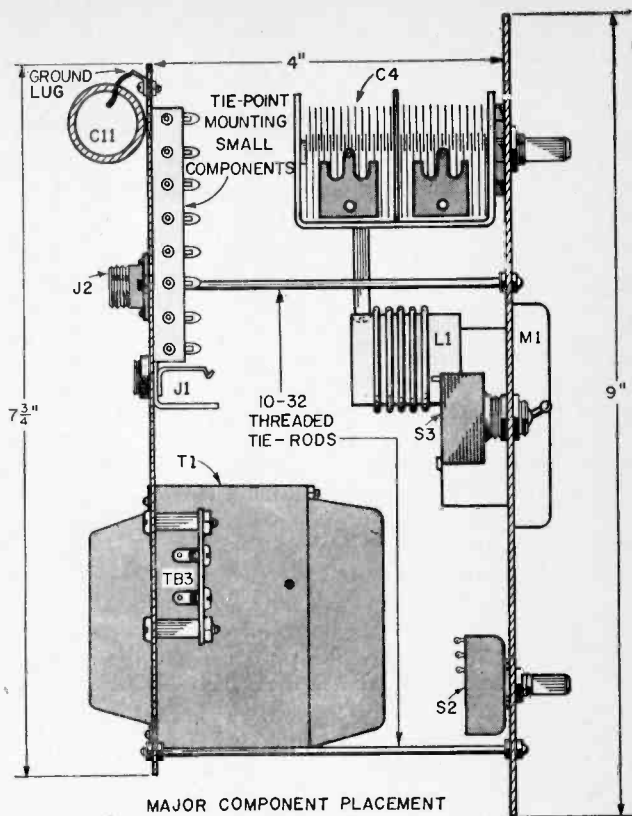Way over-rated filament windings of transformer take up much room that could have been used for components. Top bell of transformer was removed and reassembled with rear-panel cutout between bell and laminations to cover rough edges of cutout. If you open transformer case be careful of leads, winding insulation. Add ventilation holes if you send long messages.



MAJOR COMPONENT PLACEMENT
LEFT HAND SIDE

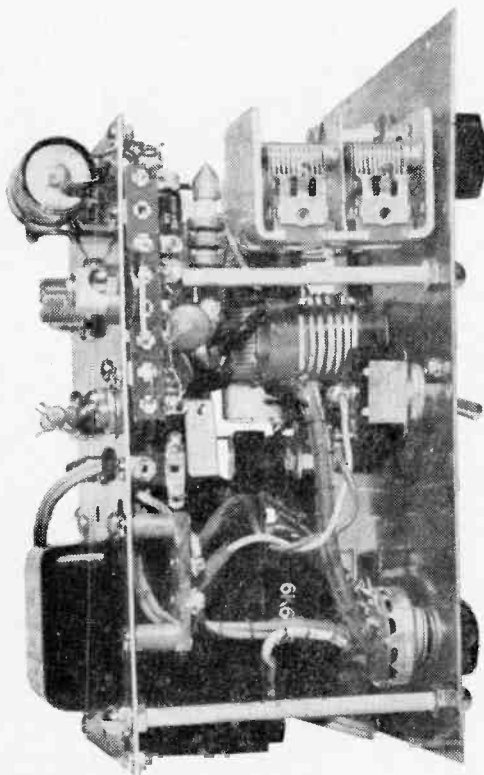

tween them. The 15-meter coil (L1—which will also cover 20 meters) is placed at right angles to the main coil just below the loading capacitor. Both coils are wound on 1 in. O.D. Lucite tubing with AWG-14 insulated automotive primary ignition wire (available at many automotive supply houses and gasoline service stations). The insulation on the wire serves to automatically *space-wind* the inductor.

The larger coil (L2) is 34 turns—tapped at the 17th. The small coil (L1) is six turns and is spaced additionally about the thickness of the wire. Both coils are used in series on 40 and 80 meters. The large coil is automatically switched out of the circuit on 15 or 20. The larger coil is supported at the bottom by a small metal strap to one of the meter mounting screws and at the top by its connection to the loading capacitor. The small coil is attached to the bottom of the loading capacitor by a convenient (threaded 6-32) hole in the bracket, of the type capacitor specified. A 1-in. 6-32 machine screw and a 3/4-in. spacer collar are used for this.

Front Panel. The power on/off indicator

HAMMING

light assembly and a small bracket (held under the mounting stud of the crystal selector switch) appear to the left. On the right of the panel is the s.p.s.t. toggle switch for power and below it, the band-change switch. The lug-fitted pigtail leads, for connection to terminals on the rear panel, can be clearly seen in the photo which also shows the 10-32 threaded rods (spaghetti covered for a more finished appearance) which clamp the two panels together. The output indicator lamp (I2), at the top center of the panel, is mounted by merely pushing it part way through a snug fitting grommet and soldering the RF lead to its base.

Putting It Together. Actual construction and wiring involve the usual drilling and cutting and normal soldering operations. And since construction of this little rig is adaptable to just about any parts you may have as well as those you choose to buy, we have included no dimensional details. However, there are two restrictions to keep in mind: component values should be as close as pos-


sible to those given and their physical sizes must be such that the cabinet and two panels will accommodate them.

Having gathered general ideas from the preceding paragraphs, your resourcefulness and initiative should enable you to duplicate this little transmitter in performance and rather closely in physical appearance. In the parts list, keyed to the schematic, we have shown the actual parts which we used, together with their electrical values. This will serve as a guide in choosing your components.

Tuning. This, of course, follows the conventional procedure; with the *tuning* capacitor, dip the milliammeter reading to minimum. With the *load* capacitor build the meter reading up to about 80 or 90 milliamperes, readjusting the tuning capacitor as required to keep the 'dip' point which, in the final setting, will coincide with the 80 to 90 milliamperere reading.

Careful planning and attention to constructional details will produce a piece of equipment with workmanship, appearance and performance you can well be proud of. Even more important, it should provide you with many hundreds of hours of pleasurable operation. ■

WORLD'S SMALLEST CLOCK RADIO?

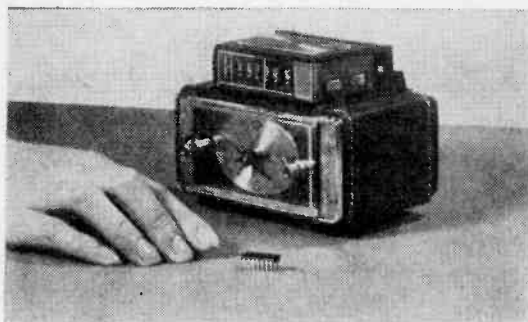

■ First consumer entertainment product to use microelectronic circuitry for all primary functions, General Electric's new miniature rechargeable radio is no larger than a pack of cigarettes. All essential electronic elements are contained in a single microcircuit.

The unique new portable comes with a recharger base containing a clock, resulting in what may be the world's smallest clock radio. The radio portion can be detached from the charger and carried anywhere. When fully charged, it will play up to 12 hours completely unattended.


The radio is the first of a full line of GE

products to incorporate microcircuits. Actually the third generation of electronic components, microcircuits are an outgrowth of both the vacuum tube, invented before the turn of the century, and the transistor, introduced in 1948.

Measuring 1 x 2 $\frac{1}{16}$ x 3 in., the new radio has a textured plastic case, a slide-rule dial, and thumbwheels for easy tuning. The clock recharger unit includes an extra speaker, giving the radio added fidelity whenever it is plugged into the recharger.

The clock radio sells for \$39.95; another model with a non-clock charger is \$29.95. ■

RECEIVERS NEED ANTENNA TUNERS TOO!

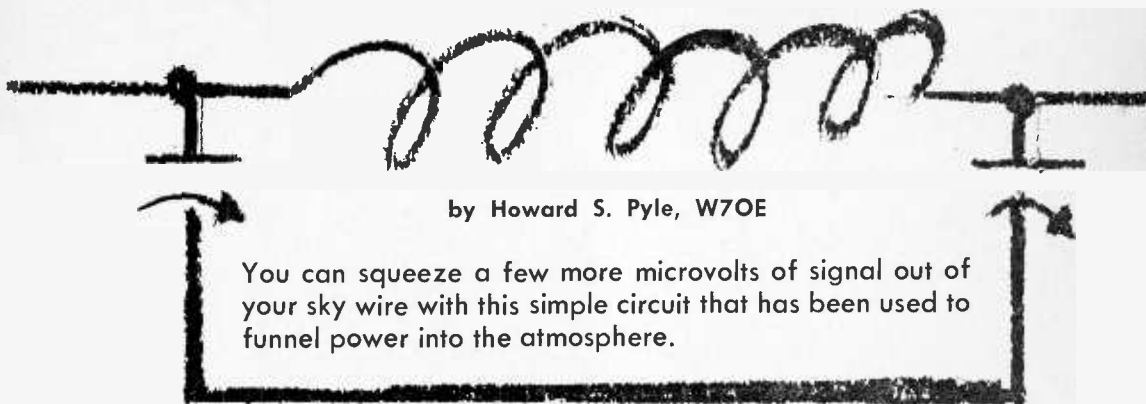

by Howard S. Pyle, W7OE

You can squeeze a few more microvolts of signal out of your sky wire with this simple circuit that has been used to funnel power into the atmosphere.

■ The expression, *antenna tuner*, is a household word around the Ham shack. Instantly it is associated with transmitting equipment. And even though 9-out-of-10 current-model Ham transmitters incorporate an integral pi-network tuning arrangement, most present-day hams have built, or purchased, and installed, an external antenna tuner—using any one of a number of circuits. The thinking is, such a device improves the transmitting capability of a station (and those who use it insist that it does) why not apply the same thinking to the receiver?


The average Ham communications receiver has little provision for resonating the antenna circuits and the receiver input. What is generally provided is nothing more or less than a trimmer capacitor in series with the input or in parallel to the RF-stage tuned circuit. Where one antenna is used for both transmission and reception, installations including an antenna tuner or coupler, often feed the incoming signal through the antenna tuner—automatically matching the antenna to the receiver-input circuits. Many however are not so well arranged.

In the case of the Ham who uses a separate receiving antenna, this antenna is invariably connected directly to the antenna terminal on the receiver.

A Wee Bit of Theory. At my station, W7OE, I use separate antennas for receiving only on the three popular amateur bands—20, 40 and 80 meters. I decided to try an external antenna tuning network. The thought was inspired through my fairly recent acquisition of one of the novel British-

made *JoySTICK* antenna systems. With the shipment was included one of their Type 5 *JoyMATCH* tuners, a simple variable LC network for use with transmitters, and a Type 3, receiver *JoyMATCH*. This latter was a conventional pi-network tuner identical to the arrangement used in practically all *transmitters* used by the Ham.

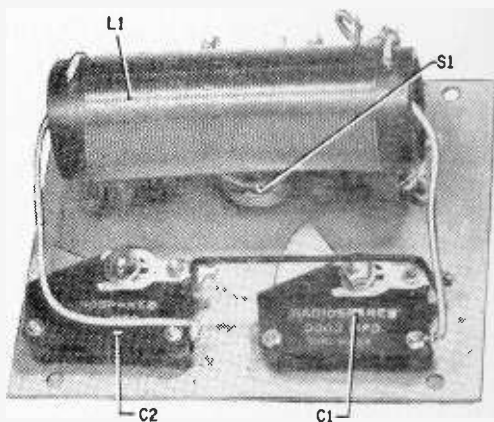As a firm believer in following manufacturers' instructions to the letter—especially in handling any electronic gear, I connected the Type 3 antenna tuner into the circuit according to the instruction sheet. As the antenna tuner incorporates a tapped inductance and variable series capacitors, close tuning over the full LC range is possible. The tap may be placed to select any amount of




It only takes four components to make a signal-boosting antenna tuner for more DX.

winding, in small increments, or to completely eliminate the tuner from the circuit.

A bit of experimenting soon indicated that using the antenna in the conventional manner (with the tuner out of the circuit), provided normal signal reception—the same as with any conventional antenna connection. However, by adjusting taps on the coil and balancing the input by adjusting variable capacitors C1 and C2 a very noticeable improvement in signal strength was immediately evident. An added bonus was that as the signal level came up, the noise level went down!

Reasoning along the same lines, it appeared that whereas the *JoySTICK* antenna was rather novel in physical construction, it nevertheless embodied the same LC characteristics of more conventional antennas. So why shouldn't *any* antenna respond with improved input to the receiver if an antenna tuner were inserted?

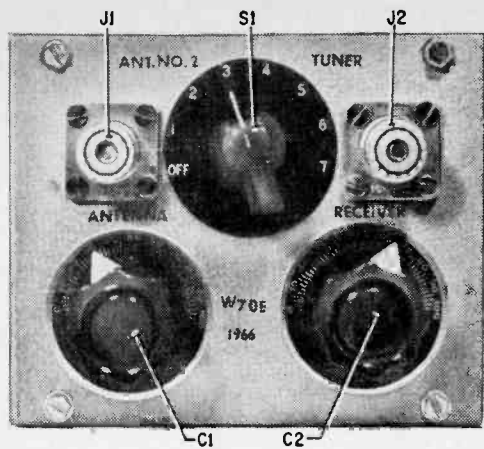Having six antennas available, I tried it with each one. Three of my antennas are dipoles—each cut to a half wavelength for one of the three popular Ham bands—20, 40 and 80. The other three, used interchangeably for receiving, are a conventional 18-foot



Front panel of antenna tuner may seem a little crowded—miniature knobs and RF connectors will give you a little more knuckle room. Connectors can go on rear.

base-loaded vertical, a random-length wire (about 75-feet) and of course, the *JoySTICK*. With the coax switching arrangement I have, I can instantly switch any one of the six antennas to any one of three transmitters or three receivers. Therefore it was possible to make comparison tests with all six antennas on the receivers only.

Significant Results. In every case substantial improvement in signal strength and signal-to-noise ratio were apparent when *any* antenna was connected to *any* receiver through the antenna tuner. After a few weeks of experimenting (through actual on-the-air operation), I was sold; the antenna tuner would stay as a permanent station accessory. As I already had the components in the Type 3 *JoyMATCH*, I simply mounted them in an aluminum utility cabinet, and wired in a rotary tap switch in place of the alligator clip originally supplied.

(Continued on page 124)

PARTS LIST

C1, C2—365 mmf variable capacitor (Lafayette 99R6217) or 15-409 mmf variable capacitor (Allied 13 U524)

J1, J2—Coaxial connector (Amphenol 83-1SPN or equiv.)

L1—80 turns, AWG 18 enameled wire on 1¼-inch dia. coil form 4-inches long (tapped every 10 turns)

S1—1-pole, 2-17 position rotary switch (Centralab 32117J or equiv.)


1—Cabinet, 3 x 4 x 5-inch aluminum utility cabinet (Bud CU728 or equiv.)

Misc.—Dial plates, hookup wire, solder, etc.

Estimated cost: \$7.00

Estimated Construction time: 2 hours

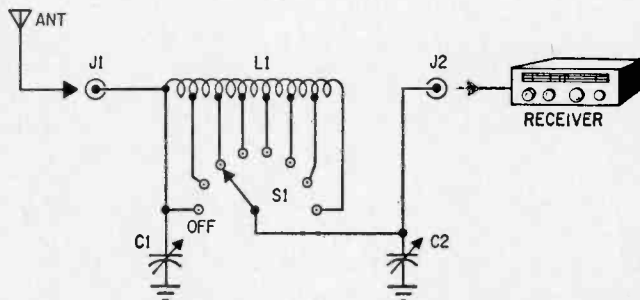
Simple circuit is quite like those used for early crystal radios. Tuner can be used to get more out of low-power rigs that do not have built-in antenna tuners or pi-networks. For high-power transmitters you'll need wide-spaced-plate capacitors and heavier wire.



All-Electronic T/R Switch for Hams

by Marshall Lincoln

K9KTL

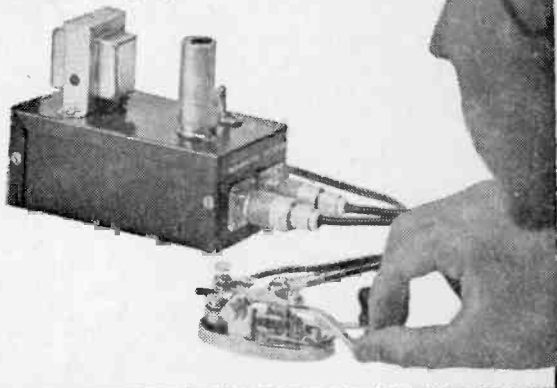

Take a hint from the professional brass pounders—use a T-R switch for instant break-in during pauses in CW transmissions—and make your CW contacts enjoyable.

■ It happens to every newcomer to the amateur CW bands. You start what promises to be a long QSO with an interesting op who has a smooth fist and a strong sig—599 and “in the clear.”


With confidence, you launch forth with a rundown on the rig, the antenna, the weather and the gossip from last night’s radio club meeting. Then you sign over to the other op,

snap the plate switch off, . . . and listen with dismay to the ten other QSOs that sprang up on your previously clear frequency while you were transmitting. You just barely manage to hear your 599 contact whisper “SRI OM — —QRM VY BAD— —HPE CU AGN 73 . . .”

Drat and Fiddlesticks. Another QSO shot full of holes by bunch of dad-blast-its who came on while you were transmitting. If you could have heard them when they started, you would have asked them to join your QSO, or moved to a different frequency to maintain contact. But now the damage has been done. Looks like it’s either buy a kilowatt or take up stamp collecting. If only there were a way to have your cake and eat it too.

There Is, You Know! With the inexpensive accessory shown here, and nothing more, you really can transmit and receive at the same time! Impossible? Not at all!

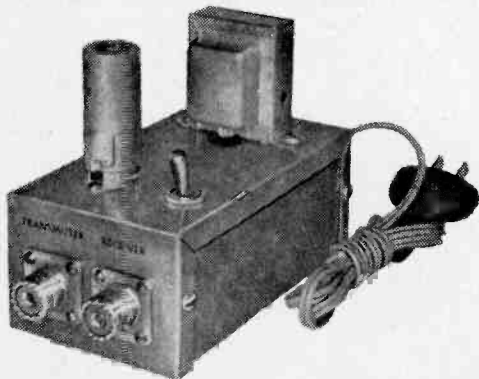This little helper for the frustrated CW man is a T-R switch. The T-R stands for transmit-receive. The CW traffic hounds



This little unit does a big job and can be stashed in any little nook on the desk.

T/R Switch for Hams

have been using such wonder boxes for years. A T-R switch is guaranteed to cure more headaches than a boxcar load of those super pain killers you see nightly on the 21-inch magic lantern. Although there are a multitude of different designs for these handy gadgets, the one shown here is one of the simplest and easiest to build—an evening or two should put you in business.

How? What it does is allow your receiver to operate *all the time*. (You don't mute the receiver when you transmit.) You monitor your own signal (always an excellent idea), and you also hear the other guy—along with any crud that shows up on the frequency—in between your own dits and dahs.

When you use a T-R switch, you take out your antenna relay—there no longer is any need for it. This is because the T-R switch does the work of the relay, and more besides. The principle is illustrated in Fig. 1. Note the transmitter is connected directly to the antenna *all the time*. The receiver is connected to the antenna through the T-R switch, which uses a vacuum tube in place of a set of relay contacts to switch the receiver into the antenna circuit whenever you open the key.

When your key is up, the transmitter is not putting power into the antenna, so the receiver is free to use the antenna for receiving signals. When you press the key down, the transmitter radiates energy into the antenna. The T-R switch jumps into action at this time to stop that bolt of energy from going into the receiver input terminals. In short, the T-R switch isolates the receiver from the antenna whenever the transmitter is keyed, and it allows normal operation of the receiver whenever the rig is unkeyed.


It's That Easy. Look at Fig. 2—it shows the working principle of a T-R switch. The grid of the tube in the switch is connected to the antenna feed line through a capacitor, which couples incoming signals to the tube. The receiver, in turn, is connected across the tube's cathode resistor to "pick off" these signals.

When the transmitter is keyed, its signal must pass from grid to cathode of the T-R tube, which effectively prevents it from passing along a sizable signal to the receiver. In


this way, the tube prevents the disaster which would occur if the receiver were coupled directly to the transmitter while it was keyed.

Although the receiver is isolated from the antenna during key-down periods, it still receives the transmitter's signal because of its proximity. As a result, you hear your own sending when your key is down, and you hear everyone else on the frequency when your key is up.

This makes it easy for another station to "break" you, since you can hear him during each tiny interval your key is up. This explains why traffic handlers use such an arrangement in their stations. If the station receiving traffic misses a word in a message, the operator merely holds his key down or sends a string of dits with his bug. The sending operator, because he has a T-R switch, hears this and stops until the receiving operator tells him what he missed. This saves a lot of time which would be

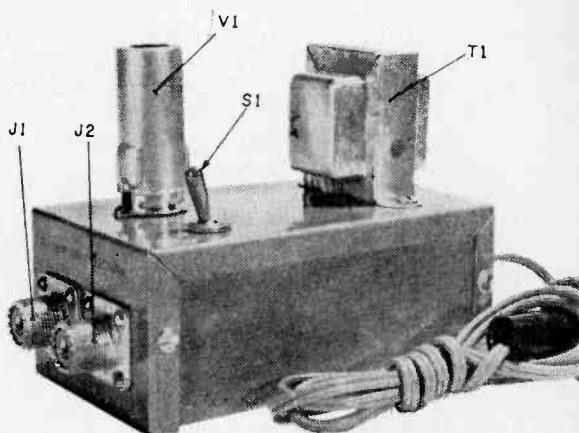

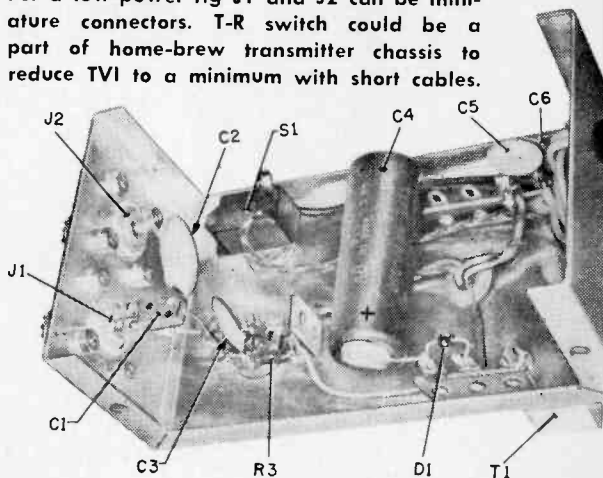For a low-power rig J1 and J2 can be miniature connectors. T-R switch could be a part of home-brew transmitter chassis to reduce TVI to a minimum with short cables.



consumed by getting "fills" after the message was sent.

The T-R switch also helps make for faster traffic work and smoother QSOs by enabling a sending operator to know immediately when interference pops up on his frequency. When it does, he can check to see if the guy he's working is still copying satisfactorily, and, if not, take corrective action. The other fellow, of course, can break in anytime to report any trouble he's having in copying.

The unit pictured here has been kept as

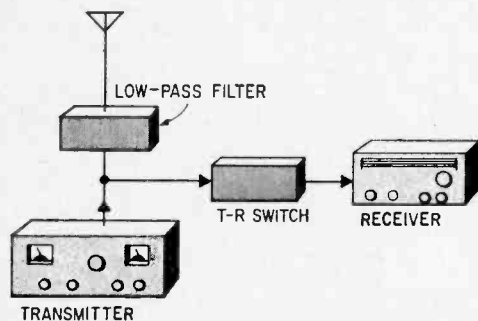


Fig. 1. Block diagram of connections makes it easy to hook up T-R switch. T-R switch, filter and transmitter can be in one unit.

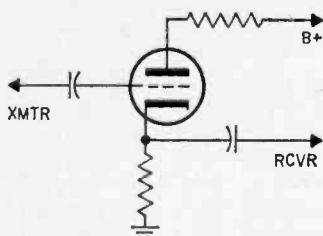


Fig. 2. Simplified circuit of the T-R switch makes it easier to understand the operation of this worthwhile addition to any station.

simple as possible while incorporating its own power supply. You can eliminate the power supply if you want to steal a little power from your receiver to operate the T-R switch. Its needs are very moderate—6.3 volts @ .15 amp (150 milliamperes) for the heater and 150 to 250 volts at a few milliamps for the plate. Fig. 3 shows the circuit for the unit pictured here.

Be sure the unit is well shielded and keep the coax lead from the T-R switch to transmitter as short as possible to guard against TVI. The simplest way to connect the antenna and T-R switch to the transmitter is with a coax T-fitting on the back of the rig. If a low-pass filter is used, it should be connected in the feed line *beyond* the T-R

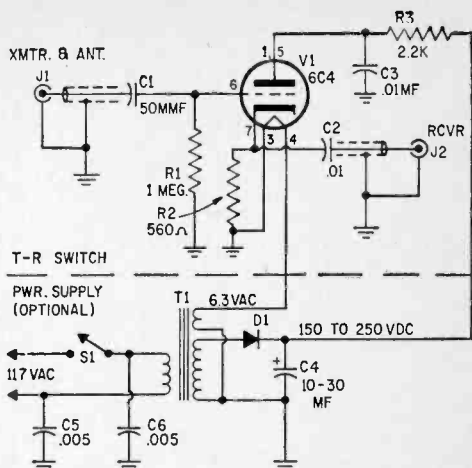


Fig. 3. Complete schematic diagram details optional DC power supply and T-R switch.

T-R SWITCH PARTS LIST

- C1—50-mmf., mica capacitor
- C2, C3—.01-mf., disc capacitor
- J1, J2—coax connector (Amphenol 83-IRTY or equiv.)
- R1—1,000,000-ohm 1/2-watt resistor
- R2—560-ohm, 1/2-watt resistor
- R3—2,200-ohm, 1/2-watt resistor
- V1—Vacuum tube (type 6C4, 6C4W, 6C4WA, 6100 or equiv.)

POWER SUPPLY PARTS LIST

- T1—primary 117VAC; secondaries, 6.3-VAC @ .15 amp and 150 to 250-VAC @ 15 ma.
- C4—10 to 30 mf., 350-V electrolytic capacitor
- D1—Silicon rectifier (Lafayette 19R5001 or equiv.)
- C5, C6—.005 mf., disc capacitor
- Misc.—Tube socket, tube shield, chassis box, coax, wire, solder, hardware, etc.

Estimated cost: \$7.50
Estimated construction time: 4 hours

switch—in other words, the T-R switch should be closer to the transmitter in the line than the low pass filter. The proper position for a low-pass filter is indicated by the dotted box in Fig. 1.

Parts Placement. It's not critical, and components may be installed differently from the arrangement shown here as long as good RF-construction practice is followed. Also, the unit can be constructed in a much smaller box than the 5 1/4 x 3 x 2 1/8-inch chassis box shown here, if you wish. However, be sure that C1 has a voltage rating high enough to safeguard it from breakdown due to the high voltage in your rig.

The power transformer (T1) in the unit is a surplus job having a 150-volt secondary. Any transformer which has a high-voltage

T/R Switch for Hams

secondary that will give 150 to 250 volts DC for the B-plus will be satisfactory. The filter capacitor and diode ratings are not critical either, as long as they have adequate voltage ratings for the transformer you select.

Hook Up. Coax connectors on the end are for connections to transmitter (and antenna) and to receiver—and don't get them mixed up! The line cord could be fed into the receiver, if you wish, so the T-R switch is turned *on* and *off* at the same time as the receiver. (Remember, the T-R switch must be turned *on*, even if you do not plan to transmit, to feed the signal from the antenna to the receiver.)

If you get heater and plate power directly from the receiver instead of building the self-contained power supply shown here, the T-R switch also will be automatically turned *on* and *off* with the receiver—a very convenient feature.

Do you now have a relay, actuated by either the transmitter or receiver change-over switch, to mute the receiver when the

transmitter plate switch is *on*? You must disconnect this relay. The receiver must operate *all the time* to get benefit of the T-R switch.

If you want to operate both phone and CW, you have to keep the muting relay in operation when working phone—otherwise, the unmuted receiver will feed a signal into the mike, causing audio feedback. So, install a switch so you can disable the muting relay when you are operating CW break-in.

Using It. When using the T-R switch, you may notice that tuning the transmitter tank circuit, even without the transmitter being turned on, will have an effect on the signal strength in the receiver. This is because the transmitter final tank is, in effect, now connected in parallel with the receiver antenna coil. So, even if you are just listening around the band, and maybe don't even have the transmitter turned on, you will have to adjust the final tank tuning capacitor to get the strongest signal in your receiver.

When you tune up the transmitter for operation on a given frequency, you automatically get the final tuning capacitor setting that will reinforce the incoming signal for maximum strength in the receiver on that frequency. ■


TV IS BEST AT THE RACES



■ Since this extensive closed-circuit TV system has been installed at the Monmouth Park Racetrack, N. J., you can forgo the many inconveniences often encountered at the track—like sitting on the hard grandstand seats, getting sunburned or caught in the press of sporting humanity. You no

longer have to worry about someone filching your favorite refreshment when you run from the bar to the rail—in fact you don't even have to unbend your elbow to be right in at the photo finish.

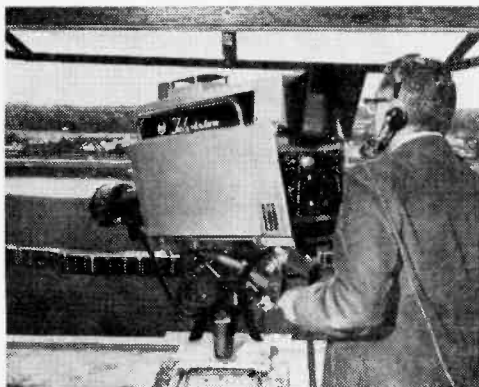Equipment made by the RCA Broadcast and Communications Products Division is used to give the track patrons, gathered around the sixty 23-inch monitors, the same picture quality they'd get at home—complete with special effects like a zoom lens for following the race; split screens, lap dissolves and text insert. ■



THE CASE OF THE BROADCASTING TOOTH

BY K.C. KIRKBRIDE

When your teeth start hearing things—that's bad. But, when they start talking back, you've had it.


■ A young man walked into the reception room of a radio station in upstate New York, claimed he could hear the station's programs without benefit of radio receiver.

Before packing and mailing the gentleman to the local koo-koo place the station employees decided to give his weird story a whirl. Taking their new-found friend to a room on another floor of the building where they could be sure he would not hear either receiver or speaker, they asked him what program was now "on the air." And he told them.

Further investigation proved a deposit of carborundum lodged in the man's tooth was acting as a rectifier, receiving radio programs, saliva in his mouth acting as a conductor. Still further investigation proved this occurrence not as rare as it seemed.

A similar incident had been reported at Bellevue Hospital, New York City, where a

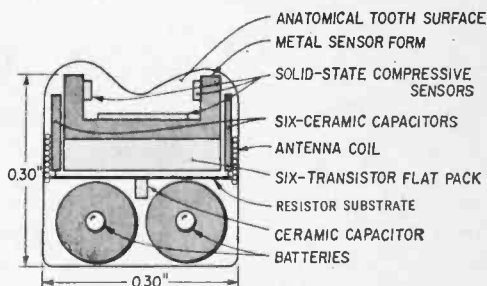famed neurophysiologist saved a similar "listener" from the jacket department when he said, "study his teeth." This specialist describes the phenomenon as one that can happen when carborundum dust seeps into a new filling, or into the well of a tooth when it is being filled, the carborundum acting as



This artist's representation of the tooth is more than 3-times actual tooth size.

BROADCASTING TOOTH

a rectifier and turning a perfectly innocent, well-meaning tooth into a radio receiver.

All of which seemed quite harmless until recently. For no one would quite think of asking dentists to deliberately add carborundum to dental fillings, and certainly no one knew how to pack a radio receiver into a tooth. But now we're not sure.


For a dentist-engineer team at the School of Dentistry, University of Michigan, have developed a tooth, packed with miniaturized

electronic components so it can broadcast.

A young volunteer sat down in a dental chair in the dentistry department at the University in Ann Arbor. When Dr. Major Ash looked at his mouth he found an upper first molar missing. In its place Ash inserted a tooth that looks like any other molar-bridge, except this one, packaged in plastic, is wired for transmitting and costs \$15,000.

As the volunteer chewed food, smoked, and even rested, the tooth telemetered how it felt about the other teeth around it so Ash and his associate, Scott, could register data for the use of all dentists on a Honeywell Visacorder located nearby.

For years it has been known nature pro-

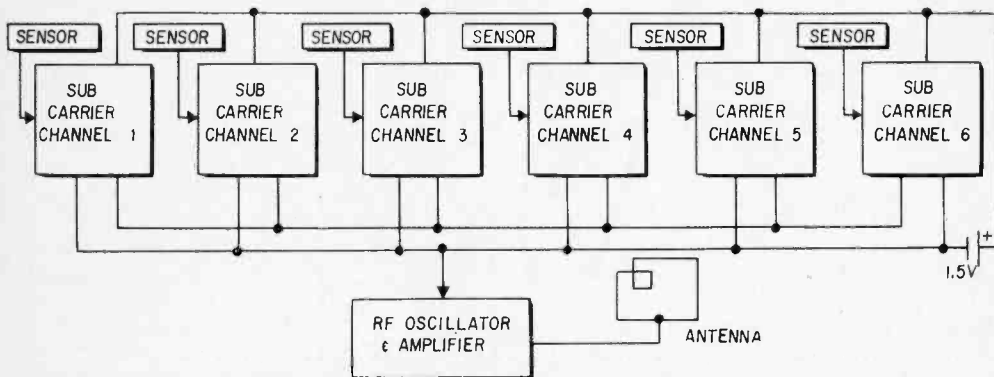

It may be hard to believe but all six of the channels, with their sensors, transistors and rechargeable cells (batteries) can be put into less than one hundredth of a cubic inch.



To study the broadcasting tooth you have to have a steady hand, a gentle touch and a stereo microscope as well as patience.

vides a pretty complex protective system for its teeth, but the strain of chewing and flaws in bite can wear a good tooth down. Ill-fitting bridgework can damage adjacent teeth, while if a dentist truly understood the stresses a tooth goes through in a day, he could design better bridgework, prevent gum complications, even formation of tartar and cavities.

The idea of attempting to solve this problem through electrical methods is not new, goes back to such men as B. Jankelson and G. Hoffman, followed later by A. A. Brewer and D. C. Hudson who overcame early disadvantages of studying the tooth's daily battles through wires extending from the mouth. This they did by trying to insert a radio transmitter into an upper denture to telemeter frequency of tooth contacts.

However, it has taken Scott and Ash, spending two years of study to fashion the ultimate electronic tooth. And before they achieved their difficult goal, they discarded

(Continued on page 116)

SILENCE IS GOLDEN

Just build Blab-Off and see for yourself how much fun it is to blast those commercials into stony silence.


■ Have you *had it*? Are you sick of Katy Winters telling you how to stop perspiration? Are you waiting for the Knight-in-Armor to run someone through with that lance instead of turning lovely grease-covered overalls sparkling white? Do you wish that kook running around with a sheet and screaming, "It's sparkling white," would step off that 300-foot cliff in the background? Do you have an insane urge to belt that blond in the mouth next time she says "Take it off"—and *it* turns out to be some jerk stripping whipped cream off his face? (What, you really believed shaving cream looked like that?)

In short, are you sick of TV commercials? If you are, why not dispatch them to the great beyond with the Blab-Off?

There you sit, the Blab-Off connected to your TV receiver and your ray gun (it's really a flashlight) on the table next to you. The man from U.N.C.L.E. has just about convinced the girl from the Society of International Noodnicks that she's on the wrong team when there's a quick cut to some idiot, dressed in a maid's uniform, flying through the air and waving a container of gook—which not only cleans something but makes your hands kissing soft in three minutes. Of course, while you can always look down at the latest issue of Playboy (concealed inside a copy of R-TV E) the audio portion of this throwback to the Inquisition is enough to make one gag on a really cold beer (and one should enjoy a really cold beer).

But this time, instead of muttering that the sponsor thinks everyone has the mind of a 2-year-old, you grab the *ray gun*, fire a

by Herbert Friedman

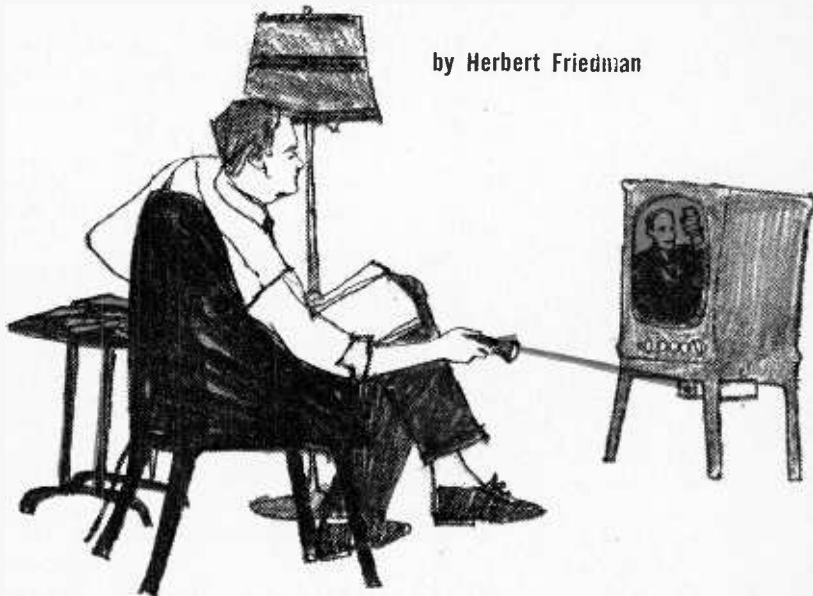

SILENCE IS GOLDEN


a 2-year-old, you grab the *ray gun*, fire a short burst of instant death ray at the TV and peace descends—no more sound. When the insult to your intelligence is over, you fire a quick burst of rejuvenating light at the TV and the sound comes back.

The Inside Story. By now you no doubt have guessed that the Blab-Off is a light-controlled relay that mutes the TV receiver's sound and turns it back on whenever you give the command. Fig. 1 shows how it's done.

to an ordinary two-cell flashlight located 30 feet from CdS1. In fact, it's not even necessary to "hit" CdS1 with the full light beam. Just sweep the flashlight beam across the area where CdS1 is located. As soon as any part of the beam, even the edges, passes over CdS1—even for an instant—the Blab-Off will be activated.

The Blab-Off's sensitivity actually creates a minor problem. It is so sensitive that it can only work in a room where the room lights are properly dimmed for TV viewing. If you enjoy watching TV while taking a sun-bath from light streaming in the window, forget the Blab-Off. The excess light will "jam" the photo-resistor.

If you plan to use the Blab-Off under

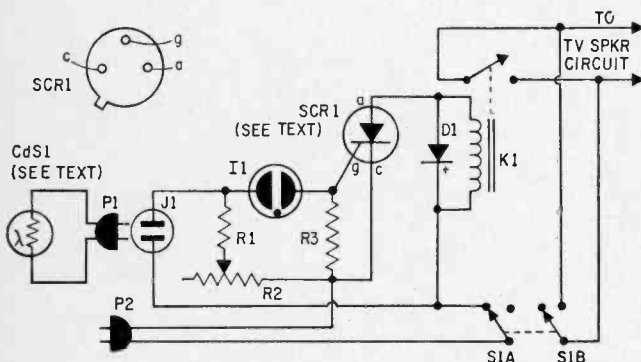

Schematic is simple. Largest component is relay with J1 about next in size. J1 and P1 can be eliminated if you can mount CdS1 in same box as other components.

Relay K1 is connected in series with SCR1, a silicon controlled rectifier. Note that photo-resistor (photo conductive cell) CdS1—which is connected into the circuit via P1 and J1—is part of a series-connected voltage divider consisting of CdS1, R1 and R2. Light falling on CdS1 lowers its resistance, thereby causing a greater voltage to appear across R1-R2. When the voltage reaches the breakdown (ionization) potential of neon lamp I1, I1 conducts, applying a voltage to the SCR gate. The SCR conducts and relay K1 is activated, thereby opening the TV speaker circuit.

How it stays open and closed. The relay is a special type known as an *impulse* or *latching relay*. Assuming K1's contacts are *closed*, a single pulse of current through the coil causes the contacts to *open*, and the contacts stay *open* even after the current pulse has passed. A second pulse will cause the relay contacts to *close* and stay *closed*. Once the contacts are either opened or closed they stay in that condition even after current is removed from the relay coil.


The Blab-Off is so sensitive it will respond

high-ambient light conditions, it will be necessary to experiment with photo-resistors having a higher resistance rating at 2 foot-candles than the model specified in the parts list. Since the Clairex type CL505 is rated at 9000 ohms at 2 foot-candles, a good experimenting model for high light levels might be the Clairex type CL704 or CL705 or some similar photo-resistor.


While many different photo-resistors will work in the Blab-Off, the CL505 was selected as its relatively large diameter (1/2 inch). This makes it sensitive to the fringes of the light beam and means that the light beam doesn't have to fall directly on the target area.

Construction. The Blab-Off consists of three units: the flashlight, the photo-resistor and its holder, and the control box.

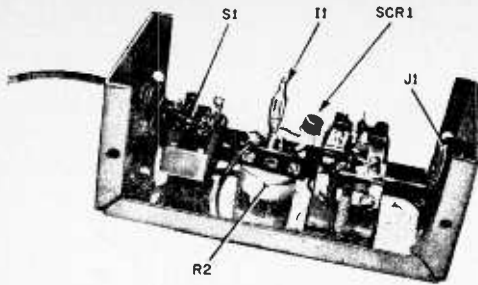The control is assembled in an aluminum chassis box or cabinet measuring 2 1/8 x 3 x 5 1/4 inches. Since the Blab-Off is operated directly from the line, take extra care that no part of the circuit is connected to or touches the cabinet. Do *not* use the cabinet as a common ground connection.



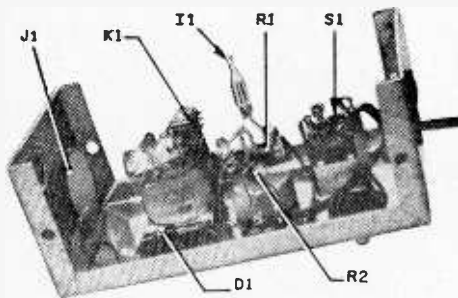Internal views of the Blab-Off show locations of most components. Once you have the major ones positioned the placement of the others will be quite obvious—even if you don't keep leads as short as practical you won't have any problems with placement.



Socket J1 is a standard chassis-mounting AC receptacle, though any socket with two *insulated* terminals may be substituted. I1 is a special neon lamp made for "dark" applications—inside an enclosure, for example—so no substitution should be made. While the Blab-Off will work with a "standard" neon such as the NE2 it will tend to be intermittent in operation.

Note extra carefully D1's connections across K1. D1, which is any standard silicon diode rated at 200 piv or higher, *must* be connected so its cathode (the end marked with a "+" or a band) "faces" power switch S1. If the diode's polarity is reversed the relay will not operate when the SCR is tripped. Diode D1 should not be eliminated as it sharply reduces relay chatter (the noise could drive you nuts, otherwise).

Also take extra note of S1's connections. When it is in the normal (N) or *power off* position, the second set of contacts short K1's contacts so the speaker is connected at all times. When S1 is set to the control (C) or *power on* position, the speaker is *on* or *off*.

In the unit shown, the terminal strip was

PARTS LIST

- CdS1—Photoconductive cell (Clairex CL505 or equiv.—see text)
- D1—750 ma, 200 piv (piv) or higher rating silicon rectifier
- I1—Neon lamp (type NE-23 or equiv.)
- J1—Jack, 2 wire insulated (see text)
- K1—S.p.s.t. latching relay (Guardian IR-610L-A115 or equiv.)
- P1—Plug to match J1 (see text)
- P2—Plug for AC line cord
- R1—22,000-ohm, 1/2-watt, resistor
- R2—1,000,000-ohm potentiometer (see text)
- R3—100-ohm, 1/2-watt, resistor
- R4—47-ohm, 1/2-watt, resistor
- S1—D.p.d.t. slide or toggle switch
- SCR1—Silicon controlled rectifier (G.E. C6B or equiv.)
- 1—Chassis box, 2 1/8 by 3 by 5 1/4 inches (Premier AMC-1006 or PMC-1006 or equiv.)
- Misc.—terminal strip, grommets, wire, solder, mounting screws, etc.

Estimated cost: \$12.00

Estimated construction: 3 hours

soldered directly to the top of R2 to conserve space. Since the leads around R2 and the terminal strip are somewhat close don't be afraid to use plastic tubing (spaghetti) freely on all bare leads.

For normal low-ambient light levels R1 is 22,000 ohms and sensitivity control R2 is 1 megohm. If you do any experimenting for high light levels R2 may be changed but R1 should never be less than 22,000 ohms.

Assembling the photo-resistor pickup.

The specified CdS1 mounts in a three-inch section of 1/2-inch copper tubing of the type used by plumbers for water pipes. (Other photo-resistors might fit into 3/8-inch tubing.) Attach a length of standard "zip" cord (or speaker wire) to CdS1's terminals and thoroughly insulate the leads, right up to the glass enclosure. Position the photo-resistor

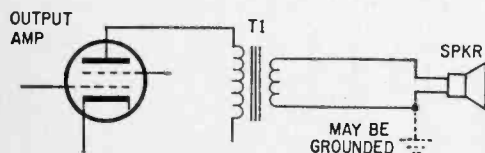


Photo-resistor is shown here somewhat larger than actual size. The connecting wires have been attached and bare leads covered to prevent shorts from occurring.

SILENCE IS GOLDEN


about half-way into the tubing and apply a liberal quantity of silicon rubber adhesive (such as RTV or Silastic) to the wire end of the tubing. When the adhesive hardens both the connecting "zip" cord and CdS1 will be held firmly in place.

Connecting the Blab-Off. The schematic diagram in Fig. 2A shows speaker output circuit of a typical TV set. Open one speaker



Factory-wired speaker connections (above) can be easily modified (below) to make connections to Blab-Off.

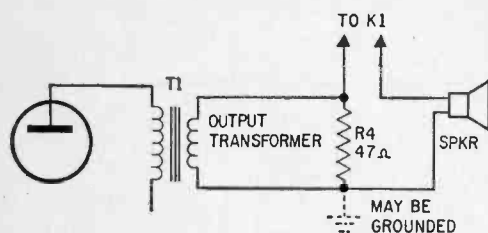R4 keeps some load on output transformer, even with the speaker disconnected, to prevent excessive plate current flow.



lead at the speaker terminal. (If one of the speaker leads is grounded open the ungrounded lead.) As shown in Fig. 2B, connect a 47-ohm, 1/2-watt resistor across the output transformer and bring out two leads from inside the cabinet—the leads to K1's contacts.


Mount the control box on the rear of the TV receiver and connect the speaker leads to K1's contacts. To avoid short circuits run the speaker leads through a rubber-grommets hole in the control cabinet.

The photo-resistor assembly can be mounted under the TV receiver; it is held in place with a single electrical pipe strap—a half-U clamp.

Adjustment. Set the room lights to the normal viewing illumination and temporarily remove the cover from the control cabinet. Turn S1 to *on*—the speaker may or may not disconnect—and adjust R1 until I1 is *not* illuminated. (If I1 stays on, SCR1 is



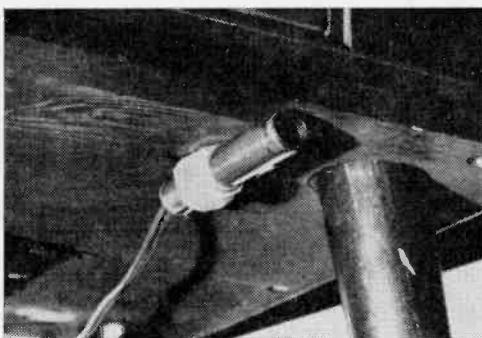
Room-temperature vulcanizing (RTV) silicone rubber (used for caulking sinks, tubs, etc.) seals leads and CdS1 into section of tubing (above). The completed light pickup (below) is shown mounted under TV cabinet.



continuously conducting and K1 might burn out.) If I1 cannot be extinguished with R1, the room illumination is too high; try painting the inside of the photo-resistor assembly black before experimenting with other photo-resistors. Set R1 to the highest value which will still cause K1 to trip when a flashlight is beamed at CdS1.

Since strong light will always trip K1, make certain the Blab-Off is always turned off with the TV receiver, or when the room lighting is raised.

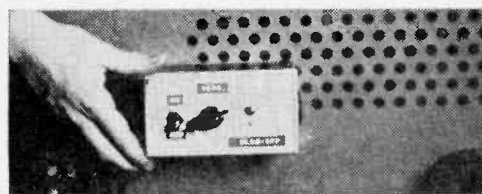Next time an aspirin commercial gives you a headache simply zap the Blab-Off with the flashlight—and bid that headache goodbye. ■



Mounted on the rear of the TV cabinet the controls for Blab-Off are easy to reach.

Making Light Work of Power Wiring

by Paul Hertzberg, K2DUX

AC power receptacles are just about the same no matter where you install them but hanging a light entails many varied techniques that are very simple—when you know how.



ADDING light fixtures is much more of a problem than adding an outlet. The styles of receptacles are quite limited by comparison—and generally they will be mounted in one of three types of outlet boxes. The most common box, used for wall outlets and switches, is the Gem box—the one that comes apart.

Round (octagonal) and square boxes in 3- and 4-inch sizes are used in different ways to hang lighting fixtures. Some are fitted with adjustable hangers (brackets).

Because of the weight of many ceiling fixtures the support must be more secure. While some light-weight lighting fixtures can be installed after the ceiling has been finished, most must be attached to brackets (or some cross member) that are fastened to the beams before the ceiling has been closed up.

Trying to refinish a ceiling to look like new after it has been broken open is quite a job—it's one for an expert!



While we can't tell you how to re-plaster a ceiling, we can show you some of the ceiling-fixture assembly methods.

So if you can work down from an unfinished attic or are finishing an attic or basement that still has an open ceiling, here are some tips on finishing sooner and ending up with a neat-looking job that you can be proud of when company comes. Now, before you roll up your sleeves to start work, turn the page



Making Light Work Of Power Wiring

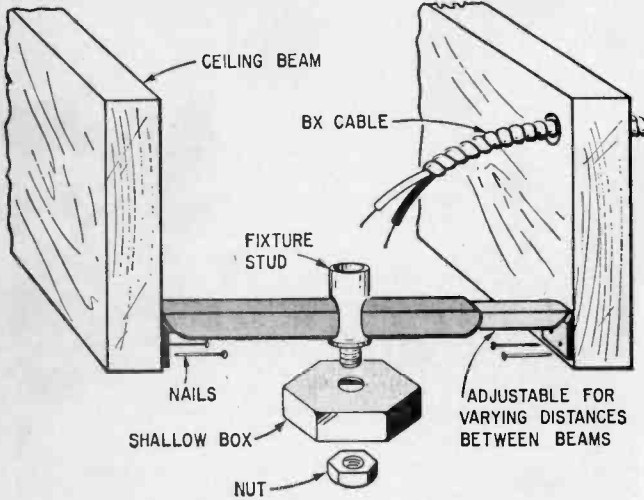
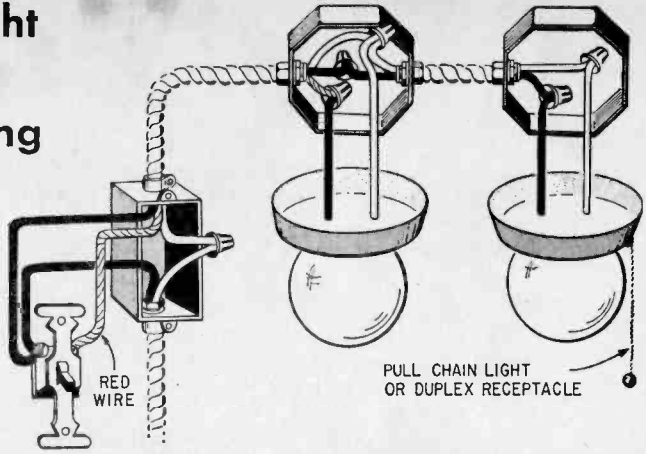
Two lights can be controlled independently (one with a pull chain or from a second switch mounted in wall box). You do need a 3-wire cable from the wall-switch box to the first ceiling box—two wires to the last box.




Nails are used to attach the hanger (bracket) between the beams. Just be careful that you don't split the edge of the beam while driving nails. Fixture stud can be positioned on hanger.


Wires may go through box or through stud and C-shaped fixture hickey. Bowl-shaped canopy covers up ceiling opening and wiring splices.

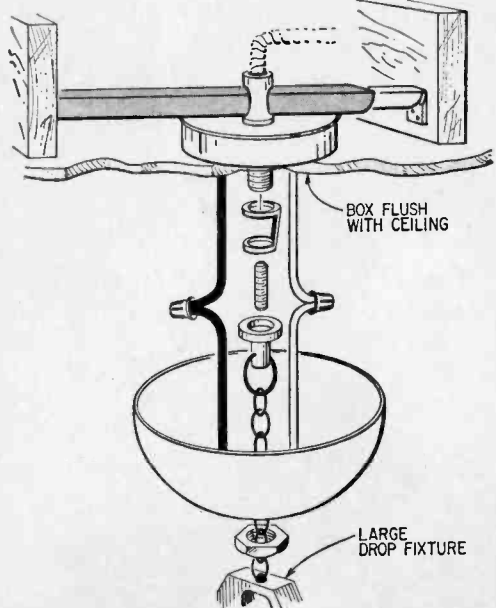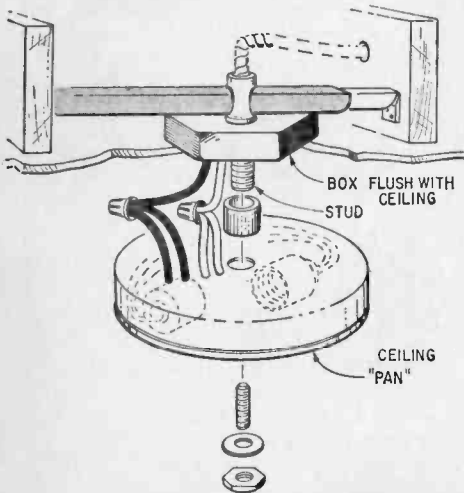Ceiling-pan fixture has two lamp sockets. Watch wiring for a flush fit to ceiling.




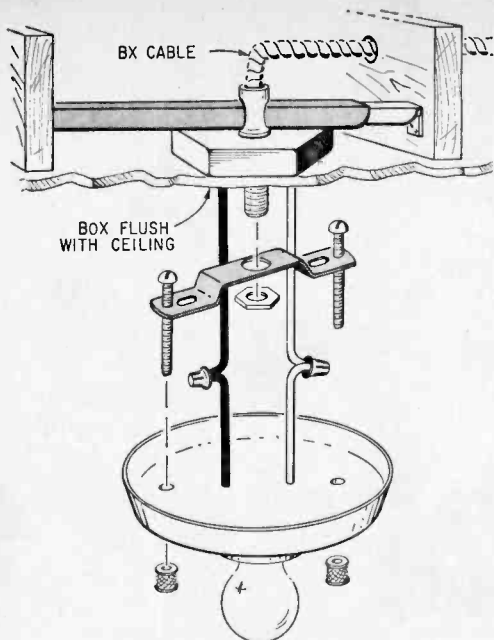

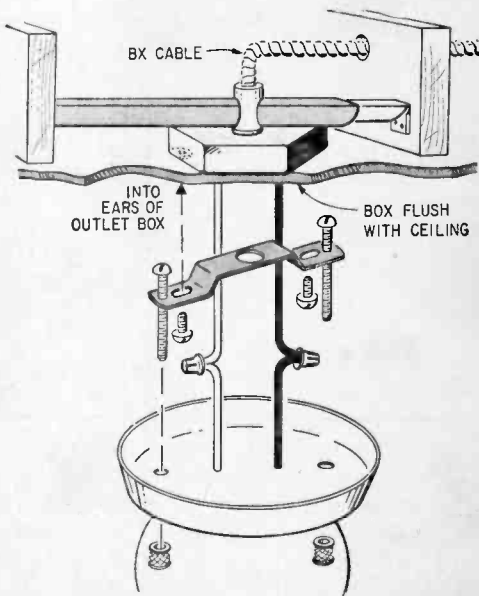Single-lamp fixture uses a fixture hanger bracket mounted on fixture stud in ceiling box. Machine screws in tapped holes bottom in fancy nuts and pull pan tight against ceiling to cover box.



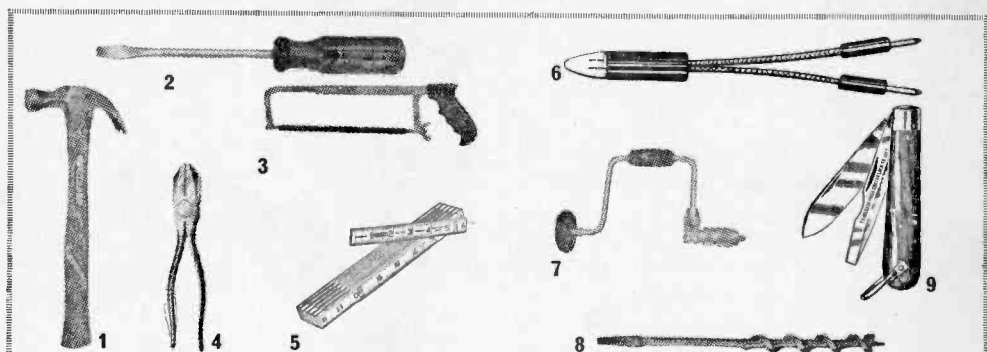Here, short machine screws attach fixture hanger to tapped holes in ears or tabs bent into edge of box. The fixture-stud extension is not needed in this type of fixture installation.



TOOLS FOR INSTALLING BX WIRING

- 1 **Claw Hammer**—for driving in staples, nails, wood supports, mounting boxes.
- 2 **Screwdriver**—3" type with insulated handle for tightening screws on connectors, outlets and switches.
- 3 **Hacksaw**—for cutting BX cable, metal supports.
- 4 **Linesman's Pliers**—for cutting wire, tightening nuts, stripping insulation.
- 5 **Folding Rule or Tape**—for measuring position of boxes, cable lengths.
- 6 **Neon Test Light**—for checking live wires, tracing circuits, testing outlets.
- 7 **Brace and Bit**—for boring holes through walls, studs, floors (a #12— $\frac{3}{4}$ -inch—bit is the right size for BX cable).
- 8 **Electric Drill**— $\frac{3}{4}$ -inch power wood bit and extension cord (if power is available from a finished area).
- 9 **Electrician's Knife**—for cutting insulation, scraping ends, wire.

COPPER WIRE CURRENT RATING

Wire Size (AWG)	No. 14	No. 12	No. 10	No. 8	No. 6
Maximum Current	15 Amps	20 Amps	30 Amps	40 Amps	55 Amps

build

a

THD

tester

A simple adapter you can use
with your AC VTVM or Hi-Z VOM.

by Herbert Friedman

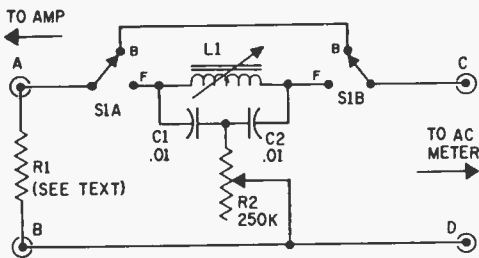


Fig. 1. This simple circuit is the heart of audio analyzers that are designed to measure the total harmonic distortion (THD) of amplifiers.

■ If you do any serious experimental work in audio, or if you've got a little audio service business going on the side, you probably know the importance of *THD* (total harmonic distortion) measurements. The *THD* of an amplifier is important because it is generally the design center for overall performance, to which the frequency response, power output, noise level, and sensitivity are referred.

Since all manufacturers specify performance, particularly power output, at a given *THD* reference level, the experimenter or service technician can easily check against the like-new performance specifications. For example, if an amplifier is rated at 20 watts for 0.1% *THD*, a repair that restores this rating can generally be presumed to have restored all other characteristics.

While it is true that amplifier distortion is also dependent on frequency as well as power output level, it has become the general practice in all but the most expensive "high performance" amplifiers to use the *THD* rating at 1 kHz (1000 cps) as the reference. And it can be generally assumed that an amplifier exceeding the distortion specifications at 1 kHz will also display evidence of a degradation in frequency response and signal-to-noise ratio. Even when a manufacturer specifies the more esoteric *intermodulation distortion*, he also gives the 1 kHz *THD* since it is a more universal measurement when dealing with reproduction of sound through a loudspeaker.

Much of a distortion meter's cost goes into making it tunable over the 20 to 20,000 Hz


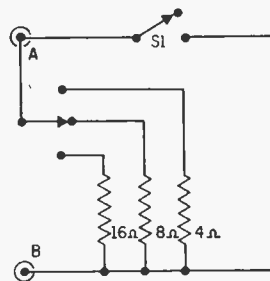


Fig. 2. R1 can be replaced by the above circuit to make amplifier-output loading easier. When testing use heavy-current rotary switch.

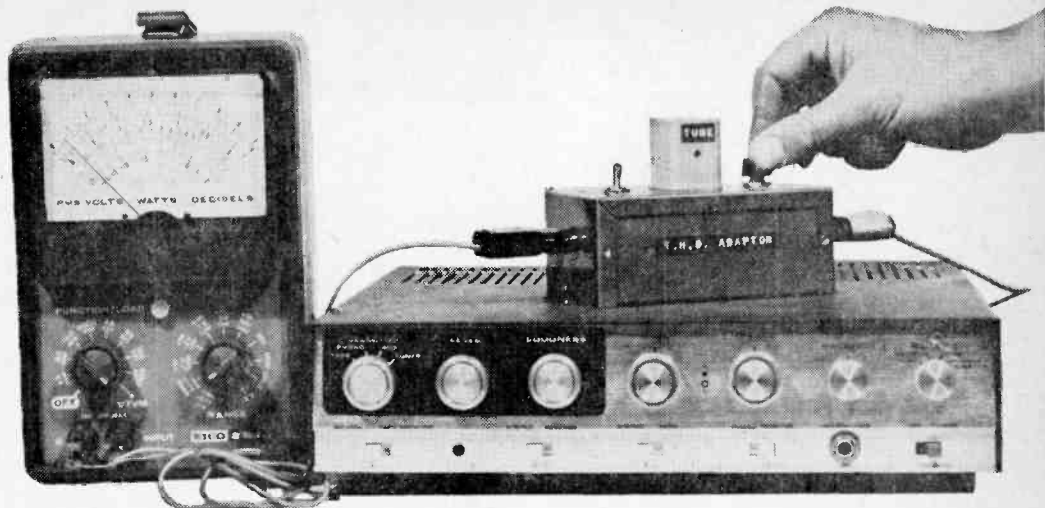

The setup is simple—connect the THD Adaptor to the output terminals of the amplifier; connect the audio (AC) VTVM to the C-D terminals of the THD Adaptor and read THD.

PARTS LIST

- C1, C2—.01 mf., 100 WVDC disc capacitor
 L1—Variable inductor, UTC type VC-15 (available from Allied Radio as their part #62Z914; \$7.50)
 R1—Amplifier load termination (see text)
 R2—250,000-ohm, linear-taper potentiometer
 S1—S.p.d.t. toggle switch
 4—Insulated binding posts
 1—Chassis box, aluminum, 5¼ x 3 x 2½" (Bud 3006A or equiv.)
 Misc.—Wire, solder, hardware, etc.
- Estimated construction cost: \$7.50 plus junk box parts. About \$10.75 with new parts.
 Construction time: 2 hours or less

(cps) range. Another high-cost circuit is the built-in AC-VTVM used to measure the distortion level. But since you get the key to overall performance by knowing the 1-kHz distortion value, you can dispense with the tunable circuits. Substitute your own AC-VTVM for the built-in job and you come up with the *THD Adaptor*, a distortion meter you can throw together in an hour for only \$7.50 plus some parts from your junk box.

How It Works. The THD Adaptor schematic diagram is shown in Fig. 1. Note that it is simply a parallel-T network for filtering 1 kHz and that it includes R1, a terminating resistor for the amplifier. If a

1-kHz sine-waveform signal is passed through a distortion-free amplifier, only 1 kHz appears at the output. If you connect a VTVM to terminals C and D, the meter would indicate zero as the filter consisting of L1, C1, C2 and R2 would "block" the 1-kHz output before it got to the meter. If the amplifier caused distortion, in addition to the 1-kHz signal there would appear at the output many harmonics of the 1-kHz input—2 kHz, 3 kHz, 4 kHz, etc. (The greater the distortion the greater the harmonic output.) Since the filter would "block" the 1-kHz signal component, only the distortion components would appear at terminals C and D.

Since $\%THD = \frac{V_{rms} \text{ Harmonic}}{V_{rms} \text{ Total Signal Voltage}} \times 100$, the percent harmonic distortion of an amplifier equals the voltage indicated across C and D divided by the voltage across R1 times 100. (Bypass switch S1 allows the meter connected to C and D to indicate the total amplifier output voltage.)

Using the THD Adaptor. Let's look at a practical application. Assume that the 1-kHz test input signal causes the meter connected to C and D to indicate 10 volts when S1 is in the *bypass* or *B* position. With S1 in the *filter* or *F* position the meter indicates 1 volt. The amplifier's percent *THD* then equals $1/10 \times 100$ or 10%.

While we have chosen convenient numbers (1 and 10) for illustration, the actual

THD tester


voltage readings could be anything. For example, an amplifier might deliver a total output voltage of 6 volts with a filtered voltage of 0.45. The %THD in this instance would be $0.45/6 \times 100$ or 7.5% THD.

While we have referred to using an AC-VTM, an ordinary VOM could be used as long as its impedance is at least 10 times the value of the amplifier's load impedance. An AC-VTVM would probably only be required when measuring voltages smaller than 0.5 Vrms (audio or AC-VTVMs go down to 1 millivolt full scale, while VOM's are generally limited to a bottom range of 1 or 3 volts.)


Building the THD Adaptor. The unit shown is built in an aluminum cabinet measuring approximately $2\frac{1}{8} \times 3 \times 5\frac{1}{4}$ inches. The layout isn't critical and you can use any component arrangement you desire. Since some transistor amplifiers don't have a common output (grounded) connection, to avoid the possibility of short circuits with the resultant destruction of the output transistors, the THD Adaptor's case is "floating"—all input and output binding posts are insulated from the cabinet.

Resistor R1, the amplifier load, should have a power rating equal to at least twice the maximum power at which the amplifier will be tested. For example, if you plan to test at 10 watts output, R1 should be rated for 20 watts. Either a single resistor or a parallel wired group (as shown) can be used.

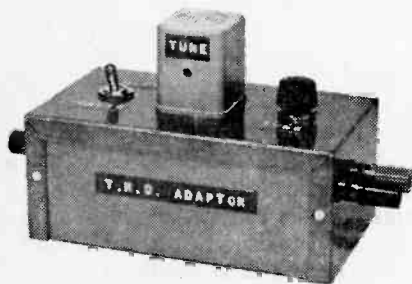If you want to make the adaptor universal, substitute the switch-selected load circuit



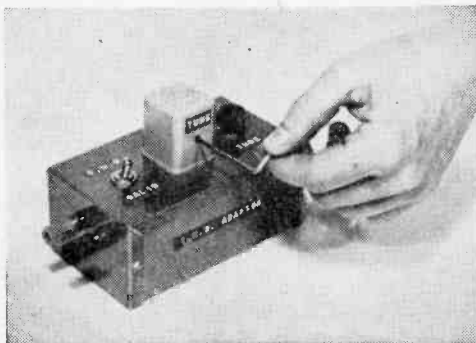When laying out chassis box be sure to space 5-way binding posts $\frac{3}{4}$ inch to fit double-banana plugs used to connect most professionally-styled laboratory instruments.



Adjustable inductor L1 is tuned for minimum output at 1 kHz—you can also tune generator to null frequency for making quick THD test.


shown in Fig. 2. While 4-, 8-, and 16-ohm terminations are more or less standard, you can add any desired load value to the selector switch.

Tuning Up. L1 is tuned via a small Allen screw in the side of its case. Connect terminals A and B to the amplifier and C and D to the AC voltmeter. Feed a 1-kHz signal through the amplifier—from a signal generator, pre-recorded tape, or phono record—and adjust L1 and R2 for minimum meter reading. L1 and R2's adjustment interact to a degree and it will be necessary to go back and forth several times. Since the tuning is extremely critical you probably will have to adjust the filter each time the adaptor is used.

Don't worry about getting an exact 1-kHz signal source as the filter tunes the range of 800 to 1200 Hz. You can tune either the inductor (L1) or the generator—whichever is easier. It won't really matter a lot if you use 990 Hz or 1010 Hz—this is 1%. And, under normal temperatures, the inductor shouldn't change much at all. So just tune for the null.

Making the measurement. Feed the test signal into the amplifier and adjust the amplifier for the desired power output. Set S1 to the B position and note the meter reading. Then set S1 to the F position and adjust L1 and R2 for minimum meter reading (a null). The %THD is equal to the B -reading/ F -reading times 100. ■

Talking Shoe Box

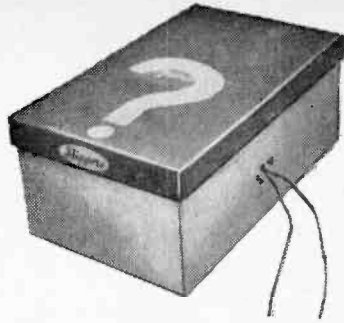

Dirt-cheap and ultra-simple, this weirdo does everything speakers do!

■ Here's a project that is exciting to build and informative; exciting because you construct it and informative because you see in operation a device that is basic to most all electronic reproducing equipment. *What is it?* It's a permanent-magnet (PM) speaker—one that operates on the same principle as the speaker in your transistor radio, or like those in a hi-fi set. We call this project the "Talking Shoe Box" speaker.


A cardboard shoe box serves as both the frame and cone. The cover of the box becomes the cone of the speaker. It vibrates in accordance with the currents that flow through a coil (called a voice coil) mounted on the inside of the cover. The vibrations of the cover compress and rarefy the surround-

ing air—putting sound waves in motion in exactly the same manner as a speaker does.

Making One. Perhaps the most important part of any PM speaker is the magnet itself. The magnet used was salvaged from a smaller speaker that had been discarded. Most electronics repair shops have one or two defective speakers around. Ask for a few defective units if you don't have any of your own. The magnet is removed from the speaker frame by giving it several light taps with a small hammer. Don't hit it too hard—each tap knocks out some of the magnetism.

The coil form used here measures a little more than 1-inch in diameter, but the size you use will depend on the magnet you have.

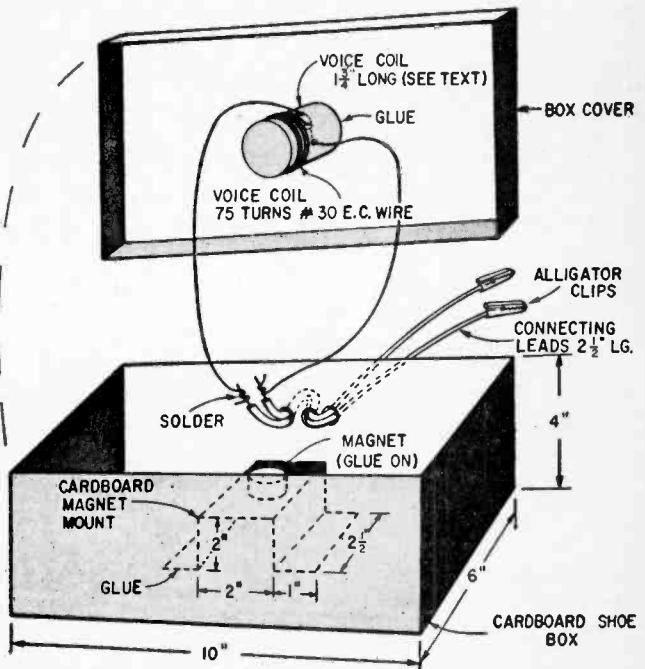Shoe box acts as frame, its cover as cone of this novel speaker. Magnet can be salvaged from a discarded PM speaker, though more powerful assemblies can often be obtained from hobby supply houses.




By Robert E. Kelland

Talking Shoe Box


The coil form must fit over the magnet with a comfortable clearance. The coil consists of about 75 turns of AWG-30 enamel-covered copper wire. The wire is scramble wound around one end of the form. Cut two slots (or make small holes) for the beginning and end of the wire. A touch of all-purpose cement will keep the coil from unwinding. The form is glued to the *exact center* of the underside of the box cover. Use diagonal lines from corner to corner to find the center point.

The magnet mount is made from an 8" x 2½" piece of stiff cardboard but there is no reason you can't use a block of wood cut to size. After forming, the magnet mount is cemented to the inside bottom of the box—the magnet is cemented to the mount. It is important that you center the magnet exactly, otherwise the coil form will rub against the magnet and cause poor operation. Use extreme care. Add a few corner braces so the cardboard magnet mount will not sway.

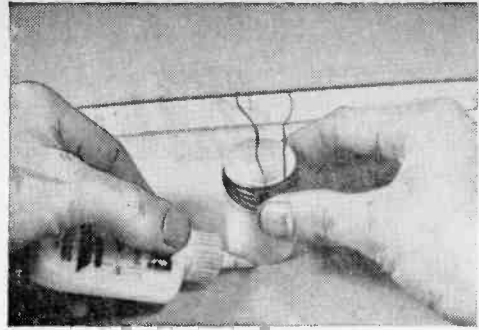Finish the "Talking Shoe-Box" speaker by scraping the enamel insulation off the free ends of the voice coil wire, and then solder two lengths of hookup wire to both ends. Weave the hookup wire through three small



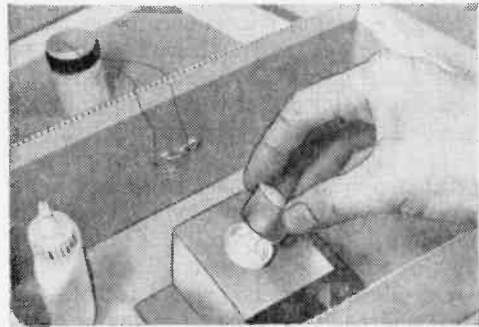Voice-coil form should be glued to the exact center of the inside of the shoe-box cover.



Cardboard mount supports carefully-positioned permanent magnet in bottom of box.

holes in the side of the box, and attach alligator clips to both ends.

Connection. To use the "Talking Shoe Box" speaker you must have access to the speaker terminals in a radio, TV or phonograph. A TV set is preferable, because the connections to the set's speaker are generally of the push-on type and are easily removed. Disconnect the speaker from the set before connecting up your home-made one.


To protect yourself from a possibly dangerous electrical shock, pull the line cord plug from the wall outlet before making any
(Continued on page 124)

PARTS LIST

- 1—Small permanent magnet (see text)
- 1—Cardboard tube 1 to 1¼-inch dia. x 1¼ inch long
- 1—Slippers or shoe box—10 x 6 x 4 inches
- 20'—AWG #30 enamel-covered wire
- 2—Alligator clips
- Misc.—Scrap cardboard, hookup wire, all-purpose cement, solder, etc.

Estimated cost: 50 cents
Construction time: 1 hour

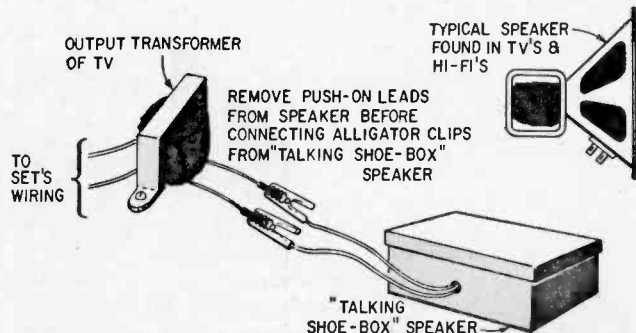TV sound will be heard over shoe-box speaker when unit is connected as shown. When interchanging speakers, be certain TV set is turned off unless one speaker or the other is actually in the circuit.



SPACE PUPPETS with Electronic Strings

Taking a spin in space someday may prove no more formidable than jetting cross-continent or around the world. But until that day arrives, most of us will happily settle for the next best thing—man-made monsters that do our ether-journing for us.

By K. C. Kirkbride



■ Ever think you would one day see space as a satellite sees it? Travel round the earth and peer down at land, seas and clouds as an astronaut does? Turn your head and view the moon, Mars and stars? Stand on a space platform, report weather conditions, survey space dangers, even repair craft on their way to far planets?

You may do just that and not too far in the future. And you won't have to spend even one day in *astronaut* or *Superman* training, for you may travel through space as you sit in your living room, watching your own non-orbiting television screen.

For, according to William E. Bradley of the Institute of Defense Analysis, in Arling-


ton, Virginia, we may one day soon put tele-puppets in space. These would be mechanical "men" strung to earth men by radio-wave strings, puppets that could survey weather, relay information, perform tasks too risky for human man to venture.

And most dramatic of all, the future tele-puppet will see space through television-camera eyes, photograph the "bright lights" and "opening nights" of the space show, relay instant live scenes to earth.

On Earth. A human operator on earth would sit before a television tube attached to his helmeted head. On his hands he would wear electrically-wired gloves. The scenes on the screen before him would be the same pic-

SPACE PUPPETS

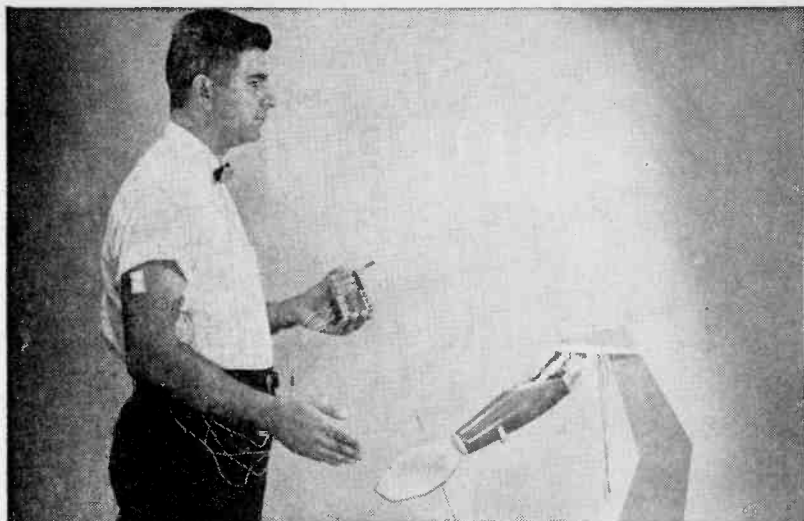Remote electrical signals from living human muscles control this artificial arm developed by Philco. Here, arm simulates handshake.



tured on a distant screen, in a space satellite.

And when he tilts his head up, down, right, left, the distant space camera would also tilt, photograph the scene before it much as a movie-camera "shoots" sequences on earth. But transmission from satellite would be so instantaneous the operator would feel he too was in space seeing the scenes the camera "sees" at the moment the camera sees them. And this "instant" feeling would be relayed to home viewers so they too would feel they were in space.

As the electrically-wired hands of the operator moved, the counterpart "hands" of the puppet twenty-five hundred miles in space would move, adjust or manipulate machinery or perform missions the earth man did at the same time.

No Lag. And all with hardly a time-lag, for radio waves, transmitted to the satellite from the operator's helmet would not only focus the camera operating in space but would pull the strings of puppet man, "telling" him what to do.

Sound fantastic? Not when you jigsaw developments in bio-chemistry, atomic energy, remote control radio and closed circuit television. For a telepuppet would draw his intricate know-how from research done in a variety of areas, research to aid war-time amputees, nuclear reactor study, even the search to improve visibility of aircraft.

First. When World War Two ended, we had more amputees than at any other time in the nation's history. Something had to be done to make life livable for tragically-maimed persons left without one arm, two

arms, sometimes no legs. The old peg leg belonged in the pirate movie, and it was an absolute "must" we find sophisticated appliances, and find them fast.




Seeking to develop new artificial limbs Philco Corporation engineers studied muscle signals as transmitted from the human brain, along the arm, to the hand, the signals that make fingers move, with the thought they might catch these signals before they reached the finger, intercept them, and power mechanical arms and hands.

Signals are picked up on the skin's surface above motor points of the muscle by silver electrodes which are connected to a micro-miniature control circuit package the size of a king-size cigarette pack.

Weak Signals. This control box amplifies the weak bio signals and treats them electronically by signal processing, permitting the circuitry to choose between signal patterns associated with motions desired and the signals identified with activity not wanted. This discrimination guides the arm, prompts it to move as the patient wants it to move.

To work out the discriminatory process built into the pack, Philco built a myocoder to preprocess and digitize signals from muscular electricity for computer analysis. The computer then classified and separated patterns and identified signals with specific activity.

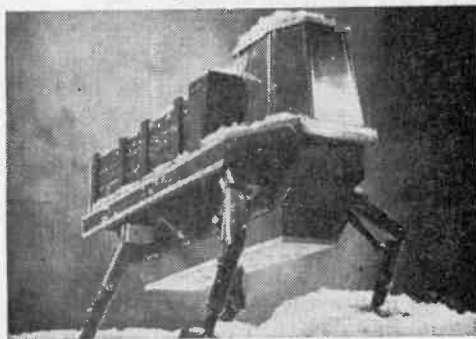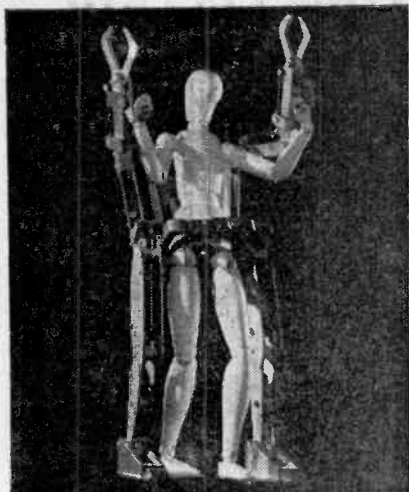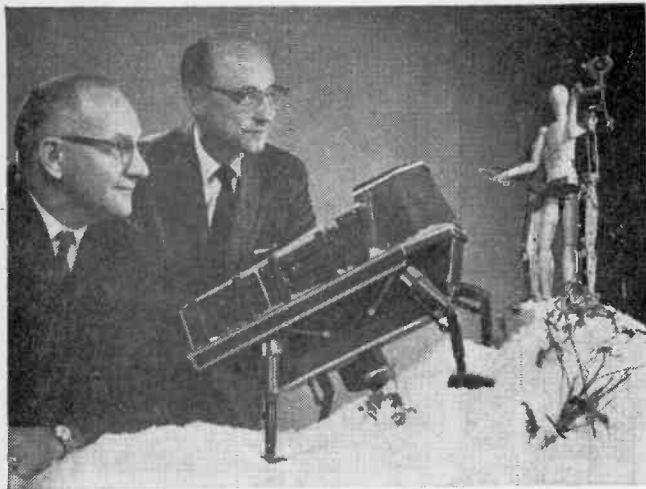Walter Wasserman, manager of Philco's Bio-Cybernetics Laboratory at Willow Grove, Pennsylvania, says, "Many control signals can be generated simultaneously by simple conscious thought and reflection." It



A "mechanical muscles" machine and a four-legged "walking truck" (shown here in prototype form) are among the possible space puppets under study at the General Electric Research and Development Center. The mechanical muscles machine (above) will enable the average man to lift a 1500-lb load without exerting more than a small fraction of this force; the walking truck (left), being built for the U.S. Army, will carry cargo over terrain that is clearly "off limits" to humans and other living things.

takes this analysis and built-in guidance to pinpoint the motion needed out of the complex signal-processing of the human nervous system.

After analyzing this signal system, designing built-in discrimination into a control package, the Philco engineers designed an artificial arm that could bend at the elbow, and turn its hand, all by remote electrical signals from living, moving muscles.

When the arm was first demonstrated, an engineer wearing silver electrodes on his arm muscles stood on one side of a room, moved his elbow and turned his head. On the far side of the room, a model of the artificial arm mimic'd exactly the actions of the live engineer.

Next Step. To put our future telepuppet together we will need add these bio-electronic advances to master-slave techniques developed in the atomic energy field. Nuclear energy presented the problem of a hostile environment man could only control by developing machine extensions of his own faculties so that machines rather than men could

pick up and handle dangerous materials.


Master-slave hands built to reach inside reactors, combined with bio-electronic artificial arm technology, soon fathered a whole series of new machines. Man-machine manipulators ably mimic a man with such ease the man operating the machine can ignore his imitating machine, and concentrate on the task at hand.

Handy Fellow. One of the first, one named Handyman, built by General Electric, consisted mainly of a pair of mechanical arms and hands, fashioned almost to human form, and connected electrically to a harness worn by the operator.

While the mechanical apparatus mimic'd its human operator, it fed back information on force and position so the operator could *feel* what the machine felt. In fact, this machine was so coupled to the operator's human sensory and motor system by feedback integration that electric signals caused the machine arm and hand to carry out precisely the motions of its human operator.

Walking Now. Next came a number of

SPACE PUPPETS

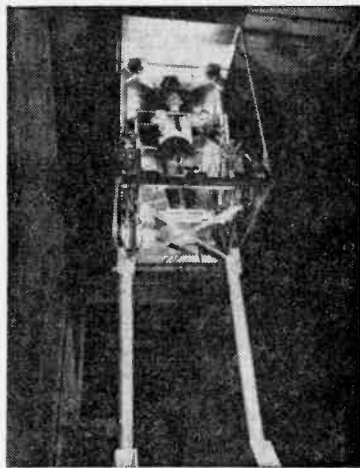

Mechanical giant towering some 18 ft. high is still another device General Electric engineers hope to perfect. Preliminary model places a human operator inside, but machine could be a pure robot.

man-machine manipulators including a "walking" machine, the "Pedipulator," controlled by human brain and nervous system with the same feedback precision of Handyman: a "walking truck" and Hardiman, a set of "mechanical muscles" that, attached to a human operator, could shame Tarzan himself when it came to weight-lifting.

While these amazing machines have so far been tested only in earth environment, advanced engineers feel they will strut their stuff every bit as efficiently in space. For bio-muscular signals have already proved remote response to radio waves. Witness the simplified test of the artificial arm on the far side of the room responding to its human counterpart.

Come See Now. But to build a true tele-puppet the engineers realized they would have to add sight to make their puppet truly human. For that, they drew again on Philco research, but this time seeking out engineers who had been trying to extend the visibility of certain types of aircraft.

How could they provide a pilot with synthetic visual displacement? That had been their first problem. They thought of one way, a remote television camera could do it, if they could find a camera small enough.

With no small commercial cameras with the proper resolution available at the time, they built their own. A very small camera, one with a grainless screen and a small electronic gun, resulted in a tube six inches long with the high resolution required.

A New Cap. Next they put the tube on the operator's head, mounted it like a miner's lamp and folded up a binocular optical system so the operator could, when he put on the helmet carrying the tube, see the scene on the screen focused in front of him.

They then servo'd the man's head by Selsyn motors to a distant television camera. And by this means were able to direct the camera by merely turning the operator's head. When he looked up, down, left or right, he felt he was "on location" as he could see exactly the scenes the camera saw with a resolution of one thousand lines.

To adapt this to space, engineers would "string" the space puppet camera to its earth operator by radio waves, so the earth operator would "see" through the counterpart camera photographing in space. And William E. Bradley thinks this camera mated with the man-machine manipulators, guided by remote radio "strings," will give us our tele-puppets in space.

Such puppets will perform tasks man can't. Such puppets will be cheaper to feed than man, and will photograph "instant" space spectacles that today only astronauts and the satellites see. Then we will sit in our living rooms, see the greatest show in space, as only space itself can produce it.

And we may even look toward the day when we will direct maneuvers in space by the move of an arm or a hand from side to side and up and down, with the grace of a symphony conductor on earth. ■

RCA TYPE WR-52A

FM-Stereo

Signal Simulator



■ It wasn't too long ago that an experienced technician could align many FM receivers and tuners by "ear". And certainly, most FM receivers could be properly aligned with the least expensive of signal generators. But stereo transmission has completely eliminated the possibility of "shortcut" alignment.

Stereo FM receivers are highly critical devices, and there is no longer such a thing as performing a *good* alignment by ear. Just the slightest alignment error and there's no more stereo—it comes out mono—or if you do get stereo there's *very poor* channel separation.

Proper FM stereo receiver alignment requires specially designed precision test gear; in fact, it requires a signal generator capable of simulating a transmitted stereo signal. Just such an item is RCA's WR-52A Stereo FM Signal Simulator.


What It Is. The WR-52A is basically two signal generators in a single cabinet. Firstly, it is a basic FM sweep generator used for

alignment of the common, or *mono*, receiver circuits. The generator RF output frequency is 100 MHz (mc.); to allow for avoiding interference to the test signal caused by reception of a station near 100 MHz, the WR-52A's output frequency can be adjusted slightly above and below 100 MHz. A built-in sweep generator provides a sweep signal of up to 750 kHz (kc.) for alignment of the receiver's IF transformers and the discriminator. (A marker generator is not part of the WR-52A; the user can utilize any signal generator for this purpose.)

What It Has. The WR-52A's stereo test circuits are more than just another signal generator for in a sense they simulate an actual stereo transmission. Starting at the bottom there is an AF oscillator providing 400 Hz, 1000 Hz and 5 kHz modulation of the FM signal; the signals are also available as an AF output for signal tracing a receiver's audio circuits. If desired, an external AF signal generator can be used for the FM signal modulation.

Both a simulated FM-stereo RF signal is available, for checking through the entire receiver, and a composite signal which represents just the stereo modulation (used for testing only the receiver's multiplex circuits). The FM-stereo signals are available as "Stereo Left" and "Stereo Right."

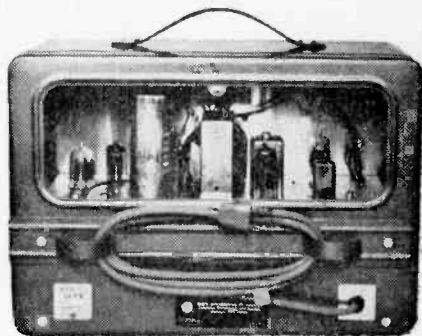
To insure proper alignment the stereo modulation can be adjusted to 100% (75 kHz deviation) by simply adjusting the modulation level until a built-in modulation



Cable bracket mounted on rear of generator provides convenient storage for unit's two output cables as well as the AC line cord.

(deviation) meter indicates 75 kHz deviation. Similarly, the 19 kHz pilot signal is set by adjusting its level to a reference mark on the meter scale representing 10% of the total stereo waveform.

Since stereo reception depends critically on the amplitude and phase of the 19 kHz pilot signal, and the 38 kHz signal which was the initial carrier frequency for the L-R multiplex modulation, the WR-52A is provided with a built-in check of its own 19 kHz pilot signal. (After all, if your generator is defective and you don't know about it the receiver alignment will be a lot less than perfect.) This internal test signal is controlled by the function switch, and proper adjustment of the 19 kHz pilot signal is a minor service procedure.

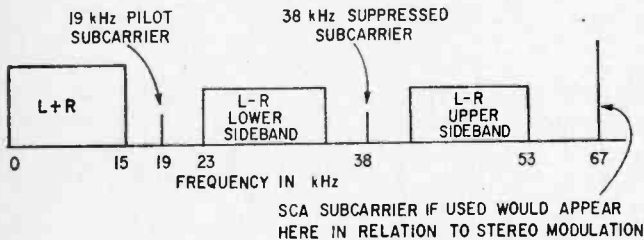

Complex nature of FM-stereo transmissions is quite evident from cross-section of FM-station's 75-kHz bandwidth. SCA modulation, where used, covers 60 to 74-kHz region.


SCA Traps. During both mono and stereo FM transmissions some stations also broadcast an SCA (subsidiary carrier assignment) signal which is multiplexed with the main carrier signal. The SCA sub-carrier's center frequency is 67 kHz with modulation extending from 60 kHz to 74 kHz. This SCA signal must be removed with traps as it would interfere with proper operation of the stereo

should be followed. The RCA illustrations in the manual provide the basic understanding of the alignment procedures everyone should know.

Similarly, the service section of the RCA manual is short but it is *complete* as to both checkout and adjustment of all generator circuits—it is not necessary to return the WR-52A to a service lab to have it checked or adjusted.

One of the most valuable features of the WR-52A is a trap door which simplifies servicing. Tubes, 19-kHz crystal, and adjustments all are readily accessible through a door at the rear of the cabinet.


While a stereo FM signal simulator is not needed in some experimenters' workshops, it is certainly a *must have* item for anyone doing service or alignment work on stereo FM receivers—one just can't do a proper alignment or checkout without it. In fact, it is a wise investment for experimenters breaking into the hi-fi service business. The RCA WR-52A Stereo FM Signal Simulator is priced at \$250.00. Prices may be slightly higher in the West. Additional information is available at your local Authorized RCA Test Equipment Distributor or by writing direct to RCA Electronic Components and Devices, Dept. 451, Harrison, N. J. 07029.

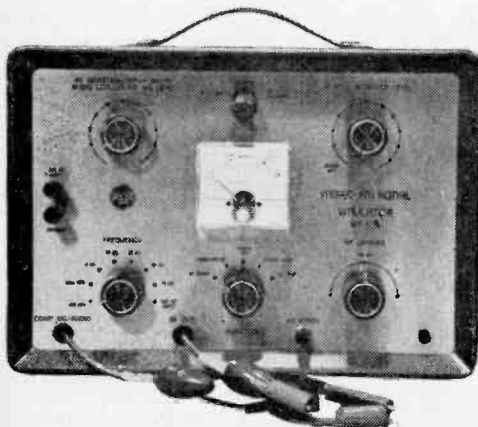

All controls are attractively grouped on front panel of the WR-52A. Meter in center of panel indicates modulation level.


RADIO-TV EXPERIMENTER LAB CHECK

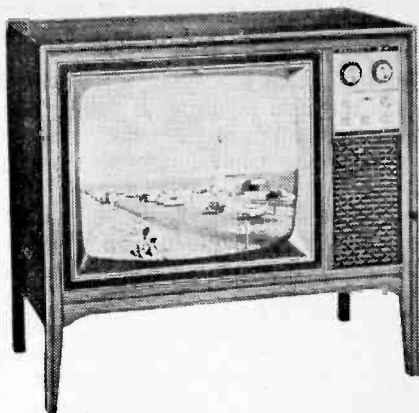HEATHKIT MODEL GR-25 25-in. Rectangular Color TV Receiver



What makes the real difference between a good and a poor *color television receiver*? No, a *good picture* is not the answer as most modern color sets deliver an acceptable color picture. The real difference between what the consumer considers a good or bad color set is the number of service calls required to keep it going and the charges for those calls. Over the life of a color set, repair and service call costs can exceed \$200. But, build the color set yourself and you will save several hundred dollars in repairs plus wind up with better color as you'll align the color reception to what *you*—not a serviceman—thinks is good to look at.

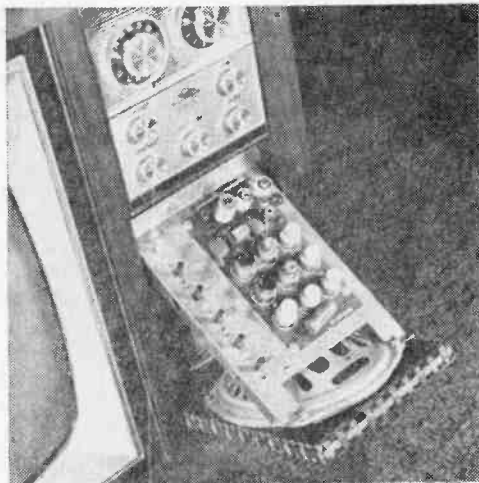No, we haven't flipped our tri-color CRT, or our shadow mask either. If you build Heathkit's GR-25 Color TV Set you can do your own servicing because, firstly, the very process of building the kit will give you the confidence to do your own color alignment,



Most-used controls appear at top right of set. Tilting special speaker panel downward exposes dynamic convergence controls.

and secondly, unlike other color receivers the Heath GR-25 has its own built-in *user oriented* service and alignment instructions. Absolutely no instruments are required to align the Heath; any test circuit you'll need is built into the GR-25.

For Example. Suppose a factory wired color receiver loses the color adjustments, or the set is moved to a new location and requires a degaussing. Obviously, this usually means a service call. But if you have a GR-25 you just lean on the speaker panel and the color dynamic convergence controls swing down in front of the set. What happens if you need a dot generator? Simple, you throw a switch on the back of the GR-25 and you get a dot pattern. Gun killers?—they're built in. As for degaussing, you do that with the supplied degausser when you build the kit so there's no big deal in doing it again. An automatic CRT degausser is built-in and works with the on-off switch.

It's Easy to Build. The actual kit construction is in a sense a *minor* assembly as the major components are supplied pre-wired—what's left for the user is the point to point wiring between the sub-assemblies and the non-critical circuitry. The combination VHF-UHF front-end is supplied pre-wired and pre-aligned. Similarly, the IF amplifiers are supplied pre-wired and pre-aligned on a printed circuit board. The user assembles the color, sound-sync, and convergence printed circuit boards. Wiring between the circuits is *via* a factory supplied wiring harness. Total construction time runs about 25 hours.

Color. When construction is completed you have an operating color receiver, just like your neighbors who have purchased theirs. The big difference is that *you* are able to adjust *your* receiver for optimum color reception. To assist you in color adjustment

the Heath service procedure is illustrated with 4-color pictures that show you exactly the results to be obtained.

Optimum color adjustment starts with the DC convergence adjustments (static alignment), and Heath's *service extras* start here. The static color gun adjustments snap into the plastic yoke and they are *knob* controlled; instead of pushing magnets around until the central dots on the screen turn white you simply *rotate* four knobs (two required for blue). The color-circuit board directly above the CRT has the dot generator on-off switch and the three gun-killers (no need to cut into the CRT wiring to kill any of the color guns for adjustment).

The dynamic convergence controls are mounted on a sub-panel behind the speaker. When the speaker is swung forward—it is hinged on the bottom—the dynamic convergence control panel swings into the position formerly occupied by the speaker. The panel contains 12 controls which adjust for convergence at the top, bottom and sides of the CRT in both the horizontal and vertical direction—central convergence is the original DC (static) adjustments. Once the dynamic convergence adjustments are made overall convergence is notably good.

To correct for pincushion distortion, when the top, bottom and sides of the picture squeeze together on the *H* and *V* central axis, there is a *user adjusted* pincushion control that is used in conjunction with the

dot generator. The controls are common to all rectangular CRT color TV receivers.


Final adjustment consists of adjusting the standard front panel *TINT* and *COLOR* controls, and the color burst phase transformer for normal flesh tones. A switch to a black and white picture indicates if the *color-killer control* needs adjustment—as evidenced by colored confetti in the picture.

And that's it. As you can see, not only are the GR-25's adjustments specifically oriented towards the non-technical constructor, but the builder, even without a technical background becomes familiar with color set adjustments and can routinely tackle color circuit re-alignment any time he is not satisfied with the color reception. At no time is it necessary for the builder to make a technical decision as far as color alignment is concerned; the built-in dot generator takes care of the technical requirements and the user makes simple mechanical adjustments whose effects can be seen directly on the CRT.

Service. Of course, it is possible for a breakdown to occur, but 99% of possible breakdowns can be handled by the builder—thanks in large measure to a very thorough service manual that indicates possible defects in 4-color photographs. In addition, there are two *signal flow* diagrams; the first showing the signal flow through individual circuits and the second indicating graphically the tubes, coils and transformers through which the individual signals pass.

We have concentrated on the service aspects of the Heath rectangular-CRT color receiver because color TV has meant a return to the service conditions of 1946-1947, when virtually everyone purchased a *black-&-white* receiver with a service contract costing in excess of \$40. Whereas *black-&-white* TV has been improved to the point where many consumers can service their own set (it's generally a tube change), just a tube change or a minor component change can mean *complete servicing* for a color receiver. Therefore, the user who can service and adjust his own color receiver saves considerable monies over the life of the set as well as *always* enjoying excellent color reception.

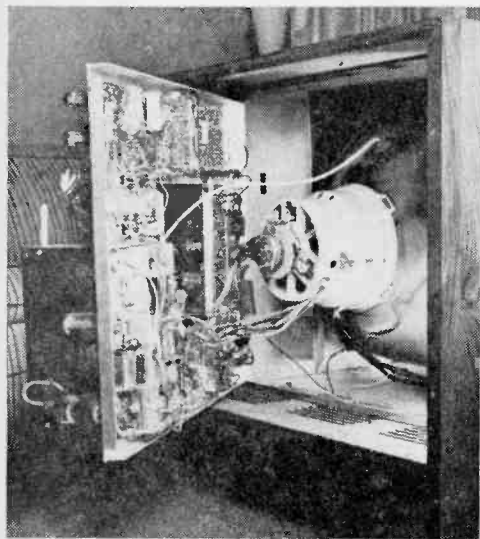Heath's 25-inch rectangular color TV kit—complete for wall or custom cabinet mounting—costs only \$469.95. Three optional cabinet styles are also available. For additional information, specifications and prices on the cabinets and other TV kits write to The Heath Company, Dept. EB, Benton Harbor, Michigan 49023.



Entire chassis on Heath GR-25 is hinged for convenient servicing. Note metal lining inside cabinet which serves as shield for CRT.

ERECTING A TV TOWER

by Homer L. Davidson

■ You don't have to be an expert to install your own TV tower. If you have a few ground tools around, such as a spade or shovel, and a strong back you are in business. A little elbow grease is all that is needed.

The TV tower has many advantages over the TV antenna pole installation on top of the house. One of the greatest assets is to get away from the wind vibration, in which the house acts as a sound board. With tight guy wires, running from the antenna mast and anchored to the house, vibration of the antenna itself, will play like a bass guitar. This noise on windy days can and will drive a person out of his mind, or make you want to push the panic button several times.

Also, the antenna on top of the house looks unsightly compared to a tower job. The antenna mast and foot mount corrodes and rusts out leaving brown rust spots on the new shingles. In level terrain the wind plays havoc with the guy wires, and if one guy wire breaks, as in many cases, down comes the antenna, mast and all. You might wind up with a damaged roof, and, of course, the antenna itself will probably be mangled and have to be replaced. And further, in parts of the country where ice and snow is a problem, it is much easier to climb a tower to fix the antenna or broken leadin.

Most TV tower installation between 20 and 40 feet do not need separate guy wires; these towers will stand alone. The cost of a TV tower will vary from \$50.00 to \$125.00 more than a roof top installation. Of course the exact amount will depend on the height of the TV tower.

Installing the Tower Base. First, pick out a good spot where the tower will not be in the way when walking or mowing the lawn. Install the tower close to the TV set or outlet.



ERECTING A TV TOWER



To plant tower you'll have to dig a hole first (left). Make it 40-inches or so deep—and some 2-foot square. If the soil is loose make base larger. Soil around new homes should be compacted or self-supporting tower may settle and tilt.



Do your digging in the cool weather and you won't be likely to have heat stroke (above). Just be sure it isn't freezing when you're ready to pour the concrete.



Work concrete into the hole—bubbles will only make foundation weak. Any looseness will increase the possibility of tower swaying and will reduce its ability to withstand bad storms, winds.



Spirit level is needed to get tower up straight. Prop it securely until concrete hardens.



If you have a small cement mixer don't wait too long between batches of concrete. It must be mixed into one solid mass. Keeping mixer close to hole eliminates need for barrowing.



You can just fill hole to within an inch or two of the soil's surface and cover with sod. Some prefer to place form around base for squared-off masonry top.

Keep away from flower beds and small shrubs. Most towers are mounted at the rear of the house, out of the way. You should never have over 100 feet of leadin wire overall. Do not mount it where the tower will block the view of a window. Locate a spot near the house where the tower will clear the eaves with a space of from 8 to 12 inches.

After you have found the best location dig a hole about 40 inches deep and 2 feet across. The diameter of the hole should vary according to the ground soil. If the soil is loose, like that around a new home, the sides will tumble in at the top. In hard firm soil a clean hole can be dug straight down. If you or your neighbor has a post hole auger handy, start first with this at the center of the hole.

Auger down a couple of feet and spade off the remainder of the dirt.

When you have dug to the required depth, you may want to scale back at the bottom. In other words, flare out the bottom of the hole. When the cement is poured into this hole we have added strength to the tower base. Keep the loose dirt picked up. Either place it in a wheel barrow and haul it away or lay down heavy paper so the dirt isn't tracked all over. If you have a good stand of green grass growing, this is a must. You will need some dirt to go on top of the cement base if you want grass growing around the tower. Do not haul it all away. You may want to fill around the house, flower beds, or low spots in the lawn with the extra



ERECTING A TV TOWER



Concrete must be firmly set before you start adding the other sections to the section set in the concrete base.



Make sure concrete has cured completely before attempting to climb or work on mast. Poorly set concrete will loosen and crumble.



loose dirt you will have left over.

If the concrete base is to support a fifty foot tower or higher, a larger and deeper base should be used. A 50 foot tower with a house bracket can be supported with a 3½ foot by 18 inch square hole. If the tower is higher, use a 2 foot square cement base.


Before the tower is placed in the hole pour in about three inches of rock gravel. Set the bottom section of the tower into the hole. Be sure that the small tapered end of the tower is up. If the tower section bolts are found in one leg, be sure to remove them before placing into the ground. Many of the new galvanized towers have a protection plug in one leg in which the mounting bolts are packaged.

Now place the tower in the hole and throw a couple of inches of gravel around the three legs. This allows moisture to drain into the gravel. In parts of the country where water will seep into the tower legs and freeze in the winter months the tower legs will split open. Splitting of the tower base will weaken the tower and may come down under strong winds. This may take years for the water to build up in the legs of the tower, but it has happened.

By placing the bottom of the tower down into the concrete a strong base is made. You can buy three-foot tower legs to go down into the concrete but a weakened bolt joint is just above the cement base. You can gain back the forty inches of sunken tower by placing

Orient the antennas—the last step. Double-check all fastenings before you start down to ground.

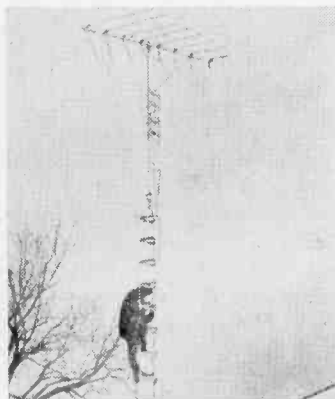Dress lead-in and attach stand-offs as you climb down mast.



Completely assemble the antennas on the ground and hoist the completed units to top of tower. If you're using a rotor mount that first.

a piece of antenna mast above the top tower section, if needed.

If you are going to mix your own cement with a small cement mixer use a 5, 3, 1 mixture. Use five parts rock to three parts sand to one part cement. These may be shoveled in or first mixed in a wooden box. It is quite expensive to have a small load of cement hauled in by a commercial cement company. You may want to check the prices first as these vary in different localities. In case there isn't a cement mixer in the neighborhood, rent one for a few dollars from a rent-all establishment.

Large rock or used brick may be used as filler. But, be sure and level up the tower

after each cement mixer load. Check the level on each leg of the tower to see if it is perfectly straight. This bottom base section must be perfectly perpendicular so the tower will not lean in any direction. Always depend upon the level or even a plumb line hung through the center of the section from the top.

It will take from four to six loads of average cement mixture to fill this type of hole. If you plan on growing grass above the tower base leave six inches for dirt fill. You may want to have a square cement base above the ground. Simply nail four pieces of 1 x 4 together and level above the ground, around the tower. Pour the cement level with the top of the boards and trowel down the top surface.

After each cement load, push the cement around in the hole. If the cement is mixed quite wet, the mixture will pour and level much easier. The hole may be a little irregular, but fill it up with the concrete mixture.

Leave the concrete set up for at least two days before attempting to work on the tower. It is best to cover the top of the cement base with heavy cardboard, or paper, while ripening and setting up. This will keep rain, snow, or foreign objects from falling in on top of the fresh cement. Have you given that level a final check? Do it now; check the level of the bottom section several times during the setting up period.

On upward. When the tower cement base has set up, you can now place the next ten foot section in place. If a reamer, or round file, is handy, clean out the sleeve of the enlarged end of the metal tower. A ten or twelve inch tapered punch will help to align up the tower ends.

One person can lift the second ten foot section of tower into place if need be. But, two men can do it a lot faster and safer. You can lift this section in place from the ground. You may have to tug on the last leg to get it to align up and then pull down on the tower. Line up the holes with the tapered punch. Insert the mounting bolts. Leave the nut and threaded end of the bolt toward the inside of the tower.

If the bolts are hammered through the tower sections, the threads will become stripped. Use the punch to align the sections so the bolt will pass easily through the legs. Do not drill the holes larger. Be sure to tighten all leg bolts until they partially flatten the sleeves, causing the sleeves to actually grip the legs inside. Upon tightening the



ERECTING A TV TOWER

bolts, there should be no vertical movement between tower section at the joints when working on the tower.

You do not need any special hoists, or gadgets to lift the tower sections in place. Simply put your arm through the second round section, from the top, and climb up the tower with the added section on your shoulder. The third section may be lifted in place with one person standing on the house and the other person on the tower. If not, one should climb to the top, stick one leg down through tower and out on the second brace. You cannot fall out of this position. A climbing belt is also useful, but not necessary when working on the TV tower.

While one person is in this position another can bring the tower section up the tower. Don't worry about the tower holding the two of you; it will hold up several people. The person in the tower can raise it and balance the tower while the other fits the sections together. Each section should be bolted before another section is raised in place.

The top tower section has a large piece of pipe for the antenna mast to stick down through. If the antenna is to be in a fixed position a set screw is located in the mast housing. A rotator may be mounted on top of this pipe and the antenna above it. You can install the rotator inside of the top section. There are rotator mounts for this type of installation.

If the rotator is to be mounted at the tip

of the tower, fasten the leadin wire to the correct terminals before mounting. Now mount the rotator in place and tape the rotator cable to one leg of the TV tower. The antenna should be folded out and leadin cable added to the antenna terminals. Wrap these terminals with friction tape and place a mast standoff within six inches of this antenna connection.

Carry the antenna up the tower and swing in place. Tighten the antenna brackets and seek the right direction for the fixed antenna. If it is to be mounted on a rotator check and see if the rotator is a north to north direction rotator. Point the antenna north and bolt in place. Be sure and face the correct end of the antenna in the northerly direction. On yaggi or flat type antennas, the shorter end always points toward the front of the antenna, or towards the TV station.

Leave a loop of wire so the rotator will turn freely and not bind as the antenna is being turned. Place an antenna mast standoff above and below this loop. Space the antenna mast standoffs every four feet down one leg of the TV tower. Do not clamp this mast strap over the rotator cable as it can, when tightened, ground out the rotator cable to the TV tower.

Be sure to keep the antenna standoffs in line down the tower. For local UHF reception, place the UHF antenna below the rotator or the large VHF antenna. If there are several UHF stations in the area, mount the antenna above the VHF antenna on the TV rotator.

Cleaning Up. Clean up the area around the base of the TV tower. If the cement mixture has splattered on the legs of the tower, let dry, and then wipe off. Protect the brick or house siding from cement splattering with cardboard or heavy construction paper.

Remove any temporary guy wires, if used. Check the direction of the TV antenna. You should zero the antenna in with someone watching the TV reception on a fixed position.

You may want to use a house bracket and extend the tower another ten or twenty feet. These brackets come in adjustable lengths and lag to the side of the house. Most towers should not be mounted more than 30 feet above the house bracket. You may go up to greater heights by guying the TV tower. Fasten a set of three guys on every twenty feet of tower. ■

TOWER MANUFACTURERS

E-Z Way Towers, Inc.
5901 E. Broadway, Tampa, Fla.
Rohn Mfg. Co.
P.O. Box 2000, Peoria, Ill.
Tri-Ex Tower Corp.
7182 Rasmussen Ave., Visalia, Calif.
Vesto Co., Inc.
20th & Clay, N. Kansas City, Mo.
Tristao Tower Co.
415 East 5th Street, Hanford, Calif.
Aermotor Towers
Broken Arrow, Oklahoma 74012

It's OK with WDDD for legit stations to broadcast on 1200 kc., but when some other outlaw muscles in on the same freq, then it's



One Too Many Pirates

by C. M. Stanbury II

■ Bill Doggit worked into the last few bars of "Honkey Tonk" and I prepared my best announcing voice nice and deep. Behind me, April tuned up her guitar. As Doggit hit his last wild note, I raised one hand and April hushed up. I switched on my mike, "This is WDDD, the swinging voice at 1200 on your dial, covering the county like a blanket, man. Right up tight." I paused for breath.

April fiddled with her guitar and accidentally struck a chord. I gave her a dirty look.

"This is your ding-dong daddy from Michigantown, Paul Arrowood, broadcasting from Studio number 4, 3000 Illinois Avenue." It was a fictitious address complete with vacant lot. "Stay tuned in for just a few minutes and WDDD will bring you an exclusive—Folk Spotlight on Miss April West." I cut my mike, switched the turntable back into the circuit, and its automatic record changer brought forth Bob Dylan. I looked at April. "Dylan's a rough act to follow, honey."

She shrugged. "Should put everyone in the mood." April sang along with "Times They Are a Changing."

WDDD was a foolproof operation. We used the transmitter of Frontier University's carrier-current station WRFU 600 kHz (kc), but with the power of its 1200 kHz harmonic boosted and a good radiating antenna added. Even if the FCC should move in, only thing they'd catch would be Frontier U's own station WRFU, which specialized in the classics and basketball.

Dylan had reached "Oxfordtown."

April nodded, brushed a strand of hair from her eyes, raven black and hanging loose. "Hey, are you sure the channel is clear?"

"Nearest station is San Antonio, Texas."


"I heard someone on yesterday morning."

Softly, she moved her shoulder in time with the music.

"Must have been WRFU."

"With Lawrence Welk?"

"What do you want me to do? Turn the

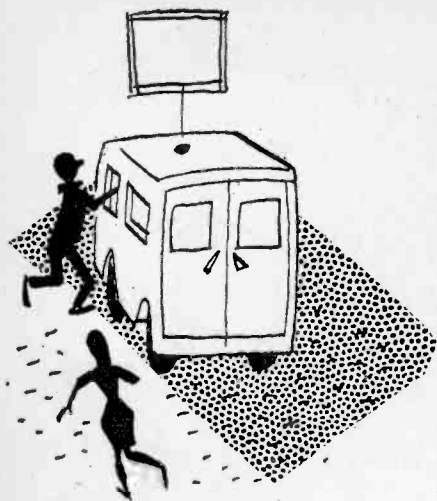

station off and listen?"

April strummed her guitar. "Yes, that's what I want you to do."

I considered it. Like until April knew yours truly had his own radio station, and a clear channel, I couldn't get to first base with all that long, lovely hair. "Okay, I'll check but it'll have to be fast or we'll lose our audience." I cut Dylan, then the transmitter. Switched on my Zenith Super Navigator and located 1200 kHz.

We both did a double take. There was another station on the channel, complete with antique version of "Sweet Sixteen." I checked to make sure I had the right frequency. I did!

April tapped her guitar and glared at the receiver.

Then yon rival announcer came through loud and clear. "This is station ASCM, the American Society for Clean Music, dedicated to stamping out rock'n roll, rhythm'n blues, jazz and all folk music, transmitting from our new crystalline studios at 3000 Illinois Avenue."

I said something to myself which I hoped April didn't catch. ASCM had not only swiped WDDD's frequency but our phony address too.

They started on "Ah, Sweet Mystery of Life." April put down her guitar, came to the receiver and nulled them with its direction finder. The thing zeroed in on Illinois Avenue. April stood with hands on her hips. "What are you going to do about it?"

"We could just wait until they go off the air."

She shook her head and set the mouth. "Or we could take my Zenith out to the

car and hunt ASCM down."

"You certainly could." April picked up the receiver and headed for my 1949 Ford.

I followed with the keys. She sat in the back while I drove. Every so often April would rock the direction finder to make sure I was still on course. As we got closer to Illinois Avenue, ASCM got so strong you could hear it loud and clear even with the null dead on them.

After 10 minutes of uninterrupted dirges, "Remember you are tuned to ASCM, the coming spot on your dial. ASCM is affiliated with the International Hygiene Alliance, a worldwide movement to sweep the Earth spotless."

At Illinois, we waited for a red light.

April swung the DF in a circle. "Can't tell whether it's North or South but try North toward 3000."

Light turned green but I hesitated. "Couldn't be 3000. That's a vacant lot, remember."

"Try North, anyway."

Somebody banged his horn behind us and I headed for 3000.

April watched the S-meter carefully. "It's getting louder." Victorious feminine tone.

ASCM switched to a series of musical V's for victory.

I looked back over my shoulder at April. "Suppose this guy is bigger than me?"

She shrugged her shoulders. "You can cross that bridge when you come to it."

It came quick. Every light turned green for us and in a few minutes I could make out 3000 ahead. Parked right in the middle of the vacant lot was a panel truck complete with portable antenna. I parked, got out and moved warily across weeds and assorted junk. April followed. Inside the truck was a little fellow with horn-rimmed glasses, mike in one hand and record player beside him on the seat. I began to feel brave. "ASCM?"

He looked up. "That's right."

I opened the door beside him. "Well, brother, you're on my channel."

He fiddled with his mike. "And who are you?"


In my most menacing voice. "WDDD."

"That's your station?"

"Yes, and 1200 is my frequency."

"According to our records it belongs to WOAI." He put down that mike and brought forth some identification. "*Federal Communications Commission, Field Inspector.*"

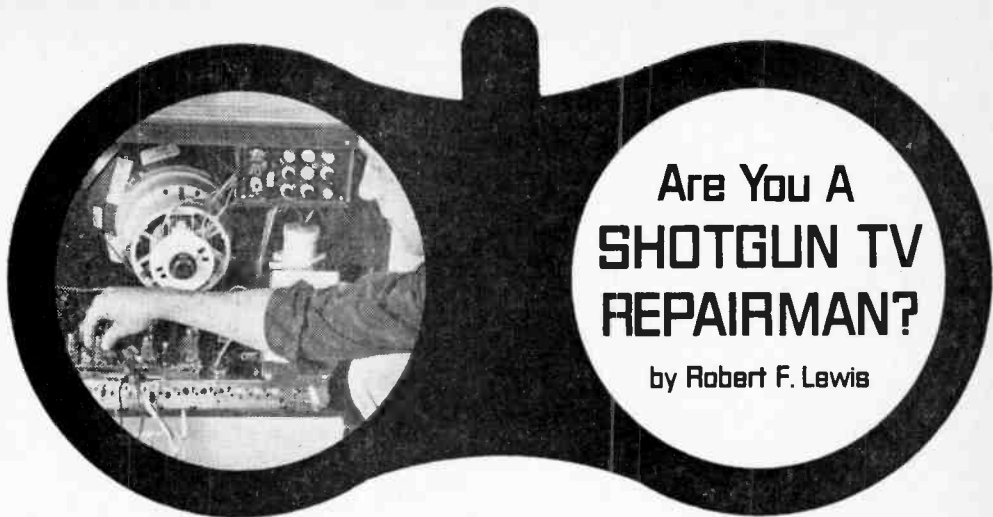April slipped away, back toward the car as the FCC fink made out my summons. ■



Are You A SHOTGUN TV REPAIRMAN?

by Robert F. Lewis

**Don't check all your TV tubes—
just those in circuits most
likely to cause those symptoms.
Know where to look!**

■ When it comes to do-it-yourself TV servicing, do you use the “shotgun” method to locate bad tubes? If you're the average, non-technical, television set owner you probably do, since you couldn't be expected to know exactly where the target is. What do I mean by the “shotgun” method? Well, here's how it works:

Your TV set is acting up. So you pull out all or most of the tubes, cart them down to the corner drug store or supermarket, and run them through the do-it-yourself tube checker. You find two or three that show a “bad” or “questionable” reading, so you buy some new ones. When you get home and plug in the new tubes, you may find that you still haven't cured the sickness. Even if you have, there's a good chance you've replaced some tubes needlessly, since a questionable tube-checker reading doesn't always indicate a bad tube.

First Step Forward. What can you do to avoid this unnecessary expense? Here are some tips that may save you considerable cash and frustration the next time you tackle the one-eyed monster!

First, unless you have some technical knowledge of television, you shouldn't ordinarily attempt to carry servicing beyond the tube-changing point. You don't have to be

an engineer or technician just to change a TV tube, but it does help to have a little familiarity with the inner workings of your set. This isn't as complicated as you might think; you can learn enough about it in the time it will take you to read this article.

Second, most TV receivers have, pasted somewhere inside the cabinet, a tube location diagram. This gives you a wealth of information; it tells you the type and location of each tube, plus the kind of job it does.

Now, with these two pieces of knowledge at hand, you should be able to direct most of your troubleshooting efforts to smaller sections of your set—to zero in on the exact tube or tubes ruining your viewing. You shouldn't have to use the expensive scatter-gun approach.

Before we go any further, let's agree to concern ourselves only with black-and-white TV. Unless you have considerable servicing know-how, it's best to leave most color TV repairs, even tube changing, to a competent repairman, since many of the circuits in color TV sets require critical adjustment for proper color rendition.

A Little Theory. What is a television picture composed of? If you look at any newspaper photograph—called a “halftone” illustration—through a magnifying glass you will

SHOTGUN TV REPAIRMAN

see that it is made up of rows of fine black dots. In the light areas of the picture the dots are very small, leaving considerable white space between. In the darker areas the black dots are larger, leaving less white space. At a distance your eye sees the whole mass as a complete picture, since it can't distinguish between the individual dots.

Now, turn on your TV set and tune it to some channel where no picture is being transmitted. Look closely at the screen. See how the picture is made up of a series of horizontal lines of light? These lines are actually traced on the screen by a rapidly moving spot of light produced when a sweeping electron beam inside the picture tube strikes the screen. The spot travels across the screen, starting at the upper left-hand corner and working down to the lower right-hand corner, in the manner shown in Fig. 1. For

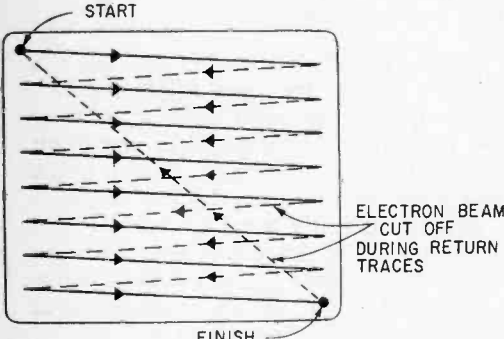


Fig. 1. Simplified diagram of TV raster does not show complicated interlacing.

the sake of clarity, we have shown the lines much farther apart than they really are on your TV screen. There are actually 525 of these lines on the screen.

When the spot gets to the lower right-hand corner, it returns almost instantly to the starting point and repeats the trace. This screen "painting" process is repeated at such a rapid rate that your eye cannot detect the movement of the spot, but sees the screen as though it were continuously lighted. The technical name for the lighted screen is the "raster." Keep this term in mind. We'll use it again later.

At the Studio. Now, if we were to break up the horizontal lines into dots of varying brightness, we would have all of the neces-

TV TROUBLESHOOTING CHART

Symptom	Possible Source of Trouble
No picture, sound or raster	Low-voltage rectifier. Filament burned out in one tube of series-connected string. Fuse.
Picture dim, does not fill screen. Sound weak.	Low-voltage rectifier.
Picture and sound weak or dead. Raster OK.	RF amplifier, oscillator, mixer, video IF amplifier, video amplifier.
Picture dead or has low contrast. Raster OK. Sound may be dead in some sets.	Video amplifier.
No sound. Picture OK.	Sound IF amplifiers, ratio detector, audio amplifiers.
Picture does not fill screen vertically. Cannot be corrected with height control.	Vertical oscillator and vertical output, low-voltage rectifier.
Picture rolls vertically. Cannot be stabilized with vertical hold control.	Vertical oscillator, sync separator, sync amplifier.
Picture does not fill screen horizontally. May also be dim.	Horizontal oscillator, horizontal output, damper, low-voltage rectifier.
Picture flops over sideways and rolls vertically.	Sync separator, sync amplifier.
Picture flops over sideways. Cannot be stabilized with horizontal hold control.	Horizontal oscillator, sync separator, sync amplifier.
Picture dim but raster fills screen. Sound OK. Sync OK. Cannot be brightened with brightness control. Image sometimes "blooms" around edges when brightness control is turned up.	High voltage rectifier, damper, picture tube.
Picture does not fill screen either horizontally or vertically.	Low-voltage rectifier.
Picture contrast fades up and down, excessively.	AGC, RF and IF amplifier tubes.

sary elements for a picture, as we saw in the newspaper illustration. In practice, this is essentially what is done. The light and dark portions of a TV picture are produced by simply varying the intensity of the electron

beam as it paints the screen. The signals that produce this variation originate in the camera in the TV studio. The image "seen" by the camera is swept by an electron beam in the same manner we have just described for the receiver picture tube. But instead of painting a scene, the camera breaks the image it sees into bits, like the dots in the newspaper illustration. These bits are sent out in sequence by the TV station, received by your TV set, and reassembled on the picture tube screen in exactly the same order and position. To create the illusion of a complete picture, these bits are broken down and reassembled at an incredibly rapid rate, several million per second. Other signals transmitted by the TV station synchronize the picture tube in your set with the studio TV station synchronize the picture tube in your set with the studio TV camera so that both will begin "painting" at exactly the same instant. The third signal transmitted by the station is the sound or "audio" signal. If the picture is in color, additional color-information signals are transmitted. Sounds fantastic, doesn't it?

same as, or similar to, those indicated on our diagram. In some cases you'll notice that a single tube does several jobs, possibly in completely unrelated sections. This is because many tubes contain two or three sets of elements in one envelope, a space-saving trick.

Sound, picture, and synchronizing signals from the TV station arrive via your receiving antenna and are all processed in the *RF amplifier, mixer, oscillator, and video IF amplifier* tubes.

These signals continue on to the *video detector* and *video amplifier* tubes where they are further processed. The picture signal is extracted and applied to the picture tube where it controls the variations between dark and light on the screen.

The synchronizing signals are routed through the *sync amplifier* and *sync separator* tubes, then applied as locking signals to the *vertical oscillator* and *horizontal oscillator* tubes.

The sound signal is separated at this point and passed through the *sound IF amplifiers*,

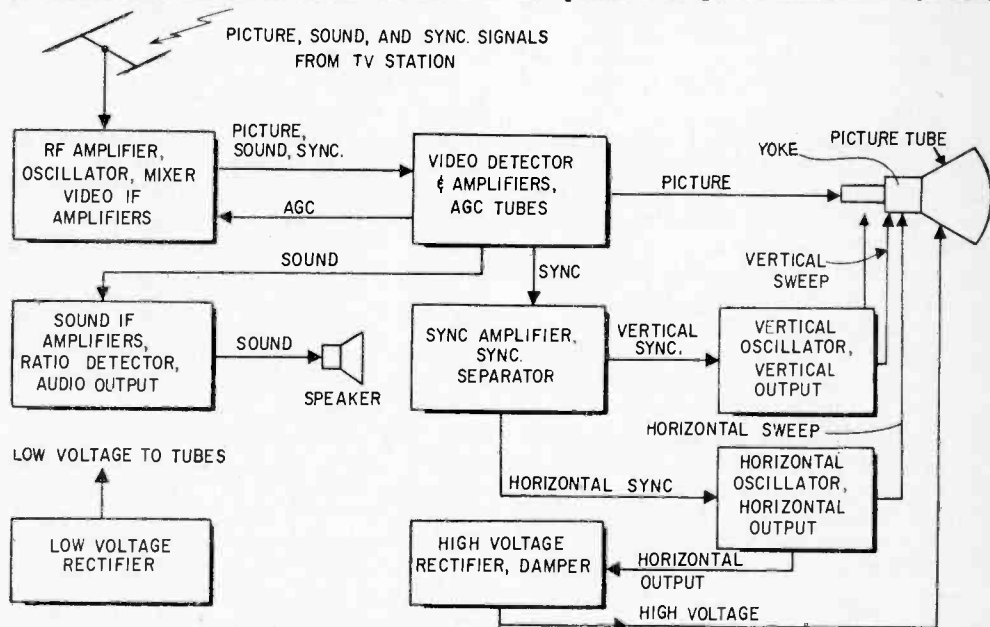


Fig. 2. Block diagram of TV circuitry is just about the same for all black & white TV sets.

Around the Block. Now, let's take a look into your TV set. Fig. 2 is a simplified block diagram showing the electronic-tube circuits in a typical black-and-white television set. Let's trace the routing of signals through the diagram. As we do this, refer to the tube location diagram in your own set and see if you can find tubes whose functions are the

ratio detector, and *audio amplifier* or *output* tubes, then to the loudspeaker.

Another circuit is the AGC or automatic gain control.

The purpose of the AGC tubes is to minimize fading or fluctuations in the picture contrast that may occur when the incoming TV signals fade. This often happens when

an airplane is flying overhead.

The *vertical oscillator* and *vertical output* tubes control the vertical sweeping of the electron beam in the picture tube. The horizontal sweeping of the beam is controlled by the *horizontal oscillator* and *horizontal output* tubes.

Every picture tube requires a potential of somewhere between 10,000 and 25,000 volts for its operation. This voltage is generated by the *horizontal oscillator*, *horizontal output*, *high voltage rectifier*, and *horizontal damper* tubes. Very little *current* is developed in most high-voltage systems, so it is generally not dangerous to human life; although if you get a jolt from it, it can be startling and uncomfortable; something like getting a shock from an automobile ignition system.

Finally, the *low voltage rectifier* tube supplies all of the lower voltages to the other tubes in your TV set. In the more recent models, a metallic rectifier is used instead of a tube for this purpose.

Zeroing In. Now that you have more than a nodding acquaintance with your TV set, how can you use this newly gained knowledge? Here's an example, a typical troubleshooting situation:

Let's assume that your picture tube screen is brilliantly lighted and that the raster completely fills the screen. Yet there is no sound and no picture. Looking at our block diagram, you can see that the sections that are common to both picture and sound are the ones that include the *RF amplifier*, *mixer*, *oscillator*, *video IF amplifiers*, *video detector*, and *video amplifier* tubes. So you proceed to check these tubes. Forget the others.

Another common TV complaint is vertical "rolling." The image keeps slipping up or down and cannot be stabilized by adjusting the *vertical hold* control. This symptom indicates that your TV set is not synchronized with the camera at the TV station. It is likely to be caused by a faulty *vertical oscillator tube*, or perhaps by a weak *sync amplifier* or *sync separator*. This narrows your search down to two or three tubes; no need to use the "shotgun" system. Our troubleshooting chart directs you to source of still more symptoms in a malfunctioning set.

Picture Tubes. The TV picture tube gen-

erally gives long life if properly installed and adjusted. Loss of electron emission due to old age is a common problem, however, and is indicated by a gradual dimming of the picture that cannot be restored by adjusting the brightness control or by replacing small tubes. The life of a picture tube that shows aging can often be extended by installing a *picture tube brightener*. However, you should not use a brightener on a perfectly good picture tube, since it increases the heater voltage and may reduce the life of the tube or even burn it out.

If you are going to use a picture tube brightener, first determine if your TV set has *series* or *parallel* connected tubes; then buy the corresponding type of brightener. If all of the tubes in your set (except the high voltage rectifier and picture tube) begin with the number 6 or 12, the tubes are probably parallel connected. If the tube designations start with various numbers other than 6 or 12, series connection is most probable.

Pulling Tubes. Here are a few tips to keep in mind when replacing the small tubes in your TV set.

1. Be sure to turn off the receiver and disconnect the power plug before working inside the cabinet.

2. Wait for the tubes to cool enough to handle before trying to pull them out.


3. Discharge the stored high voltage from the picture tube by connecting one end of a *well-insulated* wire to the TV set chassis and touching the other end of the wire to the high-voltage terminal which connects to the side of the picture tube envelope. You'll probably have to slip the wire under the edge of the rubber insulator to make contact with the high-voltage terminal.

4. When you replace a tube, be sure that the new one is the correct type number as marked on the tube location diagram. Don't switch tubes around just because they look alike, unless they have the same number.

5. Be careful not to bend the pins on miniature tubes. Be sure the pins are straight before attempting to insert tubes in sockets.

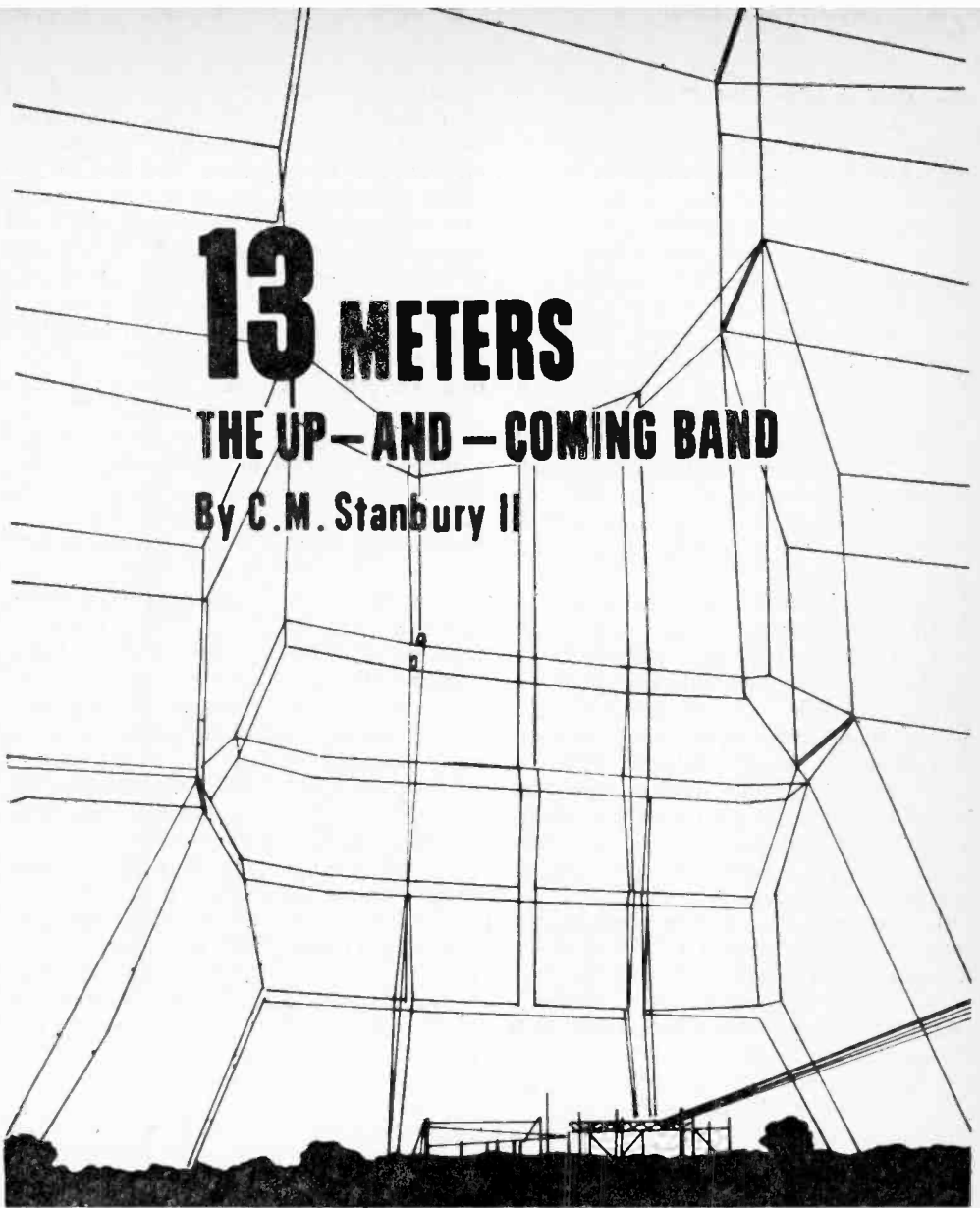6. If you doubt some of the readings you get on a do-it-yourself tube tester, recheck the tubes on another machine before investing in a new tube.

If your diagnosis fails to turn up a faulty tube because the trouble lies deeper, then you'd better turn the job over to your serviceman. However, if you're successful, you can sit back and bask in the glow of your TV set and the cash savings you've made! ■



13 METERS

THE UP-AND-COMING BAND

By C.M. Stanbury II

■ How many shortwave listeners even know there is an international broadcast band between 21,450 and 21,750 kHz (kc)? If you're one of those who didn't know, it's not surprising because due to the recent low sunspot activity the band has been virtually useless. But now as we enter a new phase in the solar cycle, these frequencies suddenly become important. Already there is a trickle of activity and it may soon become a flood.

Now we're sure it will surprise no one that *Sporadic-E skip*, a phenomena so important to the TV DXer and CBer, often occurs on 13 meters. But Sporadic-E reception is gen-

erally limited to, at best, 2000 miles, and about 1000 miles is by far the most common. Thus 13-meter E skip will produce strong signals from VOA transmitters at Greenville, N. C.; Bethany, Ohio, and Delano and Dixon, California, but not much else. International reception on these frequencies requires an active F2 layer. This is the uppermost layer of the ionosphere and its reflecting powers increase as the sunspot count goes up (but strangely enough, F2 reflection is best in winter; poorest during the summer.

When to Listen! Further, 13-meter F2 reception will peak at 1400 local time. But

wait. That is local time at the *mid-point longitude*—halfway between transmitter and receiver. Take for example an East-Coast North-American SWL (75 degrees West) and the BBC in England (0 degrees). The midpoint is 37½° West longitude and as each 15 degrees of longitude equals 1 hour, 1400 local time at 37½ degrees West occurs at 1130 EST.

Similarly, on the East Coast, reception from Oslo, Norway (10 degrees East) would occur about 20 minutes earlier. Of course it really isn't quite as cut and dried as we've indicated, nothing on shortwave is cut and dried, but nevertheless this method of rough calculation is a good guide. And again, the length of time reception occurs at these peak periods will keep pace with the sunspot count.

No Noise. With the exception of ignition noise (which depends entirely upon the listener's particular location), reflection (or lack of it) on 13 meters, is the only problem. Atmospheric noise virtually does not exist up here. And, because very few stations presently use these frequencies, interference is seldom a problem either. Which means that the band is at present ideal for novice short-wave listeners. Stations are easy to find—even on simple receivers and signals are not garbled by heterodynes.

For the uninitiated, a heterodyne is that annoying whistle produced by two transmitters only a few 1000 Hz apart. For example, if stations are separated by only 2 kHz, they will produce a noticeable 2000 Hz (cps) heterodyne even though one of the offenders may be comparatively weak. Another plus for the beginner—when 13-meter transmissions are reflected by the ionosphere, the resulting signals are generally strong, a really important factor when using low-priced receivers.

Sky Hook Facts. Also at present almost any antenna, including that random length of wire you probably use for general recep-

tion, will do. However a directional (half-wave) dipole can be readily constructed. It should be 22-feet long and run broadside to the direction from which you want to receive. For Europe and Australia it should run NW/SE; for Africa and Asia NE/SW. If possible, the lead-in should be attached to the middle of your dipole. Obviously the ideal arrangement would be a pair of dipoles at right angles to each other and a switching system which would enable you to take your pick of directional effects.

Here Comes Trouble. However, 13 meters will not stay a band solely for the novice very long. It is about to become a major daytime weapon in the shortwave radio war. Just take a look at what is happening on the bands below it. On 31, 25 and 19 meters international broadcasting is literally strangling on QRM with simply not enough channels to go around. As soon as one station finds a clear frequency, two or three others appear on that same spot within a few days. As a result the major powers have engaged in an extremely expensive, and for the most part fruitless, power race.


Obviously 13 meters' virgin territory—all 300 kHz of it beckons irresistibly. Further, as this band is normally open only to one part of the world at a time, interference can never be the problem it has become elsewhere. Even deliberate jamming will be more difficult—making it an ideal band for such stations as Radio Free Europe and Radio Liberty.

The first widespread use of 13 meters by northern latitude stations should occur early in 1967. Of southern hemisphere stations, Radio Australia is already active and during the summer of '67 (winter down there) they should be joined by Radio South Africa and possibly Radio New Zealand. While on paper 13-meter reception will not appear as reliable as on the lower bands, many broadcasters will be pushed by the QRM into *taking a chance* up here. Smart SWLs will be prepared to gamble along with them. ■

13-Meter (21,450-21,750 kHz) Frequency Guide

kHz (kc)	Station	kHz (kc)	Station	kHz (kc)	Station
21455	VOA, Tangier, Morocco	21545	R. Ghana	21670	VOA, Monrovia, Liberia
21470	BBC, England	21570	R. Nederland, Netherlands	21690	VOA, Tangier, Morocco
21485	VOA, Bethany, Ohio	21580	ORTF, Paris, France		
21495	Emisora, Nacional, Portugal	21590	R. Pakistan (Karachi)	21700	Emisora Nacional, Portugal
				21710	BBC, England
21520	SBC, Switzerland	21620	ORTF, Paris, France	21720	R. Free Europe, Portugal
	VOA, Greenville, N. C.	21630	BBC, England	21730	R. Norway
21530	BBC, England	21650	VOA, Bethany, Ohio	21740	VOA, Greenville, N. C.
21540	R. Australia	21665	R. Free Europe, Portugal		

DIGITAL CIRCUIT TRACER

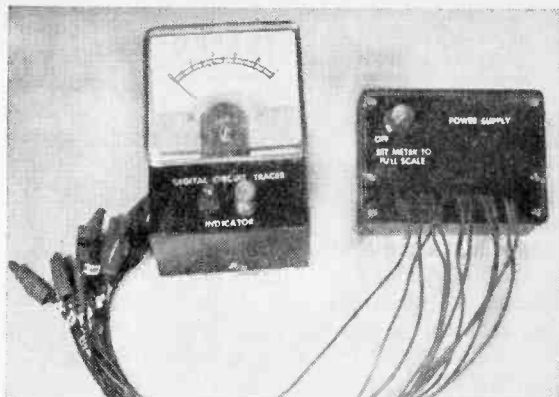

by James A. Fred

Build this adapter and watch your multimeter turn digital circuit tracer before your very eyes!

■ Guided-missile test facilities use many cables to connect the missile to the many pieces of test gear. Some cables are 100-feet long and have as many as fifty wires. Making these cables—soldering on the connectors—is a real job. Technicians normally solder the wires (if they are equal in size) to any pin in the connector. Then they test (with a lead from a buzzer, connected in series with a transformer, to a pin in the connector), touching each projecting wire

from the other end of the cable until the buzzer sounds. This method of identifying wires takes a lot of time.


What To Do? Here is what I call a *Digital Circuit Tracer*. It indicates the number (digit) of the wire you are connected to. The meter only identifies circuits from one to ten, but if you have a meter calibrated 1.2 or 1.5 at the full-scale point you can add a few more resistors or make a new meter scale.

By using color-coded insulation you can divide the cable wires into groups of ten—or whatever grouping is best for you.

How It Works. The principle upon which this circuit tester works is simple. One of the two units consists of a 1.5-volt dry-cell, a potentiometer and a voltage divider of equal-value resistors.

The resistors' value and the supply voltage are determined by the meter scale. To use a 0-1 volt meter that was on hand, the voltage divider was designed to use each one of the major scale markings as a wire (circuit) number. That is: if the meter reads .4-volt, the leads are connected to circuit 4.

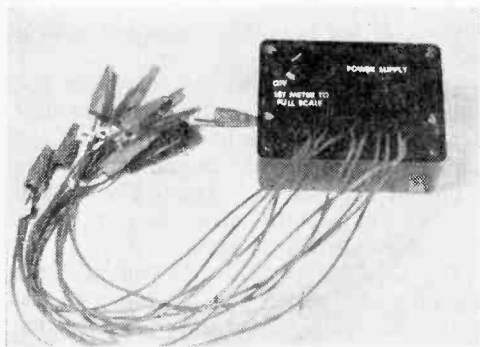The voltage divider was designed to draw 1 milliampere for long dry-cell life with



Adapter can be used with any VOM or VTVM. Miniature clips connect to one end of the circuit—common lead has dark insulator.

DIGITAL CIRCUIT TRACER

a minimum of meter loading. Potentiometer R1 is connected in series with the voltage divider to compensate for dry-cell aging. Connecting the meter leads between the *common* and *circuit-10* clip lead, R2 is adjusted for full-scale (1 volt) meter indication.

One-tenth volt (0.1) can be measured across each of the ten 100-ohm resistors in the voltage divider. The meter is a 0-1 volt indicator. With one lead on the *common* connection, 0.1 volt will be indicated when the other meter lead is on the cable wire connected to *clip 1*, 0.2 volt when connected to *clip 2*, etc. The number on the meter scale always indicates the clip lead number.


The meter can be any voltmeter—a

Power Unit. You can house circuit tracer's power unit in a phenolic box with a cover. If you use a metal cover you'll need grommets for the clip-lead wires.

Just about any size 1.5-volt dry cell can be used—the larger it is the less often you'll have to change the cell. C- or D-size flashlight cells are readily available and one should last two or three months if you use it for only a short time each day. If the cells are easy to replace, it really doesn't matter.

Resistor R13 is used to reduce the voltage drop across R1 if you can't get anything but a 1K potentiometer. When the dry cell is new you'll probably need a total resistance of about 600 ohms for the combination of R1 and R13. Just be sure the minimum-resistance position is very close to zero ohms.

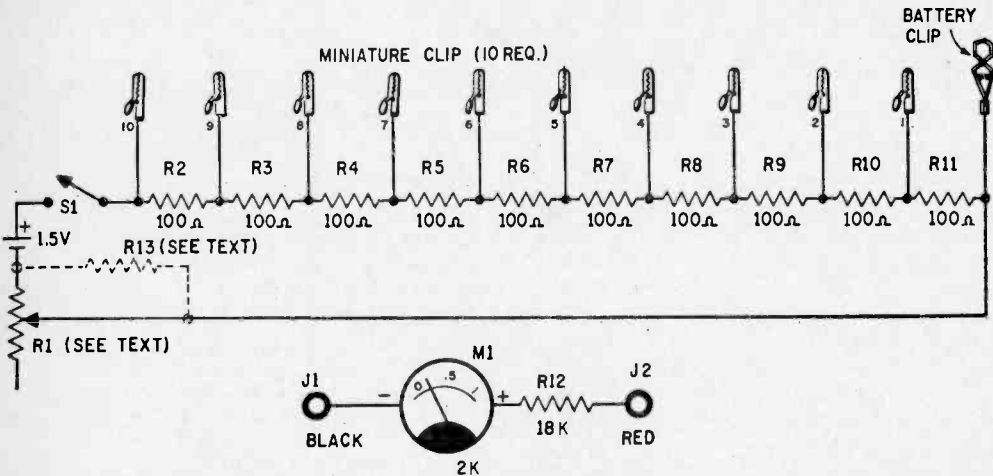Indicator. Indicator-box dimensions are determined by the size of the meter that will be used—if you put your VOM or VTVM



The schematic diagram is easy to follow and the instrument can be built by anyone who can use simple hand tools. Indicator unit can be used in place of workaday VOM or VTVM.

VTVM or VOM will do. Or you can use a 0-50 microampere basic movement with an 18,000-ohm multiplier resistor connected in series. Even a 0-1 millimeter can be used but meter loading will prevent accurate indication unless you change the voltage divider to draw a higher current. Use 10-ohm resistors in the voltage divider to draw 10-times the current drawn by the meter and the needle won't point between numbers although it might be a little off. Of course, dry-cell life will be shorter.


Construction. The components used in this tester were selected from those on hand. (Closest-available catalog parts are given in the parts list.)

to work as the indicator you won't need a box at all.


The parts list doesn't specify either the meter or the meter case since any practical physical-size meter can be used—if you can latch on to a 7-inch meter you can sit way back and not have to squint. Then again, you can put a 1-inch meter to work if it's more convenient for you.

Test and Calibrate. When you finish the assembly and wiring you are ready to test and calibrate the circuit tracer. Calibration is as easy as zeroing your ohmmeter.

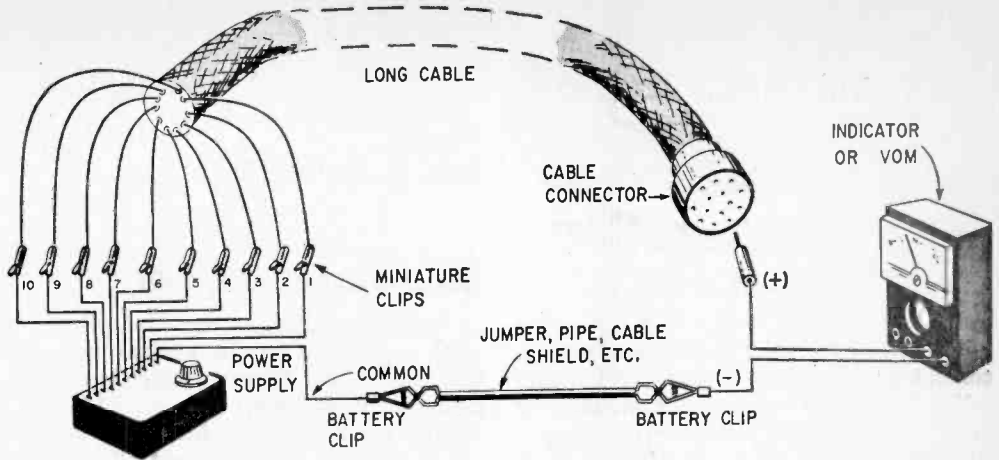
Connect the *black* lead of the power unit to the *black* binding post of the indicator or the *negative* lead of a VOM or VTVM.



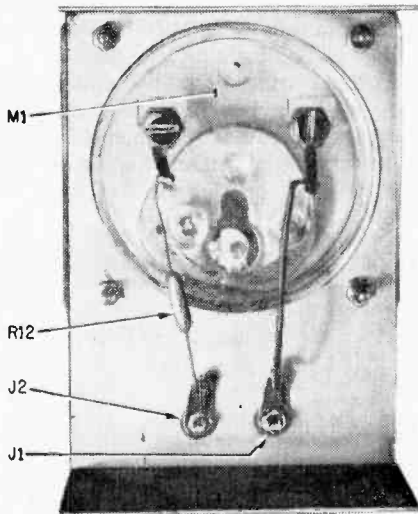The most common use for the Circuit Tracer is for checking cables. Plug is soldered to one end and power supply unit connected to the other end. Meter lead probes connector pins.



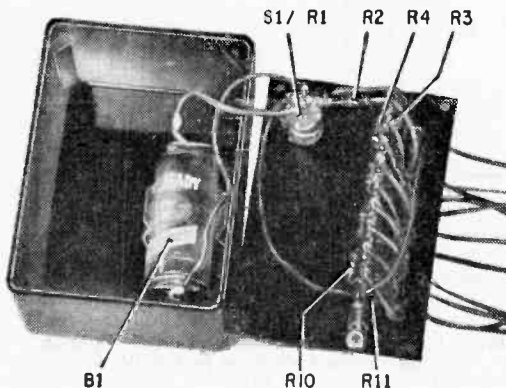Inside of indicator unit shows the meter and multiplier resistor (above). Heart of instrument is handful of resistors, wired to tie strip, connected across dry cell.



PARTS LIST

- B1—1.5-volt dry cell (any size to fit your case)
- J1, J2—5-way binding post, 1 red, 1 black, for indicator (see text) (Lafayette 99R6623 or equiv.)
- M1—Meter for indicator (see text)
- R1—500-ohm, 750-ohm or 1,000-ohm miniature potentiometer with switch (Lafayette 32R7362—see text—or equiv.)
- R2—R11—100-ohm, 1/2-watt, resistor $\pm 5\%$ (or better)
- R12—18,000-ohm, 1/2-watt, resistor $\pm 5\%$ (or better)
- R13—500- to 750-ohm, 1/2-watt resistor (see text)
- S1—S.p.s.t. switch (part of R1)
- 1—Plastic box, 2 7/8 x 4 x 1 1/16-inches (Allied 87U895 or equiv.)
- 1—Box cover—phenolic sheet (Burstein-Applebee 11A179 or equiv.)
- 1—Dry-cell holder (to fit B1)
- 1—Meter case (to fit M1—see text)
- 10—Alligator clips, miniature (Allied 45U142 or equiv.)
- 10—Clip insulators, red, for alligator clips (Allied 45U046 or equiv.)
- 1—Battery clip (Allied 45U000 or equiv.)
- 1—Clip insulator, black, for battery clip (Allied 45U054 or equiv.)
- Misc.—Knob, wire-marking number tabs, test-lead wire, terminal strip, hook-up wire, solder, machine screws, etc.

Estimated cost: \$4.00

Estimated construction time: 2 hours

Connect the *number-10* power-unit lead to the red terminal of the indicator or the positive (+) of the VTVM or VOM.

Turn the switch *on* and adjust the *Meter Set* control (R1) for a full-scale reading on the meter.

Now, in turn, connect each of the numbered leads of the power unit to the *red* (Continued on page 125)

FD

Propagation Forecast

By C. M. Stanbury II

October/November 1966

With atmospheric noise (static) dropping to respectable levels throughout the country, conditions will at least be tolerable for both DXer and general listener. But one casualty of the rising sunspot count is 41 meters, at least from the broadcast point of view. (Not that BC stations won't be heard.) This band will be dominated by Hams, who are supposed to own it—in this hemisphere anyway.

Further, daytime reception on 31 meters will not be spectacular. This means that most real DX reception, at least the rare-country variety, will take place at night. During the hours of darkness 31 meters will be open to all parts of the world while at the same time 49 and 60 will continue to of-

fer excellent Latin American reception.

As a majority of the stations you can hear on 49 and 60 meters will be of the latin variety, you must take special care to identify them correctly. Many LA stations will operate on the same spot all speaking Spanish—except Brazil (Portuguese) and Haiti (French) plus of course some English in the West Indies. The Spanish-speaking broadcasters usually identify by slogan (Radio Union, La Voz de Colombia, etc.) besides often mentioning city and country. With a little practice you'll have no trouble picking out these announcements. Incidentally, most of the French you hear on 60 meters will not be Haitian, but West African. ■

LISTENER'S TIME	0	0	0	0	1	1	1	2	2
	0	3	6	9	2	5	8	1	4
	0	0	0	0	0	0	0	0	0
	0	0	0	0	0	0	0	0	0
STATION AREA									
ASIA (except Near East)	← 31&25 → (49&41)		← 25&19 → (49&41)		19 (poor)	← 19 & 16 →		← 25 →	
EUROPE, NEAR EAST & AFRICA (N. of the Sahara)	← 49&41 →	31 (poor)	19	← 19 & 16 →		← 31&25 →		← 31 → (49)	
AFRICA (South of the Sahara)	← 31&60 →	nil	19 (poor)	← 19&16 → (25)		← 31 →		← 31&60 →	
SOUTH PACIFIC	← 31&25 →	49	31	← 25 → (poor)		← 19 → (16)		← 25 →	
LATIN AMERICA	← 49&60 →		49 (31&25)	← 25 → (19)		← 31 →		← 49&60 → (90)	

To use the table put your finger on the region you want to hear and log, move your finger to the right until it is under the local standard time you will be listening and lift your finger. Underneath your pointing digit will be the short-wave band or bands that will give the best DX results. The time in the above propagation prediction table is given in *standard time* at the listener's location which effectively compensates for differences in propagation characteristics between the east and west coasts of North America. However, Asia and the South Pacific stations will generally be received stronger in the West while Europe and Africa will be easy to tune on the east coast. The short-wave bands in brackets are given as poor second choices. Refer to White's Radio Log for World-Wide Short-Wave Broadcast Stations list.

electronic



by Jack Brayton


■ If you want to gather a crowd; be the hero of the block; put life into a dying party; or just want a fun-to-operate project then *Electronic Roulette* is designed especially for you. And besides this all-around fun aspect which, by the way, can be enjoyed by electronic enthusiasts and non-enthusiasts alike, it's also a good Science Fair project. Then—from another viewpoint—the serious experimenter should find dozens of applications for; and endless hours of experimentation in the somewhat unusual control circuits. This is especially true since three basic computer circuits are used to form a simple miniature “brain” which tells the unit exactly what to do and—when operated properly—selects numbers in a *random* fashion. The Electronic Roulette's brain actually *knows* whether or not a number on the panel is lit and in an instant decides what action to take. And, furthermore, the last command received is stored or remembered within the brain until the power is disconnected!

About The Circuit. As we've already mentioned, the Electronic Roulette is composed of three computer circuits. The complete schematic is given in Fig. 1. These circuits include a *clock*, a *flip flop* and a *coincidence* circuit. Next, let's take these circuits one at a time and see exactly what they do and how they do it.

The clock—as its name implies—generates *timing* pulses and makes sure that certain

You can gamble on this little gadget to liven up any gathering. Just plug it in, spread out the Roulette cloth and go for a Space-Age spin.

roulette

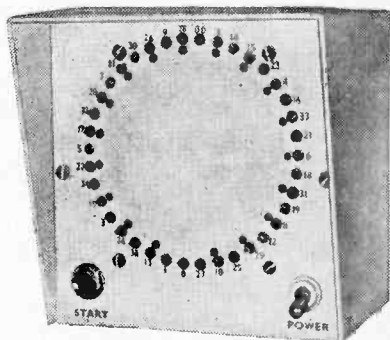

operations occur only at discrete (specific or individual) time intervals. In this instance, the pulses occur once every 2 or 3 seconds *as long as power is applied*. The exception is when the unit is first turned on, it then takes about 15 seconds for the first pulse to appear but after that they occur at shorter, regular intervals. These pulses *time* the specific instant when the motor shuts off and a number is selected. Numbers cannot be selected at any other time.

Clock pulses are generated by the circuit components Q1, R1, R2, R3, and C1. Q1 is a *unijunction* transistor and the entire circuit is a *unijunction relaxation oscillator*. And, if unijunctions are new to you, this needn't be a problem because they're simple to both use and understand.

The unijunction, of course, has 3 leads called *base-1*, *base-2*, and *emitter*. The characteristic which makes the unijunction useful is the *resistance* between *base-1* and *emitter*. It is very high until a certain, predetermined difference of potential exists across these leads. But—as soon as the difference of potential *exceeds* this level (and the emitter is positive with respect to base-1) the resistance between these leads becomes *very low*, causing a heavy current to flow.

The voltage at which the unijunction fires is called the *peak-point emitter voltage* and it's always a *fixed percentage* of the voltage which exists across the *base-1* and *base-2*

ELECTRONIC ROULETTE

leads. Now let's see how these principles are applied in the relaxation oscillator.

When power is applied to the relaxation oscillator, C1 starts to charge through R1. Initially, the emitter-to-base resistance of Q1 is very high because the voltage across C1 is not large enough to fire the unijunction. However, as soon as the charge on C1 has built up to the firing voltage (around 7 volts in this case) of Q1, the emitter-to-base resistance of Q1 becomes very low; a heavy current flows which partly discharges C1 and produces a pulse across R3.

After the emitter-to-base current falls below that which is required to hold the uni-

junction on; Q1 cuts off and C1 starts to charge again. Thus, the entire cycle is repeated and clock pulses are produced regularly at the base top of R3 until the power is turned off. The clock pulses are then coupled through D1 and C2 to the flip flop.

Flip Flop. Along with the relay (K1), the flip-flop circuit is used to control the motor and thus the homebrew rotary switch which turns the neon lamps on and off in sequence. The flip flop also stores the last command received for an indefinite period of time.

Although it may not look much like a flip flop, the components which make up this circuit are Q2, Q3, R4, R5, R6, R7, and K1 (rectifier D2 merely clamps the reverse voltages which develop across the relay coil when Q3 cuts off).

To eliminate some of the confusion which

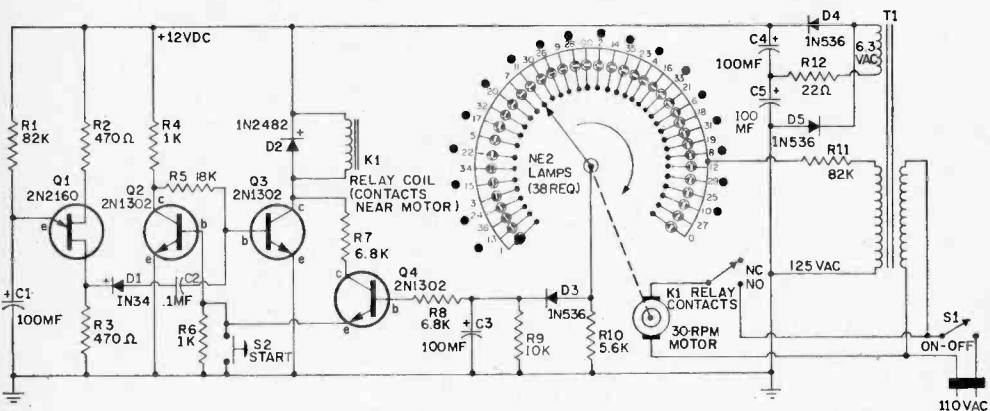


Fig. 1. Ring of neon lamps is shown as broken to make diagram easier to follow.

PARTS LIST FOR ELECTRONIC ROULETTE

- C1, C4, C5—100-mf., 12-volt electrolytic capacitor
- C2—1-mf., 25-volt (or higher rating) ceramic capacitor
- C3—10-mf., 25-volt electrolytic capacitor
- D1—General-purpose diode (1N34, 1N38, 1N56, 1N295—Lafayette 19R4901 or equiv.)
- D2—750-ma., 200-volt prv rectifier (1N2482, SK3016, 1N538 or equiv.)
- D3, D4, D5—750-ma., 50-volt prv (or higher) rectifier (1N536, SK3016, 1N440B or equiv.)
- I1-138—Neon Lamp (Type NE-2, NE-2E, NE-2H or equiv.)
- K1—S.p.d.t. 12-volt relay (Potter & Brumfield R55D or equiv.)
- MTR—30-rpm., 60 Hz (cps) motor (Cramer 117P Newark 55F393 or equiv.)
- Q1—Transistor, unijunction (2N2160 or equiv.)
- Q2, Q3, Q4—Transistor, npn, (2N1302, SK3011, 2N823, 2N556 or equiv.)
- R1, R11—82,000-ohm, 1/2-watt resistor
- R2, R3—470-ohm, 1/2-watt resistor
- R4, R6—1,000-ohm, 1/2-watt resistor

- R5—18,000-ohm, 1/2-watt resistor
- R7, R8—6,800-ohm, 1/2-watt resistor
- R9—10,000-ohm, 1/2-watt resistor
- R10—5,600-ohm, 1/2-watt resistor
- R12—22-ohm, 1/2-watt resistor
- S1—S.p.s.t. toggle switch
- S2—S.p.s.t. pushbutton
- T1—Power transformer, 117-volt pri; 125-volt, 15-ma and 6.3-volt, 600 ma sec. (Stancor PS-8415; Knight 61U410 or equiv.)
- 1—Cowl-type Minibox, 5 x 5 x 5-inches (Bud SC2133 or equiv.)
- 1—Copper-clad circuit board, unperforated 4 x 4-inch
- 1—Perforated circuit board, unclad, 3¹/₂ x 6³/₄-inches
- 1—plyboard, 1/2-inch, 4 x 4-inch
- Misc.—Linecord and plug, tie strip, spacers, machine screws, nuts, washers, circuit-board solder terminals, hook-up wire, solder, etc.

Estimated cost: \$30.00

Estimated construction time: 7 hours

might result from trying to study the flip flop and the other control circuits at the same time, we've drawn a simplified flip-flop circuit in Fig. 2. This way the circuit looks more like the ordinary flip flop—with the exception of switch S3 and capacitor C6. Assuming S3 is closed and S2 is open, let's see what happens when power is applied to the circuit.

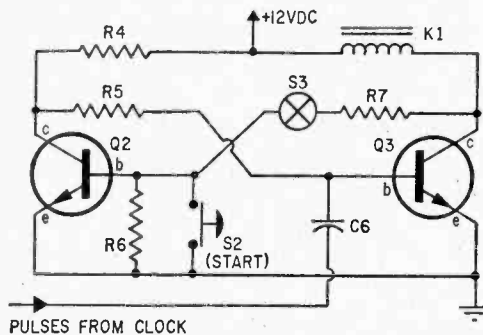


Fig. 2. Simplified diagram of Flip-flop makes it easier to understand circuitry. Callouts designations are identical with those in Fig. 1.

When power is first applied to the flip flop one of the transistors will saturate faster than the other. For the sake of this discussion we'll assume Q2 saturates faster than Q3. And, when Q2 becomes saturated its collector potential is at or near ground. This cuts off Q3 because its base current—coming through R5 and R4—has been removed (shorted to ground). Of course, since no collector current is flowing through Q3, very little current flows through relay K1. Its contacts remain *open*; and the motor is

switched off. At the same time, Q2's base is *forward biased* through K1's coil, R-7 and switch S3. Thus, this condition can be held until something causes either Q2 to *cutoff* or Q3 to *saturate*.

Momentarily closing S2 (the start switch) sends Q2 to cutoff because its base current is, at that time, shorted to ground. Then, with Q2 at cutoff and the higher Q2 collector potential which results, Q3 is forward biased through R5. This causes Q3 to saturate and removes the forward bias from Q2 *even with S2 open*. Naturally, when Q3 conducts, a heavy current flows through K-1 causing its contacts to close and the motor to run. The motor will continue to run until a *negative-going* pulse is received from the clock. The negative going pulse (produced when the unijunction goes to cutoff after firing) is coupled, through C6, to the base of Q3. This sends Q3 to cutoff and the flip flop returns to its *off* position. But—and this is most important—the equivalent flip flop cannot return to the *off* position if S3 is open or *off*. With its base circuit open it is impossible for Q2 to saturate. Of course, S3, as such, isn't really used in the actual unit. However, in the simplified flip flop it represents the third computer circuit used in the Electronic Roulette's brain.

Coincidence. This circuit is merely a transistor switch which keeps the motor running unless: clock pulse is received at the base of Q3.

The arm of the motor-driven switch is on a contact and a number is lit. If a clock pulse is received at the base of Q-3 and a number on the panel is not lit the motor

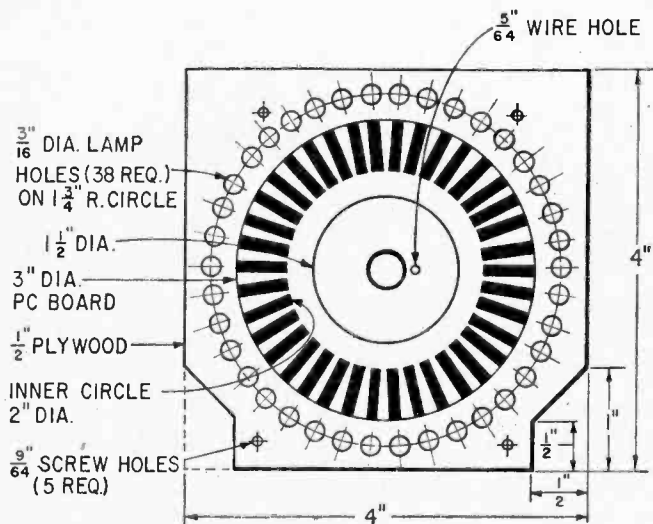


Fig. 3. Commutator is an ideal printed-circuit project which is almost impossible to manufacture as an assembled unit in a home workshop.

ELECTRONIC ROULETTE

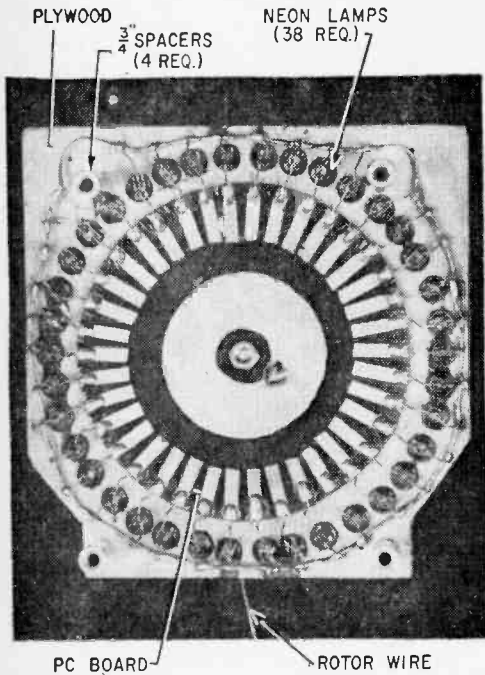


Fig. 4. View of commutator shows neon lamp connections. You could use a larger PC board and use copper-clad as a common.

relay will drop out but only for a fraction of a second. It then recloses and the unit automatically recycles. This prevents the motor-driven switch arm from stopping when a number is not lit and helps select numbers at random.

The circuit is made up of Q4, R6, R7 and R8 (R7 is used both in the flip flop and in the coincidence circuit).

Two things must occur *simultaneously* in order for this circuit to operate; and for Q4 to saturate. First, Q3 must be at cutoff—driven there by a clock pulse which causes Q3's collector potential to become positive 12 volts. Second, the base of Q4 must be *forward biased* through R8 which—as we'll show—means a number is lit on the panel. But to understand how this bias is developed we'll have to look at the lamp circuit.

The *neon* lamps used in this project need about 75 volts to fire them. The 125-VAC winding on T1 provides this high potential and *isolates* the unit from the power line. This eliminates the shock hazard which might

otherwise be present.

Looking at Fig. 1 we can see that the lamp circuit is a *series* circuit consisting of R11; one lamp (out of 38—depending on the motor-driven rotor's position) and R10. Naturally, a portion of the voltage is dropped across each component *whenever the motor's arm is on a contact* and a lamp is lit. Thus, a small AC voltage is across R10 whenever a lamp is lit. This voltage is rectified by D3; filtered by C3—providing forward bias (positive voltage) for Q4. Of course, there is no forward bias if the motor's arm is not on a contact.

When Q4 saturates current flows through R7, the emitter/collector junction of Q4, and the emitter/base junction of Q2. Some of this current also flows through R6 but most is bypassed by the base of Q2. This sets the flip flop to the *off* position and the motor shuts off and *stays* off until the start switch is once again pressed.

One question which comes up is: how do we obtain *random* number selection if stop pulses occur at *regular* intervals and the motor runs at a *constant* speed? The answer is: during an actual game there are varying lengths of time between plays and, since the timer is *always* running, there's no way of knowing how much time is left on the timer when the start button is pressed.

Of course, if the start button is pressed the instant the unit stops a pattern does emerge but even here you would have a hard time trying to pick the exact number it would stop on. Therefore, Electronic Roulette does give a good selection of numbers.

DC power (about 12 volts) for the transistors is supplied by the voltage doubler circuit shown (D4, D5, C4, C5) in Figure 1.

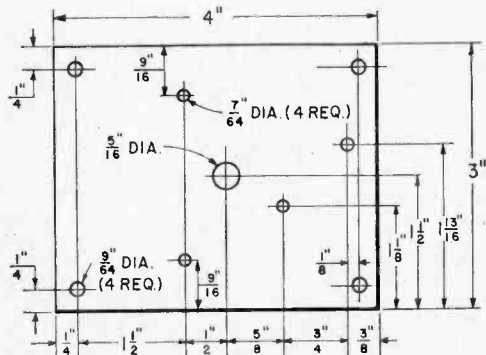


Fig. 5. Relay and motor are mounted on this insulating panel, which is mounted over the commutator board, as in Fig. 7.

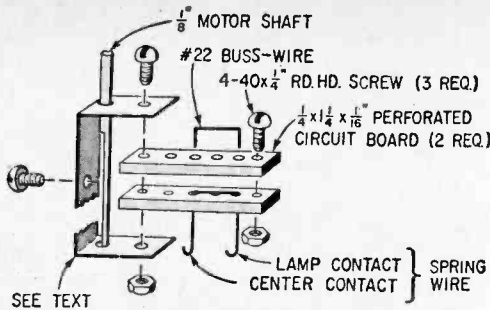


Fig. 6. Wiper arm of motor makes contact between center ring of commutator and the lamp contacts with spring-wire brushes.

R12 is a current limiting resistor that protects the diodes from current surges into C4 and C5 when the power switch is set to *on*.

Motor. All of the parts used in Electronic Roulette, except the motor, are widely available and can be obtained from any large supplier. The motor is available from Newark Electronics Corp., 223 West Madison St., Chicago, Ill. 60606 and can be ordered from them. Other motors with speeds from 30 to 60 rpm may be substituted.

Construction. The first step is laying out and drilling the panel. This is easy since we've given the lamp hole layout—along with the printed-circuit contact layout—roughly half size in Fig. 3. This template should be taped to the front panel; and the 3/16-inch lamp holes center-punched. The 1/2-inch thick block of plywood, used to mount the lamps and printed circuit contacts, should be fastened to the back of the panel (centered and the top placed flush with the cabinet top). Use four 6-32 x 3/4-inch screws at the corners as shown. Drill the 3/16-inch lamp holes in the cabinet and plywood at the same time. Also—on the side of the plywood which will be against the panel—the center hole should be enlarged at the top to 3/16-inch and to a depth of about 1/4-inch. This countersink is

for the center screw head which *does not* go through the panel. The switch-hole centers are 3/16-inch from each edge and up 3/4-inch from the bottom. Next, the *bottom front corner* flanges on the cover are cut back 1-inch in each direction to make room for the switches.

Lamp and Motor Assembly. Cut a piece of unpunched printed-circuit board (copper clad on one side only) to form a 3-inch circle. File the edges smooth and apply resist as shown in the layout (Fig. 3).

Although 1/8-inch tape resist is just right for the contacts a resist pen can also be used since layout isn't really critical. Check to make sure none of the contacts run into one another and that the copper foil in the center (around the hole) *hasn't* been covered with resist. Etch the board using a prepared solution.

When the board has been etched, washed and dried it can be attached to the plywood block using a 6-32 x 1/2-inch machine screw at the center as shown in Fig. 4.

Fig. 4 also shows how the lamps are mounted and wired. And, since the lamps are friction fitted, the holes may have to be reamed slightly if any of the lamps are too tight.

Form AWG-22 buss-wire around the *outside* as shown and—if metal spacers are used—be sure the buss-wire does not touch against the spacers. Slip a 3/4-inch piece of insulated tubing over the spacers to be certain. One wire of each lamp is soldered to the outside edge of a contact and the other is soldered to the buss-wire. Also a short length of wire should be soldered to the *center* contact and run through the hole provided.

Motor and Relay Mount. Board can be cut from any insulating material such as unclad circuit board, pressed board, phenolic, and etc. Its layout is shown in Fig. 5.

The motor-driven contact arm is much simpler to make than it might appear. Fig.

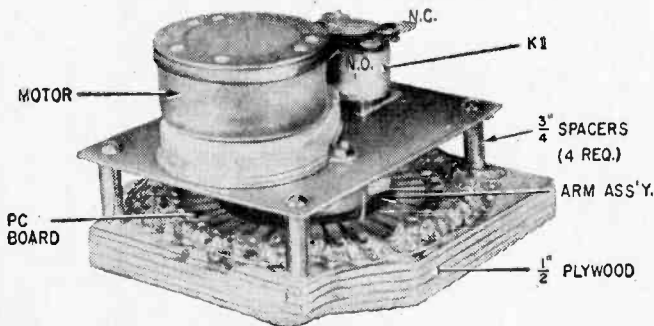


Fig. 7. Assembled drive unit shows motor, relay K1 and lamp commutator assembly. Proper alignment is very important.

ELECTRONIC ROULETTE

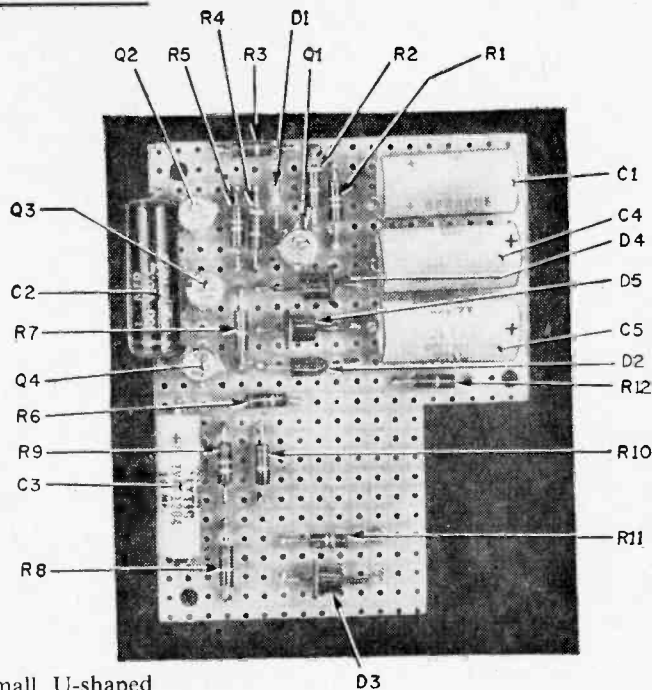


Fig. 8. Circuit-board layout shows most components used in the electronic circuitry that controls the motor-driven selector.

6 shows the details. The small U-shaped clamp is formed from $\frac{1}{4}$ -inch strip of aluminum. Holes are drilled after the clamp is bent—to be sure they're in line. The *inside* measurement of the U-shaped clamp is the same as the *thickness* of the circuit boards.

The 4-40 screw which locks the arm against the motor's shaft will *thread itself* into a $\frac{3}{32}$ -inch (or No. 41 drill) hole so no tap is necessary.

Wire for the contacts can be obtained by straightening a small spring. The bus-wire is used to fill the larger-than-needed holes in the circuit board so the contacts won't wobble.

After the contact arm has been built the motor and lamp assembly is temporarily put together as shown in Fig. 7 and the spring contacts are adjusted so they ride *evenly* around the contacts. Slight differences in contact pressure at different points on the board can be corrected by placing flat washers between the spacers and the motor board. After this, the lamp assembly can be installed in the cabinet with four 6-32 x $\frac{3}{4}$ -inch screws. Four flat washers should be placed *between the panel and the plywood* to prevent crushing the center contact wire (brought out at the bottom) and to allow room for the flange on the cover.

Most of the remaining parts are installed on a piece of perforated circuit board ($3\frac{1}{2} \times 4\frac{1}{8}$ -inch) which is laid out and notched as shown in Fig. 8. Wire it according to Fig. 2—it is then mounted on $\frac{1}{4}$ -inch spacers. Although not really necessary, it's somewhat safer to place a sheet of fish paper, or similar insulating material, between the circuit board and the cabinet to prevent shorts.

Placement of T1 and the 3-terminal tie strip, to which the line cord is attached, are not critical—watch connections. *Do not use the grounded center lug on the tie strip and be certain that the linecord junctions are thoroughly insulated from the chassis.*

Final wiring, and the panel numbers as well, are shown in Fig. 1. Also shown, and indicated by a black dot, are the numbers which should be black. The remaining numbers, except 00 and 0, are red. The zeros are green.

You need one more thing before you can begin the fun with your Electronic Roulette—a Roulette cloth. This is the playing board with all the numbers. Just spread it out on a convenient table, plug in the Electronic Roulette and give it a spin. ■

Volume 46, Part 2

WHITE'S RADIO LOG

An up-to-date Broadcasting Directory of North American AM, FM and TV Stations. Including a Special Section on World-Wide Short-Wave Stations

This is the second part of *White's Radio Log*, now published in three parts twice each year. This format permits the Editors of RADIO-TV EXPERIMENTER to offer its readers two complete volumes of *White's Radio Log* each year, while increasing the scope of the *Log* and inserting station changes as they occur.

In this issue of *White's Radio Log* we have included the following listings: U. S. AM Stations by Location, U. S. FM Stations by States, Canadian AM Stations by Location, Canadian FM Stations by Location, and the expanded, up-to-date World-Wide Short-Wave Section.

In the Dec./Jan. issue of RADIO-TV EXPERIMENTER, the *Log* will contain the following listings: U. S. AM Stations by Call

Letters, U. S. FM Stations by Call Letters, Canadian AM Stations by Call Letters, Canadian FM Stations by Call Letters, and the expanded World-Wide Short-Wave Section.

In the event you missed any part of the *Log* published earlier this year, you will have a complete copy of *White's Radio Log* by collecting any three consecutive issues of RADIO-TV EXPERIMENTER during 1966. The three consecutive issues comprise a complete volume of *White's Radio Log* that offers complete listings with last minute station change data that can not be offered in any other magazine or book. If you are a broadcast band DX'er, FM station logger, like to photograph distant TV test patterns, or tune the short-wave bands, you will find *White's Radio Log* an unbeatable reference.

QUICK REFERENCE INDEX

U.S. AM Stations by Location	102
U.S. FM Stations by States	111
Canadian AM Stations by Location	116
Canadian FM Stations by Location	117
World-Wide Shortwave Stations	117

Location	C.L.	Kc.	Location	C.L.	Kc.	Location	C.L.	Kc.	Location	C.L.	Kc.
Birmingham, Ala.	WNBF	1290	Bristol, Conn.	WBIS	1440	Carolina, P. R.	WVOZ	1400	Chicago, Ill.	KCHY	1530
	WAFI	1070	Bristol, Tenn.	WPOI	1490	Carrington, N. Dak.	KDAK	1600		KRAE	1480
	WYCE	1550		WCYE	600	Carrizze Springs, Tex.				KVVO	1370
	WCRT	1210	Bristol, Va.	WFHG	980		KBEN	1450		KEND	980
	WAQY	1220	Brockton, Mass.	WBET	1460	Carroll, Iowa	KCIM	1380		WAAF	950
	WELN	1320		WOKW	1410	Carrollton, Ala.	WRAG	590		WAIT	820
	WATV	900	Brockville, Ont.	CFJR	1450	Carrollton, Ga.	WLBB	1100		WBBM	780
	WGSN	610	Broken Bow, Nebr.	KCNI	1280	Carrollton, Mo.	KADL	1430		WCFL	1000
	WYDE	850	Bronson, Mo.	KBNM	1220	Carson City, Nev.	WBTL	1300		WCRF	1240
Bisbee, Ariz.	KSUN	1230	Brookfield, Conn.	WYB	940	Cartersville, Ga.	WKRV	1270		WEDC	1240
Bishop, Calif.	KIBS	1230	Brookfield, Mo.	KGHM	1470	Carthage, Ill.	WCAZ	990		WGN	720
Bishopville, S.C.	WAGS	1380	Brookhaven, Miss.	WCHJ	1470	Carthage, Mo.	KDMO	1490		WIND	560
Bismarck, N. Dak.	KFYR	550		WJMB	1340	Carthage, Miss.	WCEP	1480		WJSD	1160
	KBMR	1350	Brookings, Oreg.	KURJ	910	Carthage, Tenn.	WRKM	1350		WJLS	890
Bismarck-Mandan, N. Dak.	KBOM	1270	Brookings, S. Dak.	KBRK	1430	Carthage, Tex.	KGAS	1590		WMAQ	670
	KBMS	1270	Brookline, Mass.	WBOS	1600	Cartersville, Mo.	KCRV	1370		WMBI	1110
Black Mountain, N.C.	WBMS	1350	Brown, Fla.	WYJB	950	Casa Grande, Ariz.	KPIN	1260		WNUS	1390
	WFGW	1010	Brownfield, Tex.	KKUB	1300	Casey, Ill.	WKZI	800	Chicago Hgts., Ill.	WSBC	1240
Black River Falls, Wis.	WWIS	1260	Brownsville, Tenn.	WBHT	1520	Casper, Wyo.	KTIWO	1470		WMPP	1470
Blackfoot, Idaho	KBLI	890	Brownsville, Tex.	KBOR	1600		KATI	1400	Chickasha, Okla.	KWCO	1560
Blackshear, Ga.	WBSB	1350	Brownwood, Tex.	KBWD	1380	Cathedral City, Calif.	KVOC	1230	Chico, Calif.	KHSL	1290
Blackstone, Va.	WKLR	1440		KEAN	1240		KKYC	1340		KHSL	1000
Blackwell, Okla.	KLTR	1580	Brunswick, Ga.	WGTG	1440	Cayce, S.C.	WCAY	620	Chicopee, Mass.	WACE	730
Blaine, Wash.	KARI	550		WMOS	1450	Cayce, P.R.	WLEY	1080	Childress, Tex.	KCTX	1510
Blakely, Ga.	WBBK	1260		WYNR	790	Cedar City, Utah	KSUB	590	Chillicothe, Mo.	KCHI	1010
Blanding, Utah	KUTA	790	Brunswick, Maine	WCME	900	Cedar Falls, Iowa	KCFI	1250	Chillicothe, Ohio	WBEX	1490
Bloomington, Ill.	WJBC	1230	Bryan, Ohio	WBNO	1520	Cedar Rapids, Iowa	KCRG	1600		WCHI	1350
Bloomington, Ind.	WTTT	1370	Bryan, Tex.	KORA	1240		KLWV	1450	Chippewa Falls, Wis.	WBGC	1240
Bloomingsburg, Pa.	CNBR	930		WTAW	1150		WATP	600		WAXX	1150
	WHLM	550	Buckhannon, W. Va.	WBUC	1460		KVOC	1230	Christiansburg, Va.	WJJJ	1260
Blountstown, Fla.	WKMK	1370	Bucyrus, Ohio	WBCT	1360	Cedarhurst, Ga.	WGAA	1340	Christiansted, V.I.	WIVI	970
Blue Earth, Minn.	KBWE	1560	Buffalo, N.Y.	WBEN	930	Celina, Ohio	WCMS	1350	Church Hill, Tenn.	WMCH	1260
Bluefield, W. Va.	WHIS	1440		WYSL	1400	Center, Ala.	WEIS	990	Cicero, Ill.	WYUN	1450
	WKOY	1240		WEBR	970	Center, Tex.	KDET	930	Cincinnati, Ohio	WKCY	1590
Blythe, Calif.	KYOR	1450		WGR	550	Centerville, Ala.	WBIB	1590		WCPO	1230
Blytheville, Ark.	WEST	910		WKBW	1520	Centerville, Iowa	WBOG	1400		WKRC	550
Boaz, Ala.	WBSA	1300	Buffalo, Wyo.	WBOL	1120	Centerville, Miss.	WHON	1390		WLKW	700
Boca Raton, Fla.	WSBR	740	Buiford, Ga.	WDYX	1460	Centerville, Miss.	WLBS	1580		WSAI	1360
Bogalusa, La.	WKIC	1490	Burbank, Calif.	KBLA	1500	Centerville, Tenn.	WHLP	1570		WZIP	1050
	WBQX	920	Burley, Idaho	KBAR	1230	Centerville, Utah	KBBC	1000	Clanton, Ala.	WKLF	980
Boise, Idaho	KATN	1010	Burlington, Iowa	KBUR	1490	Central City, Ky.	WNES	1050	Clare, Mich.	WCLN	980
	KEOI	670		KYED	1150	Centralia, Ill.	WMTA	1380	Claremont, N.H.	WTSV	1230
	KEST	790	Burlington, N.C.	WBBS	920	Centralia & Chehalis, Wash.	WCHS	1210	Claremore, Okla.	KWPR	1270
	KGEM	1140		WBAG	1150		KELA	1470	Claremont, Pa.	WWCH	1300
	KIDO	630		WDOT	1400	Centreville, Ala.	WBIB	1110	Clarksburg, W. Va.	WBQY	1400
	KYME	740	Burlington, Vt.	WJOY	1230		KVOC	1230		WHAR	1340
	KBLR	1550		WVMT	620	Ceres, Calif.	KLOC	920	Clarksdale, Miss.	WPDZ	750
Bolivar, Mo.	WBOL	1560	Burnett, Tex.	WTSL	1340	Chadburn, N.C.	WVUE	1590		WDL	1600
Bolivar, Tenn.	KFYN	1420	Burns, Oreg.	KRNS	1230	Chadron, Nebr.	KCSR	610	Clarksville, Ark.	KLYR	1360
Bonham, Tex.	KFTQ	1250	Butler, Ala.	WPRN	1220	Chambersburg, Pa.	WCHG	800	Clarksville, Tenn.	WJZM	1400
Boone, Iowa	KFBG	1590	Butler, Mo.	KMAM	1530		WCHG	800		WDXN	540
	WATA	1450	Butler, Pa.	WYSR	680	Champaign, Ill.	WDWS	1400	Clarksville, Tex.	KCAR	1350
Boone, N.C.	WBNL	1540	Butte, Mont.	KBOW	550	Chanute, Kans.	KCRB	1460	Claxton, Ga.	WCMA	1470
Boonville, Ind.	KWRT	1370		KXLF	1370	Chapel Hill, N.C.	WCHE	1360	Claxton, Ga.	WGH	1450
Boonville, Mo.	WBIP	1400	Cabin, John, Potomac, Md.	WXLN	950	Charleroi, Pa.	WESA	940	Clayton, Mo.	KXLW	1370
Boonville, Miss.	WBRV	900	Cadillac, Mich.	WATL	1240	Charles City, Iowa	KCHA	1580		KFUO	850
Boonville, N.Y.	KHUZ	1490	Caiz, Ky.	WKDZ	1110	Charleston, Ill.	WEIC	1270	Clayton, N. Mex.	KLXK	1450
Borger, Tex.	KHBB	1600	Caguas, P.R.	WNEL	1430	Charleston, Mo.	KCHR	1350	Clearfield, Pa.	WCPC	900
	WBZ	1030	Cairo, Ga.	WVJP	1110	Charleston, S.C.	WCKE	1390	Clearwater, Fla.	WTAN	840
Boston, Mass.	WCOP	1150	Cairo, Ill.	WGRA	790		WOKI	1340		WAZE	800
	WILD	1080	Cairo, Mo.	WKRO	1490	Charleston, W. Va.	WCWA	680	Cleburne, Tex.	KCLE	1120
	WNAC	680	Cadala, Maine	WKDQ	1250		WCBS	580	Clermont, Fla.	WVSL	1340
	WEZE	1280	Caldwell, Idaho	KCID	1480	Chattanooga, Tenn.	WCBS	1490	Cleveland, Ga.	WRWH	1350
	WEEI	590	Calera, Ala.	KBGN	910		WCKV	1490	Cleveland, Miss.	WCLE	1490
	WHDH	850	Calera, Ala.	WBGE	1370	Charlotte, Mich.	WKAZ	950	Cleveland, Ohio	WDSK	1410
	WMEX	1510	Calfeux, Calif.	KICO	1490	Charlotte, N.C.	WVVA	1550		WKYC	1100
	WORL	950	Callhoun, Ga.	KGCA	900		WVVA	1550		WDC	1280
Boulder, Colo.	KBDL	1490	Camas, Wash.	KVAN	1430	Charlotte, N.C.	WBFI	1100		WERE	300
	KDEY	1360	Cambridge, Md.	WCEN	1240		WVVA	1550		WGAR	1220
Bowie, Tex.	KBAN	1410	Cambridge, Mass.	WYHR	740	Charlotte, N.C.	WAYS	610		WHK	1420
Bowling Green, Ky.	WKCT	930	Cambridge, Ohio	WILE	1270		WVVA	1550		WABQ	1540
	WBGH	1340	Camden, Ark.	KAMD	910		WKIC	1310		WJW	850
	WLBJ	1410		KJWH	1450		WSOC	930	Cleveland, Tenn.	WBAC	1340
Bowl, Green, Ohio	WMGS	730	Camden, N.J.	WCAM	1310		WST	1240		WCLF	1570
Boynton Beach, Fla.	WZZZ	1510		WKDN	800	Charlotte Amalie, V.I.	WBNB	1000	Cleveland, Tex.	KVLB	1410
	KXXX	1450	Camden, S.C.	WACA	1590		WBST	1340	Cleve. Hgts., Ohio	WJMO	1490
	KBMN	1230	Camden, Tenn.	WFWL	1220		WVOC	1480	Clewiston, Fla.	WOWY	1590
Bradbury Hgts., Md.	WPCC	1580	Cameron, Tex.	KMIL	1330	Charlotte Amalie, V.I.	WBNB	1000	Clifton, Ariz.	KCLF	1400
Braddock, Pa.	WLOA	1550	Camilla, Ga.	WCLB	1220		WBST	1340	Clifton Forge, Va.	WCFV	1250
Braddocks Heights, Md.	WMHI	1370	Campbell, Ohio	WHOT	1330	Charlottesville, Va.	WBTV	1280	Clinch, Va.	WDIC	1430
	WTRL	1490	Campbellsville, Ky.	WTCC	1450		WVNA	1070	Clinch, Ill.	WHOW	1520
Bradenton, Fla.	WBRO	1420	Cannandaigua, N.Y.	WCCR	1550		WVNA	1070	Clinch, Iowa	KCLN	1390
Bradford, Pa.	WESB	1490	Canon City, Colo.	KRDL	1400	Chase City, Va.	WMEI	980	Clinton, Mo.	KRDL	1280
Brady, Tex.	KNEL	1490	Canonsville, Pa.	WROD	540	Chattahoochee, Fla.	WVNA	1070	Clinton, N.C.	WRZR	880
Braintree, Minn.	KLIZ	1380	Canton, Ga.	WCHK	1290		WVNA	1070	Clinton, Okla.	KRDE	1320
	KYBR	1340	Canton, Ill.	WBYS	1560		WVNA	1070	Clinton, S.C.	WPCC	1410
Brantford, Ont.	KBHM	1220	Canton, Miss.	WMGO	1370	Chattanooga, Tenn.	WMOG	1450	Clinton, Tenn.	WYSH	1380
Brattleboro, Vt.	WWSA	1450	Canton, N.C.	WWIT	970		WVNA	1070	Cloquet, Minn.	WKLK	1230
	WKVT	1490	Canton, Ohio	WCNS	900		WDEF	1370	Clovis, N. Mex.	WKLC	1240
Brawley, Calif.	KROP	1300		WHF	1000		WDDO	1310		KICA	980
Brazil, Ind.	WVCM	1380		WHBC	1480	Chattanooga, Tenn.	WDXB	1490	Coachella, Calif.	KCHV	970
	KBMW	1450		WINW	1520		WN00	1260	Coalinga, Calif.	KCHX	1470
Breckenridge, Minn.	KSTB	1430	Canyon, Tex.	KCAN	1550	Cheboygan, Mich.	WCBY	1240	Coatsville, Pa.	WC0J	1420
	WCCB	1430	Cape Girardeau, Mo.	KFYV	960		WNIA	1230	Coatesville, Pa.	WC0J	1420
Bremen, Ga.	KBRO	1490		KZYA	1220		WVNA	1070	Cocoa, Fla.	WVMG	1440
Bremerton, Wash.	KBRO	1490		KGMO	1350		WVNA	1070		WKKD	860
Brenham, Tex.	KWHI	1280	Carbondale, Ill.	WCIL	1020		WVNA	1070		WEZY	1350
Brevard, N.C.	WPNF	1240	Carbondale, Pa.	WCDB	1440	Chelan, Wash.	KOZI	1220		WWBC	1510
Brewster, N.Y.	WBRW	1510	Caribou, Maine	WFST	600	Cheraw, S.C.	WCRE	1420	Cocoa Beach, Fla.	WRCT	1300
Brewton, Ala.	WEPJ	1240	Carlisle, Pa.	WHYL	960	Cherryville, N. C.	WCSL	1590	Cocoa, Wyo.	KRCK	1400
Bridgeport, Ala.	WBTS	1480		WIOO	1000	Cherryville, N. C.	WCSL	1590	Coeur d'Alene, Ida.	KVNI	1240
Bridgeport, Conn.	WICC	600	Carlsbad, N. Mex.	KAVE	1240	Cherryville, N. C.	WCSL	1590	Coffeyville, Kans.	KGFF	690
	WNAB	1450		KCCC	930	Chesapeake, Va.	WSTJ	1600	Colby, Kans.	KXXX	790
Bridgeton, N.J.	WSNJ	1240		KPBM	740	Chesapeake, Va.	KSMG	980	Coldwater, Mich.	WTVB	1590
Brigham City, Utah	KBUH	800	Carmel, Calif.	KPBM	740	Chester, Pa.	WEEZ	1590	Coleman, Tex.	KSTA	1000
Brighton, Colo.	KBRN	800	Carmi, Ill.	WR0Y	1460	Chester, S.C.	WGCD	1490	Columbia, Pa.	KCLX	1450
Brinkley, Ark.	KBRI	1570	Carnegie, Pa.	WZUM	1590	Chester, Va.	WKI1	1410	Columbia Park, Ga.	WAPL	1570
			Caro, Mich.	WKYO	1360	Chestertown, Md.	WCTR	1530	Collierville		

WHITE'S RADIO LOG

Location	C.L.	Kc.
Colorado City, Tex.	KVMC	1320
Colo. Sprngs., Colo.	KRDO	1240
	KPTK	1580
	KWOR	1390
	KSSS	740
	KYSN	1460
	KRYT	1530
Columbia, Ky.	WAIN	1270
Columbia, Miss.	WCJU	1450
Columbia, Mo.	KFRU	1400
	KCGM	1580
	WCQY	1580
Columbia, Pa.	WCOS	1400
Columbia, S.C.	WIS	560
	WOIC	1320
	WNOK	1230
	WQXL	1470
Columbia, Tenn.	WICP	1280
	WKRP	1340
Columbus, Ga.	WDAK	540
	WRBL	1240
	WHYD	1270
	WCLS	1580
	WOKS	1340
Columbus, Ind.	WCSI	1610
Columbus, Miss.	WQOY	1580
	WCBI	550
Columbus, Nebr.	KJSK	900
	KTTT	1510
Columbus, Ohio	WBNS	1460
	WCOL	1230
	WISN	920
	WOSU	1240
	WTYN	610
	WVKO	1580
Colville, Wash.	KCVL	1270
Comanche, Tex.	KCOM	1550
Commerce, Ga.	WJJC	1270
Concord, Calif.	KWUN	1450
Concord, N.H.	WUNH	1450
Concord, N.C.	WEGO	1410
Concordia, Kans.	KCKC	1390
Connecticut, Ohio	WWOW	1360
Connellsville, Pa.	WCVI	1340
Connersville, Ind.	WCNB	1580
Conroe, Tex.	KMCO	900
Conway, Ark.	WCOB	1390
	KVEE	1330
Conway, N.H.	WBNC	1050
Conway, S.C.	WLAT	1330
Coonville, Tenn.	WHUB	1400
	WPTN	1550
Coolidge, Ariz.	KCKY	1150
Cook's Bay, Dreg.	KBOO	1230
	KYNG	1420
Copper Hill, Tenn.	WLSB	1400
Coville, Oreg.	KWRO	630
Coral Gables, Fla.	WRIZ	1550
	WYCG	1080
	WCTT	1260
Corbin, Ky.	WVGO	1330
Cordela, Ga.	WMJM	1490
Cordova, Alaska	KLAM	1450
Corinth, Miss.	WCMA	1280
	WKCU	1350
Cornelia, Ga.	WCOD	1450
Corning, Ark.	KTCB	1260
Corning, N.Y.	WCBA	1350
Corona, Cal.	WCLI	1450
Corpus Christi, Tex.	KREL	1370
	KCTA	1030
	KCOT	1150
	KEYS	1440
Covington, Ky.	KVTV	1320
	KSIX	1230
	KUNO	1400
Corry, Pa.	WOTR	1370
Corsicana, Tex.	KAND	1340
Cortez, Colo.	KWFC	740
Cortland, N.Y.	WKRT	920
	KWYD	1240
	KLOO	1350
Corvallis, Oreg.	KLOO	1340
Corydon, Ind.	WPDF	1550
Coshocton, Ohio	WTNS	1560
Cottage Grove, Oreg.	KNND	1400
Cottonwood, Ariz.	KVIO	1320
Coudersport, Pa.	WFRM	600
Council Bluffs, Iowa	KFNZ	920
	KRCB	1360
	KCFP	1430
Courtney, B.C.	WQFS	1440
Covington, Ga.	KVTV	1320
Covington, La.	WARR	730
Covington, Tenn.	WKBL	1250
Covington, Va.	WKYE	1340

Location	C.L.	Kc.
Cowan, Tenn.	WZYX	1440
Cozad, Neb.	KANI	1580
Crain, Colo.	KRAI	550
Crane, Tex.	KCRR	1380
	KBSN	970
Crawfordsville, Ind.	WCVL	1550
Crescent City, Calif.	KPLY	1240
	KPOD	1310
Creston, Iowa	KSTB	1430
Crestview, Fla.	WCNU	1010
	WJSB	1050
Crewe, Va.	WVSV	800
Crockett, Tex.	KIVY	1290
Crookston, Minn.	KROX	1260
Crossett, Ark.	KAGH	800
Crossville, Tenn.	WATW	930
Crowley, La.	KSIG	1430
Crystal Lake, Ill.	WCLR	850
Cuero, Tex.	KCFH	1600
Cullman, Ala.	WFMH	1460
	WKUL	1340
Culpeper, Va.	WCVA	1490
Cumberland, Ky.	WCPM	1280
Cumberland, Md.	WCUM	1230
	WTBO	1450
Cummings, Ga.	WSNE	1410
Cushing, Okla.	KUSH	1600
Cuyahoga Falls, Ohio	WCUE	1150
Cypress Gardens, Fla.	KCTO	540
Cynthiana, Ky.	WCYN	1400
Dade City, Fla.	WDFC	1350
Dadeville, Ala.	WDVC	910
Dainierfield, Tex.	KEGG	1560
Dalhath, Tex.	KXIT	1410
Dallas, N.C.	WAAK	960
Dallas, Oreg.	KRLD	1480
Dallas, Tex.	KRLD	1080
	KIXL	1040
	KSKY	660
	KLIF	1190
	WFAA	570
	WFAX	820
	KWAB	480
	WRR	1310
Dalton, Ga.	WBLJ	1230
	WRCD	1430
	WTTI	1530
Danbury, Conn.	WLAD	800
Danville, Ill.	WDAN	1430
	WITV	980
Danville, Ky.	WHIR	1310
Danville, Pa.	WFGM	1570
Danville, Va.	WBTM	1330
	WYPR	920
	WDVA	1250
	WILA	1580
Dardanelle, Ark.	KCAK	980
Darlington, S.C.	WDAR	1350
Davenport, Iowa	WDC	1420
	KWNT	1580
	KSTT	1170
Dawson, Ga.	WDWD	990
Dayton, Ohio	WHIO	1290
	KWB	1410
	WONE	980
	WAVI	1210
	WDNT	1280
Dayton, Tenn.	WDBB	1150
Daytona Beach, Fla.	WMPJ	1450
	WRDD	1340
	KDSJ	980
Deadwood, S.Dak.	WKNR	1310
Dearborn, Mich.	WHOS	800
Decatur, Ala.	WAIF	1490
	WNSL	1400
Decatur-Atlanta, Ga.	KGUN	1010
	WDMN	1310
Decatur, Ill.	WDZ	1050
	WSDY	1340
Decatur, Ind.	WADM	1540
Decatur, Iowa	KDEC	1240
	KWLC	1240
Deer Lodge, Mont.	WDFC	1340
Deerfield, Va.	WABH	1150
Defiance, Ohio	WONW	1280
De Funiak Springs, Fla.	WSP	1280
	WZEP	1460
De Kalb, Ill.	WLKB	1360
De Land, Fla.	WDDO	1310
	WOOO	1310
Delano, Calif.	KCHJ	1010
Delaware, Ohio	WDLE	1550
Delray, Beh., Fla.	WDBF	1420
Del Rio, Tex.	KDLK	1230
Delta, Colo.	KDTA	1400
Deming, N.Mex.	WJFS	1230
Demopolis, Ala.	WXAL	1400
Denham Sprngs., La.	WLBI	1220
Denison, Iowa	KDSN	1580
Denison-Sherman, Tex.	KDSX	950
Denmark-Bamburg, S.C.	WDC	1240
Denton, Tex.	WDNT	790
Denver, Colo.	KDEN	1340
	KFML	1390
	KHOW	630

Location	C.L.	Kc.
Denver City, Tex.	KCAL	1280
De Queen, Ark.	KDAR	1590
De Ridder, La.	KDLA	1010
Des Moines, Iowa	KCBC	1390
	KIOA	940
	KRNT	1350
	KSO	1460
	KWJY	1150
	WHO	1040
Detroit, Mich.	WJBK	1500
	WJLB	1400
	WJR	760
	WJW	950
	WXYZ	1270
Detroit Lakes, Minn.	KDLM	1340
Devils Lake, N.Dak.	KDLR	1240
	KDEX	1590
Dexter, Mo.	KSPF	1260
Diboll, Tex.	KDIX	1230
Dickinson, N.Dak.	WDRN	1260
Dickson, Tenn.	WDR	1130
Dillon, Mont.	KDBM	800
Dillon, S.C.	WDSG	800
Dimmitt, Tex.	KDHN	1470
Dimuba, Calif.	KRDU	1130
Dixon, Ill.	WIXN	1460
Dodge City, Kans.	KGNO	1370
	WDR	1550
Donaldsonville, Ga.	WSEM	1500
Doniphan, Mo.	KDFN	1500
Dothan, Ala.	WAGF	1320
	WDIG	1450
	WOOF	560
Douglas, Ariz.	KAWT	1450
	WYAN	1330
Douglas, Ga.	WDMG	860
	WMOA	1310
Douglas, Wyo.	KWIV	1050
Douglasville, Ga.	WDGL	1520
Dover, Del.	WDOV	1410
	WKEN	1600
Dover, N.J.	WJAN	1510
Dover, N.H.	WTSN	1270
Dover, Ohio	WJER	1450
Dowagiac, Mich.	WDOW	1440
Doylestown, Pa.	WBUX	1570
Dublin, Ga.	WMLT	1330
	WILT	1230
Du Bois, Pa.	WGE	1420
Dubuque, Iowa	KWBH	1370
	WDBQ	1490
Duluth, Minn.	KDAL	610
	WBCB	560
	KAOH	1390
Dumas, Ark.	KDDA	1560
Dumas, Tex.	KDDD	800
Duncan, Okla.	WDR	1410
Dundee, N.Y.	WHR	1570
Dunkirk, N.Y.	WDOE	1140
Dunn, N.C.	WCKB	780
Du Quoin, Ill.	WDQN	1580
Durango, Colo.	KIUP	950
	KDGO	1240
Durant, Okla.	WFS	1270
Durham, N.C.	WDNC	620
	WSRC	1410
	WSSB	1490
	WTIK	1310
Dyersburg, Tenn.	WDSG	1450
	WTRD	1330
Eagle Pass, Tex.	KEPS	1270
Eagle River, Wis.	WERL	950
Easley, S.C.	WELP	1360
E. Grand Forks, Minn.	KRAD	1590
Eastland, Tex.	KERC	1590
E. Lansing, Mich.	WKAR	870
E. Liverpool, Ohio	WOHI	1490
East Longmeadow, Mass.	WTYM	1600
Eastman, Ga.	WUFF	710
E. Moline, Ill.	WMLN	960
E. Point, Ga.	WTJH	1260
East Prairie, Mo.	KGCL	1080
E. Syracuse, N.Y.	WEMD	1460
Easton, Md.	WEXE	1230
Easton, Pa.	WEST	1400
Eatontown, N.J.	WHTG	1410
Eau Claire, Wis.	WEAQ	790
	WBIZ	1480
	WED	1050
Eau Gallie, Fla.	WMEG	920
Edenburg, Pa.	WEND	1580
Edenton, N.C.	WCDJ	1260
Edinburg, Tex.	KURY	710
Edmonds, Wash.	KGDN	630
Edinburg, Mich.	WGRG	1090
Elba, Ala.	WELB	1340
Elberton, Ga.	WSGC	1400
El Cajon, Calif.	KDEO	910
El Campo, Tex.	KULP	1390

Location	C.L.	Kc.
El Centro, Calif.	KXO	1230
	KRM	1480
El Dorado, Ark.	KDMS	1290
	KELD	1460
Eldorado, Kans.	KBTO	850
Eldorado Springs, Mo.	KESM	1580
Eleele, Kanai, Hawaii	KUAI	720
Elgin, Ill.	WRMN	1410
Elizabeth City, N.C.	WCNC	1240
	WGAI	560
Elizabethton, Tenn.	WBEJ	1240
	WIDD	1520
Elizabethtown, Ky.	WIEL	1400
Elizabethtown, N.C.	WBLA	1440
Elizabethtown, Pa.	WHRY	1400
Elk City, Okla.	KBEK	1240
Elkhart, Ind.	WTRC	1340
	WCMR	1250
	WCFM	1540
Elkins, N.C.	WONE	1240
Elkins, W.Va.	KELK	1240
Elkton, Md.	WSEK	1550
Ellensburg, Wash.	IXLE	1240
Ellenville, N.Y.	WELV	1370
Ellsworth, Me.	WDEA	1370
Elmira, N.Y.	WELM	1410
	WENY	1230
Elmira Heights-Horseheads, N.Y.	WEHH	1590
El Paso, Tex.	KROD	600
	KELP	920
	KHEY	690
	KINT	1590
	KITZ	1030
	KSET	1340
	KTSM	1380
El Reno, Okla.	KELR	1460
Ely, Minn.	WELY	1450
Ely, Nev.	KELY	1450
Elvira, Ohio	WEOL	930
Eminence, Ky.	WEM	800
Emporia, Kans.	KVOE	1400
Emporia, Va.	WEVA	860
Emporium, Pa.	WLEM	1250
Endicott, N.Y.	WENE	1430
Englewood, Colo.	KGMC	1150
Englewood, Fla.	WENG	1530
Enid, Okla.	KERC	1390
	KGWA	960
Enterprise, Ala.	WIRB	600
Enterprise, Oreg.	KWVR	1340
Ephrata, Pa.	WGSA	1310
Ephrata, Wash.	KULF	730
Erie, Pa.	WWTN	1260
	WVET	1370
	WIET	1400
	WWGO	1450
Erwin, Tenn.	WEMB	1420
Escanaba, Mich.	WDDB	680
	WLST	600
Eseondido, Calif.	KOWN	1450
Esplanade, N.H.	WES	1340
Etowah, Tenn.	WCPH	1220
Eufaula, Ala.	WULA	1240
Eugene, Oreg.	KORE	1450
	KPIR	1500
	KASH	1600
	KATR	1320
	KENG	1280
	KUGS	590
	KWFS	1540
Eunice, La.	KEUN	1490
Eureka, Calif.	KINS	980
	KDAN	790
Eustis, Fla.	WLCO	1240
Evansville, Ill.	WEAW	1330
	WNMP	990
Evansville, Wyo.	KEVA	1240
Evansville, Ind.	WROZ	1400
	WGBF	1280
	WKY	820
	WJPS	1330
Everett, Minn.	WEVE	1340
Everett, Pa.	WED	1350
Everett, Wash.	KRKO	1380
	KWYZ	1230
Evergreen, Ala.	WBLO	1470
Exeter, N.H.	WKXR	1540
Fairbanks, Alaska	KFRB	660
Fairburn, Minn.	KFRB	900
Fairbury, Nebr.	KGMT	1310
Fairfax, Va.	WELI	1310
Fairfield, Ill.	WFII	1390
Fairfield, Iowa	KMCD	1570
Fairhope, Ala.	WABF	1220
Fairmont, Minn.	KSUM	1370
Fairmont, N.C.	WFM	1050
Fairmont, W.Va.	WMMN	920
	WTCS	1490
Fairway, Kan.	KUDL	1380
Falardo, P.R.	WMDD	1480
Fallurillas, Tex.	KPSO	1260
Fall River, Mass.	WALE	1400
Fall River, N.Y.	WVLR	1380
	KVLY	980
Falls Church, Va.	WAFX	1220
Falls City, Nebr.	KTNC	1230

Location	C.L.	Kc.	Location	C.L.	Kc.	Location	C.L.	Kc.	Location	C.L.	Kc.			
Fargo, N. Dak.	WDAV	970	Franklin, N.C.	WFSC	1050	WGBR	1150	Hamilton, Mont.	KYLQ	980	Hamilton, Ohio	WMOH	1450	
	KFGO	790	Franklin, N.H.	WFTN	1240	WGOL	1300		WMOH	980		WMOH	1450	
	KFNW	900	Franklin, Pa.	WFRA	1450	KCTI	1450		WMOH	980		WMOH	1450	
	KQWB	1550	Franklin, Tenn.	WAGG	950	KLDE	750		WMOH	980		WMOH	1450	
Faribault, Minn.	KDHL	920	Franklin, Va.	WYSR	1250	Goshen, Ind.	WKAM	480	Hamilton, Tex.	KCLW	920	Hamilton, N.C.	KCLW	920
Farmersville, La.	WFDL	970	Frederick, Md.	WYFR	950	Gouverneur, N.Y.	WIGS	1230	Hamlet, N.C.	WJBT	1460	Hammond, Ind.	WJOB	1230
Farmington, Mo.	WKTJ	1380	Frederick, Okla.	KTAT	1570	Grafton, N.D.	KGPC	1340	Hammond, La.	WFFR	1400	Hammond, Ind.	WJOB	1230
Farmington, Mo.	KREI	800	Fredericksburg, Tex.			Grafton, W.Va.	WVWV	1260	Hammond, N.J.	WNJH	1580	Hammond, Ind.	WJOB	1230
Farmington, N.M.	KREI	1390				Graham, Tex.	KSWA	1330	Hampton, S.C.	WBHC	1270	Hammond, Ind.	WJOB	1230
	KWYK	960				Grand Coulee, Wash.	KFDR	1360	Hampton, Va.	WVEC	1490	Hammond, Ind.	WJOB	1230
	KRZE	1280				Grand Forks, N.D.	KFJM	1370	Hancock, Mich.	WMPF	920	Hammond, Ind.	WJOB	1230
Farmville, N.C.	WFAG	1250				KILO	1440	Hanford, Calif.	KHMO	1070	Hammond, Ind.	WJOB	1230	
Farmville, Va.	WFLO	870				KXLD	1310	Hanover, N.H.	WTSJ	1400	Hammond, Ind.	WJOB	1230	
Farrell, Pa.	WFAD	1470						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Farwell, Tex.	KZOL	1570						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Fayette, Ala.	WVWF	990						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Fayetteville, Ark.	KHOG	1440						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	KFAY	1250						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Fayetteville, N.C.	WFAY	1230						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WFNC	940						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WFLB	1000						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WIDU	1600						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Fayetteville, Tenn.	WEKR	1240						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Fergus Falls, Minn.	KOTE	1250						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Fernandine Beach, Fla.	WVBF	1570						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Ferriday, La.	KJCF	1400						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Festus, Mo.	KJCF	1400						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Festus-St. Louis, Mo.	KXEN	1010						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Findlay, Ohio	WFIN	1830						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Fisher, W.Va.	WELD	690						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Fitchburg, Mass.	WFIM	1280						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Fitzgerald, Ga.	WBHB	1240						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Flagstaff, Ariz.	KCLS	600						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	KIKJ	1400						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	KEOS	690						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Flat River, Mo.	KFMD	1240						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Flint, Mich.	WFDL	920						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WTRX	910						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WAMM	1420						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WMRP	1570						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WKMF	1470						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WTAC	600						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WTCB	990						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Flomaton, Ala.	WJOI	1340						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Florence, Ala.	WOWL	1240						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WJMX	970						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Florence, S.C.	WOLS	1230						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WYNN	540						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Floydada, Tex.	KFLD	900						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Foley, Ala.	WHEP	1310						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Fond du Lac, Wis.	KFJZ	1450						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Fordyce, Ark.	KBJT	1570						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Forest, Miss.	WMAE	890						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Forest City, N.C.	WBBO	780						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WAGY	1320						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Forest Grove, Ore.	KWAY	1570						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Forrest City, Ark.	KXJK	950						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Ft. Atkinson, Wis.	WFAP	1400						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Ft. Bragg, Calif.	KDAC	1280						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Ft. Campbell, Ky.	WABD	1370						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Ft. Collins, Colo.	KCOL	1410						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	KXJZ	600						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Ft. Dodge, Iowa	KVFD	1400						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	KWMT	540						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Ft. Knox, Ky.	WSAC	1470						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Ft. Lauderdale, Fla.	WFTL	1400						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WVFL	1580						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Ft. Madison, Iowa	KXGI	1360						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Ft. Morgan, Colo.	KFTM	1400						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Ft. Myers, Fla.	WINK	1240						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WMYR	1410						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WCAI	1350						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Ft. Payne, Ala.	WFWA	1400						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WZOB	1250						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Ft. Pierce, Fla.	WARN	1330						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WIRA	1400						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Ft. Scott, Kans.	KMDO	1600						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Ft. Smith, Ark.	KFPW	1230						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	KFSA	950						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	KFTS	1410						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	KWHN	1320						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Ft. Stockton, Tex.	KFTS	860						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Ft. Valley, Ga.	WVPM	1150						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Ft. Walton Beach, Fla.	WNUE	1400						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WFTW	1260						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WGL	1250						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Ft. Wayne, Ind.	WOWO	1190						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WLYV	1450						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WKJG	1380						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Ft. Worth, Tex.	KJIM	870						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	KGUL	1540						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	KFJZ	1270						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	KNOK	970						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WBAP	820						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	KXOL	1360						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Fostoria, Ohio	WFOB	1430						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Fountain City, Tenn.	WGUY	1430						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
	WFOL	1450						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Fountain Inn, S.C.	WFIS	1600						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Fowler, Calif.	KLIP	1220						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Framingham, Mass.	WKOX	1190						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Frankfort, Ind.	WILQ	1570						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Frankfort, Ky.	WFYK	1490						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Franklin, Ky.	WFKN	1220						Hanover, Pa.	WHVR	1280	Hammond, Ind.	WJOB	1230	
Franklin, La.	KFRA	1390						Hanover, Pa.	WHVR	1280				

WHITE'S RADIO LOG

Location	C.L.	Kc.
Holland, Mich.	WHTC	1450
	WHYI	1280
Hollister, Cal.	KMPG	1520
Hollywood, Fla.	WGMA	1320
Holly Hill, S.C.	WHHL	1440
Holly Springs, Miss.	WKRA	1110
	WREB	930
Holyoke, Mass.	KHAL	1320
Homestead, Fla.	KPGI	1430
Homewood, Ala.	WLJD	1400
Honolulu, Hawaii	KAIM	870
Honolulu, Hawaii	KCCN	1420
	KGMB	590
	KZOO	1210
	KHAI	1090
	KPOI	1380
	KIKI	830
	KGU	760
	KHVV	1040
	KNDI	1270
	KOHO	1170
	KORL	650
	KTRG	1430
	KULA	690
Hood River, Oreg.	KIHR	1340
Hopa, Ark.	KKAR	1490
Hopewell, Va.	WHAP	1340
Hopkinsville, Ky.	WHOP	1230
	WKOA	1480
Houma, La.	KRCB	1430
Houquiam, Wash.	WWHG	1320
Hornell, N.Y.	WLEA	1480
Hot Springs, Ark.	KBHS	590
	KZNG	1470
Hot Springs, S. Dak.	KQBH	580
	WHDF	1400
Houghton, Mich.	WHGR	1290
Houghton Lake, Mich.	WHOU	1340
Houlton, Maine	KCIL	1490
Houma, La.	WDPC	940
Houston, Miss.	KBTC	1250
Houston, Mo.	KCRB	1430
Houston, Tex.	KENR	1070
	KILT	610
	KNUZ	1230
	KODA	1010
	KPRC	950
	KTHI	790
	KTRH	740
	KXYZ	1320
	KYOK	1590
Howell, Mich.	WHMI	1350
Hudson, N.Y.	WHUC	1230
Hugo, Okla.	KIHN	1340
Humacao, P.R.	WALO	1240
Humboldt, Tenn.	WHYI	740
Huntingdon, Pa.	WHUN	1150
Huntington, Ind.	WHLT	1300
Huntington, N.Y.	WGSM	740
Huntington, W. Va.	WKEE	800
	WSAZ	930
	WWTI	1470
Huntsville, Ala.	WBHP	1230
	WEUP	1600
	WFIX	1450
	WAAY	1550
Huntsville, Tex.	KSAM	1490
Huron, S. Dak.	KJIV	1340
Hutchinson, Kans.	KBAB	1450
	KWHK	1260
Hutchinson, Minn.	KDUZ	1260
Hyde Park, N.Y.	WHVW	950
Idabel, Okla.	KBEL	1240
Idaho Falls, Idaho	KID	590
	KTEE	1260
Immokalee, Fla.	WAWI	1450
Independence, Ia.	KUPI	980
	KOUR	1220
Independence, Kans.	KIND	1010
Independence, Mo.	KCCX	1510
Indiana, Pa.	WDAD	1450
Indianapolis, Ind.	WATI	810
	WBRI	1500
	WFBM	1260
	WGEE	1590
	WIBC	1070
	WIFE	1310
	WIRE	1430
	WLW	950
Indianola, Iowa	KBAB	1490
Indianola, Ia.	KBAB	1490
Indianola, Miss.	WNLA	1380
Indian Rocks Beach, Fla.	WGPN	1520
Indio, Calif.	KREO	1400

Location	C.L.	Kc.
Inglewood, Calif.	KTYM	1480
Inkster, Mich.	WCHB	1440
International Falls, Minn.	KGHS	1230
Inverness, Fla.	WYSE	1560
Iola, Kansas	WMS	830
Ionia, Mich.	WION	1430
Iowa City, Iowa	KXIC	810
	WSUI	910
Iowa Falls, Iowa	KFIG	1510
Iron Mtn., Mich.	WMIQ	1450
Irontdale, Ala.	WIXI	1480
Ironton, Ohio	WIRO	1230
Ironwood, Mich.	WIMS	1450
Irvine, Ky.	WIRV	1550
Isabella, P.R.	WISA	1390
Ishpeming, Mich.	WJPD	1240
	WCKD	970
Istip, N.Y.	WBCI	540
Ithaca, N.Y.	WHCU	870
	WKIO	1270
Iuka, Miss.	WYOD	1270
Jackson, Ala.	WHOD	1290
Jackson, Mich.	WIBM	1450
	WKHM	970
	WJCO	1510
Jackson, Miss.	WJDX	620
	WJQS	1400
	WJW	1450
	WOKJ	1550
	WWUN	1590
	WRBC	1300
	WSLI	980
Jackson, Ohio	WLMJ	1280
Jackson, Tenn.	WDXI	1310
	WJAM	1460
	WTJS	1390
Jackson, Wis.	WYLO	1540
Jackson, Wyo.	KSGT	1430
Jacksonville, Ark.	KGMR	1500
Jacksonville, Fla.	WJAX	930
	WAPE	690
	WZOK	1320
	WZLN	1050
	WMBR	1460
	WQBS	1360
	WPDQ	600
	WQIK	1090
	WRHC	1400
Jacksonville, Ill.	WLDS	1180
Jacksonville, Miss.	WJOS	1400
Jacksonville, N.C.	WJNC	1240
	WLAS	910
Jacksonville, Tex.	KEBE	1400
Jacksonville Beh., Fla.	WBIX	1010
Jamestown, N. Dak.	KEVJ	1400
	KSJB	600
Jamestown, N.Y.	WJTN	1240
	WKSN	1360
Jamestown, Tenn.	WCIC	1260
Jasper, Wis.	WGLD	1230
Jasper, Ala.	WWWF	1450
	WARF	1240
Jasper, Ind.	WITZ	990
Jasper, Tex.	KTXJ	1350
Jefferson City, Mo.	KLIK	950
	KWOS	1240
Jefferson City, Tenn.	WJFC	1480
Jeffersonville, Ind.	WYXV	1450
Jena, La.	KCKW	1480
Jennings, La.	KJEF	1290
Jerome, Idaho	KART	1400
Jerseyville, Ill.	WJBM	1480
Jesup, Ga.	WLDP	1370
John Day, Ore.	KJDY	1400
Johnson City, Tenn.	WJCV	910
	WETB	790
Johnston, S.C.	WJES	250
Johnstown, N.Y.	WIZR	930
Johnstown, Pa.	WJAC	850
	WARD	1490
	WCRD	1480
Joliet, Ill.	WJOL	1340
	WJRC	1510
Joliette, Que.	CJLM	1350
Jonesboro, Ark.	KBTM	1230
	KNEA	970
Jonesboro, La.	KTOC	920
Jonesboro, Tenn.	WKIS	1590
Jonesville, La.	KANV	1480
Joplin, Mo.	WMBH	1450
	KQYX	1560
	KFSB	1310
	KODE	1230
Junetta, Tex.	KNBL	1450
Juneau, Alaska	KJUN	1420
Juneau, Alaska	KINY	800
	KJNO	630
Kailua, Hawaii	KLEI	1190
Kalamazoo, Mich.	WKPR	1420
	WKZO	590
	WKLZ	1470
	WKMI	1360
Kallispell, Mont.	KGEZ	800
	KOFI	930
Kane, Pa.	WKZA	960
Kankakee, Ill.	WKAN	1320
Kannapolis, N.C.	WGTL	870
	WRKB	1460

Location	C.L.	Kc.
Kans. City, Kans.	KCKN	1340
Kansas City, Mo.	KCMO	810
	KMBC	980
	KPRS	1590
	WDAF	610
	WHB	710
Kaukauna, Wis.	WKAU	1050
Kenedy-Karnes City, Texas	KAML	990
Kealakekua, Hawaii	KONA	790
Kearney, Nebr.	KGFV	1340
	KRNF	1600
Keene, N.H.	WKNE	1290
	WKBK	1220
	KLOG	1490
Kemmerer, Wyo.	KMER	950
Kendallville, Ind.	WAWK	1570
Kenedy, Tex.	KAML	990
Kennett, Mo.	KBOA	830
	KHKA	1540
Kennewick-Pasco-Richland, Wash.	KEPR	610
Kenosha, Wis.	WLIP	1050
Kent, O.	WKNT	1520
Keokuk, Iowa	KOKX	1310
Kermit, Tex.	KERB	600
Kerrville, Tex.	KERE	1230
Kershaw, S.C.	WKSC	1300
Ketchikan, Alaska	KTKN	930
Kewanee, Ill.	WKEI	1450
Keyser, W. Va.	WKYR	1270
	WKLP	1390
Key West, Fla.	WKWF	1600
	WKIZ	1500
Kilgore, Tex.	WKIL	1460
Killen, Tex.	KLEN	1050
Kimball, Nebr.	KIMB	1280
King, N.C.	WKTE	1090
King City, Calif.	KRKC	1490
Kingman, Ariz.	KAAA	1230
Kings Mountain, N.C.	WKMT	1220
	KWIN	1320
Kingsport, Tenn.	WKPT	1550
Kingston, N.Y.	WBAZ	1550
	WGHQ	920
	WKNY	1490
Kingstree, S.C.	WDKD	1310
Kingsville, Tex.	KINS	1450
Kingston, N.C.	WELS	1010
	WFTC	960
	WISP	1230
Kirkland, Wash.	KYAC	1460
	KBLE	1050
Kirksville, Mo.	KIRX	1450
Kissimmee, Fla.	WKIN	1300
	WPB	1220
Kittanning, Pa.	WACB	1380
Klamath Falls, Oreg.	KAGO	1150
	KFLW	1450
	KLAD	960
	KNA	1320
Knoxville, Iowa	WBI	1240
Knoxville, Tenn.	WVVK	850
	WATE	620
	WKXX	900
	WNXX	990
	WROL	1490
Kokomo, Ind.	WIOU	1350
Kosciusko, Miss.	WLTA	1350
Laconia, N.H.	WLNH	1350
	WEMJ	1490
LaCrosse, Wis.	WKBB	1410
	WLXC	1490
	WKTY	580
Ladysmith, Wis.	WLDY	1340
Lafayette, Ga.	WLFA	1590
	WASK	1450
	WAZY	1410
	WBAA	920
Lafayette, La.	KPEL	1420
	KVCL	1330
Lafayette, Tenn.	KXEN	1480
LaFollette, Tenn.	WLAF	1450
LaGrande, Oreg.	KLBM	1450
LaGrange, Ga.	WLAG	1240
	WTRP	620
LaGrange, Ill.	WTAQ	1300
LaGrange, Tex.	KVLG	1370
Lake Geneva, Calif.	KWJ	1490
Lake Charles, La.	KLOU	1580
	KPLC	1470
	KAOK	1400
Lake City, Fla.	WDSR	1340
	WGRD	960
Lake City, S.C.	KLPT	1500
Lake Geneva, Wis.	MIR	1550
Lakeland, Fla.	WLAK	1430
	WONN	1230
	WWAB	1330
Lake Placid, N.Y.	WIRD	920
Lakeport, Cal.	KBIC	1270
Lake Providence, La.	KLPL	1500
Lake Tahoe, Calif.	KWJ	1490
Lakeview, Oreg.	KQIK	1230
Lake Wales, Fla.	WIPC	1280
Lakewood, Colo.	KLAK	1600
Lakewood Center, Wash.	KFHA	1480
Lake Worth, Fla.	WLIZ	1380

Location	C.L.	Kc.
Lamar, Colo.	KLMR	920
Lamesa, Tex.	KPET	690
Lampasas, Tex.	KCYL	1450
Lancaster, Calif.	KAVL	610
	KEVM	1380
	WNM	1300
Lancaster, N.Y.	WLAN	1300
Lancaster, Ohio	WHOK	1320
Lancaster, Pa.	WGAL	1490
	WLAN	1390
Lancaster, S.C.	WLCM	1360
	WAGL	1560
Lander, Wyo.	KOVE	1390
Landett, Ala.-W. Point, Ga.	WSD	1580
	WMO	1490
Lansdale, Pa.	WNPV	1440
Lansford, Pa.	WLSH	1410
Lansing, Mich.	WILS	1320
	WJIM	1240
	WITL	1010
Lapeer, Mich.	WMPC	1230
	WMM	1530
LaPorta, Md.	WSDM	1580
LaPlata, Ind.	WL01	1540
Laramie, Wyo.	KLME	1490
	KQWB	1290
Laredo, Tex.	KGNS	1300
	KVOZ	1490
Larned, Kans.	KANS	1510
LaSalle, Ill.	WLPO	1220
Las Cruces, N. Mex.	KWEC	1450
	KGRT	570
Las Vegas, Nev.	KENO	1460
	KLAV	1230
	KORK	1340
	KRAM	920
	KLUC	1050
	KVGC	1450
Las Vegas, N. Mex.	KFUN	1290
Latrobe, Pa.	WPKV	1570
	WQTV	1470
	WTRA	1480
	KCCD	900
Laurel, Md.	WAML	1340
Laurel, Miss.	WLAD	1600
	WLSL	1260
Laurens, S.C.	WLBG	860
Laurinburg, N.C.	WEWO	1080
	WLNC	1390
Lawrence, Kans.	KFKU	1250
	KLWN	1320
Lawrence, Mass.	WCCM	800
Lawrenceburg, Tenn.	WDXE	1370
Lawrenceville, Ga.	WLAW	1360
Lawrenceville, Ill.	WAKO	910
Lawrenceville, Va.	WLES	580
Lawton, Okla.	KSWO	1380
	KCCD	1050
Leadville, Colo.	KBRR	1230
Leaksville, N.C.	WLO	1490
Leavenworth, Kans.	KCLO	1410
Lebanon, Ky.	WLBN	1590
Lebanon, Mo.	KLWT	1230
Lebanon, Oreg.	KGAL	920
Lebanon, Pa.	WLBK	1270
Lebanon, Tenn.	WGOR	990
Leesburg, Fla.	WLBG	790
	WBI	1410
Leesburg, Va.	WGE	1290
Leesville, La.	KLLA	1570
Leighton, Pa.	WYNS	1150
Leitchfield, Ky.	WMTL	1580
Leland, Miss.	WESY	1580
LeMars, Iowa	KLEM	1410
Leمون, S.D.	KBJM	1400
LeMore, Calif.	KLAN	1320
	KOAD	1240
Lenoir, N.C.	WJRI	1340
Lenoir, Tenn.	WLIT	730
Lenoir City, Tenn.	WBLC	1360
Leonardtown, Md.	WKTK	1370
Levelland, Tex.	KLVT	1230
Levittown, Pa.	WBDB	1490
Lewisburg, Pa.	WUNS	1010
Lewisburg, Tenn.	WJIM	1490
Lewisport, Ind.	KRLC	1350
	KOZE	1300
Lewiston, Maine	WCOU	1240
	WLAM	1470
Lewistown, Mont.	KVA	1490
Lewistown, Pa.	WRFK	1490
Lexington, Ky.	WLAP	630
	WBLG	1300
	WLTN	1590
Lexington, Miss.	WXTN	1000
Lexington, Mo.	KLEX	1470
Lexington, Nbr.	KFN	1440
Lexington, N.C.	WBUI	1400
Lexington, Tenn.	WDXL	1490
Lexington, Va.	WREL	1450
Lexington Pk., Md.	WPTX	920
Libby, Mont.	KLCB	1230
	KLFB	1470
Liberal, Kans.	WJW	1270
Liberty, Ky.	WPHN	1560
Liberty, N.Y.	WVOS	1240
Liberty, Tex.	KFAZ	1050
Lihue, Hawaii	KTOH	1490
Lima, Ohio	WIMA	1150
	WCIT	940
Lincoln, Ill.	WPRC	1370

Location	C.L.	Kc.	Location	C.L.	Kc.	Location	C.L.	Kc.	Location	C.L.	Kc.
Lincoln, Me.	WLKN	1450	Madison, Ga.	WYTH	1250	McKinney, Tex.	KYAL	1600	Missoula, Mont.	KGYO	1290
Lincoln, Nebr.	WLFOR	1240	Madison, Ind.	WORX	1270	McMinnville, Oreg.	KMCM	1260		KXLL	1450
	KLIN	1400	Madison, S.D.	KJAM	1390	McMinnville, Tenn.	WBMC	960		KQTE	1340
	KLMS	1480	Madison, Tenn.	WENO	1430		WAKI	1230		KYSS	910
	KL0L	1530	Madison, Wis.	WHA	750	McPherson, Kans.	KNEZ	1540	Mitchell, S. Dak.	KURR	1490
Lincolnton, N.C.	WLON	1050		WIBA	1810	Meade, Ga.	WYIC	1410	Moab, Utah	KURA	1450
Linton, Ind.	WBTO	1800		WISM	1480	Medford, Pa.	WNGW	1490	Moberly, Mo.	KNCM	1230
Litchfield, Ill.	WSMI	1540		WKOW	1070	Medford, Mass.	WHIL	1430	Mobile, Ala.	WUNI	1410
Little Falls, Minn.	KKFD	1410		WMAD	1550	Medford, Oreg.	KMED	1440		WABB	1480
Little Falls, N.Y.	WLHF	1230	Madisonville, Ky.	WFMW	730		KSHA	860		WGOK	900
Littlefield, Tex.	KZZN	1490		WTTL	1310		KDOV	1300		WMOO	1550
Little Rock, Ark.	KARK	920	Magee, Miss.	WSIC	810		KBOY	730		WTFE	940
	KALO	1250	Magnolia, Ark.	KVMA	630	Medford, Wis.	WIGM	1490		WKRQ	710
	KLRA	1010	Makawao, Hawaii	KNUJ	1310	Medlia, Pa.	WXUR	690		WLIQ	1360
	KOKY	1440	Malden, Mo.	KTCB	1470	Melba, Pa.	WMMB	1240	Mobridge, S. Dak.	WMOZ	960
	KAAV	1090	Malone, N.Y.	WTCY	1490	Melbourne, Fla.	WHBQ	560	Modesto, Calif.	KTRB	860
	KVLC	1050	Malvern, Ark.	KBOK	1310	Memphis, Tenn.	KEGH	1130		KBEF	970
	KDKO	1510	Manassas, Va.	WMNT	1550		WHER	1430		KFIJ	1360
Littleton, Colo.	WLTN	1400	Manati, P.R.	WINF	1230		WNC	790		KDOL	1340
Live Oak, Fla.	WNER	1250	Manchester, Conn.	WFOR	1370		WIDIA	1070	Mojave, Calif.	WQUA	1230
Livingston, Mont.	KPKR	1340	Manchester, Ga.	WFXL	1450		WMPF	680	Moline, Ill.	KVGM	1490
Livingston, Tenn.	WLIV	920	Manchester, Ky.	WFXL	1450		WLOK	1340	Monahans, Tex.	KVKM	1330
Livingston, Tex.	KEEX	1440	Manchester, N.H.	WFEA	1370		WMQM	1480	Moncks Corner, S. C.	WBER	950
	KVLL	1220		WGIR	610		WREC	600	Monett, Mo.	KRMO	990
Lock Haven, Pa.	WBZP	1230	Manchester, Tenn.	WMSR	1320		KWAM	990	Monetta, Ark.	KRAM	1360
Lockport, N.Y.	WUSJ	1340	Manhattan, Kans.	KSAC	580	Mena, Ark.	KENA	1450	Monmouth, Ill.	WRAM	1330
Lodi, Calif.	KCVR	1570		KMAN	1350	Menominee, Mich.	WAGN	1340	Monroe, Ga.	WMRE	1490
Logan, Utah	KVNU	610	Manistee, Mich.	WMTL	1340	Menomonee, Wis.	WMNE	1360	Monroe, La.	KLIC	1440
	KSTU	1800	Manistique, Mich.	WTIQ	1490	Merced, Calif.	KYOS	1480		KNOE	520
	KLGN	1390	Manitou Springs, Colo.	KCMS	1490		KWIP	1580	Monroe, Mich.	WQTE	260
	WLDG	1230		WCUB	980	Meriden, Conn.	WMMW	1470	Monroe, N.C.	KRBE	960
Logan, W. Va.	WSAL	1230	Manitowoc, Wis.	WOMT	1240	Meridian, Miss.	WDCD	910		WEKZ	560
Logansport, Ind.	WSAL	1230		WOMT	1240		WID	1350	Monroeville, Ala.	WMFC	1360
Lompoc, Calif.	KKOK	1410	Mankato, Minn.	KYSM	1230		WMOX	1010	Monterey, Calif.	KIDO	630
	KLOM	1330		KTOE	1240		WOKK	1450	Montevideo, Minn.	KOMA	1240
	KNEZ	960	Manning, S.C.	KYMB	1410		WQIC	1390	Monte Vista, Colo.	KSLV	240
London, Ky.	WFTG	1400	Manassas, Va.	KDXJ	1360	Merkle, Tex.	KWFA	1500	Montezuma, Ga.	WMNZ	1050
Long Beach, Calif.	KFGX	1280	Mansfield, Ohio	WMAN	1400	Merrill, Wis.	WXMT	730	Montgomery, Ala.	WAPX	1600
	KKFD	1390		WCLR	1140	Mesa, Ariz.	KBUZ	1310		WCOV	1170
Longmont, Colo.	KLMD	1060	Maplewood, Minn.	WRCR	1010	Metropolis, Ill.	KALF	1510		WFMJ	1500
Long Prairie, Minn.	KEYL	1400	Maquoketa, Iowa	KMAQ	1320	Metter, Ga.	WMAC	920		WHHY	1440
Longview, Tex.	KFR0	1370	Marathon, Fla.	WFFG	1300	Mexia, Tex.	KBUS	1590		WMGY	800
	KLUE	1280	Marianna, Ark.	KZOT	1460	Mexico, Mo.	KXEO	1340		WRMA	950
Longview, Wash.	KEDO	1400	Marianna, Fla.	WTYS	1340	Mexico, Pa.	WJUN	1220	Montgomery, W. Va.	WMON	1340
	KBAM	1270	Marietta, Ga.	WTOT	980	Miami, Ariz.	KIKO	1340		WKHM	1430
Lookout Mtn., Tenn.	WFLI	1070	Marietta, Ohio	WFOJ	1230	Miami, Fla.	WGBS	710	Monticello, Ark.	KVSI	1420
Lorain, Ohio	WVWJ	1380		WBI0	1080		WFB	990	Monticello, Fla.	WVSO	1090
Loretto, Pa.	WWSF	1400	Marion, Ala.	WMOA	1490		WAME	1260	Monticello, Ky.	WFLW	1360
Loris, S.C.	WLSF	1570	Marion, Ill.	WBRJ	910		WMIE	1140	Montpelier, Idaho	KVSI	1450
Los Alamos, N. Mex.	KRSN	1490	Marion, Ind.	WWSA	1590	Marion, Ala.	WJAM	1310	Montpelier-Barre, Vt.	WWSK	1240
Los Angeles, Calif.	KABC	790	Marion, N.C.	WWMR	860	Marion, Ill.	WJAM	1310	Montrose, Colo.	KUBC	580
	KFI	640	Marion, Ohio	WBRN	1250	Marion, Ind.	WBAT	1400	Montrose, Pa.	WPFL	1250
	KHJ	930	Marion, S.C.	WBRN	1250	Marion, Ind.	WBR1	860	Mooresville, N.C.	WHIP	1350
	KFB	1280	Marion, Va.	WBRN	1250	Marion, N.C.	WBRN	1250	Moorhead, Minn.	KVOX	1280
	KFCF	1380	Marked Tree, Ark.	WBRN	1250	Marion, Va.	WMEV	1010	Morehead, Ky.	WMOR	1330
	KLAC	570	Marquette, Mich.	WGGH	1150	Marked Tree, Ark.	WOLD	133	Morehead City, N.C.	WMBL	740
	KMPC	710	Marshall, Mich.	WWR1	860	Marquette, Mich.	WGGH	1150	Morgan City, La.	KMRC	1430
	KNX	1070	Marshall, N.C.	WWR1	860	Marshall, N.C.	WMMH	1460	Morganfield, Ky.	WMKS	1500
	KPOL	1540	Marshall, Tex.	KDXJ	1360	Marshall, N.C.	WMMH	1460	Morgantown, N.C.	WMNC	1430
	KGBS	1020	Marshalltown, Iowa	KFBX	1230	Marshall, Tex.	KDXJ	1360	Morgantown, W. Va.	WBJR	1440
	KRDK	1150	Marshfield, Wis.	WDLB	1450	Marshall, Tex.	KDXJ	1360	Morrilton, Ark.	WCLG	1300
Los Banos, Calif.	KLBS	1330	Martin, Tenn.	WCMT	1410	Marshall, Tex.	KDXJ	1360	Morris, Ill.	WCST	550
Louisburg, N.C.	WYRN	1480	Martinsburg, W. Va.	WEPM	1340	Marshall, Tex.	KDXJ	1360	Morris, Minn.	KMRS	1230
Louisville, Ga.	WPEH	1420	Martinsville, Va.	WHEE	1370	Marshall, Tex.	KDXJ	1360	Morristown, N.J.	WMTR	1250
Louisville, Ky.	WAVE	970	Maryville, Mo.	WMVA	1450	Marshall, Tex.	KDXJ	1360	Morristown, Tenn.	WCR1	1150
	WAKY	790	Marysville, Calif.	KMYC	410	Marshall, Tex.	KDXJ	1360	Morton, Tex.	KRAN	1280
	WHAS	840	Marysville, Kans.	KNOY	1570	Marshall, Tex.	KDXJ	1360	Nosco, Idaho	KRFL	1400
	WKL0	1080	Maryville, Tenn.	WGAP	1400	Marshall, Tex.	KDXJ	1360	Nosco, Wash.	KSEM	1470
	WINN	1240	Mason City, Iowa	KGLO	1300	Marshall, Tex.	KDXJ	1360		KWIG	1260
	WFIA	900	Massena, N.Y.	KRIB	1490	Marshall, Tex.	KDXJ	1360	Moss Point, Miss.	WACY	1460
	WLOU	1350	Massillon, Ohio	WTIG	990	Marshall, Tex.	KDXJ	1360	Moulton, Ala.	WLCB	1530
	WTMT	620	Matawan, W. Va.	WHJC	1360	Marshall, Tex.	KDXJ	1360	Moultrie, Ga.	WMGA	1400
Louisville, Miss.	WLSM	1270	Mattoon, Ill.	WLBH	1170	Marshall, Tex.	KDXJ	1360	Moultrie, Ga.	WMGA	1400
Loveland, Colo.	KLOV	1570	Mauston, Wis.	WRJC	1270	Marshall, Tex.	KDXJ	1360	Moundsville, W. Va.	WEIF	1370
Loves Park, Ill.	WLUV	1520	Mayaguez, P.R.	WAEI	600	Marshall, Tex.	KDXJ	1360	Mountain Grove, Mo.	KLRS	1360
Lovington, N. Mex.	KLEA	630		WORA	760	Marshall, Tex.	KDXJ	1360	Mountain Home, Ark.		
Lowell, Mass.	WCAP	980		WPRA	990	Marshall, Tex.	KDXJ	1360	Mountain Home, Idaho.	KFLI	1240
	WLLH	1400	Mayfield, Ky.	WTLL	1300	Marshall, Tex.	KDXJ	1360	Mt. Airy, N.C.	WPAG	740
Lubbock, Tex.	KCBAD	1590	Mayfield, N.C.	WVNG	1320	Marshall, Tex.	KDXJ	1360	Mt. Carmel, Ill.	WVMC	1360
	KDAV	580	Mayodan, N.C.	WVMN	1420	Marshall, Tex.	KDXJ	1360	Mt. Clemens, Mich.	WBRB	1430
	KLBK	1340	Mayville, N.D.	KMAV	1520	Marshall, Tex.	KDXJ	1360	Mt. Oora, Fla.	WVGT	590
	KFY0	790	Mayville, N.Y.	WFTB	1240	Marshall, Tex.	KDXJ	1360	Mt. Jackson, Va.	WSIG	790
	KLL1	1460	McAfee, Okla.	KTMK	1400	Marshall, Tex.	KDXJ	1360	Mt. Jackson, N.Y.	WVAG	1310
	KSEL	950		KNE1	1150	Marshall, Tex.	KDXJ	1360	Mt. Olive, N.C.	WDJS	1430
Lueddale, Miss.	WHHT	1440	McAllen, Tex.	KR10	910	Marshall, Tex.	KDXJ	1360	Mt. Pleasant, Mich.	WCEN	1150
Ludington, Mich.	WKLA	1450	McCall, Ida.	KMCL	1240	Marshall, Tex.	KDXJ	1360	Mt. Pleasant, Tex.	KIMP	960
Lufkin, Tex.	KRBA	1340	McCamey, Tex.	KAMY	1450	Marshall, Tex.	KDXJ	1360	Mt. Shasta, Calif.	KWSD	620
	KTRF	1420	McComb, Miss.	WAFB	980	Marshall, Tex.	KDXJ	1360	Mt. Sterling, Ky.	WMST	1150
Lumberton, N.C.	WTSB	1340	McCook, Nebr.	KBR1	1300	Marshall, Tex.	KDXJ	1360	Nit. Vernon, Ill.	WNIX	940
	WRAA	1330		KWRV	1360	Marshall, Tex.	KDXJ	1360	Nit. Vernon, Ind.	WVBO	1590
Luray, Va.	WLVA	590	McGehee, Ark.	KVSA	1220	Marshall, Tex.	KDXJ	1360	Nit. Vernon, Ohio	WMVO	1360
Lynchburg, Va.	WLLL	930	McKeessport, Pa.	WNCK	1360	Marshall, Tex.	KDXJ	1360	Nit. Vernon, Wash.	KAPS	1470
	WDM5	1320	McKenzie, Tenn.	WHDM	1440	Marshall, Tex.	KDXJ	1360		KBRC	1430
	WDDG	1390				Marshall, Tex.	KDXJ	1360	Muleshoe, Tex.	KMUL	1380
	WR00	1050				Marshall, Tex.	KDXJ	1360	Mulins, S.C.	WJAY	1290
Lynn, Mass.	WLN1	1360				Marshall, Tex.	KDXJ	1360	Muncie, Ind.	WLPB	1340
Lyons, Ga.	WBTT	1340				Marshall, Tex.	KDXJ	1360		WERK	990
Macomb, Ill.	WKAI	1510				Marshall, Tex.	KDXJ	1360	Munfordville, Ky.	WLOC	1150
Macon, Ga.	WBML	1240				Marshall, Tex.	KDXJ	1360	Munising, Mich.	WTGN	1400
	WCRT	900				Marshall, Tex.	KDXJ	1360			
	WIBB	1280				Marshall, Tex.	KDXJ	1360			
	WHAZ	940				Marshall, Tex.	KDXJ	1360			
	WNEK	1400				Marshall, Tex.	KDXJ	1360			
Macon, Miss.	WMB0	1400				Marshall, Tex.	KDXJ	1360			
Macon, Mo.	KLTI	1560				Marshall, Tex.	KDXJ	1360			
Madawaska, Me.	WSJR	1230				Marshall, Tex.	KDXJ	1360			
Madera, Calif.	KHOT	1250				Marshall, Tex.	KDXJ	1360			
Madill, Okla.	KMAD	1550				Marshall, Tex.	KDXJ	1360			
Madison, Fla.	WMAF	1230				Marshall, Tex.	KDXJ	1360			

WHITE'S RADIO LOG

Location	C.L.	Kc.
Murfreesboro, N. C.	WDR	1080
Murfreesboro, Tenn.	WNS	1450
	WMTS	810
Murphy, N.C.	WRB	600
	WKRK	1320
Murphysboro, Ill.	WINI	1420
Murray, Ky.	WNBS	1340
Murray, Iowa	KMOR	1230
Muscataine, Utah	KWPC	860
Muscle Shoals City, Ala.		
	WLAY	1450
Muskegon, Mich.	WKBZ	850
	WTRF	1520
	WRUR	1600
	WMUS	1090
Muskegon, Okla.	KBIX	1490
	KMUS	1380
Myrtle Beach, S.C.	WHYB	1450
Nacogdoches, Tex.	KEE	1230
	KSFA	860
Nampa, Idaho	KFXD	580
	KAIN	1340
Nanticoke, Pa.	WNAK	730
Napa, Calif.	KNDN	1440
Naples, Fla.	WOP	1270
Narrows, Va.	WNRV	990
Nashua, N.H.	WOTW	900
	WSMN	1590
Nashville, Ark.	KBHC	1260
Nashville, Ga.	WNGA	1600
Nashville, Tenn.	WKDA	1240
	WNS	1310
	WNAK	300
	WNAH	1360
	WSIX	980
	WSM	650
	WWMG	1560
Nassau, Bahamas	ZNS-2	1240
Natchez, Miss.	WOP	1240
	WNAT	1450
Natchitoches, La.	KNOC	1450
Naugatuck, Conn.	WOWW	860
Navasota, Tex.	KWBC	1550
Nebraska City, Nebr.	KNCY	1600
Needles, Calif.	KNEE	1340
Neenah, Wis.	WNAM	1280
Neillsville, Wis.	WCCN	1370
Neon, Ky.	WNKY	1420
Neosho, Mo.	KBTN	1480
Nevada, Mo.	KNEM	1240
New Albany, Ind.	WNUW	1570
	WREY	1290
New Albany, Miss.	WNRK	1470
Newark, Del.	WRR	1260
Newark, N.J.	WJRZ	970
	WNJR	1430
	WVNJ	620
Newark, N.Y.	WACK	1420
Newark, Ohio	WCKL	1430
New Bedford, Mass.	WBSM	1420
	WNBH	1340
New Bern, N.C.	WHIT	1450
	WRNB	1490
Newberry, Mich.	WNBY	1450
Newberry, S.C.	WKDK	1240
New Boston, Ohio	WIOI	1010
New Braunfels, Tex.	KGNB	1420
New Britain, Conn.		
	WRCH	910
	WRYM	840
New Brunswick, N.J.		
	WCTC	1450
	WGNV	1220
Newburyport, Mass.	WBP	1470
New Castle, Ind.	WCTW	1550
New Castle, Pa.	WKST	1240
Newcastle, Wyo.	KASL	1280
New City, N. Y.	WRKL	910
New Haven, Conn.	WAVZ	1300
	WELI	960
	WNHT	1340
	WKOE	1240
	KNIR	1360
New Iberia, La.		
	WKPA	1150
	WNLK	1510
New Martinsville, W. Va.		
	WETZ	1330
	WCOH	1400
Newnan, Ga.	WNEA	1300
New Orleans, La.	WDSU	1280
	WNNR	990
	WBOK	800
	WNOE	1060
	WSMB	1350
	WFRS	1450
	WSHO	1230

Location	C.L.	Kc.
	WTIX	690
	WWL	870
	WWOM	600
	WYLD	940
Newport, Ark.	KNBY	1280
Newport, N.H.	WCNL	1010
Newport, Oreg.	KNPT	1310
Newport, R. I.	WAOC	1540
Newport, Tenn.	WLK	1270
Newport, Vt.	WVKE	1490
Newport News, Va.	WGH	1310
	WTID	1270
Newport Richey, Fla.		
	WGUL	1500
New Richmond, Wis.		
	WIXK	1590
New Roads, La.	KWRG	1500
New Rochelle, N. Y.	WVOX	1460
New Smyrna Beach, Fla.		
	WSBB	1230
	WOGO	1550
Newton, Iowa	KCOB	1280
Newton, Kans.	KJRG	950
Newton, Mass.	WNTN	1550
Newton, Miss.	WBKN	1410
Newton, N.J.	WVNM	1360
Newton, N.C.	WNNC	1230
New Ulm, Minn.	KNUJ	860
New York, N.Y.	WABC	770
	WADO	1280
	WBXN	1380
	WCBS	880
	WED	1350
	WHN	1050
	WHOM	1480
	WINS	1010
	WLBI	1190
	WMA	570
	WNCB	660
	WNEW	1130
	WNYC	930
	WOR	710
	WPOW	1350
	WRRL	1600
Niagara Falls, N. Y.	WHLD	1270
	WJIL	1440
Niceville-Valparaiso, Fla.		
	WNS	1340
Nicholasville, Ky.	WNVL	1250
Niles, Mich.	WNIL	1290
Niles, Ohio	WNIO	1540
Nogales, Ariz.	KNOG	1340
Nome, Alaska	KICY	850
Norfolk, Nebr.	WJAG	780
Norfolk, Va.	WTAR	790
	WVOT	1050
	WNOR	1230
	WRAP	850
Normal, Ill.	WIOK	1440
Norman, Okla.	WNAD	640
	KNOR	1440
Norristown, Pa.	WNAR	1100
Norwich, Conn.	WNB	1230
N. Atlanta, Ga.	WATY	580
N. Augusta, S.C.	WGUS	1380
	WFNL	1600
	WTHB	1550
North Bend, Oreg.	KFR	1340
North Charleston, S.C.	WNCG	910
Northampton, Mass.		
	WHMP	1400
North East, Pa.	WHYP	1530
Northfield, Minn.	WCAL	770
N. Little Rock, Ark.	KDXE	1380
North Platte, Nebr.	KXLR	1150
	KJLT	970
	KNOP	1410
	KODY	1240
No. Syracuse, N.Y.	WSQJ	1220
N. Vernon, Ind.	WOCH	1460
Northwestern, Ind.	WNWI	1080
No. Wilkesboro, N.C.		
	WKBC	810
	KNBI	1350
Norton, Va.	WNVA	1350
Norwalk, Conn.	WNLK	1350
Norwich, Conn.	WICH	1310
Norwich, N.Y.	WCHN	970
Oakdale, La.	KREH	900
Oakes, N. Dak.	KEYO	1220
Oak Grove, La.	KWCL	1280
Oak Hill, W. Va.	WOP	860
Oakland, Calif.	KEWB	910
	KABL	960
	KDIA	1310
Oakland, Md.	WMSG	1050
Oakland Park, Fla.	WIXX	1520
Oak Park, Ill.	WOPA	1490
Oak Ridge, Tenn.	WAO	1280
Ocala, Fla.	WOP	900
	WTMC	1290
	WWKE	1370
Ocean City, Md.	WETT	1590
Ocean City, Somers Pt., N.J.		
	WSLT	1520
Oceanlake, Oreg.	KBCH	1380
Oceanside, Calif.	KUDE	1320
Oella, Ga.	WSIZ	1580
Oconto, Wis.	WCOO	1200
Odessa, Tex.	KECK	920
	KOSA	1230

Location	C.L.	Kc.
	KOYL	1310
	KREL	1410
Oelwein, Iowa	KREI	950
Opallala, Nebr.	KOGA	930
Ogden, Utah	KLO	1480
	KANN	1250
	KSVN	730
	KVOG	1450
Ogdensburg, N.Y.	WSLB	1400
O. V. City, Pa.	WKRZ	1340
Okaloosa, Fla.	KFAB	1110
Oklahoma City, Okla.	KBYE	890
	KLPR	1140
	KOCY	1340
	KOMA	1520
	KTKO	1000
	KJEM	800
	WKY	930
Okmulgee, Okla.	KDKL	1240
Old Saybrook, Conn.	WLIS	1420
Olean, N.Y.	WMNS	1360
	WHDL	1450
Olin, Ill.	WVLL	740
Olympia, Wash.	KGY	1240
	KITN	920
Omaha, Nebr.	KBON	1490
	KFAB	1110
	WKOL	1290
	KOOD	1420
	KOWH	660
	WOW	590
Omak, Wash.	KOMW	680
Oneida, N.Y.	WVON	1310
Oneida, Tenn.	WBNT	1310
O'Neill, Nebr.	KBRX	1350
Oneonta, Ala.	WCRL	1570
Oneonta, N.Y.	WDS	730
Ontario, Calif.	KASK	1510
Ontario, Oreg.	KSRV	1380
Opelika, Ala.	WOP	1230
Opelousas, La.	KSLO	1230
Opp, Ala.	WAMI	860
Opportunity, Wash.	KZUN	630
Orange, Mass.	WCAT	1390
Orange, Tex.	KOGT	1600
Orange, Va.	WJMA	1340
Orangeburg, S.C.	KDQ	1150
	WOP	1580
	WTND	920
Orange Park, Fla.	WYR	550
Ord, Neb.	KNLV	1060
Oregon City, Oreg.	KYMN	1520
Orlando, Fla.	WBDO	1580
	WHOO	990
	WLD	1270
	WLOF	950
	WKIS	740
Ormond Beh., Fla.	WOXQ	1380
Orofino, Idaho	KLER	950
Oroville, Calif.	KADR	1340
Ortomville, Minn.	WDIO	1350
Osage Beach, Mo.	KRBS	1350
Oseola, Ark.	KOSE	860
Oshkosh, Wis.	WOSH	1490
Oskaloosa, Iowa	KBOE	740
Oswego, N.Y.	WSGO	1400
Othello, Wash.	KRSC	1440
Otsego, Mich.	WADP	980
Ottawa, Ill.	WYX	1480
Ottawa, Kans.	KOFD	1220
Ottumwa, Iowa	KBIZ	1240
	KLEE	1480
Owatonna, Minn.	KRFO	1390
Owego, N.Y.	WEBO	1330
Owensboro, Ky.	WOMI	1490
	WYV	1450
Owosso, Mich.	WOP	1080
Oxford, Miss.	WSU	1420
Oxford, N.C.	WOFX	1400
Oxnard, Calif.	KOXR	910
Ozark, Ala.	WOZK	900
Paducah, Ky.	WDXR	1560
	WVAD	1570
	WPAD	1450
Page, Ariz.	KPGE	1340
Painesville, Ohio	WPVL	1460
Paintsville, Ky.	WSIP	1490
Palatka, Fla.	WVFP	1260
	WSUZ	800
Palestine, Tex.	KNET	1450
Palm Bch., Fla.	WTK	1480
Palm Sprs., Calif.	KCMJ	1010
	KDES	920
	KPAL	1450
Palmdale, Calif.	KUTY	1470
Palm Desert, Cal.	KGOL	1220
Palo Alto, Calif.	KIBE	1270
Pampa, Tex.	KHHH	1230
Panama Beach, Fla.		
	WGNE	1480
	WSCM	1290
Panama City, Fla.	WDLF	590
	WPCF	1430
Paoli, Ind.	WVAK	1560
Paradise, Calif.	KNGL	930
Paragould, Ark.	KDRS	1490
Paris, Ark.	KCLL	1460
Paris, Ill.	WPRS	1450
Paris, Ky.	WPDE	1410
Paris, Tenn.	WTPR	710
Paris, Tex.	KPLT	1450
	KFTV	1250

Location	C.L.	Kc.
Parkersburg, W. Va.	WCEF	1050
	WPAR	1450
	WTFP	1230
Park Falls, Wis.	WPPF	1450
Park Rapids, Minn.		
	KPRM	1240
Parsons, Kans.	KLKC	1540
Pasadena, Cal.	KPPC	1240
	KRLA	1110
	KWKW	1300
Pasadena, Tex.	KLVL	1460
	KTKC	650
Pascagoula-Moss Point, Miss.		
	WPMP	1580
Pasco, Wash.	KORD	910
	KGRS	1340
Paso Robles, Calif.	KPRL	1230
Patohogue, L. I., N.Y.		
	WALK	1370
	WPCL	1580
Paterson, N.J.	WPAT	930
Pauls Valley, Okla.	KVLH	1470
Pawhuska, Okla.	KOSG	1500
Pawtucket, R. I.	WXTR	550
Payette, Ida.	KYET	1450
Pearsall, Tex.	KVWG	1280
Peas, Tex.	KIUN	1400
Peekskill, N.Y.	WTKA	1420
Pekin, Ill.	WSIV	1140
Pell City, Ala.	WFHK	1430
Pendleton, Oreg.	KTIA	1240
	KUMA	1290
Pennington Gap, Va.		
	WSVV	1570
Pensacola, Fla.	WBDP	960
	WBSR	1540
	WMEL	610
	WVNY	1230
	WCOA	1370
	WXCL	1350
	WMBD	1470
	WIDA	290
	WPEO	1020
Perry, Fla.	WPRY	1400
	WGKR	1310
Perry, Ga.	WPGA	980
Perry, Iowa	KDLS	1310
Perryton, Tex.	KEYE	1400
Peru, Ind.	WIP	1600
Petaluma, Calif.	KTOB	480
Petersburg, Va.	WSSV	1420
Petoskey, Mich.	WMBN	1340
Phenix City, Ala.	WPNX	1460
Philadelphia, Miss.	WHOC	1490
Philadelphia, Pa.	KYW	1060
	WCAU	1210
	WDA	1480
	WFIL	560
	WFNL	900
	WHAT	1340
	WHOC	1490
	WIBG	960
	WIP	610
	WPEN	950
	WRCP	1540
	WTEL	860
Phillipsburg, Pa.	WPBH	1260
Phillipsburg, Kans.	KIKAN	1490
Phoenix, Ariz.	KIFN	860
	KHAT	1480
	KHEP	1280
	KCAC	1010
	KOY	550
	KOOL	960
	KPHO	910
	KWJ	740
	KRIZ	1230
	KTAR	620
Phoenix City, Ala.		
	WPNX	1460
Piedmont, Ala.	WPID	1280
Piedmont, Mo.	KPWB	1140
Pierre, S.D.	KGFX	1980
	KCR	1240
Pikeville, Ky.	WLSI	900
Pine Bluff, Ark.	WPKE	1240
	KCLA	1400
	KADL	1270
	KOTN	1490
	KWTS	1570
	KPBA	1390
Pine City, Minn.	WCMP	1350
Pinellas Park, Fla.	WFSD	1500
Pineville, Ky.	WVLF	1230
Pineville, W. Va.	WVVO	970
Pinestone, Minn.	KLOH	1050
Piqua, Ohio	WVTS	1340
Pittsburg, Calif.	KIKS	990
Pittsburg, Kans.	KOAM	860
	KSEK	1340
Pittsburgh, Pa.	KDKA	1020
	KQV	1410
	WAMO	860
	WVTS	1570
	WPIT	730
	WRYT	750
	WEEP	1080
	WVSW	970
Pittsfield, Ill.	WBBA	1580
Pittsfield, Mass.	WBEC	1420
	WBRK	1340
Pittston, Pa.	WPTS	1540

WHITES RADIO LOG

Location	C.L.	Kc.
San Francisco, Calif.	KFRC	610
	KCBS	740
	KFAX	1400
	KGO	810
	KNBR	680
	KKHI	1550
	KSAY	1010
	KSFO	560
	KSOL	1450
	KYA	1260
San Gabriel, Cal.	KAIL	1430
San German, P. R.	WRJS	1060
Sanitobia, Miss.	WSAO	1550
San Jose, Calif.	KLOK	1170
	KLIV	1590
	KEEN	1370
	KXRX	1500
San Juan, P. R.	WAPA	680
	WIDA	970
	WIAC	740
	WIPR	940
	WKAQ	580
	WKVM	810
	WKYN	630
	WITA	1140
San Luis Obispo, Calif.	KATY	1340
	KSLY	1400
	KVEE	920
	KCNV	1470
San Marcos, Tex.	KOFY	1050
San Mateo, Calif.	KTIM	1010
San Rafael, Calif.	KBAL	1410
San Saba, Tex.		
San Sebastian, P. R.	WFBA	1460
Santa Ana, Calif.	KWIZ	1480
Santa Barbara, Calif.	KDB	1490
	KGUD	990
	KSR	1340
	KTMS	1250
	KACL	1290
Santa Clara, Calif.	KGNU	1430
Santa Cruz, Calif.	KSCO	1080
Santa Fe, N. Mex.	KTRC	1400
	KAFE	810
	KWVF	1200
Santa Maria, Cal.	KCOY	1400
	KHER	1600
	KSMA	1240
	KSEE	1480
Santa Monica, Cal.	KDAY	1580
Santa Paula, Calif.	KSPA	1400
Santa Rosa, Calif.	KSRQ	1350
	KHUM	1580
	KVRE	1460
	KJAX	1150
Santa Rosa, N. Mex.	KSYX	1420
Sapulpa, Okla.	KREK	1550
Saranac Lake, N. Y.	WNBB	1240
Sarasota, Fla.	WSAF	1220
	WSPB	1450
	WYND	1280
	WSPN	900
Saratoga, N. Y.		
Saratoga Springs, N. Y.	WKAJ	900
Sauk Rapids, Minn.	WVAL	800
Sault Ste. Marie, Mich.	WSOO	1230
Savannah, Ga.	WBYG	1450
	WEAS	900
	WSAV	630
	WSGA	1400
	WTOC	1290
	WSOK	1230
Savannah, Tenn.	WORM	1010
Sayre, Pa.	WATS	960
Sheffield, Ala.	WSHF	1290
Schenectady, N. Y.	WGY	810
	WQNY	1240
Scotland Neck, N. C.	WCKJ	1200
Scott City, Kans.	KFLA	1110
Scottsbluff, Nebr.	KLEB	960
	KOLT	1320
Scottsboro, Ala.	WCRI	1050
	WRSS	1330
Scottsdale, Ariz.	KDPT	1440
Scottsville, Ky.	WCKK	1250
Scranton, Pa.	WARM	990
	WEIL	630
	WGBI	910
	WICK	1400
	WSCR	1320
Seaford, Del.	WSUX	1280
Seary, Ark.	KWCF	1300
Seattle, Wash.	KAYO	1150
	KIXI	910
	KING	1090

Location	C.L.	Kc.
	KIRO	710
	KJR	950
	KOL	1300
	KOMO	1000
	KETO	1590
	KTW	1250
	KVP	570
	KXA	770
	KBLE	1050
Sebring, Fla.	WJCM	960
	WSEB	1340
Sedalia, Mo.	KDRO	1340
	KSIS	1050
Sequin, Tex.	KYD	1590
Selma, Ala.	WGWC	1340
	WHBB	1490
Selma, N. C.	WBZB	1090
Seminole, Tex.	KTFD	1250
Senatobia, Miss.	WSAO	1550
Seneca Township, S. C.	WSNW	1150
Sevierville, Tenn.	WSEV	930
Seward, Alaska	KIBH	950
Seymour, Ind.	WJCD	1390
Seymour, Tex.	KSEY	1230
Shakopee, Minn.	KSMM	1530
Shallotte, N. C.	WVCB	1410
Shamokin, Pa.	WISL	1480
Shamrock, Tex.	KYD	1590
Sharon, Pa.	WPIC	790
Shawano, Wis.	WTCH	960
Shawnee, Okla.	KGFF	1450
Sheboygan, Wis.	WHBL	1330
	WKTS	950
Sheffield, Ala.	WSHF	1290
Shelby, Mont.	KSN	1510
Shelby, N. C.	WOHS	730
	WADA	1390
Shelbyville, Ind.	WSVL	1520
Shelbyville, Ky.	WCND	940
Shelbyville, Tenn.	WHAL	1400
	WLJI	1580
Sheldon, Iowa	KWV	1350
Shen, Wash.	KMAS	1280
Shenandoah, Iowa	KMA	960
	KFNF	920
Shenandoah, Pa.	WMBT	1530
Sheridan, Wyo.	KWYO	1410
	KRDE	930
Sherman, Tex.	KRRV	1510
	KDRT	1500
Shippensburg, Pa.	WHPH	1480
Show Low, Ariz.	KVWM	970
Shreveport, La.	KANB	1300
	KBCL	1220
	KEEL	710
	KWV	1550
	KJDE	1480
	KCIJ	980
	KRMD	1340
	KWKH	1330
	KGCX	1480
Sidney, Mont.	KSID	1340
Sidney, Nebr.	WVR	1080
Sidney, O.	KHF	1420
Siler Vista, Ariz.	KHF	1420
Sikeston, Mo.	KSIM	1400
	KMPL	1520
Siler City, N. C.	WNCA	1570
Siloam Springs, Ark.	KUDA	1290
Silsbee, Tex.	KKAS	1300
Silver City, N. Mex.	KWST	1340
Silver Springs, Md.	WGMR	1050
Simcoe, Ont.	CFRS	1500
Sinton, Tex.	KTOD	1590
Sioux City, Iowa	KSCJ	1360
	KMNS	620
	KTRI	1470
Sioux Falls, S. Dak.	KISD	1230
	KELO	1320
	KNWC	1270
	KSOD	1140
Sitka, Alaska	KIFW	1230
	KSEW	1400
Skowhegan, Maine	WGHM	1150
Slaton, Tex.	KCAS	1050
Slidell, La.	WSE	1560
Smithfield, N. C.	WMPM	1270
Smithville, Tenn.	WJLE	1480
Smyrna, Ga.	WYNX	1550
Snyder, Tex.	KSNY	1450
Socorro, N. Mex.	KSRC	1290
Soda Springs, Idaho	KBRF	540
Somersett, Ky.	WFTO	480
	WLO	480
Somerset, Pa.	WVSC	990
Sonora, Calif.	KVML	1450
Sonora, Tex.	KCKG	1240
So. Bend, Ind.	WNUD	1490
	WJVA	1580
	WLE	950
Southbridge, Mass.	WESD	970
So. Boston, Va.	WHLF	1400
Southern Pines, N. C.	WEEB	990
South Charleston, W. Va.	WRDS	1410
South Daytona Beach, Fla.	WLE	1590
	WLE	1590
So. Gastonia, N. C.	WGAS	1420
So. Haven, Mich.	WJOR	940
So. Knoxville, Tenn.	WSKT	1580
So. Paris, Me.	WKTO	1450
So. Pittsburg, Tenn.	WEPG	910
So. St. Paul, Minn.		

Location	C.L.	Kc.
	KDWB	630
	WMKT	1370
So. Williamsport, Pa.	WMPT	1450
	KONI	1480
Spanish Fork, Utah	KBUB	1270
Sparks, Nev.	WHCO	1230
Sparta, Ill.	WCF	1050
Sparta, Tenn.	WKLI	990
Sparta, Wis.	WCOW	1290
	WHCO	1400
Spartanburg, S. C.	WORD	910
	WSPA	950
	WASC	1530
Spencer, Iowa	KWV	1590
Spencer, W. Va.	WSPZ	1400
Spokane, Wash.	KGA	1510
	KDNC	1440
	KPSO	1230
	KPEG	1380
	KHQ	590
	KNEW	790
	KREB	970
	KXLY	920
	KCFA	1330
	KUDY	1280
	KBR3	1340
Springdale, Ark.	KSPR	1590
	WCVS	1450
Springfield, Ill.	WMO	1470
	WTAX	1240
Springfield, Mass.	WHYN	560
	WMAS	1450
	WSPR	1270
Springfield, Mo.	KGBX	1260
	KICK	1340
	KTS	1400
	KWTO	560
Springfield, Ohio	WIZE	1340
	WBLY	1600
Springfield-Eugene, Ore.	KEED	1120
Springfield, Tenn.	WV	1590
Springfield, Vt.	KCFR	1480
Springhill, La.	KBSF	1460
Spring Lake, N. C.	WFBS	1450
Spring Valley, N. Y.	WRRC	1300
Spruce Pine, N. C.	WDE	1470
Stamford, Conn.	KDWT	1400
Stamford, Ky.	WRSL	1520
Starks, Fla.	WPXE	1490
Starkville, Miss.	WMSO	1230
State College, Pa.	WMAJ	1450
	WRSC	1390
Statesboro, Ga.	KWIS	1400
Statesville, N. C.	WSIC	1400
	WDBM	550
Staunton, Va.	WTON	1240
	WAF	900
Stephenville, Tex.	KSTV	1510
Sterling, Colo.	KGEK	1230
	KRFR	1490
	WSDR	1240
Sterling, Ill.	WSTV	1340
Steubenville, Ohio	WSPU	1010
Stevens Point, Wis.	WVNT	1010
Stillwater, Minn.	WAVN	1220
Stillwater, Okla.	KSPI	780
Stockton, Calif.	KJOD	1280
	KST	1400
	KWG	1230
Storm Lake, Iowa	KAYL	990
Streator, Ill.	WIZZ	1250
Stroudsburg, Pa.	WVPO	840
Stuart, Fla.	WSTU	1450
Stuart, Va.	WHED	1270
Sturgeon Bay, Wis.	WDRR	910
Sturgis, Mich.	WSTR	1230
Sturgis, S. D.	KBNB	1240
Stuttgart, Ark.	KWAK	1280
Suffolk, Va.	WLPM	1460
Sullivan, Ind.	WKQV	1550
Sullivan, Mo.	KSTI	1560
Sulphur, La.	KIKS	1310
Sulphur Springs, Tex.	KSST	1250
Summerville, Ga.	WGTA	950
Summerville, S. C.	WALS	980
Sumner, Wash.	KDFL	1560
Sumter, S. C.	WFIG	1290
	WDXJ	1240
	WSSC	1340
Sunbury, Pa.	WTO	1070
Sunnyside, Wash.	KREW	1230
Sun Valley, Ida.	KSKI	1340
Superior, Nebr.	KRFS	1600
Superior, Wis.	WDSM	710
	WIGL	970
	WJIC	1270
	WAKK	1320
	KSUE	1240
Susanville, Calif.	WGSB	1490
Sutton, W. Va.	WIAT	800
Swainsboro, Ga.	WDEH	800
Sweetwater, Tenn.	KXOX	1240
Sylacauga, Ala.	WFEB	1340
	WV	1400
	WMSJ	1480
Sylvia, N. C.	WSYL	1490
Sylvania, Ga.	WSYL	1490
Sylvester, Ga.	WQGA	1540
Syracuse, N. Y.	WHEB	620
	WFBL	1390

Location	C.L.	Kc.
	WNDR	1260
	WOLF	1490
	WSYR	570
	WTAB	1370
	KMO	1360
	KTAC	850
	KTN	1400
	KVI	1730
Taft, Calif.	KTKR	1310
Tahlequah, Okla.	KTLL	1350
Tahoe Valley, Calif.		
	KTHO	590
	WEYY	1580
Tallahadee, Ala.	WUZZ	1230
Tallahassee, Fla.	WMEN	1250
	WONS	1410
	WTAL	1450
	WTNT	1270
Tallahassee, Ala.	WTLS	1300
Tallahua, Fla.	KTLD	1360
Tampa, Fla.	WALT	1110
	WV	1250
	WYOU	550
	WFLA	970
	WHBO	1050
	WINQ	1010
	WTMP	1150
	WSOL	1300
Taos, N. Mex.	WY	1250
Tarboro, N. C.	WCPS	760
Tarpon Springs, Fla.	WCWR	1470
Tasley, Va.	WESR	1350
Taunton, Mass.	WPEP	1570
Tawas City, Mich.	WIDS	1480
Taylor, Tex.	WY	1250
Taylorville, N. C.	WSTH	880
	WTLK	1570
Taylorville, Ill.	WTIM	1410
Tazewell, Tenn.	WNTT	1250
Tazewell, Va.	WTZE	1470
Tell City, Ind.	WTGJ	1280
Tempe, Ariz.	KYND	1580
Tempe, Ariz.	KYND	1580
Temple, Tex.	KTEM	1400
Terre Haute, Ind.	WBOW	1230
	WAAC	1300
	WTHI	1480
Terrell, Tex.	KTER	1570
Terrytown, Nebr.	KR	1400
Texarkana, Ark.	KOS	790
Texarkana, Tex.	KMC	740
	KATQ	940
	KTFS	1400
Texas City, Tex.	KTLN	920
Thayer, Mo.	KALM	1290
The Dalles, Ore.	KODL	1440
	KL	1300
Thermopolis, Wyo.	KTRR	1490
	KTHE	1240
Thief River Falls, Minn.	KTRF	1230
Thibodaux, La.	KTIB	680
Thomaston, Ga.	WSFT	1220
	WV	1250
	WTHN	1500
Thomasville, Ala.	WJDB	830
Thomasville, Ga.	WPAX	1240
	WLD	730
Thomasville, N. C.	WTNC	990
Thomson, Ga.	WTWA	1240
Three Rivers, Mich.		
	WLKM	1510
Ticonderoga, N. Y.	WIPS	1250
Tiffin, Ohio	WTF	1600
Tifton, Ga.	WTFI	1340
	WVGS	1430
Tillamook, Ore.	KTIL	1590
Titusville, Fla.	WRMF	1050
Titusville, Pa.	WTV	230
Toccoa, Ga.	WLET	1420
	WNES	630
Toledo, Ohio	WOHD	1470
	WSPD	1370
	WTO	1560
	WCWA	1230
	WV	1250
Toledo, Ore.	KTDD	1230
Tolleson, Ariz.	KRDS	1190
Tomah, Wis.	WTMB	1460
Tompkinsville, Ky.	WTKY	1370
Tooele, Utah	KDYL	990
Topeka, Kans.	WIBW	580
	WV	1470
	WREN	1250
	KTOP	1490
Toppenish, Wash.	KENE	1490
Torrington, Conn.	WTOR	610
Torrington, Wyo.	KGDS	1490
Towanda, Pa.	WTF	1550
Townsend, Md.	WAE	1520
Trail, B. C.	CJAT	610
Travelers Rest, S. C.	WBRR	1580
Traverse City, Mich.	WTCM	1400
	WCCN	1310
Trenton, Mo.	KTNN	1600
Trenton, N. J.	WAT	1300
	WRUD	1260
	WTTM	920
Trinidad, Colo.	KCRT	1240
Troy, Ala.	WTFB	970
Troy, N.		

Location	C.L. Kc.	Location	C.L. Kc.	Location	C.L. Kc.	Location	C.L. Kc.
	WTRY 980	Victorville, Calif.	KCIN 1590	Waycross, Ga.	WACL 570	Willoughby, Ohio	WELW 1330
	WXWK 1600	Vidalia, Ga.	WVOP 970	Waynesboro, Ga.	WYK 1230	Willow Springs, Mo.	KUKU 1330
Troy, N. C.	WJRM 1390	Vieques, P.R.	WIVV 1370	Waynesboro, Ga.	WBRO 1310	Willows, Calif.	KIQS 1560
Truckee, Calif.	KHOE 1400	Ville Platte, La.	KVPI 1050	Waynesboro, Miss.	WABO 990	Wilmington, Del.	WAMS 1380
Trumann, Ark.	KTMN 1530	Vincennes, Ind.	WAOV 1450	Waynesboro, Pa.	WAYZ 1380		WDEL 1150
Truth or Consequences, New Mexico	KWBB 1380	Vineland, N.J.	WVWB 1350	Waynesboro, Va.	WAYB 1490		WILM 1450
Tryon, N.C.	KCHS 1400	Vinita, Okla.	KVIN 1470	Waynesburg, Pa.	WANB 1580	Wilmington, N.C.	WTUX 1290
Tucson, Ariz.	KTCU 1400	Vinton, Va.	WKBA 1500	Waynesville, Mo.	KJFW 1390		WKWY 630
	KXEW 1600	Virginia, Minn.	WHLB 1450	Waynesville, N.C.	KZEE 1220		WWSL 1490
	KAIR 1490	Virginia Beach, Va.	WKVK 1550	Weatherford, Tex.	KJFJ 1570	Wilmington, O.	WMW 1090
	KCEE 790	Viroqua, Wis.	WISV 1380	Weed, Calif.	KDAD 800	Wilson, N.C.	WGTM 590
	KTAN 590	Vivian, La.	KONG 1400	Weirton, W.Va.	WEIR 1430		WLLY 1350
	KCUB 1290	Vivian, La.	KNCB 1600	Weiser, Idaho	KWEI 1260		WVOT 230
	KEVT 690	Waco, Tex.	WACO 1580	Welch, W.Va.	WVE 1340	Winchester, Ky.	WVOT 230
	KHQS 940		KAWA 1010		WVCF 1400	Winchester, Tenn.	WCOT 1340
	KMDP 1330		KBGO 1580		WCNF 1400	Winchester, Va.	WHPL 610
	KKFI 1550		KGTX 1380		WNBT 1430		WWRB 1350
	KTKT 990		KWAX 920		WNOV 1390	Windermere, Fla.	WVCF 1480
	KOLD 1450		WADE 1210		WNSV 760	Winder, Ga.	WIMO 1300
Tucumcari, N. Mex.	KTNM 1400		KWLG 1530		WPKQ 560	Windom, Minn.	KDML 1300
Tulare, Calif.	KDOK 1270		KBMW 1450		KUEN 900	Winfield, Ala.	WSOR 1480
	KGEE 1370		KMVI 550		KMEL 1340	Winfield, Ala.	WEZQ 1300
Tulia, Tex.	KTUE 1260		KAHU 940			Winfield, Kan.	KNIC 1550
Tulahoma, Tenn.	WJIG 740		KWGO 1000			Winnemucca, Nev.	KNWA 1400
Tulsa, Okla.	KAKC 970		KWAL 620			Winnfield, La.	KVCL 1270
	KOME 1300		WLSE 1400			Winnier, S.Dak.	KWYR 1260
	KRMG 740					Winnssboro, La.	KMAR 1570
	KELI 1430					Winnssboro, S.C.	KNWO 1230
	KVOD 1170					Winona, Minn.	KAGE 1380
	KFMJ 1050					Winona, Minn.	WDNA 1570
Tupelo, Miss.	WELO 580					Winona, Minn.	KVNC 1010
	WTUP 1490					Winona, Minn.	KINO 1230
	KCEY 1390						
Turlock, Calif.	KCEY 1390						
Tuscaloosa, Ala.	WJRD 1150						
	WACT 1420						
	KGEB 1280						
	WTUG 790						
	WTBC 1230						
Tuscumbia, Ala.	WVNA 1590						
	WRCK 1410						
	WABT 580						
Tuskegee, Ala.	KDHI 1250						
Twenty-Nine Palms, Calif.	KTFI 1270						
	KTHI 1270						
Twin Falls, Idaho	KLIX 1310						
	KEEP 1450						
	WTRW 1590						
Two Rivers, Wis.	KZAK 1330						
Tyler, Tex.	KDOK 1490						
	KTRB 600						
	KZEY 890						
	WTRN 1340						
Urbane, Pa.	WUND 1540						
Urbansville, Ohio	WBTC 1540						
	KUKI 1400						
Ukiah, Calif.	KMSL 1250						
	KULY 1420						
Ulysses, Kan.	WVU 1460						
Union, S.C.	WENK 1240						
Union City, Tenn.	WMB5 590						
Uniontown, Pa.	WILL 580						
Urbana, Ill.	WID5 1580						
	WIBX 950						
Utica, N.Y.	WVU 1550						
	WRUN 1150						
	WTLB 1310						
	WUPR 1530						
Utuaedo, P.R.	KVOD 1400						
Uvalde, Tex.	W5VM 1490						
Uvalde, N.C.	WGOV 950						
Valdosta, Ga.	WGG 910						
	WJEM 1150						
	WVLD 1450						
Valentine, Nebr.	KVSH 940						
Vallejo, Calif.	KNBA 1190						
Valley City, N. Dak.	KDVC 1490						
Valparaiso-Nileville, Fla.	KNSN 1340						
Valparaiso, Ind.	WAYK 1500						
	WNWI 1080						
	KKFD 1580						
Van Buren, Ark.	WMTG 730						
Van Cleve, Ky.	WKKS 1590						
Vanceburg, Ky.	KISN 910						
Vancouver, Wash.	KKEY 1150						
	KGAR 1550						
	WPMB 1500						
Vandalia, Ill.	WERT 1220						
Van Wert, Ohio	WAMR 1320						
Venice, Fla.	KVEN 1450						
Ventura, Calif.	KUDU 1590						
	KUSO 690						
Vermillion, S.Dak.	KVEL 1250						
Vernal, Utah	KVSA 1380						
Vernon, Ala.	KVWC 1490						
Vernon, Tex.	WAXE 1370						
Vero Beach, Fla.	WTTB 1490						
	W0BC 1420						
Vicksburg, Miss.	WVIM 1490						
	KNAL 1410						
Victoria, Tex.	KVIC 1340						

U. S. FM Stations by States

Location	C.L. Mc.	Location	C.L. Mc.	Location	C.L. Mc.	Location	C.L. Mc.
ALABAMA							
Anniston	WHMA-FM 100.5	Anniston	WHMA-FM 100.5	Clanton	WBRC-FM 106.9	Decatur	WDRM 102.1
Athens	WJOF 104.3	Athens	WJOF 104.3	Cullman	WCRT 96.5	Decatur	WRSA 96.9
Bay Minette	WATM-FM 104.1	Bay Minette	WATM-FM 104.1		WRFH 83.7	Dotham	WOOF-FM 99.7
Birmingham	WBCA-FM 105.5	Birmingham	WBCA-FM 105.5		WKLF-FM 97.7	Fairhope	WAFB-FM 92.1
	WAPI-FM 99.5	Birmingham	WAPI-FM 99.5		WFMH-FM 101.1	Florence	WJOI-FM 107.3

WHITE'S RADIO LOG

Location	C.L.	Mc.
Gadsden	WJBY-FM	103.7
Homewood	WJLN	104.7
Huntsville	WAHR	99.1
	WNDA	92.9
Jackson	WHOD-FM	104.9
Mobile	WKRQ-FM	99.9
	WMFC-FM	98.5
	WLPR	96.1
	WFLM	108.9
Montgomery	WAJM	101.3
	WHHY-FM	101.9
	WLAY-FM	105.5
Muscle Shoals	WPJC-FM	98.3
Scottsboro	WHBB-FM	100.1
Selma	WHPD	100.1
	WMLS-FM	98.3
Sylacauga	WVNA	100.3
Tusculum	WTBO-FM	95.7
Tuscaloosa	WUOA	*91.7
	WACT-FM	105.5

ALASKA

Location	C.L.	Mc.
Anchorage	KNIK	105.5
	KBVR-FM	102.1
	KHAR-FM	103.9
College	KUAC	104.9

ARIZONA

Location	C.L.	Mc.
Globe	KWJB-FM	100.3
Mesa	KBUZ-FM	104.7
	KMND-FM	93.3
Phoenix	KRFM	95.5
	KFCA	*88.5
	KITH	101.3
	KOOL-FM	94.5
	KNIX-FM	102.5
	KOY-FM	92.5
	KMEQ	96.9
	KTAR-FM	98.7
	KYEW	93.3
	KHEP-FM	101.5
	KVWM	93.5
Show Low	KUPD-FM	97.9
Tempe	KFMN	96.9
Tucson	KCEE-FM	96.1
	KSOM	92.9
	KVOA-FM	93.7

ARKANSAS

Location	C.L.	Mc.
Blytheville	KLCN-FM	96.1
Dardanelle	KCAB-FM	102.3
El Dorado	KRIL	98.3
	KELD-FM	103.1
Fayetteville	KFAV-FM	92.1
	KNWA	103.9
Ft. Smith	KFPW-FM	94.9
	KMAG	99.1
	KTCS-FM	99.9
Harrison	KHOZ-FM	102.9
Hot Springs	KBRH-FM	96.7
	KGUS	97.5
Jacksonville	KGMR-FM	100.3
Jonesboro	KBTM-FM	101.9
	KASU	91.9
	KNEA-FM	107.9
Little Rock	KARK	103.7
	KMYO-FM	95.7
Mammouth Springs	KAMS	103.9
Oseola	KOSE-FM	98.1
Pine Bluff	KOTN-FM	92.3
Siloam Springs	KUOA-FM	105.7

CALIFORNIA

Location	C.L.	Mc.
Akiah	KLIL	94.3
Alameda	KJAZ	92.7
Anaheim	KEZR-FM	95.0
Angwin	KANG	88.1
Apple Valley	KAVR-FM	102.3
Arcata	KTOD	*90.5
Atherton	KPEN	101.3
Auburn	KAFI	101.1
Avalon	KBIG	104.3
Bakersfield	KERN-FM	94.1
	KGEE-FM	97.5
	KIFM	96.5
Berkeley	KPFA	94.1
	KPFB	*89.3
	KPAT-FM	102.9
Bishop	KHUR	99.9
Bishop	KIBS-FM	100.7
Carlsbad	KARL-FM	95.9
Carmel	KRML-FM	101.7
Claremont	KSCP	*88.7
Coachella	KCHV-FM	93.7
El Cajon	KECR	93.3
Escondido	KOWN-FM	92.1
Fremont	KFMR	104.9

Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.
Fresno	KARM-FM	101.9		KBRG	105.3		WGTV	*90.1
	KCIB-FM	94.5		KABL-FM	98.1		WMAL-FM	107.3
	KFRE-FM	93.7		KKHI-FM	95.7		WOL-FM	98.7
	KMJ-FM	97.9		KSJO-FM	92.3		WRC-FM	93.9
	KXQR	102.7	San Jose	KRPM	98.5		WTOP-FM	96.3
Garden Grove	KTBT	94.3		KSIS	100.7		WWOC-FM	101.1
Glendale	KFMU	97.1		KPLX	96.5			
	KUTE	91.9		KEEN-FM	100.3			
Hayward	KTUX	101.7	San Luis Obispo	KATY-FM	98.1			
Inglewood	KHSJ-FM	105.5		KSBJ-FM	93.3	Atlantic Beach	WKTZ-FM	96.1
La Canada	KTYM-FM	103.9	San Mateo	KCSM	*90.9		WAQB-FM	104.9
LaSerra	KUNF	*88.9		KUFY	107.7	Belle Glade	WSWN-FM	93.5
	KSDA	*89.7	San Rafael	KTIM	100.9	Boca Raton	WWOG	99.9
	KCVR-FM	97.7	Santa Ana	KWIZ-FM	96.7	Bradenton	WBRD-FM	103.3
	KLOM-FM	92.3		KYMS	106.3	Clear Water	WTAN-FM	95.7
Long Beach	KJLH	102.3	Santa Barbara	KCSB-FM	91.1	Cocoa	WEZY-FM	99.3
	KLON	*88.1		KDB-FM	93.7	Cocoa Beach	WXBR	101.1
	KNQB	97.9		KMUZ	103.3		WRKT-FM	104.3
Los Altos	KPGM	97.7		KTMS	97.5	Coral Gables	WVCG-FM	105.1
	KFCJ	88.7	Santa Clara	KSCU	*90.1	Crestview	WAAZ-FM	104.9
Los Angeles	KABC-FM	95.5		KREP	105.7	Daytona Beach	WNDB-FM	94.5
	KCBI	107.5	Santa Cruz	KSCO-FM	99.1		WMFJ-FM	101.1
	KBCA	105.1	Santa Maria	KXFM	99.1	De Funiak Springs	WZEP-FM	103.9
	KBMS	105.9		KSMA-FM	102.5	Fort Lauderdale	WWIL-FM	103.5
	KBH	98.7	Santa Monica	KGRV	*98.9		WFLM	105.9
	KFAC-FM	92.3		KSRF	103.1		WFTL-FM	106.7
	KFOX-FM	100.3	Sierra Madre	KMAX	107.1		WMJR	100.7
	KGLA	*103.5	Stanford	KZSU	*90.1		WINK-FM	96.9
	KHJ	101.1	Stockton	KUOP	*91.3	Ft. Meyers	WYR-FM	101.9
	KMET	94.1		KSTN-FM	107.3	Ft. Pierce	WARN-FM	98.7
	KMLA	100.3		KTHO-FM	103.1	Fl. Walton Beach		
	KNX-FM	93.1	Tahoe Valley	KNJO	92.7		WFTW-FM	99.3
	KPFK	*90.7	Thousand Oaks	KNHS	*89.7	Galvesville	WRUF-FM	*104.1
	KPOL-FM	93.9	Torrance	KDRF	106.7	Jacksonville	WJAX-FM	95.1
	KRRM	102.7	Tulare	KGEN-FM	94.9		WQIK-FM	99.1
	KRKK-FM	96.3		KOSO	93.1		WVY-FM	92.5
	KUSC	*91.5	Turlock	KDHI-FM	95.7		WKIZ-FM	92.5
	KXLU	*89.1	Twenty-Nine Palms	KUKI-FM	93.5	Key West	WVFM	94.1
	KHOF	99.5		KVEN-FM	100.7	Lakeland	WTLN-FM	95.3
Los Angeles-Avalon	KBIG-FM	104.3	Ukiah	KONG-FM	92.9	Maitland	WTOT-FM	100.9
Los Banos	KLBS-FM	95.9	Ventura-Oxnard	KDFM	92.1	Marianna	WMBB-FM	102.3
Los Gatos	KLGS	95.3	Walnut Creek	KSGV	98.3	Melbourne	WKAT-FM	93.3
Marysville	KRFD	92.7	West Covina	KATT	95.3	Miami	WGBS	96.3
Merced	KWIP-FM	101.5	Woodland				WIOD-FM	97.3
Modesto	KBEE-FM	103.3					WTHS	*91.7
	KTRB-FM	104.1					WEDR	99.1
Monterey	KHFR	96.9					WWPB	101.5
Newport Beach	KOCM	103.1	Boulder	KRNW	97.3		WKAT-FM	93.1
Northridge	KEDC-FM	88.5	Colorado Springs	KRCS	*91.5	Miami Beach	WAEZ-FM	94.9
Oakland	KUDE	102.1		KKFS	*90.5		WGOS	93.9
Oceanside	KUDE	102.1		KVOR-FM	92.9	Milton	WXBM-FM	102.3
Ontario	KOYA	93.5		KPIK-FM	94.3	Mt. Dora	WHY-FM	107.7
Oxnard	KPMJ	104.7		KRDO-FM	95.1	Naples	WNFM	94.5
Pacific Grove	KMBY-FM	104.9		KRYT-FM	101.9	Ocala	WMOP-FM	93.7
Pasadena	KPCS	89.3		KZFM	94.1	Okeechobee	WLMC	103.1
	KPPC-FM	106.7	Cortez	KFMI-FM	98.5	Orlando	WDBO-FM	92.3
Palmdale	KDEP-FM	104.7	Denver	KLIR-FM	100.3		WHOO-FM	96.5
Palm Springs	KCEP	91.9		KLZ-FM	106.7		WKIS-FM	103.3
Redding	KKOP	93.5		KDEN-FM	99.5		WWSQ	105.1
Redondo Beach	KCAL-FM	96.7		KOA-FM	103.5	Palm Beach	WWOS-FM	97.9
Redlands	KUOR-FM	*89.1		KOSI-FM	101.1		WPBA-FM	107.1
	KLOA-FM	105.5		KTGM	105.1	Panama City	WMAL-FM	92.9
Ridgecrest	KBBL	99.1		KIMM-FM	95.5		WDLF-FM	107.5
Riverside	KACE-FM	92.7		KBPI	95.9	Pensacola	WPFX-FM	94.1
	KDUD	92.5		KCSU-FM	90.9		WCOA-FM	100.7
Sacramento	KCRA-FM	96.1	Ft. Collins	KFMF	93.9	St. Augustine	WDFW	97.7
	KERS	*88.9		KREX-FM	92.3	St. Petersburg	WGNB	101.5
	KFBK-FM	96.9	Grand Junction	KLAK-FM	107.7		WTCX	99.5
	KJML	106.5	Lakewood	KLMO-FM	104.3		WPIN-FM	107.3
	KEBR	100.5	Longmont	KLOW-FM	102.3	Sarasota	WSPB-FM	106.3
	KHIO	105.1	Loveland	KCMS-FM	102.7		WSEB	105.3
	KJML	95.1	Manitou Springs	KAVI-FM	95.9	Sebring	WDFW	97.7
	KRAI-FM	92.9	Rocky Ford			Tallahassee	WFSU-FM	*91.5
	KSFM	96.9					WBGW-FM	98.9
	KXRO	98.5				Tampa	WDAE-FM	100.7
	KXOA-FM	107.9					WEM1	94.9
Salinas	KSBW-FM	102.5	Bridgeport	WJZZ	99.9		WFLA-FM	93.3
	KRSA-FM	100.7		WPKN	88.1		WPKM	104.7
	KERR	103.9	Brookfield	WGHF	95.9		WUSF	89.7
San Bernardino	KVCR	*91.9	Danbury	WLAD-FM	98.3		WFSU-FM	*91.5
	KFMW	99.9	Darien	WDRM	95.9		WBGW-FM	98.9
	KEBS	*89.5	Farfield	WSHU	*91.1		WDAE-FM	100.7
	KRCS	95.1	Hamden	WDEE	101.3		WEM1	94.9
	KVFM	94.3	Hartford	WHCN	105.9	West Palm Beach	WPBF	107.9
San Diego	KGOB-FM	94.1		WDRC-FM	102.9	Winter Haven	WXKL	92.5
	KFGF-FM	90.7		WCCC-FM	104.9	Winter Park	WPRK	*91.5
	KFMX	96.5		WLAE	93.7		WLOQ	103.1
	KGB-FM	101.5		WRTC-FM	*89.3			
	KITT	105.3		WVIC-FM	96.5			
	KJLM	98.1		WBSI	95.7			
	KLRO	94.9	Meriden	WESU	98.1	Albany	WGFC-FM	104.3
	KFR1	106.5	Middletown	WNHC-FM	99.1		WJZ	96.5
	KSDS	*88.3	New Haven	WYBG-FM	94.3	Americus	WDEU-FM	94.3
	KBBW	102.9		WDRN	95.9	Athens	WGAF-FM	102.5
	KSDO-FM	103.7	Norwalk	WSTC-FM	96.7		WDDL-FM	104.7
	KSEA	97.3	Stamford	WHUS	*90.5	Atlanta	WABE	*90.1
	KVFM	94.3	Stors	WATH-FM	92.5		WAVO-FM	94.9
San Fernando	KALW	*91.7	Waterbury	WVCO-FM	104.1		WPLO-FM	103.3
	KBBB	105.3		WVMM	107.9		WGKA-FM	92.9
San Francisco	KCBS-FM	88.9	Westport				WSB-FM	98.5
	KDFC	102.1					WFLA-FM	99.7
	KEAR	97.3					WLAU-FM	105.7
	KFOG	104.5					WBBQ-FM	99.3
	KFRC-FM	106.1					WIGC-FM	100.7
	KLO-FM	103.7					WYNN-FM	101.5
	KNBR-FM	99.7					WCHK-FM	105.5
	KMPX	106.9					WLBB-FM	102.3
	KOIT	93.3					WRBL-FM	102.9
	KPEN	101.3					WGBA-FM	107.3
	KRON-FM	96.5					WCOA-FM	99.3
	KSRF	94.9					WXLI-FM	92.7
	KXKK	88.5					WDUN-FM	103.9
	KCMA	*90.3					WWQT	97.1
							WKEU-FM	99.9

FLORIDA

COLORADO

CONNECTICUT

GEORGIA

DELAWARE

D. C.

WHITES RADIO LOG

Location	C.L.	Mc.
Lawrence	WCCM-FM	93.7
Lowell	WLLH-FM	99.5
Lynn	WLYM-FM	101.7
Medford	WHIL-FM	107.9
New Bedford	WBSM-FM	97.3
	WNBH-FM	98.1
N. Adams	WMNB-FM	100.1
N. Attleboro	WRLM	93.3
Northampton	WHMP-FM	99.3
Pittsfield	WYRB-FM	105.5
	WBRK-FM	101.7
Plymouth	WPLM-FM	99.1
S. Hadley	WHMC	*88.5
Springfield	WHYN-FM	93.1
	WCSB	*88.9
	WMAS-FM	94.7
Taunton	WRLM	97.3
Waltham	WCRB-FM	102.5
W. Yarmouth	WOCB-FM	94.9
Williamstown	WCFM	*91.3
Winchester	WHSR-FM	*91.9
Worcester	WAAB	107.3
	WSRS	96.1

MICHIGAN

Adrian	WLEN	103.9
Alma	WFYC-FM	104.9
Alpena	WHBS	107.7
	WATZ-FM	97.5
Battle Creek	WKFR-FM	103.3
Big Rapids	WBRR-FM	100.9
Ann Arbor	WJOM	*91.7
Bay City	WBCM-FM	96.1
	WNEM-FM	102.5
Benton Hrbr.	WHFB-FM	99.9
Birmingham	WFBI	94.7
Charlotte	WCER-FM	92.7
Cheboygan	WCBY-FM	105.1
Coldwater	WTVB-FM	98.3
Dearborn	WKNR-FM	100.3
Detroit	WDET-FM	*101.9
	WBFG	98.7
	WCHD	105.9
	WDTM	106.7
	WABX	95.5
	WDTR	*90.9
	WGPM	107.5
	WJBK-FM	98.1
	WNUZ	103.5
	WGPR	97.9
	WJR-FM	96.3
	WOMC-FM	104.3
	WQRS-FM	105.1
	WRMK-FM	98.7
	WWJ-FM	97.1
	WXYZ-FM	101.1
	WCAR-FM	92.3
E. Lansing	WKAR-FM	90.5
	WSWM	99.1
	WVIC-FM	95.7
Flint	WFBE	*95.1
	WGMZ-FM	107.9
	WWRP-FM	105.5
Grand Rapids	WFUR-FM	102.9
	WJEF-FM	93.7
	WLAV-FM	96.9
	WYON	101.3
	WOOD-FM	105.7 (s)
	WVGA-FM	104.1
	WXTO-FM	97.9
	WKLW-FM	95.7
Greenville, Mich.	WPLB-FM	107.3
Hancock	WMPL-FM	93.5
Highland Pk.	WHPR	*88.1
Holland	WJBL-FM	94.5
	WHTC-FM	96.1
Houghton Lake	WJGS	98.5
Interlochen	WGVA	103.1
	WIAA	89.7
Jackson	WIBM-FM	94.1
	WKHM-FM	106.1
Kalamazoo	WMUK	102.1
	WSEO-FM	105.5
Lansing	WIMM-FM	97.5
	WILS-FM	99.7
	WYFE	100.7
Marquette	WNMR	90.1
	WDMJ-FM	95.7
Midland	WQDC-FM	99.7
Mount Clemens	WRBB-FM	102.7
Mount Pleasant	WCMU	90.1
Muskegon	WFMF	106.1
Oak Park	WLDM	95.5
Owaso	WOAP-FM	103.9
Petoskey	WJML	89.9
	WMBN-FM	96.7
Port Huron	WHLS-FM	107.1
Royal Oak	WOAK	*89.3
	WOMC	104.3

Location	C.L.	Mc.
Saginaw	WSAM-FM	98.1
Spring Arbor	WSAE	*89.3
Sturgis	WSTR-FM	103.1
Traverse City	WDR-FM	101.9
	WTOM-FM	103.5
Warren	WPHS	91.5
Ypsilanti	WEMU	88.1

MINNESOTA

Anoka	KTWN	107.9
Brainerd	KLIZ-FM	97.1
Golden Valley	KQRS-FM	92.5
Mankato	KMSO	*90.5
	KYSM-FM	103.5
Minneapolis-St. Paul	KTIS-FM	98.5
	KWFM	97.1
	KNOF	95.3
	WPBC-FM	101.3
	KSTP-FM	94.5
	WAYL	93.7
	WCTS-FM	100.3
	KVOX-FM	99.9
	WNUJ-FM	93.1
	KCUE-FM	105.5
	WPBC-FM	101.3
	KROC-FM	106.9
	KNXR	97.5
	KFAM-FM	104.7
	KRSI-FM	104.1
	KWLM-FM	105.5
	KWOA-FM	95.1

MISSISSIPPI

Biloxi	WVMI-FM	106.3
Forest	WQST	92.5
Greenwood	WSWG	99.1
Gulfport	WROA-FM	97.1
Hattiesburg	WHSY-FM	104.5
Jackson	WJDX-FM	102.9
	WLSI-FM	96.3
	WWHO	94.7
Kosciusko	WKQZ-FM	105.1
Laurel	WNLS-FM	100.3
Louisville	WLSA-FM	107.1
Meridian	WMMI	*88.1
Miss Point	WACY-FM	104.9
Natchez	WNAT-FM	95.1
New Albany	WNAU-FM	103.5
Pascagoula	WPMP-FM	99.1
Poulatville	WRPM-FM	107.9
Pontotoc	WSEL-FM	96.7
Tupelo	WELD-FM	98.5
Vicksburg	WQMV	98.7

MISSOURI

Buffalo	KBFL	91.3
Cane Girardeau	KZYM-FM	102.9
Carrollton	KAOL-FM	101.1
Clayton	KFUD-FM	99.1
Columbia	KWVC-FM	90.5
Crestwood	KSHE	94.7
El Dorado Springs		
	KESM-FM	101.7
	KBTC-FM	99.3
Houston	WMBH-FM	96.1
Joplin	KSYN	92.5
Kansas City	KCMO-FM	94.9
	KBXE	104.3
	KTRS	90.1
	WDAF-FM	102.1
	CKMK	93.3
	KCUR-FM	*89.3
	KMBC-FM	99.7
	KPRS-FM	103.3
	KXTR	96.5
	KBAA-FM	98.9
	KRMS-FM	93.5
	KSQZ	*88.1
	KWOC-FM	94.5
	KCLU-FM	94.3
	KMSM	*88.5
	KUSN-FM	105.1
	KCFM	93.7
	KACD	107.7
	KADI	96.5
	WAMV-FM	101.1
	WIL-FM	92.3
	KSLL	*91.5
	KSTL-FM	98.1
	KRFD	106.9
	KSIS-FM	92.1
	KTTS-FM	94.7
	KTXR	101.5
	KLPW-FM	101.7
	KFBF	97.7
	KWPM-FM	93.9

MONTANA

Belgrade	KGVM-FM	96.7
Billings	KURL-FM	97.1
Bozeman	KBHF	93.7
Great Falls	KOPR-FM	106.3
Missoula	KUFM	*88.1

NEBRASKA

Beatrice	KWBE-FM	92.9
Columbus	KJSK-FM	101.1
Hastings	KICS-FM	93.5

Location	C.L.	Mc.
Kearney-Holdrege	KRNY-FM	98.9
Lexington	KRUN-FM	93.1
Lincoln	KFMQ	95.3
	KWHG	102.7
Omaha	KQAL-FM	94.3
	KFAB-FM	99.9
	KGBI-FM	100.7
	KDWH-FM	94.1
	WQW-FM	92.3
	KICN	96.1
Scottsbluff	KNEW-FM	94.1

NEVADA

Las Vegas	KORK-FM	97.1
	KRGN	101.9
	KLUC-FM	98.5
	KVEG-FM	92.3
Reno	KNEV	95.5
	KUNR	88.1

NEW HAMPSHIRE

Berlin	WNOW-FM	103.7
Claremont	WTSV-FM	106.1
Durham	WUWH	*93.3
Exeter	WPEA	*88.1
Laconia	WLNH-FM	98.3
Keene	WKNE-FM	103.7
Manchester	WKRR-FM	95.7
	WGIR-FM	101.1
Mt. Washington	WMTW-FM	94.9
Nashua	WOTW-FM	106.3
Portsmouth	WHEB-FM	100.3

NEW JERSEY

Asbury Park	WJLK-FM	94.3
	WHTG-FM	105.5
Atlantic City	WFGP-FM	96.9
	WGMG	103.7
	WRNJ	95.1
Bridgeton	WSNJ-FM	107.7
Camden	WKDN-FM	106.9
Dover	WDA-FM	105.5
E. Orange	WFLU	91.1
Eatontown	WHTG-FM	106.3
Franklin	WLVP	102.3
Franklin Lakes	WRRR	88.7
Glassboro	WGLS-FM	*89.7
Hackettstown	WNTI	*91.9
Hanover	WHPH	*90.3
Long Branch	WRLB	107.1
Millville	WMBV-FM	97.3
Newark	WHBI	105.9
	WFME	94.7
	WVNJ-FM	100.3
	WBGO	88.3
New Brunswk.	WCTC-FM	*93.3
Paterson	WPAI-FM	93.1
Princeton	WRFB	103.3
Red Bank	WFHA-FM	106.3
South Orange	WSOU	*89.5
Trenton	WBDU-FM	101.5
	WTOA	97.5
	WTSR	99.7
	WTTM-FM	94.5
Wildwood	WCMF-FM	100.7
Zarephath	WAWZ-FM	99.1

NEW MEXICO

Alamogordo	KXXI	94.3
Albuquerque	KANW	*89.1
	KBNN	95.5
	KDEF-FM	94.1
	KRST	92.3
	KHFM	96.3
	KOAT-FM	100.3
	KOB-FM	93.3
	KIQM-FM	99.9
	KHOB-FM	95.7
	KRSN-FM	98.5
	KLEA-FM	101.7
	KMFM	97.9
	KBIM-FM	94.9
	KSNN	95.5
	KKIT-FM	99.3
	KRWG	91.7

NEW YORK

Albany	WAMC	*90.3
	WHLR	103.1
Auburn	WMBO-FM	106.9
Babylon	WTFM	103.5
	WGSM-FM	94.3
	WGU-FM	102.3
	WNBF-FM	98.1
	WHRW	90.5
	WKOP-FM	99.1
	WNYE	*91.5
	WCWP	*88.1
	WBEN-FM	102.5
	WDXC	99.5
	WBFO	*88.7
	WBUF	93.3
	WBRB	94.1
	WGR-FM	96.9
	WTSL-FM	103.3
	WVOL-FM	104.1
	WYSL-FM	103.3
	WDIF	96.1

Location	C.L.	Mc.
Canton	WSLU	*89.7
Central Square	WCSQ	*89.3
Cherry Valley	WJVV	101.5
Clinton	WHCL-FM	88.7
Corning	WCLI-FM	106.1
Cortland	WKRT-FM	99.9
Denew	WBLK-FM	93.7
DeRuyter	WJUN	95.1
Elmira	WECW	*88.1
	WEHH-FM	94.3
	WENY-FM	92.7
	WSHS	*90.3
Floral Park	WLIR	92.7
Garden City	WGSU	88.3
Geneseo	WHLI-FM	98.3
Hempstead	WHLI-FM	98.3
Hornell	WWHG-FM	105.3
Ithaca	WHCU-FM	97.3
	WICB	*91.7
	WEIV	103.7
	WVBR-FM	93.5
Jamestown	WJTN-FM	93.3
	WJTV	101.7
Johnstown	WIZR-FM	104.9
Kenmore	WYSL-FM	103.3
Kingston	WGHQ-FM	94.3
Lake Success	WTFM	103.5
Liberty	WVOS-FM	95.9
Loudonville	WVCR-FM	99.1
Middletown	WASD-FM	107.1
Mt. Kisco	WRNW	107.1
	WVIP-FM	106.3
New Rochelle	WVOX-FM	93.5
New York	WABC-FM	106.3
	WBAI	99.5
	WCBS-FM	101.1
	WED-FM	90.7
	WFUV	90.7
	WHOM-FM	92.3
	WKCR-FM	*89.9
	WLIB-FM	107.5
	WNCN	104.3
	WNW-FM	102.7
	WNBC-FM	97.1
	WNYC-FM	93.9
	WNYE	91.1
	WOR-FM	98.7
	WPIX-FM	101.9
	WQXR-FM	96.3
	WRFM	105.1
	WRRB	107.7
Niagara Falls	WHLDFM	98.5
Norwich	WCHN-FM	103.9
Osageo	WHDL-FM	95.7
Plattsburgh	WQSE	104.9
Patchogue	WEAV-FM	99.9
	WALK-FM	97.5(s)
	WPAI-FM	106.1
Peekskill	WLNA-FM	100.7
Potsdam	WTSI-FM	91.1
Poughkeepsie	WKIP-FM	104.7
	WEOK-FM	101.5
Riverhead	WAPC-FM	103.9(s)
Rochester	WHEM	98.9
	WBFB-FM	92.5
	WCMF	96.5
	WIRQ	90.9
	WNYR-FM	101.3
	WROC-FM	97.9
	WRUR-FM	90.1
	WVOR	100.5
Schenectady	WVOR	98.5
South Bristol	WMIS	95.7
Springville	WSPB	*88.1
Syracuse	WAER	*88.1
	WDDS-FM	93.1
	WONO	107.9
	WSYR-FM	94.5
	WFLY	92.3
	WRPI	*91.5
Utica	WRUN-FM	105.7
Wethersfield	WBIV	105.7
White Plains	WFAS-FM	103.9

NORTH CAROLINA

Albemarle	WABZ-FM	100.9
Asheboro	WGBR-FM	92.3
Asheville	WLOS-FM	104.3
Bridgeton	WVBB-FM	97.7
Burlington	WBBB-FM	

WHITE'S RADIO LOG

Location C.L. Mc.

TEXAS

Abernathy	KWGO-FM	99.5
Abiene	KACB-FM	91.1
	KFMN	99.3
	KWKC-FM	105.1
Amarillo	KGNC-FM	93.1
	KVII-FM	94.1
Austin	KHFI-FM	98.3
	KAZZ	95.5
	KTBC-FM	93.7
	KUT	90.7
Beaumont	KHCB-FM	105.7
	KAYD-FM	97.5
	KTRM-FM	95.1
	KJET-FM	107.7
	KLVI-FM	94.1
Big Spring	KWHI-FM	106.3
Brenham	KHPC	88.1
Brownwood	KFRN-FM	99.3
	KORA-FM	98.3
Bryan	KMSC	102.1
Clear Lake City	KCLE-FM	94.9
Cleburne	WTAW-FM	97.7
College Station	KNRO-FM	106.5
Conroe	KZFM	95.5
Corpus Christi	KXIT-FM	94.3
Dalhart	KIXL-FM	104.5
Dallas	KEIR	102.9
	KMAP	105.3
	KNEP	98.5
	KNUS	98.7
	KRLD-FM	92.5
	WFAA-FM	97.9
	WRR-FM	101.1
	KVTT	91.7
Del Rio	KBOX-FM	100.3
Denton	KDNT-FM	106.1
DiBoll	KSPFL-FM	95.5
Dumas	KDDD-FM	95.3
El Paso	KVOF-FM	88.5
	KTSM-FM	99.9
Ft. Worth	KHMS	94.7
	WBAP-FM	96.3
	KFJZ-FM	95.7
	KJIM-FM	102.1
	KCUL-FM	93.9
	KNOK-FM	107.5
	KTCU-FM	89.1
	KGAF-FM	94.5
	KGBC-FM	96.5
	KELT	94.3
	KGRI-FM	100.1
	KPAN-FM	106.3
Gainesville	KVIL-FM	103.7
Galveston	KHBR-FM	102.3
Harlingen	KDCHG-FM	102.9
Henderson	KHCB-FM	102.7
Herford	KHUL	95.7
Highland Park-Dallas	KFMK	97.9
	KODA-FM	99.1
	KLEF	94.5
	KOST	100.3
	KQBE	102.9
	KRBE	104.1
	KXYZ-FM	91.5
	KTRH-FM	101.1
	KUHF	91.3
	KBNO	93.7
Hillean	KLEN-FM	93.3
Humboldt	WIRJ-FM	102.3
Huntsville	KSAN-FM	101.7
Jasper	KXTJ-FM	102.3
Lake Jackson	KLJT	107.3
Lamesa	KPET-FM	100.3
Longview	KLUE-FM	105.7

Lubbock	KSEL-FM	93.7
	KBFM	96.3
	KXTX-FM	*91.9
Marshall	KMHT-FM	97.3
McAllen	KABG-FM	98.5
Midland	KRFM	97.9
	KMOD-FM	93.3
Mt. Pleasant	KIMP-FM	100.7
Muleshoe	KMUL-FM	103.1
Odessa	KQIP	96.7
	KWMO	99.1
	KOGV	91.3
	KOYL-FM	91.3
	KPLT-FM	99.3
	KLVL-FM	92.5
	KHBL	*88.1
	KFMP	93.3
	KPCAF-FM	98.5
	KWLW	93.9
	KSIT	97.5
	KISS	99.5
	KBER-FM	100.3
	KEEZ	97.3
	KAKJ-FM	98.1
	KITY	92.9
	KMFM	96.1
	KTDD-FM	101.3
	KBM-FM	97.9
	KYLE-FM	104.9
	KTAL-FM	98.1
	KOSY-FM	102.5
	KZAK-FM	93.5
	KDOK-FM	101.5
	KTXN-FM	92.1
	KKFC	95.5
	KWBU	*89.9
	KLUR	99.9
	KNTD	95.1

UTAH

Ephraim	KEPH	*88.9
Logan	KUSU-FM	*91.5
Ogden	KBOC	101.9
	KWCR-FM	*88.1
	KBYU-FM	*88.9
	KCPX-FM	98.7
	KLUB-FM	97.1
	KSL-FM	100.3
	KSOP-FM	104.3
	KWHO-FM	93.3

VERMONT

Burlington	WJOY-FM	*98.5
	WRUV	*90.1

VIRGINIA

Arlington	WAVA-FM	105.1
	WCCV-FM	97.5
	WVVV	104.9
Blocksburg	WINA-FM	95.3
Charlottesville	WTJU	91.3
Covington	KWKE-FM	100.9
Crewe	WVSV-FM	104.7
Farmville	WFLO-FM	95.7
Fredericksburg	WVFA-FM	101.5
Gretna	WMNA-FM	103.3
Grundy	WNRG-FM	97.7
Hampton	WVEC-FM	101.3
	WVOY	*88.3
	WEMC	*91.3
Harrisonburg	WWSA-FM	100.7
	WWOD-FM	100.1
	WDSM-FM	101.7
Lynchburg	WPRW-FM	106.7
Manassas	WMEV-FM	93.9
Marion	WNRVA-FM	96.3
Martinsville	WGH-FM	97.3
Newport News	WMTI	*91.5
Norfolk	WCMS-FM	100.5
	WNOR-FM	98.7
	WPHD	104.5
	WRVC	102.5
	WTAR-FM	95.7
	WXRJ	105.3
	WYFI-FM	99.7
	WAVY-FM	96.9
Portsmouth	WRAD-FM	101.7
Radford	WCOB	98.1
Richmond	WRFK	91.1
	WRVA-FM	94.5
	WRNL-FM	102.5
Roanoke	WDBJ-FM	94.9
	WLRJ	92.3

South Boston	WROY-FM	103.7
South Norfolk	WLSL-FM	99.1
Staunton	WHLF-FM	97.5
Suffolk	WFOS	90.5
Williamsburg	WSGM-FM	89.5
	WXYW	92.9
	WCWM	89.1
	WRCI	96.5
Winchester	WRLF	92.5
Woodbridge	WHPL-FM	102.5
Yorktown	WXRA	105.9
	WYCS	91.5

WASHINGTON

Aberdeen	WDX-FM	104.7
Bellevue	KFKF-FM	92.5
Bellingham	KGMI-FM	92.9
	KERI	104.3
Bremerton	KBRD-FM	106.9
Centralia	KGME-FM	102.9
Cheney	KEWC-FM	*89.1
College Place	KGTS	91.3
Edmonds	KGFM	105.3
Ellensburg	KCWS-FM	*91.5
Eugene	KBMC	104.5
Hoquiam	KGW-FM	103.9
Lynden	KLYN-FM	106.5
Opportunity	KZUN-FM	96.1
Prosser	KACA	102.3
Richland	KCYS	95.1
Seattle	KING-FM	98.1
	KBBX	98.9
	KBLE-FM	92.9
	KETO-FM	101.5
	KIRO-FM	100.7
	KISW	99.9
	KLSN	96.5
	KOL-FM	94.1
	KRAB	107.7
	KTW-FM	102.5
	KUOW	94.9
	KIXI-FM	95.7
	KREM-FM	92.9
	KDNC-FM	93.7
	KTWD	105.7
	KXLY-FM	99.9
	KHQ-FM	98.1
	KLPS	96.5
	KLAY-FM	106.5
	KTNT-FM	97.3
	KTOY	*91.7
	KTAC-FM	103.9
	KNDX-FM	106.3
Spokane	WBKX	99.5
	WSCF-FM	93.5
	WBTV	98.1
	WVBC	88.5
	WHIS-FM	104.5
	WKAZ-FM	97.5
	WCHS-FM	96.1
	WKNA	98.5
	WTIO	105.9
	WVAF	99.9
Huntington	WKEE-FM	100.5
	WMUL	*88.1
	WVQM	103.3
	WPEM-FM	97.5
	WBJR-FM	91.9
	WCSM-FM	100.3
	WQAY-FM	94.1
	WTAP-FM	103.1
	WCEF-FM	99.3
	WKLC-FM	105.1
	WKWK-FM	97.3
	WVA-FM	98.7
	WTRF-FM	107.5
Tacoma	WBKX	99.5
	WVBC	88.5
	WHIS-FM	104.5
	WKAZ-FM	97.5
	WCHS-FM	96.1
	WKNA	98.5
	WTIO	105.9
	WVAF	99.9
	WKEE-FM	100.5
	WMUL	*88.1
	WVQM	103.3
	WPEM-FM	97.5
	WBJR-FM	91.9
	WCSM-FM	100.3
	WQAY-FM	94.1
	WTAP-FM	103.1
	WCEF-FM	99.3
	WKLC-FM	105.1
	WKWK-FM	97.3
	WVA-FM	98.7
	WTRF-FM	107.5
Yakima	WBKX	99.5
	WSCF-FM	93.5
	WBTV	98.1
	WVBC	88.5
	WHIS-FM	104.5
	WKAZ-FM	97.5
	WCHS-FM	96.1
	WKNA	98.5
	WTIO	105.9
	WVAF	99.9
	WKEE-FM	100.5
	WMUL	*88.1
	WVQM	103.3
	WPEM-FM	97.5
	WBJR-FM	91.9
	WCSM-FM	100.3
	WQAY-FM	94.1
	WTAP-FM	103.1
	WCEF-FM	99.3
	WKLC-FM	105.1
	WKWK-FM	97.3
	WVA-FM	98.7
	WTRF-FM	107.5

WEST VIRGINIA

Berkeley Springs	WBKX	99.5
Bethany	WVBC	88.5
Bluefield	WHIS-FM	104.5
Charleston	WKAZ-FM	97.5
	WCHS-FM	96.1
	WKNA	98.5
	WTIO	105.9
	WVAF	99.9
	WKEE-FM	100.5
	WMUL	*88.1
	WVQM	103.3
	WPEM-FM	97.5
	WBJR-FM	91.9
	WCSM-FM	100.3
	WQAY-FM	94.1
	WTAP-FM	103.1
	WCEF-FM	99.3
	WKLC-FM	105.1
	WKWK-FM	97.3
	WVA-FM	98.7
	WTRF-FM	107.5

WISCONSIN

Appleton	WLFM	*91.1
	WAPL-FM	105.7
	WBGR-FM	*88.1
	WBTV	*89.9
	WKWK	*88.3
	WHWC	*88.3
	WHAD	*90.7
	WIAL	94.1
	WEAU-FM	100.7
	WFAW	107.3
	WBAJ-FM	101.1
	WVCF	94.9
	WHHI	91.3
	WWSA	*89.9
Fort Atkinson	WFAW	107.3
Green Bay	WBAJ-FM	101.1
Greenfield Twp.	WVCF	94.9
Highland	WHHI	91.3
Highland Twp.	WWSA	*89.9

Janesville	WCLO-FM	99.9
Kenosha	WLIP	95.1
La Crosse	WHLA	*80.3
	WWLA	93.3
	WHA-FM	*88.7
	WIB-FM	93.3
	WISM-FM	98.1
	WIFM	104.1(s)
	WRVB-FM	102.5
	WKUB	92.1
	WHMD	*91.5
	WDLB-FM	106.5
	WZFM	98.1
	WLIN	100.7
	WFMR	96.5
	WML-FM	95.7
	WISN-FM	97.3
	WRIT-FM	102.9
	WAWA-FM	102.1
	WQFM	93.3
	WTFJ	94.5
	WBON	107.7
	WEMP-FM	99.1
	WUW	*89.7
	WEKZ-FM	94.7
	WFMK	92.3
Monroe	WJCF	95.5
Mt. Horeb	WFKM	92.3
Neenah-Menasha	WNAM-FM	99.3
	WCCN-FM	107.5
	WMKC	96.7
	WRST-FM	108.9
	WOSH-FM	*83.1
	WSUP	*90.5
	WSWW-FM	99.3
Port Washington	WGLB-FM	100.1
	WRJN-FM	100.7
	WFNY	92.1
Racine	WBOB-FM	107.9
Rhineland	WJMC-FM	96.3
Rice Lake	WRCO-FM	100.9
Richland Center	WCWC-FM	95.9
Ripon	WVLR	96.7
Sauk City	WTCH-FM	100.1
Shawano	WCOW-FM	97.1
Sparta	WSPT-FM	97.9
Stevens Point	WDRR-FM	95.9
Sturgeon Bay	WJCF-FM	105.1
Superior	WSSU	91.3
Tomah	WTMB-FM	98.5
Two Rivers	WTRB-FM	102.3
Watertown	WTTN-FM	104.7
Wausau	WUWK-FM	106.1
	WHRM	*91.9
	WRIG-FM	101.9
	WTOS	103.7
	WBKX-FM	92.5
	WSUW	91.7
	WFHR-FM	103.3

WYOMING

Cheyenne	KVWO-FM	106.3
----------	---------	-------

GUAM

Agana	KUAM-FM	99.9
-------	---------	------

PUERTO RICO

Arecibo	WCMM-FM	104.3
	WNK-FM	107.3
	WABA-FM	100.3
	WRSJ-FM	100.7
	WVQZ-FM	107.7
	WORO	92.5
	WMDM-FM	96.5
	WXRJ-FM	96.5
	WKJB-FM	99.1
	WORA-FM	97.5
	WYOE-FM	94.1
	WLEO-FM	101.9
	WPAB-FM	93.3
	WIPR-FM	*91.3
	WIAC-FM	102.3
	WITA-FM	107.7
	WOLA	105.7

VIRGIN ISLANDS

St. Croix, Christiansted	WIVI-FM	99.5
Christiansted, St. Croix	WIVI-FM	99.5

Canadian AM Stations by Location

Location	C.L.	Kc.	Location	C.L.	Kc.	Location	C.L.	Kc.	Location	C.L.	Kc.
Chicoutimi, Que.	CBJ	1580	Kentville, N.S.	CKEN	1350	Pointe Claire, Que.	CFOX	1470	Stephenville, Nfld.	CFXS	910
Chilliwack, B.C.	CJMT	1420	Kingston, Ont.	CFRC	1490	Portage La Prairie, Man.	CFAY	920	Sudbury, Ont.	CFBR	550
Churchill, Man.	CHWK	1270		CKLC	1380		CFRY	920	CHNO	900	
Cobourg, Ont.	CHFC	1230		CKWS	960	Port Alberni, B.C.	CJAV	1240	CKSO	790	
Collingwood, Ont.	CJLC	1400	Kirkland Lake, Ont.	CFPA	1230	Port Arthur, Ont.	CFPA	1230	Summerside, P.E.I.	CJRW	1240
Corner Brook, Nfld.	CKCB	1400	Kitchener, Ont.	CHYM	1490		CKPR	980	Swift Current, Sask.	GKSW	1400
	CBY	990		CKKW	1320	Prince Albert, Sask.	CKBI	900	Sydney, N.S.	CBJ	1140
	CFGB	570	Kitimat, B.C.	CKTK	1230	Prince George, B.C.	CKPG	550		CHER	950
Cornwall, Ont.	CFML	1110	Langley, B.C.	CJJC	850	Prince Rupert, B.C.	CFPR	860		CJCB	1270
	CJSS	1220	La Sarre, Que.	CKLS	1240		CHTK	560	Terrace, B.C.	CFTK	590
Courtenay, B.C.	CFCP	1440	La Tuque, Que.	CFLM	1240	Quebec, Que.	CBV	980	Thetford Mines, Que.	CKLD	1230
Cranbrook, B.C.	CKEK	570	Leamington, Ont.	CJSP	710		CFGM	1340	Thompson, Man.	CHTM	610
Dartmouth, N.S.	CFBR	790	Lethbridge, Alta.	CHCL	1090		CHRC	800	Trois-Rivieres, Que.	CHLN	550
Dauphin, Man.	CKDM	730		CJOC	1220		CJLR	1060		CHTR	150
Dawson Creek, B.C.	CJCD	1350	Lindsay, Ont.	CKLY	910		CKCV	1280	Tillsonburg, Ont.	CKOT	1510
Drumheller, Alta.	CJDV	910	Lloydminster, Alta.	CKSA	1080	Quesnel, B.C.	CKCQ	570	Timmins, Ont.	CFCL	620
Drummondville, Que.	CHRD	1340	London, Ont.	CFPL	980	Red Deer, Alta.	CKRD	850		CKGB	680
Dryden, Ont.	CKDR	900		CKSL	1410	Regina, Sask.	CKB	540	Toronto, Ont.	CBL	740
Duncan, B.C.	CKAY	1500	Marystown, Nfld.	CHCM	560		CJME	1300		CFRB	1010
Edmonton, Alta.	CBX	740	Matane, Que.	CKBL	1250		CKCK	620		CHFI	1540
	CFRN	1260	Medicine Hat, Alta.	CHAT	1270		CKRM	980		CHUM	1050
	CHFD	630	Middleton, N.S.	CKAD	1440	Revelstoke, B.C.	CKCR	1340		CJBC	860
	CHFA	680	Midland, Ont.	CKMP	1230	Richmond Hill, Ont.	CFHM	1100		CJCY	590
	CHQT	1110	Moncton, N.B.	CBAF	1300	Rimouski, Que.	CJBR	900		CKFH	1430
	CJCA	930		CKCW	1220	Rivière du Loup, Que.	CJFP	1400	Trail, B.C.	CJAT	610
	CKUA	580	Mont Laurier, Que.	CKML	610	Roberval, Que.	CHRL	910	Truro, N.S.	CKCL	600
Edmundston, N.B.	CJEM	570	Montmagny, Que.	CKBM	1490	Roynou, Que.	CKRN	1400	Val d'Or, Que.	CKVD	1230
Estevan, Sask.	CJSL	1280	Montreal, Que.	CBF	690	Ste. Anne de la Pocatiere, Que.	CHGB	1310	Valleyfield, Que.	CFLV	1370
Flin Flon, Man.	CFAR	590		CBM	940		CKSB	1050	Vancouver, B.C.	CBU	690
Fort Frances, Ont.	CFOB	800		CFCF	600	St. Boniface, Man.	CKSE	1050		CFUN	1410
Fort Simpson, N.W.T.	CFMR	1490		CFMB	1410	St. Catharines, Ont.	CKTB	610		CHQM	1320
	CKNL	560		CJAD	800	St. Hyacinthe, Que.	CKBS	1240		CJOR	600
Fort St. John, B.C.	CKLX	800		CJMS	1280		CHRS	1050		CKLG	730
Fort William, Ont.	CKLJ	800		CKAC	730	St. Jerome, Que.	CKJL	900		CKWX	1130
Fredericton, N.B.	CBZ	970		CKLM	1570	Saint John, N.B.	CBD	1110	Verdun, Que.	CKVL	850
	CFNB	550		CKGM	980	St. John's Nfld.	CBN	640	Vernon, B.C.	CJJB	940
	CFTJ	1110	Moose Jaw, Sask.	CHAB	800		CJON	930	Victoria, B.C.	CFAX	1070
Galt, Ont.	CBG	1450	Nanaimo, B.C.	CHUB	1570		VOAR	1230		CJVI	900
Gander, Nfld.	CFGB	1340	Nelson, B.C.	CKLN	1390		VOCM	590		CKDA	1220
Goose Bay, Nfld.	CHFE	1450	New Carlisle, Que.	CHNC	610		W0WR	800		CFDA	1360
Granby, Que.	CFGP	1050	Newcastle, N.B.	CKMB	810	St. Joseph d'Alma, Que.	CFGT	670	Victoriaville, Que.	CKVM	710
Grande Prairie, Alta.	CJGX	710	New Glasgow, N.S.	CKEC	1320		CHLO	1280	Ville Marie, Que.	CKVM	710
Grand Bank, Nfld.	CBT	540	New Westminster, B.C.	CKNW	960	St. Thomas, Ont.	CBA	1070		CKRB	1460
Grand Falls, Nfld.	CKCM	620	Niagara Falls, Ont.	CJRN	1000	Sackville, N.B.	CFBC	930	Wawa, Ont.	CJWA	1240
	CJCN	680	North Battleford, Sask.	CJNB	1050	Saint John, N.B.	CHSJ	1150	Welland, Ont.	CHOW	1470
Gravelbourg, Sask.	CFRG	710		CKLB	1350	Salmon Arm, B.C.	CKXR	580	Weyburn, Sask.	CFSL	1340
	CFGR	1230		CBO	910	Sarnia, Ont.	CHOK	1070	Whitehorse, Y.T.	CFWH	570
Halifax, N.S.	CJOY	1460	North Vancouver, B.C.	CKLG	730	Saskatoon, Sask.	CFNS	1170	Williams Lake, B.C.	CKWL	1240
	CBH	860	Oakville, Ont.	CHWO	1250		CFOC	600	Windsor, N.S.	CFAB	1450
	CJCH	920	Orillia, Ont.	CFOR	1570		CKOM	1250	Windsor, Ont.	CBE	1550
Hamilton, Ont.	CHML	900	Oshawa, Ont.	CKLB	1350	Sault Ste. Marie, Ont.	CJIC	1050		CKWW	580
	CKOC	1150	Ottawa, Ont.	CBO	910		CKCY	920	Wingham, Ont.	CKNX	920
	CHIQ	1280		CBOF	1250	Schefferville, Que.	CBDR	1230	Winnipeg, Man.	CBW	900
Hauterive, Que.	CHLC	580		CFRA	580	Sept-Iles, Que.	CKCN	560		CJOB	680
Huntsville, Ont.	CKAR	630		CKOY	1310	Shawinigan, Que.	CKSM	1220		CJMT	1470
Hull, Que.	CKCH	970		CKPM	1440	Sherbrooke, Que.	CHLT	630		CKRC	630
Inuwik, N.W.T.	CHAK	860	Owen Sound, Ont.	CFOS	560		CKTS	900		CKY	580
Joliette, Que.	CJLM	1350	Parry Sound, Ont.	CKAL	1340	Simcoe, Ont.	CFRS	1560		CKY	580
Jonquiere, Que.	CKRS	590	Peace River, Alta.	CKYL	610	Smiths Falls, Ont.	CJET	630	Woodstock, N.B.	CJQJ	920
Kamloops, B.C.	CFJC	910	Pembroke, Ont.	CHOV	1350	Smithers, B.C.	CFBV	1230	Woodstock, Ont.	CKOX	1340
Kapuskasing, Ont.	CKAP	580	Penticton, B.C.	CKOK	800	Sorel, Que.	CJCS	1320	Yarmouth, N.S.	CJLS	1340
Kelowna, B.C.	CKOV	630	Peterborough, Ont.	CHEX	980	Stratford, Ont.	CJOS	1240	Yellowknife, N.W.T.	CFYK	1340
Kenora, Ont.	CJRL	1220		CKPT	1420	Steinbach, Man.	CHSM	1250	Yorkton, Sask.	CJGX	940

Canadian FM Stations by Location

Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.
Belleville, Ont.	CJBQ-FM	97.1	Kitchener, Ont.	CHYM-FM	96.7	Red Deer, Alta.	CKRD-FM	98.9	Timmins, Ont.	CKGB-FM	94.5
Brampton, Ont.	CHIC-FM	102.1		CFPL-FM	95.9	Regina, Sask.	CFMQ-FM	92.1	Toronto, Ont.	CBFC-FM	99.1
Brandon, Man.	CKX-FM	96.1	London, Ont.	CFPL-FM	100.9	Rimouski, Que.	CJBR-FM	101.5		CHFI-FM	98.1
Calgary, Alta.	CHFM-FM	95.9	Merritt, B.C.	CFM-FM-3	103.9	Saint John, N.B.	CFBC-FM	98.9		CHUM-FM	104.5
Clearwater, B.C.	CFM-FM-2	92.7	Montreal, Que.	CBF-FM	95.1	Saskatoon, Sask.	CFMC-FM	103.9		CJRT-FM	91.1
	CJSS-FM	104.5		CBM-FM	100.7		CJUS-FM	89.7	Truro, N.S.	CKCL-FM	100.9
Edmonton, Alta.	CFRN-FM	100.3		CFCF-FM	92.5	Sault Ste. Marie, Ont.	CJIC-FM	100.5	Vancouver, B.C.	CBU-FM	105.7
	CJCA-FM	95.5		CJFM-FM	95.9		CKCY-FM	104.3		CHQM-FM	103.5
	CKUA-FM	98.1		CJMS-FM	94.3	Savona, B.C.	CFM-FM-1	101.9		CKGL-FM	99.3
Halifax, N.S.	CHNS-FM	96.1		CKGM-FM	97.7	Sherbrooke, Que.	CHLT-FM	102.7	Verdun, Que.	CKVL-FM	96.9
Hamilton, Ont.	CHML-FM	95.3	Oshawa, Ont.	CKLB-FM	93.5	St. Catharines, Ont.			Victoria, B.C.	CFMS-FM	98.5
Kamloops, B.C.	CFM-FM	98.3	Ottawa, Ont.	CFM-FM	103.3		CKTB-FM	97.7	Windsor, Ont.	CKLW-FM	93.9
Kelowna, B.C.	CJQV-FM	104.7		CFMO-FM	103.3		CKSO-FM	92.7	Winnipeg, Man.	CJOB-FM	97.5
Kentville, N.S.	CKWM-FM	97.7	Penticton, B.C.	CKOK-FM	97.1	Sudbury, Ont.	CJCB-FM	94.9		CBW-FM	98.3
Kingston, Ont.	CFRC-FM	91.9	Port Arthur, Ont.			Sydney, N.S.			CKQM-FM	94.3	
	CKLC-FM	98.3		CKPR-FM	94.3	Tillsonburg, Ont.	CKOT-FM	100.5		CKY-FM	92.1
	CKWS-FM	96.3	Quebec, Que.	CHRC-FM	98.1						

World-Wide Shortwave Stations

■ Although this is officially the shortwave section of White's Radio Log, we can't help but sneak a peek at the DX on the standard broadcasting band from time to time. It doesn't take very much equipment to pull

'em in, you can even inhale some excellent DX on nothing more than a 5-tube AC/DC set. Trick is to forget the internal loop antennas on these sets and string up a 100 foot wire for an antenna. It can be connected to

WHITE'S RADIO LOG

the loop antenna by simply wrapping it around the loop several times, without making an electrical connection. *Disconnect the set when doing this anyway—just for safety's sake.*

Our DX'ing is done on a slightly fancier receiver however, and some of the better stations just dropped right into the set. If you want to take a whack at BCB-DX you can whet your appetite with stations such as *Trans World Radio* in Bonaire, Netherlands Antillies (yup, some folks that operate on shortwaves). They pack a walloping signal when they test irregularly on 800 kHz, they run more than a half-a-million watts!

Radio Antilles, on the island of Montserrat in the Caribbean, has also been heard testing once in a while (according to one of our reporters) with 200,000 watts on 926 kHz.

Radio Americas, still and *always* on Swan Island (regardless of what you may read elsewhere) pounds in like a local on 1157 kHz most evenings. *Voice of America* stations bombarding Fidel from the Florida Keys can also be heard well (in Spanish) most PM's on 1040 kHz (Tortugas Key with 50 kw) and 1180 (Marathon Key with 50 kw).

Best bets also include the following winners: WOAI in San Antonio, Tex. on 1200 kHz; WWVA in Wheeling, W. Va., on 1170 kHz; WSM in Nashville, Tenn., on 650 kHz; WLW in Cincinnati, Ohio, on 700 kHz; WCCO in Minneapolis, Minn., on 830 kHz,

and WCBS in New York, N. Y., on 880 kHz. If you can't hear at least four of these stations tonight, then forget about DX'ing and take up basketweaving or stamp collecting. (*Editor: What's wrong with stamp collecting?*) Let us know how you did.

We invite our readers to send in their loggings for inclusion in these listings. Be sure to include the following information for each station reported: approximate frequency, callsign and/or station name, and time monitored in Greenwich Mean Time (24 hour clock). Address your reports to: DX Central, White's Radio Log, RAD IO-TV EXPERIMENTER, 505 Park Avenue, New York, N. Y. 10022, U.S.A.

Contributors for World-Wide Shortwave Section

Thomas A. Sherman, Williamsport, Pa.
 Ronald Tushjian, Stockton, Calif.
 Mike Thompson, Vancouver, B. C.
 Larry Nelson, Chicago, Ill.
 Rickey Vezzani, E. Northport, N. Y.
 Jerry Stuart, Lawton, Okla.
 Walter O'Brien, Jr., Clark, N. Y.
 Mary K. McNabb, Springdale, Ark.
 Julian M. Sienkiewicz, Brooklyn, N. Y.
 Leonard Kosko, Cleveland, Ohio
 Dave Mateyka, Steger, Ill.
 Carl Durnavich, Riverdale, Ill.
 Harry McDonald, Clay City, Ill.
 John M. Demchak, W. Mifflin, Pa.
 Thomas Facer, Ithaca, N. Y.
 Kerry Matthews, Miami Beach, Fla.
 Tom Kneitel, K2AES, New York, N. Y.
 Robert Orestes, Santa Ana, Calif.
 Rick Slattery, Key West, Fla.
 Skip Bradford, Commack, N. Y.
 "Mandy" Seidenberg, Forest Hills, N. Y.

The following abbreviations are used: BC- Broadcasting Company, Corporation or System; E- Emissora; R- Radio; V- Voice or Voz.

kHz	Call	Name	Location	GMT
90-Meter Band—3200 to 3400 kHz				
2420	—	R. Sao Carlos	Sao Carlos, Brazil	0330
2495	HCV44	E. la Alegria	Esmeraldas, Ecuador	0330
3200	—	R. San Pedro	S. Pedro Macoris, Dom. Rep.	0330
3232	—	R. Brazzaville	Brazzaville, Congo	0500
3265	—	R. Demerara	Georgetown, Guiana	0200
3277	—	R. Kashmir	Srinagar, Kashmir	1530
3280	—	R. Ghana	Accra, Ghana	2135
3315	—	ORTF	Ft. de France, Martinique	0100
3318	ZYV63	R. Itatiaia	Belo Horizonte, Brazil	0230
3331	—	ORTF	Dzaoudzi, Comores Isl.	1700
3345	H1AS	Onda Musical	Sto. Domingo	0445
3355	—	R. Brasileira	Uberlandia	0205

kHz	Call	Name	Location	GMT
3385	VL9BR	R. Rabaul	Rabaul, Papua	1050
—	—	ORTF	Cayenne, Fr. Guiana	0918
3435	—	R. Ondas Huallaga	Huanuco, Peru	0400
3925	VLK3	Australian BC	Port Moresby, Papua	0730
3985	—	E. R. Populares	Riobamba, Ecuador	0100
4580	—	R. Nepal	Kathmandu, Nepal	0740
4708	—	V. de Carera	Pasto, Colombia	0200
60-Meter Band—4750 to 5060 kHz				
4780	YVLA	V. de Carabobo	Valencia, Venez.	2330
4790	YVQN	Ondas Portenas	La Cruz, Venezuela	0120
4795	CP73	N. Neuva America	La Paz, Bolivia	0005
—	—	R. Brazzaville	Brazzaville, Congo	0500
4840	—	R. Sao Carlos	Sao Carlos, Brazil	0330

kHz	Call	Name	Location	GMT	kHz	Call	Name	Location	GMT
4845	—	BBC Relay	Francistown,		7195	—	V. America Relay	Monrovia, Liberia	0330
			Bechuanaland	0400	7200	—	R. Moscow	Moscow, USSR	0000
4855	—	E. Nigerian BC	Enugu, Nigeria	2230	7210	—	Senegalese BC	Dakar, Senegal	0700
4870	OCX4T	R. Cultural	Huancayo, Peru	0230	7245	—	Austrian R.	Vienna, Austria	0600
4885	HJIW	V. del Centro	Espinal, Colombia	1100	7250	—	R. Moscow	Moscow, USSR	0000
4890	VLK4	Australian BC	Port Moresby,				V. America Relay	Tangier, Morocco	2230
			Papua	0730	7265	—	R. Tirana	Tirana, Albania	2200
		Senegalese BC	Dakar, Senegal	0700	7270	—	R. Warsaw	Warsaw, Poland	2230
4895	—	S. African BC	Paradys, S. Africa	0430			S. African BC	Paradys, S. Africa	0356
4912	VTW2	R. Tarawa	Tarawa, Gilbert Is.	0655	7290	—	R. Moscow	Moscow, USSR	0000
4914	HRSY	V. del Pacifico	San Lorenzo,		7295	—	BBC Relay	Francistown,	
			Honduras	0230				Bechuanaland	0915
4935	OAX9E	R. Tropical	Tarapoto, Peru	0340	7310	—	R. Moscow	Moscow, USSR	0000
4965	—	R. Zambia	Lusaka, Zambia	0355	7330	—	R. Moscow	Moscow, USSR	0000
4972	—	R. Yaounde	Yaounde,		7344	—	R. Prague	Prague, Czech.	0145
			Cameroon	2200	7360	—	R. Moscow	Moscow, USSR	0000
5045	ZYP23	R. Imperial	Petropolis, Brazil	0010			R. Vilnius	Vilnius, USSR	2230
5055	—	R. Singapore	Singapore	1400	7570	—	R. Espana Independ	(clandestine)	2000
5065	—	R. Liberland	(clandestine)	0015	7655	—	V. America	Greenville, N.C.	2230
5910	—	Govorit Ashkabad	Ashkabad, USSR	1723	9009	4XB31	Kol Zion	Jerusalem, Israel	2040
5930	—	R. Prague	Prague, Czech.	0125	9370	—	R. Nacional	Madrid, Spain	0730
					9390	—	R. Tirana	Tirana, Albania	2200
					9520	—	R. Alma Ata	Alma Ata, USSR	0340
					9380	—	R. Alma Ata	Alma Ata, USSR	0340
					9400	—	R. Peking	Peking, China	2200
					9457	—	R. Peking	Peking, China	1800

49-Meter Band—5950 to 6200 kHz

5950	—	R. Warsaw	Warsaw, Poland	2030
5955	CP41	R. Loyola	Sucre, Bolivia	0030
5960	CP5	R. Pio XII	Siglo, Viñete, Bolivia	0200
	HRHR	V. Occidente	S. Rosa Copan, Honduras	0150
5970	—	R. Alger	Algiers, Algeria	0700
	OBX4Q	R. El Sol	Lima, Peru	0430
5970	—	R. Brazzaville	Brazzaville, Congo	0500
5974	4VB	V. Revol.	Port au Prince, Haiti	1400
		Duvalieriste		
5985	—	E. Nacional	Lisbon, Portugal	0300
5990	—	R. Canada	Montreal, P.Q.	0730
		RAI	Rome, Italy	1655
5994	ORTF	ORTF	Ft. de France, Martinique	1300
5995	—	R. Warsaw	Warsaw, Poland	1930
		V. America Relay	Tangier, Morocco	2230
6000	—	Austrian R.	Vienna, Austria	0430
6005	CFCX	Canadian Marconi	Montreal, P.Q.	0930
6010	YSS	R. Nacional	San Salvador, El Salvador	1135
6015	—	(relaying DZBC)	Manila, Philippines	1400
6020	—	R. Kiev	Kiev, USSR	1900
6025	HCJB	V. Andes	Quito, Ecuador	0530
6030	—	V. America	Greenville, N.C.	0045
	CVP	V. Praries	Calgary, Alta.	0330
6065	XEXG	R. Mexico	Mexico DF, Mexico	0415
6080	—	Swiss BC	Berne, Switz.	0130
6085	—	Swiss BC	Berne, Switz.	0115
6095	—	R. Mogadiscio	Mogadiscio, Somalia	0329
6110	—	R. Ghana	Accra, Ghana	0330
6115	—	R. Leon	Lima, Peru	0530
6120	—	Swiss BC	Berne, Switz.	0115
6125	ORU	V. de l'Amitie	Brussels, Belg.	2240
6135	—	R. Havana	Havana, Cuba	2230
		R. Warsaw	Warsaw, Poland	1830
6140	—	R. Nacional	Madrid, Spain	1315
6150	—	Australian BC	Melbourne,	
			Australia	2100
		S. African BC	Paradys, S. Africa	0356
6155	—	Austrian R.	Vienna, Austria	0500
6160	HSK4	R. Bangkok	Bangkok, Thailand	0415
6163	—	V. du Nord	Port au Prince, Haiti	1400
6175	—	R. Alger	Algiers, Algeria	2200
6195	GSF	BBC	London, England	1830
6290	—	R. Tirana	Tirana, Albania	2200
6620	—	R. Peking	Peking, China	2030
6645	—	R. Peking	Peking, China	2030
6825	—	R. Peking	Peking, China	1800
6890	—	R. Peking	Peking, China	2030
7006	—	R. Peking	Peking, China	1800
7075	—	R. Peking	Peking, China	1800
7090	—	R. Tirana	Tirana, Albania	2200
7100	—	R. Pakistan	Karachi, Pakistan	1945
7105	—	R. Nacional	Madrid, Spain	1315
		R. Brazzaville	Brazzaville, Congo	1100
		R. Nepal	Kathmandu, Nepal	0740
7115	—	R. Prague	Prague, Czech.	0100
7125	—	R. Warsaw	Warsaw, Poland	1830
7130	—	E. Nacional	Lisbon, Portugal	0800
7145	—	R. Warsaw	Warsaw, Poland	2030
7150	—	R. Moscow	Moscow, USSR	0000
7185	—	R. Vilnius	Vilnius, USSR	2230
7185	HSK7	R. Bangkok	Bangkok, Thailand	0415
7185	GSF	BBC	London, England	0500

31-Meter Band—9500 to 9775 kHz

9510	GSF	BBC	London, England	2200
9512	—	R. Alger	Algiers, Algeria	1600
9520	VLT9	Australian BC	Port Moresby, Australia	0730
		R. Tirana	Tirana, Albania	2200
	OZF5	V. Denmark	Copenhagen, Denmark	0200
9525	—	Austrian R.	Vienna, Austria	0000
		S. African BC	Paradys, S. Africa	0516
	PCJ	R. Netherland	Hilversum, Neth.	0730
		Swiss BC	Berne, Switz.	0115
9550	—	R. Habana	Havana, Cuba	2230
9555	—	BBC Relay	Monrovia, Liberia	0645
	YSS	R. Nacional	San Salvador, El Salvador	1135
	CP6	R. Illimani	La Paz, Bolivia	1100
9560	—	R. Australia	Melbourne, Australia	0645
9570	—	R. Nacional	Madrid, Spain	1315
9580	GSF	BBC	London, England	2200
9590	—	R. Netherland	Bonaire, Neth.	
		Antilles		0150
9595	—	Swiss BC	Berne, Switz.	1745
9610	—	Austrian Radio	Vienna, Austria	1100
		R. Mauretanie	Nouakchott, Mauretania	1245
9625	—	R. Canada	Montreal, P.Q.	0730
9640	—	V. America	Greenville, N.C.	0045
		Uttvar Reykjavik	Reykjavik, Iceland	2030
		R. Kiev	Kiev, USSR	1900
9645	—	E. Nacional	Lisbon, Portugal	0800
	HCJB	V. Andes	Quito, Ecuador	0600
		Vatican R.	Vatican City	2000
9650	—	R. Canada	Montreal, P.Q.	2300
		V. America	Greenville, N.C.	0045
		R. Habana	Havana, Cuba	2230
9655	—	R. Habana	Havana, Cuba	0930
9660	—	R. Nacional	Canary Islands	1730
9670	—	V. America Relay	Tangiers, Morocco	1800
9675	—	Vatican R.	Vatican City	2220
	ZYT29	R. Diario Manha	Florianopolis, Braz.	1100
		V. Free China	Taipei, Formosa	1530
		R. Warsaw	Warsaw, Poland	0700
9680	—	Australian BC	Melbourne, Australia	2245
9700	—	R. Pakistan	Karachi, Pakistan	1945
		R. Japan	Tokyo, Japan	1930
9710	—	R. Tropical	Tarapoto, Peru	1300
9715	PCJ	R. Netherland	Hilversum, Netherlands	0730
9725	4XB51	Kol Zion	Jerusalem, Israel	2040
9730	—	R. Brazzaville	Brazzaville, Congo	0500
		R. Berlin Internat.	Berlin, E. Germany	0100
9750	OAX8W	R. Sideral	Pucallpa, Peru	1215
9755	—	VTVN	Saigon, S. Vietnam	1200
9760	—	V. Vietnam	Hanoi, N. Vietnam	1530
9770	—	Austrian R.	Vienna, Austria	2300
	OAX80	R. Amazonas	Iquitos, Peru	1100
		V. Vietnam	Hanoi, N. Vietnam	1530
9860	—	R. Peking	Peking, China	2000
9874	YDF6	V. Indonesia	Diakarta, Indonesia	1700

(Continued on page 122)



V Literature Library



★ Starred items indicate advertisers in this issue. Consult their ads for additional information and specifications.

ELECTRONIC PARTS

★1. Allied's catalog is so widely used as a reference book, that it's regarded as a standard by people in the electronics industry. Don't you have the latest *Allied Radio* catalog? The surprising thing is that it's free!

★2. The new 510-page 1966 edition of *Lafayette Radio's* multi-colored catalog is a perfect buyer's guide for hi-fiers, experimenters, kit builders, CB'ers and hams. Get your free copy, today!

★3. Bargains galore! Parts, tools, test equipment, radios and many more shoppers' specials at ultra-low prices. *Progressive Edu-Kits* will send latest catalog.

★4. We'll exert our influence to get you on the *Olson* mailing list. This catalog comes out regularly with lots of new and surplus items. If you find your name hidden in the pages, you win \$5 in free merchandise!

5. Unusual scientific, optical and mathematical values. That's what *Edmund Scientific* has. War surplus equipment as well as many other hard-to-get items are included in this new 148-page catalog.

106. With 70 million TV's and 240 million radios somebody somewhere will need a vacuum tube replacement at the rate of one a second! Get *Universal Tube Co.'s* Troubleshooting Chart and facts on their \$1 flat rate per tube.

★7. Whether you buy surplus or new, you will be interested in *Fair Radio Sales Co.'s* latest catalog—chuck full of surplus buys for every experimenter.

★8. Want a colorful catalog of goodies? *John Meshina, Jr.* has one that covers everything from assemblies to zener diodes. Listed are government surplus radio, radar, parts, etc. All at unbelievable prices.

★23. No electronics bargain hunter should be caught without the latest copy of *Radio Shack's* catalog. Some equipment and kit offers are so low, they look like misprints. Buying is believing.

★6. Bargains galore, that's what's in store! *Poly-Paks Co.* will send you their latest eight-page flyer listing the latest in merchandise available, including a giant \$1 special sale.

10. *Burstein-Applebee* offers a new giant catalog containing 100's of big pages crammed with savings including hundreds of bargains on hi-fi kits, power tools, tubes, and parts.

★11. Now available from *EDI (Electronic Distributors, Inc.)* a catalog containing hundreds of electronic items. *EDI* will be happy to place you on their mailing list.

12. VHF listeners will want the latest catalog from *Kuhn Electronics*. All types and forms of complete receivers and converters.

CB—BUSINESS RADIO SHORT-WAVE RADIO

★93. *Heath Co.* has a new 23-channel all-transistor 5-watt CB rig at the lowest cost on the market, plus a full line of CB gear. See their new 10-band AM/FM/Shortwave portable and line of shortwave radios.

48. *Hy-Gain's* new CB antenna catalog is packed full of useful information and product data that every CB'er should know about. Get a copy.

107. Get with the mobile set with *Tram's* XL100. The new Titan CB base station, another *Tram* great, is worth knowing about. Get complete specifications plus facts on other accessories.

49. Want to see the latest in communication receivers? *National Radio Co.* puts out a line of mighty fine ones and their catalog will tell you all about them.

50. Are you getting all you can from your Citizens Band radio equipment? *Amphenol Cadre Industries* has a booklet that answers lots of the questions you may have.

100. You can get increased CB range and clarity using the "Cobra" transmitter with speech compressor—receiver sensitivity is excellent. Catalog sheet will be mailed by *B&K Division of Dynascan Corporation*.

54. A catalog for CB'ers, hams and experimenters, with outstanding values. Terrific buys on *Grove Electronics'* antennas, mikes and accessories.

90. If two-way radio is your meat, send for *Pearce-Simpson's* new booklet! Its 18 pages cover equipment selection, license application, principles of two-way communications, reception, and installation.

96. If a rugged low-cost business/industrial two-way radio is what you've been looking for, be sure to send for the brochure on *E. F. Johnson Co.'s* brand new Messenger "202."

101. If it's a CB product, chances are *International Crystal* has it listed in their colorful catalog. Whether kit or wired, accessory or test gear, this CB oriented company can be relied on to fill the bill.

102. *Sentry Mfg. Co.* has some interesting pony sheets on speech clippers, converters, talk power kits and the like for interested CB'ers, hams and SWL'ers, too.

103. *Squires-Sanders* would like you to know about their CB transceivers, the "23'er" and the new "55S." Also, CB accessories that add versatility to their 5-watters.

ELECTRONIC PRODUCTS

66. Try instant lettering to mark control panels and component parts. *DataK's* booklets and sample show this easy dry transfer method.

108. Get the facts on *Mercury's* line of test equipment kits—designed to make troubleshooting easier, faster and more profitable.

67. "Get the most measurement value per dollar," says *Electronics Measurements Corp.* Send for their catalog and find out how!

92. How about installing a transistorized electronic ignition system in your current car? *AEC Laboratories* will mail their brochure giving you specifications, schematics.

109. *Seco* offers a line of specialized and standard test equipment that's ideal for the home experimenter and pro. Get specs and prices today.

HI-FI/AUDIO

110. Get the latest facts on sound columns. *American Gelsos Electronics Inc.* offers a ten-page booklet giving the hows and whys plus method of installation and arrangement of sound columns.

★26. Always a leader, *H. H. Scott* introduces a new concept in stereo console catalogs. "At Home With Stereo" the 1966 guide, offers decorating ideas, a complete explanation of the more technical aspects of stereo consoles, and, of course, the complete new line of *Scott* consoles.

15. A name well-known in audio circles is *Acoustic Research*. Here's its booklet on the famous AR speakers and the new AR turntable.

16. *Garrard* has prepared a 32-page booklet on its full line of automatic turntables including the Lab 80, the first automatic transcription turntable. Accessories are detailed too.

17. Build your own bass reflex enclosures from fool-proof plans offered by *Electro-Voice*. At the same time get the specs on *EV's* solid-state hi-fi line—a new pace setter for the audio industry.

19. *Empire Scientific's* new 8-page, full color catalog is now available to our readers. Don't miss the sparkling decorating-with-sound ideas. Just circle #19.

22. A wide variety of loudspeakers and enclosures from *Utah Electronics* lists sizes, shapes, and prices. All types are covered in this heavily illustrated brochure.

24. Need a hi-fi or PA mike? *University Sound* has an interesting microphone booklet audio fans should read before making a purchase.

27. An assortment of high fidelity components and cabinets are described in the *Sherwood* brochure. The cabinets can almost be designed to your requirements, as they use modules.

95. Confused about stereo? Want to beat the high cost of hi-fi without compromising on the results? Then you need the new 24-page catalog by *Jensen Manufacturing*.

99. Interested in learning about amplifier specifications as well as what's available in kit and wired form from *Acoustech*? Then get your copy of *Acoustech's* 8-page colorful brochure.

TAPE RECORDERS AND TAPE

31. All the facts about *Concord Electronics Corp.* tape recorders are yours for the asking in a free booklet. Portable, battery operated to four-track, fully transistorized stereos cover every recording need.

32. "Everybody's Tape Recording Handbook" is the title of a booklet that *Sarkes-Tarzian* will send you. It's 24-pages jam-packed with info for the home recording enthusiast. Includes a valuable table of recording times for various tapes.

33. Become the first to learn about *Norelco's* complete Carry-Corder 150 portable tape recorder outfit. Four-color booklet describes this new cartridge-tape unit.

35. If you are a serious tape audiophile, you will be interested in the new *Viking of Minneapolis* line—they carry both reel and cartridge recorders you should know about.

91. Sound begins and ends with a *Uher* tape recorder. Write for this new 20 page catalog showing the entire line of *Uher* recorders and accessories. How to synchronize your slide projector, execute sound on sound, and many other exclusive features.

HI-FI ACCESSORIES

76. A new voice-activated tape recorder switch is now available from *Kinematix*. Send for information on this and other exciting products.

39. A 12-page catalog describing the audio accessories that make hi-fi living a bit easier is yours from *Switchcraft, Inc.* The cables, mike mixers, and junctions are essentials!

98. Swinging to hi-fi stereo headsets? Then get your copy of *Superex Electronics'* 16-page catalog featuring a large selection of quality headsets.

104. You can't hear FM stereo unless your FM antenna can pull 'em in. Learn more and discover what's available from *Finco's* 6-pager "Third Dimensional Sound."

KITS

★42. Here's a colorful 108-page catalog containing a wide assortment of electronic kits. You'll find something for any interest, any budget. And *Heath Co.* will happily send you a copy.

★44. *EICO's* new 48-page 2-color pocket-size short form catalog is just off the press. Over 250 products: Ham radio, CB, hi-fi—in kit and wired form—are illustrated. Get your copy today.

AMATEUR RADIO

46. A long-time builder of ham equipment, *Hallcrafters* will send you lots of info on the ham, CB and commercial radio-equipment.

SCHOOLS AND EDUCATIONAL

★61. *ICS (International Correspondence Schools)* offers 236 courses including many in the fields of radio, TV, and electronics. Send for free booklet "It's Your Future."

74. How to get an F.C.C. license, plus a description of the complete electronic courses offered by *Cleveland Institute of Electronics* are in their free catalog.

105. Get the low-down on the latest in educational electronic kits from *Trans-Tek*. Build light dimmers,

amplifiers, metronomes, and many more. *Trans-Tek* helps you to learn while building.

56. *Bailey Institute of Technology* offers courses in electronics, basic electricity and drafting as well as refrigeration. More information in their informative pamphlet.

★59. For a complete rundown on curriculum, lesson outlines, and full details from a leading electronic school, ask for this brochure from the *Indiana Home Study Institute*.

94. *Intercontinental Electronics School* offers three great courses: stereo radio & electronics; basic electricity; transistors. They are all described in *Inesco's* 1966, 16-page booklet.

TOOLS

★78. Do more jobs with fewer tools. *Xcelite's* bulletin N563 describes 3 double-duty sets containing midget nut and screwdrivers plus a special "piggy-back" handle that packs power and reach.

TELEVISION

★70. *Heath Co.* now has a 21" round and 25" rectangular-tube color TV kit in addition to their highly successful 23" B&W model. All sets can be installed in a wall or cabinet: all are money-saving musts!

★72. Get your 1966 catalog of *Cisin's* TV, radio, and hi-fi service books. Bonus—TV tube substitution guide and trouble-chaser chart is yours for the asking.

29. Install your own TV or FM antenna! *Jefferson-King's* exclusive free booklet reveals secrets of installation, orientation; how to get TV-FM transmission data.

97. Interesting, helpful brochures describing the TV antenna discovery of the decade—the log periodic antenna for UHF and UHF-TV, and FM stereo. From *JFD Electronics Corporation*.

RADIO-TV EXPERIMENTER, Dept. LL-809
505 Park Avenue, New York, N. Y. 10022

Please arrange to have the literature whose numbers I have encircled sent to me as soon as possible. I am enclosing 25¢ (no stamps) to cover handling charges.



	1	2	3	4	5	6	7	8	10	11	12	15	16
	17	19	22	23	24	26	27	29	31	32	33	35	39
	42	44	46	48	49	50	54	56	59	61	66	67	70
	72	74	76	78	90	91	92	93	94	95	96	97	98
	99	100	101	102	103	104	105	106	107	108	109	110	

I am a subscriber

Indicate total number of booklets requested

NAME (Print clearly) _____

ADDRESS _____

CITY _____ STATE _____ ZIP CODE _____

World-Wide SW Stations

Continued from page 119

kHz	Call	Name	Location	GMT
10530	—	R. Alma Ata	Alma Ata, USSR	0340
11240	—	R. Euzkadi	(clandestine)	2130
11660	—	R. Peking	Peking, China	1530


25-Meter Band—11700 to 11975 kHz				
kHz	Call	Name	Location	GMT
11710	—	R. Brazzaville	Brazzaville, Congo	1100
	ETLF	R. V. Gospel	Addis Ababa, Ethiopia	0330
	—	R. Australia	Melbourne, Australia	0634
	—	R. Vilnius	Vilnius, USSR	2230
11720	—	R. Canada	Montreal, P.Q.	2145
	KGEI	V. Friendship	San Francisco, Calif.	0335
11725	—	R. Brazzaville	Brazzaville, Congo	0500
11730	PCJ	R. Nederland	Hilversum, Netherlands	0730
11737	—	T-TV Marocaine	Rabat, Morocco	2030
11740	—	Vatican R.	Vatican City	1640
	VUD	All India R.	Delhi, India	1800
11750	GSF	BBC	London, England	2200
11760	—	V. Vietnam	Hanoi, N. Vietnam	1300
11785	—	Austrian R.	Vienna, Austria	1100
	—	R. Berlin Int'l.	Berlin, E. Germany	0345
	DMQ11	Deutsche Welle	Cologne, W. Germany	0745
11795	—	R. Kinshasa	Kinshasa, Congo	1000
11800	—	E. Atlantico	Canary Islands	2130
11820	—	Trans World R.	Bonaire, Neth. Antilles	0335
11825	BED69	V. Free China	Taipei, Formosa	0100
	ZYK32	R. Jornal Comercio	Recife, Brazil	2300
11835	CXA19	El Espectador	Montevideo, Uruguay	0030
	—	R. Alger	Algiers, Algeria	1600
11840	—	V. Vietnam	Hanoi, N. Vietnam	1530
	—	R. Warsaw	Warsaw, Poland	0700
	—	E. Nacional	Lisbon, Portugal	0730
11850	GSF	BBC	London, England	1600
	GSF	BBC	London, England	1600
	ETLF	R. V. Gospel	Addis Ababa, Ethiopia	0500
	LLK	R. Norway	Oslo, Norway	1700
11870	—	V. America	Greenville, N.C.	1930
11873	—	R. Lubumbushi	Lubumbushi, Congo	1500
11874	ZYN32	R. Soc. Bahia	Salvador, Brazil	0300
11885	CXA19	El Espectador	Montevideo, Uruguay	2100
	—	R. Berlin Int'l.	Berlin, E. Germany	0100
	ETLF	R. V. Gospel	Addis Ababa, Ethiopia	0430
11895	—	Austrian R.	Vienna, Austria	1100
11900	—	Austrian R.	Vienna, Austria	1100
	—	S. African BC	Paradys, S. Africa	0515
	—	R. Kinshasa	Kinshasa, Congo	1000
11905	DMQ11	Deutsche Welle	Cologne, W. Germany	0545
11910	HCJB	V. Andes	Quito, Ecuador	0600
	HSK9	R. Bangkok	Bangkok, Thailand	0415
11920	—	R. Berlin Int'l.	Berlin, E. Germany	0345
11930	—	R. Brazzaville	Brazzaville, Congo	1730
11947	—	V. Revol.	Port au Prince, Haiti	1400
	—	Duvalieriste	Haiti	1400
11960	—	R. Habana	Havana, Cuba	2230
11965	—	R. Japan	Tokyo, Japan	1930
11970	—	R. Erevan	Erevan, USSR	0700
	—	R. Brazzaville	Brazzaville, Congo	1100
12095	GSF	BBC	London, England	1800
13250	—	R. Euzkadi	(clandestine)	2130
14885	—	E. Nacional	Lisbon, Portugal	1800
14970	—	E. Nacional	Lisbon, Portugal	1800
15015	—	V. Vietnam	Hanoi, N. Vietnam	0530
15052	—	R. Libertad	(clandestine)	1300
15070	GSF	BBC	London, England	1800
15080	—	R. Peking	Peking, China	0830

19-Meter Band—15100 to 15450 kHz				
kHz	Call	Name	Location	GMT
15110	HCJB	V. Andes	Quito, Ecuador	2300
	XERR	R. Comerciales	Mexico DF, Mexico	2200

13-Meter Band—21450 to 21750 kHz				
kHz	Call	Name	Location	GMT
21500	—	R. Brazzaville	Brazzaville, Congo	1100
21520	—	Swiss BC	Berne, Switzerland	1330
21730	LLQ	R. Norway	Oslo, Norway	1700
21740	—	V. America	Greenville, N.C.	1930

CB Rigs & Rigmarole

Continued from page 12

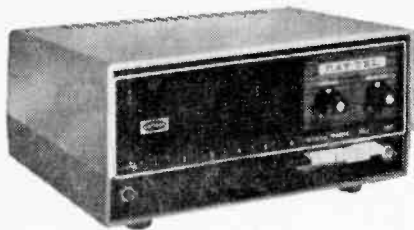

Raytheon's Ray-Tel TWR-9 CB Transceiver

operator's mouth. The 6 channels are selected by "touch tabs" on the front panel, as are other functions of the unit. Here's something else that's new: you can use the TWR-9 as a wired intercom in addition to a CB station, with the wired satellite slave unit added on as an optional accessory.

Price of the TWR-9 is \$99.95, and the satellite station is \$9.95. For more information write to Raytheon Company, Dept. PR, Lexington, Mass. 02173.

One for the Road. Lafayette Radio, 111 Jericho Turnpike, Syosset, N. Y., came up with something called the Model HB-525 23-channel mobile rig.

This is a little rig (all solid-state) with a complete set of crystals for 23 channel operation. Receiver has a 455 kHz mechanical filter, 3 position delta tuning, illuminated tuning dial. Transmitter has range boost audio, TVI filter—the whole bit! It can even be used as a PA system with very little effort.

Comes for operation on 12-volts (neg or pos ground), or on 117 VAC (with optional power supply) for \$149.95. This should be a popular unit.



Lafayette Model HB-525 CB Transceiver

I think that you'll agree that we have seldom seen so many exciting new products coming onto the market in such a short period of time. Hope that you'll be with us next issue when we'll have some more! ■

Ask Me Another

Continued from page 36

ceiver to cover the 88-108 MHz FM band. Can this be done by changing the coils on any one band except the broadcast band?

—J. D. L., Montreal, Mo.

It isn't feasible. FM broadcasting stations transmit very wide band FM requiring a different detector and broad band IF amplifiers.

No Change Needed

I own an early RCA Victor 21-inch color television set. All channels come in color. The latest color television sets reproduce black and white programs too, and color programs only when broadcast in color. Please let me know what change I can make in the circuit to convert the set into the latest type.

—F. G., New York, N. Y.

Don't change the circuit! Just place a call to the RCA Service Company and get them

to adjust it. You're not getting black and white programs in color—all your set needs is proper adjustment to kill the color when receiving black and white programs.

What Now?

An old time short wave radio was given to me recently and one tube is missing. I am unable to find a tube layout diagram. Here is a list of the tubes in place: 80, 6SF5, 6SQ7, 6F6, 6K8 and 6K7. Can you tell me the number of the tube missing?

—L. R., St. Jean, Quebec, Canada

Probably another 6K7, if there is a grid cap clip needing a tube to latch on to. Or, it might be another 6F6 if the set employs push-pull audio.

Guitar Pickup

How can I hook up an ordinary six-string guitar to an amplifier?

—M. L., Chicago, Ill.

Get a guitar "pickup" and connect it to an audio amplifier. You should be able to get one at Allied and many other radio parts stores in the Chicago area.

Talking Shoe Box

Continued from page 66

connections or disconnections. Additionally, for the protection of the set, you should not turn it on without a speaker connected to it; either the set's speaker or the home-made speaker must be across the secondary winding of the output transformer.

Science Fair. Parents and teachers will find the "Talking Shoe-Box" project quite simple for sixth and seventh graders to understand. In the preparation of an exhibit include a genuine 4- or 5-inch PM speaker for comparison of sound output and construction.

Antenna Tuner

Continued from page 46

I am of course, reporting only my own findings with a pi-network to tune the antenna circuit of my receiver. Your antenna and your receiver may already be perfectly *matched* in which case use of such a tuner would be superfluous. To find out if it will help your reception I suggest you scrounge your junk box for a couple of variable capacitors in the range of .0003 to .0005 mfd (300 to 500 mmf) and a tapped coil of some sort—or you can quickly wind one. The inductor I am using is wound on a 1¼-inch diameter form and comprises 80 turns with seven taps—one every 10 turns; the circuit in the schematic diagram is conventional. Coil and capacitors can be temporarily bread-board mounted or haywired in any convenient manner while you give the unit a whirl. If no improvement is evident through its use, your antenna is apparently well-matched to the receiver input already and you don't need the external pi-network tuner.

If you *do* find that you can peak your incoming signals to advantage, go ahead and mount your components permanently in a suitable enclosure and adopt it as a valuable station accessory. The shortwave listener will also find this coupler of considerable aid in pulling in those rare DX stations!

Tuning. Adjustments will be just the reverse of those used with a transmitter; the antenna becomes the *input* and the receiver constitutes the *load*. Pick a steady signal or even use the noise background and adjust

Admittedly, the efficiency of the "Talking Shoe-Box" speaker is considerably less than store-bought units—and commercial jobs sound better, too! Here are a few construction tips you should think about to improve speaker sound efficiency:

- The clearance between voice coil and magnet—the closer, the better.
- Magnet—the stronger the better.
- The resiliency of the cone (box cover)—should be stiff.
- The impedance of the voice coil relative to the impedance of the output-transformer's secondary winding. Exact impedance matching is best. Increase (or decrease) voice-coil impedance by adding (or subtracting) turns determined by trial and error. ■

switch S1 and C2 to peak the signal or noise. Next adjust C1 in small increments, peaking C2 again each time C1 is changed. This process corresponds to *dipping the final* and adjusting the load in tuning a transmitter but here you will be doing it *aurally* rather than *visually* unless you have an S-meter to tell the story.

Some Tips. Remember this pi-network antenna tuner can also be used for low-power transmitters. For higher-powered transmitters you'll have to use transmitting-type variable capacitors and use a heavier gauge wire. The circuit will be just the same—and since everything is adjustable none of the parts are critical.

If you can't find a 1¼-inch form for the coil use a 1-inch or 1½-inch form. If you are against winding your very own coil, then pick up an Air Dux or B&W air-RF coil. Both coil manufacturers have a 1¼-inch coil form with 8 turns per inch (32 turns for 4-inch). Both should work well with minor adjustment of capacitors. For tuning capacitors you can use those from a discarded broadcast receiver or use a smaller capacitance unit with a selector switch to connect small fixed capacitors in parallel—it'll make tuning much easier; just like having a handsread capacitor.


Also try the circuit with the end of the coil left disconnected. Shorted turns can reduce the effectiveness of L1 under some conditions. If you have to buy the 2-to-17-position switch you might want to use a coil with more turns—this could be most important for BC DX and low-frequency reception. Nothing says you can't have 17 taps on the coil—one every 10 turns. ■

Digital Circuit Tracer

Continued from page 91

bered leads of the power unit to the red binding post or positive lead of the VTVM or VOM. The indication on the meter, for each of the leads, should give a reading similar to the number on the lead. If you've used 5% or better resistors, the readings should be very close. Lead 1 should indicate 0.1 volt; lead 2, 0.2 volt; etc.

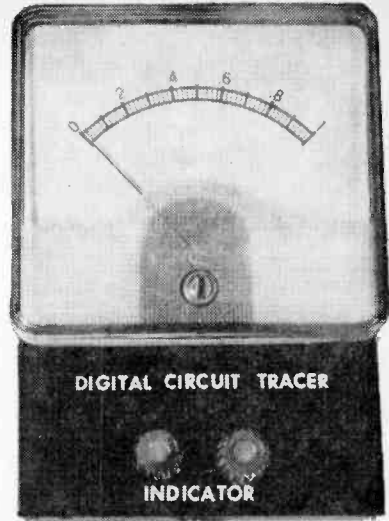Circuit Tracing. The length of wire or cable will influence the meter readings to some extent but unless the wire is very fine—or exceptionally long—you won't really be thrown for a loss. If you're using a 20,000-ohm-per-volt VOM (the 50 microamperes that flows won't lower the readings very much—a VTVM will have even less effect. ■



Front panel of Circuit Tracer contains a pair of 5-way binding posts and a meter.

BROADCASTING TOOTH

Continued from page 52

a number of transmitters and designed new ones, miniaturized components, studied solid state effects to improve them. Major problem for them was meeting size and power requirements in a miniaturized package in absence of real commercial demand for this size components.

The transmitter finally chosen has six channels of information telemetering simultaneously, six modulating codes or subcarriers on a single carrier, the code associated with a specific transducer and area of the tooth identified by frequency.

The transmitter, as Ash and Scott describe it, indicates bite forces and contacts in areas of the tooth by radiating frequency. Present size of the transmitter package is .4 by .3 by .3 inch. More work in thin film deposits, they hope, will reduce the size of the transmitter still further.

Although replaceable Mallory RS-312 batteries can be used in the tooth, the Bionetics TT-1003 batteries (.125 by .250 inch) are smaller, but can be used for short periods before recharge. Solid state sensors pick up molecular physical changes in the mouth.

Summed up, the electronic tooth packs almost enough hardware to equip a Gemini spaceship—its twenty-eight components include six tiny transmitters, solid state sensors,

six ceramic capacitors, an antenna coil, a six transistor flatpack, a resistor substrate, as well as the two rechargeable batteries.

Right now, as smart as it is, it can only broadcast a distance of one foot to a 24-channel Honeywell Visacorder, but Scott and Ash promise to add a vest-pocket amplifier they say will make it possible for the tooth to broadcast several miles.

Then we will need face the odd-ball fact we will have on this earth both sending and receiving radio-station teeth. ■



"Hurry up, Harry! I'm getting an Italian station on XIVCXII kHz."

"Pulling Power Is Amazing"

Classified MARKET PLACE

Classified Ads 55¢ per word, each insertion, minimum 10 words, payable in advance. To be included in the next available issue of RADIO-TV EXPERIMENTER, copy must be in our New York Office by October 10th. Address orders to C. D. Wilson, Manager, Classified Advertising, RADIO-TV EXPERIMENTER, 505 Park Ave., New York, N. Y. 10022.



AUTHOR'S SERVICE

WANTED Writers! Short stories, articles, books, plays, poetry. Will help place, sell your work. Write today, free particulars! Literary Agent Mead, Dept. C-38, 915 Broadway, New York, N. Y. 10010.

BOATS, MOTORS & MARINE SUPPLIES

FULL size, cut-to-shape boat patterns, blueprints. Send 60¢ for big New, illustrated "Build a Boat" catalog includes Fishing Boats, Garvies, Cruisers, Catamarans, Houseboats—Outboards, Inboards. Sailboats—7½ to 38' "How to Build a Boat" booklet \$2.50. Cleveland Boat Blueprint Co., Box 18250, Cleveland, Ohio.

BOAT Kits. Factory molded fiberglass or pre-assembled plywood. 50 models, 12' to 40'. Runabouts, Cruisers, Houseboats. Free catalog. Luger, Dept. UC-66, 9200 Bloomington Freeway, Bloomington, Minnesota.

VICRAFT Kayaks, five models, prefabricated kits from \$29.00. Dept. G.P.O., Box 145, Portage, Mich. 49081.

CINCH To Winch ton boat half effort. Stainless steel attachment fits your present winch. \$12.88. Ivey, 111 Tuckahoe Blvd., Richmond, Va. 23226.

FOR Consistent Fun, Excitement and Expert Advice, subscribe to "Camping Journal," America's Leading Camping Magazine. Only \$4.50 for 6 issues. Write Camping Journal, 505 Park Ave., New York, N. Y. 10022.

BOOKS & PERIODICALS

"REMEMBER The Scopes Trial," \$1.00. Christian Evidence League, Malverne, New York 11565.

CATALOG of all Science & Mechanics Craftprints. Send 25¢ to cover postage and handling to Craftprint Div., Science & Mechanics, 505 Park Ave., New York, New York 10022.

BUSINESS OPPORTUNITIES

I MADE \$40,000.00 a Year by Mailorder. Helped others to make money! Start with \$10.00—Free Proof. Torrey, Box 63566T, Oklahoma City, Okla. 73106.

FREE Book "990 Successful Little-Known Businesses." Fascinating! Work home! Plymouth-911-J, Brooklyn, N. Y. 11218.

RAISE capital fast—easy proven sources—Free information. Advisor, Box 48337-SM-2, Los Angeles 90048.

MAIL-ORDER Opportunity New Aid—Unprecedented Mail-Order Business. Bonus Free. Howies, 231 Forest, Centerport, New York 11721.

EARTHWORMS

BIG Money Raising Fishworms and Crickets. Free Literature. Carter Farm-O, Plains, Georgia 31780.

THERE is no charge for the Zip Code. Please use it in your Classified Ad.

FOR INVENTORS

PATENT Searches—48 hour airmail service, \$6.00, including nearest patent copies. More than 200 registered patent attorneys have used my service. Free invention protection forms. Write Miss Ann Hastings, Patent Searcher, P. O. Box 176, Washington 4, D. C.

FOR SALE—MISCELLANEOUS

BARGAINS Our Business. Catalog 10¢ Refundable. Tolocar, 2907-B West 39th Place, Chicago, Ill. 60632.

SCIENCE Experimenter—the magazine dedicated to the youth who is interested in experimentation, construction and "blue-ribbon" Science Fair entries. Send \$1.00 to Science Experimenter, 505 Park Ave., New York 10022 (includes postage and handling).

How To Write a Classified Ad That Pulls What to Say and How to Say It

Only \$1.00

Worth Its Weight In Gold

Make your classified ad pay! This handbook tells how—with examples; included is a Credit Certificate worth \$2.00 toward the cost of a classified ad in S & M. For a copy of "How to Write a Classified Ad That Pulls," send \$1.00 to C. D. Wilson, Science & Mechanics, 505 Park Ave., New York, N. Y. 10022.

HYPNOTISM

NEW concept teaches you self-hypnosis quickly! Free literature. Smith-McKinley, Box 3038, San Bernardino, Calif.

INVENTIONS WANTED

WE either sell your invention or pay cash bonus. Write for details. Universal Inventions, 298-5, Marlon, Ohio

MONEYMAKING OPPORTUNITIES

START Profitable Business in spare time. Investigate many moneymaking agency and franchise opportunities. Send 10¢ for sample copy of Income Opportunities Magazine, 505 Park Ave., New York 10022, Dept. S.

PATENT SERVICE

PATENT Searches, \$6.00; For free "Invention Record" and "Important Information Inventors Need," Write: Miss Hayward, 1028D Vermont, Washington 5, District of Columbia.

PATENT Searches—48 hour airmail service, \$6.00, including nearest patent copies. More than 200 registered patent attorneys have used my service. Free Invention Protection Forms write: Miss Ann Hastings, Patent Searcher, P. O. Box 176, Washington 4, D. C.

PERSONAL

GET out of debt—clear credit. Immediate relief—Advisor, Box 48337-EM-1, Los Angeles 90048.

LOOK Men—especially Golf Players. Cut your shoe cost. Send 25¢ for details. Delph's Leather Products, Tamaqua, Pennsylvania 18252.

BILL Problems? Poor credit no trouble. Not a loan company. Send for free application. Automatic Acceptance, 1326TV Plainfield St., Cranston, R. I., or 318TV Broadway Blvd., Reno, Nevada.

TRACTS Mailed Anywhere. Christian Tract Center, 3905 Victoria, Hampton, Va.

PETS—DOGS, BIRDS, RABBITS, HAMSTERS, ETC.

MAKE big money raising rabbits for us. Information 25¢. Keeney Brothers, New Freedom, Penna.

RADIO & TELEVISION

McGEE Radio Company. Big 1966 Catalog Sent Free. America's Best Values. Hi-Fi, Amplifiers, Speakers, Electronic Parts. Send Name, Address and Zip Code Number to McGee Radio Company, 1901 McGee Street, Dept. RTV, Kansas City, Missouri 64108.

FREE Catalog. Electronics parts, tubes. Wholesale. Thousands of items. Unbeatable prices. Arcturus Electronics-RT, 502 22nd St., Union City, N. J. 07087.

CONVERT any television to sensitive, big-screen oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans, \$2.00. Relco-A30, Box 10563, Houston, Texas 77018.

ALLWAVE Radio Kit. Tube. Transistor Included \$5.00. Headphones \$2.00. Ekeraido, Box 131, Temple City, Calif.

JAPAN & Hong Kong Electronics Directory. Products, components, supplies. 50 firms—just \$1.00. Ippano Kaisha Ltd., Box 6266, Spokane, Wash. 99207.

C.B. BUYERS' Guide—A new magazine for the buyers of Citizen's Band Electronic Equipment. Includes a Test Report Section on 5-Watt C.B. Transceivers. How to Operate on C.B.; The Social Side of C.B.; FCC Regulations. Send \$1.25—includes Postage & Handling to C.B. Buyers' Guide, 505 Park Ave., New York, N. Y. 10022.

SONGWRITERS

POEMS Wanted for musical setting and recording. Send poems. Free examination. Crown Music, 49-SC West 32, New York 1.

TREASURE FINDERS—PROSPECTING EQUIPMENT

"NEW" Scientific Instrument detects buried gold, silver, coins, treasures. \$19.95 up. Free catalog. Relco-A30, Box 10563, Houston, Texas 77018.

WATCHES, WATCHMAKING & REPAIRING


WORLD Travel Watch—Instantly tells time anywhere in the world. Free literature. Cabell Imports, 1112 Argyle Ave., Baltimore 1, Md.

BUILD, EXPERIMENT, EXPLORE, DISCOVER WITH NRI CUSTOM-DESIGNED TRAINING KITS




BUILD YOUR OWN PHONE/CODE TRANSMITTER

This is just one of seven training kits programmed into NRI's Complete Communications course. You get actual practice in building your own crystal-controlled, phone/code transmitter and putting it on the air. You experiment with modulation, "clamping" circuits, key filters, other aspects of commercial transmitter operation. Can be put on the air simply by attaching an antenna and complies with FCC regulations. As with all NRI training kits, you get the most modern features and parts.

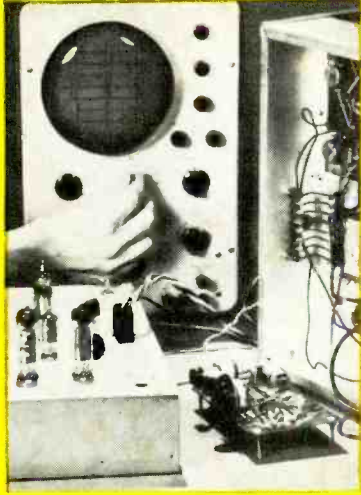

BUILD ACTUAL ANALOG COMPUTER CIRCUITS

Industry, business offices, the government and military all need trained Electronics Technicians. NRI's Industrial Electronics course prepares you. You progress through 10 carefully designed training kits, topping off your practical experience phase of training by experimenting with feedback control systems, analog computers and digital computer elements. You actually solve problems on this analog computer you build yourself. This is the *practical*, fast way to a good paying, career position.

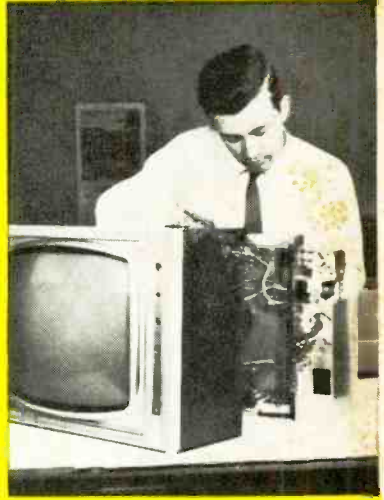

BUILD A CUSTOM-ENGINEERED TELEVISION RECEIVER

Want to earn \$3 to \$5 an hour in spare time or full-time business? In Radio-TV Servicing you learn to install, maintain, service radios, TV sets, hi-fi and stereo, other home Electronics equipment. In your training are eight training kits, including this complete, modern, slim-line TV receiver. You build it yourself, become familiar with components and circuits, learn servicing procedures... and earn extra money as you train. National Radio Institute, Washington, D.C.

Join the Thousands Who
Gained Success with NRI



"I am Frequency Coordinator for the 11th Naval District. The course was priceless." J. J. JENKINS, San Diego, Calif.



"Many thanks to NRI. I hold FCC License, am master control engineer with KXIB-TV." R. L. WOOD, Fargo, N.D.



"I am a Senior Engineering Aide. Without NRI I would still be working in a factory at a lower standard of living." D. F. CONRAD, Reseda, Calif.

Available Under NEW GI BILL

If you served since January 31, 1955, or are in service, check GI line in postage-free card.

SEE OTHER SIDE ▶

BUSINESS REPLY MAIL

NO POSTAGE STAMP NECESSARY IF MAILED IN THE UNITED STATES



POSTAGE WILL BE PAID BY

NATIONAL RADIO INSTITUTE

3939 Wisconsin Avenue

Washington, D.C. 20016

FIRST CLASS
PERMIT
NO. 20-R
Washington, D.C.



YOU GET MORE FOR YOUR MONEY FROM NRI

Below is an example of material included in just one NRI course. Other NRI home study plans are equally complete.



AMERICA'S OLDEST AND LARGEST RADIO-TV, ELECTRONICS HOME-STUDY SCHOOL

Compare if you like. You'll find—as have so many thousands of others—that NRI training can't be beat. From the delivery of your first lessons in the remarkable, new Achievement Kit sent the day we receive your enrollment, to "bite-size," easily read texts and carefully designed training equipment . . . NRI gives you more value. The picture above dramatically illustrates the material included in just one NRI course. Everything you see is included in low-cost NRI training. But NRI is more than kits and texts. It's also friendly, per-

sonal services which have made NRI a 50 year leader in the home study field.

Whatever your interest or need . . . whatever your education . . . there is an NRI instruction plan in Radio-TV Servicing, Electronics or Communications to fit your needs; tuition rates to fit your budget. Prove to yourself—your best home-study buy is NRI. Mail postage-free card today. No salesman will call. NATIONAL RADIO INSTITUTE, Electronics Division, Washington, D.C. 20016.

◀ SEE OTHER SIDE

National Radio Institute, Electronics Division
Washington, D.C. 20016

5-106

Please send me your catalog. I have checked the field(s) of most interest to me. (No salesman will call) PLEASE PRINT.

- | | |
|--|---|
| <input type="checkbox"/> Television-Radio Servicing | <input type="checkbox"/> Basic Electronics |
| <input type="checkbox"/> Complete Communications | <input type="checkbox"/> Electronics for Automation |
| <input type="checkbox"/> Industrial-Military Electronics | <input type="checkbox"/> Aviation Communications |
| <input type="checkbox"/> FCC License | <input type="checkbox"/> Marine Communications |
| <input type="checkbox"/> Math for Electronics | <input type="checkbox"/> Mobile Communications |

Check for facts on new GI Bill.

Name _____ Age _____

Address _____ Zip Code _____

City _____ State _____



**NOW 10
WAYS to
train at home
MAIL CARD
NO POSTAGE
REQUIRED**



OVER 50 YEARS
OF LEADERSHIP IN
ELECTRONICS TRAINING



ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL