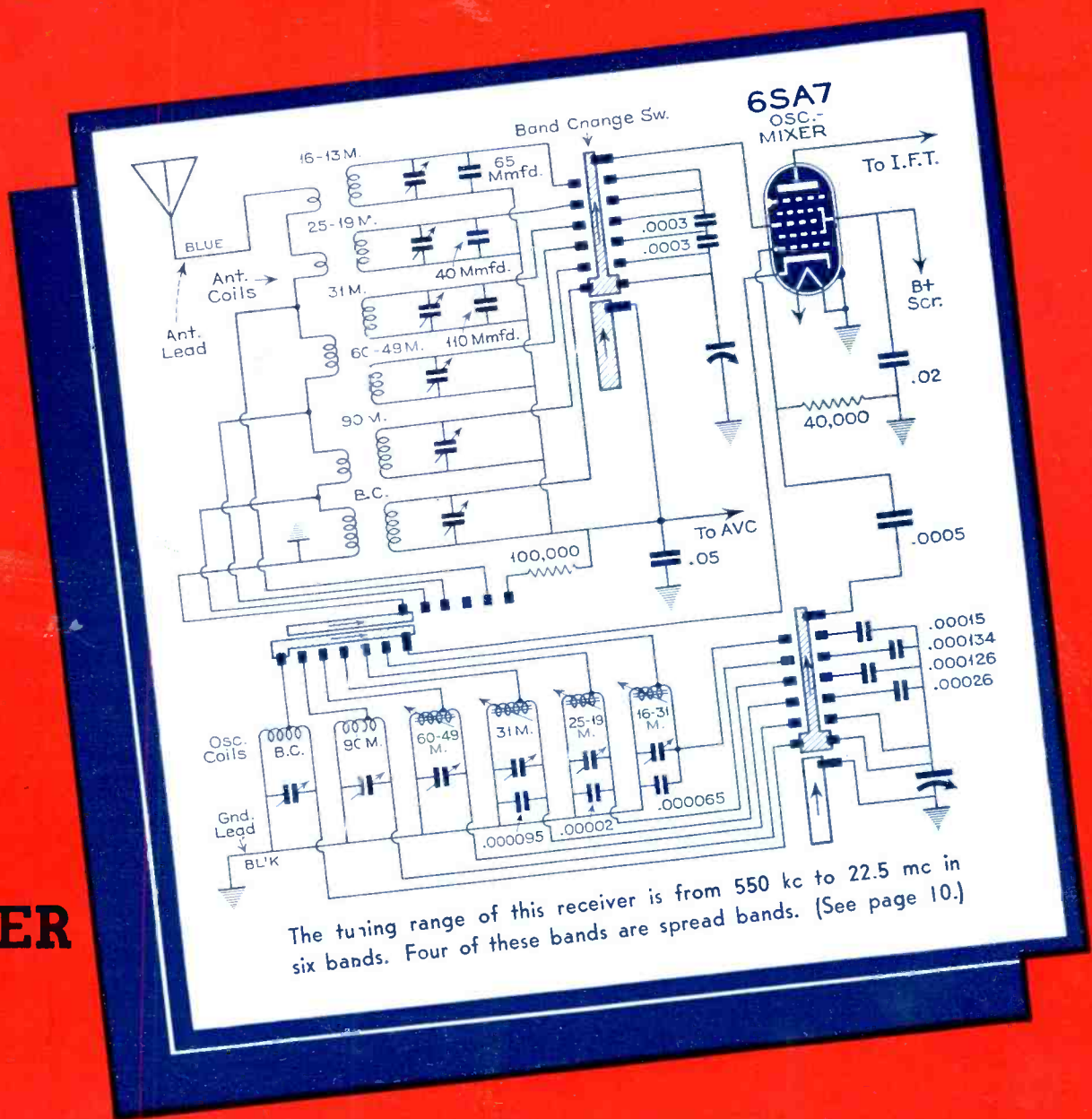


# SERVICE



DECEMBER  
1940

ANNUAL INDEX PAGES 17 to 20 INCLUSIVE

Give Your Business a Profit Present

P.R. MALLORY & CO., Inc.  
**MALLORY**



**CONDENSERS**

Mallory Replacement Condensers have proven to be just like money in the bank for thousands of radio service engineers. Millions are in use! No other line gives such complete and such dependable coverage of every replacement need. F. P. (Fabricated Plate) Capacitors made by Mallory, Mallory Tubular Condensers—now color-coded by voltage, and Fabricated Plate Tubulars Type B B each fill specific needs that are faced every working day. Be sure you can fill these needs quickly and profitably . . . specify Mallory.

**VOLUME CONTROLS**

Early in 1941, Mallory will introduce the most startling advance ever made in the field of replacement volume controls. This is a completely new Mallory development that has been years in the making. It incorporates features that will revolutionize volume control replacements. Watch this publication for an early announcement. You'll want to be first to see it . . . first to cash in on its many new advantages!



**VIBRATORS**

Mallory Vibrators have made the same important contributions in the replacement field as they have made to the efficiency of original equipment. When you install a Mallory Vibrator in an auto radio, or other battery operated receiver you know that you have given your customer the finest there is . . . and that you have fully assured customer satisfaction. Millions of Mallory Vibrators in use as original equipment testify that they have to be good.

P. R. MALLORY & CO., Inc.  
 INDIANAPOLIS INDIANA  
 Cable Address—PELMALLO

*Mallory Has Great Things in Store for You in '41*

Use  
 P.R. MALLORY & CO., Inc.  
**MALLORY**  
 APPROVED  
 PRECISION PRODUCTS

*Include* VIBRATORS • VIBRAPACKS • CONDENSERS • VOLUME CONTROLS • ROTARY SWITCHES • SINGLE AND MULTIPLE PUSH BUTTON SWITCHES • RESISTORS RADIO HARDWARE




# 10 ACOUSTICALLY CORRECT REPRODUCERS AND CABINETS

ALL WITH

*Bass Reflex*


CHOICE OF SPEAKER EQUIPMENT

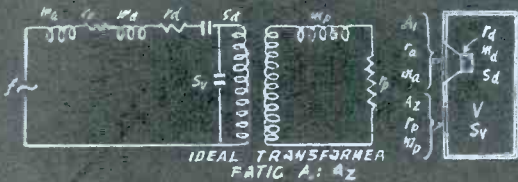


Equivalent circuit illustrating the Bass Reflex principle.




"CR" REPRODUCERS

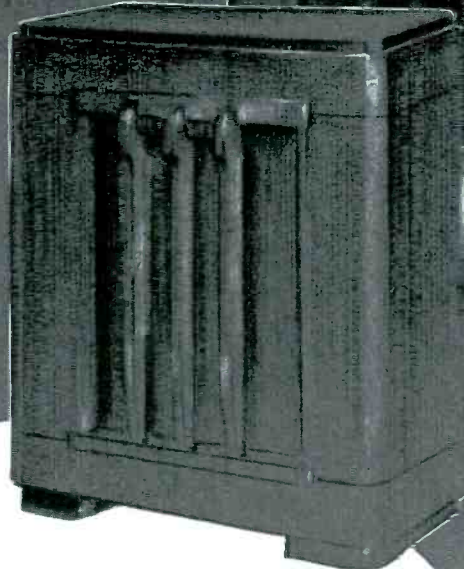

**BASS REFLEX** gives you better sound reproduction because it enables the loud speaker to function with full effectiveness, to perform even better than with an infinite baffle. This great development, originated by Jensen Engineers, is available in a complete line of acoustically-coordinated reproducers and cabinets for every application. The arresting beauty of the new "CR" Reproducers qualifies them for the finest surroundings. Equivalent performance is provided in the practical, less expensive "MT" Reproducers. Economical "ER" enclosures accommodate your choice of speakers from 8 to 18 inch sizes. Write for complete information.

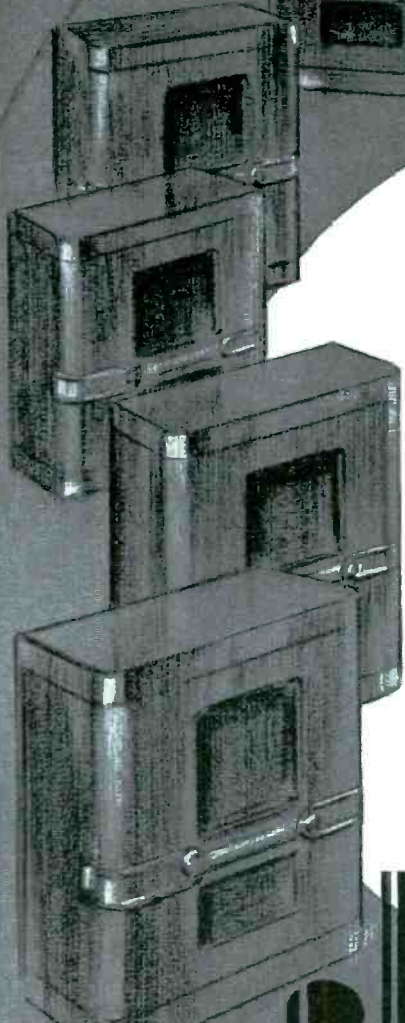

"ER" ENCLOSURES

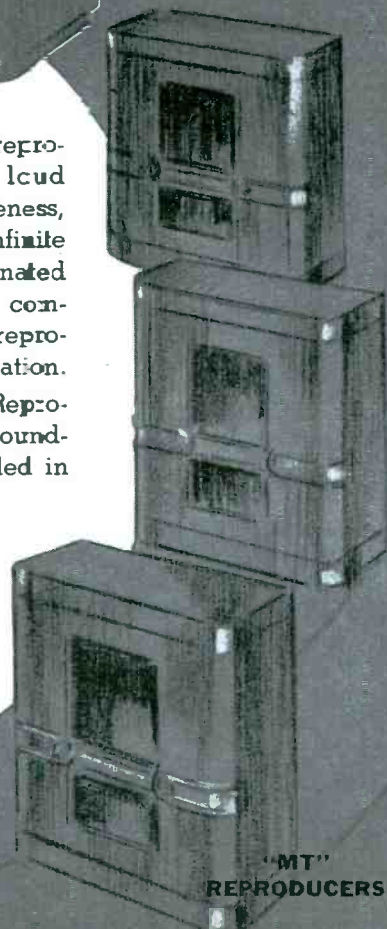

"MT" REPRODUCERS

**Jensen**  
JENSEN RADIO MFG. CO.  
6601 S. LARAMIE AVE., CHICAGO



**M**ANY large organizations employ two types of salesmen. The first of these is the "canvasser." He digs up live prospects, does the foot-work and rarely actually closes a sale. The closing of the sale, on the other hand, is handled by the second type of salesman. He makes the demonstration, discusses price, model, etc.—in short, he does the actual selling.

We have often stressed the fact that you enjoy a unique position with respect to the customer. He invites you into his home and seeks your advice. What an opportunity this presents for you to act as the canvasser for some local merchant!

With ostensibly nothing to sell, you can easily steer the conversation into related lines; find out whether your customer is in the market for some electrical appliances, for another radio set or perhaps an auto-radio receiver.

After all, you have the advantage of being regarded as an *expert*, a man who really knows the technical considerations involved and as such your advice is often welcomed. You can work with your dealers and increase both their earnings and your own.

**F**REQUENCY modulation has already reached the stage where we can state that an intimate knowledge of the servicing of f-m receivers is an immediate requirement for every Service Man. With this in mind, we present our feature article "Servicing F-M Receivers," written by no less an authority than Jack Avins, noted engineer, author and lecturer. Beginning on page 5 of this issue, Mr. Avins discusses the problems which the Service Man will encounter in receivers already in the hands of listeners throughout the country. He also gives detailed instruction concerning the alignment of this type of receiver.

His is a first-hand knowledge of the innermost workings of the particular sets about which he writes, for Mr. Avins has worked on them all; run performance tests, corrected faults, and thoroughly analyzed them, all with the purpose of being able to tell you how to fix these receivers more efficiently.

We feel sure that you will find his article both interesting and instructive.

	Page
Band-Spread Tuning (Crosley 42BR)	10
Busy Shop	22
Circuits. <i>By Henry Howard</i>	10
G. E. HM80 F-M Receiver Circuit	5
Servicing F-M Receivers. <i>By Jack Avins</i>	5
Sound Ideas. <i>By Jay Allen</i>	15
Stromberg Carlson 505H, 505HB F-M Receiver Circuit	6
Stromberg Carlson 585 A-M, F-M Receiver Circuit	13
<b>Annual Index</b>	17
<b>Associations</b>	29
<b>Book Reviews</b>	21
<b>Case Histories</b>	
Stewart-Warner Hudson DB40, SA40	23
Stromberg Carlson 520PS, 520PN, 520PG	14
Wells Gardner 6C13, 6C14, D1090, D1091. <i>By J. K. Rose</i>	14
Wilcox Gay A89, A91, A92, A93, A95	14
<b>Circuits</b>	
Airline 04BR389T R-F and First Detector	14
Admiral G6, XG6	11
Belmont Permeability Tuning	12
Crosley 42BR Band-Spread	Front Cover
Emerson Phonograph Inverters	12
F-M Limiter and Discriminator	8
G. E. HM80 F-M Receiver	5
Lafayette 1102 Inverse Feedback	14
Measuring Limiter Grid Current	9
Motorola 83F1 Motor Tuning	14
Philco 41-788, Code 121, 122	12
Precision 852 Multitester	28
RCA 16T4 Band Switching	14
Stromberg Carlson 505H, 505HB F-M Receiver	6
Stromberg Carlson 585 A-M, F-M Receiver	13
Zero Center Meter	8
<b>Cover Diagram</b>	
Band-Spread Tuning (Crosley 42BR)	10
<b>Index to Advertisers</b>	36
<b>Manufacturers</b>	
Bulletins and Catalogs	32
Displays	30
Personnel	30
New Products	35
New Test Equipment	34
Sound News	33
<b>Sound</b>	
Sound Ideas. <i>By Jay Allen</i>	15
Sound News	33
<b>Test Equipment</b>	
New Test Equipment	34
Precision 854 Multitester	28
Servicing F-M Receivers. <i>By Jack Avins</i>	5

Copyright, 1940, Bryan Davis Publishing Co., Inc

BRYAN S. DAVIS  
*President*

JAS. A. WALKER  
*Secretary*

Chicago Office:  
608 S. Dearborn Street  
C. O. Stimpson, Mgr.  
Telephone: Wabash 1903

Published Monthly by the  
**Bryan Davis  
Publishing Co.**  
Inc.  
19 East 47th Street  
New York City  
Telephone: PLaza 3-0483



PAUL S. WEIL  
*Advertising Manager*

A. GOEBEL  
*Circulation Manager*

Wellington, New Zealand  
Tearo Book Depot

Melbourne, Australia:  
McGill's Agency

Entered as second-class matter June 14, 1932, at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price: \$2.00 per year in the United States of America and Canada; 25 cents per copy. \$3.00 per year in foreign countries; 35 cents per copy.




# Constant Voltage

FOR YOUR LABORATORY, YOUR PRODUCT, OR YOUR PRODUCTION LINE



# STEAD I-VOLT

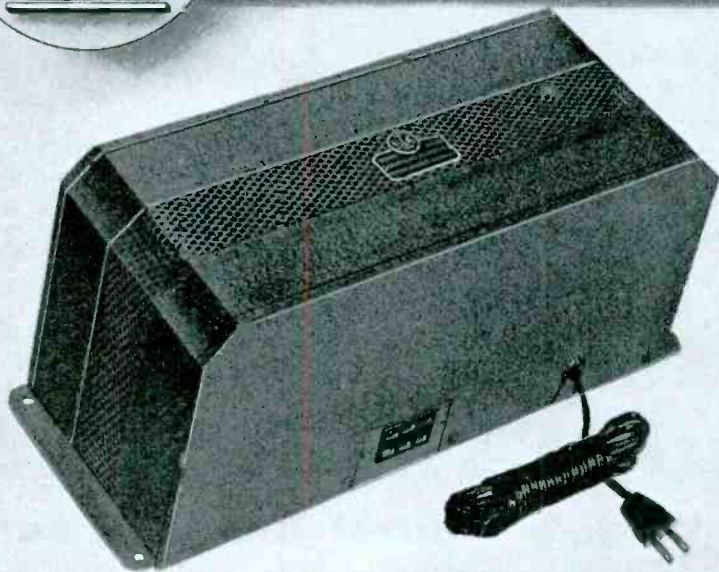


- \* ACCURACY 1%
- \* INDEPENDENT OF LOAD
- \* NO MOVING PARTS
- \* HIGH POWER FACTOR
- \* HIGH EFFICIENCY
- \* NEGLIGIBLE TIME CONSTANT
- \* LOW DISTORTION
- \* LOW TEMPERATURE RISE

## AUTOMATIC VOLTAGE REGULATORS 95-130 VOLT INPUTS . . . 110, 115, 120 VOLTS OUTPUT $\pm$ 1%

The UTC automatic voltage regulator is NEW. It involves no moving parts and effects instantaneous correction for either transient or chronic line voltage fluctuations.

### STANDARD TYPES

Type No.	Capacity VA — 60 Cyc.	Net Price
AR-1	15	\$12.00
AR-2	30	15.00
AR-3	60	21.00
AR-4	120	28.00
AR-5	250	46.00
AR-6	500	67.00
AR-7	1000	110.00
AR-8	2000	200.00

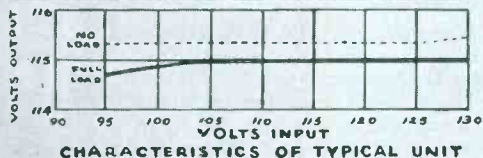

Designs for 220 volt service available at 25% increase in price, for 50 cycle units increase price 25%; for 42 cycles, 35% increase; for 25 cycles, increase price 100%. Special secondary voltages available to customers' specifications at small increase in price.

### SPECIAL UNITS

The unique design of these regulators makes possible the construction of special units with relative ease. The output can be arranged to provide filament and plate voltage, or any other special voltages that may be required. Write for details.



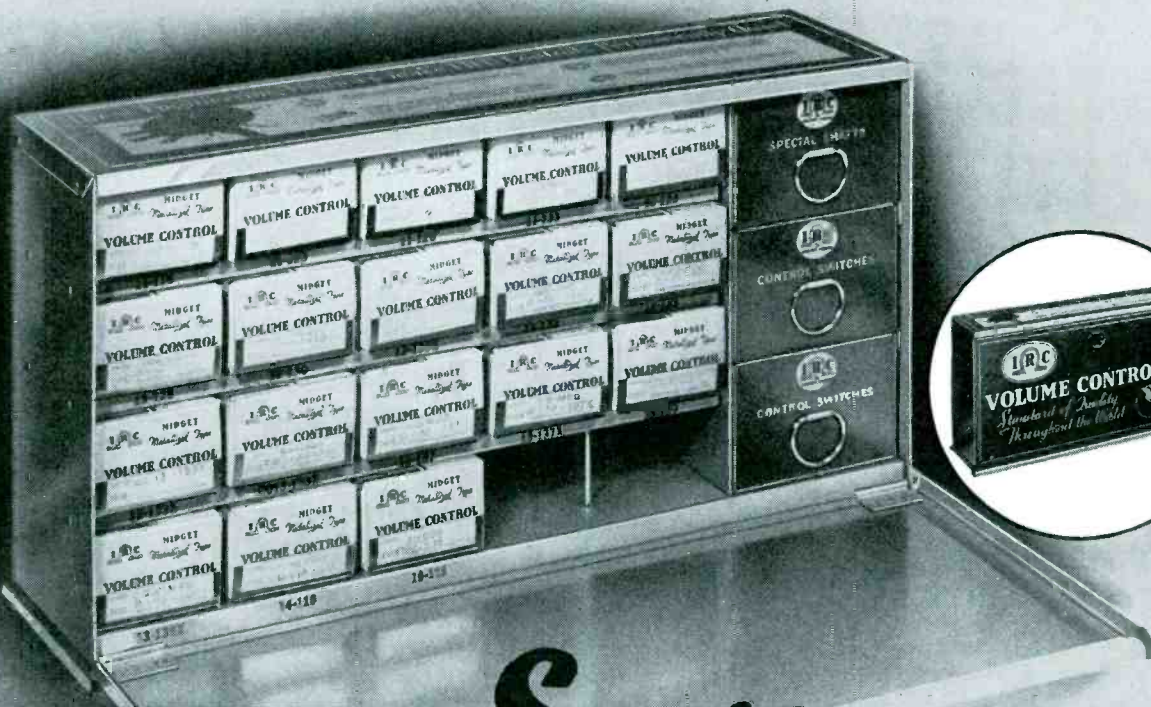
# UNITED TRANSFORMER CORP.

150 VARICK STREET ★ NEW YORK, N. Y.  
EXPORT DIVISION: 100 VARICK STREET NEW YORK, N. Y. CABLES: "ARLAB"



THE FIRST REAL MOVE TOWARD CONTROL STANDARDIZATION



Closed view of cabinet



**THE FIRST REALLY "UNIVERSAL" CONTROLS**

In every respect IRC Type D Controls are exact, smaller-size reproductions of the larger IRC Type C Controls. They are unique in that, although midgets, they are fully equal in quality to the larger controls. Nothing has been left out. Only the size is different, and the only change has been the addition of Tap-in Shafts which make them much easier to install in crowded chassis and far more universal in application. Simply select the control you need, tap in the proper shaft according to easy instructions and the job is done—quicker, easier and from a small stock that will represent a tremendous saving in time, money and effort to the average serviceman whether he replaces only a couple of controls a week or a couple of dozen. Type D's are small enough to fit almost anywhere; large enough for real dependability; sturdy enough to stand up under the most severe conditions.

**Save TIME... MONEY... EFFORT**

**on Volume Control Replacements**

- ✓ Reduce your stock and your investment.
- ✓ Have the control you need—when you need it.
- ✓ Simplify installations, speed up work, give customers faster, better, more efficient service.
- ✓ Avoid frequent need for more costly special replacements.
- ✓ Keep your controls systematically in a good-looking cabinet clean and free from injurious dust and dirt.

The 18 IRC Type D Universal ("All-Purpose") Volume Controls, 6 switches and 5 extra tap-in shafts of special design contained in this IRC Master Radiotrician's Cabinet handle from 60% to 75% of all volume control replacements as shown by actual IRC records! By supplementing them with a few additional IRC Type D Controls selected with a view to your own local requirements, you are in a position to handle the great majority of all replacements—from stock—at an investment so low it will amaze you!

You are equipped for better, faster service. You save time because it is no longer necessary to order a control every time you need one. You simplify installation because IRC Type D Controls with their Tap-in Shafts are easier to install and may be used universally for replacing "midgets" or larger "old-style" controls. You avoid frequent need for more costly special replacements because this Cabinet gives you a choice of 4 shaft types.

The handsome All-Metal Cabinet is included with your purchase. You pay only \$14.97, the standard net price of the 18 controls, 6 switches and 5 extra shafts with which it is factory-packed. See it at your IRC jobber's, or write for details and complete list of controls that are included. (Cabinets not sold empty.)



**INTERNATIONAL RESISTANCE CO.**

401 N. Broad St., Philadelphia, Pa.

**Type D UNIVERSAL VOLUME CONTROLS**



## SERVICING F-M RECEIVERS

By JACK AVINS

THE general theory of frequency modulation has been covered previously on these pages.<sup>1</sup> It is not necessary, therefore, for us to discuss the improvement which f-m makes possible, in fidelity and signal to noise ratio, over a-m. However, since this article deals with the f-m receiver, it is appropriate to consider what happens to the f-m signal as it passes through the various stages of the receiver.

To take a definite example, let us assume that the receiver is tuned to receive a 45-mc, 400-cycle, 100% modulated signal. Accordingly, the 45-mc f-m signal will vary between 45.075 and 44.025 mc at a rate of 400-cycles-per-second. This signal, with its side bands, which occupy a total band of about 150 kc, is amplified in the r-f stage (if one is used) and fed to the grid of the mixer tube. (See Figs. 1

and 2.) Assuming that the receiver has an i-f of 4 mc, the oscillator would be operating at either 49 or 41 mc to produce a beat frequency of 4 mc in the plate circuit of the mixer tube. Of course, this resulting 4-mc i-f signal has the same characteristics as the original 45-mc signal, in that its frequency varies at the same 400-cycle rate from 3.025 to 4.075 mc. This i-f signal is amplified by the several stages in the i-f amplifier and is then impressed on the grid of the limiter tube. The limiter tube has no counterpart in the a-m receiver. It is designed to suppress the very thing which is required in the operation of an a-m receiver—that is, the function of the limiter is to remove all amplitude variations in the signal and to leave only the frequency variations.

The pure frequency-modulated output of the limiter is fed to the *discrimi-*

*nator* or frequency-detector stage of the receiver. This stage corresponds to the second-detector stage in the a-m receiver, but the discriminator is designed to translate the frequency variations into the original audio signal, whereas the a-m detector translates the amplitude variations into the desired audio signal.


With the recovery of the 400-cycle note in the output of the discriminator, the signal is passed on to a *de-emphasis* circuit, placed in the input circuit of the first audio stage. From this point on, the 400-cycle note passes through the various stages of the audio amplifier and finally reaches the voice coil of the speaker.

### The Antenna

Merely because frequency modulation has the inherent property of discriminating against noise and interference, it should not be assumed that no attention need be paid to the antenna. Ac-

<sup>1</sup>"Frequency Modulation," by Jack Avins, SERVICE, Nov. 1940, p. 3.

Fig. 1. G. E. HM80 f-m receiver circuit.

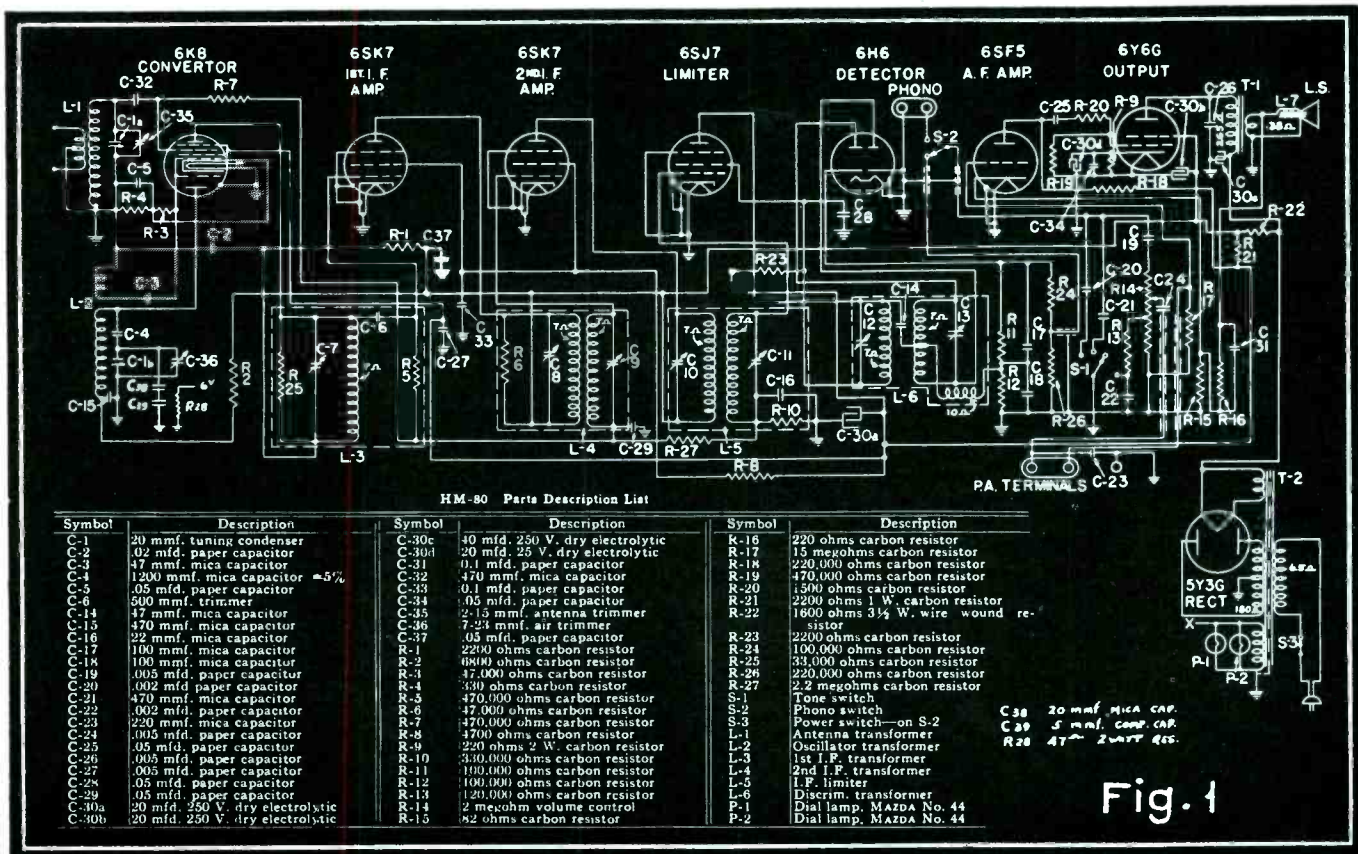

tually, wide-band f-m requires that the signal should at all times be at least twice as great as any interference which may be present. Where noise is more than half the strength of the signal, the noise will be amplified at the expense of the signal. In such cases the signal-to-noise ratio will be reduced. In locations where the signal strength is very high, almost any length of wire attached to the antenna post will be satisfactory. However, if the signal strength is low a good dipole antenna must be used. As with all antennas, its location should be as high as possible and as far away from sources of interference as is practicable. It is sometimes advantageous to rotate the antenna until the greatest desired signal is obtained.

Some combination f-m and a-m receivers are designed so that the same dipole antenna can be used for both f-m and a-m reception. In these receivers the band switch takes care of the change required in the input circuit so that the dipole can be used efficiently on the lower frequencies. In other receivers provision is made for separate antennas for the f-m and a-m bands.

#### The R-F Amplifier

The purpose of r-f amplification in f-m receivers is to provide increased selectivity; this has the advantage of reducing image and other interference. At the same time, the gain provided by using an r-f stage provides a greater signal at the limiter grid, so that more effective limiting action is obtained for weak signals.

The use of f-m as against a-m does not introduce any special problems in the r-f amplifier. In particular the required band width of 150 kc is readily obtained because of the high frequencies used for f-m transmission. Contrary to a popular misconception, there is no sideband cutting in f-m r-f ampli-

fiers, because a bandwidth of 150 kc at 45 mc corresponds to a band width of about 3 kc at a carrier frequency of 1000 kc. Thus it is just as easy to amplify a bandwidth of 150 kc at 45,000 kc as it is to amplify a 1000-kc signal which has a total bandwidth of 3 kc.

Incidentally, in the r-f section of combination f-m, a-m receivers, it is general practice to use a special 6-section tuning condenser with the lower capacity sections used for f-m and the higher capacity sections for a-m. The use of such an arrangement enables a higher L/C ratio to be obtained and at the same time provides the smaller tuning capacitance required to cover the comparatively small range from 42 to 50 mc.

In servicing the r-f portion of f-m receivers it is of great importance not to disturb the lead dress. These leads have an appreciable reactance at the high carrier frequencies used in f-m. For the same reason, wherever the replacement of by-pass condensers or other parts are required, exact duplicate parts should be used.

#### Mixer and Oscillator

The present general practice in f-m receivers is to use a single 6SA7 tube as mixer and oscillator. The tube performs satisfactorily as both an oscillator and mixer at frequencies as high as 50 mc, the upper limit of the f-m band. To increase the selectivity of the input circuit, the cathode resistor of the 6SA7 is sometimes unby-passed; this increases the selectivity by decreasing the loading of the tube across the mixer tuned circuit.

Special attention has been paid to the design of the oscillator circuit in f-m receivers in order to secure stable operation. Because of the high frequency at which the oscillator operates, even a small percentage variation or drift in its frequency will cause a considerable amount of detuning and prevent operation on the central portion of


the discriminator characteristic.

It is general practice to provide some form of temperature compensation in the oscillator circuit to achieve the required degree of frequency stability. This may take the form of a condenser which has a temperature coefficient of the right amount and in the right direction to compensate for the frequency drift which would otherwise occur as the receiver gradually comes to its normal operating temperature. Needless to say, the exact replacement condenser is required, should replacement ever be necessary. Using a condenser of the correct capacitance is not enough; it must also have the proper temperature coefficient. To assure proper operation of this form of temperature stabilization, the compensating condenser must be mounted in a definite position which should not be changed in the course of service operations. In some instances, the compensating condenser may be mounted near a resistor which acts as a heater so that the desired variation in capacitance is obtained.

To reduce the effect of variations in operating voltage to a minimum, the VR150 regulator tube has been used to regulate the plate supply to the oscillator. The regulator tube prevents variation in the frequency which might occur as a result of line voltage variation (not heater voltage, though) or as a result of variation in the B-voltage due to the variable drain on the power supply during the audio cycle.

Because of the nature of f-m, the voltage supply to the oscillator and mixer must be carefully filtered so as to prevent any hum modulation of the oscillator frequency, that is, to prevent the frequency of the oscillator from varying at a 60- or 120-cycle rate. The effect of such hum modulation is to frequency modulate the i-f signal and introduce an undesired hum into the audio signal. Even a very small percentage modulation of the oscillator frequency will cause an appreciable amount of hum in the audio output.

Fig. 2. Stromberg Carlson 505H, 505HB f-m receiver circuit.

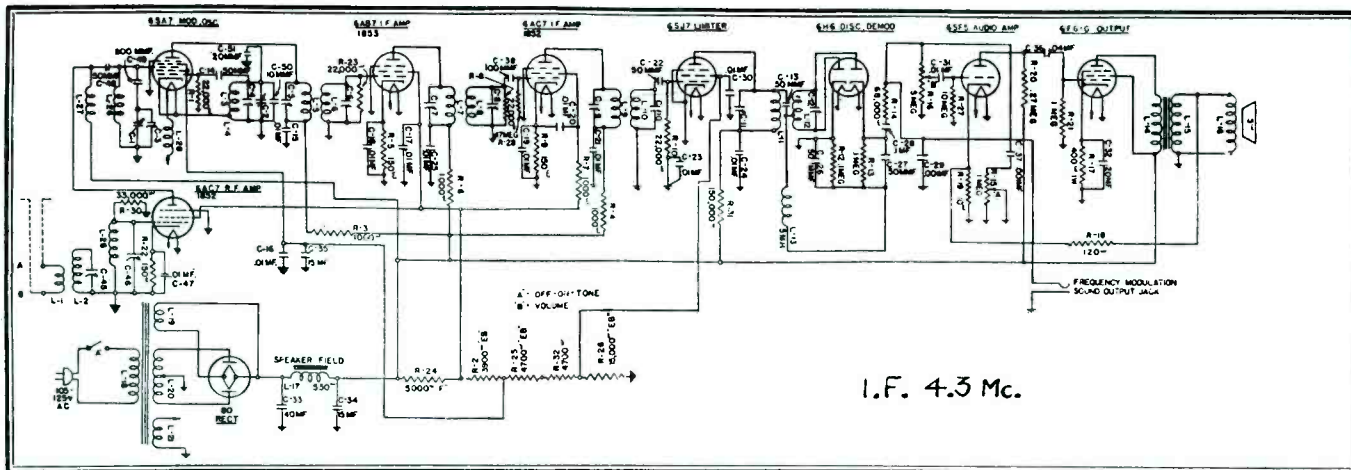



Where hum is encountered in f-m receivers, one of the first sources to be suspected (exclusive of the a-f amplifier) is the oscillator tube. This should be replaced, and if there is still no improvement, the filtering of the voltage supply to the oscillator should be checked.

F-m receivers are usually designed so that the oscillator works below the signal frequency. This is, of course, in direct opposition to the conventional practice followed in broadcast and short-wave receivers. Operating the oscillator below the signal frequency has the advantage that somewhat greater stability is secured because of the lower frequency and at the same time greater freedom from image interference is usually obtained because the image response is taken out of the television channels which lie above the f-m band. Although the latitude of the trimmer

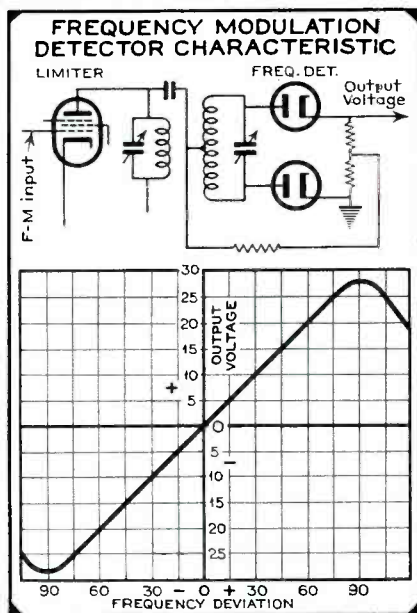


Fig. 3. The output of the discriminator is proportional to the frequency deviation of the signal from the center i-f.

will not always permit the oscillator to be aligned to the wrong frequency (above, rather than below the signal), this difference from conventional a-m practice should be kept in mind.

#### I-F Amplifier

The i-f amplifier in f-m receivers is more complex than in a-m receivers because of the higher frequency and because of the greater gain which is necessary to secure enough signal for the proper operation of the limiter. Again the higher bandwidth (150 kc) required does not present a difficult problem because the intermediate frequency is considerably higher than the 465 kc customarily used in a-m receivers. To take an average f-m i-f of say 4 mc, it is no more difficult to secure a bandwidth of 150 kc at this frequency than

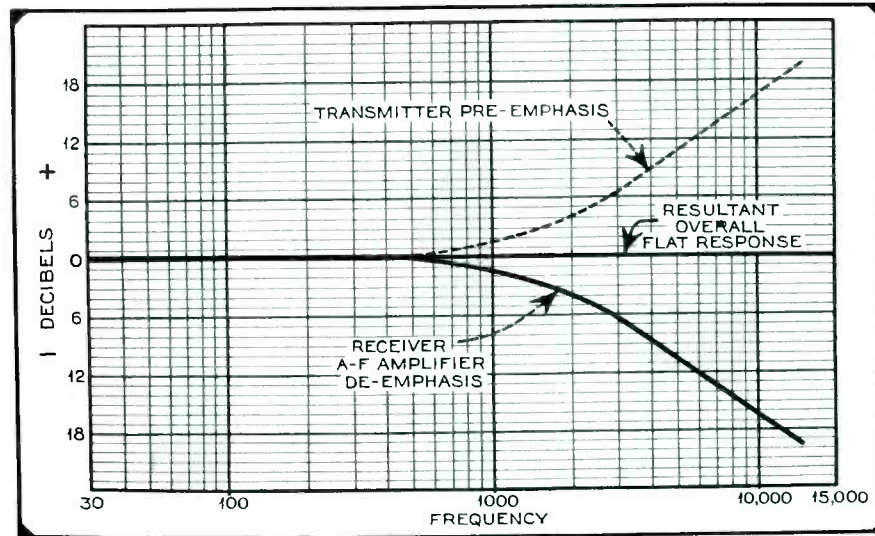


Fig. 4. The gain in the a-f amplifier of an f-m receiver is progressively lower for the higher audio frequencies.

it is to secure a bandwidth of 15 kc at 400 kc; the latter problem corresponds largely to that encountered in the high fidelity a-m receiver. Actually, the requirement for flat response over the i-f band is less severe in f-m receivers, since the limiter removes the effects of any non-uniformity in the amplification over the band. In addition to providing a bandwidth of roughly 150 kc, the f-m i-f amplifier must have sufficient selectivity so that adjacent channel interference is prevented.

In combination receivers designed for both f-m and a-m, it is common practice to use the same i-f tubes for both a-m and f-m amplification. This is usually done by connecting the f-m and a-m transformers in series (See SERVICE, Nov. 1940, p. 7.) or by providing a switching arrangement so that either the f-m or a-m transformers are automatically selected by the band switch. In some instances only one i-f tube is used for a-m, so that only the first tube uses this dual transformer arrangement. The output of the first tube then feeds directly into the a-m second detector, while the f-m output of the first i-f stage feeds into another i-f stage (for f-m only) and from this into the limiter and the discriminator. This arrangement is practical because one i-f stage is usually adequate for a-m reception, while at least two are necessary for satisfactory f-m operation.

In some combination receivers, see page 13 this issue) the i-m i-f amplifier is kept entirely separate from the a-m i-f amplifier. In receivers of this type, the only connection between the r-f and i-f section of the f-m and a-m receivers is the common power supply.

The service problems arising in connection with f-m i-f amplifiers are much the same as with a-m i-f amplifiers. Because of the higher operating frequency, and greater gain, however, it is likely that more trouble will be en-

countered as a result of regeneration and improper alignment. The precautions concerning the proper lead dress and the use of physically identical components apply with almost equal force to the i-f amplifier as well as to the r-f amplifier.

#### The Limiter

The function of the limiter is to remove any amplitude modulation which may have crept into the f-m signal. This amplitude modulation may be the result of noise or an interfering signal; it may have been present in the transmitted signal and ordinarily would be removed by the limiter; or it may be amplitude modulation hum which is introduced in the r-f, i-f or mixer. If the limiter is not functioning properly, interference or distortion from one or more than one of these possible sources may be present in the output of the i-m receiver. For this reason it is important that proper operation of the limiter be secured.

The limiter is an ordinary amplifier stage, usually a sharp cutoff pentode, which is operated at zero bias and with a low plate and screen voltage (about 90 volts). As a result of these operating conditions, the output of the limiter is limited in one direction by plate current cutoff and in the other direction by the fact that the plate current of the limiter tube can never rise above the value corresponding to the zero bias plate current. Thus, provided the signal at the limiter grid is always in excess of about 7 volts (this corresponds in most receivers to an input signal of about 10 or more microvolts) the output of the limiter will not exceed the value corresponding to a grid swing between cutoff and zero bias. If the signal falls below about 5 volts, however,

the limiter will not have sufficient signal to function properly and the entire operation of the f-m system will be impaired.

In this connection, it is worth while to point out that the discriminator responds to both amplitude and frequency variations in the signal. It is up to the limiter to remove the amplitude variations so that the discriminator can produce an output which is proportional only to the original frequency variations introduced into the signal at the transmitter. If the amplitude variations are not removed by the limiter, they will appear in the output of the discriminator in the form of noise and undesired signals.

The limiter stage contains relatively few components so that it is a simple matter to check its operation. When the limiter is functioning properly the signal voltage at the input to the limiter can be increased from about 5 volts up to above 50 volts without any appreciable increase in the signal produced in its output. The most convenient point at which to check the output of the limiter is at point A in Fig. 7 since the d-c voltage at this point is proportional to the output of the limiter. To obtain the relatively high signal voltage required at the limiter grid for this check, it is most convenient to feed the signal to the grid of the mixer tube. The r-f grid lead may have to be disconnected in order to obtain sufficient output from the signal generator, since the r-f coil has only a few turns and thus acts to short circuit the signal generator output.

The time constant of the resistor and condenser in the limiter grid circuit must be small in comparison with the highest audio frequency and high in comparison with the intermediate frequency. Since the latter is of the order of 3000 kc, whereas the former is about 15 kc, this condition is easy to realize. In practice, a value of about 2 microseconds is widely used. In the event that the improper resistor-con-

denser combination is used in the limiter grid circuit, the limiter will not function properly. Should it be necessary to replace any of the condensers or resistors in the limiter grid circuit, the specified values should be used to make the replacement.

#### Discriminator

A typical discriminator characteristic is shown in Fig. 3. As is evident in the figure the output of the discriminator is proportional to the frequency deviation of the signal from the center i-f up to a maximum limit of about 85 kc. The output of this particular discriminator is some 30 volts for a deviation of 75 kc which corresponds to 100% modulation. When the discriminator circuit is in proper adjustment, its characteristic should be linear for at least 75 kc on either side of the center frequency.

It should be understood that the characteristic shown in Fig. 3 assumes a constant input signal is being fed to the discriminator. In practice this will mean that the input signal is strong enough for the limiter to level out amplitude variations in the signal.

#### AVC in F-M Receivers

In the a-m receiver the purpose of avc is to keep the carrier level at the second detector at a constant value regardless of the strength of the input signal. Naturally the avc action does not remove the amplitude variations in the signal since this would completely remove the intelligence.

In the f-m receiver, the problem of automatic gain control is somewhat different in that the signal which is delivered to the discriminator must have a constant amplitude. As we have already seen, the limiter accomplishes this. For the limiter to be effective, however, the input signal to the limiter must be as large as possible and preferably more than 10 volts. For this reason any avc action which would tend to reduce the signal at the limiter grid to some low common level is undesirable.

For the reasons stated above it is

common practice not to use avc in f-m receivers but to depend on the limiter to remove all amplitude variations from the signal which is applied to the discriminator. To prevent overloading with a strong input signal, the use of a small coupling condenser and grid leak in the grid circuit of each of the i-f stages is common. With this arrangement, the bias generated by grid current is sufficient to provide all the necessary control action. Where avc is used in f-m receivers, it is always of the delayed type. This means that no control voltage is applied to the r-f or i-f tubes until the signal at the limiter grid is sufficiently strong so that the limiter will function effectively. This usually calls for at least ten volts to be developed at the limiter grid before the gain of the r-f and i-f amplifier is appreciably reduced.

#### Audio Amplifier

Because of the wider range covered in f-m, the design of the amplifier and speaker system differs somewhat from those used in a-m receivers. The overall frequency response, unlike that of the a-m amplifier, is not flat but the gain is

Fig. 7. The limiter removes any amplitude modulation before the signal is fed to the discriminator.


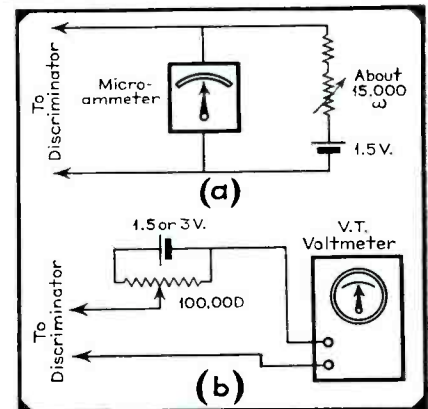


Fig. 5. A simple expedient can be employed to bring the pointer of a meter to the center of a scale for "zero-center" use.

progressively lower for the higher audio frequencies, as illustrated in Fig. 4. It will be noted that the *de-emphasis*, as this progressive attenuation is called, is the inverse or opposite of the *pre-emphasis* of the higher audio frequencies introduced at the transmitter. As a result, the overall audio response of the f-m system is flat since the *de-emphasis* in the receiver audio amplifier compensates exactly for the *pre-emphasis* in the transmitter.

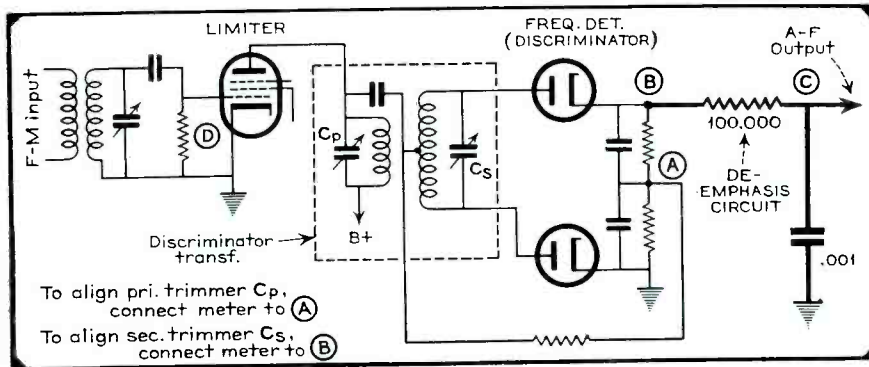Usually the *de-emphasis* in f-m receivers is accomplished by a series resistor and shunt condenser in the input circuit of the audio amplifier. When this is done the desired *de-emphasis* is obtained in the input circuit so that the frequency response of the audio amplifier and speaker can be essentially flat. The advantage of putting the *de-*



emphasis circuit in the input is that by so doing the response of the remainder of the audio system will be flat for a-m reception and for record reproduction. The usual constants for the de-emphasis circuit are about 100,000 ohms for the resistor and 0.001 mfd for the shunt condenser. This gives a time constant of 100 microseconds which is the same as that used for pre-emphasis at the transmitter. Because the frequency response of the audio system is not entirely flat, it is customary for a somewhat lower value of time constant to be used in de-emphasis circuits. Thus values of R as low as 70,000 ohms in combination with a 0.001 mfd condenser are not uncommon.

### Alignment

The alignment of f-m receivers can be carried out with a good signal generator which covers the range through 50 megacycles on fundamentals. Visual alignment equipment is not necessary although it seems probable, when f-m comes into wider use, that special frequency wobblers will be developed for the particular job of speeding up alignment of the i-f amplifier. For the present, provided the manufacturer's instructions are followed, an excellent alignment job can be done using an unmodulated signal generator.

In addition to the signal generator, a special output indicator is required for f-m alignment. The best instrument for this purpose is the electronic or d-c vacuum-tube voltmeter. The high input resistance of this voltmeter makes it possible to measure the rectified output voltage of the discriminator (at points A and B in Fig. 7) as well as the rectified voltage produced in the limiter grid circuit (at point D in Fig. 7). Measurements at each of these points in the discriminator and limiter circuits are required in order to align an f-m receiver.

If the electronic voltmeter is of the center-zero type, then the instrument can be used directly to measure the output of the discriminator at point B in Fig. 7. As the discriminator characteristic is Fig. 3 shows, the voltage at this point varies from a high positive value through zero to a corresponding high negative value, as the frequency of the input signal is varied. For this reason a center-zero type of meter is convenient in making the adjustments required in the discriminator circuit.

If the electronic voltmeter is not of the center-zero type, then a small C-battery can be placed in series with the voltmeter so as to bring the pointer to approximately the middle of the scale (with the leads shorted, of course). It is not necessary that the pointer be

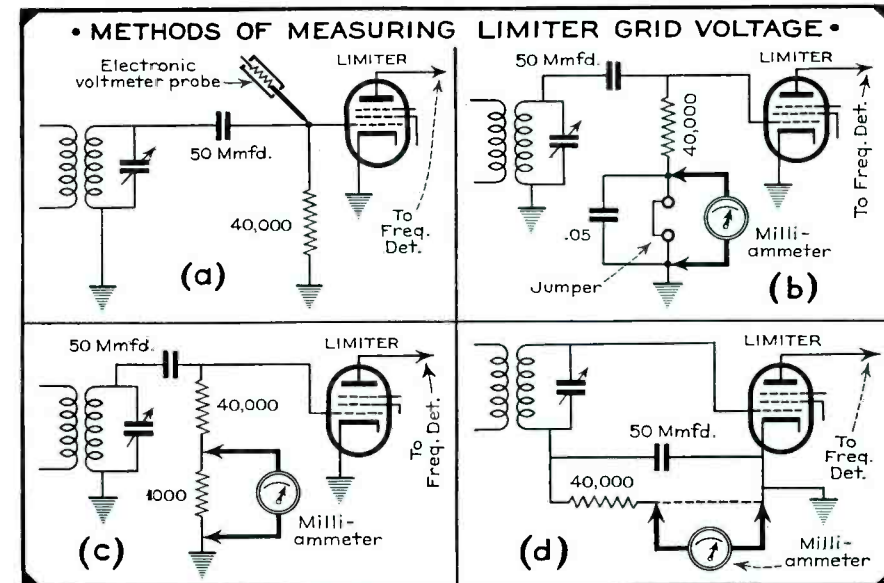


Fig. 6. Many methods can be used to measure the limiter grid current during alignment of the f-m receiver.

brought to the exact center of the scale; any convenient reference indication near the center of the scale is satisfactory. As is illustrated in Fig. 5 (b), the adjustment of the pointer can be readily made by placing a high resistance potentiometer across the battery.

In the event that an electronic voltmeter is not available, it is possible to use a center zero microammeter in adjusting the secondary winding of the discriminator. A meter having a sensitivity of about 200 microamperes is satisfactory. It should be connected to the discriminator through a resistor of about 100,000 ohms to reduce the loading on the discriminator.

Where a microammeter of the conventional left zero type is available, it can be converted into the center zero type by using the circuit shown in Fig. 5 (a). With this arrangement R is adjusted so that a center scale deflection is obtained. The meter can then be used as a center-zero instrument for discriminator alignment.

Either an electronic voltmeter or a milliammeter in the limiter grid circuit can be used to indicate the output voltage during the alignment of the i-f and r-f section of the f-m receiver. Several limiter circuit arrangements in use are shown in Fig. 6. If an electronic voltmeter is available, it is only necessary to connect it directly to the grid of the limiter tube. If a circuit similar to that at (d) is used in the receiver, however, it is preferable to connect the electronic voltmeter probe to the high side of the grid resistor rather than directly to the grid of the limiter. Regardless of the circuit it is possible to connect the electronic voltmeter probe directly to the grid, since the capacitance of the probe is isolated from the grid circuit by the one megohm resistor which is generally incorporated in the signal-circuit probe of the voltmeter.

Where an electronic voltmeter is not available, the voltage at the limiter grid can be measured by inserting a milliammeter in series with the grid resistor in the limiter grid circuit. In some receivers a jumper is provided in the grid circuit (see Fig. 6 (b)) for this purpose. An 0 to 3 milliamperere meter is satisfactory for this measurement. When the alignment is completed the jumper should be replaced, of course, so as to complete the grid circuit.

Where no jumper is provided, the same method can be used but the ungrounded end of the milliammeter should be by-passed to prevent possible feedback. The same principle also applies to the different arrangements shown in the various circuits shown in Fig. 6.

To eliminate the necessity for unsoldering leads where an electronic voltmeter is not available, one manufacturer uses a 1000-ohm resistor in series with the 40,000-ohm grid resistor. (See Fig. 6 (c).) In this circuit, the milliammeter can be connected directly across the 1000 ohms to measure the grid current. Since the meter resistance is small in comparison with the 1000 ohms, the major portion of the grid current will flow through the meter rather than through the resistor.

### Discriminator Alignment

To align the discriminator circuit, a signal at the i-f should be fed to the grid of the limiter tube. With the output indicator connected to point A in Fig. 7, the primary trimmer  $C_p$  should be adjusted for maximum output. This adjustment will not be critical.

To align the secondary winding of  
(Continued on page 25)

# CIRCUITS

See Front Cover

By HENRY HOWARD

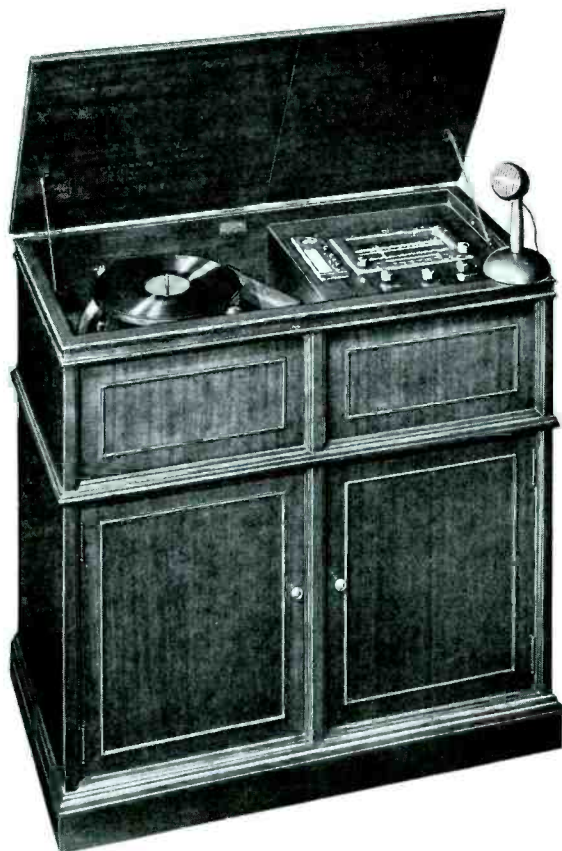


Fig. 5. (Left) Federal has introduced a series of radio-phonograph recorder combinations in console and portable models. Cabinetry ranges from the Old English to semi- and ultra-modern. Several of the console models feature automatic record-changer mechanisms.

speed (33 1/3 and 78 rpm) which is available in five of the new models. An apartment model (A85) of ultra modern cabinet design is also available, together with several models housed in cabinets styled in the eighteenth century English manner. (See Figs. 2 and 3.) Equalizers are provided in all models featuring 33 1/3 rpm.

Fig. 1. (Below) Wilcox-Gay has announced a small portable radio-recorder which they call the "Recordio, Jr." It weighs less than twenty pounds.

Federal have also added several new models to their line of radio-phonograph-recorder combinations. Both portable and console models are featured. Automatic record changing facilities are available in the large sets. (See Figs. 4 and 5.)

HOME recording is the most advertised feature of the 1941 lines, as was predicted on these pages a year ago'. Wilcox Gay have broken the field with a small reasonably priced portable radio - phonograph - recorder combination which they call the "Recordio Junior". (See Fig. 1.) The whole set, housed in an airplane luggage carrying case, weights less than



"We Expect," by Robert G. Herzog, SERVICE, Jan. 1940, p. 14.

20 pounds and will play both 10 and 12-inch recordings.

Fig. 6. Belmont 509 is a five-band, battery-operated, superheterodyne with push-button tuning. Permeability tuning is used on all bands.

The outstanding feature of the larger "Recordio" models for 1941 is dual

## Economizers

Economizers are becoming necessary features of portables. The latest wrinkle is an A battery saver consisting of a small resistor which is connected in ser-


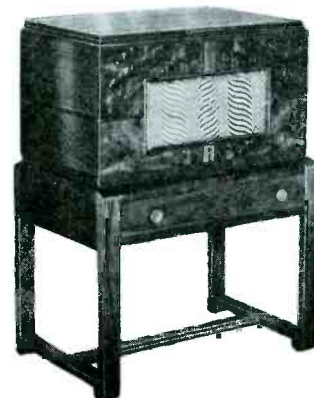


Fig. 2. (Above) Wilcox-Gay's Model A85 phonograph-radio-recorder features dual-speed (33 1/3 and 88 rpm) recording and playback.

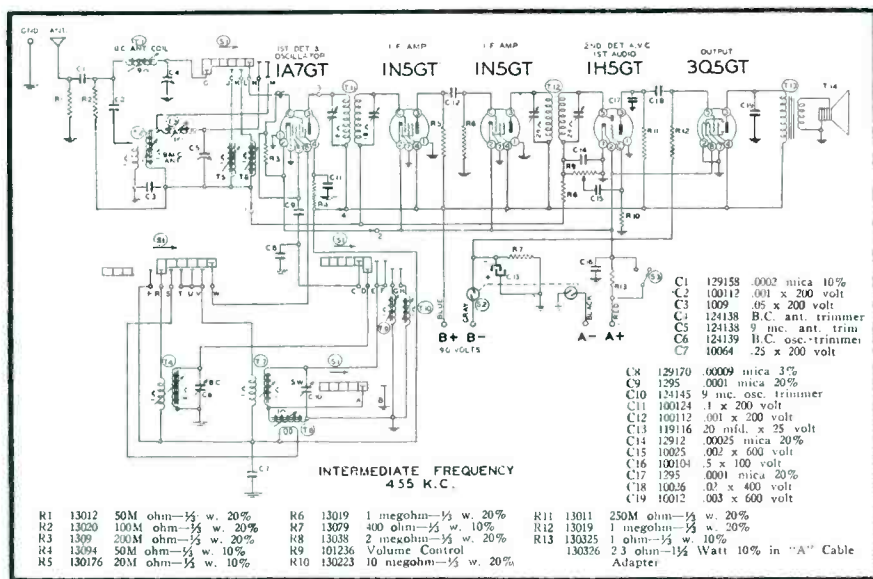ies with a battery when new. When the battery is well broken in, the resistor is shorted. This saves tube filaments as well as the filament battery and probably conserves a ma or two from the B battery. Admiral uses a 1-ohm resistor in their Model D4. Belmont does the same in their Model 509. This latter model is a rather elaborate 5-tube, 5-band receiver, has 6 push buttons, and





is provided with an adapter for two-volt storage cell operation. A 2.3-ohm, 1½-watt resistor is self-contained in a special A battery cable. (See Fig. 6.)

While on the subject of battery portables, Zenith has a new job covered with "Tufraw" genuine rawhide. Zenith advertises that this set is "guaranteed to play where other battery portables will fail, or money back". This policy is undoubtedly made possible because of Zenith's removable loop, called the "magic magnet", which may be placed in any position where it will pick up the most signal. (See Fig. 7.)

In another portable, the Admiral G6 and XG6 Series, the filaments are connected in parallel for battery operation and in series for line operation. Parallel operation of these low current filament type tubes makes for longer life. There is no tendency to overload any particular tube due to slight differences in filament resistance, or because of unequal voltage drop on the end of the series since the plate current must return through this path. This receiver is a 6-tube job with an r-f stage. A 117Z6 rectifier is used during line operation. (See Fig. 8.)

#### Philco 41-788

Philco's Model 41-788 is an elaborate 11-tube job with a 115 to 230-volt power transformer and eight tuning bands. Five of these bands are bandspread by means of a 3-gang permeability tuner. A continuous tuning range of 540 to 22,000 kc is provided. The audio end is



Fig. 3. It seems that the manufacturers have finally awakened to the fact that the radio cabinet should have some relation to the other furniture in the customer's home. The Wilcox-Gay Model A94, shown above, is a good looking example of Old English styling.

also interesting. Two phase inverter tubes are used as well as degeneration from the speaker to the input of the No. 1 phase inverter. (See Fig. 9.)

#### Emerson Inverters

Emerson has two d-c to a-c inverters for running phonograph motors on d-c sets. Synchronous vibrators having a capacity of 20 watts are used in con-

junction with a full complement of filter components to cut hash to a minimum and preserve contacts. A resistor is used in series with the vibrator to prevent fireworks and blown fuses in the event the vibrator should stick. A power



factor correcting condenser is provided across the motor terminals. (See Fig. 10.)



Fig. 7. Zenith claims their portables will work where others fail. A removable loop helps considerably.

factor correcting condenser is provided across the motor terminals. (See Fig. 10.)


#### Permeability Tuning

Belmont Model 151 is one of the few midget sets with push buttons this year. Permeability tuning is used with a slide tuner shown in Fig. 11. Ward's Airline Model 04BR515B, a 5-tube, a-c phonograph combination also uses this type of tuning. An antenna plate is used for pickup in installations where indoor antennas of this type will suffice. An interesting point is contained in switching to phonograph operation. The B supply is disconnected from the r-f and i-f stages to silence that portion of the receiver while playing records.

#### Airline 04BR389T

Ward's Airline model 04BR389T has a power transformer with five voltage taps for operation from 90 to 230 volt a-c lines. The wave-band switching also

Fig. 8. Admiral's G6 and XG6 universal portables switch from parallel filament connection on battery operation to series for line operation.

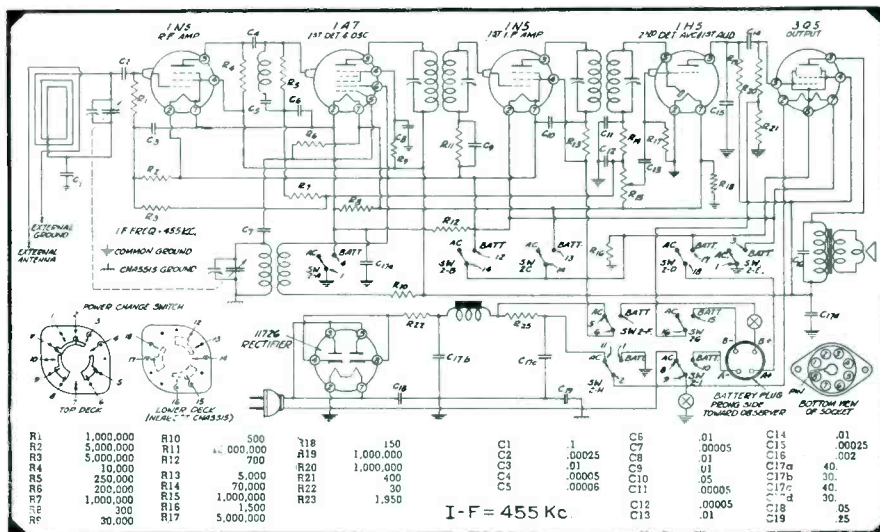

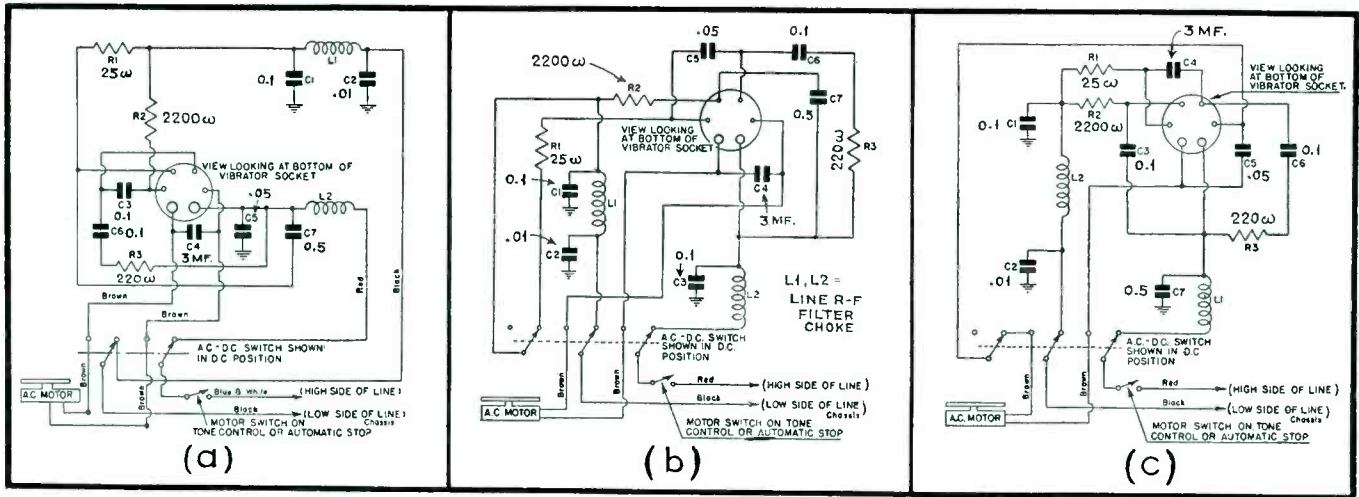


Fig. 10. Emerson has introduced a series of phonograph inverters. At a, left, a separate a-c, d-c toggle switch is used; the switch is mounted on the unit in b and also at c.

deserves attention. The antenna coils are all in series and sections are simply shorted out for the short-wave bands. The antenna coils are connected in parallel on the short wave bands. The oscillator switching looks more conventional. (See Fig. 12.)

### Motorola 83F1

Motorola Model 83F1 has a motor operated push-button tuner and an unusual 25-volt, center-tapped filament winding. The winding actually totals 33 volts for the tuning motor but two sets of 12-volt tubes are used on the 25-volt portion. The power tubes are connected in series—in Fig. 13. This model also has automatic record changing facilities.

### Crosley 42BR

Crosley Model 42BR is an 8-tube a-c superheterodyne with many advanced features, such as band-spread tuning, fly-wheel tuning drive, two i-f stages, iron-

core i-f transformers and oscillator coils for improved tracking on the short-wave bands and push-pull output. The power transformer is built for 50 cycles with four-voltage ranges from 100 to 230 volts. The tuning range covers the spectrum from 550 to 22,500 kc in six bands. The three highest frequency bands are spread by shunting fixed condensers across the gang tuning condenser as shown in the diagram on the cover. Bandspread seems to be featured in many sets this year probably because of the popularity of serious European listening for direct war bulletins.

### Stromberg-Carlson 585 F-M Receiver

With f-m rapidly gaining popular approval in many of the larger cities where stations are now operating with regular schedules, we must treat at least one f-m receiver. Probably no one has been pushing f-m more than Stromberg-Carlson. They went to town right from the beginning. Model 585 is an elabor-


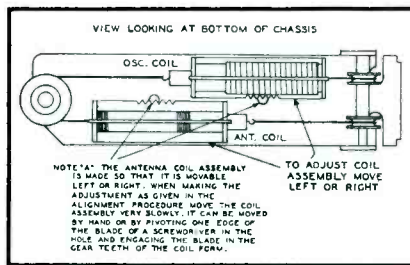


Fig. 11. A number of Belmont and Airline models use the permeability tuning unit shown above.

Fig. 9. Philco's Model 41-788 features band spread tuning with a three gang permeability tuner. The audio end has two phase inverter tubes.

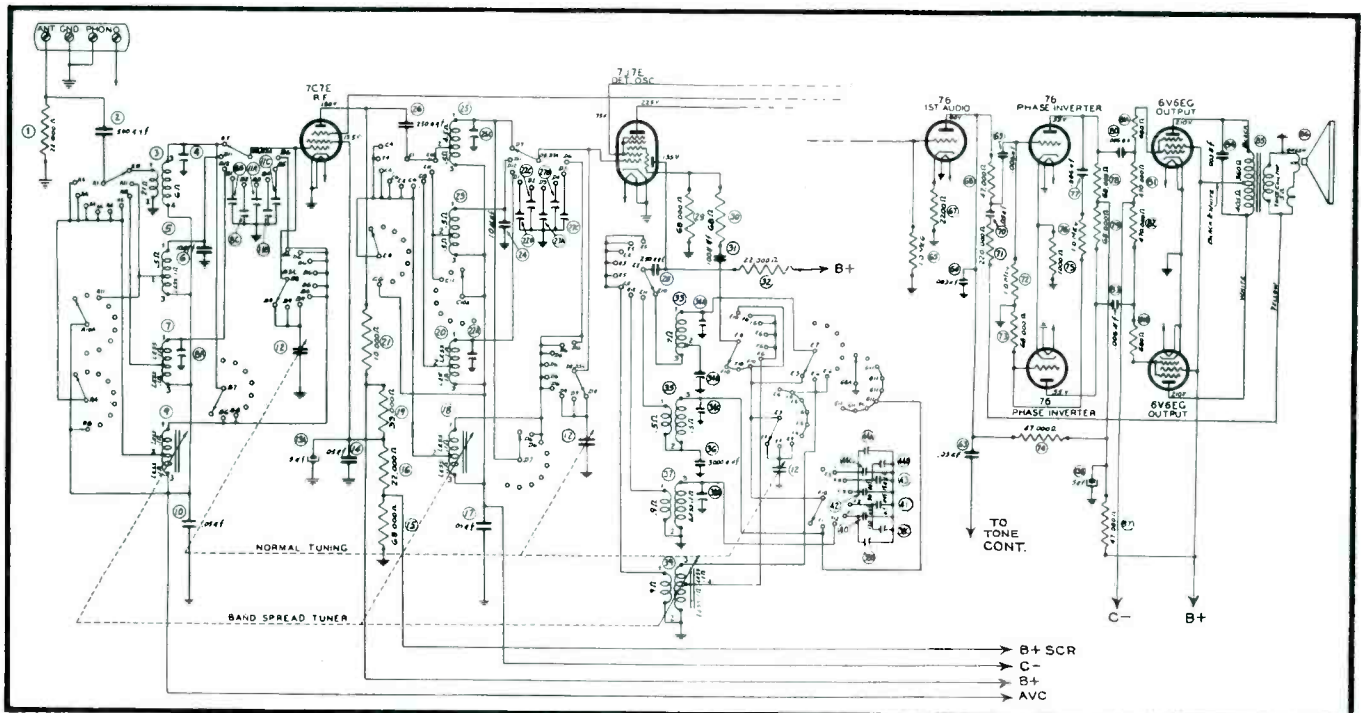



# STROMBERG - CARLSON No. 585 F.M. & A.M. RECEIVERS

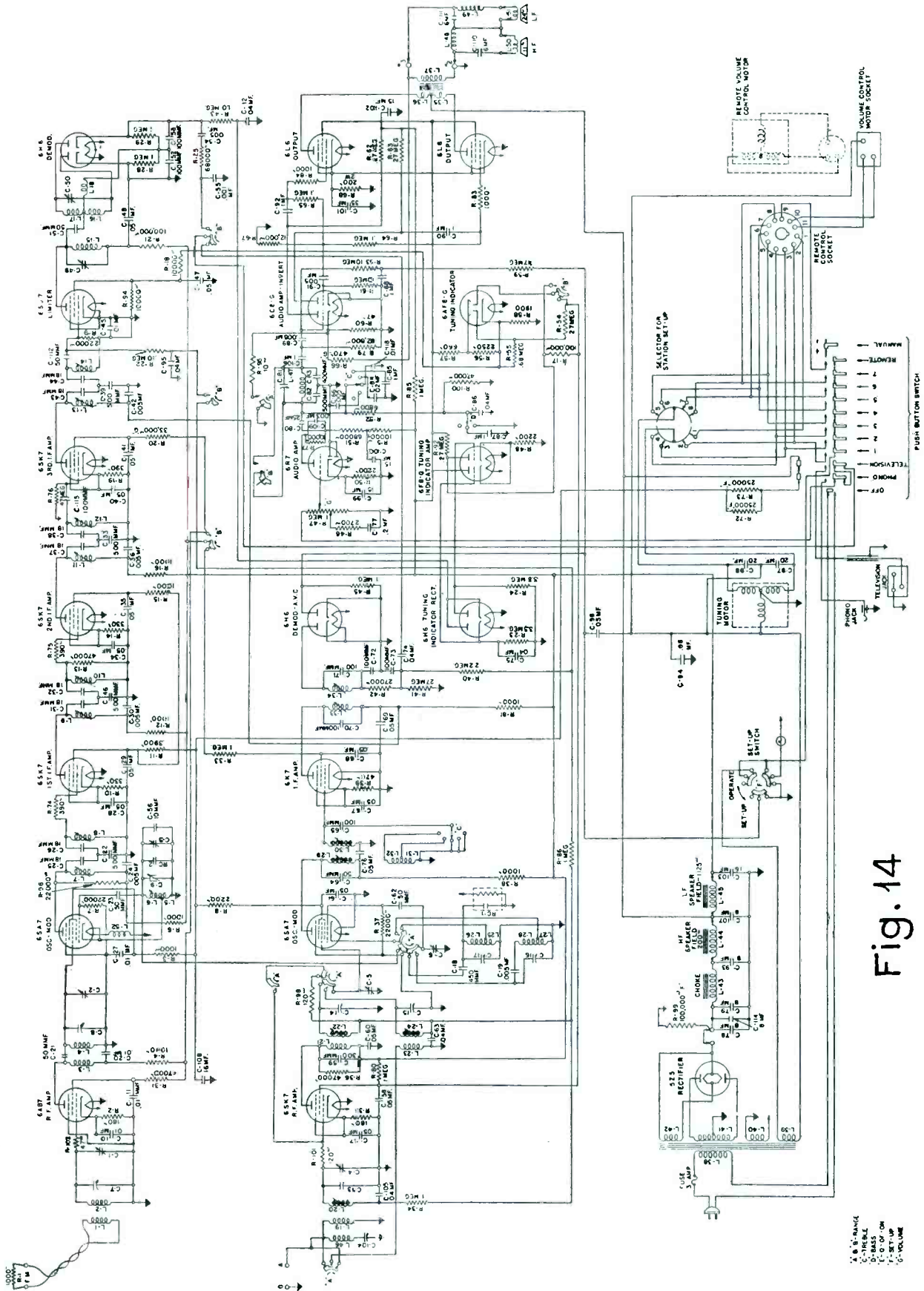


Fig. 14

V. B. - BANCE  
 C. - TRIMMER  
 D. - BASS  
 E. - G. OF ON  
 F. - G. OF ON  
 G. - VOLUME

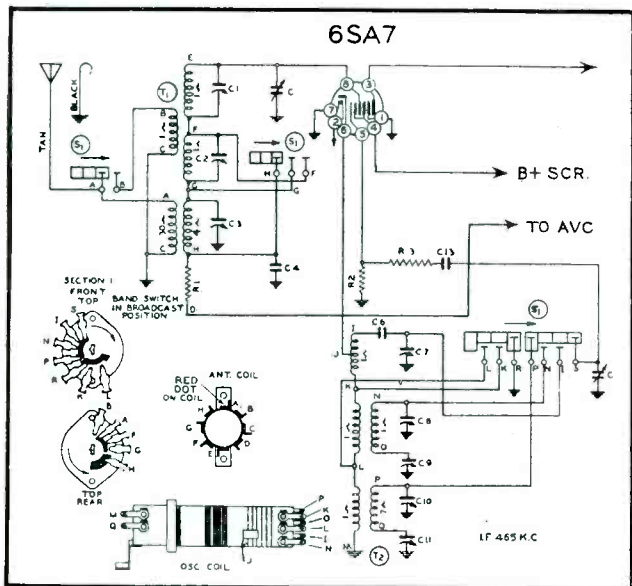


Fig. 12. (Left) Ward's Airline 04BR389T has the antenna coils for the short-wave bands in series. The band switch simply shorts out sections. The oscillator coil is more conventional, however.

ate f-m, a-m combination receiver having two completely separate r-f portions feeding an excellent audio amplifier and speaker system. Dual speakers are featured with a frequency dividing network. The treble speaker with its back completely enclosed is mounted directly in front of the bass speaker. The labyrinth is used, of course, and the complete system is capable of practically flat response from 65 to over 10,000 cycles. A remote control unit is provided, automatic tuning being obtained by a motor drive. Fig. 14 shows the output circuit as well as one of the three f-m i-f stages with its wide band coupling transformer.

### Other Models

Model 16T4 of RCA Victor is a 6-tube push-button set with an r-f stage operating on 3 bands in conjunction with two loops. Note the link (Fig. 15) which grounds the antenna coupling coil when set for loop operation.

Degeneration over the entire audio amplifier is featured in the Lafayette Model 1102, where voltage is taken from the output transformer and fed back to the cathode of the 6SQ7 first audio stage. (See Fig. 16.)

### STROMBERG CARLSON 520PS, 520PN, 520PG

*Eliminating some of the high frequencies of the 520 PS, PN and PG when playing records:* To eliminate some of the reproduction of high frequencies internally and thus eliminate the necessity for using the tone control to minimize surface noise in the reproduction of phonograph records, a 75-mmfd capacitor has been added to the circuit of these models manufactured after November 12, 1940.

This 75-mmfd capacitor is located across the 1.5-megohm resistor (R6) connected from terminal No. 3 of the 6V6 output

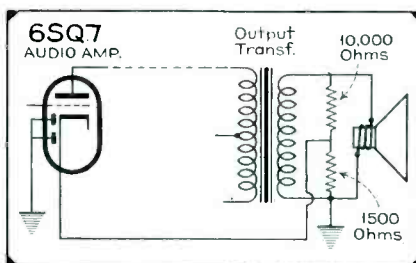


Fig. 16. (Below) Lafayette 1102 features degeneration from the voice coil to the cathode of the 6Q7 first audio amplifier stage. The proper percentage of the output voltage is selected by means of a resistance divider connected across the voice coil winding.

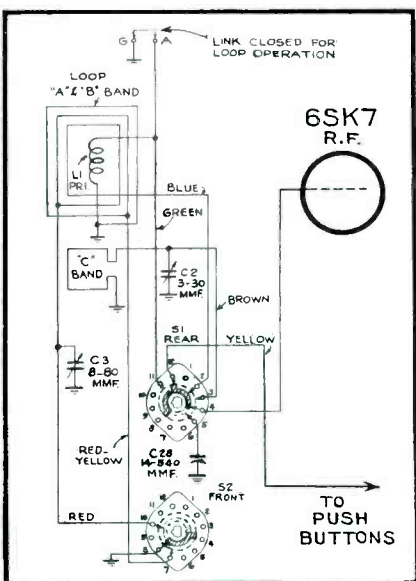


Fig. 15. (Above) Two loops are employed on the RCA 16T4 three band superheterodyne.

socket to the single point terminal block located on the mounting support bracket of the variable capacitor.

If the customer desires greater fidelity of reproduction of phonograph records this capacitor should be removed.

### WELLS GARDNER 6C13, 6C14, D1090, D1091

*External speaker grounds:* The C issue radio is equipped with a speaker that does not have to be insulated from the car ground if mounted externally and in back of the instrument panel. The voice coil and the field coil of this speaker are not connected directly to ground but, instead, are soldered to a lug insulated from ground. A bare wire connects this lug to the speaker frame—See illustration below. When the speaker in the C issue radio is mounted externally, cut off this bare ground wire. This insulates the speaker windings from car ground at the speaker mounting.

The speaker in the A and B issue radios does not have this grounding arrangement and this procedure for insulating the speaker windings from car ground cannot be followed.

The issue letter is the letter at the end of the chassis number on the chassis label. This label is on the round can in the radio.

J. K. Rose, Service Manager  
WELLS-GARDNER & COMPANY

### WILCOX GAY

A89, A91, A92, A93, A94


*Bass response and microphonism:* In dual-speed Recordio models with serial numbers over 621520, the 500,000-ohm resistor (R36), connected in shunt with the phonograph input circuit, has been changed to one of 2.0 meg.

The resistance value of R36 governs the amount of low audio frequency response (bass) that may be obtained in playing phonograph records, without encountering rumble or microphonism due to cabinet resonance. Increasing the resistance value increases the bass response, and vice versa.

By use of the 2.0 megohm resistance value, the degree of low frequency response is adjusted to a safe margin from the borderline of microphonism.

Should it be desired to increase the bass response of phonograph record reproduction in dual-speed Recordio models bearing serial numbers lower than indicated above, the highest resistance value, not to exceed 2.0 megohms, should be used in circuit position R36, that affords record reproduction at full volume entirely free from microphonism.

Fig. 13. (Below) The Motorola 83F1 has a motor operated push-button tuning arrangement.

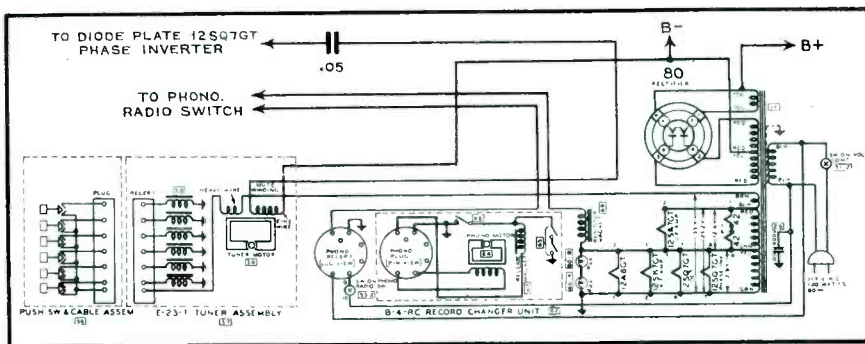



# SOUND IDEAS

By JAY ALLEN

WITH the Emergency Training Program for National Defense in the headlines, greater attention is being given to schools in general. Changes and improvements are planned on a large scale throughout the country. The addition of sound equipment is an item marked down as number one by many supervisors.

## High School Sound


At the Sunset High School, in Dallas, Texas, an installation was made (see Fig. 1) for sound reinforcement of dramatics or of any assembly that requires pick up of the entire stage. The five Shure Unidyne cardioid microphones are fed to individual inputs of an amplifier located off stage. Several speakers are used to distribute the sound to the audience.

Previously, microphones were used in the footlights but this did not provide proper coverage from all parts of the stage.

The installation was made by Wilkinson Brothers, radio parts distributors in Dallas, Texas. Elliott Wilkinson, one of the brothers, received a letter from Mr. W. T. White, principal of the Sunset High School which stated:

"Regarding the microphones installed in our auditorium, I am now ready after

Fig. 1. Five microphones (four in the back drop and one on the speakers stand) are used to pick up sound on the stage in the auditorium of this Texas high school.

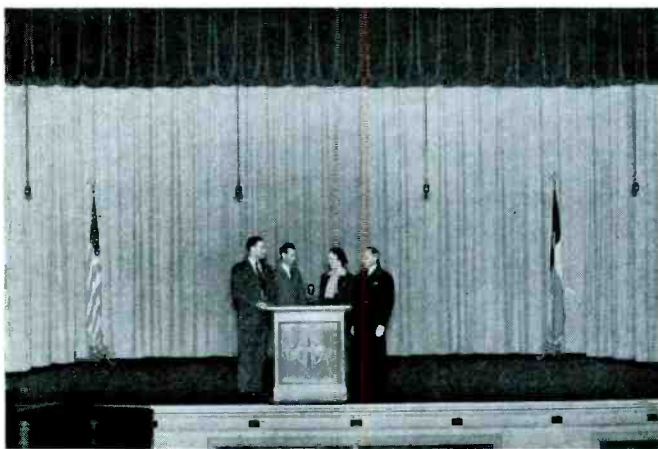

having opportunity to make sufficient tests, to report they are entirely satisfactory.

"The quality of tones reproduced by the microphones is remarkably natural. However, the thing that has been of most interest to me is whether or not group conversations and action on the stage could be amplified by the use of all microphones without distortion of individual voices. During a recent assembly which involved group action, the results were fine."

## Towboat Sound

The appearance of the new all-welded steel towboat "Tri-Cities" on its trip to various points on the Mississippi River from Hartford, Ill., has caused much comment. This has been due, not to its modern design, but more directly to the loudspeaker installed atop the pilothouse which permits voices to be heard for more than two hundred yards.

Orders from the pilothouse to engine room, captain's quarters or galley on the new boat are transmitted by a Philco sound system.

A loudspeaker atop the pilothouse makes possible ready communication with deck hands or persons ashore. The system permits transmission of orders more than 600 feet from the pilothouse—a situation frequently occurring since river towing involves the handling of long and bulky tows.

The new installation permits more

ready handling of tows passing through locks as well as expediting loading and unloading which heretofore had required relaying of verbal orders.

## Recording Studio

As an extra business feature, Allied Engineering Services, a radio service shop located at 410 Marion Avenue, Lima, Ohio, makes recordings for their patrons, at a small fee for each disc.

The equipment used, see Fig. 2 is a special rack and panel job designed by T. P. Hover, of Allied. It was built on the Allied Engineering work bench.

This feature is played up in window displays, throw-aways and other local advertising and provides a definite source for added income. Margret Hover, sales manager of Allied (shown in the photo) reports, in addition, that the recording studio helps to build store traffic and increases prestige with the customer.

With home recording taking the lime-light in the set manufacturer's advertising for 1941, business from this source should show a marked increase. Customers considering the purchase of home recording equipment will undoubtedly call upon Allied's before making any decision.

Fig. 2. By making recordings for their customers, Allied Engineering Services, Lima, Ohio, have built up a profitable side line to their already flourishing radio service business.



# Are you an "Over-the-Shoulder" reader?



**SERVICE** maintains a perpetual survey of readership. It shows that each copy of **SERVICE** is read by an average of nearly two-non-subscribers in addition to the subscriber

The Regular Yearly Subscription Rate is \$2.00—BUT, do you know that—\*

\*Practically every Chapter of every Service Organization in the U. S. and Canada uses the Group Rate for their members. All you have to do, in most cases, is to hand your Secretary a dollar and tell him to include your name in the next group he sends in.

\*Leading radio schools use the Group Plan, and all you need do is request that your name be included in the group at only a dollar a year.

\*Many leading jobbers send in group subscriptions regularly from their customers, and you, too, can be included at only one dollar a year.

## OR

By getting 3 or more of your own associates to subscribe, renew or extend their subscriptions with you—you will get **SERVICE** for a whole year—at one dollar each!

Two 2-year subscriptions at \$2.00 will also qualify,  
or one *Four-Year* Subscription at \$4.00.

Look over the Annual Index in this issue. That will show you more than anything we can say, why you need *your own* complete file of **SERVICE** in 1941.

----- **TEAR OUT AND MAIL** -----

## **SERVICE—19 East 47th St., New York, N. Y.**

Please enter annual subscriptions (12 issues) for each of the undersigned for which payment is enclosed at the rate of \$1.00 each; foreign \$2.00. (This rate applies only on 4 or more subscriptions when occupations are given.)

Name .....  
Address .....  
City-State .....  
Occupation .....  
Employed by .....  
State whether Employer is a Service Organization, Dealer, Jobber  
or Manufacturer .....

Name .....  
Address .....  
City-State .....  
Occupation .....  
Employed by .....  
State whether Employer is a Service Organization, Dealer, Jobber  
or Manufacturer .....

Name .....  
Address .....  
City-State .....  
Occupation .....  
Employed by .....  
State whether Employer is a Service Organization, Dealer, Jobber  
or Manufacturer .....

Name .....  
Address .....  
City-State .....  
Occupation .....  
Employed by .....  
State whether Employer is a Service Organization, Dealer, Jobber  
or Manufacturer .....



JANUARY, 1940 - DECEMBER, 1940

An asterisk preceding a listing indicates that a partial or complete circuit accompanies the text.

ANTENNAE

	Issue	Page
*Airline 93BR720A Loop and Antenna	Apr.	11
*Antenna vs. Loop	Apr.	34
Arvin Whip Antennae	Mar.	8
*Belden Clear Channel Antenna	Aug.	22
*Brach Noiseless Antenna	Aug.	22
*Noiseless Antennae	Aug.	21
*Outdoor Antennae. By Julius G. Aceves	Apr.	34
*Philco Noiseless Antenna	Aug.	22
Philco 1940 Portables	Nov.	17
*RCA Noiseless Antennae	Aug.	22
*Sentinel-Erila A-C, D-C Line Antenna	Apr.	11
*Stromberg Carlson 435, 455, 480 Antenna Connections	Mar.	28
Studebaker and Packard Rotary Antennae	Nov.	20
*Taco Noiseless Antennae	Aug.	22

AUTO RADIO

*ABC 550A, 600 Converter	June	16
*Arvin RE54	Mar.	8
*Arvin RE60	Mar.	8
Automobile Grounded Battery Terminal Chart	Mar.	7
*Auto Radio. By Henry Howard	Mar.	5
*Auto-Radio Installation in 1940 Cars. By Edward H. Barry	May	8
Auto-Radio Interference Elimination Chart	May	8
Chrysler-Philco C708	Oct.	38
*Crosley A169	Mar.	7
*Motorola 26C	Mar.	5
*Motorola 26C7	Mar.	5
*Philco AR7	Mar.	10
Philco AR5	Sept.	31
Philco AR9	June	16
*Short Waves for Autos. By Robert G. Herzog	June	16
*Stewart Warner Hudson SA40	Mar.	10
*Stewart-Warner Packard PA-33915. PA353832, (Stewart Warner 3341)	Mar.	6
*Stewart-Warner Packard 351099, PA351100 (Stewart Warner R3271, R3271C)	Mar.	6
*Stewart-Warner Packard PA351101, PA351102, (Stewart Warner 3291, R3291C)	Mar.	6
*Stromberg Carlson 435, 455, 480 Antenna Connections	Mar.	28
Studebaker and Packard Rotary Antennae	Nov.	20
*Studebaker 1941 Ignition Noises. Technical Features of 1940 Auto Radio Receivers (Charts)	Apr. 14. 15	
*Trayler 621	Mar.	6
*Truetone D1091, 6C14.3	Mar.	6
*Wells Gardner 6C9 Production Changes	Mar.	28
*Zenith-Nash AC4289 (Zenith 6MN496)	Mar.	5

BOOK REVIEWS

Aircraft Radio and Electrical Equipment. By Howard K. Morgan	Dec.	27
Alternating Current Bridge Methods (4th Edition). By B. Hague	Dec.	27
The Amplification and Distribution of Sound. By A. E. Greenlees	Dec.	27
Applied Acoustics (2nd Edition) By H. F. Olson & F. Massa	Oct.	26
Capacitor Manual for Radio Servicing. By Cornell Dubilier	Apr.	37
Characteristics Data Chart 13 Edition. By Raytheon Production Corp.	Sept.	29
Cumulative Index of Journal of Acoustical Society of America	June	33
Dictionary of Radio Terms. By L. O. Gordon	Oct.	26
Fundamentals of Electricity and Electromagnetism. By Vernon A. Snydam	Dec.	27
High Frequency Alternating Currents. By K. McIlwain & J. G. Brainerd	Oct.	26
Introduction to Frequency Modulation. By John F. Rider	Sept.	29
Introduction to Vector Analysis. By B. Hague	Sept.	29

Mathematics Applied to Electrical Engineering. By A. G. Warren	Dec.	31
The 1940 Radio Amateur Handbook (Seventeenth Edition)	Apr.	37
Perpetual Trouble Shooters Manual Volume XI. By John F. Rider	Aug.	15
Philco 1939 RMS Year Book. By Philco	Mar.	27
Principles and Practice of Radio Servicing. By H. J. Hicks	Dec.	31
RCA Ham Guide. By RCA Mfg. Co.	Sept.	29
RCA Victor Service Notes for 1939. By RCA Mfg. Co.	Nov.	29
Radio Handbook (Sixth Edition) Radio's Master Encyclopedia	Apr.	37
Radio Service Trade Kinks. By Lewis S. Simon	Apr.	37
Receiving Tube Characteristics Chart & Socket Connections 1275B. By RCA Mfg. Co.	Aug.	15
Safety Rules for Radio Installations. By National Bureau of Standards	June	33
Servicing by Signal Substitution. By G. N. Goldberger	Oct.	26
Servicing by Signal Tracing. By John F. Rider	Jan.	25
Supersonics: The Science of Inaudible Sounds. By R. W. Wood	Dec.	21
Television Broadcasting. By Lenox Lohr	Nov.	29
Television Receiving Equipment. By W. T. Cocking	Dec.	21
Transmitter Guide. By Thordarson Electric Co.	Oct.	26
We Present Television. By John Portfield and Kay Reynolds	Dec.	22

BUSINESS METHODS, HELPS

Advertising and Publicity	Sept.	12
Advertising with Little Expense. By Jack H. Zeilenga	Oct.	15
Busy Shop	Dec.	21
Confidence. By Ruel McDaniel	July	25
Customer Psychology. By Walter Kenworthy	Mar.	12
Dealer Cooperation. By Martin Francis	Mar.	11
Dealer Cooperation. By Martin Francis	Apr.	8
Display	Sept.	19
Flat Rate Schedule (Chart)	Feb.	12
Learn To Sell. By V. E. Jenkins	Jan.	13
Oscilloscope Helps Sales. By Murray Orman	Mar.	19
Progress. By T. D. Gibbs	Nov.	17
Sell Complete Service. By Martin Francis	Sept.	15
Service At Your Door. By Charles Hurt	Aug.	16
Service by the Day. By Ruel McDaniel	Feb.	44
Service Charges. By F. Woodson Smith	Feb.	12
Steps to Success. By W. F. Dickinson	Sept.	12
Success. By George N. Musil	June	22
Theatre Display. By M. Hoover	July	20

CASE HISTORIES†

Chrysler-Philco C708	Oct.	38
*Hudson DB40, SA40	Dec.	23
Philco 40-195, 200	Sept.	31
Philco AR5	Sept.	31
Philco 1940 Portables	Nov.	17
RCA Automatic Record Changer. By Willard Moody	Apr.	36
RCA Governor Motors	Mar.	28
RCA O-11 Phonograph Motor	June	28
RCA K105. By Willard Moody	Sept.	31
RCA RP139A, RP145 Automatic Record Changer	June	18
Silvertone 6325, 6425	June	28
*Silvertone 6326. By B. Wixon	Feb.	14
Silvertone 6346, 6346A, 6446	June	28
Silvertone 6400A, 6401A, 6402A	June	28
Silvertone 6403, 6404, 6405, 6406, 6407, 6408, 6409, 6492, 6496. By B. Wixon	Feb.	14
Stewart Warner 07-51, 07-51H. By M. J. Schinke	April	36

† This material is obtained from our readers and is representative of the actual experiences of the Service Man in the field.

	Issue	Page
Stewart-Warner 5R, 5R4, 5R5, 5R6, 5R7	Oct.	38
*Stewart Warner Hudson DB40, SA40	Apr.	36
Stewart-Warner Hudson DB40, SA40	June	28
*Stewart-Warner Hudson DB40, SA40	Dec.	23
Stromberg Carlson 60. By Willard Moody	June	28
Stromberg Carlson 400 Series. By J. E. Ward	Feb.	14
*Stromberg Carlson 460PF	June	23
*Stromberg Carlson 470PF	Apr.	36
*Stromberg Carlson 505, 515	Nov.	25
Stromberg Carlson 520PS, 520PN, 520PG	Dec.	14
*Studebaker 1941 Ignition Noises. Studebaker and Packard Rotary Antennae	Nov.	20
Webster Automatic Changer	Feb.	14
Wells Gardner 1A28, 8A30, 8A31, 8A32, OA33, 8A34, OA35, 8A36, 8A37	Feb.	39
*Wells Gardner 1A29. By J. K. Rose	Feb.	15
Wells Gardner 5D2, 6A26, 6A27. By J. K. Rose	Feb.	39
Wells Gardner 6A26, 6A27	Feb.	43
Wells Gardner 6B7. By J. K. Rose	Feb.	43
*Wells Gardner 6C9. By J. K. Rose	Mar.	28
Wells Gardner 6C13, 6C14, D1090, D1091. By J. K. Rose	Dec.	14
Wells Gardner 16A26, 16A27, 15S3. By J. K. Rose	Feb.	44
Wells Gardner 36A26, 36A27, 36D1. By J. K. Rose	Feb.	43
Wells Gardner 93 WG 5 6 2, 93WG602, 93WG603, 93WG604, 93WG605. By J. K. Rose	Feb.	44
Wells Gardner 93WG663, 93WG-668	Feb.	43
Wells Gardner 1938, 1939 Sets. By J. K. Rose	Feb.	15
Westinghouse 373Y. By Willard Moody	June	23
Wilcox Gay A89, A91, A92, A93, A94	Dec.	14

CHARTS

Automobile Grounded Battery Terminals	Mar.	7
Auto-Radio Interference Elimination	May	8
Comparative Batteries for Portables	July	6
Comparative Packs for Portables	July	8
Crystal Microphones	Feb.	22
Decibels vs. Watts Conversion Chart	Mar.	15
Dynamic Microphones	Feb.	22
Flat Rate Schedule	Feb.	12
Lock-in-Type Tubes	Nov.	14
Loktal Contact Pins	April	37
Microphone Ratings	Feb. 22, 24	
New Maximum Receiving Tube Ratings	Jan.	12
New Tube Characteristics	May	25
Standards for Dry Cell & Battery Sizes	Aug.	5
Recorder Characteristics	Feb.	26
Replacement Batteries for Portables	July	7
Replacement Batteries for Portables	Aug.	6
Replacement Batteries for Portables	Sept.	30
Technical Features of 1940 Auto-Radio Receivers	Apr. 14, 15	
Technical Features of 1940-41 Battery Portables	June 6, 7	
Television Broadcast Stations	Jan.	18
Tubes	Jan.	11
Tube Tester Readings for New Tubes	Mar. 32, 33	
Velocity Microphones	Feb.	24
CK501, CK502, CK503, CK504 Tube Characteristics	Mar.	33

COVER DIAGRAMS

*A-C, D-C, Battery Portable (G.E. HB412)	Jan.	23
Band-Spread Tuning (Crosley 42BR)	Dec.	10
*Bike Radio (Motorola B150)	July	10

\*Double Triode Converter-Oscillator—Twin Phonograph-Radio Volume Control (Philco) Oct. 8
\*Frequency Modulation (Stromberg Carlson 455) April 29
\*Phono Amplifier Wireless Record Player (Stewart-Warner) Nov. 7
\*Recorder-Radio Switching (Howard 302R, RA, RT) May 12
\*Recorder Switching, Mike Input and Audio (Arlene) Aug. 13
\*Reducing Shock Hazard. By Nathan I. Daniel Feb. 42
\*Superhet Oscillator-Photoelectric Lamp Exciter (Philco) Sept. 8
\*Two-Unit Auto Radio (Stewart-Warner Hudson SA40) March 5
\*Vibrator Operated Battery Portable (Setchell Carlson 66) June 5

EDITORIALS

Alignment Feb. 2
Auto Radio Mar. 2
Auto Radio Apr. 2
Battery Replacements July 2
Bell Pushing July 2
Color Television Sept. 2
Emergency Training Program Oct. 2
F-M Receiver Manufacturers Oct. 2
Frequency Modulation May 2
Frequency Modulation Dec. 2
Home Recording Feb. 2
National Defense Nov. 1
National Television Committee Aug. 2
Profitable Ideas July 2
Radio's 20th Birthday Oct. 2
Reallocation March 2
Resistances and Tolerances Feb. 2
Servicing and Profits Jan. 4
Sound Equipment Mar. 2
Sound Replacement April 2
Television Mar. 2
Trends June 2

FEATURES

\*A-C, D-C, Battery Portable (G.E. HB412). By Henry Howard Jan. 23
\*Acoustic Howl. By Maurice Epstein Feb. 5
Advertising With Little Expense. By Jack H. Zeilenga Oct. 15
Amplifier Ratings. By John M. Borst Mar. 14
Automatic Record Changer (Crosley 639) Mar. 25
Automatic Record Changer (RCA RP139A, RP145) June 18
Automobile Grounded Battery Terminal Chart Mar. 7
\*Auto Radio. By Henry Howard Mar. 5
\*Auto-Radio Installation in 1940 Cars. By Edward H. Barry May 8
Auto-Radio Interference Elimination Chart May 8
\*Band-Spread Tuning (Crosley 42BR) Dec. 10
Batteries for Portables. By Robert G. Herzog July 5
Batteries for Portables. By Robert G. Herzog Aug. 5
\*Battery Portables. By Henry Howard June 5
\*Browning F-M Kit March 17
Busy Shop Dec. 22
\*Chasing Signals. By J. E. Woolley Jan. 26
\*Circuits. By Henry Howard Feb. 8
\*Circuits. By Henry Howard Apr. 10
\*Circuits. By Henry Howard July 10
\*Circuits. By Henry Howard Aug. 13
\*Circuits. By Henry Howard Sept. 8
\*Circuits. By Henry Howard Oct. 8
\*Circuits. By Henry Howard Nov. 7
\*Circuits. By Henry Howard Dec. 10
Comparative Batteries for Portables (Chart) July 6
Comparative Packs for Portables (Chart) July 8
Confidence. By Ruel McDaniel July 25
Customer Psychology. By Walter Kenworth Mar. 12
Dealer Cooperation. By Martin Francis Mar. 11
Dealer Cooperation. By Martin Francis Apr. 8
Display Sept. 19
\*Electronic Music. By Nathan I. Daniel Apr. 17
Flat Rate Schedule (Chart) Feb. 12
\*Frequency Modulation (Stromberg Carlson 455) Apr. 29

\*Frequency Modulation. By Jack Avins Nov. 3
\*Gain Measurements and Signal Tracing June 14
\*G. E. HM80 F-M Receiver Dec. 5
\*G. E. H639 (A-C and D-C). By Allan Epstein Mar. 16
\*Home Recording. By Henry Howard May 12
\*Hearing Aids. By Robert G. Herzog Oct. 5
Hearing Aid Tube Characteristics Oct. 7
\*Intermittent Condensers Apr. 26
\*Learn to Sell. By V. E. Jenkins July 28
Lock-in-Type Tubes (Chart) Jan. 13
Microphone Ratings (Chart) Nov. 14
\*Modern Multitesters. By S. Gordon Taylor Feb. 22, 24
\*Modern Multitesters (Part II). By S. Gordon Taylor Sept. 10
New Maximum Receiving Tube Ratings Oct. 2
New Tubes May 25
New Tubes Aug. 26
New Tube Characteristics Chart May 25
\*Nineteen Forty Sound. By S. Gordon Taylor Feb. 17
Noise Interference. By Harry Kalker Feb. 37
\*Noiseless Antennae Aug. 21
\*Outdoor Antennae. By Julius G. Aceves April 34
\*P-M Speakers. By M. Heller Aug. 24
Philco Photoelectric Phonograph. Progress. By T. D. Gibbs July 22
Recorder Characteristics (Chart) Nov. 17
\*Reducing Shock Hazard. By Nathan I. Daniel Feb. 42
Replacement Batteries for Portables (Charts) July 7
Replacement Batteries for Portables (Charts) Aug. 6
Replacement Batteries for Portables (Chart) Sept. 30
Sell Complete Service. By Martin Francis Sept. 15
Service At Your Door. By Charles Hurt Aug. 16
Service by the Day. By Ruel McDaniel Feb. 44
Service Charges. By F. Woodson Smith Feb. 12
Service Success Contest Winners June 22
The Service Man and the Broadcasters. By Arthur Stringer April 32
\*Servicing F-M Receivers. By Jack Avins Dec. 5
\*Servicing Recorders. By C. J. LeBel Sept. 5
\*Short Waves for Autos. By Robert G. Herzog June 16
\*Signal Substitution. By G. N. Goldberger May 14
\*Signal Tracing. By Jack Avins April 5
Sound Ideas. By Jay Allen Aug. 18
Sound Ideas. By Jay Allen Oct. 19
Sound Ideas. By Jay Allen Nov. 11
Sound Ideas. By Jay Allen Dec. 15
Sound Ideas. By S. Gordon Taylor April 20
Sound Ideas. By S. Gordon Taylor June 10
Sound Ideas. By S. Gordon Taylor July 14
\*Sound Profits in a Small Town Steps to Success. By W. F. Dickinson Sept. 12
Success. By George N. Musil June 22
Standards for Dry Cell and Battery Sizes. (Charts) Aug. 5
\*Stromberg Carlson 505H, 505HB F-M Receivers Dec. 6
\*Stromberg Carlson 585 F-M, A-M Receiver Dec. 14
Technical Features of 1940 Auto radio Receivers (Charts) Apr. 14, 15
Technical Features of 1940-41 Battery Portables (Charts) June 6, 7
Television Broadcast Stations Jan. 18
Television in Natural Color Sept. 28
Television Speeds Up Mar. 21
Theatre Display. By M. Hoover July 20
\*Tolerances. By Jack Avins May 5
\*Tubes. By John H. Potts Jan. 7
Tubes Mar. 33, 41
Tube Characteristics Chart Jan. 11
We Expect for 1940. By Robert G. Herzog Jan. 15

FREQUENCY MODULATION

\*Browning F-M Kit Mar. 17
F-M Receiver Manufacturers Oct. 2
Frequency Modulation (Status, Jan. 1940) Jan. 18

\*Frequency Modulation (Stromberg-Carlson 455) April 29
\*Frequency Modulation. By Jack Avins Nov. 3
Frequency Modulation Dec. 2
\*G. E. HM80 F-M Receivers Dec. 5
\*Servicing F-M Receivers. By Jack Avins Dec. 5
\*Stromberg Carlson 505H, 505HB F-M Receiver Dec. 6
\*Stromberg Carlson 585 F-M, A-M Receiver Dec. 14

HUM

\*Input Hum. By Jay Shawn Apr. 26
RCA K105. By Willard Moody Sept. 31
\*Silvertone 6326. By B. Wixon Feb. 14
Wells Gardner 1A29 Feb. 15
Wells Gardner 5D2, 6A26, 6A27. By J. K. Rose Feb. 39
Wells Gardner 6A26, 6A27 Feb. 43
Wells Gardner 1A28, 8A30, 8A31, 8A32, OA33, 8A34, OA35, 8A36, 8A37 Feb. 39

I-F PEAKS

(See Receivers Also)
Auto-Radio Receivers for 1940.. Apr. 14, 15
Battery Portables for 1940-41... June 6

INTERMITTENTS, FADING

\*Intermittent Condensers July 28
\*RSE Condenser Tester July 28

MICROPHONES

Crystal Microphone Characteristics Feb. 22
Dynamic Microphone Characteristics Feb. 22
Microphone Characteristics Feb. 22
Velocity Microphone Characteristics Feb. 24

MOTORS

Automatic Record Changer (Crosley 639) Mar. 25
\*Motorola Automatic Record Changer Circuits Aug. 14
Phonograph Motors. By Porter Turner Mar. 41
RCA Governor Motors Mar. 28
RCA Q-11 Phonograph Motor June 28
RCA RP139A, RP145 Automatic Record Player June 18
Webster Automatic Changer Feb. 14

ON THE JOB

\*ATR PCP, PCP-F, PCP-R Phonograph Inverter June 32
Alignment Hint. By R. G. Chrouch Sept. 9
Belt Static Sept. 26
\*Crystal Cartridges Nov. 22
Emerson Phonograph Inverters Extension drill. By R. G. Chrouch Dec. 12
GTC P Twin Power Oct. 28
Loktal Contact Pins Mar. 36
Measuring Plate Current. By R. G. Chrouch Apr. 37
Noise Interference. By Harry Kalker Feb. 37
Phonograph Motors. By Porter Turner Mar. 41
Profits in Home Recording. By R. C. Powell Sept. 26
\*RCA 9901 Tube Tester Modernization Kit Mar. 32
\*Reducing Shock Hazard. By Nathan I. Daniel Feb. 42
\*Resistance Applications Feb. 38
Rollindex Tube Tester Chart Sept. 26
Service by the Day. By Ruel McDaniel Feb. 44

PARTS

(See Tubes Also)
Antennae Nov. 7
Condensers Jan. 33
Loops Nov. 7
Materials Jan. 20
\*P-M Speakers. By M. Heller Aug. 24



Parts	Nov.	7
*Permeability Tuning	Dec.	12
*Qualitative Condenser Tests	Dec.	28
*Resistance Applications	Feb.	38
Resistors	Jan.	33
Speakers	Jan.	33
*Tolerances. <i>By Jack Avins</i>	May	5

**PHONOGRAPHS, RECORD PLAYERS**

(See Recording Also)

*ATR PCP, PCP-F, PCP-R Phonograph Inverter	June	32
*Airline 04BR615A Radio Recorder	Aug.	13
Automatic Record Changer (Crosley 639)	Mar.	25
Automatic Record Changer (RCA RP139A, RP145)	June	18
Crosley 639 Automatic Changer	Mar.	25
*Crystal Cartridges	Nov.	22
*Emerson Phonograph Inverters	Dec.	12
*Emerson 8MT574 Phonograph Inverter	Oct.	8
*Emerson EO388 Phonograph Adapter	Oct.	9
*G.E. JM23 Wireless Record Player	Aug.	27
*G.E. HJ628	Feb.	11
*G.E. H639 (A-C and D-C). <i>By Allan Epstein</i>	Mar.	16
*Motorola Automatic Record Changer Circuits	Aug.	14
Philco Photoelectric Phonograph Phonograph Motors. <i>By Porter Turner</i>	July	22
RCA Automatic Record Changer. <i>By Willard Moody</i>	Mar.	41
RCA Governor Motors	Apr.	36
RCA RP139A, RP145 Automatic Record Player	Mar.	28
RCA 0-11 Phonograph Motor	June	18
Silvertone 6346, 6346A, 6446	June	28
*Stewart-Warner 11-2A Wireless Record Player	Nov.	7
Webster Automatic Changer	Feb.	14

**PUBLIC ADDRESS**

(See Sound)

**RECEIVERS**

Auto

(See Auto Radio)

*A-C, D-C, Battery Portable (G.E. HB412). <i>By Henry Howard</i>	Jan.	23
*Admiral All	Nov.	15
*Admiral G6, XG6	Dec.	11
*Admiral J6, XJ6	Nov.	16
*Admiral J55, XJ55	Oct.	9
*Airline 04BR615A Radio Recorder	Aug.	13
*Airline 04BR389T	Dec.	14
*Airline 93BR335A	Apr.	12
*Airline 93BR392A	July	11
*Airline 93BR719A	July	11
*Airline 93BR720A Loop and Antenna	April	11
*Airline 93WG510	Feb.	11
Batteries for Portables. <i>By Robert G. Herzog</i>	July	5
Batteries for Portables. <i>By Robert G. Herzog</i>	Aug.	5
Battery Portables	Jan.	15
*Battery Portables. <i>By Henry Howard</i>	June	5
*Belmont Permeability Tuning	Dec.	11
*Belmont 509	Dec.	12
*Browning F-M Kit	Mar.	17
*Circuits. <i>By Henry Howard</i>	Feb.	8
*Circuits. <i>By Henry Howard</i>	Apr.	10
*Circuits. <i>By Henry Howard</i>	July	10
*Circuits. <i>By Henry Howard</i>	Aug.	13
*Circuits. <i>By Henry Howard</i>	Sept.	8
*Circuits. <i>By Henry Howard</i>	Oct.	7
*Circuits. <i>By Henry Howard</i>	Nov.	7
*Circuits. <i>By Henry Howard</i>	Dec.	10
Communications Receivers	Jan.	16
Comparative Batteries for Portables	July	6
Comparative Packs for Portables (Chart)	July	8
*Crosley 42BR	Dec.	10
*Crosley 548, 5548	July	10
*Crosley 549	Apr.	11
*Crosley 599	Apr.	12
*Crosley 729	Apr.	11
*DeWald 545R	Aug.	14
*DeWald 545LW, 545SW	July	11

*DeWald 663, 666	July	23
*Emerson Phonograph Inverters	Dec.	12
*Emerson DU379, DU380 (Camera) Portable	Aug.	13
*Emerson DV364	Oct.	8
*Emerson EO388 Phonograph Adapter	Oct.	9
*Emerson 8MT574 Phonograph Inverter	Oct.	8
*Firestone Air Chief Westwood S7404-5, Code A343	Nov.	7
*Gamble Skogmo 797	Nov.	7
*G.E. HB412 Battery Portable	Jan.	23
*G.E. HB412 Battery Portable	June	8
*G.E. HJ612	Apr.	10
*G.E. HJ628	Feb.	11
*G.E. HJ1205, RHJS1205	Apr.	10
*G.E. H639 (A-C and D-C). <i>By Allan Epstein</i>	Mar.	16
*G.E. HJ905, HJ908	July	11
*G.E. HM80 F-M Receiver	Dec.	5
*G.E. J501, J501W, J502, J502W	Aug.	13
*G.E. J805, RJS805	July	10
*G.E. JB508, JB513, JB514	June	5
*G.E. JM23 Wireless Record Player	Aug.	27
*Howard 302R, RA, RT Radio Recorder	May	12
*Lafayette S53 Radiocorder	May	13
*Lafayette BB96 Radiocorder	May	12
*Lafayette 1102	Dec.	14
*Marine Radio	Jan.	18
*Motorola Automatic Record Changer Circuits	Aug.	14
*Motorola B150 Bike Radio	July	10
*Motorola RW1	Nov.	7
*Motorola 83F1	Dec.	14
New Features	Jan.	14
*Philco 41-230, 41-235 Code 121	Nov.	16
*Philco 41-290	Nov.	10
*Philco 41-602	Oct.	9
*Philco 41-603, 41-604, 41-605, 41-607	Oct.	8
*Philco 41-608, 41-609	Sept.	8
*Philco 41-788, Code 121, 122	Oct.	10
*Philco 41-788, Code 121, 122	Dec.	12
Police Radio	Jan.	20
*RCA 4QB, 4QB4	Apr.	12
*RCA 14BT1, 14BT2, 14BK	Sept.	9
*RCA 46X1	July	23
*RCA 46XII, 46X12, 46X13	July	12
*RCA 16T3	June	15
*RCA 16T4	Dec.	14
*RCA BF10 (Camera) Battery Portable	July	26
*RCA CV111 Power Unit	Apr.	12
*RCA V102	Sept.	8
*RCA VHR202, VHR207, VHR407	Nov.	8
*RCA V300, V301, V302	Oct.	9
Receiver Sales Figures (1939)	Jan.	14
Replacement Batteries for Portables (Charts)	July	7
Replacement Batteries for Portables (Charts)	Aug.	6
Replacement Batteries for Portables (Chart)	Sept.	30
*Sentinel Battery Set	Oct.	12
*Sentinel-Erla A-C, D-C Line Antenna	Apr.	11
*Sentinel 5 and 6 Tube A-C	Nov.	15
*Sentinel 6 Tube A-C, D-C	Nov.	10
*Servicing F-M Receivers. <i>By Jack Avins</i>	Dec.	5
*Setchell Carlson 66	June	5
*Silvertone 5701	Oct.	12
*Silvertone 5751	Oct.	9
*Silvertone 6324, 6493	July	12
*Silvertone 6326A	Oct.	12
*Silvertone 6326	Feb.	14
*Silvertone 6368, 6382	July	12
*Silvertone 6490A	Feb.	8
*Silvertone 6541	Sept.	8
*Silvertone R121, 721	Oct.	12
*Sonora KG80	June	5
*Stewart Warner 01-8A, 01-8B	Feb.	8
*Stewart Warner 05-5L	June	5
*Stewart Warner 11-2A Wireless Record Player	Nov.	7
*Stewart Warner 11-5V	Nov.	7
*Stewart Warner 11-6V	Nov.	15
*Stewart Warner 11-9B, 11-9BZ	Nov.	10
Push Button Switch	Nov.	10
*Stewart Warner Hudson DB40	Apr.	36
SA40 Production Change	April	29
*Stromberg Carlson F-M Receiver	June	23
*Stromberg Carlson 460PF Service Note	Sept.	9
*Stromberg Carlson 500	Dec.	6
*Stromberg Carlson 505H, 505HB F-M Receivers	Dec.	13
*Stromberg Carlson 585 F-M, A-M Receiver	Dec.	13
Technical Features of 1940-41 Battery Portables (Charts)	June	6, 7
*Truetone D926	Feb.	10
*Truetone D934, 6B6-2	Feb.	11

*Truetone D1080	June	8
*Wells Gardner 1A29	Feb.	15
*Wells Gardner 6D1	Feb.	11
*Wilcox Gay A72 Recorder	May	13
*Wilcox Gay A73	June	8
*Zenith 6D510, 6D525, 6D526 (Chas. 6A01, 6A10)	Aug.	2

**RECORDING**

Cutting Technique	Sept.	6
Disc Characteristics	Sept.	6
General Industries Recorder	Sept.	5
*Home Recording. <i>By Henry Howard</i>	May	12
*Howard 302R, RA, RT Radio Recorder	May	12
*Lafayette S53 Radiocorder	May	13
*Lafayette BB96 Radiocorder	May	12
New Recorder Models	Dec.	10
Profits in Home Recording. <i>By R. C. Powell</i>	Sept.	26
*RCA VHR202, VHR207, VHR407	Nov.	8
Recorder Characteristics (Chart)	Feb.	26
Recording	Jan.	20
Recording Studio	Dec.	15
*Servicing Recorders. <i>By C. J. LeBel</i>	Sept.	5
*Wilcox Gay A72 Recorder	May	13
Wilcox Gay A89, A91, A92, A93, A94 Service Note	Dec.	14

**SOUND**

(See Phonographs, etc., also)

*Acoustic Howl. <i>By Maurice Epstein</i>	Feb.	5
Airport Sound	Aug.	18
*Amplifier Ratings. <i>By John M. Borst</i>	Mar.	14
Auto Race Track Sound	Oct.	30
Ballroom Sound	July	18
Beach Sound	Oct.	22
Bridge Sound	Aug.	18
Decibels vs Watts Conversion Chart	Mar.	15
Electronic Music	Feb.	18
*Electronic Music. <i>By Nathan I. Daniel</i>	Apr.	17
Fire Department Sound	July	18
*Hearing Aid Amplifier	Oct.	7
High School Sound	Dec.	15
*Input Hum. <i>By Jay Shawn</i>	Apr.	26
Intercommunication	Feb.	29
Inter-Room Communicators	Nov.	11
Legislative Hall Sound	Feb.	20
*Lunch Room Intercommunicator	Nov.	11
Memorial Tower Sound	June	10
Microphone Ratings (Chart)	Feb. 22, 24	
Miscellaneous Applications of Sound Equipment	Feb.	23
*Nineteen Forty Sound. <i>By S. Gordon Taylor</i>	Feb.	17
Park Sound	Oct.	30
Public Address	Jan.	20
Recording Studio	Dec.	15
*Reducing Shock Hazard. <i>By Nathan I. Daniel</i>	Feb.	42
School and Church Sound	Feb.	29
School and Church Sound	June	10
Shopping for Amplifiers. <i>By D. L. Elam and B. E. Phillipsen</i>	Mar.	40
Sound Ideas. <i>By Jay Allen</i>	Aug.	18
*Sound Ideas. <i>By Jay Allen</i>	Oct.	19
*Sound Ideas. <i>By Jay Allen</i>	Nov.	11
Sound Ideas. <i>By Jay Allen</i>	Dec.	15
Sound Ideas. <i>By S. Gordon Taylor</i>	Apr.	20
Sound Ideas. <i>By S. Gordon Taylor</i>	June	10
Sound Ideas. <i>By S. Gordon Taylor</i>	July	14
Sound Profits in a Small Town	May	18
Speakers	Jan.	33
*State Fair Sound	Oct.	20
Temple Sound	July	14
Towboat Sound	Dec.	15
Unique Theatre Sound	Nov.	12

**TELEVISION**

Color Television	Sept.	2
Large Screen Television	May	29
Television Link	Mar.	2
Television (Status, Jan. 1940)	Jan.	16
Television Broadcast Stations	Jan.	18
Television in Natural Color	Sept.	28
Television Speeds Up	Mar.	21
*Television Tubes	Jan.	9

TEST EQUIPMENT

	Issue	Page
*A-C Voltmeter	Sept.	11
Alignment Hint. <i>By R. G. Chrouch</i>	Sept.	9
*Ammeter	Sept.	11
*Audio Oscillator & Gain Set	Sept.	6
*Capacity Leakage Tester	Oct.	14
*Chasing Signals. <i>By J. E. Woolley</i>	Jan.	26
*D-C Voltmeter	Sept.	10
*Distortion Meter	Sept.	7
*Electronic Voltmeter	April	6
*Gain Measurements and Signal Tracing	June	14
*Gain Sets	Sept.	7
*Jackson 652 Audio Oscillator	Nov.	30
Measuring Oscillator Grid Voltage	June	26
Measuring Plate Current. <i>By R. G. Chrouch</i>	Apr.	7
*Modern Multitesters. <i>By S. Gordon Taylor</i>	Sept.	10
*Modern Multitesters (Part II). <i>By S. Gordon Taylor</i>	Oct.	2
*Ohmmeter Circuits	Oct.	14
Oscilloscope Helps Sales. <i>By Murray Orman</i>	Mar.	19
*Precision 832 Multitester	June	35
*Precision 854 Multitester	Dec.	28
*Precision E200 Signal Generator	May	15
*Qualitative Condenser Tests	Dec.	28
*RCA 9901 Tube Tester Modernization Kit	Mar.	32
*RCA Rider VoltOhmyst	July	19
*RCA Signalyst	Feb.	16
*RCA VoltOhmyst	Nov.	28
*RSE Condenser Tester	July	28
*Radio City 308 Tube Tester	May	24
*Radio City 414 Multitester	Mar.	36
*Radio City Products 803 Multitester	Oct.	13
Rolindex Tube Tester Chart	Sept.	26
*Servicing F-M Receivers. <i>By Jack Avins</i>	Dec.	10
*Signal Substitution. <i>By G. N. Goldberger</i>	May	14
*Signal Tracing. <i>By Jack Avins</i>	April	5
Signal Tracing (and Gain Measurements)	June	14
*Solar BQC. QC Condenser Checker	June	32
Test Equipment	Jan.	20
Testing New Tubes	Jan.	9
*Triplet 1183, 1620, 1621. Tube Tester	Oct.	24
*Tube Tester	Sept.	10

TUBES

Hearing Aid Tube Characteristics	Oct.	7
Lock-in-Type Tubes (Chart)	Nov.	14
Loktal Contact Pins	April	37
Miniature Tubes	Jan.	9
*Multi-purpose Tubes	Jan.	9
New Maximum Receiving Tube Ratings	Jan.	12
New Tubes	May	25
New Tubes	Aug.	26
New Tube Characteristics Chart	May	25
*Television Tubes	Jan.	9
RCA Preferred Types	Nov.	33
Testing New Tubes	Jan.	9
Tubes. <i>By John H. Potts</i>	Jan.	7
Tubes	Jan.	32
Tubes	March	33, 41
Tube Chart	Jan.	11
1A7GT	Jan.	11
1B7GT	Jan.	11
1B8GT	Jan.	11
*1D8GT	Jan.	11
1E4G	Jan.	11
1G4G	Jan.	11
1G4GT	May	25
1G6G	Jan.	11
1LA4	Nov.	14
1LA6	Nov.	14
1LB4	May	25
1LB4	Nov.	14
1LB4G	Jan.	11
1LC5	Nov.	14
1LC6	Nov.	14
1LD5	Nov.	14
1LE3	Nov.	14
1LH4	Nov.	14
1LN5	Nov.	14
1N5GT	Jan.	11
1N6G	Jan.	11
1N6GT	Jan.	11
1P5GT	Jan.	11
1Q5G	Jan.	11

	Issue	Page
1Q5GT	Jan.	11
1R5	Jan.	11
1S4	Jan.	11
1S5	Jan.	11
1T4	Jan.	11
1T5	Jan.	11
1T5G	Jan.	11
1T5GT	Jan.	11
2W3GT	Jan.	11
2X2/879	Jan.	11
*3A8GT	Jan.	11
3C5GT	Jan.	11
3C5GT	Jan.	11
3LE4	Nov.	14
3Q5GT	Jan.	11
6A85/6N5	May	25
6AC5GT	May	25
6AE5GT	Jan.	11
6AF5GT	Jan.	11
*6AG7	Jan.	11
6AL6G	Jan.	11
6C5GT	Jan.	11
6E8G	Jan.	11
6F5GT	Jan.	11
6H4GT	May	25
6J5GT	Jan.	11
6K6GT	Jan.	11
6P5G	Jan.	11
6P5GT	May	25
6R7GT	Jan.	11
6S7GT	May	25
6S7GT	May	25
6S6GT	Mar.	41
6V6GT	Jan.	11
6W6GT	Jan.	11
6W7G	Jan.	11
7A4	Jan.	11
7A4	Nov.	14
7A5	Jan.	11
7A5	Nov.	14
7A6	Nov.	14
7A7	Nov.	14
7A7	Nov.	14
7A8	Nov.	14
7B4	Nov.	14
7B5	Nov.	14
7B6	Nov.	14
7B7	Nov.	14
7B8	Nov.	14
7C5	Nov.	14
7C6	Nov.	14
7C7	Jan.	11
7C7	Nov.	14
7E6	Jan.	11
7E6	Nov.	14
7E7	Jan.	11
7E7	Nov.	14
7F7	Jan.	11
7F7	Nov.	14
7F7	Nov.	14
7G7/1232	Nov.	14
7H7	May	25
7H7	Nov.	14
7J7	Jan.	11
7J7	Nov.	14
7L7	Nov.	14
7N7	Nov.	14
7Q7	Jan.	11
7Q7	Nov.	14
7Y4	Nov.	14
12A6	Jan.	11
12B7G	Jan.	11
12E5GT	Jan.	11
12K7G	Jan.	11
12K8	Jan.	11
12SF5	Jan.	11
12SR7	Jan.	11
14A7/12B7	Nov.	14

	Issue	Page
14A4	Nov.	14
14A5	Nov.	14
14B6	Nov.	14
14B8	Nov.	14
14C5	Nov.	14
14C7	Nov.	14
14F7	Nov.	14
14H7	Nov.	14
14J7	Nov.	14
14N7	Nov.	14
14Q7	Nov.	14
14Y4	Nov.	14
25AC5G	Jan.	11
25AC5GT	Jan.	11
25A6GT	May	25
25B8GT	Jan.	11
25C6G	Jan.	11
25D8GT	May	25
25Y4GT	Jan.	11
25Z4GT	Jan.	11
35A5	Nov.	14
35Y4	Nov.	14
35Z3	Nov.	14
35Z6G	May	25
40Z5/45Z5GT	May	25
50A5	Nov.	14
50C6G	Jan.	11
50L6GT	Jan.	11
50Y6G	Jan.	11
50Z7G	Jan.	11
70A7GT	Jan.	11
70L7GT	Jan.	11
117L7GT	Jan.	11
117Z6G	Jan.	11
*117Z6GT	Jan.	11
HY 165	Oct.	7
HY 245	Oct.	7
HY 255	Oct.	7
CK501, CK502, CK503, CK504	Mar.	33
CK 501, CK 501X	Oct.	7
CK 505, CK 505X	Oct.	32
CK 505, CK 505X	Aug.	26
1232	Jan.	11

TUNING MECHANISMS

*Band-Spread Tuning (Crosley 42BR)	Dec.	10
*Belmont Permeability Tuning	Dec.	12
Hudson DB40, SA40	June	28
*Hudson DB40, SA40 Feather-touch Tuner	Dec.	23
*Hudson SA40 Feathertouch Tuner	Mar.	10
*Motorola 83F1 Motor Tuning	Dec.	14
*Stewart-Warner 11-9B, 119BZ Push Button Switch	Nov.	10
Stewart-Warner Hudson DB40, SA40	June	28
*Stewart-Warner Hudson SA40 Feathertouch Tuner	Mar.	10
*Stewart-Warner Hudson DB40, SA40 Feathertouch Tuning	Dec.	23
Stromberg Carlson 400 Series. <i>By J. E. Ward</i>	Feb.	14
Wells Gardner 16A26, 16A27, 15S3. <i>By J. K. Rose</i>	Feb.	44
Wells Gardner 36A26, 36A27, 36D1. <i>By J. K. Rose</i>	Feb.	43
Wells Gardner 93WG562, 93WG602, 93WG603, 93WG604, 93WG605. <i>By J. K. Rose</i>	Feb.	44

SAVE \$1.00 !!!

- The Group Subscription Plan for *Service* enables a group of service men, dealers or jobbers to subscribe at one-half the usual yearly rate.
- The regular individual rate is \$2.00 a year. In groups of 4 or more, the subscription rate is \$1.00 a year. (In foreign countries, \$2.00.)
- Each subscriber should print his name and address clearly and state his occupation—whether a dealer, jobber, independent service man, service organization, etc.

Remember this Group Plan when Your Subscription Expires



## Book Reviews...

**SUPERSONICS: THE SCIENCE OF INAUDIBLE SOUNDS**, by R. W. Wood, published by Brown University, Providence, R. I., 1939, 158 pages, price \$2.00.

Professor Wood's excellent summary of supersonics is divided into two main sections, the first concerning itself with the historical development of supersonics while the latter deals with the physical and biological effects of these waves. The properties of supersonic waves are so unusual that it is greatly to be hoped that this book becomes as widely read as it well deserves.  
R. L.

**TELEVISION RECEIVING EQUIPMENT**, by W. T. Cocking, published by Iliffe & Sons, Ltd., Dorset House, London, England, 298 pages, price 7s. 6d.

This book is intended for the student or engineer who is already familiar with radio receiver design. It deals specifically with the cathode-ray type of receiver rather than projection units, the subject being treated as an extension of radio receiver theory.

The first chapter deals with general television principles and serves to acquaint the reader with the essential differences between the vision and sound receivers. This section, written in elementary terms, may be easily understood by the lay reader.

Next the author deals with the television signal. While this chapter is especially well written, the reviewer feels that it is too short to adequately cover this important subject.

The next sixteen chapters are each devoted to a separate functional portion of the television receiver. The data given on electromagnetic and electrostatic deflection is particularly good.

While the author has assumed that the reader has a knowledge of receiver design, he has studiously avoided a mathematical presentation of any portion of the subject. Simple formulas are resorted to only in those cases where mathematics can hardly be avoided. As a result *Television Receiving Equipment* is recommended to those interested in a complete but elementary treatment of television receivers.  
R. D. R.

**WE PRESENT TELEVISION**, edited by John Porterfield and Kay Reynolds, published by W. W. Norton & Co., 70 Fifth Ave., New York City, 1940, 298 pages, price \$3.00.

This book presents its subject, so to speak, through the eyes of a number of well known exponents of the varied activities of the art... such men as Waldemar Kaempffert, Alfred H. Morton, Donald Fink, O. B. Hanson, Thomas H. Hutchinson, Thomas Lyne Riley, Earle Larimore, Charles E. Butterfield, Harry R. Lubcke, J. R. Poppele, Benn Hall, and Robert E. Jones.

This treatise discusses the technique of television, facsimile and of frequency modulation. It also considers the problems of finances, the part of the actor, programming, the director, as well as other interesting aspects of the television art.

The book is intended for the lay reader and is written by men who know their subject. It is recommended to anyone interested in obtaining a composite view of the art.  
R. D. R.

(Continued on page 27)



## STOP WORRYING About Broken Delivery Promises

Cut out doing jobs in a panic. Stop racing the clock to meet delivery promises. Do away with apologies for delays. Stop working on your nerves by trying to "outguess" faulty receivers.

Make your work pleasant and profitable by KNOWING just what is in every set that comes to your bench.

Start all your jobs right—reach for your Rider Manuals. They make it easy to locate troubles quickly for they contain complete and authoritative service data on the sets you are called upon to service. They are the source upon which every successful service

shop in the world depends for data. On American-made receivers—data on alignment, I-F peaks, operating voltages, parts lists and values, voltage ratings of condensers, wattage ratings of resistors, coil resistance data, gain data, and all the other essential information that every serviceman needs for quick, easy, profitable trouble shooting.

Stop being panicked by a lack of information. Give your customers the service you promise and give your business the profits it deserves. Stop in at your jobber's today and get those volumes of Rider Manuals you've been intending to buy.

### YOU NEED ALL ELEVEN

Volume	Price	Covering	Volume	Price	Covering
XI	\$10.00	Upto May 15, 1940	VI	\$7.50	1935-36
X	10.00	1939-40	V	7.50	1934-35
IX	10.00	1938-39	IV	7.50	1933-34
VIII	10.00	1937-38	III	7.50	1932-33
VII	10.00	1936-37	II	7.50	1931-32
			I	7.50	1920-31

**JOHN F. RIDER Publisher, Inc.**

404 Fourth Avenue, New York City

Export Division: Roche-International Elec. Corp.  
100 Varick St., New York City Cable: ARLAB

**Don't Guess  
Know!**

**You NEED RIDER MANUALS**



# B U S Y S H O P

*Time is at a premium in this New England Service Shop, which manages to keep busy throughout the entire year. Successful methods, successfully applied serve to bring in a high class of service jobs that ensure fair profits. Judicious advertising in suitable local mediums also helps create a continuous volume of business.*

Successful servicing from the shop owner as well as customer standpoint is exemplified in the solidly established and increasingly prosperous business of Community Radio Laboratory, Norwood, Mass., operated by James F. Waldron.

Expert service, expertly advertised, keeps this shop filled with work the year round, at profitable rates, and this without making any calls whatsoever in homes, either for the purpose of giving estimates or performing service work.

Three dollars is the fee, minimum or per hour. Some estimates are given free and others not, depending on conditions. For example, if upon examination it is found that the trouble will take some time to isolate, and, in some cases, even require repairs before an honest estimate can be given, a charge of \$2.50 is made, which is deducted from the service charge if the owner decides to have the work done.

In addition to its principal business of home receiver servicing, Community Radio Laboratory installs and maintains police communication apparatus, builds

and sells sound equipment, noise elimination filters, electronic control devices for retail store advertising, and in fact almost anything for which there is a profitable sale.

An increasing phase of the company's activity is work done for auto-radio dealers who do not maintain a radio service department of their own. Work for such dealers requiring less than an hour is performed at a flat rate of \$1.50 per unit, while jobs requiring more than an hour are billed at the standard rate of \$3.00 an hour, with parts billed at cost plus a handling charge of 10%. A check-up of jobs of this nature over a three months' period showed time per

James F. Waldron employs photographs of his "Community Radio Laboratory" workbench in advertising copy with resulting favorable press comment and increased business. The instruments shown are, from left to right, CRA oscillograph; Model 110 signal generator; Model 111 Unisignal frequency modulator and Model 135 Unichecker on rack with a Model 79C beat frequency oscillator. We can readily see that this is one shop that is amply equipped to do efficient service work.

*Photo courtesy Clough-Brengle*



job as averaging about twenty minutes each.

Advertising of the concern, which is consistently maintained in the local newspaper at an average cost of \$25 per month, emphasizes that while no cut or bargain prices are offered, the customer is guaranteed honest treatment and full value for every dollar spent. The following example will illustrate:

---

#### OUR PROFESSIONAL SERVICE FEE

We value our time at a much higher rate than any other company we know of—but for value received we can honestly refer you to our many satisfied customers. Ask any or all of them. Three dollars is our fee, minimum or per hour. We invite you to investigate. Thank you. Community Radio Laboratory.

---

Photographs of the shop, which, as the accompanying illustration shows, is made up of latest type of instruments for rapid dynamic testing and visual precision check and alignment, have been extensively employed in advertising, with resulting favorable press comment and increased volume of high-class trade, with midget receivers absent.

Work is performed at the front of the shop, where customers are privileged to look on all they like and satisfy themselves that in work expertly performed with latest precision, time saving instruments, they are actually getting the most for their money.

"There is no better success formula for Service Men," says Waldron, "than to know your business and let the public know you know it. Expert work plus good showmanship pay excellent dividends on time and money invested."



# Case Histories

## STEWART-WARNER HUDSON DB40, SA40

**Feathertouch tuner operation:** When a push-button is depressed, it makes mechanical contact with the cam operating bar located under it, and depresses the bar so that the gathering bar can make contact with it. At the same time, the key forces the contact plate downward, making electrical contact through the contact screw. When the contact screw makes contact, it energizes the winding of the magnet assembly causing the plunger to be drawn completely into the magnet as shown in Fig. 2. The plunger is mechanically coupled to the gathering bar and gathering bar shaft, so that when the plunger is drawn into the magnet, it causes the gathering bar to be forced ahead. The gathering bar engages the cam operating bar which is depressed by the push button key and drives it forward as shown in Fig. 2. This position of the cam operating bar is indicated by the ends of the cam operating bar extending from the mechanism frame (see Fig. 3). When the cam operating bar moves forward, the cam stops attached to the bar, engage the cam, rotating it until it is in the position indicated in Fig. 2. The rotation of the cam causes the cam shaft and gear segment to rotate likewise, rotating the gang condenser to a position corresponding to the station to which this particular key is set.

**Locking mechanism:** The cam shaft assembly consists primarily of a shaft on which five cams are alternately spaced between friction collars. On the clutch end of this bar is a short threaded section upon which screws the collar which is part of the clutch and clutch spring assembly. When the cams are locked, this threaded collar is turned upon the threaded section of this cam shaft, exerting pressure upon the cams and friction collars, thus locking them securely in position. When the cams are unlocked, this threaded collar is turned so as to unscrew it and exert a minimum of pressure on the cams and friction collars. The only pressure then exerted upon the cams to hold them in position is that exerted by a spring washer near the threaded end of the shaft. Thus the cams are held so they cannot move of their own accord, but are still loose enough to permit them to be set to correspond to the desired station.

The threaded collar is connected through the clutch to the manual tuning control, permitting adjustment of the cams from outside the tuning unit.


**Clutch and de-clutch arm:** The clutch mechanism of this tuner (see Fig. 3) func-

tions every time a push button is depressed. Its purpose is to decouple the manual-tuning control and its associated gears from the automatic portion of the tuner when tuning electrically. The clutch is a dual unit, providing positive mechanical coupling between the manual tuning gears and the cam shaft, and it also has a leather friction disc which operates in conjunction with the positive coupling element to remove excessive backlash when tuning mechanically.


When the plunger is drawn into the magnet, turning the gathering bar shaft the came attached to the shaft (Fig. 3) moves downward on the riser of the declutch arm, which bears against the inside section of the clutch. When this pressure is released, the clutch return spring contracts, separating the two halves of the clutch, thus disengaging the manual tuning gears.

When the push button is again released, allowing the plunger to be withdrawn from the magnet, the cam on the gathering bar shaft moves upward on the declutch arm riser, again exerting pressure on the declutch arm, and in turn on the clutch, thus engaging the two clutch sections, and making manual tuning possible.

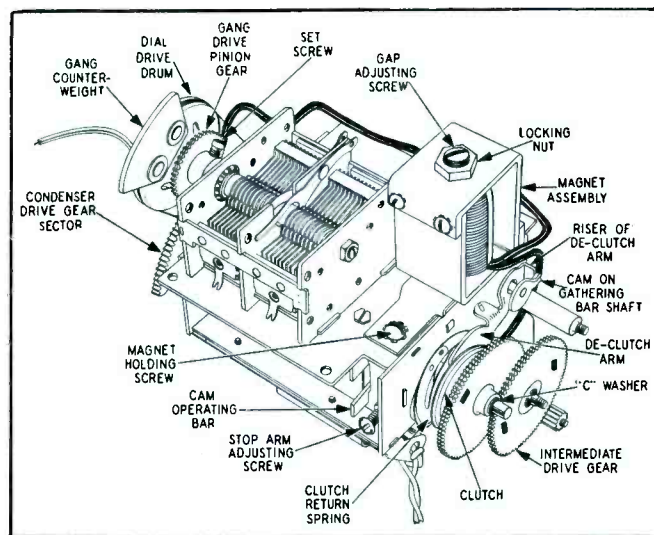**Tuner troubles. Set tunes improperly:** If the set fails to tune in stations properly, first check the set-up of the various buttons. If the set-up is incorrect, the set will tune consistently to the same point, and this condition can be remedied by resetting the buttons.



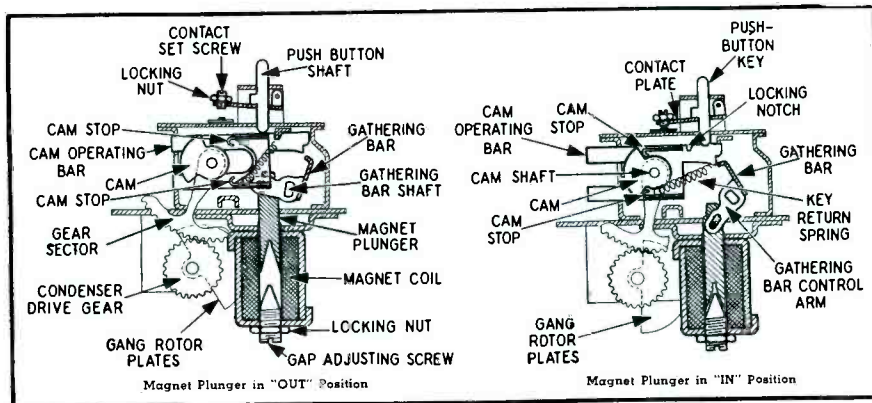Figs. 1 and 2. Push-buttons operate a solenoid which in turn drives the condenser proper.



If the set will not tune in stations, although the plunger tends to move, make sure the bristol headed set screws in the retaining collar are tight. This is the collar which is almost touched by the condenser drive gear sector when the condenser plates are unmeshed. A loose set screw may strike the unit frame, causing the plunger to stick in either the in or out position.

If the set fails to tune properly, and the dial stops at different points when approaching the station from opposite ends of the dial the mechanism may not be properly locked up. The next step is to check for binding of the mechanism. This trouble also may occur if the pulling force of the magnet is not great enough. This may occur when the battery voltage is low (below 5 volts). It may also be due to too large a gap between the plunger and the pole piece of the magnet assembly. On later sets the gap can be adjusted. The adjustable magnet assemblies are identified by the gap adjusting screw and locking nut shown in Fig. 3.

In the early type of magnet assemblies, the gap is not adjustable. If one of these magnets is found to have insufficient pull, the remedy is installation of the new type magnet assembly. However, before replacing a magnet assembly, make sure that improper tuning is not due to low battery voltage or the other causes mentioned above.

**Ends of drum rubbing brackets:** The dial drum should have a slight amount of end play. If it doesn't, it may be binding. This may be due to improper placement of the volume control mounting bracket. To correct this difficulty loosen the two screws holding this bracket and move this bracket slightly farther away from the drum.

Similar binding may also be due to a loose end cap on the dial drum. In this case, force the cap back on the drum and punch-mark the cap to hold it in place on the dial drum.



In a few cases it may be found that dial end bearing is out of line or slightly off center. The bearing can generally be bent slightly to restore it to its proper position. If this cannot be done, replace the dial scale assembly.

Binding of the drum on the mounting brackets may be due to the fact that the control units fitted too tightly in early cars. This causes the escutcheon to be forced sideways, thus pressing on the tuning controls, which may move the dial drum brackets. This binding can generally be eliminated by bending the brackets slightly



# NEW Combination Tester

TRIPLET  
MODEL 1183

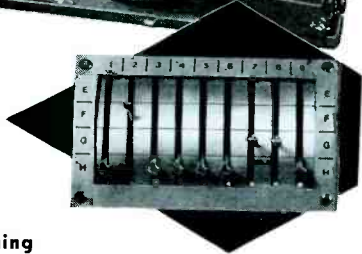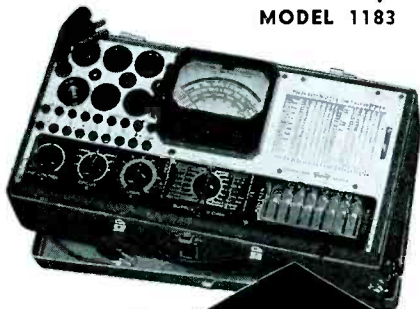

New  
Lever  
Switching

... Combining simplicity of operation with absolute flexibility, Triplet's new lever switching permits individual control for each tube element—yet test procedure is simple and quick. The switch setting shown above will permit tests of 45 commonly used different type tubes without change of position of the levers. Many tubes require only two lever switch settings—more than half—only three settings.

Model 1183 is truly a Non-Obsolescent Tube Tester, combined with a Volt-Ohm-Milliammeter and Free Point Tester. . . . three fundamental testers that you can use for many years. Volt-Ohm-Milliammeter Ranges: 0-10-50-250-500-1000 AC and DC Volts; DC at 10,000 Ohms per Volt; AC at 2000 Ohms per volt. DC Milliamperes 0-1-10-50-250; Resistance 0-500 low ohms; 0-15,000 ohms; 0-1.5 and 0-15 Megohms. Complete Free Point Tester with sockets for all tubes, including new Midgets. Tube Tester has new lever type switch. Speedex Roll Chart, removable from panel as separate unit. Dealer Net Price . . . . . \$49.84

Model 1182 Tube Tester. Same as Model 1183 but has no Volt-Ohm-Milliammeter or Free Point Tester. Dealer Net Price . . . . . \$34.84

Model 1184 Tube Tester and Volt-Ohm-Milliammeter. Same as Model 1183 but has no Free Point Tester. Dealer Net Price . . . . . \$44.84

## MODEL 666

A Complete Pocket Size Volt-Ohm-Milliammeter with AC-DC Voltage ranges: 0-10-50-250-500-1000 at 1000 ohms per volt; DC Milliamperes 0-1-10-50-250; Low Ohms, 1/2 to 300; High Ohms to 250,000 with provisions for higher readings by external batteries. Molded case and panel. Dealer Net Price \$14.00



Write for Catalog — Section 1712 Harmon Drive

THE TRIPLET ELECTRICAL INSTRUMENT CO.  
Bluffton, Ohio

outward.

Similar difficulties will be encountered if the control head is not properly installed. When mounting the head, tighten the wing nuts evenly, so the control head will not have a tendency to bind against the dash opening, which would push the escutcheon against the controls.

*Drive pulley striking antenna coil shield:* Check to see that the dial-drive pulley is properly located on condenser shaft. Its bushing should touch the condenser pinion gear.

Also, the antenna-coil shield can may be moved slightly away from the drum by loosening the two nuts holding down the can.

It may also be possible to move the en-

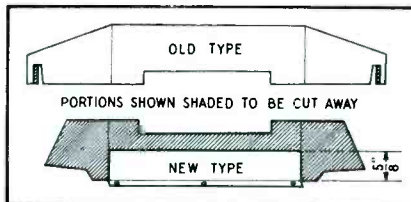


Fig. 4. Binding caused by the light diffusion plate can be corrected by cutting away a portion of the plate.

tire tuning unit slightly away from the shield can. Loosen the four screws holding down the unit and shift it.

*Tuning control fails to reach stop during unlocking:* This is probably due to the shearing off of the "C" washer on the clutch end of the cam shaft (see Fig. 3). On the earlier mechanisms, this "C" washer holding the clutch and gear assembly to the shaft was made of a fairly soft steel. Occasionally these washers may shear off if the customer continues turning the tuning wheel after the mechanism has become completely unlocked. This continued turning forces the gear and clutch assembly against the "C" washer, shearing it off completely. You can replace this washer with a new hardened washer. This can be done without removing the tuning unit from the case. First lock the mechanism, then remove the nuts holding the triangular plate on the clutch end of the tuner. Unhook the plunger return spring so that no pressure will be exerted by the clutch. The washer can now be removed and a new washer installed.

On all early sets, replace this "C" washer even if the old one is still all right.

Shearing or partial shearing of this washer may cause slipping of the clutch or sticking of the plunger in the out position.

If a bronze washer is present between the "C" washer and the gear, remove it and discard it. If a steel washer is present, it must be left in place. On early mechanisms, a 1/32 in a steel washer was used in this position and it must be left in place.

*Light diffusion plate rubs:* Two types of light diffusion plates were used; the newer type is riveted to the cover, while the older type is mounted on the unit itself. (See Fig. 4.) If the newer type of plate rubs against the dial scale due to warping of the celluloid cut this plate as shown by the shading in Fig. 4. This can be done without removing the shield from the cover. In some early units, this diffusion plate was mounted on the unit itself. In this case, enlarge the notching fitting over the dial lamp wire as shown in Fig. 4. Exercise care when enlarging the notch, as the celluloid is quite brittle and may break. Then cement the diffusion plate to the front of the contact plate assembly so that the shield rests flat against this metal plate.

# BRACH Antennae

Automobile  
Home — All types  
F-M Systems  
Television  
Police • Marine  
Multiple Systems  
Complete Kits  
Accessories

Made by World's Oldest and Largest  
Manufacturers of Radio Aerial Systems

**L. S. BRACH MFG. CORP.**  
55 DICKERSON STREET  
NEWARK, N. J.

## Public likes Airline SOUND SYSTEM ... Say P. A. Men

The clear, natural tone and volume without distortion are sound system qualities that appeal to the public and boost business for sound system men. These are assured by the Ward Airline. "People think we have the best sound system this side of Boston," says a Massachusetts man. And an Ohio man writes, "People say my Airline is the best sound system they had heard." There are literally scores of similar expressions. Outstanding results with trouble-free operation and low upkeep cost!

### Ask for Catalog

The Airline Sound System Catalog explains everything in detail. Shows how everything plugs together. No technical knowledge or experience required. Shows how the Ward direct selling plan offers immense savings. Send coupon for your FREE copy!

TIME PAYMENTS  
15-Day Trial  
Money-Back Guarantee

Montgomery Ward  
9 GREAT MAIL ORDER HOUSES  
MORE THAN 600 RETAIL STORES

MONTGOMERY WARD & CO.  
Dept. AT-42, Chicago, Ill.  
Mail at once FREE Catalog on  
Airline Sound Systems.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_



RUSH  
COUPON



## SERVICING F-M

(Continued from page 9)

the discriminator transformer, the output indicator should be shifted to point B. For this operation a center-zero instrument is desirable, as was previously explained. With the generator still at exactly the i-f, the secondary trimmer  $C_s$  should be adjusted for zero output. If an artificial zero is used, then the correct adjustment of  $C_s$  will be easily detected by the fact that there will be no change in reading as the signal input to the limiter is varied from zero to maximum. If the frequency of the generator is varied slightly in either direction, the reading of the indicator will vary on both sides of the zero deflection.

### I-F Alignment

To align the i-f amplifier it is preferable to start at the stage preceding the limiter and to align one transformer at a time. The design of practically all i-f amplifiers is such that they can be aligned at the center i-f and the response will then be satisfactory for 75 kc either side of the center frequency. The limiter will take care of any non-uniformity due to the selectivity of the i-f transformers. A factor tending to simplify i-f alignment is the heavy loading of the i-f transformers; this is used to help in obtaining the required 150-kc bandwidth.

To adjust the last i-f transformer, the signal generator should be connected to the last i-f tube and the trimmers adjusted for maximum output at the center frequency. The output indication is the voltage developed at the grid of the limiter tube. As previously explained, this may be an electronic voltmeter or a milliammeter connected in the limiter grid circuit.

When the alignment of the last stage is completed, the signal generator connection should be shifted to the preceding stage and this stage aligned in the same way. To align the first i-f transformer the signal generator should be connected to the grid of the mixer tube. Here some difficulty may be experienced in obtaining sufficient output because of the virtual short circuit across the signal generator output in the form of the few turns constituting the r-f coil. If it is not possible to obtain enough output, then the r-f grid lead should be disconnected. Usually, since single-ended tubes are used, this will mean that the lead will have to be unsoldered. A resistor, about 10,000 ohms in value, should be shunted from grid to ground to complete the grid circuit.

IT'S RCA FOR UNMATCHED QUALITY..UNBEATABLE LOW PRICES!

# Your BEST Bridge Between Amplifier and SOUND! RCA QUALITY SPEAKERS



Power Sound Projector.  
Handles 100 Watts—  
projects to 4,000 feet.  
MI-6256.




12" P.M. Dynamic—  
Handles 10 Full Watts  
with high quality.  
MI-6247A.



Directional Sound Baffle.  
Efficient. Wide Angle.  
MI-4428 for 12" Speaker.



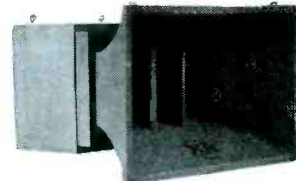Revolutionary! New RCA  
Accordion Edge Speaker.  
"Bellows Action." MI-6234.



Auditorium Wall Speaker  
Cabinet—for MI-6237, or  
other 15" P.M. Dynamic.  
MI-6223.



High Output—High  
Quality! 15" Permanent  
Field Dynamic. MI-6237.

YOU KNOW . . . and we know . . . that sound reproduction quality is more often marred by the *speaker* than by any other element in the system! That's why good speakers are your *best* Sound Investment!

Who makes the best speakers—? RCA. Why—? Because the extensive research of the greatest name in radio has found the best answers to problems of speaker design and manufacture. When you buy a modern RCA Speaker, you buy *low distortion*—for extra clarity in speech and music. You buy uniform, extended *frequency-response*—for higher-fidelity. You buy higher audio-to-sound *conversion efficiency*—for greater coverage with smaller amplifiers . . . for more actual Decibels from your Watts!

And because of the tremendous mass-production facilities of RCA, prices are pleasingly *low*! Believe your ears—*hear* RCA Speakers at your RCA Distributor's this week!



## Commercial Sound

RCA Mfg. Co., Inc., Camden, N. J. • A Service of Radio Corporation of America

Any Sound System Sounds Better Equipped with RCA Radio Tubes

This resistor is not required if there is a d-c path through the signal generator output. When the lead is replaced, the same lead dress should be observed to avoid changing the r-f alignment.

The overall i-f and discriminator alignment can be readily checked with the signal generator connected to the mixer grid. At the center frequency to which the i-f transformers are peaked, the output of the discriminator at B in Fig. 7 should be equal to zero; at this same frequency maximum output should be indicated at the limiter grid. If the output at A is not zero, a slight

adjustment of  $C_s$  will bring it to zero. To check the symmetry of the alignment, detune the signal generator about 75 or 100 kc on either side of the center frequency, and note the output at point A in Fig. 7. If the output is not the same on either side (of course it will be opposite in polarity as Fig. 3 shows), then a readjustment of the primary trimmer  $C_p$  can be made until the two values are equal.

In working on combination a-m and f-m receivers which use the same tubes for both the a-m and f-m alignment, particularly those which use the i-f



## Reach for a DANDEE!

IF ever there was a condenser that could qualify as a so-called universal or general-utility replacement, it's the new PR5 450-8 AEROVOX DANDEE. It's the most compact midjet metal-can dry electrolytic on the market . . . a genuine hermetically-sealed job . . . full-rated capacity and voltage . . . colored polarity-indicating ends . . . spun-over jacket preventing shorts and grounds—in a word, a real good electrolytic.



And now, for your convenience, these PR5 450-8 DANDEES come packed five to the box. Buy a box. Pack it in your old kit bag. And when it comes to those quick servicing jobs, just reach for a DANDEE!



### Ask Your Jobber . . .

Get a carton of DANDEES. Always have a box on hand. Also ask for our latest catalog. Or write us direct.



transformers in series, there may be some interaction between the a-m and f-m alignment. This will be very slight and unless the f-m alignment is carried out while the a-m alignment is very far off, there will be no necessity for realignment of the a-m circuits. This is also true of the a-m alignment.

### Oscillator Alignment

The alignment of the oscillator circuit is similar to the alignment of any superhetrodyne high-frequency oscillator. A convenient procedure is to feed a signal into the antenna posts at a frequency near the upper end of the f-m band at about 48 mc. Follow the manufacturer's recommendation for this frequency. Using the output indicator in the limiter grid circuit, the oscillator trimmer should be adjusted so that the dial calibration is correct. Usually no adjustment is provided at the low-frequency end of the band because of the limited tuning range. If the dial calibration is appreciably in error at the low-frequency end of the range, it can be corrected by moving the end turn of the oscillator coil slightly.


It is advisable to check the image response of the receiver to prevent misalignment of the oscillator. Unless otherwise stated by the manufacturer, the oscillator should be adjusted *below* the signal frequency. This means that the image signal will be *below* the receiver dial frequency by an amount equal to twice the i-f. For example, if the dial frequency is 48 mc, and the i-f is 4 mc, then an image response should be obtained when the *signal generator* is shifted to 40 mc.

### R-F Alignment

The alignment of the r-f circuits in an f-m receiver is conventional. To obtain the best alignment of the antenna transformers, a dummy antenna consisting of a 75-ohm carbon resistor should be used. This should be connected in series with the high side of the signal generator cable at the antenna posts of the receiver. Usually the r-f circuits are trimmed near the high frequency end of the band at about 48 mc, using the output indicator in the limiter grid circuit. The antenna and r-f trimmers should be adjusted for maximum output; to compensate for interaction between the oscillator and r-f circuits, it is best to rock the tuning condenser while the r-f adjustments are being made. Unless the wiring has been disturbed, the sensitivity of the receiver will be uniform over the band. If the sensitivity drops toward the low-frequency end of the band, then it will be necessary to adjust the inductance of the antenna and mixer grid coils so as to improve the tracking.

# BIG BOY

MODEL 860

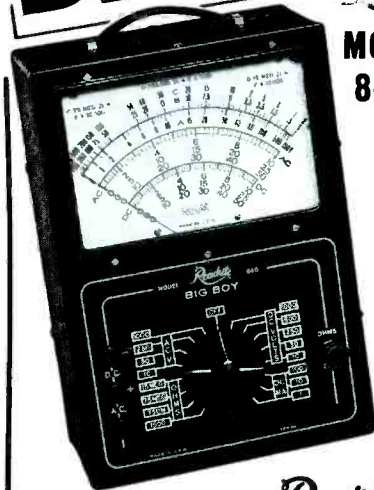

Performance . . . Eye Appeal . . . Value . . . Sensationally Priced at \$17.85, Dealer Net Price.

Readrite RANGER

Here is an AC-DC Volt-Ohm-Milliammeter with all the ranges you want . . . easily readable on the large 7" instrument with extra-long 6" scale, in a new up-to-the-minute three-tone case. DC Volts 0-10-50-250-500-1000 at 5000 Ohms per volt DC; 1000 ohms per volt AC. AC Volts 0-10-50-250-1000 at 400 ohms per volt; DC Ma, 0-1-10-100; Resistance ranges; 0-1500 Low Ohms; 0-750,000 Ohms and 0-7.5 and 0-15 Megohms. Maroon case with red and silver panel, attached handle.

Dealer Net Price, \$17.85. For Catalog Write—Section 1217, College Ave.

READRITE METER WORKS, Bluffton, Ohio

YOU WILL WANT

## "MYSTERIES of TELEVISION"

by

ARTHUR S. VAN DYCK

Executive Engineer R.C.A. License Lab.

### CONTENTS:

The Start of Television—The Iconoscope—The Receiver — The Kinescope—Propagation Through Space—Network Operation—Effects of Television—The Future—Facsimile—Electron Optics—Television Studios and Programs—Television Personnel—Questions About Television—Dictionary of Television Terms.

Told from a popular standpoint, the reader is given an understanding of how this newest branch of Radio works.

Mr. Van Dyck has served with the Marconi, Westinghouse, and General Electric Companies and is experienced in all aspects of radio-research, development, design, manufacturing and operating. He has taught electrical engineering at Carnegie Institute. He is a member of the Technical Advisory Board of RCA Institutes.

Send \$1.00 for postpaid delivery

BRYAN DAVIS PUB. CO.

Dept. B.

19 East 47th St., New York, N. Y.



## Book Reviews . . .

**AIRCRAFT RADIO AND ELECTRICAL EQUIPMENT**, by Howard K. Morgan, published by Pitman Publishing Corporation, 2 W. 45th Street, New York City, 1939, 374 pages, price \$4.50.

This is a timely book on a subject about which little information has been available. It presents in detail data regarding aircraft transmitters, receivers and accessories together with the inspection and maintenance methods used by the TWA. Complete schematics of representative transmitters and receivers are included with the text and each is completely discussed.

An effort has been made to get away from a cut-and-dried engineering presentation, thus widening the usefulness of the book to those who are not technically trained in the subject. The first three chapters are devoted to elementary electrical and radio theory, which are simply and clearly explained. J. H. P.

**ALTERNATING CURRENT BRIDGE METHODS** (4th Edition), by B. Hague, published by Pitman Publishing Co., 2 West 45th St., New York City, 1938, 587 pages, price \$8.50.

First introduced in 1923, Hague's book on bridges has long been accepted as the most complete and authoritative on this subject. In its fourth edition, the fundamental material has been supplemented to include modern developments in the field so that it is thoroughly up to date in every respect. In this latest edition, 150 pages of new matter have been added, largely devoted to modern practice in bridge measurements, new bridges and the applications of vacuum-tube amplifiers, oscillators and detectors in bridge measurements. Some consideration is given to radio-frequency bridges though, as stated in the first chapter, the book is primarily devoted to measurements which are to be made at audio frequencies. J. H. P.

**THE AMPLIFICATION AND DISTRIBUTION OF SOUND**, by A. E. Greenlees, published by Chapman & Hall, Ltd., 11 Henrietta St., Covent Garden, London, W. C. 2., England, 1938, 254 pages, price 10s. 6d.

Intended primarily for the engineer who is interested in the design, application or operation of public address or sound systems generally, this book is written in an elementary and easily understandable style. The use of mathematics, except for occasional reference to elementary laws of electricity is avoided throughout the text. It is copiously illustrated with charts, curves, and diagrams.

The opening chapters are devoted to a review of the fundamentals of electricity. Later such items as chokes, transformers, microphones, loudspeakers, radio receivers, record reproducing equipment and amplifiers are covered in some detail. Performance data are also covered in excellent style. In addition, such items as installation planning, operation and maintenance of equipment, preparation of specifications and general system aspects of sound systems are dealt with fully.

This book is well written and adequately illustrated. It is recommended to Service Men interested in the subject of sound distribution. R. D. R.



## WHAT HAS UTAH'S POLICY

### TO DO WITH YOUR SALES?

**YOU** have made your business successful by maintaining a policy which has won the confidence of your customers—has made it profitable for both them and you.

Many years ago, Utah Radio Products Company established a policy which has been strictly maintained.

Utah products are distributed through the industry's recognized channels *only*—careful selection is made to avoid unfair competition.

Utah's engineering and designing keep abreast of all industry improvements and developments.

Utah retains outstanding engineers and manufacturing experts.

Utah advertises regularly and effectively in leading publications

to inform the trade and *your* customers of the advantages which Utah products can give them.

Utah's policy is to adhere to relationships which are to the best interests of its customers and the industry as a whole. This policy has been largely responsible for the success of Utah through good times and bad. It has built Utah's 1940 business to greater volume than ever before attained.

Our firm resolve is to maintain this policy which has been so mutually beneficial. Utah Radio Products Company, 816 Orleans Street, Chicago, Illinois. Canadian Office: 560 King Street West, Toronto. In the Argentine: Ucoa Radio Products Company, S. R. L. Buenos Aires. Cable address: Utaradio. Chicago.



## SPEAKERS

VIBRATORS • TRANSFORMERS • UTAH-CARTER PARTS

**FUNDAMENTALS OF ELECTRICITY AND ELECTROMAGNETISM**, by Vernon A. Suydam, published by D. Van Nostrand Co., 250 Fourth Ave., New York City, 1940, 690 pages, price \$4.75.

This book is intended as a text for the advanced student of electricity and magnetism, much of the material coming from the author's lecture notes on the subject. Written from the viewpoint of the physicist, this excellent treatise should be equally useful as a text and as a reference book for the industrial physicist or engineer. While there are a number of excellent texts available on the subject, this book appears to have more useful fundamentals for the communications engineer than any which has come to the attention of the reviewer. It gives a clear, logical and

systematic treatment of the fundamentals which are basic to the communications field.

The chapters on magnetostatics and terrestrial magnetism are especially well written and understandable, while the data on "The Magnetic Circuit" should be quite interesting to engineers dealing with electromagnetic devices. Two lengthy chapters are devoted to complex quantities and their application to alternating-current theory. In addition, considerable data is given on a-c bridges, as well as on vacuum tubes, tube rectifiers, mercury-arc rectifiers, r-f amplification and detection, radio transmitters, piezo-electric frequency control and many other allied subjects.

This book is highly recommended.

R. D. R.

(Continued on page 31)

# PRECISION 854 MULTITESTER

**T**HE Series 854 high-sensitivity multimeter is a general service instrument featuring some thirty odd ranges for seven functions. Provision is made for d-c voltage readings at 20,000-ohms-per-volt and a-c voltage readings at 1,000-ohms-per-volt. Voltage ranges are provided up to 6,000 volts and direct current ranges from 60 microamperes (full scale) to 12 amperes. Resistance measurements can be made from a fraction of an ohm to over 40 megohms.

The commonly used voltage, current and decibel ranges are available at a single pair of polarized tip jacks through the use of a master multirange selector. This selector thus permits range change without the necessity of removing and reinserting test leads as would be required if numerous terminals were employed for the various functions.

The higher voltage ranges, namely the 1,200 and 6,000-volt ranges; the high-sensitivity, 60 and 300 microampere ranges; the output, and the 12-ampere ranges are terminated at distinctly marked, individual tip jacks. These ranges are also used in conjunction with the range selector.

## The Circuit

The ring type ohmmeter circuit used in the Series 854 is practically unaffected by battery voltage (over the useful range of battery life) or by the setting of the zero adjusting control. The circuit constants are so arranged, and the tolerances so chosen that only slight readjustment of latter control is necessary when changing from one range to another, it is said.


A dry-disc type of instrument rectifier is used to provide for a-c voltage measurements on the d-c instrument. Separate 1,000-ohm-per-volt multipliers are used for these measurements. 20,000-ohm-per-volt multipliers are used for the d-c voltage measurements. To assure higher accuracy for the a-c measurements, individual a-c voltage calibrating controls are provided.

Two separate ring type shunt networks minimize the effects of switch contact resistance during current measurements. These shunts are wire wound to an accuracy of 1 percent.
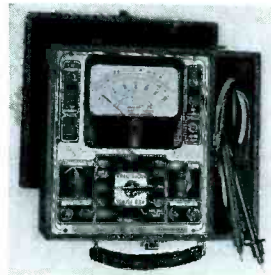
## Paper Condenser Tests

The insulation resistance or permissible leakages of paper and mica con-

densers is expressed in megohm microfarads. A good 1-mfd condenser will have an insulation resistance of approximately 450 megohms. Furthermore, insulation resistance of paper and mica condensers of similar voltage ratings is inversely proportional to its capacity, so that a 0.1-mfd condenser will have ten times the insulation resistance of a 1-mfd condenser or 4500 megohms. It therefore can be readily seen that it is not practical to use the ohmmeter method for measuring leakages in paper or mica condensers.



In the following method, a high d-c potential is applied to the condenser in series with the proper d-c volts range to determine whether or not it has low insulation resistance or abnormal leakage.

The necessary d-c potential can be obtained from an external high voltage d-c power supply or from the power output tube socket of a receiver. In the latter instance, the plate prong position of that socket will be the positive high voltage lead and the negative return or ground will be the negative lead. Voltage to be applied to the condenser should be slightly higher than its rated voltage.


1) Measure the d-c voltage obtainable from the power supply to be used. Then select the proper voltmeter range that would indicate the greatest deflection for the voltage there available.

2) With the power supply off, insert the high voltage leads into the instrument tip jacks, observing correct polarities, and insert the condenser to be tested in series with one of these leads.

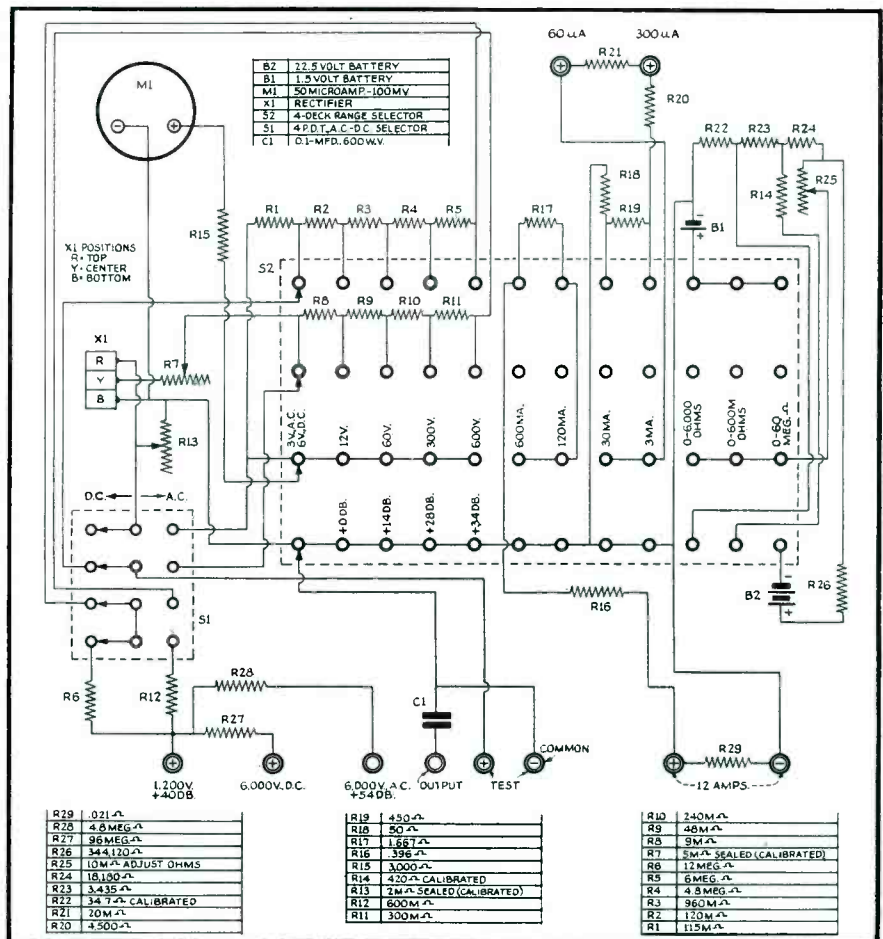3) Turn on the power supply. An instantaneous deflection due to the

*(Continued on page 30)*

The Series 854 is a 20,000-ohm-per-volt multimeter designed for complete receiver testing. Some thirty odd ranges are offered in both a-c and d-c functions.





# ASSOCIATIONS

## Trade Show for 1941

At the annual meeting of the Board of Directors of Radio Parts Manufacturers National Trade Show, Inc., held at the Stevens Hotel, in Chicago, Nov. 18, 1940, Messrs. A. A. Berard, H. E. Osmun, and J. J. Kahn, were reelected as president, vice president, and secretary-treasurer, respectively. Herbert W. Clough was elected to the Board of Directors to represent the Western Division of the Sales Managers Club. Mr. Clough began his term of office at this meeting.

The 1941 Radio Parts National Trade Show will be held at the Stevens Hotel, in Chicago, June 10 to 13, inclusive. The first three days will be devoted to the jobbing trade, and on the last day the Exhibition will be open to the radio trade in general.

### Dallas, Texas

The Dallas Radio Service Association was host to a representative group of Service Men in the Dallas trade territory at their regular monthly meeting held Dec. 6. Walter Jones, Sylvania engineer, presented a very excellent lecture on "Tube Applications." This makes the sixth in the series of 1940-41 lectures by nationally famous engineers who have been brought to Dallas by the local association as part of its educational program. The program has produced a 50 percent increase in attendance during 1940 and has resulted in very close cooperation between factory representatives, jobbers and Service Men.

*Porter T. Bennett, Secy.*


### Danville, Ill., RSA

The Danville Chapter of the Radio Servicemen of America have changed their meeting nights from the second and fourth Friday nights of each month to the second and fourth Wednesday nights of each month.

The Chapter now has club rooms at 113½ N. Vermilion St., Danville, Ill., which not only has helped increase attendance at the regular meeting but has made it possible to promote more social activities.

At the present time the entire Chapter is busily engaged in a Christmas program

George C. Connor, Hygrade Sylvania commercial engineer, is shown (at the left) pulling the winning number at a recent Service Men's gathering held in the Architect's Building, Philadelphia. The meeting was sponsored by Norman M. Sewell of Century Radio (at the mike), Sylvania distributors. W. F. Wolff, 537 W. Cambria St., Philadelphia, won the prize, a floor model stock-boy cabinet. Mr. Connor is a member of the Advisory Board on Industrial Education for the New York Board.

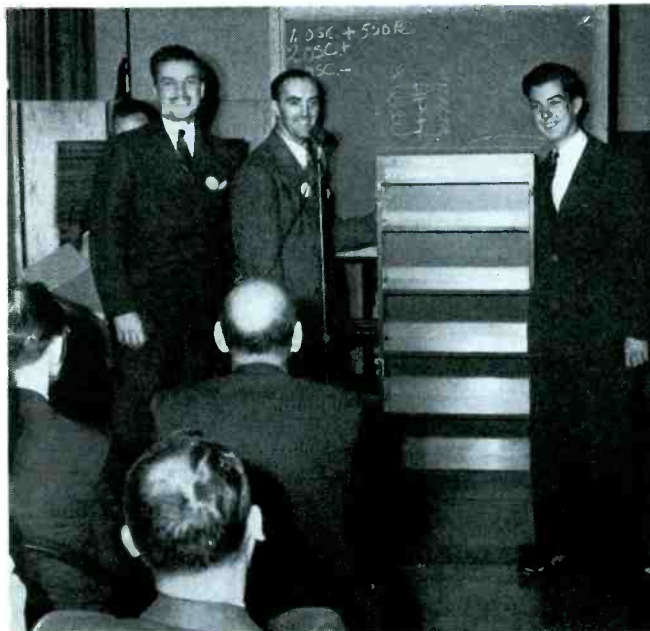

that is proving very satisfactory. Through the cooperation of the local radio station, WDAN, and newspaper, the Commercial News, we appealed to the public for discarded radios to be donated to charity. These radios are to be repaired by the Service Men in our Chapter and then distributed to the worthy needy families in this community at Christmas time. The public is responding to our plan and the radio sets are pouring in as fast as we can repair them. A few nights each week, several of the members meet at our club rooms and repair radios and discuss service problems.

*Edward C. Welch, Secy.*

### Long Island, RSA

George C. Connor, Hygrade Sylvania commercial engineer, enumerated and clarified the "Changes in Radio and Their Ramifications to the Service Man" at the December meeting of the Long Island Chapter of the Radio Servicemen of America, at Hempstead, L. I. The meeting was sponsored by the Dale Radio Corp., New

York distributors for Sylvania, and was presided over by Otto Furman, past president of the group and instructor of radio communications at the Brooklyn Technical High School.

Mr. Connor gave a report on and explanation of technical subjects which were studied and discussed at the IRE fall meeting held at Rochester, N. Y., recently. Speaking on frequency modulation, Mr. Connor declared that it is the hope of the protagonists of this new form of broadcasting and receiving to place in the homes of the American Public, sets that reproduce the full range of musical notes with a complete absence of noise, a feat not possible with amplitude modulation.

At the moment there is a conflict of f-m broadcasting standards, one being based on a horizontally polarized transmission, the other on vertical polarization. This diversity will probably be standardized by the RMA shortly.

The most annoying problem with f-m


*(Continued on page 31)*



With the arrival of Herb Clough, the Board of Directors of Radio Parts Manufacturers National Trade Show, Inc., is ready to begin preparation of plans for the 1941 Show to be held at the Stevens Hotel, in Chicago, June 10 to 13, inclusive. Left to right are H. E. Osmun (Centralab), vice-president; Herbert W. Clough (Belden Manufacturing Company), new director; Ken Hathaway, managing director; K. C. Prince, legal counsel; Arthur A. Berard (Ward Leonard Electric Company), president; and Jerome J. Kahn (Standard Transformer Corporation), secretary-treasurer, seated.



# Presenting the 1941

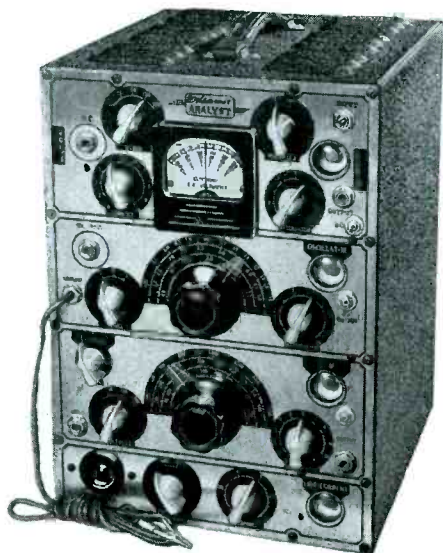

## Meissner ANALYST

Incorporating a New, Direct-Reading  
ELECTRONIC VOLTMETER

Save Time—Save Money—Handle service jobs faster with the assurance that they will "stay sold"! Almost Magical in its uncanny ability to ferret out obscure faults and lay them open for your inspection, the New Meissner ANALYST handles the receivers of yesterday, today and tomorrow—with equal efficiency and facility. Entirely fundamental in its testing procedure, it is one piece of equipment that will never become obsolete!

The New Meissner ANALYST locates faults by the "Signal Tracing" method—proven to be the fastest and most reliable. Five separate and distinct "channels" provide as many different functions, each in its own panel division with all controls accurately calibrated. Furnished with tubes and instructions, complete—ready to go to work!

No. 9-1040 New ANALYST **\$87.50**  
Complete with Tubes, Net . . .

Limited Quantity of 1940 Models  
Available at Reduced Price!

The same ANALYST that sold in kit form at \$100 list—now offered completely wired, with full set of 13 tubes—ready to operate! Similar to the New ANALYST described above except has electron-ray indicator instead of meter for DC measurements.

No. 9-1025 Net Price . . . **\$69.50**

Write for Free 1941 General Catalog

Dept. S-12



## PRECISION 854 MULTIMETER

(Continued from page 28)

charge of the condenser will be indicated on the d-c meter.

a) In the case of a good condenser, the needle pointer will recede to the zero voltage mark.

b) If the meter pointer remains above the zero mark, then this indicates that the condenser has abnormal leakage.

c) If the meter pointer remains at the indicated value of the voltage measurement obtained initially, then the condenser is shorted.

d) If no meter deflection is obtained, then this indicates that the condenser is open or that the capacity is too low in value to indicate an instantaneously noticeable meter deflection when charged.

Caution:—After this test is completed, always first disconnect the negative test lead from circuit before turning off power supply to prevent slamming of needle pointer due to discharge of condenser under test.

## Displays . . .

Emerson Radio & Phonograph Corp., 111 Eighth Ave., New York City, has released a full color display card on Emerson Radio tubes. Illustrates glass, bantam and metal types.

Something dramatic has been provided by RCA for the display of the Jr. VoltOhmyst. The display enables the prospective customer to sell himself by providing a demonstration of the instrument's principal features. It consists of a VoltOhmyst, a rectifier tube and transformer, and simple circuits for providing tests of both a-c and d-c voltages, and low and high value resistances. With three leads from the VoltOhmyst the customer can perform many tests normally required in radio servicing. Printed in yellow, red, blue and black. RCA Mfg. Co., Inc., Camden, N. J.

## Personnel . . .

Vic Mucher, in charge of sales for Clarostat Mfg. Co., Inc., Brooklyn, N. Y., became the proud daddy of a daughter (Diana Marie) December 1. Mrs. Mucher and daughter doing well, thank you!

Alfred A. Ghirardi, author, took a quick trip to visit service shops and radio manufacturers in Buffalo, Detroit and Chicago to get last minute data for a new book, about to be published.

Claude E. Murray, veteran of 30 years' service with the Willard Storage Battery Co., Cleveland, Ohio, has been appointed vice president and general manager of that company. Mr. Murray had been vice president and general manager of the company's Canadian affiliate.

# RADIART

LOOKEE! - ALL 5 SECTIONS COLLAPSE TO ONLY 2 INCHES ABOVE THE BRACKET!

**NEW**

"ALL ANGLE" ALL PURPOSE AERIALS  
FIT ALL CARS ON FENDER, COWL OR UNDERHOOD

SURE - IT COLLAPSES BELOW THE LINE OF VISION!

A-5, 5 Section Type, collapses entirely below line of vision.  
EASIEST INSTALLATION  
MINIMUM STOCK  
(only 2 types for all needs)  
WATERPROOF Shielded LEAD  
FITS ANY BODY ANGLE

Write for Bulletin 197

THE RADIART CORPORATION  
Cleveland, Ohio

## FREE! NEW 1941 PROFIT GUIDE

### Everything in RADIO!

Complete Selections . . . Guaranteed Quality

#### Replacement Parts

Everything you need in exact duplicate or universal replacement or repair parts. Tubes, condensers, resistors, transformers, hardware, tools, etc. Leading brands.

#### Latest Radio Sets

A model for every purse and purpose. Auto Sets, Midgets, Battery Portables, Table Models, Consoles, Phono-Radio and recorder combinations—for operation on AC or DC.

#### Public Address Equipment

A complete line of amplifiers, microphones, baffles, recording equipment and accessories for every type of installation—permanent, portable and mobile, from 5 to 100 watts.

#### Newest Electric Appliances

Extra profits for you! Standard Brand Electric Irons, Grills, Toasters, Perculators, Wafters, Irons, Vacuum Cleaners, Clocks, Mixers and many others, all at lowest prices.

**YOU SAVE MONEY AT RADOLEK**

**MAIL THIS COUPON TODAY**

The RADOLEK CO.  
601 W. Randolph St., Chicago, Dept. B-49  
Send the New 1941 Radio Profit Guide FREE.

Name \_\_\_\_\_  
Address \_\_\_\_\_ Dealer? \_\_\_\_\_  
Experimenter? \_\_\_\_\_ Serviceman? \_\_\_\_\_ Amateur? \_\_\_\_\_



## BOOK REVIEWS

(Continued from page 27)

**MATHEMATICS APPLIED TO ELECTRICAL ENGINEERING**, by A. G. Warren, published by D. Van Nostrand Co., Inc., 250 Fourth Ave., New York City, 1940. 384 pages, price \$4.50.

This book is written particularly for the technician who is well grounded in calculus and differential equations. It is intended to present labor saving solutions to analytical problems involving a mathematical approach.

The author begins his subject from the engineer's viewpoint rather than from that of the mathematician. Solutions by a combination of graphical and numerical computations are indicated in numerous instances. While not ignoring the beauty of many classical mathematical methods, he centers his effort on the solution of the practical problems involved.

The first few chapters in the book are devoted to such items as real and complex numbers, differentiation and integration as well as to methods and results of differentiation and integration. The body of the text is given over to the solution of representative electrical problems. R. D. R.

**PRINCIPLES AND PRACTICE OF RADIO SERVICING**, by H. J. Hicks, published by McGraw-Hill Book Co., 330 W. 42nd St., New York City, 1939, 305 pages, price \$3.00.

This book has been written especially as a text for the radio service man. Fundamental principles are explained in an elementary style so that the reader will understand the why as well as the how of servicing and operation.

The type of material and the method of its presentation would make this book an excellent text for a course in radio servicing, if the author had taken more pains to be accurate in every case. As it stands, however, because technical errors do exist the student could not always rely upon the material.

The first two chapters are devoted to the fundamentals of electricity and magnetism as well as to the principles of radio. Such items as the electromagnetic wave, the Kennelly-Heaviside layer, fading, etc., are treated in some detail. The chapter on antennas and static reduction is well written. In addition to a discussion and explanation of the functional portions of radio receivers, some 40 pages are devoted to servicing. T. H.

## ASSOCIATIONS

(Continued from page 29)

sets, Mr. Connor stated, is oscillator drift. To counteract that difficulty, it is necessary to be vigilant of three things: 1) stable oscillator design; 2) a wide i-f band pass; 3) linear frequency detector. To date not enough gain nor sufficient oscillator stability has been achieved resulting in inadequate reception. Designing the oscillator circuit to work on a lower frequency automatically provides an improvement in frequency stability. This has been accomplished with the double super-heterodyne circuit which has been used only on commercial equipment up to the present, but is now being made available for household sets.

Another circuit suggestion to overcome oscillator difficulty, Mr. Connor stated, is one suggested by James Day, assistant to Major Edwin Armstrong. It comprises a double oscillator one of which is a crystal oscillator. This set has lower drift and more gain.

# SERVICING by SIGNAL SUBSTITUTION

Copyright 1940 by Precision Apparatus Co. Brooklyn, New York

Question: **PERFORMANCE?** . . . Answer: **YES!**  
 Question: **COSTLY?** . . . . . Answer: **NO!**

*Because* 1. "S-S-S" employs **ONLY BASIC TEST EQUIPMENT . . . NO EXTRAS!**  
 2. "S-S-S" is **UNIVERSAL . . . non-obsolete**  
 3. "S-S-S" requires **NOTHING COMPLEX TO LEARN**

Modern servicing (A.M. and F.M.) requires only 3 basic instruments: The Signal Generator (such as PRECISION Series E-200); The Dynamic Mutual Conductance Type Tube Tester and a 20,000 ohms per volt Multi-Range Set Tester (such as PRECISION combination Series 954).



★ **Series 954** Combination Dynamic Mutual Conductance Type Tube Tester and 20,000 ohms per VOLT Multi-Range AC-DC Set Tester

A complete service laboratory answering the demand for a compact unit with every facility for accurate, reliable solutions of all tube test and measurement problems (A.M., F.M. and Television). A single master rotary range selector permits simple, rapid measurements in troublesome stages, quickly localized through "Servicing by Signal Substitution."  
 954 MCP—in open face portable metal case (illustrated for Series E-200). Complete with battery and extra high voltage test leads **\$61.95**  
 954 P—(illustrated above) Hardwood case. Complete **\$65.95**  
 954 PM—Standard panel mount. Complete **\$65.95**



★ **Series E-200** Modern Laboratory Type Multi-Band Signal Generator

Not only an unsurpassed Signal Generator for purposes of receiver alignment, but SPECIFICALLY DESIGNED as the key to "Servicing by Signal Substitution" . . . Nevertheless priced within the easy reach of every progressive radio service engineer.

E-200—(illustrated)—in heavy gauge metal cabinet, complete with tubes, coaxial output cable and FREE copy of "Servicing by Signal Substitution" **\$35.95**  
 E-200PM—in standard panel mount, complete **\$39.95**

**FREE** A 120 page text book "Servicing by Signal Substitution" describes this simplified approach to receiver adjustment problems. Furnished FREE with every PRECISION Series E-200. Also available at leading distributors or directly from factory at 35c — Write for it today!

More than 40 models in the New PRECISION 1941 LINE . . . 21 Dynamic Mutual Conductance Type Tube Tester and Set Tester models ranging in price from as low as \$29.95 . . . 16 Multi-Range Tester models from as low as \$14.95 . . . Signal Generators from \$35.95 . . . See them at your local distributor . . .

Ask or write for the PRECISION TEST EQUIPMENT 1941 CATALOG.

## PRECISION TEST EQUIPMENT

Standard of Accuracy **SEE THEM AT YOUR JOBBER**

PRECISION APPARATUS COMPANY • 647 KENT AVENUE • BROOKLYN, N. Y.  
 Export Division: 458 Broadway, New York City, U. S. A. • Cable Address: Morhanex

Other subjects covered were; tuning systems that avoid microphonism and reduce frequency drift; double limiters for i-f receivers and audio feedback circuits.

Representatives attending the meeting from the Dale Radio Co. were sales manager Rene Jacobs and Charles Stern, Arthur Smalkin, Dean Ellner, Robert Tremaine, Norman Leeb, of the sales and service department. Henry C. L. Johnson

Rochester, N. Y., RTG

The RTG of Rochester held their second Annual Info.-Meet on Nov. 10, in conjunction with the Fall Meeting of the IRE and RMA engineers. In spite of poor mailing of notices, for which we extend our sincere apologies, the meeting was a success in every way.

Mr. Dorman D. Israel of the Emerson Co., Mr. Walter Jones of Sylvania, and Mr. A. C. W. Saunders of the New England RTG gave interesting, educational and worth while talks. The attendance was very good, many came from distant points.

We want to thank all who attended and promise a bigger and better meet next year. A. H. Marsh, Secy.-Treas.

New Bedford, Mass., RTG

The Whaling City Chapter of the RTG held their regular meeting, Nov. 20, in Labor Temple.

After the regular business was completed, the secretary told of the Rochester Info-Meet and gave a review of the technical program for the meeting.

James L. Shepley, Secy.

# Bulletins and Catalogs...

You cannot keep up to date in a rapidly advancing industry without reading the latest catalogs and bulletins published by the manufacturers who make up that industry. Radio is no exception. Sit down now and write for the literature listed below. It is up to the very minute and may be obtained without cost directly from the respective manufacturers.

• • • • A brief folder entitled "Pick-up Facts" contains 28 interesting statements concerning phonograph pickups, as gathered from the various radio publications. Available from Audak Co., 500 Fifth Ave., New York City.

• • • • The Cornell-Dubilier 1941 Radio Capacitor Bulletin No. 185A lists mica, paper, wet and dry electrolytics, Dykanol and other types of condensers for use in radio receivers. Ratings, sizes, dimensional drawings and prices are included for each type. Copies from Cornell-Dubilier Electric Corp., South Plainfield, N. J.

• • • • Everyone interested in the purchase of a slide rule should obtain a copy of "How to Choose a Slide Rule," by Don Herold. This 24-page booklet is a humorous publication describing the various Keuffel & Esser rules and the advantages of each. Copies directly from Keuffel & Esser Co., Hoboken, N. J.

• • • • Complete information on phototubes and their applications can be found in a 16-page booklet from RCA Man-

ufacturing Co., Inc., Camden, N. J. The phototube's usefulness in various types of instruments is discussed. Circuits, characteristic curves, phototube theory and descriptive material is also contained in the publication.

• • • • Entitled "Radio's Moving Day," a booklet from RCA Manufacturing Co., Inc., Camden, N. J., offers suggestions to Service Men to take full advantage of the opportunity to get into 10 million homes to reset automatic push-button receiver controls—and to sell such other things as complete check-up, alignment, new tubes, antennae, portables and other accessories.

• • • • A 200-page general catalog has been issued by the Radio Service Laboratory of New Hampshire, 1191 Elm St., Manchester, N. H. The book contains listings on radio parts, sound equipment, test apparatus, etc.

• • • • An 8-page bulletin on "Radio Interference Elimination for Public Utilities" is available to readers of SERVICE from Sprague Products Co., North Adams, Mass. Includes description of causes and cures of radio interference on power transmission and

distribution lines as developed by Sprague engineers.

• • • • The 1941 edition of the Sprague Manual of Radio Interference Elimination has been issued by Sprague Products Co., North Adams, Mass. It is available directly from Sprague for 25c. Covers interference elimination for modern requirements, including data covering fluorescent lighting interference.

• • • • The Fifth Edition of the Stancor Hamannual has been announced by the Standard Transformer Corp., 1500 N. Halsted St., Chicago, Ill. The 48-page, 2-color book describes 12 transmitters and 6 amplifiers in complete detail. Circuits and layouts are given in each case. In addition a line of power supply kits is also offered. Copies from Standard for 15c.

• • • • Ward Products Corp., Cleveland, Ohio, will supply upon request an antenna guide (Form No. WA107) for installations of 1941 auto antennae and complete information on the Ward Flex-Angle antenna Model E3-68 which is said to fit all 1941 cars.

**MAKE MORE MONEY Quicker**

Send for new catalog of low-priced, high-quality RCP Test Equipment. Now you can have a handsomely equipped test laboratory for what you would ordinarily pay for just one or two instruments. Why tie up working capital needlessly? RCP instruments are designed to give you better equipment at less cost—just as RCP advanced engineering features give you bigger profit by making service work easier, quicker.

Write Today for RCP Free Catalog No. 124

**RCP dependable TEST instruments**

**RADIO CITY PRODUCTS COMPANY, INC.**  
88 PARK PLACE • NEW YORK.



**WHEN YOU CHANGE YOUR ADDRESS**

Be sure to notify the Subscription Department of SERVICE at 19 E. Forty-seventh St., New York City, giving the old as well as the new address, and do this at least four weeks in advance. The Post Office Department does not forward magazines unless you pay additional postage, and we cannot duplicate copies mailed to the old address. We ask your cooperation.

**KEN-RAD**

**DEPENDABLE RADIO TUBES**

Dealers and servicemen will find Ken-Rad Radio Tubes their best choice because of liberal sales and adjustment policies, plus tubes of known quality.

**KEN-RAD TUBE & LAMP CORPORATION**  
Owensboro, Kentucky



**SAVE \$1.00!!!**

- The Group Subscription Plan for Service enables a group of service men, dealers or jobbers to subscribe at one-half the usual yearly rate.
- The regular individual rate is \$2.00 a year. In groups of 4 or more, the subscription rate is \$1.00 a year. (In foreign countries, \$2.00.)
- Each subscriber should print his name and address clearly and state his occupation—whether a dealer, jobber, independent service man, service organization, etc.

**Remember this Group Plan when Your Subscription Expires**



# Sound News...

Additional information on the products described below may be obtained, without obligation, directly from the respective manufacturers.

Astatic's Model UT49 crystal microphone, shown at right, is a high impedance type with an output of -48 db below 1 volt/bar. The frequency response is rising above 500 to a maximum at 3,500 cps. A tilting head is provided.



Astatic's Model FP18 and FP38 crystal pickups are of the low pressure type with rounded jewel point. Astatic Microphone Laboratory, Inc., Youngstown, Ohio.

## ROSTRUM SOUND SYSTEM

The Erwood Rostrum portable p-a system has amplifier, speaker and microphone contained in a single case. Removal of the case cover gives access to a reading platform which is illuminated by a miniature lamp. Additional details may be obtained directly from Erwood Sound Equipment Co., 223 W. Erie St., Chicago.

## RCA RECORDER

The RCA Type 73A recorder will cut at 33 $\frac{1}{3}$  or 78 rpm from either the outside-in, or the inside-out, without changing lead screws or gears, at 96, 112, 120, 136 or 154 grooves per inch.



The recording head has a frequency response of from 30 to 10,000 cycles. The turntable is rim-driven by two motors operating simultaneously. A microscope is providing for observing the grooves as they are cut. A small shielded lamp is mounted on the adjustable microscope supporting arm to provide illumination directly under the microscope's lens. General illumination for the unit is provided by a lamp supported on a long flexible goose neck.

The 73A also incorporates an adjustable suction nozzle to draw away shavings from the cutting head. A suction pump and coupling hose are available on separate order.


## SHURE MICROPHONE

Another Stratoliner, the Model 708SH has been announced by Shure Brothers, 225 W. Huron St., Chicago. This model is designed for phone and speech applications. Output level, minus 29.7 db below 1-volt-per-bar; built in r-f filter; genuine Bimorph crystal; die cast case.
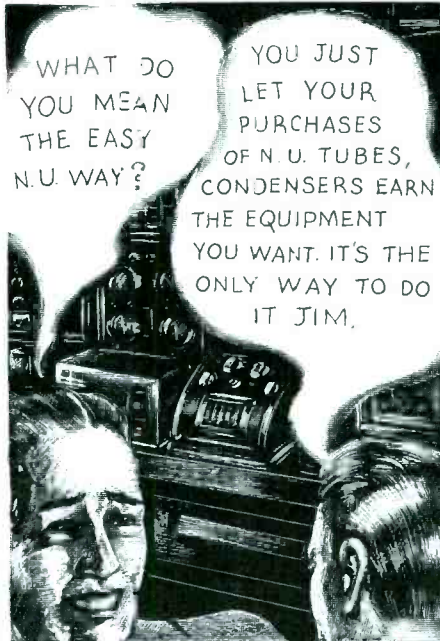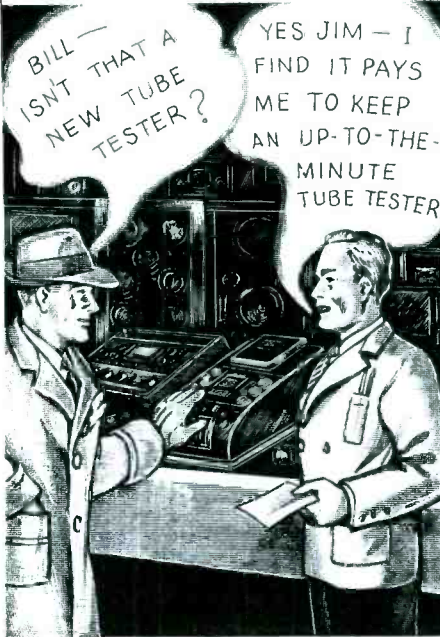
## The Best Equipped Shop in Town "GETS THE BUSINESS"



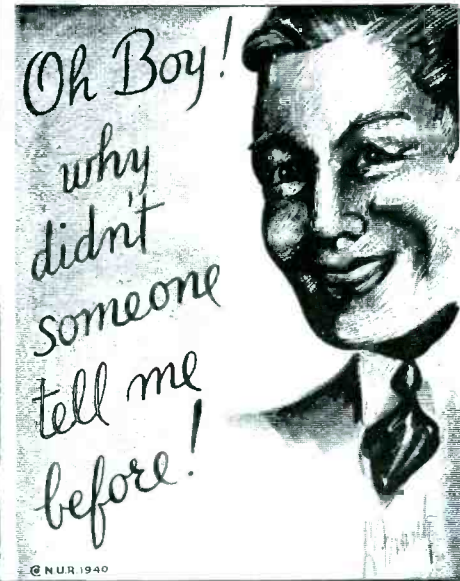AFTER GETTING HIS DEAL FIXED UP WITH THE N. U. DISTRIBUTOR,



**NATIONAL UNION RADIO Corporation**  
57 STATE STREET, NEWARK, N. J.


## TURNER ELECTRONIC PICKUP

The Turner Co., Cedar Rapids, Iowa, is marketing a magnetic unit for electronic pickup from stringed instruments. The unit may be clamped to violins, banjos, guitars, etc.
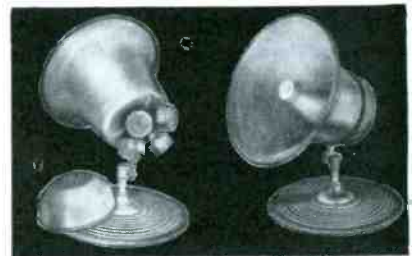
## UNIVERSITY BULL SPEAKER

University's Model 4XR reflex exponential horn type speaker is designed for 100-watts of continuous audio power. The reflex projector is acoustically equivalent to a 6-foot straight exponential horn and is made non-resonant by the use of a rubber tired rim on the edges of both the large and small bells. The driver units for this speaker consist of four University standard 25-watt units. These units are connected through a balanced multiple

acoustic drive line to the horn itself. The speaker is waterproofed for outdoor use and is supplied with a universal mounting



bracket and driver unit cover. Additional information from University Laboratories, 195 Chrystie St., New York City.



**Old Man Centralab**  
reminds you to always "specify  
Centralab" when ordering parts.



**FIXED  
RESISTORS**



**CERAMIC  
CAPACITORS**



**VOLUME  
CONTROLS**



**WAVE CHANGE  
SWITCHES**



**TOGGLE  
SWITCHES**

**Centralab**

DIVISION OF GLOBE UNION INC.  
MILWAUKEE, WIS.

## New Test Equipment

Additional information and prices  
of the equipment described below  
may be obtained, without obligation,  
from the respective manufacturers.

### HICKOK OSCILLOGRAPH

Hickok Model RF05 is designed for  
visual analysis for frequency modulated,  
amplitude modulated and television ser-  
vice work. Has self contained wide-band  
f-m oscillator for f-m and television ser-



vicing and a narrow band f-m oscillator  
for a-m receivers. Also demodulator, video  
amplifiers, signal tracer and visual a-c  
vtvm from 0.2 to 1,000 volts, it is said.  
Hickok Electrical Instrument Co., 10308  
DuPont Ave., Cleveland, Ohio.



Sprague's Model IL2 interference locator  
is a sensitive device for the location and  
isolation of radio interference. It oper-  
ates either from self-contained batteries  
or from a-c or d-c power lines. It is  
equipped with a directional loop which  
is mounted on the cabinet top when in  
use, or carried within a cover recess  
when transported. Sprague Products Co.,  
North Adams, Mass.

### GENERAL PEN-OSCIL-LITE

General Test Equipment Co., 213 Crosby  
Ave., Kenmore, N. Y., have introduced  
their Pen-Oscil-Lite, a multivibrator type  
of oscillator self-contained and fully pow-  
ered in a small pen-lite type case. The unit  
consists of a high frequency buzzer and  
battery supply and will generate useable  
oscillations of the impact excitation type  
down to the very short waves. Additional  
information may be obtained directly from  
General.

## Mr. Radio Serviceman:

# RSA MEANS BUSINESS!

New business promotion plans and new member-helps spell  
increased profits for RSA members at the start of the new  
season. Watch for the RSA Replacement Parts Guide—New  
Broadcast Promotions—New Member Helps! Don't be the last  
man in your neighborhood to join RSA. Send the coupon Today!

MAIL THIS COUPON NOW!

RADIO SERVICEMEN OF AMERICA, INC.  
304 S. Dearborn St., Chicago, Ill.

I am interested in RSA Membership. Tell me about it.

Name .....

Address .....

City..... State.....

S-12-40

Let's Grow Together  
in 1940!



**RADIO SERVICEMEN  
OF AMERICA, Inc.**

*Reliable Service Assured*  
JOE MARTY, JR., EXECUTIVE SECRETARY  
304 S. DEARBORN STREET, CHICAGO, U.S.A.




## New Products . .
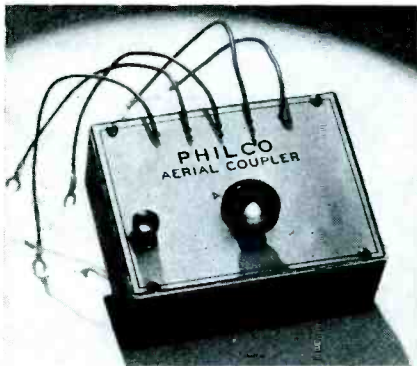
### TURNER TO MAKE VIBRATORS

The Turner Co. announces that it is now licensed to manufacture vibrators for car and other portable radios under James Patents No. 1,940,496 and No. 2,113,726 and other patents pending.

Turner will be in production and ready to make delivery Jan. 1, 1941.



Coupling a signal generator to a loop operated receiver for alignment purposes is usually a complicated and often a makeshift arrangement. In an effort to simplify this requirement, Philco has introduced a special aerial coupler shown above. Alignment will be more accurate through the use of this device, it is said. Philco Corp., Allegheny and A Streets, Philadelphia, Pa.




Electro Products Labs., 549 W. Randolph Street, Chicago, are marketing a line of power supplies for the operation of 1.4- and 2-volt receivers from the power lines. Several types (see illustration above and below) are available to meet practically every current drain, it is said. The output voltages are connected to numerous socket arrangements to accommodate the many plugs used on battery receivers in the past few years.



Actual size 4 1/2" by 9 3/4" —  
272 fast-filled pages
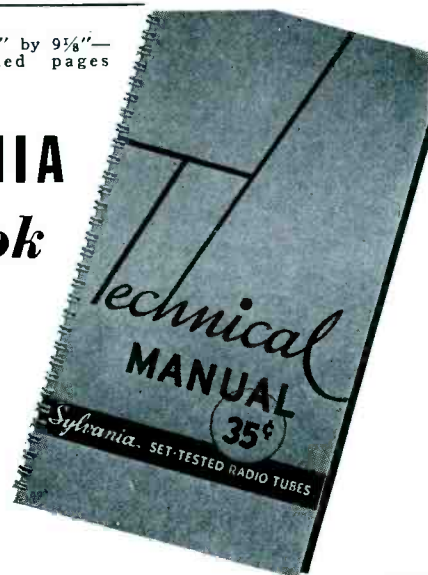
## GET YOUR COPY OF THE BIG SYLVANIA Tube Fact Book

272 Pages of Vital  
Tube Information  
Including  
Operating Conditions  
Tube Characteristics &  
Circuit Applications on  
374 Tube Types



Hygrade Sylvania Corp.  
Emporium, Pa. 8120

Enclosed is 35c. Please send me a copy of the latest edition of the Sylvania Technical Manual.

USE THIS COUPON TODAY


**SYLVANIA**  
Set-Tested Radio Tubes

Name .....

Address .....


City..... State.....

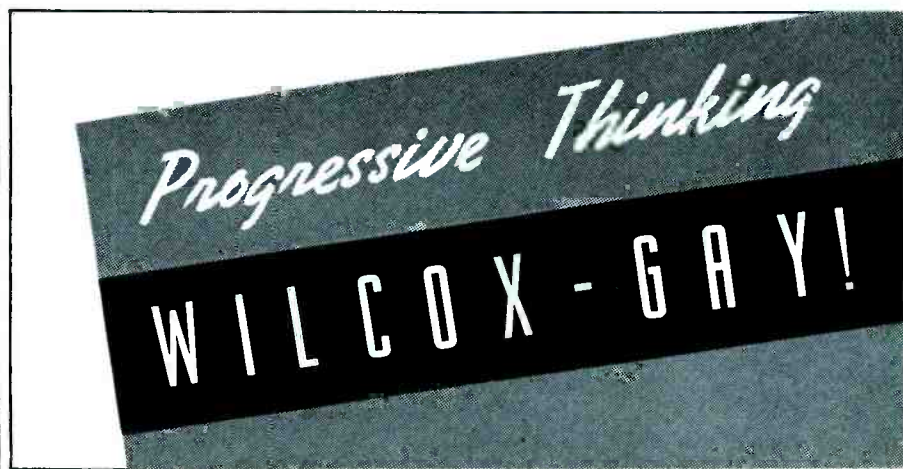Serviceman     Experimenter  
 Dealer         Amateur


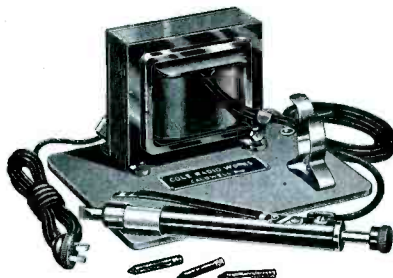
### SPRAGUE PLUG-IN FILTER

Sprague Products Co., North Adams, Mass., have designed the LF2 plug-in radio interference filter, a multiple section inductance and capacity filter for use at the power outlet to which an interfering electrical device is connected. The LF2 can



A. B. Cole, Caldwell, N. J., has introduced a quick soldering device for use on the service bench. It employs a special transformer and is said to concentrate the heat at the point of soldering. Several types of tips are supplied.



be employed with electric shavers, hair dryers, erasing machines and similar electrical equipment drawing up to 1/2 ampere.

# Simplest

## WAY TO REPLACE BALLASTS

- 4 STANDARD TYPES of Amperite Regulators replace over 200 types of AC-DC Ballast Tubes now in use.
- Not to be confused with ordinary dropping resistors. Amperite actually regulates.
- Amperite Regulators are equipped with a patented Automatic Starting Resistor which prevents initial surge and saves pilot lights.
- Amperite AC-DC Regulators; List \$1.00. Amperite Replacements for 2V Battery Set ballasts . . . . . List \$1.25

WRITE FOR REPLACEMENT CHART "S"  
**AMPERITE Co.** 561 Broadway, N. Y. C.

# AMPERITE

## SOUND ENGINEERS! Here's P.A. that Sells!

You can go to town with Sound when the equipment you feature is Lafayette. Here's quality P.A. for every purpose . . . priced for every purse. Backed by twenty years of Sound engineering, the low-cost Lafayette line for 1941 is the year's outstanding money-maker. With new, advanced features not found in any other P.A. equipment, modern streamlining and remarkable tone fidelity. Lafayette's the P.A. buy for best results—in performance and in profit! Whether you use Sound equipment or sell it, it will pay you to investigate all that Lafayette offers. Send for full details.

**LAFAYETTE'S FREE CATALOG**  
 will help you select the sound equipment best suited to your needs, give you an idea of the completeness of this line and Lafayette money-saving prices. Mail the coupon for your FREE copy today.

**Lafayette SOUND SYSTEMS**  
 NEW YORK, N. Y. 100 Sixth Ave.  
 CHICAGO, ILL. 901 W. Jackson Blvd.  
 ATLANTA, GA. 285 Peachtree Street  
 BOSTON, MASS. BRONX, N. Y.  
 NEWARK, N. J. JAMAICA, L. I.

**LAFAYETTE RADIO CORP.**  
 Dept. 5M—100 Sixth Ave., New York, N. Y.  
 or 901 W. Jackson Blvd., Chicago, Ill.  
 Rush FREE Catalog.

NAME \_\_\_\_\_  
 ADDRESS \_\_\_\_\_  
 CITY \_\_\_\_\_ STATE \_\_\_\_\_

## Index to Advertisers

	Page
A	
Aerovox Corp. . . . .	26
Amperite Co. . . . .	36
B	
Brach Mfg. Co., L. S. . . . .	24
C	
Centralab . . . . .	34
H	
Hygrade Sylvania Corp. . . . .	35
I	
International Resistance Co. . . . .	4
J	
Jensen Radio Mfg. Co. . . . .	1
K	
Ken-Rad Tube & Lamp Corp. . . . .	32
L	
Lafayette Radio Corp. . . . .	36
M	
Mallory & Co., P. R. . . . . Inside Front Cover	
Meissner Mfg. Co. . . . .	30
Montgomery Ward & Co. . . . .	24
N	
National Union Radio Corp. . . . .	33
O	
Oxford-Tartak Radio Corp. . . . .	36
P	
Precision Apparatus Co. . . . .	31
R	
RCA Mfg. Co., Inc. . . . . 25. Back Cover	
Radiart Corp., The . . . . .	30
Radio Amateur Call Book, Inc. . . . .	36
Radio City Products Co., Inc. . . . .	32
Radio Servicemen of America, Inc. . . . .	34
Radolek Co., The . . . . .	30
Readrite Meter Works . . . . .	26
Rider Publisher, Inc., John F. . . . .	21
S	
Solar Mfg. Corp. . . . . Inside Back Cover	
T	
Triplett Elec. Inst. Co., The . . . . .	24
U	
United Transformer Corp. . . . .	3
Utah Radio Products Co. . . . .	27
W	
Wilcox-Gay Corp. . . . .	35
Y	
Yaxley Mfg. Division . . . . . Second Cover	

## MORE PROFIT for Servicemen!


# Oxford

OXFORD replacement speakers provide a quick way to increased profits for radio-service dealers.

It is more economical and profitable to replace a defective speaker than to repair it.

The profit a service-dealer can make on any job depends upon the speed with which it can be completed. Trying to repair defective speakers when a new OXFORD costs so little is an expensive waste of time and effort. Thousands of service-dealers are convinced that it is sound business to replace defective speakers, because it puts extra dollars in their pockets and guarantees a satisfactory job.

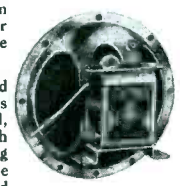
Your jobber stocks an OXFORD speaker for every application. See him today.



Model 5V is supplied either with or less transformer as desired, and is equipped with standard mounting bracket. Is available in all popular field values from 450 ohms to 2750; also 6 volt.

MODEL 5V LIST \$2.00

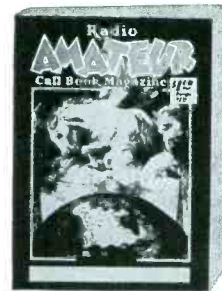**OXFORD-TARTAK** RADIO CORPORATION  
 915 W. VAN BUREN ST. • CHICAGO, U. S. A.



## SERVICEMEN

who are  
**RADIO AMATEURS**  
 buy a fresh copy today of the  
**RADIO AMATEUR CALL BOOK**

The CALLBOOK is the only publication that lists all licensed radio amateurs in the United States and foreign countries.

Complete . . . Accurate . . . Up-to-Date  
 Issued Quarterly  
 MARCH . . . JUNE . . . SEPTEMBER  
 and DECEMBER

Annual subscription \$4.00  
 Single copies \$1.25

Buy your copy now from your radio jobber or direct from:

**Radio Amateur Call Book, Inc.**  
 608 S. Dearborn St., Chicago, Ill., U. S. A.



Quality above all **SOLAR**

Wax-molded

# Sealdtite

**TUBULAR PAPER  
CAPACITORS**



SOLAR has perfected the tubular type of capacitor—now it is reliable—

Molded in hard wax — no moisture can enter—much longer life—

Buy in the blue box, 10 of a rating — or in the red box, assorted — at your jobber's — SEALED FOR SAFETY.

**SOLAR MFG. CORP. . . . Bayonne, New Jersey**



# GET MORE DONE IN '41!

## Two Shortcuts to Successful Servicing

JANUARY 1941						
			1	2	3	4
5	6	7	8	9	10	11
			16	17	18	
			23	24	25	
			30	31		

### RCA RIDER CHANALYST

The Original Signal-Tracer \$107<sup>50</sup>



NEXT year at this time . . . where will your business stand? That depends on how much business you DO . . . and THAT depends on how much time you can spend going out AFTER business!

That's why the country's top servicemen—the men who know servicing best—will tell you: "Once you've tried signal tracing with the Chanalyst, you'll never go back to slow, old methods of set-fixing! It's easier. Faster. It gives you more free time to build business because it takes less time to fix sets!"

Greatest advance in servicing since servicing began, the RCA Rider Chanalyst is the original signal-tracing instrument—still far and away the best! Learn the facts for yourself—ask your RCA Distributor for on-the-circuit proof of the Chanalyst's superiority . . . see it in action on the RCA Dynamic Demonstrator.

There are more than 4,000 owners of RCA Rider Chanalysts—ask the man who uses one!



### RCA JUNIOR VOLTOHMYST

Electronic Volt-Ohmmeter \$34<sup>95</sup>



SERVICING radios at best takes brains . . . and aptitude . . . and hard work! But why make the job harder by working with inadequate equipment? This great new d-c Electronic push-pull volt-ohmmeter costs only \$34.95 complete—and look how much you get:

11,000,000 ohms constant input resistance on d-c volts—you can check oscillator-voltages at the grid of the tube with the circuit functioning, the signal pres-

ent! And even on extreme d-c voltage overloads, the Junior VoltOhmyst has maximum meter protection! Sensitivity is as high as 3,666,666 ohms per volt—6 d-c ranges to 1,000 volts—you can read AVC, AFC, and FM Discriminator voltages accurately—measure bias-cell voltages without harmful drain. As an ohmmeter, the Junior VoltOhmyst reads from 0.1 ohm to 1,000 megohms . . . without leads to short or zero-point resetting. You can check insulation or condenser leakages accurately, easily, quickly! For extra convenience, there's an a-c Voltmeter too—rectifier-type 1,000 ohms-per-volt, that reads to 1,000 volts a-c. See it at your RCA Distributor's TODAY!



# Test Equipment

RCA MANUFACTURING COMPANY, INC., CAMDEN, N. J.  
A SERVICE OF THE RADIO CORPORATION OF AMERICA

