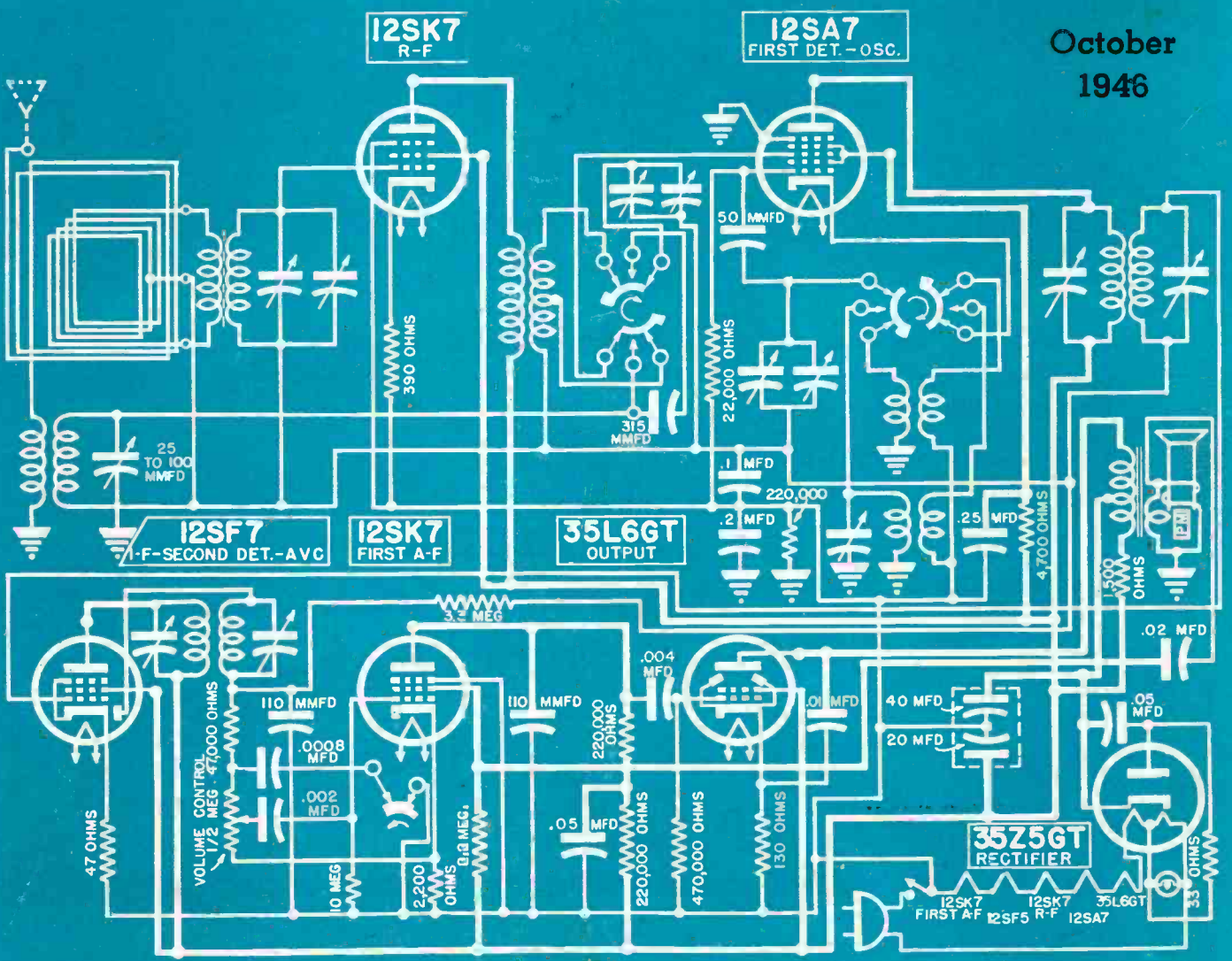


SERVICE

October
1946



Balanced loop type receiver with loop tuned indirectly through close-coupled iron-core transformer.

[See page 26.]

Now They Call Me Doc

Whenever an ailing set needs a "physical", your local prospect will go hunting for a dependable serviceman. That's why, in addition to other valuable sales aids, C-D has prepared these prestige-building decals to direct customers your way. Mount a decal on your door or window where everyone can see that you are the reliable radio servicing specialist of your community. It's free!



RELIABLE RADIO SERVICING

WE USE ONLY GENUINE

CORNELL  **DUBILIER**
CAPACITORS

QUALITY LINE SINCE 1910

WORLD'S LARGEST MANUFACTURER OF CAPACITORS

All these sales aids help to make your shop headquarters for radio service in your community.



- Newspaper Mats
- Match Books
- Counter Cards
- Stationery
- Decals
- Shipping Labels
- Postcards
- "C-D Capacitor"
- Catalogs

let yourself grow! See your local C-D jobber today and order these powerful sales builders. Most of them are free. Get on the "C-D Capacitor" mailing list now, write direct to: Cornell-Dubilier Electric Corp., South Plainfield, N. J. Other plants at New Bedford, Worcester and Brookline, Mass., and Providence, R. I.



MICA • DYKANOL
PAPER • ELECTROLYTIC

CORNELL-DUBILIER
WORLD'S LARGEST MANUFACTURER OF
CAPACITORS

KEN-RAD

RADIO TUBES

Sell Ken-Rad tubes
for top profits
Tomorrow
as well as today



NO "pig in a poke", the Ken-Rad dealership, but a SOLID tube deal with SOLID rewards now and as long as you are a dealer. Ken-Rad builds fine tubes, and — backed by General Electric's great facilities and resources — Ken-Rad tubes will stay high in quality, advanced in design.

That means customer enthusiasm, showing itself in plenty of repeat business — plus

friend-to-friend endorsement that makes a dozen new Ken-Rad buyers grow where one bought before.

For profits today with still bigger profits tomorrow, handle Ken-Rad radio tubes! Helps of all kinds are available to get you off to a flying start, so act immediately. Steal a march on local competition by joining forces with Ken-Rad

Behind Ken-Rad radio tubes stands Electronics' first and greatest name — GENERAL ELECTRIC.

Write for Booklet ETR-16, "Essential Characteristics," the most complete digest of tube information available.



KEN-RAD

DIVISION OF GENERAL ELECTRIC COMPANY
OWENSBORO, KENTUCKY

178-ED-6650

EDITORIAL

TELEVISION SERVICING received quite a thorough analysis during the recent TBA Conference in New York. Both manufacturer and Service Man presented their views on this important subject with the discussion centering on factory-trained factory-controlled servicing and factory or privately-trained but independently operating Service Shops.

Speaking for General Electric, W. L. Parkinson disclosed that Service Men of their distributors and franchised dealers will be trained to service and maintain television receivers. The distributors' technical group will be trained first, and then service courses will be held for dealers' Service Men. Discussing costs, Mr. Parkinson said that installation charges will run to about \$50 and will include a one-year warranty service. Mr. Parkinson also revealed that General Electric believes that many independent Service organizations are capable of installing and servicing television receivers and, accordingly, they will not close the door to such Service Shops who can prove themselves capable of providing a guaranteed service.

Outlining the DuMont plan, Ernest A. Marx said that DuMont has established a school to train their dealers and Service representatives, and Service Shops. In the DuMont plan, all men are carefully screened for background. If approved, they receive a thorough training in television servicing. Commenting on the equipment required to service, Mr. Marx pointed out that the very best and the most complete test equipment available will be necessary for servicing.

In the RCA plan disclosed by W. L. Jones, it was learned that the RCA Service Company will arrange for the installation of television receivers. Operating in conjunction with the RCA dealers, the Service Men of RCA will not only install the receivers but maintain them for a full year and charge from \$45 to \$50 for 7" and 10" model installations, respectively.

Discussing television servicing and the Service Man, John F. Rider said that more independent Service Men should be given an opportunity to participate in television servicing. Analyzing the advanced technical knowledge required, Mr. Rider pointed out that many Service Men had studied the art carefully and would continue their studies. These men should have the right to service television receivers, he declared. He said that there is no technique in television receivers which is so complicated that it cannot be assimilated by the better grade of Service Man intelligence. In fact, he said, the goal of the design engineer must be such that the equipment is fool proof and simple to repair.

Mr. Rider stressed that the entire industry would profit greatly if it fostered the technical advancement of independent Service Men.

A complete report on the talks by Rider, Jones and Marx, and others who participated in the TBA television servicing panel will appear in the November issue of SERVICE. Watch for it.

THAT VICIOUS PRACTICE of overcharging appears to be on the loose again. Why some Service Men will insist on price gouging is difficult to understand. They know it's illegal, and can only result in complete loss of face, and yet the price juggle continues.

It's a pity, affects everyone and shames the industry.

Active Service Shops have demonstrated time and again that there's plenty of income available for the honest operator. The shady price packing operator never really profits and is always doomed to business failure.

Overcharging must stop and promptly!

RADIO TELEVISION ELECTRONIC SERVICE

Reg. U. S. Patent Office

Vol. 15, No. 10

October, 1946

LEWIS WINNER

Editorial Director

ALFRED A. GHIRARDI
Advisory Editor

F. WALEN
Managing Editor

Electromagnetic Deflection Systems in Television Receivers. By Edward M. Noll	20
Industrial Intercommunications. By Maurice F. Kerr	30
New Models	28
Old Timer's Corner	29
Portable Oscillographs with 2" C-R Tubes. By M. W. Beacay ..	12
Sales Helps and the Service Man. By Kenneth C. Burcaw	11
Ser-Cuits. By Henry Howard	22
Service Aids	27
Servicing Helps. By Frank C. Keene	34
Tools and Accessories for the New Service Shop. By Alfred A. Ghirardi	16
CIRCUITS	
Admiral 4A1	22
Crosley 56FA	23
DeWald A500-503	24
Stewart-Warner 9014-E (Cover)	26
Zenith 4K016	23
Zenith 6G001	24
COVER	
Balanced Loop Receiver (Stewart-Warner 9014-E)	26
SERVICE AIDS	
Flexible Light Control for Repair Work	27
Loop in Cover of Tester as Antenna	27
Removing Meter Face Static Charges	27
SERVICING HELPS	
Oscillators	35
Multiple Headphone Circuits	34
Index to Advertisers	48
Manufacturers	
News	36
New Products	38
Jots and Flashes	48

Copyright, 1946, Bryan Davis Publishing Co., Inc.

Published monthly by Bryan Davis Publishing Co., Inc.
52 Vanderbilt Avenue, New York 17, N. Y. Telephone Murray Hill 4-0170



Bryan S. Davis, President
Paul S. Weil, Vice Pres.-Gen. Mgr.



A. Goebel, Circulation Manager
F. Walen, Secretary

Cleveland Representative: James C. Munn, 2650 E. 126th St., Cleveland 20, Ohio; Telephone CEDar 7783
Chicago Representative: Lawrence Wehrhelm, 5510 W. Lemoyne Ave., Chicago, Ill.; Telephone MEERimac 7919
Pacific Coast Representative: Brand & Brand, 1052 W. Sixth St., Los Angeles 14, Calif.; Telephone Michigan 1732
Brand & Brand, 1065 Monadnock Bldg., San Francisco, Calif.; Telephone Douglas 4475

Entered as second-class matter June 14, 1932, at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price: \$2.00 per year in the United States of America and Canada; 25 cents per copy. \$3.00 per year in foreign countries; 35 cents per copy.

Jensen *Speech Master* REPRODUCERS

...for clear, crisp, intelligible
Speech* Reproduction

Designed especially for speech reproduction in intercommunication and public address applications, this Speech Master family of JENSEN Reproducers, delivers clean, sharp, understandable announcements and orders. Like all JENSEN products, these Speech Masters were completely engineered to do their job efficiently and well.

MODEL NJ-300 SPEECH MASTER (Railroad Type).

PM design. Widely used in railroad intercommunication in locomotives, cabooses, signal towers and yards. Rugged case protects against shock and vibration; withstands dust, smoke and the elements. Voice coil impedance 12 ohms; power rating, 10 watts. Space provided inside case for 500-ohm impedance transformer. Overall height 11-3/4"; width 6-25/32"; depth 4-13/16". Holes provided in base for mounting in any position.

MODEL AR-10 SPEECH MASTER *ALNICO 5*. design. Specially constructed reflex horn increases efficiency in mid-frequency range, giving added effectiveness and "punch" to speech quality; prevents direct access of rain and snow to speaker diaphragm. Voice coil impedance, 4 ohms and 45 ohms; power rating, 6 watts. Space provided inside for 1/2" x 1/2" transformer. Overall diameter 10"; depth 8". Complete with mounting bracket.

MODEL AP-11 SPEECH MASTER (Panel mounting). Similar to AP-10 but without base. Mounts in 4-27/64" cut-out; clearance eyelets for mounting screws. Depth 4 1/2" from front panel. Screws and drilling template included. Voice coil impedance 4 ohms or 45 ohms; power rating, 5 watts.

MODEL AP-10 SPEECH MASTER (Desk or Wall type). PM design, desk or wall mounting. Complete with base and tilt adjustment. Double dustproofed. Rubber covered 36" cord. Internal mounting bracket for 1/2" x 1/2" transformer. Voice coil impedance 4 ohms or 45 ohms; power rating, 5 watts. Height 6-3/4"; depth 5 1/8"; diameter 5". Finish hammered gray with satin chrome trim.

MODEL NF-300 SPEECH MASTER (Navy Type). Developed for use as a loud speaker and microphone. Special case design over-rides wind and background noises for talk-back. Enclosed case and protective screen render this model proof against weather, dust and moisture *ALNICO 5*. PM design. Power rating, 10 watts; voice coil impedance 12 ohms. Mounts in 5 3/8" cut-out; six screw holes in rim. Overall diameter 6-7/16"; depth (from front of panel) 2-9/64". Finished in Munsel N4-5 gray enamel.

MODEL AP-20 SPEECH MASTER Heavy-duty unit for high-level paging and call systems in noisy industrial installations. PM design. Furnished with eyebolt for overhead suspension but available with stand for wall or table mounting. Voice coil impedance 8 ohms; power rating, 25 watts. Overall diameter 13 1/2"; depth 9"

*For full discussion of Speech requirements, see Jensen Monograph No. 4.


JENSEN MANUFACTURING CO.

6621 S. LARAMIE AVENUE, CHICAGO 38, ILLINOIS, U. S. A.
In Canada: J. R. Longstaffe, Ltd., 11 King Street, West, Toronto, Ont.



Jensen
SPEAKERS
WITH *ALNICO 5*

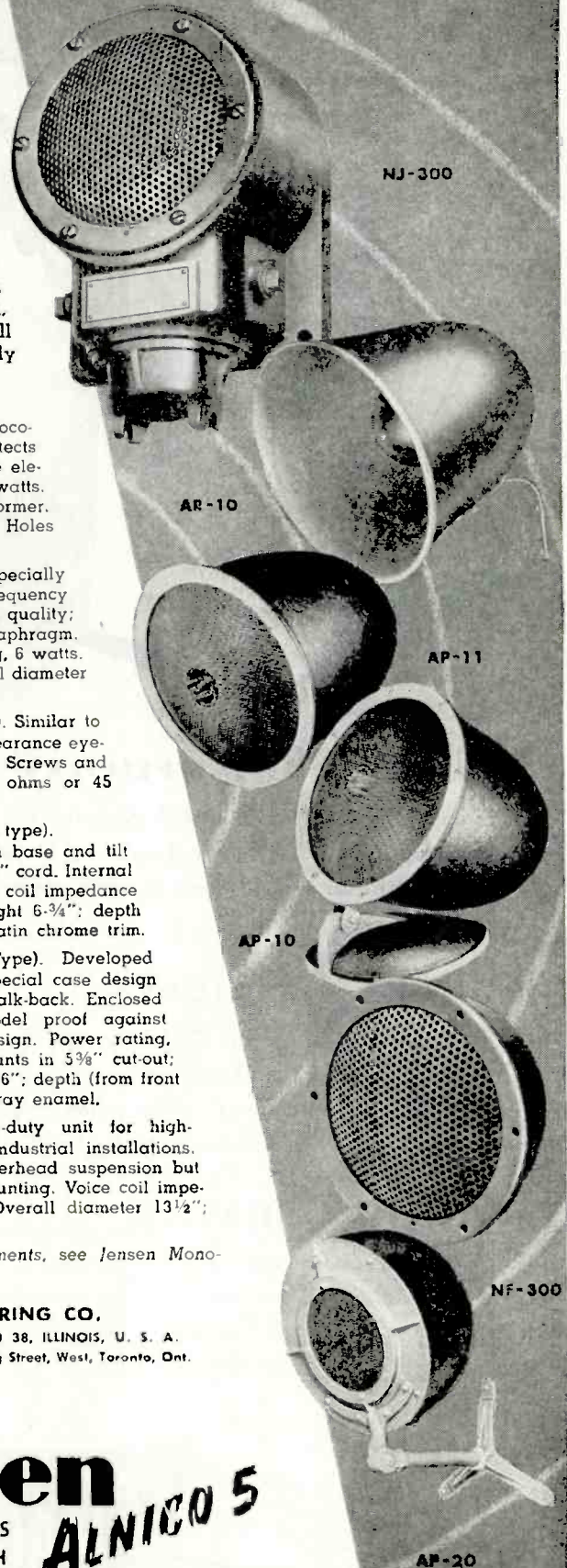Specialists in Design and Manufacture of Acoustic Equipment




5

MONOGRAPHS AVAILABLE

If you haven't yet procured these five valuable technical booklets, order now—either from your dealer or direct—at 25¢ each.

1. Loud Speaker Frequency-Response Measurements
2. Impedance Matching and Power Distribution
3. Frequency Range in Music Reproduction
4. The Effective Reproduction of Speech
5. Horn Type Loud Speakers

25¢ each

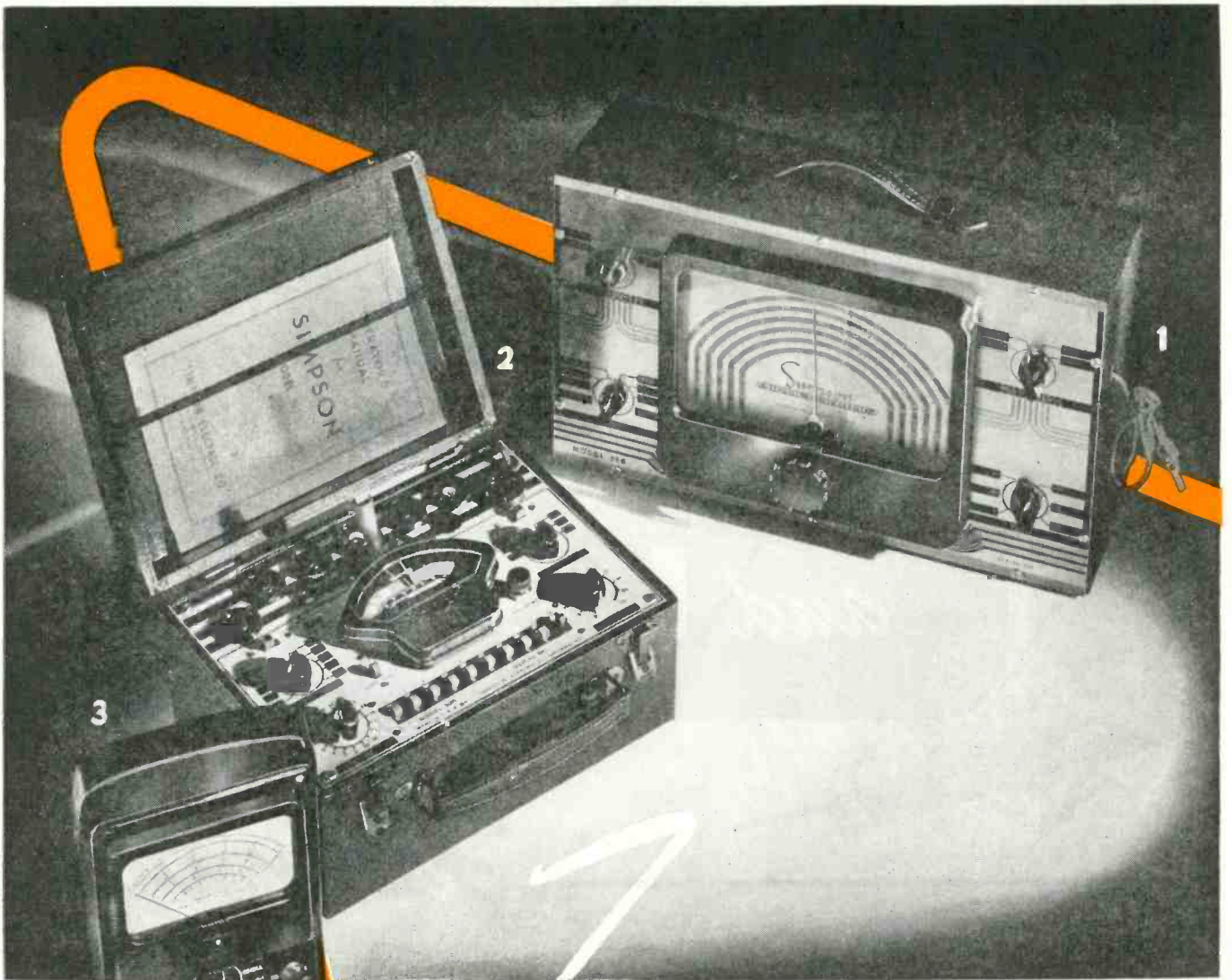

Model 31E Signal Generator.
Designed down to the most minute detail for highest accuracy, greatest stability, minimum leakage, and good wave form.....\$67.35

Model 305 Tube Tester. Tests all tubes. Provides for filament voltages from .5 volts to and including 120 volts. Spare sockets for future tube developments....\$46.25

Model 250 High Sensitivity Set Tester. 23,000 ohms per volt. D.C. Voltage ranges to 5,000 volts A.C. and D.C. Resistance ranges to 20 megohms. Current ranges to 500 milliamperes.....\$38.95

This Simpson "Big 3" *... gives servicemen a real profit-making set-up*

● The successful radio serviceman today must have the finest in test instruments for a very practical reason—that's his only hope of present and continued profits. To meet the tremendous volume of business available he must be able to "trouble-shoot" fast and *accurately* every time. Only thus can he correct trouble speedily, with satisfaction to the customers.

Simpson offers you, in three basic test instruments, the accuracy and advanced electronic engineering which have given Simpson the proudest name in the industry. They are tried-and-tested examples of the kind of instruments Simpson has always built. Their use will demonstrate that from Simpson alone can you expect "instruments that stay accurate" with construction and design that lead the field.

To dealer and to serviceman alike, Simpson offers today the assurance of continued profits that only quality can give. No Simpson instrument is ever marketed, or ever will be, unless its makers feel that, of its kind, nothing finer can be produced.

Simpson

INSTRUMENTS THAT STAY ACCURATE.

SIMPSON ELECTRIC COMPANY
5200-5218 West Kinzie Street, Chicago 44



Buy SPRAGUE and KOOLOHM

REG. U. S. PAT. OFF.

From these

ALABAMA

Bessemer—Bessemer Radio Supply
Birmingham—James W Clary
Mobile—Nelson Radio & Supply Co.
Radio Labs
Montgomery—Teague Hardware Co.
Southeastern Radio Parts Co.

ARKANSAS

Fort Smith—Wise Radio Supply
Little Rock—Southern Radio Supply
Texarkana—Lavender Radio Supply Co.

ARIZONA

Phoenix—Radio Parts of Arizona

CALIFORNIA

Bakersfield—Bakersfield Radio Supply
Fresno—Jack C. Arbuckle
Billings Wholesale Radio
Hollywood—Hollywood Radio Supply, Inc.
Long Beach—Radio & Tel. Equip. Co.
Los Angeles—Figart Radio Supply Co.
Kierulff & Co.
Nelson Brothers Co.
Radio Equip. Distributors
United Radio Supply Co.
Universal Radio Supply Co.
Modesto—Jack Warren
Oakland—W D Brill Company
E. C. Wenger Co.
Pasadena—Dow Radio Supply Co.
Sacramento—C. C. Brown Co.
Henderson Bros.
Sacramento Elec. Supply Co.
San Diego—Coast Electric Co.
Electronic Equip. Distr.
Shanks & Wright
San Francisco—Associated Radio Distrs.
C. C. Brown Co.
San Jose—Frank Quement
Santa Ana—Radio & Tel. Equip. Co.

COLORADO

Denver—Inter-State Radio & Supply Co.

CONNECTICUT

Bridgeport—Hatry & Young, Inc.
Hartford—Hatry & Young, Inc.

New Britain—United Radio Supply
Universal Radio Co.
New Haven—Thomas H. Brown Co.
Hatry & Young, Inc.
New London—Hatry & Young of New
London, Inc.
Stamford—Hatry & Young, Inc.
Waterbury—Hatry & Young, Inc.

DELAWARE

Wilmington—Radio Elec. Serv. Co.

DISTRICT OF COLUMBIA

Washington—Kenyon Radio Supply Co.
Rucker Radio Wholesalers

FLORIDA

Jacksonville—Kinkade Radio Supply
Major Appliances
Miami—Electronic Supply Co.
Major Appliances
Orlando—Radio Accessories Co.
St. Petersburg—Welch Radio Supply
Sarasota—Morley Radio Co.
Tampa—Kinkade Radio Supply
Major Appliances

GEORGIA

Atlanta—Concord Radio Corp.
Southeastern Radio Parts Co.
Specialty Dstg. Co., Inc.
Macon—Specialty Dstg. Co., Inc.
Savannah—Southeastern Radio Parts Co.
Specialty Dstg. Co., Inc.

ILLINOIS

Bloomington—J. W. Arbuckle
Chicago—Allied Radio Corp.
Concord Radio Corp.
Grant Radio Co., Inc.
Nation Wide Radio
Radio Parts Company
Kankakee—Radio Doctors Supply House

INDIANA

Angola—Lakeland Radio Supply
Richmond—Fox Sound Equipment Co.

IOWA

Cedar Rapids—Gifford-Brown, Inc.
Council Bluffs—World Radio Labs., Inc.
Des Moines—Gifford-Brown, Inc.
Radio Trade Supply Corp.
Fort Dodge—Gifford-Brown, Inc.
Ken-Els Radio Supply
Mason City—Radio-Electric Supply Co.
Sioux City—Power City Radio Company
Sioux City Radio & Appl. Co.
Waterloo—Gifford-Brown, Inc.
World Radio Laboratories, Inc.

KANSAS

Pittsburg—Pittsburg Radio Supply
Topeka—Acme Radio Supply
Wichita—Radio Supply Co.

KENTUCKY

Lexington—Radio Equipment Co.
Louisville—Peerless Electronic Equip. Co.
Newport—Apex Distributing Co.

LOUISIANA

Lake Providence—F. H. Schneider & Sons, Inc.
New Orleans—Radio Parts, Inc.
Shreveport—Dunkelman-Pace
Koelemay Sales Co.

MAINE

Auburn—Radio Service & Supply Store
Portland—Frank M. Brown Co.

MARYLAND

Baltimore—Henry O. Berman Co., Inc.
Cumberland—Cumberland Radio Whol.
Salisbury—Dealers Radio Service

MASSACHUSETTS

Boston—De Mambro Dstrs., Inc.
Hatry & Young of Mass., Inc.
A. W. Mayer Co.
Radio Wire Television, Inc.
Sager Elec'l Supply Co.
Cambridge—The Eastern Co.
Holyoke—Springfield Radio Co.
Lawrence—Hatry & Young of Mass., Inc.
New Bedford—C. E. Beckman Co.
Pittsfield—Pittsfield Radio Co.

Roxbury—Gerber Radio Supply Co.
Springfield—T. F. Cushing Co.
Springfield Radio Co.
Worcester—De Mambro Dstrs., Inc.
The Eastern Co.
Radio Electronic Sales Co.
Radio Maintenance Supply Co.

MICHIGAN

Ann Arbor—Wedemeyer Elec. Supply Co.
Battle Creek—Wedemeyer Elec. Supply Co.
Detroit—Ferguson Radio Supplies
Radio Specialties Co.
Radio Supply & Eng. Co., Inc.
Flint—Radio Tube Mds. Co.
Grand Rapids—Wholesale Radio Co.
Jackson—Fulton Radio Supply
Kalamazoo—Ralph M. Ralston Co.
Muskegon—Industrial Elec. Supply Co.
Pontiac—Electronic Supply Co.
Saginaw—Radio Parts Company

MINNESOTA

Duluth—Northwest Radio
Minneapolis—Bauman Company
Sidney Rosenthal
St. Paul—Electronic Distributing Co.

MISSISSIPPI

Greenville—The Goyer Company
Meridian—Griffin Radio Supply

MISSOURI

Cape Girardeau—Suedekum Elec. Sup. Co.
Jefferson City—Central Mo. Dstg. Co.
Joplin—M. Brotherson
Mardick Dstg. Co.
Kansas City—Burstein-Applebee Co.
Manhattan Corp.
St. Joseph—St. Joseph Radio & Supply Co.
St. Louis—Walter Ashe Radio Co.
Interstate Supply Co.
Radonics
Springfield—Harry Reed Radio & Sup. Co.

MONTANA

Butte—George Steele & Co.
Kalispell—McIntosh Music House

SPRAGUE PRODUCTS COMPANY • NORTH ADAMS, MASS.



CAPACITORS RESISTORS

Write for Catalog C-306

Distributors

NEBRASKA

Omaha—Omaha Appliance Co.
Radio Equipment Co.
Scottsbluff—Joachim Radio Supply

NEW HAMPSHIRE

Dover—American Radio Corp.

NEW JERSEY

Camden—Radio Elec. Serv. Co.
Newark—Continental Sales Co.
Krich-Radisco, Inc.
T. A. O'Loughlin & Co.
Radio Wire Tel., Inc.
Perth Amboy—Bennett's Radio Supply
Red Bank—J. H. Kelly Company
Trenton—United Tire Stores Co.

NEW YORK

Albany—Fort Orange Radio Dstg. Co.
Amsterdam—Adirondack Radio Supply
Auburn—Date's Radio Service
Binghamton—Broome Dstg. Co., Inc.
Federal Radio Supply Co.
Brooklyn—Green Radio Distributors
Stam-Burn Radio & Elec. Co.
Buffalo—Bars Radio & Electronic Parts
Dymac, Inc.
Genesee Radio & Parts Co.
Radio Equipment Corp.
Standard Electronics Co.
Elmira—LeValley-McLeod-Kinkaid Co., Inc.
Fredonia—C. R. Barker
Glens Falls—Ray Distributing Co.
Hempstead, L. I.—Standard Parts Corp.
Ithaca—Stallman of Ithaca
Jamaica, L. I.—Norman Radio Distrs.
Middletown—L & S Radio Sales
New York City—Fischer Distributing Co.
Radio Equipment Co.
Radio Wire Tel., Inc.
Niagara Falls—Niagara Radio & Parts Co.
Rochester—Beaucaire, Inc.
Masline Radio & Electronic Equip. Co.
Schenectady—Fort Orange Radio Dstg. Co.
M. Schwartz & Son
Syracuse—Broome Dstg. Co., Inc.
Syracuse Radio Supply
Troy—Trojan Radio Co.
Utica—Beacon Electronic Inc.
Watertown—Beacon Electronic Inc.

NORTH CAROLINA

Asheville—Freck Radio & Supply Co.
Charlotte—Dixie Radio Supply Co.
Southern Radio Corp.
Fayetteville—Eastern Radio Supply
Goldsboro—Signal Radio Supply
Greensboro—Dixie Radio Supply Co.
Raleigh—Carolina Radio Equip. Co.
Winston-Salem—C. R. Williams Radio Co.

NORTH DAKOTA

Fargo—Radio Equipment Co.

OHIO

Akron—Olson Radio Warehouse
Ashtabula—Morrison Radio Supply
Canton—Armstrong Radio Supply
Burroughs Radio
Cincinnati—Chambers Radio Supply Co.
Schuster Elec. Co.
United Radio, Inc.
Cleveland—Goldhamer, Inc.
Northern Ohio Laboratories
Winteradio, Inc.
Columbus—Hughes-Peters, Inc.
Whitehead Radio Co.
Dayton—Hughes-Peters, Inc.
Standard Radio & Electronic Prod. Co.
East Liverpool—Hausfeld Radio
Kent—Kladag Radio Labs.
Lima—The Northwestern Radio Co.
Mansfield—Burroughs Radio
Marion—Bell Radio Supply
Springfield—Standard Radio & Electronic Prod. Co.
Steubenville—D & R Radio Supply
Hausfeld Radio
Toledo—Toledo Radio Specialties
Warren—Radio Specialties
Youngstown—Appliance Wholesalers

OKLAHOMA

Enid—Standard Measuring & Equip. Co.
Oklahoma City—Radio Supply, Inc.
Southern Sales Co.
Tulsa—Radio, Inc.

OREGON

Portland—Bargelt Supply
Harper-Meggee, Inc.
Portland Radio Supply Co.

PENNSYLVANIA

Allentown—Radio Elec. Serv. Co.
Beaver Falls—Reliable Motor Parts Co.
Easton—Radio Elec. Serv. Co.
Eric—John V. Duncombe Co.
Harrisburg—Radio Distributing Co.
Lancaster—Eshelman Supply Co.
George D. Barbey Co.
Norristown—Kratz Bros. Co.
Philadelphia—Almo Radio Company
Consolidated Radio Corp.
Electric Warehouse
Emerson Radio of Pa.
Radio Elec. Serv. Co.
N. W. Cor. 7th & Arch Sts.
5133 Market St.
3145 N. Broad St.
Eugene G. Wile
Pittsburgh—Hamburg Bros.
The John Marshall Co.
Radio Parts Co.
Pottsville—Jones Radio Co.
Reading—George D. Barbey Co.
St. Marys—B & R Electric Co.
Scranton—Broome Dstg. Co., Inc.
Wilkes-Barre—General Radio & Elec. Co.
Radio Service Co.
Williamsport—Williamsport Radio Supply

RHODE ISLAND

Providence—William Dandreta & Co.
W. H. Edwards Co.

SOUTH CAROLINA

Columbia—Dixie Radio Supply Co.

SOUTH DAKOTA

Aberdeen—Danielson & Brost Co.
Sioux Falls—Power City Radio Co.
United Radio Supply

TENNESSEE

Knoxville—Bomar's
Chemistry Radio & Elec. Co.
C. M. McClung & Co.

Memphis—McTyier Radio Supply
Nashville—Currey's Radio Service
Radio & Appliance Corp.

TEXAS

Abilene—R & R Supply Co., Inc.
Amarillo—R & R Supply Co., Inc.
Austin—The Hargis Company
Beaumont—Montague Radio Co.
Corpus Christi—Wicks-DeVilbiss Co.
Electronic Equip. & Engin. Co.
Dallas—All-State Dstg. Co.
Crabtree's Wholesale Radio
Southwest Radio Supply
Wanslow & Co.
Fort Worth—Electronic Equipment Co.
Fort Worth Radio Supply Co.
Houston—A. R. Beyer Company
Lubbock—R & R Supply Co., Inc.
San Antonio—Olsen Radio Supply
Tyler—Lavender Radio Supply Co.
Waco—The Hargis Company
Wichita Falls—Wichita Falls Bat. & Elec.

VIRGINIA

Norfolk—Ashman Distr. Company
Roanoke—Leonard Elec. Sup. Co.
Richmond—Johnston Gasser Co.

WASHINGTON

Bellingham—Waitkus Supply Co.
Seattle—General Radio, Inc.
Harper-Meggee, Inc.
Sunset Electric Co.
Spokane—Harper-Meggee, Inc.
Tacoma—Wible Radio Supply


WEST VIRGINIA

Bluefield—Whitehead Radio Co.
Charleston—Chemistry Radio & Elec. Co.
Hicks Radio Supply
Clarksburg—Trenton Radio Co.
Huntington—Electronic Supply, Inc.
Morgantown—Trenton Radio Co.
Parkersburg—Randle & Hornbrook
Wheeling—Wheeling Radio Supply

WISCONSIN

Green Bay—Neslo Electronic Distrs.
Madison—Radio Distrs. of Madison, Wis.
Milwaukee—Radio Parts Co., Inc.

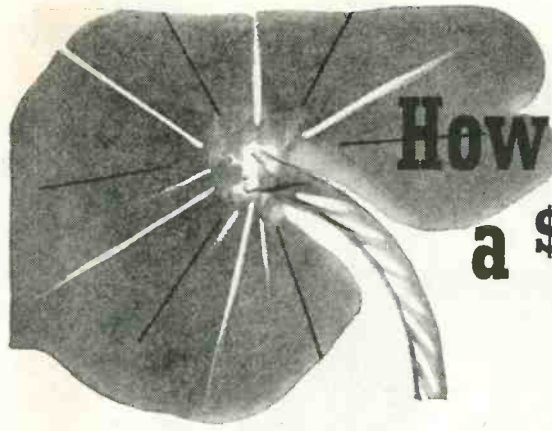JOBGING DISTRIBUTING ORGANIZATION FOR PRODUCTS OF SPRAGUE ELECTRIC CO.




How to Pull the Fuse from a \$20,000,000,000 Bomb

IMAGINE a super bomb whose explosion could rock the entire nation. Such a bomb EXISTS—but you can help render it harmless.

This bomb is \$20,000,000,000 surplus national income.

Authorities estimate that this year's total income will be \$155,000,000,000—personal taxes will total \$15,000,000,000—consumer goods and services will absorb no more than \$120,000,000,000. This leaves \$20,000,000,000. Even if banks and insurance companies absorb one-fifth of the surplus (as they did in 1945), there will still remain \$16,000,000,000 that could be used to bid up prices.

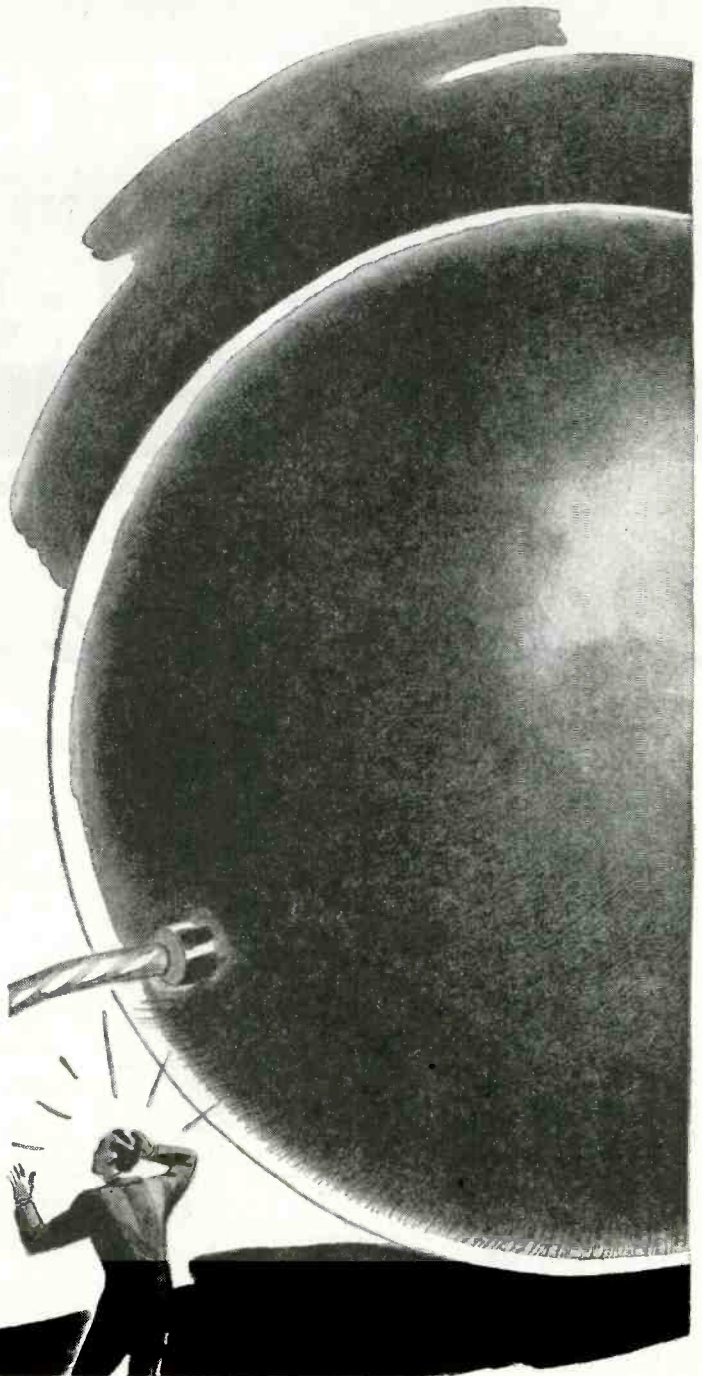You're doing yourself, your company, and your country a favor by continuing your payroll deduction plan for the regular purchase of U. S. Savings Bonds. At maturity, they pay \$4 for every \$3 invested!



THE PEACETIME PAYROLL SAVINGS PLAN —

A booklet, published for key executives by the Treasury Department, containing helpful suggestions on the conduct of your payroll savings plan for U. S. Savings Bonds.



THIS TIME IT'S FOR YOU

A booklet for employees . . . explaining graphically how the payroll savings plan works . . . goals to save for, and how to reach them with Savings Bonds.



Are you using these booklets?

If not, or if you want additional copies, just ask your State Director of the Treasury Department Savings Bonds Division.

The Treasury Department acknowledges with appreciation the publication of this message by

SERVICE

This is an official U. S. Treasury advertisement prepared under the auspices of the Treasury Department and the Advertising Council







CHECK

the features

in these Capacitor Analyzers

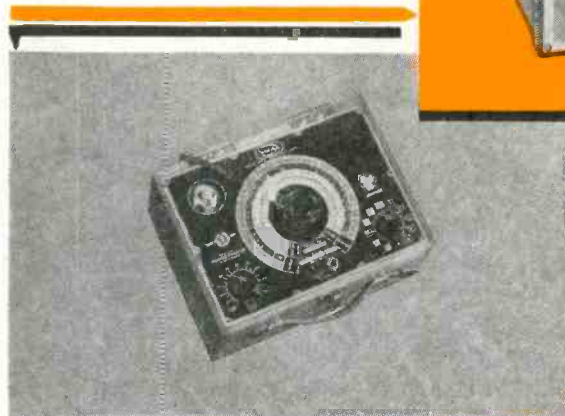

Model CBB CAPACITOR ANALYZER

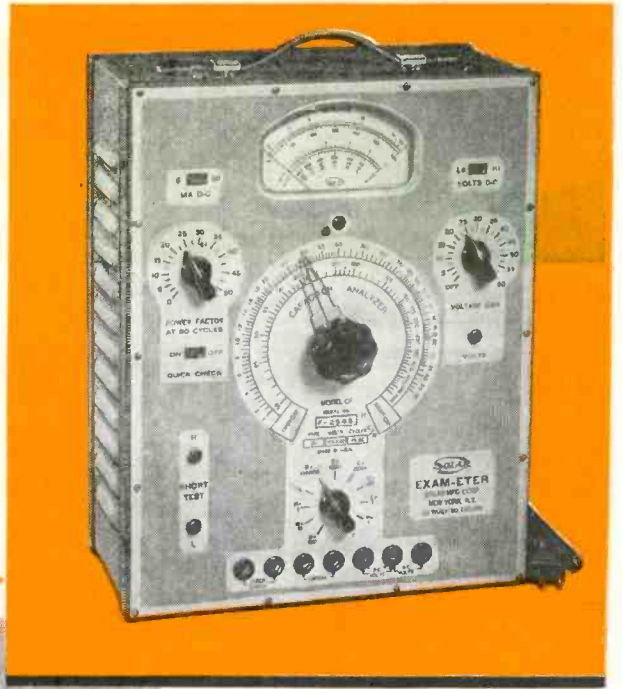

Model CF EXAM-ETER

MODEL CF

Most comprehensive of all capacitor analyzers, this sturdy, reliable instrument is designed to simplify electronic servicing.

- Has exclusive, patented "Quick-Check" circuit for qualitative tests and Intermittent checks without unsoldering capacitor leads
- Capacitance range—10 mmf to 2000 mf
- Power Factor range—0 to 55 percent
- Insulation Resistance range—3 to 10,000 megohms
- Leakage Current—Reads electrolytic leakage current directly on large 4 1/2" meter

PLUS

- ✦ Continuously Adjustable 0-550 volt D-C power supply for electrolytic tests
- ✦ 0-550 volt, 3-range D-C VTVM
- ✦ 10-50 volt, A-C VTVM
- ✦ 100 ohm to 7.5 megohm A-C resistance bridge
- ✦ JAN Quality Components for Long Troublefree Service

MODEL CBB

An up-to-the-minute version of the famous Solar Model CB, long-time standard analyzer of the radio service industry.

- Capacitance range—10 mmf to 800 mf
- Power Factor range—0 to 55 percent
- "Magic-Eye" Tube for bridge balance indication
- Simplified Neon-Lamp circuit for visual check of insulation resistance and electrolytic leakage
- Resistance Bridge—50 ohm to 2 megohm range

PLUS

- ✦ Color-coded easy-to-read scales
- ✦ Portability—small size and light weight
- ✦ Reliable components for operation in humid climates

Solar Capacitor Analyzers are fully described in Catalog IN-2, available at your distributors or directly from Solar Capacitor Sales Corp., 285 Madison Avenue, New York 17, N. Y.

SOLAR CAPACITORS

"Quality Above All"



SYLVANIA NEWS


RADIO SERVICE EDITION

OCT. Prepared by SYLVANIA ELECTRIC PRODUCTS INC., Emporium, Pa. 1946

ONE DEVICE NOW USED BY RADIO SERVICEMEN FOR GREAT VARIETY OF TESTS

Electrical Measurements Made Easy With New Sylvania Unit!

The SYLVANIA POLYMER

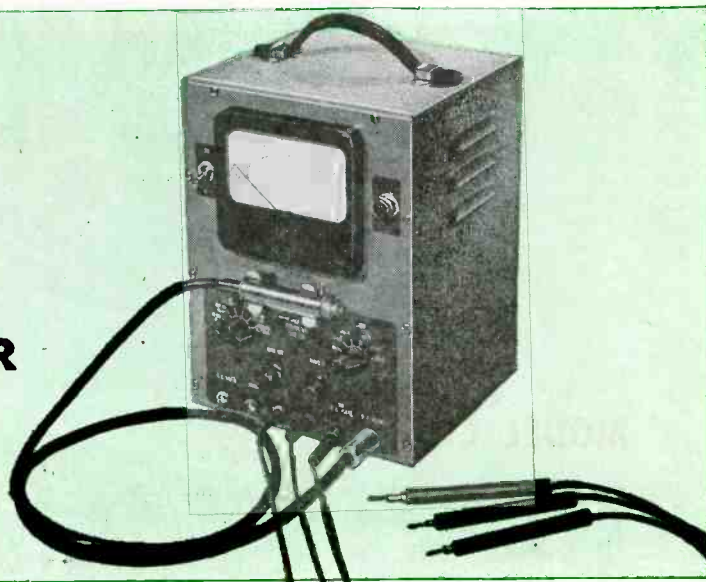

Radio servicemen now can use the new Sylvania Polymeter type 134 to facilitate a multitude of electronic measurements and tests to radio equipment.

This product of Sylvania Research is stabilized against errors due to voltage variations or gas current in tubes. All accessories included. See your Sylvania Distributor.

CHARACTERISTICS AND SPECIAL FEATURES

Tests audio, A.C. and R.F. voltages from 20 cps to 300 mc through use of proximity fuze-type tube built into handy probe. Full scale range of 3, 10, 30, 100, 300.

Measures D.C. from .1 to 1,000

volts in full scale ranges of 3, 10, 30, 100, 300, 1,000.

Measures D.C. current from .1 milliampere to 10 amperes in full scale ranges of 3, 10, 30, 100, 300, 1,000 milliamperes and 10 amperes.

Measures resistance from $\frac{1}{2}$ ohm to 1,000 megohms in full scale ranges of 1,000, 10,000, 100,000 ohms and 1, 10, 1,000 megohms.

ACCURACY

D.C. ranges $\pm 3\%$ of full scale.

A.C. ranges $\pm 5\%$ of full scale up to 30 volts and $\pm 7\%$ above 30 volts.

R.F. ranges $\pm 5\%$ of full scale up to 10 volts; $\pm 7\%$ from 10-100 volts; $\pm 10\%$ on 300 volt range.

Ohms $\pm 6\%$ to the left of $\frac{1}{2}$ scale; $\pm 13\%$ to the left of $\frac{3}{4}$ scale.

Current $\pm 3\%$ of full scale on all but 10 ampere scale which provides $\pm 5\%$ of full scale.

INPUT IMPEDANCES

R.F. ranges—2.7 megohms resistance shunted by approximately 3 mmf. capacity.

A.C. ranges—2.7 megohms resistance shunted by approximately 40 mmf. capacity.

D.C. ranges—16 megohms resistance.

Remember the Sylvania Polymeter type 134. It's beautifully styled, compactly designed, has easily read meter and dials.

SYLVANIA ELECTRIC

Emporium, Pa.

MAKERS OF RADIO TUBES, CATHODE RAY TUBES, ELECTRONIC DEVICES, FLUORESCENT LAMPS, FIXTURES, WIRING DEVICES, ELECTRIC LIGHT BULBS

SERVICE



SALES HELPS And the SERVICE MAN

I'VE TRAVELED THE COUNTRY widely on business missions and talked to dozens of neighborhood Service Shop owners, big ones and little ones, including many with freshly painted shingles. And practically everywhere there was excited talk about the shop's future and the potential healthy income in these times of shortages and run-down prewar sets. Some fellows were found to be doing a fine business because of an excellent shop location and, even more important, their sales aggressiveness in the community. Others, sad to say, were struggling along on pay-the-rent-and-taxes incomes, because of a complete disregard for *salesmanship*.

Many Service Men going into business for themselves have failed to realize the importance of selling. It's an old horse-sense axiom that, no matter how expert you are, customers just won't come to you if the fact is unknown. That puts the lie to the

by **KENNETH C. BURCAW**

*Sales Manager, Jobber Division
Cornell-Dubilier Electric Corp.*

favorite mousetrap analogy. In Tibet there's an old ragged man who carves delicate ivory figures, so tiny they look like dandruff in your palm, yet each is a perfectly formed carving in every detail. Ever hear of him? Probably not. Salesmanship could have made him famous and prosperous even in Tibet.

You Must Be a Salesman

If you will think of yourself as a salesman as well as a Service Man, business will grow almost automatically. No one is really born with selling ability. It must be acquired. The

same feeling of confidence you have in yourself must be instilled among your prospects. That's the whole essence of salesmanship. Doing that will gain more volume from a side street shop than a lackadaisical Service Shop owner on Main and Center Streets.

But there's a paradox. A busy Service Man does not have the time to keep plugging his services to the community and also maintain a steady output of repair jobs. Even a shop with several assistants requires personal attention and supervision. The problem can be solved with sales promotion helps that will stimulate repair business while you work in the shop. There is no time lost canvassing

(Continued on page 46)

Above
Assortment of sales helps available to the Service Man.

PORTABLE

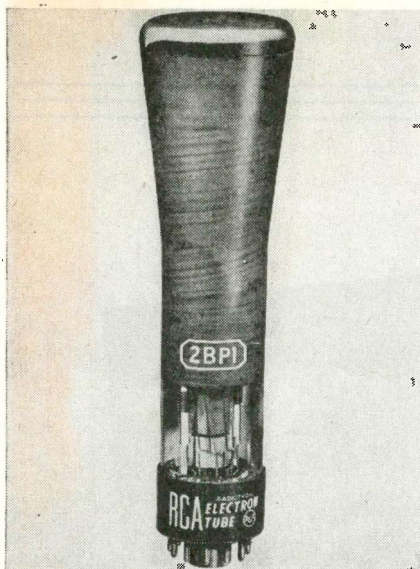



Fig. 1. A 2" cathode-ray tube recently developed for instrument application.

THE RECENT TREND TO MINIATURE test equipment has prompted the development of several unusual components, such as the recently-announced 2" cathode-ray tubes. With these tubes it has been possible to design unusually small, yet very effective, c-r Service Shop test units.

With one type of c-r tube recently developed, the 2BP1¹, designers have been able to construct a portable tester with a screen image bright enough to photograph with an ordinary camera.

In this tube, an electrostatic deflection focus type, there is an improved electron gun with a grid (No. 2) operated at high voltage so that beam current will not be affected by changes in the plate (No. 1) voltage. It also has a plate which takes negligible

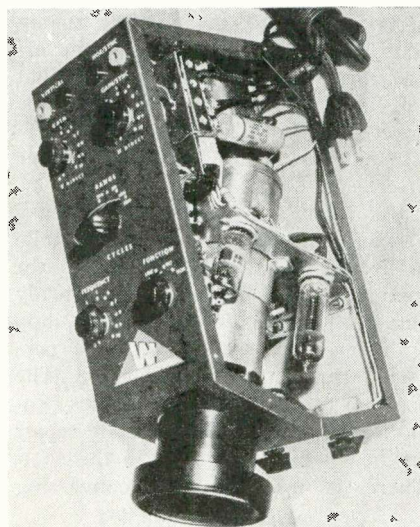View of oscillograph using 2" 2BP1-A c-r tube.
(Courtesy Waterman)



current. As a result of these features, the spot can be sharply focused on the screen, both at the center and at the edges. Low plate current permits the use of a low-current voltage-divider system and hence the use of a small filter capacitor.

Having a separate base-pin connection for each of the four deflecting electrodes, the tube is intended primarily for use in balanced electrostatic-deflection circuits. However, it is also well suited for use with unbalanced deflection because of design features which minimize spot and pattern distortion characteristic of such operation.

Tube Installation Data

The base pins of the c-r tube fit a duodecal 12-pin socket which may be installed so that the tube will operate in any position. The socket alone must not support the tube; other support, such as a yoke or saddle arrangement near the screen end of the tube, must also be used.

It is necessary to enclose the bulb in a grounded shield when operated in the presence of strong magnetic fields. The shield must be made of high-permeability metal having low residual magnetism to minimize the effects of extraneous magnetic fields. When a grounded metal shield is used around the tube, it may be necessary to insulate the high-voltage end of the tube from the shield to avoid leakage currents.

The heater is designed to be operated at 6.3 volts. The mid-tap or one side of the heater winding should preferably be connected to the cathode. If necessary, the heater may be operated with a bias of not more than ± 125 volts with respect to the cathode.

The d-c voltages for the grid and the two plates may be obtained conveniently from a high-voltage vacuum-tube rectifier. Since this tube requires very little current, the rectifier system can be of either the half-wave or the voltage-double type. Likewise, the filter requirements are simple. A 0.1 mfd capacitor will ordinarily provide sufficient filtering. If this is inadequate, a two-section filter is recommended. If the electrode voltages are obtained from a bleeder circuit, a bleeder current of 0.2 milliamperes usually is satisfactory. Considerably higher values

¹RCA.

may require more filtering than that provided by a single capacitor shunted across the d-c supply. In most applications, it is recommended that plate 2 be grounded in order that the deflecting electrodes may be operated at ground potential. With this arrangement, the heater and cathode at high negative potential with respect to ground.

In the use of cathode-ray tubes, it must always be remembered that high voltages may appear at normally low-potential points in the circuit due to capacitor breakdown or to incorrect circuit connections. Therefore, before any part of the circuit is touched, the power supply switch must be turned off and both terminals of any charged capacitors grounded.

Application Notes

Focusing of the fluorescent spot produced by the electron beam is controlled by adjustment of the ratio of plate 2 voltage to plate 1 voltage. Ordinarily, the ratio is adjusted by variation of plate 1 voltage. For this purpose, a potentiometer is required in the voltage-divider circuit.

The undeflected focused spot is normally close to the geometric center of the tube face. However, to take care of variation from tube to tube, designers provide for each pair of deflecting electrodes, at least 19 volts for each kilovolt of plate 2 voltage. By adjustment of this d-c compensating voltage on each pair of the deflecting electrodes, the spot may be centered.

Electrostatic Deflection

Two pairs of electrostatic deflecting electrodes, producing fields at right angles, are located within the bulb neck to provide for deflection of the electron beam. The electrostatic field of each pair of deflecting electrodes causes deflection of the electron beam in the direction of the gradient lines of the field and perpendicular to the plane of the deflecting electrodes; therefore, the deflections caused by the two fields are at right angles within a few degrees.

Deflection Voltages

Each pair of deflecting electrodes are normally operated at an average potential the same as that of plate 2. Each electrode of each pair is connected through a resistor of not more

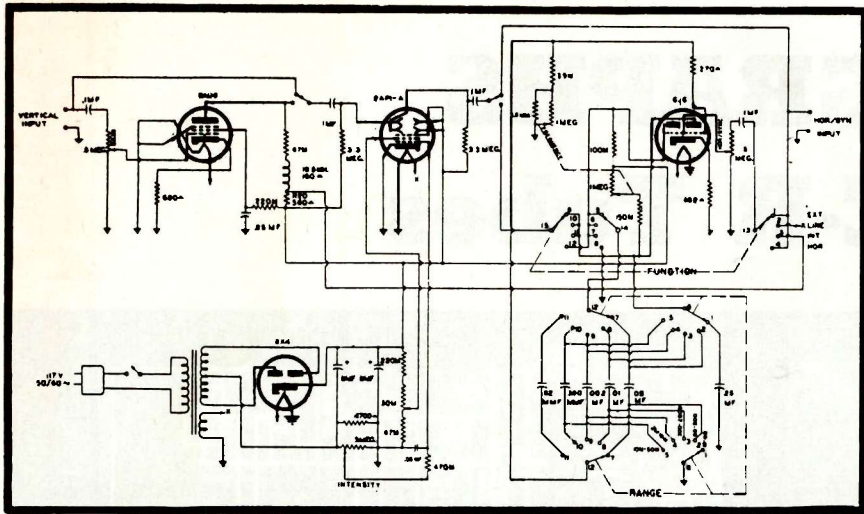


Fig. 4. Schematic diagram of the portable c-r test unit using the 2AP1-A type 2" tube.

is permissible to increase the trace brightness, for the short interval required to make the exposure, above that required for visual observation. The extent to which the beam current may be increased without harming the screen is proportional to the velocity of beam travel and pattern size, and inversely proportional to the duration of the phenomenon.

2BP1 Circuit

A circuit using the 2BP1 is shown in Fig. 2. This circuit includes desirable features for a laboratory instrument, such as balanced deflection, balanced spot centering, and provision for intensity (grid) modulation. Balanced deflection is recommended to minimize spot and pattern distortion. Spot centering is obtained by adjustment of ganged pairs of potentiometers.

Circuit Leakage

In this circuit, one side of the heater is connected directly to the cathode to prevent transformer or circuit leakage from developing any voltage between heater and cathode. A bypass capacitor of about 4 mfd may be used between the arm of the grid-bias potentiometer and cathode in case hum is present in the grid circuit.

Intensity Modulation


Intensity modulation is accomplished by introduction of the signal through

capacitor C_4 to grid 1. This capacitor has a small capacitance since the modulating signal is usually a pulse having a steep wave front. Large values of capacitance for this capacitor may require better filtering of the high voltage supply for the cathode-ray tube since the grid signal is referred to ground. The capacitor must have low leakage and must be able to withstand the plate 2 voltage.

Voltage Supply

The voltage supply for the amplifiers and the sweep (timing) oscillator has been combined with that for the cathode-ray tube. This arrangement provides additional current for the centering potentiometers and makes possible a lower high-voltage, low-current supply for the 2BP1 than

Fig. 3. Bottom view of the socket connections for 2BP1. Pin 1, heater; pin 2, grid 1; pin 3, cathode; pin 4, plate 1; pin 5, internal connections; pin 6, deflecting electrode, DJ_3 ; pin 7, deflecting electrode, DJ_1 ; pin 8, plate 2 and grid 2; pin 9, deflecting electrode, DJ_2 ; pin 10, deflecting electrode, DJ_1 ; pin 11, internal connections; and pin 12, heater.

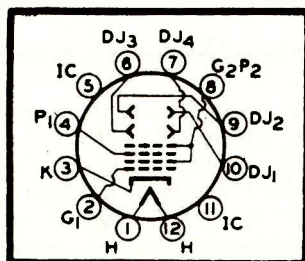

would be possible with separate power supplies.

4-Tube C-R Portable

Another 2"-type c-r tube, the 2AP1, was recently incorporated in a 4-tube portable test instrument² using a 6AU6 miniature-type pentode for the vertical amplifier, 6J6 miniature twin-triode, and 6×4 twin-diode rectifier. The 6J6 serves a dual purpose. One section is used as a horizontal amplifier, with a stage gain of 24, for a horizontal deflection sensitivity of 1 volt rms per inch. The second section is used in a multivibrator circuit as a time base oscillator, permitting linear tracing from 10 to 50,000 cps.

Bypass Switches

By pass switches on amplifier gain controls permit direct connection to both vertical and horizontal deflection plates of the c-r tube. A function switch is provided for the use of external and internal or line synchronization. Line synchronizing voltage is provided by a 6-volt filament winding. External synchronization permits the use of an audio oscillator for the creation of lissajou figures. These figures may be used to determine the frequency of an unknown audio or radio frequency. Quite often, by knowing the frequency of a spurious oscillation in a receiver, its removal is aided.

Other Controls

Other controls included are intensity, focus, and variable synchronous frequency.

The amplifiers are said to be substantially flat from 20 to 100,000 cps, with a gradual 2 db loss between low and high frequencies.


The input resistance for both vertical and horizontal amplifiers is 500,000 ohms, at a shunt capacitance of 36 mmfd.

Credits

The author is grateful to the commercial engineering department of the RCA Victor division of RCA and the Waterman Products Co., Inc., for the engineering data supplied on the 2BP1 tube and S-10-A instrument, respectively.

²Waterman Products Company, type S-10-A.

There's only

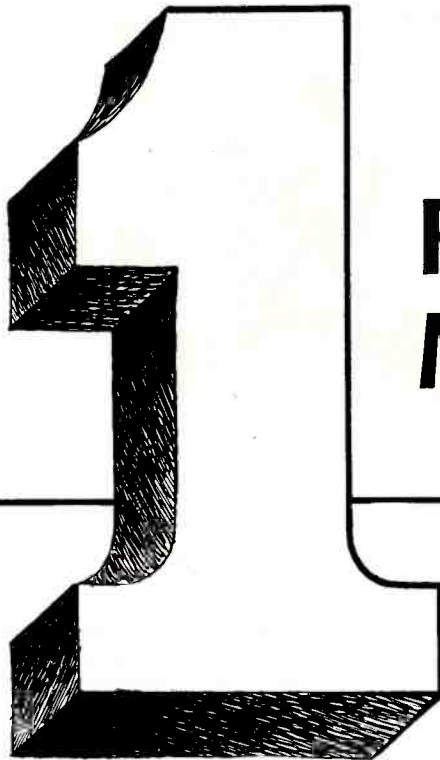

RIDER
MANUAL

BUT IT'S IN FOURTEEN VOLUMES

Rider Manuals are the only single source upon which you can depend for authoritative servicing data on pre-war American made receivers.

Rider Manuals cover the things which our 16 years of specialized publishing have proved you want and need; supplying such vital material as receiver schematics, voltage data, resistance values, chassis layouts and wiring, and trimmer connections.

Further evidence of our continuing service to the servicing industry will be found in the forthcoming Volume XV. This new volume will contain specially prepared and highly refined servicing information available from no other source—even from the set manufacturer. This supplementary material is information you need, offered in a form that will make it most useful to you. It will result in the saving of servicing time—an increase

in production worth many times the price of the volume!


Our advertisement next month will announce Volume XV and give important details on the revolutionary and exclusive features it will contain.

With Volume XV as with the other fourteen volumes "You're right with a Rider Manual!"

JOHN F. RIDER PUBLISHER, INC.

404 FOURTH AVENUE, NEW YORK 16, N. Y.

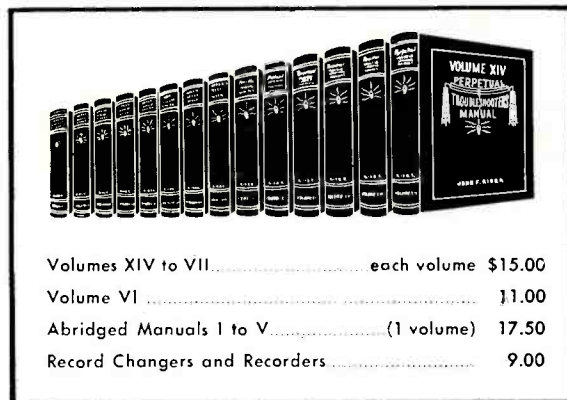Export Division: Rocke-International Corp., 13 East 40th Street, New York. Cable ARLAB



Volumes XIV to VII.....	each volume	\$15.00
Volume VI		11.00
Abridged Manuals I to V.....	(1 volume)	17.50
Record Changers and Recorders.....		9.00

RIDER RADIO BOOKS KEEP YOU IN TOUCH WITH SUCCESS



This new Rider Book, soon to be announced, will be of lasting usefulness to everyone interested in any phase of radio.

The Cathode Ray Tube at Work Accepted authority on subject . . .	\$4.00
Frequency Modulation Gives principles of FM radio . . .	2.00
Servicing by Signal Tracing Basic Method of radio servicing . . .	4.00

The Meter at Work An elementary text on meters . . .	\$2.00
The Oscillator at Work How to use, test and repair . . .	2.50
Vacuum Tube Voltmeters Both theory and practice . . .	2.50
Automatic Frequency Control Systems —also automatic tuning systems . . .	1.75
A-C Calculation Charts Two to five times as fast as slide rule	7.50

Hour-A-Day-with-Rider Series—

- On "Alternating Currents in Radio Receivers"
- On "Resonance & Alignment"
- On "Automatic Volume Control"
- On "D-C Voltage Distribution" **\$1.25 each**

RADAR—JUST OUT — \$1.00

Entertaining, Revealing, even a layman can understand explanation

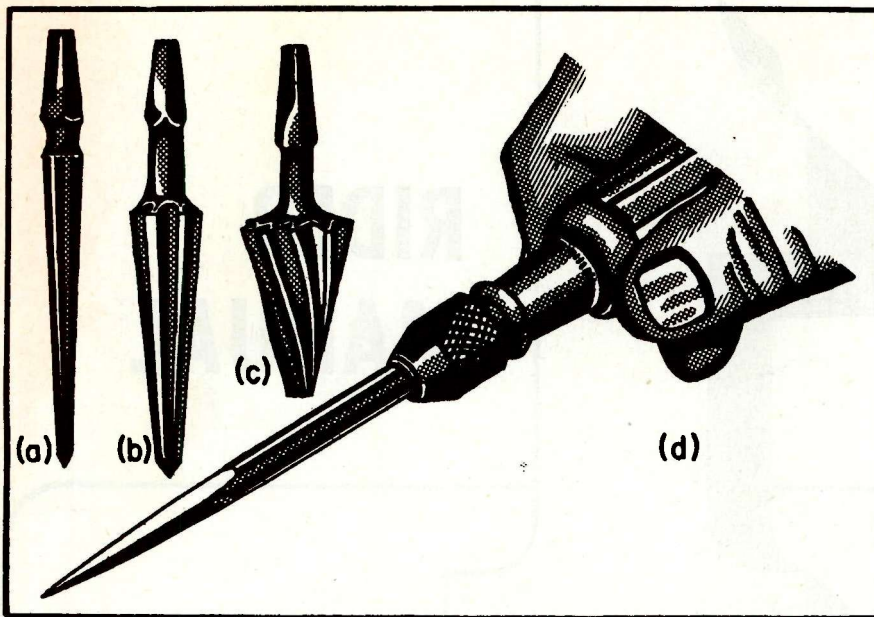


Fig. 1. Three useful sizes of tapered reamers; (a), (b), (c). A hand reamer (Stevens Walden, Inc.) is shown at (d).

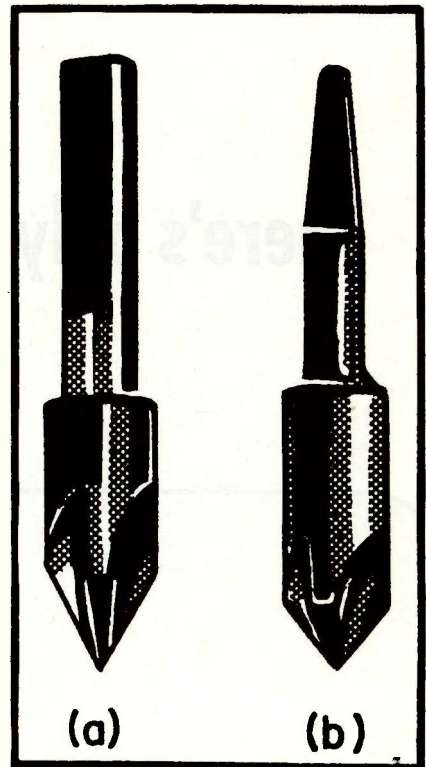


Fig. 2 (right). A round shank and a square bit shank countersink for holes that are to take flat or oval head screws.

TOOLS And ACCESSORIES

For the NEW SERVICE SHOP

CONTINUING OUR DISCUSSION of the supplementary and special-purpose tools, we come to some of the smaller, but nevertheless useful, hand tools.

[Part VI . . . Supplementary and Special-Purpose Tools]

by **ALFRED A. GHIRARDI**

Advisory Editor

Reamers

For the Service Man who does not wish to make too large an investment for an assortment of large size twist drills and an electric drill or breast drill of sufficient size to accommodate them, there is an alternative that will enable him to drill large size holes whenever necessary—but it entails more work on his part. A few tapered reamers having a square bit stock shank that fits into an ordinary carpenter's brace will serve the purpose. It is only necessary to use a few large twist drills such as a $\frac{1}{4}$ " and a $\frac{3}{8}$ " or $\frac{1}{8}$ " drill and use the tapered reamers to enlarge their holes to any desired size.

Three sizes of tapered reamers are useful; Fig. 1. In (a) appears one type with a slight taper, ranging in diameter from $\frac{1}{8}$ " at the point to a maximum of $\frac{1}{2}$ ". The reamer at (b) will enlarge holes from $\frac{3}{8}$ " up to $\frac{7}{8}$ ". The reamer at (c) will enlarge holes $\frac{5}{16}$ " up to $1\frac{1}{2}$ ". As the latter has a rather sharp taper it is useful only on

comparatively thin stock such as panels, chassis, etc

A very useful hand reamer, the *Reamawl*¹ is illustrated at (d). This is useful for quickly enlarging small holes by hand.

Countersinks

When drilling a hole for a flat-head or oval-head screw, it is necessary to countersink the hole to a taper of 82 degrees to fit the head, so that its top surface will be flushed with the work. Countersinks for this purpose are illustrated in Fig. 2. The model at (a) has a round shank so it can be used in the ordinary hand drill or electric drill. The one at (b) has a square bit shank for use in a carpenter's brace. Each can be used for countersinking either metal, wood, bakelite, etc. One of small size and having a round shank will be suitable.

Countersinks are also useful for re-

¹Produced by manufacturers of Spintite socket wrenches.

moving burrs that are caused by drilling or punching. This must be done carefully, otherwise the hole will be countersunk.

Large Hole Cutters

It is frequently necessary to cut round holes for replacement tube sockets, plugs, connectors and other receptacles in either an old or a new metal chassis. If there is sufficient space in which to work, these holes may be cut by one of the fly-cutters that will be described later, but a more accurate and rapid job can be done (and in cramped quarters if necessary) with one of the hand-type chassis punches designed especially for the purpose. Fig. 3 illustrates the two forms in which these are made.

The punch at (a) is operated by hammering the top, *punch*, portion into the lower, *die*, portion (with the chassis in between the two) while the die is resting on an anvil or other solid base. A small guide hole must be

From coast to coast
**SERVICE PROFITS
 ARE GOING UP**

(and operating costs are going down)

thanks to

SAMS PHOTOFACT* FOLDERS

Here's What Servicemen Themselves Say:



- ✓ "Your folders help give the quick service the public wants—good service, too." *Willis, Tex.*
- ✓ "They easily cut my repair work to half the original time." *Chicago, Ill.*
- ✓ "A great time saver—and cheap enough for the small shop owner." *New York City.*
- ✓ "You have what the serviceman has been waiting for all these years." *Richmond, Calif.*
- ✓ "Wouldn't swap my first set for \$100." *Ashtabula, Ohio.*
- ✓ "They make a big cut in non-productive time—especially in servicing new receivers." *Pascagoula, Miss.*

Time is the most valuable commodity you have. Cut down waste operating time and your earnings go up automatically. You, as a good business man, know that.


But maybe you don't know that Sams Radio PhotoFact Folders reduce non-productive service time by as much as 50 percent. The experience of hundreds of servicemen definitely proves that they do! PhotoFact Folders accomplish this because they give *more complete information—faster*—than any other data that has ever been available.

By means of full-page pictures, comprehensive data, voltage and resistance values, etc., they tell you everything you

want to know about radios, phonographs, intercommunication systems and power amplifiers manufactured since January 1, 1946. Released in sets of 30 to 50 folders at a time, they reach you when you need them most—just as the products described reach the market. Yet the cost, including membership in the Howard W. Sams Institute, is only \$1.50 a set. (\$1.75 a set in Canada).

Get Sams PhotoFact Folders working for you! Use the coupon below for Sets No. 5 and 6. To bring your files up to date, order the four preceding sets, too. That way your biggest expense will be behind you. Thereafter it will be an easy matter to pay as you go.

**In Each PHOTOFACT
 Folder You Get—**

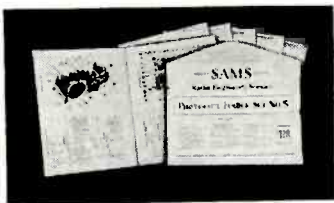

1. A cabinet-view photo of the receiver to help you establish identity and control functions.
2. A top-view photo of chassis and speaker to identify component parts and alignment points.
3. A bottom-view photo of chassis and/or accessories.
4. A complete list giving keyed reference to all parts, alignment and schematic diagram.
5. A complete full page schematic diagram of the receiver with loads of new information shown in a uniform manner.
6. Stage gain measurements listed on the schematic diagram.
7. A complete voltage and resistance analysis chart for rapid check of operational values.
8. Complete alignment instructions on the receiver consistent with the keyed alignment points indicated in top- and bottom-view photos.

PUBLICATION DATES:
 Set No. 5 . . . October 15th
 Set No. 6 . . . October 26th

Cut This Out and Mail It to Your Distributor! If you do not know his name and address, send it directly to Howard W. Sams & Co., Inc., 2924 East Washington Street, Indianapolis 6, Indiana, and we will see that your nearest distributor gets it. (In Canada write to A. C. Simmonds & Sons, 301 King Street East, Toronto, Ontario.)

**CHECK ONE OR MORE SQUARES
 PLEASE PRINT**

- Send Sets No. 5 & 6
- Send Set No. 4 Send Set No. 3
- Send Set No. 2 Send Set No. 1
- Send me a specimen folder

My (check) (money order) (cash) for Sets Nos. (at \$1.50 a set, \$1.75 in Canada) is enclosed. (If you send cash, be sure to use registered mail.)

Name _____
 Address _____
 Zone _____ State _____
 Company Name _____
 My Distributor's Name _____
 City _____

HOWARD W. SAMS & CO., INC. RADIO PHOTOFACT SERVICE

In Canada—write to A. C. SIMMONDS & SONS, 301 King Street East, Toronto, Ontario.


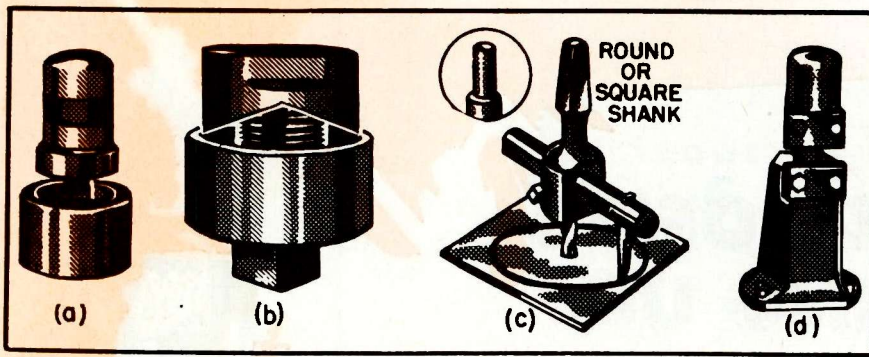


Fig. 3. At (a) and (b) are two types of chassis punches (General Hardware and Greenlee Tool, respectively) for cutting socket holes, etc. In (c) we have an adjustable fly-cutter for cutting larger round holes. (Courtesy Greenlee Tool Co.) In (d) appears a shearing punch for cutting holes of any shape. (Courtesy Insuline Corp. of America.)

Fig. 5 (right). An automatic self-positioning drill case to keep all the twist drills conveniently in one place. (Courtesy General Hardware Mfg. Co.)

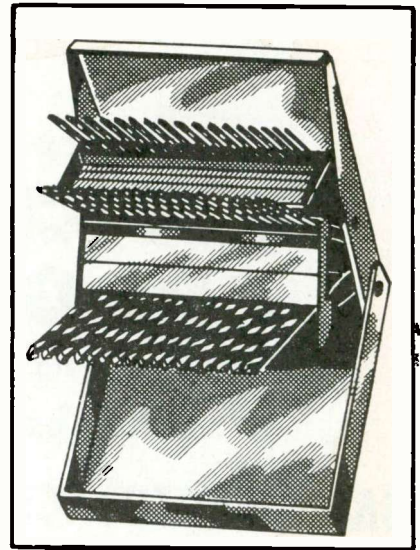

drilled in the chassis first to take the centering pin of the punch.

The screw-type punch works easily and more accurately and may be used more conveniently on assembled chassis. No hammering is necessary. A popular type is illustrated at (b).² The cap screw shown is inserted in a small centering hole previously drilled in the chassis and the shear punch is easily forced into the die by a few turns of the cap screw with an ordinary wrench. Smooth holes, requiring no filing or reaming, can be cut in metal up to $\frac{1}{8}$ " thick in $1\frac{1}{2}$ minutes or less. Ten punches are available for cutting $\frac{3}{4}$ ", $\frac{7}{8}$ ", 1", $1\frac{1}{8}$ ", $1\frac{5}{32}$ ", $1\frac{3}{16}$ ", $1\frac{1}{4}$ ", $1\frac{3}{8}$ ", $1\frac{1}{2}$ " and $2\frac{1}{4}$ " holes.

For cutting round holes of larger diameter, such as would be needed for mounting a flush-mounting meter for example, and for cutting metal, bakelite or fibre, wood, etc., adjustable fly-cutters are very popular. These are made in several types and sizes, the one illustrated at (c) of Fig. 3 being typical. The cutter is equipped with its own twist drill for drilling the pilot hole. The high speed steel cutter carried on the adjustable arm does the cutting. These cutters are made with three styles of twist drill shank: $\frac{5}{16}$ " round shank, $\frac{1}{2}$ " round shank, and square shank, for use in either a

breast drill, bench drill or hand brace. Several sizes are made; one adjustable to cut holes from $\frac{7}{8}$ " to 4" diameter will be about right for most radio uses.

Round holes are not the only kind required. It is often necessary to cut small rectangular holes in chassis for replacement transformers, chokes, etc. These may be cut out by first drilling a hole at each corner and then using a keyhole hacksaw for sawing along the straight sides of the cutout. Or they may be cut out with a cape chisel. In shops where enough of this work is done to make the purchase advisable, the square hole shearing punch illustrated at (d) will be found very useful for doing such work more quickly and accurately. It permits the cutting of any size odd-shape hole (square, rectangular, hexagon, oblong, etc.) on any size panel or chassis.

Die Stock and Dies

Although they are not absolutely necessary, a few dies for the more commonly used machine screw sizes, and a die stock (die holder) to fit them, will form excellent additions, when finances allow. A set of 4-36, 6-32, 8-32 and 10-32 dies is recom-

²Greenlee Tool Co.

mended; Fig. 4 shows a die held in a die stock. They will be useful for cleaning up burred or otherwise damaged threads on machine screws of those sizes, and for other purposes.

The procedure for using dies correctly is similar to that for tapping. The work should be held firmly in a vise, and any burr on the end of the piece to be threaded should first be removed with a file. To start the thread, the *large* side of the opening in the die should be placed over the stock and pressed down on the stock firmly, while turning it clockwise.


Twist Drill Case

For the Service Man who wants to keep a rather complete assortment of twist drills on hand and likes to have them all in one handy place ready for instant selection, a drill case of the type illustrated in Fig. 5 will solve the problem perfectly. A clearly indexed hole of proper size is provided for each drill. The case closes into the form of a compact box that protects the drills and can also be used for taking them on outside jobs. As soon as the cover is lifted, the drills automatically come up into position, the size of each drill being clearly shown by the index, as illustrated.

These drill cases are made in the following sizes: (a) for a set of *number-size* drills from No. 1 to No. 60; (b) for a set of *fractional-size* drills from $\frac{1}{16}$ " to $\frac{1}{2}$ "; and (c) for a set of *letter-size* drills from A to Z. The cases may be purchased from your hardware dealer. They are available either empty, with the complete set of drills, or with any particular drills you may select. No more fumbling in tool-filled drawers or tool boxes for the drill you want to use when you own one of these drill boxes.

Fig. 4. A small stock and several removable dies of different sizes that fit into it. These are useful for threading rods or cleaning up damaged threads or screws.



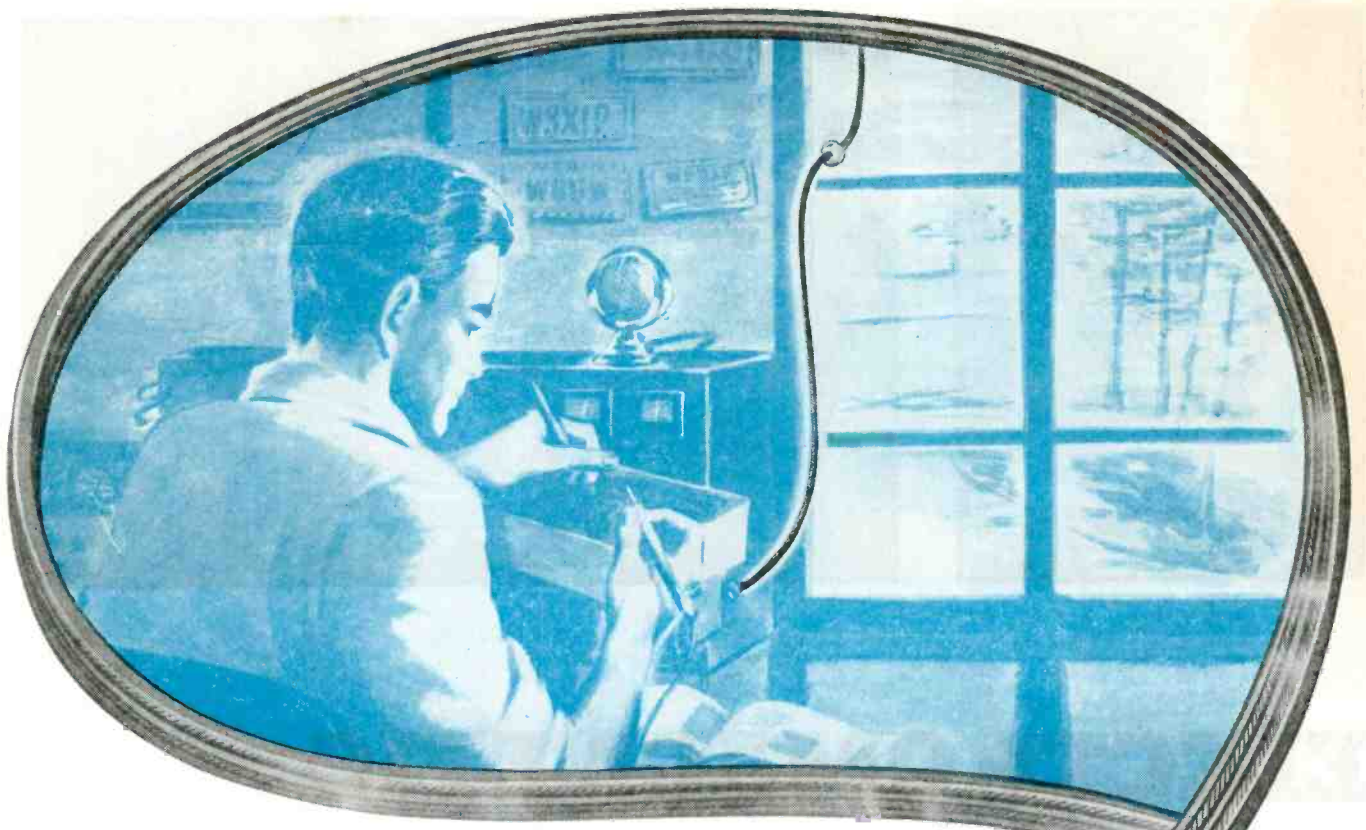

Amphenol AND RADIO AMATEURS HAVE ALWAYS WORKED TOGETHER

Radio amateurs are the most versatile technical experimenters known—and so are Amphenol engineers. Amateurs have pioneered the greatest share of electronic developments since the dawn of radio—and Amphenol has pioneered in the development of components used by hams.

Amateurs have an appreciation of the electrical engineering problems in the production of components to give the best performance. They agree that Twin-Lead, pioneered by Amphenol, is one of the most important and useful new products in the field of electronics.



AMERICAN PHENOLIC CORPORATION

CHICAGO 50, ILLINOIS

In Canada • Amphenol Limited • Toronto, Ontario

COAXIAL CABLES AND CONNECTORS • INDUSTRIAL CONNECTORS, FITTINGS AND CONDUIT • ANTENNAS • RF COMPONENTS • PLASTICS FOR ELECTRONICS



ACTUAL SIZE CROSS SECTION

75 OHM TRANSMITTING TWIN-LEAD

Amateurs asked for it — now here it is! It's the new heavy duty 75 ohm Amphenol Twin-Lead transmission line. Conservatively rated at 1000 watts for 30 mc or lower frequency. Available — now — at your distributor's.

Attenuation	Megacycles	75 ohm DB per 100 ft.	
		3.5	0.29
}	7.0	0.49	
	14.0	0.82	
	28.0	1.40	

Receiving Twin-Lead is available in 75 ohm, 150 ohm and 300 ohm impedances. Get a copy of Amphenol's new Twin-Lead bulletin from your dealer.

Other Amphenol products of interest to amateurs available at your dealer's:

Radio Tube Sockets. Industrial, standard, miniature and sub-miniature—plugs and accessories. Octal angle sockets for cathode ray applications.

Connectors. All types, with fittings — from 1 to 50 contacts.

Cables. Coax and Twinax (also connectors). Microphone cables (also connectors).

Plastics for Electronics. Plastic sheets, rods and tubes. Flexible tubing and spaghetti. Coil Dope. Molded coil forms, stand-off insulators, knobs and dial pieces.

Antennas. UHF dipoles and arrays.

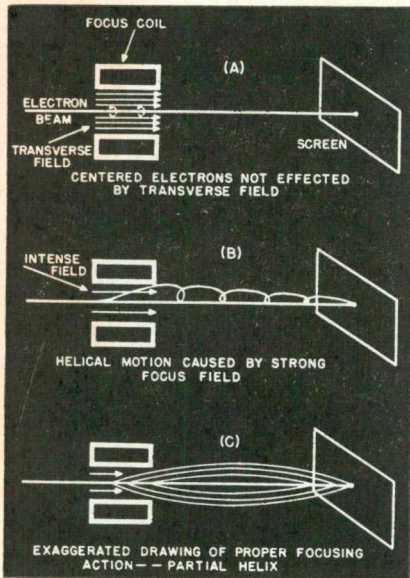


Fig. 2. Analysis of magnetic focusing.

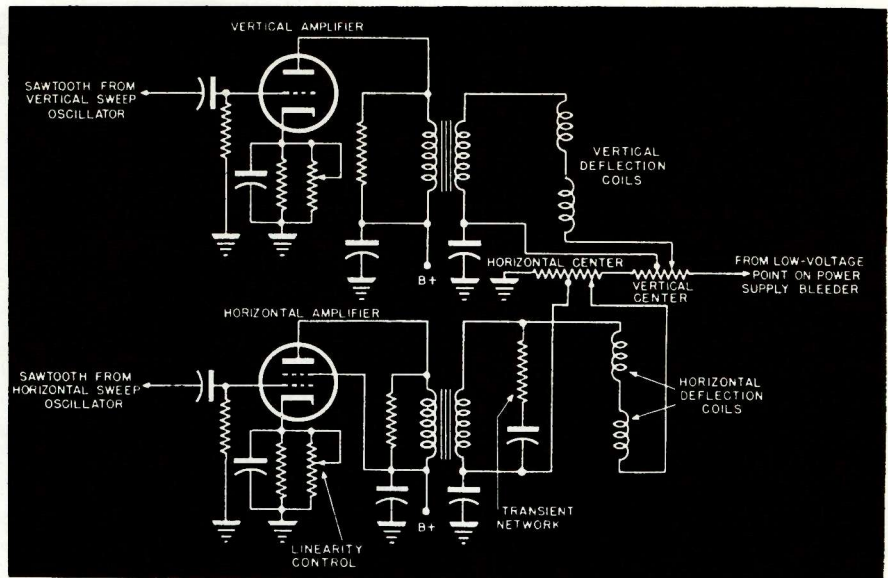


Fig. 1. Television receiver deflection amplifier.

ELECTROMAGNETIC DEFLECTION SYSTEMS In Television Receivers

by EDWARD M. NOLL

[Part II]

SO THAT WE MAY trace the horizontal and vertical deflection paths in a typical television receiver, the circuit shown in Fig. 1 is offered.

In the electromagnetic deflection amplifier the output is transformer-coupled to the deflection coils. Inasmuch as an appreciable current must flow through the coils, the amplifier is considered to be a power amplifier similar to the audio power amplifier which drives a speaker. A small variable d-c current is used for proper centering. This current is obtained by tapping across two small resistors which are inserted across the low-potential end of the low-voltage power supply.

In the cathode circuits of these amplifiers are special linearity networks which correct the small curvature still present on the sawtooth waveform. The waveform is made more linear by biasing the deflection amplifier to a non-linear portion of its characteristic. This bias must be precisely set at the proper point on the transfer characteristic to compensate for the non-linearity of the sweep waveform applied to the grid. The opposite curvature of


the characteristic produces a linear change in plate current as the sawtooth voltage rises and, therefore, a linear sweep.

Still another defect arising particularly in the horizontal sweep amplifier, which causes distortion of the waveform, are high-voltage transients. Since the horizontal sweep consists of its high fundamental frequency plus frequency components up to at least the tenth harmonic, the reactance of transformer windings and deflection coil is very high. Consequently, high-transient voltages are developed across the reactances, particularly at the start of the horizontal retrace when the change in current is very fast. These voltages often shock-excite the windings into a series of damped oscillations which modulate the sweep. To prevent high voltage transients, the secondary of the horizontal output transformer and horizontal deflections

coils are shunted by a low-value resistor combination which load the inductors heavily at high frequencies. Thus the fast retrace currents are shunted off through the resistors and do not develop transients across the high inductive reactances.

The horizontal deflection transformers and circuits must have a frequency response reasonably linear up to 150,000 cycles. Transformers must be carefully constructed to have such a high frequency response with a minimum of self-resonant tendencies. The vertical deflection amplifier is of much lower frequency and not so critical of design. The vertical sawtooth is also of greater amplitude as applied to the grid of the vertical amplifier and, consequently, a low-impedance triode has sufficient gain to develop the required current variation through the vertical deflection coils. An added advantage

(Continued on page 45)

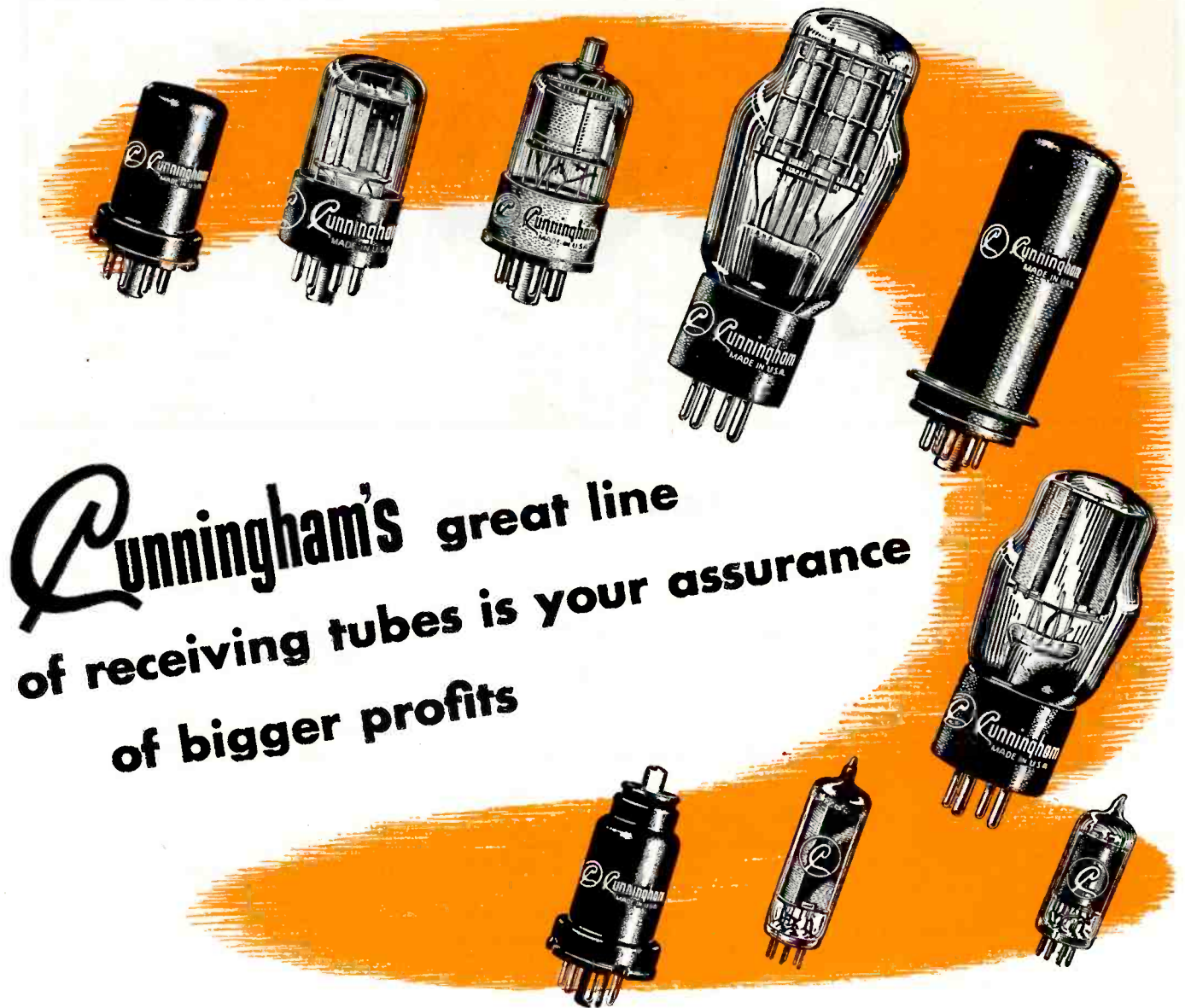


Cunningham's great line
of receiving tubes is your assurance
of bigger profits

CUNNINGHAM'S line of metal, glass, and miniature receiving tubes meets practically every service requirement. With Cunningham tubes you won't need to carry additional lines to round out your stock—and you'll seldom have to turn away a customer.

And you can be sure that Cunningham has or will have the right type tubes for the new AM, FM, and television receivers


that are on the way—because Cunningham is backed by the engineering leadership of the Radio Corporation of America.

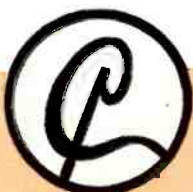Remember, too, that Cunningham Electron Tubes are *built for service*. They've been famous for over 30 years for their *consistently* high quality, long life, and top performance. That's why customers look for the big "C" in your store window when they need new tubes.



LISTEN TO "THE RCA SHOW," SUNDAYS, 2:00 P. M., EST, NBC NETWORK

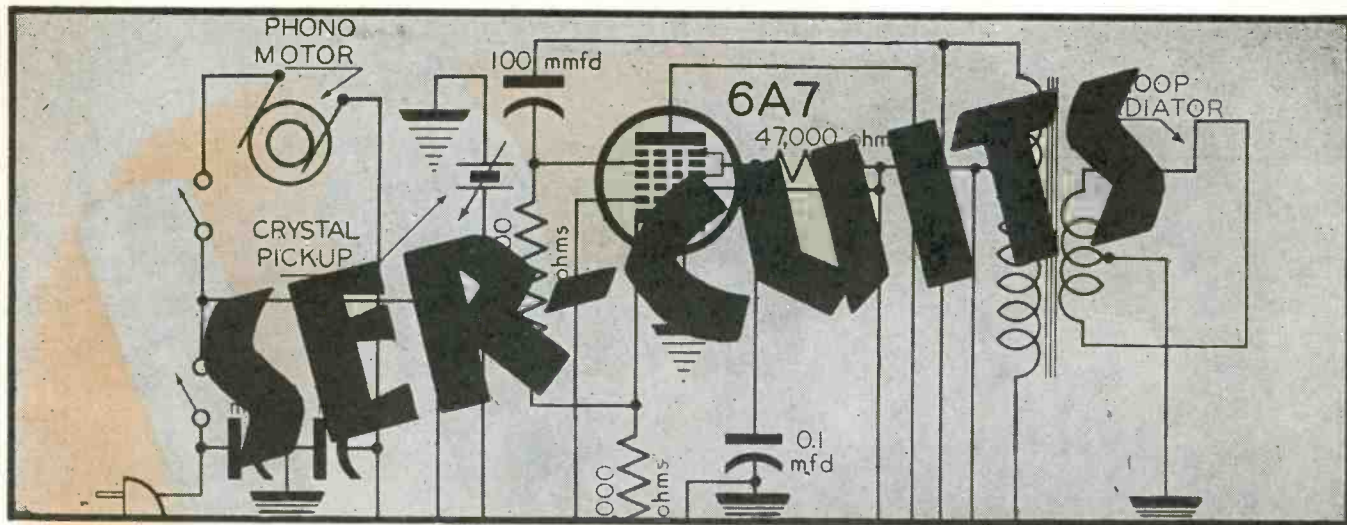**A QUALITY PRODUCT FOR RADIO SERVICEMEN
AND DEALERS BY THE RADIO CORPORATION OF AMERICA**



IN RESPONSE TO MANY REQUESTS, we offer additional data on portable and farm-type receivers this month.

by HENRY HOWARD

Admiral 4A1

An interesting permeability-tuned type portable Admiral 4A1, is shown in Fig. 1. An external antenna is capacity coupled to the input circuit in a manner similar to Belmont 4B17, but the values differ considerably, a .005-mfd capacitor appearing across a 250-mmfd capacitor giving much tighter coupling. The antenna shunting resistor is 15,000 ohms and the avc filter resistor, 470,000 ohms.

An ultraudion oscillator circuit is used with the oscillator grid at one end of the single coil and the plate grid at the other. A trimmer is connected from the grid end to ground; 250 mmfd from the plate end to ground. An r-f choke in the B supply completely isolates the 1A7 from the remainder of the set. Bias for the i-f amplifier is obtained from a 4.7-megohm grid leak. Only the 1A7 receives avc bias. An economizer switch located on the top of the

chassis inserts a wirewound .75-ohm resistor in series with the positive leg of the A battery. It is labeled *New Battery* in the open position (resistor in the circuit) and *Old Battery* in the closed position.

Zenith 4K016-4K035

Fig 2 shows another 4-tube battery set with external antenna, Zenith models 4K016-4K035, chasses 4C52-4C53. Equal avc bias is supplied to a 1A7 converter and 1N5 i-f amplifier. The power amplifier is a 1C5 instead of the usual 3Q5. The C bias resistor is 820 ohms.


Crosley 56FA

A 5-tube, 2-band farm-type receiver, Crosley models 56FA, 56FB, is shown in Fig. 3. A 1N5 t-r-f ampli-

fier is used on the broadcast band only. The waveband switch connects the signal grid of a 1A7 to the inter-stage transformer for broadcast or to the secondary of the short-wave antenna transformer and oscillator grid from broadcast to the short-wave oscillator coil. Switch also connects a 480-mmfd padder in series with the oscillator tuning capacitor; shorts secondary of the broadcast antenna transformer for short waves and bypasses the broadcast feedback coil for short waves. The 1N5 i-f works into an iron core output i-f transformer. In a 1H5 detector-avc-audio circuit we have an unusual avc and detector load arrangement. The load consists of 150,000 ohms in series with a 1-megohm volume control, in series with 3300 ohms. The latter prevents turning the volume completely off with the set turned on, thus saving many a battery.

The avc system operates through a

Fig. 1. Portable, Admiral 4A1, using an ultra-udion oscillator circuit. List of parts at right.

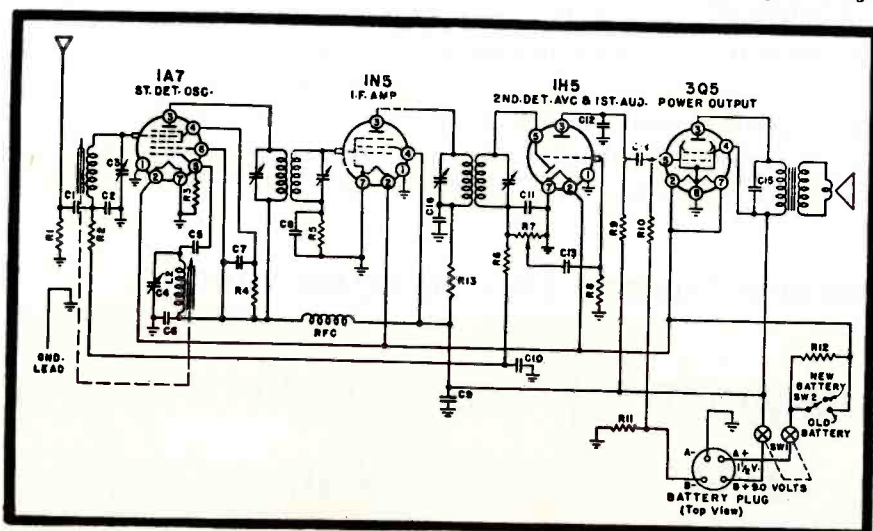

CONDENSERS

Symbol	Description
C15	.002 mfd. 600 Volt
C1, C7	.005 mfd. 600 Volt
C10	.01 mfd. 400 Volt
C5	.05 mfd. 200 Volt
C11, C12	.0001 mfd.
C2, C6	.00025 mfd.
C8	.0008 mfd.
C9	4. mfd. 150 Volt
C3, C4	Dual trimmer
C13, C16	.01 mfd. 400 Volt

RESISTORS

R12	.75 ohm ¼ w (wire)
R11	390. ohm ¼ w
R13	2200 ohm ¼ w
R1	15,000 ohm ½ w
R4	33,000 ohm ½ w
R3	220,000 ohm ½ w
R2	470,000 ohm ¼ w
R9, R10	1,000,000 ohm ¼ w
R6	2,200,000 ohm ¼ w
R5, R8	4,700,000 ohm ¼ w

10-megohm resistor to the i-f and r-f stages and through another 100,000 ohms to the converter on the broadcast band only. On short waves, the converter is biased solely by a 3.3-megohm leak bypassed by 600-mmf capacitor. The avc bus is shunted to ground through a 4.7-megohm leak. Bias for the 1L4 power amplifier is obtained from a 1000-ohm resistor in the B— lead. The B supply is bypassed by a 15-mfd capacitor, and an additional isolation filter of 4700 ohms and 15 mfd serves the 1A7 plate and oscillator circuits and the 1N5 and 1A7 screens.

Zenith 6G001

Another 3-gang 5-tube battery model, Zenith 6G001, using lock-in tubes, is shown in Fig. 4. A 1LN5 r-f amplifier has a 2.2-megohm resistor for bias and 22,000 ohms in series with the primary of the interstage transformer. A 1LA6 converter is tapped down on the secondary of this transformer, giving higher Q and sharper tuning. A tickler feedback oscillator uses a grid capacity winding with 220 ohms in series.

DeWald A500 Series

DeWald 4-tube and rectifier models,

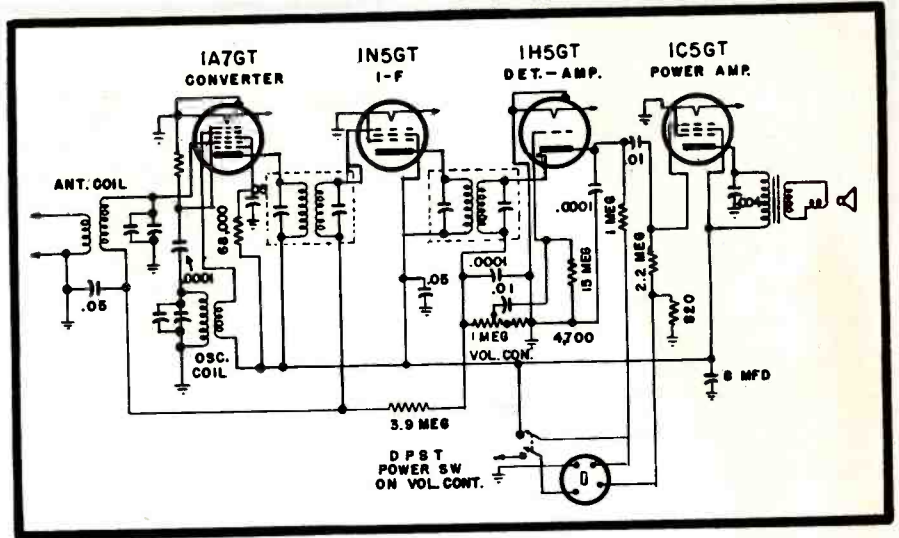


Fig. 2. A 4-tube battery set using an external antenna, Zenith models 4K016-4K035.


A500 to A503, are shown in Fig. 5. Many interesting fundamental circuit requirements have been met in these models. An antenna-resistor and capacitor has been included to eliminate resonance in the antenna. Thus i-f or image interference is minimized. The

capacitor also prevents connection of the antenna to the line plug. In the i-f stages one bypass is placed across the detector load resistor which is also the volume control. A-f blocking capacitors and suitable grid leak bias are used for the 12SQ7. A 150-ohm cathode bias is in the 50L6 circuit.

Other Circuit Features

The filament string has a 35Z5 pilot lamp and an 18-ohm surge resistor. A dual 30-mfd and 2,700 ohms for filter

Fig. 3. A 5-tube, 2-band farm-type receiver, Crosley 56FA and 56FB.

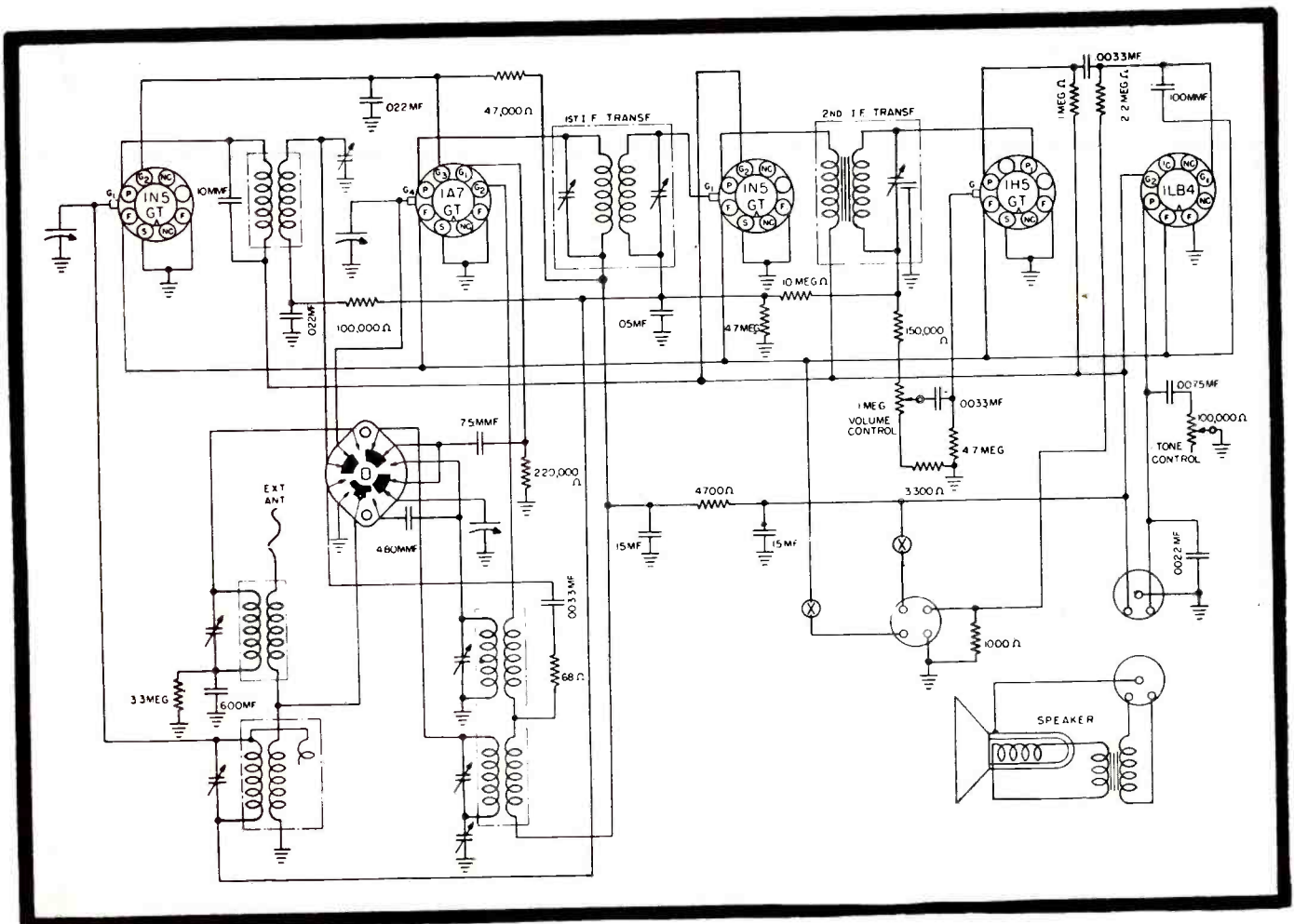


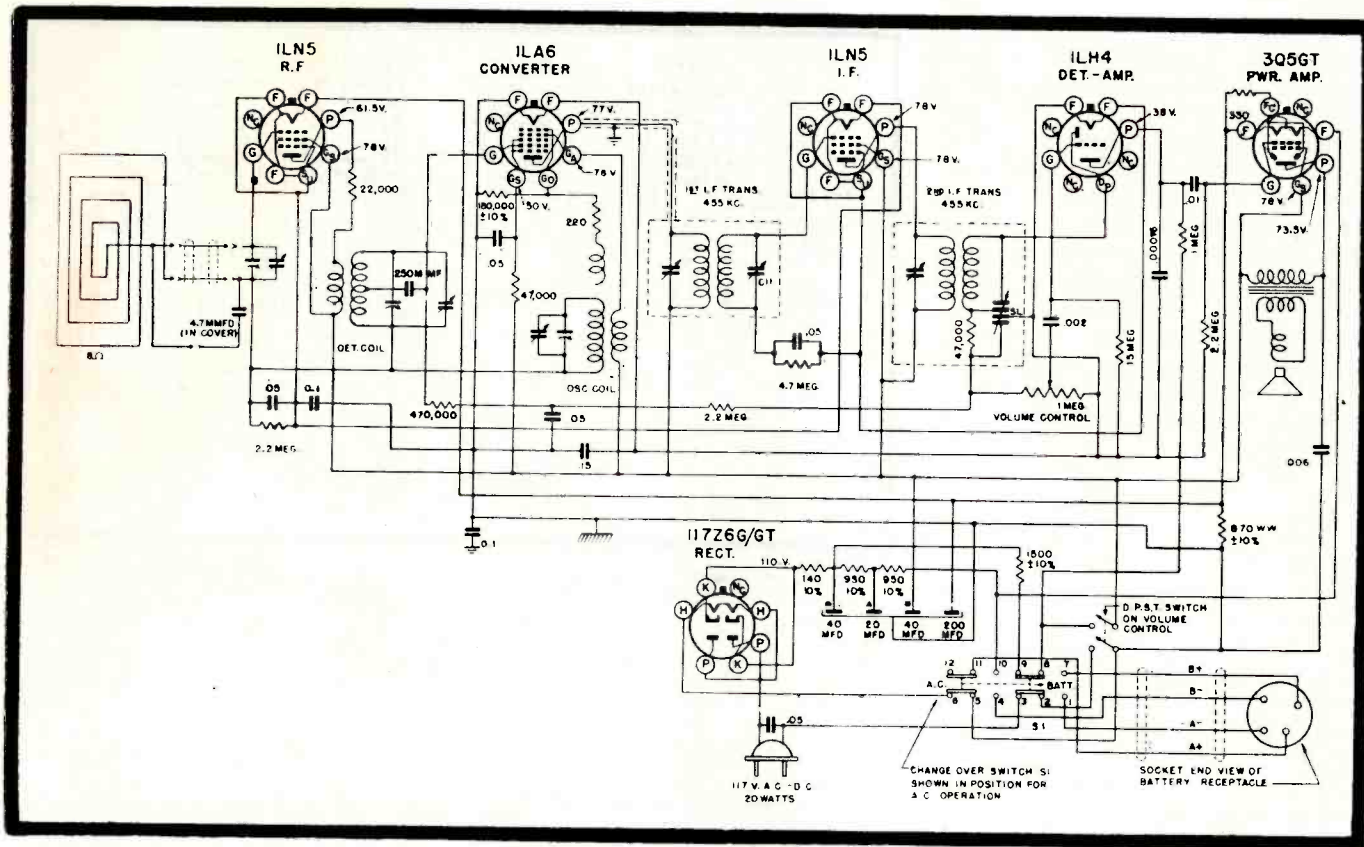


Fig. 4. A 3-gang 5-tube battery a-c/d-c model using lock-in type tubes, Zenith 6G001.

are also included. A .05-mfd r-f bypass is connected across the filter output. This is an important capacitor, for as the electrolytic capacitor dries up and the resistance increases, feed-

back through the supply, producing oscillation, may result. This capacitor prevents this possibility. To prevent modulation hum, a .05-mfd capacitor is connected to chassis.

Fig. 5. DeWald 4-tube and rectifier, A500 and A503, with an antenna resistor and capacitor to eliminate antenna resonance and minimize i-f or image interference.

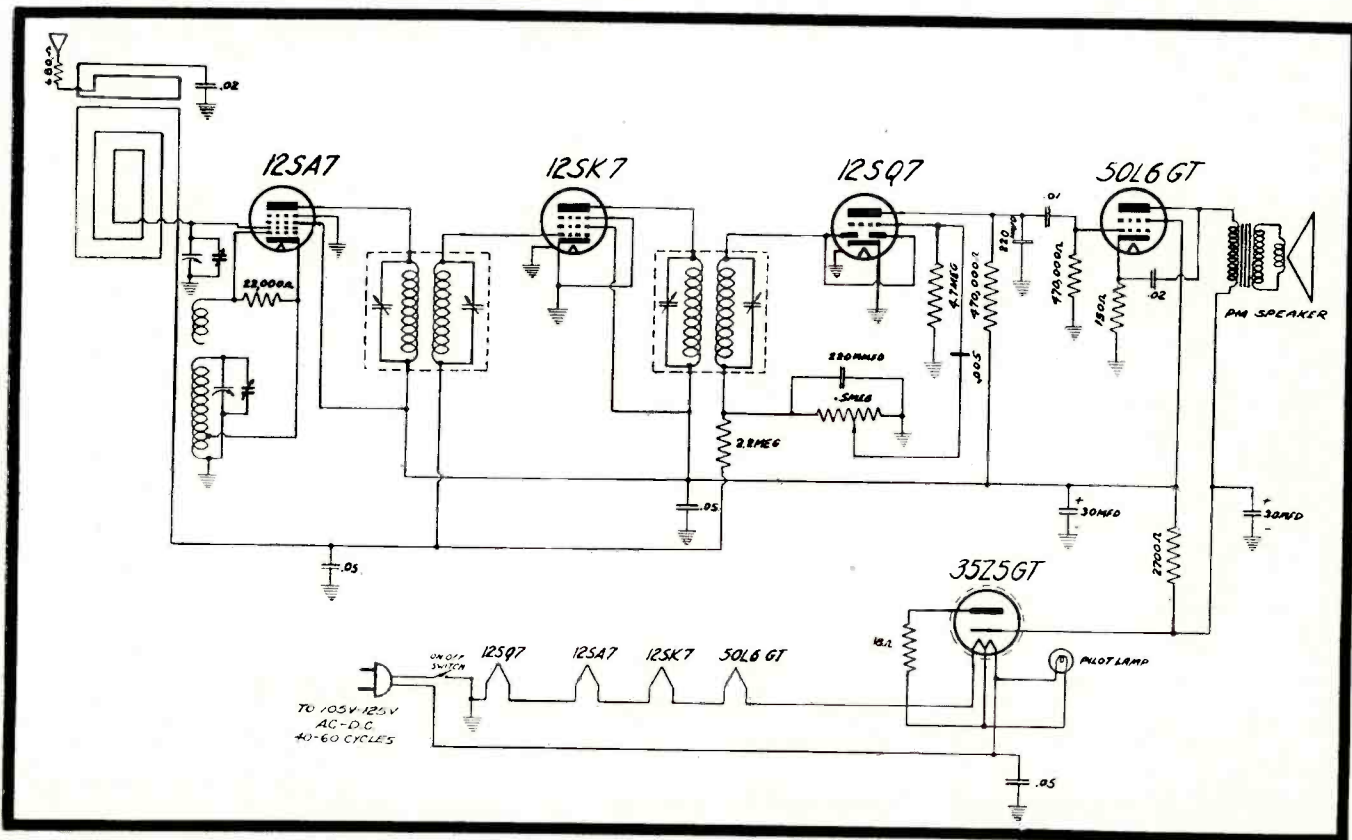


**29 DIFFERENT
RECTIFIER TUBES**

Now Replaceable

WITH THE FEDERAL SELENIUM RECTIFIER

(No. 403D2625)

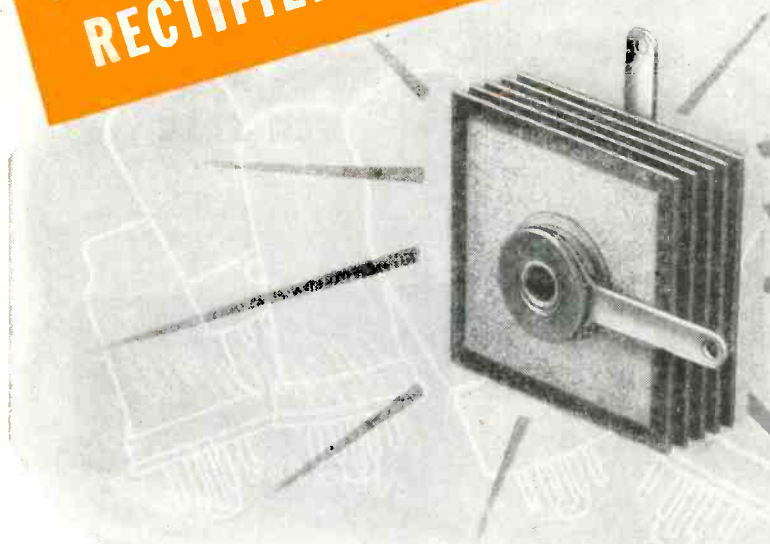

IT'S SMALLER...

COSTS LESS...

LASTS LONGER...

RUNS COOLER...

READILY INSTALLED!

-FIRST OF ITS KIND IN THE INDUSTRY!

NO less than *twenty-nine* different types of rectifier tubes are now replaceable with Federal's new, miniature, 5-plate rectifier. Available now, this replacement is also an *improvement!* For not only does it subtract from your own manufacturing costs, it adds to product quality as well... and to consumer satisfaction. Here's how:

- Saves space — only 1¼ x 1¼ x 11/16 inches — fits where tube won't
- Costs less than tube and socket it eliminates
- Long life — built to last the life of the set
- No warm-up period — starts instantly, runs cooler
- Installed in less time than tube — only two soldering jobs
- Sturdy, all-metal construction — not easily damaged
- Withstands overloads — even when charging deformed electrolytic condensers

Every one of Federal's line of "Center Contact" Selenium rectifiers is designed to give the full measure of performance that have made them the standard of the industry. A Federal engineer will show you how to put this latest model into your circuits. Write for details to Department F456.

Replacement for these Tubes:

5T4	5Y3	6Y5	25Z6	50Y6
5U4	5Y4	6Z5	35W4	50Z7
5V4	5Z4	12Z5	35Z3	117Z3
5Z3	6X5	7Y4	35Z4	117Z6
5W4	0Z4	12Z3	35Z5	0Y4
5X4	80	35Z5	35Z6	

Electrical Characteristics:

Maximum RMS Voltage	130 Volts
Maximum Inverse Voltage	380 Volts
Maximum Peak Current	1200 ma.
Maximum RMS Current	325 ma.
Maximum DC Output	100 ma.
Approximate Rectifier Drop	5 Volts

Two Federal Miniature Rectifiers in a voltage doubler circuit give 250 volts and 80 milliamperes output from 117 volt AC power source.

Federal Telephone and Radio Corporation

In Canada:—Federal Electric Manufacturing Company, Ltd., Montreal
Export Distributor:—International Standard Electric Corporation, 67 Broad St., N. Y. C.




Newark 1,
New Jersey

METROPOLITAN

Announces for the first time!

B-45 SIGNAL GENERATOR

Available
NOW
for
Immediate
Delivery!

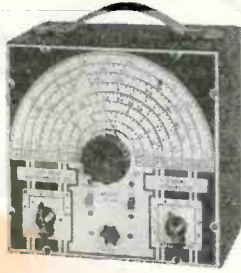


Self-modulated Signal Generator, providing a highly stable signal. Generates R.F. frequencies from 150 Kilocycles to 50 Megacycles (150 Kc. to 12.5 Mc. on Fundamentals and from 11 Mc. to 50 Mc. on Harmonics). R.F. is obtainable separately or modulated by the Audio Frequency.

Television and F.M. as well as A.M. receivers can now be speedily aligned. Modulation in the B-45 is accomplished by Grid-blocking action which has proven to be equally effective for alignment of amplitude and frequency modulation as well as for television receivers.

The R.F. Signal Frequency is kept completely constant at all output levels. This is accomplished by use of a special grid loaded circuit which provides a constant load on the oscillatory circuit. A grounded plate oscillator is used for additional frequency stability. The Model B-45 is truly portable—no external source of current required. Operates on self-contained batteries.

Direct reading—all calibrations are etched on the front panel. Complete with shielded test lead, self-contained batteries \$27.75 and instructions. Net

New Model 670 SUPERIOR SUPER-METER

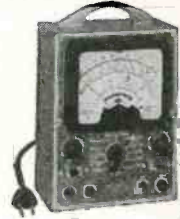

A Combination Volt-Ohm milliammeter plus capacity reactance inductance and decibel measurements. Includes a special good-bad scale for checking the

quality of electrolytic condensers at a test potential of 150 volts. Complete with test leads and operating instructions. Net

\$28.40

New Model 450 SUPERIOR TUBE TESTER



"Speedy Operation" assured by newly designed rotary selector switch which replaces the usual snap toggle or lever action switches.

Tests all tubes up to 117 volts, including 4, 5, 6, 7, 7L, Octals, Loctals, Bantam Junior, Peanut, Television, Magic Eye, Hearing Aid, Thyratrons, Single Ended, Floating Filament, Mercury Vapor Rectifiers, etc. Also Pilot Lights. Net.....

\$39.50

Write Dept. SE for FREE New 1947 Catalog!

Metropolitan
ELECTRONIC & INSTRUMENT CO.
Dept. SE 6 MURRAY STREET
NEW YORK 7, N. Y., U. S. A.
Phone: BArcly 7-5556
Cable Address: METRONICS

Balanced-Loop Receiver

(See Front Cover)

BALANCED LOOP-ANTENNAS, described a few months ago in Ser-Cuits, have become a design feature of many receivers. In the circuit shown on the cover this month appears a balanced-loop application for the Stewart-Warner 9014-E model. The loop is tuned indirectly through a close-coupled iron-core transformer which feeds a 12SK7 tuned r-f amplifier. The loop center tap is grounded to the avc bus, minimizing hum pickup. The external antenna feeds the loop primary and short-wave primary in series. The r-f stage, used on b-c only, uses a 390-ohm bias resistor without by pass. An interstage r-f transformer operates at a high Q by virtue of a reduced loading secondary tap for the 12SA7 signal grid (3). The tuning capacitor is connected across the entire secondary. On s-w, the signal grid is switched to the short-wave transformer, eliminating the r-f stage entirely. The tuning capacitor is connected in series with 315 mmfd to limit the tuning range.

A tuned-grid cathode-feedback oscillator is used with a grounded plate (screen grid) on both b-c and s-w, the grid and cathode being switched from one oscillator to the other. Unused coils are left open.

The i-f amplifier uses a 12SF7 with a 47-ohm cathode resistor and conventional transformers. The diode detector-avc bus is biased slightly positive through the detector-load resistance to the 12SK7 audio cathode by the RI drop in the 2,200-ohm cathode bias resistor. The load resistance consists of 47,000 ohms in series with a 1/2-megohm volume control. A tone control shunts the volume control with a .0008-mfd capacitor. The first a-f amplifier is unusual in several ways. First, it has a remote cut-off pentode. In addition the potentials of the elements and circuit constants are quite unique. There is, for instance, a 2.2 megohm screen-supply resistor. Degenerative feedback from voice coil to screen is provided by a .02-mfd capacitor which also serves as a supply by-pass. A separate supply filter in the plate supply consists of 220,000 ohms and .05 mfd. The plate load resistor is also 220,000 ohms.

A 35L6 output stage operates into a tapped output transformer with the B load of the remainder of the receiver tied to the other end.

NEWCOMB JOBBERS LEAD THE FIELD IN PROFITS SELLING THE FINEST EQUIPMENT MADE TODAY

**AMERICA'S
TOP QUALITY
AMPLIFIER
WILL GIVE
YOU
MORE PROFIT
PER SALE**

A sound rule for increasing jobber profits will be sent to you upon request. Write for free booklet.


Newcomb
AUDIO PRODUCTS CO.

2815 So. Hill Street, Dept E
Los Angeles 7, California

SENSATIONAL

**TRIPLITT
TUBE TESTER
ATTACHMENT
For Ease in Testing**

FOR TUBE TESTER
MODELS 2425 AND 2413

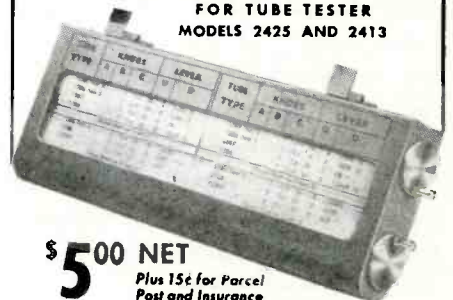


\$5.00 NET

Plus 15c for Parcel
Post and Insurance
DELIVERY AT ONCE!

Sensational! . . . New! . . . An external roll chart in a streamlined case. Quickly attached to tester case. Chart fits in carrying compartment in tester cover when not in use. Has all the advantages of a book chart in adding new data. Replacement charts available to cover new tubes at minimum charge. Handy for checking tube stocks. Order at once!

**RADIO
RADIO SUPPLY &
ENGINEERING CO., Inc.**
126 SELDEN AVE. DETROIT 1, MICH.

SERVICE AIDS

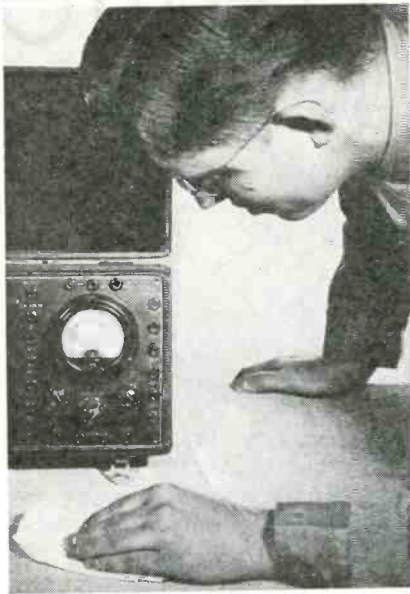

Removing Meter Face Static Charges. When polishing the glass face of sensitive meters the pointer will often move over a portion of the scale and appear to remain at a certain position. This is caused by a static charge being developed by rubbing the cloth over the glass. The charge may be neutralized by blowing one's breath on the dial face of the meter and the pointer will return to its original position.



Loop in Cover of Tester As Antenna. A small loop attached to the lid of a test unit with tape makes a convenient antenna for test purposes. As shown a test lead is connected from one terminal of the loop to the antenna post of the receiver, in which case the loop is used as a single wire antenna. It also may be easily connected in place of regular loop.



Light to Simplify Repairs. When soldering parts in dark places it is difficult to hold solder, iron and a lamp. A strip of solder wrapped around a pen lamp will solve the problem, the lamp guiding the solder to the desired point. This leaves the one hand free to apply the soldering iron.



MAKES 90 OUT OF 100 RADIO TROUBLES Easy to Repair!

Complete, Easy Instructions for Repairing Common Troubles in Practically Every Model and Make of Radio in Use Today

Eliminates Needless Testing — Enables You to Repair Two Radios in the Time Ordinarily Required for One

PAYS FOR ITSELF ON THE FIRST JOB!


TELLS WHAT TO DO EXACTLY HOW TO DO IT

As valuable to a radio repair man as a recipe book is to a cook!

\$5

What's wrong with the radio you want to repair? A defective transformer? Wiring insulation trouble? A faulty capacitor or resistor? Don't guess! Don't waste time in needless, tedious testing! Just look up that particular make and model in Ghirardi's famous **RADIO TROUBLESHOOTER'S HANDBOOK**. Nine times out of ten, this big book will tell you exactly what is wrong—and exactly how to repair it. You don't have to be an expert to use the **HANDBOOK**—and there's no better way of getting invaluable, practical service training. Over 400 pages are chock-full of this factual Case History repair data on over 4,800 receivers, auto radios and record changers of 202 different manufacturers—practically every radio set in use today! Over 300 additional pages contain hundreds of repair charts, tube charts, data on tuning alignment, transformer troubles, tube and parts substitution data, color codes—all designed to help you repair any radio ever made **EASIER, BETTER and FASTER**. Ideal for either busy service shops or for beginners. Only \$5 complete — on our 5-Day Money-back Guarantee basis.

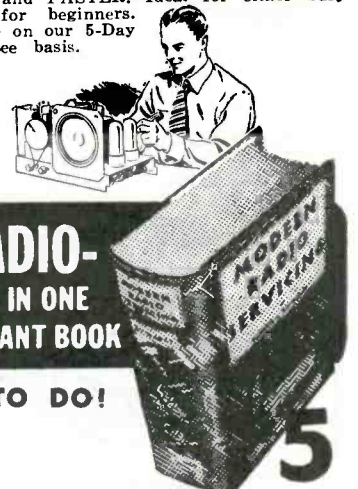Ghirardi's RADIO TROUBLESHOOTER'S HANDBOOK (above) is the ideal book to have on hand for training new helpers, repairing either cheap or expensive sets quickly and profitably, eliminating needless test time and equipment—and MAKING MORE MONEY.



ALL THE SCIENCE OF RADIO-ELECTRONIC SERVICING IN ONE GIANT BOOK

MAKES COMPLICATED JOBS EASY TO DO!

Alfred A. Ghirardi's **MODERN RADIO SERVICING** gives you a **COMPLETE, MODERN EDUCATION** in truly professional radio-electronic service methods of the kind that will be your "Open, sesame!" to the big-money opportunities that only well-trained servicemen are in a position to grasp. It is a complete, scientific servicing course from A to Z. You'll be surprised how easily understandable it makes every phase of the work even if you have had no previous service training. And, if you are already in the business, you'll be pleased to learn how this big 1300-page book will serve as a "refresher" course. Not only will it help you handle repair jobs quicker, better and more profitably, but it also will give you the necessary basic training to equip you for profitable industrial electronic work. Specifically written and designed for home study. 1300 pages; 706 clear illustrations. 720 Self-Test Review Questions make it easy for you to check your progress every step of the way. Fully indexed. Only \$5 on our famous 5-Day Money-back Guarantee.

ENDORSED BY EXPERTS EVERYWHERE

From beginning to end, **MODERN RADIO SERVICING** brings you the kind of modern professional "Know How" that will pay big dividends for years to come. Gives complete data on test instruments and their use, preliminary trouble checks, scientific circuit analysis and trouble-shooting, parts repair and substitution, how to start and operate a successful service business and many other subjects.

MONEY-BACK GUARANTEE

MURRAY HILL BOOKS, Inc., Dept. S-106, 232 Madison Ave., New York 16, N. Y.

- Enclosed find \$..... for books checked; or send C.O.D. (U.S.A. only) for this amount plus postage. I may return the books for refund within 5 days if not fully satisfied.
- RADIO TROUBLESHOOTER'S HANDBOOK \$5** (\$5.50 foreign)
- MODERN RADIO SERVICING \$5** (\$5.50 foreign)
- MONEY-SAVING COMBINATION OFFER:** Both of the above big books, only \$9.50 (\$10.50 foreign)

Name

Address

City & Dist. No. State

SPECIAL OFFER!

Let RADIO TROUBLESHOOTER'S HANDBOOK save you time on common service jobs! Let MODERN RADIO SERVICING train you for complete professional, electronic work. Get BOTH BIG BOOKS at the special price of only \$9.50 for the two. Send coupon today!

**WE SHIP ANYWHERE
IN THE WORLD**

*Internationally
Famous*

**FLANAGAN RADIO
CORP.**

RADIO TUBES



**SEND FOR
COMPLETE
LIST OF
AVAILABLE
RADIO TUBES
AND PRICES**

**CRYSTAL
PICKUPS**




\$219
each

**COMPLETE WITH
HARDWARE
LATEST DATE OF
MANUFACTURE**

CHANGERAK

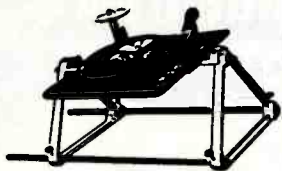Makes an ideal work and display fixture for selling new Record Changers. All new combination sets are now being made with Record Changers. Cash in on this business. Order your CHANGERAK now!



\$11.95

FREE CATALOG

Send for free catalog and prices of hard-to-get Radios, Radio Tubes, Radio Parts, Pickups, Motors, Condensers, Tube Checkers, Volt and Ohm Meters, Signal Generators, Signal Tracers, etc. Please mention Service when writing.

**FLANAGAN
RADIO CORP.**

Phila.'s Largest Stock of Radio Tubes
N. E. Cor. 7th & Chestnut Sts.
Phila. 6, Penna.—U. S. A.


NEW MODELS




U. S. Television projection-type television receiver providing a 16" x 21" image.



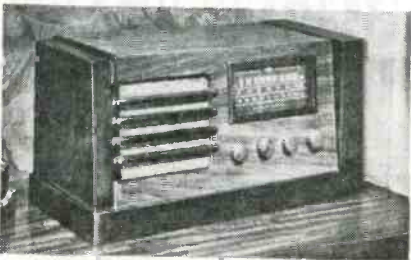Emerson model 512 a-c/d-c model with a built-in loop.



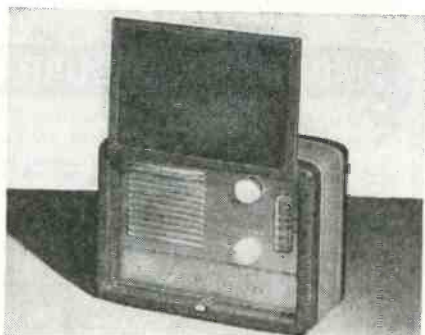Stewart-Warner 9013-A five-tube three-band a-c receiver designed for the export market. Bands covered are: 530 to 1650 kc; 2 to 7 mc and 7 to 22.2 mc.



Garod 5D s-o/d-c battery 5-tube miniature, three-way portable. Loop antenna in front-raising lid. Alnico V p-m speaker.

**name
PLEASE:**



Are you on the mailing list for our bulletins and catalogs? If not, you ought to be. We've probably got just what you want in parts, or complete rigs, and our prices are shaved paper-thin. So send us a note or post card. Keep smart company.

LAFAYETTE

Radio

RADIO WIRE TELEVISION, INC.

DEPT. FJ-8, 100 6TH AVE., NEW YORK 13, N. Y.
110 FEDERAL STREET, BOSTON 10, MASS.
24 CENTRAL AVENUE, NEWARK 2, N. J.

At Last!

A PRACTICAL

RADIO

MERCHANDISING

PLAN

*for Service
Engineers*

SEE BACK COVER



OLD TIMER'S CORNER

by **SERVICER**

DROPPED INTO PAUL'S MODERN and well-stocked radio and electronic shop the other evening and found him in a very blue mood. I knew it could not be the store and its contents which were worrying him, because of all the shops in our town, his was the best stocked. He had the same sales personnel he always had; and Paul was in the habit of making a pretty penny each year, as his income tax payments attested. So it was with considerable curiosity that I asked Paul to tell me what was the matter.

"Well," he said sorrowfully, "I have *prize trouble*."

Wha. do you mean by *prize trouble*?" I rejoined.

"Well, last week a member of the Ladies Evening Society came in and asked me to contribute to their affair. I refused because I have been consistently victimized and because I felt there was not much good to be achieved from their Society.

"Today I find that I sent a refrigerator to one of the Society members on approval, for testing, against a well-known gas model, and she has returned it with the statement that if I can't help her Society, I can't sell her anything. And that's not all. I have been told by a number of my better customers that they know all about my refusing their Society and that they will govern themselves accordingly.

"In the past five years I have given to each and every organization that came along. They have had all sorts of prizes from me, without charge. I never learned the names of the winners, except by accident, and I finally got the idea that this was just a polite form of blackmail, and that I would have no more of it. Then, with the first refusal, this happened," he ended sorrowfully.

"Looks like you're in a pickle," I said, "but wouldn't you be interested in contributing to various affairs if you knew you could turn the gift into a nice selling campaign?"

"I've thought about that," Paul replied, "but I haven't been able to hit on any particular way that I could turn the award into more business. If I could get a bit of publicity or advertising out of the gift, beyond having my name appear on the program of the affair, and having it read over the loudspeaker at the shindig, I would reconsider the whole thing.

"It's not that I begrudge giving something which may be worth anywhere up to \$25, but I do resent the pressure put upon me that if I don't give, I'll be made to suffer. That I can't stand; it goes against my grain!" Paul declared.

"Well," I said, "if that's all that's

(Continued on page 32)



SERVICE men and others concerned with the repair, improvement or modernization of existing phonograph equipment, will be interested in Astatic's line of Crystal Phonograph Pickups, to which six new models have been added. Four of these new pickups are designed for the quality reproduction of 10" and 12" records, and meet today's demand for modern design, convenient size, low needle pressure and price economy. For those interested in transcription pickups, Astatic's new, streamlined Models 400 and Nylon-400 are highly recommended.

Model 507

Model 510

Models 508 and Nylon-508

Transcription Pickups 400 and Nylon-400

THE Astatic CORPORATION
CONNEAUT, OHIO

IN CANADA: CANADIAN ASTATIC LTD., TORONTO, ONTARIO

Astatic Crystal Devices Manufactured under Brush Development Co. patents.

See Your Radio Parts Jobber or Write for New 1946 Catalog.

INDUSTRIAL INTERCOMMUNICATIONS

by MAURICE F. KERR



Fig. 1. View of dial-controlled intercommunications unit.

DURING THE PAST TEN YEARS thousands of intercommunication systems have been installed in offices, factories, warehouses and similar establishments. Nearly all of them have been of the conventional type employing one or more amplifiers with direct manual switching of desired circuits or stations. This method of operation in small systems, generally of ten stations or less, has proved very practical, pro-

viding efficient, rapid, voice communication at reasonably low cost.

In analyzing the overall requirements of a communication system for larger plants, however, many items must be considered in addition to the requirements of a smaller system. Such a system should provide:

(1) Fully selective instant voice communication to any required number of stations.

(2) Provision for answering from any station selected without going to instrument to answer.

(3) Selective hi-power paging, properly distributed to any selected area or areas.

(4) Provision for any desired number of simultaneous two-way conversations without cross talk or other interference.

(5) Automatic priority from certain points of origin for emergency calls, warning signals, alarms or other messages over the system.

(6) Simplicity of operation to facilitate correct use by inexperienced operating personnel.


(7) Privacy of communication through automatic lockout circuit when station is in use.

(8) Ability to work through severe or high noise level at either end.

(9) Dependability of service, with routine maintenance requirements concentrated at one central point.

(10) Ability to add to system as required in future without rewiring or obsolescence of installed equipment.

Fig. 2. Block diagram for a typical dial-controlled intercommunications system.

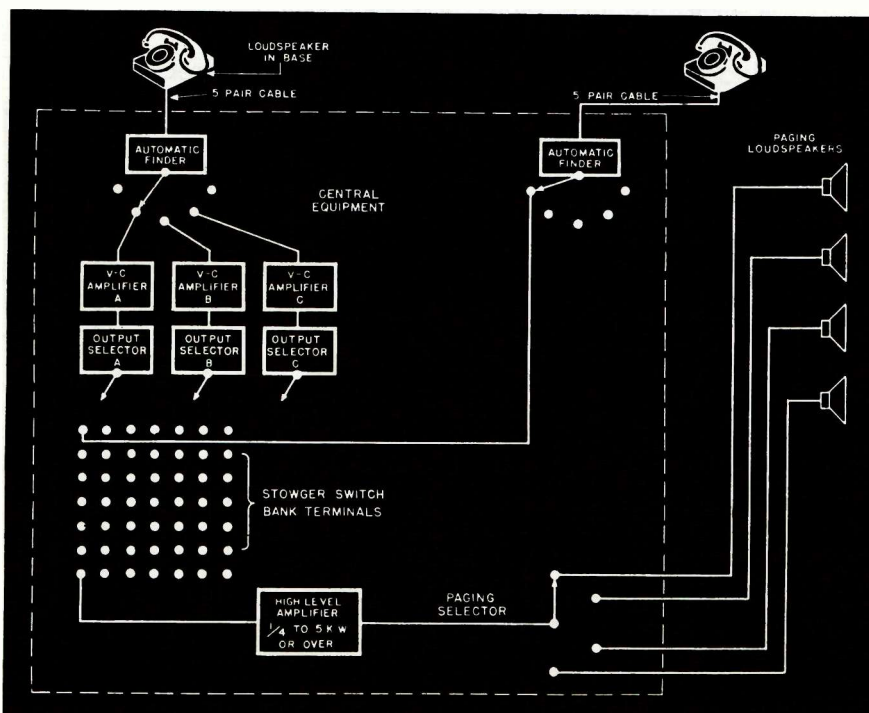

During the war a system¹ offering the foregoing features was developed. Recently technical highlights on the system were released.

In simplest form the equipment can be controlled from any desired number of instruments similar in appearance to a standard desk telephone (Fig. 1). From any of these identical stations the following service is possible:

(a) Instant two-way voice communication to any other station *regardless of number*.

(b) Hi-power paging to any selected area or an entire plant if desired.

(c) Origin of code, tone signals for routine work or alarm signals in emergency.

(d) Automatic return selection on answering of paging calls to

(Continued on page 39)

¹Dial controlled Intervox; Radio Laboratories, Inc., Seattle, Wash.



FOR
HEARING AIDS
VEST POCKET RADIOS
AIR BORNE DEVICES

UTC SUB-OUNCER SERIES


UTC Sub-Ouncer units are $9/16" \times 5/8" \times 7/8"$ and weigh only $1/3$ ounce. Through unique construction, however, these miniature units have performance and dependability characteristics far superior to any other comparable items. The coil is uniform layer wound of Formex wire . . . On a molded nylon bobbin . . . insulation is of cellulose acetate . . . leads mechanically anchored (no tape) . . . core material Hipermalloy . . . entire unit triple (waterproof) sealed. The frequency response of these standard items is ± 3 DB from 200 to 5,000 cycles.

Type	Application	Level	Pri. Imp.	D.C. in Pri.	Sec. Imp.
SO-1	Input	± 4 V.U.	200 50	0	250,000 62,500
SO-2	Interstage/3:l	± 4 V.U.	10,000	0	90,000
SO-3	Plate to Line	± 23 V.U.	10,000 25,000	3/1.5 mil.	200 500
SO-4	Output	± 20 V.U.	30,000	1.0 mil.	50
SO-5	Reactor 50 HY at 1 mil. D.C. 3000 ohms D.C. Res.				

UTC OUNCER SERIES

The standard of the industry for seven years. The overall dimensions are $7/8"$ diameter by $1-3/16"$ height including lugs. Mounting is effected by two screws, opposite the terminal board side, spaced $11/16"$. Weight approximately one ounce. Units not carrying D.C. have high fidelity characteristics being uniform from 40 to 15,000 cycles. Items with D.C. in pri. are for voice frequencies from 150 to 8000 cycles.

Type	Application	Pri. Imp.	Sec. Imp.
0-1	Mike pickup or line to 1 grid	50, 200, 500	50,000
0-4	Single plate to 1 grid	8,000 to 15,000	60,000
0-5	Single plate to 1 grid, D.C. in Pri.	8,000 to 15,000	60,000
0-6	Single plate to 2 grids	8,000 to 15,000	95,000
0-8	Single plate to line	8,000 to 15,000	50, 200, 500
0-9	Single plate to line, D.C. in Pri.	8,000 to 15,000	50, 200, 500
0-12	Mixing and matching	50, 200	50, 200, 500
0-13	Reactor, 200 Hys-no D.C., 50 Hys-2mA D.C., 6,000 ohms		

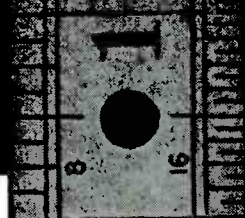

Manufacturers: Our experience in building hundreds of thousands of unceners and sub-unceners is yours for the asking. Special types, and mountings are readily available. U.T.C. engineers can help you save weight and space in the design of miniature equipment.



United Transformer Corp.

150 VARICK STREET

NEW YORK 13, N. Y.

EXPORT DIVISION: #3 EAST 40th STREET, NEW YORK 16, N. Y.,

CABLES: "ARLAB"

The handy tube-type plug-in resistor, originated by Clarostat.



Inside details, showing mica "card" or support for fine helical winding and heavy Glasohm resistor.

★ Clarostat originated and pioneered the tube-type or plug-in resistor. And Clarostat is still the only one that offers these features:

- MICA SUPPORT FOR WINDINGS
- GLASOHMS FOR MAIN LOADS
- POSITIVELY CENTERED SUPPORT
- WINDINGS CANNOT SAG OR SHORT
- POSITIVELY CHAR-PROOF THROUGHOUT
- ADEQUATE SAFETY FACTOR

Remember this inside story when buying tube-type resistors. Don't be satisfied with less! Ask our jobber for the latest Clarostat catalog listing exact-duplicate and universal types. Or write us.



CLAROSTAT MFG. CO., Inc. • 285-7 N. 6th St., Brooklyn, N. Y.

OLD TIMER'S CORNER

(Continued from page 29)

bothering you, I have an answer to your woes."

"Give, chum, give!" Paul grinned.

"Instead of giving away some definite item, why not give away a gift certificate for the face value of the item you were going to give away in the first place?" I stated triumphantly.

"I tried that," Paul said, "but it didn't work any too good. They came in and got their prize and there I was the same as before; no publicity and no advertising."

"You didn't let me finish, my fine feathered friend," I exclaimed forcibly. "There's more to it than that!"

"Continue," said Paul, "but it had better be good—very good."

"One of the prerequisites of the prize award as written on the back of your gift certificate is that the winner must permit you to take his picture receiving the gift at your store. And you should also include in writing on the back of the certificate award, that the winner must permit you to use his picture and some quotation by him about the award in your advertising."

"I begin to see some light," Paul said, interrupting.

"Then when the winner comes to your store for the choosing of the prize," I went on, ignoring his remark, "you get a good commercial photographer and take a picture of the person choosing the prize and receiving it from you. Then you write a caption that might say: 'Mrs. Sadie Prey, of 1333 Pine St., choosing a fine Red Star Midget from Paul's Radio Shoppe, 100 Broadway Ave. Mrs. Prey was the lucky winner of the Blotto game at last night's meeting of the Ladies Evening Society Bazaar, and received as her prize a gift certificate donated by Paul Prime, proprietor of the radio shop.'

"The newspaper editor will probably rewrite your caption to fit the space he wants to use, and he will probably cut the picture down to a small size, but he will probably run it. That's the important thing.

"Then you can cut the clipping from the paper and paste it on your window. That will attract some people. I would also cut out a copy to send to Mrs. Prey and another to send to the president of the Ladies Evening Society. They will appreciate your thinking of them.

"Finally, I would follow up on Mrs. Prey with a service call to see that her prize item worked properly. I would explain to her that merely because you had given her the item as the result of her winning a prize certificate, you would not thereby deprive her of the same superior service that every customer of your store gets. That creates good will.

"If the paper does not print the item, and sometimes they won't, then I would still take advantage of the situation. Paste the picture on the window with a personally written caption. Send copies to both Mrs. Prey and the president of the Society with the comment that you thought they might like to have a copy.

"And I would use Mrs. Prey's picture in advertising placed in the local paper. Moreover, you could design an



WIRES



*made by engineers
for engineers.....*

CORNISH WIRE CO., Inc.
15 Park Row • New York City, 7



The HOUSE OF A MILLION RADIO PARTS

**SERVICE MEN—
SOUND MEN—
AMATEURS—**

Write for the latest Lifetime BARGAIN BULLETIN just off the press! Thousands of money-savers in parts, supplies, equipment.

Lifetime

SOUND EQUIP. CO., Dept. 84
911-913 JEFFERSON AVE., TOLEDO 2, OHIO

TEST EQUIPMENT

PARTS TUBES SOUND

Serving the Serviceman

GENERAL ELECTRONIC SUPPLY CO.
Incorporated
203 W. 4th St., Owensboro, Ky.
Phone 2068

envelope stuffer built around the award and the picture of Mrs. Prey. You might use a headline saying:

Mrs. Sadie Prey Was Lucky . . .
And You Will Be Too . . . If You Trade at
Paul's Radio Shoppe

Because
Here You Will Find the Best Equipment and
Service at the Best Prices!

"And I would use Mrs. Prey's picture to illustrate the story. Then I would send these stuffers out to as many customers and prospects as I could dream up.

"One thing, though. If you are going to use Mrs. Prey's picture in advertising or even on envelope stuffers, you'll need a release from her. This is a statement that she will permit you to use the picture as you see fit. You don't need any lawyer to write the release for you. Just have Mrs. Prey sign a statement that reads something like this: 'In consideration of receiving the prize for which I hold a certificate, I hereby permit Paul's Radio Shoppe to use my name and picture in advertising and publicity as it may see fit.' Have her sign her name and date it, and that's that."

"That is a most unusual way to handle what is really a pesky situation," Paul said, "but I think I'll give it a try. But what if nothing happens and I don't get any new business?"

"That's the chance every advertiser takes. The fact that you might not be able to get customers hasn't stopped you from opening your store, has it? Well, you will find that if you try publicity and advertising, even if the results don't show right away, they will eventually."


"What about the gyp affairs?" Paul wanted to know.

"Well," said I, "I don't know how any business man can get out from under having to use his head and brains if he wants to stay in business. It's up to you to find out which are the gyps and which are not. One good way is to ask your bank about it, mentioning who's backing the affair. Nearly always the banker will know as he probably will have been solicited also. Then again, if the approach is by mail, you can ask the local postmaster; it being against the law to defraud by mail.

"There are many ways to find out. The local pastor, rabbi or father will know the answer if the affair is allegedly religious. You can't just make up your mind they are all gyps because one or two might be. That would be sort of like saying all men are murderers just because some men have been convicted of the crime."

"Roger!" said Paul, as he reached for the phone to tell the Ladies Evening Society that he would contribute a gift certificate worth \$25.00 for their affair.

TELEVISION CAMERA

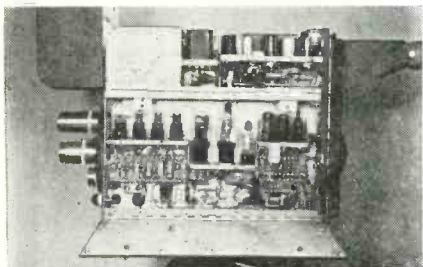


Interior of RCA television camera; pre-amplifier compartment (lower section), electronic view finder (upper section), image orthicon pickup tube (center compartment).

4.2 VOLTS OUTPUT*!!

DIRECT CONNECTION TO PENTODE OUTPUT TUBES!

. . . and only 1/8 oz. needle force

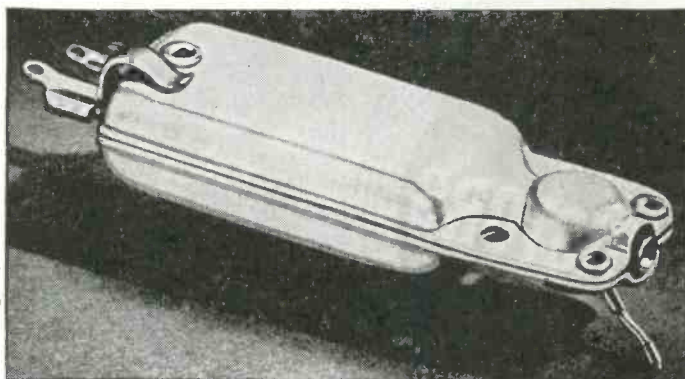

WITH THE NEW SHURE W56A

Lever-Type Crystal Pickup Cartridge

List Price \$4.45

AND



THE NEW SHURE 96A

Crystal Phonograph Pickup

List Price \$6.10

MADE POSSIBLE THROUGH THE SHURE LEVER SYSTEM • HERE'S HOW IT WORKS:

The crystal is driven by a lever which improves the transmission of needle torque into the crystal. This results in higher output and greater needle compliance. High needle compliance gives a "freedom of action" flexibility to the needle that means faithful tracking, and clearer, fuller tone qualities.

The lever arrangement absorbs the full impact of sudden jars to the cartridge or needle; this in turn gives relative shock immunity to the crystal—minimizing strain or breakage.

WHAT THE 96A DOES FOR YOU: It makes possible the saving of one stage of amplification, and it permits the use of a long-life precious-tip needle with a high-output pickup. Such a light-weight tone arm means that the records and needles will last much longer. The 96A "Glider" is less susceptible to floor vibrations, improves the playing of warped records, and is especially suitable for Vinylite records.

(*) 1000 cycle Audiotone record level using Full-Tone needle. About 3.5 volts using flexible needles. Voltage output on peaks reaches 40 volts!

WRITE FOR NEW CATALOGS 155-S and 156-S

Patented by Shure Brothers and licensed under the Patents of the Brush Development Company

SHURE BROTHERS, INC.

Microphones and Acoustic Devices

225 West Huron Street, Chicago 10, Illinois
Cable Address: SHUREMICRO





● Yes, it's Aerovox for resistors, too. The latest Aerovox catalog contains a solid page of resistor listings. It's a streamlined, most-handy, minimum stock selection geared to profitable servicing.

WIRE-WOUND RESISTORS
 "Slideohm" wire-wound vitreous-enamelled adjustable resistors in 25- to 200-watt ratings. Resistance values from 1 to 150,000 ohms. "Pyrohm Junior" fixed resistors in 10- and 20-watt, 1 to 100,000 ohms.

CARBON RESISTORS
 Insulated molded type. Crack-proof molded casing around molded carbon resistance element. 2" tinned copper pigtail leads. 10% tolerance. 1/2 and 1-watt ratings. 10 ohms to 20 megohms.

Ask for Aerovox resistors when you are ordering Aerovox capacitors. They go together! Ask for latest Aerovox catalog—or write us.



AEROVOX CORP., NEW BEDFORD, MASS., U.S.A.
 Export: 19 E. 40th St., New York 18, N.Y. • Cable: 'ARLAB'
 In Canada: AEROVOX CANADA LTD., Hamilton, Ont.

SERVICING HELPS

by FRANK C. KEENE


I PLAN TO INSTALL a multiple headphone system in a hospital and would like to have circuit showing a hookup for this. Can you help?—C. H. Carrier.

The simplest and most satisfactory type of system for bedside reception would be one using an audio supply unit with a 500-ohm line to feed headphones at each bed. Radio type systems are unsatisfactory where high r-f noise levels are present.

A typical system is shown in Fig. 1 (a). Constant load can be maintained by using a three-circuit jack (b), which would provide for the insertion of a resistor of equivalent load value to the headphone when the headphone is disconnected. A further refinement would be a T-pad attenuator, (c), so as to reduce the volume in the headset, yet maintain constant load impedance and match, between headphone and line.

The carrier-current type system can be used but this requires a complex setup. Needed are a standard receiver to feed a local mixer which would convert the receiver signal to some secondary frequency, such as an i-f frequency. This signal would then be fed to a r-f amplifier tuned to the

Fig. 1 (Carrier query). In (a) appears an audio supply system for a hospital receiving arrangement, using a 500-ohm line; (b), maintaining constant load with a 3-circuit jack; (c), T-pad attenuator hookup for constant-load impedance and matching between headphones and line.

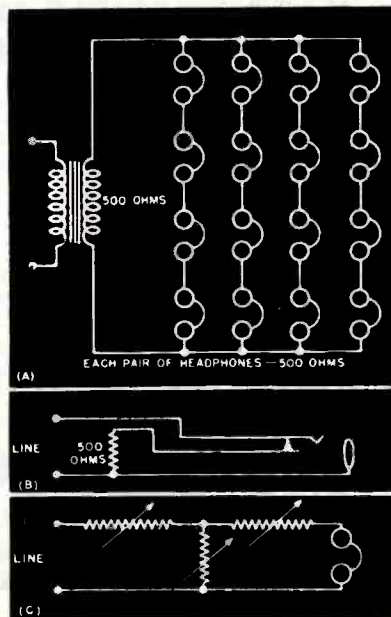

For Soldering in Tight Places . . .

DRAKE

No. 400 Soldering Iron

Smallest Industrial Iron Ever Designed

60 Watts — 1/4 in. Tip
 Only 9 in. long. Wt. only 8 oz

This mighty mite is backed by DRAKE's 25 years of soldering iron manufacturing experience. The high quality and long-service of DRAKE Soldering Irons have made them outstanding favorites with all types of radio men everywhere. The DRAKE No. 400 is an outstanding value at



Only \$4.50 List

Drake Has an Iron for Every Purpose. Ask Your Radio Parts Jobber


DRAKE ELECTRIC WORKS, INC.

3656 LINCOLN AVE. CHICAGO 13, ILL.

18 YEARS IN RADIO

Get This New Catalog By This Old Firm

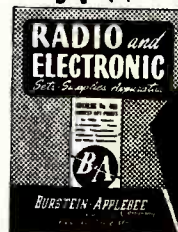Latest developments in radio and electronic parts and devices, newest ham gear, gadgets to delight the heart of the experimenter, bargains in war surplus supplies.



It's FREE To You

- Buy from B-A
- Save Time
- Save Money
- Get the Newest
- Deal with This Old House

MAIL COUPON TODAY

Don't delay, get your copy of this book.

BURSTEIN-APPLEBEE CO., 1012 McGee, Kansas City 6, Mo.

Send me FREE new catalog. SERVICE

I AM _____ STATE CONNECTION IN INDUSTRY

NAME _____

ADDRESS _____

TOWN _____ STATE _____



new frequency. The amplifier required is a class *A* type.


What would cause a receiver to pick up static, but no signal?—Jack L. Seib

This condition can almost always be traced to an inoperative oscillator.

In checking oscillator circuits, it is first necessary to determine whether the circuit is oscillating or not. This may be done by either of two methods. The first is by use of a v-t-v-m. If the circuit is oscillating, a voltage should appear across the oscillator grid shunt resistor. This voltage should be on the order of 3 to 12, depending on the tube used. The other method involves the use of a second receiver. The receiver under test is first tuned to some known frequency, preferably at the low-frequency end of the dial. The antenna wire of the second receiver is then placed somewhere near the oscillator coil. The second receiver is then tuned to the vicinity of the first receiver plus the i-f frequency of the receiver under test. For example, if the defective receiver is tuned to 500 kc, and uses an i-f of 465 kc, the second receiver should be tuned to 500 + 465 kc, or 965 kc. If the oscillator is functioning, a hush will be heard. If the second receiver uses a b-f-o, the signal of the first receiver should establish a beat note.

The most usual trouble encountered in oscillator circuits, in the order of their frequency, is defective tube, no oscillator plate voltage, broken wires on the oscillator coil or poor connection on the coil, open grid resistor, or open cathode resistor. Usually, once it has been established that the oscillator is not operating, the trouble will be obvious.

Fig. 2 (Seib query). Two typical converter circuits. Right, below, the conventional plate tickler feedback circuit. The grid voltage is developed between points *a* and *b* on the oscillator grid resistor. This voltage can only be measured with a v-t-v-m. A likely point of trouble is the ground connection on the grid coil. Left, below, the cathode type of oscillator circuit. Here, the cathode is connected to a tap on the oscillator coil. The screen grid of the circuit is actually the oscillator plate, but a bypass capacitor places it at ground r-f potential. Grid voltage is developed across the grid resistor.

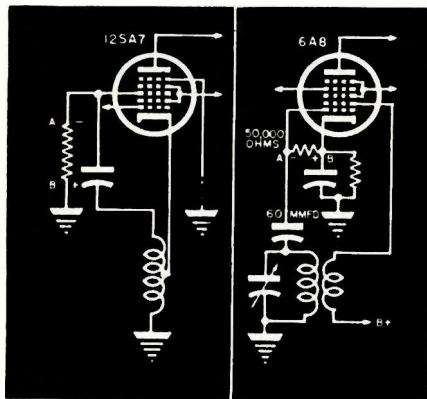

"A CHERRY BLIND RIVET for every job . . . A Cherry Rivet Gun for every need." The Cherry line of blind rivets and installation tools was conceived around this idea. And the idea continues to expand.

THE NEW G-55 HAND GUN was designed especially for small-quantity users of the larger sizes (7/32", 1/4", 9/32") of Cherry Blind Rivets. (Used with an adapter, it also installs the smaller rivets.) The more expensive pneumatic guns are primarily production line tools. But for small-quantity rivet installation, or for field work where air pressure is not available, the hand gun is perfect. The relatively inexpensive G-55 Hand Gun is light weight and easy to handle.

CHERRY BLIND RIVETS are available in aluminum, steel, brass and Monel.

For more information regarding Cherry G-55 Hand Gun, and other Cherry Rivet products, write to Dept. J-268, Cherry Rivet Company, 231 Winston Street, Los Angeles 13, Calif.

CHERRY RIVETS. THEIR MANUFACTURE & APPLICATION ARE COVERED BY U. S. PATENTS ISSUED & PENDING



Attention GI JOE!

Here's Your Opportunity to be First to

Start Your Own RADIO SERVICE SHOP

Complete Start-in-Business
Package Stocks of

TEST EQUIPMENT
TUBES, PARTS, TOOLS **\$350 up**

Act quickly! Meet the pent up demand for radio service. Turn your special service training into a profitable business of your own. No fuss. No worry. Here's everything you need—\$350 up. Details upon request! Write, wire or phone

TRIPLETT 666

"POCKET" VOM **\$15.25**

A.C.-D.C. Volts
0-10-50-250-1000
0-10-100-500 D.C. Mills
0-300-250000 Ohms
Size 3x6x2



TRIPLETT 666H
\$20.00

Same as above plus
5000 V. ranges

Triplett 6505C Output Meter
Regular **\$24.50** Special .. **\$16.50**

0-1.5-6-15-60-150 Volts. 4000 OHM Impedance.
3" Meter 100 Microamp movement

Triplett 606B .. Regular **\$16.67**
Voltage & Polarity Tester, Special **\$11.95**

Ideal for plant maintenance work! Checks 115-220-440 line at a glance! Indicates AC or DC visually! Indicates DC Polarity visually!

HALLICRAFTERS S-38



\$39.50

S-40 (replaces
S20R)

\$79.50

HAMMARLUND-HQ129X **\$168**
Speaker for HQ129X **\$10.50**

THE DEFIANT! **\$83.95** Complete
25 Watt Sound System. wired, ready to use!



A reliable amplifier with 2 mke and 1 phono inputs, two 12" 20 oz. 13 watt PM speakers with 25' cables, two 12" walnut 7 ply wall baffles; one crystal microphone with table stand and 15' shielded cable.

THE CHALLENGER! **\$69.95** Complete
25 Watt Sound System

Same as above except includes one speaker and baffle.

PHILCO BEAM OF LIGHT

Selenium Cell only, no holder **1.80**

20% deposit required on all C.O.D. orders. 2% transportation allowance on orders of \$25.00 or more accompanied by payment in full.

Write for
FREE CATALOG

RADIO SUPPLY & ENGINEERING CO., Inc.
126 SELDEN AVE DETROIT 1, MICH.

NEWS

BONOT NEEDLE DISPENSER

A self-service type of needle dispenser has been announced by the Bonot Company, Stamford, Conn.

* * *

LAIRD NOW EPDM CHAIRMAN

Roy S. Laird, sales manager of Ohmite Manufacturing Company, Chicago, has been elected chairman of the Association of Electronic Parts and Equipment Manufacturers. He succeeds J. A. Berman, sales manager of Shure Brothers.

Les A. Thayer, assistant sales manager of Belden Manufacturing Company, Chicago, is now vice chairman. Miss H. A. Staniland, sales manager of Quam-Nichols Company, Chicago, continues as treasurer for the seventh consecutive year, and Kenneth C. Prince, Chicago, attorney, continues as executive secretary.



* * *

TRI-CORE BULLETIN

A 4-page bulletin describing Tri-Core has been issued by Alpha Metals, Inc., 359 Hudson Ave., Brooklyn 1, New York.

Tri-Core is said to be a self-fluxing solder, with three cores located just beneath the outer surface of the wire.

* * *

MORRIS NOW SNYDER G-S-M

Dick Morris has been appointed general sales manager for the Snyder Manufacturing Company, Philadelphia.

Mr. Morris has been with the Snyder company for eight years.



* * *

GOLENPAUL AND JABLON NAMED PARTS SHOW DIRECTORS

Charles Golenpaul, Aerovox Corporation, New Bedford, Massachusetts, and Walter Jablon, Hammarlund Manufacturing Company, New York City, have been named directors for the 1947 Radio Parts and Equipment Trade Show.

Mr. Golenpaul and Mr. Jablon will represent the Sales Managers Club. Mr. Golenpaul was a director and the vice

For F. M. Listeners!

THE NEW

GON-SET F. M. CONVERTER

Provides New FM Band Reception (88-108 MC) for Receivers Covering Old FM Frequencies (42-50 MC)



"GON-SET" F.M. Converters are available in three bands, covering the following frequencies:

Type "A"
88 to 96 mc.
Type "B"
96 to 104 mc.
Type "C"
100 to 108 mc.


In ordering, be sure you choose the correct model covering the frequencies utilized in the area where the receiver is to be used.

\$14.95

Manufactured by

WATERPROOF ELECTRIC CO.
BURBANK, CALIFORNIA

Free Radionic Catalog

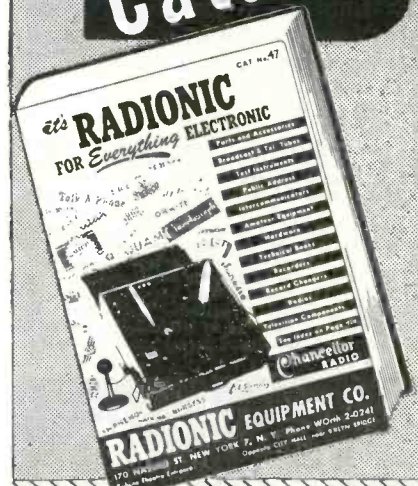

RADIONIC EQUIPMENT CO.
170 Nassau St., Dept. 2510
New York 7, N. Y.

Please send me a FREE copy of your 1947 Catalog. I understand it has thousands of items illustrated, described and priced and will be a great help to me in my search for "hard-to-find" radio equipment. **CHANCELLOR RADIOS**

Name
Address
City..... State.....

president of the 1946 show. Mr. Jablon succeeds R. P. Almy.

* * *
**KAHN OF AEROVOX RECEIVES ASA
CERTIFICATE OF APPRECIATION**

Louis Kahn, assistant chief engineer of Aerovox Corporation, recently received the American Standards Association Certification of Appreciation for volunteering his time and experience in the War Committee Work of the A. S. A.

* * *
**BRENDEL BECOMES HALLICRAFTERS
GENERAL SERVICE MANAGER**

Lynn Brendel has been appointed general service manager of the Hallicrafters Company.

Mr. Brendel, who joined Hallicrafters in 1945, will be responsible for the servicing of all Hallicrafters equipment and the operation of the company's six service centers throughout the country.

Mr. Brendel was formerly with United Motors Service as a sales and service engineer, and with the Bendix Radio Corporation in Detroit as a sales and research engineer.



* * *
STROMBERG-CARLSON P-A FOLDER

A four-page folder describing sound systems, power amplifier cabinets, amplifiers for one, two and three-microphone inputs, p-a portables, speakers, microphones, driver units and alnico V cone speakers, has been released by the sound division of Stromberg Carlson, 100 Carlson Road, Rochester, New York.

* * *
WARD LEONARD RELAY DATA

A 4-page booklet, bulletin 104, covering midget metal-base relays, has been announced by Ward Leonard Electric Co., 31 South Street, Mount Vernon, New York.

Bulletin includes coil and contact data, contact arrangement diagrams, dimension sketches of front and rear mounted units and enclosing cover data for both standard and heavy duty relays; relays designed for use in small transmitters, aircraft control circuits and applications where space is limited.

* * *
**LARRABEE AND TWYMAN NOW
JFD SALES REPS.**

Fred H. Larrabee has been appointed sales representative for Kansas, Nebraska, Iowa and Missouri by the JFD Manufacturing Co., 4117 North Hamilton Parkway, Brooklyn 19, New York. Sales headquarters are located at 6033 Main Street, Kansas City, Missouri.

B. G. Twyman & Associates, 6406 North Fairfield Avenue, Chicago 45, Ill., have been assigned the state of Illinois by JFD.


* * *
REEVES CATALOG

A catalog describing instantaneous recording discs has been announced by Reeves Soundcraft Corporation, Reeves International Building, 10 East 52nd Street, New York 22, N. Y.

STAYS ACCURATE—Year After Year



Here's a sturdy, modern test oscillator that's accurate when you buy it—and keeps its accuracy in long service. Convenient push button selection of ranges from 100KC to 30MC.

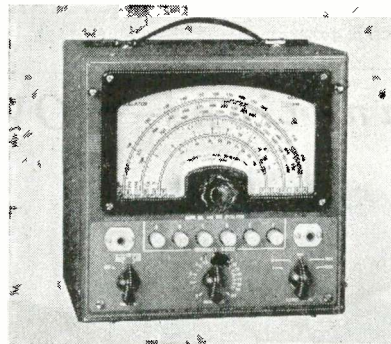

**MODEL 640
TEST OSCILLATOR**

A complete standard type oscillator for all general purpose work. Full range direct reading dial. All ranges are fundamental frequencies. No skips or harmonics calibrated.

Accuracy guaranteed to 1/2 of 1% on all ranges.

Push button selection of all ranges makes operation fast and accurate.

Glass enclosed dial prevents dust and protects the pointer.

Two circuit attenuator provides variable ratio and also vernier control.

Powerful signal output usable as pure or modulated R. F. carrier is modulated at approximately 30%. The A. F. voltage is available for external use.

Operates from 110 volts 60 cycles. Uses three tubes: rectifier, oscillator, and modulator.

Dimensions: 8 1/2" x 8 1/2" x 6 1/2".

JACKSON


Fine Electrical Testing Instruments

JACKSON ELECTRICAL INSTRUMENT COMPANY, DAYTON, OHIO

EASILY ADJUSTABLE FOR THE JOB

ADJUSTOHM RESISTORS

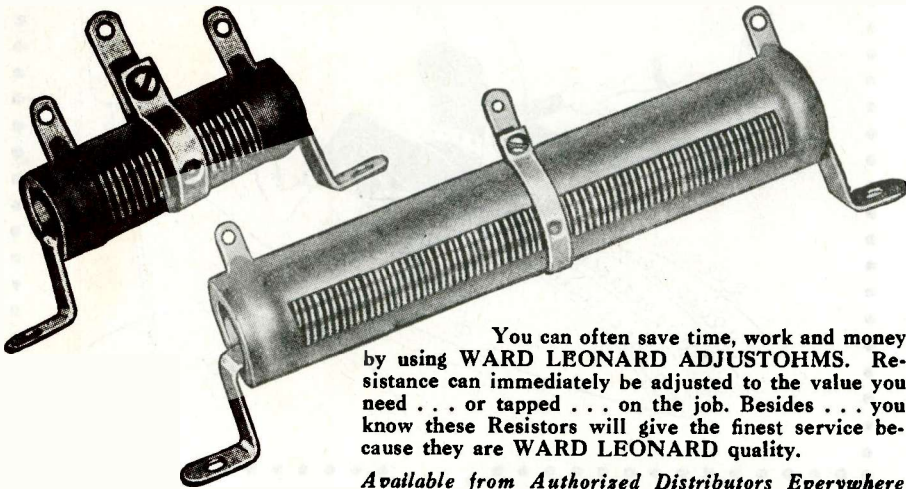Seven Stock Sizes from 10 watts to 200 watts



You can often save time, work and money by using WARD LEONARD ADJUSTOHS. Resistance can immediately be adjusted to the value you need . . . or tapped . . . on the job. Besides . . . you know these Resistors will give the finest service because they are WARD LEONARD quality.

Available from Authorized Distributors Everywhere

WARD LEONARD ELECTRIC CO.
53E W. Jackson Blvd., Chicago 4
Radio and Electronic Distributor Division


WARD LEONARD

RELAYS • RESISTORS • RHEOSTATS

Electric control devices since 1892

Send for
Catalog D-2

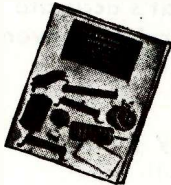Gives handy data and information on various types of Resistors and Rheostats available from stock.




Automatic Combinations—NOW!

The New Arnold Shure Automatic Wired Record Player ready for immediate delivery.

The Shure automatic record player connects easily to any radio. Its featherweight crystal pickup and quiet, smooth changer action assure high quality playing of ten 12" records or twelve 10" records. Every one of your customers can now own a fine automatic combination at a remarkably low cost.

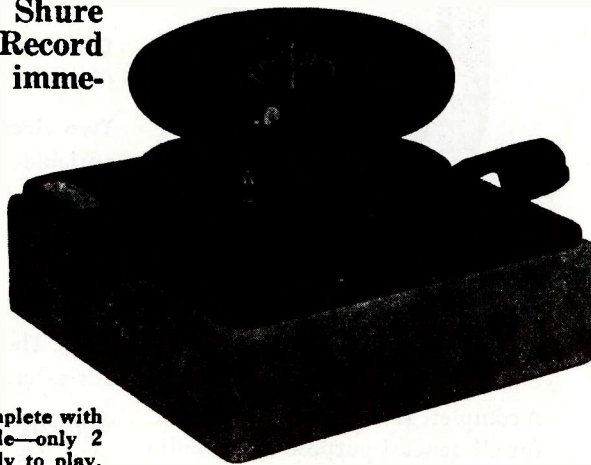Shure players are shipped complete with A.C. cord and shielded cable—only 2 wires to connect and it's ready to play.



Your price only \$21.92 net

F.O.B. Chicago, Illinois

OPA Retail Price — \$31.30 — Zone 1

OPA Retail Price — 33.87 — Zone 2

Orders are now being accepted for immediate delivery—no waiting. Terms: 2% check with order. Or 25% deposit, balance express C.O.D.

PHONO AMPLIFIERS

1-Tube Phono. Amplifier.....\$2.85 ea.
3-Tube Phono. Amplifier..... 4.50 ea.

PM SPEAKERS

4" Alnico (5) PM Speaker.....\$1.39 ea.
5" Alnico (5) PM Speaker..... 1.49 ea.
6" Alnico (5) PM Speaker..... 1.89 ea.

TUBULAR ELECTROLYTICS

100-MFD-25 V...\$.22 ea.	10-MFD-450 V...\$.29 ea.
10-MFD-50 V... .22 ea.	16-MFD-450 V... .39 ea.
20-MFD-150 V... .22 ea.	10-10-MFD-450 V... .59 ea.
30-MFD-150 V... .29 ea.	20-20-MFD-150 V... .39 ea.
40-MFD-150 V... .39 ea.	30-20-MFD-150 V... .39 ea.
50-MFD-150 V... .45 ea.	40-30-MFD-150 V... .45 ea.
8-MFD-450 V... .25 ea.	50-30-MFD-150 V... .59 ea.


NEW PRODUCTS

HI-PAR F-M ANTENNA

A non-directional f-m antenna has been produced by the Hi-Par Products Co., Fitchburg, Massachusetts.

Collector rods of aluminum alloy. Varnished hardwood support.

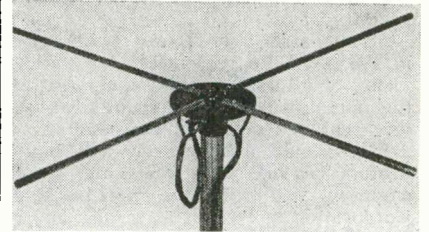Antenna said to match any standard leadin.




* * *

SOLAR DRY ELECTROLYTICS WITH PLASTIC-FILM INNER WRAP

Solar cardboard-tube dry electrolytic capacitors now feature a plastic film wrap in place of the Kraft paper liner.

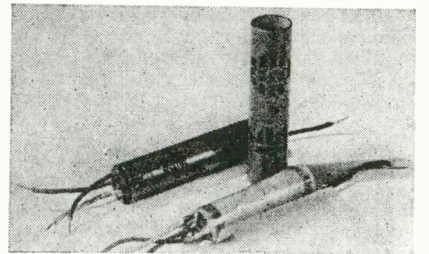
The plastic film is said to keep the electrolyte from drying out in high ambient operating temperatures, and also keep external atmospheric moisture, which may contain many impurities, from being introduced into capacitors under the alternate heating and cooling which is normal in actual service in receivers.



* * *

CENTRALAB MINIATURE RADIOHMS

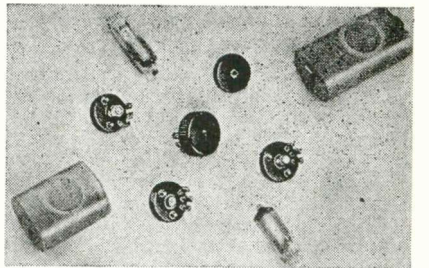A volume control, model 1 radiohm, that is said to be smaller than a dime, has been announced by Centralab, 900 E. Keefe Ave., Milwaukee 1, Wis. Unit will be available in 500 ohms to 5 meg-ohms with six tapers.



* * *

MASCO P-A SYSTEMS

A 50-watt amplifier that is said to operate from 2 to 12 speakers has been announced by the Mark Simpson Manufacturing Company, Long Island City,

(Continued on page 42)

HOLLANDER RADIO SUPPLY CO.

549 West Randolph Street Chicago 6, Illinois

INTERCOM SYSTEM

(Continued from page 30)

station originating, without called party even knowing point of origin.

(c) Either two-way, voice controlled, intercom service, or upon lifting handset at called station, telephone privacy is available. Through anti-side tone circuits ability to work through severe noise level is provided.

No ringers or other signals are required; each instrument has built-in loudspeaker adequate for office or similar coverage.

On systems up to 100 stations two-digit dial operation allows direct talking to called area as soon as dial stops on second number.

Three digits are used on up to 1000 stations. Three or four digit selection is employed on more complex paging selection.

In a typical installation all amplifiers, tubes, relays, power supplies, selectors, etc., are located in a dust sealed and locked steel cabinet located in any convenient central point. All maintenance therefore is concentrated at one location, avoiding necessity of replacing tubes or other maintenance in offices, salesrooms, warehouses, etc., with its attendant high cost and inconvenience.

Operation

Upon lifting of handset on station 11 (Fig. 2) an automatic finder (11) locates and connects to an amplifier and output selector not being otherwise used. This finder may check through twenty or more amplifiers before the handset is raised to ear level, automatically stopping and connecting to the first unused circuit. The user may immediately dial two digits for the desired station in accordance with prearranged listing of all circuits or functions.

The output selector *A* instantly follows the dial pulses, selects and connects to desired station. As soon as dial has stopped, therefore, the user may speak through the loud speaker at the selected station. Upon ceasing to speak the two-way voice controlled amplifier reverses, permitting a voice answer from the called station to be transmitted and amplified back to ear-piece at the originating station.

If the called station is already in use on another call, no connection would

(Continued on page 40)

CAPITOL RADIO ENGINEERING INSTITUTE — Where Professional Radiomen Study



NEW Know-How Means More Money in Modern Servicing!

—“Service” Mag. Photo

CREI Home Study Training in New Radio - Electronic Techniques is a \$ and Sense Investment in Your Future

PREPARE NOW FOR NEW MONEY-MAKING SERVICING OPPORTUNITIES

Foresighted radio servicemen are looking ahead to the future. A future that has unlimited opportunities and real profits for those who have the “Know-How” to SERVICE television, FM, industrial electronic equipment, and the many other new radio developments.

Join the many professional servicemen who are studying at home, the new developments, the new techniques, with CREI . . . protecting their future jobs, their businesses by acquiring the new “Know-How”, NOW!

CREI's reputation for home study training has been proved over 19 years. Important new developments have been included in our present course. Trained instructors give you personalized attention and guidance *all the way*.

Find out for yourself how CREI can help you to greater security and prosperity. Send in the coupon now! Actually see what CREI has to offer.

VETERANS! CREI IS APPROVED FOR “G.I.” TRAINING!

RESISTANCE

—To New Ideas Has Cost Many a Man a Great Future. We all know the classic stories of the people who scoffed at Edison, Ford, DeForest. It was the scoffers who lost out when the rewards poured in. Now with radio-electronics entering a great, new era, when it may well emerge in greatly magnified form, you fellows who are in on the ground floor and don't prepare now for the future fall in the same class as those early scoffers.

E. H. Rietzke
President of CREI

Capitol Radio Engineering Institute

E. H. RIETZKE, President

Dept. S-10, 16th and Park Road, N.W., Washington 10, D. C.

Branch Offices:

New York (7): 170 Broadway

San Francisco (2): 760 Market Street



MAIL COUPON
FOR FREE 36-PAGE
BOOKLET

If you have had professional or amateur radio experience and want to make more money, let us prove to you we have the training you need to qualify for a better radio job. To help us intelligently answer your inquiry—PLEASE STATE BRIEFLY YOUR BACKGROUND OF EXPERIENCE, EDUCATION AND PRESENT POSITION.

Capitol Radio Engineering Institute 8-10
16th and Park Road, N. W., Washington 10, D. C.

GENTLEMEN: Please send me your free booklet, “Your Opportunity in the New World of Electronics”, together with full details of your home study training. I am attaching a brief résumé of my experience, education and present position.

Name

Street

City..... Zone..... State.....

Check Course Practical Radio Engineering
 Practical Television Engineering

I am entitled to training under the G. I. Bill.

INTERCOM SYSTEM

(Continued from page 39)

be made, but a busy tone would be heard in the calling station earpiece.

When private conversation is desired without loudspeaker reproduction, the called party may raise his handset and a two-way telephone service is available. For executive office, a privacy key may be installed on the instrument, that when operated, prohibits any party from calling in by voice or listening to that point. An attempted call then produces a one-second low musical tone in the loudspeaker and

to the party calling, whereupon the called party may answer or in any case, the caller knows of the called party's desire for privacy. Loudspeaker volume is controlled and set to the desired level at the receiving point regardless of what channel or amplifier the voice may pass through. Earpiece volume is controlled by multiple stage limiters and compressors holding earphone volume to an optimum level even for wide levels of voice input, to insure adequate amplification for an answer remote from the pickup or answer microphone, yet preventing objectional loudness on close talking or high noise. Automatic voice control

amplifiers adjusted by oscilloscope pattern timing, operates on a fraction of a syllable, permitting instant answer or breakin.

When hi-power paging is to be used, calls are placed in same manner as calling another station except that additional numbers are dialed, to select the area or areas to be covered. Any required amount of audio power can be thus controlled from any station or selected group of originating stations.

Any station in use is automatically locked out against interference from any other calls. Upon returning handset to cradle all circuits automatically reset for next usage.

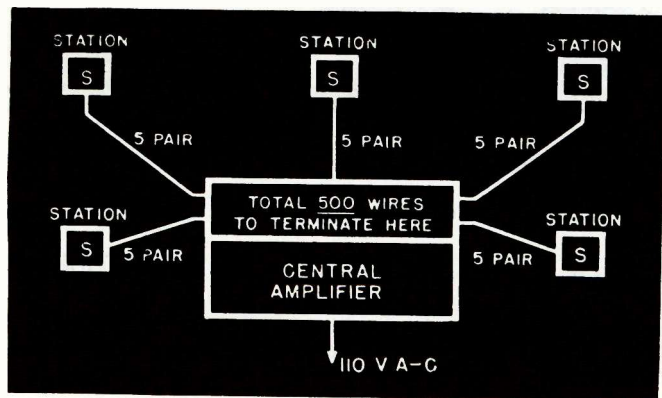


Fig. 3 (below). Setup for a conventional 50-station intercom system.

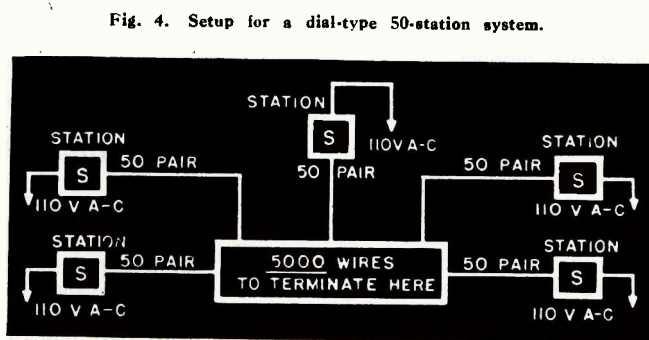


Fig. 4. Setup for a dial-type 50-station system.

In All Western States and Mexico
Immediate Mailing of
Howard Sams Photofact Folios
 Mail \$1.50 and your subscription at once.
 (If mailed in State of California, please add 5c state sales tax)

TO
RADIO TELEVISION SUPPLY CO., Inc.
 1509 So. Figueroa St.,
 Los Angeles 15, Calif.
 (Also—Permanent Leather Binder for Howard Sams Folios \$3.39)

IN PHILADELPHIA — IT'S ALMO RADIO COMPANY
 Wholesale Distributors for Supreme & Jackson Test Equipment
 Aerovox, Cornell Dubilier and Sprague Condensers
 I. R. C., Clarostat and Centralab Volume Controls
TRY US FIRST!
ALMO RADIO COMPANY
 509 Arch Street, Philadelphia 6, Pennsylvania
 LO. 3-0513 LO. 3-4559

SCENIC has . . . "hard-to-get"
TEST INSTRUMENTS!

McMURDO-SILVER "Vomax".....\$59.85	SIMPSON 260 v.o.m.....\$38.95
RADIO CITY 322 tube tester.. 41.50	SIMPSON 305 tube tester..... 46.25
RCP 802-N tube & set tester... 59.50	SIMPSON 240 "Hammer"..... 26.50
APPROVED R.F. sig. gen..... 49.50	TRIPLETT 2413 tube tester.... 48.50
WATERMAN 2" oscilloscope..... 55.00	TRIPLETT 2432 sig. gen..... 58.50
TRIPLETT 625-N v.o.m..... 45.00	TRIPLETT 886-N v.o.m..... 20.00

Also TUBES • AMPLIFIERS • SPEAKERS, etc.
 25% deposit should accompany C.O.D. orders
SCENIC RADIO & ELECTRONICS CO., 53 Park Pl., New York 7


J. V. Duncombe Co.
 WHOLESALE DISTRIBUTOR
 ELECTRONIC EQUIPMENT, TUBES and PARTS
 1011 West 8th Street Phone: 23-546 Erie, Pa.
 ALL NATIONALLY KNOWN RADIO PARTS—AMATEUR SUPPLIES,
 NATIONAL UNION, SYLVANIA AND RCA TUBES

GET TEST EQUIPMENT AT:

SUN RADIO & ELECTRONICS CO., Inc.
 122-124 DUANE ST. NEW YORK 7, N. Y. BR4day 7-1840

TUBES—PARTS
 RADIO DEALERS—SERVICEMEN
 Send for our list of available tubes and repair parts.
 Sylvania, Tung-Sol, Ken-Rad.
M. V. MANSFIELD CO.
 937 LIBERTY AVE. PITTSBURGH 22, PA.

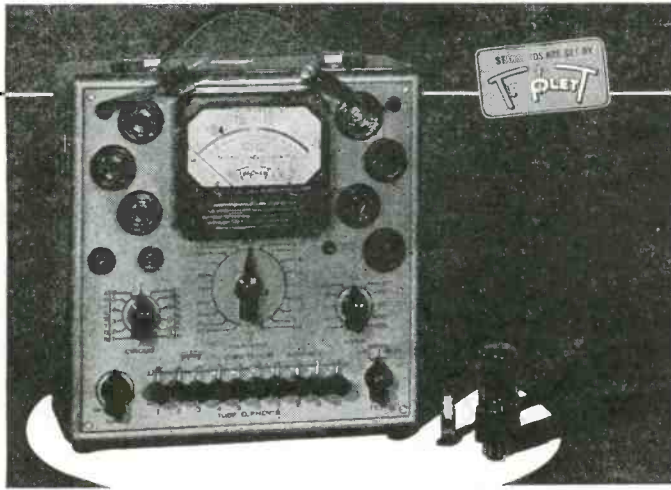WHEN YOU CHANGE YOUR ADDRESS
 Be sure to notify the Subscription Department of SERVICE at 52 Vanderbilt Ave., New York 17, N. Y., giving the old as well as the new address, and do this at least four weeks in advance. The Post Office Department does not forward magazines unless you pay additional postage, and we cannot duplicate copies mailed to the old address. We ask your cooperation.



A New
TRANSCONDUCTANCE
READING
Tube Tester

For the Man Who Takes Pride in His Work


Microhmo (Dynamic mutual conductance) readings and simplified testing—are two of the 20 exclusive features found in the new model 2425 tube tester. Transconductance readings are made possible through a simple measurement directly proportional to Gm and a properly calibrated measuring instrument. No possibility of grid overloading. "Short" and "open" tests of every tube element. Gas test rounds out full check of all tubes. New Easy-Test Roll Chart. These exclusive features, amplified by Triplet Engineering, make Model 2425 the outstanding 1947 tube tester.

Precision first

Triplet

...to last

ELECTRICAL INSTRUMENT CO. BLUFFTON, OHIO

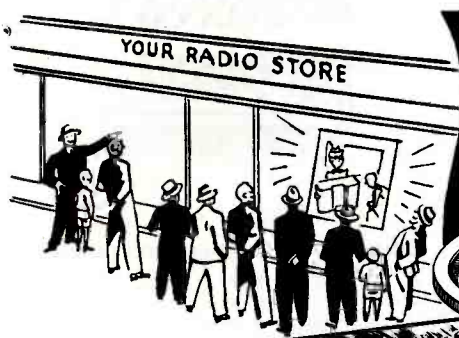

COMIC POSTER
FREE

TO DISPLAY IN YOUR WINDOW!

A crowd-pulling cartoon, size 17"x17", drawn especially for OLSON RADIO WAREHOUSE to give you. It's yours for the asking, absolutely FREE and postpaid. Display it in your window or Service Dept. for laughs — and sales!

Why do we make this offer? Because we want you to become acquainted with Olson Bargains. We will send you a Free Catalog with the poster; this Catalog lists nationally famous Radio Parts at prices that will save you plenty!

Paste this coupon on a postcard
 and MAIL TODAY

OLSON RADIO WAREHOUSE

73 E. MILL ST., DEPT. 59 AKRON, OHIO

Yes sir! Send me the Comic Poster free.

NAME

ADDRESS

CITY.....STATE.....




NEW PRODUCTS

(Continued from page 38)

New York. Other features include individual bass and treble equalizers; two high-impedance microphone inputs and one for phono pickup.

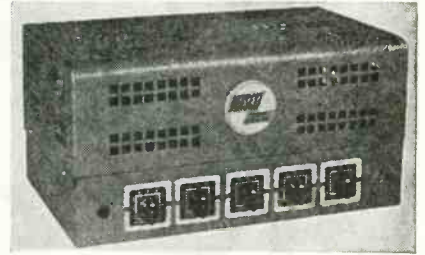Sound systems from 12 to 80 watts are also available.



* * *


MONOBLOCK CONNECTORS

A multiple-contact connector has been announced by The Winchester Co., 6 East 46 Street, New York 17, N. Y.

Molded of Melamine plastic. Two guide pins, acting as ground contacts, perform additional functions of alignment and polarization.

Multiple telescoping barriers serve to isolate contacts, increase both surface creepage and air gap between adjacent contacts. Minimum air gap of 1/4" maintained between all contacts. Contacts are designed for use with a maximum wire size of 16 AWG.

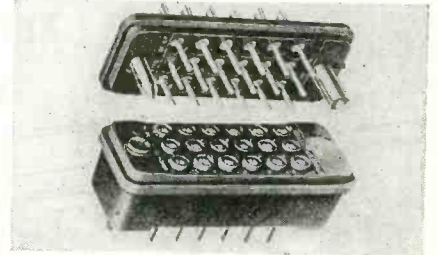Available in two sizes: 18 contacts (RE18S) and 12 contacts (RE12S).



* * *

BRUNO TOOLS HOLE-CUTTER KIT

A kit, 790, for cutting holes of various diameters in wood, metal or plastics has been announced by Bruno Tools, Beverly Hills, California.

Kit contains one adjustable hole cutter (with 1/4" shank) for cutting holes 5/8" to 1 1/4" and another cutter (3/8" shank) that cuts holes 1" to 2 1/2".



* * *

F-M CONVERTER

A unit to convert f-m receivers from 42-50 to 88-108 mc has been announced

Install an aerial the new way—

the **VERTROD** way

EASIER!
FASTER!
BETTER!



As MODERN as 4 wheel hydraulic brakes—compared to the old mechanical brakes.

VERTROD'S—20 model's cover all wave reception...
FM—AM and Television.

VERTROD—vertical models beautify buildings—eliminate poles—
insulators—filters—lightning arrester—climbing.

VERTROD—the most scientific antenna yet evolved.

The VERTROD way (with patented features) is the MODERN way. At most radio shops. Write for folder 413

VERTROD CORPORATION

60 EAST 42nd STREET • NEW YORK 17, N. Y.



You Can Now SIGNAL TRACE with a "Pencil"*

PROVAC

featuring **EDIPROBE**
*Pencil-thin RF probe

The PROVAC electronic vacuum tube volt-ohmmeter permits the laboratory engineer and radio service technician to measure every voltage required in the design laboratory and radio servicing.

Measure R.F. with the same ease as measuring D.C. with the latest development in R.F. probes. It is no longer necessary to guess at which point the signal stops.

DC Ranges: 0 to 3-10-30-100-300 and 1,000 volts. All ranges have a constant input resistance of 11,000,000 ohms. Accuracy 3% ±

AC Ranges: 0 to 10-30-100-300 and 1,000 volts. Sensitivity: 1,000 ohms per volt. Accuracy 5% ±

Electronic Ohmmeter Ranges: 0-1,000 ohms, 0-10,000 ohms, 0-100,000 ohms, 0-1 megohm, 0-10 megohms, and 0-1,000 megohms.

R.F. Voltage ranges 0/3-10-30-50 Volts to be measured on 100 Volt range.

Bridge Amplifier Circuit Meter individually calibrated for use with set of test leads, signal tracer probe and batteries.

Features of the EDIPROBE

- Smallest R.F. probe made.
- Frequency range 40 Cycles to over 100 Megacycles.
- Effective circuit loading: 3 mmf. and 1 megohm.
- Can be used as an output meter.
- Can be used for measuring decibels.
- Checks condensers for open circuit.
- Works with any standard V.T.V.M.


PROVAC Model ED 100 \$5950 VTVM Model 100 \$5250 EDIPROBE \$985 (with EDIPROBE) (without probe) (RF Probe)...

Jobbers and dealers write for exclusive Territory Distribution. Orders addressed to us will be credited to your nearest dealer.

Write Dept SJ for FREE Technical Manual

ELECTRONIC DESIGNS, Inc.

IRVINGTON, NEW YORK

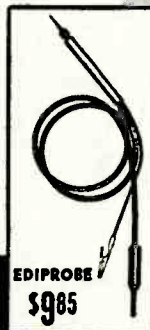

by the Waterproof Electric Company, Burbank, California.


No adjustment or tuning operations are said to be necessary with the unit itself. Size, 1½" x 2" x 4".



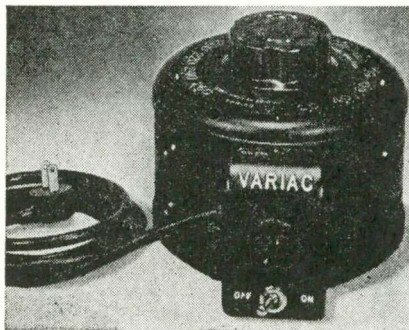G. R. 10-AMPERE VARIAC

Adjustable autotransformers, type 10 Variac, for 115-volts, rated at 10 amperes, with a 15-ampere maximum, coinciding with the capacity of commonly-used outlets, plugs, cords, and No. 14 wire lines, have been announced by General Radio Company, 275 Massachusetts Avenue, Cambridge 39, Massachusetts.

Output voltage continuously variable from zero to 17% above line voltage. Available in 6 models, 115-volt and 230-volt service.



NEWCOMB PORTABLE SOUND SYSTEM

Portable sound systems ranging from 10 to 60-watts power output, have been announced by Newcomb Audio Products Company, 2815 S. Hill St., Los Angeles 7, California.

One type, a 3-case system, includes a 30-watt amplifier, with two 12" loudspeakers.


NHI LINE FILTER

A line filter with six bypass capacitors, two iron-core chokes and two r-f chokes has been announced by New Home Industries, 216 Eldridge Street, New York 2, N. Y.

Filter design said to provide filtering of line noises, fluorescent, elevator, and r-f noises which are superimposed on the line.

SYLVANIA SILICON CRYSTAL CONVERTERS

Silicon crystal converters, types 1N21B, 1N23B and 1N25, for use as first detectors in high-frequency superheterodyne receivers, have been announced by the electronics division, Sylvania Electric Products, Inc. The crystals which are permanently preset in a cartridge approximately ¼" long and ¼" in diam-

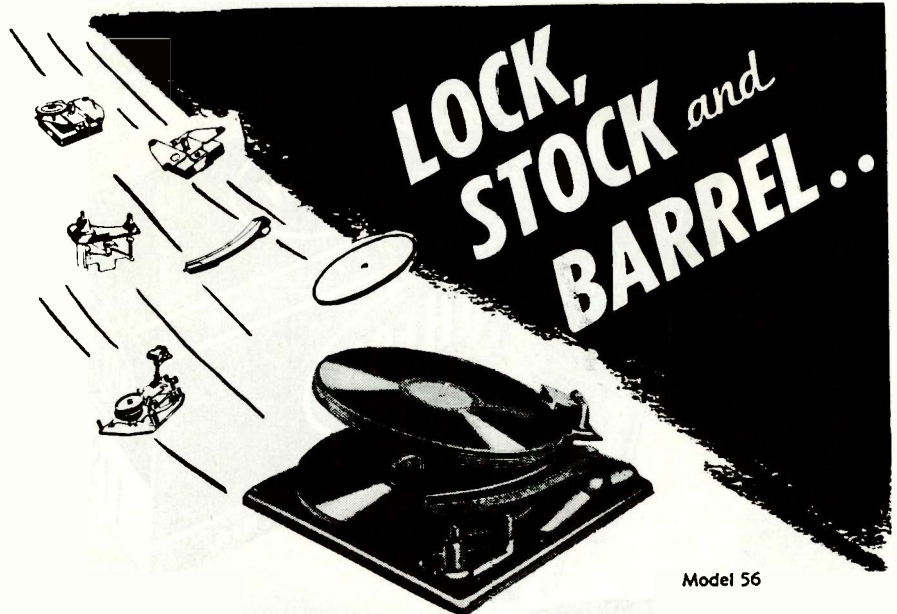

Model 56

WEBSTER *Record Changers*
are made by **WEBSTER**

From raw materials to finished record changer — that's the story at Webster-Chicago. Parts are made and line assembled under constant inspection—resulting in precision record changers that give the utmost listening pleasure and service.



- ✓ Easy to play
- ✓ Built for years of use
- ✓ Fast change cycle
- ✓ Protects records
- ✓ Automatic shut-off

The choice of music lovers

WEBSTER  **CHICAGO**


5610 Bloomingdale Avenue, CHICAGO 39, ILLINOIS

32 years of Continuous Successful Manufacturing

eter are available in three types designed for frequencies up to 10,000 mc.

Type 1N21B, designed for frequencies in the region of 3000 mc, has a 6.5-db conversion loss, maximum; thermal noise

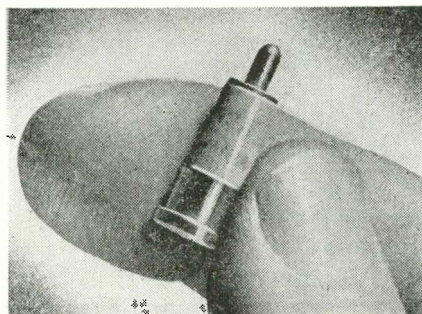ratio of 2.0, maximum; and 1-f resistive impedance of 200 to 800 ohms. Corresponding characteristics for types 1N23B and 1N25 crystals are: 10,000 mc and 1,000 mc; 6.5 db and 8.5 db; 150-600 and 100-400 ohms.



CONCORD RADIO UNIT AMPLIFIERS

Add-A-Unit type amplifiers, with plug-in type power supplies, have been announced by Concord Radio Corporation, Chicago, Ill.

Plug-in power supplies are said to provide power output increase from two to nine times. Additional output stages, to a total of six, can also be added. There is also provision for a phono-

(Continued on page 44)

RAYTHEON
MANUFACTURING COMPANY


Excellence in Electronics
RADIO RECEIVING TUBE DIVISION
NEWTON, MASSACHUSETTS CHICAGO

... and put Raytheon tubes in my set please." That's the customer specifying "Raytheon"—a name he knows to be synonymous with quality and dependability. Stock Raytheon tubes to keep your customers happy; to keep your business growing.

NEW PRODUCTS

(Continued from page 43)

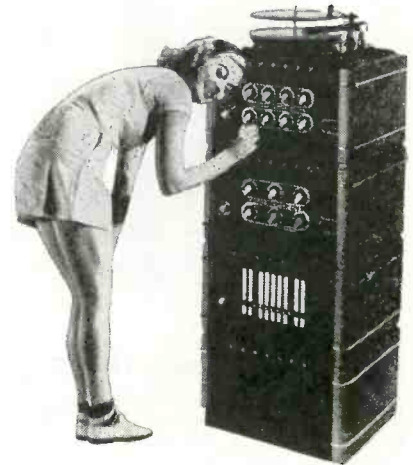player, record changer, and output volume indicator. Portable carrying cases are available.




* * *

ANDREW F-M/TELEVISION ANTENNA

An antenna for f-m and television reception, the Di-Fan, which consists of two sets of five elements extended in two different directions, has been announced by the Andrew Co., Chicago 19.

Impedance of the Di-Fan is said to be matched to the impedance of transmission line, preventing ghost images.

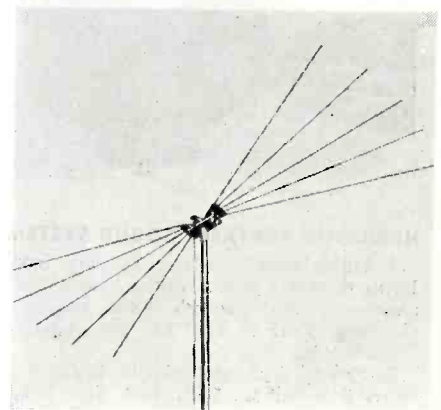Unit uses high-strength aluminum alloy elements. Supporting members are of plated steel. Available with mounting brackets for chimney or roof.



* * *

G. E. COMPOSITION RESISTORS

Composition resistors have been announced by the specialty division of G. E. Resistors are available in standard RMA resistance values and in sizes of one-half, one and two watts.

Other characteristics of the composition resistors are said to be: High resistance to humidity; pigtail leads; and ample insulation.

* * *

STERLING ELECTRONIC TESTER

A portable, graphic type servicing instrument has been announced by The Sterling Manufacturing Company, 9205 Detroit Avenue, Cleveland, Ohio.

The desired function and range are selected by means of two switches of a

A MUST IN EVERY LAB . . .


ON EVERY SERVICEMAN'S BENCH . . .

IN EVERY SERVICE KIT . . .

A pocket-size

OSCILLOSCOPE
The **POCKETSCOPE**

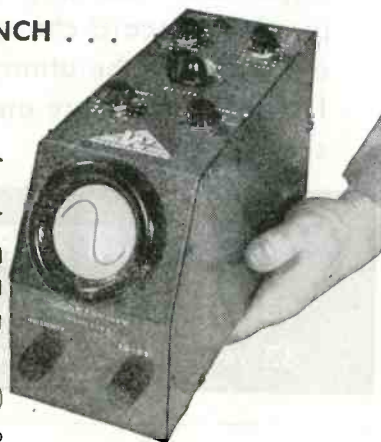- So **SMALL** in size (4" x 6 $\frac{3}{8}$ " x 10")
- So **LIGHT** in weight (5 $\frac{3}{4}$ lbs.)
- So **COMPLETE** in performance
- So **INEXPENSIVE** in price
- Plus **WIDE-ANGLE VISION**: on shelf, on floor, on bench
- Plus **RETRACTABLE LIGHT SHIELD**: for increased visibility.



A 2" "pocket-size" 'scope incorporating the cathode ray tube, vertical and horizontal amplifiers, linear time base oscillator, synchronization means and self-contained power supply.


FOR DELIVERY:

Contact your nearest jobber. If he doesn't have the POCKETSCOPE available, contact us direct.



WATERMAN PRODUCTS CO.
INCORPORATED
PHILADELPHIA 25, PENNSYLVANIA

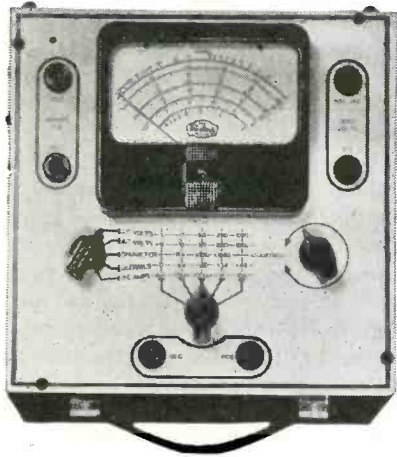graphic selector system. A function switch, is set for the *type* of measurement desired; the range switch, is set for the *range* of the type of measurement indicated by the function switch. Adjustment knob is used to set the meter pointer to zero ohms for the three ohm-meter ranges.



* * *

CANNON ELECTRIC LOW-LEVEL CONNECTORS

Multi-contact electric connectors for low-level sound uses, XL series, have been developed by Cannon Electric Development Co., 3209 Humboldt Street, Los Angeles 31, California.

Size: 2 3/32" overall length, diameter 5/8"; provides polarized contact. Has three 15-ampere silver-plated brass contacts in phenolic insert to accommodate No. 14 stranded wire.

* * *

CLARK P-A AMPLIFIERS

Ten, twenty and thirty-watt amplifiers using terminal-strip component mounting structure, have been developed by Clark Radio Equipment Corporation, 4313 Lincoln Avenue, Chicago 18, Ill.

Terminal strips are mounted so that every part is accessible to test prods and soldering iron. Amplifiers are said to have a 30 to 15,000-cps response.

TELEVISION RECEIVERS

(Continued from page 20)

of the low-impedance triode is that its plate load is essentially resistive and transient troubles are non-existent.

The horizontal amplifier must be a high-impedance pentode which has sufficient power sensitivity to convert the relatively low amplitude horizontal waveform to a large current variation through the deflection coils. A high-impedance tube, with no damping of inductive circuits, has a plate load which is reactive and, therefore, becomes a circuit vulnerable to transients, which is another reason for highly damping the horizontal output circuit. In some receivers, a small

NOW!

A BATTERY OF
SERVICE SHOP
TESTERS IN
ONE COMPACT UNIT!



COMBINATION TUBE AND SET TESTER model 805

WITH instruments mounted all over the shop, servicemen must hop around, like the proverbial one-armed paper hanger, to make their tests. Now, in one compact unit, you can have a complete service shop combination of a multi-meter tube tester, battery tester and capacitor tester. Model 805 is the perfect instrument for servicemen working in close quarters, and where time saved means money earned. This deluxe RCP instrument has been fully engineered and produced to give you the maximum in test economy and efficiency. See it at our jobber now, or write direct for the new RCP Catalog No. 129.

*Low-range ohmmeter is back-up, low-drain type; medium-range ohmmeter is powered by self-contained battery; high-range ohmmeter is operated from plug-in line supply. *Famous exclusive RCP Dynoptimum test circuit. *Complete leakage tests under rated load for all capacitors; readings on "Good-Bad" scale.

When You Go to See Your Jobber
**BE SURE TO SEE RCP—
BEST FOR EVERY TEST**

*Tests ballast and all types of receiving tubes. Neon lamp for speedy short and leakage test between elements. *Jack for headphone noise test of noisy, bad or loose connections. *Filament voltages, from 1.2 to 117 volts, accommodate all present and future tube filaments. *Full loads for "A" and "B" radio battery tests; readings on "Poor-Good" scale. *Tests individual sections of multi-purpose tubes. *Built-in "Rolindex" Tube chart, mechanically perfect, furnishes accurate tube data at the flick of a dial.

RANGES

D. C. VOLTMETER:	0/2.5/10/50/250/1000/ 5000 volts.
A. C. VOLTMETER:	0/10/50/250/1000/5000 volts.
OUTPUT VOLTMETER:	0/10/50/250/1000 volts.
D. C. MILLIAMMETER:	0/1/10/100/1000 ma.
D. C. AMMETER:	0/10 amperes.
OHMMETER:	0/250-2500/25000 ohms. 0/2.5/25 megohms.
DECIBEL METER:	-8 to +15, +15 to +29, +29 to +49, +32 to +55.

RADIO CITY PRODUCTS CO., INC.

127 West 26th Street,



New York 1, N. Y.

amount of inverse feedback in the last stage is used to reduce the effective impedance of the pentode.

Electromagnetic Focusing

Similar magnetic principles are used in focusing a beam of electrons. In this task, however, we rely more on the characteristic that there is *no reaction* between perpendicular magnetic fields but as soon as the angle departs from 90° there is *reaction*. The focus coil is mounted on the neck of the tube in a position which produces a transverse magnetic field; that is, lines of magnetic force parallel to electron beam.


This means the magnetic field surrounding the electron beam is perpendicular to the focus field and there is no interaction. Thus those electrons which move in a straight line through the electron gun toward the fluorescent screen are not affected by the focus field, Fig. 2 (A).

However, when any electrons depart from this straight line path their surrounding field is no longer perpendicular to focusing field and the motion of the beam is affected. The electrons now move in an arc and finally make a complete arc returning once

(Continued on page 46)

Presenting The New Improved JFD REMOTE-O-CABLE REPLACER

**Servicemen's
Net Cost
\$64.30.**

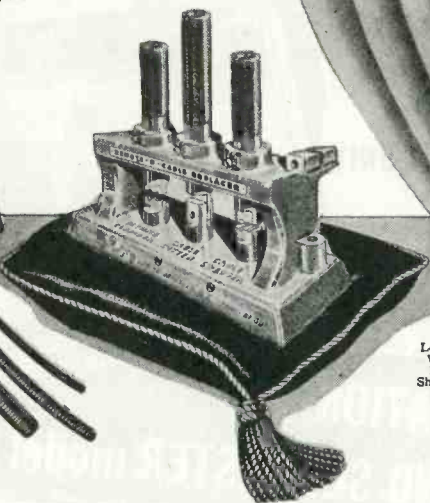

Length 10 1/4 in.,
Width 4 1/4 in.,
Height 13 in.,
Shipping Weight
29 1/4 Pounds

The Most Efficient Auto Radio Tuning Cable-Servicing Machine in Use Today!

1. SWEDGES SHAFTING TO PREVENT UNRAVELLING.
2. CUTS SHAFTING TO EXACT LENGTH.
3. REPLACES OLD FITTINGS ON NEW SHAFTING.
4. CASING GROOVE MAKES CUTTING EASY

J. F. D. MANUFACTURING CO., 4111 FT. HAMILTON PKWAY, BKLYN, N. Y.

PAID CIRCULATION NOW OVER 20,000

Advertising in **SERVICE** is read by radio and electronic servicemen who stock and sell tubes, components, batteries, accessories, test equipment, sound apparatus, etc. They can best be sold through advertising in their magazine — **SERVICE**.

Closing date November issue, November 5


SPEED UP REPAIRS WITH THESE G-C AIDS!

G-C is HEADQUARTERS for RADIO PARTS and SERVICE AIDS



All Types
of Radio
Cements,
Chemicals,
Coil Dopes,
Compounds.

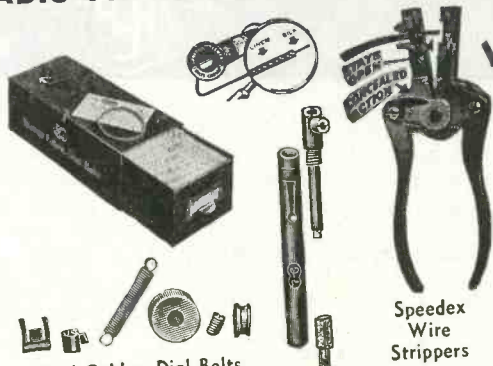G-C leads the field in supplying Radio - Electronic Manufacturers and Service Men with Parts, Tools, Radio Cements, Chemicals and Compounds. Insist on Genuine G-C Quality.



Dial Cables, Dial Belts,
Packaged Hardware,
Cabinet Repair Kits

Alignment Tools
Ne-O-Lite Testers

Speedex
Wire
Strippers

Order from Your Jobber — Send for G-C Catalog



GENERAL CEMENT MFG. CO.
ROCKFORD, ILLINOIS

TELEVISION RECEIVERS

(Continued from page 45)

again to the straight line path. The spot at which all electrons converge is the focused point, by proper setting of the current through the focus coil and proper positioning of the focus coil on the neck of the tube. The focus coil functions, therefore, as the second lens of the electron gun, first lens remaining conventional.

Were it not for the original forward velocity imparted to the electron, the divergent electron would make a complete circle and return to the center. However, its forward attraction causes it to follow a so-called helical path, Fig. 2 (B) which is a resultant of the forward attraction and the circular motion. Thus it can be seen that a number of points of convergence occur, each of which could be called a focus point. In practice, the beam is only under the influence of the focus field for a short interval at which time it is given a sufficient whirl to have the majority of electrons return at the fluorescent screen. Fig. 2 (C).

SALES HELPS

(Continued from page 11)

around for trade or waiting months and months for people to hear of the Shop through the community grapevine. And no man has enough friends or relatives to keep a business alive.

Relative Value of Sales Helps

To bring in business and to establish prestige in the community, a variety of sales helps are available from local jobbers: newspaper mats, illustrated direct-by-mail postcards, window displays, counter cards, decals, stationery, shipping labels and match books.

Of course, no amount of sales promotion will do much good unless the Service Man has made an intelligent survey of his local opportunities. If the locality warrants a Service Shop, however, then the shop warrants sales promotion too. A primary source of radio repair business can be developed through the newspapers. For instance, a local paper with a circulation of 50,000 usually charges about \$10 to run a small mat ad. Figuring inquiries at 1/2 of 1%, or 250 prospects, makes the ad an excellent investment at such low cost. If only 10% of inquiries is converted, the Service Man

would get 25 customers spending \$5
 ✕ more on the average.

Use of Postcards

Let us evaluate penny postcards. There are usually several types to select, each elaborating on the theme that the Service Man, whose imprint appears on the card, is an expert in radio repair work. The Service Man pays only the 1¢ postage for each card, and in our program can order them from his jobber in minimum quantities of 100 for any one card style. Thus, for \$1.00 it is possible to reach 100 carefully selected prospects. Let us assume that 10% is converted into actual sales, each sale totaling \$5 or more. Therefore, the Service Man gets about \$50 in business, certainly a good return. Naturally, larger mailings do not increase the percentage but they do increase the sum total in dollars received. Considering the returns, both mats and postcards are strongly recommended as primary sales promotion material for the Service Shop. Not only do they sell individually, but they support each other's selling efforts.

Choosing Displays

Unfortunately some Service Shop windows I've seen in my travels look like Indian medicine shows of the old days. Everything in it but the tomtom, and sometimes that too. A simple display sells better. It is wiser to show several good, attractive items that please the eye than a window piled up like a stockroom. After all, the space is a show window to the public which judges the Shop's ability on appearances first. No more than two display cards should be placed in any window. Too many confuse prospects.

Only one or two decals to a door! I've seen some radio shop doors that looked like the tattooed lady. The point to remember about any display is that if your customer sees too much he will remember nothing. Decals, offered to you by jobbers, should be mounted tastefully but not to obstruct the view of the shop's interior. The selections should best represent your reliable service to the community.

Interior displays must be carefully chosen too. Some interiors look like anything but a Service Shop, with cards and streamers hanging everywhere to fill in bare counter space or to hide cracks in the wall. If a display sells your service, and sells it well, then it should be used. But don't confuse the issue with umpty-nine different signs, some of which look nice but deliver no sales message for you at all. Remember, what sells for you is good for your business.

A LABORATORY QUALITY OSCILLOSCOPE For the Service Man . . .

Portable, sturdy, compact—the CRO-5A is an ideal unit for rapid, accurate, high quality service work. Check the utility and features which you have always wanted in the instrument on your bench.

- For better laboratory and production testing . . .
- For routine Service work . . .
- For studying any variable which may be translated into electrical potentials by means of associated apparatus . . .
- Designed with tubes for maximum amplification with minimum noise . . .
- Exceptionally stable trace even under adverse power line variations . . .
- Frequency response—essentially flat from 20 cycles to 350 KC . . .
- Completely self-contained . . .

Write to General Electric Company, Electronics Department SS-6407, Syracuse 1, New York.



GENERAL ELECTRIC

177-E2



10H 40 MA. CHOKE
 Extremely compact highly efficient choke well suited for auto radio receivers and AC/DC radios. Also excellent filter chokes for other receivers and amplifiers. 1 5/16" x 1 1/4" x 1 3/4" ins. Unshielded strap type mounting. **46¢**
C1601

Midget Electrolytic
 Midget dry electrolytic will handle any job requiring a polar-electrolytic capacitor. Polarity clearly indicated. Barely replaces larger wire leads. Easily replaces larger capacitors. Cap. Mid 20-20. DC-WV 160. 3/4" x 2 inches **60¢**
C3153

ROTARY SWITCH
 Single gang, 6 pole, 3 position, shorting switch. 1 5/16" dia. with 1/4" shaft dia. Threaded bushing 3/4" long. 3/8" shaft. **39¢**
5B3984

RADIO PARTS SETS • AMPLIFIERS Concord Catalog FREE!

Revised! Up-to-the minute! Listing the newest, the latest and best in RADIO PARTS, RADIO SETS, AMPLIFIERS, AMATEUR GEAR, ELECTRONIC EQUIPMENT, SUPPLIES and ACCESSORIES! Hundreds of items for every Radio and Electronic need—Condensers, Resistors, Transformers, Tubes, Test Equipment, Tools and Repair, Replacement and Maintenance Parts of every kind. ●●● All standard top quality, nationally famous makes, are fully represented in the great new Concord Catalog. Complete lines including new and hard-to-get parts and equipment at latest O.P.A. prices or lower. Thousands of items—and complete stocks ready for immediate shipment from CHICAGO or ATLANTA. Your copy of the new Concord Catalog is ready now—FREE! Mail the Coupon below.

SEE . . . COMPLETE SHOWING of ham gear, equipment, supplies and accessories for AMATEURS, ENGINEERS, SERVICEMEN, SOUNDMEN, RETAILERS.

SEE . . . the first peacetime Concord line of modern Radio Sets and Radio Phonograph combinations—featuring a host of new, approved post-war developments . . . richer tone quality . . . super-selective tuning and reception . . . high fidelity . . . new modern design cabinets.

SEE . . . the thrilling new MULTIAMP Add-A-Unit Amplifiers, entirely new and revolutionary development in amplifier engineering. Sensational flexibility, power, fidelity, and economy, exclusive with Concord!

All in the new complete Concord Catalog. Mail the COUPON Now!

CONCORD RADIO CORPORATION

LAFAYETTE RADIO CORPORATION
 CHICAGO 7 ATLANTA 3
 901 W. Jackson Blvd. 265 Peachtree Street

CONCORD RADIO CORPORATION, Dept. S-106,
 901 W. Jackson Blvd., Chicago 7, Illinois
 Yes, rush FREE COPY of the comprehensive new
 Concord Radio Catalog.

NAME _____
 ADDRESS _____
 CITY _____ STATE _____

Order from LAKE!
You'll Make No Mistake!

RADIO CABINETS & PARTS

NOW AVAILABLE!



**Postwar
2 Post
RECORD-
CHANGER**

With luxurious brown leatherette portable case. 15" L.


x 15" W. x 10" D. Latest electronic developments make this modern record-changer the finest on the market today!

Changer..... **\$19.00**
Cabinet for same..... **8.95**

DE LUXE RECORD-CHANGER and AMPLIFIER CASE

De luxe changer case with ample room for amplifier. Overall dimensions: 20" L. x 16" W. x 10" H. Sturdily built of 3/4" plywood, de luxe brass hardware throughout. Inside dimensions: 15 1/2" L. x 14 1/4" W. x 9 1/4" H.


Net **\$12.95**

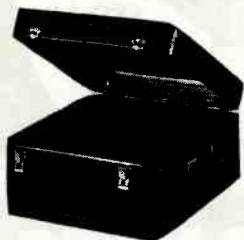

**DELUXE
PHONO
CABINET**

Covered in luxurious, genuine brown leatherette, has de-luxe brass

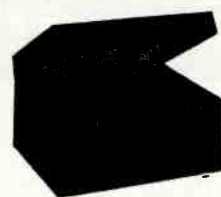hardware throughout, made completely of plywood with brown plastic handle, has padded top and bottom. Motor board 14" x 14 1/2". Overall dimensions 16" L. x 15" W. x 8" H. Your net price..... **\$8.95**



Portable Phono-graph Case of sturdy durable plywood, in handsome brown leatherette finish. Inside dimension 16 1/2" long, 14" wide, 9 1/2" high. Has blank motor board. As illustrated specially priced at

\$6.95

Also blank table cabinets of walnut veneer in the following sizes, with speaker opening on left front side: (*Note: *7 has center speaker grill.)

# 1 - 8 1/2"	L x 5 1/2"	H x 4"	D \$1.95
# 2 - 10 1/2"	L x 6 1/2"	H x 5"	D \$2.75
# 3 - 12 1/2"	L x 7 1/2"	H x 6 1/2"	D \$3.25
# 7 - 18 1/2"	L x 11"	H x 8 1/2"	D \$2.99

*Speaker Opening in center of front side.

All types of radio cabinets and parts are available at Lake's Lower prices. A large stock is listed in our catalog.

**SERVICEMEN-
RETAILERS**

Join our customer list today.
Dept. D

**Order our New Catalog Today!
Get on our mailing list!**

Lake Radio Sales Co.
615 W. Randolph Street
Chicago 6, Ill.

JOTS AND FLASHES

THE WEEK OF NOVEMBER 24TH TO 30TH will be known as National Radio Week. The National Association of Broadcasting and RMA are planning quite a sales-promotion campaign for that week. . . . The National Electronic, Radio & Television Exhibition scheduled for Grand Central Palace on October 14th to 19th was postponed to the early part of 1947. Curtailment of production and corresponding lack of receivers and parts was given as the reason for the postponement. . . . Television-antenna installation methods are now being planned for Chicago by R. Cooper, Jr., Inc., Commonwealth Edison and Television Associates. The latter unit was organized by Captain Bill Eddy, station manager of telecast station WBKB. The Cooper Company are G. E. distributors. Proposed installation charges will vary from \$50 to \$60. . . . Bernard Benson has been named purchasing agent for the Utah Radio Products Division of International Detrola Corporation. . . . Don G. Mitchell, president of Sylvania Electric, has been named to serve on the National Distribution Council. . . . Major Bernard L. Cahn is now executive assistant in charge of sales and promotion at Insuline. . . . Samuel McDonald, Jr., has been appointed to the sales staff of the radio tube division of Sylvania. He will serve in the New York and Philadelphia area. . . . Rex L. Munger has resigned as sales manager of Taylor Tubes, Inc., 2312 Wabansia Avenue, Chicago. . . . Record receiver production was established during August when over 1,500,000 sets were produced. Of these over 1,000,000 were table models and over 100,000, console and radio-phonograph models. About 20,000 f-m sets were also produced in August. . . . Barker & Williamson have leased a new plant in Bristol, Pa. The present plant at 237 Fairfield Avenue, Upper Darby, Pa., will be retained. . . . The annual convention of Hoffman Radio distributors will be held on November 6th, 7th and 8th at the Mayfair Hotel in Los Angeles. . . . The current issue of the Centralab jobber house organ contains a list of price changes on volume controls and accessories. . . . M. W. Gasner, 71 Front Street, East, Toronto, Canada, has been named Canadian representative of the National Electronic Mfg. Corp., Long Island City, N. Y., who produce auto antennas and components. . . . Elliott A. Witten is now with the advertising department of Radio Wire Television, Inc., N. Y. C. . . . E. A. Ossmann has been named factory representative for Allen B. DuMont Labs. He will operate out of Rochester and cover New York State with the exception of metropolitan New York and Long Island. . . . WABC will use new call letters, WCBS, after November 1st. The call letters of the f-m and t-v stations of CBS will also be changed to WCBS-FM and WCBS-TV. . . . Chester J. Frey has been named eastern district sales representative for the Belden Mfg. Corp., Chicago. . . . Lawrence M. Braun has resigned as vice president of ECA and ECA International to form a metal and plastics component manufacturing company, the Rich-Marc Mfg. Co., Inc., 42 W. 28th Street, N. Y. C. . . . Quam-Nichols has become an Illinois corporation. James P. Quam is president; Matt Little, Jr., vice president; P. L. Dawes, secretary and assistant treasurer and Helen A. Staniland, treasurer and assistant secretary.

ADVERTISERS IN THIS ISSUE

SERVICE INDEX—OCTOBER, 1946

AEROVOX CORP.	34
Agency: Austin C. Lescarboursa & Staff	
ALMO RADIO CO.	40
AMERICAN PHENOLIC CORP.	19
Agency: Burton Browne, Advertising	
THE ASTATIC CORPORATION	29
Agency: Wearstler Advertising, Inc.	
BURSTEIN-APPLEBEE CO.	34
Agency: Frank E. Whalen Adv. Co.	
CAPITOL RADIO ENGINEERING INSTITUTE ..	39
Agency: Henry J. Kaufman & Associates	
CHERRY RIVET COMPANY	35
Agency: Dana Jones Co.	
CLAROSTAT MFG. CO., INC.	32
Agency: Austin C. Lescarboursa & Staff	
CONCORD RADIO CORP.	47
Agency: E. H. Brown Advertising Agency	
CORNELL-DUBILIER ELECTRIC CORPORATION	
Inside Front Cover	
Agency: Reiss Advertising	
CORNISH WIRE CO., INC.	32
Agency: Hart Lehman, Advertising	
DRAKE ELECTRIC WORKS, INC.	34
Agency: William Hoffman & Associates	
J. V. DUNCOMBE CO.	40
ELECTRONIC DESIGNS, INC.	42
Agency: Bass & Weber Co., Inc.	
ELECTRO-VOICE, INC.	Inside Back Cover
Agency: Henry H. Teplitz, Advertising	
FEDERAL TELEPHONE & RADIO CORP.	25
Agency: Rickard & Co.	
FLANAGAN RADIO CORP.	28
Agency: Stewart Jordan Co.	
GENERAL CEMENT MFG. CO.	46
Agency: Turner Adv. Agency	
GENERAL ELECTRIC CO.	47
Agency: Maxon, Inc.	
GENERAL ELECTRIC SUPPLY CO., INC.	32
HOLLANDER RADIO SUPPLY CO.	38
Agency: Turner Advertising Agency	
J. F. D. MFG. CO.	46
Agency: Bergman-Jarrett Co.	
JACKSON ELECTRICAL INSTRUMENT CO.	37
Agency: Kircher, Helton & Collett, Inc.	
JENSEN MFG. CO.	4
Agency: Burton Browne, Advertising	
KEN-RAD DIV. GENERAL ELECTRIC CO.	1
Agency: Maxon, Inc.	
LAKE RADIO SALES CO.	48
Agency: Sander Rodkin Advertising Agency	
LIFETIME SOUND EQUIPMENT CO.	32
Agency: The Miller Agency Company	
MAGUIRE INDUSTRIES, INC.	3
Agency: City Advertising Agency	
M. V. MANSFIELD CO.	40
METROPOLITAN ELECTRONIC & INSTRUMENT CO.	28
Agency: Bass & Weber Company, Inc.	
MURRAY HILL BOOKS, INC.	27
Agency: The Harry P. Bridge Co.	
NATIONAL UNION RADIO CORP.	Back Cover
Agency: Hutchings Advertising Co., Inc.	
NEWCOMB AUDIO PRODUCTS CO.	26
Agency: Stevens-Hall, Advertising	
OLSON RADIO WAREHOUSE	41
Agency: Jessop Advertising Co.	
RADIO CITY PRODUCTS CO., INC.	45
Agency: Reiss Advertising	
RADIO CORP. OF AMERICA	21
Agency: J. Walter Thompson Co.	
RADIO SUPPLY & ENGINEERING CO., INC.	26, 36
Agency: Karl G. Behr Advertising Agency	
RADIO TELEVISION SUPPLY CO., INC.	40
RADIONIC EQUIPMENT CO.	38
Agency: Bass & Weber Co., Inc.	
RADIO WIRE TELEVISION, INC.	28
Agency: Reiss Advertising	
RAYTHEON MFG. COMPANY	44
Agency: Burton Browne, Advertising	
JOHN F. RIDER PUBLISHER, INC.	15
Agency: Lansford F. King, Advertising	
HOWARD W. SAMS CO., INC.	17
Agency: The Altkin-Kynett Co.	
SCENIC RADIO & ELECTRONICS CO.	40
SHURE BROTHERS, INC.	33
Agency: H. M. Gross Co.	
SIMPSON ELECTRIC CO.	5
Agency: Kreckler & Meloon, Inc.	
SOLAR CAPACITOR SALES CORP.	9
Agency: O. S. Tyson & Co., Inc.	
SPRINGS PRODUCTS COMPANY	6-7
Agency: The Harry P. Bridge Co.	
SUN RADIO & ELECTRONICS CO.	40
Agency: Bass & Weber Co., Inc.	
SYLVANIA ELECTRIC PRODUCTS, INC.	10
Agency: Newell-Emmett Co.	
TRIPLETT ELECTRICAL INSTRUMENT CO.	41
Agency: Western Adv. Agency, Inc.	
UNITED TRANSFORMER CORP.	31
Agency: Shappe-Wilkes Inc.	
VERTROB CORPORATION	42
Agency: Bass & Weber Co., Inc.	
WARD LEONARD ELECTRIC CO.	38
Agency: Henry H. Teplitz, Advertising	
WATERMAN PRODUCTS CO., INC.	44
Agency: Abner J. Gelala & Associates	
WATERPROOF ELECTRIC CO.	36
WEBSTER-CHICAGO CORP.	43
Agency: William Hoffman & Associates	




"Cardyne" Cardioid Dynamic
Models 731 and 726



"Cardax" Cardioid Crystal
Model 950



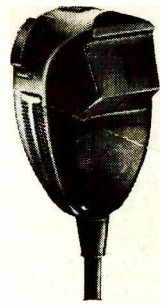Bi-Directional Velocity
Models V-3, V-2, V-1




Differential Carbon
Hand-Held Model 205-S




Model 610 Dynamic
Model 910 Crystal

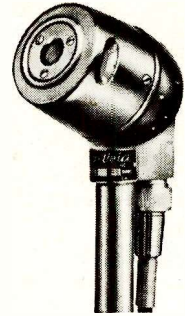No finer choice than
Electro-Voice
TODAY'S MOST COMPLETE LINE OF
MICROPHONES



Differential Dynamic
Model 606

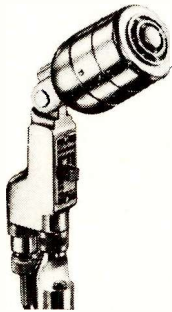


High Fidelity Dynamic
Model 630

WITH important E-V developments such as the *Mechanophase** Principle, the *Differential†* Principle, the *Acoustalloy* Diaphragm... ELECTRO-VOICE brings you the widest selection of quality microphones, for both general and specific applications. In the complete E-V line of uni-directional, bi-directional, and non-directional types, you can easily find exactly the right microphone to give you the sound pick-up and reproduction you want. A few models are shown here. ELECTRO-VOICE engineers are glad to help you on any special problems. *Send now for new E-V Catalog No. 101.*


*Patents Pending †Patent No. 2,350,010
Crystal Microphones Licensed under Brush patents.



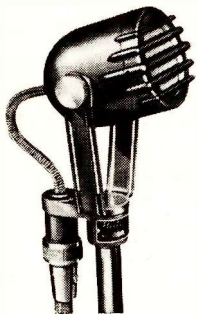
Hand-Held Dynamic Model 600-D
Differential Dynamic Model 602




Versatile Dynamic
Model 640

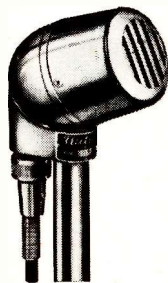

General-Purpose Dynamic
Model 605

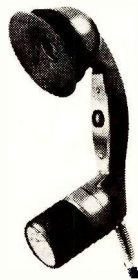

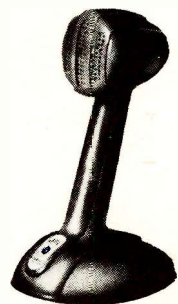Differential Handset
Model 260 Carbon, Model 660 Dynamic



Comet Crystal
Model 902

NO FINER
CHOICE THAN

Electro-Voice

ELECTRO-VOICE, INC.

BUCHANAN, MICHIGAN

EXPORT DIVISION

13 East 40th Street, New York 16, N.Y., U.S.A. Cables: Arlab

National Union Announces an
**EXCLUSIVE RADIO
 MERCHANDISING
 PLAN** for Service Engineers



HERE IT IS AT LAST! The radio line thousands of service engineers have been waiting for—yes, the radio that has *everything* the service trade needs to cash-in on today's big pent-up new set demand.

And who else but National Union could provide a merchandising plan for radio sets—so perfectly fitted to the service engineer's special needs?

For over 15 years National Union products, plans and policies have been shaped for the exclusive benefit of service dealers.

And now N.U. RADIO SETS are here—for the same service men who have so long known and used other N.U. products—and have found the N.U. way of doing business a better, more profitable one for their special type of operations.

THE LINE—5 models, of which one 5-tube and one 6-tube model are now ready; three others available in 90 days.

THE PRODUCT—Top quality throughout; precision-built chassis; beautiful cabinets in modern designs.

PERFORMANCE—Thoroughly up-to-the-minute; N.U. sets compare with the best in their class.

PRICES—Competitive with established brands.

VOLUME REQUIREMENTS—None! N.U. sets are not sold on a franchise basis. Order whatever quantity you need.

DISTRIBUTION—Sold only through N.U. Distributors and Service Dealers.



PRESENTATION MODEL No. G619. 6 Tubes. AC-DC. Tuned R.F. Stage. Superheterodyne Circuit. Loop Aerial. Automatic Volume Control. Illuminated Slide-Rule Dial. Standard American Broadcasts. Mahogany Veneer All-Wood Table Cabinet, 13" x 8 $\frac{3}{4}$ " x 6 $\frac{1}{2}$ ".



COMPANION MODEL No. 571. 5 Tubes. AC-DC. Superheterodyne Circuit. Built-in Antenna. Automatic Volume Control. 2-Gang Air Condenser Tuning. Illuminated Slide-Rule Dial. Standard American Broadcasts. Walnut Veneer All-Wood Table Cabinet, 13 $\frac{1}{8}$ " x 7 $\frac{1}{8}$ " x 8 $\frac{3}{8}$ ".

OTHER MODELS NOW BEING PLANNED

- A 3-Way (AC-DC-Battery) Portable Model.
- A Combination Table Model Radio-Phonograph with Automatic Record Changer.
- A 6-Tube Battery-Powered Farm Radio Table Model.

Here, for the first time, is a practical post-war radio line for the service engineer to handle—a group of fine modern radio sets—but *above all* a proven merchandising plan which *fits*. Ask your N.U. Distributor for the complete facts today!

NATIONAL UNION RADIO CORPORATION, NEWARK 2, N. J.

**NATIONAL UNION
 RADIOS, TUBES AND PARTS**

Transmitting, Cathode Ray, Receiving, Special Purpose Tubes • Condensers • Volume Controls • Phototubes
 Panel Lamps • Flashlight Bulbs • Radio Sets • Auto Vibrators • Ballasts • Batteries