



**BABANI PRESS No.12**

**HI-FI, P.A., GUITAR &  
DISCOTHEQUE  
AMPLIFIER  
DESIGN  
HANDBOOK**

**BY**

**B.B. BABANI**

**INCLUDES CIRCUITS UP TO 1100 WATTS OUTPUT  
TREMOLO, VIBRATO AND FUZZ-BOX ETC.**

**75p**

**HI-FI, P.A., GUITAR &  
DISCOTHEQUE  
AMPLIFIER  
DESIGN  
HANDBOOK**

**BY**

**B.B. BABANI**

**BABANI PRESS**

The Publishing Division of  
Babani Trading and Finance Co. Limited  
The Grampians,  
Shepherds Bush Road,  
London W6 7NF



1st Published November 1972

Reprinted, October 73

We invite all authors, whether new or well established, to submit manuscripts for publication. The manuscripts may deal with any facet of electronics but should always be practical. Any circuit diagrams that may be included should have been thoroughly checked by the author. If you are considering trying your hand at writing this type of book we suggest that you let us have a short summary of the subject you intend to cover. We will then be able to let you know the size of book required and perhaps give you some advice on presentation.

BERNARD B. BABANI

I.S.B.N. 0 85934 011 2

© 1972

Printed by  
Jos. Adam, Avenue E. G. Lebon 115, B-1160 Brussels, Belgium  
for Babani Press, The Publishing division of Babani Trading  
and Finance Co. Ltd., The Grampians, Western Gate,  
London, W.6

## INTRODUCTION

Dear Reader,

I would like to take this opportunity of thanking the following manufacturers of extremely high grade audio equipment for giving us permission to use data and circuitry from their technical publications and engineering departments.

G. E. C. Marconi Osram Valve Co. Ltd., Mullard Ltd., R. C. A. Ltd., Thorn Radio Valves and Tubes Ltd.

It should be noted, however, that no application should be made to any of these firms for help, further information or data with reference to any of the contents published in this book. Any help required must be sent to the publishers of this book who will then answer to the best of their ability.

We also would like to thank many technical magazines and manufacturers of audio equipment in the continent of Europe and the United States of America who have made available to us vast quantities of data.

## NOTES

This book covers the design of amplifiers up to 1100 watts output and most of these circuits are using valves. The reason is that the design of high powered Hi Fi audio amplifiers using transistors with an output of above 100 watts are difficult to construct outside of commercial laboratories etc. and the cost could be extremely high. At a later date we shall publish a handbook covering construction of high powered solid state amplifiers, as soon as we are satisfied that the home constructor can build them without any serious problems arising. Many of the circuits shown for tremolo's, vibrato's and fuzz boxes use transistors as this makes them easy to construct, cheap and portable. They may be connected to valved apparatus without any problems and will work just as well as when operated with transistorized amplifiers of lower output.

## SPECIAL NOTE FOR NORTH AMERICAN READERS

In order to help readers of this book in the U.S.A., a table of tube equivalents showing American types that may be used in place of the British tubes shown in the circuits in this book. Where no alternatives are shown, your local parts dealer will, undoubtedly, be able to supply you with a British original

British	U.S.A. Types
<b>Tubes</b>	
B309	12AT7-6061-6201-6679
DH77	6AT6-6BT6-6066
ECC82	12AU7-5814-5963-6067-6189
ECC83	12AX7-12BZ7-12DF7-5751-6057
ECL86	6GW8
EF86	6BK8-6CF8-6267
EL84	6BQ5-7189-7320
EZ90	6BX4-6X4-5993-6202
GZ34	5AR4-5AW4-5CG4-5T4-5U4-5W4
KT33C	25A6-25C6
KT66	6CN5-6L6-5881-5932
KT88	6CA7-6550
N709	6BQ5-7189-7320
U52	5AR4-5AW4-5CG4-5T4-5U4-5W4
U78	6BX4-6X4-5993-6202
U709	6BW4-6CA4
Z729	6BK8-6CF8-6267
<b>Transistors</b>	
BC109	SK3020
<b>Rectifier Diodes</b>	
BY105	SK3051

## CONTENTS

	Page
<b><u>CHAPTER 1</u></b>	
Tremolo and Vibrato Units	7
Circuit 1 - Add-On Tremolo Unit	
Circuit 2 - Tremolo Unit using 2 Valves	
Circuit 3 - Transistorised Tremolo Unit	
Circuit 4 - Combined Tremolo and Vibrato Unit for Electronic Guitars	
Circuit 5 - High Power Vibrato Add-On Unit	
Circuit 6 - Self Powered Vibrato Add-On Unit	
Circuit 7 - Transistorised Vibrato Unit	
Circuit 8 - Simple Vibrato Unit with Single Transistor	
<b><u>CHAPTER 2</u></b>	
Electronic Accessory Units for Discotheque and Musical Group Use	17
Circuit 9 - Simple Fuzz Box	
Circuit 10 - High Output Fuzz Box	
Circuit 11 - Tone Control Corrector	
Circuit 12 - General Purpose Transistorised Microphone Pre-Amplifier	
Circuit 13 - Sub-Miniature Audio Compressor	
Circuit 14 - Valved Electronic Compressor/Limiter	
Circuit 15 - Psychedelic Coloured Light Unit for Audio Amplifiers	
<b><u>CHAPTER 3</u></b>	
Amplifiers of 12 to 14 Watt Output	23
<b><u>CHAPTER 4</u></b>	
Amplifiers of 15 to 30 Watt Output	32
<b><u>CHAPTER 5</u></b>	
Amplifiers of 50 to 100 Watt Output	42
<b><u>CHAPTER 6</u></b>	
Class B Amplifiers of 175 to 200 Watt Output	51
<b><u>CHAPTER 7</u></b>	
Class AB Amplifiers of 100 to 300 Watt Output	59
<b><u>CHAPTER 8</u></b>	
Class AB Amplifiers of 300 to 1100 Watt Output	66

## CHAPTER 9

Multiple Pair Push-Pull Amplifiers 73

## CHAPTER 10

Pre-Amplifiers and Tone Control 82

## CHAPTER 11

15 Watt High Fidelity Audio Amplifiers by R.C.A. 94

## CHAPTER 12

30 Watt High Fidelity Audio Amplifiers by R.C.A. 96

## CHAPTER 13

Audio Units by R.C.A. 99

Two Channel Audio Mixer  
Magnetic Pick-Up Pre-Amplifier  
Tape Head Pick-Up Pre-Amplifier  
Ceramic Pick-Up Pre-Amplifier  
Low Distortion Pre-Amplifier  
Bass and Treble Tone Control Amplifier

## CHAPTER 14

Mullard 20 Watt Amplifier 105

## CHAPTER 15

Mullard 2 and 3 Valve Pre-Amplifiers 112

## CHAPTER 16

Brimar VP10 Mono Pre-Amplifier 124

## CHAPTER 17

20 Watt Brimar VA12 Amplifier 133

## CHAPTER 18

75 Watt Amplifier - Brimar Design 139

## CHAPTER 1

### TREMOLO AND VIBRATO UNITS

#### CIRCUITS FOR TREMOLO UNITS

Tremolo is the name given to the effect produced when an amplitude modulation is presented to the signal. This modulation functions normally at a frequency of between 5 - 15 cycles per second from a phase shift oscillator. The oscillator is controlled by a potentiometer which varies the frequency. The depth control fitted varies the output level which is the actual depth of modulation taking place. This output in commercial operations will often be fed to the biasing point of a pre-amplifying stage and, therefore, alters the bias voltage and thus varies at a regular rate the gain of this stage. The most commonly used method of achieving these variations, which can be controlled by hand, is to use a light source operated from the oscillator and a facing L.D.R. (Light Dependant Resistor). This causes the resistance of the L.D.R. to alter with the level of light presented to it and thus cause the varying oscillations. In some cases, this variation is so connected that it can short the amplified signal to earth at the rate of oscillation. This has the effect of producing a variable volume change automatically at the amplifier itself.


#### ADD ON TREMOLO UNIT PRECEEDING OUTPUT STAGE OF A VALVED AMPLIFIER Circuit 1

This circuit can be built to fit in as a permanent part of a valved amplifier using half of an ECC83 twin triode valve and very few components. It will produce excellent results.
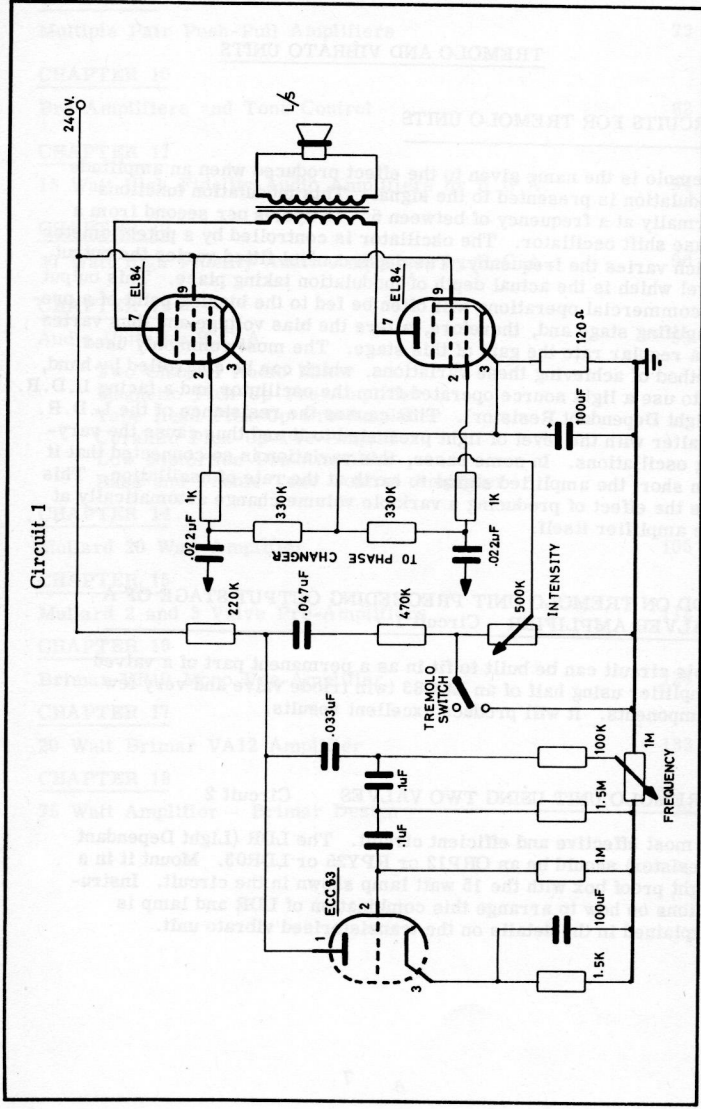
#### TREMOLO UNIT USING TWO VALVES Circuit 2


A most effective and efficient circuit. The LDR (Light Dependant Resistor) should be an ORP12 or RPY25 or LDR03. Mount it in a light proof box with the 15 watt lamp shown in the circuit. Instructions on how to arrange this combination of LDR and lamp is explained in the details on the transistorised vibrato unit.





8

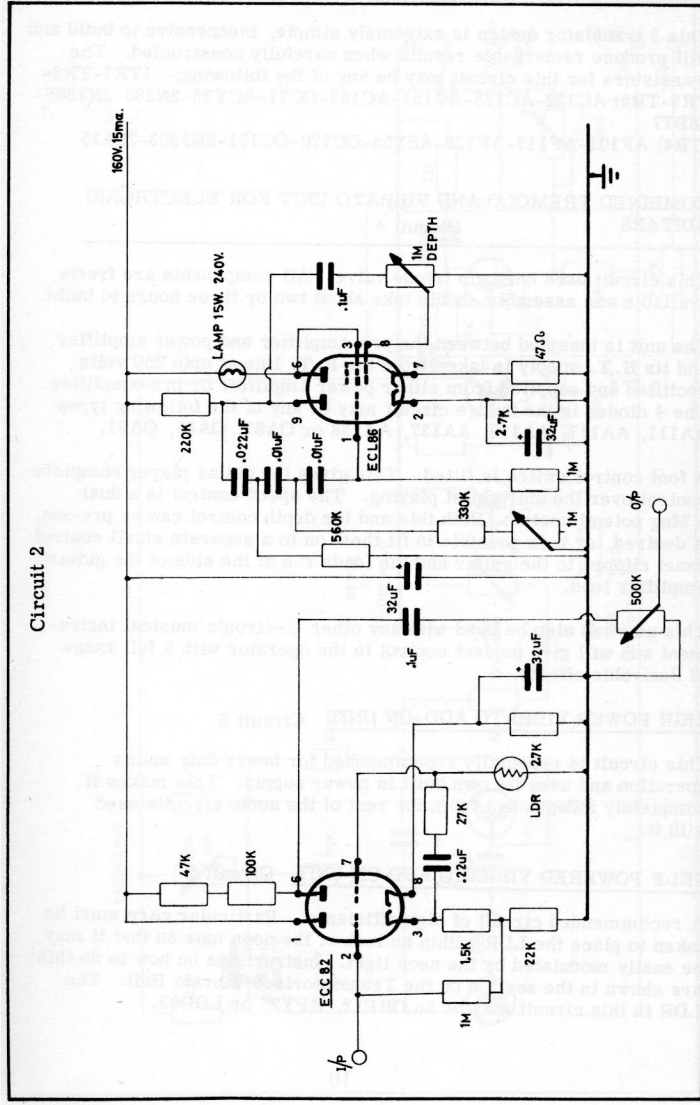ADD-ON TREMOLO UNIT PRECEDING OUTPUT STAGE OF A VALVED AMPLIFIER



9

### TRANSISTORISED TREMOLO UNIT Circuit 3

This 5 transistor design is extremely simple, inexpensive to build and will produce remarkable results when carefully constructed. The transistors for this circuit may be any of the following:- (TR1-TR2-TR3-TR5) AC122-AC125-AC151-AC163-OC71-ACY35-2N280-2N1305-2SB77  
(TR4) AF101-AF117-AF126-ASY55-OC170-OC171-2N1303-2SA15

### COMBINED TREMOLO AND VIBRATO UNIT FOR ELECTRONIC GUITARS Circuit 4

This circuit uses one twin triode valve. All components are freely available and assembly should take about two or three hours to build.

The unit is inserted between the pre-amplifier and power amplifier and its H. T. supply is taken from the H. T. line at upto 250 volts rectified and supplied from either power amplifier or pre-amplifier. The 4 diodes in the bridge circuit may be any of the following types: AA111, AA117, AA119, AA137, AA138 or OA81, OA85, OA91.

A foot control switch is fitted. This gives the guitar player complete control over the unit whilst playing. The speed control is a dual 1 Meg potentiometer. Both this and the depth control can be pre-set, if desired, or it is possible to fit them on to a separate small control panel clipped to the guitar and the leads run at the side of the guitar amplifier lead.


This unit can also be used with any other electronic musical instrument and will give perfect control to the operator with a full range of desirable effects.


### HIGH POWER VIBRATO ADD-ON UNIT Circuit 5

This circuit is especially recommended for heavy duty mains operation and uses its own built in power supply. This makes it completely independent from the rest of the audio circuits used with it.

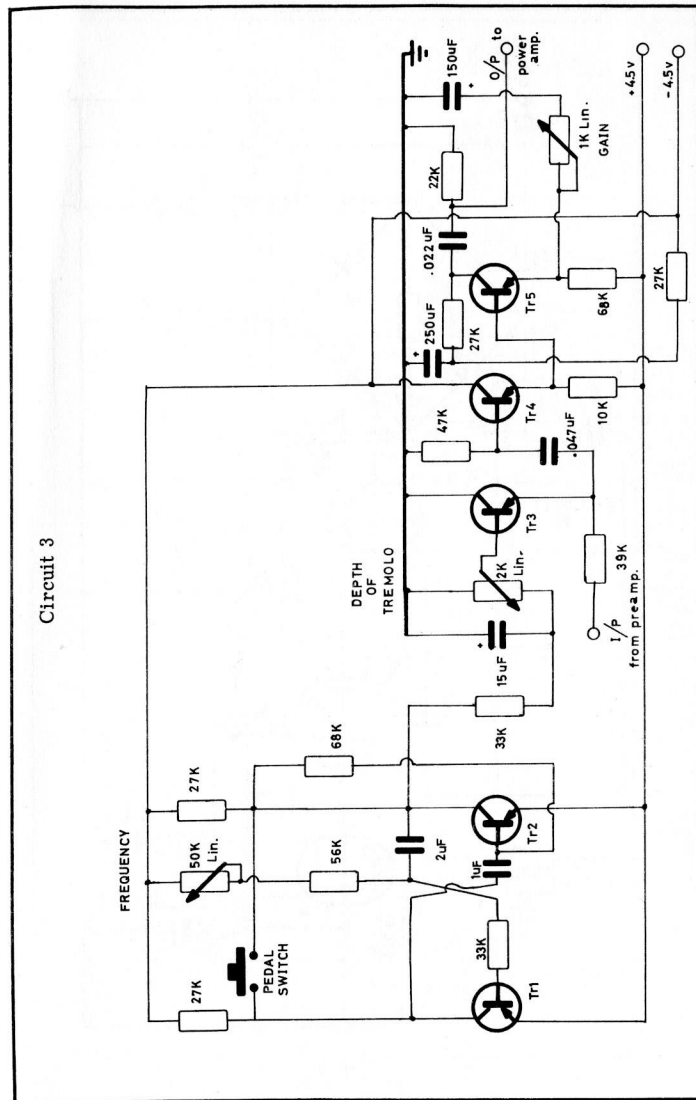
### SELF POWERED VIBRATO ADD ON UNIT Circuit 6

A recommended circuit of high efficiency. Particular care must be taken to place the LDR within an inch of the neon tube so that it may be easily modulated by the neon light. Instructions on how to do this are shown in the section on the Transistorised Vibrato Unit. The LDR in this circuit may be an ORP12, RPY25 or LDR03.



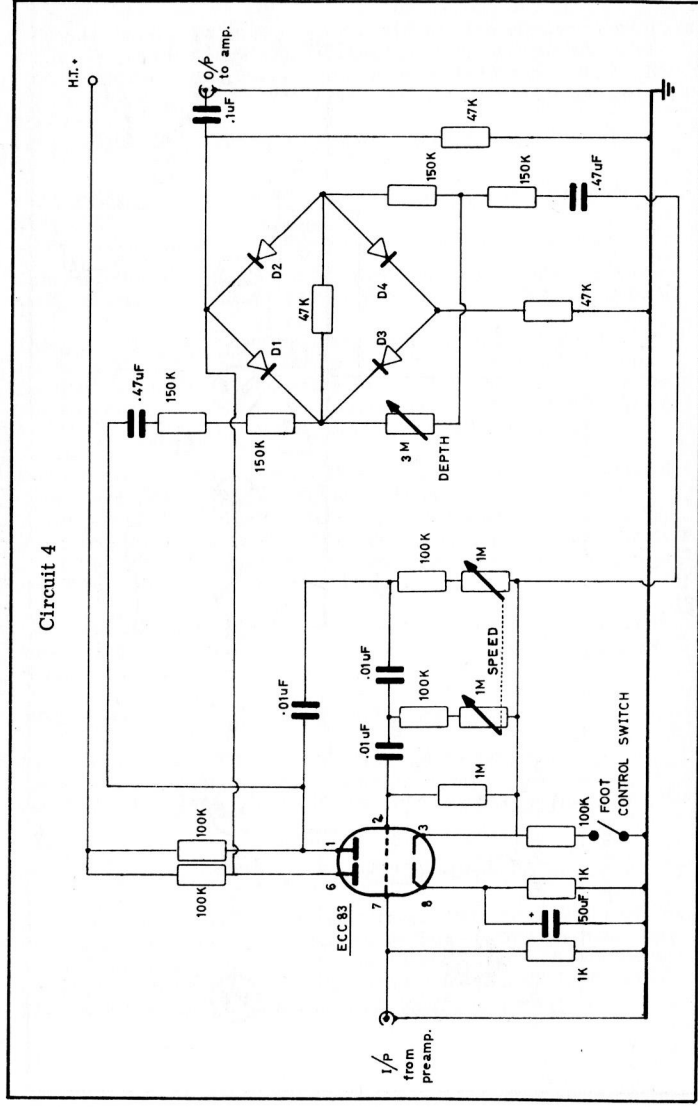


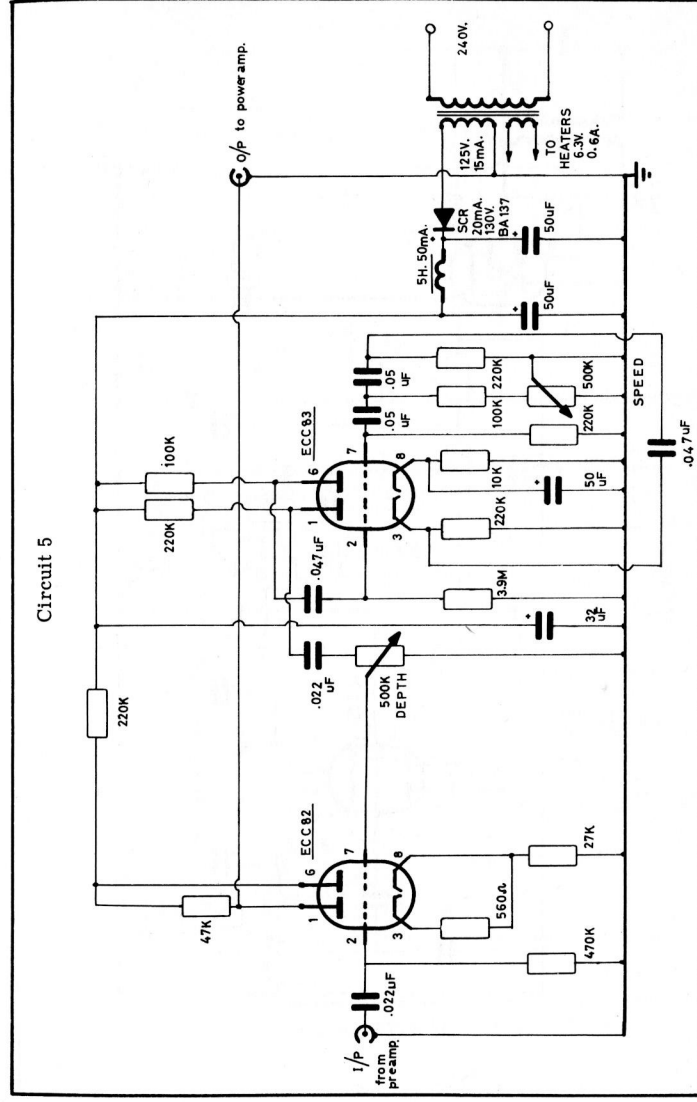COMBINED TREMOLO AND VIBRATO UNIT FOR ELECTRONIC GUITARS




HIGH POWER VIBRATO ADD-ON UNIT




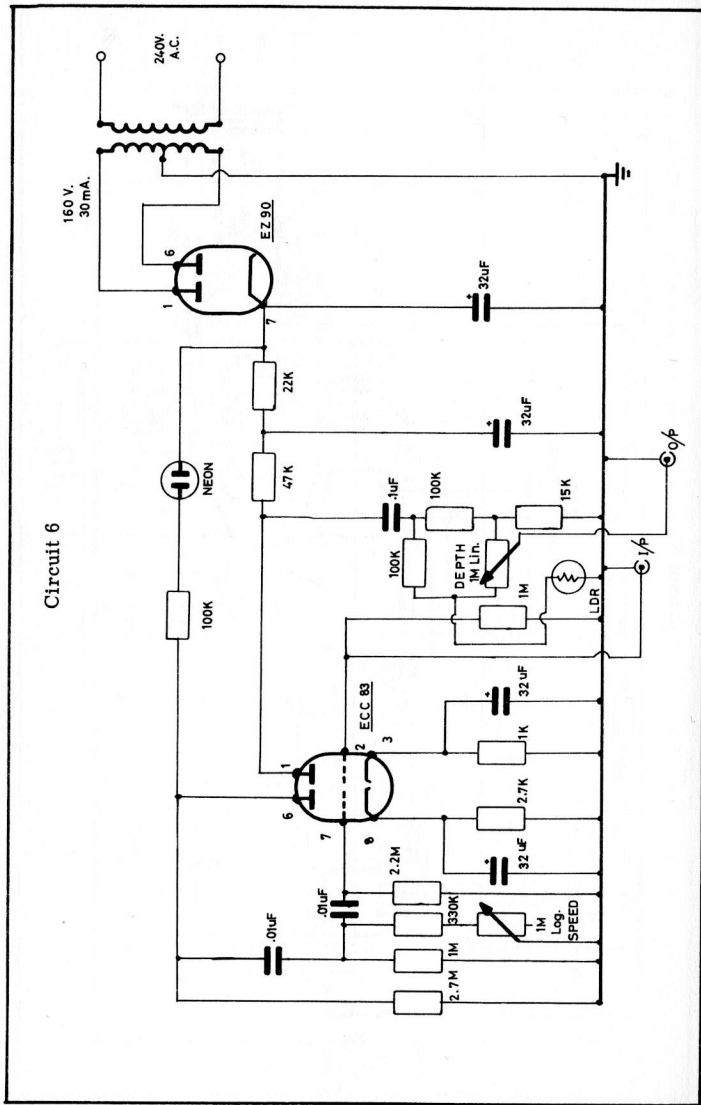

SELF POWERED VIBRATO ADD-ON UNIT

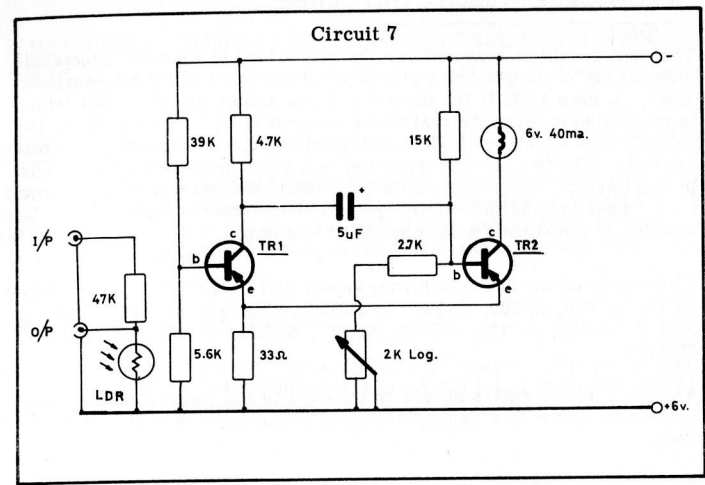

TRANSISTORISED VIBRATO UNIT

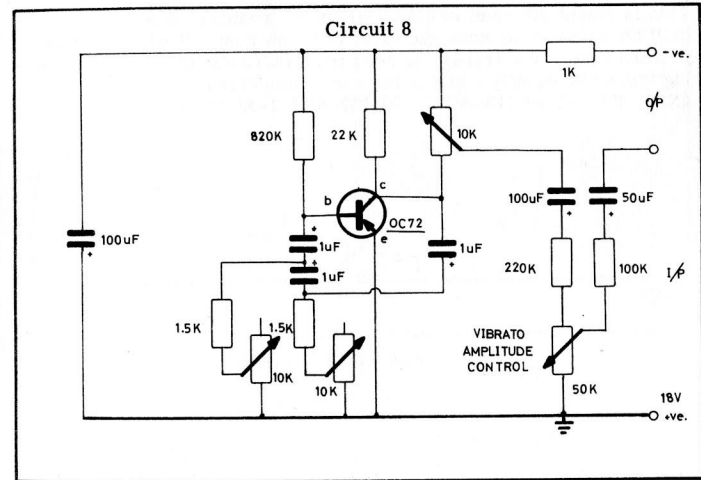

SIMPLE VIBRATO UNIT WITH SINGLE TRANSISTOR

TRANSISTORISED VIBRATO UNIT Circuit 7

This unit should be inserted into the output lead of whatever electronic musical instrument is being played and must precede the pre-amplifier stage. It uses an L.D.R. and a 6 volt low amperage bulb. The bulb is modulated to alter the resistance value of L.D.R. The L.D.R. is an ORP12 or RPY25 or LDR03 and should be fixed about one inch from the bulb. The two are then enclosed in a small plastic box which must be light proof. This can be done by painting the box with black enamel. Care in assembling this portion should be exercised as the perfect working of the vibrato unit depends on this box.

TR1 can be of any of the following types: AC122, AC125, AC151, AC163, OC71, ACY35, 2N280, 2N1305 or 2SB77. TR2 is either an AC105, AC117, AC121, AC124, AC128, AC153, ACY20, 2N1141, 2N1142 or 2N2391.

A control on/off switch should be inserted in the negative battery line and can be either foot or hand operated according to the wish of the user.

SIMPLE VIBRATO UNIT WITH SINGLE TRANSISTOR Circuit 8


This is one of the most simple designs for a vibrato unit that can be built by the amateur constructor at very low cost. It will give good performance. The transistor used is an OC72 but any of the following types are equally suitable for use in this circuit:- NKT212-2N281-2N1305-AC128-AC131-AC132-AC151-AC153-ACY36.

ELECTRONIC ACCESSORY UNITS FOR DISCOTHEQUE AND MUSICAL GROUP USEFUZZ BOXES

Fuzz boxes are a recent addition to the growing list of special effect gadgets used with electronic music. The unit operates by squaring off the sound wave form to give a very distorted output which is then clipped before being fed into the pre-amplifier and power amplifier.

SIMPLE FUZZ BOX Circuit 9

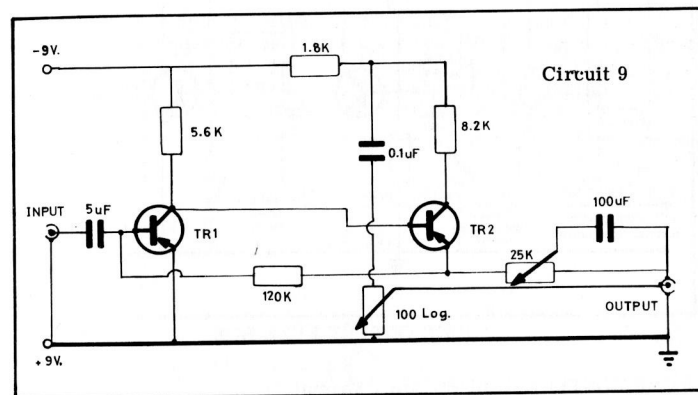
A very elementary fuzz box that will give good results. The two transistors may be any of the following types:- ACY17-ASY48-AC117-AC184-2N652A-NKT237



SIMPLE FUZZ BOX
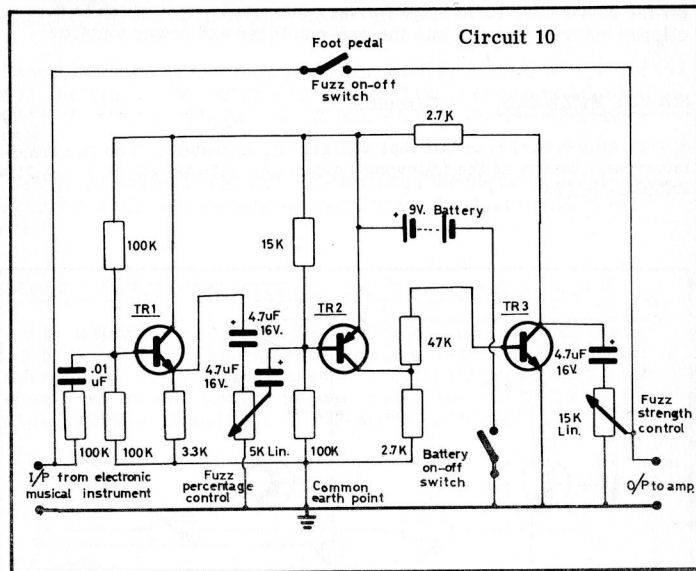
## HIGH OUTPUT FUZZ BOX Circuit 10


This design is the result of research work by R.C.A. and other well known manufacturers of audio equipment and is most effective in its performance. The transistors used are as follows:- (TR1) SK3020-BC107B (TR2) SK3005-OC45-AF127 (TR3) SK3020-BC107B. Alternatives are shown to the original in case any one has difficulty in obtaining the R.C.A. types SK3020 and SK3005 but it must be noted that the original circuit was designed around these 2 types of R.C.A. transistors.



HIGH OUTPUT FUZZ BOX
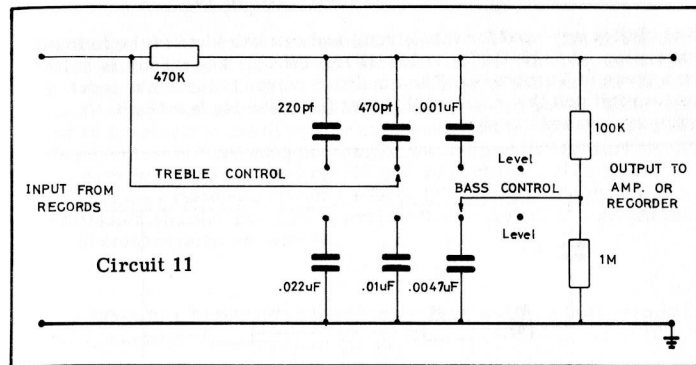
## TONE CONTROL CORRECTOR Circuit 11


This easily built gadget allows the operator to decide how much treble or bass shall be recorded on to tape or into the amplifier via inputs from either microphone, records or electronic music. This is particularly effective in dealing with old pressings which are worn or scratched and can very often extend the life of an old record which would normally be destroyed.



TONE CONTROL CORRECTOR
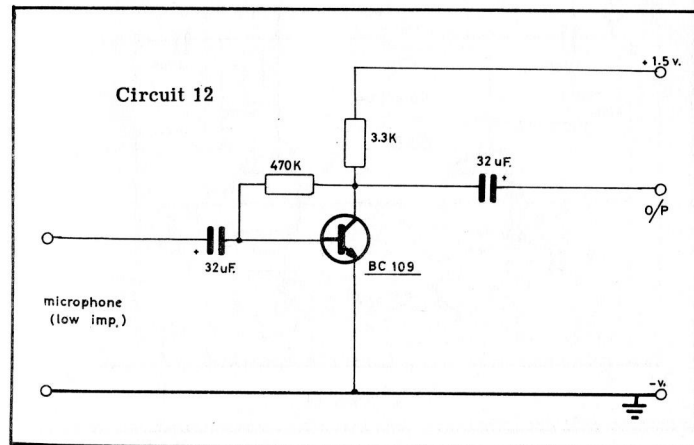
## GENERAL PURPOSE TRANSISTORISED MICROPHONE PRE-AMPLIFIER Circuit 12

This design is of Spanish origin and very easy and cheap to build. Notice that the transistor used is a n-p-n type but if one has a p-n-p, such as an OC71 or OC72, this may be used. Simply reverse the battery polarity and the 32 mf capacitors should be wired with polarity in reverse to that shown in the circuit.




GENERAL PURPOSE TRANSISTORISED MICROPHONE PRE-AMPLIFIER



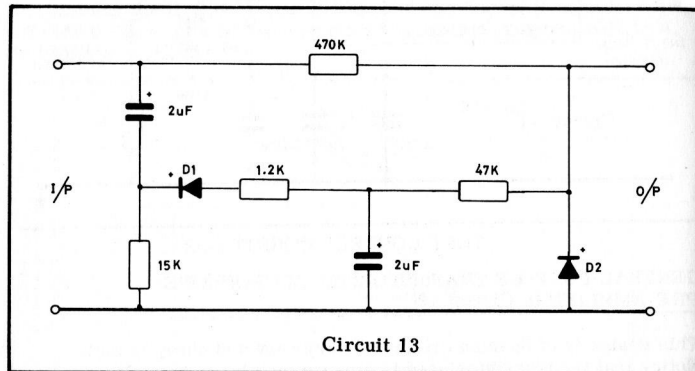
### SUB-MINIATURE AUDIO COMPRESSOR Circuit 13

Two diodes are used for this circuit and can be either of the following types:- AA119-OA71-AA113-IN541-IN542. The circuit is built on a piece of Veroboard. The amplifier output is fed to the input of this circuit and the output of this unit feeds the loudspeaker. Two units are needed for stereo.



### SUB-MINIATURE AUDIO COMPRESSOR

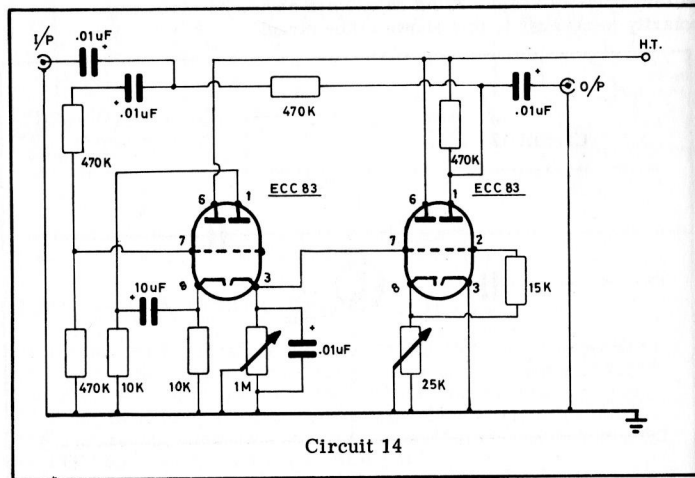


### ELECTRONIC COMPRESSOR LIMITER WITH VALVES

### VALVED ELECTRONIC COMPRESSOR/LIMITER Circuit 14

This design produces a slow expansion rate but a very fast compression. This is particularly important in recording work. The unit uses 2 twin-triode valves and can be built quite cheaply. It draws its H.T. (high tension) from any rectified supply at about 150 volts. This may be taken from either the amplifier or pre-amplifier. This unit should be placed in circuit between pre-amplifier and main amplifier. None of the component values used in this unit are critical. The 1 Meg control in the cathode circuit of the first ECC83 allows variation of compression speed. The 25K control in the second ECC83 alters the level of compression as desired.
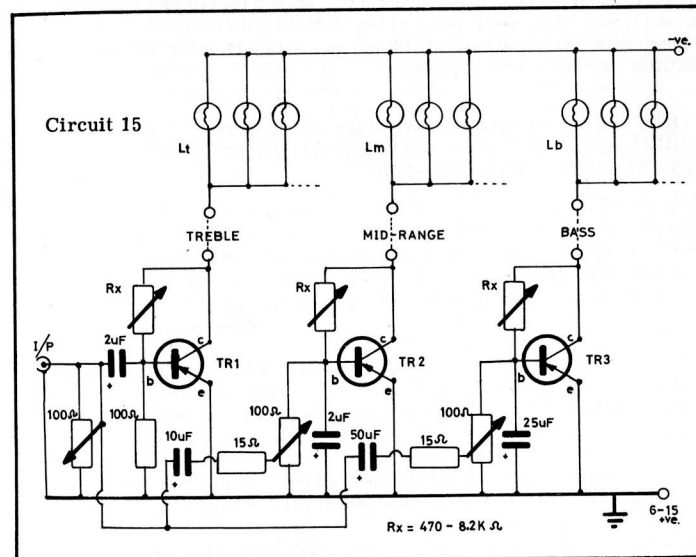
### PSYCHEDELIC COLOURED LIGHT UNIT FOR AUDIO AMPLIFIERS Circuit 15

Many discotheques and even private audio enthusiasts will like a simple circuit which can produce coloured lights which literally dance when music is being played through an amplifier. The circuit is transistorised, inexpensive and extremely easy to build and produces superb



### PSYCHEDELIC COLOURED LIGHT UNIT

## CHAPTER 3

### AMPLIFIERS OF 12 TO 14 WATTS

results with both small and large amplifiers. The unit is connected in parallel to any amplifier at the loudspeaker output point, and does not interfere with the amplifier's performance or the quality of reproduction from the loudspeakers. The circuit is not difficult to construct and the cost of the parts are extremely low.

In order to set up this unit it will be necessary to set a value for the three resistors marked Rx on the drawing and this will be somewhere between 500 - 10,000 ohms. It is recommended that each of these be a 10K ohms linear potentiometer and their values adjusted by connecting the unit to the amplifier which must be switched on but with volume control at minimum so that the different coloured lamps each show a low glowing light which can just be seen under ordinary room lighting conditions. Once this adjustment has been made it should not be altered when the amplifier has its volume turned up and music fed through it so that the lights commence to dance.

The light unit may be operated with a supply voltage from 6 - 15 volts thus enabling it to be used if necessary from car batteries when connected to mobile amplifiers. When operating on a 6 volt supply, the bulbs used for the lights should be 2 volts each at 50 to 70 ma. When used with a 12 volt supply 6 volt, 60 - 200 ma bulbs are suitable. The bulbs in each of the three sound ranges should be either coloured with a heat proof translucent paint of the desired colours or they may be placed under coloured bulb holders, which are manufactured by Bulgin, Belling Lee and other suppliers.

TR1, TR2 and TR3 may be any of the following types:- AD130-AD131-AD138 /50-AD140-AD149-2N1331-2N1333-2N1435-2N2836-2N2869-2N3611-OC16-OC26-2SB83.

**3-1. A 14W Ultra-Linear Amplifier.**—This class of amplifier is probably the most popular for use in domestic equipment. As it is frequently required to work from a diversity of signal sources—radio tuners, record players, tape recorders, microphones etc., the domestic amplifier is generally used in conjunction with auxiliary pre-amplifying and equalisation equipment. Consequently, a slight departure is made here by describing a complete amplifier with tone controls and, in addition, alternative input selection and equalisation units. Higher power amplifiers suitable for domestic use are described in Chapter 4 and separate pre-amplifier and tone control circuits are discussed in Chapter 9.

The main amplifier circuit is given in fig. 3-3 and the two types of input unit appear in figs. 3-4 and 3-5. This design is based on the very popular "G.E.C. 912-PLUS" amplifier. The full output of 12-14W (the precise value depending upon the quality of the output transformer) is obtained with less than 1% total harmonic distortion over the frequency range of 30c/s to 20kc/s. An input of 50mV will give 12W output.

Comprehensive tone controls are built into the main amplifier and both the alternative input selection units provide switching for radio input, four different record characteristics and microphone. The pre-amplifiers described in Chapter 9 are very suitable for combining with the G.E.C. 912-PLUS when the flexibility of a separate pre-amplifier and tone control unit is desired. Details are given at the end of this chapter.

One of the units contains passive networks (i.e. there is no amplification) for equalising the four record characteristics and is intended for use with crystal pickups and microphones. The alternative unit is a single-valve pre-amplifier for which details are given not only for equalising the four record characteristics from different types of pickup but also for matching radio and microphone outputs to the main amplifier.

The passive input unit (fig. 3-4) has a sensitivity of 150mV on the "record" positions of the selector switch. The "radio" and "microphone" inputs are switched straight through to the main amplifier and consequently the original sensitivity of 50mV is retained.

The pre-amplifier (fig. 3-5) can be made specifically to suit the requirements of the particular pick-up, radio and microphone used, but maximum sensitivities are: 10mV for the "record" positions of the selector switch, 1mV for "microphone," and, nominally, 50mV for "radio." The required input impedance and sensitivity at any particular position of the input selector switch will depend upon the pickup or microphone used. Table 3-II gives appropriate alter-

native values for the resistors which determine these characteristics.

The first stage consists of a Z729 low-noise pentode followed by the tone control networks, described later. Next, the first section of a B309 double triode\* is a typical voltage

\* A B719 may be used ;

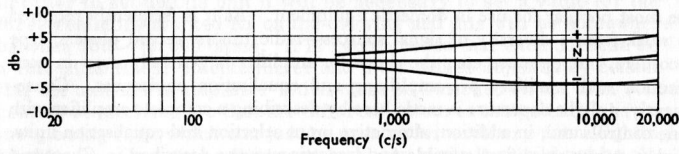


Fig. 3-1. 12W ultra-linear amplifier : effect of the "presence" control, with bass and treble controls at the level positions (mid-travel).

amplifier with negative feedback applied to the cathode circuit from the output transformer secondary. The feedback network contains an additional tone control ("presence") as described later. The second half of the B309 is a phase-splitter which feeds the N709 ultra-linear output stage, the characteristics of which are given in Table 3-1. The output transformer is tapped at 20% to 40% of the turns of each half-primary from the centre tap. The power supply is of conventional design with a U709 feeding a capacitance-input filter.

**Bass Loudness.**—This control is continuously variable, giving linear response at the centre, bass attenuation anticlockwise, and bass accentuation clockwise.

**Treble.**—This is a switched control providing a linear position, two degrees of attenuation and one degree of boost.

**Treble Slope.**—A continuously variable control which alters the slope of the high frequency cut selected by the treble switch.

**Presence.**—This switch, the effect of which is shown in fig. 3-1, is designed to vary the listener's apparent position when listening to music. It introduces a frequency-selective network into the negative feedback loop.

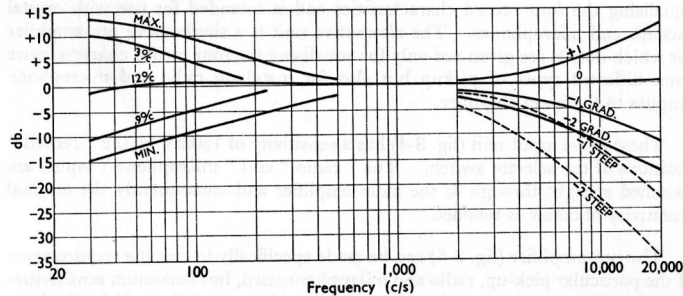


Fig. 3-2. 12W ultra-linear amplifier : the effect of the bass, treble and treble slope controls. The right-hand solid curves illustrate the four positions of the treble switch. The dotted curves show how the two treble cut curves are modified by fully rotating the treble slope control. The position of each dotted curve will alter as treble slope is decreased until, when it is at minimum, the treble response is that shown by the corresponding solid curve.

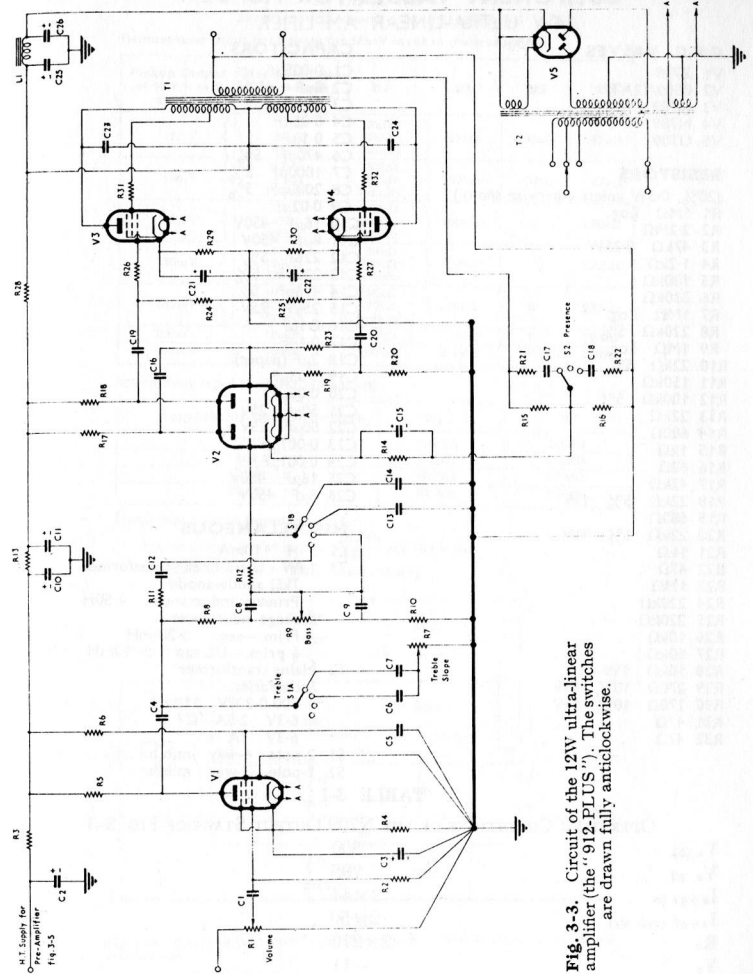


Fig. 3-3. Circuit of the 12W ultra-linear amplifier (the "912-PLUS"). The switches are drawn fully anticlockwise.



### COMPONENT VALUES FOR FIG. 3-3

#### 14W ULTRA-LINEAR AMPLIFIER

##### G.E.C. VALVES

V1 Z729  
V2 B309/12A7  
V3 N709  
V4 N709  
V5 U709

##### RESISTORS

(20% 0.5W unless otherwise shown)

R1 1M $\Omega$  Log.  
R2 2.2M $\Omega$   
R3 47k $\Omega$  0.25W  
R4 1.2k $\Omega$   
R5 100k $\Omega$   
R6 330k $\Omega$   
R7 1M $\Omega$  Log.  
R8 220k $\Omega$  5%  
R9 1M $\Omega$  Log.  
R10 22k $\Omega$  5%  
R11 150k $\Omega$   
R12 100k $\Omega$  5%  
R13 22k $\Omega$   
R14 680 $\Omega$   
R15 1k $\Omega$   
R16 68 $\Omega$   
R17 47k $\Omega$   
R18 22k $\Omega$  5% 1W  
R19 680 $\Omega$   
R20 22k $\Omega$  5% 1W  
R21 1k $\Omega$   
R22 47 $\Omega$   
R23 1M $\Omega$   
R24 220k $\Omega$   
R25 220k $\Omega$   
R26 10k $\Omega$   
R27 10k $\Omega$   
R28 10k $\Omega$  1W  
R29 270 $\Omega$  10% 1W  
R30 270 $\Omega$  10% 1W  
R31 47 $\Omega$   
R32 47 $\Omega$

##### CAPACITORS

C1 0.005 $\mu$ F  
C2 8 $\mu$ F 450V  
C3 25 $\mu$ F 25V  
C4 0.05 $\mu$ F  
C5 0.1 $\mu$ F  
C6 470pF 5%  
C7 1000pF 5%  
C8 2000pF 5%  
C9 0.02 $\mu$ F  
C10 16 $\mu$ F 450V  
C11 8 $\mu$ F 450V  
C12 22pF 5%  
C13 220pF 5%  
C14 470pF 5%  
C15 25 $\mu$ F 25V  
C16 0.1 $\mu$ F  
C17 0.1 $\mu$ F  
C18 2 $\mu$ F (paper)  
C19 0.05 $\mu$ F  
C20 0.05 $\mu$ F  
C21 50 $\mu$ F 25V  
C22 50 $\mu$ F 25V  
C23 0.001 $\mu$ F  
C24 0.001 $\mu$ F  
C25 16 $\mu$ F 450V  
C26 8 $\mu$ F 450V

##### MISCELLANEOUS

L1 10H 110mA  
T1 14W Ultra-linear transformer  
7k $\Omega$  anode-anode  
Primary inductance:  $\leq$  50H  
Leakage inductances:  
Prim.—sec.:  $\geq$  20 mH  
 $\frac{1}{2}$  prim.—UL tap:  $\geq$  10mH  
T2 Mains transformer  
Secondaries:  
300-0-300V 110mA  
6.3V 2.5A CT  
6.3V 1A  
S1 2-pole 4-way m.b.b.  
S2 1-pole 3-way m.b.b.

TABLE 3-I

#### OPERATING CONDITIONS OF THE N709 OUTPUT STAGE OF FIG. 3-3

$V_a$ (b)	300	V
$V_a$ , g2	295	V
$I_a + g2$ (o)	2 $\times$ 44	mA
$I_a + g2$ (max sig)	2 $\times$ 50	mA
$R_k$	2 $\times$ 270	$\Omega$
$V_g$	-11	V
$P_{out}$	12	W
$R_L$ (a-a)	7	k $\Omega$
$z_{out}$ (approx.)	2	k $\Omega$
D	<1	%
$V_{in}$ (rms) (to first stage)	50	mV

TABLE 3-II

#### ALTERNATIVE COMPONENT VALUES FOR FIG. 3-5

Gramophone Input (all figures for 50mV input to main amplifier)

Pickup Output (at 4cm/s as a guide)	Required Load Impedance	R2	R3	R5	R19
5mV	{ 10k $\Omega$ 22k $\Omega$ 47k $\Omega$	{ 15k $\Omega$ 47k $\Omega$ Infinity	47k $\Omega$	100k $\Omega$	47k $\Omega$
10mV	{ 22k $\Omega$ 47k $\Omega$ 100k $\Omega$	{ 33k $\Omega$ 100k $\Omega$ Infinity	100k $\Omega$	100k $\Omega$	47k $\Omega$
20mV	{ 22k $\Omega$ 47k $\Omega$ 100k $\Omega$	{ 33k $\Omega$ 100k $\Omega$ Infinity	100k $\Omega$	0	220k $\Omega$
50mV	{ 47k $\Omega$ 100k $\Omega$ 220k $\Omega$	{ 68k $\Omega$ 220k $\Omega$ Infinity	220k $\Omega$	0	220k $\Omega$
100mV	{ 100k $\Omega$ 220k $\Omega$ 470k $\Omega$	{ 150k $\Omega$ 470k $\Omega$ Infinity	470k $\Omega$	0	220k $\Omega$
200mV	100k $\Omega$	100k $\Omega$	1M $\Omega$	0	220k $\Omega$
500mV	100k $\Omega$	100k $\Omega$	2.2M $\Omega$	0	220k $\Omega$

Microphone Input (1mV for full output)

Approximate Input Impedance	R1	R7
2.2M $\Omega$	Infinity	2.2M $\Omega$
1M $\Omega$	2.2M $\Omega$	2.2M $\Omega$
470k $\Omega$	680k $\Omega$	2.2M $\Omega$
220k $\Omega$	220k $\Omega$	2.2M $\Omega$

Radio Input (Input impedance = R4)

Required input for full output =  $\frac{50 \times R4}{220}$  mV (R4 in k $\Omega$ ).

Standard value for R4 = 220k $\Omega$  (input = 50mV).

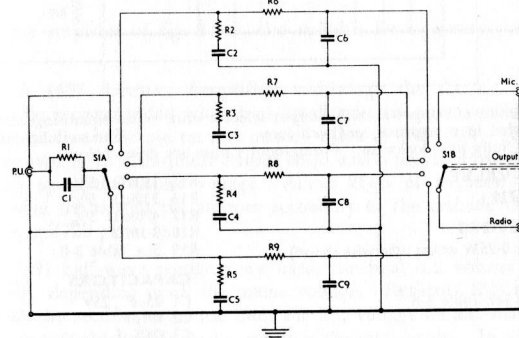


Fig. 3-4. Circuit of the passive input selector unit. Both switches are shown fully anticlockwise.

### RESISTORS

(10% 0.25W)	
R1	470k $\Omega$
R2	
R3	
R4	
R5	150k $\Omega$
R6	
R7	
R8	470k $\Omega$
R9	

### CAPACITORS

C1	470pF	10%
C2	0.002 $\mu$ F	25%
C3	0.005 $\mu$ F	25%
C4	0.005 $\mu$ F	25%
C5	0.01 $\mu$ F	25%
C6	220pF	10%
C7	100pF	10%
C8	100pF	10%
C9	33pF	10%

### SWITCH

S1 2-pole 6-way m.b.b.

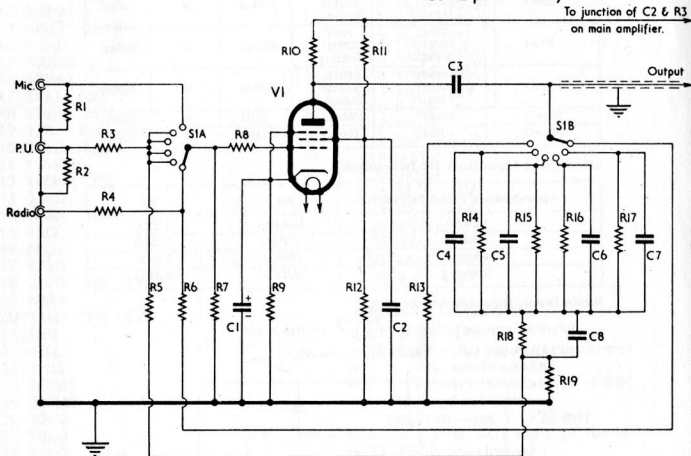


Fig. 3-5. Circuit of the pre-amplifier input selector unit. The equalising components are incorporated in a negative feedback loop. The switches are shown fully anticlockwise. Component values are given below.

### G.E.C. VALVE

V1 Z729

### RESISTORS

(20% 0.25W unless otherwise shown)

*R1	See Table 3-II	
R2		
R3		
R4		
R5		
R6	220k $\Omega$	
R7	2.2M $\Omega$	
R8	2.2k $\Omega$	
*R9	3.3k $\Omega$	5%
*R10	220k $\Omega$	5%
*R11	470k $\Omega$	5%
*R12	330k $\Omega$	5%
R13	220k $\Omega$	
R14	220k $\Omega$	5%

\*High Stability

R15	330k $\Omega$	5%
R16	330k $\Omega$	5%
R17	470k $\Omega$	5%
R18	3.3M $\Omega$	
R19	See Table 3-II	

### CAPACITORS

C1	25 $\mu$ F	25V
C2	0.1 $\mu$ F	
C3	0.05 $\mu$ F	
C4	330pF	10%
C5	150pF	10%
C6	68pF	10%
C7	33pF	10%
C8	1000pF	10%

### SWITCH

S1 2-pole 6-way m.b.b.

*Using a Separate Pre-Amplifier.*—The 912-PLUS may be converted for use with the pre-amplifier described in Section 9-3 (fig. 9-3) in the following way:

Referring to fig. 3-3, the connection to the grid of the left-hand section of V2 is removed so that the whole of the circuit to the left-hand side of V2 is discarded. The "presence" components are removed from the feedback loop, leaving only the series feed resistor R15 and the lower part of the V2 cathode resistance R16. This results in a normal application of negative feedback from the output transformer secondary to the cathode circuit of the first valve of what is now the main amplifier.

The h.t. line is terminated at C10 and C11, R13 is removed and C10, C11 are strapped to give a total capacitance of 24 $\mu$ F. The h.t. series resistor R28 is reduced to 3.3k $\Omega$  (1W) and the h.t. connection to the pre-amplifier is taken from the junction of C11 and R28. No additional decoupling is required in the pre-amplifier h.t. line. The heater supply for the pre-amplifier should consist of a separate pair of twisted wires running direct to the mains transformer.

The pre-amplifier connections should be made through an octal socket mounted on the main amplifier chassis near V2 and, to prevent damage to V2 by disconnecting the pre-amplifier when the power is switched on, a grid leak of 1M $\Omega$  should be connected between the input grid of V2 and earth.

This combined equipment will have somewhat less overall distortion than the normal 912-PLUS, the second harmonic distortion being, in fact, as low as 0.3%.

The pre-amplifier of fig. 9-2 is also suitable for operation with the 912-PLUS

**3-2. A 14W d.c./a.c. Amplifier.**—Although the d.c./a.c. amplifier is hardly to be recommended when high quality is the main consideration, fig. 3-6 shows a circuit for use on d.c. or a.c. mains of 190-250V. Two KT33C valves are used in an ultra-linear output stage which provides from 7W to 14W depending upon the mains voltage. About 20db of negative feedback is applied from the output transformer secondary to the cathode circuit of the first valve, a Z729 pentode.

Two U31 half-wave rectifiers are used, the final h.t. voltage being from 180 to 240, depending upon the mains voltage. Resistors R23 and R25, in series with the rectifier cathodes, limit the h.t. voltage on a.c. mains to about the same as that obtained from d.c. mains of the same value. In addition these resistors limit the rectifier peak current and equalise the flow through the two valves. The power supply circuit in fig. 3-6 on 190-250V a.c. or d.c. mains but, for continuous operation on 240-260V a.c., R23 and R25 may be increased to 180 $\Omega$  each in order to limit the anode and screen dissipation of the output valves.

For d.c. operation only, the rectifiers, resistors R23, R25 and the reservoir capacitor C14 may be omitted. Without rectifiers there is no protection for the electrolytic capacitors against reversed polarity of the mains and paper

types should be substituted. A lower capacitance of  $4\mu\text{F}$  will be adequate for C8 and C11 on most d.c. mains.

The current in the heater chain is controlled by a 303 barretter for mains voltages of 190-250 but for continuous operation above 240V a Type 304 should be substituted.

On low mains voltages, the resistances of L1 and T1 are important and should be as low as possible.

Table 3-III gives the operating data for the output stage of this amplifier.

### COMPONENT VALUES FOR FIG. 3-6

#### KT33C 14W DC/AC ULTRA-LINEAR AMPLIFIER

##### G.E.C. VALVES

V1 Z729  
V2 L63/6J5  
V3 KT33C  
V4 KT33C  
V5 U31  
V6 U31  
V7 Barretter 303

R21 470—1500 $\Omega$   
R22 470—1500 $\Omega$   
R23 100 $\Omega$  5W  
R24 62 $\Omega$  5W  
R25 100 $\Omega$  5W

##### CAPACITORS

C1 0.02 $\mu\text{F}$   
C2 25 $\mu\text{F}$  25V  
C3 0.1 $\mu\text{F}$   
C4 4 $\mu\text{F}$  350V  
C5 0.05 $\mu\text{F}$   
C6 0.1 $\mu\text{F}$   
C7 0.1 $\mu\text{F}$   
C8 32 $\mu\text{F}$  350V  
C9 25 $\mu\text{F}$  25V  
C10 25 $\mu\text{F}$  25V  
C11 32 $\mu\text{F}$  350V  
C12 1000pF  
C13 1000pF  
C14 32 $\mu\text{F}$  450V

##### RESISTORS

(20% 0.5W unless otherwise shown)

R1 500k $\Omega$   
R2 250 $\sqrt{\text{speech coil impedance}}$   
R3 2.2k $\Omega$   
R4 47 $\Omega$   
R5 220k $\Omega$   
R6 1M $\Omega$   
R7 15k $\Omega$   
R8 2.2M $\Omega$   
R9 15k $\Omega$  1W } matched to 5%  
R10 15k $\Omega$  1W }  
R11 1.5k $\Omega$   
R12 220k $\Omega$   
R13 220k $\Omega$   
R14 15k $\Omega$   
R15 15k $\Omega$   
R16 220 $\Omega$  5% 1W  
R17 220 $\Omega$  5% 1W  
R18 15k $\Omega$  1W  
R19 100 $\Omega$   
R20 100 $\Omega$

##### MISCELLANEOUS

L1 5—10H 200mA  
T1 14W Ultra-linear transformer  
3.2k $\Omega$  anode-anode  
Primary inductance:  $\leq 25\text{H}$   
Leakage inductances:  
Prim.—sec.:  $\geq 5\text{mH}$   
 $\frac{1}{2}$  prim.—UL tap:  $\geq 5\text{mH}$

TABLE 3-III

#### OPERATING CONDITIONS OF THE KT33C OUTPUT STAGE OF FIG. 3-6

$V_a$ (b) (approx)	235	V
$V_{a, g2}$ (approx)	220	V
$I_{a+g2}$ (o)	$2 \times 70$	mA
$I_{a+g2}$ (max sig)	$2 \times 75$	mA
$P_{a+g2}$ (o)	$2 \times 15$	W
$P_{a+g2}$ (max sig) (approx)	$2 \times 10$	W
$R_k$	$2 \times 220$	$\Omega$
$V_g$	-15	V
$P_{out}$	14	W
$R_L$ (a-a)	3.2	k $\Omega$
$Z_{out}$ (approx)	3	k $\Omega$
D	$< 0.5$	%
$V_{in}$ (rms) (to first stage)	0.5	V

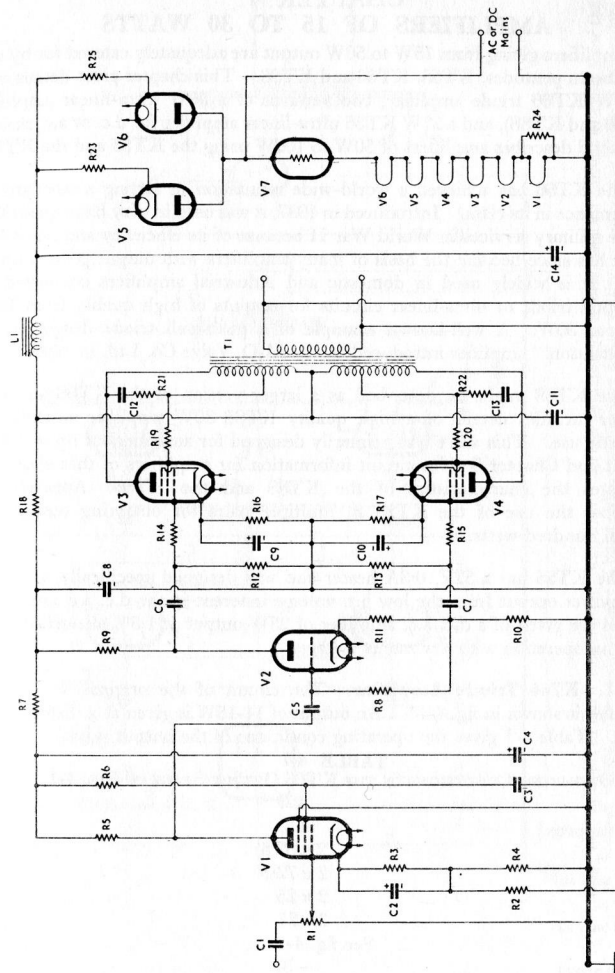


Fig. 3-6. Circuit of the d.c./a.c. 14W amplifier.



## COMPONENT VALUES FOR FIG. 4-1

### "WILLIAMSON" AMPLIFIER

#### G.E.C. VALVES

- V1 B6S/6SN7 or 2×L63/6J5  
 V2 B6S/6SN7 or 2×L63/6J5  
 V3 KT66  
 V4 KT66  
 V5 U52/5U4 or U54

#### RESISTORS

(20% 0.25W unless otherwise shown)

- R1 1MΩ  
 R2 4.7kΩ  
 R3 470Ω 10%  
 R4 33kΩ 1W  
 R5 47kΩ 1W  
 R6 1200√ speech coil impedance  
 R7 22kΩ 1W  
 R8 22kΩ 1W } Matched to 5%  
 R9 22kΩ 1W }  
 R10 470kΩ  
 R11 470kΩ  
 R12 390Ω 10%  
 R13 47kΩ 2W } Matched to 5%  
 R14 47kΩ 2W }  
 R15 100kΩ 10%  
 R16 100Ω 2W w.w.  
 R17 100kΩ 10%  
 R18 100Ω 1W  
 R19 100Ω 1W  
 R20 1kΩ  
 R21 1kΩ

- R22 100Ω 2W w.w.  
 R23 150Ω 5% 3W w.w.  
 R24 100Ω 0.5W  
 R25 100Ω 0.5W

#### CAPACITORS

- C1 8μF 500V  
 C2 200pF  
 C3 0.05μF  
 C4 0.05μF  
 C5 8μF 500V  
 C6 8μF 500V  
 C7 0.25μF  
 C8 0.25μF  
 C9 8μF 500V  
 C10 8μF 600V

#### MISCELLANEOUS

- L1 30H 20mA  
 L2 10H 150mA  
 T1 14W Output transformer  
 10kΩ anode-anode  
 Primary inductance : ∇ A 100H  
 Leakage inductance : ∇ A 30mH  
 T2 Mains transformer  
 Secondaries :  
 425-0-425V 150mA  
 6.3V 4A CT  
 5V 3A

**4-2. Two 30W Ultra-Linear Amplifiers.**—The basic circuit of fig. 4-4 may be used with either KT66 or KT88 valves and the components list on page 43 gives suitable values for each type of valve.

With negative feedback, the KT66 amplifier will give 32W output with about 0.5% distortion at an anode potential of 400V and the KT88 will give 32W with 0.25% distortion at an anode potential of 335V.\* The input signal to the first stage of the amplifier for full output in the KT66 version is 600mV whereas the KT88 version requires 500mV. With no negative feedback these figures become 120mV and 100mV respectively. It will be noted that the KT88 version has less distortion, higher sensitivity and requires a lower h.t. voltage than the KT66 for the same maximum output. If feedback is omitted the KT88 amplifier has only 1% distortion at 32W output as against the 2% of the KT66 version. As the KT88 valves are conservatively run in this circuit they will have a long life.

The output stage is preceded by a conventional double triode voltage amplifier which is fed by a triode phase-splitter comprising one half of a further double triode. The other half of this valve is the input stage voltage amplifier, which is

\*The KT88 output stage is, in fact, operated here almost in Class A, hence the reduced distortion compared with the KT66 version.

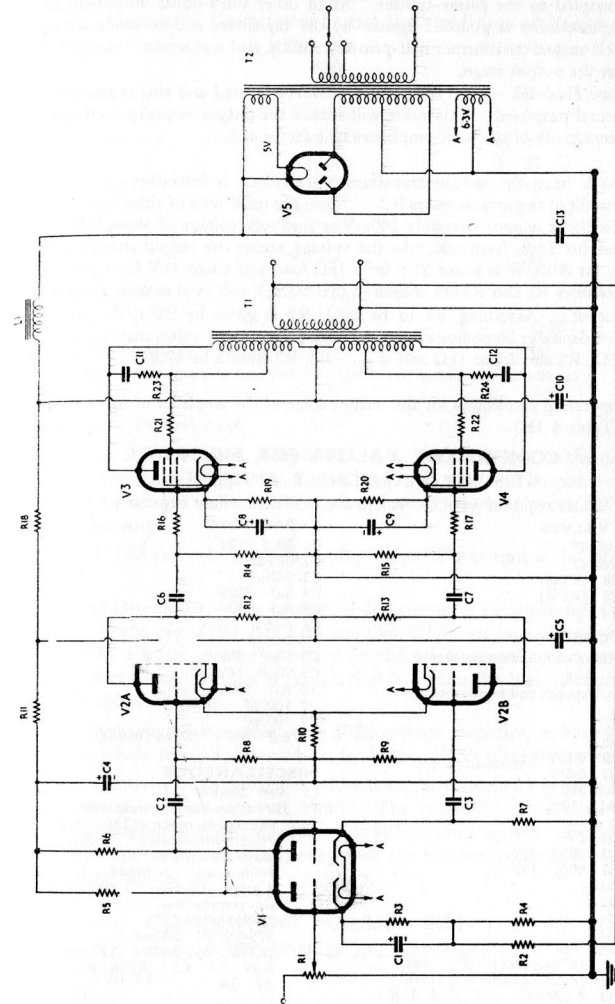


Fig. 4-4. Circuit of a 30W ultra-linear amplifier using KT66 or KT88 valves in the output stage. The component values and circuit conditions differ: see the components list opposite.



directly coupled to the phase-splitter. As in other ultra-linear amplifiers in this book, instability is guarded against by the capacitors and resistors across part of each output transformer half-primary and by grid and screen "stopper" resistors in the output stage.

**Negative Feedback.**—14db of negative feedback is used and this is adequate for all normal purposes. This value will reduce the output impedance, distortion and sensitivity of the basic amplifiers by a factor of 5.

Feedback from the output transformer secondary is introduced into the cathode circuit of the first stage via R2. Since the sensitivity of either amplifier without feedback is approximately 100mV, a feedback voltage of about 500mV is required for 14db feedback. As the voltage across the output transformer secondary for 30-32W is about 21.5 for a 15Ω load and about 11V for a load of 4Ω, the resistors R2 and R4 are chosen so that 500mV will exist at their junction at full output. Assuming R4 to be 22Ω, R2 is given by  $225\sqrt{Z_o}$  (where  $Z_o$  = the loudspeaker impedance) and the nearest standard value may be used. If  $Z_o = 15\Omega$ , R2 should be 1kΩ and if  $Z_o = 4\Omega$ , R2 should be 470Ω.

The operating conditions for the output stage of the amplifier of fig. 4-4 are given in Table 4-11.

### COMPONENT VALUES FOR FIG. 4-4 KT88 30W ULTRA-LINEAR AMPLIFIER

Values required for KT66 valves are indicated where necessary

#### G.E.C. VALVES

V1 B65/6SN7  
V2 B65/6SN7  
V3 KT88 (KT66)  
V4 KT88 (KT66)  
V5 U54

#### RESISTORS

(20% 0.25W unless otherwise shown)

R1 1MΩ Log.  
\*R2  $225\sqrt{\text{speech coil impedance}}$   
R3 1kΩ  
R4 47Ω  
R5 100kΩ  
R6 15kΩ 0.5W } Matched to 5%  
R7 15kΩ 0.5W }  
R8 470kΩ 10%  
R9 470kΩ 10%  
R10 1kΩ  
R11 22kΩ 1W  
R12 33kΩ 10% 1W  
R13 33kΩ 10% 1W  
R14 220kΩ  
R15 220kΩ  
R16 10kΩ  
R17 10kΩ  
R18 4.7kΩ 1W  
R19 400Ω (KT66 : 560Ω) 5% 5W  
R20 400Ω (KT66 : 560Ω) 5% 5W  
R21 270Ω 0.5W  
R22 270Ω 0.5W  
R23 470—1500Ω 0.5W  
R24 470—1500Ω 0.5W

\*For 14db feedback.

#### CAPACITORS

C1 50μF 12V  
C2 0.05μF  
C3 0.05μF  
C4 8μF 350V  
C5 8μF 450V  
C6 0.05μF  
C7 0.05μF  
C8 50μF 50V  
C9 50μF 50V  
C10 8μF 500V  
C11 1000pF  
C12 1000pF  
C13 8μF 500V (KT66 : 600Vt)

#### MISCELLANEOUS

L1 10H 200mA  
T1 35W Ultra-linear transformer  
6kΩ anode-anode (KT66 : 7kΩ)  
‡Primary inductance : < 50H  
Leakage inductances :  
‡Prim.—sec. : > 10mH  
‡‡prim.—UL tap : > 10mH  
T2 Mains transformer  
Secondaries :  
375-0-375V 200mA  
(KT66 : 450-0-450V 150mA)  
6.3V 5A CT (KT66 : 4A)  
5V 3A

‡Or two 16μF 350V in series.

‡With these values, R23, R24 and C11, C12 may be omitted.

TABLE 4-11  
OPERATING CONDITIONS OF THE OUTPUT STAGE OF FIG. 4-4

	KT66 Valves	KT88 Valves	
V <sub>a</sub> (b)	450	375	V
V <sub>a, g2</sub>	400	335	V
I <sub>a+g2</sub> (o)	2×62.5	2×80	mA
I <sub>a+g2</sub> (max sig)	2×72.5	2×85	mA
P <sub>a+g2</sub> (o)	2×25	2×27	W
P <sub>a+g2</sub> (max sig)	2×15	2×12	W
R <sub>k</sub>	2×560	2×400	Ω
V <sub>g</sub> (approx)	-36	-32	V
P <sub>out</sub>	32	30	W
R <sub>L</sub> (a-a)	7	5	kΩ
Z <sub>out</sub>	1.8	1	kΩ
D	0.5	0.25	%
V <sub>in</sub> (rms) (approx) (to first stage)	600	500	mV
If negative feedback is omitted, the last three values are as follows :			
z <sub>out</sub>	9	4.5	kΩ
D	2	1	%
V <sub>in</sub> (rms) (approx) (to first stage)	120	100	mV

**4-3. A 25W d.c./a.c. Amplifier.**—The main problem in the design of an amplifier for d.c./a.c. operation lies in providing adequate output power with a limited h.t. voltage, and the KT55 beam pentode has been specifically designed for this purpose.

Two KT55 valves in push-pull will provide 25W output with a mains supply of 225V.

**Circuit Description.**—The recommended circuit is shown in fig. 4-5 and it is designed round one Z729, one L63 and two KT55 valves, the h.t. supply being provided by a metal rectifier when the amplifier is operated on a.c. mains. The use of a thermionic rectifier is impracticable due to the high current required, which is about 275mA.

The input signal is applied to a Z729 voltage amplifier, followed by a conventional triode phase splitter which feeds the KT55 ultra-linear output stage.

The sensitivity of the amplifier without negative feedback is high, full output being obtained for an input of 55mV. The sensitivity is reduced to 300mV by the application of negative feedback as indicated in fig. 4-5. Before feedback is applied, the hum and noise level with the volume control at maximum is 55db below full output.

### COMPONENT VALUES FOR FIG. 4-5 KT55 25W DC/AC AMPLIFIER

#### G.E.C. VALVES

V1 Z729  
V2 L63/6J5  
V3 KT55  
V4 KT55  
V5 Barretter 303

R22 Thermistor CZ1 or TH1  
R23 63Ω 5% 5W  
R24 470-1500Ω 0.5W  
R25 470-1500Ω 0.5W

### RESISTORS

(20%, 0.25W unless otherwise shown)

R1 1M $\Omega$  Log.

\*R2 300  $\sqrt{\text{speech coil impedance}}$

R3 2.2k $\Omega$

R4 22 $\Omega$

R5 220k $\Omega$  10% 0.5W

R6 1M $\Omega$  10%

R7 10k $\Omega$

R8 1M $\Omega$

R9 22k $\Omega$  0.5W } matched to 5%

R10 22k $\Omega$  0.5W }

R11 1.5k $\Omega$

R12 220k $\Omega$

R13 220k $\Omega$

R14 10k $\Omega$

R15 10k $\Omega$

R16 185 $\Omega$  5% 5W w.w.

R17 185 $\Omega$  5% 5W w.w.

R18 10k $\Omega$  10% 1W

R19 47 $\Omega$

R20 47 $\Omega$

R21 15+15 $\Omega$  10% 10W w.w.

\*For 14 db feedback

Separate bias resistors are essential in the output stage in view of the high mutual conductance. The 50 $\mu$ F cathode bypass capacitors give a loss of 6db at 50 c/s. They may be increased to 250 $\mu$ F when this loss is objectionable.

The output transformer is tapped at 40% of the turns on each half-primary from the centre tap. The small capacitors, C12, C13 and resistors R24, R25 are required with some output transformers to prevent the possibility of spurious oscillation.

Negative feedback is applied over three stages, about 14db giving a satisfactory reduction in distortion and output impedance without introducing the danger of instability. It is probable that more could be applied with high-quality output transformers but with this value of feedback an output of 25W at 0.25% distortion is obtained. R7 and C4, in the grid circuit of the phase splitter, assist in ensuring stability by reducing the loop gain at ultrasonic frequencies—they result in a loss of 6db at 20kc/s. (See Appendix B, page 119).

A low impedance power supply is obtained by the use of components primarily designed for television receivers. L1, which should have an inductance of about 2H and a d.c. resistance of about 75 $\Omega$ , is used with two large-value electrolytic capacitors C11 and C14. On d.c. the mains adjusting resistor is not in circuit and the metal rectifier protects the capacitors against reversed polarity. The heater current of 0.3A is controlled by a barretter and thermistor.

The circuit of fig. 4-5 may be changed to pentode operation by simply connecting R19 and R20 to the output transformer centre tap. This will, of course, result in somewhat higher distortion. Compared with pentode operation the ultra-linear circuit reduces the output impedance from 9k $\Omega$  to 2.35k $\Omega$ , giving unity ratio with the anode-to-anode load. The distortion is 1.5% compared with the 2% of pentode operation. The advantages of ultra-linear operation are gained at the expense of a slight fall in the overall sensitivity of the amplifier, that is, it will require a slightly larger input signal to give the same output.

### CAPACITORS

C1 0.01 $\mu$ F

C2 50 $\mu$ F 12V

C3 0.1 $\mu$ F

C4 50 pF

C5 0.01 $\mu$ F

C6 0.1 $\mu$ F

C7 0.1 $\mu$ F

C8 16 $\mu$ F 350V

C9 50 $\mu$ F 25V

C10 50 $\mu$ F 25V

C11 200 $\mu$ F 275V

C12 1000pF

C13 1000pF

C14 100 $\mu$ F 275V

### MISCELLANEOUS

L1 1.5-2H 300mA 75 $\Omega$

T1 25W Ultra-linear transformer

2k $\Omega$  anode-anode

Primary Inductance:  $\approx$  10H

Leakage inductances:

Prim.—sec.:  $\approx$  20mH

prim.—UL tap:  $\approx$  10mH

MR1 250V 275mA (G.E.C. 13H16XG)

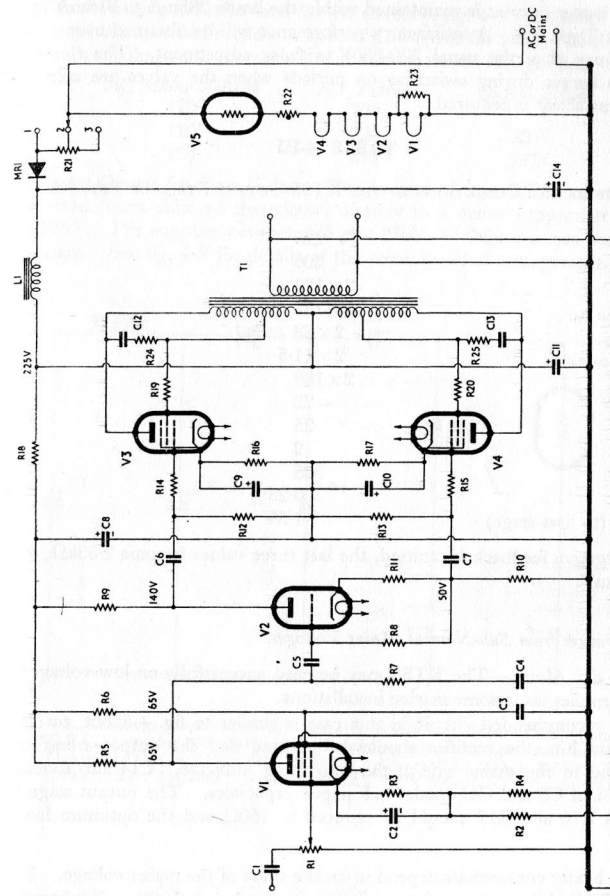


Fig. 4-5. Circuit of the 25W d.c./a.c. amplifier. R7 and C4 increase the margin of stability at high frequencies

The heater current is maintained within the limits 285mA to 315mA by the barretter Type 303. A satisfactory performance will be obtained over a rather wider range than the usual 200-250V without adjustment. The thermistor prevents surges during switching-on periods when the valves are cold. No thermistor shunt is required.

**TABLE 4-III**

OPERATING CONDITIONS OF THE KT55 OUTPUT STAGE OF FIG. 4-5

$V_a$ (b)	225	V
$V_a$ , g2	200	V
$I_{a+g2}$ (o)	$2 \times 120$	mA
$I_{a+g2}$ (max sig)	$2 \times 127$	mA
$P_{a+g2}$ (o)	$2 \times 23$	W
$P_{a+g2}$ (max sig)	$2 \times 11.5$	W
$R_k$	$2 \times 185$	$\Omega$
$V_g$	-22	V
$P_{out}$	25	W
$R_L$ (a-a)	2	k $\Omega$
$Z_{out}$	325	$\Omega$
D	0.25%	%
$V_{in}$ (rms) (to first stage)	1.5V	mV

If negative feedback is omitted, the last three values become 2.35k $\Omega$ , 1.5% and 300mV.

#### Operation from Sub-Normal Mains Voltages.

**Low d.c. Mains.**—The KT55 may be used successfully on low-voltage d.c. mains supplies, as in some marine installations.

The recommended circuit in this case is similar to fig. 4-5 but, to obtain maximum h.t., the rectifier should be omitted and the output transformer connected to the mains side of the smoothing inductor. C14 also should be omitted and C8 and C11 made 4 $\mu$ F paper capacitors. The output stage bias resistors R16 and R17 should be reduced to 150 $\Omega$  and the optimum load to 1.5k $\Omega$ .

The heater connections depend upon the value of the mains voltage. From 150 to 200V the existing series arrangement may be used with a 305 barretter, which is replaced by a suitable resistor for 125-150V. Below 125V two chains will be required, the KT55 valves being connected in series in one chain with a small resistor, if necessary, and a 303, 304 or 305 barretter in series with the remaining valves in the second chain. A suitable tapped resistor may be used, if preferred, instead of the barretter.


**Low a.c. Mains.**—For low a.c. mains voltages an auto-transformer may be used for the h.t. supply, with the heaters connected as for d.c. mains. An alternative method of obtaining the h.t. supply from low a.c. mains is shown in fig. 4-8. A voltage doubler circuit is used to give an h.t. of 220V from 110V a.c.

The smoothing inductor used for the circuit of fig. 4-8 has a lower resistance (20 $\Omega$ ) and the specified rectifier is specially designed for voltage doubling.


The h.t. voltage and power output at various mains voltages is as follows :

AC Mains Voltage	HT Voltage	Output Power
110	200	19W
110	220	23W
120	235	27W

**Heater Circuit for Four Valves.**—The heaters of four KT55 valves may be connected (via a shunted thermistor) directly to a mains supply between 200 and 215V. For supplies between 215 and 250V, additional series resistance is necessary. See fig. 4-9 for details of the recommended arrangement.

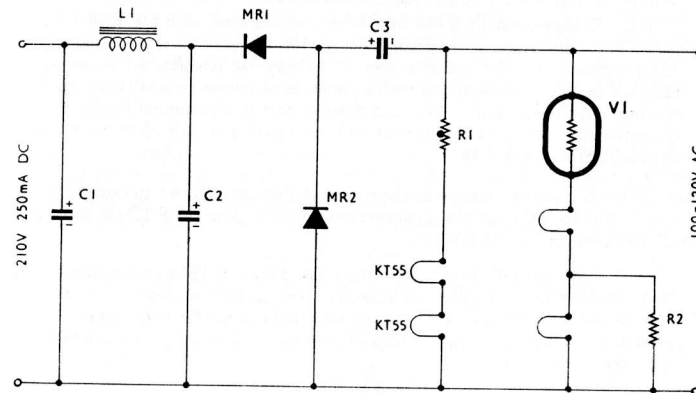

**Fig. 4-8.** Voltage doubler circuit for the KT55 amplifier. Component values : V1 : G.E.C. Barretter 303, 304 or 305 (depending upon voltage across heater chain) ; R1 : Thermistor CZ1 or TH1 ; R2 : 60 $\Omega$  5W ; C1 and C3 : 200 $\mu$ F 275V ; C2 : 100 $\mu$ F 275V ; L1 : 1H 20 $\Omega$  ; MR1 and MR2 : 250V 300mA (G.E.C. 13D8XG).

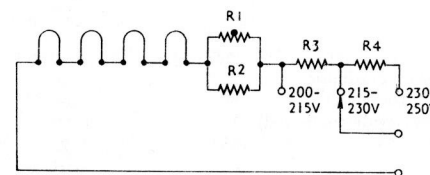

**Fig. 4-9.** Heater circuit for four KT55 valves. Component values : R1 : Thermistor CZ1 or TH1 ; R2 : 750 $\Omega$  10% 2W ; R3 and R4 : 50 $\Omega$  5% 10W.

## CHAPTER 5

### AMPLIFIERS OF 50 TO 100 WATTS

Although the amplifiers described earlier in this book, giving outputs up to about 50W, are adequate for domestic purposes and small public address equipment, the demand often arises for a 50W amplifier with a conservative rating and with the possibility of increasing its output to 100W by modifying the circuit and operating conditions. For such amplifiers the KT88 beam pentode is particularly suitable.

This chapter discusses the use of the KT88 in a design for a 50W ultra-linear amplifier with cathode bias and in a 100W fixed bias ultra-linear amplifier.

Details are also given of a relatively simple and inexpensive a.c. amplifier, with KT55 valves in the output stage, which gives 50W output at 5% distortion.

**5-1. Comparison of KT66 and KT88.**—Compared with the KT66, the KT88 has an increased anode dissipation of 35W, a higher mutual conductance and a cathode of larger emissive area. The physical characteristics are also different in that it is mounted on the more modern wafer octal base which eliminates the glass pinch. The higher anode potential permitted by this type of construction results in a power output from a push-pull pair up to twice that obtainable from the KT66.

Table 5-I overleaf compares the principal characteristics of the two valves and, as they have the same base connections, initial trials of the KT88 in existing KT66 equipment are facilitated.

It is usually possible to substitute the KT88 for the KT66 in most push-pull triode or ultra-linear amplifiers without circuit modification, since the cathode bias resistor is required to be about the same (500-600Ω) for both valves. No great increase in output will be obtained, however, unless the circuit conditions are suitably modified.

**TABLE 5-I**

COMPARISON OF KT66 AND KT88

	<i>KT66</i>	<i>KT88</i>	
$V_h$	6.3	6.3	V
$I_h$	1.27	1.8	A
$V_a$ (max.)	500	600	V
$V_{g2}$ (max)	400	600	V
$P_a$ (max)	25	35	W
$P_{g2}$ (max)	3.5	6	W
$g_m$	6.3	11	mA/V
* $P_{out}$ (cathode bias, ultra-linear)	32	50	W
* $P_{out}$ (fixed bias, ultra-linear)	50	100	W
$P_{out}$ (cathode bias, triode-connected)	14	27	W
Overall length	135	120	mm
Seated length	120	105	mm
Diameter	52	52	mm

\*Class AB1 Push-Pull.

**5-2. KT88 50W Ultra-Linear Amplifier.**—The circuit of a complete amplifier with a KT88 ultra-linear output stage giving 50W output at 0.2% distortion is shown in fig. 5-2\*. The design follows the practice for other amplifiers in this book but also incorporates the capacitors C8 and C9 shunted by R12 and R13 to ensure stability at frequencies below the cut-off frequency of the output transformer. The desirability of incorporating these components is discussed more fully in Appendix B (page 119). Also shown in fig. 5-2 are networks for reducing the amount of overshoot and consequent "ringing" in the output transformer. These are C6, R10 and C7, R11 between the first two stages. The method of introducing these networks is a variation of the recommendations given in Appendix B for eliminating high-frequency instability in feedback amplifier circuits.

In other respects, the amplifier follows conventional practice. The first double triode, V1, is arranged as a self-balancing floating paraphase phase inverter which feeds V2, the following push-pull voltage amplifier. Potentiometer R22 allows the signal input to the output stage to be adjusted for output stage dynamic balance, as explained on page 8.

The power supply incorporates a thermistor in the h.t. output line in order to reduce the surge from the directly heated rectifier while the remaining valves are warming up. The performance of this amplifier is illustrated in fig. 5-3 and the output stage characteristics are given in Table 5-II below :

**TABLE 5-II**

OPERATING CONDITIONS OF THE OUTPUT STAGE OF FIG. 5-2

$V_a$ (b)	500	V
$V_a, g_2$	425	V
$I_{a+g2}$ (o)	$2 \times 87$	mA
$I_{a+g2}$ (max sig)	$2 \times 100$	mA
$P_{a+g2}$ (o)	$2 \times 40$	W
$P_{a+g2}$ (max sig)	$2 \times 18$	W
$R_k$	$2 \times 525$	Ω
$V_g$ (approx)	-50	V
$P_{out}$	50	W
$R_L$ (a-a)	5	kΩ
D	0.2%	%
$V_{in}$ (rms) (to first stage)	500	mV

#### COMPONENT VALUES FOR FIG. 5-2

KT88 50W ULTRA-LINEAR AMPLIFIER

G.E.C. VALVES	RESISTORS	
V1 B339/12AX7	(20% 0.5W unless otherwise shown)	R5 1MΩ
V2 B329/12AU7	R1 1MΩ	R6 220kΩ 10%
V3 KT88	R2 3.3kΩ	R7 220kΩ 10%
V4 KT88	R3 100Ω	R8 1MΩ
V5 U52/5U4	R4 3.3kΩ	R9 1MΩ
		R10 10kΩ





The auto-transformer does not need to be of large size since it has only to cater for the voltage difference between the mains and the rectifier supply of 255V. It is this feature of the auto-transformer that is responsible for the excellent regulation of the power supply circuit. Satisfactory results are obtained from a transformer similar in size to those used in domestic radio receivers.

The capacitance-input filter contains two large capacitors of 160 $\mu$ F and a low-resistance 1H smoothing inductor and provides a hum-free d.c. supply.

The correct quiescent current of 70-75mA is set for each valve on the meter in the cathode circuit by adjusting potentiometers R8 and R9. Resistors R17 and R18 are meter shunts, the value of which will depend upon the meter characteristics and the type of meter circuit adopted. The potentiometer R5 in the anode circuit of the first stage is adjusted at 90% of maximum output to give equal cathode currents in the output stage for obtaining dynamic balance. Resistor R19, in the bias line, reduces the potential at C8 to 60V from the 70V it would otherwise be.

**TABLE 5-III**  
OPERATING CONDITIONS OF THE OUTPUT STAGE OF FIG. 5-5

$V_{a, g2}$ (o)	325	V
$V_{a, g2}$ (max sig)	300	V
$I_{a+g2}$ (o)	2 $\times$ 75	mA
$I_{a+g2}$ (max sig)	2 $\times$ 165	mA
$P_{a+g2}$ (o)	2 $\times$ 25	W
$P_{a+g2}$ (max sig)	2 $\times$ 12.5	W
$V_{g1}$	-50 to -55	V
$P_{out}$	50	W
$R_L$ (a-a)	2.25	k $\Omega$
$Z_{out}$	2.7	k $\Omega$
*D	5	%
$V_{in}$ (rms) (to first stage)	2 $\times$ 2.5	V

\* Assuming the othode currents are balanced at 90% of maximum output by R5

**COMPONENT VALUES FOR FIG. 5-5**  
KT55 50W ULTRA-LINEAR AMPLIFIER

**G.E.C. VALVES**

V1 B65/6SN7  
V2 KT55  
V3 KT55

**RESISTORS**

(20%, 0.25W unless otherwise shown)

R1 1M $\Omega$   
R2 1M $\Omega$   
R3 1k $\Omega$   
R4 33k $\Omega$  1W  
R5 20k $\Omega$  w.w. preset  
R6 33k $\Omega$  1W  
R7 100k $\Omega$  10%


R8 10k $\Omega$  w.w. preset  
R9 10k $\Omega$  w.w. preset  
R10 100k $\Omega$  10%  
R11 10k $\Omega$  10% 1W  
R12 10k $\Omega$   
R13 10k $\Omega$   
R14 4.7k $\Omega$  10% 1W  
R15 270 $\Omega$   
R16 270 $\Omega$   
R17 } Meter shunts  
R18 }  
R19 150 $\Omega$   
R20 470-1500 $\Omega$  0.5W  
R21 470-1500 $\Omega$  0.5W

**CAPACITORS**

C1 16 $\mu$ F 350V  
C2 0.1 $\mu$ F  
C3 0.1 $\mu$ F  
C4 160 $\mu$ F 450V  
C5 1000pF  
C6 1000pF  
C7 160 $\mu$ F 450V  
C8 32 $\mu$ F 100V

**MISCELLANEOUS**

L1 1H 350mA 20 $\Omega$   
T1 50W Ultra-linear transformer  
2.25k $\Omega$  anode-anode  
Primary inductance :  $\geq$  12H  
Leakage inductances :  
Prim.-sec. :  $\geq$  10mH  
 $\frac{1}{2}$  prim.-UL tap :  $\geq$  10mH  
T2 Mains auto-transformer (see text)  
MR1 275V 350mA (G.E.C. Z13H17XG)  
MR2 60V 10mA (G.E.C. Z11H4X)  
S1 1-pole 3-way

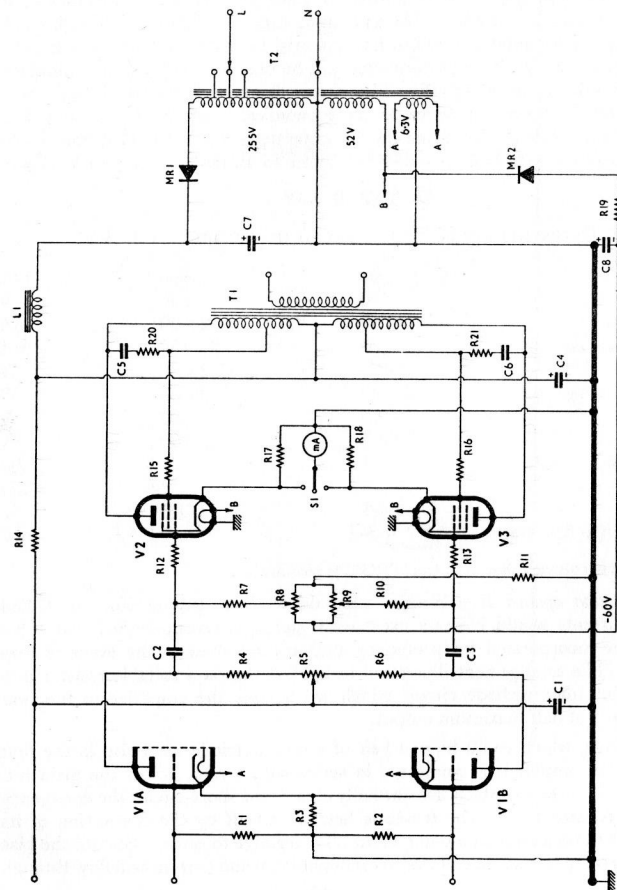

**Fig. 5-5.** Circuit of the KT55 50W amplifier. The earth line or chassis is connected to one side of the mains supply. If this amplifier is preceded by a triode phase-splitting stage such as that in fig. 5-8, the required signal input will be 2.5V.

**5-4. KT88 100W Fixed Bias Ultra-linear Amplifier.**—The circuit of this amplifier is given in fig. 5-8 and it follows, in general, the main details of the KT55 50W amplifier described in the previous section. Points of difference include the addition of a phase-splitter at the input and, of course, the h.t. power and grid bias supplies.

This amplifier provides 100W output at 5% distortion with an h.t. potential of 560V

With fixed bias, the large change in anode current necessitates a low impedance power supply and, with normal rectifier circuits, an inductance-input smoothing filter is essential. The smoothing capacitor should be of high value to prevent an instantaneous fall in h.t. potential upon the occurrence of a transient signal. Satisfactory performance will be obtained with a single inductor and a capacitance of 50-150 $\mu$ F. The circuit diagram shows two 160 $\mu$ F 450V electrolytic capacitors in series as an economical method of obtaining the required capacitance. Reducing the h.t. potential to 460V, the load impedance to 4k $\Omega$  and the grid bias to -65V results in an amplifier giving 65W output.

**TABLE 5-IV**


OPERATING CONDITIONS OF THE OUTPUT STAGE OF FIG. 5-8

$V_a$ (b)	460	560	V
$V_{a, g2}$	450	550	V
$I_{a+g2}$ (o)	2 $\times$ 50	2 $\times$ 50	mA
$I_{a+g2}$ (max sig)	2 $\times$ 120	2 $\times$ 150	mA
$P_{a+g2}$ (o)	2 $\times$ 25	2 $\times$ 30	W
$P_{a+g2}$ (max sig)	2 $\times$ 20	2 $\times$ 33	W
* $V_{g1}$	-65	-80	V
$P_{out}$	65	100	W
$R_L$ (a-a)	4	4.5	k $\Omega$
$Z_{out}$	6.5	6.5	k $\Omega$
$\dagger D$	3.6	3.6	%
$V_{in}$ (rms) (to first stage)	1 to 1.5	1 to 1.5	mV

\*A bias voltage range of at least  $\pm 25\%$  is recommended.

**Protection against Bias Failure.**—Should the bias supply fail, the KT88 anode currents would increase excessively and it is recommended that some device be incorporated for protecting the output valves in the event of bias failure. The arrangement illustrated in fig. 5-9 inserts a suitable resistor into the output stage cathode circuit which will enable the amplifier to function temporarily at half maximum output.

A triode, which could be one half of a double triode used also in the first stage of the amplifier, is connected in series with a relay across the main h.t. supply. The relay contacts are normally closed and short-circuit the emergency cathode resistor R1. The triode is held at cut-off by the connection of its grid to the bias supply at a point about 50V negative to earth. Should the bias fail, the grid of the triode will rise to earth potential and current will flow through

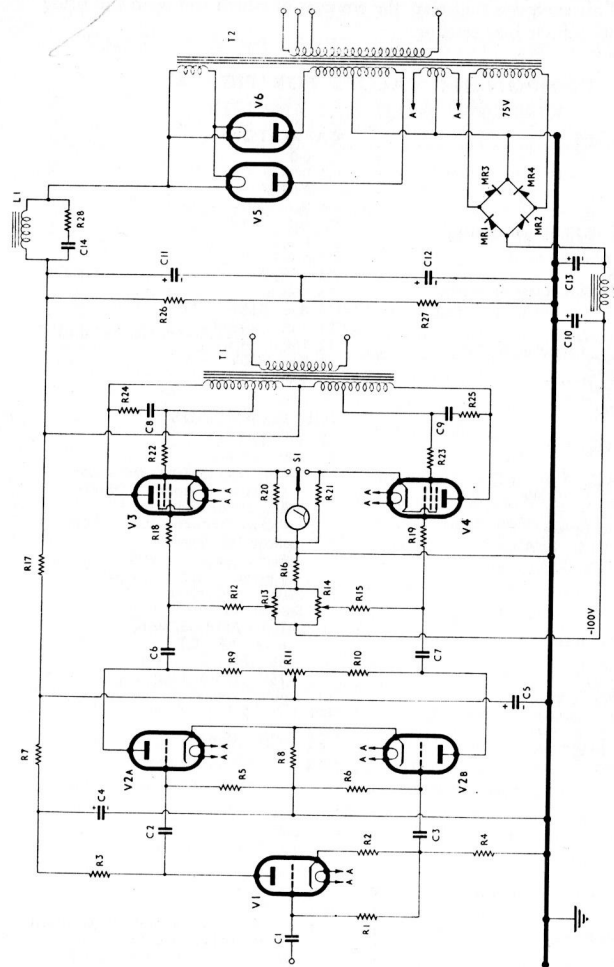

**Fig. 5-8.** Circuit of the KT88 fixed bias amplifier. Table 5-IV gives the operating conditions for obtaining either 65W or 100W maximum output from this circuit. R26 and R27 equalise the voltages across C11 and C12, the series-connected smoothing capacitors. C14 and R28 prevent the build-up of high voltage transients across L1.

the triode. This energises the relay, the contacts of which will open and bring into circuit the cathode bias resistor.

## COMPONENT VALUES FOR FIG. 5-8

### KT88 100W FIXED BIAS AMPLIFIER

#### G.E.C. VALVES

V1 L63/6J5  
 V2 B65/6SN7  
 V3 KT88  
 V4 KT88  
 V5 } U19 (or GXU50 with delay)  
 V6 }

#### RESISTORS

(20%, 0.25W unless otherwise shown)

R1 1M $\Omega$   
 R2 1.5k $\Omega$   
 R3 33k $\Omega$  1W } matched to 5%  
 R4 33k $\Omega$  1W }  
 R5 470k $\Omega$  10%  
 R6 470k $\Omega$  10%  
 R7 33k $\Omega$  1W  
 R8 1k $\Omega$   
 R9 33k $\Omega$  10% 1W  
 R10 10k $\Omega$   
 R11 33k $\Omega$  10% 1W  
 R12 100k $\Omega$  10% 0.5W  
 R13 20k $\Omega$  w.w. preset  
 R14 20k $\Omega$  w.w. preset  
 R15 100k $\Omega$  10% 0.5W  
 R16 10k $\Omega$  10% 1W  
 R17 4.7k $\Omega$  1W  
 R18 5.6k $\Omega$   
 R19 5.6k $\Omega$   
 R20 } Meter shunts  
 R21 }  
 R22 270 $\Omega$  0.5W  
 R23 270 $\Omega$  0.5W  
 R24 470-1500 $\Omega$  0.5W  
 R25 470-1500 $\Omega$  0.5W  
 R26 100k $\Omega$  10% 1W  
 R27 100k $\Omega$  10% 1W  
 R28 10k $\Omega$  0.5W

#### CAPACITORS

C1 0.01 $\mu$ F  
 C2 0.05 $\mu$ F  
 C3 0.05 $\mu$ F  
 C4 8 $\mu$ F 350V  
 C5 8 $\mu$ F 450V  
 C6 0.1 $\mu$ F  
 C7 0.1 $\mu$ F  
 C8 1000pF  
 C9 1000pF  
 C10 8 $\mu$ F 250V  
 C11 160 $\mu$ F 450V } each 100+60 dual  
 C12 160 $\mu$ F 450V }  
 C13 8 $\mu$ F 250V  
 C14 0.01 $\mu$ F 750V

#### MISCELLANEOUS

L1 5H 325mA  
 L2 20H 10mA  
 T1 100W Ultra-linear transformer  
 4.5k $\Omega$  anode-anode (100W)  
 4k $\Omega$  anode-anode (65W)  
 Primary inductance:  $\leq$  40H  
 Leakage inductances:  
 Prim.—sec.:  $\geq$  6mH  
 $\frac{1}{2}$  prim.—UL tap:  $\geq$  6mH  
 T2 Mains transformer  
 Secondaries:  
 700-0-700V 325mA  
 6.3V 5A CT  
 5V 7A  
 75V 10mA (bias)  
 S1 1-pole 3-way  
 MR1 }  
 MR2 } 75V 10mA  
 MR3 }  
 MR4 }

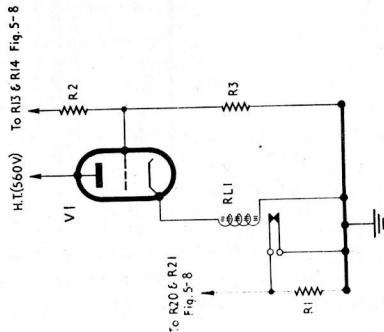


Fig. 5-9. Bias failure protection for the KT88 fixed bias amplifier. R2 is connected to the positive (earthly) junction of R13 and R14 in fig. 5-8. R2 and R3 take the place of R16 in the amplifier. The earth connection to the meter in fig. 5-8 is broken and the meter (and R20, R21) taken to R1. Component values: V1: G.E.C. L63/6J5GT; R1: 330 $\Omega$  10% 5W; R2: 6.8k $\Omega$  10% 0.5W; R3: 15k $\Omega$  10% 0.5W; RL1: 20k $\Omega$ .

## CHAPTER 6

### CLASS B AMPLIFIERS OF 175 TO 200 WATTS

The Class B amplifier is recognised as an economical method of obtaining a high audio output because of its high efficiency and the simplicity of the circuit arrangement. The absence of a separate grid bias supply renders the valve self-protective and eliminates the need for an interlock for delaying the application of h.t. until bias is established. It is necessary to qualify this statement in view of the small degree of bias used in the output stage of the amplifier of fig. 6-5. In this case, however, the bias serves only to limit the quiescent dissipation and, unlike normal fixed bias arrangements, no harm results from running the output stage for short periods of a few minutes without this bias being fully established.

Much of the distortion associated with the Class B amplifier in the past was due to the leakage inductance of the driver stage coupling transformer but this has now been largely overcome by using the cathode-coupled bridged transformer. This arrangement was discussed in more detail in Section 1-3.

This chapter describes 175W and 200W amplifier circuits containing the DA42, an indirectly heated triode designed specifically for Class B operation.

**6-1. DA42 175W Amplifier.**—The complete amplifier circuit is shown in fig. 6-1 and comprises—apart from the output stage—a KT66 driver stage, which supplies the necessary 75+75V for full output, and a push-pull intermediate stage consisting of two N709 pentodes. The resistance-coupled N709 valves are required to deliver 80+80V, and this output is obtained at low distortion because of the high h.t. voltage available, provided the screen and cathode resistors are of optimum value. The input stage may utilise any small triode such as the DH77 shown, which draws an anode current of 2mA.

The combined anode and screen current of each N709 is 6mA, and the anode and screen potentials being 150 and 60, respectively. An input not exceeding 1+1V to this stage gives an output of 80+80V at less than 2% distortion.

With 500V h.t. supply for the KT66 valves a bias of 45V is required, giving an anode current of 70-80mA for the pair. A common cathode resistance of 600 $\Omega$  is necessary to give this bias and this is partly supplied by the resistance of the half-primaries of the coupling transformer. An additional resistor (R19), common to both valves, is usually necessary. In the transformer used for the prototype, the resistance of each half-primary was about 300 $\Omega$  and R19 was found to require a value of 440 $\Omega$ .

The coupling transformer bridging capacitors are not critical in value within the limits of 2 $\mu$ F to 16 $\mu$ F.

The output transformer should have low leakage inductance between the two half-primaries and between the primary and secondary. For a 100V output line (60 $\Omega$  in this case), the primary/secondary ratio is 13:1.

The amplifier of fig. 6-1 gives 175W output at 6% distortion for an input of less than 1V r.m.s. and the performance of the output stage is displayed by the curves of fig. 6-3. Table 6-I gives the operating conditions.

## COMPONENT VALUES FOR FIG. 6-1

### DA42 175W AMPLIFIER

#### G.E.C. VALVES

V1 DH77/6AT6  
 V2 N709  
 V3 N709  
 V4 KT66  
 V5 KT66  
 V6 DA42  
 V7 DA42

R17 10k $\Omega$   
 R18 10k $\Omega$   
 R19 (See text above)  
 R20 100 $\Omega$   
 R21 100 $\Omega$   
 R22 5k $\Omega$  10% 10W  
 R23 5k $\Omega$  10% 10W

#### RESISTORS

(20%, 0.25W unless otherwise shown)  
 R1 470k $\Omega$   
 R2 1.5k $\Omega$   
 R3 22k $\Omega$  0.5W  
 R4 22k $\Omega$  0.5W } matched to 5%  
 R5 470k $\Omega$  10%  
 R6 470k $\Omega$  10%  
 R7 10k $\Omega$   
 R8 10k $\Omega$   
 R9 47k $\Omega$  0.5W  
 R10 220 $\Omega$  0.5W  
 R11 470k $\Omega$  10% 0.5W  
 R12 47k $\Omega$  5% 5W w.w.  
 R13 47k $\Omega$  5% 5W w.w.  
 R14 4.7k $\Omega$  10% 1W  
 R15 470k $\Omega$   
 R16 470k $\Omega$

#### CAPACITORS

C1 0.01 $\mu$ F  
 C2 0.01 $\mu$ F  
 C3 0.01 $\mu$ F  
 C4 4 $\mu$ F 450V  
 C5 0.5 $\mu$ F  
 C6 16 $\mu$ F 450V  
 C7 0.05 $\mu$ F  
 C8 0.05 $\mu$ F  
 C9 16 $\mu$ F 100V  
 C10 16 $\mu$ F 100V  
 C11 2000pF 1kV  
 C12 2000pF 1kV  
 C13 150 pF

#### TRANSFORMERS

T1 Bridged transformer (see fig. 6-7)  
 T2 Output transformer (see fig. 6-8)

TABLE 6-1

### OPERATING CONDITIONS OF THE OUTPUT STAGE OF FIG. 6-1

$V_a$ (b)	1 (approx)	kV
$V_a$	1	kV
$I_a$ (o)	$2 \times 25$	mA
$I_a$ (max sig)	$2 \times 140$	mA
$P_a$ (o)	$2 \times 25$	W
$P_a$ (max sig)	$2 \times 50$	W
$V_g$	0	V
$I_g$ (max sig)	$2 \times 25$	mA
$P_{out}$	175	W
$R_L$ (a-a)	10	k $\Omega$
$Z_{out}$	15	k $\Omega$
D	6	%
pdr	5	W
$V_{in}$ (g-g) (pk)	175	V
$V_{in}$ (rms) (to first stage)	$\geq 1$	V

These conditions should be used only for normal speech and music. A continuous tone at maximum output will exceed the permitted dissipation and for such applications  $R_{L(a-a)}$  must be increased by at least 20%.

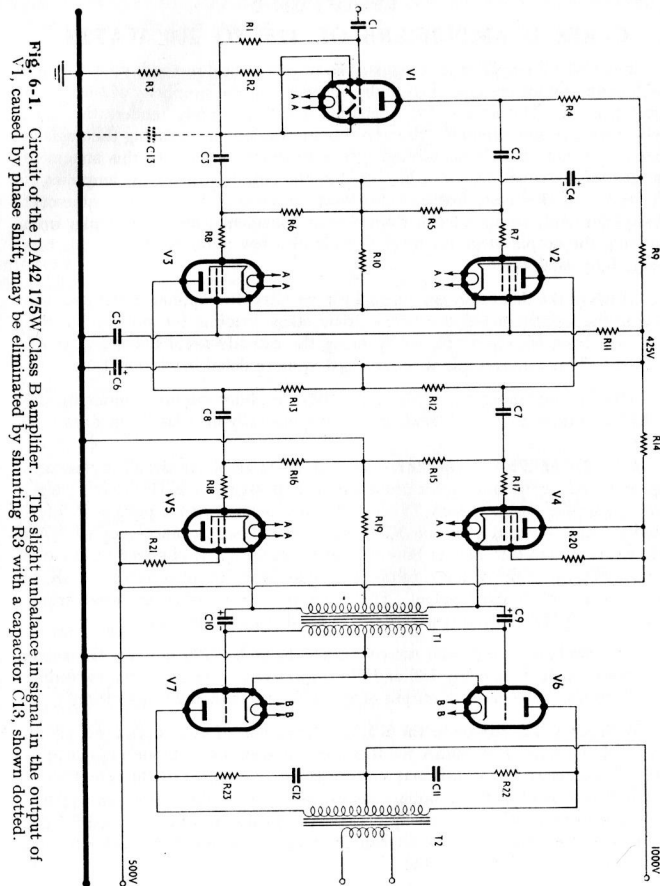


Fig. 6-1. Circuit of the DA42 175W Class B amplifier. The slight unbalance in signal in the output of V1, caused by phase shift, may be eliminated by shunting R3 with a capacitor (C13, shown dotted).

The addition of negative feedback, as described below, results in the following conditions :

$P_{out}$	175	W
$Z_{out}$	3 to 4	k $\Omega$
D	$\leq 2$	%
$V_{in}$ (rms) (to first stage)	$\leq 5$	V

**Negative Feedback.**—An improved performance is obtained at the expense of a reduction in sensitivity by adding negative feedback. The circuit modifications are given in fig. 6-2 and this arrangement applies 12-14 db feedback, which provides a damping factor of about 4.5 and reduces the distortion to 2% at 175W.


The coupling transformer T1 introduces negligible phase shift so that feedback may be taken from the output transformer secondary to the N709 cathode circuit. The single cathode bias resistor is replaced by R1 and R2, and resistors R3 and R4 provide the feedback paths from each end of the transformer secondary.

The values of R3 and R4 are determined by the load impedance but, with a 100V line (60 $\Omega$ ), they are each 3.3k $\Omega$ .


**Power Supply.**—The power supply circuit of fig. 6-4 is unconventional in that one set of rectifiers and one transformer provide two h.t. voltages, one of which is twice the value of the other. Compared with conventional circuits, this arrangement, which is described more fully in Section 1-9, would appear to offer a saving in both initial cost and space.

The rectifiers are not equally loaded, two of them having to supply the low voltage current of 100mA in addition to the 275mA at 1000V required by the DA42 stage at maximum output. However, this is well within the capability of the four U19 rectifiers specified since their rated maximum output in this type of circuit is 500mA at 4kV. The GXU50 xenon rectifier may be used as an alternative to the U19 ; a 10-second switching delay being then required.

As the power supply impedance causes some interaction between the low and high voltage supplies, a sudden demand for maximum current would cause a reaction in the 500V supply if a conventional 4-8 $\mu$ F smoothing capacitor is used in the high voltage supply. Connecting three 160 $\mu$ F, 450V electrolytic capacitors in series achieves an effective capacitance of 50-60 $\mu$ F, with a working voltage of 1350. Resistors R1, R2 and R3 equalise the voltage across each capacitor. The same principle is applied to the capacitors in the low voltage supply.

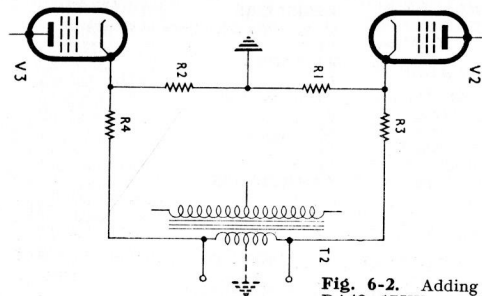

**Fig. 6-2.** Adding negative feedback to the DA42 175W amplifier. Component values : R1 and R2 : 330 $\Omega$  10% 0.5W ; R3 and R4 : 3.3k $\Omega$  10% 1W (for 100V line output). Other designations are as shown on fig. 6-1.

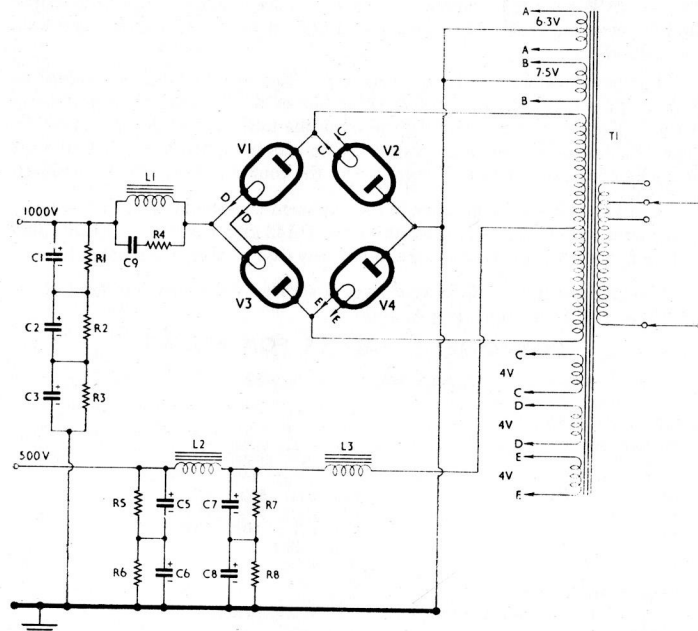

**Fig. 6-4.** Power supply circuit for the 175W and 200W amplifiers of figs. 6-1 and 6-5. Although three secondary windings can be used for the rectifier filaments, as shown, transformer winding is simplified if four identical windings are used. Component values are given below.



### G.E.C. VALVES

V1 }  
V2 } U19 or GXU50  
V3 }  
V4 }

### MISCELLANEOUS

L1 10H 275mA  
L2 10H 100mA  
L3 10H 100mA  
T1 Mains transformer  
Secondaries  
1200V CT 275mA  
6.3V 5A CT  
7.5V 2.5A CT  
4V 3.5A  
4V 3.5A  
4V 7.0A (or two 3.5A)

### RESISTORS

(10%, 1W unless otherwise shown)

R1 }  
R2 } 100kΩ  
R3 }  
R4 10kΩ 2W  
R5 }  
R6 } 100kΩ  
R7 }  
R8 }

### CAPACITORS

C1 }  
C2 }  
C3 }  
C5 160μF 450V (each 100 60 dual)  
C6 }  
C7 }  
C8 }  
C9 0.01μF 1.5kV

### CAPACITORS

C1 0.01μF  
C2 0.01μF  
C3 0.01μF  
C4 4μF 450V  
C5 0.5μF 450V  
C6 16μF 450V  
C7 0.05μF  
C8 0.05μF  
C9 16μF 100V  
C10 16μF 100V  
C11 2000pF 1kV  
C12 2000pF 1kV  
C13 8μF 500V

C14 8μF 600V  
C15 100μF 12V  
C16 150pF

### MISCELLANEOUS

L1 10H 120mA  
T1 Bridged transformer (see fig. 6-7)  
T2 Output transformer (see fig. 6-8)  
T3 Mains transformer  
Secondaries  
425-0-425V 120mA  
6.3V 5A CT  
7.5V 2.5A CT  
5V 3A

TABLE 6-II

OPERATING CONDITIONS OF THE OUTPUT STAGE OF FIG. 6-5

V <sub>a</sub> (b)	1.25 (approx)	kV
V <sub>a</sub>	1.25	kV
I <sub>a</sub> (c)	2 × 20	mA
I <sub>a</sub> (max sig)	2 × 120	mA
P <sub>a</sub> (a)	2 × 12.5	W
P <sub>a</sub> (max sig)	2 × 25	W
V <sub>g</sub> (e)	-4	V
I <sub>g</sub> (max sig)	2 × 20	mA
P <sub>out</sub>	200	W
R <sub>L</sub> (a-a)	13	kΩ
Z <sub>out</sub>	15	kΩ
D	6	%
P <sub>dt</sub>	4.5	W
V <sub>in</sub> (g-k) (pk)	200	V
V <sub>in</sub> (rms) (to first stage)	1	V

These conditions should be used only for normal speech and music. A continuous tone at maximum output will exceed the permitted dissipation and for such applications R<sub>L</sub> (a-a) must be increased by at least 20%.

**Power Supply.**—The combined power supply in fig. 6-4 cannot be used because of the common negative connection. Two separate supplies are required: one inductance-input supply giving 240mA at 1250V for the output stage and one, which may be capacitance-input, of 400-500V for the earlier stages. A suggested arrangement for the latter is incorporated in fig. 6-5.

57

### COMPONENT VALUES FOR FIG. 6-5

#### DA42 200W AMPLIFIER

### G.E.C. VALVES

V1 DH77/6AT6  
V2 N709  
V3 N709  
V4 KT66  
V5 KT66  
V6 DA42  
V7 DA42  
V8 U54

### RESISTORS

(20%, 0.25W unless otherwise shown)

R1 470kΩ  
R2 1.5kΩ  
R3 22kΩ 0.5W } matched to 5%  
R4 22kΩ 0.5W }  
R5 470kΩ 10%  
R6 470kΩ 10%

R7 10kΩ  
R8 10kΩ  
R9 47kΩ 0.5W  
R10 220Ω 0.5W  
R11 470kΩ 10% 0.5W  
R12 47kΩ 5% 5W  
R13 47kΩ 5% 5W  
R14 4.7kΩ 10% 1W  
R15 470kΩ  
R16 470kΩ  
R17 10kΩ  
R18 10kΩ  
R19 (See page 66)  
R20 100Ω  
R21 100Ω  
R22 7.5kΩ 10W  
R23 7.5kΩ 10W  
R24 47kΩ 5W  
R25 47Ω 1W

## CHAPTER 7

### CLASS AB AMPLIFIERS OF 100 TO 300 WATTS

The DA100 triode is designed for use in Class AB circuits and this chapter gives design information for Class AB1 and AB2 amplifiers which provide output powers of 175W and 270W respectively. The data includes the conditions for giving reduced outputs of 115W and 200W respectively thereby providing a choice of four amplifiers covering the range 115W to 270W.

**7-1. DA100 115-175W Class AB1 Amplifier.**—The circuit diagram of fig. 7-1 illustrates the output and driver stages of this amplifier and Table 7-1 gives the operating data. The performance is shown by the curves of figs. 7-2, 7-3 and 7-4.

The DA100 grids are not driven positive and the preceding stage is of orthodox design and consists of a pair of triode-connected N709 or KT61 valves in a transformer-coupled push-pull Class A amplifier circuit. The output stage requires an input of 150+150V r.m.s. and this is obtained from a coupling transformer having a 1:2 ratio.

A diode is shunted across each DA100 grid circuit in order to prevent "triggering." If these diodes are absent, the output valves may be seriously damaged by excessive anode current in the event of "trigger effect" should their grids be driven positive.

Meters in the DA100 anode lines enable the grid bias to be adjusted to give the correct anode currents. These meters or other anode current measuring facilities as well as the anode circuit fuse (fig. 7-5) should always be incorporated.

A suitable power supply for the output stage is given in fig. 7-5 in which two GXU50 xenon rectifiers or U19 vacuum rectifiers are used in a bi-phase half-wave circuit having a source impedance of 400Ω. The grid bias is provided by the separate circuit also shown in fig. 7-5. The power supply for the driver and earlier stages may be of conventional design.

Table 7-II gives the data necessary for operating this amplifier at a reduced anode potential to give 115W output.

#### G.E.C. VALVES

V1 N709  
V2 N709  
V3 DA100  
V4 DA100  
V5 U709 or U78/6X4

#### RESISTORS

(20%, 0.25W unless otherwise shown)  
R1 270kΩ  
R2 270kΩ  
R3 10kΩ  
R4 330Ω 10% 0.5W  
R5 330Ω 10% 0.5W  
R6 10kΩ  
R7 100Ω  
R8 100Ω  
R9 5kΩ  
R10 5kΩ

R11 1kΩ  
R12 1kΩ  
R13 10kΩ 10% 20W  
R14 10kΩ 10% 20W

Fig. 7-1.

#### CAPACITORS

C1 0.02μF  
C2 0.02μF  
C3 50μF 50V  
C4 50μF 50V  
C5 2000pF 1.5kV  
C6 2000pF 1.5kV

#### TRANSFORMERS

T1 Intervalve transformer, 1 : 2  
T2 Output transformer  
7kΩ anode-anode (175W)  
6kΩ anode-anode (115W)

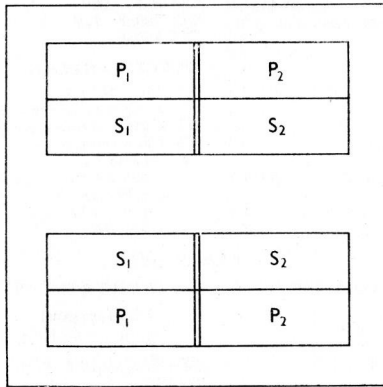


Fig. 6-7. The coupling transformer T1 in figs. 6-1 and 6-5. Winding details are as follows :

Core : Stalloy No. 4 ; square section ; no gap.  
Primary : 2000+2000 turns, 28 s.w.g.  
Secondary : 2000+2000 turns, 30 s.w.g.

The primary and secondary half-windings P1 and S1 are wound in the opposite direction to P2 and S2 so that, when the inner ends of each half-winding are joined, they are series-aiding. The number of turns in each of the four sections must be identical.

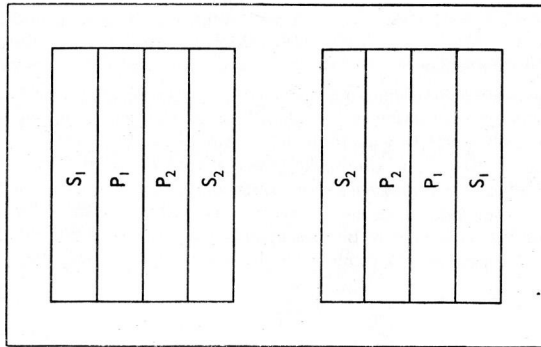


Fig. 6-8. The 100V line (60Ω) output transformer T2 in figs. 6-1 and 6-5. Winding details are as follows :

Core : Stalloy No. 66 ; square section ; no gap.  
Primary : 1250+1250 turns, 28 s.w.g.  
Secondary : 100+100 turns, 15 s.w.g.

All windings are wound in the same direction. The secondary is connected in series-aiding.

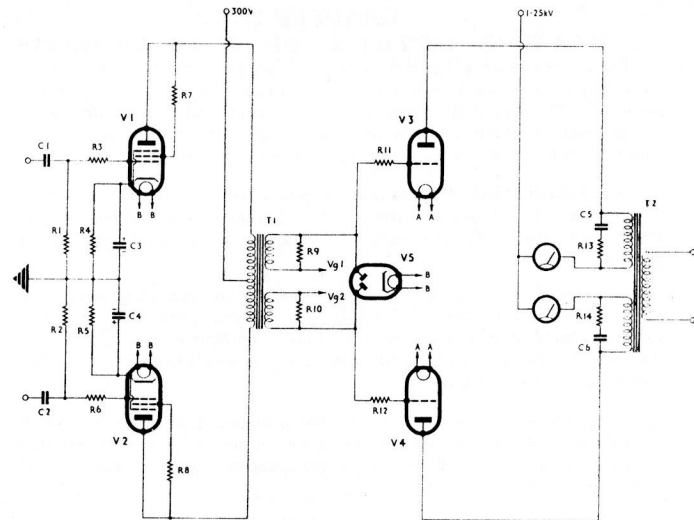


Fig. 7-1. Circuit of the driver and output stages of the DA100 Class AB1 115-175W amplifier.

TABLE 7-I

OPERATING CONDITIONS OF THE CLASS AB1 175W AMPLIFIER OF FIG. 7-1

$V_a$ (b)	1.25 (approx)	kV
$V_a$	1.25	kV
* $I_a$ (o)	$2 \times 50$	mA
$I_a$ (max sig)	$2 \times 150$	mA
$p_a$ (o)	$2 \times 70$	W
$p_a$ (max sig)	$2 \times 100$	W
$V_g$ (o)	225	V
$P_{out}$	175	W
$R_L$ (a-a)	7	k $\Omega$
D	3	%
$V_{in}$ (pk) (g-g)	$2 \times 225$	V
$V_{in}$ (rms) (to driver stage)	$2 \times 10$	V

\*Precise value unimportant and may be between 40 and 60mA.

## COMPONENT VALUES FOR FIG. 7-5

POWER SUPPLY FOR DA100 AB1 AND AB2 AMPLIFIERS

### G.E.C. VALVES

V1 U19 or GXU50  
V2 U19 or GXU50  
V3 U52/5U4G

### RESISTORS

R1 10k $\Omega$  20% 0.5W  
R2 2k $\Omega$  5W w.w.  
R3 2k $\Omega$  5W w.w.  
R4 2k $\Omega$  10% 20W w.w.

### CAPACITORS

C1 4 $\mu$ F 1.5kV  
C2 4 $\mu$ F 1.5kV  
C3 0.01 $\mu$ F 1.5kV  
C4 16 $\mu$ F 350V

### MISCELLANEOUS

\*L1 5H 300mA  
\*L2 5-25H 300mA swinging choke  
L3 20H 150mA  
T1 4V 7A  
T2 As required  
T3 Bias transformer  
Secondaries  
250-0-250V 100mA (1kV operation)  
325-0-325V 100mA (1-25kV operation)  
6V 4A CT  
6.3V CT as required  
5V 3A  
F1 500mA  
\* $> 50\Omega$  for AB2

TABLE 7-II

OPERATING CONDITIONS OF THE CLASS AB1 AMPLIFIER OF FIG. 7-1 FOR REDUCED OUTPUT OF 115W

$V_a$ (b)	1 (approx)	kV
$V_a$	1	kV
* $I_a$ (o)	$2 \times 50$	mA
$I_a$ (max sig)	$2 \times 135$	mA
$p_a$ (o)	$2 \times 55$	W
$p_a$ (max sig)	$2 \times 90$	W
$V_g$ (o)	-175	V
$P_{out}$	115	W
$R_L$ (a-a)	6	k $\Omega$
D	3	%
$V_{in}$ (pk) (g-g)	$2 \times 165$	V
$V_{in}$ (rms) (to driver stage)	$2 \times 8$	V

\*Precise value unimportant and may be between 40 and 60mA.

7-2. DA100 200-270W Class AB2 Amplifier.—This amplifier, shown in fig. 7-6, requires a driver stage capable of providing the 3W driving power for the DA100 grid circuit and two KT66 in a cathode-coupled bridged transformer arrangement are recommended.

The amplifier preceding the KT66 stage is a push-pull resistance-capacitance coupled arrangement using two N709 valves as described in Chapter 1, page 14. This circuit will provide the 200+200V required at the cathodes of the KT66 driver stage.

Meters are placed in the DA100 anode lines to enable the grid bias to be adjusted for correct anode current. It is inadvisable to omit these meters or the fuse in the anode circuit (fig. 7-5). There is no danger of "trigger effect" with the Class AB2 circuit because of the low d.c. grid circuit resistance, consequently, diodes are not required in this output stage.

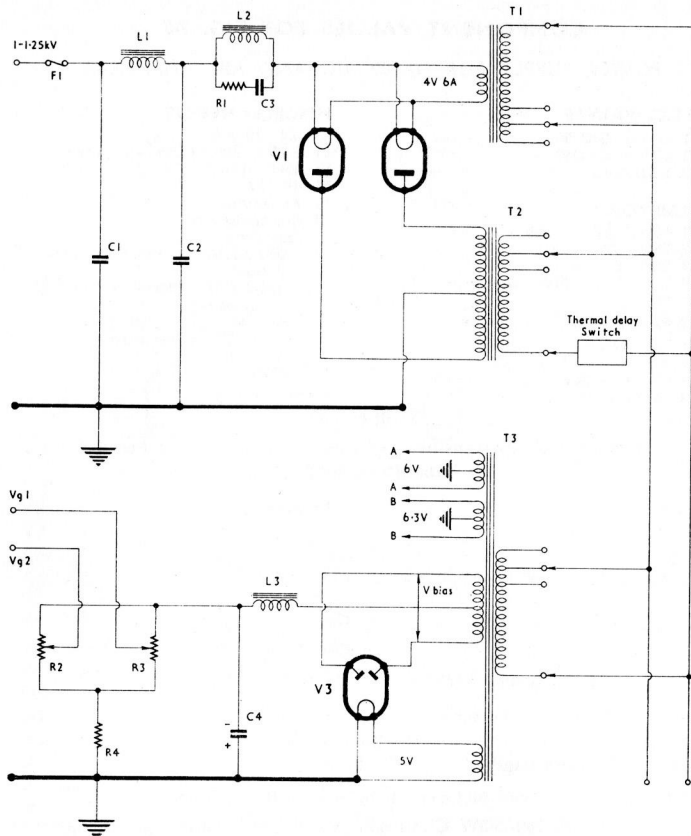


Fig. 7-5. Power supply circuit for the AB1 and AB2 amplifiers of figs. 7-1 and 7-6. The thermal delay switch at T2 is not necessary with U19 vacuum rectifiers.

The power supply of fig. 7-5 is also suitable for this amplifier and the grid bias network should provide a range of 175-250V negative to cater for differences in valve characteristics. The d.c. resistance of the inductors in the high voltage smoothing filter should not exceed  $50\Omega$ . If quality of reproduction is not important and some hum is tolerated the second inductor (L1) and capacitor (C1) may be omitted. In this event, the signal will be modulated at 100c/s ripple frequency at outputs exceeding 75% of the maximum.

The power supply for the driver and earlier stages may be of conventional design.

Table 7-III gives the output stage operating data for this amplifier and Table 7-IV the output stage characteristics for a reduced output of 200W at 1kV h.t.

TABLE 7-III

OPERATING CONDITIONS OF THE CLASS AB2 270W AMPLIFIER OF FIG. 7-6

$V_a$ (b)	1.25 (approx)	kV
$V_a$	1.25	kV
$I_a$ (o)	$2 \times 50$	mA
$I_a$ (max sig)	$2 \times 200$	mA
$P_a$ (o)	$2 \times 70$	W
$P_a$ (max sig)	$2 \times 90$	W
$V_g$ (o)	225	V
$I_g$ (max sig)	5	mA
$I_g$ (pk) (max sig)	20	mA
$P_{out}$	270	W
$R_L$ (a-a)	7	$k\Omega$
$Z_{in}$	25	$k\Omega$
D	5	%
$p_{dr}$	3	W
$V_{in}$ (pk) (k-g)	$2 \times 300$ (approx)	V
$V_{in}$ (rms) (to driver stage)	$2 \times 15$	V

TABLE 7-IV

OPERATING CONDITIONS OF THE CLASS AB2 AMPLIFIER OF FIG. 7-6 FOR REDUCED OUTPUT OF 200W

$V_a$ (b)	1 (approx)	kV
$V_a$	1	kV
$I_a$ (o)	$2 \times 50$	mA
$I_a$ (max sig)	$2 \times 150$	mA
$P_a$ (o)	$2 \times 55$	W
$P_a$ (max sig)	$2 \times 85$	W
$V_g$ (o)	-175	V
$I_g$ (max sig)	15	mA
$I_g$ (pk) (max sig)	60	mA
$P_{out}$	200	W
$R_L$ (a-a)	5	$k\Omega$
$Z_{in}$	7	$k\Omega$
D	5	%
$p_{dt}$	7	W
$V_{in}$ (pk) (g-g)	$2 \times 250$	V
$V_{in}$ (rms) (to driver stage)	$2 \times 10$	V

## COMPONENT VALUES FOR FIG. 7-6

### DA100 200-270W AB2 AMPLIFIER

#### G.E.C. VALVES

V1 N709  
 V2 N709  
 V3 KT66  
 V4 KT66  
 V5 DA100  
 V6 DA100

R13 100Ω  
 R14 (See Sect. 1-3)  
 R15 5kΩ 10% 50W  
 R16 5kΩ 10% 50W

#### CAPACITORS

C1 0.01μF  
 C2 0.01μF  
 C3 0.5μF  
 C4 0.05μF  
 C5 0.05μF  
 C6 4μF 350V  
 C7 4μF 350V  
 C8 2000pF 1.5kV  
 C9 2000pF 1.5kV

#### RESISTORS

(20% 0.25W unless otherwise shown)

R1 220kΩ  
 R2 220kΩ  
 R3 220Ω 10% 1W  
 R4 220kΩ 10% 1W  
 R5 47kΩ 3W } matched to 5%  
 R6 47kΩ 3W }  
 R7 4.7kΩ 10% 1W  
 R8 470kΩ  
 R9 470kΩ  
 R10 10kΩ  
 R11 10kΩ  
 R12 100Ω

#### MISCELLANEOUS

L1 Centre-tapped inductor 100-200H  
 T1 Bridged transformer (See fig. 6-7)  
 T2 Output transformer  
 7kΩ anode-anode (270W)  
 5kΩ anode-anode (200W)

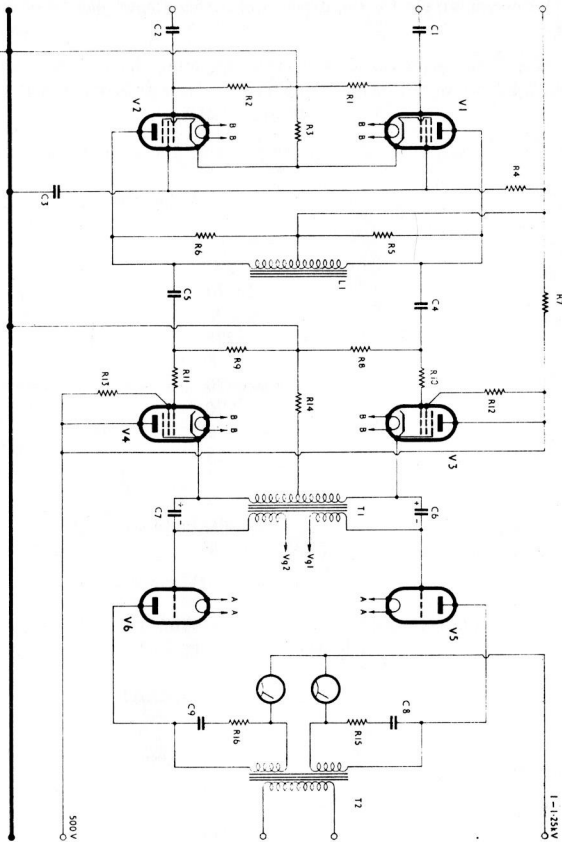


Fig. 7-6. Circuit of the DA100 Class AB2 200-270W amplifier. The cathode-coupled driver stage is preceded by two N709 beam pentodes in a push-pull voltage amplifier stage as described on page 14.




**CLASS AB AMPLIFIERS OF 300 TO 1100 WATTS**

The largest amplifiers dealt with in this book are designed round the V1505, a Class AB triode of 275W dissipation, and this chapter describes the design of both Class AB1 and AB2 circuits. The AB1 amplifier will provide up to 450W output and the AB2 amplifier up to 1100W. An output exceeding 900W requires considerable driving power and the data should be closely followed in order to obtain minimum distortion.

**8-1. V1505 300-450W Class AB1 Amplifier.**—Fig. 8-1 is the circuit diagram of the output and driver stages of this amplifier. Little explanation is required; the driver stage contains a pair of triode-connected KT66 valves which are coupled to the output stage by a transformer of 1:2 ratio. The spark gap across the output transformer primary is optional but, if it is used, the series resistor (R13) must not be omitted. A load impedance of 10kΩ is specified and this should not be reduced as a lower load will result in excessive anode dissipation at maximum output.

Fig. 8-5 contains the power supply circuit recommended for providing h.t. for the output stage. The bias voltage is provided by a normal full-wave rectifier circuit which is also shown in fig. 8-5. The KT66 driver stage power supply may be a conventional capacitance-input circuit since there is no variation in h.t. current. The KT66 valves require about 350V at 100mA.

Table 8-II gives the data necessary for operating this amplifier at a reduced anode potential to give 300W output and fig. 8-2 illustrates the corresponding performance. At this reduced level, a load impedance lower than the 10kΩ specified is permissible and this would provide a somewhat higher output

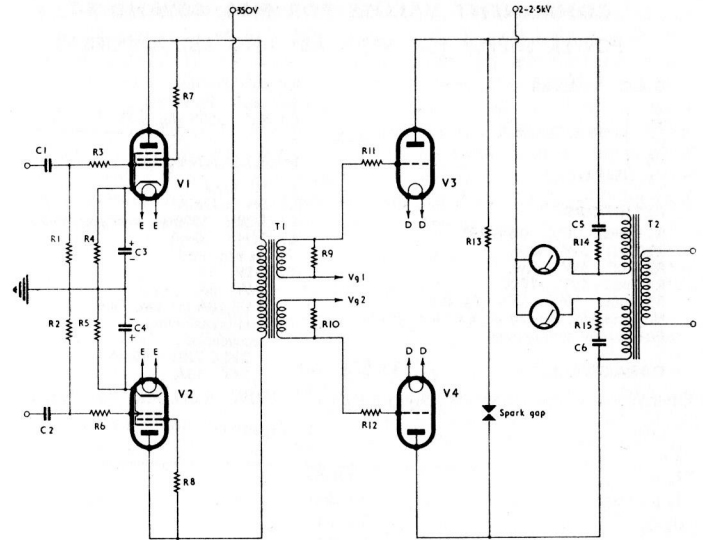

**Fig. 8-1.** Circuit of the output and driver stages of the V1505 Class AB1 300-450W amplifier. Component values are given below.

**G.E.C. VALVES**

- V1 KT66
- V2 KT66
- V3 V1505
- V4 V1505

**RESISTORS**

- (20%, 0.25W unless otherwise shown)
- R1 470kΩ
- R2 470kΩ
- R3 10kΩ
- R4 600Ω 5% 3W
- R5 600Ω 5% 3W
- R6 10kΩ
- R7 100Ω 0.5W
- R8 100Ω 0.5W
- R9 33kΩ 10% 0.5W
- R10 33kΩ 10% 0.5W

- R11 1kΩ
- R12 1kΩ
- R13 10kΩ 10% 100W (see p. 86)
- R14 10kΩ 10% 50W
- R15 10kΩ 10% 50W

**CAPACITORS**

- C1 0.02μF
- C2 0.02μF
- C3 25μF 50V
- C4 25μF 50V
- C5 2000pF 1.5kV
- C6 2000pF 1.5kV

**TRANSFORMERS**

- T1 Intervalve transformer 1:2
- T2 Output transformer 10kΩ anode-anode



To obtain 1100W output, the V1505 valves will require a driving power approximately double that needed for 900W and a considerable signal voltage is necessary. The KT66 valves (the KT88 is also suitable) must operate at an anode supply of 575V and they will each consume 55mA. The required bias of about 55V is produced by an effective cathode resistance of 1000Ω per valve made up as above.

A load impedance of 10kΩ is specified and this should not be reduced as a lower load will result in excessive anode dissipation at the half-power point—where maximum dissipation occurs in Class AB2.

The power supply circuit is the same as that recommended for the Class AB1 arrangement and is shown in fig. 8-5.

The curves in figs. 8-3 and 8-4 show the performance in detail and Table 8-III gives the output stage operating data for either 900W or 1100W output.

For an output of 600W the V1505 anode supply is reduced to 2kV and the resulting performance is illustrated in fig. 8-2. The output stage data are given in Table 8-IV. At this reduced level, a load impedance lower than the 10kΩ specified is permissible and this would provide a somewhat higher output.

**TABLE 8-III**

OPERATING CONDITIONS OF THE CLASS AB2 900-1100W AMPLIFIER OF FIG. 8-6

V <sub>a</sub> (b)	2.5 (approx)	2.5 (approx)	kV
V <sub>a</sub>	2.5	2.5	kV
*I <sub>a</sub> (o)	2×50	2×50	mA
I <sub>a</sub> (max sig)	2×275	2×300	mA
P <sub>a</sub> (o)	2×130	2×130	W
†P <sub>a</sub> (max)	2×275	2×275	W
V <sub>g</sub> (o)	-155	-155	V
I <sub>g</sub> (max sig)	30	60	mA
i <sub>g</sub> (pk) (max sig)	75	140	mA
P <sub>out</sub>	900	1100	W
R <sub>L</sub> (a-a)	10	10	kΩ
Z <sub>in</sub>	8-12	8-12	kΩ
D	6	7	%
P <sub>dr</sub>	10‡	20§	W
V <sub>in</sub> (pk) (g-g)	2×230	2×280	V
V <sub>in</sub> (rms) (to first stage)	2×5	2×6	V

\*See section 8-3, page 96.

†P<sub>a</sub> (max) occurs at half output.

‡Driver stage operating at 475V, 130mA.

§Driver stage operating at 575V, 110mA.

70

**TABLE 8-IV**

OPERATING CONDITIONS OF THE CLASS AB2 AMPLIFIER OF FIG. 8-6  
FOR REDUCED OUTPUT OF 600W

V <sub>a</sub> (b)	2 (approx)	kV
V <sub>a</sub>	2	kV
*I <sub>a</sub> (o)	2×60	mA
I <sub>a</sub> (max sig)	2×230	mA
P <sub>a</sub> (o)	2×120	W
P <sub>a</sub> (max sig)	2×170	W
V <sub>g</sub> (o)	-125	V
I <sub>g</sub> (max sig)	40	mA
i <sub>g</sub> (pk) (max sig)	95	mA
P <sub>out</sub>	600	W
R <sub>L</sub> (a-a)	10	kΩ
Z <sub>in</sub>	8-12	kΩ
D	6	%
P <sub>dr</sub>	10†	W
V <sub>in</sub> (pk) (g-g)	2×200	V
V <sub>in</sub> (rms) (to first stage)	2×4	V

\*See section 8-3, page 96.

†Driver stage operating at 475V, 130mA.

**COMPONENT VALUES FOR FIG. 8-6**

V1505 600-1100W AB2 AMPLIFIER

**G.E.C. VALVES**

V1 N709  
V2 N709  
V3 KT66  
V4 KT66  
V5 V1505  
V6 V1505

R11 100Ω  
R12 100Ω  
R13 See Sect. 8-2, page 92  
R14 10kΩ 10% 50W  
R15 10kΩ 10% 50W

**CAPACITORS**

C1 0.02μF  
C2 0.02μF  
C3 4μF 600V  
C4 4-16μF 350V  
C5 4-16μF 350V  
C6 2000pF 1.5kV  
C7 2000pF 1.5kV

**RESISTORS**

(20%, 0.25W unless otherwise shown)  
R1 470kΩ  
R2 470kΩ  
R3 220Ω  
R4 100Ω  
R5 100Ω  
R6 1.5-2.5kΩ 5W  
R7 100kΩ 10%  
R8 100kΩ 10%  
R9 10kΩ  
R10 10kΩ

**TRANSFORMERS**

T1 Intervalve transformer 1:2  
T2 Bridged transformer (see fig. 6-7)  
T3 Output transformer  
10kΩ anode-anode

71

Fig. 8-6. Circuit of the V1505 Class AB2 600-1100W amplifier.

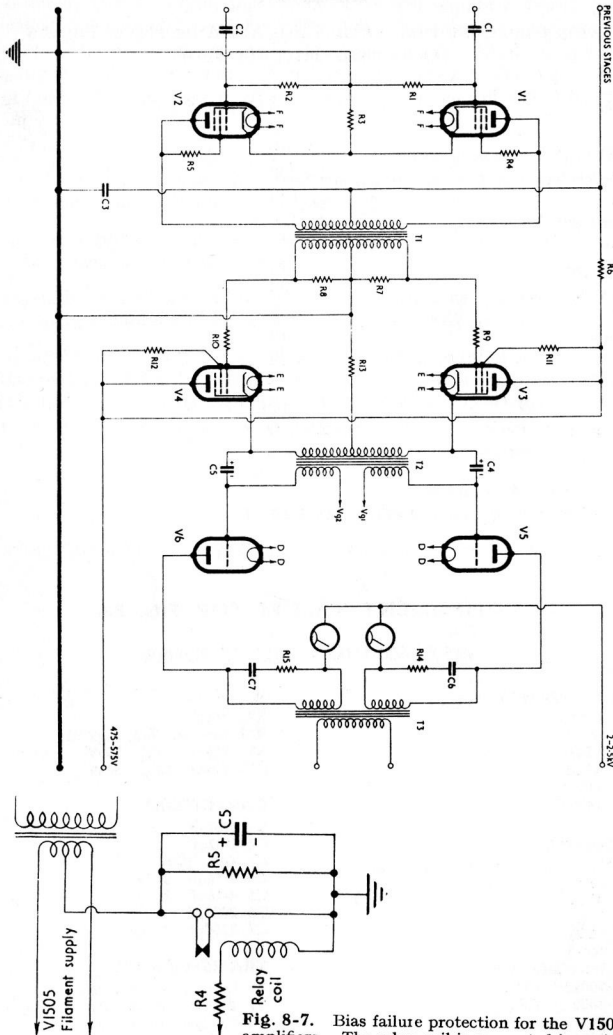


Fig. 8-7. Bias failure protection for the V1505 amplifiers. The relay coil is connected in series with R4 (fig. 8-5) and the normally-open contacts are held closed by the bias supply current. Bias failure opens the contacts and the V1505 filaments are then auto-biased by R5.

**8-3. Quiescent Current in AB1 and AB2.**—The quiescent currents selected (65mA and 50mA for anode potentials of 2kV and 2.5kV respectively) are not critical and any current of this order may be used. In both Class AB1 and AB2, the quiescent dissipation is low, at 150W, which is a desirable feature. However, too low a current will result in increased distortion whereas currents in excess of those recommended will not reduce distortion. These two values of current are chosen to give similar orders of the crossover distortion which occurs at full output as a result of the regulation of the grid bias supply circuit. Although a stabilised bias supply would remove the effect at the cost of some circuit elaboration it should be noted that the effect is virtually absent up to 90% of full output.

**8-4. Protection against Bias Failure.**—In the simple arrangement shown in fig. 8-7 a relay, with its operating coil connected to the bias supply, inserts a resistor in the V1505 filament circuit when its normally-open contacts are released by bias failure. The value of the resistor is chosen so that the V1505 valves operate with auto-bias at 100mA anode current per valve and give a reduced output of 200-300W.

## CHAPTER 9 MULTIPLE-PAIR PUSH-PULL AMPLIFIERS

When an output exceeding 100W is needed, the KT88 valve may be used in multiple pairs in parallel push-pull instead of a single pair of larger valves.\* One of the advantages of this method is the low cost of the power supply which is required to give an h.t. of only 550V. Another advantage is that a valve failure in the output stage merely reduces the available output power with a probable increase in distortion.

The circuit diagram of fig. A-1 illustrates the use of ten valves in a fixed bias ultra-linear output stage and this arrangement gives 400W output. More or less than five pairs of valves can be used, depending upon the power required.

A single control is used for grid bias adjustment and this simplifies the amplifier at the expense of somewhat higher distortion and lower output. For this to be successful the power supply must have good regulation and a suitable circuit is included in fig. A-3.

It is not essential to use accurately matched valves but the total current in each half of the push-pull stage should be equalised as closely as possible. This becomes easier with an increasing number of pairs and is facilitated by the cathode current meter built into the amplifier. The individual cathode currents will vary from about 35mA to about 60mA and each valve should be measured in turn and the valves sorted into two groups of approximately similar total current.

When the valves have been sorted and the two groups plugged into their respective halves of the amplifier, the optimum operating condition is obtained by adjusting the grid bias with R5 (fig. A-3) so that the current drawn by any single valve does not exceed 60mA. In this way an output of 400W will be obtained at a distortion of about 5%.

When using six or more valves in this type of amplifier, the value of the grid return resistors R14 and R15 is of importance and a low value is desirable. In order to facilitate the production of the necessary distortion-free input signal of 55+55V r.m.s., the output stage is driven by a pair of cathode followers V2B and V3B. With four output valves the grid resistors could be increased to 100k $\Omega$  and the cathode followers dispensed with. However, as they form parts of double triodes, the saving in cost is insignificant and, on the whole, it is preferable to retain them.

The method of measuring the cathode current of each KT88 valve is shown in fig. A-1. A resistor of 10 $\Omega$  is inserted in the cathode lead of each valve (i.e. R38, R39, etc.) and a meter M1 is connected across this resistor through switch S1 and a series resistor (R48, R49, etc.).

It was found convenient to use a meter with a full-scale deflection of 200 $\mu$ A, the value of the series resistor being such that the meter indicated 0-200mA. At full output each cathode current is about 100mA to 125mA. It may be preferred to substitute the individual cathode series resistors with a single resistor inserted between the meter and switch but the possibility of instability should be borne in mind as the individual resistors act as cathode circuit isolators.

The ultra-linear output transformer must have low leakage inductance between : primary and secondary ; half-primary and half-primary ; and each half-primary and its tap. The absolute values of leakage inductance will depend upon the number of valves used but a 400W transformer used in the prototype had the following characteristics :

Primary Inductance :	4H
<i>Leakage Inductances :</i>	
Primary to secondary :	0.75mH
Half-primary to half-primary :	0.75mH
Each half-primary to tap :	1.5mH

To prevent ultrasonic oscillation, resistor/capacitor combinations are connected between each tap and the anode terminal of each half-primary. In the prototype, C10 and R60 were also found to be desirable, the values used being 3500pF and 1k $\Omega$  respectively.

Negative feedback may be added to this amplifier in the normal way, from the secondary of the output transformer to the cathode circuit of the input valve. The values of the resistors R2 and R3 in fig. A-1 are determined by the amount of feedback and the ratio of the transformer.

Fig. A-2 illustrates a recommended layout for the output valves and is self-explanatory. Adequate ventilation should be provided ; if in doubt, a temperature sensitive paint should be used (see footnote on page 9).

**Power Supply.**—The design of the power supply is an important factor in the satisfactory operation of an amplifier of this type. The regulation should be good ; better than 10% with a current variation of 400-1200mA was obtained in the prototype. This order of regulation was achieved by using the xenon filled rectifier GXU1 which, in this application, is considerably under-run at a PIV of 1kV as against the rated PIV of 10kV. For up to six output valves, the smaller xenon rectifier GXU50 is suitable.

The circuit of a complete power supply is given in fig. A-3 and this provides the lower h.t. voltage required by the earlier stages as well as the grid bias supply.


A single inductance-input filter is shown and, with a smoothing capacitance of 150-200 $\mu$ F (obtained by series-connecting two larger capacitors), this should be satisfactory for most purposes. A further filter section may be inserted if desired. The smoothing inductor(s) should have a value of 2-3H and a d.c. resistance of about 25 $\Omega$ .

**TABLE A-1**

OPERATING CONDITIONS OF THE OUTPUT STAGE OF FIG. A-1

$V_a$ (b) (o)	570	V
$V_a$ (b) (max sig)	530	V
$V_{a, g2}$ (o)	565	V
$V_{a, g2}$ (max sig)	525	V
$I_{a+g2}$ (o) (per valve)	35 to 60	mA
$I_{a+g2}$ (max sig) (per valve)	100 to 125	mA
$I_{a+g2}$ (o) (total)	450	mA
$I_{a+g2}$ (max sig) (total)	1200	mA
$p_{a+g2}$ (o) (per valve)	35	W
$p_{a+g2}$ (max sig) (per valve)	25	W
$V_{g1}$ (approx)	-75	V
$P_{out}$	400	W
$R_L$ (a-a)	1	k $\Omega$
$Z_{out}$	1.2	k $\Omega$
D	5 to 7	%
$V_{in}$ (rms) to first stage	250	mV

If 10db of negative feedback is applied, the last three values become 400%, 2% and 750mV respectively.

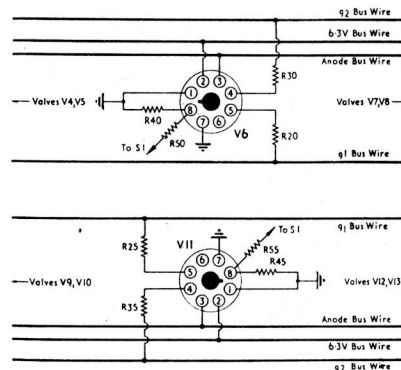

**Fig. A-2.** Recommended layout for the output valves of the 400W amplifier.



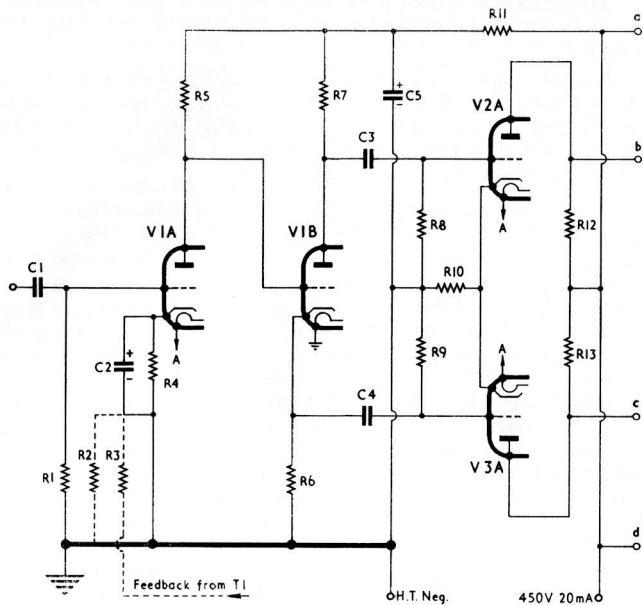


Fig. A-1. Circuit of the 400W multiple-pair amplifier, Component values are given

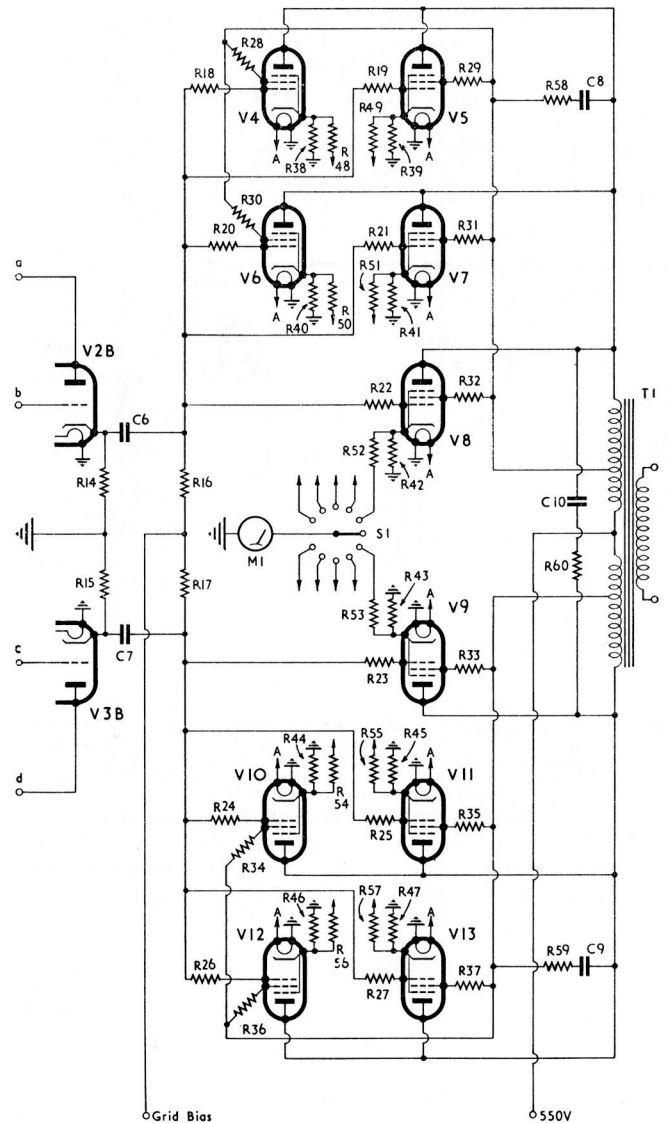

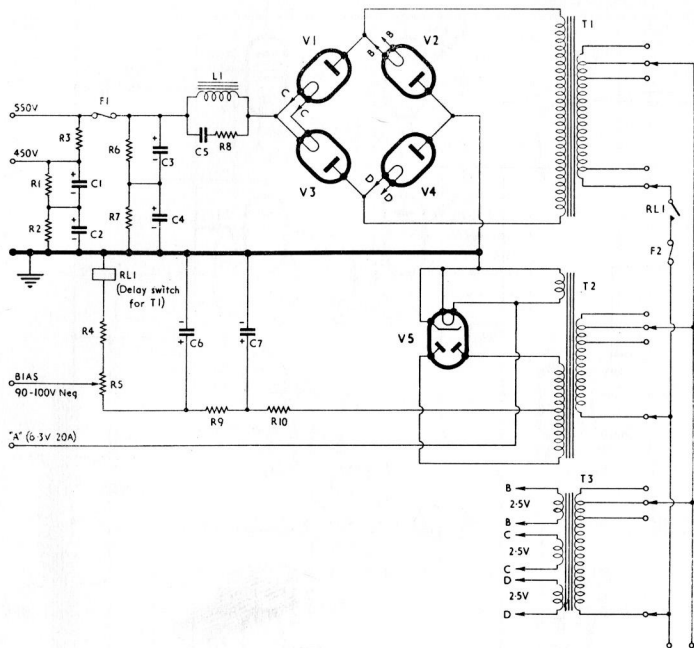



**Fig. A-3.** Power supply circuit for the 400W multiple-pair amplifier. The winding of T3 is simplified if four identical secondaries are used. To prevent mains-borne interference with nearby receivers, generated by the xenon rectifiers, a pair of capacitors (0.05 $\mu$ F, 700V a.c.) should be connected in series across the 700V winding and their junction connected to the negative (earth) line.

#### COMPONENT VALUES FOR FIG. A-1

KT88 400W AMPLIFIER

#### G.E.C. VALVES

V1-V3 B65/6SN7  
V4-V13 KT88

R48-R57 Meter series resistors,  
R58 1k $\Omega$  2W  
R59 1k $\Omega$  2W  
R60 See p. 113

#### RESISTORS

(20% 0.25W unless otherwise shown)

R1 1M $\Omega$   
R2 } See page 113  
R3 }  
R4 1k $\Omega$   
R5 100k $\Omega$  0.5W  
R6 15k $\Omega$  0.5W } matched to 5%  
R7 15k $\Omega$  0.5W }  
R8 1M $\Omega$   
R9 1M $\Omega$   
R10 4.7k $\Omega$  10% 0.5W  
R11 33k $\Omega$  0.5W  
R12 220k $\Omega$  1W } matched to 5%  
R13 220k $\Omega$  1W }  
R14 47k $\Omega$  1W } matched to 5%  
R15 47k $\Omega$  1W }  
R16 47k $\Omega$  10% 0.5W  
R17 47k $\Omega$  10% 0.5W  
R18-R27 15k $\Omega$   
R28-R37 220 $\Omega$   
R38-R47 Meter shunts, see p. 113

#### CAPACITORS

C1 0.01 $\mu$ F  
C2 50 $\mu$ F 12V  
C3 0.01 $\mu$ F  
C4 0.01 $\mu$ F  
C5 8 $\mu$ F 450V  
C6 0.25 $\mu$ F  
C7 0.25 $\mu$ F  
C8 1000pF  
C9 1000pF  
C10 See p. 113

#### MISCELLANEOUS

M1 200 $\mu$ A meter (see p. 113)  
S1 1-pole 11-way switch b.b.m.  
T1 400W Ultra-linear transformer  
1 k $\Omega$  anode-anode  
Primary inductance:  $\leq$  4H  
Leakage inductances:  
Prim.—sec.:  $\geq$  750 $\mu$ H  
 $\frac{1}{2}$  prim.—UL tap:  $\geq$  750 $\mu$ H

#### COMPONENT VALUES FOR FIG. A-3

POWER SUPPLY FOR KT88 400W AMPLIFIER

#### G.E.C. VALVES

V1-V4 GXU1  
V5 U709 or U78/6X4

#### RESISTORS

R1 100k $\Omega$  10% 0.5W  
R2 100k $\Omega$  10% 0.5W  
R3 4.7k $\Omega$  20% 2W  
R4 22k $\Omega$  20% 1W  
R5 10k $\Omega$  wirewound  
R6 47k $\Omega$  10% 1W  
R7 47k $\Omega$  10% 1W  
R8 10k $\Omega$  20% 1W  
R9 22k $\Omega$  20% 1W  
R10 1.5k $\Omega$  20% 0.25W

#### CAPACITORS

C1 32 $\mu$ F 350V  
C2 32 $\mu$ F 350V

C3 300 $\mu$ F 350V } each 100+200 dual  
C4 300 $\mu$ F 350V }  
C5 0.01 $\mu$ F 500V  
C6 2 $\mu$ F 250V  
C7 2 $\mu$ F 250V

#### MISCELLANEOUS

L1 2H 1200mA 25 $\Omega$   
T1 700V 1200mA\*  
T2 Bias transformer  
Secondaries  
150-0-150V 10mA  
6.3V 20A  
T3 2.5V 5A  
2.5V 5A  
2.5V 10A (or 2 $\times$  5A)  
F1 2A  
F2 5A

\*10V taps on primary

#### OUTPUT TRANSFORMERS AND STABILISATION

The output transformers used in the prototypes of the ultra-linear amplifiers described in this book were components of good quality made by various manufacturers. The leakage inductance was found to vary considerably, not so much between units by different makers, as between the dates of manufacture. The most recently made transformers incorporated improved methods of winding which gave very low values of leakage inductance. As a guide to this improvement, the values are tabulated below:

Relative Age of Transformer	Leakage Inductance (mH)			Comments
	P-S	$\frac{1}{2}$ P- $\frac{1}{2}$ P	$\frac{1}{2}$ P-UL tap	
Early	20-25	20	50	a-g <sub>2</sub> capacitors required for stability
Medium	10-15	10	25	Stable without capacitors
Late	5-10	5	5	Stable with 30db of negative feedback


The capacitors mentioned in the last column are those shown connected between the anode and screen of each output valve in the ultra-linear amplifier circuit diagrams in previous chapters. They have a value of 1000-2000pF and are connected in series with resistors of 470-1500 $\Omega$ .

All amplifiers and transformers were examined with a square wave generator and oscilloscope at a frequency of 5-10kc/s and it was found that the overshoot produced was roughly proportional to the leakage inductance. The earlier transformers produced an overshoot of about 25% and a ringing frequency below 40kc/s. In the later types the overshoot is reduced to less than 10% at a frequency above 100kc/s.

When negative feedback was applied it was found essential with the two earlier groups and desirable with the latest transformers to attenuate the high frequency response of the amplifier. The method of doing this is shown by the circuit of fig. B-1, in which the attenuation is achieved by a capacitor and resistor in series between the anode of the first triode amplifier stage and earth. A slightly different arrangement is necessary when the first stage consists of a balanced phase inverter such as the one used in the KT88 50W amplifier of fig. 5-2 (page 55). In this, the attenuating components (C6, R10 and C7, R11) are incorporated in each half of the phase inverter in order to maintain the balance of the stage. The principle is the same, however, and the following comments apply to both arrangements.

Referring now to fig. B-1, the optimum values of C1 and R1 will depend upon the degree of attenuation required but, with the latest transformers, values of 500pF and 10k $\Omega$  gave an attenuation of 3db at 25kc/s and 10db at 40kc/s. With these values, complete stability was obtained with feedback applied. With earlier transformers the capacitor and resistor were required to have values up to 2000pF and down to 1k $\Omega$ . All these values assume a valve impedance of about 10k $\Omega$  but if V1 in fig. B-1 is a pentode-connected Z729 with an anode load of 100-330k $\Omega$ , suitable values for C1 and R1 would be 50-200pF and 100-10k $\Omega$  respectively.

To ensure stability at very low frequencies, below the cut-off frequency of the output transformer, it is advisable to insert low frequency attenuation

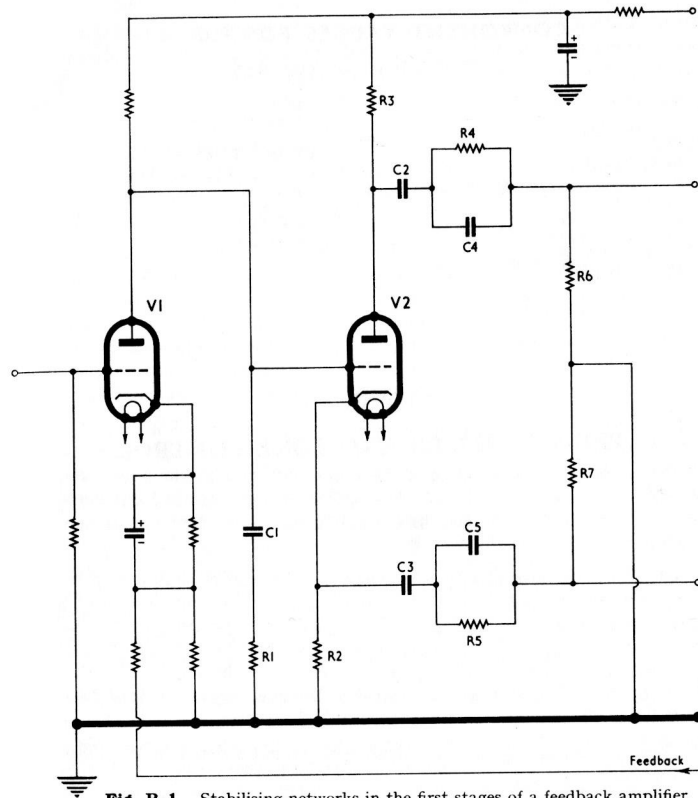

**Fig. B-1.** Stabilising networks in the first stages of a feedback amplifier. between the first and second stages within the feedback loop. The recommended arrangement is shown in fig. B-1 and consists of a capacitor and shunt resistor in each grid line between the two stages, designated C4, R4 and C5, R5. Assuming the following grid resistors R6 and R7 to be each 1M $\Omega$ , values of 5000pF and 3-3M $\Omega$  will attenuate frequencies below 25c/s and will be satisfactory with an output transformer of high primary inductance.

Low values of transformer primary inductance will need correspondingly lower and higher values, respectively, of capacitors and resistors. Values of 2000pF and 10M $\Omega$  will be found adequate for transformers of poor quality in terms of primary inductance. Low frequency instability ("motor-boating") in amplifiers containing poor-quality output transformers may be eliminated by incorporating these networks.

## COMPONENT VALUES FOR FIG. B-1

### STABILISING NETWORKS

#### VALVES

V1 } B65/6SN7  
V2 }

#### RESISTORS

(20%, 0.25W unless otherwise shown)

R1 1-10k $\Omega$

R2 15k $\Omega$  0.5W } matched to 5%

R3 15k $\Omega$  0.5W }

R4 3.3M $\Omega$  } see text above

R5 3.3M $\Omega$  }

R6 1M $\Omega$

R7 1M $\Omega$

#### CAPACITORS

C1 500-5000pF (see text above)

C2 0.05 $\mu$ F

C3 0.05 $\mu$ F

C4 5000pF

C5 5000pF

## CHAPTER 10

### PRE-AMPLIFIERS AND TONE CONTROL

This chapter discusses some of the requirements of pre-amplifiers for use with the power amplifiers described in earlier chapters and includes details of two complete pre-amplifier circuits containing record and tape equalisation and tone controls.

**9-1. The Purpose of a Pre-Amplifier.**—This can be summed up, within the context of this book, in three requirements: (a) the amplification of small signals, of the order of millivolts, to a level suitable for operating a power amplifier without adding hum and other noise; (b) frequency “equalisation” of the output from gramophone records, tape, etc.; (c) the provision of variable tone controls, which, to satisfy present-day demands requires at least bass and treble cut and bass lift.

These three requirements are dealt with in more detail in the following paragraphs.

**Amplification.**—A comprehensive pre-amplifier of the type described later in this chapter must be suitable for use with microphones, tape playback heads and low-sensitivity pickups.

The output voltage of a typical crystal microphone of the diaphragm type connected directly to the grid of the first valve is about 2mV for a sound pressure of 1 dyne/cm<sup>2</sup>. This is roughly equivalent to loud speech a foot or so from the microphone and normal conversation will give about 0.5mV. Signal magnitudes of this order will also be obtained at the input valve grid from a moving-coil or ribbon microphone connected via an appropriate step-up transformer. With such low level input voltages the hum and noise level at the grid must not exceed about 1.5 $\mu$ V for a signal-to-noise ratio approaching 50db (300:1), which is an acceptable standard for high-fidelity equipment.

The output from tape playback heads varies from about 1.5mV, at 1000c/s, for the cheapest kinds up to about 10mV for the more expensive heads. Obviously, the greater the output, the better will be the signal-to-noise ratio obtained with any given tape. Magnetic tape is recorded at constant peak flux density so that the head output falls with decreasing frequency at the rate of 6 db per octave. Consequently, the output at 50c/s will be about 24db less than that at 1000c/s, that is, about 0.1mV for a low-output head. It follows that, with this type of head, a signal-to-noise ratio of 40db (100:1) will necessitate a noise level at the grid no higher than about 1 $\mu$ V.

An input stage which meets the requirements of high signal-to-noise ratio with adequate gain can be built by using the Z729, a valve especially designed for this type of application. The pre-amplifier circuits of figs. 9-2 and 9-3 both contain a tape playback amplifier of this kind, the valve being V1 in each case. Certain precautions must be observed, particularly with the wiring of grid, heater and cathode circuits and in the use of suitable components in order to take full advantage of the performance of the valve itself.


The grid and cathode wiring must be compact and direct in order to minimise the electrostatic pick-up of hum and the magnetic loop formed by the input terminal, grid, cathode and earth must be as small as possible. A single earth connection is essential and this should be close to the input socket, which should be screened. The part of the chassis containing the input stage may, with advantage, be totally enclosed with metal screens. The heater wiring should consist of a twisted pair and should be kept well clear of the grid circuit. The heaters should be wired up from the supply end starting with the output valve and finishing with the input stage. In this way, the heater supply wires running to the first stage will carry only the current drawn by the input valve and the electro-magnetic field about these wires will be at a minimum.

Care in the choice of components used in the input stage is necessary and all capacitors should be of high quality if they are not to introduce noise due to variable insulation resistance etc. Resistors should be of the high-stability type in order to minimise noise produced by thermal agitation (Johnson noise) and other effects. The valve socket should be of unloaded plastics or ceramic material and should preferably contain a central screening boss, this being earthed together with contacts 2 and 7 which connect to the internal screening system of the Z729 valve.

**Equalisation.** As explained above, the frequency characteristic of the output from a tape playback head or gramophone pickup is not level and a suitable equalising network must be incorporated in the pre-amplifier in order to reproduce these signals with a flat frequency characteristic.

Such a network introduces a loss in amplification which must be made good and it is convenient to combine it with a valve amplifier, the amplification of which makes up for the insertion loss of the correcting circuit. By arranging the equalising network in the form of a negative feedback loop in this amplifier stage, valve distortion is reduced to a minimum.

The equalisation basically comprises bass boost of 10-15db at 50c/s for record reproduction and 24db or more at 50c/s for tape playback. This is achieved by suitably attenuating the higher frequencies, full gain being obtained only at the lowest frequencies. Fig. 9-1 is a simplified diagram of this circuit,

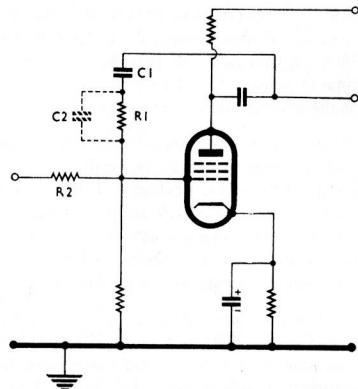

**Fig. 9-1.** Simplified circuit showing how the response of an amplifier may be modified by placing a suitable network in the feedback loop.

the corresponding valves in the full circuits of figs. 9-2 and 9-3 being V2 in each case.

The feedback loop can be made to modify the response of this amplifier stage in any desired way by introducing into it a suitable frequency selective network. To obtain bass boost, this network consists basically of C1 and R1 in fig. 9-1 and the values of these components are chosen so that the impedance of C1 becomes greater than the resistance of R1 at a particular low frequency. The amount of feedback thus becomes smaller with decreasing frequency and the amplification increases, giving bass boost. For record reproduction, high frequency de-emphasis is introduced by the addition of C2.

In the complete pre-amplifiers, a suitable equalising network is automatically switched into circuit for each type of input source. For radio reproduction the gain of this stage is reduced uniformly at all frequencies, by introducing pure resistance into the feedback loop, to suit the larger input signal from a radio tuner.

As stated above, when the signal is from a tape playback head considerable attenuation of all but the lower frequencies is necessary for true equalisation and an additional stage must precede the equalising amplifier. The requirements for this input stage were discussed under "Amplification" on page 97.

An additional amplifier is not necessary for record equalisation because the required bass boost is considerably less and, normally, the input signal is larger.

The gain control follows the equalising stage as the signal level is such that any noise generated by a potentiometer may be neglected.

**Tone Control.**—Having achieved a signal of uniform frequency characteristics from any of the input sources by the action of the equalising stage, tone controls can be introduced for adjusting the balance and frequency range to suit listening conditions, programme quality and personal taste.

Both pre-amplifier designs incorporate tone controls, those in the circuit of fig. 9-3 being somewhat more comprehensive. The details of the tone control circuits are given in the descriptions of the pre-amplifiers below.

**9-2. Pre-Amplifier Circuit No. 1.**—The circuit diagram of this pre-amplifier is given in fig. 9-2. This design, the simpler of the two described in this chapter, utilises three Z729 valves and is suitable for feeding an amplifier requiring about 0.5V input. V1 is the tape playback amplifier and the sensitivity at the input socket of this stage is 1mV. The output of this stage and the input signals from the pickup and radio sockets are connected to the grid of V2 via the input selector switch S1A.

### COMPONENT VALUES FOR FIG. 9-2 PRE-AMPLIFIER CIRCUIT NO. 1

#### G.E.C. VALVES

V1 }  
V2 } Z729  
V3 }

R28 100kΩ  
R29 470kΩ  
R30 220kΩ 5%  
R31 1MΩ Log.  
R32 22kΩ 5%  
R33 22kΩ

#### RESISTORS

(10%, 0.25W unless otherwise shown)

\*R1 2.2MΩ 5%  
\*R2 5% } See page 102  
\*R3 5% }  
\*R4 3.3kΩ 5%  
\*R5 47kΩ 5%  
\*R6 220kΩ 5%  
\*R7 470kΩ 5%  
\*R8 220kΩ 5%  
\*R9 1MΩ 5%  
\*R10 470kΩ 5%  
R11 220kΩ  
R12 220kΩ  
R13 47kΩ  
R14 470kΩ  
R15 1MΩ  
R16 10MΩ  
R17 1MΩ  
R18 10MΩ  
R19 220kΩ  
R20 22MΩ  
\*R21 3.3kΩ 5%  
\*R22 220kΩ 5%  
\*R23 1MΩ 5%  
R24 500kΩ Log.  
R25 2.2MΩ  
R26 47kΩ  
R27 1.5kΩ 5%

\*High Stability

#### CAPACITORS

C1 16μF 350V  
C2 25μF 25V  
C3 0.1μF  
C4 0.05μF  
C5 33pF 10%  
C6 330pF 10%  
C7 68pF 10%  
C8 220pF 10%  
C9 470pF 10%  
C10 25μF 25V  
C11 0.1μF  
C12 0.05μF  
C13 8μF 350V  
C14 0.005μF  
C15 25μF 25V  
C16 0.1μF  
C17 0.05μF  
C18 2000pF 10%  
C19 0.02μF  
C20 16μF 450V  
C21 1000pF 10%  
C22 2000pF 10%  
C23 0.05μF

#### SWITCHES

S1 2-pole 4-way m.b.b.  
S2 1-pole 4-way m.b.b.

Switch S1 has four positions and in clockwise order these are : radio (100mV), pickup 78 r.p.m. (20mV), pickup 33 r.p.m. (20mV) and tape playback (1mV). S1A selects the required input signal and S1B automatically inserts into the feedback loop of V2 the appropriate equalising network.

The values of resistors R2 and R3, in the pickup input circuit, will depend upon the type of pickup used. Variation of the value of R2 will alter the load impedance presented to the pickup and variation of R3 will alter the input sensitivity to suit the output of the pickup. With many moving iron (variable reluctance) pickups R2 should be open-circuited ( $R2 = \infty \Omega$ ) and R3 short-circuited ( $R3 = 0 \Omega$ ) but if this results in full output with the volume control at less than half-travel, a suitable value of R3 will attenuate the pickup output and so prevent distortion in V2. A value of  $47k\Omega$  for R2 will provide a suitable load impedance for most magnetic pickups. The output of a crystal pickup can be made similar to a magnetic type by making R2  $100k\Omega$  and reducing its output by making R3  $1M\Omega$  (see fig. 9-8).

The tone control stage consists of V3 and its associated bass and treble controls R31 and S2. Both controls utilise conventional circuits, the bass control being a potentiometer which boosts the bass as the slider travels away from the centre in one direction and cuts as it is moved in the opposite direction, with the centre position giving a level response. The treble control consists of a four-position switch giving three degrees of cut and one level position.

The input sockets and the first valve should be grouped together with a single earth connection to the chassis. The earth connection from the equalising stage (V2) should be returned to the same point. The two selector switches may be of the bakelite wafer type, with make-before-break contacts.

The grid coupling capacitors are chosen so that their combined effect produces attenuation below 30c/s in order to reduce rumble.

As the output impedance of the pre-amplifier is about  $22k\Omega$ , up to four feet of ordinary screened wire or up to twenty feet of coaxial cable may be connected without high frequency loss.

This pre-amplifier may be used as a substitute for the built-in tone controls of the 912-PLUS amplifier when the flexibility of a separate control unit is preferred. The h.t. feed for the pre-amplifier is taken from the junction of C11 and R28 in fig. 3-3 (page 28). The output of the pre-amplifier, fed into the first grid of V2 in fig. 3-3, provides the correct input signal for the 912-PLUS.

**9-3. Pre-Amplifier Circuit No. 2.**—This pre-amplifier was designed for use with the KT88 50W amplifier described in Chapter 5\* but it may be used to feed any power amplifier requiring an input signal of 0.5V. It is very suitable for use with the G.E.C. 912-PLUS amplifier as a substitute for the built-in tone control stage. Details of its use with the 912-PLUS are given in Chapter 3.

The pre-amplifier circuit is illustrated in fig. 9-3 and it is designed to operate from a gramophone pickup, a tape playback head (for which a separate input stage, V1, is used), a high-impedance microphone and a radio tuner. Choice of any of these inputs is provided by a selector switch which also automatically

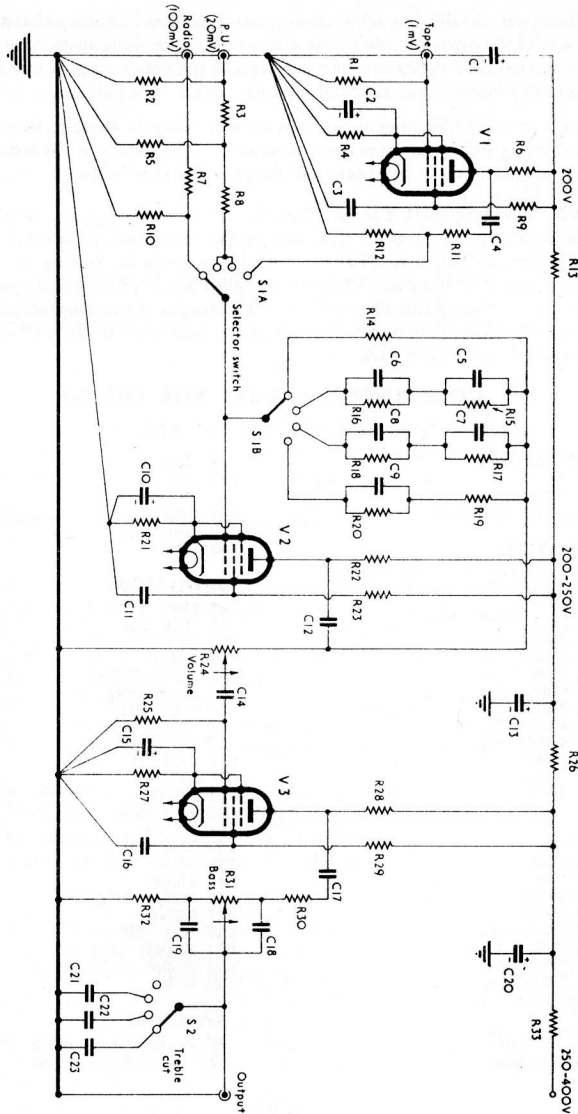


Fig. 9-2. Circuit of Pre-Amplifier No. 1. All switches are shown fully anticlockwise and the arrows at the potentiometers indicate clockwise rotation.

modifies the pre-amplifier sensitivity and equalisation to suit the selected input source.

The six positions of the input selector switch are given in clockwise order by the table below which also shows the input sensitivity, input impedance and an indication of the equalisation obtained at each position.

Switch Position	Sensitivity*	Input Impedance	Frequency Correction	
			Bass Boost at	Treble Cut at
Radio ... ..	0.2V	470kΩ	—	—
78 r.p.m. Records ... ..	14mV	50kΩ	400c/s	6kc/s
British Microgroove Records ... ..	10mV	50kΩ	500c/s	3kc/s
American Standard Records ... ..	12mV	50kΩ	600c/s	2kc/s
Tape (7½ in/s) ... ..	4mV	220kΩ	1.5kc/s	—
Microphone (high impedance) ... ..	1mV	1.1MΩ	—	—

\*Input for 0.5V r.m.s. output from pre-amplifier.

**Equalisation Networks.**—The equalising stage is of the negative feedback type as described in Sect. 9-1 above and it utilises another G.E.C. Z729 low noise pentode. The various equalisation characteristics are illustrated in figs. 9-4 to 9-7. The tape playback equalisation is based on the recommendation that tape recorded at 7½ in/s should be played back with a time constant of 100μs and that treble loss in recording should be offset by pre-emphasis.† This is equivalent to a bass boost of 6db per octave from 1500c/s and is obtained by C10 and R19 in the feedback loop. At other tape speeds, these components should be as follows :

Speed	Time Constant	C10	R19
3½ in/s	200μs	1000pF	220kΩ
15 in/s	35μs	150-220pF	220kΩ

The selector switch may be provided with more positions if these additional equalisation characteristics are required to be built into the pre-amplifier. It should be noted that R17 is connected across C10 merely to eliminate switch clicks and does not form part of the equalisation circuit.

In general, it is undesirable to compensate for tape losses by treble boosting on playback as this will accentuate tape hiss. However, a degree of treble boost

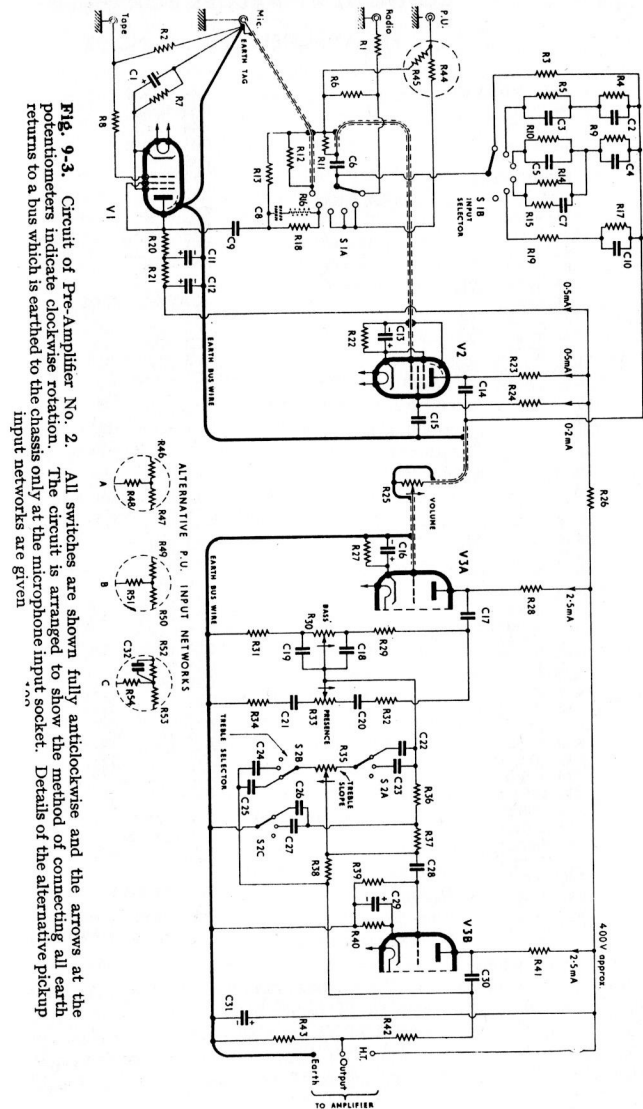


Fig. 9-3. Circuit of Pre-Amplifier No. 2. All switches are shown fully anticlockwise and the arrows at the potentiometers indicate clockwise rotation. The circuit is arranged to show the method of connecting all earth returns to a bus which is earthed to the chassis only at the microphone input socket. Details of the alternative pickup input networks are given.



## COMPONENT VALUES FOR FIG. 9-3

### PRE-AMPLIFIER CIRCUIT NO. 2

#### G.E.C. VALVES

V1 Z729  
V2 Z729  
V3 B329/12AU7

#### RESISTORS

(10%, 0.25W unless otherwise shown)

R1 470kΩ  
\*R2 220kΩ 5%  
R3 470kΩ  
R4 10MΩ  
R5 820kΩ 5%  
R6 470kΩ  
\*R7 3.3kΩ 5%  
\*R8 10kΩ 5%  
R9 22MΩ  
R10 1.5MΩ 5%  
R11 2.2MΩ  
R12 2.2MΩ  
R13 1MΩ  
R14 1MΩ 5%  
R15 10kΩ  
R16 100kΩ (see page 107)  
R17 22MΩ  
R18 220kΩ  
R19 220kΩ  
\*R20 100kΩ 5%  
R21 22kΩ  
\*R22 3.3kΩ 5%  
\*R23 220kΩ 5%  
R24 1MΩ  
R25 500kΩ Log.  
R26 22kΩ  
R27 1kΩ  
R28 47kΩ  
R29 100kΩ  
R30 1MΩ Log.  
R31 10kΩ  
R32 47kΩ  
R33 500kΩ Log.  
R34 3.3kΩ  
R35 2MΩ Log.  
R36 100kΩ  
R37 100kΩ  
R38 680kΩ  
R39 1.5MΩ  
R40 1kΩ  
R41 47kΩ  
R42 10kΩ  
R43 150kΩ

R44 100kΩ  
R45 100kΩ  
R46 47kΩ  
R47 100kΩ  
R48 10kΩ  
R49 100kΩ  
R50 100kΩ  
R51 2.2kΩ  
R52 100kΩ  
R53 100kΩ  
R54 2.2kΩ

#### CAPACITORS

C1 25μF 12V  
C2 470pF 5%  
C3 33pF 5%  
C4 220pF 5%  
C5 33pF 5%  
C6 0.02μF  
C7 82pF 5%  
C8 100pF 5%  
C9 0.05μF  
C10 470pF 5%  
C11 8μF 450V  
C12 8μF 450V  
C13 25μF 12V  
C14 0.05μF  
C15 0.1μF  
C16 25μF 12V  
C17 0.1μF  
C18 5000pF 5%  
C19 0.04μF  
C20 1000pF 5%  
C21 0.02μF  
C22 680pF 5%  
C23 330pF 5%  
C24 100pF 5%  
C25 47pF 5%  
C26 470pF 5%  
C27 220pF 5%  
C28 0.002μF  
C29 25μF 12V  
C30 0.02μF  
C31 8μF 500V  
C32 220pF 5%

#### SWITCHES

S1 2-pole 6-way m.b.b.  
S2 3-pole 3-way m.b.b.

#### \*High stability

on playback is an advantage when the playback head itself is responsible for high frequency loss. A suitable amount of treble boost may be introduced by shunting R18, in the output circuit of V1, by C8 as shown in broken line in fig. 9-3. C8 should not exceed 100pF for 7½in/s and the effect of this capacitor is shown in fig. 9-4. The limiting resistor R16, in series with C8, should be 100kΩ.

Gramophone record equalisation is obtained in the same way as for tape, e.g. for American Standard records bass boost is provided by C4 and R14 with treble roll-off or de-emphasis by C7. Resistor R15, in series with C7, is inserted to limit feedback at very high frequencies which would cause instability. It was not found necessary to include this resistor in the other feedback paths. Resistors R4, R9 and R17 eliminate switch clicks and, in addition, limit the bass boost.

The record equalisation networks are designed for use with moving coil or moving iron (variable reluctance) pickups which give an output voltage proportional to recorded velocity. The pre-amplifier input impedance and sensitivity are suitable for use with most pickups of this type, which give a maximum output of 10mV to 50mV. When using a pickup of different characteristics, such as a crystal type, the input network must be appropriately modified. Normally, with the optimum load impedance of about 1MΩ, a good quality crystal pickup gives an approximately flat response from a record, in other words it provides its own bass boost to compensate the falling bass characteristic of the record. However, it has been found that a very smooth frequency response, extending up to the high frequency peak, can be obtained if a crystal pickup is connected to a load lower than the optimum. The resulting response is very similar to that of a velocity pickup and it is then corrected by the equalising network as for a magnetic type. Fig. 9-8 shows the response of a Collaro "Studio P" crystal pickup to a British microgroove test record plotted with a normal load of 1MΩ and with a load of 100kΩ. The fall in bass in the latter curve is caused by the internal capacitance of the pickup and the result closely resembles the British Microgroove recording characteristic, also shown in the graph.

As the output of a crystal pickup is considerably greater than that of a magnetic type, the input network of the pre-amplifier must be modified to attenuate the signal to the level required for correct operation of V2. Inset in fig. 9-3 are three alternative pickup input networks. Inset "A" is for use with magnetic pickups having a maximum output greater than 50mV. Maximum output is here defined as that given by a recorded velocity of 7cm/s and corresponds to high modulation on an average record. Inset "B" is for use with good-quality popular crystal pickups, such as the Collaro "Studio P." Inset "C" is for best quality crystal pickups having a less pronounced treble peak, such as the Collaro "Transcription."

**Tone Control.**—The gain control is inserted after the equalising stage and the various tone controls are built into a following double triode amplifier stage. V3A feeds two frequency selective potential divider circuits which provide variable control of bass and "presence." Logarithmic controls are used for R30 and R33 in order to give a level response when their sliders are at the mid position. The effect of these controls is shown in fig. 9-9.

The presence control alters the level of all frequencies above about 1500c/s. It therefore alters the balance between high and low frequencies so that an increase in presence, i.e. turning the control clockwise from mid-travel thereby lifting the high frequencies, gives a more "forward" quality. This is as though the listener were to move nearer the orchestra or speaker. Conversely,

anticlockwise rotation from the mid position simulates the effect of an orchestra receding and approximates to listening from the back of the concert hall.

The signal passes from these controls to V3B, to which is applied negative feedback, the loop consisting of R38 in conjunction with isolating resistors R36 and R37. Associated with these resistors are the treble boost capacitors C22 and C23, and the treble cut capacitors C24 to C27. Appropriate combinations of these capacitors are switched into circuit by the treble selector S2 and the response curve so obtained may be modified by the treble slope potentiometer R35. This control is inoperative when S2 is at the level position but an overall cut or *boost* is obtained by rotating the potentiometer when S2 is at either of the *cut* positions. The variation in treble response with rotation of the treble slope control at both "cut" positions of S2 is shown in figs. 9-10 and 9-11.

If a normal logarithmic potentiometer is used for treble slope, it will attenuate the treble as it is rotated clockwise. An inverse log potentiometer must be used to obtain increasing treble with clockwise rotation if this is preferred.

**Rumble Filter.**—Within the feedback loop of V3B are two coupling networks, C28 R39 and C30 R42 R43, each having a time constant of 3ms. As a result, low frequencies are attenuated and positive feedback is introduced below 50c/s, the combined effect giving a flat response down to 30c/s below which the response falls steeply down to about 15c/s, when the coupling capacitors elsewhere in the pre-amplifier provide additional attenuation.

The effect of the rumble filter is shown in fig. 9-9. If it is desired to attenuate below 40c/s instead of 30c/s, R39 and R43 should be made 1M $\Omega$  and 100k $\Omega$  respectively.

**Output Impedance.**—The negative feedback on V3B maintains a low output impedance over the greater part of the frequency range of the pre-amplifier. The actual value is approximately equal to R42, i.e. about 10k $\Omega$  and up to five feet of ordinary screened wire may be connected to the output terminal with no deterioration in high frequency performance.

**Construction.**—The circuit diagram, fig. 9-3, is drawn in a way that illustrates the method of earthing all the components to a continuous earth wire which is connected to the chassis only at a tag mounted on the microphone input socket.

The two switches are bakelite wafer types, S1 having each pole on a separate wafer whilst S2 is a single wafer 3-pole 3-way switch.

The pre-amplifier earth bus wire should be connected to the main amplifier chassis only by a single wire which may conveniently be the screening braid on the signal output cable. This cable itself may be one of the elements of a multi-core cable between pre-amplifier and main amplifier.

The precautions to be taken in constructing a pre-amplifier of this type are described on page 11 and if these are borne in mind and the circuit diagram intelligently interpreted, the construction should be quite straightforward. The original article, mentioned on page 102, in which constructional information and illustrations were given, should be consulted by those with little experience in building this type of equipment.

**Power Supplies.**—The pre-amplifier was designed to draw its power supplies from the KT88 50W amplifier (Chapter 5) and the h.t. line smoothing is the minimum necessary for adequate ripple attenuation in order to maintain the h.t. as high as possible. When using the KT88 amplifier, no added h.t. decoupling is necessary because the stabilising circuits in that amplifier and its good push-pull balance contribute greatly to its freedom from instability at low frequencies. It is possible that further smoothing and/or decoupling may be required when using the pre-amplifier with a different type of power amplifier. This point is covered in Chapter 3 when using the pre-amplifier as part of the G.E.C. 912-PLUS (see page 33).

**Performance.**—The KT88 50W amplifier requires 0.5V r.m.s. input for maximum output and the pre-amplifier will supply this signal at a harmonic distortion comparable with that of the KT88 amplifier. The distortion does not increase with variation of the controls but to avoid the possibility of distortion in the equalising stage (V2) all input levels must be adjusted so that the full output of 50W from the KT88 amplifier (corresponding to 0.5V pre-amplifier output) is not obtained until the pre-amplifier gain control is beyond the centre of its travel. Given this condition, an increase in input signal level of nearly 20db can be accepted with no increase in distortion.

The signal-to-noise ratio of the complete equipment comprising the pre-amplifier and the KT88 amplifier is -76db relative to 50W with the gain control at minimum and the tone controls set for level response. With the gain control at maximum and the input sockets short-circuited to earth, the following signal-to-noise ratios were obtained at each position of the input selector on a prototype: Radio: -69db; A.S. Records: -63db; Tape: -52db; Microphone: -55db.

## CHAPTER 11

### HIGH-FIDELITY AUDIO AMPLIFIER

Class AB<sub>1</sub>; Power Output, 15 Watts

#### Circuit Description

This high-fidelity audio power amplifier can deliver 15 watts of rms output power with less than 0.4 per cent total harmonic distortion and less than 1.5 per cent intermodulation distortion. The frequency response of the amplifier is flat within  $\pm 0.5$  dB from 20 Hz to 60 kHz, and the sensitivity is such that the rated output of 15 watts is obtained for an input of 1.2 volts rms. The total hum and noise, with the input shorted, is 84 dB below 15 watts. The circuit operates from a 117-volt ac power line. The transformer-coupled ac input power is converted to dc operating power for the amplifier stages by the 5BC3 full-wave rectifier. Heater power for the amplifier tubes and the rectifier are obtained from the 6.3-volt and 5-volt secondary windings, respectively, on the rectifier power transformer ( $T_2$ ).


A high-gain pentode voltage amplifier is used as the input stage for the audio power amplifier. The output of this stage is direct-coupled to the control grid of a triode split-load type of phase inverter. The use of direct coupling between these stages minimizes phase shift and, consequently, increases the amount of inverse feedback that may be used without danger of low-frequency instability. A low-noise 7199 tube, which contains a high-gain pentode section and a medium- $\mu$  triode section in one envelope, fulfills the active-component requirement for both the pentode input stage and the triode phase inverter. Potentiometer  $R_1$  in the input circuit of the 7199 pentode section is the volume control for the amplifier.

The plate and cathode outputs of the phase inverter, which are equal in amplitude and opposite in phase, are used to drive a pair of pentode-connected 6973 beam-power tubes used

in a class AB<sub>1</sub> push-pull output stage. The 6973 output tubes are biased for class AB<sub>1</sub> operation by the fixed negative voltage applied to the control-grid circuit from the rectifier circuit. Fixed bias is used because a class AB amplifier provides highest efficiency and least distortion for this bias method.

Transformer  $T_1$  couples the audio-amplifier output to the speaker. The taps on the secondary of this transformer match the plate-to-plate impedance of the output stage to the voice-coil impedance of an 8- or 16-ohm speaker. Negative feedback of 19.5 dB is coupled from the secondary of the output transformer (speaker voice coil) to the cathode of the input stage to reduce distortion and to improve circuit stability.

Fixed-bias operation of the output stage requires that the power supply provide very good voltage regulation because the plate current of the 6973 tubes varies considerably with the signal level. The conventional choke-input type of power supply provides the required regulation. The fixed bias for the output stage is obtained from one-half the high-voltage secondary winding of power transformer  $T_2$  through a capacitance-resistance voltage divider and the 20-milliampere, 135-volt selenium rectifier. Potentiometer  $R_2$  connected across the 6.3-volt secondary winding of transformer  $T_2$  provides a hum balance adjustment for the audio power amplifier. The wiper arm of this potentiometer is connected to the junction of a resistive voltage divider across the output of the power supply. The resulting positive bias voltage applied to the tube heaters minimizes heater-to-cathode leakage and substantially reduces hum.

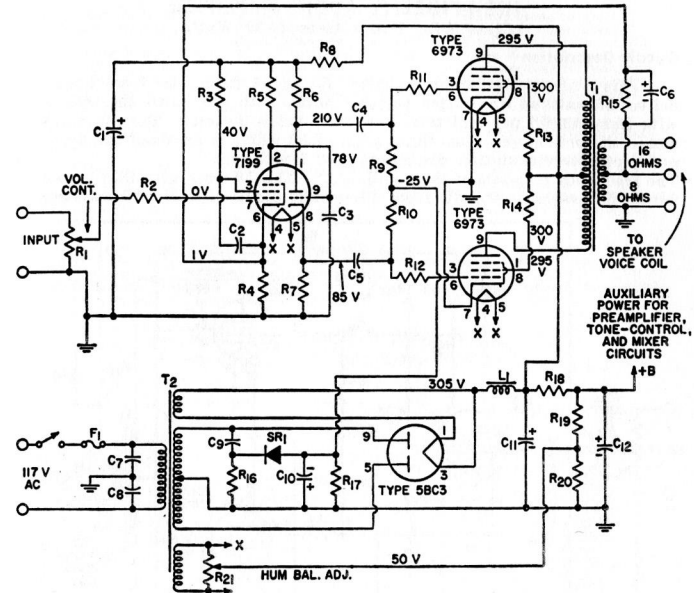

#### Parts List

$C_1=40 \mu\text{F}$ , electrolytic, 450 V.	$R_1=$ Volume control, potentiometer, 1 megohm	$R_{21}=$ Hum balance adjustment, potentiometer, 100 ohms, 0.5 watt
$C_2, C_4, C_5=0.25 \mu\text{F}$ , paper, 400 V.	$R_2=10000$ ohms, 0.5 watt	$SR_1=$ Selenium rectifier, 20 mA, 135 volts rms
$C_3=3.3 \text{ pF}$ , ceramic or mica, 600 V.	$R_3=0.82$ megohm, 0.5 watt	$T_1=$ Output transformer, (having 8-ohm tap for feedback connection) to match impedance of voice coil to 6600-ohm plate-to-plate tube load; 50 watts; frequency response, 10 to 60000 Hz; Stancor A-8056 or equiv.
$C_6=150 \text{ pF}$ , ceramic or mica, 400 V.	$R_4=320$ ohms, 0.5 watt	$T_2=$ Power transformer, 360-0-360 volts rms, 120 mA; 6.3 V., 3.5 A; 5 V., 3 A; Stancor 8410 or equiv. (see Note 1)
$C_7, C_8=0.05 \mu\text{F}$ , paper, 400 V.	$R_5=0.22$ megohm, 0.5 watt	
$C_9=0.02 \mu\text{F}$ , paper 600 V, 400 V.	$R_6, R_7=15000$ ohm $\pm 5$ per cent, 2 watts	
$C_{10}=100 \mu\text{F}$ , electrolytic, 50 V.	$R_8=3900$ ohms, 2 watts	
$C_{11}=80 \mu\text{F}$ , electrolytic, 450 V.	$R_9, R_{10}=0.1$ megohm, 0.5 watt	
$C_{12}=40 \mu\text{F}$ , electrolytic, 450 V.	$R_{11}, R_{12}=1000$ ohms, 0.5 watt	
$F_1=$ Fuse, 3 amperes	$R_{13}, R_{14}=100$ ohms, 0.5 watt	
$L_1=$ Choke, 3 H, 160 mA, dc resistance 75 ohms or less, Triad C-18X or equiv.	$R_{15}=8200$ ohms, 0.5 watt	
	$R_{16}=16000$ ohms, 1 watt	
	$R_{17}=6000$ ohms, 0.5 watt	
	$R_{18}=4700$ ohms, 2 watts	
	$R_{19}=0.27$ megohm, 1 watt	
	$R_{20}=47000$ ohms, 0.5 watt	

Notes: 1. For stereo operation from a single power supply, the power transformer  $T_2$  must be replaced by one that has a higher current rating. A Stancor Type 6315 or equivalent (370-0-370 volt rms, 275 mA) is recommended.  
2. If the amplifier oscillates or "motorboats," reverse ground and feedback connections in secondary of output transformer  $T_1$ .

# CHAPTER 12

## HIGH-FIDELITY AUDIO AMPLIFIER


Class AB<sub>1</sub>; Power Output, 30 Watts

### Circuit Description

This audio power amplifier can deliver 30 watts of rms output power with less than 0.7 per cent total harmonic distortion and less than 1.5 per cent intermodulation distortion. The frequency response of the amplifier is flat within  $\pm 0.5$  dB from 15

Hz to 40 kHz. The total hum and noise, with the input shorted, is 85 dB below 30 watts. The rated output of 30 watts is obtained for an input of 1 volt rms.

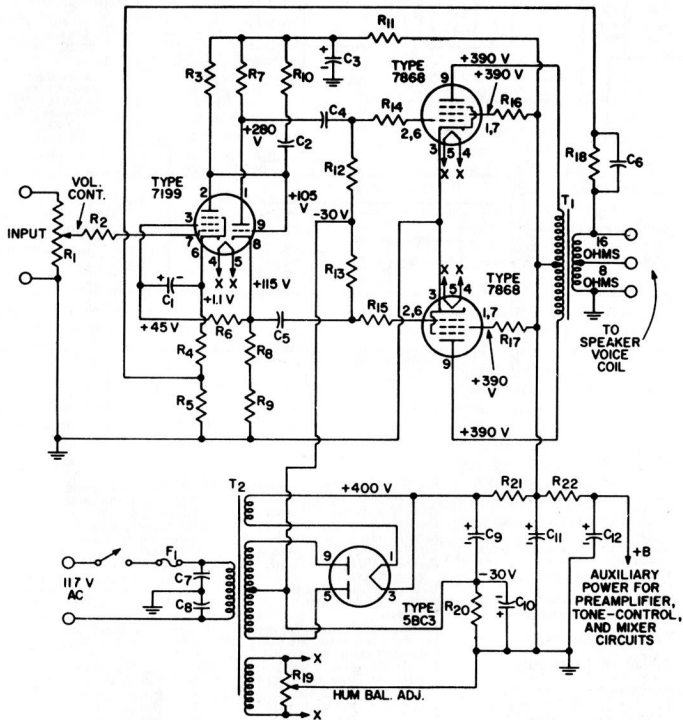The 30-watt amplifier is essentially identical to the 15-watt ampli-



fier (circuit 26-9) except that it uses 7868 beam power tubes in the output stage to develop the higher audio power output and uses a resistive network in the negative leg of the power supply, rather than a separate

rectifier, to supply the fixed-bias voltage for the output stage. A potentiometer ( $R_{19}$ ) connected across the 6.3-volt heater winding also provides the hum balance adjustment for the 30-watt amplifier.

### Parts List

$C_1=25 \mu\text{F}$ , electrolytic, 50 V  
 $C_2=22 \text{ pF}$ , ceramic or mica, 600 V  
 $C_3=80 \mu\text{F}$ , electrolytic, 450 V  
 $C_4, C_5=0.25 \mu\text{F}$ , paper, 600 V  
 $C_6=0.01 \mu\text{F}$ , paper, 600 V  
 $C_7, C_8=0.05 \mu\text{F}$ , paper, 600 V  
 $C_9, C_{11}=40 \mu\text{F}$ , electrolytic, 500 V  
 $C_{10}=100 \mu\text{F}$ , electrolytic, 50 V  
 $C_{12}=20 \mu\text{F}$ , electrolytic, 450 V  
 $F_1=$ Fuse, 3 amperes, 150 V  
 $R_1=$ Volume control, potentiometer, 1 megohm  
 $R_2=10000$  ohms, 0.5 watt  
 $R_3=0.22$  megohm, 0.5 watt


$R_4=820$  ohms, 0.5 watt  
 $R_5=10$  ohms, 0.5 watt  
 $R_6=0.18$  megohm, 0.5 watt  
 $R_7, R_8=15000$  ohms  $\pm 5$  per cent, 2 watts  
 $R_9=1000$  ohms, 0.5 watt  
 $R_{10}=22000$  ohms, 0.5 watt  
 $R_{11}=2000$  ohms, 2 watts  
 $R_{12}, R_{13}=0.1$  megohm, 0.5 watt  
 $R_{14}, R_{15}=1000$  ohms, 0.5 watt  
 $R_{16}, R_{17}=56$  ohms, 0.5 watt  
 $R_{18}=270$  ohms, 0.5 watt  
 $R_{19}=$ Hum balance adjustment, potentiometer, 100 ohms, 0.5 watt  
 $R_{20}=220$  ohms, 100 watts

$R_{21}=50$  ohms, 10 watts  
 $R_{22}=10000$  ohms, 2 watts  
 $T_1=$ Output transformer (having 16-ohm tap for feedback connection) for matching impedance of voice coil to 6600-ohm plate-to-plate tube load; 50 watts; frequency response, 10 to 50000 Hz; Stancor A-8056 or equiv.  
 $T_2=$ Power transformer, 375-0-375 volts rms, 160 mA; 5.3 V., 5 A; 5 V., 3 A; Thordarson type T22R33 or equivalent (see Note 1).

Notes: 1. For stereo operation from a single power supply, the power transformer  $T_2$  must be replaced by one that has a higher current rating. A Stancor Type 6315 or equivalent (370-0-370 volts rms, 275 mA) is recommended.  
 2. If amplifier oscillates or "motorboats," reverse ground and feedback connections in secondary of output transformer  $T_1$ .
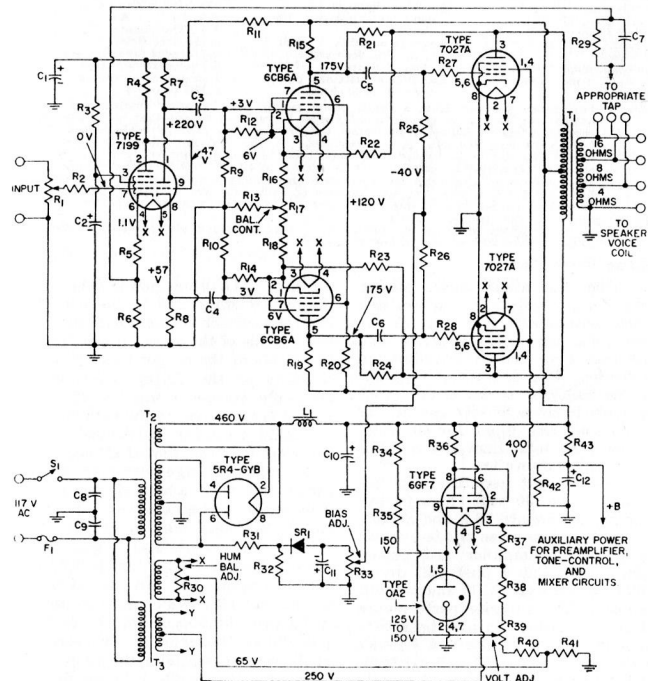
## HIGH-FIDELITY AUDIO AMPLIFIER

Class AB<sub>1</sub>; Power Output, 50 Watts



## CHAPTER 13

### TWO-CHANNEL AUDIO MIXER

Voltage Gain from Each Grid of 6EU7 to Output is Approximately 20

#### Preliminary Adjustments

The following adjustments should be made before operation:


- (1) With rectifier out of socket, adjust Bias Adj.  $R_{80}$  for -40 volts between the wiper arm and grid bus.
- (2) With speaker connected, adjust Screen-Grid Voltage Adj.  $R_{30}$  for 400 volts between pin 3 of 6GF7 and ground bus.
- (3) With input shorted, adjust Hum Bal. Adj.  $R_{30}$  for minimum hum from speaker.
- (4) With input open and Vol. Cont. set for maximum volume, adjust Bal. Cont.  $R_{17}$  for minimum hum from speaker.

#### Parts List

$C_1, C_2=40 \mu\text{F}$ , electrolytic, 450 V  
 $C_3, C_4=0.02 \mu\text{F}$ , paper, 400 V  
 $C_5, C_6=1 \mu\text{F}$ , paper, 400 V  
 $C_7=0.002 \mu\text{F}$  to 4-ohm tap;  
 0.0015  $\mu\text{F}$  to 8-ohm tap; or,  
 0.001  $\mu\text{F}$  to 16-ohm tap;  
 paper, 400 V  
 $C_8, C_9=0.05 \mu\text{F}$ , paper, 600 V  
 $C_{10}=20 \mu\text{F}$ , electrolytic, 450 V  
 $F_1$ =Fuse, 5 amperes  
 $L_1$ =Choke, 8 H, 250 mA, dc resistance 60 ohms, or less  
 $R_1$ =Volume control, potentiometer, 0.5 megohm  
 $R_2=4700$  ohms, 0.5 watt  
 $R_3=0.82$  megohm, 0.5 watt  
 $R_4=0.22$  megohm, 0.5 watt  
 $R_5=820$  ohms, 0.5 watt  
 $R_6=10$  ohms, 0.5 watt  
 $R_7, R_8=15000$  ohms, 2 watts  
 $R_9, R_{10}=1.5$  megohms, 0.5 watt  
 $R_{11}=33000$  ohms, 2 watts  
 $R_{12}, R_{13}=1.3$  megohms, 0.5 watt

$R_{14}=47$  ohms, 0.5 watt  
 $R_{15}, R_{16}=0.15$  megohm, 0.5 watt  
 $R_{17}, R_{18}=390$  ohms, 0.5 watt  
 $R_{19}=A.C.$  balance control, potentiometer, 500 ohms  
 $R_{20}=0.15$  megohm, 1 watt  
 $R_{21}, R_{22}=0.33$  megohm, 1 watt  
 $R_{23}, R_{24}=0.12$  megohm, 2 watts  
 $R_{25}, R_{26}=0.1$  megohm, 0.5 watt  
 $R_{27}, R_{28}=47000$  ohms, 0.5 watt  
 $R_{29}=600$  ohms to 4-ohm tap; 820 ohms to 8-ohm tap; or, 1200 ohms to 16-ohm tap; 0.5 watt  
 $R_{30}$ =Hum balance adjustment, potentiometer, 100 ohms  
 $R_{31}=0.12$  megohm, 5 watts  
 $R_{32}, R_{33}, R_{34}=33000$  ohms, 2 watts  
 $R_{35}$ =Bias adjustment, potentiometer 5000 ohms,

$R_{36}=10000$  ohms, 1 watt  
 $R_{37}$ =Screen-grid voltage adjustment, potentiometer, 2500 ohms, 2 watts  
 $R_{38}=15000$  ohms, 2 watts  
 $R_{39}=12000$  ohms, 2 watts  
 $R_{40}=0.22$  megohm, 2 watts  
 $R_{41}=2200$  ohms, 2 watts  
 $S_{R1}$ =Selenium rectifier, 20 mA, 135 volts rms  
 $T_1$ =Output transformer for matching impedance of voice coil to 5000-ohm plate-to-plate tube load; 50 watts; frequency response, 10 to 50000 Hz; United Transformer Corp. LS55 or equiv.  
 $T_2$ =Power transformer, 600-0-600 volts rms, 200 mA, 6.3 V, 5 A; 5 V., 3 A; Thoradson 22R36 or equiv. (see Note 1)  
 $T_3$ =Filament transformer, 6.3 volts, center tapped, 1 ampere; Thoradson 21F08 or equiv.

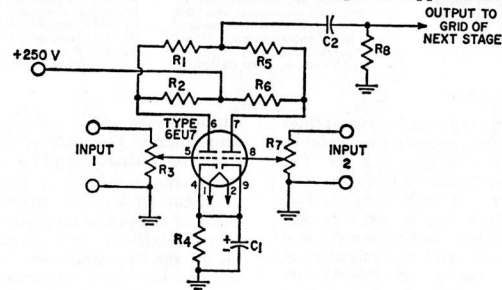

#### Parts List

$C_1=10 \mu\text{F}$ , electrolytic, 25 V  
 $C_2=0.05 \mu\text{F}$ , paper, 400 V  
 $R_1, R_2, R_3=1$  megohm,

0.5 watt  
 $R_4, R_5=0.1$  megohm,  
 0.5 watt

$R_6, R_7$ =Potentiometers, 0.1 megohm, audio taper  
 $R_8=1200$  ohms, 0.5 watt

#### Circuit Description

This high-fidelity mixer circuit can be used to combine audio-frequency program material from two sources. Each signal channel consists of a one-stage voltage amplifier using one section of a 6EU7 low-noise twin-triode. Each section of the mixer can provide a voltage gain

of about 20, and can handle an input signal of about 0.2 volt rms without overloading. The dc plate supply of +250 volts (nominal value) for the mixer stages can usually be obtained from an auxiliary tap on the power supply for the audio power amplifiers.

- Notes: 1. For stereo operation from a single power supply, the following changes are required: (a) The power transformer  $T_2$  must be replaced by one that has a higher current rating; a Unit Transformer Corporation Type H-93 or equivalent (600-0-600 volts rms, 300 mA) is recommended. (b) The 6000-ohm Bias Adj. potentiometer  $R_{30}$  should be replaced by two 10000-ohm potentiometers (one for each channel) connected in parallel. (c) A second 5R4-GYB rectifier tube should be connected in parallel with the one used for monaural operation. (Connect the corresponding sections of the other tube; do not use separate tubes for each section of the rectifier circuit.)
2. If the amplifier oscillates or "motorboats," reverse ground and feedback connections in secondary of output transformer  $T_1$ .


#### Circuit Description

This four-stage audio power amplifier can deliver 50 watts of rms power output with less than 0.1 per cent total harmonic distortion and less than 1 per cent intermodulation distortion. The frequency response of the amplifier is flat within  $\pm 0.5$  dB from 10 Hz to 50 kHz. Sensitivity is 0.4 volt rms input for 50 watts output. The total hum and noise is 70 dB below 50 watts.

The 50-watt amplifier, like the 15-watt and 30-watt high-fidelity amplifiers (circuits 26-9 and 26-10), uses a 7199 low-noise triode-pentode as an input amplifier and phase-splitter, but has a push-pull driver stage, which uses 6CB6 sharp-cutoff pentodes. The superior performance of this amplifier can also be attributed, in part, to the use of a 450-volt plate supply and a 400-volt electronically regulated grid-No. 2 supply

for the 7027A beam power tubes in the output stage and to the use of inverse-feedback loops from the plates to the grids of the output tubes, from the plates of the output tubes to the cathodes of the driver tubes, and from the voice-coil winding of the output transformer to the cathode of the input amplifier. Additional features are the operation of all heaters at a positive voltage with respect to ground and use of a balancing adjustment circuit ( $R_{30}$ ) in the heater-supply circuit to minimize hum, a grid-No. 2 voltage adjustment ( $R_{35}$ ), a grid-No. 1 bias adjustment ( $R_{31}$ ) for the 7027A output tubes, and an ac-balance adjustment ( $R_{15}$ ) which may be used to balance the outputs of the push-pull stages. Operation of the 50-watt amplifier is essentially the same as that of the 15- and 30-watt amplifiers.
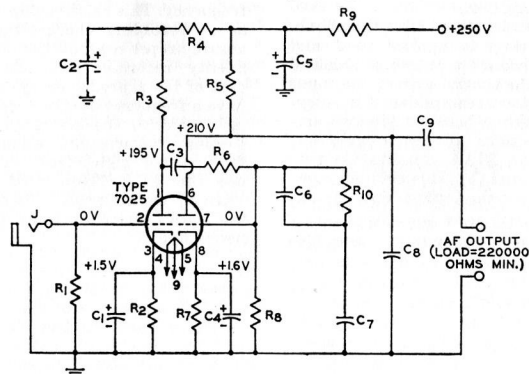
#### PREAMPLIFIER FOR MAGNETIC PHONOGRAPH PICKUP With RIAA Equalization



Sensitivity=3 millivolts rms input for output of 0.55 volt at frequency of 1000 Hz.



## Parts List

C<sub>1</sub>, C<sub>1</sub>=25  $\mu$ F, electrolytic, 25 V  
 C<sub>2</sub>, C<sub>2</sub>=20  $\mu$ F, electrolytic, 450 V  
 C<sub>3</sub>=0.1  $\mu$ F, paper, 600 V  
 C<sub>4</sub>=0.0033  $\mu$ F  $\pm$ 5 per cent, paper, 600 V  
 C<sub>5</sub>=0.01  $\mu$ F  $\pm$ 5 per cent, paper, 600 V

C<sub>6</sub>=180 pF  $\pm$ 5 per cent, ceramic or mica, 500 V (includes capacitance of output cable)  
 C<sub>7</sub>=0.22  $\mu$ F, ceramic, 500 V  
 J=Input connector, shielded, for high-impedance magnetic phono pickup (10 mV output, approx.)  
 R<sub>1</sub>=Value depends on type

of magnetic pickup used. Follow pickup manufacturer's recommendations  
 R<sub>2</sub>, R<sub>2</sub>=2700 ohms, 0.5 watt  
 R<sub>3</sub>, R<sub>3</sub>=0.1 megohm, 0.5 watt  
 R<sub>4</sub>=39000 ohms, 0.5 watt  
 R<sub>5</sub>=0.47 megohm, 0.5 watt  
 R<sub>6</sub>=0.65 megohm, 0.5 watt  
 R<sub>7</sub>=15000 ohms, 1 watt  
 R<sub>10</sub>=22000 ohms, 0.5 watt

## Circuit Description


This two-stage audio preamplifier is intended for use with high-fidelity magnetic phonograph pickups. The two amplifier stages provide an overall circuit gain of approximately 150. The 7025 twin triode used in the circuit features exceptionally low hum and noise and is designed especially for use in high-fidelity circuits that operate at low signal levels. The preamplifier is ideally suited for use as the low-level input stage for audio power amplifiers such as the 50-watt unit, circuit 27-11. For use with audio power amplifiers such as the 15- and 30-watt units, circuits 27-9 and 27-10, which require higher input signals, another low-level amplifier (e.g., the tone-control amplifier, circuit 27-20) must be inserted between the preamplifier and the power amplifier to obtain the full rated output. The heater and dc operating power required for the preamplifier can usually be obtained from the power-supply circuit for the power amplifier.

The audio signal from the phonograph pickup is applied to J and coupled through a length of shielded cable to the control grid of the input stage of the preamplifier. The interstage coupling between the two amplifier sections of the preamplifier includes an RIAA equalization network (R<sub>10</sub> and C<sub>6</sub>). This network compensates for the Orthophonic recording characteristic\* introduced into a record disc by the manufacturer. The

output from the preamplifier is coupled from the plate of the second stage by output coupling capacitor C<sub>8</sub> to the input of a tone-control amplifier (if used) or directly to the input of the power amplifier. Because of its relatively high output impedance, the preamplifier is recommended for use in systems in which the preamplifier is mounted on the same chassis as the power amplifier and/or tone-control amplifier. The preamplifier may be used at distances up to 6 feet from the following amplifier provided that the capacitance of capacitor C<sub>6</sub> is reduced approximately 30 picofarads for each foot of shielded cable used for the audio-frequency connection between the preamplifier and the following amplifier.

\* To achieve wide frequency and dynamic ranges, manufacturers of commercial recordings use equipment which introduces a non-uniform relationship between amplitude and frequency. This relationship is known as a "recording characteristic." To assure proper reproduction of a high-fidelity recording, therefore, some part of the reproducing system must have a frequency-response characteristic which is the inverse of the recording characteristic. Most manufacturers of high-fidelity recordings use the RCA "New Orthophonic" (RIAA) characteristic for discs and the NARTB characteristic for magnetic tape.
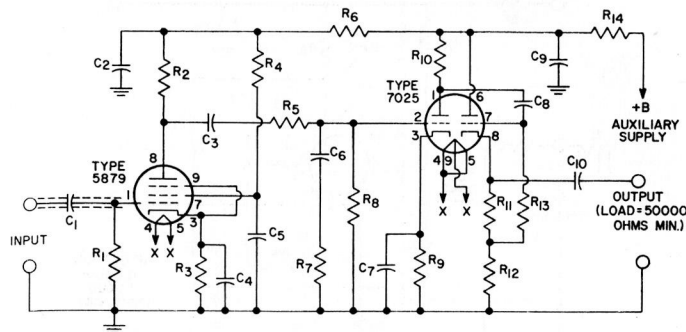
## HIGH-FIDELITY PREAMPLIFIER FOR TAPE-HEAD PICKUP With NARTB Equalization



Sensitivity=3 millivolts rms input for output of 0.55 volt at frequency of 1000 Hz.

## Parts List

C<sub>1</sub>=0.047  $\mu$ F, ceramic, 400 V  
 C<sub>2</sub>=40  $\mu$ F, electrolytic, 450 V  
 C<sub>3</sub>=0.1  $\mu$ F, ceramic, 400 V  
 C<sub>4</sub>=25  $\mu$ F, electrolytic, 25 V  
 C<sub>5</sub>=0.22  $\mu$ F, ceramic, 400 V  
 C<sub>6</sub>=0.015  $\mu$ F, ceramic, 400 V  
 C<sub>7</sub>=25  $\mu$ F, electrolytic, 25 V

C<sub>8</sub>=0.22  $\mu$ F, ceramic, 400 V  
 C<sub>9</sub>=40  $\mu$ F, electrolytic, 450 V  
 C<sub>10</sub>=0.47  $\mu$ F, ceramic, 400 V  
 R<sub>1</sub>=1 megohm, 0.5 watt  
 R<sub>2</sub>=0.1 megohm, 0.5 watt  
 R<sub>3</sub>=1000 ohms, 0.5 watt  
 R<sub>4</sub>=0.47 megohm, 0.5 watt  
 R<sub>5</sub>=0.22 megohm, 0.5 watt  
 R<sub>6</sub>=22000 ohms, 0.5 watt

R<sub>7</sub>=3300 ohms, 0.5 watt  
 R<sub>8</sub>=3.3 megohms, 0.5 watt  
 R<sub>9</sub>=1500 ohms, 0.5 watt  
 R<sub>10</sub>=0.1 megohm, 0.5 watt  
 R<sub>11</sub>=1500 ohms, 0.5 watt  
 R<sub>12</sub>=15000 ohms, 0.5 watt  
 R<sub>13</sub>=0.47 megohm, 0.5 watt  
 R<sub>14</sub>=4700 ohms, 0.5 watt

## Circuit Description

This three-stage preamplifier provides the amplification necessary to increase the output from a tape-head pickup to the level required to drive an audio power amplifier. The circuit uses a 5879 low-noise sharp-cutoff pentode in a high-gain input voltage amplifier, one section of a 7025 twin triode in a second voltage amplifier, and the other section of the 7025 in a cathode-follower output stage. Because of the low-impedance cathode-follower output circuit, the preamplifier may be installed at distances up to 50 feet from the following stage (tone-control or power amplifier) without adverse effect upon its frequency-response characteristics. The preamplifier is intended for use as the low-level input stages for an audio power amplifier, such as the 50-watt unit (circuit 27-11) or, when followed by another low-level amplifier (e.g., the tone-control amplifier, circuit 27-20), the 15- or 30-watt unit (circuit 27-9 or 27-10).


The heater and dc operating power for the preamplifier can usually be obtained from the power supply for the power amplifier.

The preamplifier provides an over-all circuit gain of 180. An input of 3 millivolts rms at the input terminals, is amplified by the pentode and triode voltage amplifiers to develop an output of approximately 0.55 volt rms at the cathode of the cathode-follower output stage. The interstage coupling between the pentode and triode voltage amplifiers equalizes the playback frequency response of the preamplifier to compensate for the NARTB recording characteristic introduced into the magnetic tape by the manufacturer. (See footnote for circuit 27-16.) The output of the preamplifier is coupled by capacitor C<sub>8</sub> to the input of the audio power amplifier or to the input of an intermediate tone-control amplifier.



## PREAMPLIFIER FOR CERAMIC PHONOGRAPH PICKUP

Cathode Follower (Low-Impedance) Output

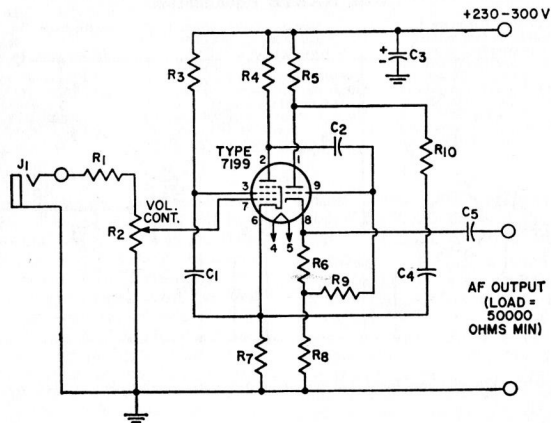

### Parts List

$C_1=0.1 \mu\text{F}$ , paper, 400 V  
 $C_2=0.01 \mu\text{F}$ , paper, 400 V  
 $C_3=20 \mu\text{F}$ , electrolytic, 400 V  
 $C_4=0.25 \mu\text{F}$ , paper, 400 V  
 $C_5=0.22 \mu\text{F}$ , paper, 600 V  
 $J_1=$ Input connector, shielded,

for high-impedance ceramic phono pickup (0.5-volt output)  
 $R_1=1.8$  megohms, 0.5 watt  
 $R_2=$ Volume control, potentiometer, 0.5 megohm, audio taper

$R_3=0.82$  megohm, 0.5 watt  
 $R_4=0.22$  megohm, 0.5 watt  
 $R_5, R_6=4,000$  ohms, 0.5 watt  
 $R_7=4700$  ohms, 0.5 watt  
 $R_8=1000$  ohms, 0.5 watt  
 $R_9=1$  megohm, 0.5 watt  
 $R_{10}=1800$  ohms, 0.5 watt


### Circuit Description

This two-stage preamplifier is intended for use with a high-impedance ceramic phono pickup. The circuit features a cathode-follower (low-impedance) output which makes it possible to install the preamplifier at distances up to 50 feet from the succeeding stage (tone-control or power amplifier). The preamplifier operates from a dc supply of 230 to 300 volts and a heater supply of 6.3 volts. These voltages can usually be obtained from the power supply for the power amplifier in the audio system.

The preamplifier uses a 7199 triode-pentode in a high-gain pentode input stage and a triode cathode-follower output stage. These stages provide the amplification necessary to increase the output from a crystal phono pickup, applied at  $J_1$ , to the level required to drive an audio power amplifier. The output of the preamplifier, coupled from the cathode of the 7199 triode section, may be applied directly to the power amplifier, or to an intermediate tone-control amplifier.
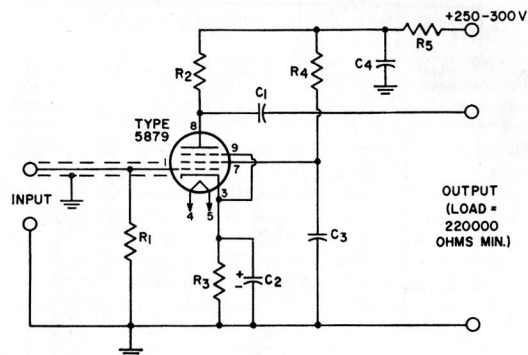
## LOW-DISTORTION PREAMPLIFIER

For Low-Output, High-Impedance Microphones



Sensitivity=3 millivolts rms input for output of 220 millivolts.

### Parts List

$C_1=0.047 \mu\text{F}$ , paper, 400 V  
 $C_2=25 \mu\text{F}$ , electrolytic, 25 V  
 $C_3=0.22 \mu\text{F}$ , paper, 400 V  
 $C_4=40 \mu\text{F}$ , electrolytic,

450 V  
 $R_1=2.2$  megohms, 0.5 watt  
 $R_2=0.1$  megohm, 0.5 watt

$R_3=1000$  ohms, 0.5 watt  
 $R_4=0.47$  megohm, 0.5 watt  
 $R_5=22000$  ohms, 0.5 watt

### Circuit Description

This single-stage preamplifier is intended for use with a high-fidelity, high-impedance crystal or dynamic microphone. The circuit uses a 5879 low-noise sharp-cutoff pentode in a conventional amplifier circuit that has a high-impedance output, a voltage gain of approximately 70, and a flat frequency response over the

audio range. Because of its high output impedance, the preamplifier should be mounted on the same chassis as the power amplifier and tone-control amplifier (if used). Heater and dc power for the circuit can be obtained from the power supply for the audio power amplifier.

## BASS AND TREBLE TONE-CONTROL AMPLIFIER

### Parts List

$C_1=0.047 \mu\text{F}$ , paper, 400 V  
 $C_2, C_3=20 \mu\text{F}$ , electrolytic, 450 V  
 $C_4=0.1 \mu\text{F}$ , paper, 400 V  
 $C_5=0.0022 \mu\text{F}$ , paper, 400 V  
 $C_6=0.022 \mu\text{F}$ , paper, 400 V  
 $C_7=0.22 \mu\text{F}$ , paper, 400 V  
 $C_8=220$  pF, ceramic or mica,

500 V  
 $C_9=0.0022 \mu\text{F}$ , paper, 400 V  
 $R_1=0.47$  megohm, 0.5 watt  
 $R_2=1500$  ohms, 0.5 watt  
 $R_3, R_{11}=15000$  ohms, 0.5 watt  
 $R_4=22000$  ohms, 0.5 watt  
 $R_5, R_7, R_{10}=0.1$  megohm, 0.5 watt


$R_6=1000$  ohms, 0.5 watt  
 $R_8=$ Bass control, potentiometer, 1 megohm, audio taper  
 $R_9=10000$  ohms, 0.5 watt  
 $R_{12}=$ Treble control, potentiometer, 1 megohm, audio taper

### Circuit Description

This high-fidelity tone-control amplifier uses a 6EU7 low-noise twin triode in a two-stage amplifier cascade that consists of an input cathode follower connected to a triode voltage amplifier through a frequency-sensitive (tone-control) interstage cou-

pling network. The bass and treble controls in the coupling network can be adjusted to provide up to 16 dB of boost or attenuation (cut) at 30 Hz and at 15 kHz. With the bass and treble controls set at the mid-range positions, the amplifier provides an

## MULLARD TWENTY-WATT AMPLIFIER

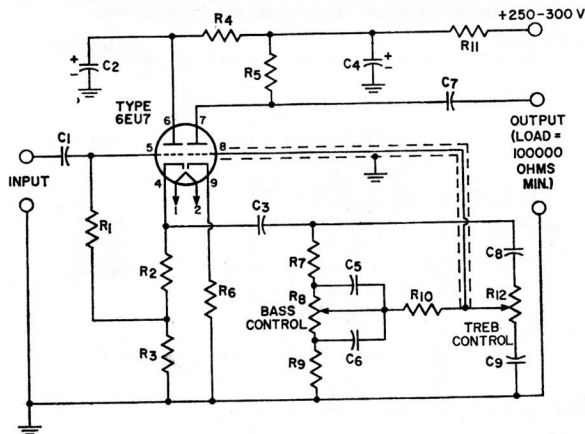

Sensitivity=0.5 volt rms input for output of 1.25 volts with controls set for flat response.

over-all voltage gain of approximately 2.5, and its frequency response is flat within  $\pm 1$ dB from 30 Hz to 15 kHz.

The tone-control amplifier is designed for use immediately ahead of an audio power amplifier, such as the 15-, 30-, or 50-watt unit (circuit 27-9, 27-10, or 27-11, respectively). Operating power for the tone-control circuit can usually be obtained from the power supply for the power amplifier. For operating convenience,

the volume control on the power amplifier may be physically located on the tone-control chassis. In this case, it is advisable to insert a 1-megohm resistor in place of the volume control on the power amplifier. If partial compensation for the reduced high- and low-frequency sensitivity of the ear at low volume levels is desired, the volume-control potentiometer may be replaced by a loudness-control potentiometer.

The circuit is designed to give the highest standard of sound reproduction when used in association with a suitable pre-amplifier, a high-grade pick-up head and a good-quality loud-speaker system.

Two Mullard output pentodes, type EL34, rated at 25W anode dissipation, form the output stage of the circuit. These are connected in a push-pull arrangement with distributed loading, and give a reserve of output power of 20W with a level of harmonic distortion less than 0.05%. The intermediate stage consists of a cathode-coupled, phase-splitting amplifier using the Mullard double triode, type ECC83. This stage is preceded by a high-gain voltage amplifier incorporating the Mullard low-noise pentode, type EF86. Direct coupling is used between the voltage amplifier and phase splitter to minimise low-frequency phase shifts.

The main feedback loop includes the whole circuit, the feedback voltage being derived from the secondary winding of the output transformer and being injected in the cathode circuit of the EF86. The amount of feedback applied around the circuit is 30dB, but in spite of this high level, the stability of the circuit is good and the sensitivity is 220mV for the rated output power. The level of hum and noise is 89dB below the rated 20W.

The rectifier used in the power-supply stage is the Mullard full-wave rectifier, type GZ34. This provides sufficient current for the amplifier (about 145mA) and also for a pre-amplifier and radio tuner if (about 40mA) required.

## CIRCUIT DESCRIPTION

## Input Stage


The EF86 input stage of the circuit of Fig. 1 provides high-gain voltage amplification, the stage gain being approximately 120 times. High-stability, cracked-carbon resistors are used in the anode, screen-grid and cathode circuits, and they give an appreciable improvement in the measured level of background noise compared with ordinary carbon resistors.

The stage is coupled directly to the input of the phase splitter. The purpose of this is to minimise low-frequency phase shift in the amplifier and to improve the low-frequency stability when negative feedback is applied. A CR network (C1, R3) connected across the anode load produces an advance in phase and thus improves the high-frequency stability of the amplifier.

## Intermediate Stage

The second stage of the circuit uses a Mullard double triode, type ECC83, and fulfils the combined function of phase splitter and driver

Fig. 1—Circuit diagram of 20W amplifier

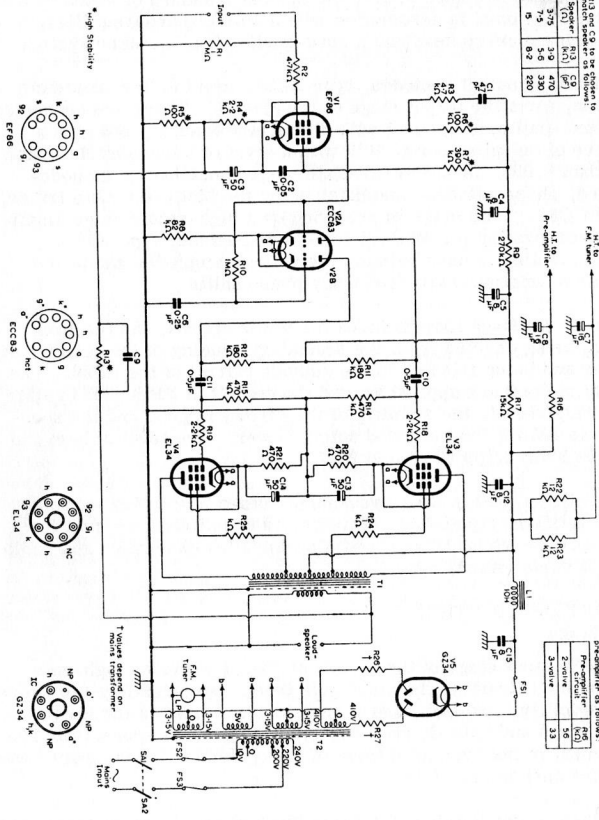

20W AMPLIFIER

LIST OF COMPONENTS 20W AMPLIFIER

Circuit ref.	Value	Tolerance (±%)	Rating (W)	Circuit ref.	Value	Description	Rating (V)
R1	1 MΩ	20		C1	47 pF	silvered mica <sup>3</sup>	350
R2	4-7kΩ	20		C2	0-05 μF	paper	12
R3	4-7kΩ	10		C3	50 μF	electrolytic	450
R4	2-2kΩ	10		C4	8 μF	electrolytic	450
R5	100 Ω	5		C5	8 μF	electrolytic	350
R6	100 kΩ	10		C6	0-25 μF	paper	450
R7	390 kΩ	10		C7	16 μF	electrolytic	500
R8	82 kΩ	10		C8	8 μF	electrolytic	350
R9	270 kΩ	10		C9	470 pF	silvered mica <sup>4</sup>	500
R10	1 MΩ	20		C10	330 pF	silvered mica <sup>4</sup>	500
R11	180 kΩ	10		C11	220 pF	silvered mica <sup>4</sup>	50
R12	180 kΩ	10		C12	0-5 μF	paper	50
R13	3-9kΩ	5		C13	8 μF	paper	50
R14	5-6kΩ	5		C14	50 μF	electrolytic	50
R15	8-2kΩ	5		C15	50 μF	electrolytic	500
R16	470 kΩ	10					
R17	470 kΩ	10					
R18	33 kΩ	10					
R19	15 kΩ	20					
R20	2-2kΩ	20					
R21	470 Ω	5					
R22	470 Ω	5					
R23	12 kΩ	20					
R24	12 kΩ	20					
R25	1 kΩ	10					
R26	1 kΩ	10					

1. High stability, cracked carbon
2. Matched to within 5%
3. Preferably matched to within 5%
4. Wire wound

Circuit ref.	Value	Rating (W)	Circuit ref.	Value	Description	Rating (V)
C1	47 pF		C9	470 pF	silvered mica <sup>4</sup>	350
C2	0-05 μF		C10	330 pF	silvered mica <sup>4</sup>	500
C3	50 μF		C11	220 pF	silvered mica <sup>4</sup>	50
C4	8 μF		C12	0-5 μF	paper	50
C5	8 μF		C13	8 μF	paper	50
C6	0-25 μF		C14	50 μF	electrolytic	50
C7	16 μF		C15	50 μF	electrolytic	500
C8	8 μF					

5. Tolerance, ±10%
6. Tolerance, ±5%

**Valves**  
Mullard EF86, ECC83, EL34 (two), GZ34

**Valveholders**  
B9A (noval) nylon-loaded, with screening skirt (for EF86) McMurdo, XM9/AU, Skirt 95  
B9A (noval) nylon-loaded (for ECC83), McMurdo XM9/AU  
B8-O (International octal) (three, for EL34s and GZ34), McMurdo B8/U

amplifier. The phase splitter is a cathode-coupled circuit which enables a high degree of balance to be obtained in the push-pull drive signal applied to the output stage.

With the high line voltage available, the required drive voltage for an output power of 20W is obtained with a low level (0.4%) of distortion. The anode load resistors R11 and R12 should be matched to within 5%, R12 having the higher value for optimum operation. Optimum balance is obtained when the effective anode loads differ by 3%. The grid resistors R14 and R15 of the output stage should also be close-tolerance components because they also form part of the anode load of the driver stage. High-frequency balance will be determined largely by the wiring layout because equality of shunt capacitances is required. Low-frequency balance is controlled by the time constant C6R10 in the grid circuits of the triode sections, and the time constant chosen in Fig. 1 will give adequate balance down to very low frequencies.

A disadvantage of the cathode-coupled form of phase splitter is that the effective voltage gain is about half that attainable with one section of the valve used as a normal voltage amplifier. However, as the mutual conductance of the ECC83 is high (100), the effective gain of the cathode-coupled circuit is still about 25 times.

#### Output Stage

The main feature of interest in the output stage is the use of two EL34s with partial screen-grid (or distributed) loading, the screen grids being fed from tappings on the primary winding of the output transformer. The best practical operating conditions are achieved with this type of output stage when about 20% of the primary winding is common to the anode and screen-grid circuit.

The anode-to-anode loading of the output stage is 7k ohms and, with a line voltage of 440V at the centre-tap of the primary winding of the output transformer, the combined anode and screen-grid dissipation of the output valves is 28W per valve. With the particular screen-grid-to-anode load ratio used, it has been found that improved linearity is obtained at power levels above 15W when resistors of the order of 1k ohm are inserted in the screen-grid supply circuits. The slight reduction in peak power-handling capacity which results is not significant in practice.

Separate cathode-biasing resistors are used in the output stage to limit the out-of-balance direct current in the primary winding of the output transformer. The use of other balancing arrangements has not been thought necessary although it is likely that some improvement in performance, particularly at low frequencies, would result from the use of d.c. balancing. It is necessary in this type of output stage for the cathodes to be bypassed to earth even if a shared cathode resistor is used. Consequently, a low-frequency time constant in the cathode circuit cannot be eliminated when automatic biasing is used.

### 20W AMPLIFIER

#### Miscellaneous

Mains input plug, 3-way, Bulgin, P340  
Mains switch, 2-pole, Bulgin, S300  
Mains selector, Clix, CTSP/2  
H.T. supply socket (f.m. tuner), 4-way, Elcom, S,04  
H.T. supply socket (pre-amplifier), 6-way, Elcom, S,06  
Fuseholders (three), Belling Lee, L356

#### Output Transformer T1

Primary Impedance:  
7kΩ for 20% screen-grid taps  
6.6kΩ for 45% screen-grid taps

#### Mains Transformer T2

Primary: 10-0-200-220-240V  
Secondaries: H.T., 410-0-410V, 180mA  
3.15-0-3.15V, 4A  
3.15-0-3.15V, 2.5A  
0.5V, 3A

#### Smoothing Choke L1

Inductance: 10H at 180mA  
Resistance: 200Ω

### Commercial Components

Manufacturer	Output Transformer Type No.	20% Taps	43% Taps	Mains Transformer Type No.	Choke Type No.
Colne	03070	03070	03069	03068	03071
Elden	486A	486	486	477	478
Gardens	AS.7034	AS.7034	AS.7034	RS.3175	CS.5142
Gilson	W.O.1342	W.O.1342	W.O.866	W.O.775	W.O.1340
Hinchley	1532	1377	1377	W.O.917	W.O.1341
Parneko	P2913	P2913	P2913	1441	1528
Partridge	—	P2913	P2913	P2646	P463
Savage	—	P2913	P2913	P3877	C10/180
Wynall	W1900C	W1900C	P6878	P6877	—
			4B14	4B32-1	W1585
			W1552C	W1584	

## NEGATIVE FEEDBACK

Negative feedback is taken from the secondary winding of the output transformer to the cathode circuit of the input stage. In spite of the high level of feedback used (30dB), the circuit is completely stable under open-circuit conditions. At least 10dB more feedback (obtainable by reducing the value of R13) would be required to cause high-frequency instability. The most probable form of instability would be oscillation with capacitive loads, but this is most unlikely to occur even with very long loudspeaker leads.

## POWER SUPPLY

The power supply is conventional and uses a Mullard indirectly-heated, full-wave rectifier, type GZ34, in conjunction with a capacitive input filter. The values of the limiting resistors R26 and R27 will depend on the winding resistances of the mains transformer used.

Their purpose, when required, is normally one of voltage control only. Where a transformer with a very low winding resistance is used, a secondary voltage rated at 400-0-400V may be found adequate. The rating of the mains transformer is such that about 40mA may be drawn from the h. t. supply to feed a pre-amplifier circuit and tuner in addition to the normal current required (about 145mA) for the amplifier.

Extra decoupling will be needed for these ancillary supplies. The smoothing components R22, R23 and C7 can only be chosen when the type of tuner to be used is known. The values given in Fig. 1 would be suitable for typical current and voltage requirements of approximately 40mA and 200V. The components R16 and C8 depend on the pre-amplifier to be used. The values given in Fig. 1 refer to the 2- and 3-valve pre-amplifiers described in the next chapter.

## PERFORMANCE

At the full rated output, the distortion without feedback is well below 1% and with feedback is below 0.05%. The distortion rises to 0.1% for an output power of 27W. The loop-gain characteristic is such that a level of at least 20dB of feedback is maintained from 15c/s to 25c/s, and of at least 26dB down to 30c/s.

Measurements of intermodulation products were made in the prototype amplifier using a carrier frequency of 10kc/s and a modulating frequency of 40c/s. The ratio of modulating amplitude to carrier amplitude was 4:1. With the combined peak amplitudes of the mixed output at a level equivalent to the peak sine-wave amplitude at an r. m. s. power of 20W, the intermodulation products, expressed in r. m. s. terms, totalled 0.7% of the carrier amplitude. At an equivalent power of 27W, the products totalled 1% of the carrier ampli-

tude. The beat-note distortion between equal-amplitude signals at frequencies of 14 and 15kc/s is 0.25 and 0.3% at equivalent powers of 20 and 27W respectively, and between frequencies of 9 and 10kc/s it is 0.2 and 0.25% at the same equivalent powers.

## FREQUENCY RESPONSE

The frequency- and power-response characteristics show that, at an output of 1W, the characteristic is flat (+1dB) compared with the level at 1kc/s from 2c/s to 100kc/s and the power response characteristic is flat (+0.5dB) from 30c/s to 20kc/s.

It is important that adequate power-handling capacity is available at the low-frequency end of the audible range and this is determined chiefly by the characteristics of the output transformer.

## SENSITIVITY

The sensitivity of the amplifier measured at 1kc/s is 6.5mV for an output of 20W when no feedback is applied, and approximately 220mV with feedback, the loop gain being 30dB. The sensitivity, with feedback, at the overload point (27W) is approximately 300mV.

The level of background noise and hum is 89dB below 20W, measured with a source resistance of 10k ohms. This is equivalent to a signal of about 5.5 $\mu$ V at the input terminals. It is possible to increase the overall sensitivity of the amplifier by 6dB while still maintaining a low background level, a high loop gain and a good margin of stability, but various design requirements of associated pre-amplifier circuits (the need for a high signal-to-noise ratio, for example) render a higher sensitivity a doubtful advantage.

## PHASE SHIFT AND TRANSIENT RESPONSE

Emphasis has been laid in the amplifier on a good margin of stability and, consequently, the phase shift is held to a comparatively low level. The shift is only 20° at 20kc/s. Excellent response to transient signals is obtained, the rise time of the amplifier being of the order of 5 $\mu$  sec.

## OUTPUT IMPEDANCE

The output stage has a low inherent output impedance, and this is further lowered by the use of negative feedback. It is approximately 0.3 ohms with a 15 ohms load for an output of 20W at frequencies of 40c/s, 1kc/s and 20kc/s. This gives a damping factor of about 50.

CHAPTER 15  
MULLARD TWO- AND THREE-VALVE PRE-AMPLIFIERS

The circuits described in this chapter have been designed principally for use with the 20 watt amplifier previously described. They can, however, be used with any power amplifier which does not require an input signal greater than 250mV for full output. Input facilities are provided for magnetic and crystal pick-up heads, tape-recorder playback heads, radio tuner units and (in the 2 valve circuit) a microphone. An auxiliary input position is provided for ancillary equipment.

An additional output position, which is independent of the tone controls, is also provided with both circuits, enabling programmes to be taken to a tape amplifier while they are being fed from the normal output position to a power amplifier. Both the auxiliary input and the additional output positions have jack sockets which are situated at the front of the chassis.

All the input sockets in each circuit are connected to one switch which selects one input at a time. In both circuits this switch also short-circuits the unused sockets to earth, an arrangement which considerably reduces the amount of 'break-through' between channels. The positions of the switch, from left to right, are: Auxiliary, Radio, Tape, Microphone (in the 2 valve circuit only) Microgroove and 78 r. p. m.

The equalisation for disc recordings conforms to the present R.I.A.A. characteristics which has been adopted by most of the major recording companies. The tape-playback characteristic is intended for use with high-impedance heads when replaying pre-recorded tapes at a speed of  $7\frac{1}{2}$  inches per second.

The tone controls used in both circuits cover a wide range of frequencies and provide boost and cut for high and low frequencies. Switched high- and low-pass filter networks are included in the 3-valve circuit so that unwanted signals such as rumble and record scratch can be eliminated.

### CIRCUIT DESCRIPTIONS

Two Mullard high-gain pentodes, type EF86, are used in the 2-valve circuit of Fig. 2. In the 3-valve circuit shown in Fig. 3, two EF86s and a Mullard double triode, type ECC83, are used.

#### First Stage of 2- and 3-Valve Circuits

All the equalisation takes place in the first stage of both circuits, and is achieved by means of frequency-selective feedback between the anode and grid of the first EF86. This arrangement has been chosen because the grid-circuit impedance of the first stage should be low. A low

impedance at this grid lessens hum pick-up and reduces the effect of plugging-in external low-impedance circuits. Furthermore, the arrangement also results in low gain in the first stage. Hence, Miller effect between the anode and grid of the first EF86, which can be troublesome when high values of resistance are used in series with the grid, is reduced.

Series resistors are used in the input circuits so that the sensitivity and impedance of any channel can be adjusted accurately. The component values given in Figs. 2 and 3 are intended for sources encountered most frequently, but the sensitivity and impedance (the impedance of the input channels includes the grid impedance of the EF86 modified by the feedback components as well as the impedance of the input network) of each channel can be altered by changing the value of the appropriate series resistor.

#### Second Stage of 2-Valve Circuit

No feedback is used in the second stage of the 2-valve pre-amplifier. The full output from the anode of the second EF86 is taken to the passive tone-control network and an auxiliary output is taken from the junction of R20 and R21 to the programme-recording jack socket.

#### Second Stage of 3-Valve Circuit

The second stage of the 3-valve pre-amplifier circuit of Fig. 3 has a linear frequency-response characteristic and its gain is reduced by a small amount of negative feedback applied at the control grid by way of the resistor R23. The output of this stage is taken from the anode to the tone-control network, and also to the programme-recording output socket. Because of the negative feedback, the tone controls have very little effect on the frequency response at this anode.




Fig. 1—Output-attenuating networks for use with both pre-amplifiers

#### Third Stage of 3-Valve Circuit

The output stage of the 3-valve pre-amplifier is made up of the filter circuits. The low-pass filter is situated between the two sections of the ECC83, and is arranged on the switch SB. It incorporates a Mullard wound pot-core inductor, type WF1428, in a pi-type network. The high-pass filter is arranged on the switch SC and consists of two RC networks in a feedback loop around the second triode section of the valve.



Fig. 2—Circuit diagram of two-valve pre-amplifier

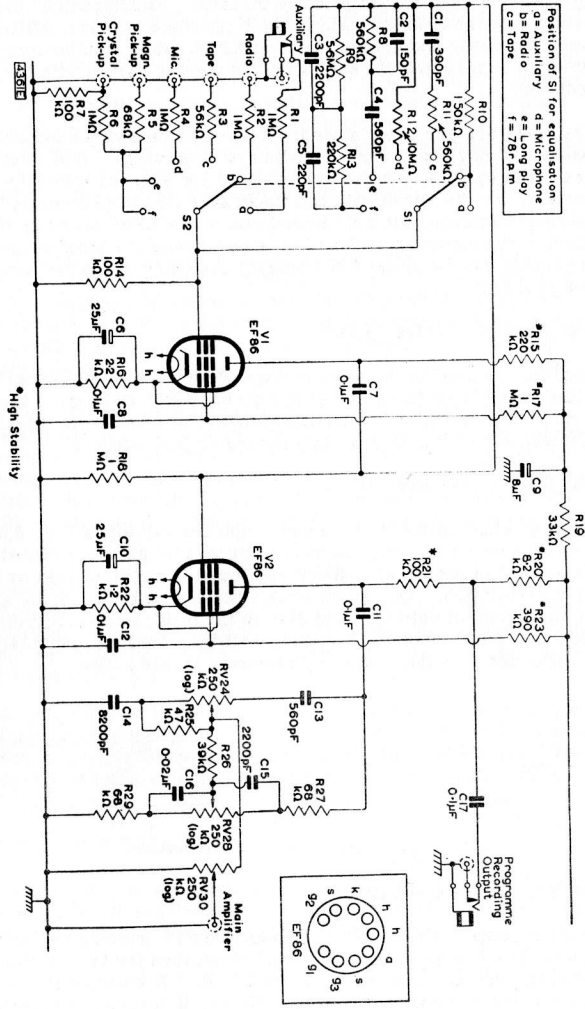

LIST OF COMPONENTS FOR TWO-VALVE PRE-AMPLIFIER

Resistors

Circuit ref.	Value	Tolerance (%)	Rating (W)
R1	M8	±1	1/4
R2	M8	±1	1/4
R3	M8	±1	1/4
R4	M8	±1	1/4
R5	M8	±1	1/4
R6	M8	±1	1/4
R7	M8	±1	1/4
R8	M8	±1	1/4
R9	M8	±1	1/4
R10	M8	±1	1/4
R11	M8	±1	1/4
R12	M8	±1	1/4
R13	M8	±1	1/4
R14	M8	±1	1/4
R15	M8	±1	1/4
R16	M8	±1	1/4
R17	M8	±1	1/4
R18	M8	±1	1/4
R19	M8	±1	1/4
R20	6.3k	±1	1/4
R21	350k	±1	1/4
R22	350k	±1	1/4
R23	350k	±1	1/4
R24	250k	±1	1/4
R25	250k	±1	1/4
R26	250k	±1	1/4
R27	6.0k	±1	1/4
R28	6.0k	±1	1/4
R29	6.0k	±1	1/4
R30	250k	±1	1/4
R31	250k	±1	1/4
R32	250k	±1	1/4
R33	350k	±1	1/4
R34	350k	±1	1/4
R35	350k	±1	1/4
R36	350k	±1	1/4
R37	350k	±1	1/4
R38	350k	±1	1/4
R39	350k	±1	1/4
R40	350k	±1	1/4
R41	350k	±1	1/4
R42	350k	±1	1/4
R43	350k	±1	1/4
R44	350k	±1	1/4
R45	350k	±1	1/4
R46	350k	±1	1/4
R47	350k	±1	1/4
R48	350k	±1	1/4
R49	350k	±1	1/4
R50	350k	±1	1/4
R51	350k	±1	1/4
R52	350k	±1	1/4
R53	350k	±1	1/4
R54	350k	±1	1/4
R55	350k	±1	1/4
R56	350k	±1	1/4
R57	350k	±1	1/4
R58	350k	±1	1/4
R59	350k	±1	1/4
R60	350k	±1	1/4
R61	350k	±1	1/4
R62	350k	±1	1/4
R63	350k	±1	1/4
R64	350k	±1	1/4
R65	350k	±1	1/4
R66	350k	±1	1/4
R67	350k	±1	1/4
R68	350k	±1	1/4
R69	350k	±1	1/4
R70	350k	±1	1/4
R71	350k	±1	1/4
R72	350k	±1	1/4
R73	350k	±1	1/4
R74	350k	±1	1/4
R75	350k	±1	1/4
R76	350k	±1	1/4
R77	350k	±1	1/4
R78	350k	±1	1/4
R79	350k	±1	1/4
R80	350k	±1	1/4
R81	350k	±1	1/4
R82	350k	±1	1/4
R83	350k	±1	1/4
R84	350k	±1	1/4
R85	350k	±1	1/4
R86	350k	±1	1/4
R87	350k	±1	1/4
R88	350k	±1	1/4
R89	350k	±1	1/4
R90	350k	±1	1/4
R91	350k	±1	1/4
R92	350k	±1	1/4
R93	350k	±1	1/4
R94	350k	±1	1/4
R95	350k	±1	1/4
R96	350k	±1	1/4
R97	350k	±1	1/4
R98	350k	±1	1/4
R99	350k	±1	1/4
R100	350k	±1	1/4

Capacitors

Circuit ref.	Value	Description	Rating (V)
C1	390 pF	silvered mica	350
C2	150 pF	silvered mica	350
C3	2200 pF	silvered mica	350
C4	560 pF	silvered mica	350
C5	220 pF	silvered mica	350
C6	220 pF	silvered mica	350
C7	0.02 μF	electrolytic	350
C8	0.02 μF	electrolytic	350
C9	0.02 μF	electrolytic	350
C10	0.02 μF	electrolytic	350
C11	0.02 μF	electrolytic	350
C12	0.02 μF	electrolytic	350
C13	0.02 μF	electrolytic	350
C14	0.02 μF	electrolytic	350
C15	0.02 μF	electrolytic	350
C16	0.02 μF	electrolytic	350
C17	0.1 μF	paper	350

Tolerance of silvered mica capacitors is 10%

Valveholders

B9A (novel) nylon-loaded, with screening skirt.  
McMurdo XM9/AU, skirt 95 (two).

Miscellaneous

Supply input socket, 6-pin, Bulgin, P194  
Input socket (six), coaxial, Belling Lee, L.604/S  
Output socket, Igranic, P71  
Output socket, coaxial, Belling Lee, L.604/S  
Selector switch, 6-way rotary, Shirley Laboratories, SBL M/S190  
Specialist Switches, SS/592

Valves

Mullard EF86 (two)

(Note: Details of proprietary switches may not be identical with those shown in the diagram.)  
Tagboard, 10-way (two), Bulgin, C125; Denco

# LIST OF COMPONENTS FOR THREE-VALVE PRE-AMPLIFIER

Resistors			
Circuit ref.	Value	Tolerance (±%)	Rating (W)
R1	1 MΩ	10	†
R2	1 MΩ	10	†
R3	56 kΩ	10	†
R4	100 kΩ	10	†
R5	2.2MΩ	10	†
R6	100 kΩ	10	†
R7	8.2MΩ	10	†
R8	2.2MΩ	10	†
R9	100 kΩ	10	†
R10	390 kΩ	10	†
R11	270 kΩ	10	†
R12	180 kΩ	10	†
R13	100 kΩ	10	†
R14	270 kΩ	10	†
R15	3.9kΩ	10	†
R16	1.5MΩ	10	†
R17	33 kΩ	10	†
R18	220 kΩ	10	†
R19	1 MΩ	10	†
R20	100 kΩ	10	†
R21	1.2kΩ	10	†
R22	470 kΩ	10	†
R23	3.9MΩ	10	†
RV24	250 kΩ logarithmic potentiometer		†
R25	47 kΩ	10	†
R26	39 kΩ	10	†
R27	68 kΩ	10	†
RV28	250 kΩ logarithmic potentiometer		†
R29	6.8kΩ	10	†
R30	270 kΩ	10	†
R31	33 kΩ	10	†
R32	22 kΩ	10	†
R33	1.2kΩ	10	†
R34	10 kΩ	10	†
R35	22 kΩ	10	†
R36	12 kΩ	10	†
R37	270 kΩ	10	†
R38	33 kΩ	10	†
R39	47 kΩ	10	†
R40	56 kΩ	10	†
R41	56 kΩ	10	†
R42	1.5MΩ	10	†
R43	220 kΩ	10	†
R44	47 kΩ	10	†
R45	1.5kΩ	10	†
R46	220 kΩ	10	†
RV47	50 kΩ logarithmic potentiometer		†
R48 (Fig. 1a)	680 kΩ	10	†
R48 (Fig. 1b)	270 kΩ	10	†
R49 (Fig. 1a)	180 kΩ	10	†
R49 (Fig. 1b)	150 kΩ	10	†

1. High stability, cracked carbon

# LIST OF COMPONENTS FOR THREE-VALVE PRE-AMPLIFIER

Capacitors			
Circuit ref.	Value	Description	Rating (V)
C1	330 pF	silvered mica	12
C2	820 pF	silvered mica	350
C3	2700 pF	silvered mica	350
C4	330 pF	silvered mica	350
C5	330 pF	silvered mica	350
C6	50 μF	electrolytic	12
C7	0.1 μF	paper	350
C8	8 μF	electrolytic	350
C9	0.1 μF	paper	350
C10	50 μF	electrolytic	12
C11	0.1 μF	paper	350
C12	0.1 μF	paper	350
C13	560 pF	silvered mica	350
C14	8200 pF	silvered mica	350
C15	2200 pF	silvered mica	350
C16	0.02 μF	paper	350
C17	50 μF	electrolytic	12
C18	0.25 μF	paper	350
C19	1800 pF	silvered mica	350
C20	820 pF	silvered mica	350
C21	390 pF	silvered mica	350
C22	8 pF	electrolytic	350
C23	33 pF	silvered mica	350
C24	820 pF	silvered mica	350
C25	820 pF	silvered mica	350
C26	1500 pF	silvered mica	350
C27	3300 pF	silvered mica	350
C28	1800 pF	silvered mica	350
C29	820 pF	silvered mica	350
C30	390 pF	silvered mica	350
C31	2700 pF	silvered mica	350
C32	2700 pF	silvered mica	350
C33	4700 pF	silvered mica	350
C34	0.01 μF	silvered mica	350
C35	50 μF	electrolytic	12

Tolerance of silvered mica capacitors is 10%.



## Output Attenuating Networks

The sensitivity and impedance of each channel have been chosen for sources which are likely to be encountered most frequently. The level of output signal from the pre-amplifier will have to be adjusted if it is to be used with power amplifiers having different sensitivities from the 20W circuit. The signal should be attenuated by using a simple potential divider as shown in Fig. 1.

## H. T. SUPPLIES

The h. t. currents taken by the 2-valve and 3-valve pre-amplifiers are respectively 3mA at 230V and 6mA at 250V. The values of the smoothing components for these supplies depend on the combination of pre-amplifier and power amplifier. Appropriate values are given in Tables 1 and 2. The points from which these supplies are taken are shown in the complete circuit diagram for the 20W amplifier.

The l. t. current taken by the 2-valve pre-amplifier is 0.4A at 6.3V and that required by the 3-valve circuit is 0.7A at 6.3V.

## CONSTRUCTION

The connection to the programme-recording output jack on the front panel of the 3-valve pre-amplifier should be made with coaxial cable from the junction of R27 and C13. This jack socket and that of the 2-valve circuit may be connected to a coaxial output socket on the back of the pre-amplifier if it is needed for a fixed recorder.

## PERFORMANCE

The values for hum and noise in the pre-amplifiers which are quoted below for each input channel have been measured with each of the pre-amplifiers connected to the 20W power amplifier. The measurements were made at the output socket of the power amplifier when the input terminals of the pre-amplifier were open-circuited. The frequency-response curves were also obtained with these combinations of pre-amplifier and power amplifier.

The sensitivity figures given provide full outputs from both pre-amplifiers. Total harmonic distortion in the two-valve pre-amplifier is less than 0.15% at the rated output level and is only 0.24% at ten times this output. Total harmonic distortion in the 3-valve pre-amplifier is less than 0.1% at the rated output and only 0.65% at ten times the rated output. A rapid increase in distortion does not occur until the pre-amplifiers are considerably overloaded.

## MAGNETIC PICK-UP POSITION

	2-valve pre-amplifier	3-valve pre-amplifier
Input Impedance	100k ohms	100k ohms
Sensitivity at 1 kc/s		
(a) microgroove	4.8mV	7mV
(b) 78 r. p. m.	13mV	12mV
Hum and Noise (below 20W)		
(a) microgroove	55dB	53dB
(b) 78 r. p. m.	57dB	58dB

This channel is most suitable for pick-up heads of the variable-reluctance type, but moving-coil types which have higher outputs can be used if a larger value of series resistance is included.

## CRYSTAL PICK-UP POSITION

	2-valve pre-amplifier	3-valve pre-amplifier
Input Impedance	100k ohms	100k ohms
Sensitivity at 1kc/s		
(a) microgroove	70mV	150mV
(b) 78 r. p. m.	210mV	270mV
Hum and Noise (below 20W)		
(a) microgroove	55dB	53dB
(b) 78 r. p. m.	57dB	58dB

Low- and medium-output crystal pick-up heads can be used for this channel. The input is loaded with the 100k ohms resistor (causing bass loss) in order that its characteristic shall approximate to that of a magnetic cartridge, and to allow the same feedback network to be used. This produces the best compromise with most types of pick-up head.

However, if the head is not suitable for this form of loading, or if its output is too high, then it can be connected to the auxiliary input socket, which is discussed fully below. With this channel, the pick-up output is fed into a 1M ohm load which compensates automatically for the recording characteristic.

## TAPE PLAYBACK INPUT CHANNEL

	2-valve pre-amplifier	3-valve pre-amplifier
Input Impedance	80k ohms (approx)	80k ohms (approx)
Sensitivity at 5kc/s	4mV	2.5mV
Hum and Noise (below 20W)	52dB	47dB

Each channel is intended for replaying pre-recorded tapes using high-impedance heads, and the characteristics adopted result in good performance with these heads. If a greater sensitivity is required, the value of the series input resistor can be decreased until the desired sensitivity is obtained.

#### MICROPHONE INPUT CHANNEL

(two-valve circuit only)

Input Impedance	1M ohm
Sensitivity	7.5mV
Hum and Noise (velow 20W)	44dB

The microphone input channel is intended for use with high-impedance systems such as crystal microphones or magnetic microphones with transformers

#### RADIO INPUT CHANNEL

	2-valve pre-amplifier	3-valve pre-amplifier
Input Impedance	1M ohm	1M ohm
Sensitivity	330mV	250mV
Hum and Noise (Below 20W)	63dB	63dB

With the values of impedance and sensitivity quoted above, this channel should meet most requirements. Other values can easily be obtained, however, by altering the feedback resistor and the series input resistor. If the input impedance of the channel is too high, it can be reduced by connecting a resistor of the appropriate value between the input end of the series resistor and the chassis.

#### AUXILIARY INPUT CHANNEL

It can be seen from the circuits that the auxiliary channel is identical with the radio input channel in both pre-amplifiers. The channels can therefore be used for high-output crystal pick-ups, or for a tape pre-amplifier. If it is desired to use a microphone with the 3-valve circuit, a separate microphone pre-amplifier or an input-mixing pre-amplifier can be connected to the auxiliary socket. The auxiliary input is taken to a jack socket at the front of the chassis. This makes it easier to connect a portable tape recorder. The jack-socket termination of the auxiliary input position is such that insertion of the jack disconnects the coaxial socket on the rear panel.

#### tone controls

Low-impedance controls have been adopted in the 2-valve circuit so that any capacitance resulting from the use of long coaxial leads between the pre-amplifier and main amplifier will have a minimum effect on the output impedance of the pre-amplifier.

#### AUXILIARY OUTPUT POSITION

The output from the second EF86 of both circuits is available at this auxiliary position enabling a record of programme material to be made with tape equipment. This additional output is taken to a jack socket at the front of the chassis. Excellent recordings can be made even when the input signal is derived from a low-output magnetic pick-up.

An output of about 250mV is available at this socket, and the impedance is low. Recording equipment plugged into this socket should not have an input impedance less than 500k ohms. The tone controls and the filter networks are inoperative when this output is used.

#### FILTER NETWORKS (three-valve circuit only)

The characteristic of the low-pass filter has a slope of approximately 20dB per octave. The components of the network are arranged for operation at 5, 7 and 9kc/s in positions (a), (b) and (c) respectively of the switch SB in Fig. 3. Position (d) of the switch gives a flat characteristic.

The characteristic of the high-pass filter has a slope of approximately 12dB per octave. Operation is at 160, 80 and 40c/s respectively at positions (a), (b) and (c) of the switch SC. Position (d) of the switch cuts at 20c/s: this is considered preferable to allowing the response to continue to lower frequencies because of the possibility of the amplifier or loudspeaker being overloaded.

## CHAPTER 16

### BRIMAR VP10 MONO PRE-AMPLIFIER DESIGNED BY

#### THORN RADIO VALVES AND TUBES LTD

The Brimar VP10 mono high fidelity pre-amplifier circuit is suitable for driving any power amplifier which requires an input of 130mV for full power output such as the Brimar VA12 20-Watt amplifier.

The VP10 pre-amplifier incorporates full equalisation in accordance with the British Standard recommendation, and controls are provided for adequate bass and treble cut or boost, input selection and output level. Low hum and noise level is obtained without stringent layout specifications.

**Tone Controls:** Continuously variable

Bass: + 17.5dB at 30c/s referred to 1kc/s.  
 Treble: + 18.5dB at 15kc/s referred to 1kc/s.

**Harmonic Distortion:** Estimated to be better than 0.03% for an output of 130mV at 1kc/s.

**Power Supply:** H.T. supply 250/260V at 2.85mA.  
 Heater supplies. 6.3V, 0.6A  
 Panel Bulb 6.3V, 0.14A

#### INTRODUCTION


Input facilities are selected as the input selector switch is rotated clockwise for magnetic pick-up, microphone, radio tuner, and tape playback. The inputs are selected one at a time, leaving the other input sockets open circuited.

The output voltage level is controlled by a 1M ohm potentiometer which performs the function of a volume control.

Two Brimar ECC807 double triodes are used in this circuit. These valves are specially designed for use in high gain pre-amplifier stages operating from low level inputs.
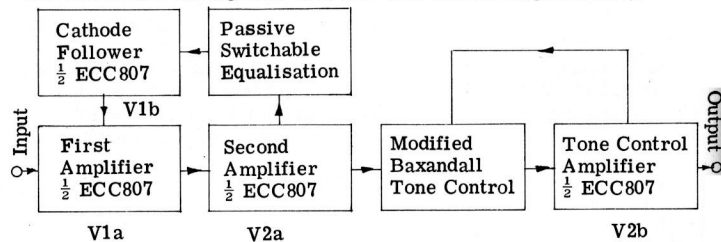
#### Circuit Description

The valves are arranged as follows: (see circuit diagram also).



#### SPECIFICATION SUMMARY

<p><b>Sensitivity</b>                      For an output of 120mV into 1M. Bass and treble controls flat.</p> <p><b>Hum and Noise</b>                      Below 20W                      Using VP10 and VA12 amplifiers</p> <p><b>Equalisation</b></p> <p><b>Feedback Factor (approx)</b>                      For an output of 130mV                      Bass and treble controls flat output level control maximum.</p> <p><b>Maximum Input</b>                      Without amplitude distortion of the output</p>	<p><b>Magnetic Pick-up</b>                      4mV at 1kc/s                      -53dB Input s/c                      R.I.A.A. u Groove recommendation.</p> <p><b>Microphone</b>                      9mV at 1kc/s                      -56dB Input o/c                      Flat + 0.5dB 10c/s to 15kc/s</p> <p><b>Radio Tuner</b>                      32mV at 1kc/s                      -58dB Input o/c                      Flat + 0.5dB 10c/s to 20kc/s</p> <p><b>Tape Replay</b>                      4mV at 5kc/s                      -54dB Input s/c                      + 21dB lift at 30c/s (B.S. Recommendation)</p>	<p>420mV</p> <p>500mV</p> <p>500mV</p> <p>370mV</p>
---	---	---



## First Amplifier

This stage operates at full gain which is of the order of 70 times. Although the cathode of this stage is connected to R3 (680 ohms) which is not bypass, the hum pick-up is negligible because R3 is shunted by the output impedance of the cathode follower V1b which is further lowered due to the additional gain of V1a and V2a.

## Second Amplifier Stage

The first stage is capacity coupled to the second stage via C11. This stage is grid current biased by R17. R16 provides some current feedback, which helps to reduce distortion.

V1a has a gain of 70 without feedback, V2a a gain of about 60 and the total gain of the two stages is 4,200. This is appropriately reduced by feedback to give the required sensitivity. Feedback is obtained from the anode circuit V2a and fed to V1a via the cathode follower V1b.

If, during switching from one input facility to another, a momentary open circuit occurs in the feedback loop, instability is likely to occur because of the high loop gain. To prevent this, a "make-before-break" selector switch is used.

## Equalisation Network

Equalisation for magnetic pick-up and tape replay is achieved by frequency selective networks, and for microphone and radio by resistive networks.

## Magnetic Pick-up

Equalisation in accordance with RIAA recommendation is provided (see magnetic pick-up response). The gain of the pre-amplifier, when switched to this channel, can be controlled by R8, which in turn controls the amount of feedback. The sensitivity of this channel is sufficient for any of the magnetic pick-ups presently available.

At the anode of V2a, the base lift continues to increase below 20c/s. C10, R19, which couple the signal into the Baxendall circuit provide a low frequency droop below 20c/s which ensures correct equalisation for the complete pre-amplifier.

At the low frequency end, when the lift is a maximum, the pre-amplifier still has about 34dB of total feedback. The maximum input voltage that can be safely used without causing amplitude distortion is 420mV.

## Microphone Input Channel

This channel is designed for a high quality low output microphone. The frequency response is flat (within +0.5dB). Phase shift correction is provided by C6 connected across R12. The gain of this channel can be controlled by R7. This channel has 54dB of feedback. To ensure level response at very low frequencies C10, R19 are included in the feedback loop.

## Radio Tuner Input

The frequency response is flat over the whole audio range. With the sensitivity figure of 31.5mV, it should be suitable for any type of tuner. Feedback in this channel is 61dB. Phase correction is provided by C5 connected across R11. Once again C10, R19 are included in the feedback loop. The gain of this channel can be controlled by R6.

## Tape Replay

The required equalisation characteristic depends upon the replay head to be used. The performance of a head is affected by the quality of the front gap, its depth, its relation to the back gap, the iron losses, self capacitance loss, and the condition of the working face. In this channel nearly 21dB's of lift at 30c/s is provided.

This should be adequate for playing back recorded tape at a speed of 3.75 inch/sec. from a reasonable quality tape replay head. At maximum lift the feedback is at least 33dB. Hence the distortion is low. As for the magnetic pick-up C10, R19 are left outside the feedback loop to provide the desired low frequency droop. The gain of this channel can be controlled by R5.

## Cathode Follower

The required feedback voltage is applied to the input valve cathode through the cathode follower (V1b). This cathode follower has a gain of 0.6 and provides a low impedance feedback voltage source to the input valve.

## Modified Baxendall Tone Control and Amplifier

This is a "see-saw" type of circuit. When the treble and bass controls are at a mid-position, the gain of the stage is unity. The base lift and cut is 17.5dB at 30c/s and treble lift and cut is 18.5dB at 15kc/s.

The lift or cut is initially provided at the end of the frequency scale without appreciably affecting the mid frequency range. A very high degree of feedback is present even at full lift, hence the distortion at this stage is extremely low. The degree of lift and cut provided should be adequate to provide compensation for room acoustics, studio and recording deficiencies, record surface noise etc.

## Bandwidth

This was measured in the microphone channel. The tone controls were set in the "flat" position and the output control was in its maximum output position. The generator had an impedance of 600 ohms and the output voltage was developed across a 1M ohm load. The frequency response was flat at 10c/s and -1dB at 20kc/s.

## Sensitivity

Measurements were made with a generator impedance of 600 ohms. Tone controls-flat, volume control maximum, output across 1M ohm.

## Hum and Noise

For this measurement the pre-amplifier was connected to Brimar VA12, which gives an output of 20 watts with an input of 130mV. DB measurements were made with respect to 20 watts with input appropriately short-circuited or open-circuited. The power amplifier was terminated with its appropriate resistive load.

## Tone Controls

The performance of the tone controls are plotted in the tone control response. The range is for bass control +18.5dB's. Generator impedance was 600 ohms and the pre-amplifier load was 1M ohm.

## Harmonic Distortion

Very low harmonic distortion in the pre-amplifier made any realistic measurements impossible for 120mV output. Hence measurements were made with an output of 1V r.m.s. The estimated distortion figure for 120mV rated output was 0.03%, since distortion is approximately proportional to output at these levels.

## Overload

Measurements were made to see the effect of overloading the inputs. A visual inspection of amplitude distortion was made using a Tektronix 535 series oscilloscope with 53/54C plug-in unit.

### Overload factor

Magnetic Pick-up: = 105 = 40dB  
Microphone: = 109 = 41dB  
Radio: = 16 = 25dB  
Tape Replay: = 92.5 = 39dB

## Transient Response

A good quality pre-amplifier should have a good transient response. A transient pulse was obtained from a Tone Burst Generator. This Tone Burst Generator has facilities to vary the on/off ratio. The output was observed on the oscilloscope and was compared with the input. The output was completely free from any ringing or high frequency attenuation effect.

## A Short Note on Layout

The specified performance of the amplifier was obtained without any special plan for layout. Due care should be taken to keep the heater leads, which should be twisted, well away from the input grid. The heater supply is balanced with respect to earth by means of resistance from each lead. Two 330 ohms resistors are wired in series across the heater leads, the centre tap is connected to earth. The power supply to the pre-amplifier should be adequately smoothed.

## D.C. Conditions

Valve Type	Point of Measurement	Voltages	D.C. Range of AVO. 8*
V1a	Anode	135	1,000 Volts
V1a	Cathode	1.15	10 Volts
V1b	Anode	207	1,000 Volts
V2a	Anode	140	1,000 Volts
V2b	Anode	160	1,000 Volts
V2b	Cathode	1.4	10 Volts

\* 1,000 Volts range resistance = 20M ohms.  
10 Volts range resistance = 200k ohms.

### Component Lists

#### Resistors (All $\frac{1}{4}$ W Rating)

Circuit Ref.	Value	Tol.	Circuit Ref.	Value	Tol.
				10M +	
RO	1 M	H.S.	R14	8.2M	H.S.
R1	220 k	H.S.	R15	1 M	+ 10%
R2	1 M	H.S.	R16	470	+ 10%
R3	680	H.S.	R17	8.2M	+ 10%
R4	22 k	+ 10%	R18	100 k	H.S.
R5	33 k	H.S.	R19	1 M	+ 10%
R6	270 k	H.S.	R20	120 k	+ 10%
R7	27 k	H.S.	R21	1 M	+ 10%
R8	47 k	H.S.	R22	1.8M	+ 10%
R9	560 k	H.S.	R23	120 k	+ 10%
R10	8.2M	H.S.	R24	100 k	+ 10%
R11	470 k	H.S.	R25	3.3k	+ 10%
R12	470 k	H.S.	R26	15 k	+ 10%
R13	820 k	H.S.			

#### Potentiometers

Circuit Ref	Value	Function
RV1	500 k	Treble control
RV2	1 M	Bass control
RV3	1 M	Output level control

Circuit Ref	Value	Type	Rating
C1	16 $\mu$ F	Electrolytic	300 Volts
C2	0.5 $\mu$ F	Metalised Paper	
C3	27 pF	Silver Mica	
C4	220 pF	Silver Mica	
C5	27 pF	Silver Mica	
C6	10 pF	Silver Mica	
C7	100 pF	Silver Mica	
C8	330 pF	Silver Mica	
C9	0.01 $\mu$ F	Visconol	300 Volts
C10	0.05 $\mu$ F	Visconol	300 Volts
C11	0.01 $\mu$ F	Visconol	300 Volts
C12	0.002 $\mu$ F	Metalised Paper	150 Volts
C13	0.002 pF	Metalised Paper	150 Volts
C14	0.01 $\mu$ F	Metalised Paper	150 Volts
C15	200 pF	Silver Mica	
C16	200 pF	Silver Mica	
C17	0.01 $\mu$ F	Visconol	150 Volts
C18	16 $\mu$ F	Electrolytic	300 Volts
C19	0.1 $\mu$ F	Visconol	300 Volts
C20	100 $\mu$ F	Electrolytic	25 Volts

#### Miscellaneous

Input and output sockets. coaxial

Switches: Made from 2 wafers 4-way 2-pole make-before-break.

Valves: 2 - ECC807

Valve Holders: 2 - B9A (noval) with screening skirt.  
2 - Screening cans.

## CHAPTER 17 POWER AMPLIFIER

The Brimar VA12 high sensitivity, high fidelity, 20 watt, audio power amplifier circuit. The output stage uses two Brimar EL506 pentodes in the class AB1 push-pull ultra linear mode.

The amplifier may be driven from a suitable pre-amplifier such as the Brimar VP10.

The valve and rectifier complement is as follows:

- |   |   |        |  |
|---|---|--------|--|
| 2 | - | EL506  | pentode output power valves,                       |
| 1 | - | ECC83  | double triode amplifier driver and phase splitter, |
| 1 | - | ECC807 | double triode high voltage gain input valve, and   |
| 4 | - | BY105  | forming a silicon H.T. rectifier bridge.           |

### PERFORMANCE

**Power Output and Distortion:** 20 watts at 1 kc/s with total harmonic distortion of less than 0.1%

**Sensitivity:** 130mV for 20 watts output.

**Bandwidth:** Flat to 0.1dB between 30 c/s and 20 kc/s at 20 watts.

**Feedback:** 36dB overall feedback.


**Hum and Noise:** 80dB below 20 watts with input short circuited.

### CIRCUIT DESCRIPTION

For the first two stages of the amplifier a high gain, low noise valve type ECC807 is used (Ref. V1a and V1b in the circuit diagram). The total voltage gain of a double triode ECC807, connected in cascade, is approximately 4900 times. Used as the input stages of the VA12 Amplifier, however, a total gain of only 380 times was required. Consequently R5 and R6 form an attenuator for the first stage and R10 and R16 an attenuator for the second stage.

It can be seen from the circuit diagram that the first three stages of the amplifier are d.c. coupled. This improves the low frequency stability when negative feedback is applied by minimising low frequency phase shift in the amplifier.

A silicon voltage regulator diode BZY88/C9V1 is used in the cathode circuit of V1a in order to give a stabilised d.c. reference to the amplifier. This is necessary for the amplifier which, apart from being d.c. coupled over the first three stages also employs d.c. feedback from the anode of V2a to the grid of V1a. Any drift or changes in H.T. voltage is, therefore, compensated for by the use of the voltage regulator diode.

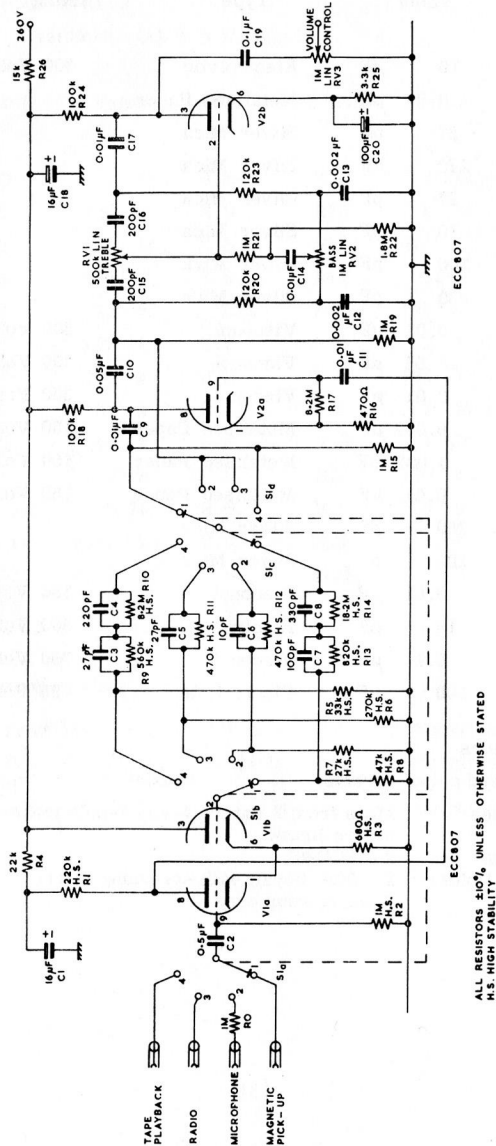

VPI0 AUDIO PRE-AMPLIFIER

V1a, V1b and V2a form part of a negative feedback loop with R7, R12, R13 and C8. This only becomes operative at frequencies below 100c/s, which compensates for the lack of low frequency feedback, due to the limitations of the output transformer, which forms part of the overall feedback loop (Ref. C15 and R27 in the circuit diagram). The negative feedback loop formed by R7, R12 and R13 also controls the overall d.c. gain. C8 causes the amount of negative feedback to be reduced as the signal frequency is raised.

To prevent high frequency instability within the amplifier a CR network (Ref. C3, R2 in the circuit diagram) is connected in parallel with R3 the anode load of V1a, giving an advance in phase.

Miller effect in V1b and V2a increases the attenuation and phase shift of the coupling circuits at high frequencies. These effects are reduced by the use of C5 and C7 which, thereby, further improves the high frequency stability of the amplifier.

The third stage, the driver and phase splitter of the amplifier uses the ECC83 double triode (Ref. V2a and V2b in the circuit diagram). To ensure sufficiently equal drive to the EL506 grids, the resistors R18, R19 and R20, R21 should be matched to within 5%.

At the junction of R11 and R14 the voltage is arranged to be the same as that of the grid of V2a. This voltage is applied to the grid of V2b, decoupled to audio by C12. The arrangement so made, provides a measure of d.c. compensation for any change of components etc. occurring in the circuitry of V2b.

The gain of the ECC83 in the cathode coupled form of phase splitter used is about 26 times. This is sufficient to provide a drive of 15V r.m.s. (distortion 0.3%) to each grid of the output stage, needed, for a total output power of 20 watts.

For the output stage two valves, type EL506, are connected in a push-pull, Class AB1, ultra linear mode. The anode-to-anode loading of the output stage is 6.6k ohms with an H.T. voltage of 438V at the centre-tap of the primary winding of the output transformer. Primary taps at 43% feed the screen grids. Anode and screen grid dissipations are 17 and 2.2 watts respectively.

Direct current, out-of-balance in the primary winding of the output transformer, is limited by the use of separate cathode-biasing resistors R26 and R25 for the two EL506 valves.

Negative feedback is taken from the secondary winding of the output transformer to V1a cathode circuit. With 36dB of feedback applied, as in circuit diagram, the amplifier is completely stable.

The H.T. supply is provided by a winding on the mains transformer and four BY105 silicon H.T. rectifiers connected in a bridge.

The bridge rectifier is connected across the mains transformer 0-320V secondary winding and is capable of supplying 150mA d.c. 108mA is drawn by the amplifier, leaving a further 42mA available for a pre-amplifier and f.m. tuner.

For such auxiliary equipment additional decoupling will be necessary since, in order not to alter the H.T. voltage for the amplifier input stage, the auxiliary supply must be connected to the reservoir condenser as shown in the circuit diagram. The mains transformer also contains two additional heater windings for use with auxiliary equipment.

NOTE: Due to the use of silicon rectifiers it is possible for 521 volts H.T. to appear immediately on switch-on, and remain until the valves draw current. This no load voltage can reach this value due to:

- (a) High mains voltage.
- (b) High secondary voltage. The rated secondary voltage, having allowed for a voltage drop in the winding, being for the loaded condition.
- (c) Two heater windings of the transformer not being used.

It is important, therefore, that capacitors across which the H.T. voltage appears should have suitable surge voltage ratings.

## CONSTRUCTION

A suggested layout is shown.

The chassis is made from 16s.w.g. aluminium sheet. Important points to note when constructing the amplifier are as follows:-

1. The ECC807 input valve must be mounted as far as possible from the mains transformer in order to minimise hum pick-up.
2. The amplifier has only one earth point, this being in the input stage.
3. Valve heaters are connected in parallel, with the ECC807 input valve being connected directly to the transformer heater winding.
4. High-stability, cracked carbon resistors are used in the input stage as they give an improved level of noise compared with standard carbon resistors. They are also used as feedback components and at points throughout the amplifier where high stability is essential.

NOTE: All resistors and capacitors are either mounted on the tag strip shown in the suggested layout or between the tag strip and the valve holders.






## GUITAR AMPLIFIER

The circuit is suitable as a 30 watt guitar amplifier when the input signal is 220mV. For increase in sensitivity the feedback components (C15 and R27) may be disconnected from the loudspeaker. The sensitivity will then be 7mV for 30 watts output.

OUTPUT TRANSFORMER  
USED IN VA12 POWER AMPLIFIER CIRCUIT

TYPE	ULTRA LINEAR PUSH-PULL
RATING	30 W
PRIMARY LOAD	6.6k OHMS ANODE TO ANODE
PRIMARY SCREEN GRID TAPS	43% OF 6.6k OHMS
PRIMARY INDUCTANCE	200 H
PRIMARY/SECONDARY LEAKAGE INDUCTANCE	20 mH

## CHAPTER 18

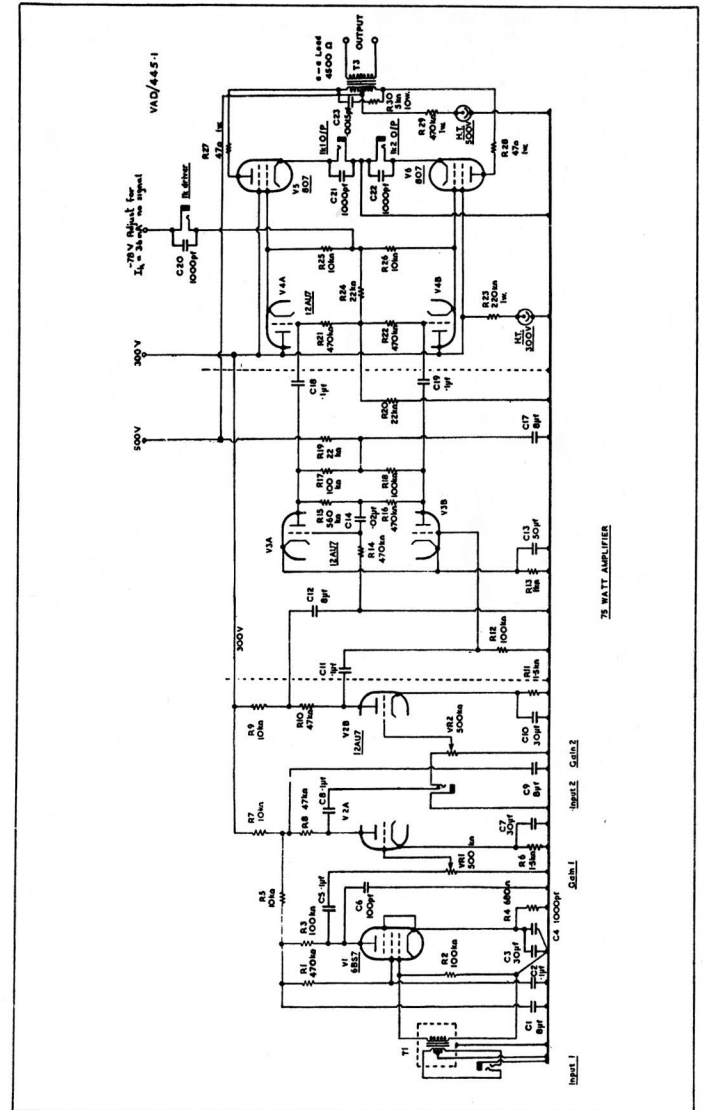

**BERNARDS & BABANI PRESS RADIO BOOKS**

BP1	First Book of Transistor Equivalents and Substitutes	40p
BP2	Handbook of Radio TV and Ind. Tube and Valve Equivalents	40p
BP3	Handbook of Tested Transistor Circuits	40p
BP4	World's Short, Medium, Long, TV & FM Broadcasting Stations Listing - International Edition	60p
BP5	Handbook of Simple Transistor Circuits	35p
BP6	Engineers and Machinists Reference Tables	20p
BP7	Radio and Electronic Colour Codes and Data Chart	15p
BP8	Sound and Loudspeaker Manual	50p
BP9	38 Practical Tested Diode Circuits for the Home Constructor	35p
BP10	Modern Crystal and Transistor Set Circuits for Beginners	35p
BP11	Practical Transistor Novelty Circuits	40p
BP12	Hi-Fi, P. A., Guitar & Discotheque Amplifier Design Handbook	75p
BP13	Electronic Novelties for the Motorist	50p
BP14	Second Book of Transistor Equivalents	95p
BP15	Constructors Manual of Electronic Circuits for the Home	50p
BP16	Handbook of Electronic Circuits for the Amateur Photographer	60p
BP17	Radio Receiver Construction Handbook using IC's and Transistors	60p
BP18	Boys & Beginners Book of Practical Radio and Electronics	60p
96	Crystal Set Construction	8p
100	A Comprehensive Radio Valve Guide - Book 1	30p
121	A Comprehensive Radio Valve Guide - Book 2	30p
126	Boys Book of Crystal Sets and Simple Circuits	25p
129	Universal Gram-Motor Speed Indicator	8p
138	How to make FM and TV Aerials - Bands 1 / 2 / 3	18p
143	A Comprehensive Radio Valve Guide - Book 3	30p
150	Practical Radio Inside Out	40p
156	Transistor Circuits Manual - No. 1	15p
157	A Comprehensive Radio Valve Guide - Book 4	30p
160	Coil Design and Construction Manual	30p
161	Radio, TV and Electronics Data Book	25p
163	Transistor Circuits Manual - No. 2	15p
170	Transistor Circuits for Radio Controlled Models	40p
174	Transistor Subminiature Receivers	32½p
177	Modern Transistor Circuits for Beginners	40p
178	A Comprehensive Radio Valve Guide - Book 5	30p
183	How to receive foreign TV programmes on your set by simple modifications	35p
191	Practical Car Radio Handbook	50p
195	High Fidelity 14 Watt Amplifier Design Chart	15p
196	AF - RF Reactance - Frequency Chart for Constructors	15p
197	Inexpensive Push-Pull Amplifier Construction Chart	15p
200	Handbook of Practical Electronic Musical Novelties	50p
201	Practical Transistorised Novelties for Hi-Fi Enthusiasts	35p
202	Handbook of Integrated Circuits (IC's) Equivalents and Substitutes	75p
203	IC's and Transistor Gadgets Construction Handbook	60p
204	Second Book of Hi-Fi Loudspeaker Enclosures	60p
205	First Book of Hi-Fi Loudspeaker Enclosures	60p
206	Practical Transistor Circuits for Modern Test Equipment	60p
RCC	Resistor Colour Code Disc Calculator	10p

**BABANI PRESS & BERNARDS (PUBLISHERS) LIMITED**  
**THE GRAMPIANS, SHEPHERDS BUSH ROAD, LONDON W6 7NF**  
**TELEPHONE NUMBER : 01 603 2581 /7296**