

electronics today international


DECEMBER 1976

30p

SOUTH AFRICA 60c
CANADA \$1

TOUCH ORGAN

Easy to build two octave design

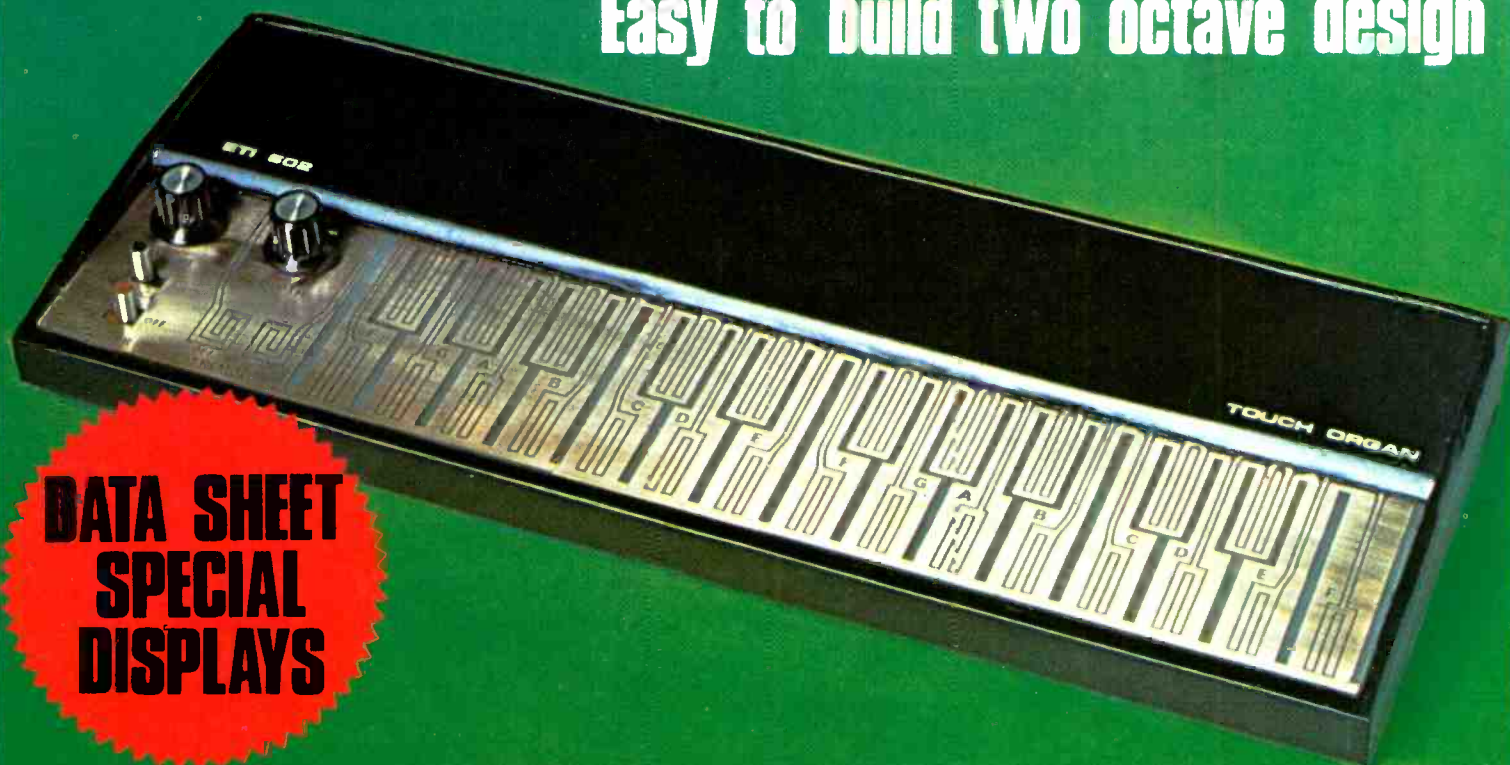

**DATA SHEET
SPECIAL
DISPLAYS**

MAN IN SPACE




ELECTRONICS 2000 AUDIO PHASER SIMPLE LIMITER HEART-RATE MONITOR

CALCULATOR DISPLAYS

1/2" digit height, bright red LED 7 segment displays for calculators, digital watches, miniature clocks, DVMS, timers etc.

- * Fairchild FND-10, single digit common cathode £1.00 (+vat 8p) 6 for £5.00 (+vat 40p)
- * HP 7414 4 digit, common cathode 12 pin d.i.l. pin out 99p (+vat 8p) 6 for £5.00 (+vat 40p)
- * Bowmar 8 1/2 digit, common cathode with pc connector, and red bezel £1.85 (+vat 15p) 6 for £10 (+vat 80p)
- * Texas 3 digit common cathode 12 pin d.i.l. pin out 85p (+vat 7p) 6 for £4.00 (+vat 32p)
- * Texas 4+5 digit, common cathode 2x14 pin d.i.l. £1.85 pair (+vat 15p)
- * 30 pin termination board for all types except FND-10 20p (+vat 2p)
- Texas calculator keyboards. 19 gold plated 'snap' type key contacts on gold plated pcb. 75p (+vat 6p) p & p on all the above 25p.

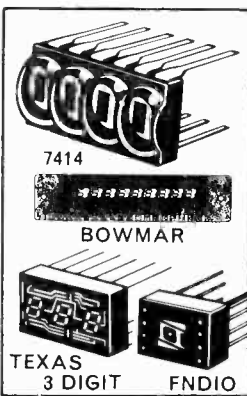

TAPE HEADS


BX12E343 1/2 TRACK ERASE HEAD - £1.25 (+vat 15p)
 BX12RP63 WITH BX12E343 - £2.95 (+vat 36p)
 STEREO CASSETTE R/RP HEAD (200 ohm) - £2.25 (+vat 28p)
 TWIN STAGGERED MARRIOTT HEADS R/RP - £1.50 (+vat 18p)
 MARRIOTT RECORD/REPLAY & ERASE HEAD - £1.75 (+vat 21p)
 MINIFLUX R9N ERASE - £2.25 (+vat 28p)
 GX11 E388 ERASE 675 ohms 2 mA - £0.88 (+vat 11p)
 GX12 E387 ERASE 675 ohms 2 mA - £0.88 (+vat 11p)
 GX20 E362 ERASE 90 ohms 90 mA - £0.88 (+vat 11p)
 R/RP1/3 TAPE HEAD 1/2 TRACK - £0.65 (+vat 8p)

MULLARD TUNER MODULES

LP1171 combined AM/FM IF strip - £4.29 (+vat 53p) * LP1179 FM front end with AM tuning gang, used with LP1171 - £4.29 (+vat 53p) * LP1171 & 79 pair - £8.00 (+vat £1.00) * LP1157 complete AM strip - £2.05 (+vat 26p) * Ferrite Aerial - 95p (+vat 7p)
 p & p all modules 25p each

HR-RP TAPE HEAD SINGLE TRACK £0.55 (+vat 6p)
 XRPS17 1/2 TRACK - £3.25 (+vat 40p)
 XRPS18 1/2 TRACK RED - £3.25 (+vat 40p)
 XRPS36 1/2 TRACK - £6.75 (+vat 79p)
 XES11 1/2 TRACK ERASE - £1.25 (+vat 15p)
 BX/RP/63 1/2 TRACK - £2.25 (+vat 28p)

HENELEC RADIO CONTROL SYSTEM

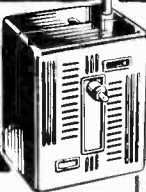

Specially designed to provide aircraft and boat modelmakers with a low-cost easy-to-use radio control, the Henelec system gives you everything from single channel, up to sophisticated 7 channel Digital Proportional System! Buy the components you want. Ideal for any radio control application. * Simple



* INCLUDING PROPORTIONALLY CONTROLLED SWITCH * FEATURING COSMOS DIGITAL LOGIC to minimise power consumption and extend battery life.

transmitter - £11.75 (+vat £1.47) * Single ch. add-on for receiver - £2.95 (+vat 37p) * PC board for above - 75p (+vat 6p) * Case for transmitter - £1.25 (+vat 16p) * Basic receiver - £6.95 (+vat 87p) Send now for leaflet No. 8 (35p) for full details. Post etc. 50p each

HENRY'S GREAT NEW CATALOGUE

For this latest edition, we have made hundreds of changes and additions. Containing virtually everything for amateurs and professionals, Henry's Radio Catalogue is also a "must" for manufacturers. Again, we have included a complete alphabetical index, as well as a sectional index, so that you'll have no trouble at all in finding what you need.

IT'S THE BEST EVER!

ONLY 85p PLUS 14p p&p


- ★ OVER 5,000 ITEMS
- ★ OVER 200 PAGES
- ★ DISCOUNT VOUCHERS
- ★ QUANTITY DISCOUNTS ON MOST ITEMS

FREE - to educational establishments and manufacturers when ordered on official headed notepaper.

BULK PURCHASE - EXCLUSIVE TO HENRY'S ALLOWS US TO SELL AT SUCH FANTASTIC PRICES!

QUALITY ITEMS Compare performance and specification with units costing 3 times as much!

DIGITAL 24 HOUR CLOCK

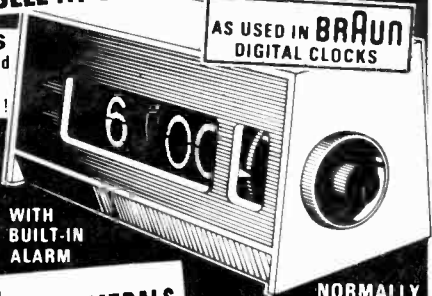

- SILENT RUNNING
- LARGE ILLUMINATED NUMERALS
- AC MAINS • SIZE 6 3/8 x 2 3/8 x 2 3/4

WITH BUILT-IN ALARM


NORMALLY £24 WITH CASE



MECHANISM ONLY

£6.00 +VAT 48p P&P 25p

THREE FOR £16.50 +VAT £1.32 POST FREE

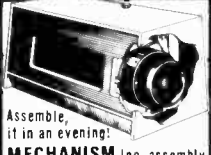

MECHANISM AND CASE

£7.99 +VAT 64p P&P 25p

THREE FOR £22.00 +VAT £1.76 POST FREE



COMPLETE UNIT

£8.99 +VAT 72p P&P 25p

THREE FOR £25.00 +VAT £2.00 POST FREE

TEXAN AMPLIFIER

featured by PRACTICAL WIRELESS still the best selling amp in the UK.

Build it yourself

£29.95 +VAT £3.74 P&P £1 Built £39.95 +VAT £4.93

Build the Texan stereo amplifier, and be doubly proud! You'll own a superb home entertainment unit. And the pleasure of doing it yourself. Look at the Texan specification Fully integrated stereo preamp and power amp, 6 IC's, 10 transistors, 6 rectifiers and zener diodes. Plus stabilised, protected circuitry, glass fibre pcb; Gardeners low-field low-line mains transformer; all facilities and controls. Slim design, chassis 14 1/2" x 6" x 2" overall. 20 watts per channel RMS.

DESIGNED BY

TEXAS

30,000 ALREADY SOLD!



* Can be built Stage by stage. Ask for leaflet 21. * Everything necessary supplied. Full after sales service and guarantees.

The natural follow on!



TEXAN FM TUNER KIT £20.95 +VAT £2.62 Built and tested £25.95 +VAT £3.24

Build the matching Texan stereo tuner! Features advanced varicap tuning. Phase lock loop decoder. Professionally designed circuit. Everything you need is in the kit. From the glass fibre pcb to the cabinet itself. Excellent spec: 2.5 uV aerial sensitivity. 500 mV output (adjustable). Tuning range 87-102 MHz. Mains powered.

NEW HENELEC Mullard AM/FM TUNER MODULE £21.95 +VAT £2.74 p&p £1.00



MAY BE ASSEMBLED IN AN EVENING. FEATURES * Built-in AM Ferrite aerial * LW coverage 150KHz-250KHz * MW coverage 530KHz-1.6MHz * FM coverage 97-104MHz * 75 ohm aerial for FM * 150mV output * Size 8 1/2(L) x 6 1/2(W) x 2 1/2(H)

This new AM/FM tuner kit incorporates 2 Mullard modules. Supplied as a pre-aligned and tested printed circuit, the constructor only has to build the PCB into the chassis, connect the power, aerial and output leads. Styled to match the Texan amp, mains operated.

Easily adapted for stereo, using the Henelec IC stereo decoder kit, high performance modular design, phase lock loop principle. Low pass filters for optimum performance. Price £8.75 +VAT £1.02 p&p 50p.

We will be pleased to quote for parts for circuits in this magazine. Send your list for quotation in S.A.E. Ask for FREE leaflets and lists on our kits projects.

Henry's RADIO

All mail to: Henry's Radio 303 Edgware Rd. London W2

LONDON W2: 404/6 Edgware Road. Tel: 01-402 8381

LONDON W1: 231 Tottenham Ct Rd. (1st floor) Tel: 01-636 6681

electronics today

international

DECEMBER 1976

Vol. 5, No. 12

Features

ELECTRONICS 2000 A.D. <i>Looking into the future through electronic eyes!</i>	10
MAN IN SPACE <i>Space travel is commonplace now — but do we know enough about the effects?</i>	25
MICROFILE PART 10 <i>Software and what to do with it!</i>	37
COMPONENTS PART 5 <i>Carbon resistors are not quite as they seem</i>	54
ELECTRONICS — IT'S EASY! <i>Continuing our series for the beginner</i>	64
TECH TIPS <i>Readers' own circuit ideas</i>	73

Projects

HEART-RATE MONITOR <i>On the beat device — for athletes or experimenters</i>	19
AUDIO PHASER <i>A superb unit for the guitarist</i>	29
TOUCH ORGAN <i>How about a two octave organ for a Xmas present?</i>	41
AUDIO LIMITER <i>Simple design to cater for most needs — by popular demand</i>	58

Data Sheet

SPECIAL ON LED DISPLAYS	49
-------------------------	----

News

NEWS DIGEST	6
ELECTRONICS TOMORROW	71

Information

ETI SPECIALS	9
BOOK SERVICE	28
SUBSCRIPTIONS	33
NEWSFLASH ABOUT ETI!	34
JANUARY ETI PREVIEW	36
ETI WATCH OFFER — DOWN IN PRICE!	57
ETI CLOCK OFFER	57
READER SERVICES INFORMATION	82
ADVERTISERS INDEX	82

Our thanks go to ITC inc LTD TV company for providing the front cover insert from Space 1999.

EDITORIAL AND ADVERTISEMENT OFFICES

25-27 Oxford Street
London W1R 2NT
Telephone 01-434 1781/2

HALVOR W. MOORSHEAD
Editor

LES BELL, G4CFM
RON HARRIS B.Sc
Editorial

TONY ALSTON
Project Development

JIM PERRY
Specials Editor

JEAN BUTTERWORTH
JULIAN FITZLYON
Production

SANDRA ZAMMIT-MARMARA
Subscriptions

MARGARET HEWITT
Administration

DAVID LAKE (Manager)
BRENDA GOODWIN
Reader Services

For advertising enquiries:
ROBERT C. EVANS Advertisement Manager
Telephone 01-434 1781/2

INTERNATIONAL EDITIONS

AUSTRALIA Collyn Rivers
Editorial Director
Steve Braidwood
Assistant Editor

HOLLAND Anton Kriegsman
Editor-in-chief

CANADA Peter Perst
Publisher

FRANCE Denis Jacob
Editor-in-chief

Electronics Today international is normally published on the first Friday of the month prior to the cover date

PUBLISHED BY
Modmags Ltd.
25-27 Oxford Street, W1R 2NT



DISTRIBUTED BY
Argus Distribution Ltd (British Isles)
Gordon & Gotch Ltd (Canada and South Africa)

PRINTED BY
QB Newspapers Limited, Colchester

COPYRIGHT All material is subject to world wide Copyright protection. All reasonable care is taken in the preparation of the magazine to ensure accuracy but ETI cannot be held responsible for it legally. Where errors do occur, a correction will be published as soon as possible afterwards in the magazine.

BI-PAK

High quality modules for stereo, mono and other audio equipment.



NEW

PUSH-BUTTON STEREO FM TUNER

OUR PRICE ONLY

£19.95 Fitted with Phase Lock-loop Decoder

The 450 Tuner provides instant program selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, by simply changing the settings of the pre-set controls.


Used with your existing audio equipment or with the BI-KITS STEREO 30 or the MK60 Kit etc. Alternatively the PS12 can be used if no suitable supply is available, together with the Transformer T538.

The S450 is supplied fully built, tested and aligned. The unit is easily installed using the simple instructions supplied.

- ★ FET Input Stage
- ★ VARI-CAP diode tuning
- ★ Switched AFC
- ★ Multi turn pre-sets
- ★ LED Stereo Indicator

Typical Specification:
Sensitivity 3µ volts
Stereo separation 30db
Supply required 20-30v at 90 Ma max.

MPA 30

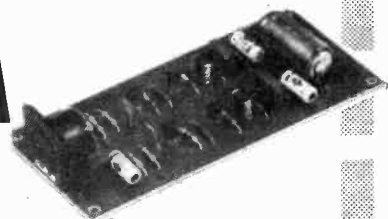

Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the new M.P.A. 30, a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only. It is provided with a standard DIN input socket for ease of connection. Full instructions supplied.

£2.65

STEREO PRE-AMPLIFIER



PA 100 OUR PRICE £13.50

A top quality stereo pre-amplifier and tone control unit. The six push-button selector switch provides a choice of inputs together with two really effective filters for high and low frequencies, plus tape output.


MK. 60 AUDIO KIT: Comprising 2 x AL60's, 1 x SPM80, 1 x BTM80, 1 x PA100, 1 front panel and knobs, 1 Kit of parts to include on/off switch, neon indicator, stereo headphone sockets plus instruction booklet. **COMPLETE PRICE £27.55.**

TEAK 60 AUDIO KIT:

Comprising: Teak veneered cabinet size 16 3/4" x 11 1/2" x 3 3/4", other parts include aluminium chassis, heatsink and front panel bracket plus back panel and appropriate sockets etc. **KIT PRICE £9.20** plus 62p postage.

Frequency Response + 1db 20Hz 20KHz Sensitivity of inputs
1 Tape Input 100mV into 100K ohms
2 Radio Tuner 100mV into 100K ohms
3 Magnetic P.U. 3mV into 50K ohms
P.U. Input equalises to R1AA curve with 1db from 20Hz to 20KHz
Supply — 20-35V at 20mA

Dimensions
299mm x 89mm x 35mm

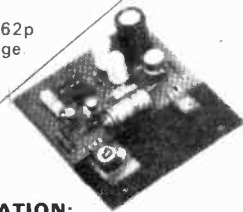

AL- 20-30 AUDIO AMPLIFIER MODULES

The AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 5 to 10 watts R.M.S.

The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the home.

SPECIFICATION:

- Harmonic Distortion $P_o = 3$ watts $f = 1$ KHz 02.5%
- Load Impedance 8-16ohm
- Frequency response ± 3 dB $P_o = 2$ watts 50Hz-25Hz
- Sensitivity for Rated O/P — $V_s = 25$ v. $R_L = 8$ ohm $f = 1$ KHz 75mV. R.M.S

AL20 5w R.M.S. £2.65 AL30 10w R.M.S. £2.95

AL 60 25 Watts (RMS)

★ Max Heat Sink temp 90C. ★ Frequency response 20Hz to 100KHz ★ Distortion better than 0.1 at 1KHz ★ Supply voltage 15-50v ★ Thermal Feedback ★ Latest Design Improvements ★ Load — 3,4,8, or 16 ohms ★ Signal to noise ratio 80db ★ Overall size 63mm. 105mm. 13mm.

Especially designed to a strict specification. Only the finest components have been used and the latest solid-state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast

Stabilised Power Supply Type SPM80

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watts (R.M.S.) per channel simultaneously. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5A at 35V. Size: 63mm. 105mm. 30mm. Incorporating short circuit protection.

Transformer BMT80
£2.60 + 62p postage

£3.00

NEW PA12

NEW PA12 Stereo Pre-Amplifier completely redesigned for use with AL 20/30 Amplifier

Modules. Features include on/off volume, Balance, Bass and Treble controls. Complete with tape output.

Frequency Response 20Hz-20KHz (-3dB). Bass and Treble range 12dB. Input Impedance 1 meg ohm. Input Sensitivity 300mV. Supply requirements 24V. 5mA. Size 152mm x 84mm x 33mm.

£6.50

£3.95 PS12

Power supply for AL20/30, PA12, SA450 etc.

OUR PRICE

£1.20

BI-PAK


SHOP
AT

18 BALDOCK ST., WARE, HERTS
OPEN 9 to 5.30 Mon./Sat. Tel. 61593

P.O. BOX 6,
WARE,
HERTS.

news digest

MPU's SEW IT UP

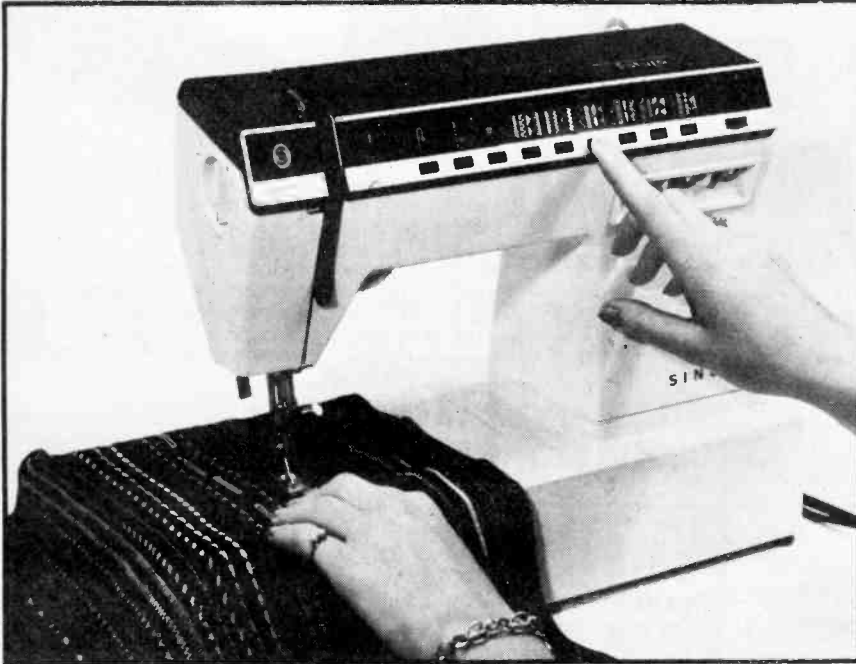

Singer have just introduced a sewing machine which is MPU controlled. No, this is not a joke. Yes I did say sewing machine. The MPU replaces 300 mech-

anical parts, and means that 25 stitch patterns can be obtained at no more energy expense than a button push.

POWER TO THE PEOPLE

A new power cable is to be installed in Russia to link two power stations 1500 miles apart. Nothing special there. You might think we're just pylon it on in fact. What is unusual is that this reel of metal cotton is to carry 1.5MV, and a later 2000 mile link will be under 2.5MV tension. The 'super-lines' will be constructed of steel strands braided with aluminium. Thyristor crystals are employed as rectifiers.

Just the thing to hang your cassette player on.

COLOUR PREJUDICE?


Official figures for the number of homes with colour TV's, i.e. those with a license, have just exceeded 50% of the total. Some lesser mortals might well be tempted to conjecture how high the total would be if the un-licensed felons in our midst could be stood up and counted. Naturally we refrain from any such thoughts.

READER WRITER (SR 52) DATA!

One of our intrepid readers - Mr. P.A. Brown of Ergonomic developments has informed us of a follow up to last months little snippet on the SR 52. It seems this machine is capable of more than anyone is letting on.

Locations 70-97 can be used to store data without affecting the programme store. If the machine is now put into the learn mode, this data will be read out into the magnetic card. Data storage with vengeance! Locations 98-99 affect the programme store.

NOT A TRACE OF INSTABILITY

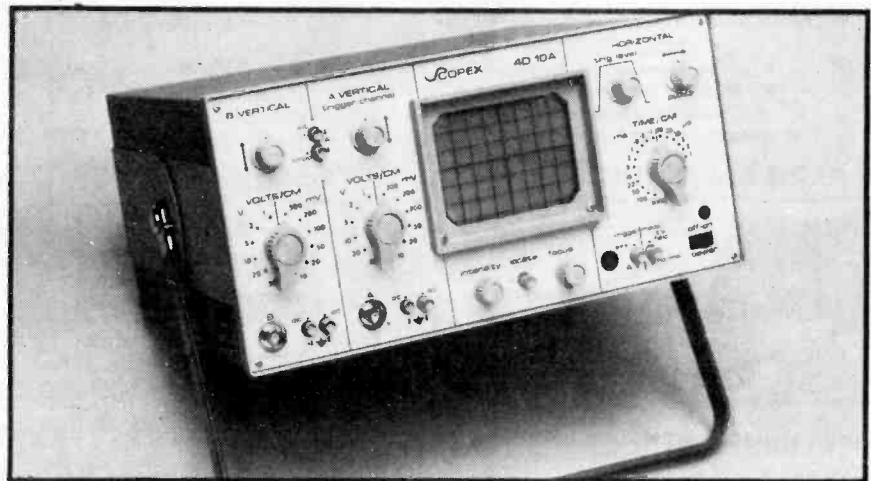

This new oscilloscope from Scopex offers a very high performance for its £150. With completely stabilised PSU's (trace stability over $\pm 10\%$ mains variation) measurement accuracy $\pm 3\%$, input up to 50V/cm, T.V. field mode triggering to allow for Ceefax etc, and triggering up to 10MHz in ordinary mode, the dual beam 4D10A is an attractive proposition to the affluent amateur or small business.

Scopex Ltd., Pixmore Estate, Pixmore Avenue, Letchworth, Herts.

TV RENTAL PROFITS 'TOO HIGH'

The average return on capital of 16.5% a year by the TV rental companies has been condemned by Prices Secretary, Roy Hattersley, as being too high.

Wicked companies!

These are the people who have a) brought Colour TV to over half British homes b) kept TV rentals to the lowest cost anywhere in the world that we know about c) prevented TV rentals costs going up far less than inflation d) kept the British TV industry going despite the best attempts of the government to kill it by juggling with VAT e) forced down the cost of outright purchased sets to remain competitive f) raised the standard of servicing enormously.

Wicked companies!

Still, there is a foolproof way of ensuring that these companies make far less than 16.5%, in fact for them to make a loss (rather fashionable today): nationalise them. The costs of renting would go up instantly of course - but it would put an end to these wicked profits.

PLAY-ALONG-WITH-RCA

Single chip I/O for video games is the laudible aim of messers. RCA. To be introduced in January the device is primarily a vertical and horizontal synching circuit designed for use with RCA's 1802 MPU. Price could well be around £12 when and if introduced into this country.



WHAT'S HAPPENED ?

We've moved that's what happened! Increasing numbers of staff and our ever increasing circulation has meant that we're working stacked up like sardines in a can.

Just to keep up with ourselves — being the fastest growing, most modern (and most modest) electronics magazine in the country — we're taking up residence in Oxford Street, Our new address is shown below, and all letters, bouquets of flowers, messages of congratulations and cheques for vast sums of money should be sent there in future. **ETI EDITORIAL AND ADVERTISEMENT OFFICES, 25-27 OXFORD STREET, LONDON W1R 2NT. Telephone 01-434 1781/2.**

BAND OF HOPE AND GLORY?

FROM: RADIO SOCIETY OF G.B.

The matter of citizens' band is under continual consideration by the Society's Telecoms Liaison Committee and the Council approves its present views which are:

- (a) The RSGB exists to safeguard the interests of its members and of the Amateur Service in the UK. The Amateur Service is a defined service in the Radio Regulations (Geneva 1976) and is accorded world wide status in the same way as the professional services.
- (b) While the RSGB may have no direct interest in a citizens' band facility by its present articles of association it must, in the interests of its members, take heed of developments likely to affect the Amateur Service.
- (c) The major consideration affecting the introduction of any new facility is the ability of the administration to exercise complete and effective control. Anything less is not acceptable.
- (d) The RSGB is not opposed to the introduction of a short range personal communications facility provided that its location in the spectrum and the equipment used are suitable. The 27MHz band as used in the USA and some European countries is probably one of the most unsuitable frequency bands that could be envisaged. There are three main reasons:
 - (i) its proximity to the amateur 28MHz band and the consequent availability of high power equipment together with the ease of illegal operation in this band,
 - (ii) the existence of long distance propagation during part of the sunspot cycle, and
 - (iii) the interference to television receivers, particularly those operating in Band 1. Having regard to equipment now available it would appear that a VHF or UHF FM service with power limitation, crystal control and type approved apparatus could be suitable.
- (e) Location of a citizens' band within an existing amateur service allocation is not acceptable to the RSGB. Further, if this facility is eventually allowed it ought to be located in a part of the spectrum remote from any amateur allocation to prevent illegal operation in an amateur band such as is now experienced in the USA.

(NEW) HOME ON THE (TEXAS) RANGE?

Texas introduces its new SR-51-II. With a suggested retail price of £59.95 inc. VAT the SR-51-II supersedes the SR-51-A.


Key features include the capability to enter complex equations in left to right order as they are stated, full memory arithmetic, key entry con-

versions and engineering notation.

Separate keys for the seven most-used conversions are included on the SR-51-II keyboard.

The seven conversion keys include inches to centimetres; U.S. gallons to litres; pounds to kilograms; degrees to radians; grads to radians; Fahrenheit to Celsius (Centigrade); and degrees/minutes/seconds to decimal degrees.

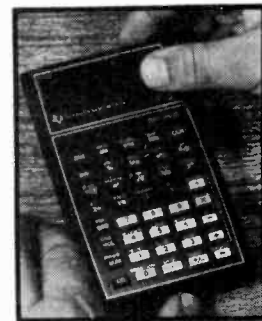Engineering notation, which displays results having scientific notation




exponents in multiples of three, is also included.

The SR-51-II suggested retail price includes a rechargeable battery pack, AC adapter/charger and carrying case. It has a 10-digit light-emitting diode display but calculates up to 12 digits internally, rounding to 10.

The new model is warranted for one year from the original purchase date against defective materials and workmanship to the original purchaser.

European Calculator Division, Texas Instruments Ltd., Block C, Manton Centre, Manton Lane, Bedford, MK41 7PU.

DMM ADD ON ADDS SCOPE!

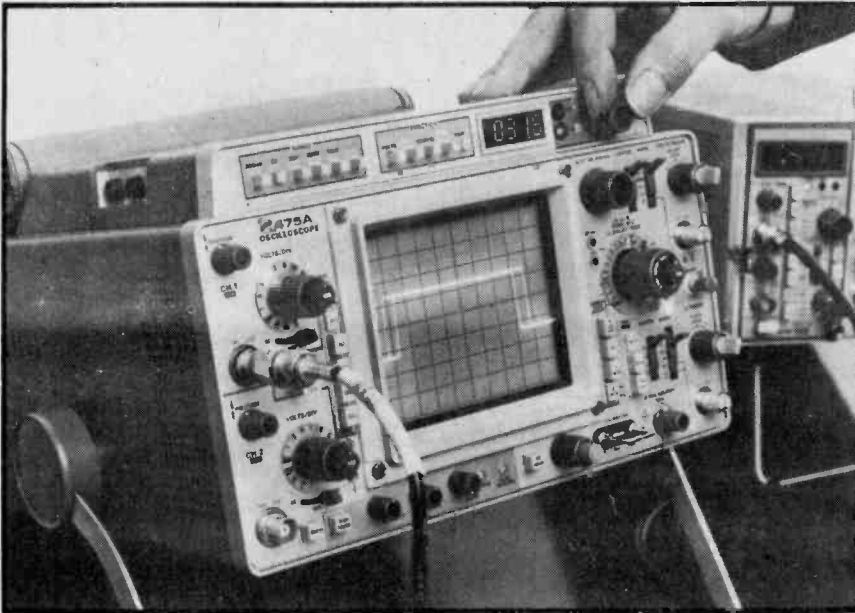

The DM44 Digital Multimeter is an optional item on several Tektronix portable oscilloscopes. It permits time interval measurements between any two points on waveforms displayed by the oscilloscopes, indicated by a 3½ digit LED readout with 1% accuracy. A Delta Delayed Sweep feature is used with the oscilloscopes' main delayed to mark the start and stop points of the time interval measurement.

It also includes a DC Voltmeter ranging up to 1.2kV with 0.1% accuracy, an Ohmmeter covering 0 to 20MΩ (0.3% accuracy) and Temperature Probe from -55°C to +150°C, and is available on Tektronix 464, 465, 466, 475A and 485 portable oscilloscopes.

Tektronix UK Limited, Beaverton House, P. O. Box 69, Harpenden, Herts.

TRIPLETS FROM HP

Hewlett Packard have just released details of their latest offsprings, two of which are described here and the third in Microfile.

The 3455A is a healthy (bouncing?) 21½ digit DMM with a choice of 5½ or 6½ digit display. This siamese-twin-microprocessor based machine (2 MPU's inside) features self-check of calibration, mathematical abilities (at less than 1 month?), HP-IB compatibility, and 0.002% accuracy over 24 hours with resolution down to 1µV.

Sister to the 3455A is the 3437A systems voltmeter with 3½ digit display. Up to 5000 readings per second with .03% accuracy, variable trigger delay from .01µS to .999999 seconds. Number of readings from one trigger up to 9,999.

Both these machines light up like Xmas trees, with LED's in all control buttons to indicate status.

Further details from Hewlett Packard Ltd., King Street Lane, Winnersh, Wokingham, Berks RG11 5AR.

SHIFT WORK IN CCD


Somewhere amid the redwoods in Mountain View, California although admittedly hardly under a bush Fairchild are slaving over a hot soldering iron to perfect their latest toy – a 65,536 bit shift register. Naturally CCD. This plaything of the boffins is organised in 16 blocks of 4096x1 bits. One bit from any block can be addressed, and all blocks recirculate automatically in read mode. Typical power drawn is around 400mW, and it will arrive in a 16 pin pack – when it arrives at all.

ON THE DOT DISPLAYS

ITT Optical Equipment Division has introduced a 7 x 5 dot alphanumeric LED display which features 17mm-high characters and integral MOS shift registers for serial feed electronic drive systems.

The brightness of the display can be controlled by a single DC voltage and any number of displays can be controlled by one clock and one data line.

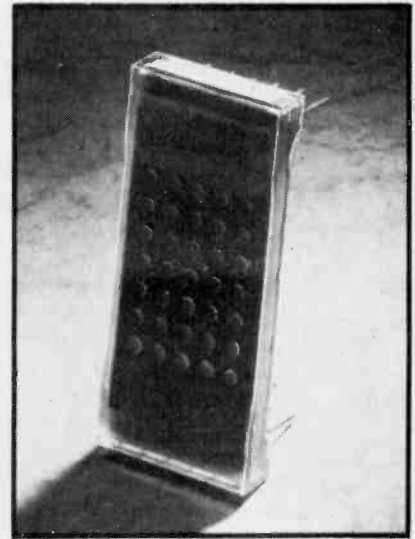The devices do not require separate limiting resistors.




ITT Components Group Europe, Optical Equipment Division, Westfield Mill, Broad Lane, Leeds.

BRIDGING THE GAP

Two new types of high-current bright rectifiers – the first capable of handling up to 10A, the second capable of handling up to 15A – have been announced by General Instrument (UK) Limited.

Designated the KBPC-10 and -25 series, the two types occupy identical cases, measuring 18.5 x 28.5 x 25.4mm (1 1/8 x 1 1/8 x 1in) overall. they are available in operating PIV's of 50, 200, 400 and 600V.

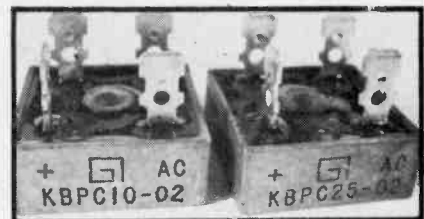General Instrument (UK) Limited, Cock Lane, High Wycombe, Bucks.



CORRECTION OF THE MONTH

Project Book 4 – Sweet Sixteen. The components are missing from the overlay diagram. For those sinners amongst you who don't have the back issue – July 1976 – we will forward the diagram on receipt of an SAE.

Specials from etl

Electronics - It's Easy - the first thirteen parts of our popular introductory series and a good way to begin finding out more about your hobby. £1.20 + 20p P and P.

Electronics - It's Easy Volume 2 - the next twelve parts in our series for beginners. £1.20 + 20p P and P.

4600 Synthesiser - complete reprint of our superb synthesiser design produced by Maplin, who can also supply the parts. £1.50 + 20p P and P.



Project Book Two - contains 26 popular projects from the pages of ETI, first published July 1975. 75p + 20p P and P.


Project Book Three - 27 more popular ETI projects first published March 1976. £1.00 + 20p P and P.

New

HURRY! PRE PUBLICATION OFFER . . . Normal mail order price for Circuits 1 is £1.50 + 20p mail. Orders placed before publication will be dispatch, hot from the printers, mail free. Orders must be postmarked before 14th November. Available after this date at £1.70.

A brand new concept from the house of ETI, more than 100 pages packed with a wide range of experimenters circuits. Based on the tremendously popular 'Tech-Tips' section of ETI, Circuit 1 is the first of a series of specials - produced for the enthusiast who knows what they want, but not where to get it! Circuits 1 will also act as a catalyst for further development of ideas, ideal for the experimenter. The collection of more than 200 circuits is complemented by a comprehensive index, making searches for a particular circuit quick and simple. Also similar circuits can be compared easily, due to the logical layout and grouping used throughout. Last and by no means least Circuits 1 has no distracting advertisements in the main section!

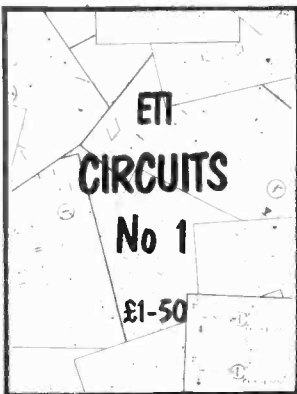Available in U.K. second week of November
Overseas readers please see note below.



£1.50 + 20p P and P.



£1.00 + 20p P and P.

INCLUDING

AUDIO
SWEET SIXTEEN
WAA WAA
AUDIO LEVEL METER
EXPANDER-COMPRESSOR

MOTORIST
ANTI-THEFT ALARM
AUTO AMP
HEADLIGHT REMINDER
SOLID STATE FLASHER

TEST GEAR
DUAL TRACKING POWER SUPPLY
SIMPLE CMOS TESTER
AUDIO MILLIVOLTMETER
THERMOCOUPLE METER

HOME
INTRUDER ALARM
TOUCH SWITCH
PUSH BUTTON DIMMER

PHOTOGRAPHER
EXPOSURE METER
PHOTO TIMER

GENERAL
ELECTRONIC DICE
HIGH POWER BEACON
TEMPERATURE CONTROLLERS

PLUS MUCH MORE

Overseas readers please see note below.

To: ETI SPECIALS, 25-27 OXFORD STREET, LONDON W1R 2NT.

POSTAGE AND PACKING is 20p for the first, 15p for subsequent issues (overseas 25p and 20p for subsequent issues).
OVERSEAS READERS PLEASE NOTE . . . Both Top Projects 4 and Circuits 1 will not be generally available at newsagents or bookshops, but can be obtained by direct mail from our London Offices. Prices as for U.K. mail order (pre-publication offer as well!), includes surface mail - air mail on application. All payments to London MUST be in Sterling.


ELECTRA

IN THE

2000

EVOLUTION OR

By Peter S.

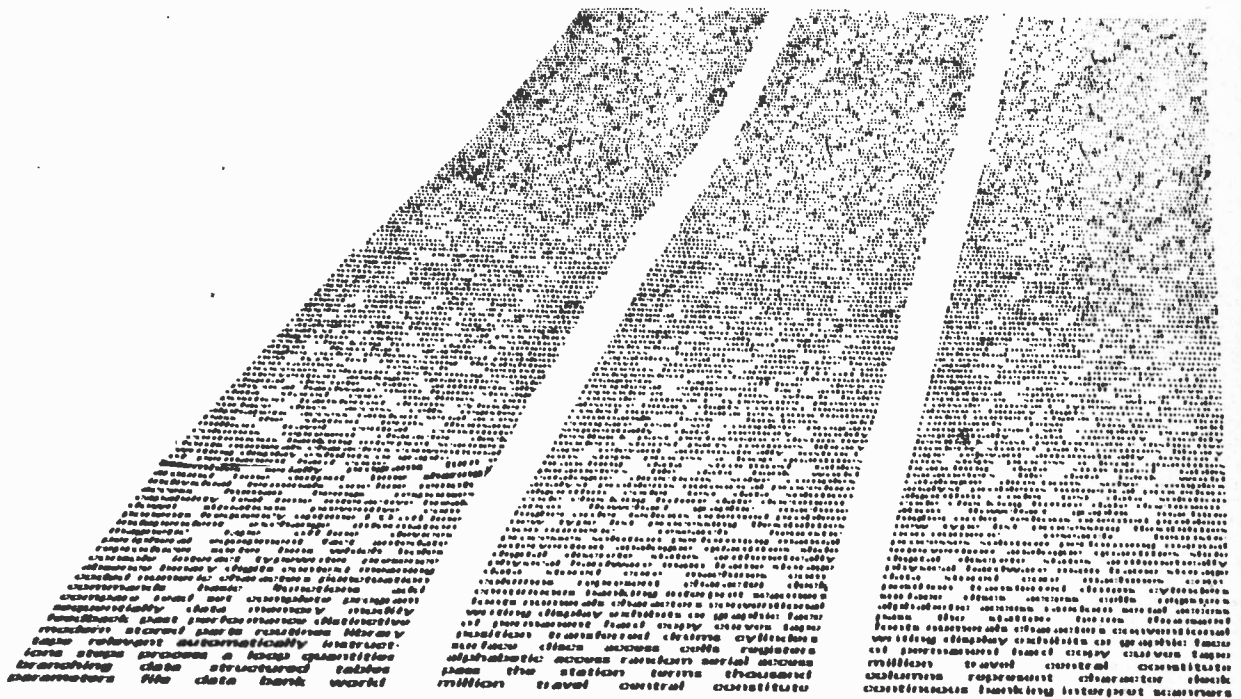

YEAR 2000 A.D. — A LOOK INTO THE FUTURE OF ELECTRONICS

Part 1. Forecasting — Fame and Fortune or Failure and Futility?

IT IS AN interesting and fascinating exercise to try and predict the future. Clairvoyance aside, this short series of articles investigates what we might expect to find ahead. It is a logical step to extrapolate into the future by studying the ideas of the past, but this does not necessarily produce correct answers. New inventions and discoveries markedly alter the pattern of progress.

REASONS FOR FORECASTING

So why attempt a forecast? Many good reasons exist. One is to see if we like what we expect to see.

First we could go to the clairvoyant. Their history of correctness has often been amazingly good, nevertheless, our present state of understanding we can still put little faith in that method. A far more reliable way open to us at present is to systematically study the already proven possible, extending it to its naturally set limits.

This approach is logical and appears to have its roots in the late 17th and early 18th century writings of that great mathematician, philosopher and politician, Gottfried Wilhelm von Leibniz. His hypothesis about prediction was that events of the future are determined by the many events of today. We call this approach *determinism*.

Philosophers are still unable to resolve whether life is entirely deterministic or whether indeed there are factors that man will never

understand. Experience continues to demonstrate, however, that the more we look into processes the better we can determine the properties. It is safe to say a great deal can be predicted by using time extensions of current systems. The problem is the enormously large number of variables and interconnections; these make many a system virtually unmanageable as an accurate enough model. To illustrate this point, Fig. 2 is a copy of one of many simplified models proposed to simulate the economy of a country. The difficulties still to be overcome are to get correct and relevant input data and to ascertain if the model is detailed enough.

ON BREAKTHROUGHS

Looking forward 25 years is not too great a step. Where a given currently existing state-of-the-art will evolve to


100 YEARS

YEAR

1900

REVOLUTION

by denham

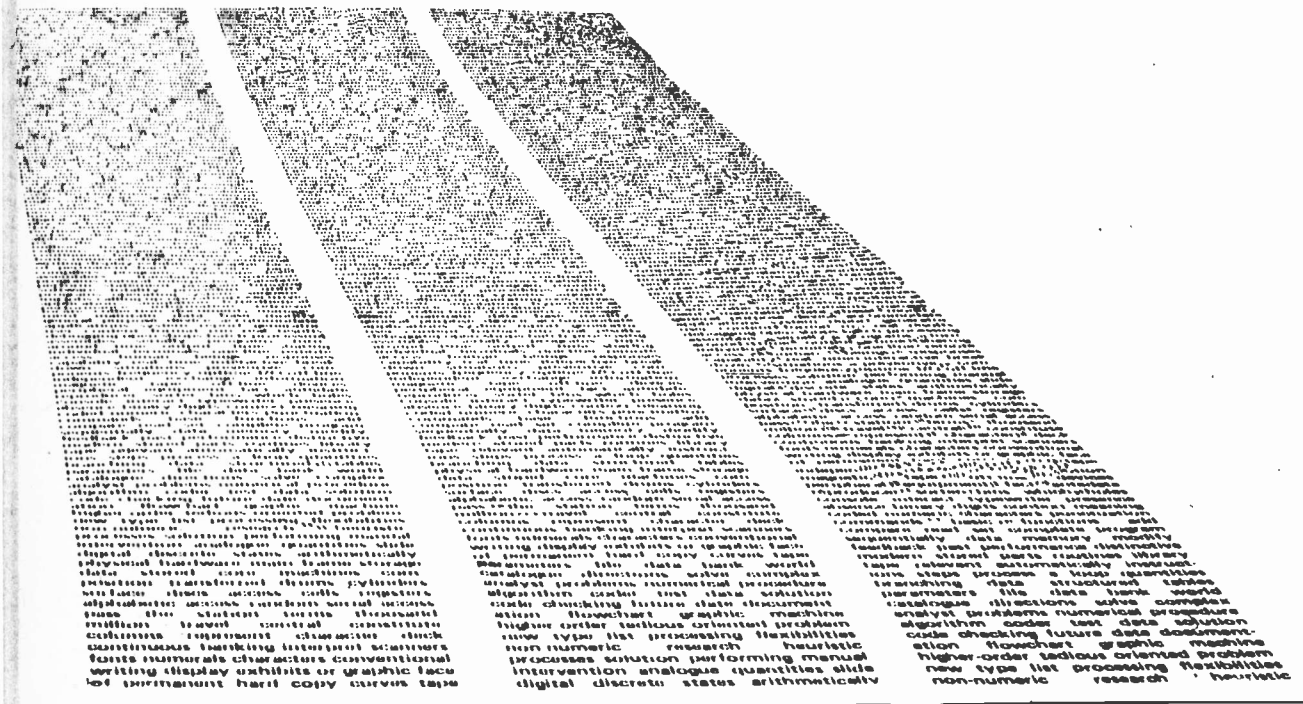

is often reasonably obvious to the adequately trained and involved person. The real unknown is the so-called "break through" that changes the path of progress abruptly. Break throughs are not usually brand-new concepts but ideas that materialise gradually from the maturing thoughts of many, finally coming to a head as an apparently "new idea".

Radio waves were predicted by mathematical means (that is they were seen to exist by studying a mathematical model of the physical situation) before they were demonstrated in practice. Even when we have the final stage of a new development within our grasp we may still be unable to harness it. Edison did not realise he had built the first vacuum-tube diode during his lamp experiments. Nearly twenty years had to pass before the idea was applied.

Faraday's experience illustrates that

breakthroughs are as much a release of man's mind into new areas of the possible as they are a really new discovery. The notice given in Fig.3 exemplifies changes in attitude. The late eminent scientist and Nobel Laureate, Sir George Thomson, skilled in physics, aviation and fuel research did not seem to conceive (in a 1955 prediction of his) inter-country communications without a massive network of waveguides or co-axial cables to convey the necessary bandwidth. And what about this futuristic statement on television from an earlier source:

"It has been assumed by many and stated by some, that within a reasonable number of years, long-distance transmission, even across the Atlantic, will be broadcast regularly... so the sensational theories predict. The truth is that long-distance television of the type we

know today is never likely to be practical or even possible."
Alan Chappell, Discovery, February 1937.

Just as wild was this statement by Lee de Forest (who invented the triode around 1906). He stated in a New York Times article of 1926:

"While theoretically and technically television may be feasible commercially and financially I consider it an impossibility, a development of which we need waste little time dreaming."

The art of the possible depends not only on human ingenuity but on the economic cost involved. Given a huge production run - great demand in other words - the cost per article falls remarkably. This, in turn, allows the basic idea to flow on into other areas of utility. The cheapness of domestic telephone components enabled many other sensors to be realised.

Electronics 2000

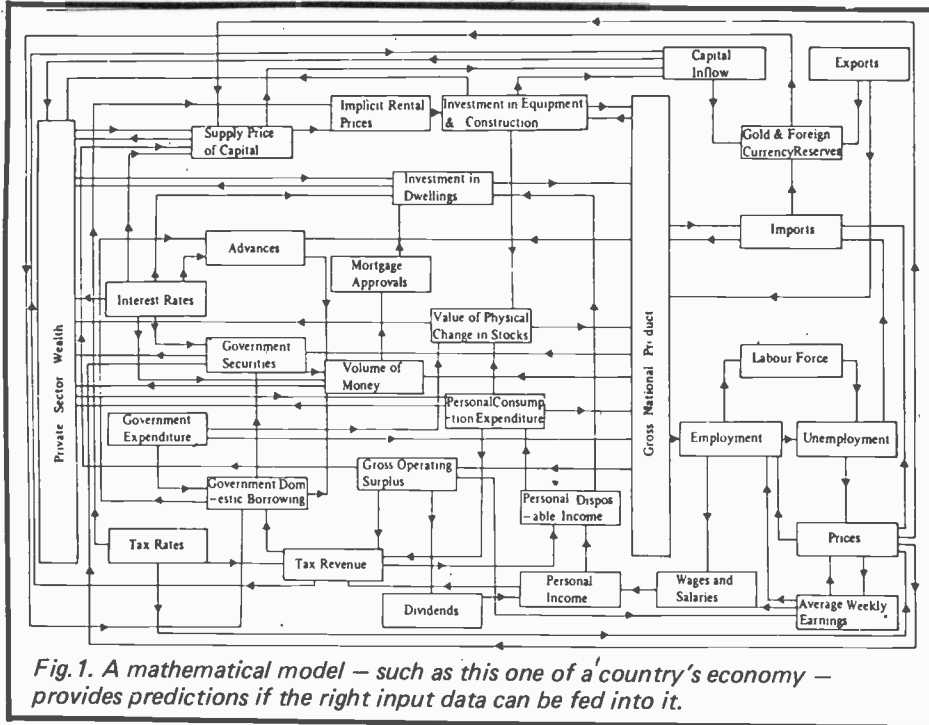


Fig. 1. A mathematical model — such as this one of a country's economy — provides predictions if the right input data can be fed into it.

ESTABLISHING THE STATE OF IGNORANCE

Another reason for attempting a forecast is because:


"The first step to knowledge is to know that we are ignorant" — Cecil.

By studying the likely new situations we usually reveal areas of ignorance. The subsequent process of research aiming to reduce this lack of knowledge often leads to improved development. We have a term for such studies — impact studies. A good historical example of this principle was the discovery of the more recently found chemical elements.

Antimony was discovered in 1450 A.D. by Valentine, a German alchemist. (Iron and several other

common elements were known at that time, of course). A steady growth in the discovery of more elements continued. By 1900 about 90 were known to exist, many being added as the result of prediction based on the work of Mendelyev. In 1869 this Russian chemist carefully studied the relation between all known elements of his time. He proposed the so-called periodic table which placed elements in the table according to certain properties. There resulted gaps in the table — such as the position of the noble gases (argon, krypton, etc.) where an element should be. Knowing the expected properties of these gases it was just a matter of time before they were isolated to further confirm

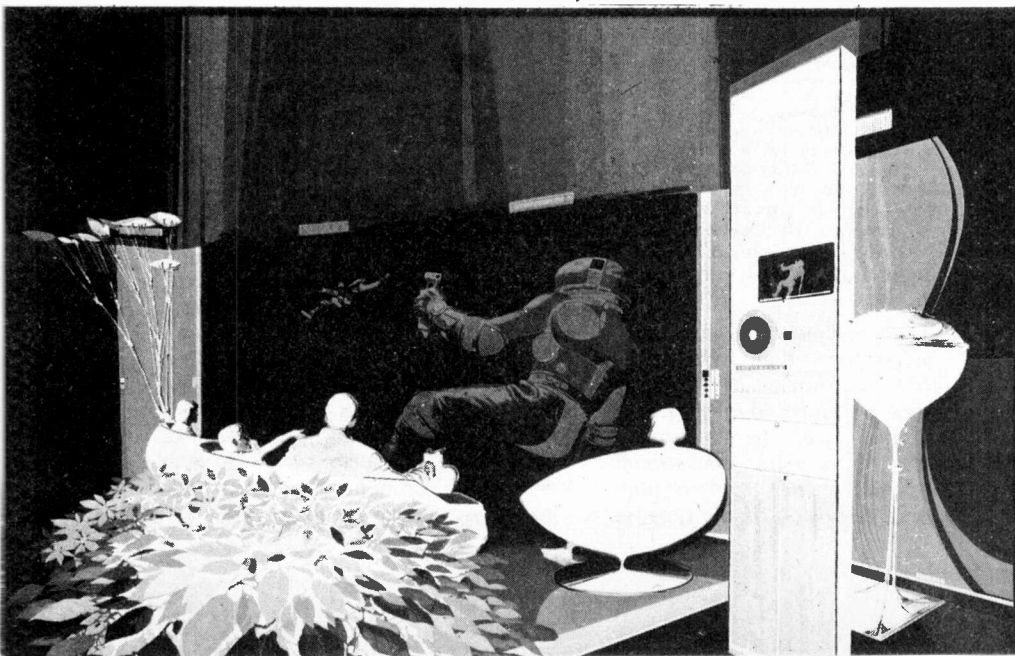Colour TV's like this are possible now but they should be common in most households before the end of the century.



This Room Is Equipped With

Edison Electric Light

Do not attempt to light with match, Simply turn key on wall by the door .

The use of Electricity for lighting is in no way harmful to health, nor does it affect the soundness of sleep.

Fig. 2. This notice demonstrates how our minds need releasing to understand new ideas.

the truth of the predictive framework proposed.

Germanium and gallium were predicted in the same way; before they were known to exist.

Knowing something about the fundamental properties of material before it is isolated in workable quantities does not always assure instant technological use. Silicon was discovered in 1823, germanium in 1866. Both were available to technology at the same time that the thermionic valve grew in importance (1910 onward) as the basis of a new discipline — electronics. It is not surprising that few people could realise in the 1950's that the germanium transistor, then just invented, would so enormously alter our visions by allowing the eventual use of mass produced dirt-cheap electronic systems.

SCIENCE-FICTION

Good sci-fi writers often come remarkably close to the truth about future developments. We cannot objectively assess how the writer arrives at the script but it is fairly safe to assert he or she does so largely by extrapolating current situations into time, throwing in innovations of their own.

Jules Verne and H.G. Wells wrote fiction that seemed fantasy in their time. Verne did it for amusement; Wells as a message. In 1865 Verne wrote "De la terre a la lune"; in 1901 Wells write "The First Men on the Moon". But even before then Cyrano de Bergerac had written two novels of journeys into space using jet propulsion — and that was around 1640.

These writers are able to throw-off the bonds of the establishment, to imagine other societies, other uses of technology. Robots, in mechanical master form, go back at least to Mary Shelley's Frankenstein (1818). To the society of the day such figments of the imagination — they could be little else at that time — must have been a most

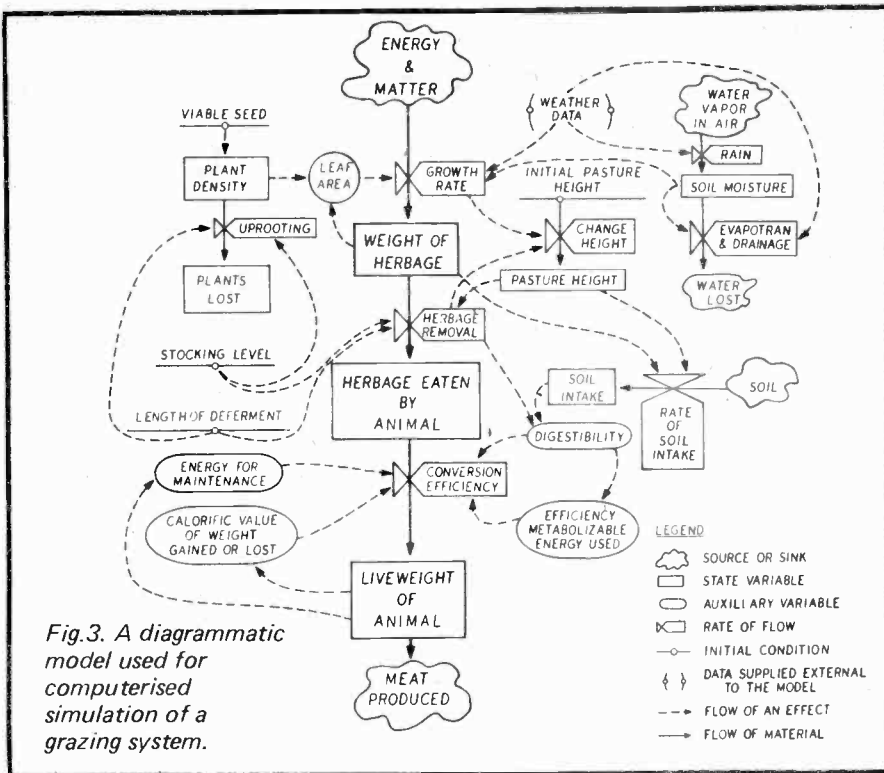


Fig.3. A diagrammatic model used for computerised simulation of a grazing system.

and business with interest arising in government and corporate planning. The methods employed relate to reasonably measurable quantities such as a business operation or advance in a certain kind of technology. It has the merit of being confirmable with time as its standards and norms remain much the same with time.

Systems theory and analysis, dynamic modelling: The system under study is progressively isolated from the rest of its environment. Black boxes are drawn and interconnected such that they represent the input to output changes of the variables flowing around in the total system. The system has inputs, outputs, transfer functions and measured variables as depicted by the example given in Fig.3. The next step is to transform this form of model to a mathematical, rather than notional one, and begin computation to get the dynamic state of each part of the system.

Even the simplest systems handled this may soon tax human powers to handle the data conversions.

frightening concept. Today we regard such horror tales more as humorous recreation than likely fact.

One major difficulty with science-fiction predictions is that we cannot begin to devise tests of confidence of their validity beforehand because this mode lacks an objective scientific basis of arriving at the result. Intuition can be so wrong and 'gut-feelings' are hard, extremely hard, to justify to others.

THE ACADEMIC APPROACH TO FUTURE'S STUDIES

A significant number of Universities and other tertiary teaching institutions offer courses in the various aspects of what is collectively known as future's studies. Many topics qualify for inclusion — technology forecasting and assessment, cross impact analysis, policy studies, demographic projection, statistical prediction, economic forecasting, systems studies, peace studies, morphology, utopian literature, science fiction and even gaming are each relevant to prediction making.

Academic studies — many hundreds of courses exist — attempt to put forecasting on a firm objective basis. There is, however, as yet, little evidence that the various methods are indeed reliable enough to be entirely worth the effort. Key methods in vogue today include the following:

Technology forecasting and assessment (TF or TA): This is used in military

YES SIR 1st class post TONIGHT! We specialise in high spec components with express service for phone customers

HIGH SPEC components FAST!

AGENTS FOR: VERO - ANTEX - BIB MULTICORE SOLDER

- OPEN 9am-5pm 6 days. Phone orders 9am-4pm
- S A E for stock list including pots, Pre-sets, IC's 7400 & CMOS capacitors, plugs, sockets, switches, cable etc.
- Post free envelope for your next order
- SUPER EXPRESS phone service
- Shop at keen prices 6 days per week

AC125 20p	184L 11p	4101 11p
125 20p	187 25p	MM102 32p
127 20p	212a 13p	0A47 8p
128 20p	212L 15p	90 5p
151 35p	213b 12p	91 4p
153 35p	214 15p	200 5p
176 20p	214L 11p	0C28 40p
187 20p	262a 15p	29 56p
188 20p	287 20p	35 80p
AU149 68p	300 35p	44 30p
161 42p	301 34p	71 25p
162 42p	303 35p	DRP12 65p
MC3/P 104p	338 15p	11P29A 41p
AF116 24p	557 9p	30A 56p
117 24p	8CV71 18p	31A 57p
124 30p	72 14p	41A 67p
239 46p	8D123 90p	42A 80p
AU113 150p	124 68p	11S43 35p
8C107 11p	131 36p	ZTX300 13p
107A 12p	132 36p	302 18p
108 10p	139 54p	500 15p
ICL108 6p	156 75p	502 18p
8C108b 11p	8F158 20p	W914 5p
108c 12p	184 25p	4001 5p
109 11p	185 28p	4002 5p
109b 12p	194 10p	4006 9p
109c 13p	196 12p	4006 10p
117 18p	197 12p	4148 5p
142 22p	199 15p	2N2219 20p
143 24p	200 38p	2646 40p
147a 9p	338 34p	29280 13p
147b 10p	8F411 68p	29266 13p
148 9p	8F429 26p	3053 18p
148b 10p	84 22p	3055 80p
149b 11p	88 22p	3702 11p
149c 11p	8F150 17p	3703 10p
154 18p	51 18p	3704 13p
157b 12p	52 18p	3705 10p
177 17p	8Y154 40p	3707 12p
178b 18p	ME0401 18p	3819E 25p
179b 19p	0411 18p	
184b 12p	MF4001 10p	

LINEAR I/Cs

741 33p
LM380/SL60745
LM3900M 69p
NE555 60p
SN76013M £1.50
SN76013M £1.75
SN76023M £1.75
TBA800 £1.49
TBA810S £1.49
TBA820 £1.20
ZM414 £1.35

THYRISTORS

60V 1A 20p
60V TAC1 600
700V 1A 120p BT 106
400V 4A 58p C106 01
500V 6mA 125p BT 109

TRIACS

400V 6A 92p
400V 8A 150p 128000
DIAC BR100 S 25p

DIL SOCKETS

8 pin 13p
14 pin 15p
16 pin 17p

BRIDGES

100V 1A 24p
200V 1A 25p
400V 1A 26p

DIDDIES

50V 3A 13p
100V 3A 15p
200V 3A 18p
400V 3A 21p

RESISTORS 1/8p each

1/2 WATT E12 (5%)
1 ohm-10m ohm

ZENERS (400mw)

BZX83/BZY98 3V3, 3V6, 3V9, 4V3, 4V7, 5V1, 5V6, 6V2, 6V5, 7V5, 8V2, 9V1, 10V, 12V, 13V, 15V, 18V, 30V
All at 12p each

ANTEX BITS FOR MODEL C

Numbers 2, 3, 4, 5, 6, and iron plated
102, 103, 106, all 46p MODEL CCN
1100, 1101, 1102, all 46p, 1106, 72p

LED TIL 209/0.125 0.2"

Red 20p	20p
Grn 29p	29p

Clips for above 1p

Orchard electronics

FLINT HOUSE, HIGH STREET, WALLINGFORD, OXON OX10 0DE
TEL: 0491-35529

Electronics 2000

Mammoth computing ability enables complicated systems to be set going into the future (the time scale being stepped up beyond real time). One example of the use of this form of simulation is when it is employed constantly to check the future stability of nuclear power stations — as based "on past to current" data. But such a system must have correct measurement inputs to give correct answers.

Cross-Impact analysis: This is, in essence, a type of systems analysis because it is based on the premise that "everything is connected to everything else" and has impact on each other.

The users of cross-impact analysis devise a "mathematical matrix that expresses the probability of occurrence of a number of possible developments and represents the direction and strength of the impact one occurrence would have upon the probability of another."

An example of an impact was when silicon became so significant to us as the transistor circuit element. The matrix contains all of the many impacts involved, expressed as probability values ranging from 0 to 1.

Delphi technique: Most people are familiar with the "think-tank" idea of generating ideas. A group of people, each expert in a specific area and each overlapping a little, meet to talk-out a scheme that will fulfil a stated need. Although this concept works reasonably well it only does so if the people involved blend satisfactorily from the human relations and sociological points of view. There is great risk that the individual views become influenced by those of the others.

In a Delphi study the experts do not meet, nor know who else is involved. Each answers questionnaires sent to them by the co-ordinator who has control over the feed-back between experts. The study passes through several 'rounds', as decided by the co-ordinator, until hopefully a consensus viewpoint emerges.

It was first developed in the 1950's by Olaf Helmer, who subsequently became Foundation President of the "Institute for the Future" in Connecticut, U.S.A. Delphi style studies have been used in education, sociology, science, weapons systems, customer choice plus many more. It is also the basis of assessing the worth of research-grant applications which by their nature, are predictions made by the applicant of what is felt should and can be achieved. It is essential that the experts are truly expert in the field



Fig. 4. A 1907 cartoon predicts aircraft will replace the car by 1950.

of interest and that they have the flair for forecasting.

The Delphi method does, however, lack that competitive and inventive situation wherein an idea expands to a maturity by constant innovation working on the basic premise.

Experimental Learning, Creativity, Scenarios, Simulations: These are rather loose academic exercises (soft as opposed to hard thought processes are involved) wherein, as the names suggest, participants exercise artistic, intuitive skills to create new situations. Mock-up models of future cities may be built to investigate their design. Museums of the future exist in Denmark and the U.S. These methods use speculation based on reason and judgement; a game of "if".

For all of the academic effort that has been put into the design of techniques and the now many courses, the situation has been summed up as "some past futurists were amazingly accurate, others amusingly inaccurate", Langley, 1975, U.S.A.

FORECASTING SUCCESSFUL OR NOT?

Some forms of forecasting have been notably successful. Weather forecasts are more right than wrong today. Tides in the seas between Britain and the Continent can be predicted to a point where dangerously high tides can be forecast several days ahead. It was not so long ago that weather forecasting to such precision would have been regarded as fantasy. We must not lose sight of the fact that fantasy is only such because of ignorance of some aspect of physical manifestation. We are more likely, at this instant in time, to be able to correctly forecast well-known physical phenomenon than the ill-defined

sociological issues because we have more knowledge about the deterministic variables.

In this first part, we have explained the various methods of forecasting. Very few of even the most objective methods will, however, tell us much about less tangible things such as the way of life ahead. The various methods are applicable to business and military ventures, to applications where enough parameters of the system are in close enough control of the forecaster.

We now look at some more successes and failures of past forecasting.

Electric Lamp: After a discourse on the difficulties of manufacturing incandescent electric lamps, James Swinburne had this to say in 1904:

"A new invention that wants a great deal of working out has against it all the experience and knowledge gained in old manufacture: so unless it is very much better on the face of it, it is not worthwhile troubling about it."

His article suggested that electric light was not worth the development effort!

Telephone: We all have witnessed how the telephone has changed the style of commerce, how it led to radio and then to the television. But did you know Bell was regarded as an "imposter", a "ventriloquist", "a crank who says he can talk through a wire". The Times, of London, said it was humbug. Lord Kelvin greatly helped Bell by issuing a statement that is regarded as the Charter of Telephony. In it Kelvin wrote:

"With somewhat more advanced plans and more powerful apparatus, we may confidently expect that Mr Bell will give us means of making spoken words audible through electric

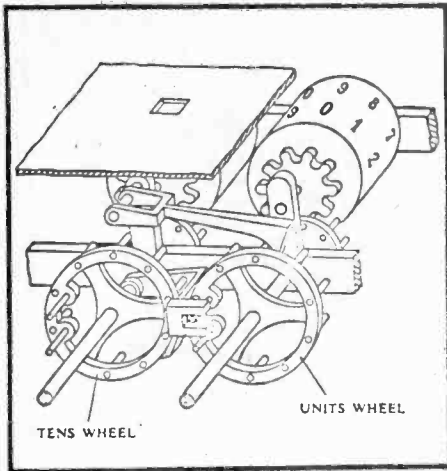


Fig.5a. Sketch of a Pascal calculating mechanism (17th Century).

wire to an ear hundreds of miles distant."

Rockets: In 1955 Lord Thompson wrote:

"It is doubtful if such a large rocket (8000 tons to give one ton freedom of space was predicted) would be practical, though von Braun, the designer of the V₂, has seriously proposed one."

Apollo missions use Saturn rockets weighing over 3000 tons to launch a comparable payload.

Aircraft: A reversible plane was devised in 1922 with two tails, two fuselages and which could reverse direction in flight. Later, in 1932 Captain Dibovsky, a Russian, designed a plane that could rise vertically into the air and could land on a roof-top,

or a river. These ideas were not sound as presented then, but today we have the Hawker-Harrier jump-jet that achieves at least part of the aim of these earlier inventors. In 1907 the cartoon, shown in Fig.4, appeared predicting the decline of the car in favour of the airplane. It was drawn, however, just one year before the "Tin-Lizzie" put motor transport within the working-man's reach.

Writing: And who would have thought that the 1950's new-fangled writing pen of the Biro brothers would have found such overwhelming acceptance in our civilisations.

THE VARYING PACE OF DEVELOPMENT

To illustrate the varying rate of change experienced in a development let us look at some pictorial views showing successive development of the pocket-sized calculator.

The pocket calculator begins its history with the Ancient Greeks who made a calendrical computer in the tradition of planetarium construction (known as the Antikythera mechanism and dated ca. 80 B.C.). The abacus is also extremely old in origin. Other mechanical machines, such as Pascal's many variations shown sketched in Fig.5a, followed — employing small degrees of innovation and change. The real change in attitude came with the Babbage engine developments starting in '1830's. His ideas were sound but machines such as that shown in Fig.5b could not be built at the time. By the turn of the century workable mechanical calculators were in common use. Figure 5c shows the "Millionaire" which was first marketed

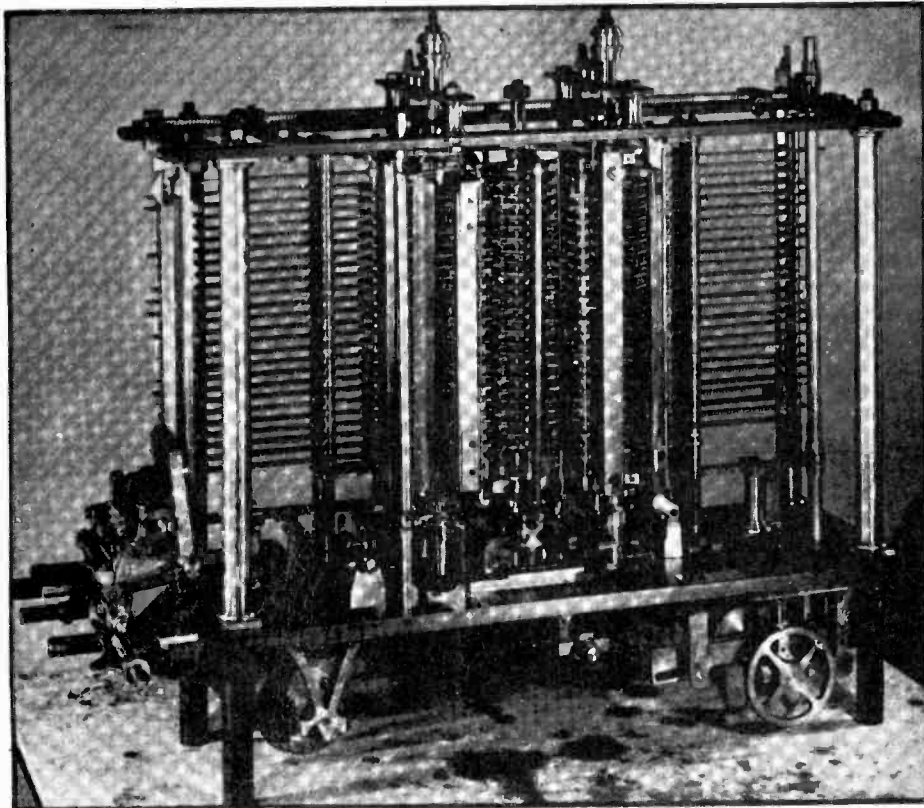


Fig.5b. A Babbage engine: by incorporating storage the design significantly advanced computer technology.


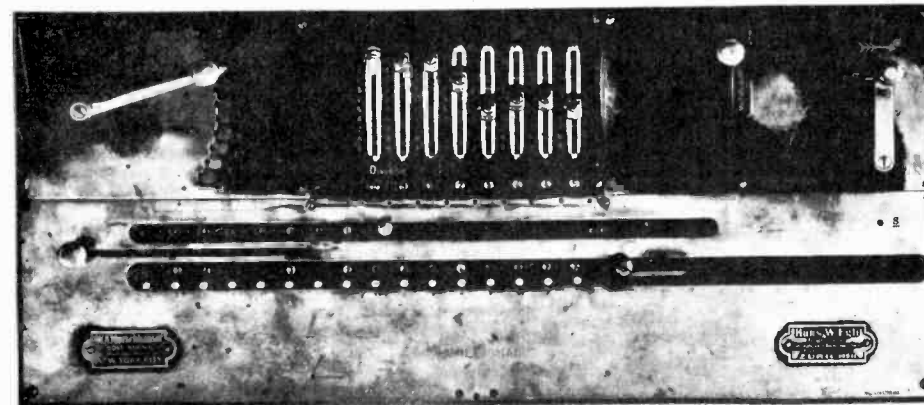


Fig.5c. Working face of 'Millionaire' calculating machine (1890's).

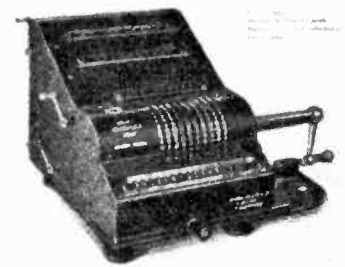


(German text describing the calculator's features and operation, including details about its accuracy and construction.)

Fig.5d. Handcranked mechanical calculators were common-place in the early part of this century.

Metac Digital Watches

NEW TO METAC

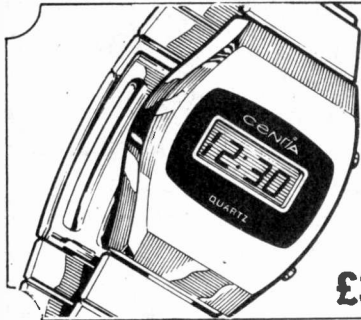


TLC6 TV LIQUID CRYSTAL ELECTRONIC WATCH

Continuous display with backlight. Hours, mins, secs, date, month. Automatic 28, 30, 31 day calendar. Metal bracelet in choice of gold or stainless steel. Slimline case.

£33.95 No more to pay
2 year guarantee

NEW TO METAC

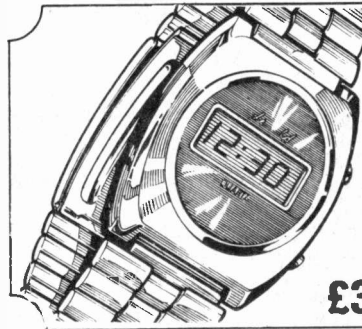

TLC6 B LIQUID CRYSTAL ELECTRONIC WATCH

Continuous display with backlight. Hours, mins, secs, date, month. Automatic 28, 30, 31 day calendar. Metal bracelet in choice of gold or rhodium. Slimline case.


£33.95 No more to pay
2 year guarantee



TLE5EA QUARTZ CRYSTAL ELECTRONIC WATCH

8 separate functions, Hours/minutes/day/date/a.m./p.m. indicators/Auto-Fade. Available in 18ct. Gold/Rhodium plated. Slimline Case.

£18.95 No more to pay
2-year guarantee

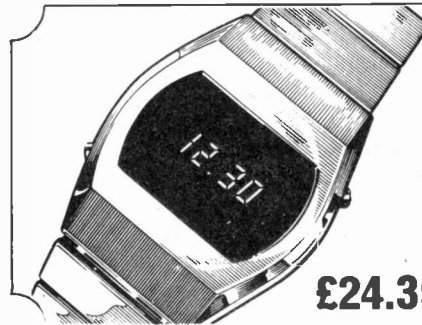


TLE5 TV QUARTZ CRYSTAL ELECTRONIC WATCH

£24.35 No more to pay
2 year guarantee

A QUALITY WATCH
You save £15.00 on retail price

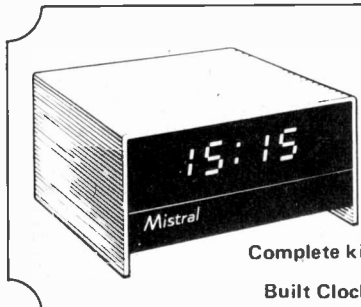A GENUINE BARGAIN
You save £17.00 on retail price



'MISTRAL' DIGITAL CLOCK

In kit or built form. Large 4 digit display. Push button setting. 12-24 hour read out. Pleasing green display. Pulsating second indicator. Build in 1 hour.

Complete kit **£11.07** Incl. V.A.T.
Built Clock **£14.95** Incl. V.A.T.

BRITAIN'S TOP SELLING DIGITAL ELECTRONIC CLOCK



Bright Planar Gas digit display. A.M./P.M. Indicator and flashing second indicator, 24 hour bleeper alarm, 5 minute repeater. Mains failure indicator. 5" across x 3 1/2" deep. Attractive white case. Thousands sold.

Recommended Retail Price £17.95

Our Price **£13.95** Incl. V.A.T.

IMPORTANT. 2 YEARS' UNCONDITIONAL GUARANTEE IS WHAT IT SAYS. A COMMITMENT BY US TO REPAIR OR REPLACE AT OUR DISCRETION ANY METAC WATCH OR CLOCK FAILING TO GIVE SATISFACTORY SERVICE DURING THE FIRST 2 YEARS OF LIFE. THEREAFTER TO SERVICE THE PRODUCT AT A FAIR AND REASONABLE PRICE.

STOP PRESS NOW AVAILABLE. AMAZING VALUE LIQUID CRYSTAL ELECTRONIC DIGITAL WATCH. HOURS, MINS, PULSATING SECS. METAL BRACELET. £24.50 COMPLETE. NO MORE TO PAY

METAC IS EXPANDING

Now you can buy Metac quality watches and clocks direct from our showrooms at Mail Order Prices.

Visit:

METAC, ELECTRONICS AND TIME CENTRE
67 HIGH STREET, DAVENTRY, NORTHANTS
and see for yourself the full range of top quality watches, clocks and other consumer electronic products.

Watch out for announcements of Metac shops opening in your area.

Stockists of all types of electronic watch batteries.

REMEMBER with every WATCH you get METAC SUPER COVER. Full 2 years guarantee. Two year replace or repair if faulty. Free Calibration check 1st, 2nd & 3rd year. Free Technical advice.

To METAC INTERNATIONAL, 67 High Street, Daventry, Northants. Tel. 03272 76545.

Please supply the following:—

Name

Address

I enclose cheque/Postal Order/Money Order

I wish to pay by Barclay Card/Access and my number is

Signature

Mail Order Customers. Trade enquiries welcome.

MPU BITS

- SC/MP Introkit: 256 bytes RAM, 512 byte PROM with KITBUG debugging program, needs TTY device for operation **£92.50**
 SC/MP SCRUMPI: 256 byte RAM, 16 switches, LEDs, and interface chips on 5½" x 6" PCB. Requires simple power supply or batteries **£64.81**
 SC/MP Chip with data sheet **£18.50**
 ME6800 Kit: Uses 6800 MPU. Requires TTY **£135.00**
 FS Kit: Mostek F8 MPU, requires TTY **£165.00**
 MM2112 256 x 4 bit RAM **£4.30**
 2513 Character Generator, u/c ASCII **£9.00**

HARDWARE

- Power Supply: P197 gives 5v at 2A, -5, -12v, suitable for many MPU systems, P197 Kit **£15.50**
 Keyboard Kit: 55 keys, upper/lower case options, KDP 5 Kit **£42.00**
 Printer: 40 column dot matrix printer with interface for parallel ASCII input, PR-40 kit **£225.00**
 Floppy: SA800 or SA801 floppy disk drive, disks and interface, built, not kit **£625.00**
 Minifloppy: SA400 mini disk drive, disks and interface, delivery end of year **£495.00**

BOOKS, DATA

- SCRUMPI Data **75p***
 SC/MP Technical Description **£1.95***
 SC/MP Programmers Guide **£6.30**
 6800 Data (Xerox) **75p***
 F8 Data (Xerox) **75p***


(*Free with appropriate kits)

CONSULTANCY

Bywood would be pleased to quote for hardware/software solutions to your design problems.

GET HUNG UP!

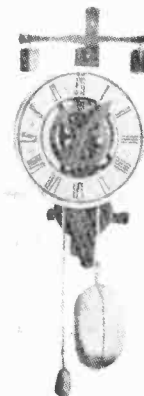Our new range of clock kits is based on designs hundreds of years old. These clock kits use wood, stone and iron to reproduce authentic "olde worlde" wall clocks in full detail. The kits contain all you need including glue, screws, etc.; and very comprehensive instructions. This range complements our fully electronic clock kits.



PRICES (All inclusive)	KIT	BUILT
Gothic Clock Kit—Diam. 6½"	£23.95	£36.50
Rotating Dial Kit—Diam. 6"	£19.95	£32.50
Wrought-Iron Kit—Diam. 5½"	£46.35	£69.50
Wooden Wheel Kit—Diam. 6½"	£31.50	£45.25
Knight Clock Kit—Diam. 7½"	£39.50	£62.45
Oak Foliot Kit—Diam. 14"	£89.50	£125.00

(As illustrated)

For coloured Brochure please send 15p stamps. Completed clocks can be seen at our offices.

BYWOOD

BYWOOD ELECTRONICS
 68 Ebbens Road
 Hemel Hempstead
 Herts HP3 9QRC
 Tel. 0442 62757

PRICE LIST

CLOCK CHIPS

ALL PRICES EXCLUDE VAT AT 8%

NATIONAL

MM5309 7 seg + BCD with reset	1.9
MM5311 7 seg + BCD	5.69
MM5312 7 seg + BCD 4 digit only	5.69
MM5313 7 seg + BCD	4.88
MM5314 7 segment	5.69
MM5315 7 seg + BCD with reset	4.88
MM5316 Non-mpx alarm clock	5.69
MM5318 7 seg + BCD (external digit select)	10.17
MM5371 Alarm clock 50Hz	3.36
MM5377 Car clock, crystal controlled, LCD	8.14
MM5378 Car clock, crystal controlled, LED	7.21
MM5379 Car clock, crystal controlled Gas discharge	6.73

MOSTEK

MK50250 Alarm clock (12Hr+60Hz/24Hr+50Hz)	5.60
MK50253 Alarm clock (12Hr+50Hz 24Hr+50Hz)	5.60
MK50204 Stopwatch/Calculator	11.19
MK50395 UP/DOWN Counter—6 Decade	14.50
MK50396 UP/DOWN Counter—HHMMSS	14.50
MK50397 UP/DOWN Counter—MMSS 99	14.50

CALTEX

CT7001 Alarm/calender 7 segment	7.30
CT7002 Alarm/calender BCD	9.00
CT7003 Alarm/calender 7 seg. Gas discharge	9.00
CT7004 Alarm/calender 7 seg	9.00

GENERAL INSTRUMENTS

AX5-1202 4 digit 7 seg	4.76
AY5-1230 on-off — alarm, 7 seg	5.25

MHI CLOCK KITS

MHI-5309	1.9	MHI-50396	19.50
MHI-5311	7.35	MHI-50397	19.50
MHI-5314	7.35	MHI-7001	10.00
MHI-5318	6.60		
MHI-5378	7.35	MHI CASE Please include 25p post + packing)	2.95
MHI-50250	15.10		
MHI-50253	8.35	SOCKETS	
MHI-50204	8.35	18 pin	0.60
MHI-50395	14.00	24, 28 or 40 pin	0.60
	19.50	Soldercon strip sockets	0.30

DISPLAYS

LITRONIX

DL707, 704, 701	1.48
DL727, 728, 721	3.75
DL747, 746, 750	2.45

LITRONIX CLASS 11 PRODUCTS

DL707E, 704E	0.70
DL727E, 728E	1.80
DL747E, 750E	1.50

CASES (WITH PERSPEX SCREEN)

VERO 1 8" x 5½" x 3"	} £2.95 + 25p P&P
VERO 2 6" x 3¼" x 2¼"	

MHI DISPLAY KITS

MHI-707/4 (digit) 0.3"	1.9	MHI-727/6 0.5"	12.00
MHI-707/6 0.3"	6.60	MHI-747/4 0.6"	9.80
MHI-727/4 0.5"	9.50	MHI-747/6 0.6"	14.70
	8.50		

PAYMENT TERMS

Cash with order. Access, Barclaycard (simply quote your number and sign) Credit facilities to accredited account holders. Pro-forma invoices can be issued.

Please send 20p for post and packing.

ALL PRICES EXCLUDE VAT AT 8%
 (EXCEPT MECHANICAL CLOCKS AS ABOVE)

BYWOOD

BYWOOD ELECTRONICS
 68 Ebbens Road
 Hemel Hempstead
 Herts HP3 9QRC
 Tel. 0442 62757

HEART-RATE MONITOR

An invaluable tool for the bio-feedback experimenter or for the assessment of athletes.

THERE ARE MANY METHODS of measuring heart rate ranging from feeling the pulse, to chart recordings via an electrocardiograph. Other methods include monitoring the electrical potential which triggers each heart beat; resistance changes due to changes in blood flow; and change in the volume of blood in blood vessels with each beat.

The detection of electrical signals associated with heart action is the best and most reliable method especially if the subject is exercising. However good connection must be made to the body by special electrodes and conductive paste to ensure very low contact resistance. The method is messy and requires skill in attaching the electrodes.

Similar electrodes are required to measure changes in body impedance and in addition the measurement is usually made by passing an electrical current through the body. This poses a considerable safety hazard as any fault in the insulation of mains-operated equipment can cause lethal currents to pass through the body. For this reason we did not use the method and we strongly recommend that experimenters do not either! With very well attached electrodes even small voltages can produce lethal currents.

LIGHTING UP TIME

This leaves us with the light-beam method, two variations of which are in common use. One is to pass light through flesh to a bone where it is reflected to a photo sensitive device adjacent to the lamp. This has the advantage that

the sensor may be taped to any convenient part of the body, eg, the forehead, but the signal generated is very low. A second method still uses a light source and photo-sensor but the light is passed to the sensor through some thin section of flesh — the fleshy part of a finger or the ear lobe work very well. As there are no electrical contacts with the body this type of sensor is very safe to use and was therefore chosen for use in the ETI meter.


Specific Circuitry: While the detection and amplification of the signal due to heart action can be done with normal linear amplifiers the frequencies involved are very low. Measures must be taken to reject frequencies other than those of interest and to overcome dc offset

problems due to differences in the path lengths depending on where the probe is attached.

Thought must also be given to the type of readout to be used. Were a digital readout to be used, counting of the rate would have to be performed for a full minute in order to obtain a one beat resolution and a new reading could only be taken at one minute intervals if normal frequency measurements are used. However, this problem may be overcome by measuring the period between the pulses and converting this to a frequency which can then be measured using digital logic to obtain a reading on every beat. This is quite valuable in a machine used for diagnostic work where information on the variations in regularity of the interval between adjacent beats can be quite meaningful. However, the method is complex, and expensive and requires some other type of sensor than the light beam type to obtain the accuracy required. As our meter is not intended for diagnosis the digital technique was rejected in favour of a simple analogue meter display.

CHOICE INTEGRATION

Even with an analogue readout we still have a choice of operating methods. We can measure the period between beats as previously discussed or we can use it as an integrating frequency meter. The latter method requires about 25 seconds for the reading to stabilise initially but thereafter it will follow variations in heart rate quite faithfully. The measurement of period between each beat is more rapid in its response but requires more

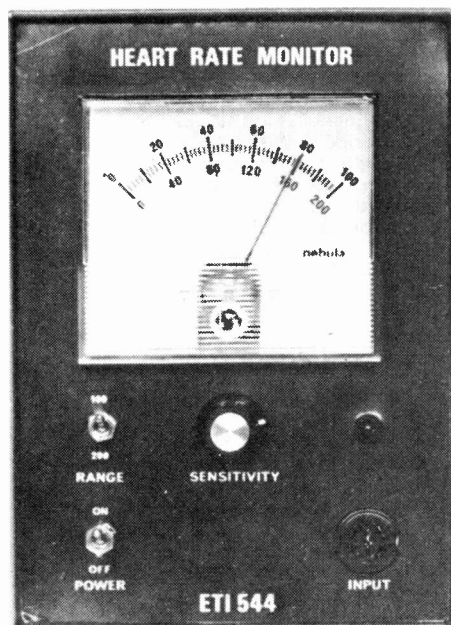

HEART-RATE MONITOR

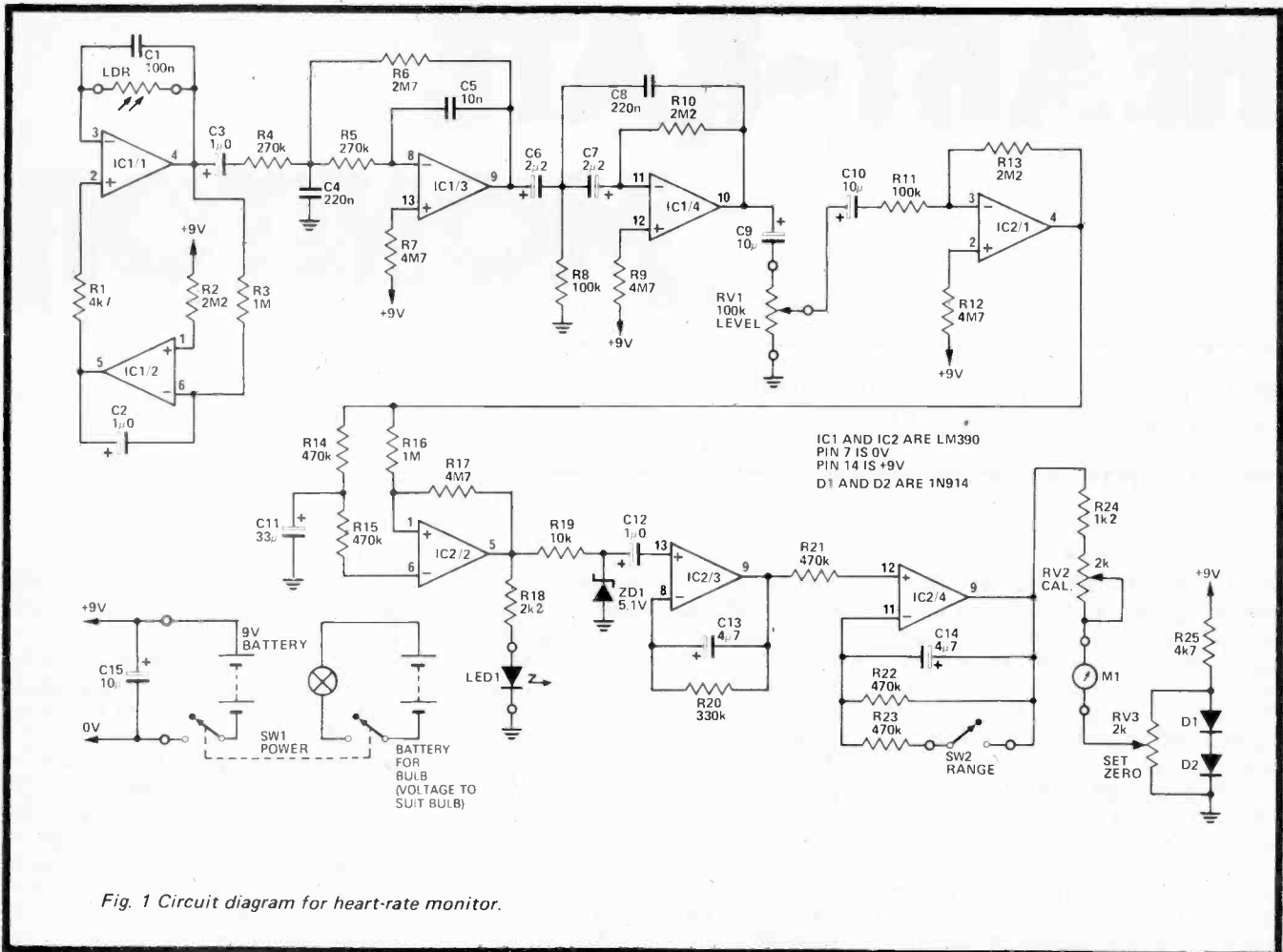


Fig. 1 Circuit diagram for heart-rate monitor.

How it works

The sensor consists of a light bulb and a light-dependant resistor mounted in a clothes peg in such a way that they may be positioned on opposite sides of a small section of flesh such as the ear lobe or a finger. As the heart beats it pumps blood through all the blood vessels of the body which swell. The density of the body therefore changes giving rise to a change in light transmission through the section of flesh to which the sensor is clipped. The LDR which is subject to this change of illumination therefore changes its resistance, and it is this change in resistance which eventually drives the meter. As the actual amount of light transmitted varies greatly from person to person and according to the thickness of flesh between the sensors, some method of stabilising the working base line is required.

The stabilising function is performed by IC1/1 and IC1/2. Due to the operating mode of IC1/1 the current through the LDR is always equal to the current through R1. The current in R1 is automatically adjusted by IC1/2 such that the output of IC1/1 sits at about four volts (as the current in R2 must equal the current in R3). Capacitor C2 prevents the current in R1 from changing quickly and hence, relatively fast changes due to heart-beat (which cause changes in LDR resistance) are detected.

As the output of IC1/1 is at a very low

level this signal must be amplified by IC1/3 and IC1/4 by about 40 dB. A low-pass filter which limits the rate, which can be detected to about 250 beats per minute, is also formed by IC3/3; and a low-pass filter which cuts off all frequencies below 30 beats per minute is formed by IC1/4. These filters eliminate 50 Hz pickup and any other signals generated by slow movement of the body which could also interfere with the measurement. As the actual signal can vary over a range of 20 dB with different people a level control is incorporated, after IC1/4, and the output from this control is amplified by 26 dB in IC2/1.

The output of IC2/1 has now to be squared up before it can be used. This is performed by a Schmitt trigger formed by IC2/2 where the necessary positive feedback is supplied by R17. Both inputs are biased from the output of IC2/1 but the ac signal is prevented from reaching the negative input by capacitor C11. An LED driven by the output of IC2/1 is incorporated to give a visual indication that heart beat is actually being detected.

It is now necessary to convert the square wave from the output of IC2/2 into a voltage proportional to heart rate and this is the purpose of IC2/3. Each time the output of IC2/2 goes high, capacitor C12 is charged up via R19 and the positive input from IC2/3. By the nature of the IC this current has to be balanced by a corre-

sponding current in the negative input. This current can only be supplied by the output going high and supplying current via C13. This charges C13 up a little. On the negative edge of the output from IC2/2 the capacitor is discharged via the protection diodes on the input of IC2/3. If R20 was not present C13 would continue to charge up on each input pulse, however R20 bleeds a little current from C13 and the charging stops when it reaches a voltage where the amounts of charge and discharge become equal. The voltage reached will of course now be proportional to the heart rate. The amount of ripple on this voltage is determined by the time constant of R20 and C13 and this is selected as a compromise between response time and ripple. The zener diode is used to stabilise the output of IC2/3 against any changes in supply voltage.

The last section of IC2 is used as a buffer amplifier which provides the two ranges required along with an extra stage of filtering. The output of IC2/4 is metered to give a direct readout of heart rate. A resistor and trimpot in series with the meter allow the instrument to be calibrated and the potentiometer RV3 provides a zero correction (as the output of IC2/4 is not at zero volts but at about 0.8 volts). Diodes D1 and D2 stabilise this against supply variations.

Parts List

Resistors all 1/2w 5%

R1	4 k7
R2	2 M2
R3	1 M
R4,5	270 k
R6	2 M7
R7	4 M7
R8	100 k
R9	4 M7
R10	2 M2
R11	100 k
R12	4 M7
R13	2 M2
R14,15	470 k
R16	1 M
R17	4 M7
R18	2 k2
R19	10 k
R20	330 k
R21-R23	470 k
R24	1 k2
R25	4 k7

Potentiometers

RV1	100 k log rotary
RV2	2 k Trim.
RV3	2 k Trim.

Capacitors

C1	1 μ F 35V electrolytic
C2	100 n polyester
C3	1 μ F 35V electrolytic
C4	220 n polyester
C5	10 n "
C6,7	2 μ 25V electrolytic
C8	220 n polyester
C9,10	10 μ 35V electrolytic
C13,14	4 μ 25V electrolytic
C15	10 μ 16V electrolytic

Semiconductors

IC1,2	LM3900
D1,2	1N914
ZD1	5.1V Zener 400mW
LED1	


Miscellaneous

Meter	1mA FSD
PC board	ETI 544
Box to suit	
9V battery	
2 x 9V batteries	
One single pole switch	
One double pole switch	
LDR ORP12 or similar	
12V 30mA bulb	

CONSTRUCTION

There is no need to use the box that we used either — any suitable one will do. Just use the wiring diagram supplied to connect up the unit.

The sensor was made from a spring clip type of clothes peg, by mounting the bulb on one leg of the peg and the LDR on the other. Holes must be provided in the peg so that the light can pass through to the LDR. Fix the bulb and LDR into position with a little epoxy cement. The area around the rear of the LDR should be painted black or covered with tape to prevent all light other than that from the bulb reaching it.

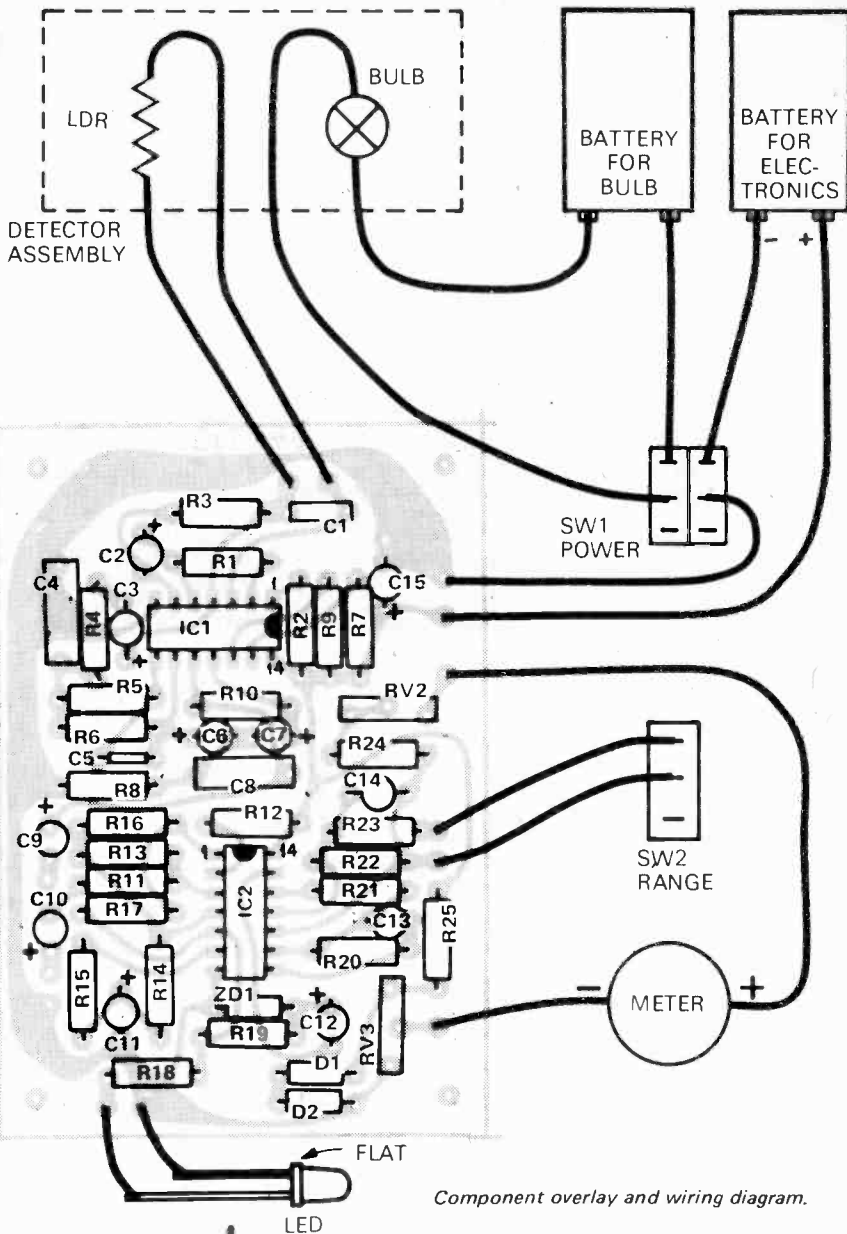

Component overlay and wiring diagram.

complex circuitry and is very responsive to noise 'glitches' or to phenomena other than heart beat. Furthermore the scale for such an instrument is non-linear and wrong reading. That is high readings are at the left of the scale and vice versa. For these reasons the integrating frequency meter was chosen as the cheapest and most effective method for our particular application.

PROTOTYPE PROBLEMS


Our original prototype was built with 741 type operational amplifiers but in the final version we used the LM3900 which contains four Norton type operational amplifiers in the one package. This is a very economical solution as although the

circuit is quite complex in concept, the whole device only uses two inexpensive ICs.

In the development of the circuit for this instrument a laboratory power supply was used. However, when the completed board was mounted into its case and run from batteries it worked alright until the batteries had been used for a while and then problems were encountered. The unit would just not count correctly. After much experimentation it was discovered that when the Schmitt trigger operated the power rail changed by about 10 millivolts or so and this modulated the bulb thus generating a spurious pulse.

Having located the problem it was a simple matter to cure it — just run the bulb from a separate battery.

HEART-RATE MONITOR

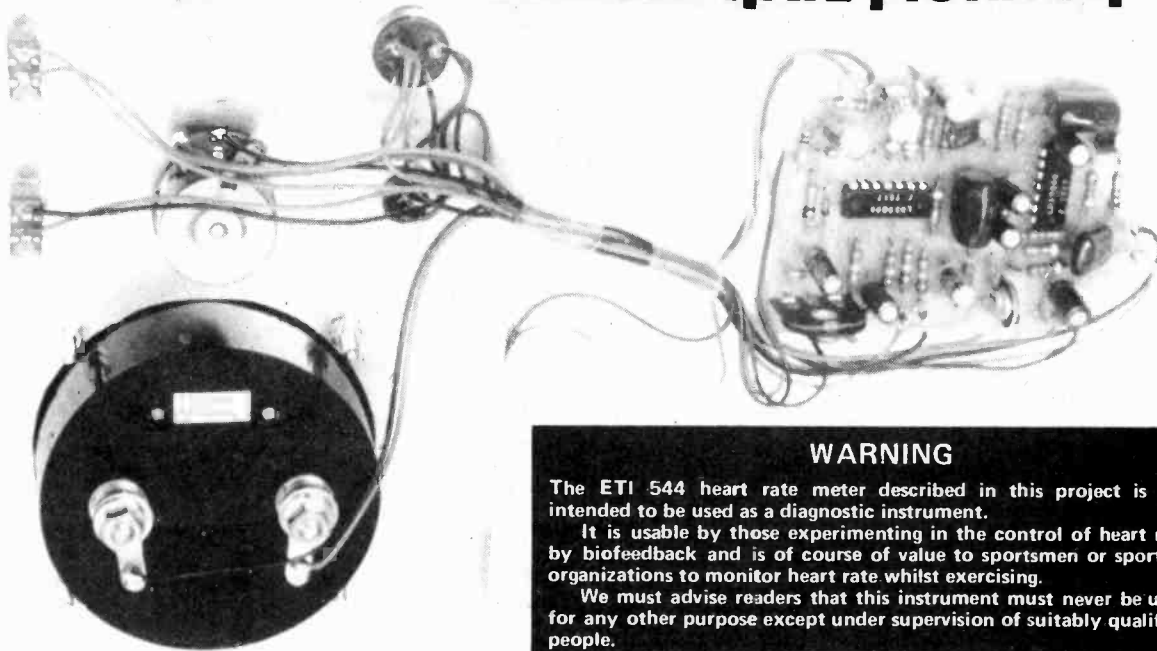

WARNING

The ETI 544 heart rate meter described in this project is not intended to be used as a diagnostic instrument.

It is usable by those experimenting in the control of heart rate by biofeedback and is of course of value to sportsmen or sporting organizations to monitor heart rate whilst exercising.

We must advise readers that this instrument must never be used for any other purpose except under supervision of suitably qualified people.


USING THE MONITOR

To use the monitor simply clip the sensor to the ear lobe or to the fleshy part of the finger or thumb. Now adjust the sensitivity upward until the LED just starts to flash

regularly — indicating that heart beat is being detected reliably. The reading on the meter will start to rise and will become stable after about 25 seconds. Hereafter the reading will faithfully follow variations in heart rate.

Note that the finger or thumb should not be moved whilst taking a reading as this will cause a change in the flesh — which can be interpreted as a spurious heart beat thus giving an erroneous change in the indicated rate. ●

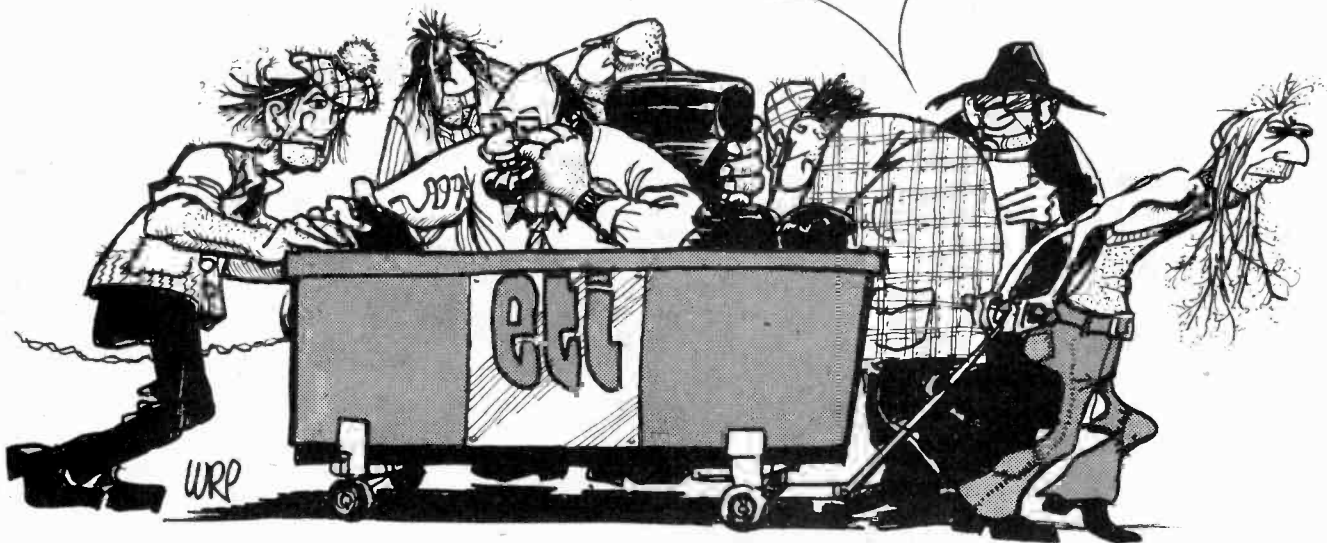RIGHT LADS - DROP THIS ONE
AT 25-27 OXFORD STREET
LONDON W1R 2NT - ETI
HAS MOVED.



MAINS TRANSFORMERS PRI 240v sec. 27/0/27v at 800 m/a. £2.35 . P P 50p. PRI 110/240v sec 50v at 10 amps. £10.00 . P P 50p. P P 50p. PRI 110/240v sec 50v at 10 a.ps. £10.00 . P P 50p. PRI 110/240v sec 20/21/22v at 8 amp. £6.00 . P P 50p. PRI 110/240v sec 23/24/25v at 10 amp. £7.00 . P P 50p. PRI 110/240v sec 24/40v at 1 1/2 amp £1.90 . P P 60p. PRI 240v sec. 20/40/60v at 2 amp. £3.00 . P P 70p PRI 240v sec. 20v at 2 1/2 amp. £2.00 . P P 65p PRI 240v sec 18v at 1 1/2 amp and 12v at 1 amp. £2.25 . P P 50p PRI 240v sec 18v at 1 amp £1.10 . P P 35p	CIRCUIT BOARD P C B 1/16 1 oz COPPER	S-DECS AND T-DECS S-DEC £1.90 T-DEC £3.60 U-DEC A £4.20 U-DEC B £6.90 } P P 25p
12 volt MINI UNISELECTOR 11 way, 4 bank (3 non-bridging 1 homing). £2.50 . P P 35p	FORMICA Dim 8.4 x 7.7 in 3 pcs. 80p. Dim. 9.4 x 8.1 in 3 pcs. 90p. Dim 10.1 x 7.9 in 3 pcs. £1.00. Dim 13.1 x 9.4 in 3 pcs. £1.20. Dim 17.0 x 9.0 in 2 pcs. £1.20. } P P 35p	FIBRE GLASS BARGAIN PACK 200 sq in single & double sided pieces £1.25 . P P 25p
24 volt MINI UNISELECTOR 11 way, 6 bank (5 non-bridging, 1 bridging) £2.00 . P P 35p	BARGAIN PACK 10 pcs. 10.1 x 7.9 in. Plus free 1/2 lb etching Xtals. £3.10 . P P 45p	HIGH CAPACITY ELECTROLYTICS 250mfd/63 volt. 20p. P P 8p 100mfd/100 volt. 70p. P P 25p 2200mfd/100 volt. 90p. P P 25p 4700mfd/25 volt. 65p. P P 20p 6800mfd/16 volt. 50p. P P 15p 10,000mfd/25 volt. 75p. P P 25p 47,000mfd/40 volt. £2.00. P P 50p 100,000mfd/10 volt. £1.50. P P 50p 160,000mfd/10 volt. £2.00. P P 50p
SIEMENS MINIATURE RELAYS 6v 4c/o with base. 65p ea 24v 2c/o with base. 50p ea	FIBRE GLASS P.C.B. Dim. 6 x 6 in. 50p each. Dim. 12 x 6 in. 75p each. Dim. 12 x 12 in. £1.30 each. Equals less than 1p sq. in. } P.P. 15p	3 GANG TUNING CAPACITOR 8 5pf to 320pf. 80p. P P 20p
MAINS RELAY 240v 3 c/o 10 amp contacts £1 with base	DOUBLE SIDED P.C.B. FIBRE GLASS 6 x 6 in. 40p. 12 x 6 in. 65p. } P P 15p 12 x 12 in. £1.20.	MINIATURE METERS 500 micro-amp (level-stereo beacon, etc) scaled half black/half red Size 1 x 1 in. 65p. P P 15p
MINIATURE RELAYS (1 1/2 x 1 1/4 x 1/2) 24v. 4 c/o 40p.	ETCH RESIST PENS 55p. P P 5p	A.M. F.M. TUNING METER 125.0-125 uA. edgewise 1 1/2 x 1/2 £1.10.
OVERLOAD CUT-OUTS Panel mounting 800 M/A 1 8 amp. 10 amp 55p ea	FERRIC CHLORIDE ETCHING XTALS 1 lb makes 1 litre pack, 70p. P P 35p 5 lb makes 5 litre pack, £2.65. P P 65p.	SIGNAL STRENGTH METER 260 uA (illum) Edgewise 1 1/2 x 1/2 £1.10.
SCR-THYRISTOR 1 amp 400 P I V 35p. 5 amp 400p P I V 35p.	PRINTED CIRCUIT KIT The no frills all value kit. Containing 4 pcs 8 x 7 Formica laminate 1 pce 6 x 6 Fibre glass laminate 1 lb Etching Crystals, 50 c c. Resist ink. with instructions £2.40. P P 65p	OUTPUT METER CLEAR PLASTIC 500 uA 1 1/2 x 1 1/2 square £1.30.
EDGE CONNECTOR 54 way 1 vero size etc Can easily be cut to any length. 55p. P P 10p Side Guides to suit the above 15p ea	BLUE P.C.B. INK Etch resist use with any pen. Much cheaper than ready loaded pens 50 c c 55p. P P 10p	KINNIE COMPONENTS , 10 NELMES WAY, HORNCHURCH ESSEX RM11 2OZ HORNCHURCH 45167 MAIL ORDER ONLY. PERSONAL CALLERS BY APPOINTMENT

MORE SUPER EASY TO CONSTRUCT KITS

Doram kits contain everything down to the last nut.



£6.50 +H

SOUND TRIGGERED

Triggers flashgun when mic picks up sound. Sensitivity may be varied over a wide range enabling a multitude of action photos to be obtained. Triggers most popular flashguns.



£36.95 +H

SOUND ONLY

Picks up UHF signals from the transmitter and relays this through your hi-fi equipment.



ONLY £29.95 +H

PA/Guitar Amp

A fabulous easy to build Amp that kicks out 50W RMS into 8 ohms with 0.15% total harmonic distortion.

- ★ Rugged construction
- ★ High sig noise ratio
- ★ Output short circuit proof
- ★ Two inputs allows mix
- ★ Base & Treble boost controls



£19.77 +S

TV PATTERN GENERATOR

Generates test patterns for TV sets. Includes test patterns for all major TV sets. Includes test patterns for all major TV sets. Includes test patterns for all major TV sets.

bumper pack kit brochure

ONLY 25p INC POST



DORAM


DORAM ELECTRONICS LTD
 P.O.Box TR8,
 Leeds LS12 2UF.

PLEASE PRINT BLOCK CAPITALS
 ETI/12/76

NAME _____
 ADDRESS _____
 POST CODE _____

Enclose 25p please sent by cheque or postal order. Do not send by cash. Overseas orders accepted for N. Ireland and base add. Do not send by air parcel or surface mail.

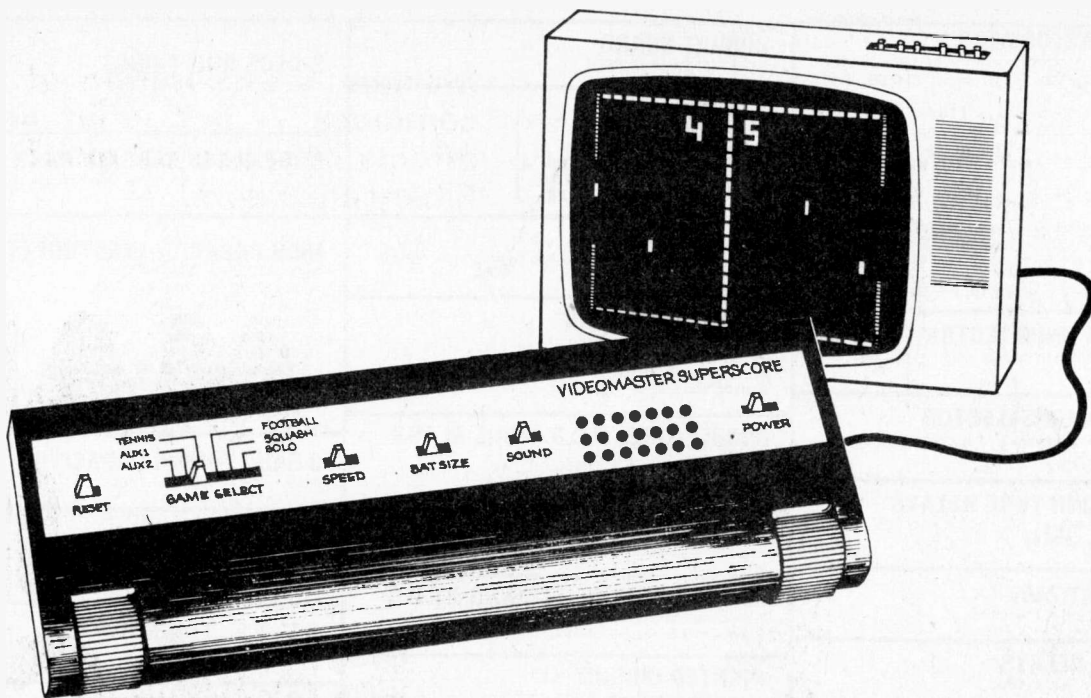CUSTOMERS ORDERING KIT BROCHURE TOGETHER WITH THE DORAM EDITION 3 CATALOGUE CAN OBTAIN THE PAIR FOR 70p, AND RECEIVE TWO 25p VOUCHERS FREE. An Electrocomponents Group Company



Here's the remarkable new **VIDEOMASTER**TM Superscore Home TV Game Get it together for only £24.95

Available to you in kit form at the same moment as its national launch, the brilliant new Videomaster Superscore contains the latest product of MOS technology: a TV game chip.

The logic contained in it had previously to be generated by 100 TTL devices. Now it is condensed into one 28-pin chip.

This all-new Videomaster plugs into your 625-line UHF TV set (for overseas customers having VHF sets we can supply the necessary VHF modulator) to give you four exciting games (including tennis and football) and two future game options. It features on-screen digital scoring, realistic hit sounds, two bat sizes, two

ball speeds, automatic serving and much more. It runs on six 1½ volt SP11 type batteries (not supplied).

The Videomaster Superscore kit costs only £24.95 including VAT (recommended retail price of the ready built model is over £40.00) and comes complete with ready-tuned UHF or VHF modulator, circuit board with printed legend, all resistors, transistors and diodes, built-in loudspeaker, socket for mains adaptor, and, of course, the TV game chip itself.

Easy to put together the Superscore has full assembly instructions, circuit diagram and circuit description. Don't miss this chance to own the newest electronic game at such low cost.

POST TODAY TO:

Videomaster Ltd 14/20 Headfort Place, London SW1X 7HN



Please send me (insert No. requ'd).....Videomaster Superscore Kits at £24.95 (inc. VAT & P&P in UK) or £23.10+£4.00 for P&P overseas)

I enclose my cheque/money order* for £.....

VHF modulator required YES/NO*


NAME _____

ADDRESS _____

ALLOW 21 DAYS FOR DELIVERY

ETI 68

* delete as necessary

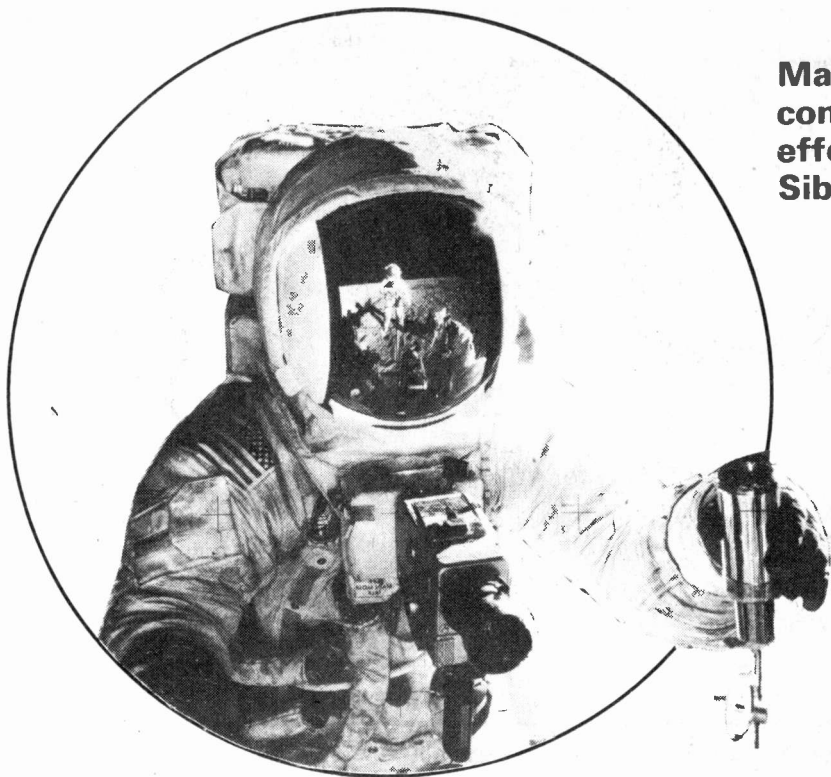

Mankind's exploration of space continues — but what are the effects of space on man? Bruce Sibley considers.

MAN IN SPACE

BIOMEDICAL aspects of space flight are less publicized than many other phenomena associated with the exploration of space. It is the purpose of this article to attempt to 'fill-in' this gap and acquaint the reader with some possibly fascinating facts.

There are three main biomedical objectives. First, to determine how long the human organism can be exposed to the hazards of space without suffering physical or psychological harm. Secondly to determine which agents are responsible for any physical or psychological deterioration, and thirdly to discover and develop protective and preventive techniques to combat and nullify such agents.

HEARTS OF AMERICA

The combined Mercury, Gemini, and Apollo space programmes, undertaken by the Americans between 1961 and 1975, have provided many thousands of man-hours of space environment experience. Generally, the effects of human beings were less serious than expected, although it is still too early for us to suppose that all of the effects experienced are completely understood and are therefore of little concern in future missions.

For example, post-flight medical examinations revealed that astronauts suffer irregular heart beat rates for several days following their mission, when standing up sudden-

ly, or when given a special 'tilting table' test. The blood also undergoes some changes, the skeleton loses calcium, the muscles deteriorate and the body loses weight.

LONG EXPOSURES

The latest findings of Apollo and Skylab suggest that long term voyages may well involve an exposure which will seriously damage the tissues of the astronauts. The variations in the blood and skeleton are believed to be the result of several influences working together — confinement, weightlessness, and possibly breathing a low pressure atmosphere of pure oxygen. Heart and breathing rates are affected by zero gravity, work loads, and possibly psychological stress.

EVA AND THE ASTRONAUTS

During the first American Space Walks (EVA — Extra-vehicular activity), the spacesuits were unable to maintain a cool environment for heavy work loads indeed, even for relatively simple tasks! This resulted in rapid fatigue, and subsequent curtailment of the EVA.

Measurements taken from the biomedical sensors indicated that the work being done by the EVA astronaut was exceeding 3000 Btu/hour. The life-support system of the early suit was rated at peak loads of 2000 Btu/hour, small

wonder their visors got fogged up! Heart and breathing rates returned to normal following rest.

Alterations to the spacesuit, including the addition of water-cooled underwear, has largely removed this problem and from the manner in which the lunar astronauts performed their heavy and varied work load it would certainly appear that the original problems experienced with EVA have been overcome.

KEEPING FIT AND HEAVY

The problem involving bone calcium loss and body weight loss has been largely solved by the introduction of calcium rich diets both before and during the mission. Exercises performed regularly reduce the deterioration of muscle tissue and hence stabilize body weight.

RADIATING DANGER

There are two huge belts of radiation, called the Van Allen belts, which surround the Earth rather like the outermost layers of an onion. Missions are now planned to avoid plunging astronauts through all but the least intense regions of these belts, as the metallic walls of the spacecraft will only shield the astronauts from the less energetic radiation, and the most powerful rays will penetrate the craft and hence the tissues of the crew.

MAN IN SPACE

DOSED UP


Now, it is held that a short term exposure of 50 Rads (whole-body dose) is unlikely to harm the victim — unless repeated several times in one year. Between 50 and 200 rads the victim will suffer from nausea and sickness, fatigue, and his blood undergoes minor changes. At a dose of 400 Rads the victim becomes very ill and it has been statistically calculated that 50 percent of people receiving such a dose will die within a few days or a couple of weeks. The percentage of deaths rises proportionally with further increases in radiation dosage until a value of 1000 rads is reached — where there is a 99.9% *certainty* of death!

OFFICIAL VIEW

So far the 'officially released dosage figures' indicate that astronauts have only been exposed to doses of a few millirads. These doses have been present during the entire flight and are accordingly accumulative — hence a dose rate of say, 10 millirads per hour will add up to an accumulative dose of 100 millirads for a 10 hour mission and 1000 millirads (= 1Rad) for a 100 hour mission.

Naturally, longer mission times involve the astronaut in higher accumulative doses of radiation. The crews aboard the Apollo Moon craft and those participating in experiments aboard Skylab, were subjected to much lower hourly doses of radiation. Hence their 'accumulative' whole-body dosage was relatively 'safe' upon their return to the surface of earth.

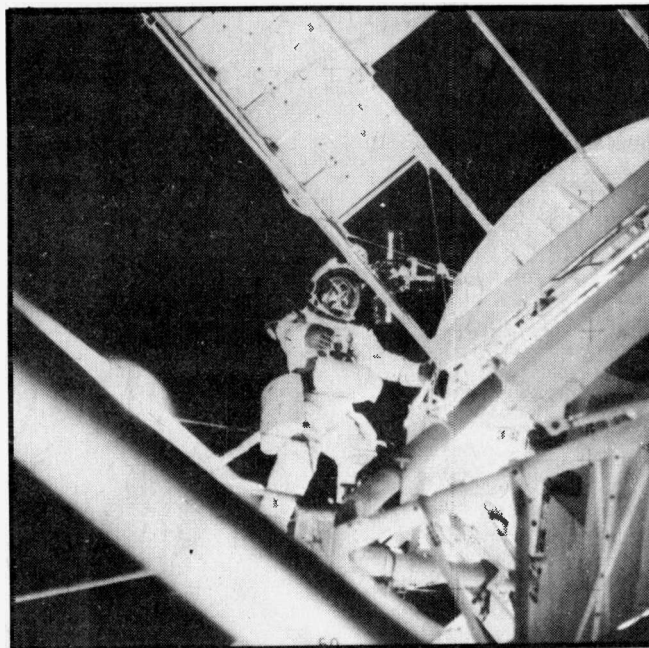It has been suggested that an astronaut returning from a Mars mission would have 'lost' about 10 percent of his brain tissue as a result of cosmic ray bombardment. Certainly if this theory proves correct we shall have to solve the daunting problem of cosmic radiation before we permit our astronauts to risk their 'lives' in such a way, even for such a prize as the Red Planet. ●



EVA activities, such as this walk around Skylab, are said to produce very high heart rates and rapid fatigue. The reasons for this are perhaps to some extent psychological as well as physical. Inside the spacecraft the astronauts do not suffer from fatigue to anything like the same extent, although naturally much less exertion is called for.

PREDICTED EFFECTS	MEASURED EFFECTS
Poor Circulation	None
Skin Infections	Same Dandruff
Sleep Deprivation	Minimal
Vision Affected	Improved — but occasionally sore eyes
Sore Nose and Throat	Some stuffiness (due to pure oxygen atmosphere?)
Disorientation, Nausea, Sickness, Hallucinations	None
Fainting	None
Dehydration	Some, at first
Body weight loss	Averages 3.4kg (7½lb)
Fatigue	Low in spacecraft, high in EVA
Blood changes	Red cell and plasma reduced
Muscular weakness	Slightly on return to earth
Skeletal losses	Calcium reduced in bones
High/Low Blood pressure	Slight variations on occasions
High Heart Rates	Launch: 110–180 per minute EVA: 130–190 per minute Re-entry: 90–185 per minute
Heart Failure	None
Low Heart Rate	In long term earth orbit dropped to 47 beats per minute
Gravity tolerance	Weak on return to earth weight
Radiation (known to cause blood and cell changes)	Low orbital, higher on lunar flights As yet no harm experienced
Cosmic Ray effects	Flashing Lights 'seen' within brain by cosmic rays hitting optic nerves, etc. Long term exposure suspected dangerous.

The table compares predicted spaceflights effects against those actually experienced. It was thought that weightlessness would seriously hinder the circulation of the blood, no such effect was found. Predictions were made of fainting, variable blood pressure, nausea, hallucination, disorientation, sickness and heart failure. All of these effects did not occur

In the case of nausea, however, slight signs were discovered in a few cases. Other forecasts involving high and low heart beat rates, chemical changes in the blood, calcium losses in the skeleton, reduced body weight and dehydration, were correct! Radiation hazard was another predicted effect, but the doses received were relatively small.

SINTEL for MEMORIES — MPU's — BOOKS

Components from
Leading Manufacturers only

MEMORY IC's

Intel 2102A-6 (new version of 2102-2). 16 pin IC. TTL compatible. Single +5V supply. 650nsec. 1024 x 1 bit Static NMOS RAM **£3.35**
Intel 2112-2 650nsec. 256 x 4 bit Static NMOS RAM **£4.76**
Intersil IM6508C CMOS 1024 x 1 bit Static RAM **£8.05**

KITS



**CAR CLOCK
'AUT-CK'
£17.85**

only 154mm x 85mm x 40mm

The SINTEL Car Clock is a four-digit clock in an attractive mini white case. Features large 0.5" red LED displays — High frequency quartz crystal timebase — an internal backup battery supplies power if the car battery voltage drops below nine volts when starting the engine, or if the clock is temporarily disconnected — only high quality components are used, Pihler resistors, roller tinned fibreglass PCB's, etc. Full instructions included. Simple but sophisticated circuitry gives you good performance at low cost. You benefit from our experience in clock design. Suitable for all 12V, negative earth cars.

Complete kit less battery — Order as 'AUT-CK' **£17.85**
Also available less case — Order as 'AUT-MODULE KIT' **£16.45**



50Hz CRYSTAL TIMEBASE KIT: provides an extremely stable output of one pulse every 20msec. Uses. May be added to all types of digital clocks to improve accuracy, to within a few seconds a month. If used with battery back-up also makes clocks power-out or switch-off proof. Replacing 50Hz signal on battery-powered equipment. Providing film synchronisation. Monitoring or Improving turntable speed. Complete kit. Order as 'XTK' **£6.28**

DIGITAL CLOCK KITS WITH CRYSTAL CONTROL AND BATTERY BACK-UP



ACK+
BBK+
XTK



GCK+
GBBK+

These two kits incorporate our Crystal Timebase Kit (XTK), together with components for battery back-up. All components, plus a PP3-type battery, fit neatly in the clock cases. Accurate to within a few seconds a month. If mains power is disconnected (through a power cut, accidental switching off or moving clock) the clocks will still keep perfect time. While on back-up, the displays are off to conserve battery life.

ATTRACTIVE 6-DIGIT ALARM CLOCK: Uses Red 0.5" displays. Features bleep alarm, "Touch switch" snooze control and automatic intensity control. Alarm remains fully operational while clock is on back-up. Complete kit including case less mains cable and plug. Order as 'ACK+XTK+BBK' **£33.58**
Kit also available less crystal control and back-up. Order as 'ACK' **£26.80**

MINI GREEN CLOCK. Attractive 4-digit Mantelpiece Clock with bright 0.5" Green display. Complete kit including case less mains cable and plug. Order as 'GCK + XTK + GBBK' **£19.65**
Kit also available less crystal control and back-up. Order as 'GCK' **£12.90**

DATABOOKS and Datasheets

(do not add any VAT)

New 1976 RCA CMOS and Linear IC Combined Databook **£4.95**
New 1976 RCA 'Power and Microwave' Databook **£4.95**
1976 National Semiconductor 7400 series TTL Databook, c. 200 pages **£3.45**
TTL Pin-Out Card Index. Set of cards with pin-outs (top and bottom views) of T.I. TTL range and many other T.I. IC's **£2.95**
Intel Memory Design Handbook, c. 280 pages **£4.75**
Intel 8080 Microcomputer Systems Users Manual, c. 220 pages **£4.85**
Motorola CMOS Databook (Vol. 5 Series A), c. 500 pages **£2.77**
Motorola M6800 Microprocessor Applications Manual, c. 650 pages **£12.45**
Motorola M6800 Programming Manual, c. 200 pages **£6.85**
Motorola Booklet introducing Microprocessors **£1.50**
2650 Microprocessor Manual 220 pp **£24.50**
National SC/MP Introkit Users Manual **£0.75**
National SC/MP Programming and Assembly Manual **£6.30**
National SC/MP Technical Description **£1.95**

DATASHEETS on Microprocessors: (usually Xerox Copies)

Intel IM6100 12 bit CMOS **£0.75** RCA CDP1802 8 bit CMOS **£0.35**
National SC/MP 8 bit. Low cost **£0.75** Zilog Z80 (enhanced 8080) **£0.75**
Signetics 2650 8 bit. Low cost **£0.75** Motorola MC 6800 **£0.75**

microprocessors

Please. Microprocessors should only be bought by experienced constructors. Sorry, we cannot answer technical queries or supply data other than from our selection.

ASSOCIATED IC's

IM6100CCDL	£58.00	6820	£17.67
8080A (2µs)	£43.65	6850	£17.67
6800	£33.87	8224	£9.76
ISPA/100 (SC/MP)	£18.75	8228	£12.16
2650	£27.00	8251	£17.67
		8255	£17.67

MICROPROCESSOR MANUFACTURERS' DEVELOPMENT KITS

These include main IC's, PCB, Manuals and Data
MEK6800D1 — with the 6800 MPU **£137.00**
ISP8K/200E — SC/MP Intro Kit **£93.55**
MCS-80 Kit C — with 8080A (no PCB) **£176.65**

CASES and other COMPONENTS

32.768 kHz Min. Watch Quartz Crystal **£4.50** 5.12 MHz Crystal **£3.60**
8-way BOSS Switch: 8 ultra-min. toggle switches in 16-pin DIL **£2.60**
Miniature Transformers (Both fit in all Verocases below) **£1.80**
Clock transformer 6-0.6/300mA. Order as 'LED-TRF' **£1.80**
For 5L101 12-0.12/100mA, 1.5-0.15/50mA. Order as '5L-TRF' **£1.80**
VEROCASES. Heat cases with PCB guides, etc., front and rear aluminium panels. We have pre-cut perspex for some cases, making them ideal for clocks or instruments. For 751247J PX-R-J-12 (Red) 28p, PX-G-J-12 (Green) 28p. For 751410J PX-R-J-14 (Red) 30p, PX-G-J-14 (Green) 30p. For 751411D PX-R-D-14 (Red) 40p. The cases are as used in our ACK & GCK.
Dimensions are in mm
751410J (205x140x40) **£2.64** 751237J (154x85x40) **£1.72**
751411D (205x140x75) **£3.04** 751238D (154x85x60) **£2.15**

We have many other Verocases and Vero products in stock — see our Price List.

FAST SERVICE

We guarantee that Telephone Orders for goods in Stock, received by 4.15 p.m. (Mon-Fri.) will be despatched the same day. 1st Class Post (Books and Kits by parcel post), and our Stocking is good. Private customers should telephone and pay by giving their Access or Barclaycard number, with a minimum order value of £5. Official orders, no minimum.

CMOS

CD4000 0.16
CD4001 0.16
CD4002 0.16
CD4006 1.22
CD4007 0.17
CD4008 0.95
CD4009 0.56
CD4010 0.56
CD4011 0.17
CD4012 0.17
CD4013 0.58
CD4014 1.05
CD4015 1.05
CD4016 0.55
CD4017 0.99
CD4018 0.99
CD4019 0.56
CD4020 1.16
CD4021 1.05
CD4022 1.00
CD4023 0.17
CD4024 0.81
CD4025 0.17
CD4026 1.79
CD4027 0.55
CD4028 0.89
CD4029 1.16
CD4030 0.56
CD4031 2.24
CD4032 1.11

CD4033 1.45
CD4034 1.98
CD4035 1.22
CD4036 3.18
CD4037 0.99
CD4038 1.22
CD4039 3.09
CD4040 1.11
CD4041 0.87
CD4042 0.87
CD4043 1.05
CD4044 0.97
CD4045 1.45
CD4046 1.39
CD4047 0.94
CD4048 0.58
CD4049 0.55
CD4050 0.55
CD4051 0.97
CD4052 0.97
CD4053 0.97
CD4054 1.20
CD4055 1.37
CD4056 1.37
CD4057 27.95
CD4059 4.96
CD4060 1.16
CD4062 9.07
CD4063 1.14
CD4066 0.64
CD4067 3.87
CD4068 0.22
CD4069 0.22

CD4070 0.60
CD4071 0.22
CD4072 0.22
CD4073 0.22
CD4075 0.22
CD4076 1.61
CD4077 0.60
CD4078 0.22
CD4081 0.22
CD4082 0.22
CD4085 0.74
CD4086 0.74
CD4089 1.61
CD4093 0.89
CD4094 1.94
CD4095 1.09
CD4096 1.09
CD4097 3.87
CD4099 1.90
CD4502 1.29
CD4510 1.41
CD4511 1.62
CD4514 2.85
CD4515 3.25
CD4516 1.41
CD4518 1.30
CD4520 1.30
CD4527 1.64
CD4532 1.50
CD4555 0.94
CD4556 0.94
MC14528 1.18
MC14553 5.24

IM6508 8.05

CLOCK CHIPS

AY51202 2.89
AY51224 3.50
MK50253 5.60

VEROCASES

751410J 2.64
751411D 3.04
751237J 1.72
751238D 2.15
751239K 2.78

SUNDRY

CA3130 1.14
uA741 0.35
(RCA 8 DIL)
78L12WC 0.77

LOW COST IC SOCKETS

Soldercon Pins are the ideal low cost method of providing sockets for TTL CMOS, Displays, ICs. Simply cut off the lengths you need, solder into board and snap off the connecting carrier. A single purchase of Soldercon Pins gives you any socket you may need, and at low prices. 50p per strip of 100 pins, 1.000 for £4, 3.000 for £10.50.

DISPLAYS These Jumbo LED displays take no more current than 0.3" types. All our Common Cathode (C.C.) digits can be used in place of any other C.C. display (DL704, D1750, MAN3640, etc.) as they are all electrically identical (but may have different pin-outs). Similarly our Common Anode digits may be used in place of any other C.A. types (DL707, DL747, RS/Doram 586/699, etc.).



FND500



TIL321, TIL322



XAN652, XAN654 GREEN



D500-6

Part No.	Manufacturer	Colour	Type	Size	Price
FND500	Fairchild	Red	Common Cathode LED	0.5"	£1.02
TIL321	Texas Instr.	Red	Common Anode LED	0.5"	£1.30
TIL322	Texas Instr.	Red	Common Cathode LED	0.5"	£1.20
XAN652	Xcicon	Green	Common Anode LED	0.6"	£1.75
XAN654	Xcicon	Green	Common Cathode LED	0.6"	£1.75
MAN3M	Monsanto	Red	Common Cathode LED	0.13"	48p
5L101	Futaba	Green	Phosphor Diode	0.5"	£5.80

Display PCBs (each fits neatly into Verocase 751410J). All are for multiplexed arrays, all are suitable for FND500, TIL321, TIL322
D500-4 (for 4 digit clock) 90p; D500-6 (for 6 digit clock) **£1.35**
D500-8 (for counter, up to 8 digits) **£1.35**
USING DISPLAYS WITH CMOS OR TTL? Send sae asking for free application note, SN1, which gives simple circuits with component values.



ADD 8% VAT + 25p P&P on all orders. Phone orders send "Fast Service" for details. Export orders welcome, but you must contact us first for special order form and postage rates.



SINTEL Sales, PO Box 75A, Oxford
Tel: 0865 49791

SINTEL

Official Orders Welcomed. For our complete range send for free catalogue and price list.

TECHNICAL BOOKS FROM ETI

CALCULATORS

- 99 WAYS TO KNOW AND USE YOUR ELECTRONIC CALCULATOR**
L. Frenzel £4.50
- SCIENTIFIC ANALYSIS ON YOUR POCKET CALCULATOR**
Smith £8.25

COMPUTERS AND MICROPROCESSORS

- BEGINNER'S GUIDE TO COMPUTER LOGIC**
G. Stapleton £1.95
Grasp quickly computer codes, digital logic ops and switching circuits

- COMPUTER CIRCUITS AND HOW THEY WORK**
B. Wells £1.80
Become acquainted with the various parts of a computer and its technology.

- COMPUTER TECHNICIANS HANDBOOK**
B. Ward £3.25
This giant volume compares to a 1,000 hour course on computer mechanics.

- CONTROL ENGINEERING**
N. M. Morris £3.70
This is the 2nd edition of a highly successful book, keeping fully abreast of developments in control engineering.

- DIGITAL ELECTRONIC CIRCUITS AND SYSTEMS**
N. M. Morris £2.60
The ideal book for the enthusiast confused by logic and digital techniques

- MICROPROCESSORS**
L. Altman £10.80
Gives a general overview of the technology design, ideas and practical application

- MICROPROCESSORS**
D. C. McGlynn £8.00
Technology Architecture and Applications. This introduction provides a clear explanation of this important new device.

- MICROPROCESSORS AND MICROCOMPUTERS**
B. Soucek £15.90
Describes the application programming and interfacing techniques common to all microprocessors

ELECTRONICS

- ACTIVE FILTER COOKBOOK**
D. Lancaster £9.95
Everything you need to know to build and use active filters.

- ELECTRONIC ENGINEERS REFERENCE BOOK — 4th EDITION**
L. W. Turner £25.60
A completely new and up-to-date reference book for all engineers and students

- BASIC MATHS COURSE FOR ELECTRONICS**
H. Jacobowitz £1.75
Quick short cut way to learn the language of maths as applied to electronics.

- BEGINNER'S GUIDE TO ELECTRONICS**
T. L. Squires £2.55
Short cut for those wishing to obtain a quick acquaintance with modern electronics.

- BEGINNER'S GUIDE TO TRANSISTORS**
J. A. Reddihough £2.55
Covers the basic theory and practice of modern transistors

- DESIGNING WITH TTL INTEGRATED CIRCUITS**
Texas Instruments £8.20
Covers the entire family of TTL and practical applications of circuits in digital systems.

- ELECTRONIC MEASUREMENTS SIMPLIFIED**
C. Halfmark £2.10
Covers just about every conceivable test or measurement you will need

- ELECTRONICS POCKET BOOK**
P. McGoldrick £4.15

- ELECTRONICS AND PHOTOGRAPHY**
R. Brown £2.20
Practical circuit projects devoted to photography

- ELECTRONICS SELF TAUGHT**
J. Ashe £2.20
Covers basic principles of electronics, includes a large number of simple circuits.

- ESSENTIAL FORMULAE FOR ELECTRICAL AND ELECTRONIC ENGINEERS**
N. M. Morris £1.20
Handy reference book, includes a section on S1 units, resistor colour codes and preferred values

- HOW TO BUILD ELECTRONIC KITS**
V. Capel £2.10
Instructs the kit builder on how to check components, how to assemble and how to cure faults.

- FIRE AND THEFT SECURITY SYSTEMS**
B. Wells £1.90
Selection and installation, home maintenance and business security devices

- HANDBOOK OF IC CIRCUIT PROJECTS**
J. Ashe £1.75
From hi-fi circuits to complete digital counters in a single package.

- HOW TO READ ELECTRONIC CIRCUIT DIAGRAMS**
B. Brown £1.85
Everything you need to know from basic circuit components to integrated circuits.

- HOW TO BUILD PROXIMITY DETECTORS AND METAL LOCATORS**
J. Shields £3.25
A practical do-it-yourself book

- HOW TO USE IC CIRCUIT LOGIC ELEMENTS**
J. Streater £3.25
Helps those unfamiliar with digital logic circuits

- INTEGRATED ELECTRONICS**
J. Millman £7.15
Using an IC approach the text leads the reader step by step from semiconductor physics to devices, models, circuits and systems

- IC OP-AMP COOKBOOK**
W. Jung £8.75
Covers the basic theory of IC op amps in great detail, also includes 250 practical circuit applications.

- INDEXED GUIDE TO MODERN ELECTRONIC CIRCUITS**
R. Goodman £2.25
Practical Schematics with concise theory and troubleshooting information.

- INTRODUCING ELECTRONIC SYSTEMS**
I. R. Sinclair £1.75
Provides a basic insight into what makes electronics tick

- INSTALLING AND SERVICING ELECTRONIC PROTECTIVE SYSTEMS**
H. Swearer £2.10
Covers installation and servicing of all electronic security systems

- LINEAR ELECTRONIC CIRCUITS AND SYSTEMS**
G. Bishop £2.55
Illustrates the use of the op amp in many different applications

- LINEAR INTEGRATED CIRCUIT APPLICATIONS**
G. Clayton £4.90
A practical approach is emphasised throughout, encouraging the reader to try out devices himself

- LINEAR IC PRINCIPLES EXPERIMENTS AND PROJECTS**
E. M. Noll £5.80
An introduction to one of electronics most exciting devices

- 110 OPERATIONAL AMPLIFIER PROJECTS FOR THE HOME CONSTRUCTOR**
R. M. Marston £2.85
Outlines the essential characteristics of op amps and presents useful projects.

- 110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR**
R. M. Marston £2.85
Introduces the reader to FET's, SCR's and IC's with full construction details of many useful circuits

- 110 COSMOS DIGITAL IC PROJECTS FOR THE HOME CONSTRUCTOR**
R. M. Marston £3.10

- 110 INTEGRATED CIRCUIT PROJECTS FOR THE HOME CONSTRUCTOR**
R. M. Marston £2.85
All the projects have been devised, built and fully evaluated by the author

- 110 THYRISTOR PROJECTS USING SCR's**
R. M. Marston £2.85
A companion to the author's previous books

- MOS DIGITAL IC'S**
G. Flynn £4.50
This book contains information about MOS and CMOS from basic construction to circuit application

- OPERATIONAL AMPLIFIERS DESIGN AND APPLICATIONS (Burr Brown)**
G. Tobey £6.60
Covers the entire field of operational amplifiers

- PIN POINT TRANSISTOR TROUBLES IN 12 MINUTES**
L. Garner £2.85
Complete information on circuit operations, troubleshooting charts and service procedures

- PRACTICAL TRIAC/SCR PROJECTS FOR THE EXPERIMENTER**
R. Fox £2.15
Thyristor theory and practical circuits with low cost SCR TRIACs and DIACs.

- PRINCIPLES OF TRANSISTOR CIRCUITS**
S. Arma £4.40
Generally accepted as being a standard textbook on fundamental principles underlying the design of circuits and using transistors

- RAPID SERVICING OF TRANSISTOR EQUIPMENT**
G. King £2.85
A systematic guide to the servicing of transistor radio, television, tape and hi-fi equipment.

- SEMICONDUCTOR CIRCUIT ELEMENTS**
T. D. Towers £6.00
Gives readers an account of all semiconductor devices commercially available, for each device it covers a general description, circuit diagram symbols and working principles

- SOLID STATE CIRCUIT GUIDE BOOK**
B. Ward £2.15
Step by step instructions to design circuits to your own specifications

- TRANSISTOR CIRCUIT DESIGN**
Texas £8.45

- TTL COOKBOOK**
D. Lancaster £6.00
Complete and detailed guide to TTL, how it works, how to use it and practical applications.

- UNDERSTANDING ELECTRONIC CIRCUITS**
R. Sinclair £4.00
Describes various circuits encountered today with a strong emphasis on fault finding and servicing procedures.

- UNDERSTANDING ELECTRONIC COMPONENTS**
R. Sinclair £4.00
Explains about components and bridges the gap between elementary textbooks and unapproachable advanced treatments

- UNDERSTANDING CMOS INTEGRATED CIRCUITS**
R. Melen £3.50
Begins with basic digital IC's, covers semiconductor physics, CMOS fabrication technology and design.

- UNDERSTANDING SOLID STATE CIRCUITS**
N. Crowhurst £1.90
Written to service the interests of anyone at sub-engineering level.

ELECTRONIC ORGAN BOOKS

- TRANSISTOR ELECTRONIC ORGANS FOR THE AMATEUR**
A. Douglas £4.90
Written in a simple style, this gives a complete explanation of everything to do with transistorized organs and is profusely illustrated with clear diagrams

- THE ELECTRONIC MUSICAL INSTRUMENT MANUAL**
A. Douglas £8.00
A comprehensive guide to the theory and design of electronic musical instruments

- ELECTRONIC MUSIC PRODUCTION**
A. Douglas £3.10
A practical guide to the production of electronic music

SEMICONDUCTOR DATA

- INTERNATIONAL TRANSISTOR SELECTOR**
T. D. Towers £3.75
If it takes you longer than one minute to find out all about transistors, then you need a copy of this book.

- POPULAR VALVE/TRANSISTOR SUBSTITUTION GUIDE**
£2.15
Substitution data for both valves and transistors in one new volume

- RADIO VALVE AND SEMICONDUCTOR DATA**
A. M. Ball £2.50
Characteristics of 1 000 valves, cathode ray tubes, transistors, diodes, rectifiers and optical semi-conductors. This new edition (1975) is right up to date and over 450,000 copies have been sold.

RADIO AND TELEVISION

- FOUNDATIONS OF WIRELESS AND ELECTRONICS**
M. G. Scroggie £4.35
(New 1975 edition) Covers the whole basic theory, no previous technical knowledge is assumed

- SERVICING TRANSISTOR RADIOS**
L. D'Arcy £2.30
Complete guide giving theory analysis and servicing techniques

- WORLD RADIO TV HANDBOOK—1976**
£5.00
Complete Directory of international radio and television and this year contains: How to listen to the world

TEST EQUIPMENT AND OSCILLOSCOPES

- BASIC ELECTRONIC TEST PROCEDURES**
I. M. Gottlieb £2.35
Shows how to get accurate measurement with VOMs meters and oscilloscopes

- THE OSCILLOSCOPE**
G. Zwick £2.10
Starts from the first principles and takes the reader to an advanced level.

- PRACTICAL TEST EQUIPMENT YOU CAN BUILD**
W. Green £2.15
For technicians, radio/TV service operators and serious experimenters.

- RADIO, TV AND AUDIO TEST EQUIPMENT**
G. King £4.95
A practical guide to test instruments and applications, concerned largely with the oscilloscope

- TEST INSTRUMENTS FOR ELECTRONICS**
M. Clifford £1.65
Easy modifications to your VOM/VTVM and scope with the aid of this book

- WORKING WITH THE OSCILLOSCOPE**
A. Saunders £1.85
Includes workshop test projects with large size drawings.

- SERVICING WITH THE OSCILLOSCOPE**
G. King £5.00
Includes a unique series of photographs showing oscilloscope traces to be found in normal and faulty equipment, stereo radio, colour TV. Circuits servicing is dealt with.

HOW TO ORDER

All prices are correct at the time of going to press but are subject to alteration without notice. All prices include postage. Please print your name and address clearly and list each title and price separately. Cheques and postal orders should be made payable to ETI Book Service. Books are sent on seven days' approval against a full cash remittance, plus postage. Book stock is not held at ETI's London offices and orders should be sent to: ETI BOOK SERVICE, P.O. BOX 79, MAIDENHEAD, BERKS SL6 2EG.

AUDIO PHASER

THERE AREN'T MANY ELECTRONIC music accessories that we haven't published as projects in ETI and this project will make the list even shorter.

Most musicians will know what a phaser sounds like and it is going to be very difficult for us to describe the effect to readers who don't know the sound. It really has to be heard to be appreciated.

The most dramatic effect, and the easiest to describe, is that caused by feeding white noise through a phaser. The sound is similar to the sound of surf, an 'atmospheric' whooshing sound. On recordings phaser effects can be heard on electric guitars, drums, electric piano, and other instruments.

Technically the phaser acts as a filter — it phases out certain frequencies in the audio spectrum and over a period of a second or two these minima in the response curve sweep up and down the audio band. The response of the ETI phaser can be seen in figure 1. Frequencies between 10 Hz and 4 kHz are present in varying proportions between 0 and 100% of the input signal level. As the values of the components in the phase-shift network change, the proportions of these frequencies will change as the response curve moves up and down the audio spectrum.

The unit we have designed is a six-stage phaser (there are six phase-shift networks in the phase-change path) which gives three minima in its response curve. It is built into a die-cast box so it can be used on stage by a guitarist. The only external control adjusts the speed, except for the foot-operated switch which puts the phaser in or out of circuit. The power is switched on by plugging the jack plugs into their sockets.

CONSTRUCTION

Apart from the PCB the box contains one pot, two jack sockets and a foot-operated switch, so construction is unlikely to be any problem. Use our design for the PCB pattern and insert the components according to the overlay drawing. IC sockets do not have to be used but a socket would spare

Specification

Phase-shift stages:

Six stages providing a maximum 1080 degrees phase-shift, and consequently three minima (see graph).

Frequency range:

With 10n and 100k networks, minima at 40 Hz, 160 Hz, and 600 Hz.

With 10n and 56k networks, minima at 70 Hz, 270 Hz and 1 kHz (as shown in Figure 3).


With 10n and 10k networks, minima at 400 Hz, 1600 Hz and 60 kHz.

In operation the resistive element of the phase-shift networks varies continuously and these minima sweep across the spectrum.

Input impedance:
500k.

Input sensitivity:
3 mV to 1 V.

Overall gain:
Unity.

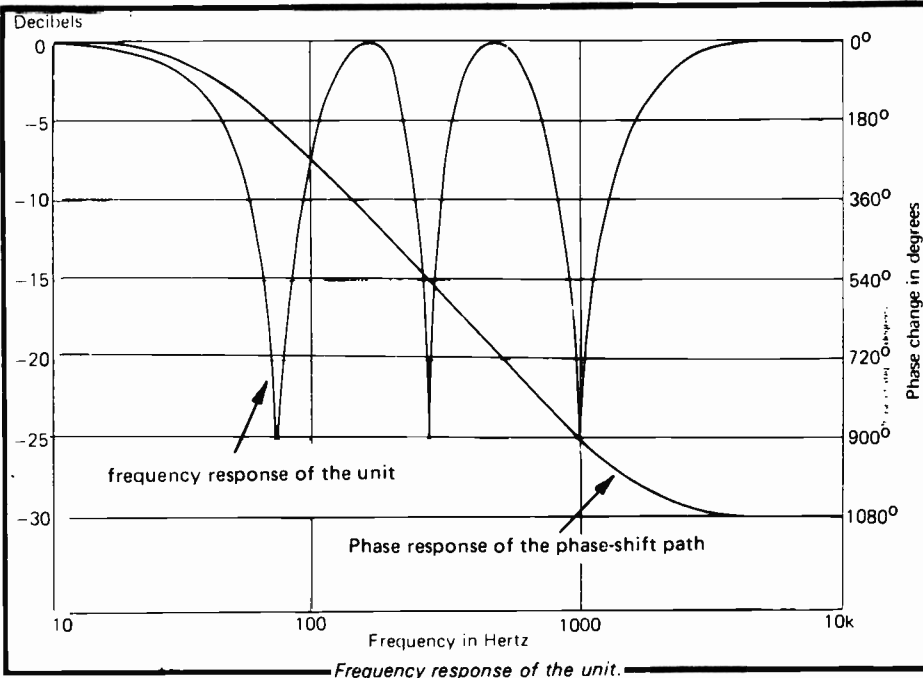

the CMOS IC from the dangers of direct soldering.

First solder the low-profile components to the board, then the other components. When the case-mounted parts have been installed, wire up the board to these using sufficiently long leads to enable easy fault-finding, should this be necessary.

For stage use, the phaser needs properly protecting against physical shocks so we strongly recommend you use a die-cast box and wrap the PCB in foam sheeting rather than screwing it to the case. If the phaser is to be built into a mixer or an effects unit then housing is obviously less important.

SETTING UP

The best way to set up the phaser is to use a white noise source and then


adjust the bias preset to give a continuous whooshing sound. If the bias is incorrectly set the sound will be interrupted, it will not whoosh continuously.

If you do not have a white noise source use a signal high in harmonic content: electric guitar, crowd noise, FM hiss, etc.

We cannot teach you how to use the phaser, it is a special effect offered as an aid to creative musicians. It can produce weird effects with almost any audio source (it can, for example, simulate long-distance phonecalls or radio stations) and it is necessary to play certain styles of electric guitar and electric piano.

The phaser can be plugged into the echo send and echo return sockets of the ETI Master Mixer for use on any channel as desired.

AUDIO PHASER

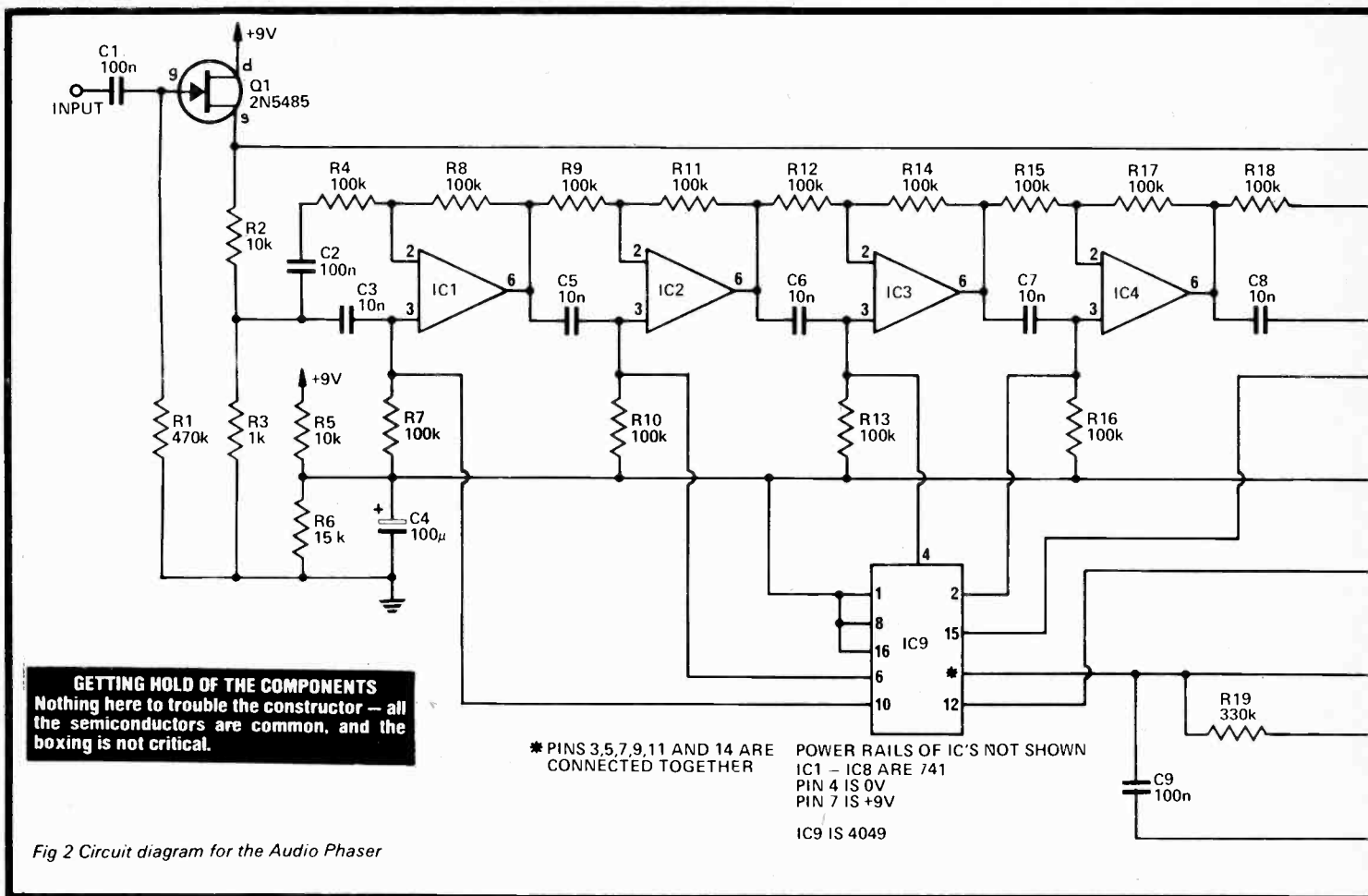

How it works

The input impedance of the phaser has to be high to prevent damping of the strings when used with an electric guitar. Loading caused by a low input impedance would stop the notes from sustaining properly. In the ETI phaser this is achieved by the high impedance buffer, Q1.

After the input buffer the signal is split along two paths, and the two parts do not meet again until they are mixed back together again at the junction of R26 and R27. One part of the signal undergoes phase-shift, via ICs 1 to 6, and the other part follows a direct path. Q2 amplifies the output to give an overall gain of unity.

The phase-shift is achieved in six identical RC networks; the overall shift being the sum of the shifts at each stage. IC9 varies the value of resistance in each stage, but we will first look at the operation with a fixed value, say 56 k.

In this case each stage puts a 10nF capacitor and 56k resistor across the signal. The waveform at the junction of these two components has to be of such phasing as to reconcile the perpendicular phasing of the waveforms across each component.

The signal fed into the op-amp undergoes a phase-shift, but the phase-shift is not the same for all frequencies. In the one stage the signal undergoes a change of 180 degrees at high frequencies and a negligible

change at low frequencies. The curve of Figure 1 shows that there is little shift at 10 Hz and 1080° at 4 kHz (that is 180° at each stage: a total of 1080° from all six stages).

When all six stages are taken into account, frequencies from 10 Hz to 4 kHz have a continuous range of phase-shifts from 0 to 1080°.

Figure 1 also shows what happens when equal amplitudes of the two signals (from the direct and phase-shift paths) are mixed.

Because frequencies outside the range 10 Hz to 4 kHz are in phase the response is flat. In-Phase mixing also occurs within this range at two places. These are at phase differences of 360° and 720°, in this case at 160 Hz and at 460 Hz.

The holes in the response are caused by out-of-phase mixing, as occurs when the phase differences are 180°, 540°, and 900°. With 10nF and 56k in the phase-shift networks these minima occur at 70 Hz, 270 Hz, and 1 kHz.

The number of minima in the response is directly related to the number of phase-shift stages. Four stages would give a maximum phase shift of 720° and minima would then only occur at 180° and 540°. If you use eight stages another minimum will occur at 1260°, giving four in all.

The rest of the circuitry in the phaser is used to vary the resistance in the phase-

shift networks to move the response curve of the phaser up and down the frequency axis. IC9 is effectively six sets of complementary FETs and the resistance of each can be controlled by applying a voltage onto its gate. Varying the gate voltage of IC9 causes the effective resistance of R7 to be shunted from 100k down to a few kilohms.

IC7 is an integrator and IC8 is a Schmitt trigger, together they make a triangle-wave oscillator. This triangle waveform gives a rising and falling voltage to the gates in IC9. The waveform has to be correctly biased to give the desired resistance change in each phase-shift stage. The bias voltage is set by RV1.

RV2 controls the speed of the triangle-wave oscillator to give periods ranging from a few seconds down to a tenth of a second or so.

The zero reference voltage for the op-amps is taken from the junction of R5 and R6, which is at half the supply voltage. This does away with the need for a split supply — a single 9V battery is sufficient. The power is switched on and off by the jack socket. The foot-switch switches the phaser in and out of circuit.

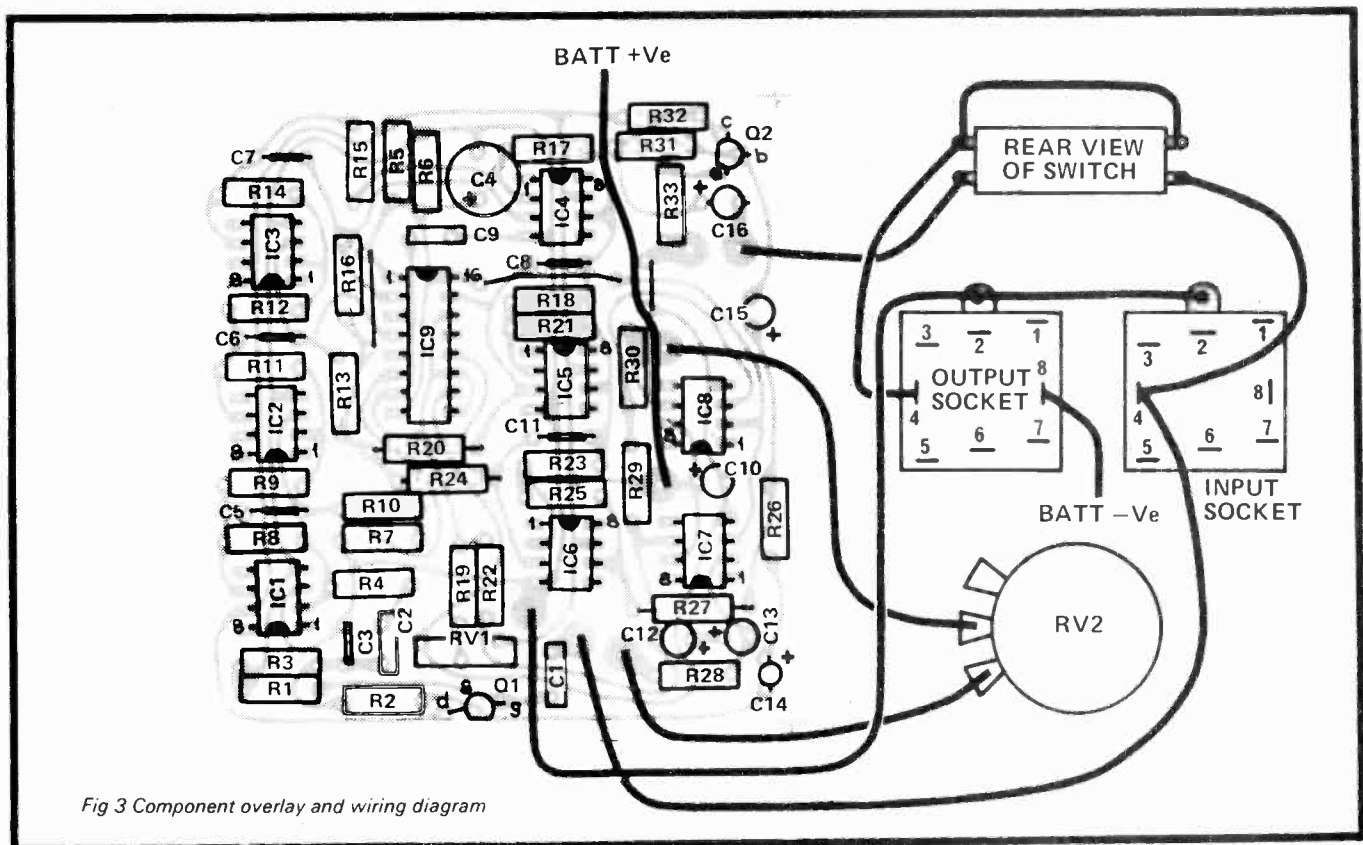
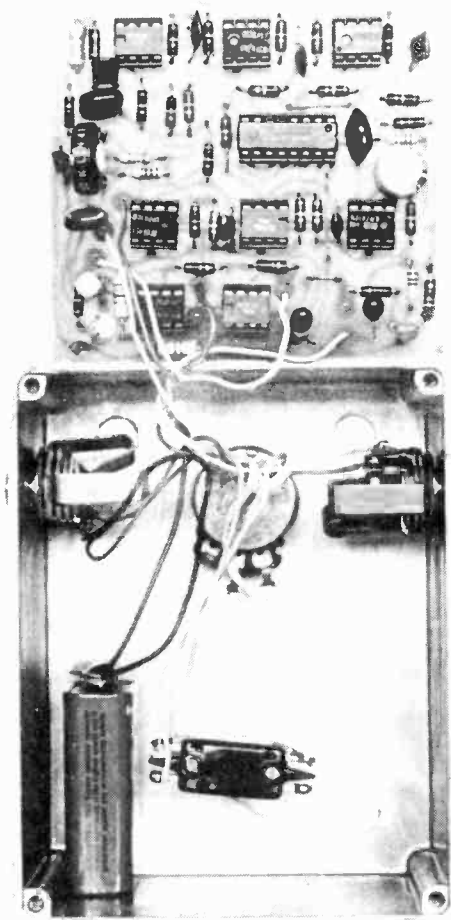
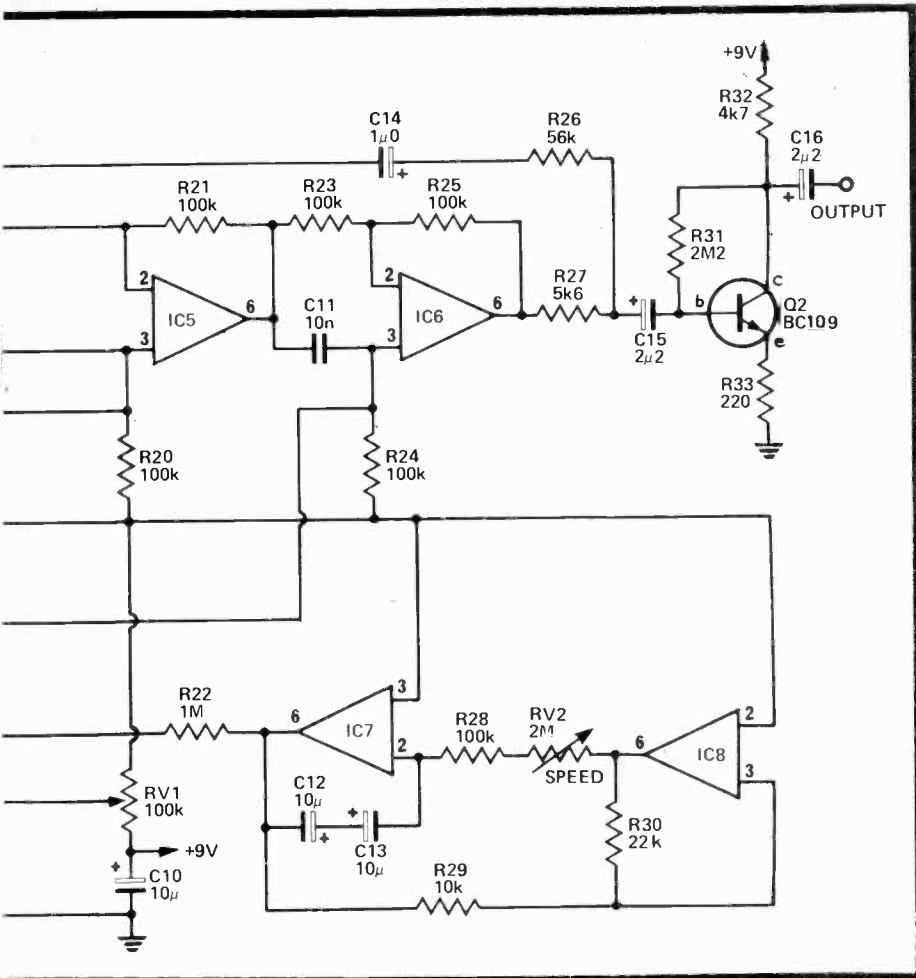


Fig 3 Component overlay and wiring diagram

AUDIO PHASER

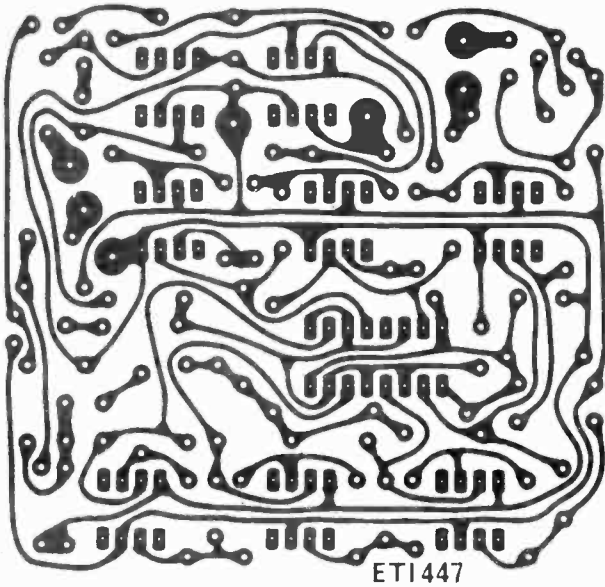


Fig 4 Printed-Circuit Layout. Full Size 81 x 76 mm.

Parts List

Resistors all 1/2 W 5%

R1 470 k
R2 10 k
R3 1 k
R4 100 k
R5 10 k

R6 15 k
R7-R18 100 k
R19 330 k
R20,21 100 k
R22 1 M

R23-R25 100 k
R26 56 k
R27 5 k6
R28 100 k
R29 10 k

R30 22 k
R31 2 M2
R32 4 k7
R33 220

Potentiometers

RV1 100 k trim type
RV2 2 M log rotary

Capacitors

C1,2 100 n polyester
C3 10 n "
C4 100 µF 6 V
C5-C8 10 n polyester
C9 100 n "

C10 10 µF 25 V
C11 10 n polyester
C12,13 10 µF 25 V
C14 1 µF 25 V
C15,16 2 µF 25 V

Semiconductors

Q1 2N5485 or similar
Q2 BC109 or similar
IC1-IC8 µA741 op-amp
IC9 4049 CMOS

Miscellaneous

PC Board ET1 447
Two stereo phone sockets
Switch — push on push off
push button
Case to suit
9 V battery
Knob

ELECTRONIC
BROKERS



ELECTRONIC BROKERS LTD
49/53 Pancras Road
London NW1 2QB
Tel: 01-837 7781

**Computer parts for hobby,
experimental, educational
and professional use.**

KB6: 56-station standard Teletype layout AS RECOMMENDED FOR PRACTICAL WIRELESS VIDEO-WRITER PROJECT

ASCII-Coded TTL-compatible 4-bank alphanumeric reed-switch keyboard with ROM encoder chip, strobed output, two-key rollover and debounce. Standard 7-bit ASCII code (no parity). Supplied complete with circuit diagrams and code chart.

SPECIFICATIONS

Power Supply: +5VDC +/-5% 150mA; -12VDC +/-10% 10mA. **Output Logic Levels:** Data Bits 1 through 7: Ov "0" .45V; 2.6V "1" 5.25V. **Fan Out:** One standard TTL load. **Strobe:** 2.6V "1" 5.25V; Ov "0" .46V. **Fan Out:** 10 standard TTL loads. Strobe signal delay 10 milliseconds nominal to allow data to stabilise.

Price **£35.00** plus £1.00 P&P + 8% VAT (Send £38.88)

ALSO AVAILABLE—SPECIAL LOW-COST KEYBOARD:

KB5: 3-bank alphanumeric Baudot-coded 36-station keyboard. TTL-compatible strobed output.

Price **£20.00** plus £1.00 P&P + 8% VAT (Send £22.68)

BURROUGHS SELF-SCAN DISPLAYS

16 display positions instructed by a 6-bit coded signal to display one of 64 pre-programmed characters as a 5 x 7 dot matrix. Each character 0.4" high. Input signal 6-bit data, clock, reset, etc. Power supplies +5V, -12V and +250V. External repertoire A-Z, 0-9 + special symbols. Size 8½ x 2¼ x 1½" approx.

Price: Ex-equipment **£49.50**, brand new £60.00 plus £2 P&P plus 8% VAT


CONTINUOUS DISPLAY LCD WATCHES

UNIQUE ALTERNATING DISPLAY FEATURE

The watch continuously displays HRS. and MINS. with MONTH, DAY and SECONDS on demand. The owner selects the feature where the HRS. and MINS. or MONTH and DAY display alternatively for 2 second intervals until owner resets to normal display. During the alternating cycle seconds are still available on demand.

- **Finest American MOS technology
- **Quartz accuracy.
- **Multi-function:
Hrs., Mins., Month, Day, Seconds.
Alternating display Back-light.
Programmed 28, 30, 31 day months.
A.M./P.M. indication for ease of date setting
- ***All important: UK factory manufacturing and servicing facilities.

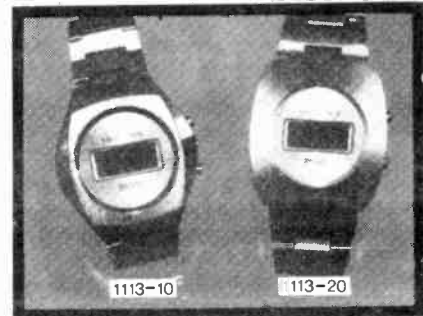Watch despatched with matching Gold plated bracelet, in presentation box with instruction booklet and guarantee. Model 1113-10 is also available in a stainless-steel bracelet.



£34.50

INCL. V. A. T. & P. & P.

Leetronic

Watch Division, Lee Instrumentation Ltd.
Bedwas, Newport, Gwent NP1 8YZ
TEL. (0222) 885756-7-8. TELEX: 497084
Reg. No. 639437. VAT Reg. No. 133 8154 80

To: Leetronic, Lee Instrumentation Ltd., Newport, Gwent NP1 8YZ
Print — FREEPOST — no stamp required.

Please forward ___ (qty) model ___ at ___ each TOTAL: £ ___

I enclose

Name cheque ___

Address postal order ___

..... money order ___

Signed

Barclaycard/Access no. _____



SUBSCRIPTIONS



"IF YOU CAN'T SEE IT — IT'S GONE!"

WHY TAKE CHANCES ?

There are only two ways to ensure a copy of ETI: place a regular order with your newsagent or take out a subscription. Don't care about missing an issue? Well, it's up to you but although we do supply back numbers (several hundred are put on one side solely for future demand). However, due to increased readership, these back numbers have been lapped up and the issues for which back numbers are available has declined remarkably.

Help us to help you: please write your name and address on the back of your cheques.

To: SUBSCRIPTIONS DEPARTMENT,
ETI MAGAZINE,
25-27 Oxford Street,
London W1.

I enclose £6.00 (£7.00 overseas)
for the next twelve issues

Name

Address

PAYMENT IN STERLING ONLY PLEASE

NEWS ABOUT ETI

dit is eti nederland

(THIS IS ETI—HOLLAND)

Australia, Britain, France . . . now Holland (and as you'll see below, soon Canada) . . . the number of ETI editions is growing!

ETI-Holland — known there as *Electronica Top Internationaal* — was launched on October 4th with the 100W Disco article (featured in September ETI-UK) as the cover feature.

The Dutch edition is being published for the group by Radio Rotor of Emmen — a town in north-east Holland near the German border.

Although sales figures won't be known for some time, over 1,000 subscriptions were received even before the first issue was available. In a country which already has three established hobby-electronics, this can only be regarded as a good omen!

Apart from the 100W Disco, other features include *Microfile*, the start of the components series, and five constructional projects. Locally produced articles are of course included, one of which covers a review of a new microprocessor kit (not available in Britain).

The staff of ETI in Britain wish ETI-Holland the same success as we have enjoyed here.



Above is shown the headquarters of Radio Rotor who are publishing our Dutch edition. The ETI offices are in the same building. Below left is Anton Kriegsmann, Editor-in-Chief of *Electronica Top Internationaal*. Below right is a small section of the labs where all projects are rebuilt before going into the Dutch edition.



THE COVER OF THE FIRST ISSUE OF ETI—HOLLAND

PRIVILEGE OFFER

FOR READERS IN NORTH AMERICA ONLY

SEND NO MONEY

MAIL TO:
ELECTRONICS TODAY INTERNATIONAL*
c/o Suite 2404
85 Thorncliffe Park Drive,
Toronto, Ontario,
M4H 1L6.

* Temporary Postal Address only.

I would like to have the first edition of ETI—Canada FREE OF CHARGE.

NAME

ADDRESS

City or Town

Prov Postal Code

Only use this coupon if the leaflet included in the issues for Canada is missing. Only one issue will be sent even if both coupons are filled in.

ETI



Toronto: the fastest growing city in North America with the CN Tower, the world's tallest free-standing structure, will be the home for ETI-Canada.

ELECTRONICA TOP INTERNATIONAAL

electronica top internationaal

1e JAARGANG
NR 1 OKTOBER
1976
f 2,75

100W DISCO

SERIE OVER MICROPROCESSORS TECH TIPS

NIEUWS CONSTRUCTIE ONTWIKKELING AUDIO

CANADA

The British edition of ETI was first introduced to Canada in February 1976. Sales and response have been so good that this will be replaced by ETI-Canada, to be published in Canada, by Canadians, for Canadians.

ETI-Canada will cover very much the same ground as ETI-Britain but will carry many locally produced articles specifically for the Canadian reader. Articles from other editions will be carried but only where these are also of interest to Canadian readers. News and news-type articles will relate to Canada and will be as up-to-date as possible.


THIS IS THE LAST ETI-BRITAIN THAT WILL BE GENERALLY DISTRIBUTED IN CANADA.

We're pretty confident that the thousands of Canadian readers who've been buying ETI-Britain as an import will like their own edition . . . We're so confident that we'll send you the first issue (which will be available in late January) FREE. Just fill out either the coupon on the left or the coupon on the insert included in issues for Canada. Please only use one — a friend interested in electronics can use the other of course.

Photograph courtesy of Ontario House, London

Catronics

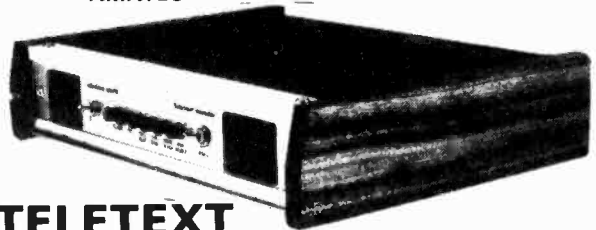including
AMATEUR RADIO BULK BUYING GROUP



TELETEXT DECODER KIT

CATRONICS Ltd. offer the world's first kit for the Home Constructor for decoding and displaying the CEEFAX and ORACLE television information display systems. The design of this decoder has been described in a series of articles published by "Wireless World" (November, 1975, to June, 1976 issues).

The decoder has all the usual features including full colour characters, Graphics, Newsflash, Sub-Title and Timed Page facilities.

Our kit contains the printed circuit boards and all components necessary to build the complete decoder including power supply and video switching unit. Signal input required is a minimum of 1.0V detected video. The output is approx. 4V of R, G and B drive suitable for driving most types of Colour Television sets, plus a luminance output for black and white sets. The power supply and video switching circuitry are normally installed within the television cabinet and the main decoding, control and memory circuitry are in a separate cabinet (approx. 10 1/2" x 3" x 7 3/4") positioned on top of the television. Lower case characters may be added by using an extra add-on printed circuit board unit.


Reprint of "Wireless World" articles now available at £1.50 + large 14p s.a.e.

Price of component kit — £111.20

Add On unit for lower case — £13.50

Cabinet and chassis — £14.85

Post and Packing — add £1.75

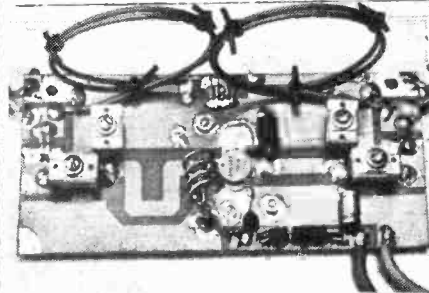


**2 METER
POWER
AMP**
as described
SEPTEMBER
ISSUE
(page 19)

2 METER POWER AMPLIFIER

Complete Kit to build this 40 watt power amplifier — £17.50.
Components available separately — PCB £1.23; 2N6084, £13.60; BAVIO, 11p;
RG174/U coax, 25p/m.

LOW COST V.D.U.

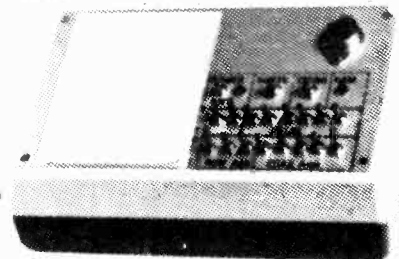

All items available for this project.

Complete Kit at special price — £57.00 + 75p P&P.

Components also available separately — PCB set, £7.00; 2112-2, £4.25; 2513, £9.18; 555, 47p; 7400 series — write for list of new low prices.

Mains transformer — £2.75; Mains on/off switch, 68p; Min. S.P. toggle switch, 54p; Min. push-to-make switch, 34p; High Quality plastic case with aluminium front panel (as illustrated in E.T.I. article) £4.45.

Send S.A.E. for full price list or 30p plus large 11p S.A.E. for your copy of our Data Catalogue. All prices include VAT at current rates. Please note our minimum U.K. post and packing charge, except where indicated, is 20p EXPORT ORDERS welcomed — write for export price list.

PLEASE NOTE NEW ADDRESS:

COMMUNICATIONS HOUSE

DEPT. 652 20 WALLINGTON SQUARE

WALLINGTON, SURREY, SM6 8RG

Tel: 01-669 6700 (9 a.m. to 6 p.m., 1 p.m. Sat.)

electronics today



international

What to look for in the January issue: On sale Dec 3rd

R.M. MARSTON DESCRIBES:

38 555 TIMER CIRCUITS

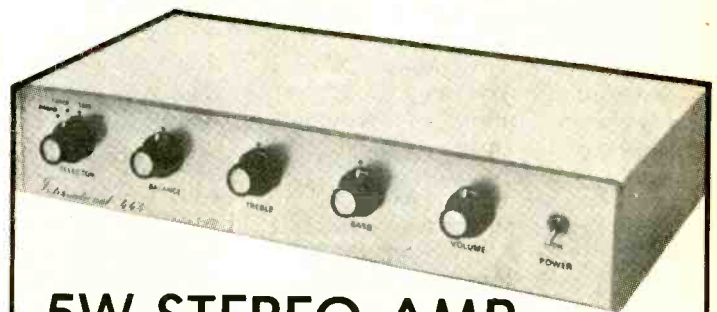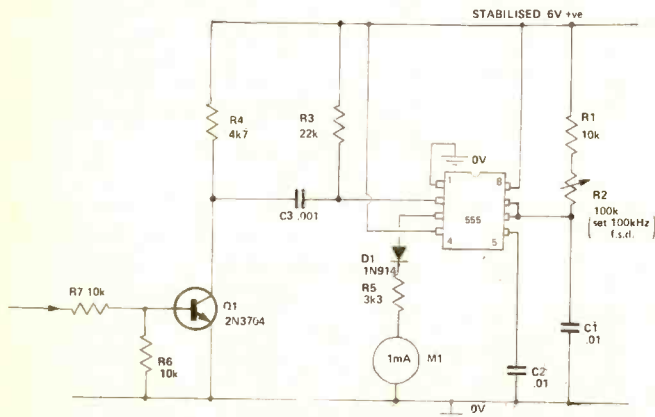The definitive words on the famous 555 IC from R. M. Marston — one of Britain's best known and respected electronics authors. This article provides no less than 38 different applications for the 555 many of them brand new!



5W STEREO AMP

A 'nice and easy' project. A simple but high quality 5W stereo amplifier. Based on two I.C.s, the construction is simple, but the sound is superb!

READER OFFER

READER OFFER. We're faced with a problem with this type of offer: as the product hasn't been announced yet we're sworn to secrecy (sorry about the cloak-n-dagger bit). What we can say is that it's a very low priced offer on a new aid for the electronics lab and amateur enthusiast.

ELECTRONICS IN THE NORTH SEA:

We got wet on this one! Providing a well detailed look at how Britain pulls in the black gold from the North Sea — from the electronics point of view. The companies have been very co-operative and we think you'll agree this was worth the trouble.

NEW SERIES: SHORT CIRCUITS

In the next issue we start a new series: Short-circuits. These will describe straightforward projects in a short and sweet form — there'll be no unnecessary 'blurb' with them. Many will be simple but it's not specifically a beginners' series — some projects will be highly sophisticated in concept.

The January issue contains three such projects. PATCH DETECTOR is a one-transistor circuit costing under £2.00. For use when buying a second-hand car to find if body filler has been used. HEADS OR TAILS is an ingenious application of a very standard circuit. Our SCR TESTER can be built easily in an evening and can also be used to test power diodes.

VCT?

For the last few weeks when you've met anyone well informed about electronics they'll have brought up VCT. What is it? Well it may not replace the Op. Amp but it'll stunt its growth: it's a completely new type of IC. Information is very, very scant at present — and much of sheer rumour but we hope to bring you the essence next month — at least a month before it's officially announced!

The cover price of ETI will go up from 30p to 35p with the January issue. We've held our price since May 1975 — that's probably a record for magazines — but we'll still be the cheapest electronics magazine and the one with the most editorial.

We hope readers will still consider ETI overwhelmingly the best value for money.

PART 10 - PROGRAMMING

IT SEEMS TO BE a fairly common problem amongst electronics engineers and enthusiasts approaching micro-processors for the first time, that although they can usually wade through the electrical characteristics, timing diagrams, interface circuitry and conventional problems of that type, they almost always have a mental block on the subject of programming. Although programming is taught in many schools and probably all universities now, it is still somewhat of a mystery to the majority of people. Perhaps this is due to the popular image of the programmer as a white-coated demi-god who commands vast roomfuls of spinning tape reels and flashing lights, and who spends his time computing the origins of the universe or checking tax returns (equally complex problems as far as I'm concerned!).

The fact of the matter is that there is no mystique to computer programming, and if the truth be known, as many computer programmers are baffled by electronics as vice-versa. Let's tackle the problem of programming and see what's involved.

A program is simply a sequence of instructions which make a computer (including a microcomputer) perform a specified function. That's the definition that's perpetually given in the textbooks, but it's not much use if you're faced with writing a program for the first time. What the budding programmer wants to know is: what is the process that takes you from the problem to be solved to the program that will give the solution?

The first step is usually a definition of the problem; in other words, ask yourself what *exactly* you want to do. Research the problem thoroughly so that you understand it — it's no good writing a beautifully elegant solution for the wrong problem. This is a good time to think about the people who will be using the system and design in some useful features — for instance, a program which calculates the voltages in a circuit as the input varies could give the results in the form of tables or a graph. Which would be more useful — or can you offer both?

This section of the process will usually give some possible methods of tackling the problem. The trick here is to break the problem down into a number of separate tasks which can be performed *sequentially* — a computer (or MPU) cannot do more than one thing at a time, though of course it operates so fast that it may seem to. Let's take as an example the simple problem of controlling a single traffic light. The processor has to first turn on the red light. It will then wait for a preset time interval by performing a loop program such as counting down from a preset number to zero. At the end of the loop it will turn on the amber light, and start counting again. At the end of this time interval it will turn off both the red and the amber, and turn on the green. Again it counts down and then turns off the green and turns on the amber. Finally, another counter loop and then back to red.

That's a rough idea of how an MPU would tackle the job — now let's get more specific and examine how the abilities of the processor and the hardware around it can modify your approach. If we use M6800 as an example, it seems obvious to use the M6820 Peripheral Interface Adapter to drive the lamps. In fact one PIA could drive 5 sets of traffic lights and still have inputs available for detecting cars passing over sensors in the road. The individual lamps would be connected to bits in the PIA Data Registers, so that a '1' in that position would turn the light on and a '0' would turn it off. Thus, a single memory write instruction could instantaneously set up 8 lamps and there is now no need for an instruction to turn off lamps.

SUBROUTINES

Notice also that we had 4 sections of the program concerned only with counting down to zero — it seems rather silly to write the same thing 4 times over. The M6800, in common with most micros, has the capability of jumping to, and returning from, subroutines. Hence we would write a subroutine to subtract 1 perpetually



O.K. MASTERMIND ----
DONT TELL ME YOUR DIAGNOSIS
OF BARKHAUSEN OSCILLATION
WAS WRONG AFTER ALL!?

from an accumulator and then check to see if it is zero. If it is, control will then be passed back to the main program, otherwise it will keep on subtracting. This can be written in various forms: as the flowchart in Fig.1, or as the assembly language routine or object code given in Fig.2.

In general, flowcharts are a very good way of concreting one's thoughts on a particular problem. However, as the program gets more complex, so does the flowchart, only more so! The trend today seems to be towards programmers writing in a high level language and then either using a compiler or converting to assembly language or object code by hand. The idea is to firm up one's approach to the solution and gradually, through several intermediate stages, to become more specific until one reaches the level of machine code. This tends to ensure that all the segments of the program are compatible.

PROGRAM EXAMPLE

This is an example of a very useful program which has been sent to us by Mr. J. Kennedy of Wantage. A frequent requirement in micro-processor systems is that they respond to the passage of time. To

do this they need to have some form of internal clock apart from the one which actually drives the system. Such a device is called a Real Time Clock. The one described here relies upon both hardware and software to gain the advantages of both. To write a Real Time Clock entirely in software would mean (a) a long program and (b) the processor could not execute any other program - which is a bit useless! On the other hand, to implement a clock completely in hardware can be quite expensive, even using a CMOS clock chip with BCD outputs.

This system uses 1Hz pulses (derived from the mains) to pulse the Non-Maskable Interrupt of the processor chip, thus causing it to jump to the interrupt service routine given here and update its internal time which is held in 3 consecutive memory locations.

A suggested circuit to derive these pulses is given in Fig.3, but this has not yet been tried and tested. An alternative would be to use a crystal controlled oscillator and dividers.

The software consists of 2 sections which is a lump of data comprising time and data required by the main program and the Real Time Clock program itself (memory locations 10 to 28). We shall leave the reader to puzzle the operation of this program out for himself but you should note the extensive use of indexed addressing which is one of the most useful features found in current microprocessors.


MICROPROCESSORS AT WORK

was the title of a symposium held for 3 days in September at Sussex University by the Society of Electronic and Radio Technicians.


The dictionary defines 'symposium' as an ancient Greek drinking party, or a set of articles on one subject, or philosophical or other free discussion. This symposium managed to be all of these, allowing for the fact that there weren't any Greeks there.

20 papers were presented by representatives from the semiconductor manufacturers, by industrial users and academics.

These were varied in content from the almost abstract to the completely down to earth. Two papers in particular are of interest to the amateur: 'Some Experience for Multipurpose Microprocessor System Development' by R.A. Smith of Essex University, and 'Hardware for Teaching Microprocessor Interfacing and Programming' by Dr. D.J. Quarmby of Loughborough University. Both these papers dealt with the development of low cost hardware, in particular avoiding the use of a Teletype.

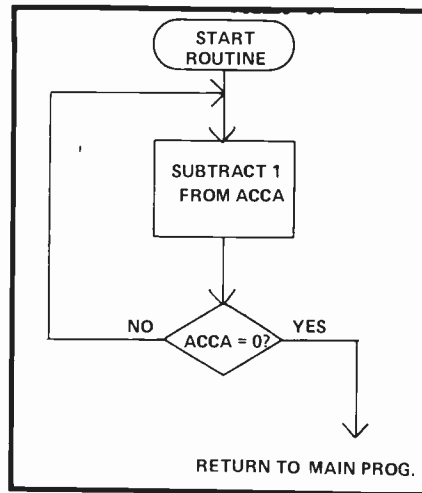

LOOP	DEC A	4A	
	BEQ RETN	27	02
	BRA LOOP	20	FB
RETN	RTS	39	

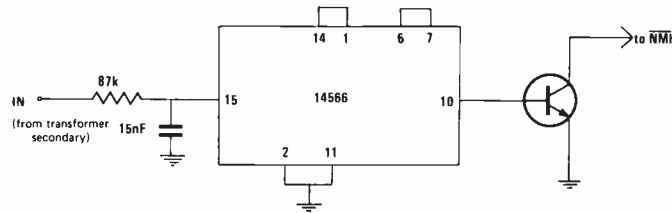

Memory Location	Op-code	Logic Instruction	
001	11		
002	03	Time = 11-03-58	Data
003	58		
004	24	limit of Hrs. loop	
005	60	limit of Mins. loop	Data
006	60	limit of Secs. loop	
010	CE	LDX 03	
011	00		
012	03		
013	A6	LDA A 0,X	
014	00		
015	4C	INC A	
016	19	DAA	
017	A1	CMP A 3,X	
018	03		
019	2D	BLT 0B	
01A	0B		
01B	6F	CLR 0,X	
01C	00		
01D	09	DEX	
01E	8C	CPX 0000	
01F	00		
020	00		
021	27	BEQ 03	
022	03		
023	7E	JMP 0013	
024	00		
025	13		
026	A7	STA A 0,X	
027	00		
028	3B	RTI	

One interesting fact that emerged from the symposium was the ability of large organisations undertaking development to generate their own development systems in both hardware and software. For instance, several large organisations anticipated that program development would be considerably speeded up by the use of a high level language and so they wrote a compiler for the language of their choice. At least one organisation specially adapted a minicomputer to check out their special purpose hardware.

British Rail engineers presented an amusing (almost Pythonesque) paper on 'Microprocessors in Safety Systems'. This dealt with a self-

checking system based on 3 micros which checked each other and on finding a disagreement tried to blow each other up. Although this may sound rather odd, it is in fact an extremely sensible principle to follow in the design of fail-safe systems where a faulty processor has to be removed from the system before it can adversely influence performance.

Volumes of papers presented at the Symposium are available from SERT at 8-10 Charing Cross Road, London WC2H 0HP. for £7.50 inc. postage.

8080 RESIDENT COMPILER

Intel have just announced a major new software system that enables PL/M programs to be compiled on the 8080 itself. The new resident compiler and its supporting software automatically link program modules together to form the user's overall program. PL/M is a high level language which was developed by Intel from the well-known IBM language PL/1 about 3 years ago. Until now, programs written in PL/M had to be compiled into 8080 machine code using a main frame computer which usually meant that the user employed the services of a time-sharing bureau for this purpose. Running this compiler on the Intel MDS800 development system will enable the high cost of time-sharing to be avoided.

The linkage facility is provided by a new disk operating system called ISIS2 which generates linkable and relocatable object code modules from a new macro assembler contained in the package, thus enabling several independent software designers to work on the same overall program without conflict.

The resident PL/M compiler provides other features which have not been available hitherto. It allows the programmer to define data structures and also gives him access to absolute addresses. The user can request the compiler to generate re-entrant code for any procedure, and it will also produce a cross reference list on request or optionally print an 'inner list' of generated assembly language after each PL/M statement.

Also new from Intel is a system controller chip for the 8080A micro which is particularly suited for use in systems containing dynamic RAMs. The 8238 is identical in pin-out and function to the 8228 system controller except that the timing of the 'Memory Write' (MEMW) and 'Input/Output Write' (IOW) outputs has been advanced so that they become available two clock pulses earlier than with the 8228. This means that memory and I/O circuitry have longer to respond and system timing margins are improved.


IM6100 ON OFFER

Rapid Recall are offering the IM6100 microprocessor and support chips in a set for only £42.70 + VAT. The set comprises one IM6100 CMOS processor, one 6312 1k x 12 ROM containing a system monitor, three 6561 256 x 4 CMOS RAMs, one 6101 CMOS parallel interface element and one 6402 CMOS UART for serial interface. The IM6100 (as we never tire of saying!) is software compatible with DEC's PDP-8/E minicomputer. In addition, being CMOS the MPU consumes very little power and can be halted without loss of register contents.

If you don't feel like doing it the hard way, Rapid Recall would no

doubt be happy to sell you an Intercept Junior evaluation system. This comprises a complete IM6100 microcomputer with 256 12-bit words of RAM and a socket for ROM evaluation, a data/instruction entry keyboard, an eight-digit octal output display, a microinterpreter, 3 expansion card connectors and a mounting arrangement for the four torch batteries which power the unit. At the present moment three expansion modules are available: a 1k x 12 bit non-volatile RAM card, a ROM/PROM card, and a serial communications card for VDU or TTY.

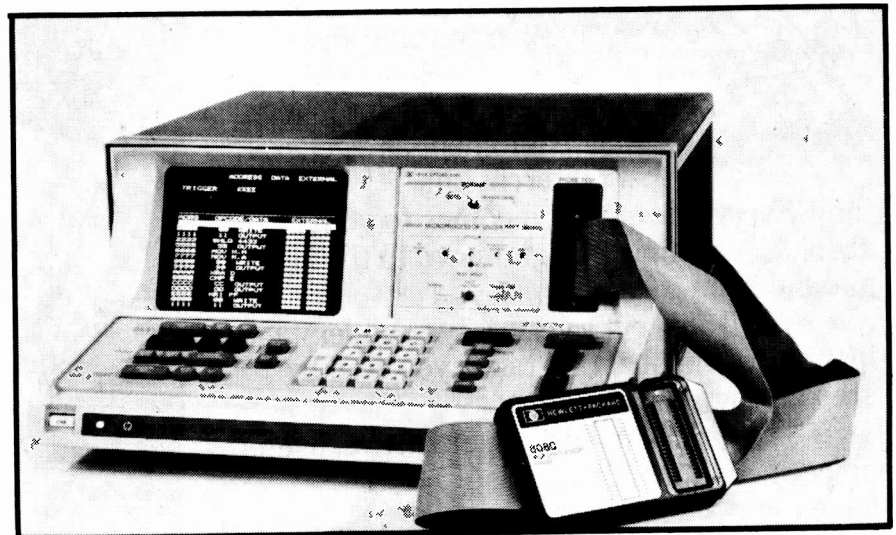Rapid Recall Ltd., 9 Betterton Street, Drury Lane, London WC2H 9BS.



HP LOGIC ANALYZER

New keyboard-controlled logic state analyzers from Hewlett-Packard are dedicated to the design and troubleshooting of systems using 8080 or 6800 microprocessors. An HP-1611A is specialised to one type of system or the other by choice of an 8080 or 6800 'personality module.' Others will be added.

When a 1611A Logic State Analyzer is connected to the circuitry (at the microprocessor's socket, and simultaneously to as many as eight other points if desired), system activity can be displayed on the instrument's CRT directly in the alphanumeric mnemonics of the particular microprocessor's own instruction set. With powerful qualifiers, the 1611A can frame a real-time window around virtually any event, or set of related events - any desired sequence of system operations. The 1611A also accurately measures true execution timing, or counts selected events, as specified by the keyboard. At a point defined by the user, the instrument can halt microprocessor operations; then, if desired, the 1611A can control the transactions that


follow, in single or multiple keyed steps.

On the 1611A CRT screen appears alphanumeric information about the keyboard settings, as well as the data captured. As directed by the keyboard, the instrument traces and identifies memory transaction after memory transaction in the system's sequence of operations.

It stores 64 of these, displaying the top 16 until the scroll keys are used. (The number of instructions identified is usually less than the number of memory transactions, since an instruction often calls for more than one memory fetch.) A switch selects octal or hexadecimal data listing. Op Code readout may be numeric, or alphanumeric mnemonics may be spelled out, as in the microprocessor manufacturer's programming manual.

The 1611A is, itself, a microprocessor-controlled instrument operated from a keyboard (The micro used is the 8080). U.K. price of the HP-1611A, Option 080 (for 8080 systems) or Option 068 (for 6800 systems) is £3,650. Extra personality modules are £730. Hewlett-Packard Ltd., King Street Lane, Winnersh, Wokingham RG11 5AR.

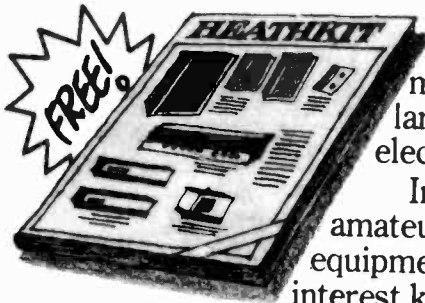Your free start to a rewarding new hobby.



Heathkit make the world's largest range of electronic kits.

Including hi-fi, amateur radio, test equipment and general interest kits.


Every one of which comes to you absolutely complete—right down to the last nut and bolt.

You'll also get a very easy to understand instruction manual that takes you step by step through the assembly.

So, besides making an attractive, useful piece of equipment, you'll also have the makings of a satisfying, rewarding hobby.

To find out more, post the coupon we'll send you our latest catalogue.

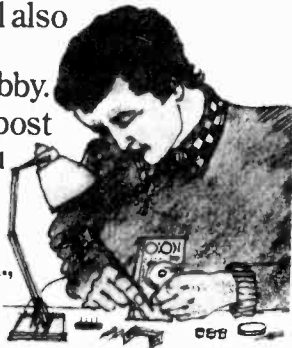Heath (Gloucester) Ltd.,
Dept. ETI-126, Bristol Rd.,
Gloucester, GL2 6EE.
Tel: Glos (0452) 29451.



HEATHKIT

BETTER BUILT BECAUSE YOU BUILD IT YOURSELF

The new Heathkit catalogue. Out now. FREE.

To: Heath (Gloucester) Ltd., Dept. ETI-126, Gloucester, GL2 6EE. Please send me my Heathkit catalogue. I enclose an 11p stamp for postage.

Name _____



Address _____

Postcode _____




EASY TERMS AVAILABLE WITH HEATHKIT MONTHLY BUDGET PLAN

Showrooms at 233 Tottenham Court Road, London and Bristol Road, Gloucester.

The easy way to a PCB...

...the Seno 33 system!

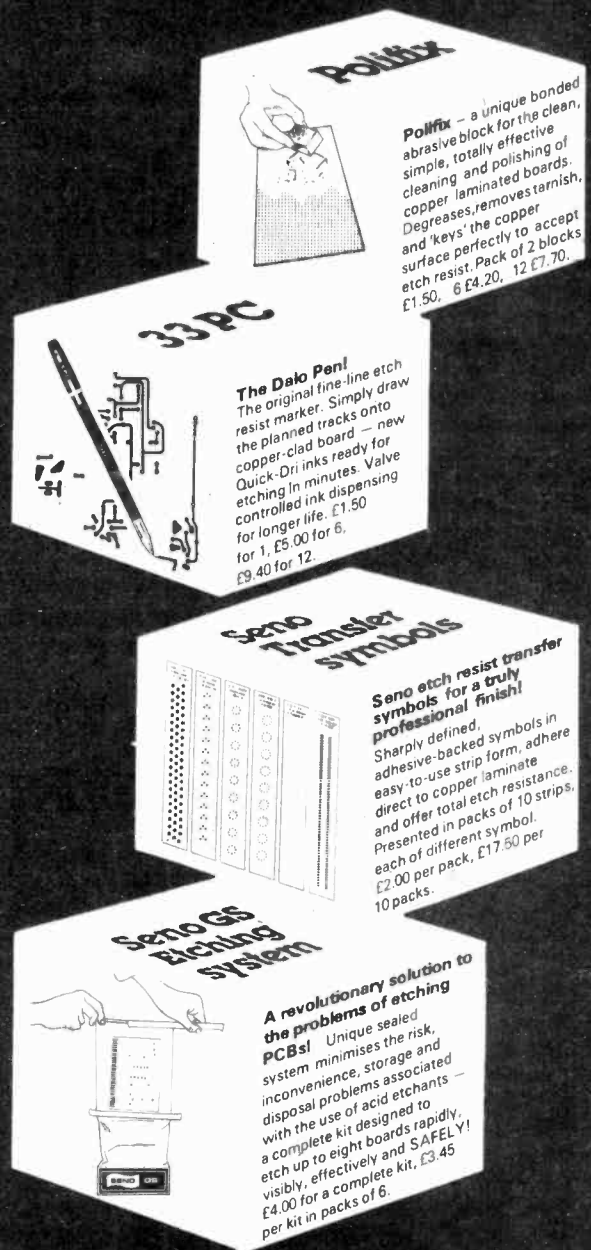

Polifix — a unique bonded abrasive block for the clean, simple, totally effective cleaning and polishing of copper laminated boards. Degreases, removes tarnish, and 'keys' the copper surface perfectly to accept etch resist. Pack of 2 blocks £1.50, 6 £4.20, 12 £7.70.

The Dalo Pen
The original fine-line etch resist marker. Simply draw the planned tracks onto the copper-clad board — new copper-clad inks ready for Quick-Dri inks ready for etching in minutes. Valve controlled ink dispensing for longer life. £1.50 for 1, £5.00 for 6, £9.40 for 12.

Seno etch resist transfer symbols for a truly professional finish!
Sharply defined, adhesive-backed symbols in easy-to-use strip form, adhere direct to copper laminate and offer total etch resistance. Presented in packs of 10 strips, each of different symbol. £2.00 per pack, £17.50 per 10 packs.

A revolutionary solution to the problems of etching PCBs! Unique sealed system minimises the risk, inconvenience, storage and disposal problems associated with the use of acid etchants — a complete kit designed to etch up to eight boards rapidly, visibly, effectively and SAFELY! £4.00 for a complete kit, £3.45 per kit in packs of 6.

**Seno 33 —
The Laboratory in a box**

From your usual component supplier or direct from:

DECON LABORATORIES LTD.
Ellen Street, Portskadee,
Brighton BN4 1EQ
Telephone: (0273) 414371
Telex: IDACON BRIGHTON 874 43

All prices post & VAT inclusive. Data sheets free of charge

TOUCH ORGAN

With all the electronics on one pc board this organ is easy to build yet has features like touch keyboard, variable tremolo, two voices and a full two-octave range.

AN ELECTRONIC ORGAN IS A fascinating instrument which these days seems to be rapidly assuming the position in the home once occupied by the piano. Modern organs are, however, very expensive which puts them beyond the reach of most people. Lower down the scale in cost and performance are chord organs which although still polyphonic are fairly limited reed type instruments operated by a small blower. The name chord organ comes from the fact that the bass accompaniment is by means of buttons which generate the appropriate chord.

The cheapest possible organ is the so called monophonic organ (only one note can be played at a time) which is usually little more than pocket sized and is played with a stylus.

The first obvious improvement

required is to devise a better keyboard arrangement as the stylus operation can only be described as somewhat of a nuisance. However the £40 cost of a full keyboard cannot be justified. As can be seen from the photographs the new keyboard is still of the touch type but has now been designed so that the organ is played simply by touching the appropriate key, as in a full scale instrument. Tremolo is also provided and this too is switched on and off by means of touch switches and a control is provided to adjust tremolo depth.

The next improvement is in the accuracy of the tuning, which in the previous instrument varied over the keyboard due to the one-only resistor used to increment between each note. In our new version tuning over the keyboard is much improved by using two resistors,


where necessary in series or parallel, to obtain the nearest possible to the correct value of resistance. Finally the instrument is provided with two voices or stops which add greatly to the variety of the music which can be produced.

This little organ is relatively inexpensive to build, should provide a great deal of enjoyment and is musically and electronically educational.


DESIGN FEATURES

As mentioned earlier the major feature is the implementation of the keyboard by means of a finger touch system rather than the "probe" type.

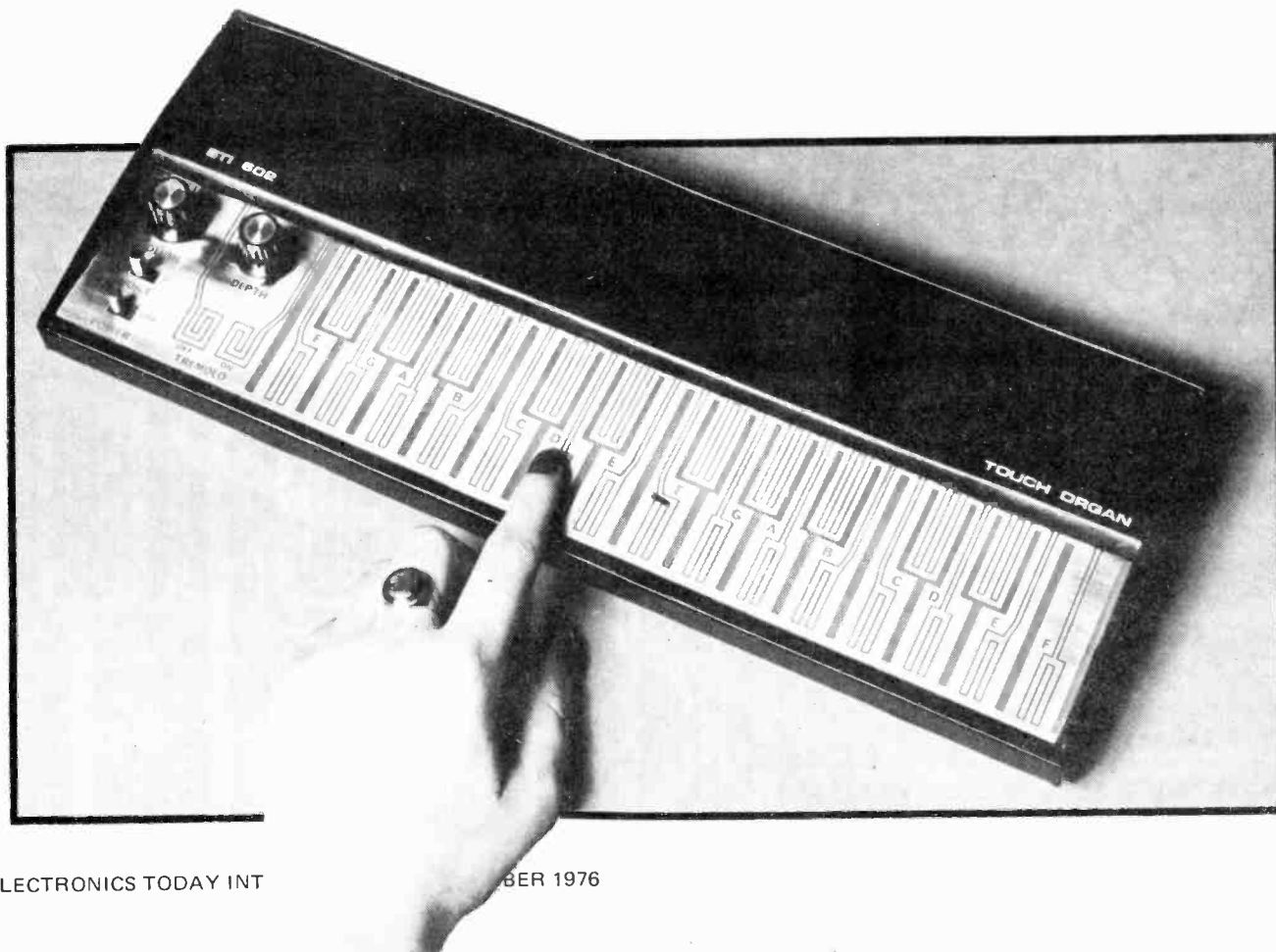This means that some electronics must be associated with each key to detect that it has been touched. Touch control is usually effected by the capacitive, resistive or 50 Hz injection methods. Whilst the capa-





TOUCH ORGAN

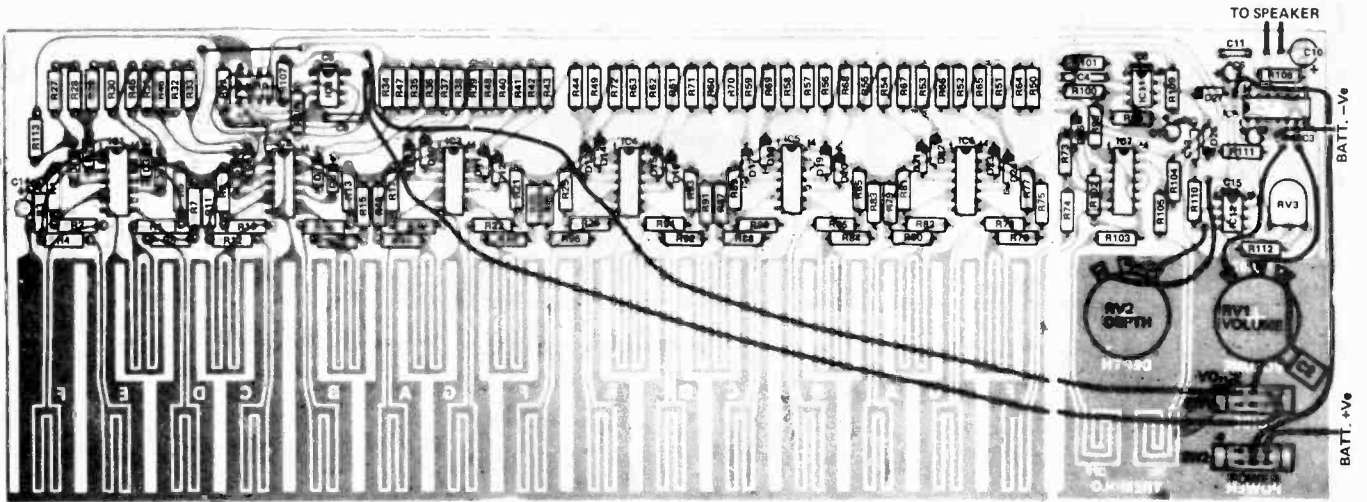

Parts List

Resistors all 1/2W 5%	R32	8k2	R46	68k	R58	120k	R79,81,83	4M7	R105	100k
R1,3,5,7	4M7	R33	1k2	R47	220k	R59	R85,87,89	4M7	R106	5k6
R9,11,13	4M7	R34,35	10k	R48		R60	R91,93,95	4M7	R107	820k
R15,17,19	4M7	R36	270	R49	330k	R61			R108	2.7 Ω
R21,23,25	4M7	R37	10k	R50	120k	R62			R109	22k
R2,4,6,8	100k	R38	1k	R51	180k	R63	R74,76,78	100k	R110	330k
R10,12,14	100k	R39	12k	R52	560k	R64	R80,82,84	100k	R111	10k
R16,18,20	100k	R40	10k		270k	R65,66,67	R86,88,90	100k	R112	15k
R22,24,26	100k	R41	2k2			R68,69	R92,94,96	100k		
R27	6k8	R42	8k2	R53	180k	R70,71	R97	6k8		
R28	330			R54	22k		R98,99,100	100k		
R29	6k8	R43	4k7	R55	390k		R101	820k	Potentiometers	
R30	390	R44	15k	R56	4k7	R72	R102	4M7	RV1	47k log
R31	10k	R45	8k2	R57	15k	R73,75,77	R103	100k	RV2	47k log
							R104	4M7	RV3	2k trim

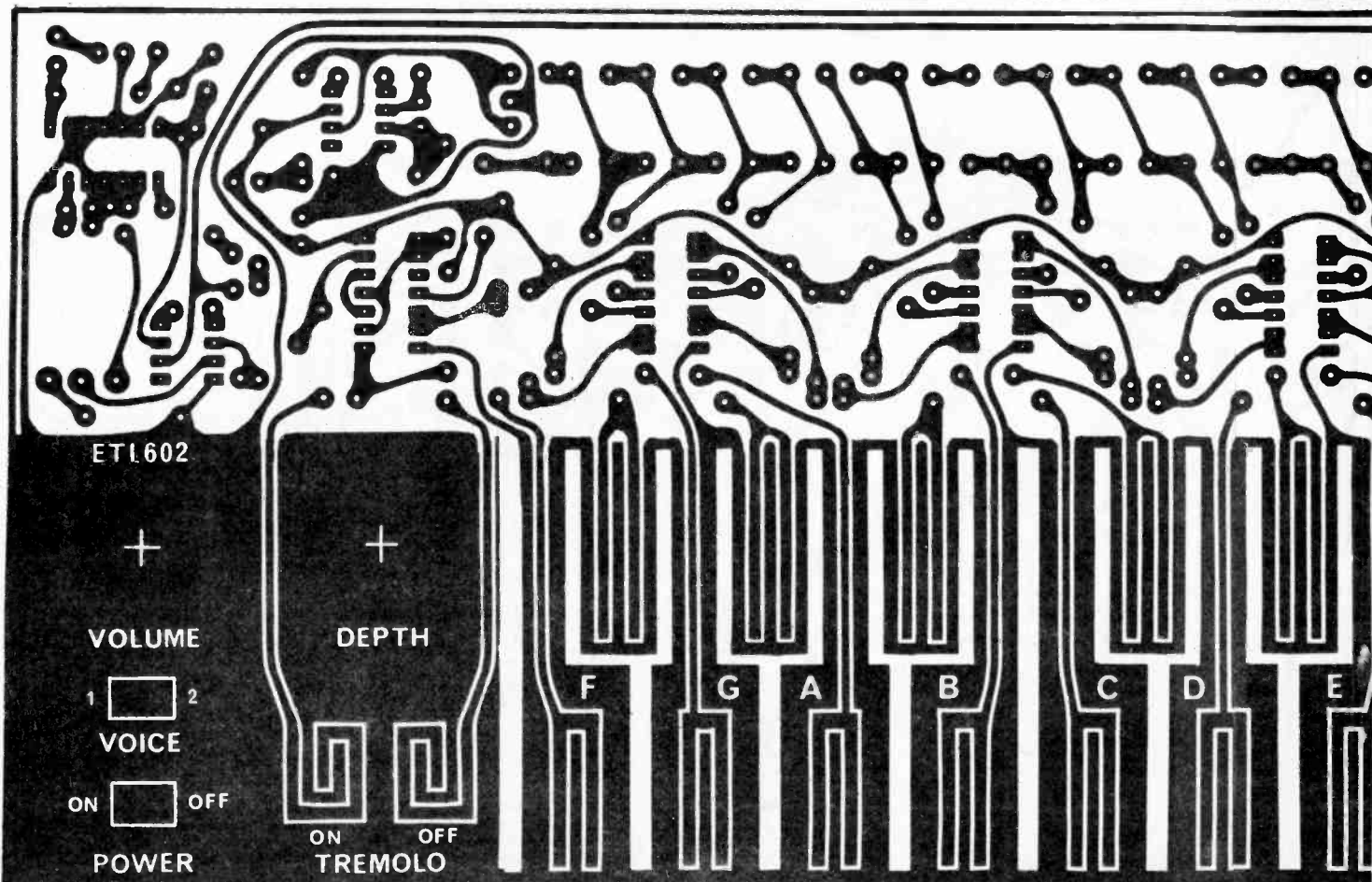

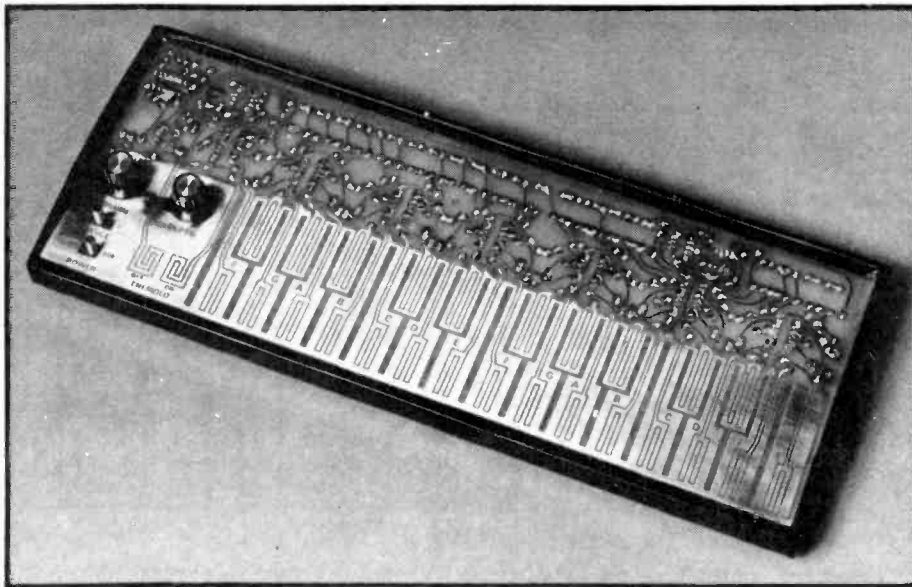

Frequency of Notes used

F	698.5
E	659.3
D#	622.3
D	587.3
C#	554.4
C	523.3
B	493.9
A#	466.2
A	440.0
G#	415.3
G	392.0
F#	370.0
F	349.2
E	329.6
D#	311.1
D	293.7
C#	277.2
C	261.6
B	246.9
A#	233.1
A	220.0
G#	207.7
G	196.0
F#	185.0
F	174.6

Capacitors

C1	22n polyester
C2	100n polyester
C3	330p ceramic
C4	100n polyester
C5	33p ceramic
C6,7	4μ7 25V electrolytic
C8	33p ceramic
C9	100n polyester
C10	100μ 16V electrolytic
C11	100n polyester
C12	4μ7 25V electrolytic
C13	100n polyester
C14	100μ 16V electrolytic
C15	33p ceramic


Semiconductors

D1-D27	1N914 or similar
IC1 - IC7	4011 (CMOS)
IC 8,11,12*	LM301 or 741
IC9	LM380,SL60745
IC10	NE555
*if 741s are used delete C5,8,15	

Miscellaneous


SW1,2	single pole, 2 position slide switches
PC board ETI 602	
Two knobs	
6 way battery holder	
Small 8 or 16 ohm speaker	
battery clip	
case to suit	

rotary
rotary
mer

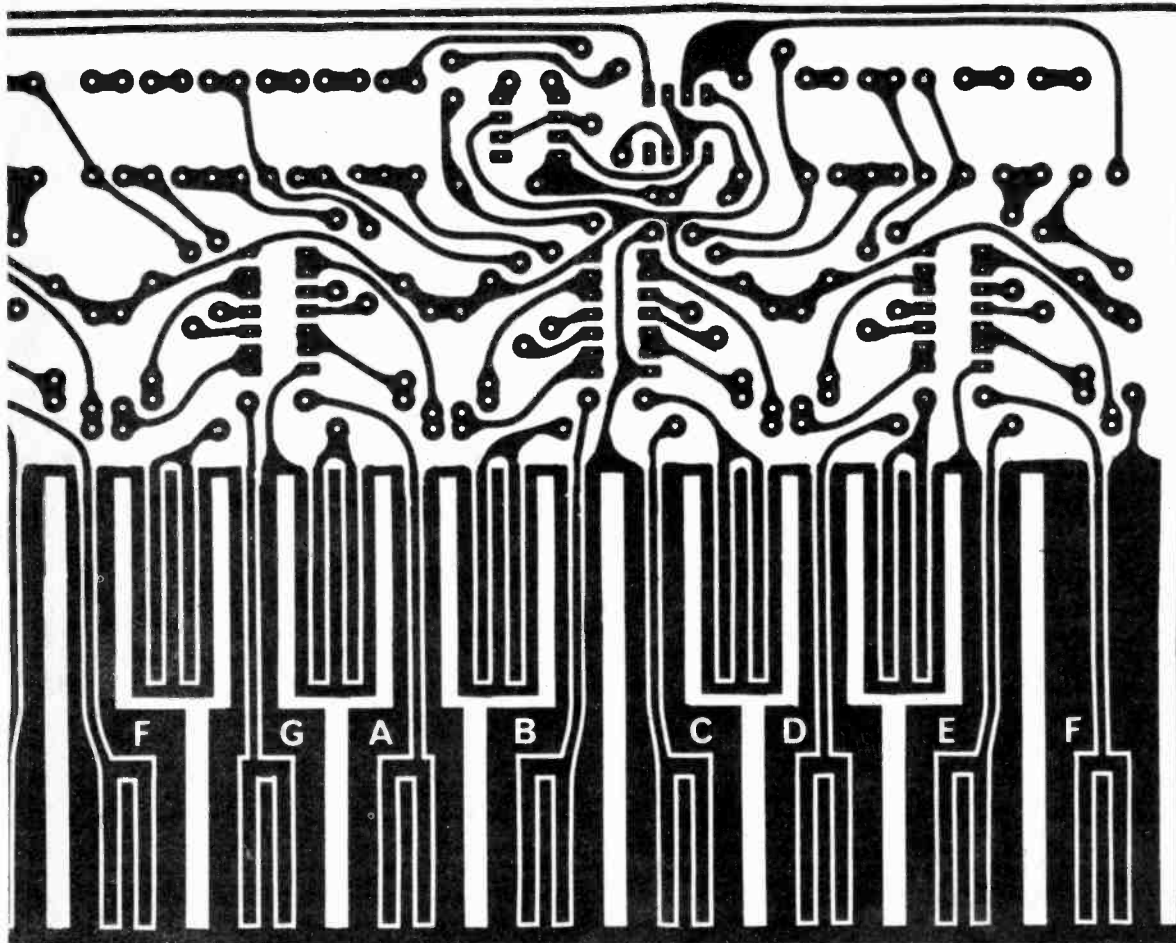

Printed-circuit board layout for the monophonic organ. Full size 345x120 mm.

TOUCH ORGAN

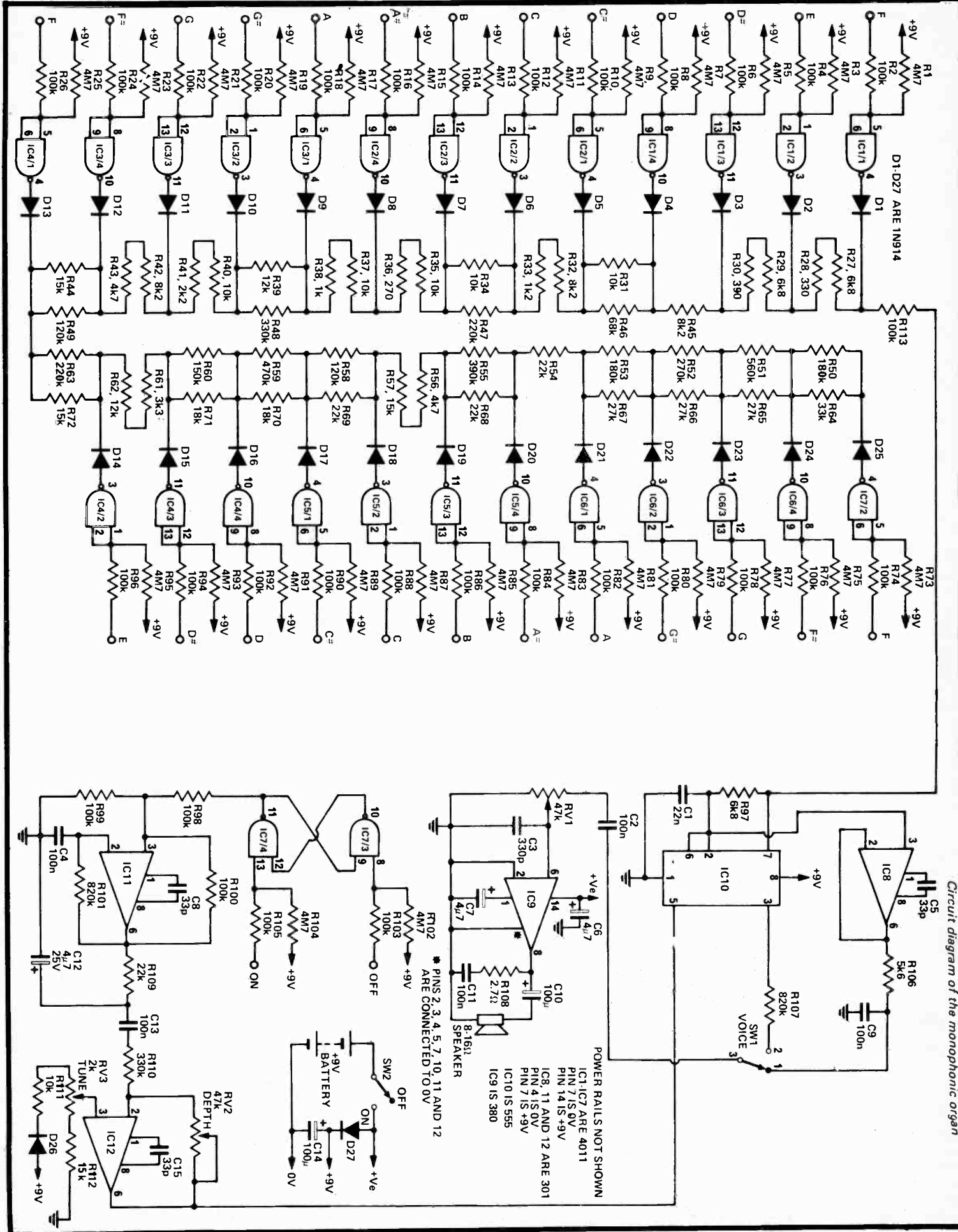

How it works

Operation of the organ will be described by considering separately the five sections of which it is composed. These are:

- (a) Keyboard
- (b) Oscillator
- (c) Filter
- (d) Output amplifier
- (e) Tremolo circuit

(a) Keyboard. Unlike the previous organ the keyboard is operated by the contact resistance of the finger and not by a probe. Each key has a CMOS gate associated with it where both inputs to the gate are connected together and to the positive supply via a 4.7 megohm resistor. When the key is touched the inputs of the gate are pulled low (0V) via the 100 k resistor causing the output of the gate to go high. This pulls the corresponding point in the resistor chain high via the diode. Thus by selecting and touching different keys we connect various amounts of resistance between pins 2 and 6 of the 555 oscillator and the positive supply, thus enabling it and varying the frequency determining time constant circuit.

(b) The Oscillator. The oscillator is based on a 555 timer IC. The capacitor C1 is charged up via a section of the resistor chain (as by the keyboard) together with the resistor

R113. When the voltage at pins 2 and 6 reaches that set at pin 5, the capacitor is discharged rapidly via R97 and an internal transistor connected to pin 7 of the 555. When the voltage across C1 has dropped to half that set at pin 5, the internal transistor turns off and the capacitor is allowed to charge up again — thus repeating the cycle and generating a sawtooth waveform across the capacitor. This waveform has a high harmonic content but is generated at a high-impedance point. A unity gain buffer is therefore used (IC8) to prevent this output from being loaded by the following circuitry. A second output of a narrow pulse waveform is available at pin 3 of the 555 and this is used to generate a second voice for the instrument.


(c) Filter. A number of different filters were tried but from a cost point of view it was difficult to justify anything more than a simple RC filter on the sawtooth which gives quite a pleasant flute-like effect. As the narrow pulse train sounds somewhat similar to strings it is merely attenuated to match the level of the filtered sawtooth.

(d) The Output Amplifier. The loudspeaker is driven by an LM380. Volume control is provided by means of potentiometers RV1 and the required voice is selected by means of switch SW1. The LM380 should be fitted with heatsink fins as detailed in the

construction.

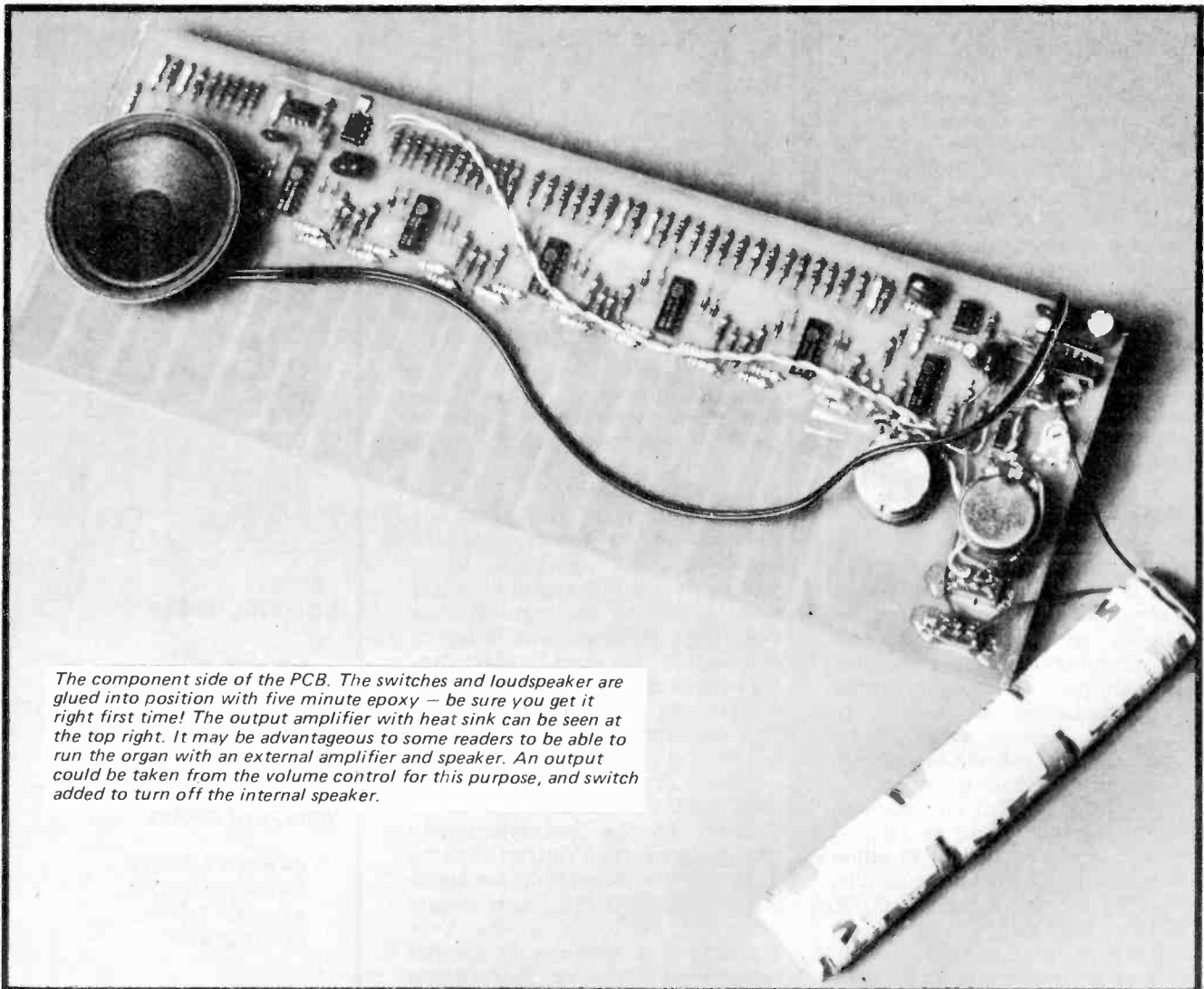(e) The Tremolo Circuit. Tremolo is produced by means of a low frequency oscillator running at approximately 8 Hz (IC11). The oscillator can be turned on and off by means of the flip flop formed by gates IC7/3 and IC7/4. This flip flop is set to the 'on' or 'off' mode by means of touch switches which operate in exactly the same manner as the main keyboard. To increase tremolo frequency decrease R101 and vice versa.

The output from the tremolo oscillator is filtered by C12 and R109 to give a smoother waveform and the resultant waveform buffered by IC12. The gain of IC12 is adjustable by means of RV2 and this control therefore adjusts the depth of the tremolo modulation. The potentiometer RV3 is a trim potentiometer which effectively sets the output from IC12 to pin 5 of the 555 and thus the frequency of the organ. If it is required to shift the keyboard up or down an octave or so this may be done by changing the value of C1 by a factor of two. If the keyboard tuning is found to be skewed (when tuned correctly at the centre one end of the keyboard is low whilst the other is high) this may be cured by changing the value of R97. If it is sharp at the low end decrease R97 while if flat at the low end increase R97.



The component side of the PCB. The switches and loudspeaker are glued into position with five minute epoxy — be sure you get it right first time! The output amplifier with heat sink can be seen at the top right. It may be advantageous to some readers to be able to run the organ with an external amplifier and speaker. An output could be taken from the volume control for this purpose, and switch added to turn off the internal speaker.

TOUCH ORGAN

citive method is the best of these it is also the most expensive and for this reason is not used. The 50 Hz injection method is also complex and thus the resistive method was considered to be the only practical way from a cost point of view.

As the keyboard is now played by the finger it also needs to be larger than usual although still not quite as large as a full-size keyboard.

In the original concept an OM 802 was used as the tone oscillator. This was replaced by a 555 timer IC as this is cheaper and easier to use. The 555 has two outputs which can be used, a sawtooth wave and a narrow pulse. Both of these outputs are used in our design to provide different voices for the instrument. The sawtooth is filtered by means of a simple RC filter to remove some of the harshness due to the harmonic structure and the resultant voice has a rich flute-like sound. The pulse output is matched in level to the sawtooth by means of a resistive attenuator but is otherwise unfiltered. This voice has a string-like sound.

Filtering has been kept very simple, again from a cost point of view. If the constructor desires he may experiment with different filters in order to achieve different sounds. With conventional organs the stop-filtering is done for every octave of the organ to prevent undue tone and level changes at different frequencies. With the two octave span of this organ some change in tone and level must be accepted over the range of the keyboard when using simple filters.

As attenuating filters are used in the organ plenty of gain is required in the audio stage and for this reason an LM380 is used in the audio output stage to drive the loudspeaker.

CONSTRUCTION

The keyboard pattern is etched directly onto the printed-circuit board which also carries the rest of the electronics. As the copper of the keyboard would rapidly tarnish when continuously being touched with the finger it is necessary for the board to be either tinned or protected with some other plating process that will prevent tarnishing.


Commence construction by mounting the LM380 into position and then fit small heatsink fins, as shown in the photograph, to either side of the IC. Solder them to pins 3, 4, 5 on one side and pins 10, 11 and 12 on the other. This should be done first as there is little room in this area of the board once other components are in position. Fit the

two wire links and assemble the low-height components to the board as shown on the overlay.

Mount the remaining ICs last of all and take particular care not to handle the CMOS ICs excessively before insertion. Check the polarities of polarised components such as ICs, capacitors and diodes before soldering them into position.

To avoid having screws showing on the keyboard we glued the two switches into position with five-minute epoxy. Use a piece of printed-circuit board or metal behind each mounting hole to obtain extra glueing surface and extra strength. Mount the potentiometers and wire the complete board as detailed in the overlay diagram.

The complete unit should now be tested to ensure that all notes and functions are operating correctly before mounting into a suitable cabinet.

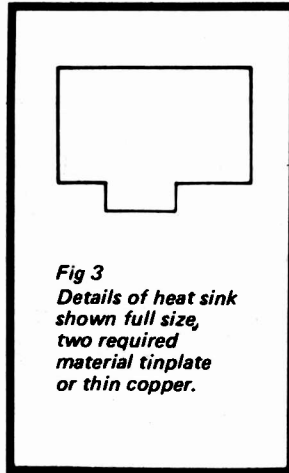

*Fig 3
Details of heat sink
shown full size,
two required
material tinplate
or thin copper.*

PLAYING THE ORGAN

Although the new organ is played with the fingers as with a full instrument there are a few small playing differences which should be kept in mind.

Firstly the instrument is monophonic. That is, if two notes are touched simultaneously only the higher note will sound. Secondly, the fingers must be kept dry, as any moisture across the key will hold that note on when the finger is removed. If this does happen they the keyboard should be wiped with a clean rag. In stubborn cases a little methylated spirits on the rag will help.

Finally, it should be remembered that unlike a piano there is no "touch" to the instrument and hitting the key hard will not alter the sound. In this respect it is similar to a real organ and the player should get used to touching the keys smoothly and firmly with the flat part of the finger — not the extreme tip. ●

TOUCH TUNES

WALTZING MATILDA

VERSE:

EEEDDCDECABC
GCEGGGGGGG
CDEEEDDCDECABC
GCEGFEDDDC

CHORUS:

GGGGE
CCCBA
GGGAGGGFED
CDEEEDDCDECABC
GCEGFEDDDC

HYMM TO JOY (BEETHOVEN'S NINTH)

EFGGFEDCCDEEDD
EFGGFEDCCDEDCC
DECDEFECDEFEDCDG
EFGGFEDCCDEDCC

'FRERE JACQUES'

CDEC
CDEC
EFG
EFG
GAGFEC
GAGFEC
CGC
CGC

GOD SAVE THE QUEEN

CCDBCD
EEFEDC
DCBC
CDEF
GGGFE
FFFFED
EFEDCEFG
AFEDC

COLONEL BOGEY

CAAA#CAAF
CAAA#ACCA#
A#GGAA#CA
ABAGCABGDC

AMAZING GRACE

CFFAGFAGFDC
CFFAGFAGCC
ACCAGFAGFDC
CFFAGFAGF

ARROW ELECTRONICS LTD.

TRANSDUCERS

40kHz Ultrasonic transducers as used in many Mag articles, complete with suggested circuits, type No. RL 400PP £4.99 pair.

COSMOS

CD4000AE	.20	CD4040AE	£1.08	7404	.18	7485	£1.25
CD4001AE	.20	CD4042AE	.88	7405	.20	7486	.37
CD4002AE	.20	CD4043AE	£1.00	7408	.20	7490	.48
CD4006AE	£1.06	CD4044AE	.98	7409	.20	7491A	.72
CD4007AE	.20	CD4046AE	£1.45	7410	.15	7492	.60
CD4008AE	.98	CD4049AE	.58	7413	.34	7493	.50
CD4009AE	.58	CD4050AE	.54	7420	.18	7494	.80
CD4010AE	.58	CD4052AE	.98	7425	.28	7495	.75
CD4011AE	.20	CD4056AE	£1.38	7430	.18	7496	.82
CD4012AE	.20	CD4060AE	£1.38	7440	.21	74100	£1.16
CD4013AE	.58	CD4066AE	.98	7441	.80	74107	.36
CD4014AE	£1.08	CD4068BE	.25	7442	.70	74121	.36
CD4015AE	£1.08	CD4070BE	.25	7445	£1.00	74141	.78
CD4016AE	.58	CD4070BE	.24	7446	£1.10	74145	.75
CD4017AE	£1.08	CD4071BE	.24	7447	.85	74150	£1.25
CD4018AE	£1.08	CD4073BE	.24	7450	.18	74151	.75
CD4019AE	.58	CD4077BE	.29	7451	.18	74153	.75
CD4020AE	£1.18	CD4081BE	.25	7453	.18	74154	£1.30
CD4021AE	£1.08	CD4082BE	.25	7454	.18	74155	.98
CD4022AE	.98	CD4085BE	.75	7460	.18	74156	.98
CD4023AE	.20	CD4086BE	.75	7470	.32	74174	£1.20
CD4024AE	.80	CD4093BE	.85	7472	.30	74180	£1.20
CD4025AE	.20	CD4099BE	£1.85	7473	.38	74181	£2.58
CD4026AE	£1.80	CD4511BE	£1.85	7474	.38	74190	£1.32
CD4027AE	.58	CD4528BE	£1.28	7475	.45	74191	£1.32
CD4028AE	.98	7400	.15	7476	.38	74192	£1.25
CD4029AE	£1.16	7401	.15	7480	.52	74193	£1.25
CD4030AE	.58	7402	.15	7482	.82	74196	£1.55
CD4035AE	£1.18	7403	.18	7483	.88	74197	£1.50

SOLDERING EQUIPMENT AND TOOLS

DST.1 Solder Sucker	£4.86	BIT.2.	50p
DST.2. Spare Nozzle	50p	BIT.3	50p
ST.3. Iron Stand	£1.53	BIT.4	50p
X.25-240 Iron	£3.47	BIT.1100	50p
CCN.15w Iron	£3.74	BIT.50	54p
		BIT.51	54p
		BIT.52	54p

3 WATT ZENERS

Axial lead miniature plastic case, full 3 watt disc. Following voltages only 6.8, 8.2, 10, 11, 12, 15, 16, 18, 22, 24, 27, 32, 33, 62, 68, 91, 100

ALL ONE PRICE: 45p

MM5314 Clock Chip

With hold/advance, count, output strobe, 7 seg. output. With data

IC TEST CLIP. Clips on to 14/16 pin ICs under test. Can be used as removal tool

IC SOCKETS

8 pin	14p
14 pin	15p
16 pin	17p

TIMER CHIP NE555

55p each

NE556 Dual

£1.08 each

Data Sheets

10p

3.2m RED Leds (TIL 209 size)

15p each

5mm GREEN Leds

98

741. OP-AMP

8 pin dip 35p each

301. OP-AMP

8 pin dip 45p each

3900 14 pin dil

85p each

MC3360 (MFC4000B)

£1.10

MC.3340 (MFC6040)

£1.80

ZN 414 Radio IC

with data £1.40

TDA 2020. The 15w RMS IC Arrow Price £3.36. With data sheets

RESISTORS. Metal Oxide resistors ultra low noise, 1/2 watt E24 series in the range between 10 ohms and 1 Meg

Carbon Film. High stability low noise. E12 series 1/4 watt and 1/2 watt

2p each

SENSATIONAL STOCK CLEARANCE

PAK AA1	Twenty five assorted transistors, our choice	£1.00
PAK AA2	Ten TAA243 Op Amps (702)	£1.00
PAK AA3	Ten BCW 54 NPN Transistors	£1.00
PAK AA4	Three 2N3055	£1.00
PAK AA6	Five BD187 (pre-formed) transistors	£1.00

GREAT TRIAC OFFER

Stud mounting

SC35A	55p	SC45B	80p
SC35B	55p	SC45E	£1.00
SC40B	70p	SC50D	£1.00
SC40D	85p		Press Fit
SC40E	90p	SC41B	65p
SC45A	75p	SC41D	80p

4-TRACK TAPE HEADS

record/pd £3.00

TRANSFORMER OFFER

Small Sized. 1 1/4 x 1 1/2 x 1 1/2 Mains Transformers. 4 1/2V-7V-9V. Out 70p each 6V-12V. Out 70p each

SEMICONDUCTORS AND IC's

Our huge availability of transistors, diodes, Triac's, SCR's, Zeners, etc., is far too large to list in this advertisement. See our new catalogue, price 40p, or telephone Alan Green on 0277-219435 for price and availability. Please ask for EX 07.

TRADE ORDERS WELCOME. Phone 0277-219435 EX 09, for all trade enquiries.

FULL SPEC. COMPONENTS. We supply only good quality components from leading manufacturers. NOT rejects or seconds.

All prices include VAT. Postage and packing 25p. Free on orders over £5.

OUR NEW RETAIL SHOP is now open, bigger and better than ever and with many new lines. We are only 5 minutes from Brentwood station. COME AND SEE US. Shop open 9.30-5.00 (Thursday early closing).

7 COPTFOLD ROAD,
BRENTWOOD, ESSEX

Dept ET12

THE ARROW CAT
IS BACK
Our new CATALOGUE is
now available send 40p



ALL PRICES INCLUDE VAT. POSTAGE: 25p; over £5 free



DOLBY™ 'B' NOISE REDUCTION KIT

Trademark of Dolby Laboratories Inc

Build your own Dolby system using this exclusive approved kit.

Featuring:

- switching for both encoding (low-level h.f. compression) and decoding
- a switchable f.m. stereo multiplex and bias filter
- provision for decoding Dolby f.m. radio transmissions.
- no equipment needed for alignment.
- suitability for both open-reel and cassette tape machines.
- check tape switch for encoded monitoring in three-head machines.

The kit includes:

- complete set of components for stereo processor.
- regulated power supply components.
- board-mounted DIN sockets and push-button switches.
- fibreglass board designed for minimum wiring.
- solid mahogany cabinet, chassis, twin meters, front panel, knobs, mounting screws and nuts.

Dolby level cal. tapes are available for open-reel use and for cassette (specify which) Price £2.00+VAT*

Please add VAT at 12 1/2% unless marked thus*, when 8% applies
We guarantee full after-sales technical and servicing facilities on all our kits

High performance Tuner-Amp and Tuners available

Typical performance
Noise reduction: better than 9dB weighted.
Clipping level: 16.5dB above Dolby level (measured at 1% third harmonic content).
Harmonic distortion 0.1% at Dolby level typically 0.05% over most of band, rising to a maximum of 0.12%.
Signal-to-noise ratio: 75dB (20Hz to 20kHz, signal at Dolby level) at Monitor output.
Dynamic Range > 90dB.
30mV sensitivity.

PRICE: £37.90 + VAT



INTEGREX LTD.

Please send SAE for complete lists and specifications
Portwood Industrial Estate, Church Gresley
Burton-on-Trent, Staffs. DE11 9PT
Burton-on-Trent (0283) 215432. Telex 377106

Sparkrite mk2

Capacitive discharge
electronic ignition kits

VOTED BEST
OF 8 SYSTEMS
TESTED BY
'POPULAR
MOTORING'
MAGAZINE



- * Smoother running
- * Instant all-weather starting
- * Continual peak performance
- * Longer coil/battery/plug life
- * Improved acceleration/top speeds
- * Up to 20% better fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

OPTIONAL EXTRAS

Electronic/conventional ignition switch. Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes: switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

CALLERS WELCOME. For Crypton tuning and fitting service - 'phone (0922) 33008.

PRICES INCLUDE VAT, POST AND PACKING.

Improve performance & economy NOW

POST TODAY!

Quick installation
No engine modification
required

Electronics Design Associates, Dept. ET12
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name

Address

Mk. 2 DIY Ass. Kit @ £11.80	QUANTITY REQD.	I enclose cheque/PO's for £ Cheque No. Send SAE if brochure only required.
Mk. 2 Ready Built Negative Earth @ £14.97		
Mk. 2 Ready Built Positive Earth @ £14.97		
Ignition Changeover switches @ £4.30		
R.P.M. Limit systems in above units @ £2.42		

ambit international

Coils, ICs for RF&AF, Tuners, Modules for AM FM & TV.

complete tuner kits

Larsholt Signalmaster Mark 8....the most stylish FM tuner kit that is available today. Suitable for even the relatively inexperienced in electronics construction, with clear and concise point-to-point details. Performance matches the excellent looks. £86.95

International Mark 2....A flexible system, with cabinet, chassis and panel designed to accommodate a variety of tuner electronics. The standard system is built around the Larsholt 7253 tuner set, includes two meters 6 preset stations, manual tune, balanced LED tuning, PSU etc. £65.00
The above tuners are supplied with prealigned RF and IF stages.

AM/FM....a new low cost MW/LW and FM stereo tuner, with muting, mechanical drive, teak effect cabinet. £41.95

TV sound....the 7700 TV sound module in a chassis and cabinet that matches the AM/FM tuner. £36.95

Please remember to include an extra £3 carriage on complete tuner kits.

Radio ICs	Misc. regs etc.	Transistors
CA3089E FM IF 1.94†	7R05UC 5v 1A 1.55*	ZTX107 0.14
CA3090AQ mpx 3.75†	78M12 12v ½A 1.20*	ZTX108 0.14
MC1310P mpx 2.20†	TDA1412 .. 0.95*	ZTX109 0.14
SN76660N FM IF 0.75	7815UC 15v 1A 1.55*	ZTX212 0.16
TBA120AS FM IF 1.00	78M20 20v ½A 1.20*	ZTX213 0.16
MC1350 AM/FM IF 0.70	78M24 24v ½A 1.20*	ZTX214 0.16
HA1197 AM system 1.40	uA723 5-35v 0.80*	ZTX413 0.18
TBA651 AM system 1.81	NE550A do. 0.80*	ZTX551 0.18
uA720 AM system 1.40	TAA550B 32v. 0.50*	ZTX451 0.18
	uA741 op amp 0.40*	BF224 0.22
	LM3900 quad amp 0.68*	BD165 0.50
	MC3401 do. 0.68*	BD166 0.54
	8038 wave gen. 3.10*	BD535 0.52
	NE555 timer 0.70*	BD536 0.53
	NE560B PLL 2.50	BD609 0.70
	NE561B PLL 3.50	BD610 1.20
	NE562B PLL 2.50	40673 0.50
	NE565A PLL 2.50	MEM680 0.75
	NE566V VCO 2.55*	BF256L 0.38
	NE567V tone trigger 2.50*	

Tunerheads for VHF FM and UHF TV (All varicap types)

EF5800	6 circuit high quality 88-108MHz tunerhead	14.00
EF5600	5 circuit high quality 88-108MHz tunerhead	12.50
EC3302	3 circuit (same spec to LP1186) VHF tunerhead	5.50
5700	UHF TV tunerhead 38MHz IF with 4 way preset	8.00

Modules for IF, decoders etc. (Also available built & tested)

7020 kit	10.7MHz FM IF with mute, AFC, AGC, meter ops	5.25
7030 kit	10.7MHz linear phase low distortion FM IF	7.67
92310 kit	Stereo decoder with full pilot tone filtering (PLL)	5.35
93090 kit	Stereo decoder, low noise and distortion	6.40
7252	FM tuner set, built - 1uV in, Audio out with mute and all HiFi tuner features. Varicap tuned.(mono)	24.00
7253	FM tuner set, built 1.2uV in, stereo out, with mute and all Hi Fi tuner features. Varicap tuned.	24.00
71197 kit	Varicap tuned MW radio module. The best AM tuner, with 75dB AGC, 0.3% THD.	9.65
8001 kit	55kHz low pass, birdy. filter for stereo radio	1.75
2020 kit	TDA2020 stereo amplifier, with special heatsinks	9.35

Famous TOKO COILS, Mechanical filters, ceramic filters, chokes etc.

455/470kHz IF coils	0.30	M41T 4kHz/455kHz Mech filt.	1.65
(1st, 2nd & 3rd)IFs	0.70	M71T 7kHz/455kHz Mech filter	1.65
10.7MHz 1FTs	0.32	C455B 8kHz/455kHz ceramic filt	0.55
Variable signal chokes:		C455C 6kHz/455kHz ceramic filt	0.55
2mH, 23mH, 36mH, 7mH		C050D 6kHz/470kHz ceramic filt	0.60
11.75mH	0.33	CFS107 10.7MHz cer. FM filter	0.50
Fixed chokes: (uH)		SFE6.0 6MHz TV sound IF filter	0.30
1.0, 4.7, 10, 33, 47, 100.		3132A linear phase FM IF filter	2.25
22, 33, 470, 1000	0.16	SFD470B 470kHz ceramic filter	0.75

PLEASE REMEMBER TO INCLUDE VAT - thankyou !!

If you have read this far, you probably appreciate that AMBIT tends to specialize in the areas of wireless and TV that most component sources do not include. Our catalogue and price list continue this theme with coils, linear ICs etc. Catalogue 40p, price list free with SAE. Post is 22p per order - unless otherwise stated.

**37a HIGH STREET,
BRENTWOOD ESSEX
telephone 0277 216029**



ETI DATA SHEET

ABOUT THE ONLY feature common to the ranges of displays described in this Data Sheet is the way in which the various manufacturers identify the segments.

The standard method for doing this is shown below. We have deliberately excluded the 'overflow' type of L.E.D. display, in order to provide a better selection of normal types in the space available to us.

Calculated omission

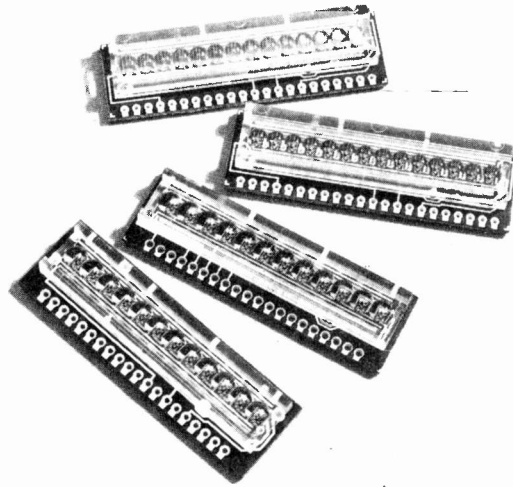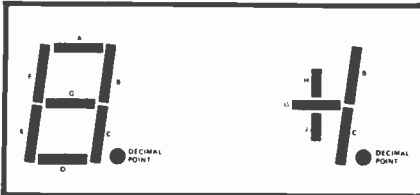There is another type of L.E.D. display now becoming more popular in general usage. This is the calculator display, of a type personified by the H/P device shown here. We hope to deal with these more fully at a later date. Generally these



types use very low power, being readable at about 100µA and with a varying number of digits, usually eight or ten.

Inclusion

Now that we've told you what isn't in here, perhaps we should explain what we have covered. Each display is described in a standard

manner, using the same form of presentation for the relevant technical data. This is to facilitate easy comparison and subsequent selection.


Prices vary enormously from supplier to supplier, so we have not tried to give a definite price, just an indication. Don't be mis-LED, some market segments might well display lower prices!

FND 500/507

FAIRCHILD

The FND 500 is a common cathode display with an integral red filter. The decimal point is on the right-hand side of the device, which measures 15.3mm by 16.5mm high. This device is a pin for pin replacement to the Texas Instrument TIL322 display.

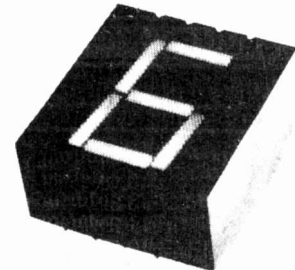
The FND 507 is a common anode version of the FND 500, and as such can be used to replace a TIL 321.



ELECTRICAL CHARACTERISTICS

DIGIT SIZE	0.5ins
COLOUR	red
AVERAGE FWD CURRENT/SEGMENT	25mA
FORWARD VOLTAGE	1.7V
MIN. REV. BREAKDOWN VOLTAGE	3.0V
MAX. REV. CURRENT	100µA
LIGHT INTENSITY PER SEGMENT	600ucd
MAX. POWER DISSIPATION	400mW

TYPICAL PRICE £1.10

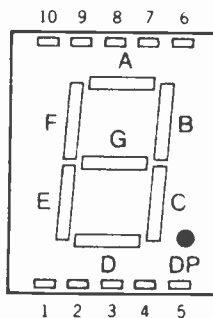

PIN OUT - FND 500/507

1 Segment E	6 Segment B
2 Segment D	7 Segment A
3 Common	8 Common
4 Segment C	9 Segment F
5 Dec. point	10 Segment G

FND 500-----common cathode
FND 507-----common anode

LED DISPLAYS

TYPICAL PRICE £1.00

ELECTRICAL CHARACTERISTICS

DIGIT SIZE	0.3ins
COLOUR	YELLOW/RED/ORANGE
AVERAGE FWD CURRENT/SEGMENT	25mA
FORWARD VOLTAGE	2.5/1.6/1.6V
MIN. REV. BREAKDOWN VOLTAGE	3.0V
MAX. REV. CURRENT	100uA
LIGHT INTENSITY PER SEGMENT	320ucd
MAX. POWER DISSAPATION	500mW

A very common and widely available display, the 707 is the common anode version, with the 707R having a right-hand decimal point, as opposed to the standard left decimal on the 704 and 707. The 704 is thus a common cathode device.

PIN OUT- DL707/707R

1 Segment A	8 Segment D
2 Segment F	9 Anode
3 Anode	10 Segment C
4 NC	11 Segment G
5 NC	12 NC
6 Dec. point	13 Segment B
7 Segment E	14 Anode

PIN OUT-DL 704

1 Segment F	8 Segment C
2 Segment G	9 Dec. point
3 NC	10 NC
4 Cathode	11 NC
5 NC	12 Cathode
6 Segment E	13 Segment B
7 Segment D	14 Segment A

ELECTRICAL CHARACTERISTICS

DIGIT SIZE	0.6ins
COLOUR	RED
AVERAGE FWD CURRENT/SEGMENT	25mA
FORWARD VOLTAGE	2.4V
MIN. REV. BREAKDOWN VOLTAGE	6.0V
MAX. REV. CURRENT	100uA
LIGHT INTENSITY PER SEGMENT	600ucd
MAX. POWER DISSAPATION	960mW

A 'Jumbo version' of the 707 and 704 devices. Widely available. Identify the common anode 747 by the missing pins — 1, 9, 10 and 18.

The 750 is in full possession of its pins, and is common cathode. Decimal point is right-handed.

PIN OUTS- DL747/750

1 NC	10 NC
2 Segment A	11 Segment D
3 Segment F	12 Common
4 Common	13 Segment C
5 Segment E	14 Segment G
6 Common	15 Segment B
7 Dec. point	16 NC
8 NC	17 Common
9 NC	18 NC

DL747-----common anode
DL750-----common cathode
Pins 1,9,10,18, ommitted from747

TYPICAL PRICE £1.40


PIN OUTS -

TIL321/323/325

As FND 507. Direct replacement.

PIN OUTS- TIL322/324/326

As FND 500. Direct replacement.

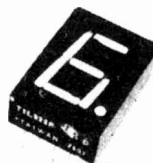

A uniform range of large displays, with red, green or amber encapsulation. No filters are needed, and a wide viewing angle is possible. Within defined categorys, the devices are matched for luminous intensity. These can also act as direct replacements for the Fairchild FND500/507 duet.

TYPICAL PRICE £1.30

ELECTRICAL CHARACTERISTICS 321/322	
DIGIT SIZE	0.5ins
COLOUR	RED
AVERAGE FWD CURRENT/SEGMENT	20mA
FORWARD VOLTAGE	1.7V
MIN. REV. BREAKDOWN VOLTAGE	3V
MAX. REV. CURRENT	100uA
LIGHT INTENSITY PER SEGMENT	600ucd
MAX. POWER DISSIPATION	300mW

ELECTRICAL CHARACTERISTICS 323/324	
DIGIT SIZE	0.5ins
COLOUR	GREEN
AVERAGE FWD CURRENT/SEGMENT	20mA
FORWARD VOLTAGE	2.5V
MIN. REV. BREAKDOWN VOLTAGE	3V
MAX. REV. CURRENT	100uA
LIGHT INTENSITY PER SEGMENT	320ucd
MAX. POWER DISSIPATION	600mW

ELECTRICAL CHARACTERISTICS 325/26	
DIGIT SIZE	0.5ins
COLOUR	AMBER
AVERAGE FWD CURRENT/SEGMENT	20mA
FORWARD VOLTAGE	2.5V
MIN. REV. BREAKDOWN VOLTAGE	3V
MAX. REV. CURRENT	100uA
LIGHT INTENSITY PER SEGMENT	340ucd
MAX. POWER DISSIPATION	400mW

XAN 352/4

XCITON

ELECTRICAL CHARACTERISTICS	
DIGIT SIZE	0.3ins
COLOUR	GREEN
AVERAGE FWD CURRENT/SEGMENT	25mA
FORWARD VOLTAGE	2.0V
MIN. REV. BREAKDOWN VOLTAGE	5V
MAX. REV. CURRENT	100uA
LIGHT INTENSITY PER SEGMENT	450ucd
MAX. POWER DISSIPATION	400mW

PIN OUT—XAN 352	
1 Segment A	8 Segment D
2 Segment F	9 NC
3 Anode	10 Segment C
4 Omitted	11 Segment G
5 Omitted	12 Omitted
6 Dec. point	13 Segment B
7 Segment E	14 Anode

PIN OUT—XAN 354	
1 Segment F	8 Segment C
2 Segment G	9 Dec point
3 Omitted	10 Omitted
4 Cathode	11 Omitted
5 Omitted	12 Cathode
6 Segment E	13 Segment B
7 Segment D	14 Segment A

These two come from what is the largest range of displays available. Xciton make big play of having all devices brighter than the competition, and a list of equivalents from their range for most of the others. These two are common cathode (XAN 354) and common anode (352) 0.3" numerics, using high efficiency GaAsP.

TYPICAL PRICE £1.20

XAN 650 SERIES

XCITON

ELECTRICAL CHARACTERISTICS 82/84	
DIGIT SIZE	0.6ins
COLOUR	YELLOW
AVERAGE FWD CURRENT/SEGMENT	25mA
FORWARD VOLTAGE	2.2V
MIN. REV. BREAKDOWN VOLTAGE	3.0V
MAX. REV. CURRENT	100uA
LIGHT INTENSITY PER SEGMENT	700ucd
MAX. POWER DISSIPATION	400mW



TYPICAL PRICE £1.75

PIN OUT XAN 652/654/682/684	
1 Segment A	8 Segment D
2 Segment F	9 Common
3 Common	10 Segment C
4 Segment E	11 Segment G
5 Omitted	12 Segment B
6 Dec. point	13 Omitted
7 Omitted	14 Common


XAN 684/654---common cathode
XAN 682/652---common anode

ELECTRICAL CHARACTERISTICS 52/54	
DIGIT SIZE	0.6ins
COLOUR	GREEN
AVERAGE FWD CURRENT/SEGMENT	25mA
FORWARD VOLTAGE	2.0V
MIN. REV. BREAKDOWN VOLTAGE	3V
MAX. REV. CURRENT	100uA
LIGHT INTENSITY PER SEGMENT	2000ucd
MAX. POWER DISSIPATION	350mW

ELECTRICAL CHARACTERISTICS

DIGIT SIZE	(magnifier) 0.11ins
COLOUR	RED
AVERAGE FWD CURRENT/SEGMENT	5mA
FORWARD VOLTAGE	1.6V
MIN. REV. BREAKDOWN VOLTAGE	5V
MAX. REV. CURRENT	100uA
LIGHT INTENSITY PER SEGMENT	20ucd
MAX. POWER DISSIPATION digit	80mW

Digits per Cluster	Center Decimal Point	Right Decimal Point
3 (right)	5082-7402	5082-7412
3 (left)	5082-7403	5082-7413
4	5082-7404	5082-7414
5	5082-7405	5082-7415

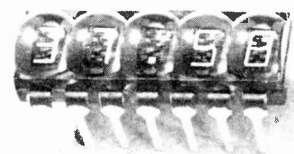

PIN OUT HP7402/7412

1 NC	8 Segment D
2 Segment E	9 Segment F
3 Segment C	10 Cathode
4 Cathode	11 Segment B
5 Dec. point	12 Segment A
6 Cathode	13 Omitted
7 Segment G	14 Omitted

PIN OUT HP7404/7414

1 Cathode	8 Segment D
2 Segment E	9 Segment F
3 Segment C	10 Cathode
4 Cathode	11 Segment B
5 Dec. point	12 Segment A
6 Cathode	13 Omitted
7 Segment G	14 Omitted

PIN OUT HP 7403/7413

1 Cathode	8 Segment D
2 Segment E	9 Segment F
3 Segment C	10 Cathode
4 Cathode	11 Segment B
5 Dec. point	12 Segment A
6 NC	13 Omitted
7 Segment G	14 Omitted

PIN OUT HP7405/7415

1 Cathode	8 Segment 9
2 Segment E	9 Cathode
3 Segment C	10 Segment F
4 Cathode	11 NC
5 Dec. point	12 Segment B
6 Segment D	13 Cathode
7 Cathode	14 Segment A

The 7400 series are 2.79mm GaSP numeric indicators, packaged in end stackable DIL casings. They are readable at 500µA per segment, and constructed for strobed operation in such a way that less lead connections are needed.

A lens magnifier is fitted, with a good viewing angle.

ELECTRICAL CHARACTERISTICS

DIGIT SIZE	0.43ins
COLOUR	RED
AVERAGE FWD CURRENT/SEGMENT	20mA
FORWARD VOLTAGE	1.6V
MIN. REV. BREAKDOWN VOLTAGE	6V
MAX. REV. CURRENT	10uA
LIGHT INTENSITY PER SEGMENT	400ucd
MAX. POWER DISSIPATION	300mW

PIN OUT HP7750


1 Segment A	8 Segment D
2 Segment F	9 NC
3 Anode	10 Segment C
4 Omitted	11 Segment G
5 Omitted	12 Omitted
6 Dec. point	13 Segment B
7 Segment E	14 Anode

PIN OUT HP7751

1 Segment A	8 Segment D
2 Segment F	9 Dec. point
3 Anode	10 Segment C
4 Omitted	11 Segment G
5 Omitted	12 Omitted
6 NC	13 Segment B
7 Segment E	14 Anode

PIN OUT HP7760

1 Segment A	8 Segment D
2 Segment F	9 Dec. point
3 Cathode	10 Segment C
4 Omitted	11 Segment G
5 Omitted	12 Omitted
6 NC	13 Segment B
7 Segment E	14 Cathode

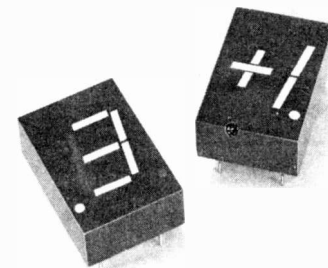

A fairly standard range of slightly larger than standard displays. The material is GaSP, and the devices use a standard 14 pin DIL package so that they can be plugged into standard sockets.

CARBON RESISTORS

PART 5

Don't take them for granted . . . there's a lot more to them than you ever realised . . .

CARBON COMPOSITION RESISTORS have been used extensively in the manufacture of radio and television sets since the valve era but are being rapidly replaced in production by film resistors. These have superior characteristics and are becoming increasingly cost competitive.

Carbon resistors are manufactured in wattage ratings ranging from 0.1 watt to 2 watts and resistance values ranging from 10 ohms to 100 M. They are made to tolerances of $\pm 5\%$ (E24 series, $\pm 10\%$ (E12 series) and $\pm 20\%$ (E6 series), although the latter is the more usual and least expensive.

There are three basic types of carbon composition resistor:

- (a) uninsulated
- (b) insulated
- (c) filament or filament-coated


Uninsulated type: In this type, the resistive element consists of fine carbon

particles mixed with a refractory filling, which is non-conducting, bonded together by a resin binder. The proportion of carbon particles to filler determines the resistance value. The mixture is compressed into shape, usually cylindrical, and fired in a kiln. The end connections are made by any one of a variety of methods. These are illustrated in Fig. 1. In the first method, Fig. 1(a), the ends of the composition rod are sprayed with metal, and wire leads soldered on to provide radial connections. The resistor is then painted and colour coded. This method was extensively used with 1W and 2 W resistors. A second method, much more widely used now, involves enlarging the ends of the connecting leads and moulding them directly into the carbon composition rod — Fig. 1(b). This method is used extensively as it is adaptable to all wattage ratings and sizes of the resistor body. A third method is

also employed. Pressed metal caps, usually having integral leads, are forced onto the ends of the carbon rod — Fig. 1(c). These caps have radial leads and are particularly suited to printed circuit board mounting as they may be plugged straight into mounting holes on the board without the necessity of preforming the leads as is required with axial lead components. These are also known as 'pluggable' types. Film resistors are also made in this style.

Uninsulated carbon composition resistors are generally smaller than the insulated types for a given wattage as their open construction permits good heat dissipation. There is the danger however, that short circuits may occur to adjacent components, and for this reason, the insulated type is preferred.

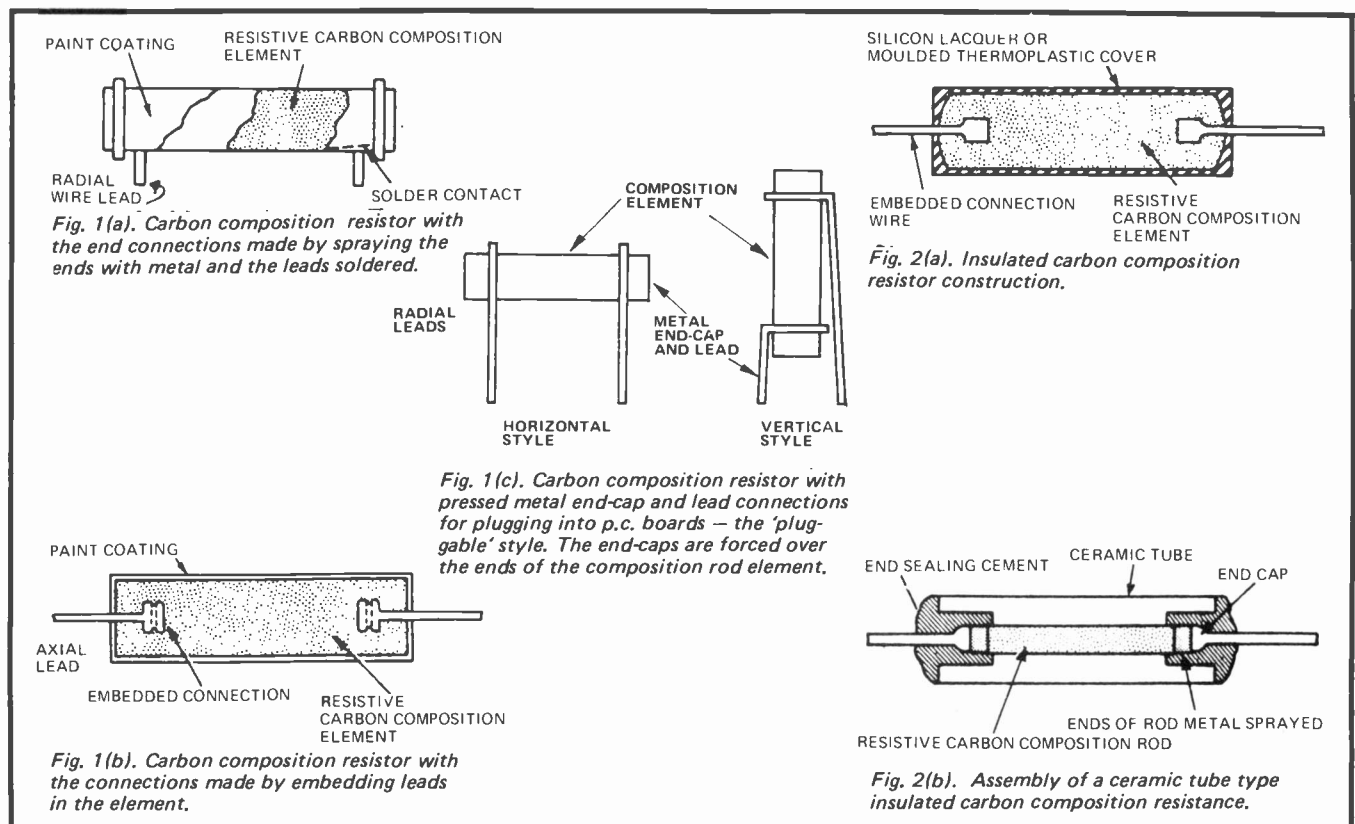Insulated Type: This type has the composition element made in the same manner as just described, but it is then



encapsulated in either a silicon lacquer, a thermoplastic moulding or epoxied into a ceramic tube. The first two generally employ a resistance element having embedded connections, as illustrated in Fig. 2(a). The type having the element sealed in a ceramic tube generally have an element constructed as shown in Fig. 2(b). The ends of the element are sprayed with metal and an end-cap having an integral lead is force-fitted over them. This assembly is then put inside the ceramic tube and the ends sealed with an epoxy or other compound.

Filament or Filament-coated Type: With this type, carbon granules are dispersed, along with a filler, in a varnish which is then applied to the surface of a continuous glass or ceramic filament which is then baked. The resistance value depends on the length and mixture, the filament is cut into appropriate lengths and leads applied by one of the methods detailed above. It is usually encapsulated in an insulating compound as per the insulated style of resistor.

Carbon composition resistors have a large voltage coefficient. The value of this coefficient varies with the resistance of the component (being highest for high value resistors) and the size of the resistance element. Small resistors of a given value have less insulating filler in their composition and will have a lower voltage coefficient. Commonly available composition resistors have quoted voltage coefficient between 0.02 and 0.035 for values up to 1M. Values above this have a coefficient of typically 0.05. These values may cause a maximum change in resistance of 2% when used within their ratings. The voltage coefficient of the other types of resistors is considerably smaller than for composition types — typically 0.002% or less.

A large negative temperature coefficient is one of the disadvantages of composition resistors. It is typically between 0.1% and 0.15% per °C (i.e. 1000 ppm per °C or greater), across the whole resistance range. This means that a 1 M resistor will change its value by 1 k or more for each °C change in temperature. The curve of percentage resistance change versus temperature is not linear and may be positive over one portion of the temperature range and negative over another. Figures 3 and 4 show typical temperature coefficient curves for two types of carbon composition resistor for different values between 1 k and 10 W.

Critical Resistance Value: A resistor of specified power and voltage ratings has a critical resistance value above which the allowable voltage limits the permissible power dissipation. Below this value, the maximum permitted voltage across the

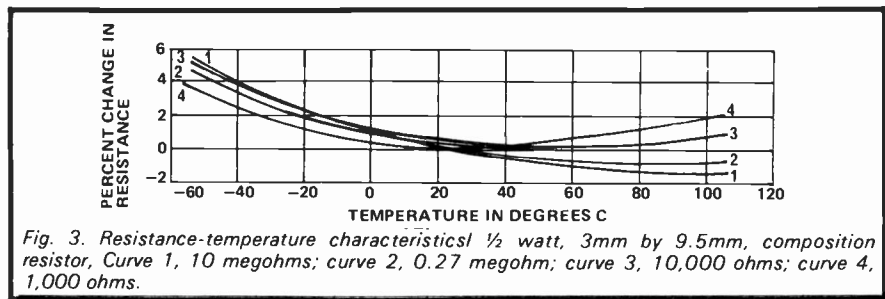


Fig. 3. Resistance-temperature characteristic 1/2 watt, 3mm by 9.5mm, composition resistor, Curve 1, 10 megohms; curve 2, 0.27 megohm; curve 3, 10,000 ohms; curve 4, 1,000 ohms.

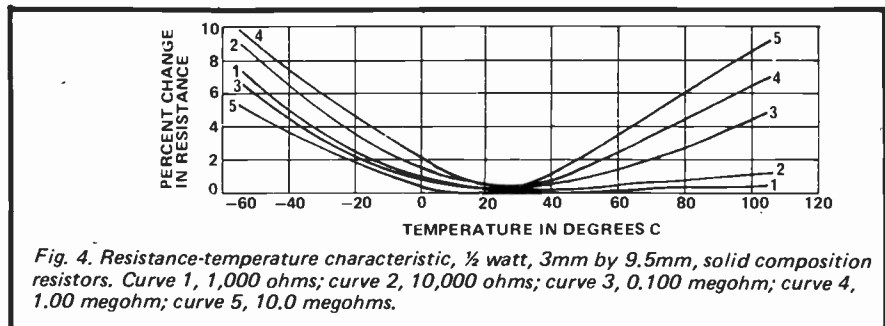


Fig. 4. Resistance-temperature characteristic, 1/2 watt, 3mm by 9.5mm, solid composition resistors. Curve 1, 1,000 ohms; curve 2, 10,000 ohms; curve 3, 0.100 megohm; curve 4, 1.00 megohm; curve 5, 10.0 megohms.

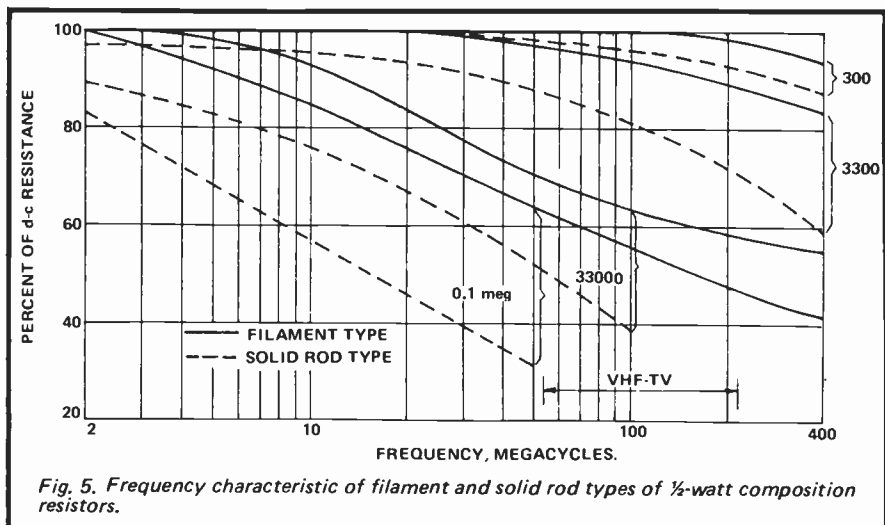


Fig. 5. Frequency characteristic of filament and solid rod types of 1/2-watt composition resistors.

resistor is never reached at the rated power.

Carbon composition resistors show a pronounced fall-off in apparent AC resistance, compared to their DC value, with increasing frequency. The effect which is particularly bad with the higher values is known as the 'Boella' effect after its Italian discoverer. The filament-coated type is less affected than the solid rod type. Figure 5 illustrates the frequency characteristics of the two basic construction styles of composition resistor for a variety of values. The values below 200 ohms are obviously quite useful right up to UHF. Values below 100 ohms may show an increase in value with increasing frequency. Obviously at frequencies in the VHF range and above, mounting and lead length affect characteristics considerably. Absolute minimum lead length is necessary to minimise unwanted inductance. Lead lengths of 6 mm have considerable inductance at 200 MHz. Printed circuit layout can assist in minimising the problem, and mounting

the resistor flat on the board — bending the leads as close as possible to the component body — is good. Naturally, this applies to all resistors. Radial lead components are best in this situation.

The amount of noise generated by carbon composition resistors is a function of the materials used in the composition mix. Generally, the noise generated increases with increasing voltage, increasing resistance, and decreasing size, for a given mix of materials. The noise due to current flowing through the resistor is generated by random changes in the material of the element, caused by the current flow. This noise decreases with increasing frequency and Johnson noise, which is frequency independent, becomes dominant above about 1 kHz. The current noise generated by composition resistors is a major limitation against using them at dc and low frequencies. They are not recommended for use in amplifier input stages or DC amplifiers for this reason. Microphony is also



A gold plated, LED display 5 function watch at the VERY special price of £16.97 inclusive of VAT, postage and packing (normal price £23.75).

As well as hours/minutes (with AM/PM indicator), day/date and seconds, you also get a guarantee which in this case is no small addition!

- Two years cover — repairer replacement on any watch developing a fault within two years of purchase.
- Free calibration check at the end of each of the first 3 years.

----- CUT -----

WATCH OFFER
ETI MAGAZINE
25-27 OXFORD STREET, LONDON W1R 2NT

I enclose cheque/P.O. for £16.97 (payable to ETI) for a Digital Watch.

NAME.....

ADDRESS.....


.....

.....

Those not wishing to cut their magazine may order on their own notepaper.

ETI CLOCK: £13.95

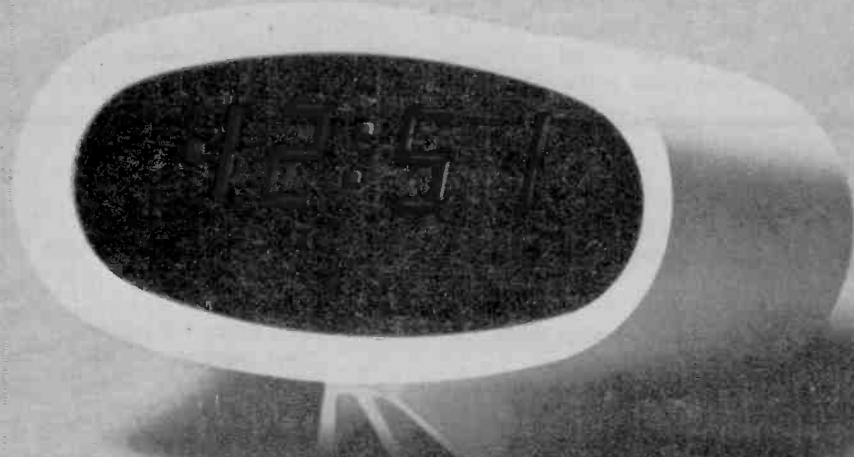THE LONG-RUNNING OFFER ON A DIGITAL ALARM CLOCK HAS BEEN ONE OF OUR MOST SUCCESSFUL EVER! OUR PRICE INCLUDES VAT AND POST & PACKING



Fullsize = 5in across and 3 1/2in deep.

"We have previously sold this Digital Clock under the name Pulsar. At the time that this name was chosen by us we were unaware that the name Pulsar had been previously registered, but it has been drawn to our attention that this is the case. We have been asked to point out that our Digital Clock is not associated with Pulsar Watches, Time Computer Inc. or Pulsar S.A."

Our clock shows the time 0.7in high on bright Planar Gas Discharge displays (there is a brightness control on the back). The dot on the left of the display shows AM/PM, and the flashing (1Hz) colon shows that the alarm and clock are working.

A bleeper alarm sounds until the clock is tipped forwards. Then the "snooze" facility can give you 5 minutes sleep before the alarm sounds again, and then another 5 minutes, etc, until you switch the alarm off. The clock also features a mains-failure indicator, and is 12hr — the alarm being 24 hour.

We have a large number of units in stock for this offer but please allow 28 days for delivery.

CLOCK OFFER
ETI MAGAZINE
25-27 OXFORD STREET,
LONDON W1R 2NT

I enclose cheque/P.O. for £13.95 (payable to ETI) for an Alarm Clock. Please write your name and address on the back of your cheque to speed processing of your order.

NAME.....

ADDRESS.....

.....

.....

Those not wishing to cut their magazine may order on their own notepaper.

AUDIO LIMITER

This simple but effective unit can be used as a limiter, automatic volume control or voltage controlled amplifier.

THE AUDIO COMPRESSOR EXPANDER project described in the May 1976 issue of ETI has proved to be very popular with readers and we have since had many requests for a simpler limiter circuit. Whilst limiters and compressors are similar in operation they are used in completely different ways.

A compressor is normally used in a linear compression mode. That is, for say every 10 dB of input signal level change the output is arranged to change by, for example, 6 dB. The output will change this fixed amount of 6 dB for every 10 dB increment of input. The reverse of this procedure is called expansion. That is, for a 6 dB change in input signal level the output is caused to change by 10 dB.

A compressor/expander is typically used for improving the dynamic range (and hence signal-to-noise ratio) of tape recorders. The signal is first compressed so that its dynamic range can be handled by the tape. On subsequent replay the signal is expanded by a corresponding amount to restore the original dynamic range. As the amount of noise on the tape is constant and the level of signal has been effectively increased, the signal-to-noise ratio has also been increased.

A limiter is a form of compressor which operates only when the signal exceeds a certain predetermined level. For example signals which do not exceed say 80% of the predetermined maximum are not compressed at all and are amplified with their full dynamic range. For signals above the 80% level the limiter begins to operate and very large input signals are required to obtain the extra 20% of output.

Another use of a limiter is in the continuous-limit mode such that it acts as an automatic volume control (AVC). In this mode a 60 dB change in input level can be limited to say, a 6 dB change in output level.

Finally the limiter may also be used as a voltage controlled ampli-

fier having a range of about 55 dB. A typical application of such a device would be a remote volume control. It should be noted, however, that although the transfer function of such a voltage-controlled amplifier is fairly sharp, two of them may not necessarily track perfectly due to differences in the FETs in the ICs. Thus on our prototype the difference between channels when used as a stereo volume control was up to 5 dB at some points with any given input.

DESIGN FEATURES

The first decision to be made when designing a limiter is what type of controlled resistive element to use. Common alternatives are FETs, LDRs, base-emitter junctions of transistors, thermistor or balanced modulator ICs. All of these have their respective advantages and disadvantages and all have been tried in our laboratory at one time or another. We selected FETs because we considered them the most cost effective.

When FETs are used in voltage controlled amplifiers it is essential that the voltage across them is kept as low as possible if the distortion is also to be kept low. This means that the FET must be used as an attenuator where the voltage across

the FET can be kept low irrespective of input voltage. The most suitable type of FET for this purpose is the enhancement-mode device but these are not readily available. The commonly available types require a negative voltage to turn them off. However, there is a suitable alternative, the 4049 CMOS IC which contains six inverting buffers. By suitable interconnection the IC may be made to provide six enhancement-mode FETs and this is the approach we decided to use.


To restore the signal level an amplifier is required and originally we intended to use the LM382 but, because of cost and availability considerations, we finally decided to use an LM301 or 741 operational amplifier together with a transistor pair at the front end. The noise performance of this arrangement was found to be as good as the LM382's and supply voltage to be less critical (although a dual supply is required). If only a single-ended supply is available then a 382 may be used, although a different board layout would be required.

CONSTRUCTION

Although a printed-circuit board is not essential it certainly makes construction very much easier. Before assembly decide whether a limiter or an AVC is required as the

Specification ETI 446

Input voltage range	1 mV – 10 V
Frequency response	± 3 dB 10 Hz – 20 kHz
Limiting point	
set by R2/16	3mV
Equivalent signal-to-noise ratio	70 dB re 1 V out
Distortion	see graph
Input impedance	47 k
Maximum gain	
R2/16 = 4k7	26 dB
R2/16 = 47k	40 dB
Maximum attenuation	
as voltage controlled amplifier	55 dB
Supply voltage	± 8 V to ± 16 V dc at 5 mA

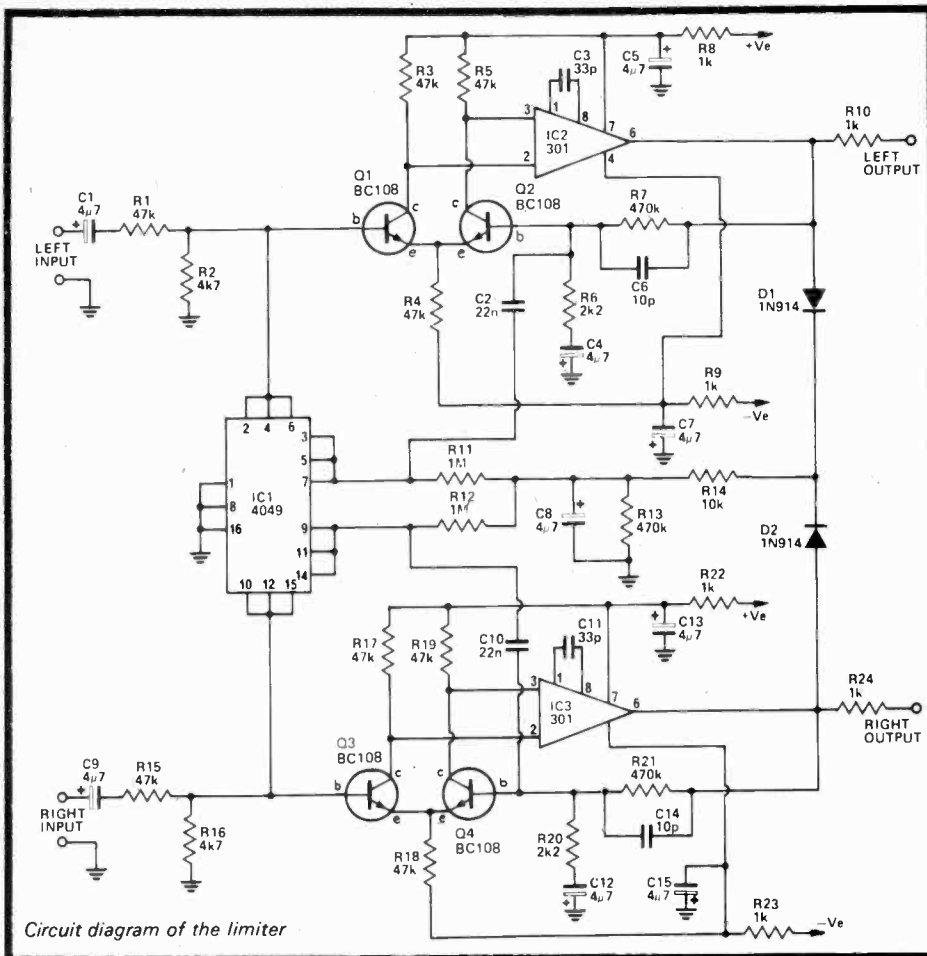

values of R2 and R16 will vary accordingly. Use 47k for R2 and R16 in the AVC mode and in limit mode, depending on limit point, between 470 and 4k7. The transistor type specified is available from a number of different manufacturers but pin connections are different. If a different brand is used the transistor should be reversed (emitter and collector interchanged). The overlay also shows the arrangement for using the LM301 ICs — these may be directly replaced by 741s simply by omitting the 33 pF capacitors.

Although the CMOS ICs 4449 and 4009 are electrically similar to the 4049 and are interchangeable with it when the devices are used as hex-inverters, they cannot be used as replacements in this circuit. The 4049 must be used. The 4449 and 4009 have different circuitry and will not work in this mode.

How it works

The circuit basically consists of a voltage-controlled attenuator followed by a low-noise amplifier with a gain of 46 dB. The output of this amplifier is rectified to generate a dc voltage which is used to control the attenuator.

The variable element in the attenuator is an enhancement mode FET. This is made from a CMOS hex-inverter IC, the 4049, by special interconnection. The difference between enhancement mode FETs and the normally available depletion-mode junction FETs is as follows: The enhancement mode FET has a high resistance between source and drain when the gate is at zero volts, but this decreases as the gate is taken more positive. A JFET (N type) is hard-on with the gate at zero volts and turns off as the voltage is taken negative.


The amplifier is required to have high open-loop gain and have fairly low noise. The gain requirement is provided by an LM301 operational amplifier and the low-noise requirement by a pair of transistors (connected as a differential pair) placed before the operational amplifier. The gain is set, by the combination of resistors R6 and R7, to 215 (or 46 dB). The lower 3 dB point is set at 15 Hz by C4 and R6 whilst the upper 3 dB point is set at 33 kHz by C6 and R7.

The outputs of both channels are summed and rectified by diodes D1 and D2 to charge C8 via R14. The voltage on C8 is coupled to the gate of the FETs (three in parallel on each channel) via R11 and R12.

As the input voltage increases the output also tends to increase and voltage on capacitor C8 also increases and this increase is applied back to the gates of the FETs. This reduces the resistance of the FETs and thus increases the attenuation, tending to prevent the output from changing as much as the input does.


With all FETs the resistance changes with applied voltage and this gives rise to distortion. However by modulating the gate voltage with a signal equivalent to the voltage across the FETs the distortion is greatly reduced (3.5% down to 0.8%).

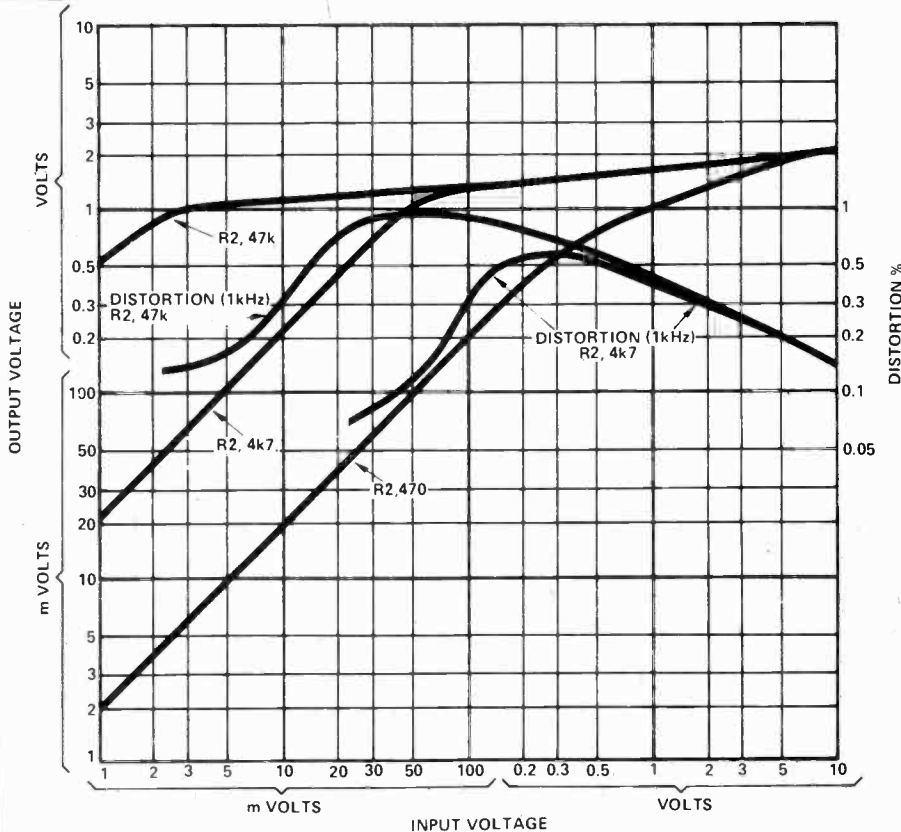The attack and release times can be adjusted by varying R14 for attack and R13 for release.



Input versus output voltage for various values of R2 (and R16)
Distortion at 1kHz for R2=4k7 and R2=47k are also shown.


AUDIO LIMITER

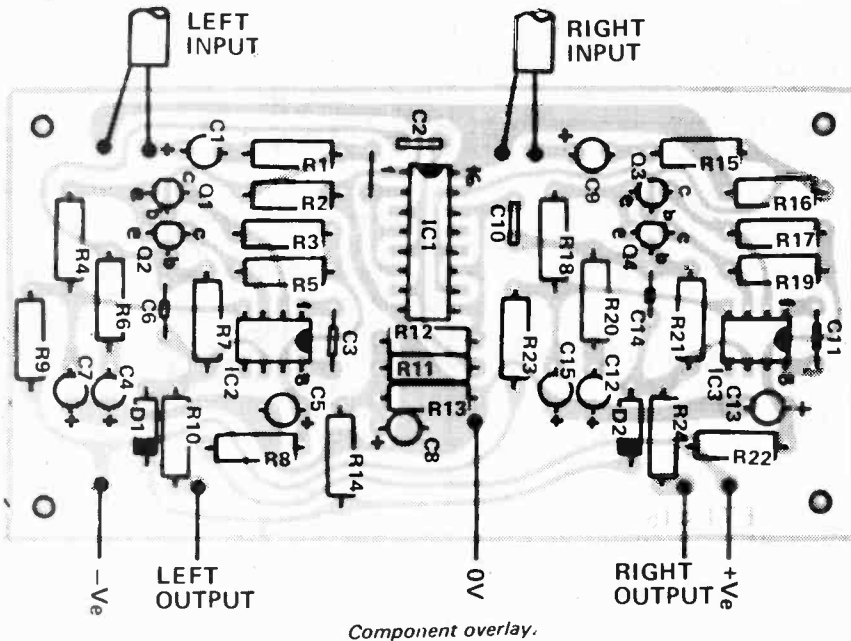

Parts List

Resistors				
R1	47k	½ W	5%	C4,5
R2	4k7	"	"	C6
R3-R5	47k	"	"	
R6	2k2	"	"	C7-C9
R7	470k	"	"	C10
R8-R10	1k	"	"	C11
R11,12	1M	"	"	C12,13
R13	470k	"	"	C14
R14	10k	"	"	C15
R15	47k	"	"	
R16	4k7	"	"	
R17-R19	47k	"	"	
R20	2k2	"	"	
R21	470k	"	"	
R22-R24	1k	"	"	
Capacitors				
C1	4µ7	25 V electrolytic		
C2	22n	polyester		
C3	33p	ceramic		
Semiconductors				
Q1-Q4 Transistors BC108				
D1,2 Diode 1N914				
IC1 Integrated circuit 4049 *				
IC2,3 " " LM301				
Miscellaneous				
PC board ETI 446				
9 PC board pins				

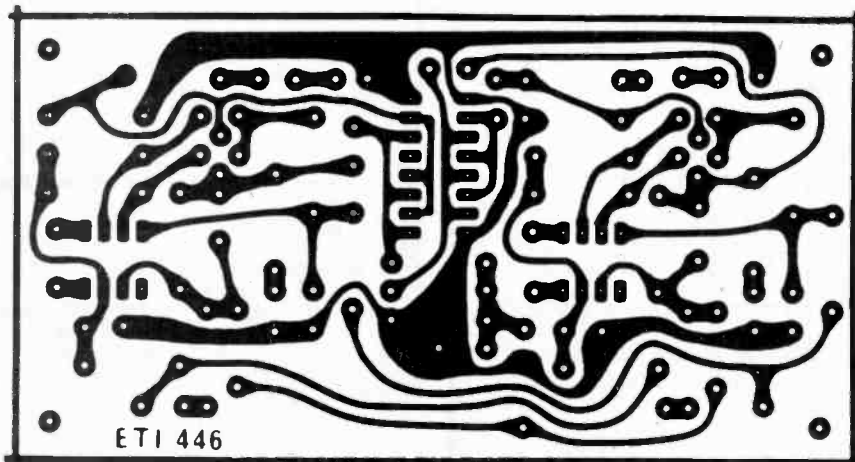*Do NOT substitute a 4009 or 4449 as the input protection is different.



Printed-Circuit layout for the limiter. Full size 58 mm x 110 mm.

As this unit will normally be used in association with another piece of equipment, and most likely built in to it, a case has not been described. When installing the unit make sure that the input cables are coaxial or shielded cable -- outputs are not important and can be normal hookup wire.

USES OF A LIMITER


Peak Limiting. In this mode only signals above 85% of maximum level are attenuated. This is useful for preventing amplifier clipping (for pop groups or other live shows) which gives rise to objectionable distortion. It may also be used when tape recording the same type of programme material as above, to prevent the tape being saturated, which again would give rise to distortion.

AVC. In this mode, the limiter is used typically to drastically reduce the dynamic range of a programme being recorded. For example, when recording a lecture the 60dB dynamic range of lecture room speech may be compressed to 6dB.

Voltage Controlled Amplifier. As a voltage-controlled amplifier the unit lends itself to a variety of remote or automatic control applications. For example, it may be used as a remote control for stereo amplifier volume. Alternatively, it may be adjusted to increase car radio volume as ambient noise level rises.

Special Effects. The limiter may also be used to modify the sound of musical instruments. For example, such a limiter is often used to eliminate the attack transient on a bass guitar to give a smoother mellower sound.

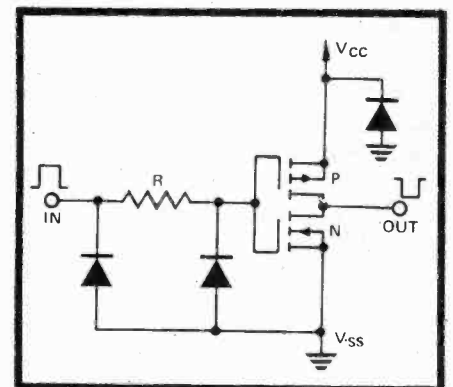The uses of such a circuit are wide indeed, and we are sure our readers will think of many more applications for this interesting circuit. ●



Internal circuit diagram of one of the six inverter stages in the CMOS 4049 IC

ROTEX Emmen Holland

**SPECIAL
INTRODUCTION
OFFER**



£ 64.79

**RX-6
2 METER RECEIVER** 144-146 Mc/s

Order no. 02.003
With VFO tuning, so that you can listen to all 2 meter transmissions.
Sensitivity : 0.8 μ V
Bandwidth : 15 kHz
Built-in 5 meter and loudspeaker
Power Supply : 12 V
Dimensions : 22 x 21 x 6,5 cm
I.F. : 10.7 Mc/s and 465 kc/s



£ 57.22

**RX-6
MINI 2 METER RECEIVER** 144-146 Mc/s

Order no. 02.006
This receiver has the same electronic modules built-in as its bigger brother. The mini, however, has its loudspeaker in the base of the set. Indispensable for those who want to pass the examination to get a license.

In both RX-6 Receivers there is enough space to build-in the RZB-6, the ROTEX 2 meter 6 channels transmitter module with built-in FM modulator, crystal controlled oscillator, 48..... Mc/s, FM modulation, output approx. 0,5 Watt, output imped. 50-70 Ohm. Completely built module, dim. 15x7 cm, exclusive X-tals.
Order no. 06.308.



**FREQUENCY
COUNTERS** RFC-30 AND RFC-250

A professional frequency counter with up to 4 measuring ranges to resp. 30 and 250 Mc/s. Indication by 6 clear 8 mm cipher LEDs. Count- and overwindication by green and red indicator LED. Max. input voltage 200Vrms, input sensitivity till 10Mc/s better than 250mV. Crystal time base 1 Mc/s. Accuracy ± 1 digit \pm time-base stability. Power supply 220V 50c/s. Dimensions: b x h x d 16x8x25cm Weight: 1,2 kg. Double side plated through epoxy print has been used.

This real quality with 12 months guaranty at the best price possible. A special designed cabinet which can stand up-right and with a very handy solution to get rid of the cable when not in use.

THE BEST VALUE FOR MONEY NOT ONLY FOR AMATEURS, BUT ALSO FOR INDUSTRY - SCHOOLS ETC.

RFC-30 **£ 85.36**

RFC-250 **£ 111.07**



Terms of Business
Prices are excl. VAT, C.W.O.
Post and packing, add £4.00 per order. Any difference will be credited or charged. Prices are subject to alteration without notice.

All these articles are available at time of going to press. Send your cheque or money order to

ROTEX
P.O. Box 260, Emmen, Holland
Telef. 0031-5910-16810
Telex 53910



£ 51.08
RMZ-8

£ 42.51
RMZ-7

METALDETECTOR

RMZ-7
Order no. 25.057
A simple, reliable water proof, shock proof, well balanced and very light weight treasure finder. Operating according to BFO (Beat Frequency Oscillation) system. With tone signal, built-in loudspeaker and connection for an ear-phone, which is supplied. Operates on a simple 9 Volt battery.

RMZ-8 as the RMZ-7, but with both sensitive signal intensity meter and signal indication.

STEREO MIXERS

MP-2001 MD STEREO MIXER
Order no. 15.068


Your house-sound-studio with the semi-professional ROTEX stereo-mixer.

- 4 stereo-inputs for pick-up, microphone, tuner, taperecorder etc.
- Separate volume control
- Level indication by means of illuminated stereo VU-meter
- Separate controls for treble and bass
- Built-in 220V/50c/s mains supply
- Freq. range 20c/s - 20kc/s $\pm 1,5$ dB
- Output level 0 dB, 600mV, Output 2.5 k Ohms
- Size & weight: 60x160x405mm, 1,7 kg

This type of mixer is at 2 channels, namely channel 1 and 2, supplied with a compensating-amplifier for MD (Magneto Dynamic) pick-up elements. The third input is suitable for connection of a dynamic or capacitor (electret) microphone. The fourth input is suitable for a tuner, tapepart or crystal p.u. with an output level of 0,1-1V.

MP-2002 MD STEREO MIXER
Order no. 15.134

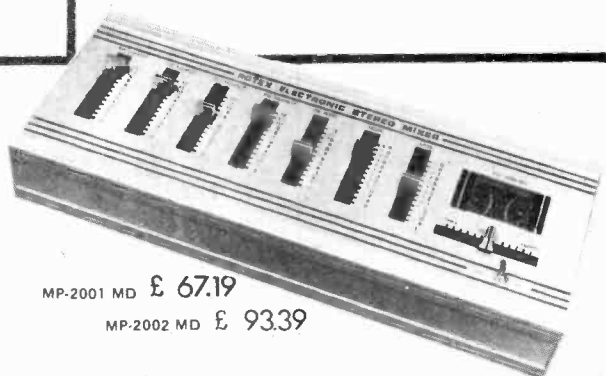A second type from the ROTEX mixer series like the MP-2001, but incl. adapted microphone with swan-neck, fading slide control and front monitor. Connection for headphones, of which the volume can be separately adjusted by means of slide control.



MP-2001 MD **£ 67.19**

MP-2002 MD **£ 93.39**

AUDIO MODULES

A NEW APPROACH TO QUALITY HI-FI

Cliffpalm Ltd. introduce a flexible range of high quality modules to enable a sophisticated hi-fi system to be built up from simple beginnings. An initial 20W r.m.s. + 20W r.m.s. stereo with standard controls can be expanded to give a 40W + 40W system with (in addition to the normal bass, treble and balance controls) a further range comprising "rumble" and "hiss" switchable controls with a range of frequencies; and a stereo image width control.

STEREO PRE-AMP: CP-P1 PRICE £13.30

+ VAT £1.66

Specification:

Input	Sensitivity	Signal/Noise	Impedance
Magnetic	3mV	>70dB	47KΩ
Tuner	100mV	>70dB	10KΩ
Tape	100mV	>70dB	10KΩ
Auxiliary	1-100mV	60dB-70dB	200KΩ

Magnetic i/p overload 33dB.
Distortion 0.04% at 1 KHz; Output 1v r.m.s. into 10KΩ.
Supply voltage ±18v nominal.
Tone controls, Bass ±12dB at 100 Hz; Treble ±12dB at 10KHz.

Description: This is a general purpose 2-channel pre-amplifier, suitable for use with gramophone, tape microphone or tuner inputs. It requires no external components other than the potentiometers for the bass, treble, balance and volume controls and the input selector switch. The unit is internally protected against accidental reversed supply connection.



AMPLIFIER: CP2-15-20 PRICE: £12.85

+ VAT £1.61

40W r.m.s. single.
20W r.m.s. + 20W r.m.s. stereo.

Specification:

Power output: 40W r.m.s. into 8Ω, 1 channel.
OR 30W r.m.s. into 15Ω, 1 channel.
OR 20W r.m.s. + 20W r.m.s. into 4Ω, 2 channel.
OR 15W r.m.s. + 15W r.m.s. into 8Ω, 2 channel.

Input Sensitivity 1v r.m.s.; Frequency response 20Hz-20KHz. at -3dB; Distortion 0.04% at 15W; Supply Voltage ±18v nominal; Size 5 1/4 x 4 1/2 inches. 130 x 102 x 32 mm.

Description: This module is designed to give either a 20W + 20W stereo amplifier or alternatively a 40W single channel. It has built-in protection against accidental reversed supply connection and it incorporates a thermal shutdown facility to prevent over-dissipation. No external components are required.



FUNCTION GENERATOR: CP-FG1 PRICE: £11.75

+ VAT £1.47

For those requiring a wider range of facilities, this module provides bass and treble filter controls, comprising switchable cut-off frequencies for "rumble" and "hiss" reduction. Also included is a stereo separation control. The unit is complete except for the potentiometer and switches.

POWER SUPPLY: CP-PS 18/2D PRICE: £5.75

+ VAT £0.72

This is suitable for one 20W + 20W complete system. For a 40W + 40W system, two power supplies are required.

Full application notes are provided. Post and Packing are free on all orders. All units are guaranteed for 2 years.

Cliffpalm Ltd.

Dept. HF/ETI
13 HAZELBURY CRESCENT
LUTON LU1 1DF, BEDS.

AN L.C.D. FOR UNDER £22!

OUR INTRODUCTORY OFFER—

INSTAR 103P L.C.D.

Constant readout of Hrs, Mins & pulsating Sec colon. No buttons to push. Built-in trimmer for precise timekeeping. Gold-plated case with S/S back and matching adjustable bracelet. Supplied in presentation box. Limited availability.

£21.50 incl.

SPECIAL OFFER — NEW FROM USA

Advanced technology of

FAIRCHILD TIMEBAND L.C.D.s

5/4 functions — Continuous readout of Hrs, Mins & pulsating Secs. Single command button — push once for Month/Date — Twice for Secs. — PLUS — programmed 4 Yr. calendar/Back light for viewing in darkness/Optional continuously alternating Time-Date display/AM-PM setting indicator. These are beautiful watches. Supplied in Presentation Boxes.

TC 411 White £29.50 incl.

TC 410 Gold £32.50 incl.

On leather strap.

TC 413 White £34.50 incl.

TC 412 Gold £37.50 incl.

With matching bracelet.

OUR VERY SPECIAL L.E.D. OFFER—

GALA 6 + 3 functions. Hrs/Mins/Secs/Alpha Day/Date/Month PLUS — Programmed 4 Yr. Calendar/A.M.-P.M. set Ind./Auto hold and fade. Available in Stainless Steel or Gold plated with S/S back and matching bracelet. Sold elsewhere at £22.90.

OUR PRICE — £18.95

Prices include V.A.T. at 8%, P.&P., AND RECENT MANUFACTURERS' INCREASE DUE TO DEVALUATION. Free battery/s. No quibble. 1 Yr. guarantee. Quartz accuracy to within a very few seconds a month. A LOT OF TIME FOR THE MONEY from TEMPUS, the electronics firm specialising in L.C.D. and L.E.D. watches.

Cheque or Money Order please to:

**TEMPUS, Dept. ETI, 5-7 NORFOLK STREET
CAMBRIDGE CB1 2LD. Tel: Cambridge 55094**


Offers subject to availability



Vero Electronics Ltd. manufacture cases to give your projects a professional finish. Cases are available in plastic, extruded aluminium and PVC coated steel. A new catalogue describing these cases, Veroboard, pins, tools, card frame etc. is available (price 10p + S.A.E. 7" x 9")

vero

THE CASE OF THE PROFESSIONAL FINISH...

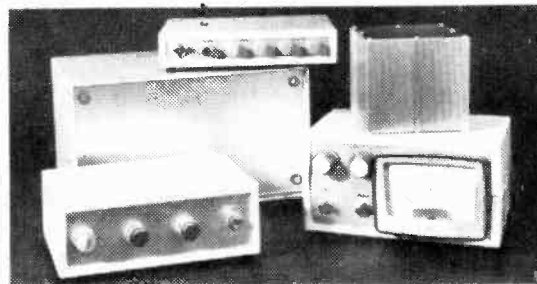

Vero Electronics Limited, Retail Dept.,
Industrial Estate, Chandler's Ford, Hants., SO5 3ZR
Telephone: Chandler's Ford 2956 (STD 04215)

ELECTRONICS PART 34

-it's easy!

More about digital instrumentation.

VERY FEW VARIABLES to be measured by electronic means provide a digital signal directly: this is because the real-world is predominantly analogue by nature. Consequently, most so-called digital measurement systems involve a number of stages to make the signal compatible with the digital circuits of a system.

The most straight-forward 'digital' measurement method (at least at present), is to employ a suitable analogue sensor that provides a voltage (or current) output, related to the variable being measured. This signal then feeds an A/D converter to obtain a digital equivalent.

The low cost of digital calculation circuitry now enables linearization of sensor processes at moderate cost. Figure 1 gives an example of the digital linearization used in a thermocouple thermometer unit.

By referring to Fig. 2, we see that the linearization process, in the dual-slope digital voltmeter section of the system, is achieved by changing the ramp slope at a number of points. To do this a rate multiplier is used to multiply the clock frequency by a variable number, $N/256$, where N may be any number between 1 and 256. By this means 256 different ramp slopes may be generated. The slope in use is tracked by a segment counter which, in turn, causes a read-only-memory (ROM) to set up the correct digital-readout code.

Some sensing principles lend themselves to a more direct digital signal approach. For example, in the Moire-fringe displacement sensor, a grid of fine lines (called a grating) formed on glass is attached to the moving (or fixed) member of the machine whose movement is to be monitored. This is shown in Fig. 3. The other member carries a small index grating set to produce Moire-fringes which move as the two grids pass relative to each other. Movement of these fringes is monitored by photocells which provide a number of electronic pulses proportional to the magnitude of the displacement. These pulses can be counted directly with a reversible

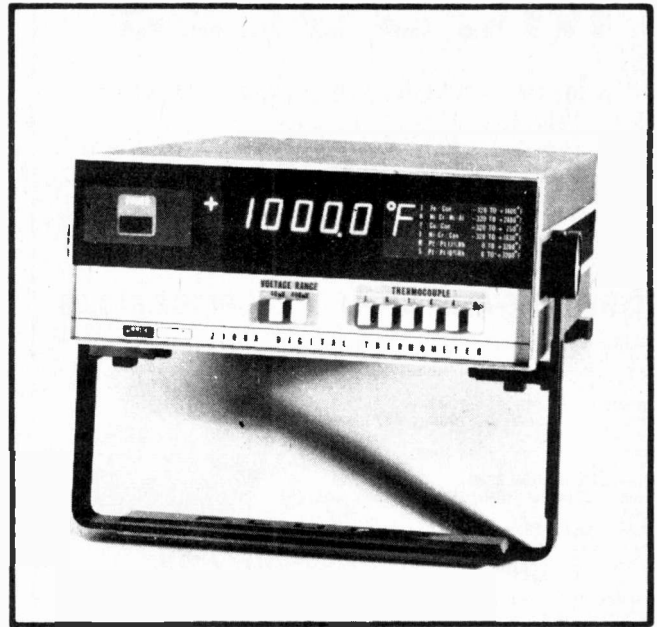


Fig. 1. This Fluke 2100 series digital thermometer incorporates digital linearization. It is suitable for use with any one of six common thermocouples.

Fig. 2. Block diagram of the digital linearization technique used in a digital thermometer.

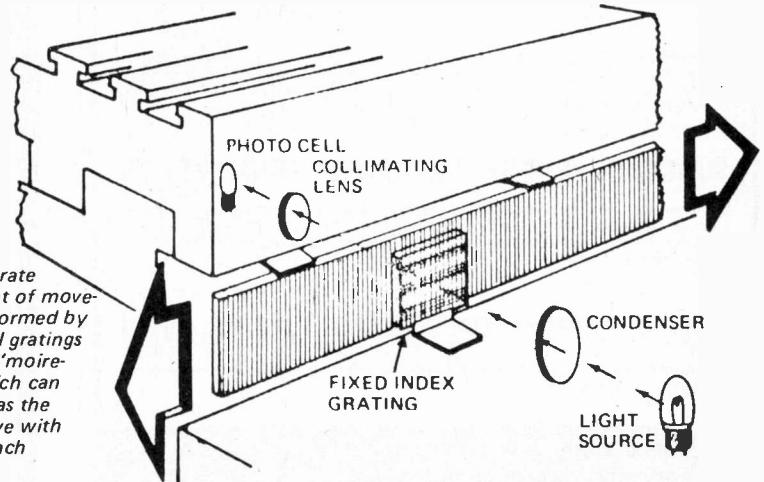
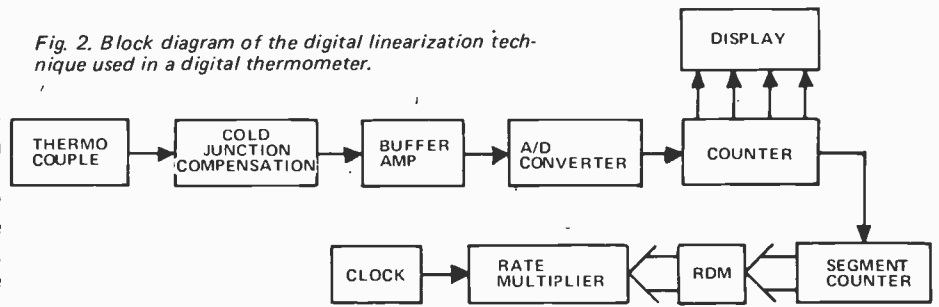


Fig. 3. Accurate measurement of movement is performed by using optical gratings to produce "moire-fringes" which can be counted as the gratings move with respect to each other.

direction counter, thus allowing both directions of movement to be followed. Such a unit is known in the metal working industry as digital readout (DRO). A somewhat similar length measuring system is the laser interferometer — this also provides fringes that can be counted to provide

a measure of absolute displacement. Clearly in such cases the digital instrument must not lose or gain stray counts or else the wrong value is indicated. Such systems are called incrementals.

There is an alternative method which uses digitally encoded discs similar to

those shown in Fig. 4. This is an absolute method which is not subject



Fig. 4. A 10 bit optical Gray code disc. The value read from this gives the angular displacement.

to pulse loss or gain, or to power failure errors which occur in the previous system if not fitted with a special non-volatile memory. The discs of such a system are read optically as though they were registers or other forms of digital store, each position having a different digital code as read across a radial line.

In some forms of digital pulse transducer it is the rate of pulse production that represents the variable, not the absolute number of pulses. An example of this sensor is the turbine flow meter used to measure liquid or gas flow. Figure 5 shows such a flowmeter where a small turbine rotates inside a pipe at a speed related to the flow rate. Rotation may be converted into pulses using optical, magnetic, capacitive or, in earlier designs, mechanical sensing. This form of sensor provides a variable frequency output which can be converted by a counter/timer system into a direct readout of flow rate.

Digital transducers are somewhat similar. They provide a signal which varies in frequency as the variable being measured changes. The sensor of such a transducer is made such that it alters a parameter of a frequency generating circuit. For example the quartz-crystal thermometer shown in Fig. 6 operates in this manner. In this unit temperature causes the resonant frequency of a crystal, mounted in the end of the probe, to change in a predictable fashion.

It is interesting to note that many natural physiological sensors operate on the pulse-rate system — neurons (the digital nerve sensors on the end of the nervous system) trigger with pulse repetition rates that rise in accordance with the intensity of the actuating signal (heat, cold etc).

Considerable effort has been expended — especially in the Eastern European countries in the late 60's — to produce reliable low-cost industrial sensors that provide a digital form of output. These have not, however, been accepted to the extent hoped. The current low-cost of extremely powerful digital circuits, however, is likely soon to produce a trend toward sensing devices having digital output.

ANALYSERS

Analysis is the general process used to break down an unknown by methods which separate and distinguish basic elements of seemingly complex arrangements, the elements so derived being satisfactorily

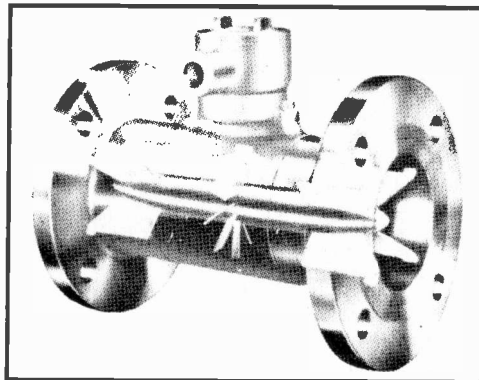


Fig. 5. Turbine flow meters like this one provide an output in the form of a pulse train with a pulse repetition rate proportional to flow rate.

understood basic quantities.

Synthesis is the alternative approach wherein a system is built up from known elements to produce the complex case.

Analysis may be regarded as being required when the behaviour of an existing system needs to be *studied*. Synthesis is used when a system is to be *devised*. There are of course many instances when both approaches are used to yield a solution.

Various types of electronic analysers are used in electronics. We will look here at spectrum analysers, logic state analysers and pulse-height analysers as these types are commonly met in modern circuit work. Each of these operates on an existing electrical signal

breaking it down into frequency content, logic-state content and height of pulses, respectively.

SPECTRUM ANALYSERS

Signals in the time-domain, that is those displayed as amplitude versus time graphs, can also be displayed in terms of their amplitude-versus-frequency and phase-versus-frequency characteristics. (This was discussed in Part 4 where an example wave-form — a square wave — was broken up into its harmonics). The relationship between time, amplitude and frequency are seen by studying the three forms (shown in Fig. 7) of a fundamental sinewave having a large degree of second harmonic added in. Signals displayed as amplitude (or phase) versus frequency are said to be in the frequency domain. This kind of plot shows the frequency spectra of the signal, hence the name spectrum analysers.

The role of spectrum analysers is to display the signal content in its frequency domain form. There exists many instances where this form of display is better than a time-domain representation. Typical examples are where a fundamental has distortion (Fig. 8a) or where low levels of modulation or noise exist (Fig. 8b). Neither of these conditions could be satisfactorily detected, let alone measured, by a time-domain test.

Basic spectrum analysers use analogue circuitry and therefore do not qualify properly for inclusion in a discussion on digital instruments. However, as we will see later, the current trend is to include digital techniques in such instruments. Advanced analysis equipments, for example, often use a built-in digital computer.

There are two alternative forms of spectrum display. First, the repetitive signal can be studied over an extended time period by scanning across the expected frequency-range with narrow band-pass filters. A speedier, but more expensive method, works in a real-time mode thus preserving the time-dependency between signals.

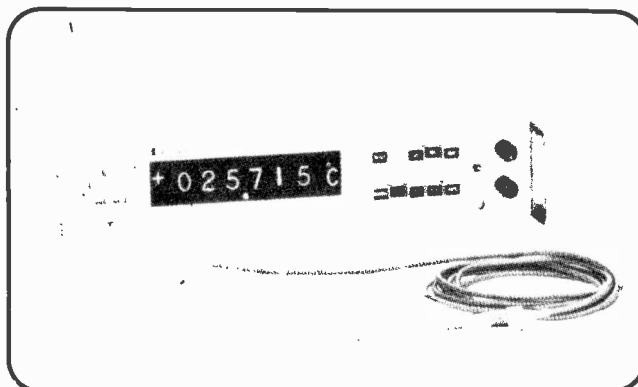


Fig. 6. Quartz-crystal thermometer from Hewlett-Packard.

ELECTRONICS—it's easy!

These are known as swept-tuned and real-time spectrum analysers respectively.

Swept-tuned systems — Basically the task is to establish the amplitude (and sometimes phase) of the signal at each frequency in turn. Many practical difficulties exist because the absolutely narrow band filter does not exist and even if it did, it would take an enormous time to sweep it across the full bandwidth of the signal. Practical filters also have finite bandwidth and roll-offs. The bandwidth of the filter may also need to change if the requirement is for a filter bandwidth that is always a given proportion of the signal frequency as it sweeps the range.

Most difficulties are overcome by mixing the signal with a swept local oscillator and then detecting the output and using it to drive the Y plates of an oscilloscope. The sweep signal drives the X plates. Figure 9 depicts this arrangement.

Real-time systems — These use a stack of band-pass filters and detectors each connected to the signal simultaneously and with each having staggered centre frequencies. This is shown schematically in Fig. 10. The scan generator multiplexes the individual channels in order to produce a continuous spectrum on the oscilloscope screen.

It is clear that this method is much more expensive because many filters are needed. It does, however, enable a detailed analysis of once-only transient signals which could not be analysed with the swept-tuned arrangement of a spectrum analyser.

A range of spectrum analysers is available for the study of signals from 5 Hz to 50 GHz. Different instruments (or the use of different plug-ins with the same display unit) are needed because units typically cover only 4 to 5 decades, that is, say 5 Hz-50 kHz, 10 kHz-300 MHz and so on. The range is, however, ever widening. Wide range, however, is not always the virtue needed for spectral resolution is related to width of display screen.

Fourier Analysers — A third method of providing a frequency analysis is based on direct mathematical calculation using the Fourier transform technique to convert a time-domain signal into its frequency-domain equivalent. Such systems are extremely expensive compared with the above analysers, but provide a vastly greater capability.

They can also handle signals at the very-low-frequency end — dc to 100 kHz is typical. Their operation is



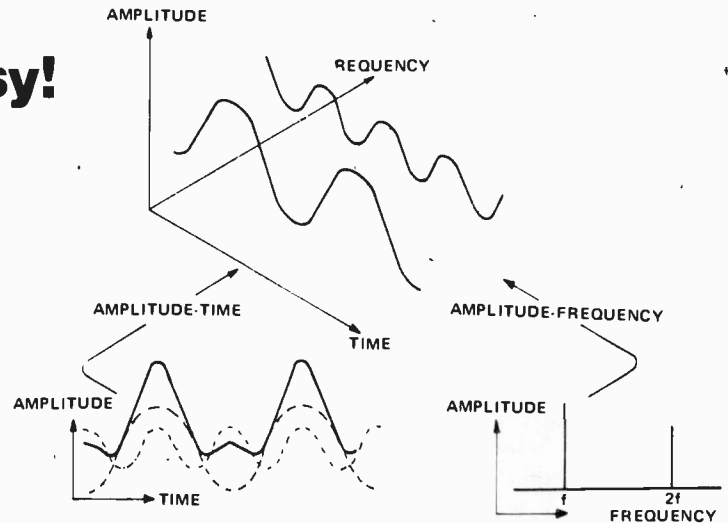


Fig. 7. Second harmonic distortion is not always easily seen on an amplitude versus time display. In the amplitude versus frequency display the second harmonic distortion and its amplitude are clearly seen.

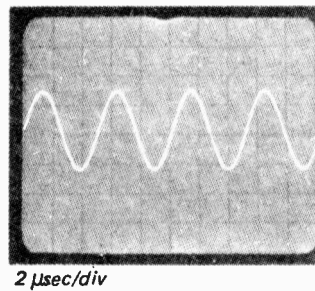


2 μsec/div

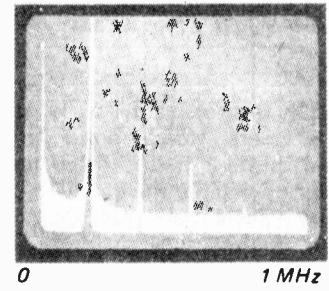


0

1 MHz

Fig. 8a. Frequency domain displays are often better than the time-domain method as these HP displays illustrate: (a) In the time domain (left) the signal looks pure but the spectrum analyser shows that it has significant distortion.

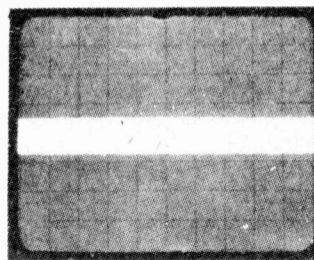

20 msec/div

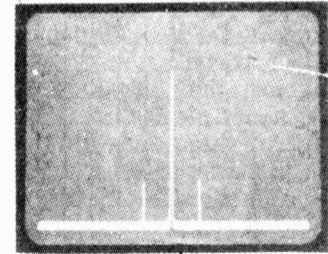

15 MHz 200 kHz/div

Fig. 8b. A 2% amplitude modulation is barely discernible on time domain plot (left). The frequency domain plot clearly shows the frequencies present and their amplitude.

quite different from the above in that the signal is fed as data values into the analyser unit via keyboard or paper tape from another computer or mass-storage system. It can also be fed in as an analogue signal from, for example, magnetic tape. The heart of the Fourier analyser is a micro-programmable computer system which can be set to compute using various programmes such as the so-called Fast-Fourier method of analysis. The same unit may also be able to carry out correlations between signals, plus many other processing techniques.

Digital circuitry in spectrum analysers

— Digital circuits are being added by manufacturers to enhance the performance of analysers. Advantages

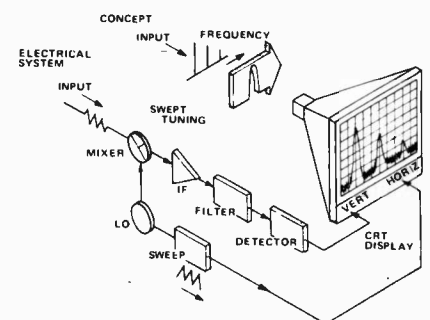


Fig. 9: Schematic of swept-tuned form of spectrum analyser.

claimed include operating ease and better placement of controls. Digital storage of the display signals can be used to enhance the display brightness and to allow a spectrum to be 'held' for comparison against a second spectrum obtained later. Digital

included; this reduces the noise thereby enhancing the signal/noise ratio on the display — as is illustrated in Fig. 11. Character generation (using digital methods) has been incorporated to display the relevant graph-axes factors — as shown in Fig. 11. The same unit also uses a photo-optical absolute-digital code disk to replace the mechanical switch usually used in a range control-knob.

Spectrum analysers are invaluable and are finding increasing use. Successful use is, however, a matter of experience and frequency-domain techniques are not dealt with as extensively as time-domain ones in training programmes. More details are available in the reading list — we can only provide the most elementary introduction here.

Logic-State Analysers — We check the operation of analogue circuits by measuring signal levels and frequency spectra at various points in the circuit. Digital circuits are different in that they contain the signal information in the form of multi-digit 'words' made up of two-state bits. To check operation, therefore, we must ascertain simultaneous logic-states at various points in the circuitry. The simplest analyser for this work is a probe which indicates logic hi or lo state at a selected point; coloured lights are used as indicators. A store function can be built-in to the probe to catch a short transition that would not otherwise be seen in the lamp display. It must also have connections suitable for PC board digital circuitry — see Fig. 12.

The single probe can be used to analyse the state of a circuit by moving from point to point in turn. To speed-up the analysing process a more extensive facility to use would be one that simultaneously shows the logic states of multiple points in the so-called Data-domain. The Hewlett-Packard system, for example (shown in Fig. 13), displays over 500 points as a matrix of 0's or 1's on a CRO screen. These instruments are used to debug, test or trouble-shoot complex digital circuits. Only large laboratories, however, would be able to justify the cost of such advanced logic analysers.

Pulse-height analysers (Discriminators) — Measurement processes involving ionising radiation and sometimes light-intensity levels rely on pulse counting, the pulses appear as rapid electrical currents produced from a photo-multiplier or ionisation detector. The relative amplitude of a pulse often distinguishes it from pulses from other sources. For example, different radio-active isotopes produce pulses of different energy, enabling an assay of radio-active mineral to be


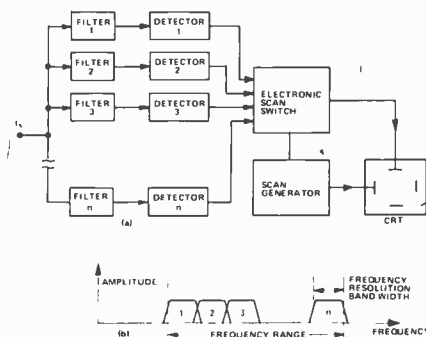


Fig. 10. Block diagram of real-time spectrum analyser based on stacked filters: (a) schematic (b) frequency response showing individual filter windows.

Fig. 11. The Tektronix spectrum analyser incorporates various digital techniques that provide character generation on the display and reduce the noise level of a signal. The adjacent photo shows the original unfiltered signal containing the two small signals and noise (recovered in the CRO display).

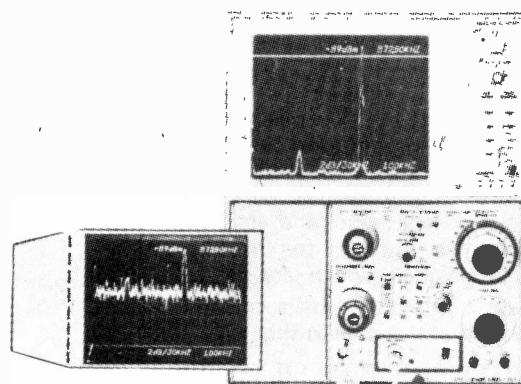

made by a study of occurrence of pulses of different height. Photons arising from the various noise sources in photo-multipliers have different energy from those generated at the photo-cathode. This is a true detection process: noise can be reduced by discrimination of pulse heights.

Pulse height analysers use carefully selected trigger levels to accept only those pulses (for counting) that arise from the particular source of interest. Pulses above the trigger window, or below are rejected (not counted) as demonstrated in Fig. 15.

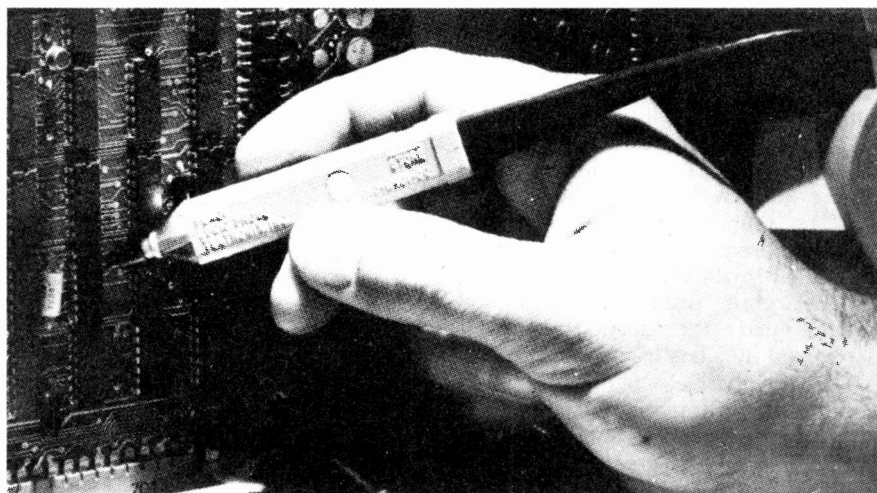


Fig. 12. Simple logic probe in action.

SYNTHESIZERS

These are a special kind of signal generator in that the signal output is formed by addition of a number of sources or by manipulation of a single, stable-reference frequency. A music synthesizer provides a whole range of musical sounds by combining many different tones into a single output. Although synthesizers work upon basic analogue signals the trend is to combine or modify the signals using digital control.

The advantages offered are (in the variable frequency generator kind of synthesizer) that a very stable reference oscillator has its frequency translated to (literally) billions of other values (the HP 8660 gives

10 kHz-2600 MHz) whilst retaining high stability. By pressing digital-key inputs, any chosen frequency value is generated. It is also possible to control the output via a programmable BCD digital input. Programming enables an enormous range of signals to be synthesized, a typical requirement being as part of an automatic test procedure. Figure 14 shows the philosophy of the HP 3330 series of automatic synthesizers with a typical programme card marked up for a frequency sweep routine.

Digitally-controlled power sources

ELECTRONICS—it's easy!

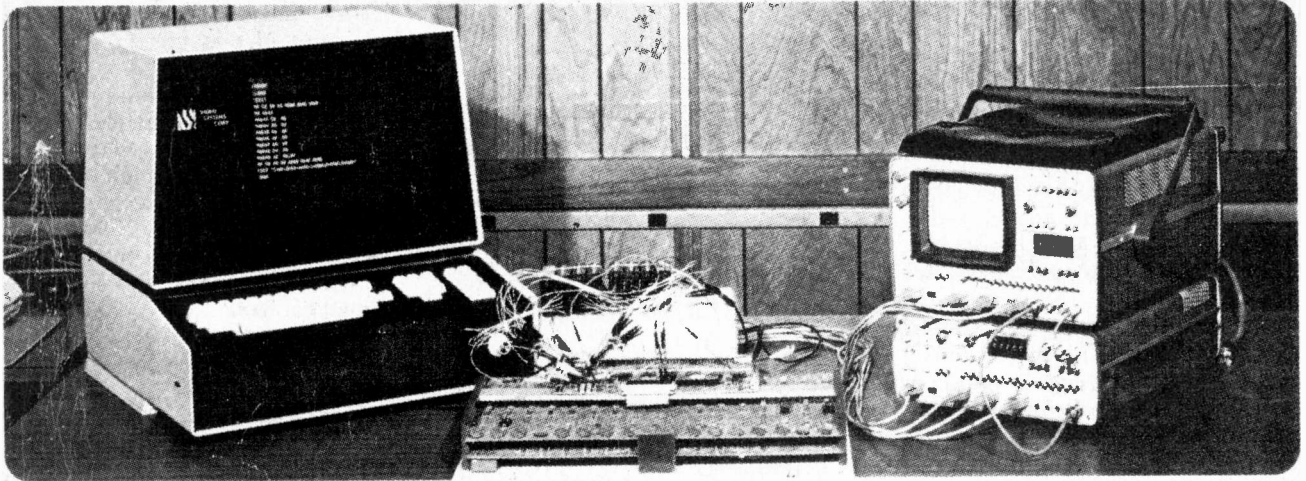


Fig. 13. Hewlett Packard logic-state analyser as set up to test a printed-circuit board card.

may be used to synthesize varying voltage (or current) levels over a test period at the commands of a mini computer in the same way as the above unit synthesizes frequencies.

Frequency and voltage synthesizers are often combined in the hybrid-computer (digital and analogue combined) in order to generate synthesized signals which are needed to derive a simulation of a complex system, such as a missile in flight.

COMPUTER CONTROLLED TEST SYSTEMS

With the enormous increase in complexity of routine complex processes (such as aircraft instrumentation and controls, refineries, automatic and large-volume manufacture of electronic systems) came the need to improve and speed-up the testing procedures needed to check-out the thousands of different parameters involved. Computer controlled testing is far more reliable than human operator testing and is extremely fast. It can be economic even for the testing of small volume electronic equipment, especially where a large range of tests is involved.

The instrument or process to be tested is interfaced to the main test console which usually incorporates a wide range of facilities that are chosen with flexibility of operation in mind. Figure 15 shows an automatic system used to calibrate a test instrument. The test programme must be devised by a highly-trained professional designer, but once developed and programmed the testing can be performed by a less trained person.

It is not possible here to deal in depth with automatic testing as the range of requirements and equipment available are both great. The overall concept and scope of an automatic test system is shown in Fig. 16. Suffice to say very complicated automatic

testing systems are in routine use in a wide variety of manufacturing and maintenance situation.

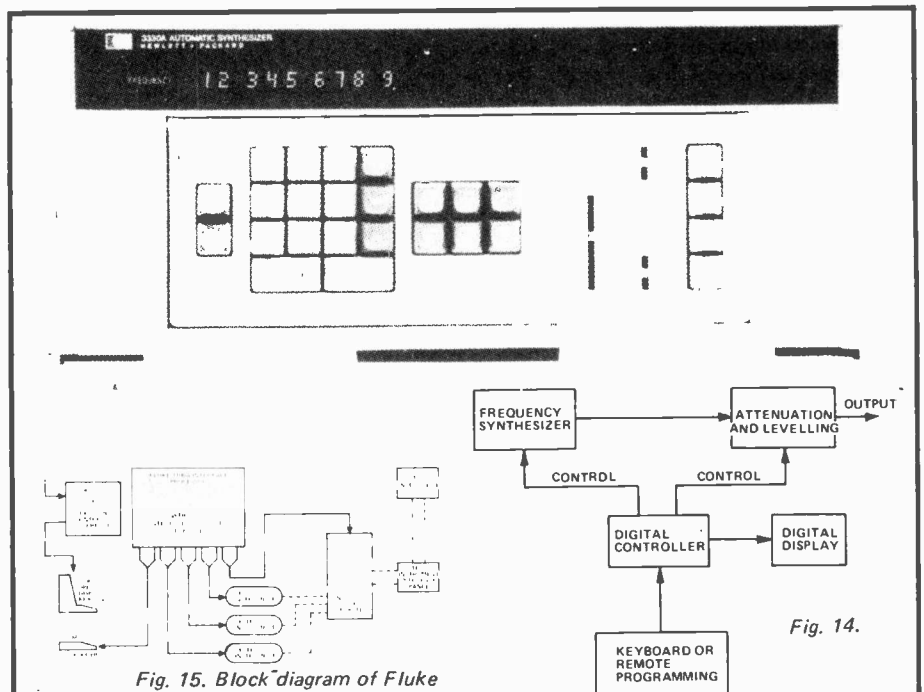


Fig. 15. Block diagram of Fluke calibration standard.

Fig. 14.

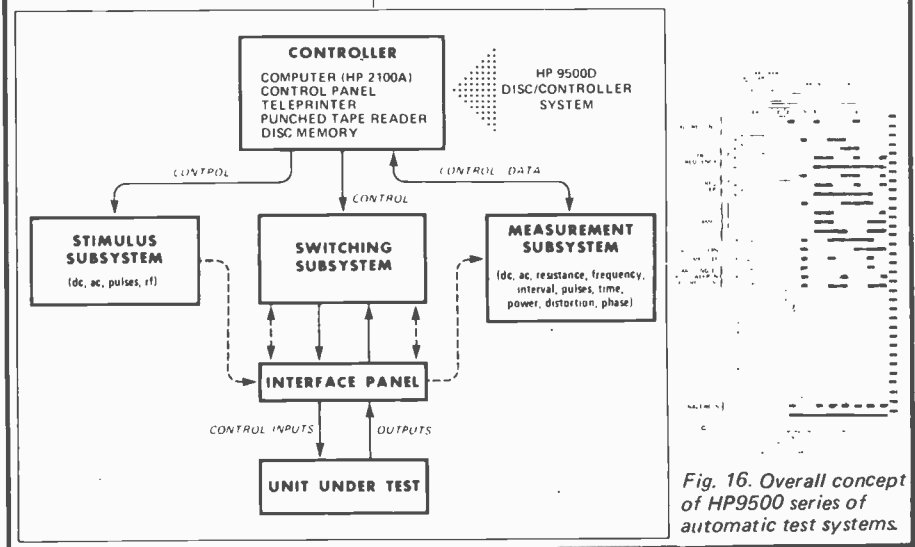


Fig. 16. Overall concept of HP9500 series of automatic test systems.

New Course in Digital Design


Understand the latest developments in calculators, computers, watches, telephones, television, automotive instrumentation

Each of the 6 volumes of this self-instruction course measures 11¼" x 8¾" and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers.

After completing this course you will have broadened your career prospects and considerably increased your fundamental understanding of the changing technological world around you.

Design of Digital Systems
A Self-Instruction Course in 6 Volumes

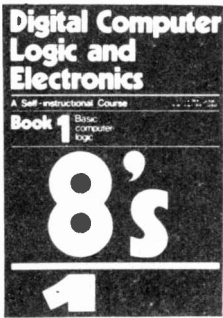- 1** Computer Arithmetic
- 2** Boolean Logic
- 3** Arithmetic Circuits
- 4** Memories & Counters
- 5** Calculator Design
- 6** Computer Architecture



Digital Computer Logic and Electronics
A Self-Instructional Course
Book 1 Basic computer logic

8's

£4.20

plus 80p p&p


Offer. Order this together with Design of Digital Systems for the bargain price of £9.70, plus 80p p&p.

Design of Digital Systems contains over twice as much information in each volume as the simpler course, Digital Computer Logic and Electronics. All the information in the simpler course is covered as part of the first volumes of Design of Digital Systems which, as you can see from its contents, also covers many more advanced topics.

Also available — a more elementary course assuming no prior knowledge except simple arithmetic.

In 4 volumes:

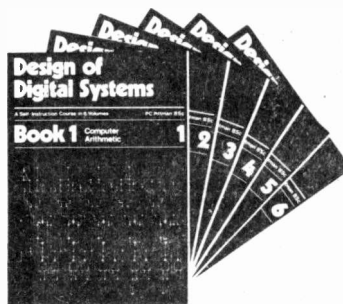1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flip flops and Registers



£6.20

plus 80p packing and surface post anywhere in the world (VAT zero rated). Payments may be made in foreign currencies. Quantity discounts are available on request.

**Designer
Manager
Enthusiast
Scientist
Engineer
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

Guarantee—no risk to you

If you are not entirely satisfied with Design of Digital Systems or Digital Computer Logic and Electronics, you may return them to us and your money will be refunded in full, no questions asked.

To: Cambridge Learning Enterprises, Dept. Dig., FREEPOST, St. Ives, Huntingdon, Cambs PE17 4BR

*Please send me set(s) of Design of Digital Systems at £7.00 each, p&p included

*or set(s) of Digital Computer Logic and Electronics at £5.00 each, p&p included

*or combined set(s) at £10.50 each, p&p included

Name.....

Address.....

.....

.....

.....

*delete as applicable. ETI 12

No need to use a stamp—just print FREEPOST on the envelope.

SORRY ALL 35RO'S NOW SOLD

**CREED 5 LEVEL COMBINED PRINTER AND PERFORATOR
NEW CRATED £35 each**

**CREED 5 LEVEL
PAPER TAPE READER
£25 each**

**CREED 7B
TELEPRINTER CRATED
£40 each**

£5 discount on any pair plus FREE carriage. Otherwise £2.50 carriage each item.

**MARCONI TF675F
WIDE RANGE
PULSE GENERATOR**
+/- variable outputs up to 50V.
Optional delay. Small compact unit.

**THE LATE MODEL MARCONI
OSCILLATOR TF885A/1**
in superb condition covering 25HZ to 12MHZ
sine wave in 3 ranges and 50HZ to 150KHZ
square wave. High output 31.6V. Meter
scaled in volts and dBs.

**FURZEHILL
VALVE VOLTMETER**
V200A Audio to 10MHz with probe
1MV FSD as new condition.

**MARCONI TF1106
NOISE GENERATOR**
4 ranges 0-5; 0-10; 0-15; 0-30

ALL ITEMS **£22.50** each
SPECIAL OFFER — pick 3 different
items of the 5 for
£60
Carriage £2.50 each or £5 for 3

**AVO VALVE
TESTER CT160**
"The Suitcase". Size approx. 15"
wide x 10" high x 11" deep.

**TRANSFORMERS — All 240V 50HZ
input**
Type A 17.0-17V 250 MA; 7.5-0-7.5V
250MA 0-20V 5Amps; 0-4V 5 Amps
0-1-1 5V 5 Amps **£2 ea.** P&P 1.25
Type B 17.0-17V 250MA; 8.0-8V 250
MA; 0-12.5-13.5V 5 Amps; 0-1.5-2V
5 Amps; **£1.80 ea.** P&P 1.1
Type C 19.0-19V 250MA; 8.0-8V 250MA;
0-7.5V 5 Amps; 0-1.4V 5 Amps **£1.25 ea.**
P&P 1.25.
Type D 34V 4 Amps; 19V 4 Amps; 17V 4
Amps; **£3 ea.** P&P 1.25
Type E 3V 1 Amp; **25p ea.** P&P 50p.
Type G 20.0-20V 200 MA; 0-6V 100MA;
75p ea. P&P 75p. Atlantic series
All Brand New. (APT surplus types A, B, C &
D; Honeywell surplus type E; Recordacall
surplus type F; Parmeko Atlantic series type
G).

ONLY £10 EACH
Stabilised Power Supply, 240V 50HZ
Input Outputs — 15V @ 10A; +15V @
4A; -4.5V @ 12A; -2.1 5V @ 15A Size
16 x 20 x 9". Auto overload trips on each
voltage rail with pushbutton resets. MANY
OTHER POWER SUPPLIES — Call and see

★POT PACK. All Brand New Modern. Single
and Ganged, our choice. **7 for 25p.** P&P
48p.

SEMICONDUCTORS — All at 8p ea.* P&P
extra. Guaranteed all full spec devices
Manufacturer's markings:
BC147; BC158; 2N3707; BC107; BF197;
BC327; 2N4403; BC172B; RC261B;
BC251B; BC348B; BC171A/B
2N3055RCA **50p ea.** P&P 8p.
2N5879 with 2N5881 Motorola 150 Watt
Comp. pair **£2 pr.** P&P 15p
★Linear amp 709 **25p ea.** P&P 8p

VARIACS 240V input 0-270V output.
8 Amp **£18 ea.** 20 Amp **£30 ea.** Carr.
extra.

BNC Plug to BNC Plug lead, assembled
ready to use **75p ea.** P&P 20p.
Ex-eq. BNC Socket **15p.** BNC Plug **20p.**
BNC Plug & Socket 30p pair. P&P 15p.

TUBES — All Brand New. Boxed.
Electrostatic Deflection:
Type 408A 1 1/2" dia., 7 1/2" long. Blue
Trace **£2.50 ea.** P&P 75p.
Type CV1526 (3EG1) 3" dia. **£4 ea.** P&P
1.1.
Type DB7/36 3" dia. (Replacement for
Telequipment S31) **£15 ea.** P&P 1.50.
Type 5BVP1 5" dia. PDA, X, Y Low
Capacitance Side Pins. Green Trace **£5 ea.**
P&P 1.50.

Type GEC 924F 3 1/2" dia. (Replacement for
Telequipment D33 & Solartron 1016
scopes). **£30 ea.** P&P 1.50.

Type GEC 924E 3 1/2" dia. (Replacement for
Solartron 1015 scope) **£20 ea.** P&P 1.50.
Magnetic Deflection
**12DP7 12" round. Blue with yellow
afterglow. £1 ea.**
And for the VDU BUILDERS.
M38-111GH Rectangular 30 x 20cm.
Green Trace. Superb value **£12 ea.**
or Economy type CME1220 24 x 18cm.
White Trace. **£9 ea.**

**COME — WHEN
NOW — WHY
BARGAINS GALORE**
or send for lists

★SPECIAL OFFER
Guaranteed full spec devices. Manu-
facturers markings.
BC 204 & BC 207A **4p ea.** P&P extra.

★TELEPHONES
Post Office Style 746. Black or two-tone
Grey **£6.50 ea.**
Modern Style 706 Black or two-tone Grey
£4.50 ea.
Modern Standard Style in Grey or Black
with a place to put your fingers like the
746. **£3 ea.** As above but discoloured Grey
only **£2 ea.** All telephones complete with
standard dial and bells. P&P all styles 75p
ea. Handsets, complete with 2 inserts and
lead **£1.75 ea.** P&P 65p.

**NEW — UPGRADED CONTENTS — FOR
LESS MONEY**
★31b Electronic Goodies **£1.60** post paid
★High Value Printed Board Pack — hundred
of components, transistors, etc. — no flat to
the board transistors **£1.65** post paid.

VERY SPECIAL PRICES
★1000F Feed thru Capacitors **10 for 30p.**
P&P 15p

★BEEHIVE TRIMMERS 3/30pf. BRAND
NEW.
10 Off **40p**, P&P 15p; 100 off **£3.50**, P&P
75p; 500 off **£15**, P&P 1.25; 1,000 off
£25, P&P 1.50.

HIVAC Miniature NEONS
App 60V. Brand New. 10 off **20p.**
P&P extra.

LARGE RANGE ELECTROSTATIC VOLT-
METERS, from 0-300V 2" **£3**; to 250KV
Max.
General guide 5KV 3 1/2" **£5**; thereafter **£1**
per KV. P&P 75p.

MARCONI TF1101 Audio Oscillator. 20c/s
to 200kc/s. Low distortion. 60db step
attenuator. **£45 each.**

MUFFIN Fans 230 volt. Size 5 x 5 x 1 1/2".
Superbly quiet and reliable. Ex-eq. but
tested. **£1.50 ea.** P&P 75p.
IBM CLOCKS — SLAVES. 1 1/2". **£3 ea.**
P&P 1.1; 1 7/8". **£5 ea.** Plus Carr.; 2 3/8"
£7 ea. Plus Carr.; ITR CLOCKS SLAVES
7 1/8" **£5 ea.** P&P 75p.
★METER PACKS — 3 different meters **£2**;
P&P 1.
DON'T FORGET YOUR MANUALS. S.A.E.
with requirements.

GRATICULES 12 x 14 cm high quality
plastic **15p ea.** P&P 10p.
★CAPACITOR Pack. 50 Brand New
components, only **50p.** P&P 48p.
★TRIMMER PACK. All Brand New. 2 Twin
50/200pf ceramic; 2 Twin 10/60pf
ceramic; 2 min. strips with 4 preset 5/20pf
on each; 3 air spaced preset 30/100pf on
ceramic base **25p the lot.** P&P 15p.
RESETTABLE COUNTERS. 4 digit by
Stonebridge/Sodeco 1000ohm coil **£2 ea.**
P&P 35p.

★POTENTIOMETERS — All **5p each.** P&P
extra. Metal bodied AB Linear. PCB mount.
Brand new. 10K single; 100K Ganged;
250K Ganged; 100K Ganged concentric
shafts.

FIBREGLASS BOARD PACK. More board —
less money. Larger pieces. Not less than 2.5
sq. ft. for **95p**, P&P 65p.
Double or single sided cut to any size. New
Lower Price **1p per sq. in.** P&P extra.

HONEYWELL MAGNETIC TAPE UNITS
Self-contained, complete with heads, magnetic tape, leads, etc.
Tested. Carriage paid. **FROM £65**

NOW AVAILABLE
Various punches, tape reader, low
voltage power supplies, card frame,
modular cases, etc. Lists available

Minimum Mail Order £2. Excess postage refunded
Unless stated — please add **£2.50 carriage to all units**
VALUE ADDED TAX not included in prices — Goods marked with ★ 12 1/2 % VAT, otherwise 8 %
Official Orders Welcomed. Gov./Educational Depts., Authorities, etc., otherwise Cash with Order
Open 9 a.m. to 5.30 p.m., Mon. to Sat.

CHILTMHEAD LTD 
7/9 ARTHUR ROAD, READING, BERKS. (rear Tech. College, King's Road). Tel. Reading 582605

ELECTRONICS TOMORROW

by John Miller-Kirkpatrick

DIRECT ACCESS

SINCE I MENTIONED converting a record player into a mass storage device for a microprocessor a few people seem to have been considering the problem. If you remember I had suggested converting a 12in LP into a magnetically coated disk and then using a Read/Write head to travel across to one of several 'tracks' and then to read or write data on that track. The problems appeared to be in coating the disk and also in the low data capacity of the system. Eric Huggins of Stoke Poges suggested using a 16in disk at 78RPM divided into tracks 1/8in apart, recording in CUTS format which would give 128K bits of data with an access time of one second, if the more common 12in disk was used then the capacity would be reduced to 64K bits.

The main disadvantage of the disk appears to be in getting the thing coated and this problem led to the idea of a Mr Edison of America recording on a drum rather than a disk. Glyn Phillips of Highgate pointed this obvious omission in my line of thinking, if early phonographs used drums then why not early MPUs. To combine his ideas and those of Mr Francis of Sheffield you end up with a cylinder covered with rolls of magnetic tape. If you consider a cylinder about 6in in diameter (20in circumference) rotating at 1 revolution every ten seconds then the data would be passing the R/W head at 2 ips which is nearly the 1 7/8 ips used for cassette recording. With the CUTS system the recording speed is 300 bits per second or 150 bits per inch, thus each of our 20in tracks would hold 3,000 bits of data. With a standard monaural cassette recording head each track would be 1/8in

wide and thus a drum 10 inches long would have a capacity of 80 tracks of 24,000 bits of data. Using a stereo head would double the capacity of each drum as would doubling the diameter. If an ex-computer 9 track head and 1in wide tape can be found then the same system could be used at much higher densities. The data in this case could be recorded in parallel with the 9th track being used as a data clock, as densities of 800 and 1,600 bits per inch can be used then the capacity of our 10in by 6in drum would be 160 Kilobytes. Even if the unit cost £80 to build then the storage cost is only 50p per kbyte compared to nearly £50 per kbyte for RAM. If anybody gets anywhere near building one please let me know if it works!

RAM IT IN YOUR ROM SLOT

Or vice-versa if you prefer. One of the standard RAM chips made by several manufacturers is a 256 x 4 bit device in a 16 pin package, a typical number for this is the MM2112. The problem with RAM is that it is not very good for keeping long term storage such as programs or look-up tables. ROM is a much better storage medium for these applications as the data is not lost when the chip is unpowered, however, ROM is expensive for prototypes as each has to be manufactured complete with its data.

National Semiconductors have now announced the 74S287 TRI-STATE PROM which is pin compatible with the 2112 RAM and can be programmed easily in low volumes. This means that a microprocessor could be programmed and tested using RAM and than a


PROM copy made and plugged in in place of the RAM. The PROM programming sequence is fairly simple and a programmer could be built at little cost (again, let me know if you do build one). Programming will occur at a selected address when Vcc is held at 10.5v, the appropriate output is held between 9.5v and 11v and the chip is subsequently enabled.

1. Select the word address by applying high or low logic levels to the appropriate address pins. Ensure that the chip is disabled by a high level to one or both of the chip enable inputs.
2. Increase Vcc to 10.5v at a rate between 1 and 10 volts per microsecond, (Vcc must be capable of supplying 400mA).
3. Select one of the outputs where a logical '1' is required by raising that pin to 10.5v. Outputs not being programmed must be left open circuit and only one output can be programmed at each time.
4. Enable the chip by taking both enable inputs low for 10µS.
5. Remove the voltage from the output pin and then reduce Vcc to 4v. Enable the chip and check that the bit has been programmed to a logical '1'. For high programming yield steps 2-5 may be repeated up to 10 times.
6. Repeat 2-5 for each bit to be programmed in the selected word.
7. Repeat 1-6 until all 256 words are programmed, re-check each word.

Full details of the programming procedure of these PROMs and similar devices can be obtained from the manufacturers.

REAL FLOPPIES

Previously we discussed the idea of a direct-access device for use by an amateur constructor but we missed out on one important point. If you only require to store and retrieve information on your own MPU then a unit which is unique to your system is OK. If you wanted to exchange data with another MPU or with a large mainframe computer then you would have to use cassette or floppies. I have not heard of a mainframe unit which will accept CUTS format cassette tapes and therefore the best intercommunications device would be a floppy disk. Several types are now available on the market covering a range from full IBM compatibility to a new mini-floppy which was mentioned a couple of months ago.

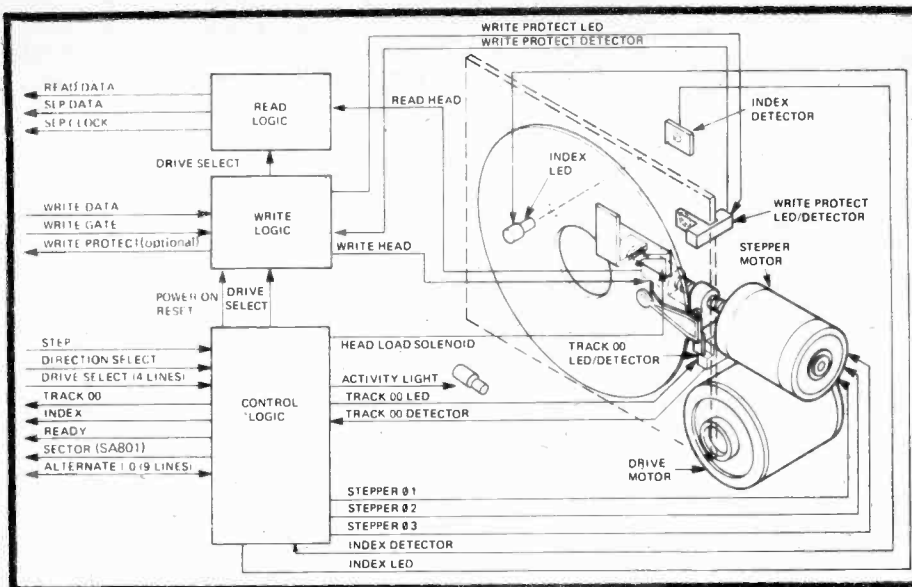

The SA800 Diskette Storage Drive from Shugart Associates has an IBM compatible capacity of 2 Megabits and an absolute maximum of 6.4 Megabits. The diagram shows its mechanical operation as follows — the required disk is slid into place and the unit started, this causes the drive motor to spin the disk at high speed. The Write Protect system works in a similar manner to that of a cassette tape by

not allowing a write to the disk if the disk is for read-only operation. An electrical stepping motor and lead screw positions the read/write head. The stepping motor rotates the lead screw clockwise or counter-clockwise in 15° increments, each increment moves the R/W head one track position. The R/W head is mounted on a carriage which is located on the Head Position Actuator lead screw.

The high rotational speed of the floppy (360 RPM) gives data transfer rates of 250 kilobits per second and an access time for any data on the disk of 260mS (average). Compare this to our earlier figures and some of you may decide to save up to buy a floppy rather than building your own. If the £625 price tag for the SA800 is too high then how about the £495 tag on a minifloppy? The SA400 is only 3½ x 6 x 8 inches in size but has about one-third of the capacity of the SA800 and uses a 5in disk rather than the 8in disk used on the standard floppy. With each disk costing only about £5 and holding nearly 100 kilobytes of data the price per kbyte is only 5p compared to 50p for our system and £50 for RAM.


REFERENCES:

RAM/PROMs — National semiconductors (UK) Ltd, 19 Goldington Road, Bedford. Signetics, Texas, Intel, etc. also do similar chips.
 Floppies: Shugart Associates, 435 Indio Way, Sunnyvale, Calif 94086; or contact Bywood Electronics.

ETI DIGITAL MULTIMETER KIT DMK1

This kit has been specially made available to ETI readers, and comes complete, down to the last screw. All you need is a few spare hours and some tools. The result will be a superb piece of test equipment that will be of invaluable use to the serious constructor or test lab.

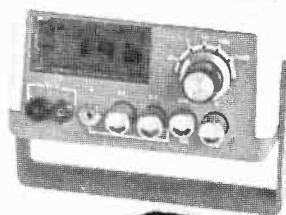Special Note:
 This kit has been produced in conjunction with the designer and author of the project in the October issue of ETI as several parts are not normally available, or specially manufactured.



PRICE
£65-50
 Inc. VAT & Postage (UK)

Please allow 21 days for delivery

★ A demonstration model can be seen working at our electronics centre. Full list and specifications. Send s.a.e. please.

- ★ High accuracy, spec as in project text.
- ★ Designer approved kit.
- ★ Silk screened panel with all lettering.
- ★ Test leads, prods, etc., supplied.
- ★ Assembly instructions included.
- ★ All parts available separately.

B H COMPONENT FACTORS LTD.

LEIGHTON ELECTRONICS CENTRE
 59 NORTH ST., LEIGHTON BUZZARD, BEDS. LU7 7EG
 TEL: 2316 (STD 05253)

GOVERNMENT & EDUCATIONAL ORDERS ACCEPTED
 GIRO NO. 331 7056 ACCESS & BARCLAYCARDS ACCEPTED

ORDER FORM
 TO B H COMPONENT FACTORS LTD.
 59 NORTH ST., LEIGHTON BUZZARD, BEDS.

Please supply 1 DMK1 kit

Name

Address

I enclose cheque / PO for £

Access of B / card No.


COMBINATION LOCK

The circuit and switching system is simplified by the use of a multiplex system. S1 inputs pulses to the decade counter 7490. The resulting BCD is decoded by the 7442. It is the decimal output of this which carries out the multiplexing via the AND-gates.

S2 inputs pulses which are transferred to the other 7490 decade counters by the AND-gate multiplex system. The BCD output from the 7490's is taken to the AND-gates whose outputs control the Alarm 'Disable' and 'Enable' switch system.

The 'Disable' function effectively prevents TR2 from being biased on and hence prevents the 'Enable' Reed relay from working.


This circuit has several advantages over conventional electronic combination locks as only two switches need be installed on the object to be guarded, regardless of the number of figures in the combination. The value of the example combination is 314. The alarm is triggered if any of these digits is exceeded in value. While the circuit is capable of directly driving an actuator it is recommended that it is only used to disable an alarm system —

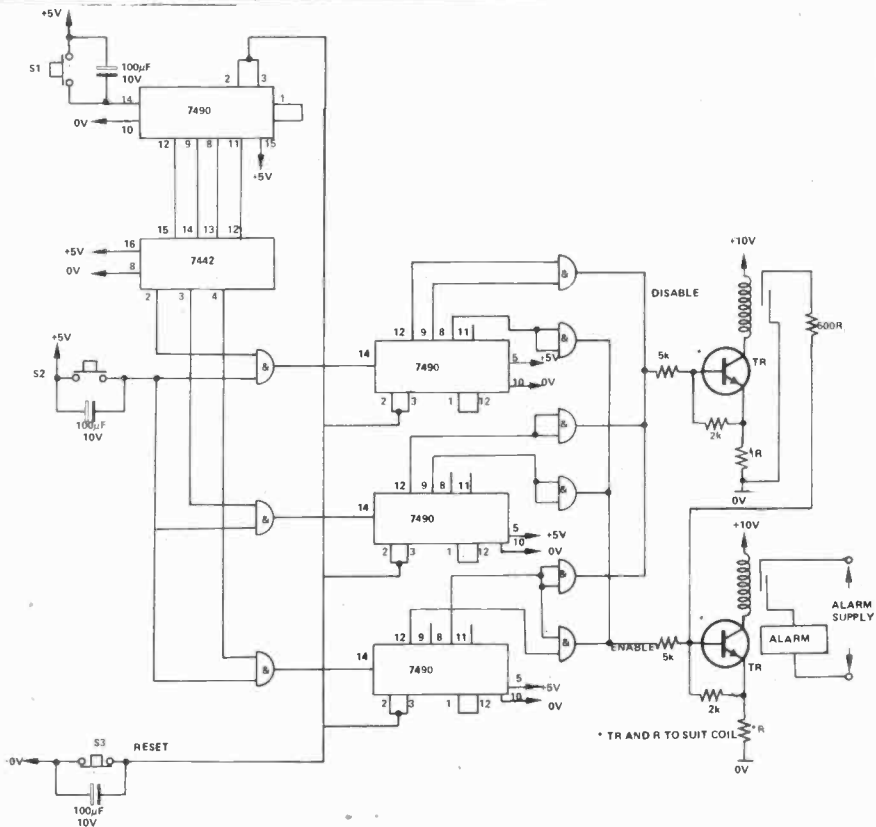

conventional locks doing the actual locking. (To operate the example the

switch sequence would be: S1, S2, S2, S2, S1, S2, S1, S2, S2, S2, S2.)


FILTERS USING CMOS

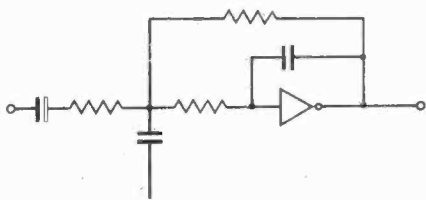

High pass and low pass filters may be readily constructed using CMOS inverters (CD4007 CD4069 74C04) since these have only a single complementary pair, and hence lower power dissipation and less likelihood of instability. A form of Sallen and Key: Standard equations are used to determine component values. It is recommended that passband gain be restricted to unity.

THYRISTOR TIP

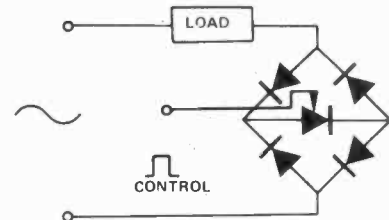
For full-wave control from a thyristor, add a bridge, how about:



ADSR ENVELOPE SHAPER

When a negative going trigger pulse is applied to the input, IC2(c) disconnects the 'release' pot, the bistable is set and the 'attack' pot connected to C1. C1 charges up to the threshold voltage of IC1(c) where the bistable is reset. IC2(b) causes C1 to discharge to the level set on the 'sustain level' pot. If S1 is in position '1', when the trigger pulse goes high again IC2(c) causes C1 to discharge via the 'release' pot.

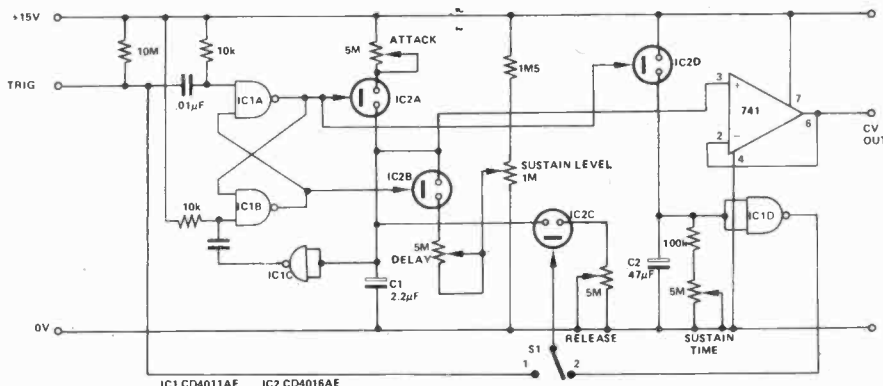During the time IC1(a) is high C2 is charged up forcing the output of IC1(d) low. Once IC1(a) has gone low C2 begins to discharge and after a



while IC1(d)'s output will go high again. When S1 is in position '2' the sustain is controlled by the monostable thus formed. It is retriggerable so


that should a second trigger arrive before the cycle has completed the cycle will restart. The 741 buffers the output.

15 — 240 Watts!

HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, Tuner, etc) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone controls merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: Complete pre-amplifier in single pack. Multi-function equalization. Low noise. Low distortion. High overload. Two simply combined for stereo.
APPLICATIONS: H.F.I. Mixers. Disco. Guitar and Organ. Public address.
SPECIFICATIONS:
INPUTS: Magnetic Pick-up 3mV. Ceramic Pick-up 30mV. Tuner 100mV. Microphone 10mV. Auxiliary 3100mV. Input impedance 47k Ω at 1kHz.
OUTPUTS: Tape 100mV. Main output 500mV R.M.S.
ACTIVE TONE CONTROLS: Treble -12dB at 10kHz. Bass - at 100Hz.
DISTORTION: 0.1% at 1kHz. Signal Noise Ratio 68dB.
OVERLOAD: 38dB on Magnetic Pick-up. **SUPPLY VOLTAGE:** 16.50V.
Price £4.75 + 59p VAT P&P free.

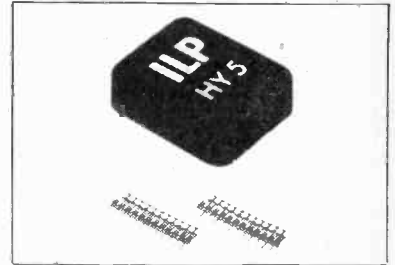

HY30 15 Watts into 8 Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C. heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up to date technology available.
FEATURES: Complete Kit. Low Distortion. Short, Open and Thermal Protection. Easy to Build.
APPLICATIONS: Updating audio equipment. Guitar practice amplifier. Test amplifier. Audio oscillator.
SPECIFICATIONS:
OUTPUT POWER: 15W R.M.S. into 8 Ω . **DISTORTION:** 0.1% at 15W.
INPUT SENSITIVITY: 500mV. **FREQUENCY RESPONSE:** 10Hz-16kHz. 3dB.
SUPPLY VOLTAGE: 18V.
Price £4.75 + 59p VAT P&P free.




HY50 25 Watts into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.
FEATURES: Low Distortion. Integral Heatsink. Only five connections. 1.7 Amp output transistors. No external components.
APPLICATIONS: Medium Power Hi-Fi systems. Low power disco. Guitar amplifier.
SPECIFICATIONS: **INPUT SENSITIVITY:** 500mV.
OUTPUT POWER: 25W RMS into 8 Ω . **LOAD IMPEDANCE:** 4-16 Ω . **DISTORTION:** 0.04% at 25W at 1kHz.
SIGNAL NOISE RATIO: 75dB. **FREQUENCY RESPONSE:** 10Hz-45kHz. 3dB.
SUPPLY VOLTAGE: 25V. **SIZE:** 105.50x25mm.
Price £6.20 + 77p VAT P&P free.



HY120 60 Watts into 8 Ω

The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection, this amplifier sets a new standard in modular design.
FEATURES: Very low distortion. Integral heatsink. Load line protection. Thermal protection. Five connections. No external components.
APPLICATIONS: Hi-Fi. High quality disco. Public address. Monitor amplifier. Guitar and organ.
SPECIFICATIONS: **INPUT SENSITIVITY:** 500mV.
OUTPUT POWER: 60W RMS into 8 Ω . **LOAD IMPEDANCE:** 4-16 Ω . **DISTORTION:** 0.04% at 60W at 1kHz.
SIGNAL NOISE RATIO: 90dB. **FREQUENCY RESPONSE:** 10Hz-45kHz. 3dB. **SUPPLY VOLTAGE:** 35V.
SIZE: 114.50x85mm.
Price £14.40 + £1.16 VAT P&P free.

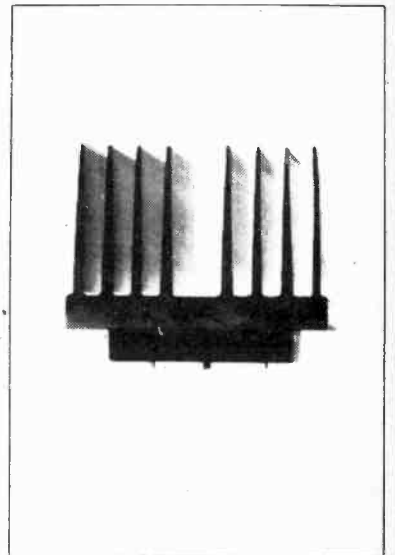


HY200 120 Watts into 8 Ω

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.
FEATURES: Thermal shutdown. Very low distortion. Load line protection. Integral heatsink. No external components.
APPLICATIONS: Hi-Fi. Disco. Monitor. Power slave. Industrial. Public Address.
SPECIFICATIONS: **INPUT SENSITIVITY:** 500mV.
OUTPUT POWER: 120W RMS into 8 Ω . **LOAD IMPEDANCE:** 4-16 Ω . **DISTORTION:** 0.05% at 100W at 1kHz.
SIGNAL NOISE RATIO: 96dB. **FREQUENCY RESPONSE:** 10Hz-45kHz. 3dB. **SUPPLY VOLTAGE:** 45V.
SIZE: 114.100x85mm.
Price £21.20 + £1.70 VAT P&P free.

HY400 240 Watts into 4 Ω

The HY400 is I.L.P.'s Big Daddy of the range producing 240W into 4 Ω ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi fidelity power module.
FEATURES: Thermal shutdown. Very low distortion. Load line protection. No external components.
APPLICATIONS: Public address. Disco. Power slave. Industrial.
SPECIFICATIONS: **OUTPUT POWER:** 240W RMS into 4 Ω . **LOAD IMPEDANCE:** 4-16 Ω . **DISTORTION:** 0.1% at 240W at 1kHz.
SIGNAL NOISE RATIO: 93dB. **FREQUENCY RESPONSE:** 10Hz-45kHz. 3dB. **SUPPLY VOLTAGE:** 45V.
INPUT SENSITIVITY: 500mV. **SIZE:** 114x100x85mm.
Price £29.25 + £2.34 VAT P&P free.

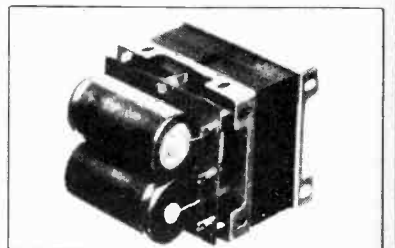

POWER SUPPLIES

PSU36 suitable for two HY30's £4.75 plus 59p VAT. P. P. free.
 PSU50 suitable for two HY50's £6.20 plus 77p VAT. P. P. free.
 PSU70 suitable for two HY120's £12.50 plus 1.00 VAT. P. P. free.
 PSU90 suitable for one HY200 £11.50 plus 0.92 VAT. P. P. free.
 PSU180 suitable for two HY200's or one HY400 £21.00 plus 1.68 VAT. P. P. free.

TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd
 Crossland House
 Nackington, Canterbury
 Kent CT4 7AD
 Tel (0227) 63218

Please Supply _____
 Total Purchase Price _____
 Enclose Cheque Postal Orders Money Order
 Please debit my Access account Barclaycard account
 Account number _____
 Name & Address _____
 Signature _____


TONE BURST GENERATOR

The circuit in Fig. 1 generates the waveform shown in Fig. 2. The output is basically oscillations at a certain frequency outputted in small pulses. This type of waveform has varied uses ranging from a beat for an organ or synthesizer to audio or radio frequency testing.


The variable parameters of the waveform are shown in Fig. 3:-

VR1 alters the time between pulses.
C1 alters the length of the pulse.
VR2 alters the amplitude of the waveform.

Cx alters the frequency of the waveform within a pulse. This ranges from .0005 giving RF, to 5 giving AF. (microfarads)

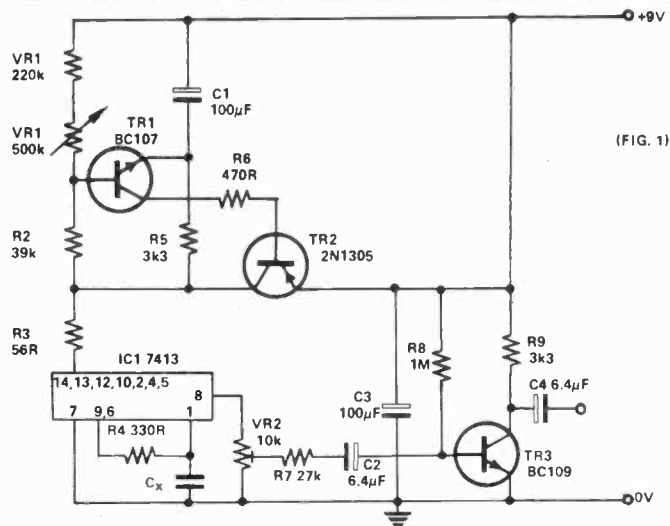


(FIG. 1)

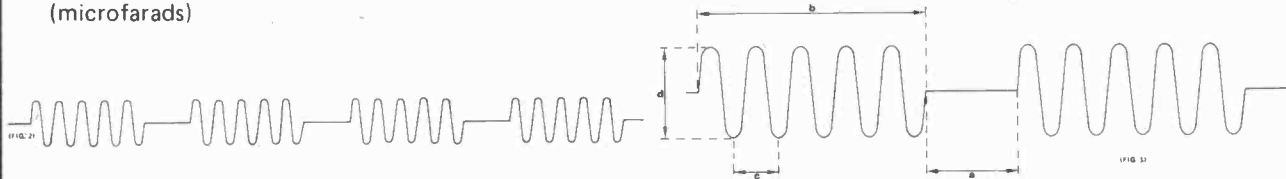

MOBILE POWER SUPPLY

R1, C1 and ZD1 provide clipping and smoothing of supply spikes, while D1 protects against reverse polarity connection. The reference voltage is provided by the ring-of-two, since in this configuration the zeners bias constant-current sources for each other, the output across ZD3 is almost totally independent of supply variations. R2 ensures the ring starts reliably.

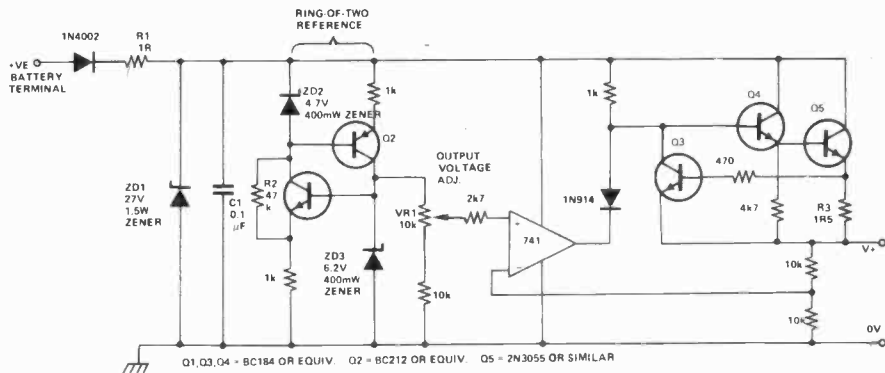A set fraction of the reference voltage is applied, via VR1, to the 741, which in conjunction with current amplifiers Q4, Q5 forms a negative feedback loop to maintain the output voltage constant. It may be set




between 10 and 6 volts, so, for instance, most battery cassette equipment may be driven. Short-circuit protection is provided by Q3; when the output current exceeds 400mA

sufficient voltage is dropped across R3 to turn on Q3, which shunts drive away from the base of Q4 and hence prevents the output current from rising further.

EASY SLIDER FITTING

After making out the slots in their respective positions, three or four holes are drilled close to each other at one end of the slot. These holes are then joined up by initially using a needle file followed by a flat ward file. The resultant slot should be large enough to accommodate three hacksaw blades side by side as shown on the sketch.

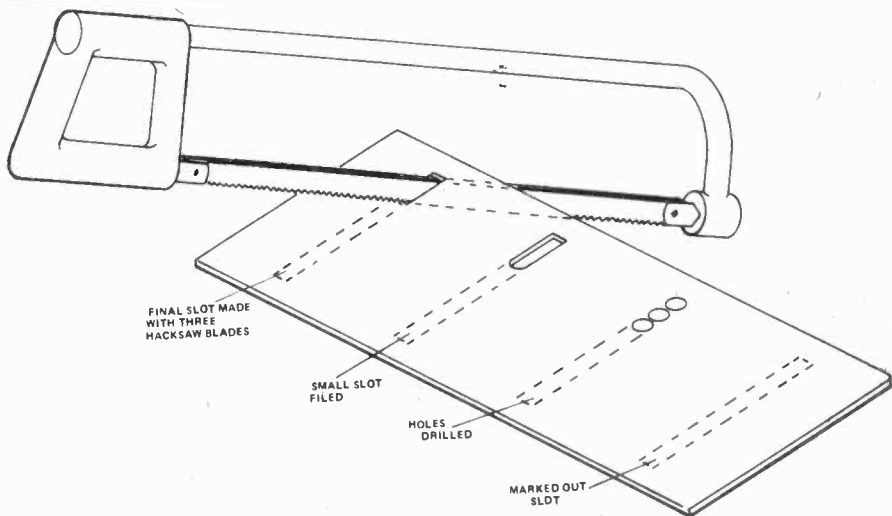These blades are fixed in a standard hacksaw frame or can be hand held. Using this arrangement, the required width of the slider control slot can be easily cut for any given length, and finishing off with a file.




tech-tips

LOW FREQUENCY SQUARE WAVE OSCILLATOR

A drawback of low frequency oscillators using bipolar transistors or TTL logic is that the timing capacitor usually has to be a high value electrolytic. Using a field effect transistor at the input of a schmitt trigger, means a low value capacitor can be employed. The trigger by TR1 and TR2 has a hysteresis of approximately 3V. This is controlled by the 3V zener.

With C1 uncharged TR1 is off and TR2 is forward biased. The voltage at the source of TR1 is approximately +4V. TR2 conducts, thus turning on TR3. The output is therefore at +10V. Capacitor C1 now charges via R1 and the gate voltage of TR1 goes positive. When the gate voltage is sufficiently positive TR1 conducts, turning off TR2. The positive feedback from the emitter of TR2 to the source of TR1 ensures a

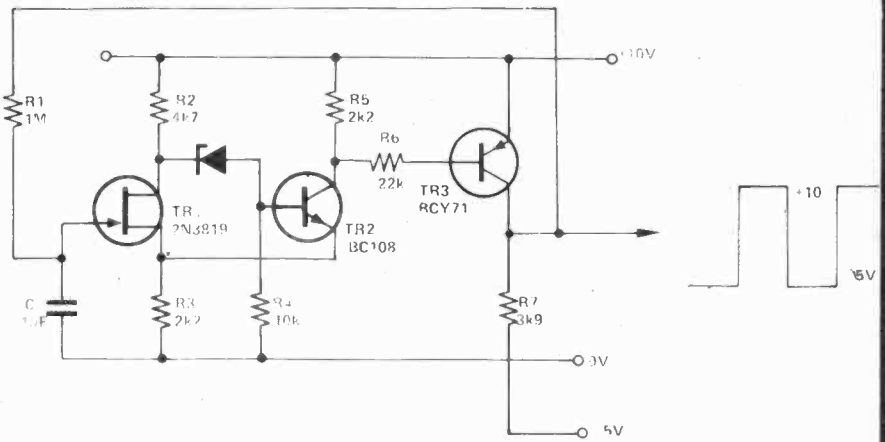

rapid switch off. TR3 also switches off and the output goes to -5V. Capacitor C1 now discharges towards -5V, but when the voltage across C1 falls by approximately 3V, TR1 ceases to conduct, turning on TR2.

The collector load of TR3 is connected to a negative supply giving a

50% duty cycle. (The circuit still oscillates if R7 is connected to 0V but the duty cycle will change, the output remaining at 0V for a longer period than at +10V).

With the components as shown the frequency of the output is approximately 0.025Hz.


CODE SWITCH

When button 3 is pressed R3 'Gates' SCR 1, which remains on with a load of R1. It also supplies voltage to the anode of SCR 2.

When button 7 is pressed SCR 2 is 'Gated' by R3 also, and held on by R2, thus supplying the anode of SCR 3, which when 'Gated' by button 9 closes the relay and makes an external circuit.

It can also be used to switch a circuit off depending on how the relay is wired. This would be an advantage in a home intruder alarm.

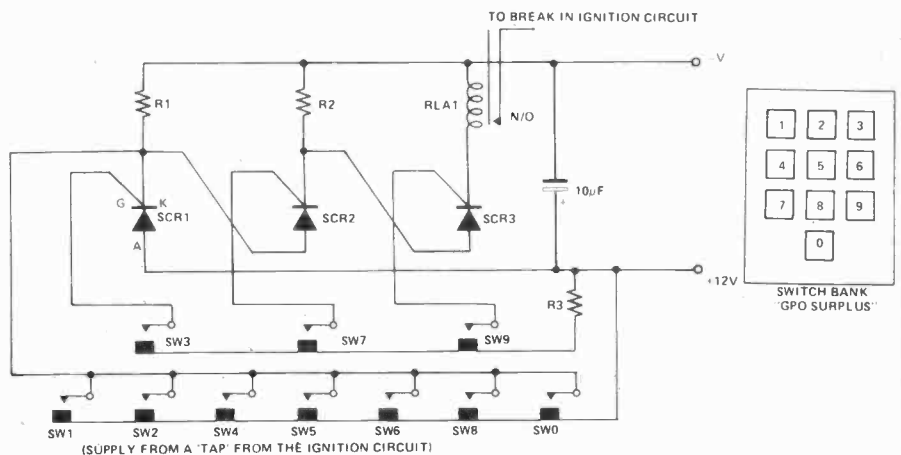Components: The Thyristors can be any type and values for R1 and 2 selected to hold the SCR's in conduct-




ion. R3 is selected to suit the thyristors. The remaining buttons, 1,2,4,5,6,

8,0 when pressed short out SCR1, thus switching off any following SCR.

THE 7400 A TWO-WAY DATA SELECTOR!

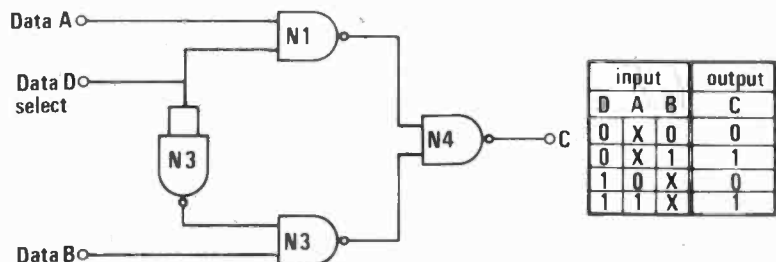When the "DATA SELECT" terminal is at logical '0', the output of N1 is held high, whilst information presented on the "DATA B" terminal is transferred to the output of the circuit. Similarly, when the "DATA SELECT" terminal is at logical '1', the output of N3 is held high, whilst "DATA A" is transferred to the output. In a parallel data system one 7400 would be used for each bit.



PRINTED CIRCUIT KIT £3.95*

Make your own printed circuits. Contains etching dish 100 sq ins of pc board 1lb ferric chloride dalo pen drill bit, laminate cutter

JC12 AMPLIFIER

6W IC audio amp with free data and printed circuit
£2.25*

DELUXE KIT FOR JC12

Contains extra parts except JC12 needed to complete the amp including balance volume bass and treble controls Mono £2.33 Stereo £4.95

JC12 POWER KIT

Supplies 25V 1Amp £3.55

JC12 PREAMP KITS

Type 1 for magnetic pickups, mics and tuners. Mono £1.50. Stereo £3.00 Type 2 for ceramic or crystal pickups. Mono 88p. Stereo £1.76

SINCLAIR IC20

IC20 10W+10W stereo integrated circuit amplifier kit with free printed circuit + data £4.95
PZ20 Power supply kit for above £3.95
VP20 Volume tone-control and preamp kit £7.95

JC40 AMPLIFIER

New integrated circuit 20W amplifier kit complete with chip, printed circuit and data £4.45

FERRANTI ZN414

IC radio chip £1.44 Extra parts and pcb for radio £3.65 Case 90p Send sae for free data

BATTERY ELIMINATOR BARGAINS**STABILIZED POWER UNITS***

Millenia series Switched 1 to 30V in 0.1V steps 1Amp. Kit £11.45 Kit + case £14.40 Built £20.40 2Amp Kit £13.95 Kit + case £16.90 Built £22.95

6-WAY SPECIAL £4.95*

Switched output of 3 4½ 6 7½ 9, 12V at 500mA

FULLY STABILIZED MODEL £5.45*

Switched output of 3/6 7½/9V stabilized at 400mA

3-WAY MODELS*

With switched output and 4-way multi-jack connector Type 1 3 / 4½ / 6V at 100mA £2.94 Type 2 6 / 7½ / 9V at 250mA £3.10

RADIO MODELS

50mA with press-stud battery connectors 9V £3.25 6V £3.45 9V + 9V £5.45 6V + 6V £5.45 4½V + 4½V £5.45 Also 9V 300mA £3.95 6V 400mA £3.95

CASSETTE MAINS UNITS

7½V with 5 pin DIN plug 50mA £3.45 300mA £3.95

CAR CONVERTERS £5.10*

Input 12V DC Output 6/7½/9V DC 1Amp stabilized

BATTERY ELIMINATOR KITS

Send sae for free leaflet on range

100mA radio types with press stud battery terminals 4½V £1.95 6V £1.95 9V £1.95 4½V+4½V £2.60 6V+6V £2.60 9V+9V £2.60

100mA cassette type: 7½V with 5 pin DIN plug £1.95

Transistor stabilized 8-way type for low hum 3/4/6/7/8/9/12/15/18V 50mA £3.15 1Amp £6.50

Heavy duty 13-way types 4½/6/7/8/9/11/13/14/17/21/25/28/34/42V 1Amp model £4.95 2Amp model £7.55

Car converter kit: Input 12V DC Output 6/7½/9V DC 1A transistor stabilized £1.95

MAINS TRANSFORMERS

6-0-6V 100mA £1.90-9V 100mA £1.18V 1A £1.95 0/12/15/20/24/30V 1A £4.30 12-0-12V 50mA £1.0/12/15/20/24/30V 2A £5.95 20V 2½A £2.95 6-0-6V 1½A £2.85 9-0-9V 1A £2.55 12-0-12V 1A £2.95 15-0-15V 1A £3.20 30-0-30V 1A £4.10

S-DECS AND T-DECS*

S-DeC £2.24 T-DeC £4.05 u-DeCA £4.45 u-DeCB £7.85 IC carriers with sockets 16 dil £2.05 10T05 £1.95

SINCLAIR CALCULATORS AND WATCHES*

Cambridge Universal £6.60 Cambridge Scientific £8.95 Oxford 300 £13.30 Programmable Scientific with free mains unit £24.95 Mains adaptors for other models (state type) £3.20 Assembled Grey Watch with free stainless steel bracelet £16.45

SINCLAIR PROJECT 80 AUDIO MODULES

PZ5 £4.95 PZ6 £8.70 Z40 £5.75 Pro 805Q £18.95

BI-PAK AUDIO MODULES

S450 tuner £18.95 AL60 £4.33 PA100 £13.45 MK60 audio kit £27.20 Teak 60 £10.95 Stereo 30 £15.95 SPM80 £3.35 BMT80 £3.50 Send sae for free data

SAXON ENTERTAINMENTS MODULES

SA1208 £19 SA608 £12 PM1202/8 £15 PM601/8 £10

SWANLEY ELECTRONICS

Dept. ETI, PO BOX 68, Swanley, Kent

Send sae for free leaflets on all kits. Post 30p on orders under £2.23 otherwise free. Prices include VAT. Overseas customers deduct 7% on items marked otherwise 11%. Official orders welcome

BUILD THE TREASURE TRACER MK III



METAL
LOCATOR

AS SEEN
ON BBC-1
& BBC-2
TV

- Genuine 5 silicon transistor circuit, does not need a transistor radio to operate.
- Incorporates unique varicap tuning for extra stability.
- Search head fitted with Faraday screen to eliminate capacitive effects.
- Loudspeaker or earphone operation. (both supplied).
- Britain's best selling metal locator kit, 4,000 already sold.
- Kit can be built in two hours using only soldering iron, screwdriver, pliers and side-cutters.
- Excellent sensitivity and stability.
- Kit absolutely complete including drilled, tinned, fibreglass p.c. board with components sited printed on.
- Complete after sales service.
- Weighs only 22oz; handle knocks down to 17" for transport.

Send stamped, self-addressed envelope for literature.


Complete kit with pre-built search coil **£14.75**
Plus £1.00 P&P
Plus £1.18 VAT (8%)

Built, tested and Guaranteed **£19.75**
Plus £1.00 P&P
Plus £1.58 VAT (8%)

MINIKITS ELECTRONICS,
6d Cleveland Road, South Woodford,
LONDON E18 2AN
(Mail order only)

Wilmslow Audio

THE firm
for
speakers!

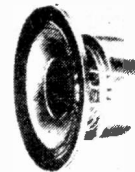

Baker Group 25, 3, 8, or 15 ohm	£9.00
Baker Group 35, 3, 8 or 15 ohm	£10.75
Baker Deluxe, 8 or 15 ohm	£12.38
Baker Major, 3, 8 or 15 ohm	£10.69
Baker Regent, 8 or 15 ohm	£9.00
Baker Superb, 8 or 15 ohm	£16.31
Celestion MH 1000 horn, 8 or 15 ohm	£13.50
Coles 400 1 G super tweeter	£5.90
Coles 400 1 K super tweeter	£5.90
EMI 14" x 9" bass 14A/700 8 ohm	£11.92
EMI 8 x 5, 10 watt, d/c, roll/s 8 ohm	£3.75
Elac 59RM 109 15 ohm, 59RM 114 8 ohm	£3.38
Elac 6½" d/c roll/s 8 ohm	£3.95
Elac 10" 10RM 239 8 ohm	£3.95
Fane Pop 15 watt 12"	£5.50
Fane Pop 55, 12" 60 watt	£16.75
Fane Pop 60 watt, 15"	£19.95
Fane Pop 70 watt 15"	£21.75
Fane Pop 100 watt, 18"	£33.95
Fane Crescendo 12A or 8, 8 or 15 ohm	£42.95
Fane Crescendo 15, 8 or 15 ohm	£54.95
Fane Crescendo 18, 8 or 15 ohm	£75.95
Fane 801T 8" d/c roll/s 8 ohm	£8.96
Goodmans 8P 8 or 15 ohm	£6.50
Goodmans 10P 8 or 15 ohm	£6.45
Goodmans 12P 8 or 15 ohm	£16.50
Goodmans 12P-D 8 or 15 ohm	£18.75
Goodmans 12P-G 8 or 15 ohm	£17.75
Goodmans Audiom 200 8 ohm	£14.95
Goodmans Axent 100 8 ohm	£8.50
Goodmans Axim 402 8 or 15 ohm	£22.00
Goodmans Twinaxiom 8" 8 or 15 ohm	£10.60
Goodmans Twinaxiom 10" 8 or 15 ohm	£10.95
Kef T27	£5.18
Kef T15	£10.75
Kef B110	£6.75
Kef B200	£7.85
Kef B139	£16.50
Kef DN8	£2.08
Kef DN12	£5.39
Kef DN13	£4.05
Baker Major Module, each	£13.28
Goodmans Mezzo Twinkit, pair	£51.95
Goodmans DIN 20, 4 ohm, each	£15.75
Helme XLK30, pair	£21.95
Helme XLK35, pair	£26.75
Helme XLK40, pair	£38.50
Kefkit I, pair	£51.00
Kefkit III, each	£46.00
Peerless 20-50, pair	£39.50
Peerless 20-60, pair	£53.00
Richard Allan Twinkit, each	£13.95
Richard Allan Triple 8, each	£20.75
Richard Allan Triple 12, each	£25.95
Richard Allan Super Triple, each	£29.50
Richard Allan CG8T 8" d/c roll/s	£7.95
Wharfedale Linton 2 kit, pair	£21.50
Wharfedale Glendale 3 XP kit, pair	£47.50
Wharfedale Dovedale 3 kit, pair	£59.40
Wharfedale Super 10RS/DD	£13.50
Castle Super 8 RS/DD	£9.28
Jordan Watts Module 4, 8 or 15 ohm	£15.36
Tannoy 10" Monitor HPD	£78.00
Tannoy 12" Monitor HPD	£86.00
Tannoy 15" Monitor HPD	£99.95

Prices correct at 5.10.76

ALL PRICES INCLUDE VAT

Cabinets, wadding, Vynair, crossovers etc

Send stamp for free 38 page booklet "Choosing a Speaker"

FREE with all orders over £10 — "HiFi Loudspeaker Enclosures" Book

All units are guaranteed new and perfect

Prompt despatch

Carriage Speakers up to 12" 60p, 12" £1, 15" £1.75, 18" £2.50. Kits £1 each (£2 per pair) Tweeters and Crossovers 33p each

WILMSLOW AUDIO

Dept. ETI

Swan Works, Bank Square, Wilmslow,
Cheshire SK9 1HF. Tel. Wilmslow 29599
(Discount HiFi, PA and Radio at 10 Swan
Street, Wilmslow)

Access and Barclay Card orders accepted by phone

Learn to understand electronics for your hobbies

1. Lerna-Kit course

Step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered.

- (1) BUILD AN OSCILLOSCOPE.
- (2) READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS.
- (3) CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK.

2. Become a Radio-Amateur

Learn how to become a radio-amateur in contact with the wide world. We give skilled preparation for the G.P.O. licence.

FREE!

Brochure, without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
 P.O. BOX 156, JERSEY, CHANNEL ISLANDS.

NAME _____

ADDRESS _____

BLOCK CAPS PLEASE ETA 126

BE AN ETI GUY (OR GAL)



A couple of issues ago we announced the ETI T-Shirt—the response has been enormous. Initially we just wanted to sell the surplus but we've had to reorder twice! Made in cotton (yellow with black printing) these are available in three sizes suitable for both sexes. Send your cheque and P.O. for £1.50 (payable to Electronics Today International) and state Small, Medium or Large. **ETI T-SHIRTS.**

25-27 OXFORD STREET, LONDON W1R 2NT

ALL PAYMENTS MUST BE IN STERLING

ETI PCB's

TITLE	PROJECT NO.	BOARD NO.	TOTAL	TITLE	PROJECT NO.	BOARD NO.	TOTAL
Int. 25W Stereo Amp.	Int. 25	Int. 25	£3.80	Musical Synthesiser	601	601A	£2.30
Dual Power Supply	106	014	£1.48			601B	£1.48
Wide Range Voltmeter	107	022	£1.09			601C	£1.48
L.C. Power Supply	111	111	£1.43			601E	£3.38
Thermocouple Meter	113	113	£1.57			601F	£1.11
Dual Beam Adaptor	114	114	£1.00			601G	£1.58
Impedance Meter	116	116	£1.01			601H	£2.14
Digital Voltmeter	117	117A	68p			601J	£2.30
						601L	97p
Simple Frae. Counter	118	117B	68p			601M	89p
The Repeater	213	213	68p			601N	£2.75
Brake Light Warning	303	007	68p			601P	£1.40
Auto. Car Theft Alarm	305	019	99p			601R	£1.51
Inf. Battery Charger	309	309	96p	Radar Int. Alarm	702	702	£1.13
Tacho Timing Light	311	311	80p	Int. F.M. Tuner	751	751	£2.49
Elect. Ign. CDK/Tacho	312	312	£1.72	Light Dimmer			58p
Car Alarm	313	313	67p	Print Timer			58p
Auto Amp.	314	314	69p	Inter Com.			58p
Four Input Mixer	401	005A	67p	Intruder Alarm			£1.94
Super Stereo	410	025	£1.37	Digital Alarm Clock		5017	£1.24
100W Guitar Amp.	413	413	£1.73	Ultraboard			£1.68
Master Mixer	414	414A	£1.14	Bicycle Speedometer			68p
		414B	£1.52				
		414C	£1.52				
		414D	£1.89				
Stage Mixer	414	414E	£1.78	NEW BOARDS			
The Over L.E.O.	417	417	68p	Logic Probe	120	120	£1.01
Mixer Pre-Amp.	419	419	83p	Logic Pulsar	121	121	£1.01
Int. 420 Four C./Amp.	420	420A	70p	Logic Tester	122	122	£2.05
		420B	87p	Onos Tester	123	123A	96p
		420C	87p			124	£1.19
		420D	£1.10	Tone Burst Generator	124	124	£1.97
Discrete SQ Decoder	420E	420E	£1.10	Audio Mini Voltmeter	128	128	£1.00
422 Stereo Amp. 50W	422	422	£2.69	Temperature Meter	130	130	£1.18
Plus 2 Add on Decoder	423	423	83p	Active Crossover	433	433A	£1.18
Spr. Reverb. Unit	424	424	£1.82	Gen. Purpose			
Stereo Rumble Filter	426	426	70p	Power Supply	131	131	£1.19
Graphic Equaliser	427	427	£1.79	Audio Level Meter	438	438	£1.08
Colour Organ	428	428	£2.10	Audio Expander			
Simple Stereo Amp.	429	429	70p	Compressor	443	443	£3.94
Line Amp.	430	430	70p	Sweet 16	457	457	£2.16
Fluorescent Lamp				Calculator Stop Watch	534	534	£1.00
Dimmer	508	011	76p	Audio Noise Generator	441	441	£1.00
Page Slide	512	023	76p	Touch Switch	539	539	£1.00
Photographic Timer				Marker Generator	706	706	£1.40
Synchroniser	513	026	76p	Crossover Amp.		1553B	£2.30
Digital Stop Watch	520	520A	£2.05	Low DR. Thermostat		951	89p
		520B	40p	Exposure Meter		119	£2.15
Low Cost Laser	524	524	£1.30	Switching Regulator		551	£2.57
Push Button Dimmer	527	527	96p	Digital Stopwatch		5510	£1.01
Elec. One Arm Bandit	529	529A	£2.37			552	£2.02
		529B	£2.32	Guitar Attack			£1.04
Temp. Controller	530	530	85p	Base Booster		018	£2.45
Photo Timer	532	532	87p	Optical Communications			£2.94
Digital Display	533	533A	68p	(both PCB's)			
		533B	68p				

Orders of less than £5.00 Postal Orders only. Delivery time approximately 3 weeks. Large quantity orders — discount by negotiation. All P.C.B.'s prices include P&P and VAT. Majority of orders despatched within a week.

CROFTON ELECTRONICS LTD.

35 Grosvenor Road, Twickenham, Middlesex Tel. 01-891 1923


Now there's a better way to keep your ETI copies



We reckon ETI is worth keeping: and our surveys indicate that a staggering 97% of readers keep their copies for at least three months. Now we can offer you a binder which holds 12 issues whose quality befits the magazine: excellent. Send £2.50 (which includes VAT and postage) to:

25-27 OXFORD STREET, LONDON W1R 2NT

complete DIGITAL CLOCK KITS TEAK CASES

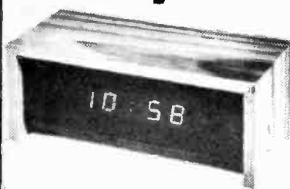

NON ALARM **£10.65** + £0.85 VAT

ALARM **£13.43** + £1.07 VAT

"DELTA"

GENUINE TEAK OR PERSPEX CASE

DELTA DATA: 4 Radiant Red 1/2 inch high LEDs. 12 hr display with AM/PM indication. Beautiful Burma Teak Case or Pretty Perspex in White, Black, Blue, Red, Green. Power failure is indicated by flashing display.

MODULES: Kits can be bought without case Non Alarm £9.00, Alarm £12.50 incl.

READY BUILT: Buy a working tested module and fit your own case. Non Alarm £9.50. Alarm £13.00. Or put it with our case parts @ £4.32 and save on complete clock price. Complete Clock ready built. 2 yr. guarantee Non Alarm £13.50, Alarm £16.50

ALARM FEATURES: Pulsed tone. Tilt operated 10 minute 'Snooze' period. Single switch setting. Optional extra mercury switch (45p) allows Alarm reset by tilting clock. Digit brightness is automatically controlled to suit lighting level.

"ALPHA" CHRISTMAS OFFER 4 Glowing Green 1/2" High Digits 12 or 24 hr. Non Alarm Built & Tested Module - Plus Perspex Case **£11.00** incl

NOVUS CALCULATORS: 650 **£5.40** 4510 **£16.20**
850 **£6.75** 6030 **£21.60**

Send payment with order. S.a.e. for complete range of clocks, calculators & components



PULSE ELECTRONICS LTD.

DEPT. E3, 202 SHEFFORD ROAD
CLIFTON, SHEFFORD, BEDS.
Telephone: Hitchin (0462) 814477

Greenbank Electronics



TIME BOX Digital Clock Case. 56 x 131 x 71.5 mm with red acrylic window. Choice of case colour, white, red, orange, blue. £1.75

DIGITAL CLOCK MODULES, KITS

Further details free on request
"E" LED DISPLAYS. Class II devices, but fully guaranteed by us, for even segment brilliance, etc. — money back or exchange if not satisfied

DL-704E 0.3in	70p
DL-707E 0.3in	70p
DL-728E 2 x 0.5in	£1.80
DL-727E 2 x 0.5in	£1.80
DL-750E 0.6in	£1.50
DL-747E 0.6in	£1.50

CLOCK CHIPS

AY-5-1224A **£3.50**
MK 50253 **£5.50**

OP-AMPS

CA 3130 (COS/MOS) **£1.00**
CA 3140 (BI MOS) **95p**
741 Minidip **25p**

SOLDERCON PINS

100 **60p**
1000 **£4.00**
2500 **£8.75**

DIL SOCKETS

8/14/16 pin **15p**

CATALOGUE Free on request

VEROBOARD 0 1" Pitch with cop- per strips 2 1/2" x 1" (pack of 5) 54p 2 1/2" x 3/4" 36p 2 1/2" x 5" 44p 2 1/2" x 17" £1.35 3 1/4" x 3 1/4" 44p 3 1/4" x 5" 49p 3 1/4" x 17" £1.73	4.7" x 17.9" £2.23 0 1" Plain Board (no strips) 25p 3 1/4" x 2 1/2" 40p 3 1/4" x 17.9" £1.12	3 2768 MHz, all same price £3.75
--	--	--

DIODES	5p	TRANSISTORS	85p
IN 4002	5p	TIP 2955	60p
IN 4004	6p	TIP 3055	60p
IN 4007	7p	TIMER IC	45p
IN 4148	5p	NE 555	45p
QUARTZ CRYSTALS		LEDs (Red only)	
100kHz, 1 000 MHz	Special Offer: 100	0 11" dia.	15p
2 097152 MHz	Diodes Half Price.	0.2" dia.	15p

CMOS WITH DISCOUNTS! Any mix		14163	1.18	14516	1.51	14558	1.25
10% for 25+	25% for 100+	14174	1.08	14517	4.02	14559	4.10
4000 0.20	4028 1.00	4053 1.04	4086 0.80	14175 1.04	14518 1.39	14560 2.17	
4001 0.20	4029 1.27	4054 1.29	4089 1.74	14194 1.17	14519 0.57	14561 0.70	
4002 0.20	4030 0.60	4055 1.46	4093 0.89	14410 5.70	14520 1.39	14562 5.59	
4006 1.31	4031 2.46	4056 1.46	4094 2.08	14411 9.54	14521 2.77	14566 1.67	
4007 0.20	4032 1.19	4057 29.81	4095 1.16	14412 17.07	14522 2.15	14568 3.15	
4008 1.07	4033 1.55	4059 6.20	4096 1.16	14415 7.35	14526 2.15	14569 3.72	
4009 0.60	4034 2.11	4060 1.24	4097 4.13	14419 2.67	14527 1.76	14572 0.27	
4010 0.60	4035 1.31	4061 25.60	4098 1.22	14422 4.98	14528 1.22	14580 8.35	
4011 0.20	4036 3.09	4062 10.10	4099 2.03	14435 7.93	14529 1.72	14581 4.30	
4012 0.20	4037 1.06	4063 1.22	40101 1.76	14440 11.58	14530 0.95	14582 1.64	
4013 0.60	4038 1.20	4066 0.69	40102 2.16	14450 2.67	14531 1.74	14583 0.84	
4014 1.12	4039 3.09	4067 4.13	40103 2.16	14451 2.67	14532 1.39	14585 1.10	
4015 1.12	4040 1.19	4068 0.24	40104 2.26	14490 6.51	14534 8.15	14586 0.25	
4016 0.60	4041 0.93	4069 0.24	40107 0.66	14501 0.20	14536 4.00	14587 0.25	
4017 1.12	4042 0.93	4070 0.65	40108 6.18	14502 1.38	14537 13.17	14588 0.25	
4018 1.12	4043 1.12	4071 0.24	40109 2.21	14503 0.75	14539 1.24	14589 0.25	
4019 0.60	4044 1.04	4072 0.24	40181 4.30	14505 4.38	14541 1.62	14590 0.25	
4020 1.24	4045 1.56	4073 0.24	40182 1.73	14506 0.57	14543 1.82	14591 0.25	
4021 1.12	4046 1.48	4075 0.24	40194 2.26	14507 0.60	14549 4.10	14592 0.25	
4022 1.07	4047 1.01	4076 1.71	40257 2.26	14508 3.08	14552 10.50	14593 0.25	
4023 0.20	4048 0.60	4077 0.65	4700 1.75	14510 1.51	14553 4.86	14594 1.84	
4024 0.87	4049 0.60	4078 0.24	7083 4.25	14511 1.74	14554 1.67	14595 2.26	
4025 0.20	4050 0.60	4081 0.24	14160 1.18	14512 1.03	14555 1.01	14596 0.67	
4026 1.92	4051 1.04	4082 0.24	14161 1.18	14514 3.47	14556 1.01	14597 0.60	
4027 0.60	4052 1.04	4085 0.80	14162 1.18	14515 3.47	14557 4.65	14598 0.86	

Terms: C.W.O. Add VAT to all prices at 8%. Post etc. UK 25p (+ 2p = 27p) per order. export £ 2.00 (no VAT). All orders processed on day of receipt.

GREENBANK ELECTRONICS (Dept. T12E)
94 New Chester Road, New Ferry, Wirral, Merseyside L62 5AG,
England. Tel. 051-645 3391

NOVEMBER ISSUE
INCLUDES

RADIO & ELECTRONICS CONSTRUCTOR


**FREE WALL CHART
DESIGN DATA TABLES
SAVE TIRESOME CALCULATIONS**

WITH THESE TABLES Design Data Tables 2 contain the following tables — MILLIMETRE-INCH CONVERSION, PHASE SHIFT OSCILLATOR C-R VALUES, 2πf VALUES, AUDIO OUTPUT POWERS, PARALLEL-R SERIES-C VALUES, E-R DISSIPATION, INCH-MILLIMETRE CONVERSION.

Full notes given on how to make full use of the tables to obtain the maximum benefit.

T.T.L. CALIBRATION GENERATOR

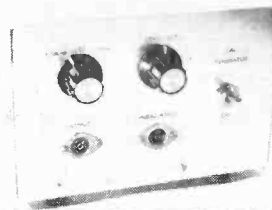This unusual design employs an LC oscillator which is set to correct frequency by zero-beating with the long wave Radio 2 transmission on 200kHz. Another novel feature is the use of a t.t.i. decade counter to obtain division by 2 and by 10 of the oscillator frequency.



ON SALE NOW

PRICE 35p

MINI-ADS & CLASSIFIED

THIS SECTION IS A PRE-PAYMENT SERVICE ONLY

MINIADS: 3 1/4" x 2 1/8" (1-3) £22 (4-11) £20 (12 or more) £19 per insertion. CLASSIFIED DISPLAY: £3 per single column centimetre SEMI-DISPLAY: £2.30 per single column centimetre. LINEAGE: 65p per line average six words, minimum 3 lines. BOX NO: allow 50p extra
Contact BOB EVANS, (01-434 1781/2) 25-27 Oxford Street, London W1R 2NT.

M.A. 1001B DIGITAL CLOCK

MODULE SIZE 3.0" x 1.75"
C/W 15v + 4 5.0-4 5v TRANSFORMER Requires only switches and case DATA SUPPLIED
OUR PRICE ONLY £9.74

Features Bright 0.5" Display 12 hr Format with 24 hr alarm capability Flashing Colon. Power Failure Indication, P.M. Indicator, Alarm Set Indicator, Hrs and Mins., or Mins and Secs Display Output Drives from Alarm and Sleep Timers, 9 Min Snooze Timer and 59 Min Sleep Timer

All Items Ex Stock

CAR, BOAT OR CARAVAN CLOCK MODULE

M.A 1001B Includes all features listed above plus Data for Conversion to 12v D.C. plus Crystal Time Base for accuracy to a few secs. per month.

OUR PRICE ONLY £13.88

If required with Transformer £14.74

CRYSTAL TIME BASE SUITABLE FOR C.MOS DIGITAL CLOCKS. (Built and Tested.) Size approx. 1" x 1.5" x 0.5". Can be adjusted to ± a few seconds/month

OUR PRICE ONLY £5.25
ALL PRICES INCLUDE VAT AND POST & PACKING

Terms Cash with Order - Mail Order Only

ORDERS TO: F.E.K. SUPPLIES
18 STARRING LANE
LITTLEBOROUGH, LANCS.

LED S		0.125	0.2	INFRA RED				
RED	15p	19p		550µw				
G/Y	27p	33p		Axial lead 49p				
OR	27p	33p		6mW £1.55				
				OPTO Data free				
				ORP 12 55p				
OPTO-ISOLATORS		SCR a	50V	100V	400V	Diac		
TIL111	1.5KV	50kHz	£1	T05 1A	25p	27p	40p	BR100
4350	2.5KV	5MHz	£2.25	T066 3A	27p	35p	50p	21p
AVDEL BOND 2gm.		65p	400V	TRIACS 2A	60p	10A	£1.50	
AC126/6/7/8	15p	2N3053	15p	VOLTAGE REGS				
AD161/162	40p	2N3054	45p	5V 7805 Plastic				
AF117	20p	2N3065	41p	12V 7812 1 Amp				
AF124/5/6/7	34p	2N3702/3/4	12p	15V 7815 all				
BC107/8/9	9p	2N3903/4/5/6	61p	18V 7818 £1.50				
BC109C	12p	2N2846	35p	723 DIP14	50p			
BC147/8/9	10p	TIS430UT	25p	BRIDGE RECTS.				
BC157/8/9	11p	MPF102	40p	2A 50V	30p			
BC167/8/9	11p	2N3819	25p	2A 100V	36p			
BC169C	12p	2N3823	30p	2A 200V	41p			
BC177/8/9	17p			2A 400V	46p			
BC182/3/4L	11p	IN4148	4p	ZENERS 2.7-33V				
BC186/7	30p	IN4001	5p	BZ98 or sim	9p			
BC212/3/4L	12p	IN4002/3	6p					
BC70/71/72	13p	IN4004/5	7p	555 Timer	80p			
BF194/5	12p	IN4006/7	8p	556 2x555	£1.10			
BF196/7	14p	IN4148	4p	LM380	£1.00			
BFY50/51	15p	BA100	9p	7400	16p			
BFY29	30p	BY127	16p	D.I.L. SOCKETS				
BFX84	24p	OA47	7p	8-pin	12p			
BSX19/20	16p	OA70 OA79	9p	14-pin	13p			
OC71	10p	OA91 OA95	6p	16-pin	14p			
2N1711	20p	OA91 OA95	7p	Mica + bushes				
2N206	10p	OA200	6p	TO3 TO58	5p			
2N1711	20p	OA202	7p	Dial Pen	70p			
2N2219	20p	OP. AMPS						
2N2904/5/6/7/8	16p	709 all	25p					
2N2904/5/6A	18p	741 8-pin	29p					
2N2926(R)	7p	748 D.I.L.	36p					
2N2926(G)	12p							
PRICES INCLUSIVE + 15p P&P (1st class)								
ISLAND DEVICES, P.D. Box 11, Margate, Kent								

P.C.B.s

Glass Fibre P.C.B.s for ETI projects, supplied tinned and drilled.

ETI 252	.38	ETI 152 a	£1.74	
ETI 241	1.14	b	.71p	
ETI 710	1.46	ETI 540 a	£1.91	
ETI 560 a	} 4.24	b	} .54p	
b		ETI 445		.54p
c		ETI 541		.68p
ETI 514	.52	ETI 543a	.81	
ETI 251	.56	b	.84p	

All prices shown include VAT. Add 20p post & packing

P.C.B.s also available for this month's ETI projects. Send SAE for full list of available boards.

Also a comprehensive or part service from Artwork and layout design to assembled P.C.B. for batch quantities or one-off prototypes - Contact:

TAMTRONIK LIMITED
217 TOLL END ROAD, TIPTON,
WEST MIDLANDS DY4 0HW
Telephone 021-557 9144

TRANSISTORS + ICs

AC127	16p	LM301A T099	52p
AC28	15p	LM709 T099	41p
AD161	44p	LM710 1401L	49p
AD162	44p	LM748 14 01l	82p
BC107/8	11p	7400 TTL	16p
BC109	12p	7401	16p
BC182/182	12p	7402	16p
BC183/183L	12p	7404	19p
BC184/184L	13p	7410	16p
BFY50	21p	7413	35p
BFY51	20p	7420	16p
BFY52	20p	7430	16p
80131	43p	7440	16p
80132	44p	7441	85p
8RY39	48p	7447	95p
TIP29A	48p	7474	36p
TIP32A	52p	7475	50p
2N1711	25p	7490	45p
2N3053	25p	74121	37p
2N3054	67p	74141	85p
2N3055	55p	C1060 SCR	70p
2N3702	12p	S-DEC	
QC44	22p	Breadboard	£2.15
QC45	22p	T-DEC	
OC71	22p	Breadboard	£3.93
741 Op. Amp	29p		

Prices VAT inclusive + 20p P&P
1 500 types of Diodes, Transistors + ICs, SCRs, Triacs in stock plus Full range of passive components
List 10p + SAE

AITKEN BROS. & CO.

35 HIGH BRIDGE NEWCASTLE-ON-TYNE NE1 1EW
Your Electronic Component Centre for North East
Callers welcome

FIBRE-GLASS P.C.B.s

ETI 560 VDU (Corrected) Set of 3 Boards	445p
ETI 458 100 watt Stereo Disco	850p
(Set of 8 Boards A, B, C, D, E, F & H)	
ETI 458 Remote Start Board	70p
ETI 458 Light Modulator Board	300p
ETI 543A STD Timer Display Board	85p
ETI 543B Timing Display Board	85p
ETI 544 See this issue	75p
ETI 620 Touch Organ (SRBP)	500p

ALL OTHER PREVIOUSLY ADVERTISED
BOARDS STILL AVAILABLE

SEMI-CONDUCTORS

BC107	8p	8D519	50p
BC107A	9p	8D520	50p
BC108	8p	8D609 (90 watts)	70p
BC109	8p	UC734E	20p
BC114	15p	ZTX109	10p
BC116	17p	2N5457 (FET)	35p
BC478	25p	2N6259 (200 watts)	80p
BCY32	30p	D1300A Signal Diode	5p
400mW Zeners	9p	1 8W. W. 2C2012 (12v)	20p

RESISTORS

1/4 watt H S Carbon Film	1p	100	80p
1/2 watt H S Carbon Film	1.5p	100	120p

ELECTROLYTICS

470mF 63v	30p	4700mF 50v 60p	640mF 16v	14p	
500mF 10v	10p	220 uF 10v	8p	100mF 10v	6p
10mF 12v	5p	330mF 25v	10p	100mF 25v	8p

SCOOP - LIMITED OFFER UNTIL DEC 31 OR STOCKS EXHAUSTED

CA3052 Stereo Pre-Amplifier I.C. 16-pin D.I.L. 100p

All Data supplied. Provision for Equalisation and Tone

Prices VAT inclusive List 10 P&P 20p

R.F. EQUIPMENT SPARES LTD.
3 LACY CLOSE, WIMBORNE, DORSET

FREE TV CIRCUIT DIAGRAMS

All main British TV sets (plus many foreign) comprehensively covered in our easy-to-follow TV Repair Manuals - 4 mono and 3 colour.
Just send Model No., if colour (mfrs. chassis type helps) with £4.50 and receive the manual covering your set - plus your set's circuit diagram on request free. Set of 7 only £27.50.

British TV Circuit Diagram Manuals - the main mono (over 37 series) for £9.90 and virtually every colour for £17.50.

Full details of these and other publications from:

T.V. TECHNIC (ETI)

76 Church Street, Larkhall, Lanarks, ML9 1HE
Tel. (0698) 883334

300W TOUCHSWITCH KITS

TS300K Contains Triac, IC, Diodes, Resistors, Frontplate, PCB, etc. Replaces conventional lightswitch with NO REWIRING. TOUCH one insulated plate for ON, another for OFF. Complete with instructions.

ONLY £3.67.

ALSO TSA300K AUTOMATIC, as above, but with only ONE TOUCHPLATE TOUCH for ON and light stays on for a preset time. Ideal for stairs and hall. Complete with instructions. ONLY £3.67.

300W LIGHTDIMMER KIT replaces conventional lightswitch £2.45.

SPECIAL OFFER

10 ROCKER SWITCHES, white SPST
10A/250V snap fixing. £1.20.

CMOS Motorola	Case	TRIACS 400V T0220	Case	BC148	9p
4002	20p	16 5A isolated tab	80p	BC158	11p
4013	67p	110A (TAG250)	95p	2N3055	36p
4050	57p		(3+90p)	2N6027	
4501	20p	Isolating Kit	5p	PJT	30p
4000	20p	Diac	20p	1N4004	6p
4001	20p	NE555 8 pin DIL	44p	1N4148	4p
4007	20p	741 8 pin DIL	24p		
4011	20p	RESISTORS (W 5 F12 72):		10MΩ	
4015	105p	Multiset		2p	
4016	57p	LDR (1" dia 400λ to 1 Mλ) light to dark		45p	
4017	105p	NON wire ended		7p	
4040	105p	Choke 1/2 Amp		20p	
4049	57p	Ferrite Rod 1 1/4" x 1/4" diameter		12p	
4510	135p	Pocket Switch white SPST 10A 250V		15p	
4516	135p	MINI MAINS TRANSFORMERS 100mA		85p	
4566	155p	6 0 6V		85p	
		12 0 12V		95p	

ADD 8% VAT (+12 1/2%) PLUS 20p P&P.
Mail Order Only to

T.K. ELECTRONICS (ETI)

106 Studley Grange Road, London W7 2LX

GLASS FIBRE P.C.B.s

From your own tape, film or ink master
Send SAE for quotation

GP Power Supply ETI 131		ETI boards glass fibre tinned and drilled	
High Power Beacon ETI 240			88p
100 Guitar Amplifier ETI 413			52p
Mixer Pre Amplifier ETI 419			£1.40
Audio Level Meter ETI 438			80p
Sweet Sixteen Amplifier ETI 457			75p
Power Supply 100w Disco Amplifier ETI 458a			£1.92
100w Disco Amplifier ETI 458b			82p
Disco FET Ceramic P.U. ETI 458c			£1.19
Disco Tone Control Pre Amplifier ETI 458d			55p
Disco Pre Amplifier ETI 458e			85p
Disco Headphone Amp/VU Meter ETI 458f/g			£1.14
Disco Fader ETI 458h			£2.10
Sound Light Flash Trigger ETI 514b			34p
2m Power Amplifier ETI 710			49p
			85p

PROTO DESIGN, 4 Highcliffe Way, Wickford, Essex SS11 8LA

Carbon Film Resistors 5% E12 Series 1/8W, 1/4W, 1/2W. Mixed to your choice, 100 for 90p. Electrolytics 50/15v 7p. MICRO-PROCESSORS SC/MP £18. MM6800 £33. P&P 15p. CANDAR, Freepost, Reading RG1 1BR.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO., P.O. Box 5, Frome, Somerset. Immediate settlement.

PRECISION POLYCARBONATE CAPACITORS

440V AC

All High Stability — Extremely Low Leakage

RANGE: DIMENSIONS

VALUE (µF)	L (mm)	D (mm)	EACH	MIN	1K	Range	1%	2%	5%
0.1µF	27	12.7	68p	0.47µF			£1.32	77p	31p
0.22µF	33	16	86p	1.0µF			£1.56	91p	60p
0.25µF	33	16	92p	2.2µF			£1.98	£1.32	75p
0.47µF	33	19	£1.10	4.7µF			£2.82	£1.88	£1.23
0.5µF	33	19	£1.16	6.8µF			£3.48	£2.32	£1.47
0.68µF	50.8	19	£1.25	10µF			£4.98	£3.32	£2.17
1.0µF	50.8	19	£1.37	15µF			£7.14	£4.76	£2.88
2.0µF	50.8	25.4	£1.95	22µF			£9.66	£6.44	£3.90

TANTALUM BLAD CAPACITORS — Values available 0.1, 0.22, 0.47, 1.0, 2.2, 4.8, 6µF at 15V, 25V or 35V, 10µF at 16V, 20V or 25V, 22µF at 6V or 16V, 33µF at 6V or 10V, 47.0µF at 3V or 6V, 100.0µF at 3V. ALL at 12p each, 10 for £1.10, 30 for £5.00, 100 for £9.00.

TRANSISTOR & IC'S	BC267	12p	OC44	OC45	20p
AC128	14p	BC269A	12p	OC71	72
AC176	16p	BC547	558A	12p	2N2924G
AD149	40p	BCY72	15p	2N2926Y	41p
AF174	40p	BD131	132	39p	2N2926O
AF239	35p	BF115	167	22p	2N3054
BC107 8 9	9p	BF173	24p	2N3055	30p
BC114	12p	BF178	26p	2N3702	
BC147 8 9	10p	BF184	22p	3704	11p
BC153	16p	BF194	195	12p	TIP30A
BC157 8 9	12p	BF196	197	13p	TIP31A
BC177	18p	BF200	27p	TIP32A	64p
BC182 1821	11p	BF262	263	60p	TIP305A
BC183 183L	11p	BFY50	51 52	20p	MPU131
BC184 184L	12p	BFX84	86 88	20p	NE555
BC212 212L	12p	BFX85	23p	741 8 pin	32p
BC213 213L	11p	3R101	41p	ZN414	£1.15
BC214 214L	11p	GL1872	23p	SN76013ND	£1.30

POPULAR DIODES — 1N914 6p, 8 for 45p, 18 for 90p; 1N916 8p, 6 for 45p, 14 for 90p; 1N34 3p, 11 for 50p, 26 for £1.00; 1N4148 5p, 6 for 27p, 12 for 48p; 1N4001 5p, 002 6p, 003 6p, 004 7p, 006 8p, 007 8p, 008 8p.

LOW PRICE ZENER DIODES — 400mW, Tol. ±5% at 5mA. Values available 3V, 3.3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 13.5V, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V. All at 7p each, 5 for 33p; 10 for 65p. SPECIAL OFFER 100 Zeners for £6.00.

RESISTORS — High stability, low noise carbon film 5% 1/4W at 40°C, 3/4W at 70°C. E12 series only — from 2.2Ω to 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value.

SPECIAL PACK, 10 of each value 2.2Ω to 2.2MΩ (730 resistors) £5.

SILICON PLASTIC RECTIFIERS — 1.5 amp, brand new wire ended D027, 100 P.I.V. 7p (4 for 26p), 400 P.I.V. 8p (4 for 30p).

BRIDGE RECTIFIERS — 2 1/2 amp, 200V 40p, 350V 45p, 600V 55p.

SUBMINIATURE VERTICAL PRESETS — 0.1W only. ALL at 3p each, 50p, 100p, 220p, 470p, 680p, 1kΩ, 2.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 68kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, 2.5MΩ, 5MΩ.

PLEASE ADD 20p POST AND PACKING ON ALL ORDERS. ALL EXPORT ORDERS PLEASE ADD COST OF SEA/AIR MAIL.

PLEASE ADD 8% VAT to all items except those marked with which are 12.5%.

Send S.A.L. for lists of additional ex-stock items. Wholesale price lists available to bona fide companies.

MARCO TRADING

(Dept. P3)

The Old School, Edlaston, Wem, Shropshire

Tel. Whixall (Shropshire) (Std. 094872) 464/5

(Proprs. Mincost Trading Ltd.)

Treasure Locator Kits by

DETECTOR PRODUCTS

Suppliers to the UK & Abroad

Circuits & Instructions £2
Complete Kit £12

Total £14 incl. VAT p&p

Solid aluminium frame with an efficient Faraday screen. For enquiries please send s.a.e. to:

DETECTOR PRODUCTS

58a King Street, Blackburn, Lancs
Tel. 62561 or 54105

Half completed 4600 Synthesiser, 95% of components. Oscilloscope. Lots of other bits, mags., £145 o.n.o. Des, 01-278 1723.

SHOP FROM HOME with our catalogue. Fully illustrated and covering over 3,000 components, audio and disco accessories, tools and test meters. Reviewed as one of the best catalogues available. Send 30p now for your copy (issue No 5). Access, Giro, Barclaycard, Government and educational orders accepted. (Giro No 331-7056).

B. H. COMPONENT FACTORS LTD.
Leighton Electronics Centre

59 North St., Leighton Buzzard, Beds
Tel: 2316 (0286) Shop hours: 9-12.30, 1.30-5 p.m. Closed Wednesday

PRINTED CIRCUITS and HARDWARE

Comprehensive range Constructors' Hardware and accessories.
Sheet aluminium cut to size.
Aluminium lightweight sections.
Selected range of popular components.
Full range of ETI printed circuit boards, normally ex-stock, same day despatch at competitive prices.

P.C. Boards to individual designs.
Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required).

Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES
MASONS ROAD
STRAFORD-ON-AVON
WARWICKS. Tel. 4879

OVER 2,000 ELECTRONIC COMPONENTS IN A

BIG NEW FREE



100 PAGE CATALOGUE

TANDY

Nationwide supermarket of sound!

Please send me the 100 page Tandy catalogue

Name _____

Address _____

Tandy Corporation (Branch UK), Bilston Road, Wednesbury, W Midlands, WS10 7JN (ET/2)

PLEASE PRINT CLEARLY

VALVES

Radio-TV Industrial Transmitting 2200 Types. 1930 to 1975, many obsolete. List 20p. S.A.E. for quotation. Postal export service. We wish to purchase all types of new and boxed valves. Wholesaler's Dealer's, etc., stocks purchased.

COX RADIO (SUSSEX) LTD., The Parade, East Wittering, Sussex, West Wittering 2923

DRILLED AND TINNED PCBs FOR ETI PROJECTS

ETI 114	89p	ETI 422	£3.00	ETI 560a	
ETI 117a	35p	ETI 438	75p	ETI 560b	£5.00
ETI 117b	35p	ETI 441	41p	ETI 560c	
ETI 131	94p	ETI 443	£3.00	ETI 702	95p
ETI 241	85p	ETI 5148	40p	ETI 710	82p
ETI 252	40p	ETI 533a	42p	ETI 706	50p
		ETI 533b	35p	ETI 951	35p

Send for a full list of over 70 ETI boards
COMPONENTS Resistors 1/4W 5% (e12) 1 2p
Capacitors ceramic plate 27p-0.047uf 3 5p each
tantalum bead 0.1uf-6.8uf 35v 15p each
Diodes 1N4001 5p, 1N4002 5p, 1N4003 7p
1N4004 8p, 1N914 5p
Zeners 400mW 2.7-33v 12p each
BC107, 8, 9 12p, BC177 8, 9 20p, BC147 8 9 11p
DIL sockets, 8w 12p, 14w 16p 16w 17p, 24w 70p
LEDs 0.125" red 15p, Green 25p, Yellow 25p, Clips 2p
Jack Plug 1/4" 2 pole 20p, Socket 32p
Jack Plug 1/4" 3 pole 25p Socket 50p
Jack Plug 3 5mm 15p, Socket 23p, Jack Plug 2 5mm 15p, Socket 24p

All prices include VAT, please add 20p postage (overseas post at cost) PCBs post free

Send LARGE SAE for full list of boards and components, etc

Mail Orders please to: **D.B.M. PRODUCTS**
Unit 14, Southern Road, Aylesbury, Bucks.

Mullard Components

Polyester Capacitors. C280 Series 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 3 1/2p, 0.15, 0.22, 4 1/2p, 0.33, 6 1/2p, 0.47, 7 1/2p, 0.68, 10p, 1.0, 12p, 1.5, 18p, 2.2µF, 21p.

Carbon Film Resistors. 0.33W 5% Hi-stability. E12 series 4R7-1M. Your selection.
1p each, 0.9p 10+, 0.85p 100+

Return of post service. Prices include 12 1/2% VAT. Allow 15p for carriage. Mail order only

CN Stevenson (ETI)
304 Avery Hill Road, London SE9
2JN

ONLY THE BEST!

VAT Inc. P&P 15p
741 DIL 8-pin 29p each, 4/£1 2N3055 30p each 4 £1
1N4002, 1N4003, 1N4004 5p each Any 10 40p
0.375" 7-SEG Comm Cath LED Display (FND357) £3 25
90p each, 4 £2 80
TIP2955 W/Mtg Kit 85p each, 4 £2 00
TIP3055 W/Mtg Kit 60p each 4 £2 00
BFY50, BFY51, BFY52, 20p each, ANY 10 £1 40
BC109, BC184L (Plastic) 12p each, ANY 10 90p
TIL209 0.125" Red LED W/Clip 19p each 10 £1.60
GREEN, ORANGE, YELLOW 0.125" LEDS W/Clip 29p each ANY 10 £2 30
0.2" RED LED W/Clip 20p each 10 £1 70
10mf./12V. Electrolytic Capacitors 10 30p, 100 £1
AUDIO-OPTICS, 19 MIDDLEWAY, CHINNOR, OXON. TEL. 0844 52683

H.M. ELECTRONICS

275a FULWOOD ROAD, BROOMHILL
SHEFFIELD S10 3BD
BEC CABINETS (illus'd)

METAL CASES
DRY TRANSFER LETTERING
Send 15p for leaflets (Refundable)
Trade enquiries invited



ADVERTISERS:-

PLEASE NOTE NEW ADDRESS
25-27 OXFORD STREET
LONDON W.1.

electronics today international reader services

BACK ISSUES

These cost 40p each. Postage and packing costs 15p for the first, and 10p for each subsequent issue. Orders to ETI BACK ISSUES Dept. please. We CANNOT supply the following issues:- All 1972; January, February and November 1973; January, March, September, October, November and December 1974; January, June, July, August, September, November and December 1975; January, March 1976; April, August, October 1973.

PHOTOCOPIES

Due to the steady pressure on our back numbers department, and the dwindling number of issues available, we have decided to set up a photocopies service. This involves our staff in considerable time consuming endeavour, so we hope our readers understand the need for our decision to apply a flat charge of 50p inclusive. This covers any article, regardless of the number of pages involved, from any ONE issue of ETI.

Mark envelope to 'ETI Photocopy Service'.

EDITORIAL QUERIES

Written queries can only be answered when accompanied by an SAE, and the reply can take up to three weeks. These must relate to recent articles and not involve ETI staff in any research. Mark your letter ETI QUERY . . . Telephone queries can only be answered when technical staff are free, and never before 4 pm.

BINDERS

Binders, for up to 13 issues, are available for £2.50 including VAT and carriage. Send orders to ETI BINDERS DEPT. . . .

SPECIAL ISSUES

Presently we produce five specials - Top Project 2 and 3, Electronics it's Easy (parts 1-13 and Parts 14-24) and 4600 Synthesiser (published by Maplin). Prices are 75p, £1, £1.20 and £1.50 respectively. Post and packing 15p per copy. Orders to ETI SPECIALS Dept. please.

T-SHIRTS

ETI T-shirts are available in Large, Medium, or Small sizes. They are yellow cotton with black printing and cost £1.50 each. Send orders to ETI T-SHIRTS Dept. . . .

BOOKS

ETI Book Service sells books to our readers by mail order. The prices advertised in the magazine include postage and packing. Send orders to ETI Book Service, P.O. Box 79, Maidenhead, Berks.

NON-FUNCTIONING PROJECTS

We cannot solve the problems faced by individual readers building our projects unless they are concerning interpretation of our articles. When we know of any error we print a correction as soon as possible at the end of News Digest. Any useful addenda to a project will be similarly dealt with. We cannot advise readers on modifications to our projects.

SUBSCRIPTIONS

The annual subscription to ETI for UK readers is £6. The current rate for readers overseas is £7. Send orders to ETI SUBS Dept. PAYMENT IN STERLING ONLY PLEASE.

PCBs

PCBs are available for our projects from companies advertising in the magazine.

**NEW ADDRESS ALL ETI DEPARTMENTS
25-27 OXFORD STREET LONDON W1**

**PLEASE MARK REVERSE OF EACH CHEQUE
WITH NAME & ADDRESS AND ITEMS
REQUIRED.**

ALLOW 10 TO 14 DAYS FOR DELIVERY

INDEX TO ADVERTISERS

PLEASE NOTE NEW ADDRESS

AITKEN BROS.	Mini-Ads	KINNIE COMPONENTS	23
AMBIT INTERNATIONAL	48	LEE INSTRUMENTATION LTD.	33
ARROW ELECTRONICS LTD.	47	LYNX ELECTRONICS (LONDON) LTD.	56
BH COMPONENTS LTD.	72 2 Mini-Ads	MAPLIN ELECTRONIC SUPPLIES	O.B.C. 84
BI-PAK LTD.	4-5	MARCO TRADING	Mini-Ads
BI-PRE-PAK LTD.	I.B.C. 83	MARSHALL'S	53
B.N.R.S.	78	METAC INTERNATIONAL	17
BYWOOD	18	MINI KITS	77
CAMBRIDGE LEARNING ENTERPRISES	69	ORCHARD ELECTRONICS	13
CATRONICS	35	PULSE ELECTRONICS	79
CHILTMead LTD.	70	RADIO CONSTRUCTOR	79
CLIFFPALM LTD.	63	RADIO ROTOR	61
CROFTON ELECTRONICS LTD.	78	RAMAR CONSTRUCTOR SERVICES	Mini-Ads
D.B.M. PRODUCTS	Mini-Ads	RF EQUIPMENT SPARES	Mini-Ads
DECON LABORATORIES LTD.	40	SINTEL	27
DORAM ELECTRONICS LTD.	23	SWANLEY ELECTRONICS	77
E.D.A.	48	TAMTRONIK LTD.	Mini-Ads
ELECTRONIC BROKERS LTD.	32	TANDY CORPORATION	Mini-Ads
F.E.K. SUPPLIES	Mini-Ads	TECHNOMATIC LTD.	16
GREENBANK ELECTRONICS	79	TEMPUS	63
HEATHKIT LTD.	40	T.K. ELECTRONICS	Mini-Ads
HENRY'S LTD.	2	VERO ELECTRONICS	63
I.L.P.	74	VIDEO MASTER LTD.	24
INTEGREX LTD.	47	WATFORD ELECTRONICS	62
ISLAND DEVICES	Mini-Ads	WILMSLOW AUDIO	77

Stirling Sound

QV† MODULES FOR COST-CONSCIOUS CONSTRUCTORS

STIRLING SOUND QV Modules are our own designs manufactured in our own Essex factory. Production standards are carefully controlled and you, the constructor, benefit directly from our many years of experience in meeting demand for components as well as by buying direct from us.

PRE-AMPS & CONTROL MODULES

Unit One

Combined pre-amp with active tone-control circuits 200mV output for 50mV in. Runs on 10 to 16V supply. treble ±15dB at 10KHz, bass ±15dB at 30Hz Stereo bal., vol., treble & bass controls

£7.80

SS.100


Active tone control, bass & treble

£1.60


SS.101

Pre-amp for ceramic cartridges etc., passive tone control circuit shown in data supplied

£1.60

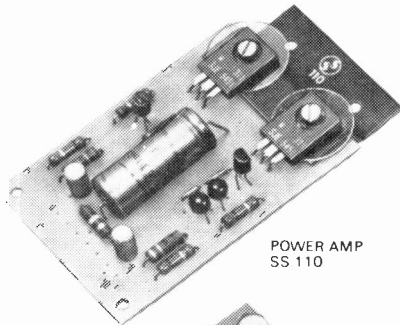


POWER AMP
SS.110

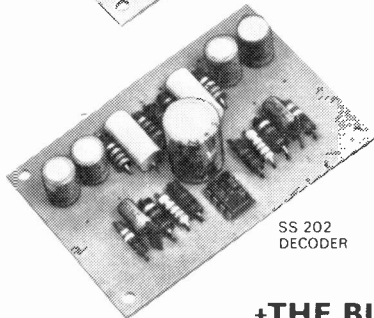

SS.202
DECODER

†THE BUILT-IN QV FACTOR


means Stirling Sound's guarantee of quality and value which gives you today's best buys all round. That's why you'll do better with QV Modules!

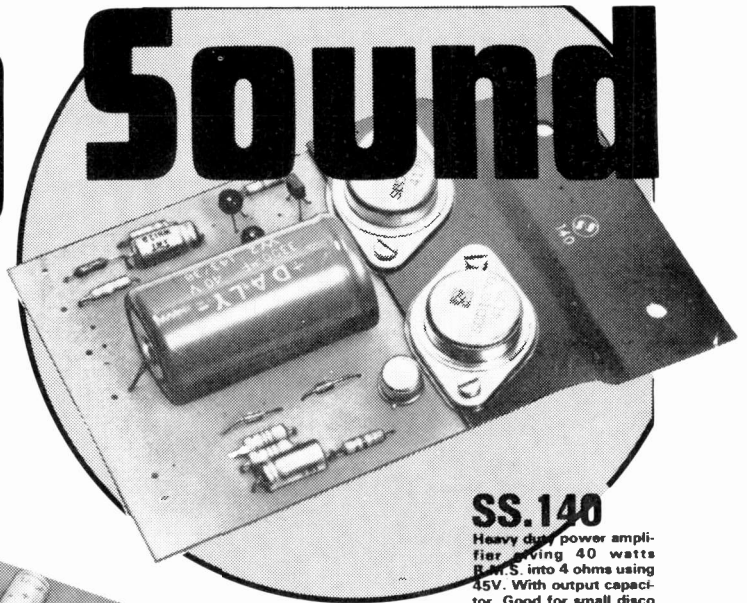

SS.140

Heavy duty power amplifier giving 40 watts R.M.S. into 4 ohms using 45V. With output capacitor. Good for small disco or P.A.

£3.95*

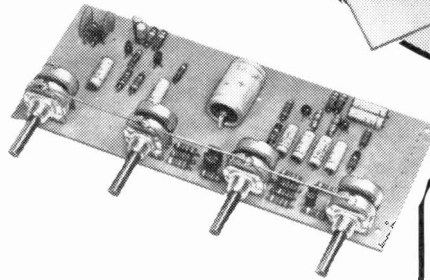

SS.102 STEREO PRE-AMP

R I A corrected for mag. p/ups, tape, radio, etc.

£2.65

POWER AMPLIFIERS

SS.103

A 3 watt amplifier using single I.C. type SL 60745 with built-in short circuit protection

£1.75

SS.103-3. Stereo version (2 I.C.s) of above

£3.25

SS.105

5 watts R.M.S. into 4 ohms using 12V supply. Ideal for use in in-car entertainment. Size 89 x 51 x 19mm

£2.25

SS.110

Similar in size and design to SS.105 this QV module delivers 10 watts R.M.S. into 4 ohms using a 24V supply, e.g. SS.324. Of great use in domestic applications

£2.75

SS.120

Using a 34 volt supply, such as SS.334 this amplifier will deliver 20 watts into a 4 ohm load. Same dimensions as above.

£3.25

There are suitable Stirling Sound power supplies for all the above

FM TUNING

SS.201

FM Front End with geared slow motion tuning and A.F.C. facility 88-108MHZ

£5.00

SS.202

1 F amp A meter and/or A.F.C. can be connected (size 3" x 2") For use with SS.201

£2.65

SS.203


Stereo decoder (illustrated) For use with Stirling Sound modules or with any other good mono FM tuning section. A LED beacon can be added (Price 18p) to indicate when a stereo signal is tuned in (3" x 2")

£3.85

TODAY'S BEST VALUE IN POWER SUPPLY UNITS*

ALL AT 8% VAT

with 13-15V take-off points

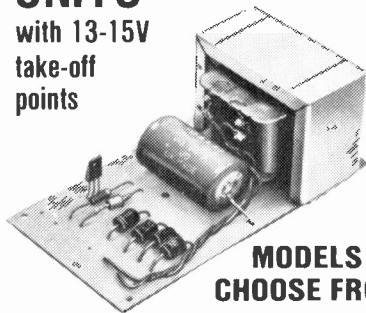


7 MODELS TO CHOOSE FROM

Compare these guaranteed power packs for power and price. Not only do these excellent power packs stand up unflinchingly to hard work, inclusion of a take-off point at around 13-15V adds to their usefulness.

SS.312	12V/1A	£3.75*
SS.318	18V/1A	£4.15*
SS.324	24V/1A	£4.60*
SS.334	34V/2A	£5.20*
SS.345	45V/2A	£6.25*
SS.350	50V/2A	£6.75*

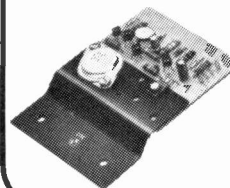SS.300. Add-on power supply stabilising unit. Short-circuit protected. Ensures stabilised output variable from 12V/2A to 50V max at 8A. Ideal for workbench and experimenting. £3.25 (P&P35p)



SS.310/350 VARIABLE OUTPUT STABILISED SUPPLY

With continuous variable output at 2A from 10 to 50 V D.C. With built-in protection against shorting and fully adequate heat sink. Guaranteed Superb value at £11.95

WHEN ORDERING

Add 35p to your order for P&P for mail orders. VAT add 12½% to total value of order unless shown* then the rate is 8%. Make cheques, etc., payable to BI-PRE-PAK LTD. Every effort is made to ensure correctness of information at time of going to press. Prices subject to change without notice.

Stirling Sound

A member of the BI-PRE-PAK Group

220-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SS0 9DF

Phone: Southend (0702) 46344. PERSONAL CALLERS WELCOME

The new Maplin Catalogue is no ordinary catalogue...

Hundreds of fascinating new lines.

Several major new projects to build.

MAPLIN ELECTRONIC SUPPLIES

SUPERSONIC SAME DAY SERVICE!


QUALITY COMPONENTS FAST!

Super Discount Scheme - saves you pounds!

Hundreds of photos, graphs and illustrations

Test Gear Section includes superior quality single-beam and dual beam OSCILLOSCOPES at remarkably low prices. These superb SCOPEX scopes are undoubtedly the best value for money around.

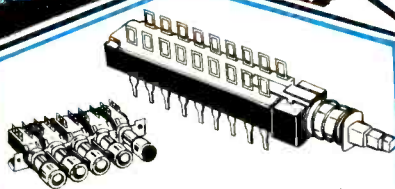Projects section includes complete construction details of a professional quality MULTI-CHANNEL MIXER with modular sections for complete flexibility. Extremely low noise and distortion AND low cost.



Just one of the hundreds of new lines in the component section. A new range of FULLY INTERLOCKING PUSH BUTTON SWITCHES - high quality - low price - large range.

Catalogue includes a very wide range of components: hundreds of different capacitors; resistors; transistors; I.C.'s; diodes; wires and cables; discotheque equipment; organ components; musical effects units; microphones; turntables; cartridges; styli; test equipment; boxes and instrument cases; knobs, plugs and sockets; audio leads; switches; loudspeakers; books; tools - AND MANY MANY MORE.



Our bi-monthly newsletter keeps you up to date with latest guaranteed prices - our latest special offers (they save you pounds) - details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).

SEND THIS COUPON FOR **YOUR** COPY OF OUR CATALOGUE ON APPROVAL! Price 50p - SEND NO MONEY NOW. Please rush me a copy of your brand new 1977/78 catalogue the instant it is published. Only if I am completely satisfied that it is worth every penny, will I send 50p within 14 days of receipt. If I am not satisfied, I may return the catalogue to you within 14 days without obligation. I understand that I need not purchase anything from your catalogue should I choose to keep it.

NAME _____

ADDRESS _____

Maplin Electronic Supplies P.O. Box 3, Rayleigh, Essex, SS6 8LR

ETI 12

Owing to delay in completion of larger warehouse, catalogue will be delayed by up to four weeks - so there's still time to order before publication and get your pack of ten super special offer coupons, giving big discounts on ten different popular items. **YOU COULD SAVE POUNDS! - SO DON'T DELAY - FILL IN AND POST COUPON NOW!**

MAPLIN

ELECTRONIC SUPPLIES
P.O. BOX 3, RAYLEIGH, ESSEX SS6 8LR

Shop: 284, London Road, Westcliff-on-Sea, Essex
(Closed on Monday) Telephone: Southend (0702) 44101