

# electronics today international

MARCH 1976

30p

SOUTH AFRICA 60c

CANADA \$1

## HENRY'S Competition Inside

ETI  
READER  
OFFER

£14.95



DATA SHEET SPECIAL  
OP-AMPS



**DISTORTION**



ETI looks at  
MICROPROCESSORS!

CANNIBALS & MISSIONARIES  
HEADPHONE-ADAPTOR  
AUDIO LEVEL METER



# electronics today

international

MARCH 1976

VOL 5. No. 3.

## Features

AMPLIFIER DISTORTION <i>Sometimes it can actually improve the sound!</i>	10
GEOLOGICAL SURVEY — PART TWO <i>Infra-red and radioactive surveying methods</i>	47
MICROPROCESSORS <i>ETI introduces 'Microfile'</i>	54
CMOS — PART TWO <i>More information and circuits</i>	59
ELECTRONICS IT'S EASY <i>Continuing with digital circuits</i>	66

## Projects

AUDIO LEVEL METER <i>Unusual method of display is used</i>	17
CANNIBALS AND MISSIONARIES <i>Our own version of 'Jaws' to play at home!</i>	24
HEADPHONE ADAPTOR <i>Properly designed circuit improves performance</i>	53
SILENT A-B SWITCH <i>Modification to our Tone-Burst Generator</i>	57
DYNAMIC NOISE FILTER — PART TWO <i>Eliminate surface noise!</i>	62

## Data Sheet Special

OPERATIONAL AMPLIFIERS <i>Data sheets</i>	30
--	----

## Index

APRIL 1972 — MARCH 1976 <i>Listing of features since ETI's first issue</i>	41
---	----

## News & Information

NEWS DIGEST	6
PROJECT BOOK 3	23
PULSAR OFFER REOPENED	23
PREVIEW OF APRIL ETI	40
ETI BOOK SERVICE	46
ETI SPECIALS	69
ELECTRONICS TOMORROW	70
TECH-TIPS	72

## Competition

ETI/HENRY'S RADIO COMPETITION <i>Up to £500 to be won in prizes</i>	38
--	----

## Special Offer

EXELAR DIGITAL ELECTRONIC WATCH <i>A fabulous product for only £14.95!</i>	45
---	----

## EDITORIAL AND ADVERTISEMENT OFFICE

36 Ebury Street  
London SW1W 0LW  
Telephone: 01-730 8282

HALVOR W. MOORSHEAD  
Editor

ROBERT C. EVANS  
Advertisement Manager

STEVE BRAIOWOOD, G3WKE  
Assistant Editor

LES BELL, G4CFM  
Editorial Assistant

JEAN BELL  
Production

## INTERNATIONAL EDITIONS

COLLYN RIVERS  
Editorial Director

AUSTRALIA  
BRIAN CHAPMAN  
Technical Editor  
BARRY WILKINSON  
Engineering Manager  
Modern Magazine Holdings Ltd  
Ryrie House, 15 Boundary Street  
Rushcutters Bay 2011  
Sydney, Australia.

FRANCE  
DENIS JACOB  
Editor in chief  
CHRISTIAN DARTEVILLE  
Editor  
Electronique Pour Vous International,  
17 Rue de Buci  
Paris, France.

Electronics Today International is normally published on the first Friday of the month prior to the cover date.

PUBLISHERS  
Modern Magazines (Holdings) Ltd  
36 Ebury Street, London SW1W 0LW



DISTRIBUTORS  
Argus Distribution Ltd

PRINTERS  
QB Newspapers Limited, Colchester

READERS' QUERIES: These can only be answered if they relate to recent articles published in the magazine. Rarely can we supply information in addition to that published. Written queries must be accompanied by a stamped addressed envelope, and telephone queries must be brief, not before 4pm and can only be answered subject to the availability of technical staff.

BACK NUMBERS: Back numbers of many issues are available for 40p each, plus 15p postage.

SUBSCRIPTIONS: Great Britain £5.00 per annum. Overseas £5.50.

COPYRIGHT: All material is subject to world wide Copyright protection. All reasonable care is taken in the preparation of the magazine to ensure accuracy but ETI cannot be held responsible for it legally. Where errors do occur, a correction will be published as soon as possible afterwards in the magazine.

READER SERVICES: See page 82 for details of all ETI Reader Services and other information.

STILL TIME TO ENTER  
HELPING HAND  
SEE P35



# BI-PAK

High quality modules for stereo, mono and other audio equipment.



OUR PRICE ONLY  
**£19.95**

The 450 Tuner provides instant program selection at the touch of a button ensuring accurate tuning of 4 pre selected stations, any of which may be altered as often as you choose, by simply changing the settings of the pre-set controls.

Used with your existing audio equipment or with the BI-KITS STEREO 30 or the MK60 Kit etc. Alternatively the PS12 can be used if no suitable supply is available, together with the Transformer T461.

The S450 is supplied fully built, tested and aligned. The unit is easily installed using the simple instructions supplied.

**NEW**  
**PUSH-BUTTON**  
**STEREO**  
**FM TUNER**

Fitted with Phase Lock-loop

- ★ FET Input Stage
- ★ VARI-CAP diode tuning
- ★ Switched AFC
- ★ Multi turn pre-sets
- ★ LED Stereo Indicator

Typical Specification:  
Sensitivity 3µ volts  
Stereo separation 30db  
Supply required 20-30v at 90 Ma max.

## MPA 30

Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the new M.P.A. 30, a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only. It is provided with a standard DIN input socket for ease of connection. Full instructions supplied.

**£2.65**

## STEREO PRE-AMPLIFIER



A top quality stereo pre-amplifier and tone control unit. The six push-button selector switch provides a choice of inputs together with two really effective filters for high and low frequencies, plus tape output.

**MK. 60 AUDIO KIT:** Comprising 2 x SPM80 1 x BTM80, 1 x PA100 1 front panel and knobs 1 Kit of parts to include on/off switch, neon indicator, stereo headphone sockets plus instruction booklet. **COMPLETE PRICE £27.55.**

**TEAK 60 AUDIO KIT:**

Comprising Teak veneered cabinet size 16 1/4" x 11 1/2" x 3 3/4", other parts include aluminium chassis, heatsink and front panel bracket plus back panel and appropriate sockets etc. **KIT PRICE £9.20.**

plus 62p postage.

Frequency Response + 1dB 20Hz - 20KHz Sensitivity of inputs  
1. Tape Input 100mV into 100K ohms  
2. Radio Tuner 100mV into 100K ohms  
3. Magnetic PU 3mV into 50K ohms  
P.U. Input equalises to R1AA curve with 1dB from 20Hz to 20KHz  
Supply - 20-35V at 20mA

Dimensions  
299mm x 89mm x 35mm.

## PA 100

OUR PRICE  
**£13.50**

## AL10-20-30

**AUDIO AMPLIFIER MODULES**

The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S.

The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the home.

**SPECIFICATION:**

- Harmonic Distortion  $P_o = 3$  watts  $f = 1$  KHz 02.5%
- Load Impedance 8-16ohm
- Size: 75mm x 63mm x 25mm
- Frequency response  $\pm 3$ dB  $P_o = 2$  watts 50Hz-25Hz
- Sensitivity for Rated O/P -  $V_s = 25$ v.  $R_L = 8$ ohm  $f = 1$  KHz 75mV. RMS

AL10 3w R.M.S. **£2.30**    AL20 5w R.M.S. **£2.65**    AL30 10w R.M.S. **£2.95**

## AL 60 25 Watts (RMS)

- ★ Max Heat Sink temp 90C. ★ Frequency response 20Hz to 100KHz ★ Distortion better than 0.1 at 1KHz ★ Supply voltage 15-50v ★ Thermal Feedback ★ Latest Design Improvements ★ Load - 3,4,5, or 16 ohms ★ Signal to noise ratio 80db ★ Overall size 63mm. 105mm. 13mm.

Especially designed to a strict specification. Only the finest components have been used and the latest solid-state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

**£3.95**

## VAT ADD 25%

### POSTAGE & PACKING

Postage & Packing add 25p unless otherwise shown. Add extra for airmail. Min. £1.00

## STEREO 30

COMPLETE AUDIO CHASSIS  
7+7 WATTS  
R.M.S.



**£15.75**

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck etc. Simple to install, capable of producing really first class results, this unit is supplied with full instructions, black front panel knobs, main switch, fuse and fuse holder and universal mounting brackets enabling it to be installed in a record plinth, cabinets of your own construction or the cabinet available ideal for the beginner or the advanced constructor who requires Hi-Fi performance with a minimum of installation difficulty (can be installed in 30 mins).

TRANSFORMER £2.45 plus 62p p & p  
TEAK CASE £3.65 plus 62p p & p.

## NEW PA12

NEW PA12 Stereo Pre-Amplifier completely redesigned for use with AL10/20/30 Amplifier Modules. Features include on/off volume, Balance, Bass and Treble controls. Complete with tape output.

Frequency Response 20Hz-20KHz (-3dB). Bass and Treble range 12dB. Input Impedance 1 meg ohm. Input Sensitivity 300mV. Supply requirements 24V. 5mA. Size 152mm x 84mm x 33mm.

**£6.50**

## PS12

Power supply for AL10/20/30, PA12, SA450 etc.

Input voltage 15-20v A.C. Output voltage 22-30v D.C.  
Output current 800 mA Max. Size 60mm x 43mm x 26mm.

OUR PRICE **£1.20**

Transformer T538 **£2.30**

## Stabilised Power Supply Type SPM80

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watts (R.M.S.) per channel simultaneously. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5A at 35V. Size 63mm. 105mm. 30mm. Incorporating short circuit protection.

Transformer BMT80  
**£2.60 + 62p postage**

**£3.00**

# BI-PAK

P.O. BOX 6, WARE, HERTS.

# news digest



## MAGNETIC CARD PROGRAMMABLE CALCULATOR

Slough, December 10, 1975. . . . .  
A handheld magnetic card programmable calculator with a recommended retail price of £250.00 (inc.VAT) has been introduced by Texas Instruments Limited, European Calculator Division.

This new programmable calculator from TI offers 20 memory registers, 10 user-definable keys and has the capability to accept 224 program steps. The algebraic entry combined with 9 levels of parentheses allows problems to be entered exactly as they are written.

The SR-52 is able to store up to 224 program steps and numbers on a single magnetic card. 20 independent addressable memory registers permit addition, subtraction, multiplication and division of any displayed quantity with any memory register without affecting the keyboard calculation in progress.

With the calculator's 23 preprogrammed key functions, trig and log, powers and roots, factorials, reciprocals, three conversions and pi can be directly executed from the keyboard.

Ten different decision instructions and five user-set flags allow the user to program the SR-52 to make repetitive decisions and branch to appropriate program segments automatically without interruption.

Other features include 10 user-defined keys and 72 user-defined labels. While any portion of a program may be called by an absolute address number, these keys and labels permit prompt and unique identification and call-out of any pertinent program segment. Indirect addressing, decrement-and-skip on zero, and two levels of subroutines provide additional programming flexibility.

In addition to an operating guide and owner's manual, the SR-52 package includes a Basic Library manual, a card case, a library of pre-recorded programs on magnetic cards, diagnostic programs for testing the SR-52 and head cleaner.

Pre-recorded and diagnostic programs will be available through retail outlets and from Texas Instruments Limited together with other pre-recorded libraries for various professional disciplines.

The Texas Instruments SR-52 carries a one-year limited warranty, from the original purchase date -- under normal use and service -- against defective materials or workmanship. Any implied warranties are also limited in duration to the one-year period from the original purchase date.

## IMPORTANT WARNING

Readers are asked to note the considerable danger involved in the production of homemade LDRs by cutting open silicon power transistors, as described on page 47 of Tech-Tips Special in the January issue. The danger lies in the fact that many power transistors contain Beryllium Oxide which is EXTREMELY TOXIC. The inhalation of Beryllia dust or fumes on a single exposure lasting minutes or seconds can cause injury to the skin or mucous membrane severe enough to endanger life or cause serious injury. If particles of Beryllia enter the skin through cuts or grazes chronic ulceration is liable to result. Our thanks go to M. P. Hearne of Campbeltown for calling our attention to this.

## SIGNETICS DROP CMOS

Our US correspondent advises us that Signetics have telexed all their US sales staff and distributors advising them that the company will be discontinuing their CMOS logic series.

Signetics' sales of CMOS products fell short of their projected target by a considerable margin. We understand that whilst the 1975 target was US\$ 200 million actual sales are not expected to exceed US\$ 120 million.

## SOLAR CELL IS 20% EFFICIENT

A 20% efficient solar cell has been developed by Varian Associates.

According to the firm, its 8mm diameter cell produces 10 watts of electricity directly from a focused sunlight beam. Varian makes the cell from a gallium arsenide material developed by IBM. Although the cells are not yet in commercial production, Varian says it plans eventually to build a system of cells that can generate 1kW.

## ELECTRONIC WATCH HAS CONTINUOUS DISPLAY

A challenge to LED and LCD watches has been launch by America's Optel Corporation. Optel have just released details of a prototype unit incorporating an 'electro-chromic' display claimed to be capable of showing a continuous readout without constant battery power.

The prototype unit is a three function device which shows hours and minutes continuously and seconds on demand. The corporation say that there are still 'some problems' with the design but claim a two to five year life for the prototype readout which they say has a 200 millisecond response time.

## NEW HEATKITS

The January 1976 Heathkit catalogue is now available (send a 10p stamp for return postage) free from their HQ at Bristol Road, Gloucester, GL2 6EE.



The most interesting new product is a seven-function programmable stop-watch. For £74.50 you get the following—

- (i) Ability to time two events simultaneously.
- (ii) Timing of two minor events (two lap times, for instance) and displaying these, whilst timing the overall event.
- (iii) Accumulation of a series of timings and display of the total; simultaneously the time elapsed from the first to the last timing is measured. Total journey time and total driving time, for example, can be measured.
- (iv) Split facility — the display will show the time-so-far at the touch of a button at any instant in the course of timing an event.
- (v) Separate timings can be taken for each "leg" of an event and then these can be totalled.
- (vi) Alarm or "upcount": counts up to a programmed time and then gives an output pulse. The count can be interrupted at any point.
- (vii) "Downcount" — the timer will count down from a programmed number and gives out a pulse at zero. Ideal for launching rockets, etc.


By combining the functions a time can be "learned" by transferring a displayed number to upcount or downcount.

Start/Stop jacks allow external triggering from photoelectric sensors, etc. Measuring range is up to 100hrs.

and programming range up to 10hrs, with a resolution of 1/100th second. Although there is nothing this device can do which can't be done using the ETI Timing Modules (Dec 75 and Jan 76 issues) the Heathkit GB-1201E is packaged nicely in a hand-hold case (5 1/3" x 2 1/6" x 2").

Other new products in the catalogue are:

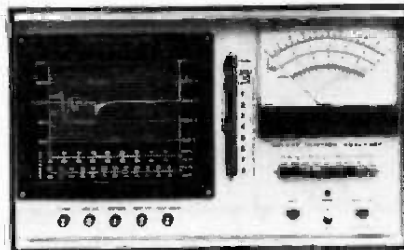- A car intrusion Alarm (£18.80).
- An Electronic Doorbell (£31.50) which allows you to compose your own tune (within 16 beats and 1 octave). The tune can be changed (for a birthday party or for Christmas, etc) behind the front panel door.
- A Digital Rev Counter (£31.80) gives a two digit readout.



An Ignition Analyser (£280.00) with a 12 inch screen and professional facilities.

An SSB Transceiver (£490) for 80 thru 10m.  
A CW Transceiver (£108.00) for 80 thru 15m.

A Synthesised 2 Meter FM Transceiver (£255.00).

A Hand-Held 2 Meter Transceiver (£144.00).


A 30MHz Frequency Counter/Timer (£78.00).

All prices include VAT and delivery in the UK and all refer to products in kit form.
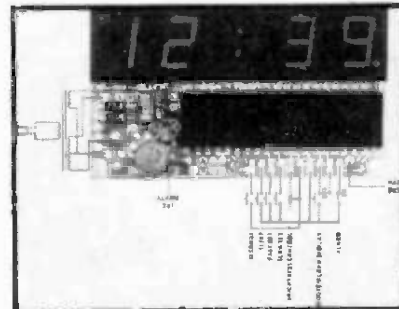
## DIGITAL CLOCK COSTS CUTS

A new clock module subsystem MA1001 requires only a transformer and switches to become a pre-tested electronic digital clock for use in radios, alarms, domestic and timing instrumentation, at approximately 50% of the cost of conventional similar designs.

The MA1001 is supplied with timing circuitry and a 4-digit LED display ready mounted on a 1.5" x 3" pcb. The LED's are 1/2" characters, and the ready-mounted MM5385N integrated MOS clock circuit (packaged 40-pin DIL) eliminates the need for separate bipolar segment-driver and digit-drive circuits. It also eliminates more than 30 resistors, as well as the RF filter capacitors sometimes required to attenuate RF interference



generated by multiplexed LED displays. The clock IC drives LED segments and digits directly, without multiplexing, which suppresses most RFI. The residual is eliminated by using a slow transition time in the output stages — 100µsecs as against the usual 1µsec.

The time-keeping frequency source can be either 50 or 60Hz, and 12-hour or 24-hour display options are available. Time is set through "Fast" and "Slow" scanning controls.

Features include alarm ON and PM indication, blinking colon, SLEEP and DOZE timers and variable brightness control capability. Alarm clock options include a transistor oscillator circuit for use with a low-cost ear-phone transducer. National Semiconductor UK Ltd., 19 Goldington Road, Bedford MK40 3LF.


## A SWINGING CALCULATOR (CURSOR?)

Now that West Hyde Developments are supplying a big range of carbon film, wirewound, vitreous wirewound resistors, and polystyrene capacitors, they have designed a 5" plastic Resistor Calculator with a built-in slide rule with which they are introducing these products to their customers. It has a



calculator on one side with a swinging cursor, which efficiently calculates power, current, voltage and resistance — any two known and two unknown, and the 5" slide rule is on the other side.

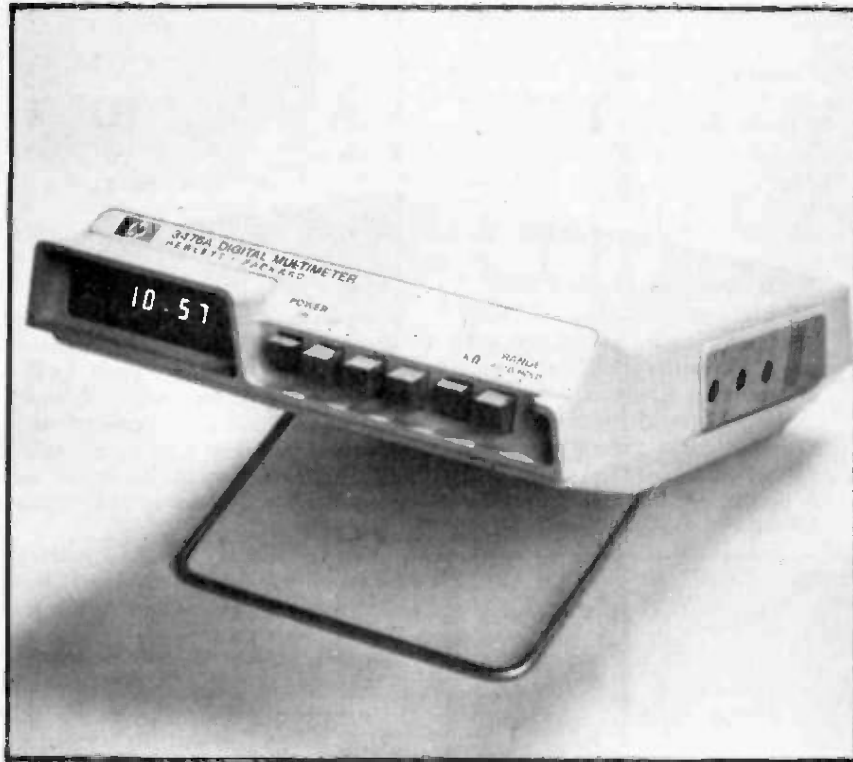These are available from West Hyde Developments Ltd., Ryefield Crescent, Northwood, Middlesex, price 61p including P and P and VAT.



## LOW-COST HP OMM

This new 3½ digit, five function, fully autoranging digital multimeter from Hewlett-Packard sells for only £144, and measures voltages from ±0.0001V DC and from 0.0003V to 700V rms AC. Resistance is measured from 0.001 kΩ to 1,000 kΩ. Current can be measured from 0.0001A to 1.1A DC and 0.0003A to 1.1A AC. Autozero, autopolarity and autoranging are built in.

Typical accuracy for DC voltage measurements is 0.5% DC current accuracy is 1.0%. One AC voltage ranges, frequency is specified to 10kHz, while AC current is to 5kHz. Accuracy of resistance measurements is within 0.6% on the three highest ranges and 0.4% on the two lower ranges. Open circuit voltage is less than 4V.

Input resistance on all voltages is 10MΩ with input capacitance of less than 30pF. The 3476 is protected to 1100V peak on all ranges. The fuse that protects the ohms function is rated 250V rms. The current function is fuse protected to 1.5A. No special fuses are required and they can be quickly replaced without dismantling the instrument.

A range hold feature is included that allows the instrument to be locked to any desired range. This feature is necessary, for example, when measuring diode resistance. It also makes repetitive measurement

faster. The LED readout gives all voltage readings in volts, all resistance readings in kilohms and all current readings in amperes.

Model 3476A is AC line powered only; Model 3476B is AC line powered and also includes rechargeable nickel cadmium batteries. Model 3476A weighs 0.71kg and Model 3476B weighs 0.9kg. UK price is £175.00 for the 3476B. Hewlett-Packard Ltd., King Street Lane, Winnersh, Wokingham, Berks RG11 5AR.

## HEATHKIT 'SCOPE COMPETITION

We now have the results of the competition in our December issue. **FIRST PRIZE** of a 10-4540 scope goes to Mr. J. Humberstone,

57 Woodhead Road,  
Sheffield S2 4TB.

**SECOND PRIZE** of a 10-4560 scope goes to Mr. A Eaves.

'Salway', Crowbrook Road,  
Askett, Aylesbury,  
Bucks, HP17 9LS.

**THIRD PRIZE** of another 10-4560 scope goes to Mr. M.L. Shirtcliffe,  
50 Lupton Crescent,  
Sheffield S87NA.



## STILL TIME FOR HELPING HAND

The closing date for this award is March 31st, 1976, so if you haven't sent your ideas in yet there is still time. Details of the problems to be tackled are given in previous issues of ETI — choose any one of three specific problems facing deaf people. By the application of your knowledge of electronics you can help spare deaf people some of the hardships they face; and ETI, in conjunction with the RNID, will help develop your ideas.

If you need more information send a large SAE to ETI HELPING HAND, ETI Magazine, 36 Ebury Street, London SW1W 0LW.

## ASTRONOMERS DETECT INDIVIDUAL PHOTONS

A digital television system for astronomy, developed by University of Arizona astronomers, is sensitive enough to detect individual photons of light coming into a telescope and record them for immediate playback.

As a result it is possible to see objects 100 times fainter than previously possible. The system is based on a special television tube — a silicon intensified target tube — that records 64 000 points of light simultaneously. The information then is sent in digital form to a computer, which removes the image's noise. Photographs or a spectrogram can be produced.

## BIPOLAR PROMs AND ROMs BOOKLET

Intel have published a 36-page booklet which provides technical information on 13 different ROMs and 24 different PROM types they manufacture. All the devices in the booklet are of Schottky bipolar construction and erasable PROMs are not included.

The booklet incorporates a data sheet for each device, an equivalents chart and gives details of PROM programming equipment.

For every Intel PROM there is a pin and performance compatible PROM, which means that no circuit changes have to be made when a project is finalized and information in PROM is committed to mask-programmed ROM.

All Intel PROMs employ polysilicon fuses which coat the surrounding area in a protective oxide layer when they are 'blown'. With polysilicon fuses there is no danger of a fuse 'growing back' as has happened before with conventional metal fuses.



# Build it yourself!



Designed by  
**TEXAS**

Featured by **PRACTICAL WIRELESS**  
SOLE U.K. DISTRIBUTORS - **HENRY'S**

Build the Texan stereo amplifier, then you can be doubly proud! For a start, you'll own a superb home entertainment unit. And have had all the pleasure of doing it yourself, with the Henry's kit.

**Look at the Texan specification**

Incorporating fully integrated stereo preamp and power amp, with 6 IC's, 10 transistors, 6 rectifiers and zener diodes. Plus stabilised, protected circuitry, glass fibre pcb; Goldeners low-field low-line mains transformer; all facilities and controls. Slim design, chassis 14" x 6" x 2" overall. 20 watts per channel RMS, less than 0.1% distortion at 1 kHz.

- ★ Can be built Stage by stage
- ★ Ask for leaflet 70.
- ★ Everything necessary supplied. Full after sales service and guarantees.

**KIT PRICE**  
**£35.00**  
inc. VAT + £1 p.p.

Built and tested  
**£45.00 inc. VAT**  
+ £1.00 p.p.

**THE NATURAL FOLLOW-ON - THE TEXAN FM TUNER KIT**

**KIT PRICE**  
**£25.95**  
inc. VAT +  
50p p.p.

Build the matching Texan stereo tuner! Features advanced varicap tuning. Phase lock loop decoder. Professionally designed circuit. Everything you need is in the kit. From the glass fibre pcb to the cabinet itself. Excellent spec: 2.5 uV aerial sensitivity. 500 mV output (adjustable). Tuning range 87-102 MHz. Mains powered.

Built and tested £30.95 inc. VAT + 50p p.p.

**VIDEO SPORT**

... all the electronic excitement you could wish for!

★ OVER 10,000 ALREADY SOLD ★ IDEAL GIFT

An up-to-the-minute game. Plugs into your own TV aerial socket! Switch on. And you're away! Choose your game - football, tennis or hole-in-the-wall. Absolutely safe. For you. Your children. And your TV. Mains powered.

List Price £42.50 inc. VAT + 50p p.p.



**HENRY'S PRICE - ONLY £29.50**

WHATEVER YOU DO, DON'T FORGET YOUR LATEST **HENRY'S CATALOGUE!**



For this new edition, we have made hundreds of changes and additions. It has over 200 pages, containing virtually everything for amateurs and professionals. And you'll have no bother at all finding everything you want, because there's a complete alphabetical index as well as a section index. Together, they put you right on course for the items you need. From Sinclair projects to educational kits. Oscilloscopes to panel meters. Coils to capacitors. Transistors to valves. Loudspeakers to microphones - all at competitive prices. Over 200 pages of vital statistics - just for you! So send now for your copy.

**ONLY 50p**

25p carr./pack.

**FREE to Educational Establishments when ordered on official headed notepaper.**

- Over 5000 items inside!
- Every copy contains a free 50p voucher.
- Many new items.
- Over 200 pages.

**HENRY'S**

SELF-SERVICE CENTRES 404 and 309 EDGWARE ROAD, LONDON W2  
Bargains galore. Call in and see for yourself!

404/6 EDGWARE ROAD, LONDON W2 01-402 8301

LOWER SALES FLOOR, 231. TOTTENHAM CT. RO., LONDON W1 01-636 6681

NEW MIDLANDS STORE


94/96 UPPER PARLIAMENT STREET, NOTTINGHAM. 0602-40403

All mail to Henry's Radio, 303 Edgware Road, London. W2

**EXCLUSIVE TO ETI READERS**


QUARTZ CRYSTAL Digital Electronic Watches

**LIGHT EMITTING DIODE**

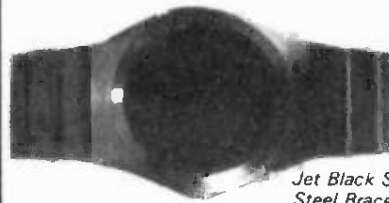


**LED MODEL TLE3**  
★ Hours  
★ Minutes  
★ Seconds **£15.80**  
+ £1.26 VAT

Jet Black Stainless Steel Bracelet

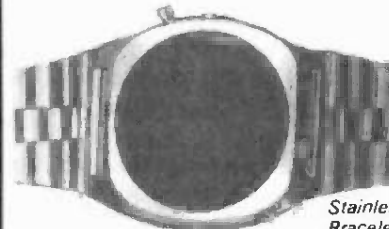

**LED MODEL TLE4**  
★ Hours  
★ Minutes  
★ Seconds **£32.75**  
★ Date  
+ £2.62 VAT

Stainless Steel Bracelet

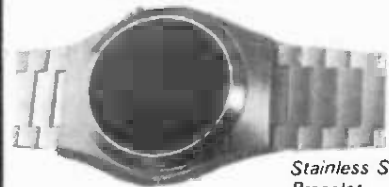

**LED MODEL TLE5**  
★ Hours  
★ Minutes  
★ Seconds  
★ Date  
★ Alpha Day **£35.53**  
+ £2.84 VAT

Stainless Steel Bracelet

**LIQUID CRYSTAL CONTINUOUS DISPLAY**



- ★ Hours
  - ★ Minutes
  - ★ Seconds
  - ★ Date
- with unique Backlight

**MODEL TLC4G**

**£38.84**

+ £3.11 VAT  
Gold plated Bracelet



**MODEL TLC4S**

**£36.40**

+ £2.91 VAT  
Stainless Steel Bracelet

- ★ One year guarantee with every watch
  - ★ Attractive presentation gift box
- Personal callers welcome

Mail order customers please add **58 pence** per order to cover postage and insurance.

**METAC INTERNATIONAL**

CROSS LANE, BRAUNSTON, NORTHANTS

Tei. Rugby 890672

Please supply the following

Name .....

Address .....

I enclose cheque

postal order  money order

I wish to pay by Barclaycard/Access and my number is

Signature .....

Money refunded in full if not satisfied

# AMPLIFIER DISTORTION

—it may sometimes be advantageous!

In this article written specially for Electronics Today International, Gordon King explains transient inter-modulation distortion and how it affects amplifier/speaker combinations.

OF RECENT MONTHS I have been endeavouring to establish meaningful correlation between the measured parameters of amplifiers and the listening room sound. This is a very difficult area of research because there are so many inter-related and variable factors involved; also because the net result is obviously a subjective impression rather than a meter reading! Nevertheless, a number of points of interest have emerged which merit discussion.

For starters, it would appear that certain parameters are advanced out of sheer 'specmanship' rather than on a basis of electro-acoustic requirements; in fact, it is sometimes possible to enhance the sound by deliberately *diminishing* a parameter. There would also appear to be a fairly important link between the subjective and the objective at the electrical interface between the amplifier and the loudspeaker. The sound field is certainly affected by the acoustical interface between the loudspeaker and the listening room.

Although this article is concerned primarily with electrical parameters, it is necessary to look at some of the acoustical aspects, too, for after all, it is the resulting sound that we listen to, not electrical signals.

The loudspeaker 'loads' both electrically into the amplifier and acoustically into the listening room; in other words, the amplifier is the electrical source for the loudspeaker and the loudspeaker the acoustical source for the listening room. It is well known of course that the output into or across a load, is influenced by the nature of the source and the load, this being applicable to acoustics as well as electrics. Sound *pressure*, in fact, is the acoustical analogue of voltage.

It is reasonable to conclude, therefore, that just as some

Detailed measurements may place two amplifiers well into the accepted hi-fi category yet, in a common signal source, loudspeaker and listening room situation, one may produce a very fine sound and the other a distinctly fatiguing sound. Fact or fiction?

**FACT!**

Given an amplifier of top-flight-measured parameters and two pairs of similar style but different make, measurement-acclaimed loudspeakers, one pair to a critical ear can be far more acceptable than the other pair, yet if the amplifier is changed the other pair may then be preferred.

Fact or fiction?

**FACT!**

---

The acoustical load presented by a particular listening room may be more acceptable to some loudspeakers than others . . .

---

electrical sources are more critical of loading than others, so are some loudspeakers. The acoustical load presented by a particular listening room may be more acceptable to some loudspeakers than others, which is one reason why a pair of loudspeakers which yield acceptable results in one room may audition less favourably in a different room. There is a case, therefore, for the loudspeaker and listening room to be measured in partnership. Although free-field (anechoic) pressure *versus* frequency plots are commonly adopted for optimising the design of loudspeakers, they are far from revealing how different loudspeakers will audition in different rooms.

It is neither difficult nor expensive for a hi-fi dealer or audiophile to measure loudspeaker/room combinations, and an inexpensive, though surprisingly accurate, method is based on the reproduction of a third-octave bands of pink noise. A 'linear' sound level meter at the normal listening position is then used to measure the sound pressure level at each band in turn over the range of 20 Hz-20 kHz, leading to the construction of a graph. This simple technique reveals eigentones and absorption effects quite dramatically, thereby indicating the adjustments required for improving the results.

Noise signal has the effect of automatically averaging the

---

It is neither difficult nor expensive to measure loudspeaker/room combinations . . .

---

sound in the listening room. Steady-state sinewave signal cannot be used. Pink noise, which is white noise with  $-3$  dB/octave (or  $-10$  dB/decade) weighting, is used because it correlates more closely with the spectral distribution of music than unweighted noise, which is white noise. It is noteworthy that the voltage of white noise is proportional to the square root of the bandwidth, and contains frequency components of constant energy per unit bandwidth. The weighting thus endows pink noise with components of constant energy per octave bandwidth.

Bruel and Kjaer have produced a calibrated record of third-octave pink noise bands (Type QR2011) which, along with a B&K sound level meter, such as Type 2206, makes it possible to 'sweep' the loudspeaker and room. The resulting overall response needs to be interpreted with care, however,

since at the higher frequencies the response fails to correlate to what we hear. This is because we judge a sound more on its starting transient rather than on its overall integrated energy. Nevertheless, low-frequency standing waves are brought to light, and modifications to loudspeaker positions, furniture positions and amplifier tone controls can often improve matters. It is hoped to publish an article in these pages later describing listening room optimisation.

The prime discrepancies between what the meter reads and what the ear discerns are related to non-linear effects both in the amplifier and loudspeaker; also, sometimes, to how the non-linearities interact electrically and acoustically. One problem in obtaining subjective correlation from a meter reading lies in the nature of the signals we are obliged to use for the measurements. Sine and square wave signals are useful, being component parts of music signal, but real music signal is much more complicated than both of these.

If it were possible to feed a loudspeaker with a perfect electrical representation of the originating sound, it is likely that the reproduction would be less palatable than that obtained by first passing the source signal through a distorting amplifier! A non-distorting signal would tend to emphasise the loudspeaker non-linearities in terms of crossmodulation of spatial, spectral and temporal co-ordinates. The reproduction would thus be modified by all the practical inadequacies of even the best of loudspeakers. Further modification would result from distortion on the electrical signal, and there is reason to believe that distortion on the signal prior to its application to the loudspeaker can, in certain circumstances, lead to more acceptable reproduction<sup>1</sup>. (So much for the straight piece of wire with gain theory — Ed)

The loudspeaker distortion co-ordinates would then themselves be crossmodulated by similar distortion

---

... a perfect representation of the original sound may be less palatable than by first passing it through a distorting amplifier!

---

co-ordinates on the signal before the loudspeaker, leading to an acoustical result more closely related to the originating sound as humanly judged, than if the loudspeaker distortion alone were present.

The nature of the distortion produced by both the amplifier and loudspeaker is thus critical, so that different types of distortion would give different subjective impressions, which is not uncommon in a system of units of different distortion types. For example, the distortion from a radio tuner can interact with the distortion of an amplifier to which it is connected in such a way that the instrument-indicated *change* in the net distortion from the partnership, as the FM tuning is adjusted within the passband of a tuned signal, lacks subjective correlation. A test condition can be established where a fall in meter distortion is accompanied by an obvious rise in subjective distortion!

It thus seems to be perfectly feasible that after establishing the most acceptable reproduction by selection

---

... a fall in measured distortion may be accompanied by a rise in subjective distortion.

---

of the amplifier and loudspeaker partnership, a detraction in subjective acceptability could well result by changing either the amplifier or loudspeaker. I believe that this is one reason why a hi-fi system whose amplifier parameters

measure in advance of those of another may not necessarily audition any better. Indeed, it could be judged subjectively inferior!

It should be understood that we are now considering hi-fi at the top equipment level, where the amplifier distortion figure is, at least, *one* place to the right of the decimal point. Distortion from this class of amplifier seems to be falling more swiftly than the distortion from comparable class loudspeakers, which is not making it particularly easy to select suitable loudspeakers for the parameters of the amplifiers.

One amplifier from the Pioneer range comes to mind. In the lab this was found to have a very low level of distortion — one of the lowest ever measured — with harmonic components down to the distortion threshold of the measuring oscillator (0.002%) over the whole dynamic range, as measured with a wave analyser to read below the wideband noise power of the simple distortion factor meter. The intermodulation distortion was also correspondingly low and there was no crossover discontinuity; yet, in partnership with acclaimed well known loudspeakers, the amplifier was judged to be less subjectively acceptable than a counterpart of similar power, bandwidth, etc. but of much higher measured distortion.

Clearly, it is becoming more important to audition loudspeakers in partnership with the amplifier with which it is going to be used. The ultimate performance of the Pioneer, just exemplified, was eventually realised only after careful loudspeaker selection.

Most of the important parameters of amplifiers are measured into resistive loads, which does not make much sense because no loudspeaker presents a purely resistive load to an amplifier. The load analogue of a loudspeaker is an impedance composed of resistance, capacitance and inductance, but the impedance is not very easily defined since it is affected to some extent by the electrical drive signal and, of course, by the impedance of the separate units and nature of the frequency dividers. Different designs of loudspeakers present different loads to amplifiers, and it is not feasible to construct load analogues corresponding to all loudspeakers for testing amplifiers! Neither is it good for the loudspeakers (nor the neighbours!) to use real loudspeakers at test loads. Thus for testing we are back to R with, perhaps, a dash of C and/or L.

There has been a tendency for designers to optimise in terms of the smallest rise-time into resistive loads, and rise-times as small as 2  $\mu\text{sec.}$  can be seen in the specs. However, there can be a dramatic change in scene when the load is made reactive by the addition of C.

For example, in Fig. 1(a) the step function applied to the input of an amplifier was around 100 nsec. rise-time. The oscilloscope was set to 5  $\mu\text{sec./div.}$ , giving the display a rise-time, via the amplifier and *resistive* load, of about 2 to 3  $\mu\text{sec.}$ , corresponding to about 140 kHz —3 dB upper-frequency response.

The trace at (b) shows the same signal from the same amplifier, but this time with the load consisting of 8 ohms in parallel with 1  $\mu\text{F.}$  Rings as bad as this can certainly affect the tonal quality of an amplifier, depending on their amplitude and period. I have suggested<sup>2</sup> a definition of settling-time as an important parameter of amplifiers when measured into a reactive load arranged either to evoke the worst condition (i.e., by selecting shunt C for the most prolonged ring, when R corresponds to the rated load) or to the load analogue of the loudspeaker which will be used with the amplifier. The definition of settling-time under ref. 2, is the time elapsed from the application of the step-function to the time that the amplifier enters and remains within a  $\pm 5\%$  error band, corresponding to  $E_0 \pm \Delta E$ , where  $E_0$  is the final settling voltage. With the

# AMPLIFIER DISTORTION

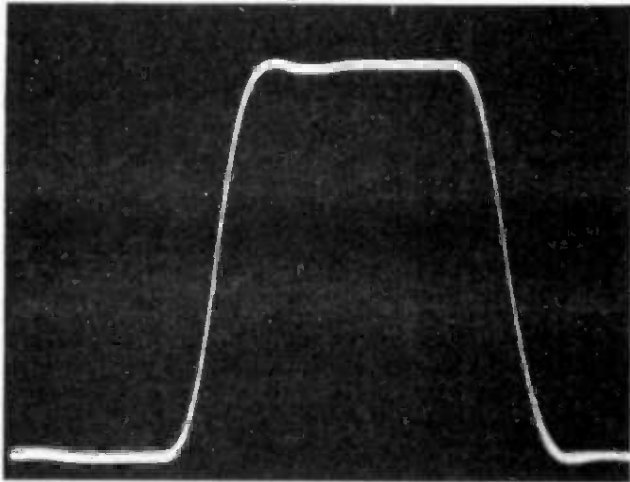


Fig. 1. Amplifier of small rise-time. (a) resistive rise-time about 4 $\mu$ sec.

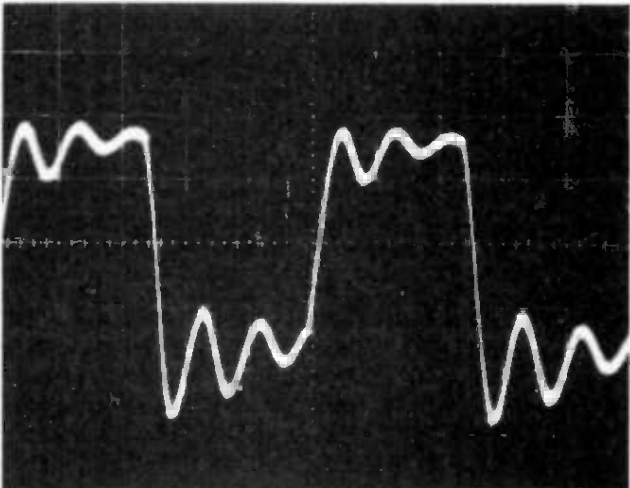


Fig. 1(b). Severe rings into reactance resulting in protracted 50 $\mu$ sec. settling-time.

settling-time referred to  $\Delta E/E_0 \times 100$ , it is in advance of 50  $\mu$ sec. in Fig. 1(b), which is unacceptable for hi-fi.

Too long a settling-time, therefore, appears to be another valid reason why some amplifiers fail to audition as well as might be expected from distortion measurements alone; also another reason why a change in loudspeaker may modify the subjective result (i.e., by changing the electrical transient performance of the amplifier).

The oscillograms in Fig. 2 reveal a more acceptable state of affairs. That at (a) is based on a 3  $\mu$ sec./div. sweep and corresponds to the resistive rise-time of a different amplifier of around 7  $\mu$ sec. (50 kHz — 3 dB response), (b) shows what happens when the resistive load is shunted by capacitance. There are no rings in this case, just a mild kink at the leading and trailing corners of the squarewave, with the settling-time corresponding to about 10  $\mu$ sec. (waveform on 20  $\mu$  sec./div. sweep). This shows the worst condition obtained with a shunt capacitance of 0.68  $\mu$ F.

There appears to be a definite tendency for amplifiers designed for dramatically small resistive rise-times (some as small as 1.8  $\mu$ sec. have been measured) to suffer prolonged settling-time as the result of severe rings into reactive loads, and hence tonal impairment when used with loudspeakers

constituting critical load conditions.

The value of designing for very small rise-times and hence for extended small-signal high-frequency response is thus obvious. A rise-time of 1.8  $\mu$ sec. implies that the amplifier is responsive well up to 200 kHz (the LW radio band!). Rise-time is related to the upper-frequency response by  $K/f$ , where K is a constant defined by the response characteristic of the amplifier or network, and f the upper-frequency where the response is 3 dB below the mid-spectrum response. When the upper-frequency roll-off approaches the so-called gaussian characteristic (i.e., when the -3 dB upper-frequency is approximately half the -12 dB frequency), K is close to 0.35; but it can range between 0.3 and 0.5, depending on the nature of the roll-off.

Of course the upper-frequency response needs to extend beyond audibility to accommodate the transient components of the music signal and thus to preserve the musical attack. However, it is difficult to argue in favour of a response much above 30 kHz, corresponding to around 12  $\mu$ sec. rise-time. We have seen that an extended response might encourage rings and increased settling-time. There is also the possibility that it might encourage 'blocking' following fast transient signals. This is called transient intermodulation distortion.

Transient components of music signals rarely exceed about 16  $\mu$ sec. owing to the limitations associated with the response and transfer characteristic of their sources. For example, a high quality FM transmission has an

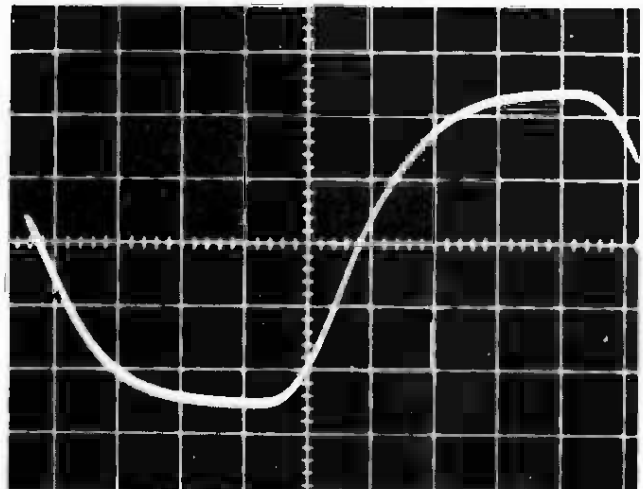


Fig. 2(a). Resistive rise-time about 7 $\mu$ sec.

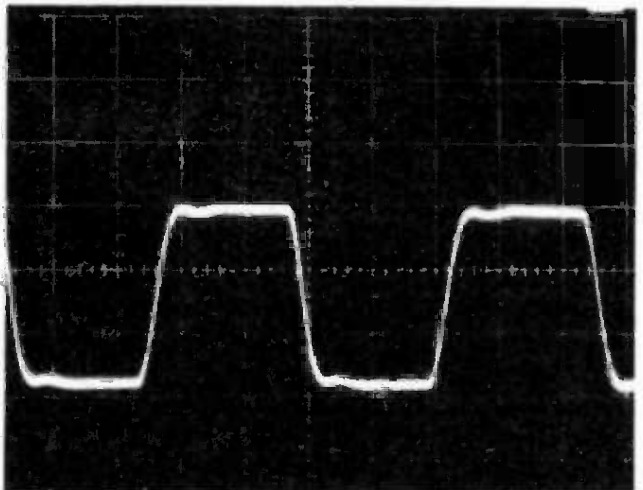


Fig. 2(b). Well controlled overshoot into reactance resulting in settling-time of 10 $\mu$ sec.

upper-frequency response limit of 15 KHz, with a swift fall into the 19 kHz pilot tone notch, thereby limiting the maximum equivalent rise-time to about 20  $\mu$ sec. Few gramophone records carry high energy information much above 18 kHz, and the same applies to tape recordings, so even from sources of this kind the music transients are not likely to be much faster than 17  $\mu$ sec. It is thus difficult to commend small-signal responses down to 2  $\mu$ sec. or less and up to 200 kHz or more!

Transient components of music signals rarely exceed 16  $\mu$ sec.

If one regards the source as a network of a given response, then, clearly, further limiting by a relatively slow amplifier response is undesirable. However, it must be remembered that the total rise-time ( $T_o$ ) of two cascaded networks of rise-times  $T_1$  and  $T_2$  is equal to the vector sum (not to the simple sum), such that  $T_o = \sqrt{T_1^2 + T_2^2}$ . Thus the degree of response limiting of the source signal by the amplifier is relatively small — certainly not calling for a rise-time as small as 2  $\mu$ sec.

Contemporary hi-fi amplifiers rely on negative feedback for extending and flattening the frequency response and for reducing non-linear distortion, particularly of the power amplifier section. The open-loop bandwidth of a power amplifier is dictated by the transistors which are available to drive the required audio power into reactive loudspeaker loads without veering too close to the secondary breakdown characteristic. This generally means that quite a lot of negative feedback must be applied to yield a viable closed-loop power response, and that lead and/or lag networks are necessary to maintain a reasonable stability

margin. Unless the ratio of the response of the power amplifier in the open-loop mode to the response of the preamplifier is of unity or greater value, the amplifier is likely to exhibit transient intermodulation distortion — tid, for short.

In other words, the overall frequency response of the hi-fi amplifier should be dictated by the roll-off of the preamplifier section and not by the power amplifier section<sup>3</sup>. This, then, clearly places a limit on the small-signal response or rise-time of the preamplifier, beyond which it is subjectively imprudent to engineer.

The mechanics of tid can be described in the following way. The total input to a feedback amplifier consists of the sum of two signals, the source signal proper and the error signal fed back antiphase. If the source signal is a very fast transient and the error signal slightly delayed owing to a relatively slow power amplifier response, the input stage of the power amplifier will momentarily receive a signal of greater amplitude than it is designed to accommodate, and severe overloading may ensue. The transient may thus be distorted, and the sudden 'shock' to the input stage may result in this closing down for a brief period, followed by a relatively slow recovery due to the action of circuit time-constants, so that information immediately following the transient is lost.

... overall frequency response should be determined by the roll off of the pre-amplifier ...

A method for the display of tid has been promulgated<sup>4</sup> and attempts have been made to measure it<sup>5</sup>, but so far there is no accepted standard for the measurement.

## ANDROMEDA ELECTRONICS LIMITED

3 Worcester Road, Malvern, Worcestershire tel. 63703

### DIGITAL I.C.'s

7400	E	14p
7401		15p
7402		15p
7403		15p
7404		18p
7405		18p
7406		43p
7407		43p
7408		18p
7409		20p
7410		15p
7420		15p
7430		15p
7440		15p
7441		92p
7470		29p
7472		18p
7473		36p
7474		33p
7490		30p
7493		50p
74121		36p
74123	£1.	02p

### LINEAR I.C.'s

741 8 PIN D.I.L.	36p
SIGNETICS 555	79p
NATIONAL LM380	£1. 35p
NATIONAL LM390-00K	
6 VOLT/800mA REGULATOR	£1. 30p

### TRANSISTORS

BC107	11p
BC108	13p
BC109	14p
2N3703	14p
2N3704	15p
BC182L	14p
BC212L	17p
2N1613	25p
RCA 40871	78p
RCA 40872	82p
2N3055	78p
2N3819	39p
TIS43	30p
TIC44	43p

### DIODES

1N4148/914	4p
1N4001	10p
1N4004	12p
1N4007	13p
G.I. 400vlt/1amp	40p
BRIDGE	
I.R. 200vlt/5amp	£1.50p
BRIDGE	
400mWt ZENERS	14p
ALL VALUES 3.3vlt	
to 33vlt	
TIL209 L.E.D.	35p
TIL211 L.E.D.	39p

### POTENTIOMETERS

AB45TYPE	
SKR -1M $\Omega$	
LOG AND LIN	28p
LOG AND LIN with	41p
switch	
LOG AND LIN GANGED	85p
PRESETS	
100 $\Omega$ - 2.2M $\Omega$ (E3SERIES)	
VERT, HOR, AND MIN	15p

### RESISTORS

0.5 WATT AND 0.25 WATT	
CARBON FILM E12 SERIES	2p

### CAPACITORS

10pF - 0.1uF (E6 SERIES)	
CERAMIC OR POLYESTER	5p

### AUDIO CONNECTORS

2 PIN D.I.N. PLUGS,	
CHASSIS AND LINE SKTS	10p
5 PIN 180° PLUGS	20p
5 PIN 180° CHASSIS SKTS	13p
5 PIN 180° LINE SKTS	21p
PHONO PLUGS (PLASTIC)	13p

MINIMUM ORDER 40p PLEASE — FREE CATALOGUE WITH EVERY ORDER  
ALL ORDERS PROCESSED IN UNDER 24 HOURS — TRADE ENQUIRIES WELCOME  
ALL PRICES INCLUDE V.A.T. AND POSTAGE — NO HIDDEN EXTRAS

# AMPLIFIER DISTORTION

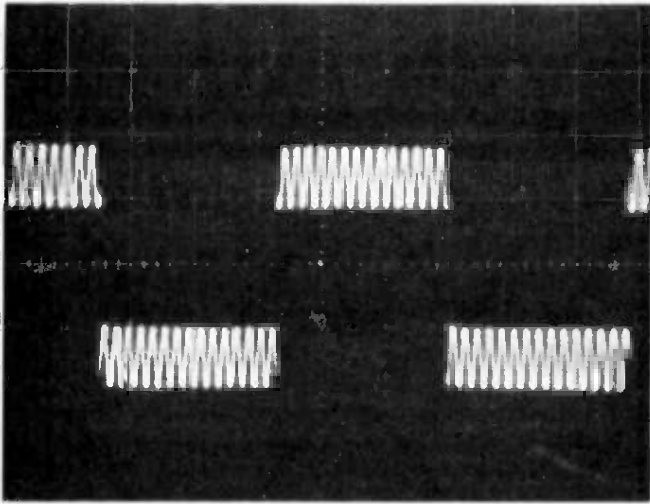


Fig. 3. Transient intermodulation distortion. (a) Test signal of square-wave plus sine wave.

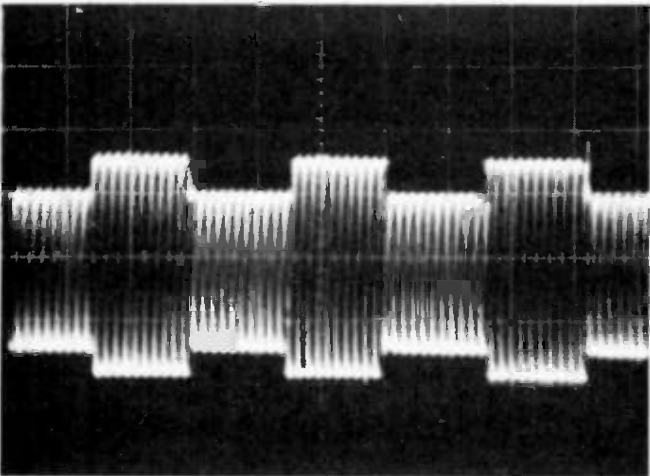


Fig. 3(b). Severe form of tid.

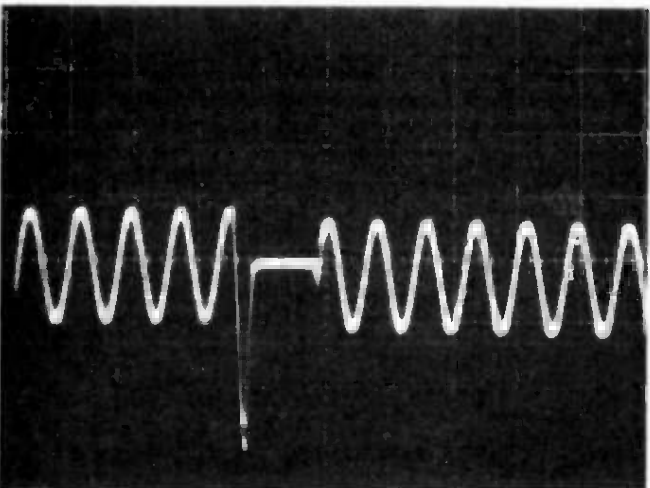


Fig. 3(c). Showing 'blocking' effect.

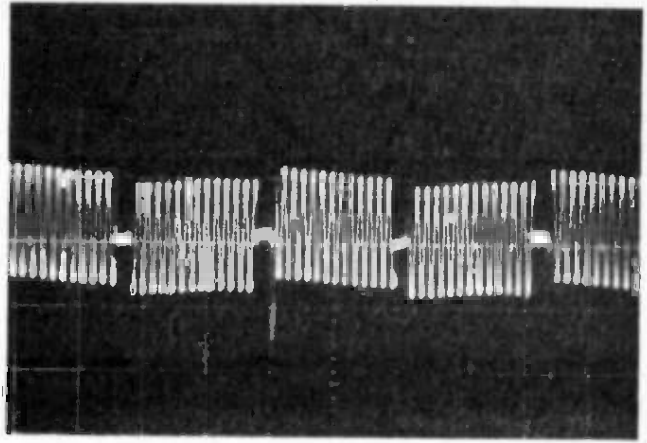


Fig. 3(d). 'Blocking' following each square wave transient.

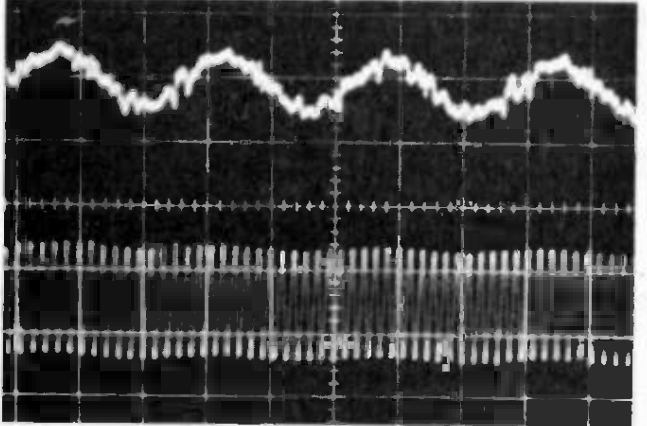


Fig. 3(e). Relative freedom from tid; bottom trace reconstituted sine wave; top trace distortion content of waveform.

The oscillograms in Fig. 3 may be of interest. Display (a) shows a test signal consisting of the addition of sine wave and square wave signals. This composite signal is applied to the input of the amplifier under test, and at the output the square wave component is cancelled out so that the sine wave component only is left for oscilloscope analysis. The square wave is cancelled by applying to a bridge circuit an inverted replica of the square wave component of the composite signal.

Display (b) shows a severe form of tid, giving asymmetrical sine wave components on the positive and negative going square wave cycles. Display (c) shows the 'blocking' effect following transients. (d) is a similar display but with less expansion. Display (e) shows the sine wave components fairly well fitted together on the bottom trace, thereby indicating minimal tid, and the distortion signal on the top trace, after passing through a distortion factor meter.

Transient intermodulation distortion tends to affect the quality of the reproduction more towards the full power drive of the amplifier, and is emphasised by treble lift. It manifests as stridence and harshness on signal peaks. While there is a real possibility of tid being responsible for lack of objective/subjective correlation (for it does not appear as a parameter in specifications or reviews), it can only occur when the rate of rise of a signal transient at the power amplifier input is in advance of the response speed of the power amplifier in open-loop mode. It is thus encouraged by a very small rise-time which is not matched by the response speed of the power amplifier, indicated by a poor or mediocre slew-rate.

It is becoming apparent that an amplifier of very low distortion factor may not necessarily produce better sound than a counterpart which fares objectively less well. In fact, the latter may audition better! Here, then, is still another reason why an amplifier of very low measured distortion may fail to perform subjectively as one might expect.

A clue to this paradox is contained in the oscillograms shown in Fig. 4. A distortion factor meter responds to the average energy in the distortion signal, but the ear is more critical of signal peaks composed of high-order harmonics than lower-order harmonics of higher energy. Display (a) indicates relatively high energy third-harmonic distortion, which would produce a fairly substantial reading on a distortion factor meter compared with display (b), where the energy is small but the amplitude of the peaks large at the crossover points. The distortion factor of (a) was around 0.25% and of (b) a mere 0.05%, yet the amplifier responsible for (a) was more acceptable in the listening room than that responsible for (b), in spite of (a) being the much greater readout!

When comparing amplifiers in terms of distortion factor, it is essential to take account of the *nature* of the distortion, since the figures alone rarely provide adequate comparative information. Alternatively, attention should be directed to the intermodulation distortion, for with suitably high measuring frequencies, such as  $f_1 = 5$  kHz and  $f_2 = 9$  kHz (1:1 ratio), a relatively high  $2f_1 - f_2$  readout is a sure indication that the crossover distortion is not very well tamed, particularly when this order increases as the power of the amplifier is reduced. Crossover distortion is generally more troublesome at low amplifier power, than at high power, the converse of tid.

Another form of bad crossover distortion is shown by display (c), where the energy is also high. This corresponds to about 0.4%, which is barely hi-fi. A commendable result is shown by display (d), the distortion being virtually down to noise threshold with no crossover artifacts; this corresponds to 0.02%.

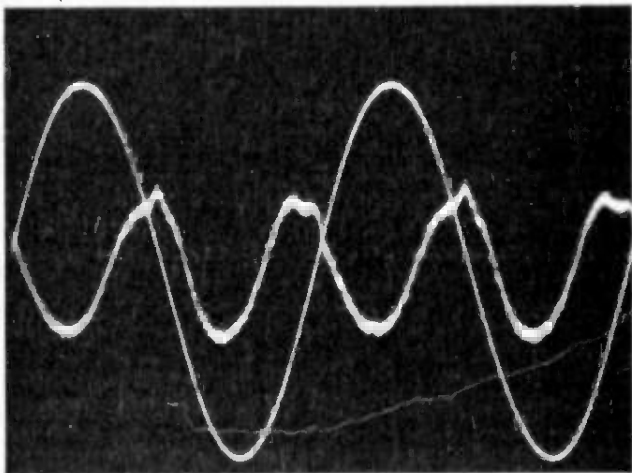


Fig. 4. Distortion factor oscillograms. (a) relatively high energy third-harmonic distortion.

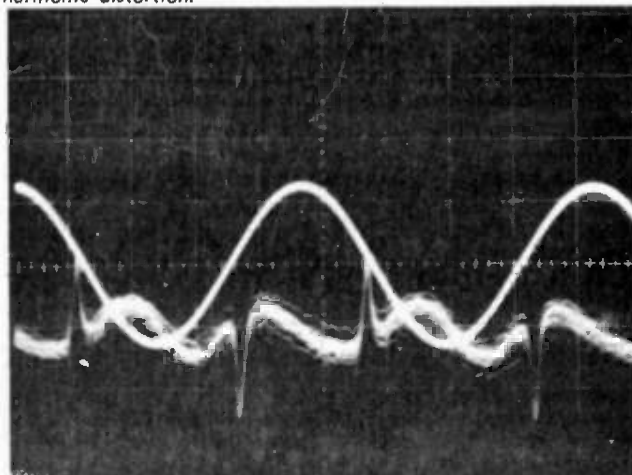


Fig. 4 (b). Low total energy but 'peaky' crossover.

... it is essential to take account of the nature of distortion — figures alone are insufficient.

Other factors responsible for the auditioning differences of amplifiers include asymmetrical overload allied with abnormally long recovery time-constant and changing quiescent current under dynamic conditions. The damping factor, too, has a bearing on the amplifier/loudspeaker partnership, and it is desirable for the amplifier's source impedance to remain at a low value right down to infrabass.

In conclusion, it is hoped that this article has given a few interesting points over which to ponder. We are learning all the time, which is half the fun of hi-fi.

#### References:

1. Richard C. Heyser, Geometrical Considerations of Subjective Audio, *JAES*, Vol. 22, No. 9, Nov. 74.
2. Gordon J. King, Settling-Time in Audio Amplifiers, *Wireless World*, March 75.
3. Matti Ojala, Circuit Design Modifications for Minimising Transient Intermodulation Distortion in Audio Amplifiers, *JAES*, June, 72, Vol. 20, No. 5, and Transient Distortion in Transistor Power Amplifiers, *IEE Transactions on Audio and Electroacoustics*, Vol. AU-18, Sept. 1970; also Transient Intermodulation Distortion in Commercial Audio Amplifiers, *JAES*, May 1974, Vol. 22, No. 4.
4. J R Stuart, An Approach to Audio Amplifier Design, *Wireless World*, Oct. 1973.
5. Gordon J. King, *The Audio Handbook*, published by Newnes-Butterworths.

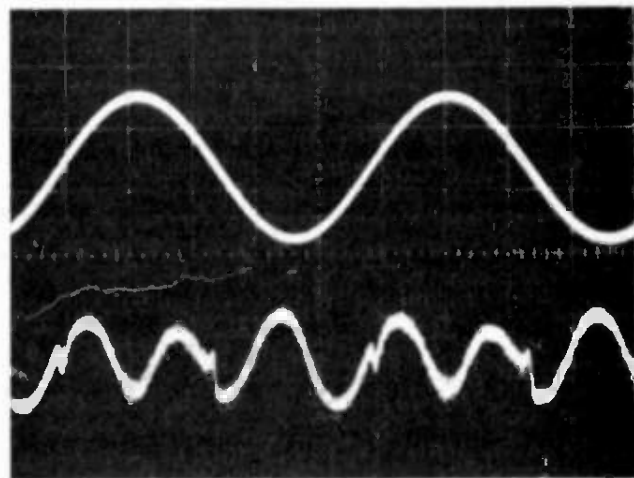


Fig. 4(c). High total energy, including crossover distortion.


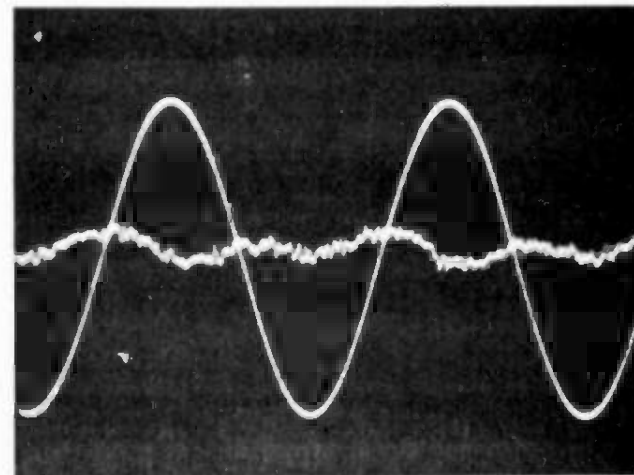


Fig. 4(d). Low energy harmonic distortion without crossover artifacts.

MHI-5309, MHI-5311, MHI-5318.


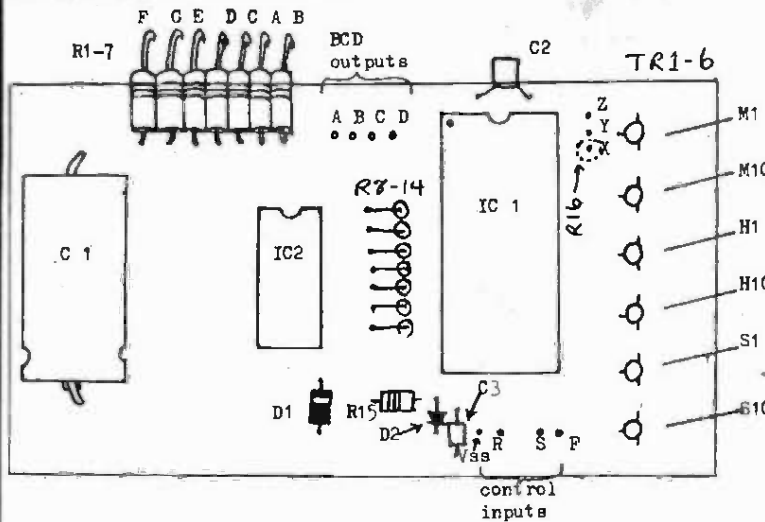


COMPONENTS LIST.

IC 1	MM5309 / 11 / 18	R1-R7	390 ohm 1/2 W
IC 2	CA3081	R8-R14	4K7 1/4 W
TR1-6	BC187 or BC213	R15-R16	100K 2 W
D1	IN4001	C1	500µF 25V
D2	IN914 or IN4148	C2	0.02µF
		C3	0.01µF

SW1-SW3 Push-ON, release-OFF

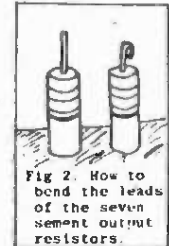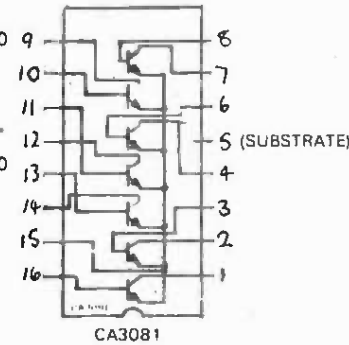TFMR Transformer must be able to deliver at least 150mA (100mA for 4 digits) and may be 6-0-6, 9-0-9, 12-0-12.



ASSEMBLY INSTRUCTIONS.

Take care when soldering not to bridge any of the line gaps between adjacent tracks on the PCB. Do not solder pins of ICs or transistors for too long or damage from overheating may occur. Never solder when power is applied. Insert and solder into place the 4 or 6 digit drive transistors. The board has been drilled to accept BC187 or BC213, if a unit with a different pinout is used then refer to makers data. Insert large smoothing capacitor (C1), being sure to check that it is the right way round. Solder into place. Insert and solder IN4001 (D1), again being careful about polarity. White band on diode indicates positive end. The power supply may be checked at this point by attaching the live transformer outputs to the points on the underside of PC board. The voltage across C1 should be within the range of 12-18v DC. Disconnect transformer. Insert and solder diode D2. Insert and solder the sixteen resistors and capacitors C2 & C3. Insert socket and solder. Insert the two ICs. DO NOT SOLDER — check the polarity, then solder. Solder wires on to the tags on the back of the board and lead these to the three push switches and to the transformer outputs (POWER OFF). The main clock board is now complete and ready for wiring to the display board. Only one end of resistors R1-R7 are soldered to the PCB, with the other ends sticking up to form connecting pins. Cut the resistor leads to about 1/4 inch long and then bend them back as shown in fig. 2. The wires to the display can now be hooked into the resistors and soldered into place. Cut the wires to be at least six inches long.

MHI-5309

A, B, C, D, are inverted BCD outputs  
 F, S, R, = Fast, Slow and Reset, V<sub>SS</sub> is the common for these switch inputs.  
 HOLD By connecting 50kHz to V<sub>DD</sub>.  
 100K between X & Y (R16).  
 Z connected to V<sub>DD</sub> to disable display

PIN CONNECTIONS.


MM5309.  
 As MM5311 except pin 16 is reset.

USES

MM5309— Stop watch or applications requiring a reset to zero function on both BCD & 7 seg outputs.  
 MM5311— General purpose clock chip interfacing to TTL or MOS.  
 MM5318— For applications requiring external digit selections such as micro processors, printers. Interfaces with MM5841 TV time display chip.

MHI-5311

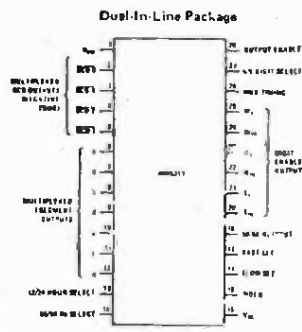as 5309 except  
 F, S, R = Fast, Slow, Hold.




MHI-5318.

as 5311 except.  
 X, Y, Z are ABC (in BCD format) of input digit address.  
 Break their track next to legend MHI-5309 on rear of PCB which connects Y to V<sub>DD</sub>.

MM5318.

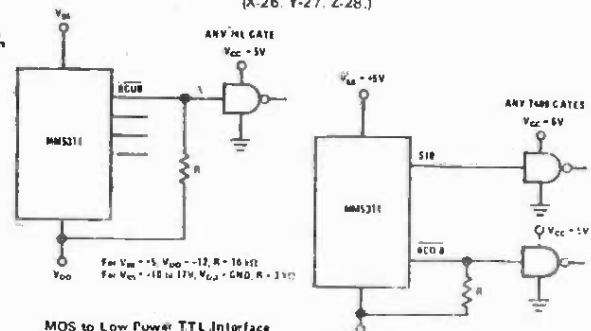As MM5311 except pins 26, 27 and 28 which are digit select lines.  
 (X-26, Y-27, Z-28.)



electrical characteristics T<sub>A</sub> within operating range. V<sub>SS</sub> = 0V, V<sub>DD</sub> = 5V, unless otherwise specified.


PARAMETER	CONDITIONS	MIN	TYP	MAX	UNITS
Power Supply Voltage	V <sub>SS</sub> (V <sub>DD</sub> = 0V)	11	14	19	V
Power Supply Current	V <sub>SS</sub> = +14V (No Output Loads)		8.0	15	mA
50/60 Hz Input Frequency		dc	50 or 60	60k	Hz
50/60 Hz Input Voltage		V <sub>SS</sub> - 2.0	V <sub>SS</sub> - 1.0	V <sub>SS</sub>	V
Logical High Level		-2.0	0	4.0	V
Logical Low Level					
Multiplex Frequency	Determined by External R & C	dc	1.0	60	kHz
All Logic Inputs					
Logical High Level	Internal 20kΩ Resistor to V <sub>SS</sub>		V <sub>SS</sub>		V
Logical Low Level		-2.0	0	3.0	V
BCD and 7 Segment Outputs					
Logical High Level	Loaded 75Ω to V <sub>DD</sub>	2.0	5.0	20	mA source
Logical Low Level				0.01	mA source
Digital Enable Outputs					
Logical High Level	Loaded 100Ω to V <sub>SS</sub>	5.0	10.0	0.3	mA source
Logical Low Level				75	mA sink

**BYWOOD ELECTRONICS**  
 68 EBBERS ROAD  
 HEMEL HEMPSTEAD  
 HERTS. HP3 9QR  
 0442 62757



# AUDIO LEVEL METER

**ETI PROJECT**  
**438**

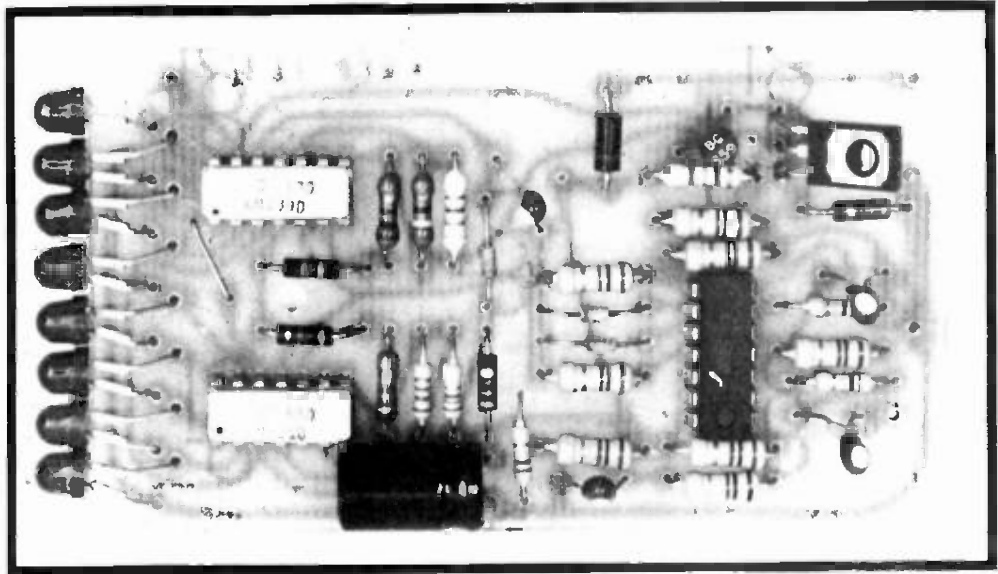

**Peak and average audio levels are indicated by a bar of light.**

HIGH-POWER amplifiers usually incorporate meters to indicate the output-power levels in each channel. These meters are often called VU meters but in most cases they resemble proper VU meters only in the way they are scaled.

A professional VU meter is the industry standard for measuring the levels of complex music waveforms. It has a scale marked from -20 to +3 VU (on a steady state signal VU correspond to dB) where '0' VU corresponds to a level of one milliwatt into 600 ohms. The meter has a carefully controlled time constant such that if a reference tone level is applied the pointer of the meter will take 0.3 seconds to reach 99% of the reference level, and will then

overshoot by not more than 1.5% and not less than 1.0%.

The professional VU meter is thus an instrument that has been designed to give a reasonable compromise between indicating the fast peaks and the average levels of a complex music waveform.

In contrast the meters fitted to some amplifiers have scales calibrated in VU but usually relying on the inertia of the meter movement to provide meter averaging. Apart from this the 0 VU point corresponds to the rated power output of the amplifier — not to 1 mW into 600 ohms (equivalent to 75 mW in 8 ohms). Strictly speaking therefore such meters should be called level or power meters, not VU meters.

Even the best of such meters are not

fast enough to indicate accurately the peak levels which occur in music and hence are useless for detecting the onset of amplifier clipping. This is vital as at clipping amplifier distortion rises rapidly.

One alternative is to use in addition to the level meter a clipping indicator that detects fast peaks which exceed a preset level. The ETI 417 OVER-LED project (Nov. 73 issue) was such an instrument — it flashed an LED when a music transient exceeded clipping level.

The circuit described in this project is best described as a 'level meter'. It uses an array of LED diodes set to illuminate at successively higher increments in music level. With this type of display an estimate can quite easily be made of channel balance, and all transients, no matter how fast, are detected and indicated.

## DESIGN FEATURES

The ETI 438 Level Meter can be arranged to indicate levels either in 'VU meter' format or in output power format. In the 'VU-meter' format the eight diodes light at 3 dB intervals from -18 to +3 VU where 0 VU corresponds to the nominal voltage required. Alternately as a power meter (remember that an amplifier cannot be driven beyond the clipping point) the top LED indicates maximum power and each lower LED indicates half the power of the one above it. The LEDs of the meter, could thus be labelled, for example (for a 100 watt amplifier) 100, 50, 25, 12.5 watts etc.


The fast attack time of the meter

## SPECIFICATION

Supply voltage	20 to 32 volts dc 15 to 20 volts dc
Supply current	16 mA dc approx.
Input sensitivity (VU meter)	500 k/v
Indication	8 LEDs 3 dB apart
Attack time	1 ms
Release time	0.5 sec.

# AUDIO LEVEL METER

Fig. 1. Circuit diagram of the level meter.

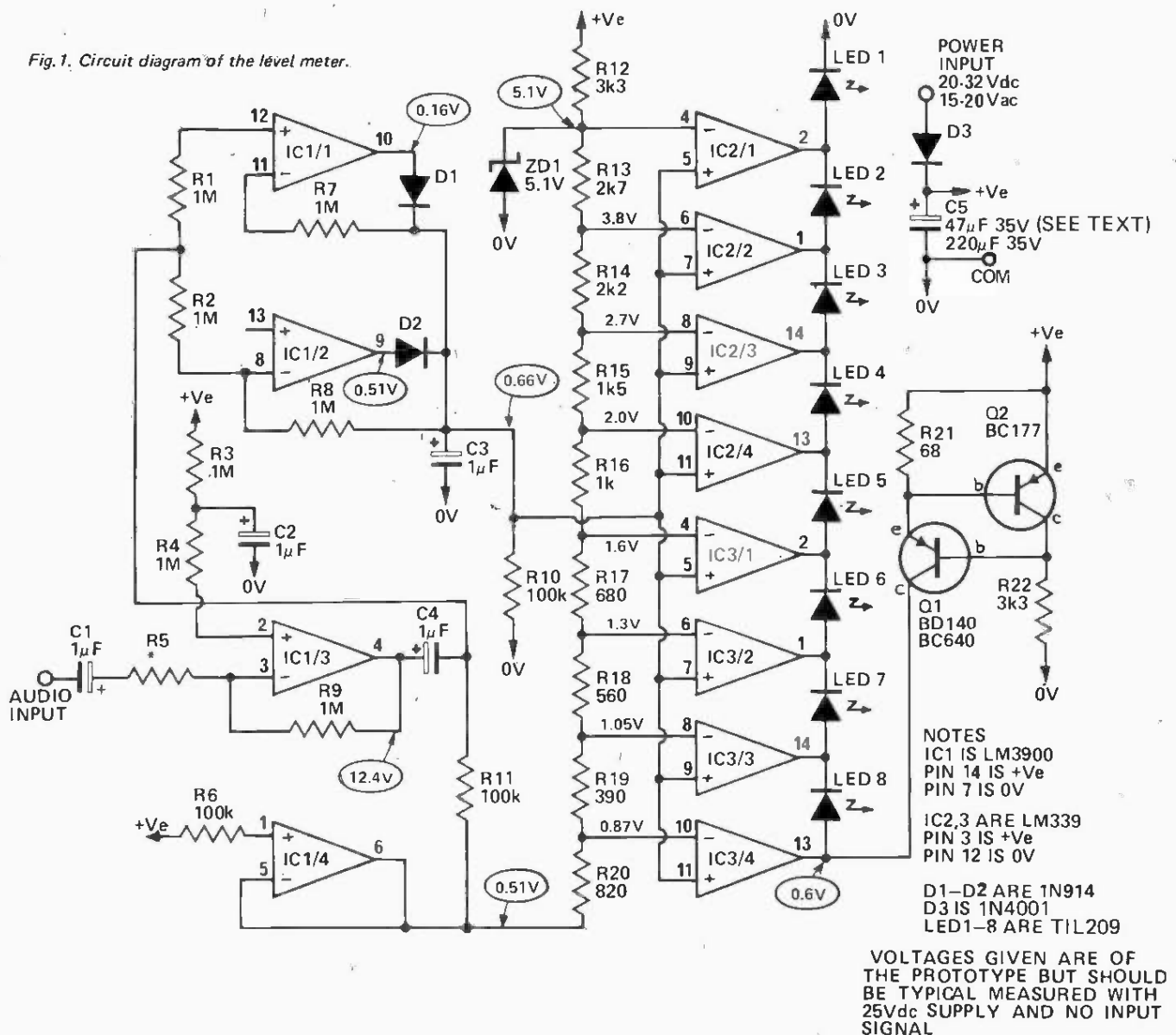

## HOW IT WORKS - ETI 438

Although the circuitry of the level meter looks complicated the complete instrument only uses three ICs. These are an LM3900 which is a quad amplifier and two LM339s which are quad voltage comparators.

The input signal is amplified and buffered by IC1/3 to provide about 2.5 volts out at 0 VU input. The value of R5 is selected to give the sensitivity required for amplifiers of different power outputs. The gain of this amplifier is equal to the ratio of R9/R5.

A positive peak detector, IC1/1, and an inverting negative peak detector, IC1/2, give an output which represents the absolute peak level. Capacitor C3 and resistor R10 provide the peak hold and decay time. IC1/4 provides compensation for the 0.6 volt offsets of the

\* LM3900 inputs.

The eight comparators are connected to a resistor divider chain the top of which is fed from a 5.1 volt supply which is stabilized by a zener. The resistor values are calculated to provide reference voltage steps at 3 dB intervals. The output of the detector is applied to all the non-inverting inputs of the comparators.

The LEDs are all connected in series and supplied with a constant current of 10 mA by the source consisting of Q1 and Q2. The outputs of the comparators are via open collector transistors which are "ON" if the input is lower than the reference voltage at the particular comparator input. With no input signal at all the comparators are all on thus shorting out all the LEDs so that none is on. As the input voltage rises the

comparators turn off in sequence allowing the 10 mA to flow through the LEDs. Thus as the voltage increases a bar of light of increasing height is formed by the LEDs.

The current drawn from the power supply is about 16 mA and is independent of the number of LEDs which are on. Supply voltage is not critical and may be anywhere between 20 and 32 volts. Providing the supply is between these limits the unit will also be insensitive to supply ripple. When working from a dc supply a 47 microfarad filter capacitor is required but if an ac supply is used then the capacitor should be increased to 220 microfarad to minimize ripple. A single diode is used to both rectify the ac input and to prevent damage due to accidental reversed polarity if a dc supply is used.

**PARTS LIST – ETI 438**

R21	Resistor	68 ohm	1/2W	5%
R19	"	390 ohm	1/2W	5%
R18	"	560 ohm	1/2W	5%
R17	"	680 ohm	1/2W	5%
R20	"	820 ohm	1/2W	5%
R16	"	1k	1/2W	5%
R15	"	1k5	1/2W	5%
R14	"	2k2	1/2W	5%
R13	"	2k7	1/2W	5%
R12,22	"	3k3	1/2W	5%
R6,10,11	Resistor	100k	1/2W	5%
R1,2,7,8	"	1M	1/2W	5%
R3,4,9	"	See Table 1	1/2W	5%
R5	"	See Table 1	1/2W	5%
C1,2,3,4	Capacitor	1 $\mu$ F	35V	
*C5A	"	47 $\mu$ F	35V	
*C5B	"	220 $\mu$ F	35V	


\* use 47  $\mu$ F for dc operation 220  $\mu$ F for ac operation

IC1 Integrated Circuit LM 3900  
 IC2,3 Integrated Circuit LM 339



D1,2 Diode IN914, BA318 or similar  
 D3 " IN4001 or similar  
 ZD1 Zener diode 5.1V 400 mW

Q1 Transistor BD 140,  
 Q2 " BC177,



LED 1-8 L.E.D. TIL209 or similar  
 PC board ETI 438

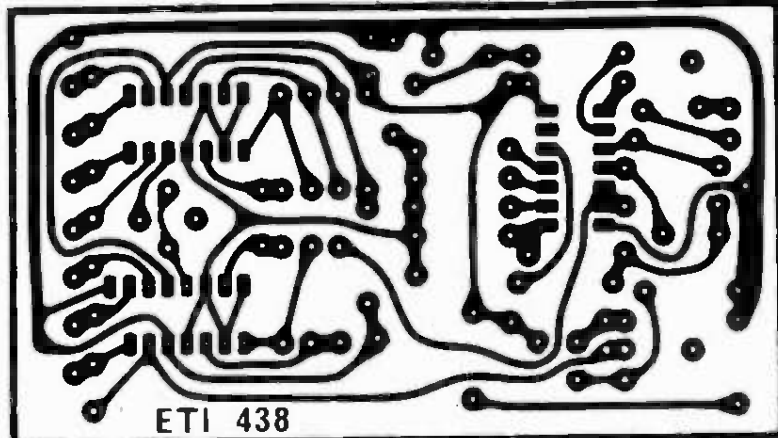


**ETI 438**

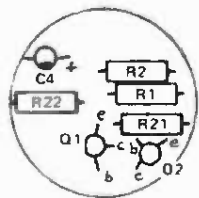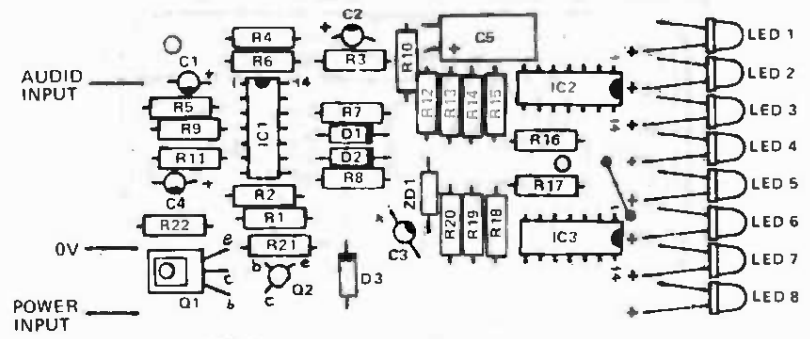


*Fig.2. Component overlay using BD140 for Q1. Circled diagram shows use of alternative BC640*

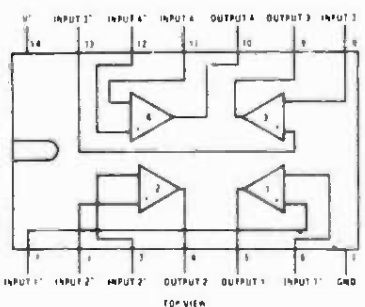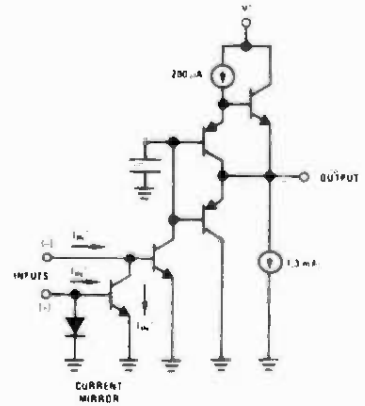

*Fig.4. Internal circuitry and pin connections of the LM3900 IC.*

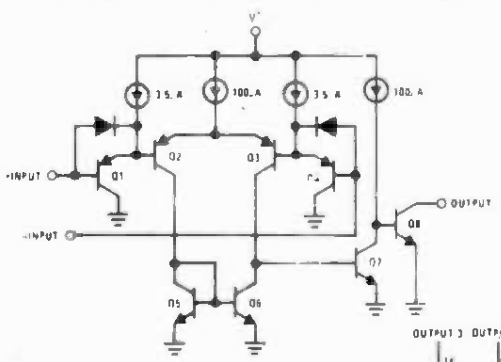

*Fig.3. Internal circuitry and pin connections of the LM339 IC.*

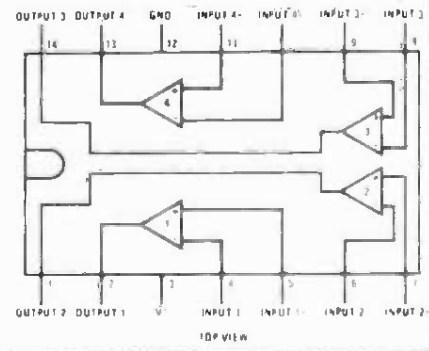

# AUDIO LEVEL METER

(less than one millisecond) ensures that even very short transients are detected, whilst the relatively slow release time (0.5 seconds) provides a reasonably-accurate, average - level indication.

In most previous designs for such meters, discrete transistors were used to build level detectors. Temperature effects and variations in gain led to inaccuracies and to calibration difficulties. These problems have largely been overcome in the ET1 438 meter by using the LM339 IC which contains four accurate level detectors in one package. Additionally the LM339 also has an open-collector output stage which enables a constant current supply for the LEDs to be used. Thus the current and LED brightness are the same no matter how many LEDs are alight.

If required the interval between LEDs may be altered by changing the values of R13 to R20. Thus for example, a 6 dB interval could be used. Additionally the display could be extended to 12 or even 16 diodes by adding comparators and LEDs and by substituting another divider chain for R20 (values would have to be calculated for the levels required). The positive inputs of the comparators would also be fed from C3 and R10.

A separate current source would be required as there is insufficient supply voltage available to light 16 LEDs in series. If the bottom LED in such a system indicates a level more than 30 dB down it may also be necessary to use a trimpot as the bottom resistor of the second divider chain to adjust for offsets etc.

The LM3900 is a quad differential amplifier which uses a current balancing technique at the input rather than the voltage balancing that is used with conventional operational amplifiers. Both the inputs "look" like the base-emitter junctions of normal transistors and both are at 0.6 volts with respect to ground. The currents into the two inputs must be equal if the output of the amplifier is to be in the linear region. In the case of IC1/3 the current into the positive input is set at about 12 microamps by R3 and R4. Current into the negative input is provided from the output by R9. If the current into the negative input is too low the output voltage will rise thus increasing the current into the negative input until balance is achieved. This self balancing ensures correct static biasing.

Gain is obtained by feeding a signal into R5 which adds or subtracts current into the negative input. For the amplifier to remain balanced there must be a corresponding shift in output voltage. The voltage gain is the ratio of R9 to R5.

TABLE 1B - POWER METER

FSD = 0 dB

R3, 4 and 9 are 100 k

POWER OUTPUT IN WATTS	VALUE OF R5		
	4 Ohms	8 Ohms	16 Ohms
5	150 k	200 k	270 k
10	200 k	270 k	390 k
15	240 k	330 k	470 k
20	270 k	390 k	560 k
25	330 k	430 k	620 k
30	360 k	470 k	680 k
40	390 k	560 k	820 k
50	430 k	620 k	910 k
75	560 k	750 k	1.1 M
100	620 k	910 k	1.2 M
150	750 k	1.1 M	1.5 M
200	910 k	1.2 M	1.8 M
250	1 M	1.5 M	2 M

$R5 = 32 \sqrt{PR}$  Where P = power in watts  
R = speaker impedance in Ohms.

## SPECIFICATION LM3900

Maximum supply voltage	32 V
Supply current	6 mA typical
Voltage gain	2800 V/V typical
Input current range	1 $\mu$ A - 1 mA
Current balance	0.9 - 1.1 at 200 $\mu$ A
Bias current	30 nA typical
Output current capability	18 mA source typical. 1.3 mA sink typical

The LM339 is a quad voltage comparator where the output of each is an NPN transistor which has an unterminated collector and its emitter connected to ground.

## SPECIFICATION LM339

Maximum supply voltage	36 V
Supply current	0.8 mA typical
Voltage gain	200 000 V/V typical
Offset voltage	2 mV typical
Bias current	25 nA typical
Response time	1.3 $\mu$ S typical
Output sink current	16 mA typical
Input common-mode voltage range	0 to (V <sup>+</sup> - 2 volts)

## CONSTRUCTION

The meter will most likely be mounted in an existing amplifier or piece of equipment and for this reason the board construction only is given.

Layout of components is non-critical but, as with any multiple IC device,

TABLE 1A - VU METER

FSD = +3 dB

R3, 4 and 9 are 1 megohm

SENSITIVITY	VALUE OF R5*
50 mV	22 k
100 mV	47 k
250 mV	120 k
500 mV	220 k
1 V	470 k

\*Sensitivity equals R5 x 500 000 ohms.

construction is greatly simplified by using the printed-circuit board specified. The usual precautions with polarities of components, such as capacitors, diodes, ICs and transistors should be observed. Some care must be taken when mounting the LEDs in order to obtain even spacing and good alignment. The long lead of the LED should be inserted in the hole furthest from the edge of the board. Put a slight curvature in the leads so that the LEDs can be aligned against the edge of the board (see photo). Take care not to bend the leads too often or too close to the body of the LED as the leads break very easily.

## CALIBRATION

Resistor R5 is selected from Table 1 and this will ensure a result within 10 percent of that required. Greater accuracy may be obtained by using a variable potentiometer, in series with R5. To adjust this potentiometer inject a signal (around 1 kHz) equal to 0 VU (VU meter) or maximum power ( $E = \sqrt{RP}$ , e.g. 4 ohms and 100 watts,  $E = 20$  volts) and adjust such that the second top LED (VU meter) or the top LED (power meter) just lights. ●

# The only 6 Function L.E.D. Watch Kit in the world . . .

for only **£18.95\***

## SABCHRON DIGITAL

Probably the only six-function LED watch kit available today, the Sabchron Digital offers more features than many other LED WATCHES. At the touch of a single button you see the exact hour, minute, second, month and day-of-month . . . PLUS an automatic date change memory which remembers whether the month contains 28, 30 or 31 days. Also, an AM/PM indicator which lights up while setting hours.

**12 36** HOURS/MINUTES

**36 47** MINUTES/SECONDS

**5 8** DATE

**12 P** AM/PM INDICATOR



## NEW CMOS IC CHIP

Containing the equivalent of over 1,500 transistors, this new IC chip features STATIC-PROTECTED TERMINALS — this means the IC can be handled safely with bare hands. It contains all the logic, decoding, multiplexing, display drive and counting circuits on a single silicon slice 1/50 square inch.

## QUARTZ CRYSTAL ACCURACY

The heart of the Sabchron Digital is a quartz crystal which provides a basic frequency of 32,768 Hz. This frequency is tuned to  $\pm 2$  parts per million via the trimmer capacitor and is divided in half 15 successive times to provide one incredibly accurate pulse every second. This means a timekeeping accuracy to  $\pm 5$  seconds per month. Careful adjustment of the trimmer can bring this accuracy to within  $\pm 1$  second per month or  $\pm 12$  seconds per year!

## ★ ORDERING INFORMATION

All prices shown in British £'s are approximate equivalents of the following U.S. Dollar prices. Complete watch kit (less case and bracelet) \$38.00. Gold-plated case only \$12.00. Total \$50.00 postpaid via registered airmail to customers in U.K., Eire and Canada. Other countries please add \$3.00 additional for postage/packing. REMITTANCE BY BANK DRAFT or INTERNATIONAL MONEY ORDER IN U.S. DOLLARS (available from all banks and national Giro offices).

# sabtronics

INTERNATIONAL

P.O. Box 64683, Dallas, Texas 75206, U.S.A.  
Tel. (214) 369-7309  
Business hours: GMT 15.00 to GMT 24.00 Hrs.

If you require any additional information please send S.A.E. and 2 International Reply Coupons.

## AUTOMATIC LED BRIGHTNESS

The Sabchron Digital features a special light sensor circuit which automatically adjusts LED display brightness according to varying light levels, thus conserving battery power. In a bright room the display brightens. In a dim room or darkness the display dims — a feature not found in many other LED watches.

## COMPLETE KIT


Contains all the components needed to build this space-age watch module, including solder, batteries and easy to follow assembly manual. If you can use a fine-point soldering iron and follow step-by-step assembly instructions, you can build the Sabchron Digital. If you have any problems, remember we're only as far as your nearest mailbox or telephone.

## PLUS THESE OTHER FEATURES

- ★ Long-life silver-oxide power cells last up to one full year with normal use.
- ★ Shock-protected, anti-magnetic.
- ★ Low component count — IC, LED package, Quartz crystal trimmer, photocell and two chip capacitors.
- ★ Universal module size — fits many LED watch cases (optional gold plated case available).
- ★ Easy time and date resetting — you can change the time or date without affecting the accuracy of other functions. A very useful feature when crossing time or date lines.
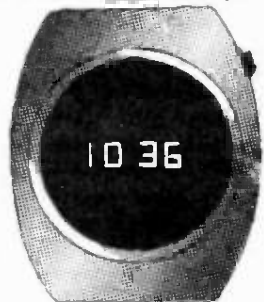
## OPTIONAL GOLD-PLATED CASE

The above price does not include a case or band. A gold-plated case as pictured (without bracelet) is available for £5.95. Note: The case is gold-plated, not "gold-tone", "gold-colour" or plastic. Elegantly styled and only slightly larger than a conventional watch, it is shown here actual size. Wear a time computer that looks like a watch, not vice versa. Cut out this case outline and try the size on your wrist.



COMPARE THE FEATURES OF THE SABCHRON DIGITAL TO OTHER LED WATCHES — THEN ASK YOURSELF WHAT OTHER LED WATCH OFFERS SO MUCH AT SUCH A REASONABLE PRICE. MAIL THE COUPON TODAY.

Sabtronics International, P.O. Box 64683, Dallas, Texas, 75206, U.S.A. Tel. (214) 369-7309.

Please send via Airmail (quantity) Sabchron Digital

6-function LED watch kits. Enclosed is a  Bank draft  International

Money Order for U.S. \$ total.

NAME

ADDRESS

(country)  
(etl/uk1)

# TELETYPE 28 - NEW SPECIAL PRICE

TELETYPE 28 without keyboard. Good condition (can be used as receive only) **£32.50**

TELETYPE 28 with housing, keyboard and Power supply **£45 ea.**

Limited quantities - information in process of being obtained - this may not be available when orders are dispatched but we guarantee to forward comprehensive information at the earliest possible time.

## Ex BEA

Control Units by Univac.

Consisting of 2 -50way plug/socket; 3 multiway switch assembly; a 2 & 4 decade push button assembly electrical reset; etc. Very good value. **£12.50 each.**

## ALWAYS A LARGE QUANTITY OF TEST EQUIPMENT, SPECIALISED UNITS, CHASSIS, ETC. CALL AND SEE

**FHACHI RAMP MODULE FX21.** 24 Volt DC input for 18 volt saw tooth output. Requires only external capacitor and 100K ohm potentiometer to control frequency range up to 100KHZ (eg 50 mfd electrolytic gives sweep of approx 1 cm per second). In or out sync capability. Price **£5.75. P. & P. 20p.**

**EX-MINISTRY CT436 Double Beam Oscilloscope DC-6 megs.** Max Sensitivity 10mv/cm. Small compact. Size 10 x 10 x 16 in. Suitable for Colour TV servicing. Price **£85 each** including copy of manual.

**FHACHI VCO MODULE FX11.** - 10MHZ-100KHZ. Size 2 x 1 1/2 x 3/4" H. Input 12V to 24V DC (not centre tapped). 18V input giving 10V constant amplitude output. Requires only 1 meg ohm potentiometer to tune entire range - or can be swept with a saw tooth input. Price **£5.75. P. & P. 20p.**

**SOLARTRON OSCILLOSCOPE TYPE CT316.** DC - 6 mc/s. Size 8 1/2" x 11" x 20". Very fine condition in Ministry transit cases. Complete with copy of manual. **£45 each.**

**GRATICULES.** 12 cm. by 14 cm. in High Quality plastic. 15p each P. & P. 8p.

**\*PANEL mounting lamp holders.** Red or green. 8p ea. **FIBRE GLASS PRINTED CIRCUIT BOARD.** Brand new. Single or Double sided. Any size 1 1/2p per sq. in. Postage 20p per order.

**\*LIGHT EMITTING DIODES** (Red) from Hewlett-Packard Brand New. 38p ea. Information: Sp. Holders 8p.

**METERS** by BIFAM type M 42, 25-0-25 micro amp Scaled 25-0-25 green, 250-0-250 red. linear. As new £2.95 ea. P. & P. 37p. **BLOCK PAPER CAPACITORS AVAILABLE.** S.A.E. with requirements

**\*PHOTOCELL equivalent OCP 71** 13p ea. **12" CRT MAGNETIC DEFLECTION.** Blue Trace, Yellow Afterglow (P7). Brand new, boxed, £4 each. Carriage £2.

**LOW FREQUENCY ANALYSER** 50Hz-50kHz ASSEMBLY AND INSTRUCTION INFORMATION S.A.E. PRICE **£27. P. & P. 75p** Board, modules and all components (excluding P.U.).

### \* TELEPHONES

**MODERN STYLE 706, BLACK OR TWO-TONE GREY.** £3.75 each. P. & P. 45p. **HANOSSETS** - complete with 2 insets and lead, £1.25 each. P. & P. 37p. **DIALS ONLY,** 50p each. P. & P. 25p.

**MODERN STANDARD TELEPHONES IN GREY OR BLACK WITH A PLACE TO PUT YOUR FINGERS LIKE THE 746** £3.00 each. P. & P. 45p.

**RELIANCE P.C.B. mounting** 270; 470; 500 ohms; 10K at 35p ea. **ALL BRAND NEW!** **VENNER Hour Meters** - 5 digit, wall mount - sealed case. Standard mains. £3.75 ea. P. & P. 55p.

**TRANSFORMERS.** All standard inputs. Gard/Parm/Part 450-400-0-400-450. 180 MA. 2 x 5 3v £3 ea.

**\*STANDARD 2 meg log pots.** Current type. 15p ea.

**INSTRUMENT 3in. Covert 5 ohm 35p ea. 50K and 100K 50p ea.**

### FANTASTIC VALUE

Miniature Transformer. Standard 240V input. 3Volt 1 amp output Brand New 65p each P. & P. 20p. Discount for quantity.

**\*CAPACITOR PACK 50** Brand new components only 80p. P. & P. 27p.

**\*P.C. MOUNT SKELETON PRE-SETS.** Screwdriver adjust 10, 5 and 2.5M at 2p ea. 1M, 500, 250 and 25K at 4p ea. Finger adjust 10, 5 and 2.5M at 3p ea. 1M, 500, 250 and 25K at 8p ea. Min P. & P. 15p.

**\*1000pf FEED THRU CAPACITORS.** Only still in stocks of 11-30p P. & P. 15p

**RECTANGULAR INSTRUMENT FANS.** American Ex-egu. Size 4 1/2 x 4 1/2 x 1 1/2" 115 Voh Very quiet £3 ea. P. & P. 47p

**DELIVERED TO YOUR DOOR** 1 cwt. of Electronic Scrap chassis boards, etc. No Rubbish. FOR ONLY **£4.50.** N. Ireland £2 extra.

**P.C.B. PACK S & D.** Quantity 2 sq. ft. - no tiny pieces. 50p plus P. & P. 20p

**\*TRIMMER PACK.** 2 Twin 50/200 pf ceramic; 2 Twin 10/80 pf ceramic; 2 min strips with 4 preset 5/20 pf on each; 3 air spaced preset 30/100 pf on ceramic base. All BRAND NEW 25p the LOT. P. & P. 15p

**ALMA precision resistors** 200K; 400K; 497K; 998K; 0-1% 27p ea.; 3-25K; 5-6K; 13K-0-1% 20p ea.

**BOURNS TRIMPOT POTENTIOMETERS.** 20; 50; 100; 200; 500 ohms; 1; 2; 2.5; 5; 10; 25K at 38p ea. ALL BRAND NEW

### RELAYS

Varley VP4 plastic covers 4 pole c/o 15K-33p; 58K-40p ea

**\*HIGH-VALUE-PRINTED BOARD PACK.** Hundreds of components, transistors, etc. - no two boards the same - no short-leaded transistor computer boards **£1.75** post paid

Large quantity LT, HT, EHT transformers and chokes.

**\*Vast quantity of good quality components - NO PASSING TRADE - so we offer 3 LB. OF ELECTRONIC GOODIES for £1.70 post paid**

**\*CRYSTALS.** Colour 4.43MHz. Brand New. £1.25 ea. P. & P. 15p

**\*Sensitive Trimmer** 3/30 pf Brand new. Qty 1-9 13p ea. P. & P. 15p; 10-99 10p ea. P. & P. 25p; 100-999 7p ea. P. & P. free

**HF Crystal Drive Unit** 19in. rack mount. Standard 240V input with superb crystal oven by Lalgear (no crystals) £5 ea. Carr. £2.00

**\*A.B. POTENTIOMETERS LIN.** 100K + 100K DUAL GANG. 25p each. Discount for quantities. P. & P. extra.

**\*METER PACKS** - 3 different meters for £2. P. & P. 55p.

**RESETTABLE COUNTERS** - 4 digit by Stonebridge/Sodaco. 1000ohm coil. £2 ea. P. & P. 35p.

## LOW FREQUENCY WOBBULATOR

**DON'T FORGET YOUR MANUALS S.A.E. WITH REQUIREMENTS**

For alignment of Receivers, Filters etc. 250KHz to 5 MHz, effective to 30 MHz on harmonics. Three controls—RF level sweep, width and frequency. Order LX63. Price **£8.50 P. & P. 35p.** As above but can have extended cover range down to 20KHz by addition of external capacitors. Order LX63E. Price **£11.50 P. & P. 35p.** Both models can be used with any general purpose oscilloscope. Requires 6-3V AC input. Supplied connected for automatic 50Hz sweeping. An external sweep voltage can be used instead. These units are encapsulated for additional reliability, with the exception of the controls (not cased, not calibrated).

### 20HZ to 200KHZ

#### SINE AND SQUARE WAVE GENERATOR

In four ranges. Wien bridge oscillator thermistor stabilised. Separate independent-sine and square wave amplitude controls. 3Mv max sine. 6V max square outputs. Completely assembled P.C. Board, ready to use. 9 to 12V supply required. **£8.85 each. P. & P. 35p.** Sine Wave only **£6.85 each. P. & P. 35p.**

### WIDE RANGE WOBBULATOR

5 MHz to 150 MHz (Useful harmonics up to 1.5 GHz) up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10:7 or TV IF alignment, filters; receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6-3V AC and use within minutes of receiving. All this for only **£6.75. P. & P. 35p.** (Not cased, not calibrated.)

## TRANSISTOR INVERTORS

TYPE A	TYPE B	TYPE C
Input: 12V DC Output: 1.3kV AC 1.5MA Price <b>£3.45</b>	Input: 12V DC Output: 1.3kV DC 1.5MA Price <b>£4.70</b>	Input 12V to 24V DC Output: 1.5kV to 4kV AC 0.5MA Price <b>£6.35</b>
Postage & Packing 36p		

### TYPE D

Input 12V to 24V DC  
Output: 14kV DC 100 micro amps at 24V  
Progressively reducing for lower input voltages  
Price **£11**

## MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SDLID STATE SWITCH.

2 HZ to 8 MHZ. Hook up a 9 volt battery and connect your scope and have two traces for **ONLY £6.25. P. & P. 25p.** **STILL AVAILABLE** our 20 MHZ version at **£9.75. P. & P. 25p.**

Unless stated - please add **£2.50 carriage to all units**  
**VALUE ADDED TAX** not included in prices—Goods marked with **★ 25% VAT**, otherwise **8%**  
Official Orders Welcomed, Gov./Educational Depts., Authorities, etc., otherwise Cash with Order

Open 9am to 5.30pm Mon to Sat.



# CHILTMHEAD LTD



7/9 ARTHUR ROAD, READING, BERKS. (rear Tech. College, Kings Road) Tel.: Reading 582605/65916

*Coming soon...*

# TOP PROJECTS No 3

Over 100 pages, packed with some of the best projects from ETI. No 1 is now a complete sell-out, No 2 is going like hot cakes. No 3 is due for publication in coincidence with the April issue...look out for details. £1.00+20p postage

## PULSAR, £13.95

WE ARE REPEATING OUR SPECIAL OFFER ON THIS DIGITAL ALARM CLOCK. WHEN WE RAN IT LAST YEAR IT PROVED TO BE ONE OF OUR MOST SUCCESSFUL OFFERS EVER! OUR PRICE INCLUDES VAT AND POST & PACKING.



Full size = 5in across and 3½in deep.

Pulsar shows the time 0.7in high on bright Planar Gas Discharge displays (there is a brightness control on the back). The dot on the left of the display shows AM/PM, and the flashing (1Hz) colon shows that the alarm and clock are working.

A bleeper alarm sounds until the clock is tipped forwards. Then the "snooze" facility can give you 5 minutes sleep before the alarm sounds again, and then another 5 minutes, etc, until you switch the alarm off. The clock also features a mains-failure indicator.

We have a large number of units in stock for this offer but please allow 28 days for delivery.

**PULSAR OFFER**  
ETI MAGAZINE  
36 Ebury Street,  
London SW1W 0LW.

I enclose cheque/P.O. for £13.95 (payable to ETI) for a Pulsar Alarm Clock.

NAME .....

ADDRESS .....


.....

.....

.....

Those not wishing to cut their magazine may order on their own notepaper.

# CANNIBALS and MISSIONARIES

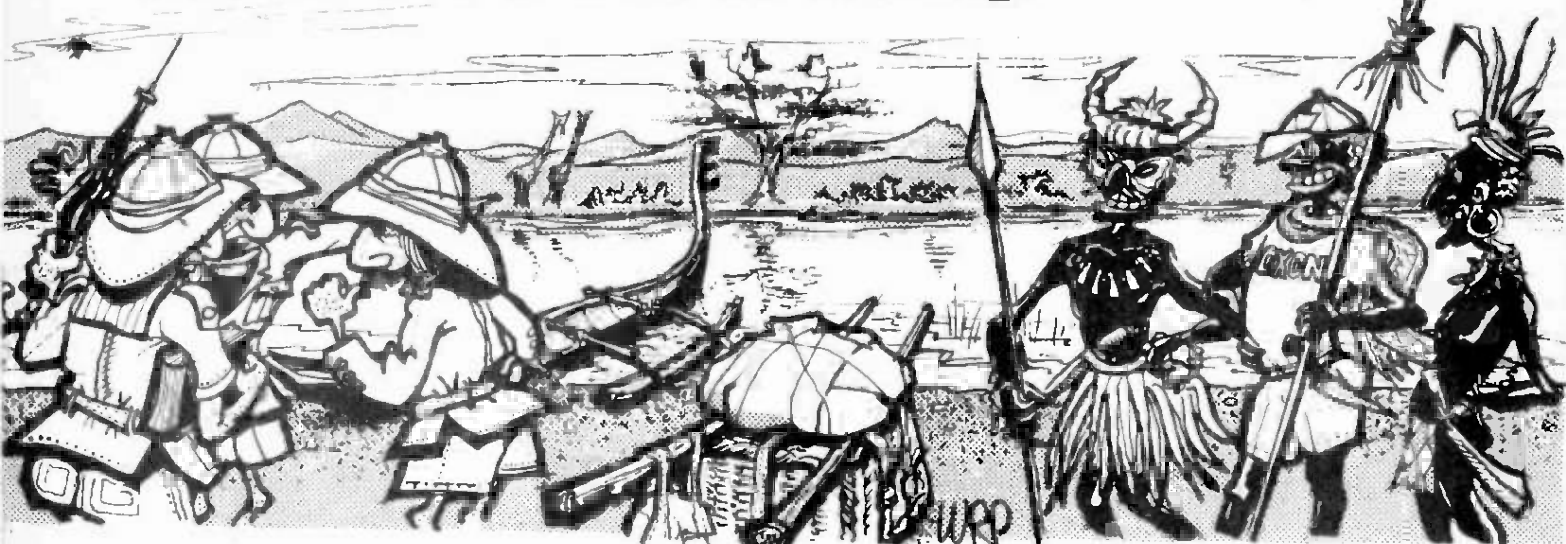

— the final river crossing problem *Designed by A.J. LOWE*

HERE'S a particularly perplexing problem provided for people with painstaking propensities. It's an electrical model of the puzzle which goes like this:

Three missionaries and three cannibals come to a river they want to cross. A little boat at the bank will carry only two people. All the missionaries can row, but only one of the cannibals can row — he'd been to Oxford. He also wears a red shirt! If at any time, on either side of the river, cannibals outnumber missionaries then the cannibals will eat the missionaries, which, understandably, the missionaries don't want. Problem: how do they cross safely?

In the model shown in Fig.1 the missionaries are represented by three switches M1, M2 and M3, and the cannibals by three switches C1, C2 and C3. The missionary switches have white levers. Two of the cannibal switches have black levers, but the switch representing the cannibal who wears a shirt and learned to row at Oxford — C2, has a red lever.

By operating the switches to represent crossings of the people involved — never more than two at a time as that's the limit of the boat, you try to solve the problem. If at any time a situation arises where, on either bank, cannibals outnumber missionaries then an alarm sounds and you've failed.

The circuitry detects situations where cannibals can satisfy their taste for eating missionaries, but it does not detect cheating — such as putting three people in the boat, or allowing a cannibal who can't row to be in the boat on his own.

## CONSTRUCTION

The prototype was assembled in a plastic box 140 mm x 100 mm x 75 mm high with an aluminium front panel. Modern telephone-type key switches were used each having four changeover switches on each side of the switch.

Figure 3 shows the bottom view of one of the switches and how its terminals are laid out. It also shows, by means of the arrow-headed lines, which terminals connect with the moving parts of the switches. The eight changeover switches which comprise one key switch have been lettered a to h for convenience and to tie in with the lettering in Fig.2.

Note carefully that the switches in Fig. 3 are shown making the circuits which they make when the switch lever is in its *central* position. When the switch lever is moved from the central position to the start side of the river it changes over only the switches on the opposite half of the switch — i.e. switched a, b, c, d. When the switch lever is moved from the centre position to the far side of the river it changes over only switches e, f, g, h.

These key switches can be bought with push-on handle covers of various colours. The prototype used white covers for the missionaries, black for two of the cannibals, and red for the cannibal C2 who wore a shirt (and went to Oxford).

Although key switches each containing a total of eight changeover switches were used in the original, actually it is only the missionaries who need all eight switches. The cannibals need only five changeovers, but it was

## 803

### HOW IT WORKS

The circuit is a switching logic circuit. See Fig. 2. The cell and buzzer are between the outer vertical rails, and if ever a way between these two rails is set up by the switches then the alarm sounds. The circuit shows all the switches in the *starting* position i.e. all the missionaries and cannibals are on the near bank. Note that when any person goes over the river *all* switches changeover. The customary dotted lines showing the connections between coupled switches have been omitted for clarity. Thus, if M1 crosses the river, switches M1a, M1b, M1c, M1d, M1e, M1f, M1g and M1h all changeover.

You can work out the circuits for the alarm to sound. Here are three examples. Suppose all three cannibals stay on the start side and M1 goes over. Then the cannibals outnumber the missionaries on the start side and so the alarm sounds — through C2b, C3b, C1b, M2d, M2c and M1d which has changed over.

Similarly, if M2 went over alone then the alarm would sound through C2b, C3b, C1b, M3d, M1d, M3b and M2a which has changed over.

And if M3 went over alone the alarm sounds through C2b, C3b, C1b, M1c, M2c, M1d and M3b which has changed over.

You can check all the 'alarm should sound' configurations on each bank of the river by visualising an alarming situation, cannibals outnumbering missionaries, and then tracing through the switches to find a circuit. Similarly the 'alarm should not sound' circuits, or rather 'no' circuits can be checked in the same way.



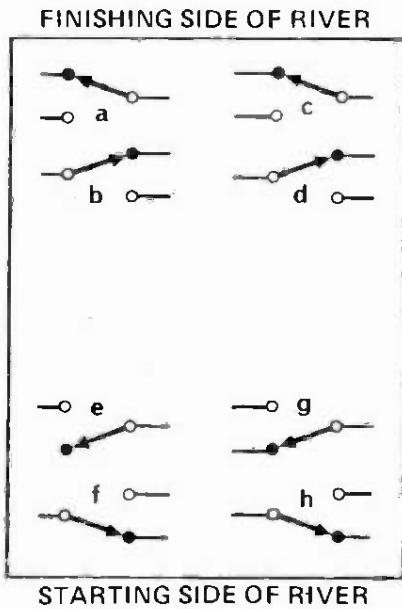


Fig. 3 Terminal layout on standard key switch with four changeover on each half. Contacts shown as being made in this diagram are with the lever in the central position.

thought simpler to buy six identical switches.

Those with access to disposal stores could probably buy enough old style key switches comparatively cheaply, to build up the necessary number of switching functions needed.

The panel aperture dimensions for a standard key switch are shown in Fig. 4.

The buzzer alarm and battery holder

**PARTS LIST**

Six standard phone type key switches type 4CL/4CL which means 4 change-over locking switches on each half of the switch.  
 e.g. Doram lever key switch type 338-018  
 One buzzer and battery holder — ex bicycle horn  
 One suitable box and panel  
 Hook up wire etc.

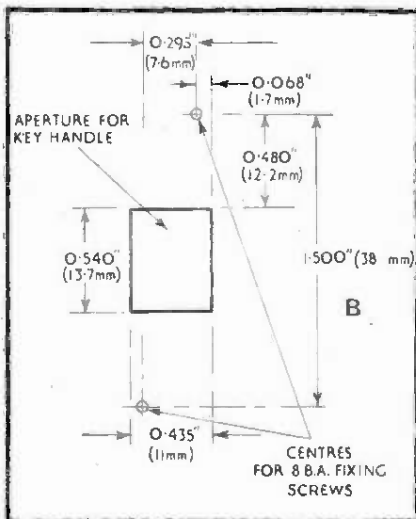


Fig. 4 Dimensions of aperture needed and hole positions for standard key switch.

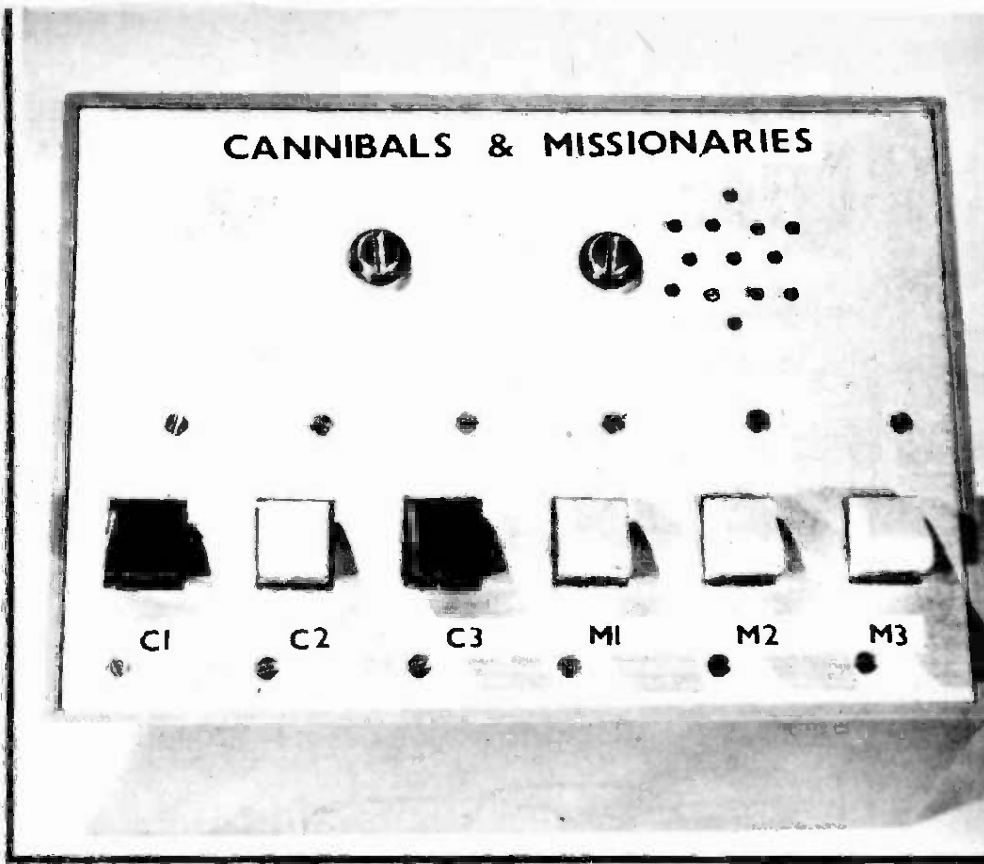


Fig. 1. The finished model. Lettering done with press-on letters on white Contact.

are all one piece — taken from a bicycle horn.

Wiring must be done carefully — very carefully! Bare wire was used in the prototype. Figure 5 shows the wiring diagram for the start side half of the switches and Fig. 6 shows the wiring of the other half. They are shown separately to minimise confusion. As can be seen from Figure 7, the switch

wiring needs considerable care. On each of Fig. 5 and Fig. 6 one lead is marked 'To Buzzer' and another 'To battery —ve'. These leads, i.e. both buzzer leads are joined together and to the buzzer; and both battery —ve leads are joined together and run to battery —ve.

When wiring up — work logically. Start with switch M3 which is on the

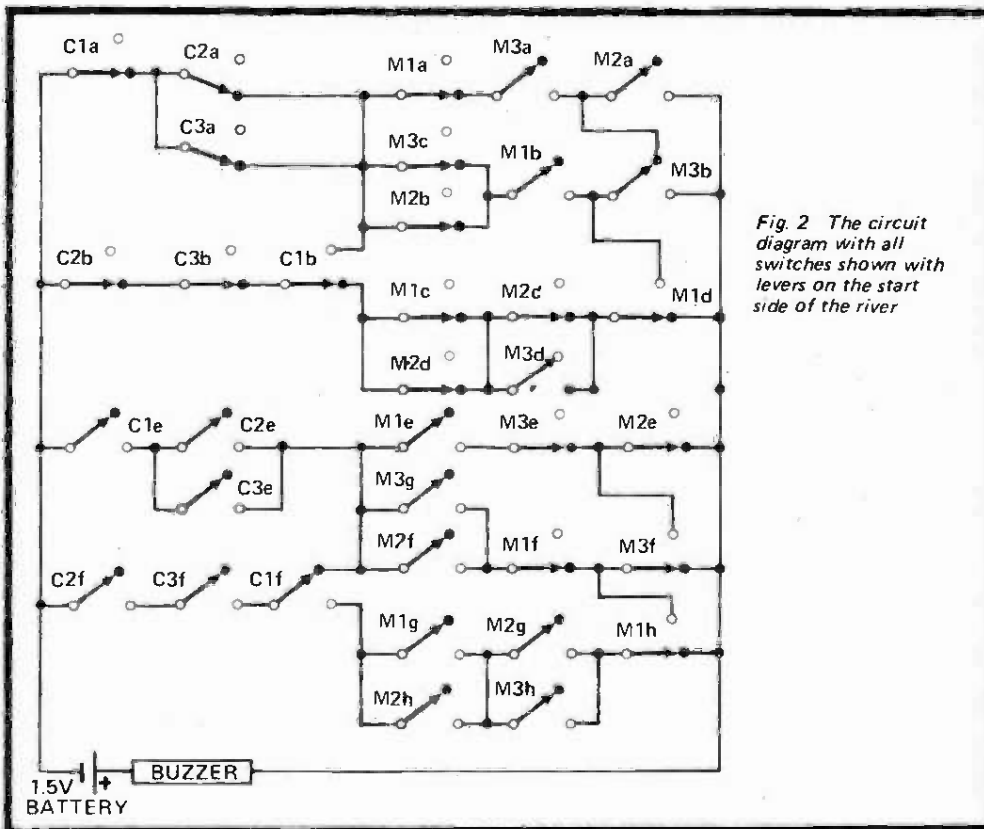


Fig. 2 The circuit diagram with all switches shown with levers on the start side of the river

# CANNIBALS and MISSIONARIES

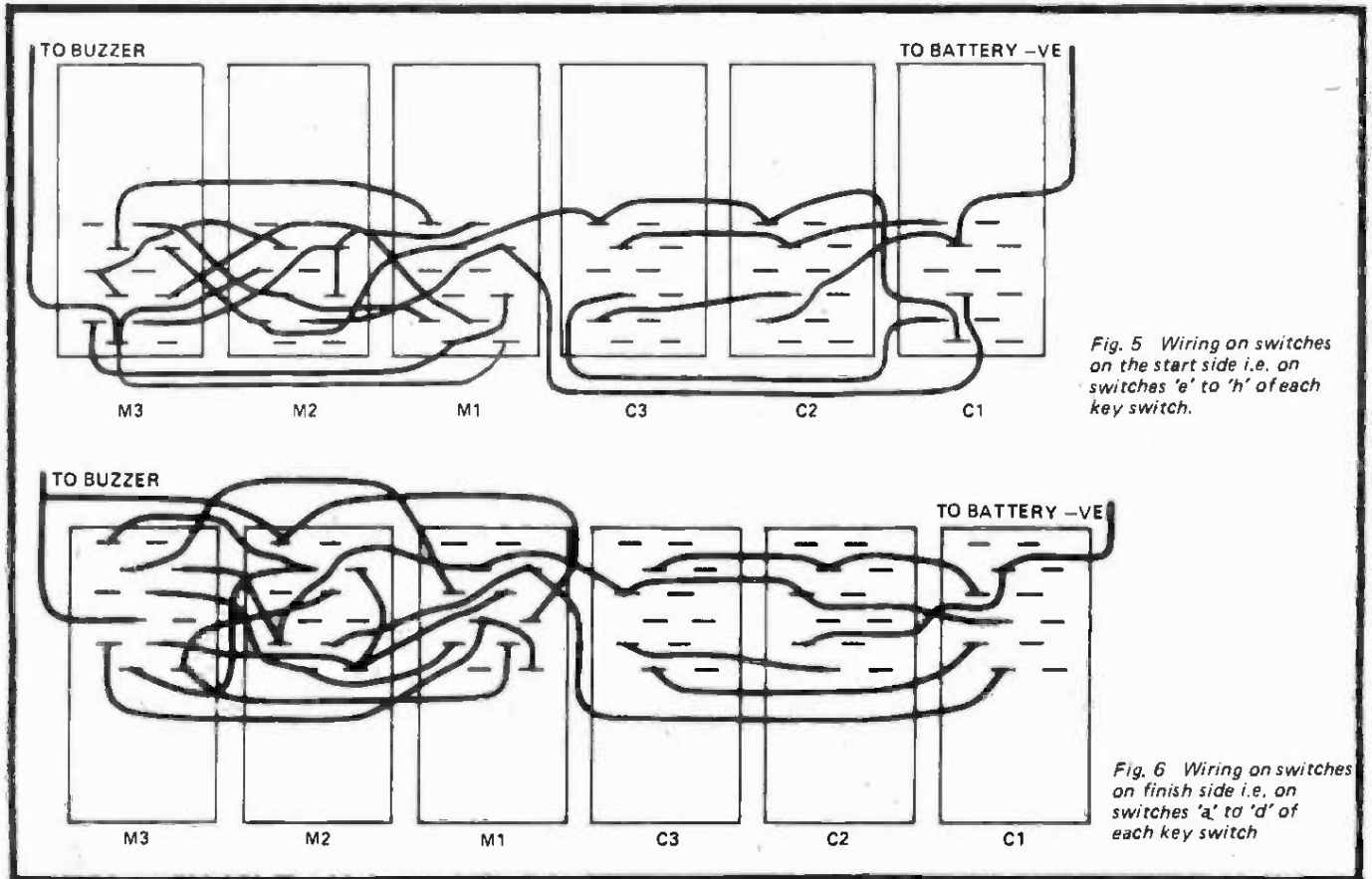


Fig. 5 Wiring on switches on the start side i.e. on switches 'e' to 'h' of each key switch.

Fig. 6 Wiring on switches on finish side i.e. on switches 'a' to 'd' of each key switch

left when the panel is upside down. Start with the top left hand terminal and make all connections to it. Then move down each terminal in turn down the left hand row of terminals. Proceed row by row to the right

making and checking connections to each terminal. It's a good idea to cross off with a pencil, each connection shown on the wiring diagrams, as soon as that connection has been made on the switches. Be sure not to miss the

short connection between switches M3e and M3f.

If you want to check through the wiring diagrams, the circuit, and the switch diagram — bear in mind that the switch diagram shows connections with the switch lever in the central position, and the circuit diagram shows the connections with the levers in the start side position.

On completion of the wiring and after insertion of the cell, the puzzle should work. Check out all the alarm situations on both banks and see that the alarm sounds when it should. Also check the no-alarm situations — i.e. when cannibals do not outnumber missionaries on either bank of the river.

Fault finding is not as daunting as it may appear at first. A logical working through the circuit diagram should help to pinpoint any problem.

## HAVE A GO

Having built the puzzle — try to solve it. It's far from easy. If all else fails — check the correct answer which is hidden somewhere in this issue.



Fig. 7 Underside view of the panel.

## P.E. CAR CLOCK KIT AVAILABLE

Send s.a.b. for details/prices, etc.

### ADVANCED ALARM CLOCK KIT

Complete kit including attractive slim case with perspex panel for 6 digit alarm clock with beep alarm, snooze and automatic intensity control, high brightness display driving; uses MK50253 IC and Jumbo 0.5in LEDs Kit also includes PCBs, active and passive components, IC skt min transformer, switches, flat cable, loudspeaker, mains cable and plug. Full instructions. Crystal control/battery back-up and touch switch snooze and alarm are optional add-ons **£27.31**

### SIMPLE & ATTRACTIVE 4-digit CLOCK KIT

(As featured in January Everyday Electronics) Ideal kit for the less experienced constructor, kit includes IC, pleasing 1/2" green display with colon, PCB, miniature transformer, slim white case with perspex front panel, and all other components except mains cable and plug. Full instructions **£15.89**

### CRYSTAL TIMEBASE KIT

All components including PCB (47mm x 59mm) to provide 50cps for clock ICs giving time accurate to a few seconds a month. Kit includes PCB, 32 768 kHz miniature watch crystal, trimmer, 3 CMOS ICs and sockets, Cs, Rs **£6.28**

### STOPWATCH

Complete Kit for Stopwatch (as in December ET1); choose 6 digit range from tens of hours to milliseconds Contents Verocase 75/1410J, red perspex front panel, Manganese batteries, clips, transistors, diodes, wiring pins, screws, sockets, pin-header, CMOS resistors, capacitors, 5.12MHz crystal, trimmer, PCBs, 6 x MAN3M displays With instructions, component layout, etc. **£31.80**

**STOPWATCH WITH ONE LATCH:** As above, but kit also includes facility to repeatedly freeze one set of displays with count continuing on the other set **£47.71**

**ADD VAT at 8% to all Prices in this advertisement.** 15p P&P on orders under £3 free on orders over £3. Orders sent by 1st Class Post. Exports No VAT 35p (Europe) £1 (Overseas) for Air Mail P&P (any excess refunded). Full Price List and Data with any order, or on request (phone or send s.a.b.)

**Official Orders welcomed,** written, phoned or telexed from Univs Polys Nat Inds Govt Departments Companies, etc. **Fastest Delivery for R&D.**

**SINTEL**

**53a Aston Street, Oxford**

**Tel. 0865 49791**

**Telex: 837650. A/B ELECTRONIC OXFORD**

## CMOS

CMOS from the leading manufacturers only

CD4000A	0.17	CD4028A	0.74	CD4053A	0.77	CD4086B	0.59
CD4001A	0.17	CD4029A	0.94	CD4054A	0.95	CD4089B	1.27
CD4002A	0.17	CD4030A	0.46	CD4055A	1.08	CD4093B	0.66
CD4006A	0.97	CD4031A	1.82	CD4056A	1.08	CD4094B	1.53
CD4007A	0.17	CD4032A	0.88	CD4057A	20.35	CD4095B	0.86
CD4008A	0.79	CD4033A	1.14	CD4059A	10.64	CD4096B	0.86
CD4009A	0.46	CD4034A	1.56	CD4060A	0.92	CD4099B	1.50
CD4010A	0.46	CD4035A	0.97	CD4061A	16.43	CD4502B	0.98
CD4011A	0.17	CD4036A	1.82	CD4062A	7.33	CD4510B	1.12
CD4012A	0.17	CD4037A	0.78	CD4063B	0.90	CD4511B	1.28
CD4013A	0.46	CD4038A	0.88	CD4066A	0.58	CD4514B	2.56
CD4014A	0.83	CD4039A	2.86	CD4068B	0.18	CD4515B	2.56
CD4015A	0.83	CD4040A	0.88	CD4069B	0.18	CD4516B	1.12
CD4016A	0.46	CD4041A	0.69	CD4070B	0.18	CD4518B	1.03
CD4017A	0.83	CD4042A	0.89	CD4071B	0.18	CD4520B	1.03
CD4018A	0.83	CD4043A	0.83	CD4071B	0.18	CD4527B	1.30
CD4019A	0.46	CD4044A	0.77	CD4072B	0.18	CD4532B	1.16
CD4020A	0.92	CD4045A	1.15	CD4073B	0.18	CD4555B	0.74
CD4021A	0.83	CD4046A	1.10	CD4075B	0.18	CD4558B	0.74
CD4022A	0.79	CD4047A	0.74	CD4076B	1.27	MC1450B	2.37
CD4023A	0.17	CD4048A	0.46	CD4077B	0.18	MC1452B	0.86
CD4024A	0.64	CD4049A	0.46	CD4078B	0.18	MC1453A	6.04
CD4025A	0.17	CD4050A	0.46	CD4081B	0.18	MC1455A	4.07
CD4026A	1.42	CD4051A	0.77	CD4082B	0.18	MC1456B	1.21
CD4027A	0.46	CD4052A	0.77	CD4085B	0.59	MCM1455A	8.05

**RCA 1975 CMOS Databook:** 400 pages of data sheets and 200 pages of circuits applications and other useful information **£2.67** (Add no VAT—post free)

**Motorola McMOS Databook (Volume 5, Series A)**

**£2.77** (Add no VAT—post free)

CLOCK ICs	DISPLAYS	VEROCASES
MK50253 <b>£5.60</b>	DL704E <b>85p</b>	75/1410J <b>£2.64</b>
MK50250 <b>£5.00</b>	FN0500 <b>£1.02</b>	(205 x 140 x 40mm)
MM5314 <b>£4.44</b>	FN05000 <b>95p</b>	75/14110 <b>£2.94</b>
AY51202 <b>£4.76</b>	MAN3M <b>48p</b>	(205 x 140 x 75mm)
AY51224 <b>£3.68</b>	5LT01 <b>£5.80</b>	<b>Flat Cable</b>
MK5030M <b>£12.50</b>	LCD <b>£9.40</b>	20-way <b>£1 per m.</b>

**DISPLAY PCBs** (each fits neatly into Verocase J) for clock with 6 x FND500, for clock with 6 x OL704, for counter with up to 8 x FND500, for counter with up to 8 x DL704 these four are **£1.35** each, for clock with 4 x FND500 **90p.**

**IC SOCKET PINS.** Lowest cost sockets for CMOS, TTL, ICs, Displays Strip of 100 pins for **50p**, 400 for **£2**, 1,000 for **£4**, 3,000 for **£10.50.**

# Sparkrite mk2

The tried, tested, proven, reliable, complete, professional, capacitive discharge, **Electronic Ignition Kit**

Sparkrite™ was voted best of 8 systems tested by Popular Motoring Magazine

## ORDER NOW

TO **ELECTRONIC DESIGN ASSOCIATES DEPT ET1 3**  
82 Bath Street, Walsall, WS1 3DE, Phone 338...

FROM Name \_\_\_\_\_

Address \_\_\_\_\_

Qty \_\_\_\_\_

SPARKRITE MK 2 DIY Assembly kit @ **£18.93**

SPARKRITE MK 2 Ready Built Negative earth @ **£13.88**

SPARKRITE MK 2 Ready Built Positive earth @ **£13.88**

Ignition changeover switches @ **£2.98**

R.P.M. Limit systems in the above units @ **£2.42**

I enclose cheque/P.O.s for £ \_\_\_\_\_

Cheque No \_\_\_\_\_

(Send SAE H brochures only required)

Sparkrite MK2 is a high performance, high quality, capacitive discharge electronic ignition system.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire because contact breaker bounce is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of blowing the transistors or the SCR. (Many capacitive discharge ignitions are not completely foolproof in this respect.)

Sparkrite can therefore give you—up to 20% better fuel consumption, instant all weather starting, cleaner plugs, they last up to 5 times longer without attention, faster acceleration, higher top speeds, longer coil and battery life, efficient fuel burning and less air pollution, smoother running, continual peak performance.

**THE KIT COMPRISES EVERYTHING NEEDED**  
Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year

guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth and 10 page installation instructions.

### OPTIONAL EXTRAS

**Electronic R.P.M. limitation.**  
This can be included in the unit or mounted over it, it is an advantage to most companies, hire firms, high performance drivers etc.

**Electronic/conventional ignition switch.**  
Gives instant changeover from Sparkrite ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device. Includes switch connectors mounting bracket and instructions. Cables included.

### PRICES

DIY assembly kit **£10.93** incl VAT post and packing.  
Ready built unit **£13.88** incl V.A.T. post and packing (Bath to fit all vehicles with coil/distributor ignition up to 8 cylinders.)

Switch for instant changeover from Sparkrite ignition to conventional ignition **£2.98** incl V.A.T. post and packing.  
R.P.M. limiting control **£2.42** incl V.A.T. post and packing (Fitted in case on ready built unit, dashboard mounting optional.)

**CALLERS WELCOME**


# DIGITAL CLOCK

MATCHED CHIP & DISPLAY

**£9.56**  
Inc. VAT, Post & Packing


**DISPLAY**  
Only Price  
**£6.36**  
Inc. VAT

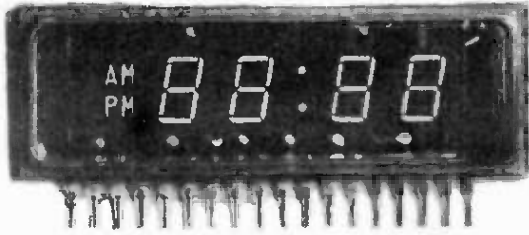**FUTABA 5-LT-01. 7 SEGMENT**  
Phosphor Diode. 12.5mm Digit  
AM/PM and colon



**CHIP**  
Only Price  
**£5.50**  
Inc. VAT

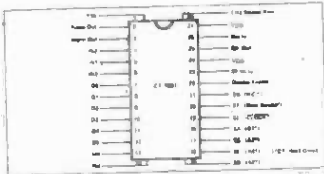**CALTEX CT7001. MOS LSI**  
28/30/31 Day Calendar  
24-hour Clock  
Snooze Alarm  
Clock Radio Feature  
Easily Settable Counters



TRANSFORMER — £2.50 INC. VAT

Payment with order

**IMTECH PRODUCTS LTD.**  
IMP HOUSE, ASHFORD ROAD, ASHFORD, MIDDX.  
Telephone: Ashford 44211  
Telex: 936291

# ELECTROVALUE

## The good components service

In relatively few years, Electrovalue has risen to a position of pre-eminence as mail-order (and industrial) suppliers of semi-conductors, components, accessories, etc. There are wide ranges and large stocks to choose from as well as many worthwhile advantages to enjoy when you order from Electrovalue.

## CATALOGUE 8 NOW READY

Enlarged to 144 New items, Opto-electronics Diagram of components, applications, I.C. circuits, etc. Better than even No. 7. Post free 40p, including voucher for 40p for use on order over £5 list value.

## DISCOUNTS

On all C.W.O. mail orders, except for some items marked NETT.

**5%** on orders list value £10 or more      **10%** on orders list value £15 or more

## FREE POST & PACKING

On all C.W.O. mail orders in U.K. over £2 list value. If under, add 10p handling charge.

## PRICE STABILIZATION POLICY

Prices are held and then reviewed over minimum periods of 3 months — With effect from Jan. 1st.

## QUALITY GUARANTEE

On everything in our Catalogue — No manufacturer's rejects, seconds or sub-standards merchandise.

# ELECTROVALUE LTD

All communications to Section 7/2, 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB. Telephone Egham 3603. Telex 284475. Shop hours 9-5.30 p.m. daily, 9-1 p.m. Sats  
NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester M19 1NA. Telephone (061) 432 4945. Shop hours daily 9-5.30 p.m., 9-1 p.m. Sats

# tecknowledged in consumer ICs - and their applications.

## SGS Audio ICs



The much heralded TDA2020 is here. And just to make sure that you don't go wrong, so is the SGS application test circuit PCB for a stereo 15 + 15 (RMS) Hi Fi amplifier.

Prices	IC	AUDIO	DISCRETES
TBA810AS	+HS 1.09	ZTX107/8/9	14p
TCA940E	+HS 1.80	ZTX413(LN)	17p
TDA2020	2.99	ZTX212/3/4	16p
FM LINEAR	ICS	BD 535 npn	7A/60v 52p
MC1350	0.70	BD536 pnp	53p
CA3089	+QC 1.94	BD377 npn	3A/50v 29p
TBA120	+QC 1.00	BD378 pnp	32p
MPX LINEAR	ICS	BD515 npn	2A/45v 27p
MC1310P	+LED 2.20	BD516 pnp	30p
CA3090AQ	+LED 3.75	BD609 npn	10A/90v 70p
		BD610 pnp	102p

## We've moved

To accommodate expanded R & D facilities, AMBIT has moved sales and administration to 25 High St. Brentwood. The existing 37 High Street premises are retained for the engineering activities.

One of the first products of this move has been the development of a TV sound tuner, from an "off air" system, using its own varicap UHF TV tuner, with ICIF amplifiers and block filters by TOKO. And then one of our best ever circuits - an electronic touch tuner, with scanning mode, and facilities for 6 preset stations. The unit is suitable for use with FM, and now AM of course, and offers a complete tuner system without any moving parts. Selection is by means of touch tuning in all cases, with manual scan and preset switching automatically interlocked.

Our R&D facilities are available for general consultancy to OEMs: further details on application. Standard project estimation fee, including project evaluation comment data is £15.00 payable in advance.

## Modules & Kits

New modules:

8011	Totally touch tuned varicap controller built	£14.99
8005	Larholt tuner/act accessory unit, with pilot tone filter and audio stages, rectifier, IC stabilizer, meter driver circuits.	£4.99 (kit)
8001	55kHz low pass filter (mpx birdy filter)	£2.35 built £1.75 (kit)
2001	Stereo scratch and rumble filter, with continuously variable operating frequencies.	£5.80 (built) £4.60 (kit)
3000	Stereo control preamp - a wide dynamic range, low distortion AF preamp, with vol, bal, bass and treble controls.	kit £5.78
2020k	The TDA2020 stereo amp kit photographed on the left.	£7.85
7700	TV-off air UHF sound tuner - built	£26.00 (4 preset stations)
9000 kit	AM/FM mpa tuner chassis, with mech. tuner	£17.50
7004 kit	MW/LW varicap tuner module, inc. ferrite rod	£9.95
7252	HiFi MOSFET FM tuner module by Larholt	£24.00
7253	HiFi FET FM tuner module inc decoder	£24.00
5600	Hi Q MOSFET varicap tunerhead by TOKO	£11.25
EC3302	FET tunerhead from TOKO	£5.00

Complete FM Tuner kits, inc Case, for use with the above modules: details SAE please. Prices range from £40 - £60.

Amongst our various accessories for entertainment electronics is a range of FM tuning, frequency and sig. strength meters with 12v, 50mA bulb. £2.50 ca.



**ambit international**  
Trade Mark  
**25 high street, brentwood,**  
**essex. cm14 4rh.** tel: (0277) 216029  
tix: 995194

Free price list with an SAE, catalogue of modules and parts 40p., including postage and VAT.

General Terms: CWO please, official bodies and companies please note min. invoice £7.50. PP for CWO orders 22p per order. (UK and Eire). Overseas customers please include sufficient for postage. VAT is not included, and must be added at 25%. In stock orders despatched within 48 hours.

# Complete the coupon and we'll send you our complete, new catalogue.



The new Heathkit catalogue is now out. Full as ever with exciting, new models. To make building a Heathkit even more interesting and satisfying.

And, naturally, being Heathkit, every kit is absolutely complete. Right down to the last nut and bolt. So you won't find yourself embarrassingly short of a vital component on a Saturday evening—when the shops are shut.

You'll also get a very easy to understand instruction manual that takes you step by step through the assembly.

Clip the coupon now (enclosing a 10p stamp for postage) and we'll send you your copy to browse through.

With the world's largest range of electronic kits to choose from, there really is something for everyone.

Including our full range of test equipment, amateur radio gear, hi-fi equipment and many general interest kits.

So, when you receive your catalogue you should have hours of pleasant reading.

And, if you happen to be in London or Gloucester, call in and see us. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road.


At either one you'll be able to see for yourself the one thing the catalogue can't show you.

Namely, how well a completed Heathkit performs. Heath (Gloucester) Limited, Dept. ET1-36 Bristol Road, Gloucester, GL2 6EE. Tel: Gloucester (0452) 29451.

Digital electronic stop watch



AM/FM 60 watt r.m.s. stereo receiver

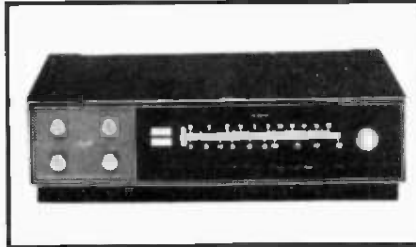

Digital rev counter



**FREE**  
SOLDERING IRON  
WORTH  
**£3.50**  
with all orders over £30

**The new Heathkit catalogue. Out now. FREE.**

To: Heath (Gloucester) Limited, Dept. ET1-36, Gloucester, GL2 6EE.  
Please send me my Heathkit catalogue. I enclose a 10p stamp for postage.

Name \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_

Full details in the catalogue. (Offer available for limited period only.)

HEATH  
Schlumberger

EASY TERMS AVAILABLE  
WITH HEATHKIT MONTHLY  
BUDGET PLAN




# ETI DATA SHEET SPECIAL

## SN72741-741 OP AMP

TEXAS

The SN72741 is Texas Instruments' version of the ubiquitous 741 op-amp. The 741 was originally introduced as the  $\mu A741$  in May 1968, and was the first monolithic op-amp to be internally frequency compensated by an on-chip capacitor.

The SN52741 is a military temperature range version of the SN72741. Both are high-performance operational amplifiers featuring offset voltage null capability. The high common-mode input voltage range and the absence of latch-up makes the 741 ideal for voltage follower applications. The devices are short-circuit protected and the internal frequency compensation ensures stability without external components. A low-value potentiometer may be connected between the offset null inputs to null out the offset null voltage as shown in Fig. 1.

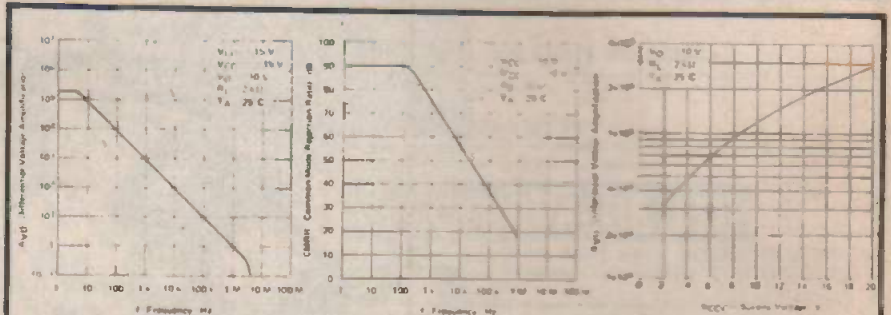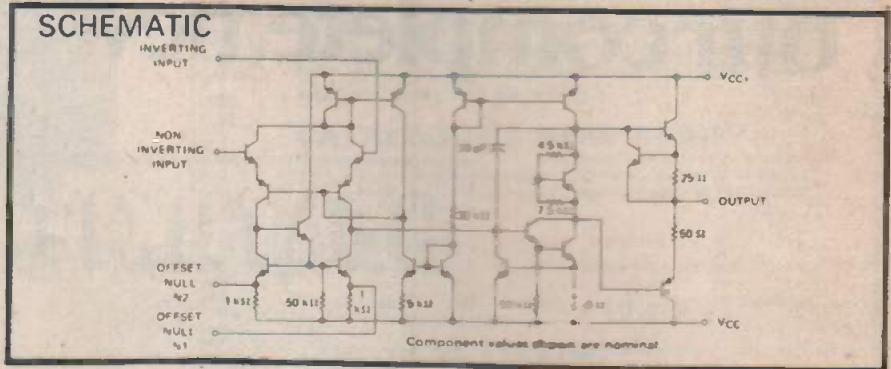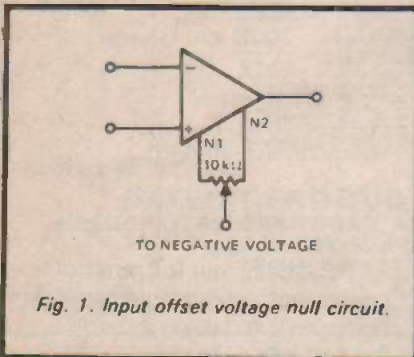

### ELECTRICAL CHARACTERISTICS


Input Offset Voltage	7.5mV max.
Offset Voltage Adjust Range	15mV
Input Offset Current	300mA max
Input Bias Current	800mA max
Input Voltage Range	12V min
Max Pk-Pk Output Voltage Swing	
$R_L$ 10k	24V min
$R_L$ 2k	20V min
Large Signal Differential Voltage Amplification	15000 min
Input Resistance	2Mohm
Output Resistance	75ohm
Input Capacitance	1.4pF
Common-mode Rejection Ratio	70dB min
Power Supply Sensitivity	150 $\mu$ V/V max
Short-circuit Output Current	25mA
Supply Current	3.3mA max
Total Power Dissipation	100mW max

### ABSOLUTE MAXIMUM RATINGS

	SN52741	SN72741
Supply Voltage $V_{CC+}$	22V	18V
Supply Voltage $V_{CC-}$	-22V	-18V
Differential Input Voltage	30V	30V
Input Voltage	15V	15V
Voltage between Offset Null Terminals (N1/N2) and $V_{CC-}$	0.5V	0.5V
Duration of Output Short-circuit	unlimited	
Continuous Total Power Dissipation		500mW

### OPERATING CHARACTERISTICS

$V_{CC+} = 15V, V_{CC-} = -15V$	
Rise Time (tr)	0.3 $\mu$ s
Overshoot	5%
Slew Rate at Unity Gain	0.5V/ $\mu$ s

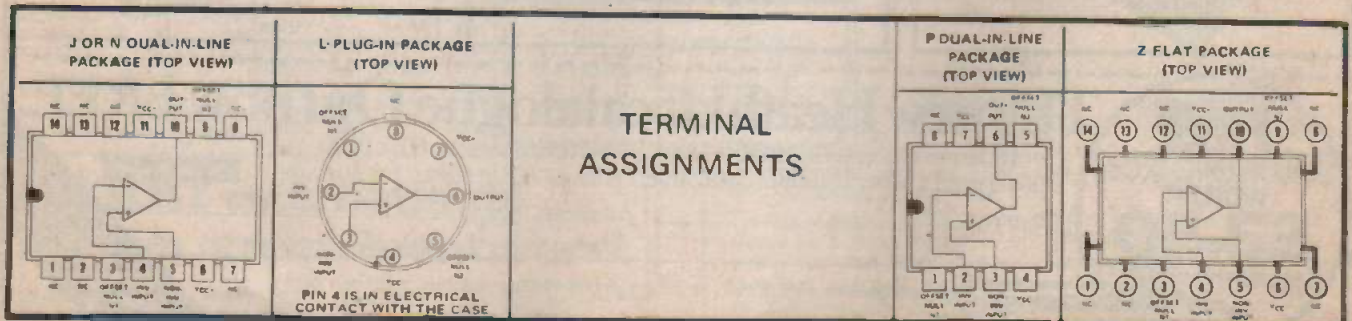

## SN72301A-301 OP-AMP

TEXAS

The SN52101A is the Texas equivalent of the LM101A. The LM101 first appeared in 1967 and the LM101A is similar to the 101 but features better dc input characteristics. The SN52101A is a full military temperature range device and so the average constructor is likely to use the SN72301A which is a commercial temperature range device for operation from 0°C to 70°C.

Both are high-performance operational amplifiers, featuring very low input bias current and input offset voltage and current to improve the accuracy of high-impedance circuits using these devices. The high common-mode input voltage range and the absence of latch-up make these op-amps ideal for voltage-follower applications. The devices are protected to withstand short-circuits at the output. The external compensation of the 101A and 301A allows the changing of the frequency response (when the closed-loop gain is greater than unity) for applications requiring wider bandwidth or higher slew rate.

A potentiometer may be connected between the off-set null inputs (N1 & N2) as shown in Fig. 5, to null out the offset voltage.

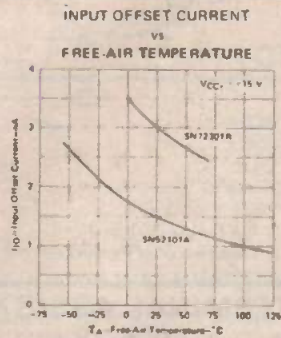


Fig. 1. Input offset current vs. free-air temp.

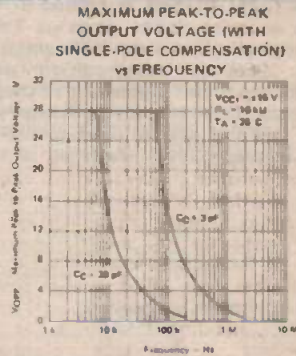


Fig. 2. Maximum p-p output voltage vs. frequency (for single-pole compensation).

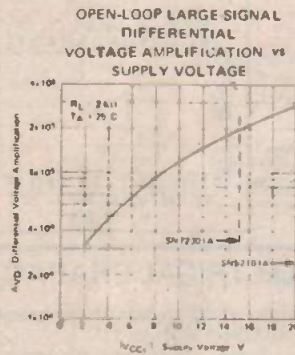


Fig. 3. Open-loop large-signal differential voltage amplification vs. supply voltage.

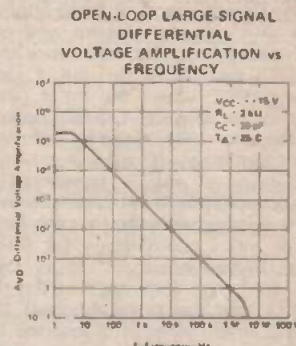


Fig. 4. Open-loop large-signal differential voltage amplification vs. frequency.


## ELECTRICAL CHARACTERISTICS

	SN72301A
Input offset voltage	2mV
Average temperature coefficient of input offset voltage	6μV/°C
Input offset current	3nA
Average temperature coefficient of input offset current	0.02nA/°C
Input bias current	70nA
Input voltage range	±12V min
Maximum pk-pk output voltage swing	
(VCC = ±15V, RL = 10K)	28V
(VCC = ±15V, RL = 2K)	26V
Large signal differential voltage amplification	200,000
Input resistance	2MΩ
Common-mode rejection ratio	90dB
Power supply rejection ratio	96dB
Supply current	1.8mA

## ABSOLUTE MAXIMUM RATINGS

	SN52101A	SN72301A
Supply voltage VCC+	22V	18V
Supply voltage VCC-	-22V	-18V
Differential input voltage	±30V	±30V
Input voltage	±15V	±15V
Voltage between N1/N2 (either offset null terminal) and VCC-	0.5V to 2V	-0.5V to 2V
Duration of output short circuit	unlimited	unlimited
Continuous total output power	500mW	500mW

## TERMINAL ASSIGNMENTS

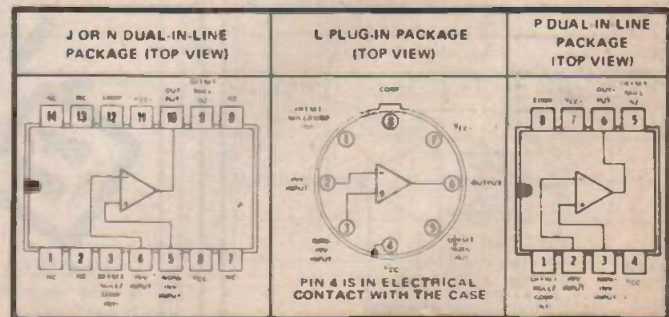

NC—No internal connection


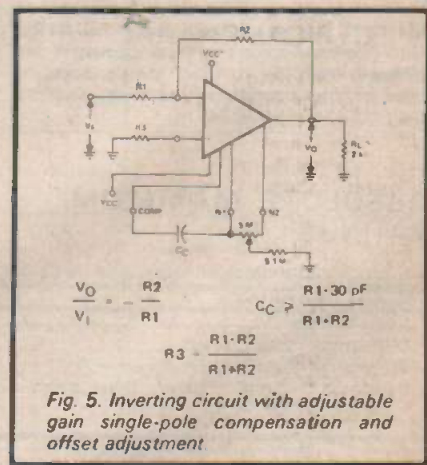


Fig. 5. Inverting circuit with adjustable gain single-pole compensation and offset adjustment.

The 108A and 308A are designed for applications requiring extremely low input bias and offset currents and offset voltages. The SN52108A has a typical input offset voltage of 300 $\mu$ V and typical input offset current of 50pA at 25 $^{\circ}$ C. Input bias current is 3nA maximum over the full temperature range. The output is protected against damage from shorting to ground or either supply and the input stage is diode-protected against excessive differential input signals. External compensation permits optimization of the frequency response for each application. The compensation circuit shown in Fig.3 can be used to make the amplifier particularly insensitive to supply noise.

**SCHEMATIC**

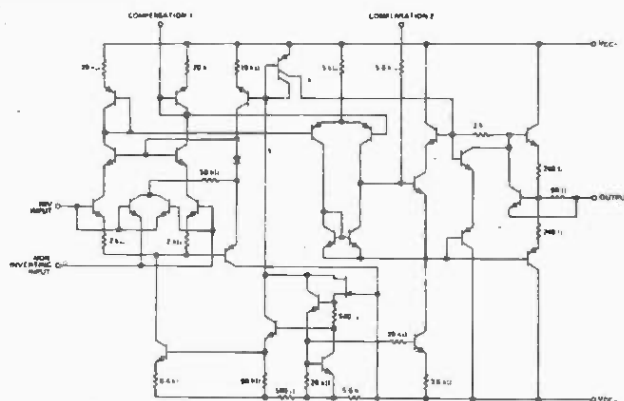

Component values shown are nominal.


**APPLICATION DATA**

Extra care must be taken in the assembly or printed circuit boards to take full advantage of the low input currents of these amplifiers.

Even with properly cleaned and coated boards, leakage currents may cause trouble at 125 $^{\circ}$ C, particularly in the L plug-in package (TO-99) where the input pins are adjacent to pins that are at supply potentials. This leakage can be reduced by surrounding the input terminals with a conductive guard ring. The guard ring is connected to a low-impedance point that is at approximately the same voltage as the inputs. As shown in Figure 4, input guarding of the 8-lead L package may be accomplished by using a 10-lead pin circle, with leads of the device formed so that the holes adjacent to the inputs are empty when it is inserted in the board. The conductive guard ring should be used on both sides of the board.

The pin configurations of both the dual-in-line and flat packages are designed to facilitate guarding, since the pins adjacent to the inputs are not internally connected to the chip. Pin connections in these packages are different from the standard pin connections used in other operational amplifiers such as the SN52741/SN72741.

**TERMINAL ASSIGNMENTS**

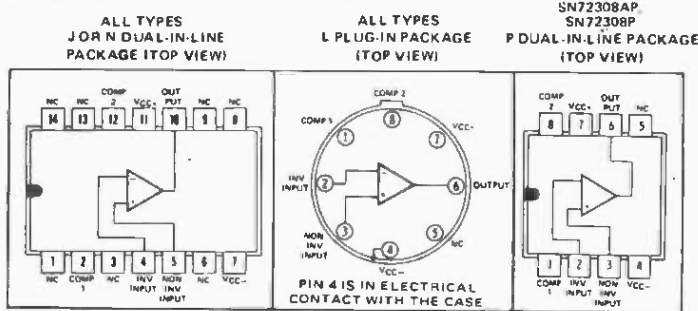

**ELECTRICAL CHARACTERISTICS:**

(values typical except where specified)  
 Input Offset Voltage .....  
 Av. Temp. coefficient of Input Offset Voltage .....  
 Input Offset Current .....  
 Av. Temp. coefficient of Input Offset Current .....  
 Input Bias Current .....  
 Input Voltage Range .....  
 Max. Pk-Pk Output Voltage Swing .....  
 Large-signal Differential Voltage Amplification .....  
 Input Resistance .....  
 Common-mode Rejection Ratio .....  
 Supply Voltage Rejection Ratio .....  
 Supply Current .....

SN 72308A	SN 72308
0.3mV	2mV
1 $\mu$ V/ $^{\circ}$ C	6 $\mu$ V/ $^{\circ}$ C
0.2nA	0.2nA
2pA/ $^{\circ}$ C	2pA/ $^{\circ}$ C
1.5nA	1.5nA
$\pm$ 14V min	$\pm$ 14V min
28V	28V
300,000	300,000
40M ohm	40M ohm
110dB	100dB
110dB	96dB
0.3mA	0.3mA

**ABSOLUTE MAXIMUM RATINGS**

Supply Voltage Vcc+ .....  
 Supply Voltage Vcc- .....  
 Input Voltage .....  
 Differential Input Current .....  
 Duration of Output Short-circuit .....  
 Continuous Total Power Dissipation (below 35 $^{\circ}$ C) .....

SN 52108A	SN 72308A	SN 52108	SN 72308
20V	18V	-20V	-18V
$\pm$ 15V	$\pm$ 15V	$\pm$ 10mA	$\pm$ 10mA
unlimited	unlimited	500mW	500mW

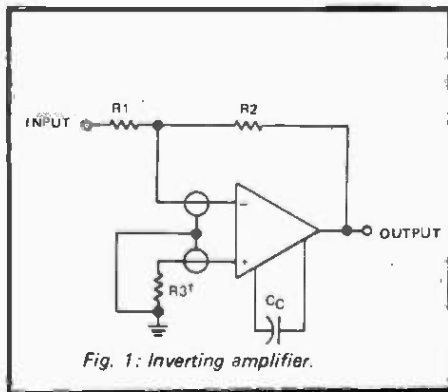


Fig. 1: Inverting amplifier.

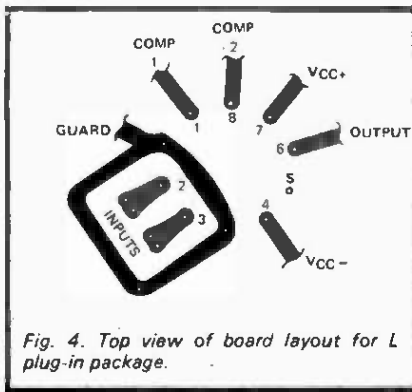


Fig. 4. Top view of board layout for L plug-in package.

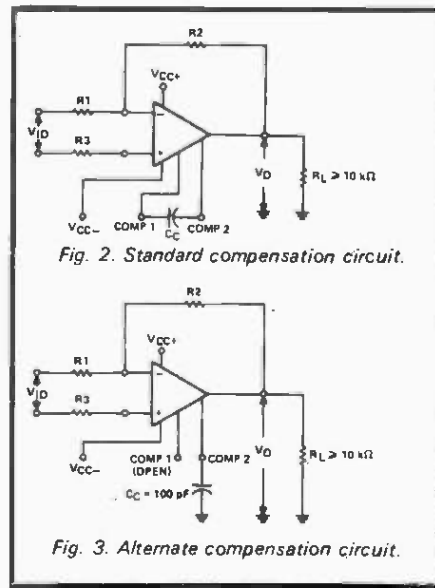


Fig. 2. Standard compensation circuit.


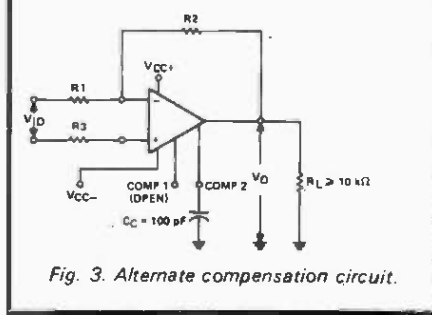


Fig. 3. Alternate compensation circuit.

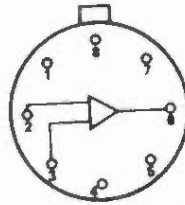

The 536 is a special-purpose high-performance operational amplifier utilizing an FET input stage for extremely high input impedance and low input current. The device features internal compensation, standard pinout, wide differential and common mode input voltage range, high slew rate and high output drive capability. Two versions are available: the SU536T has a temperature range of  $-55^{\circ}\text{C}$  to  $85^{\circ}\text{C}$ , while the NE536T covers  $0^{\circ}\text{C}$  to  $70^{\circ}\text{C}$ .



PIN-OUT DIAGRAM

1. Offset Null
2. Inverting Input
3. Non-inverting Input
4.  $V^{-}$
5. Offset Null
6. Output
7.  $V^{+}$
8. NC

**ABSOLUTE MAXIMUM RATINGS**

Supply Voltage	$\pm 22\text{V}$
Differential Input Voltage Range	$\pm 30\text{V}$
Common Mode Input Voltage Range	$\pm \text{VS}$
Power Dissipation (Note 1)	500mW
Operating Temperature Range	$0^{\circ}\text{C}$ to $\pm 70^{\circ}\text{C}$
Storage Temperature Range	$-65^{\circ}\text{C}$ to $+150^{\circ}\text{C}$
Lead Temperature (Solder, 60 sec)	$300^{\circ}\text{C}$
Output Short Circuit Duration (Note 2)	Indefinite

- NOTES:
1. Rating applies for case temperatures to  $+25^{\circ}\text{C}$ ; derate linearly at  $6.5\text{mW}/^{\circ}\text{C}$  for ambient temperatures above  $75^{\circ}\text{C}$ .
  2. Short circuit may be to ground or either supply. Rating applies to  $+125^{\circ}\text{C}$  case temperature or  $+75^{\circ}\text{C}$  ambient temperature.

**ELECTRICAL CHARACTERISTICS**

<b>INPUT CHARACTERISTICS</b>	
Large Signal Voltage Gain @ $+25^{\circ}\text{C}$	100V/mV
Input Offset Voltage @ $+25^{\circ}\text{C}$	30mV
vs Temperature (drift)	$30\mu\text{V}/^{\circ}\text{C}$
vs Common Mode Voltage (C.M.R.R.)	80dB
vs Power Supply (P.S.R.R.)	$100\mu\text{V}/\text{V}$
Input Current @ $+25^{\circ}\text{C}$	30pA
Input Offset Current @ $+25^{\circ}\text{C}$	5pA
Input Impedance	
Differential Resistance	$10^{14}\text{ohm}$
Differential Capacitance	6pF
Input Noise (0.1Hz — 100kHz)	
Voltage Noise	$20\mu\text{V r.m.s}$
Common Mode Voltage Range	$\pm 11\text{V}$
<b>OUTPUT CHARACTERISTICS</b>	
Output Current	5mA min
Open Loop Output Impedance	100 ohm
Output Voltage Swing	
$R_L = 2\text{k ohm}$	$\pm 10\text{V}$
$R_L = 10\text{k ohm}$	$\pm 13\text{V}$
Short Circuit Current	17mA
<b>FREQUENCY AND TRANSIENT RESPONSE</b>	
Gain Bandwidth Product	1MHz
Unity Gain Frequency	1MHz
Full Power Bandwidth	100kHz
Slew Rate	
Inverter	$6\text{V}/\mu\text{S}$
Follower	$6\text{V}/\text{S}$
<b>POWER SUPPLY REQUIREMENT</b>	
Power Supply Range	$\pm 6\text{V}$ to $\pm 18\text{V}$
Quiescent Supply Current at $\pm 15\text{V}$ Vs	6mA
Quiescent Power Dissipation	180mW

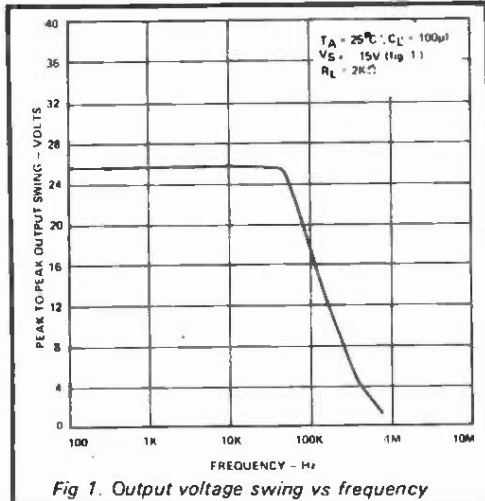


Fig 1. Output voltage swing vs frequency

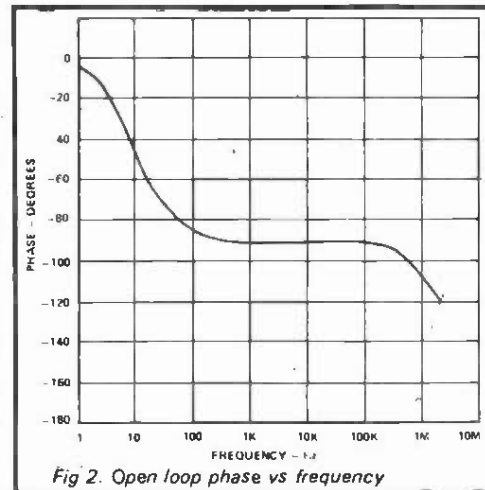


Fig 2. Open loop phase vs frequency


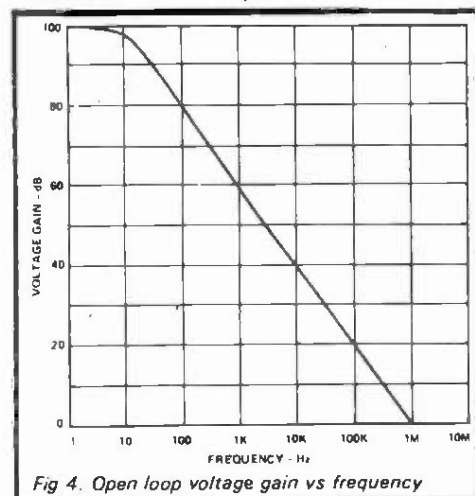


Fig 4. Open loop voltage gain vs frequency

All values typical unless specified

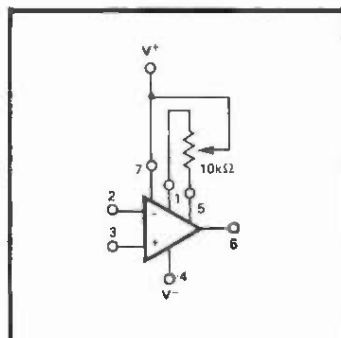

OFFSET NULL CIRCUIT

Fig 5. Offset null circuit


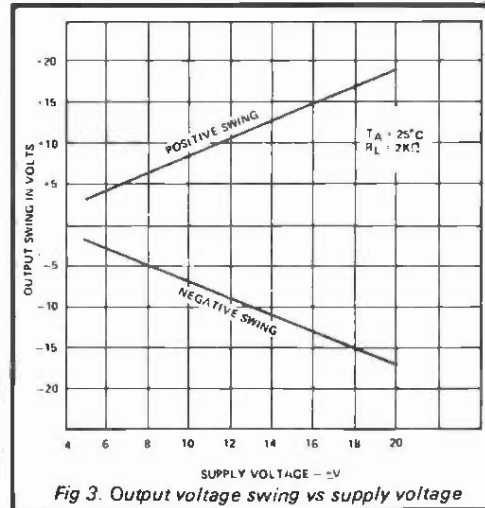


Fig 3. Output voltage swing vs supply voltage

The RCA CA3078T and CA3078AT are high-gain monolithic op-amps which can deliver milliamps of current yet only consume microwatts of standby power. Their operating points are externally adjustable and frequency compensation may be accomplished with one external capacitor. They provide the designer with the opportunity to tailor the frequency response and improve the slew rate without sacrificing power. Operation with a single 1.5V battery is a practical reality with these devices.

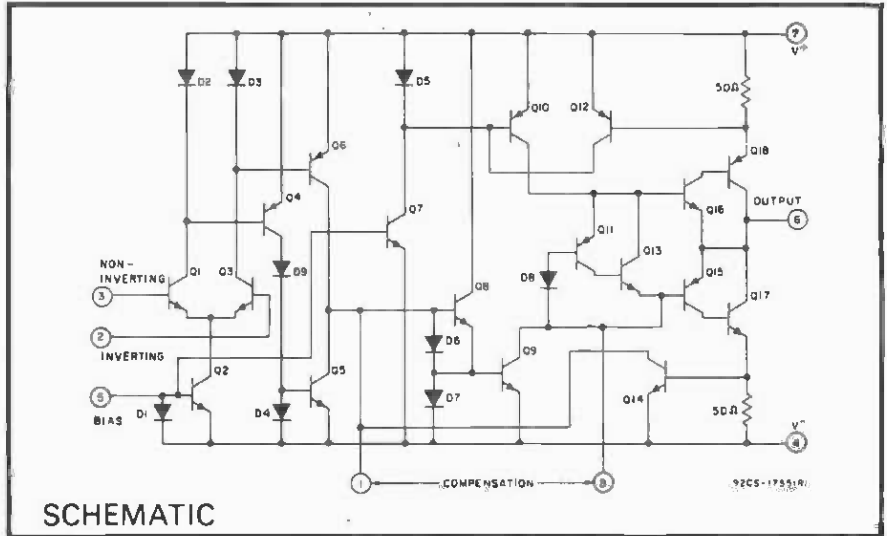The CA3078T has a minimum supply voltage of  $\pm 0.75V$  and a maximum supply voltage of  $\pm 15V$ , with an operating temperature range of  $-55^{\circ}C$  to  $125^{\circ}C$ . The CA3078AT has the same lower supply voltage limit but the upper limit is  $\pm 6V$  and the temperature range is  $0^{\circ}C$  to  $70^{\circ}C$ .




**ELECTRICAL CHARACTERISTICS**

All values typical unless specified.

	CA3078AT	CA3078T
Input Offset Voltage	0.70mV	1.3mV
Input Offset Current	0.50nA	6nA
Input Bias Current	7nA	60nA
Open-Loop Diff Voltage Gain	100dB	92dB
Total Quiescent Current	20 $\mu$ A	100 $\mu$ A
Device Dissipation	240 $\mu$ W	1200 $\mu$ W
Maximum Output Voltage	$\pm 5.3V$	$\pm 5.3V$
Common-Mode Input Voltage Range	$-5.5$ to $\pm 5.8V$	$-5.5$ to $\pm 5.8V$
Common-Mode Rejection Ratio	115dB	110dB
Maximum Output Current	12mA	12mA
Input Offset Voltage Sensitivity	105 $\mu$ V/V	93 $\mu$ V/V




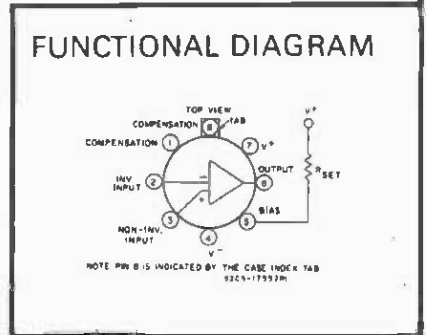
Absolute values at  $T_A = 25^{\circ}C$ .



**ABSOLUTE MAXIMUM RATINGS**

	CA3078AT	CA3078T
DC Supply Voltage (between $V^+$ and $V^-$ terminal)	36V	14V
Differential Input Voltage	$\pm 6V$	$\pm 6V$
DC Input Voltage	$V^+$ to $V^-$	$V^+$ to $V^-$
Input Signal Current	0.1mA	0.1mA
Output Short Circuit Duration	No Limitation	No Limitation
Device Dissipation	250mW (up to $125^{\circ}C$ )	500mW (up to $70^{\circ}C$ )

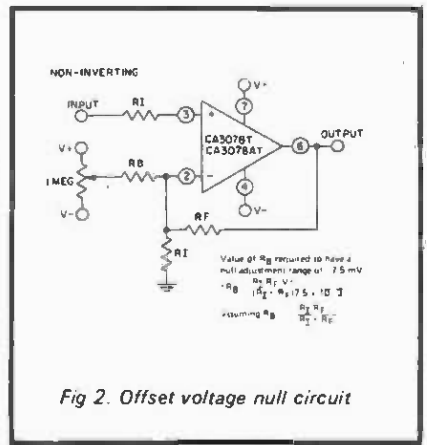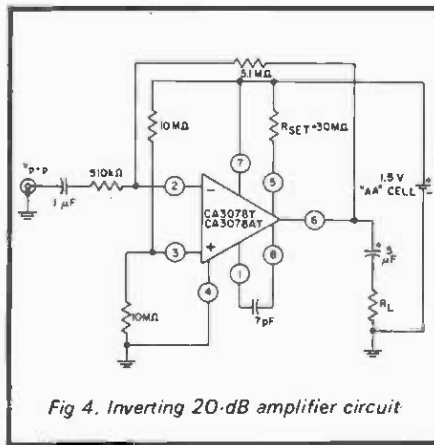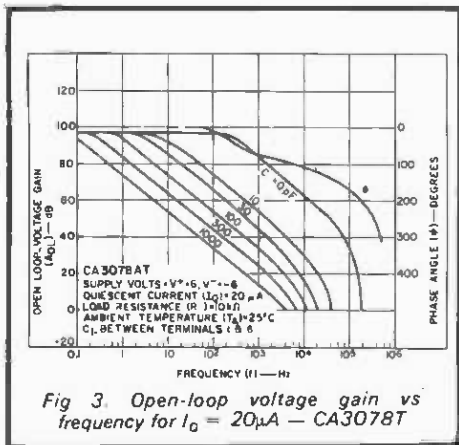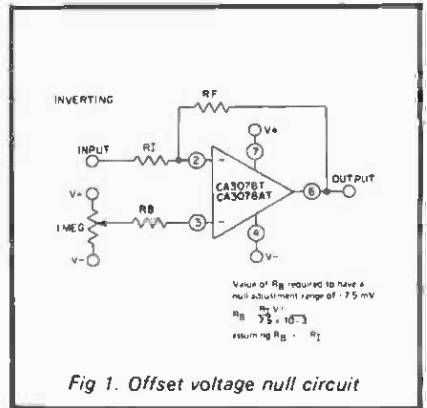\*Short circuit may be applied to ground or to either supply



## DEFINITION OF OP-AMP TERMS

**Input Offset Voltage ( $V_{10}$ )** The d-c voltage which must be applied between the input terminals to force the quiescent d-c output voltage to zero. The input offset voltage may also be defined for the case where two equal resistances ( $R_{i0}$ ) are inserted in series with the input leads.

**Average Temperature Coefficient of Input Offset Voltage ( $\alpha_{V10}$ )** The ratio of the change in input offset voltage to the change in free-air temperature. This is an average value for the specified temperature range.

$$\alpha_{V10} = \frac{(V_{10@T_{A(1)}}) - (V_{10@T_{A(2)}})}{T_{A(1)} - T_{A(2)}} \quad \text{where } T_{A(1)} \text{ and } T_{A(2)} \text{ are the specified temperature extremes.}$$

**Input Offset Current ( $I_{10}$ )** The difference between the currents into the two input terminals with the output at zero volts.

**Average Temperature Coefficient Of Input Offset Current ( $\alpha_{I10}$ )** The ratio of the change in input offset current to the change in free-air temperature. This is an average value for the specified temperature range.

$$\alpha_{I10} = \frac{(I_{10@T_{A(1)}}) - (I_{10@T_{A(2)}})}{T_{A(1)} - T_{A(2)}} \quad \text{where } T_{A(1)} \text{ and } T_{A(2)} \text{ are the specified temperature extremes.}$$

**Input Bias Current ( $I_{10}$ )** The average of the currents into the two input terminals with the output at zero volts.

**Input Voltage Range ( $V_{10}$ )** The range of voltage which if exceeded at either input terminal will cause the amplifier to cease functioning properly.

**Maximum Peak-to-Peak Output Voltage Swing ( $V_{opp}$ )** The maximum peak-to-peak output voltage which can be obtained without waveform clipping when the quiescent d-c output voltage is zero.

**Large-Signal Differential Voltage Amplification ( $A_{VD}$ )** The ratio of the peak-to-peak output voltage swing to the change in differential input voltage required to drive the output.

**Input Resistance ( $r_i$ )** The resistance between the input terminals with either input grounded.

**Output Resistance ( $r_o$ )** The resistance between the output terminal and ground.

**Common-Mode Rejection Ratio (CMRR)** The ratio of differential voltage amplification to common-mode voltage amplification. This is measured by determining the ratio of a change in input common-mode voltage to the resulting change in input offset voltage.

**Power Supply Sensitivity ( $\Delta V_{10}/\Delta V_{CC}$ )** The ratio of the change in input offset voltage to the change in supply voltages producing it. For these devices, both supply voltages are varied symmetrically.

**Total Power Dissipation ( $P_D$ )** The total d-c power supplied to the device less any power delivered from the device to a load. At no load:  $P_D = V_{CC+} I_{CC+} + V_{CC-} I_{CC-}$

**Rise Time ( $t_r$ )** The time required for an output voltage step to change from 10% to 90% of its final value.

**Overshoot** The quotient of: (1) the largest deviation of the output signal value from its steady-state value after a step-function change of the input signal, and (2) the difference between the output signal values in the steady state before and after the step-function change of the input signal.

**Slew Rate (SR)** The average time of change of the closed-loop amplifier output voltage for a step-signal input. Slew rate is measured between specified output levels (0 and 10 volts for this device) with feedback adjusted for unity gain.

# ETI HELPING HAND COMPETITION



This is our open competition to find solutions for problems facing the deaf.

This closing date is March 31st 1976. ETI and the Royal National Institute for the Deaf (RNID) are co-operating fully in the organisation of this competition.

Three problems are shown above. We invite individual readers, clubs, schools, universities, companies, in fact anybody, to develop a practical

solution. The rules are as basic as possible and impose virtually no restriction apart from insisting that any Patent Royalties are waived if the idea is produced.

The prizes, three in all, will each be a silver trophy specially designed for ETI. At the close of the competition the magazine will hand over £250 to the RNID to help with development costs. There is a £1.00 entry fee (payable to

### THE PROBLEMS

1 A sick person is being looked after by a deaf person. The deaf person has no useful hearing and requires to know whether the sick person is all right and above all needs to know if the sick person is in a state of distress anywhere in the sick room.

2 A hard of hearing person is attending a College of Further Education and has considerable difficulty in understanding what the lecturer says due to his distance from the lecturer and to the background noise in the room. A device is required to enable him to make the best possible use of his hearing.

3 Many deaf people have great difficulty in using the telephone and in fact many of them cannot use the telephone at all. The development of a writing tablet which would allow them to write a message on a small pad and for this to be communicated over the telephone line to a pad at the other end would have many great advantages. In addition the communication should be two way so that the person can receive a message or an indication that the message has been received.

RNID) and this will be added to the £250.

Background information has been prepared to help readers and say what is already known. This is available from ETI on receipt of a large self-addressed envelope. Enquiries should be sent to:

**Helping Hand,  
ETI Magazine,  
36 Ebury Street,  
London, SW1W 0LW.**

**STILL  
TIME  
TO  
ENTER  
CLOSING DATE  
31 MARCH  
1976**

Now...the most exciting Sinclair kit ever


# The Black Watch kit

At £14.95, it's

★ **practical** – easily built by anyone in an evening's straightforward assembly.

★ **complete** – right down to strap and batteries.

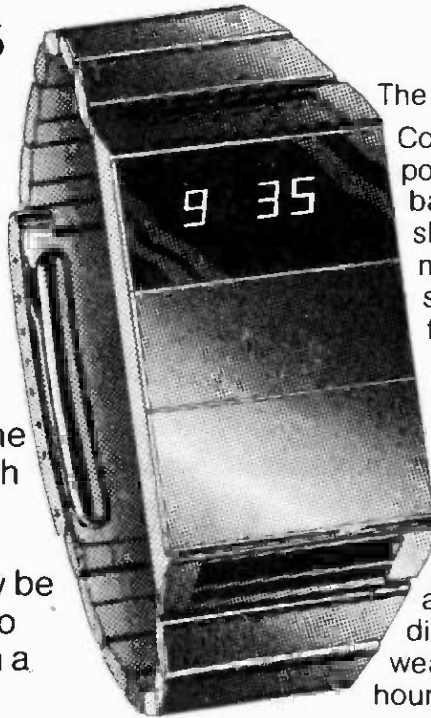★ **guaranteed**. A correctly-assembled watch is guaranteed for a year. It works as soon as you put the batteries in. On a built watch we guarantee an accuracy within a second a day – but building it yourself you may be able to adjust the trimmer to achieve an accuracy within a second a week.



The Black Watch by Sinclair is unique. Controlled by a quartz crystal... powered by two hearing aid batteries... using bright red LEDs to show hours and minutes and minutes and seconds... it's also styled in the cool prestige Sinclair fashion: no knobs, no buttons, no flash.

The Black Watch kit is unique, too. It's rational – Sinclair have reduced the separate components to just four.




It's simple – anybody who can use a soldering iron can assemble a Black Watch without difficulty. From opening the kit to wearing the watch is a couple of hours' work.

## The special features of The Black Watch

Smooth, chunky, matt-black case, with black strap. (Black stainless-steel bracelet available as extra – see order form.)

Large, bright, red display – easily read at night.  
Touch-and-see case – no unprofessional buttons.

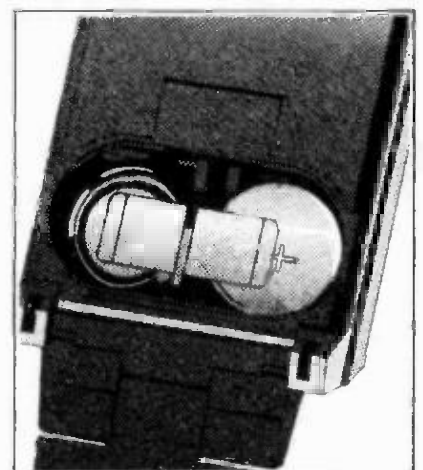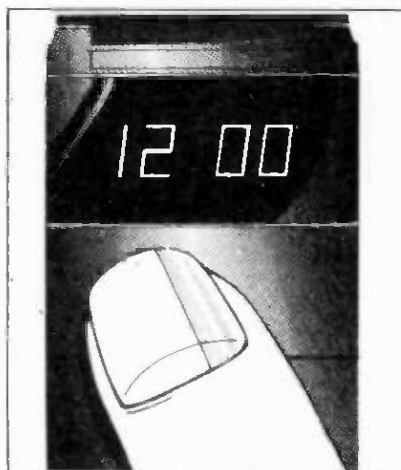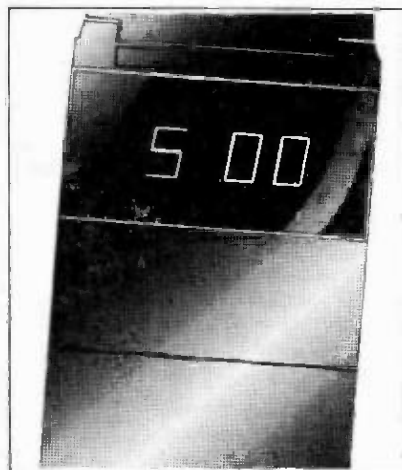Runs on two hearing-aid batteries (supplied). Change your batteries yourself – no expensive jeweller's service.



## The Black Watch—using the unique Sinclair-designed state-of-the-art IC.

### The chip ...

The heart of the Black Watch is a unique IC designed by Sinclair and custom-built for them using state-of-the-art technology—integrated injection logic.


This chip of silicon measures only 3 mm x 3 mm and contains over 2000 transistors. The circuit includes

- a) reference oscillator
- b) divider chain
- c) decoder circuits
- d) display inhibit circuits
- e) display driving circuits.

The chip is totally designed and manufactured in the UK, and is the first design to incorporate *all* circuitry for a digital watch on a single chip.
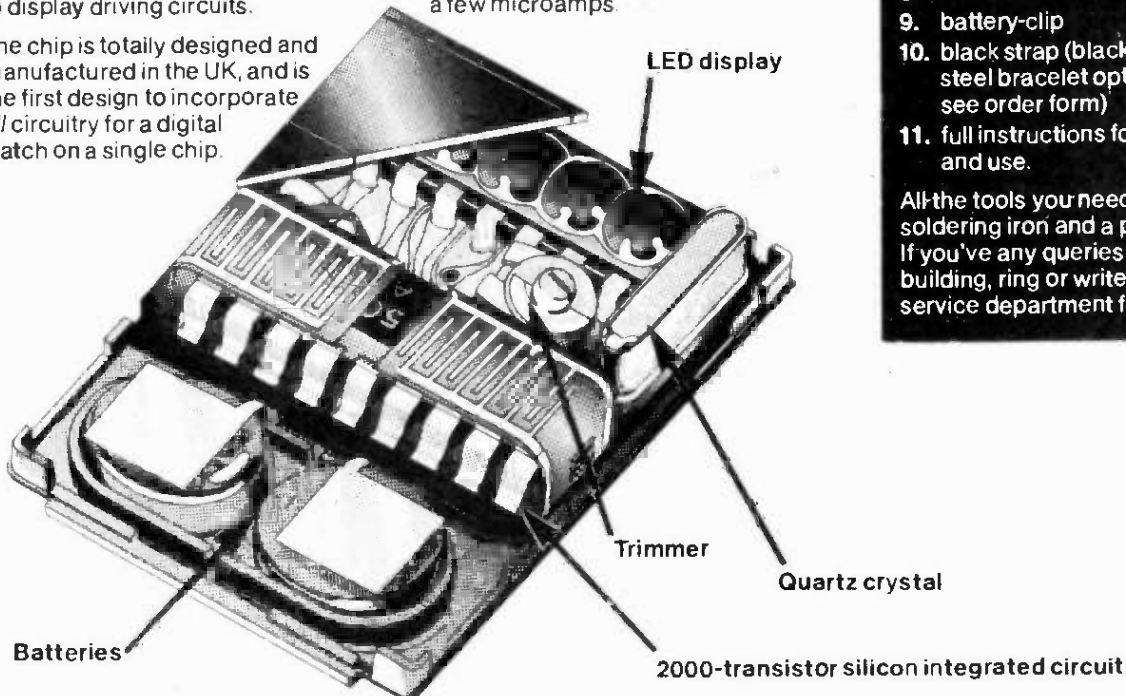
### ... and how it works

A crystal-controlled reference is used to drive a chain of 15 binary dividers which reduce the frequency from 32,768 Hz to 1 Hz. This accurate signal is then counted into units of seconds, minutes, and hours, and on request the stored information is processed by the decoders and display drivers to feed the four 7-segment LED displays. When the display is not in operation, special power-saving circuits on the chip reduce current consumption to only a few microamps.



# Complete kit £14.95!

### The kit contains

1. printed circuit board
2. unique Sinclair-designed IC
3. encapsulated quartz crystal
4. trimmer
5. capacitor
6. LED display
7. 2-part case with window in position
8. batteries
9. battery-clip
10. black strap (black stainless-steel bracelet optional extra—see order form)
11. full instructions for building and use.

All the tools you need are a fine soldering iron and a pair of cutters. If you've any queries or problems in building, ring or write to Sinclair service department for help.

### Take advantage of this no-risks, money-back offer today!

The Sinclair Black Watch is fully guaranteed. Return your kit in original condition within 10 days and we'll refund your money without question. All parts are tested and checked before despatch—and correctly-assembled watches are guaranteed for one year. Simply fill in the FREEPOST order form and post it—today!

Price in kit form: £14.95 (inc. black strap, VAT, p&p).

# sinclair

Sinclair Radionics Ltd,  
London Road, St Ives,  
Huntingdon, Cambs., PE17 4HJ.  
Tel: St Ives (0480) 64646.

Reg. no: 699483 England. VAT Reg. no: 213 8170 88.

To: Sinclair Radionics Ltd, FREEPOST, St Ives, Huntingdon, Cambs., PE17 4BR.

Please send me

Total £

..... (qty) Sinclair Black Watch  
kit(s) at £14.95 (inc. black  
strap, VAT, p&p).

..... (qty) black stainless-steel  
bracelet(s) at £2.00  
(inc. VAT, p&p).

\* I enclose cheque for £.....  
made out to Sinclair Radionics Ltd  
and crossed.

\* Please debit my \*Barclaycard/Access/  
American Express account number

Name \_\_\_\_\_

Address \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

ET1/3

Please print. FREEPOST—no stamp required.

\*Delete as required

*"I used to read  
'comics'....until  
I discovered  
ETI."*



*"Now I get it regularly!"*

There are only two ways to ensure a regular copy of ETI — place a regular order with your newsagent or take out a subscription. If you don't believe us — take a look at the recent issues no longer available listed with the Index!

Help us to help you: please write your name and address on the back of your cheques.

To: **SUBSCRIPTIONS DEPARTMENT,  
ETI MAGAZINE,  
36 Ebury Street,  
London SW1W 0LW**

I enclose £5.00 (£5.50 overseas subscriptions except Canada: \$10) for the next twelve issues of ETI.

Name .....

Address .....

March 1976

**UP TO  
£500  
TO BE WON**

**TEN PRIZES OF  
£12.50**

worth of goods selected from Henry's Self-Service Centre or Components Catalogue (inc. VAT).

**AND FIRST PRIZE OF  
£12.50**

**PLUS**

**'SALE-OF-THE-CENTURY'**

The first prize is £12.50 cash but the winner is entitled to a 90% discount if he spends the money on goods selected from Henry's Self-Service Centre or Components Catalogue.



Normally £8.10.  
81p!

**EXAMPLES**



Normally £7.78  
77p!




Normally £93.98  
£9.40!

**DOUBLE  
YOUR  
MONEY**

**HENRY'S**

RETAIL AND MAIL ORDER  
Catalogue

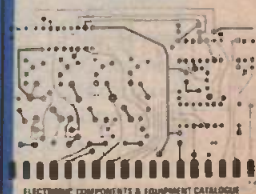

ELECTRONIC COMPONENTS & EQUIPMENT CATALOGUE

# ETI-HENRY'S

## COMPETITION



To celebrate the recent opening of Henry's Self-Service Electronics Centre at 404 Edgware Road, London W2, ETI and Henry's have arranged an easy-to-enter competition with prizes of at least £250 and up to £500 worth of goods.

First prize is £12.50 plus a 90% discount on goods purchased with this sum — or equivalent to £250 worth of goods if you affix to your entry coupon the price circle from the current Henry's catalogue.

Additionally there are 10 other prizes of £12.50 worth of goods, again worth double with proof of purchase of the catalogue.

Henry's have perhaps the best selection of components in the country and their new Self-Service Centre — the first of its kind in Britain — makes browsing and selection more enjoyable than it ever has been.

### RULES

The competition is open to readers in the United Kingdom and Northern Ireland except employees of Electronics Today International and the Henry's Group of companies and their agents. There is no entry fee but all entries must be made on the coupon cut from the magazine. No other correspondence should accompany the entry. If you wish to show proof of purchase of the latest Henry's catalogue, entitling you to double the value in prizes follow the instructions given below.

The prizes will be awarded to the first eleven correct entries drawn after the closing date of March 31st, 1976. The first prize, entitling the winner to a 90% discount will be awarded to the first correct entry selected. A method of draw will be used which gives no preference one way or the other to those entrants opting for 'Double-your-Money'.

The prize value includes VAT. Readers may submit as many entries as they wish but each must be accompanied by an original coupon. It is a condition of entry that the judge's decision is regarded as final.


## DOUBLE YOUR PRIZE VALUE!

If you stick or staple the '50p' price circle from the top right hand corner of the current Henry's Radio Components Catalogue to your entry coupon, the value of your prize will be doubled! The ten basic prizes will then be £25 worth of components and the first prize the same but still qualifying for 90% discount — making the first prize worth £250!
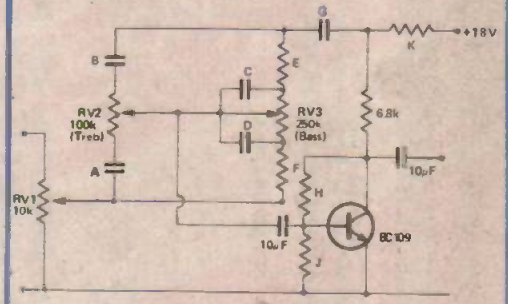
### How to enter

The circuit shown below is of a fairly standard tone control. Many of the component values are missed out and replaced by the letters A—K. A list of the correct component values is listed.


Use your skill and judgement to allocate the components next to the letters on the entry coupon. The electrolytic in the circuit is deliberately shown as a non-polarised capacitor. Components should be allocated for the best conventional performance.



Capacitors	Resistors
2.7nF	3.3kΩ
2.7nF	15kΩ
15nF	22kΩ
15nF	22kΩ
10µF electrolytic	100kΩ

A	.....	F	.....
B	.....	G	.....
C	.....	H	.....
D	.....	J	.....
E	.....	K	.....

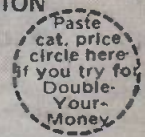To: ETI/HENRY'S COMPETITION  
ETI MAGAZINE,  
36 EBURY STREET,  
LONDON SW1W 0LW.



NAME.....

ADDRESS.....

# APRIL ETI

MORE DETAILS ON THE  
**CA3130**

THIS CMOS OP-AMP WAS FEATURED IN DATASHEET LAST NOVEMBER. NEXT MONTH WE LOOK AGAIN AT THIS REMARKABLE DEVICE AND GIVE MORE APPLICATIONS CIRCUITS.

## CONVERT YOUR CALCULATOR INTO A STOPWATCH

OR IF YOU WANT TO BUILD A CHEAP STOPWATCH BUY A CHEAP CALCULATOR AND A COUPLE OF CMOS ICS THEN FOLLOW OUR DESIGN. THE INSTRUMENT WE BUILT GAVE  $\pm 0.2\%$  ACCURACY AND MEASURED UP TO 9999.99 SECONDS (OVER 2½ HRS).

## SWITCHING REGULATOR TTL POWER SUPPLY

FIVE VOLTS AT TEN AMPS FROM THIS SIMPLE PROJECT. SWITCHING REGULATION GIVES MUCH MORE EFFICIENCY THAN SERIES REGULATION SO THE DEMANDS ON THE TRANSFORMER ARE LOWER.

## ETI AND Marshall's SPECIAL OFFER

THIS WILL BE RUN ON LINES SIMILAR TO THE OFFER WITH MARSHALL'S LAST YEAR: BIG REDUCTIONS ON TTL, CMOS, 7-SEGMENT DISPLAYS, ETC.

## ETI MICROFILE

KEEPS YOU IN TOUCH WITH THE MOST EXCITING NEWS IN ELECTRONICS. NEXT MONTH FIND OUT HOW ONE SMALL CHIP HANDLES PROBLEMS WHICH WERE PREVIOUSLY TACKLED ONLY BY ENORMOUS COMPUTERS!

## TECH-TIPS & DATA SHEET INDEX

TECH-TIPS has now been running for four years. With our index you will be able to find creative circuitry, in almost any application, without having to search for hours.

## SPACE ENVIRONMENT

The space capsule has to provide the astronaut with a comfortable environment despite the hostile temperatures, radiation, pressure, meteors, etc

APRIL ISSUE ON SALE MARCH 5TH

# electronics today

international





# GENERAL FEATURES, CONT.

**INSTRUMENTATION**

Automatic Pollution Monitor Aug 73 67  
Electronic Torque Measuring Sept 72 9  
Fine Measurement in  
Geographics Dec 72 13  
How to make measurements automatically Apr 73 33  
Improving Bridge Instruments June 73 33  
Keithley 167 Meter May 72 59  
Non-Contact Velocity Measurement Aug 72 55  
Pollution Detector Aug 72 10  
Power Supplies Pt. 1 Mar 73 64  
" " Pt. 2 Apr 73 58  
Jan 73 31  
Sophisticated VOM Dec 73 50  
Towards a Better Environment Transducers in Measurement & Control Pt. 1 May 72 50  
" Pt. 2 June 72 52  
" Pt. 3 July 72 38  
" Pt. 4 Aug 72 62  
" Pt. 5 Oct 72 51  
" Pt. 6 Dec 72 52  
" Pt. 7 Jan 73 68  
" Pt. 8 Feb 73 62  
" Pt. 9 Apr 73 31  
" Pt. 10 May 73 60  
" Pt. 11 June 73 54  
" Pt. 12 July 73 54  
" Pt. 13 Aug 73 60  
" Pt. 14 Sept 73 60  
Working with the Oscilloscope June 75 10

**LASERS**

Beating the Laser Bug Mar 73 42  
Experiments with Lasers Pt. 1 Mar 74 37  
Pt. 2 Apr 73 77  
Laser Communications Apr 73 77  
Laser Holographic Memory Dec 72 28  
Lasers Aug 73 20  
Lasers at Work Pt. 1 May 74 14  
Pt. 2 Jul 74 10  
Oct 72 76  
Spin-Flip Laser Thin-film Laser switch June 74 59

**MEDICINE**

Aid for the Blind Aug 72 54  
Biological Feedback Apr 72 30  
Brain X-ray, Breakthrough June 72 70  
Cocktail Party Phenomenon Jul 72 36  
Electronics and Your Eyes Feb 74 27  
Electronics in Medicine Pt. 1 Oct 75 10  
Pt. 2 Nov 75 44  
Flash Blindness Protection Jan 73 27  
Nuclear Heart Pacemaker Aug 72 31  
Neutron Radiography July 72 61  
Pain Killer, Electronic May 72 11  
Setting the Pace Apr 73 42

**MOToring**

Anti-Collision Radar Nov 72 82  
Breakerless Auto Ignition Aug 72 58  
Cars — Future Shock Apr 73 24  
Electronic Anti-Skid Braking May 72 37  
IC's in Vehicles Apr 72 16  
Road Safety — An Electronic Approach Dec 74 24  
Shake, Rattle and Roll June 72 37  
Solid State Taxi meter Mar 73 28

**NEW TECHNIQUES**

Analog-to-Digital Converter Aug 73 70  
The Art of Soldering July 75 13  
Charge Coupling Sept 72 42  
Constant Frequency Alternator Dec 73 39  
Controlled Temperature Soldering Nov 75 23  
Digital Fault-finding Methods July 74 26  
Electrostatic Cooling June 73 39  
Foil Construction for Batteries Nov 73 68  
High Voltage for Low Cost July 75 31  
Image Retaining Panel Sept 72 13  
Infra-red Aerial Survey Aug 72 11  
Ion Implantation Aug 72 19  
Modern Crystal Oscillators Apr 75 23  
Motional Feedback Jan 74 63  
Motor Speed Control Jan 74 64

New Scanning System May 72 69  
New Technology Dec 72 66  
Pictorial Guide to Soldering Aug 75 46  
Protecting Reed Relays June 73 62  
Reshaping by Video Oct 72 72  
Sixty Million Volts Jan 74 60  
Techniques of Digital Fault-finding July 74 18  
Technology in the 70's Aug 72 70  
Thick Film Circuits Oct 73 14  
Thin-Film Sputter Etching Nov 72 55  
Tri-state Logic Oct 72 58  
Using a Resistivity Meter July 73 32  
Wiegand Effect Aug 72 32

**OFFERS**

Advance Calculator Kit Nov 73  
Amtrom UK110/A Amplifier July 74 35  
Bi-Pak 5-in-1 Offer May 75 38  
BC108 Transistors Jan 75 31  
CT5001 Calculator Chip Aug 74 35  
Decon PCB Pen Feb 74 31  
Denshi Kits Feb 75 35  
Digital Clock Kit Sept 74 35  
Diodes Nov 74 35  
Electrolytic Capacitors Jan 75 31  
Electronic Ignition Aug 75 31  
Forty Watt Transistors July 74 35  
Jumbo LED's Jan 76 66  
LM380 Amps Dec 74 35  
LM381 Nov 74 35  
Multimeter Dec 74 35  
Novus 3500 Calculator Dec 75 45  
Pulsar Digital Clock July 75 46  
Resistors — 610 Mar 74 31  
Seven-Segment LED's Sept 74 35  
Sincral Scientific Kit Oct 74 35  
Sincral Scientific No.2 Oct 75 35  
TTL & CMOS Offer June 75 35  
Weller Solder Gun Nov 75 39  
555 Timers Mar 75 35  
6W IC (SN 76023ND) May 74 35

**PRACTICAL GUIDES**

P.G. to reed switches Pt. 1 Sept 72 48  
" " Pt. 2 Oct 72 60  
" " Pt. 3 Nov 72 39  
" " Oct 72 48  
Pt. 2 Nov 72 31  
P.G. to temperature control Pt. 1 Nov 72 56  
" " Pt. 2 Dec 72 30  
" " Pt. 3 Jan 73 40  
P.G. to Triacs Pt. 1 Apr 72 41  
" " Pt. 2 May 72 64  
" " Pt. 3 June 72 29  
P.G. to Zener Diodes Pt. 1 July 72 70  
Pt. 2 Aug 72 35

**SPACE**

Black Holes of Utmost Gravity Sept 72 20  
Gamma-Ray Star Gazing Oct 72 78  
Life on Mars Jan 73 37  
Life on Mars? Jan 76 10  
NASA — the first 15 years Jan 74 48  
Radio Astronomy Jan 75 18  
Robots in Space Nov 74 10  
Searching for the Anti-World Feb 73 14  
Space Craft Guidance Mar 75 38  
Space Spectacular Pt. 1 May 72 50  
Pt. 2 Aug 72 42  
Space Tracking Stations Apr 72 20

**SURVEYS**

Battery TV's — Ever Silver Screen Feb 74 36  
Digital Clock Kits Aug 74 50  
Directory of Hand-Held Calculators Aug 74 37  
Directory of Hi-Fi Amplifiers Nov 73 37  
Electronic Kits Jan 75 35  
Kits for the Car Nov 74 42  
Light Effect Kits Apr 74 26  
Mail Order Catalogues Apr 75 38  
Scientific Calculators Jan 76 26  
Errata Feb 76

**TELEVISION**

Battery TV Survey—Ever Silver Screen Feb 74 36  
Colour Synthesizers Jan 75 38  
Colour TV goes Digital Jan 73 48  
Early TV Cameras Oct 73 31  
Fourth TV Channel Now July 73 44  
IC's for Colour TV June 72 36  
Matrix TV Jan 75 10  
Picture-to-Signal Dec 74 10  
Pocket-sized TV Camera Feb 73 42  
School in the Sky Mar 73 50  
Teletext Takes Off July 75 18  
Understanding Colour TV Pt. 1 Feb 75 52  
Pt. 2 Mar 75 51  
Pt. 3 Apr 75 45  
Pt. 4 May 75 51  
Pt. 5 June 75 47  
Pt. 6 July 75 58  
Pt. 7 Aug 75 50  
Pt. 8 Sept 75 54  
Pt. 9 Oct 75 50  
Pt. 10 Nov 75 61  
Apr 72 67  
Oct 74 46

**Video Cassettes**  
Video-Disc Colour TV Oct 74 46

**MISCELLANEOUS**

Arc Welding Today Mar 74 24  
Automatic Cameras May 73 20  
Cooking by Microwaves Jan 74 19  
Counting Photons Feb 75 18  
Digital Servicing Tools July 74 24  
Electricity from Windmills July 73 53  
Electronic Watches Aug 72 14  
Electronic Speed Control for Motors Jan 75 48  
Electronics in the Antarctic May 72 20  
Electronics in Crime Pt. 1 Oct 74 10  
" " Pt. 2 Nov 74 47  
" " Pt. 3 Dec 74 51  
Electronics in Knitting Nov 74 18  
Electronics in the Olympics Aug 72 20  
Electronics in Small Boats Jan 73 12  
Electronics Reference Data Supplement Nov 75 —  
Exploration Archaeology July 73 26  
Fibre Optics in Cars Jan 74 50  
Fibre Optics Today Feb 73 20  
Geophysical Survey Pt. 1 Jan 76 30  
Pt. 2 Mar 76 47  
Heat Pipes Feb 74 55  
High Temperature Batteries Apr 75 14  
The Home Workshop July 75 10  
How noisy is Concorde? Sept 72 14  
Kilovolts and Megawatts Oct 73 37  
Linear electric motors Dec 73 64  
Magnetic Levitation Oct 73 26  
Magnetic River Aug 74 10  
Man and Machine Jan 74 19  
Modern Food Preservation Jan 73 65  
Multimeter Guide Dec 75 54  
Murphy's Laws Oct 72 69  
Nuclear Fallout Dec 73 16  
Numbers Oct 73 62  
Phone Phreaking Mar 73 12  
Photophone Sept 75 45  
Printed Circuits June 72 20  
Reactance Chart Sept 74 37  
Safety Barriers Oct 72 35  
Science in Art May 75 10  
Sincral Digital Watch Jan 76 17  
Solar Solution Sept 73 44  
Technical Phrases Feb 75 37  
Time check for Radio-Carbon Dating Oct 74 22  
Unreasonable Radiation Nov 73 48  
Watergate Bugging Sept 73 27  
What's Bugging You? June 72 14  
When the lights go out Feb 74 34  
Window Cleaning Electronically Oct 74 30

The numbers after the issue Date refer to the pages. Miscellaneous listings come at the end of the section.

# BOOK REVIEWS

ABCs of Infra-Red Apr 72 81  
ABCs of Integrated Circuits April 72 82  
Basic Electron Devices Dec 72 82  
Beginners Guide to Transistors June 72 79  
Beyond Freedom and Dignity May 72 82  
Computer Programming Management Apr 74 49  
Computer Security Jan 74 74  
Dictionary of Electrical Engineering Apr 74 49  
Dictionary of Electronics Apr 72 82  
Dictionary of Telecommunications May 72 81  
Digital Electronics Mar 74 33  
Electrical Engineers Reference Book Apr 74 49  
Electronic Power Supplies Dec 72 82  
Electronic Design Data Book May 73 72  
Electronics — A Course Book for Students June 73 34  
Electronics in Music June 73 34  
Feedback Amplifiers and Oscillators Oct 72 81  
Foundations for Electronics Mar 73 82  
Foundations of Wireless and Electronics Mar 74 33  
Ham Radio — a Beginners Guide May 73 72  
Illustrations in Applied Network Theory Jan 74 74  
Integrated Circuit Systems Jan 73 82  
Logical Design for Computers and Control Sept 72 81  
Newnes Radio Engineers Pocket Book Jan 73 82  
Novel Experiments with Electricity July 72 77  
Photoelectronic Devices Aug 72 78  
Power Electronics April 74 49  
Practical Thinking May 72 81  
Pulse Digital and Switching Waveforms Nov 72 85  
Radio and Electronic Laboratory Handbook Feb 73 85  
Radio Television and Audio Test Instruments June 72 79  
Reliability Engineering April 73 88  
Electronics and Scientific Instruments June 72 79  
Survey of Electronics April 73 88

Tape Questions—Tape Answers Dec 72 82  
The Greening of America Apr 72 81  
The Population Bomb June 72 79  
The Radio Amateurs Handbook Aug 72 78  
Thermistors Oct 74 34  
Thick Film Circuits Jan 74 74  
Thyristor Control Oct 74 34  
Transistor Audio Amplifiers Apr 72 82  
Transistor Audio and Radio Circuits — 2nd Edition May 73 72  
Transistor Circuit Design Tables June 73 34  
Understanding Lasers and Masers Feb 73 85  
Understanding Electronic Circuits Jan 74 74  
Understanding Solid State Electronics Mar 74 33  
Voltage and Power Amplifiers Oct 72 81  
Worlds — Antimatter — Antimatter in Cosmology Feb 73 85  
20 Solid State Projects for the Car and Garage Sept 72 81  
110 Integrated Circuit Projects Sept 72 81  
110 Semiconductor Projects for the Home Constructor May 72 82





# ANOTHER FABULOUS ETI OFFER

## THE EXELAR

Digital Watch

# £14.95!

INCLUDING VAT AND POSTAGE



The Exelar. Never heard of it? You certainly haven't heard of any digital electronic watch at this price.

Exelar is a new name for the Digital Watch products of National Semiconductor; in fact N.S. make all the electronics themselves for this new range and Exelar is a name that you'll probably get to know pretty well.

This offer is a prelude to the launch of this watch — and ETI once again has been able to arrange an enormous discount for readers. Response to offers in the past has shown that ETI readers are very quick to appreciate new technologies and the resulting products and this enables us to come up with the really good deals for which we are known.

The NW1-WS is a three-function watch: Hours, Minutes and Seconds with a typical accuracy of 5 seconds per month. The bright, easy-to-read LED display is one of the few in the industry which takes advantage of the crisp clarity of monolithic digits. The bezel is chrome plated, the back is stainless steel and the strap is leather.

The recommended retail price of the Exelar is over £20, itself setting a new record low for a built watch but using the coupon you pay just £14.95 including VAT and postage. Don't delay — an enormous response is expected.

For operation of the Exelar, press the button and the hours and minutes are displayed. Keeping the button depressed will display flashing seconds. The display stays on for 1½ seconds after touching the button. Time setting is accomplished by pressing a recessed push switch in conjunction with the display button.

### AVAILABILITY

ETI Offers in the past have been so successful that initial estimates of quantity have sometimes proved to be inadequate. Several thousand units are being stocked but if orders exceed this, delays may result.

If you have *not* received your watch before publication of the April issue, see that month's News Digest for the situation.

Although orders will be despatched as soon as possible after receipt, please allow 35 days for delivery.

For security reasons, no stocks of the Exelar are being held at ETI offices for callers.

**IMPORTANT:** Please write clearly and put your name and address on the back of your cheque and all P.O.'s. This will enable us to sort out any problems quickly.

### CUT COMPLETE COUPON


To: EXELAR WATCH OFFER  
ETI Magazine,  
36 Ebury Street,  
London SW1W 0LW.

Please find enclosed my cheque/P.O. for £14.95 payable to Electronics Today International (Exelar Offer). **IMPORTANT:** Please write your name and address on the back of your cheque and P.O.'s.

This coupon will be used to dispatch your Exelar digital watch. The offer is strictly limited to one watch per coupon. Orders will be despatched as soon as possible but please allow 35 days for delivery and read note on availability.

**OFFER CLOSES MARCH 31st 1976**

FOR OFFICE USE	
NAME .....	NAME .....
ADDRESS .....	ADDRESS .....
PLEASE USE BLOCK CAPITALS	

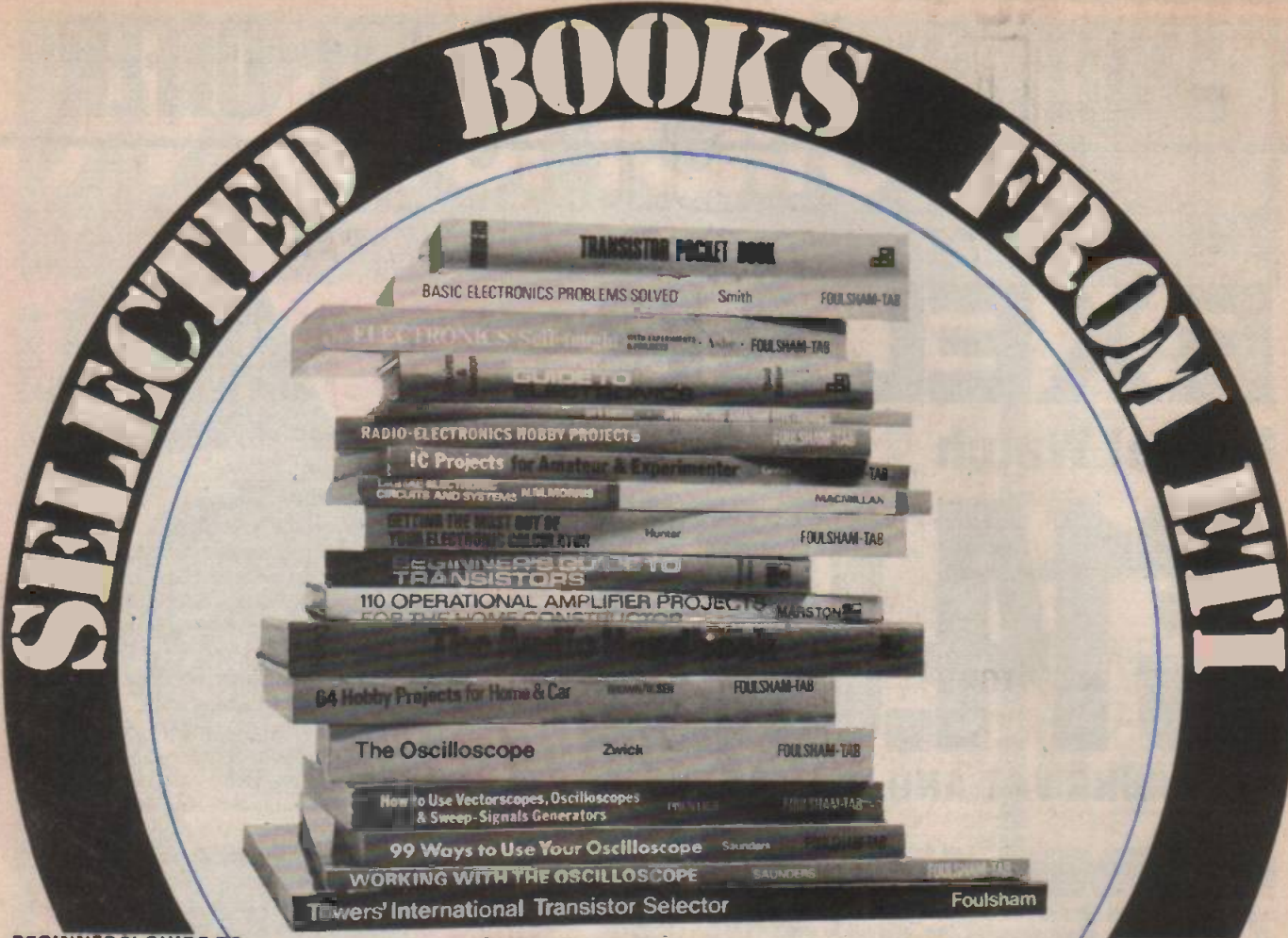

### BEGINNERS' GUIDE TO ELECTRONICS

**T. L. Squires** £2.55  
A short cut for those wishing to obtain a quick acquaintance with modern electronics.

### I.C. OP-AMP COOKBOOK

**W. J. Jung** £8.15  
Covers the basic theory of IC OP-Amp in great detail, also includes 250 practical circuit applications liberally illustrated.

### TTL COOKBOOK

**D. Lancaster** £5.80  
Complete and detailed guide to TTL, how it works, how to use it and practical applications.

### 110 OPERATIONAL AMPLIFIER PROJECTS FOR THE HOME CONSTRUCTOR

**R. M. Marston** £2.85  
Outlines the essential characteristics of the OP AMP and presents 110 useful projects.

### 110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR

**R. M. Marston** £2.85  
This book introduces the reader to useful new devices such as the FET, SCR and IC, with full constructional details of many useful circuits.

### UNDERSTANDING CMOS INTEGRATED CIRCUITS

**R. Molan** £3.25  
Begins with basic digital ICs, covers semiconductor physics, CMOS fabrication technology and design.

### INTEGRATED ELECTRONICS

**J. Millman** £5.00  
Using an integrated circuits approach this text leads the reader step by step from semiconductor physics to devices, models, circuits and systems.

### LINEAR IC PRINCIPLES EXPERIMENTS AND PROJECTS

**E. M. Holl** £5.80  
An introduction to one of electronic's most exciting devices.

### DESIGNING WITH TTL INTEGRATED CIRCUITS

**Texas Instruments** £5.55  
Covers the entire family of TTL and practical applications of the circuits in digital systems.

### OPERATIONAL AMPLIFIERS DESIGN AND APPLICATION

**G. Tobey (Burr-Brown)** £4.70  
Completely up to date, this work covers the entire field of operational amplifiers.

### BEGINNERS' GUIDE TO TRANSISTORS

**J. A. Reddihough** £2.55  
Covers the basic theory and practice of modern transistors.

### COLOUR TV THEORY

**G. F. Mutson** £4.65  
PAL Systems, principles and receiver circuitry for engineers, technicians and students.

### TV SERVICING HANDBOOK

**G. King** £5.00  
Thoroughly practical handbook, deals in detail with modern receivers.

### COLOUR TELEVISION SERVICING

**G. King** £5.90  
A practical handbook, dealing with all modern receivers.

### MAZDA BOOK OF PAL RECEIVER SERVICING

**D. Seal** £5.30  
A practical handbook with over 200 illustrations.

### THE OSCILLOSCOPE

**G. Zwick** £2.10  
Starts from the first principles and takes the reader to an advanced level.

### HOW TO USE VECTORSCOPES OSCILLOSCOPES AND SWEEP SIGNAL GENERATORS

**S. Prentiss** £1.95  
It goes into the whole subject deeply, in 250 heavily illustrated pages.

### 99 WAYS TO USE YOUR OSCILLOSCOPE

**A. Saunders** £1.80  
Describes how to solve practical problems using a scope.

### WORKING WITH THE OSCILLOSCOPE

**A. Saunders** £1.85  
A book devoted to circuits and illustrations of waveforms that should be present.

### HOW TO USE YOUR VOM VTVM AND OSCILLOSCOPE

**M. Clifford** £1.80  
This book aims to give you knowledge and help you perform a wide variety of essential tests on many different kinds of sets, appliances and equipment.

### ELECTRONICS SELF-TAUGHT WITH EXPERIMENTS AND PROJECTS

**J. Ashe** £2.20  
Covers basic principles of electronics. Projects include a large number of simple circuits.

### LOGIC CIRCUITS

**N. M. Morris** £3.10  
Aids the understanding of logical problems, discusses circuit principles including integrated circuits.

### INTRODUCING AMATEUR ELECTRONICS

**I. R. Sinclair** £1.60  
The book for the complete novice of any age, as no previous knowledge is assumed.

### TEST INSTRUMENTS FOR ELECTRONICS

**M. Clifford** £2.05  
How to build and use test instruments.

### ELECTRONICS MUSICAL INSTRUMENTS

**N. Crowhurst** £2.05  
This book looks at the fascinating subject of electronic music from almost every angle.

### EXPERIMENTING WITH ELECTRONIC MUSIC

**R. Brown and M. Olsen** £1.85  
Practical Experiments offer scope for originality and research.

### BASIC MATHS COURSE FOR ELECTRONICS

**M. Jacobowitz** £1.70  
Ohms Law and all maths for electronics written in an easy, understandable way.

### ELECTRONICS UNRAVELLED

**J. Kyle** £2.20  
A new commonsense approach to the basic principles of electronics.

### DIGITAL ELECTRONIC CIRCUITS AND SYSTEMS

**N. M. Morris** £2.60  
The ideal book for the enthusiast confused by logic and digital techniques.

### INDUSTRIAL ELECTRONICS

**N. M. Morris** £3.20  
The book concentrates mainly on semiconductor devices and circuits solutions to the many numerical problems are given. S.I. units are used throughout.

### HOW TO BUILD ELECTRONIC KITS

**V. Capel** £2.10  
Instructs the reader on how to check components, how to assemble and how to cure faults.

### FOUNDATIONS OF WIRELESS AND ELECTRONICS

**MN. G. Scroggie** £4.25  
Ninth edition of this ever-popular basic theory book which starts from scratch.

### RADIO, VALVE & SEMI-CONDUCTOR DATA

**A. M. Ball** £2.50  
Tenth edition, gives data on 1,000 valves and CRTs, 9,800 transistors, diodes, rectifiers and optical devices.

### ELECTRONICS CIRCUIT DESIGN HANDBOOK

**By the Editors of EEE Magazine** £5.20

Please list titles (with price) separately. Cheques, etc., to be payable to Electronics Today International and sent to:

**ETI BOOK SERVICE, 25 Court Close  
Bray, Maidenhead, Berks.**  
All prices include Postage and Packing.

# GEOPHYSICAL SURVEYS

PART TWO

by Martin Blanchard

THE THREE CHARACTERISTICS studied in modern airborne surveys are (a) Magnetic, (b) Radioactive and (c) Thermal. Last month we looked at the techniques and equipment used in magnetic surveys; this second part of the article covers the other two methods.

## RADIATION DETECTORS

Gamma rays are detected by the ionisation effect that they have on some materials. Early radiometric work was done using Geiger tubes but these have now been superseded by scintillation type detectors (in airborne geophysical work). The basic detector consists of a crystal (usually sodium iodide) which gives a flash of light (usually in the blue to UV region) caused by a gamma ray being absorbed and giving up its energy.

The scintillation crystal is superior to Geiger tube for two reasons: (a) it is a denser medium so detection efficiency is improved, and (b) its 'recovery time' is short. This second factor is important because several gamma rays may arrive at the detector within a short interval.

The scintillations are amplified in a photo-multiplier (PM) tube which is in direct contact with the crystal. This assembly is then mounted in a light proof container. The process of amplification begins when photons emitted during a scintillation strike the photo-cathode and displace a quantity of electrons. Due to the voltage arrangement of the PM tube plates these electrons are drawn to the next cathode in the tube where they displace a greater number of electrons. In turn these strike the next cathode and so on up the cathode chain until the output appears as a voltage pulse at the anode. The combination of crystal and PM tube is termed a detector head and is shown in Fig. 1.

## SCINTILLOMETERS

A scintillometer consists of a detector head, a power supply and a pulse counting circuit. PM tubes require

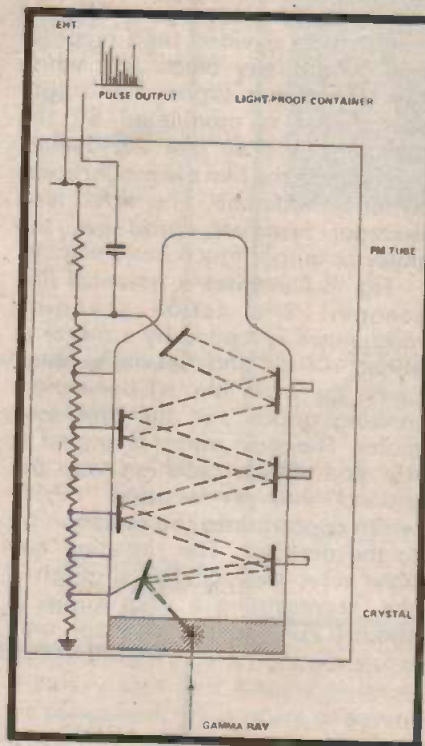


Fig. 1. Scintillation Detector Head.

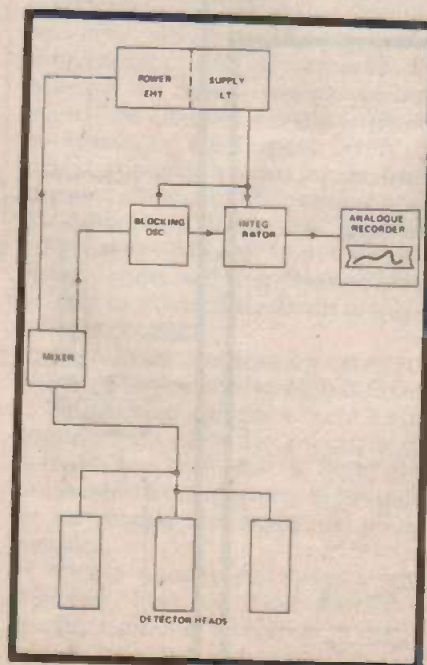


Fig. 2. Scintillometer.

an EHT supply of about 1.5kV but do not draw much current. Fig. 2 shows an early scintillometer which uses three detector heads. The heads are connected to a mixer circuit where the incoming pulses are channelled on to one signal line. The incoming pulses trigger a blocking oscillator which gives constant amplitude and width pulses to feed an integrating circuit. The integrator output is displayed on an analogue recorder. Other scintillometers use a ratemeter (for counting the pulse rate) and a digital read-out. The scintillometer counts one pulse regardless of the energy of a detected gamma ray and is therefore often called a total count detector.

## SPECTROMETERS

A spectrometer is a scintillation counter with a facility for discriminating between the various energy levels of the gamma rays being absorbed by the crystal. The intensity of each scintillation is directly proportional to the energy of the gamma ray causing it.

Each part of the radiation spectrum which is counted is termed a 'channel'. Four channels are commonly used with the channel limits set as follows:

- Channel 1: 0.9 to 2.9MeV
- Channel 2: 1.36 to 1.56MeV
- Channel 3: 1.66 to 1.86MeV
- Channel 4: 2.3 to 2.9MeV

Channel 1 is usually called the total channel and the other channels are often named after the radioactive element that has a major energy peak (or peaks) between the various limits: Channel 2, Potassium; Channel 3, Uranium; Channel 4, Thorium.

A complete spectrometer is shown in Fig. 4. This has a common detection system comprising three units each of which contains three separate detector heads. The total number of detector heads is therefore nine, each with a 6 by 4 inch crystal. This arrangement provides a good sensitivity combined

# ELECTRONICS IN GEOPHYSICAL SURVEYS

with a relatively small space requirement.

## OPERATIONAL TECHNIQUES WITH SPECTROMETERS

Because of the attenuation of gamma rays in the atmosphere and in surface material the altitude at which spectrometers may usefully be operated is limited to about 200 metres and in general the best results are obtained at the lowest possible altitude. All the spectrometer equipment is carried inside the aircraft, including the detector heads. These must be carefully sited so that there is a minimum of scattering and absorption of gamma rays by the aircraft structure. Background radiation from the aircraft (for example from luminous instruments) must also be kept to a minimum. Survey areas to be covered using a spectrometer are flown in parallel lines like magnetometer surveys. The low altitude means that a narrow line spacing must be used.

## INFRA-RED SCANNERS

IR line scanners are electro-optical devices which reflect radiation from the ground on to an IR detector. Much of the IR radiation spectrum is absorbed in the atmosphere but there are two windows at wavelengths of between 0.0003 and 0.0005cm and 0.0008 to 0.0014cm. The detectors used are manufactured from various semiconductor materials which have

different responses in parts of the IR spectrum. The materials most frequently used are, for the 0.0003 to 0.0005cm region, Indium Antimonide (InSb) and for the 0.0008 to 0.0014cm region, doped Germanium. In order to reduce their internal thermal noise these detectors are cooled to low temperatures — Indium Antimonide to 77°K (-196°C) and doped Germanium to less than 10°K (-263°C). This cooling is achieved by the use of gases such as nitrogen and helium in their liquid state.

The detector output is usually recorded on a video tape recorder and on ordinary black and white film. The film is exposed to a light source that is modulated by the detector signal so that the density variations in the film are proportional to the IR radiation. The video tape recorder however, produces the detector output much more exactly.

Fig. 5 illustrates a practical line scanner. The actual scanning mechanism is rotated by a motor at about 100rps and has three main parts: the main mirror, the synchronizing device and the film scan motor. The main mirror is angled at 45° and reflects radiation from the ground into a focusing device which concentrates the radiation on to the detector. The radiation can only enter the scanner through a slot, representing a scan angle of about 120°, so the detector only

receives a signal for one-third of a rotation cycle. The detector is cooled from an insulated flask containing liquid gas and the detector output is taken to a pre-amplifier stage. The pre-amplifier output goes to a gain control and the main amplifier and is also sampled by a gate controlled with a synchronizing pulse from a lamp and photo-electric device mounted on the scanner shaft. This device is triggered when the scanning mirror is 'looking' at the inside of the scanner housing so that the gate passes a sample of the pre-amplifier output when it is theoretically zero and any undesired signal which does occur, due to dc drift or changes in detector response, is integrated and fed back to the pre-amplifier input to adjust the no signal output to zero. After the gain control and main amplifier the signal is fed to another gate which is also controlled from a photo-electric device on the scanner shaft. This gate is 'opened' only during the 120° of scan rotation when a signal is present.

The final amplifier stage provides outputs to the monitoring oscilloscope, the video tape recorder and a voltage-to-current converter which modulates the film light source. The modulated beam from the light source is reflected on to the film by a mirror mounted on the scan shaft so that each scan builds up an image on the film. The oscilloscope display is

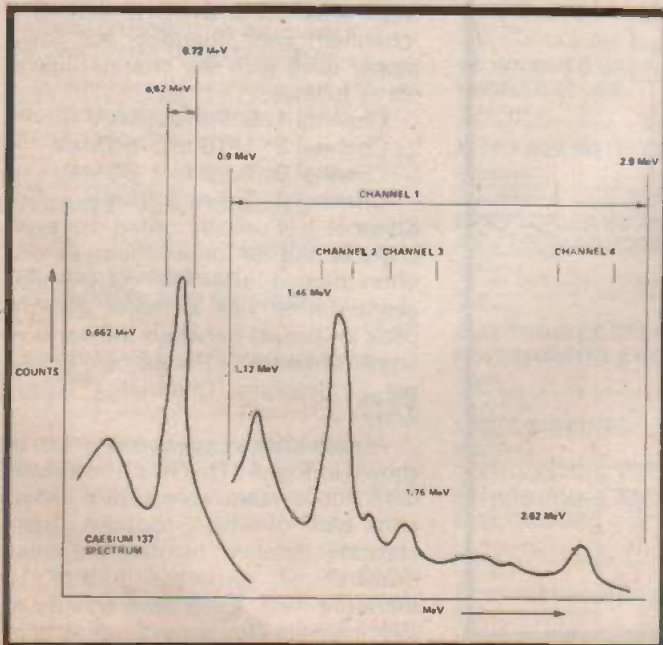


Fig. 3. Gamma Ray Energy Spectra.

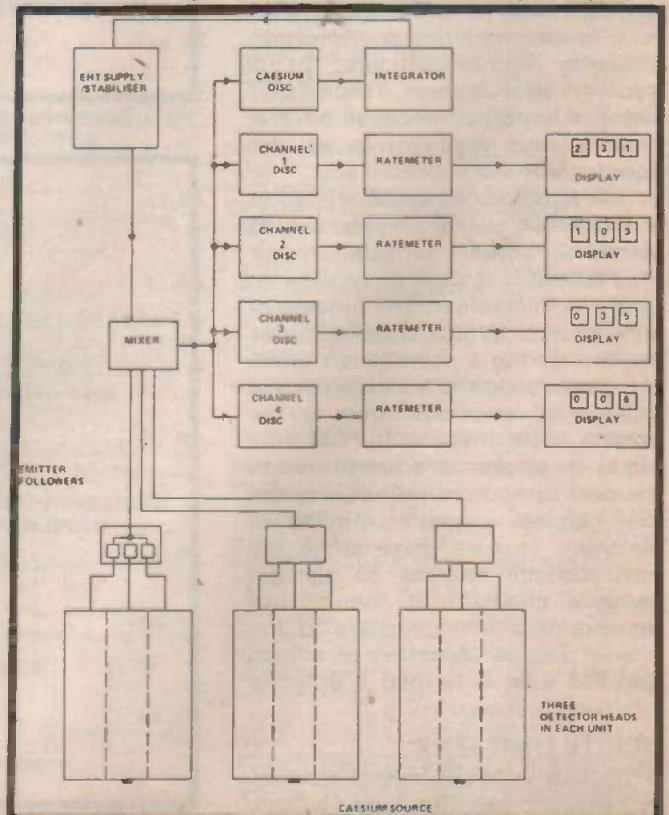


Fig. 4. Spectrometer.



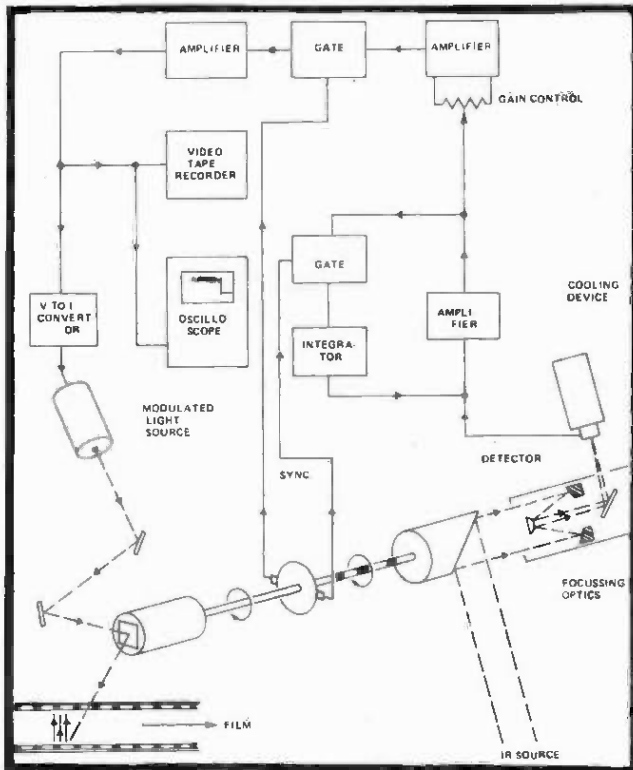


Fig. 5. above, IR Line Scanner.

viewed by the scanner operator to monitor the equipment performance and any necessary adjustment of the system gain.

## OPERATIONAL TECHNIQUES WITH IR LINE SCANNERS


The height at which IR line scanners are operated is determined by the resolution required. The lower the altitude the better the resolution, although, of course, at low altitude a smaller area is covered in each scan. The minimum operating altitude is limited for any particular aircraft speed by the scan speed if complete coverage is to be maintained. Normally temperature differences of about 0.5° C can be detected from a height of 500 metres.

The time of day when IR line scan surveys are flown is important, due to the different temperature effects occurring through a day. During the night temperature differences are often accentuated but any mist and fog tends to absorb radiation. Often a survey area is flown at two or more times of the day to provide more information for interpretation. Operation is usually stopped during high winds as these tend to 'smear' the temperature profiles.

## NAVIGATION TECHNIQUES

The problem of navigating in survey areas is a critical one. Obviously geophysical results are not very useful if the location in which they were obtained is not known exactly.

Fig. 6. Equipment used in a Spectrometer Survey.

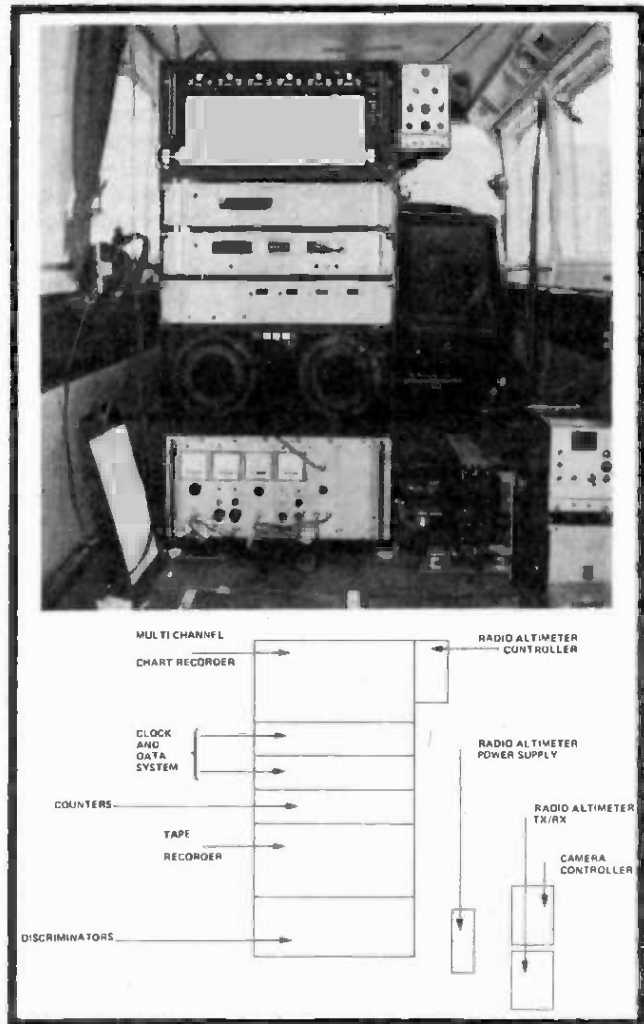

Often there are no accurate maps of a survey area and navigation must be carried out on mosaics of survey photographs (the accuracy of which is sometimes doubtful). A frequently used navigation aid is the Doppler navigator, which has the important characteristic that it requires no beacons or other external equipment. The Doppler navigator works by measuring the Doppler 'shift' of radio-frequency transmissions from the aircraft which are received back as reflections from the ground. Information derived from the frequency shifts and from the compass is used to guide the aircraft along a straight course.

The main navigation aid for checking where an aircraft has flown is the tracking camera which is run continuously while the aircraft is on a flight line and after a flight the processed film allows the flight path to be plotted on maps or photo mosaics.

All the geophysical instruments described here are flown so that a constant ground clearance is maintained. However, over rough terrain this is not possible using barometric

altimeters so radio altimeters are used. A radio altimeter transmits a swept range of RF towards the ground and then receives the reflections. The transmitted and received frequencies are mixed to produce an audio frequency signal which is the difference between the frequency transmitted at a particular instant and the frequency being transmitted when that signal returns. This frequency difference is proportional to time (i.e. to the sweep speed) and therefore to the altitude of the aircraft. The audio frequency is converted to dc to drive a pilot's indicator and provide outputs for the recording devices. Radio altimeters have accuracies of better than  $\pm 1$  meter in 150 metres.

## DATA SYSTEMS

In recent years it has become the practice to record all information from the navigational and geophysical equipment on magnetic tape. The instrument outputs are sampled at a fixed interval, the timing being controlled from a master clock which also registers on the tracking camera film to ensure correct orientation of

# GEOPHYSICAL SURVEYS



Rack of geophysical electronic equipment—Top shelf—Spectrometer console and mixer box. Centre shelf—Magnetometer console and various flight recorders. Background—Two spectrometer detector heads.

the survey data with the flight path plot. The taped data can only be read out if special facilities are available so the survey data is also recorded in analogue form on multi-channel chart recorders. This procedure also guards against un-noticed faults in the magnetic recording.

## GENERAL OPERATIONAL TECHNIQUES

Generally the need for an airborne survey is decided upon by the possibility of a specific mineral appearing in a particular area. The geophysical instrument to be used is selected for its efficiency in detecting that mineral.

Once the basic instrument has been selected a second instrument is often chosen to provide additional information to aid in interpretation. Fig. 6 illustrates some of the equipment required for a spectrometer survey. The detector heads are not shown. The type of geophysical equipment selected governs the survey operating parameters. If a spectrometer is in use the maximum operating altitude is determined by the spectrometer detection sensitivity and the minimum operating altitude by safety considerations.

Frequently, spectrometer surveys are flown at an altitude of 150 metres but this means that to maintain adequate ground coverage the flight lines must be fairly close together, say at about 400 metre spacing. The flight lines are marked on to navigational maps or photo mosaics and are flown progressively with the aid of navigational equipment. Lines that are flown in the wrong place or are subject to an equipment failure are usually reflown at the end of the survey.

When all the survey area is satisfactorily covered the geophysical information is plotted on to the grid of flight lines and contour maps are drawn. Computerised data may be printed out in the form of contour maps. Depending on the type of survey the contour lines are of equal magnetic field or equal radiometric count rate and the maps are interpreted by geophysicists and geologists to predict the location of possible mineral deposits.

Field investigation of selected sites can begin immediately and so it is that airborne geophysical surveys enable the few commercially viable sites in a very large unexplored area to be located in a relatively short time.

## 6-Digit Digital Clock Kits

- 12/24 HOUR
- 50/60 HERTZ
- BRIGHT DISPLAYS
- SLOW TIME SET
- FAST TIME SET
- TIME HOLD



# £6.95\*

+ 90p Airmail p&p

The response to our advert in the December issue was phenomenal. We are therefore extending this special offer so that you can get a second chance to purchase this fantastic bargain in case you missed the first offer. If you've been considering building a digital clock but were discouraged at the high prices, we have just removed your last excuse.

### KIT COMPRISES:

- 1 — National MM5314 Clock Chip, 12/24 hour, 50/60 Hz option.
- 6 — Bright red common cathode displays, 0.27" character height.
- 7 — NPN Segment driver transistors.
- 6 — PNP Cathode driver transistors
- 9 — Carbon resistors
- 5 — Diodes
- 2 — Disc caps
- 1 — Electrolytic filter cap
- 3 — Switches for time setting functions
- 2 — Etched, drilled and plated p.c. boards.
- 1 — Illustrated assembly instructions manual

All you provide is a 9-12v ac/200 m/a Transformer and case of your choice.

### OPTIONAL JUMBO DISPLAYS

You can have 6 — 0.5" Jumbo displays with a suitable board instead of the 0.27" types. Clock kit with 6 jumbo displays £10.95\* + 90p airmail p&p

### ★ ORDERING INFORMATION


The above prices shown in British £s are approximate equivalents of the following U.S. Dollar prices and should be used as a guide only.

Clock kit with 6 — 0.27" displays U.S. \$16.50 post paid.  
Clock kit with 6 — 0.50" displays U.S. \$24.75 post paid.  
Remittance by BANK DRAFTS or INTERNATIONAL MONEY ORDERS IN U.S. FUNDS. SENT ANYWHERE IN THE WORLD.

NO ELECTRONICS KNOWLEDGE REQUIRED TO BUILD THESE KITS

**sabtronics**  
INTERNATIONAL

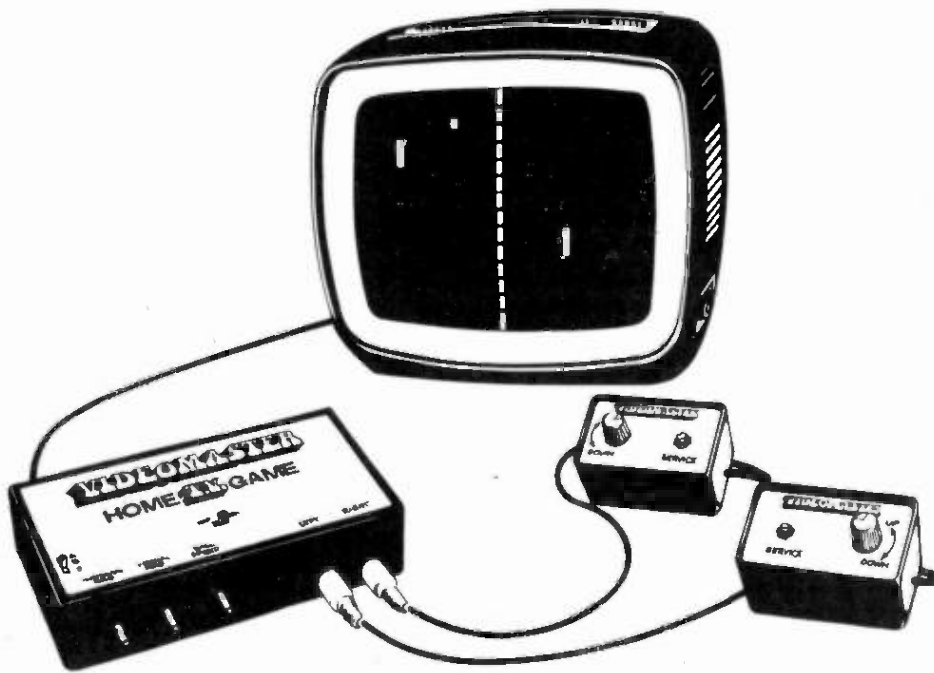P.O. Box 64683, Dallas, Texas 75206, U.S.A.



# Videomaster urge all good electronics enthusiasts to play the game

The best thing about the Videomaster Home T.V. Game Mk. III is that the sheer pleasure of building it is immediately followed by the excitement of playing three fascinating games.

The famous Videomaster is now available for you to make. It plugs into any standard UHF 625 line TV set, and it shouldn't take you longer than a few hours to build.

In detail . . . The Videomaster Mk. III has eleven integrated circuits . . . four transistors . . . eleven diodes . . . is easy to build . . . with no alignment necessary because with ready-built and tested transistorized UHF modulator, is complete with all parts . . . including fully drilled and prepared p.c.b. . . handsome plastic box . . . control leads . . . complete step by step assembly instructions . . . Runs on a PP7 9 volt battery . . . and has logic and analogue "state of the art" circuitry all with National Semiconductors CMOS devices . . . with full specification.

The cost? Only **£19.95** (+ VAT)

POST TODAY TO:

## Videomaster Ltd

119/120 Chancery Lane, London WC2A 1QU

Please send me . . . . . (insert no.) Videomaster Mk. III kits at £21.55 ea. inc. VAT. P & P

I enclose my cheque/money order for £ . . . . .

Tick if VHF Modulator required  -£1 extra

NAME

ADDRESS



ET1/6

ALLOW 14 DAYS FOR DELIVERY

TTLs by TEXAS				C-MOS LOGIC		OP. AMPS		TRANSISTORS		'2N412318p		DA90			
7400	13p	7483	80p	CD4000AE	19p	145B	Dual Op Amp Int Comp	R pin DIL	70p	BF182	33p	2N4126	18p	DA91	7p
7401	14p	7484	95p	CD4002AE	19p	301A	Ext Comp	R pin DIL	100p	BF184	22p	2N4289	20p	DA95	7p
7402	14p	7485	120p	CD4003AE	67p	3130	CD5MOS B-Polar MosFet	R pin DIL	70p	BF185	22p	2N4347	130p	DA900	8p
7403	20p	7486	30p	CD4011AE	67p	3900	Quad Op Amp	10-99	275p	BF194	10p	2N4348	160p	OA202	10p
7404	16p	7489	270p	CD4012AE	19p	709	PET Op Amp	8 1/4 pin DIL	30p	BF195	9p	2N4401	30p	IN14	4p
7405	16p	7490	40p	CD4013AE	19p	741	Int. Comp	8 1/4 pin DIL	25p	BF196	14p	2N4403	30p	IN1418	4p
7406	38p	7491	75p	CD4014AE	19p	747	Dual 741	14 pin DIL	22p	BF197	15p	40360	40p		
7407	36p	7492	45p	CD4015AE	19p	748	Ext Comp	8 pin DIL	36p	BF200	32p	40361	38p		
7408	14p	7493	40p	CD4016AE	55p	775	Programmable Op Amp	TC-5	150p	BF257	32p	40362	40p		
7409	14p	7494	40p	CD4017AE	120p					BFR39	30p	40364	120p		
7410	13p	7495	65p	CD4018AE	175p					BFR40	30p	40409	55p		
7412	23p	7496	76p	CD4019AE	175p					BFR79	30p	40410	55p		
7413	32p	74107	30p	CD4020AE	175p					BFR80	30p	40411	225p		
7414	60p	74121	30p	CD4021AE	175p					BFR88	30p	40594	75p		
7416	33p	74122	46p	CD4022AE	170p					BFX30	30p	40595	85p		
7420	14p	74123	68p	CD4023AE	19p					BFX84	26p				
7422	18p	74141	65p	CD4024AE	120p					BFX85	25p				
7423	34p	74151	72p	CD4025AE	19p					BFX86	25p				
7425	30p	74153	85p	CD4026AE	19p					BFX87	20p				
7427	37p	74154	150p	CD4027AE	75p					BFX88	24p				
7430	14p	74155	75p	CD4028AE	140p					BFX89	24p				
7432	25p	74156	75p	CD4029AE	175p					BFX89	24p				
7437	25p	74160	99p	CD4030AE	55p					BFX89	24p				
7440	14p	74161	99p	CD4031AE	55p					BFX89	24p				
7441	65p	74162	99p	CD4032AE	55p					BFX89	24p				
7442	60p	74163	99p	CD4033AE	55p					BFX89	24p				
7447	75p	74166	120p	CD4034AE	137p					BFX89	24p				
7448	70p	74166	125p	CD4035AE	137p					BFX89	24p				
7450	15p	74174	120p	CD4036AE	140p					BFX89	24p				
7451	16p	74175	85p	CD4037AE	184p					BFX89	24p				
7453	16p	74180	100p	CD4038AE	63p					BFX89	24p				
7454	16p	74181	298p	CD4039AE	190p					BFX89	24p				
7460	15p	74182	82p	CD4040AE	135p					BFX89	24p				
7470	27p	74185	135p	CD4041AE	135p					BFX89	24p				
7472	25p	74190	144p	CD4042AE	228p					BFX89	24p				
7473	30p	74191	144p	CD4043AE	37p					BFX89	24p				
7474	30p	74192	120p	CD4044AE	27p					BFX89	24p				
7475	45p	74193	120p	CD4045AE	27p					BFX89	24p				
7476	30p	74194	108p	CD4046AE	130p					BFX89	24p				
7480	50p	74195	75p	CD4047AE	200p					BFX89	24p				
7481	95p	74198	198p	CD4048AE	200p					BFX89	24p				
7482	70p	74199	180p	CD4049AE	120p					BFX89	24p				

Minimum Order £2 P&P 20p Please add VAT to total

All first grade devices Vendors, by appointment, welcome Govt. Colleges, etc orders accepted

**TECHNOMATIC LTD.**  
54 SANDHURST ROAD, LONDON, NW9  
Tel: 01-204 4333

## FREE Brochure on New KITS

Whether professional, student, teacher or amateur, the field of electronics can open up a new world for you.

Please add 15p to cover postage




CROFTON don't just sell kits. We offer you a technical back up service to ensure your success

The following is a selection of some of the more popular kits -

- ★ Mullard CCTV Camera
- ★ PE CCTV Camera
- ★ The 'Mistral' Digital Clock Kit £12.50 incl. VAT + p & p 50p Built £18.00 + p.&p. 50p
- ★ Electronic Ignition
- ★ Sound Operated Flash
- ★ P.W. Tele-Tennis Game
- ★ U.H.F. Modulator
- ★ Bench Power Supply
- ★ Wobbulator
- ★ All ETI Top Projects
- ★ Many of the Elektor Projects

NOTE PCB's for most published projects available to order

### CROFTON ELECTRONICS LTD


Dept C 124 Colne Road, Twickenham, Middx. O1 898 1569

## ETI PCB's

TITLE	PROJECT NO.	ISSUE	BOARD NO.	TOTAL INCL.	TITLE	PROJECT NO.	ISSUE	BOARD NO.	TOTAL INCL.
Int. Stereo Amp	101	Oct 1975	101	£4.21	Type Slide Synchroniser	513	Top Project No 2	025	
Dual Power Supply	105	Apr 1972	014	£1.48	Optical Stop Watch	520	Jan 1974	520A	£2.05
Wide Range Voltmeter	107	Top Project No 1	022	£1.05	Electronic One Arm Beam	529	Sept 1974	529A	£2.32
I.C. Power Supply	111	Jan 1973	111	£1.43	Temp. Controller	530	Mar 1975	530A	£2.32
Thermocouple Meter	113	Dec 1973	113	£1.57	Photo Viewer	532	Sept 1975	532A	£2.32
Dual Beam Adapter	114	Oct 1974	114	£1.07	Optical Display	533	Oct 1975	533A	£2.32
Impedance Meter	116	June 1975	116	£1.01					
Digital Voltmeter	117	Oct 1975	117A	£6.80					
Simple Freq. Counter	118	Nov 1975	118	£6.80	Radar Intruder Alarm	702	June 1975	702A	£1.13
The Revealer	213	Top Project No 1	213	£6.80	Light Dimmer		Apr 1975	702	£6.80
Brake Light Warning	303	Dec 1972	007	£6.80	Intruder Alarm		Sept 1973		£1.24
Automatic Car Theft Alarm	305	Aug 1972	019	£6.80	Digital Alarm Clock			501T	£1.58
International Battery Charger	309	Nov 1973	309	£9.80	Dashboard		Nov 1975	AA/08	£1.58
Electronic Ignition	312	May 1975	312	£1.72					
12V Tractor Auto Amp	314	May 1975	314	£7.50					
ET Home Input Mixer	401	Top Project No 2	005A	£7.50					
Super Stereo	410	Top Project No 2	025	£1.51					
100W Guitar Amp	413	Feb 1973	413	£1.13					
Mixer Mixer	414	Top Project No 1	414A	£1.14					
			414C	£1.52					
			414D	£1.52					
Stage Mixer	414	July 1975	414D	£1.89					
			414E	£1.78					
Mixer Pre-Amp	419	Dec 1973	419	£1.91					
International 420 Four Channel Amp	420	Apr 1974	420A	£1.11					
			420B	£1.21					
			420C	£1.21					
			420D	£1.21					
Discrete 50 Decoder	420E	June 1974	420E	£1.69					
Int. 427 Stereo Amp	422	Aug 1974	422	£2.97					
50 Wpm/Chan Plus Tone Add on Decoder Amp	423	Nov 1974	423	£9.10					
Stereo Rumble Filter	425	Jan 1975	425	£7.50					
Single Stereo Amp	429	Mar 1975	429	£7.50					
Line Amp	430	July 1975	430	£7.50					
Photographic Timer	517	Aug 1972	023	£7.50					

The above mentioned are a few of the more popular boards - for prices of any boards not mentioned please write, sending 15p. Includes VAT and P.&P.

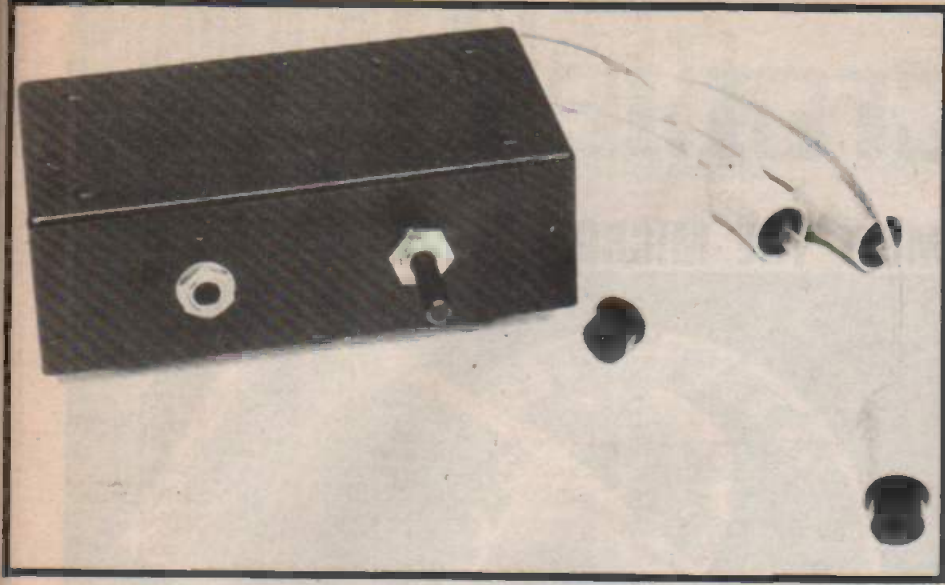**CROFTON ELECTRONICS LTD.**  
Dept. C, 124 Colne Road, Twickenham, Middx. O1-898 1569



# HEADPHONE ADAPTOR

Unit restores damping and natural stereo separation.

HEADPHONES have impedances which range from 8 ohms to 2 k ohms or more and handle a typical maximum power of 500 mW. To limit the power that may be delivered into the 8 ohm types, commercial amplifiers generally supply the headphones from the amplifier output via series resistors of around 220 ohms.

Although this technique allows the use of practically any type of headphones without fear of damage

the series resistor drastically reduces the amount of damping the amplifier can apply to the phones.

A further problem with headphone listening is that the stereo separation is unnatural in that there is little right channel information fed to the left ear and vice versa.

This simple little adaptor is inserted between the amplifier and the leads to the speakers. It restores damping, by supplying the phones from a 10 ohm



- PARTS LIST — ETI 238**
- Two 100 ohm 1 watt resistor
  - Two 10 ohm ½ watt resistors
  - Two 4-way screw type speaker connectors
  - One 100 ohm linear potentiometer
  - One stereo headphone socket with double-pole break contacts box (as required)
  - One 2-pin DIN plugs (if required)
  - Two 2-pin DIN line sockets (if required)

source, and has a blend control by which the separation between channels can be varied to obtain a more natural sound.
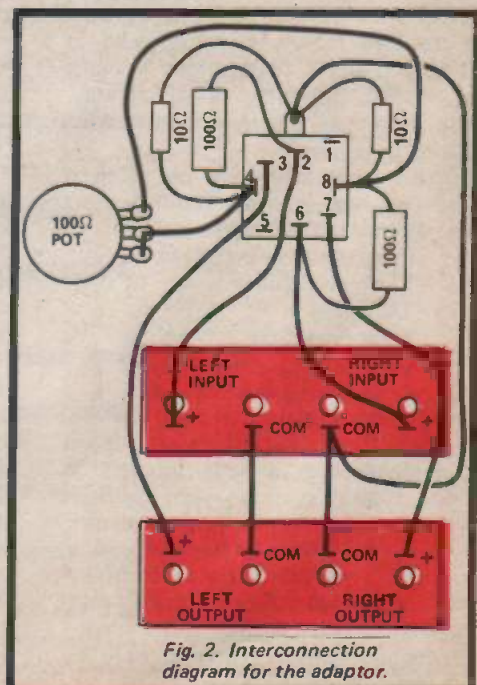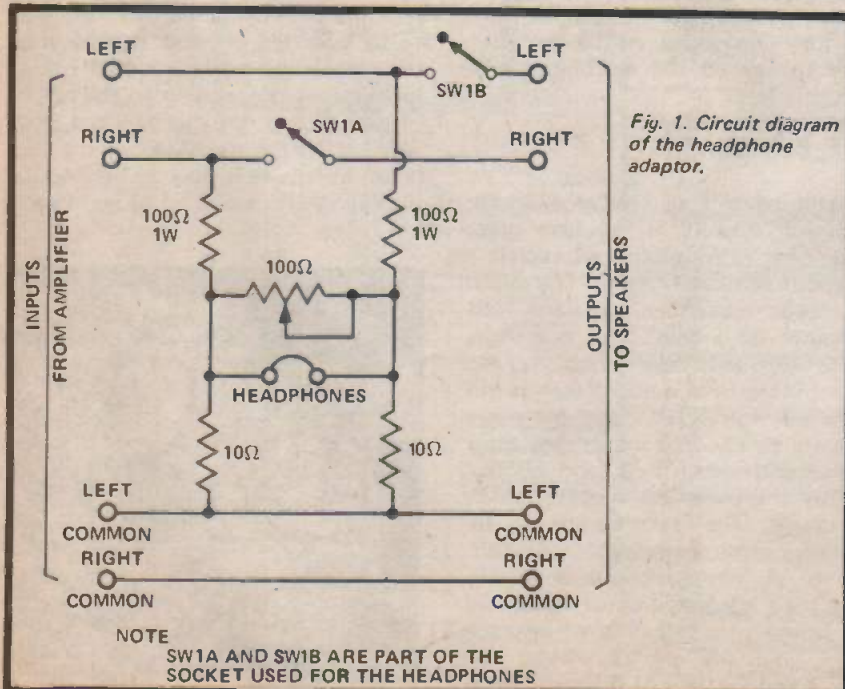
### CONSTRUCTION

We mounted the two four-way terminal strips onto the lid of a small box and the headphone socket and potentiometer through one side. The stereo-headphone socket should be the type which incorporates double-pole break contacts. This type is generally of sealed construction and has 8 pins on the back. Such a socket is necessary so that normal speaker operation is obtained until the headphones are plugged in whereupon the speakers are automatically disconnected.

Wire the unit as shown in the interconnection diagram, and, if the amplifier has DIN connectors, attach short leads, with DIN plugs and sockets, to the unit as shown in the main photograph.



## MEET THE MICRO

## ETI REPORTS



NO, YOU CAN'T USE IT FOR YOUR HOMEWORK . . . I'M LOADING IN TOMORROW'S RUNNERS AT KEMPTON!


IN THE FIRST OF several articles under the title ETI Microfile, we'd like to introduce you to our star performer who is currently enjoying fantastic reviews in the States. We refer, of course, to the multi-talented micro-processor.

This device has been getting mentions in ETI for the past few months, (N.D., Desk Top Graphics), but we've never really said what it is, what it does, or how it does it. In fact, nobody really seems to have thought of passing on microprocessor information to the interested experimenter in a comprehensive way. Micros are rapidly coming down in price and up in applications — make no mistake, the micro is here to stay, very soon many electronics enthusiasts will be using one.

"But what will they be using it for?" we hear you ask. Here's a short list of potential applications:

- Programmable calculator
- Electronic games
- TV games
- Microcomputer
- Controlling heating systems
- Controlling measurement systems etc.

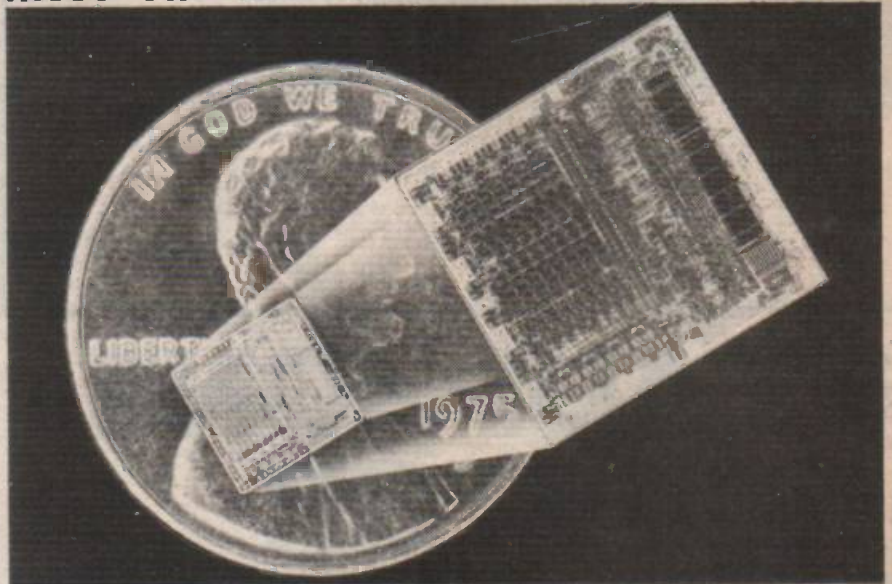Many more applications will suggest themselves with a little thought. A fairly typical system might be built around a micro to control an electric cooker in a sophisticated way so as to permit programming of complete menus with the micro automatically controlling oven settings and timing — the applications are limited only by the imagination.



The main area which we will discuss is the microcomputer, as this is the ideal way to learn about micro-processors, and is a) interesting b) educational and c) useful. It is interesting to look at American activity in this area. Magazines such as *Popular Electronics* carry full page adverts from companies supplying complete computer kits, and programs to run on them. These computers, although small and cheap, are nonetheless very powerful — in fact on many of them it is possible to use BASIC language, which makes programming quick, easy and fun. Obviously, we'll have a lot more to say on the amateur micro-computer later.

### FINE, BUT WHAT IS IT?

We still haven't said what a micro-processor actually is, so here goes. Please bear with us while we explain a bit about computer design. The micro has been described as an 'LSI computer on a chip'. This is a slight misnomer, and may lead you to expect more from a micro than it can reasonably give. It is perhaps more accurate to say that a microprocessor is the arithmetic, logic and control circuits of a computer implemented in LSI form. The definition given by one major microprocessor manufacturer is 'A Microprocessor is a very large scale integrated circuit which by the action of a sequence of instructions, externally programmable, can fulfil a wide variety of different elect-

rical functions'. None of these definitions is particularly revealing, so let's take a closer look at what's actually in a computer and, by analogy, what's in a microprocessor unit (MPU).

The modern stored-program digital computer (Fig. 1) consists of three main units — the central processing unit (CPU), the memory and the input/output interfacing. The sequence of instructions (program) which the computer is to execute is passed through the input interfacing into the memory along with the data to be operated on, and step by step, the machine works through these instructions. Depending on the results of calculations, the machine can jump forward to the next step of the program; otherwise it may go back to the beginning with a new set of numbers.



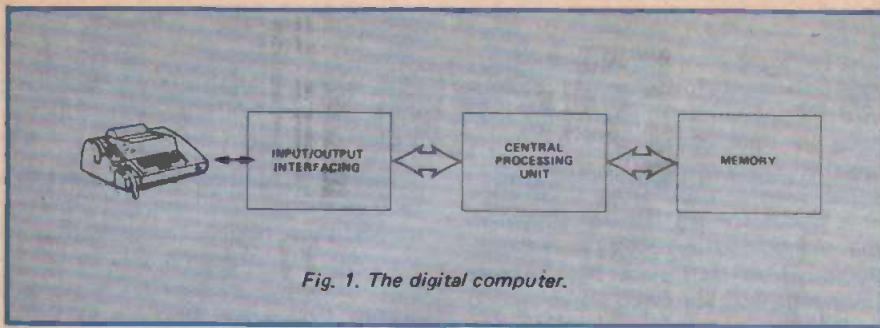


Fig. 1. The digital computer.

The instructions are fed, one by one, into the central processing unit which decodes them and 'decides' what they mean. The instructions are then executed by the arithmetic and logic unit of the CPU and the results may be tested to decide what to do next, or retained for use in the next calculation, or stored away in memory. (End of slight diversion into computers.)

This, believe it or not, is precisely what a microprocessor system does — the microprocessor itself (MPU) corresponds to the CPU, and normally has associated memory containing a program for it to execute. The important point to note here, is that to change the application of an MPU, one does not usually have to change any components, but only the program; this usually costs little or nothing and programming is actually fun — we know our readers will take to it like ducks to water.

#### HOW DOES IT DO THIS?


From this point on, we have to assume

that you, the reader, know a bit about digital logic, which you will, if you've been reading ETI for long. If you're not too sure, please, please find out now — it's definitely the coming thing — and we advertise some good books. We also have had to make a decision to work with one particular MPU, the reason being simply that if everyone works with different types, there will be a lot of duplicated and wasted effort, as really good and interesting programs worked out for one device won't work on a different type. After considerable spadework and deep thought we have opted for the Motorola M6800 family of devices, for a variety of reasons. Please note, however, that a lot of what we say applies to MPU's in general and not just the M6800.

Figure 2 shows a block diagram of a basic M6800 microprocessor system. The most noticeable thing on this diagram is the way all the devices are connected together by three buses — the control bus, the address bus and the data bus. The control bus has several lines carrying clock signals,

read/write, halt, reset and other signals for the control of the system. The address bus has 16 lines in total  $A_0-A_{15}$ , which means that the MPU can access up to  $2^{16}$ , i.e. 65 536 bytes, (8 bit words) of memory directly. This amount of memory is equivalent, roughly, to 13 completely printed pages of ETI with all kinds of special characters, typefaces and colour specified in a none-too-efficient code. So you can see there is sufficient memory potential for most applications.

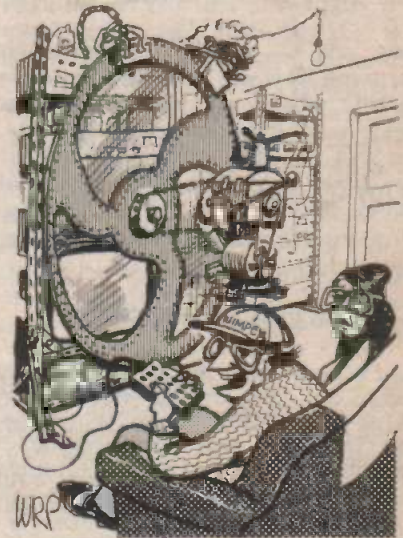The data bus has only 8 lines and will enable the MPU to input or out-



**NOW I'VE GOT ALL THE INTERNAL CONTROL FUNCTIONS PRE-PROGRAMMED I CAN RUN IT UP FROM COLD IN WELL UNDER HALF AN HOUR!**

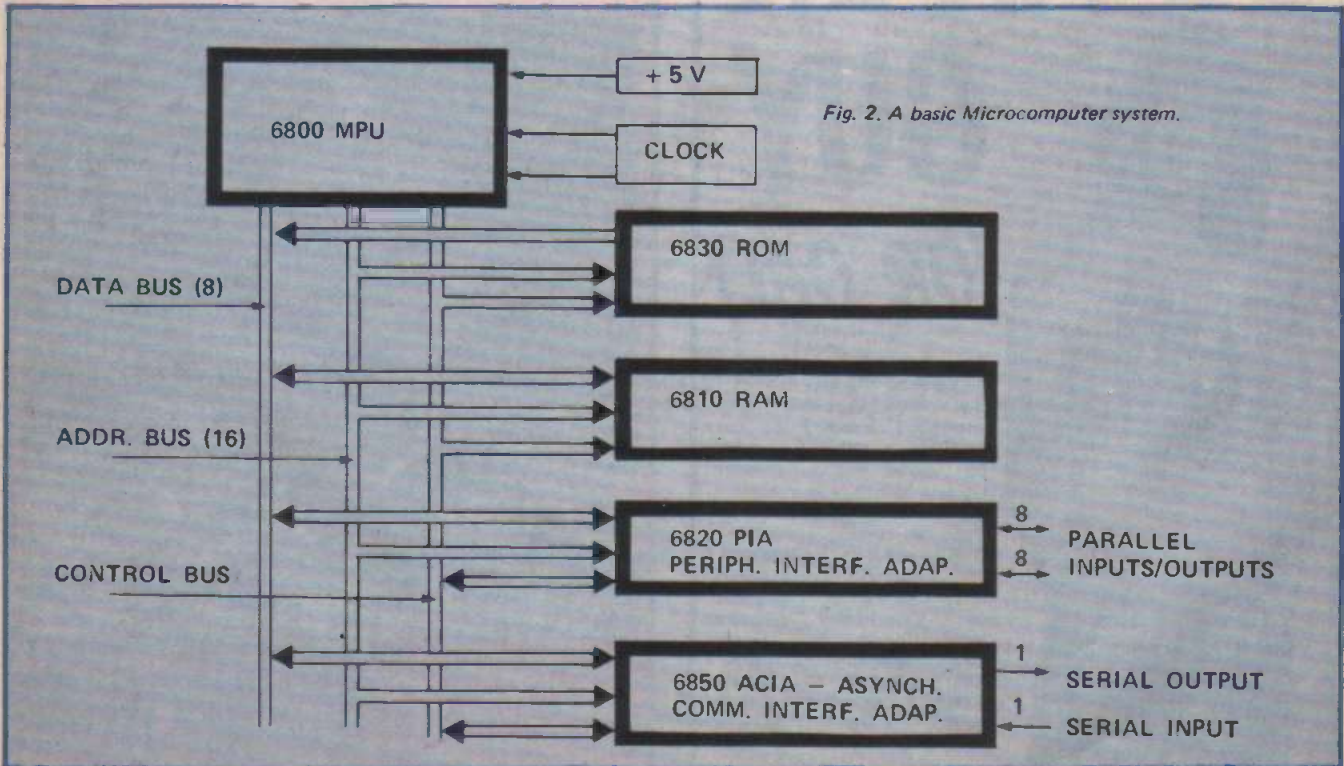


Fig. 2. A basic Microcomputer system.



Motorola's 'MPU in a suitcase.'

put any 1 of 256 different bit patterns. This will be covered in more detail when we discuss number systems. Both buses are bi-directional, so that the MPU can send or receive on either, with the added facility of disconnecting itself for special applications (Direct Memory Access, for those in the know).

### THANKS FOR THE MEMORY

Let's now look at the two blocks below the MPU — the ones labelled ROM and RAM. We'll start with RAM, or Random Access Memory. This is the memory that holds both the program and the data it will

operate upon, and the MPU can recall and store data in this memory as it works through a program. It functions in a manner similar to a rack of pigeon holes — upon selecting a particular pigeon-hole or *address*, the MPU can either read a word from it or stick in a word. The 6810 RAM shown in the diagram is a 128 byte semiconductor RAM chip made by Motorola to operate with the 6800 MPU.

RAM chips have one disadvantage — when the power is turned off, the contents are lost. This means that any programs which have to be permanently resident in the computer have to be in a different form of memory — this is usually Read Only Memory. This is programmed either during manufacture or before insertion into the circuit and cannot normally then be altered by the micro, which can only read information from it. Again, the 6830 is a Motorola part designed for the 6800 — many other parts are suitable, however.

### INPUT, OUTPUT

Referring back to Fig. 2, the two blocks at the bottom constitute the bulk of the input/output (I/O) interfacing mentioned earlier. The 6820 Peripheral Interface Adaptor has two eight-bit parallel buses each line of which can function as an input or

an output, while the 6850 Asynchronous Communications Interface Adapter is a serial I/O device. Both these devices will be dealt with in greater detail later.

With the addition of a few devices such as a clock oscillator and a power supply, these devices can be made into a complete microcomputer. However you also need some kind of input/output device e.g. teletype or video display unit and also a monitor and debug program which will enable you to load programs into memory, run them and alter them. We'll have more to say on this when we discuss programming. The final (optional) piece of hardware is a low speed modem which converts digital signals into audio tones so that programs can be saved on a cassette tape via a cheap tape recorder. This means that programs do not have to be typed in each time the computer is switched on, and is probably the computer experimenter's best value-for-money labour saving device.

Well, that rounds off this general, and very simple, introduction to microprocessors. If you're already using one, and have any interesting thoughts, we'd like to hear from you. If you're just thinking about it — watch for the Microfile heading — that's where you'll find the facts. ●

# BE AN ETI GUY (OR GAL)



A couple of issues ago we announced the ETI T-Shirt—the response has been enormous. Initially we just wanted to sell the surplus but we've had to reorder twice! Made in cotton (yellow with black printing) these are available in three sizes suitable for both sexes.

Send your cheque and P.O. for £1.50 (payable to Electronics Today International) and state Small, Medium or Large. ETI T-SHIRTS, 36 EBUWY STREET, LONDON SW1W 0LW.

*Now there's a better way to keep your ETI copies*



We reckon ETI is worth keeping: and our surveys indicate that a staggering 97% of readers keep their copies for at least three months. Now we can offer you a binder which holds 12 issues whose quality befits the magazine: excellent. Send £2.00 (which includes VAT and postage) to:

**ETI BINDERS, 36 EBUWY STREET, LONDON SW1W 0LW.**



# SILENT A-B SWITCH

Speakers may be A-B tested using this simple modification to our tone-burst generator

WHEN evaluating speaker systems in A-B listening tests, the first few seconds of listening convey the truest impression of sound quality. Listening for longer than a few seconds not only fails to give further information, but may well give a false indication. For this reason it is usual to switch rapidly between the reference speaker and the speaker under test. This is generally done by using the amplifier's A/B

## HOW IT WORKS – ETI 124 AB

As this unit is based on the operation of the tone-burst generator ETI 124 described last month, that article should be thoroughly read first. Only the changes necessary to that unit are detailed in this article.

Whilst an A-B switch would be a little simpler if designed specifically for that purpose, the modifications required to the tone-burst generator are so simple that we thought it not worth while to design a special circuit.

To make the generator act as an A-B switch it is necessary to disable the existing mode switch. We do this by plugging in an external control switch, SW6, via a stereo phone socket. The phone socket has two change-over contacts fitted which are used to disconnect the plus and minus six volts supplies from SW3 when the jack is inserted. One of the phono contacts also disconnects the plus six volts from the common of the socket when the jack is removed. As the common of the socket is required to be at plus six volts the phono socket must be insulated from the front panel which is at 0 volts.

The control switch, SW6, effectively shorts either R4 or R5 thus stopping the pulses from C2 or C3 triggering the flip-flop. When the switch is actuated there is a delay until the number of cycles as set by the front panel switch have occurred and then, at the next zero crossing, the change-over occurs. The delay is necessary to ensure that any contact bounce of the SW6 contacts does not cause unwanted switching of the circuit.

speaker selector switch, or by wiring a change-over relay in the speaker wiring.

Whilst such switching methods are simple and reliable they have one major drawback. That is that switching may take place at any point in the waveform and as a consequence switching transients may be introduced which tend to mask the subtle differences for which one is listening. Hence a method of switching at zero-crossing points would be of great value.

When the ETI Tone-Burst Generator was constructed it was realised that it contained all the circuitry needed to performance this switching task and that it could be modified to do so very simply.

The switching must be done at low level and hence the unit is used at the input of a stereo power amplifier. The reference speaker and the speaker under test are each connected to one channel of the amplifier and the silent switch switches the input to the amplifiers as required. Thus the arrangement is mono only but this is all that is required to assess the transient response and performance of a speaker in comparison to a reference speaker.

## CONSTRUCTION

The ETI 124 Tone-burst Generator should first be constructed, as detailed last month, except that the wiring to SW3 is changed as detailed in Fig. 1 and 2 of this article. The dual phono socket and the phone socket are then mounted on one side of the box. If a metal box is used make sure that the phono socket is insulated from the case of the box as it is at a potential of six volts. The switch, SW6, should be mounted in a small pill container or similar housing and fitted with a three-core cable that is terminated at the other end by a stereo phone jack. Note that the common of the switch should be connected to the common of the jack but that the other wires may be wired to either of the remaining contacts.

## USING THE SWITCH.

The audio switch requires a reasonably high level of signal to ensure correct zero-crossing switching. There are two suitable points in a conventional amplifier. The first position is between the tape-in and tape-out sockets but the second and preferable position is between the pre and main amplifiers provided that the main amplifier has a volume control that is independent of the preamplifier.

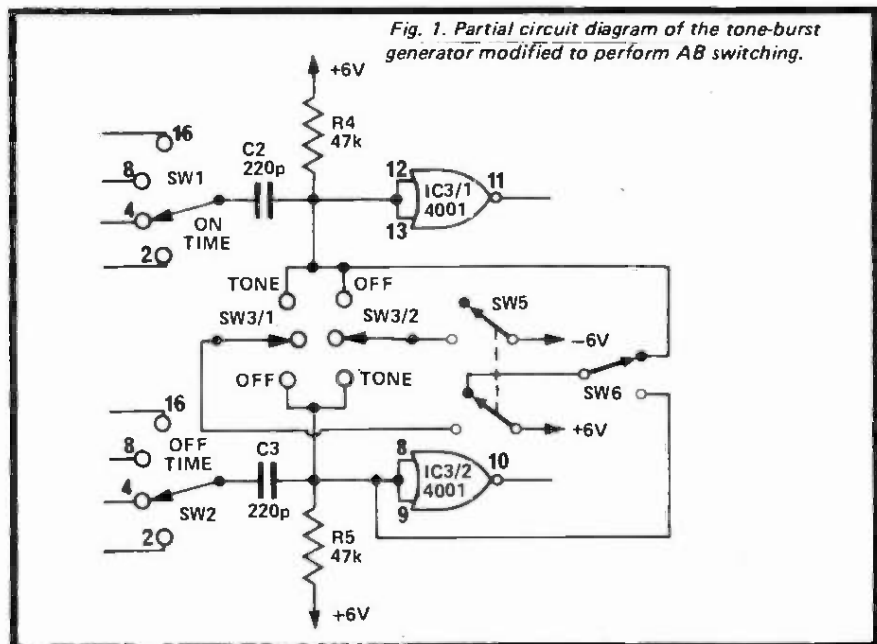


Fig. 1. Partial circuit diagram of the tone-burst generator modified to perform AB switching.

**eti project**


**124 AB**

## SILENT A-B SWITCH

To connect the unit for AB testing apply a single input, from the preamplifier (switched to mono), to the normal input socket of the generator. The normal output socket of the generator is not used but the two phono output sockets are connected back to the left and right channel inputs of the main amplifier. When SW6 is operated the mono input will be silently switched between right and left channel speakers.

If using the tape sockets the monitor switch should be in the 'monitor' position and the balance control should be adjusted so that the levels from the two speakers are apparently the same. Make sure that the tone controls are in the flat position, as they can cause phase shifts which prevent the switching occurring at the zero-crossing point.

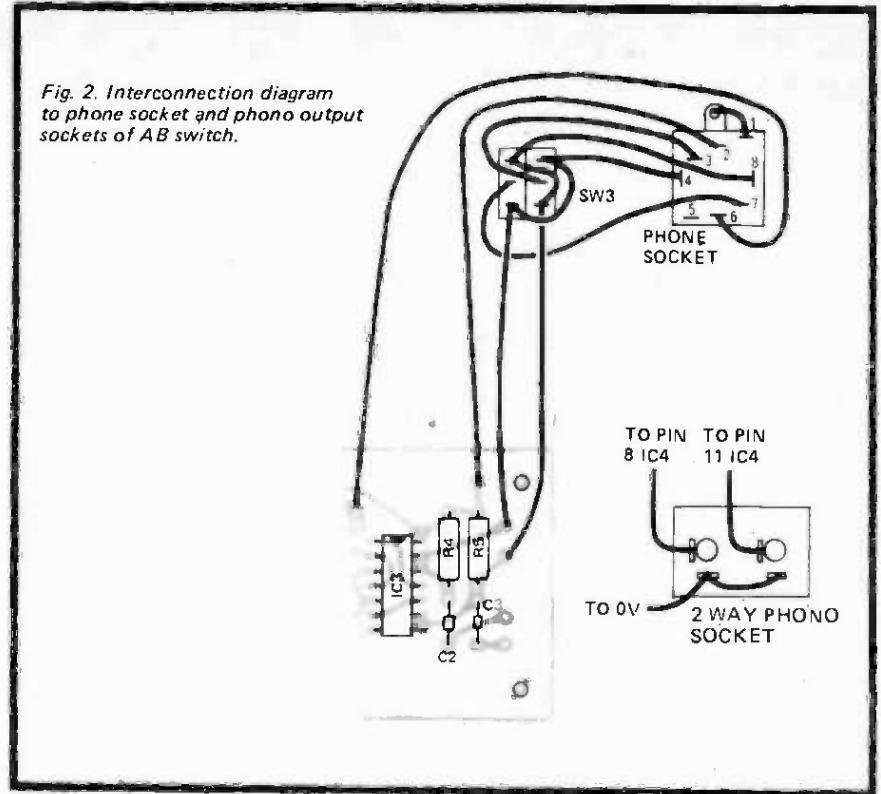If the pre and main amplifier terminals are used the preamplifier volume should be adjusted to about half way and separate volume controls used to balance for the difference in efficiencies of the two speakers. If the main amplifier does not have separate volume controls then external ones must be added if balance is to be achieved. In this case the tone controls may be used if required



without upsetting the crossover point. Change over may be effected by using either a toggle switch or a push button. The tone-burst generator

controls should be set for eight cycles on and off as this position will effectively remove any contact bounce.

## ANOTHER SPECIAL OFFER

1,000 copies of this brand new book are now in our warehouse and available at a special low price, to readers of Electronics Today International

**Paperback**  
(Published Price £3.35) **£2.65** (save 70p)

**Hardcover**  
(Published Price £7.95) **£6.50** (save £1.45)  
Both prices include postage and packing.


A Companion to *Linear Integrated Circuit Applications* which we previously offered you, this book covers a wide range of practical operational amplifier applications. It gives circuits which include component values, and suggests measurements that can be made in order to study circuit action.

### FROM THE AUTHOR

... the quickest way to learn about operational amplifiers is actually to use them in working circuits. It does not matter very much if a wrong connection is made in the experimental circuits, the operational amplifier type suggested for use in this book will tolerate quite a few mistakes and even if you destroy it it should not break you. If resistor values suggested in the circuits are not at hand try other values, electronic systems will work (in a fashion) with a considerable range of component values.
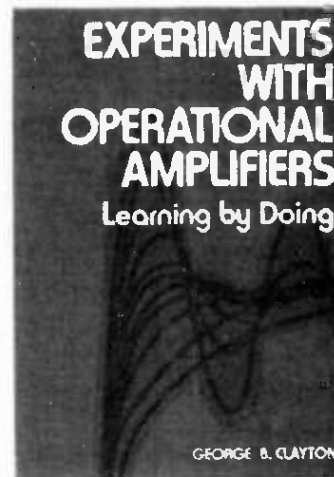
### CONTENTS

- 1 Basic Operational Amplifier Ideas
  - 2 Basic Operational Amplifier Applications
  - 3 Operational Amplifier Circuits with a Non-linear Response
  - 4 Some Signal Processing and Measurement Applications
  - 5 Operational Amplifiers used in Switching and Timing Applications
  - 6 Operational Amplifiers used for Signal Generation
- Appendix: Operational Amplifier Performance Errors



Please send me within 21 days.....copy/copies of  
**EXPERIMENTS WITH OPERATIONAL AMPLIFIERS**  
..... paperback  
..... hardback (please tick required edition)  
I enclose Postal Order/Cheque for £.....

Name .....

Address .....

(Block Letters Please)

ETI Book Services, 25 Court Close, Bray,  
Maidenhead, Berkshire, SL6 2DL.

# CMOS

## THE 4016A

THE NEXT DEVICE we are going to look at has already made a considerable impact on amateur electronics. The 4016A quad bilateral switch consists of four transmission gates of the type discussed in the last part, each with its own control input. Each switch also has a signal input and output (although these are interchangeable). When the control input is held high the input to output path behaves like a pure resistance of about  $300\Omega$  but when it is low the equivalent value is of the order of  $10^9\Omega$  at low frequency, even with fairly low supply voltages. It is impossible to give all the data which might be necessary for diverse applications here and data sheets from a manufacturer may be required by the more adventurous experimenters. In any case the pinout diagram in fig. 1 should now be self explanatory.

It should be appreciated that the output impedance of the switch is fairly high and so for low signal distortion, a load greater than  $10k\Omega$  is necessary. Using a high supply voltage (10-15V) also helps to achieve this end. The gates will pass signals above the 10MHz mark but as the frequency becomes higher, crosstalk between the switches and distortion will inevitably increase. It should be fairly clear how complicated switching systems may be realised but fig. 2 has been included to guide constructors along the right lines.

## ANALOGUE APPLICATIONS

Many uses of this device in audio equipment have already appeared in constructional articles in this magazine and so it is to two slightly less obvious applications that we shall turn now. Fig. 3 shows a sample and hold unit; when the control input is high the output tracks the input but when it goes low the output remains frozen at the value it was at the instant of transition. The operation of the circuit is generally self evident and it

may be regarded as two voltage followers, one consisting of two op-amps with the output following the input, the other is just the second op-amp which "follows" the voltage stored on the capacitor. It is advisable to take care with the layout as with all op-amp circuits due to the huge open loop gain of these devices. The value chosen for C is a compromise between "slewing rate," that is the rate at which the circuit tracks a sudden change of input and "holding ability"


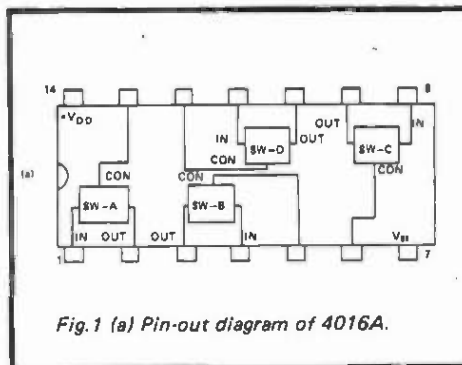


Fig. 1 (a) Pin-out diagram of 4016A.
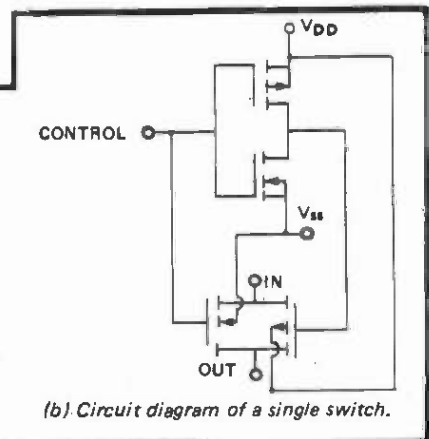
## DIGITAL COMPONENT SELECTION

There are a few fairly straight-forward uses of the 4016A in digital component selection which we will mention here because, in certain fields, they are very useful. Fig. 6 shows how to produce digitally controlled resistance and capacitance networks which will vary the magnitude of the quantity in ques-



(b) Circuit diagram of a single switch.

which is the length of time the circuit will hold a signal without unreasonable decay. To give some sort of guide, for a 10kHz square wave to the control input, a  $0.01\mu\text{F}$  capacitor seems to optimise the performance. The value of the resistors is also worth experimenting with.

An extension of the sample and hold concept is the analogue delay line which is shown in its basic form in fig. 4. The sequence of amplifiers and gates can be extended to any desired length to achieve a longer delay, the only limitation being that in extreme cases the control lines may need to be buffered. It should be observed that alternate stages of the circuit are driven by an identical clock waveform and so the circuit works by shifting the voltage on alternate capacitors during alternate clock phases. The value of the passive components and the clock frequency will have to be optimised for specific applications, low frequencies give long delays but high distortion.

tion from its basic value up to  $2^n - 1$  times that amount, where "n" is the number of gates and binary control bits. The resistor network can be used to produce a digitally gain controlled amplifier by placing it in the feedback loop of an op-amp and this can be used as a staircase generator as well as to produce more interesting waveforms. One application of the digital capacitor is to produce a digitally controlled sweep generator by using it as the capacitor in one of the multivibrators we discussed in the last part.

Clearly, any type of component may be switched in and out of circuit by the 4016A. One possibility that is useful in some circumstances is to use the information on filter design in "Electronics — it's easy" to produce digital filters of different descriptions. The main thing to remember when using all these ideas is that the impedance of the component that is being switched must, at the desired frequency of operation, be large compared to the  $300\Omega$  of the 4016A gates.

## D-A AND A-D TECHNIQUES

The next use of the quad bilateral switch we are going to consider is in the field of digital to analogue conversion but first we are going to look at the subject of conversion on its own. Fig. 6 shows a D-A converter of the type known as a weighted resistor network. The working of this circuit is easy to see and the reason it is practical in so simple a form in CMOS is that the high and low output levels from a simple gate are within a few millivolts of the supply line thus providing accurate voltage levels to the summing resistors. This simple form has disadvantages, one of which will become immediately apparent if you consider the diversity of resistor values required for an eight or nine bit version. It is for this reason that the R - 2R network shown in fig. 7 is more popular for most applications. It is difficult to explain how this configuration works without becoming involved in mathematics but it becomes fairly clear if a three bit version is written down with the voltages in and analysed.

The basic idea for one sort of A-D converter or encoder as they are often called is shown in the block

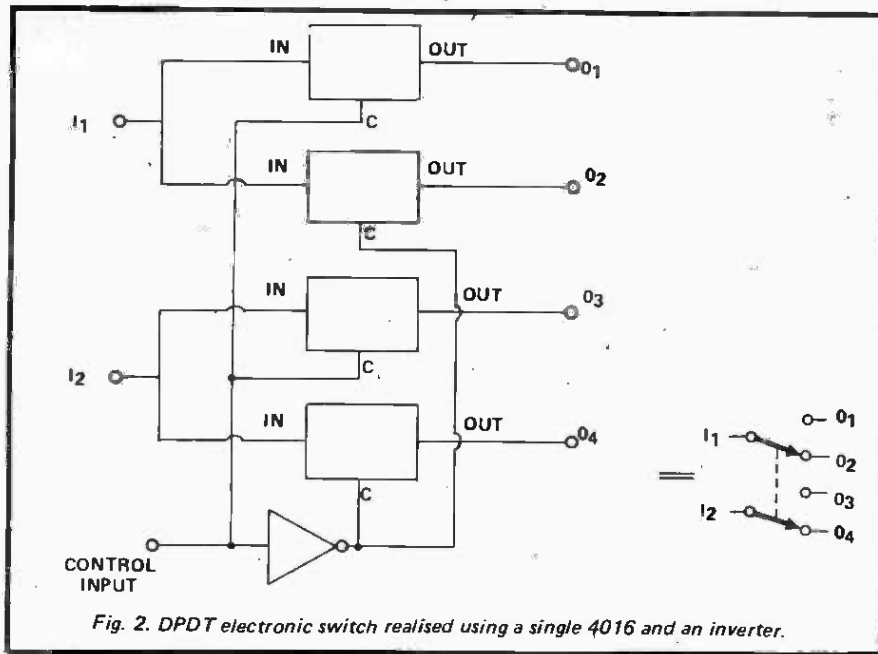


Fig. 2. DPDT electronic switch realised using a single 4016 and an inverter.

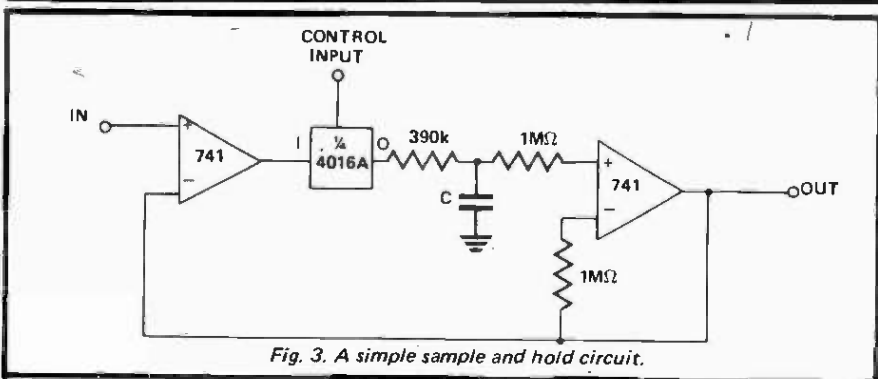


Fig. 3. A simple sample and hold circuit.

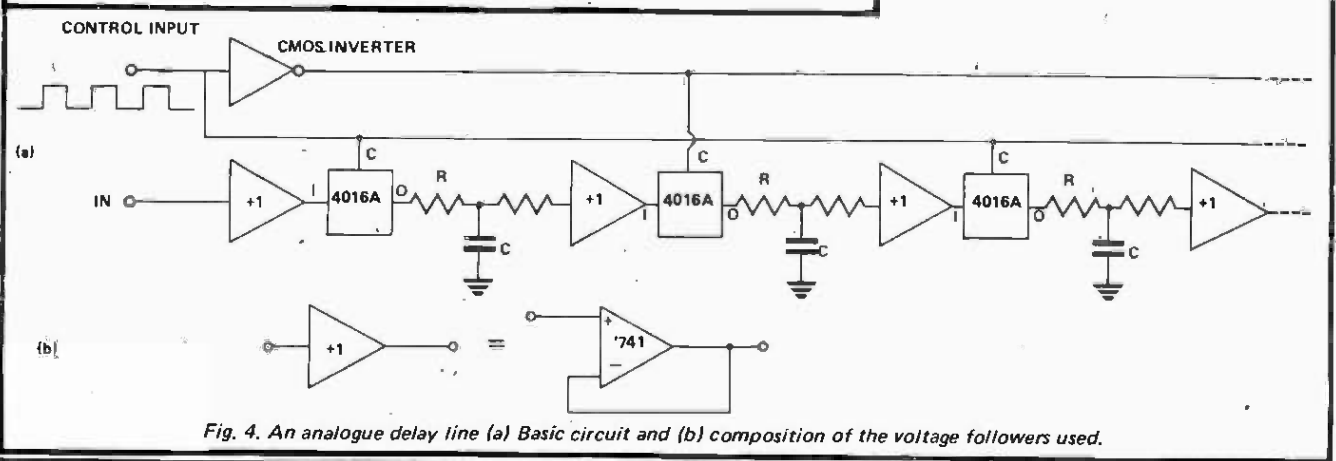


Fig. 4. An analogue delay line (a) Basic circuit and (b) composition of the voltage followers used.

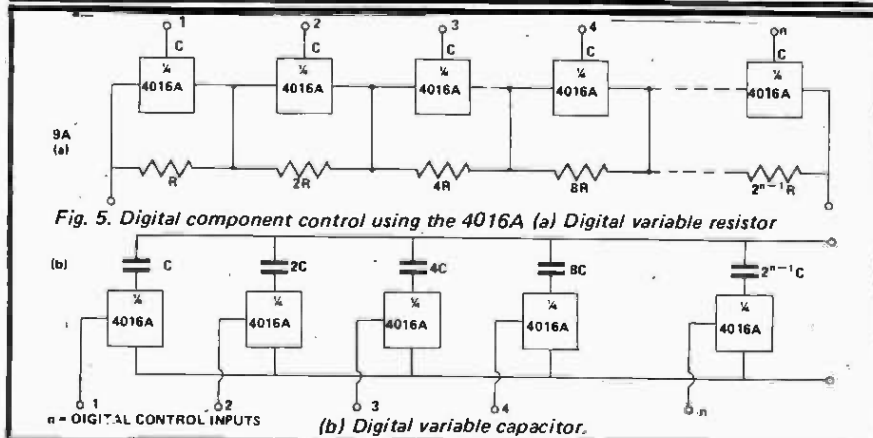


Fig. 5. Digital component control using the 4016A (a) Digital variable resistor

(b) Digital variable capacitor.

diagram of fig. 8. This variety is called a binary ramp encoder and is similar to the ramp integration method often encountered in modified form in digital measuring equipment. The principle of operation of our binary version is that a binary counter counts up from zero until it reaches the equivalent of the analogue input. Contrast this approach with the continuous counter method outlined in fig. 9. This provides a continuous approximation to the input and is thus generally more useful for continuously monitoring a single channel



# DYNAMIC NOISE FILTER

## PART TWO

by M.G. Strange

THE FILTER output is coupled to the detector via a small capacitor to make the low-frequency rolloff even steeper below 1.6 kHz. The precision full-wave detector uses diodes in the feedback circuit of an op-amp to effectively produce ideal rectification characteristics down to the millivolt region. The output amplifier doubles as a post-detection filter. Resistor R determines the gain, and capacitor C makes this stage behave as an operational integrator with time constant RC. A switch is provided for increasing the time constant by paralleling capacitor C1; this is helpful with sources having sharp impulse noise. The output of the detector/filter circuit controls the bandwidth of the dynamic suppression filter according to the curve of Fig. 9.

Early experiments showed that it is undesirable to make the no-signal cutoff lower than absolutely necessary to substantially reduce noise with a particular signal source. When the cutoff is made lower than actually needed, weak signals are unnecessarily band-limited and the dynamic filter produces such a level-dependent bandwidth contrast that its action is much more likely to be audible. Hence a BASE CUTOFF (not "BASS CUTOFF") control was found to be desirable. This control is simply a pot which offsets the detector output at zero signal level by applying a variable reference voltage to the op amp

non-inverting inputs. This voltage, variable from about -1 volt to -6 volts, establishes a "starting point" or base cutoff frequency which can be set just low enough to virtually eliminate no-signal noise.

### VARIABLE-CUTOFF FILTER

The variable-cutoff filter, Fig. 8, is the very heart of the system. Since there is some part selection and adjustment necessary, it must be checked out separately. The basic configuration is similar to that of the pre-filter, except the latter's switch-selected resistors have been replaced by field-effect transistors (FETs). FET channel resistance  $R_{DS}$  changes as a function of gate voltage  $V_{GS}$  as shown in Fig. 11, thus varying cutoff frequency. A resistor across each FET establishes a solid lower cutoff limit and smooths the control characteristic as the FETs approach their "off" state. The gate circuit network, consisting of diode D1 and resistors R1 through R5, is used to empirically shape the control curve (Fig. 9) for best audible results. Diode D1 prevents excessive positive gate drive, maintaining isolation between the gate and signal circuits.

An input attenuator (R10 and R11) limits the signal amplitude presented to the FETs to about 0.1 volt p-p at 0 VU to ensure low distortion. Output amplifier A7 makes up exactly for this

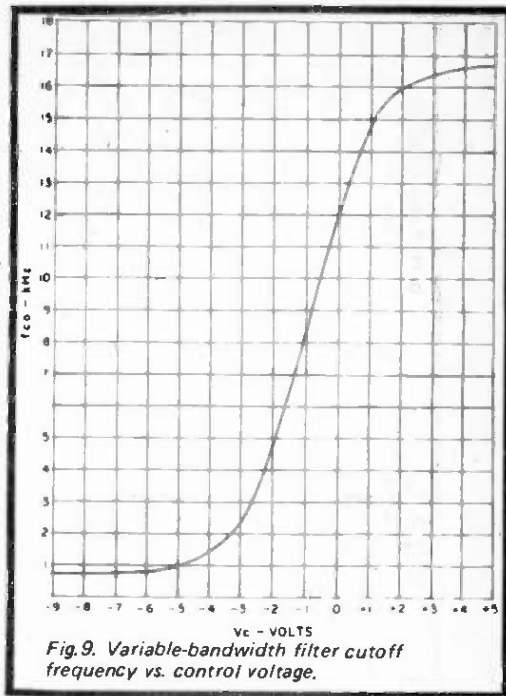


Fig. 9. Variable-bandwidth filter cutoff frequency vs. control voltage.

loss. An op amp having external frequency compensation was used here so that this relatively high-gain stage could be tailored for flat response to 15 kHz (a  $\mu$ a741 could be used, but would roll off slightly above 10 kHz). Resistors R16 and R17 attenuate the output signal by an amount equal to the gain, so that this amplifier doubles as the unity-gain buffer required for filter operation. The highest cutoff frequency is dictated by minimum FET resistance and capacitors C1 and C2. The latter should have values in a ratio of about 3:1 to produce the desired Butterworth response. Figure 10 shows the measured response of the complete filter for four values of control voltage.

Unfortunately, FETs vary widely in characteristics, even between units of the same type, so these devices must be selected. The two FETs must be reasonably well matched over at 15:1  $R_{DS}$  range for a 15:1 range in cutoff frequency (15 kHz to 1 kHz). (Dual matched FETs are available, but are more expensive and not necessarily matched for the parameter of interest here.) A transistor curve tracer is most convenient for this purpose and permits selection for best linearity as well as matching. I used N-channel 2N4220s on hand (60p each) and selected the best matched pair out of a group of six units. Figure 11 shows the  $V_I$  characteristics of one of these. There are many other inexpensive FETs which should work as well, such as the 2N5484, 2N5716, and 2N5717. In fact, any general-purpose, depletion-type FET with fairly low zero-bias current ( $I_{DSS}$ ) and pinch-off voltage ( $V_p$ ) should be usable. P-channel units would require reversing diodes D1 and D2 and the polarity of the control voltage.

If a curve tracer is not available, the

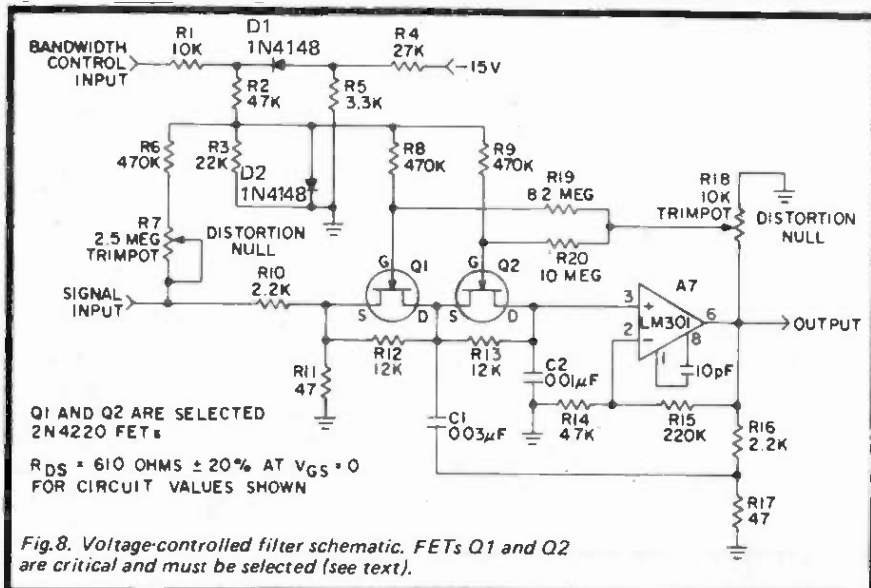


Fig. 8. Voltage-controlled filter schematic. FETs Q1 and Q2 are critical and must be selected (see text).

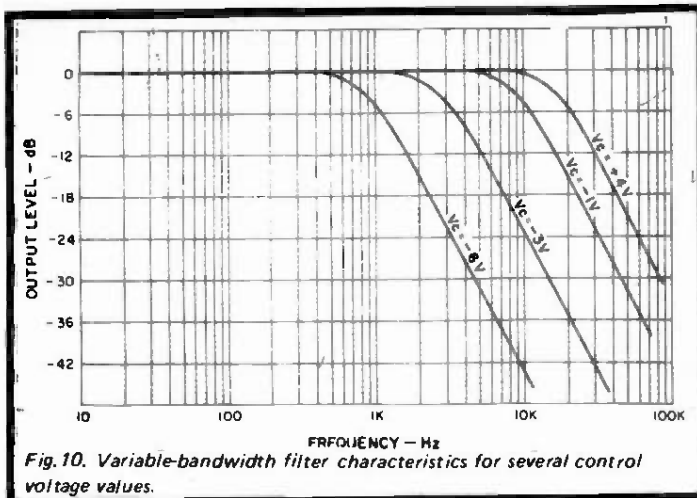


Fig. 10. Variable-bandwidth filter characteristics for several control voltage values.

setup of Fig. 12 can be used. A transistor socket will facilitate changing FETs. A good procedure is to first measure  $R_{DS}$  at  $V_{GS} = 0$ . Then increase  $V_{GS}$  (negatively for N-channel FETs) until  $R_{DS}$  is about three times the zero-bias value; this corresponds to a mid-range cutoff frequency where matching is the most critical. With this  $V_{GS}$  setting try different FETs until a 10 percent or better match is found. If  $R_{DS}$  values seem to cluster higher or lower, try another unit as a reference and try matching to it. When matched units are found, check the match at minimum  $R_{DS}$  ( $V_{GS} = +0.5V$ ) and at 10 times this value of  $R_{DS}$ . A 20 percent mismatch can be tolerated at these extremes. My 2N4220s measure 610 ohms at zero bias, 360 ohms at  $V_{GS} = +0.5V$ , and about 8 kilohms at  $V_{GS} = -0.7V$ . R11 and R12 are chosen for a cutoff of between 800 Hz and 1 kHz with the control voltage at its maximum negative value of about -6 volts. Circuit cutoff at zero FET bias should be roughly 12 kHz (see Fig. 9). A slight forward bias, limited to about +0.5 volt at the FET gates by diode D2, then boosts the cutoff to at least 15 kHz with maximum positive output from the precision detector.

Resistors R6, R7, R18, R19, and R20 reduce harmonic distortion significantly. R6 and R7 feed some

signal to the FET gate circuit so that signal voltage does not appear between source and gate, which would make  $R_{DS}$  vary slightly with instantaneous low-frequency signal amplitude and polarity. R18, R19, and R20 feed back some output signal to the gates to further reduce distortion (this is a cancellation effect, not true negative feedback).

Distortion settings are best made in the vicinity of cutoff, where FET linearity is the most critical. Connect a variable-voltage d.c. source (the slider of a 5 k pot temporarily connected between -15 V and ground will suffice) to the bandwidth control input and set it for a cutoff frequency of 2 kHz. Then, with a 2 kHz sinusoidal input at about 0 VU (2.2 V p-p), set trimpots R7 and R18 for lowest harmonic distortion at the output. It should be possible to sharply null the total harmonic content, which consists primarily of the 2nd and 3rd harmonics, to at least 60 dB below 0 VU. Then vary the cutoff frequency and make sure distortion is low for all settings. Of course, the filter itself will reduce harmonic distortion appreciably at its lower cutoff values. Lacking a distortion meter or wave analyzer, these adjustments can be made quite well by driving the input at 7 volts p-p (10 dB above 0 VU) to accentuate the

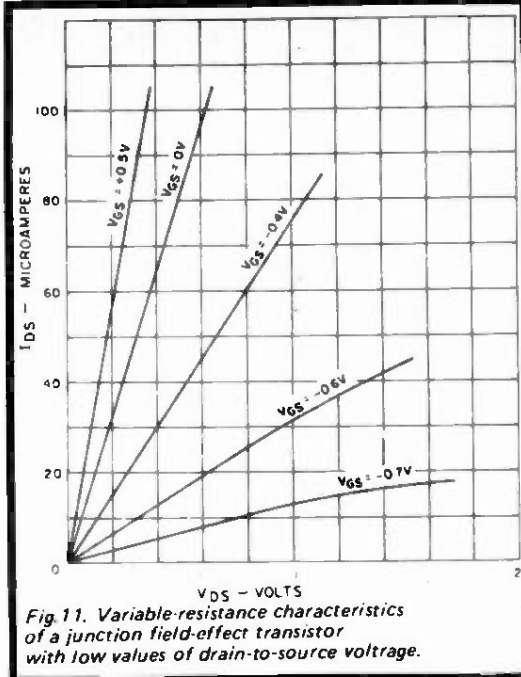


Fig. 11. Variable-resistance characteristics of a junction field-effect transistor with low values of drain-to-source voltage.

distortion and setting very carefully for a symmetrical output waveform as monitored by a 'scope. Fixed resistors, determined by two decade boxes (the settings interact somewhat), could replace the pots. These adjustments, once made, are permanent unless the FETs are changed.

Figure 13 shows the distortion of the complete noise filter measured at two fixed values of bandwidth control voltage. At normal levels, distortion is so low that it is largely a measurement of the harmonic distortion of the test oscillator. The large margin above 0 VU passes the highest programme peaks ever likely to be encountered without clipping.

The simple power supply of Fig. 14 easily supplies the power requirement of  $\pm 15$  volts at about 10 mA.

## CONSTRUCTION

The entire filter can be duplicated for about £40 with new parts. Very few components are critical and substitutes can be used in most cases. Quarter-watt, 5 percent composition resistors are suitable. Layout is not critical, since signal levels are high and impedances are relatively low. I strongly recommend that each of the functional blocks of Fig. 2 be built and checked for reasonable conformance with the curves before integration into the system. This makes troubleshooting for errors and occasional bad components much easier, practically ensuring success. My unit (Fig. 1 and lead photo) is a "breadboard in a box." The circuit is still undergoing occasional changes, even though it is a third-generation model. Parts are mounted on terminal boards which were on hand. A neater approach would be to use the

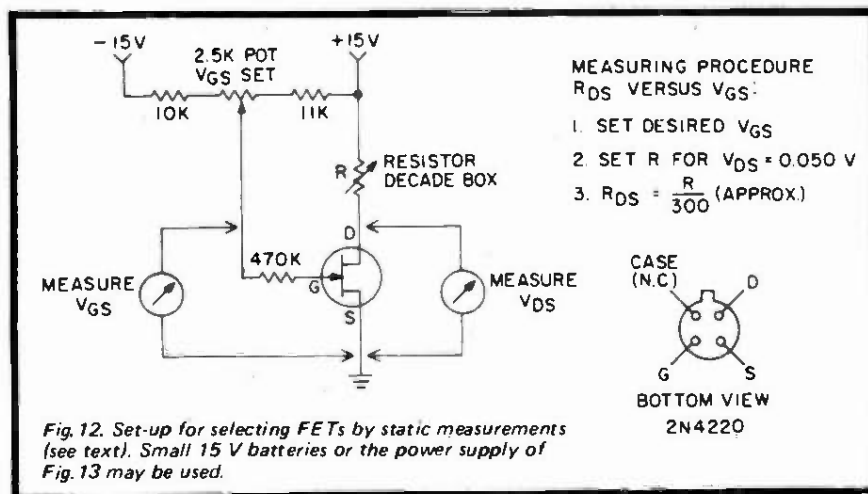


Fig. 12. Set-up for selecting FETs by static measurements (see text). Small 15 V batteries or the power supply of Fig. 13 may be used.

# DYNAMIC NOISE FILTER

commercially-available matrix-board with snap-in terminals.

## OPERATION

After checking the wiring, apply power to the unit and check for proper power supply voltages. Positive and negative supplies should both be between 14 and 16 volts with respect to ground. Much lower values would indicate a short circuit or bad op amp. Current drain should be on the order of 10 mA.

The noise filter can be conveniently connected to your audio system by means of the *Tape In* and *Tape Out* jacks included on most preamplifiers. An advantage to this connection is that the processed signal passes through the pre-amp tone controls, which can be set for the most pleasing final balance. For taping, the recorder input is paralleled with the output which drives the power amplifier.

For initial set-up experience, a record having a good frequency range and moderate, steady surface hiss is desirable. (A slightly noisy FM station can also be used, but results will not be quite as good because of the latter's flatter noise spectrum.) Initial control settings should be:

- Pre-Filter: Off
- Rumble Filter: Off
- Time Const.: Off
- Peak Rej. Freq.: 5 kHz
- Base Cutoff: CCW
- Suppr. Gain: CCW
- Dyn. Suppr.: Off
- Sig. Compare: Input

The signal should now pass through the unit unaffected, except the *Level Set* control will vary the gain from zero to 3.2 (10 dB). Set the level for 0 VU on signal peaks as you would set a recording level. Whenever the source is changed, the signal level should be reset as necessary.

Now switch the *Sig. Compare* switch to "output". The signal is now passing through the rumble filter (if used) and pre-filter, but bypassing the dynamic filter. Lowering the *Pre-Filter* cutoff setting should progressively cut off the highs. At the lower settings, which are primarily for acoustic records, the signal will sound severely band-limited. The best setting is the lowest cutoff which does not significantly affect the recorded bandwidth. I have found that with vocal music, the unfiltered sibilant sounds provide a means of judging bandwidth. If sibilants are quite strong and natural, a 7 kHz or higher cutoff is indicated. If they are

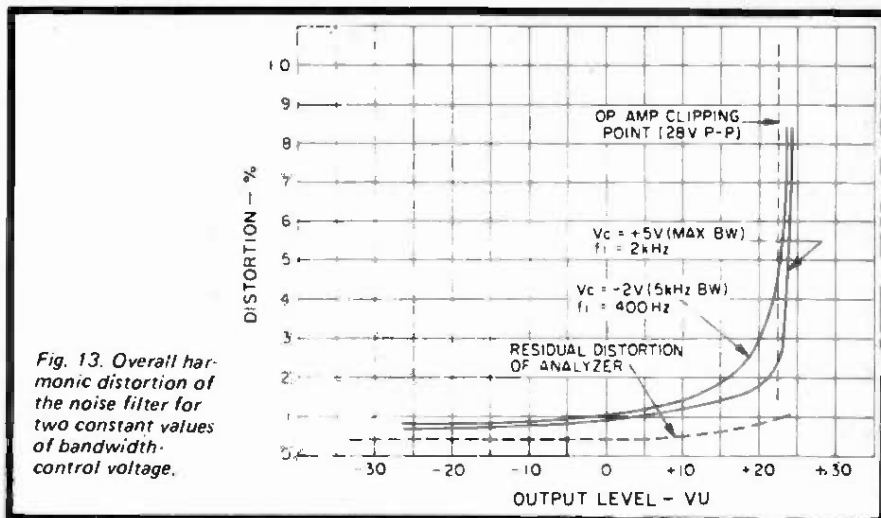


Fig. 13. Overall harmonic distortion of the noise filter for two constant values of bandwidth-control voltage.

weak or have a slight "whistling" sound, the upper limit is about 5 kHz. If sibilants are lacking, a 4 kHz or lower setting is best. Of course, the presence of high-frequency distortion may dictate a compromise setting a notch or two lower than indicated above. The filtered and unfiltered sounds may be compared at any time by means of the *Sig. Compare* switch.

The optional rumble filter is used for the occasional records which have warpage or bumps or low-frequency noise in the recording. For *acoustic* records it can be routinely left at 150 Hz, as nothing is recorded below about 200 Hz.

Next flip the *Dyn Suppr* switch to "on", putting the dynamic suppressor in the circuit. The sound should become very dull and lifeless; as the high-frequency cutoff is now 1 kHz or less. Increase the *Base Cutoff* setting until record noise just begins to be audible. The signal will probably still be quite lacking in high-frequency content (if it is not, only the pre-filter may be needed for this particular source). Now turn up the *Suppr Gain* slowly. This should "magically" restore the highs without increasing the noise level. The highest possible setting which does not noticeably

increase the noise is normally best.

At this point it is edifying to monitor the bandwidth control input signal to the variable-bandwidth filter with a d.c.-coupled oscilloscope. The instantaneous voltage here is a measure of high-frequency programme amplitude and dynamic filter bandwidth (see Fig. 9). It should follow transients rapidly and may reach saturation (about +14 volts) on musical passages having high harmonic content and on strong voice sibilants.

The *Peak Rej. Freq.* switch selects the frequency of peak rejection by choosing the appropriate filter curve (Fig. 7) for separating the bandwidth-control voltage from the input signal. The 5 kHz position is used for most electrical 78 rpm records. For acoustic records or very noisy electrical 78s where the pre-filter is set for 4 kHz or less, the 3.5 kHz position gives better results. Here the *Time Const.* switch can be set for 15 mS. The longer time constant also helps to attenuate sharp clicks and pops occurring in quiet passages, as it prevents the bandwidth from increasing rapidly enough to follow their steep wavefronts. The 7.5 kHz position is used for wideband recordings and tape.

With a little practice, you will be able

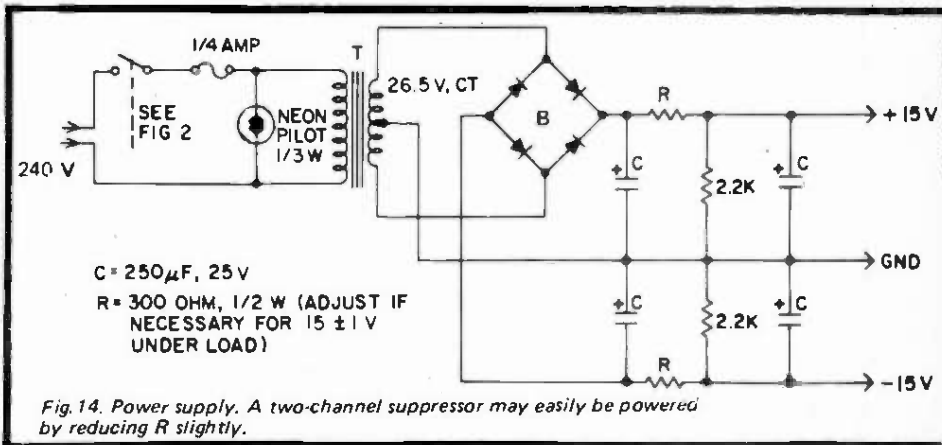


Fig. 14. Power supply. A two-channel suppressor may easily be powered by reducing R slightly.



to set the controls quickly for optimum performance. It is often best to set the *Base Cutoff* for a significant improvement, rather than to try to eliminate the noise completely. This will minimize low-level band limiting, and the suppressor will be less likely to betray its presence with obvious bandwidth changes.

## PERFORMANCE

Figures 5 and 10 indicate the bandwidth ranges available. The pre-filter and dynamic filter (slope is 24 dB/octave above both cutoffs) can together provide well over 60 dB of noise attenuation at 10 kHz and over 40 dB at 5 kHz. The overall improvement in signal-to-noise ratio is strongly determined by the character and spectrum of the noise, which varies greatly with records. With the steady hiss typical of new electrical recordings on shellac, an average improvement of 8 dB (unweighted) is realized from the dynamic filter alone. Including the effects of the rumble filter and pre-filter on band-limited material, S/N improvement can be more than 12 dB. The apparent improvement is even greater, since the ear heavily weights the higher frequencies where record noise is concentrated.

The effect of the noise filter is surprisingly great on records which were originally thought to be quiet without filtering. It is a little weird at first to hear a familiar old record with realistic strings and brass and clear voice sibilants, but with the background suddenly rendered deadly quiet. I have spent many hours listening to the records and tapes in my collection and enjoying them anew.

The noise filter works very well on tape noise, providing at least 8 dB total S/N improvement. A stereo version built for tape only could be simplified considerably, as only the *Level Set*, *Base Cutoff*, *Suppr. Gain*, and *Sig. Compare* controls would be needed. The power supply as shown can easily handle two channels.

The noise level of the filter itself depends mostly on output amplifier A7. Of several units I tried, the noise level ranged from 62 to 68 dB below 0 VU.

A few tips on the mechanical aspects of copying records are in order here. The importance of good tracking cannot be overemphasized. More can be gained here than with any amount of electronic processing. Groove radius, depth, and angle were not standardized on early discs, and experimentation with tracking force and stylus size, if possible, may yield a considerable improvement in both noise and distortion. The playback

stylus should, of course, ride on the sides of the groove. If it is too small it may ride the bottom of the groove and skate from side to side in a partially uncontrolled manner, creating severe distortion. If too large, it will ride high in the groove where it is more sensitive to surface blemishes. Also, larger styli cannot follow high-frequency modulation as well, especially on the inner record grooves. Elliptical styli are helpful on relatively wide-range 78s if the latter have not been damaged by previous playings.

Acoustic records (1925 and earlier) tend to have a larger groove, since with acoustic playback the mechanically-imparted stylus motion had to supply all the sound power. For these, a stylus of 4-mil (.004") radius may produce better results than the standard 3-mil size. Custom-made styli with a "truncated" tip (really a smooth transition from a 2- or 3-mil radius to about a 4-mil radius at the very tip) have been used to track the groove sides of 78s properly while avoiding contact with the bottom. (Truncated and other special styli are available from the International Observatory Instruments, 5401 Wakefield Drive, Nashville, Tenn. 37220). Although not a cure-all, these can give dramatic results on selected discs. A 2.5 mil stylus is best for most post-1946 transcriptions. Obviously, the pickup should have adequate lateral compliance and should produce no output for vertical motion. Incidentally, electrical recordings made before the mid-1940s are mostly recorded flat, that is, they have no high-frequency pre-emphasis, while later records have pre-emphasis of as much as 16 dB at 10 kHz.

Edison cylinders (160 rpm) and discs (80 rpm), some Pathe discs, and some early wax transcriptions are vertically modulated. Here the stylus does ride on the groove bottom, and the pickup should have only vertical response. This can be obtained (as can lateral-only response) from a suitably-phased stereo cartridge. Stylus radii of 4 to 10 mils are typical here; as always, experimentation is in order.

## FUTURE DEVELOPMENT

The experimenter may want to try to improve the performance of the circuit described. Of course, additional types of processing can be added, such as more effective click suppression at the filter input or multi-channel equalization at the output. These would be electrically independent of the noise filter, and beyond the scope of this article. However, there are some possibilities for improving the noise filter itself. Many of these, unfortunately, would require an

incongruous increase in complexity and cost.

Sharper filter cutoffs give a marginal improvement on very noisy material, but setup adjustments become more critical. Dynamic high-pass (low-cut) filtering using a simple 6 dB/octave slope might be a reasonable addition. Since the noise-rejection frequency band of the low-pass dynamic filter should complement the noise spectrum of the signal, a statistical study of record and tape noise spectra might lead to a better shape for the bandwidth-control-signal separation filter of Fig. 7. The separation filter selector could be ganged with the pre-filter cutoff switch to eliminate one control knob. Perhaps a noticeable improvement could be realized by experimenting with the shape of the bandwidth control characteristic, Fig. 9. The attack time constant could be shortened by using a more elaborate filter at the precision detector output; this would improve the response to occasionally encountered wide-band transients.

An obviously desirable change would be to replace the FET bandwidth-control filter with one of the voltage-controlled state-variable types. This would eliminate the need for FET selection, but would increase the cost severalfold. It therefore appears that the original goal of high performance per dollar has been achieved, yielding a practical design which is within reach of the hobbyist.

## References

1. Burwen, R.S., "A Dynamic Noise Filter," *J. Audio Eng. Soc.* 19, PP. 115-120, Feb., 1971.
2. Mori, T., "Designing Low-Frequency Active Filters," *Electro-Technology*, P.72, Jan. 1968.
3. Langford-Smith, F., Ed., "Reproduction From Records", *Radiotron Designer's Handbook* (Wireless Press, 1953), PP. 701-774.
4. Scott, H.H., "Dynamic Noise Suppressor," *Electronics*, PP. 96-1001, Dec., 1947.
5. Fletcher, H., "Loudness, Masking, and Their Relation to the Hearing Process and the Problem of Noise Measurement," *J. Acoust. Soc. Am.* 9, PP. 275-293, Apr., 1938.

Maplin Electronic Supplies have told us that they plan to market a kit of this project. Interested readers should contact them directly.

This article has been reprinted by permission from Audio, June 1975. Some copy and drawing changes have been made to suit European conditions.

# ELECTRONICS PART 25

## -it's easy! The algebra of logic.

MATHEMATICS is a kind of shorthand language which enables us to present a physical process, on paper, with symbols which may be manipulated in order to gain a better understanding of the process. It is thus a tool which aids understanding.

The familiar kind of algebra which relates two variables,  $x$  and  $y$ , in combinations such as  $x+y$ ,  $x-y$ ,  $x.y$ ,  $x/y$ ,  $x^y$  and others is a linear process because the two variables can hold any value. It is this kind of algebra that is performed by analogue operational amplifiers.

However, if  $x$  and  $y$  can only have two possible states, such as a voltage which is there or not there, we can ignore the actual value of the voltage (or whatever) and regard the variables as behaving according to a two-state or binary number system. Just what the two states are is of no importance whatsoever — they can be high or low, positive or negative, there or not there and even true or false.

A mathematical algebra has been developed to cope with such binary systems. It is known as Boolean algebra — the algebra of logic, and its rules are somewhat different to those of linear algebra. Before delving into the operation of Boolean algebra, it is worth tracing its historical development.

### HISTORY OF SWITCHING MATHEMATICS

Philosophers, those people who apply special skills to resolving paradoxes by the use of logic, have existed since the earliest civilisations. The Ancient Greeks were so impressed with logic that they wrote plays around Aristotle's formally arranged rules of logical deduction. The rules for this process of reasoning were handed down, largely by word of mouth, through the Dark Ages, with little, if any, recognition of their value for logic in computation. It was not until the early 19th century that the use of logical rules in calculation was established. This work was very much the result of George Boole's 1854 work (see Fig. 1) entitled "An Investigation of the Laws of Thought on which are Founded the Mathematical Theories of Logic and Probabilities", Augustus de Morgan, a contemporary, also contributed to the first systematic arrangement of Aristotle's logic.

Boole took the concepts further than the Ancients by substituting

mathematical symbols in place of the basic logical situations. This symbolic logic became known as Boolean algebra.

Little was achieved with Boole's work for the next few decades. The first machine to utilize his algebra to solve logic problems, faster than by hand, was William Jevons' logical piano of 1869. Boole's contribution, however, had to wait until the early 20th Century to find extensive application. One by one, logicians advanced the techniques of logical algebra: Pierce, Venn, Dodgson, Marquand, Pastore, Bollee. The "Principia Mathematica" of Whitehead and Russell (1910-1913) and the Hilbert and Ackermann work "Mathematical Logic" (1928) were further



Fig. 1. In 1854 George Boole, an English logician, showed how ordinary algebra could be applied to logic situations.

milestones in digital computer realisation.

Shannon's 1938 paper "A Symbolic Analysis of Relay and Switching Circuits" was a paper of very practical relevance for it described how to put Boole's rather abstract logical algebra to work in engineering and computer design. But this was not the first recorded use of electrical logic circuits. In a letter Charles S. Peirce wrote to his former student, Marquand, around 1890 he expressed, in the words and circuit diagrams shown in Fig. 2, that logical algebra could be performed with three switches in parallel or in series, also stating that he felt electricity to be one of the best ways to implement logical equipment.

Later theoretical studies concentrated on ways to ensure that switching networks contained no more switch contacts than were absolutely necessary. Unnecessary contacts can easily be unwittingly designed into complex switching networks — the "spares" are called redundant switches. Shannon, in his M.Sc. thesis (Fig. 3) prepared at the famous Massachusetts Institute of Technology, realised ways to systematically set about analysing a given switching

network in order to reduce the contact requirements to a minimum. Thus it was realized in the early 1940's that really powerful digital computers could be built using entirely electronic components.

Later in the course we will be dealing specifically with computer systems. They are, however, but a part of the total use of digital electronic methods — digital electronics finds use in an ever increasing number of instruments and devices.

### BASIC LOGIC GATES

A quite satisfactory way to begin to comprehend basic switching algebra is to think in terms of mechanical switch contacts arranged in various different configurations. That we draw them and consider them as mechanical contacts that are either open or closed, does not imply that the contacts necessarily need to be mechanical — they are, today, more often than not the solid-state switches we discussed in the last part.

Groups of switches combining digital signal levels are known as gates. We begin by considering the simplest possibilities where there are just two contacts to build with.

They can be placed in series or in parallel, as shown in Fig. 4. In each case different conditions exist between the transmission made through them for the two positions of each of the switches. We denote the switch inputs as  $A$  and as  $B$  (and  $C, D$ , etc., if more are involved) and the transmission as  $Z$ , thus using mathematical symbols to represent a physical situation. Imagine that the switches are wired in series with a lamp: when a circuit is made the lamp lights.

In the series case we need switch  $A$  and switch  $B$  to be made to obtain a transmission function  $Z$ . In the parallel case either switch  $A$  or switch  $B$  will provide transmission.

The AND and OR are basic logical functions. They need not necessarily be used only to describe electrical circuitry. They did, in fact, as we have seen, arise originally from philosophical study of truths and falsities.

Note that switch contacts are always shown in their non-actuated condition and this brings us to another basic gate function which can be realised using only one switch. If, as shown in Fig. 5, the switch  $A$  is actuated,  $Z$  is NOT enabled. If  $A$  is not actuated  $Z$  is enabled. A single switch,

The problem, especially as it is by no means hopeless to expect to make a machine for really very difficult mathematical problems. But you would have to proceed step by step. I think electricity would be the best thing to rely on.

Let A, B, C be three keys or other points where the circuit may be open or closed. As in Fig. 1, there is a circuit only if all are closed. In Fig. 2 there is a circuit if any one is closed. This is like multiplication and addition in logic.

James Clerk Maxwell, C.S. Peirce

Fig. 2. The first known description of electrical switching carrying out logic is in this letter of C.S. Peirce written around 1880.



Fig. 3. Claude Shannon published details of "modern" digital computing design in 1937.

therefore, can provide a NOT function if its contacts are closed in the non-actuated state.

Attempts to explain switching circuit action in words, as above, only applies for the simplest of situations. The descriptive method becomes prohibitive when, say, we have two switches in series, in series with two switches in parallel, as shown in Fig. 6. Describing the action of all possible switch combinations on the lamp Z using words, is an inadequate way with which to communicate the idea. And few digital systems are that easy: many contain literally thousands of AND, OR and NOT gates.

We designate an OR function by means of the '+' symbol. This does not mean the same as our normal understanding of addition. When applied to decimal numbers it means addition as we normally understand it. With binary numbers, however, it has a different meaning and still another meaning when designating an OR function. For example:

In decimal addition 1+1=2  
 binary addition 1+1=10  
 OR addition 1+1=1

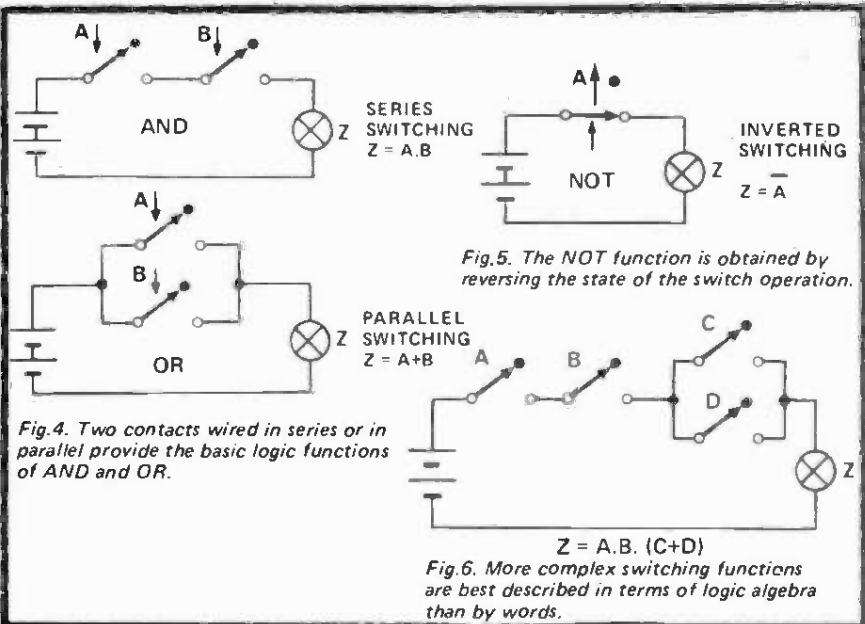


Fig. 4. Two contacts wired in series or in parallel provide the basic logic functions of AND and OR.

Fig. 5. The NOT function is obtained by reversing the state of the switch operation.

Fig. 6. More complex switching functions are best described in terms of logic algebra than by words.

In Boolean algebra the OR meaning of addition is the one that applies. Thus  $A+B=Z$  means that A OR B switch closed will produce a transmission Z.

We designate an AND function with a dot. The dot means logical multiplication and is not to be confused with normal multiplication. However the truth tables for AND

multiplication and normal multiplication are the same. Thus when we give the Boolean equation  $A.B=Z$  we mean that if switch A and switch B are both closed there will be a transmission Z.

The NOT function is designated as a line over the switches algebraic symbol giving  $Z = \bar{A}$  to mean Z is NOT transmitted when A is actuated.

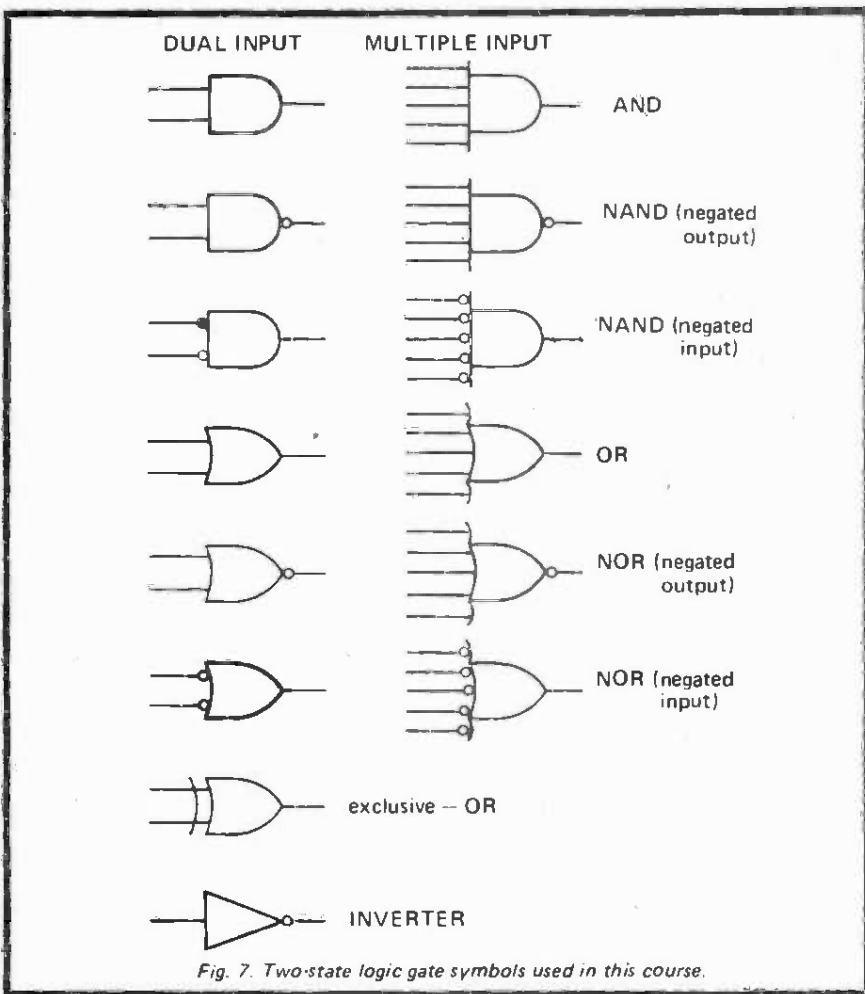


Fig. 7. Two-state logic gate symbols used in this course.

# ELECTRONICS -it's easy!

Each of these functions have a symbolic representation as black-boxes with inputs that act in certain ways to give the output. The shape of the box (or the designation within a square box) tells the viewer the function of the box.

Unfortunately there still exists more than one conventional way to draw these symbols. For this course we will use those given in Fig. 7, which are also those used in projects in Electronics Today.

The NOT function bar can be applied to any function to signify that it is negated. For instance, an OR such as  $A+B=Z$  becomes  $A+\bar{B}$  which is called a NOR function. Similarly so  $A\cdot\bar{B}$  is a NAND function.

The OR, AND, NOR and NAND functions can each have more than two inputs, for example,  $A+B+C+D=Z$ . When a function is negated its graphical symbol is also altered in some way to signify this. The convention used is the convention of the addition of a small round circle. If the circle is at the output the output is negated; if at the input the inputs are negated. The inverter (that provides negation) is basically an amplifier providing 180° phase shift so its symbol is that of an amplifier with the circle added.

## TRUTH TABLES

Before we discuss more complex gate networks by studying their inter-connection, we need to understand the concept of a truth table. This is a simply drawn table that lists the output state for the various combinations of input states.

Rather than write on and off, or high and low, true or false, it is simpler to express the two states merely as '0' and '1'. The positive logic convention considers a high-voltage level as a '1' and the low level as a '0'. Fortunately, today, just about all logic circuits used are now in integrated circuit form and they nearly all work between just two levels - which are the same for any devices from a particular logic family. This provides a compatible arrangement whereby gates and other logic system boxes (that are yet to be introduced) can each be intercoupled without having to worry about matching voltage and impedance levels. However, when transferring logic signals between devices from different logic families translator circuits will be needed to make voltage levels compatible.

Occasionally, but not commonly, it is more convenient to reverse the levels calling a 1 the lower voltage and an 0 the higher. This is denoted negative logic. Such a system is however seldom used in modern integrated-circuit logic

families.

Consider then the series contacts of Fig. 4. Assuming we use the positive logic convention where 0 represents an open contact and 1 a closed contact; it is easy to draw up columns as given in Fig. 8.

When A and B are both 0 then so also is Z, for no contacts are made. Similarly, if either A or B are open. When both A and B are closed, that is a 1 each, then Z is made. This is called a truth table.

Fig. 9 is the truth table for the parallel contacts of Fig. 4. In this case Z is 1 when A or B are 1.

An interesting property of the AND and OR functions is their dual nature when negated. For example, if we negate the inputs of the OR gate the truth table becomes that of Fig. 10,

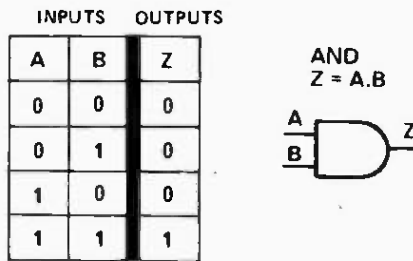


Fig. 8. Truth table for  $A \cdot B = Z$ , the AND function.

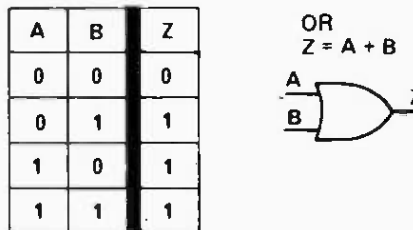


Fig. 9. Truth table for  $A + B = Z$ , the OR function.

POSITIVE LOGIC		NEGATIVE LOGIC		NAND AND (IN POSITIVE LOGIC)	
A	B	$\bar{A}$	$\bar{B}$	Z	$\bar{Z}$
0	0	1	1	1	0
0	1	1	0	1	0
1	0	0	1	1	0
1	1	0	0	0	1

Fig. 10. Truth table showing that negative logic (or negated positive logic) input to an OR gate provides NAND output.

the output of which is the NAND function. Hence a negated input OR gate is a NAND gate. Also, by similar reasoning, a negated input AND is a NOR. Put another way, in negative logic an OR becomes an AND and vice versa.

## UNIVERSAL GATES

Using the basic gates, AND, OR and NOT, we can build a logic circuit for any given Boolean expression. Where there is a plus sign (+) we use an OR gate, where there is a dot we use an AND gate and we use an NOT gate for those functions that are negated.

However it is interesting that the NAND gate can be used to obtain any desired function. It can be used to build AND, OR or NOT gates. In other words it is a universal building block, as is the NOR gate also.

Thus the majority of gates used in modern logic systems are NAND gates with the occasional use being made of NOR gates and inverters (NOT) to minimize complexity. The use of one major form of gate simplifies manufacture and reduces costs.

## FAN OUT

There exists a finite number of circuits that can be safely connected to the input, or the output, of logic elements. This number is called the fan-in and fan-out respectively, and gives the number of standard loads that can be accommodated. Fanouts of 10 and 30 are typical load factors.

## EXCLUSIVE OR

One other important gate is a special class of the OR - the exclusive OR. The logic action of this gate is seen by studying its truth table which

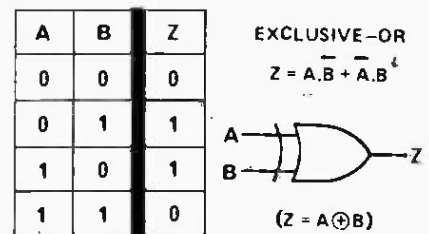


Fig. 11. Truth table for two input exclusive-OR gate.

is given in Fig. 11. In this variation of the basic OR gate the output is 1 for either A or B but not when both are 1 simultaneously. Written in Boolean algebra symbols this gate performs  $A \cdot \bar{B} + \bar{A} \cdot B = Z$ . (Symbols written as AB imply that a dot exists between them; it is common practice to omit the AND dot).

electronics  
today international

**SOLD OUT**

- THE MOST POPULAR CONSTRUCTIONAL ARTICLES.
- 2-CHANNEL MASTER MIXER
  - LOWER POWER LASER
  - ELECTRIC IGNITION
  - UHF TV PREAMPLIFIER
  - WIDE RANGE VOLTMETER
  - SIMPLE LOUDSPEAKER
  - TRANSISTOR TESTER
- PLUS MANY MORE

electronics  
-it's easy



**1. TOP PROJECTS No. 1**  
21 projects  
1974  
75p + 15p P&P

**2. TOP PROJECTS No. 2**  
26 projects  
Published July 1975  
75p + 15p P&P

**3. ELECTRONICS IT'S EASY**  
First 13 parts of our popular introductory series  
£1.20 + 15p P&P

**4. INTERNATIONAL 4600 Synthesiser.**  
Maplin, who supply the parts have reprinted this project  
£1.50 + 15p P&P

**SPECIALS**

50W STEREO AMP. TEMPERATURE ALARM. LM380 INTERCOM AND RECORD PLAYER. RUMBLE FILTER. BATTERY CHARGER. TAPE/SLIDE SYNCHRONISER. METED ...  
FAMILY ...

**ETI TOP PROJECTS No. 2**  
electronics today international **75p**

... BEATER. ... FERRY. LINEAR IC TESTER. IGNITION TIMING LIGHT. SPRING LINE REVERBERATION UNIT. ADD-ON QUAD UNIT. NI-CAD BATTERY CHARGER. DIGITAL STOPWATCH. HI-POWER STROBE. TRAFFICATOR CANCELLOR. AUDIO WATTMETER. FET 4-INPUT MIXER. PRINTIMER. AUTOMATIC CAR THEFT ALARM. IC POWER SUPPLY. OVER-LED. AERIAL MATCHER. LOGIC PROBE. PLUS MANY MORE....

**ELECTRONICS TODAY**

INTERNATIONAL 4600  
SYNTHESISER



**RES**

maplin electronic supplies

To ETI Specials, ETI Magazines, 36 Ebury Street, London SW1W 0LW  
Please send me the following special publications (please mark quantities)

TOP PROJECTS BOOK ONE (75p) TOP PROJECTS BOOK TWO (75p)  
ELECTRONICS IT'S EASY (£1.20) INTERNATIONAL 4600 (£1.50)

POSTAGE AND PACKING is 15p for the first 10p for subsequent (overseas 20p and 15p)

Please send me the issues indicated above. I enclose

NAME

ADDRESS

# ELECTRONICS TOMORROW

by John Miller-Kirkpatrick

I had found several interesting snippets about new products that I had hoped to relate to you in full this month but I have suffered from the great Post Office holdup. Information which was sent to me from Bedford had not arrived over a week later and so we will devote most of this month's column to a new American product; the data arrived from Ohio within three days of my enquiry. The new product is only a new approach to the age old problem of breadboarding circuits before setting them permanently onto Veroboard or PCBs.

The version I have, is called an ACE board made by AP products Inc of Ohio, but a similar unit is called a PROTOBOARD and is advertised regularly in the American amateur magazines. The idea is similar to the S-Dec and T-Decs that have been on sale for several years except that the new boards are built on a 0.1 inch matrix with sockets that are good enough to take ICs of any size. The board that I received is called an ACE-201K and comes in a kit form containing three plastic mouldings, aluminium base with self-adhesive area, 195 terminal strips, rubber feet and two binding posts. The unit took me less than 30 minutes to assemble and it went to work almost immediately with a new clock circuit on it. Of the three mouldings one is 48 holes long by two holes wide and contains a continuous strip of sprung metal connecting all 48 holes in one channel with a similar strip connecting all the holes in the other channel, this acts as a distribution bus for ground and supply voltage. The aluminium base is connected to the ground supply to give a good backplane for circuits that require it. The other two mouldings sit one on either side of the distribution bus and each contains two lots of 5 by 48 holes with the metal strips connecting each set of 5 holes.

Thus you end up with four lots of 48 five connector terminal strips with the distribution strip running down the centre.

This board has the capability of handling up to twelve 14 pin ICs where each pin of each IC can have up to four leads connected to it, it will handle a couple of 28 or 40 pin ICs plus transistors, capacitors, resistors, etc with plenty of tie-points left over. The two binding posts are intended to connect out to your power supply although I believe that one of the Protoboard range has a 5v 1A supply built into the unit to give a complete TTL or CMOS test bed.

## PROTOTYPER


Something that I built for my own lab a few years ago could be of interest to readers who do a lot of TTL development work and could be built using one of the above boards. I used an S-Dec as the basis of my prototyping unit and built it into the top of a smallish instrument case. The idea if the unit is to use the S-Dec sockets as inputs and outputs to standard TTL units which are built on veroboard inside the case. To build a simple unit you might require a couple of 7400s, 7402, 7404, 7406, 7410, 7420, 7490s, 7493s, etc, in fact whichever gates you usually use. You have to open up the S-Dec and remove the copper connecting strips. Each strip is then cut up into individual socket units and a wire soldered onto the back of it before carefully gluing it back into the body of the S-Dec. This is a very tedious job but you end up with about 100 individual sockets each connected to a short length of wire, these wires can then be connected to the inputs and outputs of the TTL

gates which are powered separately. If you are not too worried about propagation delays you can connect the gate outputs to invert gates so that a 7400 could behave like a 7400 or a 7408. When the unit is completed you can have a row of five holes connected to each two input gate such as — INPA, INPB, OUT, OUT, INV-OUT. By simply pushing 22swg wires into these holes you can lead off a complete 7400 gate function to the breadboard that you are presently working on without having to place a 7400 on that breadboard. The second stage of the prototyping unit is to include counters, seven-segment displays, LED lamps, BCD switches, etc and then to include a Protoboard or ACE kit on the same layout. This gives you the capability of building just about any circuit you like as a prototype without much additional cost, having proved the circuit you can then strip it down and build something completely different. One further advantage of this type of unit is that you can use up all of your 7400s with one gate blown or 7490s with no A input, etc as these can now be hidden away inside the unit. A word of warning — if you decide to build a prototyping unit make sure that all of the internal ICs are in sockets for easy replacement or to be extra sure buffer each input and output by connecting a 7407 between the wire socket and the IC in use. This means that if you do overload a gate it will be the cheap 7407 which goes not the 7490 or whatever, in this case make all of the 7407s easily accessible for replacement. Perhaps we might have an ETI Prototyper in a future issue.

If you would like to buy an ACE-201K breadboard kit you can try to contact a company called GDS in Slough but you will probably meet the unhelpful buck-passing that I did; they do sell AP products but have never heard of ACE boards. You can definitely get one from AP Products Inc, Box 110, 72 Corwin Drive, Painesville, Ohio 44077 if you send them about 27 dollars (24.95 plus postage) — this is a worthwhile investment in any lab whatever its size.
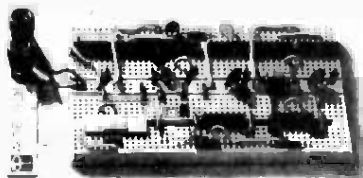
## DISPLAYS TIME AND FREQUENCY

I have previously mentioned the Futaba fluorescent (Phosphor-diode) display type 5-LT-01 for use in digital clocks and the 5-LT-03 display for use with counters especially for use with the G1 digital FM tuner chip. For those of you who



want to build a digital readout for your tuner and want to use the same display for a digital clock wait for a new display from Futaba. This has the same four digits, colon and AM/PM as the 5-LT-01 but has also got an extra digit '1' on the left, MHZ/KHZ on the right and a complete set of decimal points. Thus it can display time with colon and AM or PM or can display tuned frequency from 1.9999 to 19999 with the choice of MHZ or KHZ. The type number and price have not yet been announced but I suspect that it will cost about £7 and be available about April. At the same time Futaba have also announced a display for a digital car clock to interface with the MM5378 (the higher voltage version MM5379 might be better), the display size is about 0.25in and contains four digits plus colon. The drive voltage for the display is about 30-35 volts at about 15mA, this could easily be derived from the car voltage through a simple inverter circuit.

#### CLOCK CHIPS

One clock chip that flared into light a few years ago and then almost disappeared was National's MM5316. This is a non-multiplexed chip with four digit output which

will show hours and minutes, minutes and seconds, alarm time or 'Sleep' time, two outputs provide switching of radio or alarm with the 'Sleep' timer allowing you to go to sleep with the radio turned on. This chip was quite expensive but would drive Dynamic Liquid-Crystals or Fluorescent displays directly or LEDs via thirty transistors, the total cost of a clock using these was in the area of £50. National used the same logic on some other chips (MM5371, MM5370) but these also died in this country. Now several other manufacturers have second-sourced this chip (S1998, uPD5316, KM5139, etc) and also National have brought out some LED drive versions (I can't remember the numbers) and whichever chip you use the price is now a lot lower.

Futaba have now made the 5316 clock a little bit simpler and cheaper with the introduction of the 5-LT-02. This fluorescent display is externally very similar to the 5-LT-01 the only difference being that the display is non-multiplexed, 'Great', I hear you say, 'a non-multiplexed display for a non-multiplexed clock chip'. Futaba have been just a bit cleverer than that by making the 5-LT02 almost pin

compatible with the 5316, wiring up on veroboard would be a cinch, hand drawing a PCB would be even simpler, and at a price of about £7 it is cheaper per digit than LCD or LED. As the additional components for the clock cost less than £1 (plus a small transformer) this could work out to a very cheap DIY alarm clock. The 5-LT-02 displays should be available within a month or may well be in the UK by the time this article appears.

In case you have never heard of fluorescent displays they are very bright, green, low current (1 or 2 mA per segment), the disadvantages are a heater (5V 50mA) and a drive voltage of about 35V.

*References: Futaba Displays and National Clock chips — Bywood Electronics, 68 Ebbens Rd, Hemel Hempstead, HP3 9QRC.*

*NEC (uPD5316) and Futaba — Walter Scott, Imp House, Ashford Rd, Ashford, Middx.*


*Toko (KM5139) — Ambit International, 37a High St, Brentwood, Essex.*

*ACE-201K — GDS Sales, ??? Bath Rd, Slough. Tel Slough 30211.*

*PROTOBOARDS — Ancrona Corp, Box 2208, Culver City, California 90230.*
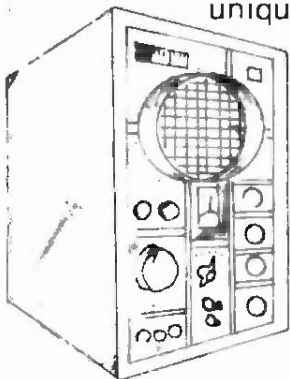
## 1. Understand electronics.


Step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered using our unique Lerna-Kit course.



- (1) Build an oscilloscope.
- (2) Read, draw and understand circuit diagrams.
- (3) Carry out over 40 experiments on basic electronic circuits and see how they work.
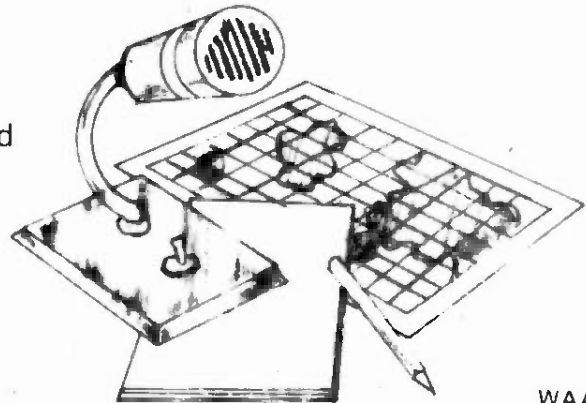
## 2. Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.



WAA

Brochure, without obligation to:

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept. ETX 36**

P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

Block caps please

**Free!**

# tech-tips


## LOW FREQUENCY EXTENDER

In circuits which have a variable frequency input, e.g. optical tachometers, vibration measuring equipment etc., the low frequency response can leave a lot to be desired. The circuit shown brought the lower 3dB point of a measuring instrument down to 0.5Hz when placed in circuit between the transducer and the instrument.

Being of small size, the circuit may be fixed inside the case of the instrument it is to serve.

The gain of the circuit may be altered by means of the feedback capacitor to give a level response compatible with the instrument to which it is connected, i.e. a higher value will give a lower gain and vice-versa.

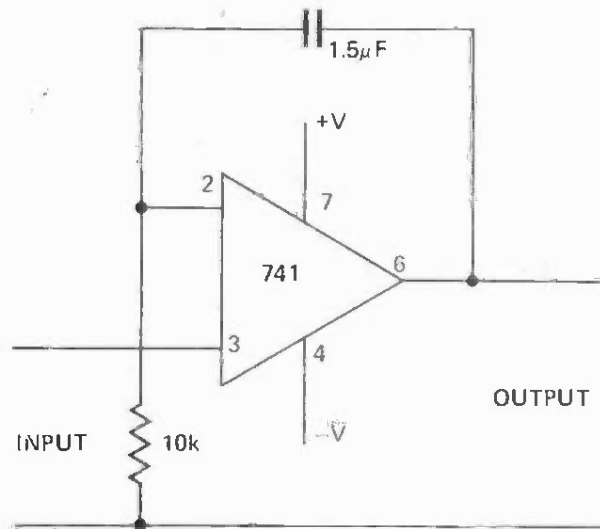The 741 IC will operate at voltages between  $\pm 5$  and  $\pm 15$ V.




## METERING A STABILISED POWER SUPPLY

It is not easy for the home constructor to make shunts of the correct value for a meter when wishing to alter its current range.

One way to monitor the current supplied by a current limited power supply is simply to measure the voltage drop across the current limiting resistor. This is usually of the order of .65V, and if the series meter (R2) is calculated to give fsd when .65V is applied, will indicate the limiting current at fsd no matter what the value of R1 may be. In effect, the limiting resistor becomes the meter shunt.

For a basic 1mA meter, the series resistor R2 will need to be about 560Ω, for a 50μA meter it will be about 12kΩ, for a 5mA meter about 120Ω and so on.

Unless individual adjustment of resistors and calibration of range is undertaken, this method cannot be absolutely accurate, but it will show whether a circuit is drawing something like its expected current. The method does have the advantage however, of the meter being within the feedback loop, and will therefore not add to the power supply output impedance, which can be important in some applications.

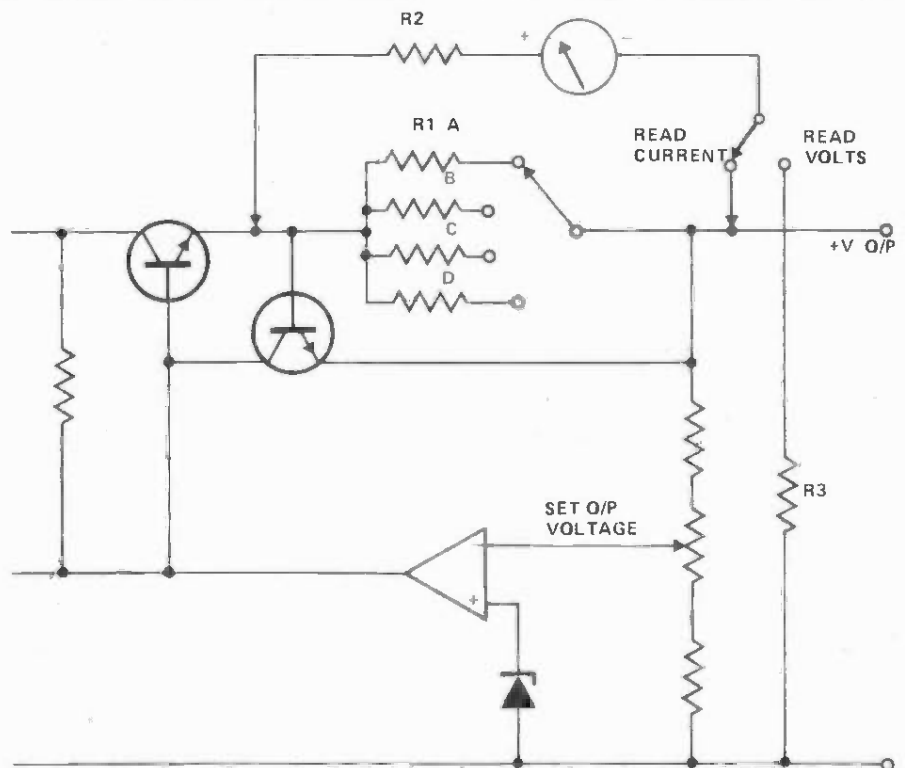

The addition of a single pole C/O switch as indicated will enable the meter to be used to set up the desired output voltage also, though it must be remembered that this will include the voltage drop across R1 if any

current is being drawn, which could lead to a difference of .5V or so between indicated and actual output voltage. R3 should be chosen to give fsd at maximum output voltage and the meter scaled accordingly.



Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items.


ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to the Editor, Electronics Today International, 36 Ebury Street, London SW1W 0LW.

## LOGIC ANALYSER


This circuit has been found useful for in-situ testing of TTL logic elements and general circuit development. An LED is used to indicate the state of the strobed input a short time (about 100ns) after the output of the 8 I/P NAND gate changes. Switch S1 is used to control whether the strobe occurs on the leading or trailing edge of the NAND gate.

The five control inputs and associated switches S2 to S6 determine when the strobe occurs relative to logic states in the circuit under test. In use, one or more of the inputs would be connected to appropriate points in the circuit, with switches S2 to S6 as described. For example, the state of a particular circuit point can be strobed each time a selected set of five other circuit points have the logic level 1,0,1,1,0 by setting the switches to +,-,+,+,-, respectively.

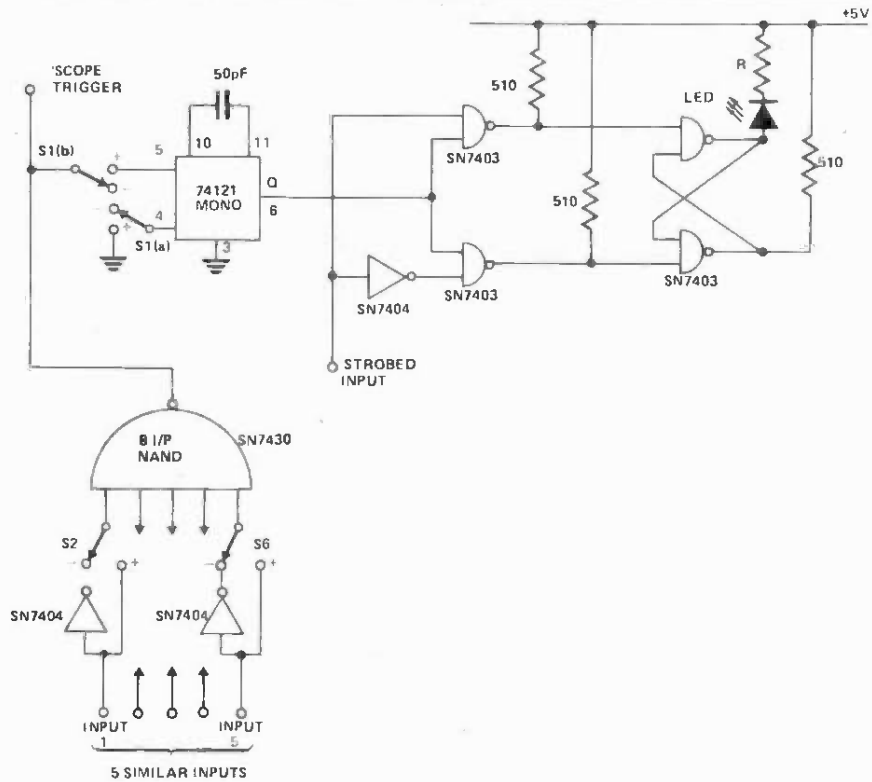An output to trigger an oscilloscope is provided to overcome a common problem in logic circuit testing of finding suitable trigger points in the circuit.



## SIMPLE ACCURATE FREQUENCY METER

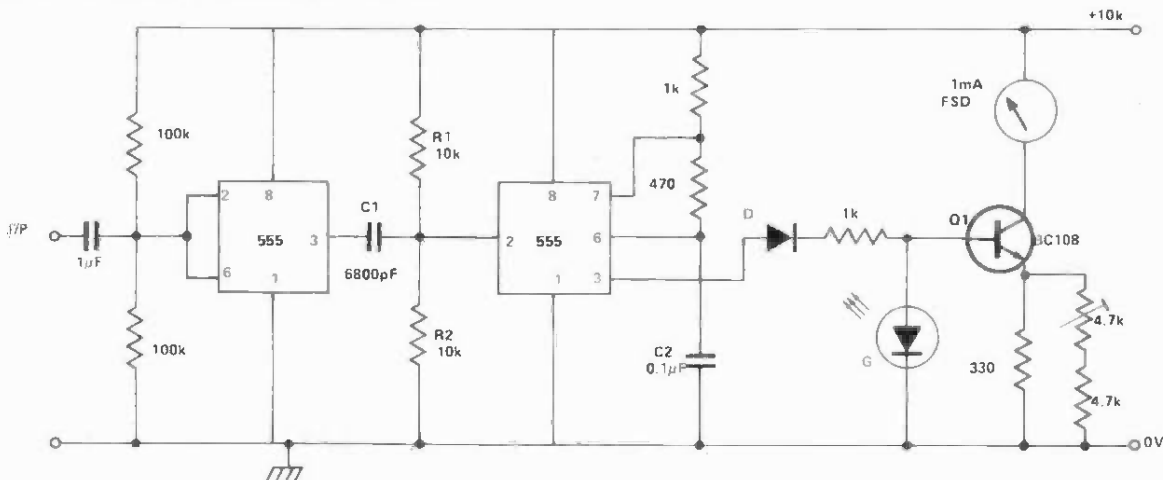

This circuit provides a meter deflection that is strictly proportional to the frequency of the input signal over the range 10Hz–300Hz. The first 555 timer IC is used as a Schmitt trigger, to convert the I/P signal to a fast-edge square wave. This is differentiated by the network C1, R1 and R2, and the resulting spikes used to trigger the

second 555, which operates as a monostable, generating constant width pulses. These are used to turn on the constant-current source Q1, so that the average current in the meter movement is proportional to the number of pulses arriving per second. A green LED is used to bias the current source as this gives near-


perfect temperature compensation; the 4k7 preset pot gives a fine adjustment for calibration purposes. When the 1mA meter shown is used, fsd is given by 100Hz. To extend the range, reducing C2 to .01µF gives an fsd of 1kHz.

# tech-tips
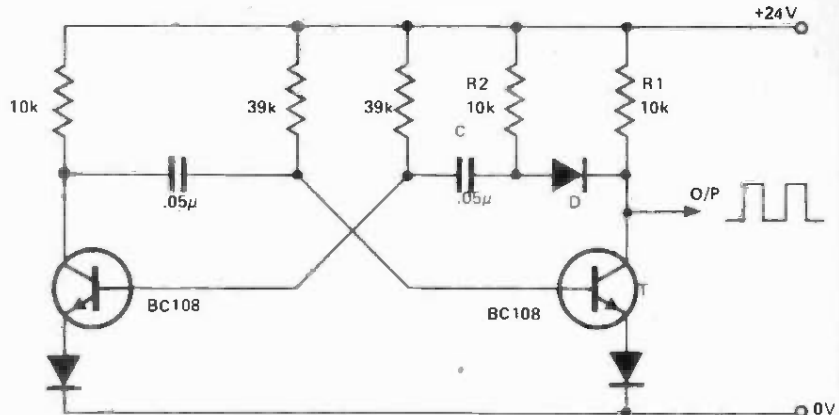
## IMPROVED MULTIVIBRATOR

Conventional astable multivibrators suffer from the disadvantage that they do not produce a good square-wave output; the leading edge of the waveform has a very slow rise since the collector resistor R1 is tied to a slowly charging capacitor C when the transistor T turns off.


This circuit prevents this effect and thus generates a clean square-wave with 400nS rise-times and 100nS full-times. This is because diode D turns off when the output begins to rise in voltage, and a fast rise is then possible. C is charged by a separate resistor R2, and apart from this multivibrator action is normal. The components shown give an operating frequency of about 700Hz.



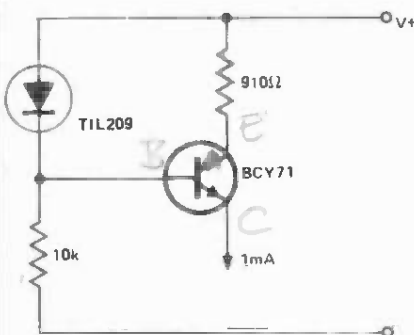
## TEMPERATURE-STABLE CURRENT SOURCE

This current source is very temperature-stable; the output current varies by less than 1% over the temperature range  $-55^{\circ}\text{C}$  to  $+100^{\circ}\text{C}$ . This is possible because the transistor is biased by an LED, whose forward voltage drop has a temperature coefficient of  $-2\text{mV}/^{\circ}\text{C}$ , the same as the base-emitter voltage of a silicon transistor. Hence near-perfect temperature compensation is possible, a great improvement over conventional methods of biasing with zener diodes.

The circuit values shown give an output current of about 1mA, though wide variation is possible by altering the value of emitter resistance. They are good for supply voltages in the range 25V to 5V.



## CARTRIDGE EQ AND RUMBLE FILTER

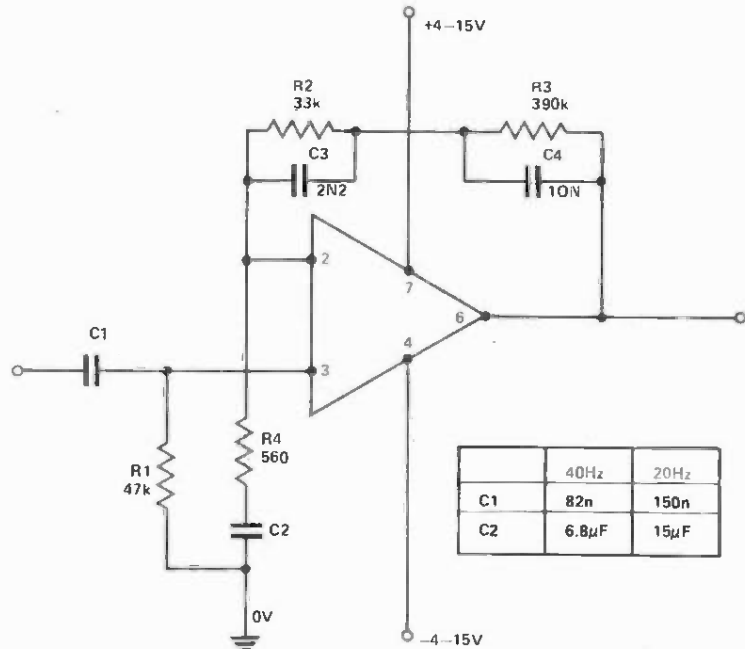

In this circuit a 741 op amp is used to provide standard RIAA equalisation for a magnetic pickup cartridge. The input signal is coupled via C1 into the non-inverting input of the IC. R1 damps the inherently high impedance at this point and provides the correct load for the cartridge. Feedback from the output, pin 6, is taken through the equalisation network R2, C3, R3 and C4 to the inverting input.

The ratio of R2 to R4 sets the midband gain at 65, 35dB. C1 and C2 together form a steep cut rumble filter whose cut off point can be set at 20 or 40Hz by selecting the appropriate component values in the table.

C2 also reduces the dc gain of the circuit to unity so that the output offset voltage will be  $\pm 5\text{mV}$  with reference to 0V.

One of the major disadvantages of discrete equalisers is overload distortion. Although the output of a magnetic cartridge may be only about 5mV normally a musical peak may well force the cartridge output to 100mV. Clearly unless a large signal swing is possible the sound emanating from the speaker is not going to be Hi-Fi.

This circuit, operating from a  $\pm 15\text{V}$  supply, has an overload factor of +35dB referred to a nominal input of 5mV, equivalent to a maximum input of 325mV!

### MAINS TRANSFORMERS

Pri. 240v. sec. 27/0/27v at 800 m/a, **£2.25**. P.P. 50p.  
 Pri. 110/240v sec. 50v at 10amps, **£10.00**. P.P. £1.50.  
 Pri. 110/240v sec. 20/21/22v at 8 amp, **£6.00**. P.P. £1.50.  
 Pri. 110/240v sec. 23/24/25v at 10 amp, **£7.00**. P.P. £1.50.  
 Pri. 110/240v sec. 24/40v at 1½ amp, **£1.90**. P.P. 60p.  
 Pri. 240v sec. 20/40/60v at 2 amp, **£3.00**. P.P. 70p.  
 Pri. 240v sec. 20v at 2½ amp, **£2.00**. P.P. 50p.  
 Pri. 240v sec. 18v at 1.5 amp and 12v at 1 amp, **£2.25**. P.P. 50p.  
 Pri. 240v sec. 18v at 1 amp, **£1.00**. P.P. 30p.  
 "TOROIDAL" Pri. 240v sec. 30v at ½ amp, **£1.65**. P.P. 30p.

### SIEMENS MINIATURE RELAYS

6v 4c/o with base, **65p** ea.  
 24v 2c/o with base, **50p** ea.

### MAINS RELAY 240v

3c/o 10 amp contacts, **80p** with base. P.P. 20p.

### GARRARD PLINTH & COVER

For Zero-100, etc. Finished in brushed aluminium and black, with hinged smoke grey perspex lid, **£11.00**.

### BLUE P.C.B. INK

Etch resist, use with any pen, much cheaper than ready-loaded pens 50ccs. Price **55p**. P.P. 10p.

### PRINTED CIRCUIT KIT

No frills, alt. value kit containing 4 pieces 8" x 7" formica laminate, 1 pce. 6" x 6" fibre-glass laminate, 1 lb. etching crystals, 50 ccs resist-ink with instructions. **£2.30**. P.P. 50p.

### CIRCUIT BOARD

P.C.8. 1/16. 1 oz. COPPER FORMICA

Dim. 8.4 x 7.7 in 3 pcs., **75p**.  
 Dim. 9.4 x 8.1 in 3 pcs., **90p**.  
 Dim. 10.1 x 7.9 in 3 pcs., **£1.00**  
 Dim. 13.1 x 9.4 in 3 pcs., **£1.20**.  
 Dim. 17.0 x 9.0 in 2 pcs., **£1.20**.  
 Post & Packing 30p each pack.

### BARGAIN PACK

10 pcs. 10.1 x 7.9 in. Plus free 1/2 lb etching Xtals, **£2.80**. P.P. 45p.

### FIBRE GLASS P.C.B.

Dim. 6 x 6 in, **35p** each.  
 Dim. 12 x 6 in, **60p** each.  
 Dim. 12 x 12 in, **£1.00** each.  
 Equals less than 1p sq. in.  
 Post & Packing 5p per sheet.

### RESIST COATED P.C.B. FORMICA

10.1 x 7.9 in, **55p** ea.  
 13.1 x 9.4 in, **70p** ea.

### RESIST COATED P.C.B. FIBRE GLASS

6 x 6 in, **50p** ea.  
 12 x 6 in, **90p** ea.  
 12 x 12 in, **£1.50** ea.  
 Post & Packing 10p per sheet.

### FERRIC CHLORIDE ETCHING XTALS

1 lb — 1 litre pack, **60p**. P.P. 15p.  
 5 lb — 5 litre pack, **£1.95**. P.P. 55p.

### S-DECS AND T-DECS

S-DEC **£1.90**. Post & Packing 20p.  
 T-DEC **£3.60**. Post & Packing 30p.  
 U-DEC A **£4.20**. Post & Packing 20p.  
 U-DEC B **£6.90**. Post & Packing 40p.

### OVERLOAD CUT-OUTS

Panel mounting 800 M/A. 1.8 amp. 10 amp. **55p** ea.

### HIGH CAPACITY ELECTROLYTICS

250mfd/63 volt, **20p**. P.P. 8p.  
 1000mfd/100 volt, **70p**. P.P. 25p.  
 2200mfd/100 volt, **90p**. P.P. 25p.  
 4700mfd/25 volt, **65p**. P.P. 20p.  
 6800mfd/16 volt, **50p**. P.P. 15p.  
 10,000mfd/25 volt, **75p**. P.P. 25p.  
 25,000mfd/40 volt, **£1.25**. P.P. 30p.  
 47,000mfd/40 volt, **£2.00**. P.P. 50p.  
 100,000mfd/10 volt, **£1.50**. P.P. 50p.  
 160,000mfd/10 volt, **£2.00**. P.P. 50p.

### 10.7 M.H.Z. CANNED I.F.S

Size 1 x ½ x ½ in, **65p**. P.P. 10p.  
**3 Gang Tuning Capacitor**, 8.5pf to 320pf, **80p**. P.P. 20p.

### MINIATURE METERS

500 micro-amp (level-stereo beacon, etc.). scaled half black/half red. Size 1 x 1 in, **65p**. P.P. 15p.


### RIBBON CABLE

8 way, 8 colours. Bonded flat side by side.  
 10 Metres, **£1.90**.  
 100 Metres, **£12.50**.
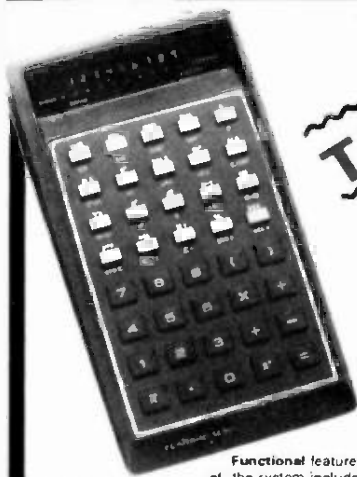
## KINNIE COMPONENTS

10 NELMES WAY, HORNCURCH  
 ESSEX RM11 2QZ  
 HORNCURCH 45167

MAIL ORDER ONLY. PERSONAL CALLERS BY APPOINTMENT



# THE POWER HOUSES

## SC60 ADVANCED SCIENTIFIC

The SC60 is the most advanced scientific and statistical calculator in its price range.

- 3 memories
- 50 functions
- 66 keyboard commands

#### Operating Features

● Algebraic mode entry ● Two nested parentheses levels ● Number entry in floating point or scientific notation ● Automatic selection of current notation for result display (scientific or floating point) ● 10 digit mantissa 2 digit exponent ● Sign selection and display (mantissa and exponent) ● Full chain calculation with any function sequence ● Three user addressable memories — "Protected" memory group includes — Sum memory — Sum-of-squares memory — Index memory.

- Functional features of the system include:
- Basic arithmetic +, −, ×, ÷
  - Trig functions (sin, cos, tan)
  - Inverse Trig functions (sin<sup>-1</sup>, cos<sup>-1</sup>, tan<sup>-1</sup>)
  - Logarithms (ln, log) ● (Anti-logs (e<sup>x</sup>, 10<sup>x</sup>))
  - Exponentiation (y<sup>x</sup>)
  - Combinatorial functions (n!, C(n,r), P(n,r))
  - Normal Distribution function (P(x))
  - Gamma function (Γ(x))
  - Arithmetic mean, standard deviation, variance, sq. rt. of sum of squares, norm.
  - Group operations (Σ, Σ<sup>2</sup>, Σ<sup>2</sup>, Σ<sup>2</sup>, Σ<sup>2</sup>, CL GRP)
  - Convenience functions (1/x, x<sup>2</sup>, √x, π)
  - Flexible memory control (STO, RCL, X↔M)
  - Factor reversal (X<sup>Y</sup>)
  - Degree/Radian selection (Trig or Inverse Trig)
  - Automatic error detection and display
  - Separate Clear operations (CE, CL, CLF, CLR)

MEMORY: three addressable memories which can also be used automatically for statistical functions, with sum memory, sum of squares memory and index memory plus index register.  
 ACCESSORIES as for SC44 SCIENTIFIC

### SC60.10 MEMORY

Also available is the SC60.10 — which has 10 operator accessible memories with protected group memory which includes sum-memory, sum of squares memory, and index memory **£64.95 inc. VAT p.&p.**



## SC44 SCIENTIFIC

(1) Operating features of the system include:

- Number entry in floating point or scientific notation.
- Automatic selection of correct notation for result display (scientific or floating point)
- Algebraic problem entry.
- Two parenthesis levels.
- 8 digit mantissa 2 digit exponent
- Sign selection and display (mantissa and exponent)
- Full chain calculation with any function sequence.

#### 1 YEAR WARRANTY

ACCESSORIES INCLUDE  
 Nicol rechargeable batteries, A/C adaptor/charger leatherette carry case, instructions, 1 year guarantee, weight 330 grams

We repair most makes of calculators, send s.a.e. for quotation

**£34.56 inc. VAT & pp.p.**

Please send me SC60 - £54 inc. VAT, p.&p.  
 or SC60.10 - £64.95 inc. VAT, p.&p.  
 or SC44 - £34.56 inc. VAT, p.&p.

NAME .....

ADDRESS .....

Orders to: **KRAMER & CO., 9 October Place, Holders Hill Road, London NW4 1EJ.** Tel 01-203 2473. Telex 888941 attention KRAMER. Registered No. 1797716. Export orders invited.

# Wilmslow Audio

**THE firm  
for  
speakers!**



Baker Group 25 3, 8, or 15 ohm	£8.64
Baker Group 35, 3, 8 or 15 ohm	£10.25
Baker Deluxe, 8 or 15 ohm	£13.75
Baker Major, 3 or 15 ohm	£11.87
Baker Regent, 8 or 15 ohm	£10.00
Baker Superb, 8 or 15 ohm	£18.12
Celestion MH 1000 horn, 8 or 15 ohm	£13.50
EMI 2A" tweeter 8 ohm	£0.77
EMI B x 5, 10 watt, d/c, roll/s 8 ohm	£3.95
Elac 59RM 109 15 ohm, 59RM114 8 ohm	£3.44
Elac 6 1/2" d/c roll/s 8 ohm	£4.06
Elac TW4 4" tweeter	£1.75
Fane Pop 15 watt 12" 8 or 16 ohm	£5.25
Fane Pop 55, 12" 60 watt 8 or 16 ohm	£13.95
Fane Pop 60 watt, 15" 8 or 16 ohm	£17.25
Fane Pop 70 watt 15", 8 or 16 ohm	£18.75
Fane Pop 100 watt, 18" 8 or 16 ohm	£26.98
Fane Crescendo 12A or B, 8 or 15 ohm	£34.50
Fane Crescendo 15, 8 or 15 ohm	£47.50
Fane Crescendo 18, 8 or 15 ohm	£62.95
Fane 807T B" d/c, roll/s, 8 or 15 ohm	£5.75
Fane 801T B" d/c roll/s 8 ohm	£9.95
Goodmans 8P 8 or 15 ohm	£5.50
Goodmans 10P 8 or 15 ohm	£5.80
Goodmans 12P 8 or 15 ohm	£13.95
Goodmans 12P-D 8 or 15 ohms	£16.95
Goodmans 12P-G 8 or 15 ohms	£15.95
Goodmans Audiom 200 8 ohm	£13.90
Goodmans Axiom 100 8 ohm	£8.44
Goodmans Axiom 402 8 or 15 ohm	£20.00
Goodmans Twinaxiom 8" 8 or 15 ohm	£10.14
Goodmans Twinaxiom 10" 8 or 15 ohm	£10.75
Kef T27	£6.06
Kef T15	£6.94
Kef B110	£8.37
Kef B200	£9.50
Kef B139	£16.95
Kef ON8	£2.31
Kef ON12	£5.99
Kef DN13	£4.50
Richard Allan CG9T 8" d/c roll/s	£8.50
STC 400 1 G super tweeter	£6.56
Baker Major Module, each	£13.44
Goodmans Mezzo Twinkit, pair	£47.19
Goodmans DIN 20, 4 ohm, each	£14.75
Helme XLK30, pair	£19.00
Helme XLK 33, pair	£24.00
Helme XLK 40, pair	£35.00
Helme XLK50, pair	£56.00
Helme XLK 60, pair	£56.00
Kelii T, pair	£53.00
Kef III, each	£48.00
Peerless 3/15 (3 sp. system) each	£17.19
Richard Allan Twinkit, each	£10.95
Richard Allan Triple B, each	£16.50
Richard Allan Triple, each	£23.95
Richard Allan Super Triple, each	£28.75
Wharfedale Linton 2 kit (pair)	£23.12
Wharfedale Glendale 3 kit, pair	£40.62
Wharfedale Dovedale 3 kit, pair	£63.12
Wharfedale Super 10 RS/OD	£15.00
Castle Super 8 RS/OD	£10.31
Jordan Watts Module 4, 8 or 15 ohm	£17.06
Tannoy 10" Monitor HPD	£67.75
Tannoy 12" Monitor HPD	£72.50
Tannoy 15" Monitor HPD	£92.95

Prices correct at 19.1.76

**INCLUDING VAT AT 25% ON HI-FI  
8% ON PRO AND PA**

Cabinets for PA and HiFi, wedding, Vynair, etc.  
Send stamp for free booklet "Choosing a Speaker"

**FREE with all orders over £10 — "HiFi  
Loudspeaker Enclosures" Book**

**All units are guaranteed new and perfect  
Prompt despatch**

Carnage Speakers 50p each, 12" and up 75p each  
tweeters and crossovers 30p each, kits 80p each (t. 1.60  
pair)

**WILMSLOW AUDIO**  
Dept. ETI

Swan Works, Bank Square, Wilmslow,  
Cheshire SK9 1HF. Tel. Wilmslow 28599  
(Discount HiFi, PA and Radio at  
10 Swan Street, Wilmslow)

# BUILD THE TREASURE TRACER MK III

METAL  
LOCATOR



AS SEEN  
ON BBC-1  
& BBC-2  
TV

- Genuine 5 silicon transistor circuit, does not need a transistor radio to operate.
- Incorporates unique varicap tuning for extra stability.
- Search head fitted with Faraday screen to eliminate capacitive effects.
- Loudspeaker or earphone operation (both supplied).
- Britain's best selling metal locator kit, 4,000 already sold.
- Kit can be built in two hours using only soldering iron, screwdriver, pliers and side-cutters.
- Excellent sensitivity and stability.
- Kit absolutely complete including drilled, tinned, fibreglass p.c. board with components siting printed on.
- Complete after sales service.
- Weighs only 22oz; handle knocks down to 17" for transport.

Send stamped, self-addressed envelope for literature.


Complete kit  
with pre-built  
search coil **£12.50**  
Plus 85p P & P  
Plus £1.00 VAT (8%)

Built, tested  
and Guaranteed **£17.50**  
Plus 85p P & P  
Plus £1.40 VAT (8%)

**MINIKITS ELECTRONICS,**  
6d Cleveland Road, South Woodford,  
LONDON E18 2AN  
(Mail order only)

# RADAR INTRUDER ALARM

MICROWAVE  
PROTECTION

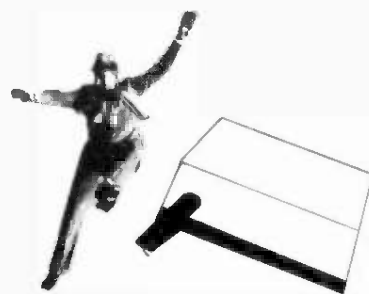

GIVES COMPLETE  
PROTECTION  
TO YOUR HOME OR  
OFFICE

- Genuine microwave doppler effect radar burglar alarm
  - Incorporates sophisticated electronic circuits
  - Can be made to project through walls, doors, glass, etc.
  - The room is filled with microwaves and cannot be entered without activating the alarm.
  - Easily installed.
  - Adjustable sensitivity filter control, to eliminate small objects.
  - No hidden wires, switches.
  - Internal alarm and outputs for external devices.
- Simply position the radar intruder alarm to give maximum room coverage and switch on.
- Battery or mains operation.

Built, tested  
and Guaranteed **£49.95**  
Plus 75p P&P  
Plus £4.06 VAT

Manufactured exclusively for  
**METAC INTERNATIONAL**  
Dept. B, Cross Lane,  
Braunston  
Daventry, Northants  
Tel. Rugby 890 672

Barclaycard, Access welcome

# LYNX ELECTRONICS (LONDON) LTD

Transistors	BC183 18p*	BF337 32p	CRS1-10 25p	2N697 12p
AC126 15p	BC183L 18p*	BFW60 17p*	CRS1-20 35p	2N706 18p
AC127 16p	BC184 11p*	BFX29 26p	CRS1-40 48p	2N929 14p
AC128 13p	BC184L 11p*	BFX30 30p	CRS1-60 85p	2N930 14p
AC128K 25p	BC207B 12p*	BFX84 23p	CRS3-05 34p	2N1131 15p
AC141 10p	BC212 11p*	BFX85 25p	CRS3-10 43p	2N1132 16p
AC141K 20p	BC212L 11p*	BFY08 26p	CRS3-20 59p	2N1304 20p
AC142 18p	BC213 12p*	BFY50 20p	CRS3-40 69p	2N1305 20p
AC142K 28p	BC213L 12p*	BFY51 18p	CRS3-60 85p	2N1711 18p
AC176 16p	BC214 14p*	BFY52 19p	MJ480 80p	2N2102 44p
AC176K 25p	BC214L 14p*	BFY64 35p	MJ481 £1.05	2N2369 14p
AC187 18p	BC237 16p*	BFY90 65p	MJ490 80p	2N2369A 14p
AC187K 25p	BC238 16p*	BR100 20p	MJ491 £1.15	2N2484 16p
AC188 18p	BC300 34p	BRY39 40p	MJE340 40p*	2N2646 50p
AC188K 25p	BC301 32p	BRY19 18p	MJE371 60p	2N2905 18p
AD140 50p	BC323 60p	BSS20 18p	MJE520 45p	2N2905A 22p
AD142 50p	BC327 16p*	BSSX21 29p	MJE521 55p	2N2928R 10p*
AD143 48p	BC328 16p*	BSSY95A 12p	OAS 50p*	2N29286 9p*
AD149 45p	BC337 17p*	BT106 £1.00	OAS 30	2N29266 10p*
AD161 35p	BC338 17p*	BT107 £1.60	OA91 8p	2N3053 15p
AD162 35p	BCY70 12p	BT108 £1.60	OC41 15p	2N3054 40p
AL102 95p	BCY71 18p	BT109 £1.00	OC42 15p	2N3055 50p
AL103 93p	BCY72 12p	BT116 £1.00	OC44 12p	2N3440 56p
AF114 20p	BD115 55p	BU105 £1.00*	OC45 18p	2N3442 £1.20
AF115 20p	BD131 36p	BU105 £1.90*	OC70 10p	2N3570 80p
AF116 20p	BD132 40p	02 £1.90*	OC71 10p	2N3702 18p*
AF117 20p	BD135 36p	BU126 £1.60*	OC72 22p	2N3703 19p*
AF118 50p	BD136 39p	BY206 15p*	OC84 14p	2N3704 18p*
AF139 33p	BD137 48p	BY207 29p*	SC40A 73p	2N3705 18p*
AF239 37p	BD138 48p	BYX36-300	SC40B 81p	2N3706 10p*
BC107 14p	BD139 8p	BYX36-600	SC40F 98p	2N3707 10p*
BC107B 16p	BD181 84p	BYX36-600	SC41A 85p	2N3714 £1.05
BC108 13p	BD182 82p	BYX36-900	SC41B 85p	2N3715 £1.15
BC109 14p	BD183 97p	BYX36-1200	SC41D 70p	2N3716 £1.25
BC109C 16p	BD232 80p*	BYX38-	SC41F 85p	2N3772 £1.60
BC117 19p*	BD233 45p*	300	ST2 29p	2N3773 £2.10
BC125 18p*	BD237 55p*	BYX38-	TIP29A 44p	2N3819 28p*
BC126 20p*	BD238 60p*	300	TIP30A 32p	2N3904 18p*
BC141 28p	BD184 £1.20	BYX38-	TIP31A 54p	2N3906 16p*
BC142 23p	BDY20 80p	600	TIP32A 64p	2N4124 14p*
BC143 23p	BDY38 60p	BYX38-	TIP34 £1.85	2N4290 12p*
BC144 38p	BDY60 64p	900	TIP41A 68p	2N4348 £1.20
BC146 9p*	BDY61 65p	BYX38-	TIP42A 72p	2N4870 35p*
BC148 9p*	BDY62 55p	1200	IN2069 14p	2N4871 35p*
BC152 9p*	BF178 28p	BZX61 series	IN2070 16p*	2N4919 70p*
BC152 25p*	BF179 36p	zeners 20p	IN4001 4p*	2N4920 50p*
BC153 18p*	BF194 18p*	BZX83 or	IN4002 5p*	2N4922 50p*
BC157 9p*	BF195 19p*	zeners 11p*	IN4003 6p*	2N4923 60p*
BC158 9p*	BF196 12p*	C106A 40p	IN4004 7p*	2N5080 20p*
BC159 9p*	BF197 12p*	C106B 45p	IN4005 8p*	2N5081 23p*
BC160 32p	BF224J 18p*	C106D 50p	IN4006 9p*	2N5082 27p*
BC161 38p	BF244 17p*	C106F 35p	IN4007 19p*	2N5084 30p*
BC168B 9p*	BF257 30p	CRS1-05 25p	2N696 14p	2N5496 66p
BC182 11p*	BF258 35p			
BC182L 11p*				

## DIGITAL DISPLAYS & LED'S

DL704 99p	DL747 1.75	2 RED LED ONLY 13p
DL707 99p	DL750 1.75	GREEN CLEAR 13p

## THYRISTORS

	8A (TO92)	1A (TO5)	3A (C106 type)	6A (TO220)	8A (TO220)	10A (TO220)
50	28	25	35	41	42	47
100	25	25	40	47	48	54
200	27	35	45	58	60	68
400	30	40	50	67	68	98
600		65	70	1.09	1.10	1.26

## TRIACS (PLASTIC TO-220 PKG, ISOLATED TAB)

	4A		6.5A		8.5A		10A		15A	
	(a)	(b)	(a)	(b)	(a)	(b)	(a)	(b)	(a)	(b)
100 V	0.80	0.60	0.70	0.70	0.70	0.70	0.83	0.83	1.01	1.01
200 V	0.84	0.84	0.75	0.75	0.87	0.87	0.87	0.87	1.17	1.17
400 V	0.77	0.70	0.80	0.83	0.97	1.01	1.13	1.10	1.70	1.74
600 V	0.96	0.99	0.87	1.01	1.21	1.26	1.42	1.50	2.11	2.17

N.B. Triacs without internal trigger diac are priced under column (a). Triacs with internal trigger diac are priced under column (b). When ordering please indicate clearly the type required.

## 74 TTL mixed prices

	1-24	25-99	100+	1-24	25-99	100+
7400 14p	12p	10p	7445 85p	71p	57p	7492 57p
7401 14p	12p	10p	7447 81p	75p	65p	7493 45p
7402 14p	12p	10p	7448 75p	62p	50p	7495 67p
7403 15p	12p	10p	7447A 85p	83p	67p	74100 £1.08
7404 16p	13p	11p	7470 30p	25p	20p	74107 35p
7405 18p	13p	11p	7472 25p	21p	17p	74121 34p
7409 18p	13p	11p	7473 30p	25p	20p	74122 47p
7410 18p	13p	11p	7474 32p	28p	21p	74141 78p
7413 28p	24p	20p	7475 47p	39p	31p	74145 68p
7417 27p	22p	20p	7476 32p	26p	21p	74154 £1.82
7420 18p	13p	11p	7482 75p	62p	50p	74174 £1.00
7427 27p	22p	18p	7485 £1.30	£1.09	87p	74180 £1.04
7430 18p	13p	11p	7486 32p	26p	21p	74181 £3.20
7432 27p	22p	18p	7489 £2.92	£2.80	£2.10	74192 £1.35
7437 27p	22p	18p	7490 48p	46p	32p	74193 £1.35
7441 75p	62p	50p	7491 65p	55p	45p	74196 £1.64
7442 65p	55p	43p				74196 £1.64

## LINEAR IC'S

301A 8 pin DIL	35p	3800 14 pin DIL	70p	565 14 pin DIL	£2.00*
307	55p	709 8/14 pin DIL	35p	566 8 pin DIL	£1.50*
309K	1.80	741 8/14 pin DIL	28p	567 8 pin DIL	£2.00*
380 14 pin DIL	90p	748 8 pin DIL	38p	CA3046 14 pin DIL	50p
381 14 pin DIL	1.60*	555 8 pin DIL	45p	CA3045	85p

Matching charge 20p per pair, P & P 20p—Overseas 80p.

## NATIONAL CLOCK CHIPS

MM5314	£3.75	MM 5316	£5.25
--------	-------	---------	-------

(Basic clock chip giving 6 digit display)  
(Sophisticated device including alarm, similar to CT 7001)

HIGHAM MEAD, CHESHAM, BUCKS. Tel. (02405) 75151

VAT—Please add 8% except items marked \* which are 25%

# FEBRUARY ISSUE

# INCLUDES

# FREE

# RADIO & ELECTRONICS CONSTRUCTOR

## WALL CHART—DESIGN DATA TABLES SAVE TIRESOME CALCULATIONS

The Design Data Tables list both capacitive and inductive reactances at radio and audio frequencies. Also given are the resistance and capacitor values required in symmetric multivibrators running at audio frequencies, sinusoidal a.c. peak, average and r.m.s. values, decibel ratios up to 100dB, maximum potentiometer currents and information on copper wire gauges.

### SPECIAL FEATURE

### 4-CHANNEL STEREO MIXER

A comprehensive design which allows four separate stereo signals to be combined at any required micing level.



## ON SALE NOW

## PRICE 35p

The

\* A Complete Kit \*  
or fully built.

# 'MISTRAL' Digital Clock



Kit £12.50 (Incl)

Built £18.00.

- ◊ Pleasant green display ◊ 24 Hour readout
- ◊ Silent Synchronous Accuracy ◊ Fully electronic
- ◊ Pulsating colon ◊ Push button setting
- ◊ Building time 1Hr ◊ Attractive acrylic case
- ◊ Easy to follow instructions ◊ Size 10.5 x 5.7 x 8cm
- ◊ Ready drilled PCB to accept components

Exetron Time Ltd. offer this unique transformerless design at a substantial saving on retail price. The kit is complete less mains lead - all you require is a soldering iron, solder, and screw driver to assemble your own digital clock.



**EXETRON (Dept ETI)**  
Regal House,  
Penhill Road,  
LANCING, Sussex.

Payment : CWO, Cheque, Access,  
Barclaycard. (Quote Number)

# New Course in Digital Design

Understand the latest developments in calculators, computers, watches, telephones, television, automotive instrumentation . . . .


Each of the 6 volumes of this self-instruction course measures 11¼" x 8¼" and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers.

After completing this course you will have broadened your career prospects and considerably increased your fundamental understanding of the changing technological world around you.
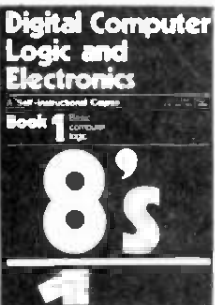
## Design of Digital Systems

A Self-Instruction Course in 6 Volumes

- 1 Computer Arithmetic
- 2 Boolean Logic
- 3 Arithmetic Circuits
- 4 Memories & Counters
- 5 Calculator Design
- 6 Computer Architecture



**Digital Computer Logic and Electronics**  
Book 1

8's

**£3.95** plus 50p p&p


Design of Digital Systems contains over twice as much information in each volume as the simpler course, Digital Computer Logic and Electronics. All the information in the simpler course is covered as part of the first volumes of Design of Digital Systems which, as you can see from its contents, also covers many more advanced topics.

Also available — a more elementary course assuming no prior knowledge except simple arithmetic.

In 4 volumes:

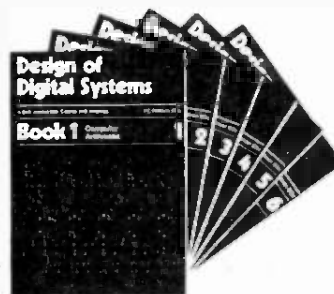1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flip flops and Registers

**Offer.** Order this together with Design of Digital Systems for the bargain price of £9.25, plus 50p, p&p.



£5.95

plus 50p packing and surface post anywhere in the world (VAT zero rated). Payments may be made in foreign currencies. Quantity discounts are available on request.

**Designer Manager Enthusiast Scientist Engineer Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

### Guarantee — no risk to you

If you are not entirely satisfied with Design of Digital Systems or Digital Computer Logic and Electronics, you may return them to us and your money will be refunded in full, no questions asked.

To: Cambridge Learning Enterprises,  
FREEPOST, St. Ives, Huntingdon, Cambs PE17 4BR

\*Please send me . . . . . set(s) of Design of Digital Systems at £6.45 each, p&p included

\*or . . . . . set(s) of Digital Computer Logic and Electronics at £4.45 each, p&p included

\*or . . . . . combined set(s) at £9.75 each, p&p included

Name.....

Address.....

.....

.....

\*delete as applicable. ETI 3

No need to use a stamp—just print FREEPOST on the envelope.

# MINI-ADS

FOR DETAILS ON ADVERTISING IN  
MINIADS, OR ELSEWHERE IN ETI,  
CONTACT BOB EVANS, 01-730 8282

## PRECISION POLYCARBONATE CAPACITORS

All High Stability—Extremely Low Leakage

440V	RANGE	DIMENSIONS (mm)	PRICE EACH	12V Range	2	3	5
0.12F	27	12.7	51p	0.47F	87p	50p	43p
0.22F	33	16	64p	1.0uF	82p	82p	52p
0.25F	33	16	67p	2.2uF	96p	75p	61p
0.47F	33	19	80p	4.7uF	£1.82	£1.13	84p
0.5uF	33	19	87p	16.8uF	£1.86	£1.38	£1.13
0.68F	50.8	19	83p	10uF	£2.40	£1.85	£1.64
1.0uF	50.8	19	£1.03	15uF	£3.22	£2.70	£2.24
2.0uF	50.8	25.4	£1.44	22uF	£4.28	£3.68	£3.06

**TANTALUM BEAD CAPACITORS**—Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8, 10uF at 15V/25V or 35V; 10uF at 16V/20V or 25V; 22.0uF at 6V or 10V; 33.0uF at 6V or 10V; 47.0uF at 3V or 6V; 100.0uF at 3V. ALL at 10p each, 10 for 95p, 50 for £4.

**TRANSISTORS & I.C.'s**

AC125	14p	BC268A/384	10p	OC71	12p
AC176	16p	*BC547/558A	12p	*2N2926G	12p
AD149	40p	BCY72	12p	*2N2926D	11p
AF178	30p	BD131/132	30p	*2N2928Y	11p
AF238	30p	BF115/167	25p	2N3054	65p
BC107/8/9	9p	BF173	9p	2N3055	50p
*BC114	12p	BF178	25p	2N3702/	
*BC147/8/9	10p	BF184	22p	3704	11p
*BC153/154	12p	*BF194/195	12p	*TIP30A	52p
*BC157/8/9	12p	*BF198/197	12p	TIP31A	50p
BC177	16p	BF200	27p	TIP32A	64p
*BC182/183L	11p	*BF262/263	90p	TIP205S	50p
*BC183/183L	11p	BFY50/51/52	20p	*MPU31	40p
*BC184/184L	12p	BFX84/86/88	20p	NE555	61p
*BC212/212L	14p	BFX85	28p	741C	32p
*BC213/213L	11p	BR101	41p	2N414	£1.15
*BC214/214L	11p	CE1872	25p	SNT6013ND	£1.30
BC267	12p	OC44/OC45	14p		

**POPULAR DIODES**—1N914 6p, 8 for 45p, 18 for 90p; 1N916 6p, 6 for 45p, 12 for 90p; 1S44 Sp, 11 for 50p, 24 for £1.00; 1N4148 Sp, 6 for 27p, 12 for 40p; 1N4001 50p; 002 6p; 003 8p; 004 7p; 006 8p; 007 8p.

**LOW PRICE ZENER DIODES**—400mW, Tol. ±5% at 5mA. Values available: 3V, 3.3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 13.5V, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V. All at 7p each; 5 for 30p; 10 for 65p. SPECIAL OFFER: 100 Zeners for £8.00.

**\*RESISTORS**—High stability, low noise carbon film 5% ±W at 40°C, ±W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ (1/20 resistors) ALL at 1p each, 8p for 10 of any one value, 78p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (1/20 resistors) £5.

**SILICON PLASTIC RECTIFIERS**—1.5 amp, brand new wire ended DO27, 100 P.I.V. 7p (4 for 26p), 400 P.I.V. 9p (4 for 38p).

**BRIDGE RECTIFIERS**—2 1/2 amp, 200V 40p, 350V 45p, 600V 55p.

**\*SUBMINIATURE VERTICAL PRESETS**—0.1Ω only, ALL at 5p each; 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1kΩ, 2.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 68kΩ, 100kΩ, 250kΩ, 680kΩ, 1MΩ, 2.5MΩ, 5MΩ.

PLEASE ADD 15p POST AND PACKING ON ALL ORDERS BELOW £5. ALL EXPORT ORDERS ADD COST OF SEA/AIR MAIL.

PLEASE ADD 8% VAT to all items except those marked with \* which are 25%.

Send S.A.E. for lists of additional in-stock items  
Wholesale price lists available to bona fide companies

### MARCO TRADING

(Dept. D3)

The Old School, Edstaston, Nr. Wem, Shropshire  
Tel. Whixall (Shropshire) (STD 094872) 464/5.  
(Prox. Minicini Trading Ltd.)

GLASS FIBRE P.C.B.s. Send 1.1 master and 30p per board plus 7p per square inch tinned or plus 9p per square inch drilled and tinned. Discount for quantity. PROTO DESIGN, 4 Highcliffe Way, Wickford, Essex.

### BARGAIN PRICE COMPONENTS

No extras

10 BC1831 Type T09275p	MJE 3055, npn	70p
10 BC213L Type-	ZN414 IC Radio, ea	£1.36
T092	Fonclen IC	£6.85
10 BC108 Type-T018 75p	TTL, 7400/1/2/3/4	17p
10 BC262 Type-T018 75p	IN4001 50V 1A ea	6p
IC Socket Pins 100 @ 75p	IN4002 100V1A ea	7p
7-2N2928 Mixed Gain 75p	IN4006 800V1A ea	13p
5 BC107 New marked 75p	IN4148 Signal Diode	6p
6 Led's TIP 209	75p	

Satisfaction guaranteed, s.a.e. for lists  
All enquiries welcome—Overseas deduct 8% VAT  
RELTRAN LTD. (Dept. ET),  
P.O. Box 18, Camberley, Surrey

**RESPONSIBLE ELECTRONICS ENTHUSIAST** urgently wanted for trouble-shooting and help with production.—Space-Age Electronics 203 1132.

**SCOOP!** 10 mfd/12V 10/20p. 100/£1. 10mfd/70V 22/mfd/50V 10/25p. 100/£1.25. 100mfd/16V 1000mfd/6V 10/30p. 100/£1.50. 1N4002/4p. 1N4004/5p. 1N4007/6p. 1N914/4p. 1N4148/4p. BRIDGES 1A/200V 2/50p. 2A/200V 2/65p. TRANSISTORS, Plastic BC107/8/9 10p. ZTX300/500 14p. ZTX304/504 22p. TIP3055/45p. TIP2955/64p. METAL CAN BC107/8/9 12p. ZN3055/73p. LEDs W/Clips TIL209/Red 16p. Green, Orange, Yellow, 21p. I.C.s 8 pin/741 25p. 555/49p. P&P/20p. AUDIO-OPTICS, 19 Middleway, Chinnor, Oxon.

**LOW-COST I.C. MOUNTING** for any size DIL package. 100 Soldercon sockets 60p. 7 and 8 hole plastic supports 5p pair. Quantity rates. SAE details and sample Trial pack 60p. (P & P, 10p/order). P.K.G. ELECTRONICS, Oak Lodge, Tansley, Derbyshire DE4 5FE.

### LED S

	0 125	0 2	INTRA RED
RED	15p	10p	550uW
G/Y	27p	33p	Actual lead 49p
OR	27p	33p	1.5mW £1.10
panel clip			15V 7815 all
			6mW £1.55
			ORP12 55p

### OPTO-ISOLATORS

IL4 1.5kV, 150kHz	£1	SCRs	50V	100V	400V
4350 2.5kV 5MHz	£2.25	1051A	25p	27p	46p
		1066 3A	27p	35p	50p
		TRiac T05 2A	400V	80p	

Order free with all OPTO

AC125/67/815p	2N2926(G)	12p	VOLTAGE REGS.
AD161/162 40p	2N3053	15p	5V 7805 Plastic
AF117 20p	2N3054	45p	12V 7812 1 Amp
AF124/5/6 7	2N3055	41p	15V 7815 all
BC107/8/9 9p	2N3702/3/4 12p	18V 7818 £1.50	723 DIP14 50p
BC109C 12p	2N3903/4/5/6	16p	
BC147/8/9 10p	2N2646	35p	BRIDGE RECTS.
BC157 8 9 11p	MPF102	40p	2A 50V 30p
BC167/8/9 11p	2N3819	25p	2A 100V 30p
BC169C 12p	2N3823	30p	2A 200V 41p
BC177/8/9 9p			2A 400V 40p
BC182/2/3/4/11p	8R100 Diac	21p	
BC186/7 30p	IN914	3p	ZENERS 6Z8B
BC212/3/4/12p	IN4001	5p	2.7 33V 9p
BCY70/71/72/13p	IN4002/3	6p	
BF194/5 12p	IN 4004/5	7p	NE555V 60p
BF196/7 14p	IN4006/7	8p	NE555 £1.10
BFY50/51 16p	IN4148	4p	LM380 £1.00
BFZ29 30p	OA47	6p	2N414 £1.10
BFZ84 24p	OA70 OA79	8p	7400 £1.6p
BSX19/20 15p	OA81 OA90	7p	
OC71 10p	OA91 OA95	6p	D.I.L. SOCKETS
2N706 10p	OA200	6p	8-pin 12p
2N1711 20p	OA202	7p	14-pin 13p
2N219 20p			16-pin 16p
2N2904/5/6/7 16p	OP, AMPs		Mica + bushes
2N2904/5/6A18p	709 all	25p	TO3 TO66 5p
2N2926(R) 7p	741 8-pin	28p	Dialo Pen 70p
	748 D.I.L.	36p	

PRICES INCLUSIVE - 15p P & P (1st class)

ISLAND DEVICES, P.O. Box 11, Margate, Kent

## P.C.B.s FOR E.T.I. PROJECTS

Active Crossover	ETI 433A	86p
Active Crossover	ETI 433B	86p
Logic Probe	ETI 120	35p
Logic Pulser	ETI 121	35p
Logic Tester	ETI 122	£1.85
50+50w Power Module	ETI 422	£3.00
Simple CMOS Tester	ETI 123a	70p
Simple CMOS Tester	ETI 123b	78p
Tone Burst Generator	ETI 124	83p
Exposure Meter	ETI 951	35p

All boards made in 1/16" Fibre Glass.  
Price includes drilling, tinning and postage.  
New projects available at £1.25 per sq. cm. for single sided or £1.5 per sq. cm. double sided (min. 35p) Prototype boards made to your requirements. Send s.a.e. for quote or full list of boards available.

**HARDWARE PACK** 6BA x 1/2" (RH) bolts, nuts, washers, 10p off each 20p inc. postage. COMPONENT PACKS for above p.c.b.s. Send s.a.e. for list.

Mail orders to **D.B.M. Products, Unit 14, Southern Road, Aylesbury, Bucks.**

**UFO CHARTS**—Wave Prediction 56p; Daily Flight Pattern 50p; TV Detection 66p; Propulsion Theory 57p; "Anti-Gravity" 57p; Map 52p; Circuits; 7-10 Digit Programmable Clock; Crystal Radiation Counter £1; Sighting Recorder 55p; 22-Range Multiferm Digital £1.05. R. & E. Highlands, Needham Market, Suffolk.

### CABINET FITTINGS

for Stage Loudspeakers and Amplifier Cabs.

Frictcloths, Coverings, Recess Handles, Strap Handles, Feet, Castors, Locks and Hinges, Corners, Trim, Speaker Bolts, etc., etc.

Send 2 x 8 1/2p Stamps for samples and list

### ADAM HALL (E.T. SUPPLIES)

Unit Q, Starline Works, Grainger Road  
Southend-on-Sea, Essex

## Epoxy-Glass PCBs

Typical prices INCLUSIVE of VAT & post!

50+50w Power Module	ETI 422	Jan 76	270p
Active Crossover 2 way	ETI 433A	Dec 75	90p
Active Crossover 3 way	ETI 433B	Dec 75	90p
4-Channel Stereo Preamp	ETI 420B	T.P.2	100p
3600 Synthesizer Amp Board	ETI 601P	June 75	120p
3600 Synthesizer VC Filter	ETI 601R	July 75	120p
CMOS Tester	ETI 123A	Feb. 76	90p
CMOS Tester	ETI 123B	Feb. 75	90p
100w Guitar Amplifier	ETI 413	T.P.1	140p
Plus Two Amplifier	ETI 420A	T.P.2	80p
Plus Two Power Supply	ETI 423	T.P.2	80p

Send 10p for full lists of PCBs and KITS for all E.T.I. and many other published Project PLUS low cost COMPONENTS

**NEW BURGLAR ALARM KIT** complete with Cass and Five Sensors KIT Price £16.00 Assembled £20.00

TTL			
7400	11p	7474	28p
7401	11p	7493	37p
7410	11p		
7416	20p	<b>LINEARS</b>	
7420	11p	CA 3046	50p
7430	11p	NE 555	50p
7437	11p	µA 741	27p
7440	11p	8C107, 108, 109	9p

**SPECIAL OFFERS**

Miniature glass encapsulated REED SWITCHES—10 for 50p  
Solid TANTALUM BEAD Capacitors 2.2uF, 47uF only—10p  
Glass-Tip Oxide Film Resistors 22K, 33K, 39K—2p  
Bulk offer 33K only—50—75p—100—120p

Mail Order Only—C.W.D.—P&P 15p—Prices VAT INCLUDED

### R.F. EQUIPMENT SPARES Ltd

3, Lacy Close WIMBORNE Dorset

## PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware, Aluminium sheet and sections, Printed circuit boards, top quality for individual designs.

Popular E.T.I. boards always in stock. Prompt service.

Send 15p for catalogue.

### RAMAR CONSTRUCTOR SERVICES

MASONS ROAD  
STRATFORD-ON-AVON  
WARWICKS. Tel. 4879



## INDEX TO ADVERTISERS

Ambit ..... p.28  
 Andromeda Electronics .. p.13  
 B.H. Components .. Miniads  
 B.I.E.T. .... p.82  
 Bi-Pak. .... pp.4 & 5  
 Bi-Pre-Pak. .... p.83  
 B.N.R.S. .... p.71  
 Bywood ..... p.16  
 Cambridge Learning .. p.79  
 C.D.I. .... Miniads  
 Chiltmead. .... p.22  
 Chromasonics ..... p.2  
 Crofton Electronics. .... p.52  
 E.D.A. .... p.27  
 Electrovalue ..... p.28  
 Exetron. .... p.78  
 Greenbank ..... Miniads  
 Heathkit ..... p.29  
 Henry's Radio. .... p.9

Imtech Products ..... p.28  
 Island Devices ..... Miniads  
 Kinnie Components ..... p.75  
 Kramer & Co. .... p.75  
 Lynx Electronics ..... p.77  
 Maplin Electronics ..... p.84  
 Marco Trading ..... Miniads  
 Marshall's. .... p.44  
 Metac. .... p.9  
 Minikits ..... p.76  
 Radio Constructor. .... p.77  
 Ramar. .... Miniads  
 R.F. Equipment. .... Miniads  
 Sabtronic ..... p.21 & p.50  
 Sinclair ..... p.36 & p.37  
 Sintel ..... p.27  
 Technomatic. .... p.52  
 Videomaster ..... p.51  
 Wilmslow Audio. .... p.76

## FIRST-CLASS VIDEO ENGINEER

Experienced in VCRs, U-matics, 2" machines and colour monitors.

Bench work.

For initial interview phone 01-580 2283.

"HEDDON VALLEY ELECTRONICS" free catalogue and order forms now available. Many popular semiconductors, resistors, condensers, etc., all at competitive prices. Prompt attention on all orders regardless of sizes, all components guaranteed. A must for the home constructor, for the price of a s.a.e. HEDDON VALLEY ELECTRONICS, Bumpsley Mill, Parracombe, Barnstaple, North Devon.

### LOOKING FOR AN ANSWER?

Here's the solution, for those who are still struggling with the Cannibals and Missionaries problem - C means either of the non-rowing cannibals, C2 means the cannibal who can row. M means any missionary.


- |                    |                    |
|--------------------|--------------------|
| 1. C & C2 go over  | 8. M & C come back |
| 2. C2 comes back   | 9. M & M go over   |
| 3. C & C2 go over  | 10. C2 comes back  |
| 4. C2 comes back   | 11. C & C2 go over |
| 5. M & M go over   | 12. C2 comes back  |
| 6. M & C come back | 13. C & C2 go over |
| 7. M & C2 go over  |                    |

### THE SCIENTIFIC WIRE CO.

Copper - Nickel Chrome - Eureka - Manganin Wires  
 Enamelled - Silk - Cotton - Tinned Coverings

No minimum charges or quantities  
 Trade and Export enquiries welcome  
 S.A.E. Brings List

P.O. BOX 30, LONDON, E4 9BW

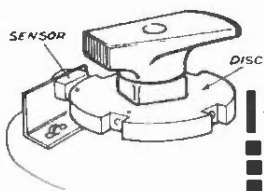

## Capacitor Discharge IGNITION

- MAXIMUM PERFORMANCE
- MAXIMUM ECONOMY
- EASY COLD START

### SYSTEM I

Professional photoelectric ignition using L.E.D. light source and reflective disc. This machined aluminium disc gives a timing accuracy far superior to other methods and is simple to fit. Unit housed in diecast box 4 1/2" x 3 1/2" x 2 1/4" Price £18.80 (Kit £16.80) State car/model/measurement across cam lobes.

### SYSTEM II

Contact breaker model as above less sensor. Price £12.80 (Kit £10.80) M/C Twin unit Price £15.00. S.A.E. for descriptive leaflet - ALL UNITS IN STOCK. Mail orders to CDI Electronic Systems Ltd, 275 Vale Road, Ash Vale, Aldershot, Hants. Demonstration/Callers to Hillside Motors, 292 Carshalton Road, Carshalton, Surrey, telephone 01-642 9973.

**CJL**

CJL LTD. P.O. BOX 34, CANTERBURY, CT1 1YT

ALL PRICES INCLUDE P&P AND V.A.T.

<b>ANTEX SOLDERING IRONS</b> (with slide on & off bits)	ST3 Stands-for all models	£1.10
15W 'C' miniature irons	SOLDER in 1lb dispenser	£0.45
3/32", 1/8", 3/16" bits-each	<b>WIRE STRIPPER &amp; CUTTER</b>	£0.85
£1.10	HAND DRILLS Leytool precision,	
'C' Elements	compact, 5/16" chuck	£3.99
18W 'G' miniature irons	<b>AERIALS</b> Extend 15-120cm	£1.50
3/32", 1/8", 3/16" bits-each	<b>CASSETTE</b> 'Head Demagnetisers'	
£1.35	Shaped pole-saves time	£3.65
'G' Elements	<b>EARPHONES</b> Stethoscope	£1.25
15W CCN Low leakage irons	<b>MICROPHONES</b> Dynamic	£2.15
3/32", 1/8", 3/16" bits-each	<b>PRINTED CIRCUIT KITS-All</b>	
£1.50	items for producing p.c.'s	£3.99
25W X25 Low leakage irons	<b>SIGNAL INJECTOR</b> -Audio through	
3/32", 1/8", 3/16" bits-each	video signals, self contained	£4.25
£1.15	<b>SPEAKERS</b> -75mm dia. 8Ω	£1.00
'X25' Elements		
'SK1', 'SK2' Soldering Kits		£3.85

## Greenbank Electronics

### FREE!

Data and suggested circuits for AY-5-1224 and MK 50253 clock chips, details of PCB's and component kits for AY-5-1224, data sheets for LED 0.3" and 0.6" displays.

### NEW!

PCB TO SUIT AY-5-1224 clock chip ..... 95p

### 4 DIGIT KITS

Kit includes: PCB, AY-5-1224 chip, 4 LED digits, transistors, diodes, resistors, capacitors, solder pins (success guaranteed), with 0.3" digits £9.95 (0.6" high digit version also available).

### CLOCK CHIPS

AY-5-1224 4 digit 12/24 hour ..... £3.66  
 MK 50253 4/6 digit alarm clock ..... £5.50

### LED DISPLAYS (ECONOMY TYPES)

DL-704E 0.3" common cathode ..... 85p  
 DL-747E 0.6" common anode ..... £1.70

Add 8% VAT to all prices, post, etc. 10p + VAT per order

**GREENBANK ELECTRONICS (Dept. T12E)**  
 94 New Chester Road, New Ferry  
 Wirral, Merseyside L62 5AG  
 Tel: 051-645 3391

HAVE YOU GOT YOURS?

CATALOGUE NO. 4 FULLY ILLUSTRATED

20p

COMPLETE WITH DISCOUNT VOUCHERS WORTH 20p

- ★ DISCOUNTS
- ★ ALL NEW STOCK
- ★ SATISFACTION GUARANTEE
- ★ DEPENDABLE SERVICE

**B H COMPONENT FACTORS LTD.**

LEIGHTON ELECTRONICS CENTRE, 59 NORTH ST., LEIGHTON BUZZARD, BEDS. LU7 7EG. Tel. (05253) 2316.

# ENGINEERS FREE

YOURSELF FOR A  
**BETTER JOB WITH MORE PAY!**



Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow **GUIDE TO SUCCESS** should be read by every ambitious engineer. Send for this helpful 76-page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.

**CHOOSE A BRAND NEW FUTURE HERE**

**CUT OUT THIS COUPON**

Tick or state subject of interest. Post to address below.

### ELECTRICAL & ELECTRONICS

- Practical Radio & Electronics (with Kit)
- Electronic Engineering Certificate
- General Elect. Eng. Certificate
- C & G Elect. Installations
- Elect. Install. & Work

- C & G Elect. Technicians

### RADIO AND TELE-COMMUNICATIONS

- Colour TV Servicing
- C & G Telecoms. Technician's Cert.
- C & G Radio, TV & Electronics Mech. Certificate
- Radio & TV Engineering Course
- Radio, Servicing & Repairs
- Radio Amateur's Exam.

### AUTO & AERO

- Motor Mechanics
- C & G Motor V. Mechanics
- General Auto Engineering
- A.M.I.M.I.
- Air Registration Board Certs.
- MAA/IMI Dip.

### CONSTRUCTIONAL

- Heating Ventilating & Air Conditioning
- Architectural Draughtsmanship & Design
- L.I.O.B.
- Carpentry & Joinery
- Plumbing Technology
- General Building
- Painting & Decorating

### MECHANICAL

- A.M.S.E. (Mech.)
- General Mech. Eng.
- Inst. Engineers & Technicians
- Maintenance Engineering
- Welding

### MANAGEMENT & PRODUCTION

- Computer Programming
- Inst. of Cost & Management Accts.

### DRAUGHTSMANSHIP & DESIGN

- General Draughtsmanship
- A.M.I.E.D.
- Electrical Draughtsmanship



**G.C.E.**

-58 'O' & 'A' Level Subjects  
-over 10,000 Group Passes!

## Aldermaston College

Dept. TET 12 Reading RG7 4PF

also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5EJ. Tel. 01-628 2721.

NAME (Block Capitals)

ADDRESS

Postcode

Other subjects of interest

Age

Accredited by C.A.C.C.

Member of A.B.C.C

**HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**

# electronics today

INTERNATIONAL

# reader services

### SUBSCRIPTIONS

The annual subscription to ETI for UK readers is £5.00. The current rate for readers overseas is £5.50. Canadian subscription rate is \$10 per year. Send orders to ETI SUBS Dept. . . .

### BACK ISSUES

The cost of a back issue is 40p. Postage and packing costs an additional 15p for the first and 10p for each subsequent copy. Send orders to ETI BACK ISSUES Dept. . . . We cannot supply certain back issues (April, May, June, July, November and December 1972; January, February and November 1973; March, September and November 1974; January, June, August, September and November 1975).

### SPECIAL ISSUES

At present we have three Special Issues available: Top Projects 2, Electronics It's Easy (Parts 1 to 13), and International 4600 Synthesiser (published by Maplin). The prices are 75p, £1.20 and £1.50 respectively; postage and packing is an additional 15p per issue. Top Projects 3 is now sold out. Send orders to ETI SPECIALS Dept. . . .

### BINDERS

Binders, for up to 13 issues, are available for £2.00 including VAT and carriage. Send orders to ETI BINDERS DEPT. . . .

### BOOKS

ETI Book Service sells books to our readers by mail order. The prices advertised in the magazine include postage and packing. Send orders to ETI Book Service, 25 Court Close, Bray, Maidenhead, Berks.

### SPECIAL OFFERS

Normally special offers are open from the date of publication to the end of the month on the cover of the issue. Usually the filling of orders and the despatch of goods is handled by the company supplying the products. In this case queries should be addressed to the company and not to ETI.

### T-SHIRTS

ETI T-shirts are available in Large, Medium, or Small sizes. They are yellow cotton with black printing and cost £1.50 each. Send orders to ETI T-SHIRTS Dept. . . .

### PCBs

PCBs are available for our projects from companies advertising in the magazine, such as Ramar and Crdton, who do an excellent service.

### EDITORIAL QUERIES

Written queries can only be answered when accompanied by an SAE, and the reply can take up to three weeks. These must relate to recent articles and not involve ETI staff in any research. Mark your letter ETI QUERY . . . Telephone queries can only be answered when technical staff are free, and never before 4 pm.

### NON-FUNCTIONING PROJECTS

We cannot solve the problems faced by individual readers building our projects unless they are concerning interpretation of our articles. When we know of any error we print a correction as soon as possible at the end of News Digest. Any useful addenda to a project will be similarly dealt with. We cannot advise readers on modifications to our projects.

### CONTRIBUTIONS

Before submitting any material for publication contact the Editor who will advise on suitability (except for letters, news & Tech-Tips).

### NEWS DIGEST

We receive 20 times more news than we have space for. If you have an interesting item we will be pleased to consider it along with the rest. The statement must be brief and preferably accompanied by a large photograph.

### TECH-TIPS

We pay for items printed in this section: send ideas for submission to ETI TECH-TIPS . . . Drawings must be as clear as possible and the text should be typed or clearly written on alternate lines. Circuits must not have been previously published and must not be subject to copyright. We cannot answer queries on published Tech-Tips.

### LETTERS FOR PUBLICATION

We do not pay for letters published and we only print them if they are very interesting or important. They should be addressed to the Editor.

### MINI-AQS & CLASSIFIEDS

This is a pre-payment service - rates on application to ADVERTISING Dept., or phone Bob Evans on 01-730-7319.

**ADDRESS FOR ETI DEPARTMENTS—**

**36 EBURY ST, LONDON SWW 0LW**

**PLEASE MARK REVERSE OF EACH CHEQUE WITH NAME & ADDRESS AND ITEMS REQUIRED.**

**ALLOW 10 TO 14 DAYS FOR DELIVERY**



# Stirling Sound Products

FROM BI-PRE-PAK

BRAND NEW MODULES FROM THE DESIGN-BENCH OF A FOREMOST BRITISH DESIGNER AND EXCLUSIVE TO B-P-P

## BUILT FOR QUALITY

THE SS125 HIGH FIDELITY POWER AMPLIFIER

### OUTPUT

25 watts R.M.S. into 8Ω using 50V  
22 watts R.M.S. into 4Ω using 33V  
[Low Imp. not less than 4Ω]

### DISTORTION

Less than 0.05% at all power levels  
[from 10KHz to 10KHz]

### FREQUENCY RESPONSE

± 1dB 15 Hz to 30 KHz [4Ω]  
± 1dB 10KHz to 30 KHz [8Ω]

### HIGH Z INPUT

100 Kohms (40dB gain/100x)

### INPUT SENSITIVITY

150mV for 25W.R.M.O. out

### HEAT SINK

Heavy duty type.


built on

### SIZE

[Inc. 40w. built on heat sink]  
4 1/4 x 3" x 1/4" high [120 x 76 x 22 mm]

★ A masterpiece of value and reliability

Not only is this Stirling Sound's best audio amplifier yet; it rightfully qualifies as one of the best of its kind yet made available to constructors. Intended above all for high-fidelity, the characteristics of the SS.125 are such that it can be used in many other applications where dependability is the prime consideration. The SS.125 integrates well with other S.S. units as well as those of other manufacturers. Incorporates new circuitry using a complementary long-tailed pair input and full complementary output circuits to give standards of performance.

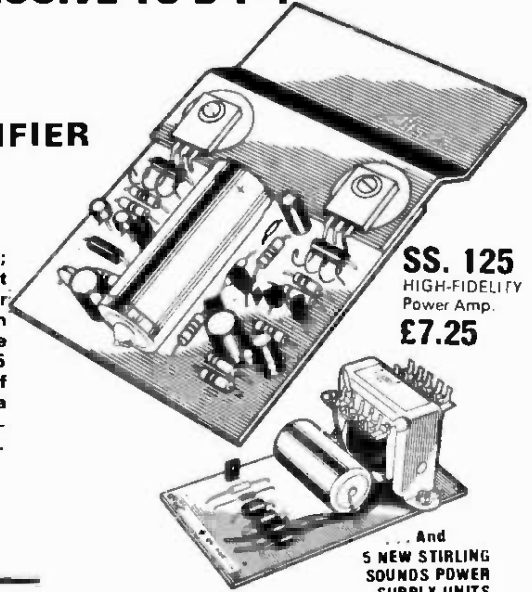

SS. 125  
HIGH-FIDELITY  
Power Amp.  
£7.25

And  
5 NEW STIRLING  
SOUND POWER  
SUPPLY UNITS

Robustly designed units in each of which is a stabilised take-off point to provide for tuner, pre-amp and control stages. Size — 5 1/4" x 3" x 2 1/2" high (P/P add 50p any model)

SS 312	12V/1A	£3.75*
SS 318	18V/1A	£4.15*
SS 324	24V/1A	£4.60*
SS 334	34V/2A	£5.20*
SS 345	45V/4A	£6.25*




Transformers for SS334 and SS345 are supplied with transformers separate from PCBs. Add 50p for P/P any model.

## MORE STIRLING SOUND MODULES

With easy to follow instructions
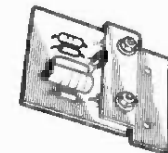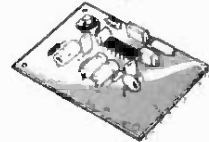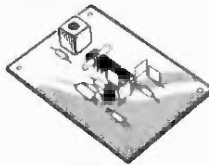
### F.M. TUNER UNITS

- SS.201 Tuner front end. Ganged, geared variable tuning. 88-108MHz. A.F.C. facility. **£5.00**
- SS.202 1 F amp A meter and/or A.F.C. can be connected (size 3" x 2") **£2.85**
- SS.203 Stereo decoder for use with SS.201 and 202 or any good F.M. tuner. A LED beacon may be attached (3" x 2") **£3.85**
- SS.105 5 watt amplifier to run from 12V (3 1/2" x 2" x 3/4") **£2.25**
- SS.110 Similar to SS.105 but more powerful giving 10W. into 4ohms **£2.75**
- SS.120 20 watt module when used with 34 volts into 4 **£3.00**
- SS.140 Delivers 40 watts R.M.S. into 4 ohms using a 45V/2A supply such as our SS.345 the power and quality of this unit are superb — two in bridge formation will give 80 watts R.M.S. into 8ohms. Size 4" x 3" x 3/4" **£3.75\***
- SS.100 Active tone control, stereo, ±15dB cut and boost with suitable network **£1.60**
- SS.101 Pre-amp for ceramic p.u., radio & tape with passive tone control details **£1.60**
- SS.102 Stereo pre-amp with R.I.A.A. equalisation, mag. p.u., tape and radio in. **£2.25**
- SS.300 Power Supply Stabiliser. Add this to your unbalanced supply to obtain a steady working voltage from 12 to 50V for your audio system, workbench etc. Money saving and very reliable **£3.25\***



### TERMS OF BUSINESS:

VAT at 25% must be added to total value of order except for items marked \* or (B%), when VAT is to be added at 8%. No VAT on overseas orders. POST & PACKING add 22p for UK orders unless marked otherwise. Minimum mail order acceptable — £1. Overseas orders, add £1 for postage. Any difference will be credited or charged. PRICES subject to alteration without notice. AVAILABILITY All items available at time of going to press when every effort is made to ensure correctness of information.

Order your Stirling Sound products from

# BI-PRE-PAK LTD

Co Reg No 820919

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.

TELEPHONE: SOUTHERN (0702)46344

FACTORY — SHOEBOURNESS, ESSEX

### A new Stirling Sound C.D.I. Unit for your car.

Even better than the original version, thousands of which are in use saving motorists appreciable time and money for petrol. Very easy to install. The Stirling Sound model incorporates switch for instant change to conventional ignition, instant adaption to pos or neg earth return anti-burglar immobilising switch, pre-set control for rev. limitation. There are no exposed parts, the unit, on p.c.b. being housed in strong enclosed metal box. With instructions and leads.

Size 7 1/2" x 4 1/4" x 2 1/2" ex. switches (193 x 117 x 54mm) (P/P — add 50p)

**BUILT & TESTED**  
KIT **£7.95**      **£10.50**

### A NEW X-HATCH GENERATOR

Operates at R.F. level

For colour and mono TV. Plugs into aerial socket of set. Operates without need for transmissions, 4 push-button operation. Runs on 4 self-contained penlite type batteries. Will fit into a large pocket. Strong plastic case. **BUILT £27.50\* KIT £25\***

### A USEFUL CATALOGUE — FREE

Send us a large S.A.E. with 10p stamp and we will send you the latest Bi-Pre Pack catalogue free by return. Packed with useful lines, it's a real money saver.

TO STIRLING SOUND (BI-PRE-PAK) LTD, 222 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO DDF

Please send

for which I enclose £

inc. V.A.T

NAME

ADDRESS

130 home

# More than just a catalogue!

## PROJECTS FOR YOU TO BUILD

4-digit clock, 6-digit clock, 10W high quality power amp., High quality stereo pre-amp., Stereo Tuner, F.M. Stereo decoder, etc., etc.

**CIRCUITS** ... Frequency Doublers, Oscillators, Timers, Voltmeters, Power Supplies, Amplifiers, Capacitance Multiplier, etc., etc.

Full details and pictures of our wide range of components, e.g. capacitors, cases, knobs, veroboards, edge connectors, plugs and sockets, lamps and lampholders, audio leads, adaptor plugs, rotary and slide potentiometers, presets, relays, resistors (even 1% types!), switches, interlocking pushbutton switches, pot cores, transformers, cable and wire, panel meters, nuts and bolts, tools, organ components, keyboards, L.E.D.'s, 7-segment displays, heatsinks, transistors, diodes, integrated circuits, etc., etc., etc.


Really good value for money at just 40p.



### The 3600 SYNTHESISER


The 3600 synthesiser includes the most popular features of the 4600 model, but is simpler. Faster to operate, it has a switch patching system rather than the matrix patchboard of the larger unit and is particularly suitable for live performance and portable use.

Please send S.A.E. for our price list.

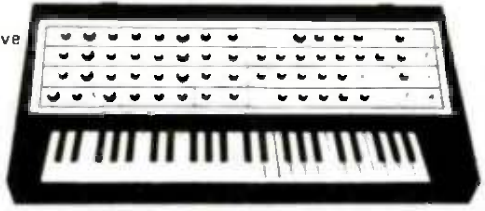
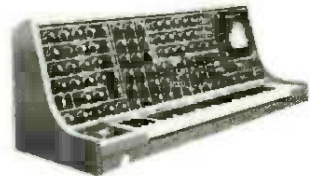
### The 4600 SYNTHESISER

We stock all the parts for this brilliantly designed synthesiser, including all the PCBs, metalwork and a drilled and printed front panel, giving a superb professional finish. Opinions of authority agree the ETI International Synthesiser is technically superior in most of today's models. Complete construction details in our booklet available now, price £1.50, or S.A.E. please for specification.



### GRAPHIC EQUALIZER

A really superior high quality stereo graphic equaliser as described in Jan. 1975 issue of ETI. We stock all parts (except woodwork) including all the metal work drilled and printed as required to suit our components and PCB's. S.A.E. for price list or complete reprint of article - price 15p.



### ELECTRONIC ORGAN

Build yourself an exciting Electronic Organ. Our leaflet MES51, price 15p, deals with the basic theory of electronic organs and describes the construction of a simple 49-note instrument with a single keyboard and a limited number of stops. Leaflet MES52, price 15p, describes the extension of the organ to two keyboards each with five voices and the extension by an octave of the organ's range. Solid-state switching and new footages along with a pedal board and a further extension of the organ's range are shown in leaflet MES53 priced at 35p (pre-publication price 15p.)



### NO MORE DOUBTS ABOUT PRICES

Now our prices are GUARANTEED (changes in VAT excluded) for two month periods. We'll tell you about price changes in advance for just 30p a year (refunded on purchases). If you already have our catalogue send us an s.a.e. and we'll send you our latest list of GUARANTEED prices. Send us 30p and we'll put you on our mailing list - you'll receive immediately our latest price list then every two months from the starting date shown on that list you'll receive details of our prices for the next GUARANTEED period before the prices are implemented! - plus details of any new lines, special offers, interesting projects - and coupons to spend on components to repay your 30p

NOTE: The price list is based on the Order Codes shown in our catalogue so an investment in our super catalogue is an essential first step.

Call in at our shop, 284 London Road, Westcliff-on-Sea, Essex. Please address all mail to



MAPLIN ELECTRONIC SUPPLIES  
P.O. Box 3 Rayleigh Essex SS6 8LR

I enclose Cheque/P.O. value \_\_\_\_\_ ETI  
For \_\_\_\_\_ copy/copies of your Catalogue  
Name \_\_\_\_\_  
Address \_\_\_\_\_

MAPLIN ELECTRONIC SUPPLIES P.O. Box 3 Rayleigh Essex SS6 8LR