

electronics today

INTERNATIONAL

ISSN. 0142-7229

DECEMBER 1980 £0.95

POLYPHONIC SYNTHESISER PROJECT



Build it for a fraction of the cost of commercial units!

FOUR Circuit design features inside

How the Universe began?

An Alarming Clock design

Audio Mixer project

...NEWS...PROJECTS...MICROPROCESSORS...AUDIO...

8K ON BOARD MEMORY!

5K RAM 3K ROM or 4K RAM, 4K ROM (link selectable) Kit supplied with 3K RAM, 3K ROM System expandable for up to 32K memory

2 KEYBOARDS!

56 Key alphanumeric keyboard for entering high level language plus 16 key Hex pad for easy entry of machine code

GRAPHICS!

64 character graphics option — includes transistor symbols! Only £18.20 extra!

MEMORY MAPPED

high resolution VDU circuitry using discrete TTL for extra flexibility Has its own 2K memory to give 32 lines for 64 characters

KANSAS CITY

low error rate tape interface.

2 MICROPROCESSORS

Z80 the powerful CPU with 158 instructions, including all 78 of the 8080, controls the MM57109 number cruncher Functions include +, -, *, /, squares, roots, logs, exponentials, trig functions, inverses etc. Range 10^{-9} to 9×10^{9} to 8 figures plus 2 exponent digits

EFFICIENT OPERATION

Why waste valuable memory on sub routines for numeric processing? The number cruncher handles everything internally!

RESIDENT BASIC

with extended mathematical capability. Only 2K memory used but more powerful than most 8K Basics!

1K MONITOR

resident in EPROM

SINGLE BOARD DESIGN

Even keyboards and power supply circuitry on the superb quality double sided plated through-hole PCB

PSI comp 80
Z80 Based powerful scientific computer design as published in WIRELESS WORLD



COMPLETE KIT NOW ONLY £225 + VAT

Cabinet size 19.0" x 15.7" x 3.3"

Television not included in price.

The kit for this outstandingly practical design by John Adams published in a series of articles in Wireless World really is complete. Included in the PSICOMP 80 scientific computer kit is a professionally finished cabinet, fibre-glass double sided, plated-through-hole printed circuit board, 2 keyboards PCB mounted for ease of construction, IC sockets, high reliability metal oxide resistors, power supply using custom designed toroidal transformer, 2K Basic and 1K monitor in EPROMS and, of course, wire, nuts, bolts, etc.

KIT ALSO AVAILABLE AS SEPARATE PACKS

For those customers who wish to spread their purchase or build a personalized system the kit is available as separate packs eg. PCB (16" x 12.5") £43.20. Pair of keyboards £24.80. Firmware in EPROMS £30.00. Toroidal transformer and power supply components £17.60. Cabinet (very rugged, made from steel, really beautifully finished) £26.50. P.S. Will greatly enhance any other single board computer including OHM SUPERBOARD for which it can be readily modified. Other packs listed in our FREE CATALOGUE.

PSI COMP 80 Memory Expansion System

Expansion up to 32K all inside the computer's own cabinet!

By carefully thought out engineering a mother board with buffers and its own power supply (powered by the computer's transformer) enables up to 3 8K RAM or 8K ROM boards to be fitted neatly inside the computer cabinet. Connections to the mother board from the main board expansion socket is made via a ribbon cable.

Mother board:

Fibre glass double sided plated through hole PCB 8 7/8" x 3 0/8" set of all components including all brackets, fixing parts and ribbon cable with socket to connect to expansion plug **£39.90**

8K Static RAM board

Fibre glass double sided plated through hole PCB 5 6/8" x 4 8/8" **£12.50**
Set of components including IC sockets, plug and socket but excluding RAMs **£11.20**
2114L RAM (16 required) **£5.00**
Complete set of board components 16 RAMS **£89.50**

8K ROM board

Fibre glass double sided plated through hole PCB 5 6/8" x 4 8/8" **£12.40**
Set of components including IC sockets, plug and socket but excluding ROMs **£10.70**
2708 ROM (8 required) **£6.00**
Complete set of board components 8 ROMs **£68.60**

★ ETI VOCODER ★



Panel size 9.0" x 5.25" Depth 12.2"

14 CHANNELS!
NOISE GENERATOR!
LED PPM METERS!
SLEW RATE CONTROL!

2 OSCILLATORS!
VOICED/UNVOICED DETECTOR!

COMPLETE KIT ONLY £195 + VAT

Kit includes FREE foot control and test oscillator!

Like all our kits the ETI VOCODER really is complete — fully finished metal work, professional quality components (all resistors 2% metal oxide), nuts, bolts, etc. — even a 13A plug! Kits also available as separate packs — See our Free Catalogue.

POWERTRAN

OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!
POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE
ANDOVER, HANTS SP10 3NM

ANDOVER
(STD 0264) 64455

PRICE STABILITY: Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until January 31st, 1981, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.
EXPORT ORDERS: No VAT. Postage charged at actual cost plus £1 handling and documentation.
U.K. ORDERS: Subject to 15% surcharge for VAT. No charge is made for carriage, or at current rate if changed.

SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.
SALES COUNTER: If you prefer to collect kit from the factory, call at Sales Counter. Open 9 a.m. - 12 noon, 1-4.30 p.m. Monday-Thursday.


MANY MORE KITS ON PAGE 8




Polyphonic synthesiser p.87



Balancing act p.19

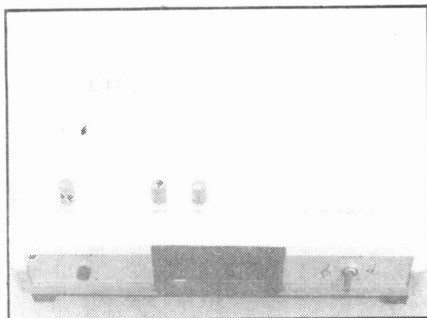

Modules and melodies p.33

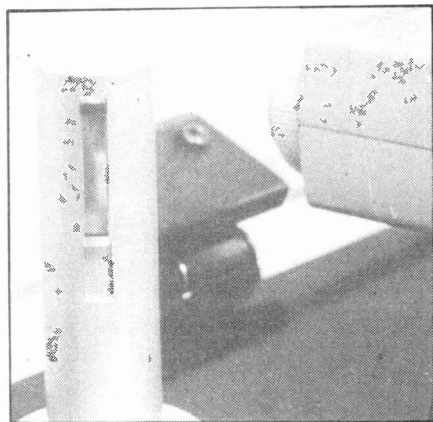

Pillar talk about hi-fi p.48

electronics today

DECEMBER 1980 VOL 9 NO 12 INTERNATIONAL

FEATURES

NEWS	11	Read all about it.
BANDPASS AND BEYOND	24	Switched capacitors and new IC filters
MICROBASICS	38	The ins and outs of hardware
AUDIOPHILE	48	Music to your ears (and hips)
TECH-TIPS	55	Over to you.
SPOT DESIGNS	63	And various other places
ASTROLOGUE	65	Watch this space
THE BIG BANG THEORY	69	Fifteen billion BC and all that
DESIGNER'S NOTEBOOK	79	VCO variations

PROJECTS

FOUR INPUT MIXER	19	Cheap combinations
MUSICAL ALARM CLOCK	32	Tunes help you wake more easily
SOUND BOARD	44	Invasion effects
MUSICAL DOORBELL	60	For visiting musicians?
BENCH AMPLIFIER	74	Versatile low-cost design
POLYSYNTH	87	A project of note(s)
FOIL PATTERNS	125	Keep on tracking

INFORMATION

NEXT MONTH'S ETI	17	Competition issue
NEXT MONTH'S CT	41	Largest issue ever
BREADBOARD '80	85	Come and say hello
BOOK SERVICE	111	Out technical library
ETIPRINTS	124	Rub 'em down

EDITORIAL AND ADVERTISEMENT OFFICE
 145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5

Ron Harris B.Sc. Editor
 Ian Graham B.Sc. Assistant Editor
 Tina Boylan Editorial Assistant
 Paul Wilson-Patterson Group Art Editor
 Paul Edwards Drawing Office Manager
 Ray Marston Project Editor
 Christopher Surgenor Group Advertisement Manager
 Steven Rowe Advertisement Manager
 Roy Perryment Advertisement Representative
 T.J. Connell Managing Director

OVERSEAS EDITIONS and their EDITORS
 AUSTRALIA - Roger Harrison
 CANADA - Halvor Moorshead
 GERMANY - Udo Wittig
 HOLLAND - Anton Kriegsman



Member of the
 Audit Bureau
 of Circulation



PUBLISHED BY Modmags Ltd, 145 Charing Cross Road, WC2
 DISTRIBUTED BY Argus Distribution Ltd. (British Isles)
 12-18 Paul Street, London
 Gordon & Gotch Ltd. (Overseas)
 PRINTED BY QB Limited, Colchester
 Covers printed by Alabaster Pressmore

Electronics Today is normally published on the first Friday in the month preceding cover date. © MODMAGS LTD 1980. All material is subject to worldwide copyright protection. All reasonable care is taken in the preparation of the magazine's contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press. Subscription Rates UK £10 including postage. Airmail and other rates upon application to ETI Subscriptions Service, PO Box 35, Bridge Street, Hemel Hempstead, Herts.



SIMPLY AHEAD
and staying there

The range grows bigger... better...

New Profile Amplifiers - Two New Series

MOSFET



CHOOSE AN I.L.P. MOSFET POWER AMP when it is advantageous to have a faster slew rate, lower distortion at higher frequencies, enhanced thermal stability, the ability to work with complex loads without difficulty and complete absence of cross-over distortion. I.L.P.'s exclusive encapsulation technique within fully adequate heatsinks has been taken a stage further with specially developed computer-verified 'New Profile' extrusions. These ensure optimum operating efficiency from our new MOSFETS, and are easier to mount. Connection is via five pins on the underside. **I.L.P. MOSFETS ARE IDENTICAL IN PERFORMANCE TO THE COSTLIEST AMPLIFIERS IN THIS EXCITING NEW CATEGORY BUT ARE ONLY A FRACTION OF PRICES CHARGED ELSEWHERE.**

Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
MOS120	60W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£25.88 + £3.88
MOS200	120W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£33.46 + £5.02


BIPOLAR

CHOOSE AN I.L.P. BIPOLAR POWER AMP where power and price are first consideration while maintaining optimum performance with hi-fi quality and wide choice of models. From domestic hi-fi to disco and P.A., for instrument amplification, there is an I.L.P. Bipolar to fill the bill, and as with our new Mosfets, we have encapsulated Bipolars within our New Profile extrusions with their computer-verified thermal efficiency and improved mounting shoulders. Connections are simple, via five pins on the underside and with our newest pre-amps and power supply units, it becomes easier than ever to have a system layout housed the way you want it.


Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
HY30	15W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£6.34 + 95p
HY60	30W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£7.24 + £1.09
HY120	60W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£15.20 + £2.28
HY200	120W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£18.44 + £2.77
HY400	240W into 4Ω	0.01%	15V/μs	5μs	100dB	£27.68 + £4.15

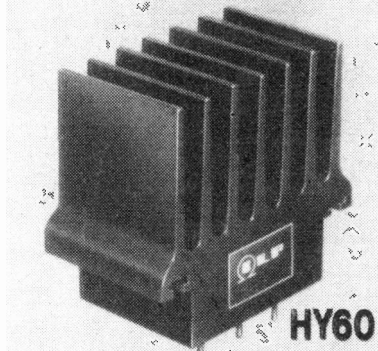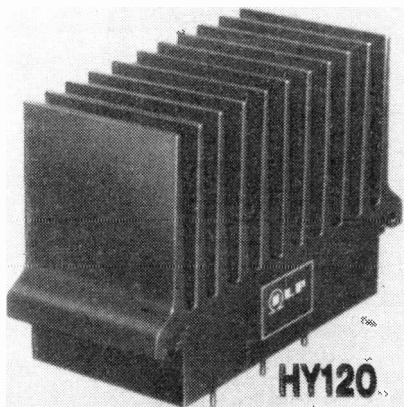

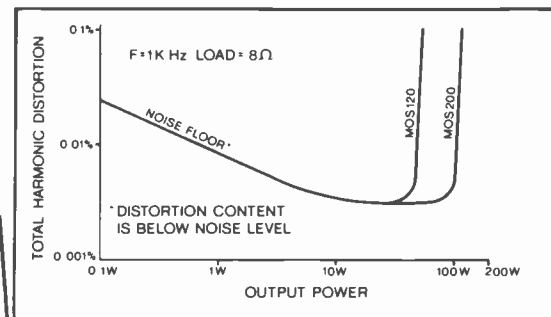I.L.P. POWER AMPS ARE ENCAPSULATED FOR THERMAL STABILITY AND LONGER LIFE



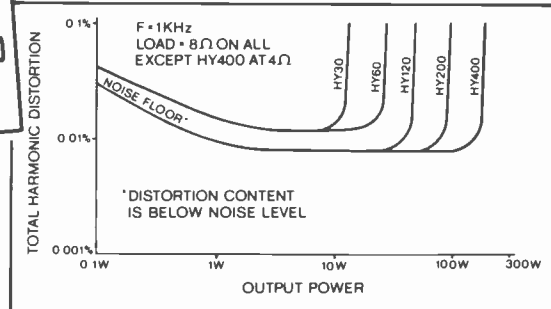Load impedance both models 4Ω - ∞ Input impedance both models 100KΩ
Input sensitivity both models 500mV Frequency response both models 15Hz-100KHz - 3dB




Load impedance all models 4Ω - ∞ Input impedance all models 100KΩ
Input sensitivity all models 500mV Frequency response all models 15Hz-50KHz - 3dB



THE NEW PROFILE EXTRUSIONS
The introduction of standard heatsink extrusion for all I.L.P. power amplifiers achieves many advantages: - Research shows they provide optimum thermal dissipation and stability. Slotted shoulders allow easy mounting; standardisation enables us to keep our prices competitive. Surfaces are matt black, anodised for lower thermal conductivity. Extrusions vary in size according to module number.

NEW PRE-AMPS

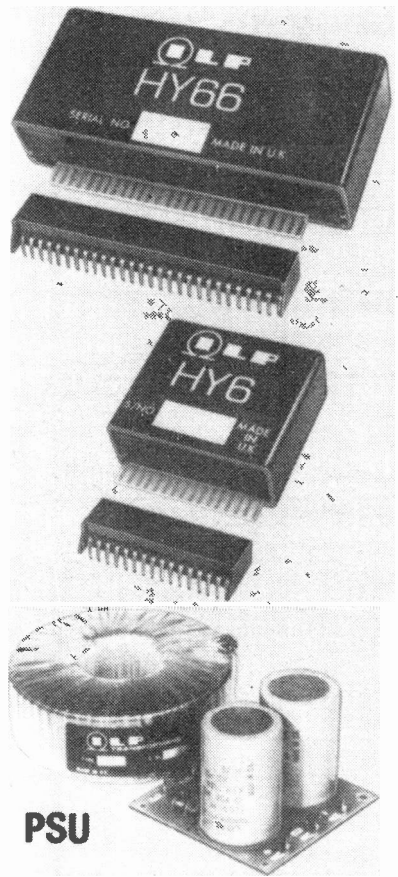


HY6 (mono) and HY66 (stereo) are new to I.L.P.'s range of advanced audio modules. Their improved characteristics and styling ensure their being compatible with all I.L.P. power-amps both MOSFET and BIPOLAR, giving you chance to get the best possible reproduction from your equipment. HY6 and HY66 pre-amps are protected against short circuit and wrong polarity. Full assembly instructions are provided. Mounting boards are available as below.

Sizes - HY6 - 45 x 20 x 40 mm. HY66 - 90 x 20 x 40 mm. **Active Tone Control** circuits provide ± 12 dB cut and boost. **Inputs Sensitivity** - Mag. PU. -3mV: Mic - selectable 1-12mV: All others 100mV. **Tape O/P** - 100mV: **Main O/P** - 500mV: **Frequency response** - D.C. to 100KHz - 3dB.

HY6 mono £5.60 + 84p VAT Connectors included
HY66 stereo £10.60 + £1.59 VAT Connectors included
B6 Mounting Board for one HY6 78p + 12p VAT
B66 Mounting Board for one HY66 99p + 15p VAT

COMPATIBLE WITH ALL ILP MODULES

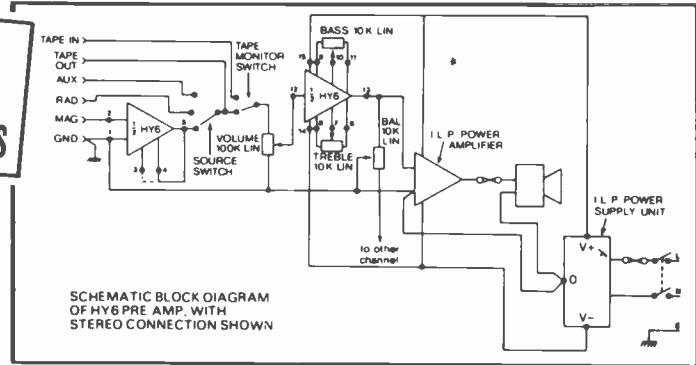

- **DISTORTION TYPICALLY 0.005%**
- **S/N RATIO - 90dB (Mag. P.U. - 68 dB)**
- **38 dB overload margin on Mag. P.U.**
- **LATEST DESIGN HIGH QUALITY CONNECTORS**
- **ONLY POTS, SWITCHES AND PLUGS/SOCKETS NEED ADDING**
- **NEEDS ONLY UNREGULATED POWER SUPPLY ± 15 to ± 60 v**

NEW POWER SUPPLY UNITS

Of the eleven power supply units which comprise our current range, nine have toroidal transformers made in our own factory. Thus these I.L.P. power supply units are space-saving, more efficient and their better overall design helps enormously when assembling building. All models in the range are compatible with all I.L.P. amps and pre-amps with types to match whatever I.L.P. power amps you choose.

- PSU30** ± 15 V at 100mA to drive up to 12 x HY6 or 6 x HY66 **£4.50 + 0.68p VAT**
- **THE FOLLOWING WILL ALSO DRIVE I.L.P. PRE-AMPS**
- PSU36** for use with 1 or 2 HY30's **£8.10 + £1.22 VAT**
- **ALL THE FOLLOWING USE TOROIDAL TRANSFORMERS**
- PSU50** for use with 1 or 2 HY60's **£9.75 + £1.46 VAT**
- PSU60** for use with 1 HY120 **£9.75 + £1.46 VAT**
- PSU65** for use with 1 MOS120 **£9.75 + £1.46 VAT**
- PSU70** for use with 1 or 2 HY120's **£13.61 + £2.04 VAT**
- PSU75** for use with 1 or 2 MOS120 **£13.61 + £2.04 VAT**
- PSU90** for use with 1 HY200 **£13.61 + £2.04 VAT**
- PSU95** for use with 1 MOS200 **£14.75 + £2.21 VAT**
- PSU180** for use with 1 HY400 or 2 HY200 **£23.02 + £3.45 VAT**
- PSU185** for use with 1 or 2 MOS200 **£24.20 + £3.63 VAT**

IN A RANGE OF 11 MODELS USING LATEST TOROIDAL TRANSFORMERS

1971-1980 TEN YEARS OF PLANNED PROGRESS

When, in 1971, Ian L. Potts founded his now world-famous company, he saw the need for a different and more rational approach to exploiting to the full, the potential that lay in modular construction. New thinking was badly needed. The result was a range of modules revolutionary in concept. The rightness of this new thinking is shown by the size of the company today, its new factory, its vast exports, its acceptance by constructors as the modules to build with. The range grows bigger and better. Exciting new lines (in no way conflicting with existing ones) are well past drawing board stage. This is why I.L.P. are simply ahead and staying there.

**NO QUIBBLE 5 YEAR GUARANTEE
 7-DAY DESPATCH ON ALL ORDERS
 BRITISH DESIGN AND MANUFACTURE
 FREEPOST SERVICE**

★ **Freepost facility**
 When ordering or writing about I.L.P. products, you do not need to stamp the envelope. Mark it FREEPOST plus the code shown in the address below. We pay the postage for you.

★ **TO ORDER** Send cheque or money order payable to I.L.P. Electronics Ltd and crossed. Or pay by ACCESS or BARCLAYCARD. Cash payments must be in registered envelope; if C.O.D. payment is wanted, please add £1.00 to TOTAL value of order.

BRITAIN'S FASTEST GROWING MODULE SUPPLIERS

To: I.L.P. ELECTRONICS LTD. CANTERBURY CT2 7EP

Please supply

..... Total purchase price £

I enclose Cheque Postal Orders International Money Order

Please debit my Access/Barclaycard Account No.

.....

NAME

ADDRESS

.....

Signature



I.L.P. ELECTRONICS LTD.

FREEPOST 4 Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP.
 Telephone (0227) 54778 | Technical (0227) 64723 | Telex 965780

Available also from MARSHALLS, WATFORD ELECTRONICS and certain other selected retailers

ALL U.K. ORDERS DESPATCHED POST FREE

WATFORD ELECTRONICS

33/35 CAIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER, CALLERS WELCOME
Tel. Watford (0923) 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P Add 40p to ALL ORDERS UNDER £10. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE. ACCESS ORDERS WELCOME.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to all prices.

We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday. Ample Free Car Parking space available.

ELECTRONIC CAPACITORS: (Values are in nF) 500V: 10.50p; 47.78p; 100.65p; 63V: 0.47, 1.0, 1.5, 2.2, 3.3, 4.7, 6.8, 8p; 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10000, 15000, 22000, 33000, 47000, 68000, 100000, 150000, 220000, 330000, 470000, 680000, 1000000, 1500000, 2200000, 3300000, 4700000, 6800000, 10000000, 15000000, 22000000, 33000000, 47000000, 68000000, 100000000, 150000000, 220000000, 330000000, 470000000, 680000000, 1000000000, 1500000000, 2200000000, 3300000000, 4700000000, 6800000000, 10000000000, 15000000000, 22000000000, 33000000000, 47000000000, 68000000000, 100000000000, 150000000000, 220000000000, 330000000000, 470000000000, 680000000000, 1000000000000, 1500000000000, 2200000000000, 3300000000000, 4700000000000, 6800000000000, 10000000000000, 15000000000000, 22000000000000, 33000000000000, 47000000000000, 68000000000000, 100000000000000, 150000000000000, 220000000000000, 330000000000000, 470000000000000, 680000000000000, 1000000000000000, 1500000000000000, 2200000000000000, 3300000000000000, 4700000000000000, 6800000000000000, 10000000000000000, 15000000000000000, 22000000000000000, 33000000000000000, 47000000000000000, 68000000000000000, 100000000000000000, 150000000000000000, 220000000000000000, 330000000000000000, 470000000000000000, 680000000000000000, 1000000000000000000, 1500000000000000000, 2200000000000000000, 3300000000000000000, 4700000000000000000, 6800000000000000000, 10000000000000000000, 15000000000000000000, 22000000000000000000, 33000000000000000000, 47000000000000000000, 68000000000000000000, 100000000000000000000, 150000000000000000000, 220000000000000000000, 330000000000000000000, 470000000000000000000, 680000000000000000000, 1000000000000000000000, 1500000000000000000000, 2200000000000000000000, 3300000000000000000000, 4700000000000000000000, 6800000000000000000000, 10000000000000000000000, 15000000000000000000000, 22000000000000000000000, 33000000000000000000000, 47000000000000000000000, 68000000000000000000000, 100000000000000000000000, 150000000000000000000000, 220000000000000000000000, 330000000000000000000000, 470000000000000000000000, 680000000000000000000000, 1000000000000000000000000, 1500000000000000000000000, 2200000000000000000000000, 3300000000000000000000000, 4700000000000000000000000, 6800000000000000000000000, 10000000000000000000000000, 15000000000000000000000000, 22000000000000000000000000, 33000000000000000000000000, 47000000000000000000000000, 68000000000000000000000000, 100000000000000000000000000, 150000000000000000000000000, 220000000000000000000000000, 330000000000000000000000000, 470000000000000000000000000, 680000000000000000000000000, 1000000000000000000000000000, 1500000000000000000000000000, 2200000000000000000000000000, 3300000000000000000000000000, 4700000000000000000000000000, 6800000000000000000000000000, 10000000000000000000000000000, 15000000000000000000000000000, 22000000000000000000000000000, 33000000000000000000000000000, 47000000000000000000000000000, 68000000000000000000000000000, 100000000000000000000000000000, 150000000000000000000000000000, 220000000000000000000000000000, 330000000000000000000000000000, 470000000000000000000000000000, 680000000000000000000000000000, 1000000000000000000000000000000, 1500000000000000000000000000000, 2200000000000000000000000000000, 3300000000000000000000000000000, 4700000000000000000000000000000, 6800000000000000000000000000000, 10000000000000000000000000000000, 15000000000000000000000000000000, 22000000000000000000000000000000, 33000000000000000000000000000000, 47000000000000000000000000000000, 68000000000000000000000000000000, 100000000000000000000000000000000, 150000000000000000000000000000000, 220000000000000000000000000000000, 330000000000000000000000000000000, 470000000000000000000000000000000, 680000000000000000000000000000000, 1000000000000000000000000000000000, 1500000000000000000000000000000000, 2200000000000000000000000000000000, 3300000000000000000000000000000000, 4700000000000000000000000000000000, 6800000000000000000000000000000000, 10000000000000000000000000000000000, 15000000000000000000000000000000000, 22000000000000000000000000000000000, 33000000000000000000000000000000000, 47000000000000000000000000000000000, 68000000000000000000000000000000000, 100000000000000000000000000000000000, 150000000000000000000000000000000000, 220000000000000000000000000000000000, 330000000000000000000000000000000000, 470000000000000000000000000000000000, 680000000000000000000000000000000000, 1000000000000000000000000000000000000, 1500000000000000000000000000000000000, 2200000000000000000000000000000000000, 3300000000000000000000000000000000000, 4700000000000000000000000000000000000, 6800000000000000000000000000000000000, 10000000000000000000000000000000000000, 15000000000000000000000000000000000000, 22000000000000000000000000000000000000, 33000000000000000000000000000000000000, 47000000000000000000000000000000000000, 68000000000000000000000000000000000000, 100000000000000000000000000000000000000, 150000000000000000000000000000000000000, 220000000000000000000000000000000000000, 330000000000000000000000000000000000000, 470000000000000000000000000000000000000, 680000000000000000000000000000000000000, 1000000000000000000000000000000000000000, 1500000000000000000000000000000000000000, 2200000000000000000000000000000000000000, 3300000000000000000000000000000000000000, 4700000000000000000000000000000000000000, 6800000000000000000000000000000000000000, 100, 15000000000000000000000000000000000000000, 22000000000000000000000000000000000000000, 33000000000000000000000000000000000000000, 47000000000000000000000000000000000000000, 68000000000000000000000000000000000000000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47000, 68000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47000, 68000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47000, 68000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47000, 68000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47000, 68000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47000, 68000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47000, 68000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47000, 68000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47000, 68000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000,

WATFORD ELECTRONICS

COMPUTER CORNER

- **SUPERBOARD II** Ready-built and tested
Only **£150**
- **PSU 5V/3A** (for above incl. RF Modulator) **£25**
- **610 Expansion Board** (8K RAM) expandable to 24K **£150**
- **CHALLENGER 1P** (Superboard cased with PSU) **£188**
- **Extra 4K RAM** (8x2114) **£18**
- **Plastic Case** Black, fits UK101 Superboard, NASCOM II etc **£25**
- **SUPERPRINT 800**, 80 column High Performance Impact Printer. Ideal for PET, NASCOM, UK101 Superboard, TRS80 etc **only £325**
- **VIDEO GENIE** based on TRS80. Utilises Z80, 12K level II Basic 16K RAM incl. Cassette Deck **£290**
- **STRINGY FLOPPY**. Combines economy of Cassette with speed & reliability of DISC (incl. 20 wafers) **£169**
- **SOFTY**. Intelligent SPROM Programmer. Connects directly to TV. Develop. copy Burn EPROMS Kit **£99**
Ready-built and tested **£120**
PSU for above (Built) **£20**
- **UHF Modulators 8MHz** **280p**
UHF Modulators 6MHz **450p**
- **KEYPADS 4 x 4 matrix** **350p**
- **Full ASCII coded 56 Key Keyboard Mod.** **75¢** **£40**
- **10x C12 Cassettes in Rack** **£5.50**
(P&P is extra on all items). Call in at our shop for Demo or write in for leaflets

SWITCHES TOGGLE 2A, 250V 32p SPST 30p DPST 34p DPDT 44p 4 pole on/off 54p	SLIDE 250V 1A DPDT 14p 1A DPDT c/over 15p 1/2A DPDT 13p 4 pole 2 way 24p	ROTARY : Make your own multiway Switch. Adjustable Stop Shafting Assembly. Accommodate up to 6 Wafers 90p Mains Switch DPST to 11H Break Before Make Wafers 1 pole/12 way 2p/6 way 3p/4 way 4p/3 way 6p/2 way 56p Spacer and Screen 6p ROTARY (Adjustable Stop) 1 pole/2 to 12 way 2p/2 to 6 way, 3 pole/2 to 4 way, 4 pole/2 to 3 way 43p ROTARY : Mains 250V AC, 4 Amp 52p
SUB-MIN TOGGLE SP changeover 59p SPST on/off 54p SPST biased 85p DPDT 6 tags 70p DPDT centre off 79p DPDT biased 115p	PUSH BUTTON DPDT Black Body Red, Blue, Grn., Yell SRL Latching 125p SRM Momentary 125p	'D' CONNECTORS (Cannon type) 9way 95p 128p — 15way 135p 195p 150p 25way 198p 284p 170p 37way 290p 398p 185p
	MINI, Non Locking Push to Make 15p Push Break 25p	
	D.I.L. SWITCHES (SPST) 4 way 85p , 6 way 95p ; 8 way 115p	


CRYSTALS 100KHz 323 455KHz 383 1MHz 323 1.008M 395 1.28MHz 392 1.8MHz 323 1.8MHz 323 1.8432MHz 362 2.4576MHz 362 3.2768M 323 3.57954M 195 4.000MHz 290 4.032MHz 323 4.433619M 135 5.0MHz 355 5.195M 323 5.24288M 425 6.0MHz 323 6.5536M 209 7.680M 323 8.0MHz 392 8.08333M 362 8.867237M 362 9.375M 323 10.0MHz 323 10.7MHz 323 12MHz 392 14.31818M 362 18MHz 323 18.432M 323 20.0MHz 323 27.648M 323 38.5667M 355 48.0MHz 323 100.0MHz 323	TRANSFORMERS (Mains Prim. 220-240V) 6.0-6V 9.0-9V, 12.0-12V 100mA 95p 3VA: 0-6V 0-6V (PCB mounting) 150p 6VA: 6V-5A 6V-5A, 9V-4A 9V-4A, 12V-3A 215p 12V-3A, 15V-2.5A 15V-2.5A 215p 12V: 4.5V-1.3A 4.5V-1.3A, 6V-1.2A 6V-1.2A, 20V-3A 235p (30p p&p) 12V-1A 12V-1A, 15V-8A 15V-8A, 20V-6A 320p (55p p&p) 20V-6A 320p (55p p&p) 50VA: 6V-4A 6V-4A, 9V-2.5A 9V-2.5A, 12V-2A, 12V-2A, 15V-1.5A 15V-1.5A, 20V-1.2A 20V-1.2A, 25V-1A 25V-1A, 30V-8A 30V-8A 365p (60p p&p) 100VA: 12V-4A 12V-4A, 15V-3A 15V-3A, 20V-2.5A 20V-2.5A, 30V-1.5A 30V-1.5A, 40V-1.25A 40V-1.25A, 50V-1A 50V-1A 695p (74p p&p). (NB. p&p charge to be added above our normal postal charge.)	ALUM. BOXES WITH LID 3x2x1" 5p 2 1/2x5 1/2x1 1/2" 75 4x4x1 1/2" 75 4x2 1/2x1 1/2" 75 4x5 1/2x1 1/2" 100 4x2 1/2x2" 80 5x4x2" 107 6x4x2" 110 7x5x2 1/2" 185 8x6x3" 185 10x7x3" 240 10x4 1/2x3" 228 12x5x3" 230 12x8x3" 275	PANEL METERS FSD 60x46x 35mm 0.50pA 0-100uA 40p 0-500uA 0.1mA 0-1mA 0.5mA 0-10mA 0.50mA 0-100mA 0.500mA 0-500mA 0.1A 0-2A 0.25V 0-20V 0.50V AC 0-300V AC
--	---	--	--

VOLTAGE REGULATORS 1A TO3 +ve -ve 5V 7805 145p 7905 220p 12V 7812 145p 7912 220p 15V 7815 145p — 18V 7818 145p —	1A TO220 Plastic Casing 5V 7805 60p 7905 65p 12V 7812 60p 7912 65p 15V 7815 60p 7915 65p 18V 7818 60p 7918 65p 24V 7824 60p —	OPTO LEDs with Clips TIL209 Red 13 TIL211 Grn. 17 TIL212 Yel. 18 TIL220 2" Red 14 2 Green, Yellow or Amber 18 7 Segment Displays Square LEDs: Red TIL307 675 Green, Yellow 30 TIL312 3" CA 105 LD271 Infra Red 40 TIL313 3" CC 105 SRH205 Detector 90 TIL321 5" CA 115 TIL32 Infra Red 65 TIL322 5" CC 115 TIL78 Detector 75 DL704 3" CC 99 BARGRAPY Red 10 DL707 3" CA 99 segments 225 DL747 6" CA 180	ISOLATORS IL74 55 DVM176 1885 TIL111/2 85 LCD 3 1/2 Digits 775 TIL114 95 LCD 4 Digits 975 TIL117 110 LCD 6 Digits 950
--	---	--	--

ETI Projects: Parts available for Digital Test Meter, DM900, 60W Amplifier System. Send SAE plus 5p for list.	LM300H 170p LM327 270p LM305H 140p LM723 38p LM309K 135p TAA550 50p LM317K 350p TBA625B 95p LM323K 550p TDA1412 150p LM325N 240p 78H05 + 5V/5A 595p LM326N 240p 78HG + 5V to +25V 5A 650p
--	---

LS245 350 LS247 136 LS248 135 LS249 135 LS251 130 LS253 95 LS257 95 LS258 120 LS259 160 LS261 450 LS266 75 LS273 180 LS275 320 LS279 88 LS280 250 LS283 90 LS290 130 LS293 130 LS295 215 LS298 215 LS299 420 LS300 175 LS302 175 LS320 270 LS323 450 LS324 200 LS325 320 LS326 330 LS327 315 LS346 185 LS347 150 LS348 190 LS352 185 LS353 185 LS365 65 LS366 65 LS367 65 LS368 90	LS373 150 LS374 150 LS375 160 LS377 199 LS378 140 LS379 215 LS384 250 LS385 420 LS386 85 LS390 140 LS393 140 LS395 210 LS396 199 LS398 275 LS399 230 LS445 140 LS447 195 LS490 245 LS568 105 LS569 105 LS570 270 LS573 750 LS574 850	4015 85 4016 42 4017 82 4018 28 4019 48 4020 99 4021 105 4022 95 4023 25 4024 75 4025 25 4026 180 4027 48 4028 82 4029 105 4030 60 4031 225 4032 125 4033 175 4034 210 4035 125 4036 365 4037 115 4038 118 4039 360 4040 105 4041 80 4042 80 4043 95 4044 95 4045 175 4046 130 4047 98 4048 65 4049 45 4050 48 4051 80 4052 80	4053 80 4054 130 4055 135 4056 135 4057 2650 4059 575 4060 130 4061 1225 4062 995 4063 120 4064 58 4067 430 4068 26 4069 26 4070 30 4071 25 4072 25 4073 25 4075 25 4076 99 4077 48 4078 30 4079 118 4081 28 4082 28 4085 90 4086 90 4089 150 4093 89 4094 240 4095 105 4096 105 4097 350 4098 115 4099 190 4100 125 4101 125 4102 125 4170 125 4171 120 4172 120 4173 125 4174 125 4175 120 4176 125 4177 125 4178 125 4179 125 4250 125	4521 250 4522 150 4526 150 4527 160 4528 120 4529 175 4530 89 4531 165 4532 140 4534 575 4536 395 4538 160 4539 135 4541 150 4543 175 4549 296 4553 440 4554 175 4555 85 4556 75 4557 425 4558 299 4559 290 4560 235 4561 95 4562 595 4566 190 4568 299 4569 250 4572 48 4574 595 4581 350 4582 150 4583 125 4584 64 4585 140 4586 140 4587 140 4659 140 4660 140
---	---	---	---	---

IT'S AS EASY AS A,B,C...

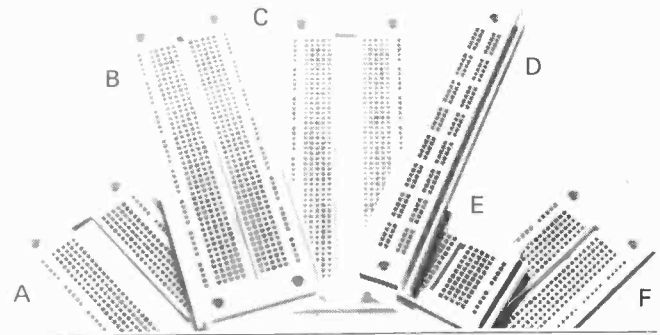

See us on STAND F1 at LONDON BREADBOARD EXHIBITION

- A EXP 650 For microprocessor chips. **£3.60**
- B EXP 300 The most widely sold breadboard in the UK; for the serious hobbyist. **£5.75**
- C EXP 600.6" centre channel makes this the Microprocessor Breadboard. **£6.30**
- D EXP 4B An extra 4 bus-bars in one unit. **£2.30**
- E EXP 325 Built in bus-bars accepts 8, 14, 16 and up to 22 pin ICs. **£1.60**
- F EXP 350 270 contact points, ideal for working with up to 3 x 14 pin DIPs. **£3.15**
- G PB6 Professional breadboard in easily assembled kit form. **£9.20** (Not illustrated.)
- H PB 100 Kit form breadboard recommended for students and educational uses. **£11.80** (Not illustrated.)

& IT'S AS EASY AS 1,2,3 with THE EXPERIMENTER SYSTEM

SCRATCHBOARD
-BREADBOARD
-MATCHBOARD

- EXP 300PC which includes one item. A matchboard pre-drilled PCB — **£1.32**
- EXP 302 which includes three items. Three 50-sheet scratchboard workpads — **£1.68**
- EXP 303 which includes three items. Two matchboards and an EXP-300 solderless breadboard — **£8.60**
- EXP 304 which includes four items. Two matchboards and EXP 300 breadboard and a scratchboard workpad — **£9.30**

The above prices do not include P&P and 15% VAT

TOMORROW'S TOOLS TODAY
CONTINENTAL SPECIALITIES CORPORATION C.S.C. (UK) Limited, Dept. 9H,
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.
Tel: Saffron Walden (0799) 21682. Telex: 817477.

NAME _____
ADDRESS _____
I enclose cheque/PO for £ _____
or debit my Barclaycard, Access, American Express card
No. _____ Exp. date _____
or Tel: (0799) 21682 with your card number and your order will be in the post immediately.

A EXP 650 £5.00	Qty. Reqd.	B EXP 300 £7.76	Qty. Reqd.
C EXP 600 £8.39	Qty. Reqd.	D EXP 4B £3.50	Qty. Reqd.
E EXP 325 £2.70	Qty. Reqd.	F EXP 350 £4.48	Qty. Reqd.
G PB6 £11.73	Qty. Reqd.	H PB 100 £14.72	Qty. Reqd.

Experimenter System

1 EXP 300 PC £2.38	Qty. Reqd.	2 EXP 302 £2.79	Qty. Reqd.
3 EXP 303 £11.04	Qty. Reqd.	4 EXP 304 £11.85	Qty. Reqd.

Boxed prices include P & P and 15% VAT FREE catalogue tick box
If no dealer in your area contact CSC direct.

Continental Specialities Corporation (UK) Limited, Dept. 9H
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

FREE BURGLAR ALARM BOOKLET

Our new FREE booklet entitled, 'Planning, Installing and Maintaining Home Intruder Alarm Systems', gives advice on how to do just that.

At Linton Electronics we do not assume that because you are concerned about Home Security you are automatically a leading authority on the subject of Intruder Detection Equipment and Systems.

Our new FREE booklet takes you step by step through the maze of all the different equipments available, explains their various functions, advantages and disadvantages, and does it all in language you can understand.

Our new FREE booklet also gives pointers as to how an intruder in your home might operate, so indicating how your Intruder Alarm System can not only be effective, but cost effective too.

In short, our new FREE booklet has been written to give you confidence in the system you install. As a mail order supplier of Intruder Alarm Equipment we feel that that is important.

Write, or telephone our answering service NOW for your free booklet. We will send your copy by return of post.



4 HELSTON CLOSE, LINTON,
BURTON ON TRENT, STAFFS.
DE12 6PN

PHONE: BURTON (0283) 761877
24 Hour Phone Answering Service

ACCESS ORDERS WELCOME

CAR ENTERTAINMENT BARGAINS

Show us that you could have purchased for less within one month of your purchase and we will refund the difference!

● **STEREO CASSETTE/RADIO.** MW and Stereo FM radio and Stereo Cassette Player, 8 watts per channel, lockable fast forward and autopost. Includes fitting kit and **FREE SPEAKERS.** Sold elsewhere for up to £85 (believe it or not). **OUR PRICE** £45 (+ £1.50 post). (For negative earth cars only)



● **7-CHANNEL STEREO GRAPHIC EQUALISER/BOOSTER AMPLIFIER.** 17 watts R.M.S. per channel. Frequency response 20Hz to 30,000Hz. ± 12dB cut/boost on each channel. Complete with fitting kit. You would pay at least £45 elsewhere. **OUR PRICE** £26 (+ £1.20 post).

SUITABLE SPEAKERS FOR EQUALISER. Adjustable angle, shelf-mounting, power handling 30 watts max. **OUR PRICE** £16 per pair (+ £1.20 post).



ELECTRIC ANTENNA. Wing mounting, including switch and fitting kit. **OUR PRICE** £10 (+ £1.20 post).

PLEASE NOTE: These goods are ready built units. All goods guaranteed one year. 10-day money back offer on all undamaged goods. Goods ex-stock at time of going to press. Send SAE for details.

MINIKITS ELECTRONICS LTD.

88D Hainault Road, Leytonstone, London E11 1EH


OLSON

PORTABLE MAINS DISTRIBUTION — NEW WITH CIRCUIT BREAKERS



**New!
Slim Jim**

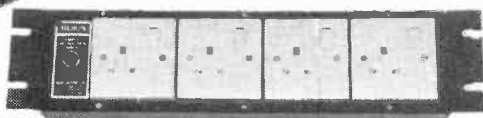Dim. 1 3/4" x 2 1/2" x 18 3/4"
£13.50 P&P £1 + VAT




3 1/2" x 19" Rack Mounting Type 13A/4SW/R **£21.50 P&P £1 + VAT**



4 feet LG. 30 amp total load Instant Trunking System for Wall or Bench Mounting

NEW! 10 sockets switched in sloping box

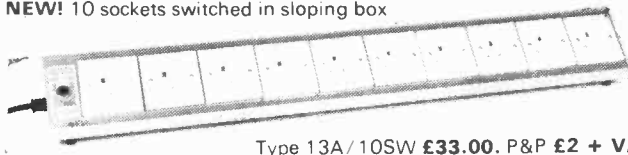

Type 13A/10SW **£33.00. P&P £2 + VAT**




COMPLETE WITH 6FT. CABLE AND 13-AMP FUSED PLUG

4 sockets 13A	£16.00
6 sockets 13A	£18.75
4 sockets 13A switched	£18.50
6 sockets 13A switched	£21.50
+ Post £1 + VAT	




ALL DISTRIBUTION PANELS ARE FITTED WITH MK SOCKETS & PLUG

Send for details of complete range

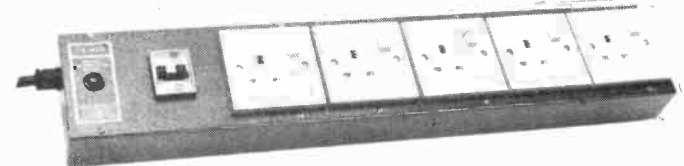

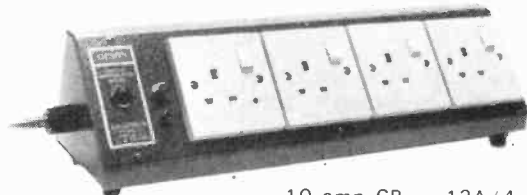Fitted with M.K. 10 amp C.B. — 13/A5 SW.CB **£33.00 + post £1 + VAT**




10 amp CB — 13A/4 SW.CB
£29.25 + post £1 + VAT

TR6 — 6 sockets switched **£27.00**

TR9 — 9 sockets switched **£32**
Plus P&P **£2 + VAT**

MAINS ISOLATING UNIT

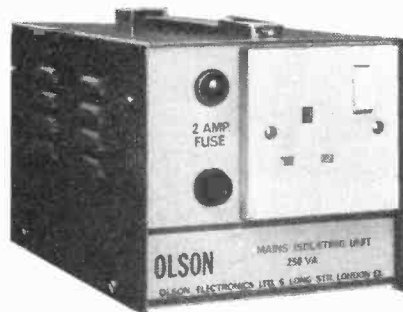The Olson mains isolating unit is an essential bench item for safety when testing and repairing mains-operated equipment. The isolating transformer has an earthed screen and is rated 250VA.



£38 + P&P £2 + VAT


OLSON ELECTRONICS LTD., FACTORY NO. 8, 5-7 LONG ST., LONDON E2 8HJ
TEL. 01-739 2343

The NEW

VIDEOTONE

YOU CANNOT BUY CHEAPER - YOU CAN ONLY GET LESS FOR YOUR MONEY!

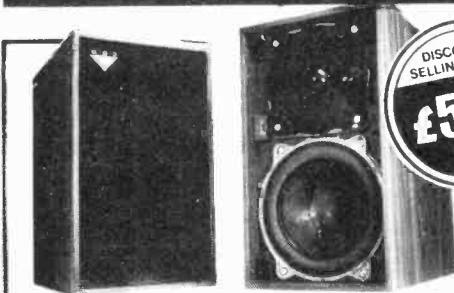Introduces DIRECT SELLING - the Ultimate Discount!!!



DISCOUNT SELLING PRICE
£50.00

LOUDSPEAKERS

The complete fully reviewed range of Videotone Speakers which dominate within their class. Now at lowest ever prices.

D 100	£38
Minimax 11	£44
GB3	£50
GB2	£60
GBS	£207
D 93	£40



DISCOUNT SELLING PRICE
£68.00

DISCOUNT SELLING PRICE
£75.00

ELECTRONICS

This new range of Electronics from Videotone redefines the words quality and value for money to a new high.

30 watt amp MC input SA4130	£75.00
Stereo Tuner ST4120	£68.00
Cassette full features SC3200	£98.00
50 Watt amplifier WA7700	£77.00
20 Watt amplifier LA2020	£58.00

CORAL CARTRIDGES

Fast becoming one of the top names

MOVING COIL
UK's No. 1 Cartridge

MC 81	£48.87
777EX	£35
777E	£25



HEAD AMP

H300	£51.75
T100	£24.75

MOVING MAGNET

555SX	£7.28
555E	£14.22
666E	£32.48

HEADSHELLS

S100	£6
S101	£7
S200	£4



MICROPHONES

MU 105-22	£29.30
MU 105-12	£22.25
MU 25 C	£17.39

TURNTABLES

Sansui SR222 Mk2	£69.00
JVC LA 11	£64.00
JVC SLQ 3	£140.00

A MESSAGE FROM VIDEOTONE

Dear Customer

You will find that the products advertised on this page are the best possible value for money. They are only low in price because we have eliminated large amounts of selling costs that other brands have to suffer. These savings are passed directly on to you. We have full brochures on any specific item you may be interested in and a competent realistic staff of engineers at our London Showrooms to help you in your choice. Our consumer protection packages are comprehensive and we offer every form of financing you may require. We carry out our own servicing and are dedicated to giving Value for Money. We are confident our products are unbeatable. You may purchase with confidence because our Engineers have specially selected them from competitive sources throughout the world and we import them directly ourselves. Remember, you have 21 days trial period on all products. That is the measure of our confidence.

Bliff. Hardcastle
Managing Director




DISCOUNT SELLING PRICE
£9.69

HEADPHONES

HP 90 Headphone	£12.65
HP 80 Headphone	£9.69

Superbly made with top flight performance.

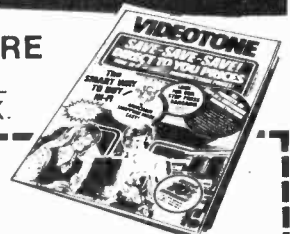SEND FOR OUR LATEST FREE BROCHURE AND DETAIL LIST OF LOCAL SALES OUTLETS IN THE U.K.



VIDEOTONE
98 CROFTON PARK ROAD,
CROFTON PARK, LONDON SE4
Tel: 01-690 8511/2

Please send me your Direct Selling Brochure and list of sales outlets.

Name _____

Address _____

E.T.I. 12/80

ALL PRODUCTS ON DISPLAY & CONTINUOUS DEMONSTRATIONS

ALL PRICES INCLUDE VAT

TRANSCENDENT 2000 SINGLE BOARD SYNTHESIZER

Designed by consultant Tim Orr (formerly synthesizer designer for EMS Ltd.) and featured as a constructional article in ETI, this live performance synthesizer is a 3 octave instrument transposable 2 octaves up or down giving sweep control, a noise generator and an ADSR envelope shaper. There is also a slow oscillator, a new pitch detector, ADSR repeat, sample and hold, and special circuitry with precision components to ensure tuning stability amongst its many features.

The kit includes fully finished metalwork, fully assembled solid teak cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or 1/2% metal film), and it really is complete — right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit — you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibreglass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesizer comparable in performance and quality with ready-built units selling for many times the price.

Comprehensive handbook supplied with all complete kits! This fully describes construction and tells you how to set up your synthesizer with nothing more elaborate than a multi-meter and a pair of ears!

**COMPLETE KIT ONLY
£168.50 + VAT!**



Cabinet size 24.6" x 15.7" x 4.8" (rear) 3.4" (front)

NEW! TRANSCENDENT POLYSYNTH

**EXPANDABLE POLYPHONIC SYNTHESIZER
AS FEATURED IN
THIS ISSUE!**



COMPLETE KIT from £320 + VAT

By brilliant design work and the use of high technology components the Polysynth brings to the reach of the home constructor a machine whose versatility and range of sounds is matched only by ready-built equipment costing thousands of pounds. This latest addition to the famous Transcendent family is a 4 octave (transposable over 7 octaves) polyphonic synthesizer with internally up to 4 voices making it possible to play simultaneously up to 4 notes. An add-on unit permits expansion up to 8 voices. Each voice is a complete synthesizer in itself with 2 VCOs, 2 ADSRs, 1VCA and 1 VCF. Being voltage controlled all voices can be adjusted simultaneously by master controls yet their own pitch and gate signals mean each voice can be operated independently from the keyboard.


Although using very advanced electronics the kit is mechanically very simple with minimal wiring, most of which is with ribbon cable connectors. All controls are PCB mounted and the voice boards plug into PCB mounted sockets. The kit includes fully finished metalwork, solid teak cabinet, professional quality components (resistors 2% metal oxide or 0.5% and 0.1% metal film), nuts, bolts, etc. Complete kit with 1 voice £320, 2 voices £368, 4 voices £464, expansion unit to extend to 8 voices £275 (all prices subject to V.A.T.). A mere fraction of what you would have to pay for a ready-built comparable instrument!

TRANSCENDENT DPX

MULTI-VOICE SYNTHESIZER

Another superb design by
synthesizer expert Tim Orr
published in
Electronics Today International

**COMPLETE KIT
ONLY
£299 + VAT!**

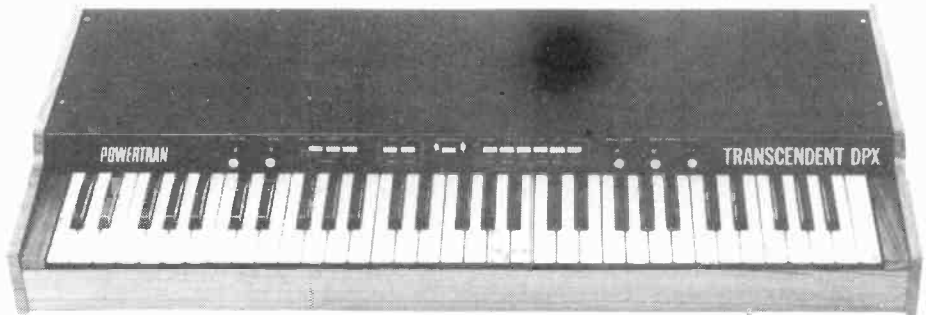

Cabinet size 36.3" x 15.0" x 5.0" (rear) 3.3" (front)

The Transcendent DPX is a really versatile 5 octave keyboard instrument. There are two audio outputs which can be used simultaneously. On the first there is a beautiful harpsichord or reed sound—fully polyphonic, i.e. you can play chords with as many notes as you like. On the second output there is a wide range of different voices, still fully polyphonic. It can be a straightforward piano as a honky tonk piano or even a mixture of the two! Alternatively you can play strings over the whole range of the keyboard or should you prefer — strings on the top of the keyboard and brass as the lower end (the keyboard is electronically split after the first two octaves) or vice-versa or even a combination of strings and brass sounds simultaneously. And on all voices you can switch in circuitry to make the keyboard touch sensitive! The harder you press down a key the louder it sounds — just like an acoustic piano. The digitally controlled multiplexed system makes practical touch sensitivity with the complex dynamics law necessary for a high degree of realism. There is a master volume and tone control, a separate control for the brass sounds and also a vibrato circuit with variable depth control together with a variable delay control so that the vibrator comes in only after waiting a short time after the note is struck for even more realistic string sounds.

To add interest to the sounds and make them more natural there is a chorus / ensemble unit which is a complex phasing system using CCD (charge coupled device) analogue delay lines. The overall effect of this is similar to that of several acoustic instruments playing the same piece of music. The ensemble circuitry can be switched in with either strong or mild effects.

As the system is based on digital circuitry digital data can be easily taken to and from a computer (for storing and playing back accompaniments with or without pitch or key change, computer composing, etc., etc.).

Although the DPX is an advanced design using a very large amount of circuitry, much of it very sophisticated, the kit is mechanically extremely simple with excellent access to all the circuit boards which interconnect with multiway connectors, just four of which are removed to separate the keyboard circuitry and the panel circuitry from the main circuitry in the cabinet.

The kit includes fully finished metalwork, solid teak cabinet, professional quality components (all resistors 2% metal oxide), nuts, bolts, etc., even a 13A plug!

POWERTRAN

**MANY MORE KITS ON PAGE 115. MORE KITS AND ORDERING
INFORMATION ON INSIDE FRONT COVER**


All projects on this page can be purchased as separate packs, e.g. PCBs, components sets, hardware sets, etc. See our free catalogue for full details and prices

DIGEST

Hi-Fi At Your Hip

Yup! It had to happen. Binatone have produced the cheap alternative to Sony's Stowaway portable cassette player. Called the HipFi, it will retail at £59.95. Backed by a nationwide advertising campaign, it has loads

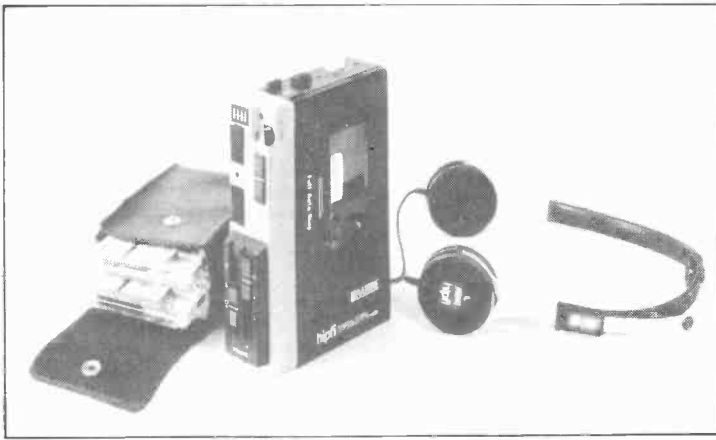of facilities: separate volume control for each channel, tone control, add-on headphones (optional extra), fast forward and rewind with cue and review, fold flat headphones for easy carrying and a direct talk line for communicating with the outside world. The three pencil alkaline batteries provide approximately eight hours playing time. See this month's Audiophile for further details.



IMPORTANT NOTICE

Readers have recently confused Electronics Today Limited as being associated with the ownership of our magazine, Electronics Today International. Our magazine is owned by Modmags Limited, part of the Argus Press Holdings Limited Group of Companies.

Electronics Today Limited advertises in our Magazine, as "Metac", but so as to prevent any further confusion we wish to make it clear that Electronics Today Limited is not owned or managed by any member of the Argus Press Holdings Limited Group of Companies.

Multi Purpose

Further to our recent Digital Multimeter Survey, we have received details of Thurlby Electronics Ltd's new Model 1503 4 1/2 digit LCD Multimeter. It has an unusually long scale length of 32,768 counts (± 15 bits) and this enables it to monitor a 1 mV change in a 30 V power rail. Thirty measuring ranges are provided covering the five basic functions

of DC and AC voltage, DC and AC current and resistance. Diode test and frequency measurement functions are also included. Maximum voltage input is 1200 V and current can be measured up to 10 A continuous, 25 A short term. The 1503 is an entirely British design and sells for £139. For further information contact Thurlby Electronics Ltd, Suite 1, Coach Mews, The Broadway, St Ives, Huntingdon, Cambs, PE17 4BN.



Breadboard 80

Whatever aspect of electronics you're into, make sure you're in London in November for this year's Breadboard exhibition. From CB to home computing,

soldering to synthesisers — demonstrations, special offers — it's all at Breadboard 80.

The exhibition runs for five days — the doors open at 10.00 am on November 26th (watch the electronics Press for full details). Don't miss it.

Jaws — OK Style

OK Machine & Tool's new 'AD' wire dispenser comes complete with its own teeth. It's a heavy duty cutting and stripping wire dispenser with precision ground steel cutters and die stamped stripping blade. The strip length can easily be adjusted from 9 1/2-51 mm and the stripping blades can be changed to handle 24 or 30 AWG (0.5 or 0.25 mm) wire. 24 and 30 AWG dispensers are available with 15.2 and 30.5 m of wire respectively. Both offer a choice of insulation colour.


The transparent case nicely avoids that embarrassing situation when you sit down to do a job, pull out a length of wire and find that you're holding the last four inches of wire in your hand. You can see through OK's dispenser how much wire is left on the roll. Refill rolls are available and easily fitted.

For more information on the 'AD' cutting and stripping wire

dispenser contact OK Machine & Tool (UK) Ltd, Dutton Lane, Eastleigh, Hampshire SO5 4AA.



TTLs by TEXAS				93 SERIES				74S SERIES				TRANSISTORS				BFR40				TIP30A				2N3055				3N204				6A 50V			
7400	11p	74293	150p	4020	100p	9301	160p	74500	60p	745114	120p	AC126	25p	BFR41	25p	TIP30C	60p	2N3442	140p	3N204	250p	6A 100V	80p												
7400	60p	74298	200p	4022	100p	9302	175p	74504	60p	745124	300p	AC127/8	20p	BFR79	25p	TIP31A	58p	2N3553	240p	40360	40p	6A 400V	120p												
7401	12p	74365	100p	4023	27p	9308	316p	74505	75p	745132	160p	AC176	25p	BFR80	25p	TIP31C	62p	2N3665	30p	40361	2	10A 400V	200p												
7402	12p	74366	100p	4024	50p	9310	275p	74508	75p	745133	75p	AC187/8	25p	BFR81	25p	TIP32A	68p	2N3584	250p	40364	120p	25A 400V	400p												
7403	14p	74367	100p	4025	20p	9311	275p	74510	90p	745136	225p	AF116	50p	BFX29	40p	TIP32C	82p	2N3620	48p	40408	90p														
7404	14p	74368	100p	4026	130p	9312	160p	74520	60p	745139	225p	BFX43	70p	BFX30	30p	TIP33C	90p	2N3702	3	40409	100p														
7405	18p	74390	200p	4027	50p	9314	165p	74530	60p	745157	250p	AD161/2	45p	BFX85	5	TIP33C	114p	2N3704	5	40410	100p														
7406	36p	74393	200p	4028	84p	9316	225p	74532	90p	745174	250p	AU107	20p	BFX86/7	30p	TIP34A	115p	2N3706/7	14p	40411	300p														
7407	36p	74490	225p	4029	100p	9321	225p	74537	90p	745175	320p	BC107/8	11p	BFX88	30p	TIP34C	160p	2N3708	9	40412	100p														
7408	17p	74451	150p	4030	55p	9322	150p	74538	60p	745194	350p	BC109	11p	BFW10	90p	TIP35A	225p	2N3773	30p	40413	300p														
7409	19p	74450	14p	4031	200p	9324	360p	74539	90p	745211	450p	BC117	20p	BFX50	30p	TIP35C	290p	2N3819	25p	40414	75p														
7410	15p	74452	16p	4032	200p	9328	250p	74540	90p	745260	70p	BC147/8	9p	BFX51/2	22p	TIP36A	270p	2N3820	3	40415	90p														
7411	24p	74453	100p	4035	110p	9370	300p	74586	300p	745373	500p	BC149	10p	BFX56	33p	TIP36C	340p	2N3823	70p	40416	100p														
7412	20p	74454	16p	4036	295p	9374	200p	745112	120p	745374	500p	BC157/8	10p	BFX90	50p	TIP41A	65p	2N3866	90p	40417	100p														
7413	30p	74455	25p	4039	295p							BC159	11p	BFX39	45p	TIP41C	78p	2N3902	700p	40418	100p														
7414	40p	74458	22p	4040	100p							BC192	12p	BSX19/20	20p	TIP42A	70p	2N3903/4	18p	40419	100p														
7414	90p	74459	21p	4041	80p							BC192	12p	BU104	225p	TIP42C	82p	2N3905/6	20p	40420	100p														
7416	27p	744510	20p	4042	80p							BC177/8	17p	BU105	190p	TIP54	160p	2N4037	65p	40421	100p														
7417	27p	744511	20p	4043	90p							BC178	18p	BU108	250p	TIP120	120p	2N4058	9	40422	100p														
7420	17p	744513	40p	4044	90p							BC181	30p	BU109	250p	TIP122	130p	2N4060	12p	40423	100p														
7421	40p	744514	50p	4046	110p							BC184	11p	BU125	150p	TIP142	130p	2N4061	2	40424	100p														
7422	22p	744520	20p	4047	100p							BC187	30p	BU180A	120p	TIP147	130p	2N4123/4	27p	40425	100p														
7423	34p	744521	40p	4048	55p							BC212	3	BU205	200p	TIP2955	78p	2N4125/6	27p	40426	100p														
7425	30p	744527	38p	4049	45p							BC214	12p	BU208	200p	TIP4055	70p	2N4401	3	40427	100p														
7426	40p	744529	40p	4050	45p							BC237	16p	MJ3001	225p	ZTX300	145p	TIS43	45p	40428	100p														
7427	34p	744532	27p	4051	80p							BC327	16p	E300	50p	TIS93	30p	2N4871	60p	40429	100p														
7428	36p	744537	30p	4052	80p							BC337	16p	E308	50p	ZTX108	12p	2N5087	27p	40430	100p														
7430	17p	744538	38p	4053	80p							BC338	16p	E310	50p	ZTX300	13p	2N5089	27p	40431	100p														
7432	30p	744542	70p	4054	150p							BC461	36p	MJ2501	225p	ZTX500	15p	2N5172	27p	40432	100p														
7433	40p	744547	75p	4055	125p							BC477/8	30p	MJ2955	90p	ZTX502	18p	2N5179	90p	40433	100p														
7437	35p	744551	24p	4056	125p							BC516/7	40p	MPS402	45p	ZTX504	30p	2N5191	90p	40434	100p														
7438	35p	744555	30p	4059	60p							BC528	15p	MJ3040	50p	2N4574	250p	2N5194	90p	40435	100p														
7440	17p	744573	50p	4060	115p							BC546	9p	MJ2955	100p	2N695	35p	2N5245	40p	40436	100p														
7441	70p	744574	27p	4063	120p							BC549C	18p	MJ3055	70p	2N697	25p	2N5296	55p	40437	100p														
7442A	60p	744575	36p	4066	50p							BC557B	16p	MPF102	45p	2N698	45p	2N5401	50p	40438	100p														
7443	112p	744576	45p	4067	450p							BC559C	18p	MPF103	4	2N706A	30p	2N5457	8	40439	100p														
7444	112p	744583	70p	4068	27p							BCY70	18p	MPF05/6	40p	2N708	30p	2N5459	40p	40440	100p														
7445	100p	744589	40p	4069	20p							BCY72	22p	MPS442	50p	2N918	45p	2N5460	60p	40441	100p														
7446A	93p	744586	40p	4070	30p							BD131/2	50p	MPS6534	50p	2N930	18p	2N5485	44p	40442	100p														
7447A	75p	744590	40p	4071	25p							BD139	56p	MPSA06	30p	2N1131	236p	2N5875	250p	40443	100p														
7448	80p	744592	70p	4072	25p							BD213	56p	MPSA02	50p	2N1613	236p	2N6027	48p	40444	100p														
7450	17p	744593	60p	4073	25p							BD242	70p	MPSA13	50p	2N1711	25p	2N6041	160p	40445	100p														
7451	17p	744596	110p	4075	25p							BD189	60p	MPSA20	50p	2N1702	70p	2N6044	160p	40446	100p														
7453	107p	744597	10p	4076	10p							BD232	95p	MPSA42	50p	2N2160	350p	2N6052	30p	40447	100p														
7454	17p	744509	80p	4081	27p							BD233	75p	MPSA44	50p	2N219A	30p	2N6059	325p	40448	100p														
7460	17p	744512	40p	4082	27p							BD235	85p	MPSA56	32p	2N222A	30p	2N6107	65p	40449	100p														
7470	36p	744513	90p	4086	72p							BD241	70p	MPSA70	60p	2N2369A	25p	2N6247	190p	40450	100p														
7472	30p	744514	45p	4089	150p							BD242	70p	MPSU06	63p	2N2484	30p	2N6254	130p	40451	100p														
7473	34p	744522	60p	4093	70p							BDY56	60p	MPSU07	60p	2N2646	45p	2N6290	65p	40452	100p														
7474	30p	744523	80p	4094	250p							BF200	32p	MPSU45	50p	2N2904	30p	2N6292	35p	40453	100p														
7475	38p	744527	60p	4095	95p							BF200	32p	MPSU65	78p	2N2906A	30p	2N6293	72	40454	100p														
7476	32p	744528	50p	4096	95p							BF256	70p	OC28	130p	2N2907A	30p	3N128	120p	40455	100p														
7480	50p	744526	50p	4097	340p							BF257/8	32p	OC35	130p	2N2926	9p	3N140	120p	40456	100p														
7481	100p	744532	60p	4098	120p							BF259	36p	TIP29A	40p	2N3053	30p	3N141	110p	40457	100p														
7482	84p	744533	30p	4099	200p							BFR39	25p	TIP29C	55p	2N3054	65p	3N201	110p	40458	100p														
7483A	90p	744536	55p	4100	220p																														
7484	100p	744537	55p	4101	220p																														
7485	110p	744539	55p	4102	180p																														
7486	34p	744545	120p	4103	180p																														
7489	210p	744547	220p	4104	99p																														
7490A	30p	744548	175p	4105	120p																														
7491	80p	744549	10p	4106	90p																														
7492A	46p	744550	10p	4107	60p																														
7493A	36p	744554	200p	4108	470p																														
7494	84p	744555	80p	4109	100p																														
7495A	70p	744556	90p	4110	300p																														
7496	65p	744557	60p	4114	250p		</																												

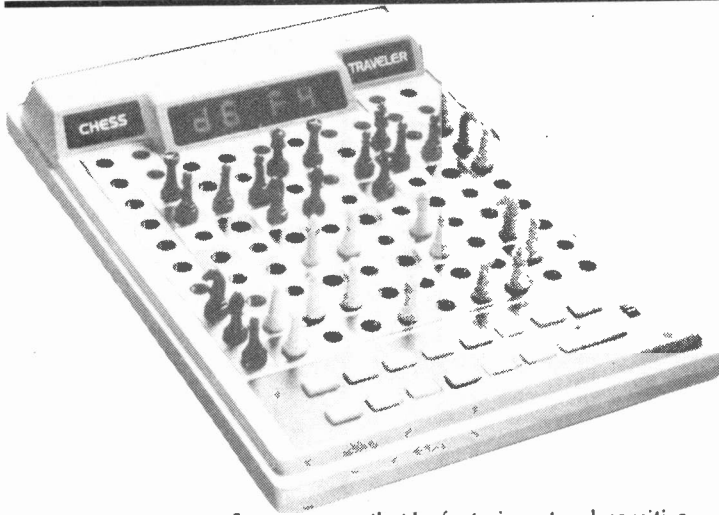

Piece Work

With the two latest additions to the successful Chess Challenger series of games, the Challenger is moving away from the concept of a chess board with a computer tacked onto the side, towards the truly electronic board. If you're wary of computers and keyboards, you may have been put off buying a chess machine up to now because of the business of entering your move on the keypad. The Sensory 8 gets round

that by featuring a touch-sensitive playing surface, by means of which the computer can 'see' the pieces and automatically enter each move. A light on each square shows the 'from' and 'to' positions. Eight levels of play can be selected and skill level can even be changed in mid-move. All the usual Chess Challenger features (position verification, problem-solving, etc.) are featured.

Following on from the Voice Chess Challenger, you can now also buy a Voice Sensory Chess



Challenger. In addition to all the Sensory 8's features, it speaks its own moves, repeats yours, calls out captures and rattles off all the board positions on command. If this dedicated dalek's voice gets a bit too much you can switch it off (unlike human opponents).

The voice version also has a built-in chess clock showing the time left for you or the computer and the elapsed time for the game. You can buy a plug-in printer to provide a copy of every move in the game. Sensory 8 sells for £129.95 and Voice Sensory for

£279.95.

Aimed at chess players with itchy feet, Ingersoll Electronics have introduced the Chess Traveller, featuring eight levels of play. The pieces push into holes on the board (with spare holes for taken pieces) and can be covered by a perspex top at half time or between games. Through the keyboard you can select skill level, verify board positions, solve problems and set up specific openings. Power is from mains or batteries. Chess Traveller retails at around £50.

Oops

Space Invasion Game

In the Space Invasion Game main circuit diagram (November 1980, p.66/67) pin 12 of IC11b is shown connected to earth. It should be connected to pin 34 of the CPU, IC15. All new boards supplied by Tangerine Computers will have this modification, so check your board before making any changes.

On the same diagram, the ICs are identified in two ways. Our own IC1, IC2, etc. notation identifies the components as they appear on the Parts List. The circled legends (A1, A2, B1, H4, etc.) are the positions of the ICs shown on the PCB supplied by Tangerine Computers.

IC20 pins 20 and 21 should be swapped over. The label adjacent to IC7c was ringed in error — it is diode D2 not position D2.

The Inch War

Length may not be everything, but JVC want to know how important it is to video tape recorder owners. They are shortly to test market four hour VHS tapes in the UK. As it is a test exercise, the new E240 tapes will be in very short supply until the experiment is complete and demand is established.

Cassette Interface

In the component overlay of the Cassette Interface project (October 1980 p.65 Fig.5) the junction of R4-R5-R6-C4 is shown connected to pin 1 of IC6. Instead it should be connected to pin 2 of IC6. The circuit diagram is correct but the foil pattern on p.109 is incorrect. Simply break the track connecting the above components to pin 1 and solder a new link across to pin 2. The Buylines information omitted from this project was included in Digest in the November issue.


Radio Control

In the Radio Control Buylines section (October 1980) the prices quoted for the transmitter and receiver do not include PCBs, receiver case or SLM three-pin gold-plated servo connector block. Prices including these items are £8.57 for the transmitter kit and £14.26 for the receiver kit (including VAT) from Ambit International.

JVC expect the demand to come from owners of their new HR7700 recorder, with which every absentee landlord worth his salt can tape up to eight programmes from different channels in a fortnight.

So, if you like the idea of four hour VHS tapes, seek out the elusive JVC test retail outlets and form an orderly queue with piggy banks at the ready.

HELP! ETI NEEDS YOU!

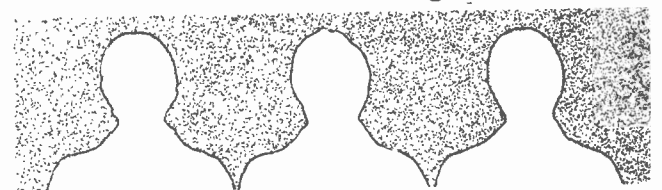

Could you be a Project Engineer for ETI? — the person who fills this position will be able to design and build up projects to the standard of finish ETI readers are used to seeing in their magazine. This calls for someone with a good knowledge of circuit design and with the patience to carry the design through to a finished state. Existing staff are available to assist in all aspects of design work. The easiest part of the job will be writing up the project once it is completed. None of the present ETI technical staff were journalists previous to joining, and no-one has found the writing a difficult task.

We have no preconceived notions of age required.

Applications should reach us as soon as possible with C.V.

Apply in writing to:
The Editor,
Electronics Today International
145 Charing Cross Road,
London WC2H 0EE



Airwaves

Sony technologists have recently developed what they consider to be "the most advanced portable communications receiver in the world." The ICF-2001 receiver is no bigger than a hard-cover book and has the capability of capturing English-language short-wave programmes from Australia to Finland, foreign language

services from all four corners of the earth, ship-to-shore, amateur and Citizens Band as well as standard medium-wave, long-wave and FM broadcasting. It has a built-in minicomputer instead of a tuning dial, so instead of searching for the frequency of your favourite (or a new) station, with this model you simply punch in the frequency you require on a pocket calculator style keyboard, or instruct it to scan wave bands and stop automatically each time it reaches an 'on air' transmission. If it's a station you want to listen

to frequently, you simply enter it into the computer memory and recall it by pressing one of the six 'preset' buttons. And that's not all! Other features include dual PLL synthesiser circuit for stable reception, auto-scan tuning, manual tuning, preset tuning, liquid crystal multi display, electronic 90 minute sleep timer and powerful 6 W output. The ICF-2001 sells for a mere £150. For further information contact Sony (UK) Ltd, Pyrene House, Sunbury Cross, Sunbury on Thames, Middlesex, TW16 7AT.

Royal Award

On September 11th this year HRH the Prince of Wales launched a new award — a challenge to industry and people with new ideas. The Prince of Wales Award for Industrial Innovation will be presented in June 1982 following a competition promoted and organised by the BBC programme 'Tomorrow's World'. The aim is to encourage people with innovative ideas to get them accepted by an industrial backer, eventually to have their ideas taken into production. The first step will be to invite people to send their ideas to 'Tomorrow's World' for scrutiny. The competition is open to institutions and individuals

alike. The closing date for this first stage is December 31st 1980.

Certificates will be presented to the winners (who will be expected to have found a commercial backer to qualify) at the end of the current series of programmes. During the following twelve months those ideas will be developed and by June 1982 the judges will decide who has made the most promising, enterprising and exciting commercial development. The winner will be awarded the Prince of Wales Award for Industrial Innovation and Production for that year. For further details contact: Unit Manager, 'Tomorrow's World', BBC TV, London, W12 8QT.

Project 80

The number of inquiries we receive on the Project 80 modular synthesiser seems to be inversely proportional to the number of shopping days left to Christmas. Is it going to finish in the December edition? Will it be miraculously transformed into Project 81 as from the January 1981 edition? Are we going to continue to support it?


Well, it won't be finished in this issue and it won't be transformed into Project 81, but we certainly are

going to continue supporting this very, very popular series. We are going to bring together in one magazine all the Project 80 articles published to date (with new additions or amendments, where necessary) together with three new modules, the keyboard design, the keyboard controller, setting up procedures and a brand new section on module and whole-system applications written by the system designer, Charles Blakey.

Watch out for the Project 80 handbook on the bookstalls in January.

Pocket Box

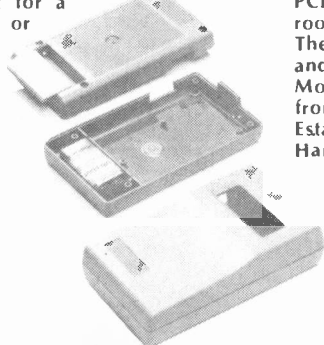A new pocket-sized, hand-held case is now available from Vero Electronics. With a 20 x 50 mm cut-out for a display or switch



panel and an integral battery compartment (PP3), it's ideal for remote control handsets and hand-held instruments. The top section will take a 71 x 107 mm PCB and the bottom section has room for a 56 x 105 mm board. The two sections snap together and are secured by four screws. More information is available from Vero Electronics, Industrial Estate, Chandler's Ford, Eastleigh, Hampshire SO5 3ZR.

Boffin Badge

The following is not to be mistaken for an ETI special offer. Address all your orders clearly to the Physics Dept. at Imperial College.

The Physics Dept.
Imperial College

Dear Sir,

This is an 'unsolicited Press Release to inform you of my latest, and rather wacky, entrepreneurial venture.

Available within the next fortnight, bona fide physicists will be able to have their very own badges with the legend:


'I am A. S. Lipson'.

The wearing of the above artefact will, of course, raise the proud owner to the very pinnacle of his subject. It is sure to become the fashionable attire for discerning readers of this publication, so be advised — order today.

Yours faithfully

The Mysterious Physicist

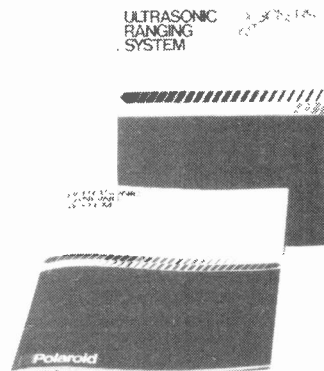P.S. Discounts are naturally available on large orders.



Sound Designing


The ultrasonic rangefinding system used in Polaroid's SX-70 sonar focusing cameras since 1978 is now available separately as a designer's kit. Polaroid can supply an attractive kit containing two sonar transducers, the necessary circuitry to convert time into distance, two 6V Polapulse batteries, a LED readout and a technical manual. Both of the transducers emit and receive four-frequency ultrasonic signals.

Applications? The system has already been used in the unlikelyst of places. When Gossamer Albatross crossed the Channel by pedal power, it had to be flown at a precise height above the brine. However, none of the commercially available altimeters give accurate readings below about 20 m. Gossamer wave-hopping was achieved using a

custom-built altimeter incorporating the Polaroid system.

Ultrasonic rangefinding could be useful to a pilot of any aircraft manoeuvring in limited air space close to the ground or to a driver who doesn't have all-round vision from his cab. In fact, any situation where a measurement of distance has to be converted into an alarm signal or a control signal could put the Polaroid kit to good use. Several medical applications spring to mind immediately — automatic focusing glasses (especially for cataract patients), sonar cane for the blind, obstacle warnings for wheelchair-users, etc.

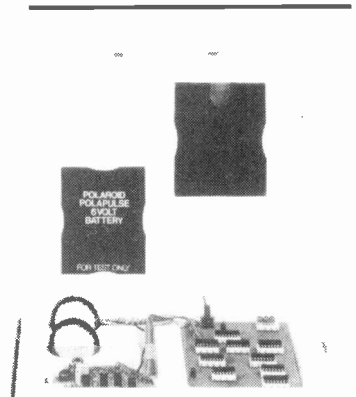For more information on the Polaroid Designer's Kit, contact Polaroid (UK) Ltd, Ashley Road, St Albans, Hertfordshire.




**NEXT
MONTH**

electronics today

INTERNATIONAL

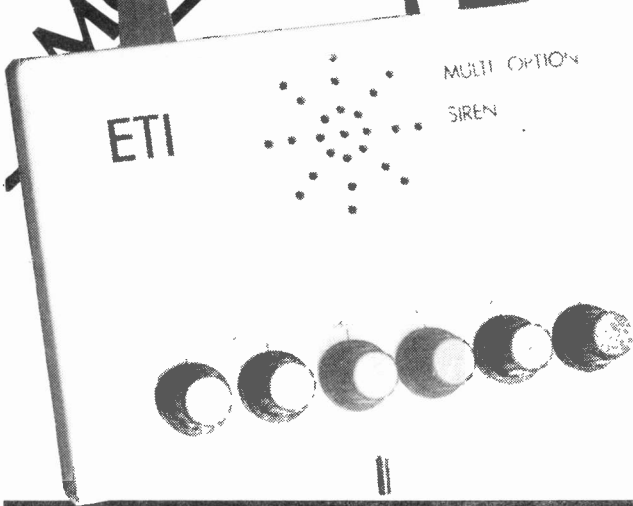Look out for the January issue on sale December 5th




DIGITAL TACHO/OVER-REV INDICATOR

Keep track of your revs with the ETI Digital Tacho and Over-Rev Indicator. Watch the revs climb the LEDs in two ranges up to a maximum of 10,000 RPM. Set the rev limit of your choice. When you exceed it, the display flashes and continues to give a true read-out — suitable for most makes of cars with four, six or eight cylinders.

FM TUNER

This attractive FM Tuner, built around the 7254 tuner module from Ambit, has been designed to match the popular Audiophile 4000 Amplifier. It offers switch selectable muting, AFC and mono/stereo. The 200 mV output can be fed directly to the input of any stereo audio preamplifier. Tuning is selected by switch or by a conventional rotary control. The design also incorporates a search and lock facility to find strong FM broadcasts in the 87.5 to 104.5 MHz band.

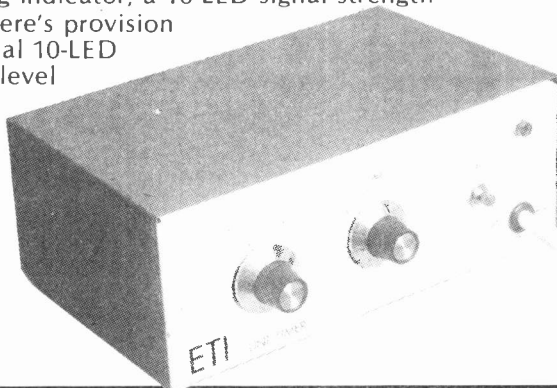And that's not all — the unit is fitted with a 20-LED tuning indicator, a 10-LED signal strength meter and there's provision for an optional 10-LED stereo audio level indicator.



MULTI-OPTION SIREN

You can build a circuit that sounds like Kojak on his way to the lollipop store; you can knock up a little black box to make a few sci-fi sound effects; you can probably even find a device to imitate a trimphone. But our Multi-Option Siren does it all. This versatile box of tricks gives you full control of tone, vibrato and shape modulation and vibrato depth and rate. That little lot offers almost limitless combinations of sounds. As if that wasn't enough, you can also select ramp or pulse output.

PULSE GENERATOR

Our battery operated delay/tone burst generator is an accurate and reliable piece of test gear, offering tone burst, pulse positive and pulse negative outputs. It features three clock generator ranges, six pulse delay ranges (from nanoseconds to milliseconds), six pulse width ranges (also from nanoseconds to milliseconds) and three tone ranges covering 1 Hz to 1 MHz in decade steps.

ELECTRONICS IN PHOTOGRAPHY

Microminiature electronic circuits and microprocessors — they've found their way into most aspects of work and play. Photography is no exception. Next month we look at what has happened to the humble 35 mm camera. You'll be amazed at what the manufacturers can pack into its compact frame.

GENERAL PURPOSE TIMER

Whether you want to time an egg or find out how long it takes to read ETI from cover to cover, our General Purpose Timer can solve your problem. There are two ranges — 1 to 10 minutes and 10 to 100 minutes. The relay output will handle up to 10 A. With the flick of a switch you can select timed make or timed break, with a neon indication of the output state — an economical project with a whole host of applications around the home and workshop.

Articles described here are in an advanced state of preparation. However, circumstances may dictate changes to the final contents.

FOUR INPUT MIXER



Four into one will go with this mini-mixer. Why not build one for your band today? Design and development by John Fitzgerald.

If you are in a band and your PA has a range of inputs you may wonder why you need a mixer. Well one of the advantages is that when your bass player thinks he is not loud enough to be heard over the rest of you, it's up to someone else to turn him up! Otherwise, you can so easily get that snowball effect where one musician turns up the volume only to be followed by all the rest and so on until every sentient being within earshot suffers premature deafness (pardon?).


Many bands these days seem to have started on nothing and are maintained on a shoe string. If yours falls into this category, then this is the project for you. No-one is going to claim it's hi-fi but it is cheap. Using 741 op-amps will produce plenty of power versus cost.

HOW IT WORKS

The heart of the circuit is IC2, an op-amp connected as a conventional 'virtual earth' summing amplifier. This stage mixes the input signals and also has a gain of 10 to compensate for the insertion loss of the passive tone control network. There are three high level inputs and one low level which is input to IC1. This stage provides non-inverting amplification with a gain of about 20. Independent volume controls are provided for each input and the signals are mixed in IC2 before being passed to the tone control network. This provides a 40 dB range of control with an insertion loss at midband of -20 dB.

This output from the tone control is AC coupled to unity-gain voltage follower IC3. AC coupling avoids the problem of wiper 'track noise', which would result from the irregular capacitor charge and discharge currents. R16 is inserted in the output of IC3 to isolate the op-amp from the large capacitive load presented by a long length of screened cable. Potentiometer RV7 provides overall volume control and capacitors C14 and C15 decouple the power supply lines. Two 9 V batteries provide power for the unit and current consumption will be just a few milliamps.

Fig.1. Circuit diagram.

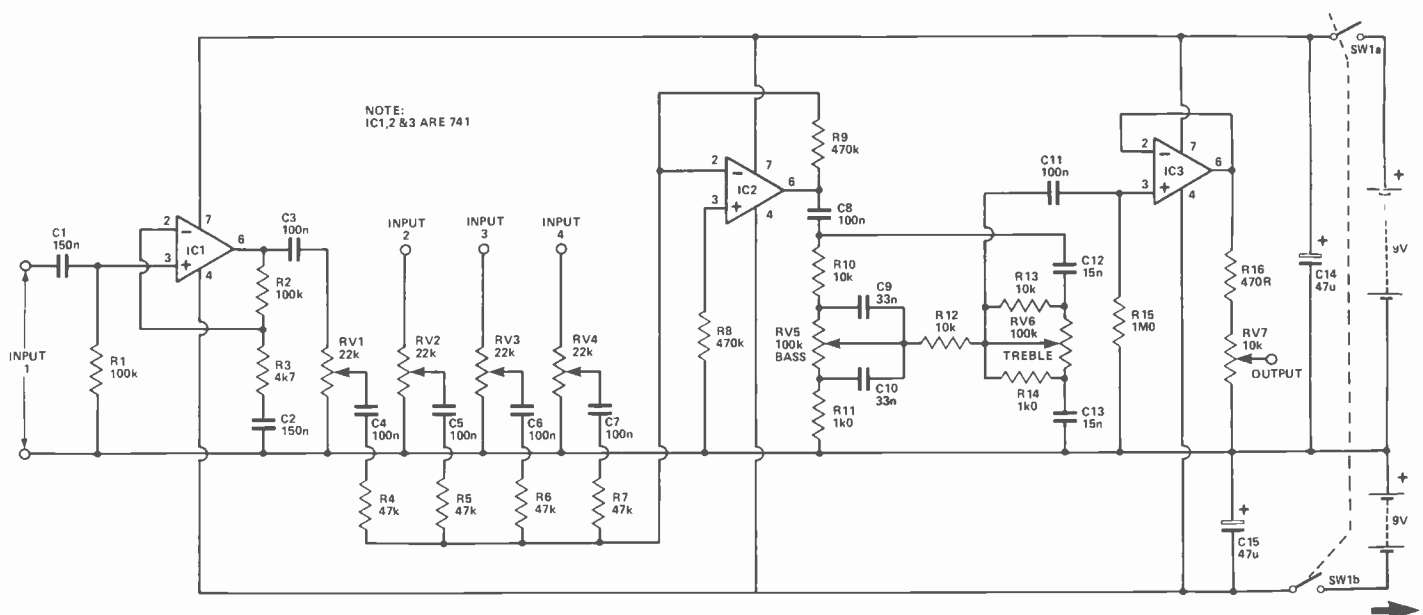

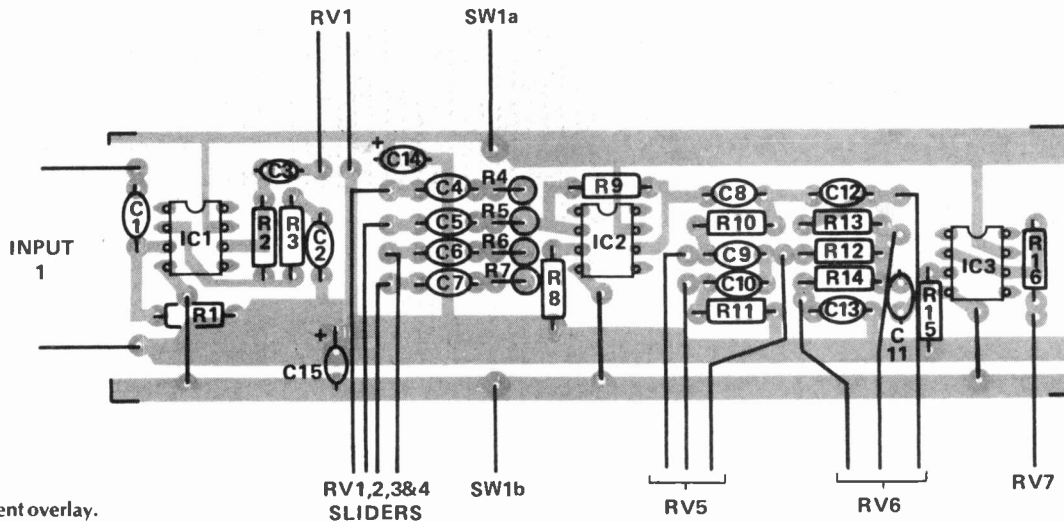


Fig. 2. Component overlay.

PARTS LIST

Resistors all ¼W 5%	
R1,2	100k
R3	4k7
R4,5,6,7	47k
R8,9	470k
R10,12,13	10k
R11,14	1k0
R15	1M0
R16	470R
Potentiometers	
RV1,2,3,4	22k logarithmic
RV5,6	100k logarithmic
RV7	10k logarithmic
Capacitors	
C1,2	150n polycarbonate
C3,11	100n ceramic
C4,5,6,7,8	100n polycarbonate
C9,10	33n polycarbonate
C12,13	15n polycarbonate
C14,15	47u 16 V tantalum
Semiconductors	
IC1,2,3	741
Miscellaneous	
Case, connectors, batteries, DPDT switch, etc.	



Construction

We built our unit into a small plastic case and mounted all the pots on the aluminium top cover, making the required connections with screened cable. Take care not to produce an 'earth loop' when connecting up. The remaining components can be mounted on our PCB; only three wire links are required to supply the op-amps' negative supply. We used polycarbonate capacitors mostly, taking advantage of their small size and good characteristics, though polyester types can be substituted. There are no special precautions to take. Just make sure you put the ICs in the right way up and get the polarity of the two tantalum capacitors right.

Remember, if you ever reverse-bias a tantalum cap by more than about 3 V it's dead certain that you'll have blown it up and it'll no longer be a capacitor; more a low-value resistor with the inevitable effect on circuit operation. No problems with this project, though. Simply build it, fix it and mix it!

BUYLINES

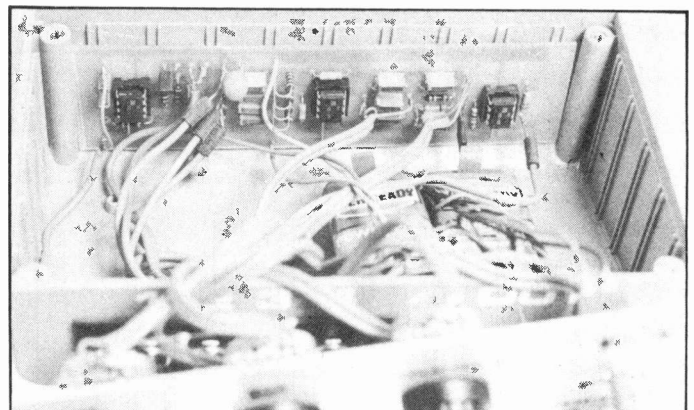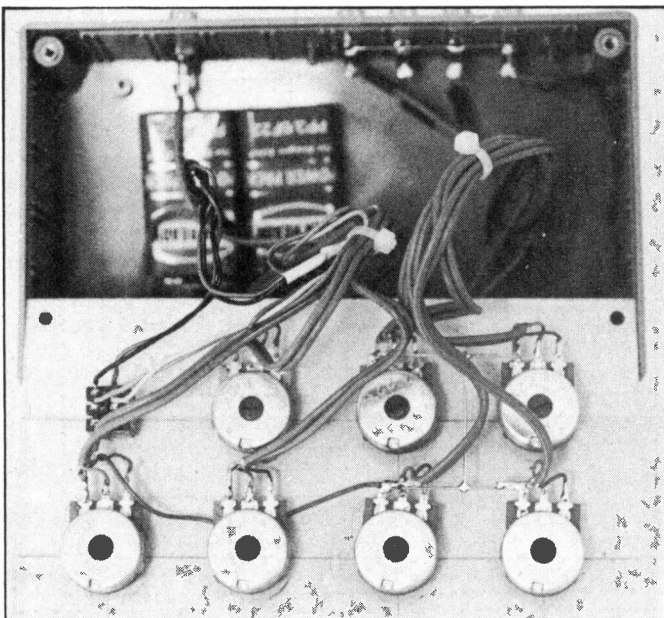All the components for this project should be readily available. In case of difficulty, the polycarbonate capacitors are available from Watford Electronics or Electrovalue.



The PCB (above) tucks neatly away at one end of the case. Make sure the case is deep enough to allow clearance of the batteries and potentiometer bodies.

Front panel control layout (left).

ETI

DORAM

DORAM ELECTRONICS LTD

Fitzroy House, Market Place,
Swaffham, Norfolk, PE37 7QH.

TEL: (0760) 21627 TELEX: 817912
VAT Reg: 324 5604 75

PROJECT PACKS

Projects for beginners

Clap switch (79026) Responds from a hand clap to switch on an electrical appliance	£6.60
Simple Sound effects (79077) Strange noises from a very simple circuit, loudspeaker included.	£5.70
Pools predictor (79053) An analogue computer that may win you a fortune.	£8.15
Talk Funny (80052) A ring modulator circuit that produces very strange results when fed with a human voice.	£9.60
Pest Pester (80130) An electronic insect repellent.	£2.35
Steam train sound effects (80019) Simulates the sound of steam and whistle.	£6.50
Electronic Nuisance (80016) Makes an annoying noise, but only in the dark!	£3.85
Cackling Egg timer (9985) An egg timer with a difference, it clucks like a hen.	£7.20

New projects

Melody Maker (80502) An electronic musical box that can play 27 tunes with organ or piano-like quality.	£23.50
LCD Counter (80117) Simple to construct frequency display for AM and FM bands.	£41.20
Linear Thermometer (80127) Simple but effective meter reading thermometer using a diode as sensor.	£13.45
Precision Power Unit (80514) Produces accurate reference voltages at presettable current limits up to 2 Amps.	£48.65
Programmable Slide Fader (81002) Mixes audio signals on tape with operation of two slide projectors.	£46.50

Audio projects

Top-preamp (80031) Mini, all IC preamplifier for use with most power amplifiers.	£34.40	
Topamp (80031) Hybrid audio power amplifier uses Philips modules for high fidelity performance. Two power levels: OM931 (output 30 Watt)	£18.50	
	OM961 (output 60 Watt)	£33.40
Stentor (79070) A high power portable amplifier for PA use.	£30.00	
Assistentor (79071) A preamplifier designed for Stentor which can also be used as a speech compressor for radio transmission.	£7.00	
Parametric Equalizer (9897) A modular system of construction to suit your equalisation requirements. Filter section (9897-1)	£6.45	
	Tone section (9897-2)	£5.20
Elektornado (9897) A single board design that can be used as either a single 100 Watt amplifier or two 50 Watt amplifiers.	£19.50	
UAA180 LED meter (9817) A two channel voltage display unit.	£13.00	
Peak Programme Meter (9860) To be used with UAA180 LED meter to give PPM display.	£3.70	
Audio Analyser (9932) An analyser that can pin point the deficiencies in an audio chain.	£14.80	
Stereo dynamic Preamp (80532) A low noise high quality disc preamplifier.	£5.20	
STAMP (80543) Super tiny amplifier with up to 1 Watt output.	£3.75	
Consonant (9945) A high quality audio control amplifier.	£34.65	
Preconsonant (9954) A preamplifier for the disc input of the Consonant.	£5.75	
Luminant (9949) A two channel LED display designed to show output levels in the Consonant system.	£20.70	

Car projects

Car Battery Charger (79517) Reliable and safe charger for all types of lead-acid batteries.	£21.70
Transistor Ignition (80082) The most significant advantages of other systems combined in one.	£20.45
Dipstick Probe (80102) Direct warning of high oil temperature. State long or short dipstick required.	£11.25
Intelligent Wiper Delay (80086) Can be set to produce delayed wipes at any predetermined interval.	£15.85
Battery Protection (80109) Automatically switches off the head lamps of a parked car.	£5.15
Battery Voltage Indicator (80101) LEDs indicate the condition of your battery.	£6.85
Active Car Aerial (80018) Improves the sensitivity of AM and FM radio reception in your car.	£13.85

Music projects

Chorosynth (80060) A cheap mini synthesizer. Send for details.	£57.90
Elektor Vocoder (80060) The first Vocoder designed to be built in kit form. 10 Channel modular construction.	£162.50
Analogue Reverberation Unit (9973) Uses a SAD1024 which can produce a delay up to 100mS.	£27.70
Guitar Preamp (77020) With three tone controls.	£6.50

Projects for the home

Touch Dimmer (78065) Room lighting controlled by a single touch.	£6.80
Ioniser (9823) Produces a high concentration of negative ions.	£9.55
Loudspeaking telephone amplifier (9987) Amplifies without direct connection.	£11.50
Proximity Detector (9974) Detects by electric field change movement in a room.	£9.80

Our Project Packs include the electronic components, the PCB, sockets and solder together with assembly instructions. Cases, knobs etc can be supplied as extra items if required. This is only part of our wide range of projects. See our catalogue for details of other projects that we can supply. You can also ring our number between 12.30 p.m. and 1.30 p.m. any weekday for a recorded announcement of any new items we have available.

Send 40p for catalogue

HOW TO ORDER

Send a cheque or postal order to DORAM ELECTRONICS LTD or write or ring with your Access account number. All our prices include VAT. Overseas customers please deduct 15%. Please add 40p to your order for postage and packing. An answering service is available to take your orders outside our normal office hours. Mail Order service only.

a de boer company



NAME _____

ADDRESS _____

Britain's first com puter kit.

The Sinclair ZX80.

£79.95

Price breakdown:
ZX80 and manual: £69.52
VAT: £10.43
Post and packing: FREE

Price includes many valuable components: see list below.

It's the same old story... a new computer kit is introduced, now made in Britain. You pick the ZX80. You do so with confidence because it's built for excellent value. So it's no wonder that you say it's better than all previous personal computers. And the response from kit owners has been tremendous.

To help you appreciate its value, the price is shown above with and without VAT. This is so you can compare the ZX80 with competing kits that don't appear with inclusive prices.

'Excellent value' indeed!

For just £79.95 (inc. VAT) and you get everything you need to build a personal computer at home. PCB with IC sockets for all ICs, case, leads for direct connection to a cassette recorder and television (black and white or colour), everything.

Yet the ZX80 really is a compact, powerful full-facility computer, matching or surpassing other personal computers at several times the price.

The ZX80 is programmed in BASIC, the world's most popular computer language for beginners and experts alike.

The ZX80 is pleasantly straightforward to assemble. Using the type of components you immediately recognise, with a good TV set connected to your TV, direct to an appropriate power source, and you're ready to go.

Your ZX80 kit contains...

- Printed circuit board, with IC sockets for all ICs
- Complete components set, including all ICs, all manufactured by selected world leading suppliers
- New rugged Sinclair keyboard, tough, sensitive, wipe clean
- Ready moulded case
- Lead-in wires for connection to a cassette TV and cassette recorder (Programs can be SAVED and LOADED on to a portable cassette recorder)
- FREE course in BASIC programming and user manual
- Optional extras**
- Mains adaptor, of 600 mA at 9V DC nominal unregulated (available separately - see coupon)
- Additional memory expansion boards, allowing up to 10K bytes RAM* (Extra RAM chips also available - see coupon)

*Use a 600 mA at 9V DC nominal unregulated mains adaptor. Available from Sinclair's dealers (see coupon)

The unique and valuable components of the Sinclair ZX80.

The Sinclair ZX80 is the best value personal computer. Quite apart from its exceptionally low price, the ZX80 has two unique advantages: the Sinclair BASIC interpreter and the Sinclair teach-yourself BASIC manual.

The unique Sinclair BASIC interpreter offers remarkable programming advantages:


- **Single key touch key word entry:** the ZX80 eliminates a great deal of tiresome typing. Key words (FOR, PRINT LIST, etc.) are entered on a single key only.
- **Line wrap:** Only lines with correct characters are accepted into programs. A cursor displays characters late, and prevents you from entering complicated programs with only one hand when you try to fit them.
- **Excellent string handling capability:** takes up to 255 characters of any length. All strings can include special characters (e.g. comma). The ZX80 also has string input to make it easy to enter what is necessary. Strings do not have to be dimensioned.
- **10 x 20 matrix dimension arrays**
- **10000 x 1 characters up to 20**
- **Variable names of any length**
- **10000 Boolean expressions, etc.**
- **Fast, precise, power fed facilities,** allows a word of code to be written in 10 program lines.
- **Responsive function keys for games and other codes,** as well as more serious applications.
- **User defined program entry**
- **PCB and ROM enable entry of machine code instructions.** 128 bytes jump to a user machine code sub routine.
- **High resolution graphics with 22 standard program lines.**
- **Microchips are fitted in a reverse under protuberance.**
- **Lines of unlimited length.**

Fewer chips, compact design, volume production - more power per pound!

The ZX80 owes its remarkable low price to its remarkable design: the whole system is packed on to fewer, newer, more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system, and monitor. And the ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer - typically storing 100 lines of BASIC. (Key words occupy only a single byte.)



The display shows 32 characters by 24 lines. And Benchmark tests show that the ZX80 is faster than all other personal computers.

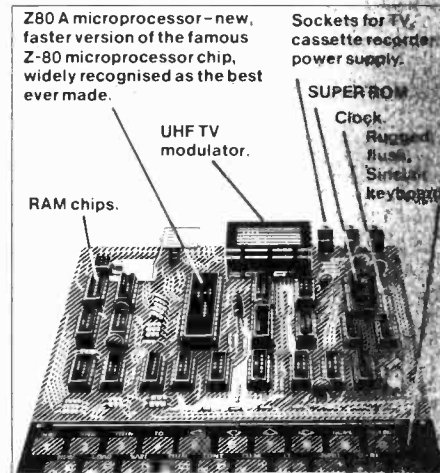No other personal computer offers this unique combination of high capability and low price.



ETI DECEMBER 1980

plete

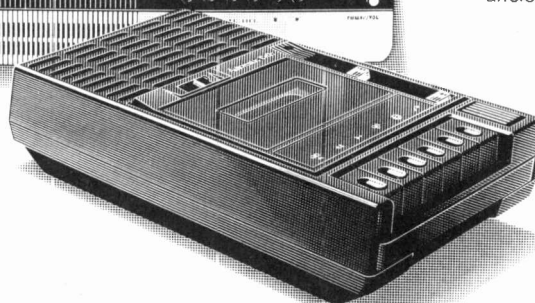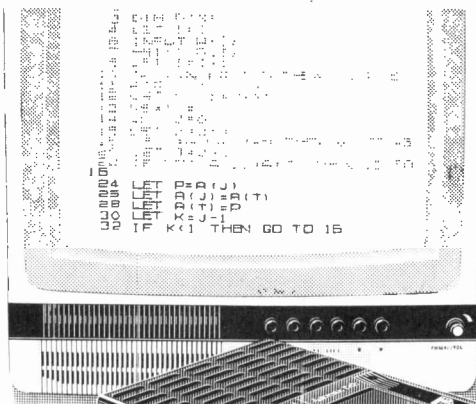

ZX80 software—now available!

See advertisements in Personal Computer World, Electronics Today International, and other journals.

New dedicated software—developed independently of Science of Cambridge—reflects the enormous interest in the ZX80. More software available soon—from leading consultancies and software houses.

The Sinclair teach-yourself BASIC manual.

If the specifications of the Sinclair ZX80 mean little to you—don't worry. They're all explained in the specially-written 128-page book free with every kit! The book makes learning easy, exciting and enjoyable, and represents a complete course in BASIC programming—from first principles to complex programs (Available separately—purchase price refunded if you buy a ZX80 later.) A hardware manual is also included with every kit.

The Sinclair ZX80. Kit: £79.95. Assembled: £99.95. Complete!

The ZX80 kit costs a mere £79.95. Can't wait to have a ZX80 up and running? No problem! It's also available, ready assembled and complete with mains adaptor, for only £99.95.

Demand for the ZX80 is very high—use the coupon to order today for the earliest possible delivery. All orders will be despatched in strict rotation. We'll acknowledge each order by return, and tell you exactly when your ZX80 will be delivered. If you choose not to wait, you can cancel your order immediately, and your money will be refunded at once. Again, of course, you may return your ZX80 as received within 14 days for a full refund. We want you to be satisfied beyond all doubt—and we have no doubt that you will be.

sinclair ZX80

Science of Cambridge Ltd
6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Tel: 0223 311488

ETI DECEMBER 1980

ORDER FORM

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Remember: all prices shown include VAT, postage and packing. No hidden extras.
Please send me:

Quantity	Item	Item price £	Total £
	Sinclair ZX80 Personal Computer kit(s) Price includes ZX80 BASIC manual, excludes mains adaptor	£79.95	
	Ready-assembled Sinclair ZX80 Personal Computer(s) Price includes ZX80 BASIC manual and mains adaptor	£99.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated)	8.95	
	Memory Expansion Board(s) (each one takes up to 3K bytes)	12.00	
	RAM Memory chips—standard 1K bytes capacity	16.00	
	Sinclair ZX80 Manual(s) (manual free with every ZX80 kit or ready-made computer)	5.00	

NB Your Sinclair ZX80 may qualify as a business expense

TOTAL £

I enclose a cheque/postal order payable to Science of Cambridge Ltd for £ _____

Please print

Name Mr/Mrs/Miss _____

Address _____

ETI/12/80

BANDPASS AND BEYOND

Here's some more from Mr. Orr. Our circuit specialist looks at the development of bandpass design, switched capacitor techniques and some new ICs.

Many machines such as spectrum analysers and vocoders use analysing filter banks, these are often quarter octave devices extending over six octaves. If quarter octave filtering is to be successful then the bandpass filter responses must be very sharp, having almost flat tops and a fast roll-off slope at either side. A poor slope would mean that the filter bank would not be able to resolve incoming signals; for example a sinewave might give a high output in several of the channels. Also, a very peaky response would give large interfilter 'dips' in the overall response (Fig.1). An approximation to the square ideal response can be obtained by using multiple tuned filters. The response of a single pole bandpass filter is shown in Fig.2.


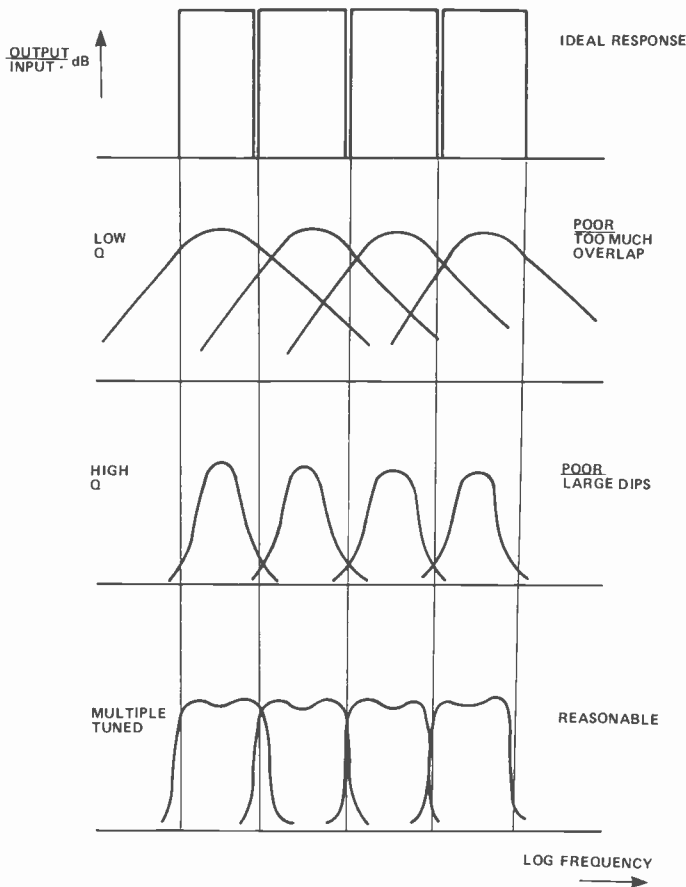


Fig.1. Various responses of an analysing filter bank.

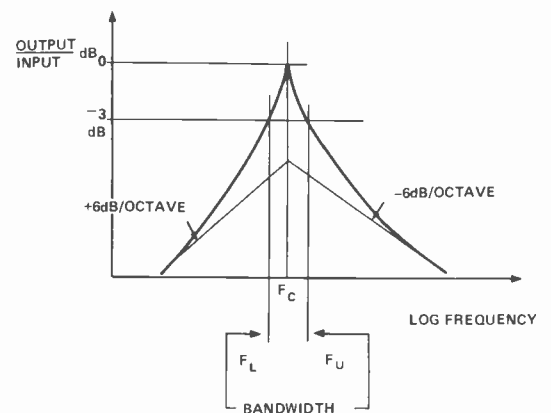

$$3\text{dB BANDWIDTH}=(F_U-F_L)$$

$$Q \text{ FACTOR}=\frac{F_C}{(F_U-F_L)}$$

$$\text{ALSO, } F_C \approx \sqrt{(F_U F_L)}$$

$$\text{FINAL ROLL OFF SLOPES}=\pm 6\text{dB/OCTAVE}$$

Fig.2. Single pole bandpass response.

By Design

When designing bandpass filters it is important to decide what type of filters to use. Figure 3 shows two bandpass responses. Response A is a peaky filter, whereas B has a flat top to it, but still has the same roll off as A. One sensible design solution would be to use bandpass filters for A, and a highpass/lowpass structure for B. A rule of thumb for making this decision is to calculate the fractional bandwidth:-

$$\frac{F_U - F_L}{F_U \times F_L}$$

If this is greater than unity then use lowpass/highpass filters, if it is less than unity use multiple tuned bandpass filters. Some standard bandpass filter designs are shown in Fig.4. The multiple feedback circuit requires only one op-amp, but is limited to low Q operation (less than 5) and the centre frequency and Q are interactive.

R _A	R _B	C	F ₁	Q	R _C	R _D	C	F ₂	Q	
3k6	360k	15n	290Hz	5	5k1	510k	15n	205Hz	5	FILTER D
1k8	180k	15n	580Hz	5	2k55	255k	15n	410Hz	5	FILTER E

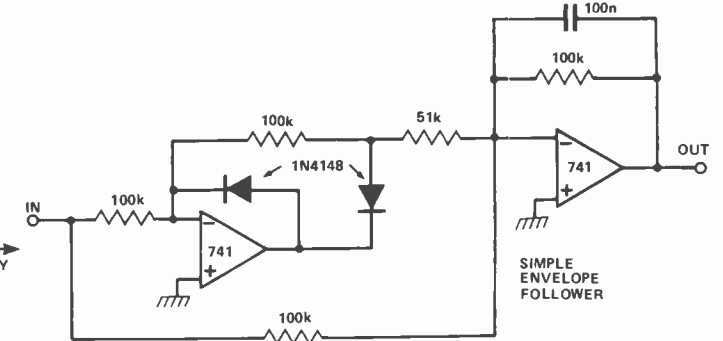
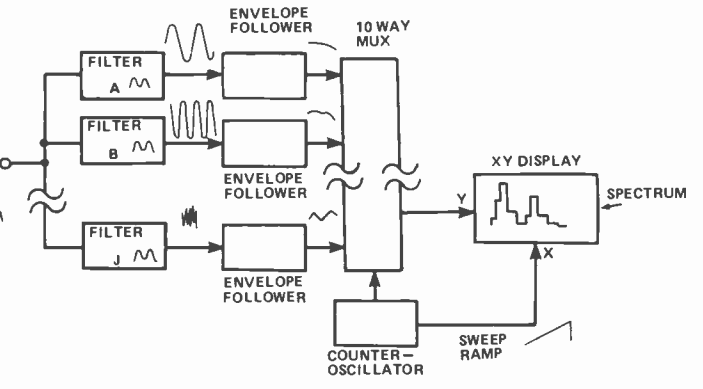
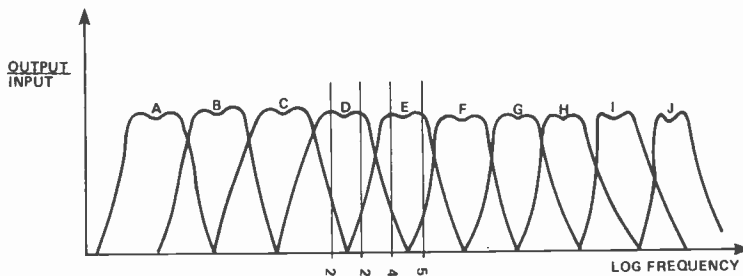
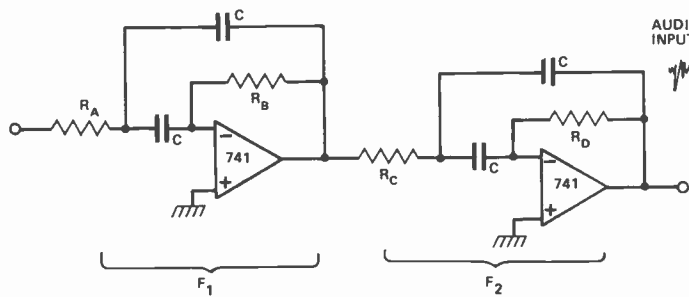


Fig. 6. An analysing filter bank suitable for a spectrum analyser. a) Circuit for each of the ten filter stages (A to J), and component values for two of the stages. b) Graph of the ten filter responses. c) Block diagram of the spectrum analyser and a suitable circuit for the envelope follower.

Other Design Applications

Figure 7 shows a design for a parametric audio equalizer. This device has variable cut and lift and a resonance and frequency control. The resonance control is arranged such that as the Q increases, the input signal is attenuated (RV2a), thus maintaining the same overall gain at resonance, independent of the Q setting. The filter is a state variable design which is situated in the feedback/feedforward loop of an op-amp. Thus RV3 controls whether overall response is a bandpass cut or lift.

The resonant frequency is tuned by RV1 and SW1 is used to switch frequency ranges. The Q factor is set by RV2.

The TCA580N (Signetics) is an IC that can be used to simulate an inductance and in doing so may be used to synthesize many conventional LCR filter circuits (Fig.8). The device has a pair of floating input terminals which generate the impression of being an inductor. This inductor is programmed by three passive components, R_{C1} , R_{C2} , C_2 . By connecting a capacitor (C_1) across the input terminals, a parallel resonant circuit (C_1L) is produced.


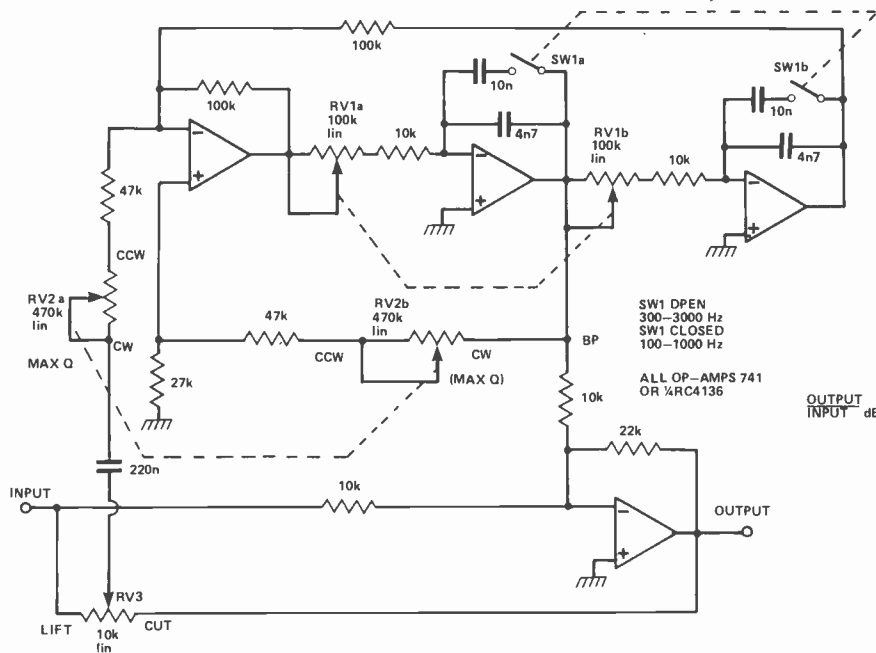


Fig. 7. A parametric audio equaliser with variable cut and lift and a resonance and frequency control.

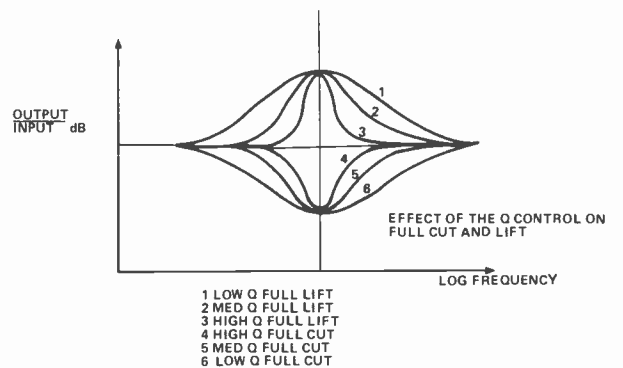

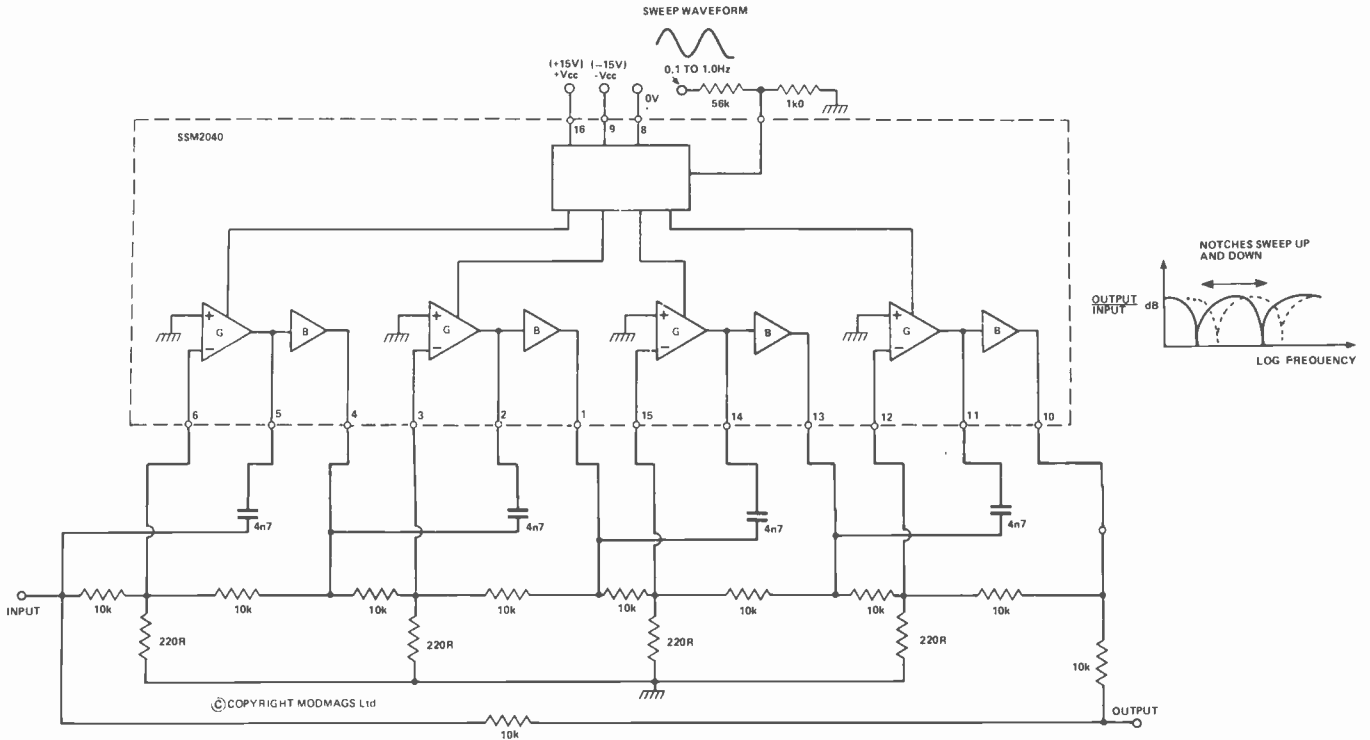


Fig.10. The SSM2040 connected as a two-notch phasing unit.

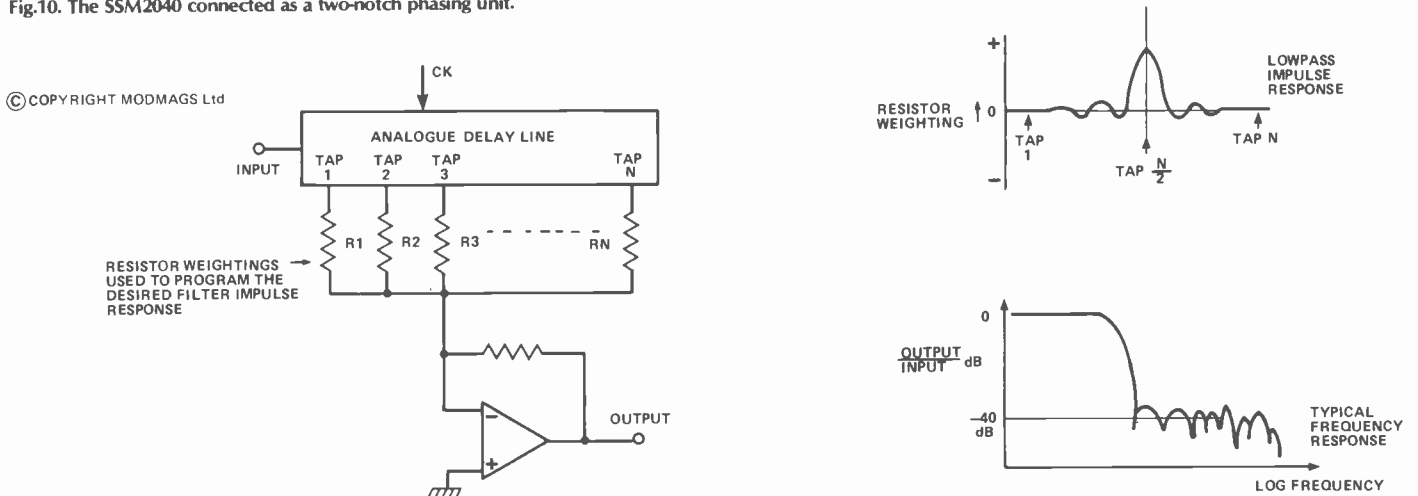


Fig. 11 The transversal filter, with graphs of impulse and frequency responses for a lowpass design.

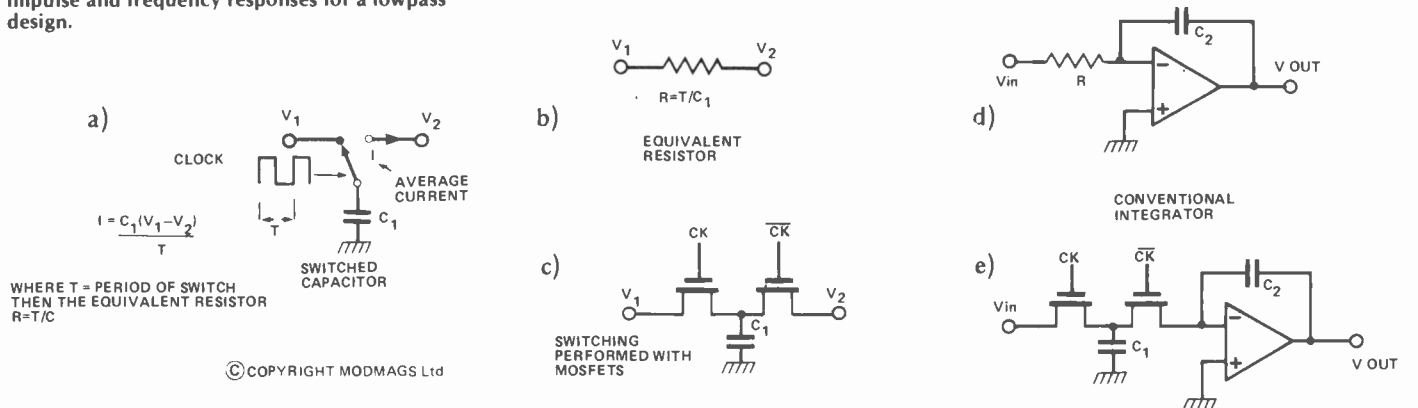


Fig.12. Switched capacitor filters. a) Basic circuit. b) The equivalent resistor. c) Practical design using MOSFETs. d) Conventional integrator. e) Replacing R with a switched capacitor enables a filter to be easily produced in IC form.

Recent Monos

A more recent monolithic device is the switched capacitor filter, which can be used to implement many standard lowpass and bandpass filter structures, Fig.12. The problem with producing monolithic recursive filters is that stable high tolerance components such as resistors and capacitors are very difficult to make, and the filter performance depends heavily upon these tolerances. However, it is possible to simulate resistors with switched capacitor techniques. With the switch as shown in Fig.12a C_1 is charged up to V_1 . When the switch is thrown to its other position the capacitor is discharged into V_2 . By continually switching the switch, a current I can be made to pass from V_1 to V_2 . This simulates a resistance R (where R equals the period of the switch divided by C_1). The switching is performed by two MOSFETs (Fig.12c) driven by antiphase clock signals. The simulated resistor can be used to construct an integrator (Figs.12d,e) which can then be used to build up conventional filter structures. For example a state variable filter would have a resonant frequency F_c , where

$$F_c = \frac{1}{2\pi RC_2}$$

but $R = \frac{T}{C_1}$

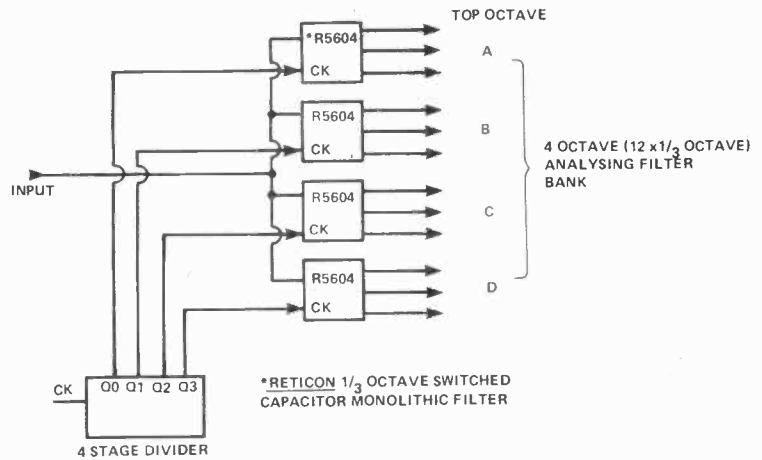


Fig.13. Switched capacitor filter bank using the R5604 from Reticon.

$$\text{therefore } F_c = \frac{C_1}{2\pi C_2 T}$$

Note that F_c is linearly proportional to $1/T$, which is the clock frequency.

Reticon make a switched capacitor bandpass filter which contains three filters at one-third octave spacing, thus making filterbank design relatively simple (Fig.13). Maybe in a few years time it will be possible to purchase a wide range of low cost monolithic filters. If that day comes, you won't need to learn how to design active filters!

ETI

3 1/2 DIGIT LCD MULTIMETER KITS

BUILD YOUR OWN PROFESSIONAL QUALITY DMM AS ALREADY USED BY HUNDREDS OF LABORATORIES, RESEARCH UNITS, UNIVERSITIES ETC. THE LASCAR RANGE OF MULTIMETERS IS NOW ALSO AVAILABLE IN KIT FORM, CONTAINING ALL PARTS NEEDED TO CONSTRUCT THESE SUPERBLY STYLED MULTIMETERS - EVEN BATTERIES AND TEST LEADS. BOTH TYPES FEATURE FIVE FUNCTIONS (AC AND DC VOLTS, AC AND DC CURRENT RESISTANCE) WITH ABILITY TO CHECK DIODES. 0.5" LCD DISPLAY WITH 'BATTERY LOW' WARNING, AUTO-POLARITY, AUTO-ZERO. FULL PROTECTION AGAINST OVERLOADS AND TRANSIENTS. CAN WITHSTAND MAINS ON ANY RANGE. RUGGED ABS CASES AND COMPREHENSIVE 1-YEAR WARRANTY.

The LMM 200 has been featured as a project in the July 80 Practical Electronics. It is a compact handheld multimeter with a 0.5% basic accuracy and 15 different ranges. It measures AC/DC voltage from 0.1mV to 500V, AC/DC current from 0.1µA to 2 Amps and resistance from 0.1Ω to 2MΩ. 200 hours battery life.

The LMM 100 is suitable for field or bench use. It has a basic accuracy of 0.1% and 25 different ranges. It measures AC/DC voltage from 0.1mV to 1Kv, AC/DC current from 0.1µA to 2 Amps and resistance from 0.1Ω to 20MΩ. Battery life is over 2,000 hours. It also features a unique 'digital hold' facility and adjustable carrying handle.

We also offer a calibration service (£5.00 + VAT = £5.75) and a trouble-shooting and calibration service (£7.50 + VAT = £8.62).



	£	P & P	VAT	TOTAL
LMM 200 Kit (PE DMM)	32.95	1.00	5.09	39.04
LMM 100 Kit	58.95	1.75	9.10	69.80
LMM 200 FULLY ASSEMBLED (INC. LEADS)	39.70	1.25	6.14	47.09
LMM 100 FULLY ASSEMBLED (INC. LEADS)	77.50	1.75	11.88	91.13

Lascar Electronics Ltd., Unit 1, Thomasin Road, Basildon, Essex. Telephone No: Basildon (0268) 727383.

To: Lascar Electronics, Unit 1, Thomasin Road, Basildon, Essex.

Please send me Data LMM 200 Kit £39.04 LMM 100 Kit £69.80
 Assembled LMM 200 £47.09 Assembled LMM 100 £91.13

Name _____
 Address _____
 Tel. No _____

I enclose cheque/P.O. value

Orders may be phoned quoting your Access or Barclaycard No
 Official orders accepted





- ORDER BY POST OR TELEPHONE WITH BARCLAYCARD/ACCESS
- ELECTRONIC TEST EQUIPMENT SPECIALISTS
- ALL PRICES INCLUDE VAT

AUDIO ELECTRONICS

- ALL MODELS ON DISPLAY
- RETAIL - MAIL ORDER - EXPORT - INDUSTRIAL
- OPEN SIX DAYS A WEEK
- CALL IN AND SEE FOR YOURSELF

SCOPES

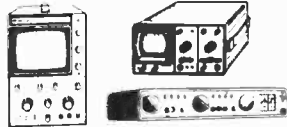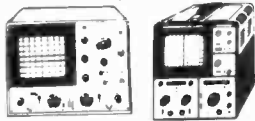A range of Scopes in stock from 5mHZ Single Trace to 50mHZ Dualtrace. Mains and Battery/Mains portables. Many on demonstration.



SINGLE TRACE (UK c/p etc £2.50)
Hm 307-3 10mHZ, 5mV, 6 x 7cm display plus component test **£170.00**
CO1303D 5mHZ, 10mHZ, 7 x 7cm display **£109.25**
SC110 10mHZ Battery portable, 10mV 3.2 x 2.6cm display (Optional case £8.80, Nicads £7.95, Mains unit £4.00)
LB0512A 10mHZ, 10mV, 5" display **£149.95**
CS1559A 10mHZ, 10mV, 5" display **£185.50**
V151 15 Mhz 1mV 5" display **£198.50**
£241.50

OPTIONAL PROBES (ALL MODELS)
 X1 **£6.50**, X10 **£8.50**, X100 **£12.95**, X1-X10 **£10.95**

All Scopes now with Free Probe(s)

DUAL TRACE (UK c/p etc £3.50)
CS1562A 10mHZ, 10mV, 5" display **£244.95**
CS1575 5mHZ 5" display **£270.00**
Hm312-8 20mHZ, 5mV, 8 x 10cm display **£287.50**
CS1566A 20mHZ, 5mV, 5" display **£323.15**
CS1352 15mHZ, 2mV, 7.5cm display, battery/mains portable (Nicads pack £29.90) **£346.15**
Hm412-4 20mHZ, 5mV, 8 x 10cm display plus Sweep Delay **£399.50**
CS1577A 30mHZ, 2mV, 5" display **£455.40**
CS1830 30mHZ, 2mV, 5" display plus sweep delay **£507.15**
Hm512-8 50mHZ, 5mV, 10x 8cm display, Delay Sweep **£667.00**
LB0514 10mHZ, 1mV (5mV) 5" display **£294.00**
V152 15 Mhz 1mV 5" display **£326.60**
V302 30 Mhz 1mV 5" display **£447.35**
V550 50 Mhz 1mV 10 x 8 cm Delay sweep + 3 channel display **£799.25**

HAMEG ● TRIO ● LEADER ● SINCLAIR

GENERATORS

(UK c/p £1.75)



TRIO ● LEADER ● CSC
 SINCLAIR ● LEVELL

RF
SG402 100KHZ - 30mHZ with AM modulation **£64.40**
LSG16 100kHz-100mHZ (300mHZ on Harmonics) **£56.50**
SG2030 250KHZ - 100mHZ low cost range **£46.95**
ARF 300 18HZ-200mHZ low cost range audio and RF **£76.95**

PULSE
2001 1HZ-100KHZ Function **£86.00**
TG105 5HZ-5mHZ **£92.50**
4001 0.5HZ-5mHZ **£105.00**

A range of Signal Generators to cover Audio, RF and Pulsing. Mains operated (TG series Battery).

AUDIO (All sine/square)
AG202A 20HZ-200KHZ **£65.55**
LAG26 20HZ-200KHZ **£69.00**
AG203 10HZ-1mHZ sine/square **£120.75**
LAG120A 10HZ-1mHZ **£137.00**

LEVELL ('M' with Meter)
152 SERIES 3HZ - 300KHZ Sine/Square **£92.00**
200 SERIES 1HZ-1mHZ Sine/Square **£92.00**
TG152D **£113.85**
TG152DM **£124.20**
TG200D **£149.50**
TG200DM **£155.25**

SWR/FS AND POWER METERS




Range in stock covering up to 150mHZ and up to 1 K watt power. PL259 sockets. Also 250 UHZ Grid Dipmeter
SWRS SWR/ S 3-150mHZ **£9.50**
SWR50 SWR/Power meter **£13.95**
110 SWR/Power 1/2-144mHZ **£11.50**
0/10/100 watts **£14.50**
171 As 110 Twin meter plus F/S **£16.50**
 Plus large range of BNC/PL259/etc leads/plugs/adaptors/connectors always in stock.
176 SWR/Power/FS 1/2-144mHZ **£16.50**
5-50 watt Plus 25-40mHZ AC match **£38.50**
KDM6 Grid Dip 1/2-250mHZ

DIGITAL MULTIMETERS

KAISE ● SINCLAIR ● LASCAR

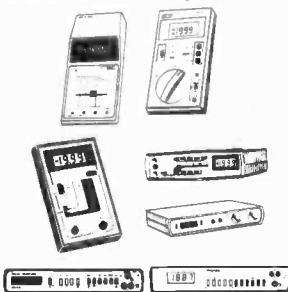
A range of LED and LCD Bench and Hand DMM's battery operated with optional Mains Adaptors - some with optional Nicads. All supplied with batteries and leads.



HAND HELD (UK post etc 85p)
TM352 3 1/2 Digit LCD plus 10 ADC and Hfe checker **£54.95**
PDM35 3 1/2 Digit 16 range LED (no AC current) **£32.95**
ME502 3 1/2 Digit LED plus 10A DC and Hfe checker **£43.95**
LM2001 3 1/2 Digit LCD 2 amp AC/DC 0.1% **£51.70**
6200 3 1/2 Digit LCD 0.2A AC/DC, Auto range **£39.95**
6220 As 6200 plus 10A AC/DC **£49.95**
6100 As 6200 plus Cont. test/range hold **£64.95**
6110 As 6100 plus 10A AC/DC **£74.95**

BENCH PORTABLES (UK c/p £1.00)
DM235 3 1/2 Digit LED 21 ranges, 0.5% AC/DC 2A **£56.50**
DM350 3 1/2 Digit LED 34 ranges AC/DC 10A **£78.50**
TM353 3 1/2 Digit LCD AC/DC 2 amp **£86.50**
TM351 3 1/2 Digit LCD AC/DC 10 amp **£107.95**
LM100 3 1/2 Digit LCD AC/DC 2 amp **£86.50**
DM450 4 1/2 Digit LED 34 ranges AC/DC 10 amp (DM series options, Carry case £8.80, Nicads £7.95, Mains adaptc £4.00).

MULTIMETERS (UK post etc 75p)

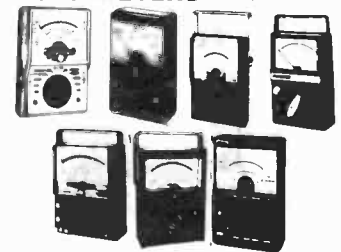


KRT101 1K/Volt 10 range pocket **£4.50**
ATM1/LT1 1K/Volt 12 range pocket **£5.95**
NH55 2K/Volt 10 range pocket **£8.95**
AT1 2K/Volt 12 range pocket de luxe **£7.95**
NH56 20K/Volt 22 range pocket **£10.95**
YN360TR 20K/Volt 19 range pocket plus hfe test **£13.95**
AT1020 20K/Volt 19 range de luxe plus hfe test **£16.95**
7081 50K/Volt 36 range plus 10 amp DC **£19.95**
TMK500 30K/Volt 23 range plus 12A DC/Cont. test **£21.50**
AT20 20K/Volt 21 range de luxe plus 10A DC and 5KV DC **£21.95**
AT205 50K/Volt 21 range de luxe plus 10A DC **£24.95**
7080 20K/Volt 26 range large scale, 10A DC plus 5KV AC/DC **£26.95**
AT2050 50K/Volt 18 range de luxe plus hfe test **£28.50**
AT210 100K/Volt 21 range de luxe plus 12A AC/DC **£29.95**
360TR 100K/Volt 23 range plus hfe checker and AC/DC 10 amps **£34.95**

CHOOSE FROM THE UK'S LARGEST SELECTION

FREQUENCY COUNTERS



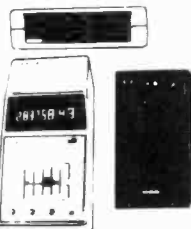Portable and Bench LCD and LED Counters up to 600mHZ. Prices include batteries and leads.



HAND HELD (UK post etc 85p)
PFM200 20HZ to 200mHZ 8 Digit LED **£54.50**
MAX50 100HZ to 50mHZ 6 Digit LED **£61.00**
MAX550 30KHZ to 550mHZ 6 Digit LED **£106.00**

BENCH PORTABLES (UK c/p £1.00)
MAX100 8 Digit LED 5HZ to 100mHZ **£89.00**
TF200 8 Digit LCD 10HZ to 200mHZ **£158.95**
7010A 9 Digit LED 10HZ to 600mHZ **£184.00**
TP600 600mHZ Pre-Scaler for TF200 **£41.00**
200SPC 6 Digit 100mHZ LED built into 0.002 HZ to 5.5mHZ pulse generator **£437.00**

CSC ● SINCLAIR ● OPTO ELECTRONICS

LOGIC PROBES MONITORS

Logic probes indicating high/low etc states that scopes can miss. all circuit powered for all IC's.
LP3 50 mHZ logic probe **£55.95**
LP1 10 mHZ logic probe **£35.50**
LP2 1 1/2 mHZ logic probe **£19.95**
LMI Logic monitor **£33.00**
 Also in stock range of Protoboard kits and breadboards.

MINI DRILLS AND KITS

(8-12 Volt 1/8" chucks)
 Small Drill plus 3 collets **£7.25**
 Medium Drill plus 3 collets **£10.50**
 Small Drill plus 20 tools **£14.95**
 Medium Drill plus 20 tools **£17.95**
 Mains Drill **£13.95**
 Mains Drill plus 20 tools **£21.50**

Stockists of electronic equipment, speakers/kits, PA equipment plus huge range of accessories ● UK carriage/packing as indicated ● Export - prices on request ● All prices correct at 1-11-80E & OE ● All prices include V.A.T.

AUDIO ELECTRONICS Cubegate Limited

OPEN SIX DAYS A WEEK

301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TELEPHONE 01-724 3564



FREE CATALOGUE!

Send large SAE (17 1/2 UK) Schools, Companies, etc. free on request.

AND NOW A DIMMER THAT MAKES TOUCH DIMMERS OBSOLETE

Two years ago TK Electronics launched a touchdimmer kit, the TD300K, which made knob controlled dimmers obsolete. This was such a great success that many magazines and more retailers soon produced similar designs. SO THAT OTHERS MAY FOLLOW, TK have designed a touch dimmer kit with an Infra Red Remote control enabling you to switch and control the brightness of your lights from the comfort of your armchair etc. (as well as manually by touching the frontplate or by using the TDE/K extension kit).


As with all our kits, these come complete with all components including RFI suppression, frontplate, a neon to help you find the switch in the dark and a neat box for the transmitter. The plastic frontplate has no metal pads to touch ensuring complete safety and enabling the plate to be covered with a decorative finish to blend with your room decor.



We have designed the light dimmer unit to fit a standard wall box, the transmitter to fit your hand and the price to fit your pocket.

In two years time everyone will be selling remote control dimmers but you can have your TDRK300K kit NOW for only **£14.30** for the dimmer unit and **£4.20** for the transmitter.

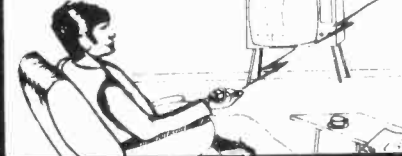For the more athletic of you the TD300K is still available at **£6.50** and the TDE/K at **£2.00**. DON'T FORGET to add 40p P&P and 15% VAT to your total purchase.



REMOTE CONTROL COMPONENTS

LD271 IR Emitting Diode	36p
SF4205 Photodiode Detector	95p
SL480 IC Pulse Amp	£1.70
SL490 32 command encoder/transmitter	£2.40
ML922 10 channel receiver + 3 analogue outputs	£4.20
ML926 16 channel receiver 4 momentary binary o/p	£1.40
ML928 16 channel receiver 4 latched binary o/p	£1.40
ML929 16 channel receiver 4 latched binary o/p	£1.40
Data Sheets per device	10p

These ICs can be used with infra red, ultrasonic or radio links, depending on range, cost and speed of operation.

RC500K KIT

If you do not require a sophisticated multi channel remote control, we have developed a simple single channel on/off infra red transmitter and receiver kit. The transmitter unit comes complete with a hand-held box and requires a PP3 (9V) battery. The receiver includes a triac capable of switching up to 500W at 240V a.c. and comprises a pre-amplifier, bistable latch and a mains power supply, making the unit completely self contained. The small size of the receiver enables the unit to be built into all kinds of equipment from lamps to tape recorders. Range approximately 20ft. **£12.50**

ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION. ADD VAT AT CURRENT RATE TO ABOVE PRICES. 40p P&P MAIL ORDER - CALLERS WELCOME BY APPOINTMENT



TK Electronics

(ETI), 11 BOSTON ROAD
LONDON W7 3SJ. 01-579 9794



TRIACS

400V Plastic Case (Texas)			
3A	49p	16A	95p
8A	58p		
12A	85p	25A	190p
6A with trigger	80p		
8A isolated tab	65p		
Diac	18p		

XMAS STOCKING FILLERS

(closing date 31.12.80)

6 x 555 ICs	£1.00
15 x 8-pin sockets	£1.00
12 x 14-pin sockets	£1.00
10 x 16-pin sockets	£1.00
15 x BC182	£1.00
15 x BC212	£1.00
2 x TIC2260 triacs	£1.00
12 x Red LEDs 0.2 / 0.1	£1.00
10 x Green LEDs 0.2 / 0.1	£1.00
10 x Yellow LEDs 0.2 / 0.1	£1.00
2 x LM380 2W audio amp	£1.50
1 x LM2917 & socket	£1.50

MINI KITS

These kits form useful subsystems which may be incorporated into larger designs or used alone. Kits include PCB, short instructions and all components.

MK1 TEMPERATURE CONTROLLER / THERMOSTAT	
Uses LM3911 IC to sense temperature (80°C max) and triac to switch heater	1KW £4.00
MK2 SOLID STATE RELAY	
Ideal for switching motors, lights, heaters, etc from logic. Opto-isolated with zero voltage switching. Supplied without triac. Select the required triac from our range	£2.60
MK3 BAR / DOT DISPLAY	
Displays an analogue voltage on a linear 10 element LED display as a bar or single dot. Ideal for thermometers, level indicators, etc. May be stacked to obtain 20 to 100 element displays. Requires 5.20V supply	£4.75
MK4 PROPORTIONAL TEMPERATURE CONTROLLER	
Based on the TDA1024 Zero voltage switch, this kit may be wired to form a burst fire power controller or a proportional temperature controller enabling the temperature of an enclosure to be maintained to within 0.5°C	3KW £5.55
MKS MAINS TIMER	
Based on the ZN1034E Timer IC this kit will switch a mains load on (or off) for a preset time from 20 minutes to 35 hours. Longer or shorter periods may be realised by minor component changes. Maximum load 1KW	£4.50

DISPLAY LIGHTING KITS

Each unit has 4 channels (rated at 1KW at 240V per channel) which switch lamps to provide sequencing effects, controlled manually or by an optional opto-isolated audio input.

DL1000K
This kit features a bi-directional sequence, speed of sequence and frequency of direction change being variable by means of potentiometers. Incorporates master dimming control. **£14.80**

DL21000L
A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a preset pot. Outputs switched only at mains zero crossing points to reduce radio interference to minimum. **£8.00**
Optional Opto Input DLA1 **80p**

SPECIAL OFFER DVM THERMOMETER KIT

photograph and matter as in HE October issue
PRICE £17.50
Closing date 31-12-80

D.I.L. I.C. SOCKETS

8 pin	8p	18 pin	17p
14 pin	12p	28 pin	24p
16 pin	14p	40 pin	38p

INTEGRATED CIRCUITS

555 Timer	21p
741 Op. Amp	19p
AY-5-1224 Clock	£2.60
AY-5-1230 / 2 Clock / Timer	£4.50
AY-3-1270 Thermometer	£8.20
ICL7106 DVM (LCD drive)	£7.00
LM377 Dual 2W Amp	£1.45
LM3795 Dual 6W Amp	£3.50
LM380 2W Audio Amp	80p
LM382 Dual / low noise Preamp	£1.00
LM386 250mW low voltage Amp	75p
LM1830 Fluid Level Detector	£1.50
LM2907 1/2 Converter (8 pin)	£1.40
LM2917 1/2 Converter (14 pin)	£1.80
LM3909 LED Flasher / Oscillator	80p
LM3911 Thermometer	£1.20
LM3914 Dot / Bar Driver	£2.10
MM74C911 4 digit display controller	£6.50
MM74C915 7 segment BCD converter	98p
MM74C926 4 digit counter with 7 seq o/p	£4.50
S5668 Touchdimmer	£2.50
S9263 Touchswitch 16-way	£4.85
SN76477 Complex Sound Generator	£2.52
TBA800 5W Audio Amp	85p
TBA810AS 7W Audio Amp	£1.00
TOA1024 Zero Voltage Switch	£1.20
TDA2020 20W Audio Amp.	£2.85
ZN1034E Timer	£1.80

All ICs supplied with data sheets
Data Sheets only 10p each device

See us on STAND F1 at
LONDON BREADBOARD EXHIBITION



CSC Continental Specialties Corporation 100 MHz Frequency Counter

5HZ TO 100MHZ

TOMORROW'S TOOLS TODAY

CONTINENTAL SPECIALTIES CORPORATION



C.S.C. (UK) Limited Dept. 9D
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex. CB11 3AQ
Telephone: Saffron Walden (0799) 21682
Telex: 817477

ETI DECEMBER 1980

Instant frequency indication from 5Hz to 100MHz; no range selection problems; a brilliant 8-digit LED display; mains or battery operation; an accuracy of 4 parts per million ± 1 count; and totally automatic operation - all this for only £77.55* with CSC's new Max-100 frequency counter.

Just take a look at our spec. Where else could you find anything similar at the price?
*Frequency range 5Hz - 100 MHz *Input impedance 1M shunted by 10pF *Sensitivity 30mV from 1KHz up to 50MHz; 120mV r.m.s. over full frequency range *Timebase accuracy ± 4 parts in 10⁶ (from 5 to 45°C) *Maximum aging rate 10 parts in 10⁶ per year *Over-frequency indication *Low-battery-power alarm *Operates from dry or rechargeable cells, an external 7.5 to 10VDC supply, or a car battery (via an adaptor)
*Dimensions: 45 x 187 x 143mm *Options: 12V adaptor; battery eliminator; r.f. antenna, low-loss r.f. tap, carrying case.

Fill in the coupon for further details . . .

*price excludes post, packing and VAT

C.S.C. (UK) Ltd., Dept. 9D Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex. CB11 3AQ

MAX 100	FREQ. COUNTER	Unit price inc P&P 15% VAT	£90.91	Qty	Rest
---------	---------------	----------------------------	--------	-----	------

Name _____
Address _____

I enclose cheque/P.O. for £ _____ or debit my Barclaycard/Access/American Express card no _____ exp. date _____


FOR IMMEDIATE ACTION - The C.S.C. 24 hour, 5 day a week service Telephone (0799) 21682 and give us your Barclaycard, Access, American Express number and your order will be in the post immediately

For FREE catalogue: tick box

MUSICAL ALARM CLOCK

This unique battery-powered alarm clock has all the usual facilities, but in addition it makes a tick-tock sound and plays a random selection of eight tunes under the alarm condition

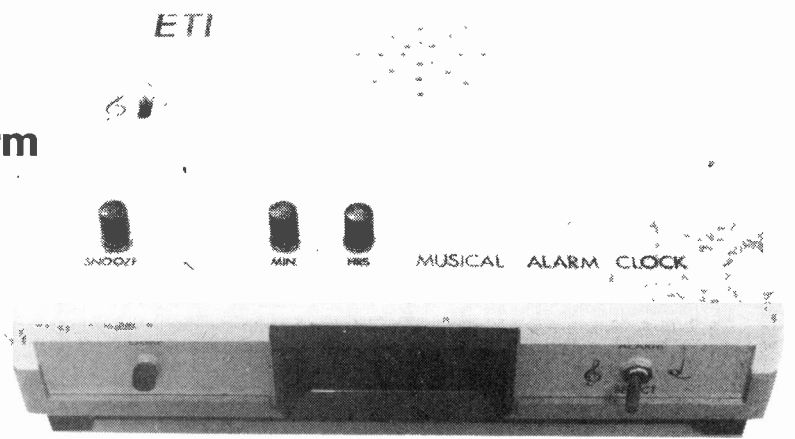Design by Ray Marston. Development by Steve Ramsahadeo.



This ETI alarm clock project has a number of unique features. First, the clock is based on a ready-built CM172 module that has a large liquid crystal readout and will give a year or two of continuous running from a single 1V5 cell. The module can be easily programmed for 'time set' and 'alarm set', remembers the 'alarm set' time indefinitely, has ten minute snooze facility, two alarm output terminals and a built-in backlight. The CM172 module forms the basis of the whole project.

The second feature of our clock is that we've provided it with a unique tick-tock sound generator circuit, so that the clock looks electronic but *sounds* like a mechanical device and can easily be located in a darkened room. The tick rate and volume are presettable, to suit individual tastes. The tick-tock circuit typically consumes a mere 9 uA of current and gives a couple of years of continuous running from a standard battery.

Finally, we've fitted our clock with a special and modestly priced microcomputer chip that, in conjunction with a handful of other components, generates a random selection of eight well known tunes under the alarm condition. The tempo, tone and volume of the tunes are variable via preset pots. The microcomputer chip is actually capable of generating a total of 24 different tunes in three selectable groups of eight tunes each (see Table 1).

In our circuit any one of the three groups can be manually selected via a switch. Electronic circuitry then randomly selects and plays complete tunes from that group, automatically inserting a random pause of up to several seconds between the end of one tune and the start of the next when the circuitry is active.

The tune-generator circuitry consumes virtually zero standby current, turns on automatically under the alarm condition, can be temporarily cancelled (for ten minutes) by a snooze button or can be disabled by either of two off switches. It can also be independently played at any time using the tune test switch. We've also provided the circuit with a switch that

gives you the option of selecting either the musical alarm or a more conventional pulsed tone alarm signal.

The complete alarm clock project uses a total of three batteries, there being a 1V5 cell for the actual clock module and two 9 V (PP3) batteries for the rest of the electronics. The 1V5 cell can be expected to give one or two years of continuous running. The two 9 V batteries should last about a year under normal usage conditions. The clock is fitted with a special switch-enable slide switch, which ensures that important functions and time settings cannot be inadvertently operated or changed by accidental switch operation at night or when the clock is packed away in a suitcase, etc.

Construction

Construction of the electronics of this project should present few problems. The basic CM172 clock module circuitry is quite independent of the alarm/tick-tock circuitry, so these two major units can be built and tested separately.

Start the construction by tackling the major mechanical problems. If you intend to use the same case as our prototype note that the front panel will need to be split into two and the upper and lower centre-front lips of the case will have to be cut away to accurately accommodate the clock bezel (a separate item, not supplied with the basic CM172 module). The bezel is then used to secure the module to the front panel.

Next, fit all the switches associated with the clock module (PB1, 2, 3, 4 and SW1, 2, 3) to the case and make the interconnections to the clock module solder pads as indicated in the circuit diagram, using a fine-tipped soldering iron. Now connect B1 (1V5) to the module (taking great care to fit it in the correct polarity) and give the clock a functional test as follows.

Turn SW1 on, press SW2 to TIME SET and use PB1 to set MINS and PB2 to set HOURS (when setting HOURS, check that the correct AM or PM indication is given at the left of the

display). Similarly, use SW2-PB1-PB2 to select the ALARM SET time, taking care to get the correct AM or PM indication. The alarm facility can be activated by turning SW3 on, in which case a treble clef musical sign will appear at the right of the display. PB4 operates a built-in backlight, for night viewing, and is intended for intermittent operation only.

Alarm/Tick-Tock Circuit

Proceed now to the construction of the alarm/tick-tock circuitry on the large PCB. Note that all ICs should be fitted in suitable sockets. The usual care should be taken to ensure that all semiconductor devices and electrolytics are fitted with the correct polarity. When construction is complete, temporarily fit speaker LS1 in place, together with SW4 and SW6. Connect B2 (9 V) in place, with its negative terminal to -ve and its positive to point A. Check that the tick-tock sound is generated and that its rate and volume are variable via presets PR4 and PR5 respectively.

Now connect B3 (9 V) in place, with its negative terminal to point A and its positive to +ve. Close tune test switch SW6 and check that the circuit randomly generates a selection of tunes, with the tempo, tone and volume variable via presets PR1, PR2 and PR3 respectively. The structure of the circuit is such that the musical alarm randomly runs through a selection of eight tunes, with an undefined pause between each tune. A total of three selections (24 tunes) are available and can be chosen by SW4 (see Table 1).

When you are satisfied that the circuitry is functioning correctly, remove all batteries (including B1), fit the speaker and switches SW4, 5 and 6 permanently in place in the case and complete the interwiring, taking special care over the connections between SW5 and the CM172 clock module. Finally, refit all batteries and give the musical alarm clock a functional check as follows.

Final Testing

Set the correct (real) time and the alarm time with SW2 and PB1-PB2, with the alarm time a minute or two away from real time. Turn the alarm function on via SW3. When the alarm

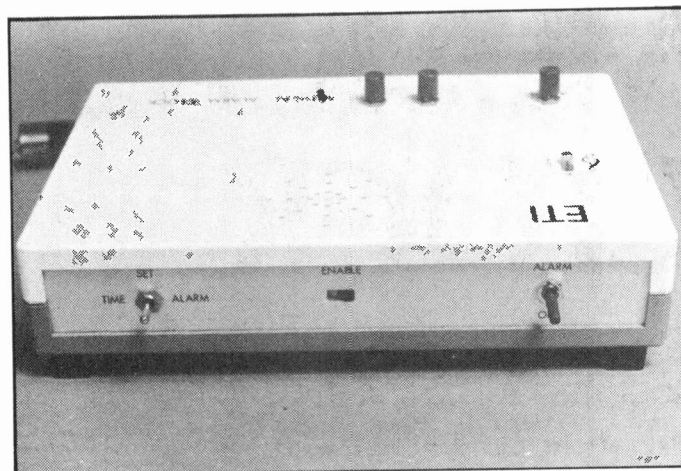
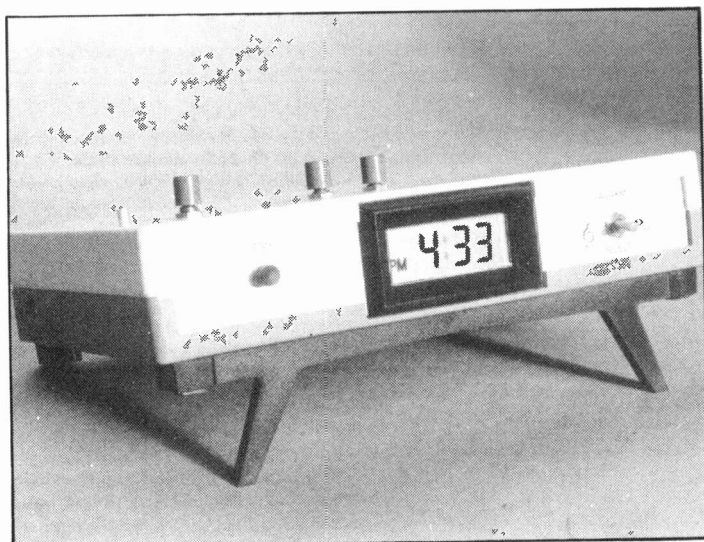


Fig.1. The back panel of the Musical Alarm Clock, showing the special switch-enable slide switch. This ensures that functions and time settings cannot be inadvertently changed.

time is reached, the alarm should be generated. The alarm will be musical with SW5 in the TUNE position or will be a pulsed-tone signal with SW5 in the TONE position.

Once the alarm has activated, it will continue to sound for about 12 minutes and then automatically turn off. If the snooze button is pressed when the alarm is activated, the alarm will immediately turn off and then automatically activate again after ten minutes. If SW3 is turned permanently off once the alarm has activated, the alarm will immediately turn off and remain off. If SW3 is momentarily turned off and then on again once the alarm has activated, the alarm will immediately turn off but will re-activate when the set alarm time is reached the following day.

IC OUTPUTS	TUNES
K1	R ₀ Greensleeves
	R ₁ God Save the Queen
	R ₂ Rule Britannia
	R ₃ Land of Hope and Glory
	R ₄ Sailors' Hornpipe
	R ₅ Westminster Chimes
	R ₆ Oranges and Lemons
	R ₇ Oh Come All Ye Faithful
K2	R ₀ Cook House Door
	R ₁ The Stars and Stripes
	R ₂ Beethoven's Ode to Joy (9th)
	R ₃ William Tell Overture
	R ₄ Red Flag / Maryland / Tannenbaum
	R ₅ Great Gate of Kiev
	R ₆ Twinkle Twinkle Little Star
	R ₇ Soldiers' Chorus (Faust)
K4	R ₀ Fate Knocking (Beethoven)
	R ₁ The Marseillaise
	R ₂ Deutschland Uber Alles
	R ₃ Toccatina in D Minor (Bach)
	R ₄ The Lorelei
	R ₅ Wedding March (Mendelssohn)
	R ₆ Colonel Bogie
	R ₇ Mozart

Table 1. Tune repertoire of the musical alarm clock.



Fig.2(Right): Circuit diagram for the ETI Musical Alarm Clock, showing alarm and tick-tock circuitry.

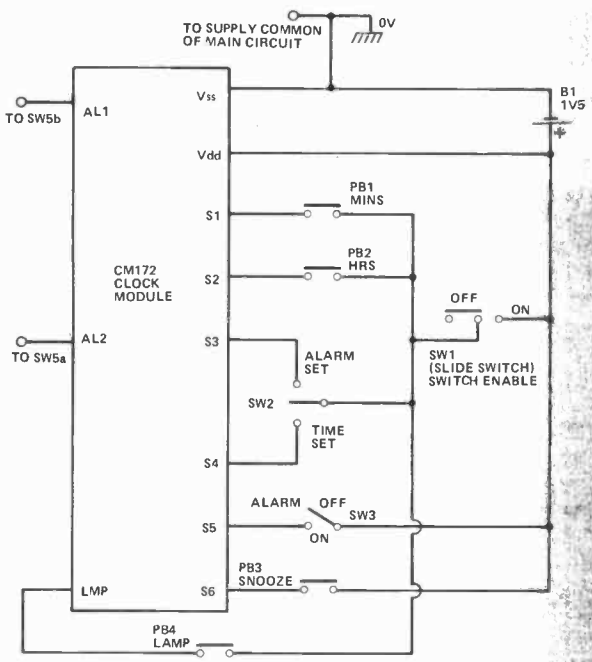
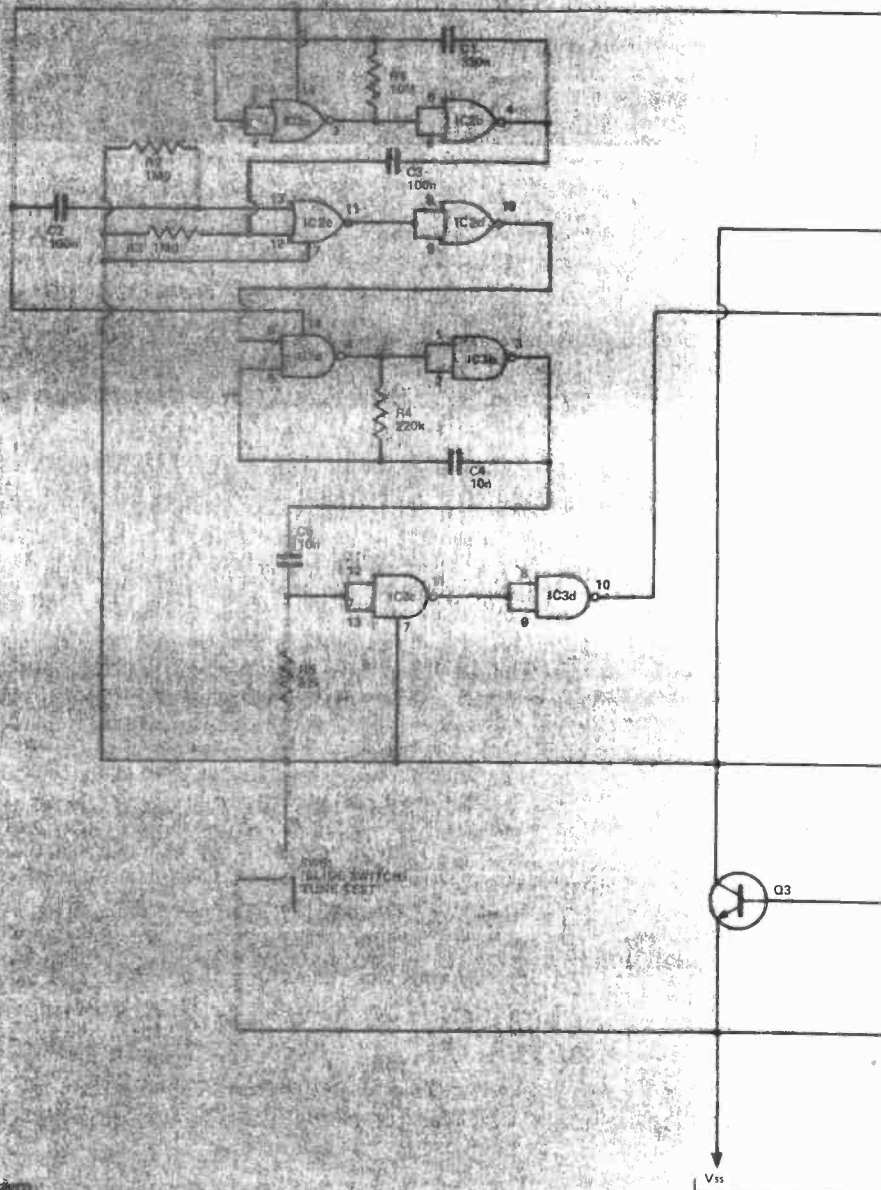


Fig.3(Above): Connections of the basic clock module for the Musical Alarm Clock.

HOW IT WORKS

The basic CM172 clock module is a ready-built, LCD-readout unit that forms the heart of our project. The module is powered by a 9V cell. Note that we've wired an enable slide-switch in series with the alarm set and time-set switches/buttons and with the back-light lamp button to guard against inadvertent operation of these mechanisms.

The CM172 module has two alarm-out terminals. In our particular application, a pulsed 1024 Hz tone (1 S on, 1 S off) is available at the AL1 output and a simple high potential is available at the AL2 output under the alarm condition. These outputs are available for a maximum of 12 minutes under the alarm condition; once activated, they can be temporarily cancelled (for ten minutes) by briefly closing snooze button PB3 or can be fully cancelled by momentarily or permanently turning SW3 off.

The CM172 circuit can be used as a stand-alone project, its operation being quite independent of the tick-tock and musical-alarm circuits used in the remainder of our alarm clock project.


The tick-tock circuitry is powered from a 9 V supply (B1) and is designed around Q6-IC4 and Q5. A prime consideration in the design of this circuit is that of very low mean current consumption. The complete circuit typically consumes a mere 9 uA or so.

Q6 and IC4a are wired as a special astable circuit, powered from B1 via D1-R17 and C1. At the start of each astable cycle, C9 is discharged, Q6 is off and IC4a output is high. C9 then charges exponentially via R14 and R16 until eventually Q6 becomes forward biased and switches the output of IC4a (a Schmitt gate) low, at which point C9 is rapidly discharged via D5 and R22 and the operating cycle is complete. The cycle then repeats ad infinitum.

The output of IC4a is then fed to differentiating network C12-R23 via the 1.4k buffer, each differentiated spike is then converted to a clean pulse with a width of about 200 uA by IC4c and IC4d and is fed to pulse amplifier Q5 via the PR5 volume control and gate diode D3. Consequently, a very narrow current pulse is periodically fed to the speaker and causes the speaker (because of its inductive nature) to ring at 10 kHz natural resonant frequency and produce a characteristic tick sound (that this design should more correctly be called a tick-tick circuit). The tick rate can be varied by R14 to suit individual tastes.

The heart of the musical alarm is IC1, a microcomputer chip that contains a simple microprocessor together with a ROM pre-programmed with 24 tunes in digital form. Any one of these tunes can

PROJECT: Musical Alarm Clock

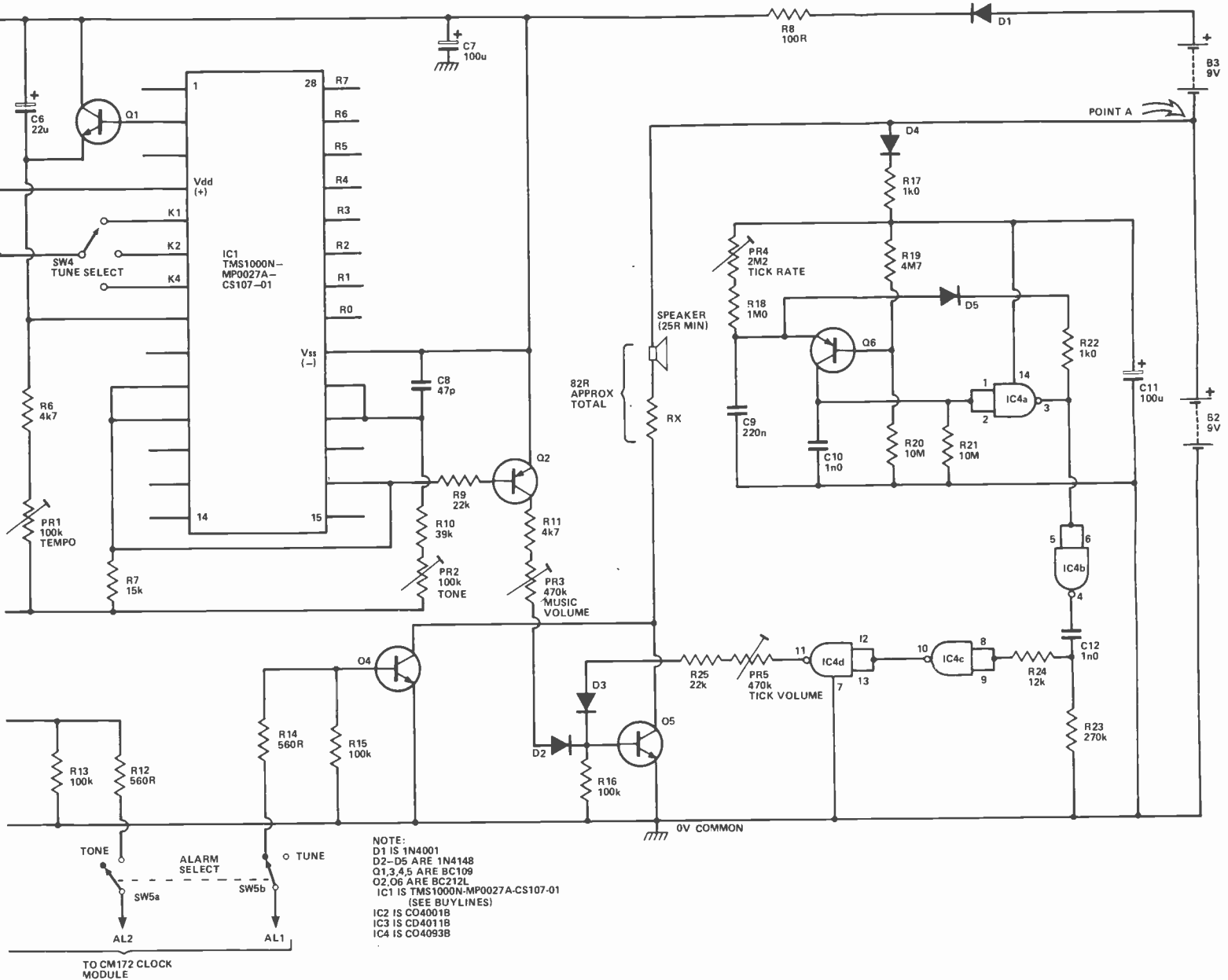

be selected by connecting the appropriate one of the $R_{\sigma}R_7$ terminals to the appropriate one of the K1, K2 or K4 terminals. Once a tune has been selected, it is made available in digitised analogue form across R7. The tune tempo is varied by PR1, the tone by PR2. The tune generator can be turned on by driving Q3 on or by closing SW6. In our application, the digitised analogue output of the tune generator is fed to the speaker via Q2-PR3 and via Q5 and gate diode D2.

The most unusual feature of our circuit is the method of tune selection and to understand this you need to know how IC1 actually works. IC1 normally selects tunes by sequentially scanning the $R_{\sigma}R_7$ pins to see if a connection exists between any of these terminals and any of the K pins, it being the time-coincidence of the feedback pulse to a K pin that causes actual selection. The scan frame is 10 mS, the scan rate is 450 μ S and the scan pulse width is 33 μ S.

In principle, therefore, it is possible to select a tune by simply feeding a narrow positive pulse to the appropriate K terminal, ignoring the R pins completely. If this pulse is frame-locked and time delayed, any required tune can be selected. If the pulse is not frame-locked, tunes will be selected at random from the available repertoire. Our cir-

cut uses this latter principle to implement random tune selection.

In our circuit IC2a and IC2b are wired as a slow (several seconds) astable. The output of this astable is converted to a periodic pulse (width about 100 mS) via C3-R3 and IC2c-IC2d and is used to gate a second astable comprising IC3a-IC3b. This astable has a period of about 3 mS and its output is converted to a 0.5 mS pulse via C5-R5 and IC3c-IC3d and fed to one of the K terminals of IC1 via SW4. The K signal thus comprises an occasional (once every few seconds) burst of 0.5 mS pulses with a 3 mS rate and causes successive tunes to be effectively selected at random.

Note that C2 and R2 are used in our circuit to ensure that the very first tune that is selected under the alarm condition is almost invariably the same, with the subsequent tunes being selected at random.

With SW5 in the tone position, the AL2 output of the clock module has no effect on our music generator circuit and the AL1 pulsed-tone signal of the clock module is fed to the speaker via Q4. When SW5 is in the tune position the AL1 output has no effect and the AL2 output is used to drive on Q3 via R12 and so activate the musical alarm circuit.

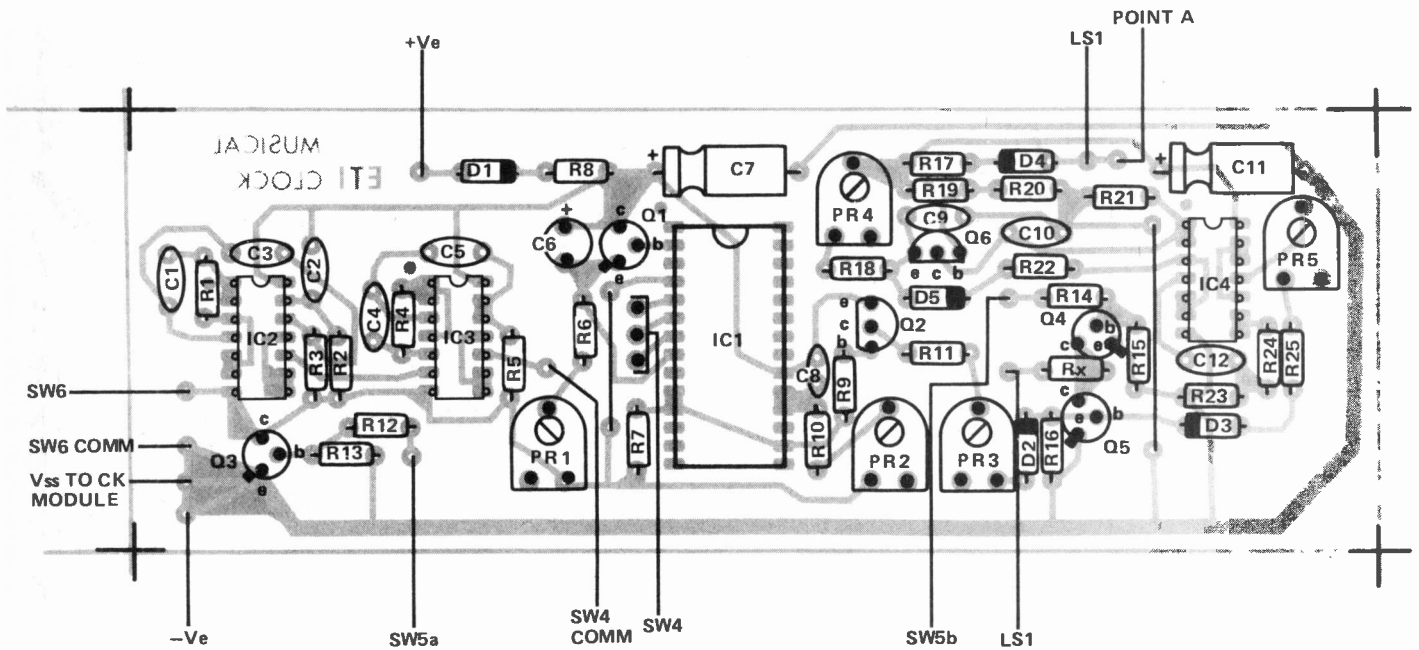


Fig.4 Component overlay for ETI Musical Alarm Clock.

PARTS LIST

Resistors All 1/4 W 5%

R1,20,21	10M
R2,3,18	1M0
R4	220k
R5	82k
R6,11	4k7
R7	15k
R8	100R
R9,25	22k
R10	39k
R12,14	560R
R13,15,16	100k
R17,22	1k0
R19	4M7
R23	270k
R24	12k
Rx	(see circuit diagram)

Potentiometers

PR1,2	100k miniature horizontal preset
PR3,5	470k miniature horizontal preset
PR4	2M2 miniature horizontal preset

Capacitors

C1	330n polycarbonate
----	--------------------

C2,3	100n polycarbonate
C4,5	10n polycarbonate
C6	22u 25 V electrolytic PCB type
C7,11	100u 25 V electrolytic axial
C8	47p ceramic
C9	220n polycarbonate
C10,12	1n0 polycarbonate

Semiconductors

IC1	TMS1000N — MP0027A
IC2	4001B
IC3	4011B
IC4	4093B
Q1,3,4,5	BC109
Q2,6	BC212L
D1	1N4001
D2-D5	1N4148
CM172	clock module


Miscellaneous

PB1,2,3,4 miniature push buttons; SW1,6 miniature slide switch; SW2 DPDT Centre off biased toggle; SW3 SPST miniature toggle; SW4 three position slide switch; SW5 DPDT miniature toggle; Vero case (order code 202-21034) plus tilt stand (202-21300G), PCB, Loudspeaker (see circuit diagram), Bezel.

BUYLINES

The clock module (CM172) and bezel is available from Ambit International. Most other components (except IC1) should be readily available from major stockists. Ambit International, 200 North Service Road, Brentwood, Essex.

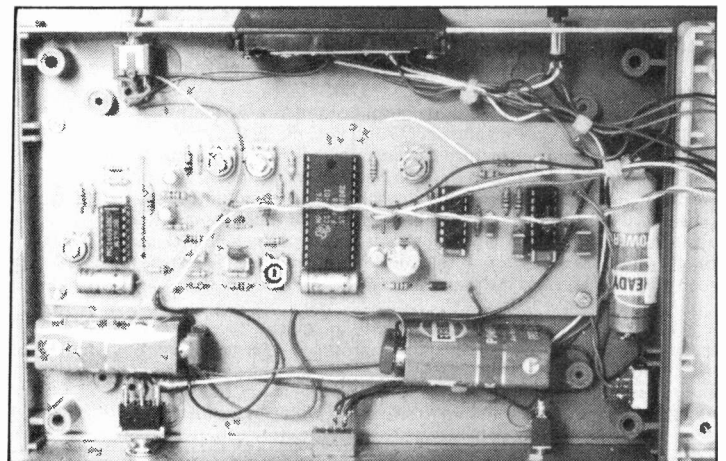IC1 is a special pre-programmed micro-computer chip and is exclusively available from Chromatronics, River Way, Harlow, Essex, under the designation TMS1000N — MP0027A. The chip costs about £5.




The photograph (right) shows the layout of our clock. Note the inclusion of three batteries.

ETI

CASTLE ELECTRONICS MICRO COMPUTER CENTRE

Now out of twelve years' experience in electronics and communication comes the South Coast's own Computer Centre. Choose from our wide range of micro-computers and support material. Ideally suited to the hobbyist about to enter the fascinating world of computers. Personal callers or mail order welcome.

NASCOM

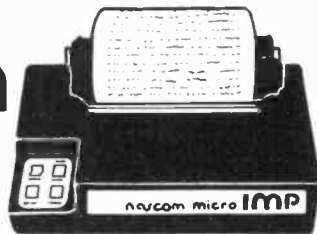


Nascom 2—£225 + VAT. Comprehensive starter system that grows with you. Powerful Z80A. 57 KeyLicon solid-state keyboard. TV or monitor. On board UART (6402). Parallel I/O with 16 lines. Kit fully documented. 8K microsoft basic in ROM.

Nascom Imp—£325 + VAT. Plain paper with standard specification. Features: 60 lines/minute. Bidirectional printing. Baud rate 110-9600.

Nascom 1—£125 + VAT Kitform —£140 + VAT readybuilt. Full range of Nascom accessories are normally held in stock. Detailed specification and full list available.

£125

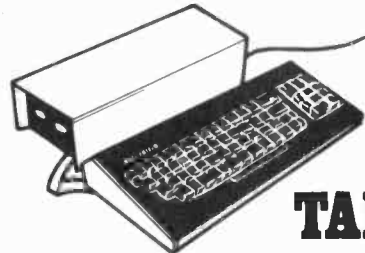

TANGERINE

Microtan 65—£69 + VAT. 6502 microprocessor. 1K Tanbug. 1K user RAM. Full TV display. 20-way keypad.
Tanex—£43 + VAT. 7K RAM. 6K RAM, 8K microsoft basic. 32 parallel I/O lines. 2 serial. 1x20mA serial. Cassette interface and motherboard. **System Rack**—£49 + VAT in black/tangerine brushed aluminium. Full Ascii keyboard with numeric keypad £49 + VAT. Cabinet available at £20 + VAT. Optional lower case pack—£9.48 + VAT. Chunky Graphics Pack—£6.52 + VAT.

£69

COMMODORE PET

Everything has been said about PET. A full range of accessories and software (both games and business) is held in stock. 8K



£399



apple

Apple 16K video output only—£695.00 + VAT.
Disc drive without controller—£299.00 + VAT.
Disc drive with controller—£349.00 + VAT. 16K add on—£69.00 + VAT. CARDS: Prototype/hobby card—£15.00 + VAT. Parallel Printer Interface Card—£104.00 + VAT. Communications Card—£130.00 + VAT. High-speed serial interface card—£113.00 + VAT. Pascal language system—£299.00 + VAT. Centronics Card—£130.00 + VAT. Applesoft Firmware Card—£116.00 + VAT. Integer Card—£116.00 + VAT.

£695

SHARP

MZ80—Sharp's dynamic entry into microcomputers. Floppy disc units plus printer now available. Price.



£499



video genie system

The Video Genie system has many uses in all spheres of life, the easy to use BASIC language means that programmes are easily written for specific applications, and pre-recorded programme tapes are available in great variety. TRS/80 software can be used with this system. The system has great scope in the home, sophisticated games programmes can introduce the computer age to all the family, who can then progress to writing their own programmes in BASIC or even machine code. Software is continuously being developed to aid home budgeting and education.

£330

Send for free brochures and price list

OTHER ITEMS: Media C12 cassettes—£5.00 + VAT for 10. 10 x 5 1/4" mini floppy discs—£27.50 + VAT Kybe or Memorex. Listing paper—£15 per box. 2000 sheets 11 x 9 1/2".
Printers: Commodore 3022, Epsom 80, Anadex DP8000 Centronics, Qume. **Service:** Full service and spares for all equipment. Microprocessor components 6502, Z80A, 2716, 2114, etc. etc. Large range of CMOS, TTL, Linear, Transistors, Capacitors, Sockets, Rectifiers, LEDs, Resistors—full list available. **Monitors:** Range of direct import U.S. monitors 12" B/w £139.95 + VAT. 12" green/black £149.95. 17" green/black price tbn. Hitachi 12" £197 + VAT, 9" £127 + VAT. **Under development**—IEEE intelligent interface for Nascom. IEEE controller, to operate Nascom on Commodore discs. Delivery January 1980. **Delivery:** All prices please add VAT at 15%. Postage and packing will be notified. Barclaycard, Access orders taken by phone.


CASTLE ELECTRONICS

7 CASTLE ST., HASTINGS, EAST SUSSEX TN34 3DY
Shop hours 0900 to 1730 Mondays to Saturdays

Telephone: Hastings (0424) 437875
Personal callers welcome

MICROBASICS

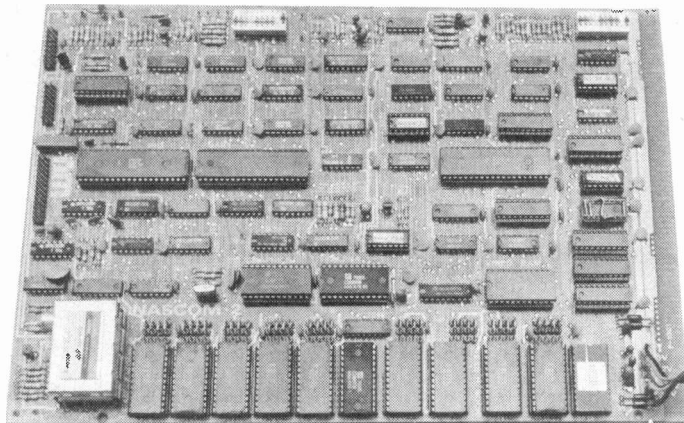This month Microbasics looks at the Ins and Outs of interfacing with computers and the special chips used. Henry Budgett explains the initials and the innards.



The NASCOM 2 is well equipped with I/O. Both the PIO (a PIA relative) and the UART can be seen centre left.

We have now reached the stage where we have a perfectly useable microcomputer system, except for one small point. We can neither communicate with it nor it with us! The electronic circuits that control these communications with the outside world are called interfaces and may, in general terms, be regarded as being one of three types; parallel, serial or system.

In this part of the series I shall deal with each in turn, leading up to the final part of the series on hardware aspects of microcomputers. Further episodes will deal with the complete system rather than the fundamentals.

Byte Sized Pieces

Parallel interfaces are generally used for local communication. They are extremely useful for transferring large amounts of data over reasonably short distances at high speed. Each transfer consists of a complete byte of data (hence the term parallel) and the interface must therefore consist of at least nine connections (the ninth being an earth or ground plane). In most cases there are more connections. These are controls which ensure that the data is sent only when needed and not sent when the receiving device isn't ready. This controlled transfer of data is known as 'handshaking' and varies in complexity from a simple strobe line, as is commonly found with ASCII keyboards, to a full-blown, defined standard such as the BS4421 interface, seldom seen nowadays outside specific institutions.

Versatile Interface

In implementing a parallel interface on a micro one generally uses a device such as a PIA (Programmable Interface Adaptor) or its close relative the VIA (Versatile Interface Adaptor). These come in a wide variety of guises but are essentially the same. The device contains a number of registers which can be directly accessed as memory locations by the programmer. Into these one may load information which will control the way the device behaves. A block diagram of a typical device is

shown in Fig. 1. Basically it consists of two 'ports' (a fairly obvious comparison) which may be set to operate as either inputs or as outputs. This behaviour is determined by the information set into the DDR (Data Direction Register). A logic '1' will select output and a logic '0' will select input.

To control the handshake there are usually two control lines provided per port. Each may be programmed to operate in a variety of modes, but a typical set-up is to have one line operating as a strobe. This signal is generated internally by the device and signals the data acceptor (that's the thing at the other end of the wire) that the data present on the lines at that instant is 'valid'. When the acceptor has taken the data off the lines it then signals back on the other control line that it has done so. This is the 'handshake'.

The programmer can monitor all these goings on by 'looking' at the various registers within the device (they appear to be memory locations) and inspecting the various data patterns. The job is thus made very easy for the programmer and the computer designer, unlike the days of minis.

Prior to the development of these devices, I/O, the ubiquitous acronym for Input and Output, was a complicated job involving logic to decode the various address and control busses and using the mildly complicated system of interrupts to find out which device needed to be serviced. Interrupts come outside the sphere of a hardware-based series because they are mainly dealt with in software.

Bits Of Information

The second interfacing method is serial connection. This, in theory if not in general practice, requires only two wires — one signal and one earth. A typical example of the species is the RS 232C interface, defined by the international telecommunications body CCITT. This (and most other examples) is driven from another fiendishly clever device acronymically known as a UART or Universal Asynchronous Receiver Transmitter.

In many of the modern devices this appears, like its parallel relative, as so much memory to the programmer and all the functions may be pre-defined in software

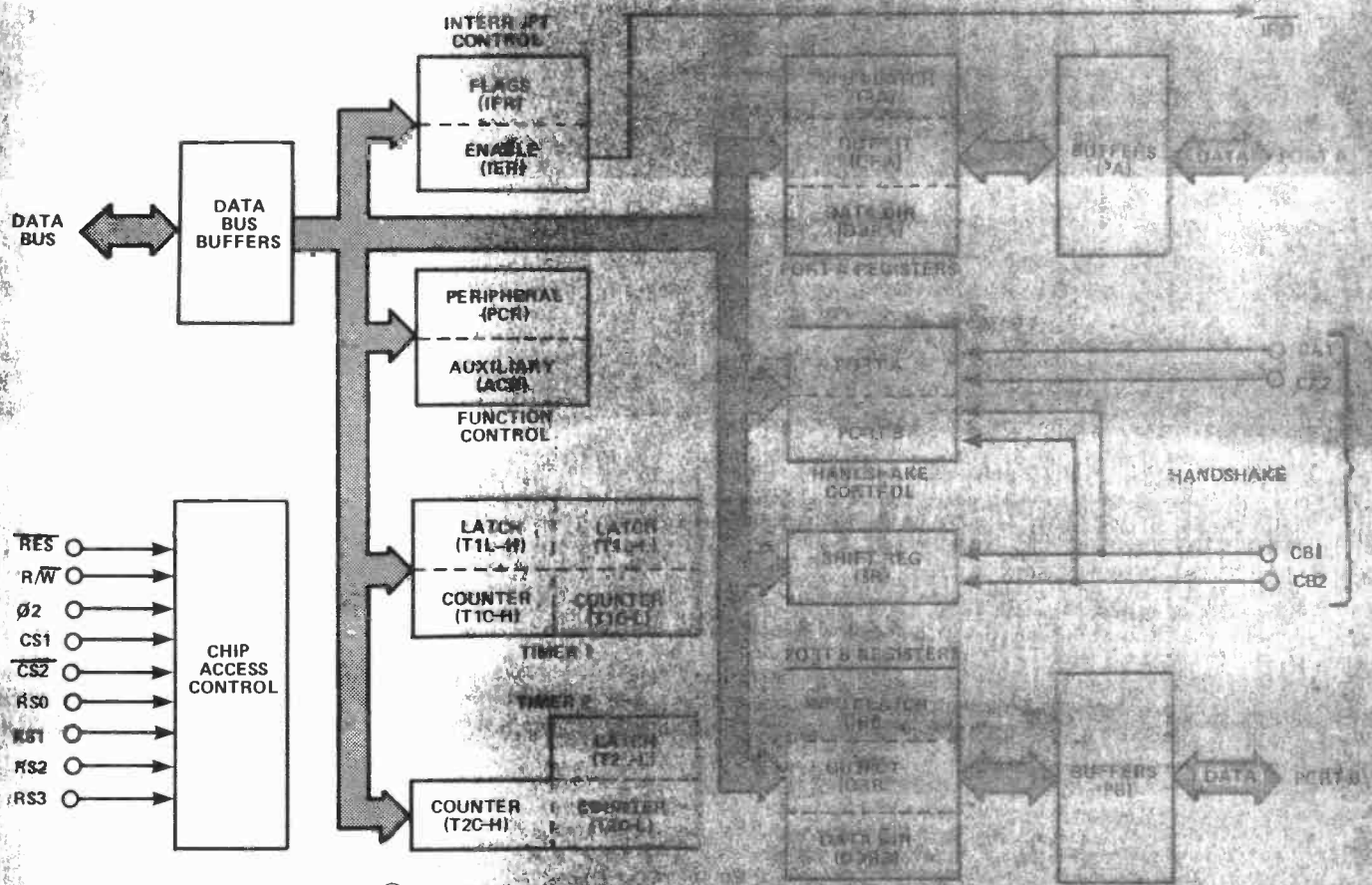


Fig. 1 A typical VIA device, the 6522, showing the various internal control registers and handshaking lines.

CONNECTOR PIN	FUNCTION	DIRECTION OF SIGNAL
1	PROTECTIVE GROUND	
2	TRANSMITTED DATA	DATA
3	RECEIVED DATA	SOURCE → ACCEPTOR
4	REQUEST TO SEND	SOURCE → ACCEPTOR
5	READY FOR SENDING	ACCEPTOR → SOURCE
6	DATA SET READY	ACCEPTOR → SOURCE
7	SIGNAL COMMON	
8	CARRIER DETECT	ACCEPTOR → SOURCE
9		
10		
11		
12		
13		
14		
15		
16		
17		
18		
19	DATA TERMINAL READY	SOURCE → ACCEPTOR
20		
21		
22		
23		
24		
25		

Table 1 The V24 signal interconnection scheme. The source can be a VDU (for example) and the acceptor a modem or even the host computer.

rather than hardware. A typical device is shown in Fig. 2. Serial transmission has to follow a definite pattern or protocol, its version of handshaking. A typical sequence would be to transmit logic '1' until ready to go, then a single 'start' bit of logic '0' followed by the data, the associated parity bit and then to terminate with two bits of logic '1'. This pattern is shown in Fig. 3. It allows the

receiving device to recognise its bit to the data.

The key to an external device is its clock. This generally runs at 11 times the serial speed of the transmission; the data is actually sampled at 11 eighth cycles which allows a certain percentage tolerance between the transmitter and receiver frequencies.

There is obviously a protocol as simple as this will not prove very reliable at high speeds and several more control lines are added to perform a handshaking function. The signal connections of the V24, a close and direct relative and purpose, identical relative, is given in Table 1. The British equivalent is based on BS 4595 Part 5 and is again regarded as compatible. For full details the relevant standards documentation should be obtained.

Serial transmissions are often made via the PSTN (or Public Switched Telephone Network) to unscramble yet another acronym. This is done with a piece of equipment known as a MODEM. Yes, that's right, it's an acronym for Modulator/Demodulator. The device converts the serial data stream into two precise audio frequencies which are sent over the telephone line and detected by a similar unit at the other end, which reconverts them into meaningful data.

Systems On The Move

The system interface is generally called the bus. It is a parallel collection of all the necessary data, address and control signals required to operate not only the main CPU board but all the memory and peripheral devices as well.

© COPYRIGHT MODMAGS Ltd

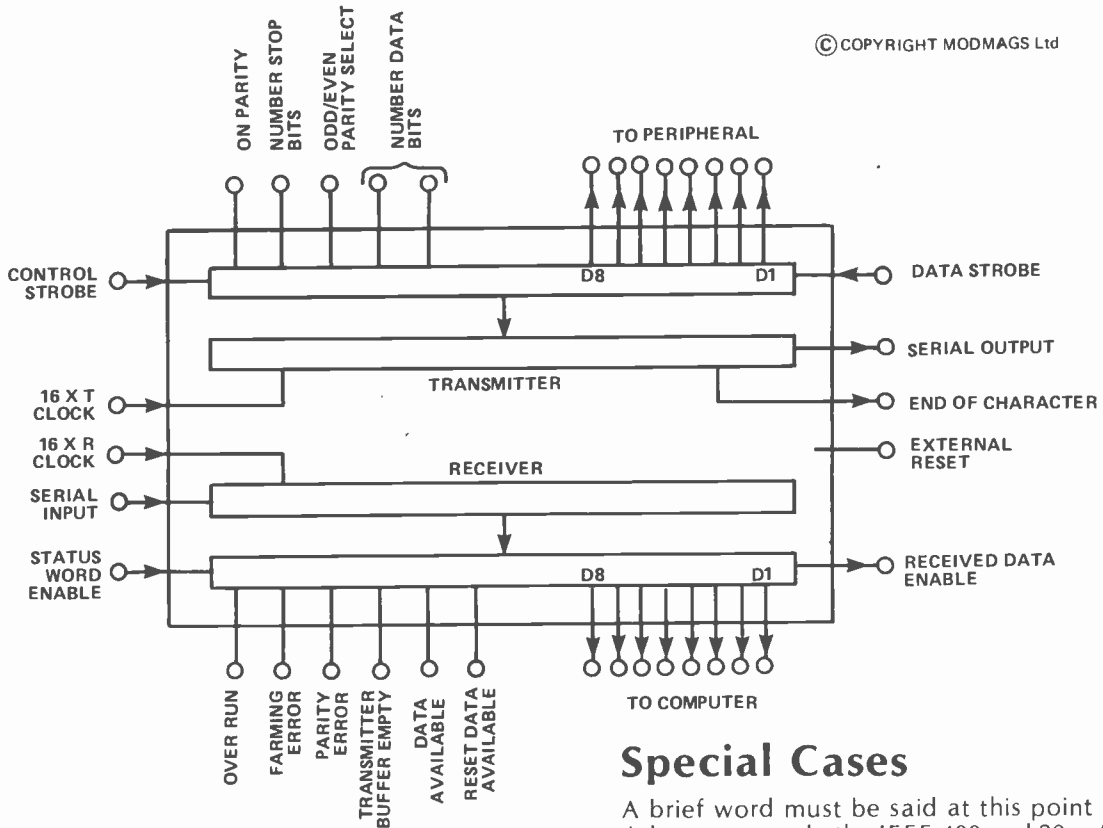


Fig.2 Block diagram of a typical UART.

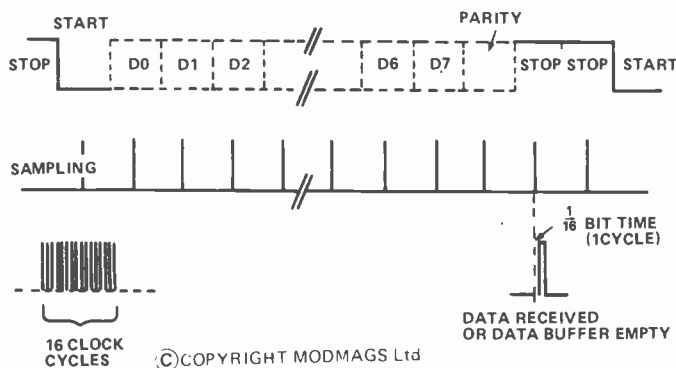


Fig.3 Timing diagram of a serial transmission.

Names such as S100, Eurobus, NASBUS, E78 and many more spring to mind, revealing that the world probably has rather more of them than is really necessary! By rights the system bus should be rigidly defined in both its operation and useage. One of the main reasons that the S100 had a bad name until the IEEE (Institute of Electronic and Electrical Engineers, of course!) got hold of it was its flexibility. This rigid defining process unfortunately takes time. We have now been waiting about three years for the E78, but perhaps even that will be slightly out of date when it arrives. If you are interested in the E78, they have produced a rather nice document, which should be available from The Secretary, E78 Committee, Avante House, 9 Bridge Street, Pinner, Middlesex HA5 3HR.

Special Cases

A brief word must be said at this point about some special cases, namely the IEEE-488 and 20 mA interfaces. The IEEE-488 or General Purpose Interface Bus came to the micro world in a rather mutilated form as the Commodore PET. Designed originally as a high speed data highway it allows multiple talkers (sources) and listeners (acceptors) to communicate along a single eight bit data bus. The bus is controlled by a number of signals and can be accessed by any of the devices. The original usage was in the laboratory where various recording instruments were connected to a single event recorder or data logger. In the case of the PET version, the pruning has resulted in one or two headaches among hardware designers, but it can be genuinely useful.

The original serial interfaces were designed around the teleprinter and teletype devices that are mainly built from solenoids. The device which controls these solenoids is very similar to the uniselectors found in old fashioned telephone exchanges and this is a current driven device. The 20 mA interface is built around a closed loop current source where the drive of 20 mA is turned on or off by a transistor which is in turn controlled by an external voltage. This allowed the interface to be electrically separated from the device, a considerable benefit as the back EMF generated by the coil of the uniselector could fry modern ICs and transistors to a turn if it escaped into the bowels of the computer.

In next month's episode we will be investigating the way in which all this magical, but rather dumb, hardware is kept together. The ingredient is, of course, that tenuous link of binary digits — software.

Post Haste

An excellent book has thudded onto my desk this month that is directly relevant to the hardware side of the series. Called 'The use of Microprocessors' by M Aumiaux and published by John Wiley & Sons it costs £12.00 in hardback and is highly recommended reading. The ISBN is 0 471 27689 8.

ETI

computing today

DECEMBER 1980

ISSN 0142-7210

60p

**FOR THE BUSINESS
OF MICROCOMPUTING**



**ON SALE AT
YOUR
NEWSAGENT
14th NOVEMBER**

CELLS AND SERPENTS

A superb new role playing game, written in BASIC for implementation on most popular computers with 8K of memory. The basic framework can be expanded almost to the limits of your imagination, and the amount of memory in your machine. Battle to the death with all the evil little nasties that lurk within the coded game cells.

MORE ON MACHINE CODE

Could this be CT's ultimate book review? We take a leaf or two out of a new publication that we think is an ideal introduction to the world of personal computing.

BASIC STOCKMARKET

Remember back in June we published a Stockmarket game? Well, we have been inundated with versions in a variety of high-level languages. This month we present the best of those submissions programmed on an RML 380Z.

GRAPHICS PART TWO

In our continuing series of the use of graphics we turn to moving things under cursor control. Not only is it educational, it's fun as well!

ZX80 TIPS

Ideas are coming in thick and fast on ways to upgrade this popular machine. We print some of the best received so far.

Articles described here are in an advanced state of preparation. However, circumstances may dictate changes to the final contents.

Send your orders to:
DEPT ETI 12, PO BOX 6, WARE, HERTS. Tel 0920-3182
 Visit our NEW shop: **3 BALDOCK ST., WARE HERTS. Telex: 817861**

BOOKS BY BABANI

BOOK NO	DESCRIPTION	£ p
BP6	Engineers & Machinists Ref. Tables	0.75
BP14	2nd Book Transistor Equivs & Subs	1.10
BP24	52 Projects Using IC741 (or equiv)	0.85
BP26	Radio Antenna Book Long Distance Reception & Transmission	1.00
BP27	Giant Chart of Radio Electronic Semi-conductor & Logic Symbols	0.80
BP32	Build Metal & Treasure Locators	1.00
BP34	Practical Repair & Renovation of Colour TVs	1.25
BP35	Handbook of IC Audio Pre-amplifier	1.25
BP36	50 Ccts use Germ/Sil/Zener Diodes	0.75
BP37	50 Projects using Relays / SCRs / Triacs	1.25
BP39	50 Field Effect Trans Projects	1.25
BP40	Digital IC Equivs & Pin Connection	2.50
BP41	Linear IC Equivs & Pin Connection	2.75
BP43	How to make Walkie Talkies	1.90
BP44	ICC555 Projects (Revised & Enlarged Edition)	1.75
BP45	Projects on Opto-electronics	1.25
BP46	Radio Circuits using ICs	1.35
BP47	Mobile Discotheque Handbook	1.35
BP48	Electronics Projects for Beginners	1.35
BP49	Popular Electronic Projects	1.45
BP50	IC LM3900 Projects	1.35
BP51	Electronic Music & Creative Tape Recording	1.25
BP52	Long Distance Television Reception (TV-DX) For the Enthusiast	1.95
BP53	Practical Electronic Calculations & Formulae	2.25
BP55	Radio Stations Guide	1.45
BP56	Electronic Security Devices	1.45
BP57	How to Build Your Own Solid State Oscilloscope	1.80
BP58	50 Circuits using 7400 Series ICs	1.35
BP59	Second Book of CMOS IC Projects	1.50
BP60	Practical Construction of Pre-amps / Tone Controls / Filters & Attn	1.45
BP61	Beginners Guide to Digital Techniques	0.85
BP62	Elements of Electronics - Book I	2.25
BP63	Elements of Electronics - Book II	2.25
BP64	Elements of Electronics - Book III	2.25
BP65	Single IC Projects	1.50
BP66	Beginners Guide to Microprocessors & Computing	1.75
BP67	Counter driver & numeral Display projects	1.75
BP68	Choosing & Using your Hi-Fi	1.85
BP69	Electronic Games	1.75
BP70	Transistor Radio Fault-Finding Chart	0.50
BP160	Coil Design & Construction Manual	0.75
BP202	Handbook of Integrated Circuits Equivs & Substitutes	1.00
BP211	First Book of Diode Characteristics & Equivalents & Substitutes	1.25
BP213	Electronic Circuits for Model Railways	1.00
BP215	Shortwave Circuits & Gear for Experimenters & Radio Hams	0.85
BP221	28 Tested Transistor Projects	1.25
BP224	50 CMOS IC Projects	0.85
BP226	Build Advanced Short wave receivers	1.20
BP227	Beginners Guide to Building Electronic Projects	1.25
RCC	Resistor Colour Code Disc	0.20

BRACKETS

Right-angle mounting brackets. Ideal for mounting, PCB panels et cetera into boxes and cases.
1BSWG - Mild steel - short face has slotted hole 6.5cm x 3.7cm long face has 3.7cm diam hole
 O/N/O 1726 Height 15cm, length 15cm, width 10cm £0.06
 O/N/O 1727 Height 25cm, length 15cm, width 10cm £0.07

SWITCHES

Description	No.	Price
DPDT miniature slide	1973	£0.16
DPDT standard slide	1974	£0.17
Toggle switch SPST 1 1/2 amp 250V ac	1975	£0.38
Toggle switch DPDT 1 amp 250V ac	1976	£0.48
Rotary on-off mains switch	1977	£0.58
Push switch - Push to make	1978	£0.18
Push switch - Push to break	1979	£0.21

Description	Colour	No.	Price
A range of rocker switches SPST - moulded in high insulation material available in a choice of colours ideal for small apparatus	RED	1980	£0.35
	BLACK	1981	£0.35
	WHITE	1982	£0.35
	BLUE	1983	£0.35
	YELLOW	1984	£0.35
	LUMINOUS	1985	£0.35

Description	No.	Price
Miniature SPST toggle 2 amp 250V ac	1958	£0.81
Miniature SPST toggle 2 amp 250V ac	1959	£0.86
Miniature DPDT toggle 2 amp 250V ac	1960	£0.92
Miniature DPDT toggle centre off 2 amp 250V ac	1961	£1.09
Push button SPST 2 amp 250V ac	1962	£1.04
Push button SPST 2 amp 250V ac	1963	£1.09
Push button DPDT 2 amp 250V ac	1964	£1.38

Description	No.	Price
Single bank wafer type - suitable for switching at 250V ac 100mA or 150V dc in non reactive loads make-before-break contacts These switches have a spindle 0.25 in dia and 30 indexing		
1 pole 12 way	1965	£0.55
2 pole 6 way	1966	£0.55
3 pole 4 way	1967	£0.55
4 pole 3 way	1968	£0.55

Description	No.	Price
Plastic button gives simple 1 pole change over action Rating 10 amp 250V ac	1970	£0.29

OPTOELECTRONICS

NEW INCREASED RANGE—ALL 1ST QUALITY LEDS (diffused)

O/No.	Type	Size	Colour	Price
1501	ARL209 (TIL209)	3mm (-125)	RED	£0.12
1502	MIL3232 (TIL211)	3mm (-125)	GREEN	£0.22
1503	MIL3333 (OPT122A)	3mm (-125)	YELLOW	£0.22
1504	ARL4850 (FLV117)	5mm (-2)	RED	£0.12
1505	MIL5251 (TIL222)	5mm (-2)	GREEN	£0.22
1506	MIL5351 (MV5353)	5mm (-2)	YELLOW	£0.22
1509	FLV1111	5mm (-2)	CLEAR (ill. Red)	£0.13

SUPER 'HI BRITE' TYPE

Type	Size	Price
1521	MIL32	3mm (-125) RED £0.12
1522	MIL52	5mm (-2) RED £0.12
1514	ORP12	Light dependent resistor £0.63
1520	QCP71	Photo transistor £0.40

LED CLIPS

Type	Price
1508/125	pack of 5 125 clips £0.17
1508/2	pack of 5 2 clips £0.21

DISPLAYS

Type	Price
DL703	7 segment D P left (30° height) Common Anode £0.85
DL707	7 segment D P left (30° height) Common Anode £0.92
DL527	7 segment D P left (50° height) Common Anode £2.08
DL727	7 segment D P right (50° height) Common Anode £2.07
DL747	7 segment D P left (630° height) Common Anode £1.73

OPTO-ISOLATORS

Isolation Breakdown—Voltage 1500—continuous fwd. current 100 mA

Type	Price
CIL74	Single Channel 6 pin DIP standard type—optically coupled pair with infra-red LED Emitter and NPN Silicon Photo Transistor O/NO 1497 £0.61
CIL074	Multi-Channel 8 pin DIP Two Isolated Channels O/NO 1498 £1.22
CIL074	Multi-Channel 16 pin DIP Four Isolated Channels O/NO 1499 £2.69

MELL II (TIL81) NPN LIGHT DETECTOR

Silicon Photo Darlington Amplifier—V_{CC} 30V V_{EC} 10V I_c 100mA Prot 300mW/IL Min 0.5 Typ 2mA I₀ 100mA nA O/NO 1495 £0.29

WIRE CONNECTORS

Entirely new range of connectors for Discrete wire. Uniquely designed Wirepost is soldered to the P.C. Board. A pre-stripped wire is inserted into the connector and easily locked by pressing the housing down. The wire is alternately removed by lifting the housing. Tin alloy plated contacts ensure good as gold performance.
 Housing consists of Thermo plastic polyester

Type	Price
1728	Single connector in red/black or white £0.12 inc VAT
1729	Three-way connector black ONLY £0.23 inc VAT
1730	Four-way connector black ONLY £0.28 inc VAT

FUSE HOLDERS AND FUSES

Description	No.	Price
20mm x 5mm chassis mounting	506	£0.18
1 1/2in x 1/4in chassis mounting	507	£0.14
1 1/2in car inline type	508	£0.18
Panel mounting 20mm	509	£0.23
Panel mounting 1 1/2in	510	£0.37

QUICK BLOW 20mm

Type	No.	Type	No.	Price				
150mA	611	7p	1A	615	6p	3A	619	6p
250mA	612	6p	1.5A	616	7p	4A	620	10p
550mA	613	6p	2A	617	6p	5A	621	6p
800mA	614	6p	2.5A	618	7p			

ANTI-SURGE 20mm

Type	No.	Type	No.	Price	
100mA	622	1A	625	2.5A	628
250mA	623	2A	626	3.15A	629
500mA	624	1.6A	627	5A	630

QUICK-BLOW 1 1/2in

Type	No.	Type	No.	Price	
250mA	631	500mA	632	800mA	634

QUICK-BLOW 1 1/2in

Type	No.	Type	No.	Price	
1A	635	2.5A	638	4A	641
2A	637	3A	639	5A	642

NUTS AND BOLTS

BA BOLTS - packs of BA threaded cadmium plated screws slotted cheese head. Supplied in multiples of 50

Type	No.	Price	Type	No.	Price
1/8in OBA	839	£1.38	1/2in 4BA	845	£0.37
1/4in OBA	840	£0.86	3/4in 4BA	847	£0.29
1/2in 2BA	842	£0.75	1in 6BA	848	£0.46
3/4in 2BA	843	£0.52	1 1/2in 6BA	849	£0.24
1in 2BA	844	£0.60	2in 6BA	850	£0.29
1 1/2in 4BA	845	£0.51			

BA NUTS - packs of cadmium plated full nuts in multiples of 50

Type	No.	Price	Type	No.	Price
OBA	855	£0.83	4BA	857	£0.35
2BA	856	£0.55	6BA	858	£0.28

BA WASHERS - flat cadmium plated plain stamped washers in multiples of 50

Type	No.	Price	Type	No.	Price
OBA	859	£0.16	4BA	861	£0.14
2BA	860	£0.14	6BA	862	£0.14

SOLDER TAGS - Hot tinned supplied in multiples of 50

Type	No.	Price	Type	No.	Price
OBA	851	£0.46	4BA	853	£0.25
2BA	852	£0.32	6BA	854	£0.25

AUDIO LEADS

No.	Type	Price
107	FM indoor Ribbon Aerial	£0.69
113	3.5mm Jack plug to 3.5mm Jack plug Length 1.5m	£0.86
114	5 pin DIN plug to 3.5mm Jack connected to pins 3 & 5 Length 1.5m	£0.98
115	5 pin DIN plug to 3.5mm Jack connected to pins 1 & 4 Length 1.5m	£0.98
116	Car aerial extension Screened insulated lead	
	Fitted plug and socket	£1.44
117	AC mains connecting lead for cassette recorders and radios 2 metres	£0.78
118	5 pin DIN phono plug to stereo headphone Jack socket	£1.21
119	2 + 2 pin DIN plugs to stereo Jack socket with alternation network for stereo headphones Length 0.2m	£1.04
120	Car stereo connector Variable geometry plug to fit most car cassettes 8-track cartridge and combination units. Supplied with infixed fuse power lead and instructions	£0.69
123	6.6m Coded Guitar Lead Mono Jack plug to Mono Jack plug Black	£1.73
124	3 pin DIN plug to 3 pin DIN plug Length 1.5m	£0.86
125	5 pin DIN plug to 5 pin DIN plug Length 1.5m	£0.86
126	5 pin DIN plug to Tinned open end Length 1.5m	£0.86
127	All colour coded Length 1.5m	£1.50
128	5 pin DIN plug to 5 pin DIN socket Length 1.5m	£0.92
129	5 pin DIN plug to 5 pin DIN plug mirror image Length 1.5m	£1.21
130	2 pin DIN plug to 2 pin DIN inline socket Length 5m	£0.78
131	5 pin DIN plug to 3 pin DIN plug 1 & 4 and 3 & 5 Length 1.5m	£0.95
132	2 pin DIN plug to 2 pin DIN socket Length 10m	£1.13
133	5 pin DIN plug to 2 Phono plugs Connected pins 3 & 5 Length 1.5m	£0.86
134	5 pin DIN plug to 2 Phono sockets Connected pins 3 & 5 Length 23cm	£0.78
135	5 pin DIN socket to 2 Phono plugs Connected pins 3 & 5 Length 23cm	£0.78
136	Coded stereo headphone extension lead Black Length 6m	£2.01
178	AC mains lead for calculators etc	£0.52

TRANSFORMERS

MINIATURE MAINS Primary 240V

No.	Secondary	Price
2021	6V-0-6V 100mA	£1.04
2022	9V-0-9V 75mA	£1.04
2023	12V-0-12V 100mA	£1.29

MINIATURE MAINS Primary 240V
with two independent secondary windings

No.	Type	Price
2024	MT1280 0-6V 0-6V RMS	£1.84
2025	MT1550-0-12V 0-12V RMS	£1.84

1 AMP MAINS Primary 240V

No.	Secondary	Price	P & P
2026	6V-0-6V 1 amp	£2.88	45p
2027	9V-0-9V 1 amp	£2.30	45p
2028	12V-0-12V 1 amp	£2.99	55p
2029	15V-0-15V 1 amp	£3.16	66p
2030	30V-0-30V 1 amp	£3.97	86p

STANDARD MAINS Primary 240V
Multi-tapped secondary mains transformers available in 1/2 amp, 1 amp and 2 amp current rating. Secondary taps are 0 19 25 33 40 50V. Voltages available by use of taps 7 8 10 14 15 17 19 25 31 33 40 25-0-25V

No.	Rating	Price	P & P
2031	1/2 amp	£3.81	86p
2032	1 amp	£5.06	86p
2033	2 amp	£6.27	1.1

2035 240V Primary 0-55V @ 2A Secondary £7.30 P & P 1.1

CASES AND BOXES

INSTRUMENT CASES. In two sections vinyl covered top and sides aluminium bottom front and back

No.	Length	Width	Height	Price
155	8in.	5 1/2in.	2in.	£2.01
156	11in.	6in.	3in.	£3.10
157	6in.	4 1/4in.	1 1/2in.	£1.93
158	9in.	5 1/4in.	2 1/2in.	£2.59

ALUMINIUM BOXES. Made from bright all folded construction, each box complete with 1/2-inch deep lid and screws.

No.	Length	Width	Height	Price
159	5 1/2in.	2 1/2in.	1 1/2in.	£0.98
160	4in.	4in.	1 1/2in.	£0.98
161	4in.	2 1/2in.	1 1/2in.	£0.98
162	5 1/4in.	4in.	1 1/2in.	£1.10
163	4in.	2 1/2in.	2in.	£0.98
164	2in.	2in.	1 1/2in.	£0.67
165	7in.	5in.	2 1/2in.	£1.54
166	8in.	6in.	3in.	£1.98
167	6in.	4in.	2in.	£1.32

SLOPE. Front aluminium boxes with black vinyl base and sides and aluminium back top and front - strong construction, easily accessible.


No.	Length	Width	Height	Price
169	2 1/2in.	5 1/2in.	2 1/2in.	£8.21
168	2 1/2in.	7 1/4in.	4in.	£6.45

Terms cash with order. Cheques/Postal Orders made payable to Bi-Pak at above address



SPACE INVASION SOUND EFFECTS

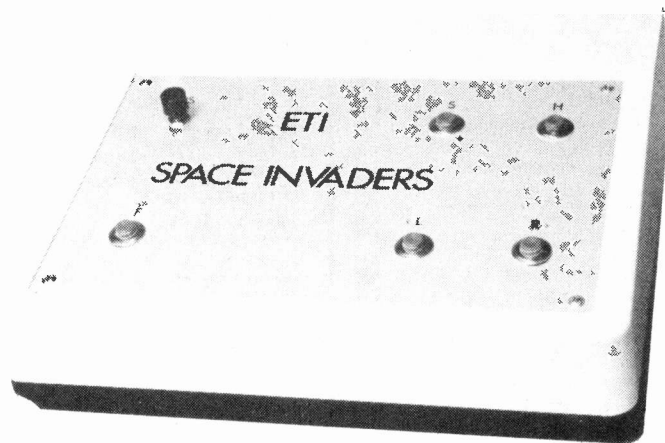Your first space invasion is but a moment away. We conclude our Invasion Game project with constructional details of the control and sound effects board. Design and development by Steve Ramsahadeo.



Last month we dealt with the main board and power supply, but before you can start repelling invaders you need a handful of controls. Our control board incorporates a sound effects generator — a must for this game.

There are four sounds in all — heartbeat, fire, saucer and explosion. The explosion is not produced by the sound board. It's taken care of by the software. When you press the start button (S on the front panel) the aliens start to advance across and

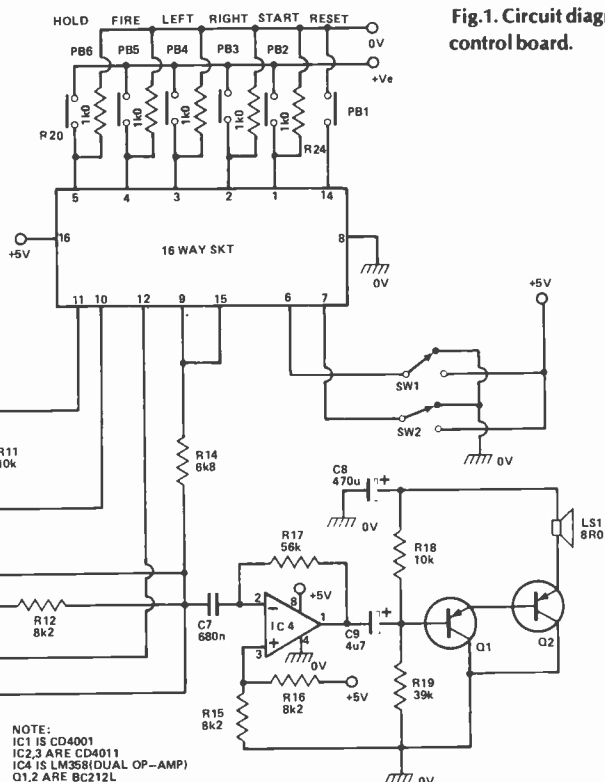
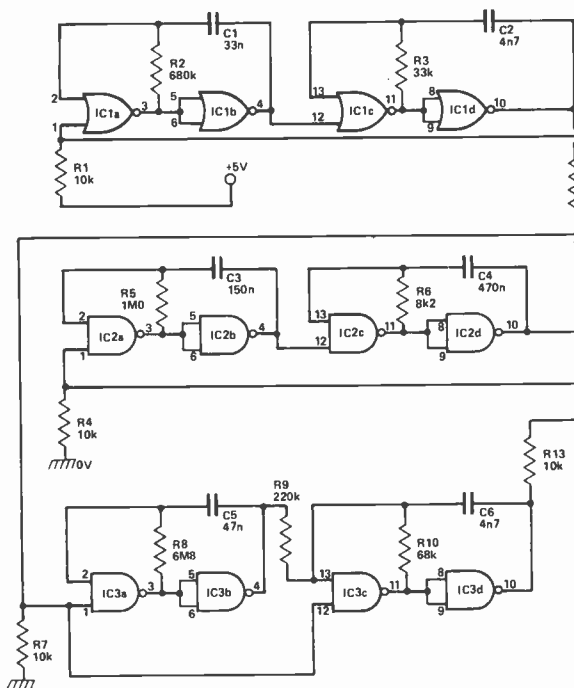


Fig.1. Circuit diagram of the control board.

NOTE:
IC1 IS CD4001
IC2,3 ARE CD4011
IC4 IS LM358(DUAL OP-AMP)
Q1,2 ARE BC212L

down the screen, accompanied by the heartbeat — an ominous pulsing sound, which speeds up as the aliens gather momentum towards you.

The universe can only be saved for humanity and Nicholas Parsons if you fight back and destroy the invaders. When you fire, the sound generator bursts into life again to let everyone know that you mean business.

BUYLINES

Tangerine Computers Ltd can supply the ETI Space Invasion project built for £99.85 all inclusive (£80.85 in kit form). The sound generator and keypad section is available built for £20.25 all inclusive (or £15.38 in kit form).

If you want to shop around for your own components, you can get the main PCB for £21.15 and the sound generator board for £5.60. The ROM is available for £17.75. Prices are all inclusive. Tangerine Computers Ltd, Forehill, Ely, Cambridgeshire.

We built the project in a new plastic desk-top, sloping front case from Vero measuring 228x216x76mm (industrial order code 65-5033K).

Vero Electronics Ltd, Industrial Estate, Chandler's Ford, Hampshire SO5 3ZR.

HOW IT WORKS

Logic instructions are transferred to and from the main board via a 16 way socket. Instructions go to IC27 on the main board via pins 1-7 and 14 and return from IC26, main board via pins 9, 10, 11, 12. For example, when the fire button (PB5) is pressed, the main board detects this and gates pin 1 of IC1a low (logic 0) via pin 11 of the socket. IC1 is wired as a dual gated NOR astable and generates a pulsed tone signal to give the 'fire' sound.

IC2 and IC3 generate the heartbeat and saucer sounds in a similar way except that these are gated on by a high (logic 1) at the respective socket pins (12 and 10), and so NAND astables are required.

The hit sound is programmed into the software and is made available at pin 9 of the 16 way socket.

IC4 acts as a summing amplifier, combining at pin 2 the outputs of the three oscillators and the hit sound (via C7). R11-14 and R17 determine the relative gain of each of the sounds. The output of IC4 is then amplified by transistors Q1 and Q2.

PARTS LIST

Resistors all ¼ W 5%

R1,4,7,11,13,18	10k
R2	680k
R3	33k
R6,12,15,16	8k2
R8	6M8
R9	220k
R10	68k
R14	6k8
R17	56k
R19	39k
R20 - 24	1k0

Capacitors

C1	33n polycarbonate
C2, 6	4n7 polycarbonate
C3	150n polycarbonate
C4	470n polycarbonate
C5	47n polycarbonate
C7	680n polycarbonate
C8	470u 25 V electrolytic
C9	4u7 16 V tantalum

Semiconductors

IC1	CD4001
IC2,3	CD4011
IC4	LM358
Q1,2	BC212L

Miscellaneous

SW1,2	SPDT miniature toggle
PB1-6	momentary push buttons
LS1	2" diameter speaker
2 off 16 way DIL IDC (Insulation Displacement Connector)	
PCB	
Vero case	

You can gamble on boosting your score to an all-time record by ignoring the aliens for the moment and firing at a flying saucer, which zooms across the top of the screen every now and then. The appearance of the saucer is heralded by its very own unmistakable sonic trademark (in other words — the racket it makes is different from the others). Keep banging away at the aliens or divert your attack to the flying saucer? It's your decision.

Construction

The unit is assembled on one PCB with a separate power supply. Construction is straightforward provided that care is taken and attention paid to the orientation of all polarised components.

Begin by inserting all wire links and Veropins followed by the IC sockets, resistors, diodes, capacitors and transistors. The ICs should be inserted last, after all the wiring to the hardware components has been completed.

The PCB fits neatly in the top left-hand corner of the specified Verocase as shown in the accompanying photographs.

A 200 mm length of 16 way Speedbloc ribbon cable using DIL (dual-in-line) connectors at each end will have to be made up. This cable will link the main board and sound board, completing the logic and power supply connections.

The pushbuttons (PB1-6) and difficulty switches (SW1,2, mounted at the rear of the case along with the mains switch) can now be wired up.

Finally, the loudspeaker is mounted at the top of the case, a few drops of Super-glue being enough to fix it firmly into place.

After checking all is well, prepare for battle!

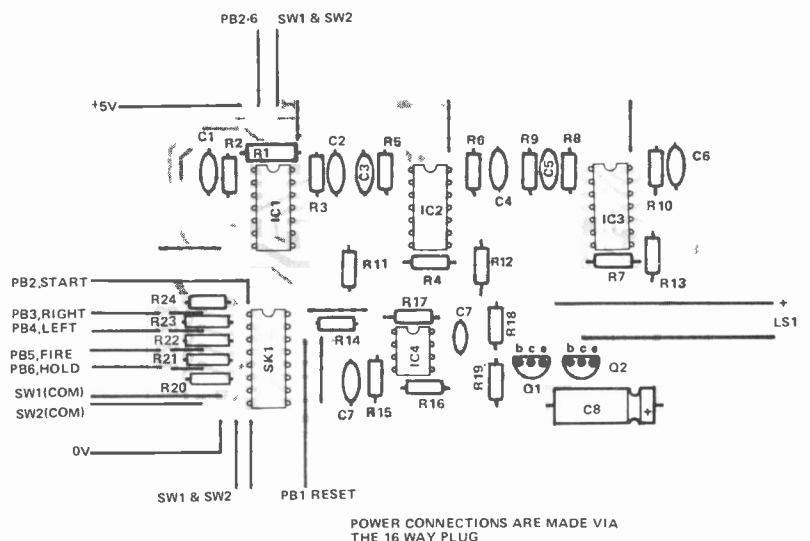
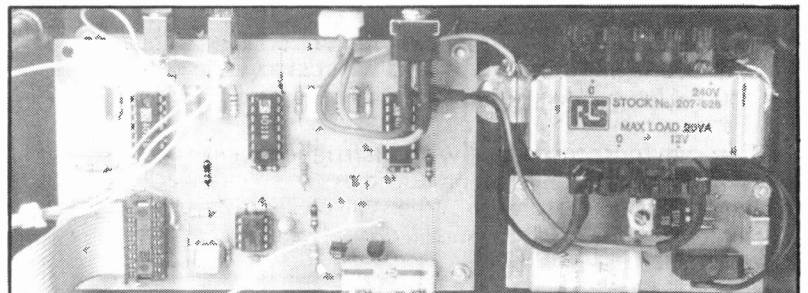


Fig.2. Component overlay.

ETI

MITRAD

The premier mail order house specialising in quality products and superior after-sales care.

SEIKO QUARTZ LCD MEMORY-BANK CALENDAR WATCH

SPECIAL PRICE ONLY £49.95
plus 85p p&p. Usually £89 or over.

- Displays hour, minute, second, month, day of the week and date in 12 hour indication – or 24 hour at the touch of a button.
- Button touch also displays month and year and dates for a designated month with Sunday dates flashing.
- Stores dates in memory up to 11 ahead, flashes 'MEMO' on designated dates.
- Illuminated time and calendar display.
- Display flashes when battery nears life end.
- Stainless steel case and wrist strap (adjustable).

In presentation case with instructions.


A LIFETIME WATCH AT A BARGAIN-OF-A- LIFETIME PRICE

Full refund if not completely satisfied.



**Mitrad, 68-70 High Street,
Kettering, Northants.
Tel: 0536 522024**

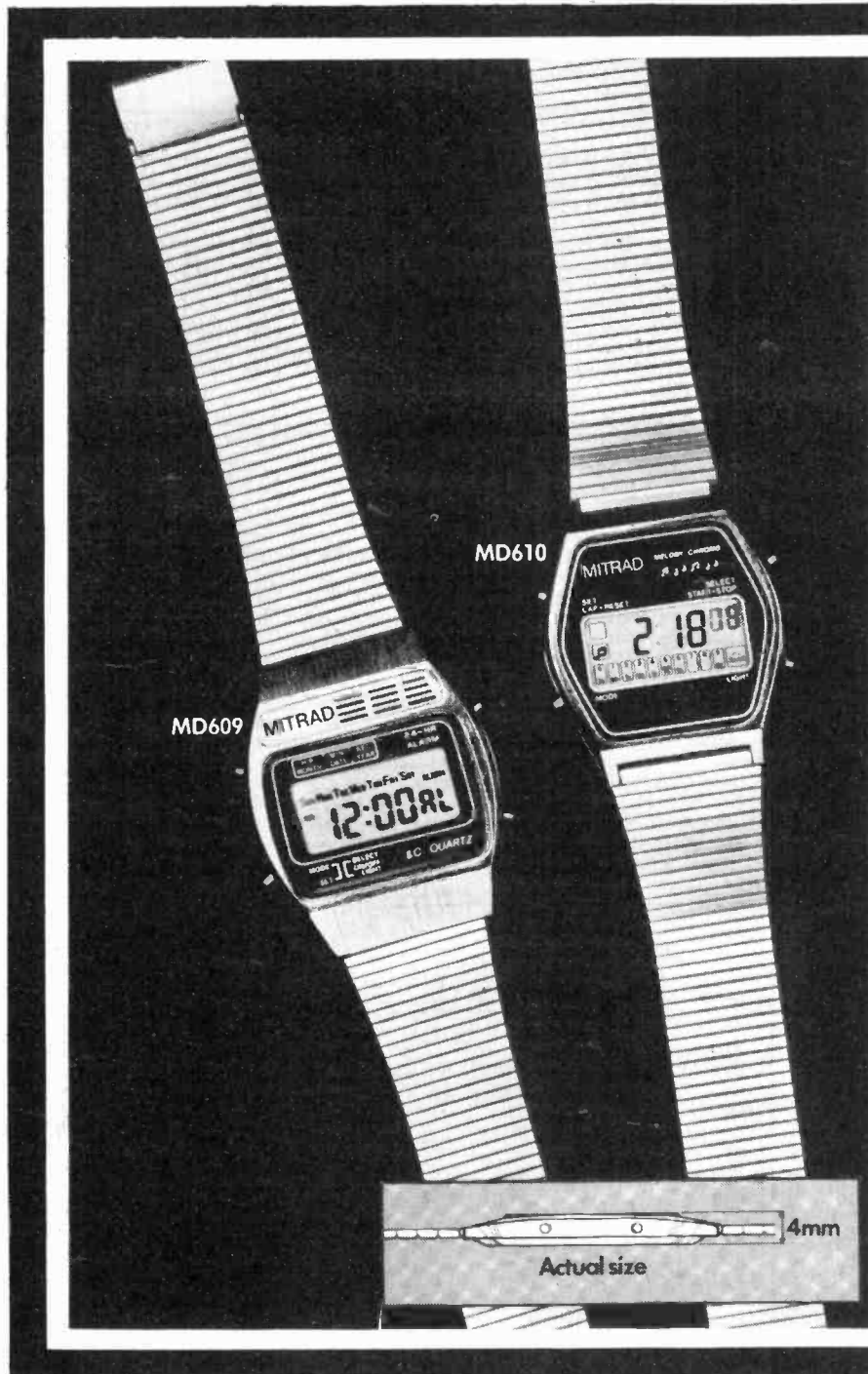This is a representative selection from the collection of guaranteed leading make and own brand watches offered through Mitrad's 7 day distribution system and backed by Mitrad's own service organisation.
For complete product range, ring or write for catalogue.
Trade price list available for bulk orders.



To Mitrad, 68-70 High Street, Kettering, Northants.
Please send me:

- | | |
|---|--|
| <input type="checkbox"/> MD609 watch(es) at £11.80 inc p&p | <input type="checkbox"/> MD606 watch(es) at £10.80 inc p&p |
| <input type="checkbox"/> MD610 watch(es) at £17.80 inc p&p | <input type="checkbox"/> MD607 watch(es) at £10.80 inc p&p |
| <input type="checkbox"/> Seiko Quartz watch(es) at £50.80 inc p&p | <input type="checkbox"/> MD608 watch(es) at £16.35 inc p&p |
| <input type="checkbox"/> MD605 watch(es) at £12.80 inc p&p | |

Total value of my order £ _____

I enclose cheque/PO or debit my Access/Barclaycard No _____

Name _____ Signature _____

Address _____ (block letters please)

☎ Credit Card holders may telephone (0536) 522024 24 hours a day stating Card Number for immediate attention. All orders despatched within seven days, subject to availability. Full refund if not completely satisfied.
Mitrad Registered in England No. 2554356.



ETI

ETI DECEMBER 1980



MD609 Gentleman's super slim flag date alarm. Only 4mm case thickness. Continuous display of hours, minutes, seconds and day; optional display of date, month, year. 24 hour alarm, alarm mode indication. Back light. Infinitely adjustable stainless steel strap. Very latest technology.
£10.95 + 85p p&p

MD610 Gentleman's dual time melody alarm chrono. Only 5mm case thickness. Continuous display of hours, minutes, seconds plus date and mode indications. 'Running horse' chrono to 1/10 sec, 12 hour alarm plays 30 seconds of 'Yellow Rose of Texas'. Infinitely adjustable stainless steel strap.
£16.95 + 85p p&p

MD605 Ladies musical alarm chrono. Continuous display of hours, minutes, seconds; optional display of day, date, month. Auto calendar. Chronograph with lap timing facilities, to 1/10 sec. 24 hour alarm plays 30 seconds of Beethoven's 'Fur Elise'. Back light. Infinitely adjustable stainless steel strap.
£11.95 + 85p p&p

MD606 Ladies five function fashion LCD watch with 3 year battery. Continuous display of hours and minutes, with month/date and date/seconds available. Auto calendar. Only 6mm case thickness. Back light. Infinitely adjustable stainless steel strap.
£9.95 + 85p p&p

MD607 Ladies slim 'sugar coated' dress watch. Continuous display of hours and minutes; optional display of month and date. Auto calendar. Back light. Integral watch and strap. In gold or silver finish.
£9.95 + 85p p&p

MD608 Gentleman's musical alarm chrono. Continuous display of hours, minutes, seconds, plus day indication. Also month and date. Chronograph with lap timing facilities, to 1/10 sec. 24 hour alarm plays 30 seconds of Beethoven's 'Fur Elise' or can be set to awaken to a single note. Back light. Infinitely adjustable stainless steel strap.
£15.50 + 85p p&p

AUDIOPHILE

Ron Harris lends an ear to a trio of record decks, from budget to top-of-the-range, and dons headphones to try the latest hip-mounted hi-fi.

This month has seen the launch of the first (of the many) Stowaway imitators — the Binatone "HipFi". (At least it's a better name.) I haven't had a chance to directly compare the two machines yet, but if the demonstration they put on at the press launch is anything to go by, Sony should be flattered but not worried.

The Hipfi sells at £59.95, as against £95 for the Stowaway and, at the launch anyway, the price differential was audibly apparent.

To say it was unimpressive is being polite. To say it sounded rotten is accurate. Impolite, but accurate.

There was a great deal of noise present in the sound, as though the treble was being boosted somewhere along the line, without the programme content at these frequencies to justify it. The headphones in use were comfortable enough, and folded flat for storage.

Overall, though, the sound was very undistinguished — rather like playing a decent cassette with the Dolby switched "out" on an encoded tape. HipFi, like Stowaway, has no Dolby — maybe Binatone were using encoded demo tapes without realising it? Most odd.

Tales Of Three Decks

Ever mindful of the call to consider budget audio more seriously within these pages, Audiophile this month takes a look at both ends of the Dual range of record decks.

The new CS505 has set a rumour rebounding around the halls that it is worthy of a high rank. Consideration was thus made with due interest and deference.

The 731Q is Dual's present top-of-the-range direct drive deck, with which the user is supplied a version of the Ortofon LM30 pickup — last seen in Audiophile hidden within an integral arm.

Just for good measure, Sony supplied me with a PSX 75 manifestation of their art, fitted with the new XL-44 moving coil pickup. Since this and the 731Q are direct competitors I thought the comparison might prove entertaining. The Dual has a slight edge in price, though, as the XL-44 is vended separately and will cost around £45 in most emporiums. It has been designed with the aim of bringing the virtues of the XL-55 Pro into more peoples' lives, by lowering the cost significantly.



CS505 — Table For All Budgets

This design is apparently meant to provide competition for such as Sansui's 222 and JVC's QLA5R decks. In order to reach a comparable price (approx £70) Dual have opted not to supply a fitted cartridge — the first time for them and a welcome development.

Features include a pitch control — unusual for a belt drive such as this — four point suspension for the whole turntable/arm assembly and a claimed ability to track high quality cartridges. Dual make great play of the arm fitted to the CS505 and on appearance it is a claim hard to justify. As you can see from the photo, it looks rather ordinary — old fashioned even.

Overall the deck is well constructed and is in stark contrast to many 'flash' oriental offerings. After seeing it around for a few weeks though, I *still* think it looks old fashioned!

Cartridge fitting is not easy by any means, but then without removable headshells or arms it never is. Dual's system of using a sub-carrier, to which the pickup is attached and which is clicked into place by the finger lift is ingenious and works well.

I fitted the Empire 400TC cartridge initially, as I felt this representative of the units that a 505 would be expected to earn its living carrying around an LP groove. Arm friction was commendably low.

Resulting Results

For a deck at this price the CS505 came through the bench test well and barring accidents, or grievous bodily harm, it is unlikely to intrude audibly to any significant extent.

After a week or so of supplication I managed to insinuate the 505 into a system next to the Sansui 222 — the great competitor. The owner of said deck was not keen at first — methinks he feared the voice of comparison.



Above: the Dual CS505 hi-fi record deck. A good clean sound quality was obtained in play.

After an evening's listening to the decks — using the Empire 400 — it transpired that both of us preferred the sound of the Dual. It came across more convincingly, with a much better mid range. Without trying a number of different cartridges, there is no ultimate way this can be taken to prove the Dual a better deck than the Sansui. It does seem, though, that the CS505 can be taken as a serious contender at least. Sound quality is undeniably good, being less muddled than most decks at the price.

Finishing Touches

Comparisons such as this allow some standard to be drawn, against which a number of people will be able to reference the facts. Physically the Dual is probably not as nice to use as the Sansui, but I would not expect this to deter many people. The final arbiter should be the sound quality and on that score the CS505 is a good product.

Baby Bio (Tracer) Growth

Biotracers are back and there are likely to be more of them this time. Last year Sony had a deck on the market with an electronic arm, in which all movement was sensed and controlled using linear motors. It cost around £600 and apparently sold "reasonably well".

The idea was obviously too good to waste on the idle rich and since then a horde of little Japanese genii has been beavering away to bring the marvels of bionic record playing to a wider audience. The result is the £270 PSX 75.



Sony PSX-75 bionic record deck. Note the pillar in the background and the prisms set into the turntable mat. These control record size indication.


The PSX 75 sells as a mid-price (eh?) general purpose record deck, which has full electronic control of the arm. Photoelectric cells are used with small prisms (mounted inside the turntable mat!) to sense record size and there is push button movement control over the arm from outside the dust cover. Quartz-locked speed — naturally — and a 'dial-on' tracking weight control are also present. This means you can set the value while the deck is actually playing a test record. Neat, that.

What I do not like, however, is the lack of a separate bias control. Twiddling the tracking force automatically selects a value for bias and this cannot be altered. I found this meant I was having to set up cartridges to higher forces than were usually needed to obtain secure tracking. Not a vital issue, maybe, but an unnecessary hindrance.


Traces of Trackers

Rather than using up half the words in the Oxford Dictionary trying to describe the Biotracer principle, deflect your eyes onto the drawing for details. Incidentally, you too can have your very own copy of this artwork. All you have to do is buy a PSX 75. The diagram comes stuck on the dust cover as transparent film!

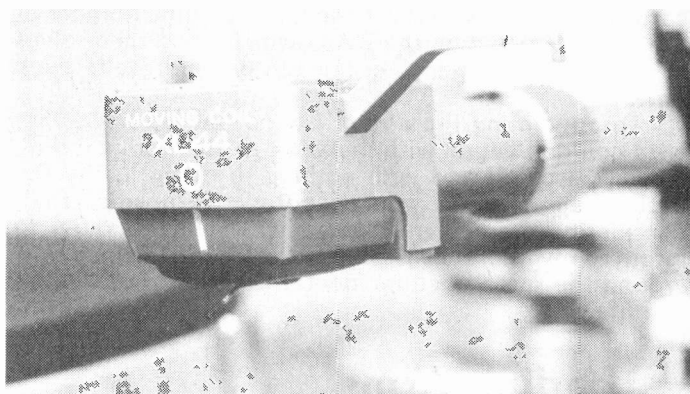
There is no setting up to do with this deck, save that required by the pickup. Arm height is adjustable too, so that vertical tracking angle can be optimised — even the arm rest moves up and down in time with the pillar!



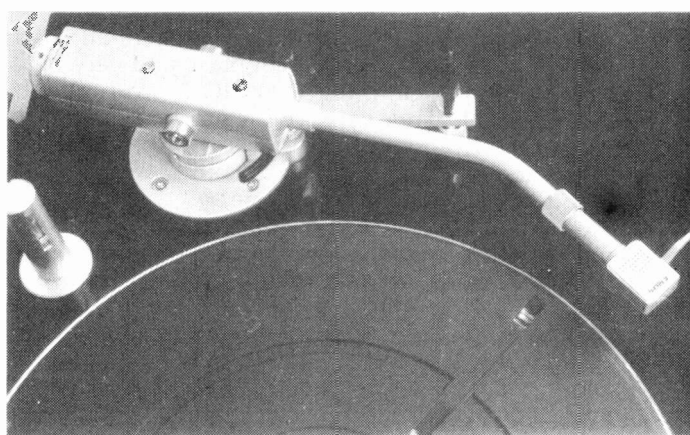Above: the XL-44 moving coil cartridge. It comes as part of its own headshell.



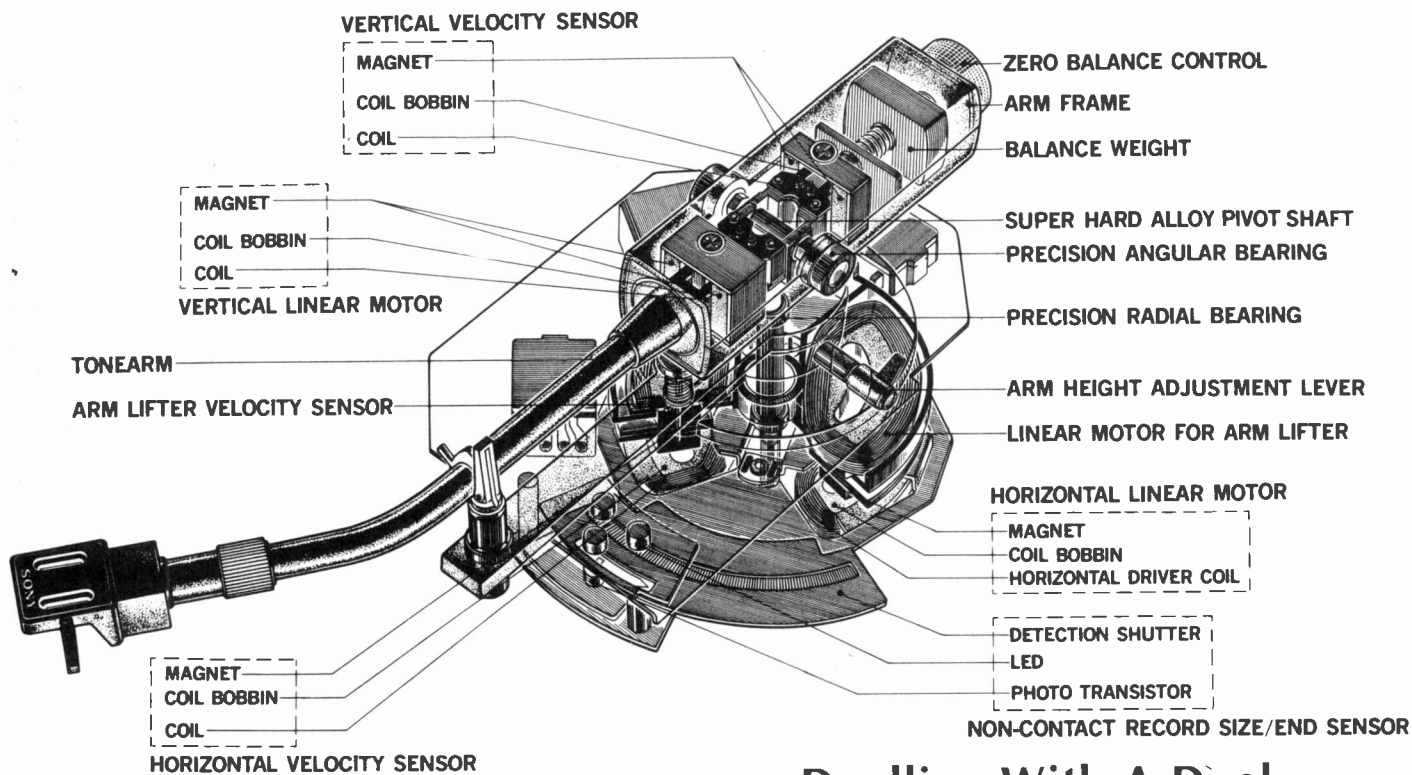Above: the mighty linear-motor driven Biotracer pickup arm. On the next page you will find an exploded diagram to explain the clever bits! →



Above: the ultimate in complexity? Note the use of two linear motors along each movement axis.

Sony supplied the deck with that XL-44 moving coil cartridge, their new baby. I tried it out with a number of head-amps, including the HA55 which Sony themselves make and recommend, obtaining similar results each time.

Disappointing I'm afraid. I liked the old XL-55 Pro, but I couldn't get on with the XL-44 at all. I found it dull, lacking in detail and with nothing to really justify the exchange of fifty pound notes. Surprising that, considering the pedigree, but it was always a relief to return to my reference pickup, a Coral MC81 (which sells around the same price incidentally) for the extra detail and life.

Loading Arms

The PSX 75 itself is an excellent performer, however. I tried a variety of top flight cartridges, including the Coral, and was returned good results with them all. That arm, bionic or not, has a fairly high mass and very high compliance units, ie Goldring G900 IGC, are best left alone. Moving coils work very well, so the loss is not an horrendous one. If you still harbour any lingering wisps of mistrust about auto-play decks, take a walk into a dealers and have a play with this one.

Despite the little prisms, I'd still recommend anyone who buys a PSX 75 to change the mat and play singles by use of the arm transport controls. Both the Metrocare mat and a GA Soundisc improved the mid-range performance of the deck, with the Soundisc cleaning up the bass considerably, too.

Overall, then, the deck is a good product, well suited to its intended market and sensibly priced. The finish is immaculate as one would expect, with the controls working well at all times.

Duelling With A Dual

As a direct competitor with the Sony, the Dual 731Q could not be more of a contrast. The arm is the exact opposite of the Biotracer. Dual have gone for refining the simplest method possible and concentrated upon resonance suppression. As you can see from the diagram, the counter weight is a complex affair and there is provision to 'tune' the arm/cartridge resonance for individual pickups, to give best bass performance.

Like all Dual decks (except the CS505) the 731Q arrives with resident cartridge — in this case an Ortofon. I reviewed the LM30 in Audiophile only recently (June 80 issue) and would refer Seekers Of The Tiniest Detail thence. Suffice it to say here, that this is a low mass, high compliance design, capable of excellent sound quality.

The 731Q has quartz speed lock and pitch control, just to be different. Here, however, the pitch lock is not disengaged if you alter the speed from nominal. Now you can have accurate 32 RPM, if the mood takes you. Why anyone would want a deck that ran at the wrong




Above: the 731Q top-line Dual. Quartz of course.


speed accurately is quite beyond me. Maybe the orchestra were a little slow one day? Speed 'em up lads! It's all quartz-locked!

Very silly.

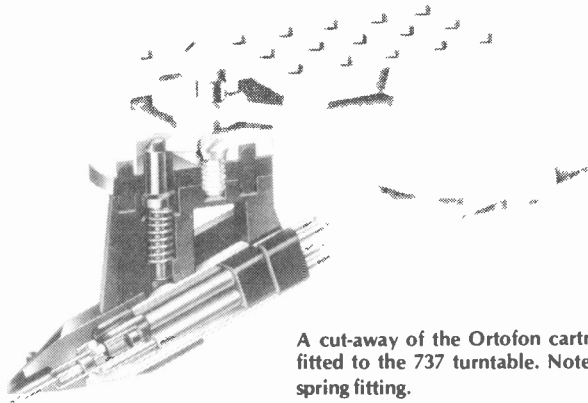
Once again, here is an expensive record deck with a mat fitted to it that would be better employed under a plant pot. In this case it is *really* bad and Dual should sell off their stocks, as floppy frisbees or something, quick,



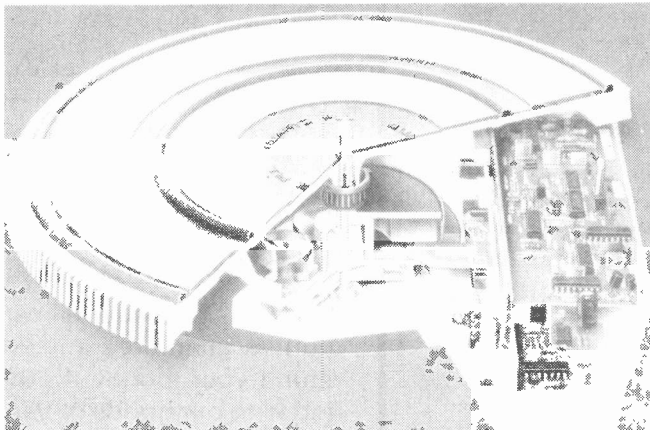A cut-away of the Ortofon cartridge fitted to the 737 turntable. Note the spring fitting.



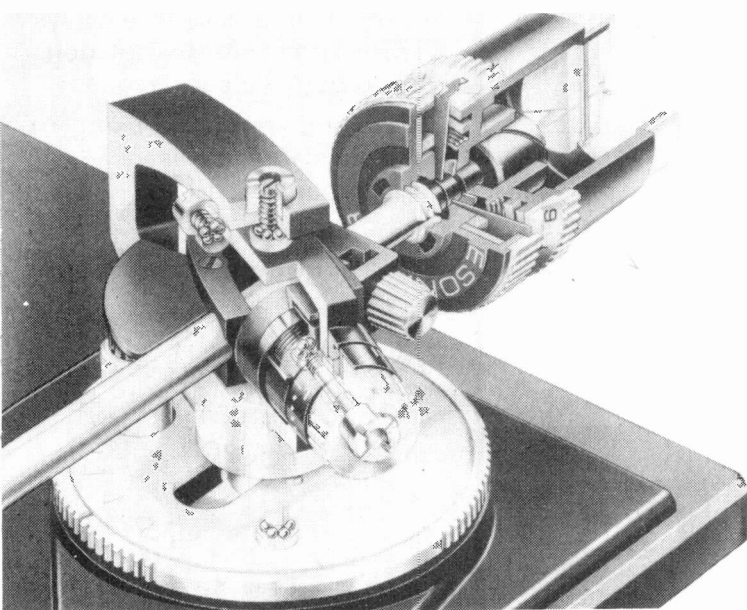Above: being a bit fond of cut-away photos, Dual supplied this shot of the 731Q circuitry. More complex than a belt of rubber is it not?



Above: even the counter-weights are complex these days. This shows the Dual's ability to mass-tune the resonance of the pick-up arm and cartridge assembly. Dead clever these continentals.

and look to something more substantial. The difference in the sound of the 731Q with a good sensible mat fitted was astounding.

With a Spectra or Metrocare in place the Dual/Ortofon is a fine combination and good value for money — as purchased, however, it simply does not allow the LM30 to do its stuff. Come on Dual, give yourselves a chance!

Comparative Studies

I suppose having mentioned the competitive links between the two decks, the question which remains to be answered is which of the two, Sony or Dual actually represents better value for all that money. The nice thing here, for me, is that the two products are so totally different in their approach to a common end that sidestepping a final choice is easy!

The Sony offers a better finish, better ergonomics and leaves the choice (and the cost) of pickup to the user. The Dual offers a very high quality cartridge as part of the package, at a lower price overall, and a very good arm which is tunable for a range of cartridges. Trouble is, having supplied you with a pickup in the first place, chances are you're never gonna use the facility to its fullest extent.

If you like the sound of the Ortofon LM30, then the Dual 731Q will probably be for you. Anyone who doesn't is stuck with it, it seems. Including a cartridge in a deal with a turntable invariably means you're selling the sound of the cartridge rather than the deck. Dual must be happy with the idea at least.

If for no other reason than that, I'd tend to prefer the Sony and go my own way with pickups. Either way you're going to need a new turntable mat and a fairly big shelf to take the deck, as neither of them is exactly compact.

At the price it is worth noting that £210 would buy you a TD160S and SME Series IIIS — a combination which would sound better than either, albeit at the cost of considerably more trouble to set-up, adjust and use.

Trailing Off

Next month we're giving the once-over to the two Pioneer cassette decks, namely the CT-200, which is the new low price metal deck and the CTF-1250, the not-so-new, not-so-low-price flagship design.

	DUAL CS505	SONY PSX 75	DUAL CS731Q	
WOW AND FLUTTER:	±0.05%	±0.035%	±0.025%	(ALL DIN)
SIGNAL-TO-NOISE RATIO:	69 dB	79 dB	75 dB	(ALL DIN B)
START-UP TIME (to 33 1/3):	2 S	1 1/2 S	2 S	
SUSPENSION:	4 point — spring	—	4 point — spring	
TRACKING ERROR:	0.16°/cm	+2, -1°	0.16°/cm	
TRACKING WEIGHT RANGE:	0-3 g	0-3 g	0-2 g	
CARTRIDGE WEIGHT RANGE:	2 g-10 g	1 g-15 g	2 g-9 g	
APPROX. PRICE:	£70	£270	£240 (inc. cartridge)	ETI

Metac

ELECTRONICS & TIME CENTRES

QUARTZ LCD 11 Function Slim Chronograph

12:30^{pm}
Hours mins secs

8 14TH
Month date day

0:00⁰⁰
Min secs 1/10 1/100



Price only
£7.95

Also available:
SOLAR CHRONOGRAPH
M9 Price £11.95

6 digit, 11 functions,
Hours, mins., secs., day,
date, day of week,
1/100th, 1/10th, secs.,
10X secs., mins.
Split and lap modes.
Back-light, auto calendar.
Only 8mm thick.
Stainless steel bracelet
and back.
Adjustable bracelet.

SAME DAY DESPATCH.

M3 Price includes POST & PACKING

QUARTZ LCD ALARM with Snooze Alarm

12:30^{pm}
Hours mins secs

8 14TH
Month date day

7:30^A
Alarm



Price only
£7.95

6 functions plus Alarm.
Conference signal,
5 minute snooze alarm,
Conference signal sounds
4 secs. before main alarm
to give advance warning
and an option to cancel.
Snooze sounds 5 mins.
after main alarm and is
always preceded by the
conference signal.

SAME DAY DESPATCH.

M4 Price includes POST & PACKING

QUARTZ LCD ALARM CHRONOGRAPH with 12/24 display

12:30^{pm}
Hours mins secs

8 14TH
Month date day

0:00⁰
Min sec 1/10th



Price only
£11.95

Also available:
SOLAR ALARM CHRONO
M7 Price £17.95

Alarm
Hours, mins, secs, day
of week, Month, date,
day of week, alarm,
hour, mins., a.m./p.m.
24 or 12 hour display
mode. Alarm test.
Chronograph, lap
time, stop watch 1/10
secs.

M64 Price includes POST & PACKING

QUARTZ LCD Ladies Day Watch

Hours, mins., secs., day,
date, back light, auto
calendar.

12:30
Hours mins

8 14
Month date

:45
Secs



Price only
£4.95

Fully adjustable bracelet.
Only 25 x 20mm and
6mm thick.
Silver or Gold.

M15 SAME DAY DESPATCH. P.&P. included

QUARTZ LCD Ladies Cocktail Watch

Beautifully designed with a very thin bracelet.

12:30
Hours mins

8 14
Month date

:45
Secs



Price only
£10.95

Hours., mins., secs., day, date,
backlight and autocalendar.
Bracelet fully adjustable to
suit slim wrists.
State Gold or Silver finish.
Only 25 x 20 x 6mm.

M18 SAME DAY DESPATCH. P.&P. included

METAC GUARANTEE

All METAC products carry 12 months guarantee and we also refund your money if not satisfied with our goods or service in the first 10 days.

METAC's well equipped service centre minimises service delays. Please note, we do not delay your order to clear cheques.

Telephone your order using
Barclaycard/Access

Number on on

**03272 -
5983**



24 hour answering service
OR COMPLETE THE
COUPON

HANIMEX Electronic LED Alarm Clock

Features and Specification:

Hour, minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright/dim modes control. Size: 5.15" x 3.93" x 2.36" (131mm x 11mm x 60mm). Weight: 1.43 lbs (0.65 kg).



M13

Price only
£10.20 Mains operated.
Thousands sold!

QUARTZ LCD 5 Function GENTS/BOYS

Hours, mins., secs.,
month, date, auto
calendar, back light,
quality metal
bracelet. 6mm thick.

12:30
Hours mins

8 14
Month date

:45
Secs



Price only
£5.95 P.&P. included

M1 SAME DAY DESPATCH.

WHOLESALE MAIL ORDER

Send for our trade price list and order details. Sell our products to your friends and earn yourself

£££'s

**NEW 24 HOUR
DESPATCH SERVICE**

METAC have opened a new even faster Mail Order and Service Centre at DAVENTRY. Orders received before 3.30 p.m. will be despatched same day.

VISIT OUR ELECTRONIC TIME CENTRES AND SEE ONE OF THE MOST IMPRESSIVE QUARTZ WATCH RANGES IN BRITAIN

**QUARTZ MELODY
Alarm Chronograph
INCREDIBLE WATCH 34 Functions**



5 independent working modes, day of week in English, French or German. (Just select the one you like). Hours, mins., secs., day, date, countdown alarm, dual time zone, 1/100th sec., stopwatch. Lap/split time, 1st and 2nd place times. Melody test function.

Price only
£16.95

Price includes
POST &
PACKING

M30 SAME DAY DESPATCH.

**SEIKO ALARM
CHRONOGRAPH**

With WEEKLY Alarm, Hours, mins., secs., month, date, day, am/pm. Weekly alarm — can be set for every day at designated time, e.g. 6.30 am on Monday, Wednesday and Friday. Alarm set time displayed above time of day. Full stopwatch functions, laptime, split etc.



Price only
£49.95

including POST & PACKING

**SAME DAY
DESPATCH.
M10**

**METAC IN
LONDON**
327 EDGWARE ROAD, LONDON, W2
01-723 4753



58 QUEENSWAY, LONDON, W2
Opposite Bayswater Tube Station
Shop open 12 hours/day, 7 days/week

Situated in the heart of London's fast-moving electronics area. A very large selection of watches and consumer electronics products. Also many bargain discount/sale items.


2nd only to Oxford Street, this is London's round-the-clock international tourist area. An excellent selection of expensive famous watches, plus all the popular models.

**METAC IN
NORTHAMPTON**
11 ST. GILES SQUARE, NORTHAMPTON
Tel: (0604) 39550




An excellent selection of watches and electronics. This shop also has televisions and video recorders to rent or buy.

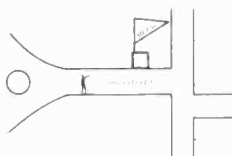**METAC IN
DAVENTRY**
67 HIGH STREET, DAVENTRY



Situated in the middle of Daventry, only a short walk from Metac's Mail Order Centre, the shop stocks a wide range of watches and consumer electronic products. You may also rent or buy televisions and video recorders here.

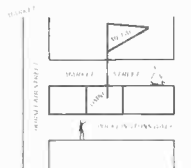**METAC IN
LEICESTER**
OMNI SHOPPING CENTRE, 27 MARKET STREET
LEICESTER



Situated in the Omni walk-round shopping centre. Metac at Omni stocks an excellent range of quality watches at very attractive prices.

ALSO IN STOCK

NEW SEIKO	Digital-Analogue Alarm Chrono	£73
SEIKO	James Bond Memory Bank Now only Pico-Quartz	£39
BEL-TIME	50 Function All Singing, all Dancing Wrist Computer	£29.95
BEL-TIME	Alarm	£12.95
BEL-TIME	Chronograph	£10.95
BULER	Swiss Digital and Quartz-Analogue Collection	
CASIO	Alarm Chrono. Lowest price anywhere. Send for details	
OTRON	Korean Waterproof Ladies' and Gent's Solar Alarm Chronographs, etc.	
TRAFALGAR	Digital-Analogue Alarm Chronograph	£29.95

Also large selection of popular Dual-time, Alarm, Countdown, Musical, Ladies' and Gent's Watches

**WANT TO KNOW HOW
THEY WORK?**

Send £1 and we will send you the 40-page Watch Report. A technical survey which describes in detail the function and operation of electronic watches in a completely unbiased and objective way.

MAIL ORDER

Mail Order is a safe and simple way to purchase goods. You are well protected by the consumer mail order laws and at Metac we combine a fast service with a genuine 10-day home approval scheme. You may examine any merchandise purchased through our mail order division, in your own home for 10 days at no cost to yourself. All postal charges are pre-paid by Metac. For more information on Metac mail order products send for our free literature, brochure and watch-care leaflets, to: **METAC ELECTRONICS LITERATURE, 47 HIGH STREET, DAVENTRY, NORTHANTS.**

POST COUPON TO: METAC (24 hour despatch centre), FREEPOST, 47a High Street, Daventry, Northants.

PLEASE COMPLETE BOTH COUPONS

Please send me

I enclose P.O./Cheque value

Barclaycard/Access No.

Name

Address

FROM:
METAC ELECTRONICS & TIME CENTRE, (ETI)
67 HIGH STREET, DAVENTRY, NORTHANTS.

Name

Address

POST, PACKING AND VAT INCLUDED IN PRICE.

TECH TIPS


CMOS Tester

C. Jordan, Sompting

This circuit was designed to test 4001 and 4011 devices which were suspected of being damaged due to static from

careless handling. Two gates on each side of the 14 pin DIL package are tested independently. Each pair is connected as an astable, the timing capacitor being switched, to allow the device to oscillate at two different frequencies.

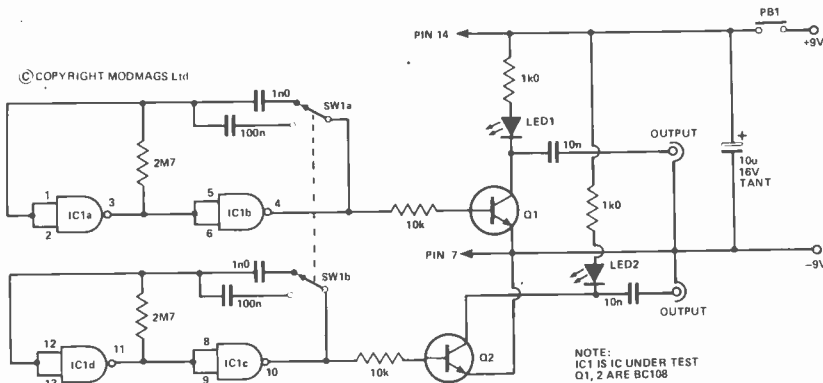The output of the astable is fed to a transistor which acts as a buffer, driving the LED and providing an audio output to a crystal earpiece. PB1 should be a push-to-make type, so that it is impossible to insert or remove a device with the power on. Although intended to test 4001 and 4011 devices, it will also quite happily test 4030, 4071, 4077, 4081 and 4093.



Digital Clock Switch


R.D. Pearson, Sheffield

This circuit was designed for a digital alarm clock such as the Hanimex alarm clock sold by ETI's marketplace. It will switch an appliance such as a light or radio on or off manually using push-button switches and will also switch the appliance on when a negative output from an alarm clock triggers it.

IC1a,b form a flip-flop driving the relay via Q1 or an LED via IC1c,d. Input triggers are provided by PB1 and PB2 which are suppressed by R3, C3 and R4, C4 to prevent erratic operation from mains transients and interference.


The ON input trigger to IC1a is driven by a negative pulse from a digital alarm clock. The easiest place to find this is on the loudspeaker of the clock using a multimeter or 'scope across the speaker terminals when the alarm is bleeping. The negative output is connected to the trigger input and the positive output to 0V.

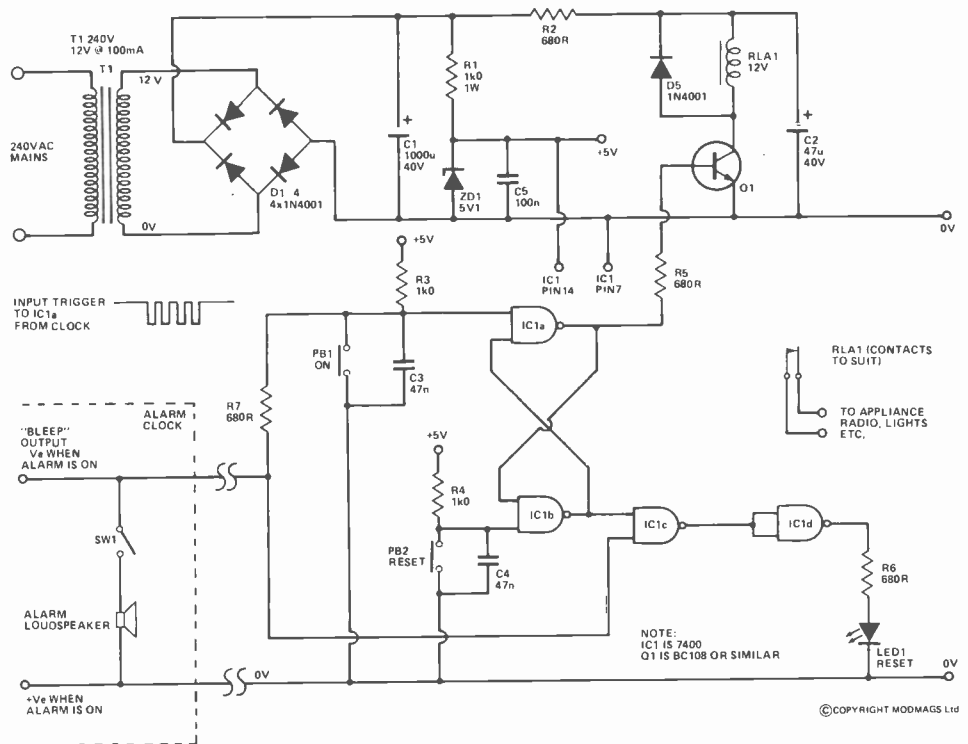IC1c,d provide a flashing LED indication that the alarm is on. If desired, switch SW1 may be connected in series with the loudspeaker.



©COPYRIGHT MODMAGS Ltd

Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items. ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International, 145 Charing Cross Road, London WC2H 0EE.

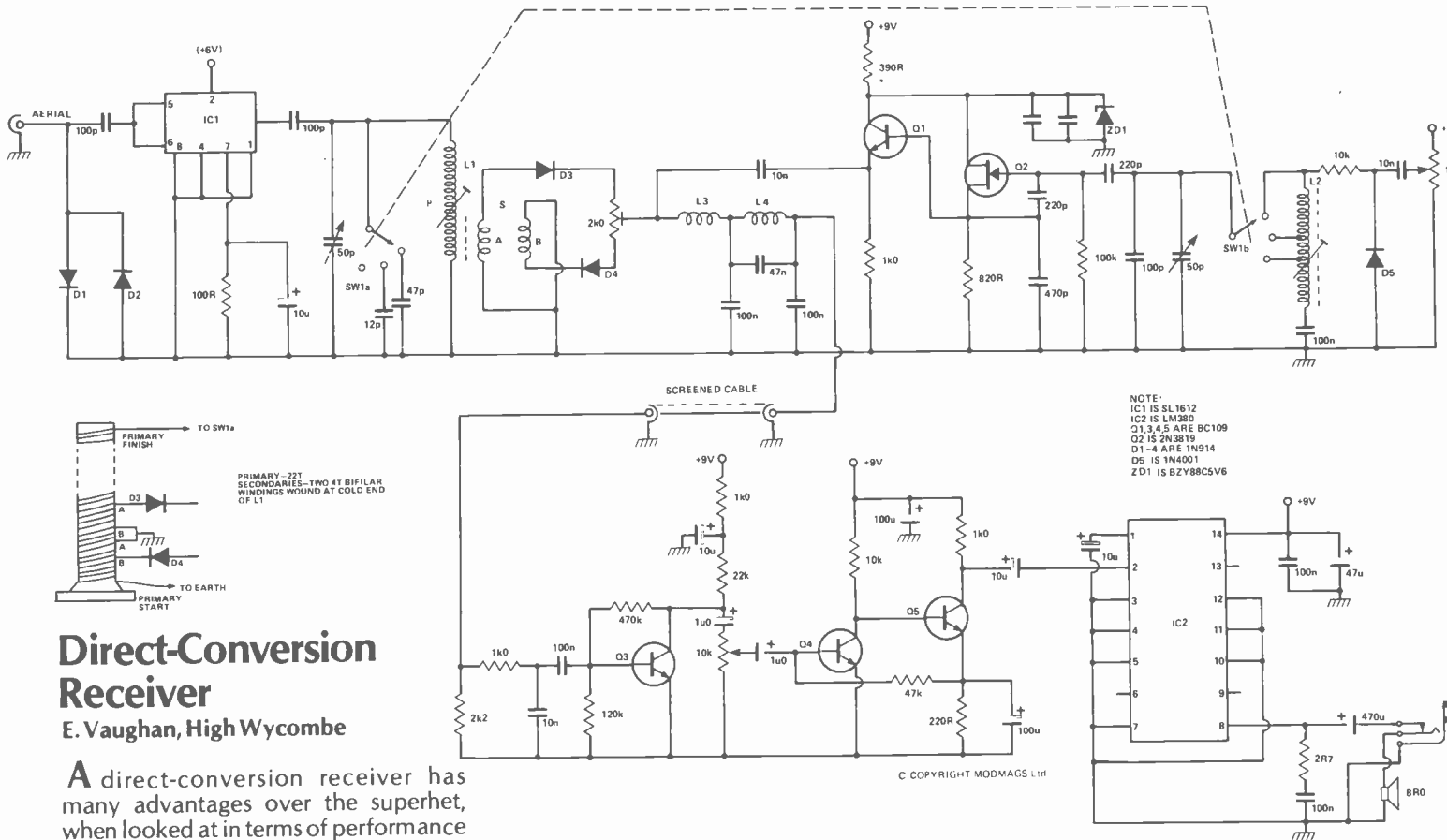

Direct-Conversion Receiver

E. Vaughan, High Wycombe

A direct-conversion receiver has many advantages over the superhet, when looked at in terms of performance versus complexity and cost (this receiver can be built for around fifteen pounds or less). The SL1612 is an RF amplifier providing pre-mixer gain. D1,2 protect the IC. The mixer is a balanced type, driving an M-derived single section lowpass filter with a cut-off frequency of 3 kHz. The oscillator is a Colpitts type followed by a buffer stage to prevent pulling of the oscillator when tuning. Although mainly for SSB and

CW, AM can be resolved by tuning to zero beat. The circuit employs varicap tuning.

Using a wire aerial 66 feet long, separated at 33 feet by an insulator and fed with 75R coax, it is possible to pick up stations from all over Europe, North and South America and Africa. When

correctly set up, this receiver should switch-tune to the 14 MHz, 21 MHz and 28 MHz amateur bands.

L1,2 are wound on 3/8 inch diameter slug tuned formers using 36 SWG wire. Winding details of L1 are shown in the diagram. L2 is 25 turns tapped at 9 and 14 turns. L3 is 1 mH and L4 10 mH.

Automatic Nicad Charger

M.G. Baker, Port Elizabeth

This circuit will charge up to eight 1V25 Nicad cells at a constant current of up to 100 mA. When the battery voltage reaches a preset level, the charger trips and charging ceases.


The voltage of a Nicad cell increases as it is charged and reaches a value of approximately 1V45 when fully charged. A battery of eight cells would, therefore, be fully charged when its voltage is 11V6. The recommended charging current of a Nicad cell is usually 10% of its mAh rating ie 50 mA for a 500 mAh battery.

To set up the circuit, connect a voltmeter across terminals A and B. PR1 is adjusted to the desired trip voltage eg

11V6 for eight cells. A milliammeter is then connected between terminals C and D. Reset button SW1 must be momentarily depressed and the required charging current is adjusted by PR2.

The battery may now be connected

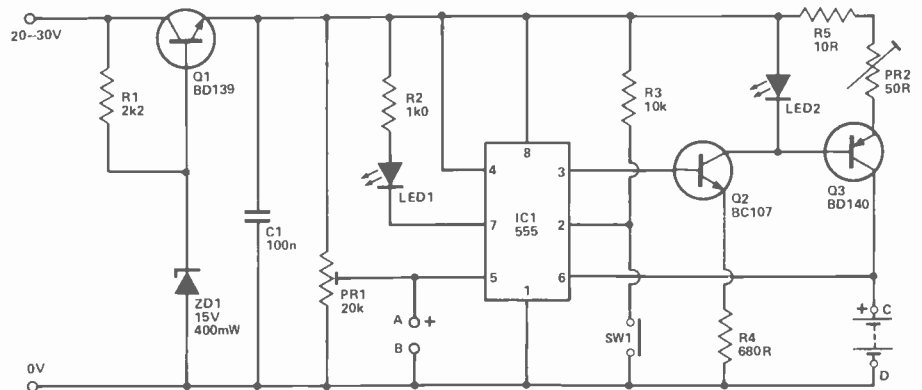between terminals C and D. When SW1 is depressed, LED 2 comes on indicating the battery is charging. When the battery voltage exceeds the preset trip voltage, the charging current drops to zero and LED 1 comes on indicating the battery is fully charged.



CHROMASONIC electronics


48 JUNCTION ROAD, ARCHWAY, LONDON N19 5RD — 50 yards from Archway Station & 9 Bus Routes
 TELEPHONE: 01-883 3705 / 01-883 2289

YOUR SOUNDEST CONNECTION IN THE WORLD OF COMPONENTS AND COMPUTERS

PETS & SYSTEMS

8N 8K RAM — £399
 16N 16K RAM — £499
 32N 32K RAM £599
 CASSETTE DECK — £55

343K Twin Floppy Disk
£695

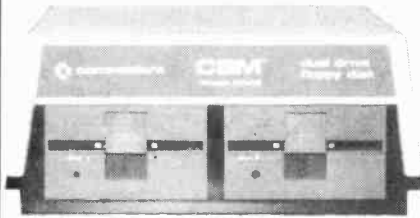


COMPLETE 32K SYSTEM £1789


NEW 32K with 80 col Screen
 Twin Disk Drive 950K **£825**
£896

All with new keyboard
 and green screen

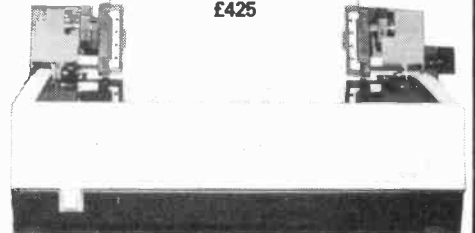FRICION FEED PRINTER
£375
Tractor Feed Printer
£425



NEW SHOP

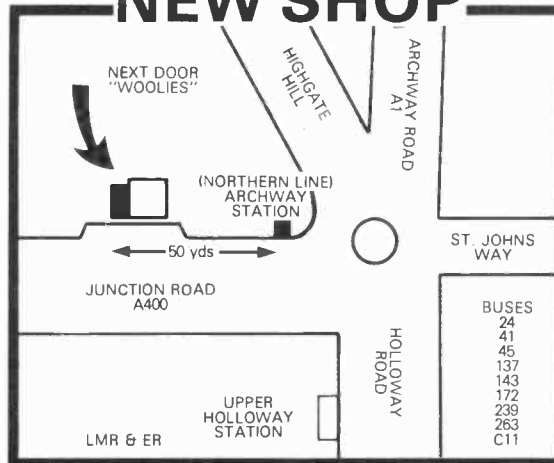

VIDEO GENIE

VIDEO GENIE based on TRS80

Utilises Z80, 12k level II Basic,
 Integral Cassette Deck, UHF O/P
 16k RAM,
 all TRS80 features

£289

MEMORY EXPANSION KIT

Suitable for UK101, Superboard expansion using 2114's each board has 16K ram capacity kit contains:

- ★ On board power supply
- ★ 4K Eprom expansion
- ★ Fully buffered for easy expansion via 40 pin socket
- ★ 8K kit **£89.95**
- ★ 16K kit **£122.95**
- ★ Printed Circuit Board **£29.95**
- ★ 40 pin-40 pin header plug **£8.50**

CASES

Available for UK101, Superboard, Nascom. Appx. DIM 17" x 15" 435 x 384 mm

PRICE £24.50
 Post & Packing £1.50

UK101 P.P.I


Built & tested. Interfaces TX80 Printer direct. Can be programmed to operate relays, motors, various other peripherals "CENTRONICS COMPATABLE"
 Plugs into IC socket. LED query display fully documented. **£29.95**

U K 1 0 1


£179 IN KIT FORM
£229 READY BUILT & TESTED
£255 COMPLETE IN CASE

4K Expansion (8x2114)
NOW ONLY £18.00

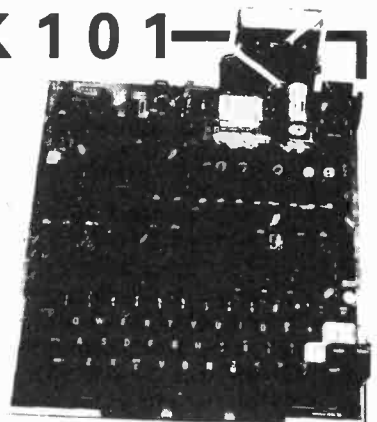- No extras required
- ★ Free sampler tape
 - ★ Full Qwerty keyboard
 - ★ 8K basic
 - ★ Ram expandable to 8K on on board (4K inc)
 - ★ Kansas City tape interface
 - ★ **NEW MONITOR ALLOWS FULL EDITING & CURSOR CONTROL** **£22.00**



PRINTERS

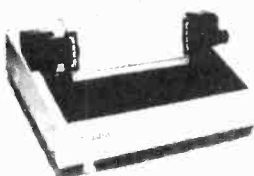

EPSON TX-80
£349

Dot-matrix printer with Pet graphics interface: Centronics, parallel, options: PET, Apple and serial.



Please add VAT 15% to all prices. Postage on computers, printers and cassette decks charged at cost. all other items P&P 30p. Place your order using your Access or Barclaycard (Min. tel order £5). Trade and export enquiries welcome. credit facilities arranged



NEW SHOP & SHOWROOM NOW OPEN

Telephone 01-883 3705/01-883 2289

UK101 SOUND

Sound Generator and combined parallel in out port kit containing P.C.B., RY-3-8910, 6820 PIA. Fully documented and demo tape. £29.95 AY-3-8910 £8.50

UK101 SOFTWARE

Space Invaders	£ 6.50
Real Time Clock	5.00
Chequers	3.00
Othello	4.00
Game Pack I	5.00
Game Pack II	5.00
Game Pack III	5.00
Screen Monitor	4.00
Assembler Editor	14.90
10xC12 Blank Tapes	4.00

CPUs

Z80 2.5Meg	7.95
Z80A 4Meg	9.95
6502	6.95
6800	6.50
8080	4.75
9900	25.95

SUPPORT CHIPS

Z80 CTC	5.95
Z80A CTC	6.95
Z80 PIO	5.95
Z80A PIO	6.95
6520	3.95
6522	6.85
6532	8.50
6821	4.25
6850	3.60
6852	4.35
8212	1.95
8216	1.95
9224	2.75
8228	3.75
8251	4.95
8253	9.75
8255	4.50
TMS9901	13.16
TMS9902	11.18
TMS9904(74LS362)	4.21

I.C. SOCKETS

	D.I.L.	W/W
8 pin	.09	.25
14 pin	.11	.35
16 pin	.12	.42
18 pin	.16	.50
20 pin	.20	.62
22 pin	.22	.65
24 pin	.24	.70
28 pin	.30	.80
36 pin	—	.99
40 pin	.40	1.10

MEMORY

D. RAMS	£	p
4027	2.75	
4050 (350NS)	2.35	
4060 (300NS)	2.39	
4116	3.95	

S. RAMS	£	p
2102A	1.30	
2102A2	1.69	
2112A	2.75	
2114/4045	2.75	
4035	1.07	
4044 5257	6.93	
6810	3.50	

BULK PURCHASE	£	p
8x2114	18.00	
8x4116	27.50	
16x2114	34.00	

EPROMs

2708	4.25
2716 (5v)	6.95
2532	29.95

ROM

2513 (UC)	5.95
-----------	------

BUFFERS

81LS95	1.25
81LS96	1.25
81LS97	1.25
81LS98	1.25
SN74365	52
SN74366	52
SN74367	52
SN74368	52
8T26	1.50
8T28	1.50
8T95	1.50
8T96	1.50
8T97	1.50
8T98	1.50

BAUD RATE GENs

MC14411	8.75
MM5307	8.75

UARTS

AY-5-1013	3.95
AY-3-1015	4.75
MM5303	4.75
TMS6011	3.55

SEND S.A.E. FOR COMPLETE PRICE LIST OR PHONE 01-883-3705

GAMES COMPUTERS

Database Games Computer	£71.88
Full range of cartridges including 'SPACE WARFARE', the new cartridge in the range from	£12.58
Compute a Tune	£18.33
Colour Cartridge	£31.55
Colour Cartridges from	£9.70
Door Tunes	£10.90
Colour stars 6 Function	£10.50
Supersports 6 Function (B/W)	£8.50

MICRO LEISURE HOBBY MODULE (home programmer)

The hobby module enables you to programme your own games computer in COLOUR. This unit fits directly into the existing cartridge slot of your 'Database Home Computer' and enables you to write your own computer/games programmes using machine code.

It incorporates its own 2K monitor and user ram with six I/O Lines. Cassette interface included to store user programme. Versions will also be available for **Teleng Rowtron/Radofin/Interton games** using the same system.

This system is capable of 3¼K user ram.	
Price ¾K user ram version	£38.67
1¼K user ram version	£44.43

All prices in this advertisement include V.A.T. and Delivery.

For further details of full range send s.a.e. to:

BRAINTREE MICRO LEISURE LTD.
92 Manor Street, Braintree, Essex
Tel: 03763 28196

HIGH QUALITY/LOW COST KIKUSUI 5520 20MHz SCOPE ONLY £230+VAT - FREE DELIVERY



- 20MHz. 5mV **5X MAG** 1mV. 10MHz
- One Touch X-Y Operation
- TV Sync. Separator (Trigger)
- Single Sweep Function
- High Brightness CRT

VERTICAL AXIS 1-2-5 sequence 11 ranges
SENSITIVITY 5 mV ~ 10V/DIV (within ± 5%)
FREQUENCY RESPONSE DC (AC 2Hz) ~ 20MHz (-3dB, 8 DIV) (WITH 5X MAG.) DC (AC 2Hz) ~ 10MHz (-3dB, 8 DIV)
RISE TIME Approx 17.5n sec (20MHz) Approx 35n sec (10MHz)
INPUT IMPEDANCE 1M Ω ± 2%, 30pF ± 2pF
INPUT COUPLING AC, DC or GND.
OPERATION MODE CH1, CH2, DUAL X-Y (DUAL automatic switching ALT and CHOP)
CHOP FREQUENCY Approx. 200 kHz
*HORIZONTAL AXIS 1-2-5 sequence, 20 ranges

SWEEP TIME 0.4µsec 0.5 sec/DIV (within ± 5%)
(WITH 5X MAG.) 0.04µsec 0.1 sec/DIV (within ± 5%)
SWEEP STOP Sweep stops and trace becomes a spot.
*EXTERNAL SWEEP MODE X-Y mode (CH1: X axis) (within ± 5%)
FREQUENCY RESPONSE DC (AC 2Hz) ~ 1MHz
INPUT IMPEDANCE 1 MΩ ± 2%, 30pF ± 2pF
X-Y PHASE DIFFERENCE within 3° at 50kHz
* TRIGGERING TRIGGER MODE AUTO, NORM, SINGLE, TV TRIGGER SOURCE INT. EXT. COUPLING AC and DC POLARITY "±" and "-" *Z AXIS SENSITIVITY 3 Vp-p (Trace becomes brighter with negative input signal)
FREQUENCY RESPONSE DC ~ 5MHz

INPUT RESISTANCE Approx. 110kΩ
*CALIBRATION VOLTAGE WAVEFORM Square wave, Approx. 1kHz
OUTPUT VOLTAGE 1Vp-p ± 3% * CRT TYPE 5-inch round-type PHOSPHOR B31 (Green) ACCELERATION VOLTAGE* Approx. 2kV EFFECTIVE AREA 8 DIV x 10 DIV (1 DIV = 9.5mm) GRATICULE ILLUMINATION Brightness is continuously variable
* POWER REQUIREMENTS AC LINE VOLTAGE 100V, 110V, 120V, 220V, 230V, 240V, ± 10% FREQUENCY 50/60 Hz POWER CONSUMPTION Approx. 40VA
*MECHANICAL SPECIFICATION MAXIMUM DIMENSIONS 250W x 210H x 435D mm WEIGHT Approx. 8 kg (17.6 lb.)




TELONIC/BERKELEY U.K.
2 Castle Hill Terrace, Maidenhead, Berkshire SL6 4JR
Tel: Maidenhead (0628) 73933 Telex: 849131 (TELBER G)

Orders to Telonic Berkeley UK

Please send me 5520 Scope(s) at £264.50 incl. VAT at 15%. I enclose PO/Cheque for or debit my Barclaycard/Access Card No.
Name (print) Signature
Address
Tel. No.

MUSICAL DOORBELL

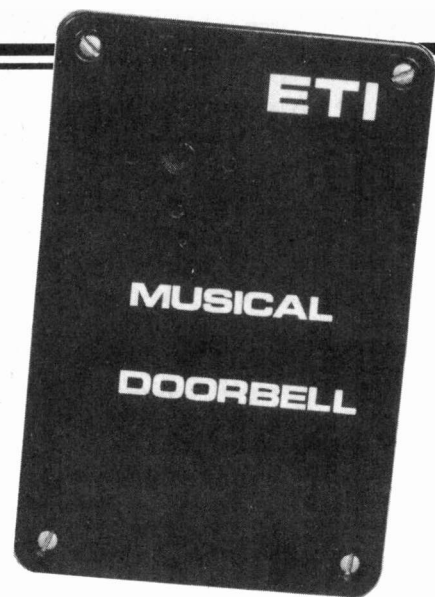

An inexpensive programmable doorbell project for your home. This instrument will play any nine-step melody of your choice. Design by Ray Marston. Development by Steve Ramsahadeo.

Modern doorbells come in two basic types, the simple electrical 'ding-dong' (chime) or the sophisticated microprocessor-controlled multi-tune (Rule Britannia, etc) types. In either case you pay your money and have to accept the sounds that the manufacturers have pre-programmed into your particular device. If you ever get tired of your bell's limited range of sounds, you have little option but to buy a new unit.

We have decided to overcome this by designing a musical doorbell project that the owner can self-program to play any desired (but brief) melody. The essence of our project is that it is simple; it is devoid of hard-to-get micros, PROMs, double-sided PCBs, etc, yet gives an entertaining performance.

Our doorbell is designed to play a nine step melody made up of a selection of five basic notes or tones. The melody lasts for 2-3 S. If the bell-button is briefly operated, the complete melody plays once only; if the bell-button is held closed, the melody repeats continuously. The unit is designed so that the owner can select or 'program' his own melody by hard wiring the interconnections between various pins on the unit's PCB.

The nine step, five note choice enables any one of a selection of almost two million (5^9) different melodies to be programmed into the unit!

A feature of our doorbell is that it incorporates a bistable electronic switch that connects power to the unit in such a way that it consumes virtually zero power when in the 'standby' mode. Whenever the bell-button is pressed, the bistable connects power to the unit for the duration of the tune play and then automatically disconnects the power when the melody is complete; this facility ensures long battery life.

Construction

Construction of this unit should present very few problems, if the overlay is followed with care. Note that IC1 and IC3 are CMOS devices and are best mounted in suitable sockets. Also note that an insulated link is connected between pin 3 of IC2 and pin 14 of IC3 on the underside of the board and that Veropins are used to facilitate top-side connections on the PCB.


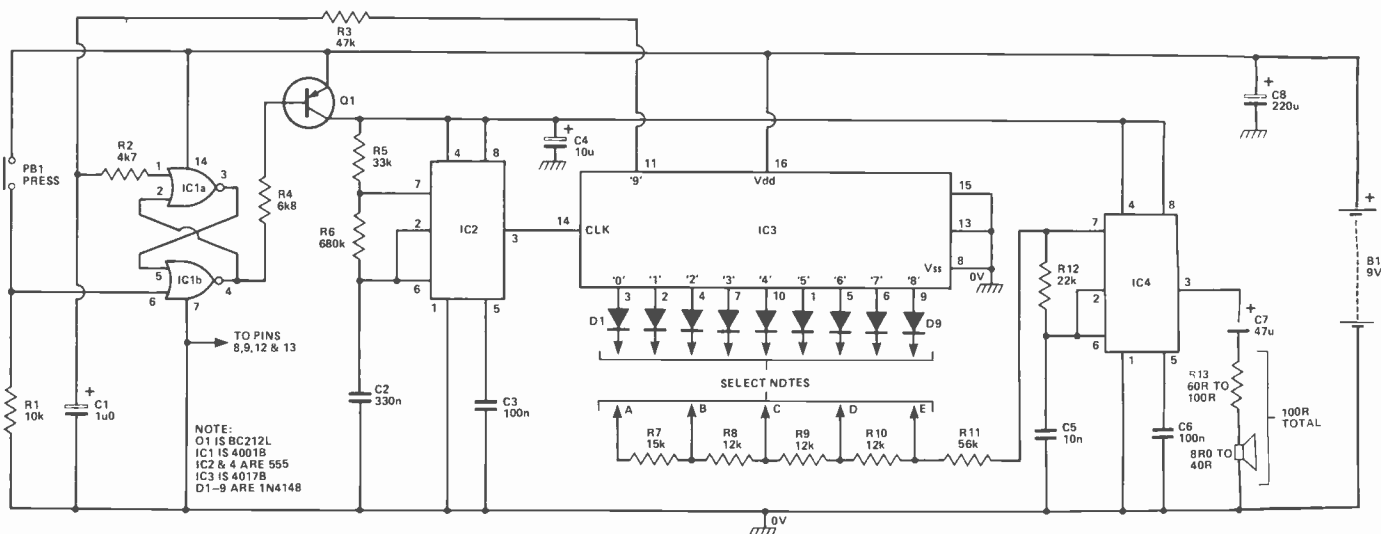


Fig. 1. Circuit diagram of the Musical Doorbell. The connections you make between diodes D1-D9 and the points A-E determine the tune that is played.

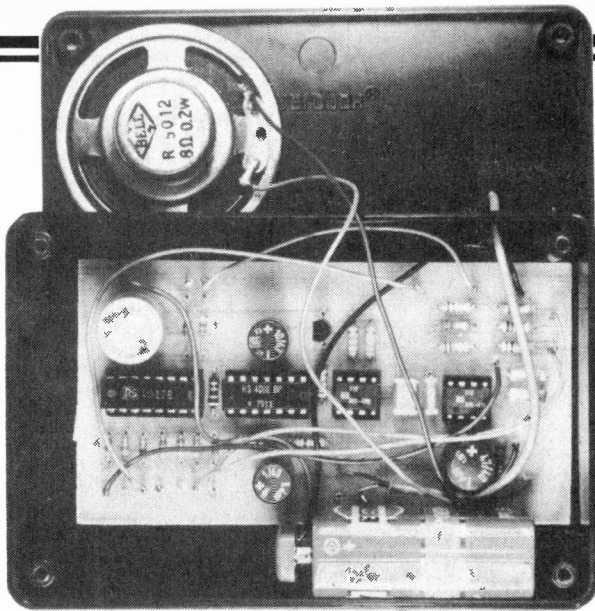

Everything fits in the case except the pushbutton; the wire to this can be seen leaving the Verobox.

When construction of the PCB is complete, connect up a suitable speaker, battery and push-button switch and prepare to give the unit a functional check. When selecting a speaker, note that output volume is proportional to speaker impedance and that a high impedance unit will give the loudest results.

When you are ready to try out the unit, connect a flying lead from D1 to one of the A — E note-select points and press PB1 to test the first note in the sequence. You can then wire in the D2 to D9 note-selection connections, one at a time, to establish the rest of the sequence, testing the unit at each step in the wiring sequence.

Once you've finished 'programming' your unit you can fit the PCB, battery and speaker into a suitable box, hang the unit on your front door and finally connect it up to a suitable push-button switch.

HOW IT WORKS

The circuit comprises a bistable (IC1) and a transistor power switch (Q1), two 555 astable multivibrators (IC2 and IC4) and a 4017 decade counter/divider (IC3). The bistable (IC1) is designed around two gates of a CMOS 4001B and controls the base bias of Q1, which in turn controls the positive power supply connections to IC2 and IC4, the two 555 chips.

Normally, the output (pin 4) of the bistable is high, so Q1 receives no base drive and is cut off. Under this condition, IC2 and IC4 consume no power: IC1 and IC3, being CMOS devices, also draw negligible power under this condition. The entire circuit, in fact, consumes a typical 'standby' current of only a microamp or so.

The circuit is activated by briefly pressing PB1, thereby causing the IC1 bistable to change state and connect power to the IC2 and IC4 astables via Q1. IC2 is wired as a low frequency astable (a few Hertz) and delivers clock pulses to IC3. IC3 is a 4017B decade counter/divider; it has ten decoded outputs, which sequentially go high on the arrival of successive new clock pulses, only one output being high at any given time. In our application, the first nine decoded outputs are used to sequentially select (via D1 to D9) timing resistors in a second astable, the IC4 tone generator, which drives a speaker via C7.

The first nine clock pulses from IC2 thus cause nine tones to be sequentially selected via the R7-11 resistor network. On the arrival of the tenth clock pulse, pin 11 of IC3 goes high and resets the IC1 bistable via R3 and C1, thereby cutting off Q1 and removing power from IC2 and IC4, thus completing the operating cycle.

The action of the IC1 bistable is such that, if PB1 is briefly pressed, the instrument plays a single sequence of nine notes (total duration is 2-3 S) and then automatically switches off. If PB1 is held closed, however, the sequence continuously repeats. Note that the owner can set up any tone sequence that he wishes by suitably interconnecting the diode outputs of IC3 to the 'A' to 'E' selection pins on the R7-11 note-selection chain.

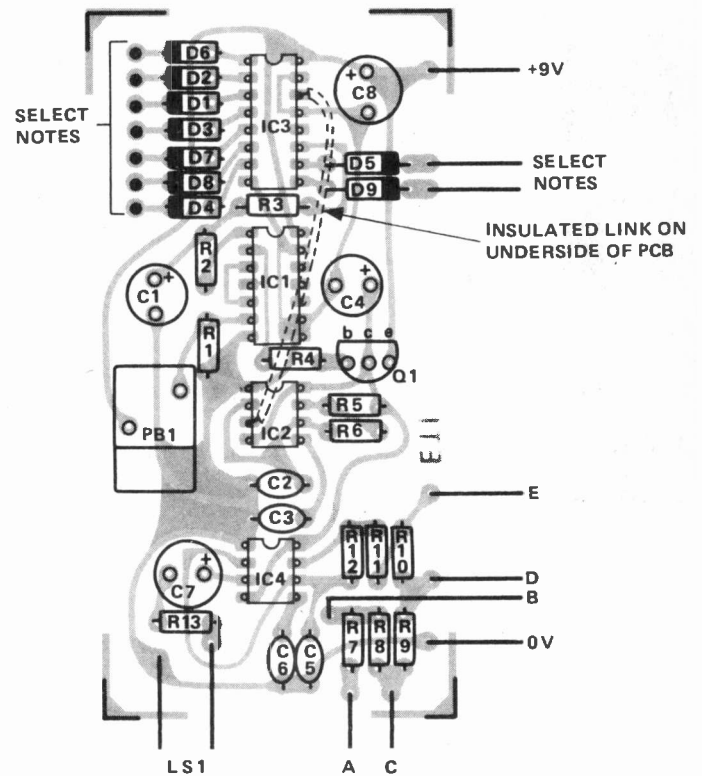


Fig. 2. Component overlay.

PARTS LIST

Resistors All ¼W, 5%	
R1	10k
R2	4k7
R3	47k
R4	6k8
R5	33k
R6	680k
R7	15k
R8,9,10	12k
R11	56k
R12	22k
R13	100R

Capacitors	
C1	1u0 63 V electrolytic PCB type
C2	330n polycarbonate
C3,6	100n polycarbonate
C4	10u 63 V electrolytic PCB type
C5	10n polycarbonate
C7	47u 25 V electrolytic PCB type
C8	220u 25 V electrolytic PCB type

Semiconductors	
IC1	4001B
IC2,4	555
IC3	4017
Q1	BC212L
D1-9	1N4148

Miscellaneous	
LS1	Any 8R0 to 40R speaker: see text
PB1	momentary action
B1	PP3
Case	

BUYLINES

All components used in this project are common types, readily available from many of our advertisers.

Make sure of your Heathkit catalogue... write now.



**Autumn
1980
catalogue
out now.**

Keep up to date with the world's finest electronic kits—with the Heathkit catalogue. 48 product packed pages contain photographs and specifications of the widest possible range of kits. Everything from doorbells to digital clocks, multimeters to microcomputers.

Heathkit make it easy to build, easy on your pocket, and as with 13 million Heathkit builders over 34 years, your success is guaranteed.

Make sure of your copy of the Heathkit catalogue. Send the coupon today, plus 25p in stamps and beat the demand.

To: Heath Electronics (U.K.) Limited, Dept (ET12),
Bristol Road, Gloucester, GL2 6EE.

Please send me a copy of the Heathkit catalogue.

I enclose 25p in stamps.

Name _____


Address _____

**Soldering
Iron offer
FREE** N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the Heathkit catalogue without having to use this coupon. When you receive your catalogue you will get details of this free offer.

HEATHKIT

Telequipment S61 SINGLE TRACE LIGHTWEIGHT 5 MHz OSCILLOSCOPE

**LARGE
5" DISPLAY
CRT**

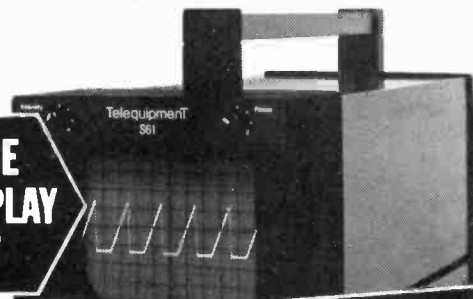

**DIRECT FROM
MANUFACTURER**

SCOOP PURCHASE

NEW!

Unused, Ex-stock,
to manufacturer's
full specification

**ONLY
£122 + VAT**

**90 DAY
GUARANTEE**

This offer cannot be repeated.
Available only whilst stocks last.

- BANDWIDTH** DC to 5MHz (−3dB)
- DEFLECTION** 5mV/div to 20V/div
- SWEEP SPEEDS** 500ms/div to 1μs/div
- TRIGGERING** Variable control or Auto
- SOURCE** Internal, External or Line
- C.R.T.** 5" tube 8 x 10 divisions (each division nominally 1cm)
- DIMENSIONS** 280mm High, 160mm Wide, 370mm Deep, Weight 6.0kg

For complete spec. of the Telequipment S61, or to order direct — complete and post coupon today. Personal callers welcome. Only 5 mins from Camden Town underground. Come and see our complete range of 'Blue Chip' Used Test & Measuring Equipment.

HOW TO ORDER

Fill in coupon and return with your cheque made payable to Carston Electronics Ltd. (Remember to include packaging & dispatch fee. U.K. mainland only.) Or we can debit your Barclay Card or Access Account — tick box as appropriate. Allow 21 days for delivery to your door.

To CARSTON ELECTRONICS LTD.

Shirley House, 27 Camden Road,
London NW1 9NR Telephone 01-267 5311

Please send me the Telequipment S61 scope — I enclose my cheque for £151.80 (which includes £10 net, packing and dispatch + VAT on total).

Please charge my ready-credit card Barclay/Access, account No. _____

Please send me further information on the S61 and details of your complete range of 'second user' equipment

Signature _____

Name: Mr/Mrs/Miss
(BLOCK CAPITALS PLEASE)

Address for delivery _____


Post Code _____

Registered No. 890082 England. 12/ET



Sound Triggered Flash Unit

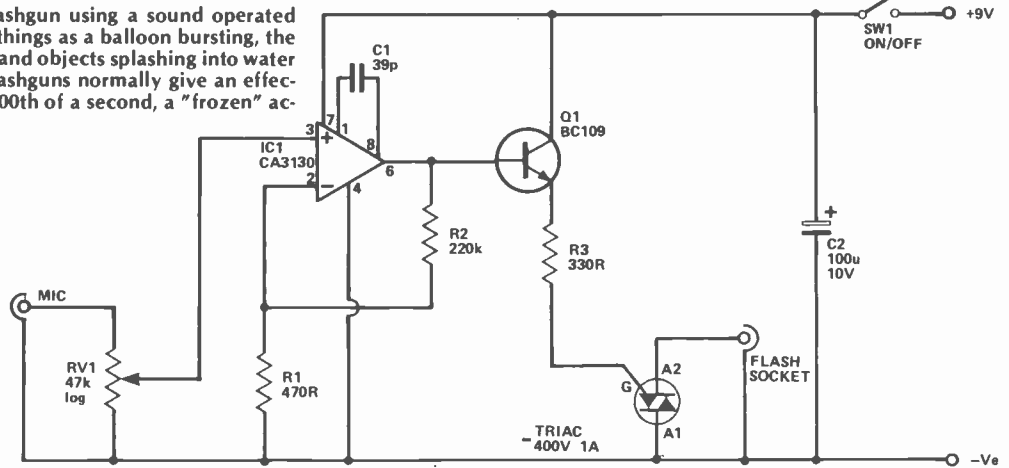By triggering an electronic flashgun using a sound operated switch, photographs of such things as a balloon bursting, the cork leaving a champagne bottle and objects splashing into water can be taken. Since electronic flashguns normally give an effective shutter speed of around a 1000th of a second, a "frozen" action photograph is obtained.



The photograph must be taken under fairly dark conditions so that the ambient light does not give an exposure if the camera's shutter is set to "B" and opened.

The circuit is based on operational amplifier IC1 which is used in the non-inverting amplifier mode. R1,2 are a negative feedback network which set the gain of the unit at about 500. RV1 (sensitivity) biases the non-inverting input to the negative supply rail. Ideally the input should be fed from a crystal or high impedance dynamic microphone, but the unit will work quite well using a low impedance dynamic microphone or even a high impedance speaker as the signal source.

Q1 is used as a discrete emitter follower output stage which provides the relatively high trigger current required by the triac. R3 is a current limiting resistor. Under quiescent conditions the output of IC1 will be at virtually negative supply potential, and the triac, therefore, receives no gate current. When a signal is

received by the microphone, positive going signals are amplified by IC1 to give an output that is a few volts positive. The triac then receives a strong gate bias, causing it to trigger and give a low resistance across its A1 and A2 terminals. These terminals connect to the flashlead via a suitable socket (or flash extension lead with the unwanted plug removed) and the flashgun is, therefore, fired. The circuit operates almost instantly, giving very little delay between the commencement of the sound and the flashgun being triggered. Sometimes more interesting photographs can be obtained by introducing a small delay.

This can be achieved by moving the microphone a metre or two away from the object(s) being photographed.

The current consumption of the unit is approximately 4 mA. It is advisable not to advance RV1 much more than is absolutely necessary in order to give reliable triggering, as frequent spurious operations of the unit could otherwise result.

Conquer the chip.

Be it a career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.

MASTER ELECTRONICS LEARN THE PRACTICAL WAY BY SEEING AND DOING

- Building an oscilloscope. ● Recognition of components.
- Understanding circuit diagrams. ● Handling all types Solid State 'Chips'.
- Carry out over 40 experiments on basic circuits and on digital electronics.
- Testing and servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.


MASTER COMPUTERS

LEARN HOW TO REALLY UNDERSTAND COMPUTERS, HOW THEY WORK - THEIR 'LANGUAGE' AND HOW TO DO PROGRAMS.

- Complete Home Study library. ● Special educational Mini-Computer supplied ready for use. ● Self Test program exercise.
- Services of skilled tutor available.

MASTER THE REST

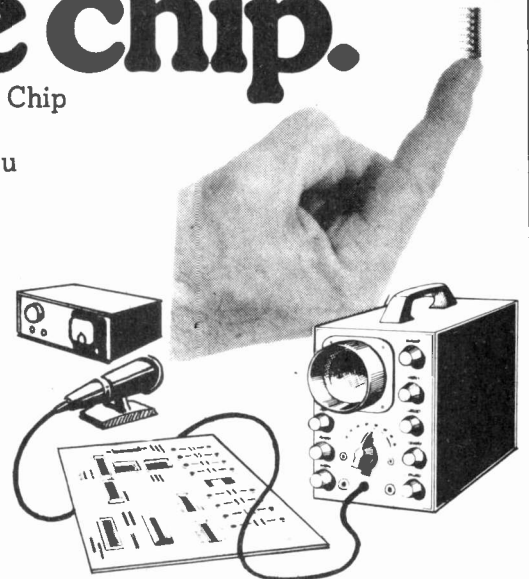- Radio Amateurs Licence. ● Logic/Digital techniques.
- Examination courses (City & Guilds etc.) in electronics.
- Semi-conductor technology.
- Kits for Signal Generators - Digital Meters etc.



FREE	Please send your FREE brochure without obligation to -	I am interested in -
	Name	PRACTICAL ELECTRONICS
	Address	COMPUTER TECHNOLOGY
	OTHER SUBJECTS
		<small>(Please state your interest!)</small>
	
BLOCK CAPS PLEASE		
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL		
4 CLEVELAND ROAD, JERSEY, CHANNEL ISLANDS. ET1/12/813		

Greenbank

Greenbank Electronics
 (Dept T12E) 92 New Chester Road, New Ferry
 Wirral, Merseyside L62 5AG
 (Tel: 061-845 3391)



TERMS, NAT. CWO. Cheques etc payable to Greenbank Electronics and crossed. Add VAT to all prices at 15% except where stated otherwise. Post etc: (UK 35p + 5p VAT = 40p) per order. Export: NO VAT but add 35p (Eire), 75p (Europe) and £2.50 elsewhere. Access, Barclaycard, Visa, telephoned orders accepted. (Polys, universities, gov't depts, etc can telephone their orders for immediate despatch on account.)



UV EPROM ERASERS

UV 140, UV 141



Two easy to use units designed for both the professional and amateur UV-prom user

Features

- Can erase up to 14 proms.
- Special short wave ultraviolet tube
- Erase time variable between 5 and 50 minutes in 5 minute steps (preventing over exposure which may shorten prom life).
- Siding tray carries proms on conductive foam
- Safety interlock switch prevents the timing circuit from operating and switching on the tube with the tray open.
- Mains On and "Tube On" indicators.
- Smart textured case
- Complete instructions supplied

Supplied complete with mains plug and flex

Model UV141. Price £77.70

Also available without timer as

Model UV140. Price £61.20

Tex Microsystems "EPROMPT" UV ERASER



A low cost alternative to the above erasers (UV 140/141) claimed by the manufacturer to erase up to 32 chips in 15-30 mins. This is the cheapest eraser we have seen. The unit has no timer, power switch or safety interlock switch. The user places up to 32 chips into loose conducting foam in the erasure tray (16 along the base, 8 on each side). The chips are held in place by the UV tube which sits in the tray. (Unlike the UV 140/141, no special precautions have been taken to prevent the seepage of UV light, but the manufacturers state that "Incident light from this device is quite safe at distances above 12 inches".)

(Dimensions - 325x64x38mm)

EPROMPT ERASER: Price £33.00

MICROPROCESSORS

COMPUTER BOARDS

- 114 x 203 mm fibreglass gold plated edge connector. Buffered SC/MP CPU £9.40
- SC/MP Protoboard £9.40
- Z80 CPU card £9.40
- VOU 'A' set £8.90
- VOU 'B' £8.90
- VOU 'C' three £9.40
- EPROM Programmer £9.40
- [2708s] £9.40
- 4k PROM board [204s] £9.40
- 8k PROM board [2708s] £9.40
- 2k RAM board [2102s] 1k-2k £9.40
- 8k RAM board [2114s] 1k-8k £9.40
- Type interface £8.90
- Keyboard interface £8.90
- PSU 5v + 12v - 12v board £8.90
- PSU 5v - 12v board £5.50
- 15BUS 11 13 slot backboard £11.50
- 13" x 14" approx. Epoxy Glass. Inlaid

NEW COMPUTER BOARDS

The following computer boards have been added to the range for use with the Z80 (114x203mm fibreglass with gold plated edge connector).

- Z80 CPU [2+MHz] £8.95
- Z80-CTC [2+MHz] £5.80
- Z80-P10 [2+MHz] £6.10
- [Add £1 for the 4MHz version of any of the above 3 chips]
- 6800 MPU £6.55
- 6802 MPU £9.95
- 6805 £19.95
- 6810 [128 x 8 RAM] £3.25
- 6810 [128 x 8 RAM] £3.75
- 6820. 6821 PIA £3.96
- 6845 £22.30
- 6850 ACIA £4.85
- MC6880 £2.64

SC/MP II RAM I/O

- SC/MP II [4MHz] £10
- 1Ks 8154 RAM I/O £9.40
- 6502 £7.95
- 6520 PIA £6.22
- 6522 £7.95

CMOS

- COSMAC COP 1802CE £10.50
- COSMAC COP 1802E £6.85
- COP 1864 £7.25

STATICS (Mostly 4050s)

- 2101-256 x 4 £2.25
- 2102-1K x 1 £1.20
- 2111-256 x 4 £1.95
- 2112-256 x 4 £2.25
- 2114/4045-1K x 4 £2.25
- 9 x 2114 £17.84
- 2141-1K x 4 £5.50
- 4118-1K x 8 £8.95

DYNAMICS

- MK 4115 16K 250ns £2.75
- MK 4816 2K x 8 £30.52

UV ERASABLES

- 5204 [512 x 8] £11.50
- 2708 1K x 8 £3.95
- 7515/2516 2K x 8 Single 5v £6.95
- 2532 4K x 8 [5v] £37.00
- PROMWASHING each Prom 50p (+30p +VAT)

CMOS

- 5204/2708/2516 Programming Service: £7.50/£7.50/£15.00 each prom. Price does not include prom. we accept handwritten/typed source code - must be hexadecimal.
- PROM WASHING SERVICE: 50p each prom

UV PROM ERASER

- UV140 £61.20
- UV141 £77.70
- EPROMPT £33.00

INTERFACE

- 81S395/6/7/8 £1.40
- 75149 LED driver 50p
- 75492 92p
- ZM425 £3.95
- 8226/8228 £2.64
- IL74 48p

CRT Controller: Uarts

- Thompson CSF 96364E £11.50
- AY-5-1013 JART TR 1602 £4.00
- AY-5-1013A £4.70
- AY-3-1014A £5.60
- AY-3-1015 £6.60

CHAR. GEN. KEYBOARD ENCODER

- MCM 66760 £9.75
- MK 2302 £15.29
- RO-3-2513 (5V Uppercase) £6.00
- DM 8678 CAB/BWF £14.27
- AY-5-2375 £9.75

FIRMWARE

- ZM0M for Z80 [1 x 2708] £14.95
- 2K Tiny BASIC for Z80 [2 x 2708] £19.95
- 4K NIBL for SC/MP [4 x 2708] £49.95
- 4K NIBL MM for SC/MP [4 x 2708] £49.95
- 1K Various. for SC/MP [1 x 2708] £14.95

UV PROM ERASER

- 1K Elektor Junior 1x2708 £19.95
- 1K ELB06 [3x5204] £35.00
- ETIBUS 2 [1x5204] £14.95
- ETIBUS 2 [1x5204] £14.95
- SCMP/K8 [1x5204] £14.95

MODULATORS

- UM1111 E36 UHF Ch.36 Vision Modulator £2.50
- UM1231 UHF Ch.36 Vision Modulator wide bandwidth (for computers etc.) £4.70
- 7805 75p
- 7905 £1.08
- 7812 97p
- 7912 75p
- 7805 £5.61

QUARTZ

32.768KHz (Watch)	£3.23
60 KHz	£9.95
100.0 KHz	£3.62
200.0 KHz	£3.92
204.8 KHz	£3.92
262.144 KHz	£3.92
307.2 KHz	£3.92
312.5 KHz	£3.92
455.0 KHz	£4.95
1.000 MHz	£3.62
1.200 MHz	£3.92
1.800 MHz	£3.92
1.8432 MHz	£3.62
2.000 MHz	£3.62
2.097152 MHz	£3.92
2.500 MHz	£3.92
2.56250 MHz	£3.62
3.000 MHz	£3.62
3.2768 MHz	£3.23
3.579545 MHz	£1.95
3.825 MHz	£3.92
4.000 MHz	£2.90
4.032 MHz	£3.23
4.096 MHz	£3.23
4.194304 MHz	£3.23
4.433619 MHz	£1.25
4.800 MHz	£3.23
4.800 MHz	£3.23
4.9152 MHz	£3.23
5.000 MHz	£3.23
5.0688 MHz	£3.23
5.120 MHz	£3.23
5.185 MHz	£3.23
6.000 MHz	£3.23
6.144 MHz	£3.23
6.400 MHz	£3.23
6.55360 MHz	£3.23
7.000 MHz	£3.23
7.168 MHz	£3.23
7.680 MHz	£3.23
7.86432 MHz	£3.23
8.000 MHz	£3.23
8.08333 MHz	£3.62
8.388608 MHz	£3.23
8.867237 MHz	£3.23
9.375 MHz	£3.92
9.800 MHz	£3.92
10.000 MHz	£3.23
10.245 MHz	£3.23
10.700 MHz	£3.92
10.92 MHz	£3.23
11.000 MHz	£3.92
12.000 MHz	£3.92
14.000 MHz	£3.92
14.31818 MHz	£3.23
16.000 MHz	£3.92
18.000 MHz	£3.23
18.432 MHz	£3.23
20.000 MHz	£3.23
20.1134 MHz	£3.23
24.0 MHz	£3.92
26.690 MHz	£2.90
27.0 MHz	£3.92
27.145 MHz	£2.10
27.948 MHz	£3.92
38.6666 MHz	£2.23
40.000 MHz	£3.23
100.000 MHz	£3.23
116.000 MHz	£3.23

VEROBORD

- 0.1" Pitch with copper strips
- 2 1/2" x 1" [back of 5] 74p
- 2 1/2" x 3 1/4" 53p
- 2 1/2" x 5" 62p
- 2 1/2" x 17" £1.86
- 3 1/4" x 3 1/4" 62p
- 3 1/4" x 5" 59p
- 3 1/4" x 17" £2.40
- 4.7" x 17.9" £3.14
- 0.1" Plainboard (no strips)
- 3 1/4" x 2 1/2" 38p
- 1.000 MHz £3.92
- 3 1/4" x 5" 59p
- 3 1/4" x 17" £1.56
- Terminal pins £1.50/500
- V-Q DIP board £1.17
- DIP breadboard £2.91
- Spot lace cutter 93p
- Pin insertion tool £1.28

SOLDERCON PINS

- 100 50p £0.95

DIL SOCKETS

- 8/14/16 pin 10p/12p/13p
- 18/20/22 pin 18p/20p/25p
- 24 pin DIP board 40p/40p/50p
- 24 pin Teatool lever type zero insertion force £8.50

EDGE CONNECTORS

- 43 way. 0.1" pitch, wire wrap, polarizing slot pin 37
- Single sided [1 x 42] £3.11
- Double sided [2 x 42] £4.10

TIMER ICs

- NE555/556 29p/49p

DP-AMPS (AN Mini dips)

- CA 3130C 84p
- CA 3140C 35p
- UA 741 [Texas] 22p

LED DISPLAYS

- DL 704E 99p
- DL 727E/728E £2.00
- DL 747E/750E £1.80
- FW 500/560 £1.20

LIQUID CRYSTAL DISPLAY

- 4 x 0.5" Digits 40 pin DL £9.95

CLOCK CHIPS

- AY-5-124A £2.60
- MK 50553 £5.60
- MK 50366 £6.50

SIX DECADE COUNTERS

- MK 50365/6/7 £9.90
- MK 50398/9 £7.50

SWITCH MODE PSUs



- AC 5221S 5V/10A £69.90
- AC 9221S 5V/5A, 12V/1A -12V/1A -5V/0.1A £86.80
- AC 5421S 5V/20A £99.20
- AC 9421S 5V/10A, 12V/2A -12V/2A -5V/0.1A £126.50

DATA

Note: in this section all data books are subject to 0% VAT. For postage see 'Terms' at top of page.

- 113 page Electronic Projects Index 72-77 (North Tyneside Libraries) £1.50
- £650 page COSMOS Databook (RCA) £4.95
- c31 page A Guide to SC/MP Programming by Dr. Drury (Kemtron) £3.75
- c20 page A Guide to Kitbug (Kemtron) 75p
- c24 page NIBL Reference Guide (National) £3.45
- Data for 4116 (Mostek) £2.30
- c6 page data for MK 4118 50p
- 16 page data for IMS 8154 RSP.8A/650 (National) 50p
- 20 page data for SC/MP [1 National] 50p
- C20 page CDP 1802 MPU User Manual (RCA) £4.50
- c45 page Fixed Point Binary Arithmetic Routines for COSMAC £4.50
- c31 page Floating Point Arithmetic Routines for COSMAC (listings excluded) £4.50
- c43 page COSMAC MPU Product Guide (RCA) 75p
- c15 page CDP 1802 Instruction Summary 25p
- c70 page Understanding CMOS (RCA) £1.50
- 1 page COSMOS Pocket Selection Guide (RCA) 25p
- c21 page COSMOS Digital Integrated Circuits (RCA) 75p

Please check availability of Z80 Data Pack before ordering.
Z80 DATA PACK £14.95
 This contains all the data we can obtain on the Z80 CPU. Depending on our own supplier, the data is either loose sheets, photocopied or bound volumes, or a combination of both. The weight of the set of data is about 1/2 kilos, and some information on other processors, memories, and systems is often included.

- c175 page Home Computers: Beginners glossary and Guide by Miller and Suppl (Dilithium) £4.95

ASTROLOGUE

Satellites in Surrey and spying on storms. Ian Graham has news of a British spacecraft and the latest addition to the World Weather Watch network.

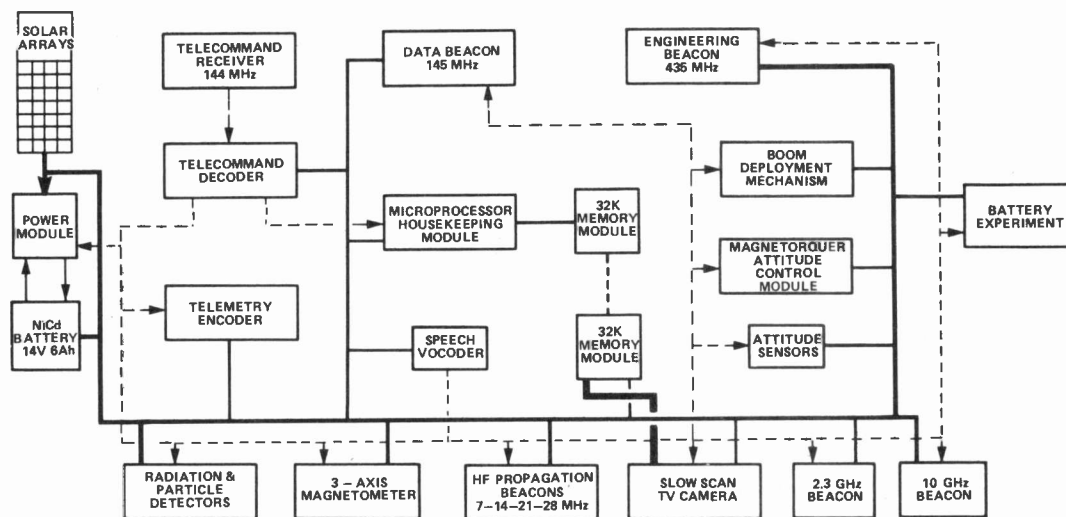


Fig.1 System diagram of the UK amateur scientific spacecraft — UOSAT.

Just over a year ago scientists and engineers began building Britain's first amateur satellite — UOSAT. It isn't a British copy of its American predecessors (the OSCAR series), whose function was to improve long distance VHF and UHF communications. UOSAT has much broader and far-reaching mission objectives — to allow radio amateurs and amateur scientists to study the electromagnetic propagation properties of the atmosphere from HF to microwave frequencies, stimulate active participation in space science (particularly in schools, colleges and universities), establish sources of hardware for the AMSAT programme and pave the way for future amateur spacecraft, possibly operating at new frequencies. That's an ambitious list of objectives.

The project is supported by British industry and research organisations, AMSAT, RSGB (Radio Society of Great Britain) and the University of Surrey, where the spacecraft is being built. A great deal of the design work is complete and systems testing is under way.

On Board

The Propagation Studies Experiment will carry beacons transmitting from 7 MHz up to over 10 GHz, particle radiation counters and a magnetometer. The Education Experiments comprise an Earth-pointing slow-scan TV camera and a synthesised voice telemetry system. The payload will also include two Future

Systems Experiments — a two axis, Earth-pointing, gravity gradient spacecraft stabilisation system and an on-board microcomputer to investigate image processing, telemetry/command management and data store/dissemination.

Even when the Space Shuttle is operational, a satellite launch will be an expensive operation in terms of a project such as UOSAT. Fortunately, NASA have agreed to launch UOSAT free of charge as a piggy-back 'passenger' with the Solar Mesosphere Explorer (SME). SME is due to be placed in a circular polar orbit in September 1981 by a Delta 2301 launcher. UOSAT will be placed in a 530 km Sun-synchronous orbit.

Although Astrologue is naturally largely devoted to the multi-million dollar/pound/rouble headline-grabbing space shots it makes a pleasant change to hear of projects like UOSAT. If your university or business is managing or contributing to a space programme in any way, I'd like to hear about it.

One Small Launch . . .

GOES-D, the latest American weather satellite, is now safely in a slightly elliptical orbit about 40,000 km above the equator following a successful launch from Cape Canaveral on September 9th. Over the next few weeks GOES-D's engines will be used to circularise the orbit at 35,600 km. During its planned lifetime of seven years, Geostationary Operational Environmental

Satellite D will, like its predecessors, gather and transmit information on weather conditions over Canada, the United States and South America and a large area of the Atlantic.

Although GOES-D is concerned with American weather, the GOES satellites are part of a worldwide system — the World Weather Watch (WWW) project. Europe has contributed its Meteosat series to WWW, which, as the name suggests, maintains a global weather monitoring service.

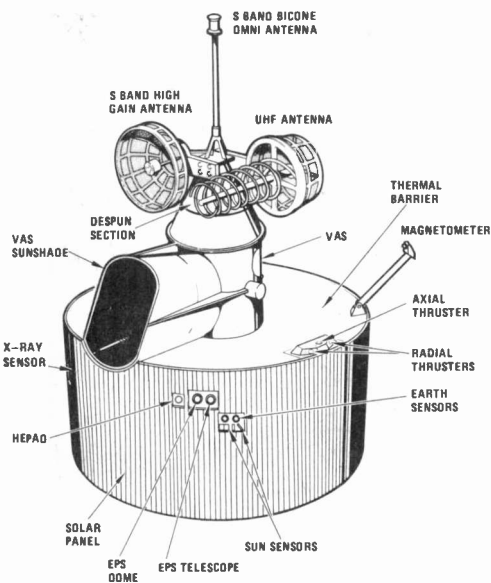


Fig.2 A quick guide to the GOES satellite. Notice the main experiment (VAS) behind its sunshade. The antennae are carried on the despun section (top).



GOES-D has now been redesignated GOES-4. It's the first satellite to be put in orbit as a joint operational and research mission of the National Oceanic and Atmosphere Administration (NOAA) and NASA. This is the first picture to be received from GOES-4, transmitted on September 24th. South America is clearly visible on the right. The remnants of Hurricane Hermine are still swirling over Southern Mexico and Honduras. Storms which begin far out into the Pacific Ocean (two can be seen here) can be tracked, giving ample time to warn major population centres.

... But A VAS Difference

The Hughes Aircraft Company are building three of the spacecraft (GOES-D, E and F), the main instrument of which is a visible and infra-red spin-scan radiometer (VISS) atmospheric sounder. The whole instrument is called a VAS for short (thank goodness). The VAS will look down on the atmosphere and gather information on temperature and moisture at different altitudes.

It doesn't sound very exciting, but in fact the onset of very severe weather conditions is characterised by the

development of higher and higher cloud tops. Up to now the instruments used could not look down through the highest clouds and watch cloud building at lower altitudes.

On The Data Trail

The information collected by VAS is processed and transmitted to the Wallops Island (Virginia) receiving station, where it is further processed and sent back up to the satellite for relay to US users.

The satellite also carries instruments to detect solar protons and electrons, alpha particles, X-rays and magnetic fields — information useful in telecommunications and power distribution.

The Hardware

GOES-D weighs in at a shade under 400 kg (orbital weight). It's basically a cylinder covered with solar cells and surmounted by antennae (overall height 12 ft, by 7 ft in diameter). The main body spins at 100 RPM, but the antennae are held stationary with respect to Earth.

The spinning motion is used to photograph the Earth. A frame is exposed each time the craft spins round. After each spin, a scanning mirror in the camera turns slightly, so that the camera gradually scans from pole to pole. It takes around 1800 steps to produce a full image of the Earth in 18 minutes.

During the recent eruption at Mt St Helen's a GOES satellite tracked the cloud of volcanic ash across the US.

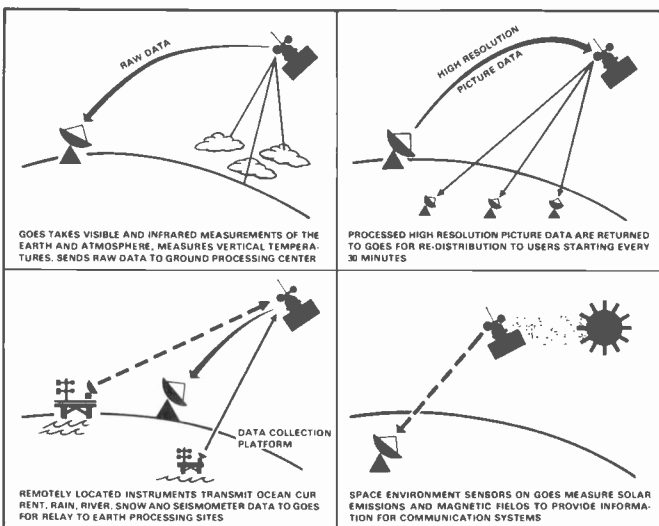


Fig.3 On the GOES data trail, complete with American spelling.



Freeport A
Birmingham
B19 1BR
ELECTRONICS
021-233-2400

- FREEPOST ON ORDERS
- VAT INCLUSIVE PRICES
- ADD 30p P&P
- 24 HR PHONE ANSWERING SERVICE
- ACCESS
- VISA
- CASH
- CHEQUE

ALL PRICES IN PENCE EACH UNLESS OTHERWISE STATED

C-MOS (BUFFERED)				LINEAR				SEMICONDUCTORS			
HEF4006	22	HEF4044	105	HEF4512	138	CA3046	84	IN914	5	BC182L	12
HEF4001	22	HEF4046	133	HEF4516	127	CA3080E	77	IN4001	5	BC184	11
HEF4002	22	HEF4047	109	HEF4517	478	CA3130E	99	IN4002	5	BC184L	12
HEF4003	119	HEF4049	57	HEF4518	118	CA3140E	48	IN4004	7	BC212	11
HEF4007	22	HEF4050	57	HEF4519	69	CA3189E	293	IN4007	9	BC212L	12
HEF4008	100	HEF4051	87	HEF4520	118	LM301AN	34	IN4148	4	BC214	11
HEF4011	22	HEF4052	90	HEF4521	235	LM339N	78	IN5402	15	BC214L	12
HEF4012	22	HEF4053	90	HEF4528	124	LM339N	104	2N2399	21	BC547	13
HEF4013	57	HEF4066	62	HEF4532	150	LM381AN	198	2N2946	46	BC548	11
HEF4014	105	HEF4067	475	HEF4534	638	LM3900N	75	2N2926G	13	BC549	12
HEF4015	100	HEF4068	22	HEF4539	138	MC3403P	156	2N3053	9	BC557	15
HEF4016	57	HEF4069	22	HEF4585	122	NE551	131	2N3054	55	BC558	15
HEF4017	100	HEF4070	22	HEF4724	214	NE538T	289	2N3055	55	BCY10	15
HEF4018	100	HEF4071	23	HEF40097	113	NE555N	28	2N3702	9	BCY21	15
HEF4019	58	HEF4072	23	HEF40098	92	NE568N	86	2N3704	9	BD131	39
HEF4020	112	HEF4073	23	HEF40106	78	NE568N	171	2N3705	10	BD132	39
HEF4021	107	HEF4075	23	HEF40150	149	NE570N	485	2N3773	297	BD139	39
HEF4022	103	HEF4076	130	HEF40192	149	NE571N	505	2N3819	22	BD140	39
HEF4023	22	HEF4077	22			RC4138	146	2N3820	39	BF890	333
HEF4024	76	HEF4078	23	Voltage Regulators				T8A120S	88	BF895	29
HEF4025	22	HEF4081	23			TD4102Z	713	2N3904	9	BFY86	17
HEF4026	54	HEF4082	23			UA741CN	20	2N5457	39	BFY50	17
HEF4027	22	HEF4085	80			LM309DA(K)	119	2N5459	35	BFY61	17
HEF4028	89	HEF4086	80			UA723CN	42	40673	88	BFY39	50
HEF4029	113	HEF4093	63			JA7805CU	78	TL084CN	156	BSX20	21
HEF4030	58	HEF4094	219			UA7812CU	78	UA741CT	47	LC8960	2850
HEF4031	250	HEF4104	206			UA7815CU	78	Zener		TP131	48
HEF4035	138	HEF4502	114			UA7812CU	97	Diodes		TP32	54
HEF4040	94	HEF4505	714			UA7815CU	97	Diodes		TP42C	76
HEF4041	97	HEF4508	230			JA78L05CS	38	400mW CAV7-C33		TP2955	75
HEF4042	83	HEF4510	135			UA78L15CS	38	BZY88/BZ X79		TP3055	60
HEF4043	100	HEF4511	157			UA78L15CS	38	+ Voltage		TP543	36

CAPACITORS				ELECTROLYTIC RADIAL LEADS			
Electrolytic Axial				Polyester Radial Leads			
-10% to +50% Tol. Cap 018 - µF				Dipped Type, C280/352 Style			
µF	V	18	28	40	63	100	150
1.0	16	9	9	0.01	352	380	µF
1.5	16	9	9	.0015	7	1.5	7
2.2	16	9	9	.0022	6	7	11
3.3	16	9	9	.0033	6	7	11
4.7	16	9	10	.0047	6	7	14
6.8	16	8	10	.0068	6	7	17
10	16	8	10	.01	6	8	10
15	16	8	10	.015	6	8	10
22	16	8	10	.022	6	8	10
33	16	8	10	.033	6	8	10
47	16	8	11	.047	6	8	10
68	16	9	13	.068	7	8	10
100	16	9	13				
150	16	9	13				
220	16	10	13				
330	16	10	13				
470	16	10	13				
680	16	10	13				
1000	16	10	13				
1500	16	10	13				
2200	16	10	13				

RESISTORS				SKELETON PRESETS, MINIATURE			
Carbon Film, Fixed				0.1W, E3 Values, 100R-1M, Lin. Vertical Mounting			
0.25W, E24 Values IRO-10M, 5% Tol. 2 each Res RD%				8 Min. Preset V			
100/100 (Mult 10/Value)				8 Min. Preset H			
0.5W, E12 Values IRO-4M7, 10% Tol. 3 each Res RD%				+ Value			
+ Value				Skeleton Presets, Standard			
Metal Film, Fixed				0.3W, E3 Values, 100R-4M7, Lin. Vertical Mounting			
0.5W, E24 Values, SR-1M, 2% Tol. 8 each Res MR30				11 Std. Preset V			
2.5W, E12 Values, TOR-27K, 5% Tol. 16 each Res PR52				11 Std. Preset H			
+ Value				+ Value			
Metal Glaze, Fixed				Potentiometer, Rotary			
0.5W, E24 Values, IM-33M, 5% Tol. 16 each Res VR37				0.5W, E3 Values, 1K-2M2 Lin			
+ Value				39 Ro Pot Lin			
				0.25W, E3 Values, 4K7-2M2 Log			
				45 Ro Pot Log			
				+ Value			
				Potentiometer, Slider			
				0.5W, E3 Values, 2K2-47K Lin.			
				45 Sp Pot Lin			
				0.25W, E3 Values, 1K0-1M0 Log			
				45 Sp Pot Log			
				+ Value			

MAINS TRANSFORMERS				PLASTIC BOXES - BOSS INDUSTRIAL MOULDINGS			
Order Code				Moulded Box and Close Fitting Flanged Lid			
Secondaries may be connected in series or parallel to give wide voltage range				ABS Box, C/W Brass Bushes, and Lid In Orange			
Primaries 0.220, 240V				Order Code			
8VA - Clamp Type Construction 235 each				L112 W82 D31 99 Case B1M2003 OR			
Approx. 18% Regulation F C 54, H36, W35				L150 W80 D50 131 Case B1M2005 OR			
0.4 5V, 0.4 5V Secondaries Trans 8VA				L190 W110 D80 223 Case B1M2008 OR			
0.5V, 0.6V				Plastic Boxes with Metal Lids			
0.12V, 0.12V				Recessed Top Box			
0.15V, 0.15V				ABS Base, C/W Brass Bushes, In Orange			
0.20V, 0.20V				1mm Aluminium Top Panel Finish Grey			
				Order Code			
20VA - Clamp Type Construction 360 each				L85 W58 D28 112 Case B1M4003 OR			
Approx. 18% Regulation F C 70, H48, W46				L111 W71 D42 180 Case B1M4004 OR			
0.4 5V 0.4 5V Secondaries Trans 20VA				L161 W98 D53 208 Case B1M4005 OR			
0.8V, 0.6V				Diecast Boxes			
0.12V, 0.12V				Draught Box and Flanged Lid			
0.15V, 0.15V				Aluminium Box and Lid in Natural Finish			
0.175V, 0.175V				Order Code			
0.20V, 0.20V				L113 W83 D31 124 Case B1M5003 NA			
				L152 W82 D50 216 Case B1M5005 NA			
				L192 W113 D81 334 Case B1M5008 NA			

VERO ELECTRONICS PRODUCTS				SWITCHES			
2.5" x 5" 1" pitch Veroboard 71				Miniature Toggle - Honeywell			
3.75" x 5" 1" pitch Veroboard 79				SPDT C/O/H 67 SW 8A1011			
2.5" x 1" 1" pitch Veroboard (5) 85/Pack				SPDT Double Bias To Centre 80 SW 8A1021			
3.75" x 5" 1" pitch Plain Board 88				DPDT 90 SW 8A1041			
5.82" x 2.9" 1" pitch V-O-DIP Board 135				DPDT C/O/H 111 SW 8A2021			
Spot Face Cutter 107							
Pin Insertion Tool for 040 type pin 147							
DS Pins 040 (100) 44/Pack							
SS Pins 040 (100) 44/Pack							
Veroboard Kit (1 open, 2-wire, 25-comb) 454/Kit							
Veroboard Combs (25) 109/Pack							
Veroboard Wires (2) 109/Pack							

GMT ELECTRONICS PROJECTS	KIT	BUILT UP
FREE-STANDING COMPLETE TELETEXT UNIT - FULL SPEC	£199-90	£275-00
TELETEXT DECODER BOARD + REMOTE HAND CONTROL	£135-90	£160-00
TELETEXT COMPATIBLE TUNER AND P. S. U.	£ 46-90	£ 57-00
TELETEXT COMPATIBLE PAL ENCODER + MODULATOR	£ 22-90	£ 35-00
F. E. T. OUTPUT 100W MONO POWER AMPLIFIER MODULE	£ 27-50	£ 35-00
X-BAND DOPPLER RADAR ALARM MODULE - MARK II	£ 35-90	£ 44-00
ONE AMP P. S. U. MODULE (SPECIFY 5 OR 12 VOLTS)	£ 7-50	£ 10-00
SIMULATED INERTIA MODEL TRAIN CONTROLLER	£ 22-50	£ 35-00
SIMULATED INERTIA SLOT RACER CONTROLLER	£ 27-50	£ 40-00
MODEL TRAIN STEAM SOUND SIMULATOR MODULE	£ N/A	£ 5-00



We use advanced winding technology to make our toroidal transformers. They have only half the weight and height of their laminated equivalents and are appreciably more efficient. Our toroids cost virtually the same as the older types which they are rapidly replacing. Induced hum is reduced by a factor of ten. Supplied with rigid mounting kit with centre bolt, steel and neoprene washers.

30VA	70mm dia. x 30mm	£4.71	160VA	110mm dia. x 40mm	£8.88
Weight 0.45 Kg			Weight 1.8 Kg		
(+£1.00 p.p. + 0.86 VAT)			(+£1.40 p.p. + £1.54 VAT)		
TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT	TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
1X010	6+6	2.50	5X012	12+12	6.66
1X011	9+9	1.66	5X013	15+15	5.33
1X012	12+12	1.25	5X014	18+18	4.44
1X013	15+15	1.00	5X015	22+22	3.63
1X014	18+18	0.83	5X016	25+25	3.20
1X015	22+22	0.68	5X017	30+30	2.66
1X016	25+25	0.60	5X018	35+35	2.28
1X017	30+30	0.50	5X028	110	1.45
			5X029	220	0.72
			5X030	240	0.66
50VA	80mm dia. x 35mm	£5.19	225VA	110mm dia. x 45mm	£10.59
Weight 0.9 Kg			Weight 2.2 Kg		
(+£1.10 p.p. + 0.94 VAT)			(+£1.50 p.p. + £1.81 VAT)		
2X010	6+6	4.16	6X014	18+18	6.25
2X011	9+9	2.77	6X015	22+22	5.11
2X012	12+12	2.08	6X016	25+25	4.50
2X013	15+15	1.68	6X017	30+30	3.75
2X014	18+18	1.38	6X018	35+35	3.21
2X015	22+22	1.13	6X026	40+40	2.81
2X016	25+25	1.00	6X028	110	2.04
2X017	30+30	0.83	6X029	220	1.02
			6X030	240	0.93
80VA	90mm dia. x 30mm	£5.76	300VA	110mm dia. x 50mm	£12.27
Weight 1 Kg			Weight 2.6 Kg		
(+£1.20 p.p. + £1.04 VAT)			(+£1.60 p.p. + £2.08 VAT)		
3X010	6+6	6.64	7X016	25+25	6.00
3X011	9+9	4.44	7X017	30+30	5.00
3X012	12+12	3.33	7X018	35+35	4.28
3X013	15+15	2.66	7X026	40+40	3.75
3X014	18+18	2.22	7X028	110	2.72
3X015	22+22	1.81	7X029	220	1.36
3X016	25+25	1.60	7X030	240	1.25
3X017	30+30	1.33			
3X028	110	0.72			
3X029	220	0.36			
3X030	240	0.33			
120VA	90mm dia. x 40mm	£6.72	500VA	140mm dia. x 60mm	£16.35
Weight 1.2 Kg			Weight 4 Kg		
(+£1.30 p.p. + £1.20 VAT)			(+£1.70 p.p. + £2.71 VAT)		
4X011	9+9	6.66	8X017	30+30	8.33
4X012	12+12	5.00	8X018	35+35	7.14
4X013	15+15	4.00	8X026	40+40	6.25
4X014	18+18	3.33	8X028	45+45	5.55
4X015	22+22	2.72	8X033	50+50	

THE BIG BANG THEORY

Over billions of years gas clouds condensed into stars and planets. The primeval soup bubbled. Self-replicating organisms writhed. Fish struggled onto the land and took their first breath of air (dramatic stuff). The result of it all — A.S. Lipson. Here, he discusses how it all began.

One of the many questions that has intrigued man since he first learned to speak is that of the origin of the universe. How did it all begin? Where did our world come from and what caused its existence? Scientists, being only human, (or so we are told) have not been immune to this type of curiosity — even Isaac Newton hypothesized about the origins of the stars. However, it is only fairly recently (during the second half of this century) that any research on this topic has been viewed as 'respectable', or fit material for a serious investigation. During this time, two main opposing theories as to the origin of the universe have developed; the Steady-state theory and the Big Bang theory. It is the latter which tends to be generally accepted these days, as we shall see later. But first we'll need to look at some of the background information.

The Red Shift Mystery . . .

It was found during the 19th century that when light from the Sun was passed through a narrow slit and then split into a spectrum by a prism, the spectrum showed hundreds of tiny dark lines across it. The reason for this was not known until the advent of quantum mechanics this century, but it was noted that the lines always occurred in the same positions in the spectrum, corresponding to set frequencies or wavelengths of the light. In 1868, it was found by Sir William Huggins that not only were all the same lines found in the spectra of stars, but in some stars, the lines were shifted very slightly from their positions in the solar spectrum. Sometimes the shift was towards shorter wavelengths; the blue end of the spectrum, and sometimes to longer wavelengths; the red end of the spectrum. With a disappointing lack of originality these two changes became known as the blue shift and the red shift, respectively. In order to explain the shifts, Huggins used an analogy with sound. When you are standing still, and are suddenly passed by a fast moving car (of course Huggins, working in 1868, did not explain it in terms of cars, but anyway. . .) which is emitting some sound, you may have noticed that as the car passes you the pitch of the sound drops. (Producing the eeeee-owwww sound beloved of motor sport enthusiasts.)

This change in pitch, or frequency of the sound waves is caused by the relative velocity between the car and yourself. It follows that light, which is also a wave, is affected in the same way by relative motion between the object emitting it and the object receiving it. In fact, the light from a star moving away from us at great speed is shifted slightly to the red end of the spectrum, and a star moving towards us has its light shifted very slightly to the blue end of the spectrum. This explains the red and blue shifts. Now, it so happens that the wavelength of the dark lines in a spectrum is one of those quantities which physicists find relatively easy to measure with extreme accuracy. By doing this, and comparing the wavelengths of dark lines in the spectra of stars to the wavelengths of the same lines in the spectrum of the Sun, it is possible to calculate fairly precisely just how fast a star is moving towards or away from the Earth.

In The Beginning . . .

Things really began to get interesting, though, when astronomers looked at the shifts in the spectra of other galaxies. They discovered that the distant galaxies appear to be moving away from our own galaxy — the Milky Way. There are one or two exceptions; for instance, the Andromeda Nebula, the closest large galaxy to our own, appears to be moving towards us at about 300 kilometres per second. In general, however, the other galaxies seem to be moving away. In fact it appears that almost every galaxy we can see is rushing away from every other galaxy. This can be simply expressed by saying that 'the universe is expanding'. As a general rule, distant galaxies show a distinct red shift in their spectra and the further away the galaxy, the greater the red shift tends to be, indicating that the further away a galaxy is, the faster it is likely to be travelling away from us.

It began to look as though a long time in the past, all the galaxies were squashed up together and then a massive explosion sent them flying apart. This is the bare bones of what became known as the Big Bang theory and various calculations have shown that if this is indeed what happened, then the 'beginning' — the creation of the universe — took place about 10-20 billion years ago. →

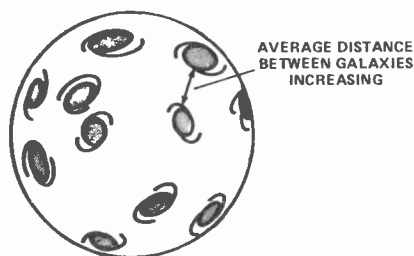


Fig.1 If you visualise our three-dimensional universe as being on the two-dimensional surface of an expanding balloon, you can see that, although the galaxies are getting further away from each other, the centre of expansion is not on the surface.

Before Genesis

Some cosmologists, however, were somewhat unhappy with this explanation of the expansion of the universe. It involves a 'beginning' and therefore raises the awkward question of what was 'before'. In fact, it was reasoned, it would be much more satisfying philosophically if a theory could be found which did not involve a 'beginning' for the universe, (this idea, that a theory ought to be philosophically satisfying, is not quite as silly as might be thought. Time and again in physics, the theory which *feels* best has been the correct one). In the late forties Hoyle, Bondi and Gold proposed the Steady-state theory. This takes care of the expansion of the universe in a most ingenious manner; although the various galaxies are receding from each other all the time, new matter is continuously being created to 'fill up the gaps'. As more matter is created, it collapses by gravitational attraction to form new galaxies. Thus there is no need in this theory for there ever to have been a beginning — the universe is as it is simply because it has always been the same. According to the Steady-state theory, there never was a beginning to the universe, and presumably there will never be an end — it will just keep expanding, old galaxies dying, new ones forming. This theory does have a certain 'neatness' about it that is rather satisfying.

As a first impression it might seem that it would be impossible to tell which of the two main theories — Big Bang or Steady-state — is correct. The only real difference to the universe now would be that, if the Steady-state theory is correct, the rate of expansion would be constant, whereas if the Big Bang theory is correct, the expansion would be slowing down somewhat, as gravitational attraction attempts to pull the galaxies back together again. This slowing-down, however, is far too slight for us to be able to measure. So how can we decide which theory is correct?

Well, for a start, there are one or two things which can only be explained in terms of the Big Bang theory. One of these is the abundance of the element helium in the universe — there is far too much of the stuff around for it to be explained in terms of the Steady-state theory (exactly why doesn't really concern us here). Another is the 'three degree Kelvin microwave background' — which we will consider later. Finally, there is this; according to the Steady-state theory, the universe has always been much the same as it is now, whereas according to the Big Bang theory, it has only evolved to its present state slowly, and it was different in the past. If only we had some way of looking at the past of the universe, we could compare it with the present. If the two were largely similar, we could conclude that the Steady-state theory is roughly correct. If, however, there was a noticeable difference in, say, the structures of galaxies then and now, we might conclude that

the Big Bang theory is correct. But we can't look at the past. Or can we? When we look at the stars, we do not see them as they are, but as they were when they emitted the light we see. Light takes only about eight minutes to reach us from the Sun, but nearly four and a half years from even the closest star. When we look at the more distant galaxies, we see them as they were many millions of years ago. Evidence is not 100% conclusive (it rarely is in cosmology) but weighing the facts one against the other, it seems it is the concept of the 'Big Bang' that is correct.

The Microwave Background

Now it is time, then, to elaborate a little on the Big Bang theory. A common misconception is that this theory states that about 15 billion years ago, a massive explosion occurred at one point in space, throwing out matter which eventually condensed into stars, galaxies, planets and (finally) us. In fact, this is not correct. The explosion is not imagined to have occurred at one particular point in space. It took place at every point in space, occupying the entire universe. It makes no sense, then, to ask "Where was the explosion?" The best way of understanding this is to imagine our universe as being on the two-dimensional surface of a balloon, which is being inflated. It makes no sense to ask where on the surface of the balloon is the centre of expansion; every point is just as much the centre as any other.

We will now see what it is thought the precise beginning of the universe was like. Nobody actually knows what the universe was like during the first few fractions of a second; our knowledge only starts after this. After the first tenth of a second or so, the vast and intense quantities of energy that had just sprung into existence with the universe were making the temperature of the universe an incredible 30 billion degrees on the Kelvin scale (at temperatures as high as this, the Kelvin and Centigrade scales are virtually identical). Apart from the pure energy in the form of photons, a lot of electrons and positrons were in existence, together with equally large numbers of particles called neutrinos. In addition, there was a slight contamination of heavier particles, like protons and neutrons. After a second or so, the temperature had dropped to only ten billion degrees or so and this was still far too hot for protons and neutrons to form atomic nuclei. This process didn't begin until three or four minutes after the beginning,

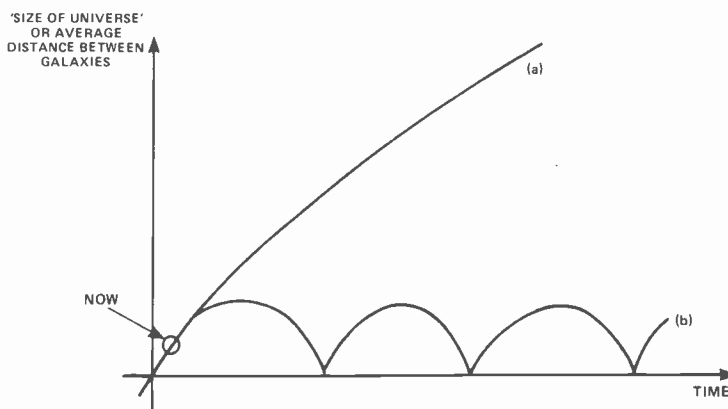


Fig.2 Will the universe keep expanding (a) or will the gravitational attraction be strong enough to make it collapse again, only to start another expansion (b)?

when the temperature had dropped to a mere (. . . a mere . . . !!! . . .) 900 million degrees. Even though nuclei had been able to form, there was still far too much energy for electrons to be able to join up with the nuclei to form stable atoms. It took nearly three quarters of a million years for that to occur and by that time, most of the original electrons and positrons had vanished. (When an electron meets a positron, the two disappear, giving off energy. This is what is thought to have happened, leaving just a few particles behind.) Gradually, gravity clumped the atoms together, and then clumped the clumps, to form stars and galaxies. Eventually, life developed: but that happened much later.

Cold Radiators

So how can we test this theory? Well, if it is correct, there should still be some radiation hanging around from this beginning. The appropriate calculations have been performed, and it turns out that the radiation ought to be roughly equivalent to that emitted by a perfect radiator at a temperature of about three degrees Kelvin (minus 270° Centigrade). This doesn't seem to be a lot, (things that cold don't radiate much heat) but despite this it is measurable. In the mid-sixties, Penzias and Wilson measured this 'three degrees Kelvin radiation background', more or less by accident. At first they blamed poor readings on their equipment and on a pair of pigeons which had nested inside the horn-shaped antenna they were using!

That's it then. It looks very much as though the Big Bang theory is in fact the correct explanation of the origin of the universe. There are still unanswered questions, however.


What's on Next?

We've seen an explanation of how the universe began, but how will it end? Will it just keep expanding, getting larger and larger and cooler and cooler, or will gravitational attraction pull the galaxies back together again, the expansion of the universe slowing and eventually stopping, then 'going into reverse'? This depends on exactly how much matter there is in the universe. If there is enough, then the gravitational pull will be strong enough to make the universe collapse back in again. If not, then the expansion will continue. In the former case, the universe is said to be 'closed', and in the latter case, 'open'. Either way, the human race will certainly be long extinct before it happens. So we may never know which is the case. Some evidence seems to indicate that the universe is closed; some that it is open. Until fairly recently, it seemed that the universe was probably closed. However, it is now thought possible that the sub-atomic particles known as neutrinos might have mass, contrary to what has been thought for many years. There are so many neutrinos in the universe that, if this is the case, it might be enough to make the difference between an open and a closed universe.

We will finish with one more fascinating possibility. It has been suggested that, if the universe does collapse back on itself, it would first return to its original state of intense heat, and then possibly explode outwards again, beginning the whole thing all over again. We can imagine the universe forever exploding outwards, contracting again, exploding, contracting . . . Perhaps the universe we live in is formed from the remnants of the cycle before. . . . Sadly we shall never know. . . .

ETI

**NEW! DMM
BREAKTHROUGH!**

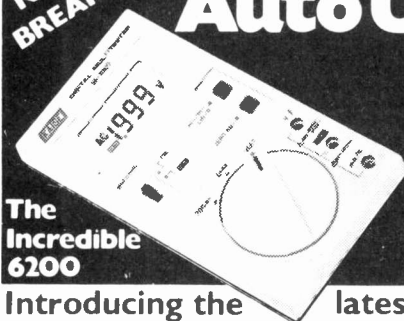

The Incredible 6200

If you want an Autoranging, Auto Unit Display, 3½-digit LCD DMM.

For only £39.95 (inc VAT)

We've got to hand it to you!

Introducing the latest professional state-of-the-art 3½-digit DMM – at really old-fashioned prices! From just an unbelievable £39.95 inc. VAT, plus £1.15 p&p!

- * 1mV, 100µA and 0.1Ω resolution!
- * Measures AC voltage to 600V!
- * Measures DC voltage to 1000V!
- * Measures resistance to 2 Megohms!
- * Low power Ohm ranges!
- * Displays mV, V and mA!
- * 0.8% accuracy!
- * Zero adjustment!
- * 3 other models too!

This one-off price is so unbelievably low because the A/D converter and display are custom-built. This is a genuine, no corners cut, top-spec DMM that gives you all the features above and 200 hrs continuous battery life on the 3½-digit LCD display 'auto' 'Batt' warning, pair of test leads, batteries, spare fuse and 6 months' guarantee! This offer can't last for ever, so buy now. Remember a DMM in the hand . . .

Plus three other DMMs in the range!

- 6220 As the 6200 plus 10 Amp AC/DC measurement! **ONLY £49.95 inc VAT***
 - 6100 With Continuity check! **ONLY £64.95 inc VAT***
 - 6110 As 6100 plus 10 Amp AC/DC measurement! **ONLY £74.95 inc VAT***
- Add £1.15 p&p please

I believe you! Please send me the DMMs as marked

- _____ 6200 @ **£41.10** each, inc. VAT, p&p Total price £_____
- _____ 6220 @ **£51.10** each, inc. VAT, p&p Total price £_____
- _____ 6100 @ **£66.10** each, inc. VAT, p&p Total price £_____
- _____ 6110 @ **£76.10** each, inc. VAT, p&p Total price £_____

Total cash cheque enclosed £_____

Cheques payable to
Maclin-Zand Electronics Ltd please
38 Mount Pleasant, London WC1X 0AP
Tel 01-278 7369 01-837 1165



Maclin-Zand

Making state-of-the-art affordable

ACCESS orders taken. Please write card no. and signature

ACCESS NO. _____

Name _____

Address _____

Signed _____

To: Maclin-Zand Electronics Ltd, 38 Mount Pleasant, London WC1X 0AP
For overseas orders, please add £5 to cost of total order package 3ETI

World famous for quality, reliability and value for money. 20,000,000 customers can't be wrong!

Now Casio, the new technological leaders, take a giant step forward in time with

THE ULTIMATE WATCHES



AA81 Analogue Display



AA82 Digital Display

You have to hand it to Casio for the best of both worlds!

LCD ANALOGUE/DIGITAL ALARM CHRONOGRAPHS with around 40 functions

- **LCD Analogue.** Independent display of hours and minutes with synchronous digital seconds. can be used as a dual time.
- **Digital.** Independent display of hours, minutes, synchronous seconds, day and date.
- **Auto calendar.** Four year calendar is set for 28 days in February.
- **Professional Stopwatch.** Measures net, lap and 1st and 2nd place times in units 1/100 second to 12 hours. A signal confirms start/stop operation and sounds at 10 minute intervals.
- **Daily reminder alarm.** Sounds at the pre-set time with a carousel type display for 30 seconds. "Alarm on" symbol.
- **Countdown Alarm.** Measures normal and net times from 1 minute to 60 minutes. 30 seconds alarm with amazing "Star Burst" display. 10 minute signal. Start/stop signal.
- **Time Signal.** Every half-hour on the half-hour. Every hour on the hour. Two tones.
- **Tone control.** Tone pitch can be varied in 10 steps.
- **Lithium battery.** Approx. 18 months life using alarm for 90 seconds and nightlight for 3 seconds daily. ± 15 secs./month accuracy. "Merry-go-round" demonstration display. Water resistant case. 8.65mm thick. Mineral glass. Matching stainless steel bracelet.

AA81 chrome case, s/s bracelet (£34.95)

£29.95

AA82 stainless steel case and bracelet

£39.95

AA81G gold plated front, s/s back

£49.95

Tune in to Casio. 12 melodies will alarm you — the price won't!

12 MELODY ALARM CHRONOGRAPHS with countdown alarm and four date memories.

- **Time display.** Hours, minutes, seconds, am/pm, 12 or 24 hour format.
 - **Calendar.** Day, date and month auto 4 years calendar.
 - **Daily Alarm.** 7 melodies, one for each day of the week, including "American Patrol."
 - **Hourly time signal.** With "Big Ben" type tune. When date memories are set, the chosen melody is played instead of the time signal. Easily switched on or off.
 - **Date memory.** Select "Trinkled" or "Wedding March" to be played instead of hourly chimes on the set day. Press the calendar button for additional renditions.
 - **Birth day memory.** "Happy Birthday" is played instead of hourly chimes, or when the calendar button is pushed. The message "Happy" is also displayed.
 - **Christmas Memory.** On December 25th "Jingle Bells" is played instead of the hourly chimes, or when the calendar button is selected.
 - **Countdown alarm.** From 1 second to 1 hour. At zero a chime sounds for 10 seconds and the count continues positively for 1 hour.
 - **Stopwatch.** Net, lap and 1st & 2nd place times from 1/10 second to 1 hour. A signal confirms start/stop operation. A signal sounds at 1 minute intervals.
- Picturesque moving display of notes played. One touch melody demonstration. Built-in speaker. Back-light. 2 year battery. Mineral glass. Water resistant case.
- M-12** Resin case and strap, s/s trim. **M-1200** All s/s 9.0mm thick case.



M12
(£26.95)
£24.95



M1200
(£34.95)
£29.95

AROUND 40 FUNCTIONS


NEPTUNE WOULD GIVE HIS LEFT ARM FOR ONE!

Get in the swim with Casio — 300 feet down! 100 METRE WATER-RESISTANT ALARM CHRONOS with countdown alarm timer

- **Amazing FIVE YEAR** battery life. Around 30 functions.
- **Timekeeping mode.** Continuous display of hours, minutes, seconds, am/pm, day, date and month. 12 or 24 hour. Time is always visible regardless of play modes. Auto 4 year calendar set at 28 days for February.
- **Professional Stopwatch.** Net, lap, and 1st and 2nd place times from 1/100 second to 1 hour. A signal confirms start/stop operation, and sounds at 10 minute intervals.
- **Daily reminder alarm.** Sounds for 30 seconds at the pre-set time. "Alarm on" symbol.
- **Countdown Alarm.** Normal and net times from a maximum of 12 hours. Start/stop and 10 minute signals.
- **Time signal.** Sounds every half hour on the half hour, and every hour on the hour. (Two tones.) The time signal, with symbol can be switched on or off.
- **Lithium battery.** Approx. 5 years life, using alarm for 100 secs and nightlight for 3 seconds per day, ± 15 seconds per month accuracy. Mineral glass.
- **100 METRE WATER RESISTANT CASES.** **W-100.** Resin case 9.65 thick, resin strap. **W-150C.** S/s case, resin strap. **W-150B** All stainless steel.



W100
£19.95

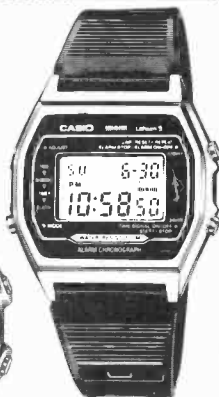

W150C
£25.95

100 METRE WATER RESISTANT



W150B
£32.50

See also A250 on opposite page

Send 25p for our illustrated catalogue

Price includes VAT and P&P. Send your company order, cheque, P.O. or phone your ACCESS or BARCLAY-CARD number to:

TEMPUS

Dept. ETI, FREEPOST, 164-167 East Road, Cambridge CB1 1DB. Tel: 0223 312866

GUARANTEED LOWEST PRICES — GUARANTEED QUALITY

We promise to **BEAT** any lower advertised price by an extra 2½% — Just send details and your remittance for the lower amount*

Casio and Seiko watches are **water resistant** and won't drown in the rain. They do not eat expensive batteries. The **quality cases** won't wear your cuffs away, nor will plating wear off in a few months. Unlike the usual plastic type, the **mineral glass** face will not easily scratch or mar. The **high quality modules** have a failure rate of around 1% or less — not 25% or more. They are **guaranteed** accurate and functions do not interact. Spares and servicing are available **after** the guarantee expires, from UK service departments.

JOIN THE KEYBOARD REVOLUTION!

With the amazing new **CASIOTONE 201**

A remarkable new concept in electronic keyboard instruments using a totally new technology. Pitch, timbre and harmonics of 29 instruments have been measured, digitalised and stored in electronic chip memory for faithful reproduction.

A 4-sound memory function allows switching between any 4 pre-selected instruments. This polyphonic instrument can play full chords of up to 8 notes on its 29 white and 20 black keys spanning 4 octaves. Vibrato and tone switches. Foot volume and sustain pedal options. Echo jacks. 3x33½x9½ inches. Weight 15lbs. Black or woodgrain finish. AC only.

ONLY £245 (rrp £285)



CASIOTONE M-10

Four instruments on the move!
Polyphonic playing of piano, organ, violin and flute. 19 white and 13 black keys span 2½ octaves. Vibrato switch. 2x16½x5½ inches. Weight 3.5lb. Integral speakers. O/p jack. Mains/battery.


ONLY £69 (r.r.p. £79)



12 PRE-PROGRAMMED MELODIES

Clock, calendar, 11-note melody maker, calculator, square roots, %. Alarm 1, 7 tunes, one for each day. Alarm 2: a fixwz tune. Hourly chimes. Date memories. 4 anniversary tunes. MQ-1200 (below). Desk or bedside. Built-in loudspeaker. Volume control. Nightlight. Powered by three AA size batteries. (£22.95). 19/16 x 6 x 2¼ inches.

£19.95

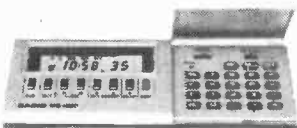

ML-90 (right)
Kiss keys
Stopwatch
7/32 x 2½ x 4½"
(£22.95)

£19.95

THE SPACE INVADERS ARE BACK!

MG-880 (left)
¼x2½x4½"
£10.95
(£12.95)

This time right in your pocket. An action-packed speed game that will give you hours of skilful entertainment and chair-gripping excitement. Never another dull spare moment. Also an 11-note melody calculator, pre-programmed "When The Saints Go Marching In". Full memory, %. Auto power-off facility.

MG-770 (right)
Kiss touch keys
5/32x3¾x2½"
(£14.95)

£12.95



A250 ALARM CHRONOGRAPH

(Left). The same module and functions as the W100 and W150 watches shown opposite but in a standard water resistant chromed case with s/s bracelet.

£24.95

A251. All stainless steel version. **£37.50**

F80E ALARM CHRONOGRAPH

(right). 1/10 second to 12 hours. Hourly chimes. Water resistant resin case and strap (£17.95)

£15.95



F300 Sports Chronograph **£12.95**. **S220** Chronograph **£25**. **F7C**. **£8.95**. **C80** Calculator Watch **£24.95**. **C801** **£29.95**.

* Providing the advertiser has stocks and we make a small profit!

See opposite page for ordering details

SEIKO

FROM £37.50

DFT 048

ALARM CHRONOGRAPH
Countdown timer
Hours, minutes, seconds, alpha day and date. 24 hour alarm and hourly time signal. Stopwatch times in units of 1/100 second to 12 hours, net lap and 1st & 2nd place. Countdown alarm timer up to 1 hour. Backlight. Stainless steel. Hardlex glass. Water resistant.

ONLY £37.50



DFT 038 100 METRE Water resistant

Suitable for swimming, water skiing etc.

Functions as DFT 048 above.
£49.95



DER 048 ALARM CHRONOGRAPH Weekly alarm Countdown alarm

Hours, minutes, seconds, day, date and month. Weekly programmable alarm. Hourly chimes. Interval countdown alarm timer from maximum of 16 hours. Stopwatch times in 1/100 up to 20 minutes, then in seconds to 12 hours. Net lap, 1st & 2nd place timing. Double display function. Stainless steel. Hardlex glass. Water resistant.

ONLY £52.50



DER 018 100 METRE Water resistant

Suitable for swimming, water skiing etc.

Functions as DER 048 above.
£69.95



All Seiko watches have an international 12-month guarantee.

DUO DISPLAY

Independent analogue display of hours and minutes, with sweep second hand. Digital display of hours, minutes, seconds, am/pm (12 or 24 hour format). Day and date auto 4 year calendar function. 24 hour alarm with alarm on symbol and hourly chimes. 1/100 second stopwatch to 1 hour, normal and net. 2 year battery with battery life indicator. Stainless steel. Water resistant. Hardlex glass.

JET 010 (illustrated)
Equivalent to HV013

ONLY £62.50

JET 018 (Equivalent to HV011)
JET 028 (Equivalent to HV005)
JET 994 Gold plated, champagne dial
JES 994 (Equivalent to HX008)



£62.50
£62.50
£92.50
£67.50

CASIO Ladies' Watches

Hours, minutes, ten seconds, seconds (by flash) a.m./p.m. Day, date and month. Stopwatch or dual time (except alarm watch).



L-20
Chrome
£14.95


Chrome
£16.95
87Q GL-13B
Gold Plate
£24.95

87QL-21B
All s/s
£16.95

A550 s/s
Alarm
£24.95

BENCH AMPLIFIER

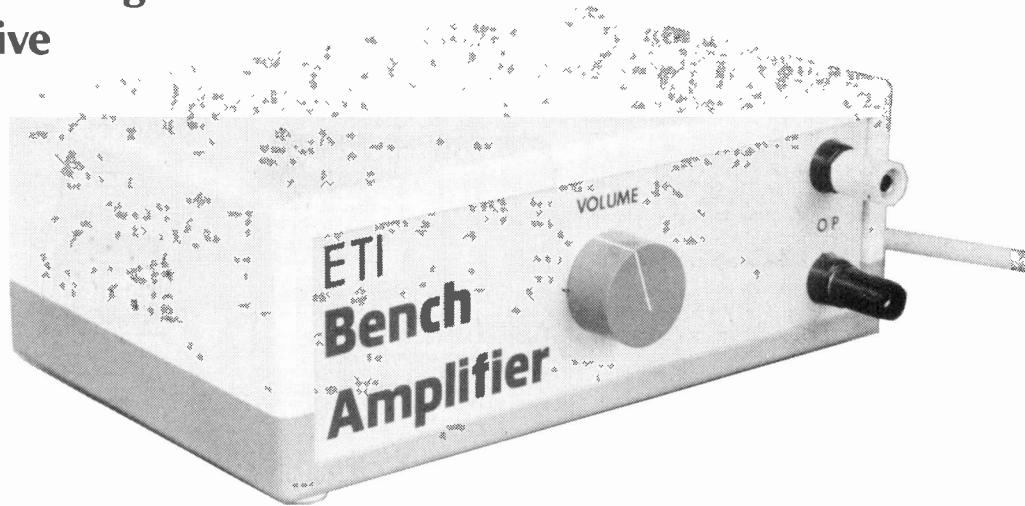Yet another useful piece of test gear from ETI. This time it's an inexpensive but good quality bench amplifier for use with an external speaker. Design by Ray Marston. Development by Steve Ramsahadeo.



Bench amplifiers are fairly simple pieces of workshop test gear which are useful for testing the functional performances of tuners, signal sources and speaker assemblies, etc. They also act as useful standby power amplifiers when not being used in the 'test gear' mode.

Our bench amplifier has been designed with low cost and good functional performance in mind. The unit has a high-impedance (10 M) input stage which is accessed via a pair of panel-mounted terminal sockets. The unit is mains powered

and can deliver approximately 4 W into an 8R0 speaker. The bench amplifier is designed to be used with external speakers, which are connected to the instrument via a second set of panel-mounted terminal sockets.

The amplifier works best when used with external 8R0 speakers, but can in fact be used with any speaker impedances in the 4R0 to 16R range. Fidelity is reasonably good, with distortion typically being less than 0.1% at 1 W at 1 kHz. The frequency response is virtually flat to 200 kHz.


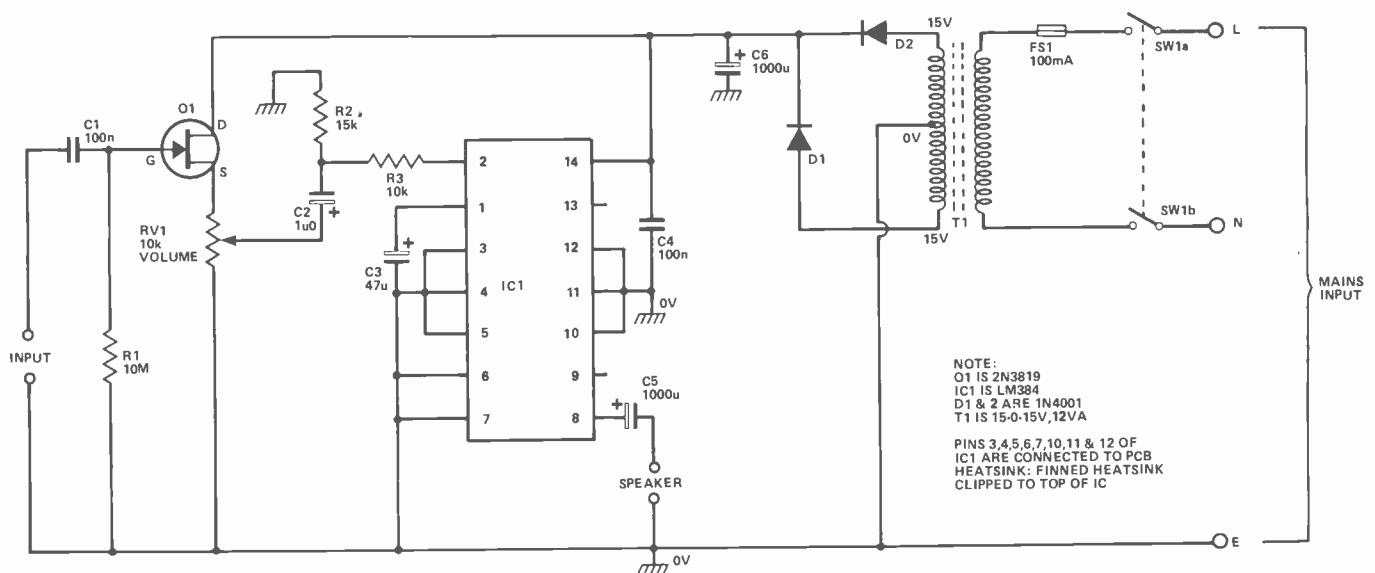


Fig. 1. Complete circuit diagram for the ETI Bench Amplifier.

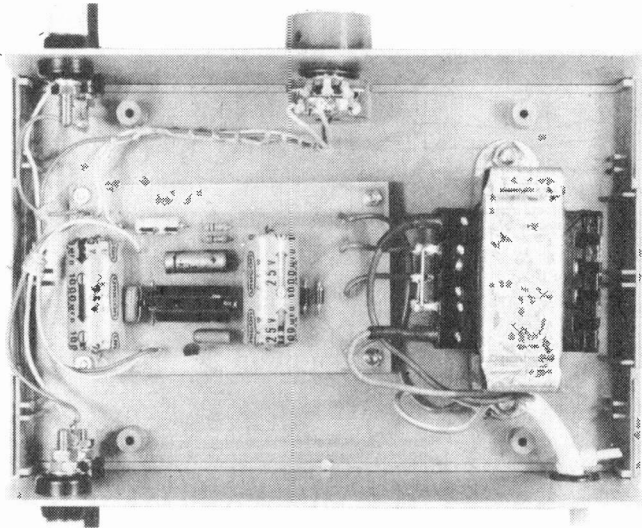

This photograph shows everything fitted, wired up and ready to go. Volume and output sockets are on the front panel, input sockets are on the back. Note the heatsink on the IC.

Construction

The circuit is very simple, so construction should present few problems. IC1 should be soldered directly to the PCB, without the use of a socket. This IC uses a modest area of PCB foil as a partial heat sink and has additional sinking provided by a finned clip-on heat sink (see Buylines). The PCB should be provided with ten Veropin terminals, to facilitate connections to T1, RV1 and the input and output terminals.

When PCB construction is complete, fit it into a suitable cabinet (we used a Verobox on our prototype) and make the inter-connections to T1, RV1 and the input and output terminals. On our prototype we omitted FS1 and SW1 from the actual unit, since these facilities are already provided by the fused mains plug and the switched power socket of our bench installation. We fitted volume control RV1 and the speaker terminals to the unit's front panel and fitted the input terminals to the rear. Note that holes should be drilled in the sides (or top) of the completed cabinet, to aid heat dissipation.

When construction is complete, fit a suitable speaker (ideally 8R0) in place, connect a suitable input signal and switch the unit on. Check that good quality reproduction is obtained (the unit will drive roughly 4 W into an 8R0 speaker) and that the volume can be varied via RV1. The unit is then complete.

HOW IT WORKS

There really is not a great deal we can say here, as the circuit is so simple. Q1 is a high-impedance FET (field effect transistor) and is used as a unity-gain buffer amplifier. Its output is fed to the input of IC1 via RV1, the volume control.

IC1 is a 5 W power amplifier (actually an up-rated version of the LM380 2 W IC), with an integral heat sink that is coupled to the three centre pins on either side of the IC package. The output of the power amplifier is passed to an external speaker via C5 and the whole shebang is mains powered via T1-D1-D2 and C6.

The output of the IC is (according to the manufacturers) short circuit proof and can work into any speakers with impedances in the 4R0 to 16R range. In practice, the circuit works best with 8R0 speakers. To ensure adequate power handling capability, our IC is soldered to a PCB heat sink and is also fitted with a finned clip-on heat sink.

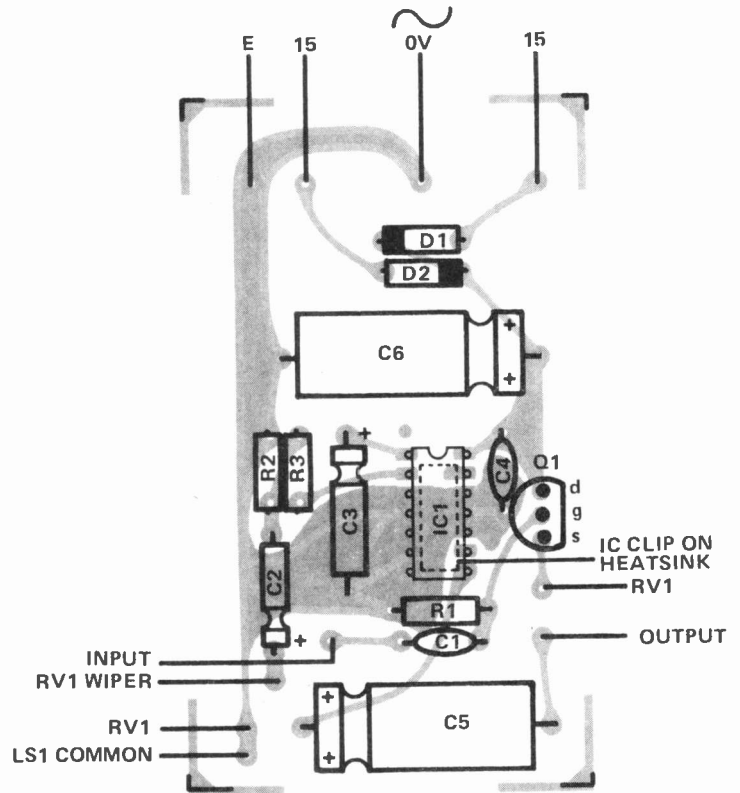


Fig. 2. Component overlay of the Bench Amp.

PARTS LIST

Resistors all ¼ W 5%

R1	10M
R2	15k
R3	10k

Potentiometer

RV1	10k logarithmic
-----	-----------------

Capacitors

C1, 4	100n polyester
C2	1u063 V axial electrolytic
C3	47u 25 V axial electrolytic
C5, 6	1000u 25 V axial electrolytic

Semiconductors

Q1	2N3189
IC1	LM384
D1, 2	1N4001

Miscellaneous

FS1 100 mA and holder, SW1 DPDT miniature toggle, T1 15-0-15 12 VA mains transformer.

BUYLINES

All components used in the ETI Bench Amplifier should be readily available from major stockists. The clip-on heat sink can be obtained from Watford Electronics.

NEW THE TUSCAN S100

A Z80 based S100 Computer System.

TUSCAN main board. The heart of the system with Z80, video, Ram, Rom, and I/O plus five S100 slots for expansion.

A range of firmware options available.

Available in Kit Form or Assembled.

All components available separately.

Houses two 5 1/4" drives for a compact business system
Professional case will house the complete system
Two keyboard options
Hinged lid for easy access
Stylish finish ideal for office or home.

KITS
from
£195 + VAT
delivery Ex-Stock

TANGERINE

COMPUTER SYSTEMS

"MICRON"

EX-STOCK


the latest line in superb products on demonstration from your London stockist

£396.00
inc. VAT
BRITISH DESIGN

- 6502 based microcomputer
- VDU alpha numeric display
- Powerful monitor TANBUG
- 8K RAM
- 32 parallel I/O lines
- 2 serial I/O lines
- RS 232 C/20mA loop, with 16 programmable Baud rates
- Four 16 Bit counter timers
- CUTS cassette recorder interface
- Data bus buffering
- Memory mapping control
- 71 Key ASCII Keyboard, including numeric keypad and with auto repeat
- Including metal cabinets for both keyboard and modules
- Including power supply
- 10K Microsoft BASIC

CENTRONICS QUICK PRINTER

List Price
£459
incl. VAT

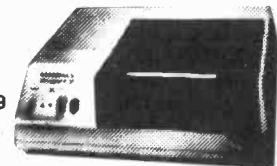

OUR PRICE
plus
VAT

EXCLUSIVE TO HENRY'S
50% OFF MAKER'S PRICE **£195**

for: Software selectable 20, 40 and 80 column using 120mm aluminium-ised paper. 1 roll supplied. 150 lines per minute.
TANDY, PET, NASCOM
Centronics parallel data interface for Nascom, Tandy, etc.
240 volt mains input. ASCII character set Paper feed, and on/off select switches 'BELL' signal Weight 10lbs Size: 13" x 10 1/2" x 4 1/2"

MONITORS
New and Reconditioned
FROM £35

NASCOM PRODUCT LIST + VAT

I/O board kit less I/O chips	45.00
UART + BAUD rate generator + crystal for I/O board	16.00
Econographics kit for additional 128 characters (N1 only)	30.00
2708/2716 Programmer suitable for N1 and N2 under NAS-SYS	£20.95
Nascom 19" rack mounting card frame for N1 and N2	32.50
Nas-DA disassembler 3 EPROM for Nas-sys	37.50
MK36271 8K BASIC in 8K x 8 ROM	
Naspen VS in 2 EPROM	30.00
Nas-svs monitor in 2 EPROM	25.00
4 Games Tape	£6.50
Nasbug T4 2 x EPROM	25.00
Tiny Basic 2 x EPROM	25.00
Super Tiny Basic 3 x EPROM	37.50
Super Tiny Basic upgrade 1 x EPROM	12.50
Type Software	
ZEAP 2 tape and documentation for Nas-sys	30.00
8K BASIC tape and documentation for N1	15.00

THE HENELEC DISK SYSTEM

FOR NASCOM and any other Z80 8080 Microcomputer with an uncommitted P10

DISKS

- The Henelec controller card plugs direct into a Z80 P10 and controls up to 3 double-sided mini-floppy drives giving a maximum 480K system.
 - General Purpose FDC control software for simple DOS or for CPM.
 - Simple DOS software for NASCOM 1/2 under NAS-SYS
 - OR ROM CB10S for CPM on NASCOM 1/2 incorporating the major NAS SYS features. Maximum 60K CPM system
 - New MD prom supplied for N2/CPM
- TWO SYSTEMS**
- SIM-DOS "Floppy Tape Recorder" with 1 drive PSU firmware, etc. Double sided £380 plus VAT
 - CPM System with 1 drive, double sided PSU firmware, etc. £450 plus VAT
 - Additional Drives with PSU £206 plus VAT

COMPUTER KEYBOARDS

APPLE COMPUTER KEYBOARD

52 Key 7 Bit ASCII coded Positive Strobe +5V - 12V Size 13x4 1/4" Sturdy Construction Sloping Keys Black/White print. Made in USA for Apple Inc **Brand New £36 incl VAT.** Post £2.50 Individually packed in ANTI-STATIC FOAM

71 KEY ASCII KEYBOARD INCLUDING NUMERIC KEYPAD. £49.00 plus £7.35 VAT TOTAL £56.35. Uses gold crosspoint keys. Includes keypad and ribbon cable. Only available as fully assembled and tested




CARTER 57 key ASCII keyboard. Conventional key board. 128 ASCII characters including control keys. Parallel output with strobe. Shift lock. + 5 V and -12 V DC. 12" x 5.5" x 1.5" Black keys with white legends. **39.34 + VAT.**

FERRANTI - "SIZE 14 x 6 x 3" SLOPING FRONT" 55 Key ASCII Coded in steel case. Complete with Plug and Cable with circuit to convert to T.T.L. levels. In good condition at only **£19.95 + VAT, P/P £2.50**

nascom-2

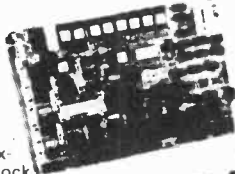MICRO-KIT COMPUTER WITH IMPROVED 16k B RAM Board



Ex-stock

only **£335**

+ VAT
Full after sales service

Firmware & MOS ICs Software

Zeap Assembler (4, 1Kx8 EPROMS) **£50**
Nas Pen text editor (2, 1Kx8 EPROMS) **£30**
Expansion boards (in kit form)
48K RAM **£210** ● 32K RAM **£175.00**
16K RAM **£140**

EPROM CARD (NASCOM compatible) KIT. Suitable for 16 x 2708 or 16 x 2716 or mixed 1 x NASCOM 8k BASIC ROM **£66.00.** BASIC programmers aid. Self locating tape **£14.95.**

POWER SUPPLY £29.50

NASCOM-1

12" x 8" PCB carrying 5LSI MOS packages, 16 1K MOS memory packages and 33 TTL packages. There is on-board interface for UHF or unmodulated video and cassette or teletype. The 4K memory block is assigned to the operating system and video display leaving a 1K user RAM. The MPU is the standard Z80 which is capable of executing 158 instructions including all 8080 code.

Build price **£140 + VAT.**

Nascom-1 Kit Price
£125
Plus VAT
+ P&P £1.50

325



PLAIN PAPER £325 PRINTER Fully built and housed in a stylish enclosure for just **£325 plus VAT.**

INTERFACES WITH ALL MICRO COMPUTERS

The Nascom IMP (Impact Matrix Printer) features are

- 60 lines per minute. ● 80 characters per line.
- Bi-directional printing. ● 10 line print buffer.
- Automatic CR/LF. ● 96 character ASCII set (including upper/lower case, \$, £).
- Accepts 8 1/2" paper (pressure feed). ● Accepts 9 1/2" paper (tractor feed).
- Tractor/pressure feed. Baud rate from 110 to 9600. ● External signal for optional synchronisation of baud rate.

IDEAL FOR WORD PROCESSING

Microtan 65 kit	£69.00	Tanex assembled	53.00
Microtan 65 assembled	79.00	Tanex (expanded)kit	106.50
Lower case option	9.48	Tanex (expanded)assmbld	116.50
Graphics option	6.52	Serial I/O option	12.87
20 way keypad	10.00	Tanram kit	34.00
Full ASCII keyboard	49.00	Tanram assembled	44.00
Tanex kit	43.00	Tanram (expanded)assbld	190.00

SEND FOR COMPLETE COMPUTER BROCHURE FREEPOST TO ADDRESS BELOW

MEMORIES Discounts 10% for 4, 15% for 8, 20% for 16	
MK 3880 (N280)	7.60
MK 3880-N4 (Z80A)	7.95
MK 4116 16K x 1 dy RAM	6.50
MK 4027 4K x 1 dy RAM	2.25
2102 1K x 1 static RAM	1.00
4118 1K x 8 static RAM	12.75
	2708
	2716
	IM6402 UART
	2114 1K x 4 static RAM
	8080A
	5.95
	15.00
	4.50
	3.25
	5.25

ADD VAT 15% TO YOUR ORDER EXCEPT WHERE STATED



HENRY'S

Computer Kit Division
404 Edgware Road, London, W2, England I.E.D.
01-402 6822

Official Export & Educational Orders Welcome
Our telex: 262284
Mono Ref. 1400 Transconics


Active Tone Controls

This tone control circuit is easy to incorporate in a stereo amplifier, disco unit, or whatever, as it has a high input impedance (over 100k), a nominal voltage gain of unity and a low output impedance. The usual bass and treble controls are included in the unit, with about 12 dB of boost and cut being available at 100 Hz and 10 kHz. The noise and distortion produced by the circuit are both extremely low due to the large amount of negative feedback used and the unit can handle output signal levels of several volts RMS without clipping.

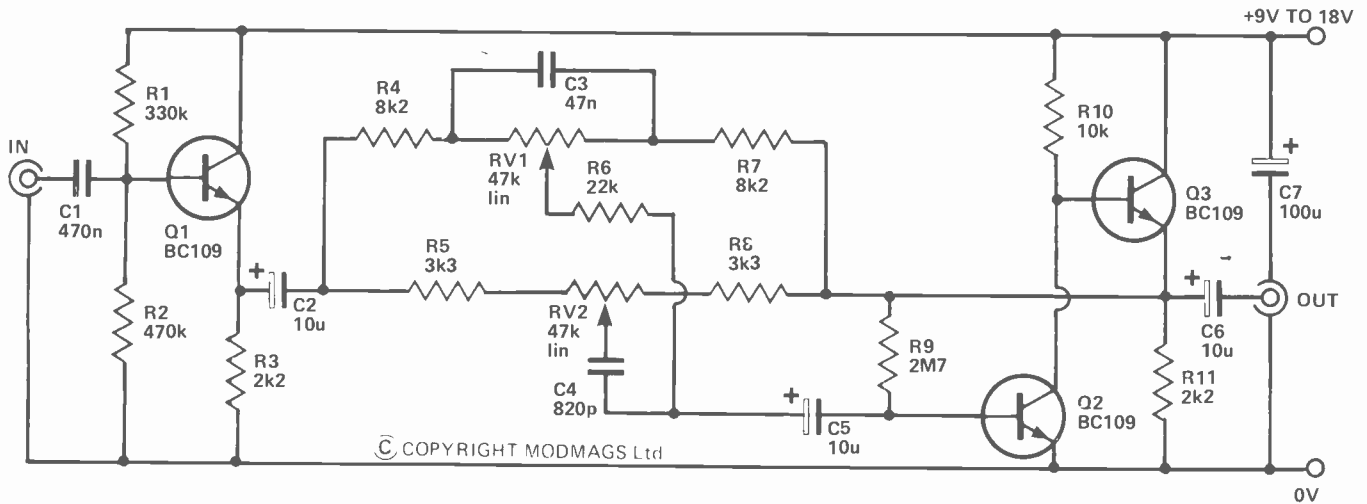Q1 is used in a straightforward emitter follower buffer stage that gives the unit a high input impedance. C2 couples the output of Q1 into the

tone control circuitry. This is an active circuit which provides frequency-selective negative feedback over an amplifier. The amplifier uses Q2 as a conventional common emitter stage direct-coupled to emitter follower output transistor Q3. The latter gives the unit a low output impedance.

The tone control networks are slightly simpler than the usual "Baxandall" configuration, but give a perfectly acceptable level of performance. RV1 controls the bass while RV2 is the treble control. Feedback is at a maximum with the sliders of the potentiometers to the right and at a minimum with the sliders set fully to the left. Of course, the gain of the circuit is inversely proportional to the level of feedback. Maximum feedback therefore corresponds to maximum cut and not to full boost. The current consumption of the circuit is a little under 1 mA per supply volt.




© COPYRIGHT MODMAGS Ltd

OHIO SCIENTIFIC SUPERBOARD 2


50ZH BLACK AND WHITE VERSION
£159 + 15% VAT POST FREE
50ZH COLOUR VERSION £215 + 15% VAT

THIS UNIQUE SPECIAL OFFER

- ★ If bought with Superboard or Colourboard these items are at the reduced prices shown first.
- ★ Add 15% VAT. Modulator and power supply kit £1 (£25). 4K extra ram £20 (£24). Display expansion kit, approx 30 lines x 54 characters. £15 (£20). Case £23 (£26). Colour conversion board fully assembled £55 (£55).
- ★ Cassette recorder £13 (£15). Extended monitor £20 (£20). Assembler/Editor £25 (£25). 610 Expansion board £160 (£160). Mini-Floppy with psu and 2 copies DOS £275 (£275).

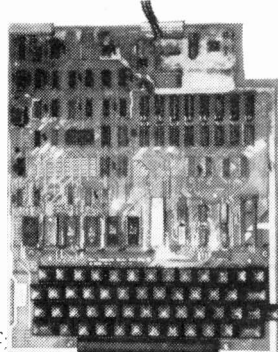


SHARP COMPUTERS

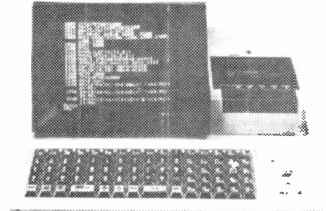

The brilliant new Japanese computer MZ80-K which is beating the hell out of PET. 20K ram expandable to 48K. Built in VDU screen, music function and cassette. Displays 40 characters x 25 lines and 80 x 50 on graphics. £438 + 15% VAT.

MZ80P3 Printer £515 + 15%
MZ80 FD Floppy Disc £772 + 15%
MZ80 I/O Interface £96 + 15%
PC1211 £94 + 15% CE121 £13 + 15%

SUPER PRINT 800MST

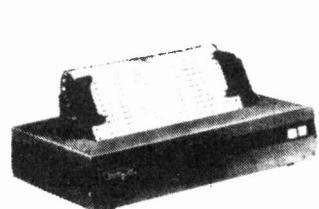

The ideal impact matrix printer for Superboard. UK101 pet apple trs80 mz-80k 60 lines/minute 72, 80, 96, 120 and 132 chr/line. Tractor and friction feed. Graphics and user definable chr sets. RS232, 20ma IEEE488 and centronics I/O. SPECIAL OFFER. Supplied with free word processor program and interface components for Superboard. £359 + 15% VAT.

SWANLEY ELECTRONICS


Dept. ET1, 32 Goldsæl Rd., Swanley, Kent BR8 9EZ

Mail order only. Please add 35p postage. Prices include VAT unless stated. Lists 27p post free. Overseas customers deduct 13% Official credit orders welcome.

ETI DECEMBER 1980

TV GAMES

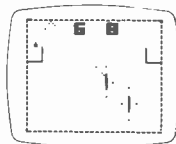AY 3-8550 chip £4.00, kit £5.25.
Stunt cycle AY-3-8765 chip + kit £20.95. 10 game paddle 2AY-3-8600 chip £5.95, kit £7.03. Modified shoot kit £5.28. Colour generator kit £9.95.



MAINS TRANSFORMERS

6 0-6V 100ma 96p, 1 1/2a £3.12, 9 0-9V 75ma 96p, 1a £2.88, 2a £4.73, 12-0-12V 100ma £1.20, 1a £3.50. 15-0-15V £3.78.

JC12 and JC20

Integrated circuit audio amplifier chips with data and printed circuits. JC12 6 watts £2.50. JC20 10 watts £3.78.

CONTINENTAL SPECIALITIES PRODUCTS

EXP300 £6.61, EXP350 £3.62, EXP325 £1.84, EXP650 £4.14, EXP4B £2.64.

STABILIZED POWER KITS

TTL computer supplies 5v 2a £8.18, 5v 4a £13.88. 8-way types 3/4v/6v/12v/15v/18v 100 ma. £3.12, 1a £7.80, 2a £11.81. Variable voltage models 2 18v 100ma £3.12, 1-30v 1a £8.10, 1 30v 2a £14.52.

PRINTED CIRCUIT MATERIALS

PC etching kits economy £2.72, standard £5.06. 40 sq in pcb 50p, 1 lb FeCl1 £1.60. Etch resist pens economy 50p, dolo 90p, drill bits 1 3/2nd in or 1mm 35p. Etching dish 92p. Laminated cutter £1.30.

BI-PAK AUDIO MODULES
AL30A £4.53, PA12 £9.31, PS12 £1.75, T53B £2.70, S450 £27.90, AL60 £5.62, PA100 £19.24, SPM80 £5.26, BM180 £6.06, Stereo 30 £23.94, AL80 £8.56.

COMPUTER GAMES

New Sensory Chess Challenger 8 £119, Chess Challenger 7 £79, Chess Champion 6 £49.95, Checker Challenger 2 £33, Star chess £62, Atari Video computer cartridges £14.85 (except chess £43.95, backgammon £33.95 and space invaders £27.50). Special offer video computer plus space invaders £146.

S-DEC AND T-DECS

S Dec £3.78, T Dec £4.59, 16 dil adaptor £2.31.

COMPONENTS

1N4149 0.9p, 1N4002 3.7p, 2114 memory chips, low current 300ms £3.45, 723 14 dil 36p, NE555 8 dil 26p, 741 8 dil 20p, bc 547, bc549 bc182, bc184, bc212, bc214 6.1p, tip 32c 43p, tip4c 48p, bd132 32p, Fuses 20mm x 5mm cartridge 15, 25, 5 1 2 3 5a quickblow 2p, Resistors, 5% 1/4W E12 10R to 10M 1.5p, 0.8p for 50¢ of one value Polyester capacitors 160v 015, 060mf, 2.8p, 047, 1mf 4p, 01mf 3p, 022, 033mf 3.3p, 15 22 33mf 4.9p, 47mf 8p, Polystyrene capacitors £12.63v 10 to 1000pf 4p, 1n2 to 10n 5p, Ceramic capacitors 50V E6 E22pf to 47n 2.5p, electrolytic capacitors 50v 5 1, 2mf 6p, 25v 5, 10mf 8p, 16v 22, 33mf 9p, 47, 68mf 5p, 100mf 7p, 330 470mf 8p, 1000mf 11p, Zeners 4000mW E24 2v7 to 33v 7p, Preset pots subminiature 0.1W horn or ven 100 to 2M2 8p, Potentiometers 1/4W 4K7 to 2M2 single 29p, dual 71p, 1/2 red LEDs 11p, IC sockets 8 dil 8.7p, 14 dil 10.1p, 16 dil 12p.


BATTERY ELIMINATORS

3-way types with switched output and 4 way multi jack 3/4v/6v 100ma £2.94, 6/7v/9v 300ma £3.45. 100ma radio types with press-stud connectors 9v £4.77, 6v £4.77, 4.5v £4.77, 9v £4.77, 9 + 9v £5.99, 6 + 6v £5.99, 4.5v + 4.5v £5.99. Cassette recorder mains unit 7 1/2v 100ma with 5 pin din plug £4.77. Fully stabilised type 3/6/7 1/2v/9v 400ma £6.95. Car converters 12v dc input output 7 1/2v 300ma £1.19, output 3/4v/6/7 1/2v/9/12v 800ma £3.04.

BATTERY ELIMINATOR KITS

100ma radio types with press-studs 4 1/2v £1.64, 6v £1.64, 9v £1.64, 4 1/2 + 4 1/2v £2.30, 6 + 6v £2.30, 9 + 9v £2.30. Cassette type 7 1/2v 100ma with din plug £1.64. Heavy duty 13 way types 4 1/2v/6/7 1/2v/11/13/14/17/21/25/28/34/42v 1a £6.62, 2a £10.56. Car converter input 12v dc output 6/7 1/2v/9v 1A stabilised £1.62.

SINCLAIR PRODUCTS

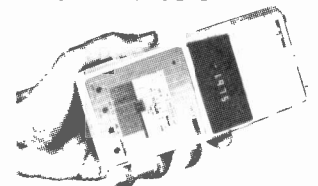

SC110 10MHz oscilloscope £144.95. PFM200 £51.95, case £2.07, adaptor £4.20, connector kit £13.95. Microvision tv £89, adaptor £6.88, POM35 £34.23, adaptor £4.20, case £2.07, DM350 £76.70, DM450 £102.17, DM235 £55.55. Accessories for all 3 models rechargeable batteries £7.99, mains adaptor/charger £4.20, case £8.90. Enterprise prog calculator £19.95, TG105 £87, TF200 £150.

DESIGNER'S NOTEBOOK

This month Ray Marston takes an in-depth look at the VCO section of that ubiquitous CMOS chip, the 4046B phase-locked loop.

The 4046B CMOS chip is probably one of the most versatile and least-used of all the ICs in the CMOS range. The device glories in (or suffers from) the descriptive title of 'micropower phase-locked loop' and there is a widespread misconception amongst many electronics amateurs and professionals that the device can only be used in PLL applications. In fact nothing could be further from the truth.

The Inside Story

The 4046B actually contains a pair of phase-comparators, a zener diode and one VCO or voltage-controlled oscillator. All of these sections are independently accessible via the IC pin-outs. The VCO section of the device is probably the most versatile and cost-effective voltage-controlled oscillator on the market. It produces a well-shaped symmetrical square wave output, has a top-end frequency limit in excess of 1 MHz, can be voltage-scanned through a 1,000,000:1 range (1 Hz to 1 MHz) when used with a single timing resistor or through any range from 1:1 to infinity (0 Hz to 1 MHz) when used with a pair of timing resistors.

If that were not enough, the voltage-controlled oscillator can also be independently gated on and off via an INHIBIT terminal, can be operated from any supply in the range 3-18 V and can, when used in conjunction with one of the 4046B's phase comparators, produce a two phase output. The linearity of the VCO is typically a healthy 1% or so.

Basic 4046B VCO Circuits

Figure 1 shows the internal block diagram and the pinouts of the 4046B phase-locked loop IC. The device contains two types of phase comparator, a VCO and a zener diode. In practical PLL applications, the VCO and one or other of the comparators are interconnected to form a 'loop', which causes the VCO to lock the the mean frequency of an input signal connected to pin 14.

For our present purposes the most important element of the IC is the VCO, or voltage controlled oscillator. The operating frequency of the oscillator is governed by the value of a capacitor connected between pins 6 and 7 (minimum value 50 pF), by the value of a resistor wired between pin 11 and ground (minimum value 10k) and by the voltage applied to VCO-input pin 9 (any value up to the supply voltage in use).

Figure 2 shows the simplest possible way of using the VCO section. Here, the pin 9 'voltage control' input is tied permanently high and the circuit acts as a basic square wave oscillator, with its frequency variable over a 10:1 range by RV1. Note at this point that the VCO output (pin 4) is tied directly to the pin 3 phase comparator input. If pin 3 is allowed to float, the comparators tend to self-oscillate at about 20 MHz and superimpose an HF signal on the top part of the VCO output waveform.

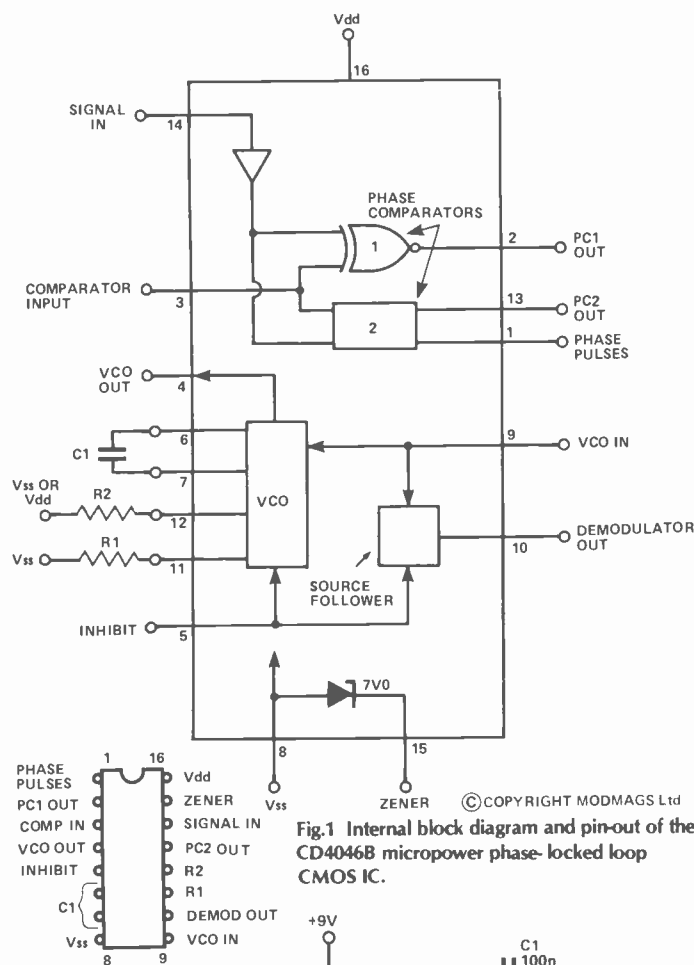


Fig.1 Internal block diagram and pin-out of the CD4046B micropower phase-locked loop CMOS IC.

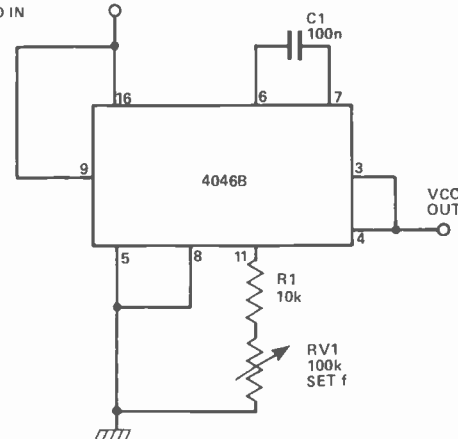


Fig.2 Simple variable-frequency (200 Hz to 2 kHz) square wave generator. →

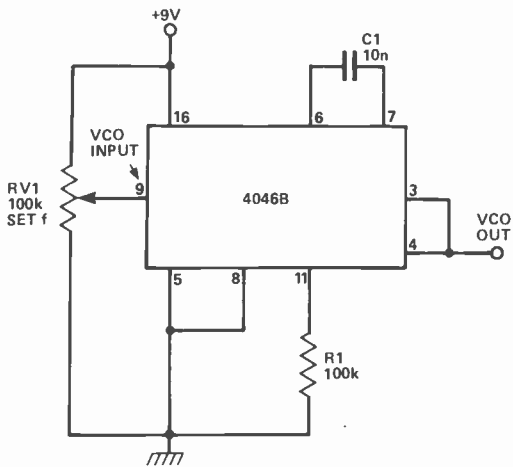


Fig.3 Wide range VCO with frequency variable from near zero to 1.4 kHz via the pin 9 voltage.

Ranging Far And Wide

Figure 3 shows how to connect the 4046B as a genuine wide-range VCO. Here, R1-C1 determine the top (maximum) frequency that can be obtained and RV1 controls the actual frequency via the pin 9 voltage. The frequency falls to near-zero (a few cycles per minute) with pin 9 at 0 V. The effective control range of pin 9 varies from roughly 1 V below the supply value to 1 V above zero, ie RV1 has a 'dead' control area of several hundred millivolts at either end of its range.

Figure 4 shows how these 'dead' areas can be eliminated by wiring a silicon diode in series with each end of RV1. The circuit also shows how the minimum operating frequency can be reduced to absolute zero by wiring a high value resistor (R2) between pins 12 and 16. Note here that, when the frequency is reduced to zero, the VCO output randomly settles in either the logic 0 or logic 1 state.


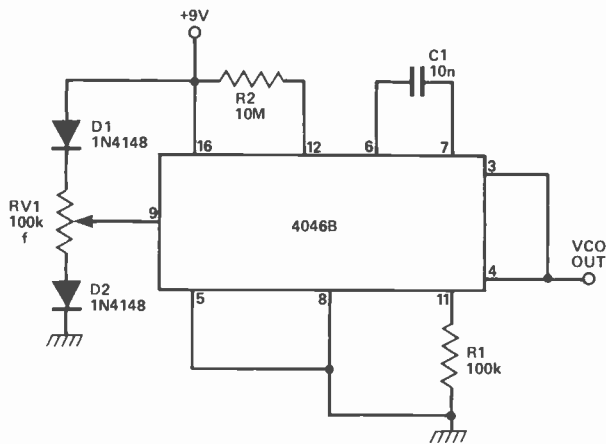


Fig.4 Wide range VCO with frequency variable down to absolute zero.

Figure 5 shows how the pin 12 resistor can alternatively be used to determine the minimum operating frequency of a restricted-range VCO. Here, f_{min} is determined by R2-C1 and f_{max} is determined by C1 and the parallel resistance of R1-R2.

Figure 6 shows an alternative version of the restricted-range VCO, in which f_{max} is controlled by R1-C1 and f_{min} is determined by C1 and the series combination of R1 and R2. Note that, by suitable choice of the R1 and R2 values, the restricted-range VCO can be made to span any range from 1:1 to near-infinity.

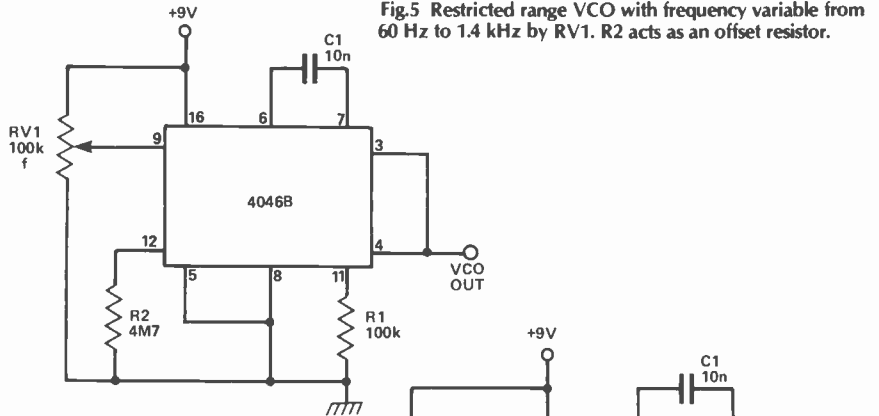

© COPYRIGHT MODMAGS Ltd

Fig.5 Restricted range VCO with frequency variable from 60 Hz to 1.4 kHz by RV1. R2 acts as an offset resistor.

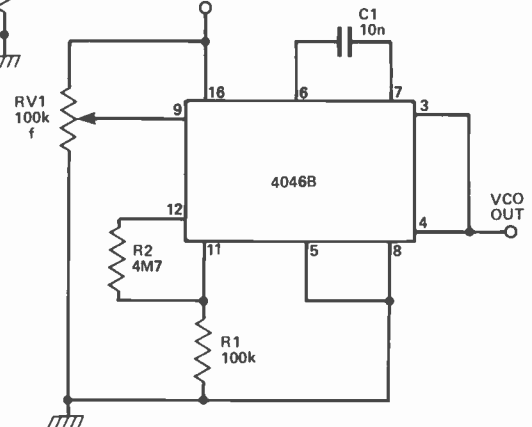


Fig.6 An alternative restricted range VCO, in which f_{max} is controlled by R1-C1 and f_{min} by (R1 + R2)-C1.

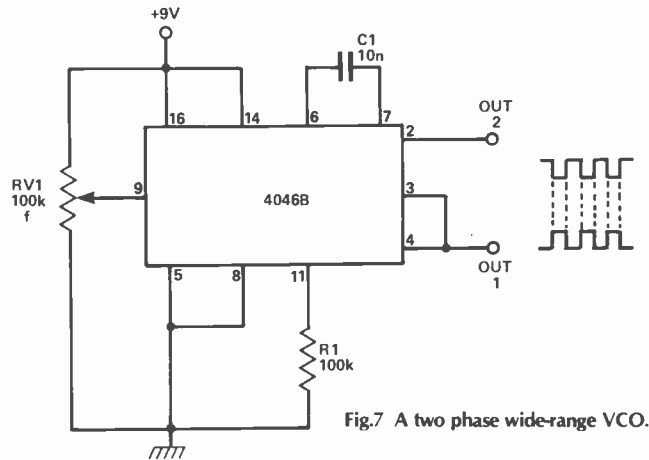


Fig.7 A two phase wide-range VCO.

Square Pear

The VCO can be made to generate a pair of anti-phase square wave outputs by connecting its output to the phase-comparator input, taking the signal input (pin 14) high and taking the anti-phase output from pin 2. Figure 7 shows the connections. Note that this circuit makes use of the IC's built-in EX-OR gate (phase comparator 1).

The VCO section of the 4046B can be disabled by taking pin 5 of the package high (to logic level 1). This feature enables the VCO to be gated on and off by external signals. Figure 8 shows how the VCO can be manually gated via a push button connected directly to pin 5, while Fig.9 shows how the circuit can be gated electronically by an external gate inverter. Alternatively, if the two phase output facility is not required, the internal EX-OR phase detector can be used to provide gate inversion, as shown in Fig.10. Note in this latter case that pin 4 is not connected to pin 3.

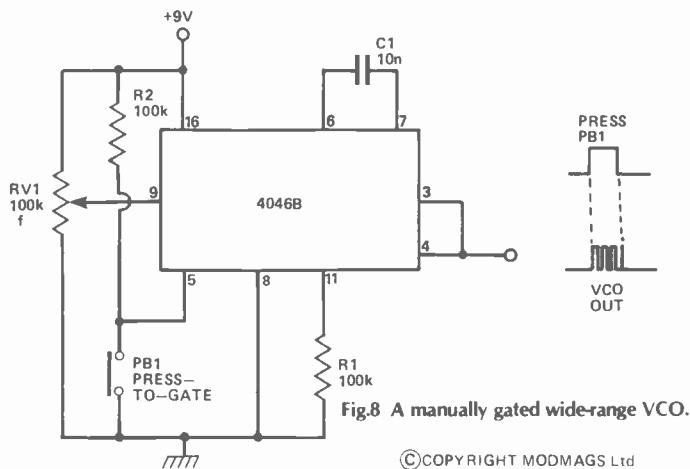


Fig.8 A manually gated wide-range VCO.

©COPYRIGHT MODMAGS Ltd

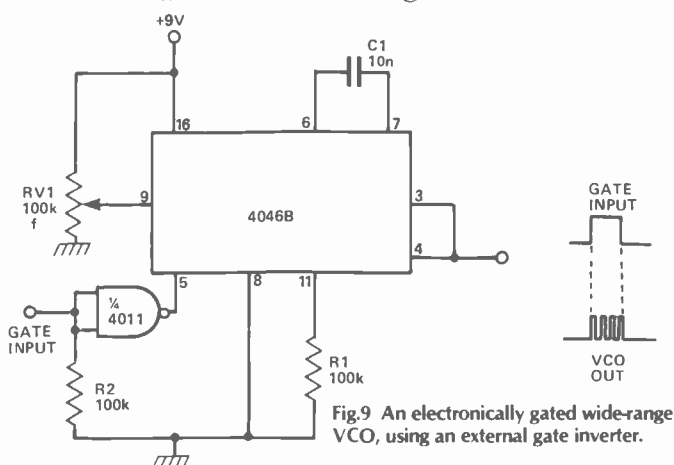


Fig.9 An electronically gated wide-range VCO, using an external gate inverter.

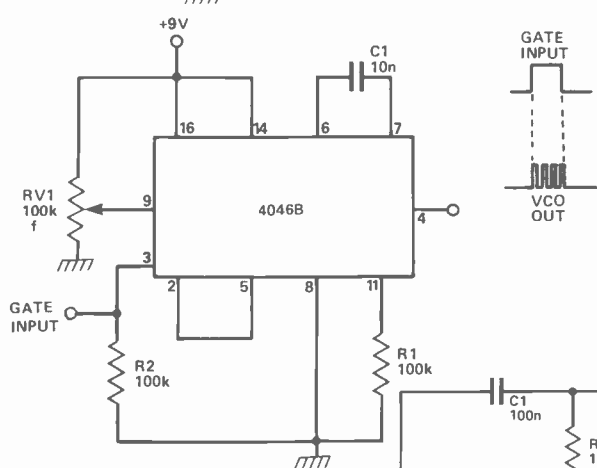


Fig.10 An electronically gated wide-range VCO using the internal EX-OR phase detector for gate inversion.

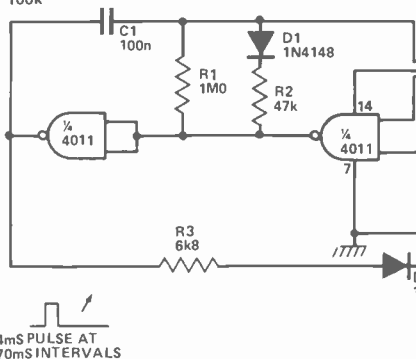


Fig.13 Phaser sound generator circuit.

©COPYRIGHT MODMAGS Ltd

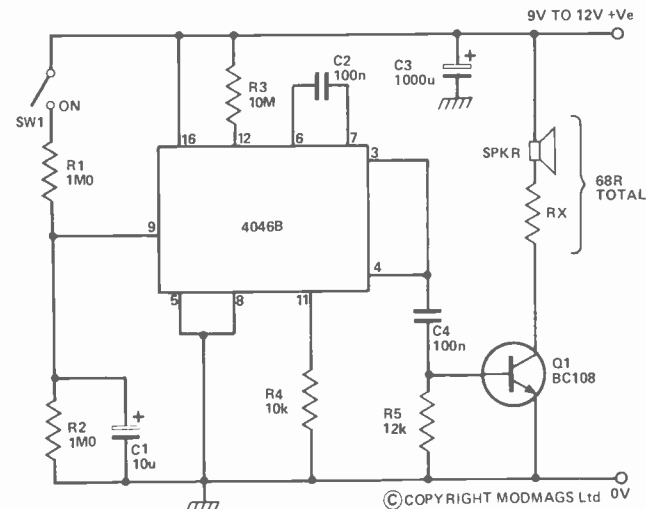


Fig.11 An electronic siren giving slow rise and fall of its operating frequency.

©COPYRIGHT MODMAGS Ltd

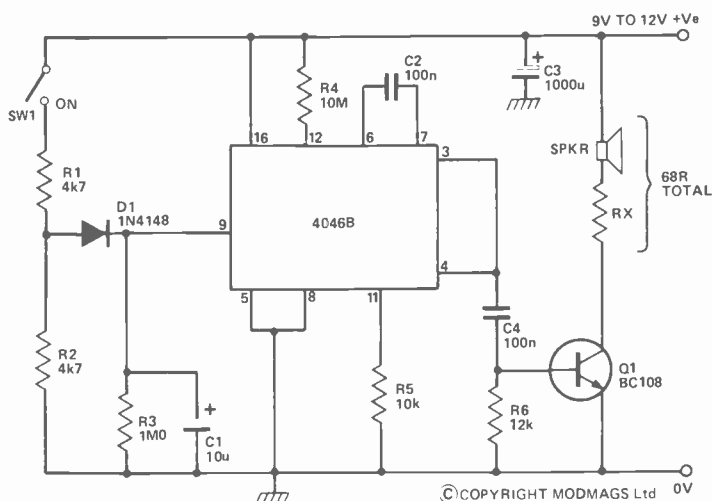


Fig.12 This quick-start siren gives a rapid rise and slow fall of its operating frequency.

©COPYRIGHT MODMAGS Ltd


and the VCO frequency rises slowly from zero to a maximum value. When SW1 is opened, C1 discharges via R2 and the operating frequency slowly decays to zero. The VCO output is AC-coupled to the speaker via C4 and Q1.

The Fig.12 quick-start siren is similar to the above, except that C1 charges rapidly to half-supply volts via R1-R2 and

Sirens And Sound Effects

Figures 11 to 14 show some practical siren and sound effects generator VCO circuits. Figure 11 is a conventional siren circuit. When SW1 is closed, C1 charges exponentially via R1

Fig.14 Combined pulsed tone/warble tone alarm generator. The high tone is determined by R3, the low tone by (R3 + R4).

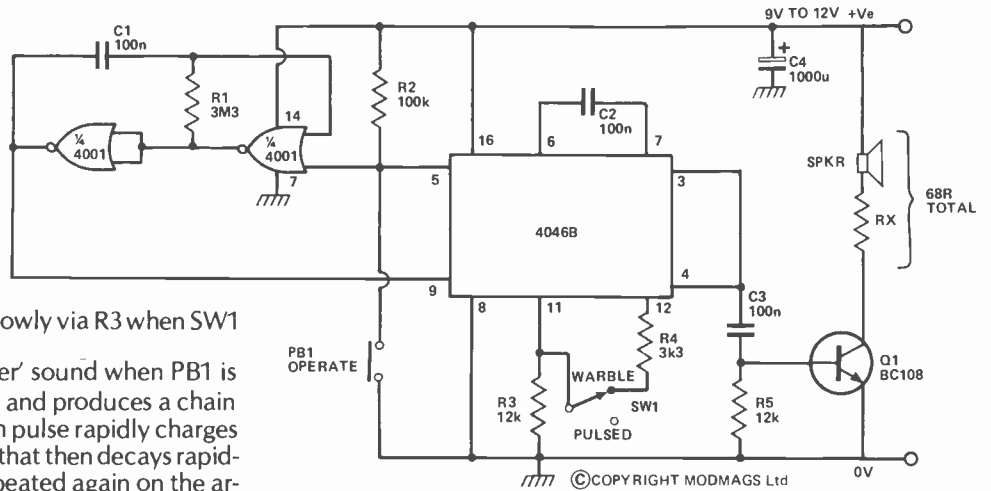

D1 when SW1 is closed and discharges slowly via R3 when SW1 is opened.

The Fig.13 circuit produces a 'phaser' sound when PB1 is closed. The 4011 astable is gated by PB1 and produces a chain of 4 mS pulses at intervals of 70 mS. Each pulse rapidly charges C2 via R3 and D2, to produce a high tone that then decays rapidly as C2 discharges via R5, only to be repeated again on the arrival of the next pulse.

The Figure 14 circuit generates either a pulsed tone or a warble tone signal (depending on the setting of SW1) when PB1 is closed. PB1 is used both to enable pin 5 of the 4046B and to

frequency (tens of kHz) and effectively generates a random number of clock pulses. When PB1 is released, Q1 turns off and the VCO timing is governed by R8. Simultaneously, C1 rapidly discharges to half-supply volts via R1-R2-D1, so the VCO operates at only 100 Hz or so. C1 then slowly discharges via R3 and the VCO frequency slowly decays to zero over a period of about 15 S.

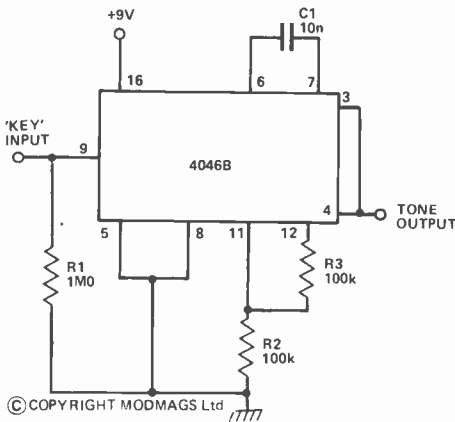


Fig.15 FSK generator -- logic 0 = 1.2 kHz, logic 1 = 2.4 kHz.

gate on the 4001 astable, which then applies a rectangular (alternatively fully-high and fully-low) waveform to pin 9. In the pulsed mode the VCO generates zero frequency when pin 9 is low. In the warble mode it generates a tone that is 20% down on the high tone when pin 9 is low.

Miscellaneous VCO Circuits

Figures 15 to 19 show a miscellany of 4046B VCO circuits. The Fig.15 circuit is that of a FSK generator which produces a 2.4 kHz tone when a logic 1 signal is applied to pin 9 and a 1.2 kHz tone when a logic 0 signal is applied. The high tone is controlled by R2 and the low tone by R2 and R3.

Figure 16 is a 220 kHz FM generator. The internal zener of the 4046B (pin 15) is used to provide a stable 7V0 supply to the x20 3140 inverting amplifier, which is quiescently biased at 3V5 by the R2-R3 potential divider. The pin 9 VCO signal is thus a mean 3V5 potential amplitude modulated by an amplified version of the AF input signal, which thus frequency-modulates the output of the VCO.

Running Down

The Fig.17 circuit is that of a run-down clock generator of the type used in dice and roulette games. When PB1 is pressed, C1 charges to a high voltage via D2. Simultaneously, Q1 is biased on via D3-D4 and effectively connects R6 between pin 11 and ground. Under this condition, the VCO operates a high

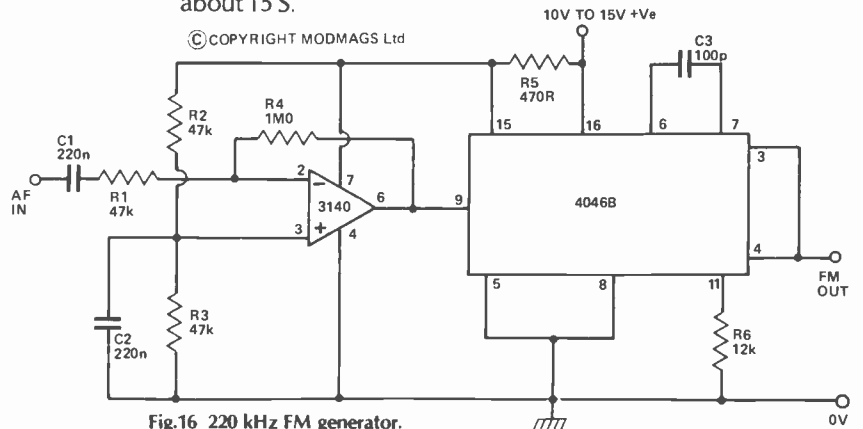


Fig.16 220 kHz FM generator.

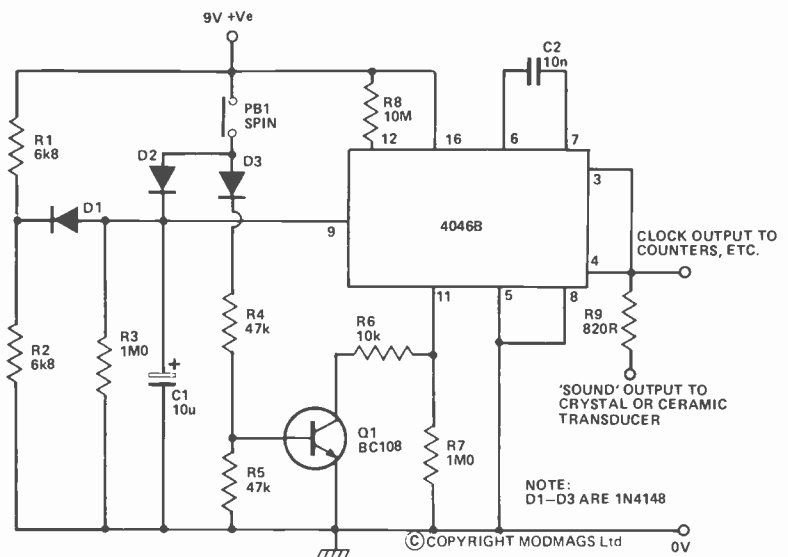


Fig.17 Run-down clock/sound generator for use in dice/roulette games. The circuit is suitable for use with edge-sensitive clock circuits only. The output can be used to directly clock most types of counter and can be fed, via R9, to crystal or ceramic transducers to directly produce 'run down' sounds. When the run-down is complete this circuit may settle in either logic 0 or 1, so it cannot safely be used to clock level-sensitive circuitry.

ETI

Unique in concept - the home computer that grows as you do! New! - The Acorn Atom



£120 An outstanding personal computer kit
plus VAT and p&p.

Also available ready-built
£150
plus VAT and p&p

The ATOM - a definitive personal computer. Simple-to-build, simple-to-operate. But a really powerful full-facility computer. And designed on an expandable basis. You can buy a superb expanded package now - tailored to your needs. Or, you can buy just the standard Atom kit, and, as you grow in confidence and knowledge, add more chips. No need to replace your equipment. No need to worry that your investment will be overtaken by new technology. As you need more power, more facilities, you can add them!


*The picture shown demonstrates mixed graphics and characters in three shades of grey provided by the Standard Atom

The standard ATOM kit includes:

- Full sized QWERTY keyboard
 - Rugged polystyrene case
 - Fibreglass PCB
 - 2K RAM
 - 8K ROM
 - 23 integrated circuits
 - Full assembly instructions including tests for fault-finding.
- (Once built, connect it to any domestic TV and power source)

- Power requirement: 8V at 800 M A. ATOM power unit available.

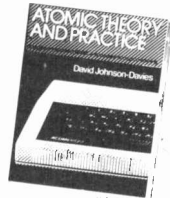See coupon. PLUS FREE MANUAL written in two sections - teach yourself BASIC and machine code for those with no knowledge of computers, and a reference section giving a complete description of the ATOM's facilities. All sections are fully illustrated with example programs.



The ATOM concept

Adding chips into sockets on the PCB allows you to progress in affordable steps to large-scale expansion. You can see from the specifications that the RAM can be increased to 12K allowing high resolution (256 x 192) graphics. Two further ROM chips, e.g. maths functions, can be added directly to the board giving a 16K capacity. In addition to 5 I/O lines partly used by the cassette interface, an optional VIA device can provide varied I/O and timer functions and via a buffer device allow direct printer drive. An optional module provides red, green and blue signals for colour. An in-board connector strip takes the ATOM communications loop interface. Any number of ATOMs may be linked to each other - or to a master system with mass storage/

hard copy facility. Interface with other ACORN cards is simplicity itself. Any one ACORN card may be fitted internally. So you can see there are a vast number of modular options and additions available, expanding with your ability and your budget.

The ATOM hardware includes:

- Memory from 2K to 12K RAM on board (up to 35K in case)
- 8K to 16K ROM (two 4K additions)
- 6502 processor
- Video Display allows high resolution (256 x 192) graphics and red, green and blue output
- Cassette Interface - CUTS 300 baud
- Loudspeaker allows tone generation of any frequency
- Channel 36 UHF Modulator Output
- Bus output includes internal connections for Acorn Eurocard.

The ATOM software includes:

- 32-bit arithmetic ($\pm 2,000,000,000$)
- High speed execution
- 43 standard/extended BASIC commands
- Variable length strings (up to 256 characters)
- String manipulation functions
- 27 32-bit integer variables
- 27 additional arrays
- random number function
- PUT and GET byte
- WAIT command for timing
- DO-UNTIL construction
- Logical operators (AND, OR, EX-OR)
- LINK to machine-code routines
- PLOT DRAW and MOVE.



4a Market Hill,
CAMBRIDGE CB2 3NJ

Your ACORN ATOM may qualify as a business expense. To order complete the coupon below and post to Acorn Computer for delivery within 28 days. Return as received within 14 days for full money refund if not completely satisfied. **All components are guaranteed with full service/repair facility available.**

Please send me the following items:

Quantity	Item	Item price inc. VAT + p&p	TOTALS
	ATOM KIT 8K + 2K (MIN)	@ £140 00	
	ATOM ASS 8K + 2K (MIN)	@ £174 50	
	ATOM KIT 12 + 12K (MAX)	@ £255 00	
	ATOM ASS 12 + 12K (MAX)	@ £289 50	
	1K RAM SETS	@ £11 22	
	4K FLOATING POINT ROM	@ £23 30	
	6522 VIA	@ £10 35	
	PRINTER DRIVE	@ £3 17	
	Buffer (LS 244)	@	
	MAINS POWER SUPPLY (1.5 amps)	@ £10 20	
	TOTAL		

To: Acorn Computer Ltd., 4a Market Hill, CAMBRIDGE CB2 3NJ

I enclose cheque/postal order for £
Please debit my Access/Barclaycard No.

Signature
Name (Please print)
Address

Telephone No.
Registered No 1403810. VAT No: 215 400 220

ETI/11/80




SPECIAL PURCHASE



OF TOP QUALITY LCD MULTIMETERS

AC/DC
CURRENT
22
RANGES

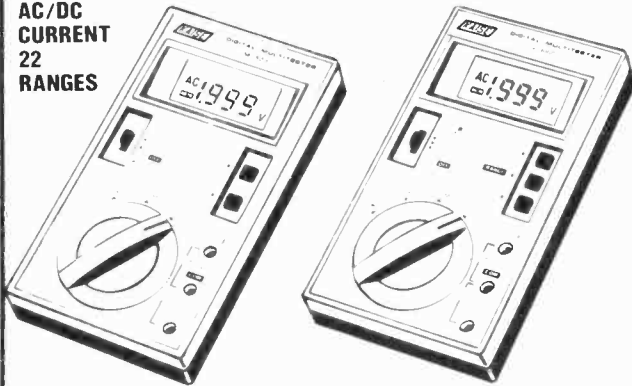

6100

6200

CHOOSE FROM FOUR MODELS

- ★ 3½ digit autoranging (volts / ohms)
- ★ 200 hours battery life (2 pencils)
- ★ 10 amp AC/DC (6220 & 6110) ★ 1000v DC 600v AC
- ★ 200mA AC/DC (6200 & 6100)
- ★ Range hold facility (6100 & 6110)
- ★ Unit and range sign (6110 & 6220)
- ★ Continuity buzzer (6100 & 6110)

RESOLUTION

100 µVDC, 1 mVAC
10 µA AC/DC 0.1 ohm
10 mA on 10A, AC/DC

OTHER FEATURES (ALL MODELS)

Low power OHms Range
Zero Adjust key
Battery Warning
In circuit resistance test
Size 155 x 85 x 28mm. 250g.

ACCURACY

6100/6110
0.5% DC Volts
1% DC Current
1.2% AC Current
0.5% Resistance

6200/6220
0.8% DC Volts
1.3% DC Current
1.4% AC Current
0.8% Resistance

6200 **£39.95**

6220 **£49.95**

6100 **£64.95**

6110 **£74.95**

- ★ All prices include batteries / leads and UK Vat (UK c/p 65p)
- ★ Order by Post or Telephone, with Barclay or Access

OR CALL IN AND SEE FOR YOURSELF

Prices correct at 1 11 80 E&OE

Cubegate Limited OPEN 9-6 SIX DAYS A WEEK

AUDIO ELECTRONICS

301 EDGWARE ROAD, LONDON, W2 1BN

TELEPHONE 01-724 3564



FREE CATALOGUE!

Send large SAE (17½p UK) Schools, Companies, etc. free on request.

From Mr / Mrs / Miss
(Block capitals please)

Ref: ETI

Address

Please supply Qty.

Models

I/We enclose (incl. 65p post)

Chq / PO value

Or debit Barclay / Access No

THE ZX80 COMPANION

Second Edition—THE MONITOR REVEALED

This best-selling Sinclair ZX80 manual has now been extended to include a detailed explanation of the monitor, routines and entry points. Send £10 cheque / P.O. to:

LINSAC
68 Barker Road, Middlesbrough
Cleveland TS5 5ES

Send s.a.e. for latest catalogue of ZX80 programs — games, educational and utilities — in lower-priced packages.

Also available: ZX80 Monitor Listing

TV SOUND TUNER ETI SEP 80 PROJECT

All parts available / send for list

ALSO

No. 1 for Teletext Kits
TV Spare Parts and Components

Callers welcome at Shop Premises

MANOR SUPPLIES

172 WEST END LANE, LONDON NW6 1SD
TELEPHONE: 01-794 8751

Near West Hampstead Jubilee & British Rail Stations

Professional ASCII Keyboards

ONLY
£29.95
ADD + VAT
SCOOP
POST £1.50



The 'APPLE' Computer Keyboard

- 52 KEY 7 BIT ASCII CODED
 - POSITIVE STROBE. +5V - 12V
 - FULL ASCII CHARACTERS
 - PARALLEL OUTPUT WITH STROBE
 - POWER LIGHT ON CONTROL
 - NATIONAL mm 5740 CHIP. TTL OUTPUT
 - SUPERBLY MADE. SIZE 12x5.5x1.5ins
 - BLACK KEYS WITH WHITE LEDGENS
 - ESCAPE, SHIFT, RETURN & RESET KEYS
- Complete with CIRCUIT & DATA

Ideal for use with TANGERINE
TRITON

Ex-Stock from HENRY'S TUSCAN
APPLE & most computers

This is definitely the **BEST BUY**
Supplied **Brand NEW** in manufacturers original jacking
(ANTI-STATIC)

Just post remittance total £35.95 (incl. VAT & Post)




Henry's



Computer Kit Division

404 Edgware Road, London, W2, England
01-402 6822

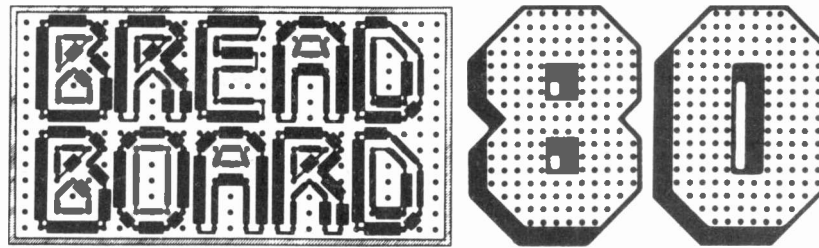COMPUTERS AUDIO RADIO MUSIC LOGIC TESTGEAR CB GAMES KITS



COMPONENTS DEMONSTRATIONS SPECIAL OFFERS MAGAZINES BOOKS



It's all at Breadboard '80

This is **the** exhibition for the electronics enthusiast. From November 26 -30 there is only one place in the universe for the electronics enthusiast to be — Breadboard '80, at the Royal Horticultural Hall in London. The majority of leading companies will be exhibiting, including all the top monthly magazines in the field. There will be demonstrations on most stands and many feature special offers that are EXCLUSIVE to Breadboard!

All aspects of this fascinating field are catered for, from CB to home computing, so whether you want to buy a soldering iron or a synthesiser — or just keep up to date with your hobby — don't miss Breadboard '80.

Royal Horticultural Halls
Elverton Street
Westminster London SW1
November 26-30 1980



Send in Advance tickets — GET ADVANCE TICKETS
Please send: tickets@ £1.00 (Student/Child/OAP)
tickets@ £1.50
I enclose P.O./Cheque for £.

26th Nov — WEDNESDAY — 10am-6pm
27th Nov — THURSDAY — 10am-8pm
28th Nov — FRIDAY — 10am-6pm
29th Nov — SATURDAY — 10am-6pm
30th Nov — SUNDAY — 10am-4pm

NEW

PRACTICAL ELECTRONICS PROJECT 125 WATT POWER AMP KIT

SPECIFICATIONS

Max. Output power 125 watt RMS
 Operating voltage (DC) 50-80 Max.
 Loads 4-16 ohms
 Frequency response Measured at 100 watts 25Hz-20kHz
 Sensitivity for 100 watts 400mV @ 47K
 Typical T.H.D. @ 50 watts 4 ohms load 0.1 %
 Dimensions 205 x 90 and 190 x 36 mm

The P. E. power amp kit is a module for high power applications—disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, the

output stage uses four 115 watt transistors normally only two would be used, result, a high powered rugged unit. The PC Board is backprinted, etched and ready to drill for ease of construction, and the aluminium chassis is performed and ready to use, supplied with all parts and circuit diagrams.




AS FEATURED IN PRACTICAL ELECTRONICS OCTOBER ISSUE

125 watt power amp kit **£9.50** plus £1.00 p&p
ACCESSORIES **£1.00** plus 20p p&p
 Suitable L.S. coupling electrolytic
 Suitable Mains Power Supply Unit **£7.50** plus £2.75 p&p
 sufficient for one power amp

DIY STEREO BARGAIN PACKS FEATURING FAMOUS BUILT MULLARD PREAMP MODULES

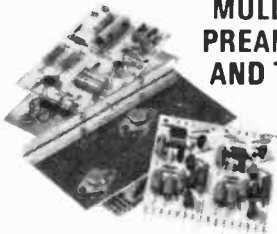
MULLARD STEREO PREAMP MODULES AND TWO 12 WATT POWER AMP KITS.



In easy to build form P.C.B.s backprinted, etched and drilled ready to use.

BUILD A 12 WATTS PER CHANNEL STEREO AMPLIFIER ACCESSORIES AND L.S. KIT EXTRA (not available separately) £6.00

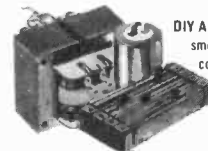DIY PACK 1 2 x power amp kits LP1182/ preamp module, suitable for ceramic and auxiliary inputs. **£6.00** plus £1.10 p&p
 DIY PACK 2 2 x power amp kits LP1184 preamp module suitable for magnetic ceramic and auxiliary inputs. **£8.50** plus £1.15 p&p
 DIY SPEAKER KIT Two 8" x 5" approx. 4 ohm bass. **£3.50** plus £1.70 p&p



DIY ACCESSORIES Mains transformer smoothing capacitor rectifier 4 x slider controls, for base, treble and volume.

£3.00 plus £1.60 p&p

ACCESSORIES: Available only at time of purchase of Bargain Packs


12 + 12 WATT AMPLIFIER KIT NOTE for use with 4 to 8 ohms speakers.

With up-to-the-minute features. To complete you just supply screws, connecting wire and solder. Features include dim input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 24 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus 2 power amplifier assembly kits and mains power supply. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs. Easy to assemble teak simulate cabinet and ready made metal work. For further information instructions are available price 50p. Free with kit. Size 9 1/4" x 8 3/4" x 4" approx.

NOTE: for use with 4 to 8 ohms speakers.

£13.95 plus £2.55 p&p

BSR chassis record deck with manual set down and return, complete with stereo ceramic cartridge **£8.50** plus £2.75 p&p when purchased with amplifier. Available separately **£10.50** plus £2.75 p&p.
8" SPEAKER KIT. 2 Philips 8" approx. speakers. **£4.75** per stereo pair plus £1.50 p&p when purchased with amplifier. Available separately **£6.75** plus £1.50 p&p.
STEREO MAGNETIC PRE-AMP CONVERSION KIT all components including P.C.B. to convert your ceramic input on the 12 + 12 amp to magnetic. **£2.00** when purchased with kit featured above. **£4.00** separately inc p&p.

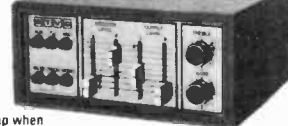

BSR Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 rpm spindle adaptor ideally suited for home or disco use.



£12.25 plus £2.75 p&p Size approx 13" x 11"

PHILLIPS RECORD PLAYER DECK GC037

Size approx 15 1/4" x 12 1/4"
 Hi Fi record player deck, 2 speed, damped cueing, auto shut-off, belt drive with floating sub chassis to minimise acoustic feedback. Complete with GP401 stereo magnetic cartridge—LIMITED STOCK. UNBEATABLE OFFER AT



£27.50 complete plus £2.75 p&p

OFFER! SAVE MONEY by purchasing 12 + 12 amp kit, BSR record deck and speaker kit together for only **£25.50** p&p £4.50.

PRACTICAL ELECTRONICS CAR RADIO KIT **£10.50** (Constructors pack 7) plus £1.75 p&p



2 WAVE BAND MW LW
 * Easy to build * 5 push button tuning
 * Modern styling design * All new unused components
 * 6 watt output * Ready etched & punched P.C.B.
 * Incorporates suppression circuits * Now with tape input socket

All the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue. Features: Pre-set tuning with five push button options, black illuminated tuning scale, with matching rotary control knobs, one, combining on/off volume and tone-control, the other for manual tuning, each set on wood simulated fascia. The P. E. Traveller has a 6 watts output, neg ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. The radio fits easily in or under dashboards. Complete with instructions.

CONSTRUCTORS PACK 7A

Suitable stainless steel fully retractable locking aerial and speaker (approx. 6" x 4") is available as a kit complete **£1.95** p&p £1.00

PACK 7A may only be purchased at the same time as Pack 7. NOTE: Constructor's pack 7A sold complete with radio kit **£15.20** including p&p.

FEATURED PROJECT IN PRACTICAL ELECTRONICS.



30 + 30 WATT STEREO AMPLIFIER BUILT AND TESTED

Viscount IV unit in teak simulate cabinet; silver finished rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape and auxiliary. Rear panel features fuse holder, OLN speaker and input socket 30 + 30 watts. RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers. Size 14 1/4" x 10" approx.

READY TO PLAY **£32.90** plus £3.30 p&p



323 EDGWARE ROAD, LONDON, W.2
 21E HIGH STREET, ACTON W3 6NG
 ACTON. Mail Order only. No callers.

ALL PRICES INCLUDE VAT AT 15 %

All items subject to availability. Price correct at 1.10.80 and subject to change without notice

For further information send for instruction booklet 20p plus stamped addressed envelope

NOTE: Persons under 16 years not served without parent's authorisation

BARGAIN OFFER!!



ARISTON PICK UP
 Ariston pick-up arm manufactured in Japan. Complete with headshell. **£11.95** plus £2.50 p&p
 Listed price over £30.00


100 WATT MONO DISCO AMPLIFIER

Brushed aluminium fascia and rotary controls. Size approx 14" x 4" x 10". Five vertical slide controls, master volume, tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level controls (PRL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak. **£76.00** plus £4.00 p&p




50 WATT MONO DISCO AMPLIFIER

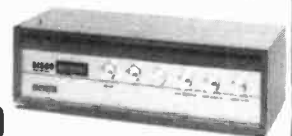Size approx 13 1/4" x 5 1/4" x 6 3/4". 50 watts rms, 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume



£30.60 plus £3.20 p&p

POLYSYNTH

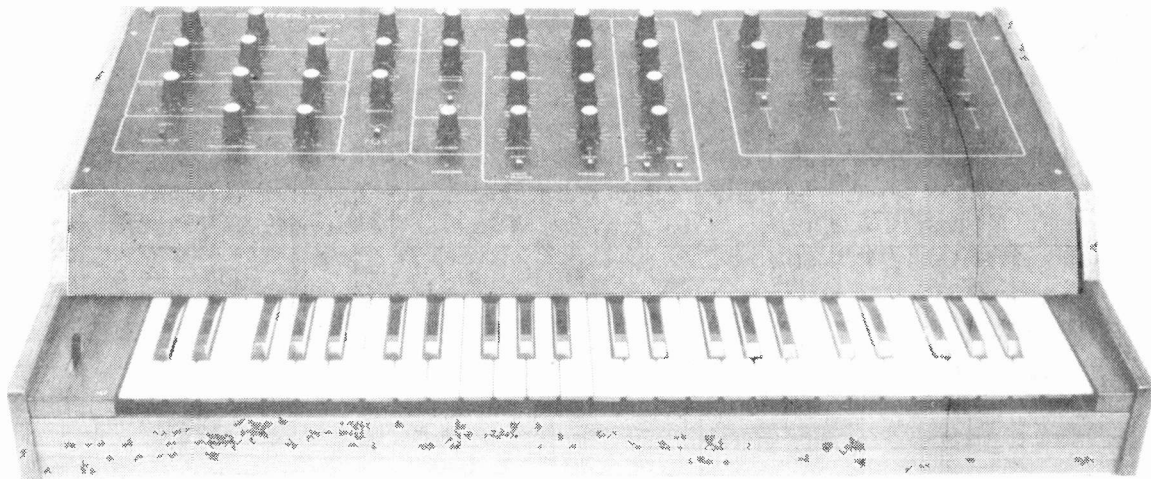

The Transcendent Polysynth is no ordinary synthesiser — it's a family of them. Each of its voices is a complete synthesiser in itself with two VCOs, two ADSRs, a VCA and a VCF in addition to all the usual synthesiser functions. Design and development by Tim Orr.

The Polysynth is a four octave polyphonic music synthesiser. The standard unit has four voices making it possible to play up to four notes simultaneously. Each voice is a complete synthesiser in itself, having two VCOs, two ADSRs, one VCA and one VCF. The voices are totally voltage controlled which enables them to be ganged up in a bus system. So when the master sustain level is adjusted, the sustain level on all voices is set to the same value. However, by providing independent pitch and gate signals, it is possible to control each voice from the keyboard and yet have a common control over the other parameters. The machine can be expanded (with an extra mother board (PS4), four voice boards (PS7) and a panel board (PS6)) to a system with eight independent voices.

The design has minimal wiring (Fig.1), most of which is made with preformed ribbon cable links. Also, the four voice boards, which require nearly 50 signals each, plug into a Molex connector bus system.

All the common controls, such as ADSR parameters, modulation oscillators, volume and noise level are located on the left hand panel board (PS5).

The right hand board (PS6) handles the individual parameters of oscillator tuning and the voice on/off control. Both the panel boards deliver their signals to the mother board (PS4) which then distributes them to the voice slots. Pitch and gate parameters are independently fed to the voices, these signals being generated by PS1, 2 and 3.



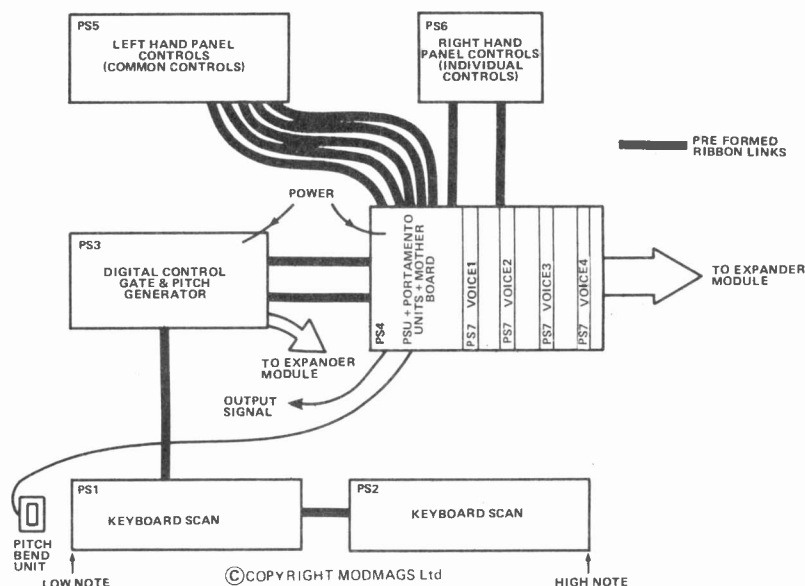
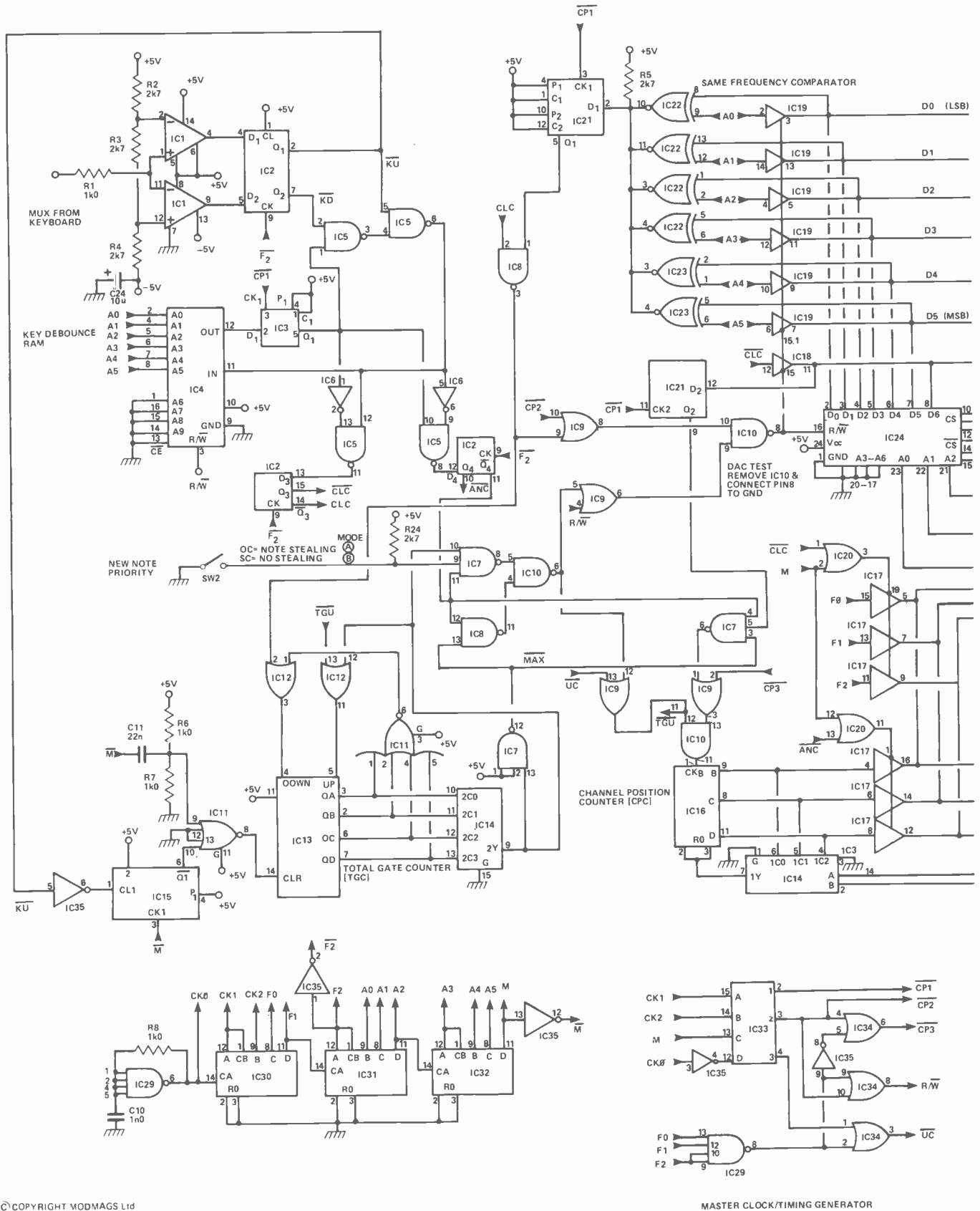



Fig.1 Board-to-board connections. The voice boards (PS7) simply plug into the mother board (PS4) using Molex connectors.

Fig.2 Circuit diagram of PS3, the digital board. In this and other diagrams there is a central overlap to make things easier to follow.

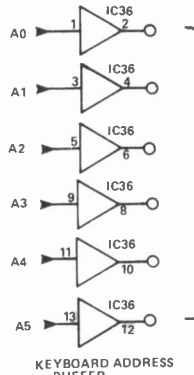

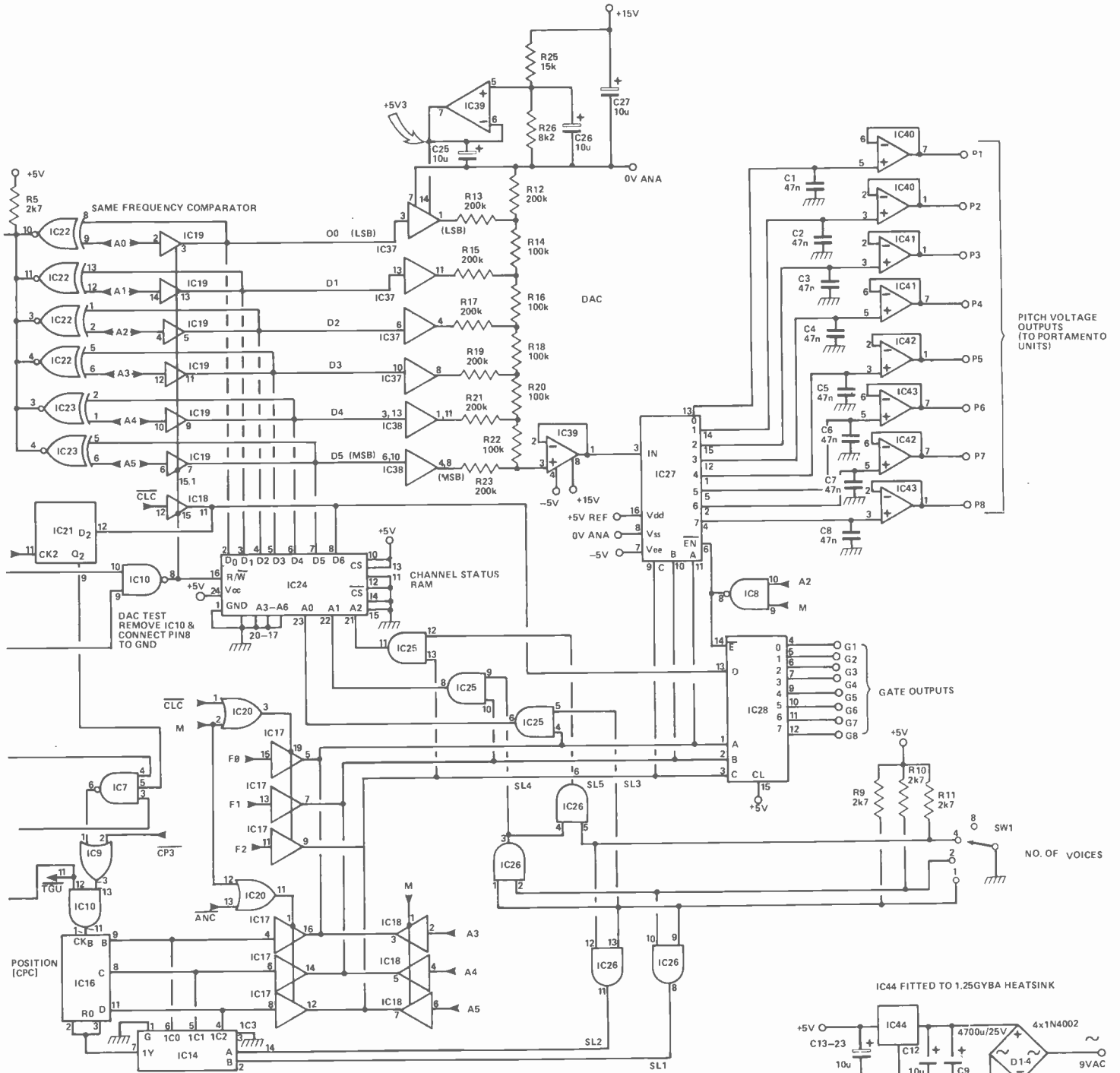

NOTE:
 IC1 IS 75107
 IC2 IS 74LS175
 IC3, 15, 21 ARE 74LS74
 IC4 IS 2102
 IC5, 8 ARE 74LS00
 IC6, 35 ARE 74LS04
 IC7 IS 74LS10
 IC9, 12, 20, 34 ARE 74LS32
 IC10, 25, 26 ARE 74LS08
 IC11 IS 7425
 IC13 IS 74LS193
 IC14 IS 74LS153
 IC16, 30, 31, 32 ARE 74LS93
 IC17 IS 74LS244
 IC18, 19 ARE 73LS367
 IC22, 23 ARE 74LS266
 IC24 IS 6810
 IC27 IS 4051B
 IC28 IS 74LS259
 IC29 IS 74LS13
 IC33 IS 74LS42
 IC36 IS 7407
 IC37, 38 ARE 4041B
 IC39 IS 1458
 IC40, 41, 42, 43* ARE TL082
 IC44 IS 7805
 D1-4 ARE 1N4002
 *IC42, 43 ONLY REQUIRED IN EIGHT-VOICE SYSTEM

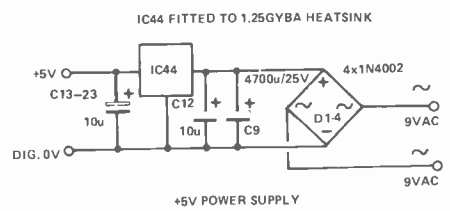

TYPICAL POWER DEMAND +5V 400mA
 -5V 20mA
 +15V 20mA

HOW IT WORKS : DIGITAL CONTROL PS1, 2, 3

The synthesiser decides which notes are being played by digitally scanning the keyboard and analysing the received data. A high frequency oscillator (Fig.2, IC29 pin 6) generates the master timing for the system, which is then divided down by a 12 stage divider (IC30,31,32). The signals generated by this section are used to construct various timing waveforms. A0 to A5 are sent to the keyboard scan circuitry, PS1,2 (Fig.4). This is a 49-way multiplexer. The six bit code can address 64 locations, but as the keyboard only has 49 notes the other 15 locations remain unused. The bottom part of the code (A0,1,2) addresses each eight bit multiplexer whilst the top three bits (A3,4,5) are decoded by IC8. The outputs of IC8 then enable each of the seven multiplexers in turn so that a complete keyboard is produced. When a note is unpressed it generates -5V and when it is between contacts it is an open circuit.

Figure 5 shows a typical keyboard scan output. The unused top 15 addresses have been arranged to generate a key unpressed signal. A power clear circuit has been included to clear the system when the machine is powered up.

The keyboard output is fed to a voltage comparator, IC1, Fig.2. In-

tegrated circuits IC1,2,3,4,5 form a circuit block that decides when to assign a new channel to a voice (ANC) or to clear an existing one (CLC). The problem of channel assignment is very complex.

The synthesiser has only four voices, so the question to be answered is 'what should happen if more than four keys are pressed at once? Should the system ignore the extra keys or should it reassign voices to the extra notes? If reassignment (referred to as note stealing) is to be used, then which notes should be taken, the first or last note played, or the highest or lowest in pitch?


There is no 'correct' solution other than a voice per note.

Two modes of operation have been provided. Mode A permits note stealing, where the oldest channels are reassigned to new notes, when the selected number of notes is exceeded on the keyboard. Mode B does not allow more than the selected number of notes to be assigned. Extra notes are ignored.

The digital electronics is best considered as consisting of a series of modules.

The 'Total Gate Counter' is used to keep count of the number of channels in use at any point in time.

Fig.3 Component overlay of the master clock/timing generator. Dots indicate through-board connections on the double-sided PCB.

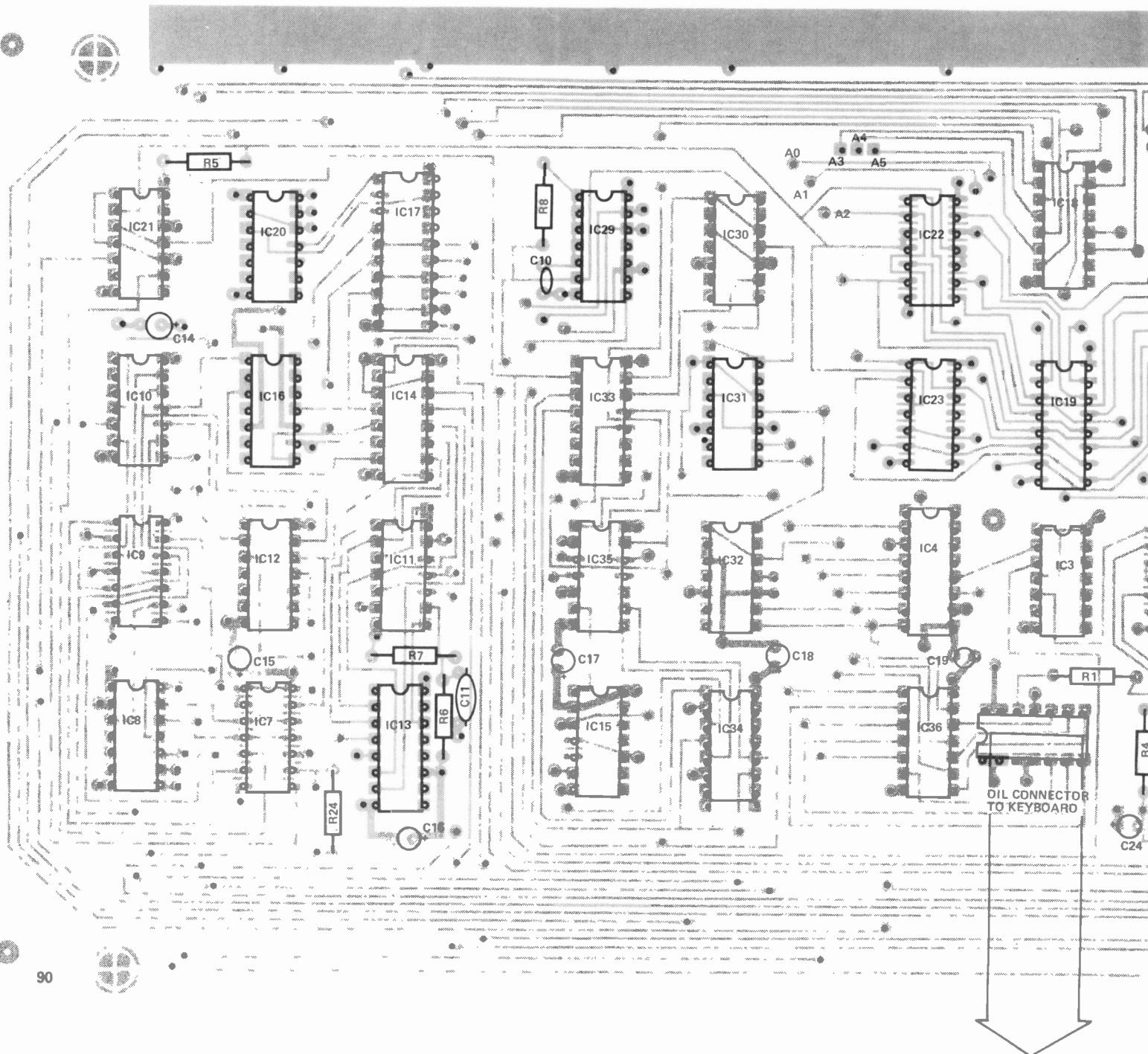

HOW IT WORKS : DIGITAL CONTROL PS1, 2, 3

The 'Channel Position Counter' decides which will be the next channel to be assigned. In mode B, if a channel is already in use, then it will skip it and continue on until it finds a free one. In mode A, the channel position counter indicates the oldest channel which will then be reassigned if no free channel is available.


The 'Channel Status RAM' stores the pitch and gate parameters, the number of parameters stored being determined by the selector switch SW1. Data bits D0 to D5 generate pitch and bit D6 is the gate signal. The 'Same Frequency Comparator' comes into operation when a note is released. When this occurs, the circuit removes the gate signal from the respective memory location but rewrites the pitch data which would otherwise be cleared!

The electronics in Fig.2 generate gate and pitch signals which are fed to the synthesiser voices. Some typical waveforms are shown in Fig.9 for a four note selection. Each note pressed generates a gate and pitch signal and assigns a voice channel. When a note is released the gate signal is lost, but the pitch value remains until the channel is reassigned. The gate signals are distributed via an eight way addressable latch, IC28. The pitch signals are distributed via an eight way multiplexer driving

eight sample and hold units (IC27,40,41,42,43). In a four voice system IC42,43 are omitted.

The pitch data is generated by a precision DAC (IC37,38,39). This converts the six bit code into an analogue voltage using an R/2R network.

A typical DAC error is shown in Fig.11. When the MSB of the code changes from 0 to 1 the step size is too small, which results in an error for all codes where the MSB is 1. Generally the worst errors are generated at the changeover point of the high bits of the code, Fig.12. The synthesiser is exceptionally sensitive to errors of this nature and so the DAC must be accurate to ten bits even though it is only converting six bits. A ten bit accuracy will give a worst error of 1 part in 32 (3% of a semitone) per step, which is only likely to occur when bits D5 and/or D4 change state. To obtain this performance 0.1% tolerance, 25 ppm/°C metal film 100k and 200k resistors are used. For superior performance the resistors can be matched for a 2 to 1 ratio using the best matched pairs at the MSB end of the DAC. Using this technique worst step errors of about 1.5% can be obtained. The DAC is powered from a +5V3 reference voltage, which results in a +1V/octave output.

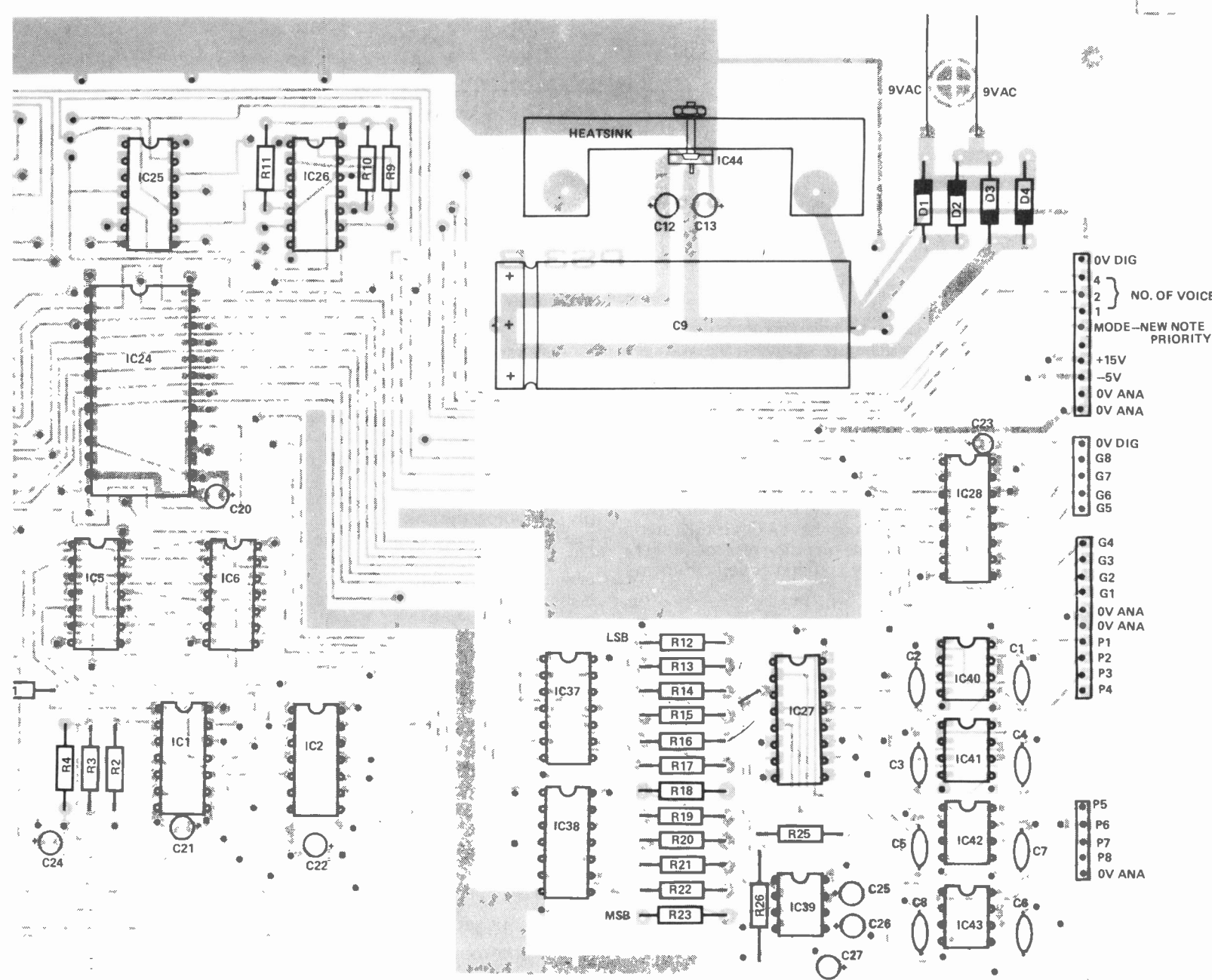

PARTS LIST : PS1, 2

Keyboard Multiplexer

Resistors all ¼ W 5%

R1,2	100k
R3	1k0
R4	5k6
R5	4k7
R6-18	2k7

Capacitors

C1-5 10u 16 V tantalum

Semiconductors

IC1-7	4051
IC8	74LS42
Q1	BC212L
D1	1N4148

Miscellaneous

PCBs PS1 and PS2, 8 off 16 pin DIL sockets, 14 pin DIL socket, 49-note keyboard, 49 keyboard contacts (single pole), full length bus bars, self-adhesive cable clamp.

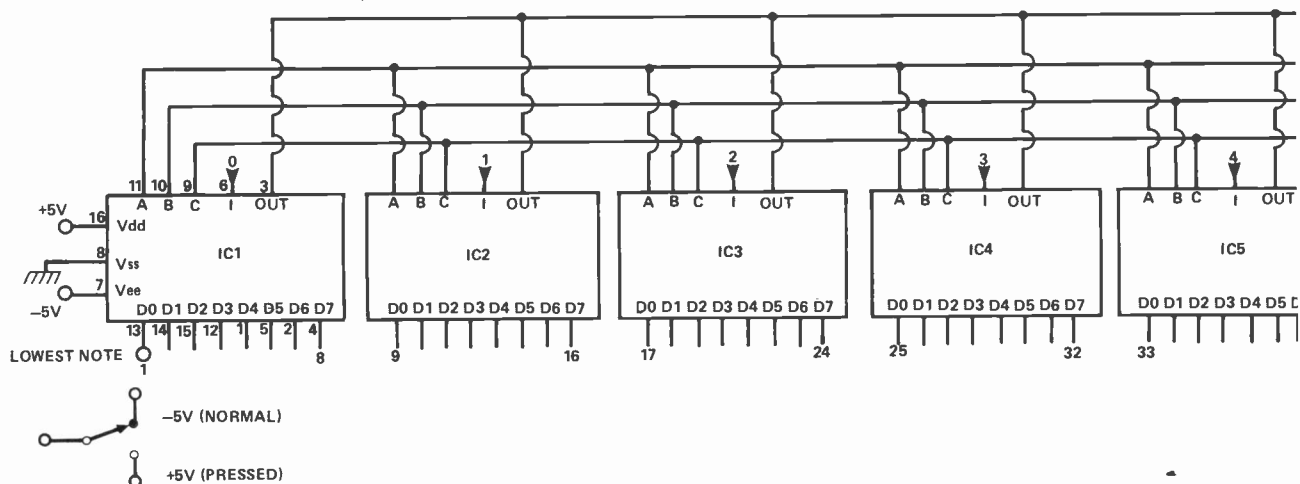


Fig.4 Circuit diagram of the keyboard multiplexer. (PS1 and PS2).

Testing the DAC

Set the number of voices to one and measure pitch voltage one. Use note C to generate octaves. The voltage should be $1\text{ V} \pm 2\%$ per octave. If possible measure the voltage for each note of the keyboard, using a $4\frac{1}{2}$ digit DMM. The semitone step change should be $83.3\text{ mV} \pm 3\%$. Repeat for pitch outputs two, three, four. If you are unable to do this you can rely upon a musical ear when driving the voice modules!

Another test is to remove IC10 and link pin locations 7 and 8 with a piece of wire. The DAC (IC39, pin 1) will then draw out a full range ramp (64 steps) which must have NO VISIBLE step errors. Be careful when inserting the precision resistors. Don't bend them too close to their body and don't overheat them when soldering them in.

Keyboard Construction

Bend the end wire on the contact blocks as shown in Fig.13. Thread the 49 contact blocks onto the two bus bars, making certain that the contact wire is between the two bars. Use a clean cloth for handling them to avoid grease contamination.

Glue the blocks into position on PS1 and 2 and then solder the bent wire ends into position. When the assembly is mounted on the keyboard adjust each wire contact so that there is a 1 mm clearance between it and the plunger.

The Mother Board

The mother board distributes the common and independent synthesiser parameters from the panel boards to the individual voices, which plug into the 50-way voice slots. It also

houses the power supply, LED drivers, portamento circuits and output volume control.

Power Supply


The power supply produces $\pm 15\text{ V}$ and -5 V . The positive rail is generated by a precision voltage regulator (IC1, Q4, Fig.7) which is mirrored by IC2, Q2, Q3 to produce the negative rail. The positive rail should be set to $+15\text{ V}$ ($\pm 10\text{ mV}$) by adjusting PR1, with no voices plugged in. Check that the negative rail is $-15\text{ V} \pm 75\text{ mV}$ and that the -5 V rail is $-5\text{ V} \pm 200\text{ mV}$. Now plug in the voices and recheck the supply rails. Allow the unit to 'burn in' for 24 hours and then readjust the positive rail to $+15\text{ V}$ if necessary. Lock PR1 into position with a small blob of nail varnish. All the oscillator frequencies and pitch spreads depend on the power supply being stable and so if PR1 is altered then the tuning of the whole machine will be lost!

LED Drivers

The LED drivers (IC4, IC5 Fig.8) buffer the TTL gate signals from PS3 to the voice LEDs on PS6. These LEDs can be used to test the digital control section. Set the 'Nos. of voices switch' to four. A new LED will come on, in sequence, as notes on the keyboard are held down. The LEDs will go off when the respective notes are released. Repeatedly tap a single note. This will cause an illuminated LED to cycle around the four voices. If you tap two or three notes, then two or three LEDs respectively will cycle around. Now switch to two voices.

Voices 1 and 3 turn on and off together and so do voices 2 and 4.

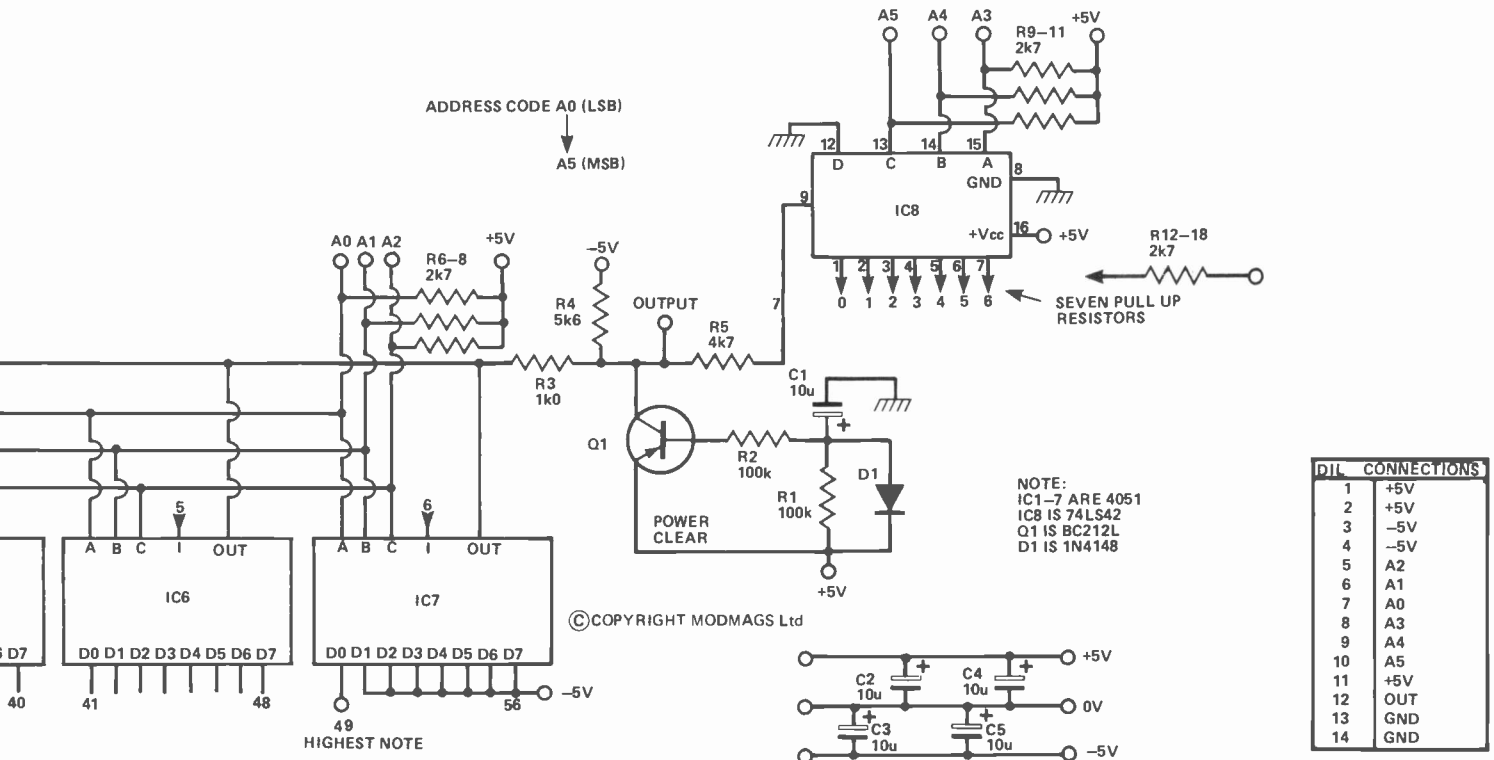Switch to one voice. Now all the LEDs will act in unison. Next switch to eight voices and repeatedly tap a note. The four



PARTS LIST : PS3

Resistors all 1/4 W 5% unless otherwise stated

R1,6,7,8	1k0
R2,3,4,5,9,10,11,24	2k7
R12,13,15,17,19,21,23	200k 0.1% metal film
R14,16,18,20,22	100k 0.1% metal film
R25	15k 1% metal film
R26	8k2 1% metal film

Capacitors

C1-8	47n polycarbonate
C9	4700u 25 V electrolytic
C10	1n0 ceramic
C11	22n polycarbonate
C12-27	10u 16 V tantalum

Semiconductors

IC1	75107
IC2	74LS175
IC3,15,21	74LS74
IC4	2102
IC5,8	74LS00
IC6,35	74LS04
IC7	74LS10
IC9,12,20,34	74LS32
IC10,25,26	74LS08

IC11	7425
IC13	74LS193
IC14	74LS153
IC16,30,31,32	74LS93
IC17	74LS244
IC18,19	74LS367
IC22,23	74LS266
IC24	6810
IC27	4051B
IC28	74LS259
IC29	74LS13
IC33	74LS42
IC36	7407
IC37,38	4041B
IC39	1458
IC40,41,42,43*	TL082
IC44	7805
D1-4	1N4002

*IC42,43 only required in eight-voice system

Miscellaneous

PCB PS3, 5 off 8 pin DIL sockets, 28 off 14 pin DIL sockets, 9 off 16 pin DIL sockets, 20 pin DIL socket, 24 pin DIL socket, DIL connectors and ribbon cable, Redpoint 1.25GYBA heatsink, cable clamp.

LEDs will come on in sequence and then there will be a four note gap whilst the unit addresses the other four voices that live in the expander module.

Now the mode selection. Select four voices and mode A. Play and hold down a four note chord with the left hand. Now press four notes at once with the right hand, and then release the right hand. The LEDs will go out, indicating that the right hand 'stole' the four voices and then released them, in doing so turning them off. Repeat this procedure in Mode B. The LEDs will remain on.

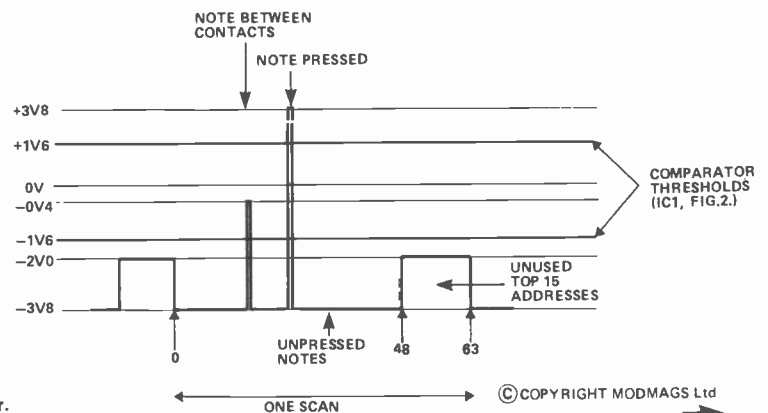


Fig.5 Output of keyboard multiplexer.

©COPYRIGHT MODMAGS Ltd



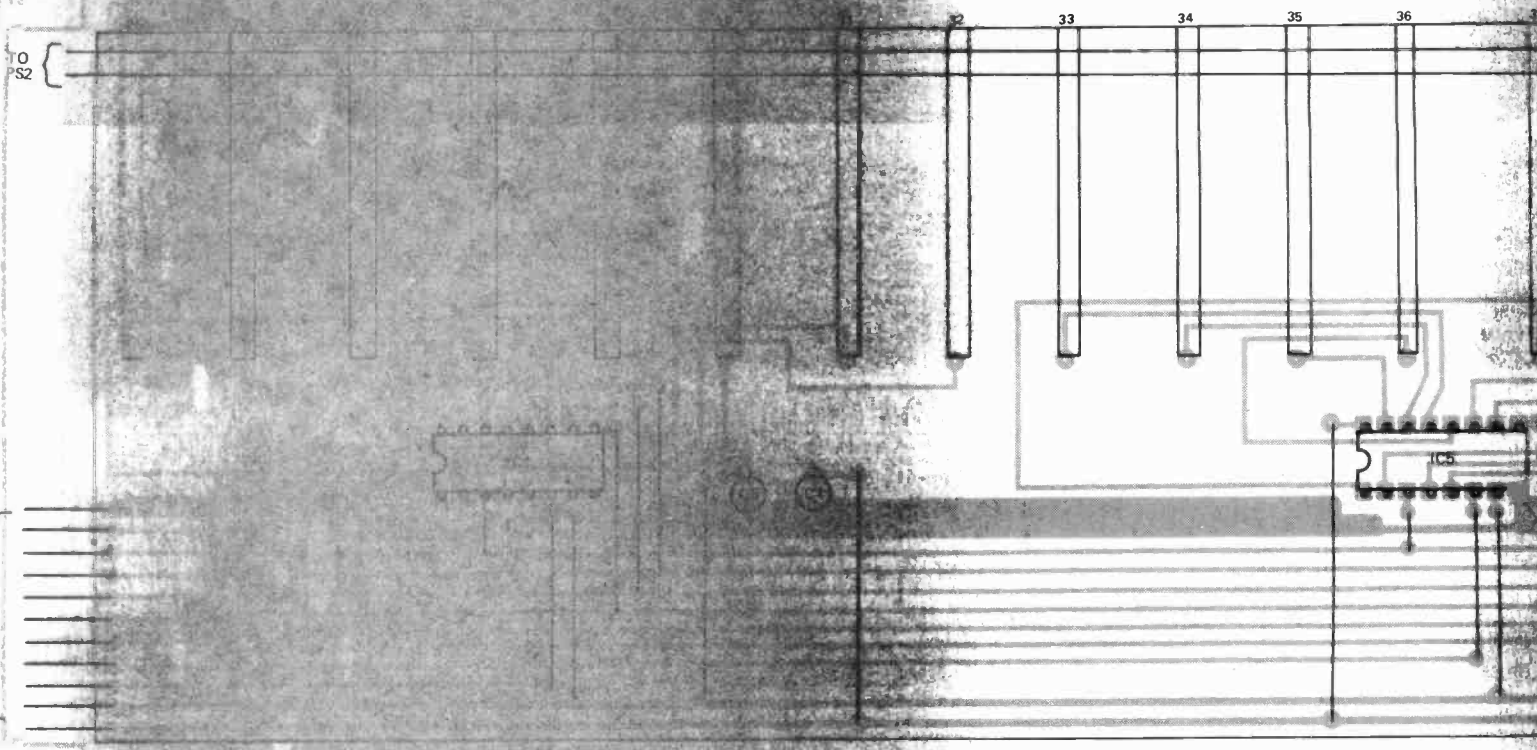
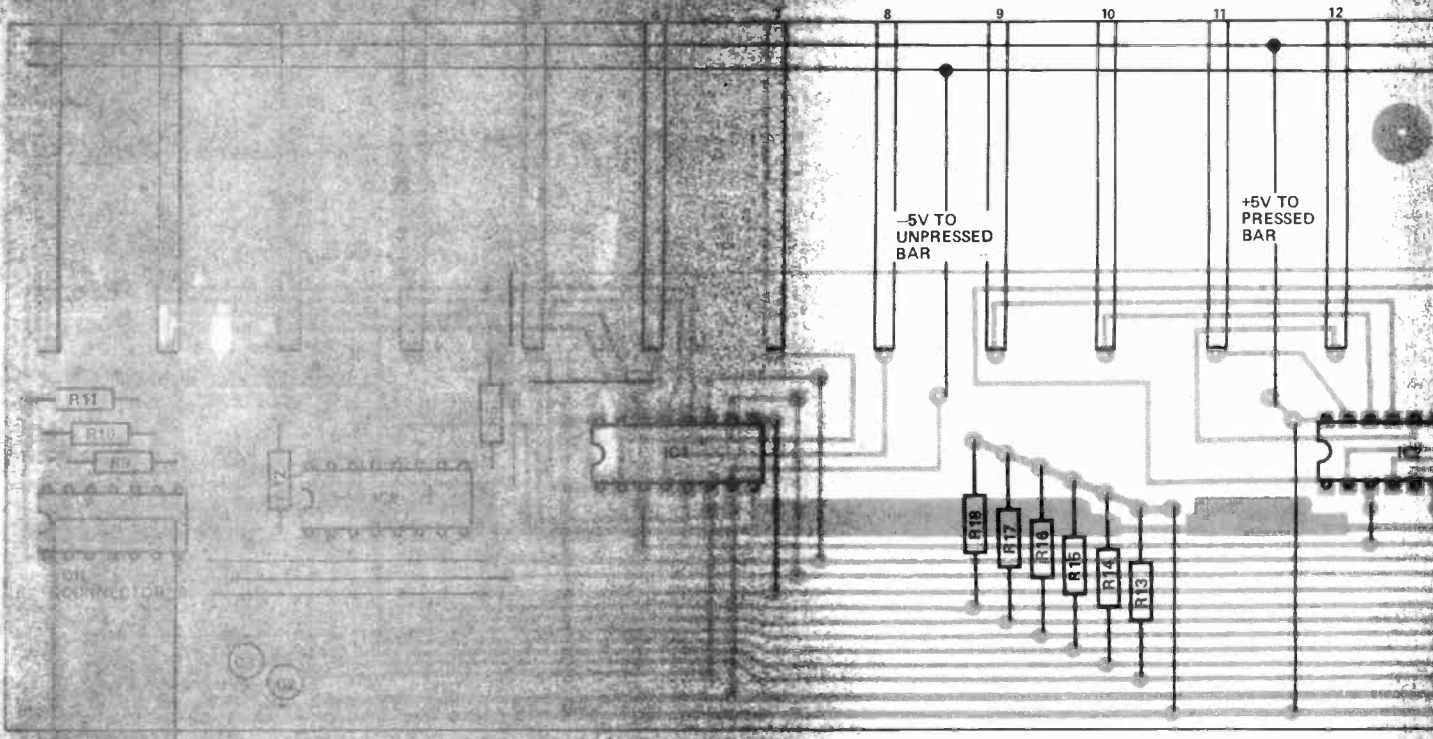


Fig 5 PS1 labels of all PS2010s together form the multi-pin PS2 keyboard

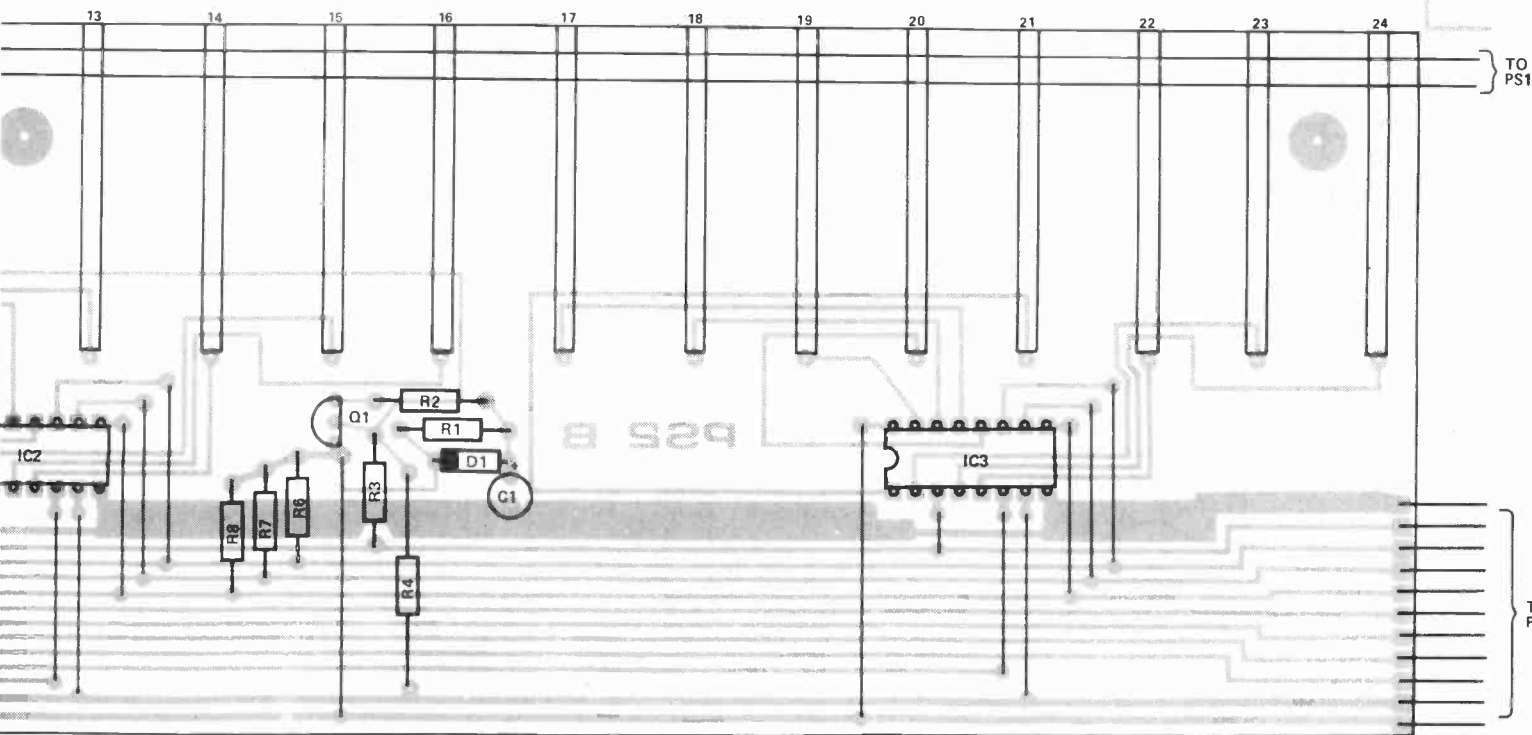

HIGHEST NOTE

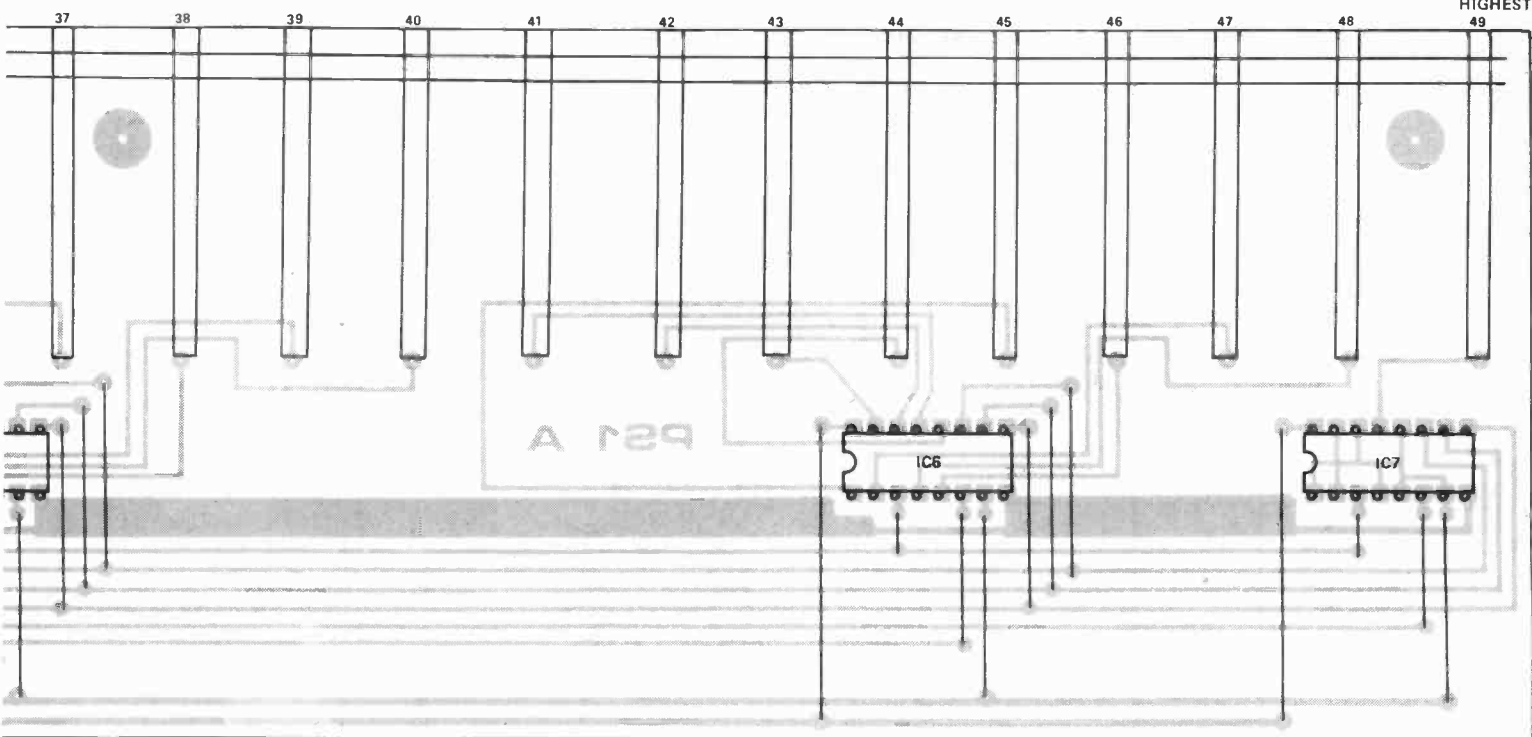

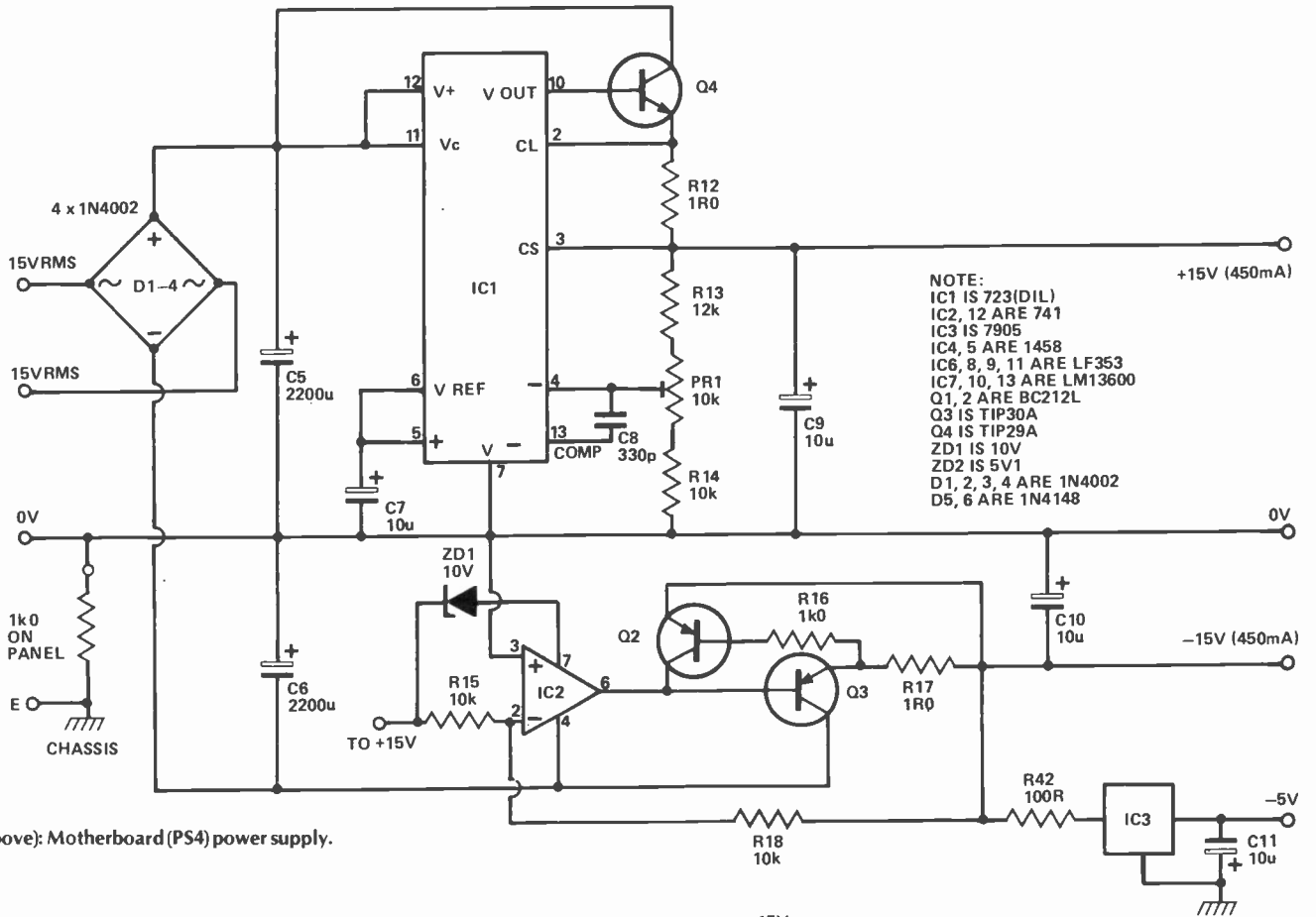


Fig.7 (above): Motherboard (PS4) power supply.



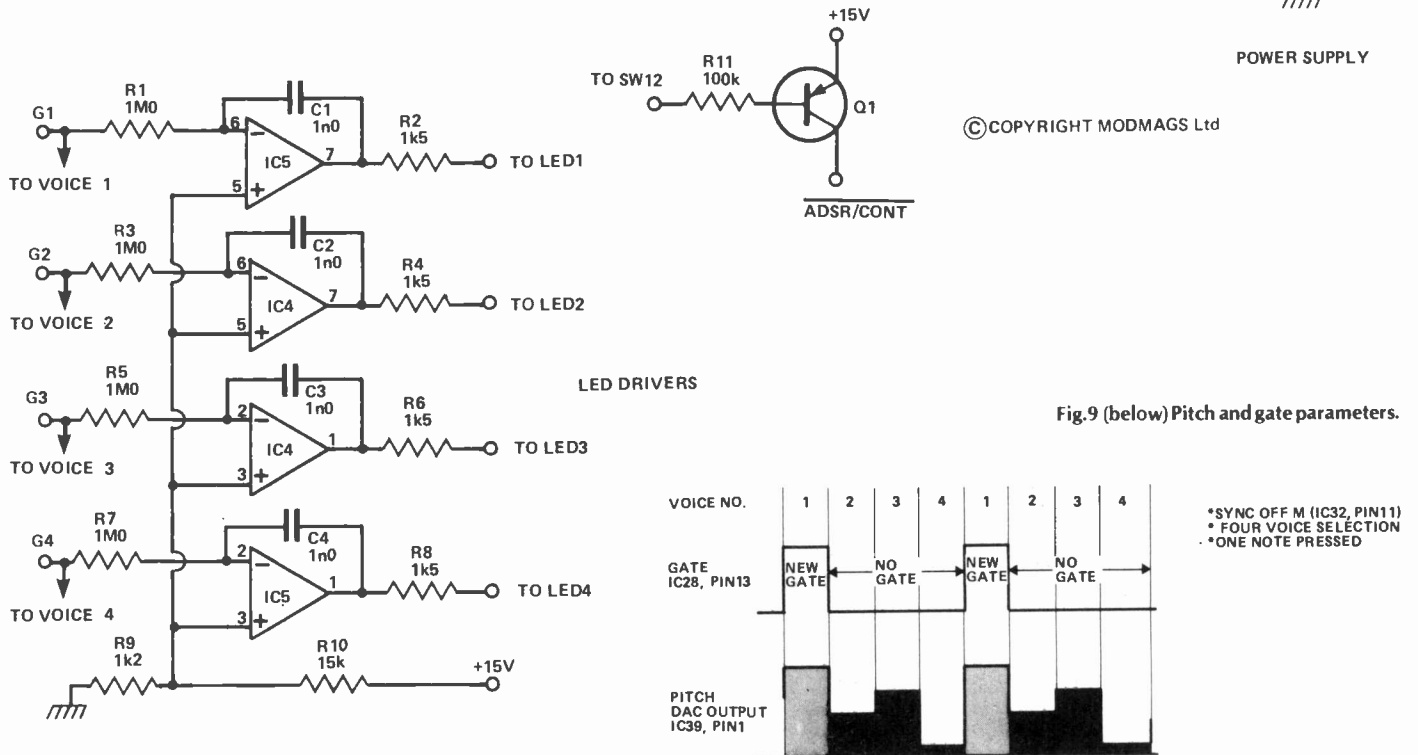


Fig.8 Motherboard LED drivers.

Fig.9 (below) Pitch and gate parameters.

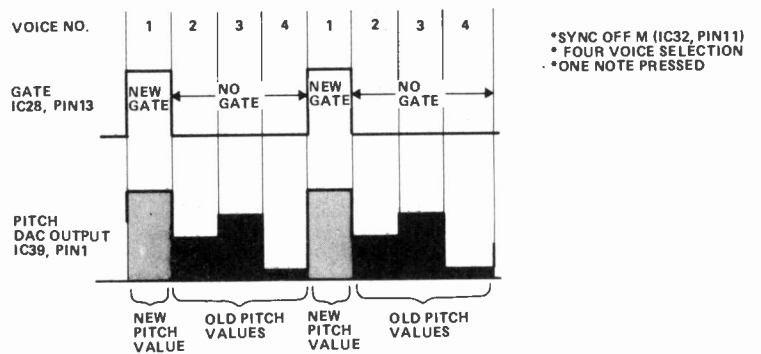


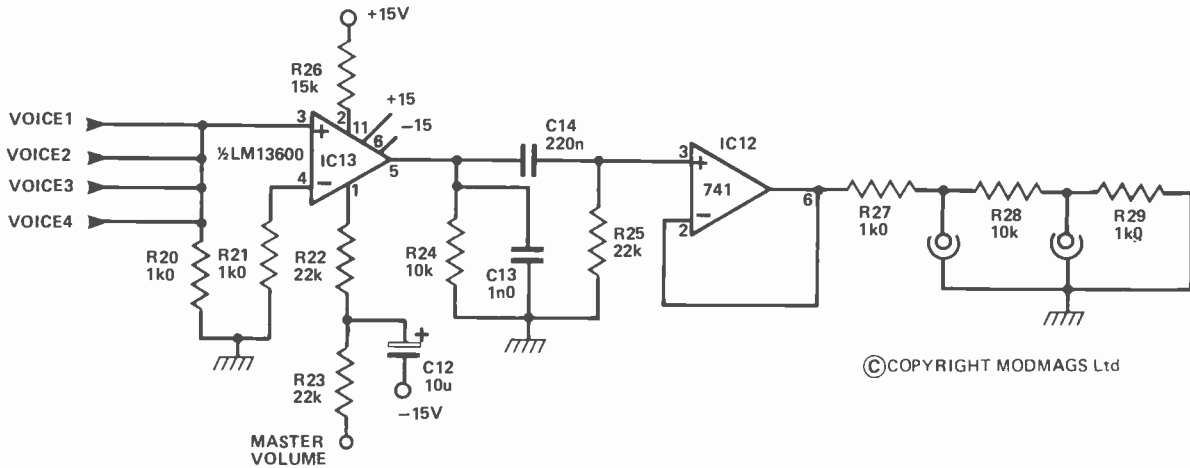

©COPYRIGHT MODMAGS Ltd

PORTAMENTO

	RA	RB	RC	CA	CB
1	R30	R31	R32	C15	C16
2	R33	R34	R35	C17	C18
3	R36	R37	R38	C19	C20
4	R39	R40	R41	C21	C22

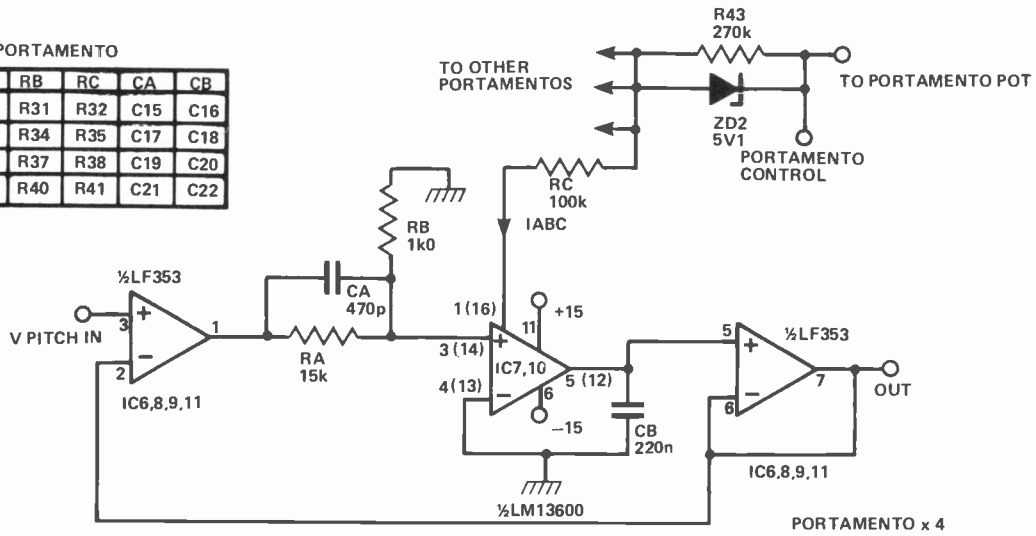

PORTAMENTO x 4

Fig.10 Motherboard portamento, master volume and pitch bend controls.

BUYLINES

Powertran Electronics can supply a complete kit of parts for each option of the Transcendent Polysynth.

- 1 voice £320
- 2 voices £368
- 4 voices £464
- 4 voice expansion kit £275

All prices are exclusive of VAT. Powertran Electronics, Portway Industrial Estate, Andover, Hants SP10 3NM.

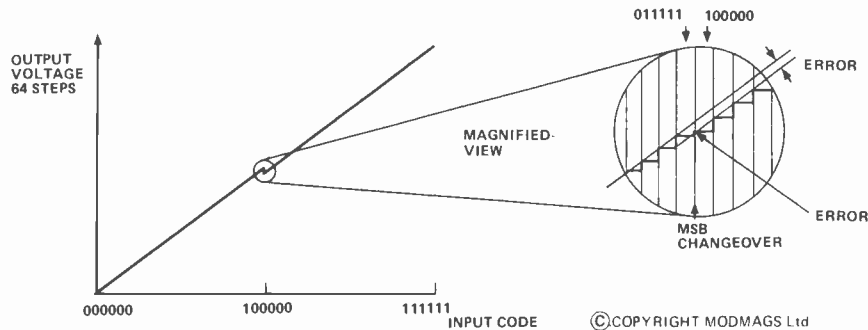
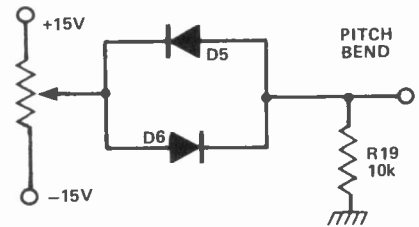


Fig.11 (left) Typical DAC error.

©COPYRIGHT MODMAGS Ltd


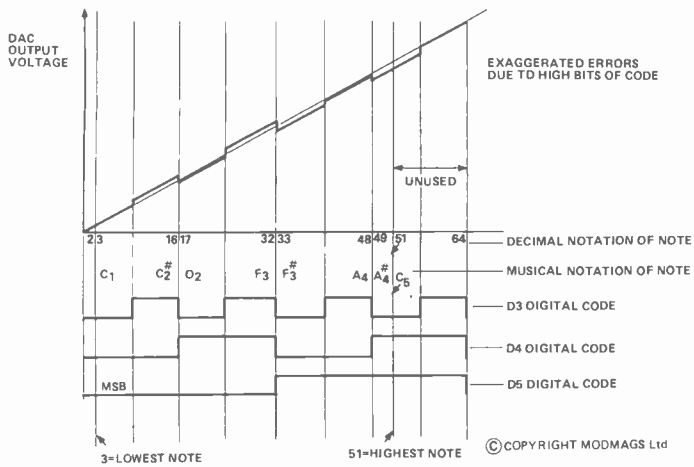


Fig.12 Points of worst error in the DAC

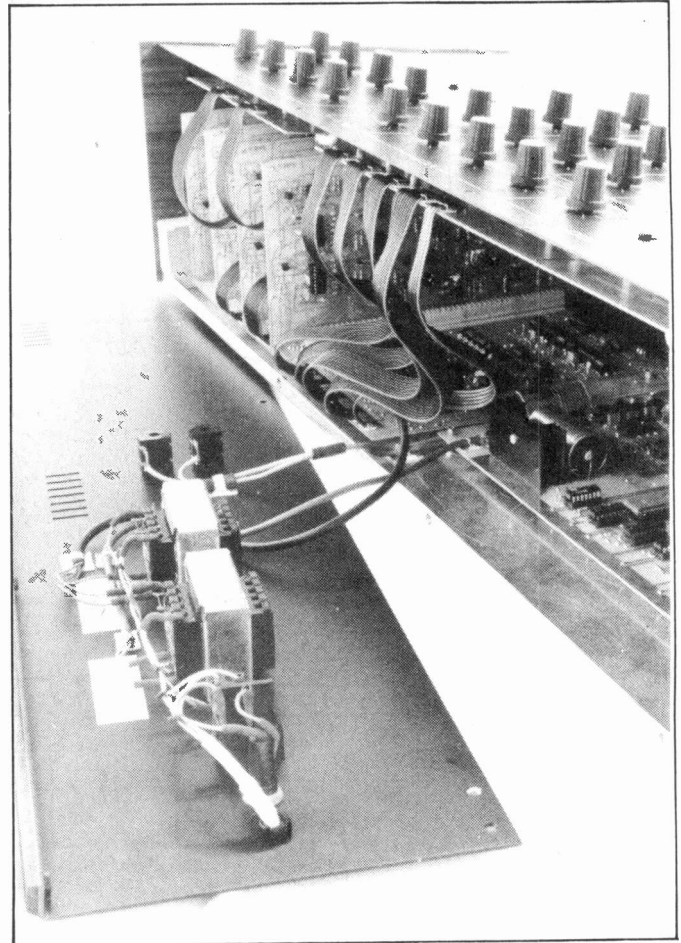

The power supply is mounted on the rear panel.

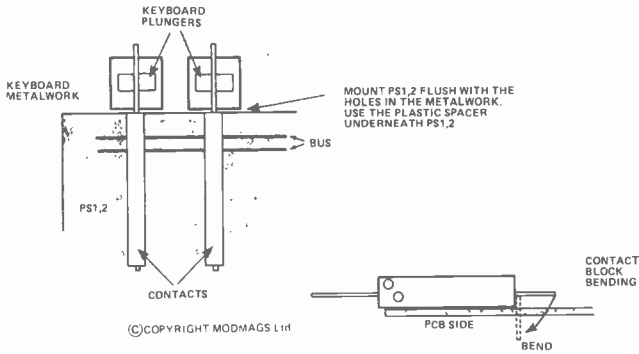


Fig.13 Mechanical assembly of keyboard plungers.

ADJUST FOR 1mm CLEARANCE WITH KEY NOT PRESSED USING LONG NOSED PLIERS.


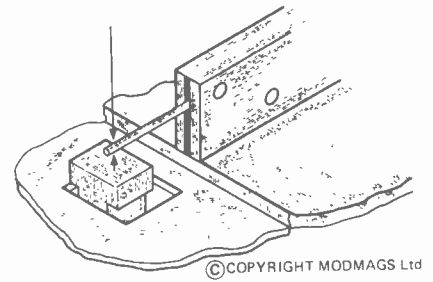


Fig.14 Adjustment of 1mm gap above keyboard plunger.

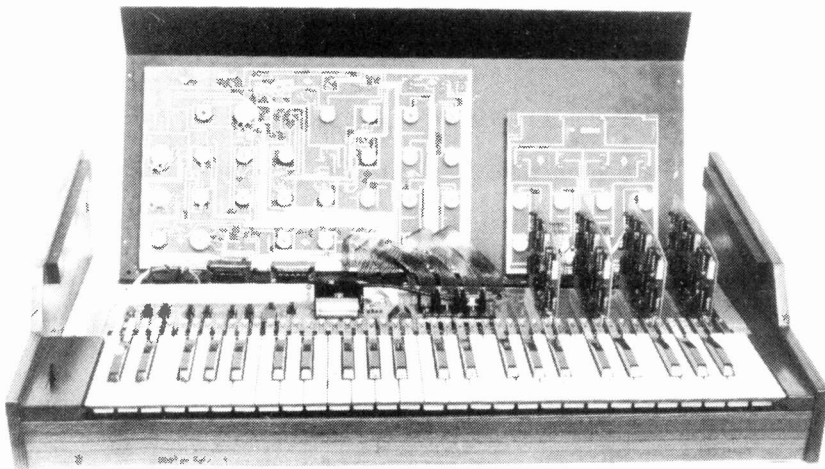

The top panel can be raised to show control board PS5 and PS6.

Next month we conclude the Polysynth project with details of the control and voice boards. (PS5, 6 and 7).

CAMBRIDGE LEARNING

SELF-INSTRUCTION COURSES

It's faster and more thorough than classroom learning: you pace yourself and answer questions on each new aspect as you go. This gives rare satisfaction - you know that you are really learning and without mindless drudgery. With a good self-instruction course you become your own best teacher.

Understand Digital Electronics

In the years ahead digital electronics will play an increasing part in your life. Calculators and digital watches mushroomed in the 1970's - soon we will have digital car instrumentation, cash cards, TV messages from friends and electronic mail. After completing these books you will have broadened your career prospects and increased your knowledge of the fast-changing world around you.

DIGITAL COMPUTER LOGIC AND ELECTRONICS £7.00

This course is designed as an introduction to digital electronics and is written at a pace that suits the new beginner. No mathematical knowledge is assumed other than the use of simple arithmetic and decimals, and no electronic knowledge is expected at all. The course moves painstakingly through all the basic concepts of digital electronics in a simple and concise fashion; questions and answers on every page make sure that the points are understood.

Everyone can learn from it - students, engineers, hobbyists, housewives, scientists. Its four volumes consist of:

- Book 1** Binary, octal and decimal number systems; conversion between number systems; conversion of fractions; octal-decimal conversion tables.
- Book 2** AND, OR gates; inverters; NOR and NAND gates; truth tables; introduction to Boolean algebra.
- Book 3** Positive ECL; De Morgan's Laws; designing logic circuits using NOR gates; dual-input gates.
- Book 4** Introduction to pulse driven circuits; R-S and J-K flip flops; binary counters; shift registers; half-adders.

DESIGN OF DIGITAL SYSTEMS £12.50

This course takes the reader to real proficiency. Written in a similar question and answer style to Digital Computer Logic and Electronics, this course moves at a much faster pace and goes into the subject in greater depth. Ideally suited for scientists or engineers wanting to know more about digital electronics, its six volumes lead step by step through number systems and Boolean algebra to memories, counters and arithmetic circuits and finally to an understanding of calculator and computer design.

- Book 1** Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; octal-binary systems; binary multiplication and division.
- Book 2** OR and AND functions; logic gates; NOR, exclusive OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgan's Laws; canonical forms; logic conventions; karnaugh mapping; three state and wired logic.
- Book 3** Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.
- Book 4** Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).
- Book 5** Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address, decoding; instruction sets; instruction decoding; control programme structure.
- Book 6** Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.

Flow Charts and Algorithms

are the essential logical procedures used in all computer programming and mastering them is the key to success here as well as being a priceless tool in all administrative areas - presenting safety regulations, government legislation, office procedures etc.

THE ALGORITHM WRITER'S GUIDE £4.00

explains how to define questions, put them in the best order and draw the flow chart, with numerous examples.

GUARANTEE No risk to you.


If you are not completely satisfied, your money will be refunded upon return of the books in good condition.

CAMBRIDGE LEARNING LIMITED, UNIT 17, RIVERMILL SITE, FREEPOST, ST. IVES, HUNTINGDON, CAMBS., PE17 4BR, ENGLAND. TELEPHONE: ST. IVES (0480) 67446

All prices include worldwide postage (airmail is extra) - please ask for prepayment invoice). Please allow 28 days for delivery in U.K.

Microcomputers are coming - ride the wave! Learn to program.

Millions of jobs are threatened but millions more will be created. Learn BASIC - the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flowcharting, coding the program, debugging, clear documentation. Harder problems are provided with a series of hints so you never sit glassy-eyed with your mind a blank. You soon learn to tackle really tough tasks such as programs for graphs, cost estimates, compound interest and computer games.

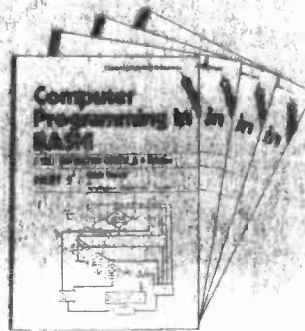

COMPUTER PROGRAMMING IN BASIC £9.00

- Book 1** Computers and what they do well; READ, DATA, PRINT, powers, brackets, variable names; LET, errors; coding simple programs.
- Book 2** High and low level languages; flowcharting; functions; REM and documentation; INPUT, IF... THEN, GO TO; limitations of computers; problem definition.
- Book 3** Compilers and interpreters; loops, FOR... NEXT, RESTORE; debugging; arrays; bubble sorting; TAB.
- Book 4** Advanced BASIC; subroutines; string variables; files; complex programming; examples; glossary.

THE BASIC HANDBOOK £11.50

This best-selling American title usefully supplements our BASIC course with an alphabetical guide to the many variations that occur in BASIC terminology. The dozens of BASIC 'dialects' in use today mean programmers often need to translate instructions so that they can be RUN on their system. The BASIC Handbook is clear, easy to use and should save hours of your time and computer time. A must for all users of BASIC throughout the world.

A.N.S. COBOL £5.90

The indispensable guide to the world's No. 1 business language. After 25 hours with this course, one beginner took a consulting job, documenting oil company programs and did invaluable work from the first day. Need we say more?

ORDER FORM

Please send me the following books:-

- Digital Computer Logic & Electronics @ £7.00
- Design of Digital Systems @ £12.50
- Algorithm Writer's Guide @ £4.00
- Computer Programming in BASIC @ £9.00
- BASIC Handbook @ £11.50
- A.N.S. COBOL @ £5.90
- Your Booklist (Free)

I enclose a *cheque/PO payable to Cambridge Learning Ltd. for £..... (*delete where applicable)

Please charge my:

* Access/American Express/Bardlaycard/Diners Club/Eurocard/VISA/Mastercharge/Trustcard

Credit Card No.

Signature
Telephone orders from credit card holders accepted on 0480 67446 (AnsaFone).


Overseas customers (incl. Eire) should send a bank draft in sterling drawn on a London bank, or quote credit card number.

Name

Address

Cambridge Learning Limited, Unit 17, Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs PE17 4BR, England (Registered in England, No. 1328762)

3 CHANNEL SOUND/LIGHT CHASER
LB31000SLC **£29.90**



A high performance sound to light system which automatically switches to a chase when the music ceases. Super sensitive with an anti interference circuit, the unit will operate from practically any amp and control up to 1,000W/channel, 5Hz to 70K. Controls: bass/mid/treble/master sensitivity/chase speed.

STEREO DISCO MIXER/PREAMP
LBPA3
M - Magnetic
C - Ceramic **£30.70**



Magnetic or ceramic deck versions - please state
NEW ADVANCED MODEL AVAILABLE
All the requirements of a stereo disco preamp on one board, left and right deck mixers/tones controls/mic. mixer/tones/mic. auto fade over decks and P.F.L. The unit can be used with either LB100/150/250 CBOA3P5 Regulated supply **£10.50**.
Full set of pots - **£8.63** Sliders - **£11.21**


3 CHANNEL SOUND/LIGHT
LB31000SL **£21.40**



All the advantages of the SLC without chase. Controls: bass/mid/treble/master sensitivity.

LPBA2 **£17.20** LBPA1 **£19.50**
A four channel mixer and tone stage for mics, guitars, etc. Can be used with any LB amps. Set of pots **£2.74**, sliders **£5.23**.
A stereo hi-fi preamp and tone stage for mag. p.u./tape/tuner, etc. Set of pots **£3.27**, sliders **£4.49**.

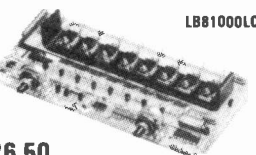2/4/8 CHANNEL CHASER
LB81000LC **£26.50**




All logic chaser system for use with up to 8 channels at 1,000 watts each. Facilities include footswitch trigger and module cascading (16, 24, 32 channel, etc.), chase speed and re-cycle delay.

3-WAY ACTIVE CROSSOVER
LBACO1 **£17.90**



Bass/mid/treble active crossover with stage booster! Available with crossover points of 200 or 300Hz, and 2K or 3KHz (please specify) LBPSU1 supply for LBACO1.

4 CHANNEL SEQUENCER
LB41000LS **£17.50**



A 4 channel sequence generator for banks of lamps up to 1,000W per channel. Two speed controls, cross effect to provide settings between seconds and rapid burst.


POWER AMPLIFIERS
Tough dealing power amps for use in sound systems. Open/short circuit protection and fused. Heavy gauge heatsinks and rugged a/p devices fall operate down to 4 ohms.

25W R.M.S.	100W R.M.S.	150W R.M.S.	250W R.M.S.
20Hz to 60K 0.07% THD 3608 S/N LB25	5Hz to 25K 0.1% THD 11008 S/N LB100	5Hz to 25K 0.1% THD 11008 S/N LB150	5Hz to 25K 0.1% THD 11008 S/N LB250
£11.20	£18.20	£26.50	£39.50

Note all models are available with either 500mA or 775mA sensitivity. Please state when ordering.

POWER SUPPLIES
LB25PS **£11.20** P/P £1.20
LB100PS **£14.70** P/P £1.40
LB150PS **£18.00** P/P £1.40
LB250PS **£24.50** P/P £1.70

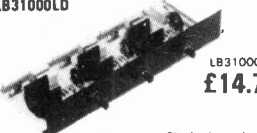1 AND 3 CHANNEL DIMMERS
LB31000LD **£14.70**



Single channel version LB11000LD **£6.70**
Power dimmer units for theatre/stage applications up to 1,000W per channel, with on board suppressing. The unit is also available without rotary pots for use with sliders - LB31000LD (no pots) **£13.50**; Sliders **75p** each.

LBRLD1 **£5.70**
A de-thump unit for use with any LB power amps.

ROPE LIGHTS/DRIVER
LB41000LC-S **£22.70**



24 feet ropes Red/Yellow Blue/Green
ROPE LIGHTS £41.40
A four channel chaser up to 1,000W per channel, with a sound trigger facility. The music input signal modulates the speed of the chase giving an excellent sound/light effect. The unit will control up to 10 ropes with chase speed and trigger level control.

PIEZO HORNS **£5.75** P/P 50p



CELESTION LOUSPEAKERS (8 ohms)
G12-46 (12 inch 65W) **£20.70** P/P £1.70
G12-100 (12 inch 100W) **£26.45** P/P £1.70
G12-126 (12 inch 125W) **£46.00** P/P £2.00

L & B ELECTRONIC MODULES
PROFESSIONAL ENGINEERING BY PROFESSIONALS
45 Wortley Road, West Croydon, Surrey
CRO 3EB. Tel. 01-689 4138

NEW - MINI MODULES - NEW
Ingenuously designed mini pre-amplifier building blocks for use in music and P.A. applications. You choose the type and number of units you require for your particular system and mount each module via its control direct onto your panel.
LBMM1 Pre-amp for mics, guitars etc
LBMM2 Mixer for up to 6 LBMM1/2/3/4/5
LBMM3 Bass/boost/cut for either LBMM1/2/3/4/5
LBMM4 Mid-boost/cut for either LBMM1/2/3/4/5
LBMM5 Treble boost/cut for either LBMM1/2/3/4/5
LBPSU1 ± 15V supply for up to 8 modules
LBPSU ± 15V regulated for up to 50 modules
MM1 £4.60; MM2 £5.20; MM3 £5.70; MM4 £5.70; MM5 £5.70; PSU1 £6.20; RPSU £14.60.
Mini Module Discount. Any types between 10 and 24 (quantity) - 20%; 25+ - 30%
Mini Module Discount. Any types between 10 and 24 (quantity) - 20%; 25+ - 30%
Each module is manufactured from the highest quality components, fully tested, supplied with a connection and circuit diagram and guaranteed for twelve months.
All prices shown are VAT inclusive. Please include 50p post/packing except where individually stated. To mail order send cheque/P.O./registered cash/Barclaycard or Access number. C.O.D. service £1 extra. For the new Autumn catalogue send 50p (Full spec shown)

Happy Memories

4116 200ns	£3.45	2114 200ns	£3.45
2114 450ns	£2.95	2716 5 volt	£7.95
2708 450ns	£4.75		

MEMOREX SOFT-SECTORED MINI-DISCS for PET, TRS-80, etc. Supplied in **Free Library Case**
£19.95 per 10

Low Profile I.C. Sockets by Texas
Pins 8 14 16 18 20 22 24 28 40
Pence 10 11 12 16 17 20 21 28 37

Memory Upgrade Kits for Apple, 2020, TRS-80, etc. **from £30** please phone

Quantity prices available on request. Government and Educational Orders welcome. Trade accounts opened.

ALL PRICES INCLUDE V.A.T. POSTAGE FREE ON ORDERS OVER £10, OTHERWISE ADD 30p.


Access and Barclaycard Welcome

HAPPY MEMORIES
Dept. ETI
Gladestry, Kington
Herefordshire HR5 3NY
Telephone (054422) 618

enter the computer age video genie system

- 12K MICROSOFT BASIC
- 16K RAM, UHF MODULATOR
- INTERNAL CASSETTE
- SECOND CASSETTE INTERFACE

£330 + VAT

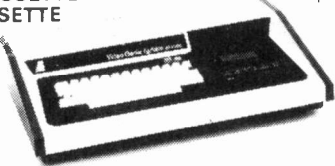

- 80 COLUMNS
- 70 LINES PER MINUTE
- GRAPHICS CHARACTERS
- INTERFACES TO MOST MACHINES

£395 + VAT



- 100's OF PROGRAMS AVAILABLE
- TRS-80 LEVEL II SOFTWARE COMPATIBLE

GENERAL NORTHERN MICROCOMPUTERS
Middles Street, Blackhall
Hartlepool, Cleveland

BARCLAYCARD ACCEPTED

27 MHz Radio Control Monitor


A radio control monitor such as that described here is invaluable when setting up a radio control transmitter. This circuit has good sensitivity and it is unnecessary to have the monitor in very close proximity to the transmitter in order to obtain a signal of adequate strength even when it is used with a low power transmitter.

The signal picked up by the telescopic aerial is coupled directly into the tuned circuit. The core of L1 is adjusted so that CV1 is able to tune the monitor to any frequency within the 27 MHz radio control band. The setting of this core is not too critical, since the unit covers somewhat more than the entire band.

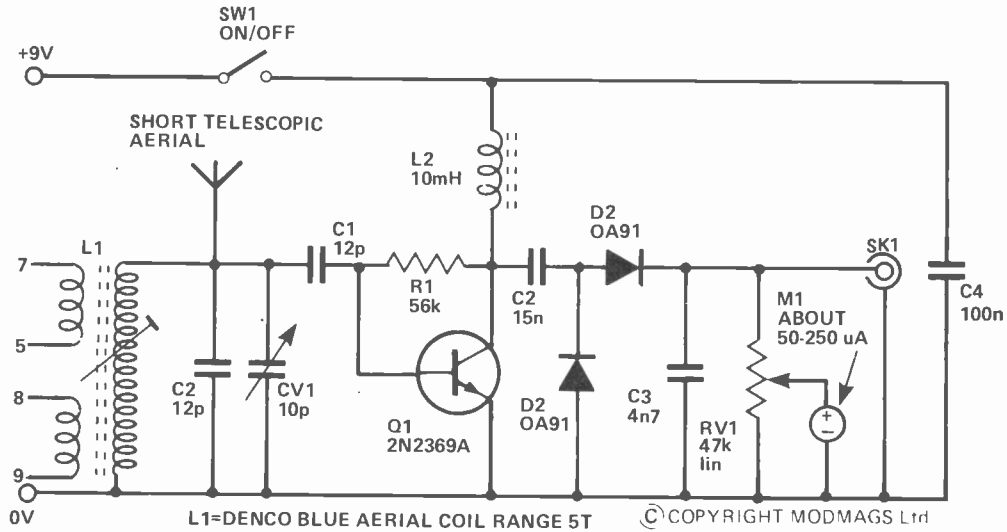Q1 is used as a common emitter amplifier with L2 as its collector load and R1 to provide base biasing. C1 couples the signal in the tuned circuit to

the input of the amplifier. The value of C1 is chosen to give optimum signal transfer. The high impedance signal in the tuned circuit is matched to the low input impedance of Q1 by a sort of capacitive divider action (the input capacitance of Q1 forming the other section of the capacitive divider).

C2 couples the output of Q1 to a straightforward rectifier and smoothing circuit. This produces a positive bias voltage which is roughly proportional to the strength of the received signal. This bias voltage is used to drive M1, which gives a comparative indication of received signal strengths. An inexpensive meter is perfectly suitable for use in the unit due to the arbitrary scaling. RV1 can be used to reduce the sensitivity of the unit, if necessary. The modulation signal of the transmitter (if it is an AM type) can be monitored using a crystal earphone connected to SK1. Current consumption is approximately 10 mA.




Target Electronics

Official orders welcomed, Govt./Educational Dept., etc.

16 Cherry Lane, Bristol BS1 3NG
Telephone: 0272 421196

nm
Nascom Microcomputers

Panel Meters

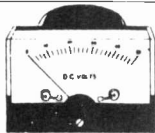

Dims:- 50 x 45 x 33mm. Require 38mm dia. cut out

cat.	F.S.D.	
MU50	0 - 50 U.A.	£3.20 + 15% VAT P&P 35p 10 plus 10% Discount
MU100	0 - 100 U.A.	
MU1	0 - 1 MA	
MUVU	"VU"	

Dims:- 60 x 47 x 33mm. Require 38mm dia. cut out

cat.	F.S.D.	
T21	0 - 50 U.A.	£3.75 + 15% VAT P&P 35p 10 plus 10% Discount
T22	0 - 100 U.A.	
T23	0 - 500 U.A.	
T24	0 - 1 MA	
T25	0 - 5 MA	
T26	0 - 10 MA	
T27	0 - 50 MA	
T28	0 - 100 MA	
T29	0 - 500 MA	
T30	0 - 1 AMP	
T31	0 - 2 AMP	
T32	0 - 25 Volts	
T33	0 - 50v AC	
T34	0 - 300v AC	
T35	"VU"	
T36	"VU"	
T40	50 - 0 - 50 U.A.	£4.75 + 15% VAT P&P 35p 10 plus 10% Discount
T41	100 - 0 - 100 U.A.	
T42	500 - 0 - 500 U.A.	
T43	0 - 30v DC	
T43	0 - 30v DC	

Dims:- 110 x 82 x 35mm. Require 58mm dia. cut out

cat.	F.S.D.	
O43	0 - 30 U.A.	£4.75 + 15% VAT P&P 35p 10 plus 10% Discount
O45	0 - 50 U.A.	
O410	0 - 100 U.A.	
O420	0 - 200 U.A.	
O450	0 - 500 U.A.	

Illuminating kit for meters. T21-T43/O43-O450.

cat.	F.S.D.	
IK2		60p + 15% VAT



Dims:- 52 x 52 x 33mm. Require 45mm dia. cut out

cat.	F.S.D.	
MS50	0 - 50 U.A.	£2.88 + 15% P&P 35 10 plus 10% Discount
MS100	0 - 100 U.A.	
MS1	0 - 1 MA	
MSVU	"VU"	


Speakers

cat.	ins	ohms	watts	
3812	1 1/2	8	0.2	75p +
4512	1 3/4	8	0.2	15%
5012	2	8	0.2	VAT
1W2	2 1/4	8	0.2	P&P 30p
3W80	2 1/2	8	0.3	10 Plus
64SS	2 1/2	64	0.3	10%
A0300	3	8	0.5	Discount

Phone in your Access or Barclaycard
Order Cat 30p Post paid



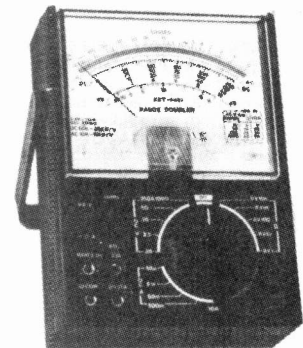MULTI-TESTER 50000 OHMS/VOLT WITH RANGE DOUBLER




DC-Volts	0-125-250 mV 0-1.25-2.5-5-10. -25-50-125-250 -500-1000 Volts
AC-Volts	0.5-10-25-50 -125-250-500 1000 Volts.
DC-Current	0-2 5-5-25-50 -250-500 mA 0-5-10A
Resistance	0-2K-20K-200K 0-2M-20MΩ
Size	H170 x W124 x D50uv.
	KRT 5001
	£14 + VAT P&P 75p



B.K. ELECTRONICS


A SOUND CHOICE

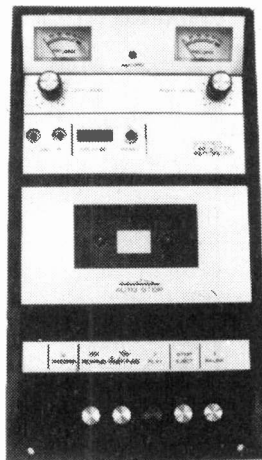★ PROMPT DELIVERY ★ PRICES INCLUDE V.A.T. ★ AMPLE STOCKS
A PERSONAL SERVICE FROM A SMALL EXPANDING COMPANY



6 piano type keys


STEREO CASSETTE TAPE DECK ASSEMBLY. Comprising of a top panel assembly and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. Brand new, ready built and tested. **Features:** Pause, control, auto stop, 3 digit tape counter, illuminated twin VU meters with individual record, level controls, secondary inputs for twin microphones. **Input Sensitivity:** 6 MV (with level control set at max). **Input Impedance:** 47 kOhms. **Output Level:** To both left and right hand channels 150 MV. **Output Impedance:** < 10k. **Signal to noise ratio:** 45 dB nominal. **Power Supply Requirements:** 12V AC at 300M/A. **Connections:** All connections to the unit are via a wander lead terminated with a nine pin plug (socket provided). **Dimensions:** Top panel — 11 1/2in x 6 1/2in. Mechanism fits through a cut out 5 3/4in x 10 1/2in. Clearance required under top panel 2 1/4in. Supplied complete with circuit diagram etc. **Price £30.50** plus £2.50 postage and packing. Suitable mains 12-volt transformer. **£3.00.**

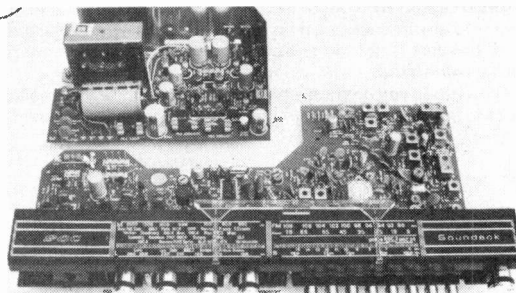

GEC AM/FM STEREO TUNER AMPLIFIER CHASSIS. Originally designed for installation into a music centre. Supplied as two separate built and tested units which are easily wired together. **Note:** Circuit diagram and interconnecting wiring diagrams supplied. **Rotary Controls:** Tuning, on/off volume, balance, treble, bass. **Push-button controls:** Mono, Tape, Disc., AFC, FM (VHF), LW, MW, SW. **Power Output:** 7 watts RMS per channel, at better than 2% THD into 8 ohms. 10 watts speech and music. **Frequency Response:** 60Hz-20kHz within ± 3dB.

Tape Sensitivity: Output — typically 150 mV. Input — 300 mV for rated output. **Disc Sensitivity:** 100mV (ceramic cartridge). **Radio:** FM (VHF), 87.5MHz — 108MHz. Long wave 145kHz — 108kHz. Medium wave. 520kHz — 1620kHz. Short wave. 5.8MHz — 16MHz. **Size:** Tuner — 2 3/4in x 15in x 7 1/2in approx. Power amplifier — 2in x 7 1/2in x 4 1/2in approx. 240V AC operation. Supplied complete with fuses, knobs and pushbuttons, and LED stereo beacon indicator. **Price £21.50** plus £2.50 postage and packing.

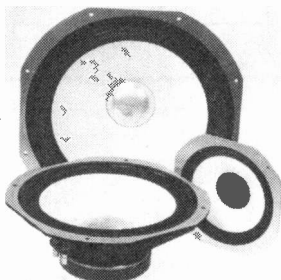NEW RANGE QUALITY POWER LOUSPEAKERS (15", 12" and 8"). These loudspeakers are ideal for both hi-fi and disco applications. Both the 12" and 15" units have heavy duty die-cast chassis and aluminium centre domes. All three units have white speaker cones and are fitted with attractive cast aluminium (ground finish) fixing escutcheons. Specification and Price.—




15" 100 watt. Impedance 8ohm 50 oz. magnet. 2" aluminium voice coil. Resonant Frequency 20Hz. Frequency Response to 2.5KHz. Sensitivity 97dB. **Price £32 each.** £2.00 Packing and Carriage each.

12" 100 watt. Impedance 8 ohm 50 oz magnet 2" aluminium voice coil Resonant Frequency 25Hz. Frequency Response to 4KHz. Sensitivity 95dB. **Price £23.70 each.** £2.00 Packing and Carriage each.


8" 50 watt. Impedance 8 ohm. 20 oz. magnet 1" aluminium voice coil. Resonant Frequency 40Hz. Frequency Response to 6KHz Sensitivity 92dB **Price £8.90 each.** £1.00 Packing and Carriage each.

PIEZO ELECTRIC TWEETERS — MOTOROLA

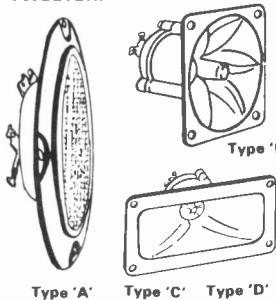Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



Type 'A' 3in round with removable wire mesh. Ideal for bookshelf hi-fi speakers. **Price (Type 'A') £3.60 each;** **Type 'B'** 3 1/2in super horn. For general purpose speakers disco and PA systems, etc. **Price £4.60 each.** **Type 'C'** 2in x 5in wide dispersion horn. For hi-fi systems and quality disco etc. **Price £6.20 each.** **Type 'D'** 2in x 6in wide dispersion horn. Frequency response extending down to mid-range (2000 c/s) suitable for hi-fi systems and quality disco. **Price £9 each.** Post and Packing, all types, 15p each (or SAE for Piezo leaflets).

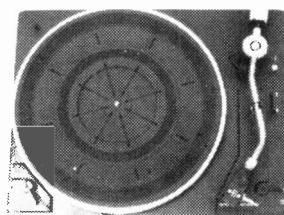

JVC TURNTABLE. JVC Turntable supplied complete with an Audio Technica AT10 stereo magnetic cartridge. ★ 'S' shaped tone arm. ★ Belt driven. ★ Full size 12in platter. ★ Precision calibrated counterbalance weight (0.3 grms.) ★ Anti-skate (bias) device. Nylon thread weight. ★ Damped cueing lever. ★ 240V AC operation. (50Hz). ★ Cut-out template supplied. Size — 12 3/4in x 15 3/4in (approx). **Price £28.50** plus £2.50 postage and packing.

DE-SOLDERING PUMP




This de-soldering pump made to a very exacting specification is ideal for the removal of small components from printed circuit boards, etc. Comes complete with spare PTFE tip. **£5.30** post free.

FIRE ALARM CENTRAL CONTROL UNIT (S.T.C.)


Ideal for Fire or Burglar Alarm Systems

- ★ Responds to normally open or closed switches (or smoke detectors etc.)
 - ★ Complete with an internal EXIDE lead acid accumulator (dry charged) as a back-up for mains failure. This is trickle charged.
 - ★ 6v-2 amp output for Fire/Burglar alarm, etc
 - ★ Re-set button for silencing Fire/Burglar alarm
 - ★ Internal buzzer which sounds if re-set button if pressed until initiating switch is cleared.
 - ★ Wall mounting, complete with red case, approx 11" x 7 1/2" x 4"
 - ★ 240v AC operation.
- Price £18.50** + £3 postage and packing.

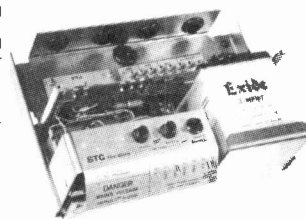

LOUDSPEAKER

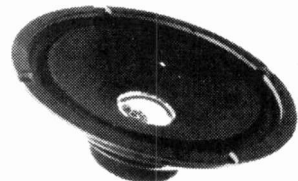High quality full range 8" loudspeaker 15 watts RMS. 80HM. Rolled surround with aluminium centre dome. **Price £3.75 each** + 75p Postage and Packing each.



B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.



1

GENTS QUARTZ LCD, 5-function. Hours, minutes, secs, month, date, backlight. **ONLY £4.95**

2

GENTS QUARTZ LCD. SAME AS 1 - Alternative style. **ONLY £4.95**

3

QUARTZ LCD Slim Chronograph, 11-function. Hours, mins, secs, 6 digit-month, date, day of week, 1/100 sec stopwatch, split and lap modes, backlight. **ONLY £7.95**



4

QUARTZ LCD ALARM. 6 digit, hours, mins, secs, day, date. 24-hour alarm with on/off indicator. **ONLY £8.95**

5

QUARTZ LCD Alarm/Chronograph. 22 functions. Hours, mins, secs, day, date, month, 1/10 sec stopwatch, split and lap modes, 12 and 24 hour modes, 24 hour alarm. **ONLY £12.95**

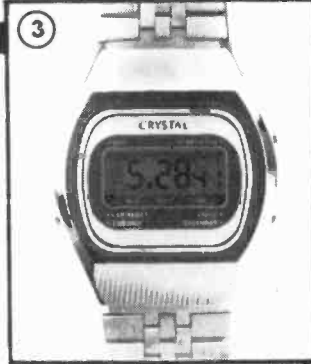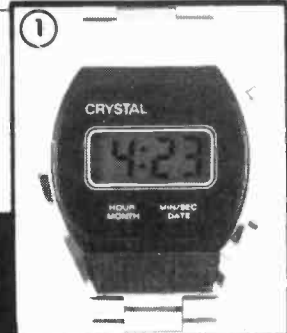We don't believe you can find better value combined with quality, than these - our special introductory prices. Compare the savings we offer and order now.




6

QUARTZ LCD Musical Multi-Alarm/Chronograph. 6-digit. Hours, mins, secs, day, date, 1/100 second stopwatch, split and lap modes, 24 hour alarm, dual time zone. **ONLY £13.45**

14

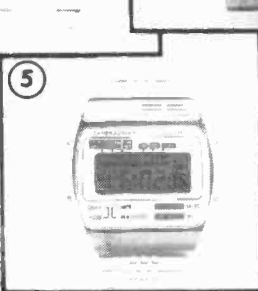CREDIT CARD CALCULATOR. Very slim with standard 4 functions plus memory, percentage and square root. Complete with a mock leather wallet with credit card pocket. **ONLY £6.95**



7

LCD TRAVEL ALARM CLOCK. This tiny clock makes a very unusual gift and is also very practical. Continuously displays hours and minutes with Auto Calendar and Backlight at the touch of a button. Full 24-hour alarm, complete with standard travelling case and stand. **£10.95**

13

MELODY ALARM CHRONOGRAPH. This watch actually plays "The Yellow Rose of Texas" at alarm time, also includes time, date, 1/10th of a second stopwatch and Dual Time Zone. The facestyle may vary from illustration slightly. **Only £14.95**





8

LADIES QUARTZ LCD. 5-function as Gents No. 1. Available with black or white face. **ONLY £5.95**

12

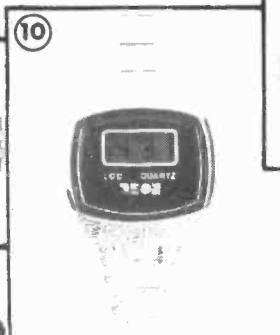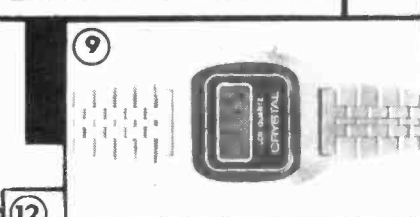A very practically sized mains operated **DIGITAL ALARM CLOCK** - this item is extremely well finished and looks equally at home by the bedside or in the living room. With snooze/repeater alarm. You could not even buy the components to build your own for this price. Available at the amazingly low price of **only £8.95 + 80p p&p**






9

LADIES QUARTZ LCD. SAME FUNCTIONS AS 8. - Alternative style. Available with black or white face. **ONLY £5.95**

11

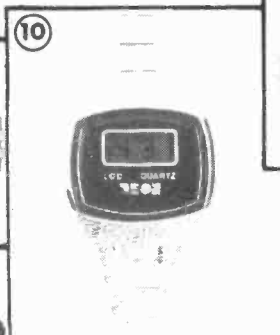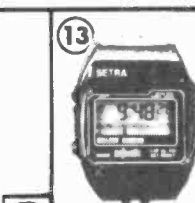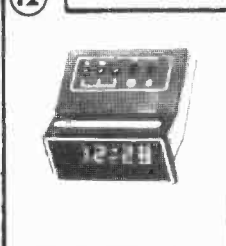LADIES QUARTZ LCD SAME AS 10. Alternative "Round" shape. Available in gold or silver colour. **ONLY £8.95**



10

LADIES QUARTZ LCD. 5 functions. Dress Style. Functions same as 1. Available in gold or silver colour. **ONLY £8.95**

All watches have fully adjustable, matching stainless steel straps, and demonstration battery fitted (this battery is not guaranteed). Please add 60p for each spare battery required.

All products carry a Full 7-Day Money Back Reassurance plus 12 Month Guarantee. Prices include VAT

Send stamped addressed envelope for Colour Brochure of 120 other bargains.

ABELMOOR LTD

78 CASTLE STREET, MELBOURNE, DERBY, DE7 1DY

Please send me items..... (list numbers)

I enclose cheques/P.O.s for £.....

NAME.....

ADDRESS.....


Please add 35p P/P per item

ETI 4


Active 'Scope Probe

Most oscilloscope probes that provide a tenfold boost in input impedance (usually from 1M Ω to 10M Ω) are passive devices and consequently give a corresponding tenfold reduction in voltage gain. This active probe circuit gives an input impedance of approximately 10M Ω shunted by only about 5 to 10pF and has a voltage gain of almost exactly unity. It will not have any significant effect on the bandwidth of the equipment when used with an oscilloscope whose bandwidth is 10 MHz or less and which is AC coupled (the probe is mainly intended for use when investigating high impedance audio or RF signals). Signal levels of up to about 3 V RMS can be handled without clipping, or about 6 V RMS if the supply voltage is raised to 18 V.

The obvious choice for a circuit of this type would at first seem to be a FET used in the source follower mode as this can provide a high input impedance, low input capacitance, low output impedance and nominally unity voltage gain. The problem with such a circuit is that the true voltage gain is only about 0.9 to 0.95, which would obviously have an adverse effect on the accuracy of any form of calibration fitted to the 'scope. Therefore, the circuit finally devised uses Q1 as a common source amplifier, which directly drives common emitter amplifier Q2. There is a 100% negative feedback loop from the collector of Q2 to the source of Q1 and this gives the circuit almost precisely unity voltage gain. This arrangement retains the attributes of a source follower stage and gives good results in other respects as well. Gate biasing for Q1 is provided by R1-3 while DC blocking at the input and output is provided by C1 and C2 respectively. Current consumption of the unit is about 5 mA.

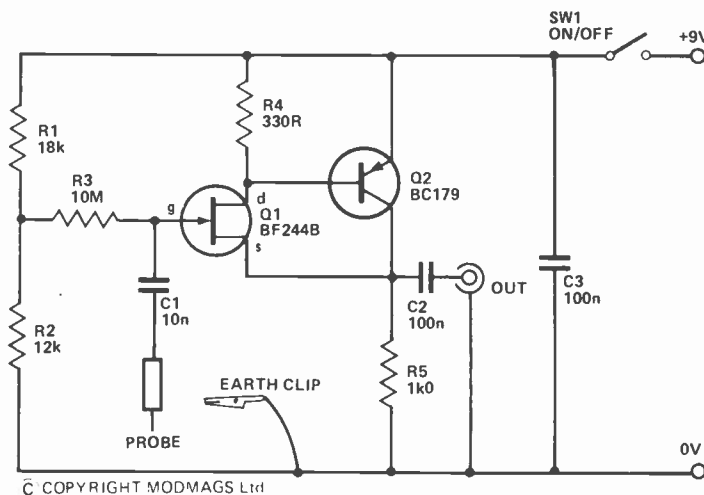

© COPYRIGHT MODMAGS Ltd

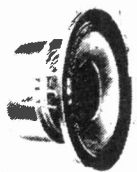

Wilmslow Audio

THE firm for speakers!

SEND 50P FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC, AND DISCOUNT PRICE LIST.

AUDAX - AUDIOMASTER - BAKER - BOWERS & WILKINS - CASTLE - CELESTION - CHARTWELL - COLES - DALESFORD - DECCA - EAGLE - ELAC - EMI - FANE - GAUSS - GOODMAN'S - HARBETH - ISOPHON - I.M.F. - JORDON - JORDAN WATTS - KEF - LOWTHER - MCKENZIE - MISSION - MONITOR AUDIO - MOTOROLA - PEERLESS - RADFORD - RAM - ROGERS - RICHARD ALLAN - SEAS - SHACKMAN - STAG - TANNOY - VIDEOTONE - WHARFEDALE.

WILMSLOW AUDIO


SWAN WORKS, BANK SQUARE
WILMSLOW, CHESHIRE SK9 1HF.

Tel. 0625-529599 FOR MAIL ORDER AND EXPORT OF
DRIVE UNITS, KITS, ETC.

Tel. 0625-526213 (SWIFT OF WILMSLOW) FOR HI-FI
AND COMPLETE SPEAKERS.

The 'WINTON' 50+50 WATTS

**PRICE
REDUCED**

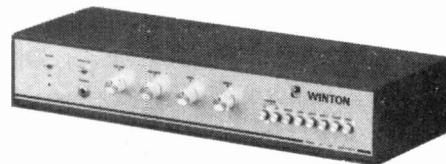

- ★ Power MOS-FET output stage.
- ★ Bi-Fet op-amps.
- ★ Disc, Tuner, Tape and two auxiliary inputs.
- ★ HF & LF Active filters.
- ★ Very low noise disc input stage.
- ★ Easy to build.
- ★ Unconditionally stable.
- ★ Non-magnetic chassis.

During the past eighteen months the WINTON amplifier has set a new standard for Hi-Fi kits and is highly regarded throughout the world. Taking around twenty hours to build and not requiring special equipment for setting up, it represents incredible value for money and is undoubtedly one of the best kits around today. The amplifier with the Ultra Clean Sound, 50+50 watts of its, so clean you'd swear it was sterilised.

A 12p stamp will bring you the full details or better still, send your cheque for the best amplifier kit around. POWER MOS-FETS RULE, O.K.

COMPLETE KITS of all parts necessary to build the P.W. WINTON £133.50 **£115.00**
ALSO NEW — the Persuader speech processor. Suits all standard rigs, CB or amateur **£38.18**

Order with complete confidence (C.W.O. only please) from:

T. & T. ELECTRONICS (Dept. E)
Green Hayes, Surlingham Lane, Rockland St. Mary
Norwich NR14 7HH. Telephone 05088 632

PRICE INCLUSIVE OF V.A.T. & CARRIAGE
Callers by appointment only

**WE HAVE ALL THE NEW ATARI®
VIDEO GAME PROGRAM™
CARTRIDGES.**

ATARI £86 + VAT
SILICA SHOP

**TELEPHONE FOR FREE COLOUR
BROCHURE 01-301 1111**

ELECTRONIC GAMES

ATARI
SPECIAL PRICE
£86 + VAT




INTELLIVISION MATTEL
Available August 1980
This is the most advanced TV game in the world. Expandable next year into a full microcomputer. COLOUR CATALOGUE AVAILABLE WITH DETAILS ON ALL THE CARTRIDGES
£173.87 + VAT



CHESS COMPUTERS
NEW RANGE AVAILABLE AUGUST 1980
We specialise in computer chess machines & stock over 30 different models from £20 to £300
Send for further details




TELETEXT
CEEFAX
RADOFIN TELETEXT Add on Adaptor
£173 + VAT



SPACE INVADERS
HAND HELD + CARTRIDGES
ATARI ADETRONIC
PRINZTRONIC
RADOFIN DATABASE etc.
We keep a full range!
Send for catalogue listing latest high machines



BRIDGE COMPUTER
★ Plays 1/2/3 or 4 Hands
★ Problem Mode
★ Audio Feedback
★ Instant Response
★ Auto scorekeeping




BACKGAMMON COMPUTERS
OMAR 1
OMAR 2
CHALLENGER
GAMMONMASTER
From £38 to £108. Send for further details



24-TUNE DOOR BELL
£13.65 + VAT



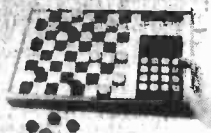DRAUGHTS COMPUTER
★ Solves Problems
★ Rejects illegal moves
★ 2 level machine £43 + VAT
★ 4 level machine £77.78 + VAT




LEISURE
★ CHEAP TV GAMES
★ TELEPHONE ANSWERING MACHINES
★ AUTO DIALERS
★ CALCULATORS
★ DIGITAL WATCHES
★ PRESTEL
★ HAND HELD GAMES

FREE CATALOGUE
For a free copy of our 32 page catalogue, send a 12p stamp to Silica Shop Ltd or Telephone 01-301 1111

MAIL ORDER SERVICE - Free postage & Packing
TELEPHONE & MAIL ORDERS - 01-301 1111
102 Bellegrave Road, Welling, Kent DA16 2QF
Tel: 01-301 1111

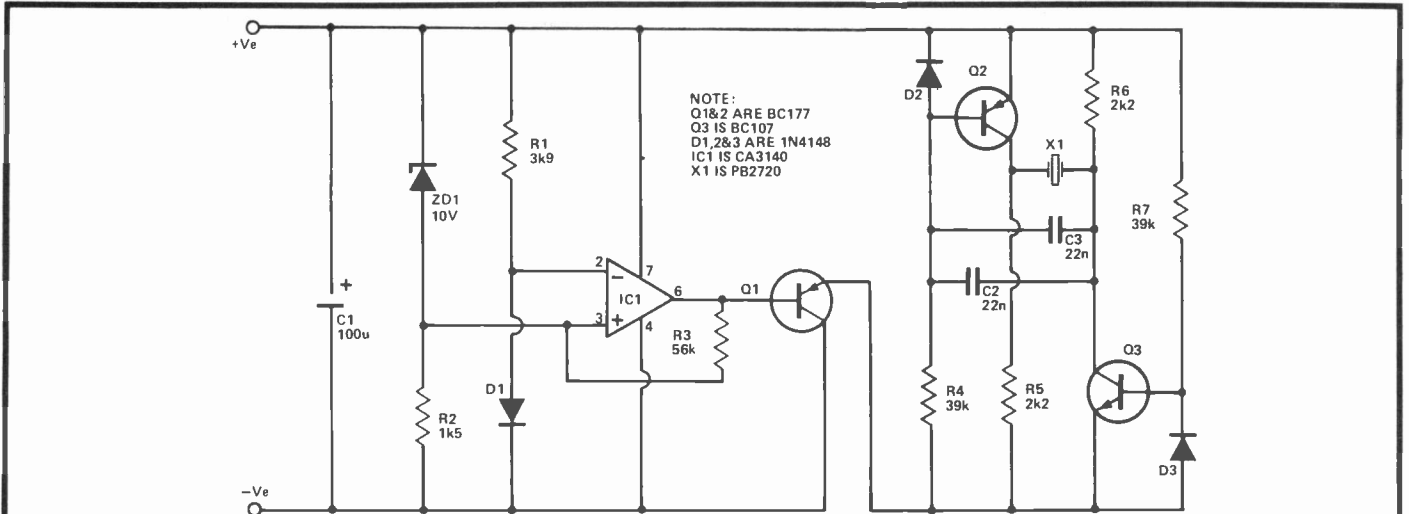SILICA SHOP
SILICA SHOP LTD Dept 2112
102 Bellegrave Road
Welling, Kent DA16 2QF
Tel: 01-301 1111



Car Battery Alarm

This circuit is intended for use with a 12 V car or boat battery and sounds an alarm if the battery voltage drops below about 10 V. An audible alarm is used in preference to the more usual indicator light because an audible signal is far less likely to be missed.

IC1 and its associated circuitry form a voltage detector circuit; IC1 is used here as a voltage comparator rather than an operational amplifier. R1 and D1 provide a stabilised potential of about 0V7 to the inverting input of IC1. The voltage supplied to the non-inverting input is equal to the supply voltage minus the nominal 10 V dropped through zener diode ZD1. Thus the potential at the non-inverting input will normally be about 2 V or more and since this is higher than the voltage fed to the other input the output assumes the high state. Therefore Q1, an emitter follower buffer stage, becomes cut off and no power is fed to the audio alarm circuit at its output.

If the supply voltage falls below about 10V7, then the voltage fed to the non-inverting input falls below the reference level at the other input and IC1's output goes low. Q1 is then switched on and power is connected to the alarm circuit fed from its output. Due to imperfections in the performance of practical zener diodes, the actual voltage at which the alarm is triggered is a little lower than the theoretical one and is typically a fraction over 10 V (or 11 V if preferred, by using an 11 V component in the ZD1 position). R3 is used to introduce a small amount of positive feedback which ensures that the unit switches cleanly from one state to the other and prevents erratic operation.

The alarm generator circuit uses Q2 and Q3 as an astable multivibrator and these drive ceramic resonator X1 with the anti-phase signals at their collectors. This gives the necessary large voltage swing to X1 and produces a reasonably loud output at about 2 kHz or so.

AVOID DANGER from RADIATION WITH OUR RADIATION DETECTOR

Recommended for: Civil Defence, Fire, Hospital, Medical and general use

General Information:

Pocket dosimeters provide an accurate, reliable and immediate method of measuring the integrated dose of radiation received by those exposed to ionising radiation. The dose may be read at any time and in any place, providing a source of light is available.

Principle:

The dosimeter is an ionisation chamber type using a quartz fibre electroscope as the indicating element. A microscope is used to project the image of the moving quartz fibre element on to a graticule scale. The quartz fibre is mounted on a wire electrode, which in turn is supported by a high quality insulator. When the instrument is charged, positive charges distribute themselves over the wire electrode and quartz fibre causing the fibre to bend away from the electrode. The fibre will take up a position depending on the amount of charge on the system.

When the surrounding air in the ionisation chamber is ionised negative ions will be attracted to the positively charged electrode thereby reducing its charge. The resulting fibre movement will be related directly to the quantity of radiation producing the ionisation. The fibre movement can thus be calibrated directly in roentgen units and the rate of movement of the fibre will be proportional to the roentgens received per unit time.

Construction:

The microscope, electroscope and ionisation chamber are housed in an outer skin which may be of brass or aluminium. At one end of the tubular case is fixed a charging assembly and at the other an eye-piece window. These two assemblies are soldered into the outer case to ensure a hermetic seal.

Each dosimeter is provided with protective end cap translucent window so that the cap need not be removed for reading.

Dosimeters meet vibration, drop, salt spray humidity, water immersion and temperature tests


- BE PREPARED, EVERY HOME SHOULD HAVE ONE ●

YOU CAN'T SEE IT
 HEAR IT
 FEEL IT
 BUT YOU CAN DETECT IT

WILL READ ALPHA-BETA & GAMMA RADIATION

Features:

- THESE UNITS WILL READ AUTOMATICALLY THE AMOUNT OF RADIATION IN THE AIR
- THIS INSTRUMENT IS ONLY A LITTLE LARGER THAN A FOUNTAIN PEN
- CLIPS ON TO YOUR TOP POCKET
- WEIGHT LESS THAN 3 OZ.
- CONTAINS THREE LENSES
- FULLY CHARGED, TESTED AND GUARANTEED REFURBISHED BY US
- BRITISH DESIGN AND MANUFACTURE, RUGGED CONSTRUCTION
- MANUFACTURER'S LIST PRICE OF SIMILAR MODEL IS OVER £25
- BUY NOW WHILST STOCKS AVAILABLE. DELIVERY BY RETURN POST

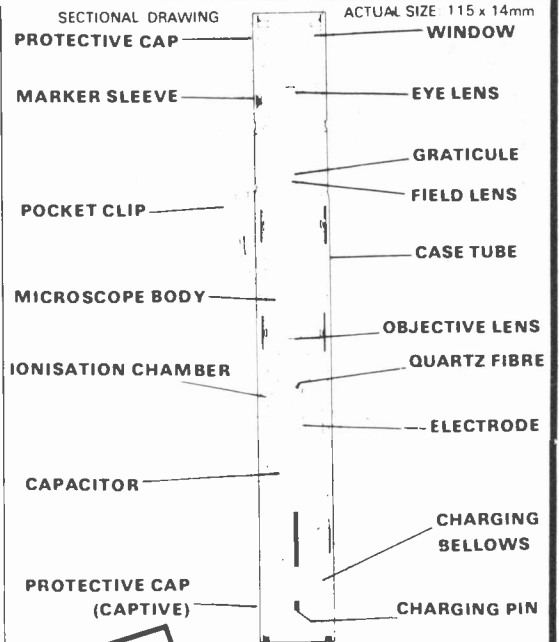

SAVE £20

£5.95 + VAT 89p plus post 70p

Manufacturer's current list price similar model is over £25



HENRY'S

Mail Order Division
 404 Edgware Road, London W2, England I.E.D.



Supplied complete with Data and information on radiation and detectors.

All units are checked and tested just prior to despatch by first-class mail in proper protective packing.

VIEW THRU LENS



DISCO LIGHTING KITS!!!


First class constructional projects. c/w glass fibre P.C.B.'s & full instructions. No extra components needed to make a top rate working unit.

LK1 3 channel sound-to-light.
£9.90 300 w/channel 1v - 100w input

LK3 2kW slider dimmer
£15.50 suitable for clubs/pubs.
A professional unit c/w
FACE PLATE

LK2 3 channel 3kW
£17.90 zero voltage firing
200mV - 100 watts input.

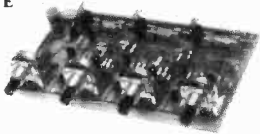LK4 4 channel 4kW
£16.50 audio - forward/reverse
auto - two speed ranges.



Suitable case for
LK 1/2/4 **£3.50**
100w spots ES or BC
£1.50.

Coloured pigmy lamps
65p.
8m rope lights
£49

ALL KITS C/W
circuit, comprehensive
instructions & full
parts guarantee

Carriage on above 70p


UNREPEATABLE HI-FI BARGAIN

3 WAY LOUDSPEAKER KIT C/W BAFFLE (pre-cut)

Comprises:

- ★ 6 1/2" linen surround bass unit
 - ★ 5" mid-range unit
 - ★ 3" tweeter
 - ★ 3 way crossover, fixing screws & baffle
 - ★ 20 watts handling capability.
- Full instructions provided
Must be heard to be believed!!

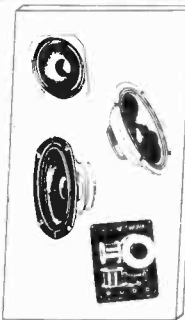£10.50 or 2 kits for £20 Carr. £1 per kit



SAXON ENTERTAINMENTS (ETI)

327-333 Whitehorse Rd., Croydon, Surrey CR0 2HS.
(01) 684 8007

Order by phone - Access/Barclaycard/C.O.D.
Open Mon. - Sat. 9am - 5pm.

ASCII KEYBOARD £39.00 inc. V.A.T., P. & P.

Brand new, type KB060. Designed for ease of use with 60 keys arranged in stepped rows, auto. repeat, 2-key rollover. UC + LC ASCII coded. S.a.e. for details.

THE ZX80 MAGIC BOOK £4.75

Edition 2 containing 15-plus programs for machines with 1-3K RAM: Hammurabi, Othello, Music, Micromon. Programming tips. Using USR. Hardware notes.

23 + 23 WAY ZX80 EDGE CONNECTOR £3.00

MICROPROCESSOR POWER SUPPLY £29.30

Type PZ100. Cased. Assembled and tested. Stabilised outputs + & - 12V at 350mA total; + 5V at 1A.

ALL PRICES INCLUDE UK DELIVERY AND 15% V.A.T.

TIMEDATA Ltd.

57 Swallowdale, Basildon, Essex

PARNDON ELECTRONICS LTD.

44 Paddock Mead, Harlow, Essex. CM18 7RR Tel. 0279 32700 (Dept No. 22)

RESISTORS: 1/4 Watt Carbon Film E24 range $\pm 5\%$ tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded and colour coded
£1.00 per hundred mixed (Min 10 per value)
£8.50 per thousand mixed (Min 50 per value)
Special stock pack 60 values. 10 off each **£5.50**

DIODES: IN4148 3p each. Min order quantity - 15 items.
£1.60 per hundred

DIL SWITCHES: Gold plated contact in fully sealed base - solve those programming problems.
4 Way **86p** each. 6 Way **£1.00** each. 8 Way **£1.20** each

DIL SOCKETS: High quality. low profile sockets.

8 pin - **10p.** 14 pin - **13p.** 16 pin - **15p.** 18 pin - **19p.** 20 pin - **25p.**
22 pin - **29p.** 24 pin - **35p.** 28 pin - **39p.** 40 pin - **57p.**

ALL PRICES INCLUDE V.A.T. & POST & PACKING - NO EXTRAS
MIN ORDER - U.K. £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE

A. Marshall (London) Ltd., Kingsgate House,
Kingsgate Place, London NW6 4TA
Industrial Sales: 01-328 1009
Mail Order: 01-624 8582 24hr. service
A Division of: 325 Ebury Road, London W.1.
40 Crickwood Broadway, London NW2 85 West Regent St. Glasgow
108A Stokes Croft, Bristol.

Marshall's

We now supply the extremely reliable and cost conscious LEADER range of testgear.

SINGLE TRACE OSCILLOSCOPES

LBO 510A 5 4MHz 20mV	£125.00
LBO 512A 5 10MHz 10mV	£170.00
LBO 513A 5 10MHz 10mV	£215.00
LBO 507A 5 20MHz 10mV	£239.00

DUAL TRACE OSCILLOSCOPES

LBO 3085 3 20MHz 2mV	£419.00
LBO 520A 5 20MHz 10mV	£229.00
LBO 520A 5 35MHz 5mV	£475.00
LNO 514 5 10MHz 5mV	£255.00

T.V. RADIO TEST GEAR

LSG 16 Signal Generator	£ 49.00
LSG 231 FM Stereo Signal Generator	£169.00
LCG 397U PAL B Pattern Generator	£189.00

AUDIO TEST GEAR

LAG 26 Audio Generator	£ 60.00
LAG 120A Audio Generator	£119.00
LDM 170 Distortion Meter	£225.00
LFM 39A Wow/Flutter Meter (Dist)	£249.00
LFM 39A Wow/Flutter Meter (Dist)	£299.00
LAV 191 Audio Tester	£239.00
LAG 125 Low Distortion Audio Generator	£229.00

GENERAL TEST GEAR

LCR 740 LCR Bridge	£135.00
LTC 906A Transistor Checker	£ 90.00
LVT 72 FET Transistor Checker	£119.00
LTC 907 Transistor Checker	£139.00
LAT 61 Attenuator	£135.00
LAT 45 Attenuator	£ 75.00
LFG 1300 Sweep Function Generator	£299.00

AMATEUR RADIO

LDM 815 DIP Meter	£ 43.00
LIM 870A Antenna Impedance Meter	£ 41.00
LPM 880 HF Power Meter	£ 69.00
LPM 885 SWR/Watt Meter	£ 44.00
LAC 895 Antenna Coupler	£ 85.00
LAC 896 Antenna Coupler	£ 41.00
LAC 897 Antenna Coupler	£ 41.00

Please send large SAE for special catalogue. All prices exclusive VAT/carriage.

The new Marshall's 80/81 catalogue is now available. A veritable treasure house of components, test gear, tools, etc.



Lots of old friends, but also many new products including leader test gear, Crimson Hi Fi Modules, Rechargeable Ni Cad batteries and chargers (very competitive). More components including SN74ALS series, new tools etc. Available by post, UK 75p post paid: Europe 95p post paid: Rest of world £1.35 post paid.

SINCLAIR INSTRUMENTS

Digital Multimeter

PDM35	£ 34.50
DM235	£ 52.50
DM350	£ 72.50
DM450	£ 99.00

Digital Frequency Meter

PFM200	£ 49.80
--------	---------

Low Power Oscilloscope

SC110	£139.00
-------	---------

NEW

TF200 Frequency Meter
£145.00

TGF105 Pulse Generator
£ 85.00

CRIMSON ELEKTRIK HI FI MODULES

CE608 Power Amp	£20.09
CE1004 " "	£23.43
CE1008 " "	£26.30
CE1704 " "	£33.48
CE1708 " "	£33.48
CPS1 Power Unit	£19.52
CPS3 " "	£23.52
CPS6 " "	£30.00
CPR1 Pre Amp	£32.17
CPR1S Pre Amp	£42.52

All Prices + VAT + postage/packaging

Don't forget! We also carry an impressive range of semi conductors, passive components, electro mechanical components, tools etc.



MUSICAL MICRO 24 TUNE DOOR BELL



BUILD THE WORLD FAMOUS CHROMA-CHIME

Give your friends a warm welcome. Yes, think how delighted and amazed they will be to hear the musical Chroma-Chime play when they press your button!

The Chroma-Chime uses a microcomputer to play 24 well-known tunes. The kit is simplicity itself for ease of construction. Absolutely everything needed is supplied, including:

- ★ Resistors, Capacitors, Diodes, Transistors, I.C. Socket and all hardware
- ★ Texas Instruments TMS 1000 microcomputer
- ★ Comprehensive kit manual with full circuit details
- ★ Ready drilled and legended PCB included

**ONLY
£11.95**
+ 75p p&p
UK ONLY

Plays 24 well-known tunes including:

Star Spangled Banner, William Tell Overture, Greensleeves, Rule Britannia, Colonel Bogey, Oh come all ye faithful, plus many other popular tunes.

- ★ No previous microcomputer experience necessary
- ★ All programming retained is on chip ROM
- ★ Fully guaranteed
- ★ Ideal present any time

TMS 1000N 

—MP0027A Micro-computer chip available separately if required. Full 24 tune spec device fully guaranteed. This unique chip can be used not only for electronic door-chimes, but for other projects requiring musical output. Car Horns Musical Boxes Alarms Amusement Machines Public Address etc.

£4.95

ALL CHROMATRONICS PRODUCTS SUPPLIED WITH MONEY BACK GUARANTEE

Please send me ETI 12 80

TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX
Telephone: (0279) 418611

NAME


ADDRESS

I enclose cheque/PO value £
or debit my ACCESS/BARCLAYCARD account no.

Signature

CHROMATRONICS

Here

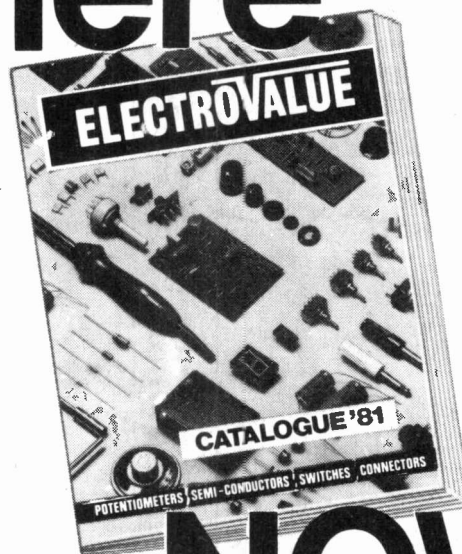

NOW

ELECTROVALUE CATALOGUE '81

as included FREE with December issue of
PRACTICAL ELECTRONICS

It's work-bench size for keeping alongside your favourite journal for instant reference to stock and technical data.

**NEW
LARGE
FORMAT**

With more to choose from than ever - all the items you have learned to depend on being obtainable from Electrovalue PLUS MANY NEW ONES to bring Catalogue '81 bang up to date. The V.A.T. inclusive price list that goes with it will hold for at least 4 months before the next one is issued.

Yes - you will enjoy dealing with Electrovalue - prices are keen - service is tops.

**FREE
FOR THE
ASKING**

Write, phone or call if you haven't yet got Catalogue '81 - and you will receive yours by return. (We pay postage).

AND YOU GET BONUS DISCOUNTS AND FREE U.K. POSTAGE TOO, WHEN YOU BUY FROM ELECTROVALUE.

ELECTROVALUE LTD. (Dept. ETI), 28 St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB. Telephone: (STD 0784) (London 87) 33603 Telex: 264475.

Please send me my FREE COPY OF ELECTROVALUE CATALOGUE '81.

Name

Address

ETI BOOK SERVICE

How to order: Make cheques etc payable to ETI Book Service. Payment by sterling only please. Orders should be sent to: ETI Book Service, 145 Charing Cross Road, London, WC2A 4AB. Prices include P&D. Prices are in pounds unless otherwise stated.

BEGINNERS

- Beginners Guide to Electronics Squires £4.25
- Beginners Guide to Transistors Reddihough £4.25
- Beginners Guide to Integrated Circuits Sinclair £4.25
- Understanding Electronic Circuits Sinclair £5.10
- Understanding Electronic Components Sinclair £5.10
- Beginners Guide to Radio King £4.25
- Beginners Guide to Audio Sinclair £4.25
- Understanding Electronics, Waring £4.90

COOKBOOKS

- TV Typewriters Cookbook £7.75
- CMOS Cookbook £8.20
- Active Filters £11.30
- IC Timer Cookbook £7.65
- IC Op-Amp Cookbook £10.00
- Video Cookbook £6.50
- TTL Cookbook £7.55
- The Basic Cook £4.00 inc. p/p
- IC Converter Cookbook £9.50
- Master IC Cookbook Hallmark £7.45

APPLICATIONS

- Fire and Theft Security Systems B. Weis £2.15
- How To Build Electronic Kits Capel £3.25
- 110 Electronic Alarm Projects R. M. Marston £4.95
- 110 Semiconductor Projects for the Home Constructor R. M. Marston £4.95
- 110 Integrated Circuit Projects for the Home Constructor R. M. Marston £4.95
- 110 Thyristor Projects Using SCRs R. M. Marston £4.95
- 110 Wave Form Generator Projects R. M. Marston £4.95

COMPUTING & MICROPROCESSORS

- What is a Microprocessor? 2 cassette tapes plus a 72-page book £10.00
- Beginners Guide to Computers and Microprocessors with Projects C. Adams £6.05
- Basic Computer Games Ahl £6.05
- Basic for Home Computers A self-teaching guide B. Albrecht £6.00
- Illustrating Basic D. Alcock £4.25
- Troubleshooting to Microprocessors and Digital Logic Goodman £5.90
- Z-80 Microcomputer Handbook W. Barden £7.75
- How to Program Microcomputers W. Barden £7.25
- Introduction to Microcomputers and Microprocessors A. Burns £4.30
- Microprocessors in Instruments and Control R. J. Bibber £12.10
- Basic Basic J. S. Coan £7.40
- Advanced Basic J. S. Coan £6.40
- Getting Acquainted with Microprocessors L. Frenzel £7.25
- Beginners Guide to Microprocessors C. M. Gilmore £4.50
- 1001 Things to do with Your Personal Computer Sawusch £6.00
- Beginning Basic R. E. Gosling £4.75
- Microprocessor Programming for Computer Hobbyists N. Graham £7.15
- Miniprocessors from Calculators to Computers Heiserman £4.95
- Microcomputers, Microprocessors, Hardware, Software and Applications J. L. Hilburn £17.40
- Basic Programming J. G. Kemeny £8.20
- Microprocessor Systems Design E. Klingman £17.65
- Intro to Microprocessors Leventhal £11.00
- Microprocessors — Technology, Architecture & Applications R. F. McGlynn £11.30
- Interactive Computing with Basic Monro £4.35
- Basic with Style P. Nagin £4.50
- Software Design for Microcomputers Ogdin £8.85
- Microcomputer Design Ogdin £7.45
- Microcomputer Base Design Peatman £6.10
- Hands on Basic with a PET Peckham £10.50
- Complete Microcomputer Systems Handbook £8.75
- 6800 Software Gourmet Guide and Cookbook Scelbi £9.20
- 8080 Software Gourmet Guide and Cookbook £9.20
- The 8080A Bugbook: Microcomputer Interfacing & Programming P. H. Rony £8.35
- 8080/8085 Software Design Titus £7.60
- 57 Practical Programs & Games in Basic Tracton £6.65
- How to Design, Build and Program Your own Working Computer System £7.10
- Your Own Computer Waite £2.25
- Microprocessor/Microprogramming Handbook Ward £6.20

LOGIC

- Logic Design Projects with Simulations £17.25
- Practical Digital Design Techniques £11.90
- Designing With TTL Integrated Circuits £10.95
- How To Design a Computer Logic System £11.95
- 110 CMOS Digital Logic Projects for the Home Constructor R. M. Marston £4.95
- Understanding CMOS Integrated Circuits £10.95
- MSB Digital Logic £11.95

TEST INSTRUMENTS

- The Test Instrument £11.95
- AVR Digital Oscilloscope £11.95
- AVR Digital Oscilloscope £11.95
- AVR Digital Oscilloscope £11.95

OP-AMPS

- Applications of Operational Amplifiers £11.95
- 110 Operational Amplifier Projects for the Home Constructor R. M. Marston £4.95
- Designing with Operational Amplifiers £11.95
- 110 Operational Amplifier Projects for the Home Constructor R. M. Marston £4.95

COMMUNICATIONS

- Communications Systems £11.95
- Digital Signal Processing £11.95
- Electronic Communications Systems £11.95
- Frequency Synthesis £11.95
- Principles of Communication Systems £11.95

THEORY

- Introduction to Digital Filtering £11.95
- Transistor Circuit Design £11.95
- Foundations of Wireless Technology £11.95
- Electronic Circuit Design Handbook £11.95
- Master Guide to Electronic Circuits £11.95

REFERENCE

- Electronic Reference Handbook £11.95
- Electronic Components £11.95
- Electronic Diagrams £11.95
- Microprocessor Handbook £11.95
- Microprocessor Handbook £11.95
- Microprocessor Handbook £11.95
- Microprocessor Handbook £11.95
- Microprocessor Handbook £11.95

MISCELLANEOUS

- Electronic Fault Finding £11.95
- Electronic Fault Finding £11.95
- Electronic Fault Finding £11.95
- Electronic Fault Finding £11.95

fallen behind recent advances
 just starting out
 need a design reference book?
 ETI Book Service can help you
 view our books on our
 on the internet

£395
incl.VAT& P&P



micron

'MICRON' may sound small - but we all know that it's much larger than an atom!

The un-beatable features of Microtan 65 and Tanex have been brought together to give you Micron, a ready built and tested computer of outstanding value. Fully supported by comprehensive documentation, Micron represents an ideal starting point in personal computing. We've taken a full O.E.M. licence for Microsoft Basic, which means that you'll have the support of the most popular Basic available, (as used on PET, APPLE, TANDY etc.). If you want to expand Micron there's no problem, just move into the system rack and choose from the range of Microtan modules. Read the information, study what the magazines have to say about us and compare what we have to offer with other systems, then we feel sure that you'll be convinced that we've produced an excellent product.

- FULLY BUILT, TESTED AND CASED.
- 6502 BASED MICROCOMPUTER.
- VDU ALPHA NUMERIC DISPLAY.
- 8K RAM.
- 32 PARALLEL I/O LINES.
- 2 TTL SERIAL I/O LINES.
- 1 SERIAL I/O PORT WITH RS232/20mA LOOP, AND 16 PROGRAMMABLE BAUD RATES.
- 300 / 2400 BAUD FILENAMED CASS. INTERFACE.
- DATA BUS BUFFERING.
- MEMORY MAPPING CONTROL.
- 71 KEY ASCII KEYBOARD, INCLUDING NUMERIC KEYPAD.
- POWER SUPPLY INCLUDED.


SOFTWARE

- 10K EXTENDED MICROSOFT BASIC.
- ALL THE USUAL BASIC COMMANDS.
- INTEGER AND REAL NUMBERS.
- INTEGER AND REAL ARRAYS.
- INTRINSIC FUNCTIONS: ABS, INT, RND, SGN, SIN, SQR, TAB, USR, ATN, COS, EXP, LOG, TAN.
- USER DEFINED FUNCTIONS.
- READ AND DATA STATEMENTS.
- DUMP AND LOAD PROGRAMS.
- PROGRAM EDITING COMMAND.
- STRING FUNCTION FOR TEXT I/O.
- BASIC CAN CALL MACHINE CODE SUB-ROUTINE.
- USER MACHINE CODE INTERRUPT HANDLER INTERFACES WITH BASIC.
- XBUG.
- DATA CASSETTE FILE HANDLING IN BASIC

TANGERINE
COMPUTER SYSTEMS LIMITED

Forehill Works
Forehill Ely Cambs England Tel: (0353)3633

microtan 65

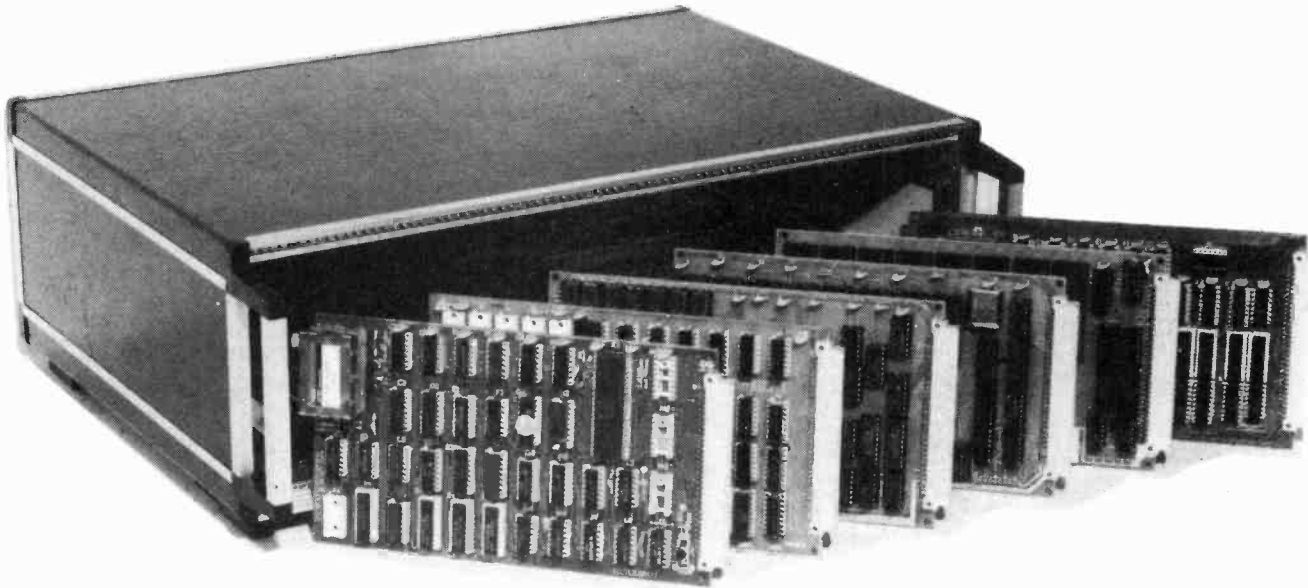

The Microtan system is rapidly becoming accepted as the ultimate approach to personal computing. Start with Microtan 65, a 6502 based single board computer, and expand to a powerful system in simple and in-expensive stages. The Microtan system is a concept and not an afterthought, this means expansion is easy and very efficient! Unlike many other systems, you'll find it difficult to outgrow Microtan, and you won't be wasting your money on a product that will only last you a few months! When you are ready to expand, Tanex is waiting. The features offered by Tanex are tremendous, and you can start into them for just £49.45! Cassette interface, 16 I/O lines, two 16 bit counter timers, data bus buffering, memory mapping and a further 1K of RAM are standard. From thereon expansion is simple, just plug in extra integrated circuits to get yourself 8K of RAM, a further 16 I/O lines and two more counter timers a serial I/O line with RS232/20mA loop and full modem control, XBUG - a firmware package containing cassette file handling routines, plus a line-by-line assembler (translator) and dis-assembler, PLUS 10K EXTENDED MICROSOFT BASIC, a suped-up version of the Basic as used by major manufacturers such as Apple, Tandy and Nascom, NO OTHER LOW COST MICROCOMPUTER OFFERS YOU THIS SUPERB PACKAGE. O.K. so you want more memory, try Tanram for size! Upto 40K bytes on one board starting for as little as £50.60. RAM freaks will be pleased to hear that our system mother board offers page memory logic which will support 277K Bytes, satisfied? To house these beautiful modules you can choose between our mini-rack (as used on Micron), which accepts Microtan and Tanex, or our system rack pictured above. The system rack will support 12 modules. What are these extra modules? Well for starters there's a couple of I/O modules, parallel and serial offering upto 128 I/O lines organised as 16 8 bit ports and 8 serial I/O ports respectively. Shortly we'll be introducing high definition (256x256) colour graphics, A to D and D to A modules, IEEE 488 Bus interface, a PROM programmer, disc controller and TANDOS - a 6502 CPM system. So there's plenty to keep you busy. Send for more details, and find out how you can get started for just £79.35!

ALL PRICES QUOTED INCLUDE V.A.T.

AIM 65, KIM 1, SIM 1 USERS- READ ON!

We have produced a T.V. interface module which simply connects to the expansion socket of your computer and produces a display of 16 rows by 40 characters! Of even more interest will be our Buffer module, which allows you to expand into our system rack, giving you access to the full range of Microtan modules.

Please underline the information required.

AIM T.V. INTERFACE. MICROTAN SYSTEM.

NAME: _____

ADDRESS: _____

PLEASE ENCLOSE 12p STAMP. THANK YOU.

BUILD YOUR OWN METAL DETECTOR VLF/TR VCO/TR IB/TR BFO ...

Pre-aligned search heads — test equipment not required. Literature available in return for SAE. Manuals and parts sold separately: write or phone for price. Export welcome: write for quote.



Shadow VLF/TR. Full specification discriminator, not just ferrous/nonferrous indication. It works by measuring the conductivity of the target; now you can reject nails bottle caps even aluminium foil and ring pull tabs! Full ground effect exclusion over normal or high permeability soils. The head is thermally and capacitively shielded. 4 modes: deepseeking VLF plus 3 TR discriminating ranges. Push button "memory" tuning. Performance equals commercial detectors costing £200! As described in ETI. Complete kit now only £87.67 inc. VAT & post!

Shadow TR/1B

Individual parts: Search head £21.33 PCB £6.80 Case £5.33 Adjustable shaft assy. £5.10. LM393 £1.12 Manual (gives more info. than ETI article — and extra function) £1.12. All inc. VAT & post! (Other parts also available separately)

Shadow TR/1B (illustrated). A true transmit receive/induction balance detector at a budget price for anyone who doesn't need discrimination. Waterproof and thermally insulated search head. Good sensitivity Built-in speaker and headset jack. Complete kit £33.60 inc. VAT and Post.

Shadow TR/VCO. An advanced version of the TR/1B Use as a sensitive 1B machine or switch to VCO mode when the sound changes to a varying pitch, allowing easier use over mineralised ground and enabling detection of negative, high permeability anomalies. Kit price £38.67 inc VAT and Post.

Matching stereo headphones for all Shadow models £5.85 inc. VAT and Post.

Shell Kit. Consists of the (hard to find) hardware items, for detectors of your own design. Fully adjustable shaft with handle, search head mouldings (int. diam. 185mm) with hinge assembly, special clips to mount your own control housing (any box is suitable). Completely non-metallic and undrilled. With assembly instructions £14.45 inc. VAT and Post

**ALTEK (ETI), 1 Green Lane
Walton-on-Thames Surrey**

Order by post or phone (24 hours). Access & Visa Cards quote number. Callers by appointment only please. Phone (093 22) 44110 anytime!

Electronic Kits for the Thrifty!

Build 50 Interesting Projects on a P.C. Chassis with surplus components from our "Spares-Box."

EXPERIMENTER'S PRINTED CIRCUIT KIT

Contents: 4 small boards to suit the enclosed designs. Etching Powder, Resist Paint, Solvent, Degreaser and Etching Instructions; also 50 Circuit Diagrams, Chassis Plans and Layouts for simple Crystal Sets, Transistor Radios, Transmitters, Amplifiers, Intercoms, Radio Control, Metal Detector, Photoelectric and Ultrasonic Alarms, "Perpetual Motions", Light-Beam Telephone Instruments, Testers, Gadgets, etc. You can build at negligible cost with "Surplus" or reclaimed parts and transistors you already have.

Price: £1.70. Postage and Packing 30p.

PHOTOELECTRIC KIT

A kit of basic parts to build a simple I.R.-sensitive Photoelectric Switch. Contents: Phototransistor, Transistors, Diode, Resistors, Connector, Latching Relay, Chassis Board, Case, Screws and full instructions.

Price: £4.50. Postage and Packing 50p.

OPTICAL KIT


A kit of parts to build an I.R. folded-beam Projector and Receiver to suit the above kit. Contents: 2 Lenses, 2 Mirrors, 2 45-deg. blocks, Infra-Red Filter, Lampholder, Building Plans. Price £3.70. Postage and Packing 30p. Both kits together make an Invisible-Beam Alarm.

EXPERIMENTAL ELECTRONICS

335 Battersea Park Road, London, SW11 4SL

Send s.a.e. for full details of all kits and circuits

STEREO DISCO EQUIPMENT

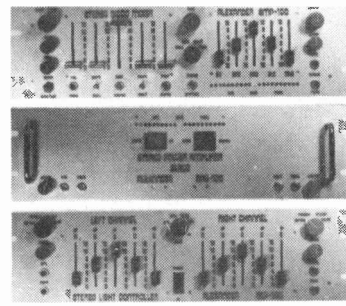

SMP100 5 channel stereo mixer

3 BAND GRAPHIC EQUALISER • AUTOFADE • PREFADE MONITORING • INT. 100dB BUILT AND TESTED

SAU100 100 watt stereo amplifier

100/100 WATTS/8 OHMS • 100/150 WATTS/4 OHMS • 300 WATTS MUF0

SLP100 5+5 chan. stereo lighting controller

19" RACK MOUNTING • DIMMING • STROBE • RANDOM • CHASE • SOUND • ZERO-X TRIAC DRIVE OPTO-COUPLED


KIT 121 65 BUILT AND TESTED £39.00 45 SHACKLETON SPRING JUNE STEVENAGE MK18TS

MODULE KITS from £5.30 built and tested from £6.60

ALEXANDER SYSTEMS

The 2001 sweeps the board at only £75*

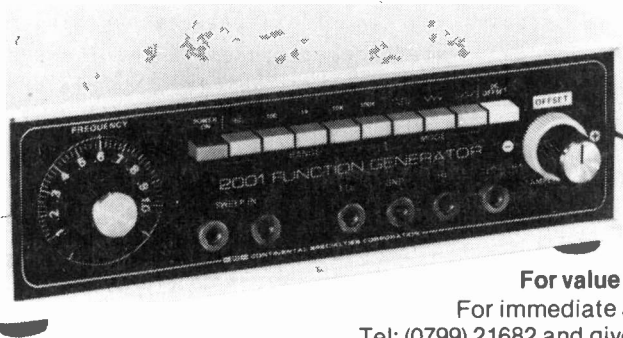See us on STAND F1 at LONDON BREADBOARD EXHIBITION



Get all the waveforms you need — 1 Hz to 1 MHz in five overlapping ranges: stable, low-distortion sine waves, fast rise/fall-time square waves, high linearity triangle waves — even a separate TTL square wave output. Plus high- and low-level main outputs.


An applied DC Voltage at the Sweep input can shift the 2001's frequency; or sweep up to 100:1 with an AC signal. A pushbutton activates the DC Offset control, which shifts the output waveform up or down on command.

For value for money the 2001 sweeps the rest off the board.

For immediate action — The C.S.C. 24 hour, 5 day a week service Tel: (0799) 21682 and give us your Access, American Express, Barclaycard number and your order will be in the post immediately or just clip out the coupon.

* price excluding P&P and 15% VAT

CONTINENTAL SPECIALTIES CORPORATION

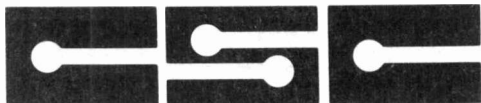

C.S.C. (UK) Limited, Dept. 9HH
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ
Tel: Saffron Walden (0799) 21682 Telex: 817477

Continental Specialties Corporation (UK) Limited Dept. 9HH
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ

Model 2001 Sweepable
Function Generator

£87.98. (inc. P&P
and 15% VAT)

Qty
Reqd.

For FREE catalogue
tick box


Name Address

I enclose PO/Cheque for £..... or debit my
Barclaycard/Access/American Express No exp date

JUST COMPARE OUR CASH AND CARRY PRICES!

NEW REDUCED PRICES

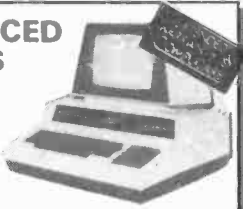8K **£399**
 16K **£499** } VAT
 32K **£599**
 RRP £795 for 32K



The PEDIGREE PETS Very popular for home & business use. 8K Microsoft Basic in ROM. 8K Pet 32K & 16K with new improved keyboard. All with green screen. Cassette Deck **£55** extra. Full range of software available. Interface PET IEEE — Centronics Parallel. Not decoded **£49.00** + VAT. Decoded **£77.00** + VAT.

NOW IN STOCK SUPER 80 COLUMN PET
 only **£825** + VAT

SPECIAL SCOOP GET YOURSELF A PRINTER FOR YOUR PET AND SAVE A FORTUNE

only **£299** + VAT



Interface Cards **£49**
 Full Pet Graphics including cables. Ready to go **EX-STOCK**.
 Interfaces with APPLE, PET, EXIDY, TRS80, COMPUKIT and NASCOM.

NASCOM 2 DISC DRIVES

Add a powerful, double density, mini floppy disc to your Nascom system.

- Disc Controller Card (includes Nasbus 6 S100 interface)
- Will control 4 Drives
- CPM operating system
- Extended Disc Basic Compiler
- Power supply included

One Disc System — **£499** + VAT
 Additional Disc Unit — **£299** + VAT



NASCOM 2 GAMES TAPE


featuring Space Invaders and Android Nim, Re-numbering program and other goodies!
£7.50 + VAT

NEC SPINWRITER
 only **£1490** + VAT



NEC's high quality printer uses a print "thimble" that has less diameter and inertia than a daisy wheel, giving a quieter, faster, more reliable printer that can cope with plotting and printing (128 ASCII characters) with up to five copies, friction or tractor fed. The ribbon and thimble can be changed in seconds. 55 characters per second bidirectional printing — with red/black, bold, subscript, superscript, proportional spacing, tabbing, and much, much more.

TEAC DISK DRIVES

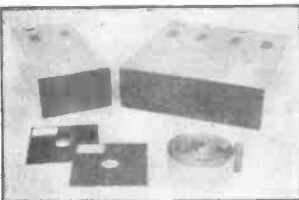

- TEAC FD-50A has 40 tracks giving 125K Bytes unformatted single density capacity.
- The FD-50A can be used in double density recording mode.
- The FD-50A is Shugart SA400 interface compatible.
- Directly compatible with Tandy TRS80 expansion interface.
- Also interfaces with Video Genie, SWTP, Heathkit, North Star Horizon, Superbrain, Nascom, etc, etc.
- Disk selection for Daisy chaining up to 4 Disks.
- Disks plus power supply housed in an attractive grey case.

Single Disk Drive **£225** + VAT Double Disk Drive **£389** + VAT

COMP POCKET COMPUTER GREATEST BREAKTHROUGH YET



£99.90 + VAT

COMPUTER POWER THAT ONCE FILLED A ROOM CAN NOW BE CARRIED IN YOUR POCKET!

- Programs in BASIC • "QWERTY" Alphabetic Keyboard • 1.9K Random Access Memory • Long Battery Life.

Computer power that once filled a room can now be carried in your pocket! It's easy to load with ready-to-run software from cassette tape (interface and recorder optional) or program it yourself in easy-to-learn BASIC. 24-character liquid crystal readout displays one line at a time. Special feature is advanced non-volatile memory allows you to power on and off without losing the contents of memory. Note: Memory must be transferred to tape before changing batteries. Automatic statement compaction squeezes every ounce of memory space. Features power-off retention of programs and data. Powerful resident BASIC language includes multiple statements, math functions, editing, strings, arrays and much more. Multiple program loading capability subject to RAM availability. Carrying case and batteries included.

Program	Each	Program	Each
Real Estate	£13.95	Games 1	£8.95
Civil Engineering	£13.95	Business Statistics	£10.95
Aviation	£13.95	Business Financial	£10.95
Math Drill	£8.95	Personal Financial	£10.95

EXTENDED WARRANTY BY COMPUKARE

EXATRON STRINGY FLOPPY FOR TRS80



(Expansion interface not needed)
 only **£169** + VAT

High Speed storage medium that is cheap and reliable. Includes 20 wafers - M/C monitor - BUS EXPN cable. **£169**

COMMERCIAL • EXPANDABLE • COMPLETE TRS 80 • MODEL II

EXTENDED WARRANTY BY COMPUKARE
 COMING SOON
 26 megabyte Hard Disc multi-user DOS



WE USE THIS MACHINE IN OUR BUSINESS

1 DISK EXPANSION Room for 3
 500K per Drive gives total of 1.5M Byte — 1 Drive plus Cabinet **£799** + VAT



This new unit from the world's most successful micro company is now available immediately with software. The basic unit comes complete with 64 thousand characters (bytes) of Memory. The built in 8" Floppy disc adds another 1/2 million extra characters including the disc operating system. More disc expansion is now available. The Model II is a complete unit with a full keyboard including a numeric pad and 12" screen which gives 24 lines of 80 characters. The computer is supplied with both the disc operating system and the Level III Basic. A full self test routine is written into the power up procedure to eliminate incorrect operation. Both serial and parallel expansion sockets are standard. A printer is a plug-in operation. Both hardware and software necessary to talk to a mainframe are included. Terminal usage is very possible. With the addition of CPM2 you can operate with COBOL, FORTRAN, MBASIC, CBASIC in which languages are many other applications packages i.e. accounting, payroll stock etc.

64K 1-Disk Model II **£1995.00** + VAT
 RRP £2250.00
 CP/M2 **£95.00** C BASIC **£75.00** FORTRAN **£220.00**
 CIS COBOL **£400.00** M BASIC **£155.00** WORDSTAR **£255.00**

EPROM 2716 **£12.50** + VAT

EXTENDED WARRANTY BY COMPUKARE

only **£325** - VAT



TRS80 LEVEL 2 16K


Fully converted to UK T.V. Standard. Comes complete with easy to follow manuals. UK Power Supply. — Cassette Leads — Sample tapes. Special box to enable you to plug into your own TV. Recommended for first time buyers. Just plug in and go. Full Range of Software Available.
 Interface to Centronics Parallel for TRS80 **£75.00** + VAT

only **£295** - VAT
 Expand your TRS80 by 32K

TRS80 EXPANSION INTERFACE


32K Memory on board
 Centronics parallel port
 Disk controller card. Real time clock. Requires Level II Basic. Interface for 2 cassette decks. Complete with power supply.

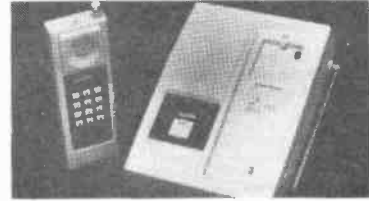YOU NEED NEVER MISS AN IMPORTANT CALL AGAIN TWO CORDLESS TELEPHONE SYSTEMS — DIRECT FROM USA



THE ALCOM only **£147** + VAT

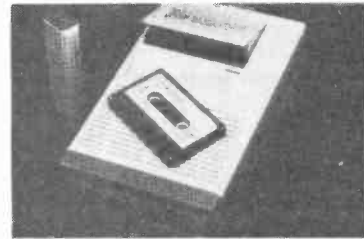Base station connects to your telephone line. Remote handset clips to your belt and gives you push-button dialling — Bleeps when call arriving — Nicad rechargeable batteries. Charger in base unit.



LOW COST TELEPHONE ANSWERING MACHINE only **£99.95** + VAT

Microprocessor controlled answering machine. Plug into your phone line. Records any phone call messages. Remote bleeper enables you to listen to your messages from anywhere in the world. Uses standard cassettes. Comes complete with mains adaptor, microphone, remote bleeper, base unit, cassette with 30 sample pre-recorded messages.

THE VIDEO GENIE SYSTEM



EG3000 Series
16K WITH **£289** + VAT
 • 16K user RAM
 plus extended 12K Microsoft BASIC in ROM • Fully TRS-80 Level II software compatible • Huge range of software already available • Self contained, PSU, UHF modulator, and cassette • Simply plugs into video monitor or UHF TV • Full expansion to disks and printer • Absolutely complete — just fit into mains plug.

COMING SOON

THE MARTELL TV GAME

LEAR SIEGLER model 310 Ballistic printer. Save £400. **OUR PRICE ONLY £950** or make us an offer.
DEC VT52. Used but clean **£650.**
TERMINAL 30 PRINTER WITH TWIN CASSETTE. 30 cps. Standard 232. **£700** or offer.
NEWBURY VDU with Keyboard Model 24-80 **£350** or offer.
CIPHER VDU with separate Keyboard (No case). Printer, port, reverse video/flashing etc **£375** each or offer.
CALCOMP 564 BARREL PRINTER. MUST GO **£650.**
CIL PLOTTER on STAND. Ex-Ministry VGC. **£850.**
FACIT 4001 READER with 2 spoolers 4015. **£475** the set. Please make an offer we can accept.
FACIT PUNCH with 5107 CONTROLLER **£250.**
DICOM Disk Drive B" Ex-Ministry Clean **£120** each.
TELETYPE PUNCH in Silent Case **£45** each.
ARCTURUS A18D, 16 bit mini. With Data. Another gift **£425.**
COMPUTER AUTOMATION ALPHA 16 with TTL Input Interface. Massive Documentation & quantity of paper tapes. And again a gift at **£390.**
HEWLETT PACKARD 2114A COMPUTER. No Interface. No data. HENCE **£475.**
TELETYPE ASR 33 with 20ma Loop **£350** each, 232 available at extra cost. KSR as above **£225** each.
TWIN SHUGART Floppy Drives a **£450** gift.
A FEW OLIVETTI PRINTERS & KEYBOARD Type Te300 still available — please enquire.

STEPPING MOTORS
 200 Steps — 20-oz/in. torque, 12/24 volt input 4-wire.
£12 each. P&P **£1.50**

STEPPING MOTORS
 200 Steps. 20 oz/in. torque. 120 volt operating 3-wire.
£4 each. P&P **£1.50**

BC172	5p	BC212B	5p	74C20	25p	2N5449	5p	BC251	5p
BZY884V7	10p	SN76550	5p	74C08	25p	2N3053	15p	BC171A	5p
BZY8813V	10p	IC7451	10p	74C10	20p	TIS92	10p	BF760	5p
2N3006	5p	MC4001	15p	MC4049	35p	TIS93	10p	4013	30p
1N4305	5p	MC4012	15p	2N3704	8p	BC337	8p		
BZX79C12	10p	MC4020	75p	2N5447	5p	BC327	8p		

MONSANTO DISPLAY type MAN 101A 0.3" display. **£1** each.
 REGULATORS — all at **45p** each.
 MC7805, 7812, 7815, 7912
 MC1496L 70p. TIS 50 — **10p** each. MC4016 — **25p** each. 74100N — **75p** each.
 Miniature 4.7K PRESET 10 for **25p**, 100 for **£2**.
 16 pin DIL Socket **10p**, 14 pin SIL Socket **8p**
 LED type TIL 209 Red with holder **10p** each.
 SLOTTED OPT SWITCH supplied with data — normally over **£2**. OUR PRICE **75p** each.
 ROCKER SWITCHES 2 pole c/o — **15p** each.
 Spring Action TERMINALS — normally over **30p** ea. OUR PRICE **15p** each.
 TOROIDAL TRANSFORMER 0-115V-230V Input; 13.5V-0-13.5V rated 8VA output **£1.70** each. P&P **75p**.
 Sub-min TRANSFORMER 0-120-240V Input. 12V-0-12V rated 4VA. Output **75p** each. P&P **50p**.
 L.E.D.s Standard White **12p**; Standard Yellow **15p**; Small White **8p**.

DIODES
 All new full spec. devices IN3063 BAX 13; 1S44; 1N4148; 1N3470; 1N4151
 100 off **£1.50** — 1,000 off **£10**.

MUST CLEAR
LARGE QUANTITY OF PHOTO MULTIPLIERS
 all with information. British. Approx. 2" window **£2** each. British. Approx. 5" window **£3.50** each. American. Approx. 2" window **£4** each. Special American version by RCA **£6** each. P&P all photomultipliers **£1.50** each.

BLUE THERMAL PAPER
 430ft roll 8 1/2" wide
£2 per roll P&P **£1.75**

MARCONI Signal Generator type TF144H	£225
R&S UHF Signal Generator 280-940MHz USVO	£85 ea.
R&S ATTENUATOR 0-100db 50 ohm. DPR BN18042/50	£65 ea.
R&S Power Signal Generator 0.1-30MHz SMLR BN41001	£120
R&S Direct Capacitance Meter KKH BN5201	£30
MARCONI voltmeter TF1041C	£175 ea.
MARCONI Signal Generator TF144H/4 Light front No Case	£85
R&S Z Graph type ZDD BN3562	£22.50 ea.
EHT UNIT 230V 60cs 25VA 7.5KV	£375
R&S SWOB BN4244/2/50. POLYSCOPE 1 As New	£450
STOODART Radio Interference & Field Intensity Meter complete with Power supply 375-1000MHz. No linking cable	£175 ea.
RACAL Signal Generator type 365A. AM/FM 1-320MHz	£350
B&K Automatic Freq. Response Recorder type 3302 (Beat from Osc type 1014 with Recorder type 2304)	£120 ea.
MARCONI Signal Generator TF801D/1/S	£80
MARCONI Signal Generator TF801B	£250 ea.
MARCONI UNIVERSAL BRIDGE TF1313 1/4%	£130
MARCONI AM/FM Signal Generator TF995A/2	£80
MARCONI Carrier Deviation Meter TF791C	£45
ADVANCE 1 Meter type T2	£40 ea.
OSCILLOSCOPES — wide range from	

The above is a very small fraction of the test gear we have available. The prices we believe are fair — you persuade us they should be less. We will at least have the courtesy to listen. Call and see but please phone to make sure the items are still available.

LEDEX ROTARY SOLENOIDS 115V DC. No switch assembly. **15p** ea.
DIAMOND H CONTROLS ROTARY SWITCH, Single pole 10-way. Printed Circuit Mount. New **10p** ea. 100 off **£7**.
DELAY LINE, 50 nanoseconds, 3 connections — ground-in-out. Size 2"x7/16"x5/16". New **25p** ea.
PULSE TRANSFORMER, Sub min. Size 1/2 x 5/16 x 1/4". Secondary centre tapped. New **20p** ea.
MOTOR by Inland Motor Corp DC High Torque Reversible. Usable torque at 5V. Max voltage 24V **£2.50** ea. P&P **£2**.
REMO TV TYPE MULTIPLIER, Two high voltage outputs and focus. **£1** each.
DON'T TAKE CHANCES. Use the proper EHT CABLE **10p** per metre or **£7.50** per 100 metres/drum. P&P **£2**.
PHOTOGRAPHIC LAMPS, Pearl 230V 500 watt. Screw cap **75p** ea. Box of 12 **£5.50**. P&P **£50**.
RAPID DISCHARGE capacitors 80mfd 4kV **£5** each. P&P **£2**.
MYSTERY IC PACK, Some 40 pin — good mixture — all new devices. **251c** for **£1**. P&P **50p**. You find out what they are and we will buy the information from you.
VACUUM PUMPS — TRAPS, ETC. Send for list.
DECOUPLING CAPACITORS 0.05mfd. 10V, 0.01mfd. 250V 33k. 330pf All values 100 for **£1.50**.
E.H.T. Capacitor 600pf BKV 20p each.
10-way MULTI COLOUR RIEBON CABLE. New **40p** per metre. **10 metres** for **£3**.
GEC UHF 4-button tuner **£1.50** each.
CENTRAUR 115V FANS 4 1/2" x 4 x 1 1/2" **£4.50** ea.
EX-USED equipment, tested. **80p** each.
CONTACTORS, Heavy Duty 24V DC 5 make **£1** each.
GEC UHF/VHF 6-button tuner **£2** each.
DIGITAL 24-HOUR CLOCK with built-in alarm as used in Braun Digital clocks. Silent running. Large illuminated numerals AC mains. Size 6 1/2 x 2 1/4 x 2 1/4". **ONLY £3.75** each.
931A PHOTO MULTIPLIER in stainless steel container with window and built-in resistor network **£2** each. P&P **£1**.
RANCO 250V 18A THERM OSTATS with Control knobs calibrated 50-200 degree C **£2.50** each.
SOLID STATE UHF TUNERS, 30 ac **£1** each.
BRAND REX blue wire wraps, 30 metres for **£1**. P&P **25p**.
SLIDER CONTROL 500K Log. Single track. Complete with knob. Length 3 1/2". **25p** each.
TRANSFORMERS
AUTO 240V input 115 V, 1 Amp output **£1.25** each. P&P **£1.25**.
240V input, Soc. 6V 1.86A. Size 2 1/2 x 2 x 2". Good quality **£1.50** each. P&P **£1**.
240V input, Soc. 12V 0.92A. Size 2 1/2 x 2 x 2". Good quality **£1.50** each. P&P **£1**.
240V input 12V 100MA. Size 6C x 40 x 42mm **50p** each.
240V input, Soc. 12-0-12V 50MA. Size 53 x 45 x 40mm **£1**.
115V input, Soc. 5V 250MA. Size 1 1/2 x 1 1/2 x 1 1/2" **2 for 50p**.

SEMICONDUCTORS 1N4005 — 5p; 1N4002 — 3p.
At 5p each:
 BC147, BC157, BC158, BC237, BF197, OA90, OA81, BC148B, BA154, BA243
At 25p each:
 TIP31, TIP41A, 2N296, AF139, 2TX341, BY127 10p, BF181 20p, BD239 49p, BD241 40p, MA343AT 49p, BD228 50p, BD233 & BD234 Comp Pair 25W — **80p** per pair at **50p** each.
REGULATOR TBA625, 8 to 20V in — 5V out 100MA T05 Con. **50p** each BF256C 20p.
TV AMPLIFIER TBA 120 20p each.
Integrated Circuits
 7453 5p 74474 7p 75J25 £1
 7451 5p 74451 7p SN15862 4p
 7451 5p 74538 10p MC4028 69p
 7402 12p 74502 12p 7417 14p
 7476 20p 74154 70p 7417 14p
 7495 35p 74154 70p 7441 40p
 74122 12p 74C02 16p 74C86 50p
 74C00 17p 74C04 18p 74C161 24p
 74C74 18p
MOTOROLA DUAL in Line 6 pin Opto Coupler **30p** each. Gold plate tester version **50p** each.
EPROMS 2708 £5.50 each.
SMITHS encapsulated transistorised AUDIO LOGIC WARNING DEVICES 4V-12V. Can be driven from TTL **65p** each.
ELECTROSTATIC VOLTMEETERS, 7.5KV **£8** each. P&P **£1.50**. Other ranges available. Please enquire.
TRIMMERS, Sub min 0.25 to 1.25 pf, 1 to 4.5pf 7 to 45pf. All at **6p** each.
HONEYWELL humidity controllers **50p** each.
THRYSITOR TIMER, Solid State, 15 secs adjustable (reset) in plastic relay case. Standard 7-pin base. Series delay **50p** each.
MINIATURE PC MOUNT SLIDE SWITCH, Single pole 3-way **10p** each.

VARIACS Ex-Equipment. Good condition 8 Amps **£25** ea.
20 AMPS **£35** ea.
 Some 3 phase available. Please enquire.

CRYSTALS **50p** each.
 Flat metal case — 19.2KHZ, 844 KHZ, B7G — 10MHZ

LOUD HAILERS, Transistorised hand-held, no leads. Standard internal batteries supplied. Howl Switch. **£20** ea. P&P **£2**
INFRA RED QUARTZ LAMPS, 230V 620 Watts. Size 1 3/8" x 1/4" dia. **£1.50**.
BRIDGE RECTIFIER, 2 Amp **50p** ea.
PHOTODIODE DETECTOR 4" fly leads, **25p** ea.
AMPHENOL, 17-way chassis mount edge connectors 0.1 spacing, **15p** ea.
I.E.C. Standard MAINS LEAD, Moulded (3 vertical flat pins centre offset) **60p** ea.
FANS, 115V 13 Watts. Size 3/4 x 3/4 x 1 1/2" BRAND NEW. **£4.50** ea. Secondhand **£2.50** ea.
 Miniature **MOTORS** 12V with geared wheel (8 teeth 3/16" dia). Size 1 1/4 x 1/4" dia. New **30p** ea.
MOTOR 12V DC with pulley and integral semiconductor. Speed Control. New **£1** ea.

MINIMUM ORDER £3 VALUE OF GOODS. MINIMUM P&P £1 — where P&P not stated please use own discretion — excess refunded. **CARRIAGE ALL UNITS. £5 CARRIAGE ON ALL UNITS. P&P OR CARRIAGE AND VAT at 15% on total MUST BE ADDED TO ALL ORDERS**
CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday inc.
BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome.

LARGE EX-MINISTRY SPEAKERS, OUTSIDE 15 ohm or 500 ohm. Tested. **£25** each or 5 for **£100**
 Some EHT Transformers and Capacitors available. Please enquire.
TELEPHONES 706 style black, grey or blue **£5.50** ea. 746 style black or grey **£7.50**. Older style black **£2.50** each. Discoloured grey **706 £4** ea. P&P **£1** 50p per telephone. INSERT can be used as Microphone / Earpiece (Like used as insert in telephone but superior quality) Ex-Min. Brand new wrapped **75p** each, or 10 for **£6**.
DC SERVO MOTOR 110V 2.5Amp continuous. Double shaft. Brand new 4 wire. 4 brush **£25** ea. Plus carriage.
PC Mount POTS, Wire wound with knob 200 ohm & 10ohm. **10p**
CAPACITORS at **5p** ea — 0.1 or 400V Small rec. block PC Mount German Class 3300pf, 220nf 250V Capacitor 0.1mfd 250V AC — **10p** ea.
4 DIGIT 7 SEGMENT per digit plus a figure one to the left plus a centre minus sign to the left of the figure one with decimal places between digits. Good brilliance at 1.5V, 15 connections **£2.50**

709 DIL 14-PIN OPERATIONAL AMPLIFIERS
 at **8p** each
 100 off 25% discount.

MINIATURE KEYBOARD
 Push contacts, marked 0-9 and A-F and 3 optional function keys. **£1.75** each. P&P **65p**.

MAGNETOS
 — Brand New, Boxed
 Ex-Ministry

Originally for Ministry aircraft, therefore finest quality — very reliable.
 Ridiculous **£4.75** each

STEPPING MOTORS

North American Phillips, 5 volt 3.3 Amp operation. 2 wire PPS 0-200 revs per min 0-250 used. Tested **£16** each. P&P **£1.50**.

MUST CLEAR POLARAD SPECTRUM ANALYSER

5" Display. These are supplied with STU 2 plug-in. 1 to 45 GHZ.
£95 each

TRANSISTOR INVERTOR

115V AC 1.7 Amp Input. Switching is at 20KHz. Output windings from Pot Core. Can be rewound to suit own purpose or unit can be broken for host of components. Circuits supplied. **£1.25** each. P&P **£2**.

EDDYSTONE RXS

770R used tested **£95** each
730/10 used tested **£77.50** each
940 24V inverter version. Special Government Quality vgc **£165** each

TANTALUM BEAD CAPACITORS. 4.7uf 25V. 10 off **£1**; 100 off **£7.50**. 330uf 6.3V 15p ea.

TEXAS Low Profile 40pin IC Sockets **45p** ea.
SMALL TRANSFORMER, 240V Input. Output 2 windings 12V and 24V 1 amp. **£2** each. **SO SIMPLE SO SAFE**.
 Fit a push button **CIRCUIT BREAKER** Small, compact, 3 ratings 0.8, 1.8 and 10Amp. State which one when ordering. **75p** each.
AMP METER 2 1/2" dia. Scaled 0-60. Basic 75MV FSD. Complete with external 60 Amp Shunt. **£2.50** ea. P&P **£1.50**.

ALWAYS FRESH STOCKS OF SCOPES, TEST GEAR etc.

PHONE OR CALL

STEPPING MOTORS

6/12 position with additional where the rotor is coils. Device can be used as a tacho. Diagram supplied. Will actually work on 5 volts, 12/24 recommended.
£1.50 each P&P **75p** or 5 for **£5** P&P **£1.50**.

INFRA RED IMAGE CONVERTER type 9606 (CV 144)

1 1/4" diameter. Requires single low current 3KV to 6KV supply. Individually boxed. With data.
£12.50 each P&P **75p**
 Infra Red Lamps also advertised

KEYBOARD PAD

Size 3x2 1/2 x 2 1/2" high with 12 Alma Reed Switches. Blue keys marked in green 0-9 and a star with one blank.
£4 each, P&P **£1**, or 5 for **£15** P&P **£2**.

CHILTMHEAD LTD
NORWOOD ROAD, READING **TELEPHONE NO. READING 669656**
 (2nd turning left past Heading Technical College in King's Roac then first right — look on right for door with "Spoked Wheel")

CLEF KITS



High Quality Electronic Musical Instruments under the personal supervision of Specialist Designer A. J. BOOTHMAN.

JOANNA 72 & 88 PIANOS

Six and 7 1/4 Octave Electronic Pianos with unique Touch Sensitive Action as used in the P. E. JOANNA, which electronically simulates piano key inertia — a feature not available in any other design. Build this widely acclaimed professional instrument, for either Domestic or Stage use, from our top quality Component kits.

SIX OCTAVES — £207.00
7 1/4 OCTAVES — £232.00

P.E. STRING ENSEMBLE

The versatile String Synthesizer with a fantastic sound at an economic price. Split Keyboard facility with a range of impressive voices.

COMPONENT KIT — £169.00

Back up TELEPHONE advice is available from the designer to supplement the clear instructions included with the above Kits.

P.A.s — SPEAKERS — CABINETS

Units can be supplied to add to the Component Kits, including Domestic or Stage Cabinets and portable tubular legs.

P.E. MASTER RHYTHM

A User Programmable Rhythm Generator for up to 24 selectable patterns on Eight tracks. Three instrumentation settings select from twelve instruments, and sequence operation gives up to 16 Bar pattern groups.

COMPONENT KIT—£79.00

ELECTRONIC ROTOR

Two-speed organ rotor simulator plus a three-phase chorus generator. Easily integrated with existing organ.

COMPONENT KIT £89.00.

KEYBOARDS (SQUARE FRONT)

49 NOTE C-C £23.80

73 NOTE F-F £37.00

88 NOTE A-C £45.00

All Keyboards are easily cut to provide your required length and compass. Quantity enquiries welcome.

BUILDING SERVICE

We are specialists in Electronic Piano Manufacture and can build your Piano for you — see lists.

INFORMATION

Please send S.A.E. quoting items of interest. Telephone BARCLAYCARD orders can be accepted. All prices include V.A.T., carriage & Insurance.

Showroom:

44a Bramhall Lane South

EXPORT

Enquiries welcome — in Australia please contact JAYCAR (Sydney).

CLEF PRODUCTS (ELECTRONICS) LIMITED

(Dept. E.T.I.), 16 Mayfield Road, Bramhall, Cheshire, SK7 1JU. 061-439 3297

Rapid Electronics

Guaranteed same day Despatch

- Quality Product
- Free Catalogue

- Vast Stocks
- Competitive Prices

Pack	Item	Price	Pack	Item	Price
A10	10 PP3 battery leads	50p	F11	10 BC108 trans.	90p
A72	10 3.5mm jack plugs	80p	F26	10 2N3704 trans.	80p
A73	10 3.5mm jack sockets	80p	F27	10 2N3819 trans.	190p
A74	10 Std. jack plugs	130p	H11	20 1N4002 diodes	75p
A75	10 Std. jack sockets	170p	H50	20 0A91 diodes	110p
A84	10 5 pin 180 DIN plug	120p	H60	100 1N4148 diodes	180p
A85	10 5 pin 180 sockets	100p	H70	5 C106D thyristors	200p
C20	10 Min. slide switch	130p	J10	20 0.2in. red LEDs	170p
C30	10 Push to make sw.	130p	J15	50 0.2in. red LEDs	400p
C31	10 Push to break sw.	170p	J20	100 0.2in. red LEDs	750p
C40	Pair Ultrasonics	350p	J30	20 0.2in. green LEDs	280p
C32	Submin. SPST toggle	60p	J50	20 0.2in. yellow LEDs	280p
C33	Submin. DPDT toggle	80p	J80	4 FND500 CC displays	350p
C50	20 Texas 8 pin sockets	170p	K5	5 741 op amps.	90p
C51	20 Texas 14 pin sockets	200p	K40	1 LM324 op amp.	50p
C52	20 Texas 16 pin sockets	220p	K20	5 CA1340 op amps.	225p
E10	Resistor kit. 10 ea value 1W 4.7Ω 1M.650 resistors	480p	K85	5 NE555 timers	110p
E34	10 10u 25V radial elec	50p	L8	5 4011 CMOS	130p
E37	10 100u 25V radial	75p	L9	4013 CMOS	40p
E44	10 1u 35V tantalum	100p	L11	4017 CMOS	75p
E54	10 0.1 C280 polyester	50p	L19	4049 CMOS	45p
			M20	Dalo pen	80p

For quality components at competitive prices by return of post Rapid Electronics must be your first choice!


All prices include VAT. Please add 50p postage and packing on orders below £10. Send SAE for our complete catalogue.

Rapid Electronics Limited
Hillcroft House, Station Road, Eynsford, Kent

QUALITY DOES NOT HAVE TO COST VERY MUCH!

ALL PRICES INCLUDE VAT

BECKER Hi-Fi Speakers

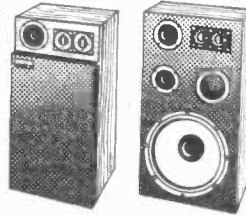


All models multi-speaker systems

With controls, attractive woodgrain finish. RMS ratings for 8 ohm.

- 10.35 10" 3 speaker system 35 watts 23" x 13" x 10 1/2" £75.00 pair
- 12.45 12" 4 speaker system 45 watts 26 1/2" x 14 1/2" x 11" £85.00 pair
- 12.60 12" 4 speaker system 60 watts 26 1/2" x 14 1/2" x 11" £99.00 pair
- 15.90 15" 5 speaker system 90 watts 28" x 17 1/2" x 11 1/2" £130.00 pair

(UK c/p £5.45 pair)

On Demonstration to callers.

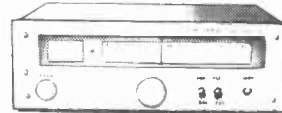

SCOTT T516 STEREO FM/AM TUNER

HIGH QUALITY STEREO FM/AM TUNER BY SCOTT OF USA.

Overall size 5" x 14 1/2" x 12". Brand new and fully guaranteed at a special low price. (C/P £1.55)

£38.95

On demonstration for callers.




JVC BELT DRIVE TURNTABLE

JVC TURNTABLE WITH FREE AUDIO TECHNICA AT100 STEREO CARTRIDGE.

- * S' shaped tone arm
 - * Belt drive
 - * 12" Platter * Calibrated counter-balance weight
 - * Anti-static device
- Size 12 3/4" x 15 1/4" (C/P £1.55)

£29.95

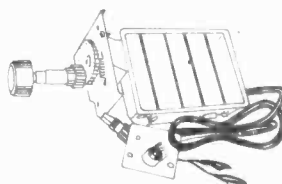

TV SOUND FROM YOUR HI-FI

High quality TV sound converter plugs into aerial socket of your FM tuner. 9 volt battery operated (battery not supplied). Nothing to look at... but just listen!

(UK Post etc. 50p)

On Demonstration for callers.

(As reviewed in 'Popular Hi-Fi' July 1979) £8.50

1000's SOLD



SEAS SPEAKER KITS

8 ohm



Professional sound hi-fi speaker kits with high sensitivity (89-92dB). Extended frequency response (223' 50-20kHz, 253' 35-25kHz). Designed and made in Scandinavia to the highest quality. All supplied with complete cabinet plans, tweeters/crossovers/leads etc. * On Demonstration to callers.

- * HI-FI 223. 30/45 watt 3 speaker 8" system £43.50 pair
- * HI-FI 253. 60/100 watt 3 speaker 8" system £34.50 each
- * HI-FI 403. 60/100 watt 3 speaker 10" system £44.50 each
- * HI-FI 603. 80/150 watt 3 speaker 8" system £64.50 each

(UK C/P £2.50)

COMPLETE RANGE OF SEAS

CHASSIS SPEAKERS ETC

ALWAYS IN STOCK

ALSO STOCKISTS FOR

AUDAX, GOODMAN'S, KEF, PEERLESS ETC.

PIEZOELECTRIC TWEETERS



Clean sound, very low distortion tweeters. No crossover required. Suitable up to 100 watts — more in series.

- 1 Mid range horn for disco/pa/groups £6.95
- 2 Tweeter horn for hi-fi/disco/pa £5.50
- 3 Popular hi-fi and disco £4.40
- 4 Flat type hi-fi £3.50

On Demonstration to callers.

UK P/P 50p (up to 4 items).

STEREO ACCESSORIES

- * GE1305 Hi-Fi frequency equaliser £62.95
- * 1987 Economy version £49.95
- * APM 200 Peak programme meter (twin scale) £39.95
- * MS3219 Twin Scale audio output meter £12.95
- * MC350 Tape echo chamber £58.95

FREE CATALOGUE

Large range of speakers/stereophones/microphones/mixers/PA equipment etc — and much more!
Plus huge range of test equipment.
ALL PRICES INCLUDE VAT
SEND LARGE 17x11 SAE
ALL PRICES CORRECT AT 1.11.80 E&D


AUDIO ELECTRONICS Limited

301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND.
TELEPHONE 01-724 3564 OPEN 9-6 Mon-Sat

ORDER BY POST OR TELEPHONE WITH BARCLAYCARD/ACCESS OR CALL IN AND SEE FOR YOURSELF



MUSICAL

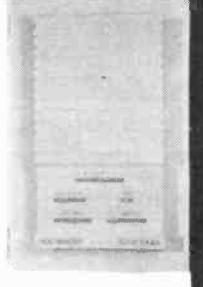

DOOR BELL
This is a computerised doorbell. You can set it to play any one of 24 tunes (27 tune model is also available). It runs on batteries and has controls for volume and tempo. There is a test button as well. It can be easily connected to your existing bell push and there is facility for connecting a second bell push (back door) which plays different tunes to that of front door.

£13.95

COMPUTE-A-TUNE
Compute-a-tune actually memorises tunes (up to 32 notes), played on its 2 octave keyboard and replays them with added effects. It has four pre-programmed tunes and a jack socket for playing through external amplifier.

£19.95

ULTRA SLIM DUAL-TIME MELODY ALARM
Super slim dual-time musical alarm and 1/10th sec chronograph with lap time. Only 5mm case thickness. Normal display is hours, minutes, seconds or date, day of the week, alarm and p.m. indication. Plays "Yellow Rose of Texas." (Chrome colour)

A208S £13.50

ULTRA SLIM ALARM CHRONOGRAPH
WITH 12/24 HOUR DISPLAY
Only 6.5mm thick including a special battery hatch. Normal display is hours, minutes, seconds, day of the week and p.m. indication. Display mode can be either 12 or 24 hour cycle. Other features include 24-hour alarm, 1/10th second chrono with lap time and backlight. (Chrome colour)

A201S £13.50

LADIES MUSICAL ALARM
Ladies' 6-digit Musical Alarm. Plays "Jesu Joy of Man's Desiring." Normal display is hours, minutes, seconds, day of the week and alarm indication. Other features include 4-year auto calendar, backlight and fully adjustable stainless steel bracelet. (Chrome colour)

A207S £11.95

DUAL TIME ALARM CHRONOGRAPH
Incredible value for money. Sold elsewhere for £19.95. Normal display is hours, minutes, seconds or date, day of the week, p.m. and alarm indicator. Other features include, 2nd time zone, 1/10th sec. chrono, backlight and 24-hours alarm. Buy now while the stock lasts. (Chrome colour)

LM20 £10.95

MUSICAL ALARM CHRONOGRAPH
Normal display is hours, minutes, seconds, day of the week and alarm indicator. Other features include, 1/10th sec chronograph with lap time facility, month, date, backlight, 24-hours musical alarm. Plays "FUR ELISE"

A205S £13.50

LADIES' SNOOZE ALARM
Exceptionally good value for money. Normal display is hours, minutes, p.m. and alarm on indications, other features include 4-year auto calendar, backlight, 24-hour alarm with Snooze facility, fully adjustable, stainless steel bracelet. (Chrome colour)

LM102 £8.50

MEMORY CALENDAR ALARM-CHRONO
Memory calendar to year 2009. 24-hour alarm with 10 minute snooze facility, 1/100th sec. chrono with split and lap time. Displays hours, minutes, seconds or date, day of the week, flag and alarm indicator. It has fully-adjustable stainless steel bracelet. (Chrome colour)

LM73 £14.95

GENT'S 6 DIGITS ALARM WITH DAY OF THE WEEK
Normal display is hours, minutes, seconds, day of week, p.m. indicator and alarm indicator. (Model A203L has extra large digit for better readability). It has a very useful 24-hour repeat alarm and 4-year auto calendar. (Chrome colour)

A203S £7.95

LADIES' SUGAR COATED DRESS WATCH
Ladies' 9 function LCD watch. Hours, minutes, seconds, month, date, backlight Auto date/time display mode, 4-year auto calendar. This watch has an optional auto date/time display mode. In this mode time and date is alternatively displayed every 2 seconds. (Chrome or gold)

LM39 £7.95

AKHTER INSTRUMENTS LTD. 11-15 BUSH HOUSE HARLOW, ESSEX CM18 6NS Tel. 0279 414464

PHONE YOUR BARCLAYCARD OR ACCESS NUMBER FOR IMMEDIATE DESPATCH 24-hour service

BARCLAYCARD

MOTORS. 1.5V Model motors 22P. Sub. min. Big inch. 115V DC 3 rpm motor 32p. Replacement 8 track 12V DC motors 55p. Geared mains motors. 2 1/2 rpm. 75p. 115V AC 4 rpm motor 95p. Cassette motors. 5-8V DC ex. equip. 70p. 9V DC Cassette motors 95p. 6V Cassette motors. new standard jap. type £1.25.

BUZZERS. Miniature solid state type. 33x17x15mm. 70db at 3 foot 15ma drain. operates 4-15V DC 75p. each. LDUO 12 volt buzzer 50x30mm. 63p. Carriers 12V DC Miniature alarm sirens £7.55. 12V DC SIREN all metal rotary type. high pitched wail. £8.50. Rotary alarm siren. 12V DC. red plastic unit with mounting bracket. 58x75mm. £4.50.

RELAYS. 2 types both operate on 12V DC. sealed plastic case types. 1-350 ohm with 2 make 5 amp contacts 75p. 2-1,000 ohm with 2 changeover 1 amp contacts 75p.

SPECIAL OFFER SEMICONDUCTORS. 2N5062 SCR 18p. 8X5D4 opto isolator 25p. CA3130 95p. CA3020 45p. TDA1151 25p. 741 22p. 723 35p. NE555 24p. NE556 50p. CD4069 15p. IN4005 10 for 35p. BD238 28p. BD439 28p. 7415 35p. 74414 75p. TIL305 alpha numeric display £2.50. MAX93A 3mm LED displays 45p. Min. LDRs 30p. LEDs 0.2" CLEAR 15p. GREEN 12p. RED 10p. Infra-red clear LED 30p. MPU131 PUTs. 40V. 200ma. 375mW 15p. 2N3773 £1.70. Texas R1038 [T03] Power trans. 50p. TAG4443 SCR 45p.

NEW STOCK ITEM - We are now stocking Expo mini hand-held drills. these are a precision British-made tool, ideal for P.C. board drilling, model makers etc. They operate on 12V DC. Drill kit supplied in plastic hinged case, with drill and 21 accessories, drills, sanders, reamers, buffers, etc. complete kit only £14.25. Drill only £7.25. Dr.H stand to suit vertical drill press £12.95 (postage 60p).

RECORDING TAPE. Low noise mylar. supplied unboxed: 7" 1200' £1.00. 7" 1800' £1.75. 10" 3500' £5.00.

JACKSONS C804 50 PF variable tuning condensers. Standard 1/4" spindle. 50p each.

TOOLS. SOLDER Sucker, good section, lellon nozzle. £4.99. Side cutters 5" £1.45. Pliers 5" £1.45. NEON DRIVER 8" LONG 50p. MIYAMA 16 pin IC test clip £1.85. 5 PIECE precision screw and driver sets. individual handles. £1.05. JUMPER TEST LEAD SETS 10 pairs of leads with insulated crabs each end 90p. CRIMPING TOOL, a combination type for crimping red, blue and yellow terminations also incorporates a wire stripper (6 gauges) and wire cutter. insulated, handles. only £2.30.

MICROPHONES. Min. Tie pin. Om. uses det. aid battery (supplied) £4.95. Low cost condenser ECM105 Omni. 600ohms, on/off switch standard jack plug £2.95. EM507 Condenser. uni. 600ohms. 30-18kHz. highly polished metal body. £7.95. DYNAMIC stick microphone dual imp. 600ohms or 20k. 20-15kHz. attractive black metal body. £7.75. EM506 Condenser. cardioid. uni. 600ohms or 50k. heavy chromed copper case. £12.95. DYNAMIC P.A. Mike. mobile radio etc. thumb switch 50k imp. £2.75. CASSETTE replacement microphone with 2.5x3.5 plugs £1.35. INSERT crystal replacement 35x10mm 40p. GRUNDIG Electret inserts. with built in FET preamp 3-6V DC. £1.00.

SPECIAL OFFER DEC TYPE BREADBOARDS. Micro DEC "A" with 2 16 pin DIL carriers £3.95. Approximately half original selling price.

FLUORESCENT LAMPS. For caravans, boats, etc. welta fitting, perox. diffuser. 12V DC. 8 watts. on/off switch £4.95.

COPPER LAMINATED PRINTED CIRCUIT BOARD. Fibreglass Single Sided type (approx. 2mm thick) 150x50mm 40p. 200x90mm 55p. Double-sided Fibreglass 1mm thick. 180x135mm 45p. PAXDLIN BASED TYPE: (2mm thick). 180x135mm 40p. 200x200mm 50p.

TAPE HEADS. Mono cassette. £1.75. Stereo cassette £3.90. Standard 8 track stereo £1.95. BSH MM 1330 1/4 track 50p. BSR SRP90 1/4 track £2.10. TD10 dual head assembly 2 heads both 1/4 track R/P with built in erase £1.25.

SWITCHES. Sub. min. Toggle. SPST 8x5x7mm. 42p. DPDT [8x7x7] 55p. DPDT Centre off [12x11x9mm] 77p.

PUSH SWITCHES [16x6x6mm]. red top. push in make 15p each. push on break version black vinyl 17p each.

SLIDE SWITCHES all OPOT 15x8x12mm 13p. 16x11x9mm 13p. 22x13x8mm 13p. 22x13x8 centre off 14p. Multipole slider double actha [12 tags] 29x9x11mm 25p.

ROTARY SWITCHES (w/keys) 3PAW. 4PW. 2P5W and 1P12W all 35p each.

16 pin D.I.I. SWITCHES only 42p each.

RIBBON CABLE 8-way single core miniature 22p per metre.

INCAOS. AA size 1.2 volts 500ma £1.10 each.

MOTOROLA PIEZO ELECTRIC TWEETERS
3" direct radiating type £3.65

PIEZO TWEETERS, require no crossover and can be used with systems up to 100 watts. Frequency response 3.8 to 28kHz.

MULTI-SOUND HORN SYSTEMS. ideal disco use. 6 controls. will give 81 various sounds. supplied with P.A. term. speaker. operates on 12V DC £19.50.

RANK ARENA stereo cartridge pre-amplifier modules: suitable for magnetic cartridges. new, supplied with connection details. £1.95.

FINNED HEATSINKS. Supplied undrilled. 4mm thick. 27mm high. 75x124mm 60p. 150x124mm 95p. Smaller version 27mm thick. 75x108mm 48p. TRANSISTOR SOCKETS T05 or T018 9p each. T03 type 15p each.

ALUMINIUM PROJECT BOXES. 18 S.W.G. with fitted lid and screws. AB1 3x2x1 52p. AB2 4x3x1.5m 62p. AB3 4x3x2m 66p. AB4 6x4x2m 74p. AB5 6x4x3m 92p. AB6 8x6x2m £1.05. AB7 8x6x3m £1.25.

ANTEX SOLDERING IRONS. All 240V AC. Model C 15 watts £3.95. Model ICX 17 watts £3.95p. Model X25 25 watts £3.95p. ST3 SOLDERING IRON STAND. suits all Antex irons £1.65.

TRANSUDERS. REC/SENDER. 40KHZ 13.50 pair.

TRANSFORMERS. All 240V DC primary (postage per transformer is shown in brackets after price). MINIATURE RANGE 6-0-6 100ma. 9-0-9 75ma. 12-0-12 50ma all 79p each [15p]. 12V 200ma 75p [15p]. 0-6-0 5 280ma £1.20 [20p]. 6V 500ma £1.10 [22p]. 12V 2A £2.35 [45p]. 12-0-12 2A £2.75 [50p]. 15-0-15 1A £2.25 [45p]. 30-0-30V 1A £2.85 [54p]. 20-0-20V 2A £3.65 [54p]. 0-12-15-20-30V 2A £4.75 [54p]. 20V 2.5A £2.35 [54p].

TRIAc XENON PULSE TRANSFORMERS. 11 [6P0 style] 32p. 11p15 1 sub. mm. pcb mounting 65p.

PROJECT BOXES. Sturdy ABS black plastic boxes with brass inserts and lid. 75x55x35mm 55p. 95x7x35mm 75p. 115x9x37mm 87p.

VERO HAND HELD BOX. White ABS. 24in x 3.7 in tapered. with screws 68p each.


VERO POTTING PLASTIC Boxes with lid and screws 70x50x20mm. black. 43p each.

KRT101 M/METER. 1,000 opv. 1KV AC/DC Volts. 150ma DC current. Resistance 0-2.5k. 0-100k. £4.35.

NH55 M/METER. 2,000 opv. 1KV AC/DC Volts. 100ma DC. Resistance 0-10k. 0-1 MEG. £5.50.

YN360 M/METER. 20,000 opv. 1KV AC/DC Volts. 250ma DC. 4 resistance ranges to 20 Meg. also has built-in transistor tester with leakage and gain ranges £12.50.

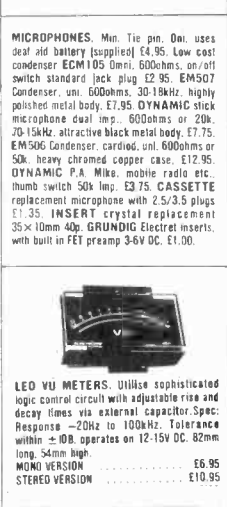LED VU METERS. Utilise sophisticated logic control circuit with adjustable rise and decay times via external capacitor. Specs: response -20db to 100kHz. Tolerance within ±0.8. operates on 12-15V DC. 82mm high. 54mm high. MONO VERSION £6.95 STEREO VERSION £10.95



16 pin D.I.I. SWITCHES only 42p each.

RIBBON CABLE 8-way single core miniature 22p per metre.

INCAOS. AA size 1.2 volts 500ma £1.10 each.

TRANSFORMERS. All 240V DC primary (postage per transformer is shown in brackets after price). MINIATURE RANGE 6-0-6 100ma. 9-0-9 75ma. 12-0-12 50ma all 79p each [15p]. 12V 200ma 75p [15p]. 0-6-0 5 280ma £1.20 [20p]. 6V 500ma £1.10 [22p]. 12V 2A £2.35 [45p]. 12-0-12 2A £2.75 [50p]. 15-0-15 1A £2.25 [45p]. 30-0-30V 1A £2.85 [54p]. 20-0-20V 2A £3.65 [54p]. 0-12-15-20-30V 2A £4.75 [54p]. 20V 2.5A £2.35 [54p].

TRIAc XENON PULSE TRANSFORMERS. 11 [6P0 style] 32p. 11p15 1 sub. mm. pcb mounting 65p.

PROJECT BOXES. Sturdy ABS black plastic boxes with brass inserts and lid. 75x55x35mm 55p. 95x7x35mm 75p. 115x9x37mm 87p.

VERO HAND HELD BOX. White ABS. 24in x 3.7 in tapered. with screws 68p each.

VERO POTTING PLASTIC Boxes with lid and screws 70x50x20mm. black. 43p each.

35 WATT RMS STEREO SPEAKER SYSTEM. Woofer, Squawker, Tweeter (controlled) in black heavy alloy cabinets. 7 1/2" x 4 1/2" x 4 1/2" £35.75 pair P&P £1.95.

SPECIAL OFFER DEMAGNETIZER. Curved probe type. suitable for reel to reel or cassette machines. operates on 240V AC only £1.95.

POWER SUPPLIES. Switched type plugs into a 13 amp socket has 3-4, 5-6, 7.5 and 9 volts DC out at either 100 or 400ma switchable £3.45. HC244R stabilised power supply 3-6-7.5-9V DC at 400ma. has polarity reversing and on off switch and is fully regulated to give exact voltage from no load to maximum current 15.50.

TRANSFORMERS. All 240V DC primary (postage per transformer is shown in brackets after price). MINIATURE RANGE 6-0-6 100ma. 9-0-9 75ma. 12-0-12 50ma all 79p each [15p]. 12V 200ma 75p [15p]. 0-6-0 5 280ma £1.20 [20p]. 6V 500ma £1.10 [22p]. 12V 2A £2.35 [45p]. 12-0-12 2A £2.75 [50p]. 15-0-15 1A £2.25 [45p]. 30-0-30V 1A £2.85 [54p]. 20-0-20V 2A £3.65 [54p]. 0-12-15-20-30V 2A £4.75 [54p]. 20V 2.5A £2.35 [54p].

TRIAc XENON PULSE TRANSFORMERS. 11 [6P0 style] 32p. 11p15 1 sub. mm. pcb mounting 65p.

PROJECT BOXES. Sturdy ABS black plastic boxes with brass inserts and lid. 75x55x35mm 55p. 95x7x35mm 75p. 115x9x37mm 87p.

VERO HAND HELD BOX. White ABS. 24in x 3.7 in tapered. with screws 68p each.

VERO POTTING PLASTIC Boxes with lid and screws 70x50x20mm. black. 43p each.

35 WATT RMS STEREO SPEAKER SYSTEM. Woofer, Squawker, Tweeter (controlled) in black heavy alloy cabinets. 7 1/2" x 4 1/2" x 4 1/2" £35.75 pair P&P £1.95.

SPECIAL OFFER DEMAGNETIZER. Curved probe type. suitable for reel to reel or cassette machines. operates on 240V AC only £1.95.

POWER SUPPLIES. Switched type plugs into a 13 amp socket has 3-4, 5-6, 7.5 and 9 volts DC out at either 100 or 400ma switchable £3.45. HC244R stabilised power supply 3-6-7.5-9V DC at 400ma. has polarity reversing and on off switch and is fully regulated to give exact voltage from no load to maximum current 15.50.

KRT101 M/METER. 1,000 opv. 1KV AC/DC Volts. 150ma DC current. Resistance 0-2.5k. 0-100k. £4.35.

NH55 M/METER. 2,000 opv. 1KV AC/DC Volts. 100ma DC. Resistance 0-10k. 0-1 MEG. £5.50.

YN360 M/METER. 20,000 opv. 1KV AC/DC Volts. 250ma DC. 4 resistance ranges to 20 Meg. also has built-in transistor tester with leakage and gain ranges £12.50.

HANDY BENCH VICE. 1" jaw opening £2.95. 6" motorised alarm bells. 65ma. 88dB £9.95.

Terms. Cash with order (official orders welcomed from colleges etc) 30p postage please unless otherwise shown. VAT inclusive prices. S.A.E. for illustrated lists.

PROGRESSIVE RADIO
31 CHEAPSIDE, LIVERPOOL L2 2JD
ALL ORDERS DESPATCHED BY RETURN POST

MIGHTY NINETY PACKS

SUPER VALUE PACKS ALL AT 90p EACH
POSTAGE 15p PER PACK UP TO FOUR PACKS
FIVE OR MORE POST FREE
BUY SIX PACKS AND GET A SEVENTH PACK FREE!

MN1. 300 ¼-watt Resistors pre-formed for P&C Mtg.
MN2. 200 ¼ & 4-watt Resistors.
MN3. 100 1 & 2-watt Resistors.
MN4. 50 Wirewound Resistors.
MN5. 100 metal oxide Resistors. 1%, 2% and 5%
MN6. 12 asstd. potentiometers.
MN7. 25 asstd. skeleton pre-set Resistors.
MN8. 50 asstd. Electrolytic Capacitors.
MN9. 100 asstd. Ceramic Capacitors. Ptte, disc, tub and monolithic etc.
MN10. 100 mixed capacitors. Polyester, Polystyrene, Metallised, Radial and Axial types.
MN11. 20 asstd. Silve Mica Capacitors.
MN12. 8 Tantalum Bead Capacitors (useful values).
MN13. 20 asstd. Transistors. BC. 2N Series + Power etc.
MN14. 40 IN4148 Diodes.
MN15. 5 Light Sensitive Devices.
MN16. 20 min. wire-ended Neons.
MN17. 2 12-volt Relays. Ex nearly new equip.
MN18. 3 Encapsulated Reed Relays. 9-12v. coil, d-pole and t-pole.
MN19. 2 24-volt Relays. Ex nearly new equip.
MN20. 1 240-110 to 12-volt. 100ma Transformer.
MN21. 1 240-110 to 24-volt 100ma Transformer.

MN22. 8 2" Led s with clips, 4 red, 2 yellow, 2 green.
MN23. 116 asstd. screws, nuts, washers, self-tappers etc.
MN24. 100 asstd. small springs.
MN25. 50 asstd. pop rivets.
MN26. 50 asstd. insulated crimps.
MN27. 200 items, grommets, spacers, cable markers, plastic screws, sleeving, tie wraps etc.
MN28. 20 asstd. fuses. 1¼" 20mm etc.
MN29. 75mts equipment, wire, asstd. colours and sizes.
MN30. 3 x 2m length 3 core, mains cable.
MN31. 12 asstd. trimmer capacitors compression film. Air-spaced etc.
MN32. 15 30pF Beehive trimmers.
MN33. 20 coil formers, ceramic, plastic, reed relay etc.
MN34. 25 min. glass reed switch.
MN35. 10 asstd. switches, toggle, slide micro etc.
MN36. 10 ex equipment panel lamps (no rubbish).
MN37. 10 asstd. audio connectors. Din phono etc.
MN38. 1 PCB with triac control IC data inc.
MN39. 1 oscillator PCB loads of components. (no data).

PLEASE QUOTE NO. OF PACKS WHEN ORDERING

CHORDGATE LTD.

75 FARINGDON ROAD
 SWINDON, WILTS.
 Tel. Swindon (0793) 33877
 RETAIL SHOP AT ABOVE ADDRESS

SEE US
 AT
 BREADBOARD
 80

CALCULATORS

ALL EQUIPMENT NEW, BOXED AND FULLY GUARANTEED
 Order with confidence and pay no more

PROGRAMMABLE SCIENTIFIC


Casio FX501P	£46.95
Casio FX502P	£66.95
Casio FA1 Adaptor-Cassette Interface	£19.95
Casio FX501P with FA1	£64.95
Casio FX502P with FA1	£84.95
Texas T157	£28.95
Texas T158	£67.95
Texas T158C	£86.95
Texas T159	£176.95
Texas PC100C	£176.95
Sharp EL5101 16 Digit	£46.95
Sharp EL5100 24 Digit	£56.95
SPECIAL OFFER	
Texas T158C with PC100C	£250.00
Texas T159 with PC100C	£350.00
Includes mains adaptor/charger	

TEXAS ACCESSORIES in stock e.g. Libraries, etc

Maths/Utilities, Applied Stats/Electrical Engineering	Each	£25.95
Surveying, Structural Engineering	Each	£62.95
PL100C Rolls 10 off		£21.95
Battery Packs State model or BP number		£6.95
Texas T1 Programmer		£51.95
Texas TI51 111		£28.95

QUALITY WITH FULL GUARANTEE

See Page 11 September E.T.I

	ML 71	£21.95
	ML 81	£21.95
	ML 82	£19.95
	ML 90	£19.95
	ML 720	£15.95
	ML 831	£12.95
	ML 860	£15.95

CASIO CLOCK CALCULATORS

MQ6	£17.95	AQ 2200	£18.95
AQ1600 new model	£15.95	MQ 12	£18.95

CASIO SCIENTIFICS

8 DIGIT

FX68	£18.95	FX100	£14.95
FX81	£13.95	FX510	£18.95
FX330	£15.95	FX3200	£20.95
FX2600	£18.95	National NS108	£17.95

10 DIGIT

* ALL PRICES NOW INCLUDE V.A.T., POST AND PACKING *
 Cheque with order or C.O.D. 75p. Extra up to £100

FREEPOST NO STAMP NEEDED. S.A.E. WITH ENQUIRIES PLEASE
 CALCULATOR SALES & SERVICE, Redditch, Worcs. FREE POST
 B98 0BR

ETI DECEMBER 1980

Special Offer -
£2 OFF!

2

SUPERB NEW KITS!



1st
 Top of all systems
 tested by independent
 national authority
 July '79

C300/ES200

high performance electronic ignition, to add power, economy, reliability, sustained smooth peak performance, instant all weather starting, to your car.

Surefire has sold in its thousands in ready made form from big name accessory firms, but it is now available in quality kit form to fit all vehicles with coil ignition up to 8 cylinders

ES200. A high performance inductive discharge ignition incorporating a power integrated circuit (special selection) electronic variable dwell circuit (maximises spark energy at all speeds) pulse processor (overcomes contact breaker problems) Coil governor (protects coil). Long burn output. Negative earth only. Compatible with all rev. counters

C300. In it's ready built form (C3000) it came top of all systems tested by an independent national authority July '79. A high energy capacitive discharge ignition incorporating a high output short circuit proof inverter, top grade Swedish output capacitor, pulse processor circuit, transient overload protection. Fast rise bidirectional output ideal for fuel injection, sports carburation, oily engines. Compatible with most rev. counters. (Low cost adaptors available for rare cases Application list enclosed with each kit. Note: Vehicles with Smiths Jaeger rev. counters code RVI on dial will require adaptor type TCI)

What's in the kits. Surefire's own precision anodised aluminium extruded case. P.C. mounted security changeover switch, static timing light. Special selection Motorola semi-conductors. Capacitors, resistors etc. selected after 5 years experience. Glass fibre pcb, solder, complete down to last washer. Fully illustrated comprehensive instructions and full technical back up service



Suretron Systems (UK) Ltd. Dept. ET19
 Bayer Buildings, Lower Bristol Road, Bath, BA2 3EF. Tel: Bath (0225) 332317

Name

Address

Phone order with Access Barclaycard
 VAT and P & P inc


Quantity
 required

ES200: Neg	£13.95	£11.95	
C300: Pos	£17.95	£15.95	
C300: Neg	£17.95	£15.95	
Tacho Adapt. TCI		£3.90	

Enclose
 cheq PO s

£
 Cheq No

Quantum Electronics

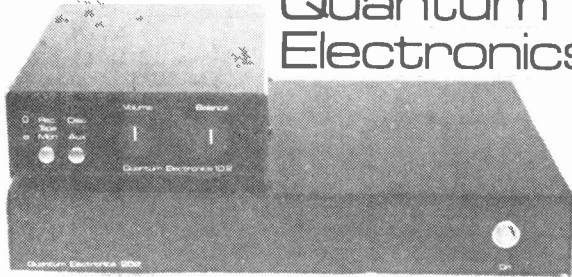

The 102, shown above, must be the most cost-effective pre-amp available, catering for auxiliary, 2 or 3 head tape and providing a perfect match for any cartridge, moving coil or magnetic, by using our unique low-cost matching card to define the sensitivity and cartridge loading. Prudent choice of components and elegant circuitry give outstanding objective and subjective performance (see Popular Hi-Fi August). The module used in the 102 is available separately, as are suitable mains supplies and moving coil head amp/modules. There are two matching stereo power amp kits which are supplied with built and tested circuit boards, requiring only straightforward assembly and point to point wiring. The new ready-built 'D' versions feature separate d.c. supplies for each channel and other refinements which elevate their performance into the super-fi class but which are not incorporated in the kits. Our power amp modules and supplies below enable an amp of high specification to be constructed.


★ COMING SOON: ACTIVE CROSSOVERS ★

102 pre-amp: module only £63.50; built £92.00

45W channel: kit, P2, £100.50; built, 202D £151.00
110W/channel: kit, P4, £126.00; built, 204D £185.00

POWER AMP MODULES AND SUPPLIES

QE 1708, 1704, £31.96
QE 1004, £20.69

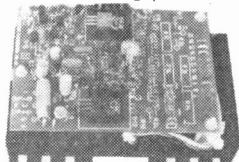


M1504, 1508, £35.79 M2603, £50.28
M854, £26.00 M2308, £53.96

We offer a wide range of modules to suit virtually any application with an honest specification unbeatable at the price. They are available in both the popular medium duty 'L' bracket format for 60 to 170 W 'module rating' (150W r.m.s.) and also in high dissipation versions using various heatsink combinations. Correct choice of module allows reliable continuous operation at up to 300W r.m.s. (M2603/M85/3 ohms) without premature cut off or the need for external circuitry. Matching toroidal power supplies with single and double d.c. sections are available. Exemplary specification includes the less than 0.1% at 1kHz; 30V/uS slew rate; noise below 110dB; integrity protected against overload and high d.c. output offset; stable into any load.

★ EXCELLENT TRADE PRICES ★

We also build rack mounting power amplifiers, sub-assemblies and special modules to individual specifications. Please telephone with your enquiry.

NEW DELUXE SPEAKER KITS

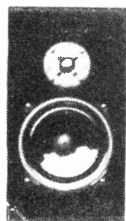

SYSTEM 1
£69.00



SYSTEM 2
£89.00



SYSTEM 3
£159.00



SYSTEM 4
£359.00

PRICES PER PAIR INC. BAFFLES

Have you wondered why the existing sources of speaker kits offer a bewildering choice of systems, particularly combinations of 200mm bass unit and tweeter? Don't they know which ones are best? If so, why bother with the rest! Well we have sorted out these super kits so you can order in confidence, knowing you get our full endorsement of their performance and value. The kits incorporate professionally finished front baffles with the drive units already mounted so all the fiddly work is done for you. All that is left to do is to make a simple box. Crossover networks, foam and terminals are included. Systems 1 and 2 use a 200mm bass and 25mm dome tweeter from Son Audax, System 2 being a reflex design that we enthusiastically recommend. System 3 is a competitive 3-way I.B. using Seas bass and mid with a Son Audax tweeter, cleverly incorporating a stand at the bottom of the enclosure, as does System 4, undoubtedly the best kit on the market, using a Volt 250mm bass driver with a 250mm ABR on the rear baffle (also supplied), a modified Peerless mid and Son Audax tweeter. We will also be retailing selected drive units at competitive prices, e.g. Son Audax 200mm bass, 20B25J4 £13.50; 25mm tweeter, HD100D25, £9.00. All our prices include V A T and delivery. Export no problem — please send for a specific quote by return. All equipment can be wired for 110V mains. Please send a large S A E. or dollar bill for our full information and review reprints.

SWEDEN: LJUD HI-HI, SÖDRA KASERNGATAN 14 B, S291 33 KRISTIANSTAD.
USA: OX DISCO, BOX 123, CLAYMONT, DELAWARE 19703.
8 ALBION ST. LEICESTER Tel. 546198

AITKEN BROS.

35 High Bridge,
Newcastle upon Tyne
Tel: 0632 26729

thandar

Test Equipment from Sinclair Electronics



PDM35 DIGITAL POCKET MULTI-METER

LED DISPLAY DC volts (4 ranges) 1mV to 1000V AC volts 1v to 500v DC current (6 ranges) 1nA to 200mA Resistance (5 ranges) 1Ω to 20MEGΩ £39.95. AC adaptor £4.25. Padded carrying case £1.95. MN1604 Battery £1.28. Size 157x76x32mm



PFM200 frequency meter.

LED display Range 20Hz to 200MHz Accessories as for PDM35 Size 157x76x32mm £57.95.



DM235 BENCH-PORTABLE DIGITAL MULTIMETER

LED display DC volts (4 ranges) 1mV to 1000V AC volts (4 ranges) 1mV to 750V DC current 1µA to 1000mA Resistance (5 ranges) 1Ω to 20MEGΩ £60.98. Carrying case £8.95. AC Adaptor/Charger £4.25. Rechargeable battery pack £8.95. Size 255x148x40mm



DM350 & DM450. BENCH-PORTABLE DIGITAL MULTIMETERS

DM350 3½ digit LED display £83.95. DM450 4½ digit LED display £114.95. Both provide six functions in 34 ranges. DC voltage 10µV to 1200V (100µV on DM350). AC voltage 100µV to 750V DC current 1nA to 10A. AC current 1nA to 10A Resistance 10mΩ to 20mΩ (100mΩ on DM350). Carrying case £8.95. AC adaptor/charger £4.25. Rechargeable battery pack £8.95. Size 255x148x40mm.




SC110 LOW POWER PORTABLE OSCILLOSCOPE

The SC110 has a 10MHz bandwidth and sensitivity down to 10mV per division. Full trigger facilities are provided including Bright line and Auto with TV line and frame filtering £159.85.




TF200 FREQUENCY METER

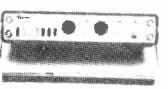LCD display The TF200 measures frequencies from 10Hz to 200MHz with a resolution of at least 1ppm (typically better) across the whole measurement range £166.75.




TG105 PULSE GENERATOR

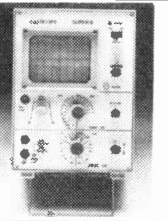The TG105 is a mains operated 5Hz to 5MHz pulse generator with independent TTL and 500 variable outputs. Period and pulse width are each selected by a 6 position range switch plus vernier control £98.75.



CALSCOPE SUPER 6 £186.30

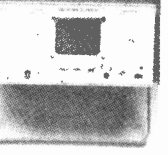A portable single beam 6MHz bandwidth oscilloscope with easy to use controls. High gain to 10 mv/cm and wide time base range from 1µs to 100 ms/cm. Full specification to request. Professional scopes you can afford



CALSCOPE SUPER 10 £251.85.

A dual trace 10MHz instrument of the very highest performance and quality. It has an accuracy of 3% which is achieved by the use of built-in stabilised power supplies which keep the trace rock steady over a wide range of mains fluctuations. Full specification on request

Please write or phone for illustrated brochure giving full technical specifications for any of the 'thandar' products

BARCLAYCARD



Education Establishment Orders Accepted

PHONE OR SEND YOUR ACCESS OR

BARCLAYCARD NUMBER

ALL PRICES INCLUDE POSTAGE AND VAT

HAND HELD GAMES

Supersonic Mastermind	£21.00
Galaxy Invaders	£22.95
Mattel Soccer	£21.50
ENTERPRISE 4 in 1	£24.95
3 Games and calculator in one	
Electronic Mastermind	£12.90
U.F.O. Master Blaster	£24.95
Amaze-A-Tron maze game	£18.95
Touch Me by ATARI (like Simon)	£26.95
Football (two players)	£24.95
ZAP missile game	£11.95
"DIGITS (like Mastermind)	£14.95
Space Invaders	£21.95

ALL GAMES HAVE SOUND EFFECTS EXCEPT

ATARI video computer

£99.95

Sargon 2.5 Chess	£278.00
Super System 3 Chess	£149.95
SPACE INVADERS CART	£29.95
STAR CHESS T.V. Game	£63.35
DATABASE Prog. T.V. Game	
NEW £89.95	
NEW £59.95	
CHESSMATE 8 Level	
CHESS CHALLENGER 7	£84.00
CHESS CHALLENGER 10	£155.00
VOICE CHALLENGER	£219.00
CHECKER CHALLENGER 2	£54.00
CHECKER CHALLENGER 4	£90.00
ZODIAC Astrol Computer	NEW £29.95
Snooze Alarm	£14.90
EL-MAC 5MHz Scope	£139.90
EL-MAC 3" 5MHz Scope	£115.00
RADAT 10MHz Scope	£169.00
PDM35	£36.50
PFM	£52.30

S.a.e. Enquiries. Please allow up to 21 days for delivery. All prices inc. of VAT.

PINBALL WIZARD

The latest from the U.S.A.
 * Still available *
 Featured in Nov. issue of E.T.I.
 Home TV Game — B/W Kit
 Basic Kit **£28.90**
 Contains everything except box and controls
 Box & Controls — **£6.50**. Mains Adaptor — **£3.90**
 Play 7 games with 4 options on each game
 4-Pinball games 2-Basket, 1-Breakout
 Versatile car alarm kit **£18.90**
 See review in Hobby Electronics November
 CHROMA CHIME 24 tune door chimes kit **£10.75** Built **£15.95**
 C.B. Aerials and Accessories

COMPUTERS — Home, Business etc.

Videogenic System 16k	£368.00
1K	£458.85
16K	£573.85
ORCERER 16K	£861.35
ORCERER 32K	£918.85
PERBOARD II 4K	£180.00
UK 101 Kit 4K	£205.85
Built 4K	£286.35
TRS80 Level 2 16K	£409.40
5 1/4" Floppy Drive	£271.40
Dual Drive	£506.00
NASCOM 2 Kit	£339.25
HEATH WH89	£1,805.00
HEATH WH14 Printer	£586.50
Kit	£115.00
By Built	£138.00
Intelligent EPROM Programmer	
Sharp Software	
PRINTERS FLOPPY DISCS BOOKS	



X10 Battery Tester Charger

Tests all sizes of batteries including watch and camera types. Also tests lamps, fuses and continuity.
 The addition of a 4.5 to 9, volt DC adaptor converts the X10 into a useful charger for all sizes of NICAD batteries.

Complete with test leads, instructions and 9 volt battery.

£13.55
 incl postage and VAT

Suitable AC/DC adaptor **£3.95**

N.T.C. SERVICES
 331 East Prescott Road
 Liverpool L14 2DD
 051 228 4690

NTC

N.I.C.
 61 BROAD LANE, LONDON N.15 4DJ
 Day 01-808 0377; Eve 01-889 9736

TTL CMOS 74LS LEDs
LB ELECTRONICS
LINEAR RAMS EPROMS SURPLUS
TELEPHONE: UXBRIDGE 55399

PCB OFFERS

(1A) 100 bit shift register PCB. 115mm x 94mm containing 9 x 7491, 6 x 7496 and 1 x 7441. Terrific bargain 85p, p&p 30p. Data General Nova 3 PCB 4K memory £40 each + £2 p&p

MPU CORNER

2122 (200ns), £3. 2114 (450ns) £4.50.

Texas Instruments. 2716 single rail. Brand new. Full spec. £6.95 each p&p 25p. 2708 (400ns) £4.50.

MK 1002P (dual 128 bit Shift Reg) 35p.

LM711CH (Voltage Comparator) 30p.

(All Full Spec)

2526 Character Generator (64 x 9 x 9) £2.95 + data & p&p 25p.

MM5240 AA/J Character Generator £3.50 + data p/p 25p.

International rectifier SOLID STATE RELAY

type A2402. Output 240 VAC 2.5 amps input 90-240 VAC/45-200 VDC £6.00 p/p 25p

D TYPE CONNECTORS

9 Way. sockets (solder) 55p.

15 Way. wirewrap plugs only 75p.

50 Way. skt (wirewrap) £1.65.

50 Way. skt £1.45, p&p 25p.

25 Way Male to Female with covers plus minimum 1 metre of cable (12 way) £4.00 each p/p 35p.

COVERS

25 Way 75p (plastic), p&p 25p.

37 Way 90p (plastic), p&p 25p.

DISPLAYS

HP 5082 4 digit DIL display full spec £1.50 each, p&p 25p. Large quantities POA.

MAN 72 7 seg CC £1.25, p&p 25p.

Burroughs Panaplex 9 Dig. + skt and bezel £1.00, p&p 25p.

LED 3 Digit DIL 55p, p&p 25p.

Bowmar 9 digit. 1 in LED with red bezel. (As used in calculators) £1.00 + 25p p&p

SUPERSAVER 1

Ribbon Cable Headers 16 DIL Jermy, gold plated, with cover 45p, p&p 25p.

Ansley Header plugs. 14 Way 75p, 16 Way 95p, 24 Way £1.80. (Insulation piercing type), p/p 25p.

Ansley I/O Header plugs. 1in 26 Way 65p, 26 Way (right-angled) 85p. 40 Way £1.00 p/p 25p.

SUPERSAVER 2

Tantalum Capacitors 25 volt. 4.7 uF. 14 for £1.00, p&p 25p.

SUPERSAVER 3

PRICE SMASH FND 500 .5in. LED displays, full spec 50p each, p&p 25p, large quantities POA.

SUPERSAVER 5

Battery eliminator 6VDC 200MA 240V AC input ideal for calculators, radio, etc., give away price 95p each. Large quantities P.O.A. p&p 35p.

SUPERSAVER 6

RS 338-383 Miniature Decade Thumbwheelswitch. £1.65, p&p 25p

SUPERSAVER 7

SN74116 Dual 4 Bit latch 75p, p&p 25p

SN7418 Arithmetic Logic Unit. 80p, p&p 25p

SN74194 4 Bit Register. 50p p&p 25p.

SN74198 8 Bit Shift Register. 75p p&p 25p.

SUPERSAVER 8

ITT 4cx 250b brand new full spec £7.50 each p&p 25p

SUPERSAVER 9

5 digit 7 segment DIL LED .11" displays 4 for £1.50 p/p 25p.

SUPERSAVER 10

9 way male/female connector, ELCO 8129, 0.1 inch pitch, gold-plated PCB mounting, ideal for bussing two PCBs together. Superb value, 35p, p&p 25p.

SUPERSAVER 11

74LS266 50p. 74LS245 £2.40. 74LS240 £1.00. 74S260 35p. P&P on all above 25p

SUPERSAVER 12

TMS 3128NC Static shift register. £1.50, p&p 25p.

SUPERSAVER 14

Recording Designs Ltd digital cassette deck. 50-100 Baud RS232C 240V input. A professional superb deck. £68.00, p&p £2.00.

SUPERSAVER 15

5K multitrans trimtops. PCB mounting, per box of 14 £2.50, p&p 25p.

SUPERSAVER 16

Yet another star bargain. Astec UM111E36 modulator 65p each, p&p 25p.

LEDs (Full spec.)

TIL209, red 10p. 0.2in, red 12p. 0.2in, green 28p. 0.2in, yellow 28p.

RL54 red Axial lead. 15p. P&P on all above 25p.

VERNITRON Ceramic filters type FM4 10 vMHz 45p, p&p 25p.

TRANSISTORS, BD236 40p, BC183L 10p, BF195 10p, TBA 810S, with data. 85p, 4-way DIL switches. 75p. MC1303 Dual Stereo preamp with data. £1.25. 7in. Nylon cable ties 100 for £1.50. All p&p 25p.

NEW SN76477 (Yes, back in stock). Sound Generator IC (Train, plane, explosion, laser gun, etc.), with data £3.25, p&p 25p.

PCB KEYBOARD, 65mm x 82mm. 18 key Clickers less Key tops, ideal Hexadecimal use 35p, p&p 25p.

CAPACITOR SCOOP, 1 600uF at 10v, 160uF at 25v. Axial lead. 2 dozen for £1 + 25p p&p.

MINI FANS 80mm x 80mm approx. 115v. Brand new. £4.50 + £1.00 p&p.

IEC mains chassis plug 75p suitable socket 35p, p&p 25p.

GIVEAWAY
22 pin low profile dil socket, gold plated.
12p EACH
p&p 25p

Just arrived. ITT 2082 Data Modem.

Brand new and boxed, with manual. 600/1200 Baud. Data Modem to CC ITT. V24/RS232C. Channel centre frequencies 1300 and 1700Hz (600 Baud) or 1300 and 2100Hz (1200 Baud). Synchronous or asynchronous operation over 2 or 4 wire, switch or dedicated lines, built in self and lines test functions. Some of the best equipment we have ever obtained. £115.00 each, p&p £3.00. (Fraction of original cost).

IC HOLDERS (Low-profile)

8 DIL	12p	14 DIL	15p
16 DIL	17p	18 DIL	20p
22 DIL	28p	24 DIL	35p
28 DIL	45p	All p&p	35p

WE STOCK a vast range of TTL, CMOS, some 74LS. MINIATURE TOGGLES, etc.

PSUs. We have a large stock of power supplies at very realistic prices (callers).

RELAYS

ITT 700 ohm Single pole changeover. 45p. Banor resettable double pole changeover 12V £1. Both p&p 25p.

CIRCUIT BREAKERS

4450v AC 65v DC 0.5A 50p; ditto 7A 80p, p&p 25p.

ALLEN KEYS, 7/16in 5p; 12 for 50p; p&p 25p.

ASR33 (with tape punch reader), generally overhauled. £185.00 inc. of VAT.

CENTRONICS 101A Dot Matrix printer. Fully overhauled. 165 char/sec. £450.00 inc. VAT. Carriage at cost. As above dual headed 300 char/sec £650 inc. VAT.

C.P.U. TYPE 10660. These devices are brand new, supplied with comprehensive, data sheet for experimental use or hang them on your Christmas tree! 4 for £1. p&p 25p.

ICL POWER SUPPLY (exchange units) 240V AC input.

Output +24V at 2 amps DC, -24V at 2 amps DC (adjustable to 12V) +5V at 4 amps DC -100V DC and 6.3V AC. £12.00. Callers only.

Terms cash with order (official orders welcomed from colleges, etc). All enquiries s.a.e. please. All prices inclusive of VAT, unless otherwise stated. Postage as shown per item.

FOR THE PROFESSIONAL USER. CP Clare Keyboard switches with buttons (blank) 65p each p&p 25p.

BURROUGHS keyboard, 96 key station. On-board crystal and TTL. Brand new and boxed. 500mm x 190mm. At the time of advert no data. No keytops at all. Clare pender. Reed switches. Bargain £12.00 each, p&p £1.50.

PLEASE DO NOT ORDER GOODS FROM OLD ADVERTS. PHONE BEFORE ORDERING

SURPLUS STOCKS PURCHASED FOR CASH

LB ELECTRONICS
 11 HERCIES ROAD
 HILLINGDON, MIDDLESEX
 UB10 9LS, ENGLAND

All enquiries s.a.e. please

Telephone answering machine service out of business hours.

New retail premises, now open Mon. Tues. Thurs. Fri. and Sat. 9.30-6.00 Lunch 1-2.15 weekdays. Closed all day Wednesday. We are situated just off the A40 opposite Master Brewer

ALL PRICES INCLUSIVE OF VAT

UXBRIDGE 55399
 All components full spec.

GREENWELD

443A Millbrook Road Southampton SO1 0HX

All prices include VAT @ 15% — just add 40p post

SLIDER POT SCOOP!!!

Made by Pifer types PL40CP & PL60C Silly prices for superb goods!
 PL40CP — 69x16x9mm 40mm slide length
 220R 2k2 or 10k lin only Prices (any mix) 1 24
 20p; 25-99 17p; 100+ 14p.
 PL60C — 84x10x7mm 60mm slide length 5k
 10k 22k and 100k log only Prices (any mix)
 1 24 25p; 25-99 22p; 100+ 17p.

BUZZERS, MOTORS & RELAYS

7401 Powerful 6V DC buzzer all metal construction 50mm dia x 20mm 70p.
 2402 Miniature type buzzer 6 9 or 12V only 22x15x16mm Very neat 53p.
 2450 Miniature 6V DC motor high quality type 32mm dia x 25mm high with 12mm spindle Only 11p.
 A372 Audible Warning device — solid state circuit drives high efficiency transducer to give high output Voltage read 4 18V Can also be driven direct from TTL or CMOS Module size 45x21x12mm Comprehensive data supplied 11.50
 W892 Heavy Duty 12V relay ideal for car use — single 15A make contact Coil 25R in sealed metal can with mounting bracket 85p.
 W890 DIL Reed relay SPCO 2 4-10V 200R coil Only 12.20.
 FSRA60 Latching relay 2 x 10A contacts 1M 1B Coil is 250R and rated 60V ac but works on 18-24 DC Solid Encapsulation with screw terminals makes it ideal for use 11.20.

REGULATED PSU PANEL

Exclusive Greenweld design — better spec than anything on the market being offered at the price Panel 110x82x33mm high contains all components including bridge rectifier and smoothing capacitor Ready built and tested — just add a 30V 2A transformer and two pots for a fully variable voltage and current supply

SPEC Output voltage 0-28V
 Output current 20mA 2A
 Source impedance 0R1
 Open circuit ripple 10mV

Send SAE for full details of the many ways this useful module can be used together with price list of parts for various options Only 16.75

1N4004 & 6 DIODES

Special purchase of 1A rects Russian made Packed in boxes of 300 18.50 per box 4 boxes 130.00; 10 boxes 175.00

DISC CERAMICS

0 22uF 12V 9mm dia Ideal for decoupling 100 for 12.75; 1000 12.00.
 0 05uF 12V 15mm dia 100 11.50; 1000 12.00. Pack of disc ceramics assorted values and voltages — 200 for 11.00

TRANSFORMERS

Mains primary 50V 20A sec 120.00. Mains pri 110V 15A sec 140.00.

P.C. ETCHING KIT Mk IV

The best value in the market — contains 100 sq ins copper clad board 1lb Ferric Chloride Etch resist pen abrasive cleaner two miniature drill bits etching dish and instructions All for 14.95.

1981 CATALOGUE

Now in the process of compilation available NOV 75p will reserve you a copy sent as soon as printed

BULK SUPPLIES

All new full spec. devices. Prices are for a minimum of 100 of any one device and exclude VAT, which must be added at 15%. Minimum order value from this section is 10+VAT+post. VAT receipt on request.

RESISTORS

Min 1/4W 5% carbon film 1R 10M (10% over 1M) all 1.00
 The following values only at 1.50 1 000 per value 4R7 8R2 18R 39R 56R 220R 1k 4k7 18k 33k 39k 47k 220k 390k 560k 680k 820k

MIN. PRESETS

0 1W miniature type open construction All values from 100R to 1M vertical or horizontal mounting All at .042.

The following values only at .03 470R 470RH 500RH 1k 1k5 2k 2k2 2k5 4k7 4k7
 Also some Pifer enclosed type at .042 150RV 200RH 2kV

POTS

5k lin 100k lin 220k lin 500k log 1M lin All with std. bush and spindle .14.

ELECTROLYTIC CAPS

2 2 75 R	.028	47 63 R	.045
2 2 63 A	.032	100 6 3 A	.020
4 7 10 R	.022	100 35 R PC	.035
4 7 25 R	.028	220 16 A	.055
4 7 50 R	.034	220 25 R	.065
10 16 R	.030	220 70 A	.075
10 25 R	.032	330 50 A	.075
10 25 R PC	.022	330 100 A	.085
10 25 A	.036	470 16 R	.080
10 50 A	.040	470 100 RC	.150
10 100 R	.042	1000 40 A	.230
15 40 A	.030	1000 63 A	.280
22 10 R	.021	2200 10 A	.080
22 25 A	.025	2200 25 A	.280
22 25 R	.027	2200 40 RC	.350
22 63 A	.040	1300 10 A	.090
33 16 A	.022	1300 25 A	.180
47 6 A	.015	1700 10 A	.100
47 25 A	.032	4700 25 RC	.250
47 35 R	.038	4700 40 RC	.35
47 40 A	.045	10000/15 RC	.250

R = radial leads A = axial leads RC = tag ended can R PC = short radial leads for PC mounting

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

ALL PACKS CONTAIN FULL SPEC BRAND NEW MARKED DEVICES — SENT BY RETURN OF POST VAT INCLUSIVE PRICES

K001 50V ceramic plate capacitors 5% 10 of each value 22pF to 1 000pF total 210 13.69.
K002 Extended range 22pF to 0 1 uF 330 values 15.53.

K003 Polyester capacitors 10 each of these values 0 01 0 015 0 022 0 033 0 047 0 068 0 1 0 15 0 22 0 33 0 47uF. 110 altogether for 15.07.

K004 Mylar capacitors min 100V type 10 each all values from 1 000pF to 10 000pF total 130 for 14.05.

K007 Electrolytic capacitors 25V working small physical size 10 each of these popular values 1 2 2 4 7 10 22 47 100uF Total 70 for 13.59.

K008 Extended range as above also including 220 470 and 1000uF. Total of 100 for 16.05.

K021 Miniature carbon film 5% resistors CR2 or similar 10 of each value from 10R to 1M 112 series. Total 610 resistors 16.15.

K022 Extended range Total 850 resistors from 1R to 10M 18.50.
K043 Zener diodes 400mW 5% BZY88 etc 10 of each value from 2 7V to 36V E24 series Total 280 for 16.37.

CALC CHIPS 60p!!!

New full spec supplied with data type MK50321 — full function inc memory Only 60p

DISPLAYS

8 and 9 digit 7-segment bubble type for above chips — most have minor faults, dud segment, etc Mixture of 2 or 3 different types with data 5 for 11.00

NICADS

Ex-equip size C approx 11 each; 10 for 18.00

COMPONENT PANELS

2525 Contains 11 800mA 60V 2N5061 SCRs 11 6V8 zeners 11 1N4004 diodes plus Rs, Cs, etc Only 11.
 Z529 74 Series ICs — Gates and complex logic 20 assist ICs on panels 11; 100 ICs 14.
 Z527 2x6V reed relays 6x 2S030 or 2S230 6x 400V recls plus Rs Only 50p.

TTL, LINEAR, OPTO

All new full spec — Fairchild SGS
TTL 5400, 5401, 5402, 5403, 5404, 5405, 5410, 5421, 5430, 5450, 5451, 5453, 5460 — All 12p ea. 5470, 5472, 5474, 5475, 5476, 5480, 5486, 5490, 54107, 54121, 54122 — all 20p ea. 5492, 54126 — 40p ea. Others (74S 74) on B L 12 (SAE please).
LINEAR 9665 or 9666 7 x 50V Darlingtons in 16 DIL 60p; 75452 or 4 dual periph driver 70p; X1444 7 CMOS P-channel buffers 15V 16 DIL 24p.
OPTO Isolators FCD831 60p; TIL115 118 60p; FPE100 106 infra red LED 12.50; FND847 7 seg 0 8" CA 12.00; FND850 CC 12.00. (Data on request for linear & opto devices)

VEROBLOC BREADBOARD

New from Vero this versatile aid for building and testing circuits can accommodate any size of IC Blocks can be joined together Bus strips on X & Y axis — total 360 connexion points for just 14.15.

POLYESTER CAPS

01	400V	C296	.025
015	250V	C280	.025
022	400V	C280	.025
068	250V	Advance	.025
22	250V	C280	.035
22	250V	Advance	.035
22	100V	Mimbox	.035
47	250V	C280	.05
47	160V	C296	.04
10	250V	C280	.055
15	63V	Filmcap	.065
22	150V	Filmcap	.086
33	100V	Wima MKS	.15
47	100V	C281	.195
47	100V	Wima MKS	.235
68	100V	Wima MKS	.285

LEO's TANT BEADS

3mm red	.055	5mm yellow	.09	1 5 35	.06
3mm yellow	.08	5mm green	.09	3 3 25	.08
3mm green	.08	3mm clips	.02	10 25	.15
5mm red	.06	5mm clips	.02		

MINIATURE CERAMIC CAPS

Thompson CSF miniature type in the following values
 3 9pF 4 7pF 22pF 33pF 47pF 47pF 68pF 82pF 100pF 560pF 2700pF All 5% except 10k 120k
 Prices up to 82pF 17 1000 100pF 19 1000 560pF 15 1000 2700pF 19 1000
 Samples on request (see please)
 Mullard min ceramics 33pF 5% 100V 17 1000 330pF 2% 100V 18 1000 3300pF 10% 100V 113 1000
 Stettner min ceramics 330pF 5% 63V 17 1000 022uF 63V 114 1000
 Lemco 047uF 63V 116 1000

SEMICONDUCTORS

741 .12 555 .19 7401 .08 7405 .09 74174 .21 4001 .17 4011 .17 S1 signal diodes like IN4148 by TI on bandolerised reels of 10k 180 (1k 10) IN4002 125/k IN4006 134 k IN4007 136 k Ge signal diode OK14 120 k SCRs 7P4M (C1060) 4A 400V .26 2N5060 8A 30V .15 CR201 1A 200V .18.
 See July's advt for transistors send sae for latest bulk buyers list

LCD QUARTZ WATCHES

Special Offer Gent's LCD Alarm Only 17.50
 Slim Gent's Chronograph 17.50
 Gent's Alarm Chronograph 110.50
 Musical Alarm Chronograph, Plays Yellow Rose of Texas 113.25
 Slim Musical Melody Alarm Chronograph 113.25
 Gent's 5 Function LCD 14.50
 Ladies' 5 Function LCD 15.50
 Ladies' 5 Function Sugar-coated oval face or square face Silver or gold colour 18.25
 Ladies' Dress 5 Function, oval or square face, silver or gold colour 19.50
 Christmas Stocking Filler, digital Mickey Mouse watch Ideal for the kids 17.00
 Add 35p P & P to all items

Gent's Quartz Analogue with Calendar 18.95



Money-back guarantee if returned within 14 days

**D. K. SUPPLIES 5A
 HALFPENNY LANE
 PONTEFRAC, W.
 YORKS**

All goods carry 12 month guarantee (S A E for fuller list and brochure) Prices include VAT



PLEASE MENTION ETI WHEN REPLYING TO ADVERTS

QUESTION?

1. Is your hobby home computing or electronics?
2. Do you understand the application of IC's, Transistors, Diodes, etc?
3. Have you used or applied analogue or digital techniques?
4. Are you applying TTL Logic to your home computer?
5. Are you programming your home computer using simple software techniques?

If the answer is YES to any of these questions then why not consider turning your hobby into a career — applying your knowledge to servicing electronic equipment ranging from basic terminals and data processing machines through to advanced micro-processor systems.

We will train you through to advanced technology at the company training school, fitting the individual in at their own level.

We have vacancies over the whole of the U.K. especially in the London area, with the successful applicants working from home, usually in a radius of no more than 60-70 miles.

We supply all tools and test equipment, plus a company car which is available for private use.

If you are interested, then why not contact **Mr. C. Marklew** on 0249 813771 to discuss your own career opportunities in confidence, or write to:

KODE SERVICES LIMITED

Station Road, Calne, Wiltshire

ETIPRINTS

ETIPRINTS are a fast new aid for producing high quality printed circuit boards. Each ETIPRINTS sheet contains a set of etch resistant rub down transfers of the printed circuit board designs for several of our projects.

ETIPRINTS are made from our original artwork ensuring a neat and accurate board. We thought ETIPRINTS were such a good idea that we have patented the system (patent numbers 1445171 and 1445172).


PARTS LIST

Shown below is the listing for the last year's ETIPRINTS.

Earlier sheets are available, ring for details.

038	Buffer Moving Coil Preamp Process Controller	Jan 80	040B	ETI 80 - PSU Tuning Fork Filter Coin Toss	Feb 80	042B	Touch Dimmer, Battery Charger RC Guardian (Top, Bottom) 1&2	Apr 80
039A	Hum Filter Logic Probe	Dec 79	041A	ETI Audiophile ETI VCA Signal Trace ETI HC Electromyogram	Mar 80	043	IR60 preamp, Receiver, PSU, Servo Tester, VU - PPM	May 80
039B	Long Period Timer Rain Alarm Touch Switch Flash Trigger Pseudo Random Noise Gen	Dec 79	041B	VCM Heater Controller	Mar 80	044A	IR60 Function Board (Top & underside) Control Circuit, Line Transmitter, Tape Response Meter Ohmmeter	June 80
039C	Function Generator	Dec 79	042A	300W Amp Module	Apr 80	044B	FM receiver PSU & Monitor Amp Drum Synth (function board)	June 80
040A	ETI 80 - VCO and VCLFO	Feb 80	033	Fuel Level Monitor, Alarm, Screen Controller Dynamic Noise Reducer	Sep 79			

HOW IT WORKS

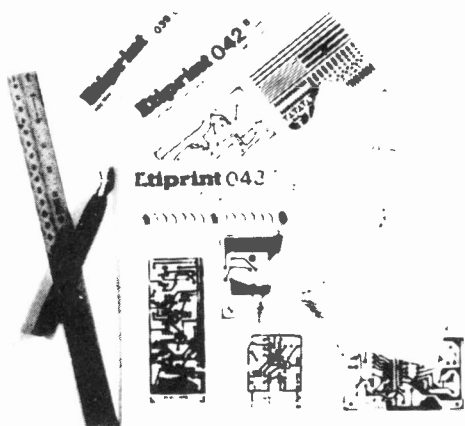

Lay down the ETIPRINT and rub over with a soft pencil until the pattern is transferred to the board. Peel off the backing sheet carefully making sure that the resist has transferred. If you've been a bit careless there's even a 'repair kit' on the sheet to correct any breaks!

ETIPRINTS

BUY LINES

ORDER TODAY


Send a cheque or PO (payable to ETI Magazine) to

ETI PRINT, ETI MAGAZINE 145 Charing Cross Road,
London WC2H 0EE.


Price £1.20p.

PCB FOIL PATTERNS


ETI BENCH AMPLIFIER

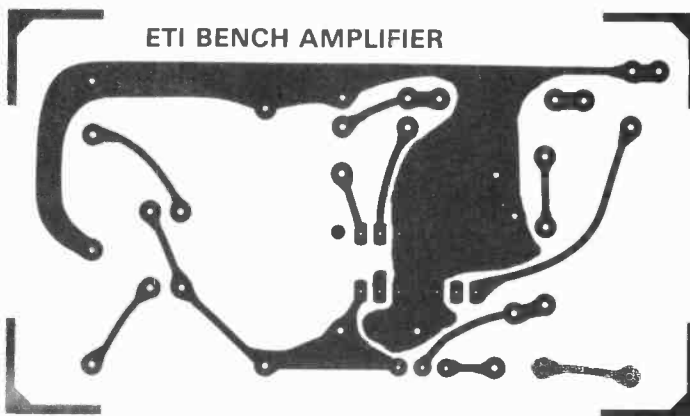

ETI MIXER

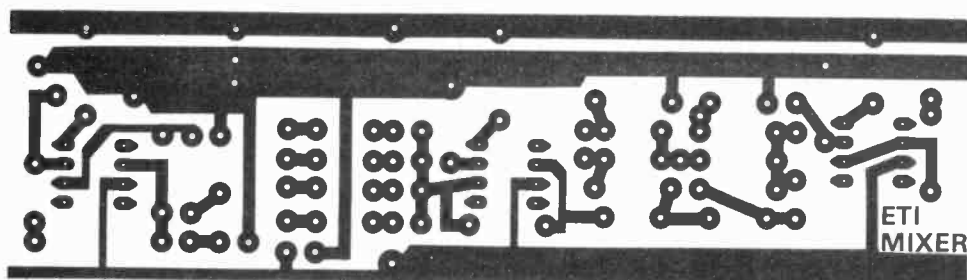


ETI DOORBELL

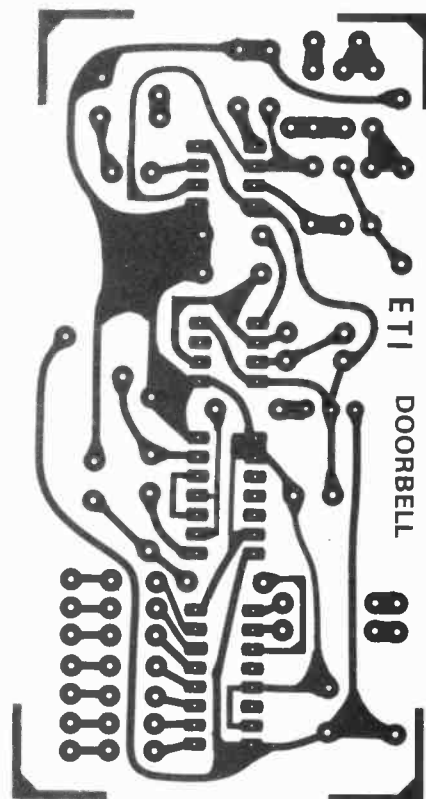


ETI

SOUND BOARD

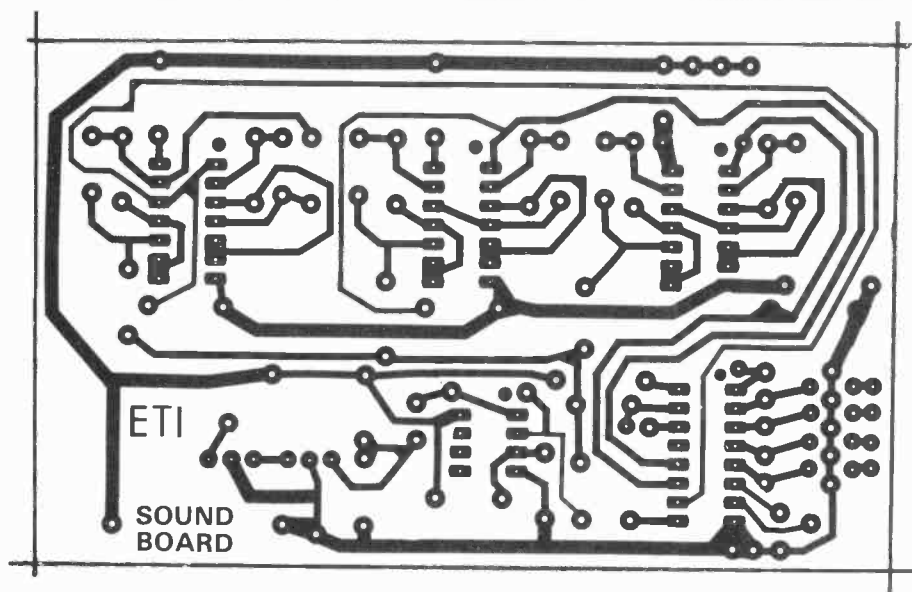

MUSICAL
ETI CLOCK

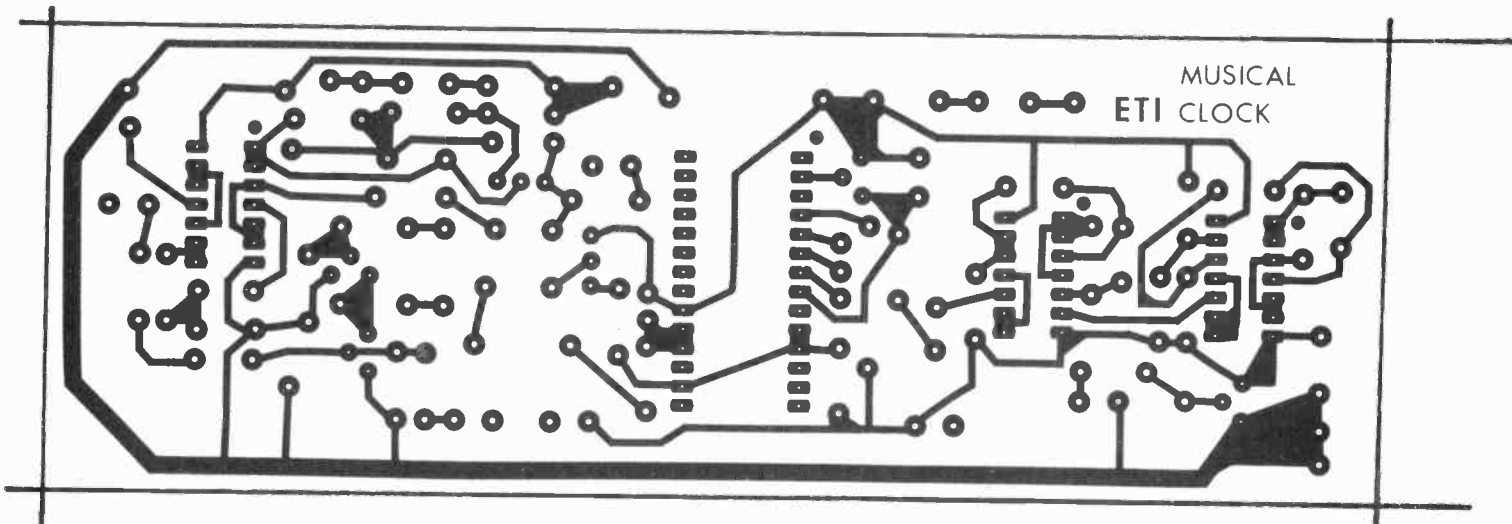

CLASSIFIEDS

RATES

1-3 insertions £7 per scc
 4-11 insertions £6.50 per scc
 12 insertions £6 per scc
 24p per word (min. 15 words)
 Box No. of application


All advertisements in this section must be pre-paid
 Closing Date:- 1st Fri. month preceding publication

Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request).

SEND TO:- ETI CLASSIFIED, 145, CHARING CROSS ROAD, LONDON WC2H 0EE. TEL: 01-437 1002

UK101 NASCOM 1 & 2

ADD-ON COLOUR SYSTEM



DAZZLING COLOUR GRAPHICS FOR UK101 & NASCOM

- Professional bit-addressable 'pixel' system
- 3072 colour cell definition
- 8 Colours foreground + 8 background
- FREE SOFTWARE: Plot, Line, Circle (Basic + Z80)
- Animated Demonstration Program
- Modulator included for use with normal TV

KIT: only **£45** Built & Tested: only **£60**
 Also available separately:


COLOUR MODULATOR

- R G B inputs, PAL/UFH output
- Unlimited colour combinations
- TTL etc Interface details supplied
- 1000's already in use!

KIT: only **£12** Built & Tested: only **£18**

— please add VAT at 15% to all prices
 — Barclay/Access orders accepted by telephone

WILLIAM STUART SYSTEMS Ltd Dower House, Billericay Road, Herongate, Brentwood, Essex CM13 3SD. Telephone: Brentwood (0277) 810244



ASSEMBLY & WIRING SERVICES

P.c.b assembly. Panel wiring. Video game/home comp. assembly. Design Development. Q.C. / Insp. / Test. Prototype. Pre-Production etc
 LARGE / SMALL BATCH or HOBBY

For these and general services at competitive rates contact:

BRAINTREE MICRO LEISURE LTD.
 92 Manor Street, Braintree, Essex
 Phone: Three Rivers 28196 (STD 03763)

HP-41C PROGRAMMABLE CALCULATOR

plus two memory modules and software. Five months old. The lot for £220 o.v.n.o. Telephone Fareham 280042.

T.T.L. LOGIC PROBE.

Suitable for testing computer boards or single chips; send £9.90 or telephone: C/Card No. (095389) 420, R. A. Eng., Forncett End, Norwich.

WIRRAL SEMICONDUCTORS. D.C. / A.C. Converters:

VP5 derives — 5v. from + 5v., 595p. 5/12D derives ± 12v. from single +5v. input dimensions approx. 20mm + 30mm x 10mm, 995p. DS318 5/500MHz power splitter 495p. TTL: 74154 95p. 8242 50p. CMOS: 4016 30p. 4023 25p. 4047 95p. 1702A Eprom 425p. 3/8" square screwturn pots., 10K, 20K, 95p. CD5/25 trimmer 3.5pf to 25pf, 95p. AX121B-4 14-pin di1 Reed relay 5v. operation. 95p. Data sheets available on request. Orders less than £5 add 30p post. 177 Brookdale Avenue, Greasby, Wirral, Merseyside L49 1SR.

PRINTED CIRCUITS and HARDWARE

Comprehensive range Constructors Hardware and accessories

Selected range of popular components Full range of HE printed circuit boards normally ex-stock, same day despatch at competitive prices
 P.C. Boards to individual designs Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required)

Full range of etch resist transfers and other drawing materials for p.c. boards

Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES

MASONS ROAD
 STRATFORD-ON-AVON
 WARWICKS. Tel. 4879

ELECTRONIC KITS.

Largest range of kits in the U.K. Everything from Stroboscope Lights to Transmitters, at unbeatable prices — send S.A.E. for free catalogue to: Eastling Electronics (Kits), 64b Hawthorn Road, Winton, Bournemouth.

MAPLIN PIANO I.C. KIT,

still sealed in original packing. Project never begun. £25. Derby 512015.

SHARP COMPUTERS NEW LOW PRICES

Pocket Computer PC1211, complete with cassette interface. CE 121 **£108.95.**
 M280 Computer 20K **£504.85-48K £573.85**
 M280 P3 Line Printer **£585.50.** M280FD Disc Drive **£885.50.**
 M280 I/O Expansion Interface **£109.25.**
 All prices include VAT and UK delivery

ELKAN ELECTRONICS
 28 Bury New Road, Prestwich
 Manchester M25 8LD

The DT400 Series are designed and manufactured by SAFGAN in England!

SAFGAN Presents DT-400 Series from £159 + VAT


HIGH QUALITY DUAL TRACE OSCILLOSCOPES AT PRICES EVERYONE CAN AFFORD

Model DT-410	4" CRT	5mV	10MHz	@ £159 + VAT
Model DT-412	4" CRT	5mV	12MHz	@ £172 + VAT
Model DT-415	4" CRT	5mV	15MHz	@ £185 + VAT

SPECIFICATION FOR ALL MODELS

- * CH1, CH2: 5mV/div, 20V/div in 12 col. 1/2/5 steps
- * BANDWIDTH: 10MHz (DT-410), 12MHz (DT-412)
- * BANDWIDTH: 15MHz (DT-415)
- * TIME BASE: 0.5µs/div, 200ms/div in 18 cal 1/2/5 steps.
 X5 Expansion to 100 ns/div
 X5 Multiplier to 1s/div
- * XY FACILITY: Matched Inputs X=CH1, Y=CH2
- * TRIGGER: Level Control, = Slope
 Bright Line AUTO NORMAL, TV Triggering
 CH1, CH2 0.5div, EXT Trig 100mv
- * Z Modulation
- * Graticule blue, ruled 8x10div (6.4x8cm²)
- * Size: H215mm W165mm D280mm. Weight 4.5kg
 PROBE (X1-REF-X10) £11.50+VAT

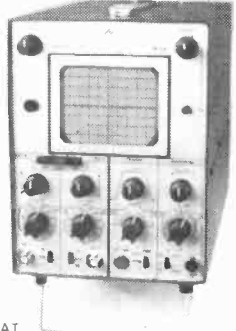Orders to: **SAFGAN ELECTRONICS LTD.** (Goods + 15% + £3 P&P)
 56 BISHOPS WOOD, ST. JOHNS, WOKING, SURREY GU21 3QB. Tel. WOKING 69560
 Official Government and Educational orders accepted or WOKING 66836



DT-400 Series
Distributors required. Please enquire



C
C
T
V

C
A
M
E
R
A

£110.00 + P/P £3.45 (inc. VAT)
+ VAT (£16.50) Optional extra manual
£6. Total £129.95

BEST OFFER EVER
**Camera Kit, Lens,
Vidicon & Modulator**

CROFTON

Tel: 01-891 1923 For full details


OSCILLOSCOPE £12. Easy-build converter plugs into TV aerial socket and converts to large screen oscilloscope. (Components cost under £12). Circuit and plans £3. — Kerr, 27 Coles Road, Milton, Cambridge, CB4 4BL. (Callers by appointment.)

TRANSFORMERS MANUFACTURED to specification, many popular types ex-stock. Fast turn around on volume production. Send enquiries to Louth Transformers, Queen Street, Louth, Lincs. Tel: (0507) 606436.

OVERSEAS MERCHANTS ATTENTION. Doorbird sings out a warning when doorknob is touched. Entry-alert plus burglar alarm. IC new design. Reliable long-lasting battery. Sample £3.75. Details: G.P.O., 12022A, Hongkong.

If it's a case of making your project look good, then use one of ours.

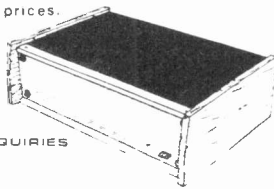
Simply send a S.A.E. for Details and prices.




TRADE ENQUIRIES INVITED

H. M. ELECTRONICS
271a/275a Fulwood Road.
Broomhill
Sheffield S10 3BD

DIGITAL WATCH BATTERY REPLACEMENT KIT



These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener. Also one doz assort push-pieces, full instructions and battery identification chart. We then supply replacement batteries — you fit them. Begin now. Send £9 for complete kit and get into a fast-growing business. Prompt despatch.



BOLSTER INSTRUMENT CO. (ETI9)
11 Percy Avenue, Ashford, Middx, TW15 2PB

SCOOP OFFER
PINBALL WIZARD

As featured E.T.I. November 1979
Complete kit of Electronic Parts inc. P.C.B.
ONLY £16.50 incl. del.
PLUS
FREE MAINS ADAPTOR
Hurry whilst stocks last—
Normal price of this kit and adaptor **£32.80**

Mail order only from:
**I. T. Clarke, 2 Service Bay, Staple Tye
Harlow, Essex**
Note: Kits do not include case or controls.

SPEED — VERSATILITY — ECONOMY



Designed originally for logic wiring applications, it is now accepted and used extensively throughout industry, education and research. ROADRUNNER is used by hobbyists, students, technicians, designers and engineers, to carry out work on:—
*P.C.B. REPAIRS *ANALOGUE BREADBOARDING *SIMPLE LOGIC WIRING *COMPLEX INTERCONNECTING OF MICROS AND MEMORIES.

EURO INTROKIT **£16.70**. PROJECT KIT **£8.18**. MINKIT (A) **£7**. PENCIL WITH LOADED 'OSE' BOBBIN **£2.81** WITH T.C.W. BOBBIN **£2.76**. STRIPS GLUE FIX 20/PKT 6" LONG **£3.20**. HIGH DENSITY GLUEFIX 20/PKT 6" LONG **£3.20**. PRESS FIX 20/PKT **£3.20**. SINGLE HIGH DENSITY D-SIDED EUROCARD **£5.18**. SINGLE SIDED **£3.80**. DOUBLE HIGH DENSITY D-SIDED EUROCARD **£8.60**. PROJECT CARD **£2.50**. BOBBINS BLUE 4/PKT **£2.12**. GREEN 4/PKT **£2.12**. GOLD 4/PKT **£2.12**. PINK 4/PKT **£2.12**. 1 OF EACH COLOUR **£2.20**. TINNED COPPER 2/PKT **£0.96**. ADHESIVE **£0.41**. SOLDERING IRON 420 C **£5.52**. REPLACEMENT WELLER TIPS — PTA48 430 C **£1.40**. PTA49 480 C **£1.40**.

Please add 40p for P&P + VAT to all orders

**FOR FURTHER INFORMATION ON
ROADRUNNER PRODUCTS SEND
LARGE S.A.E. TO:
T. J. BRINE ASSOCIATES
FREEPOST, Haslemere, Surrey GU27 3BL**

HALF-PRICE MEMORIES. 4k x 8-bit static ram boards £50; 4k x 8-bit prom boards (1702A) £30. 1702A proms £2.50 each. All assembled and tested. Phone Chip-pling Sodbury 317626 (evenings).

TELEPHONE ANSWERING MACHINES, Super Phones, Radio Phones, etc. Ring C.W.A.S. 0274 682674

**INTENSIVE COURSES IN
BASIC
AND
PASCAL**

including hands on mini-computer operation

These intensive courses are intended to instruct from minimal knowledge to an operational capability of computer programming. Courses are fully residential, allowing maximum time for instruction and programming.

BASIC — Weekends from Friday Evening to Sunday Afternoon.

PASCAL — Weekdays Monday Morning to Friday Afternoon inclusive.

For further details, dates available, fees
Phone (0401) 43139, or write
CLEVELAND BUSINESS SERVICES
(Dept. ETI-2), Cleveland House
Routh, North Humberside HU17 9SR

**BARGAINS FOR THE QUARTZ
ELECTRONIC HANDYMAN
BRANDED QUARTZ
ALARM CLOCKS**

**ORIENT/PRESIDENT
JAPANESE** **KIENZLE/PRESIDENT
GERMAN**



(1) (2)

Returned to Service Department within guarantee period

(1) Recommended price when perfect **£12.95**. To facilitate repair **5 offered for £11.95** inclusive of VAT

(2) Recommended price when perfect **£12.95**. To facilitate repair **5 offered for £11.95** inclusive of VAT

These will be sold as received from our customers with the existing fault(s) and without guarantee

UK ONLY
Discounts available on large bulk purchases.

**PRESCOTT CLOCK &
WATCH CO. LTD.**
Prescott House, Humber Road, London NW2 6ER

CIRCUIT DESIGN, Prototype construction. Analogue or Digital, Single Circuits or Complete Instruments/Systems. Write A. J. ATTWOOD, C.Eng., MIERE, Heathercote, Heatherton Park, Taunton, Somerset, TA4 1ET or Phone Bradford-on-Tone (082-346) 536.

COPPER CLAD BOARD, double sided fibre glass. 6" x 6", 70p. 12" x 6" £1.40. Also complete PCB service from Artwork to Production. H.C.R., 1 Bankside, Off New Street, Chelmsford.

**ETCH RESIST TRANSFER
KIT SIZE 1:1**

Complete kit 13 sheets 6in x 4 1/2in **£3**, with all symbols for direct application to P.C. board. Individual sheets 30p each. (1) Mixed Symbols (2) Lines 0.05 (3) Pads (4) Fish Plates and Connectors (5) 4 Lead and 3 Lead and Pads (6) DILS (7) BENDS 90° and 130° (8) 8—10—12 T O 5 Cans (9) Edge Connectors 0 15 (10) Edge Connectors 0 1 (11) Lines 0 02 (12) Bends 0 0 2 (13) Quad in Line

MAIL ORDER P.C.B. COPPER CLAD BOARD 1/16"

2" x 12" 11 Pieces for **£1** + Post 50p
3" x 12" 8 pieces for **£1** + Post 50p
4" x 12" 6 pieces for **£1** + Post 50p
5" x 12" 5 pieces for **£1** + Post 50p
6" x 12" 4 pieces for **£1** + Post 50p
7" x 12" 3 pieces for **£1** + Post 50p
8" x 12" 2 pieces for **£1** + Post 50p
2" x 16" 9 pieces for **£1** + Post 50p
3" x 16" 6 pieces for **£1** + Post 50p
4" x 16" 5 pieces for **£1** + Post 50p
5" x 16" 4 pieces for **£1** + Post 50p
6" x 16" 3 pieces for **£1** + Post 50p

PAXOLIN INSULATION BOARD

1/32" 5" x 16" 8 pieces for **£1** + Post 50p
1/16" 5" x 16" 5 pieces for **£1** + Post 50p

FRONT AND REAR PANEL TRANSFER SIGNS

All standard symbols and wording. Over 250 symbols, signs and words. Also available in reverse for perspex, etc. Choice of colours, red, blue, black or white. Size of sheet 12" x 9". Price **£1.20**.

GRAPHIC TRANSFERS WITH SPACER ACCESSORIES

Available also in reverse lettering, colours red, blue, black or white. Each sheet 12" x 9" contains capitals, lower case and numerals 1/8" kit or 1/4" kit. **£1.20** complete. State size

All orders despatched promptly.
All post paid
Shop and Trade enquiries welcome
Special Transfers made to order
E. R. NICHOLLS
P.C.B. TRANSFERS
DEPT. ETI2
46 LOWFIELD ROAD, STOCKPORT, CHESHIRE
061-480 2179

CENTURION ALARMS

BURGLAR ALARM EQUIPMENT AT UNBEATABLE VALUE JUST LOOK!

Order No.
100 ALARM TRIGGER MODULE. 100% Solid State Battery operation Pos & Neg Rings N/C for 4-wire contacts N/O for Mats. etc One Amp Switching Capacity Only £9.95
210 Quality White Flush fitting 4-wire MAGNETIC REED CONTACT + matching magnet £1.10
220 Surface 4-wire MAGNETIC REED CONTACT £1.50
240 PRESSURE MAT. Standard size 4-wire 30" x 15" £2.20
250 PRESSURE MAT. Stair size 4-wire 23" x 8 1/2" £1.73
260 VIBRATION DETECTOR. Pendulum type in Ivory Case with contacted Lid + self-adhesive backing Adjustable sensitivity £3.50
360 SIX INCH UNDER DOME BELL £9.95
390 BEST QUALITY BELL HOUSING. PVC coated metal, not to be confused with the cheaper decoy covers Fully signwritten with our Centurion insignia £9.50
400 DECOY P.V.C. BELL COVER £6.60
 Note All equipment operates on 12 Volts DC.
710 SCOOP Offer SMOKE ALARMS. Self-contained ionisation Type (1.5% obscuration) with low battery warning at the UNREPEATABLE PRICE of only £8.75 While Stocks Last!!!
 Terms. Add 15% VAT to Prices + 40p Postage & Packing



No Minimum Order.
 Access telephone orders welcome on
0484 35527 or send S.A.E. for Full List to

CENTURION ALARMS & ELECTRONIC SALES, Dept. HE, 265 Wakefield Road, Huddersfield, W. Yorks HD5 9BE.

OPTICAL FIBRES carry light. Tough, wire-like, excellent for communications, lighting, electrical isolation, etc. Introductory pack totals sixteen feet of four assorted types, plus illustrated guide. Send £3.55. Quantum Jump Ltd., 53 Marlborough Road, Tue Brook, Liverpool 13.

ZX80 BREAKOUT—a genuine continuous non-flicker game—a superb achievement in 1k memory—listing and details £4.00, or send s.a.e. for list of other ZX80 specials to: K. Macdonald, 26 Spiers Close, Knowle, Solihull, B93 9ES.

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolac Light Sensitive Lacquer — now greatly improved and very much faster. Aerosol cans with full instructions. £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibre-glass Board approx. 1mm thick £1.75 sq. ft. Post/packing 60p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

ETI PCB'S

Buy it with Access

TRS 80 SOFTWARE NOW AVAILABLE

CROFTON ELECTRONICS LIMITED

35 GROSVENOR ROAD, TWICKENHAM MIDDLESEX TW1 4AD Tel: 01-891 1923

EXACT TIME?
MSF CLOCK is ALWAYS CORRECT — never gains or loses, self setting at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto GMT/PST and leap year, also parallel BCD output and audio to record and show time on playback, receives Rugby 60KHz atomic time signals, built-in antenna, 1000K range, ABSOLUTE TIME, £54.80.
V.L.F.-7 EXPLORE 10-150KHz. Receiver £13.70.
60KHz RUGBY RECEIVER, as in MSF Clock, serial data and audio outputs. £15.70.
 Each fun-to-build kit includes all parts, printed circuit, case, instructions, postage etc. money back assurance so GET one NOW.
CAMBRIDGE KITS
 45 (TM) Old School Lane, Milton, Cambridge

VIDEO MUSIC

The amazing Videograph, as featured recently in Electronics Today International links your Hi-Fi with any Colour TV to produce a Fantasia of hypnotic visual effects. The system displays stereo music as brilliantly coloured waveforms against an ever changing background. For the technically minded a square-wave signal generator is built-in permitting advanced demonstrations of transient response etc. Truly the ultimate accessory for any Hi-Fi system!

DIY KIT ONLY £33.95
 Case & Controls £15.95
 or READY BUILT £69.95

WILLIAM STUART SYSTEMS LTD
 1000 Maple Road, Weybridge, Middlesex, TW20 2EX
 Tel: 0181 871 1111

BURGLAR ALARM Component Catalogue out now. Ring: C.W.A.S. 0274 682674.

SMALL REED SWITCHES 10p. Magnets 8p and 15p. Reed Relays, 6v, 9v, 12v, 40p. 30 Untested i.c.s. 35p. Postage 22p. Grimsby Electronic Components, Lambert Road, Grimsby, Humberside. List 15p.

ZX80 Softwares, Hangman, Dice, Mastermind, Fruit Machine, Dog and Cat, Lunar Landing, all £1 each or 6 games for £5. Enclose own cassette or 30p. Stephen Wan, 121 Woodbine Avenue, Wallsend, NE28 8HE.

150 ASSORTED RESISTORS £1. 100 assorted capacitors £1. 100 IN4148 £1. P. and P. 20p. S.a.e. lists of components, mikes, meters. Dept. T, D.B. Products, 1 Holly Tce., York, YO1 4DS.

MICROTYPE

READY CUT CASE FOR SUPERBOARD, UK 101, NASCOM 2. (ALSO AVAILABLE WITH BLANK KEYBOARD FOR HOMEBREW, NASCOM 1, ETC.)

PRODUCED IN BLACK ABS PLASTIC, COMPLETE WITH SCREWS AND INSTRUCTIONS SPACE FOR EXPANSION, FORCE FEED FAN, NUMERIC PAD AND ADDITIONAL KEYS ONLY £24.95 + £1.50 P&P + VAT
 SEND CHEQUES OR P.D.'S FOR £29.90 TO
 MICROTYPE, P.O. BOX 104, HEMEL HEMPSTEAD, HERTS HP2 7QZ
 SAE FOR DETAILS DEALER & DEM. ENQUIRIES WELCOME

TO CLEAR
 24 x 6520P 45 x 2708C
 28 x 6503AP 243 x TIL 321
 Offers to:
ELECTROTECHNICAL SERVICES
 6 HINTON ROAD, UXBRIDGE, MIDDLESEX

HIGH QUALITY PCB'S

From your own artwork master negative or positive maximum 12" x 12"

Manufactured in glass fibre tinned and drilled
 Express service for prototypes and small production runs
 Small compact circuit boards assembled
 Gold plating for reliability where edge connectors are used
ANODISED SELF-ADHESIVE FASCIA PANELS WITH LEGENDS
 Manufactured from your own artwork master
 Various colours available brushed and satin finish
 Express service and competitive prices

Send artwork or phone for prices
 125W 5% C.F. Resistors £12 Series 1p each
 IN4148 Diodes 2p each

Ecoscope Instruments Ltd.
 51 Sandilands Street, Glasgow, G32
 041-778 2555

£99 SYNTHESISER DIY. Professional results, easy-build. S.A.E. Dewtrion, 254 Ringwood Road, Ferndown, Dorset, BH22 9AR.

MIXED. 100 Transistors £3.50. 25 ICs £1.50. Post paid. Valves. Early radios. Various electronics. Lists 15p. Sole Electronics (ETI), 37 Stanley Street, Ormskirk, Lancs. L39 2DH

THREE WISE OFFERS FROM KLIFCO!
 60w. Fibreglass Modules (60v.) £9.95. Quality Stereoamp Chassis 60 + 60w. (60v.), protected 3Ω min, din sockets, controls, selector/vc, etc., £9.95. 60w. complete Hi-Fi Amplifiers (240v.), stereo/case/knobs/magnetic pickup/everything, £24.00. All new, inclusive, tested + data. Leaflets s.a.e.! Klifco Electronics, 1 Regent Road, Ilkley, W. Yorkshire. Merry Christmas Folks!

NASCOM-2, 32k, Nas-pen, Graphics, Rom, PSU, in micro case. Disagreement with solicitor forces sale, £450. Phone Erith 32835.

CS SPARES

Original transistors and integrated circuits for all types of 40/120/24C etc. channel rigs.

McLAUGHLIN ELECTRONICS
 44 Carlisle Road
 Londonderry
 Northern Ireland BT48 6JW
 Tel. 0504 65002

ADAM HALL
 Cabinet & Flightcase Fittings, fretcloths, coverings, handles, castors etc., Jacks & sockets, Cannons, Bulgins, reverb trays, Emilar compression drivers, AKG mics, Celestion speakers, ASS glassfibre horns.
 Send 30p postal order for illustrated catalogues to
ADAM HALL (E T SUPPLIES)
 Unit B, Charlton Court
 Grainger Road, Southend-on-Sea
 Essex SS2 5BZ

ASSISTANT FILM RECORDISTS MANCHESTER

To work in sound transfer and dubbing areas operating sound recording and reproduction equipment for a wide range of programmes. Some mobile film recording work involved. Candidates must have professional experience and practical knowledge in this field, current driving licence and normal hearing.

Salary: £5,425-£6,725 p.a. (starting salary in accordance with qualifications and experience).

Candidates lacking experience may be considered for appointment as TRAINEES at a starting salary of £3,865. p.a.

Relocation expenses considered.

Contact us immediately for application form (quote ref. 2390/ET and enclose s.a.e.): **BBC Appointments, London W1A 1AA. Tel: 01-580 4468, Ext. 4619.**

SLOAN ELECTRONIC EQUIPMENT			
117 ORBY DRIVE, BELFAST BT5 6AG. 35p Post			
SPEAKER Ω - 1½"	AUDIO LEADS 5 Pin Din Plug to 5 Pin Din Socket	8 C 108	10p
ET	5 Pin Din Plug to 4x3.5mm Plug	8 F Y 5 2	20p
PP3 CLIP 10p	4 x (Phono Plug to Phono Plug), all £5p each.	NE555	Timer
100 RESISTORS 85p	EARPHONE ON 3.5mm PLUS 12p	74-1	Op-Amp 17p
OPCO ROCKER 22p	5 Pin Din 180° 2 Pin Din 2.5mm	Plug 12p 9p 11p	Socket 12p 10p

PLEASE MENTION
ETI
WHEN REPLYING
TO ADVERTS

Earn £20-£100 p.w.
in your spare time
by introducing the revolutionary new
Flip-Caller telephone to your friends.
Features micro-chip controlled
push-button dialling and memory
recall. Sells itself. Generous
commission. For details write to Dept. ETI

IDL SUPERPHONE
P.O. Box 31, Twickenham TW2 5RL




ADVERTISEMENT INDEX

ACORN COMPUTERS	83	ELECTROVALUE	109	NIC MODELS	122
AITKEN BROS.	121	EXPERIMENTAL ELECTRONICS	114	N.T.C.	122
AKHTER INSTRUMENTS	118	GENERAL NORTHERN MICROCOM- PUTERS	100	OLSEN ELECTRONICS	8
ALEXANDER SYSTEMS	114	GMT ELECTRONICS	103	PARNDON ELECTRONICS	108
ALTEK INSTRUMENTS	114	GREENBANK	64	T. POWELL	120
AMBIT INTERNATIONAL	54	GREENWELD	123	POWERTRAN	2, 10, 115
AUDIO ELECTRONICS 30, 84 & 117		HAPPY MEMORIES	100	PROGRESSIVE RADIO	118
BAYDIS	103	HEATH ELECTRONICS	62	QUANTUM ELECTRONICS ...	121
BI-PAK SEMICONDUCTORS 42 & 43		HENRY'S RADIO 76, 84 & 107		RAPID ELECTRONICS	117
BK ELECTRONICS	102	ILP	4, 5 & 67	J. W. RIMMER	120
BNRS	63	KEELMORE LTD.	104	RISCOMP LTD.	16
BRAINTREE MICRO-LEISURE .. 59		KODE SERVICES	123	R.T.V.C.	86
CALCULATOR SALES & SERVICE 119		LASCAR ELECTRONICS	29	SAFGAN ELECTRONICS	126
CAMBRIDGE LEARNING	99	LB ELECTRONICS	122	SAXON ENTERTAINMENTS .. 108	
CARSTON ELECTRONICS	62	L. & B. ELECTRONICS	100	SCIENCE OF CAMBRIDGE . 46 & 47	
CASTLE ELECTRONICS	37	LINSAC	84	SILICA SHOP	106
CHILTMEAD	116	LINTON ELECTRONICS	8	SURETRON SYSTEMS	119
CHORDGATE	119	MACLIN-ZAND	71	SWANLEY ELECTRONICS	77
CHROMASONICS	58 & 59	MANOR SUPPLIES	84	TANGERINE COMPUTERS 112 & 113	
CHROMATRONICS	109	MAPLIN	132	TARGET ELECTRONICS	101
CLEF PRODUCTS	117	MARSHALLS	108	TECHNOMATIC	12
COMP, COMP, COMP .. 130 & 131		METAC	52 & 53	TELONIC	59
CRIMSON COMPONENTS	18	MICROCIRCUITS	78	TEMPUS	72 & 73
CROFTON ELECTRONICS	16	MINIKITS	8	TIMEDATA LTD.	108
C.S.C.	7, 31 & 114	MINIM AUDIO	103	TK ELECTRONICS	31
DELTA TECH & CO.	16	MITRAD	15, 22 & 23	TRANSAM COMPONENTS ... 68	
DISPLAY ELECTRONICS 110 & 120		MOUNTAINDENE	67	T. & T. ELECTRONICS	105
DK SUPPLIES	123	E. R. NICHOLLS	127	VIDEOTONE	9
DORAM ELECTRONICS	21			WATFORD ELECTRONICS ... 6 & 7	
				WILMSLOW AUDIO	105

MPA 200 100 WATT (rms into 8Ω) MIXER / AMPLIFIER

Featured as a constructional article in ETI, the MPA 200 is an exceptionally low priced — but professionally finished — general purpose high power amplifier. It features an adaptable input mixer which accepts a wide range of sources such as a microphone, guitar, etc. There are wide range tone controls and a master volume control. Mechanically the MPA 200 is simplicity itself with minimal wiring needed making construction very straightforward.

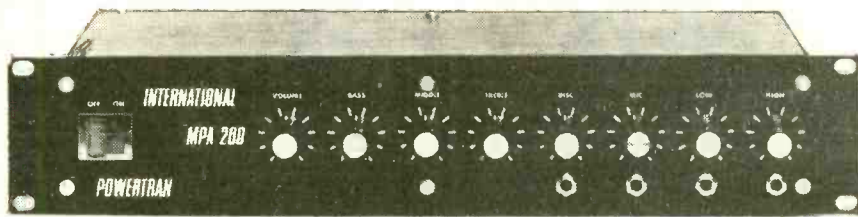The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc. — complete down to the last nut and bolt!



Panel size 19.0" x 3.5". Depth 7.3"

**COMPLETE KIT
ONLY
£49.90 + VAT!**

**MATCHES THE
CHROMATHEQUE 5000
PERFECTLY!**

CHROMATHEQUE 5000 5 CHANNEL LIGHTING EFFECTS SYSTEM

This versatile system featured as a constructional article in ELECTRONICS TODAY INTERNATIONAL has 5 frequency channels with individual level controls on each channel. Control of the lights is comprehensive to say the least. You can run the unit as a straightforward sound-to-light or have it strobe all the lights at a speed dependent upon music level or front panel control or use the internal digital circuitry which produces some superb random and sequencing effects. Each channel handles up to 500W and as the kit is a single board design wiring is minimal and construction very straightforward.

Kit includes fully finished metalwork, fibreglass PCB controls, wire, etc. — Complete right down to the last nut and bolt!




Panel size 19.0" x 3.5". Depth 7.3"

**COMPLETE KIT
ONLY
£49.50 + VAT!**

POWERTRAN

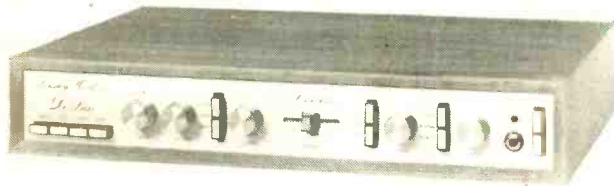
**SYNTHESIZER KITS ON PAGE 10. MORE KITS AND ORDERING
INFORMATION ON INSIDE FRONT COVER.**



DE LUXE EASY TO BUILD LINSLEY HOOD 75W STEREO AMPLIFIER £85.00 + VAT

This easy to build version of our world-wide acclaimed 75W amplifier kit based upon circuit boards interconnected with gold plated contacts resulting in minimal wiring and construction delightfully straightforward. The design was published in Hi-Fi News and Record Review and features include rumble filter, variable scratch filter, versatile tone controls and tape monitoring while distortion is less than 0.01%.

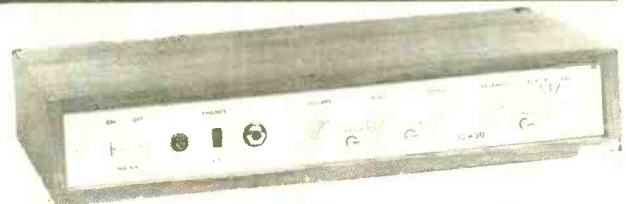All kits also available as separate packs (e.g. PCB, component sets, hardware sets, etc.). Prices in our FREE CATALOGUE.



T20 + 20 20W STEREO AMPLIFIER £33.10 + VAT

This kit, based upon a design published in Practical Wireless, uses a single printed circuit board and offers at very low cost, ease of construction and all the normal facilities found on quality amplifiers. A 30 watt version of this kit (T30+30) is also available for £38.40 + VAT. **MATCHING TUNERS — See our FREE CATALOGUE!**

Above 2 kits are supplied with fully finished metalwork, ready assembled high quality teak veneer cabinet, cable, nuts, bolts, etc. and full instructions — in fact everything!

BLACK HOLE

**MUSIC EFFECTS DEVICE — AS FEATURED
IN ELECTRONICS TODAY INTERNATIONAL!**

The BLACK HOLE designed by Tim Orr, is a powerful new musical effects device for processing both natural and electronic instruments, offering genuine VIBRATO (pitch modulation) and a CHORUS mode which gives a 'spacey' feel to the sound achieved by delaying the input signal and mixing it back with the original. Notches (HOLES) introduced in the frequency response, move up and down as the time delay is modulated by the chorus sweep generator. An optional double chorus mode allows exciting antiphase effects to be added. The device is floor standing with foot switch controls, LED effect selection indicators, has variable sensitivity, has high signal/noise ratio obtained by an audio compander and is mains powered — no batteries to change! Like all our kits everything is provided including a highly superior, rugged steel, beautifully finished enclosure.

COMPLETE KIT ONLY £49.80 + VAT (single delay line system)

De Luxe version (dual delay line system) also available for **£59.80 + VAT**

Cabinet size 10.0" x 8.5" x 2.5" (rear) 1.8" (front)



NOBODY CAN GET NEAR OUR PRICES EXCEPT OUR CUSTOMERS

RRP £540 **only £399** - VAT
ANADEX DP8000

Super Quality Low cost printer Tractor Feed with full 96 ASCII character set Accepts RS232C at baud rates between 100 and 9600 and Parallel Bt data Attaches either directly or through interfaces to Pet, Apple, TRS80, Sorcerer, Nascom, CompuKit etc.

THE NEW ANADEX DP9501
A PROFESSIONAL PRINTER

● Bi-directional printing
 ● Up to 220 chars/line with 4 print densities
 ● 500 char buffer
 ● RS232C and Centronics Parallel interface built in
 ● Full software control of matrix needles allowing graphics capability
 ● 200 chars/sec ● Adjustable width tractor feed.

All this for only **£895 + VAT**

THE ATARI VIDEO COMPUTER GAMES SYSTEM **£83.00**

Atari's Video Computer System now offers more than 1300 different game variations and options in twenty Game Program™ cartridges!

Most Cartridges only **£13.90 + VAT**
 Prices may vary with special editions Basic Maths Airsea Battle, Black Jack, Breakout, Surround, Spacewar, Video Olympics, Outlaw, Basketball, Hunt & Score, Space War, Sky Diver, Air Sea Battle, Codebreaker, Miniature Golf

Extra Paddle Controllers - **£14.90 + VAT** * Keyboard Controllers - **£16.90 + VAT**
SPACE INVADERS NOW IN STOCK £25

NEW TV GAME BREAK OUT

Has got to be one of the world's greatest TV games. You really get hooked. As featured in ET! Has also 4 other pinball games and lots of options. Good kit for upgrading old amusement games.

MINI KIT PCB, sound & vision modulator, memory chip and de code chip. Very simple to construct. **£14.90 + VAT**
OR PCB **£2.90** MAIN LSI **£8.50** Both plus VAT

WE ARE NOW STOCKING THE APPLE II EUROPLUS AT REDUCED PRICES

16K **£599**
 32K **£649**
 48K **£659** } VAT

Getting Started APPLE II is faster, smaller, and more powerful than its predecessors. And it's more fun to use too because of built-in features like:

- BASIC — The Language that Makes Programming Fun.
- High-Resolution Graphics (in a 54,000-Point Array) for Finely-Detailed Displays.
- Sound Capability that Brings Programs to Life.
- Hand Controls for Games and Other Human-Input Applications.
- Internal Memory Capacity of 48K Bytes of RAM, 12K Bytes of ROM; for Big-System Performance in a Small Package.
- Eight Accessory Expansion Slots to let the System Grow With Your Needs.

You don't need to be an expert to enjoy APPLE II. It is a complete, ready-to-run computer. Just connect it to a video display and start using programs (or writing your own) the first day. You'll find that its tutorial manuals help you make it your own personal problem solver.

EUROPE'S FASTEST SELLING ONE BOARD COMPUTER
COMPUKIT UK101

★ 6502 based system — best value for money on the market ★ Powerful 8K Basic — Fastest around ★ Full Qwerty Keyboard ★ 4K RAM Expandable to 8K on board. ★ Power supply and RF Modulator on board. ★ No Extras needed — Plug-in and go. ★ Kansas City Tape Interface on board. ★ Free Sampler Tape including powerful Dissassembler and Monitor with each Kit. ★ If you want to learn about Micros, but didn't know which machine to buy then **this is the machine for you.**

40 pin Expansion Jumper Cable for CompuKit expansion **£8.50 + VAT**

Build, Understand and Program your own Computer for only a small outlay **KIT ONLY £179 + VAT NO EXTRAS NEEDED**

Available ready assembled, tested & ready to go **£229 + VAT**

NEW MONITOR FOR COMPUKIT UK101
 ● In 2K Eprom 2716 ● Allows screen editing ● Saves data on tape ● Flashing cursor ● Text scrolls down **£22.00 + VAT**

FOR THE COMPUKIT

Assembler/Editor	£14.90	Game Packs	
Screen Editor Tape	£5.90	1. Four Games	£5.00
		2. Four Games	£5.00
		3. Three Games 8K only	£5.00

All Prices exclusive VAT

Super Space Invaders (8K)	£8.50
Space Invaders	£5.00
Chequers	£3.00
Real Time Clock	£3.00
Case for CompuKit	£29.50

HITACHI PROFESSIONAL MONITORS

9" — ~~£129~~ **£99.95**
 12" — ~~£199~~ **£149**

● **Reliability** Solid state circuitry using an IC and silicon transistors ensures high reliability. ● **500 lines horizontal resolution** Horizontal resolution in excess of 500 lines is achieved in picture center. ● **Stable picture** Even played back pictures of VTR can be displayed without jittering. ● **Looping video input** Video input can be looped through with built-in termination switch. ● **External sync operation** (available as option for U and C types) ● **Compact construction** Two monitors are mountable side by side in a standard 19-inch rack.

ENGLISH COLOUR TV/ AMERICAN NTSC COLOUR MONITOR

Suitable for Apple, Atari and Texas 99/4 **£295 + VAT**

8MHz Super Quality Modulators	£4.90
6MHz Standard Modulators	£2.90
C12 Computer Grade Cassettes	10 for £4.00
Anadex Printer Paper — 2000 sheets	£25.00
Floppy Discs 5 1/4" Hard end Soft Sected	£3.50
Floppy Disc Library Case 5 1/4"	£3.50
Verocases for Nascom 1 & 2 etc.	£24.90
Keyboard Cases	£9.90

MEMORY UPGRADES

16K (8 x 4116) **£29.90 + VAT**
 4K CompuKit (8 x 2114) **£29.90 + VAT**

SPECIAL OFFER

We will part exchange your Sinclair ZX80 for any of our products.

Refurbished ZX80's—fully guaranteed **£69.90 + VAT**
 (Supply dependant upon stocks)

We have one of the largest collections of Computer Books under one roof, along with racks of software for the PET and TRS80. **Come and see for yourself.**

NOW OPEN

OUR NEW SHOWROOM & SALES CENTRE AT
 311 Edgware Road,
 London W2.
 Telephone: 01-441 2922

SPECIAL—ONCE IN A LIFETIME OFFER!

RRP £740 **£499 + VAT**

16K **£399**
 32K **£449**
 48K **£499** + VAT

EXIDY SORCERER

For Personal or Business Use.
 32K or 48K memory 8K MicroSoft Basic in ROM Dual Cassette I/O RS232 I/O Parallel I/O (Centronics). Expansion available through optional extra S100 Motherboard. 69 Key keyboard including 16 key numeric pad.

Please add VAT to all prices — including delivery. Please make cheques and postal orders payable to **COMP SHOP LTD.**, or phone your order quoting **BARCLAYCARD, ACCESS, DINERS CLUB** or **AMERICAN EXPRESS** number. **CREDIT FACILITIES ARRANGED** — send S.A.E. for application form.

MAIL ORDER AND SHOP:
 14 Station Road, New Barnet, Hertfordshire, EN5 1QW (Close to New Barnet BR Station — Moorgate Line).
 Telephone: 01-441 2922 (Sales) 01-449 6596 Telex: 298755 TELCOM G

NEW WEST END SHOWROOM:
 311 Edgware Road, London W2. Telephone: 01-262 0387

OPEN — 10am - 7pm — Monday to Saturday

- ★ **IRELAND:** 30 Marlborough Street, Dublin 1. Telephone: Dublin 749933
- ★ **COMP SHOP USA,** 1348 East Edinger, Santa Ana, California, Zip Code 92705 Telephone: C101 714 5472526

COMP SHOP "Europes Largest Discount Personal Computer Stores"

COMP COMPUTER COMPONENTS (Part of the Compshop Ltd. Group)

BARCLAYCARD VISA AMERICAN EXPRESS DINERS CLUB INTERNATIONAL ACCESS

The new MAPLIN CATALOGUE is out on December 5th

A massive new catalogue from Maplin that's bigger and better than ever before. If you ever buy electronic components this is the one catalogue you must not be without. Over 300 pages, it's a comprehensive guide to electronic components with thousands of photographs and illustrations and page after page of invaluable data. We stock just about every useful component you can think of. In fact, well over 5000 different lines, many of them hard to get from anywhere else. Hundreds and hundreds of fascinating new lines, more data, more pictures and a new layout to help you find things more quickly.

MAPLIN

Maplin Electronic Supplies Ltd.
All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR
Telephone: Southend (0702) 554155. Sales (0702) 552911.
Shops:
159-161 King Street, Hammersmith, London W6. Telephone: (01) 748 0926
284 London Road, Westcliff-on-Sea, Essex. Telephone: Southend (0702) 554000
Both shops closed Mondays.



On sale
in all branches
of W H Smith
from Dec 5th
price £1

Breadboard 1980
26th to 30th November
Open 10 a.m. till 6 p.m. (and till 8 p.m. Thursday, 4 p.m. Sunday)
Royal Horticultural Halls,
Elverton Street, London
(Nr. St. James's Park Underground)
Visit our huge stand and
see our new 'single-chip' organ,
a new sequencer/composer,
and lots more.
Don't miss it!!

Post this coupon now for your copy of our 1981 catalogue price £1.
Please send me a copy of your 320 page catalogue. I enclose £1 (Plus 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the UK send £1.68 or 12 International Reply Coupons.
I enclose £1.25

Name _____

Address _____