

everyday electronics

JAN. 72


15p

**A NEW MAGAZINE
BRINGING A FASCINATING
HOBBY TO EVERYONE**


**PROJECTS EASY TO CONSTRUCT
THEORY SIMPLY EXPLAINED**



LAUGH SIMULATOR

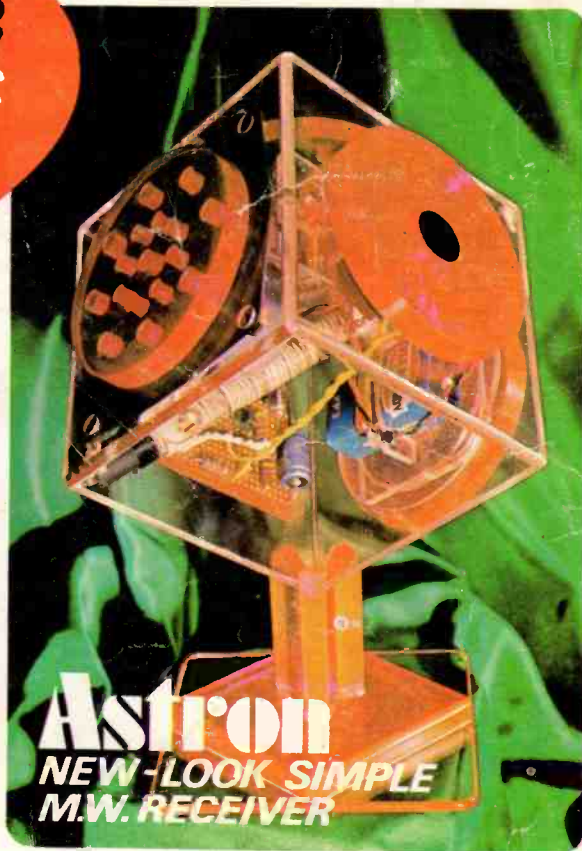

**Astron
NEW-LOOK SIMPLE
M.W. RECEIVER**

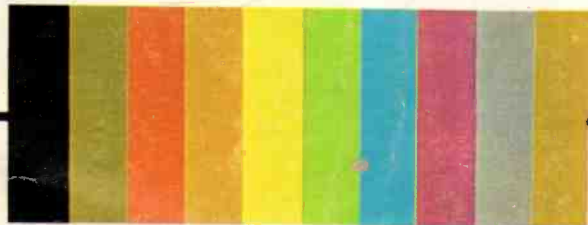

**TEACH-IN PART 3
RESISTOR COLOUR CODE
EXPLAINED**



**REMOTE
TEMPERATURE
COMPARATOR**

ADCOLA Soldering Instruments add to your efficiency

THE NEW 'INVADER'

ADCOLA L.646

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit*.

Standard temp. 360°C at 23 watts.

Special temps. from 250°C—410°C.

PRICE
£1.85

*Additional Stock Bits (illustrated) available

COPPER

B 38 $\frac{1}{4}$ " — 3.2 mm CHISEL FACE

B 14 $\frac{1}{8}$ " — 2.4 mm CHISEL FACE

B 24 $\frac{3}{16}$ " — 4.75 mm SCREWDRIVER FACE

B 12 $\frac{1}{8}$ " — 4.75 mm EYELET BIT

B 58 $\frac{1}{2}$ " — 6.34 mm CHISEL FACE

LONG LIFE

B 42 LL $\frac{3}{16}$ " — 4.75 mm CHISEL FACE

B 38 LL $\frac{1}{4}$ " — 3.2 mm CHISEL FACE

B 14 LL $\frac{3}{16}$ " — 2.4 mm CHISEL FACE

B 44 LL $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.



ADCOLA PRODUCTS LTD.
(Dept. Y), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.
Telephone: 01-622 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851

* Write for price list and catalogue

SAFELOC

of robust construction


Safe, quick and secure it connects 2-core and 3-core bare-ended flexible leads to the mains (A.C. only).

The concept was pioneered by Rendar, and introduced to the market 13 years ago.

Safebloc saves time. No need to fit a plug for tests. No danger, as no current can pass with the lid open.

Invaluable for testing and demonstrations in industry and shops, the work bench and the home.

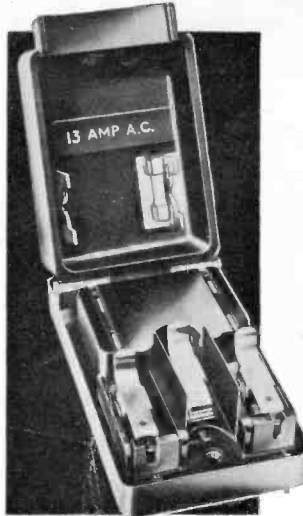Ask for Safebloc at your local stockist — or you can order it direct from the manufacturer.



If ordering by post, send cash with order.

PRICE £2.60+10p P.&P. EACH

Special bulk order wholesale and industrial rates on application



RENDAR®

Rendar Instruments Ltd., Victoria Road,
Burgess Hill, Sussex. Tel. Burgess Hill 2642

FELSTEAD (EE3) ELECTRONICS

LONGLEY LANE, GATLEY, CHEADLE, CHESHIRE SK6 4EE

Selection from our list, sent free for stamped addressed envelope. (Free overseas). Cash with Order only—No COD or Caller service. Charges (Min. 6p.) in brackets after all items apply to G.B. & Eire only. Regret Orders under 25p. plus charges unacceptable. SAE please, for enquiries or cannot be replied to. Overseas Orders welcomed.

RECORDING TAPE: Finest quality/value British Mylar available: STANDARD 5" 600ft 38p; 5" 900ft 60p; 7" 1200ft 56p; LONG PLAY 5" 900ft 56p; 5" 1200ft 56p; 7" 1800ft 90p. (7p on 5" and 5 1/2", 9p on 7"). Other sizes, Cassettes and accessories in list. **GARRIDGES:** All with standard fittings and stylus. Mono GP67 85p; Stereo-compatible Mono GP91/8C £1.10; STEREO GP93 £1.40; Stereo Ceramic GP94 £1.95. Comparatives shown in list with more types incl. Sonotone 9TAHC Goldring &c. at lowest prices (6p) **DIAMOND STYLUS:** Single tip types: Aces GP37 GP59 GP65/67 GP71. BBR TCS/LP/ST. COLLARO C, P and DC284; GARRARD GC2, GC3, GC12, GC510; RONETTE BF40, O, P and T; PHILIPS 3301 (3060, 3066, 3302, 3304) 3010 (12, 13, 16); SONOTONE ST9/TOT. ALL AT 40p each (6p). Double-tin turn-over types (78 sap. on other side). For ACOS GP73, GP91 (for cartridges GP93, GP94 &c.) GP91SC (for stereo-compat. types) GP104, BBR ST4 (ST3, ST5), ST9 (ST8), ST12/14/15, SONOTONE 2TA, 9TA, 9TAHC, PHILIPS 3306 (3310, 3224, 3228/22, GP280) GARRARD GCM21, 22, GC823, GKS25 and 26, GCM21T and 22T, GKM24T, GCS231, GKS25T & 26T GCM31, GCS36, GCS39, GCS38, KS40A, KS41B, etc. ALL AT 75p (6p). **DOUBLE DIAMOND STYLUS:** (Same dia. tip each side: no 78) for all types £1.50 (6p). **PICK-UP WIRE:** Super thin twin flex screened, sheathed, 6p per yard. (Up to 6 yds, 6p, over charges paid.) All sapphires in list. **MICRO-PHONES:** CRYSTAL: LAPEL 14", clip/hand, lead 3.5mm jack plug 32p (6p). CM20 Cream Plastic hand 52p; CM21 Grey Plastic Hand/Desk 62p; both have 3.5mm jack plug and lead (6p either). "STICK" 60 £1.02; CM70 "PLANET" Metal, tapered, with neck cord, adaptor for stands £1.47; "MIC 91" hand/Desk 81p; "MIC 45" Curved metal hand grip £1.00. All with leads (all 6p). **MICROPHONE INSERTS** Diam. 1.75" or 0.9" either size 27p (Up to 6 for 6p.) **DYNAMIC:** 209 Cardioid Ball, 50K/600 Ω, built-in volume control, on/off switch, special 20ft lead, the best value anywhere £6.30; UD130, uni-dir. mesh ball 50K/600 Ω jack plug, cable, adaptor, 24.80; DM160, omni-dir. ball mesh, 50K, cable, adaptor, jack plug £3.874 (27p each). **SPEAKERS:** 8411 very popular 12" ROUND, fitted tweeter, 3 or 16 ohms (state which) £1.874 (27p) — or pair for stereo £4.95 charges paid. **SMALL 2 1/4" 3 Ω or 8 Ω, state which 37p (6p).** More speakers in list. **HEADPHONES:** High resistance 2000 Ω adjustable 82p (7p). **EARPIECES** with lead and min. 2.5mm or 3.5mm (state which) jack plug, MAGNETIC 9p. CRYSTAL (3.5mm plug only) 24p (up to 3 for 6p. any type). **SOLDERING IRON.** Slim, modern, British high speed, 81", all parts replaceable, highest quality fully guaranteed £1.073 (10p). **TRANSFORMERS:** Sub-min 11x11x12mm, OUTPUT (3 Ω for OC72, &c.) 14p, or DRIVER 15p (6p) 12 for 6p. **CONNECTING WIRE.** Packs of 5 coils, each coil 5 yds, astal. coils. **SOLID CORE 14p.** FLEXIBLE or SUPER THIN for transistor wiring &c. either 16p. (Any pack 6p). **RETRACTABLE FLEXIBLE LEADS.** (CURLIES): With phono plug ea. end 6ft 25p, 12ft 38p. With phono plug/phone socket other end 6ft 25p. 12ft 42p (6p lead any type). **VIBRATORS.** 12V 4-pin non-synch 121HD4, 24" ex. pins 27p. SAME but 3 1/4" ex. pins, USA. 20p. 12V 7-pin, synch. (12B7) 24" ex. pins 62p (6p any type). **TRANSISTORS &c.** AC126 121p, AD15 20p, AF16 16p, AF17 20p, OA1 10p, OA10p, OA10p, OA81 10p, OC44 14p, OC45, OC71, OC72, OC75, OC81, OC810, OC820, all at 12p each, OC170 20p, OC171 12p, BY100/800piv 14p. Many more incl. power types, thyristors, &c., in list. **MAINS NEONS,** 4y leads 10p. **NEON SCREWDRIVER** (pocket tester) 17p (6p either). **MAINS BATTERY ELIMINATOR.** Input 240V AC, Output 3, 6, 74 and 9V DC by switch selector. On/off switch, pilot lamp, leads, plug, adaptor to suit most transistor sets and cassette recorders. Suitable for model use. £2.15 (24). **OUR CURRENT LIST** (see heading) includes more details of all above plus cartridge replacement table, many unrepeatable Special Offers, and cable, croc. clips, Volume controls, Din plugs, CO-AX, standard, miniatur, phono plugs, sockets and adaptors, Tape Recording and Record Player accessories, panel and Test meters and equipment, Multimeters, min. motors, test prods, switches—rotary, toggle, slide cabinet, lamp &c.—electrolytics, terminals, Veroboard, valve holders, extension aerials for cars and portable sets, ind. lamps and bulbs, dials, mikes, telephone amplifiers and pick-ups, dials, drive cord, inter-coms, sub (testing) boxes, stereo headphones etc., etc.



Merry Christmas



from

HOME RADIO

★Give **YOURSELF** a Christmas present! Post this Coupon with Cheque or P.O. for 70p for a copy of our Components Catalogue.

Please write your Name and Address in block capitals.

Name

Address

HOME RADIO (Components) LTD.
Dept. EE, 234-240 London Rd., Mitcham, CR4 3HD

To all customers—past, present and future—Home Radio send the Season's Greetings, hoping not only that you have a happy Christmas, but that the fun and satisfaction you get from radio and electronics will continue through the coming years.

Needless to say, we are confident that we can help to ensure the happy fulfilment of all your projects and plans. The service we offer to constructors and enthusiasts has won us a reputation second to none. Our famous catalogue is acknowledged as "the Bible of the components world". Have you an up-to-date copy?

The price of 70p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

YATES ELECTRONICS

(FLITWICK) LTD

RESISTORS

1/2W Iskra high stability carbon film—very low noise—capless construction.
1/4W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm. 4WV
Erie wire wound.

Power watts	Tolerance	Range	Values available	Price
1/2	5%	4.7Ω-2.2MΩ	E24	1.00 +
1/2	10%	3.3MΩ-10MΩ	E12	1.00 +
1/4	10%	1Ω-3.9Ω	E12	1.00 +
1/4	5%	4.7Ω-1MΩ	E12	1.00 +
4	10%	1Ω-10Ω	E12	6p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log 1/2W, lin 1/4W).
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch 24p.

SKELTON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C.
mounting (0-1 matrix).
Sub-miniature 0-1W, 5p each. Miniature 0-25W, 6p each.

SEMICONDUCTORS

AC126	12p	BFY52	22p	OC81	12p	2N3055	72p
AC127	12p	BSY56	30p	OC82	12p	2N3702	15p
AC128	12p	BSX21	25p	ORP12	48p	2N3703	14p
AD140	40p	BY124	71p	IN4001	71p	2N3704	171p
AF115	20p	BYZ10	20p	IN4002	10p	2N3705	15p
AF117	20p	BYZ13	20p	IN4003	11p	2N3706	12p
BC107	10p	OA85	7p	IN4004	12p	2N3707	181p
BC108	10p	OA91	7p	IN4005	13p	2N3708	10p
BC109	10p	OA202	7p	IN4006	13p	2N3709	11p
BFY50	22p	OC71	12p	IN4007	13p	2N3710	12p
BFY51	22p	OC72	12p	2N2926	11p	2N3711	14p

ZENER DIODES

400mW 5% 3.3V to 30V, 15p.

ROTARY SWITCHES

2P2W, 1P12W, 2P6W, 3P4W,
4P3W, 23p.

BRUSHED ALUMINIUM PANELS

12in x 6in=25p; 12in x 21in=10p; 9in x 2in=7p.

DEPT. E.E.

ELSTOW STORAGE DEPOT,
KEMPSTON HARDWICK,
BEDFORD.

C.W.O. PLEASE. POST AND PACKING,
PLEASE ADD 10p TO ORDERS UNDER £1.

Catalogue which contains data sheets for most of the
components listed will be sent free on request.
5p stamp appreciated.

10% DISCOUNT TO ALL CALLERS ON SATURDAYS

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0-001μF, 0-0015μF, 0-0022μF, 0-0033μF, 0-0047μF, 0-0068μF, 0-01μF,
0-015μF, 0-022μF, 0-033μF, 3p, 0-047μF, 0-068μF, 0-1μF, 4p, 0-15μF, 6p, 0-22μF, 71p,
0-33μF, 11p, 0-47μF, 13p.
160V: 0-01μF, 0-015μF, 0-022μF, 0-033μF, 0-047μF, 0-068μF, 3p, 0-1μF 3p, 0-15μF,
4p, 0-22μF, 5p, 0-33μF, 6p, 0-47μF, 71p, 0-68μF, 11p, 1-0μF, 13p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0-01μF, 0-015μF, 0-022μF, 3p, 0-033μF, 0-047μF, 0-068μF,
31p, 0-1μF, 4p, 0-15μF, 0-22μF, 5p, 0-33μF, 6p, 0-47μF, 81p, 0-68μF, 11p, 1-0μF, 13p,
1-5μF, 20p, 2-2μF, 24p.

MYLAR FILM CAPACITORS 100V

0-001μF, 0-002μF, 0-005μF, 0-01μF, 0-02μF
21p, 0-04μF, 0-05μF, 0-068μF, 0-1μF, 31p.

CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

CAPACITOR DEVELOPMENT PACK

Selection of 100 ceramic and polyester capacitors, 100pF to 1-0μF, £2.90.

ELECTROLYTIC CAPACITORS—MULLARD C426 SERIES

6p each
(μF/V): 10/2-5, 40/2-5, 160/2-5, 320/2-5, 500/2-5, 8/4, 32/4, 64/4, 125/4, 250/4,
400/4, 6-4/6-4, 25/6-4, 50/6-4, 100/6-4, 200/6-4, 320/6-4, 4/10, 16/10, 32/10, 64/10,
125/10, 200/10, 2-5/16, 10/16, 20/16, 40/16, 80/16, 125/16, 1-6/25, 6-4/25, 12-5/25,
25/25, 50/25, 80/25, 1/40, 4/40, 8/40, 16/40, 32/40, 50/40, 0-64/64, 2-5/64, 5/64, 10/64,
20/64, 32/64.

ELECTROLYTIC CAPACITORS Miniature P.C. mounting

(μF/V): 10/12, 50/12, 100/12, 200/12, 5/25, 10/25, 25/25, 100/25.

5p each.

VEROBOARD

2 1/2 x 3 1/2	0-1	0-15
2 1/2 x 3 1/2	22p	17p
2 1/2 x 5	24p	21p
3 1/2 x 3 1/2	24p	21p
3 1/2 x 5	28p	28p
17 x 2 1/2	75p	57p
17 x 3 1/2	100p	78p
17 x 5 (plain)	—	82p
17 x 3 1/2 (plain)	—	60p
17 x 2 1/2 (plain)	—	42p
2 1/2 x 5 (plain)	—	12p
2 1/2 x 3 1/2 (plain)	—	11p
Pin insertion tool	52p	52p
Spot face cutter	42p	42p
Pkt. 50 pins	20p	20p

JACK PLUGS AND SOCKETS

Standard screened	18p	2-5mm insulated	8p
Standard insulated	12p	3-5mm insulated	8p
Stereo screened	35p	3-5mm screened	13p
Standard socket	15p	2-5mm socket	8p
Stereo socket	18p	3-5mm socket	8p


D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin
Plug 12p. Socket 8p.

BATTERY ELIMINATOR

£1-50
9V mains power supply. Same size as PP9 battery.

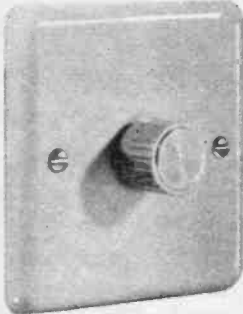Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The ivory mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300 w or 600 w of all lights except fluorescents at mains voltages from 200-250 v, 50Hz. The DIMMASWITCH has built-in radio interference suppression:

600 Watt - £3.20. Kit Form £2.70

300 Watt - £2.70. Kit Form £2.20


All plus 10p post and packing.

Please send C.W.O. to:—

DEXTER & COMPANY

5 ULVER HOUSE, 19, KING STREET,
CHESTER CH1 2AH Tel: 0244-25883,
As supplied to H.M. Government Departments.

VEROBOARD

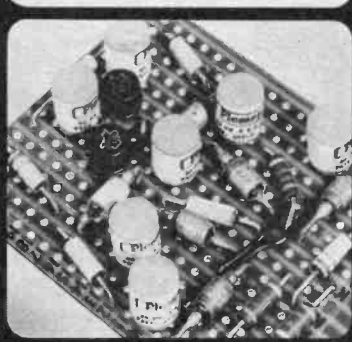

VEROBOARDS GIVE A PROFESSIONAL
FINISH TO YOUR WORK

0.1" and 0.15" pitch, plain and copper

clad universal circuit boards.

AVAILABLE FROM YOUR LOCAL RETAILER.

TRADE DISTRIBUTOR N. Rose (Electrical) Ltd., London, W.C.1.



VERO ELECTRONICS LTD.
Industrial Estate, Chesham's Ford,
SOS 32R Tel: Chesham's Ford 2521

INSTRUMENTAL AUDIO EFFECTS

SUPER "FUZZ" UNIT KIT. CONNECTS
BETWEEN GUITAR & AMPLIFIER. OPER-
ATES FROM 9v BATTERY (not supplied).
ALL COMPONENTS AND PRINTED CIRCUIT
BOARD WITH FULL INSTRUCTIONS. KIT
PRICE: £2-60 post paid.

CREATE "PHASE" EFFECT ON YOUR
RECORDS, TAPES ETC., UNIQUE CIRCUITRY
ENABLES YOU TO CREATE PHASE
EFFECT AT THE TURN OF A KNOB. OPER-
ATES FROM 9v BATTERY (not supplied)
COMPLETE KIT OF COMPONENTS WITH
PRINTED CIRCUIT BOARD & FULL INSTRU-
CTIONS. KIT PRICE: £2-60 post paid.

MAIL ORDER ONLY.

S.A.E. ALL ENQUIRIES.

DABAR ELECTRONIC PRODUCTS

98a, LICHFIELD STREET,
WALSAIL, STAFFS. WS1 1UX

28watts, r.m.s. 40Hz to 40kHz \pm 3dB



Viscount III Audio Suite complete **£49**



There are two stereo amplifiers—the R100 for ceramic cartridges, the R101 for magnetic and ceramic. Both incorporate FETs (FIELD EFFECT TRANSISTORS), just like top-priced units. FETs give you more of the signal you want, and almost none of the background hiss you don't. Both units have a jack socket to plug in headphones and there's a separate output for tape recorder. Filters (an unusual feature in this price range) and tone controls give a wide range of bass and treble adjustment which compensate for input deficiencies and domestic acoustic conditions.

PRICES SYSTEM 1

Viscount III R101 amplifier	£22.00 + 90p p&p
2 x Duo Type II speakers,	£14.00 + £2 p&p
Garrard SP25 Mk. III with MAG.	
cartridge plinth and cover	£23.00 + £1.50
	p&p
Total	£59.00

Available complete for only **£52.00 + £3.50 p&p**

SYSTEM 2

Viscount R101 amplifier	£22.00 + 90p p&p
2 x Duo Type III speakers	£32.00 + £3 p&p
Garrard SP25 Mk. III with MAG.	
cartridge, plinth and cover	£23.00 + £1.50
	p&p
Total	£77.00

Available complete for **£69 + £4 p&p**

SYSTEM 3

Viscount III Amplifier R100	£17.00 + 90p p&p
2 x Duo Type II speakers, pair	£14.00 + £2 p&p
Garrard SP25 Mk. III with CER, diamond	
cartridge, plinth and cover	£21.00 + £1.50
	p&p
Total	£52.00

Available complete for only **£49.00 + £3.50 p&p**

SPEAKERS Duo Type II

Size approx 17" x 10½" x 6½". Drive unit 13" x 8" with parasitic tweeter. Max. power 10 watts. 3 ohms. Simulated Teak cabinet. £14 pair + £2 p&p.

Duo Type III Size approx 23½" x 11½" x 9½". Drive unit 13½" x 8½" with H.F. speaker. Max. power 20 watts at 3 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32 pair + £3 p&p.

SPECIFICATION R101

14 watts per channel into 3 to 4 ohms. Total distortion @ 10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K. equalised within \pm 1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities; headphone socket, power out 250mW per channel. Tone controls and filter characteristics. Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. Signal to noise ratio: (all controls at max) R101—P.U.1 and radio—65dB. P.U.2. —58dB. R100 same as R101 but P.U.2 (for crystal cartridges) 450mV into 3 Meg. Cross talk better than -35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx 13½" x 9" x 3½".

R+TV

Radio and TV Components (Acton) Ltd. 21E High Street, Acton, London W3 6NG
323 Edgware Road, London, W.2. Mail orders to Acton. Terms C.W.O. All enquiries S.A.E.
Goods not despatched outside U.K.

Sinclair Q16/Micromatic

Q16 High fidelity loudspeaker

The Q16 employs the well proven acoustic principles specially developed by Sinclair in which a special driver assembly is meticulously matched to the characteristics of the uniquely designed cabinet. In reviewing this exclusive Sinclair design, technical journals have justly compared the Q16 with much more expensive loudspeakers. Its shape enables the Q16 to be positioned and matched to its environment to much better effect than is the case with conventionally styled enclosures. A solid teak surround with a special all-over cellular foam front is used as much for appearance as its ability to pass all audio frequencies without loss.

This elegantly designed shelf mounting speaker brings genuine high fidelity within reach of every music lover.

Specifications:

Construction: Special sealed seamless sound or pressure chamber with internal baffle.

Loading: up to 14 watts RMS.


Input Impedance: 8 ohms.

Frequency response: From 60 to 16,000 Hz. confirmed by independently plotted B and K curve.

Driver unit: Special high compliance unit having massive ceramic magnet of 11,000 gauss, aluminium speech coil and special cone suspension for excellent transient response.

Size and styling: 9½ in. square on face x 4½ in. deep with neat pedestal base. Black all over cellular foam front with natural solid teak surround.

Price £8.98.

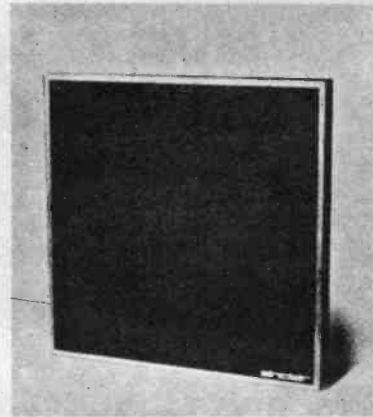

Britain's smallest radio

Considerably smaller than an ordinary box of matches, this is a multi-stage AM receiver brilliantly designed to provide remarkable standards of selectivity, power and quality for its size. Powerful AGC counteracts fading from distant stations; bandspread at higher frequencies makes reception of Radio 1 easy. The plug-in magnetic earpiece provided, matches the Micromatic's output to give wonderful standards of reproduction. Everything including the special ferrite rod aerial, and batteries is contained within the minute attractively designed case. Whether you build a Micromatic kit or buy this amazing receiver ready built and tested, you will find it as easy to take with you as your wrist watch, and dependable under the severest listening conditions.

Specifications:

Size: 36 x 33 x 13 mm (1.8 x 1.3 x 0.5 in.)

Weight: including batteries, 28.4 gm (1 oz.)

Case: Black plastic with anodised aluminium front panel and spun aluminium dial.

Tuning: medium wave band with bandspread at higher frequencies (550 to 1,600 KHz).

Earpiece: Magnetic type.

On/off switching: By inserting and withdrawing earpiece plug.

Kit in pack with earpiece, case, instructions and solder **£2.48.**

Ready built, tested and guaranteed, with earpiece **£2.98.**

Two Mallory Mercury batteries type RM675 required from radio shops, chemists, etc.



To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send _____

Name _____

Address _____


for which I enclose cash/cheque/money order

E.E. JA

Sinclair Radionics Ltd., London Rd, St. Ives
Huntingdonshire PE17 4HJ.
Telephone St. Ives (048 06) 4311

sinclair

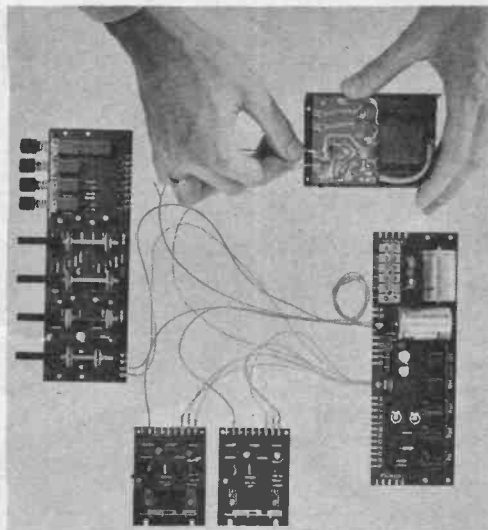Project 605 the new simple way to assemble Sinclair high fidelity modules



For several years now you have been able to assemble your own high fidelity system to world beating standards using Sinclair modules. We have progressively improved these technically but hitherto the method of assembly at your end has remained the same – there has been no alternative to a soldering iron. Now for those who prefer not to solder, there is an alternative – Project 605.

In one neat package you can now obtain the four basic Project 60 modules plus a fifth completely new one – Masterlink – which contains all the input sockets and output components you previously bought separately. Also in the Project 605 pack are all the inter-connecting leads, cut to length and fitted at each end with plugs which clip straight onto the modules, eliminating soldering completely. The pack contains everything you need to build a complete 30 watt stereo amplifier together with a clear well illustrated Instruction Book. All you have to do is to arrange your modules in the plinth or case of your choice and then clip them together – the work of a few minutes.

Your hi-fi system will, as we said, match the finest in the world and you can add to it at any time to increase power or extend the facilities. For example a superb stereo FM Tuner unit is obtainable for only £25.

Guarantee If within 3 months of purchasing Project 605 directly from us, you are dissatisfied with it, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail, Air-mail charged at cost.

sinclair

Sinclair Radionics Ltd., London Road.,
St. Ives, Huntingdonshire PE17 4HJ.
Telephone: St. Ives (04806) 4311

Specifications

Output – 30 watts music power (10 watts per channel R.M.S. into 3Ω).

Inputs – Mag. P.U. – 3mV correct to R.I.A.A. curve 20–25,000

Hz ± 1dB. Ceramic pick-up – 50mV. Radio – 50 to 150mV.

Aux. adjustable between 3mV. and 3V.

Signal to noise ratio – Better than 70dB.

Distortion – better than 0.2% under all conditions.

Controls – Press buttons for on-off, P.U., radio and aux. Treble

+15 to –15 dB at 10 kHz. Bass +15 to –15 dB at 100 Hz.

Volume, Stereo Balance.

Channel matching within 1dB.

Front panel – brushed aluminium with black knobs.

Project 605 comprises Stereo 60 pre-amp/control

unit, two Z-30 power amplifiers, PZ-5 power supply

unit, the unique new Masterlink, leads and instructions

manual complete in one pack. Post free

£29.95

To SINCLAIR RADIONICS LTD., ST. IVES, HUNTINGDONSHIRE PE17 4HJ

Please send Project 605 post free Details and list of stockists

Name

Address

for which I enclose £29.95 cheque/money order/cash. E.E. 3B

CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER
DEPT.
No. 11
MAYES RD.
LONDON
N22
6TL

COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY (WE CLOSE ALL DAY THURSDAY)

13 SOUTH MALL, EDMONTON, N-9 803 1685

MIDGET FLEX CONNECTOR
Approx. 2 amp rating.
Two pin non reversible midget flex connector. Approx. size: 2in. x 1/2in. Ideal for loudspeaker connections, etc. 8p plus 2p P. & P.

MAINS TRANSFORMER
Fused Primary 240V. Secondary 220V @ 50M/A. 6-3V. @ 1A. This transformer is made to a very high standard and is a small size: 2in. x 2 1/2in. x 2 1/2in. 63p plus 15p P. & P.

HIGH QUALITY IMPORTED HEADPHONES

1,000 Ω per phone ... **80p**
2,000 Ω per phone ... **88p**
Plus 10p P. & P. per pair.

STEREO HEADSET
8 ohm impedance, complete with plug and 5ft lead. A very comfortable phone set. Listen to stereo without noise interrupting the pleasure. Wonderful value. **£2.50** plus 10p P. & P.

LOW VOLTAGE AMPLIFIER Few only at
5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output. With high IMP input this amplifier will work as a record player, baby alarm, etc. amplifier.



2N3055
POPULAR POWER TRANSISTOR
Now at our Low Price 80p each
Please include 5p P. & P.


BARGAIN S.C.R.
TESTED THYRISTOR
400 volt. 3 amp.
45p each for £2.00
Please include 5p P. & P.



C.R.I.C. MANUFACTURERS REJECT BUT EXPERIMENTERS DELIGHT
Try the following Projects—
1. Stabilised Power Supply
2. Motor Speed Control
3. OBC or Door Buzzer
4. Windscreen Wiper Control
All possible with this Scopop I.C. We supply circuit information with every order.
I.C.R.I.C. — 12p 5 C.R.I.C. — 50p
Please include 5p P. & P. up to 5 I.C.S.



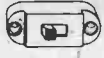
D.P.D.T. SLIDE SWITCH
SIZE
1 1/2 ins long 3/4 wide
13p
each
3p Postage



WAFER SWITCHES
1 pole 12 way
2 pole 2 way
2 pole 3 way
2 pole 4 way
2 pole 6 way
3 pole 4 way
4 pole 3 way
22p each. Please inc. 5p P. & P. Up to 3 switches.



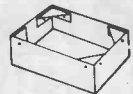ALUMINIUM CHASSIS
Made from 18 gauge aluminium 4 sided chassis with corner brackets. All are 2 1/2" depth.
6x3—41p 12x3—53p 14x 9—84p
6x4—45p 12x5—61p 16x6—86p
8x6—53p 12x8—80p 16x10—108p
10x7—83p 12x8—80p
Please send 10p per chassis P. & P.



CAPACITORS
Mini Electrolytics all values up to 100MFD @ 15V—7p each. Small P.P. Capacitors only in packs of 10 but you can mix values—25p for 10.
250MFD @ 25V—15p
500MFD @ 25V—21p
1000MFD @ 25V—27p
2000MFD @ 25V—34p
3000MFD @ 25V—45p
5000MFD @ 25V—58p
Please inc. 10p. P. & P. with orders under £2 value.

PRINTED CIRCUIT BOARD
8x6—10p 10x8—15p
9x5—10p 12x12—30p
Please inc. 3p. per board P. & P.




POTENTIOMETERS
All types 1" and less diameter. SINGLES DUAL
5K Log or 5K
10K Lin Less 10K
25K Switch 25K Less
50K Switch 50K
100K 17p ea, 45p.
250K Double 250K
500K Pole 500K each
1M Switch 1M
2M 25p ea, 2M



RESISTORS
We stock all recognised values of resistors all at 10% or closer tolerance. We regret we can only mail them in lots of ten. You can send for mixed values.
All Midget types.
4 watt lots of 10—13p
1 watt lots of 10—13p
1 watt lots of 10—25p
Please include 3p P. & P. for each 10 resistors.

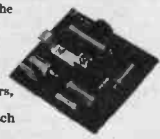EA1000 3 WATT AUDIO AMPLIFIER MODULE
An Audio Amplifier designed around the TAA621 Linear I.C.—
Supply Voltage ... 9-24V
Speaker Imp. ... 8-16 ohm
Frequency ... 50Hz-25kHz
Overall Size ... 2in x 3in x 1in
Ideal Amplifier for radios, record players, stereo units, etc.
Full technical data and diagrams with each module. All guaranteed and a bargain at



£2.63 + 5p P. & P.

YOUR OWN PROFESSIONAL SOLID STATE CLOSED CIRCUIT TELEVISION CAMERA

ONLY **£70** INCLUDING LENS & VIDICON TUBE

Designed by the Mullard Educational Service, and shown on the BBC's 'Tomorrow's World' programme, the Linstead camera provides a composite output comprising sync. pulse and picture information.
Free 78-page manual
We give you a superb, fully illustrated 78-page construction and service manual with this kit. Apart from full assembly instructions, a complete description of basic camera principles, vidicon tube operation and circuit diagram, this manual shows all waveforms within the circuitry. We also supply a copy of the BBC Test Card F.



The basic kit, excluding lens and tube costs only **£45**
A COMPLETE FULLY CONSTRUCTED AND TESTED CAMERA COST ONLY £99.85

Components are also available separately (for instance mains transformer £2.50 each).
For full details, send S.A.E. today.
Dept. E/E
RoslynWorks, Roslyn Rd.
LONDON, N.15
Telephone: 01-802 5144

Linstead ELECTRONICS

AERIAL BOOSTERS
We make four types of Aerial Boosters. L45 825 U.H.F., L12 V.H.F. TV, L11 V.H.F. Radio, L10 M/W & S/W. Price L45, L12 & L11 £2.95, L10 £2.45.

VALVE BARGAINS
Any 5 = 45p, 10 = 70p:
ECC82, ECL80, EP80, EP85, EP183, EF184, EB789, EB91, EY86, PC834, PC839, PC97, PCF80, PCF86, PCL82, PCL83, PCL84, PCL85, PL36, PY83, PY82, PY800, PY801, 30L18, 30C15, 6-30L2.

TRANSISTOR BARGAINS
We offer the following brand new, marked transistors for sale. Any 5—40p, 10—75p: BC113, BC115, BC117, BC171, BC136, BC153.

PRINTED CIRCUIT BOARD
8x6 by 4 ins boards complete with etching compound and instructions—40p.
MAINS DROPPERS
Three section 33-33-33 Ohms 9p.

POST & PACKING under £1.5p Over £1.10p. S.A.E. for leaflets on all items. Money back guarantee if not completely satisfied.

VELGO ELECTRONICS

62B Bridge Street, Ramsbottom, Bury, Lancs.

WILSIC SOUND EFFECTS KITS WAH-WAH PEDAL KIT (Illustrated)




Kit comprises a SELECTIVE AMPLIFIER MODULE KIT to convert the FOOT VOLUME CONTROL PEDAL (as photo) to Wah-Wah operation. Amplifier module £1.75, pedal unit £5.13, COMPLETE KIT £6.50 add 38p for assembly of module, but please note we cannot supply kits fully built.

REVERBERATION UNIT KIT. For dimension effect. Connects between sound source, mic., etc., and amplifier. Battery powered. COMPLETE KIT £9.20 (excluding case £7.50). Assembled in slimline cabinet £12.50.
VIBRATO UNIT KIT. Foot pedal unit with variable speed and depth controls. COMPLETE KIT £5.25.
SEND 15p for the WILSIC PLANS BOOK, with full details of these kits; circuits, drawings and price lists.

LATEST CATALOGUE 5p (stamps)
WILSIC ELECTRONICS LTD.
6 COPLEY ROAD, DONCASTER, YORKS.

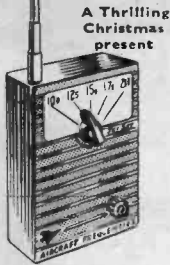EAVESDROP ON THE EXCITING WORLD OF AIRCRAFT COMMUNICATIONS — JUST OUT V.H.F. AIRCRAFT BAND CONVERTER



A Thrilling Christmas present

Many thousands of v.h.f. Aircraft Band Converters now selling in U.S.A. Listen in to AIRLINES, PRIVATE PLANES, JETPLANES. Eavesdrop on exciting cross-talk between pilots, ground approach control, airport tower. Hear for yourself the disciplined voices hiding tenseness on talk-downs. Be with them when they have to take nerve-ripping decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including HEATHROW, GATWICK, LUTON, RINGWAY, PRESTWICK ETC., ETC. CLEAR AS A BELL. This fantastic fully transistorised instrument can be built by anyone nine to fifteen in under two hours. (Our design team built four—everyone worked first time). No knowledge of radio or electronics required. No soldering necessary. Fully illustrated simply worded instructions take you step-by-step. Uses standard PP3 battery. Size only 4 1/2" x 3" x 1 1/2". All you do is extend rod aerial, place close to any ordinary medium-wave radio (even tiny portables) NO CONNECTIONS WHATSOEVER NEEDED. Use indoors or outdoors. THERE WILL BE ENORMOUS DEMAND FOR THIS NEW DESIGN. SEND NOW, ONLY £2-37 + 23p p. & p. for all parts, including case, nuts, screws, wire, etc., etc. (Parts available separately).

ONLY £2-37

FIND BURIED TREASURE! TREASURE LOCATOR TRANSLISTORISED

NOW IT'S HERE AT LAST, after experimenting for four and a half months with a multitude of different circuits and carrying out actual field tests with prototypes, our design team have come up with this real winner. This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phones used)—uses

any transistor radio which fits inside—no connections needed. FINDS GOLD, SILVER, LOST COINS, JEWELLERY, KEYS, WAR SOUVENIRS, ARCHAEOLOGICAL PIECES, METALLIC ORE, NUGGETS ETC., ETC. Outdoors or indoors. Extremely sensitive, will signal presence of certain objects buried several feet below ground. No knowledge of radio or electronics required. Can be built with ease in one short evening by anybody from nine years of age upwards, with the wonderfully clear, easy to follow, step-by-step, fully illustrated instructions—it really is as easy as A.B.C. transistorized—no valves. Uses standard PP3 battery. No soldering necessary. Size of detector head 13 1/2" x 10" x 2 1/2". Great demand expected at this

ONLY £2-37



Makes Fantastic Christmas Gift

remarkably low price—ORDER WHILE FREE SENT STOCKS LAST. All parts including detector head case, nuts, screws, wire, simple instructions etc., etc. ONLY £2-37 + 27p p. & p. (Sectional handle as illustrated 75p extra). Parts available separately. Made up looks worth £15

BUILD 5 RADIO AND ELECTRONIC PROJECTS

TOTAL BUILDING PRICE £1-97



Makes exciting Christmas present

phone, knobs, screws, etc. all you need. Presentation Box 37p extra as illus. (if required) (extra parts available separately) No soldering necessary. Send only £1-97 + 23p p. & p.

Amazing Radio Construction set! Become a radio expert for £1-97 A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated Step-by-step plans, all Transistors, loudspeaker, personal

EXAMINE AT HOME FOR 7 DAYS. YOUR MONEY REFUNDED IN FULL IF NOT 100% DELIGHTED.

CONCORD ELECTRONICS LTD (Dept. EE13)

8 Westbourne Grove, London W.2. (Nr. Bayswater & Queensway Tubes. 1 minute ABC Cinema) Callers welcome 9 a.m.-6 p.m. inc. Saturday

ONLY FIND BURIED TREASURE WITH THIS £4-95 READY BUILT & TESTED

Treasure Locator Module



Makes an exceptional Christmas present

BRAND NEW FULLY TRANSLISTORISED PRINTED CIRCUIT METAL DETECTOR MODULE. Ready built and tested—just plug in a PP3 battery and it's working. Put it in a case, screw a handle on and YOU HAVE A PORTABLE TREASURE LOCATOR EASILY WORTH ABOUT £20! Extremely sensitive—penetrates through earth, sand, rock, wood dirt, water, etc.—EASILY LOCATES COINS, GOLD, SILVER, WATCHES, JEWELLERY, NUGGETS, METALLIC ORE, HISTORICAL RELICS, BURIED PIPES, KEYS, NAIL-IN-TREES, ETC., ETC. Signals exact location by "beep" pitch increasing as you near buried metallic objects. PRINTED CIRCUIT SEARCH COIL so stable and sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIN! You could even pay for your holidays with two or three days electronic beachcombing—it's almost like having a licence to print money! Unclaimed treasure now exceeds the combined wealth of all nations. ORDER NOW WHILE PRESENT STOCKS LAST—TREMENDOUS DEMAND EXPECTED AT THIS REMARKABLY LOW PRICE. DEMONSTRATIONS DAILY. ORDERS DESPATCHED IN STRICT ROTATION. SEND NOW £4-95 + 30p carr. etc. (High quality Danish Stethoscope headphones £2-75 extra if required).

SHORTWAVE TRANSISTOR RADIO

ONLY £2-25

Can be built in one evening



Ideal Xmas Gift

At last! After trying countless circuits searching for easy build, work first-time short waver. Giving advanced world-wide performance, we chose this 'Sky Roma'. Anyone from 9 years up can follow the step-by-step, easy-as-ABC, fully illustrated instructions. (We built ten prototypes and everyone worked first time) no soldering necessary. 76 stations logged on rod aerial in 30 mins.—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Use PP3 battery. Transistorised (no valves). Size only 3" x 4 1/2" x 1 1/2". A tremendous demand anticipated price held to only £2-25 + 17p p. & p. for all parts incl. Cabinet, screws, instructions etc. (Parts available separately).

SOOTHE YOUR NERVES, RELAX WITH THIS AMAZING RELAXATRON

CUTS OUT NOISE POLLUTION—SOOTHS YOUR NERVES! Don't underestimate the uses of this fantastic new design—the RELAXATRON is basically a pink noise generator based on avalanche operated transistors. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. For instance, many people find a rainstorm mysteriously relaxing, a large part of this feeling of well-being can be directly traced to the sound of falling raindrops—a well known type of pink noise. A group of Dentists have experimented on patients with this pink noise—NO ANESTHETICS WERE USED! The noise ostensibly created a most definite reaction on these patients, nervous systems with the results that their pain systems were blocked. IF YOU WORK IN NOISE OR DISTRACTING SURROUNDINGS, IF YOU HAVE TROUBLE CONCENTRATING, IF YOU FEEL TENSED, UNABLE TO RELAX—then build this fantastic Relaxatron. Once used you will never want to do without it—use this amazing pink noise generator whenever you feel uneasy, can't relax or wish to concentrate. TAKE IT ANYWHERE, pocket sized. Uses standard PP3 batteries (current used so small that battery life is almost shelf-life) CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones, Components, Nuts, Screws, Wire, etc. etc. no soldering. Send only £2-25 + 25p p. & p. (parts available separately.)

Ideal Christmas Gift


only £2-25



GET A GOOD NIGHT'S SLEEP—EVERY NIGHT! INGENIOUS ELECTRONIC SLEEP INDUCER

Ideal Xmas Gift

only £2-75

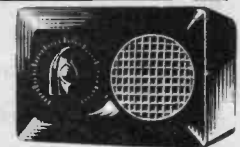

CAN'T SLEEP AT NIGHTS? DO YOU WAKE UP IN THE NIGHT AND CAN'T GET OFF TO SLEEP AGAIN? WOULD YOU LIKE TO BE GENTLY SOOTHED OFF TO SATISFYING SLEEP EVERY NIGHT? Then build this ingenious electronic sleep inducer. It even stops by itself so you don't have to worry about it being on all night. The loudspeaker produces soothing audio-frequency sounds, continuously repeated—but as time goes on the sound—gradually become less and less—until they eventually cease altogether, the effect it has on people is amazingly very similar to hypnosis. A control is provided for adjusting the length of times etc., all transistor, can be built by anyone over 12 years of age in about two hours. No knowledge of electronics or radio needed. Extremely simple, easy-to-follow, step-by-step, fully illustrated instructions included. No soldering necessary. Works off standard batteries—extremely economical. Size only 3" x 4 1/2" x 1 1/2"—take it anywhere. All parts including case, loudspeaker, components, nuts, wire, screws, etc. etc. THERE WILL BE A GREAT DEMAND FOR THIS UNIQUE NEW DESIGN—SEND NOW £2-75 + 25p p. & p. (parts available separately).

REAL WORKING ELECTRONIC ORGAN



ONLY £2-75

Makes a thrilling Christmas present

Don't confuse with ordinary electric organs that simply blow air over mouth-organ type reeds etc. Eight months were spent in creating and testing this superb, revolutionary electronic organ. Fully transistorized—no valves. Proper self-contained loudspeaker. Fifteen separate keys span two full octaves—play the 'Yellow Rose of Texas', play 'Silent Night', play 'Auld Lang Syne', play lots and lots of similar tunes on this real working electronic organ. Although it's no theatre organ it's certainly no tiny thing, it measures 13 1/2" x 10 x 2 1/2". You have the thrill and excitement of building it together with the pleasure of playing a real, live, throbbing electronic organ. Take it anywhere—play it anywhere. NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED—NONE WHATSOEVER. No soldering necessary. It really is as simple as a.b.c. to make. Anyone from nine years upwards can build it easily in one short evening following the fully illustrated, step-by-step, simply worded instructions. BIG DEMAND ANTICIPATED FOR THIS UNIQUE INSTRUMENT at our low, low building price, ONLY £2-75 + 23p p. & p. for all parts, including case, loudspeaker, transistors, condensers, resistors, knobs, transformer, volume control, wire, nuts, screws, simple (but full) instructions, etc., etc. Uses standard battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting Christmas gift for someone.

ANTEX

the soldering appliance specialists



CN.240/2 Miniature soldering iron 15 watt 240 volts, fitted with nickel plated 3/32" bit and packed in transparent display box. Also available for 220 volts. Price **£1.70**

CN.240 Miniature soldering iron 15 watt 240 volts, fitted with iron coated 3/32" bit. Up to 18 interchangeable spare bits obtainable. This iron can also be supplied for 220, 110, 50 or 24 volts. Price **£1.70** (Supplied in standard pack)

G.240 Miniature soldering iron 18 watt 240 volts extensively used by H.M. Forces. Suitable for high speed soldering and fitted with iron coated 3/32" bit. Also available for 220 volts. Spare bits 1/8", 3/16" and 1/4" are obtainable. Price **£1.83** (Supplied in standard pack)



CCN.240 New model 15 watt 240 volts miniature soldering iron with ceramic shaft to ensure perfect insulation (4,000 v A.C.). Will solder live transistors in perfect safety, fitted with 3/32" iron coated bit. Spare bits 1/8", 3/16" and 1/4" available. Can also be supplied for 220 volts. Price **£1.80**

CCN.240/7 The same soldering iron fitted with our new 7-star high efficiency bit for very high speed soldering. The bits are iron coated, nickel and chromium plated. Price **£1.95**



E.240 20 watt 240 volts soldering iron fitted with 1/4" iron coated bit. Spare bits 3/32", 1/8" and 3/16" available. Can also be supplied for 220 and 110 volts. Price **£1.80**.

ES.240 25 watt 240 volts soldering iron fitted with 1/8" iron coated bit and packed in a transparent display box. Spare bits 3/32", 3/16" and 1/4" available. Can also be supplied for 220 and 110 volts. Price **£1.83**



SK. 1 SOLDERING KIT

The kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, heat sink, cleaning pad, stand and booklet "How to Solder." Also available for 220 volts.

Price **£2.75**



SK. 2 SOLDERING KIT

This kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, Heat Sink, 1 amp fuse and booklet "How to Solder"

Price **£2.40**.



MES. 12

A battery operated 12 volts 25 watt soldering iron complete with 15' lead, two crocodile clips for connection to car battery and a booklet "How to Solder" packed in a strong plastic wallet.

Price **£1.95**



from electrical and radio shops or from
Antex Ltd. FREEPOST, (no stamp
required) **Plymouth, PL1 1BR.**
Telephone 0752 67377/8

Please send the Antex
colour catalogue.

I enclose cheque/P.O./Cash
(Giro No. 2581000)

Please send the following:

Name _____

Address _____

EE.2

SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.
 • LOW COST • QUICK DELIVERY • OVER 200 RANGES IN STOCK • OTHER RANGES TO ORDER

NEW "SEW" DESIGNS!

CLEAR PLASTIC METERS

TYPES W.100
100 x 80 mm.

50μA	£3-80	20V. D.C.	£3-10
50-0-50μA	£3-45	50V. D.C.	£3-10
100μA	£3-20	300V. A.C.	£2-30
100-0-100μA	£3-45	1 amp. D.C.	£2-10
500μA	£3-35	5 amp. D.C.	£2-10
1mA	£3-10	300V. A.C.	£2-10
		VU Meter	£3-75


BAKELITE PANEL METERS

TYPE S-80
80 mm. square fronts

50μA	£3-20	50V. D.C.	£2-80
50-0-50μA	£3-10	300V. D.C.	£2-80
100μA	£2-75	1000-100μA	£3-10
100-0-100μA	£3-10	5 amp. D.C.	£2-80
500μA	£2-80	1mA	£2-80
1mA	£2-30	20V. D.C.	£2-80
		VU Meter	£3-87


"SEW" CLEAR PLASTIC METERS

Type MR.85P. 4 1/2 in. x 4 1/2 in. fronts.



50μA	£3-80	10V. D.C.	£2-80
50-0-50μA	£3-10	50V. D.C.	£2-80
100μA	£3-30	300V. D.C.	£2-80
100-0-100μA	£3-30	15V. A.C.	£2-80
200μA	£3-00	8 Meter 1mA	£2-87
500μA	£2-90	VU Meter	£3-60
500-0-500μA	£2-80	1 amp. A.C.*	£2-80
1mA	£2-80	5 amp. A.C.*	£2-80
1-0-1mA	£2-80	10 amp. A.C.*	£2-80
5mA	£2-80	20 amp. A.C.*	£2-80
10mA	£2-80	30 amp. A.C.*	£2-80

Type MR.38P. 1 21/32 in. square fronts.



50μA	£2-10	5 amp. A.C.*	£2-80
50-0-50μA	£1-80	10 amp. A.C.*	£2-80
100μA	£1-80	20 amp. A.C.*	£2-80
100-0-100μA	£1-75	30 amp. A.C.*	£2-80
200μA	£1-85	50V. D.C.	£2-80
500μA	£1-80	300V. D.C.	£2-80
500-0-500μA	£1-80	15V. A.C.	£2-80
1mA	£1-80	50V. A.C.	£2-80
1-0-1mA	£1-80	100V. A.C.	£2-80
2mA	£1-80	5 Meter 1mA	£2-70
5mA	£1-80	VU Meter	£2-10
10mA	£1-80		
20mA	£1-80		
50mA	£1-80		
100mA	£1-80		
150mA	£1-80		

Type MR.52P. 2 1/2 in. square fronts.

50μA	£2-30	10V. D.C.	£2-00
50-0-50μA	£2-80	50V. D.C.	£2-00
100μA	£2-00	300V. D.C.	£2-00
100-0-100μA	£2-00	15V. A.C.	£2-10
500μA	£2-00	500V. A.C.	£2-10
1mA	£2-00	8 Meter 1mA	£2-10
5mA	£2-00	VU Meter	£3-20
10mA	£2-00	1 amp. A.C.*	£2-00
100mA	£2-00	5 amp. A.C.*	£2-00
1 amp.	£2-00	10 amp. A.C.*	£2-00
5 amp.	£2-00	20 amp. A.C.*	£2-00

Type MR.65P. 3 1/2 in. x 3 1/2 in. fronts.

50μA	£3-37	10V. D.C.	£2-80
50-0-50μA	£2-75	50V. D.C.	£2-80
100μA	£2-75	300V. D.C.	£2-80
100-0-100μA	£2-65	15V. A.C.	£2-30
200μA	£2-65	500V. A.C.	£2-30
500μA	£2-40	8 Meter 1mA	£2-37
500-0-500μA	£2-20	VU Meter	£3-37
1mA	£2-20	1 amp. A.C.*	£2-20
5mA	£2-20	5 amp. A.C.*	£2-20
10mA	£2-20	10 amp. A.C.*	£2-20
50mA	£2-20	20 amp. A.C.*	£2-20
100mA	£2-20	30 amp. A.C.*	£2-20

***MOVING IRON—**
ALLOTHERS MOVING COIL
 Please add postage

SEW EDUCATIONAL METERS



Type ED.107. Size overall 100mm x 90mm x 108mm. A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 2" mirror scale. The easily accessible to working. Available in the following ranges:

50μA	£5-00	20V d.c.	£4-40
100μA	£4-65	50V d.c.	£4-40
1mA	£4-40	300V d.c.	£4-40
50-0-50μA	£4-65		
1-0-1mA	£4-40	Dual range	
1A d.c.	£4-40	500mA/5A d.c.	£4-65
5A d.c.	£4-40	5V/50V d.c.	£4-65
10V d.c.	£4-40		

EDGWISE METERS

Type PE.70. 3 1/8 in. x 1 1/2 in. x 2 1/2 in. deep.

50μA	£3-10	500μA	£2-75
50-0-50μA	£3-00	1mA	£2-45
100μA	£2-80	300V. A.C.	£2-45
100-0-100μA	£2-80	VU Meter	£3-40
200μA	£2-90		

Send for Illustrated brochure on SEW Panel Meters—discounts for quantities.

MULTIMETERS for EVERY purpose!

MODEL TE-300. 30,000 O.P.V. Mirror scale, overload protection 0.5/3/15/60/300/1,200V. D.C. 0.6/3/12/60/600/1,200V. A.C. 0.3/0.5/1mA/6mA/60mA/300mA/600mA. 0.8K/80K/800K/8 meg. ohm -20 to +63 db. £5 97s. P. & P. 15p.



MODEL PL436 20KΩ/Volt D.C. 8kΩ/Volt A.C. Mirror scale. -6/3/12/30/120/600V D.C. 3/30/120/600V A.C. 50/500μA/50/1 Meg. 10/100K/1 Meg. 0. P. & P. 12p.

MODEL 5025 57 Ranges, Giant 5 1/2 in. Meter, Polarity Reverse Switch. Sensitivity: 50K/Volt D.C. 5K/Volt A.C. D.C. Volts: 12.5, 25, 125, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.C. Volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.C. Current: 25, 50mA, 2.5, 5, 25, 50, 250, 500mA, 5, 10 amp. Resistance: 2K, 10K, 100K 1MEG, 10 MEG. Decibels: -20 to +85 db. £12-50. P. & P. 17p.

TMK MODEL TW-20CB FEATURES RESETTABLE OVERLOAD BUTTON. Sensitivity: 20KΩ/Volt D.C. 5KΩ/Volt A.C. D.C. Volts: 0-0.5, 2.5, 10, 50, 250, 250, 1,000V. D.C. Currents: 0-0.05, 0.5, 5, 50, 500mA, 10 amp. Resistance: 0-5K, 50K, 0-500K. 5 MEG. Decibels: -20 to +52db. £11-50. P. & P. 17p.

ROUND SCALE TYPE PENCIL TESTER MODEL TS 68 Completely portable, simple to use pocket sized tester. Ranges 0.3/30/300V AC and DC at 2,000 ohm. p.v. Resistance 0-20K ohms. Only £1-97 P. & P. 13p.

TMK MODEL 117 F.E.T. ELECTRONIC VOLT METER Battery operated, 11 meg input, 26 ranges. Large 4 1/2" mirror scale. Size 5 1/2" x 4 1/2" x 2 1/2". DC VOLTS 0.2-1,000V. AC VOLTS 3-300V RMS. 8-800V P-P. DC CURRENT 12-12MA. Resistance up to 2000M ohm. Decibels -20 to +51 db. Complete with leads/instructions. £17-50. P. & P. 20p.

TE-40 HIGH SENSITIVITY A.C. VOLTMETER 10 meg. input 10 ranges: 0.1/0.03-1/3/13/10/30/100/300V. R.M.S. deca-1/2 ModB. Decibels -40 to +50dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. £17-50. Carr. 25p.

TE22 SINE SQUARE WAVE AUDIO GENERATOR Since 20cps to 200 kc/s on 4 bands. Square: 20cps to 30 kc/s. Output impedance 5,000 ohms, 200/250V. A.C. operation. Supplied brand new and guaranteed with instruction manual and leads. £17-50. Carr. 37p.

TE-20RF SIGNAL GENERATOR Accurate wide range signal generator covering 120 kc/s-260 Mc/s on 6 bands. Directly calibrated, variable R.F. attenuator. Operation 200/240V A.C. Brand new with instruction manual. £18. P. & P. 37p. B.A.E. for details.

TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-11.1 meg Ω. G. Ranges ± 1% L. 1 μ H - 111 μ H. HENRY'S 6 Ranges 2 = % C. 10pF ± 110mF. 6 Ranges ± 2%. TURNS RATIO 1:1/1000-1:11100. 6 Ranges ± 1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/4 x 5 x 2 1/2 in. £20. P. & P. 25p

MODEL LT.101 1000 O.P.V. 0.1/0.5/250/1000 V. D.C. 0.1/0.5/250/1000 V. A.C. 0.1/100 M.A. 0.1/50 K ohms. £1-97. P. & P. 15p.

TMK MODEL MD.120 Mirror scale. 20K/Volt D.C. 10KΩ Volt A.C. 50/500/300/600/3,000 V. D.C. 0.6/120/1,200 V. A.C. Current 0-60μA/0 -12/0 300mA. 0-60K/0-6 MegΩ. -20 to +63 db. £4-82s. P. & P. 15p

MODEL 500 30,000 O.P.V with overload protection mirror scale 0.5/2.5/10/25 100/250/500/1,000V. D.C. 0.2/5/10/25/100/250/500/1,000V. A.C. 0.5/0.5/0.5/5/50/500mA. 12 amp. D.C. 0.60/K/6 Meg. 100 Meg Ω. £8-71. Post paid.

TMK LAB TESTER. 100,000 O.P.V. 6 1/2 in. Scale Buzzer Short Circuit Check. Sensitivity: 100,000 O.P.V. D.C. 5K Ω/Volt A.C. D.C. Volts: 2.5, 10, 50, 250, 1,000 V. A.C. Volts: 3, 10, 50, 50, 250, 500, 1,000V. D.C. Current: 10, 100μA, 10, 100, 500mA, 2.5, 10 amp. Resistance: 1K, 10K, 100K, 10MEG, 100 MEGΩ. Decibels: -10 to +49 db. Plastic Case with Carrying Handle. Size 7 1/2 in. x 6 1/2 in. x 3 1/2 in. £18-90. P. & P. 25p.

RUSSIAN 22 RANGE MULTIMETER Model U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2-5/10/50/250/500/1000V. D.C. 2-5/10/50/250/500/1000V. AC DC Current 100 mA/1/10/100mA/A. Resistance 300 ohms/3/30/300K/3M Ω. Complete with batteries, test leads, instructions and carrying case. 10. OUR PRICE £25-87 P. & P. 25p.

TO-2 PORTABLE OSCILLOSCOPE A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2CPS-1 MHz. Input Imp. 2 meg Ω 25 P.P. Illuminated scale. 2in. tube. 115 x 180 x 230mm. Weight 8lb. 220/240 V a.c. Supplied brand new with hand-book. £22-50. Carr. 50p.

FTC-401 TRANSISTOR TESTER Full capabilities for measuring A, B and ICO. NPN or PNP. Easily adaptable for checking diodes. Supplied complete with instructions, battery and leads. £26-87. P. & P. 15p.

HONEYWELL DIGITAL VOLTMETER VT.100 Can be panel or bench mounted. Basic meter measures 100 μV to 100V. D.C. but can be used to measure a wide range of AC and DC volt, current and ohms with optional plug in cards. Specification: Accuracy: ± 0.2% ± 1 digit. Resolution: 1mV. Number of digits: 9 plus fourth overrange digit. Overrange: 100% (up to 1999). Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100V. D.C. Input: Fully floating (2 poles). Input Power: 110-230V. A.C. 50/60 cps. Overall size: 5 1/2 in. x 2 1/2 in. x 8 3/16 in. AVAILABLE BRAND NEW AND FULLY GUARANTEED AT APPROX. HALF PRICE. £49-87s. Carr. 50p.

G. W. SMITH & CO (RADIO) LTD. Also see next two pages

HI-FI EQUIPMENT

SAVE UP TO
33 1/3% OR MORE
SEND S.A.E. FOR
DISCOUNT PRICE LISTS
AND PACKAGE OFFERS!



RECORD DECKS

- B.S.R.**
- Mini Monof £4-97
 - CI294 £8-70
 - M80 £10-75
 - 610 £14-85
 - 510 £11-85
 - 310 £9-65
 - 810 £24-47
 - MP60 T.P.D.1 £17-45
 - MP60 T.P.D.2 £15-85
 - 610 T.P.D.1 £20-97
 - 610 T.P.D.I. £18-75
 - 210 Package* £9-85
 - H.T.70 £15-55
 - H.T.70 Package £20-25
- THEORENS**
- TD125 £59-65
 - TD125AB £34-25
 - TX25 £6-70
 - TD150AII £24-50
 - TD150AIII £40-25
- * Mono + Stereo Cartridge
All other models less Cartridge
Carriage 50p extra any model.



- TX11** £3-77
- GARRARD**
- 2025 T/C* £8-50
 - 3500* £9-75
 - SP25 III £10-50
 - SL55B £13-45
 - AP74 £18-90
 - SL72B £23-95
 - SL75B £26-50
 - SL95B £32-95
 - 401 £27-45
 - ZERO 100A £34-97
 - ZERO 100B £41-97
- GOLDRING**
- GL69/2 £19-50
 - GL69/P3 £26-95
 - GL75 £29-97
 - GL73P £38-50
 - LD99/75 £37-75
 - G99 £19-95
- PIONEER**
- PL12AQ £36-50

RECORD DECK PACKAGES

- Decks supplied ready wired in plinth and cover fitted with cartridge.
- Garrard 2025 T/C with Sonotone 9TAHCD £13-95
 - Garrard SP25 Sonotone 9TAHCD £15-95
 - Garrard SP25II Goldring G800... £18-95
 - Garrard AP76 Goldring G800... £23-95
 - B.S.R. MP60 Audio Technica AT 35... £21-00
 - Goldring GL69/2 Goldring G800... £37-50
 - Goldring GL75 Goldring G800... £42-50
 - Goldring GL75 Goldring G800... £48-65
- Carriage 50p extra any model.



SPECIAL PURCHASE

Brand new 18" 100 watt speakers. Made by Celestion or Fane. 18" 100 watt rms. 35 cps bass resonance. Limited stock only.

Each Carr. 50p

£13.95




SINCLAIR EQUIPMENT

- Project 60. Package offers.
- 2 x Z30 amplifier, stereo 60 pre-amp, PZ5 power supply, £16.75 Carr. 37p.
 - Or with PZ6 power supply £18.95 Carr. 37p.
 - 2 x Z50 amplifier, stereo 60 pre-amp, PZ8 power supply, £20.25 Carr. 37p.
 - Transformer for PZ8, £2.97 extra.
 - Add to any of the above £4-87 for active filter unit and £13-90 for pair of Q16 speakers.
 - Project 60 FM Tuner £20.25 Carr. 37p.
 - All other Sinclair products in stock.
 - 2000 Amp £23.75 Carr. 37p.; 3000 Amp £31.50 Carr. 37p.; Neoteric Amp £49.95 Carr. 37p.
 - IC10/IC12 £2-50
 - NEW PROJECT 605 — £20.97 Carr. 37p.



LATEST CATALOGUE

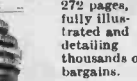
Our new 6th edition gives full details of a comprehensive range of HI-FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 50p 272 pages, fully illustrated and detailing thousands of bargains.



SEND NOW

ONLY **37 1/2 p**
P & P 10p

TELETON SAQ-206 STEREO AMPLIFIER

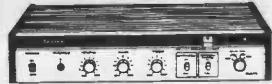

Latest exciting release. Brand new model. 6 + 6 watts rms. Inputs for mag, xtal, aux tape. Volume, bass, treble, sliding balance, scratch filter and loudness controls. List £32.50 OUR PRICE £18-50 Carr. 37p.



TELETON F.2000 AM/FM STEREO TUNER AMPLIFIER

Probably the most popular budget tuner/amp. and now offered at a ridiculous low price. 5 watts r.m.s. per channel. Tape/Cer phono inputs. AFC/Built-in MPX. List £51. OUR PRICE £28-75. Carr. 50p.


SUGGESTED SYSTEM

F.2000, Garrard 2025/T/C Changer fitted stereo cartridge, with plinth and cover and pair of G.W.S.'s 3 way Speakers. Total Rec. Price £97-73. OUR PRICE £54-65. Carr. £1.



TRANSISTORISED FM TUNER

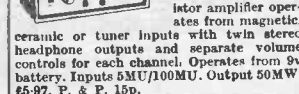6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6 x 4 1/2 in. 3 T.P. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. £9-37. P. & P. 12p. Stereo multiplex adaptors £4-97.



HA-10 STEREO HEADPHONE AMPLIFIER

All silicon transistors amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9v battery. Inputs 5MU/100MU. Output 50MW. £5-97. P. & P. 15p.

NS-1600W STEREO AMPLIFIER

Exceptional budget price amplifier. All silicon transistor. Handsome Walnut input selector.



separate balance, volume, treble, bass controls. Output 2 x 6W RMS. Inputs Mag. Tape. Xtal. Tuner, Tape Out. £14-75. Carr. 37p.

EA-1 REVERBERATION AMPLIFIER


Self contained, transistorised, battery operated. Simply plug in microphone, guitar, etc. and output into your amplifier. Volume control, depth of reverberation control. Beautiful walnut cabinet. 7 1/2 x 3 1/2 in. £5-97. P. & P. 15p.

BH.001 HEAD-SET AND BOOM MICROPHONE

Moving coil. Ideal for language teaching, communications. Headphone imp. 16 ohms. Microphone imp. 200 ohms. £4-62. P. & P. 15p.

HOSIDEN DH-085 DE-LUXE STEREO HEADPHONES

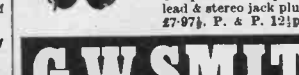Features unique mechanical 2 way units and fitted adjustable level controls. 8 ohm impedance. 20-20,000cps. Complete with spring lead & stereo jack plug £7-97. P. & P. 12p.



TO-3 PORTABLE OSCILLOSCOPE


3in. tube. Y amp. Sensitivity 0.1v p-p/CM. Bandwidth 1.5 cps-1.5 MHz. Input imp. 2 meg Ω 25vF X amp. sensitivity 0.9v. p-p/CM. Bandwidth 1.5 cps-800KHz. Input imp. 2 meg Ω 20pF. Time base. 5 ranges 10 cps-200 KHz. Synchronisation. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 15 1/2 lb. 220/240V. A.C. Supplied brand new with handbook. £37-50. Carr. 50p

RUSSIAN C1-16 DOUBLE BEAM OSCILLOSCOPES

5 MHz Pass Band. Separate Y1, Y2 amplifiers. Calibrated triggered sweep from .2 sec to 100 milli sec/cm. Supplied complete with all accessories and instructions £87. Carr. paid.

BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

Sine 18-200,000 Hz: Square 18-50,000 Hz

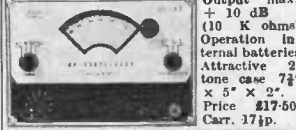

Output max. +10 dB (10 K ohms) Operation internal batteries Attractive 2-tone case 7 1/2 x 5 1/2 x 2 1/2 in. Price £17-50. Carr. 17p.


TE-16A Transistorised Signal Generator

400KHz-30MHz. An inexpensive instrument for the handyman. Operates on 9v battery. Wide easy to read scale. 800KHz modulation. 5 1/2 x 5 1/2 x 3 1/2 in. Complete with instructions and leads. £7-97. P. & P. 20p.




TEIS TRANSISTORISED GRID DIP METERS

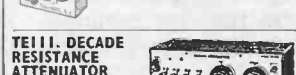Six ranges. 440 Kc/s-280 Mc/s. Operates on 9v. battery. Full instructions. £12-50. P. & P. 17p.




TEII. DECADE RESISTANCE ATTENUATOR

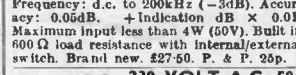Variable range 0-111dB. Connections, Unbalanced T and Bridge T. Impedance 600 Ω range (0.1B x 10) + (1dB x 10) + 10 + 40 + 30 + 40dB. Frequency: d.c. to 200KHz (-3dB). Accuracy: ±0.05dB. +Indication ±B x 0.01. Maximum input less than 4W (50V). Built in 600 Ω load resistance with internal/external switch. Brand new. £27-50. P. & P. 20p.



230 VOLT A.C. 50 CYCLES RELAYS

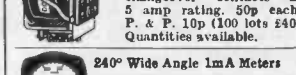Brand new. 3 sets of changeover contacts at 5 amp rating. 50p each. P. & P. 10p (100 lots £40) Quantities available.



240° Wide Angle 1mA Meters


- MW1-6 60mm square £4-97
- MW1-8 60mm square £3-97

P. & P. extra



RP214 REGULATED POWER SUPPLY

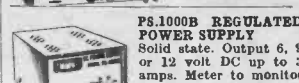Solid state. Variable output 0-24v DC up to 1 amp. Dual scale meter to monitor voltage and current. Input 220/240V A.C. Size 185 x 85 x 105mm. £8-97. P. & P. 25p.



PS.1000B REGULATED POWER SUPPLY

Solid state. Output 6, 9 or 12 volt DC up to 3 amps. Meter to monitor current. Input 220/240V A.C. Size 4" x 3 1/2" x 6 1/2". £11-87. P. & P. 25p.




UNR-30 RECEIVER

4 Bands coverage 550Kc/s-30Mc/s. B.F.O. Built-in Speaker 220/240V. A.C. Brand new with instructions. £15-75. Carr. 37p.



LAFAYETTE HA-600 SOLID STATE RECEIVER

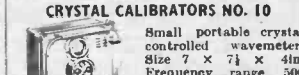General coverage 150-400Kc/s. 550 Kc/s-30Mc/s. FET front end. 2 mech. filters, product detector, variable B.F.O., noise limiter, S. Meter, Bandspread. RF Gain. 15" x 9 1/2" x 8 1/2". 18 lbs. 220/240V. A.C. or 12v. D.C. Brand new with instructions. £45. Carr. 50p.



CRYSTAL CALIBRATORS NO. 10

Small portable crystal controlled wavemeter. Size 7 x 7 1/2 x 4in. Frequency range 500 Kc/s-10 Mc/s (up to 30 Mc/s on harmonics). Calibrated dial. Power requirements 300V. D.C. 15mA and 12V D.C. 0.5A. Excellent condition. £4-47. Carr. 37p.

HELICAL POTENTIOMETERS ITT MCPM15 10 TURN 2 1/2 WATTS

Available 500 ohm, 1K, 5K ohm. £1-25 each. P. & P. 15p.

B.C. 221 FREQUENCY METERS

latest release 125 KHz-20 MHz. Excellent condition. Fully tested and checked and complete with calibrator charts. £27-50 each. Carr. 50p.

SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS

Compact and panel mounting. Ideal for control of lamps, drills, electrical appliances etc. Input 230/240V. A.C. Output continuously variable from 20v-230v. Model MR 2305 5 amp 85 x 46 x 43mm £3-71. Model MR 2310 10 amp 90 x 68 x 60mm £11-97. Postage 12p.

AUTO TRANSFORMERS

- 0/115/230V. Step up or step down. Fully shrouded.
- 150 W. £23-71 P. & P. 17p
 - 300 W. £25-25 P. & P. 22p
 - 500 W. £4-97 P. & P. 32p
 - 1000 W. £7-25 P. & P. 37p
 - 1500 W. £8-97 P. & P. 41p
 - 5000 W. £38-00 P. & P. £1

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush vaper. Continuous rating. Wide range exact. Single hole fixing, jin. dia. shafts. Bulk quantities available.

25 WATT 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms, 72p. P. & P. 7p.

50 WATT 10/25/50/100/250/500/1000/2500 or 5000 ohms, £1-05 P. & P. 7p.

100 WATT 1/5/10/25/50/100/250/500/1000 or 2500 ohms, £1-37 P. & P. 7p.



"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

- Excellent quality - Low price - Immediate delivery
- S-280 General Purpose Bench Mounting
 - 1 Amp £7-00
 - 2.5 Amp £8-05
 - 5 Amp £11-75
 - 10 Amp £15-90
 - 12 Amp £23-60
 - 20 Amp £49-00
- S-280B Panel Mounting
- 1 Amp £7-00
 - 2.5 Amp £8-05
- Please add postage
- ALL MODELS INPUT 230 VOLTS, 50/60 CYCLES, OUTPUT VARIABLE 0-260 VOLTS.**
- Special discounts for quantity



G.W.SMITH & CO. (RADIO) LTD

27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715
3 LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204
34 LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155
311 EDGWARE RD, LONDON, W.2 Tel: 01-262 0387.

DPEN 9-6 MONDAY TO SATURDAY

All Mail Orders to -
11-12, Paddington Green,
London, W.2
Tel: 01-262 6562
(Trade supplied)

everyday electronics

PROJECTS....
THEORY.....

CONTACT MADE

First, we wish to thank all who have written and commented on our new publication. The friendly and congratulatory remarks will encourage all those concerned with the production of *Everyday Electronics* to ensure it fulfills our declared intentions. The various suggestions and advice offered, and yes the critical (yet generally pertinent) comments, will all be given consideration. Some will undoubtedly make their mark on our pages in the course of time.

There is just one little point to emphasise at this stage. There is a limit to what we can fit into any single issue, so have patience please if your particular special requirement has not appeared so far. *Everyday Electronics* is, after all, still very young: although (we admit with some pleasure) the warm and familiar manner already adopted by many of our correspondents tends to belie this fact.

FULL CYCLE

One of our readers remarks that electronics appears to have turned a complete cycle, since we are back again to dry batteries. One could, in fact, look back a stage further and recall that radio or "wireless" reception relied on the solid state crystal. So, strange as it may seem to some, there is in a sense a similarity between the primitive equipment used in those far off days and the highly developed devices employed in the advanced technology of today.

Back once more to batteries; the possibility of operating transistors and other semiconductor

"crystal" devices from low voltage supplies is of course one of the reasons why modern electronics has acquired a wide popular appeal as a constructive pastime.


GROWTH AREA

While thinking figuratively of turning full cycle, the vast growth in coverage and influence that has taken place over the years must not be overlooked.

The current situation is vastly different to those ancestral days when radio was the one and only useful function performed by electronics, outside the physicist's laboratory. Nowadays, the area embraced by electronics is tremendous in extent—practically boundless in fact—and is conveniently divided into a number of fields of specialised activity. It is our intention to explore in time as many of these different fields as possible—bearing in mind, of course, the limits we have set ourselves in terms of technical complexity and material cost.

CHEERS!

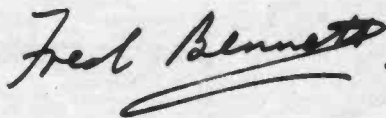Finally, we take this opportunity to wish all our readers—young or old, novice or old hand, including bottle reared types now undergoing conversion to solid state—a Merry Christmas and a happy and constructive 1972.



Our February issue will be published on Friday, January 21

EDITOR F. E. BENNETT • M. KENWARD • B. W. TERRELL B.Sc.
ART EDITOR J. D. POUNTNEY • P. A. LOATES • S. W. R. LLOYD
ADVERTISEMENT MANAGER D. W. B. TILLEARD

© IPC Magazines Limited 1972. Copyright in all drawings, photographs, and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden.

All reasonable precautions are taken by EVERYDAY ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

Subscription Rates including postage for one year, to any part of the world, £2.35.
Everyday Electronics, Fleetway House, Farringdon Street, London, E.C.4. Phone: Editorial 01-634-4452; Advertisements 01-634-4202.

....EASY TO CONSTRUCT
....SIMPLY EXPLAINED



VOL. 1 NO. 3


JANUARY 1972

CONSTRUCTIONAL PROJECTS

TEMPERATURE COMPARATOR For measuring temperature changes in liquids by D. Bollen	134
TRANSISTOR-MICROPHONE Crystal type with "long lead" by T. A. White	140
ASTRON RECEIVER A simple transistor radio in unusual case by M. A. Rambaut	152
ELECTRO LAUGH Have "fun" with this ingenious device by Gerry Brown	158

GENERAL FEATURES

EDITORIAL	132
RUMINATIONS by Sensor	138
SHOP TALK This month's constructionals by Mike Kenward	139
ELECTRONICS AND THE MUSIC SCENE by B. W. Terrell	144
TEACH-IN Part 3: Resistance and colour code by Mike Hughes	148
MEMORY STORE Retrieval by John Watt	161
READERS' LETTERS	162
COMPONENT BUYING AND SUPPLYING Part 3: The Contributor by A. Sproxtton	166

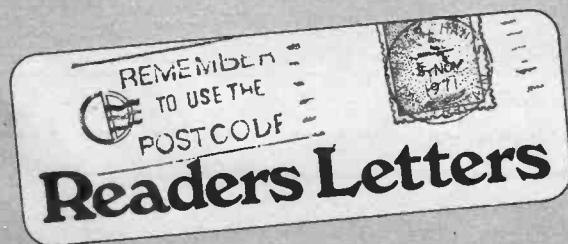

We welcome your views and suggestions concerning Everyday Electronics, and this month we publish a selection of readers' letters. If you write to us for advice please note you must include a s.a.e.

Unfortunately we cannot prepare special designs, circuits or wiring diagrams, nor can we answer technical queries over the telephone, or queries concerning commercial equipment or subjects or designs not discussed in our pages.


Remote Temperature Comparator

By D. BOLLEN

Approximate cost of components

£

4.25 excluding case

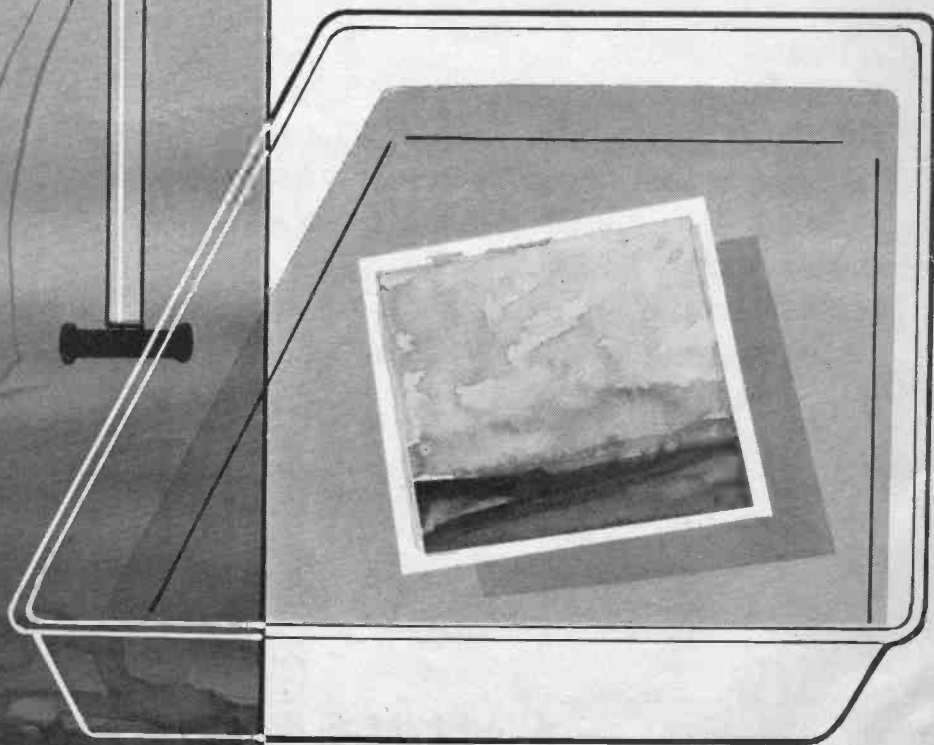

VERY small fluctuations of temperature, such as occur in fish tanks, in photographic solutions, and in thermostatically controlled rooms, are quite difficult to observe with an ordinary thermometer. The concern here is not so much with accuracy as sensitivity.

A highly accurate mercury thermometer covering 0 to 40 degrees Centigrade would be incapable of measuring increments of, say, 0.1 degrees C unless it had a stem several feet long and even then would suffer from an appreciable thermal lag.

The electronic expanded scale thermometer described here was designed to offer a high sensitivity at low cost, and can measure short-term temperature changes as 0.01 degree C. Deviations from any pre-selected temperature

between 0-40 degrees C are displayed on a centre zero meter, with three switched ranges covering 0.1-0.01 degrees C, 1-0.1 degrees C, and 10-0.10 degrees C. The coarse range is useful for quick checks of relatively large temperature differences, in a glasshouse for example.


THERMISTOR SENSOR

In the basic circuit of the thermometer, Fig. 1, a thermistor sensor (RTH1) and a variable resistor VR1 form a voltage divider across the battery supply rails. Over a limited range of temperature, and for differing settings of VR1, the voltage across the thermistor will vary linearly, and inversely with temperature at a rate of approximately 100mV per degree C.

BASIC CIRCUIT

The basic circuit diagram shown in Fig. 1 operates as follows: at a selected temperature VR1 is first adjusted to make the voltage present at the base of TR1 equal to that of TR2, and thus gives zero volts between the collectors of the two transistors. Subsequently, any small change of thermistor temperature will produce a voltage change at the base of TR1, which will be amplified by TR1 and TR2 and displayed by the meter. Circuit amplification is determined by R1, hence this resistor can be selected for the required full scale temperature reading.


Fig. 1. Shows the basic theoretical circuit diagram of the comparator

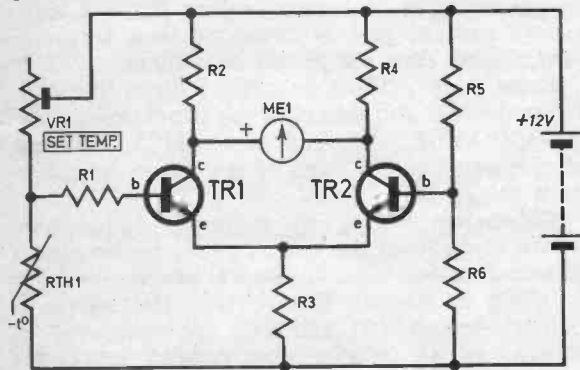


THERMOMETER CIRCUIT

The complete circuit diagram of the thermo-

Fig. 2. The complete circuit diagram of the comparator with plug-in probe.

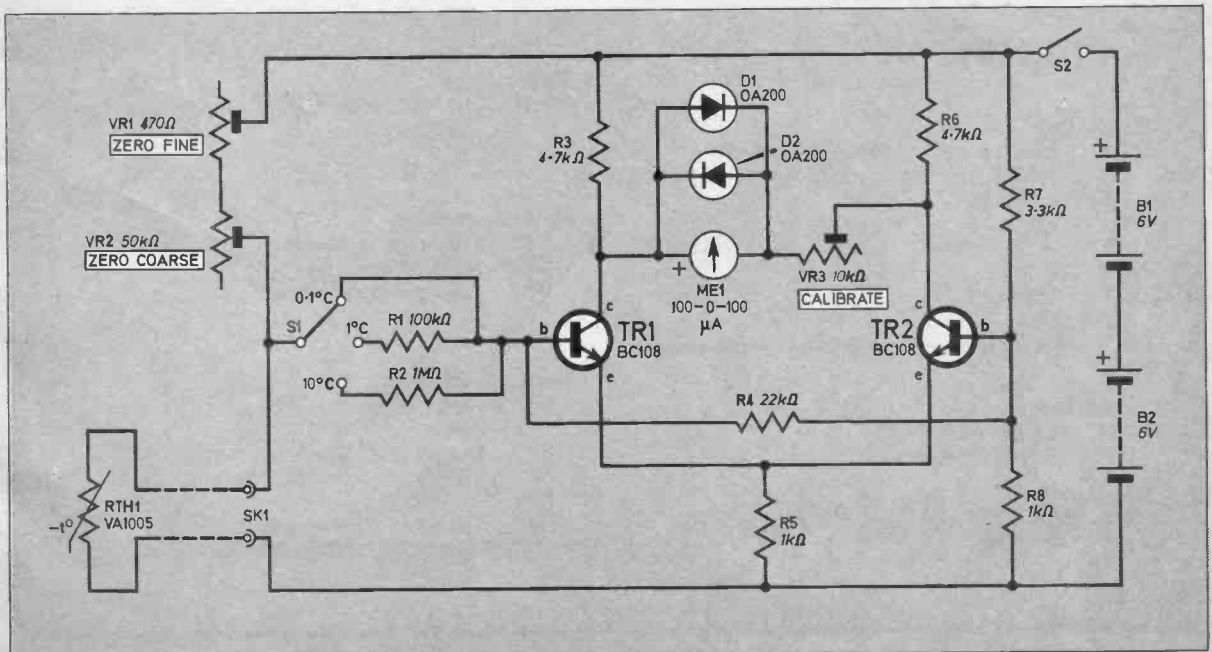

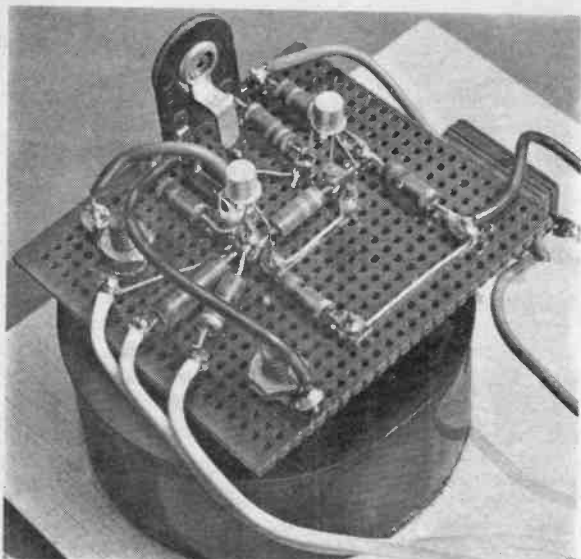

Shows the component board mounted on the back of meter.

meter is shown in Fig. 2. VR1 and VR2 provide fine and coarse adjustment of the initial voltage across thermistor RTH1, and circuit parameters are arranged to yield an input resistance of approximately 10 kilohm at the base of TR1. Hence, switched values of 100 kilohm and 1 Megohm, for R1 and R2 respectively, will offer decadal gain steps. Although this method of range switching is not particularly accurate, it is at least simple and does allow the instrument

to be calibrated on its 10 degree C range against an ordinary thermometer.

Meter ME1 in Fig. 2. is protected against severe overloads when the circuit is unbalanced by the limiting diodes D1 and D2. Variable resistor VR3 in series with the meter is used to calibrate the thermometer.

CONSTRUCTION AND WIRING

To keep construction as simple as possible, the circuit panel used is a piece of plain, 0.1 inch matrix perforated s.r.b.p. (synthetic resin bonded paper), measuring 2.2 x 2.5 inches, with terminal pins, and all components and interconnecting wiring links are on one side only, see Fig. 3.

Cut the panel to size and drill two holes to fit the meter terminals, then insert all terminal pins and solder resistors, VR3, links, and panel leads in position. When the panel has had a few minutes to cool down, solder the two transistors and the pair of diodes to their terminal pins, taking care not to overheat them.

Front panel drilling details are given in Fig. 4. After drilling and lettering the panel, mount S1, S2, VR1, VR2, SK1, and meter ME1. Bolt the circuit panel to the back of the meter complete with solder tags.

Commence wiring by soldering the appropriate leads from the circuit panel to the meter terminal solder tags. A general wiring diagram is given in Fig. 5. Ensure that the wires to potentiometers VR1 and VR2 are connected as shown, so as to give the correct rotational "sense" when zeroing the meter.

Components....

Resistors

R1	100k Ω $\frac{1}{2}$ watt metal oxide $\pm 2\%$
R2	1M Ω $\frac{1}{2}$ watt metal oxide $\pm 2\%$
R3	4.7k Ω
R4	22k Ω
R5	1k Ω
R6	4.7k Ω
R7	3.3k Ω
R8	1k Ω

All $\frac{1}{2}$ watt carbon $\pm 10\%$ unless otherwise stated

Transistors

TR1	BC108 Silicon npn
TR2	BC108 Silicon npn

Diodes

D1	OA200
D2	OA200

Thermistor

RTH1	VA 1005 (or R.S. Components Ltd., TH2A)
------	---

Potentiometers

VR1	470 Ω carbon linear
VR2	50k Ω wirewound
VR3	10k Ω skeleton preset

Miscellaneous

ME1	100-0-100 μ A 1k Ω internal resistance meter
S1	Single pole three-way wafer
S2	Single pole on-off toggle
BY1, BY2	PP1 (2 off, 6V each)
SK1	Two-way socket with plug
	Piece of s.r.b.p. 2.2 x 2.5 inches

Remote Temperature Comparator

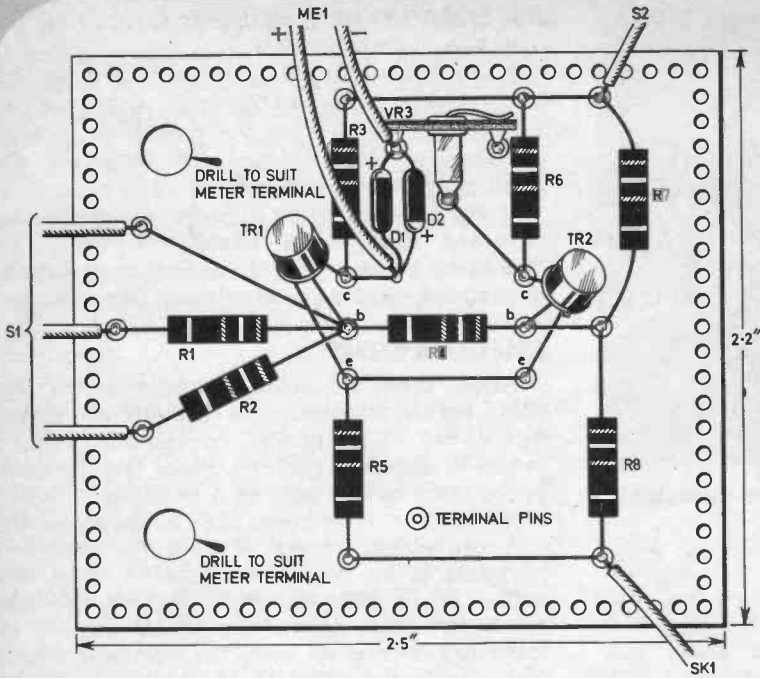


Fig. 3. The wiring and component layout. There are no connections on the underside.

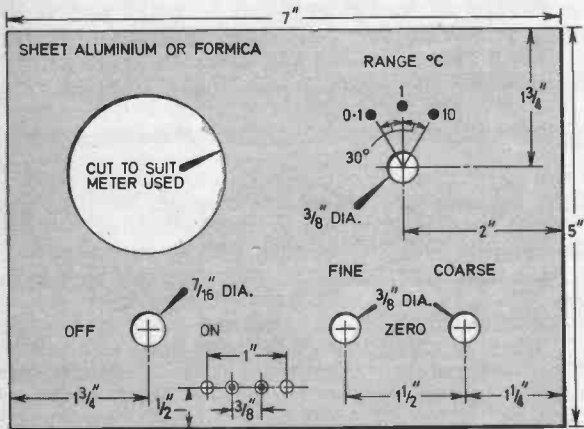


Fig. 4. (left) The dimensions of the front panel which can be made from aluminium sheet or formica.

Fig. 5. (bottom left) The wiring and components on the rear of the front panel. Note the wiring to potentiometers VR1 and VR2.


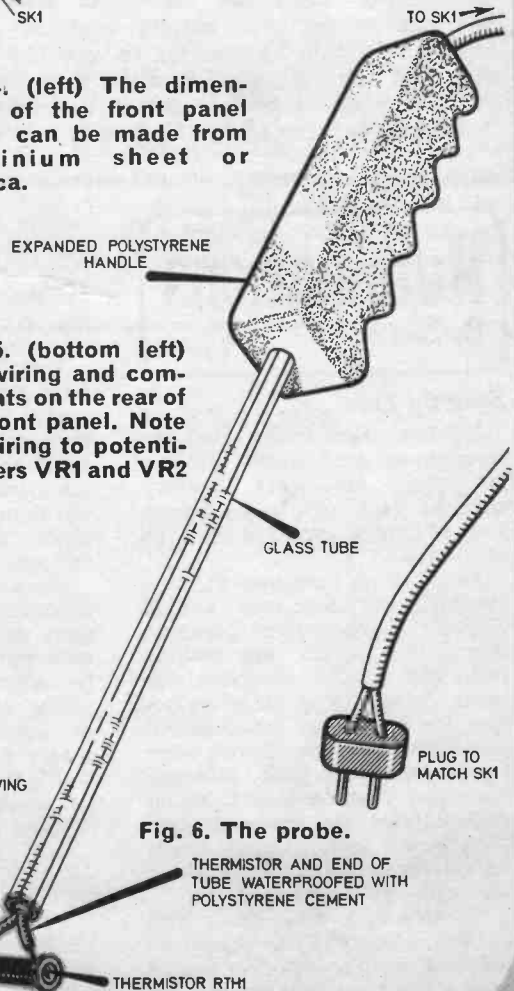
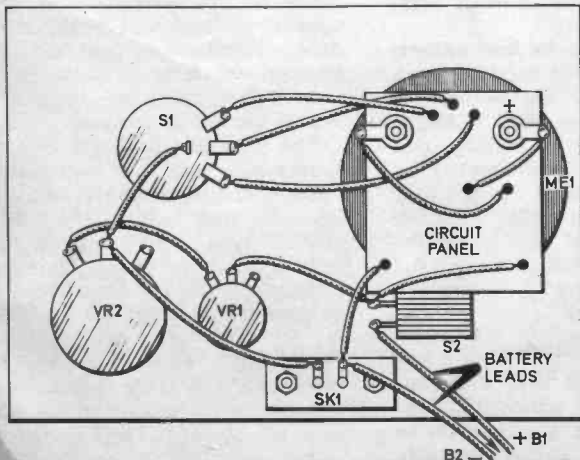


Fig. 6. The probe.

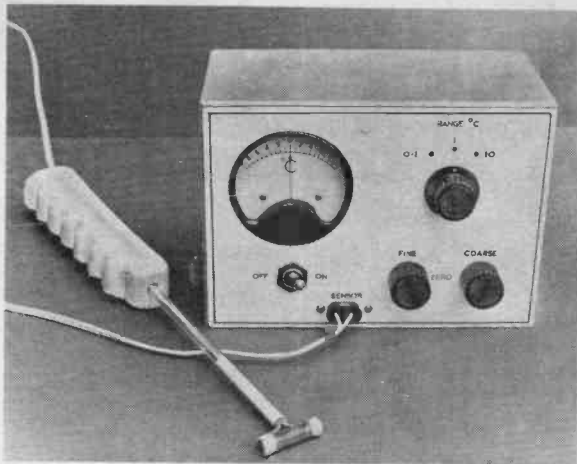

The assembled remote temperature comparator in case complete with probe.

As a preliminary check that the circuit is functioning, insert the thermistor wires into SK1 and connect the battery leads to a 12V supply. It should be possible to zero the meter with VR1 and VR2 at each of the three settings of S1. The meter pointer should rise when the thermistor is warmed by the fingers.

THERMISTOR PROBE

Details of a thermally insulated probe are given in Fig. 6, where the thermistor is mounted at one end of a length of glass tubing which is in turn retained in a hand grip made of expanded polystyrene. Both glass and expanded polystyrene are very poor conductors of heat.

If the probe is to be used for measuring temperature changes in liquids, the thermistor should be given a liberal coating of polystyrene cement to render it completely impervious.

CALIBRATION

Allow time for soldering heat to be dissipated before attempting to calibrate the thermometer. Set VR1 and VR3 to mid-track, and S1 in the 10 degree C position. Place the thermistor probe close to the bulb of a centigrade thermometer on a table and zero ME1 by means of VR2.

A convenient source of heat for calibration purposes is an adjustable reading lamp fitted with a 60 or 100 watt bulb. Position the lamp about two feet above the thermometers and leave it switched on until the standard thermometer indicates a rise of 10 degrees C. Allow a minute or so for readings to settle down, then adjust VR3 for full scale deflection of ME1. If necessary, switch the lamp on again to maintain the 10 degree C rise above ambient. □

Ruminations

By Sensor

Speedy Fido

My homeward route takes me through an area where terraces of small nineteenth century cottages, each with its yard wide strip of garden, crowd to the edge of the road.

As I drove southwards, one evening, the sun was setting behind the cottages and I became aware that a car approaching from the opposite direction was being driven by a large yellow dog. My feelings of astonishment and fear were soon allayed when I saw that the car, although travelling fast, was well under control. The dog sat erect and alert in his seat, swaying gently as the car followed the bends in the road.

Reassured, although still curious, I watched the dog-driven car and as our vehicles passed each other I saw that the car was a left-hand drive model with a

human driver at the wheel. I had not seen him earlier because the right hand side of the road was in shadow, although the dog, sitting up in the right hand seat, was clearly visible.

Well, I thought, "Why shouldn't dogs drive cars?" They can be taught to lead the blind and to herd and pen sheep, perhaps they could be taught to drive! A dog's intelligence is somewhat limited, but then, we have all met human drivers who appear to suffer from the same disability.

Dogs appear to be less aggressive, less competitive, less arrogant and therefore potentially safer drivers than men. It might be argued that a driving dog whose attention is distracted by the scent of a bitch could cause a very dangerous traffic situation—this is true; but men in similar situations are equally dangerous to other road users!

Master and Slave

I read recently that a system has been devised which will prevent the starting of a vehicle to which it is fitted, if the seat belts of the driver and front seat

passenger are not worn correctly. Contacts beneath the front seats and in the buckles of the belts, together with an ultra sonic transmitter and receiver, ensure that the ignition cannot be switched on, when the seats are occupied, until the belts have been fastened correctly. The ultrasonic transmitter is positioned within the belt such that the receiver is only activated when the seat belt is in its correct position. Provision is made for manoeuvring, at slow speeds, without seat belts, and a delay mechanism prevents the ignition switching off immediately should the belts be unbuckled whilst the car is moving.

The idea fills me with dismay. I normally wear my safety belt, I find it comfortable and comforting. My seat belt is the "automatic" type which allows the wearer to move freely and only locks when the car is accelerated or decelerated rapidly.

I wouldn't mind an electronic "watchdog" reminding me to fasten the belt (I do forget sometimes) but I rather resent the role of slave to an inanimate

Please turn to page 165



Transistors

WE have received some enquiries about the coding of 2N2926 transistors. There are three types Green (G), Orange (O), and Yellow (Y) and the prices can vary by relatively large amounts, some suppliers sell all three types at one price while others charge more for Green types. The only difference between them is the gain, the Green are the best, then Orange and lastly Yellow. In applications such as the *Snap Sequence Indicator* (November 1971 issue) any type can be used, in some applications the Green type must be used. If we do not give a specific type buy the cheapest—or Green if they are all the same price. If we quote Orange then Green or Orange will suit but Yellow may not work.

Having said something about component buying in general, let us now get down to specific problems arising from this issue.

Astron

After looking through all the adverts, and all the catalogues that we have been sent we can only find one supplier of the tuning capacitor for the *Astron* and that is Home Radio. The price is rather high and if you find another supplier you may be able to undercut our approximate cost.

Diodes for the *Astron* may also prove difficult, Davian Electronics, P.O. Box 38, Oldham, Lancs., can supply at a very competitive price. One other buying problem could be the loudspeaker, however you do not have to use that

specified, any 35 ohm loudspeaker will do provided it is not bigger than the one given.

Perspex buying may be difficult in some areas, we managed to buy ours from a small sign making firm. They cut the pieces to size and sold us a small bottle of chloroform to glue it all up with. You will just have to hunt around for your nearest supplier or buy the kit from Kaspex, 16 Seymour Road, Tilbury, Essex.

Remote Temperature Comparator

Few buying problems with the *Remote Temperature Comparator*, the glass tube will probably be more difficult to get than any of the components. We get Biro pen refills in glass tubes and these would be good for the job if the closed end were carefully cut off. If you cannot find a source of tube then a chemist may be able to help. As a last resort thin Paxolin tube could be used.


Electro Laugh

Unusual though the *Electro Laugh* is the components are all readily available. Main point to watch on this one is the price of the transistors, because there are a number of them in the circuit any slightly high priced will push up the cost of the project beyond reason. We have given no case details as the unit could be incorporated in other equipment (as an alarm) or encased in any way required.

Transistor-Microphone

The only problem we can foresee with the *Transistor-Microphone* is not concerned with the electronic component buying but with obtaining the Paxolin tube used for the handle. If you cannot find a supplier write to Home Radio. You could also use Paxolin tube for the insert and preamp housing—the 1 $\frac{3}{8}$ inch size should be suitable.

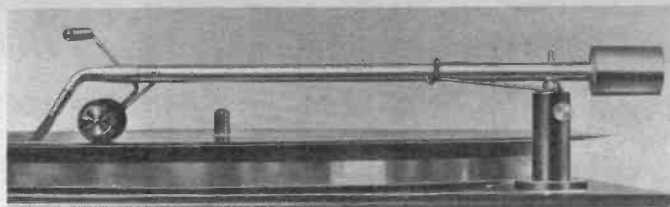It is important to use a miniature horizontal type skeleton pre-




set for the microphone as this fits on the board and is clear for adjustment—vertical types are not easy to adjust due to other components getting in the way.


New Products

Three new products that may interest you have appeared in the office this month, first, a Groove-Kleen from Bib (shown above). This record cleaner is chrome finished, has a pre-set balance weight and a self adhesive stand. Complete with a brush for cleaning the dust roller, the cleaner costs £1.99.

Also from Bib is a 36-page booklet entitled *Hi-Fi Stereo Hints and Tips* by John Borwick, B.Sc. (technical editor of *The Gramophone*). This booklet deals with the installation, care and use of hi-fi equipment and costs 25p, available from audio dealers and newsagents.

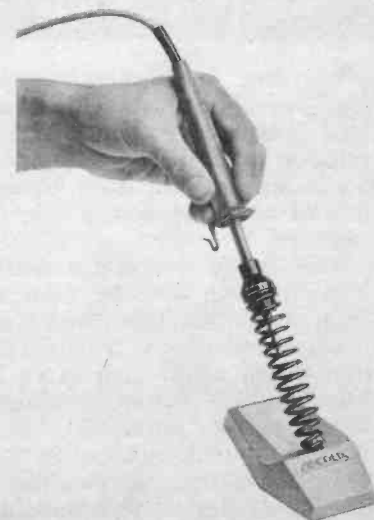Having mentioned an iron stand last month and shown it with an Adcola Products Invader soldering iron we have now been sent information on a stand specially made for the Invader iron. Shown below, the stand has a non-slip rubber base and integral bit wiping sponge. Price for this portable stand that can also be used with other irons is £1.49.



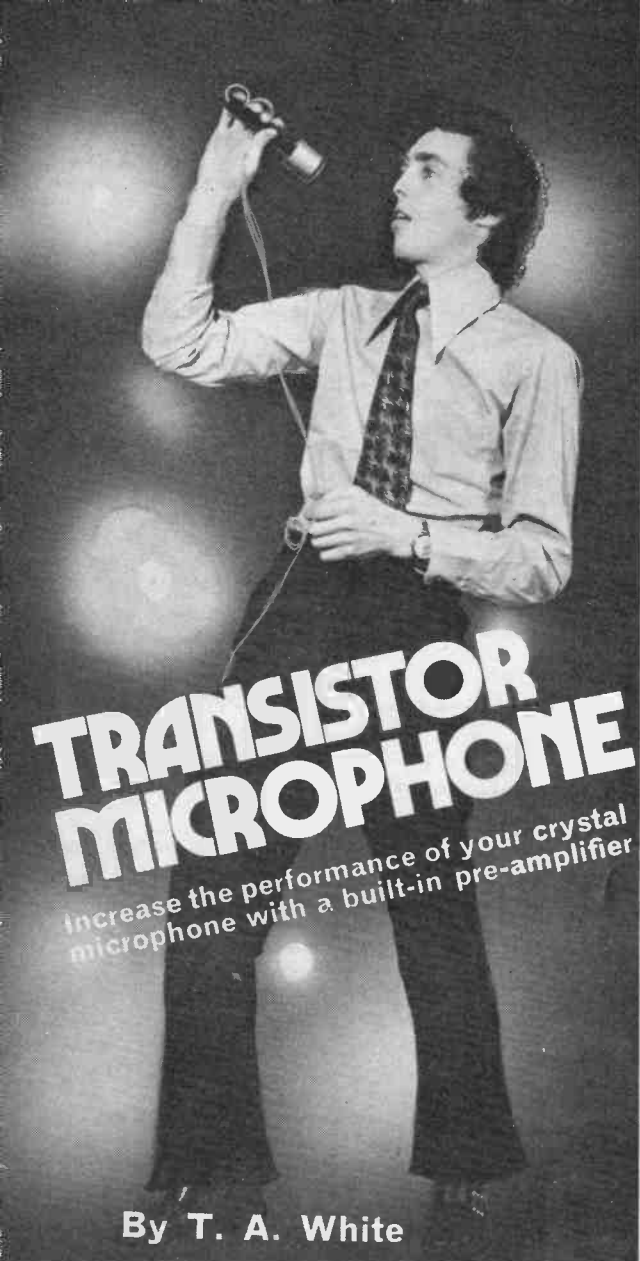

TRANSISTOR MICROPHONE

Increase the performance of your crystal microphone with a built-in pre-amplifier

By T. A. White

CRYSTAL and high impedance dynamic microphones cannot usually be used with long leads unless a transformer of some description is inserted, since hum and noise pick-up is high. A miniature transformer, however, is expensive, especially when high fidelity is required.

This article describes a method whereby such a microphone may be used at long distances from equipment with which it is to be employed. A microphone pre-amplifier is fitted at the microphone end which acts as an impedance transformer (high to low), whilst also providing useful voltage gain.

This circuit is unusual in that the power for the pre-amplifier is obtained from the main equipment and is fed along the same coaxial

lead as used for transmitting the signal from the microphone to the main amplifier.

PRE-AMP SUPPLY

The principle of operation is shown in Fig. 1. First let us consider the d.c. power supply to the pre-amplifier; this is derived from the main amplifier power supply, through the centre conductor to the positive terminal of the pre-amplifier. Resistors R_a and R_b determine the voltage supplied to the pre-amplifier.

Therefore, if the pre-amplifier takes a current I amps, then the voltage reaching the pre-amplifier is given by:—

$$V_{\text{pre-amp}} = V_s - I(R_a + R_b) \quad \dots (1)$$

where V_s is the supply voltage.

The pre-amplifier described here was designed to operate with a 10V supply. The current required is 2mA.

If the voltage tapping on the main amplifier is V_s and we make R_a equal to R_b , equation (1) reduces to:—

$$R_a = R_b = 250(V_s - 10) \text{ ohms}$$

It must be stressed at this point that this particular method of obtaining the power supply from the main amplifier should only be used with low voltage transistor amplifiers with a maximum voltage tapping of 50V.

The prototype was designed for use with a Baily amplifier which has a 20V tapping. Any transistor amplifier with a similar supply may be used.

Therefore, with a 20V supply,

$$R_a = R_b = 2.5 \text{ kilohm}$$

Since the supply to the pre-amplifier is not critical 2.2 kilohm was used for R_a and R_b .

To understand how the signal gets through to the power amplifier we must take a look at Fig. 2. Since both R_a and R_b are decoupled, they appear as extra loads on the pre-amplifier output. In other words, instead of just R_L (the input resistance of the main amplifier) loading the pre-amplifier, R_a and R_b also appear, in parallel.

It is obvious that these must not load heavily; in other words each resistor (R_a and R_b) must not be less than 2 kilohm. The signal voltage developed at the output of the pre-amplifier still appears at the input of the main amplifier, merely by travelling along the centre conductor as usual.

CIRCUIT

The pre-amplifier circuit is shown in Fig. 3.

Approximate cost of components



1.70 inclusive

Components....

Resistors

R1	100k Ω
R2	100k Ω
R3	1.5M Ω
R4	15k Ω
R5	100 Ω
R6	1k Ω
R7	1k Ω
R8	470 Ω
R _a , R _b	See text

All $\frac{1}{4}$ watt \pm 10% carbon

Capacitors

C1	0.05 μ F ceramic
C2	100 μ F elect. 6V
C3	100 μ F elect. 6V
C4	25 μ F elect. 12V
C5	160 μ F elect. 12V
C6	160 μ F elect. 50V (See text)

Transistors

TR1	2N2926 (G) silicon <i>n</i> p <i>n</i>
TR2	2N3702 silicon <i>p</i> n <i>p</i>

Potentiometers

VR1	1k Ω horizontal skeleton preset
-----	--

Miscellaneous

MIC 1 Microphone insert (Acos), 0.1 inch matrix Veroboard (10 \times 14 holes), $\frac{3}{8}$ inch diameter Paxolin tube, screened cable, sheet aluminium

It is simply a high impedance input two-stage amplifier having a variable voltage gain, from 1.5 to 10; this is varied by VR1 and is useful where the sensitivity of the microphone may vary. As drawn, the circuit is suitable for crystal microphones or ceramic cartridges.

If the pre-amplifier is to be used for matching magnetic pick-ups, tape heads or dynamic microphones the input must be modified as shown in Fig. 4.

If to be used with an amplifier which has a stabilised supply as the prototype was, C6 is not required. However, for unstabilised supplies this will be necessary.

COMPONENT ASSEMBLY

The complete circuit is built on a piece of


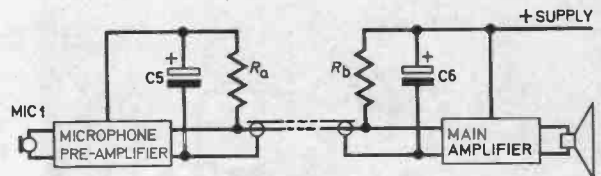


Fig. 1. Shows how the power supply for the pre-amplifier is obtained from the main amplifier.

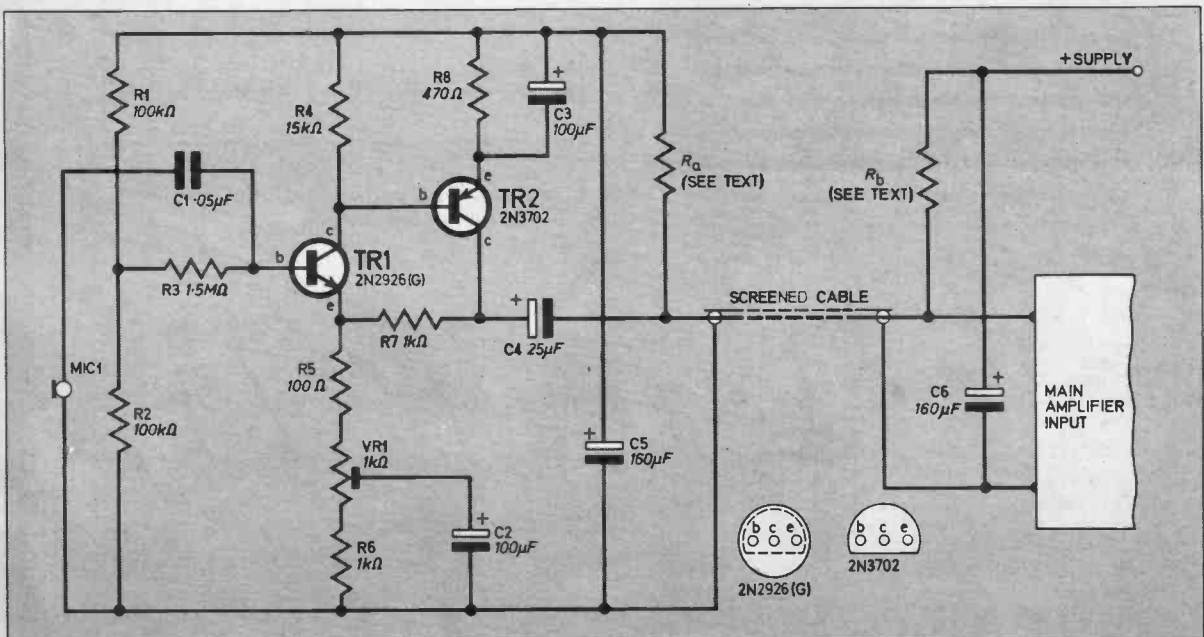

Fig. 2. Schematic diagram indicating additional loads on the pre-amplifier output.

Fig. 3. The circuit diagram of the pre-amplifier. Also shown are the base connections of TR1 and TR2.



TRANSISTOR MICROPHONE

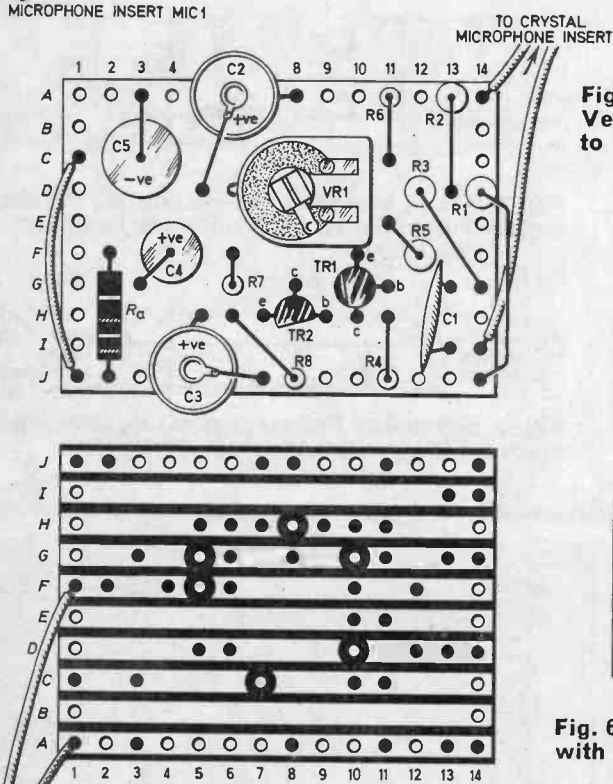
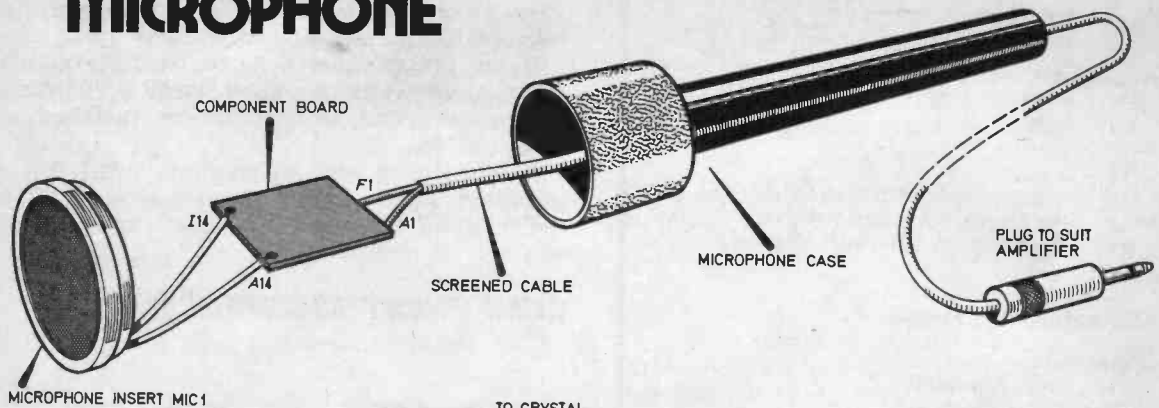


Fig. 5. (left) The layout on the top side of the Veroboard with (below) regions of copper strip to be removed.

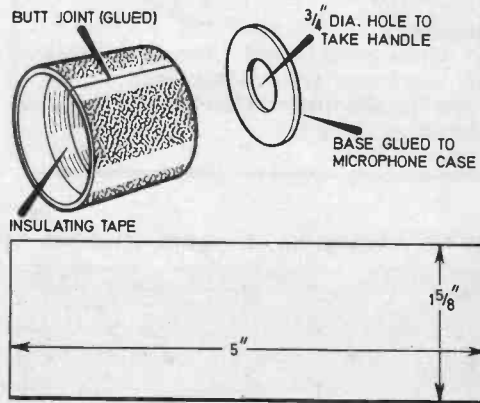


Fig. 6. (above) The cylindrical microphone head with "unrolled" dimensions.

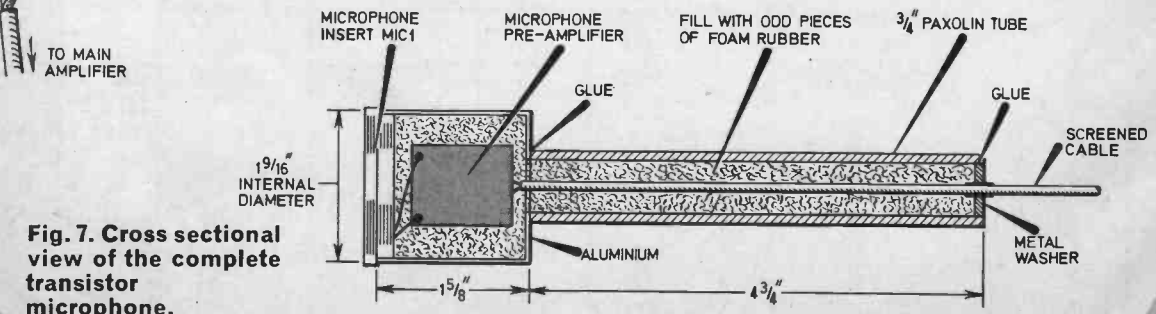


Fig. 7. Cross sectional view of the complete transistor microphone.

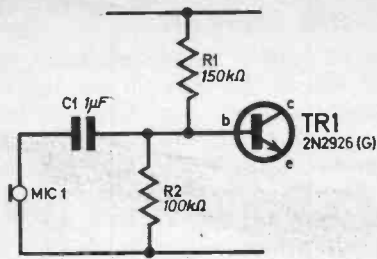


Fig. 4. Circuit diagram of the modification to be made at the input for matching to magnetic pick-up, tape head or dynamic microphone.

0.1 inch matrix Veroboard (10 x 14 holes). The layout of the components is shown in Fig. 5. Note that most of the components are mounted on their ends; this has been done to limit the overall size of the board so that the microphone head is as small as possible.

All components should be soldered in position on the top side of the Veroboard as shown. The transistors should be the last components to be mounted and a heat shunt should be used on the leads when soldering them in position. Before soldering TR1 and TR2, refer to the lead connections given in Fig. 3. to check that they are correctly mounted.

Also, be careful when soldering the leads to the crystal insert as too much heat may damage the crystal.

It is important to use screened cable for the output from the pre-amplifier, otherwise a lot of interference will be picked up.

CASE

The transistor-microphone is shown in Fig. 7 in cross-section. The top cylindrical part is made from a piece of $\frac{1}{8}$ inch aluminium sheet, dimensions 5 x $1\frac{5}{8}$ inches which is bent as shown in Fig. 6. and glued in position. The Paxolin tube is then pushed through the hole and held in position with Araldite as is the small metal washer at the other end of this tube.

ASSEMBLY

Begin to assemble by threading the screened cable through the Paxolin tube and then fill the tube with small pieces of foam rubber. Next line the inside of the cylinder and base with insulating tape and place the component board in position as shown in Fig. 7. Fill with more foam rubber.

The insert should then be placed in position and secured with glue. The transistor microphone is now complete and ready for connection to main amplifier.

Finally the circuit may also be used for high impedance transducers, the response of the pre-amplifier going well beyond the audio spectrum. □

ENSURE GREATER SAFETY
SAFETY
 with the 'DRIVER ALERT' system

Invaluable to the motorway driver—prevents "dozing" at the wheel.

Waa-Waa Pedal

Add excitement and sound variation to your music—simply built with CIR-KIT.

Rain Sensor

Keep your washing dry with the aid of this automatic alarm device.

Stick Down Wiring

Another popular method of circuit construction fully explained in words and pictures

All in the February Issue



The application of electronics to "pop" music—musical instruments and special effects devices

How many people, when they are listening to a piece of music either on the radio, record player, tape recorder, or live performances, realise the extent to which electronics plays in bringing this music to them.

Without electronics, modern-day "pop" music would not exist, for it is from basic electronic principles that these "new" sounds are derived.

Musical sounds relying almost entirely on electronic principles and theory really only started in a big way back in the "mid-fifties", with the introduction of the solid "electric" guitar. The sound produced by this instrument caught on immediately and was an overnight success with the younger generation of this time—and still is with present-day teenagers although the overall sound has become more sophisticated with the addition of special effect devices to be described in this article.

It is true to say that electronics and its application to the musical field has played a major role in shaping the music we hear today. It is fair to say that electronics has revolutionised modern-day music, and in the future will play an even bigger part both in existing sounds and creating totally new ones.

ELECTRIC GUITAR

Without doubt the "electric" guitar has become one of the most (if not the most) popular musical instruments. Although tuned in the same way as an ordinary acoustic guitar, having similar string length and fretting arrangement, the sound produced is vastly different—a much smoother and at the same time, harder, more solid, sound is produced with a wide range of tone.


Now all electric guitars have situated below the strings a magnetic pick-up which consists of a central magnet located under each string with copper wire (many turns) wound around this magnet. When the steel strings are plucked and caused to vibrate, the steel, being magnetic, affects the magnetic field around the string causing a current to flow in the copper coil (conductor). This current (signal) as then passed to an amplifier where it is made more powerful—powerful enough to drive a loudspeaker.

Interposed between the pick-up and amplifier there is usually a tone and volume unit, the volume being nothing more complicated than a potential divider, while the tone control is a little more involved. A typical tone circuit merely provides a control over the amount of bass and treble that is required. A full tone circuit usually has both treble boost/cut and bass boost/cut.

For convenience, these controls are located on the guitar itself, and are separate and additional to those incorporated in the main amplifier.

ELECTRONICS and the MUSIC SCENE


By B. W. Terrell B.Sc.

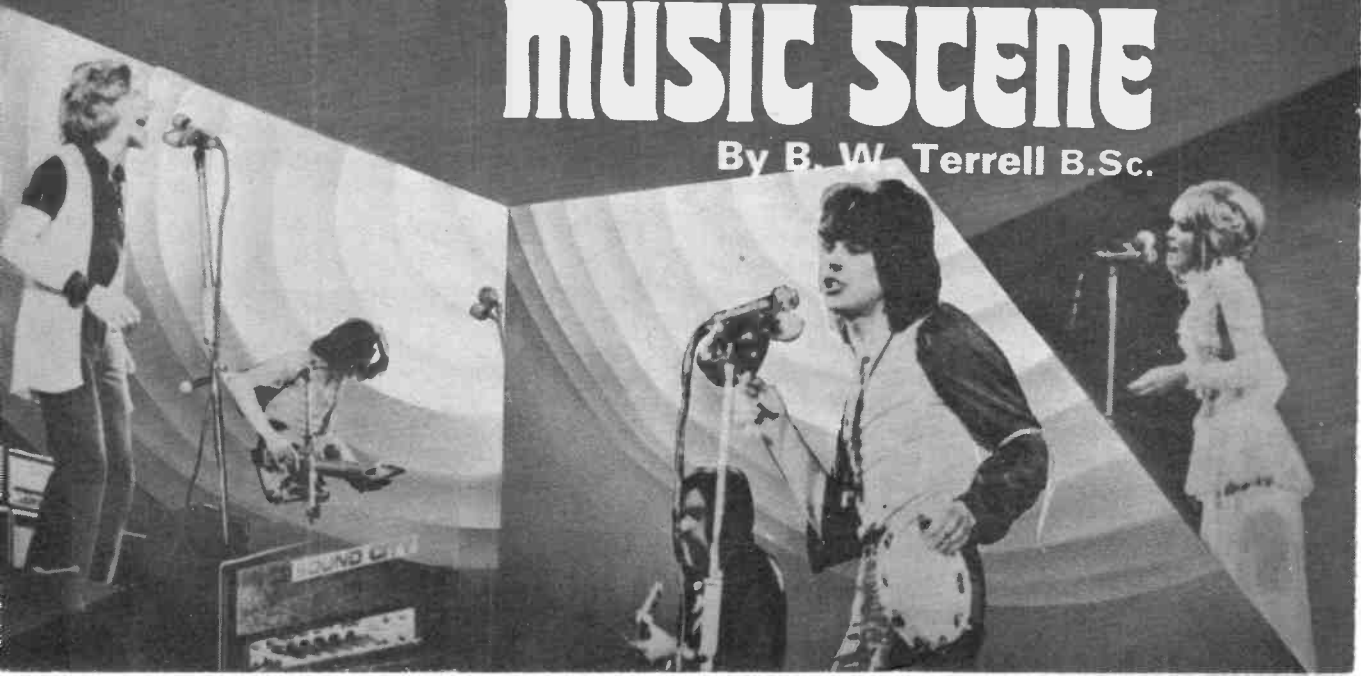

AMPLIFIERS

All electric guitars and other electronic musical instruments need an amplifier of one sort or another to enable them to be heard.

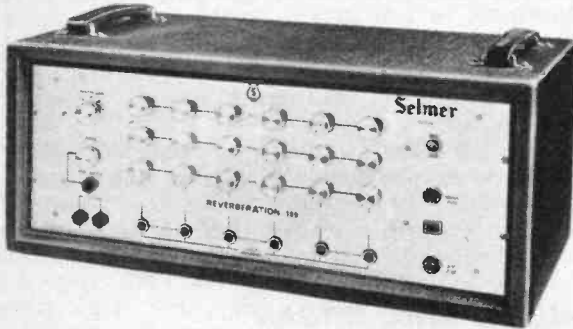The amplifier is the most used piece of electronic circuitry in the modern music field. Without it hardly anybody would be able to hear what is being played. It is an absolutely essential piece of equipment when playing to an audience, whether for amplifying an "electronic" sound, or amplifying conventional musical instruments such as acoustic guitar, violin, piano or trumpet via a microphone.



A typical amplifier in use on the "pop" scene today. It can deliver up to 100 watts. There are six independent inputs with individual treble/bass controls and two of these inputs have built-in "reverb" units.

TREMOLO/VIBRATO

The tremolo and vibrato units were of the very first "special effects" devices to be devised, and they are often confused with one another because they produce very similar sounds. Nowadays they are nearly always incorporated in power amplifiers designed for "pop" work.

The electronic principle evident in both of these devices is that of modulation, that is to say, the signal produced by the musical instrument is mixed with the output from a low-frequency oscillator whose amplitude (vibrato) or frequency (tremolo), can be varied. The sound produced in both cases is a low frequency regular pulsating effect superimposed on the signal, which is both pleasant and melodious.

Most tremolo units also incorporate the vibrato effect as well, and the two controls found on this unit are marked "depth" and "speed" and can be used in any combination to provide the desired effect. The depth control varies the amplitude of the oscillator output, while the speed control alters the frequency.

ECHO CHAMBER

Another "effectual" box that falls into the same general category as the above is the echo-chamber. This electro-mechanical instrument had its heyday with the music played by such groups as the "Shadows" and at the time was

extremely popular. It sounds novel, and as its name implies, produces an echo (or echoes) a short time after the original signal has been played, each successive echo being attenuated.

The idea is fairly simple, but its design and operation are quite involved. Its operation relies on the technology of the tape recording industry since in effect it is a small magnetic tape recorder but with a difference—the tape used takes the form of a small loop about 1 foot in circumference and there are several playback heads set specific distances apart. Basically what happens is that the input signal is recorded on to the tape by the record head of the machine, and then played back at each of the playback heads in turn, thus producing an echoing sound.



A completely electronic portable echo and reverberation unit combined. Can be used with both electronic musical instruments and microphone.

REVERBERATION UNIT

A similar device to the "echo-chamber" is the reverberation unit—more commonly referred to as a "reverb".

The effect on the musical instrument input signal is to make it sound "ghostly" rather like the sound produced when singing, talking, or playing an instrument in an empty room or hall.

This effect called reverberation is produced naturally in such enclosures because the hard surfaces, walls, ceiling and floor, cause the sounds to be bounced back and forth across the room or hall, gradually being attenuated

and eventually dying away.

This effect can be simulated electronically by applying a theory of electricity which says that the velocity of sound through materials such as air, water and metals is considerably slower than when it is passed as electronic signals through circuitry. The input signal firstly passes into a pre-amplifier and is then split into two channels. One half passes straight through to the output whilst the other half is transmitted as sound pressure waves through a "delay" spring line via an electromagnetic unit, and then picked up at the other end by a similar device which reconverts the acoustic signal to an electrical one again.


The two split signals are then mixed and passed to the main amplifier. The output sound is composed of two distinct effects, a short-term echo and the reverberation sound which continues for some time.

FUZZ BOX

Perhaps the most popular special effect so far devised is the fuzz sound which has only really been made possible by the introduction, and relative cheapness, of the transistor. It is very rarely incorporated "inside" any other equipment and is usually found in a small box and operated by a footswitch when desired.

The fuzz unit, or as it is sometimes called—tone bender—can be used with any musical instrument but is found usually in use by "heavy pop" groups on lead guitar and here again is limited in most cases to solos. The effect is quite dramatic.

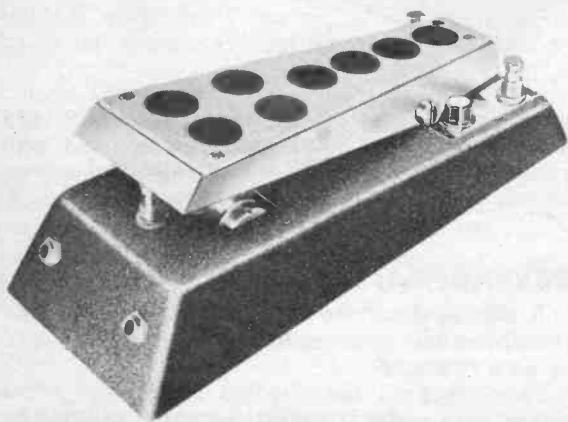The circuitry of the fuzz box is quite simple—a two-stage transistor amplifier with the second stage in an overdriven state so that the input waveform is clipped and distorted.



A combined fuzz and waa-pedal for use with guitar and electronic organ.

WAA-WAA

In recent years a new sound emerged which has been given the name waa-waa and whose

sound bears little resemblance to the input signal.

The waa-waa effect used chiefly in the pop music field by inputting a guitar or other electronic musical instrument to a band-pass filter whose resonant frequency can be varied. When this is done rapidly, the so called waa-waa effect is obtained.

This instrument again is entirely dependent on transistors and in this case, on their "noiseless" switching properties.

The heart of this device is the band-pass filter whose resonant frequency is able to be continually changed from a position in the bass spectrum to one in the treble spectrum, in a smooth but fast operation. This can quite easily be done by switching the capacitors in the filter mechanically, but then loud clicks will be heard and these are unwanted.

The noiseless switching is accomplished by using the output from a transistor multivibrator to suitably bias the other transistors "loaded" with the capacitors so that they can be switched in and out of the filter network.

ELECTRONIC ORGAN

Although the electronic organ has been in existence for quite a considerable time its presence was not felt to any great extent until comparatively recently when the transistor appeared on the scene of commercial musical products.

Previous to this, electronic organs were constructed using valves, and since many valves are required in their circuitry they were extremely heavy and bulky and not easily transportable.

The transistor, because of its size and low weight, solved the problem of transportation and overall size, and now that transistors are considerably cheaper (and have been for some-time) than their valve equivalents, people have been able to afford to buy themselves an electronic organ and keep it in their own homes. Thus electronic technology has made possible an extremely popular and versatile musical instrument for use by many.

On inspecting the "workings" of a modern transistorised organ one may think the circuitry is extremely complicated due to the many hundreds of components and wires to be seen, but when it is broken down into sections it is seen to consist of quite basic circuits and principles.


Essentially, the electronic organ is a bank of oscillators, in general, twelve very stable and accurate oscillators each made to oscillate at each of the frequencies of the twelve notes in the musical scale in a high pitch region above soprano.

These oscillators, generally with outputs of the square and sawtooth variety to ensure the presence of harmonics, are then stepped down

by successive frequency-dividers to give a wide range of musical notes extending over many octaves.

Depressing the keys on the keyboard merely "completes the circuit" of the oscillator and produces an audible sound.

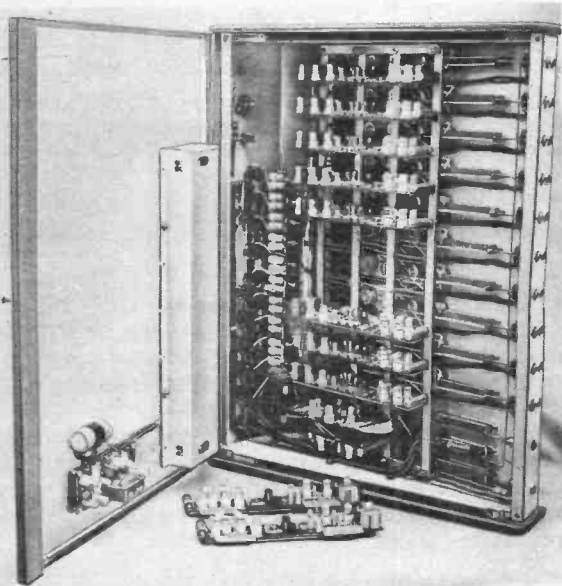There are many "stops" on the larger type of organ which when placed in circuit by pushing down bring in wave shaping circuits to produce sounds of similar pitch and character to other musical instruments—in fact nearly all musical instruments in use. Also a lot of organs have the built-in special effects, discussed above, such as fuzz, waa-waa, tremolo, echo, reverberation and many others.



A ten-channel audio mixing unit with built-in "reverb". Each channel has its own tone controls and slider volume control. (above) The electronics within—its size and compactness is due to the use of semiconductors.

The Ring Modulator—a new addition to the special effects field producing music with a decidedly "electronic" character—for use with musical instrument and microphone.



OTHER DEVICES

Other "electronic-music-boxes" on the market include the electronic piano, electronic drum-beats, ring modulator, the music synthesiser, and the latest device—a completely electronic drum kit.

The present trend in designing these devices is firstly to completely analyse the waveform of the audio signal produced by musical instruments, with the aid of an oscilloscope and filter networks, and then devise wave shaping circuits to shape the output from various kinds of oscillators, to produce a similar, if not exact sound.

The Moog synthesiser was the first commercial instrument of this kind but the EMS Synthi-100 is perhaps the ultimate in present electronic music and is an extremely complex piece of equipment which can produce almost any sound desired. The main use of the electronic synthesiser is in the professional recording studio using multitrack recording systems, and really falls outside the scope of this article—but, however, deserves a mention.

Yes, electronics really has played a leading part in recent years in changing the musical sound, especially on the pop scene. Many of the effects devices mentioned in this article are easy to construct and full theoretical and construction details of some of these will be published in later issues of *EVERYDAY ELECTRONICS*. A fuzz box was described in the December 1971 edition, and there will be a waa-waa in the February 1972 issue. □

ELECTRONIC CIRCUITS -
..... IN THEORY and PRACTICE

TEACH-IN

... FOR BEGINNERS

By Mike Hughes M.A.

3

RESISTANCE

LAST month, we implied that there was a relationship between electrical current, voltage and resistance. This month we shall show what this relationship is but first of all let us see the effect of controlling an electric current with a resistor, and then talk a little about resistors themselves.

To do this we shall have to be a little in advance of our knowledge of the workings of an electronic component called a potentiometer. This does not matter provided one realises that it is only a device for controlling the electrical resistance of a circuit. We have built four such potentiometers into the Demo Deck; now is the time to start making use of this piece of equipment.

EXPERIMENT

We shall start by controlling the brightness of a bulb using a potentiometer. This is a technique that most people understand in practice but may not fully understand in principle. First connect up the simple circuit shown in Fig. 1. This uses the battery B1, the potentiometer VR1 (which has a value of 100 ohms) and the lamp LP1. Ensure that the battery is 9V (i.e. two 4.5 volt batteries connected in series) and that the lamp is a 6 volt 0.06 amp type.

No soldering is needed at this stage. Simply cut some insulated wires to length, strip off about a quarter of an inch of insulation from each end and interconnect the terminals of the Demo Deck. Before making the final connection make sure that the knob of VR1 is turned fully anticlockwise.

When this connection is made the lamp should light up, but only dimly. If the knob of VR1 is now turned clockwise the lamp will brighten. By turning the knob we are in fact reducing the resistance of VR1. The lamp needs an electric current of 0.06 amp to flow to light up to its brightest level. The lamp itself has a resistance to the flow of current and is so designed that when it is connected across a battery of 6 volts this is the current that flows.

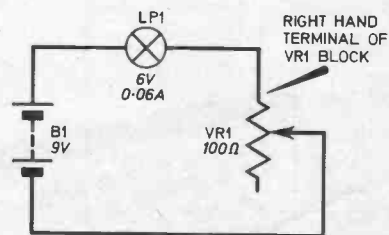


Fig. 1. Circuit diagram for illustrating the current flow through a bulb. VR1 controls the brightness of the bulb.

By introducing VR1 into the circuit we are increasing the total resistance and even though we are operating from a higher voltage, i.e. 9V than the bulb should be run from, we are not allowing the necessary 0.06 amp to flow. As we reduce the value of VR1 we allow more and more current to flow, until the resistance of VR1 becomes zero. At this point maximum current will flow, which, incidentally, will be greater than that which should be allowed to flow

through the lamp because we are operating from 9V instead of 6V. If the bulb is allowed to run at this full current for too long it will "blow". You are therefore advised to carry out the experiment with some discretion.

UNITS OF RESISTANCE

Electrical resistance is measured in units called ohms. Because of the wide range of currents we come across in electronics from amperes to millionths of an ampere, it should, even at this stage seem reasonable to expect that resistance values range from ohms to millions of ohms. This is indeed the case. Because we shall frequently be referring to resistance value in diagrams, we use the symbol Ω (omega) to represent "Ohm" and to save writing large numbers of zeros (which could lead to errors) we use abbreviations to denote thousands and millions of ohms. One thousand ohms would be written $1k\Omega$ (k standing for kilo). When speaking we say "one kay"; 120,000 ohms would be 120 kilohm. The abbreviation for a million is M (mega); 2,200,000 ohms would be written 2.2 Megohm and would be stated as "two point two meg".

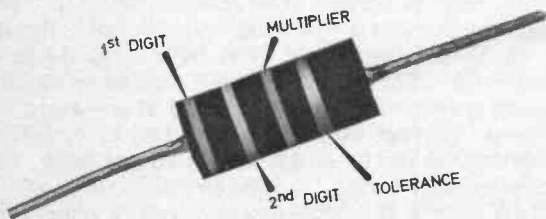


Fig. 2. A carbon composition type resistor showing international colour coding used to identify the values of such resistors.

COLOUR CODE

Due to the small size of $\frac{1}{4}$ watt and smaller carbon resistors, it is impracticable to print values on the body. To indicate the ohmic value and tolerance of a resistor a colour code, known as the international colour code, has been devised and is given in Table 1. Due to its versatility it is used on all carbon resistors.

Usually there are four coloured bands on the resistor body, the first three indicating the ohmic value and the fourth band giving the tolerance limit. The code should be read starting with the band nearest to the end of the resistor body (usually the other end has a metallic, gold or silver, band).


The first band gives the value of the first digit, the second band gives the second digit whilst the third band gives the multiplying constant, or more simply, the number of zeros to place after the first two digits. The fourth band indicates the tolerance, see Fig. 2.

Table 1: RESISTOR COLOUR CODE

Colour	Digit (1st 2 bands)	Multiplying Factor (3rd band)	Tolerance \pm per cent (4th band)
Black	0	1	—
Brown	1	10	1
Red	2	100	2
Orange	3	1000	3
Yellow	4	10,000	4
Green	5	100,000	—
Blue	6	1,000,000	—
Violet	7	10,000,000	—
Grey	8	100,000,000	—
White	9	1,000,000,000	—
Gold	—	0.1	5
Silver	—	0.01	10

No fourth band indicates a tolerance of ± 20 per cent

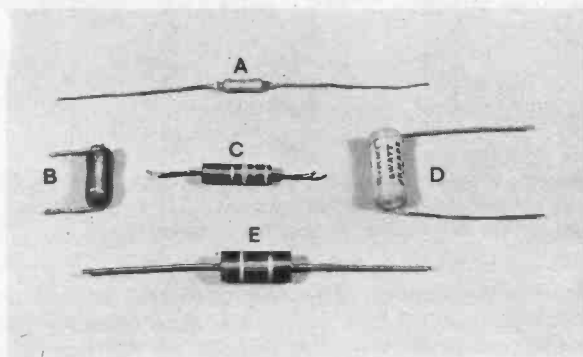If the third band is a metallic one, i.e., gold or silver, then the multiplying factor is less than unity, 0.1 and 0.01 respectively. Therefore, when the third band is gold, divide the first two digits by 10. If it is silver divide by 100.



Various types of resistor: (A) high stability (B) low value (C) and (E) carbon composition types (D) high wattage wire wound.

PREFERRED VALUES

Because of the wide range of possible values of resistors, an international standard of "preferred values" has become universally accepted. These values are based on the following grid of numbers:

1.0	1.5	2.2	3.3	4.7	6.8
1.1	1.6	2.4	3.6	5.1	7.5
1.2	1.8	2.7	3.9	5.6	8.2
1.3	2.0	3.0	4.3	6.2	9.1

The values may be the above numbers expressed directly as ohms or as any multiples of ten of these numbers.

It is very difficult to make a resistor having exactly one of these values and so all resistors have a tolerance to their actual value. Usual tolerances are ± 20 , ± 10 and ± 5 per cent (%).

VARIABLE RESISTORS

We have already experienced the use of a variable resistor—in actual fact we used a device which in electronics is more commonly called a potentiometer. The difference between a variable resistor and a potentiometer is that the former has only two connections, one to the end of a resistive strip and the second to a wiper that is made to traverse the resistive strip, usually in a circular path. The potentiometer has three terminals one to each end of the resistive strip and the third to the wiper. Fig. 3 shows the circuit symbol for potentiometers.

One can come across a range of values of potentiometer very similar to fixed resistors and again, power dissipation has to be specified. Usually $\frac{1}{2}$ watt devices are used and these are certainly the least expensive but power ratings can go as high as 5 watts in quite everyday circuits.

Tolerance does not usually matter a great deal with variable components, but an important feature of a potentiometer is its "Law". A linear

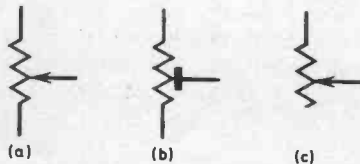



Fig. 3. Circuit symbols for (a) spindle type (b) preset potentiometers. Diagram (c) is what should be termed a "variable resistor".

law potentiometer (usually referred to as a "Linear pot") has a resistance that changes in exact proportion to the degree of rotation of the shaft; a logarithmic device ("Log pot") has a resistance that increases logarithmically with the degree of shaft rotation. This type of potentiometer is most usually encountered when used as a volume control, because there is a logarithmic relationship between the sensitivity of the ear and electrical signal that produces the power in the loudspeaker.

There are two physical types of potentiometer; one is a manually controlled device for use with a knob, and the other is a preset device which is usually set up with a screwdriver.

In some circuits, particularly experimental ones, it may be found that a fixed resistor is called for, but the exact value cannot be accurately specified. In this case the designer may call upon a "skeleton preset" potentiometer. This is identical to a conventional preset potentiometer except that it is usually smaller and as the name suggests has no enclosure.

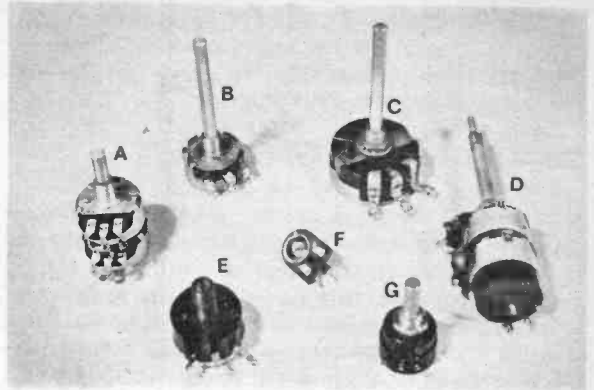For the next stage you will be needing three fixed resistors, so see if you can work out the colour codes for the values and identify them. We need 1 kilohm, 10 kilohm and 22 kilohm.




Different kinds of potentiometers: (A) ganged (B) and (C) general carbon types (D) ganged with on/off switch (E) T.V. type preset (F) skeleton preset (G) general wire wound.

OHM'S LAW

We shall now carry out a simple experiment to verify Ohm's Law. This is the fundamental relationship on which all electronics is based. While we promised the bare minimum of mathematics this is one simple piece which ought to be fully understood. We have already encountered Ohm's Law without realising it. It simply states that the magnitude of an electric current flowing through a resistor is directly proportional to the e.m.f. across the resistor. In mathematical terms I is proportional to V or $V = I \times R$ where R is the proportionality constant and is called the resistance.

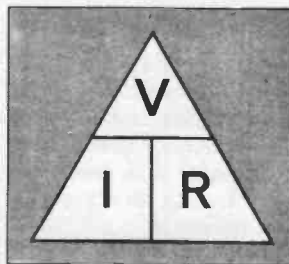Therefore by knowing two values, say V and R we can calculate I . Knowing I and V we can calculate R . The triangle below is a simple way of remembering Ohm's Law.



$$\begin{aligned} R &= \frac{V}{I} \\ V &= IR \\ I &= \frac{V}{R} \end{aligned}$$

V is measured in volts
 I is measured in amperes
 R is measured in ohms

These units must be used otherwise you will obtain wrong answers from your calculations.

VERIFICATION OF OHM'S LAW

Let us show that the current flowing through a resistor is exactly inversely proportional to the value of resistance for a given voltage. Ensure

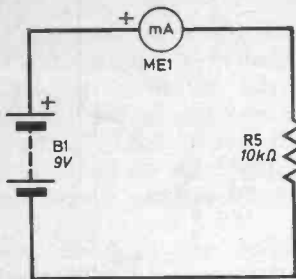


Fig. 4 (a). The circuit used to verify Ohm's Law.

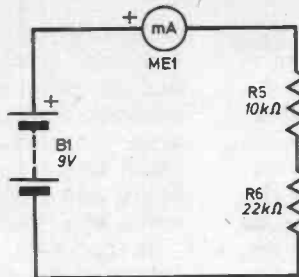


Fig. 4 (b). Resistors in series.

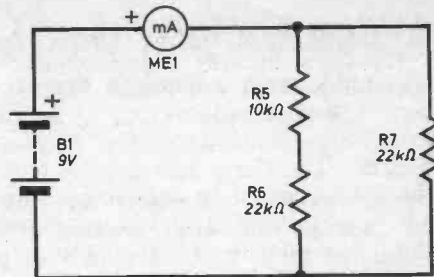


Fig. 4 (c). Resistors in parallel.

that B1 of the Demo Deck is set for 9 volts and connect a 10 kilohm resistor between two terminal lugs by careful soldering (only solder the resistor by the ends of the wires so that it may be re-used later). Now connect the resistor, battery and meter in series according to the circuit diagram of Fig. 4(a). Note that we have now introduced a symbol ME for the meter. For the purpose of this experiment we can ignore the fact that the meter has a resistance of its own. Use a meter with a full scale deflection of 1mA.

Provided that you have connected the meter the correct way round (the positive terminal connected to the leg of the circuit which is closest to the positive terminal of the battery), the meter should show a reading. The meter should read approximately 0.9mA (1mA is 0.001 amperes and is referred to as 1 milli-amp). Remember that all components have a tolerance and that the output voltage of a new battery is always nominally high therefore do not expect to get an exactly similar reading. Therefore we can say that an e.m.f. of 9 volts across a 10 kilohm resistor will force a current of 0.9mA through the resistor: we could have calculated this by Ohm's Law,

$$I = \frac{V}{R}$$

$$I = \frac{9}{10,000}$$

$$= 0.0009 \text{ amperes or } 0.9\text{mA}$$

We can now carry out a simple but very significant experiment by working the equation backwards thus finding out the value of unknown resistors.

RESISTORS IN SERIES AND PARALLEL

Connect a 10 kilohm and 22 kilohm resistor in series and measure the current when they are placed in the circuit shown in Fig. 4b. The current measured should be approximately 0.28mA. Using Ohm's Law, calculate the effective resistance of both resistors in series.

Obviously it is

$$R = \frac{9}{0.00028}$$

$$= 32,000 \text{ ohms or } 32 \text{ kilohm.}$$

We could have arrived at this result simply by adding the values of the two resistors together. The rule for calculating the total resistance of any number of resistors in series is

$$R_{\text{total}} = R_1 + R_2 + R_3 + \text{etc.}$$

Leaving the 10 kilohm and 22 kilohm resistors in series, now connect a third resistor of 22 kilohm in parallel across both as shown in the circuit of Fig. 4c. Now what is the total resistance of the three resistors? First of all measure it experimentally: the current should be approximately 0.69mA giving, using Ohm's Law, a resistance of 13 kilohm. Obviously the relationship is not quite so simple as it was with series resistors, nevertheless it is fairly straightforward. The rule for calculating the total effect of resistors in parallel is

$$\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \text{etc.}$$


For the simple case of two resistors in parallel this simplifies to

$$R_{\text{total}} = \frac{R_1 \times R_2}{R_1 + R_2}$$

In our case the resistance of the two resistors in series is 32 kilohm therefore (if we work in thousands of ohms)

$$R_{\text{total}} = \frac{32 \times 22}{32 + 22} = 13 \text{ kilohm}$$

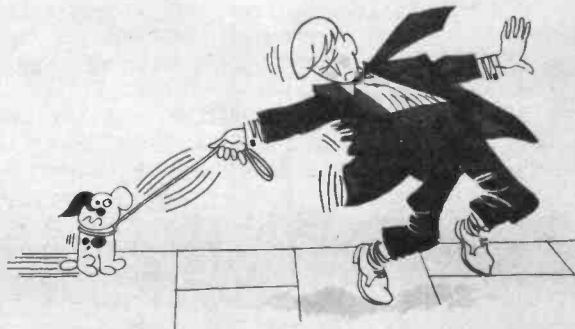Next Month: Building a simple voltmeter on the Demo Deck, and a discussion on power in electronic circuits.



A simple m.w. reflex circuit receiver. Easy to build, with a modern design case.

THIS receiver contains no coils or chokes except the aerial winding which has been designed to be made as easily as possible. The resulting receiver is simple to construct and must be considered one of the best designs published for the inexperienced home constructor.

Providing the Veroboard layout drawing is followed carefully and the aerial wound as described the Astron should work "first time" without any instability or tuning problems.

The Astron employs four transistors, the first transistor being used in the reflex mode. This enables one transistor to do the work of two and hence much more gain can be obtained than

is normally possible. The performance is not to the same standard as that of a superhetrodyne but is adequate for the reception of local stations. Operating the receiver in the London area the three medium wave B.B.C. stations could be received together with Radio Luxembourg and some continental stations during the hours of darkness.


In the past many reflex designs have been published but the majority require complicated, and other hard to get components.

Approximate cost of components

£ 3:00 excluding case

ASTRON

by M. A. Rambaut

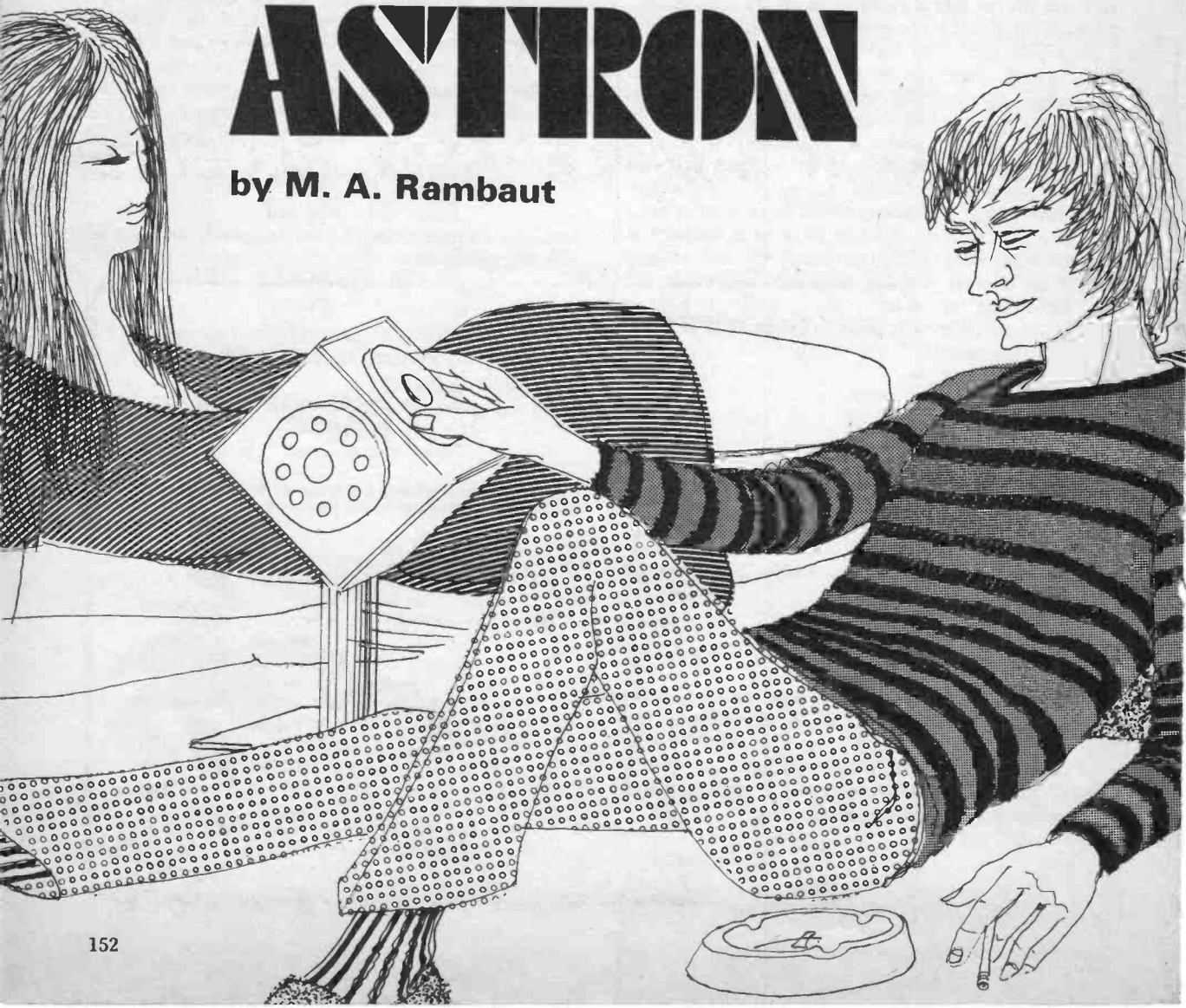

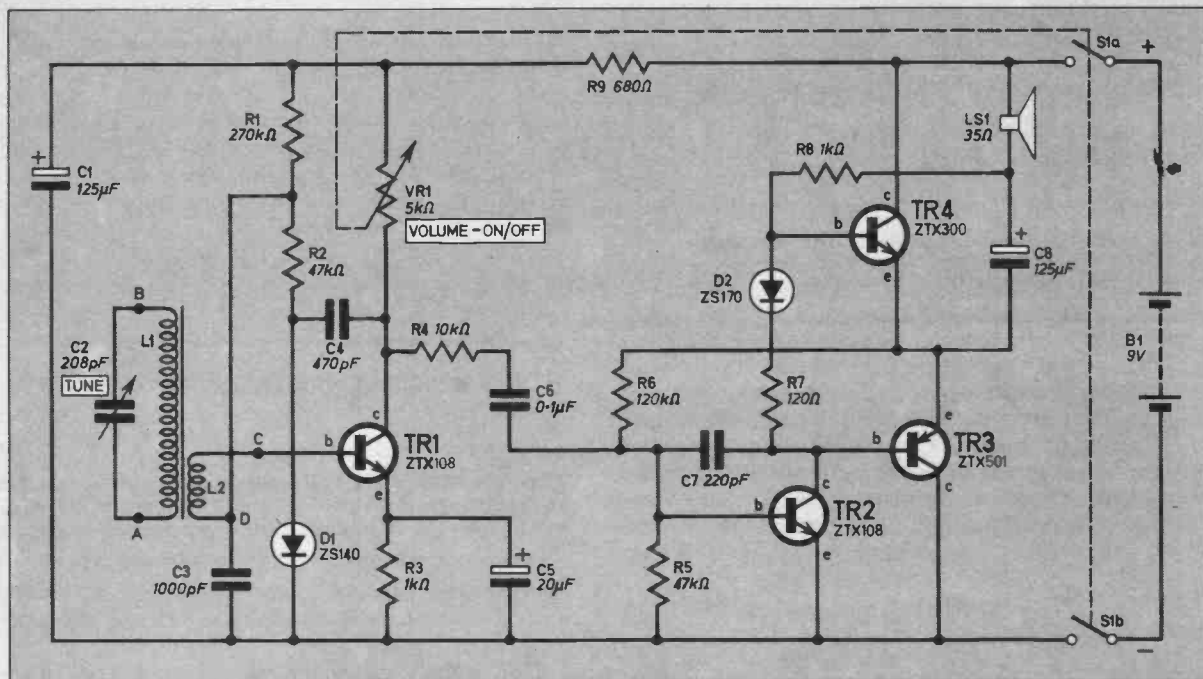


Fig. 1. Circuit diagram of the Astron m.w. receiver.

NEW LOOK SIMPLE M.W. RECEIVER

Components....

Resistors

R1	270k Ω
R2	47k Ω
R3	1k Ω
R4	10k Ω
R5	47k Ω
R6	120k Ω
R7	120 Ω
R8	1k Ω

All $\frac{1}{4}$ W $\pm 10\%$ carbon

Capacitors

C1	125 μ F elect. 16V
C2	208pF variable
C3	1000pF
C4	470pF
C5	20 μ F elect 16V
C6	0.1 μ F
C7	220pF
C8	125 μ F elect 16V

Semiconductors

TR1	ZTX 108 silicon <i>npn</i>
TR2	ZTX 108 silicon <i>npn</i>
TR3	ZTX 501 silicon <i>pnp</i>
TR4	ZTX 300 silicon <i>npn</i>
D1	ZS 140
D2	ZS 170

Miscellaneous

VR1	5k Ω log carbon potentiometer with d.p.s.t. switch (S1)
LS1	3 $\frac{3}{8}$ inch 35 Ω loudspeaker
B1	9V battery (PP3 type) and connector
L1	formed from 90 turns of 28 s.w.g. enamelled copper wire
L2	formed from 8 turns of p.v.c. covered 7/0076in connecting wire

6 inch ferrite rod, $\frac{3}{8}$ inch diameter
 Connecting wire, Veroboard 2in x 3in x 0.1in matrix, materials for case (see Fig. 5 and text)
 4BA fixings
 A kit of Perspex parts for a similar case to that described, including turned knobs, is available from KASPEX (mail order only).


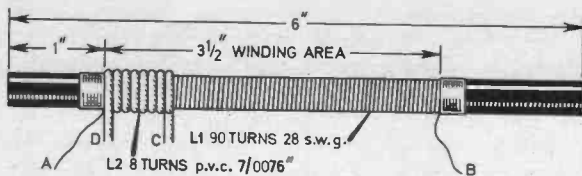
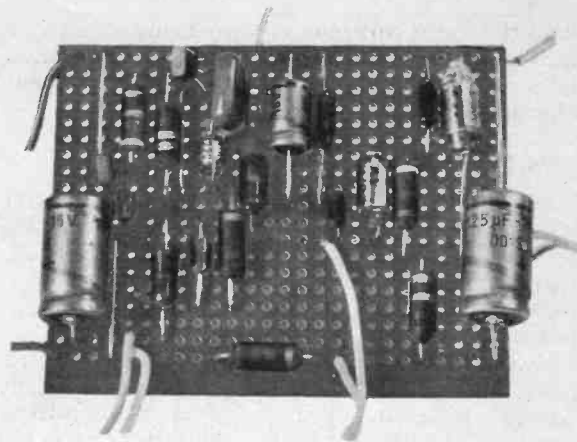
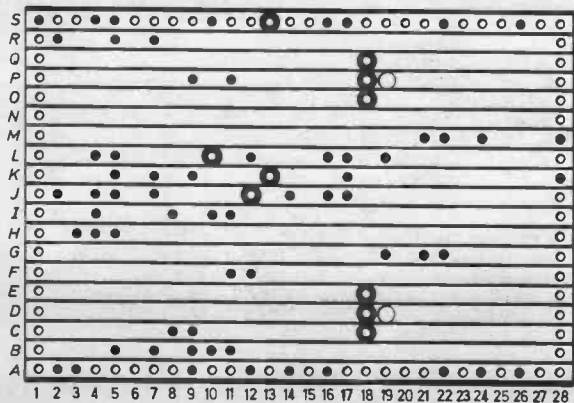


Fig. 2. Detail of aerial coil on ferrite rod.

CIRCUIT DESCRIPTION—First Stage

The signal is picked up by the ferrite rod aerial and tuned by the tuned circuit C2, L1 Fig. 1. it is then coupled from the tuned circuit to the first transistor TR1 by L2. This allows the high impedance of the tuned circuit C2, L1 to be matched to the low impedance of the transistor input without damping the tuned circuit and

Fig. 3. Veroboard layout and wiring, showing both sides of the board.

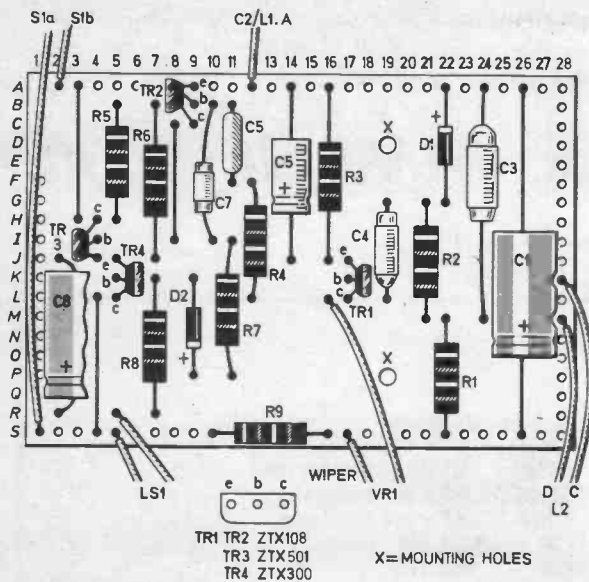

The top side of the Veroboard showing all the components mounted in position ready for connection to the other components shown in Fig. 4.

losing selectivity and gain. Transistor TR1 then amplifies the signal and feeds it to the detector circuit containing D1.

The 470pF capacitor C4 is a much lower impedance to the r.f. (radio frequency) than the 10 kilohm resistance R4 hence the signal tends to go through the capacitor. The a.f. (audio frequency) component now left after detection by D1 is passed through R2 and L2 to the base of the first transistor; C3 helps to filter out any residual r.f. The signal is now amplified for the second time by TR1. This time the a.f. signal sees C4 as a high impedance compared with R4 and so the signal current flows to TR2 base.

AUDIO STAGE

Transistors TR2, TR3 and TR4 make up a push-pull amplifier, TR3 and TR4 are a complimentary output pair and TR2 is the driver. The signal is amplified by TR2 and the positive cycles of the audio signal are fed through TR4 via D2 and the negative cycles are fed through TR3. The two signals recombine at C7 after amplification, giving the output signal. This is then fed to the loudspeaker LS1.

THE DIODE

Diode D2, R7 and R8 set the standing or bias current in the output stage and R5 and R6 set the working point and gain of the stage. Capacitor C6 removes the residual r.f. component from TR1 output waveform. Resistor R9 and C1 smooth out variations in supply voltage caused by large a.f. currents in the output stage so preventing low frequency feedback and possible oscillation.

The volume control VR1 works by adjusting the load on TR1; if there is no load resistance then the collector is connected to the supply voltage and cannot swing up or down in voltage with varying collector current. The larger the

load the more collector voltage swing is possible in theory, but in practise the load is limited because distortion occurs due to non-linear characteristics of the device.

WINDING THE AERIAL

Most people do not like winding coils and many are put off building a radio simply because of this. The drawings and photograph show clearly how the aerial coils in the Astron are wound and the winding should not present any problems.

Take the ferrite rod and mark where the coil has to go (Fig. 2.). Wind on one turn of plastic adhesive tape just outside the winding area and then reverse the tape so that the adhesive side is on the outside. Continue to wind on enough tape, inside out to cover the winding area, finish by reversing the tape for one turn to secure it to the rod. The primary (L1) is now wound on, the reversed adhesive tape holding it in position.

Simply hold one end of the 28s.w.g. enamelled copper wire and wind 90 turns around the rod trying to keep a small space between each turn. Do not worry if some turns touch each other but try not to get any turn on top of previous turns. When all 90 turns are in place wind one turn of adhesive tape around each end to hold the coil. The wires at each end should be left about 6 inches long so that they can be connected to the board.


Next wind on the secondary (L2) on top of L1. L2 is wound in the same direction as L1, using p.v.c. covered seven strand wire (the type normally used for connecting up wire); this wire is called 7/0076 inch p.v.c. covered. Starting at the earth end of the previous winding put on 8 turns of this wire keeping each turn tight and close together. Leave about 4 inches of wire at each end to connect to the Veroboard and tie a knot or twist these wire ends together to hold the coil.

CIRCUIT BOARD







With the aerial wound the components can be mounted on the Veroboard. The board shown in Fig. 3. is cut to size and drilled for mounting holes before the copper strips are cut away as shown. Mount all components and flying leads except the transistors and leads to L2. Next check for correct polarities and positions and then mount the transistors, if in doubt about your ability to solder transistor leads quickly and cleanly use a heat shunt on the leads.

The next stage is to wire the board to the remaining components as shown in Fig.4, but do not place them in a cabinet yet. Finally check the circuit and connect the battery observing correct polarity, switch on the receiver, turn the volume fully up and listen for a hissing sound that will show that the output stages are functioning. Slowly tune C1 using a plastic knob

Fig. 4. Wiring diagram of the components of the Astron. The parts are shown in their relative positions as they are mounted in the case.

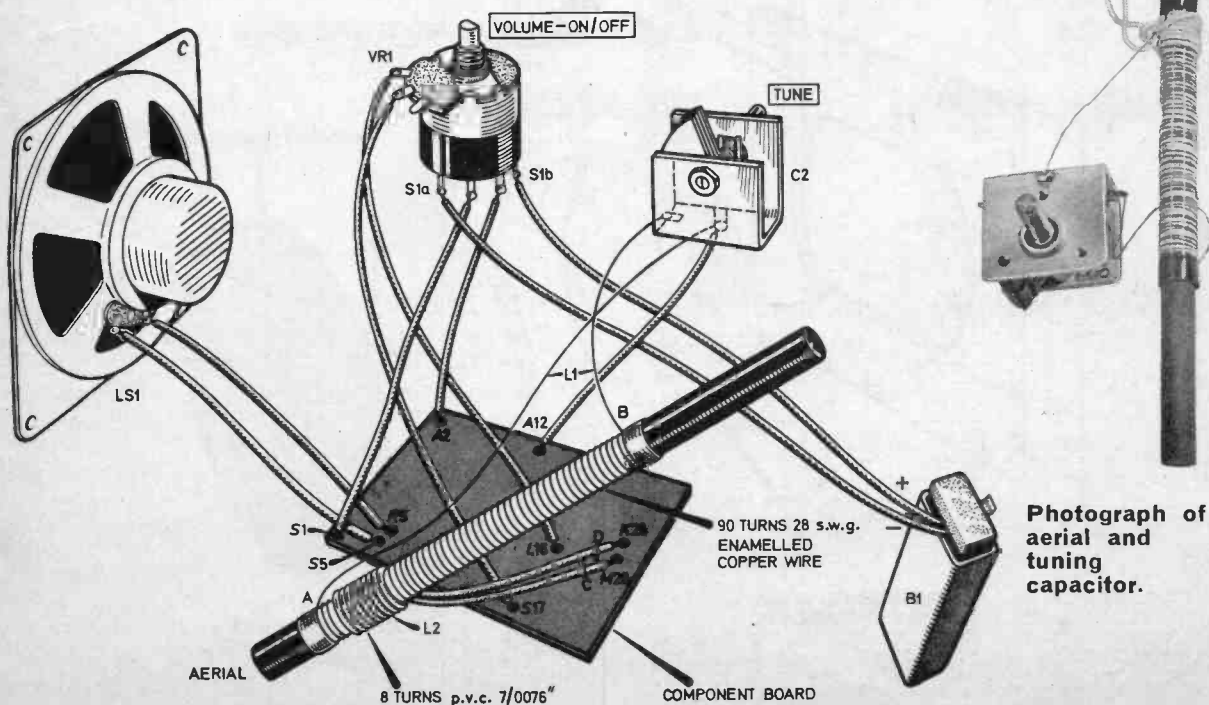

ASTRON

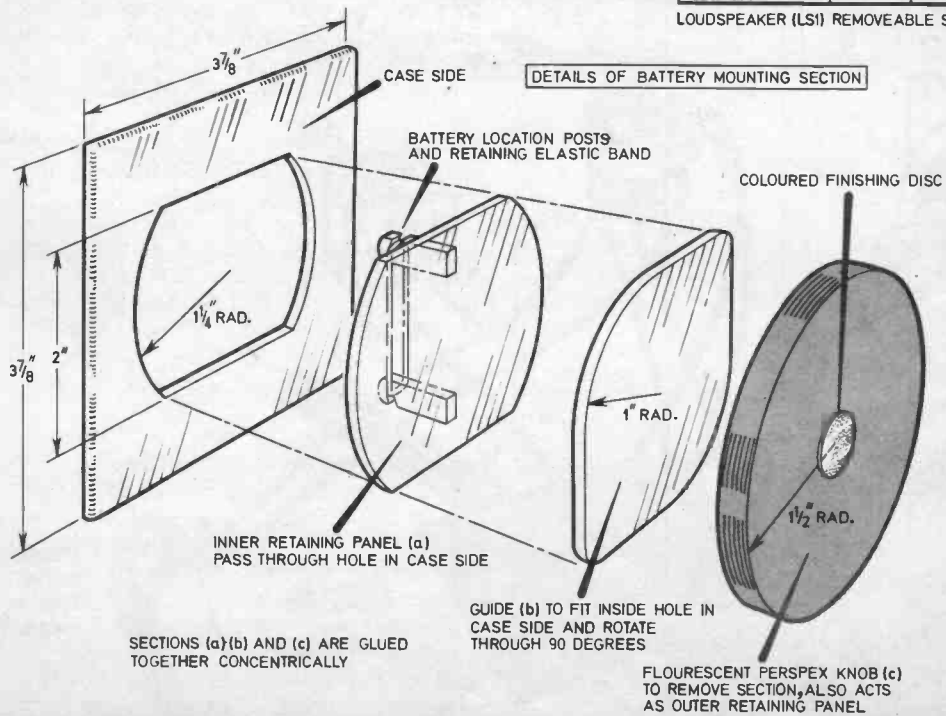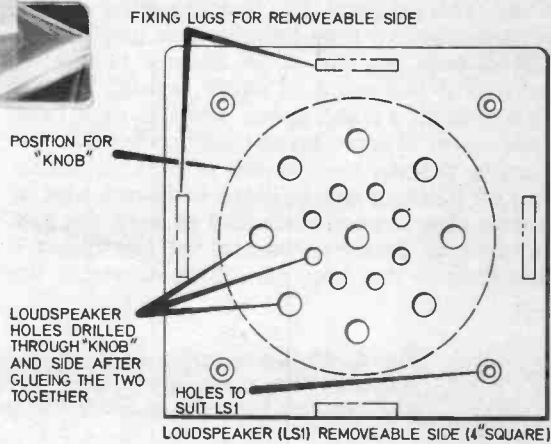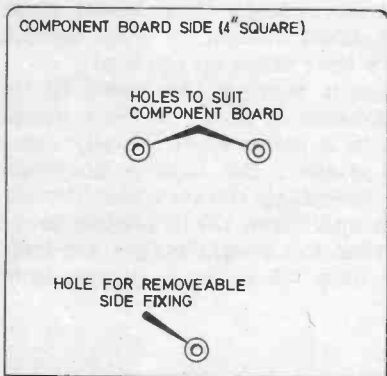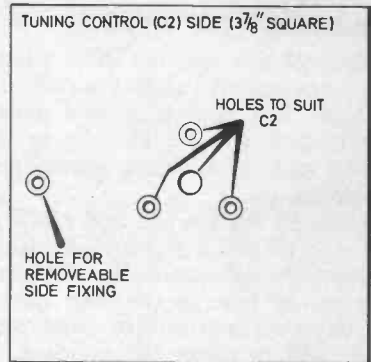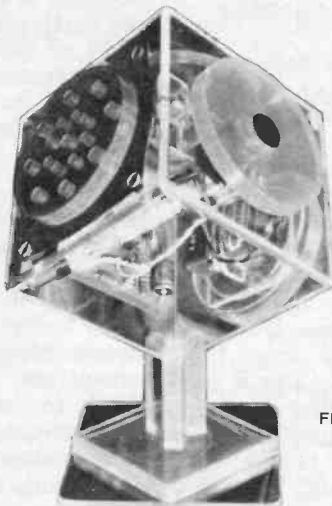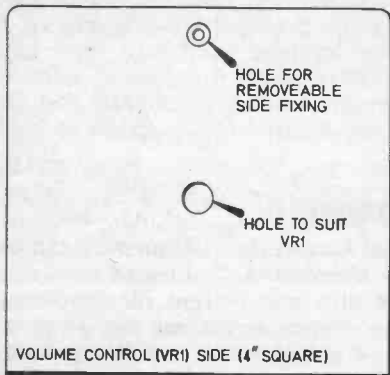

until a station is heard and revolve the aerial for maximum output. If all is well the receiver can be set aside and the cabinet constructed. If the receiver fails to operate this is probably due to a wiring fault or a damaged transistor.

CABINET

The cabinet shown in the photograph is a cube of 4 inch side made entirely from Perspex. Fig. 5. shows the basis of construction of the case which consists of four squares of $\frac{1}{8}$ inch thick perspex each having 4 inch sides and two squares of $\frac{1}{8}$ inch Perspex having $3\frac{7}{8}$ inch sides.

In the prototype a section of one side was made removable for battery replacement, drawings of the construction of this section are shown in Fig.5. The side housing the loudspeaker was also made completely removable for insertion of the receiver parts and servicing; this side is held by four countersunk 4BA screws.

All sides should be cut and filed to shape with all mounting holes cut and cleaned up before assembly. The case is glued together using chloroform or polystyrene cement as used for

Fig. 5. (opposite), The case in part form. The base and plain side are not shown. The plain side is 4in square and has one hole for the removeable side fixing.

MATERIALS: $\frac{1}{8}$ inch thick clear Perspex for all sides, sections (a) and (b), fixing lugs and lower part of base. $\frac{3}{8}$ inch thick fluorescent Perspex for knobs (4 off), upper part of base and mounting pillars (3 off).

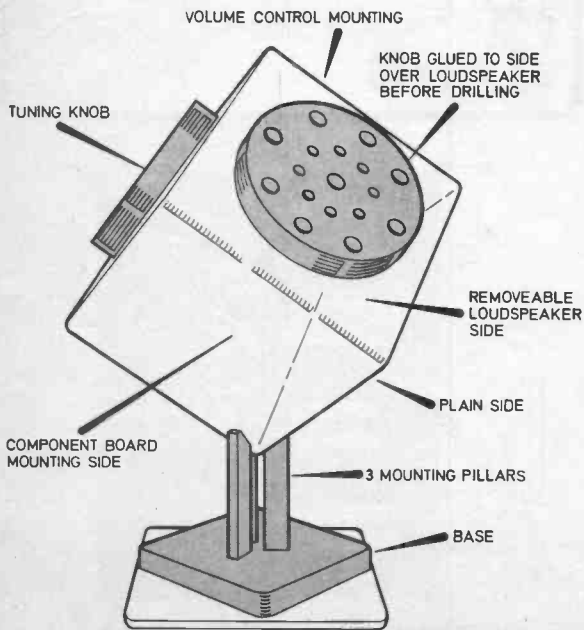


Fig. 6. The complete case.

model making. When the five fixed sides have been glued up the sixth side should be fixed with screws—the nuts can be held on the flanges using Evostick—and all corners rounded, using a file and polished with emery paper and metal polish; Solvol Autosol polish is very useful for this purpose (obtainable from motor accessory shops).

The prototype “knobs” are made of 3 inch squares of $\frac{3}{8}$ inch thick fluorescent Perspex. these were turned to form a disc on a metal turning lathe, $\frac{1}{4}$ inch holes through the centre of each disc can be used with suitable bolts to hold the material. An $\frac{1}{8}$ inch by $\frac{5}{8}$ inch diameter recess should be made in the centre of one side of one knob for the volume control nut. Four “knobs” are used, one for volume on/off, one for tuning, one stuck over the speaker with holes drilled through it and the fourth for the battery section.

The tuning knob is made a tight fit on the tuning capacitor C1 by indenting the spindle with a large pair of pliers (the cutting part is useful for this) and twisting the knob on. A similar fixing can be used for the volume control unless the spindle is made of plastic. In this case file a flat on the spindle—if it does not already have one—and glue a small “flat” (made of Perspex) in the hole, carefully file the flat on the spindle until the knob will just press tightly on to the spindle.

STAND

The stand is made from a 4 inch square of $\frac{1}{8}$ inch Perspex, a 3 inch square of fluorescent $\frac{3}{8}$ inch Perspex and three 2 inch long fluorescent Perspex pillars, $\frac{3}{8}$ inches square. The three pillars are filed at an angle at one end so that each fits against one side of the cube which is “standing” on one corner Fig. 6. Filing this angle is rather difficult but with care and patience the resulting stand will be sturdy.

When glueing the sections it is best not to polish the edges to be glued. It was also found that the edges of the fluorescent Perspex give an orange hue if not polished, but this will disappear if they are polished. The three stand pillars were polished so that their four sides look the same, but the edges of the knobs and stand were not; the front cover illustration shows the effect of this.

Once the cabinet is finished all the parts can be mounted as shown in Fig. 4. and the connecting wires cut to the correct length and soldered up. Make sure that the loudspeaker will clear the aerial, if it will not, carefully file the ends of the aerial so that it fits deeper into the case. Foam rubber pads at the ends of the aerial will prevent it moving around in the case. Small coloured discs of sticky backed fabric placed over the spindle ends will finish the knobs neatly.



The Electro Laugh

by Gerry Brown

Although originally designed as a laughter simulator, this device can also be used as an electronic bell or in any other alarm system requiring an audible output.

As the title implies, this device produces a kind of electronic laughter. At the early paper stages of the design, the device represented only quite a small challenge but as the idea progressed it was not long before it became evident that even such an ostensible simple sound such as a laugh is fairly difficult to achieve.

BASIC DESIGN

Before the device can operate at all, it must obviously have some kind of a "voice." This is provided by a simple audio oscillator of fre-

quency about 1kHz; but this must be modified in some way to make it resemble laughter. See Fig. 1.

Unfortunately, there isn't a "standard laugh" that we can model our electronic replica on, so the choice must be an average of many types.

On analysis, most laughter seems to begin at a given point in the audio spectrum, and fairly rapidly drop to a frequency about an octave or so below, rather like a football cheer in reverse. This kind of sound (musically known as a glissando) can easily be produced using the output voltage from a simple integrator driven from a low frequency square wave oscillator to vary the frequency of the voice generator. In our device this is referred to as the "reversed-cheer" generator.

Also, most laughter in addition to displaying the reversed-cheer, interrupts this characteristic in short bursts, each burst causing a sort of warbling effect on the already frequency diminishing signal. To achieve this an additional oscillator, the "giggle-generator" is employed. The "giggle-generator" constantly switches the frequency of the "voice-generator" from one fixed point in the voice spectrum to another.

Under operating conditions, the voltage from the integrator section of the "reversed-cheer" generator will be rising and falling, resulting in a corresponding rise and fall in the pitch of the voice, but if preferred, the rising portion

Approximate cost of components



2.00

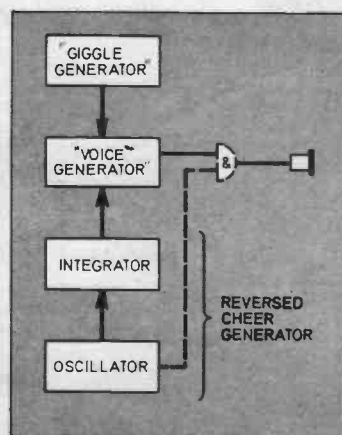


Fig. 1. Schematic diagram of the Electro Laugh. The "banking gate", shown dotted, may be connected to produce a different kind of laughter.

Components....

Resistors

R1	2.2k Ω
R2	22k Ω
R3	22k Ω
R4	2.2k Ω
R5	2.2k Ω
R6	10k Ω
R7	10k Ω
R8	2.2k Ω
R9	2.2k Ω
R10	4.7k Ω
R11	1k Ω
R12	1k Ω
R13	4.7k Ω

All $\frac{1}{4}$ W $\pm 10\%$ carbon

Capacitors

C1	100 μ F elect. 12V
C2	100 μ F elect. 12V
C3	10 μ F elect. 12V
C4	39 μ F elect. 12V
C5	250 μ F elect. 12V
C6	0.33 μ F
C7	0.15 μ F

Transistors

TR1-TR6 2N2926 (orange) Silicon npn (6 off)

Miscellaneous

- TL1 Earphone 100-250 Ω impedance
- S1 Single-pole push-to-make switch
- B1 12V battery, 2 x PP1 (6V) or equivalent, plus suitable battery clip

Miniature plastic preserves container
Veroboard: 2 $\frac{3}{8}$ x 2 $\frac{1}{2}$ inch 0.1 matrix (23 x 37 holes)

of the tone can be inhibited by employing a blanking gate to control the voice-generator. The blanking gate is shown dotted in the schematic diagram, Fig. 1.

CIRCUIT OPERATION


The Electro Laugh utilises three square wave oscillators, each employing an astable flip-flop. Apart from the circuit values which set the individual operating frequencies, circuit functions are virtually identical and only one flip-flop (multivibrator) need be described.

Consider the oscillator in the "reversed-cheer" generator circuit, Fig. 2. Upon initially switching on, we can assume that TR1 is conducting, and in this condition the collector side of C1 will be at almost ground potential. As a result C1, which will have already charged to nearly rail potential, will begin to discharge. At this time C2 will rapidly charge close to rail potential. When C1 has discharged to approximately 0.6V (i.e., the V_{be} of TR2) TR2 will start to turn on, and due to the feedback between the two halves of the circuit, a rapid transition will occur resulting in TR2 turning hard on and TR1 turning off. The process then repeats as before with C2 discharging and C1 charging, until TR1 turns on again and TR2 turns off. This will continue indefinitely, or until the circuit is switched off.

The discharge rates of C1 and C2 are essentially set by the value of R2 and R3, while the overall time constant ($1.4CR$) determines the operating frequency. The charging times for C1 and C2 are reliant on the values of R1 and R4, which in general are small enough to be ignored.

During the time that TR1 is turned off, the positive potential at its collector is free to charge capacitor C5. The potential across C5

Fig. 2. The complete circuit diagram.

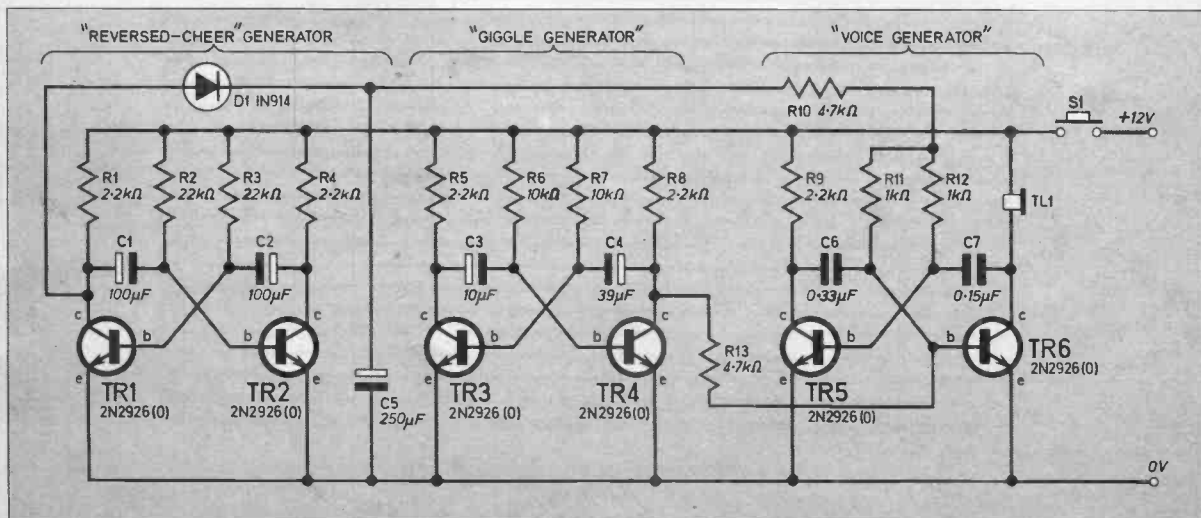

The Electro Laugh

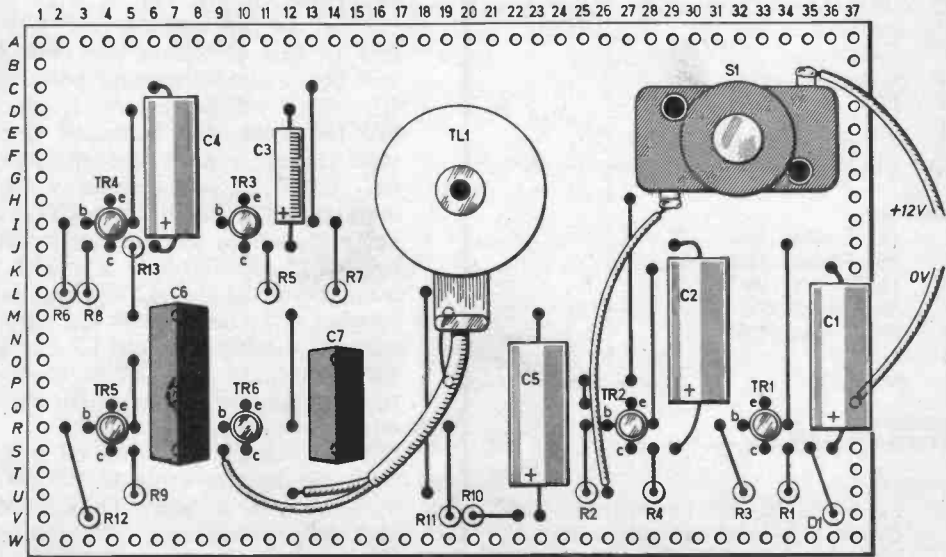


Fig. 3. The wiring of the components on the top side of the Veroboard.

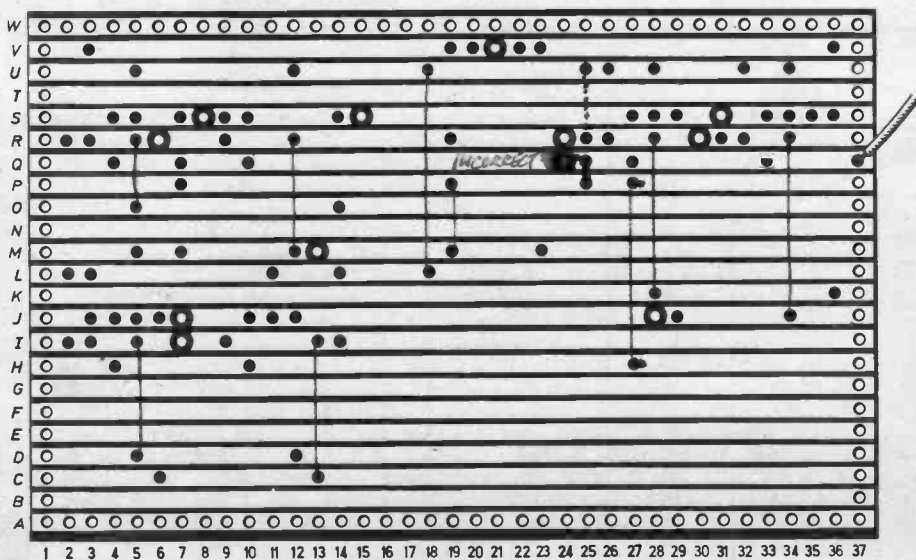


Fig. 4. The areas of copper strip to be removed.

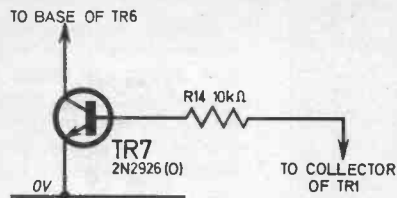


Fig. 5. The blanking gate.

thus rises towards rail potential while TR1 is in the non-conducting state. However, when it is the turn of TR1 to conduct, D1 is reverse-biased and C5 slowly discharges through R10, R11, R12, and the bases of TR5 and TR6. This process of charging and discharging C5, constantly alters the voltage points at which C6 and C7 (in the "voice-generator") begin their discharge. As a result the overall time-constant of this circuit is affected and, hence, the frequency of the output signal. Therefore, the rising (charging) potential across C5 does not result in a rising pitch.

The effect of the "giggle-generator" output is to momentarily swing the frequency of the "voice-generator" during the reversed-cheer characteristic. This is accomplished by coupling the collector of TR4, via R13, to the base of TR6.

CONSTRUCTION

The device is built on 0.1 inch matrix Vero-board which is shown in Fig. 3. During construction, all relevant breaks in the copper strips should be made prior to fitting components. It should be noted, too, that transistors

and diodes are best mounted last in order to minimise damage from overheating while other components are in the course of being soldered into position.

The switch and earphone can be fixed in position by using an impact-adhesive such as Evo-Stik. The earphone used in the prototype sports a horn which makes it into a mini-loud-speaker. This is obtained as a ready-made item from a plastic preserves container. A hole should be drilled in the base of the container to accommodate the output nozzle of the earphone. The container should then be fixed in place with an impact-adhesive.

When the device has been constructed, all wiring etc., should be checked thoroughly before finally connecting it to the battery.

BLANKING GATE

If desired, a different laughter sound may be obtained by connecting in a blanking gate as shown in Fig. 5. With this in the circuit, the voice generator is prevented from functioning, by grounding the base of TR6, whenever TR7 is turned on. In other words, only the falling (discharging) action of the integrator on the "reversed-cheer" generator will be presented to the output.

CONCLUSION

At first sight this may seem a frivolous project, but it will give many hours of fun and enjoyment to all members of the family and can later, if desired, be used as an electronic "laughing" bell. □

MEMORY STORE

Retrieval By

John Watt

"NO laddie, an ohm is *not* the place where a volt lives!" my RAF sergeant instructor said to me—something I knew already, but he had to get his little jokes in.

In point of fact, he wasn't a bad bloke (for a sergeant) and did teach me quite a lot of radio—or wireless as it seemed to be called then—and of course basic electronics and basic radio deal in much the same sort of techniques, and are just the sort of grounding that is so useful, no matter whether you are amateur or professional. With the evening classes to HNC standard that followed, I felt I had all the theoretical knowledge I needed and concentrated on practical construction thereafter.

Simultaneously, a number of friends expressed interest in audio—hi-fi they called it, but does anybody ever admit to lo-fi? (In any case, I always thought it was fidelity and infidelity). Anyway, I found myself testing and sometimes modifying what they had built. If you have such acquaintances this is a good way to start, for very often one can hear what is being done, in the absence of test equipment.

However, I can honestly say that I have never regretted spending money on test instruments and a small multirange meter, at least, should be in every constructor's kit.

Whatever you make though, should you wish to alter something, either in an attempt to improve the performance or just to get it working properly in the first place, do remember the Golden Rule—alter only *one* thing at a

time, for it is then so much easier to determine what is happening and more important, why.

Do not imagine that everybody else has a large well equipped workshop for their constructional activities, like the professionals, while you, the poor struggling amateur, have to make do with one corner of the kitchen table. Put your foot down! Insist on *all* the kitchen table! Better still, even a small bench in a shed or garage (the car can stay outside if you get your priorities right), which can thus be left overnight with the latest "EE" project on it while building proceeds, will suffice; I use a corner of my house roof space, partitioned off with insulation board for winter warmth. If you can leave a particularly awkward piece of work for a few days undisturbed, it is surprising how easy it suddenly becomes on your return to it.

REMEMBER
TO USE THE
POSTCODE



Readers Letters

Beginners Bits

Congratulations on your first issue! At last an electronics publication whose avowed philosophy is to interest and involve the beginner in this very important field of technology.

I don't know if it is your intention to start a correspondence column in your magazine, but perhaps you could advise me of the relative merits of different material and different shape soldering iron bits suitable for a beginners use. I have a soldering iron, but too large a bit for electronic purposes.

M. S. Peters
Thorne, Yorks.

Standard copper soldering iron bits are quite suitable for electronic work and most people prefer 1/8 inch or 3/16 inch chisel face types for general work. Iron coated, or various types of plated bits are available and these will last longer than the standard copper bit.

Rare Screwdriver

Not wishing to criticise your first issue, but I could not help noticing (on page 31) that a screwdriver with 3/16 inch shaft and a 4 or 6 inch blade would be rather difficult to find. This I think should be the other way round.

However, I congratulate you on this excellent magazine which I feel caters for beginners, like myself and also people more advanced in the hobby.

Wishing you the very best of luck.

C. M. Thompson
Cheltenham, Gloucs.

Contents

Your new magazine is welcome indeed to fill the need of amateur constructors. I think I express a common feeling of hope, that its contents will not be too professional, its constructional projects not too big or complex, and its news not concerned with sophisticated radar systems supplied to

Middle East Shiaks. All this should be left to big brother, *Practical Electronics*.

Regular readers of any magazine like to hear of other readers experiences, and difficulties, so failing space for readers letters why not a chatty column commenting and answering extracts from readers letters?

Is it not possible to contrive some "big" breakthrough on the advert scene? Not only are they nearly the same every month, but the same as all the other monthlies as well! This greatly reduces any inclination to take both of your magazines. I feel sure there must be immense difficulties, however—probably insurmountable.

I wish EVERYDAY ELECTRONICS lots of success.

Vincent S. Evans
Parbold, Lanc.

We hope that this page will fulfill your first requirement Advertisers please note the second!

Too Fast

I must start by apologising for criticising your first edition but as the magazine is supposed to cater for the beginner, perhaps you will bear with me, as I am just that, an absolute beginner in the field that your magazine is intended for.

I started, as suggested by the article *Component Buying and Supplying*, and ordered a catalogue for 70p, and ran into difficulty as soon as the catalogue arrived. I was unable to positively identify the components required for the *Demo Deck*.

The first snag was the perforated board as there is none listed as quoted under components required, and my local dealer could only find packets of strip in his catalogue with the matrix size quoted.

Secondly, the M.E.S panel mounting lamp holders are quoted in various sizes and require the lens colours to be stated when ordering, and this is not given in your magazine.

Finally there are no 3 3/8 inch speakers listed in the catalogue, and again my local dealer said this was an awkward size, and asked for alternatives. As I was unable to quote alternatives I asked him to order it for me. And apart from a gloomy forecast of a fortnight's delivery, he said the firm concerned were rather expensive to deal with.

Hoping this will be considered constructive.

D. Pratley
Innsworth, Gloucs.

First the bouquet: congratulations on producing a magazine filling an obvious gap. As a complete beginner I just did not know where to start. This first issue seems to fill the bill. Please keep up this high standard.

Now the brickbats: as already stated, I am a complete beginner. In your *Teach-in* you quote components for the *Demo Deck* as follows:

1 Veroboard 0.25 inch matrix (from reading advertisements are we to assume this should have been 0.15 in matrix?) Also no indication of board size (1 sq. inch or 10 sq. feet?).

2 Milliamp meter (SEW MR38P or similar). But what range? The SEW adverts quote ranges from 1mA to 10 amp.

Could you please put me right on these points and then I can order the components to construct the *Demo Deck*.

A. Bryan
Flintshire, N. Wales.

Firstly, the list published in our first issue was only a short advanced list—as you will now know, we published a comprehensive list in the Demo Deck article last month. One point that has come to light is that R. S. Components Ltd. now quote the matrix size for the board as 6.33mm instead of 0.25 inches (the board is not Veroboard). Since this board is sold in standard size (6 3/4 in x 5 1/4 in) we did not give dimensions. We quoted 1 one milliamp meter—that is a one-millamp range. You could use any small 35 ohm loudspeaker for the Demo Deck.

A two week delivery date is by no means unusual for electronic components and this is one reason we published the advanced list, however two weeks is much longer than the normal delivery time from R. S. Components Ltd who operate a same day return

DISCOUNTS UP TO

60% ON BRANDED GOODS

ALL BRAND NEW
in manufacturer's sealed cartons
GUARANTEED 12 MONTHS.

SONY · LEAK · SINCLAIR · TELETON · ARMSTRONG ·
THORENS · PHILIPS · K.E.F. · TEAC · ROGERS · PIONEER

SPECIAL OFFER £18

Garrard SP25 Mk. III
Goldring G800H
Teak plinth and tinted cover.
Ready wired for immediate use.
Please add £1.25 for post and packing.

TURNTABLES

Please add 75p for P. & P.

Garrard SP25 Mk. III	£10.25
Garrard Zero 100—Auto (New Product)	£40.95
Garrard Zero 100—Single Play (New Product)	£37.95
Garrard 2025C with Sonotone 9TAHC	£8.95
Garrard SL65B	£13.50
Garrard AP76	£19.95
Garrard 401	£27.00
BSR MP60	£36.00
Pioneer PL12AC	£36.00
Thorens TD125	£62.50
Thorens 150AB11	£42.50
Goldring GL69/2	£20.00
Goldring GL69 P2	£26.95
Goldring GL75	£27.95
Goldring GL75P	£35.95

AMPLIFIERS

Please add 50p for P. & P.

Alpha Highgate FA212	£27.50
Alpha Highgate FA300	£29.00
Alpha Highgate FA400	£33.00
Armstrong 521 (cased)	£44.95
Armstrad 8000 Mk. II	£16.95
Armstrad IC2000	£34.00
Dulci 207	£15.95
Dulci 207m	£21.00
Leak 30 Delta Range (New Product)	£51.00
Leak 70 Delta Range (New Product)	£61.00
Metrosound ST20E	£26.00
Philips R580	£18.00
Pioneer SA500	£36.00
Pioneer SA700	£45.00
Pioneer SA900	£92.00
Rogers R/brook Chassis	£35.50
Rogers R/brook Cased	£39.50
Rogers R/bourne Chassis	£44.00
Rogers R/bourne Cased	£48.50
Sansui AU101	£32.00
Sansui 555A	£59.95
Sansui AU666	£75.00
Rotel RA301	£32.75
Rotel RA601	£49.80

All prices correct at time of going to press.

GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. E.E.3 174 Pentonville Road, London, N1. Telephone 01-278 1769
Dr: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.

MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS: Please note that cheques can only be accepted together with cheque cards (not Barclay Card).

2 minutes from KING'S CROSS, EUSTON & ST. PANCRAS on main road leading to the East and West Country


Sinclair 2000 Mk. II	£22.50
Sinclair 3000	£32.50
Sinclair PRO 60/2+Z30 PZ5	£15.00
Sinclair PRO 60/2+Z30 PZ6	£17.75
Sinclair PRO 60/2+Z50	£22.95
Sinclair AFU	£4.70
Sinclair 605 (New Product)	£20.50
Goodmans Max. Amp.	£37.95
Teleton SAQ206B (New Prod)	£17.95
Wharfedale	£49.75
Sinclair IC12 integrated circuit amplifier	£1.85
Eagle TSA149 7wRMS	£24.95
Eagle TSA151 15w RMS	£34.50

CARTRIDGES

Please add 10p for P. & P.

Goldring G850	£3.75
Goldring G800	£6.50
Goldring G800E	£10.50
Goldring G800SE	£15.50
Sonotone 9TAHC Diamond	£1.75
Shure M3DM	£4.50
Shure M445/77C	£7.00
Shure M55E	£8.75
Shure M75E	£12.75
Shure V15 Type 2	£27.75
Shure M44E	£7.00
Shure M31E	£8.50
Shure M32E	£8.00
Audio Technica AT35	£12.95

PLINTHS & COVERS

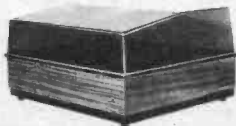

£3.20

(As illustrated)
Plus 35p post and packing
Finished in real teak veneer with tinted dust cover. Ready to use (fully assembled). Suitable for Garrard SP25; 2025TC; 3000; AT60; 2000; 2500; 3500; 5100; 1025; SL65B. Also for BSR, McDonald MP60 and others.

For AP76; AP75; SL72B; SL75; SL95B. £4 plus 35p P. & P.
Also finished in walnut to match Japanese equipment—at no extra charge.

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns. Certs.
- Radio Amateurs' Examination
- Radio Operators' Certs.
- General Certificate of Education, etc.

Now available, Colour T.V. Servicing

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 147, Intertext House, Stewarts Road, London, SW8 4UJ

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.).....

NAME..... AGE.....

(Block Capitals Please)

ADDRESS

1/72

Member of the ABCC

Accredited by the CACC

INTERNATIONAL CORRESPONDENCE SCHOOLS

RUSSIAN WORLD BEATER!

JUST ARRIVED!

The Fabulous BRAND NEW

WORLD WIDE RECEPTION
THOUSANDS OF TRANSMISSIONS AND STATIONS THE WORLD OVER!

VEF 204
8 WAVEBAND

10 TRANSISTOR PLUS 2 DIODES PORTABLE RADIO

AND NOW WITH SHIP-TO-SHORE MARINE BAND

BATTERY MODEL £13.97p
BOX POST ETC. 50p
MAINS/BATTERY ELIMINATOR £1.38p extra



WE COULDN'T EVEN MAKE THEM FOR OUR FANTASTIC PRICE!

*COMPARE ITS PERFORMANCE

with £42 RADIOS!

Important! This very latest model incorporates all the latest technological improvements and supersedes all earlier models! Yes **DESIGNED FOR WORLD WIDE RECEPTION**—it'll probably make your present radio seem like a "crystal set"! It even incorporates a special **MARINE WAVEBAND** to receive spoken communications from ship-to-shore! We're almost giving them away at only **£13.97**—a mere fraction of even today's Russian miracle price! Compare performance with **£42** radios! *Refund if not astounded! Purer and sweeter tone than ever! Wider band spread for "pin-point" station selection. The Russians have really surpassed themselves this time proving again their ability in the field of space communications. Yes, 8 separate wavebands including Standard Long, Medium and Short waves to cover the world. **PLUS special "ship-to-shore" MARINE BAND!** Thousands of different transmissions and stations at your fingertips 24 hours a day, including ships at sea, etc., and messages from all over the world—truly nothing is secret! You must hear it to believe it. Superb, sweet tone—controlled from a whisper to a roar! Push-pull output! Separate **ON/OFF volume & Treble/Bass** tone controls. Press-button dial illumination! Take it anywhere—runs economically on standard batteries or through battery eliminator from 220/240v. AC mains. Internal ferrite rod plus telescopic aerial. It's also a fabulous **CAR RADIO!** Black & Chrome case 11ins x 9ins overall approx. Made to give years of perfect service. Complete with **WRITTEN GUARANTEE**, manual with simple operating instructions & circuit diagram. **ONLY £13.97** (with mains/battery eliminator £1.38 extra). **POST 50p**. Standard batteries 88p extra. Can also be used through extension amplifier, tape recorder or public address system. Send today or call. **(SORRY—**we cannot change these new radios for any earlier model already purchased!)

THIS FANTASTIC OFFER ONLY FROM US! SAVE £20.25 NOW!

BATTERY/MAINS AC/DC

Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER



This equipment's got EVERYTHING!

WITH REMOTE CONTROL MICROPHONE

OUR PRICE £23.75 CARR. ETC. 35p
RECOMMENDED RETAIL PRICE £44

FANTASTIC (even by our standards) Brand new—the latest sensation in the world of sound! First class makers! Not only a fabulous **V.H.F. AM/FM Radio AND Cassette Tape Recorder and Player** combined, but it also runs off standard batteries or mains (simply plug in the 220/240v. A.C. line cord). Now, you can record and play back anything, anywhere! You can even tape direct from the Radio as you Listen! **RECOMMENDED RETAIL PRICE GENUINELY £44 YET WE OFFER AT ALMOST HALF PRICE!** Just look at these wonderful features:—★Press-button Keyboard Keyboard Control panel! ★New "pop-up" Cassette ejection system! ★"MAGIC EYE" Visual Battery check/recording level indicator! ★Separate **ON/OFF**, volume and **HI-LO** volume tone controls! ★Heavy duty built-in speaker! ★Earphone (for personal listening or "Monitoring") and extension speaker socket! ★Remote control microphone! ★Built-in swivel telescopic extension aerial (24 inches approx!) Magnificently made case, size 11ins x 9ins x 3ins overall approx., with carry handle. (DESIGNS VARY SLIGHTLY.) Takes standard 30, 60, 90 or 120 minute Philips Cassette Tapes obtainable everywhere. But wait, the amazing built-in full circuit **V.H.F. AM/FM** Radio gives you superb clarity of tone and incredible station selection—Unique rotating Station Selector Dial—get all local city & regional stations in every part of the country plus **B.B.C. National VHF**. Picks up dozens of foreign stations and short mobile transmissions. Also fabulous in your car. You could pay **££££**'s more for a Car Radio or Car Cassette Player **ALONE!** **OUR FANTASTIC PRICE, ONLY £23.75 CARR. ETC. 35p**. Complete with simple instructions, personal listening earphone, remote control microphone with on/off switch and microphone stand, with written guarantee. **BONUS OFFER—Standard Batteries and Cassette Tape 25p extra. Refund 7pcc.**

LATEST SHIPMENT JUST ARRIVED!

ONLY FROM US!

BRAND NEW RUSSIAN WORLD BEATER.

WE COULDN'T EVEN MAKE THEM FOR THIS PRICE!

6 WAVEBAND 10 TRANSISTOR PORTABLE RADIO

WORLD WIDE RECEPTION
THOUSANDS OF TRANSMISSIONS AND STATIONS THE WORLD OVER!

£9.97p BOX POST ETC. 43p



***COMPARE ITS PERFORMANCE with £34 RADIOS!**

NOT JUST A RADIO—BUT TECHNOLOGICAL MAGIC!
THE LATEST MODEL, SUPERSEDING ALL PREVIOUS MODELS:—FANTASTIC BRAND NEW RUSSIAN "MERIDIAN" 6-WAVEBAND PORTABLE RADIO DESIGNED FOR WORLD WIDE RECEPTION. Only put into production after incorporation of every conceivable possible up-to-date technological improvement had been carefully considered and thoroughly examined. So advanced it will probably make your present radio seem like a "crystal set"! It's far better than any 6 wave radio even they have produced. Finest value we've ever offered! We're almost giving them away at **£9.97**—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with that of **£34** radios! ★Instant refund if you are not astounded! Purer and sweeter tone than ever! Much wider band spread than hitherto for "pin-point" station selection. Once again the Russians have proved their fantastic ability in electronics—brilliantly reflecting their advanced micro-circuitry techniques in the field of space-ship and satellite communications. Yes, 8 separate wavebands, including Standard Long, Medium and Short Waves to cover world! Unique side control waveband selection unit gives incredible ease of station tuning! Thousands of different transmissions and stations at your fingertips 24 hours a day, even ships at sea and messages from all over world—nothing is secret! The radio enthusiast has the world in his hand! Superb, sweet tone—controlled from a whisper to a roar. Push-pull output! Separate **ON/OFF** volume & Treble/Bass tone controls! Take it anywhere—runs economically on standard batteries. Internal ferrite rod aerial plus built-in telescopic aerial extending to full 33in. length. It's also a fabulous **CAR RADIO**—any speed, requires no additional aerial. **UNIQUE!** Elegant Black, White and Chrome finish case. **SIZE 10 1/2" x 8" x 3 1/2"** overall approx. Magnificently designed, made to give years of perfect service. With **WRITTEN GUARANTEE**, manual with simple operating instructions and circuit diagram. **ONLY £9.97, POST ETC. 43p**. Standard batteries 25p extra. Can also be used through extension amplifier tape recorder or public address.

BRAND NEW! SAVE £13.98 NOW! FIRST CLASS MAKER'S

Cassette TAPE RECORDER and PLAYER



RECOMMENDED LIST PRICE £26.97p
OUR PRICE £12.99p
POST ETC. 50p

WITH REMOTE CONTROL MICROPHONE

MAKE NO MISTAKE—this is the **EXPENSIVE** model with "PIANO KEYBOARD" CONTROL PANEL and SPECIAL RECORDING LEVEL! **SAVE £13.98!** Due to price we cannot mention famous makers name—but rest assured you're getting one of the **BEST** Our latest cassette model—no fiddling with awkward tape and reels, just "slap in" a cassette and off you go! (takes 30, 60 and 90-minute standard Philips Cassette tapes obtainable everywhere). Amazing performance ensures perfect tapings and superb reproduction. Remote control microphone. Separate volume control! Rapid rewind! Beautiful tone from a whisper to a roar! Completely self-contained—record anywhere. Separate jacks for remote control microphone, etc. Size 9" x 4 1/2" x 2 1/2" overall approx. Case design can vary slightly. With carry handle. With **WRITTEN G'TEE** and instructions. **Only £12.99, post 30p.** **ALSO AVAILABLE: SPECIAL BATTERY MAINS AC/DC MODEL**, ready to plug in. **£3.50 extra** if required. Refund 7pcc. **BONUS** one per customer. Cassette tape, set of Standard batteries and microphone stand all for **51p extra** if required.

SHOPERTUNITIES LTD. SL

Dept. EE/F/2, 164 UKBRIDGE RD, (facing Shepherds Bush Green), LONDON W12 8AQ. (Thurs. 1, Fri. 7). Also 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thursdays 7 p.m.). **BOTH STORES OPEN MONDAY-SATURDAY FROM 9 a.m.-6 p.m.**

service to the trade. Please note that R. S. Components Ltd will NOT supply direct to private individuals.

Black Box

I am writing to congratulate you on your initiative in starting the new magazine EVERYDAY ELECTRONICS. I am particularly impressed by the way you give information which will be of interest and help to beginners in their future studies of electronics, as well as details regarding the construction of various projects.

If I may make a suggestion regarding the article on the record player by Mr. E. Pusey, I think that it would have been more helpful to beginners if the integrated circuit had not been treated as a mysterious black box.

Whilst it may not have been necessary to give the full circuit diagram, I think it would have been better if a block diagram of the amplifiers used in this integrated circuit had been given and shown connected to the pins. In this way, even if only input and output connections to individual amplifiers were shown, I am sure this would have been more helpful to the beginner, and by showing how basically simple they are, possibly encourage them to experiment further with integrated circuits.

However, I hope you will not take these suggestions amiss, as I think you have started a first class magazine which is ideal for beginners in electronics. I am sure that many people who thought this interesting hobby far beyond them will now realise that if approached systematically, it is just as simple as any other hobby—and more fun!

Cyril Bogod B.A.E.C.
Penarth, Glam.

Colour Sequence

I am writing to you about an article in EVERYDAY ELECTRONICS November, 1971.

The article is the Snap Sequence Indicator. It is shown that transistors 2N2926 are needed but when I looked up this component it was available in three different colours, green, yellow, and orange.

Could you possibly tell me which one I should use.

N. Sherwood
Scunthorpe, Lincs.

See Shop Talk.

Everyday Electronics, January 1972

Partial Control

I have just completed the construction of the Windscreen Wiper Control in accordance with the instructions contained in your first issue. Unfortunately the unit only works for half of the travel of the variable resistor.

The present variation in relay contact closing periods is from a minimum of seven seconds to a maximum of 20 seconds.

All the components used were as recommended with the exception of C4 for which the preferred value of 0.47 μ F was substituted.

I should be obliged for your suggestions as to the possible cause of the units malfunction.

R. Bacon
West Heath, Birmingham.

We have tried to simulate your fault on our prototype and we suspect that it is due to transistor leakage and RLA not being quite sensitive enough. Reduce R3 to 22 kilohms—this will slightly affect the timing range, mainly at the lower end, but should cure the fault.

Starting Again

I have recently purchased the first edition of EVERYDAY ELECTRONICS and on going through the pages I must admit the compilation is excellent—especially the enlarged diagrams.

It takes me back to the old catswhisker and crystal days but since the all-mains sets I have lost touch with components; electronics seems to have turned a complete cycle, back again to dry batteries.

Your *Beginners Brief* and *Teach-In* are very useful as it will keep me in touch with new parts and also help me pick up from where I left off.

Wishing you every success.

P. J. Brown
London, N.W.6.

Scottish Credit

Mr. A. Sproxtion in his article on component buying mentions the bank credit gyroscheme. On inquiring at my own local bank I find that the issuing of forms and the writing of the order on the back of the said form is not known nor is countenanced. Perhaps the system as described by Mr. Sproxtion applies only to England—or could Mr. Sproxtion comment in his next article.

J. M. Neil
Lanarkshire.

I am sure you have been wrongly informed. We frequently receive orders written on the back of credit transfer forms issued by Scottish banks. In fact, Scottish banks are listed in a brochure "Bank Money Transfer Services" available from any bank.—Alan Sproxtion.

Six Volt Cars

Whilst I must congratulate you on your first issue of EVERYDAY ELECTRONICS, I am disappointed that like many other practical journals, your projects for car owners are ignoring the many like myself who still have a 6 volt battery. May I beg therefore that you either give suitably modified circuits to operate from a 6 volt supply or alternatively a circuit for a 6 to 12 volt d.c. convertor.

This could perhaps have adequate output current to operate the Windscreen Wiper Control already featured plus a transistorised ignition system and tachometer which I hope you will also feature in due course.

One other item I personally would like to see covered, is a vacuum tube voltmeter, or its transistorised equivalent. This would be extremely useful for checking constructed items and general servicing.

R. T. Edwards
Herts.

Point taken; we will be looking at the needs of the 6V system, and some future projects may be aimed at the motorist whose car has a 6V supply.

Ruminations

continued from page 138

master. My attitude is quite illogical, I know; I accept, with gratitude, the thermostats and time switches that control the heating of my house and of my hot water, also the other automatic controls, of various kinds, in my home and car. Why should I resent the seat belt "watchdog"? Perhaps, because I believe that the human brain, combined with its encompassing body, forms the most wonderful, the most sophisticated, computer and control system that could ever be imagined. Electronic aids can be a great help to us, but must we surrender our responsibilities to them?

COMPONENT BUYING & SUPPLYING

No. 3 Contributors

Final article of a series

by Alan Sproston, Home Radio (Components) Ltd.

TRUST the editor will forgive me if I first go back in time, . . . since no writing on constructional articles would be complete without a reference to the one and only F. J. Camm. He was editor of innumerable publications, ranging from *Cycling* to *Movie Making* and including, of course, *Practical Wireless*. (I wonder by the way if readers know that F.J.'s brother Sir Sydney Camm designed the famous Hawker Hurricane, which shared honours with the Spitfire in the Battle of Britain!)



. . . he would find some valve or other at the bottom of his junk box

All the same, F.J.'s constructional articles used to drive us poor component suppliers crazy. He would find some valve or other at the bottom of his junk box and design a brilliant constructional article around it. The poor reader would build it carefully and then come to us to purchase the vital valve. We would listen to the customer with incredulity and say "But Sir—that valve was obsolete ten years ago!"

Another thing, F.J. would never use preferred values (probably there were none in his junk box)

and it was quite useless for us to try and tell a customer that a 500 ohm resistor was unobtainable but that a 470 ohm resistor would do the job equally well.

Better Today

The situation is infinitely better today and writers of constructional articles are only too willing to check with us, the suppliers, that the items they wish to specify are available; and we for our part are only too pleased to assist them.

Even so projects sometimes go astray through no one's fault, and I call to mind two recent ones. One called for a "Maka Switch", and the other some Electroniques coils, and in each case the appearance of the articles coincided with the decision of the makers to cease making the required items. We have, as I mentioned in my previous article managed to resurrect the Maka Switch Kits and I'm even hopeful that we may eventually be able to put back the Electronique coils. I think one can say, in these two instances, that no one was to blame and when you consider the large number of such articles published in a year the record is a good one.

Alternatives, Tolerances

I think one way designers could help us and the customers is to indicate where alternatives can safely be used and to give a clear indication of maximum tolerances that can be allowed, because writers' statements are held in such reverence by the customers (and we don't quarrel with this, it is their right) that it is no use our suggesting that they could use a 5 per cent resistor instead of a 10 per cent—"Mr. X of EVERYDAY ELECTRONICS says 10 per cent and therefore 10 per cent it must be!" I think, for example, electrolytic



. . . I trust the editor will forgive me if I just go back in time

capacitors represent a field where a wider choice could be offered, especially when you remember the tolerances are around minus 30 per cent to plus 70 per cent so instead of saying one must use 32 microfarad rated at 10 volts, say a capacitor of between 25 to 100 microfarads with a rating of 10-100 volts may be used provided the physical size will allow it to be fitted.



. . . provided the physical size will allow it to be fitted

Again, where speakers are specified (and here I exclude apparatus of either the high power or high fidelity class): is it really all that critical whether the unit employed is 3 ohm, 7½ ohm or 15 ohm? I personally doubt it, again provided the physical size is right, but how much easier for the customer and in turn for us if the recommended speaker is specified as 3½ inch diameter, impedance 3-15 ohm!

Advance Notice

I did suggest several years ago that the magazines might tell us in advance what articles were going to be published and give us a list of the parts required, but they pointed out (quite rightly) that they could not possibly circularise

The components you want for EE designs plus good service, prompt delivery & attractive discounts

ELECTROVALUE

Electronic Component Specialists


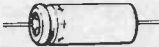
THIS MONTH'S SELECTION OF POPULAR ITEMS FROM THE ELECTROVALUE CATALOGUE

TRANSISTORS

No.	Type	Purpose	Price
2N697	SE. NPN	General	18p
2N1304	Ger. NPN	"	26p
2N1805	NPN	"	26p
2N2646	Sil. UJT	Oscillator, SCR driver	47p
2N2924	NPN	Small sig. amp	11p
2N3055	NPN	High power	60p
2N3702	PNP	Low power	13p
2N3704	NPN	Low power	18p
AC128	Ger. PNP	Small sig./driver	20p
AC128	NPN	Low power	20p
AD149	FNP	High power	58p
AC176	NPN	Low power	18p
AD161	NPN	Med. power	33p
AD182	PNP	Med. power	36p
BC108	Sil. NPN	Small signal	11p
BC109	NPN	Low noise	12p
BC188	NPN	Small signal	10p
BC189	NPN	Low noise	11p
BF194	NPN	RF amp.	14p
BFY51	NPN	Med. current	20p
OA90	Ger. diode	RF detector	6p
OA91	"	General	5p
SD1	"	Silicon Rectifier 1 amp	10p
W02	"	Silicon bridge 1 amp	40p

(Sil. = Silicon. Ger. = Germanium)

CAPACITORS

Non-polarised		Electrolytic	
			
		1mF 40V	6p
		5mF 64V	6p
		10mF 64V	6p
		20mF 64V	6p
		25mF 25V	6p
		50mF 25V	6p
		80mF 25V	6p
		100mF 25V	7p
		220mF 25V	10p
		470mF 25V	12p
		1000mF 25V	20p
		2000mF 25V	30p
		5000mF 25V	62p
Polystyrene			
10pF	3p		
22pF	3p		
100pF	3p		
220pF	3p		
470pF	3p		
1000pF	3p		
2200pF	3p		
4700pF	4p		

Polyester M K T		Many other higher and lower ratings will be found in the catalogue.
0.01mF	5p	
0.02mF	5p	
0.047mF	6p	
0.1mF	6p	
0.22mF	6p	
0.47mF	10p	
1mF	14p	

RESISTORS

¼ watt and ½ watt. all at 1p each in the following values (in ohms) :-

10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and all values in this series up to 10 Megohms.

Power Resistors

3 watts—7p each; 7 watts—9p each.

Values as for ¼ watt series, but up to 10 Kohms only.

Many other types and values available.

Full details in catalogue.

VEROBOARD

The universal circuit building board

Unclad, 0.1" matrix

2" x 3.75" 10p

2.5" x 3.75" 15p

5" x 3.75" 25p



Copperclad Veroboard also in stock in all standard sizes and matrices; also edge connectors, pins, etc.

PEAK SOUND ENGLEFIELD 840

Brilliantly designed hi-fi amplifier with facility to take add-in stereo FM tuner. Superb performance. 20+20 watts RMS into 8 ohm speakers. As advertised £49.50. Brand new, and guaranteed in maker's carton

£33.50

(+75p carr in U.K.)

VOLUME CONTROLS, ETC.

Very wide ranges carried including the following popular types :-

4.7Kohms, 10Kohms, 22 Kohms, 47, 100, 220, 470 Kohms; 1 Megohm, 2.2 Megohms.

Log or linear tracking

MONO 12p each; STEREO (matched tracks) 42p

Any type with double pole mains switch—12p extra



STEREO BALANCE CONTROLS

Log/Antilog, 10K, 47K, 1M
Dual antilog 10K only.

MAIN LINE AMPLIFIERS

70 watt power amplifier in module form ready to build into any system. With full instructions.

Amplifier module net £12.60

Power supply kit net £6.00

Matching pre-amplifier kit (for magnetic or ceramic pick-up) net £3.30

Note—All the above prices are for mono.

FOR STEREO for building into your own cabinet. Two amplifier modules and pre-amp kits are required with matched controls plus one power supply kit, nett price £38.40

OVERSEAS CUSTOMERS WELCOME

COMPONENTS DISCOUNTS

allowed on all items other than those at net prices.

10% on orders for £5 or more

15% on orders for £15 or more

POSTAGE & PACKING FREE on orders for £2.00 or more. Please add 10p if under.

Overseas orders welcomed. Prices subject to alteration without prior notice.

To ELECTROVALUE, ENGLEFIELD GREEN, EGHAM, SURREY

Please send a Goods to value of £..... as detailed on sheet attached, plus FREE copy of catalogue.

b Copy of catalogue. (strike out item which does not apply)

NAME

ADDRESS

Enclosed please find £.....cash/cheque/money order.

EE. 3


ELECTROVALUE

28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY,

Telephone: Egham 5533 & 4757 (STD 0784-3)

Hours 9-5.30: Sat. 1.0 p.m. Telex: 264475

R.C.S. PORTABLE PLAYER CABINET

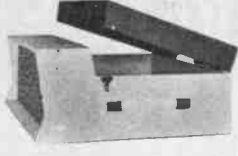

Really smart appearance with space for R.C.S. Amplifiers and most modern autochangers. Size 13 x 15 x 8in. Chrome fittings. Carrying handle. Two-tone resin covered. Red/Grey or Mottled Blue and Grey or Wood Grain effect. £4 Post 25p.

BSR C.109 SUPERSLIM STEREO AND MONO

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250V. Size 13 1/2 x 11 1/2 in. Above motor board 3 1/2 in. below motor board 2 1/2 in. with STEREO and MONO XTAL £7.75 Post 25p.



GARRARD SINGLE PLAY TA MK II Ideal £10

Discotheque or Hi-Fi. Stereo/Mono. GARRARD PLAYERS with Sonotone PT4 Cartridges, Stereo Diamond and Mono Sapphire. SP25 Mk III £12. Model 3500 Stereo and Mono Autochanger £14. Post 25p.

RCS DE-LUXE 3 WATT AMPLIFIER. Ready made with 2-stage triode pentode valve, 3 watts output. Tone and volume controls. Isolated mains transformer, knobs, loudspeaker valves ECL82, EZ90. Response 50-12,000 cps. Sensitivity 200mV. Post 25p. £4

R.C.S. TEAKWOOD BASE. Ready cut out for mounting (State player make and model) £2-75

R.C.S. PLASTIC COVERS FOR ABOVE BASE. £2-75

EMU PICK-UP ARM with mono xtal and stylus £1.95. HI-FI PICK-UP CARTRIDGES. Diamond Stereo/Mono. GP4 £2-50; GP94 £2-50; GP83 £2-00; Mono GP91 £1-50; GC8 £1-25; AC08 L.P. only 50p.

E.M.I. WOOFER AND TWEETER KIT £5-75 Post 25p

Comprising a fine example of a Woofer 10 1/2 x 6 1/2 in. with a massive Ceramic Magnet, 4oz., Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2 in. square has a special light-weight paper cone and magnet flux 10,000 lines. Impedance Standard 8 ohms. Maximum Power 12 watts. Useful Response 35 to 18,000 cps. Base Resistance 45 cps.

WEYRAD P50-TRANSISTOR COILS

RA2W Ferrite Aerial. 65p Spare Cores 3p. Osc. P50/1A/C 30p Driver Trans. LEDT4 3p. I.F. P50/2CC 470 kc/s. 33p Printed Circuit, PCA1. 50p. 3rd I.F. P50/3CC 33p J.B. Tuning Gang. 85p. P51/1 or P51/2 33p Weyrad Booklet 10p. P50/3 33p OPT 35p. Mullard Ferrite Rod 8 x 1/4 in. 20p. 8 x 1/4 in. 25p.

VOLUME CONTROLS

Long spindles. Midget Size 9 K ohms to 2 Meg. LOG or LN. 1/5 15p. DP. 25p. STEREO LIS 55p. D.P. 75p. Edge 5K. S.P. Transistor 25p. WIRE-WOUND 3-WATT POTS. Small type with small knob. Values 10 K to 30 K. Carbon 30 K to 2 meg. 25p. WIRE-WOUND 3-WATT STANDARD-SIZE POTS. LONG SPINDLE. 40p. 10 OHMS to 100 K.

VEROBOARD 015 MATRIX

2 1/2 x 5 in. 28p. 2 1/2 x 3 in. 17p. 3 1/2 x 3 in. 28p. 3 1/2 x 5 in. 30p. EDGE CONNECTORS 16 way 25p; 24 way 38p. PINS 36 per packet 81p. FACE CUTTERS 38p. S.R.B.P. Board 015 MATRIX 2 1/2 in. wide 9p per lin. 3 1/2 in. wide 4p per lin. 5 in. wide 5p per lin. (up to 17 in.). S.R.B.P. undrilled 1/4 in. Board 10 x 8 in. 15p. BLANK ALUMINIUM CHASSIS 18 s.w.g. 9 in. sides. 7 x 4 in. 45p; 9 x 7 in. 60p; 11 x 7 in. 70p; 13 x 9 in. 90p; 14 x 11 in. 95p; 15 x 14 in. 99p; 11 x 3 in. 50p. ALUMINIUM PANELS 18 s.w.g. 6 x 4 in. 9p; 8 x 8 in. 15p; 14 x 3 in. 16p; 10 x 7 in. 19p; 12 x 5 in. 20p; 12 x 8 in. 28p; 16 x 6 in. 28p; 14 x 9 in. 34p; 12 x 12 in. 40p. 1 1/2 inch DIAMETER WAVE-CHANGE SWITCHES 25p. 2p. 2-way, or 3p. 8-way or 3p. 4-way 25p each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way 25p. 1 inch DIAMETER Wavechange "MAKITS" 1 p. 12-way, 8p. 8-way, 3p. 4-way, 4p. 3-way, 6p. 2-way, 1 waler 60p, 2 waler 90p. Extra walers up to six 80p each. TOGGLE SWITCHES 14p; dp. 18p; dp. dt. 23p.

"THE INSTANT" BULK TAP ERASER & HEAD DEMAGNETISER

200/250V. A.C. £2-35 Post 25p

HI-FI STOCKISTS. RETURN OF POST DESPATCH.

RADIO COMPONENT SPECIALISTS

List 5p. Written guarantee with every purchase. (Export: Remit cash and extra postage.)

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zenor Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer Input 200/240V. A.C. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V. DC at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. £2 POST FREE Details S.A.E.

GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar. Can be used with Battery 9-12V or H.T. 200-300V. D.C. operation. Size 1 1/2 x 1 1/2 x 1". Response 25 cps. to 25 Kc/s. 26db gain. For use with valve or transistor equipment. Full instructions supplied. Brand new. Guaranteed. Details S.A.E. 90p Post 10p

NEW TUBULAR ELECTROLYTICS

2/350V .. 14p	250/25V .. 14p	18-18/500V .. 55p
4/350V .. 14p	500/25V .. 35p	50+50/350V .. 55p
8/450V .. 14p	1000/25V .. 20p	60+100/350V .. 38p
16/450V .. 14p	1000/50V .. 47p	32+32/250V .. 18p
32/450V .. 20p	8+8/450V .. 18p	32+32/450V .. 33p
25/25V .. 10p	8+16/450V .. 20p	350+50/325V .. 50p
50/50V .. 10p	18+16/450V .. 25p	32+32+32/350V .. 43p
100/25V .. 10p	32+32/350V .. 25p	100+50+50/350V .. 48p

SUB-MIN. ELECTROLYTICS 1. 2. 4. 5. 8. 16. 25. 30. 50. 100. 200mF 15V 10p; 500mF 15V 18p; 2000mF 25V 42p. CERAMIC 1pF to 0.01 mF. 4p. Silver Mica 2 to 5000pF. 4p. PAPER 350V-01 4p. 0.5 13p; 1mF 15V; 2mF 150V 15p. 500V-001 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p. SILVER MICA. Close tolerance 1%. 2-2-500pF 8p; 500-2-200 pF 10p; 2-700-5-800pF 20p; 8-800pF-0.01, mid 30p; each. TWIN GANG. 40-0 205p; 179pF, 65p; Slow motion drive 385+385 with 25+25pF, 50p. 500pF; Slow motion, standard 45p; small 3-gang 500pF £1.60.

SHORT WAVE. SINGLE. 10pF 30p; 25pF 55p; 50pF 65p.

CHROME TELESCOPIC AERIAL, swivel base, 23in. 20p. TUNING. Solid dielectric. 100pF. 500pF. 35p each. TRIMMERS. Compression 30, 50, 70pF, 5p; 100pF, 150pF, 8p; 250pF, 10p; 500pF, 10p; 750pF, 10p; 1250pF, 10p. SILICON REC. 40-LUCAS CDE500 Bridge 70V 5 amp £1 RECTIFIERS CONTACT COOLED 1 wave 60mA 38p; 55mA 48p. SILICON BYZ13 30p; BY100 30p; BY127 30p. EX-GOVERNMENT TRANSISTORS 250V AC/DC Red or Amber 20p. RESISTORS 1/4 W. 1 W. 20p. 1/2 W. 20p. 10 ohms to 10 meg. HIGH STABILITY. 1 W. 2% 10 ohms to 1 meg. 10p. Ditto 5% Preferred values 10 ohms to 10 meg. 4p. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K, 10p each; 2 1/2 watt, 1 ohm to 2 ohms 10p

PHILIPS TRANSISTOR FM STEREO MULTIPLEX DECODER.

As used in LEAK Troughline Tuner. Brand New. Pre-aligned with 9 semi-conductors. 24V. DC at 8mA. Complete with circuit and component details. POST £4 FREE

MAINS TRANSFORMERS ALL POST 25p each

250-0-250 80 mA. 6.3 v. 4 amp. £1.40
250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £2.00
350-0-350 90 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £2.00
300-0-300 v. 120 mA. 6.3 v. 3 a. CT.; 6.3 v. 2 a. £2.50
MINIATURE 200 v. 200 mA. 6.3 v. 1 a. 2 1/2 x 2 1/2 in. 75p
MIDGET 220 v. 45 mA. 6.3 v. 2 a. 2 1/2 x 2 1/2 in. 90p
P.E. AURORA TRANS. 12 + 12v. 500mA £1.50
MINI-MAINS 20v, 100mA. 1 1/2 x 1 1/2 in. 50p
HEATER TRANS. 6.3v. 3 a. 80p
Ditto tapped sec. 1 p., 2, 3, 4, 6.3 v. 1 amp. 80p
GENERAL PURPOSE LOW VOLTAGE. Tapped Outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. £2.00
1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60. £2.00
2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60. £3.00
AUTO TRANSFORMERS 115v. to 230v. or 230v. to 115v. Input/Output. 150w. £2.00; 500w. 25; 1000w. 42.
CHARGER TRANSFORMER. Input 200/240V for 6 or 12v., 11 amp. £1.20; 2 amp. £1.50; 4 amp. £2.00.
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12 v. outputs. 1 amp. 40p; 2 amp. 55p; 4 amp. 85p. All transformers Postage 25p extra.

E.M.I. 1 1/2 x 8in. LOUDSPEAKERS

With twin tweeters and crossover, 10 watt. £4
State 3 or 8 or 15 ohm. (As Illustrated) Post 15p
With flared tweeter cone and ceramic magnet, 10 watts. £2-25
Flare 10,000 gauss. £2-25
State 3 or 8 or 15 ohm. Post 15p
Recommended Teak Cabinet Size 16 x 10 x 9 in. Post 25p £5

LOW MINI-MODULE £3-25 LOUSPEAKER KIT

Post 25p
Triple speaker system combining on ready cut baffle. 4 in. chipboard 16 in. x 8 in. Separate Bass, Middle and Treble loudspeakers and crossover condenser. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 15 ohm. TEAK VENEERED BOOKSHELF ENCLOSURE. 18 x 10 x 9 in. Modern design with 25p
futed wood front. Highly recommended. £5 Post 25p

ALL MODELS "BAKER SPEAKERS" IN STOCK

BAKER 12in. MAJOR £9



30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell's. Bass resonance 40 c.p.s. Rated 20 watts. Voice coils 3 or 8 or 15 ohms. Post free
Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £11-50

BAKER "BIG-SOUND" SPEAKERS

'Group 25' 12 inch £7
25 watt 3 or 8 or 15 ohm
'Group 35' 12 inch £9
35 watt 3 or 8 or 15 ohm
'Group 50' 15 inch £19
50 watt 8 or 15 ohm
TEAK HI-FI SPEAKER CABINETS. Fluted wood front For 12in. dia. speaker 20 x 13 x 9in. £9. Post 25p For 13 x 8in. speaker 16 x 10 x 9in. £5. Post 25p For 10 x 6in. speaker 16 x 8 x 6in. £4. Post 25p LOUSPEAKER CABINET WADDING 18in. wide, 15p ft.

GOODMANS HI-FI WOOFER

8 ohm, 10 watt. Large ceramic magnet. Special Cambria cones surround P.A. Columns. Hi-Fi Enclosures Systems, etc. £4

ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps. to 18,000 cps. Size 3 1/2 x 3 1/2 in. Deep. Rating 10 watts. 3 ohm or 15 ohm models. £1-90 Post 10p

Horn Tweeters 2-16kc/s, 10W 8 ohm or 15 ohm £1-50. De Luxe Horn Tweeters 2-19 Kc/s, 15W, 8 ohm £3. TWO-WAY 300cps CROSSOVERS 3 or 8 or 15 ohm 95p. SPECIAL OFFER! 80 ohm, 2 1/2 in. dia.; 35 ohm, 2 1/2 in.; 3in 25 ohm, 2 1/2 in. dia.; 3in. dia.; 8 x 4 in.; 8 x 5 in. £1 EACH. 15 ohm, 3 1/2 in. dia.; 7 x 4 in.; 8 x 5 in. TYPE 8 ohm, 6 x 4 in.; 3 ohm, 2 1/2 in. 3in. 5in. 5 x 3in. 7 x 4 in. LOUSPEAKERS F.M. 3 OHMS. 6 1/2 in. £11.10; 8 x 5 in. £11.25; 8 x 2 1/2 in. 90p; 8 1/2 in. £1.75; 10 x 6 in. £2.50. 5in. WOOFER 8 watts max. 20-10,000 cps. 8 or 15 ohm. £1-80. ELAC 10in. 10W. De Luxe Ceramic, 8 ohm. £4. RICHARD ALLAN TWIN CONE LOUSPEAKERS. 8in. dia. 4 watt; 10in. dia. 5 watt; 12in. dia. 6 watt 3 or 8 or 15 ohm models £1.95 each. Post 15p. OUTPUT TRANS. EL84 etc. 25p. MIKE TRANS. 50:1 25p. SPEAKER COVERING MATERIALS. Sample Large S.A.E. GOODMAN'S OUTPUT TRANSFORMER 5 watt wash-up pot for valves EL84 etc., 3.8 and 15 ohms 85p. Post 20p.

BAKER 100 WATT ALL PURPOSE POWER AMPLIFIER

4 inputs speech and music. 4 mixing facilities. Response to 10-30,000 cps. Matches all loudspeakers. A.C. 200/250V. Separate Treble and Bass controls. Guaranteed Details S.A.E. £39 POST FREE



ALL EAGLE PRODUCTS

ILLUSTRATED EAGLE CATALOGUE 20p. Post Free.
BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4
BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. STEREO VERSION OF ABOVE £4-25.
BARGAIN FM TUNER 88-108 Mc/s. 3in. Transistor. 9 volt. Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 in. £10
BARGAIN FM TUNER as above less cabinet £7-50
BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. £3-50
COAXIAL PLUG 6p. PANEL SOCKETS 6p. LINE 18p. OUTLET BOXES, SURFACE OR FLUSH 25p. BALANCED TWIN FEEDERS 5p. 80 ohms or 300 ohms. JACK SOCKET Std. open-circuit 1 1/4 in. closed circuit 25p. Chrome Lead Socket 45p. Phono Plugs 5p. Phono Socket 5p. JACK PLUG Std. Chrome 15p; 3.5mm Chrome 15p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 25p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS, 5p; CERAMIC 5p; CAN 5p.

E.M.I. TAPE MOTORS Post 15p.

120v. or 240v. A.C. 1,200 r.p.m. 4 pole 135mA. Spindle 0.187 x 0.75in. £1-25
Size 3 1/2 x 2 1/2 in. (Illustrated). BALFOUR GRAM MOTORS 120v. or 240v. A.C. 1,200 r.p.m. 4 pole 50mA. Spindle 1/4 x 3/20. Size 2 1/2 x 2 1/2 in. Post 15p 85p

CUSTOMERS FREE CAR PARK. CALLERS WELCOME

337 WHITEHORN ROAD, CROYDON
Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.)
Buses 50, 68, 159 pass door. Rail Selhurst Tel. 01-684-1665

every component supplier and it would be unfair to give such information to some advertisers and not to others.

On reflection, I confess we would still be caught out occasionally even if we had this advance list simply because it is always impossible to forecast how popular a given design will be.

Let us say we have a certain coil in stock, that ordinarily sells at two dozen a year. Unknown to us, one of the magazine contributors uses it in a constructional article and the sales rocket to 100 a week. The poor coil manufacturer who sold a few hundred a year finds the demand increased to hundreds of thousands and so

his delivery which was 14 days becomes six months.

Sometimes there is no interest at all and with another one, we are inundated with requests for parts. We, of course, cannot lay out large sums of money without knowing whether there will be any sale for what we are buying!

Outlook Very Bright

I hope these three articles have been of some use to the general reader in enabling him to understand some of the problems involved. In conclusion I would like to hazard a guess at what the future holds in store for the electronics constructor. I think the outlook is very bright and the amateur constructor will be able to purchase more and more sophisticated parts to experiment with. We may go through a period where we seem in fact to be offering a decreased range. For example we stock 10 per cent and 5 per cent resistors at present, but if by buying large quantities we could offer you 5 per cent at nearly the same price as 10 per cent it would save us stocking a whole range, and you the consumer would be no worse off, in fact slightly better off.

This will happen because manufacturers are trying to sell larger and larger quantities! One can see their point of view, it costs them the same in administration costs to sell 10 as 10,000!

Another field where this same effect may occur is in toggle switches. We list four varieties: s.p.s.t., s.p.d.t., d.p.s.t., and d.p.d.t

switches. It is not difficult to see that the function of all four types could be performed by just one of them, namely the d.p.d.t. The difference in cost between the various types is not very great, so that if we were able to persuade you to use the d.p.d.t. in every case, we could buy four times the quantity and so bring the price down!

You will see what I mean in an apparent restriction in range—the actual restriction is nil!

However, while we have magazines like EVERYDAY ELECTRONICS and their contributors giving us such challenging and interesting designs, suppliers who are anxious to please, and above all customers like yourselves with such boundless enthusiasm, none of us need worry too much about the future!

Post Script

Since these articles appeared I have been delighted to receive a number of interesting letters, some containing constructive ideas. I will mention one small happening that occurred about the time the first issue of EVERYDAY ELECTRONICS appeared. A customer who had not dealt with us before required some components urgently. He telephoned us at 10 a.m. and gave us the order. He then sent the money by telegram or telegraph and we received it at 11.30 a.m. We were able to despatch his order the same day. I mention this as it is a method of ordering that I had overlooked and one that could be a life saver in an emergency.



... it is always impossible to forecast how popular a given design may be



... none of us need worry about the future!

G. F. MILWARD 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

SPECIAL 50p PACKS. ORDER 10 PACKS AND WE WILL INCLUDE AN EXTRA ONE FREE !!!

RESISTORS, 1/4 watt		
assorted	100	50p
Wire-wound 1 to 3 watt	20	50p
5 to 7 watt	15	50p
10 watts	10	50p
Multi-tapped	12	50p
PAPER CONDENSERS		
TV types	50	50p
Miniature	100	50p
ELECTROLYTIC CONDENSERS		
Suitable for Mains		
Radio/TV	10	50p
Transistor types	20	50p
Mixed (both types)	15	50p
POLYSTYRENE CONDENSERS	100	50p
MULLARD POLYESTER COND.	50	50p
SILVER MICA WIRE-WOUND 3-Watt	100	50p
SLIDERS	15	50p
VOLUME CONTROLS		
Assorted	5	50p
NUTS AND BOLTS. Mixed length/type		
8 B.A.	100	50p
6 B.A.	100	50p
4 B.A.	100	50p
2 B.A.	100	50p
METAL SPEAKER GRILLES		
7 1/2in. x 3 1/2in.	6	50p
EARPIECES, MAGNETIC		
No Plug	6	50p
2-5mm Plug	4	50p
3-5mm Plug	4	50p
500 MICRO-AMP LEVEL METERS	1	50p
VEROBOARD, TRIAL PACK 5 BOARDS + CUTTER	50p	

TRANSISTORS		
P.N.P. Untested but mainly O.K.	50	50p
N.P.N. Untested but mainly O.K.	50	50p
O.P. 71 equivalent	5	50p
Light-sensitive Diodes (These produce up to 1ma from light)	10	50p
OC44 Mullard 1st grade	4	50p
OC45 Mullard Boxed	5	50p
2G378 Output, Marked	5	50p
2G371 Driver, Marked	5	50p
AS722, Marked	5	50p
BY 127 Rectifiers	4	50p
IN4007 Rectifiers (1200V peak)	4	50p
STC 3/4 Rectifiers	6	50p
DIODES (OA 81 & OA 91) 40	5	50p
WIRE		
Solid Core. Insul. 100yds.	50p	
Stranded ditto	50yds.	50p
SOLAR CELLS		
Large Selenium	2	50p
Small	3	50p
(6 cells will power a Micro-matic radio)		
CO-AXIAL CABLE		
Semi Air-spaced 15yds.	50p	
CRYSTAL TAPE RECORDER		
MIKES		
CRYSTAL EARPIECES	1	50p
3-5mm Plug	2	50p
TRANSISTORISED Signal Injector Kit	1	50p
TRANSISTORISED Signal Tracer Kit	1	50p
TRANSISTORISED CAR REV. COUNTER KIT (Needs 1 ma. meter as indicator)	1	50p

STOCKTAKING CLEARANCE! IMPOSSIBLE TO REPEAT!
We have huge numbers of components in quantities too small to advertise individually. In order to "clear the decks" we have made up parcels containing a mixture of carbon and wire-wound resistors, electrolytic and paper condensers, controls, transistors, diodes etc., for a tiny fraction of normal price. It is emphasised that these are mixed parcels only—contents cannot be stipulated! Sold only by weight.

Gross weight 2 lb. £1 (postage 20p)
Gross weight 5 lb. £2 (postage 30p)

G. F. MILWARD, Drayton Bassett, Tamworth, Staffs. Postage (minimum) per order 15p.

Unrepeatable Offer ! ! ! !
Surplus VEROBOARDS, 3 1/2" x 2 1/2" x .15"
Only 10p each or £1.00 per dozen

TANTALUM CAPACITORS. COMPARE THE PRICE—ONLY 10p EACH ! ! ! !

Sub-miniature types		Miniature types			
0.047µF 50 volts	0.022µF 20 volts	5.6 µF	35 volts		
0.056µF 50 volts	0.033µF 20 volts	8.2 µF	10 volts		
0.07 µF 20 volts	0.047µF 20 volts	15 µF	35 volts		
0.1 µF 20 volts	0.068µF 35 volts	18 µF	35 volts		
0.1 µF 50 volts	0.12 µF 35 volts	22 µF	15 volts		
0.18 µF 20 volts	0.15 µF 35 volts	27 µF	120 volts		
0.33 µF 35 volts	0.22 µF 50 volts	56 µF	15 volts		
0.47 µF 35 volts	0.47 µF 50 volts	56 µF	20 volts		
0.68 µF 20 volts	0.68 µF 35 volts	150 µF	6 volts		
1.0 µF 15 volts	0.68 µF 50 volts				
2.2 µF 3 volts	1.0 µF 35 volts	Standard			
2.7 µF 15 volts	1.0 µF 75 volts	6.8 µF	50 volts		
2.7 µF 35 volts	1.8 µF 20 volts	7.5 µF	20 volts		
3.0 µF 12 volts	2.2 µF 20 volts	8.2 µF	150 volts		
10.0 µF 1.5 volts	2.7 µF 50 volts	12 µF	35 volts		
	3 µF 12 volts	12 µF	50 volts		
	3.3 µF 15 volts	39 µF	20 volts		
	4 µF 20 volts	82 µF	20 volts		
	4.7 µF 35 volts	050 µF	15 volts		
	5.6 µF 6 volts	270 µF	6 volts		

NEW ! NEW ! NEW ! NEW !

An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.

Method: Spray copper laminate board with light-sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner.
Light sensitive aerosol spray £1
Developer spray 50p

STEREO - NOW YOU CAN BUILD YOUR OWN

Mullard Unilex modules need no soldering, no knowledge of electronics. They make the stereo amplifier so simple that anyone can build it in an hour, for around £16. Connect the record deck and speakers and you've built your stereo system. For the comprehensive instruction book 'Do-it-yourself Stereo' and stockist list post this coupon today with a 25p P.O.



Room 512, Mullard House, Torrington Place, London WC1E 7HD.

Mullard UNILEX

Name _____
Address _____

E/E.1.72

CEC 136A

"Stella 99"

INSTRUMENT CASES



Size 6"W x 4"H x 4"D

Price £1.25p + 25p p.p.

We Believe the Finest Instrument Case in the Country. Beats all competitors for Price and strength

Fibreglass Press Moulded in Grey, and Blue. Supplied with 4 Rubber Feet. 18 SWG Alloy Chassis. 16 SWG Alloy Front Panel. Front Panel has Protective Film for marking out and protection. Chromed die cast handle. The case has two sets of Runners Moulded in which will take Alloy or P.C. Board Chassis. Same day off-the-shelf delivery. This size of case can be turned on end to make 4"W x 6"H x 4"D. Please advise if handle and feet to be supplied loose. Panel Punching available on 100 up. Trade and quantity discounts on request.

Full list of Accessories Available, sent with each order, i.e. Switches, Panel Lamps, Amplifiers, Fuses, etc.

E. R. NICHOLLS
46 Lowfield Road, STOCKPORT, CHESHIRE
Tel: 061-480 2179

BI-PRE-PAK



TELEPHONE DIALS
Standard Post Office type.
Guaranteed in working order.

ONLY 50p

8 RELAYS FOR £1

Various Contacts and Coil Resistances. No individual selection. Post & Packing 25p

NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0.3 to 0.5V. 0.5 to 2mA.	50p
B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values.	50p
H8	4	BY127 Sil. Recs. 1000 PIV. 1 amp. plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H12	50	NKT155/259 Germ. diodes, brand new stock clearance	50p
H18	10	OC71/75 uncodded black glass type PNP Germ.	50p
H19	10	OC81/81D uncodded white glass type PNP Germ.	50p
H28	20	OC200/12/3 PNP Silicon uncodded TO-5 can	50p
H29	20	OA47 gold bonded diodes coded MCS2	50p

NEW UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1, 2N706A, BSY95A, etc.	50p
B60	10	7 Watt Zener Diodes Mixed Voltages	50p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
H10	25	Mixed volts, 1/2 watt Zeners Top hat type	50p
B1	50	Germanium Transistors PNP, AF and RF	50p
H15	30	Top Hat Silicon Rectifiers, 750mA, mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1 each



OUR VERY POPULAR 3p TRANSISTORS


TYPE "A" PNP Silicon alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" PNP Silicon plastic encapsulation.

FULLY TESTED AND MARKED SEMICONDUCTORS

4p		6p	
AC107	0-15	OC170	0-23
AC126	0-13	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-13	OC201	0-25
AC176	0-25	2G301	0-13
ACY17	0-15	2G303	0-13
AF239	0-37	2N711	0-30
AF186	0-50	2N1302-3	0-20
AF139	0-37	2N1304-5	0-25
BC154	0-25	2N1306-7	0-30
BC107	0-13	2N1308-9	0-35
BC108	0-13	2N3819FET	0-45
BC109	0-14		
BF194	0-15	Power Transistor:	
BF274	0-15	OC20	0-30
BFY50	0-20	OC23	0-30
BSY25	0-57	OC25	0-25
BSY26	0-13	OC26	0-25
BSY27	0-13	OC28	0-30
BSY28	0-13	OC35	0-25
BSY29	0-13	OC36	0-37
BSY95A	0-15	OC36	0-30
OC41	0-13	AD149	1-25
OC44	0-13	ALY10	1-25
OC45	0-13	25034	0-25
OC71	0-13	2N3055	0-43
OC72	0-13	Diodes	
OC81	0-13	AAY42	0-10
OC82	0-13	OA95	0-19
OC83	0-20	OA79	0-09
OC139	0-13	OA81	0-09
OC140	0-17	IN9114	0-07

F.E.T. PRICE BREAKTHROUGH!!

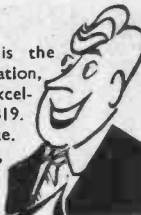This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3B23E. It is also an excellent replacement for the 2N3819. Data sheet supplied with device. 1-10 30p each, 10-50 25p each, 50+ 20p each.



BULK BUYING CORNER

NPN/PNP Silicon Planar Transistors, mixed, untested, similar to 2N706/6A/8, BSY26-29, BSY95A, BCY70, etc. £4-25 per 500; £8 per 1,000.

Silicon Planar NPN Plastic Transistors, untested, similar to 2N3707-11, etc., £4-25 per 500; £8 per 1,000.

Silicon Planar Diodes, DO-7 Glass, similar to OA200/202, BAY31-36, £4-30 per 1,000.

NPN/PNP Silicon Planar Transistors, Plastic TO-18, similar to BC113/4, BC153/4, BF153/160, etc., £4-25 per 500; £8 per 1,000.

OC44, OC55 Transistors fully marked and tested, 500+ at 8p each; 1,000+ at 6p each.

OC71 Transistors, fully marked and tested, 500+ at 6p each; 1,000+ at 5p each.

3B23E Field effect Transistors. This is the 2N3823 in Plastic Case, 500+ 13p each; 1,000+ 10p each.

1 amp Miniature Plastic Diodes:

IN4001, 500+ at 4p each; 1,000+ at 3p each.
IN4004, 500+ at 5p each; 1,000+ at 5p each.
IN4006, 500+ at 6p each; 1,000+ at 5p each.
IN4007, 500+ at 8p each; 1,000+ at 7p each.

FREE CATALOGUE AND LISTS FOR

TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS & SUBSTITUTION CHARTS



CLEARANCE LINES

COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

NOW ONLY 50p each post and packing 23p.

Quantity	1-10	10-50	50+
BB105 Varicap Diodes	10p	8p	6p
OC71 or 72 Fully Tested Unmarked	5p	5p	4p
Matched Sets. 1-OC44 and 2-OC45's. Per Set.	25p	20p	15p
Matched Sets of OC45's 1st and 2nd IF	15p	12p	10p
OA47 Gold-Bonded Diodes, Marked and Tested	3p	3p	2p
1-watt Zener Diodes 7-5, 24, 27, 30, 36, 43 Volts	5p	4p	3p
10-watt Zener Diodes 5-1, 8.2, 11, 13, 16, 24, 30, 100 Volts	20p	17p	15p
Micro Switches, S/P, C/O	25p	20p	15p
1-amp Bridge Rec's 25-volt	25p	22p	20p

INTEGRATED CIRCUITS

SL403D Audio Amp, 3-Watts	2-00	1-95	1-80
709C Linear Opp. Amp.	50p	40p	35p
Gates, Factory Marked and Tested by A.E.I.	25p	22p	20p
J. K. Flip-Flops Factory, Marked and Tested by A.E.I.	40p	35p	30p
PA234 1-watt Audio Amp.	1-00	90p	80p
UL914 Dual 2 1/2 Gate	40p	35p	30p

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 15p each
16 pin type at 16p each.

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines: **B.P.I. Transistor Equivalents and Substitutes;** 40p

This includes many thousands of British U.S.A., European and C.V. equivalents. **The Iiffe Radio Valve & Transistor Data Book 9th Edition;** 75p
Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.
Send for lists of these English publications.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME.....

ADDRESS.....

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE

BI-PRE-PAK LTD

DEPT. E, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF
TELEPHONE: SOUTHEND (0702) 46344

BRAND NEW GUARANTEED

SEMICONDUCTORS & COMPONENTS
SOLE AGENTS FOR SOLID STATES DEVICES INC., (USA), IN U.K.

RETURN OF POST SERVICE

TRANSISTORS

TTL LOGIC I.C. NEW PRICES

4C301	20p	2N3404	32p	40310	45p	BCY12L	13p	B8X28	32p	NKT281	27p
2G302	20p	2N3405	45p	40311	45p	BCY13	27p	B8X41	27p	NKT401	87p
2G303	20p	2N3414	25p	40312	47p	BCY31	30p	B8X61	82p	NKT403	60p
2G306	42p	2N3415	25p	40314	37p	BCY32	50p	B8X76	22p	NKT404	75p
2G308	30p	2N3416	37p	40320	47p	BCY33	25p	B8X77	27p	NKT405	75p
2G309	30p	2N3417	37p	40323	32p	BCY34	30p	B8X78	27p	NKT406	62p
2G371	15p	2N3570	15p	40324	47p	BCY38	40p	B8Y10	27p	NKT408	62p
2G372	20p	2N3572	25p	40329	37p	BCY41	27p	B8Y11	27p	NKT452	62p
2G381	25p	2N3605	27p	40329	27p	RCY40	50p	B8Y24	15p	NKT453	47p
2N404	25p	2N3606	27p	40334	37p	BCY42	15p	B8Y25	15p	NKT603F	32p
2N696	20p	2N3607	25p	40347	57p	BCY43	15p	B8Y26	17p	NKT603F	32p
2N697	17p	2N3702	11p	40348	52p	BCY44	32p	BCY27	17p	NKT674F	30p
2N698	20p	2N3703	10p	40350	42p	BCY58	22p	BCY28	17p	NKT677F	30p
2N706	12p	2N3704	11p	40361	47p	BCY59	22p	BCY29	17p	NKT713	25p
2N705A	12p	2N3705	10p	40362	57p	BCY60	87p	BCY32	17p	NKT1049	30p
2N708	15p	2N3706	09p	40370	32p	BCY70	20p	BCY36	25p	NKT1049	30p
2N709	62p	2N3707	11p	40406	57p	BCY71	25p	BCY37	25p	NKT1049	30p
2N718	25p	2N3708	07p	40407	40p	BCY72	17p	BCY38	22p	NKT1049	30p
2N726	30p	2N3709	09p	40408	62p	BCZ10	27p	BCY39	22p	NKT1049	30p
2N727	30p	2N3710	09p	40410	62p	BCZ11	48p	BCY40	32p	NKT1049	30p
2N914	17p	2N3711	12p	40467A	57p	BD116	11.12p	BSY61	32p	NKT1049	30p
2N916	17p	2N3716	11.25p	40468A	37p	BD121	65p	BSY62	32p	NKT1049	30p
2N918	30p	2N3716	11.80p	40600	67p	BD123	82p	BSY63	47p	NKT1049	30p
2N929	22p	2N3791	22.00p	AC107	30p	BD124	60p	BSY64	40p	NKT2039	30p
2N930	27p	2N3818	35p	AC109	20p	BD131	75p	BSY65	90p	NKT2039	30p
2N1090	22p	2N3823	27p	AC122	25p	BD137	75p	BSY66	90p	NKT2039	30p
2N1091	22p	2N3854	27p	AC128	20p	BDY10	11.37p	BSY79	47p	NKT2039	30p
2N1131	25p	2N3854A	27p	AC154	22p	BDY11	11.62p	BSY82	52p	NKT2039	30p
2N1132	25p	2N3855	27p	AC176	26p	BDY17	11.50p	BSY90	52p	NKT2039	30p
2N1302	17p	2N3856A	30p	AC187	62p	BDY18	11.75p	BSY95A	18p	NKT2039	30p
2N1308	17p	2N3856	30p	AC188	37p	BDY19	11.97p	BSY94	42p	NKT2039	30p
2N1304	25p	2N3856A	30p	ACY17	27p	BDY20	11.51p	BSW70	12p	NKT2039	30p
2N1305	22p	2N3858	25p	ACY18	25p	BDY38	97p	C111	75p	NKT2039	30p
2N1306	25p	2N3858A	30p	ACY19	25p	BDY60	11.25p	C24	25p	NKT2039	30p
2N1307	25p	2N3859	27p	ACY20	25p	BDY61	11.25p	C25	55p	NKT2039	30p
2N1308	30p	2N3859A	32p	ACY21	30p	BDY62	11.00p	C428	40p	NKT2039	30p
2N1507	17p	2N3866	11.50p	ACY26	20p	BF115	25p	C428	37p	NKT2039	30p
2N1613	25p	2N3877	40p	ACY40	20p	BF163	37p	D16P1	37p	NKT2039	30p
2N1631	35p	2N3877A	40p	ACY41	25p	BF167	18p	D16P2	40p	NKT2039	30p
2N1632	30p	2N3900	37p	ACY44	40p	BF173	18p	D16P3	37p	NKT2039	30p
2N1638	27p	2N3900A	40p	AD140	52p	BF177	30p	D16P4	40p	NKT2039	30p
2N1639	27p	2N3901	37p	AD151	57p	BF178	30p	GET102	92p	NKT2039	30p
2N1671B	11p	2N3901	37p	AD150	30p	GET113	30p	OC20	75p	NKT2039	30p
2N1711	25p	2N3904	35p	AD161	37p	BF180	35p	GET114	20p	OC22	50p
2N1889	82p	2N3905	37p	AD162	37p	BF181	32p	GET118	20p	OC23	60p
2N1893	87p	2N3906	37p	AF106	42p	BF184	25p	GET119	20p	OC24	60p
2N2147	82p	2N4068	17p	AF114	25p	BF185	42p	GET120	62p	OC26	50p
2N2148	87p	2N4069	17p	AF120	35p	BF192	17p	GET123	62p	OC28	27p
2N2160	87p	2N4060	12p	AF116	25p	BF195	15p	GET180	30p	OC29	27p
2N2193	40p	2N4061	12p	AF117	25p	BF196	42p	GET187	20p	OC29	62p
2N2193A	42p	2N4062	12p	AF118	62p	BF197	42p	GET189	22p	OC35	50p
2N2194A	42p	2N4244	47p	AF119	20p	BF198	42p	GET189	22p	OC36	62p
2N2217	27p	2N4286	17p	AF124	22p	BF200	52p	GET186	22p	OC41	22p
2N2218	27p	2N4286	17p	AF125	20p	BF201	52p	GET197	22p	OC42	25p
2N2219	25p	2N4287	17p	AF126	20p	BF225	15p	GET198	22p	OC44	30p
2N2220	25p	2N4288	17p	AF127	17p	BF237	23p	MJ400	11.07p	OC45	12p
2N2221	25p	2N4289	17p	AF139	37p	BF238	23p	MJ420	11.12p	OC46	15p
2N2222	30p	2N4290	17p	AF178	42p	BF244	23p	MJ421	11.12p	OC70	15p
2N2270	47p	2N4291	17p	AF179	72p	BFW61	47p	MJ480	11.02p	OC71	12p
2N2297	30p	2N4302	47p	AF180	42p	BFX12	22p	MJ481	95p	OC72	12p
2N2368	17p	2N4303	47p	AF181	42p	BFX13	22p	MJ480	95p	OC74	22p
2N2369	17p	2N4307	47p	AF239	42p	BFX29	30p	MJ481	11.25p	OC75	22p
2N2369A	17p	2N5023	57p	AF279	47p	BFX30	30p	MJ490	11.00p	OC76	22p
2N2410	42p	2N5029	47p	AF280	62p	BFX42	37p	MJ491	11.37p	OC77	30p
2N2483	27p	2N5030	42p	AF211	32p	BFX44	37p	MJ1800	22.17p	OC81	20p
2N2484	27p	2N5034	42p	AS727	37p	BFX45	67p	MJE260	82p	OC82	25p
2N2539	29p	2N5174	45p	AS727	37p	BFX84	25p	MJE520	82p	OC83	25p
2N2540	22p	2N5175	52p	AS728	27p	BFX85	32p	MJE521	72p	OC84	25p
2N2613	35p	2N5176	45p	AS729	27p	BFX86	25p	MPP102	42p	OC139	32p
2N2614	30p	2N5222A	40p	AS736	25p	BFX87	27p	MPP103	37p	OC140	32p
2N2646	52p	2N5245	45p	AS760	25p	BFX88	25p	MPP104	37p	OC170	30p
2N2656	32p	2N5246	45p	AS761	32p	BFX89	62p	MPF383	37p	OC71	30p
2N2711	25p	2N5249	67p	AS754	25p	BFY9A	70p	MPB388	32p	OC200	40p
2N2712	25p	2N5265	23.25p	AS786	32p	BFY10	32p	NKT0013	47p	OC201	60p
2N2713	27p	2N5286	22.75p	AU103	11.25p	BFY11	42p	NKT124	42p	OC202	75p
2N2714	30p	2N5287	22.62p	AS221	42p	BFY17	22p	NKT125	27p	OC203	42p
2N2865	62p	2N5305	37p	BC107	10p	BFY18	32p	NKT126	27p	OC204	42p
2N2901	30p	2N5306	40p	BC108	10p	BFY19	11.45p	NKT128	27p	OC205	60p
2N2904A	32p	2N5307	37p	BC109	10p	BFY20	11.50p	NKT135	27p	OC207	75p
2N2905	37p	2N5308	37p	BC113	15p	BFY21	42p	NKT137	32p	OC271	42p
2N2905A	40p	2N5309	62p	BC115	15p	BFY24	45p	NKT210	30p	ORP12	60p
2N2906	25p	2N5310	42p	BC116A	15p	BFY25	25p	NKT211	30p	ORP61	60p
2N2906A	27p	2N5384	47p	BC118	10p	BFY26	30p	NKT212	30p	P346A	22p
2N2907	30p	2N5385	27p	BC121	20p	BFY29	50p	NKT213	30p	TIS34	62p
2N2923	15p	2N5386	32p	BC122	20p	BFY30	50p	NKT214	22p	TIS43	27p
2N2924	15p	2N5385	47p	BC125	20p	BFY41	50p	NKT215	22p	TIS44	10p
2N2925	15p	2N5386	52p	BC126	20p	BFY43	62p	NKT216	37p	TIS45	10p
2N2926	20p	2N5367	37p	BC140	37p	BFY60	23p	NKT217	42p	TIS46	11p
Green	14p	2N5457	37p	BC147	10p	BFY61	20p	NKT219	30p	TIS47	12p
Yellow	12p	2N5472	12p	AS736	35p	BFX38	23p	NKT223	27p	TIS48	12p
Orange	12p	2R820	22.00p	BC149	12p	BFY73	17p	NKT224	25p	TIS49	12p
2N3011	30p	2R102	50p	BC152	17p	BFY66A	57p	NKT225	22p	TIS60	17p
2N3014	32p	2R103	25p	BC157	20p	BFY76	30p	NKT229	30p	TIS61	12p
2N3053	18p	2R104	25p	BC158	11p	BFY78	42p	NKT237	35p	TIS62	12p
2N3054	46p	2R501	32p	BC159	18p	BFY77	57p	NKT238	25p	TIS93	22p
2N3055	32p	2R306	35p	BC160	62p	BFY90	67p	NKT240	27p	OC71	22p
2N3133	30p	2R503	27p	BC167	11p	BFW58	27p	NKT241	27p	TIS61	25p
2N3134	30p	3N83	62p	BC168B	10p	BFW59	25p	NKT242	20p	TIS62	27p
2N3135	25p	3N128	70p	BC168C	11p	BFW60	25p	NKT243	62p	TIP29A	50p
2N3136	25p	3N140	77p	BC169B	11p	BFX25	11.85p	NKT244	17p	TIP30A	60p
2N3390	25p	3N141	72p	BC169C	12p	BFX29	11.80p	NKT245	20p	TIP31A	62p
2N3391	20p	3N142	67p	BC170	18p	BFY10	11.45p	NKT246	27p	TIP32A	75p
2N3391A	30p	3N143	67p	BC171	16p	BFY39	16p	NKT262	30p	TIP33A	75p
2N3392	17p	3N152	87p	BC172	15p	B8X19	17p	NKT264	20p	TIP34A	11.02p
2N3393	15p	R.C.A.	52p	BC175	22p	B8X20	17p	NKT271	20p	TIP34A	22.05p
2N3394	15p	40650	55p								

BUDGET HIGH-FIDELITY STEREO SYSTEMS



PREMIER STEREO SYSTEM "ONE" Consists of the new Premier 800 all transistor stereo amplifier, Garrard 2025 T/C auto manual record player unit fitted stereo mono ceramic cartridge with diamond stylus and mounted in teak finish plinth with perspex cover and two matching teak finish loud-speaker systems. Absolutely complete and supplied ready to plug in and play. 800 amplifier has an output of 5 watts per channel with inputs for ceramic and magnetic pick-up, tape and tuner also tape output socket and headphone socket. Controls: Bass, Treble, Volume, Balance, Selector, Power on/off. Mono/Stereo switch. Stereo Headphone socket. Black leatherette cabinet with aluminium front panel. Size: 12½" x 6½" x 2½". (Amplifier available separately if required £18-25. Carr. 40p).

ONLY
£40-95
carr. £1-75

PREMIER STEREO SYSTEM "TWO", as above but with Garrard SP25 MK III and magnetic cartridge. **ONLY** £48. Carr. £1-75.

ONLY
£57-75
carr. £1-75

PREMIER STEREO SYSTEM "THREE". This consists of KLINGER KC903 stereo amplifier giving 6 watts r.m.s. per channel with Bass, Treble, Volume and Balance Controls. Inputs for Magnetic and ceramic pick-up, tuner, tape in and out. Stereo earphone socket. Garrard SP25 Mk. III in teak finish plinth with cover and fitted Sonotone 9TAHCD diamond stereo cartridge. A pair of RMP Speakers size 16½" x 10½" x 9" fitted EMI units complete the matching system. **ONLY** £57-75. Carr. £1-75.

FREE

STEREO HEADPHONES

and all leads and plugs supplied with all systems.

PREMIER HI-FI OFFERS

- Philips 580 Stereo Amplifier (List £29-00) **£21-00**
- Rogers Ravensbrook II Stereo Amplifier in teak case (List £52-50) **£39-50**
- Rogers Ravensbourne Stereo Amplifier in teak case (List £64) **£49-00**
- Metrosound ST20E Stereo Amplifier in teak case (List £39-50) **£28-50**
- Goldring GL75 less cartridge (List £41-61) **£29-00**
- Garrard SP25 III less cartridge **£11-30**
- Garrard SP25 III with Goldring G800 cartridge (List £28-35) **£15-50**
- Garrard AP76 less cartridge **£19-50**

Garrard 3500 with Sonotone 9TAHC stereo cartridge (List £15-50) **£9-97**

Garrard 2025 T/C with Sonotone 9TAHC Diamond Cartridge **£9-97**

Garrard 2025 T/C with Sonotone 9TAHC Diamond Cartridge ready wired in teak plinth with cover **£14 00**

Carriage and Insurance 50p extra any item.



TAPE CASSETTES

C60 (60 min.)	37p	3 for £1.05
C90 (90 min.)	62p	3 for £1.50
C120 (120 min.)	87p	3 for £2.55

P. & P. 5p.

FREE CASSETTE HEAD CLEANER with every 10 cassettes purchased.

All cassettes can be supplied with library cases at 3p. extra each

SP25 MKIII SPECIAL!



GARRARD SP25 MK III SINGLE RECORD PLAYER with GOLDRING 800 MAGNETIC STEREO CARTRIDGE as available. COMPLETE IN TEAK PLINTH WITH RIGID PERSPEX COVER. Total list price over £34.

PREMIER PRICE
£18-90
P. & P. 50p.



HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2½in speaker units with soft padded ear muffs. Adjustable headband. 8 ohms impedance. Complete with 6ft lead and stereo jack plug.

£2-47 P. & P. 25p.

STEREO STETHOSCOPE SET Low Imp. £1.25 P. & P. 10p

MONO STETHOSCOPE SET Low Imp. 52p. P. & P. 10p.




E.M.I. 13x8in. HI-FI SPEAKERS

Fitted two 2½in tweeters and crossover network. Impedance 8 or 16 ohm. Handling capacity 10W. Brand new.

£3-47 P. & P. 40p

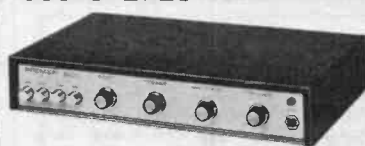NEW LOW COST PREMIER 800 STEREO AMPLIFIER



A truly high quality stereo amplifier—compare the specification, compare the price. Output: 5 watts per channel. Frequency response: 30-20,000 Hz = 2 db. Distortion: 1%. Output Impedance 8 ohms nom. Inputs equalised to R.I.A.A. Magnetic 4mV. Ceramic 100mV. Tuner 100mV. Tape 100mV. Tape out 150mV. Din sockets for inputs and outputs. Stereo headphone socket. Attractive slim line design black leatherette cabinet with aluminium front panel. Size 12½" x 6½" x 2½". **ONLY** £17-25. Carriage 40p.

ONLY £16-25 Carr. 40p.



WELLER "EXPERT" SOLDER GUN. Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant dual heat. 100/140 watt. 240 volt A.C. **£4-25** P & P 30p

"Marksmen" Soldering Iron. Lightweight ¼" pencil bit. Ideal for regular bench use and around the home. 25 watt. 240 volt A.C. £1-50 P & P 15p

"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

LP8 3" 250'	P.V.C.	28p	LP6 5½" 1200'	P.V.C.	75p
TT3 3" 450'	POLYESTER	37p	DT8 5½" 1800'	POLYESTER	£1-12
DT3 3½" 600'	POLYESTER	57p	TT6 5½" 2400'	POLYESTER	£1-87
SP6 5" 600'	P.V.C.	42p	SP7 7" 1200'	P.V.C.	62p
LP6 5" 900'	P.V.C.	50p	LP7 7" 1800'	P.V.C.	75p
DT5 5" 1200'	POLYESTER	75p	DT7 7" 2400'	POLYESTER	£1-25

TAPE SPOOLS 3" 5p, 5", 5½", 7" 9p.
Post and Packing 3" 5p, 5", 5½", 7" 10p, (3 reels and over Post Free).



PREMIER RADIO

10 & 23, TOTTENHAM COURT ROAD, LONDON, W.1 TEL: 01-636 3451/2639
HEAD OFFICE & MAIL ORDER DEPT. 23, TOTTENHAM CT. RD. TEL: 01-636 3451



Everyday Electronics Classified Advertisements

RATES: 7p per word (minimum 12 words). Box No. 7p. extra. Semi-display—£4.50 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Department, "EVERYDAY ELECTRONICS," I.P.C. Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD.

RECEIVERS and COMPONENTS

NEW GUARANTEED DEVICES ORDER WITH CONFIDENCE

MICROCIRCUITS:

SN76013 (like IC12) £1.50; 709 36p; 741 36p; PA230 90p; PA234 86p; PA237 £1.55; SL402A £1.75; SL702C 40p.

TTL GATES 15p; FLIPFLOPS 37p.

TRANSISTORS:

2N3055 54p; BC107B 9p; BC108C 9p; BC109C 9p; BCY 70 16p; BFX 86 15p; ME0402 21p; ME0411 20p; ME0412 20p; ME0413 15p; ME1002 11p; ME4101 11p; ME4102 12p; ME6101 15p; ME6102 19p; ME8001 17p; MP8111 35p; MP8112 45p.

1 AMP RECTIFIERS:

50V 3p; 100V 4p 200V 5p; 400V 6p.

BRIDGES: 50V 30p; 100V 31p; 400V 33p.

3 AMP RECTIFIERS: 400V 12p. 200V 10p.

PRINTED CIRCUIT RESIST PEN: 80p.

Discounts begin at 10 off.

JEF ELECTRONICS (E.E.1)

York House, 12 York Drive, Grappenhall, Warrington, WA4 2EJ. Mail Order Only. C.W.O. P & P 7p per order. Overseas 65p.

Money back if not satisfied.

List free on application.

DO-IT-YOURSELF ... We stock a large range

of audio and electronic components at very competitive prices, e.g.: Chassis speakers, cross-over networks, hi-fi speaker kits (Wharfedale & Peerless), BAF sound absorbent, speaker grille fabrics, inductors, resistors, electrolytics (reversible and polarised), transistors, etc. Send for FREE list. (2 x 3p stamps for fabric samples.) Mail-order ONLY. No callers please.

AUDIOSCAN

Dept EE172

4, PRINCES SQUARE, HARROGATE, YORKS.

POLYSTYRENE CAPACITORS 125v Values from 150pf to 0.015 (No 4700pf) 15p dozen, post 5p IC'S ON PANELS 7400 Series at least 10—75p, post 10p with details. COMPUTER PANELS, 6-BC108, DIODES 15p, post 5p, 4—50p, post 10p. AMERICAN PANELS total at least 30—transistors, first grade components, details provided 3—55p, post 10p. PANELS with 10 x BSX28, 500 Meg Silicon PNP 35p, post 5p. MIXED PANELS 6 for £1, post 15p, no midget panels, plenty of components, at least 60—transistors. FERRITE ROD 7 x 1 12p, post 8p each, 27p for 5. LAZ POT CORES ex equipment, 20p post paid. QBF12 on panel ex equip. 35p post paid. COPPER CLAD FAXOLIN single sided 13 x 11, 40p, post 8p each. COMPUTER RELAYS DDDT 700 ohm coil, weigh 1/2 oz, also weigh 1/2 oz, carry 2 amp and 5000 ohm coil weigh 14oz carry 2 amp. 55p post paid. Larger relay 700ohm weighs 1 1/2 oz. 35p post paid. SMALL SYNCHRONOUS MOTOR with gear train 900—2500v 30p post paid. ELECTROLYTICS 5,000mfd 25v 40p post paid.

ASSORTED PANELS WITH RES, CAPS, DIODES, INDUCTORS.

3 lb. 75p post paid.

J.W.B. RADIO

75 HAYFIELD ROAD, SALFORD 6, LANCs.

MAIL ORDER ONLY

COMPLETE PRINTED CIRCUIT AUDIO KITS

5 watt Power Amplifier £3.44. Postage and 3-5 watt. Power Amplifier £2.86. Packing 10p. 3 watt Stereo System £7.90

Full instructions and diagrams sent with all kits. Also available Printed Circuit kits, Component boards and a range of linear integrated circuits. LECTRON (Dept. EE), King Alfred Way, Cheltenham, Glos. Mail orders only.

RECEIVERS and COMPONENTS

APPROXIMATELY 10 silicon NPN general purpose transistors, also diodes, components, on 5 x 5in. panel, 17p. 5 panels 70p. 25 for £2.50. 100 for £8.10. SAE lists, data, free samples. Pawson, 114 South Street, Armadale, W. Lothian.

SERVICE SHEETS

SERVICE SHEETS (1925-1971) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. HAMILTON RADIO, 54 London Road, Bexhill, Sussex. Telephone: Bexhill 7097.

EDUCATIONAL

TECHNICAL TRAINING in Radio, TV & Electronics through world-famous ICS. For details of proven home-study courses write: ICS (Dept. 566), Intertext House, London, SW8 4UJ. Accredited by the CACC.

HOLIDAYS

HOLIDAY FOR BOYS. 14/16 years, Summer 1972. Tuition and practical work in electronics (and tape recording), engineering (Karting), photography. 11 days in Norfolk—£16. Write for free brochure: Inter-School Christian Fellowship, c/o 1 Hubbard Road, London SE27 9PJ.

MISCELLANEOUS

RECORD TV SOUND using our loud-speaker isolating transformer. Provides safe connection to recorder. Instructions included. 70p + 10p P&P. CROWBOROUGH ELECTRONICS (E.E.), Eridge Road, Crowborough, Sussex.

PROFESSIONAL CONTROL PANELS

with **FASCIA KIT**

MAKE YOUR OWN PANELS IN PERMANENT, ANODISED, SELF-ADHESIVE ALUMINIUM. NO SPECIAL EQUIPMENT NEEDED. EASY TO FOLLOW INSTRUCTIONS. CHOICE OF SILVER ON BLACK, RED, BLUE, GREEN. TRIAL KIT (36 sq. in.) .. £1.28 carr. pd. No. 1. KIT (54 sq. in.) .. £1.88 carr. pd. No. 2. KIT (72 sq. in.) .. £2.39 carr. pd. MPE Ltd., Dpt D.E. Bridge St. Clay Cross, Derbys

12 VOLT FLUORESCENT LIGHTS



Beat Power Cuts. 12 ins 8 watt Tube, ideal for Caravan, Tent, Emergency Lighting, etc. Fully Transistorised, Low Battery Drain. With ON/OFF Switch and 12V Socket to run other Lights or 12V Equipment.

Unbeatable at **£3.30** post paid

or in kit form **£2.90**

EASY TO CONSTRUCT
SALOP ELECTRONICS Callers welcome
23 Wyle Cop
Shrewsbury, Shropshire Large S.A.E. for lists

MISCELLANEOUS—continued

BUILDING THE

EE Record Player ?

FOR A CHRISTMAS PRESENT ?

WE CAN SUPPLY **SL403D**

and— I.C. Amplifier

ONLY £1.99

plus 9p p & p

FREE with SL403D ONE

Nippiboard 1A

and 3

TWO SL403D £3.90

plus 10p p & p

FREE

Nippiboards 1A

from

NIP ELECTRONICS PO. Box 11

St Albans

new nippiboard

THE PRINTED WIRING BOARD FOR

TRANSISTOR CIRCUITS

EE Home Sentinel -- Type 1A srbp 15p.

EE Windscreen Wiper Control --

Add 4p p & p. -- Type 1B fibreglass 18p.

Ask for details of multiple pattern NIPPBOARD.

Also suitable for other EE, PE, P.W. projects.

NIP ELECTRONICS Dept NB/EE

P.O. Box 11 St Albans Herts

JOHN SAYS...

RING MODULATOR by Dewtron is professional, transformerless, 5-transistor, has adjustable FI/F2 rejection. Module £7. Unit £8.90. WAA-WAA Pedal kit of all parts, incl. all mechanics & instr. Only £2.95. AUTO RHYTHM from Dewtron modules. Simple unit for waltz, foxtrots etc. costs £18.00 in module. SYNTHESISER MODULES and other miracles. Send 15p for illust. list. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get all the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE, LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.20 NOW

TO: BOFFIN PROJECTS'

DEPT. KEE.

4 CUNLIFFE ROAD,

STONELEIGH, EWELL, SURREY

FASCIA PANELS, DIALS, NAME-PLATES etc. (single or multiples) in etched aluminium to individual specification. Hardware supplies for constructors, s.a.e. details and list.

R. A. Marsh,
29 Shelbourne Road,
Stratford on Avon, Warwks.

LOOK AT THESE PRICES

CARTRIDGES

Acos GP67-2, GP91-38C £1.25; Acos GP93-1 £1.50; Acos GP94-1 £1.82; Sonotone 9TAHC £2.49. All above in makers' cartons. BSR X4H £1.50.

THIS MONTH'S SPECIAL OFFER

Garrard SP25 Mk. III with KS40A cartridge. In good quality teak plinth with perspex dust cover. Complete with all leads ready to use £20. SP25 Mk. III deck only less cartridge £12.87.

PLUGS & SOCKETS

Phono plugs, assorted colours 4p, 45p per doz.; Coaxial plugs, aluminium 7p; Coaxial couplers 7p; 2 pin DIN plugs 15p; 3 pin DIN plugs 15p; 5 pin DIN plugs 17p; 2 pin, 3 pin & 5 pin DIN sockets 7p; Wander plugs 2p; sockets 3p; Banana plugs 5p; Sockets 5p; 3.5mm J/Plugs 7p and 12p; Standard J/Plugs with solder terminals 10p; Chrome 15p; Side Entry J/Plugs black and chrome 24p; Insulated j/sockets - o/cset 20p, o/cset 17p.

ELECTROLYTIC CAPACITORS

40F 150v 4p; 80F 500v 15p; 100F 150v 4p; 120F 25v 4p; 160F 450v 14p; 160F - 160F 460v 23p; 300F 10v 4p; 500F 25v 7p; 1000F 9v 4p; 1000F 12v 4p; 13000F 30v 18p; 100F 16v 7p; 50000F 25v 60p; 10,000uF 25v 75p; 20,000uF 30v £1.05.

GEORGE FRANCIS (DEPT EE)

12 - 14, MIDDLE GATE, NEWARK, NOTTS.
Telephone: Newark 4733.

CHROMASONIC electronics

supply only brand new guaranteed goods

LOW NOISE HI-STABS

1 watt 5%, all E24 values 3 for 2p plus p. & p. 6p for up to 50 resistors + 1p for each additional 50.

INTEGRATED CIRCUITS

PA234 85p MC1304P £2.50 TAA700 £2.00
PA237 £1.55 MC1305P £2.50 TAD100 £1.85
PA246 £1.80 MPC4000P 15p μ A709C 45p
SL403D £2.12 MFC4010P 75p μ A710 45p
MC1303L £1.55 TAA661B £1.90 μ A741C 70p

TRANSISTORS & DIODES

AC127/8 17p BF115 25p 2N3055 55p
AC187/8 30p BF173 25p OA81/90/91 7p
AD161 pair MJE340 67p OA200 10p
AD162 63p OC71 15p IN4001 8p
AF114/5/6/7/18/ OC72 17p IN4004 10p
BC107/9 12p 2N3702/3 12p IN4005 12p
BC108 11p 2N3704 17p IN4007 18p
BC147/9 15p 2N3705/6/7 15p W005 40p
BC148 12p 2N3708/9/10/11 W01 45p
BC168/68 15p 2N1711 12p W02 48p
BC167/59 20p 2N1711 25p BZY88 15p
2N2926 Q/Y 15p

MULLARD C280 POLYESTER CAPACITORS

.01uF, .015, .022, .033, .047, 3p, .068uF 31p, .1uF, .15, 4p, .22, 5p, .33, 61p, .47, 8p, .68 11p, 1uF, 13p, 1.5uF 20p, 2.2uF 24p.

MULLARD ELECTROLYTICS, C426, C431, C437, etc.

2.5uF 6.4v 6p 250uF 25v 10p 1250uF 40v 42p
10uF 16v 6p 230uF 40v 13p 2000uF 25v 42p
25uF 25v 8p 300uF 40v 28p 2500uF 40v 63p
50uF 25v 10p 500uF 64v 38p 2500uF 64v 77p
100uF 16v 4p 1000uF 16v 16p 4000uF 25v 63p
125uF 16v 6p 1250uF 25v 38p 4000uF 40v 77p

MODULES FULLY ASSEMBLED & TESTED

F.M. STEREO I.F. STRIP £3.50 + p. & p. 25p
F.M. FRONT END £5.00 + p. & p. 25p
F.M. STEREO DECODER £5.25 + p. & p. 25p

GARRARD SP25 Mk.III with 9TAHC £12.72 + p. & p. 50p.
CARBON TRACK POTS, single gang log or lin 12p, Dual gang log or lin 40p. Mains Switch + 12p.

SKELETON PRESETS Vert. or Horiz., 0.1w 5p, 0.25w 7p.

MAINS TRANSFORMER. Sec. 20-12-0-12-20V @ 0.7A £1.75 + p. & p. 30p.

SWITCHES: Toggle SPST 18p. P/Button SPST 37p.
BULB & HOLDER 6V, 0.06A 15p. CERAMIC CAP.
.01uF 30V 10p, Silvered Mica 25p/7p, 680pf 8p.

1972 CATALOGUE 10p, post free unless indicated, p & p. on all orders is 6p
56 FORTIS GREEN ROAD, LONDON. N.10

EX COMPUTER PRINTED CIRCUIT PANELS 2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 50p, P. & P. 7p. With a guaranteed minimum of 35 transistors. Data on transistors included.

SPECIAL BARGAIN PACK. 25 boards for £1, P. & P. 18p. With a guaranteed minimum of 85 transistors. Data on transistors included.

PANELS with 2 power transistors similar to OC28 on each board—components 2 boards (4 x OC28) 50p, P. & P. 6p.

9 OA5, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long leaded on panels 13in x 4in. 4 for £1, P. & P. 25p.

709C OPERATIONAL AMPLIFIER T05

8 lead I.C. 1 of 50p. 50 off 35p. 100 off 20p.

250 MIXED RESISTORS 62p
1/2 & 1 watt.

150 MIXED HI STABS 62p
1/2 & 1 watt 5% & better.

QUARTZ HALOGEN BULBS

With long leads. 12V 55W for car spot lights, projectors, etc. 50p each. P. & P. 5p.

GPO EXTENSION TELEPHONES

with dial but without bell. 95p each. P. & P. 30p. £1.75 for 2. P. & P. 50p.

BARGAIN RELAY OFFER

Single pole change over silver contacts 25V to 50V. 2.5k Ω coil. 8 for 50p. P. & P. 5p.

KEYTRONICS mail order only
44 EARLS COURT ROAD
LONDON, W.8 01-478 8499



YOURS FREE FOR 7 DAYS

The 'New Picture-Book' way of learning BASIC ELECTRICITY (5 VOLS.) BASIC ELECTRONICS (6 VOLS.)

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

This carefully planned series of manuals has proved a valuable course in training technicians in Electricity, Electronics, Radio and Telecommunications.

WHAT READERS SAY

"HOW UNDERSTANDABLE"

Pleased to say how understandable your books are, I now have a sound knowledge of the subject. A.K., Hull.

"INVALUABLE"

Invaluable for my training as a Technician. W.J., Stockport.

"A MATHEMATICAL IDIOT"

They have an easy approach to learning that a mathematical idiot like myself can easily understand. K.L.Y., Ashton-u-Lyme.

■ To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

■ Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY £4.50 Cash Price, or Down Payment of £1.00 followed by 4 fortnightly payments of £1.00 each. Total £5.00. BASIC ELECTRONICS £5.40 Cash Price, or Down Payment of £1.00 followed by 5 fortnightly payments £1.00 each. Total £6.00. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

■ Tick Set required (Only one set allowed on free trial)

■ BASIC ELECTRICITY BASIC ELECTRONICS
Prices include Postage and Packing.

■ Signature _____ (If under 21 signature required of parent or guardian)

■ NAME
BLOCK LETTERS _____

■ FULL POSTAL
ADDRESS _____

POST NOW FOR THIS OFFER!!

A TECH-PRESS PUBLICATION

Everyday Electronics, January 1972

DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work, £2 less plus; £2-26 with fitted 13 amp plug; £2-40 with fitted 15 amp plug, plus 23p P. & I.



MULTI-SPEED MOTOR

Six speeds are available 500, 860 and 1,100 r.p.m. and 8,000; 12,000 & 15,800 r.p.m. shaft is 1/2 in. diameter 230/240v. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor size approx. 2 in. dia. x 5 in. long. Price 88p plus 23p postage and insurance.



20 AMP ELECTRICAL PROGRAMMER

Learn in your sleep! Have Radio playing and kettle boiling as you awake—switch-on lights to ward off intruders—have warm house to come home to. All these and many other things you can do if you invest in an Electrical Programmer. Made by the famous Smiths Instrument Company. This is essentially a 230/240 volt mains operated clock and a 20 amp Switch, the switch-off time of which can be delayed up to 12 hours (continuously variable not stepped). Similarly the switch-on time can be delayed. This is a beautiful unit, size 5 1/2 x 3 1/2 x 2 1/2 in. deep. Metal encased, glass fronted with chrome surround. Offered at £2-40 plus 23p postage and insurance.




RESETTABLE FUSE

How long does it take you to renew a fuse? Time yourself when next one blows. Then reckoning your time at £1 per hour see how quickly our resettable fuse (auto circuit breaker) will pay for itself. Price only £1 each or £11 per dozen, specify 5, 10 or 15 amp—simply fit in place of switch.



SPARTAN Portable RADIO

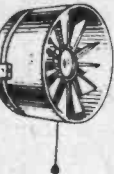Long and medium wave, 7 transistor, size 6in. x 4in. x 1 1/2in. with larger than usual speaker giving very good tone. Built-in ferrite aerial and telescopic aerial for distant stations. A real bargain complete with leather case, carrying sling, earplug and case £3-75 plus 26p post and ins.



EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchens, bath-rooms, factories, changing rooms, etc., it's so quiet it can hardly be heard. Compact, 5 1/2" casing with 5 1/2" fan blades. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector, and fixing brackets. £2 plus 36p post and ins.

MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 50p. Postage 10p for first one then 5p for each one ordered.



KITS FOR PREVIOUS PROJECTS

Kits of parts available as follows:—

HOME SENTINEL INTRUDER ALARM
Electronic Components with case £3-75

SNAP INDICATOR
All components but not case or battery 75p.

WINDSCREEN WIPER CONTROL
All components including metal for chassis £1-50.

RECORD PLAYER
All components, but not case, loudspeaker, record deck or pick-up £4-50


DEMO DECK
Components as listed 26 POST PAID

FUZZ BOX
All parts including box £1-85.

PHOTOGRAPHIC COLOUR TEMPERATURE METER
Electronic components less case £2-65


CAPACITOR DISCHARGE CAR IGNITION

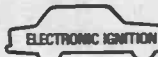This system which has proved to be amazingly efficient and reliable was first described in the Wireless World about a year ago. We can supply kit of parts for improved and even more efficient version (P.W. June), price £4-95. When ordering please state whether for positive or negative systems. Plus 30p post.



RADIO STETHOSCOPE

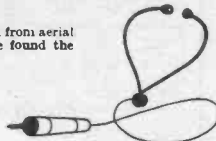Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. £2—twin stethoscope instead of earpiece 75p extra post and ins. 20p.



STANDARD WAFER SWITCHES

Standard size 1 1/2 wafer—silver-plated 5-amp contact, standard 1" spindle 2" long—with locking washer and nut.

No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way
1 pole	40p	40p	40p	40p	40p	40p	40p	40p	40p
2 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p
3 poles	40p	40p	40p	40p	70p	70p	70p	95p	95p
4 poles	40p	40p	40p	70p	70p	70p	70p	£1-20	£1-20
5 poles	40p	40p	70p	70p	95p	95p	95p	£1-45	£1-45
6 poles	40p	70p	70p	95p	95p	95p	95p	£1-70	£1-70
7 poles	70p	70p	95p	£1-20	£1-20	£1-20	£1-20	£1-95	£1-95
8 poles	70p	70p	95p	£1-20	£1-20	£1-20	£1-20	£2-20	£2-20
9 poles	70p	70p	95p	95p	£1-45	£1-45	£1-45	£2-45	£2-45
10 poles	70p	70p	95p	£1-20	£1-45	£1-45	£1-45	£2-70	£2-70
11 poles	70p	95p	95p	£1-20	£1-70	£1-70	£1-70	£2-95	£2-95
12 poles	70p	95p	95p	£1-20	£1-70	£1-70	£1-70	£3-20	£3-20

TANGENTIAL HEATER UNITS

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW element and 1kW element allowing switching 1, 2 and 3kW and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only need control switch. £3-50. 2kW Model as above except 2 kilowatts £2-50. Don't miss this. Control Switch 35p. P. & P. 40p.



ASTRON RADIO & TEMPERATURE COMPARATOR

FEATURED IN THIS ISSUE

To receive these kits quickly send quoted approx. price and any change due will be refunded.



HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting aimed and signs, Signalling, etc. Price from makers probably over £10 each. Special snip price £5-75 plus 26p post and insurance. Don't miss this terrific bargain.



INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A once-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade devices, definitely not sub-standard or seconds. 4 of the ICs are single silicon chip GP amplifiers. The 5th is a monolithic NPN matched pair. Regular price of parcel well over £5. Full circuit details of the ICs are included and in addition you will receive a list of many different ICs available at bargain prices 55p upwards with circuits and technical data of each. Complete parcel only £1 post paid. **DON'T MISS THIS TERRIFIC BARGAIN.**



BATTERY CONDITION TESTER

Made by Mallory but suitable for all batteries made by Ever Ready and others, most of which are zinc carbon types but also mercury manganese—nicad—silver oxide and alkaline batteries may be tested. The tester puts a dummy load on the battery and the meter scale indicates the condition depending upon which section the pointer rests. The section reads "replace", "weak" or "good". The tester is complete in its case, size 3 1/2" x 6 1/2" x 2" with leads and prods. Price £1-75 plus 20p postage.

Where postage is not stated then orders over £5 are post free. Below £5 add 20p. Semi-conductors add 5p post. Over £1 post free. S.A.E. with enquiries please.

100 THINGS YOU CAN MAKE

Send S.A.E. today for list of 100 constructor projects — instruments — alarms — counters — locks — radios, etc., etc.

THERMOSTATS

Type "A" 15 amp. for controlling room heaters, greenhouses, airing cupboard. Has spindle for pointer knobs. Quickly adjustable from 80-80°F. 40p. Calibrated dial 20p extra. Suitable box for wall mounting 25p.

Type "B" 15 amp. This is a 17in. long rod type made by the famous Sanvic Co. Spindle adjusts this from 60-85°F. Internal screw alters the setting to this could be adjustable over 30° to 1000°F. Suitable for controlling furnace, oven, kiln, immersion heater or to make flame-stat or fire alarm. 43p plus 12 1/2p post and insurance.

Type "D" We call this the Ice-stat as it cuts in and out at around freezing point. 2/3 amps. Has many uses one of which would be to keep the loft pipes from freezing. If a length of our blanket wire (16 1/2 50p) is wound round the pipes. 40p.

Type "E". This is standard refrigerator thermostat. Spindle adjustments cover normal refrigerator temperature. 60p

Type "F". Glass encased for controlling the temp. of liquid—particularly those in glass tanks, vats or sinks—thermostat is held (half submerged) by rubber nucker or wire clip—ideal for flat tanks—developers and chemical baths of all types. Adjustable over range 50° to 160° F. Price 80p



TREASURE TRACER

Complete Kit (except wooden battens) to make the metal detector as the circuit in Practical Wireless August issue. £2-95 plus 20p post and insurance.

DRILL CONTROLLER NEW IKW MODEL

Electrically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1-50 plus 13p post and insurance. Made up model also available. £2-25 plus 13p post and p.



HIGH ACCURACY THERMOSTAT

Uses differential comparator I.C. with thermister as probe. Designer claims temperature control to within 1/7th of a degree. Complete kit with power pack £5-50.

AUTO-ELECTRIC CAR AERIAL

with dashboard control switch—fully extendable to 40in. or fully retractable. Suitable for 12v. positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. £5-75 plus 26p post and ins.



AUTO-LITE

as circuit in this month's issue Practical Wireless. Kit of parts £1-20 post paid.

TOGGLE SWITCH

3 amp. 250v. with fixing ring 7 1/2p each, 75p doz.

CAR ELECTRIC FLUG

Fits in place of cigarette lighter. Useful method for making a quick connection into the car electrical system. 88p each or 10 for £3-42.

ROCKER SWITCH

15 amp self-fixing into an oblong hole. Size approximately 1" x 1" 6p each, 10 for 64p.

MAINS RELAY BARGAIN

Special this month are some single, double and treble pole changeover relays. Contact rated at 15 amps. Operating coil wound for 240V A.C. Good British Make. Ex-unused equipment. Size approx. 1 1/2" x 1". Open construction
Single pole 25p each 10 for £2-25
Treble pole 85p each 10 for £3-18



BALANCED ARMATURE UNIT

500 ohm, operates speaker or microphone, so useful in intercom or similar circuits, 33p each, £3-50 doz.



J. BULL (ELECTRICAL) LTD.

(Dept. E.E.) 7 Park Street, Croydon CRO 1YD

Callers to: 102/3 Tamworth Road, CROYDON

Everyday Electronics, January 1972

Build yourself a TRANSISTOR RADIO

NEW! ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND. VHF AND LOCAL STATIONS AND AIRCRAFT BAND

Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mw Transistors. Car Aerial and Tape Record Sockets. Switched Earpiece Socket complete with Earpiece. 10 Transistors plus 3 Diodes. 7in x 4in Speaker. Air Spaced ganged Tuning Condenser with VHF section. Volume on/off, Wave Change and Tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

Total building cost

£8-50


P. P. & Ins. 50p

(Overseas P. & P. £1)



ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL

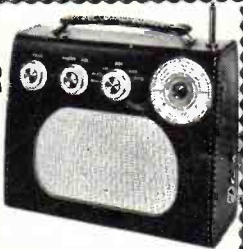

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mw transistors. Car aerial and Tape record sockets. Selectivity switch. Switched earpiece socket complete with earpiece. 8 transistors plus 3 diodes. 7in. x 4in. Speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts).

Total building cost **£6-98** P. P. & (Overseas P. & P. £1) Ins. 41p.

Exclusive to readers of "EVERYDAY ELECTRONICS" "EVERYDAY SEVEN"



MEDIUM and LONG WAVE PORTABLE.


Specially designed circuit for easy construction incorporating 7 transistors and 2 diodes, air spaced tuning capacitor, push pull output using 600 mw transistors, heavy duty loud-speaker for quality sound and room filling volume, internal Ferrite Rod aerial, Volume/on/off control, tuning control and wave change switch. Handsome, strongly made wooden case, size 11 1/2" x 7 1/2" x 3 1/2" with carrying handle and black knobs with spun silver inserts. The ideal radio for those who are comparatively inexperienced in electronic construction. Easy build plans are supplied free with parts or available separately for 25p.

Total building costs **£4-98** P. P. & (Overseas Post £1) Ins. 41p

ROAMER SIX

6 Tunable Wavebands: MW, LW, SW1, SW2, Trawler band plus an extra M.W. band for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Easy build plans and parts price list 15p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

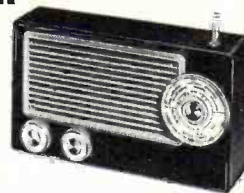Total building costs **£3-98** P. P. & (Overseas P. & P. £1) Ins. 26p



POCKET FIVE

3 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc.

7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5 1/2 x 1 1/2 x 3 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-23** P. P. & (Overseas P. & P. 65p) Ins. 21p



TRANSONA FIVE

NOW WITH 3in SPEAKER

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone 3in. moving coil speaker. Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-50** P. P. & (Overseas P. & P. 65p) Ins. 22p




TRANS EIGHT

8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

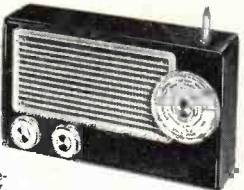Total building costs **£4-48** P. P. & (Overseas P. & P. £1) Ins. 31p



NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAM. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT.

COMPONENTS INCLUDE:

Tuning Condenser: 2 Volume Controls: 2 Slider Switches: 4*2 1/2" Speaker: Terminal Strip: Ferrite Rod Aerial: 3 Plugs and Sockets: Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1/2" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction

All parts including Case and Plans **£5-50** P. P. & (Overseas P. & P. £1) Ins. 31p



FULL AFTER SALES SERVICE

• Callers side entrance Barratts Shoe Shop
• Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER TEN EVERYDAY SEVEN
ROAMER EIGHT TRANS EIGHT
TRANSONA FIVE ROAMER SIX
POCKET FIVE EDU-KIT

Parts price list and plans for

Name

Address

EE.3

HENRY'S RADIO LIMITED

ENGLAND'S LEADING ELECTRONIC CENTRES

HENRY'S RADIO

HI-FI · ELECTRONIC COMPONENTS · TEST · PA · DISCOTHEQUE · LIGHTING · MAIL ORDER

10th EDITION CATALOGUE



350

pages fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information

PRICE 55p
POST PAID
(40p FOR CALLERS)

10,000

Stock lines at Special Low Prices and Fully Guaranteed

PLUS! FIVE 10p VOUCHERS FOR USE WITH PURCHASES

Send to this address—Henry's Radio Ltd., (Dept. EE), 3 Albemarle Way, London, E.C.1.—for catalogue by post only.

All other mail to "303", see below

A NEW HENRY'S CATALOGUE IS A MUST FOR ELECTRONICS TODAY!

HOME EQUIPMENT



AF105 50k/V multimeter (illus.). Price £8-50, p.p. 20p. Leather case £1-42.
200H 20k/V. Price £3-87, p.p. 20p. Case 62p.
500 30k/V multimeter. Price £8-87, p.p. 20p. Leather case £1-50.
THL33 2k/V. Price £4-12, p.p. 15p. Leather case £1-15.
TE55 Valve voltmeter. Price £17-50, p.p. 40p.
SE250B Pocket pencil signal injector. Price £1-75, p.p. 15p.



SE500 Pocket pencil signal tracer. Price £1-50, p.p. 15p.
TE20D RF generator. Price £15, p.p. 40p.
TE22D Matching audio generator. Price £17, p.p. 40p.
TE15 Grid dip meter. Price £12-50, p.p. 40p.
T03 Scope 3 in. tube. Price £37-50, p.p. 50p.
TE22 Audio Generator. Price £17, p.p. 40p.
CI-5 Pulse Scope. £39-00, p.p. 50p.
U4341 AC/DC Multitester and transistor tester. AC & DC Current. In steel case. Price £10-50, p.p. 15p.
TMK 500 30k/V Multitester. Price £8-87, p.p. 13p. Leather case £1-98.
LARGEST RANGE of Panel Meters, Edge Meters and Test Equipment of every sort. Full details in latest catalogue—see above.

LOW COST HI-FI SPEAKERS



E.M.I. Size 13 1/2" x 8 1/2". Large Ceramic Magnet. TYPE 150 6 watt, 3, 8 or 15 ohms £2-12. Post 22p.
TYPE 150TC Twin cone version £2-75. Post 22p.
TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. £3-50. Post 25p.
TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms. £7-50. Post 28p.



POLISHED CABINETS For 150, 150TC and 450 £4-50. Post 30p.

SPEAKER KITS

WHARFEDALE 4-8 ohms. PEERLESS 8 ohm Systems.
Unit 3. 8" 15W £10-50. 20-3 8" 30W £11-25.
Unit 4. 12" 25W £14-25. 20-3 8" 40W £16-75.
Unit 5. 12" 35W £20-25. 4-30 12" 12" 40W £22-75.
GOODMANS DIN 20 KIT 20W 4ohm £11-75
Carriage etc. 50p each or 75p per pair for Kits.

STEREO HEADPHONES

With stereo jack. Post 15p.
Dulci SH650D £2-25
Rotel RH600 £4-67
Akai ASE95 £5-50
Eagle SE30 £5-97
Koss K711 £7-97
Pioneer SE30 £9-45
Koss PRO4A £15-50



HI-FI TO SUIT EVERY POCKET



SAVE UP TO 40% ON LIST UP TO £100 PRICES PLUS FREE 'BIB' Groov-Clean Record Cleaner Value £1-99

ROTA 1500. 5 + 5 watts. Garrard 2025TC with 9TAHC diamond ceramic. Plinth/Cover. 5DL1 Compact Speakers. Size 15 x 10 1/2 x 7-7/8. SAVE £47-75 Carr. £27

TELETON '206', Garrard SP25 Mk. 111, Goldring G800 Series Cart., Plinth/Cover. New 15 watt Quality SDL1 Bookshelf Speaker Systems, all leads, etc. £30-00 SAVE £54-95 Carr. £2

TELETON F2000, Med. Wave, Stereo FM Tuner Amplifier, Garrard 2025TC, 9TAHC Diam., Plinth/Cover. New 15 watt Speaker Systems as above, all leads, etc. SAVE £36 £59-95 Carr. £2

ROTA 2200 10 + 10 Watt. Garrard SP25 111/G800H, Plinth/Cover. New 15 watt SDL2 Twin Speaker Systems, all leads, etc. SAVE £32 £61-00 Carr. £2

LOW PRICES PLUS 12 MONTHS GUARANTEE & DEMONSTRATIONS

FREE LATEST SPECIAL PRICE LIST & STEREO SYSTEMS Ref. 16/17

FREE BROCHURES * P.A., DISCO AND LIGHTING No. 18 * TRANSISTORS, I.C.'s No. 36

20 WATT I.C. AMPLIFIER Toshiba 20 watt Power Amplifier, £4-57. Toshiba Pre-Amplifier I.C., £1-50. Data and suggested circuits No. 42, 19p. SL403D 3 watt I.C. with 8 page data and circuits £1-50. IC12 6 watt I.C. £2-50.

NIXIE TUBES (post 15p per order) XN3 or XN13 0-9 side view with data sheet, 85p each. GN4 end view 0-9 with socket and data, £1-75. All I.C.'s for Digital Clocks in stock. HENRY'S CLOCK CIRCUIT No. 29/2 15p.

BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS 300 kc/s BAND-WIDTH, PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION, MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7. Tuning meter £1-75. TOTAL £6-97, p.p. 20p. Cabinet 100p. Decoder Kit £5-97. Mains unit (optional) Model PS900 £2-47. Mains unit for Tuner and Decoder PS1200 £2-62.



HIGH QUALITY SILICON AMPLIFIERS AND PRE-AMPLIFIERS

Self powered Silicon—FET Pre Amplifiers. Push button selectors, tape record/play, adjustable levels, drive up to 4 x PA25 or 2 x PA50 per channel.

FET 9/4 Mono or single channel. All facilities plus microphone. Mixing. Price £12-50. FET 154 Stereo with all facilities, magnetic cart. input etc. Price £16-50

SILICON POWER AMPLIFIERS RMS OUTPUT PA 25 25 watts into 8 ohms £7-50. PA 50 50 watts into 4 ohms £9-50. MU442 Power Supply for 1 or 2 PA25's or 1 only PA50, £6-00. Post 20p. FREE BROCHURE No. 25 ON REQUEST. NO SOLDERING—ALL UNITS INTERCONNECTING. ON DEMONSTRATION AT "356".

TERRIFIC SAVINGS!

GARRARD - BSR - THORENS GOLDRING - PIONEER CONNOISSEUR



CHASSIS (P)	ASSEMBLED (P)	ASSEMBLED (P)
(less cartridge)	(less cartridge with cover)	(with cart. P & C)
*SP25 Mk111 £11-30	MP60(TDIP) £17-75	2025TC/9TAHCD £13-95
†AP76 £19-97	HT70 PC £24-00	
●MP60 £11-30	PL12AC £36-50	SP25/3-G800H £18-95
●MP610 £15-15	GL72 PC £36-95	
●HT70 £16-60	GL75 PC £43-75	AP76-G800 £29-95
GL72 £22-95	TD150AB/ £45-50	
GL75 £28-97	TX11 £32-25	
Dual 1215 £39-00	BD2	

CHASSIS WITH CARTRIDGE (P) SPECIAL PRICE WITH CARTRIDGE—ADD
*2025TC/9TAHCD £9-50 All magnetic Recommen-
*3000/9TAHCD £9-90 dended Y940 (=AD-
TEAK *P11T Std. £3-00 76K) £3-25; AT66 £4-95;
PLINTH *BN1 Deluxe £8-00 G850 £4-25; AT21 £9-60;
WITH *P4/T4 Std. £4-25 G800 or G800H £6-55;
COVER *BN4 Deluxe £8-00 M44-7 or C £7-45; 909X
(State *P6/T6 Std. £3-00 £7-32
deck) *BSR Deluxe £6-25
Post etc. = Chassis 50p, with plinth/cover 70p, Plinth/Cover 30p Carts. 15p.

300mW TRANSISTOR AMPLIFIER MODEL 4-300

Fully assembled 4TR Amplifier. Size 5 1/2 x 1 1/2 in. 1-10mV adjustable sensitivity. Output 3-8 ohms. Fitted Vol. control. 9 volt operated. Thousands of uses plus low cost. Price £1-75, p.p. 15p (or 2 for £3-25, p.p. 15p).



SINCLAIR PROJECT 60 PACKAGE DEALS — SAVE POUNDS!

2 x Z30 amplifier, stereo, 60 pre-amp, PZ5 power supply, £16-75, Carr. 40p. Or with PZ6 power supply £18-25. Carr. 40p. 2 x Z50 amplifier, stereo 60 pre-amp, PZ8 power supply £20-25, Carr. 40p. Transformer for PZ8 £2-45 extra. NEW! Project '605' stereo system £20-97. Any of the above with Active Filter unit add £4-75 or with pair Q16 speakers add £16. Also new FM Tuner £20-25. 2000 Amplifier £24-50, p.p. 50p. 3000 Amplifier £31-50. Also IC12 £2-50.

"BANDSPREAD" PORTABLE TO BUILD

Printed circuit all transistor design using Mullard RF/IF Module. Medium and long Wave bands plus Medium Bandspread for extra selectivity. Also low motion geared tuning, 600 mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance. TOTAL COST TO BUILD £7-98. P.P. 32p (Battery 22p). All parts sold separately—Leaflet No. 2. '77' PORTABLE (as previously advertised) £6-98, p.p. 35p from stock—Leaflet No. 1.



MORE OF EVERYTHING AT LOW PRICES ALWAYS FROM HENRY'S * Components in stock for most published designs—send large S.A.E. with list for parts quote for your circuit.

Electronic Components, Audio and Test Gear Centre
356 EDGWARE ROAD, LONDON, W.2.
Tel: 01-402 4736

High Fidelity Sales & Demonstrations Centre
354 EDGWARE ROAD, LONDON, W.2.
Tel: 01-402 5854

P.A., Disco & Lighting Centre
309 EDGWARE ROAD, LONDON, W.2.
Tel: 01-723 6963

Mail Orders, Special Bargain Shop, Industrial Sales
303 EDGWARE ROAD, LONDON, W.2.
Tel: 01-723 1008/9

"354" & "356" OPEN SIX FULL DAYS A WEEK 9 am to 6 pm MONDAY TO SATURDAY