

An exciting hobby.... for everyone

# everyday electronics

JUNE 74

20p

## FREE ENTRY COMPETITION

Win a —  
CHINAGLIA  
MULTIMETER



3 EASY TO BUILD PROJECTS

ee  
TEST GEAR FIVE



R.F. SIGNAL GENERATOR

30m 8160m




AMATEUR BANDS RECEIVER
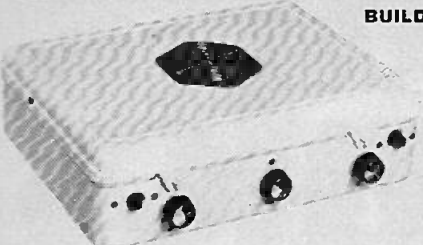
# NEW EDU-KIT MAJOR

COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT.

BUILD THESE PROJECTS WITHOUT  
SOLDERING IRON OR SOLDER.



Total Building Costs

**£7-23** P.P. & Ins. 44p.  
(Overseas P. & P. £1-85p.)

(+ 10% VAT 12p)

★ 4 Transistor Earpiece Radio ★ Signal Tracer ★ Signal Injector ★ Transistor Tester NPK-PNP ★ 4 Transistor Push Pull Amplifier ★ 5 Transistor Push Pull Amplifier ★ 7 Transistor Loudspeaker Radio MW/LW ★ 5 Transistor Short Wave Radio ★ Electronic Metronome ★ Electronic Noise Generator ★ Batteryless Crystal Radio ★ One Transistor Radio ★ 2 Transistor Regenerative Radio ★ 3 Transistor Regenerative Radio ★ Audible Continuity Tester ★ Sensitive Pre-Amplifier.

★ 24 Resistors ★ 21 Capacitors ★ 10 Transistor★ 31 loudspeaker ★ Earpiece ★ Mica Baseboard ★ 3 12-way connectors ★ 2 Volume controls ★ 2 Slider Switches ★ 1 Tuning Condenser ★ 3 Knobs ★ Ready Wound MW/LW/SW Coils ★ Ferrite Rod ★ 6 1/2 yards of wire ★ 1 yard of sleeving, etc. ★ Parts price list and plans 50p (FREE with parts).

# NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT



Nine Transistors.

9 Tunable wavebands as Roamer Ten.

Built in ferrite rod aerial for MW/LW. Retractable chrome plated telescopic aerial for VHF and SW. Push Pull output using 600 mw transistors. 9 Transistors and 3 diodes, tuning condenser with V.I.F.P. section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange control. Attractive all white case with red grille and carrying strap. Size 9 1/2" x 7" x 2 1/2" approx. Parts Price list and Plans 30p (FREE with parts)

Total Building Costs

**£6-95** P.P. & Ins. 44p.  
(Overseas P. & P. £1-85p.)

(+ 10% VAT 69p)

# ROAMER TEN

with VHF including aircraft. 10 Transistors.

Latest 3 watt Ferrite Magnet Loudspeakers, 9 Tunable Wavebands. MW1, MW2, LW, SW1, SW2, SW3. Trawler Band. VHF and Local Stations also Aircraft Band. Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600 mw Transistors. Car Aerial and Tape Recording Sockets. 10 Transistors plus 3 Diodes. Ganged Tuning Condenser with V.I.F.P. section. Separate coil for Aircraft Band. Volume on/off. Wave change and tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 80p (FREE with parts). Total building costs



**£8-50** P.P. & Ins. 52p.  
(Overseas P. & P. £1-85p.)

(+ 10% VAT 85p)

# NEW EVERYDAY SERIES

Build this exciting New series of designs

E.V. 5 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and loudspeaker. Attractive case with red speaker grille. Size 9" x 5 1/2" x 2 1/2" approx. Parts price list and Plans 15p. Free with parts.

Total Building Costs **£2-73** P.P. & Ins. 30p

(Overseas P. & P. £1-25p.)

(+ 10% VAT 27p)

E.V. 6 Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc., MW/LW coverage. Push Pull output. Parts price list and Plans 15p. Free with parts.

Total Building Costs **£3-60** P.P. & Ins. 30p

(Overseas P. & P. £1-25p.)

(+ 10% VAT 36p)

E.V. 7 Case and looks as above. 7 Transistors and 2 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" loudspeaker. Parts price list and easy build plans 20p. Free with parts.


Total Building Costs **£4-08** P.P. & Ins. 31p

(Overseas P. & P. £1-85p.)

(+ 10% VAT 40p)
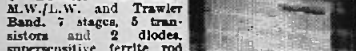
# POCKET FIVE

3 Tunable wavebands. M.W./L.W. and Trawler Band. 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, moving coil loud speaker, attractive Black and Gold Case. Size 5 1/2" x 1 1/2" x 3 1/2" approx. Plans and parts price list 15p. (Free with parts).



Total Building Costs **£2-28** P.P. & Ins. 26p  
(Overseas P. & P. £1-25p.)

(+ 10% VAT 22p)

# ROAMER EIGHT Mk 1 NOW WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mw transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt Ferrite Magnet Loudspeakers. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

Total Building Costs **£6-98** P.P. & Ins. 47p

(Overseas P. & P. £1-85p.)

(+ 10% VAT 69p)

# TRANSONA FIVE

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and parts price list 15p (Free with parts).



Total Building Costs **£2-50** P.P. & Ins. 26p  
(Overseas P. & P. £1-25p.)

(+ 10% VAT 25p)

# TRANS EIGHT

8 TRANSISTORS and 3 DIODES


6 Tunable Wavebands; MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 8in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

Total Building Costs **£4-48** P.P. & Ins. 33p

(Overseas P. & P. £1-25p.)

(+ 10% V.A.T. 44p)

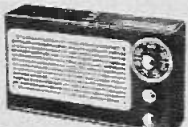• Callers side entrance "Lavells" Shop  
• Open 10-1, 2.30-4.30 Mon.-Fri.-9-12 Sat.



"EDU-KIT"

Build Radios, Amplifiers, etc. from easy to follow diagrams. Five

units including master unit to construct

Components include:

Tuning Condenser; 2 Volume Controls; 2 Slider Switches; Fine 3" Tone Moving Coil Speaker; Terminal Strip; Ferrite Rod Aerial; Battery Clips; 4 Tap Leads; 10 Transistors; 4 Diodes; Resistors; Capacitors; Three 1/2" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).

Total Building Costs **£5-50** P.P. & Ins. 33p

(Overseas P. & P. £1-85p.)

(+ 10% VAT 59p)

# ROAMER SIX Case and looks as Trans-Eight

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3, Trawler band plus an Extra Medium waveband for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 8in. Speaker. 8 stages-6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Plans and parts price list 25p (FREE with parts).

Total Building Costs **£3-98** P.P. & Ins. 31p

(Overseas P. & P. £1-85p.)

(+ 10% VAT 59p)

# RADIO EXCHANGE CO

61a HIGH STREET, BEDFORD, MK40 1SA Tel. 0234 52367

Reg. no. 788372

I enclose £..... for

Name.....

Address.....

(Dept. E.E.6.)



# YES, SIR!

... there are over  
**8,000 electronic  
components  
WITHIN A FEW  
FEET OF YOU!**



**That is, assuming you are on the telephone, and  
that you don't keep it at the top of the garden!**

*If you're not on the phone, the distance is between you and your nearest post box*



**240 pages  
Over 8,000 items  
Nearly 2,000 pictures**

The first thing you need, to enable you to get all your components quickly, easily, economically, is a copy of the 240 page Home Radio Components Catalogue. Apart from listing the vast range of lines we stock, the catalogue contains details of our popular Credit Account Service and many other items of useful information. For example, as there are several ways of ordering, several ways of paying and several ways of delivery, the pros and cons of all the methods are clearly set out in the catalogue. We have the reputation of providing the best-organised service ever offered to buyers of electronic components. Of course, to make good use of this service you need the catalogue. It costs 55 pence, plus 22p post and packing, and when you receive your copy you'll agree it's the best investment you've made for a long time. Moreover with the catalogue we give you 10 Vouchers each worth 5 pence against orders, an up-to-date Price List and a Bookmark with a useful list of technical abbreviations.

**Send off the coupon today. Your  
catalogue will come by return post.**

**Only 55p. plus 22p POST AND PACKING**

**POST THIS COUPON**  
with cheque or P.O. for 77p.

The price of 77p applies only to customers  
in the U.K. and to BFPO addresses

Name \_\_\_\_\_

Address \_\_\_\_\_

**HOME RADIO (Components) LTD. (Regn. No. Lond  
Dept. EE, 234-240 London Road, Mitcham CR4**









### AUDIOTRONIC Model ATM1

Top value 1,000 opv pocket multi-meter. Ranges—0/10/50/250/1,000 volt AC and DC. DC current 0/1mA/100mA. Resistance 0/150k ohms. Decibels: -10 to +22dB. Size 90 x 60 x 28mm. Complete with test leads.

**OUR PRICE £2.95** P&P 15p

### AUDIOTRONIC Model ATM5

Jewel movement, attractively moulded case with edgewise ohms adjustment. Ranges: 0.3/1.5/150/300/1200V AC. (2500 opv). 0.4/30/300/600V DC. (5000 opv). 0.300 uA/0.300mA DC. Resistance: x 10, 5 & x 100. -10 to +16dB. Supplied with battery test leads and data booklet. Size: 121 x 73 x 29mm.

**OUR PRICE £3.50** P&P 15p

### MODEL C1092 MULTIMETER

Features 5,000 opv jewel movement and a good selection of range functions. Edgewise ohms adjustment. Ranges—0.3/1.5/150/300/1,200V AC (2,500 opv). 0.6/30/300/600 V DC (5,000 opv). DC current 0.300/300mA. Resistance: R x 10, R x 1,000. -10 to +16dB. Complete with battery, test leads and data booklet. Size: 120 x 73 x 28mm.

**OUR PRICE £3.75** P&P 35p

### MODEL TH12

20,000 opv. Overload protection. Slide switch selector. 0/0.25/2.5/10/50/150/1000V DC. 0/10/50/250/1000V AC. 0-50uA/250mA. 0-20k/2 Megohms.

**OUR PRICE £5.95** P&P 15p

### HIKOKI Model 720X VOM

A versatile, accurate measuring instrument. 20,000 opv. 0/5/25/100/500/1000V DC. 0/10/50/250/1000V AC. 0-50uA/250mA. 0-20k/2 Megohms.

**OUR PRICE £5.97** P&P 20p

### MODEL PL436

20,000 opv DC. 8000 opv AC. Mirror scale. 6.3/12/30/120/600V DC. 3/30/120/600V AC. 60/600uA/60/600mA. 10/100k/1 Meg/10 Meg Ohm. 20 to 46dB.

**OUR PRICE £6.97** P&P 15p.

### U4323 MULTIMETER

20,000 opv. Simple unit with audio/IF oscillator. Suitable for general receiver tuning. Ranges: 0.5/2.5/10/50/250/500/1000V DC. 2.5/10/15/250/500/1000V AC. 0.05/0.5/5/50/500mA DC. Resistance: 5/50/500 ohms/5/10/100k ohms/1 Meg Ohm. Supplied in carrying case complete with test leads.

**OUR PRICE £7.00** P&P 20p

### MODEL HIKOKI 730X

30,000 opv. Overload protection. \$30 60 300 600 1200V DC. 12 60 600 1200V AC. 120 uA 30mA 300mA. 2K 200K. 2 Meg Ohm. 10 to 63dB.

**OUR PRICE £7.50** P&P 15p.

### MODEL TE300

30,000 opv. Mirror scale. Overload protection. 0/0.6/3/15/60/300/1200V DC. 0/5/30/120/600/1200V AC. 0/30uA/6mA/60mA/300mA/600mA. 0/8k/50k/800k/5 Meg Ohms. -20 to +65dB.

**OUR PRICE £7.50** P&P 15p

### U4324 MULTIMETER

High sensitivity, overload protected. 20,000 opv. Ranges: 0.6/1.2/3/12/30/60/120/600/1200V DC. 3/6/15/60/150/300/600/900V AC. Current: 0.06/0.6/6/60/600mA. 3A DC. Resistance: 0.3/3/30/300/1000/5000 ohms/0.5/5/50/500k ohms/5 Megohms. Decibels: -10 to +12dB. Size 167 x 98 x 63mm. Supplied complete with test leads, spare diode and instructions.

**OUR PRICE £8.00** P&P 20p

### TMK MODEL TW50K

46 ranges, mirror scale. 50kV/DC 50kV/AC. DC Volt: 0.125/0.25/1/2.5/5/10/25/50/125/250/500/1000. AC Volt: 1.5/3/10/25/50/125/250/500/1000. DC current: 25/50/100/250/500/1000V. AC current: 0.5/2.5/5/10/25/50/100/250/500/1000. Resistance: 10k/100k/1 Meg/5 Meg ohms. -20 to +81.5dB.

**OUR PRICE £8.50** P&P 17p

### U4325 MULTIMETER

20,000 opv. Overload protected. Ranges: 75mV/2.5/10/25/100/250/500/1000V DC. 2.5/10/25/100/250/500/1000V AC. Current: 50uA/1.5/25/100mA/0.5/2.5/5/25/100mA. 0.5/2.5/5/25/100mA. Resistance: 0.3/3/30/300k ohms. Size: 205 x 110 x 84mm. Supplied complete with leads, crocodile clips and steel carrying case.

**OUR PRICE £8.75** P&P 20p

### U91 Clamp VOLT AMMETER

For measuring AC volt and current without breaking circuit. Ranges: 300/600V AC. Current: 10/25/100/250/500A. Accuracy 5%. Size 283 x 94 x 36mm. Complete with carrying case, leads and fuses.

**OUR PRICE £10.50** P&P 20p

### U4312 MULTIMETER

extremely sturdy instrument for general electrical use. 657 opv. 0/0.3/1.5/7.5/30/60/150/300/600/900V DC & 75mV/0.3/1.5/7.5/30/60/150/300/600/900V AC. 0/300uA/1.5/15/150/600mA/1A. 3A DC. 0/1.5/15/60/150/500/1000V AC. 0/200/3k/30k ohms. DC accuracy 1%. AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions.

**OUR PRICE £9.75** P&P 25p

### MODEL 500

30,000 opv with overload protection. Mirror scale. 0/0.5/2.5/10/25/100/250/500/1000V DC. 0/2.5/10/25/100/250/500/1000V AC. 0/50uA/500uA. 500mA. 12A DC. 0/80k/6 meg/60 megohms.

**OUR PRICE £13.95** Carr. paid  
Leather case for above £1.75

### HIKOKI 750X VOLT-OHM-MILLIAMMETER

43 ranges: 0-0.3/0.6/1.5/3/6/12/30/60/150/300/600/1200V DC. 0-3/6/15/30/60/120/300/600/1200V AC. Current: 0-30/60uA/1.5/3/15/30/150/300mA/6/12A. Resistance: 0-3200k/320Megohms. Overload protected. -10 to +17dB. Output: 0.3/6/15/30/60/120/300V. Accuracy: ±3% DC, ±4% AC. Sensitivity: 50,000 opv DC, 5,000 opv AC. 4 inch meter. Built-in protection. Size: 57 x 102 x 153mm.

**OUR PRICE £11.95** P&P 40p

### HIKOKI MODEL 700X

100,000 opv. Overload protection. Mirror scale. 0.2/0.6/1.2/3/15/30/60/120/300/600/1200V DC. 1.5/3/6/12/30/60/150/300/600/1200V AC. 15/30uA/3/30/60/150/300mA/6/12A. DC 2k/20k/2M/200M Ohms. -20 to +66dB.

**OUR PRICE £14.95** P&P 20p

### Model HT100B4 MULTIMETER

Overload protected, shock proof circuit. 9.5uA Meter with mirror scale. Sensitivity: 100kV. Polarity change switch. Ranges: 0.5/2.5/1.5/250/2500/1,000 Volts DC. 2.5/10/50/250/1,000 Volts AC. DC resistance: 0-20/200k/2M Meg. ohms. DC current: 10/250uA/2.5/25/250mA. AC current: 0-10A. -20 to +62dB. Operates from 2 x 1.5V batteries. Size: 180 x 134 x 79mm.

**OUR PRICE £15.00** P&P 40p

### MODEL AS.1000 VOM

100,000 opv. Mirror scale. Built-in meter protection. 0.3 12 60 120 300 600 1200V DC. 0.6 30 120 300 600V AC. 0/10A 5 60 300mA. 12 Amp. 0.2K 200K 2M 200 Meg Ohm. 20 to 17dB.

**OUR PRICE £17.50** P&P 20p.

### KAMOEN HM720B FET VOM

Input impedance 10 Megohms. Ranges: 0.25/1.2/5/10/100/500V DC. 0/2.5/10/50/250/1000V AC. 0/25uA/2.5/25/250mA DC. 0/5k/50k/500k/5M 500 Megohms.

**OUR PRICE £21.00** P&P 30p

### KAMODEN 72.200 Multimeter

High sensitivity center. 200,000 opv. Overload protected. Mirror scale. Ranges—0/0.6/3/2/10/60/600/1200V DC. 0/3/12/60/300/1200V AC. 0/6uA/60uA/600uA/6mA/60mA/12A DC. 0/7.2A AC. -20 to +53dB. 0/2k/20k/200k/2M/20Meg Ohms.

**OUR PRICE £22.50** P&P 30p

### U4317 MULTIMETER

High sensitivity instrument for field and laboratory work. Knife edge pointer, 86mm. mirror scale. Ranges: 100mV/0.5/2.5/10/25/50/100/250/500/1000V DC. 0.5/2.5/10/25/50/100/250/500/1000V AC. Current: 50uA/0.5/1.5/10/50/250mA/1.5A DC. 0.25/0.5/1/5/10/50/250mA/1.5A AC. Resistance: 0.5/10/100/200 ohms/15k/30/300k ohms. Decibels: -5 to +10dB. Battery operated. Size: 210 x 115 x 90mm. Supplied in carrying case complete with leads.

**OUR PRICE £15.00** P&P 20p

### MODEL U4311 Sub-standard Multi-range Volt-Ammeter

Sensitivity 330 Ohms/Volt AC and DC. Accuracy 0.5% DC. 1% AC. Scale length: 165mm. Ranges: 0/300/750uA/1.5/3/7.5/15/30/60/150/300/750mA/1.5/3/7.5/15/30/75/150/300/750V AC. 0/3/7.5/15/30/75/150/300/750V DC. 0/75/150/300/750mV/1.5/3/7.5/15/30/75/150/300/750V AC. Automatic cut out device. Supplied complete with test leads, manual and test certificates.

**OUR PRICE £49.00** P&P 50p

### TE40 HIGH SENSITIVITY AC VOLT METER

10 Meg input. 10 ranges: 0.001/0.03/0.10/3/10/30/100/300V RMS. Scale: 2.5kHz. -40 to +50dB.

supplied complete with leads and instructions.

**OUR PRICE £17.50** P&P 25p

### TE65 VALVE VOLT METER

28 ranges. DC volts 1.5-1500V. AC volts 5-1500V. Resistance up to 1000 Megohms. 200/240V AC. operation. Complete with probe and instructions.

**OUR PRICE £17.50** P&P 30p  
Additional probes available: RF £2.12; HV £2.50

### LB3 TRANSISTOR TESTER

Tests ICB and B. PNP/NPN. Operates from 9V battery. Instructions supplied.

**OUR PRICE £3.95** P&P 20p

### MODEL AF.105 VOM

50,000 opv. Mirror scale. Meter protection. 0.3/3/12/60/120/300/600/1200V DC. 0.6/30/120/300/600/1200V AC. 0.30uA/60/300mA. 12 Amp. 0.10K. 1m/80m/100 Meg Ohms. 20 to 17dB.

**OUR PRICE £12.50** P&P 20p.

### LB4 TRANSISTOR TESTER

Test PNP or NPN transistors. Audio indication. Operates on two 1.5V batteries. Complete with instructions etc.

**OUR PRICE £4.50** P&P 20p

### U4341 Multimeter & Transistor Tester

27 ranges. 16,700 opv. Overload protected. Ranges: 0.3/1.5/6/30/60/150/300/600V DC. 1.5/7.5/30/150/300/750V AC. Current: 0.05/6/60/600mA DC. 0.3/3/30/300mA AC. Resistance: 0.05/0.5/25/200/500k ohm/2 Megohms. Battery operated. Supplied complete with probes, leads and steel carrying case. Size: 115 x 215 x 90mm.

**OUR PRICE £10.50** P&P 20p

### KAMOEN HMG500 insulation resistance tester

Range 0-1,000 Megohms. 500V. Battery operated. Wide range meter 4" x 4". Complete with deluxe carrying case, batteries and instructions.

**OUR PRICE £19.95** P&P 30p

### S100TR MULTIMETER TRANSISTOR TESTER

100,000 opv. Mirror scale. Overload protection. 0/0.12/0.6/3/15/30/60/120/600V DC. 0/12/60/600V AC. 0/10k/1 Meg/100 Meg. -20 to +50dB. 0.01 to 0.2 MF. Transistor tester measures Alpha, Beta and ICB. Complete with instructions, batteries and leads.

**OUR PRICE £15.95** P&P 25p

### C15 PULSE OSCILLOSCOPE

For display of pulsed and periodic wave-forms in electronic circuits. VERT. AMP. Bandwidth: 10MHz. Sensitivity at 100kHz V/div: 5mV. HOR. AMP. Bandwidth: 500kHz. Sensitivity: 100kHz V/div: 0.2-25. Preset triggered sweep 1-3000us. Free running 20-200 kHz in nine ranges. Calibrator pins. 220 x 360 x 430mm. 115-230V AC.

**OUR PRICE £39.00** Carr. paid

### RUSSIAN C116 Double Beam OSCILLOSCOPE

8 MHz in electronic circuits. VERT. AMP. Bandwidth: 10MHz. Sensitivity at 100kHz V/div: 5mV. HOR. AMP. Bandwidth: 500kHz. Sensitivity: 100kHz V/div: 0.2-25. Preset triggered sweep 1-3000us. Free running time base 50Hz/1MHz. Built-in time base. Calibrator and amplitude Calibrator. Supplied complete with all accessories and instructions.

**OUR PRICE £87.00** Carr. paid

### MODEL TE15 GRID DIP METER

Transistorised. Operates as Grid Dip Oscillator. Absorption-Type Meter and Deciling Detector. Frequency range 440kHz-280MHz in six coils. 500uA meter. 9V battery operation. Size: 180 x 80 x 40mm.

**OUR PRICE £19.95** P&P 20p

### SWR METER MODEL SWR3

Handy SWR meter for transmitter antenna alignment, with built-in strength meter. Accuracy 5%. Impedance 57 Inductively 100uA DC. Full scale 5 section color scale antenna. Size 145 x 50 x 60mm.

**OUR PRICE £4.25** P&P 25p

### AT201 Decade ATTENUATOR

Frequency range 0-200kHz. Attenuator 0-111dB. 0.1dB step. Impedance 600 ohms. Input power maximum 300mW. Size: 180 x 90 x 56mm.

**OUR PRICE £12.50** P&P 37p

Also see following pages  
**ALL PRICES EXCLUDE VAT**



**HIGH QUALITY CONSTRUCTION KITS**  
**WE ARE APPOINTED STOCKISTS AT ALL BRANCHES**

All kits are complete with comprehensive easy to follow instructions and covered by full guarantee.

Post and Packing 15p per kit.

- AF20 Mono amplifier..... £1.80
- AF25 Mixer..... £3.60
- AF30 Mono pre-amplifier..... £2.71
- AF35 Emitter amplifier..... £2.27
- AF80 0.5W mic. amplifier..... £4.22
- AF305 Intercom..... £5.52
- AF310 Mono amplifier..... £5.91
- AT5 Automatic light control..... £2.58
- AT25 Window wiper robot..... £5.82
- AT30 Photo cell switch unit..... £5.70
- AT50 400W trisic light dimmer/speed control..... £4.80
- AT56 2,200W trisic light dimmer/speed control..... £6.90
- AT60 1 channel light control..... £7.80
- AT65 3 channel light control..... £14.55
- GP304 Circuit board..... £4.94
- GP310 Stereo pre-amplifier for use with 2 x AF310..... £21.27
- GP312 Circuit board..... £11.45
- GU330 Tremolo control..... £7.50
- HF61 Diode detector..... £3.32
- HF65 FM transmitter..... £2.70
- HF75 FM receiver..... £2.87
- HF310 Mono pre-amplifier..... £15.87
- HF325 Deluxe FM tuner..... £2.12
- HF330 Decoder (HF310/325)..... £9.96
- HF380 Iw/vhf serial amplifier..... £4.94
- HF325 broadband aerial amp..... £7.77
- LF380 Quadraphonic device..... £11.38
- M160 Multi-vibrator..... £1.71
- M191 VU Meter..... £4.65
- M192 Stereo balance meter..... £4.97
- M1302 Transistor tester..... £8.44
- NT10 Stabilised power supply 100mA, 9V..... £6.15
- NT300 Stabilised p. supply..... £12.51
- NT305 Voltage converter..... £4.50
- NT315 Power supply 240V AC 104.5/15V DC, 500mA..... £8.57

**Amateur Electronics by Josty-Kit**, the professional book for the amateur — covers the subject from basic principles to advanced electronic techniques. Complete with circuit board for AE1.

**OUR PRICE £3.30 (No VAT)**  
 P&P 25p plus VAT.

- AE1 100mW output stage..... £1.50
- AE2 Pre-amplifier..... £1.15
- AE3 Diode receiver..... £1.82
- AE4 Flasher..... 95p
- AE5 3-stage multi-vibrator..... 95p
- AE6 Monostable multi-vibrator..... 93p
- AE7 RC generator..... 97p
- AE8 Bass filter..... 90p
- AE9 100V transformer..... 80p
- AE10 CCIR filter..... 90p

**SPECIAL BARGAIN !! STEREO SOUND SPEAKERS**

Matched pair of stereo bookshelf speakers. Deluxe teak veneered finish. 4-ohm, 150Watts peak. 368 x 190mm, 8 ohms, 8 watts RMS, 18 watts peak. Complete with Din lead.

**OUR PRICE £12.95 P&P 50p**

**SPECIAL BARGAIN! FERGIUSON 3408 HI-FI SPEAKERS**

High quality 2 way speaker systems. 2x 4-ohm, 150Watts, 150Hz-18kHz. Size: 560 x 240 x 255mm, approx. Wood grain finish with black fronts.

**OUR PRICE £26.95 PR, P&P £1**

**FM TUNER CHASSIS**

6 transistor high quality tuner. Size only 153 x 101 x 63mm 3 IF stages. Double tuned discriminator. Ampic output to feed most amplifiers. Operates on 9V battery. Covers 88-108MHz. Ready built, ready for use. Fantastic value for money.

**OUR PRICE £5.95 P&P 20p**

**Model A1018 FM TUNER**

6 transistor high quality unit — 3 IF stages and double tuned discriminator. For use with most amplifiers. Covers 88-108MHz. Powered by 9V battery.

**OUR PRICE £13.50 P&P 30p**  
 Stereo multiplex adapter. £5.95 extra.

**ALL PRICES EXCLUDE VAT**

**Also see previous page**

**TRANSISTORISED LCR. A.C. BR/8 MEASURING BRIDGE**

A new portable bridge offering excellent accuracy at low cost. Resistance 6 ranges 0.1 ohm-11.1 megohm = 1 microhenry 111 henries = 2% Capacity 6 ranges 10pF-1110 pf = 2% Turns Ratio 6 ranges 1:1/1000-1:11100 = 1% Bridge Voltage at 1.000cps. Operates from 9-volt battery. 100 micro-amp meter indication. Size 74 x 57 x 25mm.

**OUR PRICE £25.00 P&P 25p**

**TE16A TRANSISTORISED SIGNAL GENERATOR**

5 ranges, 400kHz to 30 MHz. An inexpensive instrument for the handy-man. Operates on 9V battery. Wide easy to read scale. 800kHz modulation. Size: 149 x 149 x 92mm. Complete with instructions and leads.

**OUR PRICE £8.97 P&P 25p**

**MODEL TE20 RF SIGNAL GENERATOR**

Six bands, 120kHz-260MHz. Dual output RF terminals. Separate variable audio output. Accuracy ± 2%. Audio output to 2V. Power requirements: 105-125V, 220-240V AC. Size: 193 x 265 x 150mm. Complete with test leads etc.

**OUR PRICE £17.50 P&P 40p**

**TE-20D RF SIGNAL GENERATOR**

Accurate wide range signal generator covering 120 kHz-500 MHz on 6 bands. Directly calibrated. Variable RF attenuator audio output. Xtal socket for calibration. 220/240V a.c. Brand new with instructions. Size 140mm x 215mm x 170mm.

**OUR PRICE £17.50 P&P 30p**

**ARF 300 AF/RF SIGNAL GENERATOR**

All transistorised compact fully portable. AF sine wave 18Hz to 220 kHz. AF square wave 18Hz to 100kHz. Output Squares/Sine wave 10V. P.P RF 100kHz to 200MHz. Output 1W maximum. 220/240V AC operation. Complete with instructions and leads.

**OUR PRICE £29.95 P&P 50p**

**MODEL MG100 SINE SQUARE WAVE AUDIO GENERATOR**

Range 19. 220,000Hz. Sine Wave 18-100,000 Hz Square Wave. Output Sine or Square wave 10V. P. to P. Size 180 x 90 x 90mm. Operation 220/240V. A.C.

**OUR PRICE £19.95 P&P 37p**

**MCA220 Automatic Voltage Stabiliser**

Input 88-125V AC or 176-250V AC. Output 120V AC or 240V AC. 200V/A rating. P&P 50p

**OUR PRICE £11.97**

**PS100B Regulated POWER SUPPLY UNIT**

Solid state. Output 6, 9 or 12V DC up to 3 Amp. Meter to monitor current. Input 220/240V AC. Size: 100 x 82 x 159mm.

**OUR PRICE £11.97 P&P 25p**

**PS200 Regulated POWER SUPPLY UNIT**

Solid state. Variable output 5-20V DC up to 2 Amp. Independent meters to monitor voltage and current. Output 220/240V AC. Size: 190 x 136 x 98mm.

**OUR PRICE £19.95 P&P 25p**

**POWER RHEOSTATS**

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fixing. 1/2" diameter shafts. Built-in anti-rotation.

25 WATT 10/25/50/100/250/500/1000/2500 Ohms **£1.15 P&P 10p**

50 WATT 10/25/50/100/250/500/1000/2500/5000 Ohms **£1.62 P&P 10p**

100 WATT 1/5/10/25/50/100/250/500/1000/2500 Ohms **£2.34 P&P 15p**

**AUTO TRANSFORMERS**

0/115/250V. Step up or step down. Fully shrouded.

80 WATTS **£2.75 P&P 18p**

150 WATTS **£3.50 P&P 18p**

300 WATTS **£4.50 P&P 23p**

500 WATTS **£6.95 P&P 33p**

1000 WATTS **£9.50 P&P 38p**

1500 WATTS **£12.50 P&P 43p**

2250 WATTS **£20.95 P&P 50p**

5000 WATTS **£44.95 P&P £1**

**CP110 CHASSIS PUNCH SET**

Carefully machined top grade steel. Contains 1/2", 5/8", 3/4", 1" and 1 1/8" punches complete with gripper and accessories.

**OUR PRICE £3.00 P&P 40p**

**YAMABISHI VARIABLE VOLTAGE TRANSFORMERS**

Excellent quality at low cost. Input 230V 50/60Hz. Output 0-260V. MODEL S26B BENCH MOUNTING

1A £10.50 30p

2.5A £12.00 35p

5A £17.50 37p

10A £33.75 50p

15A £33.75 50p

20A £29.50 75p

25A £85.00 125p

30A £95.00 130p

40A £120.00 150p

**MODEL S260B PANEL MOUNTING**

1A £10.00 30p

2.5A £12.00 35p

**240° Wide Angle 1mA METERS**

MW 1-6 60x60mm **£6.50 P&P 15p**

MW 1-8 80x80mm **£6.90 P&P 15p**

**BV05 Vernier TUNING DIAL**

App. 7:1 ratio planetary drive vernier dial. Log scale 0-180 degrees. Blank scales 1-5. Dial size 128 x 76mm. Overall size 190 x 117 x 41mm. Deep including knob and coupling. 1/2" diam. shaft

**OUR PRICE £11.62 P&P 15p**

**WALKIE TALKIES**

SKY FION 100mW **OUR PRICE £24.95 per pair**

P302 Two Channel 300mW **OUR PRICE £52.50 per pair**

P1003 Three Channel 1 Watt **OUR PRICE £71.25 per pair**

P&P 50p per pair

Not licitiable for use in U.K.

**RUH6 Reflex Horn Speaker**

Built-in driver unit. Impedance 16 ohms. Power rating 10W. Resonance 380-7000Hz. Size approx. 6" x 6". Weather and shock protected.

**OUR PRICE £4.97 P&P 30p**

**TRIO 9R590S RECEIVER**

Four bands covering 550kHz to 30 MHz continuous and electrical broadcast spread on 10, 15, 20, 40, and 80 mtrs. 8 valve plus 7 diode circuit. 4 to 8 ohm output and phone jack. SSB, CW, AM, variable BFO. 5 Meter and separate band spread dial. IF frequency 445kHz. audio output 15 watt. Variable RF and AF gain controls. 115/250V AC, with instructions.

**Our Price £42.50 CARR. PAID**

**BELTEK W5400 CAR TRANSCIVER**

Solid state mobile transceiver for 12 volt DC neg. Transmits and receives on any 12 of 28 channels between 144 and 146MHz. Power output 10W and 1W switchable. Controls: On/off/volume, squelch and channel selector. Internal 3" speaker. Complete with dynamic mic. PTT switch, three sets of crystals for 144.48, 144.6 and 145MHz, mounting bracket and instructions. Size 150 x 70 x 220mm.

**OUR PRICE £75.00 P&P 50p**

**HITACHI FLUORESCENT LANTERN L1901**

A portable battery operated lantern ideal for home, motoring, camping etc. Approx 10" tall. Provides brilliant light from 9 1/2 watties (not supplied).

**OUR PRICE £7.90 P&P 25p**

**OT55B DIGITAL CLOCK MECHANISM**

24 hour alarm setting. on/off and auto alarm 'sleep' switch. Illuminated rotary dial with hours, minutes and seconds. Automatically turns off radio, TV, light etc. and with auto switching will turn on again when required. 240V AC operation. Switch rating 250V-3 Amp.

**OUR PRICE £5.95 P&P 30p**

**KE630 3 Station INTERCOM**

Master and two sub-stations. Can be used on desk or wall mounted. Complete with cable and batteries.

**OUR PRICE £5.25 P&P 50p**

**LH02S STEREO HEADPHONES**

Light weight headphones with padded ear pieces. 4/16 ohms 20-20,000Hz. Complete with 6' lead and plug.

**OUR PRICE £1.97 P&P 30p**

**TE1018 Deluxe Mono High Impedance Headset**

Sensitive magnetic headset with soft ear pads. Impedance 2,600 ohms (600 ohms DC). Frequency response: 200-4,000Hz.

**OUR PRICE £2.25 P&P 30p**

**DH02S STEREO HEADPHONES**

Wonderful value and excellent performance combined. Adjustable head band. Impedance 8 ohms 20 12,000Hz. Complete with lead and plug.

**OUR PRICE £2.50 P&P 30p**

**TE1035 Stereo HEADPHONES**

Low cost with excellent performance. Foam rubber earcups. Adjustable headband. 8 ohms impedance. Frequency response 25Hz-18kHz. Complete with cable and stereo jack plug.

**OUR PRICE £2.60 P&P 30p**

**SH8DV MONO/STEREO HEADPHONES**

Volume control for each channel. 4/16 ohms impedance. Frequency response 20Hz-18kHz. Complete with 10ft. coiled lead and jack plug.

**OUR PRICE £4.97 P&P 30p**

**BH001 HEADSET and Boom Microphone**

Moving coil. Ideal for language teaching, communications etc. Headphone impedance 16 ohms. Mic impedance 200 ohms.

**OUR PRICE £5.95 P&P 30p**

**EMI LOUSPEAKERS**

Model 350 13 x 8" with single tweeter/crossover. 20-20,000Hz. 15 watts RMS. Available 8 or 15 ohms.

**OUR PRICE £7.50 each P&P 37p**

Model 450 13 x 8" with twin tweeter/crossovers. 55-13,000Hz. 8 watts RMS. Available 8 or 15 ohms

**OUR PRICE £3.62 each P&P 25p**

**SPECIAL PURCHASE LIMITED QUANTITY! Tannoy 12" DR/8 Bass Speakers**

8 ohms 30 watt Heavy duty, ideal for Hi Fi P.A. Group

**OUR PRICE £12.50 P&P 50p**





# BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD



## Telephone Corner

COMPLETE TELEPHONES

Normal Household Type

EX. G.P.O. Only **£1.05**, P & P 45p each

## TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order

Only **27 1/2p** POST & PACKING 16p

## Ex GPO Push Button Intercom Telephones

Exactly as internal telephone systems still in everyday use where automatic internal exchanges have not yet taken over. Available in 5, 10 or 15 ways. Complete with circuits and instructions. Necessary 24 pair cable 22p per yard. Price of each instrument is independent of the number of ways.

**£2.75 p.p. 38 1/2p** Per Instrument

Cable can be sent by Parcel Post. Post and Packing per 50 yds. 73p.

Extension Telephones, 71p each, p.p. 27p. £1.31 for 2. P & P 55p.

These phones are extensions and do not contain bells.

## Electronic Transistor Ignition £6.60

Complete kit incl. V.A.T. p. & p. 11p

Ready built & tested unit £9.90 inc. V.A.T. Now in kit form, we offer this "up-to-the-minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features. Transistor and conventional switchability, burglar proof lock-up and automatic alarm, negative and positive compatibility.

## New X Hatch

Our new vastly improved Mark Two Cross Hatch Generator is now available. Featuring plug in IC's and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's tool box—and only measures 3" x 5 1/2" x 3". We have already received a large order from a major T.V. Rental company.

Ready built unit only **£10.92** Complete kit **£8.72**

(Includes V.A.T. and p. & p. but no batteries)

## Over 1,000,000 Transistors in stock


We hold a very large range of fully marked tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

### Our very popular, 4p transistors

TYPE "A" PNP Silicon alloy, TO-5 can  
TYPE "B" PNP Silicon, plastic encapsulation  
TYPE "E" PNP Germanium AF or RF  
TYPE "F" NPN Silicon plastic encapsulation  
TYPE "G" NPN silicon similar ZTX 300 range  
TYPE "H" PNP silicon similar ZTX 500 range


**8 RELAYS FOR VARIOUS TYPES P & P 271p £1.10p**

## High Speed Magnetic Counter

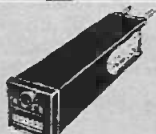

4 digit (non-reset) 24v or 48v (state which) 4 x 1 x 1in, 33p, p.p. 5p.

## Plastic Power Transistors

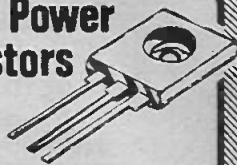

NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1. VCE. Min 15. HFE Min 15.  
1-12 13-25 26-50  
40 Watt 22p 20p 18p  
90 Watt 26p 24p 22p

Range 2. VCE. Min. 40. HFE Min 40  
1-12 13-25 26-50  
40 Watt 33p 31p 29p  
90 Watt 38p 36p 33p

Complementary pairs matched for gain at 2 amps, 11p extra per pair. Please state NPN or PNP on order.

LM380 Audio I.C. as featured in Practical Wireless December issue complete with application data £1.10

### INTEGRATED CIRCUITS

We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

**METRICATION CHARTS** now available. This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc. Pocket Size 15p Wall Chart 18p

**LOW COST DUEL IN LINE I.C. SOCKETS** 14 pin type at 16p each. Now new low profile 16-pin type at 18p each / type

### BOOKS

We have a large selection of Reference and Technical Books in stock.

Send for lists of publications

## Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

11p P & P on this Pak.

Please ask for Pak P.1. only **55p**

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME .....

ADDRESS .....

ALL PRICES INCLUDE 10% VAT

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 11p post and packing per order OVERSEAS ADD EXTRA FOR POSTAGE

BUY THESE GOODS WITH ACCESS

## Tested and Guaranteed Paks



- |     |     |   |     |
|-----|-----|---|-----|
| B79 | 4   | IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic             | 55p |
| B81 | 10  | Reed Switches, 1" long, 1/4" dia. High Speed P.O. type      | 55p |
| H35 | 100 | Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.  | 55p |
| H38 | 30  | Short lead Transistors. NPN Silicon Planar types            | 55p |
| H39 | 6   | Integrated Circuits. 4 Gates BMC 962, 2 Flip Flops BMC 945  | 55p |
| H41 | 2   | Sil Power transistors comp pair BD131/132                   | 55p |
| H63 | 4   | 2N3055 type NPN Sil. power transistors. Below spec. devices | 55p |
| H64 | 4   | 3819 N Channel FETs 2N3819 In plastic case                  | 55p |



## Unmarked Untested Paks

- |     |     |  |     |
|-----|-----|--|-----|
| B1  | 50  | Germanium Transistors PNP, AF and RF                     | 55p |
| B66 | 150 | Germanium Diodes Min. glass type                         | 55p |
| B84 | 100 | Silicon Diodes DO-7 glass equiv. to OA200. OA202         | 55p |
| B86 | 100 | Sil. Diodes sub. min. IN914 and IN916 types              | 55p |
| H16 | 15  | Experimenters' Pak of Integrated Circuits, Data supplied | 55p |
| H34 | 15  | Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.      | 55p |
| H67 | 10  | 3819N Channel FETs plastic case type                     | 55p |

## Make a rev counter for your car

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

**£1.10p each**

**BI-PRE-PAK LTD**

Ref. No. B20/119

Dept. E. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.

TELEPHONE: SOUTHEND (0702) 46344.




### PSYCHEDELIC LIGHTING UNIT IN KIT FORM

Make this fascinating three-channel unit from a kit which contains all components needed to produce an ever changing light display. Takes its drive from the speaker terminals of a record player, tape recorder or portable radio. Will drive a total of 2kW of coloured lamps at 240 volts. Supplied complete with PVC covered steel cabinet with holes ready punched for controls and cable outlets. Master control included. Coloured lamps not supplied. Price per kit £11.95.
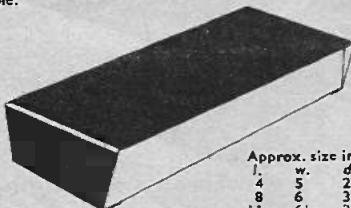
### METAL CABINETS

These attractive steel cabinets are PVC covered in a range of colours, and offer an economically priced unit for the home constructor. The chassis, which has a white satin PVC finish, provides an easily accessible building area, with an integral fascia panel. The cabinet is supplied complete with stick-on feet.

Colours available include Green, Grey, Black, White and Blue. Every effort will be made to supply a selected colour, but please give alternatives if possible.



Approx. size in ins.			Price
l	w	d	
4	5	2½	75p
8	6	3	£1.60
11	6½	3	£2.04

Other sizes to special order. HOLES PUNCHED in front or back panels to your own requirements. Please send S.A.E. for quotation.

### FIXED VOLTAGE REGULATORS

TO3 case. Gives stabilised supply. MVR 5 V, MVR 12 V, MVR 15 V. All priced at £1.98

### VEROBOARD

	0.1	0.15
2½ x lin	7p	7p
2½ x 3½ in	27p	20p
2½ x 5 in	29p	29p
3½ x 3½ in	29p	29p
3½ x 5 in	31p	32p

### D.I.L. REED RELAY

Operates direct from 5 volt TTL logic elements. Normally open contact rated at 0.25A, 100V d.c. Price each £1.50

Our CATALOGUE, priced at 25p post free in U.K., shows most of the R.S. range of professional components. Prices include VAT. All orders over £1 POST FREE—U.K. only. Overseas postage at cost. S.A.E. with all queries please.

## CELETRON-E

P.O. Box No. 1, Llantwit Major, Glamorgan, Wales CF6 9YN

# JOSTY KITS FROM ELECTRO SPARES

The Josty appointed stockists

\* ALL KITS POST FREE! \* ALL PRICES INCLUDE VAT!


It makes practical sense to invest in Josty Kits. They come complete with everything you need — all the components ready to use, including even the solder. Plus easy-to-understand, fully comprehensive instructions, and a cast-iron guarantee. Just look at the list of Josty Kits available now from Electro Spares. Remember, every price includes VAT, and every Kit is post free.

Model No.	Josty Kit Retail Price List	Total RRP inc. VAT	AT30 Photo Cell Switching Unit	6-27
AF20	Mono Transistor Amplifier	5-28	AT50 400w Triac Light Dimmer Speed Control	5-28
AF25	Mixer	3-96	AT56 2,200w Triac Light Dimmer Speed Control	7-59
AF30	Mono Transistor Pre-Amplifier	2-87	AT5 Automatic Light Control	2-84
AF35	Emitter Amplifier	2-50	GU330 Tremelo Unit for guitars, etc.	8-25
AF80	Small 0.5 W Amplifier for microphone	4-65	HF61 Diode Detector	3-66
AF305	Intercom	8-28	HF65 Frequency modulated FM transmitter	2-97
AF316	Mono Amplifier (for Stereo use two)	6-50	HF75 FM Transistor Receiver	3-16
M160	Multivibrator	1-88	HF310 FM Tuner Unit	17-39
M1302	Transistor Tester	9-30	HF325 De-Luxe FM Tuner Unit	26-63
M191	Vu-Meter	5-01	HF330 Stereo Decoder for use with HF310 or HF325	10-95
M192	Stereo Balance Meter	5-47	GP310 Stereo Pre-Amp to use with 2, AF310	23-39
LF380	Quadrophonic Device	12-50	GP312 Basis circuit board	12-60
AT60	Psychedelic Light Control, Single Channel	8-58	Plus many others.	
AT65	Psychedelic Light Control, 3 Channel	16-00		
AT25	Window Wiper Robot	6-40		
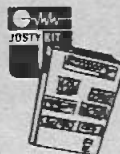
### 'AMATEUR ELECTRONICS'

Specially produced by the makers of Josty Kits to give you a professional insight into the fascinating world of electronics. Written with the amateur in mind from start to finish, "Amateur

Electronics" is an ideal introduction to the whole subject — from first principles to advanced electronic techniques. The price includes a circuit board for making ten Josty Kit projects. Only £3.30, plus 20p p & p. No VAT. Send S.A.E. now for a free 8-page colour brochure all about Josty Kits and Amateur Electronics.



### COMPONENT LISTS FOR "EVERYDAY ELECTRONICS" PROJECTS

You only need to have constructed a few projects as published in "Everyday Electronics", to know what a problem it is to get every component just when you need it. Electro Spares have devised the complete solution. Now you can get lists of all the components required for any of the projects in this issue. Just send us a stamped addressed envelope, and tell us which project you are interested in. The list shows a separate price for each item, as well as a price for the complete kit. You can buy any one or more components to suit yourself.

Save money — and time — buy all your components from one source

**GUARANTEED COMPONENTS FROM ELECTRO SPARES**  
Every single component you buy from us is a new branded product from a reputable manufacturer. And it carries the manufacturer's full guarantee.

# ELECTRO SPARES

The Component Centre of the North  
288 ECCLESALL RD., SHEFFIELD S11 8PE (B)  
Tel: Sheffield (0742) 668888



## become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

**free!** Brochure, without obligation to:

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL** P.O. Box 156, JERSEY

NAME:

ADDRESS:


EEB 6.4.  
BLOCK CAPS please

# A complete kit!

The kit comes to you packaged in a heavy-duty polystyrene container. It contains all you need to assemble your Sinclair Cambridge. Assembly time is about 3 hours.

**Contents:**

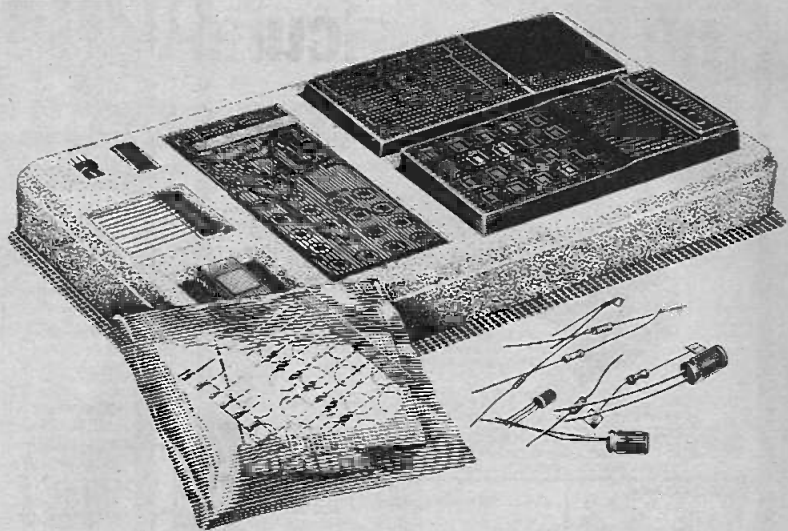1. Coil.
2. Large-scale integrated circuit.
3. Interface chip.
4. Thick-film resistor pack.
5. Case mouldings, with buttons, window and light-up display in position.
6. Printed circuit board.
7. Keyboard panel.
8. Electronic components pack (diodes, resistors, capacitors, transistor).
9. Battery clips and on/off switch.
10. Soft wallet.



**This valuable book – free!**

If you just use your Sinclair Cambridge for routine arithmetic – for shopping, conversions, percentages, accounting, tallying, and so on – then you'll get more than your money's worth.

But if you want to get even more out of it, you can go one step further and learn how to unlock the full potential of this piece of electronic technology.



How? It's all explained in this unique booklet, written by a leading calculator design consultant. In its fact-packed 32 pages it explains, step by step, how you can use the Sinclair Cambridge to carry out complex calculations.

# sinclair

Sinclair Radionics Ltd, London Road,  
St Ives, Huntingdonshire  
Reg. no: 699483 England  
VAT Reg. no: 213 8170 88

304

**Why only Sinclair can make you this offer**

The reason's simple: only Sinclair – Europe's largest electronic calculator manufacturer – have the necessary combination of skills and scale.

Sinclair Radionics are the makers of the Executive – the smallest electronic calculator in the world. In spite of being one of the more expensive of the small calculators, it was a runaway best-seller. The experience gained on the Executive has enabled us to design and produce the Cambridge at this remarkably low price.

But that in itself wouldn't be enough. Sinclair - Iso have a very long experience of producing and marketing electronic kits. You may have used one, and you've almost certainly heard of them – the Sinclair Project 60 stereo modules.

It seemed only logical to combine the knowledge of do-it-yourself kits with the knowledge of small calculator technology.

And you benefit!

**Take advantage of this money-back, no-risks offer today**

The Sinclair Cambridge is fully guaranteed. Return your kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee a correctly-assembled calculator for one year.

Simply fill in the preferential order form below and slip it in the post today.

**Price in kit form: £24.95 + £2.50 VAT. (Total: £27.45)**

**Price fully built: £29.95 + £3.00 VAT. (Total: £32.95)**

EE 6 74

To: Sinclair Radionics Ltd, London Road,  
St Ives, Huntingdonshire, PE17 4HJ

Please send me Name \_\_\_\_\_

a Sinclair Cambridge calculator kit at  
£24.95 + £2.50 VAT (Total: £27.45)

a Sinclair Cambridge calculator ready  
built at £29.95 + £3.00 VAT  
(Total: £32.95) Address \_\_\_\_\_

\*I enclose cheque for £ \_\_\_\_\_, made  
out to Sinclair Radionics Ltd, and  
crossed. \_\_\_\_\_

\*Please debit my \*Barclaycard/Access  
account. Account number \_\_\_\_\_

\*Delete as required. PLEASE PRINT



# The Sinclair Cambridge... no other calculator is so powerful and so compact.

## Complete kit - £24.95! (PLUS VAT)

### The Cambridge - new from Sinclair

The Cambridge is a new electronic calculator from Sinclair, Europe's largest calculator manufacturer. It offers the power to handle the most complex calculations, in a compact, reliable package. No other calculator can approach the specification below at anything like the price - and by building it yourself you can save a further £5.50!

### Truly pocket-sized

With all its calculating capability, the Cambridge still measures just  $4\frac{1}{2}'' \times 2'' \times \frac{11}{16}''$ . That means you can carry the Cambridge wherever you go without inconvenience - it fits in your pocket with barely a bulge. It runs on ordinary U16-type batteries which give weeks of life before replacement.

### Easy to assemble

All parts are supplied - all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our service department will back you throughout if you've any queries or problems.

### The cost? Just £27.45!

The Sinclair Cambridge kit is supplied to you direct from the manufacturer. Ready assembled, it costs £32.95 - so you're saving £5.50! Of course we'll be happy to supply you with one ready-assembled if you prefer - it's still far and away the best calculator value on the market.



### Features of the Sinclair Cambridge

- \* Uniquely handy package.  $4\frac{1}{2}'' \times 2'' \times \frac{11}{16}''$ , weight  $3\frac{1}{2}$  oz.
- \* Standard keyboard. All you need for complex calculations.
- \* Clear-last-entry feature.
- \* Fully-floating decimal point.
- \* Algebraic logic.
- \* Four operators (+, -, x, ÷), with constant on all four.
- \* Constant acts as last entry in a calculation.
- \* Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £30.
- \* Calculates to 8 significant digits, with exponent range from  $10^{-20}$  to  $10^{29}$ .
- \* Clear, bright 8-digit display.
- \* Operates for weeks on four U16-type batteries. (MN 2400 recommended.)

# everyday electronics

PROJECTS...  
THEORY....

## POCKETS AND PROJECTS

The tide of rising prices and inflation does not look like subsiding, yet. All we can hope for in our most optimistic mood is that the peak of the flood has now been experienced (and suffered) and that the tide will soon be on the ebb. At any rate, most of us will have to continue to consider very carefully any proposed expenditure in the immediate future.

Whether hobbies and leisure pursuits in general suffer or prosper in times of financial difficulty is an interesting debating point. One cannot generalise, of course, since a lot depends upon the nature of the hobby and the personal circumstances of the individual.

Some leisure pursuits are entirely recreational and possibly extravagant in outlay for services or equipment. Of a different nature are the many traditional crafts that can be taken up for fun but provide an additional permanent bonus in the form of some tangible result from the effort expended.


To the list of established traditional crafts, we must now include electronics. With the introduction of simple-to-use circuit devices, most of the old terrors of electronics have disappeared. The average man in the street can be as happily engaged in building and experimenting, as the technically trained expert. The nature of this subject allows useful and interesting involvement at all levels. One can restrict one's interest to quite a modest level; or one can progress

practically without limitation—save that of the depth of pocket—to the highest heights, by building ambitious and technically complex projects.

Among electronics magazines for home constructors, EVERYDAY ELECTRONICS is unique in covering the modest end of the business *exclusively*. This means we devote much of our attention to the absolute beginner and help him (or her) on the way, by explaining in plain language the basic facts of life: about both the theory of electronic circuits and the practice of assembling electronic projects from readily available, and generally inexpensive, components.

Now that we have come back to "money," this is a good opportunity to mention another EVERYDAY ELECTRONICS exclusive feature—The Cost Box. Desirable as a particular design may be, the expenditure involved is likely to be a decisive factor in determining whether or not to go ahead. So we ensure that readers have a good idea as to the probable cost of each and every constructional project we present.

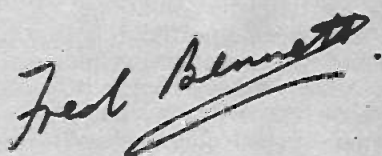The shrewd constructor will appreciate the good investment our projects provide!



Our July issue will be published on Friday, June 21

EDITOR F. E. Bennett ● ASSISTANT EDITOR M. Kenward ● B. W. Terrell B.Sc.  
ART EDITOR J. D. Pountney ● P. A. Loates ● K. A. Woodruff  
ADVERTISEMENT MANAGER D. W. B. Tilleard

© IPC Magazines Limited 1974. Copyright in all drawings, photographs, and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden.

All reasonable precautions are taken by EVERYDAY ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Everyday Electronics Fleetway House, Farringdon Street, London, E.C.4. Phone: Editorial 01-634-4452; Advertisements 01-634-4202.



**EASY TO CONSTRUCT  
SIMPLY EXPLAINED**



VOL. 3 NO. 6

JUNE 1974

## CONSTRUCTIONAL PROJECTS

<b>FREEZER TEMPERATURE ALARM</b> Warning of freezer failure by T. P. Manning and R. D. Wilder	308
<b>AMATEUR BANDS RECEIVER</b> A direct conversion receiver for 80m and 160m by R. A. Penfold	322
<b>R.F. SIGNAL GENERATOR (E.E. Test Gear Five)</b>	329

## GENERAL FEATURES

<b>EDITORIAL</b>	306
<b>READERS' LETTERS</b> Your news and views	313
<b>TEACH-IN '74</b> Lesson 9: Inductance and the Transformer by Phil Allcock	314
<b>ELECTRONICS AND THE MOTOR CAR</b> Part 2 by C. S. Pointer	319
<b>RUMINATIONS</b> by Sensor	321
<b>SHOP TALK</b> Component buying problems by Mike Kenward	328
<b>JACK PLUG AND FAMILY</b> Cartoon	328
<b>COMPETITION</b> Multimeters to be won!	338
<b>SEMICONDUCTOR PRIMER</b> Facts and figures by A. P. Stephenson	341
<b>DOWN TO EARTH</b> The amplified diode by George Hylton	342

Publisher's Annual Subscription Rate, including postage to any part of the world, £2.95. International Giro facilities Account No. 5122007. State reason for payment "message to payee". Address to Everyday Electronics, Subscription Department, Carlton House, Great Queen Street, London, WC2E 9PR. Binders for volumes 1 to 3 (state which) and indexes for volume 1 and 2 available for £1.25 and 11p respectively, including postage, from Binding Department, at the above address.

We are unable to supply back copies of Everyday Electronics or reprints of articles and cannot undertake to answer readers' letters requesting designs, modifications or information on commercial equipment or subjects not published by us. An s.a.e. should be enclosed for a personal reply. Letters concerning published articles should be addressed to: The Editor, those concerning advertisements to: The Advertisement Manager, both at the address shown opposite.

**NEXT MONTH**  
**A special call to**  
**all subscribers**

see page 337 for more details



**T**HE position for effective operation of a deep freeze unit is usually outside and remote from the kitchen or lounge and very often it is situated in the garage and may only be visited once a day or less. If the deep freeze unit develops a fault it may be sometime before this is discovered and by that time the contents may be spoiled.

The unit to be described here will help to prevent this spoiling by giving an audible and visual alarm when the temperature in the freezer compartment varies by more than plus or minus 1.5 degrees. In this way the fault is brought to your attention, and repairs and/or other arrangements can be made immediately, such as lagging the freezer until repairs are carried out or moving the contents to another freezer.

### CIRCUIT DESCRIPTION

The circuit diagram of the Freezer Temperature Alarm is shown in Fig. 1. The unit uses a differential amplifier IC1 whose voltage output, pin 6, is proportional to the difference in voltage between the two inputs, pins 2 and 3.

The voltage on pin 3 is held constant by the potential divider effect of resistors R7 and R8, the potential at their junction being set at half the supply voltage i.e. 6V. The voltage applied to pin 2 is controlled by the potential divider effect of the resistance chain R9, VR1 and RTH1.

Potentiometer VR1 is a preset control, wired to act as a variable resistor for setting up pur-

poses. At a given temperature, VR1 can be adjusted so that the voltage appearing on pin 2 is the same as that at pin 3, in this instance there will be no voltage at the output (pin 6).

Now a thermistor is a component whose resistance varies in a known way with temperature so that when the temperature changes the voltage at pin 2 changes, and thus an output voltage is produced. The unit has been designed such that a 1.5 degree temperature change (with G14 thermistor) produces sufficient output voltage to operate relay RLA.

When the relay contacts, RLA1, close, power is available to operate the astable multivibrator composed of TR1, TR2 and associated components. The frequency of the multivibrator is 1Hz (approximately) determined by the timing components R1, C6 and R4, C5. Therefore the output from the collector of TR2 is a train of positive pulses and these are fed via R5 to the


FOR  
GUIDANCE  
ONLY

ESTIMATED COST\*  
OF COMPONENTS  
including V.A.T.

£7.10

excluding case

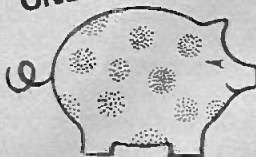\*Based on prices prevailing at  
time of going to press



# FREEZER TEMPERATURE ALARM

BY T.P. MANNING & R.D. HIDER

**Gives an audible  
and visual alarm  
if the temperature  
inside the freezer  
varies.**





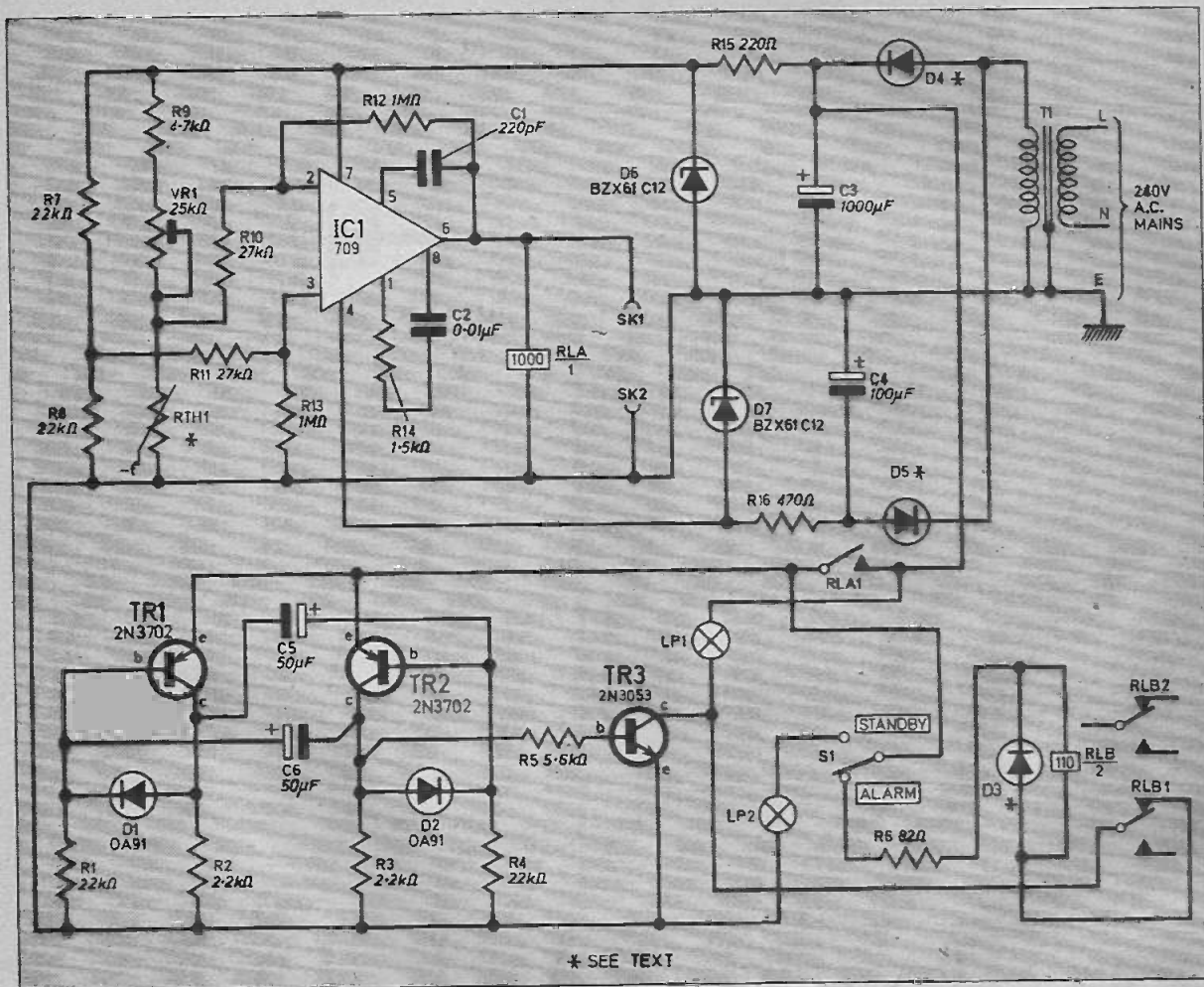


Fig. 1. The complete circuit diagram of the Freezer Temperature Alarm.

base of TR3.

Each time a positive voltage is applied to the base of TR3, it is biased into conduction and TR3 collector falls to almost zero volts causing almost 20 volts to be placed across the lamp LP1 causing the latter to be illuminated. The net result of the pulse train is to cause LP1 to flash on and off thus giving the visual alarm.

With S1 in the position shown, RLB is in parallel with LP1 and is energised each time LP1 is illuminated. Contact RLB1 is wired so that when the relay is energised, the contact is pulled in and breaks the circuit causing the relay to become de-energised. As this happens, RLB1 springs back and makes the circuit again and the cycle is repeated.

This process happens very quickly and the relay contact is made to "buzz" thus giving the audible alarm. This is the principle on which the simple bell works.

With S1 in its other position the buzzer is taken out of circuit and this is indicated by the illumination of LP2. This is useful in setting up the unit as the buzzer can be annoying.

Resistor R6 is incorporated in series with RLB to drop the voltage across the relay to 12V.

If desired, the audible and visual alarm can be omitted and another alarm of your choice, e.g., a buzzer can be employed, contact RLA1 switching it on (the contacts are rated at 200mA maximum). In this case all circuitry below relay contact RLA1 in Fig. 1 is not required.

### P.C. BOARD

The component board used in the prototype was a home made printed circuit type, the full-size drawing of which is shown in Fig. 2.

The easiest way of making the board is to thoroughly clean a piece of copper clad board, size 140 x 90mm and then with either enamel paint or a Dalo pen (etchant resist) cover in the areas shown in black on the master drawing—these are the areas of copper to remain after etching.

When the etchant resist has completely dried, check the board for mistakes, ragged edges and uncovered areas and when completely satisfied, the board should be immersed in a dish of dilute

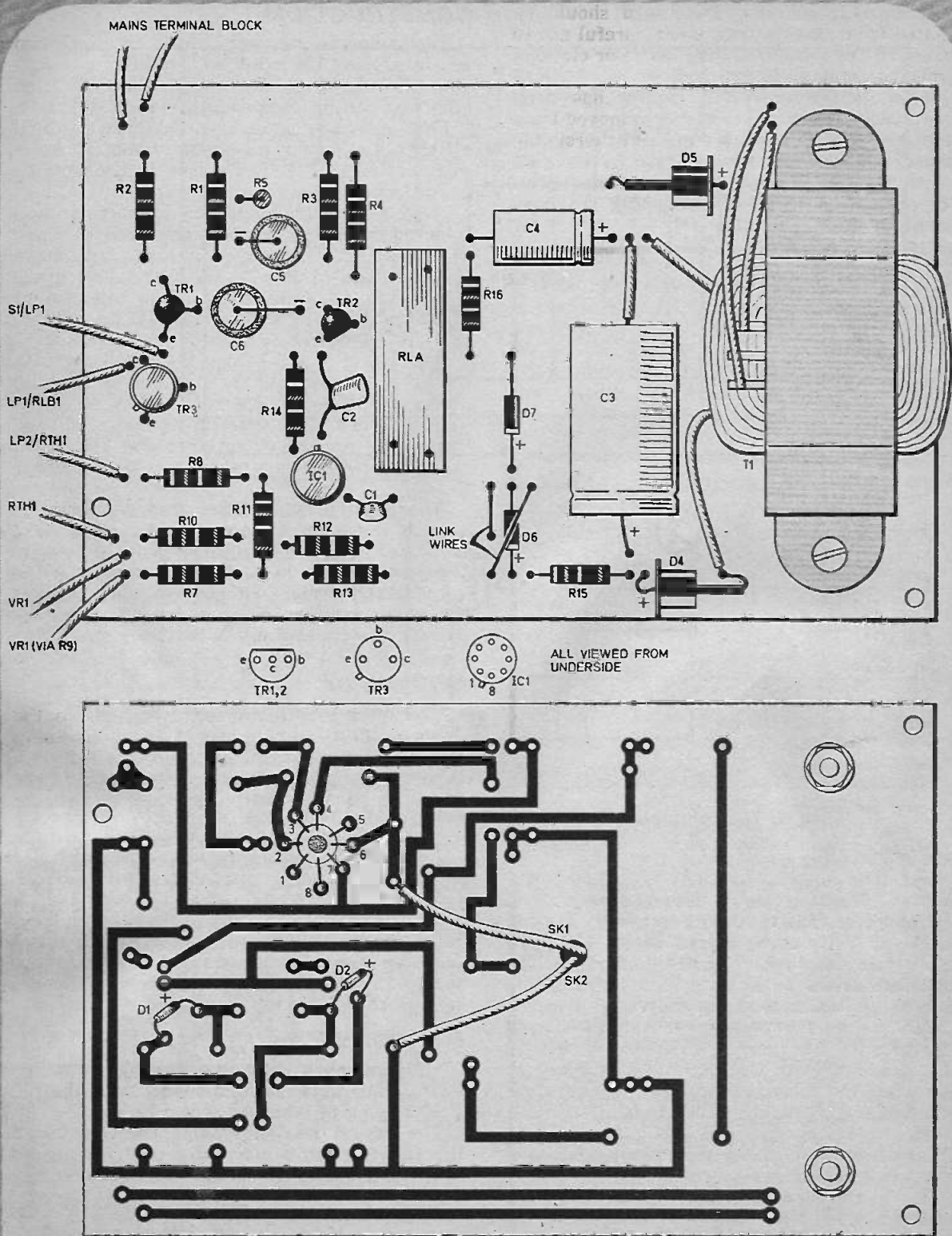


Fig. 2 (top). The layout of the components on the top side of the printed circuit board and (below) the full-sized master drawing of the copper pattern on the underside of the board.



ferric chloride solution. The board should be agitated from time to time being careful not to get any of the solution on the hands or clothing as it is poisonous and corrosive.

When all the unwanted copper has been etched away, the board should be removed from the dish with a pair of tweezers and thoroughly washed under running tap water.

Now clean off the resist and drill all the necessary holes. The board is now ready for component assembly.

## Components....

### Resistors

R1	22k $\Omega$
R2	2.2k $\Omega$
R3	2.2k $\Omega$
R4	22k $\Omega$
R5	56k $\Omega$
R6	82 $\Omega$
R7	22k $\Omega$
R8	22k $\Omega$ —see text
R9	4.7k $\Omega$
R10	27k $\Omega$
R11	27k $\Omega$
R12	1M $\Omega$
R13	1M $\Omega$
R14	1.5k $\Omega$
R15	220 $\Omega$
R16	470 $\Omega$

All  $\frac{1}{2}$ W  $\pm 10\%$  carbon

### Capacitors

C1	220pF
C2	0.01 $\mu$ F
C3	1000 $\mu$ F elect. 25V
C4	100 $\mu$ F elect. 25V
C5	50 $\mu$ F elect. 25V
C6	50 $\mu$ F elect. 25V

### Semiconductors

TR1, 2	OC71 germanium pnp (2 off)
TR3	2N3053 silicon npn
D1, 2	0A91 (2 off)
D3	BY234
D4, 5	IN92 or any 1A 50V diode (2 off)
D6, 7	BZX61, 12V 1W Zener (2 off)
IC1	709 differential amplifier TO-99 case
RTH1	G14 thermistor—see text

### Miscellaneous

VR1	25k $\Omega$ carbon preset TV type
S1	single-pole changeover toggle
SK1, 2	4mm insulated sockets, one red, one black (2 off)
T1	mains/15V 500mA secondary
LP1, 2	m.e.s. 20V 100mA lamps and panel mounting lampholders, one amber lens, one clear lens (2 off)
RLA	9-12V reed relay with coil resistance greater than 200 ohms (type RR (9-12) colour blue)
RLB	12V with changeover contacts and coil resistance 110 ohms (Omron)
Copper clad board size 140 x 90mm; 2A terminal blocks, 2-way and 3-way; length of three core mains cable; 4BA nuts, bolts, washers and stand off spacers; metal case.	

SEE  
**SHOP  
TALK**

## CONSTRUCTION

The prototype unit was built in an aluminium box measuring 150 x 100 x 65mm with a removable lid. This should be the minimum size used otherwise all the components will not fit inside.

First, obtain or build a suitable box and drill all the fixing and components mounting holes as indicated in Fig. 3. The box should now be painted or covered.

The components should now be mounted and soldered in position on the printed circuit board as detailed in Fig. 2 paying special attention to the polarities of the diodes, capacitors, integrated circuit and transistors. Use a heatsink when soldering the semiconductors. Do not connect the flying leads at this stage.


Next position and secure the components to the lid of the box and the two sets of terminal blocks to the bottom half of the box as shown in Fig. 3, and then wire up as indicated. The mains lead should be let into the box via a rubber grommet and a cable clip used to anchor it.

When completely satisfied that the wiring is correct, secure the component board to the base of the box with 4BA fixings and stand-off spacers and place the lid in position ensuring that the lid mounted components do not touch any of the board mounted components and more important, the transformer.
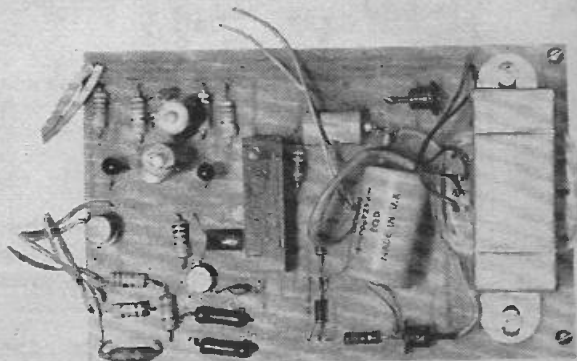
## SETTING UP

Disconnect the thermistor, switch S1 to the alarm position and plug in and switch on. Lamp LP1 should flash and the buzzer sound. Switch S1 to the standby position and LP2 should light up and the buzzer cease to operate; LP1 should still flash.

If all is satisfactory, switch off the unit and insert the thermistor in its terminal block on a length of twin cable and place the thermistor inside the deep freeze cabinet. It will depend on the model of the freezer how access is obtained, but in chest type freezers it is sufficient to lay the thermistor on the seal so that



Photograph of the completed piototype component board.

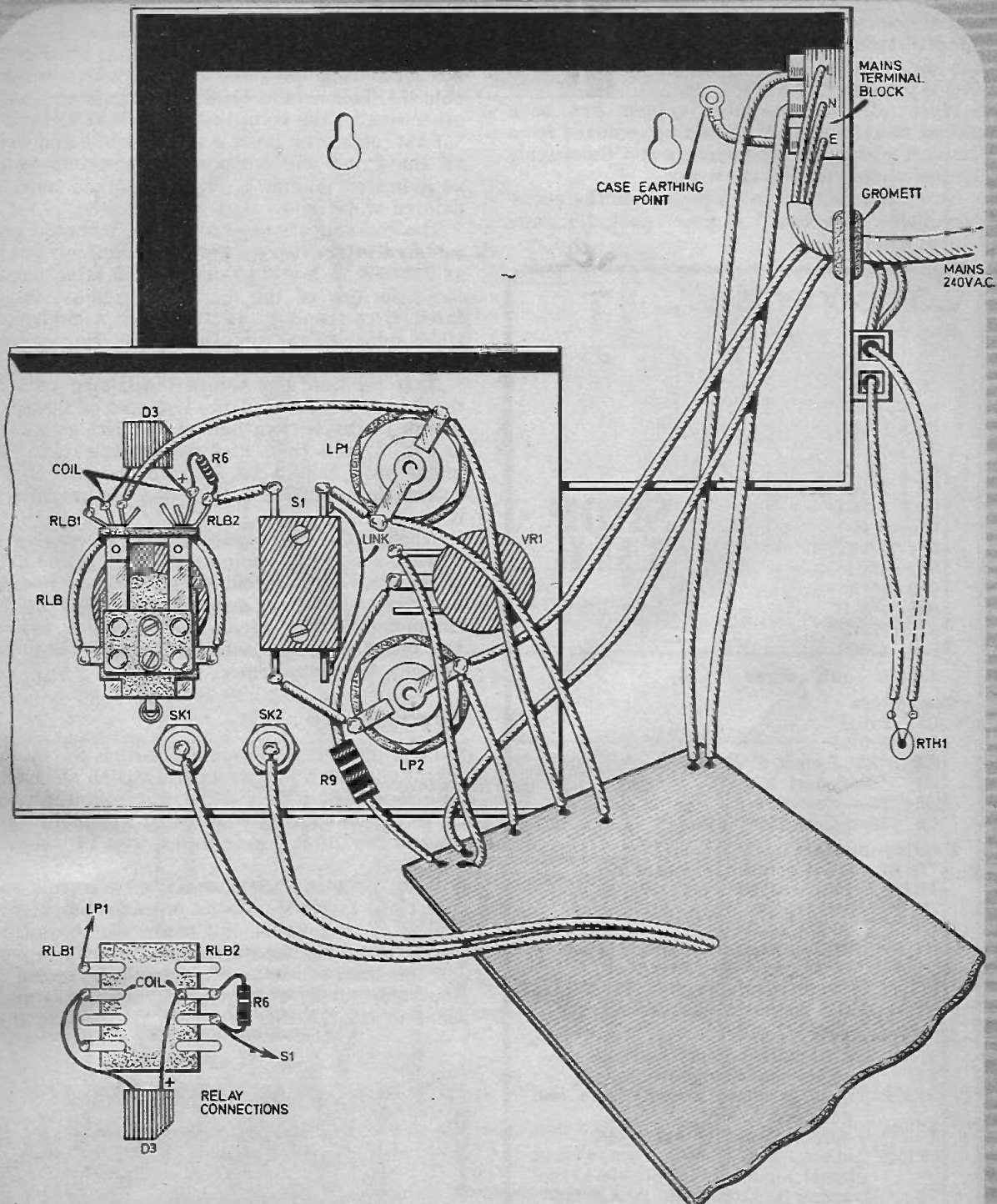


Fig. 3. The wiring up of the component board to the case mounted components. Also shown is the wiring around the buzzer relay.

# FREEZER TEMPERATURE ALARM



the lid closes down on the wires, the thermistor hanging in the freezer compartment.

With the freezer working normally, and set to "0" degrees centigrade, allow the thermistor to stabilise at the working temperature and then switch on the unit with S1 at alarm. Now connect a d.c. voltmeter set to read 10V in SK1 and SK2 and adjust VR1 to read zero volts. The lamp should stop flashing and the buzzer should cease to operate.


The Freezer Temperature Alarm will now trigger if there is a change of plus or minus 1.5 degrees centigrade. The length of the cable between the thermistor (in the freezer) and the unit adjacent to a convenient power point in the room of your choice can be as long as necessary (within reason).

## THERMISTOR


The foregoing setting up procedure is applicable where a type G14 thermistor is used, however, it is not essential that this particular type is used as any other type can be used providing its resistance is known or can be identified at 0, +2 and -2 degrees centigrade in which case

Replace R8 with a resistor of the value of the thermistor at 0 degrees centigrade. (2) With a resistor of the same ohmic value as the thermistor at +2 degrees centigrade fitted in place of the thermistor, adjust R12 and R13 until the alarm just comes in. (3) Remove this resistor and refit the thermistor and set up as described above.

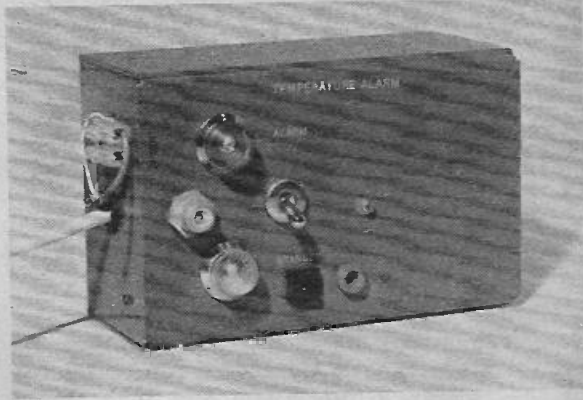the following procedure should be used: (1)



Photograph of completed unit.

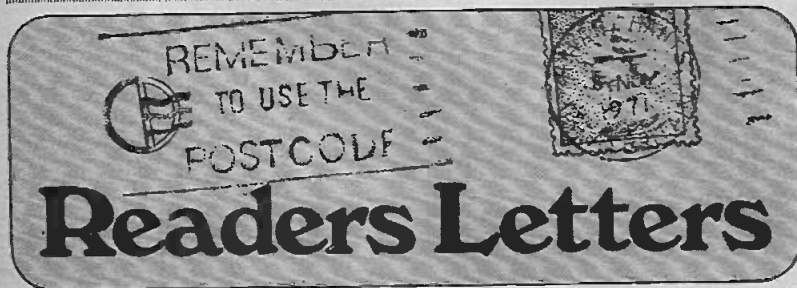

## Current Flow

I purchased the March '74 issue of E.E. today just to see how you were getting on as I have often recommended to friends that reading E.E. was a good introduction to the subject.

However having studied page 163 I am sorry to say that I will think twice before doing so again. How A. P. Stephenson can, in the space of two inches reverse the direction of current flow without a single word of explanation is beyond me. The effect of this rubbish on a person trying to grasp how a transistor works is confusing to say the least, and can only make the subject more difficult to understand.

Perhaps Mr. Stephenson would like to note that electron flow and current flow are the same thing, moving in the same direction (We only need "holes" wandering backwards, or is it forwards, to add to the confusion

and mumbo jumbo which exists.)

Please realise that your publication is read by school children who can ill afford to be mixed up by those who should know better.

Alexander C. Young,  
Director, Wilton Electronics  
(Scot.) Ltd.,  
Glasgow.

Your confusion over the difference between conventional current and electron flow is understandable because years ago I had the same trouble. The mix up started in the years of the pioneers, Kirchhoff, Ohm and Faraday when it was arbitrarily decided that "current" flowed from positive to negative and arrows showing directions have traditionally followed this convention. "Electrons" (which came later) were found to flow in the opposite direction—hence the confusion.

Regarding your specific criti-

cism, perhaps you might care to re-examine the offending "two inches of my article" and note that Fig. 7.1 is labelled "Electron-Flow" and Fig. 8.1 is labelled "Current Flow." The difference between electron flow and current flow was pointed out in the November 1973 issue of E.E.—A. P. Stephenson.

## Transistor Assisted Ignition

I have read with great interest in this month's magazine (April '74) of the Transistor Assisted Ignition. As I have a 6V system on my car, please could you tell me if this is suitable or would I need different components.

M. Steeden,  
Faversham, Kent.

We are looking into the suitability of the unit and we hope to publish some comments on the Transistor Assisted Ignition for 6V cars in the near future.

## Please Take Note


In the *Semiconductor Primer* page 281 last month. It was stated that  $I_{FE}$  was base current

this should have been collector current  
collector current  
base current

# TEACH-IN '74

FOR BEGINNERS IN ELECTRONICS...  
THEORY AND EXPERIMENTS

TUTOR: PHIL ALLCOCK\*

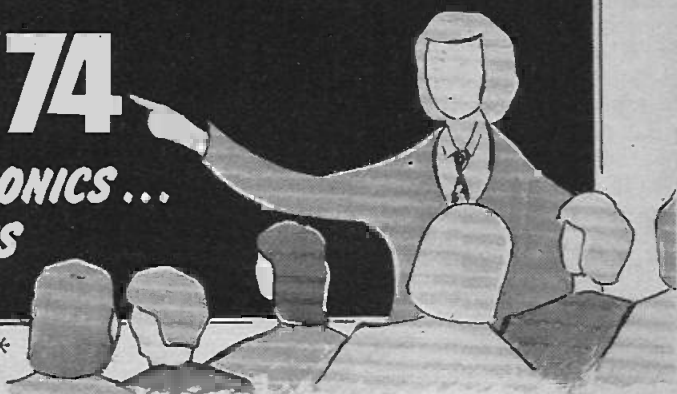

## LESSON 9 Inductance and the Transformer

INDUCTANCE is measured in terms of a basic unit known as the "henry" and it is a fundamental property that inductance can be related to the voltage across a coil and the rate of change of current through it. The symbol for a coil or inductor is given on the wall chart and the usual sub-divisions of the basic unit of one henry can be used e.g.  $1\text{mH} = (1/1000)\text{th}$  of one henry.

If a coil has an inductance ( $L$ ) of one henry and the current through it is made to change at a rate of 1 amp/sec., then a voltage difference of one volt will be present between the ends of the coil due to electromagnetic induction. The changing current sets up a changing magnetic field or flux and the voltage exists only whilst the current is changing.

A constant current of say one ampere would give zero voltage since the magnetic field and flux would be fixed. Obviously this is another example of a component that depends on the rate of change of a quantity. The voltage variation that would occur from the given current waveforms are shown in Fig. 9.1, it can be seen that in each case the coil voltage is given by

$$\text{Voltage} = L \times (\text{Rate of change of current}).$$

Consistent units are volts, henries and amps./second.

### REACTANCE

The sine wave variation, of current or voltage, will always have the standard shape and so it is possible to work out the maximum value of the rate of change which occurs each time the sine-waves passes through the zero axis. For the instantaneous current  $i$ , we can write

$$i = I_m \sin(2\pi ft).$$

Where  $I_m$  is the peak value of the wave and  $f$

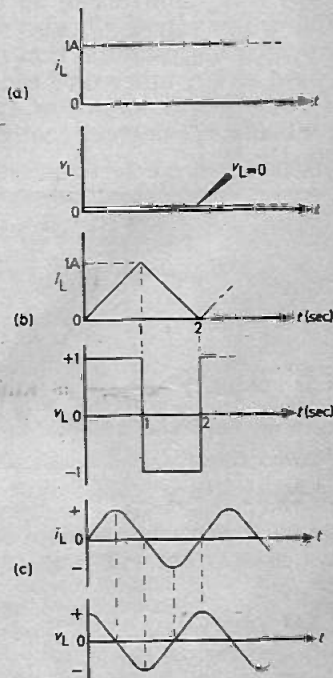
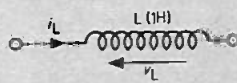


Fig. 9.1. Voltage and current waveforms for an inductor.

is the frequency in Hz. The maximum rate of change is given by  $2\pi f I_m$  whilst at the peaks of the wave, the rate of change is always zero. Using these facts we can write the peak voltage across the coil  $L$  as:

$$\begin{aligned} \text{peak voltage} &= L \times (2\pi f I_m) \\ &= (2\pi f L) \times (\text{peak current}). \end{aligned}$$

The quantity  $2\pi f L$  is shown as the inductive reactance of the coil and is a measure of its

\* North Staffordshire Polytechnic. Any communications arising from the Teach-In '74 series must be addressed to Everyday Electronics, Fleetway House, Farringdon Street, London E.C.4).

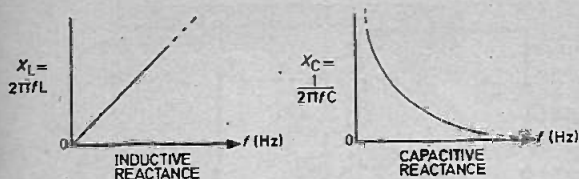


Fig. 9.2. Variation of reactance with frequency.

ability to limit alternating current flow. It is measured in ohms, just like resistance, but does not depend in any way on the resistance of the wire used for the coil. An ideal (perfect) coil would have no wire resistance but would have a reactance that depends on frequency  $f$  and inductance  $L$ , Fig. 9.2 shows how inductive reactance varies with frequency for a given value of  $L$ . A similar result can be obtained for the capacitor. If the voltage is written as  $V_m \sin(2\pi ft)$  then:

peak current =  $C \times$  (maximum rate of change of voltage)

$$I_m = C \times 2\pi f V_m$$

hence  $V_m = I_m \times \left( \frac{1}{2\pi f C} \right)$

The quantity  $\frac{1}{2\pi f C}$  is known as capacitive reactance and the variation with frequency is also given in Fig. 9.2. It is important to realise that a 90 degree phase displacement also occurs with the inductor, but in this case the current lags the voltage by 90 degrees (i.e. the voltage leads the current this time).

## RESONANCE

It is possible to produce some very interesting and useful effects by combining inductance and capacitance together. Since practical coils invariably have resistance we can simulate a real coil by studying an ideal resistor in series with an ideal inductor. Thus a series LCR circuit could be represented by the circuit of Fig. 9.3a.

If the current is assumed to be sinusoidal, the voltage across each element can be obtained using the ideas previously discussed and the total instantaneous voltage can then be obtained by addition of the individual voltage waveforms. The waveforms are shown in Fig. 9.3a and it is easy to see that the variations of voltage across  $L$  and  $C$  are in the opposite sense and therefore tend to cancel each other.

If the peak values are equal the cancellation will be perfect and this condition is known as series resonance. For cancellation, we must

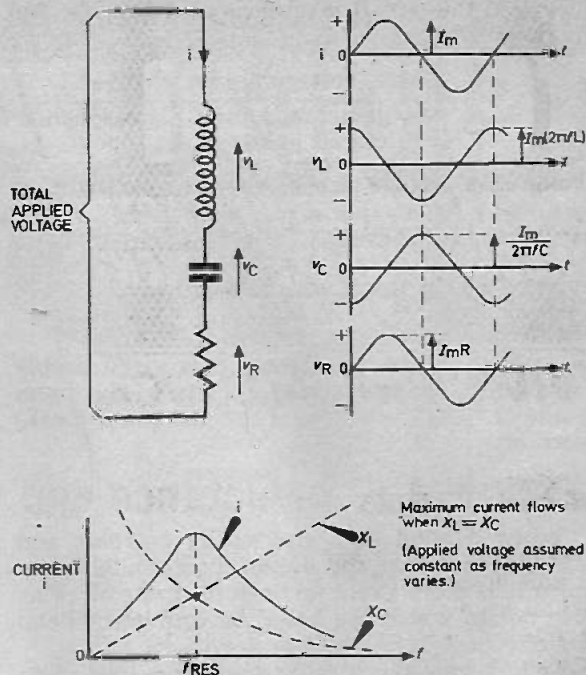


Fig. 9.3a (top) Voltage waveforms for an LCR series circuit. (b) Variation of current in a series resonant circuit.

make the peak values of  $v_L$  and  $v_C$  equal and this requires that

$$2\pi f I_m = I_m \left( \frac{1}{2\pi f C} \right)$$

rearranging terms gives  $f^2 = \frac{1}{(2\pi)^2 LC}$

hence  $f$  (resonance) =  $\frac{1}{2\pi\sqrt{LC}}$  Hz.

Thus, at this frequency (which depends on the  $L$  and  $C$  values) the voltages  $v_L$  and  $v_C$  completely cancel each other out, and the voltage across the complete LCR circuit is exactly the same as the voltage across the resistor. In fact at this one frequency the circuit behaves as a simple resistor of value  $R$ .

At other frequencies the total voltage (for a given current) will increase since the cancellation of  $v_L$  and  $v_C$  will be incomplete. If we apply a constant voltage at various frequencies to a series LCR circuit the current will vary as shown in Fig. 9.3b. Note that at the resonant frequency the current is at its maximum value.

## CIRCUIT MAGNIFICATION

At resonance the voltage across either  $L$  or  $C$  can be considerably greater than the voltage applied to the circuit. The ratio of these voltages



is called the circuit magnification factor  $Q_0$  and is given by

$$Q_0 = \frac{\text{Max. voltage across whole}}{\text{Max. voltage across } L \text{ (or } C \text{) at resonance circuit at resonance}}$$

Since the voltage across the whole circuit at resonance equals that across  $R$  we have

$$Q_0 = \frac{(2\pi fL) I_m}{R I_m} = \frac{2\pi fL}{R}$$

Note that the voltage across  $R$  is given simply by Ohm's law and therefore has a maximum value of  $I_m \times R$ , where  $I_m$  is the maximum (peak) current.

### R.M.S. VALUES

When dealing with alternating currents and voltages that have the standard sinusoidal waveform it is more usual to work in terms of *effective values* which are based on equivalent heating effects.

To illustrate this idea let us suppose that when we pass an alternating (sinusoidal) current, of peak value  $I_m$  amps, through a resistance of value  $R$  ohms, the *average* power dissipation is given by  $P_{AV}$ . (The instantaneous power will be fluctuating throughout each cycle as the current varies.) If we set up an equal value resistor with a *steady* current  $I$  and adjust  $I$  to give the *same average power dissipation* as in the first resistor, then  $I$  is defined as the effective or root-mean-square (r.m.s.) value of the alternating current. For sinusoidal currents the relationship is

$$I \text{ (r.m.s.)} = \frac{\text{peak current}}{\sqrt{2}} = \frac{I_m}{\sqrt{2}}$$

Since  $\frac{1}{\sqrt{2}} = 0.707$ , the r.m.s. value of the

current is approximately 71 per cent of the peak current. A similar proportionality exists between r.m.s. and peak voltages providing the waveform is sinusoidal.

### MEASUREMENT OF ALTERNATING CURRENT/VOLTAGE

All the measurements made so far in the series have been possible using a 0-1V or 0-10V voltmeter. The moving coil of the  $100\mu\text{A}$  meter carries the current and rotates due to the interaction of the magnetic field of the coil and the permanent magnet system which surrounds the moving coil. The coil also experiences a restoring force provided by the fine "hair springs" and thus rotates until all the forces balance.

If we apply an alternating voltage to our 0-10V voltmeter the coil will try to rotate one way,

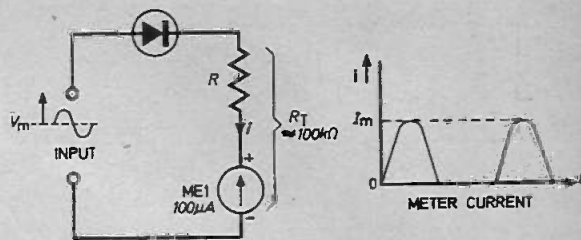


Fig. 9.4 "Halfwave" voltmeter circuit.

then the opposite way and the net deflection will be zero. Only if the applied waveform has a non-zero average value (over one cycle) will the meter respond.

To make a simple voltmeter for alternating voltages we can use a diode in series with the usual meter circuit so that current can flow only for one half cycle of the input. If we neglect the forward voltage drop across the diode the meter will respond to the *average* value of the half-wave voltage variation as shown in Fig. 9.4. The current in the meter consists of a series of unidirectional half-sine wave pulses having a peak value of  $V_m/R_T$  where  $R_T$  is the total resistance of  $R$  and the meter together. The average value of this current can be shown to be  $I_m/\pi$  i.e.  $0.318(I_m)$ . Thus a sinusoidal voltage of say 10 volts (r.m.s.) would have a peak value of  $10\sqrt{2}$  volts and since  $R_T$  is approximately 100 kilohms the peak current can be found.

$$I_m = \frac{14.14}{100,000} = 141.4\mu\text{A}.$$

For this input, the meter will indicate a current of  $141.4 \times 0.318 = 45\mu\text{A}$ .

In practice the forward voltage drop across the diode would give a reading somewhat less than this. Assuming that 0.6 volts is "lost" across the diode the actual reading will be about  $43\mu\text{A}$ .

By using four diodes it is possible to get almost double this deflection, for the same voltage input, by passing current through the meter for each half cycle in the *same* direction.

The circuit for this full-wave rectifier meter is shown in Fig. 9.5. When  $A$  is positive with respect to  $B$ , diodes  $D1$  and  $D2$  conduct and  $D3$  and  $D4$  are reverse biased. When  $B$  is positive with respect to  $A$ , the roles of the diodes are changed and  $D3$ ,  $D4$  now conduct. Note that current flow in the meter is always in the same direction. Since the number of current pulses/sec. is now doubled, the average current and therefore the meter reading is doubled.

The improvement is not exactly a factor of two since the circuit now introduces two diodes in series each half cycle and the voltage drop is therefore increased. The meter will indicate approximately  $80\mu\text{A}$  for a 10 volt r.m.s. input.

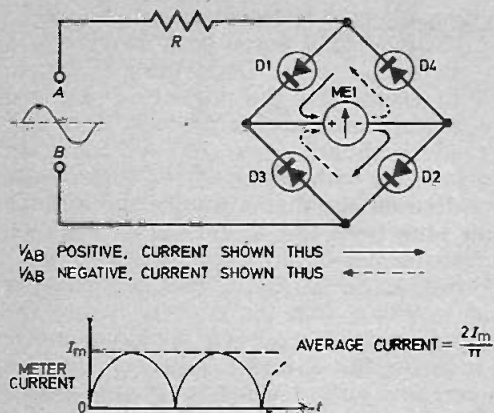


Fig. 9.5 "Full-wave" voltmeter circuit.

### THE ALTERNATOR

We have introduced the idea of alternating voltage and current and also examined the behaviour of resistance, capacitance and inductance in situations involving alternating current. The usual household mains supply is generated at a power station by an electrical machine known as an alternator. (Yes, you are right! A smaller version of the same device is used in the electrical system of the modern car.)

In its simplest form a coil of wire (the rotor) is turned between the poles of a magnet. See Fig. 9.6. Connections are made to the ends of the coil by contacts which press on two slip rings. When the coil rotates in the magnetic field produced by the (stator) magnets a voltage is induced in the coil by electromagnetic action.

The voltage is found to depend on the rate of change of magnetic flux linking the coil and the situation is illustrated in Fig. 9.7. The rate of change of flux linkage is seen to be a maximum when the coil sides are actually moving across the magnetic field lines (which merely represent the actual magnetic field in our diagram) and is a minimum when the coil sides are moving along the field lines.

The generation of one complete cycle of the sine waveform that is produced by this alternator is shown in Fig. 9.7 and it can be seen that the voltage  $V_{AB}$  measured between the two slip rings reverses polarity every half revolution of the coil.

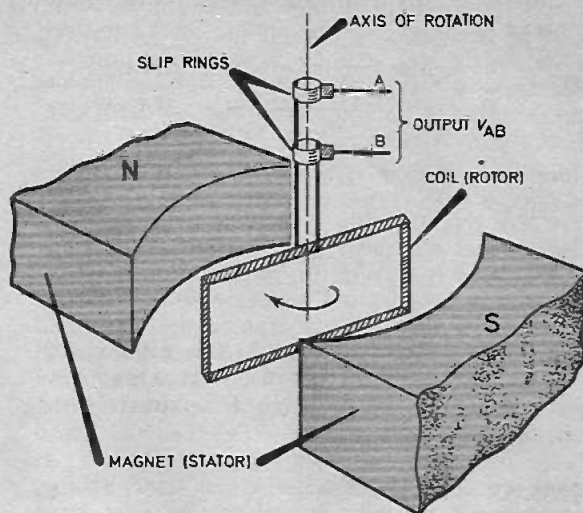


Fig. 9.6. A diagram of a simple alternator.

In the power station the rotor coil is driven by a steam turbine and the speed of rotation is held fairly constant. Since each revolution gives one complete cycle a constant alternator speed will produce an output having a constant frequency (number of cycles per second). Use is made of this constant frequency feature in the household (mains) electric clock which employs a synchronous motor that revolves in step (i.e. synchronism) with the mains supply frequency.

### TRANSFORMER PRINCIPLE

It is not necessary to use a permanent magnet and a moving coil to utilise the electromagnetic induction effect. The essential requirement is a flux linkage which can be changed with time and the resulting voltage will always depend on the rate of change of the flux linkage. A transformer is simply a set of two or more coils that share a common core of magnetisable material, such as soft iron, and in use one coil is used to set up a time varying magnetic field which links with the other coil or coils to generate an output voltage.

It will be apparent from what we have said so far that the transformer can only work if the magnetic field in the core is made to change and because of this a transformer cannot be

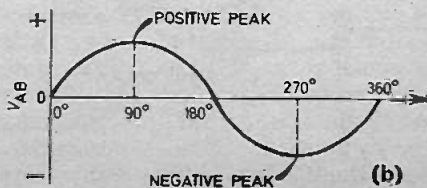
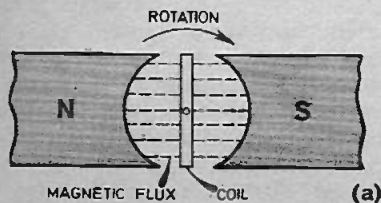


Fig. 9.7a. Coil position for zero output voltage  
(b) Variation of  $V_{AB}$  with coil angle for one complete cycle.

usefully employed with direct (steady) current.

One of the greatest attractions of alternating current is that it can be used in conjunction with transformers to change voltage levels (magnitudes) either up or down without significant loss of power. The efficiency of a well designed transformer is usually in excess of 95 per cent.

We will examine the transformer in more detail since it is obviously a very useful component and is widely used in electronic systems, especially in power supplies derived from mains.

One of the coils of the transformer is called the **primary** and may consist of many thousands of turns of fine insulated wire (for mains inputs). The other coil, which is wound on the same magnetic core, but is electrically insulated from the primary coil, is known as **secondary** coil. Transformers can have one or more secondary coils and the coils may have different numbers of turns.

**Next month:** More on transformers, plus the reed relay, and loudspeaker.

## TUTOR BOARD EXPERIMENT

### Test No. 19

The Friedland bell transformer can supply 3, 5 or 8 volts (r.m.s.) from normal 240 volt mains supplies. The low voltage output is quite safe but the windings should never be short circuited. The mains (primary) coil must be connected to a suitable lead and plug, to fit the outlets in use in the home. **Under no circumstances should any connections be made, or changed, with the**

**mains plug connected to the household supply.**

Where possible use a fused plug fitted with a low current fuse (1 amp). Do not use a 13 amp fuse as this cannot give the protection required with low power consumption devices. If in any doubt, readers should seek the assistance of someone familiar with mains wiring techniques. **Always switch off the mains supply and remove the mains plug from the socket before connecting the transformer to any Tutor Board circuit.**

Using two leads to the 3 volt transformer secondary winding, join the transformer to the half-wave voltmeter circuit (Fig. 9.4). The meter should indicate the average value of the low voltage rectified output when the mains is connected. The diode can be a 1N4001 or similar type. Repeat the test using the 5 volt and 8 volt output of the transformer in turn.

Always disconnect the mains before altering the transformer connections. Check that the readings agree with the theory. The 3, 5 and 8 volt markings are only approximate (r.m.s.) values and the results may be affected by mains voltage variation from the nominal 240V.

Restore the connections to the 3 volt transformer winding and repeat the measurement with a 250 $\mu$ F capacitor connected across the meter and its 100k $\Omega$  resistor. The positive side of the capacitor should be connected to the diode cathode and the negative side to the meter negative terminal. The circuit can be set up on the Tutor Board, as shown in Fig. 9.9, which uses the switch S1 to connect the capacitor as required.

In this test the voltmeter responds to the **peak** voltage when S1 is closed. Check your results to see if they are consistent.


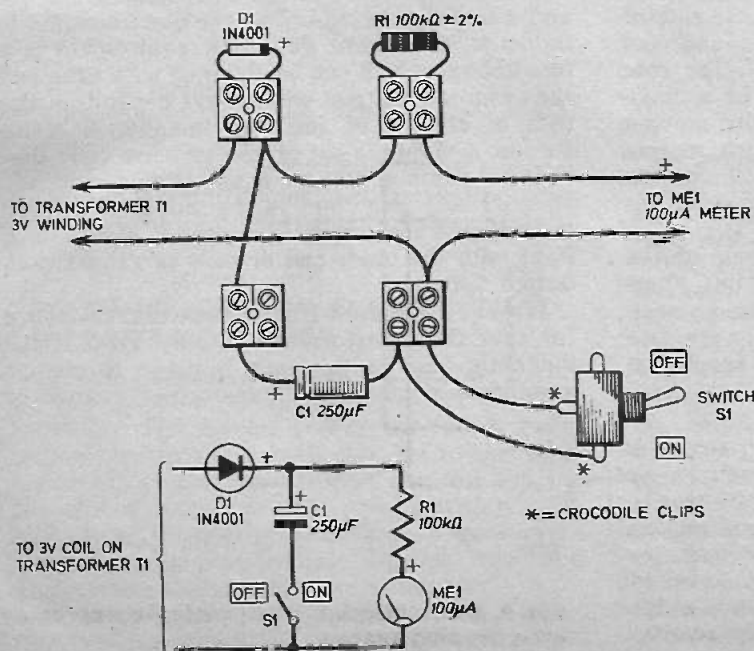


Fig. 9.9. Test circuit and wiring on the Tutor Board for Test No. 19.

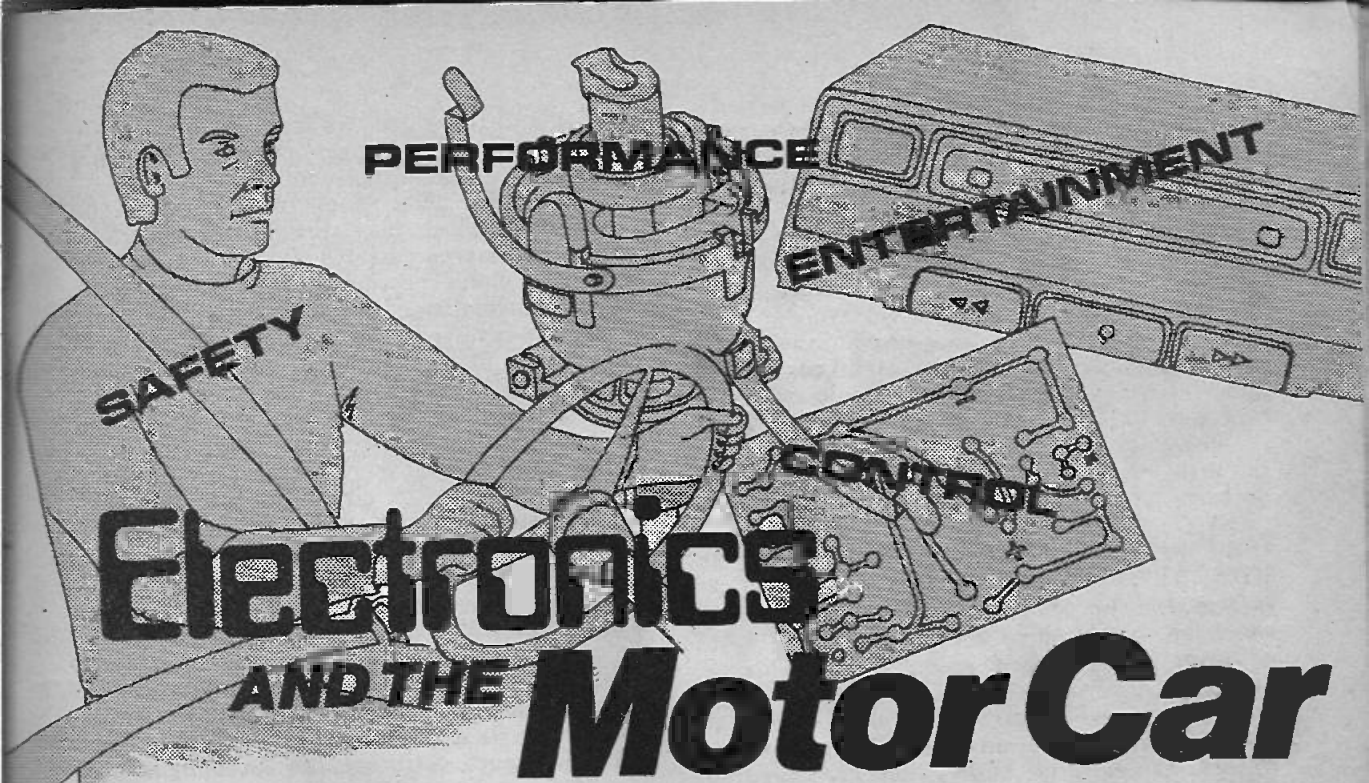



By C.S. POINTER

HAVING dealt with electronics related to diagnosis, performance and safety last month we now move on to control and security.

### CONTROL AND VEHICLE SECURITY

Electronic control may be applied to many systems and units in the car. With custom built thick film integrated circuits which are now being used throughout the electronics industry, electronic control is becoming more practical. Electronic intermittent wiper controls have been available for some time and are now being fitted to some modern cars.

Electronic control of electrical cooling fans uses a thermistor sensor and a Schmitt trigger circuit to switch a relay or power transistor in the fan motor circuit.

Light sensors together with amplifiers and power switching circuits are used in systems which dip the interior mirror when the light from the following cars falls on the mirror light sensor, or systems which detect the light from on-coming vehicles and then dip the headlamps, Fig. 6 shows the block diagram of a headlamp dipping unit.

Car alternator voltage regulators use electronics to control alternator output voltage and limit current output. The regulator units monitor the rectified output from the alternator and regulate the output by varying the field produced by the field winding thus providing constant voltage output. The three-phase output from the alternator being rectified by semicon-

ductor diodes mounted on a suitable heatsink. The various regulator units vary from printed circuit assemblies to thick film integrated circuits.

There are under development several vehicle speed control systems either using roadside transmitter units or cables under the road sur-

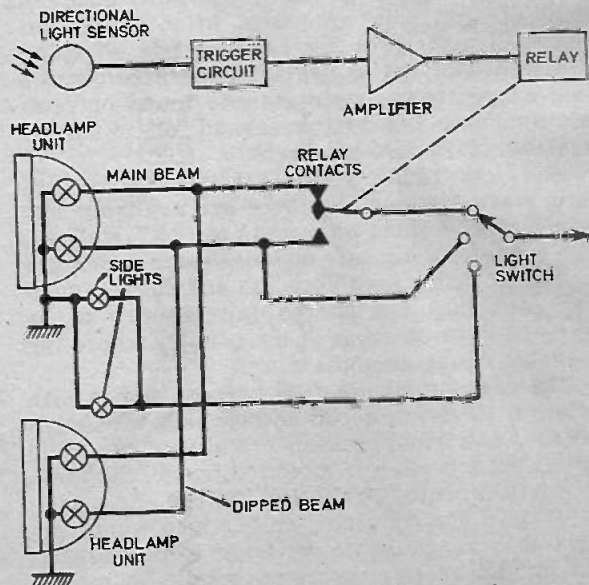


Fig. 6. Block diagram of an automatic car headlamp dipping system.



The Heathkit engine analyser, a useful instrument for the practical man.

face to transmit information to vehicle mounted receivers connected to the speed control unit, or using a dashboard mounted control unit enabling the driver to select a cruising speed and the unit will control the vehicle speed at the set value until any of the normal car controls, accelerator, brakes, etc. are operated thus reverting speed control to the driver.

Vehicle security systems include alarms and immobilising systems. Alarms switching the car horn on and off, or operating a siren are triggered by various sensors mounted on the car, door switches, mercury switches detecting vibration caused by an intruder or triggered from the ignition switch if the alarm has not been reset.

## ENTERTAINMENT

The car radio is probably the most common item of electronic equipment fitted to cars on the road today. The car radios produced today are transistorised or contain integrated circuits and range from simple manual tuned or push button single and dual waveband sets to station seeking, multiwave band sets.

Most car radios receive medium wave and long wave stations but there are available sets which receive short wave and f.m./v.h.f. stations, the range of v.h.f. sets includes some which are equipped with stereo decoders and stereo amplifiers enabling f.m. stereo programmes to be enjoyed in some areas of the country where the signal is strong enough.

There are available dual purpose radios with internal batteries, aerial and speaker which can be used as normal portable radios until the radio is pushed into the car mounted frame, the radio is then connected to the car battery and aerial; also there are converter units which when connected to any medium wave car radio converts the radio to receive shortwave bands.

Together with car radios, increasing numbers of tape players and record players are being fitted to cars. Tape players are becoming very

popular and there are two main systems in use today, these are compact cassette units and eight-track cartridge stereo units.

The cassette units range from simple mono player units which play through the car radio amplifier to stereo cassette players with built in amplifiers, mono recorder and f.m. stereo radio.

A new development in the cassette player field is the auto-reverse stereo player shown in Fig. 7. This unit is fitted with small magnets on each take-up turntable which switch reed switches. When the end of cassette tape is reached and the take-up turntable stops revolving, the drive clutch slips. The absence of an output signal from the reed switch circuits due to the turntable stopping, trigger, via a control circuit, a solenoid which reverses the cassette drive direction and switches from one pair of tape head windings to another. The unit gives continuous music without the need to remove and turn over the cassette at the end of the track; the direction of play can be reversed at any time by pressing a panel mounted button. Also fast forward/fast reverse facility is available.

The compact cassettes can be bought pre-recorded or recorded using the standard domestic cassette recorders which are in wide use today.

The eight track cartridge player uses a cartridge which contains an endless loop of tape with eight tracks which are pre-recorded with four stereo programmes. There are available eight track cartridge players with radio and for some units there is available a converter which slots into the unit in place of the cartridge giving f.m./v.h.f. stereo radio reception.

Modified versions of the cartridge player which take cartridges recorded with quadrophonic programmes, two programmes each of four channels played through four speakers mounted at each of the four corners of the car.

One or two of the more expensive cars have as optional equipment television receivers mounted out of the driver's view, but these are few and far between.

## COMMUNICATION

Car communication using transmitter/receiver has been in use for a long time, used by police, fire brigade, ambulance, taxis and many large

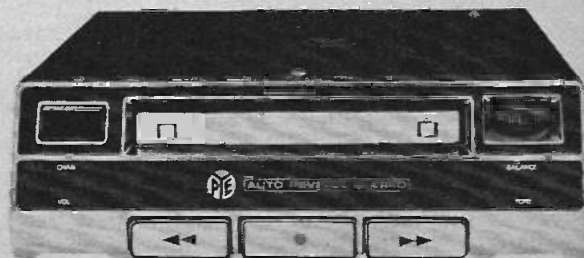


Fig. 7. The Pye auto reverse stereo tape player.

companies for communication between base and cars on the road. The private motorist and the company executive can now in some areas have fitted to his car a GPO radio telephone or a transmitter/receiver hired from a company running a radiophone service.

Under development is a system which is intended to relay traffic information and warnings to the driver through the car radio. Roadside transmitters being used to transmit local information when conditions arise requiring warnings to be given, a receiver mounted in the car picks up the signals and interrupts the normal programmes with the warnings. The receiver may be a separate unit connected to the car radio or it may be part of the radio itself.

## CONCLUSIONS

In order to power some electronic equipment from a car electrical system it may be necessary to include a power unit to convert the 12V or 6V d.c. supply to a higher or lower voltage or to a.c. voltage, such as the d.c./a.c. inverter in E.E. July 1972. (No longer available.)

By use of these various power supplies a wide range of electronic equipment may be powered from the car electrical supply.

As the electronics industry develops new and more advanced techniques many of these may benefit the motorist indirectly in making available more items of electronic equipment to the motorist and motor manufacturers.

In general electronic units fitted to production cars are of the plug-in type making replacement fairly simple. The majority of electronic equipment is very reliable and should last for the life of the car.

Large electronic digital computer systems are used in production control, car design, spares distribution by the large manufacturers and in some countries used car testing is computer controlled.

This article has covered some of the applications of electronics connected with cars and motoring, which is a very wide field. □



A compact m.w. and l.w. car radio complete with fixings and speaker from Bosch Ltd.

## Ruminations By Sensor

### Anyone for Tennis?

An ingenious variation on the pin table theme is getting around the country. The apparatus looks like a large table model TV but its circuits probably have more in common with radar than with television. When the appropriate coins are put into the slot, a spot of light begins to bounce across the "court" and short vertical lines, which represent racquets, can be moved vertically by the players' controls in order to intercept the "ball".

The apparatus emits a realistic echoing "plunk" when the "ball" hits the racquet and the "ball" bounces back to the opponents on the other side of the "court".

If the ball goes out of court the player is admonished by a suitable "brrrp" noise and the score points on the screen record the error.

Apart from enjoying my game of electronic tennis—even though I lost, I got a lot of fun from speculating how the thing works. No doubt many readers will have a shrewd idea of what lies behind the electronic court—indeed, I would not be surprised to see something of this nature appear as a constructional project in the future.

### On Load

I read recently that one of Britain's fast breeder reactors is now producing power, a whole 100 watts of it! This is just a start of course, the reactor output will be in megawatts when things really get going.

My own knowledge of nuclear power generation is minimal and I ought to refrain from comment, but the thought of this huge and highly complex and expensive

plant somehow sweating away to generate 100 watts seems ludicrous—like the mountain labouring and giving forth a mouse.

Britain led the world in nuclear power generation but the suggestion made some weeks ago that the CEBG were thinking of buying American built reactors leads one to suppose that we may be falling behind. I hope that this is not the case.

This country has been accused of being very good at research but poor at production, and there is certainly some measure of truth in the accusation. I have known many engineers and physicists who had an aversion for production and "sordid commercialism" and wished only to spend their lives "playing" in the laboratory. Certainly, a research laboratory can provide a comfortable, sheltered environment where one can work happily doing one's own thing, but is this the best way of getting things done?

Perhaps the root of most of the problems lies in our educational system, is it too academic?




80m & 160m

# AMATEUR BANDS RECEIVER

BY R.A. PENFOLD

A direct conversion receiver that will receive s.s.b. and c.w. transmissions.

ALTHOUGH some years ago a.m. (amplitude modulation) was probably the main form of transmission used on the amateur bands, this is no longer the case, and a form of transmission known as s.s.b. (single sideband) has now almost entirely replaced a.m. The main advantage of s.s.b. is that it makes full use of the output power of the transmitter, as unlike an a.m. transmission, only part of the signal that contains the information to be sent is transmitted, and the rest is suppressed. This is especially important when one considers the low transmitter power limit enforced on the amateur bands.

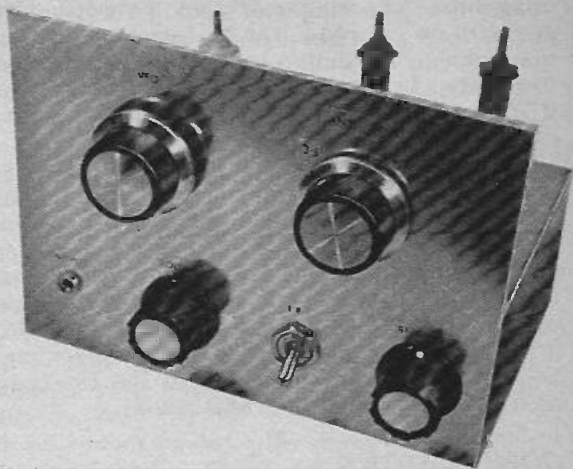


Another advantage is that an s.s.b. signal occupies less than half the band space occupied by an equivalent a.m. signal, which helps to ease the problem of overcrowding on the bands.

Ordinary a.m. receivers are unsuitable for s.s.b. reception, and for the other main mode used, c.w. (continuous wave—morse code). The circuitry used in amateur receivers is therefore rather specialised. The most simple type of receiver suitable for amateur band reception is the direct conversion type. The receiver described here is of this type, and covers two amateur bands, 80 metres (3.5 to 3.8MHz), and 160 metres (1.8 to 2MHz). The receiver is battery powered, and the output is for high impedance headphones.

## DIRECT CONVERSION OPERATION


A direct conversion receiver is so called as it converts the received r.f. (radio frequency) signal direct to an a.f. (audio frequency) signal, using a mixing process; Fig. 1 shows a block

Fig. 1. Block diagram of a direct conversion receiver.

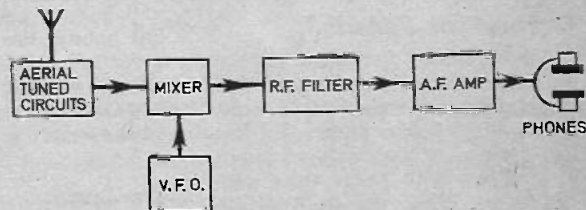

FOR GUIDANCE ONLY

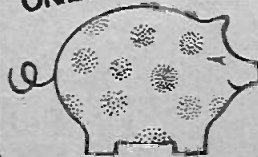ESTIMATED COST\* OF COMPONENTS including V.A.T.



£8.20 plus chassis and headphones

\*Based on prices prevailing at time of going to press

diagram of the stages of such a receiver. The mixer forms the heart of the receiver. The output of this is equal to the two sets of input frequencies, plus their sum and difference frequencies.

Supposing for instance that a 3.7MHz c.w. signal is to be resolved, by tuning the v.f.o. (variable frequency oscillator) to 3.701MHz, and the aerial tuned circuits to peak the signal, the output will be: 3.7MHz and 3.701MHz (the input frequencies), the sum of the two, 7.401MHz (3.7+3.701), and the difference between the two, 1kHz (3.701-3.700).

The r.f. filter will remove the r.f. part of the output signal, and only allow the audio frequencies to pass to the audio amplifier. In our example the 1kHz signal is the only audio signal.


The v.f.o. frequency can be either just above or just below the transmission frequency (3.700-3.699 also equals 1kHz). In practice the oscillator would be tuned to whichever side gives the

most interference free signal. The audio signal does not have to be at 1kHz, and the v.f.o. is adjusted to give the frequency that the operator finds most acceptable.

An s.s.b. transmission consists of a variety of radio frequencies, which when properly mixed with oscillations of the correct frequency, produce the original audio frequencies. The mixing process operates in the same way as for a c.w. signal, except that instead of one radio frequency producing one audio frequency, a complex radio signal produces the complex sound of the human voice.

Tuning an s.s.b. signal is more critical than tuning a c.w. one as, if the v.f.o. is slightly off tune, the audio signal will sound rather high, or rather low pitched. There are two types of s.s.b. signal, lower sideband, and upper sideband. With lower sideband the v.f.o. is tuned just above the signal frequencies, and with upper sideband it goes just below them.

Fig. 2. Complete circuit diagram of the 80 and 160m Amateur Bands Receiver.

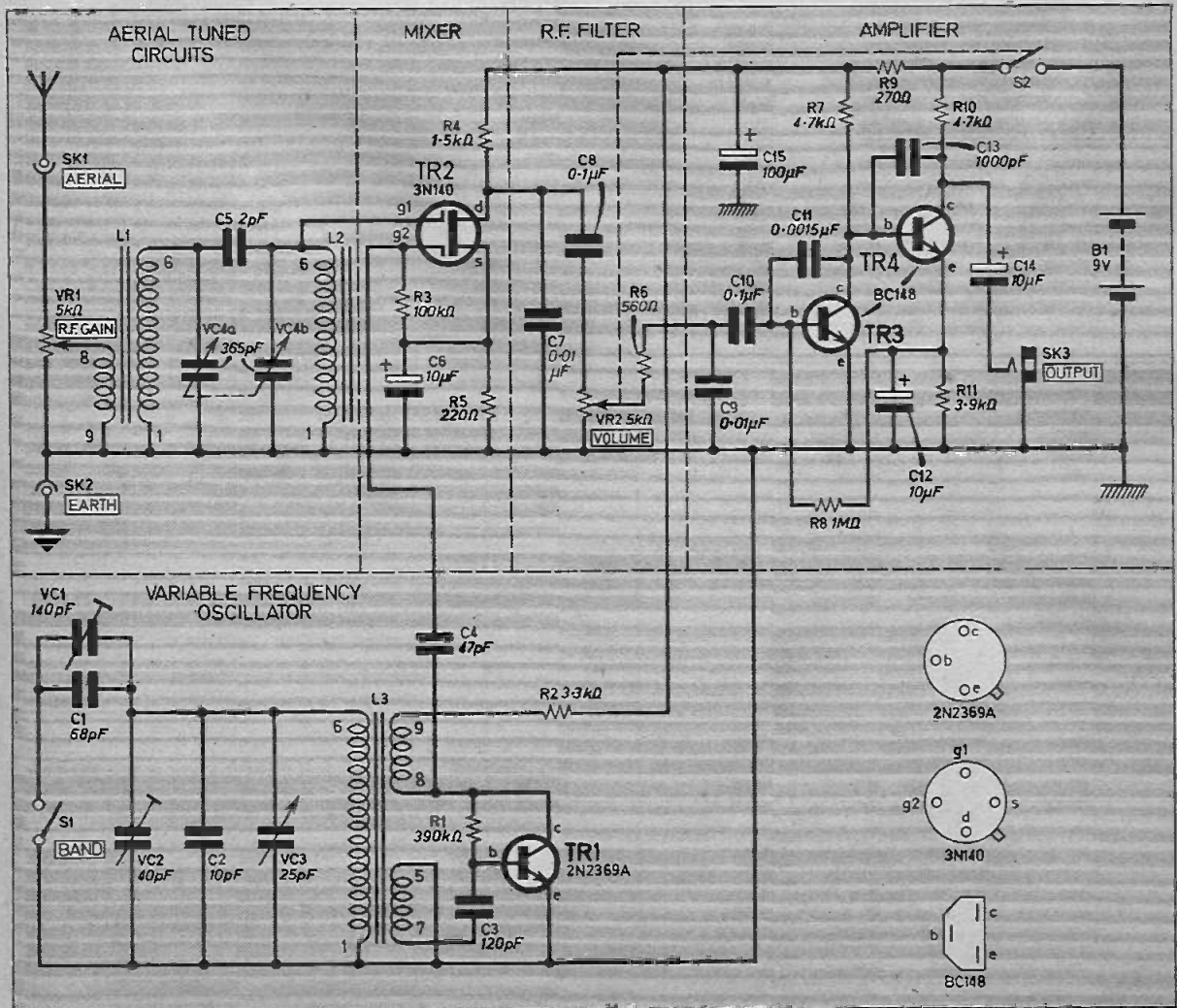

## CIRCUIT

A circuit diagram of the receiver is shown in Fig. 2. TR1 is used in a simple v.f.o. This is tuned by VC3. With S1 open this tunes the 80 metre band, and with S1 closed the additional capacitance of VC1 and C1 allow the 160 metre band to be tuned.

Transistor TR2 is the mixer, and uses a special type of transistor, a dual-gate MOSFET. The aerial signal couples via the r.f. gain control, VR1, and the input tuned filter to one input of TR2. The input filter can be tuned to either band by adjusting VC4. The v.f.o. couples to the other input of TR2, and it modulates the aerial signal, the mixed output appearing at the drain of TR2.

Capacitor C7, C9 and R6 form the r.f. filter, TR3 and TR4 form a high gain two stage audio amplifier, feeding a pair of high impedance headphones. Potentiometer VR2 is the volume control, and is ganged with the on/off switch S2. Low frequencies are attenuated by the low value of the coupling capacitors, C8 and C10, and the two feedback capacitors, C11 and C13 give high frequency attenuation. This gives a considerable reduction in noise, and reduces adjacent channel interference.

## CHASSIS AND PANEL

A ready made 150×100×50mm aluminium chassis is used. The front panel is made from 18 s.w.g. aluminium, and measures 150×115mm. This will probably have to be cut from a larger piece.

The three coils are mounted in ordinary B9A valveholders. The 20mm diameter cut outs for these are most easily made using a 20mm chassis punch. The coil holders are each mounted by two 6BA bolts. A 6BA solder tag is mounted on one of the mounting bolts of the holder for L1, and another on one of those for L3 (see Fig. 5). Control VC4 is mounted by two short 4BA bolts which pass through the appropriate holes in the chassis from underneath, and screw into the two threaded holes on the underside of the capacitor.


Mounting holes for SK1 and SK2, must be made to suit the particular make of socket used. The positions of the mounting holes for the component panels are marked using the panels themselves as templates. The chassis and panel are held together by SK3, VR2, S1 and VR1.

## COMPONENT PANELS

The bulk of the circuitry is contained on two component panels, one for the v.f.o., and the other for the mixer and audio stages. These are made using 0.1 inch matrix plain board. Construction of these is illustrated in Fig. 3 (oscillator), and Fig. 4 (mixer). The boards are cut to the sizes shown from the larger size in which the board is sold, using a small hacksaw.

The components are mounted in the positions shown, and their lead outs are bent over at 90 degrees on the reverse side of the panel. These are then soldered together, this wiring also being shown in the respective figures. In most cases the component leads are long enough to

Fig. 3. Layout and wiring of the variable frequency oscillator board.

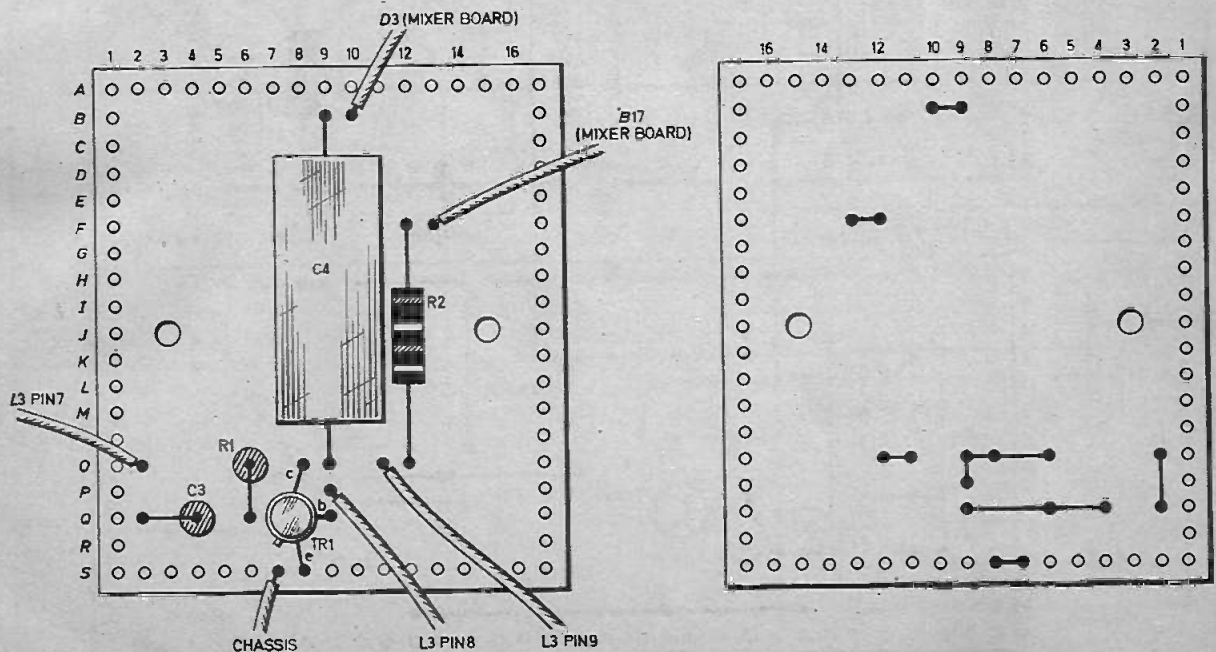



facilitate this, but in a few cases it will be necessary to use short lengths of tinned copper wire as extension leads.

For anyone new to this method of construction, it is advisable to start with the v.f.o. panel, as this is simpler. Transistors TR3 and TR4 have special lead outs which "plug" into the board, TR2 is supplied with a wire clip which shorts all the leads to its case. **This must not be removed until all the wiring has been completed, and checked, otherwise the device could be damaged.**

Where leads emanate from the panel, thin insulated leads are soldered in place. The approximate length of these can be judged by reference to the unit itself, and the complete wiring diagram of the receiver, Fig. 5. These can be made slightly on the long side so that the free ends of these can be cut to length, and connected up when the panels have been mounted.

The completed panels are mounted by two 6BA bolts for each. Two extra nuts are placed over each bolt between the chassis and the board, in order to hold the underside wiring of

the board slightly clear of the chassis.


The wiring diagram, Fig. 5, is largely self explanatory, and the main points to bear in mind are that all wiring should be as short as possible, and to make sure that VC1 and VC2 are mounted so that they can be easily adjusted. The battery is mounted on a small aluminium bracket glued on one side of the chassis. This can be seen in the photographs.

### SETTING UP



The receiver has no internal aerial of any kind, and a long wire aerial is required. A short indoor aerial will probably provide reception of a few stations, but for serious listening a proper aerial is essential. This consists of a long length of wire (16 s.w.g. or 7/22) insulated and set as high as possible. The ideal length is 40m (132ft), but 20m (66ft) should be quite adequate.

An earth connection may improve reception, this can be made with a buried metal plate or pipe connected to SK2, which connects to the receiver.

Fig. 4. Layout and wiring of the mixer and amplifier board.

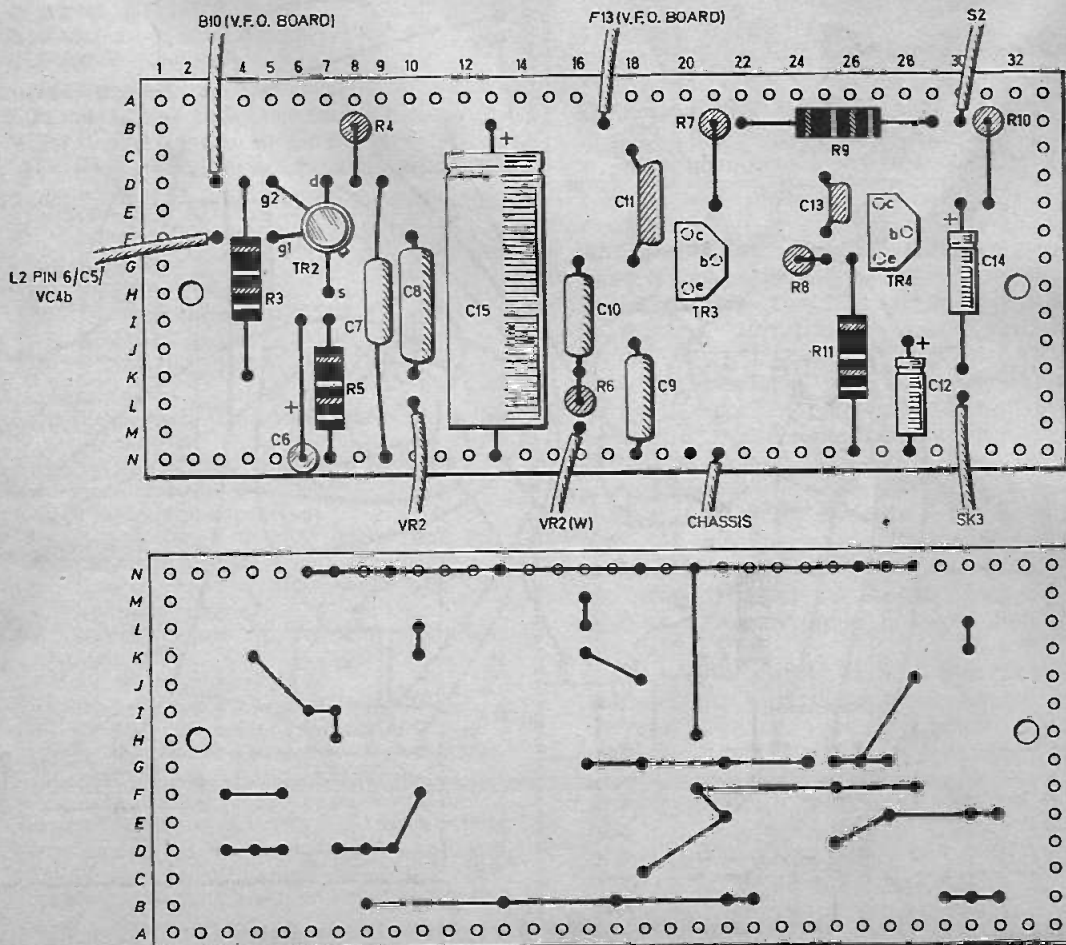

# AMATEUR BANDS RECEIVER

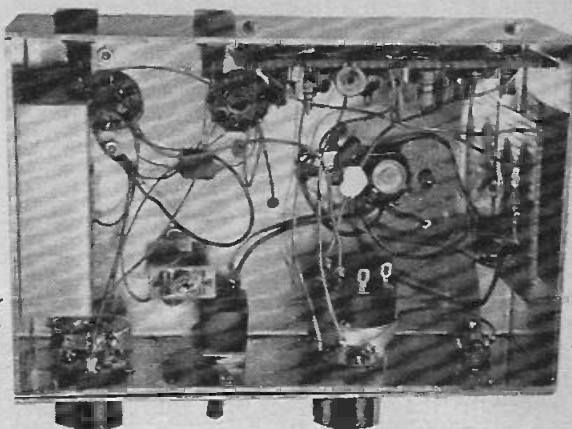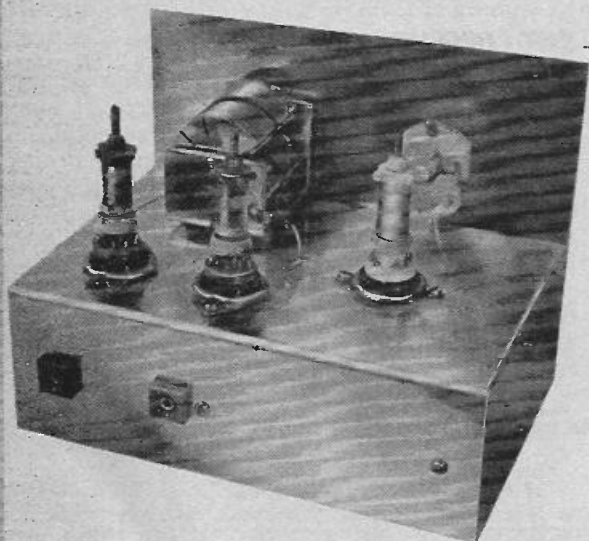

Above. Photograph of the underside layout and wiring.

Left. Photograph of the back of the completed receiver.

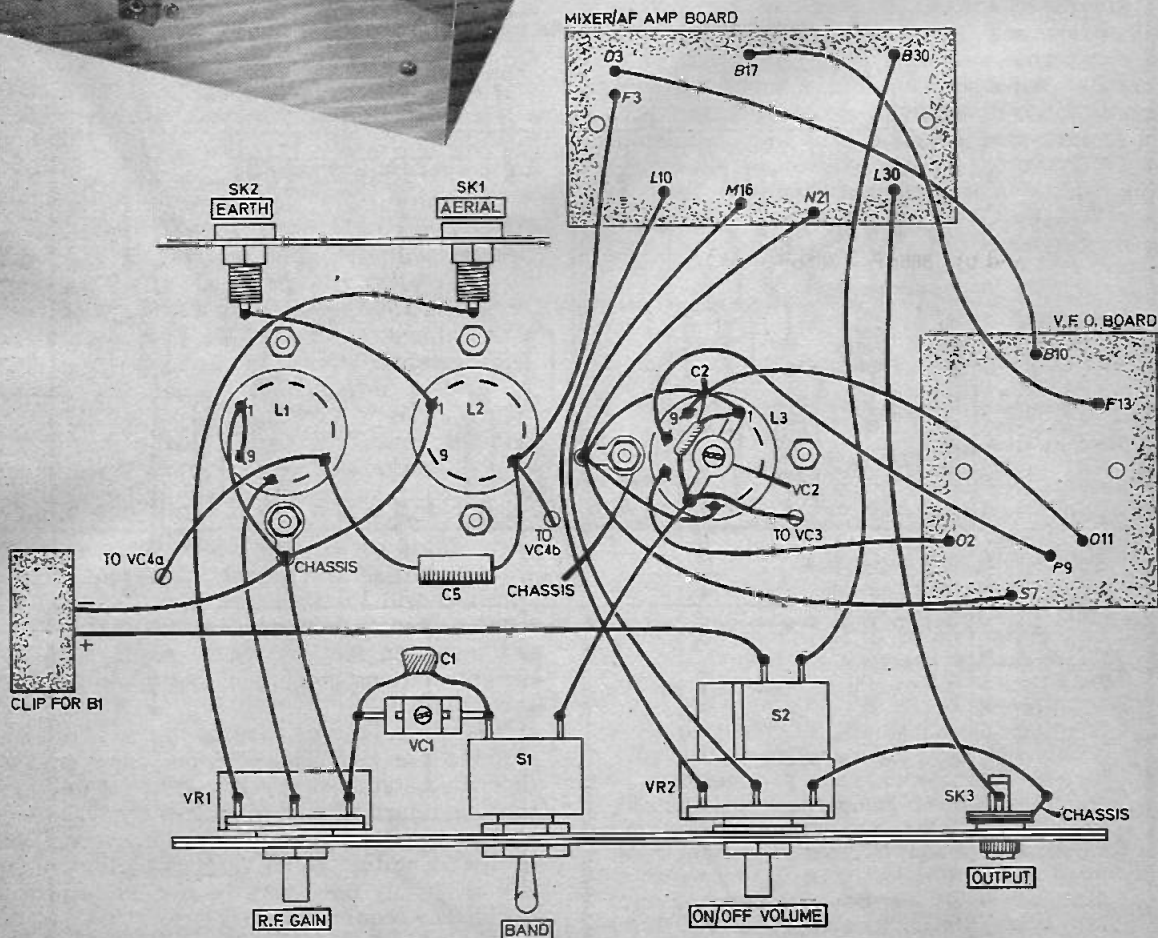


Fig. 5. Layout and wiring of the underside of the receiver.

## Components . . . .

### Resistors

R1 390 k $\Omega$	R7 4.7k $\Omega$	SEE <b>SHOP TALK</b>
R2 3.3 k $\Omega$	R8 1M $\Omega$	
R3 100k $\Omega$	R9 270 $\Omega$	
R4 1.5k $\Omega$	R10 4.7k $\Omega$	
R5 220 $\Omega$	R11 3.9k $\Omega$	
R6 560 $\Omega$	All $\frac{1}{4}$ W $\pm$ 10% carbon	

### Potentiometers

VR1 5k $\Omega$ lin carbon
VR2 5k $\Omega$ log. carbon with switch (S2)

### Capacitors

C1 68pF ceramic or silver mica
C2 10pF ceramic or silver mica
C3 120pF polystyrene
C4 47pF silver mica
C5 2pF silver mica
C6 10 $\mu$ F elect. 10V
C7 0.01 $\mu$ F Mullard C280
C8 0.1 $\mu$ F Mullard C280
C9 0.01 $\mu$ F Mullard C280
C10 0.1 $\mu$ F Mullard C280
C11 0.0015 $\mu$ F ceramic disc
C12 10 $\mu$ F elect. 10V
C13 1,000pF ceramic
C14 10 $\mu$ F elect. 10V
C15 100 $\mu$ F elect. 10V

### Variable Capacitors

VC1 30/140pF mica compression trimmer
VC2 10/40pF ceramic trimmer
VC3 25pF air spaced variable (Jackson C804)
VC4 (a and b) 365pF +365pF dual gang air spaced variable (Jackson type O)

### Semiconductors

TR1 2N2369A silicon <i>n</i> p <i>n</i>
TR2 3N140 dual gate MOSFET
TR3 BC148 silicon <i>n</i> p <i>n</i>
TR4 BC148 silicon <i>n</i> p <i>n</i>

### Miscellaneous

SK1 Single wander socket with plug for aerial
SK2 Single wander socket with plug for earth
SK3 3.5mm jack socket
L1 Denco range 3 blue aerial coil (for transistor usage)
L2 Denco range 3 blue aerial coil (for transistor usage)
L3 Denco yellow r.f. coil (for transistor usage)
S1 s.p.s.t. toggle switch
S2 s.p.s.t. switch incorporated in VR2
B1 9V PP3 type battery and connector
150mm x 100mm x 50mm aluminium chassis, front panel, B9A valveholders (3 off for coil mounting), 4000 $\Omega$ impedance headphones fitted with 3.5mm jack plug, 0.1 inch matrix plain perforated Veroboard, two small and two large control knobs, 4BA and 6BA fixings, connecting wire, wire for aerial and earth.

Before the set is ready for use, VC1 and VC2 must be adjusted to give the correct frequency coverage, and the cores of the coils have to be peaked. The cores of L2 and L3 are adjusted so that the metal threaded portions protrude about 10mm. The core of L1 is similarly adjusted for a protrusion of 13mm.

Having given the set a final check for mistakes, remove the clip on TR1 and turn on, switch S1 should be set to the 80 metre band. Assuming that no test gear is available, the only way to find the correct setting of VC2 is to try various settings until one is found which allows VC3 to tune the whole of the band. The 80 metre band is usually fairly crowded (especially at weekends), and this makes it quite easy to locate the limits of the band.

When VC2 has its final adjustment, VC1 can be adjusted for correct coverage of the 160 metre band. This is likely to be more difficult, since this band is shared with marine transmissions, and a lower transmitter power limit is enforced. This makes it less popular than other bands, and it is mainly used for local contacts. In some areas there may be very little activity on this band at all.

If there are two closely spaced settings of VC4 which will peak signals, the core of L1 is adjusted slightly (probably inwards) to give a single setting which produces a single peak.

## OPERATING NOTES

The output is suitable for high impedance headphones (4000 ohms) which plug into SK3. Results will probably be best if the volume control (VR2) is kept at a fairly high setting, and the r.f. gain (VR1) is advanced no further than is necessary to provide an adequate signal. It is essential that the aerial trimmer (VC4) is always adjusted to peak the incoming signal, so as to give the proper sensitivity, and to reject unwanted signals. Remember that this control works independently of the wavechange switch (S1), and needs totally different settings for the two bands.

As stated earlier, the 160 metre band is used mainly for local contacts and most stations received will be no more than about 50 miles distant. Many British and European stations will be heard on the 80 metre band, with more distant stations coming in when conditions are favourable.

It is worth bearing in mind that most 80 metre stations use l.s.b. (lower side band), and it is therefore standard practice when scanning the band to start at the high frequency end (the vanes of VC3 unmeshed). This way, as one tunes towards a station, it will sound very high pitched, and it is only necessary to further adjust VC3 to give the required pitch.

By tuning from the other end of the band it would be necessary to tune through the station, and then readjust, which is less convenient.  $\square$





**T**HIS month we have been taking another look at our approximate cost box and in view of the changeable state of the market, have felt it prudent to modify somewhat the wording. Obviously there must be some "give and take" in such matters, but we believe most readers appreciate the general guidance the cost box offers.

One item that is usually omitted from the approximate cost is the case for any particular project. This is mainly, because most suppliers offer various cases at various prices and quite often readers are able to construct their own cases either from wood or metal.

### R.F. Signal Generator

Still continuing on the case theme, we promised to supply the name and address and cost for the

Olsen case again and also a supplier for knobs for the E. E. Test Gear Five series.

The Olsen case type 25A with louvres is available in light green, dark green, blue and silver grey with front panels in light green, white or cream for £3.45, including postage packing and V.A.T. from Olsen Electronics Ltd, 5 Long Street, London, E.2.

Similar knobs to those shown, with a skirt and indicator line (type R62) are available from Re-An Products, Burnham Road, Dartford, Kent. Top cap colours available are red, blue, green, yellow and black—state which when ordering. The knobs cost 14p each plus 20p post and packing plus V.A.T. on the total.

The dial and pointer used on the R. F. Signal Generator are available from Home Radio Components. The Denco coils are available direct from Denco (Clacton) Ltd., 355/7/9 Old Road, Clacton-on-Sea, Essex CO15. The "red" types cost 44p each and 8p should be sent with each order to cover post packing. Add 10 per cent V.A.T to total.

### A. F. Oscillator

The Wima capacitors for the A.F. Oscillator can no longer be obtained from Combined Electronic Services as mentioned in our March issue.

However Trannies are able to supply Mullard C281 types which they have selected for less than ±5 per cent tolerance. The total cost for the six capacitors required including selection, V.A.T. and postage is £1.46—about the same as from the previous supplier.

### Freezer Alarm

Most of the components for the Freezer Temperature Alarm should be readily available. The pre-set control should be a T.V. type—that is a panel mounting enclosed type, as opposed to a skeleton pre-set.

The reed relay used in the prototype is an R. S. Components device and should be available through most component suppliers who can order it from them. Readers are not able to buy direct—a situation about which we have heard a few rumours, and we hope to see a retail outlet in the future.

The reed relay can in fact be replaced by almost any type with a coil resistance of more than 200 ohms and the correct working voltage but, of course, this would be unlikely to fit on the board.

### Amateur Bands Receiver


The Amateur Bands Receiver also uses Denco coils (see R.F. Signal Generator above) and these are also available direct from Denco. The Range 3 blue, two are required, and the yellow r.f. cost 44p each, once again include 8p for post and packing and add 10 per cent V.A.T to the total. The 3N140 MOSFET can be obtained from either Arrow Electronics or Marshall's. The addresses and prices are: Arrow Electronics Ltd., 7 Coptfold Road, Brentwood, Essex. CM14 4BN, 92p plus V.A.T., no charge for post and packing. A. Marshall and Son (London) Ltd., 42 Cricklewood Broadway, London, NW2 3HD, £1.00 including V.A.T., post and packing.

## JACK PLUG & FAMILY...





# R.F. SIGNAL GENERATOR

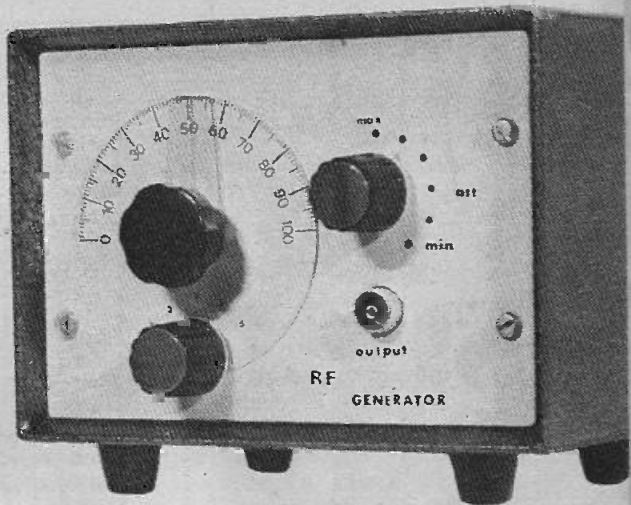

**T**his project is the last and most difficult of the E.E. Test Gear Five series. However, readers who have already built one or more of the other instruments will have gained sufficient experience to make a success of this project.

An r.f. signal source is essential for work with radio receivers. With the aid of a signal generator, circuits can be tested and aligned from the detector, back through the receiver to the aerial socket. It is very difficult to carry out any serious work or repairs to radio receivers using only signals picked up from broadcast transmissions.

The actual circuit itself is quite simple, but the necessity to switch ranges, to have a reasonable attenuator and the care needed in wiring means that the mechanical layout of the instrument is more critical than the previous projects. The instrument covers frequencies from 200kHz to 30MHz in five ranges.

For work with f.m. receivers, the fourth harmonic of range 5 may be used to provide signals in the f.m. band (80 to 120MHz).

The generator is amplitude modulated (a.m.), but useful signals can be picked up by f.m. receivers nevertheless.

## THE R.F. OSCILLATOR

Previous instruments in this series have featured an integrated circuit as the main active component. This instrument employs a field effect transistor (f.e.t.).

A field effect transistor is very much like an npn transistor but with a very high base impedance. The source, gate, drain electrodes are similar in function to the emitter, base, collector or, for those who remember valves, cathode, grid and anode. The field effect transistor is so much like a valve that many valve circuits can be readily adapted to work with them.

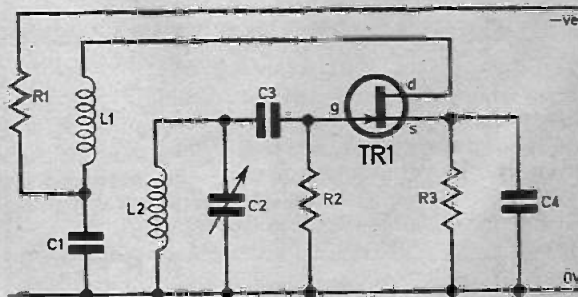


Fig. 1. The basic r.f. oscillator circuit.

The basic r.f. oscillator circuit is shown in Fig. 1. Coil L2 and variable capacitor C2 form a highly selective tuned circuit, signals being passed from this circuit via C3 to the gate input of the transistor. These signals are amplified at the drain output of the transistor and coupled via L1 back to the tuned circuit.

When the circuit is switched on, oscillations build up until limited by other components in the circuit; R1 and C1 provide decoupling which ensures that the end of L1 is connected to earth through C1. Components C3 and R2 form an automatic bias circuit which controls the amplitude of the oscillation, whilst R3 and C4 work in conjunction with R1, R2 and C3 to set the working current in the transistor.


FOR GUIDANCE ONLY

ESTIMATED COST\* OF COMPONENTS including V.A.T.

£7.10

Excluding Case

\*Based on prices prevailing at time of going to press

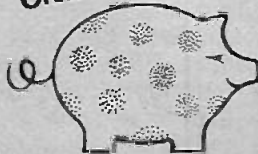

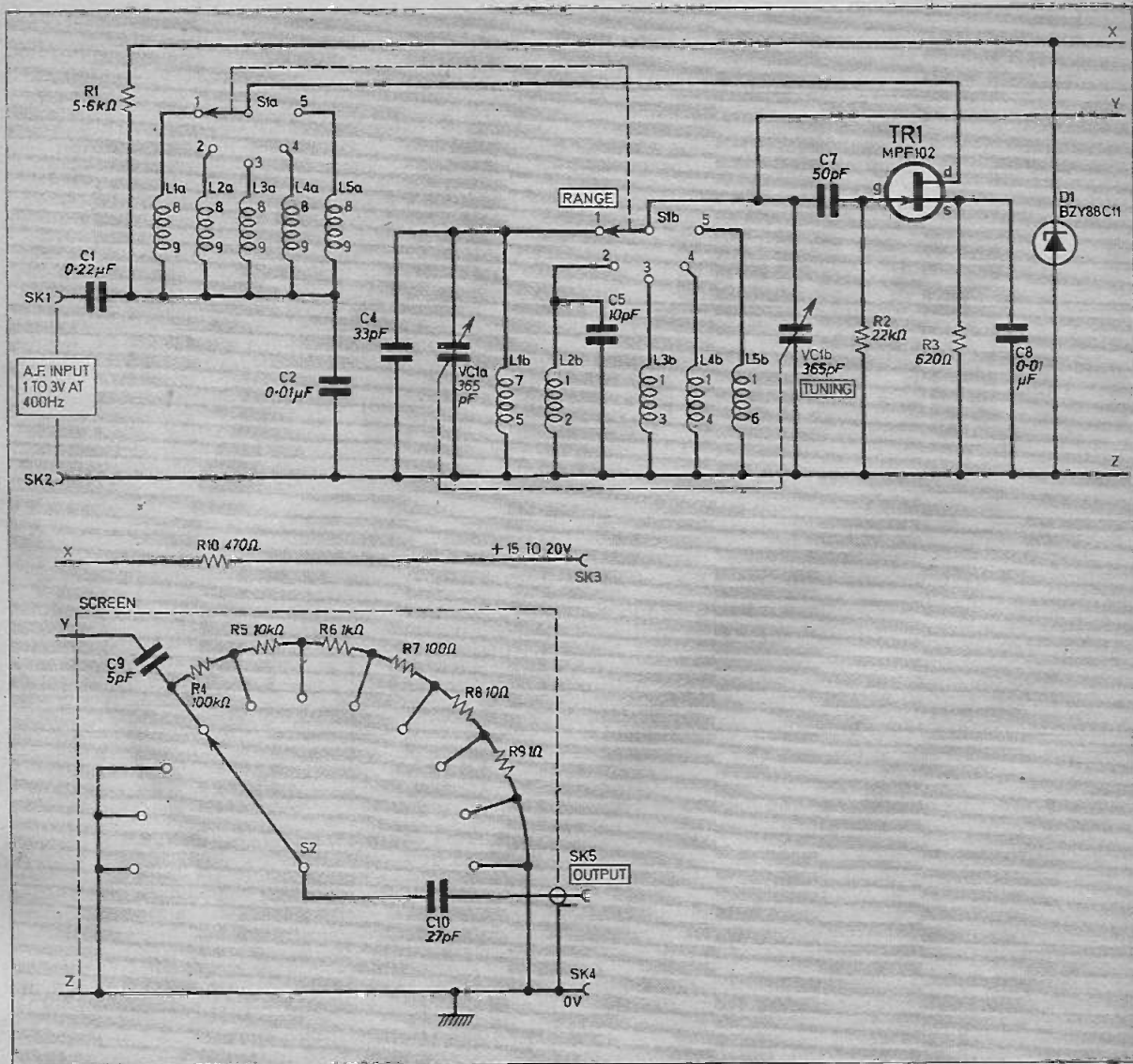


Fig. 2. The complete circuit diagram of the R.F. Signal Generator.

This basic circuit is used in many signal generators and as the local oscillator of superhet receivers.

### THE SIGNAL GENERATOR

The full R.F. Signal Generator circuit is given in Fig. 2. Although this circuit looks rather large, with many long wires connecting the components, it is only drawn this way for clarity. In fact, when the instrument is wired the very minimum of wire must be used.

The similarity between this and the basic circuit of Fig. 1 is quite evident. However, the differences are important. For example an input of 400Hz is fed to the r.f. generator from an audio oscillator. This is the modulation.

Signal generators can be used without modulation for some work, but in the majority of

applications a modulated signal is necessary.

The A.F. Oscillator, the second project in the E.E. Test Gear Five series (March 1974) makes an ideal modulator. Set the a.f. oscillator to 400Hz with its output voltage set to 2 volts and this will modulate the r.f. carrier properly. The main function of resistor R1 should now be clear, it enables the voltage supply to TR1 to be moved up and down in response to the modulating input signal, thereby modulating the carrier. Capacitor C1 is chosen to couple an adequate signal at 400Hz, whilst C2 is chosen to provide sufficient r.f. decoupling without seriously affecting the modulation.

The main oscillator TR1 is identical to the basic circuit shown in Fig. 1 except that five switched ranges are used via S1a and S1b. To simplify the building of the instrument, readily available oscillator coils designed for superhet



local oscillators have been chosen. The use of these means that some trimming is necessary on the two lowest ranges, ranges 1 and 2. Capacitors C4 and VC1a (half of the twin gang tuning capacitor) trim L1b so that it extends down to 200kHz. Coil L2b is trimmed with a simple fixed capacitor C5. The ranges thus covered are:—

Range 1	198kHz to 638kHz
Range 2	600kHz to 2.01MHz
Range 3	1.6MHz to 5.44MHz
Range 4	5MHz to 13.5MHz
Range 5	10.9MHz to 31.2MHz
4th harmonic (Range 5)	80.4MHz to 122MHz

## Components....

### Resistors

R1	5.6k $\Omega$
R2	22k $\Omega$
R3	620 $\Omega$
R4	100k $\Omega$
R5	10k $\Omega$
R6	1k $\Omega$
R7	100 $\Omega$
R8	10 $\Omega$
R9	1 $\Omega$
R10	470 $\Omega$

All  $\frac{1}{4}$ W carbon  $\pm$  5%

SEE  
**SHOP  
TALK**

### Capacitors

C1	0.22 $\mu$ F
C2	0.01 $\mu$ F
C4	33pF silver mica
C5	10pF silver mica
C7	50pF silver mica
C8	0.01 $\mu$ F
C9	5pF silver mica
C10	27pF silver mica
VC1	365pF twin gang variable (Jackson)

### Semiconductors

TR1	MPF102 n-channel f.e.t.
D1	BZY88 11 volt 400mW Zener

### Coils

L1	Denco Red Range 1
L2	Denco Red Range 2
L3	Denco Red Range 3
L4	Denco Red Range 4
L5	Denco Red Range 5

### Miscellaneous

- S1 two-pole five-way miniature Maka switch
- S2 one-pole eleven-way ceramic type
- SK1, 2, 3, 4 insulated screw terminals, one off each red, black, green, yellow (4 off)
- SK5 panel mounting co-axial socket
- Eddystone die cast box size 98 x 57 x 25mm;
- 90mm diameter dial calibrated 0-100 through 180 degrees of arc; Perspex pointer to suit dial; transistor socket; knobs (3 off); Olsen type 25A case with louvres.

These ranges are adjusted by the dust core adjuster in the coils, but due to the complete absence of padders (very low value trimmer) and trimmers different layouts and wiring will affect the ranges actually obtained, therefore great care must be exercised in the construction and wiring to ensure that it is as close as possible to the original shown here.

Finally, the output is fed via C9 to a simple attenuator. This attenuator uses an 11-way ceramic switch. The ranges adjacent to the wiper are unused and connected to earth in order to reduce capacitive coupling between the strong input signal and the attenuated output. Some coupling is unavoidable in such a simple arrangement so calibration of this attenuator is not possible, especially at the higher frequencies. It does however give a useful range of attenuation from a maximum output of about 500 millivolts.

## CONSTRUCTION DETAILS


As with the previous four instruments, the R.F. Oscillator is housed in a type 25A Olsen case with louvres. However, unlike the others no circuit board is used for the components, everything being mounted on the front panel and other major components.

First it is necessary to make up a simple aluminium bracket as shown in Fig. 3, before bending this bracket, it must be drilled as shown. Secondly, the front and back panels must be drilled as shown in Fig. 4. Finally, a diecast "Eddystone" box must be cut and drilled to house the attenuator switch, Fig. 5.



Fig. 3. The aluminium bracket for holding the coils.

ALL DIMENSIONS IN mm

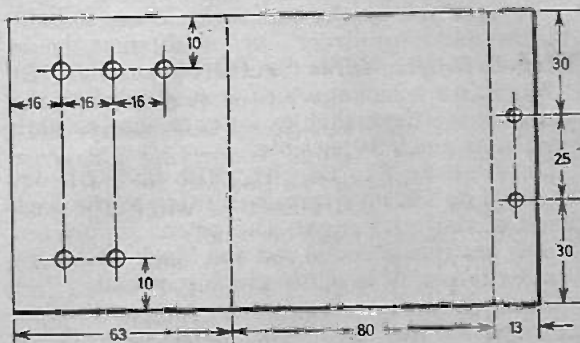

Next, mount the variable capacitor and range switch S1 onto the front panel and the coils onto the aluminium bracket bent into shape. When these components are mounted, the switch, coils and tuning capacitor must be very close to each other, as shown in the photograph and Fig. 6. It is essential that the coils of ranges 4 and 5 are as close as possible to the range switch.

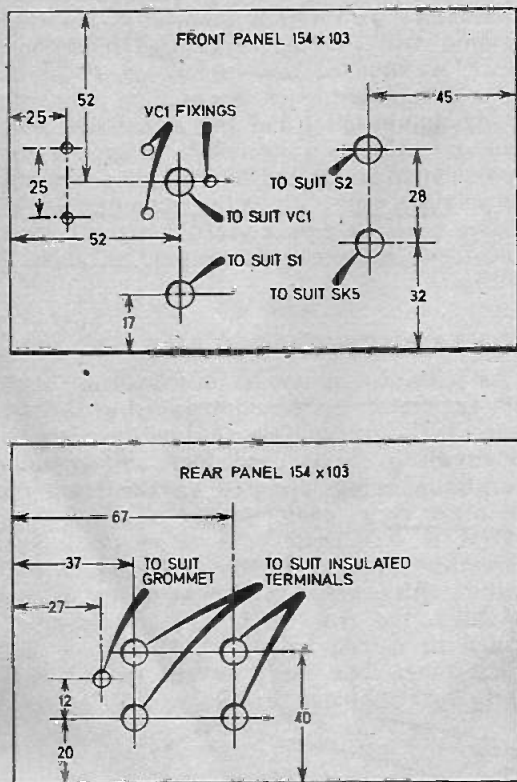


Fig. 4. Front and rear panel drilling details.

The coils, range switch and wiring to components VC1, C7, C5, C8, TR1, R2 and R3 should now be wired using the *shortest possible wiring* according to Fig. 6. In particular, the earth wire from pin 5 on coil 5 should go direct to the earth terminal of the tuning capacitor.

The oscillator works best if the wires take the shortest and most direct route, no attempt should be made to loom wires together. Transistor TR1 is fitted into a socket which is suspended in the wiring above the switch in order to shorten path lengths as much as possible.

Components C1, C2, R1, R10 and D1 are mounted on the four terminals fitted to the back panel of the instrument. The power supply terminals are colour coded red and black whilst the modulation input uses two green terminals.

Two wires join the group of components mounted on the back panel to those mounted on the front panel, these are the earth connection and the wire leading to pins 9 on the coils.

The attenuator is wired separately, compo-


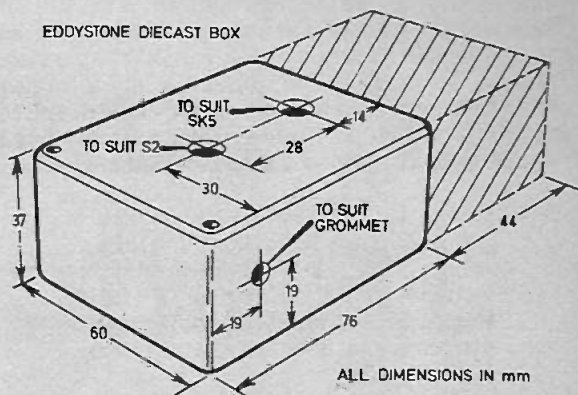


Fig. 5. Drilling and cutting details for the Eddy-stone diecast box for housing the attenuator.

nents R4 to R9, C9 and C10 all being fitted to the attenuator switch. A short wire is led out of the box from C9 to connect the attenuator to the tuning capacitor. The coaxial socket is bolted to the diecast box using countersunk screws so that when the retaining nut is removed from the attenuator switch the whole assembly can be offered up flush to the front panel and held in position by refitting the retaining nut to the switch. Having done this the wire from C9 can be connected using the shortest possible length of wire.


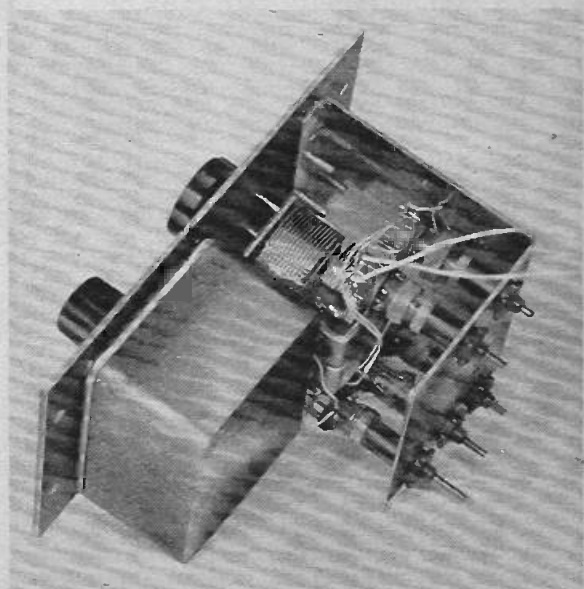
The instrument wiring is now complete, but two or three checks of this wiring is recommended. Transistor TR1 is very delicate and can



Photograph of the completed prototype front panel showing mounting of coils to bracket, and bracket to front panel.

# R.F. SIGNAL GENERATOR

Fig. 6. (below) The layout and wiring up details of the components mounted on the front panel. The coil mounting bracket has been drawn opened up, for clarity, thus showing the bases of the coil formers head on; (above) The layout and wiring of the components on the rear panel.

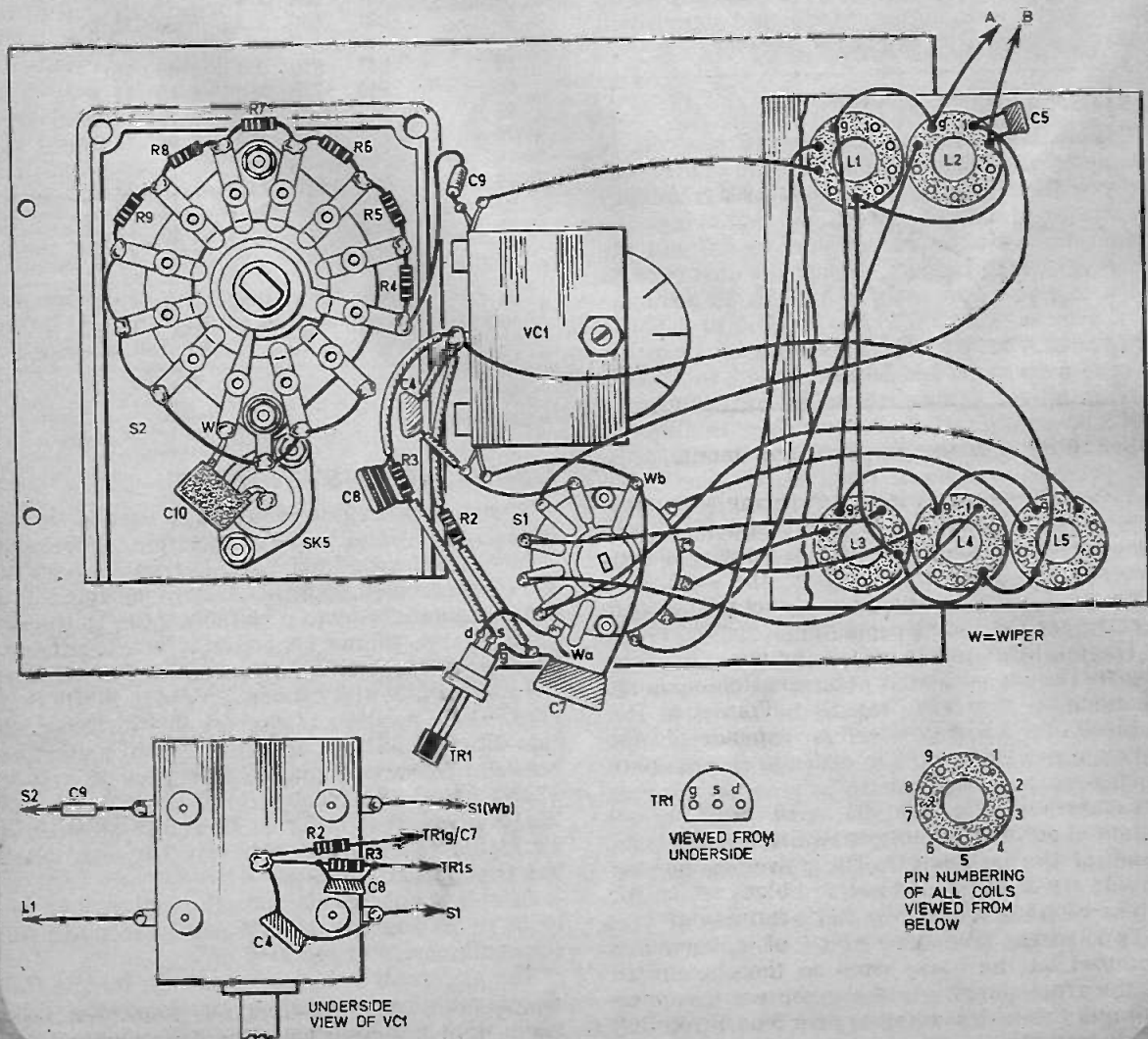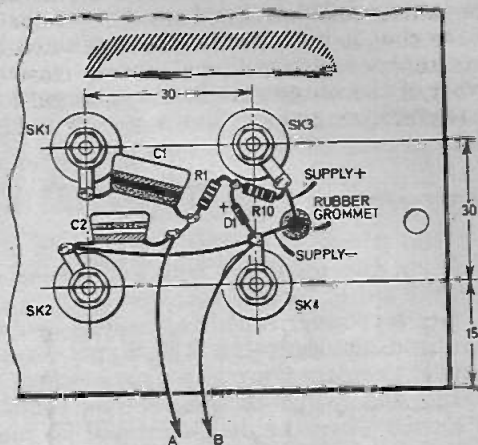



easily be damaged by an error in the wiring. Finally, the front panel is marked up using let-raset and the 0-100 dial and pointer are fitted.

The dial is held in place by cutting a hole in the bottom and trapping it under the retaining screw of the range switch. The pointer is a standard Perspex one cut down in size to suit the dial.

## TESTING

If the wiring is correct and TR1 is in good condition the oscillator will work. It is tested with the aid of a radio receiver.

Place a receiver tuned to the long or medium waveband alongside the R.F. Signal Generator. Connect the generator to a power supply set to 18 volts and switch on. The receiver should pick up signals when the dial is rotated on ranges 1 and 2, long and medium wave. These signals will be received as quiet spots on the receiver dial.

Next connect the audio generator to the modulation terminals having first set the controls to 400Hz and 2 volts output. Modulated signals will now be received by the radio receiver.

## CALIBRATION

Calibration is simple for those with access to frequency measuring equipment and difficult for those without it. First, for those with frequency measuring facilities. Start by removing the modulation, set the dial pointer to 100 and the range switch to range 1. Adjust the dust core on coil 1 to give a frequency of 198kHz. In a similar way, set range 2 to 600kHz, range 3 to 1.6MHz and range 4 to 5.0MHz. Rotate the dial pointer to read 5 divisions and adjust range 5 to 31MHz. Having set the calibration points for each range make up a calibration chart as show in Table 1.

For those without frequency measuring facilities proceed as follows. First, set all dust cores about half way out on their adjusting screw. The unit must be calibrated against known radio station frequencies by setting the dust core into its correct position.

For example, range 1 can be calibrated against the BBC long wave transmission on 200kHz (1500 metres) as follows: tune a radio receiver to 200kHz then set the dial pointer on the generator to 98; a beat note should be heard in the receiver. The core adjuster on range 1 is now adjusted to give zero beat, (as near as possible), in the receiver. Range one is now as close as possible to the calibration chart. Each range should now be set against a known transmission standard so that every range is as close as possible to the calibration chart.

If a suitable receiver is not available or you don't know the frequency of a station, leave the dust core set half way until an opportunity to calibrate presents itself. Ranges 1 to 4 should be calibrated between pointer position 80 and 100 and Range 5 as near to 5 as possible.

**Table 1: Calibration chart for the prototype R. F. Signal Generator**

Dial position	Range and frequency (MHz)					FM
	1	2	3	4	5	
0	·640	1·99	5·53	13·5	31·1	
5	·632	1·95	5·43	13·4	31·0	
7·5	·609	1·86	5·21	13·1	30·5	122
10	·574	1·73	4·88	12·6	29·9	119·6
12·5	·539	1·64	4·54	12·1	28·6	114·4
15	·507	1·56	4·26	11·6	27·5	110
17·5	·475	1·45	3·95	11·1	26·1	104·4
20	·447	1·35	3·70	10·4	24·8	99·2
22·5	·423	1·28	3·49	9·95	23·6	94·4
25	·402	1·22	3·31	9·54	22·5	90
27·5	·383	1·16	3·14	9·16	21·4	85·6
30	·366	1·11	3·00	8·82	20·5	82
35	·338	1·02	2·76	8·22	19·0	76
40	·316	·958	2·57	7·74	17·7	
45	·297	·898	2·42	7·33	16·7	
50	·281	·850	2·29	6·97	15·8	
55	·267	·810	2·17	6·65	15·1	
60	·256	·776	2·08	6·40	14·4	
65	·245	·744	1·99	6·15	13·9	
70	·236	·717	1·92	5·94	13·3	
75	·228	·693	1·85	5·74	12·9	
80	·221	·670	1·79	5·57	12·5	
85	·214	·649	1·74	5·40	12·1	
90	·209	·631	1·69	5·26	11·7	
95	·203	·614	1·64	5·12	11·4	
100	·198	·600	1·6	5·0	11·2	


## USING THE INSTRUMENT

A signal generator is normally used with the modulation connected. For example, suppose it is necessary to adjust the i.f. transformers of a radio receiver 465kHz. A wire must be fed from the generator to a suitable input to the i.f. channel, the tuning capacitor is often suitable. The generator is switched on and set to 465kHz.

Inspection of the calibration chart shows that range scale position 17·5 gives 480kHz and position 20 gives 453kHz, therefore, 465kHz must be between these two readings. In fact 465kHz is 12kHz above the frequency at position 20 and 15kHz below that at 17·5. Therefore, 465kHz is estimated to be about half way between these two readings at 18·75.

As this is only an estimate the dial may be set to 18 or 19 and still be sufficiently accurate for the realignment of receiver i.f.'s.

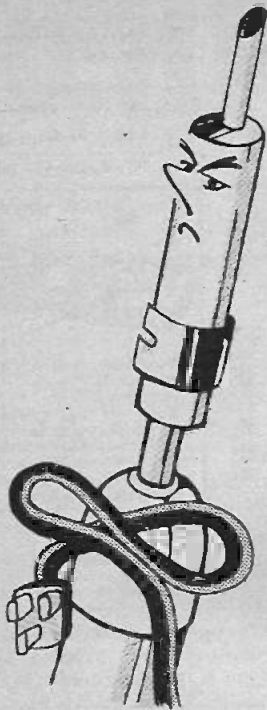The generator is accurate enough for the full alignment of any receiver providing the final calibration is carried out using a broadcast transmission of known frequency. □



# The Iron Will...

You know the type . . . whenever you need him to do one thing he'll want to do the other. And nothing will make him change his mind.

It's the same with some people's soldering irons.

Hopelessly inefficient heat control can give an iron a will of its own and make soldering operations a nightmare. If this is what soldering means to you it's time you woke up to Antex.

Just choose a new model from the comprehensive Antex range of advanced soldering instruments, with unique constructional advantages . . . low leakage characteristics, interchangeable bits to match solder-joint requirements, and really precise heat control.

## Choose ANTEX—the warm hearted iron

(and keep your cool)

**MODEL X25 ▶**  
220-240 Volts or 100 120 Volts. The leakage current of the NEW X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live". Tested at 1500v. A.C. This 25 watt iron with its truly remarkable heat-capacity will easily "out-solder" any conventionally made 40 and 50 watt soldering irons, due to its unique construction advantages. Fitted long-life iron-coated bit 1/8". 2 other bits available 3/32" and 3/16". Totally enclosed element ceramic and steel shaft. Bits do not "freeze" and can easily be removed.  
**PRICE £2.15** (rec. retail) P & P 10p.  
Suitable for production work and as a general purpose iron.

**MODEL SK.1 KIT**  
Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.  
**PRICE £3.64** (rec. retail) P & P 12p.







**MODEL G ▶**  
18 watt miniature iron, fitted with long-life iron-coated bit 3/32". Voltage 240, 220 or 110. 2 other spare bits available 1/8" and 3/16".  
**PRICE £2.37** (rec. retail) P & P 10p.

**MODEL CCN**  
220 volts or 240 volts. The 15 watt miniature model CCN also has negligible leakage. Test voltage 4000v. A.C. Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32". 4 other bits available 1/8", 3/16", 1/4" and 3/64" including Heat Shield.  
**PRICE £2.48** (rec. retail) P & P 10p.

**MODEL MLX KIT**  
Battery operated 12v. 25 watt iron fitted with 15' lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with booklet "How to Solder".  
**PRICE £2.76** (rec. retail) P & P 12p.

**MODEL SK.2 KIT**  
Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, and "How to Solder" booklet.  
**PRICE £3.53** (rec. retail) P & P 10p.

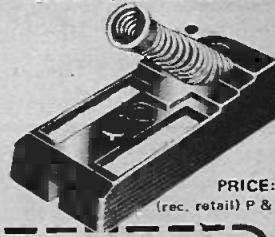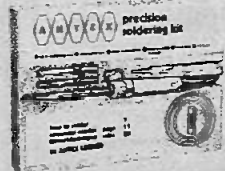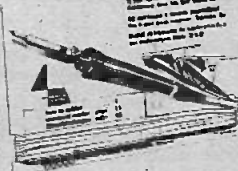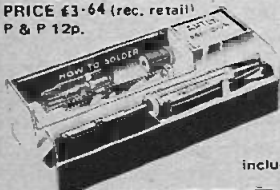**ST3 Stand** — This stand is made from high grade insulation material with a chromium plated strong steel spring. It is suitable for all models and replaces all previous stands. The two sponges at the side which are easily replaceable serve to keep the soldering bits clean. Spare bits can be accommodated as shown on the illustration.



ALL PRICES include VAT at 10%

**PRICE: £1.00** (rec. retail) P & P 10p.



Please send the following:

Please send the ANTEX colour catalogue.

I enclose cheque/P.O./Cash (Giro No. 258 1000) EE6

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

From radio or electrical dealers, car accessory shops or in case of difficulty direct from:  
**ANTEX LTD. FREEPOST PLYMOUTH PL1 1BR**  
(no stamp required) Tel 0752 67377



# Out now!

# Free



Heathkit offer you a wonderful range of audio, household, amateur radio and test equipment in kit form.

All our electronic kits are designed to be built by you. No previous soldering or electronic knowledge is necessary as every kit is supplied with a detailed Construction Manual which leads you step-by-step through the assembly, adjustment and operation of your Heathkit.

Write now for your FREE copy of the Heathkit Catalogue or visit one of our Showrooms and see our full range of products for yourself. You'll be amazed at what you can make in just a few evenings with Heathkit—the world's largest selling electronic kits.

## Free

Please send me the FREE Heathkit Catalogue & details of Monthly budget plans.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_

HEATH

Schlumberger

HEATH (GLOS.) LTD. DEPT. EE/6/74  
 Bristol Road,  
 Gloucester GL2-6EE

## Trannies

4 Bush House,  
 Bush Fair, Harlow,  
 Essex.

★ PRICES INCLUSIVE  
 OF V.A.T.

★ Retail Shop open 9 to  
 5.30 Mon to Sat.

★ Post & Package 15p.

★ 1974 Catalogue 20p.

### RESISTORS

½ watt 5% carbon.....	1p
½ watt 5% carbon.....	1p
½ watt 10% carbon.....	2p
range 10 ohms to 4.7 megohms	
½ watt m/o 2%.....	4p
range 10 ohms to 1 megohms.	

### VEROBOARD

0-1	0-15
24p	19p
2½ x 5	27p
3½ x 3½	27p
3½ x 5	31p
17 x 2½	82p
17 x 3½	82p
17 x 5 (Plain)	£1-10
Pin insertion tool	57p
Spot face cutter	46p
Pk 36 Pins	20p

### VOLUME CONTROLS

Potentiometers  
 Carbon track 500Ω to 2.2MΩ.  
 Log or Linear.  
 Single 13p. Dual gang (stereo) 44p.  
 Single type with D.P. switch 13p extra.

### DISCO UNITS



Complete System £187.50,  
 carr. £4.50.

Includes  
 ★ DJ 100 watt amp with full  
 PFL & mixing facilities.

★ Trannies Disco console with  
 2 Garrard SP25 turntables.

★ Pair 50 watt speakers.  
 ★ Headphones & mic.

Terms: No Deposit £2.47  
 weekly over two years (total  
 £225.48).

Other systems (100 watt)  
 starting from £149.95.

Send for list or pay us a visit.

We stock a large range of electronic semi-conductors at competitive prices. Our summer 74 catalogue is now available at 20p.

### £1 BARGAIN PACKS

- £1 10 Silicon NPN Power Transistors (2N3055) tested/unmarked.
- £1 30 Plastic FET's unmarked/untested, similar to 2N3819.
- £1 20 TO5 transistors NPN or PNP, state which, 2 to 5 amp untested/unmarked.

£1 20 TO18 transistors PNP like BC178, BC179 etc. untested/unmarked.

£1 30 Plastic 2N3055 unmarked/untested TO220 case.

£1 10 General Purpose, fully tested FET's.

★ any 5 packs £4.50 ★ P/P 25p for each pack

We stock a large range of electronic semi-conductors at competitive prices. Our Summer 74 Catalogue is now available at 20p.

### Electrolytic Capacitors

<b>4 VOLT</b>	<b>16 VOLT</b>	<b>40 VOLT</b>
47µF 6½p	15µF 6½p	47µF 6½p
100µF 6½p	33µF 6½p	100µF 9p
220µF 6½p	150µF 6½p	68µF 10p
330µF 6½p	100µF 8p	220µF 11p
1000µF 13p	220µF 9p	470µF 19p
4700µF 29p	680µF 17p	680µF 25p
	1000µF 17p	1000µF 25p
	1500µF 25p	2200µF 44p
	2000µF 43p	
<b>6.3 VOLT</b>	<b>25 VOLT</b>	<b>63 VOLT</b>
33µF 6½p	10µF 6½p	1µF 6½p
68µF 6½p	10µF 6½p	2.2µF 6½p
150µF 6½p	22µF 6½p	4.7µF 6½p
470µF 11p	47µF 6½p	220µF 6½p
680µF 13p	100µF 8p	10µF 6½p
1500µF 18p	150µF 8p	22µF 6½p
2200µF 18p	220µF 10p	68µF 10p
3300µF 26p	470µF 13p	100µF 11p
	680µF 20p	150µF 13p
	1000µF 22p	220µF 19p
	2200µF 29p	6.8µF 6½p
	5000µF 68p	10µF 6½p
<b>10 VOLT</b>	<b>40 VOLT</b>	
22µF 6½p	150µF 11p	
47µF 6½p	6.8µF 6½p	
1000µF 6½p	15µF 6½p	
220µF 8p	470µF 6½p	
330µF 10p	1000µF 44p	
470µF 10p		
1000µF 11p		
1500µF 20p		
2200µF 24p		

### Resistors

½ watt 5% carbon 1p	AC126 15p
½ watt 5% carbon 1p	AC127 15p
½ watt 10% carbon 2p	AC128 15p
Range 10 ohms to 4.7 megohms.	AC187k 26p
½ watt m/o 2% ... 4p	AC187 16p
Range 10 ohms to 1 megohms.	AC188k 26p

### Veroboard

0-15	0-1
24p	19p
2½ x 5	27p
3½ x 3½	27p
3½ x 5	31p
17 x 2½	82p
17 x 3½	82p
17 x 5 (Plain)	£1-10
Pin insertion tool	57p
Spot face cutter ...	46p
Pack of 36 pins	20p

### Transistor

AC126 15p	OC28 55p
AC127 15p	OC35 48p
AC128 15p	OC36 54p
AC187k 26p	OC71 15p
AC187 16p	2N3053 26p
AC188k 26p	2N3054 55p
AD140 49p	2N3055 49p
AD149 49p	2N3055 49p
AD161 42p	2N3819 28p
AD162 42p	40636 66p
AF114 16p	
AF115 16p	
AF116 16p	
AD117 16p	
BC107 12p	
BC108 12p	
BC109 13p	
BC147 12p	
BC148 12p	
BC149 13p	
BF194 16p	
BF195 18p	
BFY50 19p	
BFY51 20p	
BFY52 20p	
OC25 48p	
OC28 55p	
OC35 48p	
OC36 54p	
OC71 15p	

### Mullard Polyester Capacitors

**C280 SERIES**  
 250V P.C. mounting: 0.01µF, 0.015, 0.022 3½p, 0.033, 0.047, 0.068 4p, 0.1 4½p, 0.15, 0.22 5½p, 0.33 7p, 0.47 9½p, 0.68 12p, 1µF 14p, 1.5µF 22p, 2.2µF 27p

**C296 SERIES**  
 400V: 0.001µF, 0.0015, 0.0022, 0.0033, 0.0047 3p, 0.0068, 0.01, 0.015, 0.022, 0.033 3½p, 0.047, 0.068, 0.1 4½p, 0.15 6½p, 0.22 8½p, 0.33 12p, 0.47 14p.

160V: 0.01µF, 0.015, 0.022, 0.033, 0.047, 0.068 3½p, 0.1 4p, 0.15 4p, 0.1 4½p, 0.15, 0.22 5½p, 0.33 7p, 0.47 9½p, 0.68 12p, 1µF 14½p, 1.5µF 22p, 2.2µF 24p.



# NEXT MONTH...

*Every second counts!  
Keep a check with our....*

## TELEPHONE CALL CHARGE CALCULATOR!!



With the recent increase in call charges it is now more necessary than ever to keep a check on your wife's phone calls! This device gives a digital readout in pounds and pence of the accumulated cost of your STD telephone calls over any time period.

**New charges for telecommunications services**  
Changes for users of telecommunications services will be implemented on 14 October 1974. It is essential that the normal user of the telephone be made aware of the changes in advance.

**Telephone Services**  
Changes for users of telecommunications services will be implemented on 14 October 1974. It is essential that the normal user of the telephone be made aware of the changes in advance.

**Telephone Calls**  
Changes for users of telecommunications services will be implemented on 14 October 1974. It is essential that the normal user of the telephone be made aware of the changes in advance.

**Telephone Services**  
Changes for users of telecommunications services will be implemented on 14 October 1974. It is essential that the normal user of the telephone be made aware of the changes in advance.

**Telephone Calls**  
Changes for users of telecommunications services will be implemented on 14 October 1974. It is essential that the normal user of the telephone be made aware of the changes in advance.

**Telephone Services**  
Changes for users of telecommunications services will be implemented on 14 October 1974. It is essential that the normal user of the telephone be made aware of the changes in advance.

**Telephone Calls**  
Changes for users of telecommunications services will be implemented on 14 October 1974. It is essential that the normal user of the telephone be made aware of the changes in advance.

**Telephone Services**  
Changes for users of telecommunications services will be implemented on 14 October 1974. It is essential that the normal user of the telephone be made aware of the changes in advance.

**Telephone Calls**  
Changes for users of telecommunications services will be implemented on 14 October 1974. It is essential that the normal user of the telephone be made aware of the changes in advance.

**Telephone Services**  
Changes for users of telecommunications services will be implemented on 14 October 1974. It is essential that the normal user of the telephone be made aware of the changes in advance.

**Telephone Calls**  
Changes for users of telecommunications services will be implemented on 14 October 1974. It is essential that the normal user of the telephone be made aware of the changes in advance.

**Telephone Services**  
Changes for users of telecommunications services will be implemented on 14 October 1974. It is essential that the normal user of the telephone be made aware of the changes in advance.

**Telephone Calls**  
Changes for users of telecommunications services will be implemented on 14 October 1974. It is essential that the normal user of the telephone be made aware of the changes in advance.

**Telephone Services**  
Changes for users of telecommunications services will be implemented on 14 October 1974. It is essential that the normal user of the telephone be made aware of the changes in advance.

**Telephone Calls**  
Changes for users of telecommunications services will be implemented on 14 October 1974. It is essential that the normal user of the telephone be made aware of the changes in advance.

**Telephone Services**  
Changes for users of telecommunications services will be implemented on 14 October 1974. It is essential that the normal user of the telephone be made aware of the changes in advance.

**Telephone Calls**  
Changes for users of telecommunications services will be implemented on 14 October 1974. It is essential that the normal user of the telephone be made aware of the changes in advance.

## GENERAL PURPOSE 5W AMPLIFIER

This compact amplifier has a built in loudspeaker and gives 5W r.m.s. output with full bass and treble control. Three input sensitivities make it suitable for use with most electronic musical instruments, tape recorders and record players with ceramic and crystal pick-up cartridges.



... and REMEMBER  
chance to ENTER


ever  
elect

# FREE ENTRY


# COMPETITION
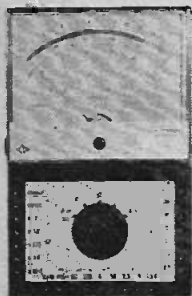
## ... WIN A CHINAGLIA MULTIMETER!


One of these high quality multimeters can be yours—free! Thirteen meters are being presented as prizes in this exciting competition, open only to Everyday Electronics readers.



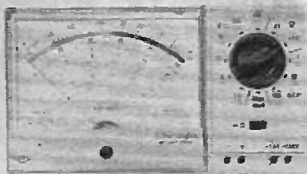First prize, a Chinaglia Dino electronic multimeter which utilises f.e.t.s. to provide a d.c. input impedance of  $200\text{k}\Omega/\text{V}$  and an a.c. impedance of  $20\text{k}\Omega/\text{V}$ . This instrument has 33 ranges, all with high accuracy and costs over £28.



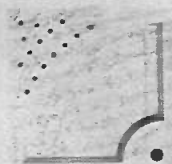Second and third prize, a Chinaglia Minor multimeter with a sensitivity of  $20\text{k}\Omega/\text{V}$  on d.c. and  $4\text{k}\Omega/\text{V}$  on a.c. ranges. This instrument is a versatile pocket-sized instrument, having 25 ranges all with high accuracy. It sells for over £13.



Ten runner-up prizes, a Chinaglia Cito pocket multimeter designed specifically to provide a low cost instrument for everyday use. Sensitivity  $20\text{k}\Omega/\text{V}$  on d.c. ranges and  $2\text{k}\Omega/\text{V}$  on a.c. ranges. With 24 high accuracy ranges the Cito sells for over £10.

### HOW TO ENTER

Place the eight multimeter features, given below, in what you consider to be their order of importance to the average reader working on typical Everyday Electronics constructional projects.

For example, if you consider that "A.C. current ranges" is the most important of them all, write "C" in the box marked 1st on your entry coupon; the key letter of your choice goes into the second box and so on for all eight.

### IMPORTANT

Another free entry coupon will appear in the July issue of Everyday Electronics.

The closing date is Monday 22nd July 1974, to allow plenty of time for you to obtain the second entry coupon from our next issue and post two different attempts in one envelope if you wish.

- A Anti-parallax mirrored scale.
- B Degree of accuracy.
- C A.C. current ranges.
- D Resistance ranges beyond  $1\text{M}\Omega$ .
- E Clearly marked, well arranged controls.
- J High sensitivity (ohms/volt).
- K Large, easy to read scale.
- L Overload Protection.

FREE ENTRY COUPON

### COMPETITION RULES

There is no entry fee, but each attempt must be fully completed in ink on the proper printed coupon cut from Everyday Electronics, and bear the entrant's own full name and address.

Every accepted entry will be examined and the first prize, as described, will be awarded to the entrant who, in the opinion of an expert panel of judges, and in any one attempt, has shown the most skill and judgement in listing the eight features in order of importance. The other prizes will be awarded to the senders of the 12 next best attempts in order of merit. No entrant may win more than one prize.

In the event of a tie or ties for any of the prizes, a further eliminating contest will be conducted by post between the tying competitors to determine such winner/s or winning order.

Any entry which does not comply with the printed instructions or is received after the closing date will be disqualified, as will any received mutilated or illegible, incomplete, bearing alterations, or with more than one key letter in each space. No responsibility will be accepted for entries lost or delayed in the post or otherwise.

The judges' decision, and that of the Editor of Everyday Electronics in all other matters affecting the competition, is final and legally binding. No correspondence can be entered into.

The competition is open to all readers in Great Britain, Northern Ireland, and the Channel Isles except employees (and their families) of IPC Magazines, the printers of Everyday Electronics or of Chinaglia (U.K.) Ltd.

The winners will be notified, and the result announced in the earliest possible issue of this magazine.

ulberry Walk, London, S.W.3

Everyday Electronics, June 1974

# Project 80

the slimmest, most elegant hi-fi modules ever made


Living with hi-fi takes on new meaning with Project 80 modules. They can be assembled virtually anywhere, creating opportunities to install systems hitherto only dreamed about and never before made practical. Quality and reliability are everything you could wish for. Units are mounted by 6BA bolts at rear passing through drilled holes, cases are in black with white embellishment.



2 1/2" high, 3/4" deep  
Slider controls  
New circuitry
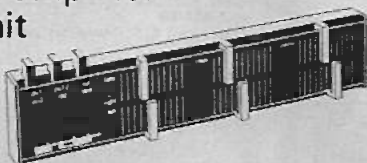
## Stereo 80 pre-amplifier and control unit

Each channel has independent tone and volume slider controls enabling exceptionally good environmental matching to be obtained. A virtual earth input stage forms part of the up-dated circuitry which includes generous overload margins. Clear instructions with template are supplied.




Size - 260 x 50 x 20mm (10 1/2 x 2 x 3/4 ins)  
Inputs - Mag. P.U. 3mV RIAA corrected; Ceramic P.U., Radio, Tape  
S/N ratio - 60dB  
Frequency range - 10Hz to 25KHz + 3dB  
Power requirements - 20 to 35 volts  
Outputs - 100mV + AB monitoring for tape  
Controls - Press button for tape, radio and P.U. Sliders for Volume, Bass and Treble.

R.R.P. £11.95 +£1.19 V.A.T.
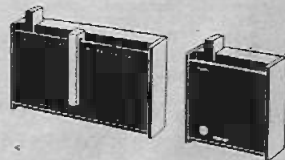
## Project 80 FM tuner and stereo decoder

FM Tuner  
Size - 85 x 50 x 20mm  
Tuning range - 87.5 to 108 MHz  
Detector - i.c. balanced coincidence.  
AFC - Switchable  
One 26 transistor i.c.  
Twin dual varicap tuning  
Distortion 0.2% at 1 KHz for 30% modulation  
4 pole ceramic filter in i.f. section  
Sensitivity - 4 microvolts for 30dB quieting  
Output - 300mV for 75 KH deviation




Decoder - With gallium arsenide tuning beacon and 19-transistor i.c.  
Size - 47 x 50 x 20mm

FM tuner R.R.P. £11.95 +£1.19 V.A.T.

Decoder R.R.P. £7.45 +0.45p V.A.T.

## Project 80 active filter unit

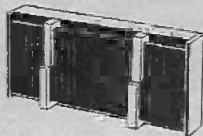

Size - 108 x 50 x 20mm (4 1/4 x 2 x 3/4 ins)  
Voltage gain - minus 0.2dB  
Frequency response - 36Hz to 22KHz, controls minimum  
Distortion - at 1KHz - 0.03% using 30V  
HF cut off (scratch) - 22KHz to 5.5KHz, 12dB/oct. slope  
L.F. cut off (rumble) - 28dB at 20Hz, 9dB/oct. slope

R.R.P. £6.95 +0.69p V.A.T.

## Z.40 & Z.60 power amplifiers

Z.40  
Size - 55 x 80 x 20mm  
Input sensitivity - 100mV  
Output - 15W RMS continuous 8 Ω (35V).  
Frequency response - 10Hz - 100KHz ± 1dB  
Signal to noise ratio - 64dB  
Distortion - less than 0.1% at 10W into 8 Ω  
Power requirements - 12-35 volts

R.R.P. £5.45 +0.54p V.A.T.



Z.60  
Size - 55 x 98 x 20mm  
Input sensitivity - 100-250mV  
Output - 25W RMS 8 Ω (45V).  
Distortion - typically 0.03%  
Frequency response - 10Hz to more than 200KHz ± 1dB  
S/N ratio - better than 70dB

R.R.P. £6.95 +0.69p V.A.T.

## Sinclair power supply units



### PZ.8

The worlds most advanced unit in its class. It is a stabilised unit. Re-entrant current limiting makes damage from overload or even direct shorting impossible, a principle never before incorporated in a commercially available constructor module. Normal working voltage (adjustable) 45V.  
R.R.P. £7.98 +0.79p V.A.T.  
Without mains transformer  
PZ.5 30V unbalanced  
R.R.P. £4.98 +0.49p V.A.T.  
PZ.6 35V stabilised  
R.R.P. £7.98 +0.79p V.A.T.

## Guarantee

If, within 3 months of purchasing any product direct from us, you are dissatisfied with it, your money will be refunded on production of receipt of payment. Many Sinclair appointed Stockists also offer this guarantee.

Should any defect arise in normal use, we will service it without charge. For damage arising from mis-use a small charge (typically £1.00) will be made.

# sinclair

R.O. London Road, St Ives, Huntingdon, PE17 4HJ Phone St. Ives (0480) 64311 Reg. No. 699483 England

To SINCLAIR RADIONICS LTD. ST. IVES, HUNTINGDON PE17 4HJ

Please send post paid \_\_\_\_\_

for which I enclose Cash/Cheque for £ \_\_\_\_\_

including V.A.T.

Name \_\_\_\_\_

Address \_\_\_\_\_

BLOCK LETTERS

6.74





**THE WEST HYDE PRESTIGE CASE**  
The smartest of the West Hyde cases, all anodised aluminium, with top & bottom panels only, in black PVC covered steel (plain or louvered). Free standing or 18" rack mounting with aluminium brackets. Supplied as stock, fully assembled, with S.S. Pozidrive screws.

Prices include panels, feet, P. & P. and VAT. State whether 1, 2, or Full Panels required.

BC21 (31" whole rack)	£13-46	Pr. brackets 88p	Extra for louvers 74p
BC22 (31" half rack)	£10-90	88p	74p
BC31 (31" whole rack)	£15-53	£1-24	74p
BC32 (51" half rack)	£12-79	£1-24	74p




A smart miniature case in tough, rigid, high-gloss black A.B.S. Front panels in either aluminium or white PVC/Steel. Built-in slots for PC cards, dividers, or screens. Chassis or PC boards can be supported on 'P' clips from internal pillars. Excellent as encapsulation boxes. Also available without panel and screws. Minimum order £1.

M2 65mm x 100mm x 50mm	1 off 10 off
2 1/2" x 3 1/2" x 2"	51p 45p
M3 100mm x 130mm x 50mm	
3 1/2" x 5" x 2"	87p 58p

Prices include P. & P. and 10% VAT. Less for quantities.


## CORTIL handles

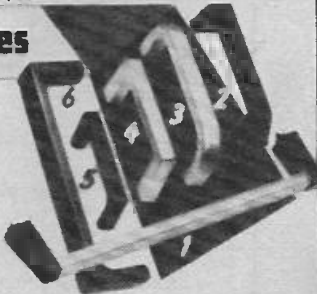(1) No. 265  
Anodised aluminium centre bar. Black plastic brackets with moulded-in core. 75mm @ 87p. 5 more sizes up to 154mm.  
(2) No. 281.1  
Nylon 112mm. Load 50 Kg. @ 45p.  
(3) No. 277  
Al., ground, polished, anodised. 88mm @ 84p, 120mm @ £1-06.  
(4) No. 255  
Satin all. 57-5mm @ 84p, 102mm @ £1-01, 145-5mm @ £1-17.  
(5/6) No. 250  
Black nylon Very comfortable. 75mm @ 29p, 110mm @ 41p, 155mm @ 67p.  
Prices include VAT. Less for quantity. P. & P. 20p any quantity. Write or phone for new catalogue.


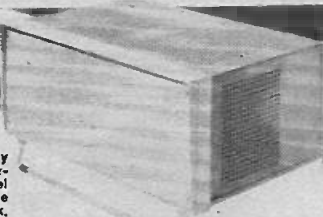
## AMTRON VENTILATED METAL CASES

Ideal for Stabilised Power Supply Units. A lightweight case with perforated sides and top. The front panel is of heavy gauge anodised all. The top, bottom, sides and back interlock, secured by 4 screws. The front frame is a clever moulding holding the panels allowing for 4 hidden fixings for a chassis if required (not supplied). Integrally moulded front feet also form the mounting for the tilt support which is standard with this matt blue painted case.



Height	Length	Depth	Code	1 off
120mm	234mm	138mm	00/3009-00	£5-40
120mm	234mm	138mm	00/3009-10	£5-01
120mm	234mm	188mm	00/3009-20	£7-07

Incl. feet tilt, VAT and P & P.  
Less for quantity

## CORTIL MOD-2

The design of these cases permits the instrument to be built or serviced within their external panels. 48 shapes. Low cost. Blue PVC/Steel with white P.V.C. coated aluminium panels.

W.	H.	D.	1 off	W.	H.	D.	1 off
A 4-5"	3"	6-5"	£3-60	M 4-5"	3"	13"	£4-44
B 4-5"	7"	6-5"	£4-44	N 4-5"	7"	13"	£5-44
C 4-5"	10"	6-5"	£4-91	O 4-5"	10"	13"	£6-01
D 9"	3"	6-5"	£4-91	P 9"	3"	13"	£5-44
E 9"	7"	6-5"	£5-44	Q 9"	7"	13"	£6-01
F 9"	10"	6-5"	£6-23	R 9"	10"	13"	£6-01
G 13"	3"	6-5"	£5-44	S 13"	3"	13"	£6-01
H 13"	7"	6-5"	£6-23	T 13"	7"	13"	£6-41
I 13"	10"	6-5"	£6-91	U 13"	10"	13"	£10-20
J 18"	3"	6-5"	£6-23	V 18"	3"	13"	£8-41
K 18"	7"	6-5"	£8-41	W 18"	7"	13"	£10-20
L 18"	10"	6-5"	£10-20	X 18"	10"	13"	£12-21

Woodgrain: D @ £5-44, E & G @ £6-23, H @ £8-91  
Prices include screws, rubber feet, one or two chassis according to size, and P. & P. and VAT.  
Prices correct to 31st May 1974

## WEST HYDE

WEST HYDE DEVELOPMENTS LTD., RYEFIELD CRES., NORTHWOOD HILLS, NORTHWOOD, MIDD. HA5 1NN.  
Tel: Northwood 26841 or 25732. Telex: 923231

# SPARKRITE MK II

## ELECTRONIC IGNITION KIT



### COMPRISES

Everything:—  
Ready Drilled Case and Metalwork, Cables, Coil Connectors, Silicon Grease, Printed Circuit Board, 5 year guaranteed components and a full 8-page instruction leaflet.

**WHEN COMPLETE THE UNIT CAN BE FITTED TO YOUR CAR IN ONLY 15 MINUTES USING THE STANDARD COIL AND CONTACT BREAKER POINTS: TO GIVE YOU:—**

Instant all weather starting. Up to 20% fuel saving. Longer battery life. Higher top speed. Faster acceleration. Spark plugs last about five times longer. Misfire due to contact breaker, bounce electronically eliminated. Purer exhaust emission resulting in less air pollution. Contact breaker burn eliminated.

Suitable for all petrol engines up to 8 cylinders

### KIT PRICE ONLY £11-62

Ready Built Car Unit	£14-85	(prices include V.A.T. and post & packing)
Single coil C.B. Motor Cycle Unit	£17-60	
Twin coil C.B. Motor cycle unit	£23-24	When ordering state positive or negative earth and 6 or 12 volt.
Triple coil C.B. Motor cycle unit	£27-50	

MOTOR CYCLE UNITS NOT AVAILABLE IN KIT FORM

### ORDER NOW FROM

ICE ELECTRONIC SYSTEMS DEPT E.E.  
114 PARK FARM ROAD  
BIRMINGHAM B43 7QH

## ENGINEERS

# FREE

## YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost B.I.E.T. home study course. There are no books to buy and you can pay-as-you-learn.

The B.I.E.T. guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.



POST NOW

### CUT OUT THIS COUPON

#### CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

Practical Radio & Electronics (Technatron) Engineering	<input type="checkbox"/>	Radio Amateurs Practical TV Colour Television Computer Electronics	<input type="checkbox"/>	General Electrical Engineering Society of Engineers (Electrical Eng.)	<input type="checkbox"/>
Television Maintenance & Servicing General Radio & TV Engineering	<input type="checkbox"/>	C & G LI Radio	<input type="checkbox"/>	Electrical Installations and Wiring (Primary)	<input type="checkbox"/>
Radio Servicing, Maintenance and Repairs	<input type="checkbox"/>	TV Servicing Cert.	<input type="checkbox"/>	C & G Electrical Technicians (Primary)	<input type="checkbox"/>
City & Guilds Radio, TV Electronics	<input type="checkbox"/>	Post Master General 1st & 2nd class Certs.	<input type="checkbox"/>	C & G Telecommunications	<input type="checkbox"/>
Mechanics	<input type="checkbox"/>	C & G Electrical Engineering Practice	<input type="checkbox"/>		
		C & G LI Installations and Wiring	<input type="checkbox"/>		

To B.I.E.T. BEE 04 Aldermaston Court, Reading RG7 4PF QK BEE 04

NAME (Block Capitals Please)

ADDRESS

Other subjects

Age

Accredited by C.A.C.O. Member of A.B.C.O.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGISTS

# SEMICONDUCTOR PRIMER

By A. P. STEPHENSON

## 13 THE TRANSITION FREQUENCY

The gain of a transistor is not independent of frequency.

As frequency is increased,  $h_{fe}$  remains fairly constant until a certain upper limit is reached.

Beyond this frequency, the  $h_{fe}$  falls, and eventually reaches unity.

The transition frequency  $f_T$  is this limit, where

$f_T$  = frequency at which  $h_{fe}$  has fallen to unity.

As an example, the BC107, BC108 and BC109 all have an  $f_T$  of 300MHz, providing  $I_c$  is held at around 10mA.

A transistor is naturally a useless animal at its transition frequency, but  $f_T$  is a useful figure for the following reason:

As frequency is successively halved, the gain is doubled (which is a convenient method of predicting the gain at high frequencies).

Thus, the BC108 will have an  $h_{fe}$  of 1 at 300, 2 at 150, 4 at 75, and 8 at 37.5MHz.

This simple relation only holds for about four or five "halvings." Eventually, the figure for  $h_{fe}$  reaches its normal mid-frequency value, which in most cases will be at about  $\frac{1}{10}$ th  $f_T$ .

The BC108 published figures of  $h_{fe} = 125$  (minimum) which means this figure is valid up to about 30MHz.

## 14 CHOICE OF COLLECTOR CURRENT

Some humans are said to be highly strung or touchy and sensitive.

All transistors are touchy and sensitive!

Changes in d.c. operating bias, temperature and signal frequency all tend to change the so called constants such as  $h_{fe}$  and noise figure.

Detailed data sheets always include numbers of graphs, showing how the constants change  $I_c$ ,  $I_b$  temperature etc. In the absence of these, the following broad rules can be accepted:

- (1)  $h_{FE}$ ,  $h_{fe}$  rises as d.c. collector current rises. Therefore it is wise to design with fairly high  $I_c$  values, (at least 1mA or more). BC108, BC109, BC107 will still operate reasonably with  $I_c$  as low as 10 $\mu$ A but with much reduced  $h_{FE}$  and  $h_{fe}$ .

- (2) Transistor input resistance ( $r_{in}$  or  $h_{ie}$ )  
 $r_{in}$  falls as  $I_c$  is increased. Thus for high  $r_{in}$  a low  $I_c$  should be used

- (3) Highest operating frequency  
This rises as  $I_c$  is increased, because  $h_{fe}$  rises. For very high operating frequencies, 10mA or more is customary.

- (4) Noise  
Transistors generate some noise. This noise is reduced if  $I_c$  is kept very low. Thus for low noise input stages, operate with very low  $I_c$  value (10 or 20  $\mu$ A).

## 15 PRODUCTION SPREADS

The range of variation expected between the manufacturers published data and the actual values found in a given transistor specimen are often substantial.

Semiconductor manufacture has improved enormously in the last five years but there are still very wide "production spreads" in any given transistor.

$h_{fe}$  is the worst offender of all. Taking the BC109 as a typical example, the user must expect to find any value between 240-900, representing a variation of almost 400 per cent!

Almost every other data item suffers wide variations. Superficially, it would appear that predictable design is impossible, but such is not the case for the following reasons:

- (a) Manufacturers quote three figures for most data, called **Typical**, **Minimum** and **Maximum**. Thus the **minimum**  $h_{fe}$  for BC109 is guaranteed to be 240.

The procedure adopted for design is based on the philosophy of "worst-case conditions" which is nothing more than adopting a pessimistic attitude—expecting all BC109 specimens to be the worst ones in the range. An attitude like this can lead occasionally to elation but never disappointment.

(b) Use of negative feedback in practically every circuit. Negative feedback always tends to reduce the effects of production spreads because the gain of such a stage is almost independent of the transistor! To illustrate this point, an equation for the voltage gain of an amplifying stage is

$$A = \frac{R_c}{R_e}, \text{ where } R_c, R_e \text{ are resistors}$$

Without negative feedback, the gain would vary widely with different specimens of transistor.

# DOWN TO EARTH

By GEORGE HYLTON

"I've come across the term 'amplified diode voltage stabilizer.' What is this, and what is it used for?"

To begin with, look at a diode stabiliser without any amplification (Fig. 1). This makes use of the fact that, once a junction diode conducts, increasing the current through it doesn't increase the voltage very much. A silicon diode begins to conduct at about 0.5V. At its maximum safe current the voltage drop across it is about 1V.

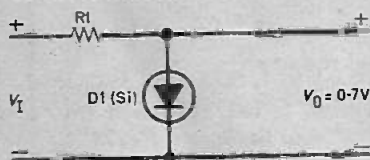


Fig. 1. Simple diode stabiliser circuit.

Both voltages vary from diode to diode, but an average voltage drop at a moderate current is always near 0.7V. (For germanium the voltage is about 0.3V, but remember that this applies only to junction diodes, not point-contact diodes).

In Fig. 1,  $V_1$  is the unstabilised input voltage.  $R_1$  absorbs the unwanted part, leaving  $V_0$ , the stabilised output, at around 0.7V. If  $V_1$  is about 2.7V, and an output of 0.7V, 1A is required, then  $R_1$  must drop 2V at 1A; i.e.,  $R_1$  must be 2 ohms. Readers familiar with Zener diode stabilisers will see that the design procedure for this circuit is the same.

Who wants a 0.7V stabilised supply? The usual requirement is for higher voltages. You can increase the voltage by connecting a number of diodes in series: two give 1.4V, three 2.1V and so on. If more than a few volts is needed, it's cheaper to use a Zener, which gives better stabilisation anyway.

## AMPLIFICATION

This is where the amplified diode circuit comes in. It will give

any voltage you like, using only one diode. The circuit (Fig. 2) seems wrongly named. No diode!

But the base-emitter junction of TR1 is a diode. It begins to pass current (if TR1 is a silicon transistor) at about 0.5V, turning on the transistor in the process, of course. The resulting collector current, flowing through  $R_1$ , pulls down the output voltage  $V_0$ , just as in the simple diode stabiliser.

The difference is that the base voltage  $V_B$  is only a part of the output voltage, because  $R_2$  and  $R_3$  form a voltage divider. If  $V_B$  is one-tenth of  $V_0$ , then TR1 will not begin to conduct until  $V_0$  reaches about 5V. To make TR1 conduct strongly calls for a  $V_0$  of perhaps 7V, so the circuit is a 7V stabiliser.

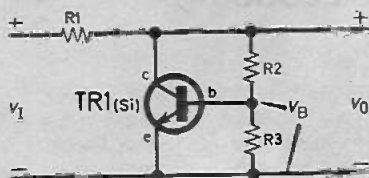


Fig. 2. Stabiliser using amplified diode principle.

By varying the ratio of  $R_2$  to  $R_3$  the stabilised output can be adjusted to any voltage within the capacity of the transistor. However, if the stabilised voltage is very large the stabilisation is poor, and the circuit is best suited to lowish output voltages.

Amplified diodes are often used in integrated circuits, in the form shown in Fig. 3. Here  $R_2$  and  $R_3$  are absent because the whole of the output voltage is fed back to the base. A silicon transistor still works as a transistor under these conditions and behaves like a simple diode with sharper turn-on. It is often referred to as a "diode" or a "shorted transistor".

In Fig. 4, an amplified diode (TR1) is used for setting up the base bias of a complementary


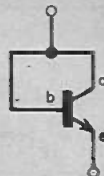


Fig. 3. Amplified diode found in integrated circuits.

output pair in a class B amplifier. The adjustability of the arrangement makes it very useful here, and the low voltage needed is just what the circuit can provide.

Fig. 4. Using an amplified diode for setting bias.

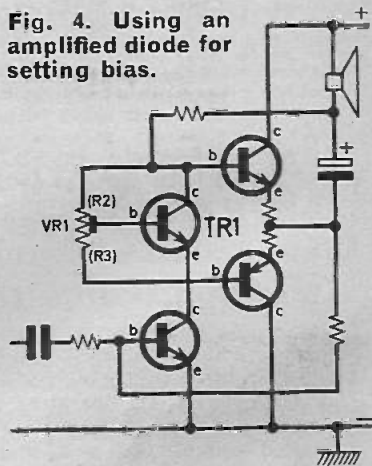

### 4-STATION INTERCOM



£13.95

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 47p

### MAINS INTERCOM NEW MODEL

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £22.95 per pair P. & P. 60p

### INTERCOM BABY ALARM



OUR PRICE ONLY £6.50

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire and Battery. P. & P. 35p

### TELEPHONE AMPLIFIER



£4.95

Why not boost business efficiency with this incredible Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Complete with Battery. P. & P. 27p. Full price refunded if not satisfied in 7 days.


WEST LONDON DIRECT SUPPLIES (PW12)  
169 KENSINGTON HIGH STREET, LONDON, W.8.


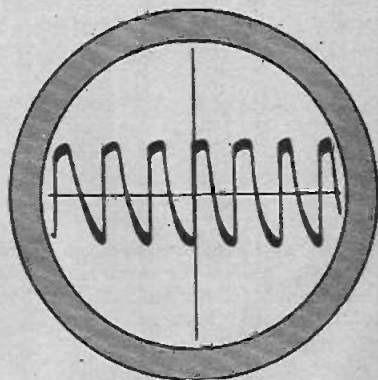
# look! electronics really mastered

... practical  
... visual  
... exciting!

no previous knowledge  
no unnecessary theory  
no "maths"



RAPY


## BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

### 1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.
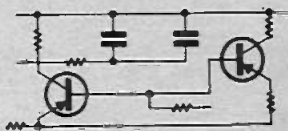
### 2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

### 3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

**FREE** POST NOW for BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**  
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:

*we do not employ representatives*

NAME

**BLOCK CAPS**

ADDRESS

PLEASE EEL 6.4.

**special free gift also to all our students**



# -the lowest prices!

## BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed

Pak No.	EQVT
T1 8 213713	OC71
T2 8 21374	OC75
T3 8 21316	OC81D
T4 8 21381T	OC81
T5 8 21392T	OC83
T6 8 21344B	OC44
T7 8 21345B	OC45
T8 8 21378	OC78
T9 8 21395A	2N1302
T10 8 21417	AT17

All 55p each pak

**WD 100 NIXIE DRIVER TRANSISTOR.**  
Suitable replacement for 88X 21, 407, 2N 1893 129.

1	25	100+
0-19	0-17	0-18

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqty. 2XN300 6p each. Any Qty.

**GP 100 TO3 METAL CASE GERMANIUM**

V<sub>ceo</sub>=80V, V<sub>ceo</sub>=50V, I<sub>C</sub>=10 amps, P<sub>tot</sub>=30W, h<sub>FE</sub>=30-170.  
Replaces the majority of germanium power transistors in the OC, AD and NKT range.

1	25	100+
0-48	0-44	0-40

**GP 300 TO3 METAL CASE SILICON**

V<sub>ceo</sub>=100V, V<sub>ceo</sub>=60V, I<sub>C</sub>=15 amps, P<sub>tot</sub>=115W, h<sub>FE</sub>=20-100T, 1MHz. Suitable replacement for 2N 3005, 2N3171 or 2N 100-2.

0-55	0-53	0-51
------	------	------

**NEW 8th EDITION**

**TRANSISTOR EQUIVALENTS BOOK.** A complete cross-reference and equivalents book for European, American and Japanese Transistors. Exclusive to B.F. PAK. £1.55 each.

**A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE STOCK. SEND FOR FREE LIST.**

## UT 46 UNIJUNCTION TRANSISTORS

Suitable replacement for T18 43rand BEN 3000 also electrically equivalent to 2N2649

0-30	0-28	0-22
------	------	------

## GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18

SIM. TO 2N708/8, BSY 27/28/95A. All usable devices no open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N906, 10Y7/9. When ordering, please state preference NPN or PNP.

Pak No.	2p	5p
20	For	0-55
50	For	1-10
100	For	1-52
500	For	8-25
1000	For	14-30

## SIL. G.P. DIODES 2p

300mA, 30-0-55  
40PIV (Min.), 100-1-65  
Sub-Min. 500-8-60  
Fully Tested 1,000-0-90  
Ideal for Organ Builders.

## R 2400 TO3 NPN SILICON HIGH VOLTAGE

V<sub>ceo</sub> 250V, V<sub>ceo</sub> 100V, I<sub>C</sub> 6 amps, P<sub>tot</sub> 30W, h<sub>FE</sub> typ. 20  
fT - 5MHz.

1	25	100+
0-55	0-50	0-44

## ADI61/162

M/P COMP GERM TRANS. OUT LOW-FREQ. PHASE OP 75p PWR PAIR.

## LOOK FOR OUR AUDIO & ELECTRONIC COMPONENTS

ADVERTISEMENTS in PRACTICAL ELECTRONICS RADIO CONSTRUCTOR

## SILICON PHOTO TRANSISTOR, TO-18 Lens and NPN Sim. to BFX25 and P21. BRAND NEW. Full data available. Fully guaranteed.

Qty. 1-24 25-99 100+  
Price ea. 69p 44p 38p

## QUALITY TESTED SEMICONDUCTORS

Pak No. Price 2p

Q1	20 Red spot transistors PNP	0-55
Q2	16 White spot R.F. transistors PNP	0-55
Q3	4 OC 77 type transistors	0-55
Q4	6 Matched transistors OC44/45/81/81D	0-55
Q5	4 OC 75 transistors	0-55
Q6	5 OC 72 transistors	0-55
Q7	4 AC 128 transistors PNP high gain	0-55
Q8	4 AC 126 transistors PNP	0-55
Q9	7 OC 81 type transistors	0-55
Q10	7 OC 71 type transistors	0-55
Q11	2 AC 127/128 Complementary pairs PNP/NPN	0-55
Q12	3 AP 116 type transistors	0-55
Q13	3 AP 117 type transistors	0-55
Q14	3 OC 171 H.F. type transistors	0-55
Q15	7 2N2926 Sil. Epoxy transistors mixed colours	0-55
Q16	2 12T260 low noise Germanium transistors	0-55
Q17	5 NPN 2 x 8T.141 & 3 x 8T.140	0-55
Q18	4 MADT'S 2 x MAT 100 & 2 x MAT 120	0-55
Q19	3 MADT'S 2 x MAT 101 & 1 x MAT 121	0-55
Q20	4 OC 44 Germanium transistors A.F.	0-55
Q21	4 AC 127 NPN Germanium transistors	0-55
Q22	20 NKT transistors A.F. R.F. coded	0-55
Q23	10 OA 292 Silicon diodes sub-min.	0-55
Q24	8 OA 91 diodes	0-55
Q25	15 IN914 Silicon diodes 2A PIV 75mA	0-55
Q26	8 OA95 Germanium diodes sub-min IN89	0-55
Q27	2 10A PIV Silicon rectifiers IN425R	0-55
Q28	2 Silicon power rectifiers BYZ 13	0-55
Q29	4 Silicon transistors 2 x 2N896, 1 x 2N897, 1 x 2N898	0-55
Q30	7 Silicon switch transistors 2N706 NPN	0-55
Q31	6 Silicon switch transistors 2N708 NPN	0-55
Q32	3 PNP Silicon transistors 2 x 2N131, 1 x 2N132	0-55
Q33	3 Silicon NPN transistors 2N1711	0-55
Q34	7 Silicon NPN transistors 2N2369, 500MHz (code F397)	0-55
Q35	3 Silicon PNP TO-5, 2 x 2N2904 & 1 x 2N2905	0-55
Q36	7 2N3845 TO-18 plastic 300 MHz NPN	0-55
Q37	3 2N3853 NPN Silicon transistors	0-55
Q38	7 NPN transistors 4 x 2N3703, 3 x 2N3702	0-55

## ELECTRONIC SLIDE-RULE

The MK Slide Rule, designed to simplify Electronic calculations features the following scales: Conversion of Frequency and Wavelength. Calculation of L, C and fo of Toned Circuits. Reactance and Self Inductance. Area of Circles. Volume of Cylinders. Resistance of Conductors. Weight of Conductors. Decibel Calculations. Angle Functions. Natural Logs and e<sup>x</sup> Functions. Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and Hp. A manual for every electronic engineer and enthusiast. Size 7 1/2" cm x 4cm. Complete with case and instructions. Price each: £3.69

## FULL RANGE OF ZENER DIODES

VOLTAGE RANGE 2-237V, 400mV (DO-7) Volume of Cylinders. Resistance of Conductors. Weight of Conductors. Decibel Calculations. Angle Functions. Natural Logs and e<sup>x</sup> Functions. Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and Hp. A manual for every electronic engineer and enthusiast. Size 7 1/2" cm x 4cm. Complete with case and instructions. Price each: £3.69

## NEW LOW PRICED TESTED S.C.R.'s

PIV 1A	5A	5A	5A	10A	10A	30A
P1V1A	T05	T05E	T06T064	T048T048T048T048	T048T048T048	T048T048T048
50-26	0-28	0-39	0-39	0-52	0-55	0-59
100-28	0-37	0-52	0-52	0-55	0-64	0-70
200-39	0-41	0-54	0-54	0-53	0-67	0-83
400-48	0-52	0-62	0-62	0-74	0-83	1-02
600-69	0-63	0-75	0-75	0-85	1-07	1-38
800-70	0-77	0-88	0-88	0-99	1-32	1-69

## SIL. RECTS. TESTED

PIV 200mA	750mA 1A	1-5A	3A	10A	30A
50-0-4	0-06	0-06	0-08	0-16	0-23
100-0-4	0-07	0-06	0-15	0-18	0-26
200-0-6	0-10	0-07	0-16	0-22	0-27
400-0-7	0-15	0-08	0-22	0-30	0-41
600-0-8	0-18	0-11	0-26	0-38	0-50
800-0-11	0-19	0-12	0-28	0-41	0-51
1000-0-12	0-28	0-16	0-33	0-51	0-70
1200	0-37	0-42	0-63	0-83	1-10

## INTEGRATED CIRCUIT PAKS

Manufacturers' "Full Outlets" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC99	12 x 7400	0-85	UIC46	8 x 7446	0-55	UIC90	5 x 7490	0-85
UIC98	12 x 7401	0-85	UIC48	8 x 7448	0-55	UIC91	5 x 7491	0-85
UIC97	12 x 7402	0-85	UIC50	12 x 7450	0-85	UIC92	5 x 7492	0-85
UIC96	12 x 7403	0-85	UIC51	12 x 7451	0-85	UIC93	5 x 7493	0-85
UIC95	12 x 7404	0-85	UIC53	12 x 7453	0-85	UIC94	5 x 7494	0-85
UIC94	12 x 7405	0-85	UIC54	12 x 7454	0-85	UIC95	5 x 7495	0-85
UIC93	8 x 7406	0-85	UIC56	8 x 7456	0-55	UIC96	5 x 7496	0-85
UIC92	8 x 7407	0-85	UIC70	8 x 7470	0-85	UIC90	5 x 74100	0-85
UIC91	12 x 7410	0-85	UIC72	8 x 7472	0-85	UIC91	5 x 74101	0-85
UIC90	12 x 7420	0-85	UIC73	8 x 7473	0-85	UIC141	5 x 74141	0-85
UIC89	12 x 7430	0-85	UIC74	8 x 7474	0-85	UIC161	8 x 74161	0-85
UIC88	12 x 7440	0-85	UIC76	8 x 7476	0-85	UIC154	5 x 74154	0-85
UIC87	5 x 7441	0-85	UIC80	5 x 7480	0-85	UIC159	5 x 74159	0-55
UIC86	8 x 7442	0-85	UIC81	5 x 7481	0-85	UIC199	5 x 74199	0-55
UIC85	5 x 7443	0-85	UIC82	5 x 7482	0-85	UIC91	25 Assorted	74's £1-65
UIC84	5 x 7444	0-85	UIC83	5 x 7483	0-85			
UIC83	5 x 7445	0-85	UIC86	5 x 7486	0-85			

Packs cannot be split, but 25 assorted pieces (four mix) is available as PAK UIC91

## POST OFFICE TELEPHONE DIALS 60p each.

F.E.T.'S  
2N3819 31p 2N5458 35p  
2N3820 55p 2N5459 44p  
2N3821 30p 2N5460 66p  
2N3823 81p MFF105 41p

## CADMIUM CELLS

FREE One 55p Pak of your own choice free with orders valued £4 or over

## 2N3055

115 WATT SIL PWR NPN 55PEACH

## DIACS TRIACS

FOR USE WITH TRIACS  
BR100 (D32) 41p each

10 AMP POTTED BRIDGE RECTIFIER on heat sink 100PIV, 95p each

Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

# B.F. PAK

P.O. BOX 6, WARE - HERTS  
Postage and packing add 11p. Overseas add extra for airmail.  
Minimum order 55p. Cash with order please.  
Guaranteed Satisfaction or Money Back



# Henry's

**DON'T RELY ON YOUR MEMORY  
BUY NOW AT BARGAIN PRICES**  
Hi Fi and Transistors - Up to date  
Brochures on request

**HENRY'S  
CATALOGUE**  
Due to rapid price changes,  
shortages of paper and raw  
materials, all prices in the  
existing catalogues no longer  
apply. Call or phone for latest  
prices. A new catalogue will  
be available for Aug/Sept. 1974.



**UK's  
LARGEST RANGE  
OF KITS &  
GADGETS**



## TEST EQUIPMENT MULTIMETERS

- (carr. etc. 30p)
- ITI-2 20K Volt Slimline 5 95
  - M210 (Case £1.25) 20K Volt Slimline de-luxe 6 75
  - TLH33D 2K Volt Robust 7 50
  - U437 10K Volt Steel case. AC up to 40 KHz 4 95
  - AF105 (Case £1.90) 50K Volt 11 95
  - UA313 20K Volt AC current. Steel case 10 50
  - U4341 Plus Built in transistor tester 10 50
  - Model 500 (Case £1.95) 30K Volt 9 95

## OTHER EQUIPMENT

- SE250B Pocket Signal Injector 2-10 carr. 15p
- SE500 Pocket Signal Tracer 1-70 carr. 15p
- TE15 Grid Dip meter 400KHz-280MHz 15-00 carr. 30p
- TE40 AC Multivoltmeter 1-2MHz 19-75 carr. 35p
- TE65 28 Range valve voltmeter 22-50 carr. 40p
- TE20D 120KHz-500MHz RF Generator 18-95 carr. 40p
- TE22D 20KHz-200KHz Audio Generator 19-95 carr. 40p
- SE350A Deluxe Signal Tracer 12-50 carr. 20p
- SE430 Volts/ohms/R-C sub./RF field/RF gen. 14-75 carr. 20p

## New Revolutionary Supertester 680R

- 680R Multi-tester £18.50
- | Accessories          | Price |
|----------------------|-------|
| Transistor tester    | 11-00 |
| Electronic voltmeter | 10-00 |
| Amplifier            | 11-95 |
| Temperature probe    | 11-95 |
| Gauss meter          | 11-95 |
| Signal Injector      | 5-95  |
| Phase Sequence       | 5-95  |
| EHT Probe            | 5-95  |
| Shunts 25/50/100A    | 4-50  |

## A SELECTION OF INTERESTING ITEMS

- C3025 Compact transistor tester 6-95 p & p 15p
- Q4002 Photoelectric System £13-70
- E1310 Stereo mag. cart. preamp. 4-30 p & p 25p
- Easiphone D1201 telephone amplifier 7-50 p & p 25p
- D1203 Teleamp. with PU coil 4-95 p & p 20p
- LL1 Door Inter. comm. and chime 6-40 p & p 25p
- 1 Kw Dimmer/contactor 3-00 p & p 10p
- 8" Twin spring unit For 3-30 p & p 15p
- 16" Twin spring unit Reverbs 6-85 p & p 25p
- US50 Ultrasonic Switch Transmitter/Receiver £12-75
- C3041 1-250 MHz £2-25
- C3043 5CH 1-300 MHz £5-75
- VHF 105 Aircraft Band Converter 4-50 p & p 15p
- B2005 4 ch. mic. mixer 4-20 p & p 15p
- B2004 2 ch. Stereo mixer 6-75 p & p 15p
- PK3 Kit. Etch your own ptd circuits £1-95 p & p 20p

## BUILD THIS RADIO

Portable MW/LW radio kit using Mullard RF/IF module. Features MW—bandspread for extra selectivity. Slow motion tuning. Fibre glass PVC cabinet. 500MW output. All parts £7-98 (battery 22p), carr. etc. 32p.



## EXCLUSIVE: SPECIAL OFFERS

- MW/LW CAR RADIO AKAI GXC40 + or - Earth with speaker Stereo cassette recorder, and fixings. £8-50 c/p. 30p. £59-95 c/p. 50p.
- 8 TRACK CAR STEREO Pair Akai ADM micro- (+ Earth) with speakers in phones. £8-95 c/p. 20p. Pds & fixgs. £12-50 c/p. 40p.
- Portable Battery Cassette TAPE PLAYER—for car or Tape Player £7-25.
- Car Lighter Plug n' socket for all cassette and radio £7/9 volt. output (state width) £1-95 each.
- Rotel Stereophones £4-50 MAINS UNIT for BC808
- RH700 £6-75 BC811M £2-95 (state model)
- RH430 £3-30
- Rotel RA310 15+15 watt COMPACT RECORD Stereo Amplifier (List £52-00) £34-92. Complete with Speakers (List £54-50) Price £38-98. Plus Cassette Recorder £12-75 free pair of stereo phones.


## SPECIAL PURCHASES

**UHF TV TUNERS CHANNELS 21 to 64**  
Brand new transistorised geared tuners for 625 Line Receiver IF output. £2-50. Post 20p.



## EASY TO BUILD KITS BY AMTRON—EVERYTHING SUPPLIED

- | Model No. | Description  | Price |
|-----------|--|-------|
| 310       | Radio control receiver                             | 3-29  |
| 300       | 4-channel R/C transmitter                          | 6-61  |
| 345       | Superhet R/C receiver                              | 6-61  |
| 63        | Simple transistor tester                           | 1-94  |
| 115       | 8 watt Amplifier                                   | 4-50  |
| 120       | 12 watt amplifier                                  | 4-73  |
| 125       | Stereo control unit                                | 6-61  |
| 130       | Mono control unit                                  | 4-18  |
| 605       | Power supply for 115                               | 5-31  |
| 610       | Power supply for 120                               | 5-31  |
| 615       | Power supply for 2 x 120                           | 5-31  |
| 230       | AM/FM aerial amplifier                             | 6-64  |
| 240       | Auto packing light                                 | 3-29  |
| 240       | Auto packing light                                 | 6-90  |
| 275       | Mic. preamplifier                                  | 6-98  |
| 570S      | LF generator 10Hz-1mHz                             | 21-45 |
| 575S      | Sq. wave generator 20Hz-20KHz                      | 19-77 |
| 590       | SWR meter  | 9-47  |
| 630       | STAB Power supply 6-12v 0-25-0-1A                  | 9-24  |
| 690       | DC motor speed Gov.                                | 3-31  |
| 700       | Electronic Chaffinch                               | 7-82  |
| 760       | Acoustic switch                                    | 12-57 |
| 780       | Metal Detector (electronics only)                  | 10-91 |
| 790       | Capacitive Burglar alarm                           | 7-92  |
| 835       | Guitar preamp.                                     | 4-98  |
| 840       | Delay car alarm                                    | 6-99  |
| 875       | CAP. Discharge ignition for car engine (-Ve Earth) | 13-99 |
| 80        | Scope Calibrator                                   | 2-85  |
| 255       | Level indicator                                    | 6-98  |
| 525       | 120-160MHz VHF timer                               | 16-31 |
| 715       | Photo cell switch                                  | 8-97  |
| 795       | Electronic continuity tester                       | 4-87  |
| 860       | Photo timer  | 15-51 |
| 235       | Acoustic Alarm for driver                          | 8-61  |
| 485       | Quartz XTAL checker                                | 9-90  |
| 220       | Signal Injector                                    | 2-30  |
| 390       | VOX  | 15-50 |
| 432       | Testakt!   | 19-30 |
| 670       | Buffer Battery Charger                             | 6-55  |
| 850       | Electronic Keyer                                   | 16-75 |
| 820       | Electronic Digital Clock                           | 58-50 |

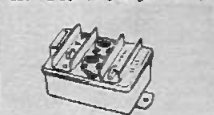

**ALL KITS OFFERED  
SUBJECT TO  
STOCK  
AVAILABILITY**  
Prices correct at  
time of preparation.  
Subject to change  
without notice.

## BUILD THIS TUNER

MW/LW Radio Turner to use with any amplifier. Features Mullard RF/IF module Ferrite aerial, built in battery. Excellent results. Size 7" x 2 1/2" x 3 1/2". All parts £4.85, carr. 15p.

## MULTI-USE & RADIONIC KITS

- 10-1 10 Projects 3-60
  - 50-1 10 Projects 8-00
  - 150-1 150 Projects 13-20
  - Telephone Communicator 7-20
  - X20 20 (Elec.) Projects 4-95
  - X40 40 (radio) Projects 9-45
- (carr. packing 40p)

All transistor circuits with hand books

**TBA800 5 WATT I.C.**  
Suitable alternative to SL4003. 5/30 volt operated. 8/16 ohm 5 watt output. With circuits and data £1-50.



**STROBE TUBE ZFT4A.** Suitable for December '73 Trap. Electronics £3-00.



- ST2 (D32) DIAC 25p
- CR51/40 SCR 45p.
- ZFT4 £3-00
- ZFT8 £3-50

## JUST A SELECTION

- \*TBA800 5 Watt IC £1-50
  - \*Sinclair ICR 6 Watt IC £1-80
  - \*ZN4141C Radio £1-20
  - \*Ultrasonic Transducers £5-90 pr.
  - \*3015F SEG Indicator £1-70
  - TTL 209 LED 24p each. 22p each per 10
- \* With circuits/data sheet
- OVER 1500 DIFFERENT SEMI-CONDUCTOR DEVICES IN STOCK**  
Free stock list—latest edition (Ref. 36) on request. Includes radio valves, I.C.'s Rectifiers, Trilacs, SCR's, LED's, etc. More types—better prices—discounts for quantity small or large.

## GARRARD BATTERY TAPE DECK



GARRARD 2 speed 9 volt tape decks. Fitted record/play and oscillator/Erase heads. Wind and rewind controls. Takes up to 4" spools. Brand new complete with head circuits. £9-50 carr. 30p.

## TOP QUALITY SLIDER CONTROLS

60mm stroke high quality controls complete with knobs (post, etc. 15p any quantity).

Singles Log and Lin 5K, 10K, 22K, 50K, 100K, 250K, 500K, 1 Meg. 45p each.

Ganged Log and Lin 10K, 22K, 50K, 100K, 250K, 500K, 1 Meg. 45p each. (Quantity discounts available)


Complete with knobs.

## MARRIOT TAPE HEADS

- 4 TRACK MONO or 2 TRACK STEREO
  - '17' High Impedance £2-50
  - '18' Med. Impedance £2-50
  - '36' Med. Impedance £5-00
  - R730/E73 2 track mono Record/Erase low imp. 75p pair.
  - Erase Heads for '17', '18' and '36' £1-00
  - '63' 2 track mono, Hi Imp. £1-75
  - '43' Erase Head for '63' 75p
- (Post. etc. 15p any qty.)

## SINCLAIR, MINIATURE AMPLIFIERS & TUNER/DECODER

- | Model | Description                                      | Price |
|-------|--|-------|
| 4-300 | 0-3 watt 9 volt                                  | 1-75  |
| 104   | 1 watt 9 volt                                    | 3-10  |
| 304   | 3 watt 9 volt                                    | 3-95  |
| 855   | 3 watt 12 volt                                   | 4-10  |
| E1208 | 5 watt 12 volt                                   | 5-10  |
| 808   | 10 watt 24 volt                                  | 4-95  |
| 410   | 10 watt 28 volt                                  | 4-95  |
| E1206 | 30 watt 45 volt                                  | 9-95  |
| E1210 | 2 1/2 + 2 1/2 watts                              | 7-75  |
| RES50 | 5 watt IC mains operated Amplifier with controls | 6-30  |
| SAC14 | 7+7 watt Stereo with controls                    | 11-75 |
| SAC13 | 15 + 15 watt Stereo with controls                | 14-95 |

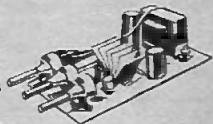

## POWER SUPPLIES FOR EVERY PURPOSE

- (All cases unless stated chassis)
- 470C 6 7/8 volt 300 mA (includes Multi-Adaptor for Tape Recorders, etc.) 2-15 post 20p
  - Car Lighter Voltage Adaptors 300mA (State voltage 6v, 7 1/2v, 9v) 1-95 ea. post 25p
  - SC202 3 6/7 1/8 volt 400mA 3-65 carr. 30p
  - HC244R Stabilised version 4-90 carr. 30p
  - P500 9 volt 500mA 3-20 post 20p
  - P11 24 volt 500mA (chassis) 2-90 post 20p
  - P15 26/28 volt 1 amp (chassis) 2-90 post 20p
  - P1080 12v 1 amp (chassis) 4-50 post 20p
  - P1081 45v 0-9 amp (chassis) 7-50 post 20p
  - P12 4-12 volt 0-4-1 amp 7-15 post 35p
  - SE101A 3/6/9/12 volt 1 amp (Stab.) 12-50 post 25p
  - RP104 6/7 1/2/9/12 1 amp (Stab.) 12-95 post 30p

## FIBRE OPTICS

0-01 Diam. Mono Filament £3-00 per 50 metre reel 0-13 Diam. 64 Fibres Sheathed, £1-00 per metre. SPRAYS 15mm Diam. (Mares Tail Spray £10-50 7mm. Diam. £5-00)



All types offered subject to availability. Prices correct at time of press E & OE. 10% VAT to be added to all orders. UK post etc. 15p per order unless stated.

# Henry's RADIO LIMITED

EDGWARE ROAD, LONDON W2

404-406 Electronic Components and Equipment 01-402 8381  
309 PA - Disco - Lighting High Power Sound 01-723 6963  
303 Bargains Store (Callers only)  
Home and Car Entertainment Centres London and branches now open  
120 Shaftesbury Avenue, London W1 01-437 9692  
144 Burnt Oak Broadway, Burnt Oak, Edgware 01-952 7402  
190-194 Station Road, Harrow, Middlesex 01-663 7788/9  
354-356 Edgware Road, London W2 01-402 5854/4736

All mail to  
303 Edgware Road,  
London W2 1BW  
All stores open 9 am to  
6 pm six days a week  
Hi-Fi - Tape Equipment  
Discount Stock List  
Free at all stores

# ELECTROVALUE

Present

## THIS MONTH'S SELECTION OF GUARANTEED-TO-SPECIFICATION COMPONENTS

Everything Brand New ★ Attractive Discounts ★ Free Postage (U.K.)

### TRANSISTORS

and semi-conductors of many types from simple diodes to ICS. photo-sensitive devices, threshold switches, etc. etc.

#### MINITRON DIGITAL INDICATORS

3015F Seven segment filament, compatible with standard logic modules, 0-9 and decimal point; 9mm characters in 16 lead DIL (some alphabetical symbols available) £1-20

Suitable BCD decoder driver 7447 £1-15

3015G showing + or - & 1 dec. pt. £1-20

### CAPACITORS

#### DALY ELECTROLYTIC

In cans, plastic sleeved  
1000mF/25V 22p 5000/25V 62p  
1000/50 41p 5000/50 £1-18  
2000/50 57p 5000/100 £2-91

#### POLYESTER TYPE C.280

Radial leads for P.C.B. mounting. Working voltage 250V d.c.

0-01, 0-015, 0-022, 0-033, 0-047 ea. 3p

0-068, 0-1, 0-15 ea. 4p

0-22, 5p; 0-33 7p; 0-47 8p; 0-68 11p; 1-0 14p;

1-5 21p; 2-2 24p

#### SILVERED MICA

Working voltage 500V d.c.

Values in pFs—2-2 to 820 in 32 stages ea. 6p

1000, 1500 7p; 1800 8p; 2200 10p; 2700, 3600 12p;

4700, 5000 15p; 6800 20p; 8200, 10 000 25p

#### TANTALUM BEAD

0-1, 0-22, 0-47, 1-0 mF/35V ea. 13p

2-2/16V, 2-2/35V, 4-7/16V, 10/6-3 ea. 13p

4-7/35V, 10/16V, 22/6-3V ea. 16p

10/25V, 22/16V, 47/6-3V 100/3V ea. 18p

#### POLYCARBONATE

Type B42540 Working Voltage—250V

Values in mF: 0-0047; 0-0068; 0-0082; 0-01; 0-012; 0-015 ea. 3p

0-018; 0-022; 0-027; 0-033; 0-039; 0-047; 0-056 ea. 4p

0-068; 0-082; 0-1

#### CERAMIC PLATE

Working voltage 50V d.c.

In 26 values from 22pf to 6800pf, each, 2p

### POTENTIOMETERS

#### ROTARY, CARBON TRACK. Double wipers

for good contact and long working life

P.20 SINGLE linear 100ohms to 4-7megohms, ea. 14p

P.20 SINGLE log. 1Kohms to 2-2megohms, ea. 14p

J.P.20 DUAL GANG lin. 4-7Kohms to 2-2megohms, ea. 48p

J.P.20 DUAL GANG log. 4-7Kohms to 2-2megohms, ea. 48p

J.P.20 DUAL GANG Log/antilog 10K, 22K, 47K, 1 megohm only ea. 48p

J.P.20 DUAL GANG antilog 10K only ea. 48p

2A DP mains switch for any of above 14p extra.

Decades of 10, 22 and 47 only available in ranges above.

Skeleton Carbon Presets Type PR, horizontal or vertical 6p each.

#### SLIDER

Linear or log, 4-7K to 1 meg. In all popular values

Eaculcheon plates, black, white or light grey, ea. 30p

Control knobs, blk/wh/red/yel/grn/blue/dk. grey/lt. grey ea. 7p

### JACKS AND PLUGS

#### Sockets

2-circuit unswitched S1/SS 12p

2-circuit /2 break contacts S1/BB 15p

3-circuit unswitched (Not GPO) S3/SSS 17p

3-circuit with 3 break contacts S3/BBB 20p

2 circuit with chrome nut and black/white/red/green or grey unswitched SS/SS 16p

with 2 break contacts S5/BB 20p

Miniature 3.5mm 2-circuit, (black) 2 br. cont S6/BB 9p

#### Plugs

2 circuit screened top entry P1 24p

slide entry SEP1 36p

Line socket mono 231 40p

Line socket stereo 244 45p

3 circuit unswitched, blk/grn/wh. P4 35p

2 circuit, unswitched, blk/wh/red/bl/grn/gy P2 18p

3 circuit screened top entry P3 53p

slide entry SEP3 55p

Miniature 3-5mm 2-circuit screened P5 13p

Min. 3-5mm 2-circ. unscrmd. various colours P6 10p

## EV CATALOGUE 2nd printing

112 pages, thousands of items; Illustrations; diagrams; much useful technical information. The 2nd printing of this catalogue has been updated as much as possible on prices. It costs only 25p post free and includes a refund voucher for 25p for spending when ordering goods list value £5 or more.

### INSULATED SCREW TERMINALS

In moulded polypropylene, with nickel plate on brass. With insulating set, washers, tag & nuts. 15A/250V in blk/brown/red/yel/grn/bl/gy/wh.

Type TP.1, ea. 14p

Suitable plugs Type TP4, 4mm each 7p

Type TP2, 2mm each 4p

### ZENER DIODES

Full range E24 values: 400mW: 2-TV to 33V, 14p each; 1W: 6-8V to 82V, 21p each; 1-5W: 4-7V to 75V, 48p each; 20W: 7-5V to 75V, 69p each. Clip to increase 1-5W rating to 3 watts (type 266F), 5p.

### RESISTORS

Code Watts Ohms 1 to 9 10 to 99 100 up

(see note below)

C 1/3 4-7-470K 1-3 1-1 0-3 nett

C 1/2 4-7-10M 1-3 1-1 0-3 nett

C 3/4 4-7-10M 1-5 1-2 0-32 nett

C 1 4-7-10M 3-2 2-5 1-92 nett

MO 1/2 10-1M 4 3-3 2-3 nett

WW 1 0-22-3-9 9 8 8

WW 3 1-10K 7 7 6

WW 7 1-10K 9 9 5

Codes:

C = carbon film, high stability, low noise.

MO = metal oxide, Electrofil TR5, ultra low noise.

WW = wire wound, Plessey.

Values: All E12 except C 1/2W, C 1/2W, and MO 1/2W.

E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.

E24: as E12 plus 11, 13, 18, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Tolerances:

5% except WW 10% ±0-05Ω under 10Ω and MO 1/2W 2%.

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.) Prices for 100 up in units of 100 only.

### VEROBOARD

Copper clad 0-1 matrix—2-5 x 3-75 Ins. 27p; 3-75 x 3-75 Ins.—30p; 2-5 x 5 Ins.—30p; 3-75 x 5 Ins.—33p.

Copper clad 0-15 In. matrix 2-5 x 3-75 Ins.—20p;

3-75 x 3-75 Ins.—30p; 2-5 x 5 Ins.—30p; 3-75 x 5 Ins.—36p.

Vero spot face cutter (any matrix) 48p.

0-040 pins (for 0-1 matrix) per 100—36p.

0-052 pins (for 0-15 matrix) per 100—36p.

### ELECTROLYTICS

Axial Lead	3V	6-3V	10V	16V	25V	40V	63V	100V
0-47	—	—	—	—	11p	—	11p	—
1-0	—	—	—	—	—	—	—	8p
2-2	—	—	—	—	11p	—	—	8p
4-7	—	—	—	11p	—	—	—	8p
10	—	—	—	—	—	8p	9p	8p
22	—	—	8p	—	—	—	—	8p
47	8p	—	8p	8p	8p	8p	8p	10p
100	9p	8p	8p	8p	9p	10p	12p	19p
220	8p	8p	9p	10p	11p	17p	28p	—
470	9p	10p	10p	11p	13p	17p	24p	45p
1,000	11p	13p	13p	17p	20p	25p	41p	—
2,200	15p	18p	23p	26p	37p	—	—	—
4,700	25p	30p	35p	44p	—	—	—	—
10,000	42p	46p	—	—	—	—	—	—

### KNOBES

In a great variety of modern types, for 1/8" shaft, from plastic to solid aluminium including pointer and numbered types.

### CONNECTORS

DIN from two way to 7 way plugs and sockets, phono types mains connections, etc. etc. Page 88 in Catalogue 7

### BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in "Wireless World." Simple to assemble, fantastically good results and a greater money saver. Carries 10 watts RMS, 15 ohms impedance. Size 18in x 12in x 10in. Complete kit, including pack-flat cabinet, £14-90.

The size and weight of this product obliges us to charge 70p part cost of carr. in U.K.

Equaliser Assembly, £2-30.

Loudspeaker Unit 59RM109, £2-45.

Cabinet Kit (to Baxandall design), £10-45.

Cross-over choke for additional bass unit in full kit above, £1-30.

## This is EV Service

### DISCOUNTS

Available on all items except those shown with NETT PRICES: 10% on orders from £5 to £14-99, 15% on orders £15 and over.

### PACKING AND POSTAGE FREE

In U.K. For pre-paid mail orders, except Baxandall. For order list value £2 and under there is an additional handling charge of 10p.

### GUARANTEE OF QUALITY

All goods are sold on the understanding that they conform to manufacturers' specifications and satisfaction is guaranteed as such—no rejects, 'seconds' or sub-standard merchandise is offered for sale.

### GIRO ACCOUNT No. 38/671/4002

Prices quoted do not include V.A.T., for which 10% must be added to total nett value of order. Every effort is made to ensure correctness of information and prices at time of going to press. Prices subject to alteration without notice.

All postal communications, mail orders etc. to Head Office at Egham address, S.A.E. with enquiries requiring answers.

## ELECTROVALUE LTD

28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB  
Telephone Egham 3603 Telex 264475 Shop hours 9-5.30 daily; Sat. 9-1 p.m.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA  
Telephone (061) 432 4945 Shop hours 9-1 p.m. 2-5.30 daily; Sat 9-1 p.m.

Please quote Dept. EE.6 when writing.

U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

# R T V C

# FOR AUDIO ON A BUDGET

## PUSH BUTTON<sup>(\*)</sup> CAR RADIO KIT



*The first time Motor magazine have nominated a push button car radio for their Top Ten Accessory Awards*



### NOW BUILD YOUR OWN AWARD WINNING PUSH BUTTON CAR RADIO

Technical specification:

- 1.) Output 2.5 watts R.M.S. into 8 ohms. For 12 volt operation on negative or positive earth.
  - 2.) Integrated circuit output stage, pre built three stage IF Module.
- Controls Volume, manual tuning and five push buttons for station selection, illuminated tuning scale covering full medium and long wave bands.  
Size Chassis 7 ins. wide, 2 ins. high and 4- $\frac{1}{8}$  ins. deep approx.

*NOTE:* The ability to solder on a printed circuitboard is necessary to complete this kit successfully. Circuit diagram and comprehensive instructions 55p free with kit.

#### Car Radio Kit

**£6.60 + 55p. postage & packing.**

Speaker including baffle and fixing strips

**£1.65 + 23p. postage & packing.**

Recommended Car Aerial - fully retractable and locking.  
**£1.35 post paid.**

## STEREO 21



## QUALITY SOUND<sup>(\*)</sup> FOR LESS THAN £19.00

Stereo 21 easy to assemble audio system kit, - no soldering required. Includes:-

- BSR 3 speed deck, automatic, manual facilities together with ceramic cartridge.
- Two speakers with cabinets.
- Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

For the technically minded:-

Specifications:

Input sensitivity 600mV; Aux. input sensitivity 120mV; Power output 2.7 watts per channel; Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs. Overall Dimensions, Speakers approx. 15 $\frac{1}{2}$ " x 8" x 4". Complete deck and cover in closed position approx. 15 $\frac{1}{2}$ " x 12" x 6". Complete only **£18.95**

Extras if required.

Optional Diamond Stylus **£1.37**

£1.60 p & p.

Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance. **£3.85.**



## DISCO AMPLIFIER

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Outputs 20 watts R.M.S. into 8 ohms (suitable for 15 ohms).

Inputs \*5 Electrically Mixed Inputs. \*3 Individual Mixing controls. \*Separate bass and treble controls common to all 5 inputs. \*Mixer employing F.E.T. (Field Effect Transistors). \*Solid State Circuitry. \*Attractive Styling.


#### INPUT SENSITIVITIES

1) Crystal Mic or Guitar 9mV. 2) Moving coil Mic or Guitar 8mV. 3). 4). 5) Medium output equipment (Gram. Tuner. Monitor. Organ, etc.) - all 250mV sensitivity.

AC Mains 240V. operation.  
Size approx. 12 $\frac{1}{2}$ " x 6 ins x 3 $\frac{1}{2}$ " ins  
**£15.00 + 60p.**

**postage & packing**

## DISCO 50

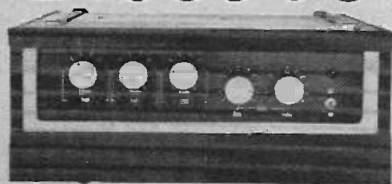


### 45 WATT R.M.S. MONO DISCOTHEQUE AMPLIFIER

Ideal for Disco Work. Output Power: 45 watts R.M.S. Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K. Size: 19 $\frac{1}{4}$ " x 10 $\frac{1}{2}$ " x 8ins. approx. Amplifier **£27.50 + £1.50 p. & p**

Special Offer: Disco 50 plus two 15" E.M.I. speakers type 14A/780 (as illustrated on opposite page). Complete **£57.00 + £4.00 p&p.**



# COMPLETE (\*) STEREO SYSTEM

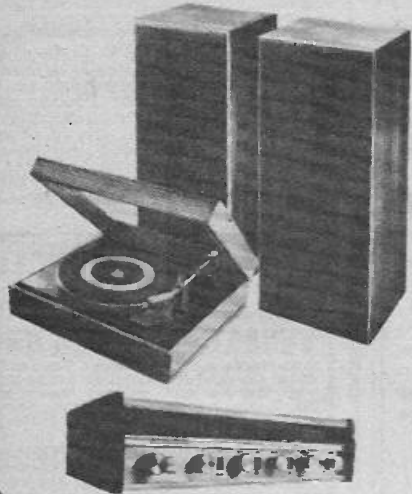

**£51.00**

**40 Watt Amplifier.**  
Viscount III - R102 now 20 watts per channel.  
System I includes:  
Viscount III amplifier - volume, bass, treble and balance controls, plus switches for mono/ stereo on/off function and bass and treble filters. Plus headphone socket.  
**Specification**  
20 watts per channel into 8 ohms.  
Total distortion @ 10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K. equalised within  $\pm 1$ dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power).  
Tape out facilities: headphone socket, power out 250mW per channel. *Tone controls and filter characteristics.* Bass:  $\pm 12$ dB to  $-17$ dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble  $\pm 12$ dB to  $-12$ dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max.)  $-58$ dB.  
Crosstalk better than 35dB on all inputs.  
Overload characteristics better than 26dB on all inputs. Size approx.  $13\frac{1}{2} \times 9 \times 3\frac{1}{2}$ ".  
Garrard SP25 deck, with magnetic cartridge, de luxe plinth and hinged cover.  
Two Duo Type II matched speakers - Enclosure size approx.  $17\frac{1}{2} \times 10\frac{1}{2} \times 6$ " in simulated teak. Drive unit  $13 \times 8$ " with parasitic tweeter

**Complete System £51.00**

**£69.00**

**System II**  
Viscount III amplifier (As System I)  
Garrard SP. 25 (As System I)  
Two Duo Type IIIA matched speakers - Enclosure size approx.  $31 \times 13 \times 11\frac{1}{2}$ ". Finished in teak veneer. Drive units approx.  $13\frac{1}{2} \times 8\frac{1}{2}$ " with 3" HF speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20kHz.

**Complete System £69.00**

**PRICES: SYSTEM 1**  
Viscount III R102 amplifier £24.20 + £1 p & p  
2 Duo Type II speakers £14.00 + £2.20 p & p  
Garrard SP25 with MAG. cartridge de luxe plinth and hinged cover £21.00 + £1.75 p & p  
**total £59.20**

**Available complete for only £51.00 + £3.50 p. & p.**

**PRICES: SYSTEM 2**  
Viscount R102 amplifier £24.20 + £1.00 p. & p.  
2 Duo Type IIIA speakers £39.00 + £4.00 p. & p.  
Garrard SP25 with MAG cartridge de luxe plinth and hinged cover £21.00 + £1.75 p. & p.  
**total £84.20**

**Available complete for only £69.00 + £4 p. & p.**

# EMI SPEAKERS AT FANTASTIC REDUCTIONS

**THE ULTIMATE COMPLETE SPEAKER SYSTEM**  
EMI LE 315 listed price **£86.00**



A professional standard five way speaker system with enclosure giving top quality performance.  
**Enclosure Dimensions**  
approx. (3ft. x 2ft. x 1ft.).  
**Drive Units**  
Hand built - 15" diameter bass with 3" voice coil, - two 5" diameter Mid Range units, - two 3 1/2" HF. units, plus matching crossover panel with two variable potentiometers for mid and high frequency adjustment.  
**Power Handling**  
Continuous rating 35 W rms. Peak power rating 70 W.  
**Frequency Response**  
20 Hz 20,000 Hz, Imp. 8 ohms.

**Our price £45.00 + £3.50 p. & p.**



**15" 14A/780 BASS UNIT**  
Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz. flux density 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3" voice coil.

**Recommended retail price £40.80, OUR PRICE £18.70 + £1.50 p & p + £1.50 p & p Special Offer.**



**950 KIT**

Five matched speakers and crossover unit for handling up to 45 watts, frequency response from 20 to 20,000 Hz. Huge 19" x 14" (approx.) high efficiency Bass-Speaker with 16,500-gauss magnet built on a heavy diecast frame. The four 10,000 gauss tweeters, each 3 1/2" dia. approx., are fed by the crossover which critically adjusts signal for maximum fidelity. Impedance at 1 kHz is 8 ohms. Bass coil 2", others 0.5". Recommended list price £44.00.

**OUR PRICE £19.50**



## BUILD YOUR OWN STEREO AMPLIFIER (\*)

For the man who wants to design his own stereo - here's your chance to start with Unisound - pre-amp, power amplifier and control panel. No soldering - just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

**£7.64 + 55p. p & p**



## 8 TRACK CARTRIDGE PLAYER (\*)

Elegant self selector push button player for use with your stereo system. Compatible with Viscount III system, Unisound module and the Stereo 21. Technical specification: Mains input, 240V. Output sensitivity 125mV. Comparable unit sold elsewhere at £24.00 approx.

**Yours for only £10.95 + 90p. p & p**



Just write your order giving your credit card number

**DO NOT SEND YOUR CARD**

● Mail orders to Acton. Terms C.W.O. All enquires Stamped Addressed Envelope. Goods not despatched outside U.K.

● Leaflets available for all items listed, thus (\*) Send stamped addressed envelope.



Radio and TV Components (Acton) Ltd.

**21 High Street, Acton, London W3 6NG /c**  
**323 Edgware Road, London W2**

Personal Shoppers — Edgware Road: 9a.m. - 5.30p.m. Half day Thurs.  
Acton: 9.30 a.m. - 5 p.m. Closed all day Wed.

**NO OVERSEAS ORDERS**

Everyday Electronics, June 1974

# Everyday Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 20p. extra. Semi-display—£6.00 per single column Inch. Advertisements must be prepaid and addressed to Classified Advertisement Department, "EVERYDAY ELECTRONICS," I.P.C. Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD.

## EDUCATIONAL

**CITY & GUILDS EXAMINATIONS.** Make sure you succeed with an ICS home study course for C & G Electrical Installations, Telecommunications, Technicians and Radio Amateurs. Free details from:—International Correspondence Schools, Dept. 731M, Intertext House, London SW8 4UJ.

**COLOUR TV SERVICING.** Make the most of the current boom. Learn the technique of servicing Colour & Mono TV sets through new home study courses, approved by leading manufacturers. Also radio and audio courses. Free details from:—International Correspondence Schools, Dept. 731M2, Intertext House London SW8 4UJ.

**TECHNICAL TRAINING.** Get the qualifications you need to succeed. Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering & Programming. Also self build radio kits. Free details from:—International Correspondence Schools, Dept. 731M3, Intertext House, London SW8 4UJ.

## FOR SALE

**TELEQUIPMENT OSCILLOSCOPE** S31R and handbook £55. Choules, 43 Ashbrook Road, Old Windsor, Berks. Windsor 62711.

## RECEIVERS and COMPONENTS

**COMPONENTS GALORE.** Pack of 500 mixed components manufacturers surplus plus once used. Pack includes Resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers etc. Send £1+10p p. and p. c.w.o. to CALEDONIAN COMPONENTS, Strathore Road, Thornton, Fife.

**SILICON TRANSISTORS.** Unmarked, untested, 25 for 35p. Silicon diodes, tested, unmarked, 50VP.1V 150MA, 30 for 35p. I. CIS 74 series untested, unmarked, 25 for 35p. Why not try a pack? 1 pack of each for 95p. Selected Semiconductors, 17 Coniston Way, Elm Park, Hornchurch, Essex.

**SPECIAL PACK** of components, 25 resistors, 10 diodes, 20 capacitors, all tested and guaranteed. Also contains 20 transistors, untested manufacturers rejects. Send 50p to Felectronics, 6 The Grassing, Carlisle.

**3 ASS. M.C. METERS** 2-5" £1-15 (27p).  
**WIRE ENDED NIBBS** 10—20p (10p).  
**COPPER CLAD FAX PANELS** 5 1/2" x 5 1/2" 0—45p c.p. 7 1/2" x 9" 0—£1-25 c.p.  
**T.V. CONVERGENCE PANELS** 2 x AC128, 3 slugged coils, 3 slide switches, 11 w.w. pots, 3 carbon presets, 2 ferrite chokes etc. £1-10 c.p.  
**WALUP AKS P** 100 ohms mica caps 85p c.p. Send 10p for lists of others plus panels etc. Refund on purchase.  
**7LB ASSORTED COMPONENTS** £1-65 c.p.  
**2LB ASSORTED PANELS** £1-65 c.p.  
**J. W. B. RADIO**  
2 Barnfield Crescent, Sale, Cheshire M23 1NL  
Postage in brackets Mail order only

**TUNBRIDGE WELLS.** components from Teleservice, 108 Camden Road, Tunbridge Wells, Kent. Telephone 31803.


## SERVICE SHEETS

**SERVICE SHEETS** for Televisions, Radios, Transistors, Record Players, Tape Recorders, etc., from 5p with free Fault-Finding Guide. Over 10,000 models available. S.A.E. enquiries. Catalogue 20p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 429066.

## MISCELLANEOUS

**BEGINNERS,** we exist for you. Instruction, components, constructional kits. Send S.A.E. to Electrolern, Lyburn Lodge, Nomansland, Wiltshire.

## LOUDSPEAKERS

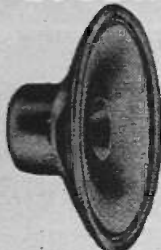

Speakers, kits and cabinets for D.I.Y., Hi Fi, P.A., Disco, etc. by EMI, Fane, Goodmans, Baker, Elac, Richard Allan, Wharfedale, etc. Send for free booklet "Choosing a speaker"

## WILMSLOW AUDIO

Dept. H. Swan Works, Bank Square, Wilmslow, Cheshire SK9 1HF  
Tel. Wilmslow 29599

**PRESSURE SWITCH PADS** size 8in x 2 1/2in. Suitable for your alarm systems. Price 90p each, plus postage and packing. Phelmetrics, 233 Seymour Grove, Manchester M16 9QS.

**RADIO & TELEVISION AERIAL BOOSTERS** £2-95p, five television valves 45p. 50p bargain transistor packs, bargain £1 resistor and capacitor packs. UHF-VHF televisions £7-50, carr. £1-50p. S.A.E. for 3 leaflets. ELECTRONIC MAIL ORDER (BURY) LTD., Bridge Street, Ramsbottom, Bury, Lancs.

## WIRE

H.C. Copper, P.V.C. Insulated 24 A.W.G. (0.2 m.m.2) in P.V.C. Colours Black, Yellow, Blue or White. Reels 8ozs £0-95; 1lb £1-80; 2lbs £3-50; 4lbs £8-75 including VAT and postage larger Reels available C.W.O.

**H. A. WAINWRIGHT & CO. LTD.,** 9A Farncombe Street, Farncombe, Godalming, Surrey.  
Tel: Godalming 23545.

**SUPERB INSTRUMENT** cases by Bazelli, manufactured from heavy duty PVC faced steel, choice of 70 types; send for free list: Bazelli Instrument Cases, Dept 24, St. Wilfrid's, Foundry Lane, Halton LA2 6LT, near Lancaster.

**AMAZING OFFER!** **ELECTRIC SOLDERING GUN** WITH BUILT IN TRANSFORMER

**UNIQUE SEE IN THE DARK LIGHT** **INSTANT HEAT** **ONLY £2-25 P&P25p**

A MUST FOR EVERY DIY MAN

This Soldering Gun is a MUST for D.I.Y. Men, Motorists, Mechanics, etc. A rugged, strong construction that will last a lifetime. Now you can do all those repairs that would normally cost you 5/6 at any electrical shop. Voltage 240 AC. 50c/s. LIMITED QUANTITY AVAILABLE. Similar model sells at £4-50. C.W.O. Immediate despatch. Refund if not delighted.

**V.G.S. INTERNATIONAL (SGE10)**  
Pickworth, Sleaford, Lincolnshire.

**CONSTRUCTION AIDS.** Screws, nuts, spacers, etc., in small quantities. Aluminium panels punched to spec, or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards—masters, negatives and boards, one-off or small numbers. Send 6p for list. **RAMAR CONSTRUCTOR SERVICES,** 29 Shelbourne Road, Stratford-on-Avon, Warks.

## 71B BARGAIN PARCELS

Hundreds of new resistors, capacitors, pots, switches. Also crystals, computer panels & loads of odds & ends. Only £1-65 (40p)

## VERSATILE POWER UNIT

Contains Mains Transformer, 2A Thermal Cut-out and Bridge Rect. Will give 1-7-10-5V output with 2 extra capacitors (provided). Ideal for Nick-Cad Battery Charger, 6V TTL supply, Cassette or Radio, etc. Brand new with Information 71p (20p).

## 3W TAPE AMPLIFIERS

Very sensitive 4 valve amplifier with tone & volume controls giving 3 watts into 3 ohms. Only £1-65 (40p); Also available in cabinet with 7 x 4" speaker and non-standard tape deck. Mains-operated, fully tested. £3 (£1 up to 200 miles, £1-20 over) Suitable cassette £1 (30p). Spare head 30p.

## FERRIC CHLORIDE

Anhydrous to mill-spec. 1lb 50p (20p) 3lb £1-20 (30p), 10lb £3-50 (60p).

**SURPLUS COMPONENTS:** 800 ass'd resistors £1 (20p); 300 capacitors all types £1 (30p); 25 10X crystals 75p (30p); 40 ass'd. pots £1 (30p). VAT NOT INCLUDED—ADD 10% TO TOTAL. Carr in brackets, small parts 4p. SAE list.

## GREENWELD ELECTRONICS [EE2]

24 Goodhart Way, West Wickham, Kent, BR4 0ES.  
Shops at 21 Deptford Broadway, SE8,  
Tel 01-492 2909 & 38 Lower Addiscombe Rd, Croydon.

**MINI MAINS TRANSFORMER** 30 x 30 x 37mm. Cool, quiet, British. Pri. 220/250V. Type MT3, 5-0-5V rms, 300mA, £1. MT7, 7-0-7V, 120mA, £1. VAT included. Use MT3 for 5V or 6V rectified d.c., MT7 for 9V or 18V. Circuits supplied. Mail order only, UK post 5p per order. Amatronic Ltd., 336 Selston Road, South Croydon, Surrey CR2 0DE.

## DON'T LOOK

unless you can resist the temptation to get these super 'attention-getters':

- ★ Pocket-sized **MAXI-VOLT** Blg 2inch Spark Generator (instant 15,000 volts). Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz. (85g.) send £1-35 for your Maxi-Volt now!
- ★ Unique **TRANSMITTER-RECEIVER** Kit. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send £5-90 for yours now!
- ★ **Psychedelic MINI-STROBE** Kit. Take a pocket-sized lightning storm to Disco's and parties. 'Brain-freeze' 'em with vari-speed stop-motion flashes. Includes super case too. Send £2-20 now! (All prices include V.A.T., packing, and postage.)

Send remittance to:  
**BOFFIN PROJECTS,**  
4 CUNLIFFE ROAD,  
STONELEIGH, EWELL, SURREY  
(Mail order U.K. only)  
Or for more details, send 20p for lists, plus free design project sheet.

**A BONANZA FOR CONSTRUCTORS—  
B. SUPPLIES OFFER**

CURLIES, 8ft., 3-core, 15p ea. 4-core, 20p ea. STRAIGHT Cords, 25ft., 4-core, 25p ea. DIODES, Silicon, CV7040 (OA 202), 3' leads 4 for 25p DIALS, (GPO Type), plastic face, metal mech. 30p ea. TRANSISTOR panels, type M4, comprising: 5 BCY34, 4 ACY 17, diodes, resistors & capacitors (for new equipment—rel. long leads) 50p ea. **INTRODUCTORY OFFER:** 1 of each above plus surprise item for £1-25; (offer ends 31-7-74) MONEY back guarantee—prices Inc. VAT and pp. ORDERS or SAE for complete list to:-

38, HEATHWOOD GARDENS SWANLEY  
KENT BR8 7HN

**INTER-LOCKING  
PLASTIC STORAGE DRAWERS**

NEARLY  
KITCHEN!  
TIPS!  
**DISCOUNT  
PRICES**




Newest, neatest system ever devised for storing small parts and components; resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. Build up any size cabinet for wall, bench or table top. **SINGLE UNITS** (5" 2 1/2") £1-75 Dozen. **DOUBLE UNITS** £3-00 Dozen. **TREBLE (3D)** £2-90 for 8. **DOUBLE TREBLE 2** drawers in one outer case (6D2) £4-25 for 8. **EXTRA LARGE SIZE (6D1)** £3-90 for 8. **PLUS QUANTITY DISCOUNTS!** Order £10 and over Deduct 5% in the £. Order £20 and over Deduct 7% in the £. Order £50 and over Deduct 10% in the £. Add 35p P. & P. to all orders under £10. Orders over £10 P/P/IC free.

Please add 10% VAT to total remittance  
(Dept. EE6), 124 CRICKLEWOOD BROADWAY, LONDON N.W.2  
01-450 4844.

**FLAIRLINE  
SUPPLIES**

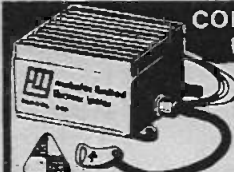**CONTACTLESS ELECTRONIC  
IGNITION BY MOBELEC**



**FROM ONLY £13-95 p&p 25p**

We break the price barrier with this trouble-free inductive discharge contactless ignition which replaces contact points by a solid-state trigger-head giving high energy spark for excellent cold-weather starting and super-smooth tick-over. Designed for 4 or 6 cylinder neg. earth cars at a price you can afford. Easy to fit, clear illustrated instructions, free fitting kit. State model, make and year. Other Mobelec capacitive discharge E series models available. Mobelec E series for high performance engines. 4 & 6 cylinder NEG. AND POS. EARTH. £22.82. 8 cyl. £24.75. Post free.

**SILHILL PRODUCTS**

Dept EE/6 226 Mary Street,  
Birmingham B12 9RJ. Tel:  
021-440 3600.

**MICROJET WELDER**



**A TINY FLAME UP TO 5000°F!**  
£13-25  
THE FLAME TIPS

Precision tool using combination of butane and compressed oxygen or micronox. A pencil lead thin flame size. Adjustable to 5,000°F. Cuts metals, welds, brazes and solders gold, silver. Ideal electricians, opticians, dentists, silversmiths, modellers, jewellery, clock-makers. Up to 40 minutes' use on fuel supplied. Replacement set of 2 micronox, 1 butane cylinder, £1.50 extra inc. post. Our Price £13-25 + 35p p. & p. Send £13.60.

**BINOCULAR MAGNIFIER**



See close-up work with less eye strain & fatigue. Lightweight adjustable headband. Powerful optically ground lenses from Continental glass-works. Can be worn over normal glasses. An essential aid in modelling, industry, home and work-aholic. Stamp collecting. Jewellers watchmakers and any fine work 2 1/2 x magnification. £6-65 + 40p. p. & p. x model 65p extra. State model.

**TWIN-BEAM SPEC-LAMP** — Worn just like a pair of spectacles. Two powerful spot lamps illuminate working area. Can be worn with Binocular Magnifier. Battery operated. Only £2-75 + 10p p. & p. send £2-85.  
**JOHN DUDLEY & CO. LTD.** (Dept. EE6), 301 Cricklewood Lane, London, NW2. Tel.: 01-458 5917. Callers welcome. Easy Parking.

**YATES ELECTRONICS  
(FLITWICK) LTD**

**DEPT. E.E., ELSTOW STORAGE DEPT.  
KEMPSTON HARDWICK,  
BEDFORD.**

**C.W.O. PLEASE. POST AND PACKING  
PLEASE ADD 10p TO ORDERS UNDER £2.**

Catalogue which contains data sheets for most of the components listed will be sent free on request. 10p stamp appreciated.

Callers Welcome Mon. to Sat. 9 a.m.-5 p.m.

**PLEASE ADD 10% VAT**

**RESISTORS**

1W Iskra high stability carbon film—very low noise—capless construction.  
1W Mullard CR25 carbon film—very small body size 7.5 x 2.5 mm.  
1W 2% ELECTROSIL TRS.

Power watts	Tolerance	Range	Values available	1-99	Price
1	5%	4-7Ω-2.2MΩ	E24	1-3p	1-1p
1	10%	3-3MΩ-10MΩ	E12	1-3p	1-1p
1	2%	10Ω-1MΩ	E24	3-5p	3-1p
1	10%	1Ω-3-9Ω	E12	1-3p	1-1p
1	5%	4-7Ω-1MΩ	E12	1-3p	1-1p
1	10%	1Ω-10Ω	E12	8p	7p

Quantity price applies for any selection. Ignore fractions on total order.

**DEVELOPMENT PACK**

0-5 watt 5% Iskra resistors 5 off each value 4-7Ω to 1MΩ.  
E12 pack 325 resistors £2-40. E24 pack 650 resistors £4-70.

**POTENTIOMETERS**

Carbon track 5kΩ to 2MΩ, log or linear (log 1/2W, 1in 1/2W).  
Single, 14p. Dual gang (stereo), 49p. Single D.P. switch 28p.

**SKELTON PRESET POTENTIOMETERS**

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C. mounting (0-1 matrix).  
Sub-miniature 0-1W, 5p each. Miniature 0-25W, 7p each.

**SMOKE AND COMBUSTIBLE GAS DETECTOR—GD1**

The GD1 is the world's first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector. Detector GD1 £2. Kit of parts for mains operated detector, including GD1 but excluding case £5-60. Suitable case £1-50. Kit of parts for 12 or 24V battery operation, including GD1 and PC Board £7-70. As above for PPG battery £6-90. Note: the battery operated kits incorporate our patented circuit to minimise battery drain—typically 90mA for 24V.

**PRINTED BOARD MARKER**

Draw the planned circuit onto a copper laminate board with the P.C. Pen allow to dry, and immerse the board in the etchant. On removal the circuit remains in high relief. 87p

**MULLARD POLYESTER CAPACITORS C206 SERIES**

160V: 0-01μF, 0-015μF, 0-022μF, 0-033μF, 0-047μF, 0-068μF, 3p. 0-1μF, 3 1/2p. 0-15μF, 4 1/2p. 0-22μF, 5p. 0-33μF, 6p. 0-47μF, 7 1/2p. 0-68μF, 11p. 1-0μF, 13p.

**MULLARD POLYESTER CAPACITORS C250 SERIES**

250V P.C. mounting: 0-01μF, 0-015μF, 0-022μF, 3p. 0-033μF, 0-047μF, 0-068μF, 3 1/2p. 0-1μF, 4p. 0-15μF, 0-22μF, 5p. 0-33μF, 6p. 0-47μF, 8 1/2p. 0-68μF, 11p. 1-0μF, 13p. 1-5μF, 20p. 2-2μF, 24p.

**MYLAR FILM CAPACITORS 100V: 0-001μF, CERAMIC DISC CAPACITORS**

0-002μF, 0-005μF, 0-01μF, 0-02μF, 3p. 0-04μF, 100μF to 10,000μF, 2p each. 0-05μF, 0-023μF, 0-1μF, 4p.

**ELECTROLYTIC CAPACITORS**

(μF) 1-63, 1-5/63, 2-2/63, 3-3/63, 4-7/63, 6-9/40, 6-8/63, 10/25, 10/63, 15/16, 15/40, 15/63, 22/10, 22/25, 22/63, 33-6/3, 33/16, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6-3, 68/16, 100/4, 100/10, 100/25, 150/6-3, 150/16, 220/6-3, 220/16, 330/4, 6p. 47/63, 100/40, 150/25, 220/25, 330/10, 470/6-3, 7p. 68/63, 150/40, 220/40, 330/16, 1000/4, 18p. 470/10, 680/6-3, 11p. 100/63, 150/63, 220/63, 1000/10, 12p. 470/25, 680/16, 1500/6-3, 13p. 470/40, 680/25, 1000/16, 1500/10, 2200/6-3, 18p. 330/63, 680/40, 1000/25, 1500/16, 2200/10, 3300/6-3, 4700/44, 21p.

**SOLID TANTALUM BEAD CAPACITORS**

0-1μF 35V	2-2F 35μV	22μF 16V	12p
0-22μF 35V	4-7F 35μV	33μF 10V	
0-47μF 35V	6-8F 25μV	47μF 6-3V	
1-0μF 35V	10F 25μV	100μF 3V	

**VEROBOARD**

0-1	0-15
2 1/2 x 3 1/2	24p
2 1/2 x 5	28p
3 1/2 x 3 1/2	28p
3 1/2 x 5	32p
17 x 2 1/2	85p
17 x 3 1/2	120p
17 x 3 1/2 (plain)	76p
17 x 2 1/2 (plain)	41p
2 1/2 x 5 (plain)	12p
2 1/2 x 3 1/2 (plain)	11p
Pin insertion tool	62p
Spot face cutter	52p
Pkt. 50 pins	20p

**JACK PLUGS AND SOCKETS**

Standard screened	28p	2-5mm Insulated	12p
Standard insulated	18p	3-5mm Insulated	12p
Stereo screened	48p	3-5mm screened	18p
Standard socket	28p	2-5mm socket	11p
Stereo socket	38p	3-5mm socket	11p

**D.I.N. PLUGS AND SOCKETS**

2 pin, 3 pin, 5 pin 1800, 5 pin 2400, 6 pin, 7 pin  
Plug 12p. Socket 8p.  
4 way screened cable, 25p/metre.  
6 way screened cable, 30p/metre.

**BATTERY ELIMINATOR**

9V mains power supply. Same size as PP9 battery. £1-79



# UNILEX MULLARD 4 WATT HI-FI AMPLIFIER FOR ONLY £1.60

Sensational "once in a lifetime offer" because Mullard over-produced—definitely not repeatable—our stocks (now over half sold) are cleared. HI-FI 4 transistor amplifier complete in case ready to use. Batt. car or mains operated—freq. range 50Hz-15KHz—distortion better than 2%. Comes complete with guarantee and data FREE to purchasers. Great handbook published by Mullard "tells all you need to know" to build your own stereo. Post and VAT 33p. Pair of speakers for same £3.80.

## EXPERIMENTER PRINTED CIRCUIT KIT BUILD 60 INTERESTING PROJECTS

CONTENTS: (1) 2 Copper Laminate Boards 4 1/2 in. x 2 1/2 in. (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resid. Solvent. (6) Etchant. (7) Cleanser/De-greaser. (8) 16-page Booklet Printed Circuit for Amateurs. (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit: (10) Essential Design Data Circuits: Cassin Plans, etc. for 60 TRANSISTORED PROJECTS. Circuits to suit everyone's requirements. Price £1. post paid.



### MINIATURE SEALED RELAY

American made. Our Ref. No. REL A1. Measures only 1/4" wide x 1/2" thick and 3/4" high and it's a double change over, we don't know the contact rating but estimate this at 3/5 amps. The coil resistance is 600 ohms and 9-12 volt will close it. Ideal for models and miniature equipment. It's a plug in relay but we supply complete with base. Price 36p each including base.




### MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PPI, PPS, PPA, PPF, PFG, PPH and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only £1.40, plus 20p postage.
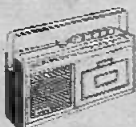
### THIS MONTH'S SNIP CASSETTE TAPE PLAYER

With remote control dynamic microphone. A really first class Japanese made battery operated tape recorder and player. Push button operated and with automatic level control of recording. Takes standard cassettes and has device which prevents pre-recorded cassettes being wiped clean or accidentally re-recorded. Separate jacks for the microphone which has motor stop/start switch and for recording from radio and for being powered by external mains unit. Nice tone and complete with batteries and carrying handle. A bargain at 29.95 plus 35p post etc.



ONLY £1 FOR 7 ELECTRIC MOTORS

7 Powerful battery motors as used in racing cars and power models. Output and types vary to make them suitable for hundreds of different projects—tools, toys, models, etc. All brand new, reversible and for 1 1/2 to 12 v. Bats. wiring diagrams included. Post and VAT 30p. FREE. Details of how to make miniature power station.

**J. BULL (ELECTRICAL) LTD.**  
(Dept. EE) 7 Park Street,  
Croydon CRO 1YD. Callers to:  
102/103 Tamworth Rd. Croydon

# INSTRUMENTAL AUDIO EFFECTS

SUPER "FUZZ" UNIT KIT. CONNECTS BETWEEN GUITAR & AMPLIFIER. OPERATES FROM 9v BATTERY (not supplied). ALL COMPONENTS AND PRINTED CIRCUIT BOARD WITH FULL INSTRUCTIONS. KIT PRICE: £2.88 post paid.

CREATE "PHASE" EFFECT ON YOUR RECORDS, TAPES ETC., UNIQUE CIRCUITRY ENABLES YOU TO CREATE PHASE EFFECT AT THE TURN OF A KNOB. OPERATES FROM 9v BATTERY (not supplied) COMPLETE KIT OF COMPONENTS WITH PRINTED CIRCUIT BOARD & FULL INSTRUCTIONS. KIT PRICE: £2.88 post paid.

MAIL ORDER ONLY.  
S.A.E. ALL ENQUIRIES.

## DABAR ELECTRONIC PRODUCTS

98a, LICHFIELD STREET,  
WALSALL, STAFFS. WS1 1UZ

# ELECTRONI-KIT

Electronic fun for all ages

THE MOST VERSATILE ELECTRONICS KITS.

All components are beautifully encapsulated in unbreakable transparent plastic blocks. Perfect connections are made WITHOUT SOLDERING, SCREWING OR WIRING.

INCREDIBLE VALUE. Build, dismantle and rebuild projects any number of times and invent your own experiments too.

COMPLETELY SAFE. Instructive and FUN - all kits operate from 9v. battery only.

VALUABLE MANUALS included with every kit.

No previous knowledge is required, even with the biggest kits.

Kit 2A-30 projects £10.25  
Radios, amplifiers, alarms, microphones, Morse, etc.

Kit 3A-100 projects £20.45  
AE 2A plus electronic birds, etc., electronic organs, metronome, guns, light and sound, burglar alarms, etc.

SAD-105 project: £25.25  
As 3A plus solar cell experiments and complete sophisticated control

PPS-1, etc.

ADD-150 projects: £35.95  
As 3ADX plus Relay and Meter experiments: ion concentration, volume, output, field intensity, volt., resistance meters, ammeter, illuminometer, etc. and many more.

ADD-ON parts and manuals available as required.

The three larger kits include Electrical experiments too.

All prices include Battery, VAT & p. & p.

Cheque/P.O. (or Sp. for Literature) to:

Satisfaction guaranteed

ELECTRONI-KIT LTD, 408 St. John's Street,  
London, EC1. [01-278 4579]

### SINCLAIR CALCULATORS

Cambridge Kit £19.95 (£22.25)  
Cambridge Assembled £21.95 (£25.50)  
Executive with Memory £34.95 (£37.75)  
New Sinclair Scientific £39.95 (£42.25)

### FERRANTI ZN414

IC radio chip with data £1.20 (23p). Also available kit of extra parts to complete a radio £2.39 (40p). Send see for free leaflet

### SINCLAIR PROJECT 80

AFU £8.95 (69p)  
Z40 £5.45 (54p)  
Z60 £6.95 (69p)  
Q16 £7.70 (77p)  
PZ5 £4.98 (49p)  
PZ6 £7.98 (79p)  
Z28 £7.98 (79p)  
Dacoder £7.45 (74p). Trans. for PZ8 £2.95 (50p).  
Tuner £11.95 (£11.19). Stereo 80 £11.95 (£11.19).  
Project 805 £26.95 (£26.69)  
2 x Z40/Stereo 80/PZ5 £25.00 (£25.00)  
2 x Z40/Stereo 80/PZ6 £27.75 (£27.77)  
2 x Z60/Stereo 80/PZ8/Transformer £33.11 (£33.11)  
Write for our most competitive quotation. We specialize in exporting Project 80 and charge only token postage on large airmail orders.  
Send see for free leaflet on new quadraphonic adapter for use with Project 80 £9.95 (£10.30)



### SINCLAIR SUPER IC12

6W rms power  
With 44 page booklet and printed circuit  
£2.10 (43p)



### DELUXE KIT FOR THE IC12

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1.60 (27p). Stereo model with balance control £3.60 (48p)

### IC12 POWER KIT

Supplies 28V 0.5 Amps £2.67 (50p)

### LOUDSPEAKERS FOR THE IC12

5" x 8 ohm £1.10 (27p). 5" x 8" 8 ohm £1.55 (37p)

### PREAMP KITS FOR THE IC12

Type 1 for magnetic pickups, mics and tuners. Mono model £1.35 (25p). Stereo model £2.40 (36p)  
Type 2 for ceramic or crystal pickups. Mono 65p (16p). Stereo £1.30 (25p)

SEND SAE FOR FREE LEAFLET ON KITS

### BATTERY ELIMINATOR BARGAIN

The most versatile battery eliminator ever offered. Switched output of 3, 4, 5, 7, 9 and 12V at 500 mA. £4.15 (70p)



### Other eliminators stocked:

50mA:—6V £1.80 (30p). 9V £1.60 (30p). 7.5V cassette type £2.25 (30p). Double 6 + 6V £2.50 (35p). 9 + 9V £2.50 (35p)  
500mA:—Higher current deluxe models. 6.7 & 9V (state which) £2.85 (50p).

### S-DECS AND T-DECS

S-DEC £1.98 (31p)  
T-DEC £3.63 (47p)  
H-DEC A £3.99 (51p)  
H-DEC B £6.99 (81p)



### IC carriers:

16 pin dill.—plain 81p (15p). With socket £1.77 (25p)  
10 TO5.—plain 78p (15p). With socket £1.68 (24p)  
Experiment outlets:—A £1.50 (26p), B £1.77 (29p), C 80p (15p), D £2.40 (35p), E £4.20 (53p)

### ZIPPY CABINETS

Attractive plastic instrument cases in 4 sizes. 80 x 50 x 30mm 60p (25p). 115 x 65 x 40mm 87p (30p). 155 x 90 x 50mm £1.20 (35p). 210 x 125 x 70mm £1.80 (45p).

### ECONOMICAL QUADRAPHONICS

£3.95 (£1.30)  
Complete self contained matrix quadraphonic synthesizer in attractive cabinet. Just feed output of ordinary stereo hi-fi into it and hook up to 4 speakers to obtain the latest experience in sound. Send see for free leaflet.

### SWANLEY ELECTRONICS

P.O. Box 68, Swanley, Kent BR8 8TQ

Please add the sum shown in brackets after the price to cover the cost of post and VAT. Official credit orders from schools, etc. welcome. No VAT charged on overseas orders.

# FREE!

## Over 150 ways to engineer a better future

**HIGHER PAY**      **A BETTER JOB**  
**SECURITY**

### find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

#### Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".— Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.


"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold"—Student C.C.P., Bucks.

#### FIND OUT FOR YOURSELF

These letters—and there are many more on file at Aldermaston Court—speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T. Dept. BEE01, Aldermaston Court, Reading RG7 4PF.

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.** Everything you need to know

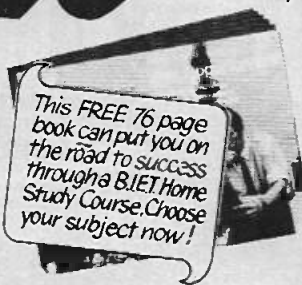about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.



**CUT OUT THIS COUPON**

Tick or state subject of interest. Post to address below.

<input type="checkbox"/> MECHANICAL Society of Engineers—A.M.S.E. (Mech.) <input type="checkbox"/> Institute of Engineers & Technicians (A.M.I.E.) <input type="checkbox"/> CITY & GUILDS Gen. Mech. Eng. <input type="checkbox"/> Maintenance Eng. <input type="checkbox"/> Welding <input type="checkbox"/> Gen. Diesel Eng. <input type="checkbox"/> Sheet Metal Work <input type="checkbox"/> Eng. Inspection <input type="checkbox"/> Eng. Metallurgy <input type="checkbox"/>	<input type="checkbox"/> DRAUGHTSMANSHIP Institute of Engineers <input type="checkbox"/> Designers (A.M.I.E.D.) <input type="checkbox"/> General Draughtsmanship <input type="checkbox"/> Elec. Draughtsmanship <input type="checkbox"/> Architectural Draughtsmanship <input type="checkbox"/> Technical Drawing <input type="checkbox"/>	<input type="checkbox"/> A.B.T. Clerk of Works <input type="checkbox"/> Construction Surveyors Institute—L.C.S.I. CITY & GUILDS General Building (all branches) <input type="checkbox"/> Heating & Vent. Inst. Clerk of Works <input type="checkbox"/> Site Surveying <input type="checkbox"/> Health Engineering <input type="checkbox"/> Road Construction <input type="checkbox"/> Quantities. <input type="checkbox"/> Estimates <input type="checkbox"/> Hydraulics <input type="checkbox"/> Structural Eng. <input type="checkbox"/>
<input type="checkbox"/> ELECTRICAL & ELECTRONIC Society of Engineers—A.M.S.E. (Elec.) <input type="checkbox"/> CITY & GUILDS Gen. Electrical Engineering <input type="checkbox"/> Electrical Installations <input type="checkbox"/> Electrical Maths <input type="checkbox"/> Computer Electronics <input type="checkbox"/> Electronic Eng. <input type="checkbox"/> Practical Radio & Electronics (with kit) <input type="checkbox"/>	<input type="checkbox"/> RADIO & TELE-COMMUNICATIONS CITY & GUILDS, Radio, TV/ Electronics <input type="checkbox"/> CITY & GUILDS Telecoms. <input type="checkbox"/> Gen. Radio & TV Eng. <input type="checkbox"/> Radio Amateurs Exam <input type="checkbox"/> Radio Servicing <input type="checkbox"/> TV Servicing <input type="checkbox"/> Colour TV <input type="checkbox"/>	<input type="checkbox"/> GENERAL Agricultural Eng. <input type="checkbox"/> Council of Eng. Institutions <input type="checkbox"/> Farm Science <input type="checkbox"/> Plastics <input type="checkbox"/>
<input type="checkbox"/> MANAGEMENT & PRODUCTION Institute of Cost & Management <input type="checkbox"/> Accrnts. <input type="checkbox"/> Computer Programming <input type="checkbox"/> Works M'nt. <input type="checkbox"/> Work Study <input type="checkbox"/> Gen. Production Eng. <input type="checkbox"/> Estimating & Planning <input type="checkbox"/> Storekeeping <input type="checkbox"/> Management Skills <input type="checkbox"/> Quality Control <input type="checkbox"/>	<input type="checkbox"/> AUTOMOBILE & AERONAUTICAL Institute of the Motor Industry <input type="checkbox"/> A.M.I. MAA/IMI <input type="checkbox"/> CITY & GUILDS Auto Eng. <input type="checkbox"/> Gen. Auto Eng. <input type="checkbox"/> Motor Mechanics <input type="checkbox"/> Auto Diesel Eng. <input type="checkbox"/> Garage M'nt. <input type="checkbox"/> ARB Aero Engineering Certs. <input type="checkbox"/> Gen. Aero Eng. <input type="checkbox"/>	<input type="checkbox"/> <b>G.C.E.</b> — choose from 58 'O' & 'A' level subjects.
		<input type="checkbox"/> <i>Supplementary courses for Nat. Certificates.</i>
		<input type="checkbox"/> <i>Coaching for many exams, including C &amp; G</i>

**POST TODAY FOR A BETTER TOMORROW**

To B.I.E.T., Dept. BEE01      QN  
Aldermaston Court, Reading RG7 4PF      BEE01

NAME \_\_\_\_\_  
Block Capitals Please  
ADDRESS \_\_\_\_\_

OTHER SUBJECTS \_\_\_\_\_      AGE \_\_\_\_\_

*Accredited by C.A.C.C. Member of A.B.C.C.*  
**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**

Published approximately the third Friday of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4 4AD. Printed in England by Index Printers Ltd., Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/Sia) Ltd. South Africa—Central News Agency Ltd. Publisher's Subscription Rate (including postage): For one year to any part of the world £2.95. Everyday Electronics is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.



# Henry's

**DON'T RELY ON YOUR MEMORY  
BUY NOW AT BARGAIN PRICES  
Hi Fi and Transistors - Up to date  
Brochures on request**

**HENRY'S CATALOGUE**  
Detailed price lists for general goods, Hi-Fi and Hi-Fi components and Hi-Fi accessories. A complete list of all the products available in our stores. Available for £1.00 (plus postage) or £2.00 (plus postage) for a 12-month subscription. Write to: Henry's, Dept. H, 364-366 Edgware Road, London W2 01-402 8791.

## BUILD THE TEXAN



You pay less  
VAT with Henry's  
Low Prices

Now built and used by thousands of satisfied customers. Features slim design overall size in cabinet 15 1/2" x 2 1/2" x 6 1/2". 6-IC's, 10 transistors, stabilisers Gardners low field transformer. Fibre Glass PC Panel, complete chassis work. Now available built and tested as well as in kit form. **HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES - DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE RELIABILITY AND EASE OF CONSTRUCTION FACILITIES.** On/off switch indicator, headphones socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector: Mag. P.U., Radio Tuner, Aux. Can be altered for Mic., Tape, Tape-head, etc. Constructional details Ref. No. 530p.

### 20 + 20 WATT IC STEREO AMPLIFIER



As featured by Practical Wireless 1972

Kit price **£28-50** (+VAT+50p carr/packing) or built and tested **£35-00** (+VAT + 50p carr/packing) as illustrated.

## BUILD THE NEW HENELEC STEREO FM TUNER

A completely new high stability stereo FM tuner. Features variable capacity diode tuning, stabiliser power supply, IC Decoder, high gain low noise IF stages. LED indicators. Tuning meter, AFC, easy to construct and use. Plain operated. Slim modern design with fibre glass PC, teak cabinet, etc. Available as a kit to build or ready built. Overall size 8" x 2 1/2" x 6 1/2". Produced to give high performance with a realistic price. (Parts list and constructional details Ref. No. 530p). Henry's are sole distributors UK and Europe.



Kit price **£21-00** (+VAT) or built and tested **£24-95** (+VAT)

**LIVING SOUND LOW NOISE TOP QUALITY CASSETTES MADE BY EMI TAPES LTD. TO INTERNATIONAL STANDARDS ESPECIALLY FOR HENRY'S. ALL POST PAID LESS THAN 1/2 REC. PRICES COMPLETE WITH LIBRARY CASES**

	3 for	6 for	10 for	25 for
C 60	£1-10	£1-98	£3-00	£7-40
C 90	£1-46	£2-80	£4-60	£11-25
C 120	£1-80	£3-45	£5-45	£13-45



Quantity and trade enquiries, invited  
**LEARN A LANGUAGE—complete with phrase book. German — French — Spanish — Italian £1-36 per course. £5 for any 4.**

## EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT

- DISCO MINI A complete portable disco, fitted mixer/preamp, 2 decks all facilities. **£98-50**
- As above but with Slider Controls **£118-50**
- 100 watt amplifier for above **£49-50**
- SDLS 100 watt mixer/amplifier with slider controls **£69-00**
- R50 50 watt mixer/amplifier **£49-50**
- R100 100 watt mixer/amplifier **£57-50**
- DISCO AMP 100 watt mixer/amplifier **£73-00**
- Northeast:
- 400 40 watt mixer/amp **£37-50**
- 800 80 watt mixer/amp **£45-00**
- DISCO MIXER/PREAMPLIFIERS (OP for up to 6-100 watt amplifiers)
- SDLI (rotary controls) **£49-50**
- SDLII (slider controls) **£58-50**
- DISCO VOX (slider controls) the complete disco preamp **£72-00**
- DJ100 100 watt power amplifier for above **£49-50**
- DJ30L Mk II 3 channel 3kw sound to light **£36-00**
- DJ30L Mk III slider controls **£45-50**
- DJ DISC LITE as 30L-2 plus variable speed flashes **£54-00**
- Carlboro Reverberation Unit **£44-00**
- Disc anti-feedback microphone **£11-95**
- Colt 150 watt liquid wheel projector **£23-50**
- 150 watt QI liquid wheel projector **£50-00**
- 150 watt QI cassette wheel projector **£50-00**
- Spare Effects and liquid cassettes large range of patterns **£6-00**
- 6 inch liquid wheels **£5-00**
- Various cassettes **£6-00**
- Mini spot bank fitted 3 lamps **£12-95**
- Auto Trilite (mini with flashers) **£17-00**
- Bubblemaker with liquid **£22-50**

Mixers/Mics/Speakers/Lighting  
U.K.'s largest range of Disc Lighting. **FREE STOCK LIST REF. No. 18 ON REQUEST.**  
**AKG / RESLO / DJ / CARLSBRO / EAGLE MICS., STANDS, MIXERS, CABINETS, CHASSIS AND COMPLETE SPEAKER SYSTEMS, MEGAPHONES, TURN-TABLES PUBLIC ADDRESS COMPONENTS.**



All prices carr. paid (UK) (VAT EXTRA)  
Barclaycard/Access call, write or phone your order 01-723-6963—easy terms for callers.

## EXCLUSIVE DECCA KELLY SPEAKERS



12 watt speaker Tweeter systems, 8" Bass/Mid/Bass and Melinex Domed HF radiator plus crossover £12-50 per pair of systems (carr./packg. 40p) or built into veneered cabinets, size 18 x 12 x 6 1/2" £19-50 pair (carr. £11)

## HI-FI TAPE EQUIPMENT



U.K.'s largest range with discounts and demonstrations for callers. Latest stock lists on request (Ref. No. 17). Phone 01-402-4736 for Barclay/Access Card. Direct orders and latest prices.

## TRANSISTORS/SEMI-CONDUCTORS

U.K.'s largest range for every application. Small quantity discounts. Also Trade, Export and Industrial enquiries invited. Latest stock list (Ref. No. 36) including valves on request.

## ELECTRONICS SUPPLIES

Specialists in electronics for more than 30 years. Trade and industry supplies—every type of component and equipment.



## NEW SINCLAIR PROJECT 80

- Stereo Pre-Amplifier **£11-95**
- Audio Filter Unit **£6-95**
- Z40 15 Watt Amplifier **£5-45**
- Z60 25 Watt Amplifier **£6-95**
- PZ5 Mod. for 1 or 2 Z40 **£4-98**
- PZ6 Mod. (S Tab) 1 or 2 Z40 **£7-98**
- PZ8 Mod. (S Tab) 1 or 2 Z60 **£7-98**
- TRANSFORMER FOR PZ8 **£3-95**

NEW FM TUNER **£11-95**  
STEREO DECODER **£7-45**

All items post paid.

## LOW COST HI-FI SPEAKERS

### SPECIAL OFFERS

- EMI 13" x 8"—full range speakers (post 20p each or 30p pair)
- \*150T-8 ohms Twin Cone 10 watt £2-20 each or £4-00 pair.
- \*450 10 watt C/o Twin Tweeters 3, 8 or 15 ohm £3-85 each
- EW 15 watt 8 ohms C/o Tweeter £5-25 each or £7-00 per pair
- 350 20 watt C/o Tweeters 8 or 15 ohms £7-80 each
- \* Polished wood cabinet £4-80 post 35p.



### 8 ohms full range (post 20p)

- FR4 4" 5 watt **£4-75**
- FR65 6 1/2" 10 watt **£6-30**
- FR8 8" 15 watt **£8-50**
- FR23 9 x 6" 15 watt **£8-40**
- BASS & MID RANGE—8 ohms (post 20p)
- AA12 5" 15 watt **£3-75**
- B110 5 1/2" 15 watt **£7-20**
- B200 5" 15 watt **£8-50**
- B139/2 13" x 8" 30 watt LF **£13-75**

### TWEETERS AND CROSSOVERS (post 20p)

- \*K2006 10 watt 8 or 15 ohms **£2-10**
- FHT6 15 watt 8 ohms **£3-35**
- K2011 30 watt 8 ohms **£4-80**
- T77 KEF **£5-50**
- Axcent 100 20 watt 8 ohms **£5-52**
- K4009 1kHz/5kHz C/o **£2-70**
- SN75 3kHz var. C/o **£3-10**

### SPEAKER KITS (carr. etc. 35p)

- 20-2 8" 30 watt **£24-50 pair**
- 20-3 40 watt **£35-95 pair**
- LINTON 2 20 watt **£18-30 pair**
- GLENDALE 3 30 watt **£32-95 pair**
- DOVEDALE 3 50 watt **£51-50 pair**
- KEF KK2 **£55-00 pair**
- KEF KK3 **£78-00 pair**

## BUILD YOURSELF A POCKET CALCULATOR

A complete kit, packaged in a polystyrene container and taking about 3 hours to assemble—that's the Sinclair Cambridge pocket calculator from Henry's. Some of the many features include interface chip, thick-film resistor pack, printed circuit board, electronic components pack. Size 4 1/2" long x 2" wide x 1 1/2" deep. Free of charge with the kit for the more advanced technologist is a 32-page booklet explaining how to calculate Logs. Tangents. Sines etc.

**£19-95** Also available assembled ready to use. **£22-50** + VAT. + VAT.



10% VAT to be added to all orders. Export supplied. Prices and descriptions correct at time of proof. Subject to change without notice. E & O.E. Like a permanent job at Henry's? Experienced and trainee salesmen required. Tel. 01-402 8791. See page 346 of this magazine

**Henry's RADIO LIMITED**  
EDGWARE ROAD, LONDON W2

402-406 Electronic Components and Equipment 01-402 8381  
309 PA - Disco - Lighting High Power Sound 01-723 8963  
303 Bergains Store (Callers only)  
Home and Car Entertainment Centres London and branches now open.  
120 Shaftesbury Avenue, London W1 01-437 9682  
144 Burnt Oak Broadway, Burnt Oak, Edgware 01-952 7402  
190-194 Station Road, Harrow, Middlesex 01-863 7788/9  
364-366 Edgware Road, London W2 01-402 5854/4736

All mail to 303 Edgware Road, London W2 18W  
All stores open 9 am to 6 pm six days a week  
Hi-Fi - Tape Equipment  
Discount Stock List  
Free at all stores