


www.hi-fiworld.co.uk

hi-fi

NOVEMBER 2000

No54

World

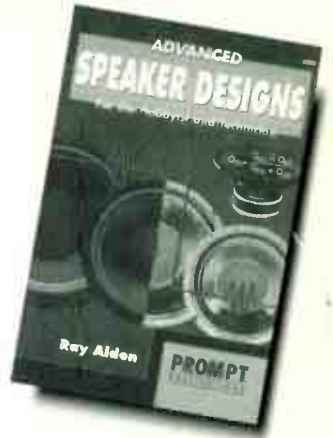

**THIS MONTH'S
BOOK REVIEW:**
*Advanced
Speaker Designs*
by Ray Alden



CLEAN AND FAST!



Plus:

● news, letters
and more...

Build a compact and sensitive loudspeaker

diy supplement/contents

No54



HI-FI WORLD
IMEX HOUSE,
THE PARK BUSINESS CENTRE,
KILBURN PARK ROAD,
LONDON, NW6 5LF

Web Site
www.hi-fiworld.co.uk
www.worldaudiodesign.co.uk

Subscriptions & Back Issues
9.30am - 2.30pm
+44 (0)1923 270833

Private & Trade Classified Ads
+44 (0)171 625 3134
Fax: +44 (0)171 328 1844

Contact Numbers
9am - 5pm Mon - Fri

Editor
Nick Lucas
+44 (0)171 625 8032
wad@hi-fiworld.co.uk

Sub Editor
Noel Keywood

Design & Production
Tyrone Taylor
+44 (0)171 625 3129
Fax: +44 (0)171 328 1844

Contributors
Richard White
Gary Devon

Photography
David Noble
+44 (0)171 625 3134

Sales and Marketing Manager
Amanda Sweeney
+44 (0)181 864 4760
Fax: +44 (0)181 864 4780

Accounts
Michael Ogazi
+44 (0)171 289 3533
Fax: +44 (0)171 328 1844

Credit Control
Louise Palfrey
+44 (0)1923 270833
Fax: +44 (0)1923 270833

Publisher
Noel Keywood

WORLD AUDIO DESIGN
Technical Manager
Nick Lucas
Tel/Fax: +44 (0)171 625 8032
wad@hi-fiworld.co.uk

Distributed by
Comag Magazine Marketing,
Tavisstock Road, West Drayton,
Middlesex UB7 7QE
Tel: +44 (0)1895 444 055

Printed by
Southernprint, Dorset.
Tel: +44 (0)1202 622 226

All unsolicited submissions are made at the owner's risk. We accept no responsibility for such submissions, nor do we undertake to return them.

No material may be reproduced from this magazine without the publisher's written permission.
© Audio Publishing Ltd

ALL RIGHTS to the designs are reserved by **World Audio Publishing Ltd**. They are published for single use by private individuals. They are not to be used for commercial gain without prior permission from **World Audio Publishing Ltd**.

World Audio Publishing Ltd accept no responsibility for accident or injury arising from the construction or use of any of the designs published. All of the projects in this supplement have gone through rigorous listening and test procedures. The performance and specification of these projects can only be guaranteed on kits bought directly from **World Audio Publishing Ltd**.

DIY NEWS

Micronas introduce an MP3 chip and electro-harmonix introduce a 300B **5**

CLEAN & FAST!

A compact loudspeaker that is fast but sensitive too, from Gary Hollands **7**

PHASE SPLITTERS - PART II

Designer Gary Devon looks at advanced Phase Splitters **13**

ADVANCED SPEAKER DESIGNS

Noel Keywood reviews a book on loudspeaker design **18**

LETTERS

Phono stage queries and KiT 88 tweaks **19**

ADVERTISERS' INDEX**22****NEXT MONTH**

Coming next month in DIY supplement No.55 is our new budget KEL84 Stereo Integrated Amplifier, featuring upfront the triode/pentode ECF80 followed by two EL84 power output valves per channel in push-pull (ultra linear) on the output, thumping out around 15 watts into an 8 ohm load. The KEL84 has a classic look and a small footprint. This simple kit is a must for all those readers itching to start DIY, on a budget.

Watford Valves

7 DAYS A WEEK 9AM - 9PM THE AUDIOPHILES CHOICE

All output valves multi-tested and digitally matched

Full no quibble guarantee. Expert advice on all valve amps

ECC81	Philips	5.00	GZ32	Harma	9.00
ECC82	Philips.	5.00	GZ32	Philips	25.00
ECC83	Philips	6.00	GZ34	Harma	8.00
ECC83	R.F.T	8.00	KT66	Harma	25.00
ECC83	Tungsrsm	15.00	KT66	GEC	80.00
ECC83	Mazda G	15.00	KT88	Sovtek	20.00
ECC83	Mazda S	18.00	KT88	Svetlana	34.00
ECC803S	Tesla.	20.00	2A3	Sovtek	18.00
E83CC	Siemens	25.00	5687WB	Philips	5.00
ECC85	R.F.T.	5.00	5881WXT	Sovtek	5.00
E88CC/6922	Harma	12.00	6550C	Svetlana	18.00
ECL86	Harma	6.50	6550WE	Sovtek	16.00
EF80	Mazda	6.00	6AU6WC	Philips	3.50
EF86	Tesla	12.00	6B4G	Sovtek	28.00
EL34WXT	Sovtek.	6.00	6C33C-B	Russian	28.00
EL34EH	Sovtek	10.00	6CG7	EI	8.00
EL34	Svetlana	8.50	6CG7	GE	14.00
EL34L	JJ/Tesla	8.50	6GK5	GE	7.00
EL84	Sovtek	4.50	6L6GC	Svetlana	12.00
EL84	Telefunken	35.00	6SL7GT	Sylvania	8.00
E84M	Russian	6.00	6SN7GT	Tungsol	18.00
EL84	Philips	15.00	7119	Amperex	12.00
PL519	Mullard	12.00	7199	G.E.	15.00
EL519	EI	12.00	12AX7LPS	Sovtek	8.00

QUAD II KT66 SPECIAL OFFER

Many satisfied customers have found the Harma KT66 offers performance equal to the GEC KT66 at a fraction of the cost. Each valve undergoes a high plate volt test and comes digitally matched on plate current and transconductance.

At only £25 each these KT66's really are an audio bargain and this month only, if you buy 4 pieces and mention Hi-Fi World, we will also supply 2 Harma GZ32s absolutely FREE.

Leaving you to simply enjoy the music!

For our full Harma range and testing, see our website:

www.watfordvalves.com

WATFORD VALVES 3 RYALL CLOSE,
BRICKET WOOD, ST ALBANS, HERTS AL2 3TS

Fast mail order/next day delivery/World Wide shipping
1000's more valves stocked. Prices exclude VAT and carriage.



01923 893270

Fax: 01923 679207

www.watfordvalves.com



Lockwood Audio

SPEAKER MANUFACTURERS'
SURPLUS DRIVERS

Examples:

25mm	Tweeters	Soft or Anodised
110mm	ICT;MF; Bass	
120mm	Bass/Mid	Shielded
135mm	Bass/Mid	
165mm	Mid;Bass/Mid	
172mm	Bass Long throw	
200mm	Bass;Mid/Bass*	
386mm	Bass	
Various	Ellipticals	
4/6/8/16 ohm	pressed/cast/moulded frames	

Crossovers: Termination Panels:Spikes & sockets etc.

*as used in HI FI WORLD Horn Enclosure !

AT A FRACTION OF ORIGINAL COST

Phone Fax email for details

Lockwood Audio

email: sales@lockwood-audio.co.uk

Unit 8, 724 Field End Road, Ruislip, Middlesex, HA4 0QP
Phone +44 (0)20 8864 8008 Fax: +44 (0)20 8864 3064
credit & debit cards welcome



BRITISH SUB BASS
OMP

100 WATT SUB BASS
Loudspeaker Amplifier
Panel. WWW.BKELEC.COM/SUB.HTM



Ideal for
building
Audiophile
and Home
Theatre
subwoofer
loudspeaker
Projects

FEATURES:- *100W R.M.S. into 8 ohm *High and Low Level Input *Toroidal Transformer *Short Circuit Protection *D.C. Speaker Protection *Frequency Roll Off, Lower 10Hz, Upper 60Hz to 240Hz(Fully Adjustable) *AC3 Compatible Filter can be by passed for 5-1 Formats. *Airtight Construction *Tens of Thousands of our panels already in use. *Complete with Leads
SPECIFICATION:*Power 100W RMS @ 8 ohms*F.Resp 10Hz-15KHz -3dB *Damping Factor >200 *Distortion 0.05% *S/N A Weighted >100dB *Supply 230V. A.C. *Weight 2.7Kg *Size H254 W254 D95mm

The above item may be ordered by post, fax, e-mail or phone and payment is welcome by cheque or credit card.PRICE: £117.44 + £5.00 P&P Incl VAT

B.K.ELECTRONICS
UNIT 1 COMET WAY
SOUTHEND-ON-SEA
ESSEX SS2 6TR

Web: <http://www.bkelec.com>
E-mail: Sales@bkelec.com
TEL: 01702-527572
FAX: 01702-420243



KIT & COMPONENT NEWS

MICRONAS INTRODUCE NEW MP3/AAC CHIP

Micronas, who claim to be the world leader in MP3 decoder ICs, recently announced a new decoder chip, the MAS3509F. Although not strictly for the D.I.Y. market, keep your eyes open, because this chip may well start to appear through specialist suppliers and electronic stores, especially on the internet.


Their MAS3507D, an MP3 flash-

point out that, in conjunction with their application board, the 3509 can interface SanDisk's Compactflash, Multimediacard and SD Card memory. By incorporating the SanDisk SD Card, the Micronas chip can handle SDMI compliant music from the major music groups. Hubertus von Janecek, marketing manager Advanced Audio for Micronas, said: "Micronas is

a range of SD Card AAC/MP3 players to the Far East market at the MAS2000 show. This technology has yet to reach Europe, even though Micronas is a Swiss/German company employing 1200 people and SanDisk are Californian. Fast acting DIYers could, with the new MAS3509 chip, beat the Japanese to it.

Gentlemen, man your soldering irons!

www.micronas.com

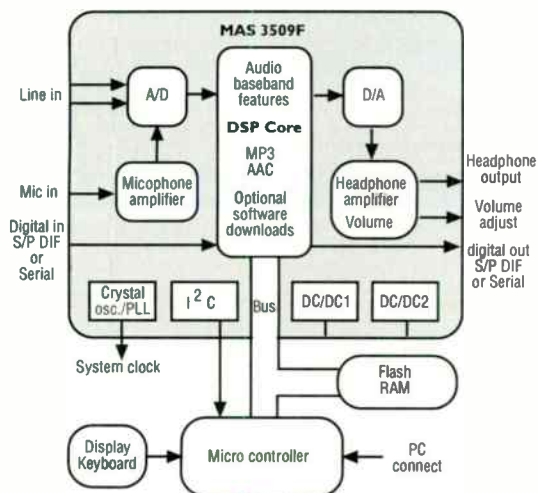

The new MAS 3509 chip from Micronas. There's a mic preamp so it can be used for voice recording and even S/P DIF (Sony/Philips Digital InterFace) for direct connection to CD players. Two DC/DC converters step up battery volts to supply external chips. Flash RAM in the form of SD Card, Multimediacard or CompactFlash can be addressed. The DSP core can decode AAC as well as MP3 and will accept software download. The extras needed to make a player are also shown here.

player chip released in 1997, contributed to a world-wide revolution in MP3 by allowing companies to build players cheaply and quickly. Micronas claim to have sold no fewer than 2 million 3507s. One found its way to Japanese constructor Takeshi Akamatsu (<http://elm-chan.org/>) who has posted up a DIY feature giving details on how to build a player (see - http://www.2s.biglobe.ne.jp/~elm/reports/mpc/report_e.html).

The new 3509 chip adds AAC decoding to the MP3 capability of the earlier 3507. Micronas interestingly

gearing its MAS 3509F application board for future trends in digital audio. One of those trends in digital audio players is the increased usage of the MultiMediaCard and SD Card for memory. Not only do these cards make possible the design of tiny systems, but the SD Card also enables downloading and listening to music under a secured environment. SanDisk cards are rapidly gaining industry wide acceptance in music applications."

As Hi-Fi World reported last month, Panasonic recently introduced

NEW TUBES FROM ELECTRO-HARMONIX

Electro-Harmonix have a new 300B EH that they claim perfectly matches the a.c. and d.c. characteristics of Western Electric's original, so it can be substituted directly, without circuit modification. The 300B EH has a 40W plate dissipation and is directly heated (i.e. no cathode), like the original.

www.ehx.com



Ansar Supersound Polypropylene Axial Capacitor



Audio specific. For transparent & detailed sound with EXTREMELY low distortion. High purity imported metalised polypropylene Tol 5%

Part no	Description	L x 0 mm	Price
CPW100N	Ansar 100nF 630V	32 x 6.5	1.60
CPW150N	Ansar 150nF 630V	32 x 7.5	1.60
CPW200N	Ansar 220nF 630V	32 x 9.0	1.60
CPW330N	Ansar 330nF 400V	32 x 8.0	1.60
CPW470N	Ansar 470nF 400V	32 x 9.0	1.80
CPW680N	Ansar 680nF 400V	32 x 10.5	1.80
CPW1U0	Ansar 1uF 400V	32 x 12.5	1.80
CPW1U5	Ansar 1.5uF 400V	32 x 14.7	1.80
CPW2U2	Ansar 2.2uF 400V	43 x 14.8	1.80
CPW3U3	Ansar 3.3uF 400V	43 x 17.6	2.20
CPW4U7	Ansar 4.7uF 400V	43 x 20.7	2.50
CPW6U8	Ansar 6.8uF 400V	43 x 22.8	3.00
CPW8U0	Ansar 8uF 400V	43 x 26.5	4.00
CPW10U	Ansar 10uF 400V	43 x 29.5	4.00
CPW15U	Ansar 15uF 400V	55 x 34.1	5.50
CPW22U	Ansar 22uF 400V	55 x 39.3	7.00
CPW25U	Ansar 25uF 400V	55 x 42.0	7.50
CPW30U	Ansar 30uF 400V	55 x 44.7	8.50
CPW50U	Ansar 50uF 400V	83 x 46.0	11.50
CPW60U	Ansar 60uF 400V	83 x 51.7	13.50
CPW75U	Ansar 75uF 400V	83 x 55.1	19.00
CPW80U	Ansar 80uF 400V	83 x 56.8	19.50
CPW100U	Ansar 100uF 400V	115 x 55.1	20.00
CPW125U	Ansar 125uF 400V	115 x 60.9	26.00

Dual Polypropylene Smoothing Capacitors

To replace old electrolytics or for new designs. Wire tails.

Part no	Description	L x 0 mm	Price
CPW1616	Propyl 16x16 400V	100 x 50	25.00
CPW3232	Propyl 32x32 400V	115 x 61	30.00

Philips Polypropylene Axial 1%

Blue coated Film & Foil. Epoxy coated, low inductance metal foil & film. Supremely stable. Tolerance 1%

Part no	Description	Price
CPW47P	Propax 47pF 630V	0.40
CPW100P	Propax 100pF 630V	0.40
CPW150P	Propax 150pF 630V	0.35
CPW220P	Propax 220pF 630V	0.35
CPW330P	Propax 330pF 630V	0.35
CPW470P	Propax 470pF 630V	0.35
CPW680P	Propax 680pF 630V	0.35
CPW1N	Propax 1nF 400V	0.45

Part No	Description	Price
CPP1N5	Propax 1.5nF 250V	0.45
CPP2N2	Propax 2.2nF 250V	0.45
CPP3N3	Propax 3.3nF 250V	0.45
CPP4N7	Propax 4.7nF 160V	0.50
CPP6N8	Propax 6.8nF 160V	0.50
CPP10N	Propax 10nF 63V	0.65
CPP22N	Propax 22nF 63V	0.75
CPP33N	Propax 33nF 63V	1.10
CPP47N	Propax 47nF 63V	1.30

Audio Electrolytics Radial

105 deg C +PLUS+ low impedance. These superior electrolytics offer a low impedance path to the signal, resulting in a very open & detailed sound. The use of high temperature materials ensure that these capacitors enjoy a long & stable life.

Part no	Description	Price
1Y150	Lo Imp Hi Temp 1uF 50V	0.25
2U2Y50	Lo Imp Hi Temp 2.2uF 50V	0.25
4U7Y100	Lo Imp Hi Temp 4.7uF 100V	0.25
10Y63	Lo Imp Hi Temp 10uF 63V	0.25
22Y63	Lo Imp Hi Temp 22uF 63V	0.30
47Y63	Lo Imp Hi Temp 47uF 63V	0.35
100Y63	Lo Imp Hi Temp 100uF 63V	0.50
220Y50	Lo Imp Hi Temp 220uF 63V	0.75
470Y63	Lo Imp Hi Temp 470uF 63V	1.25
1000Y35	Lo Imp Hi Temp 1000uF 35V	1.50
2200Y50	Lo Imp Hi Temp 2200uF 50V	2.25
4700Y25	Lo Imp Hi Temp 4700uF 25V	2.50

Trobo High Ripple Reservoirs

Excellent for Audio. Long life. High reliability 100VDC caps with screw terminals

Part no	uF/Voltage	Price
10000C100	10000uF 100V	20.00
22000C100	22000uF 100V	30.00

Alcap Bipolar Electrolytics

Axial leads 50V Tol. 10% Primarily for use in speaker crossovers.

Part no	Description	Price
CAB1	Alcap 1uF	0.25
CAB2U2	Alcap 2.2 uF	0.40
CAB3U3	Alcap 3.3uF	0.40
CAB4	Alcap 4uF	0.40
CAB5	Alcap 5uF	0.40
CAB6U8	Alcap 6.8uF	0.50
CAB8	Alcap 8uF	0.50
CAB10	Alcap 10uF	0.50
CAB16	Alcap 16uF	0.65
CAB20	Alcap 20uF	0.65
CAB25	Alcap 25uF	0.65
CAB35	Alcap 35uF	0.65
CAB50	Alcap 50uF	0.75
CAB60	Alcap 60uF	0.85
CAB80	Alcap 80uF	1.00
CAB100	Alcap 100uF	1.10

Monacor Air Cored Inductors.



A range of professional air cored inductors for 80 or 40 crossovers/filters for use up to 300W. 1.2mm enamelled copper wire wound on air spaced plastic bobbins.

Part No	Specification	Price
P15	150uH 0.150 8x19mm	£2.00
P22	220uH 0.150 8x19mm	£2.50
P33	330uH 0.20 8x19mm	£3.00
P47	470uH 0.250 50x19mm	£3.50
P68	680uH 0.350 59x19mm	£4.50
P100	1mH 0.40 59x19mm	£5.50
P150	1.5mH 0.50 70x30mm	£6.50
P220	2.2mH 0.60 70x30mm	£8.00
P330	3.3mH 0.750 70x30	£10.00

Monacor Ferrite Inductors



A range of professional high efficiency ferrite cored inductors with very low ohmic losses for 80 or 40 crossovers or filters for use up to 400W. 1.4mm enamelled copper wire (1.3mm on F1000) wound on plastic bobbin.

Part No.	Specification	Price
F220	2.2mH 0.150 400W 55x31mm	£6.50
F330	3.3mH 0.20 330W 65x39mm	£9.50
F470	4.7mH 0.250 140W 65x39mm	£12.00
F680	6.8mH 0.350 120W 65x39mm	£12.00
F1000	10mH 0.450 100W 65x39mm	£13.50

High Quality Valves

Part No.	Description	Price
6550C	OUTPUT VALVE	£26.00
6L6GT	OUTPUT VALVE	£4.50

Part No.	Description	Price
6SN7GT	OUTPUT VALVE	£4.50
6V6GT	OUTPUT VALVE	£3.95
ECC81	TRIODE	£4.50
ECC82	TRIODE	£4.50
ECC83	TRIODE	£4.50
EF86	LOW NOISE PENTODE	£9.90
EL34	OUTPUT VALVE	£8.50
EL84	OUTPUT VALVE	£3.50
G234	RECTIFIER	£6.50
KT88	OUTPUT VALVE	£20.00

Valve Holders - High Quality Valve Bases. Chassis Mounting With Screw Fittings.

Part No.	Description	Price
B9AC	B9A VALVE HOLDER CERAMIC	£1.50
B9AG	B9 VALVE HOLDER PORCELAIN PLUS GOLD PLATED PINS	£3.00
OCTC	OCTAL VALVE HOLDER CERAMIC	£2.00
OCTG	OCTAL VALVE HOLDER PORCELAIN PLUS GOLD PLATED PINS	£4.00

Fully Gold Plated Phono (RCA) Plugs with spring coil cable grip.



Part No.	Description	Price
PPG5A2	PAIR GOLD PLUGS for up to 5mm CABLE	£1.50 pair
PPG8A2	PAIR GOLD PLUGS for up to 8mm CABLE	£1.50 pair

Very High Quality Phono (RCA) Plugs



Very high quality satin grey metal with heavy gold plated connectors. Top collet cable grip & PTFE insulators. Very low noise.

Part No.	Description	Price
PPG8H2	GOLD PTFE PLUGS for up to 6mm CABLE	£3.50 pair
PPG8H2	GOLD PTFE PLUGS for up to 8mm CABLE	£3.50 pair

Extra High Quality Gold Plated Phono Oxygen Free (RCA) Leads (pairs)



Highly flexible oxygen free cable with extra moulded-in control / grounding wire.

Part No.	Length/Colour	Price
LPP1QG	0.8 Metres/Green	£5.50
LPP2QG	1.5 Metres/Green	£6.50
LPP5QG	5 Metres/Green	£11.00

Bas Reflex Tuning Ports



A range of adjustable plastic ports for use in various sizes of loudspeaker cabinets. d=diameter L=adjustable length (mm)

Part No.	Dimensions	Price
R35	d=35L=110-210	£2.50
R50	d=50L=150-280	£3.00
R70	d=70L=128-245	£3.50
R100	d=100L=160-122	£5.50
R85	d=85 angled 45° for narrow cabinetL=210-310	£6.50

High Quality Components at the right price. Please add £3.00 carriage + VAT to all orders. Credit Card phone orders accepted.

Cricklewood Electronics Ltd, 40 & 42 Cricklewood Broadway, London NW2 3ET. Tel: 0208 452 0161 Fax: 0208 208 1441



Vacuum Tubes for Audio Are Back!

Glass Audio brings together yesterday's tube with today's improved components, voltage control, and the exciting new Soviet tubes, to make smooth sound in your livingroom possible again!

YES!

Please send my first issue of *Glass Audio*. I'll pay just \$45.00 for six issues (1 year); \$80.00 for 12 issues (2 years) of the best information on tubes to be found anywhere. I understand that my satisfaction is guaranteed!

Name _____

Street & Number _____

City _____ Postal Code _____

Country _____

REMIT IN US \$ DRAWN ON A US BANK ONLY. PRICE GOOD THROUGH DECEMBER 31, 1995.

We Accept MC/VISA.

Glass Audio

PO Box 176, Dept. HFWS, Peterborough, NH 03458-0176 USA
Phone: (603) 924-9464 or FAX 24 hours a day (603) 924-9467

CLEAN & FAST!

GARY HOLLAND DESIGNS A COMPACT, SENSITIVE NEAR-WALL LOUDSPEAKER THAT SUITS BOTH VALVE AND TRANSISTOR AMPLIFIERS.



With KLS-14 we set out to design a compact loudspeaker that will work happily in most environments and with all types of amplifiers. In particular, it must be suited to valve amplifiers.

Designing a loudspeaker to work with both valve and semiconductor amplifiers raises several extra considerations. The output impedance of valve amplifiers is higher and the output power lower than their semiconductor counterparts. Consequently, a loudspeaker designed for valve amps must first of all be sensitive, and secondly present a friendly load impedance with as little reactance as possible to minimise risk of audible coloration. Happily, there are no trade-offs here. Solid-state amplifiers also prefer a friendly load and give a better performance too, so it's a worthwhile design aim.

Good sensitivity and even load impedance are just two of the requirements for our loudspeaker design. The others are as follows:

- 1) Compact but with good bass extension.
- 2) Room friendly; can be used close to walls.
- 3) Sounds good with semiconductor amps and valve amps.
- 4) Straightforward to build.

A Butterworth alignment is usually considered optimal for bass rolloff, but a higher target Q of around 1 was chosen to give a peak in the bass response. This will give the loudspeaker's bass a touch of slam and it will still sound good working away from walls.

The next step is to find a bass unit that will work in the chosen cabinet. It has to be sensitive (powerful magnet and efficient motor) and well controlled in its working range, and also have electrical and mechanical parameters suitable for closed box workings different to reflex working. These include a long voice coil travel because, unlike reflex loading, coil excursion in a sealed box design increases at system resonance. A higher Q unit is also needed for closed box systems to prevent over-


damping the bass.

The first decision to make is what type of cabinet system should be used, reflex or sealed box? While reflex designs offer deep bass, they can suffer with pipe resonances that extend right up into the midrange. This spurious noise can be as much as -10 dB below the main output, adding noticeable coloration. The problem of port resonances can be overcome, but at the expense of greater complexity, this design must be as straight forward as possible. I also want to exploit the lucid midrange that is one of the great strengths of valve amplifiers. Bass extension for a closed box design is not a great problem as long as the right drive unit/box combination and alignment is chosen. For the optimum choice between compactness and bass extension I chose 20 litres for the cabinet volume.'

After some searching an 8 inch unit from Seas emerged. It has a doped paper cone with a low loss rubber surround mounted on a low resonance magnesium chassis. A large diameter


MEASURED PERFORMANCE

GRAPH 1

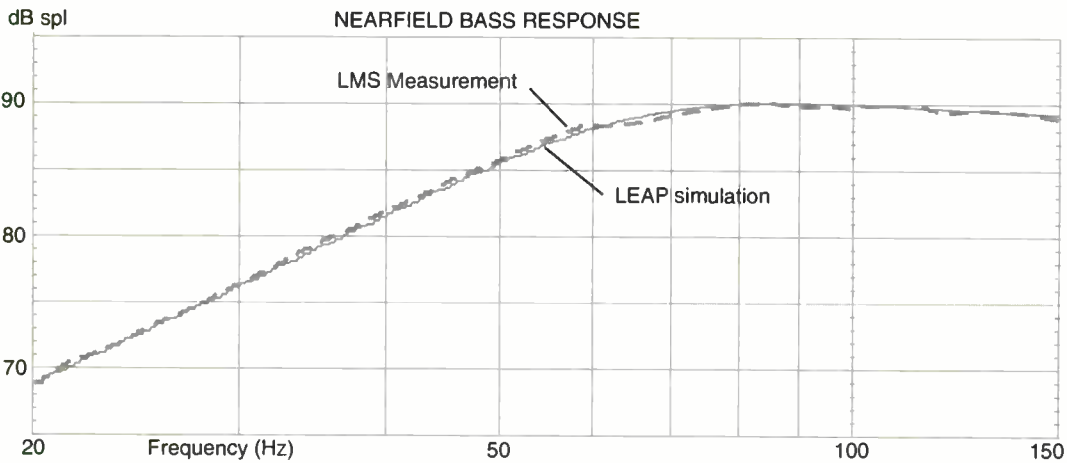


LEAP design software predicted a well damped bass response rolling off smoothly below 55Hz (-3dB). Nearfield measurement (LMS) showed real life response correlated perfectly. In use wall placement will lift bass level a little.

GRAPH 2

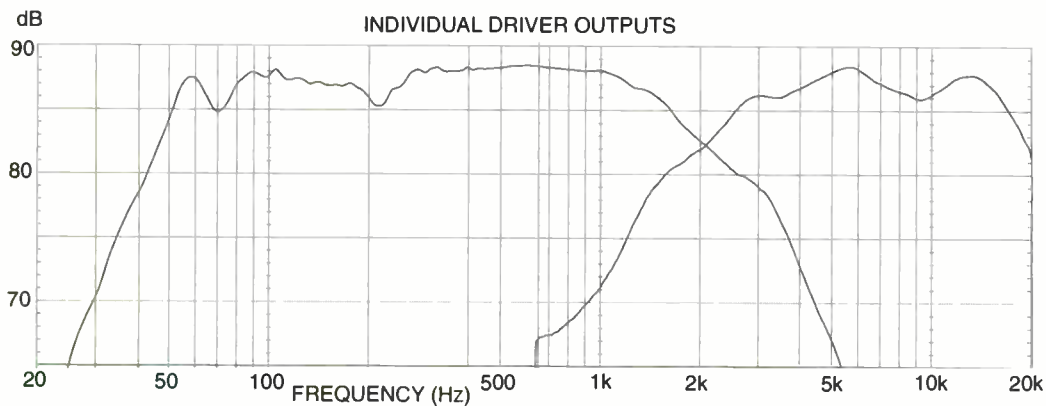


Measured at one metre the individual drivers roll in and out smoothly. It is important that there are no "throw ups" in the roll off region, to avoid colouration.

GRAPH 3

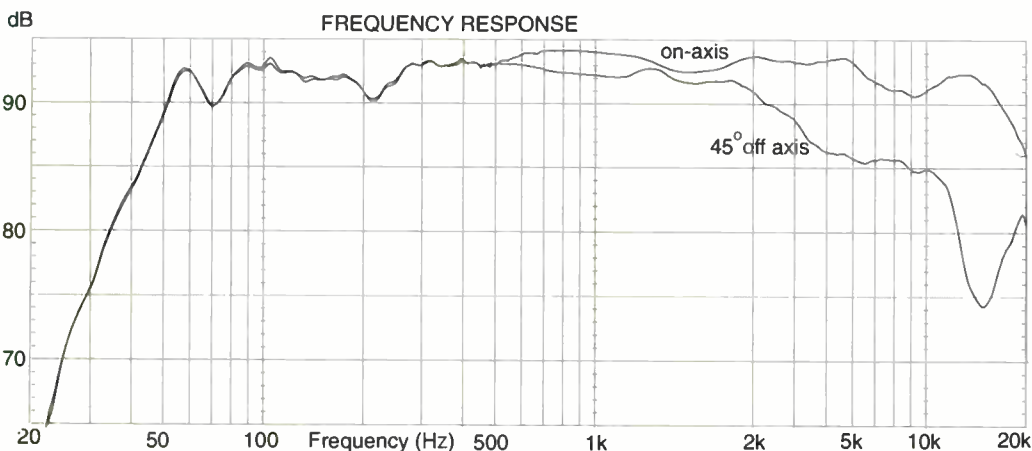

Overall frequency response of KLS-14 at one metre runs evenly from 55Hz up to 18kHz. Because the cabinet is "infinite baffle" bass rolls off less quickly than reflex, so low bass output is substantial for a compact cabinet. The horn tweeter rolls down above 2kHz, when measured off-axis.

GRAPH 4

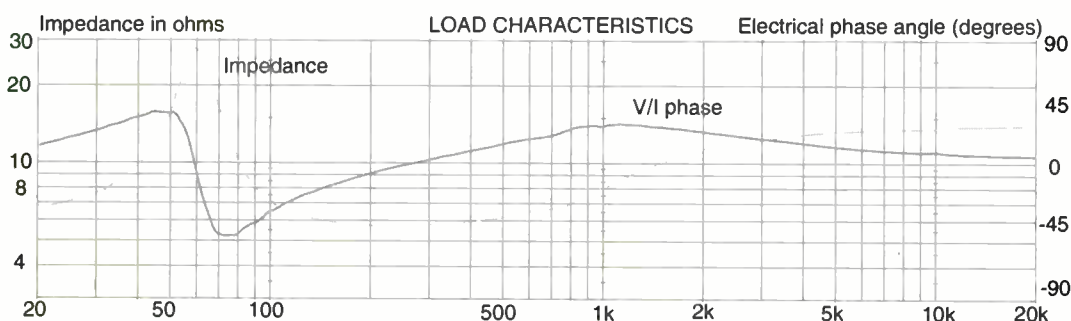

Impedance of KLS-14 is smooth, demonstrating low reactance (energy storage) and phase angles. The load is resistive where there is no rate of change of impedance (point of inflexion), as this twin trace shows.

PERFORMANCE FIGURES

Frequency response	50Hz - 18 kHz +/- 3dB
Sensitivity	89dB
Nominal impedance	8 ohms
Minimum impedance	5.75 ohms
crossover frequency	2.1 kHz
Rec. amp power	10 - 100 watts

The crossover region has a slight but fairly minor dip, this is due to the bass unit response dropping a little and then continuing its natural roll off. The treble unit takes over in the upper mid/lower treble region and runs quite smoothly up to 8 kHz, then dips a little. The 3dB resonant peak that existed has now been pulled down to the same level as the rest of the treble with the use of a Zobel network across the treble unit - see Graph 3 on p10.

The off-axis response (45degrees) shows the same on-axis trend until the tweeter cuts in. The increase in directivity caused by horn loading shows as falling response above 2 kHz. This means there will be less reflected energy from room walls, floor and ceiling, so conversely direct energy will be in greater proportion. Consequently the speaker will be more tolerant of nearby surfaces. The amount of treble energy in this case can be altered by merely adapting the angle of the speakers - see Graph 3 on p10.

Treble level will sound neutral with a valve amp. However, with brighter sounding semiconductor equipment there may be a need to lower the level, which may be adjusted by varying the value of the resistor R2 in the treble section. A value of 10 ohms sets the output at 88 dB. If the value is increased to 12 ohms the treble output is lowered by 1 dB to 87 dB. Dropping the value to 8.2 ohms increases output to 89 dB.

LOAD IMPEDANCE

As a load KLS-14 is reasonably friendly. The box/driver resonance shows up at 60 Hz with a Q of about 1.0. From here the impedance drops to just under 6 ohms in the mid range area. At around 500 Hz the impedance curve starts climbing and levels out to about 14 ohms in the treble region. Overall there are no dramatic changes for an amplifier to cope with, which means little reactance - see Graph 4 on p10.

CONCLUSION

Nearly all the design goals I set out at the beginning have been achieved in this design. Although the KLS-14 loudspeaker has been

conceived with valve amplifiers in mind, this design aims are equally suited to semiconductor amplifiers. The KLS-14 is easy to build and versatile, and will perform well with almost any amplifier in most normal environments with the minimum of fuss.

Gary Holland is a professional loudspeaker designer acting for companies worldwide.

Using industry standard techniques his work gives readers access to a professional design, as well as showing how commercial designers develop a modern loudspeaker, through theory and all-important measurement.

KLS-14 crossover components.

Bass unit	Seas CA21RE	x1
Treble unit	Vifa H26TG-35-06	x1
Wire	1mm stranded core	x1
Terminals	Bi-wire cup	x1
Wadding	Foam/long hair wool	
* All drive units/terminals to have gaskets *		

Inductors

1mH	0.3ohms DCR, 1mm wire	x1
0.3mH	1ohm DCR air core	x1

Capacitors

33mF	50v +/-5% DF 4%	x1
8.2mF	50v +/-5% DF 4%	x1
3.3mF	50v +/-5% DF 4%	x1

Resistors

10 R	10 watt	x1
6.8 R	7 watt	x2

KLS14 Speaker Kit is available as a kit from World Audio Publishing Ltd

	UK (inc. vat & p&p)	Overseas (exc. vat & p&p)
KLS14D Drive unit pack	£125.00	£107.00
KLS14C	£165.00	£140.00
(drive unit pack with crossover etc., but not the wood)		

Call or fax Nick Lucas on: + 00 44 (0) 1908 218836 (9am-5pm, Monday-Friday)
e-mail to: orders@worldaudiodesign.co.uk

For overseas freight charges, please call, fax or e-mail.

Falcon Acoustics Ltd

Falcon Electronics, Basically Sound

<http://www.falcon-acoustics.co.uk>

DRIVE UNITS: by FOCAL & Seas, and a pick of the best from other manufacturers.
100+ CROSSOVER NETWORKS: - Active & Passive, Components, Accessories, COMPONENTS

SOLENE Polypropylene capacitors. 0.1mFd. to 100mFd.

Polyester and Polycarbonate Film Capacitors. 0.1mFd. to 10mFd.

ALCAP Reversible Electrolytic Capacitors (Non-Polar); 50v, 100v & Low Loss. 2mfd. to 600mFd
FALCON Custom-wound Inductors.

FERRITE:- Standard, High Power, Super Power, Super Super Power + AIRCORED 0.56 -1.25mm wire
NEW IRON DUST. 1mm wire

TAPPED INDUCTORS:- 0-10mH in 1mH steps & 0-1mH in 0.1mH steps

AUDIO AMATEUR PUBLICATIONS

NEW- Valves for Audio Frequency Amplifiers from Philips Technical Library plus lots in P/L.

Back year sets of Speaker Builder, Audio Amateur & Glass Audio, plus the Audio Anthology Set.

Altogether 50+ books and 50+ Audio Amateur's magazine year sets. 1999 sets available



'State of the Art' Units & Kit Designs

C800 Mk II

82 litres

3 way floor standing

92 dB/watt system

-3dB point of 32Hz.

PolyKevlar 10" bass & 5" midrange

Titanium dioxide dome tweeter



From a wide range of High-Tech Loudspeaker units.

Unit Spec Booklet available 30p.

Please send A4 SAE with 40p stamp (66p with PL) +30p extra stamps.

SUPPLIERS TO THE TRADE SINCE 1972

Send for our FREE price list PL29: Just send a large S.A.E. (44p stamp) or US\$2 bill overseas.

Europe US\$1 bill or 3 International Reply Coupons (IRC) to:- (Dept HFW) Tabor House,
Norwich Road, MULBARTON, Norwich, Norfolk. NR14 8JT Tel (0)1508 578272

A MESSAGE.....

from the U.K.s Premier Valve-equipment Repair & Restoration Centre:

"IT DOESN'T MATTER whether your equipment is Old, New, in Kit form, Valve, Solid-state, Audio or R.F."

We...

Repair, Restore, Re-calibrate, Re-align:-
Tape recorders by *Revox, Tascam (up to 1")*, *Teac, Akai* ;
Valve amps., pre-amps., tuners, cinema amps.,
theatre-organ amps., industrial p.a. amps. from *Radford, Quad, Leak, Kalee, Clarke & Smith, Compton, Parmeko, RCA, Allotbass etc* ;
Valve Communications Receivers and Transmitters
(to 30 MHz/2kW/6'6 tall) by *KW, Marconi, Labgear, Eddystone, Redifon, Ajax, RCA, Tiger* and so on.

We will...

Build that Kit for you or
Re-build it if you've had a go but it's gone pear-shaped.

We will...

Custom-build for you a published Classic design or
Design something special and build the prototype
(A 250-watt AB2 high level modulator, Sir? No problems!!)

All this,

as well as being an Authorised Service Centre for such respected names of the Digital Era as *Denon, Pioneer, Kenwood, Yamaha*.

Overall, some pretty comprehensive facilities.... and it will take only a few minutes of your life plus a few pence from your pocket to call/fax and discuss your requirements: **0113 244 0378**

We are:


AUDIO LABORATORIES (LEEDS)

3 Kildare Terrace Industrial Estate,
Leeds LS12 1DB, England

Website: www.audiolabs.co.uk

NEW PRODUCTS FOR VALVE PRE AMPS

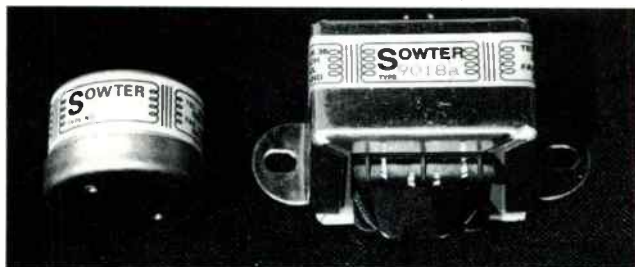Full range of Mumetal input and output transformers for balanced and unbalanced pre-amps, microphone amps, equalizers etc.



SOWTER EST. 1941
TRANSFORMERS

For the true "valve sound" and elimination of hum and interference in your own or vintage designs. A new range and custom service for low power transformers to complement our power amplifier products. Transformers built to order 2-4 weeks delivery. Full technical support. Free catalogue. Visa, MasterCard, JCB etc.

E A Sowter Ltd
PO Box 36 IPSWICH
IP1 2EL England
Tel: (+44) (0) 1473 252794
Fax: (+44) (0) 1473 236188

E-Mail: sales@sowter.co.uk
techsupport@sowter.co.uk
Call or visit our Website for catalogue and information
<http://www.sowter.co.uk>

TECHNICAL & GENERAL

SOME NECESSITIES - FROM THE ORIGINAL CLASSIC TURNTABLE SPECIALISTS

CONNOISSEUR			P&P
BD1/2 Drive Belt		£11.60	£1.90
BD1/2 Motor Suspension kit		£14.50	£2.50
SAU.2 Headshell		£17.50	£2.90
SAU.2 Connecting Lead		£16.50	£3.20

GARRARD Standard Models			
Wired arm tubes:	from	£14.50	£2.90
Cartridge carriers (sliders)		£12.50	£1.90

301/401 Transcription models			
Original Thrust pad assembly		£12.50	£2.50
Original Idler tension spring		£3.25	£1.90
Original Brake pad		£2.40	£1.90
Xeroxcopy Owners Manual 301 incl. full size mounting template		£9.30	£1.90
	401	£7.20	£1.90

Replacement 301 control knobs On-Off/Speed select	pair	£21.50	£2.90
Replacement 301 suppressor unit		£6.20	£2.50
Replacement 301 motor pulley (-2%), (-1%), (Std), (+1%)	each	£16.20	£2.50
Replacement 301 Chrome plated mounting bolts	set	£7.20	£2.50
Recommended Lubrication set - early 301 or 301/401	(specify)	£6.20	£1.90

GALDRING/LENCO			
Idler wheel (lock-nut or clip fixing)		£21.20	£2.90
Tension spring		£3.25	£1.90
Arm pivot bearings - with fitting instructions		£9.25	£1.90
Spindle/Main bearing assembly complete	GL.69/72	£21.00	£3.90
	GL.75/78	£25.00	£3.90
Chassis suspension springs (set of 4)	set	£19.50	£3.90
Headshells	from	£22.25	£2.80
Instruction books	from	£4.50	£1.90

THORENS			
TD.124 series			
Idler wheel	original	£28.50	£2.90
Idler wheel	our redesigned replacement	£16.50	£2.90
Drive belt		£17.50	£1.90
Suspension rubbers ('mushrooms')		£16.50	£2.90
TD.150/160			
Drive Belt		£14.70	£1.90
Suspension springs (-1%), (Std), (+1%) (set of 3) set		£13.50	£2.90
Suspension - main bushes (set of 3) set		£13.50	£2.90
Armboards TD.150 blank		£12.50	£2.50
" TD.160 "		£10.20	£2.90


CECIL WATTS Dustbugs & spares - incl. Preener wicks

Cartridges and styli for 78s and Mono LPs in addition to current Stereo LPs

TECHNICAL & GENERAL

PO BOX 53, CROWBOROUGH, EAST SUSSEX, TN6 2BY
TELEPHONE: 01892 654 534

GOING FOR BALANCE a new phase splitter

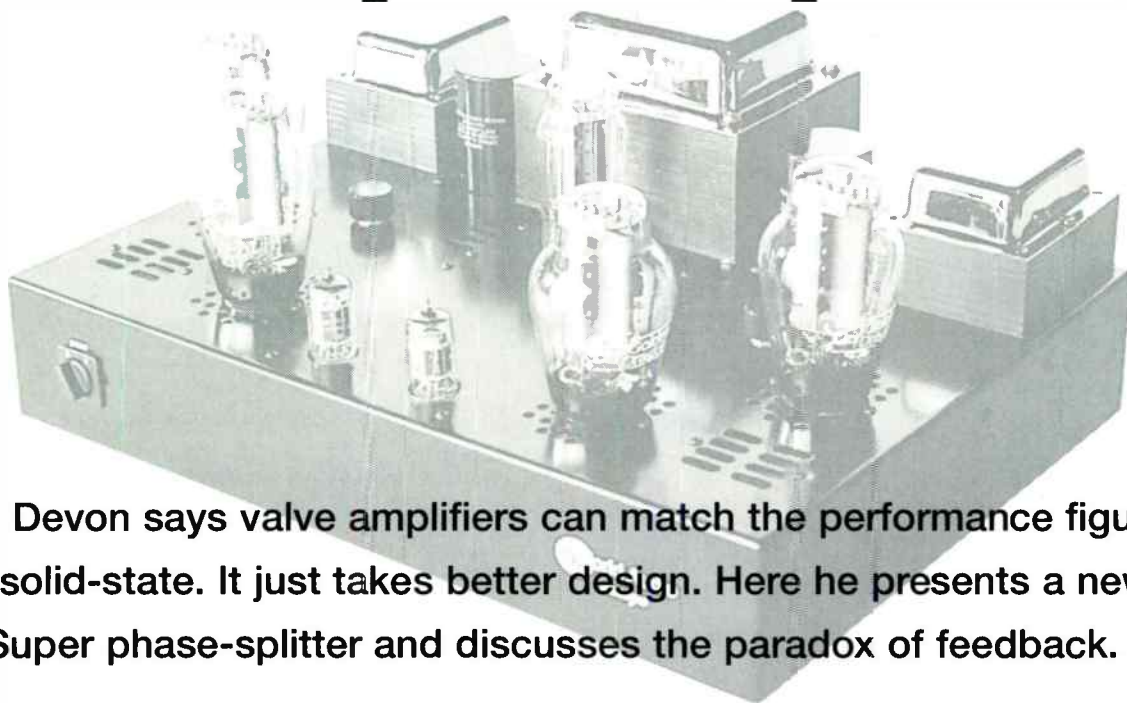

Gary Devon says valve amplifiers can match the performance figures of solid-state. It just takes better design. Here he presents a new Super phase-splitter and discusses the paradox of feedback.

In my last article (DIY Supplement No53, October 2000 issue) I outlined the valve phase splitter (or inverter) circuits in common use. These have appeared in classic circuits such as the Mullard 5-20, Williamson and so on.

It's been said that these circuits are as good as it gets for valve amplifiers. However, I have found that they have limitations. Problems arise from the fact that none of them achieve accurate balance between the two antiphase output signals. This increases even-harmonic distortion, as well as intermodulation distortion.

If the output transformer is well designed and constructed the cancellation effect of even-harmonics in a push-pull output stage functions well for the output valves alone, but not for earlier stages unless driven by a well balanced signal. Balance must be maintained over the full audio frequency range, a difficult proposition.


Most amplifiers include some degree of negative feedback. The benefit of negative feedback is diminished by the less-than-ideal performance of classic phase splitters because they limit the ability of the amplifier circuit to reject the distortion signal. One of the seeming paradoxes of negative feedback is that the

Diagram 1 - A classic long-tailed pair, which share a constant current source (I), or 'tail load'. This circuit arrangement is also used widely with transistors.

amplifier requires good (theoretically it should be perfect) open-loop linearity for it to function. Therefore, any improvement to the phase splitter / drive circuitry will give a double benefit to an amplifier using loop feedback. Better open-loop linearity results in less distortion in the first place, but because the open-loop linearity is better the feedback will be more effective. The evolutionary sideline of feedback-free amplifiers avoids this paradoxical problem of course.

To achieve any particular distortion figure, less feedback will be required or, with a given amount of feedback, less distortion will be present.

Diagram 1

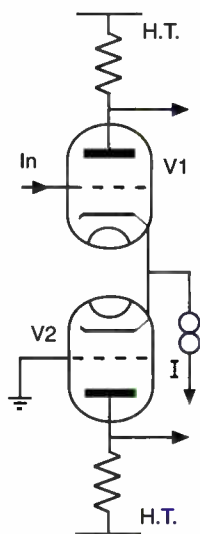

Reducing the even-harmonics changes the timbre of an amplifier. The result is a drier and crisper sound, with a more finely etched background. As the amplifier's linearity before feedback has been increased, intermodulation is also reduced so there is less background hash. This type of sound is far less "valve like", so to some it is less desirable.

I want to briefly outline methods which can be introduced to valve amplifier design where the measured performance can be made to approach or equal that of a solid-state amplifier. As with the previous phase splitter article I have included no equations as the intention is to provide reading material rather than a lesson in electronics.

The circuit topologies I have developed are quite esoteric. I have held them close to my chest for some time. Perhaps someone else has done the same thing already, I do not know.

In the last article the long-tailed pair was introduced. Essentially there are two valves with a common cathode connection, as in Diagram 1. If the tail load is a perfect current source then any signal which is present at one anode *must* also be present 180 degrees phase shifted at the other. This is because the total current is shared by the two valves. If the current in one valve increases then it must decrease by an equal amount in the other.

This is the beginning of a perfect phase splitter. It only functions perfectly with a

Audiophile Sound • Professional Finish • Affordable

Our aim at Riverside Audio is to enable the home constructor to build valve amplifiers which combine true audiophile sound quality with the professional finish of high-end products at an affordable price.




The Riverside 4040 is an integrated amplifier featuring dual mono construction, five line level inputs and both 4 and 8 Ω outputs. The chassis is hand polished stainless steel and includes a matt black valve cover. The amplifier delivers 40 Wrms per channel at less than 0.1% distortion. Kit £625, fully built £725.

The Riverside P2 moving magnet phono amplifier is designed to partner the Riverside 4040 for those who enjoy the vinyl sound. High accuracy equalization is provided for a moving magnet input to a generous line-level output. Kit £225, fully built £275.

Contact Riverside Audio for further information and pricing. Most parts are available separately - even down to individual components. Riverside Audio can also design special audio mains and output transformers.

Riverside Audio, 18 Riverside, Cambridge CB5 8HL
Telephone (01223) 512253 Facsimile (01223) 572629
Internet—<http://www.riverside-audio.demon.co.uk/>

Speaker Kits From IPL Acoustics

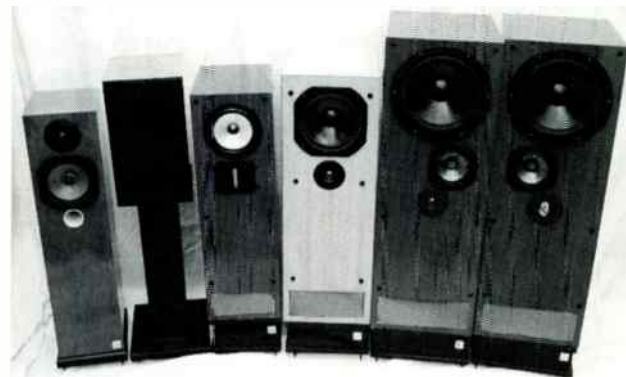

IPL Acoustics are pleased to announce their latest range of speaker kits which include no less than seven transmission lines, three conventional speakers, two AV centre speakers, and an active subwoofer kit.

IPL kits are designed to the very highest specification using sophisticated Audiosuite testing system to ensure smooth response, correct phase, and low distortion. Only the best drivers and crossover components are utilised.

Our two new flagship transmission line kits include the:

S3TLM RIBBON which incorporates a superb custom built aluminium coned 6.5" bass mid unit and the unique new IPL Ribbon tweeter.

S5TL GOLD which incorporates the Audax 10" HDA bass unit, the 5" HDA mid unit, and the highly acclaimed Audax piezo GOLD dome tweeter in a transmission line enclosure. The sound quality of all IPL speakers compare well with commercial speakers costing 3-4 times the cost of the kit and are tunable to suit your room and system.

If you would like further details of our range, which includes drivers, Quality components, and Silver PTFE cables, please send a 40p A4 S.A.E. to **IPL Acoustics, Chelsea Villa Torrs Park, Ilfracombe, Devon, EX34 8AY. Tel: 01271 867 439**
Website: www.marketsquare.co.uk/ilfracombe/iplacoustics.htm



WIRE & INSULATION

introduce **DESKADEL** Products

731/733 Ormskirk Road • Pemberton
Wigan • Lancashire • England • WN5 8AT
TEL/FAX: 44 - 1 - 942 887171

The *DESKADEL* range of HI-Fi interconnect, speaker cables, hook-up wires and tone arm wires are precision manufactured featuring *PURE SILVER* conductors insulated with *PTFE* in a variety of designs to suit all applications. Using only the finest materials and the latest manufacturing techniques we aim to provide a selection of quality products for superb natural sound reproduction on a scale previously unheard.

DISTRIBUTORS

Switzerland
ARBELOS

Tel/Fax: 41-613616466

UK

AUDIO SYNTHESIS
Tel: 44-1-159224138
Fax: 44-1-159229701

Holland
ANALOGUE AUDIO PRODUCTS
Tel/Fax: 31-30-6044342

Belgium
DESKADEL INT BVBA
Tel: 32-3-8892231
Fax: 32-38609181

INTERNATIONAL TRADE ENQUIRIES WELCOME

constant current tail. This circuit also has the advantage of allowing good power supply rejection, as long as the following stages are also well balanced.

Such a stage loses a lot of gain (50% reduction) when driven by a single-ended input signal, which is the norm.

Diagram 2

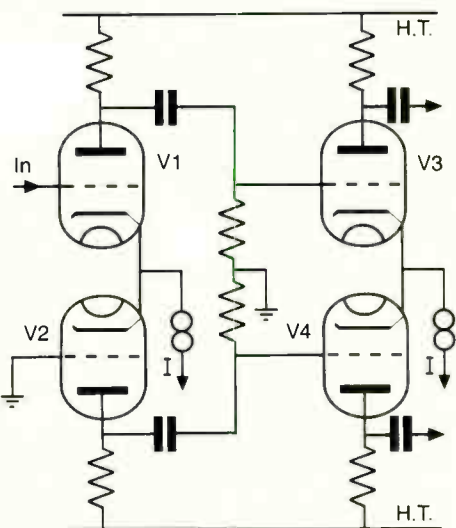


Diagram 2 - Two stages cascaded give good gain and balance, but introduce three LF time constants, limiting feedback.

What if we were to cascade two such stages to increase the gain to a point where feedback could be incorporated? See diagram 2. Now, dependant on the valves used, we will have as much gain as we would probably need. Also, any slight imbalance that appears from the first long tailed pair will be cancelled by the rejective capability of the second pair.

Diagram 3

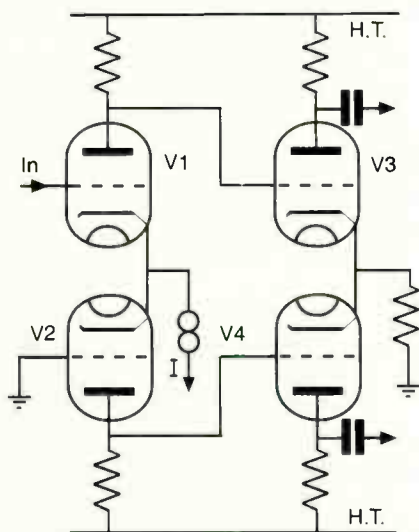


Diagram 3 - Direct coupling eliminates one time constant, allowing more feedback to be applied.

The trouble with this arrangement is that when we apply feedback around the whole loop of a practical amplifier the low frequency stability isn't very good because we have three low frequency time constants within the loop. Firstly, the coupling capacitors from

V1/V2 to V3/V4; then from V3/V4 to the output valves and finally the output transformer's finite primary inductance.

How about direct coupling the first stage to the second to eliminate one of the time constants, as in Diagram 3? It looks good on paper and now we only require a resistor as a tail load for the second pair. But we find that we have a problem when we use real world valves. Any slight difference between the anode voltages of V1/V2 is amplified by V3/V4

and the whole system has a serious DC offset. Also, we may need a seriously high anode voltage because the cathodes of the second long tailed pair are already at the potential of the first's anodes.

Somewhere between DC and AC coupling would seem to be the order of the day, as in Diagram 4. Now we are getting somewhere. We can apply a

sensible DC voltage to the grids of the second long tailed pair, say 50V. Also, the coupling network allows decent low frequency stability, unlike pure AC coupling. What we have is effectively a low frequency step network. If we used two ECC83 valves in cascade the gain would be over 2000. That's quite a lot, unless triode output valves are used or we are looking at a ridiculously sensitive power amplifier. We could use lower gain valves maybe, or how about placing a local loop around our phase splitter/ drive stage, as in

Diagram 5?

This circuit now has Super Balance right across the audio range and way beyond. The local feedback also reduces the effect of the low frequency step into the bargain, so bass quality is supreme. The extra resistors in the cathodes of V1/V2 help mop up any D.C. imbalance. The resistors marked Rf apply the local shunt feedback.

Overall feedback in a complete

Diagram 4

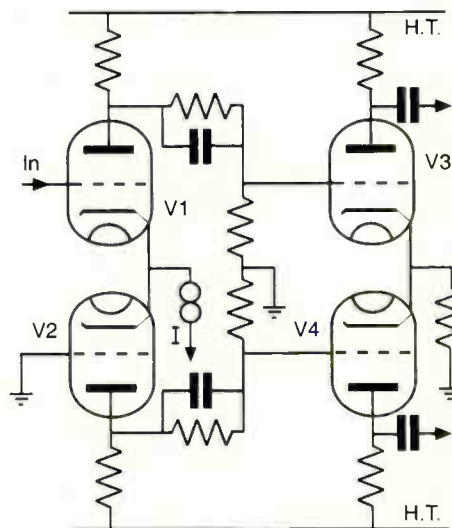


Diagram 4 - Direct coupling again, as in Diagram 3, but with resistors. Gain differences between V1 and V2 will be amplified by V3 and V4 to produce serious D.C. offset.

amplifier would be applied to the grid of V2 via a suitable attenuation network. An example amplifier is illustrated by diagram 6.

Diagram 5


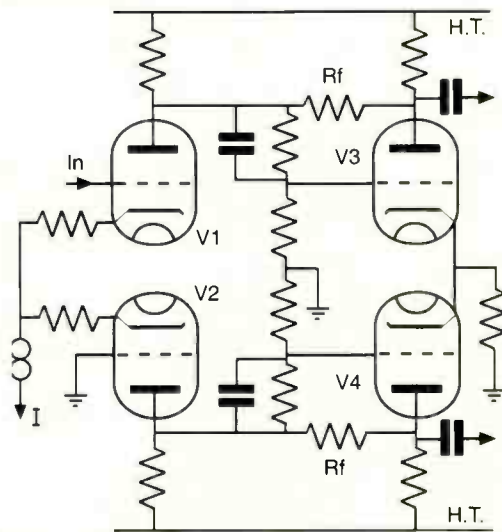


Diagram 5 - Adding local D.C. and A.C. feedback from anode of V3 and V4 back to the grids via resistors Rf gives 'Super Balance'.

ADVANCED SPEAKER DESIGNS

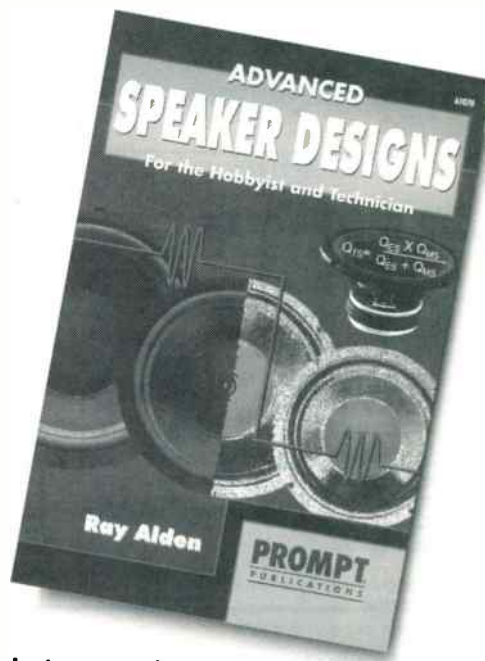From the USA, author Ray Alden presents the calculations needed to design a loudspeaker. Noel Keywood gets his calculator out.



In the Preface of this book author Ray Alden tells us where's he's coming from. "After 27 years teaching maths...it was apparent there was hardly any course that applied mathematical abstractions". So "I began a one year course in 'speaker building'". "Theory was taught and the 'speakers designed using mathematics". "Using scientific calculators you will be able to make quick work of complex equations". "The book will give you an intuitive feeling of how speakers work".

There's a place for this sort of book and, designing loudspeakers myself for Hi-Fi World, I quite like to have basic equations to hand. Nowadays computer programs are fast, sophisticated, relatively cheap and not prone to error. But there's always a need to sit down and plough through a few sums, all the same. Don't expect this book to answer all your loudspeaker design questions, especially if you prefer a practical approach and would rather avoid theory.

Having said all this, there is a need to know 'base theory'.. In my view if you don't understand, for example, that reactive components store and return energy then you will never really understand what is going on in any loudspeaker, which is a giant collection of springs and masses, inductors and capacitors, all interacting. So a good base theory book, which this one attempts to be, is always welcome.

Ray Alden is no M.G. Scroggie. He speeds through the physics. The equations come thick and fast, with not much discussion about the mechanism they describe. To some extent this is an inevitability in a book that attempts to cover a massive subject in 124 pages. So by page 10 we've been through A.C. theory in a chapter entitled

The Three Basic Components of Loudspeaker Design and by page 24 we've learnt how to obtain Thiele-Small parameters and measure the frequency response of a loudspeaker under Drivers Parameters. In truth these subjects demand books in themselves but the text here is concise enough and good as a guide.

A wry smile came to my face where Alden says "Your scientific calculator will handle exponents and logarithms very quickly. Don't be intimidated by this equation or any of the others that follow; it's just a matter of pressing the correct buttons"! You need to know how to handle the maths before pressing the buttons. The book is best for science students fluent with the not-too-complex maths involved, but keen to learn more about loudspeaker design. Which is what you would expect considering Alden's background. Its explanations of loudspeaker behaviour I would not dispute; the research appears careful. There are enough usefully concise explanations to make the book a valuable quick reference for equations and outline theory. On page 72, for example, I found a clear diagram of crossover orders and radiation phase angles.

Chapter 3 deals with "Sealed Enclosures" (infinite baffle) and Chapter 4 the much beloved Vented Enclosure, or reflex port loudspeaker. After these basic types comes a Chapter on Computer Aided Design, which concentrates solely on a programme called TOP BOX.

After a chapter on Subwoofers comes an all-important chapter on Crossovers. Again, it is concise and useful, but at 16 pages relatively short and by no means a complete guide. Crossover design is, ultimately, a juggling act, using the sort of theory provided within this book, but also measurement. KEF

once adopted a rigorously mathematical approach to produce highly complex solutions, so it can be done this way, but then they started out with enormously sophisticated device models in the first place, before number crunching. I wasn't surprised to see Richard Small's name appear (p37) in this book; he worked at KEF in the 1970s, contributing substantially to this theoretical approach.

At the rear of the book there's a Chapter with seven loudspeaker build projects. It is very condensed and relies upon American Radio Shack drive units, since *Advanced Speaker Designs* was "Printed in the United States of America" and hails originally from Texas. As a note at the front of the book clearly states, the use of other drivers will produce different results, so the designs will be difficult to recreate by U.K. constructors.

Advanced Loudspeaker Designs fulfils a specific need, being best suited to engineering and science students, or those with a bent for maths. Nowadays computers usually take the work out of button pressing, but all the same it is useful to have a short, concise guide to the basic maths, like this one. Its concise technical explanations of how speakers work many will find valuable too I believe.

ISBN 0-7906-1070-1
Howard Sams & Co.
Indianapolis, Indiana, USA.

This book is available from our World Library
(see p76/77 for the order form)
Book Code: I 680
Price: £18.95 + £2.00 UK p+p

D.I.Y. LETTERS

Chris Logan from Sydney, Australia, asks about improving our Series II PHONO stage. and Gary Devon replies. Peter Moore builds and then modifies our KiT88 valve power amp..Check out his DIY web addresses.

PREAMP QUERIES


It's a good idea to offer a modular pre-amp - Supplement 51, June 2000 - though I have a few queries about its design, and hopefully these are of interest to the readers.

Why the substantially larger load resistor - R29/R30 - for the second valve stage than that of the first stage, though still only a relatively small cathode resistor - R27/R28? Won't the combination result in the second stage being biased in the non-linear portion of the valve's operation?

R6 in the power supply unit is shown as 0.1R. Would it not require a value of at least 1R there to be of any practical effect?

Apparently, a better defined bass sound can be

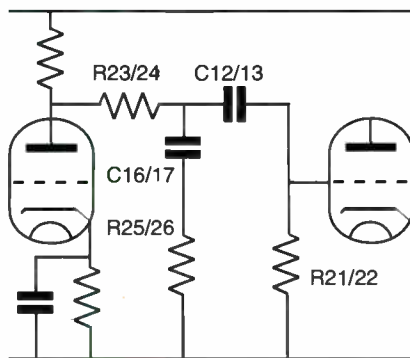achieved by placing the A.C. coupling capacitor differently in an RIAA circuit so there will be less interaction between it and the 3180uS time constant



section. Such placement necessitates repositioning the grid resistor also, so my alternative is above - Please publish the D.C. voltages at each of the valve's anodes and cathodes. It's

most useful for builders to check to see if they have correctly assembled the kit and to ascertain if each valve is OK. Most builders will know such

voltages may vary a little from the published values.

Whilst on the topic of valve circuits, are any of your contributors or readers able to sketch the basic circuit of the Loyez phase splitter? I cannot find it in the Radio

Designers Handbook or elsewhere. I suspect it is a colloquial name for a well known circuit.


Thank you for your very interesting DIY Supplements. **Chris Logan, Sydney, Australia.**

Thanks for the letter Chris, you have brought up some interesting points. As with anything there are many and varied ways of approaching an audio design. When it comes to the bottom line there are two major practical factors which must be considered.

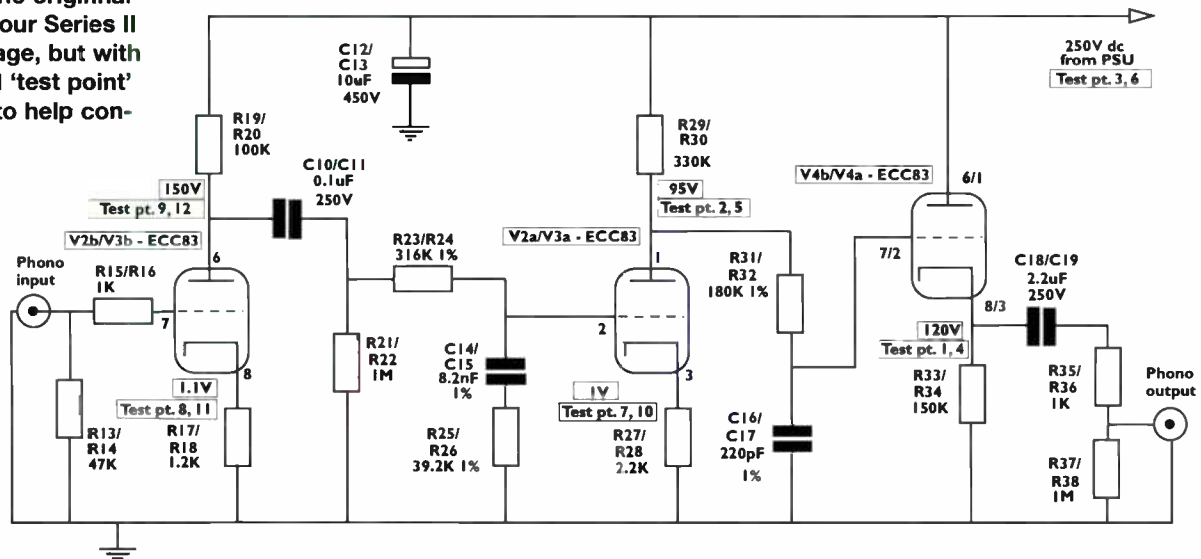- 1) The design must function as intended, and
- 2) all of the components used in the design must be operated within their physical limits.

There are improvements which could be made in terms of component quality and circuit sophistication, but if all of these were implemented we end up with a £10,000 super preamp which is no longer a practical proposition. A line must be drawn somewhere and in general we offer readers a

At right: the original circuit of our Series II Phono stage, but with additional 'test point' voltages to help constructors.



SUBSCRIPTIONS



UK SUBSCRIPTION £27

VISIT OUR WEBSITE: www.hi-fiworld.co.uk

Get your issue of **hi-fi world** straight to your door!

Get to our amazing classified ads first and grab a bargain!!

Run by dedicated hi-fi engineers and enthusiasts, **Hi-Fi World** has become famous for its informative reviews and radical kit designs.

OVERSEAS SUBS RATES

Surface Mail	£40
Airmail Europe	£50
Airmail Middle East & South-East Asia	£60
Airmail USA, Canada, Australia, Japan, Korea & China	£70

MISSED AN ISSUE?

Back issues also available at a cost of £3.50 only (includes P&P), payment by cheque only - overseas please contact us for details. Send cheque to: **Hi-Fi World, Freepost LON3478, London, W9 1BR.**

Credit Card Hotline Monday - Friday 9.30am - 12.00 noon: Tel: +44 01923 270 833 Fax +44 01923 260 588

By post: Make cheque or postal order payable to: **Audio Publishing Ltd**, sent in an envelope marked: **Hi-Fi World, Freepost LON3478, London, W9 1BR**

HI-FI WORLD SUBSCRIPTION FORM

I would like to pay by cheque made payable to Audio Publishing Ltd. Credit Card Airmail Surface Mail

Please debit my VISA/MASTER/SWITCH Card No. (Switch card issue No. _____)

Expiry Date: _____ Cardholder Signature: _____



Name _____

Address _____ Delivery Address (if Different) _____

Post Code _____

Daytime Tel: _____

Start Issue _____

good basic design upon which they can experiment if they so wish.

Another hidden danger of implementing 'improvements' is that unless those improvements are synergistic the final design ends up an expensive mess.

If I answer your questions one by one.

1) In the phono section the second stage operating conditions were chosen to give an anode voltage of approximately 100V. This voltage was chosen to DC bias the cathode follower, but without placing too much stress on the cathode follower heater-cathode insulation. The high load value gives a load line with a shallower slope, giving a greater, more linear swing at the lower anode voltage. Check out the operating condition on the ECC83 characteristic curves.

2) R6 is there to reduce the peak charging current into the reservoir capacitor. Only a small resistor is required as the peak currents are so high.

3) Rearranging the L.F. time constant network so that it appears before the DC blocking capacitor is a good idea in theory. The problem is that now we have the full anode voltage of the previous valve across the time constant capacitor when the unit is running, with the possibility of the full HT voltage across it when warming up. This presents problems when it comes to selecting components. A high accuracy polystyrene capacitor of 350V rating of the value required is not so readily available as the low voltage one chosen. The HF time constant before the cathode follower requires a far smaller value component which can easily be found at the required voltage. Hence the circuit being as it is.

4) We do publish voltages and there were some on the original diagram, although they were difficult to see because the diagram ended up smaller than ideal in terms of legibility. The same diagram, with larger type and addi-



tional test point info is published here.

I am not familiar with the 'Loyez' phase splitter. As you say, it could be a common type masquerading under a different guise.

Gary Devon

TWEAKING KIT88

Any DIY or kit hi-fi is a haven for the tweeker. We all strive to obtain maximum performance. Let me recount my journey. I was fortunate to listen to your KiT88 prior to owning my own, something rare in DIY. I wouldn't say I was an expert in valve technology but I felt competent to build it with the safety precautions put in place by World Audio Design. I built three kits before this one.

It took me around seven hours to complete. Finally, switch on arrived and, like my previous kit amps, it worked first time. Around ten hours later it suffered an output tube failure, something that bemused me a little, since amps. built


three years ago are still going strong. The WAD schematics give a 10% tolerance on voltage readings and I found I was close to these limits but not over.

A quick search on the internet proved one thing: how various valve manufacturers vary in claimed power ratings. The supplied JJ Teslas have one of the highest claimed limits. The JJs were replaced by WAD

without quibble.

I also ran to my local Maplin and purchased four Chinese KT88s. When the anodes glowed cherry red these were swiftly returned too! Now I was understanding how component quality was critical for sound and reliability.

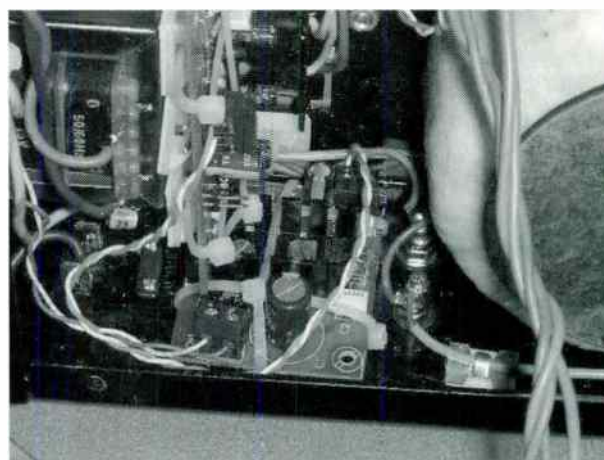On the subject of valve configuration, many ways are available for a push-pull ampli-




The switch on-relay board, nestling by the mains transformer. It delays switch on, allowing the heaters to warm up thoroughly before HT is applied.

er like the KiT88. I believe the KiT88 uses a compound type bias - "a mixture of fixed and cathode bias". I have listened to both and feel that cathode bias alone offers a better overall balance and is less critical as regards valve tolerance. I removed components BR3, C4 and R5 and replaced R3 with a wire link; the four cathode resistors R13,14,15 &16 were

still able to drive my Tannoy R2s to annoying levels if the urge arose.

Within the signal path I replaced the stock carbon pot with a Danish Audio stepped attenuator. I played around with the article in the December 1998 Hi-Fi World supplement on how to design a DIY stepper and had excellent results. Unfortunately, fitting this within

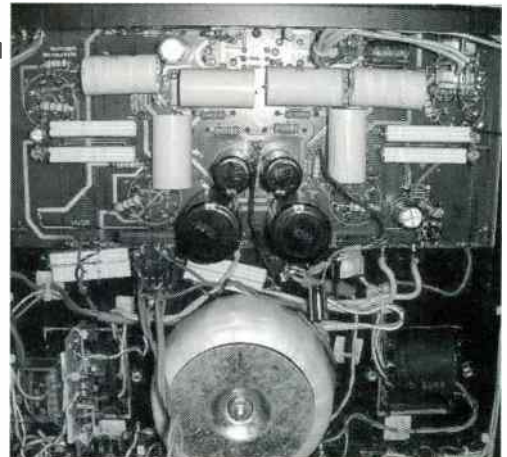the KT88s, a simple process of removing grid resistors R6,12, 32 & 33 and fitting 100Ω 1W resistors between G2 & Anodes of each KT88. Keeping within GEC's recommendations the cathode resistors were replaced with 560Ω 11W.



replaced with 470Ω 11W - something near to GEC's spec for their KT88.

Something I found useful was running the amp off a Variac; this helped me to measure voltages and evaluate the sound quality with less power. With the cathode resistors I noticed an increase in voltage across them as I approached full mains level so C9,10,11 &12 were replaced with 100V Black Gates - my first exotic capacitors. Now my amp was a little less powerful but, to my ears, smoother in presentation and

the KiT88 was problematic so I opted to purchase the DACT with its surface mount resistors from Audiocom.

There is a wealth of exotic caps available from a few pounds to hundreds of pounds. Here I set about replacing all of the signal caps, not going for paper-in-oil at this time but 47uF 600V polyester caps from RS Components. With these I found vocals much more open and precise with lip smacking accuracy.

Moving onto configuration, I have now triode connected

Using

Sovtek's KT88 I found a little redness in the anode although this was only on a single tube. To reduce B+ two 100Ω 17W resistors in parallel were put in line on both legs of the HT supply. I prefer the sound of valves with slightly less volts applied to them, IMO sounding warmer and less harsh.

In the pictures you will notice additional circuit boards; these offer a soft start and delay to the HT supply using two 50W 4K7 resistors bolted to the base. This drops HT until a relay triggers around thirty seconds after applying HT. Obviously, this doesn't offer extra performance to the sound but does protect the valves. Many commercial high-end amps do not have this feature.

That about wraps things up for now but I should mention some people who have given me assistance in understanding valve amps.

Thanks to following -

Nick Lucas

www.worldaudiodesign.co.uk

<<http://www.worldaudiodesign.co.uk>>

Suppliers of KiT88

Thorsten Loesch

www.audioasylum.com/audio/tubes

<<http://www.audioasylum.com/audio/tubes>>

> Audio forum

Mark Bartlett

www.audiocom-uk.com

<<http://www.audiocom-uk.com>>

Component suppliers

Derek Rocco

www.watfordvalves.com

<<http://www.watfordvalves.com>>

Valve Suppliers

The Guys at Langrex Supplies for

Mullard CV4003/Westinghouse

6AU6 supply

Peter Moore

pete.m@solarcom.in2home.co.uk

Audio Link	IFC	Falcon Acoustics	12	Riverside Audio	14
Audiolab Leeds	12	Glass Audio	6	Sowter Transformers	12
Billington Export	IBC	IPL Acoustics	14	Sugden	IBC
BK Electronics	4	Langrex Supplies	IFC	Technical & General	12
Chelmer Valve	IFC	Lockwood Audio	4	Watford Valves	4
Cricklewood Electronics	6	PM Components	BC	Wire & Insulation	14

**COMPETITIVE WHOLESALE PRICES
BILLINGTON EXPORT LTD**

New old stock - Government or Original boxes unless marked * which are White box

On these types ONLY you can obtain these WHOLESALE prices for a MINIMUM ORDER ONLY £50


	1-19	20-49	50-99	100-199	200+
3D21 STC Data available	£12.00	£9.50	£9.50	£7.50	£7.00
6AK5 Mullard	£1.95	£1.95	£1.95	£1.95	£1.30
6AM5 Mullard UK	£3.00	£2.00	£1.60	£1.35	£1.25
6AK6 Brimar UK	£1.00	£0.65	£0.45	£0.38	£0.38
6AU6WC * USA	£1.43	£1.43	£0.95	£0.85	£0.66
6AU8A GE/RCA USA	£0.75	£0.75	£0.75	£0.75	£0.75
85A2* East European 90 day guarantee	£1.80	£1.20	£1.20	£1.20	£1.10
807 Russian	£6.60	£4.40	£3.00	£2.90	£2.70
5644 Raytheon	£3.90	£2.60	£2.50	£2.40	£2.30
5755 Raytheon	£2.63	£2.63	£2.63	£2.63	£1.75
7327 Sylvania, may be similar to ECC82	£1.35	£1.35	£0.90	£0.90	0.90
ECL86/6GW8. Try PCL86 which is a similar valve at an amazing low price! Data available					
EF86. Use EF95 which is a similar valve. EF95 is P7G base. EF95 is recommended in Glass Audio. Data available.					
EF95 Mullard UK	£1.95	£1.95	£1.95	£1.95	£1.30
EL34 see 3D21 possible alternative					
EL84 near equivalent try 6CH6	£1.95	£1.95	£1.40	£1.30	£0.80
6CH6 Brimar UK, similar to EL84 Mullard but different pin out.					
No discounts possible. Data available.	£1.95	£1.95	£1.40	£1.30	£0.80
PC86 Zaerix East Europe	£3.68	£3.68	£2.45	£2.45	£2.45
PC900/4HA5 East European	£1.72	£1.72	£1.15	£1.15	£0.90
PCC84/7AN7 Mullard UK	£1.50	£1.00	£1.00	£0.90	£0.80
PCC89 Russian	£1.50	£1.00	£0.90	£0.75	£0.65
PCL86/14GW8 Polish or Russian made using					
Philips technical expertise	£0.53	£0.53	£0.53	£0.53	£0.37
SV811-3 Svetlana	£19.50	£16.00	-	-	-
TT21 Billington Gold Chines	£27.00	£18.00	£18.00	£16.00	-
UCL82 * Russian	£1.80	£1.20	£1.20	£1.10	£1.00

1,000,000 valves in stock, including E88CC, ECC81, ECC82, ECC83, EF86 EL34, EL84, KT66, KT88, 6SL7, 6SN7, 300B, 807, 845, 6080 and sockets. Please enquire for RETAIL or WHOLESALE prices. We also stock the excellent BILLINGTON GOLD brand and limited quantities of Mullard, GEC, etc.

MASTERCARD, VISA and most credit/debit cards accepted.
IE GILLMANS ESTATE • BILLINGSHURST • SUSSEX RH14 9EZ UK

Visitors by Appointment only

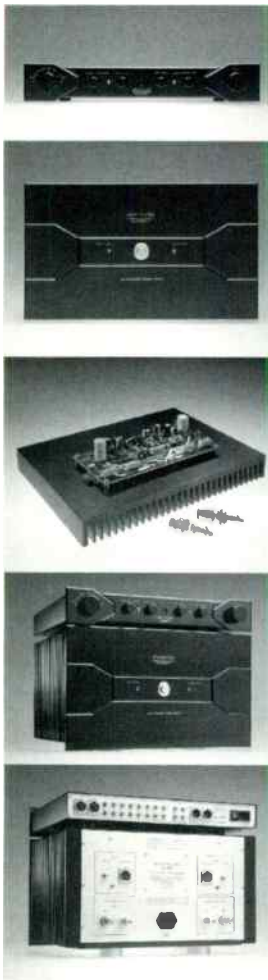Tel: (0) 1403 784961 • Fax: (0) 1403 783519 • Email: sales@bel-tubes.co.uk



SUGDEN audio products



Masterclass from the original CLASS A company

New products from Sugden

Wide-bandwidth d.c coupled high current class A power amplifier and matching pre-amplifier. Available as a stereo power amplifier you can upgrade or balanced monoblocks.

Handcrafted from the finest materials and components, Sugden guarantee to add an extra dimension to your listening pleasure. Our superior wide-bandwidth designs will increase the dynamic range and sonic accuracy of your audio system - without fatigue.

With over thirty years experience in design and manufacturing Sugden has become a reference for reviewers, musicians and audiophiles around the world. Prices start at £549.00 for the Audition series so why settle for anything less?

J. E. Sugden & Co Limited
Valley Works, Station Lane, Heckmondwike,
W. Yorks. WF16 0NF
Tel. 01924 404088 Fax 01924 410069
Email jesugden@compuserve.com



Golden Dragon

Precision Audio Tubes

Please enquire for any tube not listed. We have an inventory of over 2,500 different types in stock.

Golden Dragon High Quality Pre-amplifier Tubes

12AT7A/E81CC/ECC81	£ 6.95
12AU7A/E82CC/ECC82	£ 6.95
12AX7A/E83CC/ECC83	£ 6.95
12BH7A	£ 9.95
6DJ8/E88CC/ECC88	£10.95
6SN7GT/ECC33	£ 8.95

KT66R	£69.95 pr
KT88R	£69.95 pr
6550WA	£67.95 pr

Golden Dragon Special Quality Pre-amplifier Tubes

E81CC-01	Gold Pins Low Microphony Low Noise	£10.50
E82CC-01	Gold Pins Low Microphony Low Noise	£10.50
E83CC-01	Gold Pins Low Microphony Low Noise	NEW £ 9.50
E88CC-01	Gold Pins Low Microphony Low Noise	£14.50

Golden Dragon Power Tubes

	Matched Pair	Matched Quad	Matched Octet
EL34 Super	£25.00	£50.00	£100.00
EL34M	£25.00	£50.00	£100.00
E84L (special quality EL84)	£12.50	£25.00	£50.00
EL156 Octal	£75.00	£150.00	£300.00
6L6WGB	£25.00	£50.00	£100.00
KT66	£25.95	£52.00	£104.00
KT66 Super	£65.00	£130.00	£300.00
KT88	£57.95	£116.00	£232.00
KT88 Special (Gold plated)	£67.95	£136.00	£272.00
KT90	£65.00	£130.00	£260.00
KT90LX	£75.00	£150.00	£300.00
350B	£29.95	£60.00	£120.00
6L6GC	£19.95	£40.00	£80.00
6550A	£42.95	£86.00	£172.00
6550A Special (Gold plated)	£64.95	£130.00	£260.00
50CA10	£84.95	£170.00	£340.00
807	£25.00	£50.00	£100.00

Golden Dragon Triodes

	Singles	Per matched pair	Per matched quad
2A3 4 pin	£22.50	£50.00	£100.00
2A3 Octal	£22.50	£50.00	£100.00
211	£28.50	£60.00	£120.00
811A	£11.50	£25.00	£50.00
845	£36.50	£75.00	£150.00
805	£36.50	£75.00	£150.00

Golden Dragon T300B Range

300B Super	£79.00	£160.00	£320.00
4.300B	£84.00	£170.00	£340.00
4.300B LX Super	£124.00	£250.00	£500.00

We have a vast range of tubes available from manufactures all over the world including rare and vintage types. an 80 page booklet of valves available is updated monthly and can be provided at a cost of £2.50 per copy U.K. £4.00/\$7.00 rest of world or you may telephone our Sales Desk for a prompt quotation.

Prices exclude VAT and Carriage. Please add carriage charge of £2.50 for UK orders and VAT at 17.5%

P.M. COMPONENTS LTD, Selectron House, Jenkins Dale Industrial Estate, Chatham, Kent. ME4 5RD
Tel 01634 848500, Fax 01634 848676, e-mail: 101650,2424@Compuserve.com

The Valve. Golden Dragon



Simply, The Best.

For more information contact:

PM Components Ltd, Selectron House, Jenkins Dale Industrial Estate,
Chatham, Kent. ME4 5RD

Tel 01634 848500, Fax 01634 848676, e-mail: 101650,2424@Compuserve.com