

October '79

45p

Hobby Electronics



TANTRUM

At long last

FREQUENCY METER

Hertzometer

HOBBYTUNE

HE music box

ELECTRONIC GAMES

Play the game!

MULTI SIREN

Annoy the neighbours

MICROWAVE COOKING


Cook your goose.

Tecknowledgedgey for sale.

The Mark III FM Tuner

DIY Hi-Fi will never seem the same again. Ambit's Mark III tuner system is electrically & visually superior to all others. Some options available, but the illustrated version with reference series modules: £149.00 + £18.62 VAT

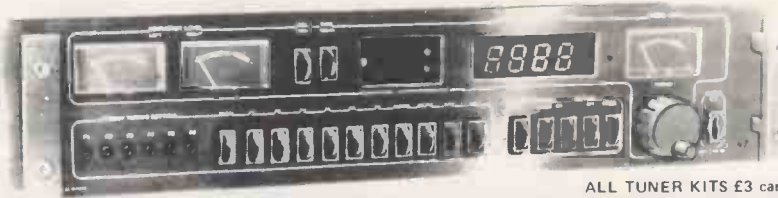With Hyperfi Series modules
£185.00 + £23.12



ALL TUNER KITS £3 carriage

Digital Dorchester All Band Broadcast Tuner: LW/MW/SW/SW/SW/FM stereo

A multiband superhet tuner, constructed using a single IC for RF/IF processing - but with all features you would expect of designs of far greater complexity. The FM section uses a three section (air gaud) tuned FET tunerhead, with ceramic IF filters and interstage tuning; AM en-plays a double balanced mixer input stage, with mechanical IF filters - plus a BFO and MOSFET product detector for CW/SSB reception. Styled in a matching unit to the Mark III FM only tuner, employing the same degree of care in mechanical design to enable easy construction. MW/LW reception via a ferrite rod antenna.

Electronics only (PCB and all components thereon) £33.00 + £4.12 VAT

Complete with digital frequency readout/clock-timer hardware £99.00 + £12.37 VAT

Complete with MA1023 clock/timer module with dial scale £66.00 + £8.25 VAT

Hardware packages are available separately if you wish to house your own designs in a professional case structure. Please deduct the cost of electronics from complete prices.

LW/MW/FM LCD Digital Frequency Display - July FW feature

Update your old radio, or build this into a new design. Or use it as a servicing aid - this low power unit with LCD display reads direct frequency in kHz/mHz, or with usual AM/FM IF offsets for received frequency. Low power LCD means no RF! - 15-20mA at 9v even with the divide by 100 prescaler. FM resolution is 100kHz, AM 1kHz. Sensitivities better than 10mV

Complete kit £19.50 +*£1.56 VAT. Built and tested version £24.00 +*£1.92 VAT

Various other DFM systems described in our catalogue part 2 - including a one chip solution to providing digital display of FRG7 kHz dial, combined with clock/timers etc.



PW SANDBANKS PI METAL LOCATOR

Maintaining our professional approach to home constructor kits, we offer the pulse induction 'Sandbanks'. Now with injection molded casing for greatly improved environmental sealing. £37.00 +*£2.96vat.

VHF MONITOR RX WITH PLESSEY IC

4/9 channel version of the PW design but using standard 3in OT crystals, and TOYO 8 pole crystal filter with matching transformers. Coil sets from our standard range to cover bands from 40 to 200MHz. Complete module kit £31.25 +*£3.90vat.

ETI - REMCON RADIO CONTROL

A tried and tested RC system with a full set of supporting hardware from a well known manufacturer. Please send for details - and watch our ads for further news of developments in RC products.

Radio and Audio Modules : The biggest range/ best specs.

EF5801/3/4 6 stage varicap tunerheads with LO feed and various levels of sophistication. New 5804 include pin AGC loop 'on board'. 5801:£17.45+£2.18vat 5803:£19.75+£2.47vat 5804:£24.95+£3.18vat. Frequencies in 40-180MHz on appcn.
EF5402 4 stage varicap with TDA1062, compound FET/Bipolar input stage, low noise, balanced mixer, pin agc, osc output. A worthy successor to the 5400. £10.75+£1.34vat

The 5402 is available centred on a wide range of frequencies from 30MHz to 180MHz. Non standard units £14.75+£1.84 - 3 weeks.
8319 4 stage varicap tunerhead from Larsholt using MOSFET RF and mixer stages. New temperature compensated oscillator for wide ranges of ambient temperature £13.45+£1.68vat
7252 Complete Larsholt FM tuner less stereo decoder. £26.50+£3.31vat
7253 Stereo FM tuner from Larsholt with FET head. (as 7252)
944378 Hyperfi stereo decoder. The very best. £19.95+£2.49vat
911223 Pilot cancel stereo decoder, priced to make the MC1310 as obsolete as it now deserves to be. £12.50+£1.56vat
Inotec 1-A fully DC tuned and switched LW/MW/FM stereo tuner to interface with synthesiser control etc. A first! Details O/A.

COMPONENTS for Radio and Audio ICs, HMOS etc.

The list is too long to attempt here, but AMBIT specializes in all types of semiconductor for radio reception, including devices operating from DC to 5GHz. New low cost SBL1 diode ring mixers (equiv case MD108 etc) - first with HMOS fets, now with a PCB for DC amplifier, and offset sense and protection relay for speakers. See catalogue and updates for most info, please send an SAE for information on anything you cannot find in catalogues.

Radio ICs	cost + vat	Stereo ICs	cost + vat	AF power ICs	cost + vat
CA3089E	1.94 24	MC1310P	1.50 19	LM380N	1.00 12
CA3189E	2.45 30	uA758	2.20 27	TBA1810AS	1.09 14
HA1137W	2.20 27	CA3090A	2.75 34	TDA2002	1.95 24
SN76660	0.75 9	HA1196	3.95 49	TBA820M	0.75 9
TDA1090	3.35 42	HA11223	4.35 54		
TDA1083	1.95 24	KB4437	4.35 54		
TDA1220	1.40 17	KB2224	2.75 34		
SL6640	2.75 34				
MC3357	3.12 39	Preamp ICs/switches			
HA1197W	1.40 17	TDA1028	3.50 44	25J48/25K 134 HMOS	
MC1496	1.25 16	TDA1029	3.50 44	9.90 +£0.80 vat(Pair)	
LM373/4	3.75 49	TDA1074	4.14 52	Signal fets/transistors and	
		KB4438	2.22 28	TOKO COILS & FILTERS!	

OSTS: Remember all OSTS stocks are obtained from BS9000 approved sources - your assurance that all devices are very best first quality commercial types. Some LPSN TTL is presently in great demand, so please check by phone before ordering.

TTL-Standard AND LP Schottky

N'	LSN'	N'	LSN'	N'	LSN'	N'	LSN'	N'	LSN'	N'	LSN'		
7400	13	20	7455	35	24	74126	57	44	74185	134	74377	1054	
7401	13	20	7460	17		74128	74		74188	275			
7402	14	20	7463		124	74132	73	78	74190	115	92	74378	93
7403	14	20	7470	28		74133		29	74191			74379	130
7404	14	24	7472	28		74136		40	74192	105	180	74368	37
7405	18	26	7473	32	38	74138		60	74193	105	180	74390	140
7406	38		7474	27	38	74139		60	74194	105	180	74393	140
7407	38		7475	38	40	74141	56	74	74195	95	137	74395	139
7408	17	24	7476	37	38	74142	265	74	74196	99	110	74396	133
7409	17	24	7478		38	74143	312	74	74197	85	110	74398	180
7410	15	24	7480	48		74144	312	74	74198	150		74399	150
7411	20	24	7481	86		74145	65	97	74199	160		74445	22
7412	17		7482	69		74147	175	74	74247		90	74447	140
7413	30		7483A		110	74148	109	191	74248		90	74468	110
7414	51		7484	97		74150	99		74249		93	74670	249
7415	30	24	7485	104	99	74151	64	84	74251		90		
7416	30		7486	205		74153	64	54	74253		105		
7417	30		7489	204		74154	36		74258		120		
7420	16	24	7490	33	90	74155	54	110	74259		108		
7421	29	24	7491	76	110	74156	80	110	74259		420		
7422	24	24	7492	38	78	74157	67	55	74260		153		
7423	27		7493	32	99	74158		60	74261		353		
7425	27		7494	78		74159	210		74266		100		
7426	36	27	7495A	65	99	74160	62	130	74273		124		
7427	27	29	7495	58	120	74161	92	78	74275		312		
7428	35	32	7497	185		74162	92	130	74279		73		
7430	17	24	74100	119		74163	92	78	74283		120		
7432	25	24	74104	63		74164	104	130	74290		90		
7433	40	32	74105	62		74165	105		74293		95		
7437	40	24	74107	32	38	74166			74295		120		
7438	33	24	74109	63	38	74167	70		74298		100		
7440	17	24	74110	54	54	74168			74324		242		
7441	74		74111	68		74169		200	74327		247		
7442	70	99	74112			74170	230	200	74352		100		
7443	115		74113			74172	625		74353		100		
7444	112		74114		38	74173	170		74357		237		
7445	94		74116	98		74174	87	120	74365		49		
7446	94		74118	83		74175	87	110	74366		715		
7447	82	89	74119	119		74176			74367		49		
7448	56	99	74120	115		74177	78		74368		49		
7449	89	99	74121	25		74180	85		74373		77		
7450	17	24	74122	46	57	74181	165	350	74374		77		
7451	17	24	74123	48	73	74182	160		74375		77		
7453	17		74124		137	74183		210					
7454	17	24	74125	38	44	74184	175						

CD4000 CMOS

4000	17p				
4001	17p	4059	563p	4522	149p
4002	17p	4060	115p	4527	157p
4006	109p	4063	109p	4628	102p
4007	18p	4066	53p	4529	141p
4008	80p	4067	400p	4530	90p
4009	58p	4068	25p	4531	141p
4010	58p	4069	20p	4532	125p
4011	17p	4070	20p	4534	614p
4012	17p	4071	20p	4536	380p
4013	55p	4072	20p	4538	150p
4014	95p	4073	20p	4539	110p
4016	52p	4075	20p	4541	141p
4017	80p	4076	30p	4543	174p
4018	80p	4077	20p	4549	399p
4019	20p	4078	20p	4553	440p
4020	93p	4081	20p	4554	153p
4021	82p	4082	20p	4556	77p
4022	90p	4085	82p	4557	386p
4023	17p	4086	82p	4558	117p
4024	76p	4089	150p	4559	388p
4025	17p	4089	50p	4560	218p
4026	180p	4094	190p	4561	65p
4027	58p	4095	105p	4562	303p
4028	72p	4097	372p	4566	159p
4029	100p	4098	110p	4568	281p
4030	58p	4099	122p	4569	303p
4031	250p	4100	90p	4572	25p
4032	100p	4101	90p	4590	60p
4033	100p	4102	180p	4162	90p
4034	58p	4103	58p	4163	90p
4035	120p	4174	104p	4583	84p
4036	250p	4175	95p	4584	63p
4037	100p	4194	95p	4585	100p
4038	105p	4501	23p		
4039	250p	4502	91p		
4040	83p	4503	59p		
4041	90p	4506	51p		
4042	85p	4507	55p		
4043	85p	4508	248p		
4044	80p	4510	99p		
4045	150p	4511	149p		
4046	130p	4512	98p		
4047	99p	4513	206p		
4048	60p	4514	260p		
4049	55p	4515	300p		
4050	55p	4516	125p		
4051	65p	4517	382p		
4052	65p	4518	103p		
4053	65p	4519	57p		
4054	120p	4520	109p		
4055	135p	4521	236p		

Micromarket

8216	1.95	2114	£10
8224	3.50	2708	£1
8228	4.78		
8251	6.25		
8255	5.40		
8255	5.40		
8212	2.30		
2102	£1.70		
2112	£3.40		
2513	£7.54		
4027	£5.78		

Development
MEK6800 £20
TK80 £306
AMI Synthesizer
TI, Intersil
Harris etc. OA

MEMORIES
2102 £1.70
2112 £3.40
2513 £7.54
4027 £5.78

MISC. LSI/Scalars/DVMs
NE555 30p NE556 75p NE558 180p
LM3909 72p 95H900C /320MHz / 80p
11C90DC /650MHz £14.00
ICM7216BI 8 decade 10MHz DFM/timer with direct LED drive and all counter features £19.82
ICM7217A1B1 4 decade programmable cntnr £9.50
ICM7207 clock pulse generator IC £4.95
ICM7208 7 decade counter/display driver £14.95
ICM7106CP LCD DVM IC (3 digit) £9.55
ICM7106CPK LCD DVM KIT £24.80
ICM7107CP LED DVM IC £9.55
ICM7107CPK LED DVM KIT £20.65
SP8629 divide by 100 200MHz scalar £4.20
MSL2318 divide by 100 to 175MHz min divide by 10 to 45MHz min £4.20

PLEASE REMEMBER TO ADD 8% VAT TO ITEMS LISTED UNDER OSTS

LINEARS non consumers

BIMOS	LM324N	71p	
CA3130E	84p	LM339N	66p
CA3130T	80p	LM349N	166p
CA3140E	60p</		

Hobby Electronics

Vol. 1. No. 12

October 1979


Monitor 6 **Kit Review** 27 **Analogue Frequency Meter** 45
 What's new? How it Hertz

Tantrum Stereo Amplifier 10



Worth the wait

Home Computing 16

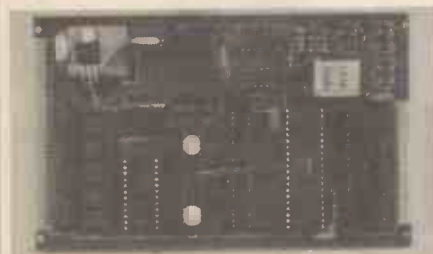

Don't get Baud

Clever Dick 15

Wish he was

Back Numbers 21

They're going fast

Subscriptions 21

Cheap at half the price

Hobbytune 23



Music Maestro please



Hot volts

Market Place 30

Psst, wanna bargain Guv

Chit-Chat 32

It's Ray Marston again

Short Circuits ... 36, 56, 72

Try these for size

Next Month's HE 37

Happy Birthday to us!

Electronic Games 38



Telly tournament time

ETI Next Month 49

No 1 but we're working on it

Microwave Cooking 50



Radio Chickens?

Hobbyprints 57

Couldn't be easier

Specials 57

Now read this

Multi-Option Siren 58



Kojak kit

CB Special 62

Hurry up they're going fast

Breaker One-Four 63

Buddies and Baddies

Into Linear ICs 66

Part four already?

Books from HE 72, 74

Enlarge your library

Hobby Electronics
 145 Charing Cross Road,
 London WC2H 0EE
 01-437 1002 (4 lines)

Published by Modmags Ltd.

Distributed by Argus Distribution Ltd.

Printed by QB Ltd, Colchester

Hobby Electronics is normally published on the second Friday of the month prior to the cover date

Editor: Halvor Moorshead

Editorial Asst: Rick Maybury

Project Team: Ray Marston, Steve Ramsa-

hadeo, John FitzGerald, Keith Brindley

Production: Diego Rincon, Pete Howells.

Technical Artists: Paul Edwards, Tony Strakas

Advertising: Chris Surgenor, Steve Rowe, Joy Cheshire, Sandie Neville

Admin Staff: Margaret Hewitt, Bren Goodwin, Tim Salmon, Tracey Campbell, Loraine Radmore, Loraine Stout, Marlin Felix, Halina Di-Lallo.

Copyright. All material in this publication is subject to world-wide copyright protection. Permission to reproduce printed circuit board patterns commercially or marketing kits of the projects must be sought from the Editor. All reasonable care is taken in the preparation of the magazine to ensure accuracy but Modmags cannot be held responsible for it legally.

ALL PRICES IN PENCE EACH UNLESS OTHERWISE STATED

CAPACITORS				Electrolytic Can Type				Miniature Low Value									
Electrolytic Axial Leads -10% to +50% Tol				High Ripple, IEC Grade 1, Low E.S.R. Supplied complete with Vertical Fixing Clip				Polystyrene, Axial, ±1% Tol., > 63V D.C. Wkg									
µF	V d.c.	16	25	2200 µF	16V	2.6A	3.6A	1.0	424	632	630	629	nF	424	632	630	629
1.0				4700 µF	16V	2.6A	3.6A	1.2					100	16	6		
1.5				10000 µF	16V	5.8A	8.1A	1.5					120	16	8		
2.2				22000 µF	16V	9.8A	13.7A	1.8					150	16	8		
3.3				2200 µF	25V	1.3A	1.8A	2.2					180	16	6		
4.7				4700 µF	25V	4.6A	6.4A	2.5					220	16	6		
6.8				10000 µF	25V	9.0A	11.2A	3.3					270	18	8		
10				22000 µF	25V	12.8A	17.9A	3.5					300	18	8		
15	7	7	8	1000 µF	40V	0.9A	1.2A	4.7	5				390	18	5		
22				2200 µF	40V	2.4A	3.3A	5.6	5				470	18	5		
33	7	7	8	4700 µF	40V	5.6A	7.8A	6.8	5				560	16	5		
47				10000 µF	40V	9.2A	12.8A	8.2	5				680	16	5		
58	8	7	10	1000 µF	70V	1.8A	2.5A	10	5				820	16	5		
100	8	8	12	2200 µF	70V	4.0A	5.6A	12	5				1000	16	5		
150	8	9		4700 µF	70V	7.5A	10.5A	15	5				1200	16	5		
220	12			1000 µF	100V	4.0A	5.6A	18	5				1500	18	6		
330				2200 µF	100V	7.8A	10.9A	22	5				1800	18	6		
470								27	5				2200	18	6		
680	19	28	36					33	5				2700	18	6		
1000	23	28	55					39	5				3300	18	6		
1500	32	36						47	5				3900	18	6		
2200	38							56	6				4700	23	7		
								68	6				5600	23			
								82	6				6800	23			
													8200	23			

Tantalum Bead				Electrolytic Radial Leads				Trimmers				
-20% Tol.				-10% to +50% Tol.				250V D.C. Wkg. Film Dielectric, Miniature				
µF	V d.c.	3.15	6.3	µF	V d.c.	6.3	10	1.4 - 4.1pF	19	Cap 808 A	.8 - 3.8pF	46
.01				.47				2 - 8pF	19	Cap 808 B	.8 - 6.8pF	48
.015				.68				2 - 20pF	21	Cap 808 C	1 - 13pF	61
.022				1.0				5.5 - 59.5pF	29	Cap 808 D	1.7 - 19.7	62
.033				1.5								
.047				2.2								
.068				3.3								
.1				4.7								
1.5				6.8								
2.2				10								
3.3				15								
4.7				22								
6.8				33								
10				47								
15				68								
22				100								
33				150								
47				220								
68												
100												

VERO ELECTRONICS PRODUCTS

2.5" x 5", 1" pitch Veroboard	59	VERO 21069J
3.75" x 5", 1" pitch Veroboard	56	VERO 21072D
2.5" x 1", 1" pitch Veroboard (5)	70/Pack	VERO 21076C
3.75" x 5", 1" pitch Plain Board	56	VERO 21078E
5.82" x 2.9", 1" pitch V-Q DIP Board	111	VERO 21094E
Spot Face Cutter	99	VERO 21013A
Pin Insertion Tool for .040 type pin	122	VERO 21015F
DS Pins .040 (100)	38/Pack	VERO 21087G
SS Pins .040 (100)	38/Pack	VERO 21017B
8mm Board Standoff (100)	181/Pack	VERO 21321K
15mm Board Standoff (100)	215/Pack	VERO 21322D
19mm Board Standoff (100)	226/Pack	VERO 21323D
Verovire Kit 11 open, 2 wire, 25 comb	375/Kit	VERO 21341D
Verovire Combs (100)	407/Pack	VERO 21339F
Verovire Wire (4)	228/Pack	VERO 21340G
Flip Top Box, Small, Black	192	VERO 21317D
Flip Top Box, Large, Black	250	VERO 21319J

HARDWARE

D.I.L. Sockets		Order Code	
8 Pin Low Profile Socket Tin	11	DIL SKT 8	
14 Pin Low Profile Socket Tin	13	DIL SKT 14	
16 Pin Low Profile Socket Tin	14	DIL SKT 16	
24 Pin Low Profile Socket Gold	15	DIL SKT 24	
28 Pin Low Profile Socket Gold	78	DIL SKT 28	
40 Pin Low Profile Socket Gold	127	DIL SKT 40	

Heatsinks		Order Code	
Individual Type for 1 x T05 50°C/W	10	Sink SF	
Individual Type for 1 x T06 10.5°C/W	26	Sink TV2	
Individual Type for 1 x T03 7.2°C/W	24	Sink TV3	
Individual Type for 1 x T0126 17°C/W	23	Sink TV4	
Individual Type for 1 x T0220 17°C/W	23	Sink TV5	

P.C.B. Components		Order Code	
Date Pen, Blue Ink, Slow Drying	92	Pen 33PC	

Fuseholders		Order Code	
Suit 20mm x 5mm fuses		Fuse/H20B	
P.C.B. Mounting, Open Type	8	Fuse/H20C	
Chassis Mounting, Open Type	17	Fuse/H20P	
Panel Mounting, Screwdriver Slot	77	Fuse/H20T	
Panel Mounting, Finger Release	56	Fuse/H20P	

Fuses		Order Code	
20mm x 5mm Glass		Fuse 20	
Quick Blow, Range 100mA-5A	8	A/S Fuse 20	
Slow Blow, Range 250mA-5A	22		

Lampholders, Panel Mounting		Order Code	
Similar in Style to Fuse/H 20P		Lamp LV	
Low Voltage Type Suits LES and M/F Bulbs		Lamp N	
Low Voltage, Red, Amber or Green	75		
Internal Neon 200/240V Red or Amber	95		

Bulbs, Low Voltage, L.E.S.		Order Code	
6V, 0.36W; 6.5V, 1W; 14V, 0.75W	22	Bulb LES	

RESISTORS

Carbon Film, Fixed		Order Code	
0.25W, E24 Values IRD-10M, 5% Tol.	1.5 ea.	90p/100 (Mult 10/Value)	E7.90/1000 (Mult 100/Value)
0.5W, E12 Values IRD-4M7, 10% Tol.	2 ea.	1.25p/100 (Mult 10/Value)	E10.10/1000 (Mult 100/Value)

Metal Film, Fixed		Order Code	
0.5W, E24 Values, SR1-H, 2% Tol.	6 ea.	3.80/100 (Mult 10/Value)	E32.40/1000 (Mult 100/Value)
2.5W, E12 Values 10R-27K, 5% Tol.	13 ea.	7.90/100 (Mult 10/Value)	

Metal Glaze, Fixed		Order Code	
0.5W, E24 Values, IM-33M, 5% Tol.	10 ea.	5.40/100 (Mult 10/Value)	

Skeleton Presets, Miniature

0.1W, E3 Values, 100R-1M, Lin. Vertical Mounting	7	Min Preset V
0.1W, E3 Values, 100R-1M, Lin. Horizontal Mounting	7	Min Preset H

Skeleton Presets, Standard

0.3W, E3 Values, 100R-4M7, Lin. Vertical Mounting	10	Std Preset V
0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting	10	Std Preset H

Potentiometer, Rotary

0.5W, E3 Values, 1K-2M Lin.	34	Pot Lin
0.25W, E3 Values, 4K7-2M Log.	34	Pot Log

ACCESS
BARCLAYCARD
CASH
CHEQUE

- FREEPOST ON ORDERS
- VAT INCLUSIVE PRICES *
- ADD 30p P&P
- 24 HR TELEPHONE ANSWERING SERVICE

GMTELECTRONICS B

Freepost

Birmingham B19 1BR

TEL ORDERS WELCOME

★ DUE TO VAT INCREASE PLEASE ADD 5% TO ORDERS

DIGITAL INTEGRATED CIRCUITS

4000 Buffered CMOS - High Speed

5-15V 'B' Series, Up to 20MHz

7400 T.T.L.

HEF4000	14	HEF4046	100	HEF4514	250	N7400N	9	N7444N	83	N74122N	39	N74102N	60	N74LS28N	32	N74LS138N	85	N74LS253N	105
HEF4001	14	HEF4047	87	HEF4515	299	N7401N	11	N7445N	65	N74123N	37	N74194N	80	N74LS30N	16	N74LS139N	85	N74LS257N	104
HEF4002	14	HEF4048	28	HEF4518	90	N7402N	11	N7446A	62	N74125N	32	N74195N	79	N74LS32N	24	N74LS153N	76	N74LS281N	107
HEF4006	95	HEF4050	28	HEF4517	382	N7403N	11	N7447A	51	N74126N	32	N74198N	120	N74LS33N	32	N74LS154N	122	N74LS260N	26
HEF4007	14	HEF4051	69	HEF4518	69	N7404N	12	N7448A	44	N74128N	74	N74199N	139	N74LS37N	24	N74LS158N	80	N74LS261N	300
HEF4008	30	HEF4052	72	HEF4519	55	N7405N	12	N7449N	13	N74132N	40	N74221N	160	N74LS38N	24	N74LS159N	80	N74LS266N	40
HEF4011	14	HEF4053	72	HEF4520	85	N7406N	25	N7451N	13	N74145N	60	N74279N	116	N74LS40N	22	N74LS157N	54	N74LS273N	130
HEF4012	14	HEF4066	37	HEF4521	188	N7407N	27	N7453N	15	N74147N	125	N74298N	200	N74LS42N	53	N74LS160N	60	N74LS279N	116
HEF4013	32	HEF4067	380	HEF4528	99	N7408N	93	N7454N	13	N74148N	83	N74365N	150	N74LS51N	22	N74LS161N	120	N74LS290N	90
HEF4014	84	HEF4068	14	HEF4532	120	N7409N	13	N7460N	13	N74150N	65	N74366N	150	N74LS54N	16	N74LS161N	78	N74LS293N	100
HEF4015	60	HEF4069	14	HEF4534	510	N7410N	11	N7470N	26	N74151N	46	N74377N	120	N74LS55N	22	N74LS162N	130	N74LS298N	100
HEF4016	35	HEF4070	14	HEF4539	110	N7411N	18	N7472N	22	N74153N	55	N74388N	150	N74LS73N	29	N74LS163N	78	N74LS324N	170
HEF4017	55	HEF4071	14	HEF4543	155	N7412N	17	N7473N	23	N74154N	96	N74399N	150	N74LS75N	40	N74LS164N	90	N74LS325N	105
HEF4018	65	HEF4072	16	HEF4555	78	N7413N	23	N7474N	23	N74155N	53	N74400N	150	N74LS76N	33	N74LS170N	200	N74LS366N	105
HEF4019	46	HEF4073	16	HEF4556	78	N7414N	26	N7475N	28	N74156N	48	N74411N	150	N74LS78N	33	N74LS171N	100	N74LS367N	105
HEF4020	98	HEF4075	16	HEF4557	386	N7416N	22	N7476N	26	N74157N	49	N74422N	150	N74LS83A	15	N74LS174N	100	N74LS368N	105
HEF4021	85	HEF4076	35	HEF4565	97	N7417N	22	N7480N	43	N74158N	54	N74433N	150	N74LS85N	70	N74LS175N	100	N74LS373N	150
HEF4022	82	HEF4077	14	HEF4574	171	N7420N	11	N7483N	63	N74160N	74	N74444N	150	N74LS92N	33	N74LS181N	320	N74LS374N	150
HEF4023	14	HEF4078	16	HEF4097	90	N7421N	26	N7485N	85	N74161N	74	N74455N	150	N74LS93N	16	N74LS190N	91	N74LS375N	100
HEF4024	45	HEF4081	16	HEF4098	73	N7425N	27	N7486N	23	N74162N	74	N74466N	150	N74LS94N	16	N74LS192N	70	N74LS378N	160
HEF4025	14	HEF4082	16	HEF4099	62	N7426N	22	N7489N	30	N74163N	74	N74477N	150	N74LS95N	23	N74LS193N	128	N74LS383N	35
HEF4027	32	HEF4085	64	HEF4106	119	N7427N	22	N7491A	30	N74164N	65	N74488N	150	N74LS98N	16	N74LS195A	130	N74LS390N	170
HEF4028	52	HEF4086	64	HEF4101	119	N7428N	30	N7492N	33	N74165N	65	N74499N	150	N74LS99N	22	N74LS196N	116	N74LS393N	170
HEF4029	60	HEF4093	50	HEF4102	119	N7430N	11	N7493N	31	N74166N	93	N74510N	150	N74LS101N	16	N74LS197N	38	N74LS395N	180
HEF4030	46	HEF4094	175	HEF4103	119	N7432N	21	N7494N	74	N74170N	134	N74521N	150	N74LS102N	22	N74LS199N	38	N74LS399N	180
HEF4031	26	HEF4104	166	HEF4104	119	N7433N	30	N7495A	48	N74171N	111	N74532N	150	N74LS103N	23	N74LS200N	40	N74LS400N	180
HEF4035	110	HEF4502	91	HEF4105	119	N7437N	21	N7496N	46	N74174N	63	N74543N	150	N74LS104N	38	N74LS201N	38	N74LS401N	180
HEF4040	68	HEF4505	571	HEF4106	140	N7438N	21	N74100N	88	N74175N	62	N74554N	150	N74LS105N	38	N74LS202N	38	N74LS402N	180
HEF4041	75	HEF4508	51	HEF4107	140	N7439N	60	N74107N	25	N74180N	80	N74565N	150	N74LS106N	24	N74LS203N	40	N74LS403N	180
HEF4042	54	HEF4510	70	HEF4108	119	N7440N	12	N74109N	42	N74181N	165	N74576N	150	N74LS107N	16	N74LS204N	40	N74LS404N	180
HEF4043	78	HEF4511	110	HEF4109	117	N7442N	40	N74116N	148	N74182N	69	N74587N	150	N74LS108N	22	N74LS205N	40	N74LS405N	180
HEF4044	94	HEF4512	98			N7443N	79	N74121N	23	N74183N	65	N74598N	150	N74LS109N	24	N74LS206N	37	N74LS406N	180

LINEAR INTEGRATED CIRCUITS

CA3011	92	NE592K	162
CA3018	75	RC4136	130
CA3020	191	TBA1205	79
CA3026A	96	TC4580	346
CA3046	76	TC4720	450
CA3048	245	TC4740	450
CA3080E	70	TOA1008	326
CA3089E	253	TOA1022	648
CA3130E	90	TOA1028	338
CA3140E	38	TOA1029	338
CA3189E	266	TOA1034B	217
LM301AN	30	TD2581	266
LM308N	95	TD2640	292
LM318N	200	TL081CP	75
LM319N	216	TL084CN	140
LM324N	216	UA709CT	46
LM339N	71	UA709CN	40
LM381N	110	UA710CN	41
LM381AN	180	UA711CN	65
LM382	120	UA714CT	42
		UA714CN	18
		UA747CN	50
		UA748CN	35

OPTO ELECTRONICS

Light Emitting Diodes, Individual		Order Code
.125" (3mm)	Red	14 CQY54
	Green	17 CQY95
	Yellow	19 CQY97
Panel Mounting Clip to suit.		3 LED3 Clip
.2" (5mm)	Red	5 CQY24A
	Green	17 CQY94
	Yellow	19 CQY96
Panel Mounting Clip to suit.		5 LED5 Clip
Light Emitting Diodes - 7 Segment Display		
.3" (7.6mm) C. Anode R.H. Decimal Pt. Ref.		160 XAN3061
C. Anode R.H. Decimal Pt. Green		199 XAN3051
C. Cathode R.H. Decimal Pt. Red, Low current drain		160 XAN3074
.8" (15.2mm) C. Anode L.H. Decimal Pt. Red		230 XAN6620
C. Anode L.H. Decimal Pt. Green		230 XAN6520
C. Cathode L.H. Decimal Pt. Red		230 XAN6640
Photoreistors		
ORP12		90 ORP12
ORP61		90 ORP61
Phototransistors		
OCF21		180 OCF21
BPX25		175 BPX25
BPX29		175 BPX29
Photocoupler		
FCD820		150 FCD820

SWITCHES

Miniature Toggle - Honeywell		Order Code
SPDT	C/O/O	2A/250V A.C., 5A/28V D.C.
SPDT	Double Bias To Centre	58 SW 8A1011
SPDT	Single Bias To Centre	67 SW 8A1021
DPDT	Bias	75 SW 8A1041
DPDT	C/O/O	76 SW 8A1051
DPDT	Double Bias To Centre	77 SW 8A1061
DPDT	Single Bias To Centre	80 SW 8A2011
DPDT	Bias	92 SW 8A2021
		99 SW 8A2041
		96 SW 8A2061
Miniature Push - C & K		
SP	Push To Make, Momentary	0.5A/250V A.C., 1A/28V D.C.
SP	Push To Break, Momentary	54 SW 8531
		54 SW 8533
Slide - Switchcraft		
OPDT	Standard Actuator	36 SW 46206
DPDT	Slide Actuator, Voltage Change, Marked 110/240	43 SW 46206F

SEMICONDUCTORS

Diodes							
IN827	393	IN4006	7	BB110G	61	OA202	9
IN914	4	IN4007	8	BY127	15		
IN916	5	IN4148	3	BY206	34		
IN921	4	IN4001	15	BYX10	19		
IN4002	4	IN4004	16	OM47	10		Microwave
IN4003	6	5AX13	5	OA90	7	BAW95D	1091
IN4004	6	BAV38	27	OA91	7	CL8960	2592
IN4005	7	BB106(4)	122	OA200	9	CX11YC	1280
Zener Diodes							
400-mW C4V7-C33		1.3W CV75-C75					
BZV88/BZX79 + Voltage	8	BZX61 + Voltage	16				
Transistors							
2N929	37	2N4427	206	BC478	24	6SK88	18
2N1993	30	2N4556	158	BC547	12	NJ340	48
2N215A	28	2N4558	134	BC548	10	MPE102	32
2N2222	21	2N4850	122	BC548B	15	OC28	107
2N2369	19	2N5294	43	BC549	12	OC35	95
2N2369A	20	2N5416	108	BC549B	20	OC45	82
2N2646	42	2N5457	35	BC557	14	OCF71	180
2N2694	29	2N5458	30	BC558	14	TIP29A	41
2N2895	28	2N5459	32	BC559	17	TIP29C	53
2N2904	24	2N6258	432	BCY34	97	TIP30A	44
2N2904A	40	40673	80	BCY70	10	TIP30C	57
2N2905	22	AC188	22	BCV71	14	TIP31A	43
2N2905A	24	AD161	38	BCV72	15	TIP31C	58
2N2906	19	AD162	38	BD131	35	TIP32A	49
2N2907	22	BC107	10	BD132	35	TIP32C	63
2N2907A	25	BC107B	14	BD135	38	TIP41A	59
2N2918	330	BC108	10	BD136	37	TIP41C	69
2N2926	11	BC108B	14	BD137	38	TIP42A	59
2N3053	17	BC108C	16	BD138	39	TIP42C	69
2N3054	50	BC109	10	BD139	35	TIP295	68
2N3054A	141	BC109B	17	BD140	35	TIP3055	54
2N3055	50	BC109C	18	BF115	28	TIS43	32
2N3055A	7	BC147	7	BF180	37	ZTX109C	14
2N3055B	86	BC148	9	BF181	37		
2N3340	30	BC149	8	BF257	35		
2N3342	141	BC157	10	BF258	37		
2N3702	8	BC158	9	BF259	36		
2N3703	11	BC159	11	BF290	303		

Monitor



LASERISED LETTERS

If you can tear your eyes away from the photograph for one minute we'll tell you all about laser printing. The machine on the right is an extremely sophisticated laser printer. Now for some pretty impressive statistics (it's all in the mind) how about 10,000 personalised letters per hour of 20,000 lines of type per minute. The big bonus in using such a technique is the ability to personalise each and every letter with the recipient's name — cheaply. This means that there's a strong possibility that those endless circulars that come through your letter-box could have your name on it.

Laserprint, the company responsible, have already tried a test sample of 10,000 letters, half of them personalised, to see whether having your name on a letter or circular makes any difference to the response and it appears that it does. So next time you get a letter from one of those mail order companies with your name on it, don't just throw it straight in the bin, look at it, it may have been printed by laser, now you can throw it in the bin.

SMOKEY BEARS GET NEW RIGS



No, they're not CBs, they're the all new Motorola VHF MX350 hand portable transceivers recently delivered to the Fife constabulary, 60 in all, to replace their ageing existing equipment. All the new units are two-channel switchable and such is their durability that during the evaluation period not one fault occurred to the 12 sets used. The transceivers deliver 2.5 watts RF into the antenna, mounted on a remote mike/speaker to avoid body absorption of RF. The internal rechargeable batteries will last approximately 8 hours under normal conditions and can be fully recharged within 1 hour. There, we've resisted the temptation to make any jokes about CB, and any suggestions that the officer in our picture is saying "Breaker One Four," are totally untrue.



NEW PICTURE BOX

For the first time JVC have introduced a video cassette recorder with slow motion facility. The new machine rejoices under the title HR-3660. (We are starting a campaign to get manufacturers to think up more inspiring names for their products).

All the now standard features are to be found, audio dubbing, 8 day digital clock/timer and 3 hour recording capacity. The slow-motion feature has a variable speed and even a freeze capability to stop the recording on any selected frame. There is also a speed up facility (double speed) to allow the viewer to

whizz through the irrelevant or boring bits, a speech compression circuit ensures that speech is still understandable even at double speed.

As an added bonus the HR-3660 has a wired in remote control unit that operates most of the recorders functions. The VHS format on this machine is fully compatible with other 1/2" VHS recorders and will accept an input from a variety of colour cameras. No price as yet, the launch date will be September so any enquiries can be made to; JVC (UK) Ltd, Eldonwall Trading Estate, Staples Corner, 6-8 Priestley Way, London, NW2 7AF.


News from the Electronics World

MONEY BOX

What does time-money and mortgage loan calculations? Give up? How about compound interest, annuities, investment yields schedules, accumulated interest, and principle interest splits, (whatever they may be)? If you understood all that chances are you're in the market for Texas's new financial button box. The TI-44 is the first multi-mode slimline calculator in the UK with pre-programmed financial, profit margin, and statistical functions.

The TI-44 has a constant memory feature, retaining information even when switched off. Something called APD (Automatic Power Down) turns the calculator off automatically after seven minutes of non-use, battery life should be around 1 000 hours under normal conditions.

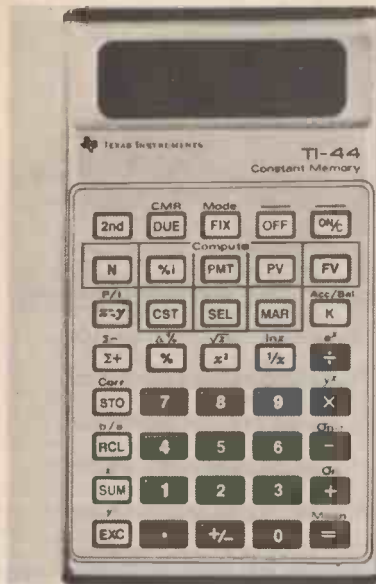Now its our turn for statistics, weight 85 grammes, size, 13.5 by 7.4 by 0.69 centimetres. Complete with carrying case and manual it has a suggested retail price of £36.95 (inc VAT). It should be available now from your local calculator stockist.



CLASSY CASIO

Casio must have taken our recent comments on the lack of new calculators to heart, we're almost back to our old level of five a month. Stories of new machines are coming in thick and fast. Latest arrival is the JR-110 (Casio are nearly the worst offenders when it comes to naming their products, we'll start our campaign with them). This little box (only 24 x 13 x 5 cm) has a lot of useful features. The mini-printer is backed up by a ten digit display, a plethora of mathematical functions and all powered by four penlight batteries or optional AC adaptor.

A nice touch is the inclusion of a switch to turn off the keyboard when not in use (these puns are getting worse!). Recommended retail prices which are usually quite meaningless are; £74.95 for the JR-110 and £64.95 for the JR 101 which does not have a separate display. Casio can be found at their usual address which is: 28 Scrutton Street, London EC2A 4TY.



DIGITAL DEFENCE

Something new in car protection from across the big pond. It is blessed with the name 'Steal Stopper' and comprises a small keyboard attached to your dashboard. Upon entering the car it must be fed with a secret four digit code. Providing the correct code is entered it will enable the car's ignition. The system will also prevent the ignition from being 'Hot Wired' from inside the car; a possible 11 880 combinations will effectively remove any 'lucky guessers' from pinching your car. The system can also be disengaged by pressing a further code to enable the car to be parked in garages or attendant operated car-washed (must be American). Price over here is £29.95 from Kramer and Co., 9 October Place, Holdershill Road, London NW4 1EJ.

KIT CAT

T. K. Electronics, the people who supplied us with this month's Kit Review sample have also shown us their latest catalogue and very interesting reading it makes too. T. K. stock a good selection of most common components and a few uncommon ones too — all at reasonable prices. It is always good to see a large data content in these catalogues, these small touches make them very useful additions to your library. The last few pages of the catalogue are devoted to TK's range of kits. They seem to specialise in lighting control, from disco to domestic, we were very impressed with the Touch controlled light dimmer. For your copy write to T. K. Electronics; 106 Studley Grange Road, London, W7 2LX.

LED ASTRAY

Have you ever wondered why you've never seen blue LEDs? Now for the first time the truth can be told — they're very difficult to make. Several large companies have for some time been engaged in trying to develop blue LEDs, mostly with little success. One company however, Siemens have not given up and are rumoured to be very close to producing blue LEDs on a commercial basis. One problem has dogged the LED story from the beginning, the materials used, Expital Silicon Carbide (SiC for short) are difficult to produce in sufficient quantity in the correct size. The crystals used need to be quite large physically, around 1 square centimetre.

As with all research, 'mother is the necessity of invention.' Perhaps if sufficient demand for blue LEDs existed it would hasten their development. We at HE ever keen to help in such matters would like to suggest that, if the Police could be persuaded to place a large enough order, possibly for indicator lamps on their walkie-talkies, their introduction to the general public could be that much sooner.

ERRATA 1

The Combination lock in the September issue (it does work, really) had a couple of errors on the wiring of SW1 and SW2. They are as follows: connection D now goes to tag 1 on SW2, connection F now goes to tag 11 on SW2, C to tag 8 on SW1 and E to tag 4 on SW2.

In the how it works, first paragraph RS now reads R3, third paragraph R7 now reads R5, fifth paragraph R10, is now R8, final paragraph, the bypass capacitors ar C3, C6 and C8 and R11 should read R9. Thanks to Mr R. Bleach for his prompt assistance and be assured that heads will roll.

ERRATA 2

The Ultra Switch nearly escaped but not quite. One thing to look out for however was the values of C5 and C6 on the Ultra-Switch (Page 46, 47) the values shown on the parts list are correct, the decimal point slipped a little on the circuit diagram.

ERRATA 3


We just caught this one in time, on the overlay for Starburst (Sept HE page 26) one or two of the proverbial gremlins did their worst. R 14, 13 and 12 should now read R 7, 8, 9. The connections for 9 V and 0 V are back to front. Sorry again.

The latest kit innovation!

from Sparkrite

*Sparkrite -
has featured by Shaw Taylor
in "DRIVE IN"*

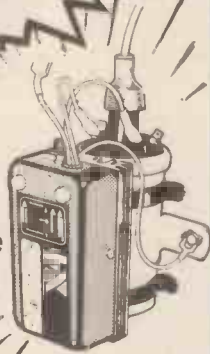the quickest fitting
CLIP ON
capacitive discharge
electronic ignition
in KIT FORM



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE - Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £4.25 inc. VAT, post & packing.

Electronics Design Associates, Dept. HE10
82 Bath Street, Walsall WS1 3DE. Phone: (9) 614791.

Name

Address

Phone your order with Access or Barclaycard

Including postage and packing UK only

QUANTITY REQ'D.

Send SAE if brochure only required

X4 KIT £17.95 inc. VAT

TACHO PULSE SLAVE UNIT
£4.25 inc. VAT

I enclose cheque/PO's for


£

Cheque No.

Access or Barclaycard No.

S. & R. BREWSTER LIMITED

WHY PAY MORE?

	PRICE EACH	P & P Extra EACH
 18 watt Soldering Iron available in 12, 110 & 240 Volts, fitted with No. 20 bit	£4.43	+ 24p
SPARE BITS No. 19 size 1.5mm or No. 20 size 3 mm or No. 21 size 4.5 mm or No. 22 size 6 mm	52p	—
No. 78. I.C. Desoldering Bit	£1.04	+10p
No. 1920L Long Life Bit	£1.12	10p
SAFETY STAND	£4.23	+ 70p
SOLDER Savbit 20'	61p	+ 9p
Savbit 10'	32p	+ 5p
Lowmelt 10'	76p	+10p

INDUSTRIAL/RETAIL ENQUIRIES WELCOME FOR THE ABOVE

We also Offer & Recommend for Mail Order & Personal Callers Only

	PRICES EACH including V.A.T. and P & P
Oryx 50 Temperature Controlled Soldering Iron	£11.75
Spare tips for above	£1.39
Isotip quick charge rechargeable Soldering Iron	£24.60
Spare tips for above	£3.42
Cable 7/0.2 11 Colours 100 meter reel	£2.40
0.1 Veroboard 3 1/2" X 11 1/2"	£2.00
0.1 Veroboard 4 1/2" X 18"	£4.50
Copper Clad board single sided	75p
Watchmakers Side Cutters	£5.85
Watchmakers Pliers	£4.75
Transformer 100VA 2 X 12V 4.1A	£11.20

OTHER ITEMS ALSO AVAILABLE ASK FOR LIST S.A.E.

MAIL ORDER DEPT.
86-88 Union Street, Plymouth
PL1 3HG Tel:(0752) 65011



Please Quote your Number when ordering.



Master Electronics

The practical way

No maths needed~ No dull theory~

Step by step we take you through all the fundamentals of electronics and show you how easily the subject can be mastered.

- 1) BUILD AN OSCILLOSCOPE
- 2) READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS
- 3) CARRY OUT OVER £) EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK

Also

- We provide practical tuition for:-
- 3) Digital Electronics
 - 1) Radio amateurs licence.
 - 4) Computer Technology
 - 2) City and Guilds certificates.
 - 5) Test instrument kits

Mark your interest(s) with an x in box provided.

British National Radio & Electronics School,

NAME

P.O. Box 156, Jersey, Channel Islands

ADDRESS

HE01/10

(block caps please).

Tantrum

We've had a few mumbles and grumbles concerning the lack of audio projects in recent issues. Nuff said — up come the project boys with a first rate 25 watt stereo amplifier.

AMPLIFIER CONSTRUCTION is full of such heart-breaking terms as: — mains hum, earth loops, harmonic distortion, low signal to noise ratio etc., etc. ad nauseam. Mention any of these terms to a professional (let alone an amateur) audio engineer and you will see him turn a deep yellow colour and cower into a corner whimpering to himself or take a long, long holiday. Incidentally, this is the sort of thing which happens in our projects lab 3 or 4 times a week, hence the name of this project — TANTRUM.

Amplifier design has been known to push many a good audio engineer over the top and turn to digital circuits (the easy way out). However, we at HE have faced up to the subject with a great deal of trepidation, hard work and dutch courage and finally have the solution.

The HE TANTRUM is a stereo amplifier using good

design and construction techniques which upon completion will reward the builder with a 25 watt stereo amplifier with a signal/noise ratio of over 70 dB, negligible mains hum (due to the special construction techniques) and distortion of less than 0.1% (the human ear can't even pick that up).

Now, we don't often boast but though we say it ourselves, we have produced a printed circuit board layout for the pre-amplifier which is nothing short of superb. The distortion and noise figures for the pre-amp are remarkably low. On first sight the board might appear large but the quality obtainable using this layout far outweighs the minor disadvantage of size. Besides, the use of on-board switches and pots presents an enormous reduction in interwiring (and therefore noise levels) to be achieved. It also eases cabinet construction problems.



Inside the HE Tantrum, the modular construction results in a very neat and practical design

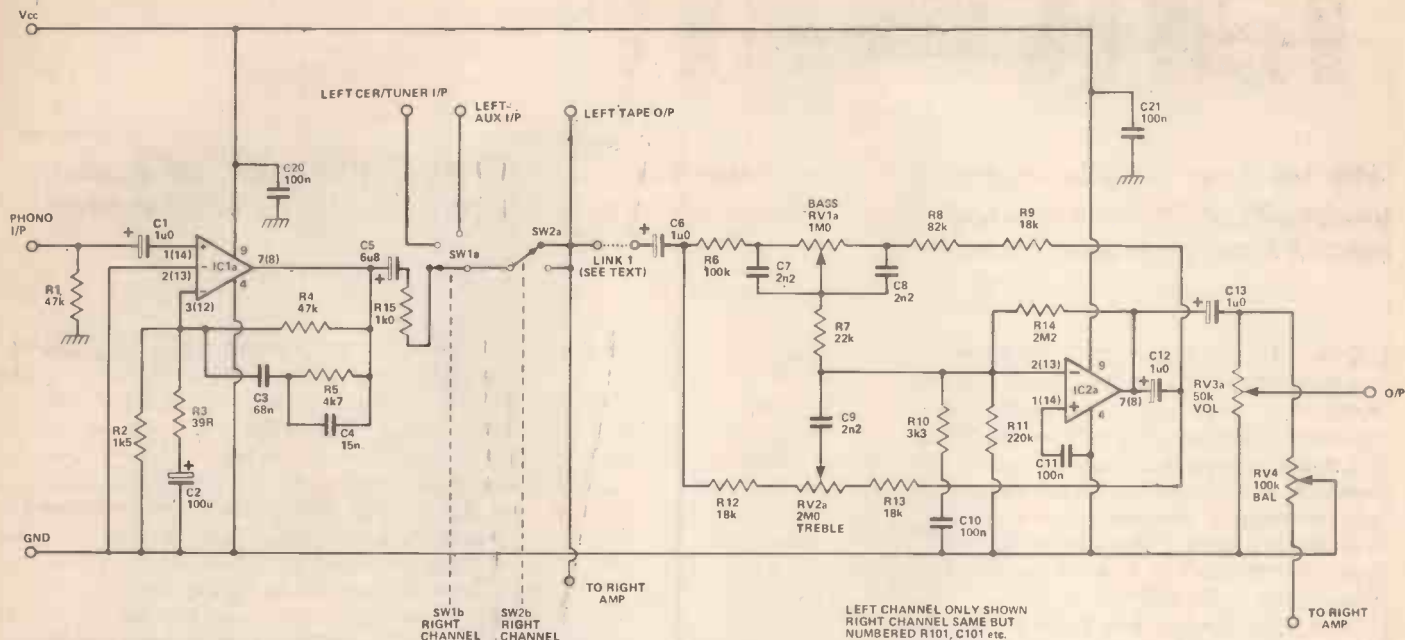


Fig. 1. Main circuit diagram for the Tantrum, only the left channel is shown

How it Works

Any audio amplifier has two basic parts to it:—the pre-amplifier and the power amplifier (three parts if the power supply is taken into account).

The pre-amplifier is a voltage amplifier dealing with low voltage inputs, for example from a magnetic phono cartridge (which produces a signal of about 5 mV). The output from the pre-amp is normally set at a few hundred millivolts, enough to drive the power amp. Tone controls and volume are normally provided in this section.

The power amp is a current and voltage amplifier, to provide the power to drive the speaker. Because the power amps in TANTRUM are modular and are bought complete and tested there is little need for circuit explanation.

The design of the pre-amp is centred around two LM 381 dual, high quality op amps. IC 1 is used as a RIAA equalisation amplifier. This is necessary

when using a magnetic phono cartridge, as certain frequencies are emphasized on the recording of a record and consequently need to be de-emphasized on playback, hence the term equalise.

The second LM 380 is used for tone control, the controls being in the standard Baxendall type circuit.

The RIAA equalization is provided for in the feed-back loop of IC1, likewise the bass and treble controls are in the feedback Loop of IC2. Equalization and tone control can be obtained using passive resistors and capacitors, but significant noise is introduced, due to voltages across these components. Theoretically, an op amp produces no current flow through the components in its feedback loop. These 'active' components produce much less noise than any type of corresponding passive circuit.

We looked around and sampled power amplifiers which might fulfill 3 criteria:—

- 1) ease of use
- 2) adequate power levels
- 3) low noise and distortion figures

Integrated circuit amplifiers tend to have high distortion figures, while discrete components (transistors, etc.) amps can get very involved and are more often than not troublesome to build — and so, for these reasons we decided on the use of purpose built amplifier modules which are obtainable ready built to high specifications. A great many such amps were discussed and researched until a suitable one was found. The chosen one is the AL 60, available from BI-PAK (See Buy-lines).

This is a power amplifier of very respectable quality which, with only one extra capacitor and a power supply will provide up to 25 watts RMS of power. The distortion and noise figures for the modules are low and, when connected, give a very acceptable sound output.

As an added extra to TANTRUM we have included links 1 and 2 in the PCB so that a remote volume control along ultrasonic principles can be used. This is planned for a future issue of HE, until then insert links 1 and 2.

CONSTRUCTION

The pre-amplifier should be constructed first. Do this very carefully. Make sure you have the correct sized

Parts List

RESISTORS (All 1/4W, 5%)

R1, 4, 101, 104	47K
R2, 102	1K5
R3, 103	39R
R5, 105	4K7
R6, 106, 108	100K
R7, 107	22K
R8	82K
R9, 12, 13, 112, 113	18K
R10, 110	3K3
R11, 111	220K
R14, 114	2M2
R201	6K8
R301, 302	270R

POTENTIOMETERS

RV1	1 Meg Dual Lin
RV2	2Meg Dual Lin
RV3	50K Dual Log
RV4	100K Single Lin

CAPACITORS

C1, 12, 13, 101	1u0 Tant 25 V
C6, 106, 112, 113	1u0 Elect 63 V
C2, 102	100u Tant 25 V
C3, 103	68n Polyester
C4, 104	15n Polyester
C5, 105	6u8 Tant 25 V
C7, 8, 9, 107, 108, 109	2n2 Polystyrene
C10, 11, 20, 21, 110, 111	100n Polyester
C201	4700u Elect 63 V
C202	10u Elect 40 V
C203	22u Elect 40 V
C301, 302	To suit speakers used

SEMICONDUCTORS

IC1, 2	LM 381
BR 201	2 Amp 100 V Bridge Rectifier
Q201	BD 131
D201	33 V Zener Diode

MISCELLANEOUS

SW1, 2	Push Button Signal Switches (DPDT) with mounting bracket
SW3	DPST Mains Toggle
Neon	
FS201	1.5A Fuse + Chassis Holder
FS202, 203	750 mA Fuse + PCB mounting holder
T201	Mains/30 V 50 VA Transformer
2 x Power Amp Modules (see Buylines)	
Case to suite	
Approximate cost £35.00.	

Buylines

All parts for the pre-amplifier, power supply and ancilliary hardware should be readily available at any reasonable component stockist. The power amplifier modules, the AL 60's are distributed solely by Bi-Pak, The Maltings, 63A High Street, Ware, Hertfordshire, who for a limited period are offering the modules to Hobby TANTRUM constructors for the greatly reduced price of £4.85 VAT inclusive. A pleasing gesture.


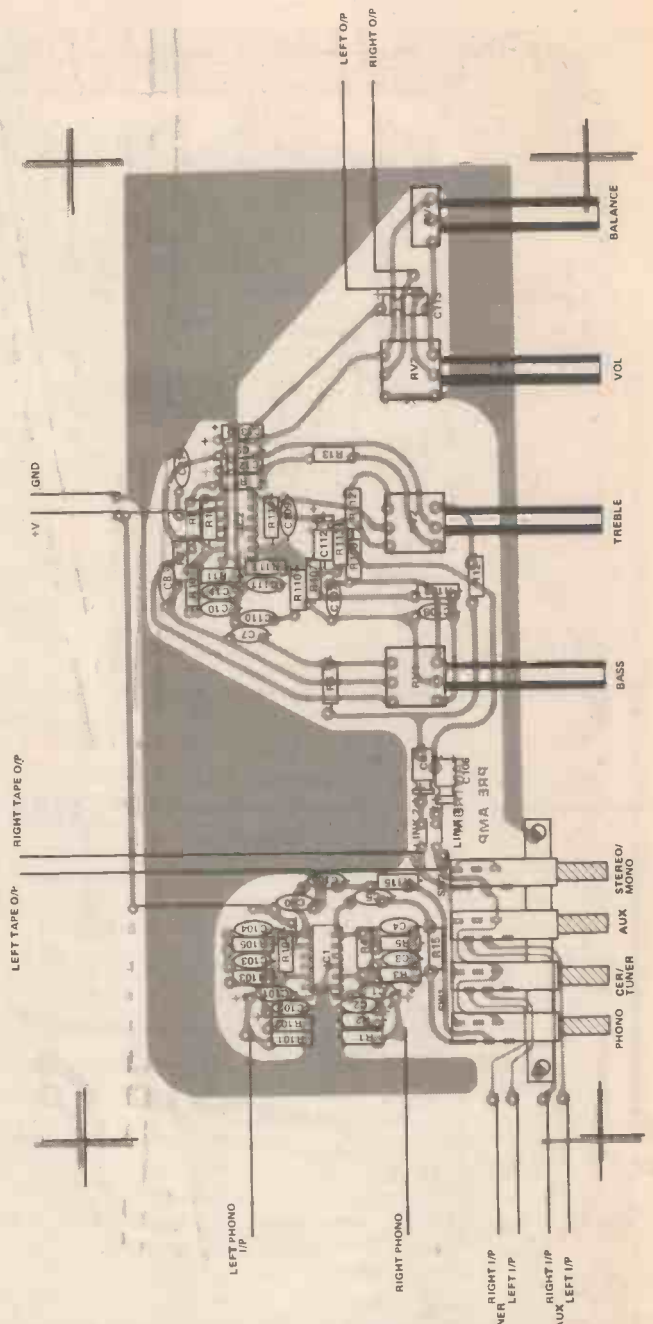


Fig. 2. Overlay diagram for Tantrums main board.

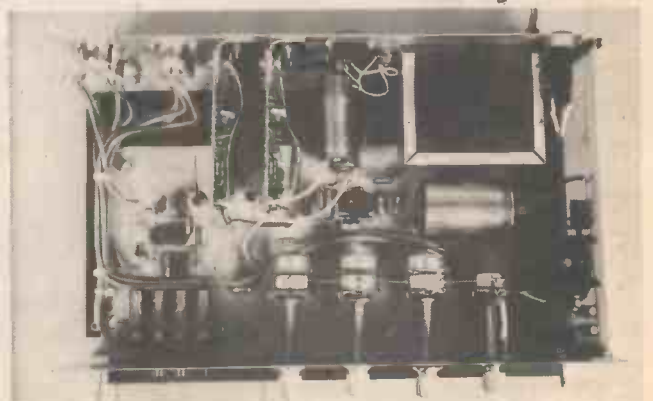

The two power amplifier modules (upper) can be seen mounted onto the rear of the case

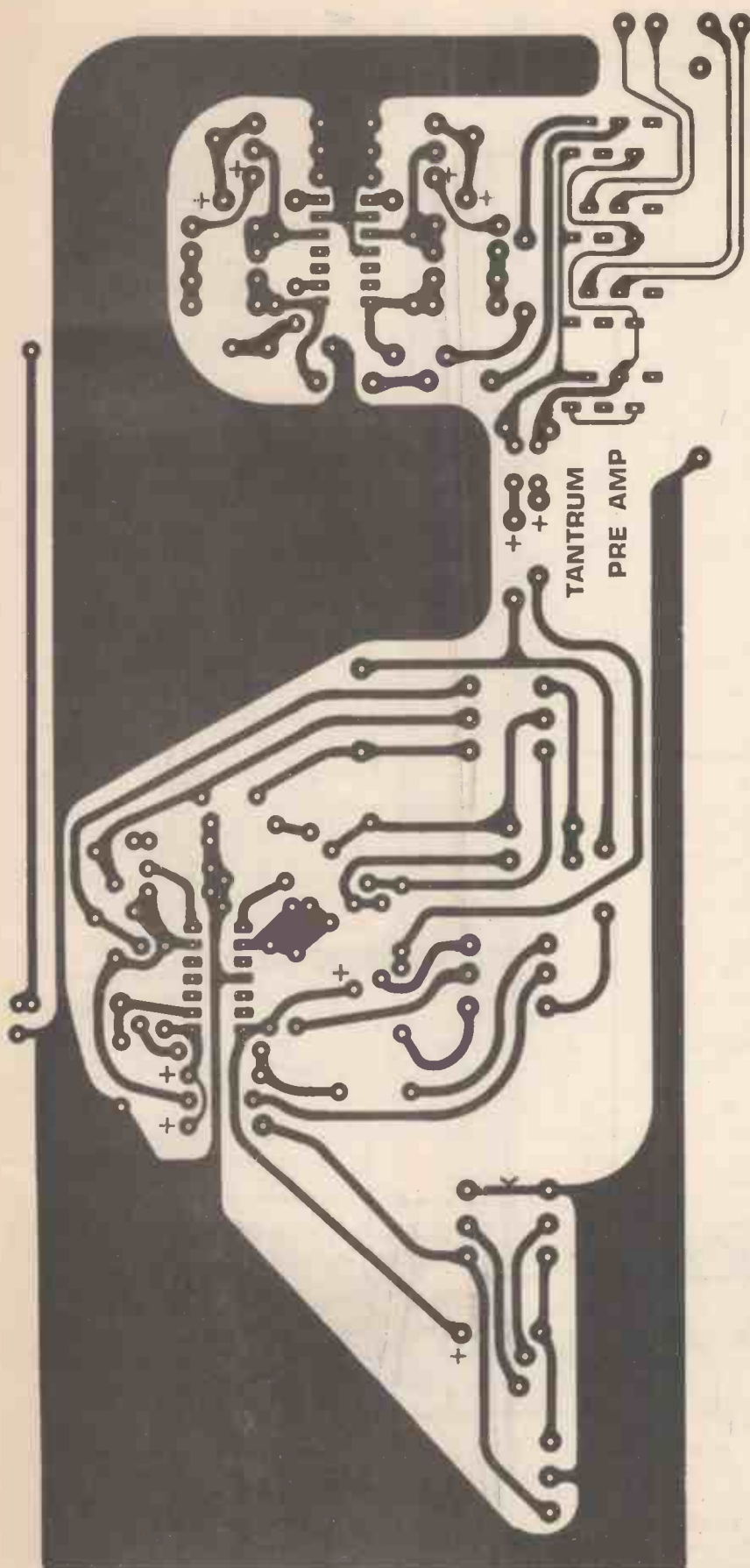


Fig. 3. PCB foil pattern for the main board.

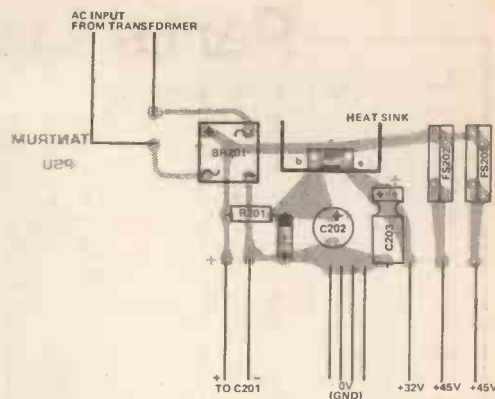


Fig. 4. Overlay diagram for Tantrums PSU.


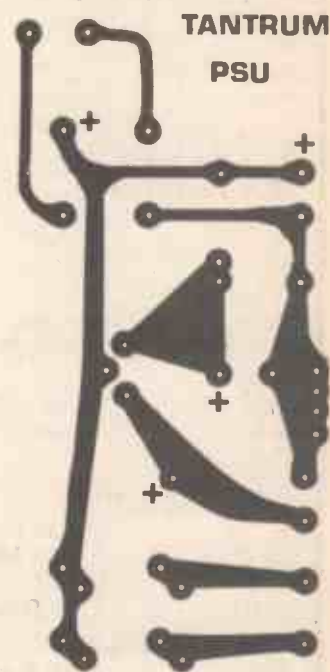


Fig. 5. PCB foil pattern for the PSU module.

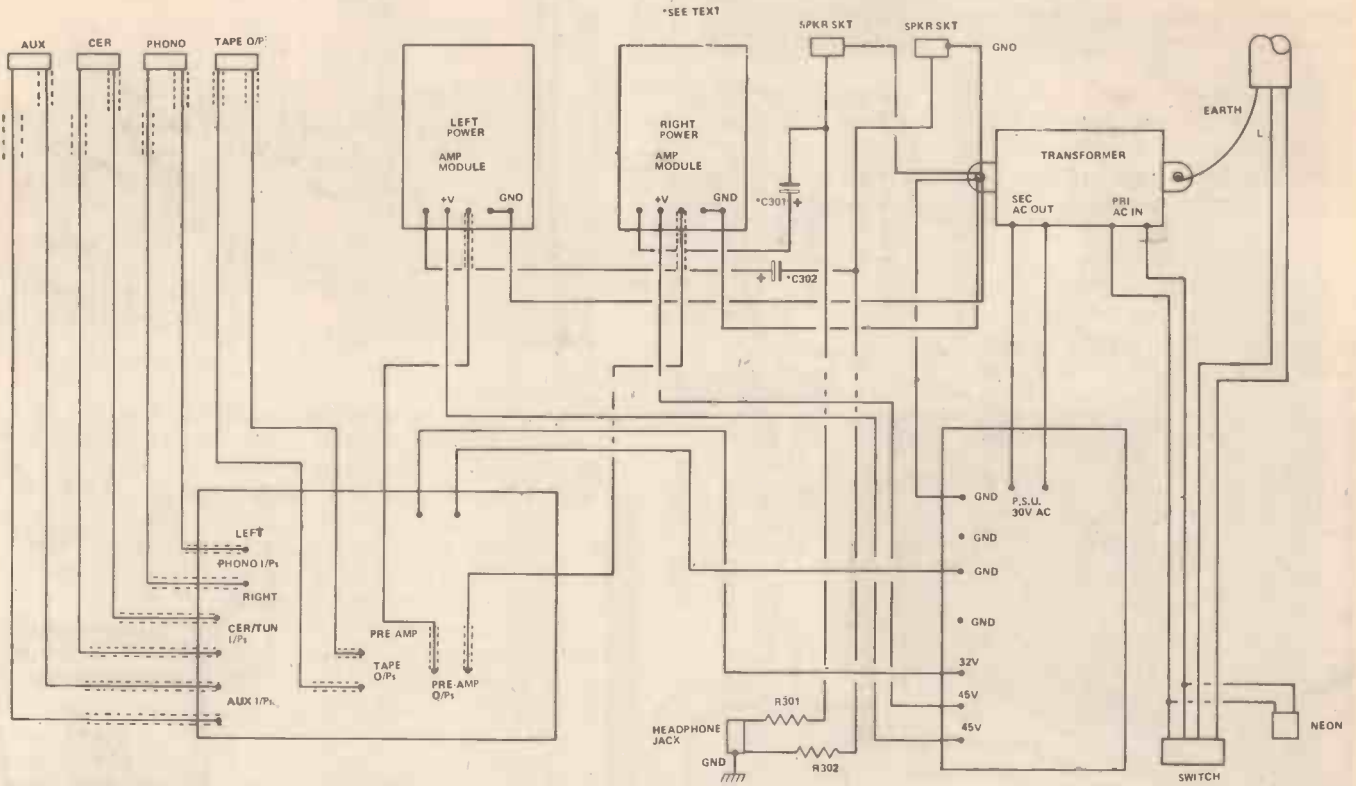

Close-up of the connections to the input sockets, note the use of screened lead



9.6
Fig. 6. Interwiring diagram for the pre-amp, PSU and power amplifier modules


FS2 and FS3, clipped into PCB fasteners which make a nice neat job, are necessary to protect the amplifiers in the case of overload.

C201 is mounted separate to the power supply board and hard-wired into circuit. This is best left until final assembly.

push button switches for SW1 and SW2 as sizes vary slightly from manufacturer to manufacturer. The on-board pots can be of the PCB type, or you can simply drill larger than average holes (1.5mm) and insert ordinary potentiometers (as we did with our prototype). To do this the tags have to be bent carefully through 90 degrees

and then shaped using pliers to fit through the PCB holes. This is a simple job and provides a suitable alternative to obtaining the more expensive, difficult to obtain PCB pots. The bodies of the pots should be all connected to earth via a length of single strand wire to provide screening.

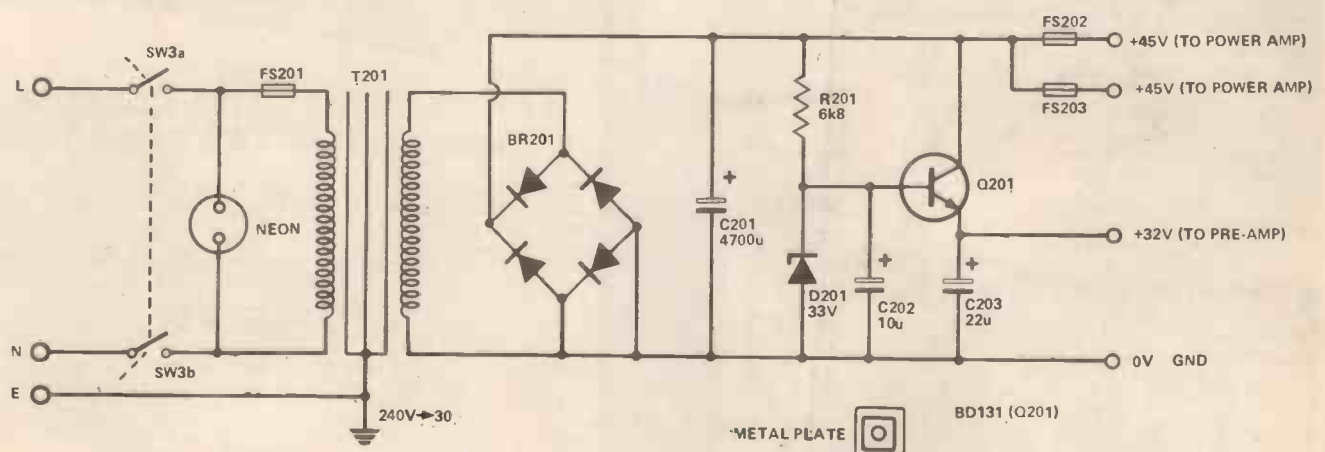Construct the power supply next — being careful that the bridge rectifier and the transistor are inserted correctly. Note the polarity of the zener diode. The heatsink should be attached to the transistor with a nut and bolt, smearing the connecting surfaces with heat-sink compound (this helps to dissipate heat) before




NOTES:
 Q201 IS BD131
 D201 IS ZENER 33V
 BR201 IS 2 AMP 100V BRIDGE RECTIFIER

Fig. 7. Circuit diagram for the PSU for Tantrum.


fastening together. Make sure the metal heatsink is not touching anything else metallic as a short circuit could result.

Note in the interwiring diagram the use of a single point earth for the power amplifiers, taken to a convenient point on the chassis (we used a transformer mounting bolt) close to the power amps. The earth return from the speakers also goes to this point. This single point earth system is used in audio equipment to minimise the effects of the high currents flowing through the leads, on the pre-amplifier.

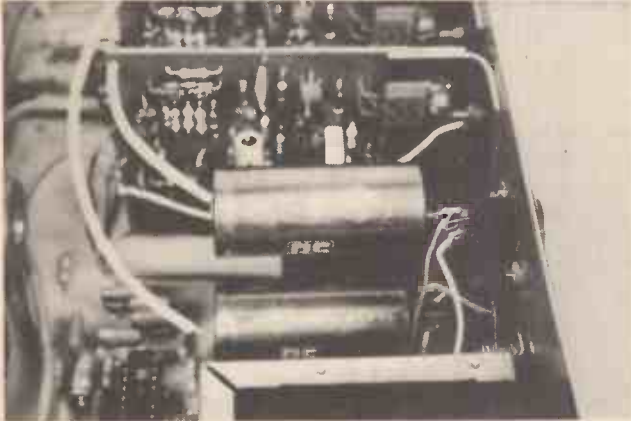Follow the inter-wiring diagram when connecting the modules. Use if possible a length of ribbon cable, colour coding each strand. This can only be used for power supply connections, power amp outputs and the leads



Close up of the power amp mounting.

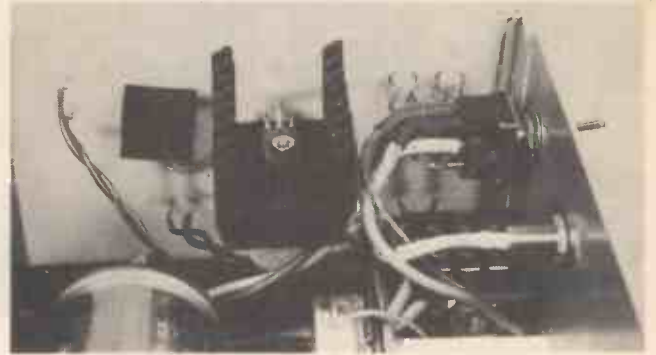

Close-up of the PSU module, note the heat-sink on the regulator

from the speaker DIN socket to the headphone jack. Any low level signal leads ie pre-amp I/P and O/P leads need to be screened low loss cable.

Finally, R301 and 302 are hard-wired in series with the left and right headphone outputs (taken from the speaker DIN sockets). These cut the power down to a reasonable level for headphones.

Full connecting instructions are supplied with the Bi-Pak modules. A capacitor has to be connected between power amp O/P and speaker DIN socket. The value of this capacitor depends upon the impedance of the speakers to be used although incorrect values will only affect the bass response of the amplifier. According to Bi-Pak information the values of C301 and C302 are 1000 uF when using 3-4 ohm speakers, 470 uF for 8 ohm speakers and 220 uF for 16 ohm.

TEE SHIRTS

We won't guarantee HE Tee-Shirts will make your soldering any better, we won't even claim it will make your projects work first time. What we will say is that it will protect your body from harmful Ultra-Violet radiation from the sun, embarrassing Tomato Ketchup stains on your hairy chest and overweight wallets (if bought as directed in sufficient quantity).

Yes folks, for just £2 all inclusive you can be the first kid on your block to own a brand new HE Tee-Shirt. If you buy more than one your torso need never be left unprotected whilst your other one is in the wash.

Send your cheque, PO or anything negotiable to:
HE TEE SHIRTS, 145 Charing Cross Rd, London WC2H 0EE.



MiniM



LET US TURN YOUR HI-FI ON with our DIGITAL TIMER

The Minim Digital Timer is an accurate 24 hour clock, with the facility to switch mains operated equipment ON and OFF at independently pre-set times; it can switch appliances up to 1.5 kW — the biggest hi-fi, TV, heaters, lights, etc. It is very easy to set the time and lights illuminate to clearly show the settings. Housed in an attractive teak veneered cabinet size 7in. x 5in. x 2in. approximately

Price £39.95

Please send me further details of your Digital Timer.

Name

Address

H1

★MINIM AUDIO LIMITED
Lent Rise Road, Burnham, Slough SL1 7NY
Telephone: Burnham 63724

Home Computing


The advent of the microprocessor has brought computer technology into the home, yet the subject remains shrouded in mystery. Peter Howells attempts to explain some of the basics.

HAVING TAKEN LEAVE OF MY SENSES for long enough to agree to write this article, and having subsequently found that there was no way out, I tried to ask myself the question, 'What makes a Home Computer different to any other computer?' The only answer that appeared was 'Nothing.' A Home Computer, it seemed to me, only became such because lots of people have

A complete, if rather tatty, computer system based on the Commodore PET. The PET consists of MPU, memory (with BASIC interpreter in ROM), keyboard, cassette drive and VDU. Also in the picture is a printer so that a permanent record may be kept of output. A setup like this can handle most requirements.

them at home. Is this a fair picture? The answer, based on a wide experience of The Way Things Are in the World, is immediately obvious, and no. Most 'Home Computers' are bought and used by schools, colleges and businesses.

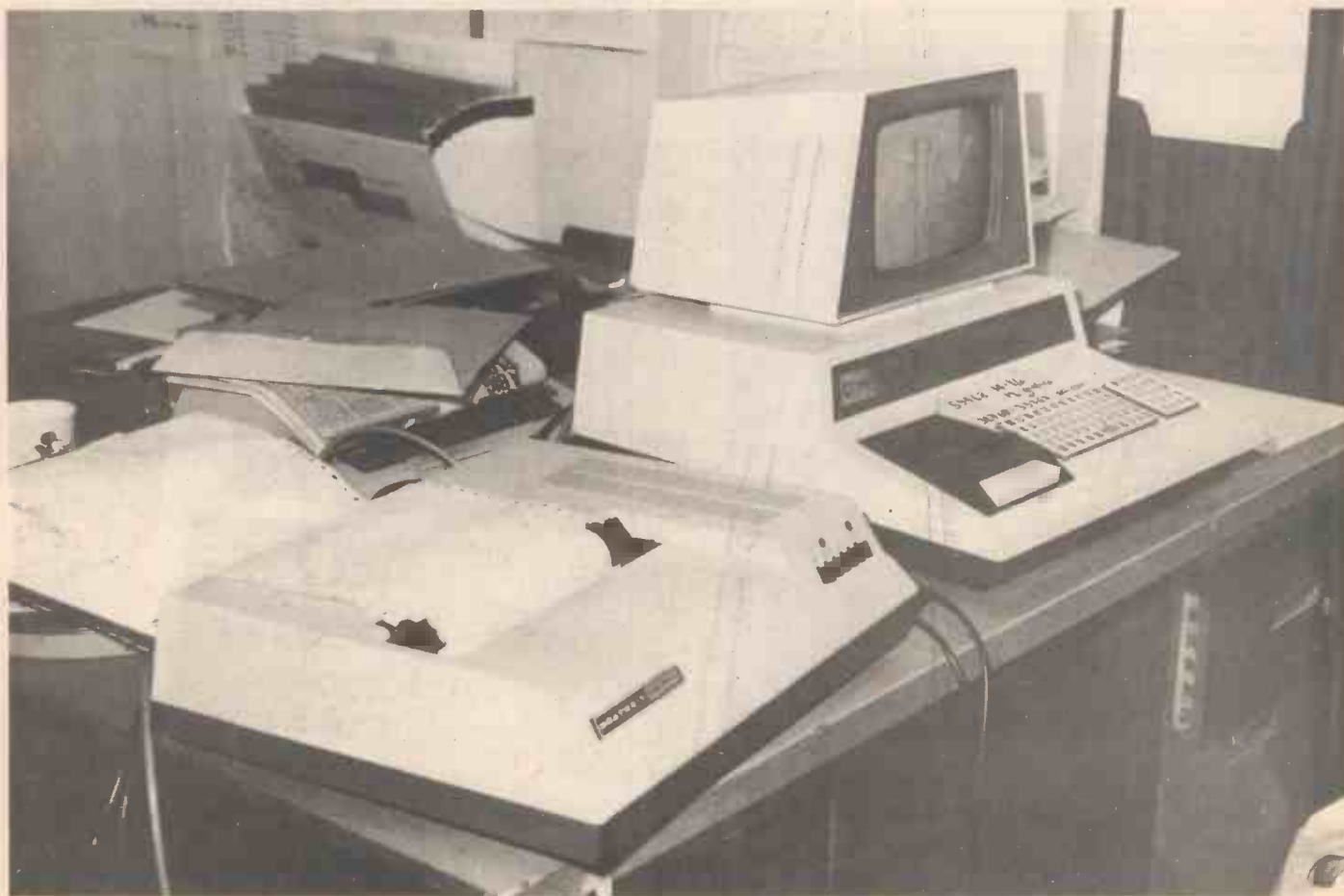The term 'Home Computer' is a misnomer, the only real justification for it being that the machines are now small enough, light enough, sturdy enough and cheap enough for people to own and use them at home. Anyhow, having got your computer home, the next question to come up is what does one do with it? The



answer is 'Anything you want.' Computers can, and have been, put to many varied uses. There is no reason why yours should not also do these things. All that needs to be done is for the necessary hardware to be hooked on and the right program loaded. And here comes the crunch; hardware tends to get expensive and programs tend to get complicated. Hardware is the mechanical end of the computing business; it refers to all the physical bits and pieces without which the computer becomes deaf, dumb and blind; keyboards, printers, TV displays, disc and cassette drives and all that. The programs, also known as 'software', are the sets of instructions which guide the computer as to how to use the hardware; when to 'listen' to the cassette, what to do about what it 'hears', and what to 'say' about what has been heard and done, say on a printer.

Neither of these aspects of computing can function without the other, and both become very closely inter-related. Both are, however, very different beasts and should, initially, be looked at separately.

HARDWARE

The heart of the small computer is the microprocessor unit (MPU). This can perform basic mathematical and logical functions on data. The data appears in the form of electrical signals representing strings of binary digits (Bits). The bits are usually arranged in sets of eight, known as a byte. The MPU must also have some form of input in order to select which of its repertoire of functions to perform on the data. This, too, is of the form of electrical signals representing bits. The mathematical

A drive for floppy discs. The magnetic disc has the advantage over tape of being much faster in use and has a much larger capacity. The unit above can take up to two discs — a most useful feature as data could be input from one, processed, and the output recorded on the other.

functions, performed in binary arithmetic, are very basic: add and subtract. Multiplication and division are

This counter is instrumental in the decision making ability of the computer. Having ascertained that a certain state of affairs exists, it may become necessary for a different course of action to be followed. The counter thus becomes reset, according to the instructions, to point to a set of instructions that deal with the situation. This is the 'jump if' type of instruction, and is what allows the computer to become rather more than a pocket calculator.

If I leave the impression that each function is pretty straightforward I am wrong. The steps within even a binary addition, to say nothing of subtraction, are numerous and convoluted: fetch the first datum, save it, fetch the second datum, add them (there are eight bits here), indicate a carry or overflow, save the answer, etc.

All the data and instructions that the MPU has access to must come from somewhere, and this is where memory comes into the picture. Memory can be, and usually is, pictured as rows of pigeon holes. Each one has a unique label, or address. The counter referred to usually done the hard way — repeated addition and subtraction. The logical functions are those of Boolean algebra: AND, OR, NOT etc. I don't intend to go into the intricacies of binary arithmetic or Boolean algebra as literature on the subjects is plentiful, but suffice it to say that the mathematical functions make possible the calculator aspect of a computer, and the logical ones give it the decision making capability. In addition to mathematics and logic, the MPU must be able to obtain the data and the instructions from the correct place and in the correct order, and there are a number of 'get' and 'put' functions to this effect. To get instructions in the correct order there will be a counter to record where in the memory (more on this later) the next instruction is.



earlier points to these addresses. 'Inside' each pigeon hole are to be found, in sets of eight, the electric signals that form either an instruction or a datum, and these can be extracted or replaced by the MPU. At least, sometimes they can.

Memory comes in two types: random access memory (RAM) and read only memory (ROM). RAM can be read, erased or replaced by the MPU. It is used for holding transitory data — totals that are changing, intermediate results of calculations or the program that is currently being run and which will be replaced by something different. ROM is used for storing fixed and unchanging data — this is usually a program, or sets of programs for performing standard jobs (such as calculating sines and cosines etc); the plug-in cartridges for many of the video games available usually consist of a ROM with the program for the game held on it. ROM has the advantage that the data held by it remains intact when the power goes off — the computer can come to life at the flick of a switch (not so long ago starting up a computer was a long job; having turned on the power the memory had to be loaded by hand, using sets of switches to set the state of each bit, with a short program which could then be run to load more memory with more complex programs; a process known as 'bootstrapping' as it was similar to the concept of pulling oneself up by one's bootstraps.) It is also worth mentioning EROMs, PROMs and their offspring EPROMs. The 'E' stands for erasable, and the 'P' for programable. A PROM can have data written to it and then have it frozen in place, usually by a high voltage charge. An EROM can have the data it contains erased, usually by exposure to ultra-violet light. It is not difficult to guess what you can do with an


EPROM. All this means is that it is a lot easier to create a ROM without having it custom built.

Having looked at memory in general it is also worth looking at a couple of types of specific memory which figure prominently in today's small computer. One is the memory mapped VDU (Visual Display Unit) area. Here some specific hardware is used to directly translate an area of memory into a picture on a TV screen. To give an example, the PET has a section of memory, with addresses 32768 to 33767, the binary contents of which are translated into a display of 40 characters per line and 25 lines on its built-in VDU. Each byte can specify any one of 256 characters on the screen, and the section of memory consists of 1000 characters. Thus to cause any specific display to appear one is required to insert the relevant data into the memory locations corresponding to the required positions on the screen. The other is the I/O RAM type of device of which there are too many to mention. What happens here is that, in effect, a section of memory is shared by the MPU and a peripheral device such as a printer. The printer will take any data appearing at the specific address as something to be output, in this case printed as a character on paper.

Two types of communication with the outside world by the MPU have now been mentioned — through a VDU and through a printer. Both, you may have noticed, are in the same, single, direction — from the MPU to you (or whoever else may be on the receiving end). This is called Output. There are numerous other forms of output, although the most common are the direct-to-human types of printer or VDU. In theory, at least there is no reason why the output should not take any form desired. In practice only the more useful forms are employed.

Useful output is output that can be read or understood by people and/or things. It can, for instance, be a control signal to a machine or data on a punched or

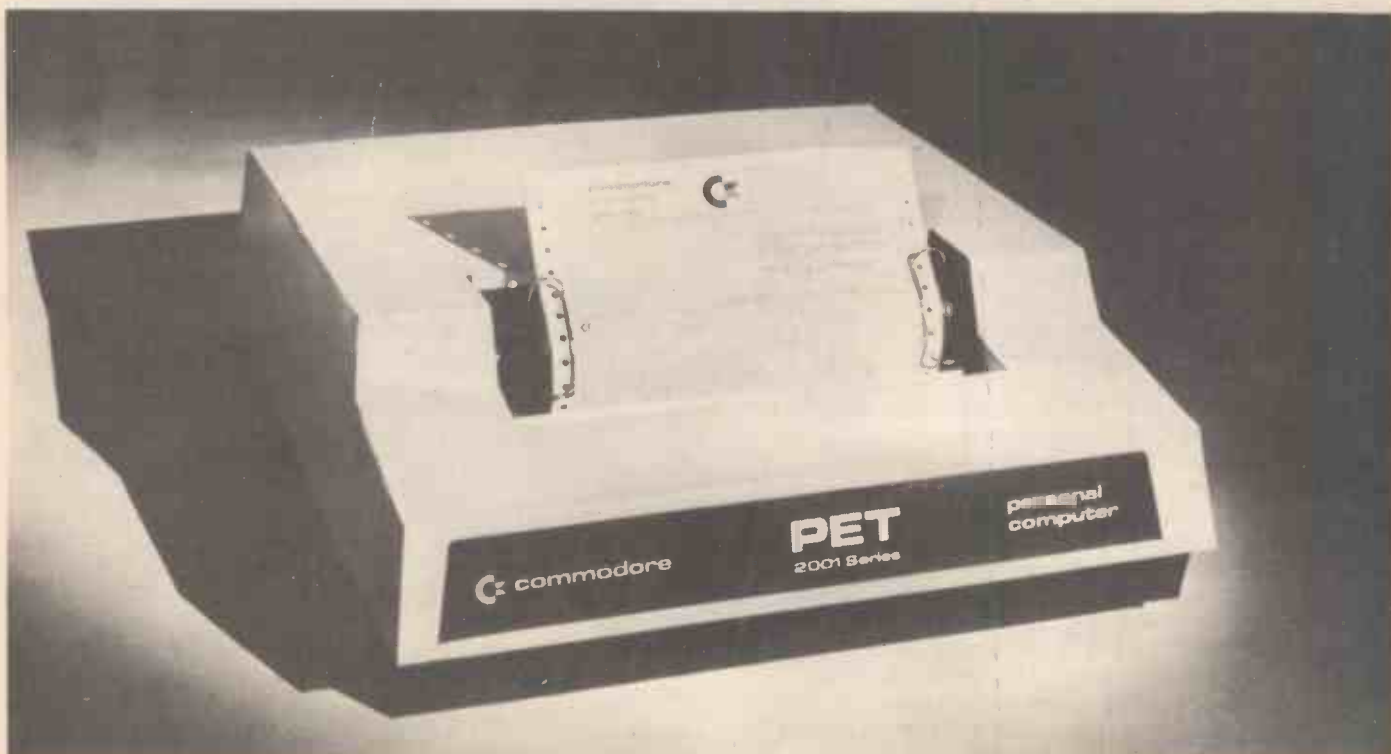Again from commodore is this printer. Printed copy does not, unlike a VDU, fade when the power is turned off, but as it needs mechanical devices to produce it, takes a lot longer to produce.



Home Computing



Some machines of the larger and more expensive variety. Bottom left are some disc drives which take disc packs, rather than single floppy discs, and have a staggering speed and capacity.

magnetic tape which would then be used as input to another program.

Input is the other major requirement for an operating computer system. The programs that are run and the data that is operated on have to get into memory somehow. This is most commonly done via a keyboard initially, but where large and complex amounts of data are to be transferred a more convenient medium, such as a magnetic tape or disk is used.

SOFTWARE

Having glanced briefly at the hardware requirements of a computer it becomes worth looking at what keeps it working: the sets of instructions to the MPU which are called a program. When you turn on the computer and plug in the printer not a lot will happen until the MPU starts following some instructions. In a small computer there will practically always be a monitor program available in ROM, which will start to run when the power comes on. The monitor, at its most basic, will allow the user to examine and alter locations in the RAM, and thus enter a program, and then to cause the MPU to jump from the sequence of instructions of the monitor to the user's own program. At this level input would probably be via a small keypad and output to a calculator display. A more complex monitor program would accept input from a typewriter keyboard and a cassette, and output to a memory mapped VDU.

Hexadecimal (Hex for short) is a term often heard in connection with monitor programs. It is a counting system: standard decimal arithmetic is based on a count of ten, binary on two, and hex is based on sixteen. It becomes a convenient shorthand method of representing binary — it is a lot easier to understand 6 (in decimal) as 6 (in hex) than as 110 (in binary) or 11 (decimal) as A (hex) and 1011 (binary). In hex the figures 0 to 9 represent the equivalent decimal values, and the letters A to F to represent the values ten to fifteen (when you get to sixteen you carry). When working in hex you are working in the binary code to which the MPU will respond, but made that little bit more readable.

Another program that is commonly available in ROM, but which sometimes must be loaded into RAM, by the monitor, from tape or disk, is called a BASIC interpreter. When this program is run the system will look for input data from the user. The data is entered through the keyboard and consists of instructions to the computer,

but written in a way that is very much like the English language. Having typed in the program in BASIC and instructed the interpreter to get to work, it will examine each line of the program and convert this into the equivalent binary code, put it into RAM, and then execute it. It is not the program that was typed in that runs, but the interpreter as guided by the program. As it is the interpreter program that is running it is possible to have it produce messages on the spot, so a misspelt instruction is spotted immediately. To the user it appears that the program in BASIC runs directly on the computer which, in turn, comes out with helpful (sometimes) remarks.

All this takes time, particularly as sections of a program which are repeated are interpreted each time they are used and with a complex program the time taken becomes very noticeable. It is far more efficient to run a program in machine code straight from RAM. While hex is a lot easier to handle than binary code, a string of hex digits is still a bit much to try to read and understand. It makes a lot of sense to use words or abbreviations to represent the instructions, and then have a computer program translate this into binary code. Such a program is called an assembler, and takes as the program written in words as input and produces the binary coded version as output. This can then be stored, and loaded into RAM by the monitor so that it can be run, at any time.

You can make life still easier for the computer user. There are programs called compilers which take a program written in a code which, like BASIC, is very much akin to English (FORTRAN, COBOL and ALGOL are but a few of many examples). As with an assembler the program code is translated into binary code which can be stored and used at any time.


And there is more to come. Research into speech recognition is very advanced, and the days of Hal, the computer in the film 2001, are approaching on schedule.

But all this doesn't tell you what to do with your computer. For myself, I'm happy to write and play games programs. The Klingons will never take me alive.

A combined VDU output and keyboard input of the type that has become very popular.



CLEVER DICK

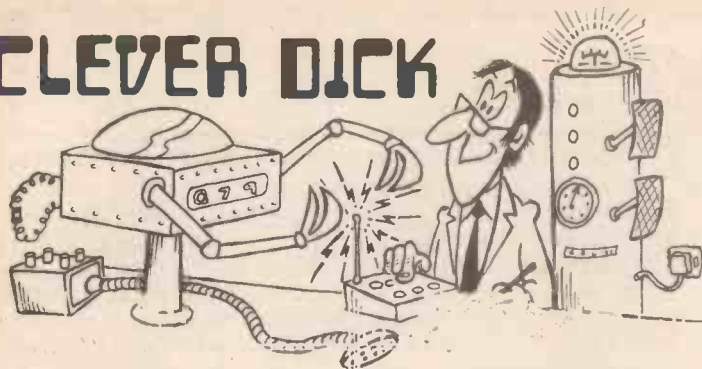

NO MESSING ABOUT this month, we've got a lot to get through. Our first enquiry comes from the Department of Physics, Pinderfields General Hospital in Wakefield. John Mason the area physicist asks:

Dear Dick,

In the article on Display Techniques (June HE) you mentioned a firm called Itron as manufacturing a large range of fluorescent displays.

We are developing terminals for bedside use in a neurosurgical ward and are trying to incorporate a large bar-graph display, possibly including some alphanumeric information. I would be grateful if you could let me have the address of Itron and if possible any information you may have on LCD matrix displays.

Yours,

John Mason
Wakefield, West Yorks

No sooner said than done John. Itron are a Japanese company and their products are distributed by: ITT Meridian Ltd, West Road, Harlow, Essex CM20 2BT. We've been in touch with Tim Orr (the author) and he recommends a company called Hamlin for the LCD displays, they live at: Park Road, Diss, Norfolk. Hope we've been of some help.

Now for a regular request, PCBs, a lot of people seem to be afraid of making their own PCBs, not so Mr Buchan.

Dear Dick,

I am a regular reader of HE as an amateur. I have recently started a job as a mechanical draughtsman and PCB layout engineer, the latter being a new subject to me. Could you please advise me of a source of information which will help me to produce printed circuit layouts and circuit diagrams, using ICs if possible.

L. G. Buchan
Suffolk

Some people try to make out that PCB design is an art, this is just not so. It would be impossible to outline all the ins and outs in such a small space so we would recommend you try looking in our special 'Into Electronics Plus' there is a large feature on PCB manufacture and we can assure you its really very easy. We might be doing a feature in the near future covering PCB design so keep your eyes peeled for that one.

We thought we had heard the last of the White Noise Generator but this was not to be (a good project just won't lie down). Mr J. Hendry writes to us with a somewhat strange request.

Dear Dick,

I am building the White Noise unit (Hope you remember to get the PCB the right way round — Dick) as

Quite a varied postbag this month. We have had one or two letters on the article Display Techniques, concerning some of the companies mentioned. Batteries, too, seem to trouble some of our readers, find out why.

featured in the May edition of HE and would like to know whether connecting the unit to the power amplifier of my stereo record player would damage my stereo in any way. I have already built the graphic equalizer for my record player and it would be a simple case of unplugging the equalizer and plugging in the noise unit. Advice please.

J. Hendry
Montrose, Angus

It would seem from reading Hi-Fi magazines (yes we do read other people's stuff) that most manufacturers spend a large amount of time in trying to eliminate noise from their system but doubtless you have your reasons. Of course you can connect the White Noise Generator up to your stereo, you may find you will need some attenuation, try connecting a 10k pot across the output and taking the output from the wiper. Good luck (Hmmm, strange people).

Our final question comes from Richard Carsons (another clever Dick?), he has a problem with power supplies:

Dear C.D.

Why is it so many circuits require odd-voltage supplies? Cases cost more the larger they are, so with microelectronics why do we have to pay a small fortune for a case that is larger than we really need, just so there is room to take all the batteries? TTL devices, for example, often require a specific supply of 5-5½ V, but batteries come in 1½ (or multiples of) or 9 V, such as the trusty PP3. Mains supplies are not convenient if something is to be really portable.

A PP3 is a small handy battery, so is there any way that it can be used and the voltage reduced (potential divider etc. How useful are the 'hearing aid' type cells, are these 1½ V? If so, 6 of these in a clip would make a very small 9 V supply but would they have enough capacity to drive anything?

Richard Carsons
Surrey

Quite an interesting problem Richard, much of the TTL family of ICs have already been replaced with the more versatile CMOS type of IC so that particular problem should disappear before too long. In the meantime if you cannot use CMOS a small IC voltage regulator is probably the best way to derive 5 V from a 9 V battery, potential dividers tend to be less efficient. Try the 7805 or equivalent. As for hearing aid batteries they are usually only 1.1 or 1.2 V mercury or alkaline cells but can supply considerable current for long periods, trouble is they are rather expensive, you would be better off using re-chargeable Ni-Cads. We have a feature on power supplies and batteries coming up soon, you may find that helpful. See you next month.

HE Back Numbers

Shown here are all the past issues with their major features and projects. All are available (at the moment) for just 60 pence each, including post and packing. Send your order to:

**Hobby Electronics
Backnumbers Dept.
145 Charing Cross Road
London, WC2H 0EE**



NOVEMBER 78 (Hobbyprint A)

Projects: Stereo Amplifier, Digital Clock, Wah-Wah Pedal, Bedside Radio.
Features: The Edison Effect, Robots, Hi-Fi Specs, Kit Review, Transducers, Metal Locators etc.



DECEMBER 78 (Hobbyprint B)

Projects: Metronome, Photon Phone, Audio Mixer, Electronic Dice.
Features: Deep Space Communications, Understanding Bias, Lasers, Photocells, Calculators, The Tesla Controversy etc.



JANUARY 79 (Hobbyprint C)

Projects: Graphic Equaliser, Touch Switch, Vari-Wiper, Flash Trigger.
Features: BASIC programming, Viewdata, Starship Daedalus, Pinball Machines, etc.



FEBRUARY 79 (Hobbyprint D)

Projects: Short Wave Radio, Sine/Square Generator, Scratch/Rumble Filter, Car Alarm Project.
Features: Video Tape Recorders, Radioactivity, CA 3130 Circuits, Computer Glossary etc.



MARCH 79 (Hobbyprint E)

Projects: Light Chaser, Tone Controller, Photographic Timer, Cassanova's Candle.
Features: TV Signals, Test Gear, SW Aerials, Interfering Waves, Communications Satellites, etc.

Shown next to each issue is the relevant code letter to use when ordering Hobbyprints. (See Hobbyprints ad. elsewhere in this issue.)



APRIL 79 (Hobbyprint F)

Projects: Model Train Controller, Cistern Alarm, Transistor Tester.
Features: The Telephone System, TV Aerials, Electronics in Warfare, Catalogue Survey etc.



MAY 79 (Hobbyprint G)

Projects: Power Supply; Parking Meter Timer, Digibell, White Noise Effects.
Features: Feedback, Electronic Music, AB Circuits, 555 Circuits, Aerial Tuners, Varicap Diodes etc.




JUNE 79 (Hobbyprint H)

Projects: GSR Monitor, Envelope Generator, Drill Speed Controller.
Features: Citizen Banned, Display Techniques, Moving Coil Meter, Electronics in Music Pt 2, etc.



JULY 79 (Hobbyprint I)

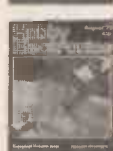Projects: Shark, Baby Alarm; Point Controller, Linear Scale Ohmmeter.
Features: Cassette Decks and Tapes, Binary Numbers, Fixed Resistors, Short Circuits Special, etc.



AUGUST 79 (Hobbyprint J)

Projects: Home Security System, LED Tachometer, Injector/Tracer, Constant Volume Amplifier.
Features: Security Installation, Variable Resistors, Tools, Satellite Power etc.



SEPTEMBER 79 (Hobbyprint K)

Projects: Combination lock, Light dimmer, Starburst, Ultrasonic Switch.
Features: Electronic Timekeeping, Thyristors, Radio Control, FET Special.

SUBSCRIPTIONS

WHY MISS OUT?

To: Subscriptions
Hobby Electronics
P.O. Box 35
Bridge Street
Hemel Hempstead
Herts


I would like a postal subscription to HE starting with the issue. I enclose payment (£6.50 for UK and Eire, £7.50 elsewhere, £11.50 air mail).

Name

Address

You can't beat The System.

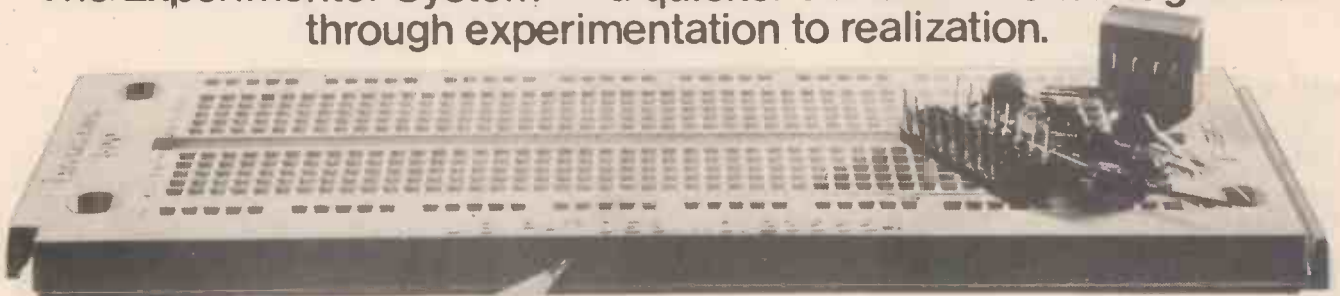The Experimentor System™ — a quicker transition from imagination through experimentation to realization.



Experimentor solderless breadboard.



Experimentor Scratchboard™ workpads.



Experimentor Matchboard™ pre-drilled PCBs.

When you have a circuit idea that you want to make happen, we have a system to make it happen quicker and easier than ever before: The Experimentor System.

You already know how big a help our Experimentor solderless breadboards can be. Now we've taken our good idea two steps further.

We've added Experimentor Scratchboard workpads, with our breadboard hole-and-connection pattern printed in light blue ink. To let you sketch up a layout you already have working so you can reproduce it later.

With Experimentor Matchboard you can go from breadboard to the finished product nonstop! We've matched our breadboard pattern again, this time on a printed circuit board, finished and ready to build on. All for about £1.32.

There's even a letter-and-number index for each hole, so you can move from breadboard (where they're moulded) to Scratchboard™ (where they're printed) to Matchboard™ (where they're silkscreened onto the component side) and always know where you are.

When you want to save time and energy, you can't beat The Experimentor System.

1. EXP-300PC, which includes one item: A Matchboard pre-drilled PCB. **£1.32** 2. EXP-302, which includes three items: Three 50-sheet Scratchboard workpads. **£1.68** 3. EXP-303, which includes three items: Two Matchboards and an EXP-300 solderless breadboard. **£8.60** 4. EXP-304, which includes four items: Two Matchboards, an EXP-300 breadboard and a Scratchboard workpad. **£9.30**

CONTINENTAL SPECIALTIES CORPORATION



EUROPE, AFRICA, MIDEAST: CSC UK LTD.
Dept. 14 W
Shire Hill Industrial Estate Units 1 and 2
Saffron Walden, Essex CB 11 3AQ
Telephone: SAFFRON WALDEN (0799) 21682
TLX 817477

CONTINENTAL SPECIALTIES CORPORATION, DEPT. 14 W

Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex.

Name _____

Address _____

Inc P&P and 15% VAT

1. EXP 300PC £2.38	Qty. Reqd.	2. EXP 302 £2.79	Qty. Reqd.	FREE Catalogue tick box <input type="checkbox"/>
3. EXP 303 £11.04	Qty. Reqd.	4. EXP 304 £11.85	Qty. Reqd.	I enclose cheque/ PO for

£ _____

Phone your order with Access, Barclaycard or American Express

Card No. _____ Expiry date _____

Hobbytune


Build a full feature monophonic organ for less than ten pounds

HOBBYTUNE IS A SELF-CONTAINED, battery-powered stylus organ with a number of novel features. You can select between four independent voices, use them all at once or in combinations for a full chorus sound. Vibrato is available and the depth of modulation is fully adjustable enabling effects from a gentle 'harmonica' beat to a modern synthesizer sound to be produced.

A twenty note keyboard was chosen as the best compromise between economy and performance. This gives a scale in the key of 'C' ranging between 'G' and 'D' including sharps and flats; the 'black' notes. Though only an octave with a fourth below and a tone above, the range of the instrument can be extended by judicious use of the stops as square and triangle outputs are

available both at the fundamental pitch and an octave below.

The vibrato frequency is fixed, though it is very easy to change if required by selection of three capacitors. Though designed for use with its built-in amplifier and loudspeaker, Hobbytune can be easily modified to plug into your home stereo amp by taking an output from the slider of the volume control. Also the keyboard can be extended to any desired size by addition of further tuning resistor networks. As each note can be individually adjusted the instrument can be tuned very accurately avoiding the generation of unwanted 'blue' notes. The unmodified instrument, built as described here proved to be very popular in the office and the tone was very pleasant with more than adequate volume.

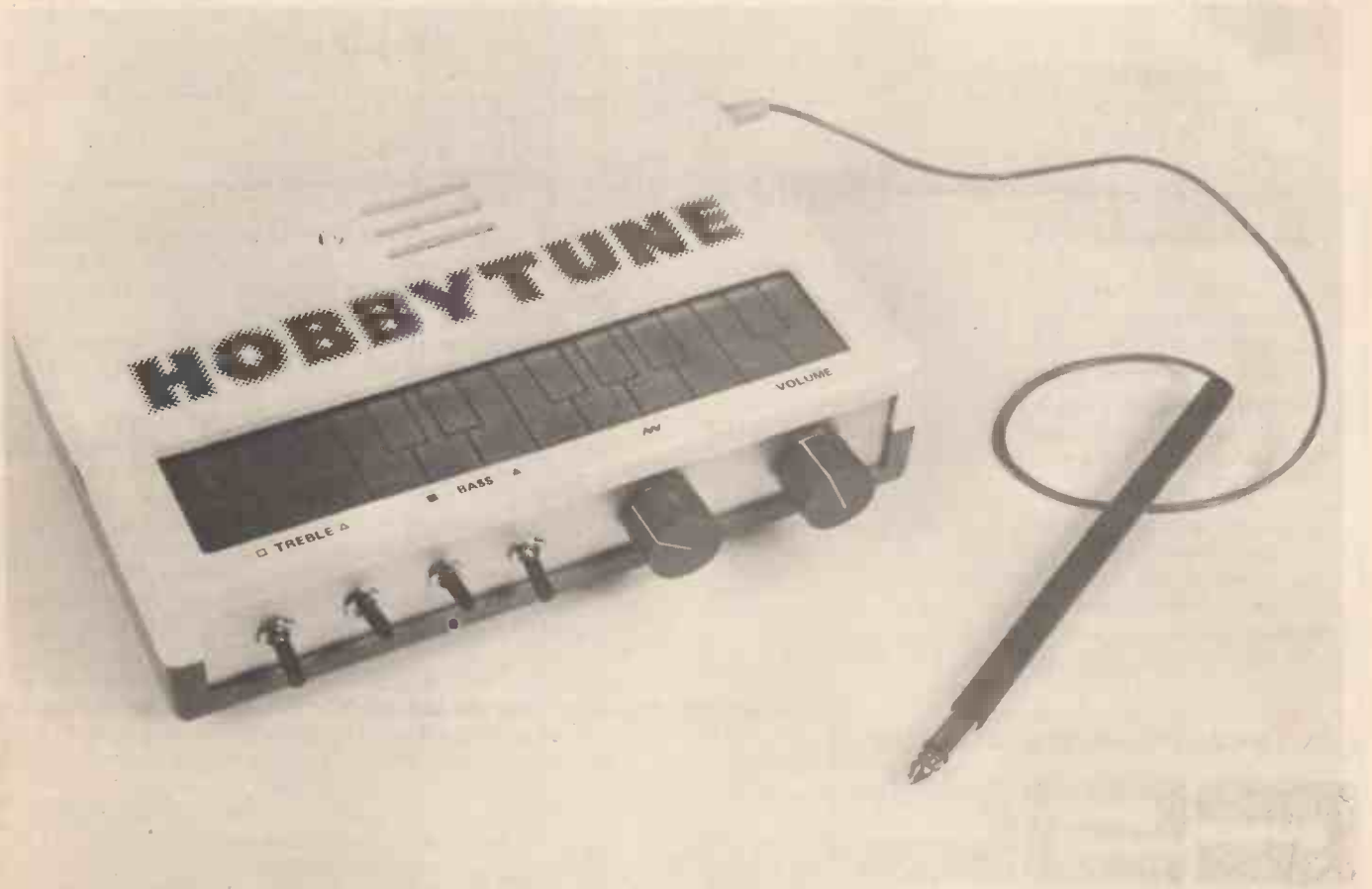

The Hobbytune awaiting a guiding hand, note the use of an old jack-plug for the stylus

Fig. 1. Circuit diagram for the HE Hobbytune

NOTES:
 IC1 IS 4027B
 IC2 IS LM389
 D1, D2 ARE 1N4148
 ZD1 IS 6V2 400mW


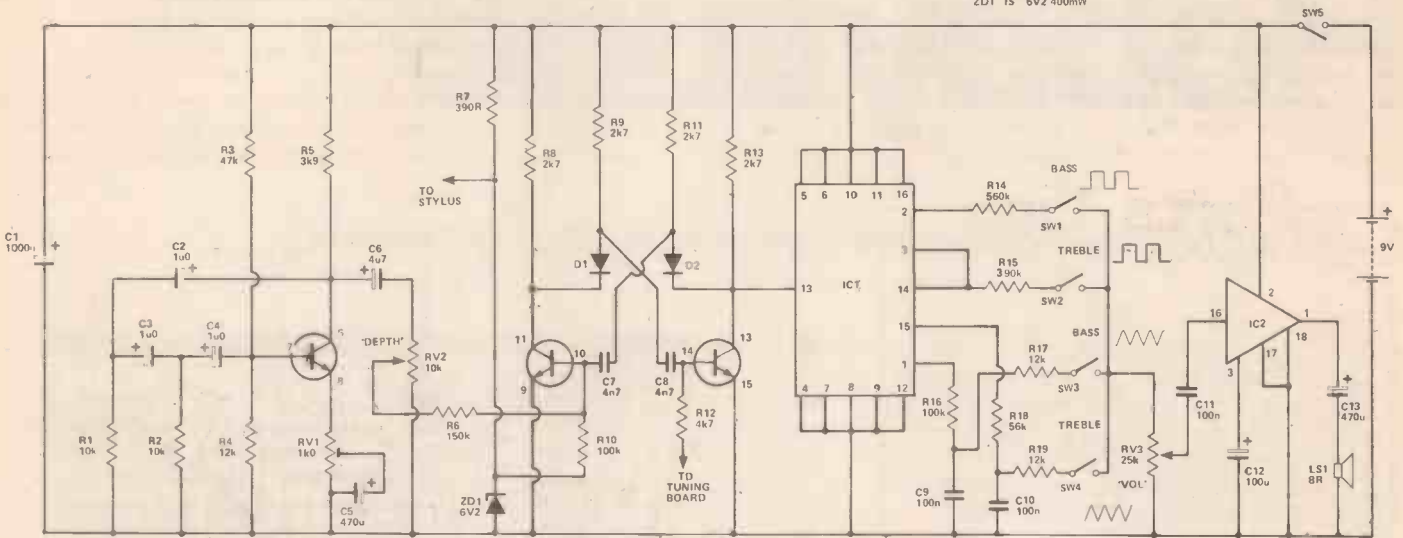


Fig. 2. Circuit diagram for the resistor tuning network

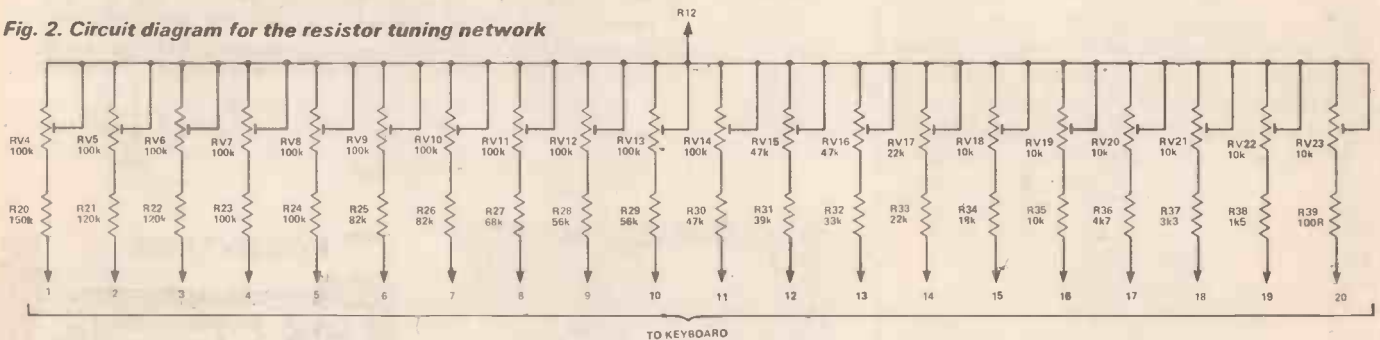

How it Works

Circuit operation may be most easily understood by considering it as four separate sections. The master tone generator, vibrato oscillator, divider and waveshaping circuits and the audio amplifier. We will look at these in more detail.

The master tone generator is formed by two transistors (pins 9, 10, 11 and 13, 14, 15) connected as an astable multivibrator. The only unusual feature of this circuit is the inclusion of diodes D1, 2 and resistors R9, 11. These components steer current into the timing capacitors C7, 8 on the positive going edges of the waveform and enable clean fast squarewaves to be obtained at the transistor collectors. This ensures reliable triggering of the CMOS divider IC1. Frequency is altered by adjustment of resistance between R12 and the junction of R7 and ZD1. The zener diode is included to provide a measure of protection against falling battery voltage. The frequency may be altered by injecting a current into the base of either transistor. In this circuit, the modulation voltage is applied to R6. Modulation depth is controlled by adjustment of RV2.

The modulation signal, an approximation to a sine wave at between 5 to 10 hertz, is obtained from the phase-shift oscillator built around one transistor (pins 6, 7, 8) which runs continuously. C2, 3, 4

set the frequency of oscillation and should be adjusted equally if a change is required. RV1 sets the gain and should be adjusted so that the stage just oscillates. The easiest way to do this is with the master tone generator working and the modulation depth control set at maximum. Simply play a note by touching the stylus to the keyboard, adjust RV1 and listen to the result. The best sine wave and most attractive effect is obtained when the circuit is just oscillating.

There is little to say about IC1. It simply divides the master tone generator output by two and divides its own output by two again producing two squarewave signals of equal duty cycle an octave apart. As signals are available from both the Q and Q outputs, one of these is simply attenuated by a resistive divider (R14, RV3) whilst the other is shaped by a lowpass RC filter formed by R16, C9. Values of the waveshaping and attenuating components are not critical though those shown gave good results in the prototype.

IC2 contains an audio amplifier with a voltage gain fixed at about 20 and bias set internally. C12 is a decoupling component while C11 and C13 couple the signal input and output respectively. C1 is the overall supply decoupling capacitor.

TAKE TWO

Only two integrated circuits are used in the unit. Do not be misled by the circuit diagram, the three transistors and the audio amp are all contained in a single package, the LM389 from National Semiconductor. The other device is an ordinary CMOS dual JK flip-flop configured

as two divide by two counters. This ensures symmetrical waveforms are available for waveshaping. Very simple RC filters are used to perform waveshaping and square and triangle waveforms are available. These approximate to string and woodwind sounds. More complex tone formation would have been prohibitively expensive and is really unnecessary as the tones produced by the simple techniques used sound very good.

Parts List

RESISTORS (All 1/4W 5%)

R1, 2, 35	10k
R3, 30	47k
R4, 17, 19	12k
R5	3k9
R6, 20	150k
R7	390R
R8, 9, 11, 13	2k7
R10, 16, 23, 24	100k
R12, 36	4k7
R14	560k
R15	390k
R18, 28, 29	56k
R21, 22	120k
R25, 26	82k
R27	68k
R31	39k
R32	33k
R33	22k
R34	18k
R37	3k3
R38	1k5
R39	100R

POTENTIOMETERS

RV1	1k preset
RV2	10k lin
RV3	25k lin
RV4, 5, 6, 7, 8, 9, 10,	
11, 12, 13, 14	100k preset
RV 15, 16	47k preset
RV17	22k preset
RV 18, 19, 20, 21,	
22, 23	10k preset

CAPACITORS

C1	1,000 μ electrolytic
C2, 3, 4	1 μ tantalum
C5, 13	470 μ electrolytic
C6	4 μ 7 tantalum
C7, 8	4n7 polyester
C9, 10, 11	100n polyester
C12	100 μ electrolytic

SEMICONDUCTORS

1C1	4027B
1C2	LM389
D1, 2	1N4148
ZD1	6 V2 400 mW

MISCELLANEOUS

SW1, 2, 3, 4, 5	SPST
LS1	8 ohm 2 1/4"
Stylus (see text)	case to suit
	Approx. cost £8

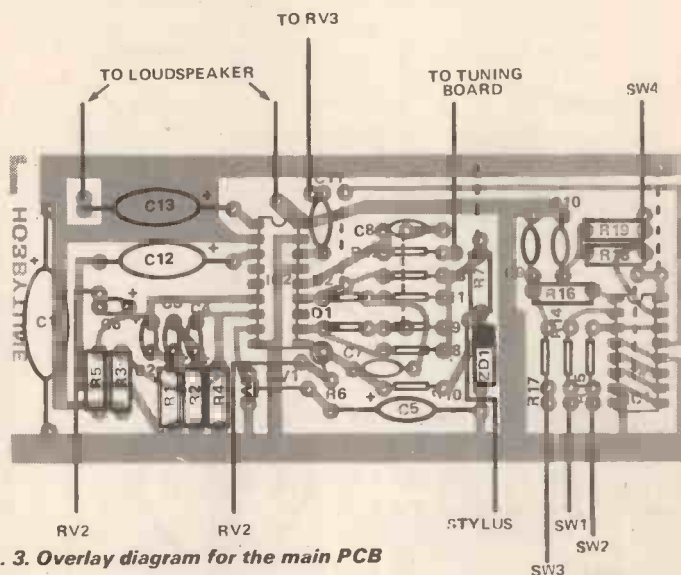


Fig. 3. Overlay diagram for the main PCB



Close-up of the main electronics

Buylines

The only component likely to cause any problems here is the LM389 which is available from Marshall's, as is a suitable 18 pin Dill socket.

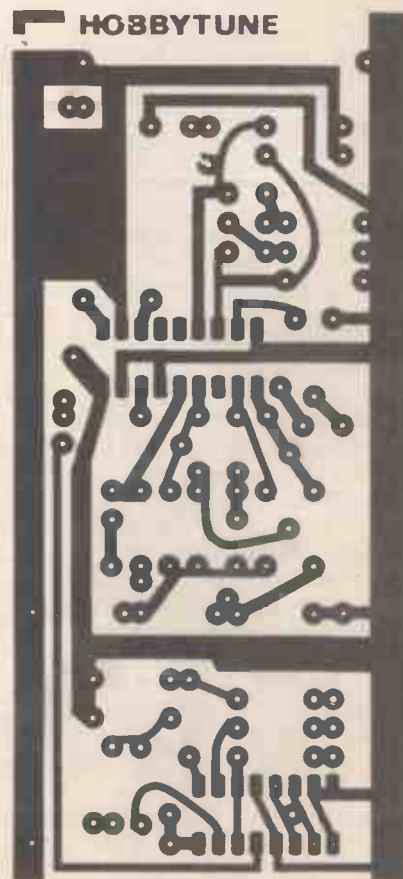


Fig. 4. PCB foil pattern for the Hobbytune main board

CONSTRUCTION

The organ is assembled on three PCBs. Other methods may be used but use of our PCBs will greatly reduce the chance of errors creeping in and simplify construction. To enable flexibility of layout and design, the main circuitry is contained on one board while another carries the tuning resistors. The third board is used as the keyboard. Keyboard and tuning board may be mounted together, simplifying the interwiring and producing an efficient use of space as shown in our photos.

Construction should proceed in the usual order. Insert and solder the links first followed by the IC holders, resistors, capacitors and diodes. Make the connections

between the case mounted components and complete the interwiring between boards. A connector may be used for the stylus if required or a wire may be brought out directly from the board.

If all looks well, connect a battery (we used six HP7s giving nine volts) and switch on. By selecting a voice and touching the stylus to the keyboard, a tone should be produced. You can now tune the instrument by adjustment of the trimmer resistors.

Anything from a disused test probe to a ball point pen may be used as a stylus. We used part of an old quarter-inch jack plug with good results.

Once the instrument is in tune, you can begin playing in earnest. Some sample tunes are included here . . . and you know what practice makes.

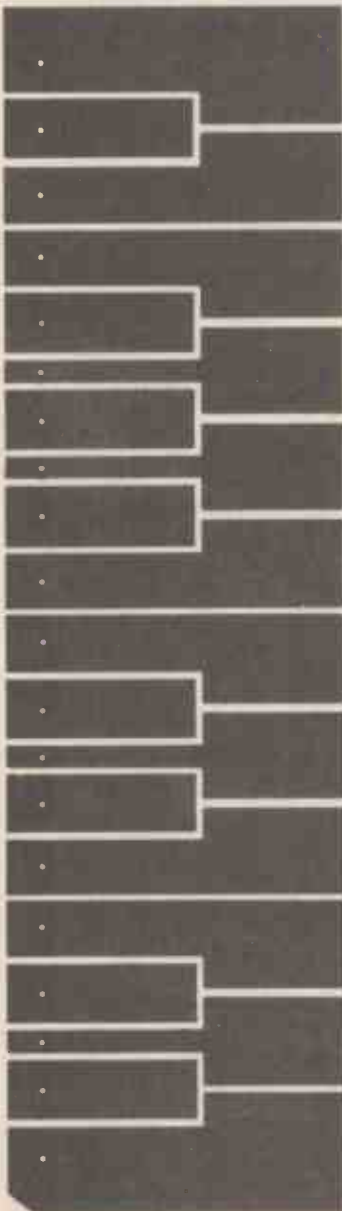


Fig. 6. PCB pattern for the keyboard

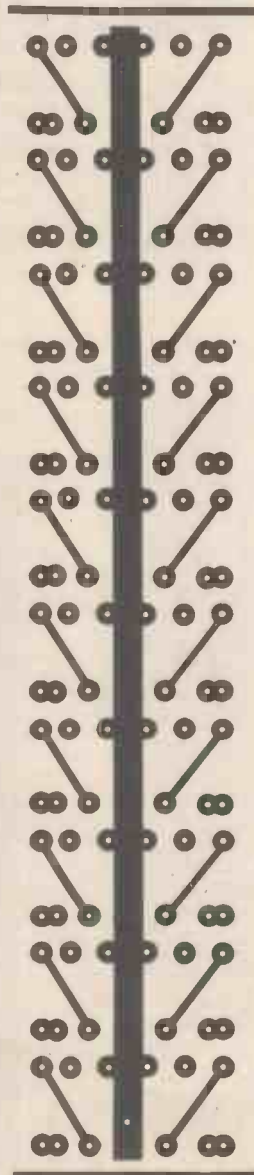


Fig. 7. PCB foil pattern for the resistor tuning board

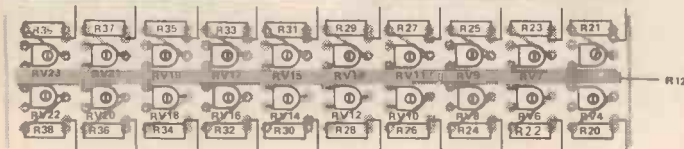


Fig. 5. Overlay diagram for the tuning board


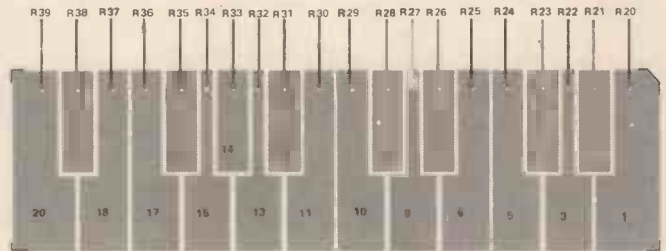


Fig. 8. Connections for the Hobbytune keyboard

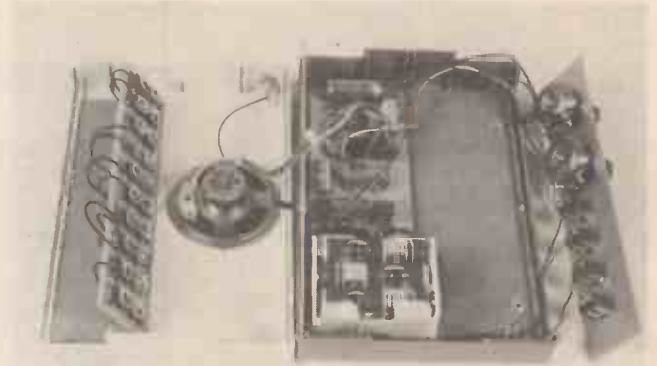

Hobbytune — naked to the world, we strongly advise any budding musicians to use our PCB design to ensure an easy and trouble-free project

HOBBYTUNES

AMAZING GRACE

6, 8, 11, 15, 13, 11, 15, 15, 13, 11, 8, 6, 6; 8, 11, 15, 13, 11, 15, 18, 18.

TELSTAR

6, 1, 3, 6, 11, 10, 8, 6, 8, 1, 11, 10, 8, 6, 8, 1, 13, 15, 13, 6, 13, 11, 10, 3, 10, 8, 10, 10, 11, 10, 8, 6, 8, 8, 10.

LAND OF HOPE AND GLORY

6, 6, 5, 6, 8, 3, 1, 11, 11, 10, 11, 13, 8, 10, 10, 12, 13, 15, 20, 13, 18, 18, 17, 15, 13.

Kit Review

DIGITAL PANEL METER

It's time to remove that tube of mercury and replace it with a digital thermometer using a liquid crystal display.

WHAT IS THE TEMPERATURE TODAY? Your starter for 10 — a popular question. But can you answer without squinting, putting your specs on, even taking wild guesses, in the end giving an uncertain answer. If you happen to fit into any of these categories then it's about time that you had an electronic thermometer.


Our kit this month is based around a digital panel meter IC. This 40 legged giant can be used either as a digital voltmeter (DVM) or a thermometer. (The DVM can be set for a 200 mV or 2 V full scale reading). From this basic circuit the thermometer can be built with the addition of just a few components (to be exact two resistors, one preset and a diode). The diode is used as the temperature sensor which is connected via a screened lead. Calibrating the thermometer is very simple. By placing the sensing diode into ice and then into boiling water, two presets are adjusted to give a 000.0 and a 100.0 display respectively.

Being homiothermic creatures (constant body temperature to you and me) at heart we decided to build the thermometer, voltmeters tend to be a bit boring anyway. Having made our choice we were ready to reveal the hidden contents.

OPEN SESAME


The most fragile component we encountered was the liquid crystal display, this was carefully packed between two polystyrene containers, minimising any damage through transit. The CMOS IC was housed in the usual anti-static holder. The rest of the components were all neatly packed into a plastic bag with the component count being fairly low, it made checking the contents against the parts list relatively easy, we found no omissions here, everything was included, even a length of solder.

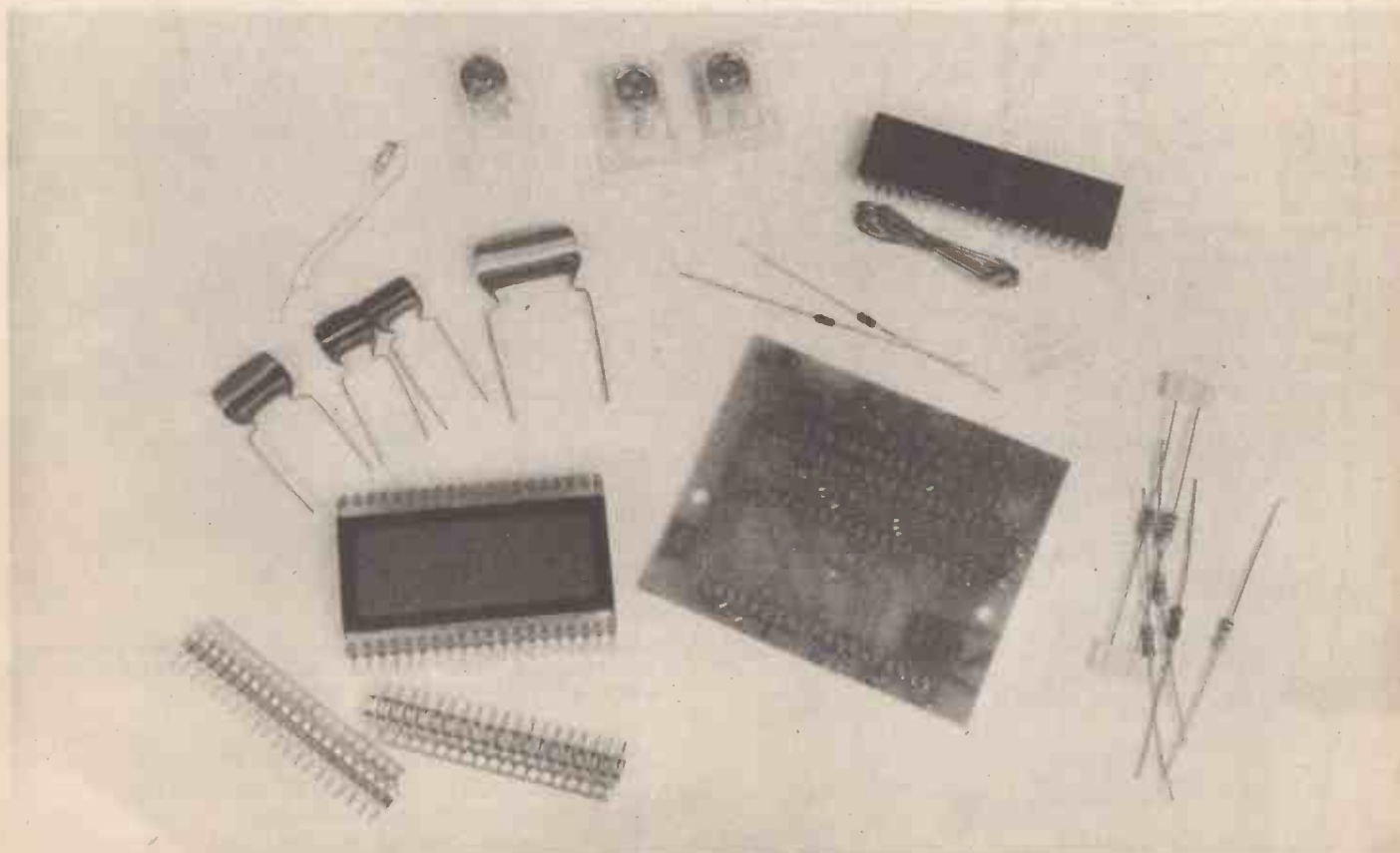The instruction leaflet starts off by giving hints on



The assortment of parts laid bare for inspection.

soldering and assembling of PCB's, always good to see, this is followed by a brief description of the available functions on both options. To aid recognition, the capacitor colour code was given for the individual capacitors used, though for some reason there was no mention of the resistor code. However, this should not present a great problem to a studious Hobby reader as an early back issue would rescue you.

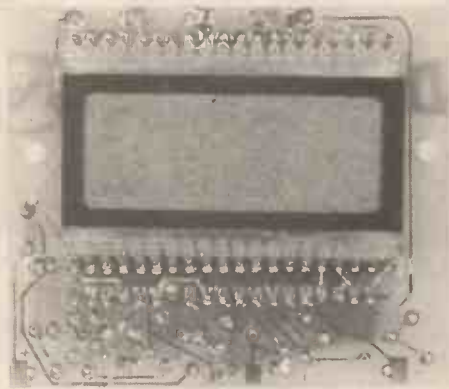


The liquid crystal display mounted on the copper side of the PCB.

PUTTING IT TOGETHER

The instructions show two component overlays; we recommend that they both be structured closely before construction commences. After identifying all the components and inserting them in their respective place and applying the trusty soldering iron, the next stage was to make up a DP (decimal point) driver circuit. There are three suggested circuits, two give a fixed DP the other a floating point. The thermometer uses a fixed decimal point.

As there was no provision made on the PCB for the components, all connections required were brought to the edge of the board. The circuit can then be hand-wired on the edge of the PCB. (It is worth noting that these components are not included in the kit as requirements will vary). To complete the construction you'll need to find a length of screened cable and attach the sensor diode to one end, observing the polarity. Total construction time was approximately 20 minutes.

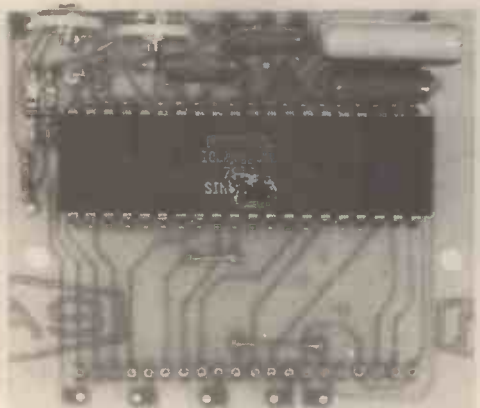Upon checking things over we noticed that C5 had suffered a crack on one side. This was due to the pitch




The completed PCB, note the use of Soldercon pins for mounting the IC, so take care when inserting the device.

spacing being fractionally out. The wretched component was pulled out 'gracefully' and replaced this time standing it further above the PC board. Doing this will reduce the tension placed on the component.

MOMENT OF TRUTH

Reaching for a PP3 power was applied to all parts, to our dismay we were confronted with a blank display — back to the drawing board. With the aid of the component overlay and much head scratching the mistake was found, a missing link (in more ways than one!) was the problem. Trying once more, we inserted the link — and it worked!

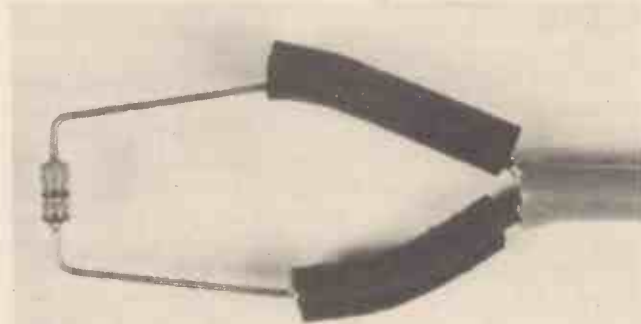
In use the thermometer proved sensitive enough to the surrounding atmosphere, even by blowing onto the sensor diode gave a significant change in temperature.



The diode sensor shown wired onto the screened lead.

CONCLUSION

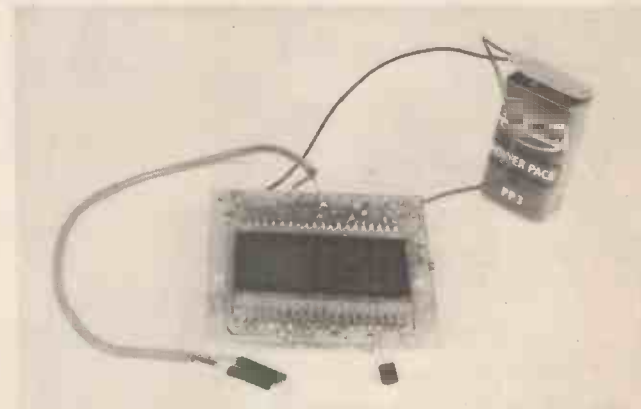Overall a neatly packaged and well presented kit, giving clear simple instructions, it was pleasant to find that there were no major problems. Therefore, if you are new to the game and need some experience in building then this is the kit for you! It has two added compensations, it will ensure that your temperature as well as heart-beat will remain constant — because it works!



The thermometer in its full glory with the decimal point driver on the edge of the PCB. The display is showing a genuine atmospheric temperature reading.

The DVM/thermometer kit is available from TK Electronics 106 Studley Grange Road, London, W7 2LX. Price £20.75 plus VAT. However if you are prepared to wait a few months for 'the special Autumn offer' commencing in Oct/Nov then the kit will be offered at the price of £17.50 plus VAT.

GREENWELD

443F Millbrook Road Southampton SO1 0HX

All prices include VAT @ 15% — just add 30p post

VERO OFFCUTS

Packs of 100 sq ins of good size pieces about 4x3" in the following types:
 K541 0.1" copper clad **£1.50**
 K542 0.15" copper clad **£1.60**
 K544 0.1" plain **£1.50**
 Also pieces 2½x1" — 10/£1.20 100/£9
 17x3¾"x0.1" sheets, 10/£16.50

Large range of Standard Veroboard and boxes/cases in stock. Details in Catalogue, 45p.

SCOPIII Verobox type 2522, unused but has 3 ½" holes in one end and 1 ½" hole in the other, so instead of **£3.96**, we are selling these at **£1.85**

SWITCHES

Push-button banks — 20 types listed on Bargain List No 8, free with cat (45p) or send SAE. Samples:

W473 3 interlocking 4PCO + 2 independent, 70p

W481 5 interlocking 4PCO 70p
 Both types supplied with free knobs!

W106 DPCO slide switch 23x15x7mm 10/£1.20; 100/£9

W107 SPCO min slide switch with 2 wires attached, 10/80p 100/£6

W508 SPCO 5A microswitch with 29mm lever 20x12x6mm 38p 10/£3.00

W302 Rocker switch on/off 10A white, 22p 10/£1.80

W305 Rocker SPCO, centre off, 10A rating, white, 30p 10/£2.30 100/£19

BUZZERS & MOTORS

Z401 Powerful 6V DC, all metal construction, 50mm dia x 20mm 70p

Z402 Miniature type, 3-9V, only 22x15x16mm. Very neat, 65p

Z450 Miniature 6V DC motor, high quality type 32mm dia x 25mm high, with 12mm spindle. **Only £1**

Z451 12V high torque motor 30mm dia x 40mm high, with 10mm spindle, 65p

Z452 6V DC motor with gearbox giving final shaft speed 700rpm. Spindle is threaded OBA. Ex-equip **£1**

Z453 As above, but 300rpm and unthreaded spindle. **£1**

TRANSFORMERS

PA 100V line speaker type. Pri tapped 0.625W-10W in 5 steps. Sec 4 or 8 ohm **£1.75 10/£15 100/£110**

Mains pri, 3 sec windings, 8, 25 and 40V, each at 100mA. A selection of voltages from 8 to 73V is therefore obtainable. 57x48x36mm with flying leads, **£1.50**
 Mains pri, sec 40V @ 250mA **£1.75**

AERIALS

X901 Telescopic 8 section 970mm long extended, 175mm collapsed. Swivel joint. 2BA fixing hole in base. **75p**

X904 Ferrite rod 140mm x 9mm LW/MW/coupling coils, each independently moveable **64p**

X905 As above, but LW/coupling coil together on moveable former. **55p**

CLOCK CASE BARGAIN

Z472 Oval format, overall size 130x68x87mm deep, with built in stand. Rear panel drilled to accept 4 switches + alarm. **60p**

THE AMAZING GREENWELD CATALOGUE

FEATURES INCLUDE:

- 50p Discount Vouchers
- Quantity prices for bulk buyers
- Bargain List Supplement
- Reply Paid Envelope
- Priority Order Form
- VAT inclusive prices

PRICE 30p + 15p POST

3W Amp Module

Ready built and tested, this handy amplifier will prove very useful around the workshop. Just requires 17V ac source (and 8R spkr) as bridge rect and smoothing cap are mounted on the PCB. The 4 transistor circuit provides enough sensitivity for most applications. Supplied complete with circuit diagram and wiring details. **Only £1.75**. Suitable transformer **£2.20**.

LINEAR IC BARGAIN

We have just received a large consignment of popular linear ICs that have failed the manufacturer's stringent tests. However, on checking through a few hundred we have found that quite a large proportion tested in a simple oscillator circuit are functional, so are offering them in packs as follows:

Type	Pack-age	% good	qty	price
702	140IL	65%	25	£1.20
709	80IL	75%	20	£1.20
709	140IL	50%	30	£1.20
710	T099	30%	40	£1.20
710	140IL	30%	40	£1.20
720	140IL	80%	20	£1.20
741	T099	40%	25	£1.20
748	T099	70%	15	£1.20

Connexion data is supplied. One of each pack, **£8.50**

DISC CERAMIC PACK

Amazing variety of values and voltages from a few pF to 2.2µF! 3V to 3kV! 200 **£1 500**
 £2.25 1000 **£4.00**

DIODE SCOOP!!!

We have been fortunate to obtain a large quantity of untested, mostly unmarked glass silicon diodes. Testing a sample batch revealed about 70% useable devices — signal diodes, high voltage rects and zeners may all be included. These are being offered at the incredibly low price of **£1.25/1000** — or a bag of 2500 for **£2.25**. Bag of 10,000 **£8**. Box of 25,000 **£17.50**. Box of 100,000 **£60**

VU METERS

V002 Twin type. 2 meters 40x40mm and driver board, supplied with circuit and connexion data. **£3.50**

V003 New type, just in. Twin type moulded in one piece, 80x40mm (no driver board but suitable circuit supplied) **£2.50**

NOW THIS IS SOMETHING NEW! and so simple to construct

CONTROL UNIT CONSTRUCTION KIT for DISCO LIGHTS, GROUPS, HOME DISPLAYS etc.

KIT £15.95 inc. VAT

A new world in lighting effects is opened to the amateur interested in miniature electronics evolved for the space and computer programmes. This comes to you NOW, in kit form, an easy to construct 4-Channel 'Chaser' Unit, which when connected to a light display of your own design, will supply an on/off sequence giving the effect of chasing or moving lights. It has a speed control and has the ability to automatically make the lights appear to move forwards, backwards or alternate between the two. The unit is designed to fit into your equipment or into a box of its own. Size of completed unit 180x95x30mm. Price **£15.95** including VAT. P & P 30p extra. The 4-Channel 'Chaser' Unit can also be purchased assembled, tested and guaranteed by qualified staff. Special price **£21.95** including VAT. P & P 30p extra.




Send today cheque/postal order to —
COOK ELECTRONICS
 304A HIGH STREET, WATFORD, HERTS. WD1 2JE

Random Electronic EASY DICE

Build your own 'EASY DICE' from the 5 integrated circuits and full components supplied, including box and descriptive instructions.

Complete
 or
 Kit

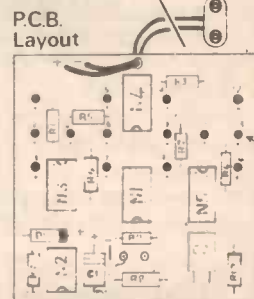

All you need is a soldering iron
TWO DICE FACES TOUCH CONTROL...

- a *Self Assemble Dice **£3.95**
- b *Ready built Dice **£4.75 (INCL. P+P)**

Order now from **Fringewood Electronics Ltd**
 1 Hatton Court Ipswich Suffolk (0473 210151)

Amount enclosed £

Name

Address

please state amount required in appropriate box a b

Car Audio


Manual
MW/LW



Full medium and long wave tuning. Complete with speaker and mountings. Suitable for positive or negative chassis. Latest model.

£10.25 + £1.00 Post

Push-Button
MW/LW

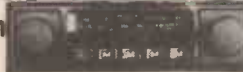

One LW, four MW buttons plus manual tuning. Complete with speaker and mountings. Latest model, negative chassis only.

£15.95 + £1.00 Post

Stereo FM/
Cassette



+ MW
Standard cassettes and FM in stereo plus medium wave. Tone and balance controls. Fast forward facility on tape. Adjustable shafts. Suitable for 4 or 8 ohm speakers (not supplied). This model is discounted elsewhere at £50 up.

£40.95 + £1.00 Post

Stereo
Speaker Set



Suitable for above stereo unit. Good quality in surface mounted casing, 5W nominal, 8W peak.

£4.00 (pair)

+ 70p Post

Telescopic Car Antenna

Multi-section standard type, suitable for angled mounting with locking key.

£1.60 + 30p Post

Metal Detectors

Treasure Tracer Mk III

The original Treasure Tracer. Sales exceed 7,000. 5-transistor circuit with Varicap tuning. Sensitive, stable BFO design. Built-in speaker and earphone. Fitted with Faraday shield. Kit supplied with pre-built search head.

Kit. **£18.60 + £1.00 Post**
Built **£23.95 + £1.00 Post**

★ Induction Balance Model

Built with sensitivity up to 10in on single coin; fitted with speaker and meter; PP3 battery; 7in dia. search head. Telescopic stem. Excellent pin-pointing, positive reaction to non-ferrous, negative reaction to iron. This model's normal price is £39.95!

£24.50 + £1.00 Post

All goods guaranteed one year. 10-day money-back offer. Goods ex-stock at time of going to press. Callers by appointment only please. Send s.a.e. for illustrated leaflet.

Minikits Electronics Ltd.

6H Cleveland Road
S. Woodford
London E18 2AN

HE MA

CLOCK RADIO



You probably won't believe us as we're selling the goods but we're going to tell you anyway! We have *rejected* eight clock radios for Marketplace, they were all cheap enough but the quality was so poor that we couldn't have lent our name to them. However, we are now able to offer a portable LCD Clock Radio to you which meets our standards.

The clock is a 12-hour one with AM/PM indicated and a back light. The radio is Medium Wave with very nice quality for a small speaker. The alarm can be either a beep-beep type or the radio, there's also a snooze facility.

The cylindrical construction is in keeping with the very modern styling. The tuning dial is actually incorporated into one of the end caps!

We won't even mention the RRP — but just check on comparable prices — you'll find ours a bargain.

An example of this Clock Radio can be seen and examined at our Charing Cross Road offices.

£17.95

(Inclusive of 15% VAT and Postage).

To:
CLOCK RADIO Offer,
HE Magazine,
145 Charing Cross Road,
London WC2H 0EE.


Please find enclosed my cheque/PO for £17.95 (payable to HE Magazine) for my Clock Radio.

Name

Address

Please allow 28 days for delivery.

DIGITAL ALARM

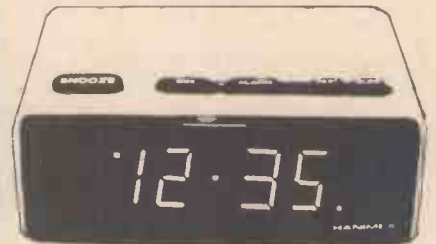

THIS IS THE THIRD digital alarm clock that we are offering (we regret the earlier versions are no longer available). We have sold thousands and thousands of these and our buying power enables us to offer a first rate branded product at a really excellent price.

The Hanimex HC-1100 is designed for mains operation only (240V/50Hz) with a 12 hour display, AM/PM and Alarm Set indicators incorporated in the large display. A switch on the top controls a Dim/Bright display function.

Setting up both the time and alarm is simplicity itself as buttons are provided for both fast and slow setting and there's no problem about knocking these accidentally as a 'locking' switch is provided under the clock. A 9-minute 'snooze' switch is located at the top.

An example of this clock can be seen and examined at our Charing Cross Road offices.

£10.60

(Inclusive of 15% VAT and Postage).

To:
Hanimex Alarm Offer
HE Magazine
145 Charing Cross Road,
London WC2H 0EE

Please find enclosed my cheque/PO for £10.60 (payable to HE Magazine) for a Hanimex Digital Alarm Clock.

Name

Address

Please allow 28 days for delivery.

MARKETPLACE

LCD CHRONO



We feel we've got to tell you carefully about this offer which we're introducing for the first time. Why? Because our price is so enormously lower than anywhere else you may suspect the quality.

The display is LCD and shows the seconds as well as the hours — and minutes — press a button and you'll get the date and the day of the week.

Press another button for a couple of seconds and you have a highly accurate stopwatch with hundredths of a second displayed and giving the time up to an hour. There is a lap time facility as well — and of course a back light.

Our Chrono comes complete with a high grade adjustable metal strap and is fully guaranteed.

£11.95

(Inclusive of 15% VAT and Postage).

To:
LCD Watch Offer
ETI Magazine
145 Charing Cross Road,
London WC2H 0EE

Please find enclosed my cheque/PO for £11.95 (payable to HE Magazine) for my LCD Chronograph.

Name

Address

.....

.....

Please allow 28 days for delivery.

ALARM-CHRONO LCD



This new addition to our unbeatable selection of bargains is no ordinary LCD watch. It's a slim, multi-function, dual time chronograph alarm watch, no less.

This model will show hours, minutes, seconds, date, day of the week, stop watch, split time, alarm and alternate dual time zone — not all at once, of course. There is also a night light.

Hours, minutes, seconds and day of the week are displayed continuously, while the date will appear at the touch of a button. The day of the week is indicated by a flag. When used as a stopwatch, the maximum count is 0.1secs. short of thirteen hours.

£19.95

(Inclusive of 15% VAT and Postage).

To:
ALARM/CHRONO LCD WATCH Offer,
HE Magazine,
145 Charing Cross Road,
London WC2H 0EE

Please find enclosed my cheque/PO for £19.95 (payable to HE Magazine) for my Alarm/Chrono LCD watch.

Name

Address

.....

.....

Please allow up to 28 days for delivery.

Hobby Chit~Chat

LET THERE BE LIGHT

This month our chief designer Ray Marston looks towards those dark evenings and suggests some ways they may be illuminated, electronically of course.

NOW THAT THE SUMMER is drawing to a close many of our readers will no doubt be thinking of tackling major DIY jobs around the house. If complete or partial rewiring of the home lighting circuits figures in your 'jobs-to-be-done' list, you should find this month's 'Chit-Chat' article of interest. The feature is devoted entirely to household lighting circuits.

I completely rewired my own house a couple of years ago, and had to cut some fifty feet of channeling, through brick and plaster, to accommodate new lighting cable runs. Half of that channeling was used to provide two-way switching for the landing light and three-way switching for the hall light. That experience made me realize how awkward conventional single- and multi-way light switching is to install. Since then, I've designed a few electronic circuits that can be used to replace conventional switches and greatly simplify the rewiring problem. Some of these multi-input switching circuits are shown in Figures 1 to 5.

In use, these circuits are intended to be mounted in the ceiling space and wired to the ceiling rose of the lamp in question. The ON/OFF switches can be modern keyboard push-button types, fixed to a flat blanking plate that can be screwed to a wall without any need for recessing. The wiring between the ON/OFF switches

and the electronic unit can be lightweight twin-flex, which can be buried in a channel of groove measuring little more than 1/8in wide and deep. The circuits can accept any number of input switches, so multi-input switching ceases to be a problem.

If you're thinking of building any of these circuits, remember that they carry mains voltage, so proceed with caution, otherwise death may seriously damage your health.

CIRCUITS WITH INDIVIDUAL ON AND OFF BUTTONS

Figures 1 and 2 show multi-input electronic switches that employ individual ON and OFF buttons. The Fig 1 circuit uses relay contacts to switch power to the lamp. The Fig 2 circuit switches the lamp directly via a Triac or 'solid-state relay'.

The operation of the Fig 1 circuit is very simple. IC1 is a quad 2-input CMOS NOR gate, and two of its gates are cross-coupled to form a basic bistable circuit. When one of the 'ON' switches is momentarily operated the CMOS circuit locks into a state in which its output (pin 4) is high, thus driving relay RLA on via Q1 and activating the lamp via relay contacts RLA/1. The


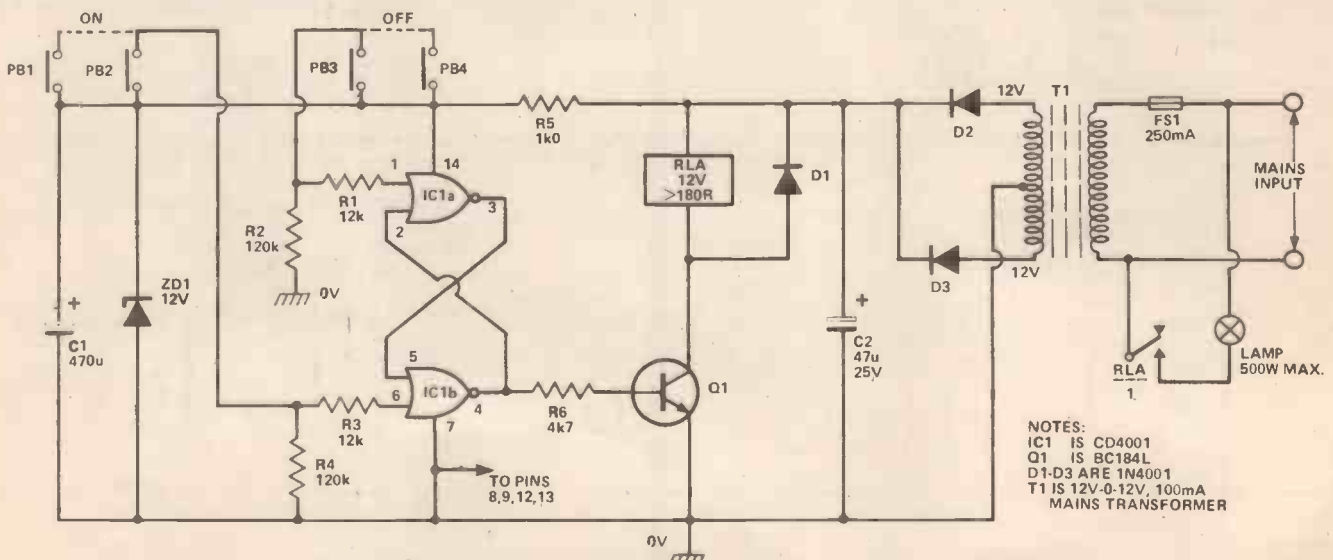


Fig. 1. A relay-output, multi-input electronic light switch using individual ON and OFF push-button switches.

Fig. 2. A Triac-output, multi-input electronic light switch using individual ON and OFF push-button switches.

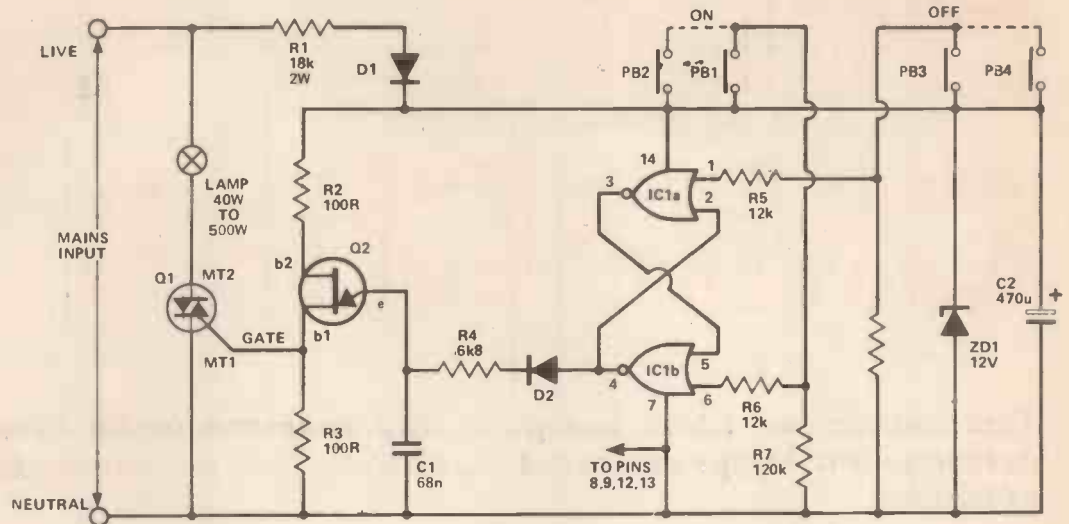NOTES:
 Q1 IS 400V, 8A TRIAC
 Q2 IS TIS43 UNIJUNCTION
 IC1 IS CD4001B
 D1 IS 1N4004
 D2 IS 1N4148



bistable remains in the ON state until one of the OFF switches is momentarily operated, at which point the output of the bistable locks into the low state, and Q1 and the relay and lamp turn off. The power supply for the circuit is derived from the mains via step-down transformer T1 and the associated rectifier/smoothing network.

The operation of the Fig 2 circuit is only slightly more complicated. Here, when an ON switch is operated the output of the CMOS bistable switches high and enables unijunction oscillator Q2, which feeds a chain of trigger pulses to Triac Q1 which turns on and activates the lamp. When an OFF switch is operated the output of the bistable switches low and disables the unijunction oscillator, so the Triac and lamp turn off. The power supply to the CMOS and unijunction circuit is derived from the mains via R1-D1 and ZD1-C2.

CIRCUITS WITH SINGLE ON/OFF BUTTONS


Figures 3 to 5 show multi-input electronic switches that employ single ON/OFF buttons or touch pads, so that the lamp changes state (from ON to OFF, or vice versa) each time that a button or pad is operated. The Fig 3 circuit uses relay contacts to switch power to the lamp.

The Fig 4 circuit also has a relay output, but is activated via touch pads rather than switches. The Fig 5 circuit switches the lamp directly via a triac.

All of these circuits are designed around a CD4013 dual D-type flip-flop, and use only one half of the IC, configured as a divide-by-two circuit. The clock input pulses to this circuit must have rise times less than 15 uS. In the Fig 3 circuit the clock pulses are obtained by operating one or other of the push buttons. Each time a button is closed, C2 charges rapidly via C1 and the button switch, and provides the required fast-rise-time clock pulse: C2 discharges slowly via R2 when the button is opened, thus eliminating false-triggering via switch-bounce effects, etc. Q1 and the relay and lamp change state each time a push-button switch is operated.


Figure 4 shows how the above circuit can be modified for operation via so-called 'touch pads'. Normally, the input of IC1a is held high via R1. Whenever a finger is pressed against a touch pad, the skin resistance pulls the input of IC1a low by potential-divider action and causes IC1a output to switch high and rapidly charge C2 via D1. The transition in the C2 voltage is amplified (and effectively speeded up) via IC1b and IC1c, thus providing the required clock pulse to IC2.

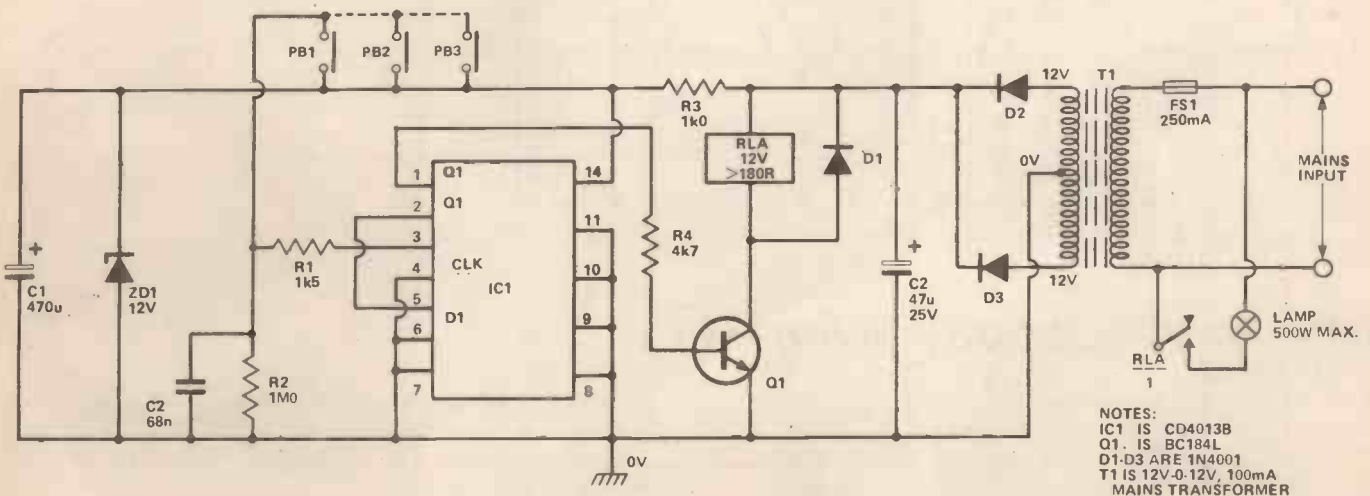If you decide to build or experiment with the Fig 4



NOTES:
 IC1 IS CD4013B
 Q1 IS BC184L
 D1-D3 ARE 1N4001
 T1 IS 12V-0.12V, 100mA
 MAINS TRANSFORMER

Fig. 3. A relay output, multi-point electronic light switch using single ON/OFF push-button switches.

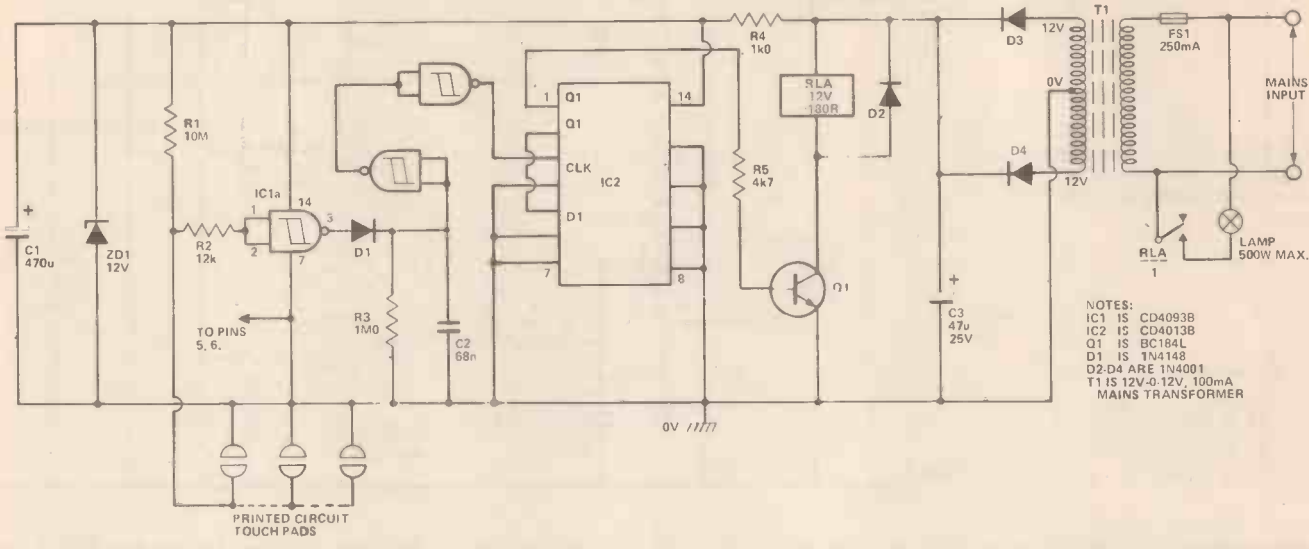


- NOTES:
 IC1 IS CD4093B
 IC2 IS CD4013B
 Q1 IS BC184L
 D1 IS 1N4148
 D2-D4 ARE 1N4001
 T1 IS 12V-0.12V, 100mA
 MAINS TRANSFORMER

Fig. 4. A relay output, multi-input electronic light switch using single ON/OFF 'Touch pad' switches.

circuit, note that the IC1 circuitry is rather susceptible to hum pick-up, so the connections to the touch pads should be made via screened or twisted flex. Also, the touch pads can be disabled by moisture or dampness. The touch pads can, however, be formed in a variety of decorative patterns, and the circuit can make an excellent conversation piece.

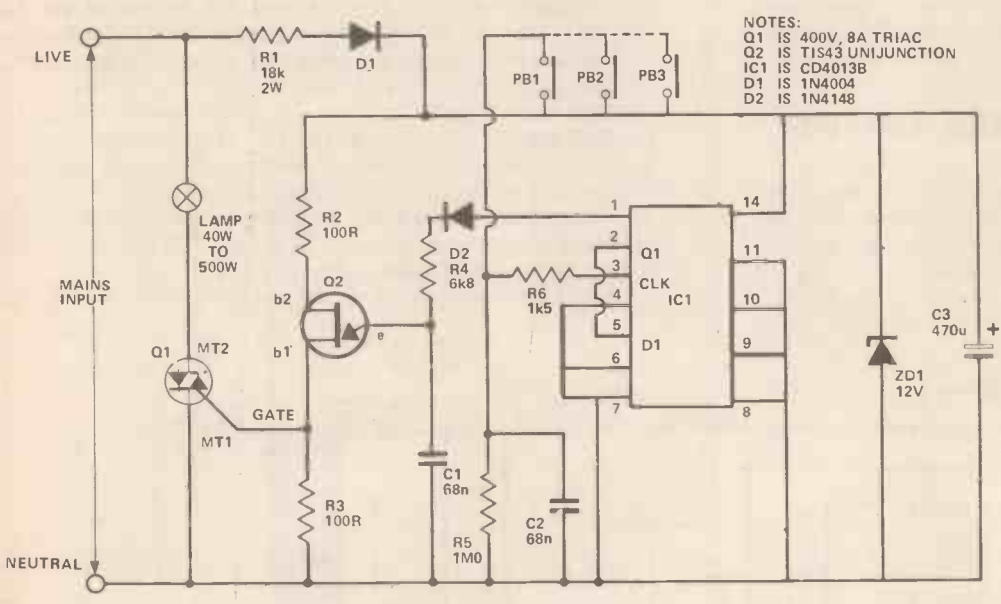Finally, Fig 5 shows a Triac-output version of the multi-input push-button operated circuit. Here, the output (pin 1) of IC1 changes state each time a push button is operated. When the output is high, unijunction oscillator Q1 is enabled via D2, and feeds trigger pulses to the gate of Triac Q1, which turns on and activates the lamp. When the output of IC1 is low Q2, Q1, and the lamp are off.



- NOTES:
 Q1 IS 400V, 8A TRIAC
 Q2 IS TIS43 UNIUNCTION
 IC1 IS CD4013B
 D1 IS 1N4004
 D2 IS 1N4148

Fig. 5. A Triac output, multi-input electronic light switch using single ON/OFF push button switches.

ELECTRONIC PORCH LIGHT SWITCHES

While we're on the subject of rewiring, how about adding a touch of class to your home by fitting a sophisticated porch-light switching system? Possibly the Fig 6 circuit, which turns the light on automatically when darkness falls. Or the Fig 7 circuit, which turns the light on for a fixed period (about ten minutes) whenever the

START button (a 2-pole door bell switch?) is operated. Or perhaps the 'intelligent' circuit of Fig 8, which does the same job as the Fig 7 circuit, but operates under dark conditions only.
 The Fig 6 circuit can be set for manual or automatic operation via SW1. Assume that SW1 is in the AUTO

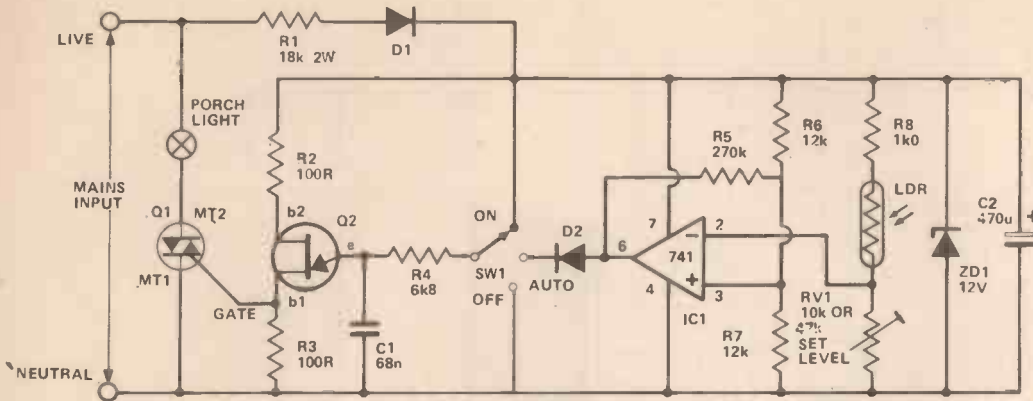


Fig. 6. An automatic (dark activated) porch light.

NOTES:
 Q1 IS 400V, 1A TRIAC
 Q2 IS TIS43 UNIJUNCTION
 IC1 IS 741 OP-AMP
 D1 IS 1N4004
 D2 IS 1N4148
 LDR IS ORP12 OR SIMILAR


position. Operational amplifier IC1 is wired as a light-sensitive switch, with its trigger level adjustable via RV1. The output of the op-amp is high under dark conditions, thus enabling unijunction oscillator Q2 and turning Triac Q1 and the lamp on. Under bright conditions the op-amp output is low, so Q1-Q2 and the lamp are off.

If you build this circuit, place the LDR in a position where it won't be influenced by the shadows of people or animals standing in the porch, or by the light of the porch lamp. RV1 should initially have a value of 10k, but can be increased to 47k if you can't get enough adjustment to give triggering at your required 'darkness' level.

The Fig 7 circuit can also be set for manual or automatic operation via SW1. Assume that SW1 is set to the AUTO position. IC1 is a 555 timer. Its output (pin 3) is normally low, but goes high for a period determined

by the R7-C2 values when a negative-going START command is fed to pin 2. At the end of the period the output automatically switches low again. The period can be terminated part way through the cycle by briefly operating OFF switch PB2, or can be extended by operating REFRESH switch PB3. Q1-Q2 and the lamp are on when the output of the IC1 is high, and are off when it is low.

Finally, Fig 8 shows how the above circuit can be modified so that it only operates under dark conditions. Here, the LDR and RV1 act as a potential divider whenever PB1 is closed, and ensure that a suitable trigger pulse (below 1/3rd of the supply voltage) is fed to IC1 only when PB1 is closed under dark conditions. The LDR must be placed in a position where it won't be influenced by the shadows of people or animals standing in the porch.

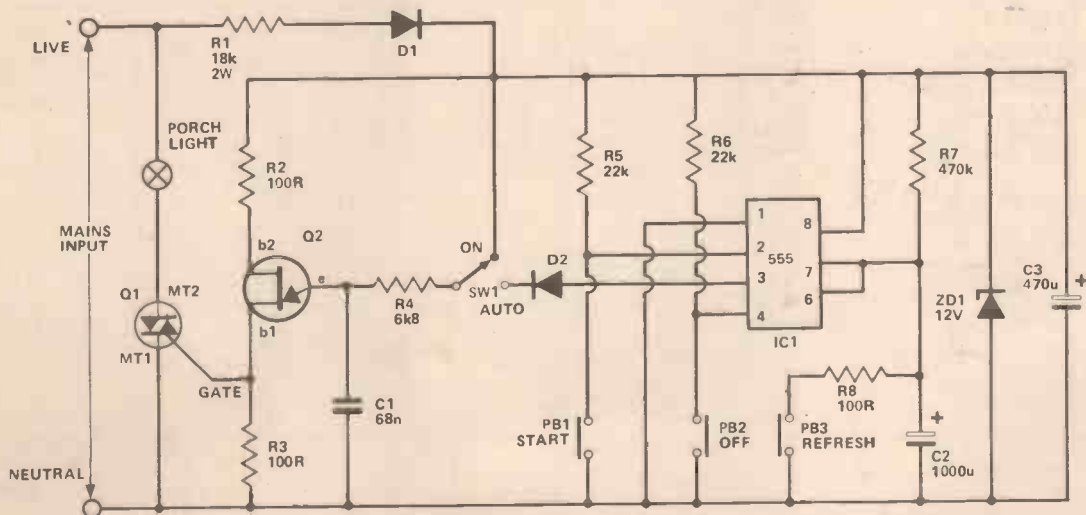

NOTES:
 Q1 IS 400V, 1A TRIAC
 Q2 IS TIS43 UNIJUNCTION
 IC1 IS 555 TIMER
 D1 IS 1N4004
 D2 IS 1N4148

Fig. 7. An auto turn-off porch light. The light turns on when the 'start' button is operated and turns off automatically after about ten minutes. The period can be extended by operating the 'refresh' button part way through the cycle, or the period can be terminated by pressing the OFF button.

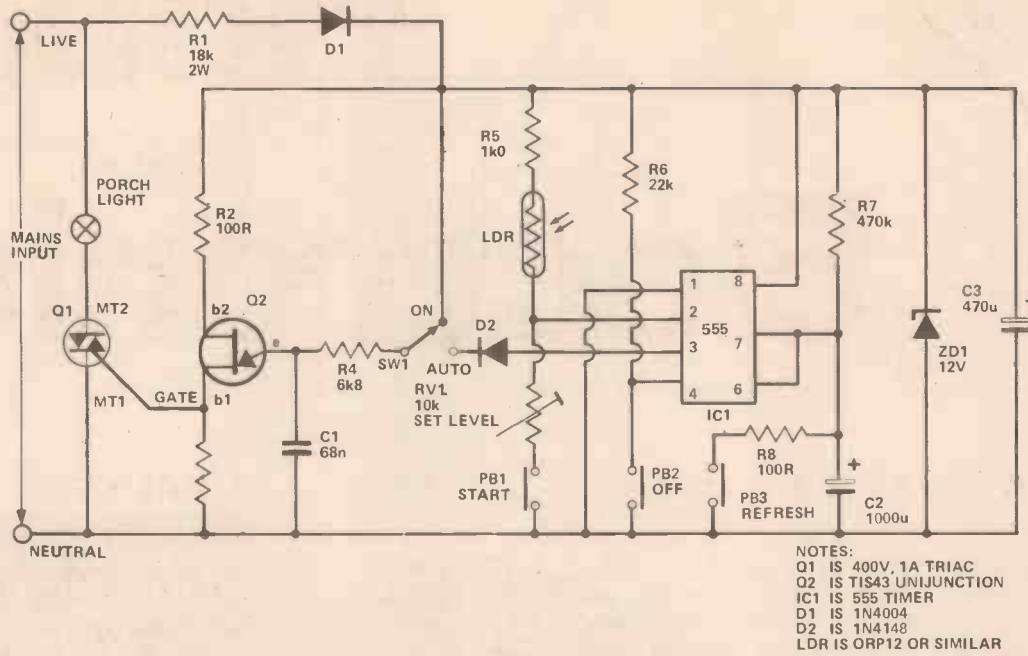


Fig. 8. An 'intelligent' auto turn-off porch light. The light only operates under 'dark' conditions.

Note in the Fig 2, 4, 5, 6, 7 and 8 circuits that we've shown the LIVE side of the mains going to the lamp and the NEUTRAL side going (effectively) to the switches. This conflicts with normal practice. You can reverse the input connections if you prefer.

Again we must emphasise that mains electricity is fatal stuff to play around with. We strongly advise against anyone not completely familiar with mains electricity not to build these circuits unless they have expert assistance. We would hate to lose any of our readers. **HE**

Short Circuit

LOW BATTERY VOLTAGE INDICATOR

This circuit can be used to monitor a supply voltage of between about 5 and 25 volts (30V absolute maximum) and will switch on a warning light if the supply falls below some predetermined threshold level.


Although only five components are used, the circuit is actually quite sophisticated, giving good reliability and precision. This is due to the use of an 8112 voltage detector IC. A comparator forms the heart of the device, and a highly stable internally generated reference voltage is fed to the inverting (-) input of the comparator. Its non-inverting (+) input is available at pin 3, and in this circuit it is fed from the supply lines via the potential divider circuit which consists of R1 and RV1. The output of the comparator is available at pin 4, but is obtained by way of a constant current generator which limits the output current to a nominal figure of 7 mA.

If the voltage at the non-inverting input exceeds the reference voltage, the output assumes the high state and LED indicator D1 is not switched on. If

the non-inverting input voltage falls below the reference level, the output then goes low and power is applied to D1. The constant current source limits the LED current to a suitable level. In practice RV1 is adjusted so that with the supply voltage at its minimum

acceptable level the non-inverting input is at a potential just marginally higher than the reference voltage. In other words it is adjusted for the lowest voltage that does not cause D1 to be switched on. A fall in supply voltage below the threshold level then takes the

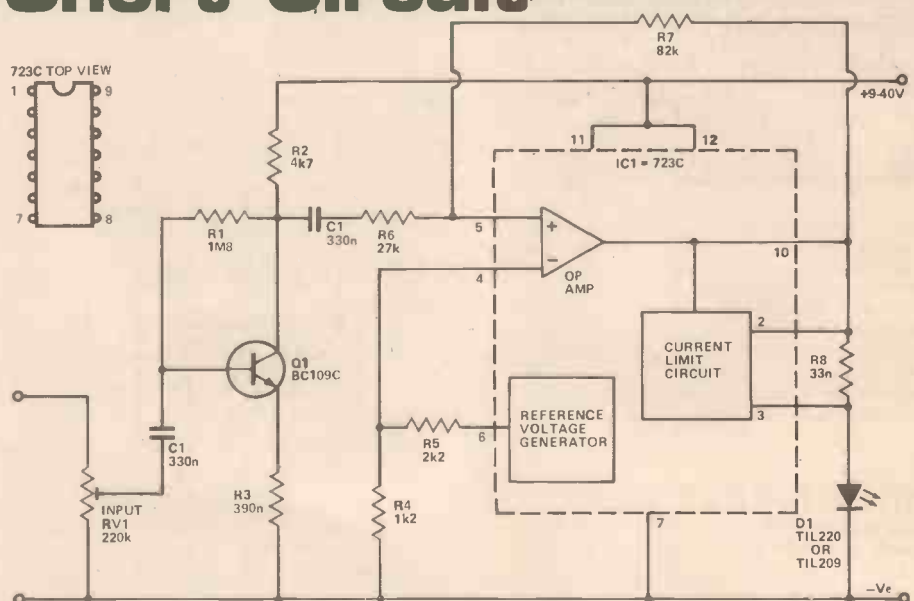non-inverting input below the reference voltage and switches on the warning light. C1 decouples any stray pick-up which could otherwise cause spurious triggering of the circuit. The quiescent current consumption is typically only about 50 uA.



**Next
Month**

Hobby Electronics

HAPPY BIRTHDAY TO US

Yes, it's HE's first birthday next month, as a special treat to all our readers we will be featuring an eight page pull-out section containing masses of useful data. How to de-code those colour coded components, how to connect up all those little legs on ICs and transistors, everything in fact (well, nearly everything) you'll ever need to know.

TV BROADCASTING




Even if you can only get two channels (industrial action notwithstanding) you can still find out all about how those exciting episodes of Crossroads and the Magic Roundabout (no they're not using the same actors) reach the flickering picture box in the corner of your living room. What dramas never reach the watchful eye of the camera, how high is Nicholas Parsons in real life, these are some of the questions that probably won't be answered next month.

WRIGHT FIRST TIME


Congratulations to Mr D. J. Wright of Bodmin, Cornwall, and Mr P. R. Cheeseman of Birstall, Leicester, for winning the first and second prizes in our August Scope competition — more details next month. In the meantime we'll be contacting all the winners and runners-up by post.

HEBOT

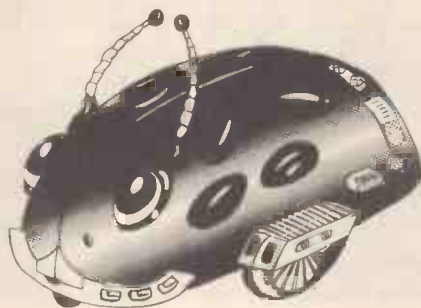

From the darkest corners of the HE workshop comes a new terror to strike fear into the hearts of brave men (and women, if they dare). HEBOT is here, from an original design by the Gonoids of Andromeda it will over the next few months develop into a creature to rid you of the mother-in-law for ever. The first part next month will describe how to assemble the locomotive and propulsive support mechanism (Chassis and drive gear to mere earthlings) and basic sensory perceptors. The basic module will perform evasive manoeuvres and month by month we will attempt to increase its 'intelligence' until it is able to exist on its own. If our plans are fulfilled they will wipe out the human race HEBOTs will control the universe . . . Exterminate, we will exterminate . . .

INTO LINEAR ICs

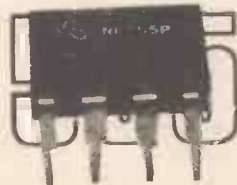

This month just over half-way through the series, Ian Sinclair takes leave of the 741 to start anew with the famous 555 timer, as usual all of the circuits are practical, tried and tested. For those of you following the series with the Eurobreadboards we will include all of the codings for the board.

KIT REVIEW



Something out of the usual in the way of kits next month, we shall be looking at a rather novel car burglar alarm. This new kit should be of interest to anyone wanting to protect their vehicle, without having to take out a second mortgage to buy the kit.

BREAKER ONE FOUR



Following our disclosure this month you can be sure that next month's Breaker One Four will have some more very interesting revelations. Remember Breaker One-Four is Britain's first and best, regular Citizens Band feature.

MINI-MODULES

We've been promising some Vero-Board based projects. Well, here they are, ten of them, all using a commercially sized piece of strip board. All of the Modules can be used either as building blocks for larger, more ambitious projects or used on their own as projects in their own right.

The November issue will be on sale October 12th

The items mentioned here are those planned but circumstances may affect the actual contents




It's playtime kiddies: The juvenile staff of HE aided and abetted by the playful, Rick Maybury have put the latest crop of electronic games through their paces.

OTHER ELECTRONIC MAGAZINES PLEASE NOTE, do not under any circumstances attempt to do an electronics games survey, you just won't be able to get any work done. It's not the constant distraction of bleeps, squarks and other outlandish noises, not even the perpetual outbursts of cheering and booing from other members of the office staff, it's the near impossible task of tearing yourself away from the games long enough to put pen to paper.

Having tied our hands behind our backs to prevent any spurious attacks of button pushing and typing with our noses we'll attempt to elaborate on some of the latest machines that have put this months HE in serious jeopardy. If this issue has more than its usual quota of spelling mistakes, you'll know why.

A GAME IN THE HAND

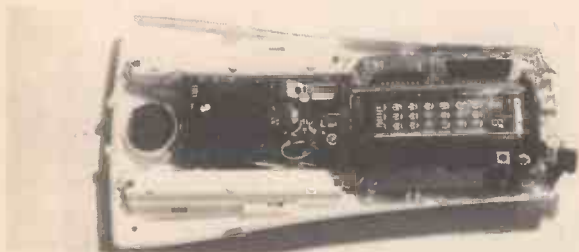Basically all the electronic games we've managed to prise away from the various companies (take them back, please or there won't be another issue of HE) fall into one



Inside the Master Blaster, the green LED display (right) can be seen with the three rows of flying saucers and the score.

of three categories. The first (and probably oldest) are the video games, they're the ones you plug into the back of your telly. The second group are the most recent arrivals to the electronic games field, the hand-held games. Usually not much larger than a medium sized pocket-calculator and with one or two exceptions, they play only one game. The final and definitely the most demanding are the specialist and novelty, micro-processor games, such as the many versions of chess, backgammon, and now completely new games like Simon.

HISTORICAL NOTE

Without doubt, electronic games are a product of the seventies. (Although versions of electronic dice etc have been the mainstay of several notable electronic magazines for many years).

Undoubtedly the daddy of them all was the famous AY 38500 games IC from General Instruments. It was the first truly domestic version of the now legendary pub game of 'tennis'. It offered four basic 'ball and paddle' games of tennis, squash, solo and football, as well as a rather dubious shooting game that rarely had a range of more than a few feet. All the games had sound effects, and were revolutionary in that all the video processing, sync, sound, and video information were generated on one 28 pin chip. To get the games going required only a simple oscillator, paddle controls, modulator and a power supply.

The eventual demise of the AY 38500 was brought about by the development of the so-called programmable game. Instead of producing large quantities of

'dedicated' games, ie putting all the video generating circuits on one chip, the games manufacturers kept all the standard circuitry in a basic control box, along with a set of controls etc and loaded the various game information into the everpresent microprocessor via a IC memory or PROM. (Programmable Read Only Memory) These proms are usually standard 'off the shelf items', the game information is permanently 'burned' onto the IC by fusing microscopic links within the IC.

Perhaps it's a little unfair to say the dedicated game is dead, one company, Teleplay, have succeeded in making a sort of programmable TV game with the dedicated chips although we fear that sooner or later the supply of new games using this format will dry up. However its worth bearing in mind that these machines are very much cheaper than the present generation programmable games.

All the current crop of TV games are in full colour (of course) and the sound is modulated onto the TV speaker.

Examples of the old AY 38500 ICs are still to be seen on sale for as little as 50p in some cases, so it will not be disappearing just yet. Indeed black and white versions can still be bought in Woolies and Dixons for under a tenner.

It's interesting to note that the company that developed the idea of using TV sets for such purposes still hold the patents and presumably are still raking in the royalties, perhaps we should patent some of our projects, you never know

POWER TO YOUR POCKETS

Now you can rule the universe from the comfort of your own jacket pocket. Its always been a little impractical to carry a TV set around with you (unless you've got a Sinclair Microvision and very good eyesight) so it was a logical step for the games manufacturers (with spare capacity after flooding the calculator market perhaps) to




It took us a long time to think up a convincing excuse to print this picture, we finally decided the HE just visible in the centre was justification enough.

turn their attention to the portable market. All of the games are pretty much the same requiring a degree of manual dexterity (with a couple of exceptions, like Mastermind) to destroy malevolent UFOs, drive race cars or play soccer. Nevertheless the accompanying sound effects coupled with an almost paranoid horror of being beaten by a machine ensures that they will not be put down till they have either been beaten or thrown in disgust at the nearest brick wall. One or two of our samples came perilously close to ending their days in a less than solid-state.

BRAIN GAMES

Our last group are what might be called the 'thinking mans' electronic games, they include the almost unbeatable chess, backgammon and now bridge, playing microprocessors, they've all had the treatment. The other new games (as opposed to chess, being hundreds of years old) include Simon, somewhat overrated, and Zodiac, a fortune telling micro. Lastly we have Owl, from the look of the box we would deduce its intended for the 5-10 years age range but without exception every member of the HE staff has secretly played with it!

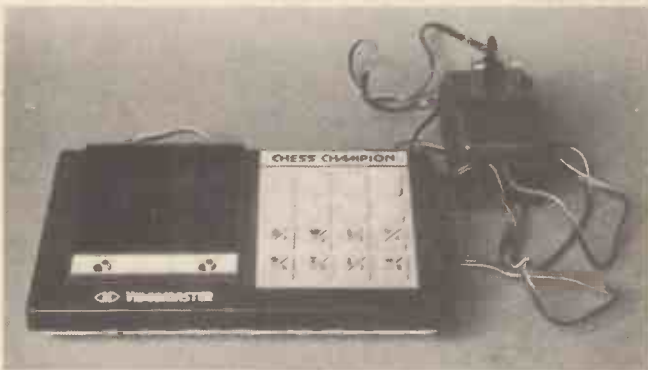

The Videomaster Chess Champion with its external AC adapter. Unlike the Challengers you require a separate board and pieces.


TURN THE TABLE

So now read on. On the following pages we've included as many details as possible but as always 'one mans meat'. All we can say is, go along to your local stockist and play with a few, then after two days if he still hasn't managed to get you out of the shop buy one.

LIST OF SUPPLIERS

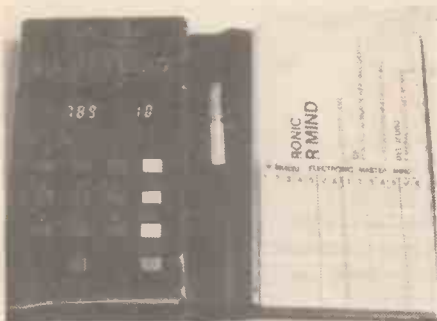1. Spectrum Marketing
12 The Shrubberies
George Lane
South Woodford
London, E18
2. NIC Models
27 Sidney Road, London N22 4LT
3. Videotime Products
56 Queens Road, Basingstoke
Hampshire
4. Comp Computer Components
14 Station Road, New Barnet
Herts.
5. Milton Bradley Ltd
Century House
61-63 Uxbridge Road, Ealing
London W5 5SA

HAND HELD GAMES Hand-held games are being hailed as the latest 'craze' in the 'States. Well, crazes come and go (whatever happened to Skateboards?) but this time we believe these games will really catch on. Most of the games are fairly limited in that they only play one or two



MASTERMIND

An electronic version of the very popular board game, the machine sets up a 3 to 5 digit code that the player must guess (or work out if you're very clever) by entering numbers on a keyboard. The game comes in a very attractive wallet with score cards and a pen. The game allows up to two players, where the opponent can manually set a code. Battery operated, no sound effects, price £15.85, supplier (2).

A real thinking man's game, the wallet and pen made it even more attractive especially for long train journeys. It may look a little pricey but we considered that it would have lasting appeal and was not a game that could ultimately be beaten as it would constantly generate new and random codes.



ENTERPRISE

At the time of going to press we had not actually received a sample of Enterprise so we can only go by the publicity handout. It has 3 games as well as being full four function calculator, the games are Speedway, Pontoon and Brain Drain. Battery operated, no sound effects, price £24.95, supplier (2).

We can't really comment on this one, but from our picture of it it looks very interesting indeed. We liked the idea of it having a calculator, something other manufacturers might consider.



LIL GENIUS

This is definitely one for the kids, it is a mathematical game, you simply enter in your sum and by pressing a series of buttons the bespectacled youth will flash either his green eye if you are right or his red eye and sound a buzzer if you are incorrect. Battery operated, sound effects, price £6.45, supplier (1).

This was one of the least pretentious games, unashamedly for the 5 year olds, well worth thinking about if you have a budding mathematician in the family and your maths are none too hot.



UFO MASTER BLASTER

This game has one of the more dramatic displays, the object of the game is to launch your missiles before the approaching flying saucers reach your position at the bottom of the small screen. Your missiles are controlled by a 3 position switch and launched by pressing the red fire button. Battery operated, sound effects, price £21.95. Supplier (1).

The sound effects on this game are superb, a really exciting, though somewhat pricey game. We particularly like the futuristic looking case which ensured it was never left alone for long.



BATTLESTAR GALACTICA

Another variation on the Master Blaster type game, though this time without the superb graphics of that game. The object of the game is to destroy with the aid of steerable missiles oncoming UFOs. Battery operated, sound effects, price £15.90 supplier (2).

For anyone with limited funds and a yen for the space war type game this would be ideal. This is again a reaction game, the object is to destroy as many UFOs as possible in a given time, but ultimately beatable with perseverance.

games (with exceptions) but they are like like good books, difficult to put down. We won't recommend any specific games, after all "one man's meat . . .", what we will say is, look out for the games that are not easily beaten and won't be put to one side after a couple of hours play.



SOCCER

A one or two player game, the 'pitch' (or half of it at least) is represented by little LED men dashing about trying to prevent your man from scoring a goal. Your man is moved about by a series of four positional controls and a 'shoot' button kicks the ball from his position. There are two game speeds and each shot can be deflected by opposing players, who really do whizz about on the fast speed. Battery operated, sound effects, price £21.50 supplier (2).

A very interesting game, especially for football fans, the sound effects, goal scoring tune and half time whistle are most impressive. We found that the fast speed was almost impossible to play except by luck. Definitely one for the football buffs.



DIGITS

An electronic variation on the mastermind theme, the machine sets up a hidden code which the player then must guess in as few attempts as possible, it was unfortunate that this game was so similar to the genuine Mastermind game from Invicta, interesting nevertheless. Battery operated, no sound effects, price £13.95, supplier (1).

A good game for enthusiastic code-breakers, as we have said the genuine Mastermind is somewhat similar if not better. Worth thinking about if cash is tight, otherwise the proper Mastermind for a few pounds more is a better deal.



ROAD RACE

The object of this game is to steer a race car indicated by a bright LED up a race track full of slower cars. The car will progress up the track until it either reaches the end or is hit by a slower car whereupon it will be knocked back down the track. The track has to be covered four times before the game is over. Battery operated, sound effects, price £15.90 supplier (2).


Quite a novel game, although we suspect that the displays used in Road Race and Battlestar are the same. Again once the game had been beaten it rather lost its appeal. Good table top game to leave lying around when the neighbours call.



AMAZE-A-TRON

This is basically a maze game not relying on any kind of manual dexterity. In all there are 8 variations and the player must find his or her way from the starting point to the finishing point using coloured pegs on a keyboard. This game is unusual in that it has a two player game. There are apparently over one million variations so it should retain interest for some time. Battery operated, sound effects, price £17.95, supplier (1).

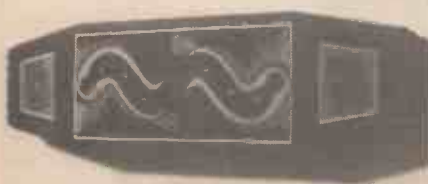Quite an interesting game, we particularly like the little tunes and sound effects it made during the game, again this game produces a certain amount of frustration, especially to the impatient. Worth considering.



ZAP

A two player game, each player has to punch a large button which reverses a snake-like line of LEDs, the speed of the LEDs increases until the line of light eventually 'breaks through' and hits the home base. A score is indicated after each round by a number of LEDs at each end. Battery operated, sound effects, price £10.95, supplier (1).

Not one of our favourite games, we found that it was, to a certain extent easy to beat, good fun nevertheless. This game would probably suit a lower age range as adults tended to get rather brutal with it.

VIDEO GAMES There are numerous variations on the AY38500 type games and as most people have either got one or have played one we won't be reviewing a particular model. One dedicated game, **Starchess**, we have included because we felt that it was just about the best single game machine we have ever seen.



ATARI VIDEO COMPUTER

The Atari was the first of the so-called 'cartridge programmables'. The current range comprises some 30 cartridges offering up to 50 games and variations. Four different types of controllers (two sets come with the basic unit). We found that for most of the games the basic paddle and joystick controllers are quite adequate. The new Chess cartridge is claimed to be one of the strongest chess programmes yet, unfortunately our sample was an American standard NTSC cartridge so we were unable to fully assess it on our telly. Powered by external AC adaptor sound effects on TV speaker, basic price £159.95 additional cartridges £14.95 supplier (3).

This game and its range of cartridges brought the office to a complete standstill for over a week until someone had the bright idea of taking it home. (Bring it back please). The graphics are superb in colour and although the novelty games like Outlaw, Basketball and Combat are good fun we found the simpler games of skill and reaction like Breakout (just like the pub game but with many interesting variations) and Surround had a longer lasting appeal. A really great game if you're prepared to spend a few bob. Highly recommended.



STARCHESS


Based very loosely on the ancient game of Chess this game does not actually play, rather it displays. All the pieces except the pawns (and King) make the same moves as in ordinary chess but have the added capability of being able to 'fire' missiles at your opponent from a limited missile store and 'warp' from the board (and return after a random time onto a random square). Powered by an AC adaptor, sound effects on internal speaker, price £63.93 supplier (2).

Well, what can we say, this is our kind of game, requiring a great deal of thought and skill (like a conventional game of chess). We thought it a pity that you couldn't play ordinary chess, but the superb sound effects and clever graphics more than made up for that. We particularly liked the way the pieces resembled space vehicles and the very good hand controllers. Recommended for bored chess enthusiasts.



This game is unusual, in that it is programmable but uses 'dedicated' chips. Compared with the Atari it has less to offer in the way of variety but considering the price difference it is well worth thinking about. The game is available in either ready built or kit form, additional controllers coming with each game as required. Powered by AC mains adaptor, sound on TV speaker, price £35.00 supplier (4).

There can be no doubt that apart from Starchess the only TV games worth buying are the programmables. Single game units tend to become obsolete very quickly indeed. The Teleplay comes somewhere between the two provided the manufacturers can keep a supply of new games coming it will give the larger more sophisticated games like the Atari a hard time. We liked it a lot and would recommend it to anyone. Even as a kit it is well worth buying because it will keep you interested that little bit longer.

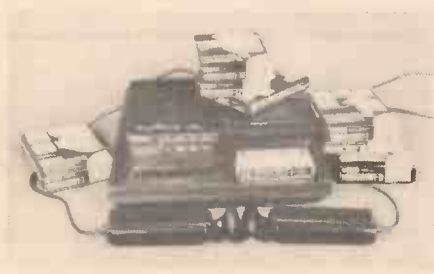

GRANDSTAND

This programmable video game represents a good balance between the Atari and Teleplay, it is a good deal cheaper than the Atari, as shown by the quality of graphics. This is not however a reflection of the games themselves, they are all very challenging. Powered by external mains adaptor, sound effects, price £79.95 additional cartridges £12.95, supplier (3).

We were slightly disappointed by the hand controls, they lacked the precision control of the Atari, we felt they had tried to incorporate too many actions onto too small a unit, they would have been much better offering maybe two different types of control box. The games were all very good (Breakout could have been even better with different controls) the maze game we especially liked. Worth considering if your funds lie somewhere between the Atari and Teleplay.


Electronic Games

SPECIALIST GAMES We decided to call these 'specialist' games simply because they couldn't be put into any other category. From the most up-to-date speaking Chess Challengers to the Marksman game (a secret favourite) they cover so many different fields it would be impossible to call them anything else.

CHESS CHALLENGERS

At the moment there are three Chess Challengers in the series. The latest arrival being the Voice Chess Challenger that actually speaks its moves. It has 9 levels of play from beginner to expert and an 'infinite' mode that will continue to compute a move until told to do otherwise. All of the Challengers have many, many important features, far too numerous to list here. We strongly recommend that you go along to your local stockist and look very carefully at what is on offer. Also worth bearing in mind are the excellent Boris Chess computer and the Video-Master Chess machine. All the Challengers operate from an external AC adaptor, prices, Voice Challenger — £249.95, Challenger 10 (10 levels) £169.95 and Challenger 7 (7 levels) £99.95 Supplier (1).

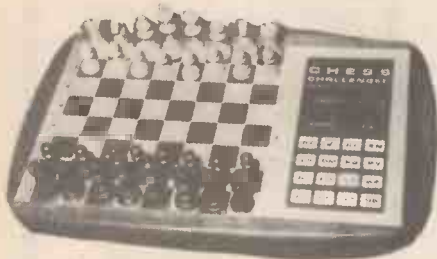
It's difficult to give an appraisal of any of these machines, we're all lousy chess players, our advice is to go along to your local stockist and give them a quick game. Convenience of use is pretty much a matter of choice, we prefer the ones that include a board and a set of pieces.



BRIDGE, BACKGAMMON AND CHECKER CHALLENGERS

Three relatively new games, the Bridge machine in particular is very advanced. The Checker Challenger (Draughts) is great fun but just a little pricey. The backgammon game again has many important features but we felt in all cases that the price of these games put them firmly into the 'enthusiasts only' bracket. All are powered by AC adaptors, prices; Bridge Challenger £299.95, Checker Challenger £54.95 and Backgammon Challenger £94.95. Supplier (1).

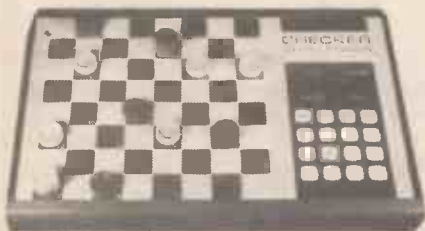Without going too deeply into these very sophisticated machines we would think that they have only a limited appeal, especially at those prices but are well worth considering if you are really keen on one particular game. All of the machines seen play their respective games extremely well and a good to above average player would be hard put to consistently beat any of them.



SIMON

Outwardly this looks like a rather simple sort of game, Simon generates a random sequence of flashing lights that the player (or players) has to duplicate by pressing the appropriate button. The sequence gets longer and longer until a mistake is made whereupon it blows the loser a raspberry. Battery powered, sound effects, price — around £29, supplier (5).

A great game for parties though not much fun on your own. Worth considering if you do a lot of entertaining, it will quickly cure any dull moments.



ZODIAC

This is claimed to be the first Astrology computer, when supplied with information such as date of birth etc, it will make certain 'do or don't' predictions, complete horoscopes and what your stars fortell on a past, present or future basis. Battery powered, price £25.95, supplier (1).

We wouldn't recommend anyone to take this too seriously but as a source of amusement it may be well worth looking at. Just the thing for clairvoyant aunts perhaps?



MARKSMAN

This game was one of our favourites, an Owl shaped target (poor Owl) has to be 'shot' with a beam of light from a replica .38 revolver. When the target is hit the Owl's eyes light up and it emits a rather pitiful squarking noise from its nether regions, great stuff. Battery operated, sound effects, price £5.90, supplier (2).

There's no doubt about it, this game was great fun. The gun sights were a little inaccurate but that was easily compensated for. We found the range to be in excess of 20 feet with fresh batteries. Avoid the temptation to blow on the gun barrel as this steams up the lens. Great for Christmas.



INTRODUCING FROM BELTIME — PICOQUARZ MICROPROCESSOR ALARM CHRONOGRAPH



- ★ 2 alarms
- ★ 2 chronos
- ★ hourly chime
- ★ stainless steel
- ★ mineral glass

30501 SHS

Hours (program 12 or 24), minutes, seconds, day (multi-language program). Date, 1/100th sec chrono 24 hrs, countdown chrono with alarm, back-light.

ONLY £39.95
(inc. VAT P&P)
RRP £69.95



GRANDSTAND — £79.95
inc.
21 Videocarts — **£12.95 each**
PHILLIPS G7000 —
£149.95 inc
12 Videopack — **£13.95 each**
ATARI VCS — £159.95 inc
14 Game Program **£14.95 each**

FULL DETAILS ON REQUEST

VIDEO GAMES
New cart-ridges now in stock



LCD ALARM

24-hr. alarm
Hours, mins, secs., date, month, back-light, auto calendar.
Adjustable stainless steel bracelet.

12-month guarantee

ONLY £12.95
(inc. VAT P&P)

VT10
Same day despatch

LCD ALARM CHRONOGRAPH VT06

All usual features.
Perpetual calendar, day, date, month and year.
24-hr. alarm with on/off indication.
1/10 second chronograph measuring set, lap and first and second place times.
Dual time zone facility.
Night light.
12-month guarantee



Same day despatch
Same as ET1 offer

ONLY £17.95 (inc. VAT P&P)

LADY'S LCD ALARM

24-hr. alarm
Hours, mins, secs., date, month, back-light, auto calendar.
2 time zones bracelet
countdown alarm
12-month guarantee



VT15

ONLY £19.95 (inc. VAT P&P)
gilt or silver

SOLAR LCD ALARM CHRONOGRAPH

24-hr. alarm with on/off indication.
1/10 second chronograph measuring net, lap and first and second place times.
Dual time zone facility.
Night light.



Same day despatch

ONLY £27.95 (inc. VAT P&P)

VT12

12-month guarantee, 15% VAT included, Cheques or P.O.s or telephone Card No. to




VIDEOTIME PRODUCTS, 56 QUEENS RD.

BASINGSTOKE, HANTS RG12 1REA. Tel: (0256) 56417 or 26620 TLX: 858747
FACTORY AGENTS WANTED MONEY BACK GUARANTEE. OFFERS SUBJECT TO AVAILABILITY. TRADE ENQUIRIES WELCOME



Metal Cases

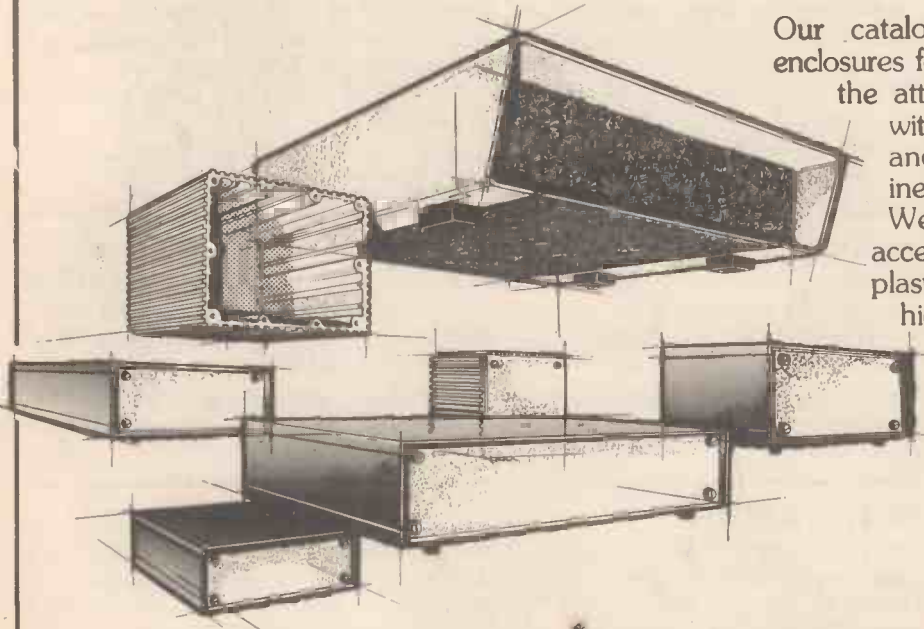

Our catalogue contains small metal enclosures for every application including the attractive new G range cases, with unique integrated chassis and sloping visor front and the inexpensive kit-form Veropak. We've also got circuit boards, accessories, module frames and plastic boxes — all to the highest standard to give your equipment the quality you demand. Send 25p to cover post and packing and the catalogue's yours.



VERO ELECTRONICS LTD RETAIL DEPT.
Industrial Estate, Chandler's Ford,
Hampshire SO5 3ZR
Tel: (04215) 62829

Analogue Audio Frequency Meter

Get in tune with the modern age . . . economical testgear — made to measure

THIS LINEAR SCALE AFM will enable you to resolve frequencies from 10Hz to 100kHz in four decade ranges. It is low in cost yet high in performance. Accuracy is unaffected by the waveshape of the input signal and the unit is sensitive to input levels down to about 200 mV. The input circuit features a protection diode network and the maximum safe input voltage is effectively limited by the rating of the coupling capacitor C1. The unit operates from a single 9 volt battery and

current drain is low giving a useful life from a PP3 or equivalent source.

CHEAP CHIPS

Only two relatively cheap chips are used; a 3140 bi-MOS op-amp which performs signal pre-amplification and conditioning, driving an ordinary 555 timer configured in the monostable mode. Timing components are selected by a five position range control which also



Calibrating the HE Audio Analogue Frequency Meter against the workshop signal generator. For those without any test equipment an alternative method is outlined in the text

functions as the power switch. Only a handful of other components are required and accuracy, after calibration, is determined by four fixed resistors.

CONSTRUCTION.

Construction may take many forms. However, use of a PCB aids assembly and reduces any chance of error. Our design is highly recommended. In any event, all leads should be kept as short as possible to avoid stray coupling; keeping signal input leads away from the 555 for example.

Construction should proceed in the usual order. Insert the IC holders first, followed by the passive components; resistors and capacitors, paying close attention to the

orientation of the polarised components. Finally insert the diodes and plug the IC's into their sockets. Pin one is indicated by an indent at the top of the package or a dot by the pin itself. Note that the signal 'low' input is separate from the 0V line.

CALIBRATION AND USE

Calibration of the instrument is very straightforward owing to the high input impedance. With the unit switched to the 100Hz range, touch the input with your finger. There will generally be enough stray mains field to provide an adequate signal. This should cause a deflection on the meter and RV1 can be adjusted until a reading of 50 Hz is obtained.

How it Works

The input signal is applied to C1. R1, D1 and 2 provide protection against high input levels. IC1 is a high input impedance op-amp configured as a Schmitt trigger with R5, 6 setting the hysteresis. C2, R2, 3 provide a mid-voltage bias source.

The output of IC1 consists of a train of square waves at the same frequency as the input signal. This triggers the 555 timer which produces a monostable pulse of period determined by selection of range resistor, R9 through R12 at the output pin 3 from each negative excursion. The trigger pulse must be shorter than the output pulse and differentiating network C3, R7, 8 is used to accomplish this.

To avoid inaccuracies owing to falling battery voltage, the output of IC2 is clamped at 5 V6 by ZD1 and the meter is driven via current limiting network RV1, R14. A 5 V6 zener is chosen as it has

a low temperature coefficient. This means that its voltage exhibits little change per degree change in temperature. The reason for this is that the negative and positive temperature coefficients of the zener and avalanche effects almost cancel out in 'zener' diodes of this voltage.

The only possible source of trouble worth mention may be failure of the 555 to trigger at all. This could be caused by the value of C3 being too small. Trouble from this source is unlikely. However, C3 should be as small in value as possible consistent with reliable triggering.

Current pulses from IC2 are averaged in the meter whose deflection indicates the input frequency. To allow for variations in component tolerances, full scale deflection corresponds to about a 75% duty cycle. C5 is a supply decoupling component.

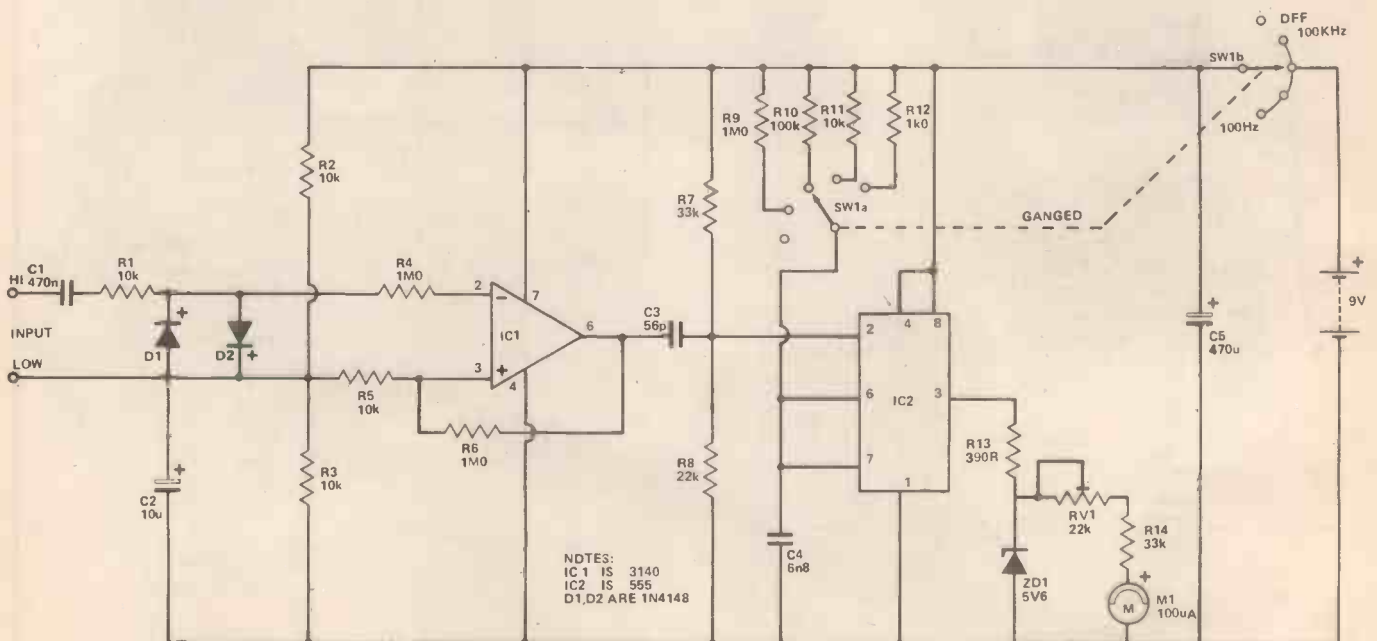


Fig. 1. Circuit diagram of the HE Analogue Frequency Meter

Frequency Meter

Of course if a signal generator of known accuracy is available, you can set up the unit on any desired range. However, the technique described above will enable useful results to be obtained. A feature of the instrument is that only one range need be calibrated; the others falling into line automatically.

In use, select the highest range (100 kHz), this automatically applies power to the unit, then connect the unknown input signal. The reading can be noted and a lower range selected if required. This is to avoid spurious readings which can be obtained on the lower ranges owing to retriggering of the 555 by high frequency input signals. There are no other adjustments to make so all you need now is something whose frequency you can measure (how about the HE siren in this issue?) **HE**


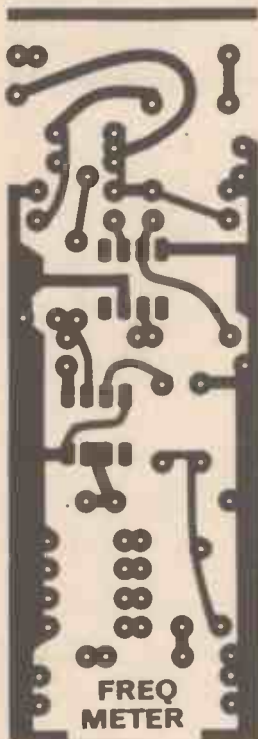


Fig. 2. PCB foil pattern for the AFM

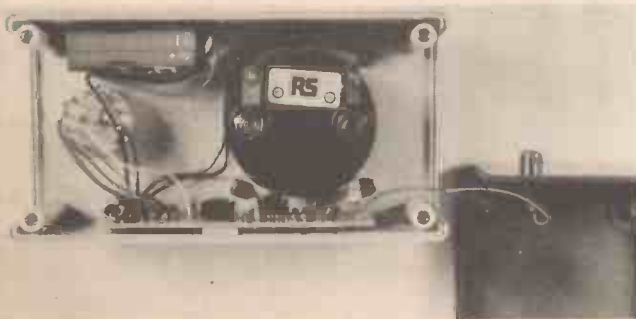

Buylines

All the components should be readily available. Any size 100 μ A meter may be used. Choose one to suit your case . . . and pocket.


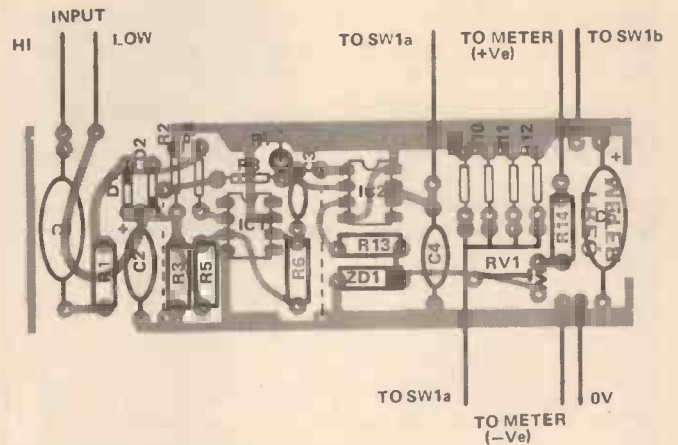


Fig. 3. PCB overlay for the AFM

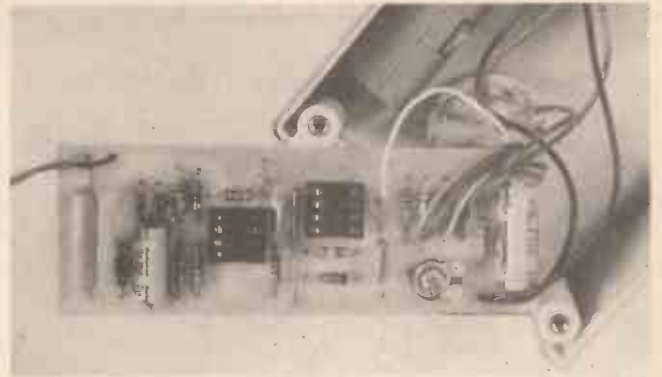

Parts List

RESISTORS (all 1/4W, 5%)

R1, 2, 3, 5, 11	10k
R4, 6, 9	1M
R7, 14	33k
R8	22k
R10	100k
R12	1k
R13	390R

POTENTIOMETER

RV1	22k preset
-----	------------

CAPACITORS

C1	470n polyester
C2	10 μ tantalum
C3	56p polystyrene
C4	6n8 polyester
C5	470 μ electrolytic

SEMICONDUCTORS

IC1	3140
IC2	555
D1, 2	1N4148
ZD1	5 V6

MISCELLANEOUS

Meter	100 μ A FSD
SW1	2 pole 5 way case to suit
PCB	

Approx cost £8

POWER AMPLIFIER CP2-15/20



Each CP2-15/20 contains two identical amplifiers, each of which can give 20 Watts rms into 4 Ohms (15W into 8 Ohms). Alternatively the module may be connected to give 40 Watts into 8 Ohms. Protection is provided against short and open circuit loads, reverse supply connection (as all Magnum Modules) and thermal overload. Transient performance is virtually unaffected by loading and free from overshoot and TIM distortion. THD is typically 0.03% at 1kHz. All this adds up to a versatile and robust amplifier of extremely 'clean' and 'musical' performance.

CP2-15/20 £14.80 incl. (U.K.) £16.80 incl. (Export).

Also available: Pre-Amplifiers, Peak Programme Monitors, Filters, Stereo Image Width Control, Compressor/Expander, Active Crossovers, Power Supplies, Interconnection PCBs, plus all pots, switches, etc.

MAGNUM AUDIO Ltd.

DEPT. HE9, 13 HAZELBURY CRESCENT
LUTON, BEDS. LU1 1DF
TEL: 0582 28887

SEND LARGE S.A.E. FOR DETAILS

SUPERBOARD II AVAILABLE NOW AT £263.35

LOOK!

SPECIAL OFFER. Limited quantity. **MARKSMAN** electronic game. Consists of a Pistol and an Owl target. Shoot the owl dead centre and it responds with flashing eyes and a chirping noise.

Sells in shops for £10-£14
Now Only £5.90
SPACE ALERT ONLY £15.90 EACH
AUTO RACE



FOOTBALL VERSION £21.50

All prices inclusive - P & P free

N.I.C. MODELS

27 Sidney Road, London N22 4LT
01-889-9736

CHESS CHAMPION

6-Level Chess Computer.
Now Low Price £63.95, with adaptor.
STAR CHESS colour TV Game. A space age Chess game.

~~£60-10~~ Our Price **£63.35**, with adaptor.
ELECTRONIC MASTERMIND
Play nine games against the computer, 3, 4 or 5 digits. ~~£16-05~~ Now **£12.85**.

CHROMA-CHIME 24-tune door chimes. **KIT £10.50. BUILT £15.30.**

LOOK!!!

5-pin DIN to 4 x 3.5mm JACK PLUGS. Leads can be used for Audio by replacing Jack Plugs with Phono plugs or use it with your computer by changing DIN plug to Phono plugs. **ONLY £1.25.**

NEW PRICE

SAVE £3

Please allow up to 21 days for delivery

SINCLAIR PRODUCTS. New 10MHz scope pos. PFM200 £52.69, case £3.40, adaptor £3.40, connector kit £11.27. Microwave TV UK model £91.44, mains adaptor £6.88. PDM35 £29.76, mains adaptor £3.40, case £3.40. DM350 £71.82. DM450 £102.17, DM235 £52.66, rechargeable batts £7.99, mains adaptor £3.04, case £9. Enterprise prog calculator with accessories £23.37.

COMPUTER GAMES Star Chess £62, Chess Champion 6 £64, Chess Challenger 7 £91, Chess Challenger 10 £152.50, Voice Challenger £239, Checker Challenger 2 £46, Checker Challenger 4 £88, Atari video computer £147, cartridges £14.32. COMPONENTS 1N4148 1.4p, 1N4002 3.1p, 741 18P, bc182b, bc183b, bc184b, bc212b, bc213b, bc214c 5p, resistors 1/4W 5% £12.10R to 10M 1p, 0.8p for 50+ of one value, 16V electrolytics .5/1/2/5/10/22uF 5p, 100uF 8p, 1000uF 10p, 1 lb FeCl₂ £1.20, data pen 84p, 40 sq ins pcb 64p, polystyrene capacitors E12 63V 10 to 1000pF 3p, 1n2 to 10n4p, ceramic capacitors 50V E5 22pF to 47n2p, zeners 400mW E24 2p7 to 33v 7p, preset pots submit 0.1W 100 to 4M7 7.2p.

TV GAMES AY-3-8500 + kit £9.53. Rifle kit £5.27. AY-3-8610 + kit £16.51. Stunt cycle chip + kit £16.72. AY-3-8603 chip £9.48.

TRANSFORMERS 6-0.6V 100ma 76p, 1/2a £2.50, 6-3V 1/2a £2.01, 9-0.9V 75ma 76p, 1a £2.12, 2a £2.77, 12-0.12V 100ma 92p, 1a £2.65 IC AUDIO AMPS with pcb. JC12 6W £2.08. JC20 10W £3.14.

BATTERY ELIMINATORS 3-way type 7 1/2/9V 300 ma £3.14, 100ma radio type with pre-studs 9V £3.57, 9V+9V £4.79, Car converter 12v input, output 4 1/2/6/7 1/2/9V 200 ma £2.88.

BATTERY ELIMINATORS 3-way type 6 7/9V 300ma £3.14, 100ma radio type with pre-studs 9V £3.57, 9V+9V £4.79, Car converter 12v input, output 4 1/2/6/7 1/2/9V 800ma £2.66

BATTERY ELIMINATOR KITS 100ma radio type with pre-studs 4 1/2V £1.69, 6V £1.49, 9V £1.49, 1 1/2V+4 1/2V £1.92, 6+9V £1.92, 9+9V £1.92. Stabilised 8-way types 3/4 1/2/6 7/12/15/18 100ma £2.98, 1Amp £6.81, stabilised power lvs 2-18V 100ma £2.98, 1-30v 1A £5.95, 2-30v 2A £11.86, 12v car converter 6 7/12/15 1A £4.44.

T-DEC AND CSC READBOARDS s-dec £4.05, u-dec £4.28, u-dec £4.69, u-dec £7.16, 16 bit adaptor £2.31, exp4b £2.64, exp300 £6.61, exp350 £6.62, exp325 £1.84.

BI-PAK AUDIO MODULES s450 £24.03, AL60 £4.97, PA100 £17.33, spm80 £4.57, bm80 £6.08, 100 £17.33, AL30 £4.04, PA12 £1.77, PS12 £1.42, MA60 £36.23.

SWANLEY ELECTRONICS

Dept. HE, 32 Golds Rd., Swanley, Kent.

Post 30p extra. Prices include VAT. Official and overseas orders welcome. Lists 20p post free.

Largest range of quality components in the U.K. — over 8,000 types stocked

Marshall's

Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Also 325 Edgware Road, NW, Tel: 01-723 4242. Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133. And Bristol: 108A Stokes Croft, Bristol. Tel: 0272 426801/2

Head Office and Mail Order to Dept. HE
A. Marshall (London) Ltd.
Kingsgate House, Kingsgate Place
London NW6 4TK. Tel: 01-634 0805
Telex 21442

RESISTORS FIXED CARBON

Wattage	Tolerance	Temp. Coeff.	Value Range	Temp. Range	Price
0.25	±5%	Tel	Available to £12	range 10° to 100°	2p each
0.5	±5%	Tel	Available to £12	range 10° to 100°	3p each
1.0	±10%	Tel	Available to £12	range 10° to 100°	5p each
2.0	±10%	Tel	Available to £12	range 10° to 100°	9p each

WIRE WOUND

Wattage	Tolerance	Temp. Coeff.	Value Range	Temp. Range	Price
2.5	±5%	Tel	Following values only:	10p each	
5	±5%	Tel	Following values only:	12p each	
10	±5%	Tel	Following values only:	14p each	

MULLARD MR25/MR30 SERIES METAL OXIDE

Wattage	Tolerance	Temp. Coeff.	Value Range	Temp. Range	Price
0.5	±2%	Tel	Available to £24	range 10° to 100°	4p each

TOOLS

Item	Price
Diagonal Cutters	£3.40
Round Nose Pliers	£3.25
Flat Nose Pliers	£3.20
Snipe Nose Pliers	£3.20
End/Top Cutters	£3.80

BOXES AND CASES

Material	Dimensions	Price
ALUMINIUM	8x2 1/2 x 4 1/2"	£0.85
ALUMINIUM	8x4 1/2 x 6 1/2"	£1.90
ALUMINIUM	8x6 1/2 x 8 1/2"	£2.40
ALUMINIUM	8x8 1/2 x 10 1/2"	£2.25
ALUMINIUM	8x10 1/2 x 12 1/2"	£2.35
ALUMINIUM	8x12 1/2 x 14 1/2"	£2.70

ABS PLASTIC

Material	Dimensions	Price
ABS PLASTIC	3 1/2 x 2 1/2 x 1 1/2"	£0.55
ABS PLASTIC	3 1/2 x 2 1/2 x 1 1/4"	£0.85

RAACO STORAGE BOXES

Size	Price
2 sizes — 4 configurations	86 £0.76
89 £1.62	
810 £1.78	

VERO CASES

Material	Price
ANODISED ALUMINIUM FRONT PANEL, TWO-TONE HANDLES, CLIP TOGETHER	£2.50
VCC1-85 x 40 x 154mm	£3.15
VCC3-85 x 80 x 154mm	£3.65

TTL see catalogue for full range

IC	Price
74LS00N	£0.26
74LS01N	£0.26
74LS02N	£0.26
74LS03N	£0.26
74LS04N	£0.26
74LS05N	£0.26
74LS06N	£0.26
74LS07N	£0.26
74LS10N	£0.26
74LS11N	£0.26
74LS12N	£0.26
74LS13N	£0.26
74LS14N	£0.26
74LS15N	£0.26
74LS16N	£0.26
74LS17N	£0.26
74LS18N	£0.26
74LS19N	£0.26
74LS20N	£0.26
74LS21N	£0.26
74LS22N	£0.26
74LS23N	£0.26
74LS24N	£0.26
74LS25N	£0.26
74LS26N	£0.26
74LS27N	£0.26
74LS28N	£0.26
74LS29N	£0.26
74LS30N	£0.26
74LS32N	£0.26
74LS33N	£0.26
74LS37N	£0.26
74LS38N	£0.26
74LS40N	£0.26
74LS42N	£0.26
74LS44N	£0.26
74LS47N	£0.26
74LS48N	£0.26
74LS49N	£0.26
74LS50N	£0.26
74LS54N	£0.26
74LS55N	£0.26
74LS56N	£0.26
74LS57N	£0.26
74LS58N	£0.26
74LS59N	£0.26
74LS60N	£0.26
74LS61N	£0.26
74LS62N	£0.26
74LS63N	£0.26
74LS64N	£0.26
74LS65N	£0.26
74LS66N	£0.26
74LS67N	£0.26
74LS68N	£0.26
74LS69N	£0.26
74LS70N	£0.26
74LS71N	£0.26
74LS72N	£0.26
74LS73N	£0.26
74LS74N	£0.26
74LS75N	£0.26
74LS76N	£0.26
74LS77N	£0.26
74LS78N	£0.26
74LS79N	£0.26
74LS80N	£0.26
74LS81N	£0.26
74LS82N	£0.26
74LS83N	£0.26
74LS84N	£0.26
74LS85N	£0.26
74LS86N	£0.26
74LS87N	£0.26
74LS88N	£0.26
74LS89N	£0.26
74LS90N	£0.26
74LS91N	£0.26
74LS92N	£0.26
74LS93N	£0.26
74LS94N	£0.26
74LS95N	£0.26
74LS96N	£0.26
74LS97N	£0.26
74LS98N	£0.26
74LS99N	£0.26

NEW 1978 CATALOGUE

48 pages — largest range of quality components in the UK — over 8000 line items — 50p post paid, 40p to callers

MAIL ORDER
See 40p pp 10 orders.
Tel: credit card orders £10 min
ACCESS — BARCLAYCARD

3 1/2 DIGIT LCD AND LED PANEL METER KITS

Low-cost, easy-to-assemble kits using the new Intersil 71067 A/D converters. Intersil's 7106 is the first single-chip CMOS A/D for driving LCD displays — including backplane — directly. The 7107 is the first single-chip CMOS A/D for driving instrument-size LED displays directly without buffering. Each provides parallel seven segment outputs, ideal for DVMs, DPMs and anywhere modern digital displays are needed. Both have internal reference and clock and both are CMOS so you get low noise (<12 1/2 μV) comparable with the finest bipolar devices, and low power (10 mW max @ 10V).

ICL 7106E(LCD) - 26 99 SPECIAL OFFER £19.90
ICL 7107E(LED) - 21 99 SPECIAL OFFER £15.90
CHIP ALONE ICL 7106CP SPECIAL OFFER £8.90

CAPACITORS Polyester 250VDC — Radial Leads

Value	Price
0.01	£0.06
0.015	£0.06
0.022	£0.06
0.033	£0.06
0.047	£0.06
0.068	£0.06
0.1	£0.06
0.15	£0.06
0.22	£0.06
0.33	£0.06
0.47	£0.06
0.68	£0.06
1.0	£0.06
1.5	£0.06
2.2	£0.06
3.3	£0.06
4.7	£0.06
6.8	£0.06
10	£0.06
15	£0.06
22	£0.06
33	£0.06
47	£0.06
68	£0.06
100	£0.06

ELECTROLYTICS — MULLARD

Value	Price
16 Volt	£0.10
25 Volt	£0.10
50 Volt	£0.10
63 Volt	£0.10
100 Volt	£0.10
150 Volt	£0.10
200 Volt	£0.10
250 Volt	£0.10
300 Volt	£0.10
350 Volt	£0.10
400 Volt	£0.10
450 Volt	£0.10
500 Volt	£0.10
550 Volt	£0.10
600 Volt	£0.10
650 Volt	£0.10
700 Volt	£0.10
750 Volt	£0.10
800 Volt	£0.10
850 Volt	£0.10
900 Volt	£0.10
950 Volt	£0.10
1000 Volt	£0.10

TANT BEADS

Material	Price
POLYESTER EXTENDED FOIL	£0.10
RADIAL PLASTIC	£0.10
METALLISED PLASTIC	£0.10
POLYESTER EXTENDED FOIL	£0.10
RADIAL PLASTIC	£0.10
METALLISED PLASTIC	£0.10

KNOBBS AND SWITCHES

Item	Price
M1 Black plastic with mach metal insert 25mm dia	£0.25
M2 as M1 but with pointer	£0.31
M3 Black plastic with mach insert and calibrated shunt	£0.33
Car Radio knob with chrome top	£0.39

electronics today

international

What to look for in the November issue: on sale October 5th

TECH TIPS SPECIAL

Tech Tips has always been one of the most popular features of ETI. We're certainly not short of contributions. We thought it was about time we gave Tech Tips the deluxe treatment it deserves. Next month we have an 8-page Tech Tips Special — 8 pages of your ingenious suggestions for circuit designs.

TV GAMES UNIT

Hooked on telly tennis or football? We've been carrying out some in-depth testing of (playing with) a TV games unit for you to build.

You can play pin-ball, break-out and solo target basketball. The target basketball game is particularly difficult as you not only have to stop the ball falling off the bottom of the screen, but also press a button to shoot it up towards the target at the same instant as it hits your bat.

Break-out proved to be the star of the system. You gradually knock bricks out of the wall until your ball breaks through and hits the rear wall. It bounces back at break-neck speed and — shock, horror — your bat has shrunk to half size. If you manage to clear the screen, another wall springs up.

The sneaky part is that when you reset the unit, the last score is also displayed on the screen along with your current score. So, of course you have to beat your last score — even if you have to play all night. It's addictive.



GOT A LEAKY MICROWAVE OVEN?

You don't know, do you. If you use a microwave oven a lot, you'll naturally want to know how much radiation is leaking out to your kitchen. If you glow in the dark, you've got a good idea already.

To put your mind at rest, build our microwave oven leak detector. It couldn't be simpler.



KEEP YOUR ROLLING STOCK UNDER CONTROL

We present the ultimate in train controllers. Need something to do on the long winter nights? Do your train set proud with the latest miracle from our design team's secret development lab. — somewhere in Charing Cross Road.

The central control unit gives you exceptionally fine speed control without the overheating problems you can expect from inferior designs. There's a built-in track cleaner to strip nasty oxides from the track and you can choose either conventional or push-button control.

OK, so now you've got the train trundling along on gleaming rails, but how do you tell it where to go? A capacitor discharge unit allows you to control up to 16 sets of points or relays.

If you prefer to put your feet up while bringing the 8.10 to a graceful halt, there's even a two-wire hand controller that lets you control four complete systems (tracks) and shows you which set of points is selected for switching.

Full details of this major model railway project will be in the November issue of ETI.



Much has been said lately on the subject of Microwave Cooking, is it safe, are they cheaper and quicker than ordinary methods of cooking? Find out for yourself. Dr. B. Minakovic of the University of Oxford, one of the countries leading experts takes the lid off the world of Microwaves.

INVENTED SOME TWENTY YEARS AGO, domestic microwave ovens are still somewhat rare in this country, although common in the U.S. and Japan. Industrial applications of microwave heating, on the other hand, are quite widespread and range from tyre processing to biscuit-making and the drying of peas.

The main advantage of cooking by microwaves is speed — anything from two to four times faster than by conventional means. This does not mean that one can improve very much on an electric kettle to boil water, but certainly it will cook a chicken faster than a gas or an electric cooker, despite its lower power rating.

Cooking by microwaves requires some change in cooking habits. For instance, there is no need to warm up a microwave oven before food is put into it, as it is often done with an ordinary oven. Also, there are no more temperature settings to worry about because all cooking is controlled by time.

In contrast to radiant heat, microwaves penetrate almost instantaneously into food and produce heat by agitating the atoms and molecules. The result is fairly uniform heating through the food, but without a crust or surface browning. This may be a desirable feature in some cases, for instance, when warming up or preparing pre-cooked food. When, however some crust or surface browning is necessary the cooking has to be finished off in an ordinary oven.

BROWNE

To obviate the necessity of transferring the food from one oven to another some ovens are fitted with radiant electric elements. In others one can now use a so-called "browning-dish" which is designed to absorb microwaves and hence produce sufficient radiant heat to

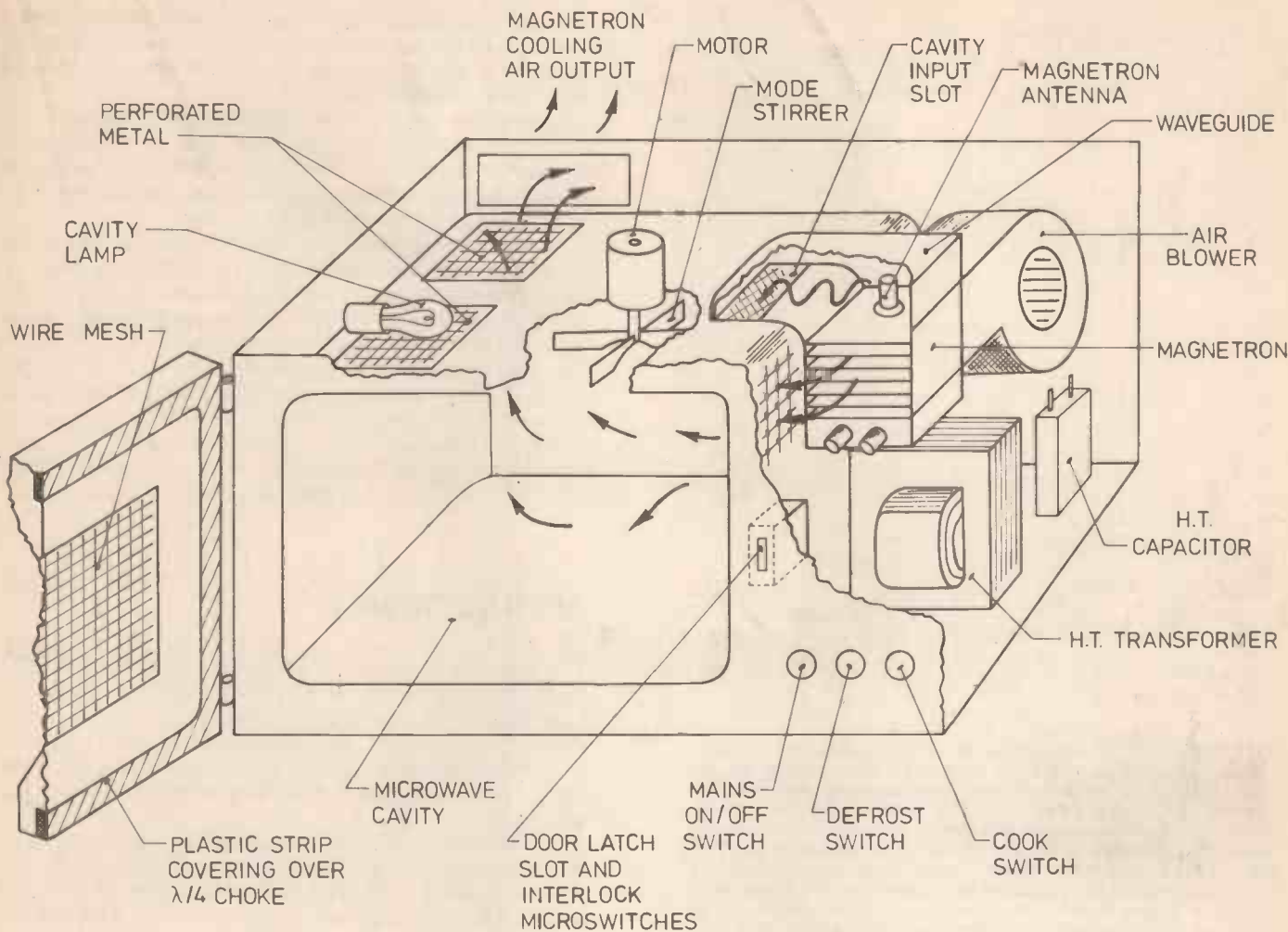


Fig. 1: Basic features of a microwave oven.

cause some browning. It should be noted that ordinary glass and pyrex dishes are not heated, being poor absorbers of microwaves. The oven, usually made of stainless steel, is also not heated because metal walls are good reflectors of microwaves. Metal utensils or dishes behave similarly and must not be used in a microwave oven. Apart from screening food from microwaves, they could produce spurious reflections which could adversely affect operation of the microwave source (magnetron) and even damage it.

Condensation on the cold oven walls is prevented by ducting into the oven the hot air from the magnetron cooling circuit, so the vapours are blown out as quickly as they are formed. As a result an oven never gets really dirty and occasional wiping with a soapy cloth is all that is usually necessary to keep it clean.

Defrosting of frozen food is possible, too. This process, however, must not be regarded just as warming up. Ice, unlike water is a poor absorber of microwaves so will take somewhat longer to heat up. If heating is too rapid, water pockets which are formed will enhance local heating, causing hot spots or even burning. This can be prevented by switching the microwave power off and on, so that the heat has time to diffuse from hot spots into

the frozen region and there produce more thawing. Typical times are 7-15 sec for "off" and 5-10 sec for "on," the exact timing being determined by the power rating of the oven. The switching sequence is controlled electronically and all that a user has to do is to set the timer according to the quantity of food and depress the defrost button.

BACTERIA

The practice of defrosting food by letting it stand overnight at room temperature is rather dangerous, because, once a certain temperature is reached bacteria will start to multiply and food poisoning is possible. This cannot happen with microwave defrosting simply because the time is too short. In any case, there is some evidence that in fact microwaves tend to kill bacteria as most of them are good microwave absorbers. It is important to remember that any kind of food processing involves a certain degree of risk from bacteriological infection, so all food should only be handled in scrupulously clean conditions.

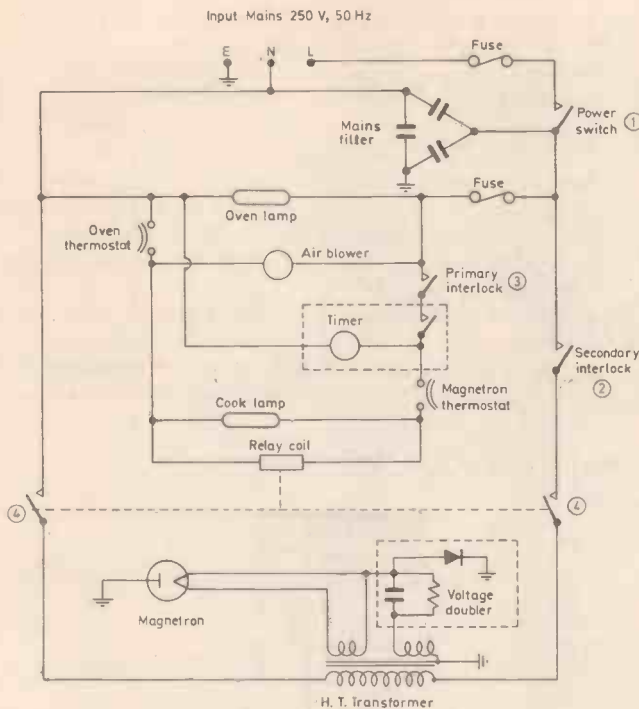


Fig. 2: Simplified circuit diagram of a microwave oven.

Magnetron HT of 4.5 kV is produced by stepping up the mains input to 2.3 kV and the half-wave doubling. The doubling circuit, consisting of a capacitor and a rectifier diode, generates a square-wave at the mains frequency. The polarity is negative so that the anode (magnetron body) can be earthed. The effect of mains fluctuations is reduced by operating the HT transformer core near magnetic saturation. The interlock switches 2 and 3 are operated by the door latches and therefore the magnetron is energised only whilst the door latches are engaged, i.e. the door is closed.

For clarity, the defrosting circuit has been omitted from the diagram.

HOW DOES IT WORK?

Radio waves, microwaves, heat, light and X-rays are examples of electromagnetic waves. Although identical by their nature, they exhibit many different properties simply because of their vastly different wavelengths (frequencies). Microwaves, developed during World War II were named so because in comparison with ordinary radio waves, their wavelengths are very small, 100mm or less.

When food or some non-metallic material is placed in a microwave field, the electric field penetrates into it and forces electrons, protons and ions into oscillations along the direction of the field and at the same frequency. Internal friction then produces heating. The rate of heat generation depends on the field strength, its frequency and a parameter $\tan \delta$ which characterises the "lossiness" of a material. Materials with low $\tan \delta$ like quartz and PTFE cannot be heated by microwaves. An electric field propagating through a lossy material decays in amplitude at a rate inversely proportional to the square root of frequency.

A microwave field can penetrate several centimetres

into the food before it becomes very weak. This distance is known as the depth of penetration. Infra-red radiation (heat), on the other hand, penetrates less than a millimetre and thus heats the surface only and from there the heat spreads inwardly mainly by conduction, a relatively slow process. So, the essential difference between microwave and ordinary heating is that microwaves penetrate deeply into food whereas the ordinary heat radiation is absorbed at the surface.

The internationally allocated frequency band for microwave cooking is centred at 2450 MHz corresponding to a wavelength (λ) of 12.24cm (use $f\lambda = c$, c is the speed of light, 3×10^{10} cm/sec). There is no special reasons why it should be exactly 2450 MHz. A few hundreds of MHz up or down would hardly matter as far as the cooking or the depth of penetration is concerned, and equally the rate of heat generation would be hardly affected. The main reason for this allocation is that this band is not much good for anything else and it does give a reasonable depth of penetration.

MAGNETRON

The essential features of a typical modern microwave oven are shown in Fig. 1. The microwave cavity, as the oven itself is usually called, is a rectangular metal box, large enough to accommodate an oversized chicken. Microwave power is fed in at the top through a large slot via a short waveguide with a magnetron antenna at the other end.

On entering the cavity microwaves spread out in all directions and undergo a series of reflections from wall to wall, passing through the food on each transit. The situation is analogous to a beam of light in a closed box with mirror walls.

Furthermore, as in the case of light, destructive or constructive interference will take place between the overlapping waves and providing the cavity dimensions are the multiples of the cavity half-wavelengths, there will be set up a three-dimensional standing wave pattern. In technical terms, the cavity is said to be resonant. Fig. 3 shows such a standing wave pattern of the electric lines of force.

Food or any other object in the cavity will distort the standing wave pattern, but nevertheless the cavity may remain resonant simply because the Q factor will be reduced too, and so the resonant range will be widened.

The heating pattern of a cavity corresponds to the electric field pattern: strong heating in the regions with strong electric field and no heating at all where the electric field falls to zero. Clearly, an oven producing an array of cold and hot spots would not be very satisfactory for cooking. Fortunately, the heating pattern can be smoothed out by perturbing the electric field with a small metal propeller or "the mode stirrer" as it is usually called. As the name suggests, the mode stirrer moves the electric field standing wave pattern to and fro, so the cold spots at one instant become hot at the next and so on. Of course, in addition to this heat will also spread out by the ordinary conduction process. The mode stirrer is always mounted on the ceiling of the cavity and protected from accidental damage by a plastic sheet of low $\tan \delta$. Some manufacturers prefer a turn-table for the food to a mode stirrer, the others fit both.

Microwave Cooking

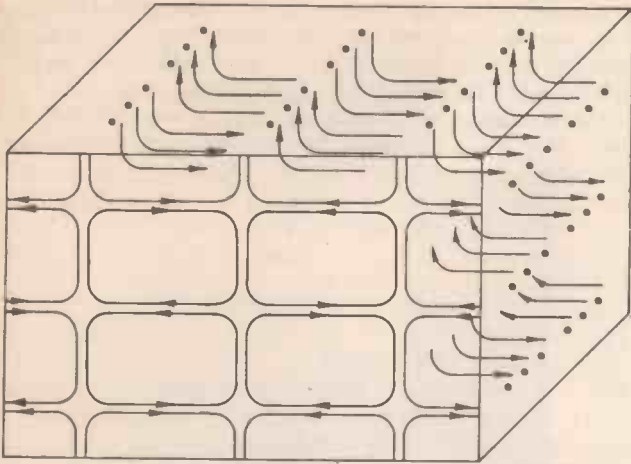


Fig. 3: The electric field standing wave patterns in a microwave oven.

The arrows indicate the direction of the electric field at an instant of time — they are reversed once every cycle, 2450 million times per second!

Power for a microwave oven comes from a magnetron. Typical microwave power rating is 500 W for a small domestic oven, increasing to around 2000 W for a catering model. The nominal guaranteed life of a small magnetron is 1000 hours, but experience shows that with careful use, this can be doubled or even trebled. In any case, bearing in mind that a microwave oven runs only for relatively short periods, 1000 hours can be equivalent to about 3 years of normal use.

EFFICIENCY

The efficiency of cooking magnetrons ranges from 50% for small units to about 75% for bigger ones. Although cooking magnetrons are designed to tolerate large load variations, an oven must not be run empty because microwaves would be reflected back into the magnetron and cause damage by overheating the cathode or the ceramic seals. Some microwave ovens are fitted with a manual power control for reducing the power output when the loading is very light — otherwise the loading should be artificially increased by putting into the oven a small cup of water.

Microwave leakage from an oven occurs mainly through the door seals and the window wire mesh. There may be also some leakage through the poor joints in the box due to poor shielding of the magnetron HT terminals.

The leakage between the door and the cavity flange is prevented by incorporating into the door frame $\lambda/4$ chokes, see figure 4.

When a wave leaking through the small gap between the door and the cavity flange reaches the slot B it is almost completely reflected back because of the discontinuity. By the time it reaches again the input plane A the wave will have travelled a total distance $\lambda/2$ and therefore it will be in the antiphase with just incoming wave and hence cancel it. In terms of impedance, the input plane A behaves as a short circuit. A small fraction of the wave that leaks past the discontinuity at B

continues to the short circuit C where is reflected back to B. Any leakage from B to the outside is suppressed by the lossy rubber strip, mounted along the edge of the metal box. The $\lambda/4$ choke slot is normally covered with a plastic insert to prevent accumulation of dirt.

The door window is not absolutely necessary but it does help one to follow the progress of cooking in the lit-up oven. A wire mesh is used to prevent radiation through the window. The mesh is protected from accidental damage and from dirt by plastic sheets on both sides of the window.

The interlocks operated by the door latches are another very important safety feature. They ensure that the microwave power cannot be switched on whilst the door is open even if the cooking switch is depressed.

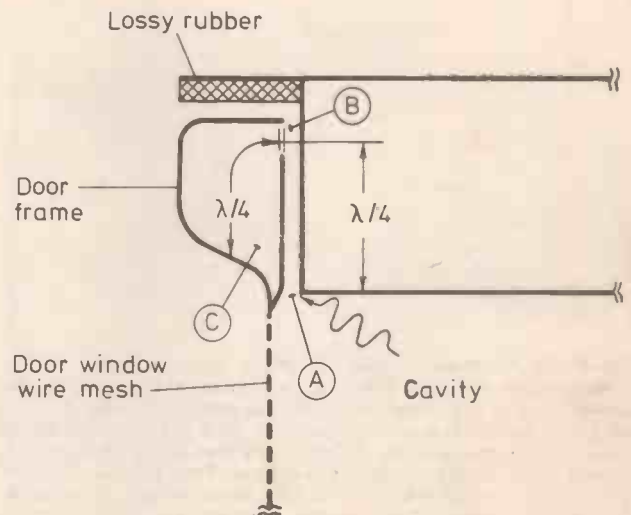


Fig. 4: Cross-section of the door frame showing $\lambda/4$ choke which reduces microwave leakage.

DANGER FROM MICROWAVES?

Microwave hazards arise mainly from internal heating and should not be confused with radio-activity which is far more dangerous. Eyes and genital organs are very sensitive to microwaves and can be damaged by fairly small doses. Prolonged exposure to microwaves can result in eye cataract, a condition in which the lens of the eye becomes clouded.

There is considerable disagreement as to what is the safe power density. The generally accepted figure is about $10\text{mW}/\text{cm}^2$, although some sources claim that this is still too high. Microwave ovens are normally designed for $1\text{mW}/\text{cm}^2$ or less and if necessary this could be even further reduced by another factor of 10 — at a marginal increase in the price.

Of course, a damaged door flange can increase the leakage above the permitted level and there is no way of detecting it without a leakage meter. A good practice is never to put one's face into the door window and to operate the oven from an arm's-length distance. Then, even if something does go wrong one will be fairly safe.

Claims that small leakage from a microwave oven can cause cancer are an absolute rubbish. In fact microwaves of slightly longer wavelength are used daily in hospitals, in diathermy, with beneficial results.

Microwave Cooking

TESTING A MICROWAVE OVEN

Power test — Pour exactly 1 litre of water into a plastic beaker and having measured the water temperature, heat it in the oven for exactly 4 minutes. On removal, stir the water lightly with the thermometer and again measure its temperature. Calculate the temperature rise from the two readings (in °C) and multiply it by 17.5 to obtain the microwave power in watts.

If the measured temperature rise is too large for the thermometer available, use two litres of water or half the heating time — in either case use 35 as the conversion factor.



Heating pattern in a microwave oven (recorded in a horizontal plane 4in. above the cavity bottom). Dark areas indicate strong heating, light areas weak or no heating. (Courtesy Western Dynamics Ltd.)

CHECKING UNIFORMITY OF THE ELECTRIC FIELD

When a small neon lamp is put into a microwave field it glows bright red if the field is strong enough to ionize the gas in it. This fact is used here to sample the electric field in a microwave oven.


Bed the neon lightly into a lump of plasticine, its leads pointing upwards to act as an antenna. Normally the leads are too long and should be reduced to about 2cm or less, so that the lamp is not overheated.

If necessary, sensitivity can be improved by bending the leads apart, to form a Vee. This type of an antenna is

directional, so try various orientations and positions.

If several neons are available stick them on a strip of perspex, about 2cm apart. An oven must never be run empty so do this test with a cup of water in it.

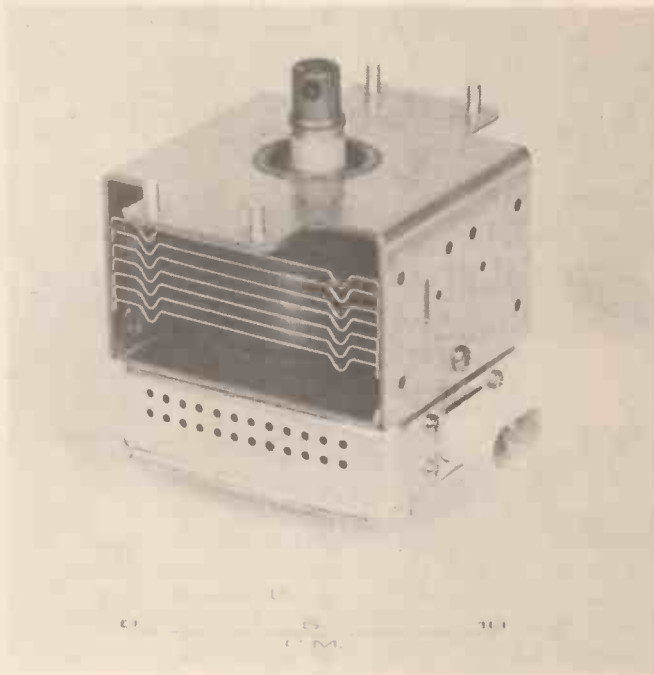The leakage field outside an oven is far too weak to ionize the gas in a neon lamp and no glow will be observed.



*Microwave oven magnetron.
(Courtesy Toshiba Ltd.)
Out put power 840 W
Peak operating voltage 4.5 kV
Average anode current 350 mA
Cooling by blowing air through fins
Focussing by ferrite magnets*

WARNING

In operating a microwave oven always follow the maker's instructions. Do not remove the covers because this will not only expose high voltage terminals but also increase the microwave leakage.

Also do not poke wires or sharp objects into the door seals or cavity perforations for this can significantly increase the microwave leakage.

HE

*Dr. B. Minakovic,
Microwave Laboratory,
Department of Engineering Science,
University of Oxford,
Parks Road,
Oxford,
OX1 3PJ.*

STEVENSON

Electronic Components

CMOS			
4001	13p	4020	50p
4002	13p	4022	50p
4007	13p	4023	13p
4009	30p	4024	40p
4011	13p	4025	13p
4012	13p	4026	13p
4013	28p	4027	28p
4015	50p	4028	45p
4016	28p	4029	50p
4017	47p	4040	55p
4018	55p	4041	55p
		4042	55p
		4043	50p
		4044	90p
		4049	25p

FULL DETAILS IN CATALOGUE!

TTL			
7400	10p	7473	20p
7401	10p	7474	22p
7402	10p	7475	25p
7404	12p	7476	20p
7406	22p	7477	20p
7408	12p	7478	20p
7410	10p	7479	25p
7412	22p	7480	25p
7414	30p	7481	25p
7416	10p	7482	30p
7418	12p	7483	35p
7420	12p	7484	35p
7422	10p	7485	35p
7424	12p	7486	45p
7426	12p	7487	45p
7428	12p	7488	45p
7430	12p	7489	45p
7432	18p	7490	25p
7434	18p	7491	25p
7436	18p	7492	30p
7438	18p	7493	30p
7440	18p	7494	45p
7442	18p	7495	35p
7444	45p	7496	45p
7446	50p	7497	35p
7448	50p	7498	35p
7450	12p	7499	90p

OPTO			
LED's	0.125in.	0.2in	each 100+
Red	TIL209	TIL220	9p 7.5p
Green	TIL211	TIL221	13p 12p
Yellow	TIL213	TIL223	13p 12p
Clips	3p	3p	
DISPLAYS			
DL704	0.3 in CC	130p	120p
DL707	0.3 in CA	130p	120p
FND500	0.5 in CC	100p	80p

SKTS			
8pin	8p	18pin	14p
14pin	10p	20pin	16p
16pin	11p	22pin	17p
24pin	18p	28pin	22p
32pin	40p	40pin	32p
3 lead T018 or T05 socket. 10p each			
Soldercon pins: 100:50p 1000:370p			

PCBS			
VEROBOARD			
Size in.	0.1in.	0.15in.	Vero Cutter 80p.
2.5 x 1	14p	14p	
2.5 x 3.75	45p	45p	
2.5 x 5	54p	54p	Pin insertion tool 108p
3.75 x 5	64p	64p	
3.75 x 17	205p	185p	
Single sided pins per 100 40p 40p			
Top quality fibre glass copper board. Single sided. Size 203 x 95mm. 60p each.			
Delco pens. 75p each			
Five mixed sheets of Alfac. 145p per pack.			

RESISTORS			
Carbon film resistors. High stability, low noise 5%.			
E12 series. 4.7 ohms to 10M. Any mix:			
0.25W	each	100+	1000+
0.5W	1p	0.9p	0.8p
	1.5p	1.2p	1p
Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg-ohm (650 res) 0.5W £7.50. 0.25W £5.70.			
METAL FILM RESISTORS			
Very high stability, low noise rated at 1/2W 1%. Available from 51ohms to 330k in E24 series. Any mix:			
0.25W	each	100+	1000+
		3.5p	3.2p

LINEAR			
LF356	80p	NE531	98p
LM301AN	26p	NE555	23p
LM308	60p	NE556	60p
LM318N	75p	NE567	100p
LM324	45p	RC4136	100p
LM339	45p	SN76477	230p
LM378	230p	TB800	70p
LM379S	410p	TBA810S	100p
LM380	75p	TDA1022	620p
LM390	50p	TL081	45p
LM390S	65p	TL084	125p
LM3911	100p	ZN414	80p
MC1458	32p	ZN425E	390p
MM57160	590p	ZN1034E	200p

TRANSISTORS			
AC127	17p	BCY72	14p
AC128	16p	BD131	35p
AC176	18p	BD132	35p
AD161	38p	BD139	35p
AD162	38p	BD140	35p
BC107	8p	BFY50	15p
BC108	8p	BFY51	15p
BC108C	10p	BFY52	15p
BC109	8p	MJ2955	98p
BC109C	10p	MPSA06	20p
BC147	7p	MPSA56	20p
BC148	7p	TIP29C	60p
BC177	14p	TIP30C	70p
BC178	14p	TIP31C	65p
BC179	14p	TIP32C	80p
BC182	10p	TIP2955	65p
BC182L	10p	TIP3055	55p
BC184	10p	ZTX107	14p
BC184L	10p	ZTX108	14p
BC212	10p	ZTX300	16p
BC212L	10p		
BC214	10p		
BC214L	10p		
BC477	19p	1N914	3p
BC478	19p	1N4001	4p
BC548	10p	1N4002	4p
BCY70	14p	ITT Full spec. product.	
BCY71	14p	1N4148	-£1.40/100. £11 1000

DIODES			
1N914	3p	1N4006	6p
1N4001	4p	1N5401	13p
1N4002	4p	BZY88 ser.	8p
ITT Full spec. product.			
1N4148	-£1.40/100.	£11 1000	

CAPACITORS			
TANTALUM BEAD			
0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1 & 2.2uF @ 35V		each	8p
4.7, 6.8, 10uF @ 25V			13p
22 @ 16V, 47 @ 6V, 100 @ 3V			16p
MYLAR FILM			
0.001, 0.01, 0.022, 0.033, 0.047, 0.068, 0.1		each	3p
0.068, 0.1			4p
POLYESTER			
Mullard C280 series			
0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1		each	5p
0.15, 0.22			7p
0.33, 0.47			10p
0.68			14p
1.0uF			17p
CERAMIC			
Plate type 50V. Available in E12 series from 22pF to 1000pF and E6 series from 1500pF to 0.047uF			

RADIAL LEAD ELECTROLYTIC			
63V 0.47 1.0 2.2 4.7 10			5p
	22 33 47		7p
			13p
			20p
25V 10 22 33 47			5p
			8p
			10p
			15p
			23p

CONNECTORS			
JACK PLUGS AND SOCKETS			
	screened	unscreened	socket
2.5mm	9p	13p	7p
3.5mm	9p	14p	8p
Standard	16p	30p	15p
Stereo	23p	36p	18p
DIN PLUGS AND SOCKETS			
	plug	chassis socket	line socket
2pin	7p	7p	7p
3pin	11p	9p	14p
5pin 180°	11p	10p	14p
5pin 240°	13p	10p	16p
1mm PLUGS AND SOCKETS			
Suitable for low voltage circuits, Red & black. Plugs: 6p each Sockets: 7p each.			
4mm PLUGS AND SOCKETS			
Available in blue, black, green, brown, red, white and yellow. Plugs: 11p each Sockets: 12p each			
PHONO PLUGS AND SOCKETS			
Insulated plug in red or black			9p
Screened plug			13p
Single socket	7p	Double socket	10p

SOLDERING IRONS
 ANTEX X25 (25W) or ANTEX CX (17W) 390p each
 Reel of solder (39.6M) 240p each

LOUDSPEAKERS
 56mm dia. 8ohms. 70p 64mm dia. 64ohms. 75p
 64mm dia. 8ohms. 75p 70mm dia. 8ohms. 100p
 Magnetic earpiece including 2.5 or 3.5mm plug. 15p each
 Crystal earpiece including 3.5mm plug. 30p each

SWITCHES
 Subminiature toggle. SPDT 70p. DPDT 80p
 Standard toggle. SPST 34p. DPDT 48p.
 Slide switches (DPDT) miniature or standard 15p.
 Push to make switch. 15p. Push to break switch. 20p.
 Wavechange switches: 1P12W, 2P6W, 3P4W, 4P3W. 43p

CONTROL KNOBS
 Ideal for use on mixers etc. Push on type with black base and marked position line. Cap available in red, blue, green, grey, yellow & black. 14p.

MISCELLANEOUS
 Connection cable available in single or stranded packs of eight colours.
 Single Stranded
 8 metre pack 18p 18p
 40 metre pack 85p 80p

BATTERY CLIPS
 Battery clips for PP3 with lead. 6p each.
 Battery clips for PP9 with lead. 10p each.
 Miniature crocodile clips in red or black. 8p each.
 Red or black probe clips. 20p each.

HEATSINKS
 T018 push to fit heatsink 10p each.
 T05 pushfit heatsink 9p each
 T0220 twisted vane heatsink 20p each.
 T03 twisted vane sink 22p each.

Murata Ultrasonic Transducers. 180p each. 350p pair.
BOXES
 Quality black ABS boxes by BIM. All dimensions in mm.
 100 x 50 x 25 90p each 150 x 80 x 50 140p each
 120 x 65 x 40 125p each 190 x 110 x 60 220p each

REGULATORS			
78L05	30p	7805	60p
78L12	30p	7812	60p
78L15	30p	7815	60p
		7905	80p
		7912	80p
		7915	80p

We now offer one of the widest ranges of components at the most competitive prices in the U.K. See catalogue for full details. We welcome callers at our shop in College Rd, Bromley, from Mon-Sat, 9am-6pm (8pm on Weds and Fridays). Special offers always available.
 We also provide an express telephone order service. Orders received before 5pm are shipped same day. Contact our sales office now with your requirements.
TELEPHONE: 01-464 2951/5770.

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits 100+ 10%, 1000+ 15%. Prices VAT inclusive. Please add 30p for carriage. All prices valid to April 1980. Official orders welcome.
ORDERS DESPATCHED BY RETURN POST
 HARCLAYCARD & ACCESS WELCOME

Mail orders to: STEVENSON (Dept HE)



PLEASE WRITE FOR YOUR FREE COPY OF OUR 80 PAGE CATALOGUE OF COMPONENTS. CONTAINS OVER 2500 STOCK ITEMS.


76 College Road, Bromley, Kent BR1 1DE.

ALL PRICES INCLUDE 15% V.A.T.

TWO TONE ALARM

Audio alarm generators are needed in a number of applications, such as fire and burglar alarm systems. This circuit generates a penetrating two tone alarm signal having an output power of between about 250 mW and 4 W RMS depending on the speaker impedance and supply voltage used. For low power applications a 9 volt supply and a speaker impedance of about 64 to 80 ohms will give a nominal output power of 250 to 300 mW for a current consumption of around 55 to 70 mA. Where high volume is needed, a 12 volt supply and 8 ohm speaker will give an output power of about 4 W RMS at a mean current consumption of about 700 mA.

The circuit is based on two of the four Norton amplifiers contained in the LM3900N IC. A Norton amplifier is in many ways similar to an ordinary operational amplifier, but it is the comparative input currents rather than the input voltages that determine the output voltage. IC1b is used in a type of relaxation oscillator which generates the audio tone. Initially the bias current flowing into the non-inverting input takes the output high, and C2 begins to charge

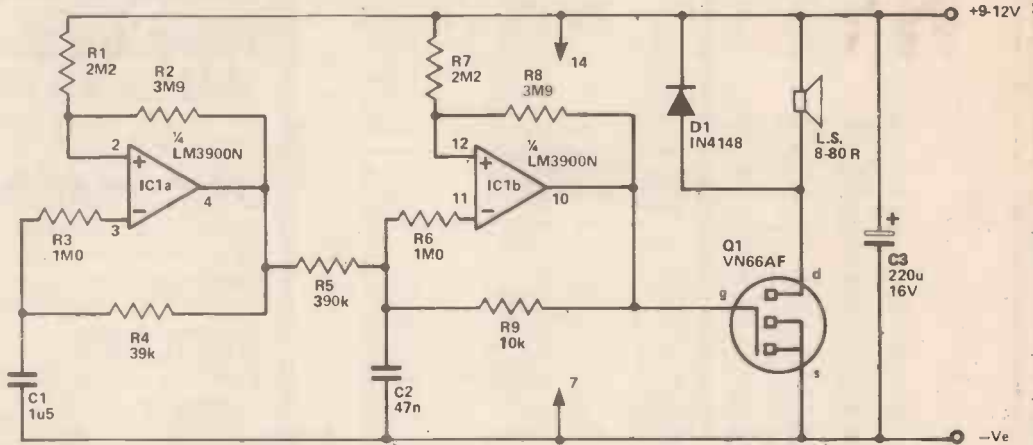

via R9. This causes the current flowing into the inverting input through R6 to gradually increase as the voltage on C2 builds up, until it exceeds the non-inverting input bias current. The output of IC1b then goes low, causing C2 to discharge through R9 until the inverting input current becomes less than that flowing into the non-inverting input. IC1b output then goes high, and the procedure starts again from the beginning, giving continuous oscillation. Note that when IC1b output went from the high to the low state, this

resulted in R8 draining off some of the non-inverting input bias current where it had previously added to it. This makes it necessary for C2 to considerably discharge before the current into the inverting input drops below that applied to the non-inverting input. This effect is a form of "hysteresis", and is essential to the operation of the circuit. R8 also provides positive feedback which ensures that one IC1b output starts to change polarity it rapidly and reliably switches from one state to the other.

The squarewave output of IC1b


is at quite a high impedance, and so the loudspeaker is driven by way of a common source amplifier using VMOS transistor Q1. IC1a is used in a second oscillator circuit, but this has component values which give oscillation at a frequency of only a few Hertz. Its output is loosely coupled to C2 by R5, and it frequency modulates the tone generator to produce a sort of warbling effect. This gives a much more noticeable and less easily masked signal than a straight forward audio tone.

Short Circuits

555 I.C. MONOSTABLE CIRCUITS (1-Timer)

In the monostable multivibrator mode the 555 IC requires a trigger pulse which takes the trigger input below 1/3 of the supply voltage. The normally low output then goes high for a period determined by a C-R network, the pulse length being approximately 1.1 CR seconds. The device is a retriggerable type, and the output therefore stays high until the trigger pulse ceases, if the latter is longer than the pulse given by the C-R timing circuit.

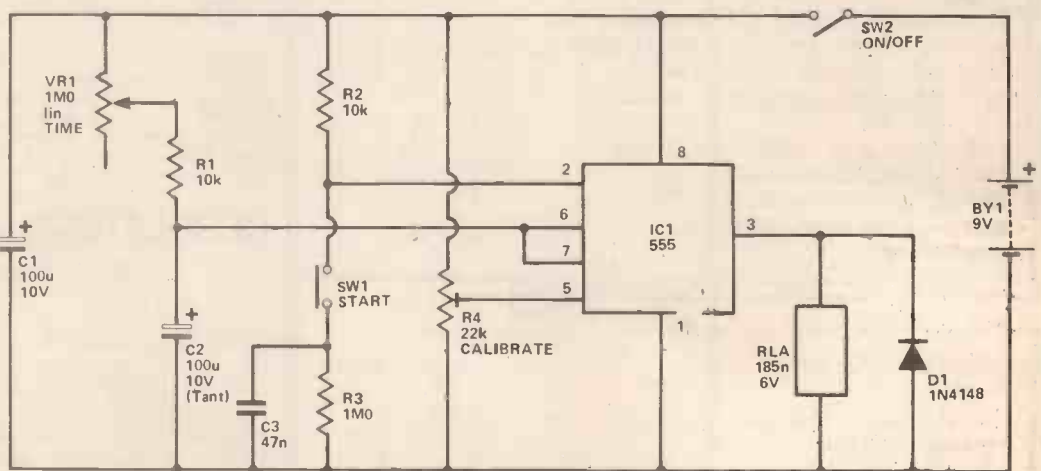The first circuit is for a timer having a 1 to 100 second range, and suitable for use as an enlarger timer, for example. It is triggered by depressing SW1 so as to generate a brief negative pulse as C3 charges via R2. This makes it impossible to prolong the output pulse and produce a



false output period by keeping SW1 depressed. C3 is quickly discharged by R3 when SW1 is released, rendering the trigger circuit ready for the next operation.

The tolerance of timing components RV1, R1, and C2 make it impossible to obtain a highly

predictable time range, and this is overcome by the inclusion of R4. Normally the output pulse ends when the charge on the timing capacitor reaches 2/3 V+ (it is held uncharged until the circuit is triggered, and is discharged when the 1/3 charge level is reached). R4 can be used to

raise or lower the threshold voltage so as to extend or shorten (respectively) the output pulse, as necessary to obtain the appropriate timing range. The output pulse at pin 3 is used to operate the controlled equipment by way of a relay, and D1 is simply a protective diode.

Hobbyprints



We're just etching to tell you about HOBBYPRINTS, we know you won't be able to resist them. They're so good we've even patented the idea (1445171 and 1445172). If you're board with all those untidy strip boards or semi-permanent bread boards then read on.

After many months of extensive research we think we've come up with the ideal solution (Ferric Chloride?) to all of those problems people have with making really professional PCBs. (Puns come at no extra charge).

Seriously though, the HOBBYPRINT rub-down transfer, (very similar to the rub-down lettering) is the answer to the project builders prayer. PCBs take up a disproportionate amount of time, using HOBBYPRINTS a typical PCB can be finished in under half an hour. Because HOBBYPRINTS are produced from our original artwork there's no likelihood of making a mistake. They can even be used as photographic masks for ultra-violet PCB production.

Each sheet of HOBBYPRINTS contains all the PCBs for any particular month (an average of four PCBs), so for only 75 pence including VAT and Post and Packing that's not bad value. For a list of projects refer to back numbers ad.

ORDER TODAY

Send cheque or postal order (payable to Hobby Electronics) to:

**HOBBYPRINTS,
HOBBY ELECTRONICS,
145 CHARING CROSS ROAD
LONDON WC2H 0EE.**

75p INCLUSIVE OF VAT AND POSTAGE.

Please mark the letter(s) of the HOBBYPRINTS on the outside of the envelope.

SPECIALS FROM MODMAGS

Mark your envelopes Specials, and send them to Specials, Modmags Ltd, 145 Charing Cross Road, London, WC2H 0EE.

ETI CIRCUITS

Books 1 & 2.

Each volume contains over 150 circuits, mainly drawn from the best of our Tech-Tips. The circuits are indexed for rapid selection and an additional section is included which gives transistor specs, and plenty of other useful data. Sales of this publication have been phenomenal — hardly surprising when the circuits cost under 1p each!

£1.50 + 25p P&P each.



electronics tomorrow



ELECTRONICS TOMORROW

Comprised entirely of new material, the edition covers such diverse topics as Star Wars and Hi-Fi! The magazine contains projects for everyone — none of which have appeared in ET1 — and a look at the future of MPUs, audio, calculators and video. How can you not read it?

75p + 25p P&P.

TOP PROJECTS

Book 1 + 2: £2.50 + 25p P&P.

Master mixer, 100W guitar amp., low power laser, printmeter, transistor tester, mixer preamp., logic probe, Ni-Cad charger, loudhailer, scope callibrator, electronic ignition, car theft alarm, turn indicator cancellor, brake light warning, LM3800 circuits, temperature alarm, aerial matcher, UHF-TV preamp., metal locator, four input mixer, IC power supply, rumble filter, IC tester, ignition timing light, 50W stereo amp. and many more.


Book 3: SOLD OUT! Book 4: £1.00 + 25p P&P. Book 5: £1.00 + 25p P&P. Book 6: £1.00 + 25p P&P.



TOP PROJECTS

Book 7: £1.25 + 25p P&P.

ER II loudspeaker, CCD phaser, 3-channel tone control, bass enhancer, continuity tester, bench supply, LCD digital multimeter, digital frequency meter, wide range oscillator, ETI wet, egg timer, house alarm, porch light, torch finder, light dimmer, IB metal locator, electronic bongos, puzzle of the drunken sailor, race track, ultrasonic switch, tic-tac radio, rev counter, Transcendent 2000, spirit level.

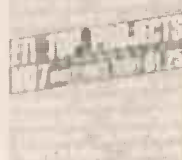

ELECTRONICS — IT'S EASY

Books 2 & 3.

Our successful beginners' series came to an end some time ago now, and the whole series is available from us in reprint form. The three books between them contain all the information presented in the series (sometimes in more detail) and together form an excellent starting point for anyone interested in learning the art of electronics.

£1.20 + 25p P&P each.



INTO ELECTRONICS PLUS

The complete series of Ian Sinclair's series Into Electronics Plus a selection of some of the most popular and informative articles from HE. Everything from Home Computing to making your own PCBs. £1 + 25p P&P.

Multi Option Siren


Subtle Susurrations from a Sensational Sonic Siren

ECONOMY AND VERSATILITY are the key features of this unit. We are not saying you can produce any siren sound, but there is enough variety available to keep anyone happy for hours if not days. Build two and saturate your senses in stereo. You can reproduce a great American police siren and a World War two air raid alert and a whole universe of effects as well.

Possible applications include burglar alarms, sound effects units, a 'button-box' to amuse the kids or just put it through your stereo and annoy the neighbours.

COMPLETE CONTROL

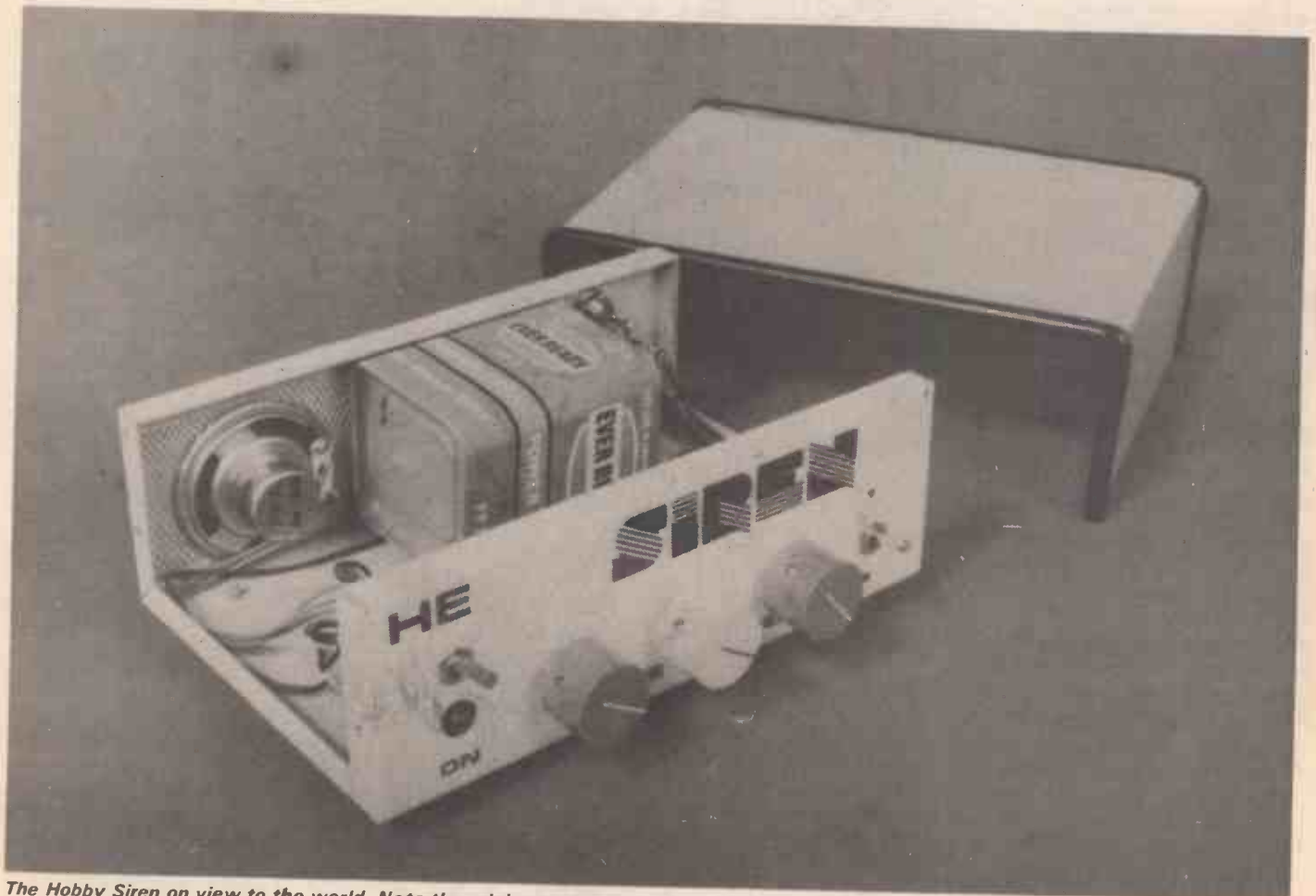Four independently adjustable parameters give you fingertip control over the rise and fall times of the control voltage, the sensitivity of the voltage controlled oscillator and the basic centre frequency of the unit. You can switch between a square wave or triangle waveshape from the control oscillator and the control oscillator period may be varied between several seconds and several hertz.



The Hobby Siren on view to the world. Note the miniature speaker which produces suprisingly loud volume and the use of a large battery for extra long life.

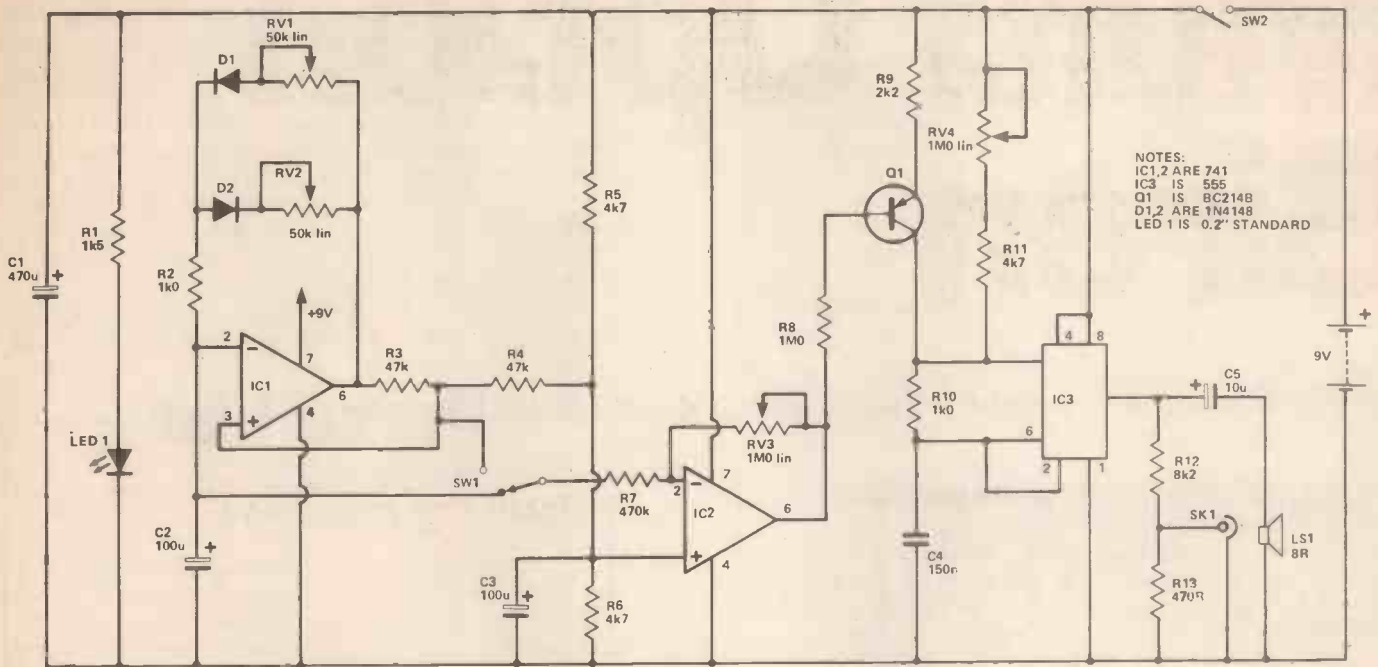


Fig. 1. Circuit diagram of the HE Multi Siren

How It Works

Circuit operation is quite straightforward. IC3 is configured as a voltage controlled oscillator and produces the audio frequency tone. RV4 provides direct control over the frequency while Q1 provides an electronic control. Frequency is altered by changing the voltage applied to R8 and thus the current into Q1. C4 is the timing capacitor.

The control voltage is derived from the slow oscillator built around IC1. IC2 is used to amplify this signal and controls the depth of modulation

applied to the VCO by adjustment of feedback resistor RV3. IC1 is connected as a conventional op-amp stable multivibrator with the exception of diodes D1, 2 which are used to steer current through RV1 and RV2 on alternate half cycles. R2 limits the maximum current flow.

Power 'on' is indicated by LED 1 and current is limited to about 5 milliamps by R1. A mid-voltage point is provided by R5, 6 decoupled by C3 and overall supply decoupling is provided by C1.

TO WORK, TO WORK

The unit may find uses at home or in the family wheel-mobile. Although characterised for use at 9 volts, satisfactory operation will be obtained from a car battery (up to 14 volts) provided capacitors of suitable voltage rating are employed.

A miniature one and a half inch monitor loudspeaker was incorporated in the prototype and the sound output was surprisingly loud (we could hear it all over the office much to everyone's great delight?). If you want real pulverising power, a low level output is provided for an interface to your sound system. The output level is suitable for an amplifier line input; about 500 mV peak to peak, but can be easily changed by selection of two resistors.

The electronic 'works' of this sonic sensation are built around three readily available and inexpensive chips, two 741 op-amps and the ubiquitous 555 timer. The 555 is employed in a novel configuration as a voltage controlled oscillator with one of the

timing resistors replaced by a transistor current source. Only a few other inexpensive components are required.



A few simple to operate controls enable the production of an amazing variety of effects.

Multi Option Siren

CONSTRUCTION

Construction is uncritical and should be simplicity itself. Layout is unimportant and any scraps of veroboard, blob board, breadboard or cheeseboard (copper-clad only) may be pressed into service. Though if you are too haphazard you may have problems troubleshooting the monster you've created. For a trouble-free, no hassles, right first time project use of a PCB is recommended. Our design is best (or so we keep telling ourselves).

None of the component values are critical and you can change almost anything to achieve that elusive

sound you seek. However, polarity of diodes and capacitors is important and these should be checked first if you experience any problems. Also pay close attention to the pin out of Q1. A BC214B is recommended. The 'L' suffix version follows TO92A form and requires some brutal twisting of the tranny's little legs to get it right. Once your project is built and working you won't want to switch off until you have explored the infinite variety of effects available. For this reason a PP7 is the suggested power source. A PP3 would have a very short life!

The Hobby siren was designed and built in two days. It was easy, it was cheap. Go and do it! **HE**



A bird's eye view of the Siren showing the component layout. Note the phono output socket on the rear panel.

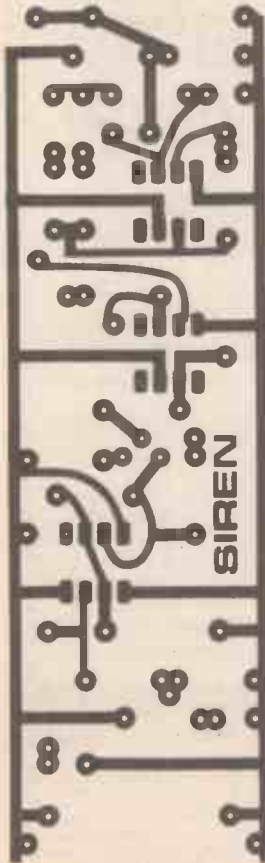


Fig. 2. PCB Foil pattern for the Siren

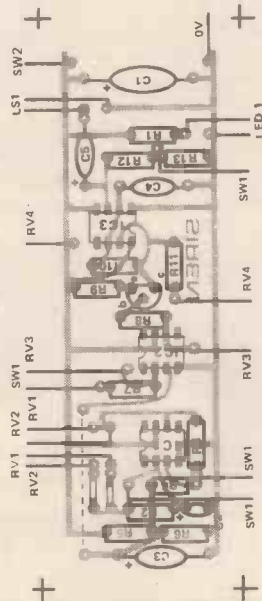


Fig. 3. PCB Overlay for the Multi Siren

Parts List

RESISTORS (All 1/4W 5%)

R1	1k5
R2, 10	1k
R3, 4	47k
R5, 6, 11	4k7
R7	470k
R8	1M
R9	2k2
R12	8k2
R13	470R

POTENTIOMETERS

RV 1, 2	50k lin
RV 3, 4	1M lin

CAPACITORS

C1	470μ electrolytic
C2	100μ tantalum
C3	100μ electrolytic
C4	150n polyester
C5	10μ electrolytic

SEMICONDUCTORS

IC1, 2	741
IC3	555
Q1	BC214B
D1, 2	1N4148
LED 1	standard 0.2"

MISCELLANEOUS

SW1	SPDT
SW2	SPST
SK1	phono socket
LS1	8 ohm loudspeaker
PCB	case to suit

Approx. cost £4

Buylines

The components for this circuit should be readily available. Note that Q1 is a BC214B. A BC214L will work in the circuit as will almost any PNP silicon transistor, however, the transistor pin-out is different. Any size of loudspeaker may be used and values other than 8 ohm will give useable results.

AUTUMN SALE

24 HOUR CLOCK / APPLIANCE TIMER KIT



Switches any appliance up to 1KW on and off at preset times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, PCBs & full instructions.

CT1000K Basic Kit **£12.00**
CT1000KB with white box (56x131x71mm) **£14.00**
Ready Built **£19.00**

OPTO



4EDs
0.1" Red **9p**
0.2" Red **9p**
0.2" Green **12p**
0.2" Yellow **12p**

Square LED
Red. Size:
5x2.5x9mm
high
20p

"0.2" Red LEDs 25 at **£1.25**



DL727 0.5" 2 digit Display CA **£1.00**



DL34M 0.1" magnified 4 digit 7-segment display. **£4.50**



Liquid Crystal Display. 0.5" 3 1/2 digit **£8.10**

BOXES



Moulded in high impact ABS. Supplied with lids and screws. Black or white.
PB2 95x71x35mm **65p**
PB3 115x95x37mm **70p**

ZENER DIODES

400mW 3.3V-30V **8p**
1.3W 7.5-30V **15p**

RESISTORS

1/4W 22ohm-10M
Pack of 10 (one value) **10p**
10 packs (mixed values) **80p**

TRIACS

400V Plastic Case (Texas)

3A **49p** 16A **90p**
8A **62p** 20A. **165p**
12A **70p** 25A **190p**



6A with trigger **80p**
8A isolated tab **82p**
Disc **18p**

LIGHTING CONTROL KITS

Directly replace conventional light switches and control up to 300W of lighting. No mains rewiring. Insolated touchplates. Easy to follow instructions.

TD300K TOUCHDIMMER. Single touchplate with alternate action. Brief touch switches lamp on and off, longer touch dims or brightens lamp. Neon lamp helps find the switch in the dark. **£6.00**

TDE/K Extension kit for TD300K for 2-way switching etc. **£1.50**

TSD300K — TOUCHSWITCH & DIMMER. Single touchplate, small knob controls brightness. **£4.50**

TS300K — ON/OFF TOUCHSWITCH. Two touchplates. **£3.50**

TSA300K — AUTOMATIC. Single touchplate: Time delay variable 2 secs. to 3 1/2 mins. **£3.50**

LD300K — LIGHTDIMMER KIT. **£2.50**

DIGITAL VOLTMETER / THERMOMETER KIT



Based on the ICL7106. This Kit contains a PCB resistors, presets, capacitors, diodes, IC and 0.5" liquid crystal display.

Componentes are also included to enable the basic DV kit to be modified to a Digital Thermometer, using a single diode as the sensor. Requires a 3mA 9V supply (PP3 battery) **£17.50**.



INTEGRATED CIRCUITS

555 Timer **21p**
741 Op. Amp **18p**
AY-5-1224 Clock **£2.60**
AY-5-1230 Clock / Timer **£3.80**
AY-5-1232 Clock / Timer **£3.80**
ICL7106 D.V.M. **£7.00**
ICM7217 Counter **£7.90**
TDA1024 Zero Voltage Switch **£1.20**
LM3911 Thermometer **£1.00**
LM3914 Dot / bar Driver **£2.60**
MM57160 (stack) Timer **£5.95**
S566B Touchdimmer **£2.60**
S9263 Touchswitch **£4.85**
ZN1034E Timer **£1.80**

All ICs supplied with data and circuit.

ALL COMPONENTS ARE BRAND NEW AND TO MANUFACTURERS SPECIFICATION. ADD VAT AT CURRENT RATE TO ABOVE PRICES PLUS 25p P & P. MAIL ORDER — CALLERS WELCOME BY APPOINTMENT.

TK Electronics

106 STUDLEY GRANGE ROAD
LONDON W7 2LX. TEL: 01-579 9794

AS REVIEWED IN HOBBY ELECTRONICS

The teleplay Colour Programagame

ENGLANDS MOST POPULAR TV GAME KIT

now back in stock at reduced prices



TELEPLAY

have produced a new product of easy to assemble cartridge games, for you and all your family, that will not go out of date. Just ADD each new cartridge, as it becomes available, and your colour video centre will be up to date the Teleplay way. You will save pounds in the long run. Works OK on Blackm and White TV.

The Teleplay Kit consists of a Professional Finished Inject Mounted Box — Joystick Hand Controls — one cartridge which consists of 10 games — Football, Tennis, Solo Squash (1 & 2 players). Shoot etc. Mains Adaptor. All holes are pre-drilled — No Special equipment required. You'll be surprised how easy it is to assemble this professional kit! Instruction Manual supplied separately at 0.45p. TELEPLAY GIVES YOU TWICE THE FUN BUILDING AND PLAYING THE MOST PROFESSIONAL TV GAME KIT EVER OFFERED.

Electrical knowledge is not a necessity to assemble this project — just simple soldering.

Every 3 months a NEW game will become available to you and those already under production include Submarines, Space War, Wipe Out and many more. The price of these will vary from £12 to £19 depending upon the complexity of the game. All Cartridges fully assembled.

STUNT CYCLE 4 games — Cartridges and Hand Controls — **£12.90**

WIPE OUT — 6 games — **£11.90**

TANK BATTLE — Cartridge and Hand Controls — **£18.90**

ROAD RACE — 2 games — Cartridge — Controls already with basic kit — **£10.90**

EUROPE'S LARGEST STOCKIST OF TV GAME COMPONENTS.

Please add VAT to all prices — Delivery at cost, will be advised at time of purchase. Please make cheques and postal orders payable to COMP, or phone your order quoting BARCLAYCARD, ACCESS, DINERS CLUB or AMERICAN EXPRESS number. CREDIT FACILITIES ARRANGED



COMP COMPUTER COMPONENTS

14 STATION ROAD, NEW BARNET, HERTFORDSHIRE TEL: 01-441 2922 (Sales)
CLOSE TO NEW BARNET BR STATION — MOORGATE LINE 01-449 6596
OPEN — 10am to 7pm — Monday to Saturday TELEX: 298755

All Products Ex-Stock Please check availability

(Part of the Compshop Ltd. Group)


CITIZENS BAND

SUMMER '79

75p

A Special from the Publishers of

**Hobby
Electronics**



Yes, it's here at last, the first British book on CB. The 72 page special from the staff of Hobby Electronics contains a massive technical section, dealing with aerials, accessories, How to SWR, even a review of a microprocessor controlled 'rig from the States. We have given all the major organisations involved with CB a chance to put their case, everyone from the CBA to the radio control modellers. The legal side of CB in the UK. CB around the world, cartoons, scenes from the film 'Convoy', and a comprehensive dictionary of CB slang, codes etc. Plus much much more. We're sure this will become a much sought after 'standard' work so why miss out. It should be on your newsagents shelves now. If you have any difficulty in obtaining your copy write to us at HE enclosing 75 pence plus 25 pence postage and packing.

The address to write to is:
Citizens Band Special,
Hobby Electronics,
145 Charing Cross Road,
London WC2H 0EE.

Breaker One-Four

Send any news, comments, or information you may have to:
**Breaker One Four,
Hobby Electronics,
145 Charing Cross Road,
London WC2H 0EE.**

This month at the risk of getting egg on our faces we'll make a prediction, and just in case we're wrong all the latest news from the current (illegal) CB scene including a full roundup of all the clubs that have contacted us so far.

CB TO BE LEGALISED IN NOVEMBER! We thought long and hard about printing this.

We have very good reason to believe that there's a better than 50-50 chance that CB will be legalised in November and almost certainly within the next six months.

Now to justify this rather dramatic statement. During the course of a month we receive many, many letters and phone calls on CB, quite a fair proportion contain predictions of one kind or another. Most, if not all are fairly groundless, this month, however, from quite independent sources, almost at opposite ends of the country and almost simultaneously came a common story, CB in November.

By nature we are very sceptical, especially after what we said last month about rumours, so in the normal course of events we would dismiss all of this as just sheer coincidence. The clincher came a couple of weeks ago in the shape of a letter sent into us from Keith Townsend. This letter, which we have every reason to believe to be genuine, comes from an MP, more than that we cannot disclose, suffice it to say, we're convinced.

It's been a month of coincidences, we received a copy of the proposals drafted by the SMAE (Society of Model and Aeronautical Engineers), the governing body of the R/C modellers, sent to HMG. They propose that the frequencies for radio control be moved to somewhere more suitable, possibly the almost international 35 MHz spot. What makes this even more significant is the fact that we have just heard from a very reliable source that these proposals might be implemented — in November. Now isn't that interesting?

To further encourage these events we've handed over our petition, sorry it was a bit sudden but we felt that things were beginning to happen very quickly indeed so we needed to make our presence felt as soon as possible (in fact around 15 000 times), so we're confident that some considerable weight has been added to the proceedings. Thank you to everybody who took the trouble to lend their monniker to our little campaign, you may just have helped change the law!

That really is all we can say at the moment, before anyone gets too carried away let us just say it is only a very strong possibility, not definite and it is still illegal to use CB in this country at the moment. So don't just sit back, now is the time to send that letter to your MP, keep pestering the phone-in radio programmes, strike while the iron is hot (no, not that kind of strike) and keep your fingers crossed, more details next month.

IN THE MEANTIME

Now back to business, we received through the post (quite anonymously) a notice which we have been led to believe is now being issued to all police stations. Basically it is a guide to police officers on how to identify CB rigs and users, the notice is accompanied by a selection of rather dated photographs of rigs and aerials along with a list of names of popular rigs (also dated as one or two of the manufacturers went out of business several years ago).

At the end of the notice is given a couple of phone numbers for police officers to call if (and are holding under the Customs and Exise act) they have detained an operator using CB equipment. The point of all this is to remind you that 27 Megs equipment is illegal and as such you risk up to a £400 fine and/or imprisonment. Smokey bear does know about CB, you have been warned.

400 CHANNELS!

We have some news from across the water of moves to increase the number of CB channels to an almost incredible 400, they propose to use a frequency of 900 megs which would give an effective range of about 50 kilometres. Now what you may ask would anyone need 450 channels for? Believe it or not it's to be used for home computers to allow them to talk to one another. What a good idea, how about letting us humans communicate Home Office?

One of our correspondents has just returned from a visit to the States, he tells us that the American CB market has been completely swamped, so much so in fact he was actually offered brand new 40 channel rigs at around three dollars each (that's about £1.50), the chap had apparently got a warehouse full of them, about 3 million to be precise. Eat your hearts out.

CB PERSONALITY

We wondered how long it would be before CB produced a personality, not long judging by how prolific one breaker, 'Mack The Hack', has become. After his first letter in the July HE he received a good deal of letters, we felt he had something original to say so we asked (via our contacts) him to write something for our 'special'. Now we see he has appeared in Bandstand with another article. How about a manager Mack?

PAGERS AND PACE MAKERS

After we asked last month about the problem of interference of CB and paging systems we got quite a bit of response. It's obvious when you think about it, both questions answer themselves. If 27 MHz does interfere with pacemakers, the hospitals that carry out the operations had better not use pagers on 27 MHz. In fact we did find out that the very first pacemakers of about 20 years ago did suffer from instability in the presence of strong (and we mean strong) RF fields; this was soon put right and no one today need worry about such interference, except that is if they make a habit of climbing TV transmitting towers.

Getting back to pagers it would seem most commercial systems are to be found at around 31 MHz, there are still, however, many older (and a few new systems) still on 27 MHz. Most operate at around 10 watts RF with an effective range of only 4 or 5 miles. The system uses coded bursts of tone to page an individual receiver. We're assured by a gentleman who has been involved in the design of many systems that unless you could whistle some pretty fancy tunes you'd be hard put to upset them.

CB STICKERS

As you may have guessed, our free car-stickers have been somewhat popular. If you haven't received yours yet please bear with us. If you still haven't sent in for yours yet, it's a four inch diameter cling-film type window sticker and it's costing us a small fortune so please enclose an appropriately sized SAE, we would hate to have to squeeze them in a small envelope.

If you live in London you may have seen the welcome publicity given to our campaign by our friends at the Evening News, thanks to all concerned.

TEE-SHIRTS

Our friends at the 10.4 Club tell us they've produced a club Tee-Shirt, the logo used was submitted by members of the club as part of a competition. If you should wish to adorn your torso with an example of their work write to the club at the address in the club section.

ANTENNA CATALOGUE

For anyone interested in CB/11 metre antennas a company called Telecommunications Accessories Ltd are marketing an extensive range of mobile and base station aerials. They have a very interesting catalogue (free on request) just crammed full of goodies. A very good looking "disguised" car aerial (CB/11 metre) may be of interest to our security conscious 'Ham' friends, it retails at around £20.00.

For further information and a catalogue, why not drop Telecommunications Accessories a line at, Thame Industrial Estate, Bandet Way, Thame Oxon OX9 3SS.

CB SLANG

Thanks again to everyone who took the trouble to write in, we are still waiting for some "clean" entries to the Slang competition, one entry from a young lady called Starduster was just a little too long to publish, how about something a little shorter next time?

BAND TOGETHER

IF YOU can remember back to our first Breaker One-Four we asked for details of any CB clubs that may be lurking out there in breaker land. So for the first time we present a list of all the clubs that have been in touch with us (so far) and their addresses.

The Citizens' Band Association (CBA)
President: James Bryant
16 Church Road, St Marks Road, Cheltenham, Glos. GL51

The United Kingdom Citizens' Band Campaign (UKCBC)
Chairman: Bernie Murray
32 Downbank Avenue, Barnehurst, Kent DA7 6RP

The 10.4 Club
Chairman: Ray Threadwell
83 Essex Close, Walthamstow, London, E17

The Midland Citizens' Band Radio Club (MCBRC)
Chairman: K. Townsend
Unit 19, York Terrace, Birmingham B18 5AF


The Weymouth CB Club
Chairman: Ray Howes
39 St Thomas Street, Flat 1, Weymouth, Dorset

Citizens' Band Radio Action Group
Chairman: Steve James
55 Dartmouth Road
Forest Hill
SE23
Meeting place: Dutch House Pub, SE9, every Wednesday evening.

We won't claim this is a comprehensive list, news of clubs is coming in every day and as this article is prepared during the beginning of the month one or two news items might be a little out of date. So if you have got anything for Breaker one-four make sure it gets to us well in advance. As and when news of clubs arrives we will endeavour to let you know.

Well, that's it for another month, you may have noticed the extra page, that's because of all the extra news, keep it up.

STAY LUCKY AND BREAKER BREAK

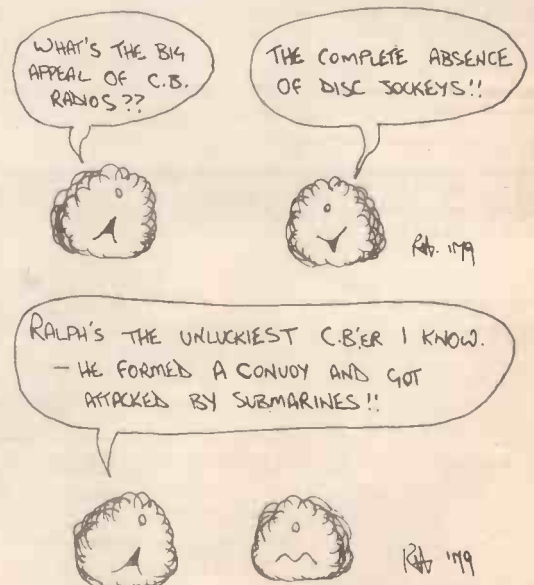

24 TUNE DOOR CHIMES

DOOR TUNES £17.13 + VAT

Waddington's Videomaster announce a doorbell that doesn't go Brrringg, Ding-Dong or Bzzzz. Instead it plays 24 different classical and popular tunes. It will play the tune you select for your mood, the season or the visitor you are expecting to call. Door tunes is not only great fun and a wonderful ice breaker, but is also very functionally and beautifully designed to enhance your home. There is something for Christmas, something for your continental visitors or your relations from the states, and even something for the Queen. Door tunes is easy to install and has separate controls for volume, tone and tempo.



T.V. GAMES

PROGRAMMABLE £29.50 + VAT. COLOUR CARTRIDGE TV. GAME.

The TV game can be compared to an audio cassette deck and is programmed to play a multitude of different games in COLOUR, using various plug-in cartridges. At long last a TV game is available which will keep pace with improving technology by allowing you to extend your library of games with the purchase of additional cartridges as new games are developed. Each cartridge contains up to ten different action games and the first cartridge containing ten sports games is included free with the console. Other cartridges are currently available to enable you to play such games as Grand Prix Motor Racing, Super Wipeout and Stunt Rider. Further cartridges are to be released later this year, including Tank Battle, Hunt the Sub and Target. The console comes complete with two removable joystick player controls to enable you to move in all four directions (up/down/left/right) and built into these joystick controls are ball serve and target fire buttons. Other features include several difficulty option switches, automatic on screen digital scoring and colour coding on scores and balls. Lifelike sounds are transmitted through the TV's speaker, simulating the actual game being played. Manufactured by Waddington's Videomaster and guaranteed for one year.



EXTRA CARTRIDGES:

ROAD RACE — £8.87 + VAT.

Grand Prix motor racing with gear changes, crash noises

SUPER WIPEOUT — £9.17 + VAT.

10 different games of blasting obstacles off the screen.

STUNT RIDER — £12.16 + VAT.

Motorcycle speed trials, jumping obstacles, leaping various rows of up to 24 buses etc.

NON-PROGRAMMABLE TV GAMES

6 Game — COLOURSCORE II — £13.50 + VAT.

10 Game COLOUR SPORTSWORLD £22.50 + VAT.

CHESS COMPUTERS

STAR CHESS — £56.09 + VAT. PLAY CHESS AGAINST YOUR PARTNER.

using your own TV to display the board and pieces. Star Chess is a new absorbing game for two players, which will interest and excite all ages. The unit plugs into the aerial socket of your TV set and displays the board and pieces in full colour for black and white on your TV screen. Based on the moves of chess. It adds even more excitement and interest to the game. For those who have never played, Star Chess is a novel introduction to the classic game of chess. For the experienced chess player, there are whole new dimensions of unpredictability and chance added to the strategy of the game. Not only can pieces be taken in conventional chess type moves, but each piece can also exchange rocket fire with its opponents. The unit comes complete with a free 18V mains adaptor, full instructions and twelve months guarantee.



CHESS CHALLENGER 7 — £85.65 + VAT. PLAY CHESS AGAINST THE COMPUTER.

The stylish, compact, portable console can be set to play at seven different levels of ability from beginner to expert including "Mate in two" and "Chess by mail". The computer will only make responses which obey international chess rules. Casting, on passant, and promoting a pawn are all included as part of the computer's programme. It is possible to enter any given problem from magazines or newspapers or alternatively establish your own board position and watch the computer react. The positions of all pieces can be verified by using the computer memory recall button.



ELECTRONIC CHESS BOARD TUTOR £17.17 + VAT

A special bulk purchase of these amazing chess teaching machines enables us to offer them at only £19.75 less than half recommended retail price. The electronic chess tutor is a simple battery operated machine that can actually teach anyone to play chess and improve their game right up to championship level. This machine is not only for total beginners but also for established players wanting to play better chess. Unit contains the electronic chessboard with 32 chess pieces, a 64 page explanatory booklet and a set of 32 progressive programme cards including 6 beginners cards, 16 check mate positions, 9 miniature games, 5 openings, 3 end games, 28 chess problems and 2 master games.

OTHER CHESS COMPUTERS IN OUR RANGE INCLUDE:

CHESS CHAMPION — 6 LEVELS £43.95 + VAT.

CHESS CHALLENGER — 10 LEVELS — £138.70

+ VAT.

BORIS — MULTI-LEVEL TALKING DISPLAY


£163.04 + VAT.

DRAUGHTS COMPUTERS

CHECKER CHALLENGER 2 LEVELS £43.98 + VAT. 4 LEVELS £80.09 + VAT.

The draughts computer enables you to sharpen your skills, improve your game, and play whenever you want. The computer incorporates a sophisticated, reliable, decision making microprocessor as its brain. Its high level of thinking ability enables it to respond with its best counter moves like a skilled human opponent. You can select offence or defence and change playing difficulty levels at any time. Positions can be verified by computer memory recall. Machine does not permit illegal moves and can solve set problems. Computer comes complete with instructions, mains adaptor and twelve months guarantee.

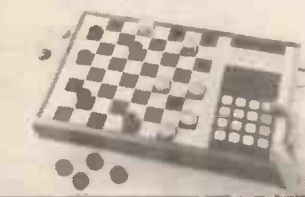PLAY DRAUGHTS/CHECKERS AGAINST THE COMPUTER



FOR FREE BROCHURES — SEND S.A.E

For FREE illustrated brochures and reviews on TV and chess games please send a stamped addressed envelope, and state which particular games you require information on.

Callers welcome at our shop in Welling — demonstrations daily — open from 9am-5.30pm Mon-Sat (9am-1pm Wed).

To order by telephone please quote your name, address and Access/Bardaycard number.

Postage and Packing FREE

AJD DIRECT SUPPLIES LIMITED, Dept. HE10, 102 Bellegrave Road, Welling, Kent DA16 3QD. Tel: 01-303 9145 (Day) 01-850 8652 (Evenings)


THE NEW

EUROSOLDERSUCKER

This 195mm long, all metal, high suction, desoldering tool with replaceable Teflon tip enables removal of molten solder from all sizes of pcb pads. Primed and released by thumb, it incorporates an anti-recoil system and built in safety guard. Only £7.25 inc. VAT & P.P.

THE UNIQUE

EUROBREADBOARD

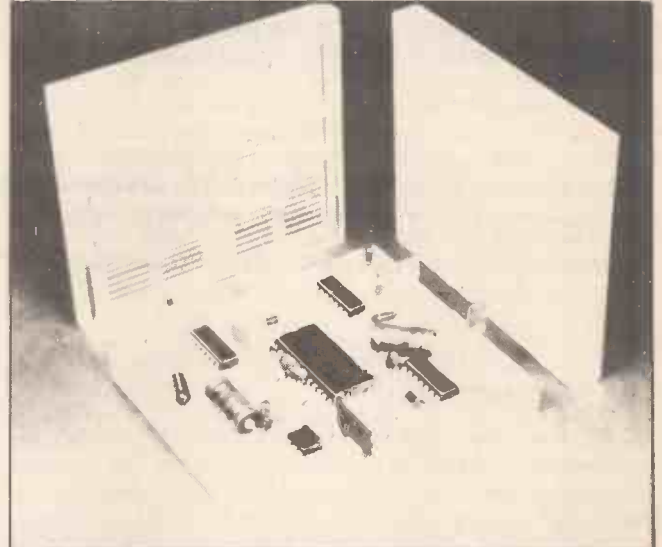

Logically laid out to accept both 0.3" and 0.6" pitch DIL packages as well as Capacitors, Resistors, LED's, Transistors and components with leads up to .85mm dia.

500 individual connections in the central breadboarding area, spaced to accept all sizes of DIL package without running out of connection points, plus 4 Integral Power Bus Strips around all edges for minimum inter-connection lengths.

All connection rows and columns are now numbered or lettered enabling exact location indexing.


Double-sided nickel silver contacts for long life (10K insertions) and low contact resistance (< 10m. ohms).

Easily-removable, non-slip rubber backing allows damaged contacts to be rapidly replaced.

No other breadboard has as many individual contacts, offers all these features and costs only £6.20 each or £11.70 for 2 — inclusive of VAT and P.P.

Snip out and Post

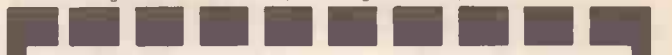David George Sales, r/o 74 Crayford High St., Crayford, Kent DA1 4EF



David George Sales
r/o 74 Crayford High Street,
Crayford, Kent, DA1 4EF.

HE 10/79

Please send me 1 EuroSolderSucker @ £7.25
or 1 EuroBreadBoard @ £6.20 Please
or 2 EuroBreadBoards @ £11.70 Tick

(All prices are applicable from July 1st, 1979 and include VAT & P.P., but add 15% for overseas orders).

Name

Company

Address

Tel. No

Please make cheque/P.O.'s payable to David George Sales

Into Linear ICs

By Ian Sinclair Part 4

Continuing with our old friend the 741, Ian Sinclair takes a look at Comparator action, as always these practical circuits can be tried out on a Eurobreadboard, location numbers are given on each circuit.

ONE OF THE MANY ADVANTAGES we obtain by having two separate inputs to the 741 amplifier IC is comparator action. An electrical comparator is a circuit which has two inputs and whose output depends on which input is at a higher voltage. Many control systems use forms of comparators which are not electrical — a thermostat, for example, gives a signal which is off or on depending on whether the bending of a bimetal strip is enough to overcome the tension of a spring. Non-electrical comparators can now be replaced by the action of the 741.

To see how the 741 can act in this way, think back to the action of the two inputs. Imagine a 741 connected to its supplies (Fig. 4.1). Ideally, if we connected both + and - inputs to earth, the output voltage would also be at earth. Because of slight differences in the components inside the IC, however, this may not happen, and the output voltage can be above or below earth voltage, even when the inputs are both at earth. The output voltage can be corrected by using the offset balance control circuit which was noted in Part 3 and is recalled in Fig. 4.1a.

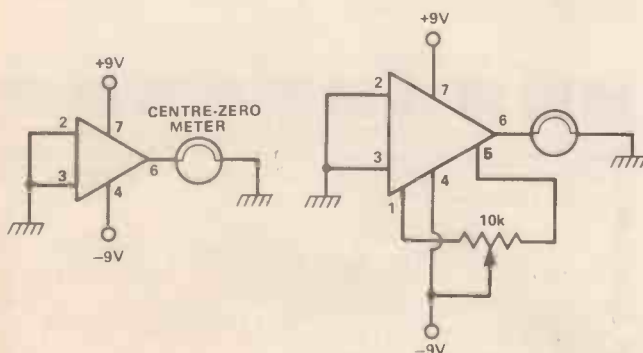


Fig. 4.1 Offset — the output of a 741 may not be at zero volts when both inputs are at zero (a). Using an offset balance potentiometer (b) allows us to zero the output. This adjustment is seldom required.

Suppose, then, that we've fixed both the inputs at earth voltage and that the output is also at earth voltage. If we now raise the voltage at the + input very slightly, the output voltage will rise, usually to somewhere

around positive supply voltage. If we change the voltage on the + input in the other direction, the output voltage will fall, and can go almost as low as the voltage of the - supply. We get the same sort of action if we keep the + input fixed at earth voltage and then change the voltage of the - input slightly. In this case, though, the action is inverted — the output voltage goes to near + supply voltage when the - input voltage is lowered, and the output voltage goes to around - supply when the - input voltage is raised relative to earth.

COMPARATIVELY SPEAKING.

This is the comparator action which we need — when one input voltage is changed so as to equal the other, there is a large change of output voltage. A simple example of this comparator action is shown in the light-meter circuit of Fig. 4.2. In this particular circuit,

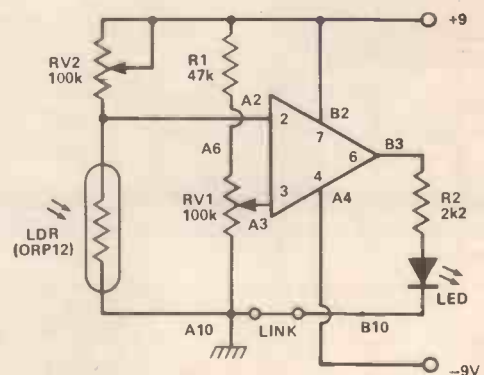


Fig. 4.2 A simple light meter. RV2 presets the range of light values which can be read, and RV1 is used to measure the light by adjusting RV1 until the LED just changes over (lit to unlit, or unlit to lit).

the - input is connected as shown to the junction of the preset RV2 and the photoresistor LDR1. The photoresistor, as its name suggests, has a resistance value which depends on the amount of light which strikes it;

the greater amount of light the lower the resistance. In darkness, the LDR has a high resistance, around 1M, so that in our circuit, the voltage at the — input is high in darkness. This voltage is limited by RV2. RV1 supplies the + input steady voltage, so that this voltage can be varied by turning the shaft of the potentiometer RV1.

In darkness, LDR1 will have a high resistance, but with the component values shown, the voltage at the + input cannot be set to such a high value, and the voltage of the — input will be higher than the voltage of the + input at any setting of the potentiometer. Because of this, the output voltage will be low, and LED1 doesn't glow. If some light now reaches LDR1, however, the resistance of the LDR drops, and the voltage of the — input will also drop. By adjusting the potentiometer setting, we may be able to set the voltage at the + input equal to, or slightly greater than, the voltage at the — input. Just as the voltages at the inputs equalise, the output voltage will rise sharply, so that the LED will start to glow. A different amount of light reaching the LED will mean that a different setting of RV1 is needed to make the LED just switch on. We can fit a pointer knob to RV1, and use a scale under the pointer to indicate light level readings. One useful application of this circuit is to compare the amounts of light falling on photographic paper under an enlarger when very different amounts of enlargement, or different negatives, are used. When the light meter is used in this way, a diffusing slide, or a piece of tracing paper should be held momentarily under the lens of the enlarger to prevent the focused image from striking the LDR.

ONE DEGREE MORE.

The circuit of Fig. 4.3 acts as an electronic thermometer, making use of a combination of linear amplification and comparator action. The diode D1 is, like all silicon diodes, temperature sensitive, so that a small temperature change will cause the voltage across the diode to change.

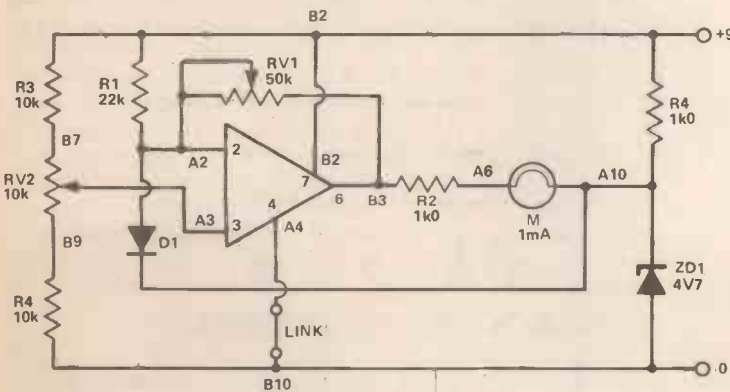


Fig. 4.3 An electronic thermometer circuit. RV1 is a sensitivity control, and RV2 is the 'set-zero' control. Don't forget the A4-B10 link.

The negative feedback circuit, through RV1, keeps the — input at the same voltage as that of the + input but because only a fraction of the output voltage is fed back, the output voltage changes much more than the input voltage — there is voltage gain. This causes the meter M to deflect, providing the temperature reading.

The two variable resistors act to set the scale of the thermometer. RV2 is used as the zero set; it is adjusted when the diode is at the lowest temperature of its desired range so that the meter reads zero at this temperature. RV1 is a sensitivity control which affects the gain of the amplifier. When the diode is at the highest temperature of the desired range, RV1 can be adjusted so that the meter reads full-scale. Every thermometer must be calibrated at two temperatures, and these two adjustments make this possible. If a Celsius scale (NOT Centigrade, even if the BBC doesn't know any better) is needed, the meter can be scaled 0 to 100, and the calibration made with the diode in melting ice for the 0°C point and in the steam over boiling water for the 100°C point.

We don't always need precise temperature readings, very often all we need is a warning of some dangerous temperature level, like freezing point or boiling point. For warning devices, we can use more sensitive detectors and much more amplification, as in the frost-warning circuit of Fig. 4.4 This is a circuit which

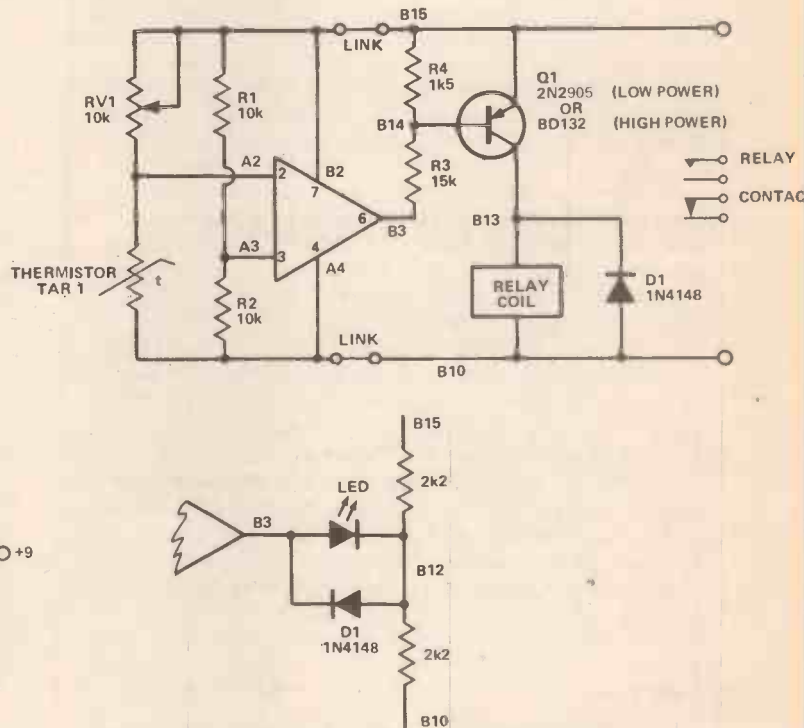


Fig. 4.4 Frost warning. This circuit (a) operates a relay when the temperature drops to a value set by RV1. For a car-mounted frost warning (b) the LED is used in place of the relay. Both versions are show for 12 V operation.

operates a relay at some low temperature, so that heating can be switched on (in a glass-house, for example) or alarm bells sounded. The same basic circuit can also be used as a car ice alarm, with the detector mounted on the bumper and the indicator LED on the dash.

FROST WARNING

The temperature detector device for this circuit is a thermistor, an NTC type, whose resistance increases greatly as it is cooled. Such a thermistor is not suitable

for temperature measurements because of resistance plotted against temperature is nothing like a straight line. This shape of graph suits us very well for the detection of small changes of temperature, however, so that we can make use of thermistors for this sort of task. In the circuit of Fig. 4.4 the + input of the 741 is held at a steady voltage, which is earth when dual supply voltages are used, or +6 V when a car battery is used (as shown) as the supply for the 741. The thermistor is connected in a potential divider circuit with the variable RV1, and the pot can be adjusted so the voltage across the thermistor just rises above the voltage of the + input when the thermistor is at the danger temperature. Since the voltage across the thermistor is the voltage at the - input of the 741, this slight rise in voltage is enough to cause the output voltage of the 741 to drop to a level near that of the - supply (near zero volts in the car-battery version). For an LED warning, this is all that is needed, but for switching other circuits the relay-driving transistor Q1 may be added. This is a PNP transistor which is cut off when the output voltage of the 741 is high, but which conducts when the 741 output voltage switches over. The resistors, R3 and R4 prevent too much current from flowing in the base circuit of this transistor when the output voltage of the 741 is low. Relay RL1 is operated when Q1 conducts, and diode D1 protects the transistor from the voltage surge, caused by the inductance of the relay, when the transistor switches off.

USING POSITIVE FEEDBACK

One disadvantage of the comparator action of the 741 is that it is too sensitive for a lot of purposes. Imagine, for example, a 741 comparator being used in a washing-machine in a thermostat circuit for the hot water. The action of the thermostat is to start the motor (which agitates the clothes) when the water reaches the correct washing temperature. If we used a straightforward 741 comparator, the motor would certainly be started whenever the temperature was equal to the setting on the dial, but if the temperature dropped slightly, even by one tenth of a degree, as the water was stirred about, then the comparator would switch back again, stopping the washing action until the temperature rose again. This stop-and-start action would continue for a long time, causing annoyance, wear on the motor and drive belts, and causing the wash cycle to be much longer than it need be.

How can we get round this? The solution we have used for as long as we have had mechanical thermostats depends on what is called hysteresis. Hysteresis means that switch-on and switch-off don't occur at the same position, or voltage, or setting or whatever. Take an ordinary light switch, for example — it doesn't tremble between on and off when you hold the switch knob half-way over. The switch is fitted with a spring which causes it to snap-over. When you switch on, the snap-over happens at about two-thirds of the movement; but to switch back again you need to move the control knob to about two-thirds over in the other direction (Fig. 4.5). A mechanical thermostat also has this snap action, which prevents small changes of temperature from causing the contacts to open and close alternately in the way our 741 comparator would act. Is there any way we can modify a comparator circuit so as to have this desirable hysteresis?

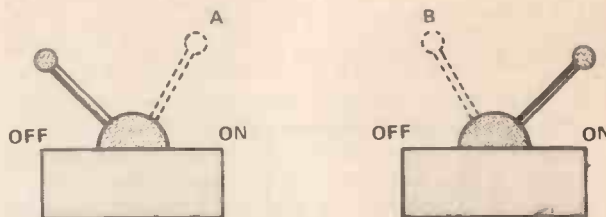


Fig. 4.5 Hysteresis in a light-switch. From the OFF position, the lever has to be pushed to position A to snap over and switch ON. From the ON position, the lever has to be pushed to position B before it snaps to OFF.

There is indeed, and the method uses positive feedback in small quantities. A comparator circuit which includes some positive feedback is shown in Fig. 4.6.

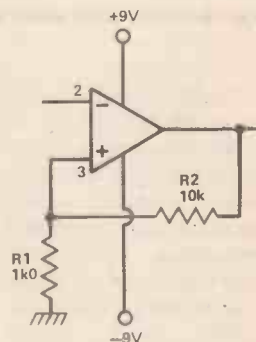


Fig. 4.6 Adding some hysteresis to a comparator (dual supply voltage).

with R2 added to the basic circuit. If we remove R2 for the moment, the circuit is of an ordinary comparator, which will switch over when the input (to the - input of the 741) is at earth voltage. Because the - input is an inverting input, the output voltage is high while the - input voltage is lower than earth voltage, and the output voltage is low while the - input voltage is higher than earth voltage. Now let's see how it works when R2 is fitted in. We'll make it easier by taking some actual values — make R1 = 1K and R2 = 10K, and see what happens. Imagine that the - input voltage is low, below earth voltage. That means that the output voltage is high, around +9 V. Now the potential dividing action of R2, R1 will make the voltage at the + input equal to $9 \times 1/11$, which is 0.82 V, so that nothing can change until the voltage at the - input reaches this level. That's the first change, then, the input voltage that's needed to switch the output from high to low is now +0.82 V instead of 0 V.

CONTROLLED HYSTERESIS

When the 741 switches over the output voltage will drop to around -9 V. Now that makes the voltage at the + input one eleventh of -9 V, which is -0.82 V, and that's the voltage which the - input will have to get to if it's to switch over the output voltage again. There's now some hysteresis in the comparator circuit, 0.82 V in each direction, so that the comparator, once it has switched over in one direction will not be switched back by a small change at the input. We can control the amount of hysteresis by changing the amount of positive feedback. The greater the division ratio of the potential divider, R1, R2, the less feedback we have, and also the

less hysteresis. Fig. 4.7 shows an example of positive feedback used to produce hysteresis in a comparator which is used with a single-ended voltage supply.

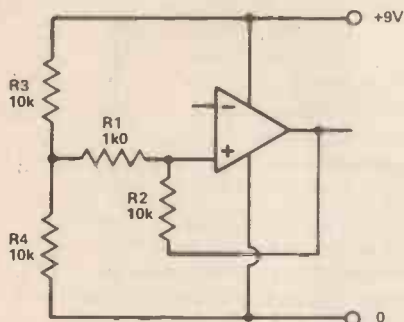


Fig. 4.7 How to arrange for hysteresis when a single supply is used.

The battery-state indicator of Fig. 4.8 makes use of a very small amount of positive feedback, causing hysteresis, to obtain a snap-over action. The circuit is intended to give a visible warning of low battery voltage, and the voltage at the - input of the 741 is set by a zener diode, ZD1 at a value which is less than half of the voltage of the battery whose state is to be monitored — the example is for a car battery of nominal 12 V. A value of about one third of battery voltage is suitable for this 12 V application. The "BATTERY CHECK" input is taken to a potentiometer, RV1, whose tap is connected to the + input of the 741. The positive feedback is provided by a 2M2 resistor which is connected between the output and the + input of the 741. This large value resistor provides a small amount of positive feedback which is enough to ensure that the indicator does not flicker on and off as the load on the battery changes.

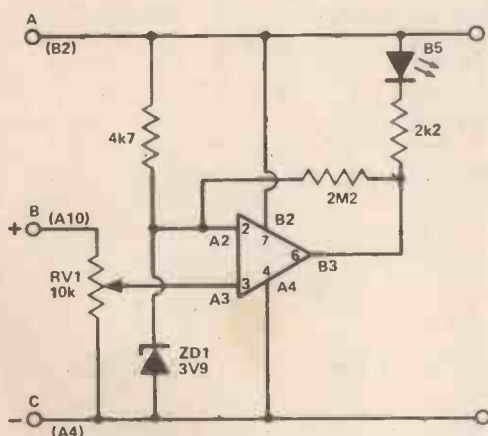


Fig. 4.8 A battery checker. As a self-contained battery checker, the batter to be checked is connected between B and C. For use as a built-in car battery checker, A and B should be linked, and the unit powered from the car battery.

To set up the circuit, a voltage equal to that of a run-down battery is connected to the CHECK terminals, making sure that the polarity is correct. The potentiometer RV1 is then adjusted until the LED just glows. A fresh battery should then cause the LED to turn off — if it

doesn't, then a larger value should be used for R2. Once the circuit has been set up, the state of any 12 V battery can be checked by connecting to the CHECK terminals. If the LED glows, the battery is exhausted.

By connecting the free end of RV1 (at B) to the + supply, the circuit can be used to check its own battery. In this form, the circuit can be used as a built-in battery warning which can be installed on the dash of a car.

OSCILLATOR CIRCUITS

When positive feedback is used in a circuit, oscillation is possible if some timing circuit exists to set the frequency of oscillation. There are quite a number of possible timing circuits, each of which works in a rather different way, so that a large number of possible oscillator circuits exist. One such circuit is the phase-shift oscillator, named after the networks of resistors and capacitors shown in Fig. 4.9. This network consists of three

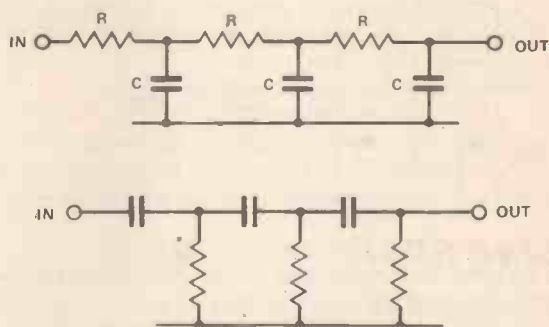


Fig. 4.9 Two forms of a resistor-capacitor phase-shift circuit.

potential dividers, each one consisting of a capacitor and a resistor. Each of these potential dividers not only attenuates (reduces the amplitude of) a signal at its input, it also changes the phase of the output signal as compared to the input. Three such potential dividers connected together will therefore cause considerable attenuation, and also considerable phase shift.

One of the unique things about a sine wave is that when it passes through a phase-shifting circuit, its shape is not affected. As a result, when a sine wave is phase-shifted by 180°, the effect on the shape is exactly the same as that of inverting the sine wave (Fig. 4.10). When

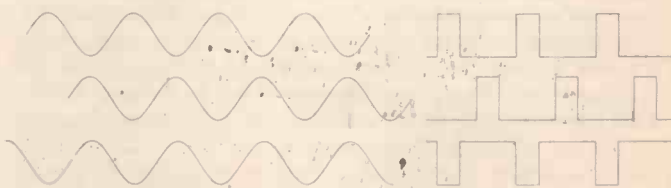


Fig. 4.10 The effects of 180° phase shift (b) and inversion (c) on two different wave shapes. Both inversions and 180° phase shift have the same effect on a sine wave — but not on other waveforms.

we use three stages of phase-shifting, it is fairly easy to get a total phase shift of 180° (that's 60° per divider) at one frequency — but not at any other frequencies. If such a phase-shift network is now connected between the output and the - input (yes, the - input!) of a 741,

then at most frequencies the feedback will be negative but at the frequency which is shifted by 180° the feedback will be positive.

A typical circuit is shown in Fig. 4.11, using a single-ended power supply. The + input is connected to the half-supply voltage which is provided by the potential divider action of R1, R2. The resistors R3, R4, R5 in the phase-shift network are also used for bias, since there is feedback of DC through them; this DC feedback is not affected by the capacitors C1, C2, C3. For AC waves, however, C1, C2, C3 along with R3, R4, R5 cause phase shifts which at one particular frequency will cause the feedback to be positive instead of negative. In

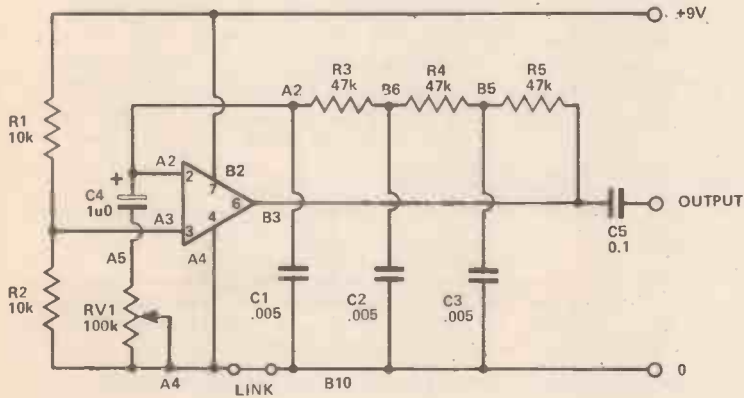


Fig. 4.11 Phase-shift oscillator circuit. RV1 should be adjusted so that the circuit is just oscillating.

this simple design, RV1 controls both frequency and waveshape; as the value of RV1 is increased, the frequency of oscillation drops and the amount of feedback increases. Increasing the amount of feedback, however, causes the waveshape to distort, and RV1 should be adjusted so that the circuit is just oscillating. The output signal can be heard by connecting a crystal (NOT magnetic) earpiece to the output, or by using the output from C5 to drive an amplifier.

By contrast, the circuit of Fig. 12 uses quite a different network called the Wien bridge, and formed by C1, R3, RV2, R4 and C2. This circuit has the peculiar property of having no phase shift at one particular frequency; the frequency is selected by the values of the components which are used. In the circuits shown, the frequency can be varied by varying RV2, a double-ganged potentiometer. With this Wien bridge network connected between the output and the input of the 741, the feedback will be positive only at the frequency which is **not** phase-shifted, and this will therefore be the frequency of oscillation. The bias is set by R1 and R2, C3 is a bypass capacitor which prevents any feedback signal from being phase-shifted by R2.

Unlike the phase-shift oscillator, there is no potentiometer used in this circuit continually to control the amount of feedback, because the gain of the 741, once correctly set, is controlled by feedback to the -input. This negative feedback through RV1 is of both DC and signal, and the signal feedback is also potential divided by the connection of Lp1 to the -input. Lp1 passes only signal currents because of the use of the isolating capacitor C4. In practice, RV1 is set so that the waveshape is good, and this potentiometer need not be adjusted again.

How does it work? Well, we've explained the oscillation part of it already, but not the negative feedback part. The bulb Lp1 is, like any light bulb, a resistor whose value gets greater as the current heats up the filament. With a small output signal, the resistance of Lp1 is low, so that RV1, Lp1 act as a potential divider which feeds only a small fraction of the output signal back to the -input. That means that the gain of the 741 is large, so that the positive feedback action will start an oscillation whose amplitude will increase at each cycle. As the signal amplitude increases, however, more current flows through Lp1, making the resistance greater and so causing the potential division to be less. That, in turn, means less gain, so decreasing the amplitude of oscillation. The circuit then settles down with a fixed and stable amplitude of oscillation. Why stable? If the amplitude increases, there's more signal current through Lp1 causing more resistance and so more negative feedback, less gain — and so less amplitude. If the amplitude decreases, there's less signal current through Lp1, causing less resistance, less negative feedback, more gain = and so more amplitude. That's stability, meaning that the amplitude of the output signal will not change when we alter the frequency by adjusting RV2. If the amplitude was correctly set by RV1 so that the output is a pure sine wave, then that's how it will stay even when the frequency is adjusted. The diode limiter shown in Fig. 4.12b is useful for a fixed-amplitude output.

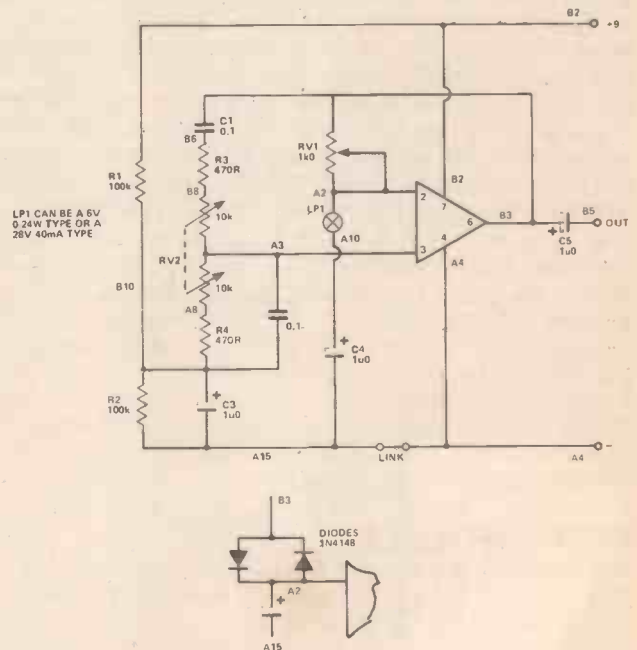


Fig. 4.12 (a) Wien-bridge circuit (b) A diode stabilising network which can replace Lp1, RV1 to give 1 V p-p output.

SQUARE-WAVE AND PULSE CIRCUITS

Just to show how versatile this 741 circuit is, we can use it in a variety of applications which generate square waves and pulses by making use of both positive and negative feedback. The circuit of Fig. 4.13 is a square wave generator with a single supply voltage. R1 and R2

form a potential divider which sets the voltage across R2 to half of the supply voltage, and the chain of resistors R4, RV1, R3 feed back a fraction (Set by RV1) of the output voltage to the + input. A bit of the output voltage is also fed back through R5 to the -input but the voltage at this input can't rise or fall instantly because C1 is connected between the -input and earth.

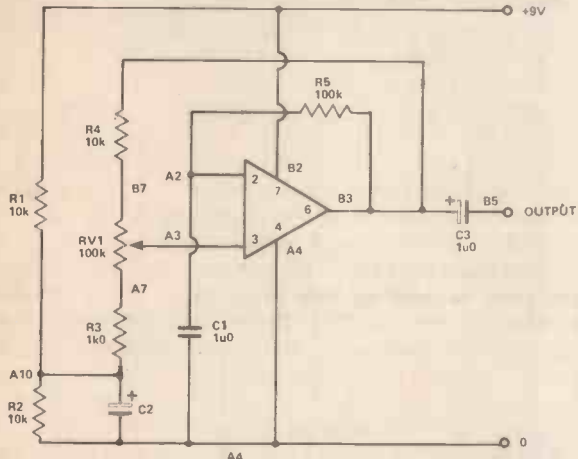


Fig. 4.13 A square-wave oscillator. RV1 is the frequency control.

Imagine that the voltage at the output has been low, and has just switched high. The voltage at the -input will be higher than half of supply voltage because of the positive feedback through R4, RV1, R3; but the voltage at the -input will be about as low as it was before the changeover because C1 has had no time to charge. C1 will now charge through R5, and the voltage at the -input will rise steadily. When the voltages at the two inputs are equal, the output will switch low again. The positive feedback will now ensure that the voltage of the +input is now less than half of the supply voltage (it's that hysteresis again), but the voltage at the -input can't switch over suddenly. C1 now discharges through R5 and the voltage at the -input drops steadily until it's enough to allow the circuit to switch over again. The output is therefore a squarewave whose frequency is decided by the values which are used for R5 and C1. Values of 470K and 6μ8 give very low frequency square waves, so that the switching action can be followed by a multimeter connected to the output, or by a LED and limiting resistor similarly connected.

MONOSTABLE

A monostable is a circuit which generates a single pulse (Fig. 4.14) of voltage when it is triggered by an input. The importance of the monostable is that the duration and voltage of the output pulse can be controlled, but any suitable input pulse will cause the trigger action, so that it converts tired old pulses into bright new ones. It's used in car-engine rev-counters, in digital clocks, in radar and in most circuits which make use of pulses. It's also used to generate time delays, so that an output pulse is delivered some time after an input (trigger pulse).

Fig. 4.15 shows a 741 monostable circuit, which is a bit more complicated than most of the circuits we've used so far. Since it uses a single-ended voltage supply, R1 and R2 are needed to set that vital half-supply voltage for biasing both inputs. Diodes D1, D2 are connected between the inputs and the bias supply, so

that the voltages at the inputs can't rise much above half supply voltage, but can freely fall below this voltage. The capacitor C1 which is connected between the -input and the half-supply voltage point also prevents the -input voltage from changing rapidly. R6 and R3 form a potential divider which provides hysteresis by feeding a fraction of the output back to the +input.

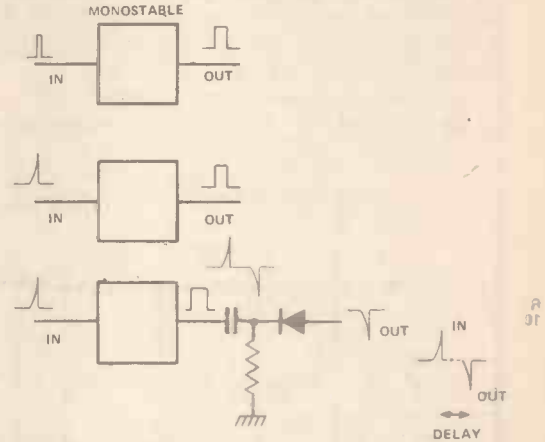


Fig. 4.14 The monostable action (a) A trigger pulse in produces a pulse of definite time (pulsewidth) out, even if the trigger pulse is poorly shaped (b). An output which is delayed with respect to the input (c) can also be obtained.

When the circuit is switched on, the voltages will adjust themselves so that D1 and D2 are just conducting, and the output voltage is just a bit higher than half supply voltage — and it can stay that way, biased steadily and not oscillating. If we now have a signal input consisting of a short negative pulse, the voltage at the +input will drop momentarily. Because of the voltage gain of the 741, the output voltage will also drop, and the positive feedback through R6, R3 will keep things that way. D2 is now cut off, and the output voltage keeps the +input biased low. Meanwhile at the -input, C1 slowly discharges through R5, and the voltage drops steadily,

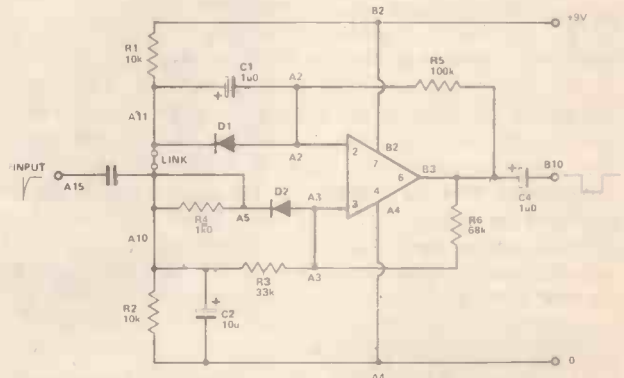


Fig. 4.15 A monostable circuit using a 741. The values of C1 and R5 are chosen so as to produce a long output pulse, but values such as .001 uF and 47K could be used to produce a very brief pulse.

so that D1 is also cut off. When the voltage at the -input equals the +input, the circuit switches over. The voltages (output and both inputs) start to rise. The voltage at the +input rises until D2 conducts and then can't rise any higher. The voltage at the -input rises more slowly, and is then also caught and held by D1, preventing another cycle of oscillation.

HE

BUYING TIME?

Make sure it's CASIO

New Lithium batteries outlast most solar watches.

From Casio's New Collection comes one of the most sophisticated executive watches available today,

THE 81CS-36B ALARM CHRONOGRAPH

LC Display of hours, minutes, seconds, day; and with day, date, month and year perpetual automatic calendar.

4-5 YEAR BATTERY

1/100 second chronograph to 7 hours. Net, lap and first and 2nd place times.

User optional 12 or 24 hour display.

24 hour alarm.

User optional hourly chime.

Backlight

Mineral glass.

Stainless steel case.

Water resistant to 100ft. (3 at)



£35.95

CASIO F-8C 3-YEAR BATTERY

8-digit display of hours, minutes, seconds and date, with day and a.m./p.m. Auto. calendar.

Backlight.

Resin case and matching strap.

Mineral glass.

Water resistant to 66ft. (2 at).

RRP £12.95

Real quality and value for money.



CASIO F-200

Sports chrono

Hours, minutes, seconds, a.m./p.m.; and with day, date and month auto. calendar.

1/100 sec. chrono to 1 hour.

Net, lap and 1st and 2nd place times.

Resin case and matching strap.

Mineral glass.

Water resistant to 66ft. (2 at).

Silver oxide battery.

RRP £17.95

£15.95

NEW LOWER PRICES

Casio 95QS-31B chronograph £23.95

Casio 95CS-31B chronograph £29.95

MELODY 80 Now only £23.95

ISN'T IT WORTH PAYING A LITTLE MORE FOR QUALITY AND RELIABILITY?

Fully guaranteed for 12 months.

Most CASIO products available from stock. Send 25p for illustrated brochures of this superb range of quality watches and calculators.

Price includes VAT and P&P. Send your Company order, cheque, P.O. or phone your ACCESS or BARCLAYCARD number to:—

TEMPUS

Dept. HE, Beaumont Centre

164-167 East Road

Cambridge CB1 1DB


Tel. 0223 312866

AD INDEX

AJD DIRECT SUPPLIES	65	GREENWELD	29	RAMAR	73
AMBIT INTERNATIONAL	2	MAGNUM AUDIO	48	STEVENSONS	55
B.N.R.S.	8	MAPLIN	76	SWANLEY	48
S + R BREWSTER	8	MARSHALLS	48	TEMPUS	73
COMP. COMP. COMP	61	MENOCREST	29	TK ELECTRONICS	61
COOK ELECTRONICS	29	METAC	75	VERO	44
C.S.C.	22	MINIKITS	30	VIDEOTIME	44
DAVID GEORGE SALES	65	MINIM AUDIO	15	WATFORD	9
E.D.A.	8	NIC MODELS	48		
GMT ELECTRONICS	4&5	PRESCOTT CLOCK & WATCH CO	73		



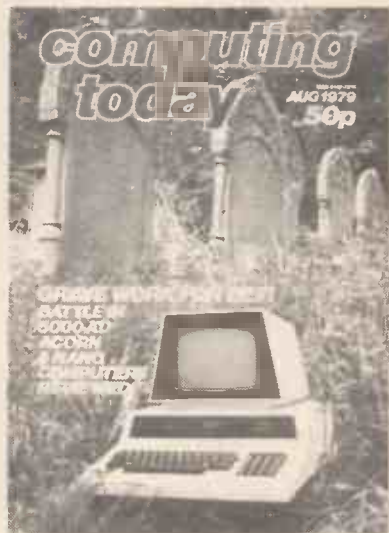First there was ETI, catering for the middle-range to advanced electronics enthusiast. Then there was HE which was aimed at the newcomer to the field. Now there is Computing Today from the same stable. CT covers the area of



small-business and amateur computing and deals with both software and hardware. CT's sixth issue (cover date of August) is out now — 50p at your newsagent.

OSCILLOSCOPE FOR SALE. Heath 10-18V 5MHz AC Valve Single Beam, in perfect working order with manual. £55. Phone: 01-969 6150 evenings and ask for Norman Simons.

PRINTED CIRCUITS and HARDWARE

Comprehensive range Constructors' Hardware and accessories.

Selected range of popular components Full range of HE printed circuit boards, normally ex-stock, same day despatch at competitive prices

P.C. Boards to individual designs Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required)


Alfac range of etch resist transfers, and other drawing materials for p.c. boards

Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES
MASONS ROAD
STRATFORD-ON-AVON
WARWICKS. Tel. 4879

INTRODUCTION TO MICROPROCESSORS AND COMPUTING. 50 pages of diagrams and explanation to get you started. Price £2.30 + 45p postage. EDUCATIONAL DATA AND TECHNICAL SERVICES
59 Station Road, Cogenhoe, Northampton NN7 1LU

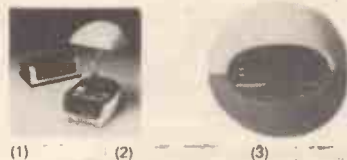BARGAINS FOR THE ELECTRONIC HANDYMAN BRANDED LED DIGITAL ALARM CLOCKS



Returned to Service Department within guarantee period.

(1) With alarm repeat — S.R.S.P. of £17.00 offered at £3.95 inc. VAT.

(2) With luxury lamp and repeat alarm as featured in most major U.K. Mail Order catalogues, S.R.S.P. £31.00—offered at £7.95 inc. V.A.T.

(3) With integral luxury light and repeat alarm also as featured in most major U.K. Mail Order catalogues, S.R.S.P. of £32.00—offered at £7.45 inc. V.A.T.

These will be sold as received from our customers with the existing fault(s) and without guarantee.

Discounts available on large bulk purchases

PRESCOTT CLOCK AND WATCH COMPANY LIMITED

Prescott House, Humber Road, London NW2 6ER

Hobby Electronics Book Service



POPULAR ELECTRONICS BOOKS

Sinclair, I. R., Introducing Electronic Systems	£1.80
Sinclair, I. R., Introducing Amateur Electronics	£1.55
Sinclair, I. R., Electronic Fault Diagnosis	£3.45
Sinclair, I. R., Repairing Pocket Transistor Radios	£2.50
Sinclair, I. R., Oscilloscope In Use	£3.00
Sinclair, I. R., Understanding Electronic Components	£4.00
Sinclair, I. R., Understanding Electronic Circuits	£4.00
Kitchen, H. T., Handtools For Electronic Workshop	£2.75
Kitchen, H. T., Electronic Test Equipment	£5.00
Capel, V., How To Build Electronic Kits	£2.20
Darr, J., How to test almost everything electronic	£3.50
Brown, R. M., How to read electronic circuit diagrams	£4.10

AUDIO

Earl, J., Audio Technicians Bench Manual	£3.50
Earl, J., Pickups and Loud Speakers	£3.50
Earl, J., Tuners and Amplifiers	£3.00
Earl, J., Cassette Tape Recorders	£5.25
Earl, J., ABC of Hi-Fi	£4.25
Capel, V., Microphones In Action	£3.00
Capel, V., Improving Your Hi-Fi	£3.50
Capel, V., Creative Tape Recording	£4.00
Hellyer, H. W., Tape Recorders	£4.25
Sinclair, I. R., Audio Amplifiers For Home Construction	£2.75

RADIO CONTROL

Aldridge, D., Transistorised Radio Control For Models	£3.50
Drake, J., Radio Controlled Helicopter Models	£3.95
Jeffries, C. R., Radio Control For Model Yachts	£1.85
Safford, E. L., Radio Control Manual	£2.45

COOKBOOKS

Tracton, K., BASIC Cookbook	£4.10
Lancaster, D., TTL Cookbook	£7.00
Lancaster, D., RTL Cookbook	£4.65
Lancaster, D., CMOS Cookbook	£8.20
Jong, W., IC Op Amp Cookbook	£10.00
Lancaster, D., T.V. Typewriter Cookbook	£7.75
Lancaster, D., Cheap Video Cookbook	£7.00
Jong, W., IC Timer Cookbook	£7.50
Lancaster, D., Incredible Secret Money Machine (a how to cook book for setting up your computer or technical business)	£4.95

QUESTIONS AND ANSWERS

SIMPLE AND CONCISE ANSWERS TO MANY QUESTIONS WHICH PUZZLE THE BEGINNER.	
Coker, A. J., Q & A On Electric Motors	£1.90
Hellyer, H., Q & A On Radios and T.V.	£1.90
Hibberd, R., Q & A On Integrated Circuits	£1.90
Jackson, K., Q & A On Electricity	£1.90
Brown, C., Q & A On Hi-Fi	£1.90
Brown, C., Q & A On Transistors	£1.90
Brown, C., Q & A On Electronics	£1.90
Reddihough, J., Q & A On Colour T.V.	£1.90
Miller, H., Q & A On Electric Wiring	£1.90

CONSTRUCTOR GUIDES

Graham, P., Simple Circuit Building	£2.60
Colwell, M., Electronic Diagrams	£2.60
Colwell, M., Electronic Components	£2.60
Colwell, M., Printed Circuit Assembly	£2.60
Ainslie, A., Practical Electronic Project Building	£2.60
Colwell, M., Project Planning and Building	£2.60

BEGINNER'S GUIDE

Sinclair, I. R., Beginner's Guide To Tape Recording	£3.35
Sinclair, I. R., Beginner's Guide To Integrated Circuits	£3.35
Sinclair, I. R., Beginner's Guide To Audio	£3.35
King, G. J., Beginner's Guide To Radio	£3.35
King, G. J., Beginner's Guide To Television	£3.35
King, G. J., Beginner's Guide To Colour T.V.	£3.35
Guilou, F., Beginner's Guide To Electric Wiring	£3.35

PROJECT BOOKS

Marston, R. M., 110 Cosmos Digital IC Projects For The Home Constructor	£3.95
Marston, R. M., 110 Wave Form Projects For The Home Constructor	£3.95
Marston, R. M., 110 Op Amp Projects For The Home Constructor	£3.95
Marston, R. M., 110 Semiconductor Projects For The Home Constructor	£3.95
Marston, R. M., 110 Thyristor/SCR Projects For The Home Constructor	£3.95
Marston, R. M., 110 Electronic Alarm Projects for The Home Constructor	£3.95
Marston, R. M., 110 Integrated Circuits Projects For The Home Constructor	£3.95
Marston, R. M., 20 Solid State Projects For The Car and Garage	£3.20
Marston, R. M., 20 Solid State Projects For The Home	£3.20

Note that all prices include postage and packing. Please make cheques, etc. payable to Hobby Electronics Book Service (in sterling only please) and send to:

Hobby Electronics Book Service,
P.O. Box 79,
Maidenhead, Berks.

QUARTZ LCD 5 Function

Hours, mins., secs., month, date, auto calendar, back-light, quality metal bracelet.

£6.65

Guaranteed same day despatch.
Very slim, only 6mm thick.



M1

SOLAR QUARTZ LCD 5 Function

Genuine solar panel with battery back-up. Hours, mins., secs. Day/date. Fully adjustable bracelet. Back-light. Only 7mm thick.

£8.65

Guaranteed same day despatch.



M2

QUARTZ LCD 11 Function SLIM CHRONO

6 digit, 11 functions. Hours, mins., secs., date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet.

Metac Price

£10.65 Thousands sold!

Guaranteed same day despatch



M3

QUARTZ LCD ALARM 7 Function

Alarm Hours, mins., secs. Month, date, day. 6 digits. 3 flags plus continuous display of day and date or seconds. Back-light. Only 9mm thick

£12.65

Guaranteed same day despatch



M4

MULTI ALARM 6 Digits 10 Functions

- ★ Hours, mins., secs.
- ★ Month, date, day
- ★ Basic alarm.
- ★ Memory date alarm.
- ★ Timer alarm with dual time and 5 country zone.
- ★ Back light.
- ★ 8mm thick.

£18.65



M5

FRONT-BUTTON ALARM Chrono Dual Time

6 digits, 5 flags, 22 functions. Constant display of hours and mins. plus optional seconds or date display. AM/PM indication. Month, date. Continuous display of day. Stop-watch to 12 hours 59.9 secs. in 1/10 second steps. Split and lap timing modes. Dual time zones. Only 8mm thick. Back-light.

£22.65

Guaranteed same day despatch.



M6

SOLAR QUARTZ LCD Chronograph with Alarm Dual Time Zone Facility

6 digits, 5 flags, 22 functions. Solar panel with battery back-up. 6 basic functions stop-watch to 12 hours 59.9 secs. in 1/10 sec. steps. Split and lap timing modes. Dual time zones. Alarm. 9mm thick. Back-light. Fully adjustable bracelet.

£27.95

M7



ALARM CHRONO with 9 World Time Zones

- ★ 6 digits, 5 flags.
- ★ 6 basic functions
- ★ 8 further time zones.
- ★ Count-down alarm.
- ★ Stop-watch to 12 hours 59.9 secs. in 1/10 sec. steps.
- ★ Split and lap timing modes.
- ★ Alarm.
- ★ 9mm thick.
- ★ Back-light.
- ★ Fully adjustable bracelet.

£29.65

M8



SOLAR QUARTZ LCD Chronograph

Powered from solar panel with battery back-up. 6 digit, 11 functions. Hours, mins., secs., day date, day of week. 1/100th, 1/10th secs. 10X secs., mins. Split and lap modes. Back-light. Auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£12.65

Guaranteed same day despatch.



M9

SEIKO Alarm Chrono

LCD, hours, mins., secs., day of week, month, day and date, 24 hour Alarm, 12 hour chronograph, 1/10th secs., and lap time. Back light, stainless steel, HARDLEX glass. List Price £130.00

METAC PRICE
£105.00



M10

SEIKO MEMORY BANK Calendar Watch M354

Hours, mins., secs., month, day, date in 12 or 24 hour format all indicated continuously. Monthly calendar display, month, year and all dates for any selected month over 80-year period. Memory bank function. Any desired dates up to 11 can be stored in advance. 2-year battery life. Water resistant.

List Price **£130**

Metac Price **£79.50**

M11



Dual Time-Alarm Chronograph

Mineral glass face. Battery hatch for DIY battery replacement. Top quality finish with fully adjustable bracelet.

Spec. same as M6

£35.00

M12



HANIMEX Electronic LED Alarm Clock



Features and Specification:
Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright/dim modes control. Size: 5.15" x 3.93" x 2.36" (131mm x 11mm x 60mm). Weight: 1.43 lbs (0.65 kg).

£9.65 Thousands sold!
Mains operated.

Guaranteed same day despatch.

M13

HANIMEX Portable LCD Clock Radio

- ★ Back-light.
- ★ Batteries supplied free.
- ★ Quartz crystal controlled.

£17.95



M14

HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and the order details clearly, enclose 30p for post and packing or the amount stated. All products carry 1 year guarantee and full money back 10 day reassurance. Battery fitting service is available at our shops. Also Electronic Calibration Service. All prices include VAT.

Metac Wholesale:

Trade enquiries: Send for a complete list of trade prices and minimum order details. Telephone Orders: Credit card customers can telephone orders direct to Daventry or Edgware Rd., 24 hour phone service at both shops: 01-723 4753 03272-76545.



CALLERS WELCOME
Shops open 9.30 - 6.00.

QUARTZ LCD Ladies 5 Function.

Only 25 x 20mm and 6mm thick. 5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference.

£9.95

Guaranteed same day despatch.



M15

PRICE BREAKTHROUGH ONLY

£18.95



OUTSTANDING FEATURES

- **DUAL TIME:** Local time always visible and you can set and recall any other time zone (such as GMT). Also has a light for night viewing.
 - **CALENDAR FUNCTIONS** include the date and day in each time zone.
 - **CHRONOGRAPH/STOPWATCH** displays up to 12 hours, 59 minutes, 59.9 seconds.
 - On command stopwatch display freezes to show intermediate (split/lap) time while stopwatch continues to run. Can also switch to and from timekeeping and stopwatch modes without affecting either's operation.
 - **ALARM** can be set to any time within a 24-hour period. At the designated time, a pleasant, but effective buzzer sounds to remind or awaken you!
- Guaranteed same day despatch.

M16

Metac

ELECTRONICS
& TIME CENTRES

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753

MAPLIN



This superb organ – build the first working section for just over £100. Full specification in our catalogue.



Touch operated rhythm generator, the 'Drumsette'. Construction details 25p. (Leaflet MES49). Specification in our catalogue.



Multimeters, analogue and digital, frequency counter, oscilloscopes, and lots, lots more at excellent prices. See cat. pages 106 and 183 to 188 for details.



61-note touch-sensitive piano to build yourself. Full specification in our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages – some in full colour – it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



A range of highly attractive knobs is described in our catalogue. Our prices are very attractive too!



The 3800 synthesiser build it yourself at a fraction of the cost of one ready-made with this specification. Full details in our catalogue.



A pulse width train controller for smooth slow running plus inertia braking and acceleration. Full construction details in our catalogue.



Speakers from 1½ inch to 15 inch; megaphone, PA horns, crossovers etc. They're all in our catalogue. Send the coupon now!

Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue (enclose 70p (plus 37p p&p) if I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.07.

NAME _____

ADDRESS _____


HE 10 79



A wide range of disco accessories at marvellous prices. Our catalogue has all the details.



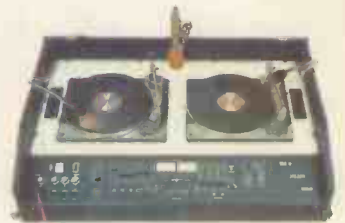A very high quality 40W per channel stereo amplifier with a superb specification and lots of extras. Full construction details in our catalogue.



A genuine 150W per channel stereo disco to build yourself. Full specification in our catalogue.

MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:—
 P.O. Box 3, Rayleigh, Essex SS6 8LR.
 Telephone: Southend (0702) 554155.
 Shop: 284 London Road, Westcliff-on-Sea, Essex.
 (Closed on Monday).
 Telephone: Southend (0702) 554000.