

SEPTEMBER - NOVEMBER 1983

Price 70p

# Electronics

THE MAPLIN MAGAZINE

## Rewiring Your House

WHAT TO BUY & WHAT TO DO

RS232 INTERFACE FOR  
SPECTRUM & DRAGON

A LOOK AT THE  
NEW ATARI'S

ELECTRONIC LOCK  
FOR CAR OR HOME

SYNCHIME SOUND  
EFFECTS BOX



**SYNCHIME**




INTERFACING  
THE BBC MICRO -  
ALL THE INS AND OUTS EXPLAINED


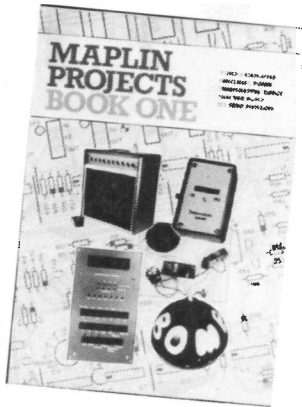
# DID YOU MISS THESE ISSUES?

Copies of issue 1 are now sold out, but a reprint of the projects from issue 1 is available and contains:



**Universal Timer.** A comprehensive programmable controller for up to 4 mains appliances. There is storage for up to 18 program times, ons or offs and relay outputs. Complete construction details.

**Combo Amplifier.** Superb 120W MOSFET power amp with low-noise BI-FET pre-amp having built-in flanger, inputs for guitars, keyboards or microphones, and five step equaliser. Complete construction details.


**Temperature Gauge.** Coloured LED indication of 10°C to 100°C. Complete construction details.

**Pass The Bomb!** Low-cost easy to build electronic version of pass-the-parcel — keeps the kids amused for hours!

**Plus six easy to build projects on Veroboard:** Car Battery Monitor — Colour Snap Game — CMOS Logic Probe — Peak Level Indicator — Games Timer — Multi-Colour Pendant.

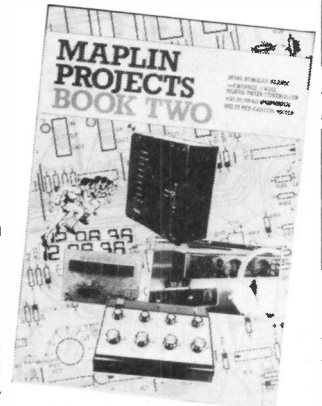**All this for just 70p. Order As XA01B (Maplin Project Book Volume 1 No. 1). Price 70p NV**

Copies of issue 2 are now sold out, but a reprint of the projects from issue 2 is available and contains:



**Digital Multi-Train Controller.** Our superb digital train controller can control up to 14 locomotives individually on the same track. Any four loco's can be controlled simultaneously. The unit has automatic short-circuit protection and because it uses digital control a DC supply is present all the time for carriage light etc.


The locomotive modules will fit in most modern 00-scale engines. Complete construction details.

**Home Security System.** Full construction details of our new home security system offering a high degree of protection for domestic or commercial premises coupled with excellent long-term reliability. The unit's features are: six independent channels, 2-wire or 4-wire operation, detects open or short circuit or just resistance change, tamper-proof main cabinet and external cabinet. The external cabinet has its own protection as well. There are presettable entry and exit delay timers. With the extra peripherals being added each issue, this is a really veratile system.

**Digital M.P.G. Meter.** An easy to build device that will help you to make your motoring more economical. The unit has a large easy to read LED display. Complete construction details.

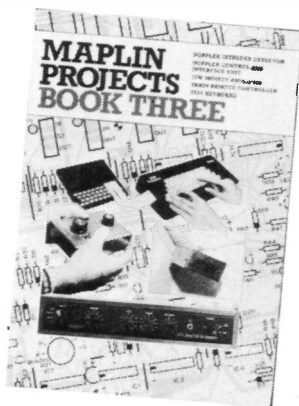**All this for just 70p. Order As XA02C (Maplin Project Book Volume 1 No. 2). Price 70p NV**

Copies of issue 3 are now sold out, but a reprint of the projects from issue 3 is available and contains:



**ZX81 Keyboard.** A full size, full travel 43-key keyboard with the electronics to make graphic symbols, function mode and shift lock, single key selections. The two-colour legend for the keys is the same as the ZX81 keyboard. The keyboard plugs directly into the sockets in the ZX81 and a special adaptor is supplied to run the keyboard from the ZX81 power supply, so there's no

soldering in the ZX81 at all. This full-size keyboard gives you fast, reliable entry — use it once and you won't be able to do without it again!


**Stereo 25W MOSFET Amp.** Supplied as a complete kit including wooden cabinet and printed and punched chassis, this superb 25W rms per channel amplifier has inputs for magnetic pick-up, tape deck, tuner and auxilliary. The kit is extremely easy to build, all but 5 components mounting directly on the pcb. There are only 7 interconnecting wires in all and when completed, no setting-up is required. With its superb frequency response, low noise, low distortion and the grandeur of MOSFET-sound, the amplifier is second-to-none at the price.

**Radar Doppler Intruder Detector.** Home Office type-approved microwave unit gives coverage adjustable from about 2m to 20m. May be used on its own, or with our Home Security System.

**Model Train Controller Remote Control Facilities.** Full details of infra-red, radio or wired remote control units for our Digital Multi-Train Controller.

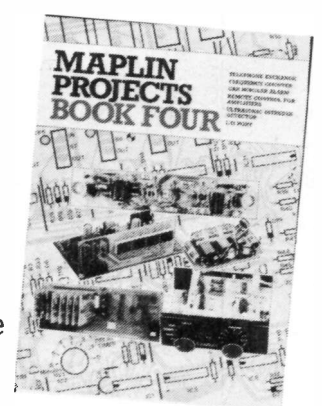**All this for just 70p. Order As XA03D (Maplin Project Book Volume 1 No. 3). Price 70p NV**

Copies of issue 4 are now sold out, but a reprint of the projects from issue 4 is available and contains:



**Telephone Exchange.** A complete telephone exchange with up to 32 extensions on 2-wire lines. Ideal for the home, office, or small factory. Save £££'s on rental charges. Full construction details for up to 16 lines in this book.

**Remote Control for Amplifier.** Adjust volume, balance, and tone whilst you sit back and relax with our infra-red remote control. Designed for use with our 25W MOSFET Amp, but can be fitted to most amplifiers.

**Frequency Counter.** This superb, easy-to-use, low-cost, 8-digit frequency counter with superior specification covers the 10Hz to 6000MHz band. Incorporates full push-button control, electronic switching, and one input for the whole range.

**Ultrasonic Intruder Detector.** This easy-to-build ultrasonic receiver covers up to 400 square feet; though more than one can be used for larger areas. The unit automatically adjusts itself to transmit at the frequency where the transducers give their maximum output. Up to three of these units may be connected to our home security system.

**All this for just 70p. Order As XA04E (Maplin Project Book Volume 1 No. 4). Price 70p NV**

## TWO NEW SHOPS THIS AUTUMN

Coinciding with the publication of this issue of "Electronics" is the opening of our first new store this year. Doors open at 9 a.m. on Tuesday, 16th August, at 8 Oxford Road, Manchester (Tel. 061-236-0281), and we'll be open from 9 to 5.30 Tuesdays to Saturdays from then on.

We're easy to find too; right opposite the BBC between Piccadilly and the University complex, just a few steps from Manchester's Oxford Road Station and about five minutes walk from the city centre. There is excellent parking on meters in the adjacent side roads and we're about five minutes drive straight in from junction 10 on the M63 at the start of the M56.

The big difference with this store is that part of the sales area will be self-service, where you can browse around and choose the parts you want. Counter service will be available as well and upstairs you'll find our computer demonstration area along with hundreds and hundreds of different software packages for Atari, BBC, Commodore 64, Dragon, Sord M5, Spectrum and VIC20.

Our second new store this year takes us to the other end of the country. On November 1st we'll be opening in Southampton, to give us a base in the South of the country. You'll find us at 46-48 Bevois Valley Road (Tel. 0703 25831). The shop has sold electronic components for many years and will start to stock the Maplin range from mid-August, but the full range will not be available until November.

As always, of course, the big event of the year for us is the publication of our new catalogue, and this year it's a massive 480 page book with tons of additional data and pictures. The new catalogue will be on sale at the Electronic Hobbies Fair for just £1, so make sure you get along there as it promises to be a super show. In the pleasant, relaxed atmosphere of the Alexandra Pavilion from October 27th to 30th, we'll be demonstrating lots of our projects and kits and you can see some of the large range of Heathkit products, including the incredible microprocessor controlled robot, Hero 1. We look forward to meeting you there.

The one major difference in the new catalogue is that now you will find everything with its price on the page. And that means in the next issue of this magazine we'll have an extra eleven pages of projects and features. See you then!

Cover illustration by Tony Worsfold

### Mail Order

P.O. Box 3, Rayleigh, Essex SS6 8LR.  
Telephone: (0702) 552911

### Shops at:

159-161 King Street, Hammersmith,  
London W6

Telephone: (01) 748 0926  
8 Oxford Road, Manchester  
Telephone: (061) 236 0281

Lynton Square, Perry Barr,  
Birmingham  
Telephone: (021) 356 7292

284 London Road, Westcliff, Essex  
Telephone: (0702) 554000

46-48 Bevois Valley Rd, Southampton  
Telephone: (0703) 25831

All shops closed Mondays

# Electronics

THE MAPLIN MAGAZINE

September to November 1983 Vol. 2 No. 8

## CONTENTS

### Projects

<b>Codelock</b> .....	12
<i>An electronic key to give extra security</i>	
<b>Doorbell For The Deaf</b> .....	42
<i>Soundlessly attracts your attention</i>	
<b>Dragon 32 I/O Ports</b> .....	23
<i>Versatile I/O ports accessible from BASIC</i>	
<b>Dragon 32 RS232/Modem Interface</b> .....	54
<i>Simply plugs into ROM expansion socket</i>	
<b>Logic Probe</b> .....	48
<i>Instantly understandable 7-segment readout at low cost</i>	
<b>Minilab Power Supply</b> .....	16
<i>All the voltages you need for your test bench</i>	
<b>Synchime</b> .....	2
<i>Bell and gong sounds to complement the Syntom and Synwave</i>	
<b>ZX Spectrum RS232/Modem Interface</b> .....	60
<i>With self-contained operating system</i>	

### Features

<b>First Base</b> .....	46
<i>Continuing our guide to digital techniques for beginners</i>	
<b>Heathkit</b> .....	14
<i>More fascinating kits for cars, education and the test bench</i>	
<b>Interfacing the BBC Micro</b> .....	20
<i>How to program the user port for control or measurement</i>	
<b>Machine Code Programming with the 6502</b> .....	51
<i>Part 2 of this series that lets you get right into your micro</i>	
<b>Rewiring Your House</b> .....	6
<i>First part of two giving you the lowdown on the electrician's secrets</i>	
<b>Say It With Satellites</b> .....	40
<i>More news of those orbits in the sky</i>	
<b>Using The Commodore 64</b> .....	58
<i>Get to grips with the sprites in your machine</i>	

### News

Atari: The Next Generation .....	5
Classified Advertisements .....	39
Coming Shortly .....	38
Corrigenda .....	38
Exhibition News .....	39
Maplin News .....	38
Maplin 1984 Catalogue .....	64
Modem News .....	59
New Books .....	45
Price List of Catalogue Items .....	27
Price List of Items in this Issue .....	38
Price List of Items Since Catalogue .....	37
Software From Atari .....	15
Subscriptions .....	64
Top Twenty Books .....	38

### Editorial & Production

**Editor** Doug Simmons  
**Production Manager** Sue Clark  
**Technical Editors** Robert Kirsch  
 Dave Goodman  
 Peter Blackmore  
**Art Editor** Roy Smith  
**Technical Artists** John Dudley

**Published by** Maplin Electronic  
 Supplies Limited  
 P.O. Box 3, Rayleigh, Essex  
**Printed by** Eden Fisher (Southend) Ltd  
**Typeset by** Quillset Typesetting  
**Distributed by** Spotlight Magazine  
 Distribution Limited  
 1-11 Benwell Road,  
 London N7

**Copyright:** All material is subject to world wide Copyright protection, and reproduction or imitation in whole or part is expressly forbidden. All reasonable care is taken to ensure accuracy in preparation of the magazine but Maplin Electronic Supplies Ltd cannot be held legally responsible for its contents. Where errors occur corrections will be published as soon as possible afterwards. Permission to reproduce printed circuit board layouts commercially or marketing of kits must be sought from the Publisher. © Copyright 1983 Maplin Electronic Supplies Ltd.

**SYNCHIME**  
**SYNCHIME**  
**SYNCHIME**  
**SYNCHIME**



- ★ Complements the Syntom and Synwave projects.
- ★ Makes a metallic chiming sound, similar to bells, gongs etc.
- ★ Delay variable from 50ms to 5s.

by Robert Penfold

The popular Maplin "Syntom" and "Synwave" projects are capable of synthesising a wide range of percussive sounds, such as drum and hand-clap sounds. The only obvious gap in their "repertoire" is metallic chiming sounds similar to bells, gongs, etc. The "Synchime" unit has been designed to fill this gap, and it has also been designed to match the "Syntom" and "Synwave" units. It can be triggered by tapping the case (or striking a drum on which the unit is mounted) or using a 5 volt positive trigger signal. The envelope shaper has a fast attack time and a decay time which can be varied from about 50 milliseconds to approximately 5 seconds. The other three controls are a straight forward combined volume and on/off type, plus separate frequency controls for the two oscillators. The latter give a wide operating range of about 100Hz to 7kHz so that a wide range of effects can be obtained. The output signal level is up to about 5 volts peak to peak from a low impedance source, which is more than adequate to drive any normal power amplifier.

## Block Diagram

A ring modulator and two audio oscillators are used to generate the basic sound signal, as can be seen from the block diagram of Figure 1. A ring modulator is a form of mixer, but it is more like the mixer circuits used in superhet radio receivers than a normal audio mixer. In other words, it heterodynes the two sets of input frequencies to produce sum and difference frequencies at the output. For example, a 1kHz signal at one input

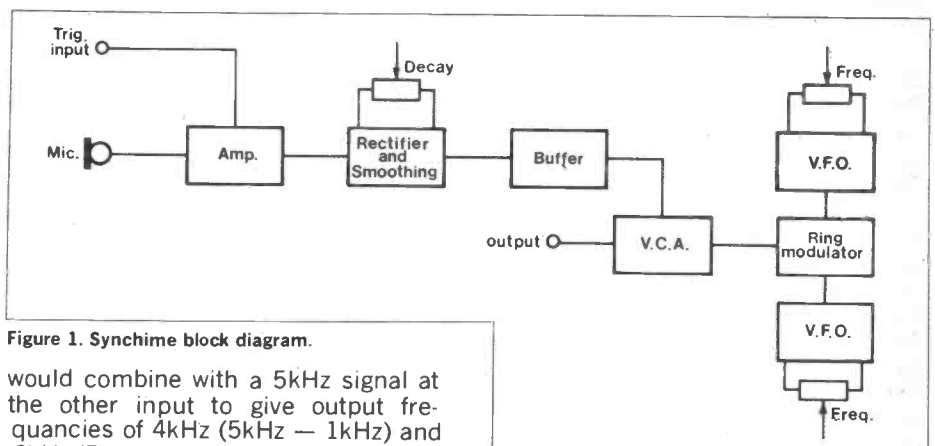


Figure 1. Synchime block diagram.

would combine with a 5kHz signal at the other input to give output frequencies of 4kHz (5kHz - 1kHz) and 6kHz (5kHz + 1kHz).

A ring modulator is a double balanced mixer, which simply means that both of the input signals are balanced or phased out at the output so that only the sum and difference frequencies appear at the output. In practice there is some breakthrough of the input signals at the output, but this is not really of any great significance. The important thing is that the new frequencies generated by the mixing action should be the dominant part of the output signal.

With most instruments the pitch of the sound produced is determined largely by a single dimension, such as the length of a string or a tube. This gives an output spectrum which consists of a fundamental signal plus harmonics of this signal. Instruments which use metal resonators are often two dimensional (plate-like) or three dimensional (bell-like) objects which consequently have more than one fundamental frequency, and mechanically produce a sort of heterodyne effect. A ring modulator fed by two

oscillators therefore gives a good electrical analogy of a metallic instrument, and this system generates the desired types of sound.

In order to obtain a realistic percussive sound it is essential to have suitable envelope shaping. A simple fast attack, plus relatively slow decay time is adequate, and this is obtained using an amplifier driving a rectifier and smoothing circuit. When the amplifier receives either a trigger pulse or pulses from the microphone, due to its low output impedance it rapidly charges the capacitor in the smoothing circuit. The discharge rate is controlled by a variable resistor, and this has a value which enables a very long discharge time to be achieved if desired. The output of smoothing circuit is fed to the control input of a V.C.A. which is used to process the output of the ring modulator before it is fed to the output socket.

## The Circuit

Figure 2 shows the complete circuit diagram of the "Synchime" unit.


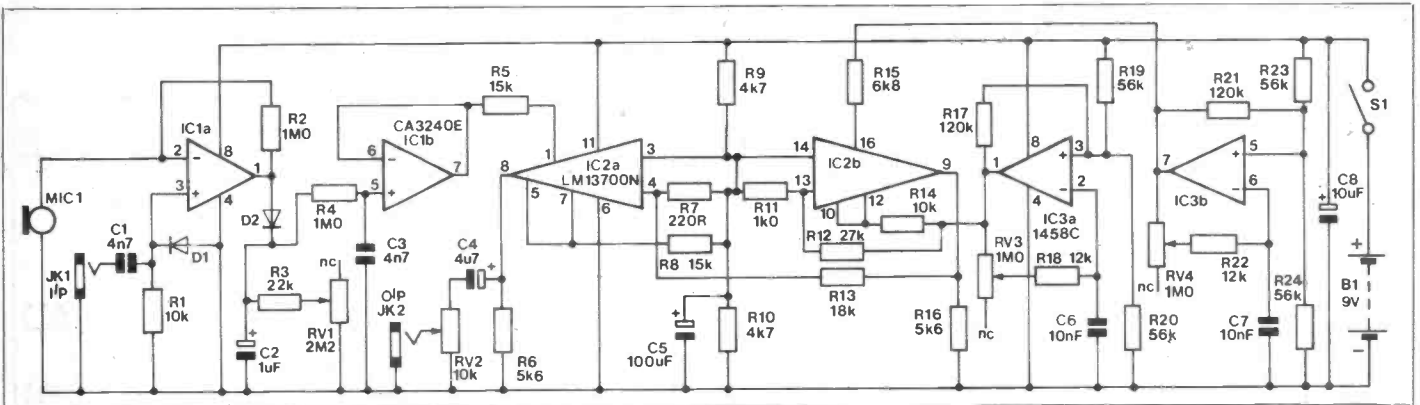


Figure 2. Synchronizer circuit diagram.

The two audio oscillators are based on the two sections of IC3, and a well known oscillator configuration is used here. The output is a roughly square waveform, and this seems to give good results in the present application due to the strong harmonics which produce a complex signal at the output of the ring modulator.

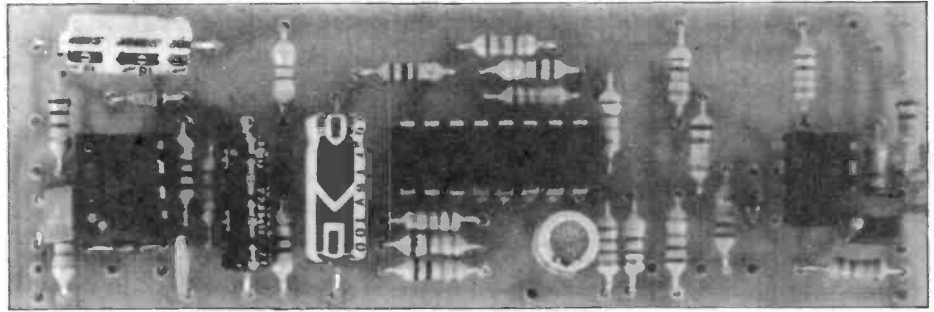IC2b is one section of an LM13700N dual transconductance amplifier, and this is the main component of the ring modulator. The output of IC3b is coupled to the amplifier bias input of IC2b via R15. The latter is needed because it is the bias current fed to IC2b that determines its gain, and not



the control voltage. Adding R15 in series with the amplifier bias input gives a bias current that is roughly proportional to the applied voltage, and gives the required voltage controlled operation.

The output of IC3a is fed to the non-inverting input of IC2b, and it is amplitude modulated by the signal from IC3b to give the heterodyne action and generate the new frequencies at the output. There is little breakthrough of the signal fed to the amplifier bias input and there is no need to add any components to phase out this signal. The same is not true of the signal fed to the inverting input of the modulator, and this does need to be balanced out. This is achieved by including R14 which feeds some of the input signal to the output of the transconductance amplifier. As the signal is inverted through the amplifier this gives the required cancelling, and the value of R14 is chosen to give a high degree of attenuation with the input to R15 at its average level.

Of course, the signal from IC3a is not totally blocked from the output. When the signal to the amplifier bias input is higher than its average level the gain of the transconductance amplifier increases and its output impedance reduces. This increases the signal from the amplifier and decreases the signal obtained via R14 so that the circuit is unbalanced. Similarly, if the signal to the amplifier bias input falls below its average level, the gain of the amplifier reduces, its output impedance rises and the signal obtained by way of R14 increases so that the circuit is again unbalanced. This provides a proper ring modulator action with a signal applied to just one input producing no significant output, but the mixed signal being produced if both inputs are fed with a signal.

R16 is the discrete load resistor for the emitter follower buffer stage at the output of IC2b. From here the signal is coupled by R13 to the input of the V.C.A. This uses the other section of IC2 as a straight forward V.C.A. which has its

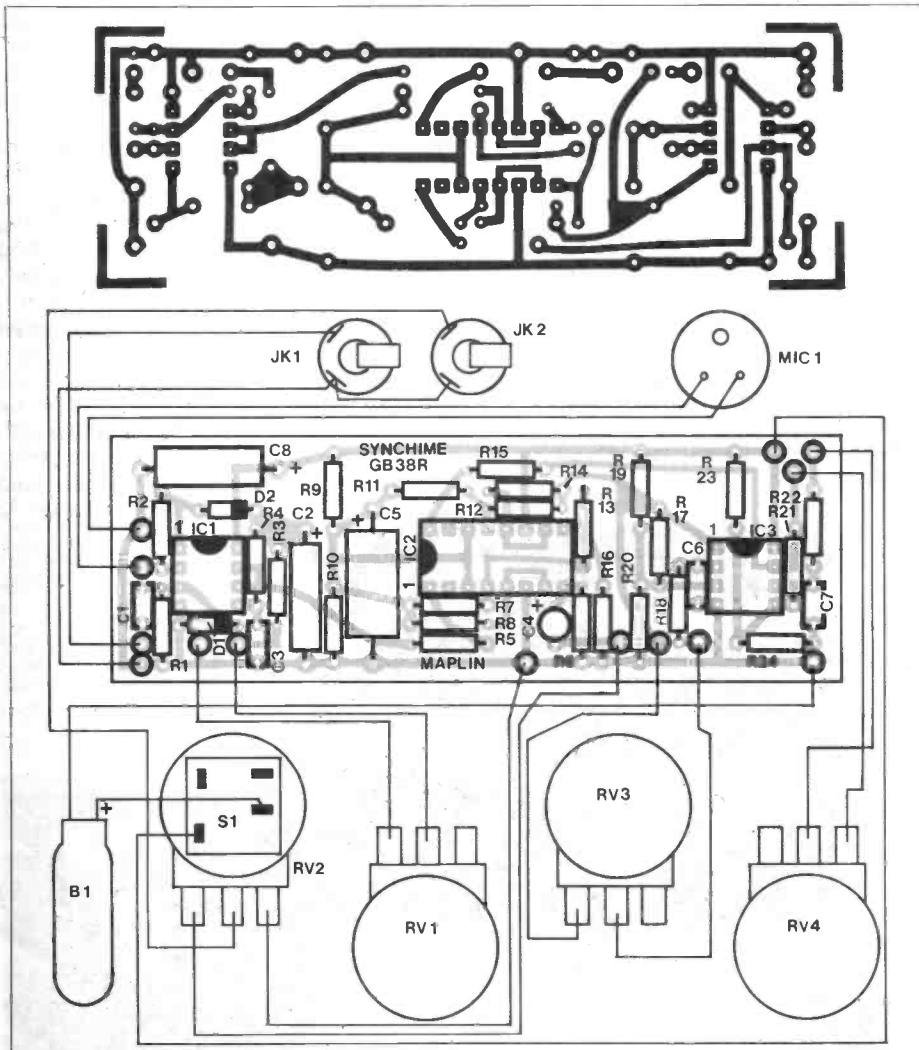


Figure 3. PCB layout.

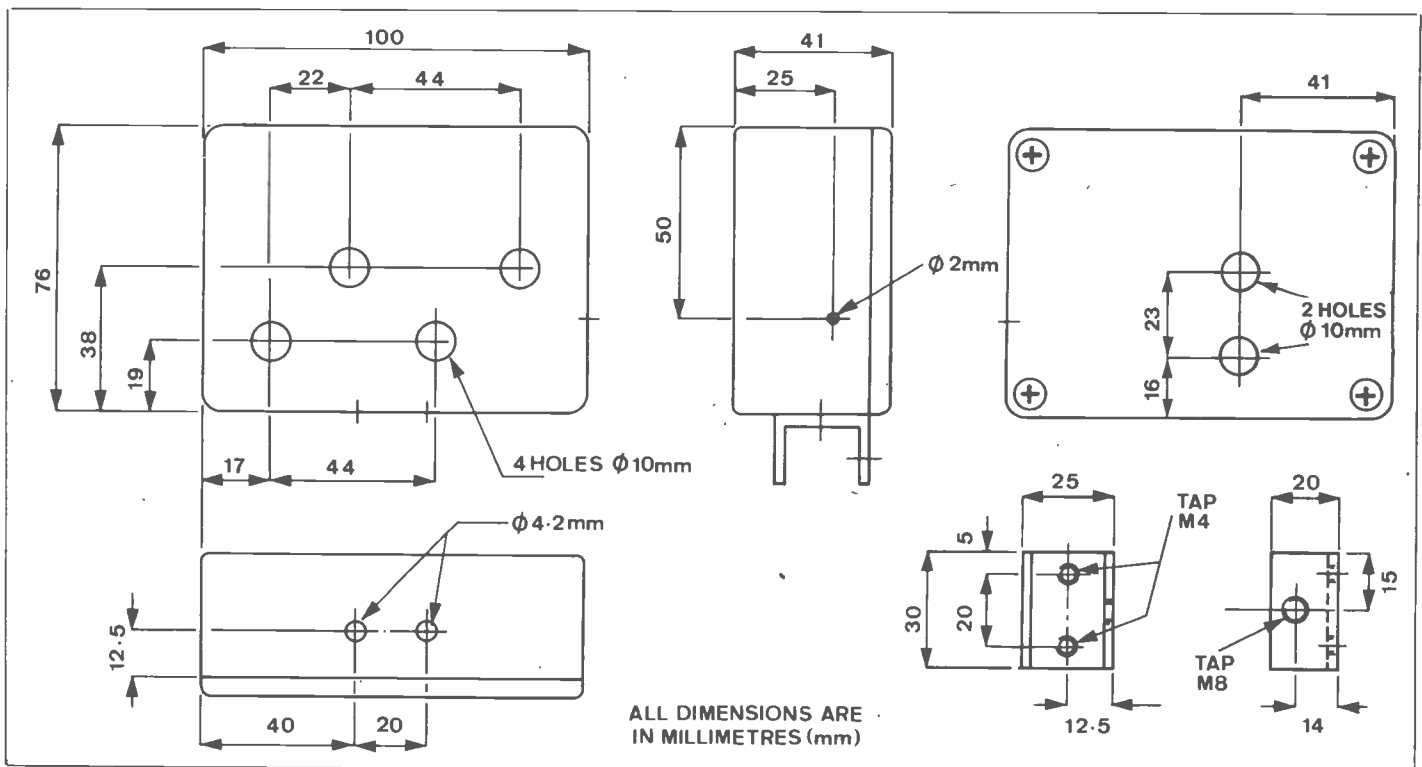


Figure 4. Case drilling details.

output coupled to output socket SK2 through volume control RV2.

IC1a is used as the input amplifier and it has Mic1 directly coupled to its inverting input. This is acceptable as the microphone is a crystal type, and it is actually a crystal earphone which is inexpensive but adequate for this application. R2 has been made quite high in value to give good sensitivity, but if necessary the value of this component could be changed to match the sensitivity of the unit to that of a Syntom or Synwave unit.

R1 biases the non-inverting input of IC1a to the negative supply rail so that the output also assumes this level under quiescent conditions. Negative input half cycles from the microphone drive the output of IC1a positive, but negative half cycles have no effect. The trigger signal is applied to the non-inverting input via C1, and a positive input pulse therefore gives the required positive output from IC1a. C1 is included so that long input pulses are effectively shortened and do not hold the envelope shaper "open".

D2 enables IC1A to charge smoothing capacitor C2, but prevents C2 from discharging into IC1a. It can only discharge through R3 and RV1, and RV1 therefore controls the discharge (decay) time of the circuit. R4 and C3 prevent the circuit from having an excessively fast attack time which would cause a loud "click" each time the unit was triggered. IC1b is the buffer amplifier which ensures that the smoothing circuit feeds into a suitably high input impedance. Note that the CA3240E device used in the IC1 position has a class A output stage which enables its output to go within a few millivolts of the negative supply rail so that the V.C.A. is cut off under quiescent conditions.

Other dual operational amplifiers such as the 1458C and LF353 cannot produce a low enough output voltage and will not operate properly in this circuit.


## Construction

Details of the printed circuit and wiring are shown in Figure 3. The layout of the board is such that crowding of the components occurs in several places, but this is inevitable given the number of components and the size of the board. However, construction of the board is not difficult provided the specified types of capacitor are used and the small components are fitted into place first. IC1 has a PMOS input stage and it should therefore be fitted in an 8 pin DIL socket. The normal MOS handling precautions should be observed when dealing with this device. Veropins are fitted to the board at points where connections to the microphone, battery, and other off-board com-

ponents will be made. When the board is installed in the case there is insufficient room to take wires over or under the board, and connections from the off-board components have to be made to the underside of the board. Either double sided pins must be used, or single sided pins inserted from the component side of the board must be fitted.

There is only just enough space for all the components inside the case, and the layout is very critical. Figure 4 shows the correct positions for the controls, sockets, and microphone, and it is advisable to follow this as closely and accurately as possible. The microphone, as explained earlier, is actually a crystal earphone. The transparent section of this is unscrewed from the main section and discarded. The screw at the rear of the unit is removed together with the rear cover which will come away with this screw. This screw is then used

*Continued on page 11*

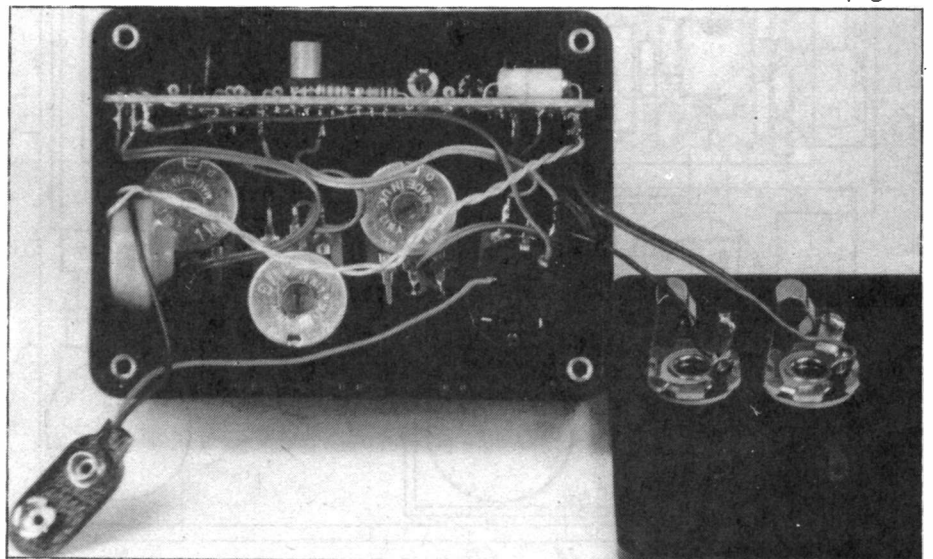

# THE NEXT GENERATION

A superb new range of high quality computers from Atari at very competitive prices. The range comprises three new computers similar to the existing 400 and 800, but with the following additional features:

- 24K ROM operating system and BASIC either or both of which may be software switched out.

- Help key to give background information on selected programs.
- 4 special function keys.
- International character set.
- Software compatible with almost all existing software for Atari.
- 11 graphics modes.
- 5 text modes.
- External processor bus for

future peripherals including a Z80 CP/M module running CP/M2.2 with its own 64K RAM.

- 256 colours — up to 128 displayable at one time.

Just to set to rest once and for all the popular misconception that Atari computers are just games machines, an expander box will be available in the new year with two RS232C interfaces,

a parallel Centronics interface and slots for eight expansion boards. These will include an IBM interface, Z80 interface, 128K RAM disk, Winchester disk controller, modem, 80-column card, real-time clock, voice recognition card and several others. Now let's take a look at this world-beating new range, line by line.



## The Atari 600XL Home Computer


*Simply — more features for your money.*

This stylish new computer replaces the Atari 400, yet features a typewriter-style keyboard like the old 800 model. The single cartridge slot is centrally placed above the keyboard, so program cartridges can be inserted or removed while the computer is on, without disrupting its operation. The computer is supplied with 16K RAM fitted, but a further 48K RAM is also available which simply plugs into

the parallel interface port on the computer's back panel to bring the total up to 64K and exactly match the spec of the 800XL. Unlike the American version, the British version is supplied with a socket for a monitor as well as TV. And the price for all that is just amazing.

\*†Order As AF77J (Atari 600XL) Price £159.95

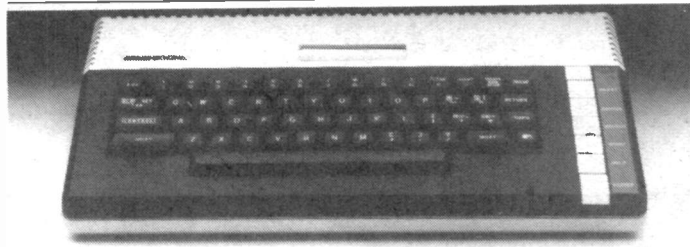\*\*†Order As AF79L (48K RAM FOR 600XL) Price £99.95



## The Atari 800XL Home Computer

*Complete with a full complement of 64K RAM.*

In a slightly deeper case than the 600XL, the 800XL is a natural replacement for the Atari 800, maintaining all the old features and adding all the new ones

described above, yet at a far lower price!

\*\*††Order As AF78K (Atari 800XL) Price £249.95

## Atari 1020 Colour Printer

A new plain paper printer to replace the old 822 thermal model. The printer can produce four-colour graphics and text. It can create graphs, charts, artistic designs and comes complete with programs that let you draw on the screen and plot on paper directly, using a joystick and any Atari computer. In standard format mode the printer prints 10 characters per inch at a speed of 10 characters per second. The four-colour print head prints and plots vertically and horizontally and 2 sets of colour pens (red, blue, green and black) are provided.


\*†Order As AF83E (1020 Colour Printer) Price £199.95

\*\*†BK80B (Paper for 1020)

Price TBA

\*\*†BK81C (Rainbow Pen Pack)


Price TBA

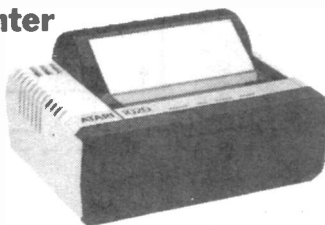
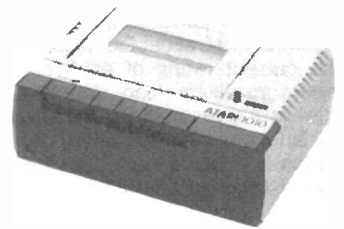
## Atari 1010 Program Recorder


Replacing the Atari 410 is the newly styled 1010. It maintains the dual format of the previous recorder, permitting data on one stereo track and audio on the other. An automatic volume control assures perfect record and playback levels and the top-mounted control buttons have a positive touch. Data transmission rate is 600 bits per second giving a capacity of about 100K bytes on a C60 cassette.

\*Order As AF80B (Atari 1010 Recorder) Price £49.95


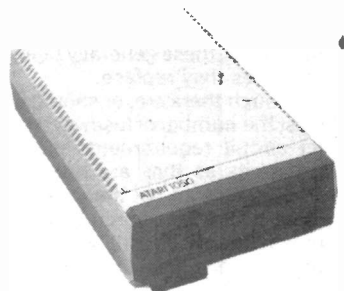
## Atari 1050 Disk Drive


This is the new replacement for the 810, and has an improved positive-feel loading mechanism. All new 1050 drives will be supplied with DOS III which permits a higher data packing density so that you can store up to 127K bytes on each side of a disk. You can of course still call a single-density mode which is fully compatible with disks recorded or pre-programmed for the 810, or convert single-density data to the new format. In addition you can of course plug up to 4 of these drives directly onto any Atari computer giving



you over half a Megabyte of on-line storage! The attractively designed, sleek new model is about half the height of the 810.

\*†Order As AF81C (Atari 1050 Disk Drive) Price £299.95

## Atari 1027 Letter-Quality Printer

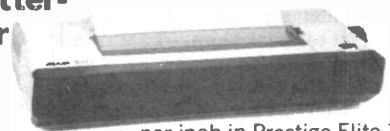

This new printer represents a low-cost technological breakthrough in letter-quality printers. It contains a five-wheel print-head that creates fully-formed characters like a daisy-wheel, but at a fraction of the cost. It's ideal for use with a word processor like Atariwriter for example. It prints 12 characters

per inch in Prestige Elite 12 face at a speed of 20 characters per second. The printer accepts single sheets of paper and features bi-directional printing and 80 column. There is also an underlining facility.

\*†Order As AF82D (1027 Letter Printer) Price £299.95

\*\*†BK82D (Replacement Ink Roller For 1027) Price TBA

## More New Products

The new Atari product line is swelled by a whole range of new products due for release in November '83 and January '84. They include Atari's new flagship computer, the 1450XLD which in addition to all the features on the 800XL includes 4 programmable keys with 12 preprogrammed functions, and a double-sided dual-density disk drive offering 254K bytes capacity. The price should be under £500!

Also coming soon are a Light

Pen, a Graphics Tablet, a new Joystick, an 80-column matrix Printer and a super new Trak-Ball controller that may sell for as little as £30! In addition to all this is the Expansion Box and its range of plug-in cards and the CP/M module described above. We'll have all the latest details in our next issue or for a more detailed specification of this brilliant new range get a copy of our new 1984 catalogue on sale from October 30th.

\* Prices are tentative, please check with us before ordering.

\*\* Prices not known at time of going to press.

† Available from mid-September 1983.

†† Available from mid-October 1983.

**Please note:** The above represents the very latest information from Atari (UK) at the time of going to press, but please check any specific point with us before ordering.

# Rewiring Your House

by Geoffrey Burdett

The modern home electrical installation consists of a number of circuits of various current ratings to meet the required total expected load in kilowatts. The current rating of each circuit is the maximum likely load demand which in aggregate gives the total maximum current demand on the installation. Most circuits originate at a combined mains switch and fuse distribution board, termed a consumer unit.

The fuse distribution section of the consumer unit comprises a number of fuseways, one for each circuit. Although traditionally termed fuseways, in many instances miniature circuit breakers (mcb's) are fitted into the fuseways instead of fuse units, these generally being superior to the fuses they replace.

Although there are, or should be initially, at least the number of fuseways in the unit to meet circuit requirements plus others to add circuits as they are needed over the years this is often not the case.

Where only one circuit is added, it is common practice to fit what is termed a mains switch and fuse unit, or switchfuse unit which is really a one-way consumer unit.

Such practice lacks foresight, and although only one circuit is added at the time it is better to allow for at least another circuit which means fitting a multi-way consumer unit. Whether a switchfuse unit or a multi-way consumer unit, this, with the existing consumer unit, is connected separately to the mains by the electricity board, usually via a service connector box.

Some installations have yet another consumer unit, for off-peak storage heating and water heating, time controlled by a time switch so that the circuits and appliances are energised only during the off peak period eg. about 7 hours overnight when electricity is supplied at about half price. See tariffs.

## Circuit cables

Most houses are now wired in pvc flat sheathed cable. The cable termed twin and earth has two insulated current carrying conductors, one red, the other black, and an uninsulated copper earth conductor now called the circuit protective conductor (cpc) and formerly the earth continuity conductor (ecc), because it is electrically continuous throughout the installation and terminated at the central earthing point, the earth electrode. In some parts of an installation 3-core plus earth flat pvc sheathed cable is used, usually in switching circuits containing more than one switch for the one light or for different lights in the same area. eg 2-gang, 3-gang assembly etc.

The core colours of 3-core and earth cable are red, yellow, and blue respectively plus the uninsulated earth conductor. The colours have no significance in home wiring but represent the three colours of the phases of a 3-phase electricity supply system. When used on single phase circuits


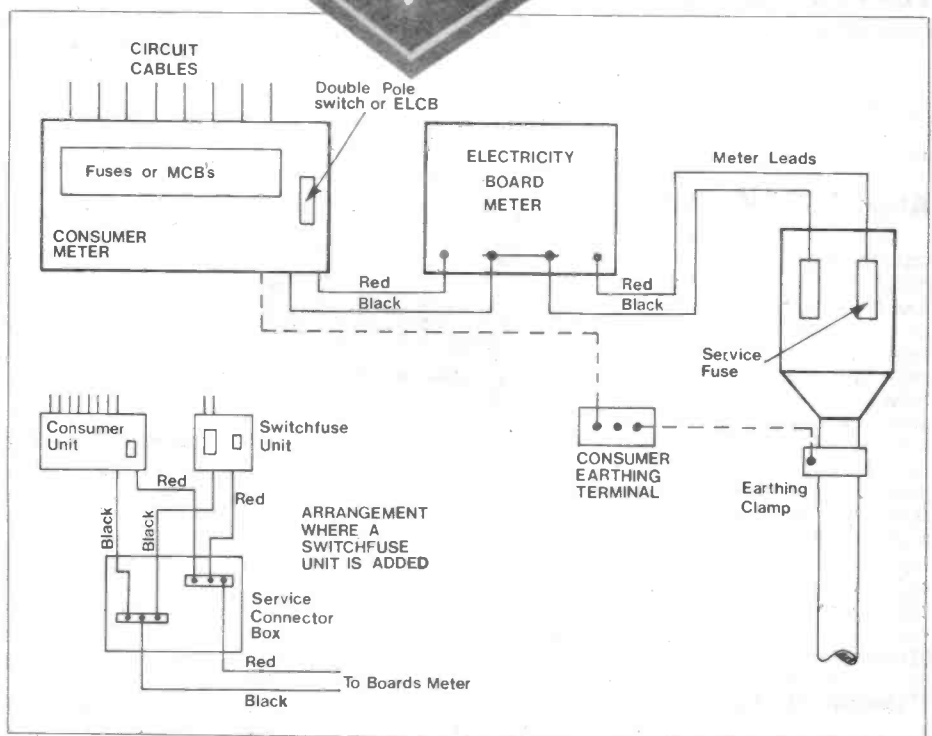


Figure 1. Arrangement at mains supply.

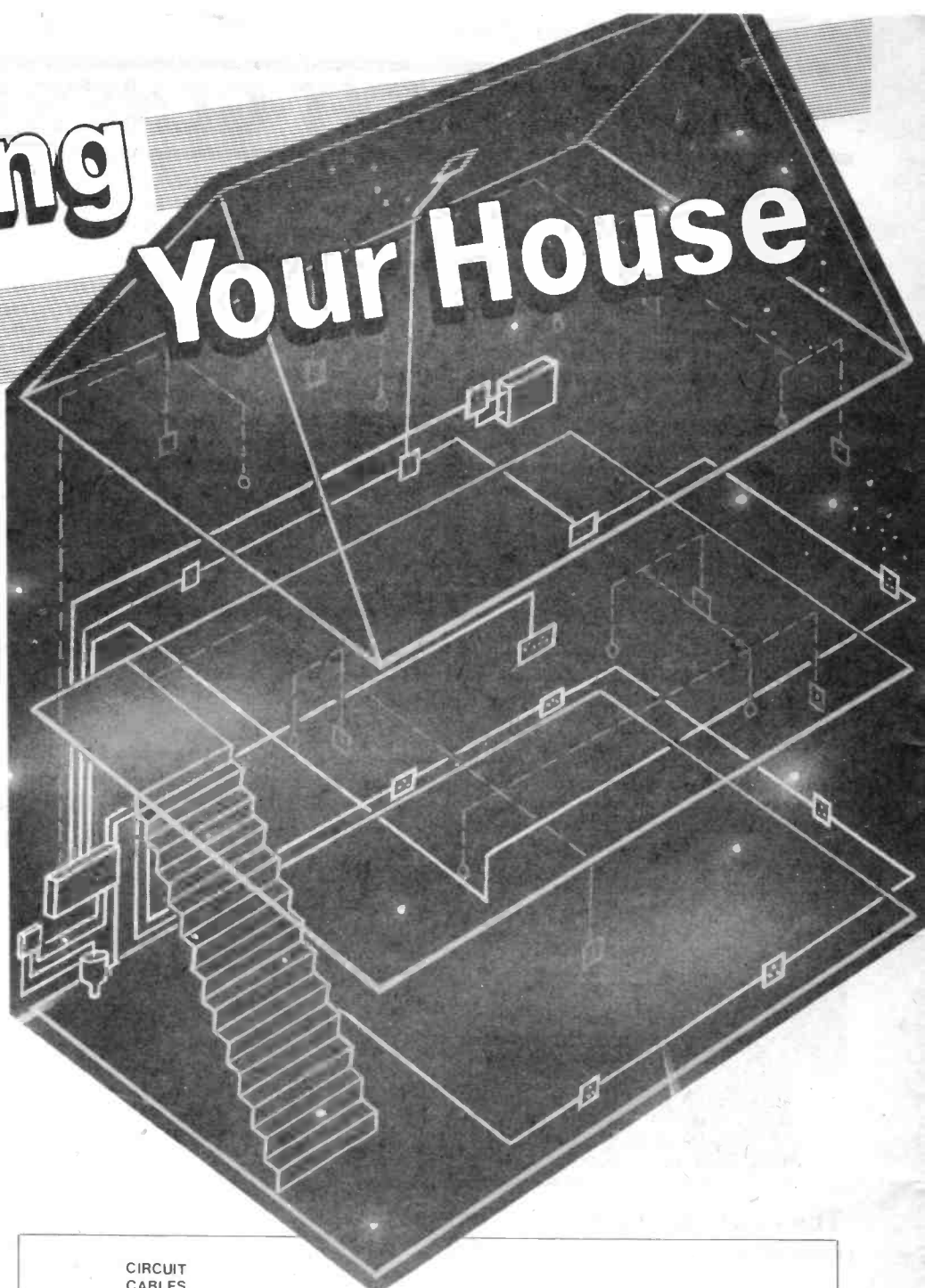

## REWIRING YOUR HOUSE

in the home for single pole switching the conductor ends should be enclosed in red sleeving or insulation tape as they are all live conductors.

Circuit cables are sold normally in 50m and 100m reels though they can be bought in shorter cut lengths where a limited amount only is required, this usually being the case with 3-core and earth cable and all the larger sizes of cables used in the home installation. Some homes are wired throughout in plastic conduit using non-sheathed pvc insulated cables in various colours. The cables are single-core and the colours are red, black and green/yellow striped, respectively.

The red is used for the live conductors, the black mainly for the neutral but is sometimes used as a live, suitably identified with red sleeving. The green/yellow conductor is the earth conductor.

Plastic conduit is also used in some twin & earth and 3-core & earth wiring, but as the cables are sheathed the conduit does not have to be continuous. It is used at switch drops and other vertical drops as well as in horizontal cable runs. Another form of enclosure for sheathed cables is plastic mini-trunking run vertically or horizontally on walls and ceilings.

### Sizes of cables

The size of a cable is given as the cross section area in  $\text{mm}^2$  of its current carrying conductor, the earth conductor in such composite cables usually being smaller since it carries current only to clear a fault. Earth conductors run independently are sized according to their cross section area in  $\text{mm}^2$ .

Circuit cables each have a specific size of current carrying conductor, the size determining the maximum current it is designed to carry without further rise in temperature. Possible voltage drop on long runs is also a factor considered when choosing a cable. The cable sizes used in home wiring circuits range from  $1\text{mm}^2$  to  $10\text{mm}^2$ , with larger sizes for the connection of the consumer unit to the meter, these being termed meter leads or meter bights.

The  $1.0\text{mm}^2$  cable is used for lighting circuits, the  $10\text{mm}^2$  cable for cooker circuit cables. The intermediate sizes of cables for other circuits. See table 1 for the current ratings.

### Circuit wiring accessories

In addition to the cables there are various components used in circuit wiring. The mounting box is among the most important wiring accessories, though often omitted. It is used for mounting socket outlets switches, fused connection units and a host of other accessories, these having open backs. The function of the box, in addition to being a ready mount for the accessory, is to enclose the unsheathed ends of cables, flex and connectors where used, in a non-combustible chamber.

There are two principal types of mounting box: moulded plastic and metal. The moulded plastic box is for mounting the accessory on surfaces and the metal box is for flush mounting the accessory, the box being sunk into the plaster or wall.

The boxes are of various sizes and depths. The most used box is the one-gang for mounting a single one-gang accessory. It is square in shape, approximately  $87 \times 87\text{mm}$ , the faceplate of the switch or other accessory being the same size. The metal box is slightly smaller at  $86 \times 86\text{mm}$  so that the accessory faceplate overlaps the box and covers the gap in the plaster.

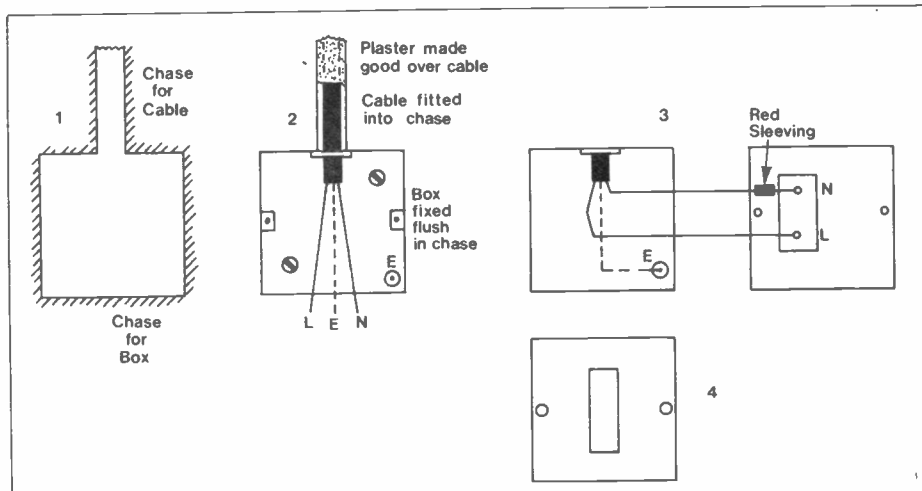


Figure 2. Sequence in fixing a flush lighting switch.

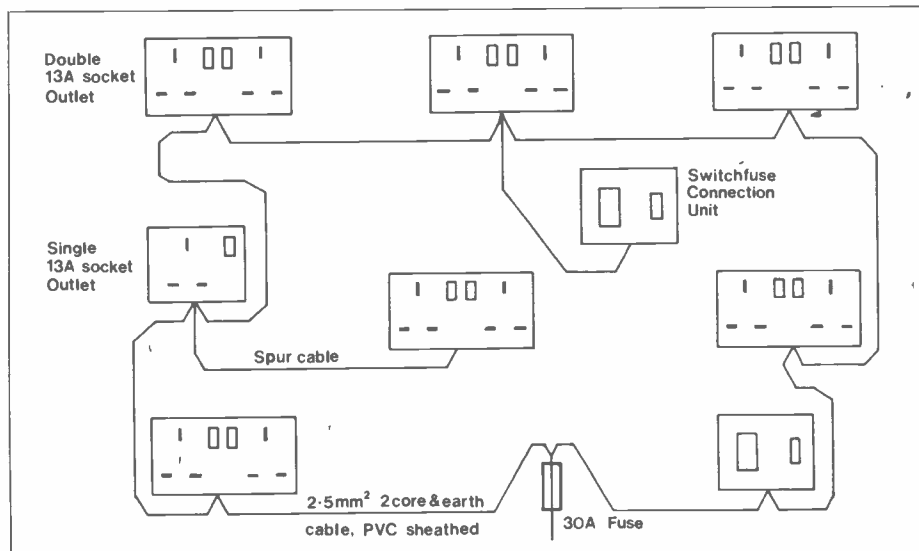


Figure 3. Ring circuit.

### Depth of boxes

The boxes for lighting switches are plaster depth 16mm deep, and the plastic box 17mm.

For socket outlets the standard box has a depth of 25mm and deeper boxes where needed depending upon the accessory and the room needed in the box for cable connections. All have two or more screwed lugs for fixing the accessory, these being tapped M3.5 metric. Some lugs are adjustable for levelling the accessory after the box is fixed.

Socket outlets and plateswitches are actually flush fitting components, although surface mounted or flush mounted according to the type of box. Surface sockets are entirely different. They are self contained, and usually have an enclosed back for direct mounting on a suitable surface, the sheathed cable passing right into the accessory. Some versions are, however, mounted on a slim pattress block. There are also surface type switches, these usually being metalclad and sold complete with metal surface boxes. Whatever the type of box or accessory it is essential that the pvc

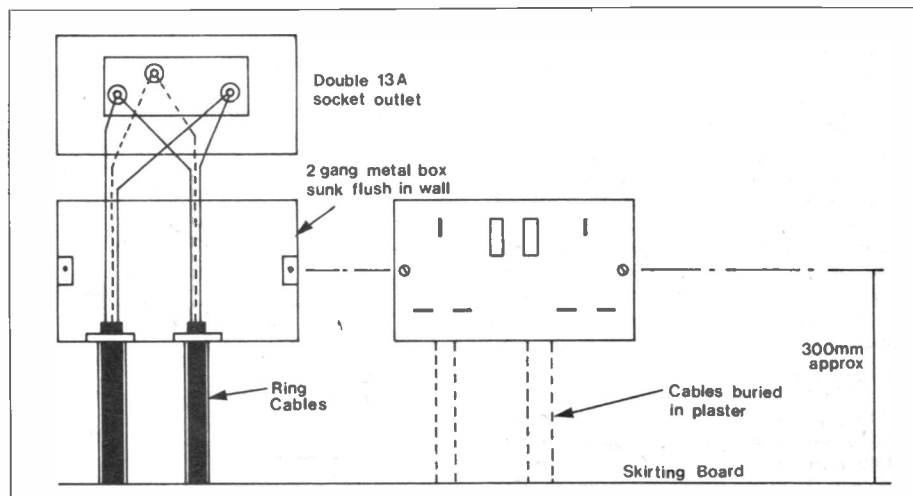


Figure 4. Fixing and connecting a ring socket outlet on the wall above a skirting board.

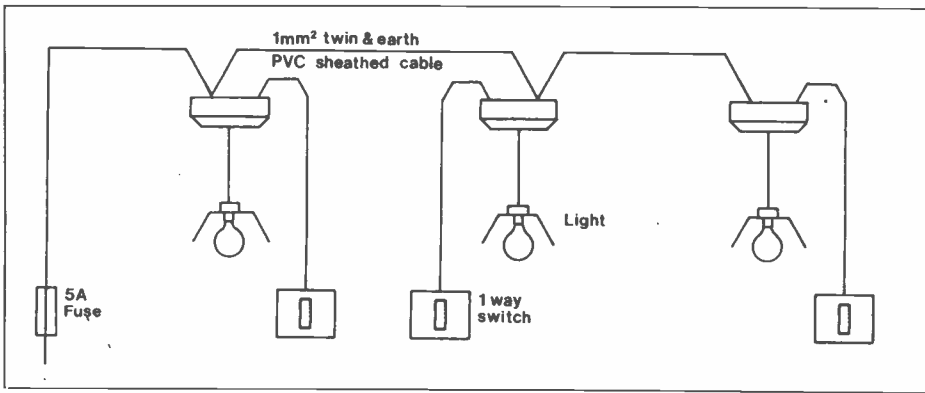


Figure 5. Lighting circuit wired on the loop-in system.

cable sheathing terminates within the accessory or its box.

The modern ceiling rose has no box and does not need one. It has an integral backplate, enabling it to be fixed direct to the surface of the ceiling. Thin plastic sections are knocked out of the backplate into which the sheathed cables are passed. Some batten lampholders and other ceiling fittings have an integral backplate, and need no box. However, most of the special pendant fittings do require a mounting box. This is a circular conduit box termed a BESA box, having a back outlet and fitted flush into the ceiling to support the ceiling plate and the fitting. Two screwed lugs are M4 metric. The box can be plastic, but where it is to support a fitting in excess of 3kg a metal box is necessary. The box is fixed to timber between joists, with a hole drilled to take the box outlet.

Most wall lights, as well as spotlights, also need to be mounted on boxes, to join the circuit wires to the flex wires and to contain the cable connector.

## Lighting switches

The modern lighting switches are termed plate switches because of their faceplate, usually moulded plastic but sometimes metal. Most fit a one-gang slim or plaster depth box. The switch assembly can be a single switch, either 1-way, 2-way or intermediate, or it can comprise two or three switches in the one gang, these would all be 2-way switches which can be used for either one-way or two-way. Where four, five or six switches are required in the one position, a 2-gang faceplate and a 2-gang box are used.

## Other switches

There is a whole range of switches used for other circuits including 20A double-pole, these requiring a deeper box. Cord operated switches used in the bathroom and bedroom are also made in one-way, two-way and double pole versions with and without neon indicator.

## Socket outlets

The modern socket outlet used in the home installation is the 13A with fused plug having square pins, and has largely replaced the old round-pin 2- and 3-pin plugs and sockets of 15A, 5A and 2A current rating. As already explained, most sockets are of the flush type, either switched or non-switched, with or without neon indicator, in single and double versions.

## Junction boxes

Junction or joint boxes used in home wiring systems are plastic, usually circular and have three or four terminals or banks of terminals. They are made in current ratings of 5A, 20A and 30A.

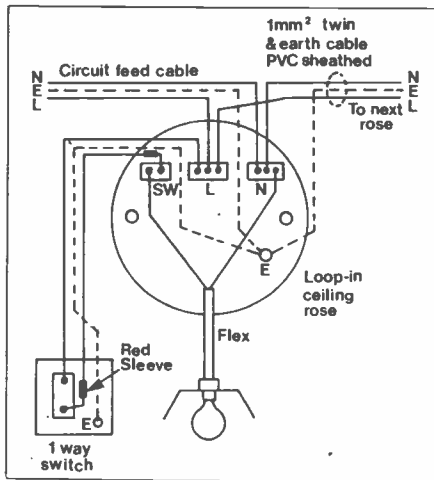


Figure 6. Connections at a ceiling rose on the loop-in system.

## The ring circuit

A ring circuit, or ring final circuit to give it its official title, consists of a pvc flat sheathed cable starting at a 30A fuseway or mcb in the consumer unit, and runs throughout the various rooms, finally returning to the same fuseway terminals, forming a complete loop or ring, the connections being made at either the terminals of a ring socket or at a joint box.

## Why a ring?

The ring circuit was designed in 1943/44 as a post war measure to enable dwellings to be equipped with an ample supply of socket outlets with the minimum of cable, when copper was in short supply. Before the advent of the ring a 15A socket outlet had to be supplied from a separate circuit, which meant 6 circuits for 6 15A socket outlets. However, abuse of the system over the years meant that sockets had been added to the original circuits, with subsequent danger

from overload on the old wiring.

Therefore a circuit was designed to allow a number of power sockets to be supplied from a single circuit, which would save cable and require only one fuseway in the consumer unit, or fuseboard. The alternative was a radial circuit, which to supply a number of 13A socket outlets would mean a very heavy and costly cable. The cable would have to be of 30A current rating and its conductors would be too large for looping in and out of terminals of socket outlets. Ultimately the circuit in the form of a ring was devised using cable half the current rating at 15Amps. For about the same cost the cable supplying the ring would be nearly twice the length, cover a wider area, and be able to supply more socket outlets than a single run of cable.

Since each socket outlet connected to the ring cable would in effect be supplied by two cables (outgoing and incoming), this gave the circuit a current rating of 30A to match the circuit fuse or mcb. The size of the circuit cable was 7/029 imperial which had a current rating of 15 amps, but was updated to 21 amps, as is its metric equivalent 2.5mm<sup>2</sup> now used to wire ring circuits.

Local fusing at each outlet was made necessary because the circuit fuse is 30A and requires anything up to 60 amps to blow. The local fuse is in the plug, so that it protects the appliance and flex connected to it against short circuit current. The current rating (maximum) of a plug fuse is 13A which is the equivalent of a little over 3000 watts. The rectangular shape of the plug pins was chosen so that it could not be plugged into any other existing socket nor could any other plug be plugged into the 13A socket outlet.

The number of 13A outlets (sockets and fused connection units) which may be supplied from any one ring circuit is unlimited but the area in which the outlets are fixed must not exceed 100m<sup>2</sup>. The logic is that adding sockets within a given area does not itself increase the load or current demand but to increase the area is likely to, so far as space heaters are concerned.

## Spurs

As mentioned, a spur is a cable branching off the ring cable at a convenient point, which can be the terminals of a ring socket or a 30A joint box inserted into the ring cable. Its principal purpose is to supply a socket outlet or a fixed appliance via a fused connection unit off the main route of the ring cable. This arrangement saves cable, but as it is a single length of 2.5mm<sup>2</sup> having a current rating of only 21 amps it may supply only one outlet. This can be either a single or a double socket or a fused connection unit. The number of spurs on a ring circuit must

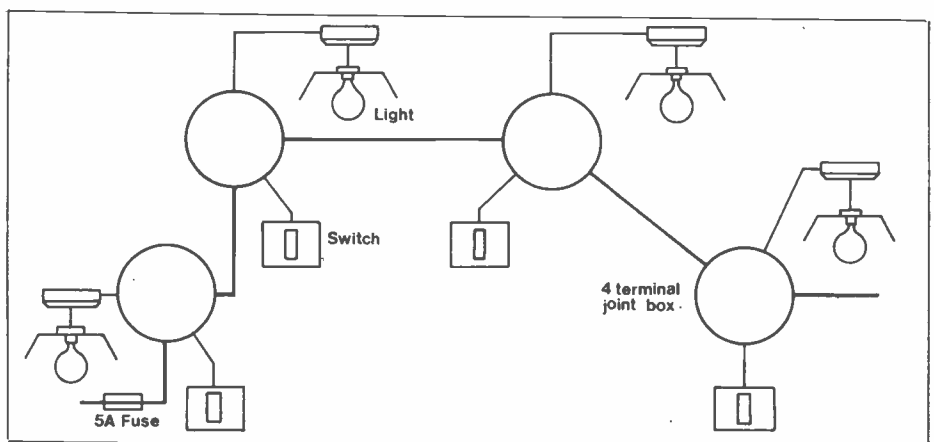


Figure 7. Lighting circuit wired on joint box system.

## REWIRING YOUR HOUSE

not exceed the number of socket outlets connected to the ring cable. Chiefly, spurs should be limited mainly for future extensions rather than to install initially, except where significant saving in cable can result.

### Lighting circuits

A lighting circuit is a radial circuit, which means that the circuit cable terminates at the last light on the circuit and does not return to the fuseway to form a ring.

A ring is not necessary, since the cable is smaller, and can extend throughout the house if necessary, and the number of lighting points will still be consistent with the current rating of the circuit fuse or mcb.

There are two principal methods of wiring lighting circuits, or rather lighting points, and either or both methods can be used on any one circuit. These are the loop-in and the joint box methods.

### Loop-in method

With the loop-in method the lighting circuit cable is run from a 5A fuseway in the consumer unit to each of the lighting points, starting at the nearest, looping out to the next, and so on until the last on the circuit, where the cable terminates.

Then, from each lighting point, a length of the same cable is run to the respective switch position, usually on the wall of the same room or area, eg hall or landing, and in some instances, such as in the bathroom, to a ceiling switch next to the access door. All the cable joints are made in the ceiling rose which also serves as a joint box with ready access in the same room.

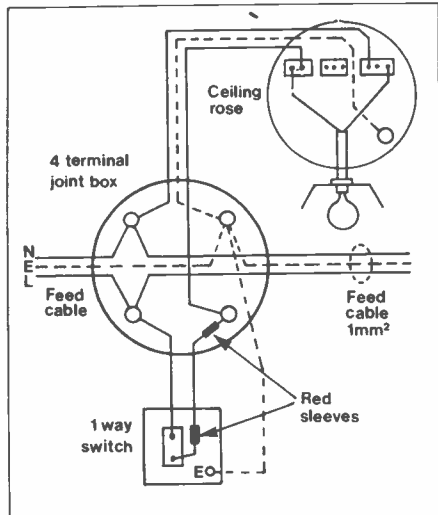


Figure 8. Joint box system.

### Joint box method

With the joint box method the lighting circuit cable is run from the 5A fuseway to a series of 4-terminal 15A joint boxes, one for each light, and its switch situated in a convenient position between each light and its switch.

Then from a joint box two additional cables are run, one to the light the other to the switch, making a total of four cables, two feed cables plus the light and switch cables, except at the last joint box where there is only one feed cable. All joints are made in the joint boxes, which being situated in the ceiling voids or roof space are comparatively inaccessible, which is the main disadvantage of the joint box method. The main advantage is that less cable is normally used.

### Mixed method

Although there are two methods, both September 1983 Maplin Magazine

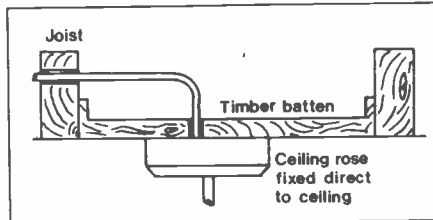


Figure 9. Fixing a ceiling rose.

can be applied to any one circuit, some lights being wired on the loop-in system, usually where ceiling roses are used. On other lights with no loop-in facilities, such as wall lights and some ceiling fittings and pendants, the joint box system is used with only one cable going to the light.

In rewiring the loop-in system is usually employed, since the new cables are run under the floorboards with the minimum disturbance and there is no need to allow for the fixing of joint boxes. Where the circuit cables are run in the roof space for the upstairs lighting the joint box method is often used, with the joint boxes fixed between joists.

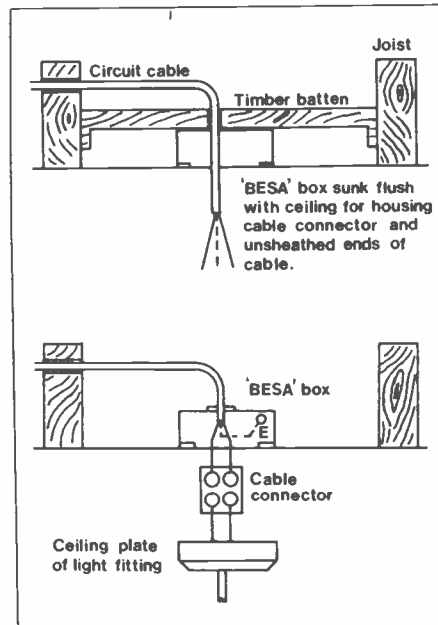


Figure 10. Fixing a light pendant fitting other than a ceiling rose.

### Number of lights per circuit

A lighting circuit of 5A is on a 240V electricity supply equal to 1200 watts. This is the maximum which should be connected to the circuit. However regulations stipulate that a light containing a tungsten filament bulb is assessed at 100 Watts for any bulb, up to and including 100 Watts. Bulbs of higher wattage are assessed at the actual wattage. 12 bulbs at 100 watts each total 1200 watts, which is the maximum permitted. This means that the circuit may serve twelve lampholders, provided none contain bulbs of higher wattage than 100W. Where there are higher wattage bulbs the number of lampholders are reduced proportionately. With one or more 2- and 3-light fittings plus higher wattage bulbs the number of lights on a circuit should definitely not exceed eight, and preferably no more than six, so that the area affected by a fuse blowing is limited; this also allows for future additions of one or more lights on a circuit. A house of 3- or 4-bedrooms usually requires two lighting circuits but where wall lights and spotlights are included the number will be more.

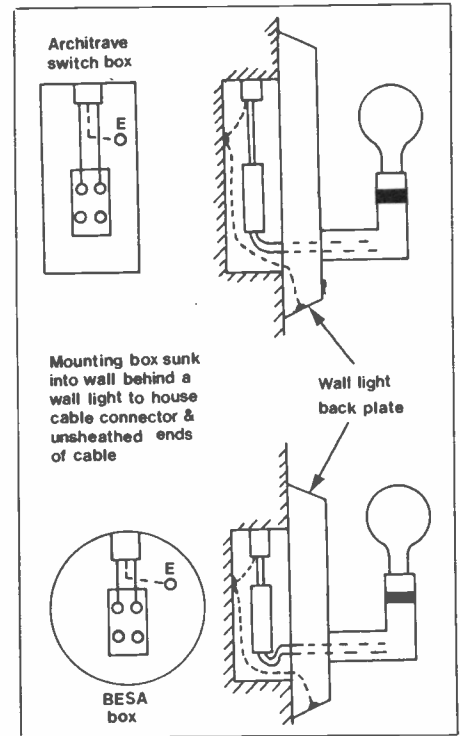


Figure 11. Mounting wall lights.

Fixed lighting, especially spotlights, can be supplied from a ring circuit via a fused connection unit fitted with a 3A fuse. Cable used for a lighting circuit is, as already explained, 1.0mm<sup>2</sup> twin & earth pvc sheathed with some sections wired in 3-core and earth pvc sheathed cable.

### Installing lighting fittings

The simplest lighting fitting is the plain pendant comprising ceiling rose, flex and pendant lampholder. The ceiling rose of the wired pendant is connected to the circuit cables and fitted direct to the ceiling, with wood fixing between the joists to support it. See figure 9 for connections. Batten lampholders and some enclosed lighting fittings are similarly connected, but as already explained a special pendant having a ceiling plate is connected to a circular box fixed flush with the ceiling. The circuit wires are connected to the flex using cable connectors housed in the box. See figure 10.

Wall lights are fixed either to a round box or are mounted over an architrave switch box and fixed direct to the wall. See figure 11.

### Fixing switches

A wall switch is fixed to a box mounted on the wall at a height of about 1.4m above floor level. For surface mounting a plastic box is used. This is fixed to the wall by two No.8 wood screws in holes drilled and plugged in the wall. A section of thin plastic is knocked out of the edge of the box and the cable threaded through. The end of the sheathing within the box is stripped off, and about 10mm of insulation from the end of each of the two insulated conductors. A piece of red sleeving or red pvc insulation tape is fitted over the end of the black wire, and the two conductors are connected to the two terminals of the one-way switch. The bared end of the earth conductor is enclosed in green yellow striped pvc sleeving and the conductor is connected to the earth terminal of the box. If a 2-way switch is used one conductor is connected to the common terminal of the switch, the other to the L2 terminal, and the switch fixed to the box with the Top on the faceplate at the top so that the rocker will be down to switch the light on.

## REWIRING YOUR HOUSE

For flush mounting the plastic box is fitted into a plaster depth chase cut into the plaster and, using No.8 wood screws, fixed to the wall in the two drilled and plugged fixing holes. For a cord operated ceiling switch the cable is passed through a removed section of thin plastic in the backplate, the ends prepared and the black conductor with red sleeving connected to the switch terminals and the sleeved earth terminal connected to the earth terminal on the backplate.

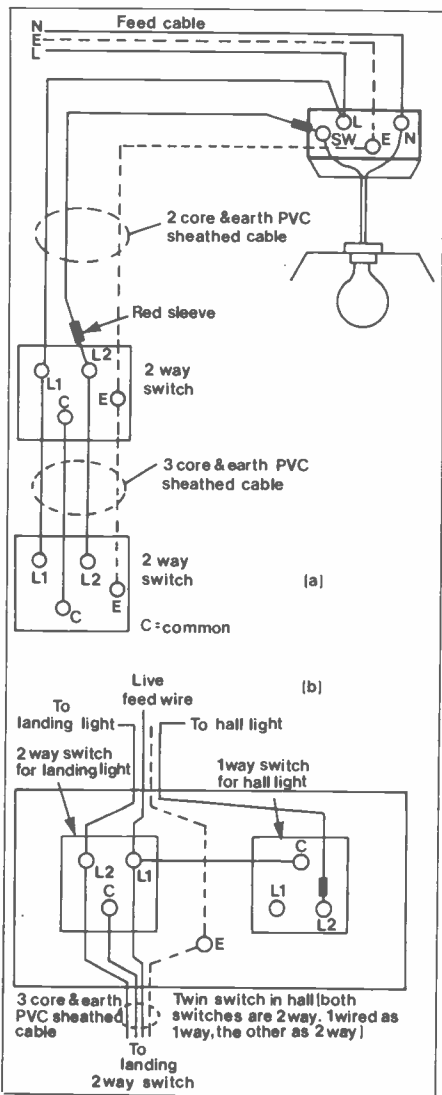


Figure 12. Two way switching circuit with hall and landing wiring.

### Two-way switching

Where a light is to be controlled by two switches in different positions a 3-core and earth cable is run from the first switch position to the second switch position and a 2-way switch fixed at each. The connections at each switch are shown in figure 12.

### Intermediate switching

Where a light is to be controlled by three or more switches in different positions intermediate switching is used. This is a 2-way switching circuit with a 2-way switch at each end and one or more switches fixed in intermediate positions between the two 2-way switches. One intermediate switch is needed for each extra switch position. An intermediate switch is an ordinary plate switch of the rocker type, but has four terminals instead of the two of a 1-way switch and three of a 2-way switch.

The 3-core and earth cable running

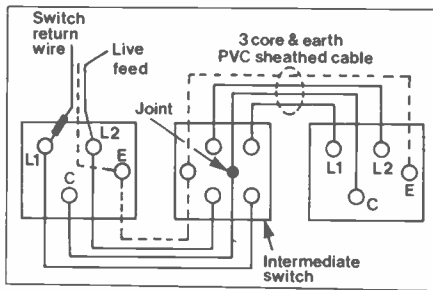


Figure 13. Intermediate switching.

between the two 2-way switches is cut at each intermediate switch and the yellow and blue wires connected to the terminals as shown in figure 13. The red wire running from the common terminal of one 2-way switch to the common terminal of the other 2-way switch is not connected to an intermediate switch, but because the cable is cut the conductor is jointed in the mounting box of the intermediate switch so that it is continuous from one 2-way switch to the other.

### Dimmer switches

Where a light is to be controlled by a dimmer switch instead of a rocker switch the dimmer switch replaces the rocker switch without any need for modification in the wiring. Most dimmer switches fit the shallow or plaster depth switch. They are made in one and two-gang assemblies, to fit a one-gang box and control more than one light.

Where the light is fluorescent a dimmer switch cannot be used, though there are special dimmers and fluorescent fittings that can be used, but an extra switch wire has to be run from the switch to the fluorescent lighting fitting.

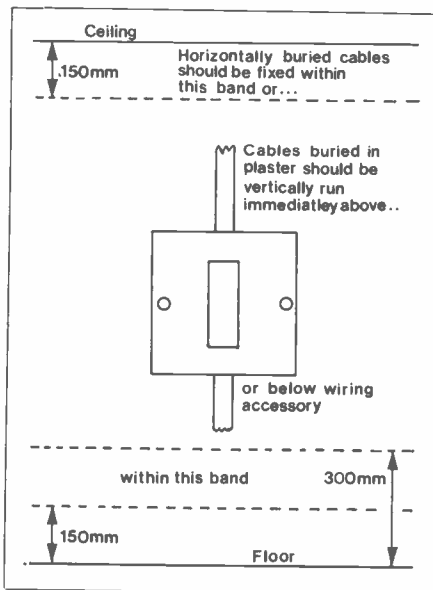


Figure 14. Laying horizontal cables.

In a roof space where polystyrene granules are used for heat insulation pvc sheathed cables must be situated where they do not come into contact with them, as the pvc is adversely affected by it. If it is not possible to avoid the insulation the cables should be enclosed in plastic conduit. Generally cables in the roof space should be situated away from walkways and the cold water storage cistern where they are likely to be disturbed.

### Running circuit cables

The various circuit cables are normally run in the void between the ceiling and floorboards above the ground floor of a 2-

storey house. These cables serve the lighting points and switches in the room below. Ring circuit cables supply socket outlets in the first floor rooms, and cables to an immersion heater and other apparatus are also run in this void. In the roof space are mainly lighting cables feeding the lights and switches in the rooms below, though the cable to the shower in the bathroom is sometimes run in the roofspace to a ceiling switch in the bathroom.

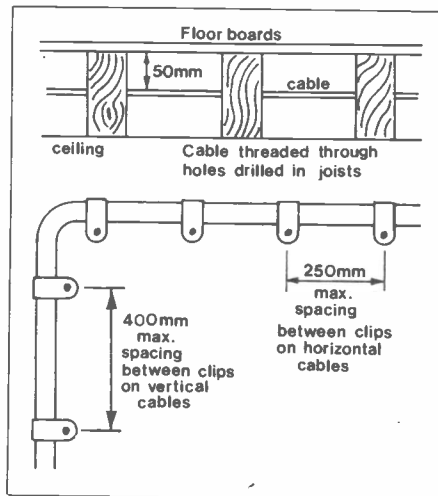


Figure 15. Fixing cables.

On the ground floor cables are run in the void below the floorboards where it is a suspension floor, but if the floor is solid cables may be run in conduits before the screed is laid, otherwise they are run behind skirting boards. PVC sheathed cable may in fact be run anywhere along the house structure, fixed to the surface or buried in the plaster without the need for protection from the risk of mechanical damage.

Cables clipped to the surface must have fixings not more than 250mm apart for horizontal runs and not more than 400mm apart for vertical runs. Where cables are buried in the wall they should be as far as practicable be run vertically exactly above or below the switch or socket outlet they feed so that anyone later fixing shelves will know where to expect them. Where horizontal buried cables cannot be avoided they should be run in a band 150mm from the ceiling or between 150mm and 300mm above floor level. Where cables are run under floors and cross joists they must be threaded through holes drilled in the joists not less than 50mm below the tops of the joists.

It is neither necessary nor desirable to enclose pvc sheathed cables in conduit where buried in the wall since they are unaffected by plaster, and the extra chopping away can damage the wall structure. In houses under construction it is usual to enclose them so they stay in place and are not damaged by the plasterer's float during plastering.

### Permission to wire

No permission is required in Britain to carry out home electrical installation work, though where the house is rented permission may be necessary from the owner. Neither electricity boards nor local authorities or any other official body has any jurisdiction in respect of wiring. The work should however conform to the IEE Wiring Regulations published by the Institution of Electrical Engineers and recognised as a code of good wiring practice by all official bodies, including electricity boards and government departments. The regulations,

## REWIRING YOUR HOUSE

contrary to popular belief, are not statutory, and an electricity board has no powers to refuse connection to its mains of an installation, or parts of it, which do not strictly conform to the current IEE wiring regulations, but a board can and will refuse connection to its mains of any installation which is dangerous and as such does not conform to the Electricity Supply Regulations. These are statutory and are quoted in the application form signed by a consumer when requiring a supply of electricity.

An installation conforming to IEE Wiring Regulations is deemed to satisfy the requirements of the Electricity Supply Regulations and the electricity board must connect it to the mains. In these circumstances the board must connect the installation, whether carried out by a recognised contractor or by the householder himself.

From a contractor the board requires a test certificate, and may waive its own test and inspection. The householder who is unable to complete a test certificate can expect the board to test the installation through they are not obliged to do so. The test is at the option of the electricity board and is mainly to satisfy them that the installation will not adversely affect the supply to other consumers. It is important to note that good workmanship using correct material is necessary to conform to the regulations.

### Electricity tariffs

A tariff is the means by which an electricity board calculate the amount to charge a consumer for electricity and the service provided. Basically, all tariffs consist

of a fixed quarterly charge plus a charge for each unit of electricity consumed. Most domestic tariffs are of this type, though where a lot of electricity is consumed during off-peak times the charge for the electricity may be reduced, or even halved. A popular off-peak domestic tariff is the Economy 7 which provides electricity over a 7-hour night period at a cheaper rate.

Electricity consumed is registered on a 2-rate meter, and all electricity consumed during the 7-hour period is cheaper, whereas in some former off-peak tariffs only the electricity consumed by storage heaters qualified for the cheaper rate.

Even though the cheap rate now applies to all electricity consumed during the off peak period it is not usually financially beneficial to adopt the tariff, because the day time rate is higher than the standard rate per unit on the ordinary tariff. It is therefore advisable to have the tariff temporarily for at least two quarters (one summer

the other winter) so that a comparison may be made.

\*These current ratings apply where the cables are clipped direct to the surface. Ratings are lower for enclosed cables and some other situations, but are all suitable for the circuits specified.

Circuits	Fuses	Colours
Lighting	5A	White
Ring	30A	Red
Immersion heater	15A	Blue
Storage heater and 20A Radial Circuit	20A	Yellow

### Current ratings of house wiring cables

The various cables used in house wiring with their sizes, current ratings, and the principal circuits in which they are used are as follows:

Cable size mm <sup>2</sup>	Current rating* amps	Circuits
1.0	16	lighting
1.5	20	lighting and 15A single socket circuits
2.5	28	ring circuits and 20A radial circuits
4.0	36	radial circuits (30A)
6.0	46	cooker circuits, shower unit circuits
10	64	cooker circuits
16	85	meter leads
25	108	meter leads

### SYNCHIME Continued from page 4

to mount the microphone inside the case.

The printed circuit board fits into the top set of horizontal mounting rails in the case with the component side facing upwards. It will probably be necessary to angle C7 slightly inwards so that it fits under one of the corner mounting pillars of the case. Before finally fitting the board in place complete all the point-to-point style wiring. There is space for the PP3 size battery to fit between the sockets and the microphone, and a piece of foam material can be used to wedge this firmly in place.

### Testing

With SK2 coupled to an amplifier and

the volume control advanced, tapping the unit should give an output, and using RV1 it should be possible to control the duration of each burst of output signal. The two pitch controls can be a little confusing at first, and it has to be remembered that the main output signals are the sum and difference signals produced by the fundamental frequencies of the two oscillators. The fundamental frequencies themselves appear at the output at a very low level, and might not be apparent at all.

In practice this means that quite a low pitch can be obtained if both pitch controls are set for a high output frequency, since the difference fre-

quency might then be just a few tens of Hertz. With a little experimentation you should soon discover the types of sound that are produced at various control settings. At most settings of the pitch controls the output sounds quite discordant, but with the two oscillators set some musical interval apart, normal chime type sounds will be obtained. Good effects can be obtained with the two oscillators just fractionally off-tune, so that a low frequency beat not is obtained. At most settings of the frequency controls the output signal contains a wide range of frequencies, and filtering the output signal can expand the range of effects that can be obtained.

### SYNCHIME PARTS LIST

Resistors — All 0.4W 1% Metal Film

R1,14	10k	2 off	(M10K)
R2,4	1M	2 off	(M1M)
R3	22k		(M22K)
R5,8	15k	2 off	(M15K)
R6,16	5k6	2 off	(M5K6)
R7	220R		(M220R)
R9,10	4k7	2 off	(M4K7)
R11	1k		(M1K)
R12	27k		(M27K)
R13	18k		(M18K)
R15	6k8		(M6K8)
R17,21	120k	2 off	(M120K)
R18,22	12k	2 off	(M12K)
R19,20	56k	2 off	(M56K)
RV1	2M2 lin pot		(FW09K)
RV2	10k switched log pot		(FW63T)
RV3,4	1M lin pot	2 off	(FW08J)

Capacitors

C1,3	4n7 ceramic	2 off	(WX76H)
C2	1uF 63V axial elect		(FB12N)
C4	4u7 63V P.C. elect		(FF03D)
C5	100uF 10V axial elect		(FB48C)

C6,7	10nF mylar	2 off	(WW18U)
C8	10uF 25V axial elect		(FB22Y)

Semiconductors

IC1	CA3240E		(WQ21X)
IC2	LM13700N		(YH64U)
IC3	1458C		(QH46A)
D1,2	1N4148	2 off	(QL80B)


Miscellaneous

JK1,2	Std Open Jacks	2 off	(HF91Y)
S1	Part of RV2		
B1	9 volt PP3 size		
Mic 1	Crystal earpiece		(LB25C)
	Case type MB2		(LH21X)
	Synchime PCB		(GB38R)
	8 pin DIL socket		(BL17T)
	Control knobs	4 off	(YG40T)
	Blue cap		(QY01B)
	Green cap		(QY02C)
	Red cap		(QY04E)
	Yellow cap		(QY06G)
	Battery connector		(HF28F)
	Wire	1 Pkt	(BL00A)
	Synchime Front Panel		(BK77J)


A complete kit of all parts is available.

Order As LK15R (Synchime Kit)

Price £10.90

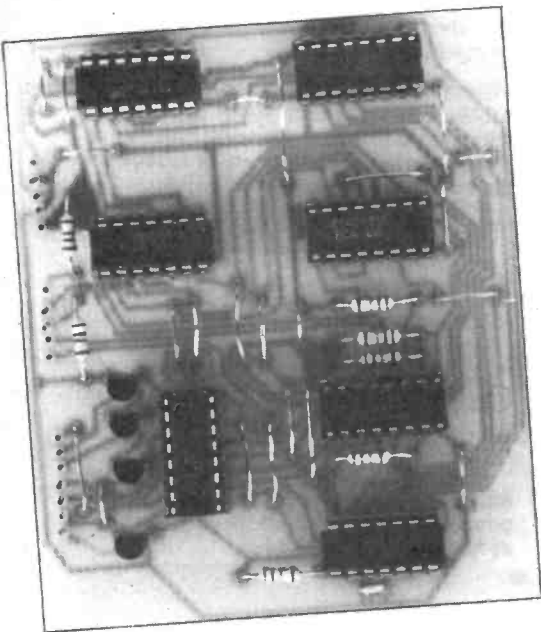

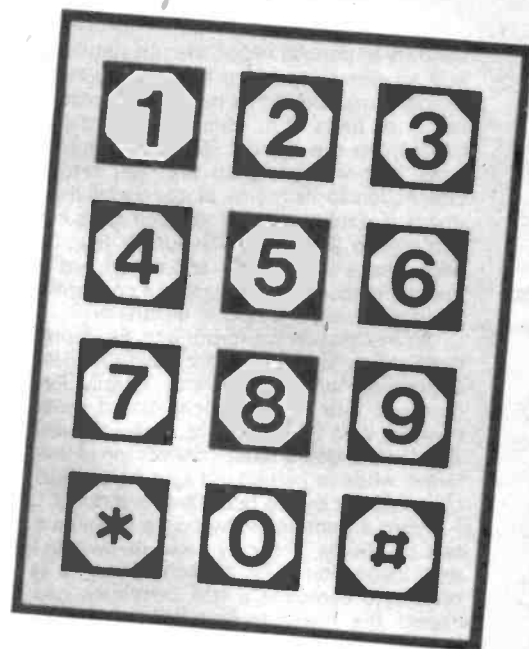CODE  
 LOCK  
 CODE  
 LOCK  
 CODE  
 LOCK



With the current accent on home security, there have been many designs appearing recently for circuits to protect electrically operated doors or to add to the security of an existing alarm system, by using a code, known only to the owner, that will only disable the associated circuitry when correctly entered on an appropriate keyboard.

Fully programmable units have rarely been included due to their tendency to be costly, consequently extensive use of dummy switches, to fool the unauthorised persons, has been made. This normally means that a soldering iron is the only means of changing the code should it be required (and it frequently is).

The system shown here is fully programmable. A four digit code is used which can be stored and changed at any time simply by switching between read and write mode. (All the external components, plus the PCB but excluding the keypad, should be mounted in a case that is also protected by this device, to prevent access to the read/write switch or any other part of the unit that could render it inoperative).

### Circuit Description

The keypad is anoted in exactly the same way as a push-button telephone, with digits 0-9, a hash key and an asterisk key. The hash key is used to arm the system, i.e. take the active high output 'high' and the active low output 'low'. The asterisk key is used to reset the system. This causes the memory address pointer and the number of correct entries counter to be reset to zero. (This also happens on every fourth keystroke). The keys 0-9 are used to enter the code. The four transistors TR1-TR4 are included to allow the use of an SPST type keypad. When a key is pressed, the encoder chip IC2 converts the row/column

by Nigel Fawcett

- ★Fully programmable
- ★Will work with Maplin Home Security System
- ★Has a wide range of applications

CODE  
 LOCK  
 CODE  
 LOCK  
 CODE  
 LOCK

matrix into a binary code. If either the hash or asterisk symbols are pressed then the system performs a reset or an arm function respectively. If a number key is pressed then operation depends on the state of S1. In write mode, the code is written into the current memory location of the 4\*4 bit register chip IC3. The address pointer is stepped onto the next location.

In read mode, the code is sent to the 4063 4-bit comparator IC4, this is then compared with the contents of the current memory location of IC3. If both codes match, then the number of correct entries counter is incremented. In either place the memory pointer is stepped on. If after four consecutive entries bit 2 of the counter is set, then the system will be disarmed, otherwise a reset is performed. Half of IC5 is used as the memory pointer, the other half being the output counter. Half of IC1 is wired as an astable multivibrator to generate the 16kHz clock for IC2, whilst half of IC7 is configured as a flip-flop to provide the active high and active low outputs. The remaining gates are used to decode the arm and reset conditions and to provide the correct polarity for certain data signals.

### Construction

Insert all the wire links and resistors. Mount the four transistors and all the IC sockets. The three PCB mounted edge sockets should now be fitted and S1 wired to the appropriate plug. When the PCB has been thoroughly checked for bad joints or short circuits the IC's can be inserted into their sockets.

There are no special setting up procedures.

A five volt power supply is required and the connections for this as well as the wiring to the circuit being protected, are made to SK3. The keypad and S1 should now be connected to SK1 and SK2.

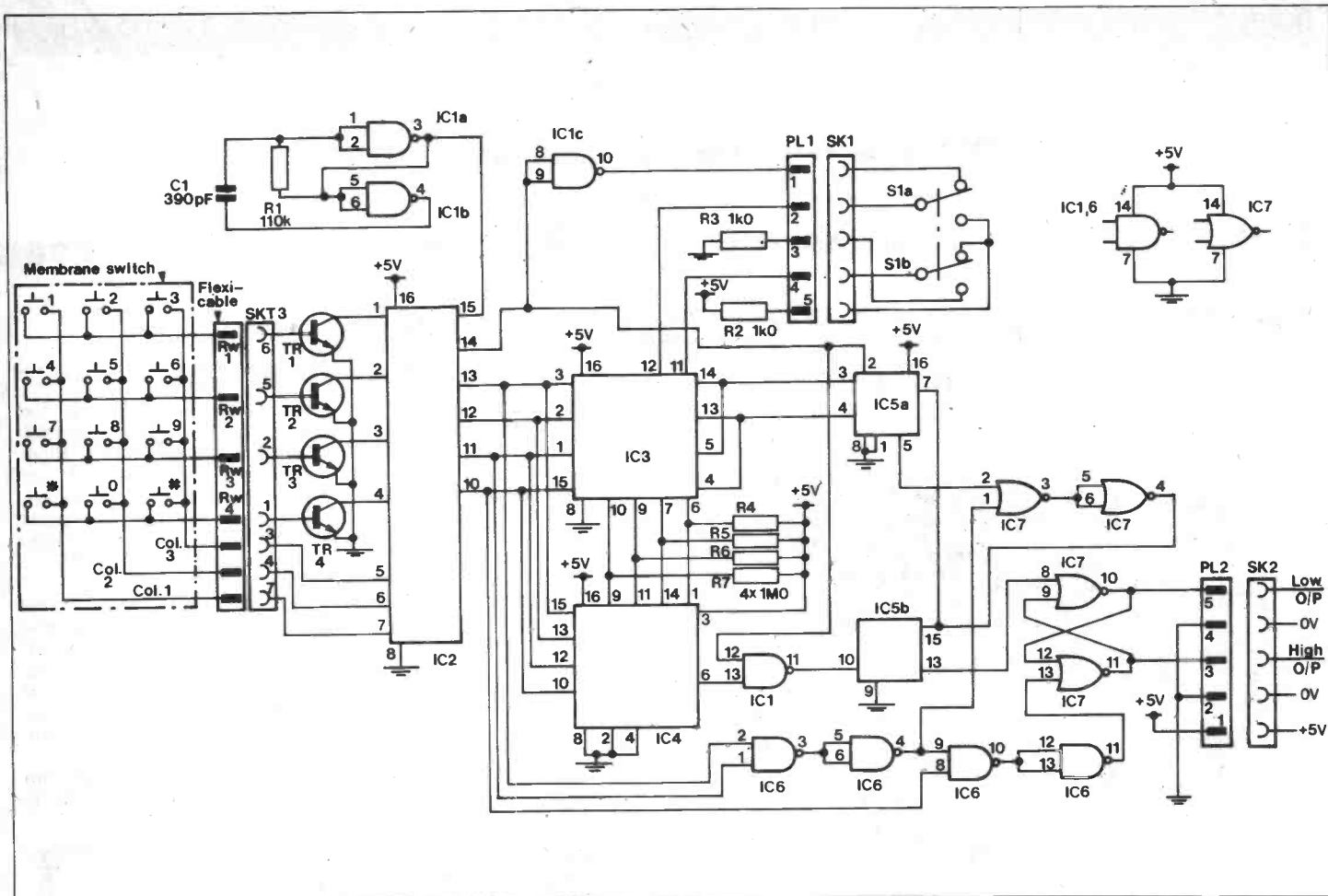


Figure 1. Codelock circuit diagram.

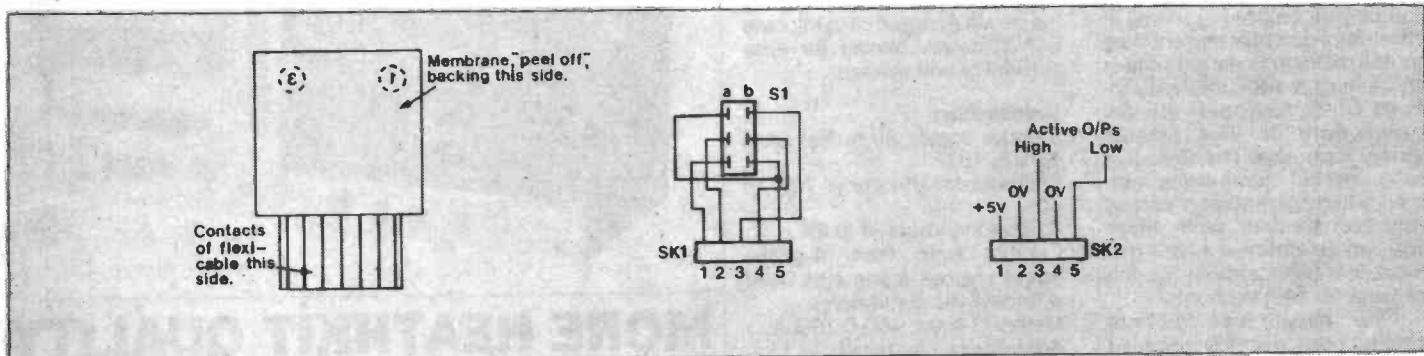


Figure 2. Pinouts.

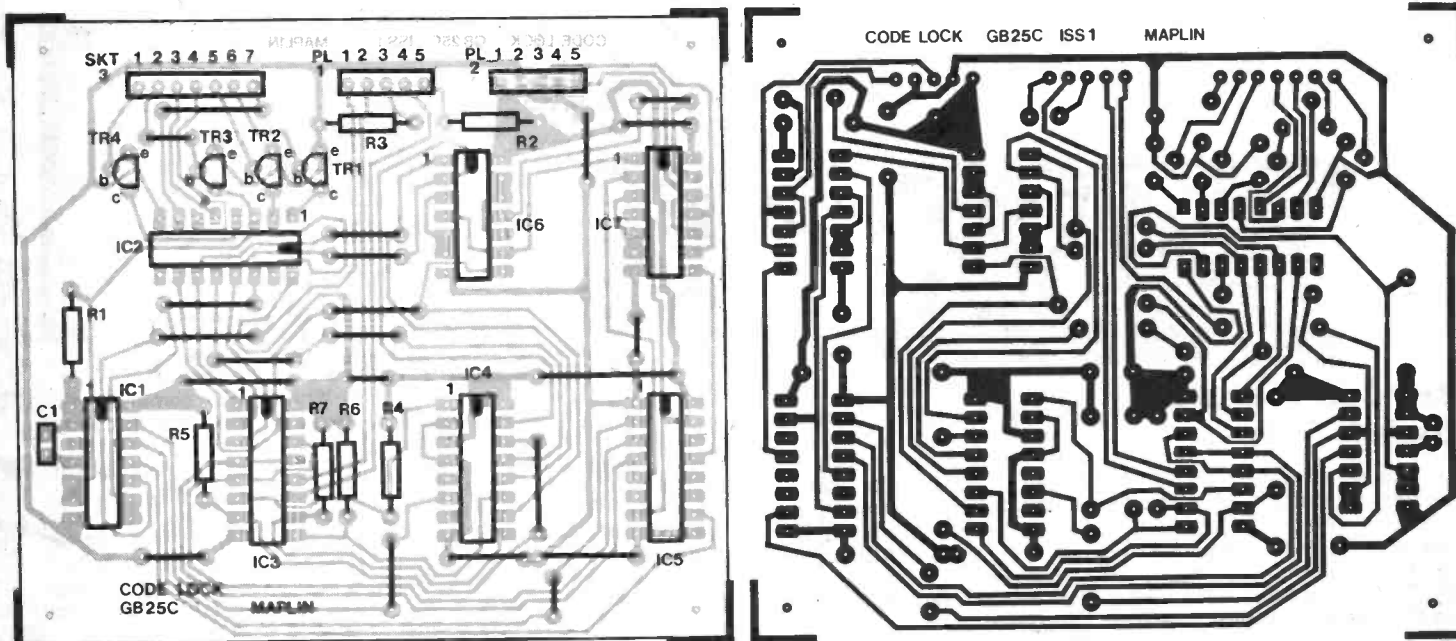



Figure 3. PCB layout.

# Heathkit

This month: Car projects, more training courses, more test gear.

## FASCINATING CAR PROJECTS

### Exhaust Gas Analyser

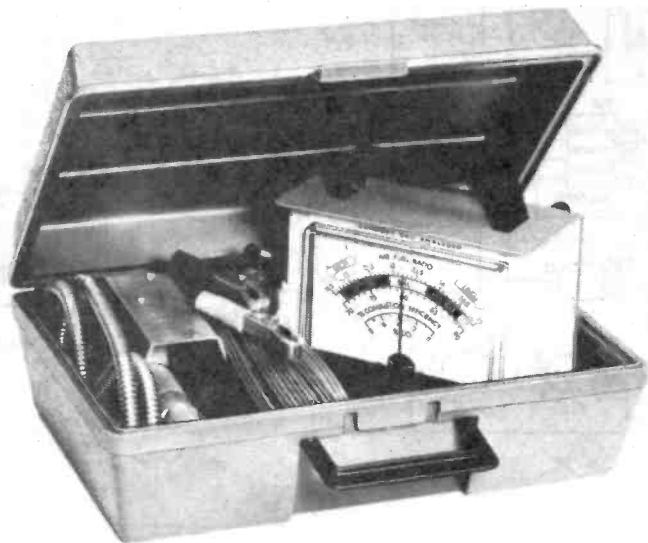

Possibly the best way to guarantee your engine is running at maximum potential and emitting as few pollutants as possible is by testing it with this easy-to-build kit. By measuring thermal conductivity of your exhaust gases, it can show the air-to-fuel ratio, overall combustion efficiency and percentage of carbon monoxide present. From these you can determine if a car's fuel mixture is unnecessarily too rich or weak for best economy.

The easy-to-read 114mm colour-coded meter is designed to hang on a partly open window or stand upright without marring paint finishes. The removable sensor/probe assembly uses a flexible stainless steel tube for safe conduction of all gaseous

material. The instrument is housed in a rugged carrying case with foldaway handle for easy portability and storage.

#### Specification

3 meter scales: Air to fuel ratio: 11.5 to 15.0.

Combustion efficiency: 70% to 90%.

Carbon monoxide: 0 to 8%.

Exhaust type: From 4-stroke petrol engines (cannot be used with catalytic converters).

Meter: 114mm, 100-0-100uA.

Accessories supplied: 2.13m battery cord; 6.4m sensor cord;

762mm exhaust flexible tube.

Power requirement: 6V or 12V car battery at 150mA.

Order As **HK31J (Exhaust**

**Analyser) Price £119.95**

### Low-Cost Charging System Tester

This easy-to-use, lightweight, portable instrument will check-out your car's charging system components with three quick tests. The tester will show you if the battery has sufficient charge to start the engine, if the battery is being charged by the alternator, if the voltage regulator is

faulty and if the alternator stator windings and rectifier diodes are functioning properly. The tester may be used with cars with a negative chassis, 12V charging system that has an alternator or any 12V, negative ground charging system that employs a 3-phase alternator using six rectifier diodes. Size 140 x 64 x 19mm.

Order As **HK29G (Charge System Tester) Price £24.95**

## Professional Ignition Analyser


Designed for the hobbyist yet perfect for the professional garage, this superb kit assures you of a precision tune-up every time. Rock steady parade patterns are made possible by the latest design in inductive pickup circuitry and switch selection of 4, 6 or 8 cylinders. Dwell measurements are indicated on the big 200mm (8in.) meter.

The unit has two voltage ranges, 0 to 2V for corroded connections and points measurements and 0 to 20V for battery condition and general distribution checks. Cylinder selection buttons can be pushed in multiple numbers so that


banks of cylinders can be shorted for carburettor balance and for display of one or more cylinders. Both parade and superimposed displays of primary or secondary waveforms with 10:1 and 2:1 trace expansion are available on the 305mm (12in.) display.

Rugged high-temperature oil and petrol resistant neoprene cables provide easy, positive connections to engine. For use with 4, 6 or 8 cylinder 4-stroke or 2-rotor Wankel engines and standard, transistorised or CD ignition systems.

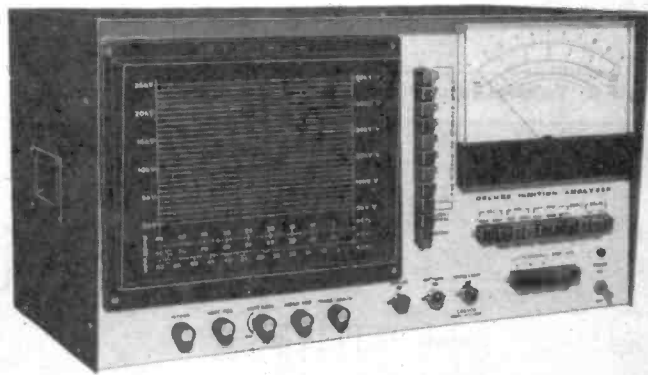Order As **HK30H (Prof Ignition Analyser) Price £549.95**


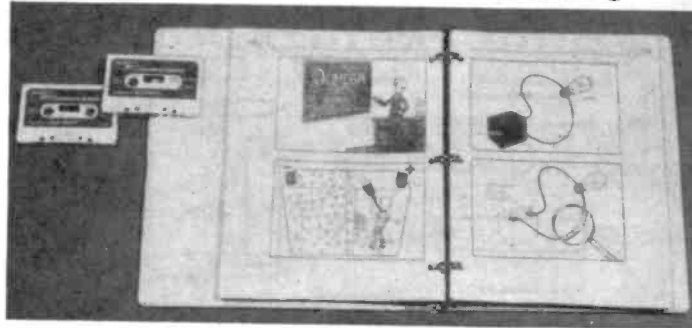
## MORE HEATHKIT QUALITY TRAINING COURSES



### BASIC ELECTRICITY COURSE

No technical background is required for this course which uses audio-visual teaching methods to introduce you to electricity. A programmed-instruction text, enhanced by clear visuals and two audio cassettes, teaches you each concept in an easy to follow sequence to build a solid foundation. A specially written workbook reinforces the learning process.

When you complete the course you will know the basics: Ohm's law, series and parallel circuits, electromagnetism, direct and alternating current, generators, motors and basic meter operation. This course serves as a valuable introduction to the Heathkit Basic Electronics series (described in our last issue).

Order As **HK32K (Basic Electricity) Price £34.95**

Maplin Magazine September 1983




## HEATHKIT

### An Introduction To Microprocessors EC6800

This course requires no previous knowledge and shows you how microprocessors operate, number systems and codes and computer arithmetic and microprocessor programming. The course is divided into six concise self-instruction units with detailed illustrations.

A typical microprocessor is described in the final units and programming experiments placed throughout the text assist your understanding.

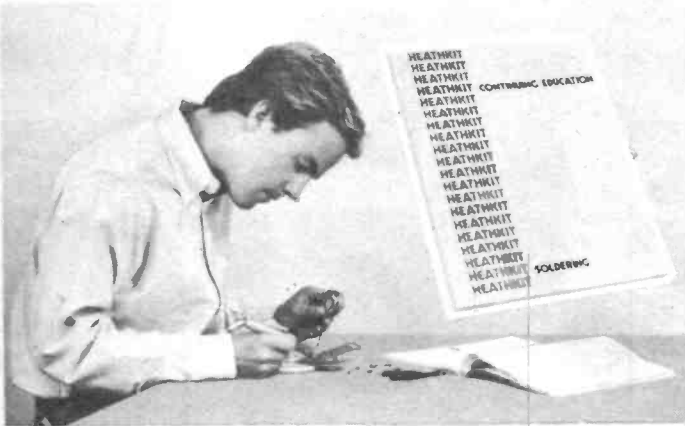
Order As **HK36P (Intro To Micros)** Price £34.95


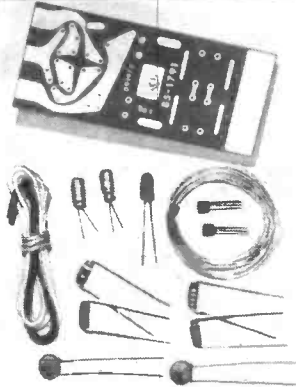
### Soldering Course

With 95% of all returned kits found to be faulty due to poor soldering, here's a course that could benefit many hobbyists. Using the proven programmed instruction format, the step-by-step text begins with mechanical connection and progresses through tinning, temperature control, different types of solder etc. A practice kit complete with circuit board, components and solder is provided for construction of a two transistor light oscillator. Soldering iron and tools are not included.

Order As **HK33L (Soldering Course)** Price £19.95



### Trainer For Intro to Micros Course

For use with the course described above, this trainer, a mini digital computer has an 8-bit parallel NMOS bus-orientated central processing unit. You can access memory locations, enter programs, single-step through programs and alter memory.

Order As **HK37S (Trainer For EC6800)** Price £99.95




## TWO SUPERB TEST GEAR KITS
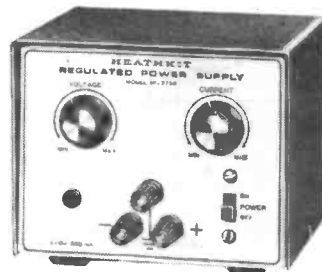
### RCL Bridge

A very useful power source for the test-bench. The unit has a continuously variable output voltage from 1V to 15V DC at up to 500mA and features 500mV line and 50mV load regulation. The "floating ground" system enables the supply to furnish positive or negative output voltages.

The programming terminals on the rear of the cabinet enable you to use an AC or DC voltage from another source to control the output voltage of this power




supply. The unit has fully adjustable current limiting. Size 146 x 140 x 110mm.

Order As **HK35Q (15V Regulated Supply)** Price £49.95
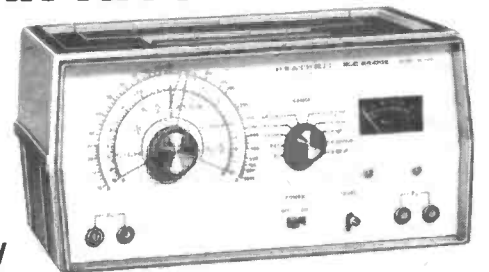
### 1V to 15V Regulated Power Supply

This quality kit allows you to measure capacitance from 10pF to 10uF, inductance from 10uH to 10H and resistance from 10 to 10M. Oscillator frequencies of 1kHz, 10kHz and 100kHz (or



external source) are provided. Provided with a rugged moulded cabinet and component clips. Require two 9V batteries.

Order As **HK34M (RCL Bridge)** Price £54.95

### NEW SOFTWARE FROM ATARI

Available now:

- KF16S** Qix (16K Cart) £29.95
- KF19V** E.T. Phone Home (16K Cart) £29.95
- KT22Y** Donkey Kong (16K Cart) £29.95
- KF18U** Atariwriter (16K Cart) £59.95
- KT23A** Biorhythm (8K Cass) £14.95
- KT24B** Timewise (32K Disk) £22.95
- KF10L** Defender (16K Cart) £29.95
- KF11M** Galaxian (16K Cart) £29.95
- KF52G** Home Filing Manager (16K Disk) £34.95

Due for release in August:

- KT25C** Eastern Front - 1941 (16K Cart) £29.95
- KF47B** Juggles Rainbow (16K Cass) £22.95
- KF48C** Juggles Rainbow (16K Disk) £22.95
- KF49D** Juggles House (16K Cass) £22.95
- KF50E** Juggles House (16K Disk) £22.95
- KF51F** Speed Reading (16K Cass) £59.95
- KT26D** Mickey In The Great Outdoors (16K Cass) £22.95
- KT27E** Mickey In The Great Outdoors (32K Disk) £22.95
- KT28F** Ms. Pac-Man (16K Cart) £29.95
- KT29G** Tennis (16K Cart) £29.95
- KT30H** Logo (16K Cart) £59.95
- KT31J** Family Finances (32K Disk) £TBA



Due for release in September:

- KT32K** Microsoft BASIC II (16K Cart) £TBA
- KT33L** Donkey Kong Jr. (16K Cart) £29.95
- KT34M** Pengo (16K Cart) £29.95
- KT35Q** Pole Position (16K Cart) £29.95
- KT36P** Robotron (16K Cart) £29.95
- KT37S** Peter Pan (16K Cass) £22.95
- KT38R** Peter Pan (32K Disk) £22.95
- KT39N** Atari Music I (16K Cass) £TBA
- KT40T** Atari Music I (32K Disk) £TBA


Due for release in October:

- KT41U** Atari Music II (16K Cass) £TBA
- KT42V** Atari Music II (32K Disk) £TBA
- KT43W** Joust (16K Cart) £29.95
- KT44X** The Learning Co. (48K Disk) £TBA
- KT45Y** Alice In Wonderland (16K Cass) £22.95
- KT46A** Alice in Wonderland (32K Disk) £22.95

Due for release in November:

- KT47B** Soccer (16K Cart) £29.95
- KT48C** Millipede (16K Cart) £29.95

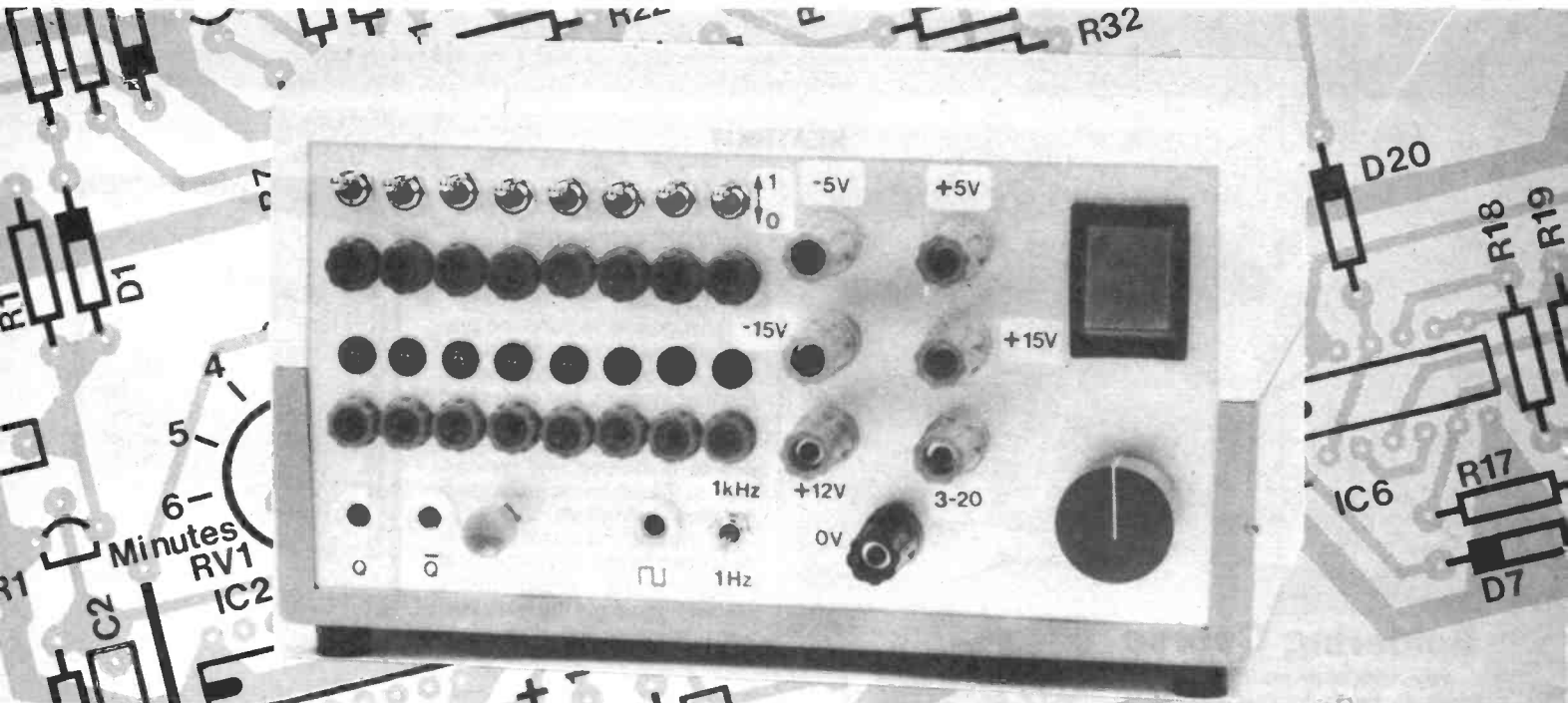Please note that the above represents the best information we have available from Atari (UK) Ltd. at the time of going to press, but delivery dates and prices may change, so please check with us before ordering.



# The Maplin MINILAB

by Graham Dixey C.Eng., M.I.E.R.E.

## Introduction

The idea for 'Minilab' developed from the need, or desire, to test and experiment with a wide range of digital and linear circuits. This usually necessitates a variety of different supply voltages. For example, when experimenting with op-amps, a dual 15V supply is needed; TTL digital circuits require a +5V supply and some other digital circuits need +12V and -5V e.g. microprocessors and related chips. An infinite variety of linear circuits exist that need unspecified voltages, but usually they are in the range 0 to +20V. The fixed voltages mentioned need to be held within close limits while the same is true of the variable supply once it has been set to a given value; in other words, regulated supplies are essential.

Before the advent of 'chip regulators' such a design to meet all of the foregoing requirements simultaneously would have been rather complex. The general availability of chip regulators that cover a wide range of voltages and current ratings e.g. 7805 (+5V, 1A) or 79L05 (-5V, 100mA) make design and construction simple — there are few external components. The L200 variable voltage regulator is a boon since a very simple variable voltage stabilised supply with current limit facility can now be built at very low cost. In this design the variable voltage supply can deliver a nominal +3 to +20V at 0.45A, though you may well get up to 24V out, and if you want more current, the regulator can give you up to 2A; however, you will have to reduce R4 to about 0.25 ohms and this will also assume that the other outputs are not loaded at the same time, since the

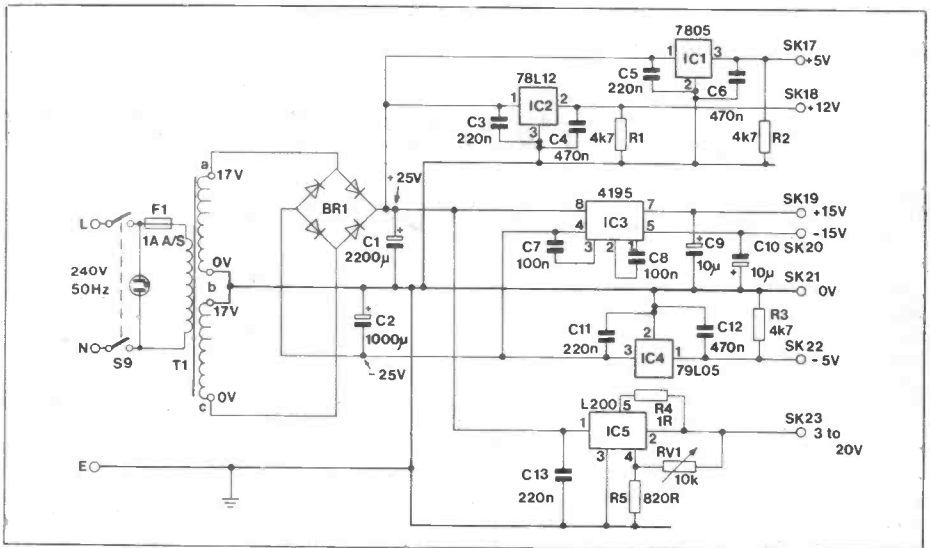


Figure 1. Power supplies.

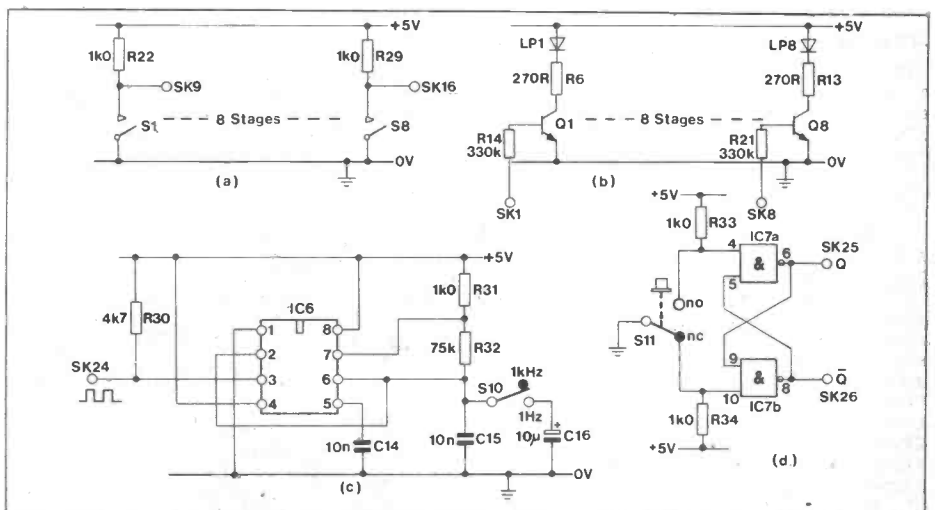


Figure 2. TTL circuits a. TTL level switches b. TTL level indicator c. 1Hz/1kHz TTL oscillator d. de-bounced TTL switch.


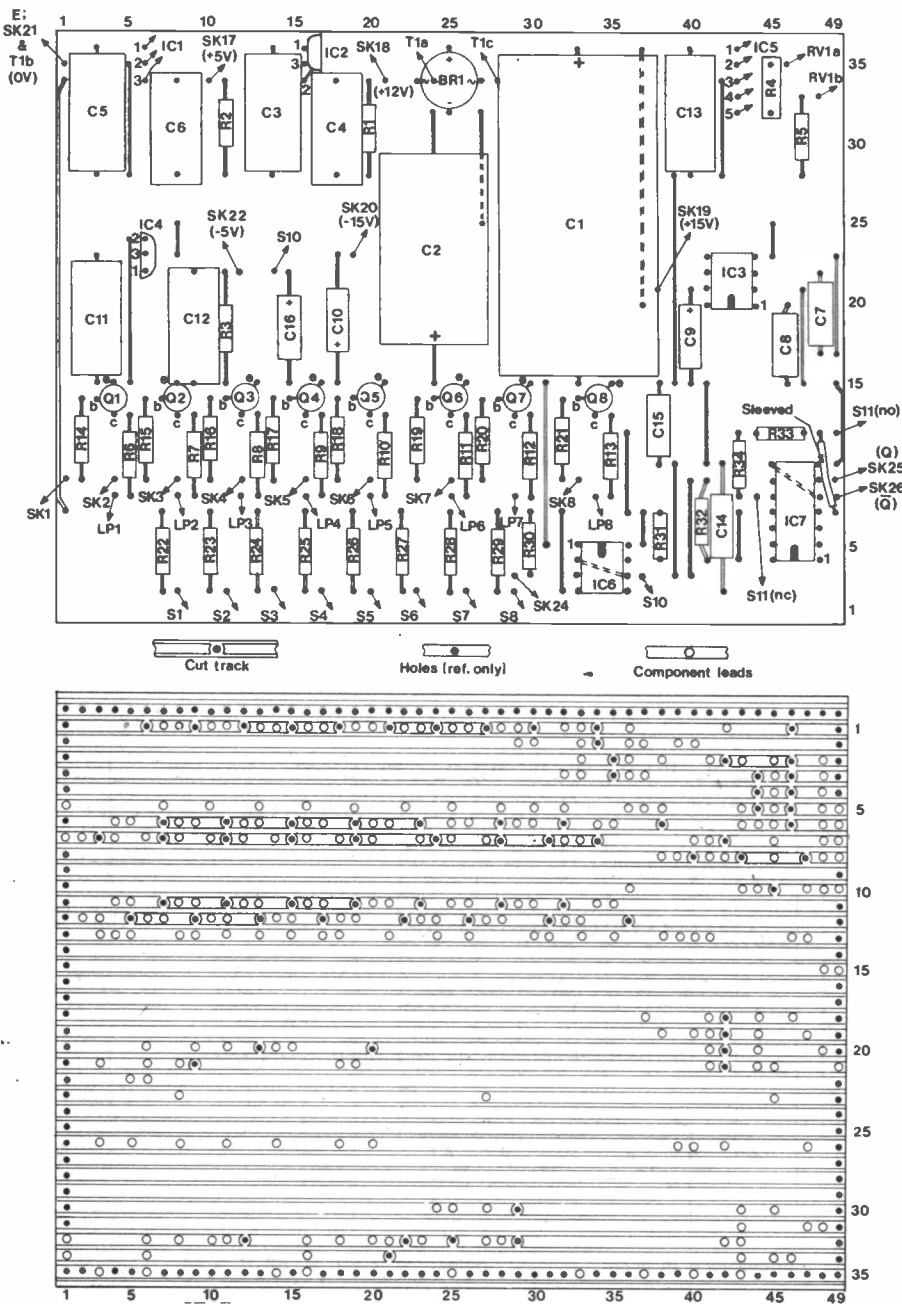


Figure 3. Circuit board details.

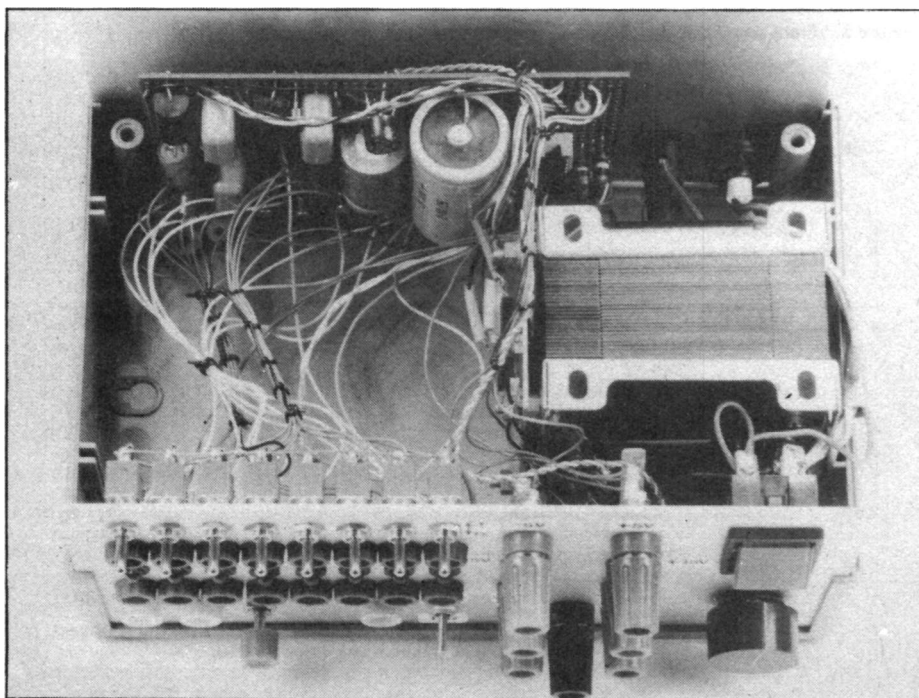

limiting factor is the transformer and rectifier, both of which have a rating of 2A.

While a multichannel power supply is useful in its own right, I thought it a good idea to incorporate a few extra, useful but simply provided facilities at the same time.

As a start, there is a set of switches and related sockets that allow the setting-up of eight independent logic levels as inputs to any circuit or system e.g. as variables A, B, C . . . X, Y, Z to a logic gate circuit; or as an 8-bit input to the input/output port of a micro-computer.

Along similar lines is the set of LEDs and associated sockets that will monitor logic levels, whether in a TTL gate circuit, at the outputs of a counter or shift register, or at a microcomputer's input/output port.

In order to study counter or shift register operation a TTL clock input is required. A 1Hz/1kHz square-wave generator provides this facility but there is also a 'debounced' switch so that the operation of such circuits can be observed 'pulse at a time'.

All of the above facilities are shown on the circuits of Figures 1 and 2.

## Construction and Testing

As good a starting point as any is the circuit board, which is 0.1" pitch Veroboard, the actual matrix being 49 holes by 36 holes. Use the lower diagram of Figure 3 to identify the 'cut holes' and deal with these first. Then, returning to the face of the board, identify the position of all wire links; fit these (use 22 s.w.g. or 24 s.w.g. T.C.W.), not forgetting those short links beneath the sockets of IC6 and IC7; also noting the sleeved link adjacent to IC7. After this the component order is not too important; a suggested one is: IC sockets, resistors, capacitors, bridge rectifier, transistors and, for the moment, nothing else. Stop now and check that what you have done is correct. What you do next depends upon your level of self-confidence. If you wish to proceed with caution you could, for example, follow the following plan.

First, wire the two transformer secondaries in series (link shown as T1b in Figure 1). Then connect the other two secondary connections (T1a and T1c) to the bridge rectifier (Figure 3) and fit a temporary mains lead and plug. Observing due precautions with regard to personal safety, plug in and check with a DC voltmeter that you have 25V across each of the reservoir capacitors C1 and C2, noting the polarities of these voltages. If these measure correctly then at least the transformer, rectifier and smoothing circuit is alright. Now disconnect from the mains and hook up the connections to IC1 (the heatsink doesn't matter at the moment). Plug in again and check that you have +5V where you should have on the board. Repeat this pro-

cedure for IC2-IC5 in turn until you have all the supplies working; for IC5 you will have to hook up temporary connections to the 10k pot. If all is well you can test the transistor switches Q1 to Q8 by temporarily fitting an LED from each of R6-13 to +5V in turn and each time, using an insulated wire link, touching +5V onto the socket side of each of the base resistors to check whether the LED lights or not.

Concerning the hardware, a standard Verobox is suggested in which there is ample room for the transformer, heatsink and circuit board. The transformer is mounted at the extreme right hand end of the box, long axis vertical and with the mains tappings adjacent to the mains switch. The heatsink (Figure 4) is mounted vertically on the free end of the transformer with four screws, nuts and washers. The heatsink must be spaced off from the transformer frame to prevent the screws which mount IC1 and IC5 from touching the transformer laminations; this is easily done with a small tubular spacer or simply an extra nut behind the heatsink. These two ICs must be mounted on the heatsink by means of a TO220 mounting kit for each (mica washer and plastic bush) to insulate them from each other and from the heatsink itself (N.B. these mounting kits are termed 'TO66 plastic' in the Maplin catalogue and the appropriate part number is given in the parts list). The circuit board can be mounted at the rear of the box using a small angle bracket at each end. The redundant holes in ROW 1 can be opened up where required and there should be no risk of short circuits to any components on ROW 2 if the brackets are fitted right at the ends of the board. If the components face forward the board can sit quite close to the back panel and wiring from the board to the front panel can be carried out without any undue difficulty. Naturally these wires (all identified in Figure 3) are connected to the circuit board before it is mounted in place; estimate a little more for the length of

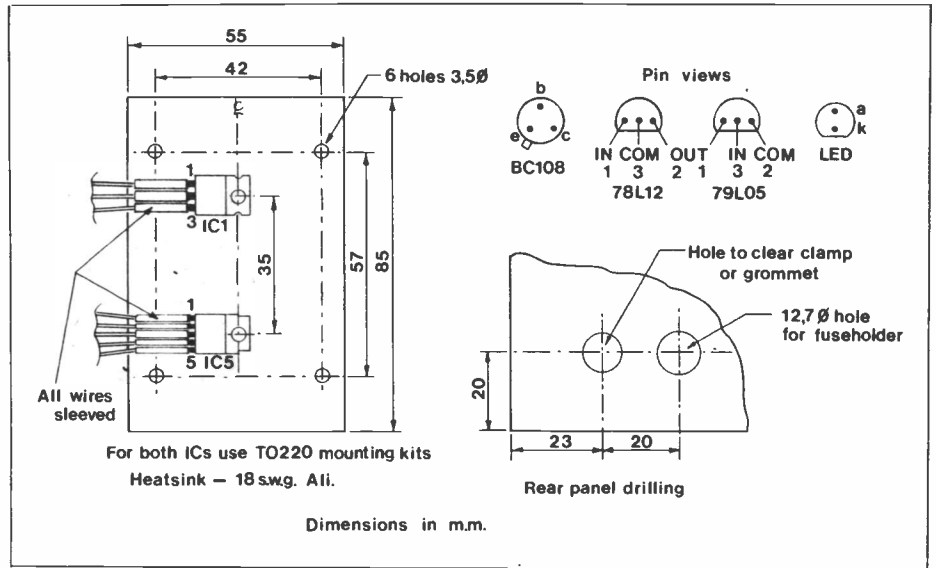


Figure 4. Heatsink, rear panel drilling and pin-outs.

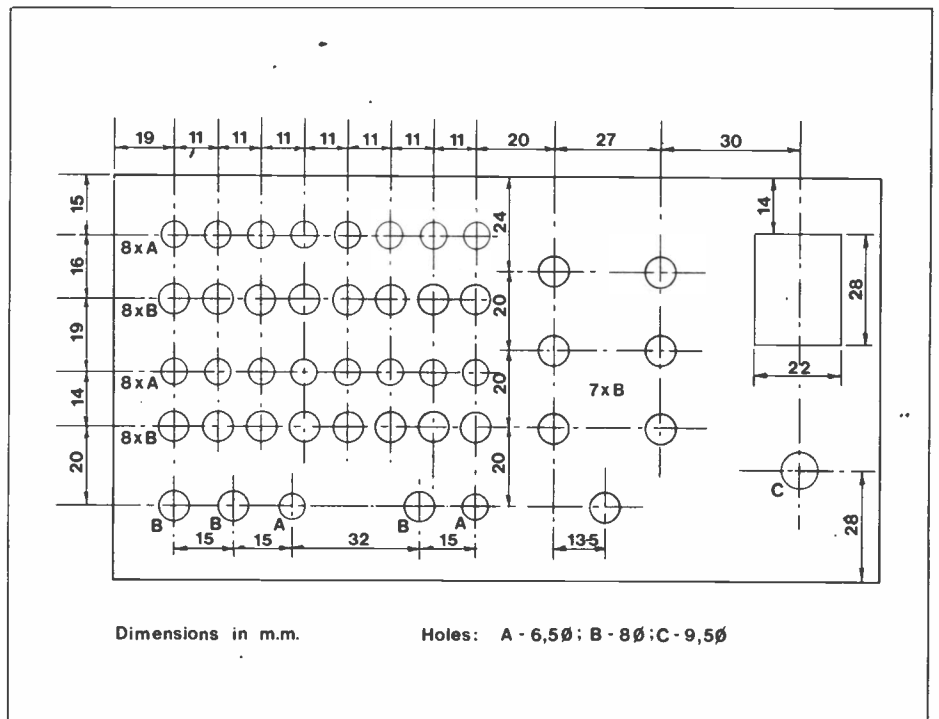


Figure 5. Front panel drilling.

### PARTS LIST FOR MINILAB

Resistors — All ½W 5% carbon unless specified

R1,2,3,30 4k7 4 off (S4K7)

R4 (3W wirewound) 1R (W1R) — (S820R)

R5 820R (S270R)

R6-13 270R 8 off (S330K)

R14-21 330k 8 off (S1K)

R22-29,31,33,34 1k0 11 off (M75K)

R32 (metal film 0.4W) 75k (FW02C)

RV1 10k linear pot.

Capacitors

C1 2200uF 40V elect. (FB91Y)

C2 1000uF 25V elect. (FB83E)

C3,5,11,13 220nF polyester 4 off (BX78K)

C4,6,12 470nF polyester 3 off (BX80B)

C7,8 100nF polyester 2 off (BX76H)

C9,10,16 10uF 25V elect. 3 off (FB22Y)

C14,15 10nF polyester 2 off (BX70M)

Semiconductors

Q1-Q8 BC108 8 off (QB32K)

IC1 7805 (QL31J)

IC2 78L12 (WQ77J)

IC3 4195 (XX02C)

IC4 79L05 (WQ85J)

IC5

IC6

IC7

BR1

LP1-8

Miscellaneous

T1

S1-8,10

S9

S11

SK1-8

SK9-16

SK17,18,19,23

SK20,22

SK21

SK24

SK25,26

F1

L200

555

7400

W01

LED

Clip for above

Transformer 0-17V, 0-17V @ 2A

Case (Verobox)

Sub. min. toggle switch

Mains switch DPST (with neon)

Min. push-button switch SPDT

10mm cap green

4mm socket — green

4mm socket — brown

4mm terminal — red

4mm terminal — blue

4mm terminal — black

4mm socket — yellow

4mm socket — white

DIL socket 8-pin

DIL socket 14-pin

Mounting kit TO220

Fuseholder 20mm

1A antisurge fuse

Veroboard 10347

(YY74R)

(QH66W)

(QX37S)

(QL38R)

(WL27E)

(YY40T)

(WB22Y)

(LL07H)

(FH00A)

(YR70M)

(BK68Y)

(BK71N)

(HF72P)

(HF71N)

(HF07H)

(HF03D)

(HF02C)

(HF75S)

(HF74R)

(BL17T)

(BL18U)

(WR23A)

(RX96E)

(WR19V)

(FL09K)


A complete kit of all parts, excluding the case, is available for this project. Order As LK09K (Minilab kit). Price £32.50.

each wire than is actually needed. As a tip to make life that bit easier, the two wires to the pot. are best wired to the pot. first and then to the circuit board, since the pot. tends to be obscured by the transformer once the front panel has been dropped into place.

There is little comment to make on the front panel wiring except to point out the bus-bars used to common the anodes of the LEDs (and taken to the +5V terminal SK17) and a similar bus-bar on switches S1-S8, which is taken to the 0V terminal SK21. Figure 6 shows all of these details and identifies the position of all front panel components. The front panel drilling details appear on Figure 5.


The rear panel has only two holes (details in Figure 4), which are for the mains cable clamp or grommet and the fuseholder. This is best drilled and put aside until all else is finished. This simply means wiring from the circuit board to the front panel, dropping the rear panel into place, completing the mains wiring via fuse F1 and testing the complete 'Minilab' to see that the following facilities exist:

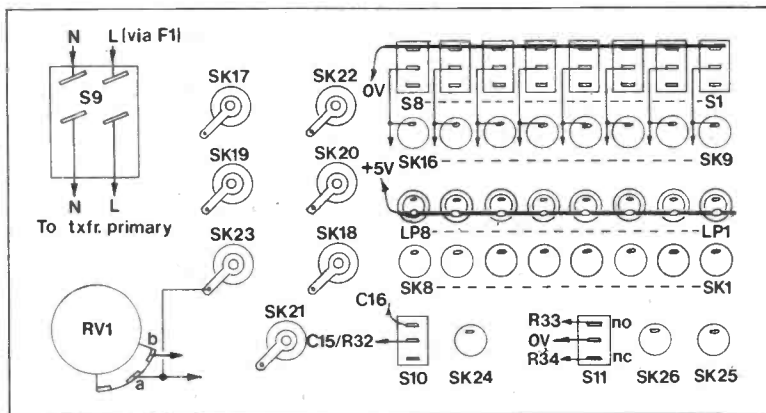- +5V @ 1A      Eight TTL outputs
- +5V @ 100mA    Eight TTL inputs
- +12V @ 100mA    1Hz/1kHz TTL oscillator
- +15V @ 50mA    One bounce-free, TTL pair of complementary outputs (Q and Q̄)
- +3V to +20V @ 450mA



Busbars shown are 22 sw.g. T.C.W.

Figure 6. Front panel rear view — component identification.

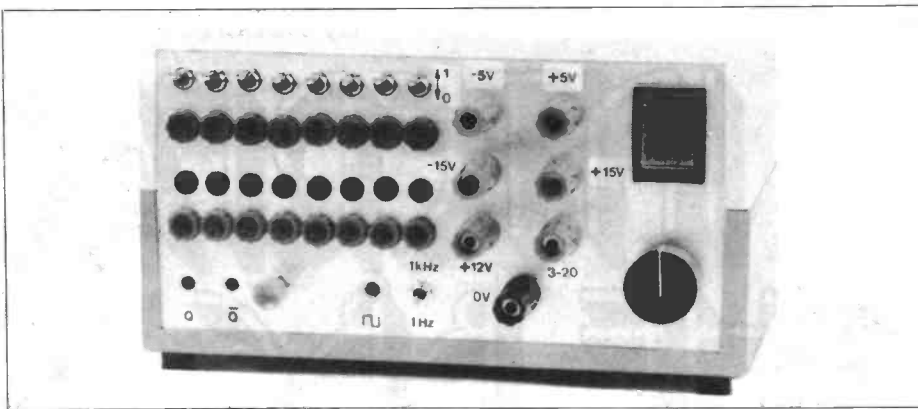


## CODELOCK *Continued from page 13*

### Application

The applications for a circuit such as this are many and varied, making it difficult to list all of the possibilities, however here are some suggestions.

First and foremost, any form of burglar alarm is an obvious candidate. Here the usual key that would be used to Arm or Disarm the system could be replaced by a Codelock, or as an even more security conscious suggestion, it could be inserted in parallel with the keyswitch, which would mean that both the key and the secret code would be required before the alarm could be deactivated.

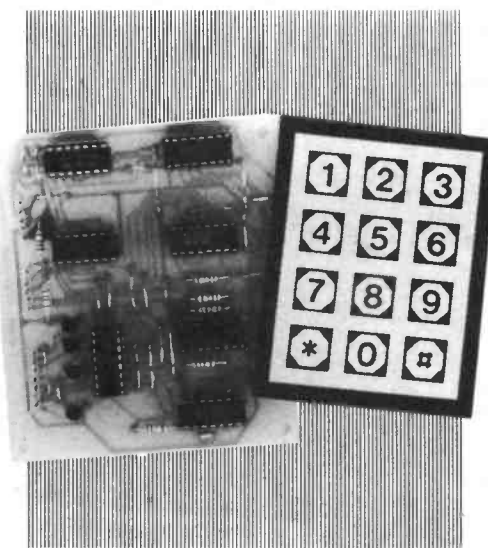The second most obvious application would be to use the Codelock in conjunction with a commercially available electric door lock. This would give



tremendous security to, say a computer room, photographic darkroom, office or any number of places where unwelcome visitors would rather be kept out.

Lastly, any device that is normally operated by means of an ordinary switch, could have a Codelock to replace the said switch, barring the devices use from those other than yourself or those to whom you have disclosed the code. In this, and indeed most applications, the output from the Codelock would have to drive a relay or some form of servo or triac to act as the mechanical part of the switch. It is because of the number of different ways in which the Codelock could be utilised, that no final drive circuitry has been included, as this would depend on how it is to be used.

## PARTS LIST CODE LOCK

Resistors: All resistors 0.4W 1% metal film unless specified.

R1	110k		(M110K)	IC5	4518BE	(QX32K)
R2,3	1kΩ	2 off	(M1K0)	IC7	4001BE	(QX01B)
R4-7	1MΩ	4 off	(M1M0)	Miscellaneous		
Capacitors:				SW1	Switch sub. min. slide	(FH35Q)
C1	390pF ceramic		(WX63T)	SK3	Membrane Switch	(BK72P)
Semiconductors				PL1,2	Flat Flex Connector	(BK73Q)
TR 1-4	BC 548	4 off	(QB73Q)	SK1,2	Minicon plug 5 way	2 off (FY93B)
IC1,6	4011BE	2 off	(QX05F)		Minicon latch housing 5 way	2 off (BH66W)
IC2	MC14419		(QY55K)		Minicon terminal	10 off (YW25C)
IC3	74LS170		(YF72P)		PC Board	(GB25C)
IC4	4063BE		(QW41U)			

A complete kit of all parts is available.  
Order As LK14Q (Code Lock kit) Price £19.98.

The BBC model B microcomputer seems to be popular with those who are interested in using a computer for control or measurement applications, and it is well suited to this type of use. It seems to have more input and output sockets than any other microcomputer currently available, including a four channel 12 bit analogue to digital converter, serial and parallel printer interfaces, an 8 bit (plus handshaking lines) user port, and the 1MHz Bus which enables additional input and output ports to be easily added. It also has a fast version of BASIC plus a built-in assembler which makes it relatively easy to use machine code when very high speed operation is essential.

A certain amount of information about interfacing the BBC micro is given in the "User Guide" provided with the machine, but some of this can be a little difficult to understand unless you are already familiar with the techniques and interface devices

used. In this article topics such as programming the user port, using the handshaking lines, and adding extra ports to the 1MHz Bus will be covered, filling in some of the detail which is absent from the "User Guide."

## User Port

Both the parallel printer and user ports are provided by a 6522 VIA (Versatile Interface Adaptor) device, and this is also used to provide the machine with its Basic "TIME" function. The two timer/counters of the 6522 are available to the user, but these can only be used in machine code programs and would not normally be used directly. In most applications the Basic "Time" command is adequate, and the direct use of the timer/counters will not therefore be considered here.


The two 8 bit ports of the 6522 (called the

"A" and "B" ports) are very similar, and each bit of both ports is individually programmable as an input or an output. However, an important point to bear in mind is that the "A" port is used to drive the parallel print output via a 74LS244 buffer. This is a tri-state buffer, but it is permanently enabled so that it operates as a straightforward TTL buffer. The printer port can therefore be used in much the same way as the user port, but only if output lines are required. The data lines of the parallel printer port cannot be used as inputs.

Writing to the appropriate register of the 6522 determines whether each data line of the "B" port is designated as an input or an output. This is called the "data direction register" and is at hex address FE62. Writing a 1 in a bit of this register causes the corresponding data line to operate as an output, and a 0 causes the corresponding data line to act as an input. For example, sending 15 (00001111 in binary) to the data direction register sets the four higher data

*by Robert Penfold*

# INTERFACING THE BBC MICRO

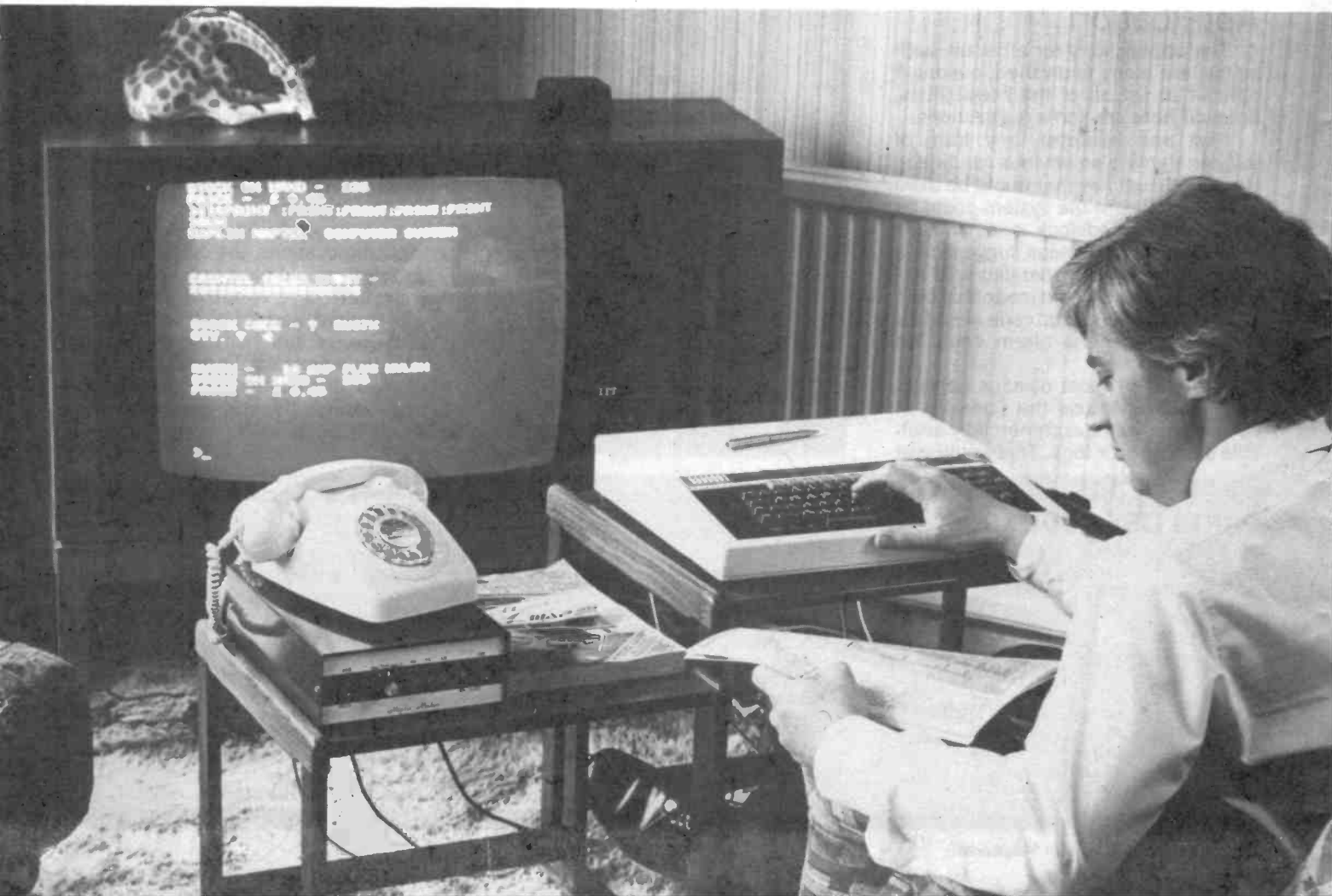

## INTERFACING THE BBC MICRO

lines (PB4 to PB7) as inputs, and the four lower lines (PB0 to PB3) as outputs.

With BBC BASIC the usual PEEK and commands are replaced by a question mark (?) which denotes that the number which follows is an address. Thus, in order to write 15 to hex address FE62 the program line would read:-

```
?&FE62 = 15
```

The "&" before the address is needed to inform the computer that the address number is in hex and not in decimal.

It is important to note that address &FE62 is the location of the data direction register and this is not the address used when reading from or writing to the user port. The relevant address for this is &FE60. As a safety measure the data direction register is set to zero at switch on so that there can be no problems if a peripheral device is feeding an input signal to the user port. If you type:-

```
PRINT ?&FE60 RETURN
```

into the computer, 255 should be printed on the screen, since pull-up resistors take the user port inputs to logic 1 if they are simply left floating. Wiring some of the lines to OV pins of the port should give a suitably modified result if the command is retyped.

If you remove the shorting wires and try typing:-

```
?&FE62 = 255 RETURN
```

```
?&FE60 = 15 RETURN
```

the data lines of the user port are all set as outputs by the first line, and the second sets PB0 to PB3 high and PB4 to PB7 low. The outputs latch, and the appropriate output states can be confirmed using a logic probe or multimeter.

In some applications it is necessary to read just one bit of the user port, or to read several bits one at a time. Strictly speaking this is not possible, but using the logic AND function it is possible to mask all but one bit. For example, suppose we wish to know if PB4 is low or high. If it is at logic 1 this line adds 16 to the number returned from the user port, and it is therefore ANDed with the number 16. For the sake of this example we will assume that the number returned from the user port is 255. The two numbers are logic ANDed bit by bit, as shown below, giving a logic 1 in the binary result only if that particular column has a 1 in both the figures being ANDed (i.e. in both the first number AND the second).

```
255 11111111 user port
16   00010000 number used to mask all
      but PB4
16   00010000 answer
      If PB4 was low and the number returned
      from the user port was (say) 239 this would
      give the following result:-
239 11101111 user port
16   00010000 number used to mask all
      but PB4
0    00000000 answer
```

If you try typing into the computer:-

```
PRINT ?&FE60 AND 16 RETURN
```

the number returned should be 16. Taking PB4 and any of the other input lines to OV should return to 0 if the command is repeated.

By using the appropriate mask number it is possible to effectively read any one bit or selected bits of the user port.

### Handshake Lines

When a computer is sending data to or receiving data from a peripheral device it is often necessary to have some form of synchronisation so that data transfers are only attempted when both pieces of equipment to deal with them. It is for this purpose that handshaking lines CB1 and CB2 are



provided on the user port. CB2 can be used as an input or an output, but CB1 can only be used as an input.

Some of the ways in which these lines are used are quite complex and go beyond the scope of this article, but there are some relatively simple but useful ways in which they can be used. CB1 and CB2 are made to operate in the required manner by writing the appropriate number to the Peripheral Control Register which is at address &FE6C. An input from one of these lines gives a change in one bit of the Interrupt Flag Register which is located at address &FE6D. When CB1 is activated it sets bit 4 of the Interrupt Flag Register high, and when used as an input CB2 sets bit 3 of this register high. In other words the number returned from ?&FE6D is raised by 16 and 8 (in decimal) respectively.

CB1 is the more simple of the two handshaking lines since it only has two modes of operation, and it is controlled by one bit of the Peripheral Control Register (bit 4). CB2 has four input modes and four output modes and is controlled by three bits of this register (bits 5 to 7). The table given below summarizes the modes of CB1 and CB2.

Binary/ Decimal No.	Mode of Operation
0/0	CB1 high to low handshake input
1/16	CB1 low to high handshake input
000/0	CB2 high to low handshake input
001/32	CB2 high to low independent input
010/64	CB2 low to high handshake input
011/96	CB2 low to high independent input
100/128	CB2 high to low handshake output
101/160	CB2 high to low pulse output
110/192	CB2 constant low output
111/224	CB2 constant high output

When dealing with CB1 it is simply a matter of selecting a high to low or low to high transition to set the interrupt flag. With CB2 there are the same two options, plus the two independent modes. When using the handshake modes the relevant bits of the Interrupt Flag Register can be reset by reading from or writing to the user port, or by writing a 1 to the appropriate bit or bits of the Interrupt Flag Register (i.e. use ?&FE6D = 16 to reset the CB1 flag, ?&FE6D = 8 to reset the CB2 flag, or ?&RE6D = 24 to reset either of them). With the independent modes this second method is the only way of resetting the flags.

The simple program given below can be used to try out the CB1 and CB2 inputs.

```
10 ?&FE6C = 0
20 CLS
30 PRINT ?&FE6D
40 ?&FE6D = 24
50 TIME = 0
60 REPEAT UNTIL TIME = 100
70 GOTO 20
```

This simply prints the value of ?&FE6D and updates the reading at roughly one second intervals (the delay time set by lines 50 and 60). Line 10 sets all the control registers at zero so that both CB1 and CB2 set their respective interrupt flag registers during a transition from the high state to the low one, and they are both used in the handshake mode. By taking CB1 and (or) CB2 low the initial reading of 0 should change to 8, 16, or 24, as appropriate. However, line 40 resets the interrupt flags and the reading should soon return to zero. As the handshake mode is used, reading from the user port (by putting X = ?&FE60 at line 40, for example) should also reset the flags. By changing the number at line 10 the other input modes can be tried using this program.

The CB2 output modes are quite straightforward. In the two constant modes CB2 is set high or low as required, and is independent of the other user port lines. In the pulse mode it provides a 1us negative pulse each time data is sent to the user port, and in the handshake mode it goes low when data is sent to the user port. It can then only be reset to the high state by an active transition on CB1.

The lower four bits of the Peripheral Control Register function in the same way as bits 4 to 7, but they control lines CA1 and CA2 of the printer port. The printer port is at ?&FE61 and its Data Direction Register is at ?&FE63. The interrupt flags for CA1 and CA2 are bits 1 and 0 respectively of ?&FE6D.

### 1MHz Bus

An 8 bit user port is obviously very useful, but you may well find that more inputs or outputs are required. The most simple solution to the problem is to use the parallel printer port, but this only provides another 8 lines plus handshaking lines and the 8 data lines (as explained earlier) can only be used as outputs. The 1MHz Bus offers great scope for expansion, and some simple hardware is all that is needed to provide one or two extra input or output ports.

The circuit diagram on page 503 of the "User Guide" shows the various inputs/outputs available on the 1MHz Bus, and this includes the data bus (D0 to D7) and the lower 8 address bus lines (D0 to D7). Only the lower 8 address lines are needed as the upper 8 lines are decoded and provided in the form of lines NPGFC and NPGFD. The former pulses negative when any address in page FC is addressed, and the latter similarly pulses low for any page FD address. This gives a generous quota of 512 addresses for user hardware from ?&FC00 to ?&FDFF, although Acorn only recommend ?&FC00 to ?&FCFE for user applications. The other addresses are allocated to such things as an extra 64k of memory, a Teletext Unit, and a Prestel Unit. However, if you do not intend to add equipment of this type to the 1MHz Bus, and just require a simple input or output port, it is very easy to make these additions.

Figure 1 shows how an 8 bit input port can be added. This circuit is based on a 74LS244 octal tri-state buffer, and this must be enabled (by taking pins 1 and 19 low) each time there is a read operation to the port. The most simple way of achieving this is to simply connect these pins to NPGFC or NPGFD, but a drawback of this system is that an accidental write operation to the port would result in the MPU and the port simultaneously placing an output on to the data bus. This possibility can be eliminated by gating the read/write line and NPGFC or NPGFD so that IC1 can only be enabled during read operations (when the read/write line is high). In this circuit the necessary gating is provided by three of the 2 input NOR gates of IC2.

## INTERFACING THE BBC MICRO

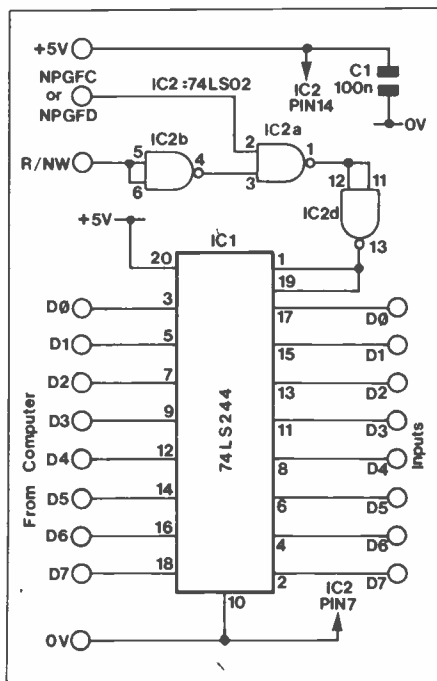


Figure 1. Adding an input port to the 1MHz Bus.

A simple output port can be added using the circuit of Figure 2. This is just a 74LS273 octal D type flip/flop which is fed from the data lines and is latched by the negative pulse from the NPGFC or NPGFD line each time a write operation is performed. As the port cannot place an output onto the data bus there is no need to gate the read/write line with the NPGFC or NPGFD line.

With both of these circuits the port will respond to any address from &FC00 to &FCFF if the NPGFC line is used, or from &FD00 to &FDFF if the NPGFD line is used. This permits only one piece of hardware per line to be used, and it is therefore better to use a more sophisticated system if further expansion is contemplated. Another limitation of these simple circuits is that they do not provide handshake lines, and there is just a negative pulse from the NPGFC or NPGFD line each time a port is written to or read from.

### 6821 PIA

A more elegant solution to additional input/output ports is to use a 6821 PIA (Peripheral Interface Adaptor) plus full decoding of A0 to A7 address lines, as shown

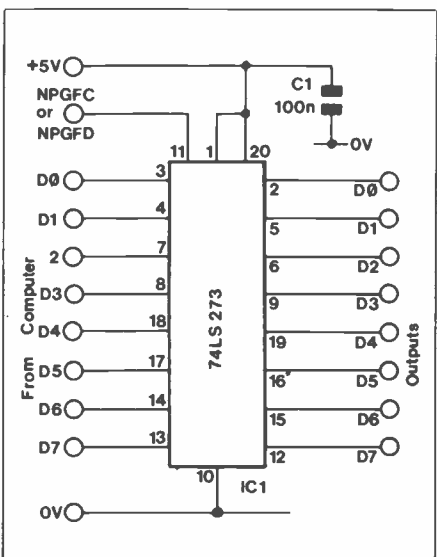


Figure 2. A simple output port for the 1MHz Bus.

in the circuit of Figure 3. This gives two 8 bit ports with each line individually programmable as an input or output. There are also two handshake lines per port.

IC1 is a 74154 (or 74LS154) 4 to 16 line decoder, and this has 16 outputs, one of which will be in the low state if the device is enabled. Which output this is depends on the binary number fed to the four address inputs of the device (A0 to A3). These inputs are fed with the A4 to A7 lines of the 1MHz Bus, and output 12 (C in hex) of IC1 is the only one which is used in this case.

IC1 has two enable inputs which must be taken low in order to permit normal operation of the device, and these are fed from the A2 and A3 lines of the 1MHz Bus. The remaining two address lines (A0 and A1) are fed to the Register Select inputs of IC2 and determine the operating mode of this device.

D1, D2, and R1 form a simple gate which gives a negative signal to the negative chip select input of IC2 when the NPGFC line is activated, and the A2 to A7 lines of the 1MHz Bus are at the correct states to operate IC1. This places IC2 at the four addresses from &FC00 to &FC3, which is within the range of addresses that Acorn recommend for user applications. This leaves all the other 508 addresses in pages &FD and &FC available for use.

The reset input of IC2 is fed from the NRST line so that the device is reset at switch-on or when the BREAK key is operated. The read/write input of IC2 is fed from the corresponding line of the 1MHz Bus so that IC2 is automatically set to the appropriate mode. The enable (E) input of the 6821 has a slightly misleading name, and this must be fed with the clock signal so that the computer and the PIA are correctly synchronised. Although the BBC micro has a 2MHz clock, this is divided by 2 to give a 1MHz clock frequency for peripheral devices, including the internal 6522 VIA, incidentally. Thus a standard 6821 can be used for IC2, and it is not necessary to employ the faster 68B21. The two interrupt request outputs of IC2 have open drain driver transistors so that they can be wired together to give an OR function. They can be connected to the interrupt request line of the 1MHz Bus, but it is only worthwhile doing this if you fully understand the use of interrupts, and actually intend to use them. Otherwise it is better to leave these outputs unconnected, so that the possibility of producing an unintentional interrupt and "crashing" the computer is eliminated.

### Using the Ports

There are six registers in the 6821; the data direction register (DDR) for port A, the port A peripheral register, the port A control register, and the equivalent three registers for port B. With the circuit only occupying four addresses it is obviously not possible to gain direct access to all six of these. It is only possible to directly access the port A and port B control registers at ?&FCC1 and ?&FCC3 respectively. These registers control access to the other four registers, control the handshake lines of their respective ports, and receive inputs from these lines.

In order to gain access to a DDR, bit 2 of the corresponding control register must be set to zero. As all the registers are reset to zero at switch-on this initially gives direct access to the port A and port B DDRs at ?&FCC0 and ?&FCC2 respectively. Use of the DDRs is much the same as for the 6522, with bits being set at 0 or 1 to set the corresponding port data lines and inputs or outputs. The reset at switch on sets all the

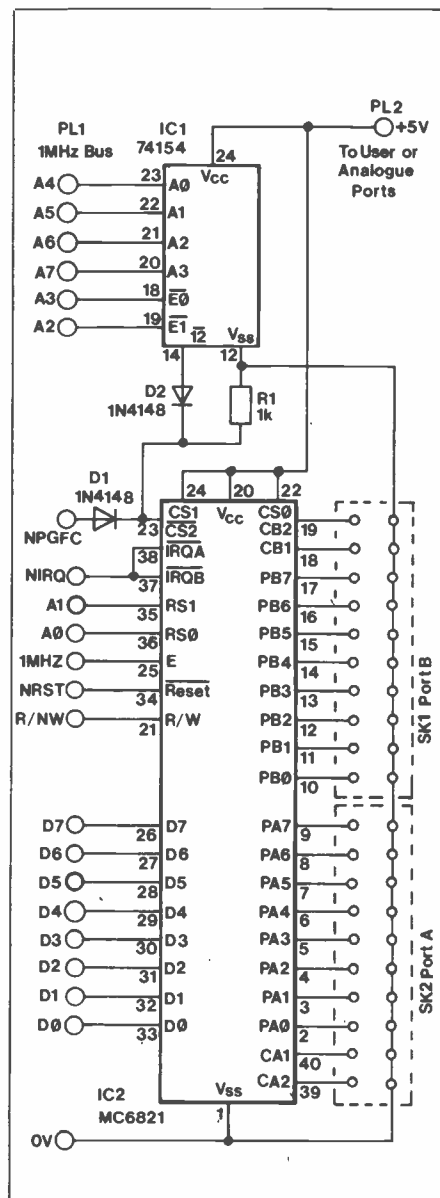


Figure 3. Two 8-bit in/out ports using a 6821 PIA.

data lines as inputs initially.

Read and write operations to the ports are performed via the peripheral registers, and bit 2 of the correct control register is set at 1 (e.g. ?&FCC1 or ?&FCC3 = 4) to give access to the A and B peripheral registers at ?&FCC0 and ?&FCC2 respectively. In other words there is both a peripheral register and a DDR at each of these addresses, and whichever of these is required is selected by setting bit 2 of the appropriate control register at 1 or 0. For example, to send the value 65 to port A the following program could be used:-

```
10 ?&FCC1 = 0 (if required, gives access to DDRA)
20 ?&FCC0 = 255 (Sets port A lines as outputs)
30 ?&FCC1 = 4 (gives access to peripheral register A)
40 ?&FCC0 = 65 (writes 65 to port A)
```

The table shown in Figure 4 should be helpful when writing programs which use the two 6821 ports. Port A and port B are slightly different, and port A, for instance, has pull-up resistors when it acts as an input, whereas port B does not. In practice there is unlikely to be any problem in using either port with TTL ICs to drive transistor switches, etc., but if in doubt the 6821 data sheet gives a substantial amount of information about the output drive capability and input requirements.

Continued on page 26



# Dragon 32

## Input/Output Ports

- ★ Two 8 bit ports with TTL and tri-state bus compatibility
- ★ Four norm/inv latched ports
- ★ Two opto and two relay switched ports
- ★ Module plugs into cartridge socket
- ★ Fully programmable from BASIC using PEEK and POKE

by Dave Goodman

Our port interface module allows the Dragon 32 to communicate with external devices such as micros, domestic electrical systems, i.e. central heating and security control, or peripheral control of the computer.

Input/Output ports consist of eight terminals, each of which can access the computer data bus. Information is passed along the bus, to or from the Central Processing Unit (CPU), by enabling the port with appropriate control signals. POKEing data in decimal form (0 to 255) will result in an eight bit binary code being written to the port, whilst PEEKing will read presented information and take action according to program requirements.


### Circuit Description

The four address codes 49152 to 49155 are used to control IC2, using R2 enable signals. Port B, PB0 to PB7 are TTL compatible with normally low outputs, while port A, PA0 to PA7 are tri-state bus compatible outputs. Port C is selected, along with port B, by enabling IC3 with IC1c. Input or output signals present at port B will operate RLA, RLB via IC3 A,B; the dual opto isolator IC5 via IC3c,d, and enable the four bit latch IC4.

PC4 to PC7 Q outputs are normally high, and Q are normally low (OV). D1 to D8 buffer port C from port B, making it write only and accessible either from the CPU or externally with +5V to 0V signal levels.
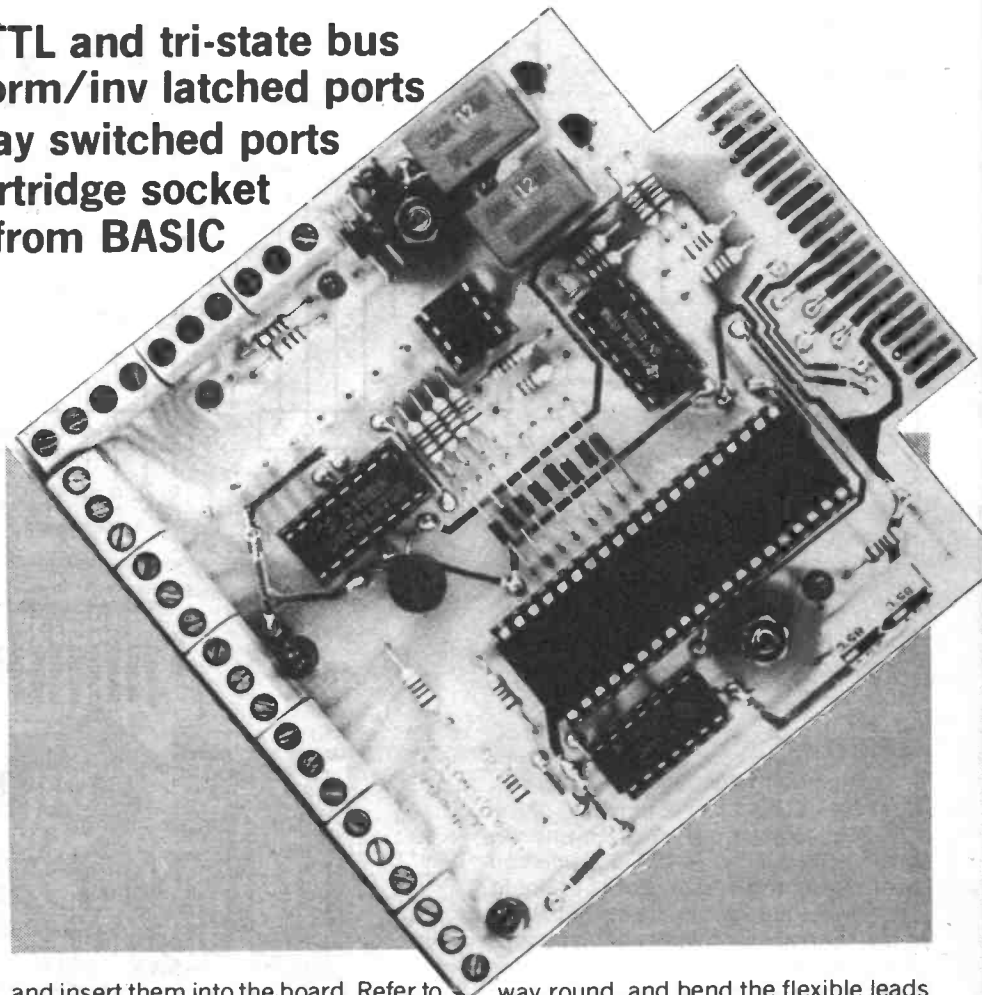
### Construction

Insert 32 track pins from side two, through the holes marked with a circle. Solder these to both sides of the PCB. Bend all the leads of the 18 resistors, September 1983 Maplin Magazine




and insert them into the board. Refer to the parts list for values, and if using 5 band 1% resistors note that colour coding begins at the end opposite to that of the solitary brown band. Fit D1 to D8. These diodes are usually blue in colour, with a black band at one end. This band must be aligned with the white band legend on the PCB. Fit diodes D9 and D10. Although they are larger in size and black in colour the band rule still applies. Capacitors C1 to C4 may now be inserted. C1 and 2 are tantalum types with a + sign printed on the body. Fit the lead closest to this through the hole marked + on the PCB. C4 has a - sign, not a + sign. Take this into consideration before you fit it. All 5 IC sockets can now be fitted, along with TR1 and TR2.

It is advisable, at this stage, to solder all fitted components and remove excess leads before continuing further. Insert both relays. They will only fit one

way round, and bend the flexible leads over each pad to secure. LEDs 1 and 2 are the larger LEDs, and 3 and 4 the smaller ones. These can all now be fitted. Each cathode (k) is recognised either by the shorter of the leads, or by a flat section on the body skirting.

Place 6 of the three way terminals in positions PA0 to PA7 and PB0 to PB7. The remaining 2 three way terminals to relay port PC0 and PC1. The four way terminal is fitted to PC2,3 position. Check each terminal faces the outside edge of the PCB before soldering, then insert the 8 vero pins in positions PC4 to PC7. Solder, trim, and inspect your work, then fit all 5 ICs.

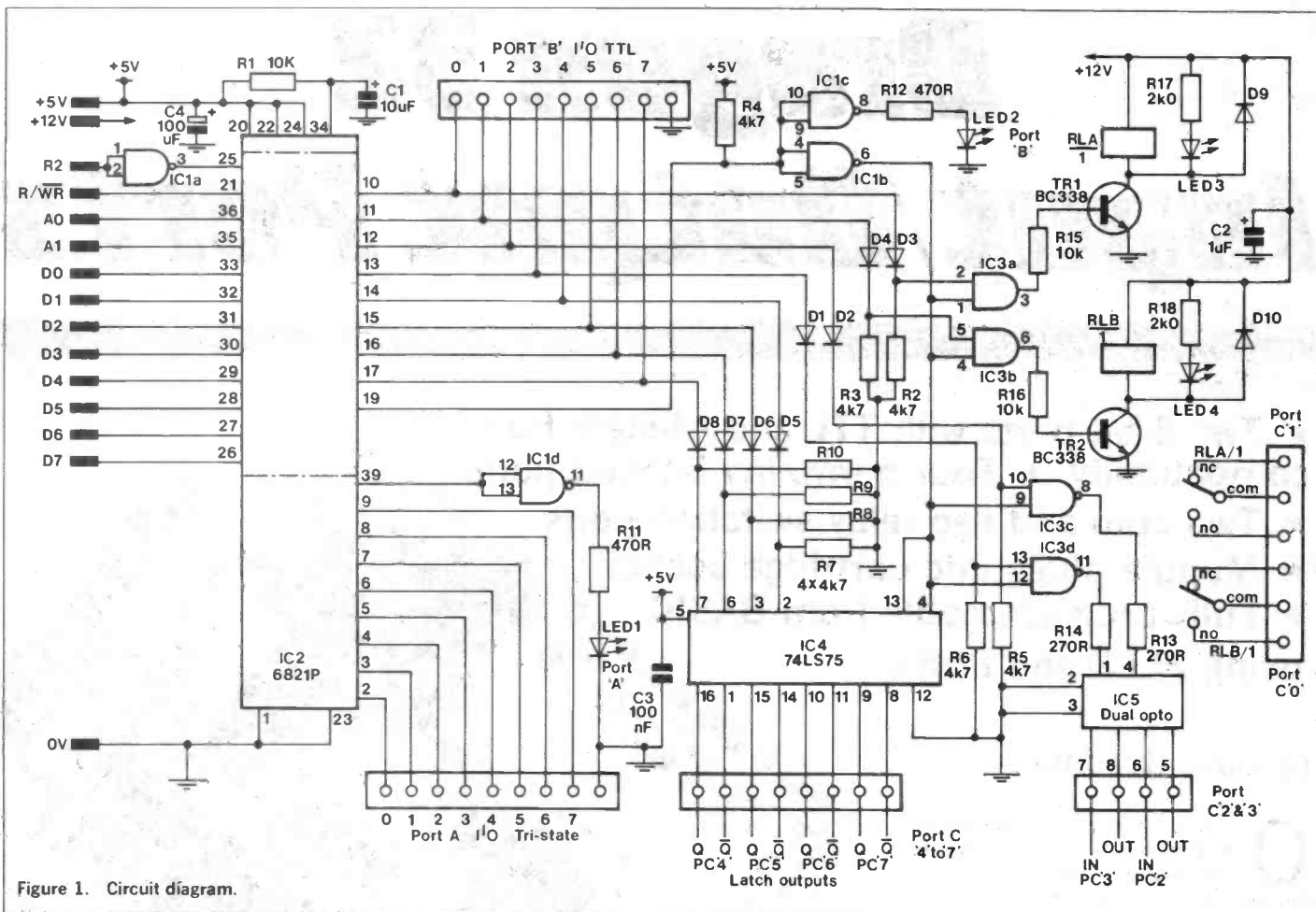Two rubber feet, bolts and nuts can be fitted to side 1 of the PCB, through the 4BA holes drilled for this purpose. They have been included to prevent wobble and excess strain on the edge connector, which could result in lost data or worse. Provided that all instruc-



tions have been carefully followed and the module has been correctly built, plug it into the cartridge socket, with component side 2 upwards.

## Testing

With a voltmeter set to read 5V DC, connect the negative lead to one of the 0V terminals on port A or B, and the positive lead to pin 14 of IC1. Switch on the Dragon, and a reading of +5V should show that the supplies are correct. Wait a few seconds for the display to appear and confirm that all is well so far. If this does not happen, switch off immediately and remove the module, check that the computer is functioning correctly.

Type POKe 49155, 48 ENTER and LED 2 will operate. Type POKe 49153, 32 ENTER and LED 1 will operate. POKe either of these addresses with 0 to extinguish the LEDs. With all four LEDs off, type POKe 49155,52:POKe49154,1 ENTER. LEDs 2 and 3 will operate, along with RLA.

Type POKe 49154,2 ENTER. LED 3 will go out and LED 4 will operate, RLA release and RLB operate. To check that both relays are working, use a meter set to ohms x 1 between COMM and NO or NC on port C, PC0 and PC1. RLA contacts are at PC0 and RLB contacts at PC1.

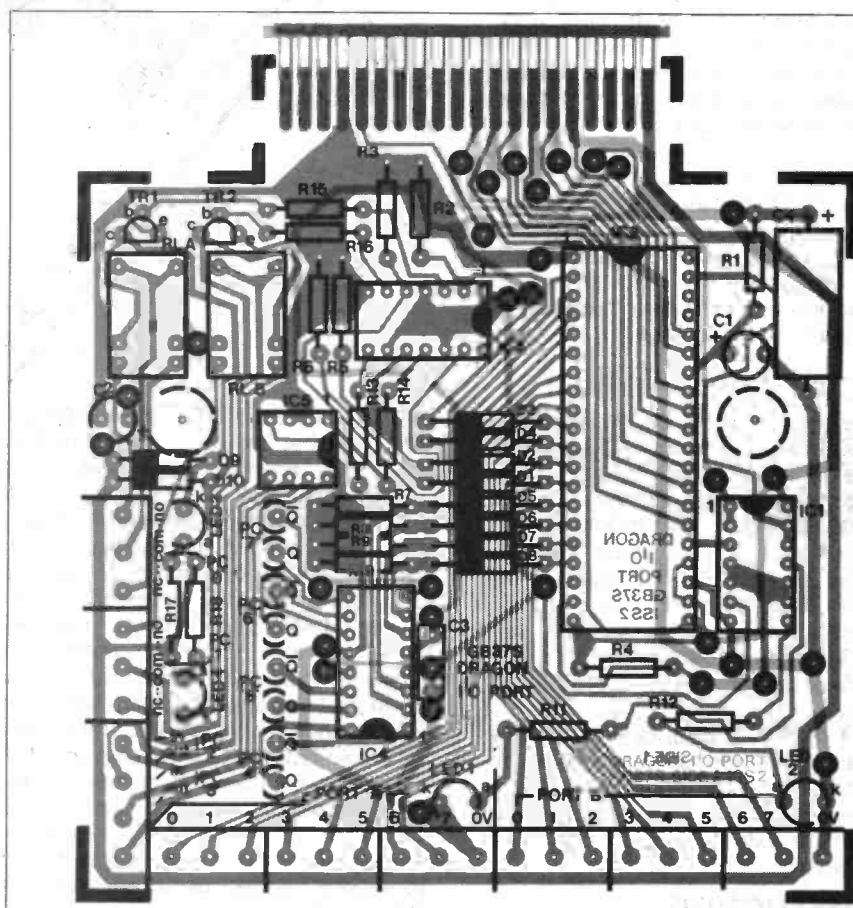


TABLE 1. PORT C


DATA CODE	PC0 RLA	PC1 RLB	PC2 OPT	PC3 OPT	PC4 Q	PC4 Q1	PC5 Q	PC5 Q1	PC6 Q	PC6 Q1	PC7 Q	PC7 Q1
0	0	0	0	0	1	0	1	0	1	0	1	0
1	1	0	0	0	1	0	1	0	1	0	1	0
2	0	1	0	0	1	0	1	0	1	0	1	0
4	0	0	1	0	1	0	1	0	1	0	1	0
8	0	0	0	1	1	0	1	0	1	0	1	0
16	0	0	0	0	0	1	1	0	1	0	1	0
32	0	0	0	0	1	0	0	1	1	0	1	0
64	0	0	0	0	1	0	1	0	0	1	1	0
128	0	0	0	0	1	0	1	0	1	0	0	1

1=+5V OR 'ON', 0=0V OR 'OFF'

PROGRAM 1.

```

1 CLS
2 PRINT@5,"DRAGON I/O PORT TEST":PRINT
3 INPUT"ENTER PORT (A,B OR C)":P$
4 IFP$<"A"OR P$>"C"THEN3
5 INPUT"ENTER MODE(IN OR OUT)":M$
6 IFM$="IN"AND P$="C"THEN5
7 IFM$="IN"OR M$="OUT"THEN8 ELSE5
8 CLS@:PRINT"PORT-":P$;"-":M$:"PUT"
9 REM PORT CODES
10 IFP$="A"THENP=49153:N=36
11 IFP$="B"THENP=49155:N=4
12 IFP$="C"THENP=49155:N=52
13 IFM$="IN"THEN20
14 REM PORT A-C O/P
15 POKE P,0:POKE P-1,255:POKE P,N
16 GOSUB27
17 PRINT@32,"":INPUT"ENTER DATA(0-255)":D$
18 IFD$="P"THEN POKE P-1,0:POKE P,0:GOTO1
19 D=VAL(D$):POKE P-1,D:GOTO17
20 REM PORT A,B I/P
21 POKE P,0:POKE P-1,0
22 POKE P,4:POKE P-1,0
23 PRINT@20,"DATA="
24 GOSUB27
25 GOSUB28
26 GOTO1
27 PRINT@448,"**** ENTER P TO RE-SELECT ****":RETURN
28 A$=INKEY$:IFA$=""THEN PRINT@25,PEEK(P-1):GOTO28
29 RETURN
    
```

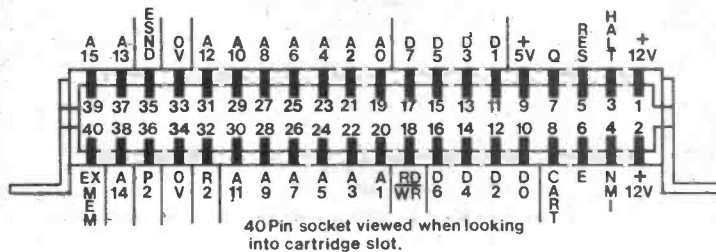

40 Pin socket viewed when looking into cartridge slot.

Figure 3. Dragon cartridge socket pinouts.

Opto ports PC2 and PC3 are checked by connecting an ohmmeter across the In/Out terminals of PC2 and typing POKE 49154,4. The In terminal is the positive input to the opto isolator, so connect the negative lead of your ohmmeter to this terminal and the positive lead to the Out terminal. This may appear to be contradictory, but is necessary because on most multimeter ohm ranges the internal battery positive appears at the negative terminal, due to switching arrangements. Full on resistance is about 200ohms. Type POKE 49154,8 to turn PC2 off and PC3 on. Repeat the meter check to PC3. Maximum off resistance is extremely high, and may be considered to be open circuit. POKE 49154 with 0 to turn off PC0-3.


When using opto-isolators, note that they function as a low current switch and can only handle up to 20V at 8ma. Higher currents, up to 25mA at 5V can be switched providing that the load does not exceed 150mW.

Both relays can switch up to 1A at 100V or 24V DC, but will not handle mains voltages.

Port C, PC4 to PC7, when enabled will follow PB4-7 on the Q outputs and their inverse on the Q outputs. If port C is disabled the outputs will remain latched until reaccessed. Outputs are TTL levels, 0V to 4V approximately.

Table 1 lists the various options available at port C and the data codes (0 to 255) used for operating them.

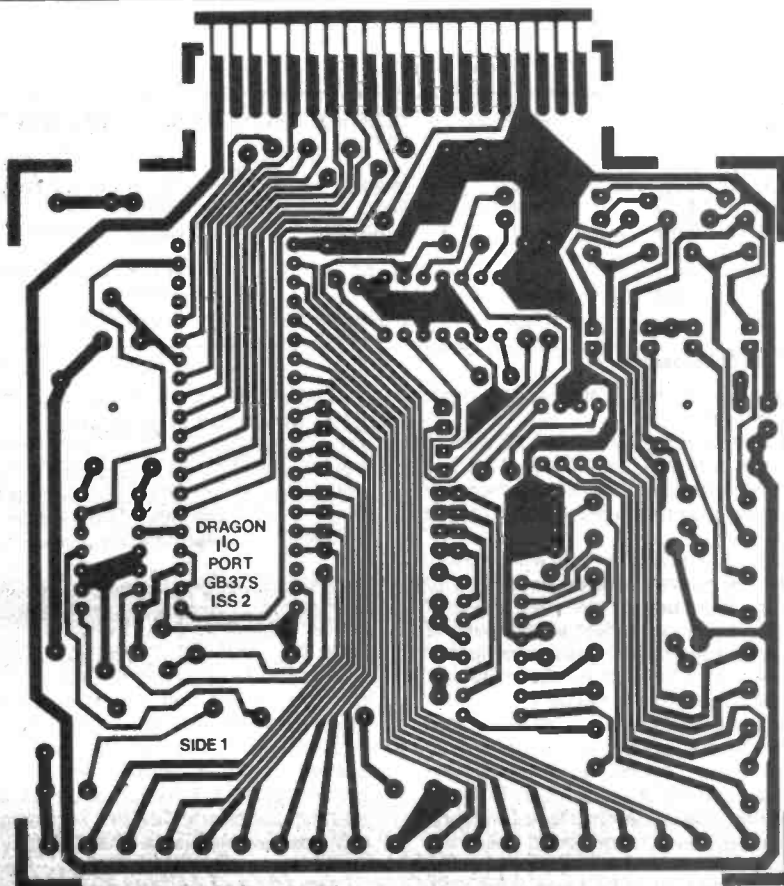To keep the operation of IC2 as simple as possible a list of routines used for accessing each port appears at the end of this article. For further information, comprehensive data



sheets for the 6821 are available, but are really only for technically minded constructors.

Type in Program 1 to continue testing the port, RUN and ENTER. The program asks for a port to be entered, so enter A. Enter OUT mode. Connect the voltmeter to PA0 and 0V, then enter 1. This should give a reading of +4.5V. Repeat this on pins PA1 to 7, entering data codes 2,4, 8, 16, 32, 64, and 128. Only one PA output should be high, the others should be at 0V. Obviously, any decimal code from 0 to 255 could be entered, and the binary coded output calculated, then checked with the meter on port A.

Enter the program again, this time selecting port A,IN. The display is slightly different and input data is required, to be read and printed after

```

ACCESS ROUTINES
PORT A
-----
POKE 49153,0 <CONTROL REGISTER>
POKE 49152,N <DATA DIRECTION REGISTER>
POKE 49153,4 <ACCESS OUTPUT REGISTER>
POKE 49152,DATA <0-255:WRITE>
OR PEEK<49152> <0-255:READ>

PORT B
-----
POKE 49155,0 <CONTROL REGISTER>
POKE 49154,N <DATA DIRECTION REGISTER>
POKE 49155,4 <ACCESS OUTPUT REGISTER>
POKE 49154,DATA <0-255:WRITE>
OR PEEK<49153> <0-255:READ>

PORT C<AND B>
-----
POKE 49155,0
POKE 49154,255 <OUTPUT MODE>
POKE 49155,52 <ENABLE PORT C>
POKE 49154,DATA <0-255>

N=BITS 1 TO 8 ONK(1) FOR OUTPUT MODE
OR BITS 1 TO 8 OFF(0) FOR INPUT MODE

LED 1 <PORT A>
-----
POKE 49153,32

LED 2 <PORT B/C>
-----
POKE 49155,48

```

DATA=. Because port A is tri-state, a no input reading of 255 (PA0-7 = high) is shown. Connect PA0 to 0V and data will be 254, or 255 - 1. Remove 0V from PA0 and reconnect to PA1. This time DATA= 253 or 255-2. Repeat tests on PA2 to PA7 in turn and check DATA=251,247, 239, 223, 191 and 127.

Type P, followed by B,IN and ENTER. Unlike port A, these inputs are normally low so connect PB0 to +5V for DATA=1. Repeat on PB1 to 7 for DATA= 2,4,6,8,16,32,64 and 128, or try different combinations as before.

By now, the module should be working correctly and be ready for use. If not, there may be edge connector problems, or the PCB may require further support. Fault-finding may be performed with the aid of a voltmeter and the access routines.

## PARTS LIST DRAGON I/O PORT

Resistors — All 0.4W 1% metal film unless specified.

R1,15,16	10k	3 off	(M10K)
R2-10	4k7	9 off	(M4K7)
R11,12	470R	2 off	(M470R)
R13,14	270R	2 off	(M270R)
R17,18	2k0	2 off	(M2K0)
<b>Capacitors</b>			
C1	10uF 16V Tantalum		(WW68Y)
C2	1uF 35V Tantalum		(WW60Q)
C3	100nF Disc		(BX03D)
C4	100uF 25V axial electrolytic		(FB49D)
<b>Semiconductors</b>			
D1-8	1N4148	8 off	(QL80B)
D9,10	1N4001	2 off	(QL73Q)
TR1,2	BC338	2 off	(QB69A)
IC1	74LS00		(YF00A)
IC2	6821P		(WQ46A)
IC3	74LS08		(YF06G)

IC4	74LS75		(YF32K)
IC5	Dual opto		(YX94C)
LED1,2	Red LED	2 off	(WL27E)
LED3,4	Mini Red LED	2 off	(WL32K)
<b>Miscellaneous</b>			
RL A,B	P.C. board		(GB37S)
	Relay ultra min SPDT	2 off	(YX94C)
	3-way P.C. terminal	8 off	(RK72P)
	4-way P.C. terminal		(RK73Q)
	D.I.L. socket 40 pin		(HQ38R)
	D.I.L. socket 16 pin		(BL19V)
	D.I.L. socket 14 pin	2 off	(BL18U)
	D.I.L. socket 8 pin		(BL17T)
	Trackpin	1 pkt	(FL82D)
	Veropin 2145	1 pkt	(FL24B)
	Feet cab	1 pkt	(FW19V)
	Bolt 4BA 1/4"	1 pkt	(BF02C)
	Nut 4BA	1 pkt	(BF17T)

A complete kit of all parts is available. Order As LK18U Price £13.95.

## Interfacing the BBC Micro Continued from Page 22

### Handshake Lines

The two handshake lines of each port provide similar facilities to those of the user port, but there is no independent input mode, and there are differences in the way in which they are set up and used. As inputs, the handshake lines can either set their respective interrupt outputs low on an active transition, or they can be used with these outputs disabled. We will only consider the A port, but the B port is used in the same way. CA1 is controlled by bits 0 and 1 of control register A, and its output is at bit 7 of this register. CA2 is controlled by bits 3 to 5 and gives an output at bit 6. The logic AND facility of the computer can be used in the way described earlier to test the state of the just bit 6 or bit 7 of the control register. Table 1

Binary/ Decimal No.	Mode Of Operation
00/0	CA1 high to low, interrupt disabled
01/1	CA1 high to low, interrupt enabled
10/2	CA1 low to high, interrupt disabled
11/3	CA1 low to high, interrupt enabled
000/0	CA2 high to low, interrupt disabled
001/8	CA2 high to low, interrupt enabled
010/16	CA2 low to high, interrupt enabled
011/24	CA2 low to high, interrupt enabled

Table 1

ADDRESS	RS1	RS0	CONTROL REGISTER BIT 2	REGISTER SELECTED
&FCC0	Low	Low	High	Peripheral Register A
&FCC0	Low	Low	Low	DDRA
&FCC1	Low	High	Irrelevant	Control Register A
&FCC2	High	Low	High	Peripheral Register B
&FCC2	High	Low	Low	DDRB
&FCC3	High	High	Irrelevant	Control Register B

Figure 4. 6821 addresses.

details the way in which the various input modes are obtained.

Note that CB2 is different to CA2 when it is used as an output in that in the first mode it is reset by a write operation, and in the pulse mode the pulse is produced when writing to the port.

Often both handshake lines will be used, and then the number written to ?&FCC1 or ?&FCC3 is the sum of the two decimal numbers in the above tables which give the desired operating modes. Remember to add a further 4 to this figure if access to the port (rather than the DDR) is needed.

In this article it has been assumed that the input and output devices will be directly addressed, but Acorn recommend the alternative method of using OSBYTE calls. This is simply because directly addressing peripheral devices will not work if one of the second processors is added to the Tube. It is possible to write to an output port using a \*FX command (\*FX151,96,255 writes 255 to the user port DDR for example), but it is not possible to send a numeric variable in this way, or to read from a peripheral device. It is

Table 2 shows the various ways in which CA2 can be used as an output.

Binary/ Decimal No.	Mode of Operation
100/32	set high by activating CA1, low by read operation
101/40	high to low pulse during read operation
110/48	constant low output
111/56	constant high output

Table 2

possible to read from an input port using a machine code routine, as described in the "User Manual" (but note that this stores the answer in the Y register and not in the accumulator). It is much easier to directly address peripheral devices, and is probably not worthwhile using the OSBYTE calls unless it is essential to do so.

The 12 bit analogue to digital converter of the BBC micro is very useful for application where a fast sampling rate is not needed. It is quite simple to use and is fully described in the "User Guide".

# PRICE LIST

All prices shown in this price list are valid from 15th August 1983 to 12th November 1983

Please note new telephone number for Sales Only (0702) 552911

Prices shown in this list include VAT at 15% where applicable. Items marked NV are rated at 0% and the price shown applies both to inland and export orders. Overseas customers should add up the total cost of all items except those marked NV and deduct 13% to arrive at the total price excluding VAT. Alternatively multiplying the total price (except NV items) by 0.87 will give the total price excluding VAT. Please add extra for carriage on all overseas orders. Carriage will be charged at cost.

Although postage charges to customers living in the Republic of Ireland and in the UK, but not on the UK mainland, are the same as to mainland addresses we regret that we must levy an additional charge of £5 on each order containing any items marked "Delivery by Carrier".

Will customers from the Republic of Ireland please add 40p and then 35% to the cost of their order now that the Irish pound is not equivalent to sterling, to cover the rate difference and negotiation fees. We will refund any difference; please state cheque or credit note. Alternatively if you pay by bank draft drawn in pounds sterling on a London bank, then you need add nothing extra. Bank drafts drawn in pounds sterling on a London bank should be readily available from your local bank.

All prices are for the unit quantity shown in the catalogue (unless shown otherwise on this list) i.e. each, per pack, per metre etc. All prices include postage and packing. There is a 50p handling charge which must be paid on all orders having a total value of under £5.00.

The price list is intended for use with our 1983 catalogue and applies to all mail orders. Prices in our shop are generally lower on heavy items as mail order prices include postage and packing costs.

Copies of manufacturers' data sheets are available for most IC's - price 40p each.

NYA Not yet available  
 NA Not available  
 DIS Discontinued  
 TEMP Temporarily out of stock  
 OOP Out of print  
 FEB Out of stock, new stock expected in month shown  
 † While stocks last  
 NV Indicates that item is zero rated for VAT purposes  
 ★ See Amendments to Catalogue  
 \$ Please add £6 carriage if your order contains one or more items marked thus

## TRADE QUANTITIES

The letter in brackets after the price indicates the minimum quantity of that item you can buy and qualify for a trade price. If you buy less than the quantity shown then the price is that shown. If you want to buy the quantity shown or more of that item, then please contact us for a trade price. If no trade quantity is shown, then the price shown is the best price we can offer regardless of the quantity. Trade quantities shown for wires or cables of any type is in metres, not reels or parts of metres. Trade quantities for nuts, bolts, washers, Hiatts etc. refers to the number of packs, i.e. to qualify for a trade price on Tag 2BA for example (trade quantity 500), you will need to order 500 packs which is equal to 5000 tags. Most items in the price list have a letter in brackets after the price which indicates the trade quantity as follows:

- (A) Trade quantity 5
- (B) Trade quantity 10
- (C) Trade quantity 25
- (D) Trade quantity 50
- (E) Trade quantity 100
- (F) Trade quantity 250
- (G) Trade quantity 500
- (H) Trade quantity 1000

## Prices charged will be those ruling on the day of despatch

1983 Catalogue Page No.	VAT inclusive PRICE	1983 Catalogue Page No.	VAT inclusive PRICE	1983 Catalogue Page No.	VAT inclusive PRICE	1983 Catalogue Page No.	VAT inclusive PRICE	
<b>Page 15</b>				<b>Page 25</b>				
XF30H Private Attack Poster.....	£1.00 NV(D)	XQ53H Mast Bracket Type 3.....	£8.50 (B)	RK48C 8-Section Antenna.....	£1.26 (D)	<b>BOOKS</b>		
XF12N Maplin Poster.....	DIS	XQ54J Mast Bracket Type 8.....	£12.75 (A)	RK49D 6-Section Antenna.....	96p (D)	<b>Page 29</b>		
<b>AERIALS</b>				LB10L Telescopic Aerial 1.22m.....	£4.52 (C)	WA27E Basic Elec & DC Ccts.....	£12.74 NV(A)	
XQ223A Trucolour TC13 Grp B.....	£16.50 (A)	XQ55K Lashing Kit Type 4.....	£9.85 (B)	YL43W TVI Filter.....	£4.25 (B)	WA28F Basic AC Ccts.....	£10.95 NV(A)	
XQ24B Mushkiller FM235T.....	DIS	XQ56L Lashing Kit Type 6.....	£16.99 (A)	XB54J Aerial Rotator.....	£39.95 (A)	RL27E Book NB147.....	£8.53 NV(B)	
XQ25C Mushkiller FM244T.....	£17.80 (A)	XQ58N Lashing Kit Type 9.....	£12.24 (A)	<b>BATTERIES</b>				
XQ27E Mushkiller FM264T.....	£22.20 (A)	XQ60Q Mast D.....	£3.94 (C)	YG00A Ni Cad AA.....	£1.25 (D)	WG10L Book JW787.....	DIS	
XQ28F Mushkiller FM284T.....	DIS	XQ61R Mast E.....	£7.85 (B)	YG02C Ni Cad C.....	£3.33 (C)	RH64U Book NB047.....	DIS	
XQ29G Trucolour TC10 Grp A.....	£10.50 (A)	XQ62S Mast G.....	£15.95 (A)	YG03D Ni Cad D.....	£4.99 (B)	RL31J Book NB157.....	£5.42 NV(C)	
XQ30H Trucolour TC10 Grp B.....	£10.62 (B)	XQ63T Mast M.....	£6.39 (B)	HW31J Nicad PP3.....	£4.99 (B)	RL29C Book NB152.....	£3.45 NV(C)	
XQ31J Trucolour TC10 Grp C.....	£10.32 (B)	BW46A Masthead UP1300W.....	£11.84 (A)	RK46A PCB Mounting 3.6V Bat.....	£2.45 (C)	RQ22Y Book NB245.....	£5.98 NV(C)	
XQ32A Trucolour TC10 Grp E.....	£9.94 (B)	BW50E Power Unit PU1240.....	£14.65 (A)	WY22Y Ni-Cad Charger.....	£7.95 (B)	RR02C Book NB200.....	£3.24 NV(C)	
XQ32K Trucolour TC13 Grp A.....	£12.24 (A)	<b>Page 26</b>				<b>Page 30</b>		
XQ33L Trucolour TC13 Grp B.....	£12.20 (A)	YY73Q Amp XB1U.....	£15.80 (A)	YG00A Ni Cad AA.....	£1.25 (D)	XW31J Book MM639.....	£1.95 NV(D)	
XQ34M Trucolour TC13 Grp C.....	£12.20 (A)	BK06G Amp VX1B.....	£17.99 (A)	YG02C Ni Cad C.....	£3.33 (C)	XW12N Book NB386.....	£4.56 NV(C)	
XQ35D Trucolour TC18 Grp A.....	£13.95 (A)	YG22Y Xtra Set Amp.....	£16.99 (A)	YG03D Ni Cad D.....	£4.99 (B)	+ RH05V Book NB048.....	£4.89 NV(C)	
XQ36F Trucolour TC18 Grp B.....	£13.85 (A)	RW36P Pluggack 200.....	£1.08 (E)	HW32K PP3 Nicad Charger.....	£9.95 (B)	+ WG71N Book BP94.....	£2.10 NV(C)	
XQ37S Trucolour TC18 Grp C.....	£13.25 (A)	BW51F Diplexer UF20.....	£6.24 (A)	YK31J Univsl Ni-Cad Chgr.....	£9.95 (B)	XW00A Book FT882.....	£7.25 NV(C)	
XG24B Trucolour TC18 Grp E.....	£13.25 (A)	BW52G Splitter CS1000.....	£7.86 (B)	HW32K PP3 Nicad Charger.....	£9.95 (B)	WA44X Undrstndng Auto Elec.....	£5.23 NV	
<b>Page 21</b>				BW53H Splitter SB20.....	£5.98	RL13P Book NB099.....	£3.22 NV	
XQ38R Extragain XG5.....	£17.60 (A)	YQ23A Aerial Splitter SB11.....	£4.26 (C)	XX09K AC Adaptor BR300.....	£4.45 (C)	RH21X Book BP27.....	65p NV	
XQ39N Extragain XG8 GroupA.....	£22.80 (A)	YQ23A Splitter CS200.....	£4.72 (C)	HF27E Clips PP9.....	£14p (C)	RH53H Book BP160.....	£1.40 NV	
XQ40T Extragain XG8 GroupB.....	£23.50 (A)	HX87U Surface Co-Ax Outlet.....	75p (E)	HF28F PP3 Clip.....	9p (H)	XW53B Book NB454.....	£4.66 NV	
XQ41U Extragain XG8 GroupC.....	£22.50 (A)	<b>Page 24</b>				RL06G Book NB0740.....	£4.99 NV	
XQ42V Extragain XG8 Wdbnd.....	£21.95 (A)	BW54J Sfce Dble Co-Ax Outt.....	£2.74 (C)	HF28F PP3 Clip.....	9p (H)	RH05F Book BP7.....	50p NV	
XQ43W Extragain XG14 GroupA.....	£37.60 (A)	BW55K Flush Co-Ax Outlet.....	£2.99 (E)	RK43W Heavy Duty Clips.....	DIS	RL02C Book NB059.....	£7.49 NV	
XQ44X Extragain XG14 GroupB.....	£37.60 (A)	BW56L Fish Dbl Co-Ax Outt.....	£2.65 (C)	YR59P 1.5V Batt Box.....	16p (D)	+ RH04E Book BP6.....	85p NV	
XQ45Y Extragain XG14 GroupC.....	£37.30 (A)	BW57M TV/FM Outlet.....	£4.65 (C)	YR60Q 3V Batt Box.....	22p (D)	<b>Page 31</b>		
XQ46A Extragain XG14 Wdbnd.....	£37.30 (A)	BW58N Aerial Switch.....	£4.35 (C)	YR61R 4.5V Batt Box.....	33p (F)	RQ23A Book BP53.....	£3.20 NV	
XQ45E Extragain XG21 Wdbnd.....	£33.60 (A)	LB09K 75/300 Balun.....	£1.30 (D)	HF29G 6V Batt Box.....	29p (G)	RH21X Book BP27.....	65p NV	
XQ51F Super-Set Top.....	£9.64 (B)	RK47B 3dB Attenuator.....	£1.95 (D)	HO31B 9V Batt Holder.....	35p (F)	XW33H Book NB156.....	£1.40 NV	
XY30H Toptena.....	£5.55 (B)	BW59P Attenuator 5dB.....	£1.98 (D)	+ YR62S 12V Battery Box.....	85p (E)	XW53T Book JM671.....	£2.99 NV(C)	
XQ52G Caratenna CA7.....	£10.25 (A)	BW60Q Attenuator 12dB.....	£1.95 (D)	RK45Y 12V NiCad Batry Box.....	49p (F)	WA51F Book BP107.....	£2.45 NV	
<b>Page 22</b>				LB11M FM Tape Aerial.....	60p (E)	WA55K Book BP113.....	£2.45 NV	
BW42V Univ. Clamp Type 1.....	£1.95 (D)	YG20W Ferrite Rod 810.....	33p (E)	HF95D HP11 Batt Box.....	39p (F)	XW64U Book NB449.....	£5.58 NV	
BW43W Mast Bracket Type 2.....	£2.55 (C)	YG22Y Ferrite Rod 101.....	48p (F)	HF97F HP2 Batt Box.....	79p (E)	WA21X Undrstndng Dig Elec.....	£5.18 NV	
<b>TRADE QUANTITIES</b>				YG23A Ferrite Rod 102.....	79p (E)	WA11M Book JW748.....	£8.34 NV	
The letter in brackets after the price indicates the minimum trade quantity. For details please see page 27				LB12N MW/LW Aerial.....	£2.35 (C)	<b>Page 32</b>		
<b>September 1983 Maplin Magazine</b>				<b>Page 33</b>				
				RQ06G Book NB209.....				£8.45 NV
				RH631 Book NB041.....				£3.28 NV
				RF10L Book BP728.....				£2.20 NV
				RL33L Book NB188.....				£8.68 NV
				XW87U Book AG530.....				£4.55 NV
				WA24B Undrstndng Communctns.....				£5.23 NV
				RH00A Book BP1.....				£1.50 NV
				RH11M Book BP14.....				£2.15 NV
				WG30H Book BP85.....				£3.25 NV
				RR39N Towers Transistor Bk.....				£11.25 NV
				RL34M Book NB189.....				£8.43 NV
				WA52G Book BP108.....				£2.45 NV
				RQ68Y Book FT938.....				£10.20 NV
				<b>Page 34</b>				
				WA18U TI Dig IC Guide.....				£4.50 NV
				WG58N Book FT1199.....				£9.61 NV
				WA12N TI Bipolar Micro.....				£5.75 NV
				WA15R TI 9600 Data.....				£12.63 NV
				RQ54J 280 Data.....				TEMP
				WG23A Book JW568.....				£28.74 NV
				WA07H TI Bipolar Memory Data.....				£1.45 NV
				WA06G TI MOS Memo Data.....				£5.28 NV

1983 Catalogue Page No.	VAT inclusive PRICE	1983 Catalogue Page No.	VAT inclusive PRICE	1983 Catalogue Page No.	VAT inclusive PRICE	1983 Catalogue Page No.	VAT inclusive PRICE
WG22Y Book JW567	£25.99 NV	Page44		XW98G Book FT1070	£8.20 NV	WA81C Making Most of ZX81	£8.15 NV
WG67U Book BP101	65p NV	WA600 Book FT1076	£6.40 NV	R002C Book Sybex C207	£14.64 NV	WG83E Book MM113	£3.18 NV
RQ25C Book NB278	£5.32 NV	WAS9F Book FT139	£3.84 NV	Page54		WA91Y Book NB223	£6.64 NV
+RL07H Book NB076	£7.64 NV	RL04E Book NB071	DIS	WA93E Get Acquainted ZX81	£5.61 NV	WA83E	£5.61 NV
RL17T Book NB115	£1.95 NV	RR00A Book NB195	£10.20 NV	WA92A Book NB129	£6.64 NV	WA85G 34 ZX81 Games	£4.57 NV
RQ26D Book NB319	£5.24 NV	WG86T Book AG471	DIS	WA41U Advanced 6502 I/Face	£12.18 NV	WA79L Explosive Games ZX81	£5.58 NV
Page35		WG34M Book NB472	£5.32 NV	WA20C Book MM495	£9.98 NV	WA42V 30-Hour BASIC	£7.90 NV
RR28F Book NB2028	£15.48 NV	WA90X Book NB473	£4.99 NV	WG81C Book FT1330	£8.87 NV	WA38R Book BP109	£1.95 NV
WA29G Book BP88	£2.25 NV	XW54J Book NB439	£3.54 NV	WV19V Book HD166	£10.98 NV	WA56L Book BP114	£2.70 NV
+R067X Book BP61	£1.95 NV	WG59F Book BP891	£2.15 NV	WV80B Book C202	£1.72 NV	WG99H Book MM973	£7.63 NV
RB25C Book BP225	£1.95 NV	WV92A Book WDXG	£5.74 NV	XW81C Book D302	£1.39 NV	Page65	
RR21X Book NB879	DIS	XW27E Book NB402	£6.94 NV	WA05F 6502 Assembly Subs	£13.95 NV	WA84F ZX81 Companion	£5.62 NV
RR37S Photocell Apps Book	£4.35 NV	Page45		WA45Y Beyond Games	DIS	WA03D Peek, Poke, Byte & RAM	£6.13 NV
RF12N Book BP42	£1.50 NV	WV99H Book FT1054	£6.75 NV	Page55		WA03B ZX81 ROM by Logan	£10.12 NV
WG43W Book BP447	£5.17 NV	RB22Y Book BP222	£1.40 NV	WG63T Book HD183	£7.20 NV	WA82D ZX81 Machine Code	£7.10 NV
WA26D Understrng Optonics	£1.50 NV	RB26D Book BP226	£2.15 NV	WV70M Book M3	£12.95 NV	WA86T Sinclair Machine Cde	£10.19 NV
WA09K Opto Theory/Practice	£7.99 NV	RF18U Book BP43	£1.99 NV	WG68V Book BP102	£1.95 NV	WK01B Spectrum Sinclair	£6.83 NV
WA08J Tl To Data	£5.50 NV	WG52E Book NB502	£4.52 NV	WA04E 68000 Assembly Prog	£15.64 NV	WK00A Prog Your Spectrum	£6.81 NV
LY05F Book BP45	£1.99 NV	WG95D Book FT1305	£9.72 NV	XW65A Book M2	£13.25 NV	WK003 Spectrum Programmer	£6.89 NV
Page36		WG98B Book FT1233	£11.62 NV	R015R Book Sybex M13	DIS	WA78K 20 Prog For Spectrum	£8.13 NV
XW34M Book BP67	£2.05 NV	WG80B Book FT1185	£6.94 NV	WG65W Book JW095	£9.40 NV	WA98G 60 Games Spectrum	£4.57 NV
XW62S Book BP82	£2.25 NV	R058N Book BP55	£2.00 NV	WG21X Book HD167	£11.32 NV	Page66	
WG85G Guide To Solar Elect	£4.95 NV	XW43W Book NB467	£5.64 NV	WA54J Book BP112	£2.75 NV	LH56L Potting Box Min	16p (G)
RR03D Book NB201	£4.45 NV	XW91Y Book WRTV	£12.10 NV	Page56		LH57M Potting Box Small	28p (G)
RR27E Book NB2026	£4.62 NV	Page46		XW72T Book C280	£14.13 NV	LH58N Potting Box Medium	DIS
RR04E Book NB203	£4.46 NV	WA97F Book NB156	£7.12 NV	R017P Book Sybex M15	DIS	LH59P Potting Box Large	34p (F)
WG90X Book AG475	DIS	RQ03L Book BP222	£1.40 NV	XW78K Book C281	DIS	LH02C ABS Box P1 White	£1.45 (D)
WG01B Book NB447	£5.99 NV	WA61R Book FT1409	£2.05 NV	WA88V Book NB120	£4.95 NV	LH14Q ABS Box P1 Grey	£1.45 (D)
WG44X Book AG600	£4.45 NV	+XW98E Book FT933	£9.15 NV	WG16S Book JW331	£9.62 NV	YK48C Snap Box B1	£1.10 (D)
RR09K Book NB229	£4.56 NV	+WG20V Book AG652	£3.78 NV	WA74R Instant Basic Book	£9.28 NV	+YK49D Snap Box B2	£1.40 (D)
RF09K Book BP227	£2.20 NV	WG97F Book KN035	£4.17 NV	+YK49E Snap Box B3	£1.99 (D)	+YK51F Snap Box B4	£2.30 (D)
RL10L Book NB230	£1.92 NV	WG70M Book KN400	£4.32 NV	WG62V Book HD165	£8.64 NV	LH20W ABS Box MB1	£1.26 (D)
+XW89W Book AG437	£4.10 NV	WG73Q Book BP96	£2.10 NV	WG21X Book HD167	£11.32 NV	LH22Y ABS Box MB3	£1.49 (D)
Page37		RH59F Book NB016	£5.49 NV	WA54J Book BP112	£2.75 NV	LH23A ABS Box MB4	£3.25 (C)
RR11M Book NB231	DIS	RQ11J Book NB268	DIS	XW49D Book MM304	£4.74 NV	WY03D ABS Box 2002	£1.36 (D)
WA53H Book BP110	£2.15 NV	LW28F Book BP46	DIS	Page57		LH60Q ABS Box 2004	£1.68 (D)
+RH17T Book BP48	£1.92 NV	Page47		WV50E Book MM266	£6.66 NV	LH61R ABS Box 2005	£1.98 (D)
RQ28F Book BP92	£1.75 NV	RH57M Book NB001	£11.20 NV	RL45Y Book HD106	£11.33 NV	LH62S ABS Box 2006	£3.42 (C)
+WA34M Book BP92	£1.75 NV	RL24B Book NB144	DIS	WV58W Book NB415	£5.21 NV	LH63T ABS Console M1005	£2.64 (C)
RQ29G Book BP49	£1.99 NV	WG89W Book NB132	£3.86 NV	+WG13P Book JW204	£7.18 NV	LH64U ABS Console M1006	£4.25 (C)
XW67X Book BP80	£2.25 NV	WV88V Book AG569	£3.70 NV	WA69A Microsoft Basic Book	£11.68 NV	YK24L Calc-Style Verobox	£4.94 (C)
WG98T Book BP98	£2.25 NV	XW32K Book BP70	60p NV	WV04E Book FT1055	DIS	Page67	
WA35O Book BP99	£1.95 NV	R059P Book NB367	£2.75 NV	WG69G Book HD534	£10.20 NV	LH65V ABS Console M6005	£2.96 (C)
WA36P Book BP103	£1.95 NV	RR77J Book FT732	DIS	WV04E Book FT1055	DIS	LH66W ABS Console M6006	£3.82 (C)
WG57M Book FT1300	£17.21 NV	RF17T Book NB420	£1.94 NV	WV04E Book FT1055	DIS	LH67X ABS Console M6007	£5.20 (B)
+WG28F Book BP83	£2.15 NV	RL14Q Book NB101	£5.39 NV	WV04E Book FT1055	DIS	LH68Y ABS Console M6005	£4.55 (C)
Page38		RR24B Book NB970	£6.32 NV	WG64F Book JW415	£6.95 NV	LH68Z ABS Console M8007	£6.94 (D)
RB21X Book BP221	DIS	Page48		WV04E Book FT1055	DIS	YR72P Pcb Guide Adapter	9p (H)
RR19V Book NB864	DIS	RH58N Book NB014	£3.34 NV	WV04E Book FT1055	DIS	WY00A Metal Panel Bx M4003	£1.98 (D)
RF08J Book BP39	DIS	RF17T Book NB420	£1.94 NV	WV04E Book FT1055	DIS	WY01B Metal Panel Bx M4004	£1.98 (D)
RR13H Book BP37	£1.92 NV	RL12N Book NB089	DIS	WV04E Book FT1055	DIS	WY02C Metal Panel Bx M4005	£2.88 (D)
RL05F Book NB074	£6.88 NV	RL21X Book NB134	DIS	WV04E Book FT1055	DIS	+LH06Q Pedal Switch Box	£5.99 (D)
+XW17T Book HD760	£7.64 NV	RL23A Book NB137	£13.85 NV	WV04E Book FT1055	DIS	LF03D Display Box	£5.99 (D)
RL36P Book NB435	DIS	RR27E Book BP34	£1.96 NV	WV04E Book FT1055	DIS	HY25C Display Box	£1.25 (D)
RL41U Book NB534	DIS	WA94C Book NB577	£4.96 NV	WV04E Book FT1055	DIS	Page69	
RB25C Book BP97	£1.95 NV	Page49		WV04E Book FT1055	DIS	HQ478 Tilt Leg Large	£1.68 (D)
WA37S Book BP105	£1.95 NV	WV57M Book BP100	£2.15 NV	WV04E Book FT1055	DIS	LH00A Verobox 101	£4.36 (C)
WG52E Book BP76	£2.05 NV	+WA98E Book NB186	£6.23 NV	WV04E Book FT1055	DIS	LH01B Verobox 102	£4.92 (C)
WG27P Book BP93	£2.10 NV	WA95D Book NB506	£12.67 NV	WV04E Book FT1055	DIS	L003J Verobox 103	£1.95 (D)
Page39		WG77J Book NB553	£3.44 NV	WV04E Book FT1055	DIS	L010B Verobox 104	£14.95 (A)
WG50E Book NB500	£4.56 NV	WG02C Book NB475	DIS	WV04E Book FT1055	DIS	L022C Verobox 105	DIS
WG10H Book NB478	£6.32 NV	RF14Q Book NB274	DIS	WV04E Book FT1055	DIS	L030D Verobox 106	£3.64 (C)
WG35O Book HD893	£3.96 NV	XW26D Book NB180	£11.20 NV	WV04E Book FT1055	DIS	L040E Verobox 107	£3.96 (C)
WA95D Book FT1349	£11.69 NV	LW29G Book BP47	DIS	WV04E Book FT1055	DIS	L060G Verobox 202	£7.24 (B)
WA49D Book BP104	NOV	WG69A Book AG602	£8.75 NV	WV04E Book FT1055	DIS	L070H Verobox 203	£9.64 (A)
WG91Y Book FT1261	£7.20 NV	WV85G Book AG510	£6.95 NV	WV04E Book FT1055	DIS	L080J Verobox 211	£4.69 (C)
RH18U Book BP24	£1.35 NV	RF13P Book NB238	DIS	WV04E Book FT1055	DIS	L090K Verobox 212	£4.95 (C)
RL30H Book NB153	£3.82 NV	RF13P Book NB238	DIS	WV04E Book FT1055	DIS	L100L Verobox 213	£4.95 (C)
WA50E Book BP106	£2.15 NV	RF13P Book NB238	DIS	WV04E Book FT1055	DIS	L007H Verobox 214	£5.68 (B)
LY04E Book BP44	DIS	WV83E Book AG512	£6.17 NV	WV04E Book FT1055	DIS	L008J Verobox 215	£6.24 (B)
XW38R Book NB480	£6.75 NV	Page50		WV04E Book FT1055	DIS	L009K Verobox 216	£6.93 (B)
+RQ27E Book BP50	£1.60 NV	RF15R Book NB252	£13.61 NV	WV04E Book FT1055	DIS	L111M Verobox 217	£6.64 (B)
Page40		RF15R Book NB252	£13.66 NV	WV04E Book FT1055	DIS	LH25C Verobox 222	DIS
RB23A Book BP223	DIS	RQ36P Book BP51	£1.95 NV	WV04E Book FT1055	DIS	+LH26D Verobox 223	£5.40 (B)
+WA30H Book BP97	£1.95 NV	RF18F Book BP38	DIS	WV04E Book FT1055	DIS	Verobox 301	76p (E)
XW20W Book BP65	£1.75 NV	WG09K Book JW266	£13.98 NV	WV04E Book FT1055	DIS	LH13P Verobox 302	DIS
RL01B Book NB058	£6.78 NV	WG40T Book HD753	£27.99 NV	WV04E Book FT1055	DIS	L110L Verobox 303	£1.48 (D)
RH28F Book BP35	DIS	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LH51F Verobox 305	£2.82 (C)
WG29G Book BP84	£2.15 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LH14Q Verobox 401	99p (D)
RB24B Book BP224	£1.55 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	XB88R Verocase 501	£16.24 (A)
RQ66W Book BP59	£1.75 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	XB89V Verocase 502	DIS
RR07H Book NB165	£6.92 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LH47C Verobox 503	£16.20 (A)
RL44X Book BP58	£1.72 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	L000B Top Box 601 Bk	£3.00 (A)
WA62S Book NB769	£6.48 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LQ007 Flip - Top Box 602 Bk	£5.25 (B)
RL43W Book BP56	£1.95 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LH02F Verobox 701	£6.24 (B)
WG54J Book NB535	£4.56 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LH28F Verobox 702	DIS
Page41		WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LH30H Verobox 705	£8.42 (B)
RB10L Book NB269	£5.63 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	Page70	
RF20W Book HD734	£8.90 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LF08J Box AB7	£1.25 (D)
XW30H Book MM700	£2.39 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LF09L Box AB8	DIS
WG44X Book BP71	£1.90 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LF10L Box AB9	£1.15 (D)
+RL42V Book NB346	£4.05 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LF11M Box AB10	£1.35 (D)
WG51F Book NB501	DIS	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LF12N Box AB11	£1.25 (D)
XW31L Book NB501	£4.54 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LF13P Box AB12	99p (E)
XW08J Book BP60	£1.65 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LF14Q Box AB13	£2.25 (C)
WG46A Book BP90	£2.15 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LF15R Box AB23	£1.65 (D)
XW46A Book MM513	£2.90 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LF16S Box AB24	£1.75 (D)
RL40T Book NB338	£4.34 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LH10L Box AB28	£1.50 (D)
Page42		WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	XB65L Chassis AC54	£2.10 (C)
+RH52G Book BP220	£1.05 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	XB89Y Chassis AC86	£3.25 (D)
RH22Y Book BP29	DIS	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LF02C Case WB1 Viny	£1.99 (D)
XW37S Book BP69	£1.85 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LH37S Case WB2 Viny	£3.06 (C)
+XW11M Book BP379	£4.10 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LH38R Case WB3 Viny	£3.64 (C)
RH15F Book BP19	DIS	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LH40T Case WB5 Viny	£6.20 (B)
XW47H Book MM396	£2.19 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LH41U Case WB6 Viny	£6.82 (B)
WG53H Book BP529	£2.16 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LH42V Case WB7 Viny	£7.85 (B)
XW51F Book BP75	£2.00 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LH43W Case TP1 Teak	£2.20 (C)
RH50E Book BP216	DIS	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LH45Y Case TP3 Teak	DIS
XW07H Book BP75	£2.15 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LH46A Case TP4 Teak	DIS
RQ30H Book NB353	£6.94 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LH47H Case TP5 Teak	DIS
WG60G Book BP95	£2.15 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LH48C Case TP6 Teak	£7.22 (D)
Page43		WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LH71N Box DCM5002	£2.82 (D)
RQ80B Book FT926	£6.60 NV	WV04E Book FT1055	DIS	WV04E Book FT1055	DIS	LH72P Box DCM5004	











1983 Catalogue Page No. VAT inclusive PRICE
Page222
Page223
Page224
Page225
Page226
Page227
Page228
Page229
Page230
Page231
Page232
Page233
Page234
Page235
Page236
Page237
Page238
Page239
Page240
Page241
Page242
Page243
Page244
Page245
Page246
Page247
Page248
Page249
Page250
Page251
Page252
Page253
Page254
Page255
Page256
Page260
Page261
Page262
Page263
TRADE QUANTITIES
The letter in brackets after the price indicates the minimum trade quantity. For details please see page 27.
September 1983 Maplin Magazine









# MAPLIN NEWS MAPLIN NEWS

## COMING SHORTLY

- ★ An ORIC Talkback
- ★ Personal Stereo Dynamic Noise Limiter
- ★ Syndrum Interface
- ★ Microphone Pre-amp/Limiter
- ★ Pseudo Stereo AM Radio
- ★ NiCad Charger Timer
- ★ Spectrum I/O Port
- ★ TTL/RS232 Converter
- ★ 1K ZX81 RAM Extension
- ★ Part 2 of the Telephone Exchange
- ★ VIC Extendboard with 3K RAM Pack
- ★ Logic Pulsar
- ★ Frequency Meter Adaptor
- ★ An Auto-Waa pedal
- ★ A Spectrum Keyboard
- ★ Part 2 of the House Wiring Article

## CORRIGENDA

### Vol. 2 No. 5

Modem: R4b should be 12k.

### Vol. 2 No. 7

VIC20 RS232 INTERFACE: Since this project was published, a few improvements have been made.

R4,8,12 and 16 are now 4k7.

Four extra resistors (R33-36 inc.) value 4k7, have been added to each of the input lines Sin, DCD, CTS and DSR.

The power supply section of the circuit has been redesigned, see sketch below. C3 is a 100uF Reversolytic, R37 is a 47R 1/2W Standard resistor and D5 to 7 are IN4001.

Note: The PCB (GB28F) has been modified to accept these new components and the kit (LK11M) has the new parts supplied.

SIMPLE SWEEP OSCILLATOR: Some components in the PARTS LIST have been changed.

C4,6,7,8 are now 100uF 25V P.C. Electrolytics (FF11M).

C11 is 220nF polyester (BX78K).

4 DIL sockets 8 pin (BL17T) are required, and 2 DIL sockets 16 pin (BL19V) are needed.

Note: The Kit (LK06G) contains these parts.

CMOS CRYSTAL CALIBRATOR: In the PARTS LIST, TR2 should be BC108 not EC108.

ENLARGER TIMER: In Figure 4, the pin out designated 2N6073 should be uA 78L12AWC and vice versa.

## Price list of new items in this issue

BK68Y	SPCO Nonlock Switch	£1.99
BK71N	10mm Cap Green	6p
BK72P	Membrane Switch	£9.64
BK73Q	Flat Flex Connector	
	7-way	62p
BK77J	Synchime Front Panel	£1.25
BK79L	0.156" 2 x 22 Way P.C. Edgecon	£3.50
FG23A	2 x 28-Way P.C. Edgecon	
B20W	Doorbell P.C.B.	£1.92
GB25C	Code Lock P.C.B.	£2.92
GB29G	Dragon RS232 Interface P.C.B.	£3.62
GB30H	Probe Upper P.C.B.	98p
GB31J	Probe Lower P.C.B.	98p
GB37S	Dragon I/O Port P.C.B.	£2.95
GB38R	Synchime P.C.B.	£1.20
GB42V	Spectrum RS232 Interface P.C.B.	£3.95
LK09K	Mini-lab Kit	£32.50
LK12N	Dragon RS232 Interface Kit	£13.75
LK13P	Logic Probe Kit	£9.95
LK14Q	Code Lock Kit	£19.98
LK15R	Synchime Kit	£10.90
LK18V	Dragon I/O Port Kit	£13.95
LK21X	Spectrum RS232 Interface Kit	£17.95
QY54J	Low Current Display	£2.89
QY55K	MC 14419	£3.86
QY57M	2716/M7	£8.50

## MAPLIN'S TOP TWENTY BOOKS



1. (3) De Re Atari (WG56L) (cat. P62)
2. (2) Games for the Atari by S. Roberts (WA47B) (cat. P62)
3. (1) Audio Circuits and Projects by Graham Bishop (XW46A) (cat. P41)
4. (4) Cost Effective Projects Around the Home by John Watson (XW30H) (cat. P41)
5. (6) Projects for the Car and Garage by Graham Bishop (XW31J) (cat. P30)
6. (11) Remote Control Projects by Owen Bishop (XW39N) (cat. P43)
7. (—) Understanding Telephone Electronics by George L. Fike and George E. Friend (WK45Y) (see note)
8. (5) Master Memory Map (XH57M) (cat. P62)
9. (10) Electronic Security Devices by R. A. Penfold (RL43W) (cat. P40)
10. (8) The 6809 Companion by M. James (WG88V) (cat. P63)
11. (16) The TTL Data Book (WA14Q) (cat. P33))
12. (17) Programming the 6502 by Rodney Zaks (XW80B) (cat. P54)

13. (7) VIC Programmers Reference Guide (WA33L) (cat. P63)
14. (19) How to Use Op-Amps by E. A. Parr (WA29G) (cat. P35)
15. (13) Atari BASIC Learning by Using by Thomas E. Rowley (WG55K) (cat. P62)
16. (—) Radio and Electronics Colour Codes and Data Chart (RH05F) (cat. P30)
17. (15) Electronic Synthesiser Projects by M. K. Berry (XW68Y) (cat. P50)
18. (12) Power Supply Projects by R. A. Penfold (XW52G) (cat. P38)
19. (9) The BBC Micro — An Expert Guide by Mike James (WK04E) (cat. P63)
20. (—) VIC Revealed by Nick Hampshire (WA32K) (cat. P63)

These are our top twenty best selling books based on mail order and shop sales during April, May and June 1983. Our own publications and magazines are not included. We stock over 500 different books to do with electronics and computing and the full range is shown on pages 29 to 65 of the 1983 catalogue, page 15 of issue 6, pages 60 and 61 of issue 7, and of course the new books section of this magazine. Note: For full details of WK45Y please see page 60 of issue 7 of this magazine.

## NEW ITEMS PRICE LIST *Continued from page 37*

Sword of Fargoal (+16K) 1C-KK09K	Price £20.75	HK13P Digital Techniques Trainer	Price £89.95	BK67X Moisture Scale	Price £0.20	LK03D MOSFET Bridging Amp Kit	Price £9.95
Tank Arcade 1C-KH18U	Price £11.95	HK14Q Assembled Digital Techniques Trainer	Price £169.95	GA16S Panic Button PCB	Price £1.25	LK04E Scratch Filter Kit	Price £29.90
Typo 1E-KK18U	Price £29.95	KH15R Microprocessor Course	Price £99.95	GA17T MOS-Amp Bridge PCB	Price £1.96	LK05F DX'ers Audio Processor Kit	Price £14.95
<b>CONNECTORS</b>		HK16S Interfacing Micros Course	Price £99.95	GA96A Programmable Timer PCB	Price £1.49	LK06G Sweep Oscillator Kit	Price £18.95
BK74R 0.156in 2 x 12 way PC Edgcon	Price £2.36	HK17T Advanced Micro Course	Price £99.95	GB09K Modem Main PCB	Price £5.20	LK07H Enlarger Timer Kit	Price £27.50
<b>HEATHKIT</b>		HK18U Microprocessor Trainer	Price £189.95	GB10L Modem PSU PCB	Price £1.75	LK08J ZX81 Modem Interface Kit	Price £24.95
HK01B Digital Digital Alarm Clock	Price £34.95	HK19V Assembled Microprocessor Trainer	Price £329.95	GB11M Sound Generator PCB	Price £2.25	LK10L Crystal Calibrator Kit	Price £16.95
HK02C Informer Alarm	Price £69.95	HK20W Hero Robot	Price £1,599.95	GB12N Inverter PCB	Price £1.99	LK11M VIC20/64/RS232 Interface Kit	Price £9.45
HK03D Infra-Red Alarm	Price £149.95	HK21X Robotics course	Price £99.95	GB13P Scratch Filter PCB	Price £2.20	LW95D Inverter Kit	Price £49.95
HK04E Electronics for Hobbyists	Price £64.95	HK22Y Practice Oscillator	Price £24.95	GB14Q ZX81 TV Sound/Inverse Video PCB	Price £2.20	LW96E Sound Generator Kit	Price £10.95
HK05F DC Electronics Course	Price £49.95	HK23A Dip Meter	Price £79.95	GB17T VIC20 Talkback PCB	Price £3.36	LW97F Panic Button Kit	Price £4.50
HK06G AC Electronics Course	Price £54.95	HK24B Cantenna Dummy Load	Price £29.95	GB18U ZX81 Talkback PCB	Price £2.45	LW98G Programmable Timer Kit	Price £8.45
HK07H Semiconductor Electronics Course	Price £54.95	HK25C Antenna Coax Switch	Price £24.95	GB19V DX'ers Audio Processor PCB	Price £1.90	LW99H Modem Kit	Price £39.95
HK08J Electronic Circuits Electronic Course	Price £64.95	HK26D RF Oscillator	Price £54.95	GB21X CMOS Crystal Calibrator PCB	Price £2.72	<b>SEMICONDUCTORS</b>	
HK09K Test Equipment Course	Price £64.95	HK27E Audio Generator	Price £145.95	GB22Y Sweep Oscillator PCB	Price £3.25	QY39N 4412VP	Price £14.74
HK10L Experimenter Trainer	Price £74.95	HK28F Capacitance Meter	Price £139.95	GB23A ZX81 Modem Interface PCB	Price £4.75	QY43W XR2211CP	Price £4.45
HK11M Assembled Trainer	Price £159.95	<b>MUSICAL &amp; EFFECTS</b>		GB24B Enlarger Timer PCB	Price £3.96	QY50E SP0256	Price £11.98
HK12N Digital Techniques Course	Price £79.95	XG30H Echo Machine EM-006	Price £55.00	GB28F VIC2C RS232 Interface PCB	Price £2.90	QY52G 2716/M6	Price £8.50
		<b>PROJECTS AND KITS</b>		LK00A VIC20 Talkback Kit	Price £24.95	QY53H BF173	Price £0.41
		BK66W Modulator UM1286	Price £11.90	LK01B ZX81 Talkback Kit	Price £19.95	<b>WOUND COMPONENTS</b>	
				LK02C ZX81 TV Sound and Inverse Video Kit	Price £19.95	XG29G Inverter Transformer	Price £22.50



# CLASSIFIED

## VARIOUS

**MAPLIN STEREO** cassette deck kit (P.234 in catalogue). PCB's assembled, otherwise unbuilt, vgc, including all packing and accessories, cost £40. Sell £25. Tel. Bristol (0272) 772965).

**100 ELECTRONICS** magazines for sale, consisting 62 Practical Electronics, 31 Practical Wireless, 7 Elektors. Offers invited. Phone Pete (Formby 79388).

**A.S.R.33 TELETYPE** with papertape, £50 ono, connoisseur BD2 turntable M75ED2, vgc, £30; Lowrey TG1 organ, immaculate, £400. Caterham 47784 after 7 p.m.

**SX 200** scanning monitor receiver 12v input, complete with brackets for mobile use, set top antenna, large scale circuit diagrams incl. modification and instruction booklet, £125. 0695 31614.

**538A KIKUSUI** 5MHz oscilloscope, hardly ever been used, still in box. Interests changed to computing. Swap for 16K Spectrum or offers. M. Swanson, High Street, Spilsby, Lincs.

**FOR SALE**, Practical Wireless, April 1972 to April 1981, £25 ono. Can deliver locally. Tel. Fence Houses (Durham STD) 854734.

## MUSICAL FOR SALE

**MIXER FRONT** panel, Allen & Heath 16 into 4 into 2 studio mixer, fully punched & legended; £20. Canvey 694900.

**MAPLIN S600S** synthesiser, professionally built, cash needed so only £100 more than component value. £700 ono. 0264 4850 (Andover).

**KORG MS10** synthesiser, as new, with guarantee, £200; swop for BBC A/B micro in good condition, 16K ZX81. Lots of hardware, £100. 36 Sunningdale Avenue, Lowestoft, Suffolk. Tel. (0502) 64729.

If you would like to place an advertisement in this section then here's your chance to tell Maplin's 180,000 customers what you want to buy or sell, absolutely free of charge. We will publish as many advertisements as we have space for. To give everyone a fair share of the limited space, we will print 30 words free of charge. Thereafter the charge is 10p per word. Please note that only private individuals will be permitted

to advertise. Commercial or trade advertising is strictly prohibited in the Maplin Magazine. Please print all advertisements in bold capital letters. Box numbers are available at £1.50 each. Please send your advertisement with any payment necessary to: Classifieds, Maplin Mag, P.O. Box 3, Rayleigh, Essex SS6 8LR. For the next issue your advertisement must be in our hands by 5th October 1983.

**MAPLIN 5600** synth. kit, complete order without components and cabinet, PCB's, mounting brackets, front-rear panels, hinges, book, still unpacked. Catalogue price £68. Sell £30. Phone 01-840 4336.

**CRUMAR STAGE** piano, 60 note, 3 voice, sustain pedal, case and stand, ideal for group, home or studio, £150 ono. Banbury 720056.

**FOR SALE** electronic organ, Casio 403, plays 25 different instruments, 16 rhythms, plus much more. Still under guarantee. £200 ono. Tel. 01-891 3079.

**ALAN DOUGLAS** electronic organ (dismantled), 2.6in manuals, all coils, chassis, generators, valves, frame, room wanted, buyer collects, £30. Tel. 061 761 2952.

## COMPUTERS FOR SALE

**MZ80K 48K** 48k, with Basic and Pascal, manuals and software, £300 ono. 15 Stramane Close, Brant Road, Lincoln. Lincoln 42036.

**VDU-FERRANTI** with green display, ideal as monitor and keyboard. Documentation supplied. Includes high current psu 5v and #12V, £50 ono. Tel. Orpington 71317.

**ZX81 #16K** with sounder, + Zonix prog. Sound generator + manual/books/tapes all nearly new, £89. Peter Cunningham, 11 Berwyn Ave., Penyffordd, near Chester. Tel. Caergwile 760172.

**ATARI 400 16K** program recorder, basic cartridge, many books, magazines, manuals. Four game cartridges. Lots of extras including joysticks. Cost £450+, sell for £350 ono. Tel. 0375 672077.

**NASCOM 2** with NAS-SYS 1, 16K memory, wooden box, two available at £150 each. Foulds, 42 Cotswold Avenue, Ipswich. Tel. 214004.

**MAPLIN ZX81** Talk-Back un assembled for sale or exchange with ZX81 or ZX80 assembled or un assembled. Offers. Hamid Reza Tajzadeh, 4th Floor, No. 11 Street, No. 3, Noarmack Tehran 16479, Iran.

## CLUB DETAILS

**ALWAYS WELCOME**, new members to help support free enterprise in space, promote space exploration and oppose the moon treaty. For further information write to Free

Space and Space Settlers Society(MM), c/o Christ Forrest, 8 Barton Bridge Close, Raglan, Gwent.

**UNIQUE** non-commercial scheme helps with the purchase, sale and exchange of Atari VCS cartridges. Pilot scheme by Atari enthusiasts for all Atari users. S.A.E. for details to The Secretary, V.G.E.S., 25 Rona Road, London, NW3 2HY.

## WANTED

**WANTED URGENTLY** manual/circuit any data (or loan for copy and return), postage refunded. For Furzeehill Oscilloscope type 0100 (1956). P. Merriman, 41 Wattleton Road, Beaconsfield, Bucks, HP9 1SD.

**WANTED CIRCUIT** diagram of a single channel on/off radio control system to operate on any frequency. Mr. D. Corder, Low Weasdale, Newbiggin-on-Lune, Kirkby Stephen, Cumbria.

**FIELD TELEPHONES**, pair wanted, any type, including handset, bell and hand-generator. Preferably USA type EE8 in leather case. Phone 0234 67729 (Sundays).

**TRANSCENDENT 2000** required, must be in good condition, unfinished kits considered. £56. Mr. C. Fyson, 17 Kitchener Road, Hampton Park, Southampton, Hampshire SO2 3SF.

**WANTED** audio pre-amp I.C. (number Nikko G0003) and circuit diagram/service manual for Nikko TRM 30-amplifier. Would consider complete amplifier.

Contact Andy Bryson 26 South Crescent, Adrossan, Ayrshire (0294-63829).

**WANTED: INFORMATION** on I.C. No. A-Y-1224A (Digital Clock), am having very great difficulty in obtaining this particular chip. Contact S. R. Jefferies, 47, Nutfield Road, Coulsdon, Surrey CR33JP. 01-668 2833.

# EXHIBITION NEWS

Maplin are pleased to announce that they will be exhibiting at no less than three different shows over the next few months. In addition to all our normal displays of computers and software we will have, on show for the first time, our new robot, Hero 1. Hero can see, speak, detect moving and stationary objects and determine their distance, pick up small objects, move in any direction, and learn from your instructions. He will be meeting the public at selected times throughout the shows, and would be very pleased to make your acquaintance.

The Maplin Modem will also be working, together with a demonstration of Maptel and Cashtel, the Maplin shopping-by-computer system that points the way to the future, allowing you to buy goods and access information 24 hours a day.

A representative of the Atari User Group will be on hand to answer questions at all three

shows, and the latest issue of the User Group magazine will be on sale.

The Great Home Entertainment Spectacular is the first of the shows, and printed on this page you will find a voucher worth £1 off the

normal price of your entrance ticket. The show organisers have planned a series of competitions and games, treasure hunts, live performances, product demonstration, and computer games, so there should be something for everyone. The

show is open from 11.30 am to 9.00 pm every day except Monday, when it will open at 5.00 pm, and it runs from the 17th to the 25th of September at Olympia, London. Tickets are £3 adults, £2 children.

From the 29th of September to the 2nd of October we have the second in our series of shows, the 6th Personal Computer World Show, at the Barbican, London. Opening hours are from 10.00 am to 7.00 pm every day except Sunday, when the show closes at 5.00 pm. Tickets are priced at £3 for adults, £2 for children.

Finally, we have the Electronic Hobbies Fair at Alexandra Palace, London, from October the 27th to the 30th. The show is open from 10.00 am to 6.00 pm every day except Sunday, when closing time is at 5.00 pm. Tickets are priced at £2.00 for adults, £1.00 for children.

We look forward to seeing you.



## Ups and Downs

It is usually only the more interesting space shots which attract the attention of the news media. This often gives the impression that satellite launches are few and far between, with perhaps the odd Space Shuttle launch now and then. Nothing could be further from the truth, for there are many launches of all manner of craft throughout the year. Most of these are put up by the Big Two, America and Russia, but quite a few launches are made by countries such as Japan, India and, of course, Britain. Some indication of the numbers involved may be obtained from the following; in December of last year the Russians launched seven satellites of various types, and of the total of 121 launches during 1982, 101 were Russian, 18 from the USA, 1 from Japan and 1 from China.

Most of the Soviet satellites were military in nature, ranging from the surveillance devices mentioned in a previous issue to communications satellites. Such activity is not an unusual event, for during January of this year, the Russians launched another four rockets; one of these is particularly interesting, since it carried aloft a batch of no less than eight small military communications satellites.

It should be no surprise to find the Japanese active in the business of satellites, and doubtless they see it as another area to exploit with their usual acumen. The first Japanese satellite launched in 1983 was a communications satellite, launched from the Tanegashima Space Centre near Takazaki on the 4th February. This was followed by an astronomical satellite, Astro-2, launched on the 20th February from the Kagoshima Space Centre. This last satellite will be used for detecting and monitoring celestial X-ray sources.

With all these satellites going up it is not surprising that there are many that come down. Some of these come down of their own accord, due to the decay of a relatively low orbit, whilst some are brought down deliberately. These, of course, are the military surveillance satellites which are recovered in order to retrieve the information they contain without divulging the contents by transmitting it over a radio link. During December 1982 and January and February 1983, fourteen space-craft were recovered or re-entered, most of them of Russian origin.

## Amateur Satellites

Many radio Hams will be waiting with anticipation for the launch of the latest amateur satellite, the so-called Phase 3-B, aboard the Arlane launch vehicle. Some readers may recall that the last attempt to use this launcher to put a payload aloft ended with the whole lot splashing down in the Atlantic. This was attributed to a breakdown in the third stage turbo-pump. As a consequence, the launch of the next mission has been put back while this component is rigorously checked over in order ensure that there is no repetition of such an expensive failure. The amateur satellite will again be going as a 'piggy-back' payload, the main satellite in this case being the European communications satellite, ECS-1.

If this launch proves to be successful, and by the time you read this it should have gone, then another satellite will be available for amateur use, which will then be known as OSCAR 10.

The prior satellite to this one, OSCAR 9, is still not completely out of the woods. This 'bird' is rather different from other amateur satellites, in that it carries scientific experiments and no transponders. A transponder is a sort of space repeater, used for re-transmitting radio signals over large dis-



# Say it with SATELLITES

by Mike Wharton

tances. Unfortunately, complete control has not been regained since it came back on the air, and it must be feared that its orbit will decay beyond the point of no return before it is able to realize its full potential.

## Space Astronomy

The number of satellites dedicated to research from the vantage point of space continues to increase. During May this year a satellite was launched by the European Space Agency, ESA, to study distant X-ray sources. Called EXOSAT, its two-year mission will be to observe some of the most unusual and violent events in the known Universe. For example, it is intended to be used to examine the disappearance of matter into 'black holes' as well as the massive out-pouring of X-rays from some of the remote radio galaxies. One particular feature of this craft is its ability to be pointed at these sources to an accuracy of one thousandth of a degree of arc, which is claimed to be some fifty times better than hitherto achieved.

Another similar space-craft, but one which is observing a completely different part of the electro-magnetic spectrum, is the Infra Red Astronomical Satellite, IRAS. A


recent achievement of this craft was the detection of a comet, which eventually became visible to the naked eye; in recognition of this the comet was named IRAS-Araki-Alcock. This craft was mentioned in a previous article, and the supply of liquid helium used to cool the infra-red sensors seems to be holding up well and it has provided a great deal of information to astronomers on this part of the spectrum.

## Space Shuttle

The next scheduled flight of the American Space Shuttle will be in the autumn this year. The primary aim of this flight will be to carry the joint U.S.-European Spacelab aloft. One of the interesting aspects of this flight is that NASA has given the go-ahead for one of the crew, Dr. Owen Garriott, to take an amateur 2-metre band transceiver with him. Thus it will be possible for radio amateurs all over the world to make contact with the call 'CQ from W5LFL aboard the Space Shuttle', for W5LFL is Dr. Garriott's amateur call-sign. Exactly how successful this proves to be only time will tell, and certainly one of NASA's stipulations is that any transmissions must not interfere in any way with the planned mission of the Space Shuttle.

Maplin Magazine September 1983

ECS

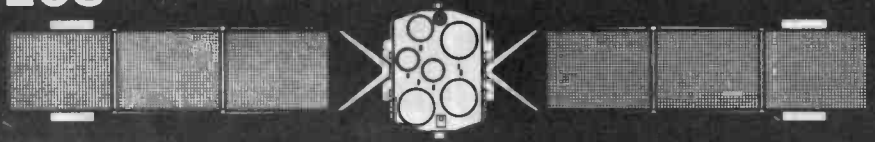


## DBS—the continuing story

Finally, a few words on the latest developments in Direct Broadcasting by Satellite. This service is the one which is already enjoyed on a somewhat limited basis in some parts of the world, and which is intended to be available in Europe by the end of 1986. The satellite which will carry the TV signals is Olympus (previously L-Sat) presently being built by the British Aerospace Corporation. The U.K. has been allocated five d.b.s. channels in the 12 GHz band and the first two of these will be made available for two new BBC programme services. The three remaining U.K. d.b.s. channels will, no doubt, be allocated in future years. The channel bandwidth available with this system is around 10 MHz, which is appreciably larger than the 5.5 MHz offered by terrestrial

transmissions. This has led to suggestions that the extra bandwidth should be used to improve the definition of the system. There are several ways in which this could be done; one method would use the same number of lines and frames as at present, 625 and 50 fields per second, but circuitry in the receiver would store the video information and enable the production of a picture with 1250 lines or 100 fields per second or possibly both. Although there is no more information transmitted, a display with much less line structure and free from flicker could be visually more pleasing. The longer term goal is to transmit true high-definition television (h.d.t.v.), where the picture would actually be generated and transmitted on higher line and field rates, and hence would genuinely contain more information. The difficulty here is that real h.d.t.v. requires a bandwidth of about 30 MHz and is thus beyond the capacity of the presently planned channels in the 12 GHz band.

Some may wonder if all this activity is not going to be overshadowed by developments in cable TV. Although cable TV, whether distributed by optical fibre or coaxial cable, does give some freedom from the bandwidth restrictions, the development of such systems must be regarded as a long-term project and as such it is almost impossible to put a time scale on them. On the other hand, satellite TV is almost upon us and is immediately available to everyone, with a suitable TV that is, which cable TV will not be.

ARIANE

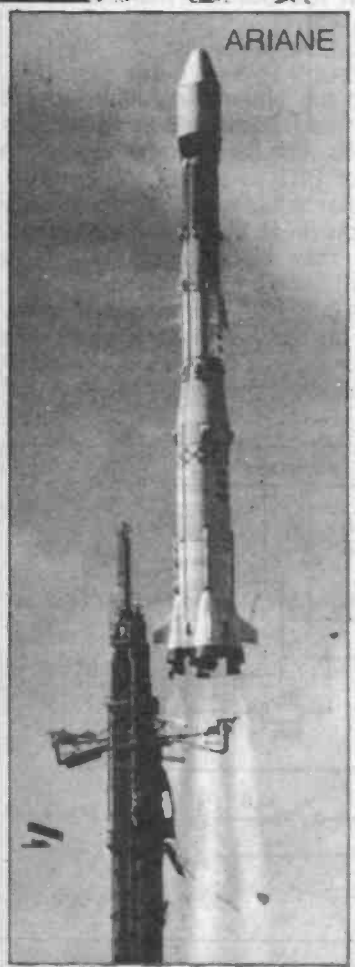

- ★ Attracts attention with or without noise
- ★ Uses existing doorbell components
- ★ Simple to instal

# Doorbell for the Deaf

by Garfield Dean

For the hard of hearing or the deaf a doorbell is obviously useless. This circuit is an attempt to increase the chance of getting the attention of a deaf person by flashing a light or lights on and off several times in the deaf person's room(s). Also the bell can be made to ring several times for the benefit of anyone who is only hard of hearing and also for the person who pushed the bell switch.

## Circuit Description

Figure 1 shows a typical doorbell system. Figure 2 shows the circuit for the doorbell for the deaf which uses all of the existing hardware. There are two 7555 timers, the first of which is in monostable mode with a period of about 2-20 seconds determined by RV1, R2 & C2. When the push switch is pressed, the output of IC1 goes high for 10 seconds and this enables IC2 to work in a stable mode (i.e. oscillate) at a rate of once every two seconds set by C3, R3, R4 & RV2. IC2 turns the relays on and off which in turn switches the bell and lights on and off about 5 or 6 times. A 5A fuse is included in the lighting circuit for safety. S2 disengages the bell relay if, for example, children are sleeping. S1 disengages the light relay if it is necessary that the lights don't flash, e.g. for a photograph. also this allows normal doorbell operation simply by turning S1 off and setting RV1 to give one ring per push. D1 prevents large back EMFs from the relays destroying the rest of the circuit.

Note that the 7555 timer has been used instead of the 555 timer, because of the long time constants involved and for the lower power consumption in standby mode (useful if the circuit is battery operated).

The P.S.U. is the easiest part of the circuit but may need the most careful looking at, depending on the existing doorbell. If you have no doorbell at present or if your doorbell power supply is not suitable (see below) then the circuit for the power supply in figure 3 will work. BR1 rectifies the 8V A.C. and

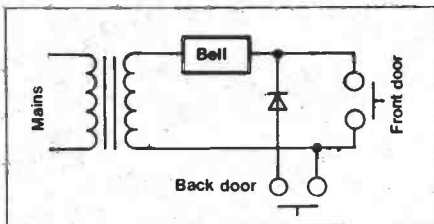
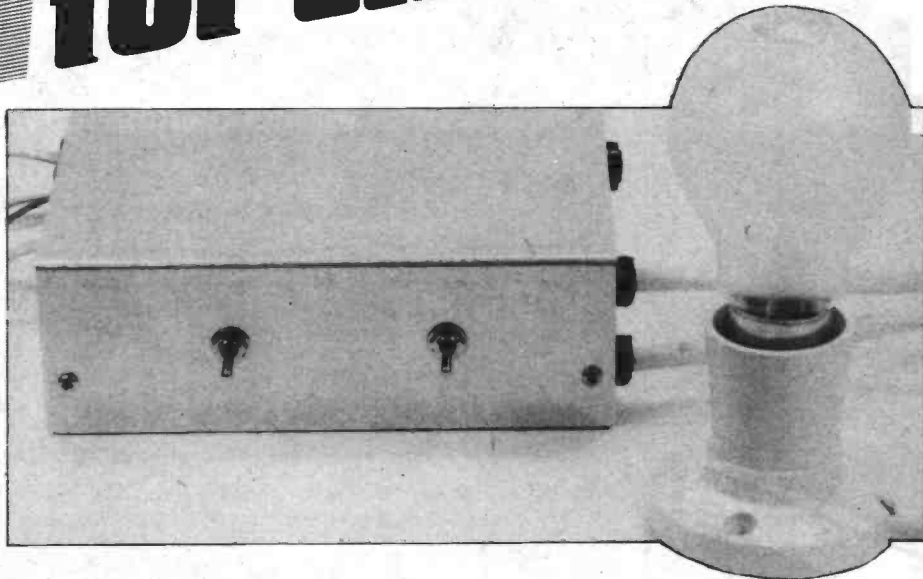


Figure 1

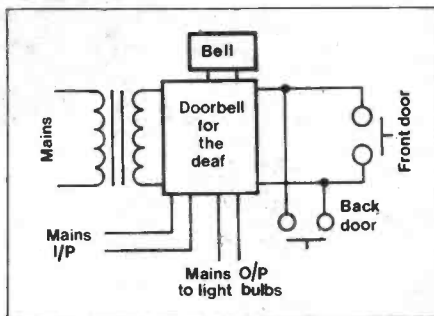


Figure 1a

this is then smoothed by C1. IC3, C4 & C5 provide extra smoothing and voltage dropping if required. D2, if fitted, prevents wrong connection by a D.C. supply. With the Maplin transformer the regulator is not used and a wire link is used in the position marked for D2 (Figure 4b).

A suitable supply is:

a) D.C. 9-15V — In this case BR1, C1 and the optional regulator should not be fitted. D2 should be fitted as in figure 4b. Also links should be fitted in place of BR1 as shown in figure 4c. (Note that batteries will run down every 6 months or so, and therefore a transformer may be a better long term solution).

b) A.C. 8-12V — From a Bell Transformer (as this is built for the job). The power supply is built as if using the Maplin transformer; but make sure that

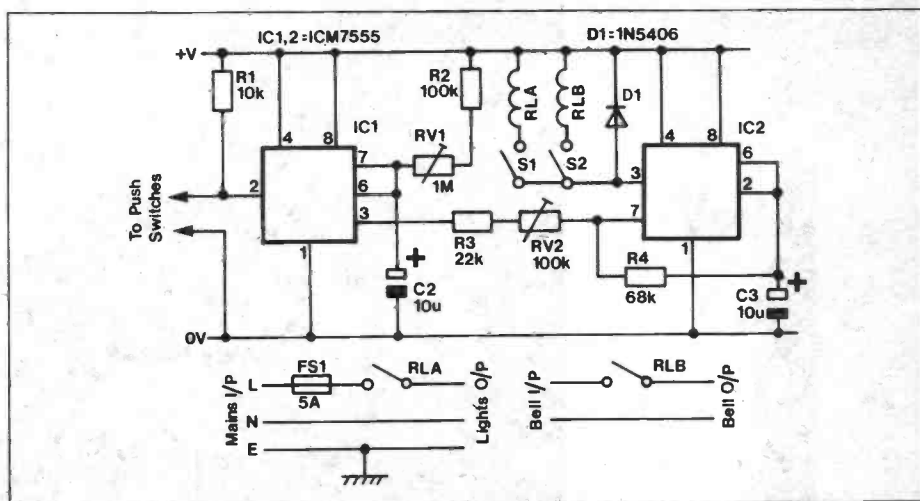


Figure 2. Circuit diagram.

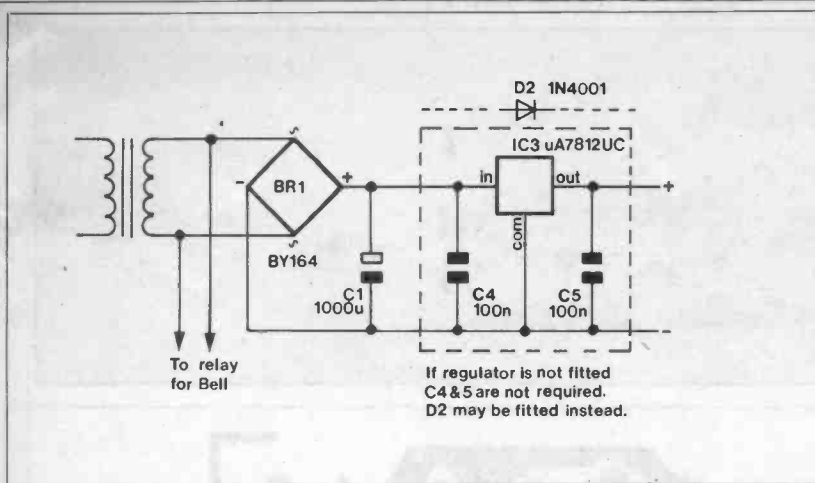


Figure 3. Power supply.

the connections to the bell (via relay B) come from the pair of transformer windings that the bell was originally connected to.

c) A.C. 12-20V — From a Bell Transformer. The power supply is built as for the Maplin transformer but uses the optional regulator section. Also connections to the bell (via relay B) should come from the pair of transformer windings that the bell was originally connected to.

## Constructional Details

The P.C.B. should be built up as in figure 6 by soldering in components in order of increasing height, inserting veropins into the low voltage output holes. Remember that you will only need to use some of the components listed for your type of power supply.

Check the P.C.B. after completion, especially for solder blobs, dry joints and correct polarity of devices; an electrolytic capacitor connected the wrong way round makes a nasty mess when it blows up. The unit is now ready for testing. Temporarily short across each of the two sets of contacts going to the switches S1 and S2.

Put RV1 and RV2 in their mid-positions and temporarily connect the input to the P.S.U. Give a trial push of the doorbell by shorting the two veropins for the bell push together. Both relays should click on and off several times. RV1 adjusts the total length of time the doorbell operates for after a bell push. RV2 adjusts the length of time between individual flashes of the lights (should these need frequent alteration then potentiometers can be used).

If the unit does not work there are 3 main things to check:

- 1) Is the voltage across IC1 pins 1 and 8 between 9 and 16V? If not then the power supply is at fault.
- 2) If the output of IC1 does not go high for 2-20 seconds when the bell is pushed, then IC1 or an associated component are at fault.
- 3) If the output of IC2 does not oscillate between positive and negative supply when IC1 output goes high, then IC2 or an associated component is at fault.

The P.C.B. will now be ready to be fitted into a case. For a functional unit an AB13 case can be used, but for a


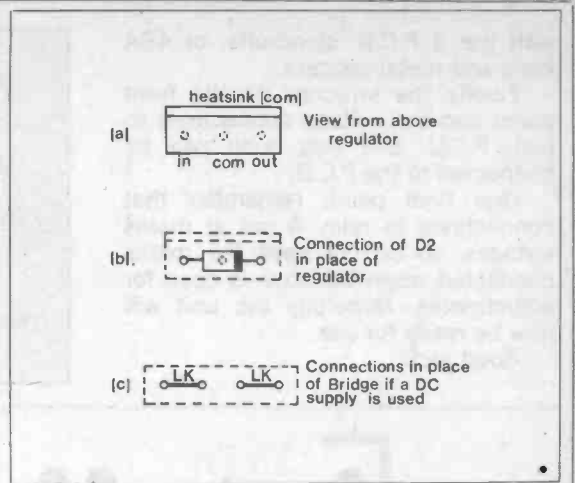


Figure 4.

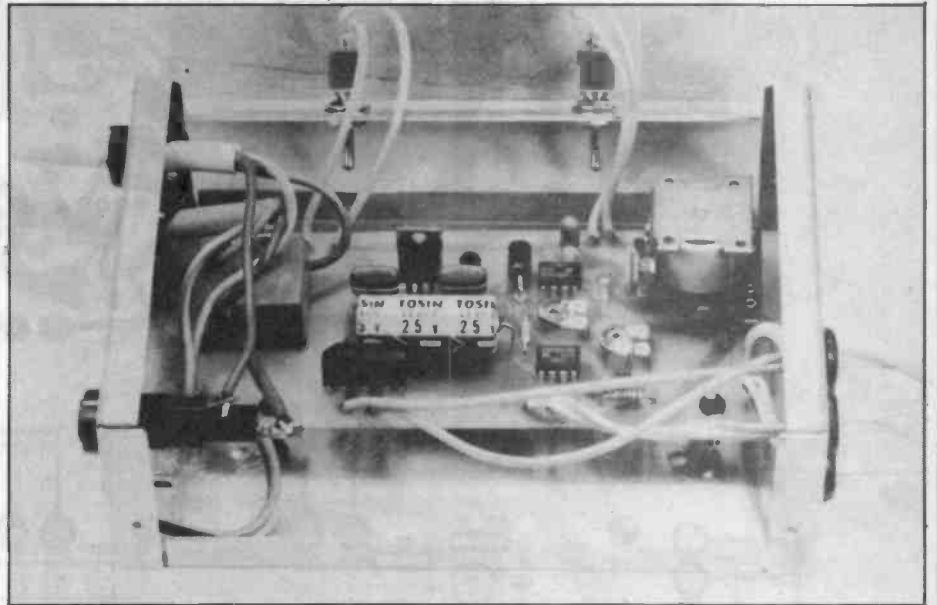

more attractive finished product a type 215 Verocase should look better. A suggested set of drilling details for an AB 13 case are shown in figure 5.

When drilling is complete, fit grommets and the fuse holder where marked and insert the mains wires coming from

outside the unit.

Solder these wires directly to the P.C.B., along with an extra earth lead, connected to a solder tag which should be attached to the case with a 4BA bolt and shakeproof washer.

Then fix the P.C.B. down to the case

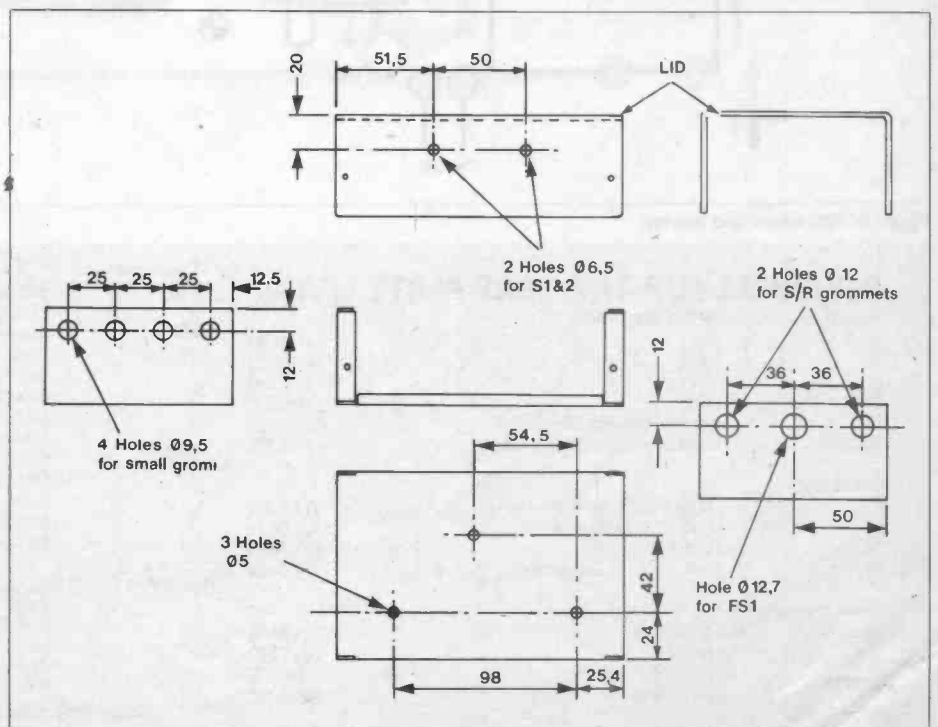


Figure 5. Drilling instructions.

with the 3 P.C.B. stand-offs, or 4BA bolts and metal spacers.

Finally the switches on the front panel and low voltage connections to bell, P.S.U. and bell push can be connected to the P.C.B.

One final point: remember that connections to relay A are at mains voltage's, so do not have the mains connected when the case is open for adjustments. Hopefully the unit will now be ready for use.

Good luck!

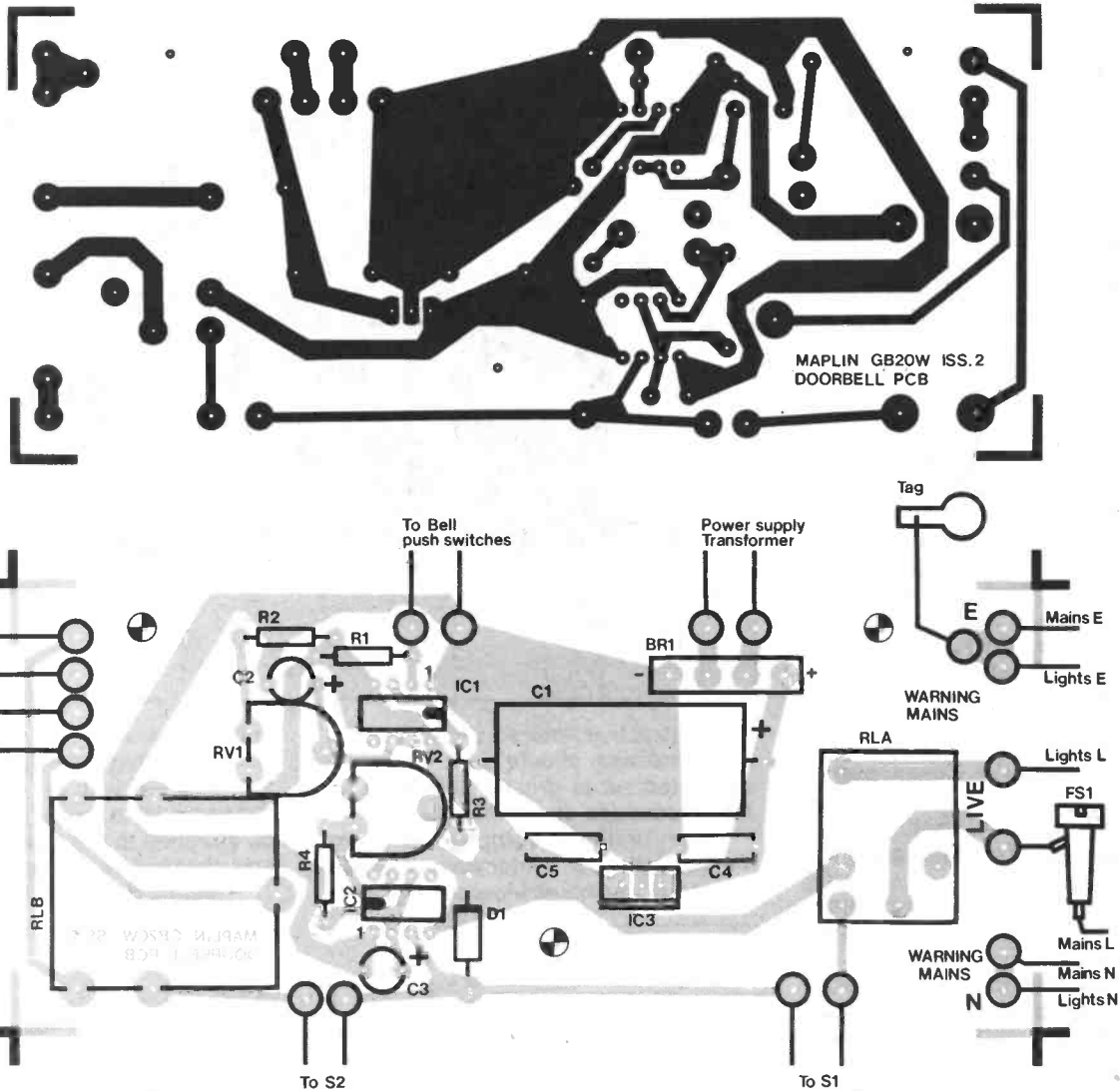
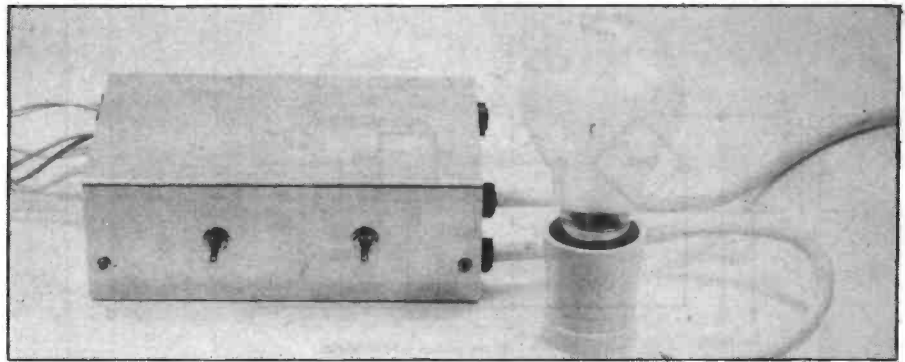


Figure 6. PCB layout and overlay.

## DOORBELL FOR THE DEAF PARTS LIST

Resistors — All 0.4W 1% Metal Film

R1	10k	(M10K)
R2	100K	(M100K)
R3	22k	(M22K)
R4	68k	(M68K)
RV1	1M Hor-sub min Preset	(WR64U)
RV2	100K Hor-sub min Preset	(WR61R)

Capacitors

C1	1000uF 25V Axial Electrolytic	(FB83E)
C3	10uF 25V Tantalum	(WW69A)
*C4,5	100nF Polyester	2 off (BX76H)
C2	22uF 16V PC Electrolytic	(FF06G)

Semiconductors

D1	1N5406	(QL85G)
*D2	1N4001	(QL73Q)
IC1,2	ICM7555	2 off (YH63T)
*IC3	uA7812UC	(QL32K)

Miscellaneous

S1,2	Sub-min Toggle A	2 off	(FH00A)
RLA	10A Mains Relay		(YX97F)
RLB	Open Relay 6V		(FX23A)
FS1	Fuse 5A 20mm Safefuseholder 20		(WR07H)
	Grommet small	4 off	(RX96E)
	SR Grommet 6W-1	2 off	(FW59P)
	Stand-off Short	3 off	(LR49D)
	BY164		(FW16S)
*BR1	Doorbell PCB		(QF43W)
	Case AB13		(GB20W)
	Mains Cable	As reqd	(LF14Q)
	Veropin 2141	1 pkt	(XR03D)
			(FL21X)

If there is no existing doorbell, suitable components are:—

Bell	(FL38R)
Bell Transformer	(FL37S)
Bell Push	(FQ08J)
Bell Push + Nameplate	(FQ09K)
Wire to bell push	(XR39N)

Note components marked \* may or may not be used, see text.

# New Books

## Practical Electronic Building Blocks Book 1

by R. A. Penfold

Virtually any circuit will be found to consist of a number of distinct stages when analysed. Some circuits are specialised, but in most cases they are built up from building blocks of standard types. This book is designed to aid electronics enthusiasts who like to experiment with circuits and produce their own projects, and gives the circuits and produce their own projects, and gives the circuits for a number of useful building blocks with details of how to change the parameters of each circuit to suit individual requirements where relevant.

1983. 110 pages. 180 x 110mm.

Order As WK51F (Book BP117)  
Price £1.95 NV

## Practical Electronic Building Blocks Book 2

by R. A. Penfold

This is the sequel to Book 1, and follows much the same pattern using different circuits. The two books do not overlap, and have been specifically written to complement each other, Book 1 dealing mainly with circuits to generate signals and Book 2 with circuits that process them.

1983. 94 pages. 180 x 110mm.

Order As WK52G (Book BP118)  
Price £1.95 NV

## The Pre-Computer Book

by F. A. Wilson

Aimed at the absolute beginner with no knowledge of computing, this entirely non-technical discussion of computer bits and pieces and programming is written mainly for those who do not possess a microcomputer but intend either to one day own one or simply wish to know something about them. Also highly recommended for the new computer owner who may be beset with uncertainties and, also, the person who cannot understand the jargon and technical terms used by most manufacturers in their sales leaflets.

1983. 78 pages. 180 x 110mm.

Order As WK50E (Book BP 115)  
Price £1.95 NV




## Mastering the Colour Genie

by Ian Sinclair

This book covers the BASIC of the Colour Genie, including the use of the colour graphics and sound, as well as the very comprehensive set of data filing/handling instructions. A whole host of programs are illustrated for you to enjoy as you become more proficient and able. You are shown how to write your own programs so that you are soon in command of this powerful machine.

1983. 148 pages. 234 x 155mm.

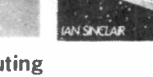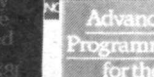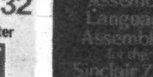Order As WK54J (Master the Colour Genie)  
Price £6.95 NV



## Assembly Language Assembled for the Sinclair ZX81

by Anthony Woods

The ZX81 does not allow you to enter assembly language programs directly, they have to be translated into machine code before they will run. There is, however, a software solution. One company has produced the ZXAS assembler and ZXDS disassembler programs which can be used to translate assembly language automatically to and from machine code, using standard Zilog mnemonics. This book has been designed especially for use with these programs. At the same time, it is structured in such a way that the reader can learn to program in assembly language just as easily as they learnt BASIC.

1983. 154 pages. 234 x 153mm.

Order As WK60Q (ZX81 Assembly Language)  
Price £7.65 NV

## The Complete Spectrum ROM Disassembly

by Dr Ian Logan & Dr Frank O'Hara

Every routine in the ROM has full comments on what its function is and how it relates to the other functions in the ROM. Overall, the 16K ROM program offers an extremely wide range of BASIC functions and commands, and this book makes all the functions and entry points available for use in your own programs or for modifications into special routines.

1983. 232 pages. 214 x 141mm.

Order As WK57M (Spectrum ROM Disassembly)  
Price £9.95 NV

## The Dragon 32 Games Master

by Keith & Steven Brain

This book shows you how to write your own top class games, taking you line-by-line from the first principles of writing the simplest games right through to the design, construction and testing of adventure games which can rival commercial software in complexity and presentation.

1983. 200 pages. 239 x 152mm.

Order As WK58N (Dragon, Games Master) Price £7.40 NV

## Lynx Computing

by Ian Sinclair

Aimed at all users, this book starts at the very beginning with how to set up the machine. It then goes on to guide you step-by-step until you become sufficiently expert to write your own programs and start using your machine creatively. Many useful programs are included and you will continue to find the book useful as a handy reference even after you have mastered all the techniques.

1983. 148 pages. 234 x 155mm.

Order As WK55K (Lynx Computing)  
Price £7.85 NV

## Discovering BBC Micro Machine Code

by A. P. Stephenson

You can unlock your micro's latent powers with machine code, generate fast-moving graphics, make more effective use of peripherals and ancillary equipment, save precious memory and get to know your machine better. This book will show you how to get started, using many short programs and routines.

1983. 148 pages. 234 x 155mm.

Order As WK56L (BBC Machine Code)  
Price £7.85 NV

## Advanced Programming for the 16K ZX81

by Mike Costello

A description of the techniques that can be applied to the ZX81 in order to overcome some of its inherent limitations. This involves some investigation of the ZX81's operating system, discussion of BASIC sub-routines, as well as details of the application of Artificial Intelligence techniques to programming for the ZX81. Later chapters are devoted to the use of assembly language programming techniques, hybrid programming techniques, hybrid programming — mixing BASIC with machine code, and developing utility programs to suit the user's own particular needs.

1983. 126 pages. 234 x 153mm.

Order As WK59P (Advanced 16K ZX81 Programming)  
Price £6.55 NV

## BASIC and PASCAL in Parallel

by S. J. Wainwright

This book takes the two languages and develops programs in both simultaneously. Emphasis is placed on structured programming by the systematic use of control structures; and modular program design is used throughout. Example programs are used to illustrate the program structures as they are introduced, and the reader can learn by example. As the title suggests, the book is intended as a bilingual introduction to programming which can be used to learn both languages simultaneously, and to learn programming techniques which are compatible with both languages.

1983. 60 pages. 180 x 110mm.

Order As WK53H (Book BP126)  
Price £1.50 NV

## Electronics For Technicians

by G. D. Bishop

A comprehensive basic reference text for the fast-changing world of electronics. The book is designed to cover all the electronics content of the revised T.E.C. Certificate and Diploma programmes, fit a wide range of related courses including C.S.E. and 'O' level electronics, suit first-year degree courses and those fresh to the world of electronics. It includes a number of large clear diagrams supporting the text, together with photos where necessary. The text follows the pattern of the associated T.E.C. unit syllabus, but it has been extended where necessary to create a comprehensive electronics text.

1983. 134 pages. 234 x 202mm.

Order As WK61R (Electronics for Technicians)  
Price £5.95 NV

## The Commodore 64 Programmers Reference Guide

This tells you all you need to know about your Commodore 64. The perfect companion to the User Guide, the manual presents detailed information on every thing from graphics and sound to advanced machine language techniques. This book is a must for all CBM 64 owners. Comes complete with circuit diagram.

1983. 486 pages. 216 x 135mm.

Order As WK62S (CMB64 Programmers Ref Guide)  
Price £13.25 NV

## How to Design and Make Your Own PCBs

by Robert Penfold

This book should enable you to familiarise yourself with both the simple and more sophisticated methods of producing PCBs. The emphasis is very much on the practical aspects of design and construction, and is highly recommended to all newcomers to electronics.

1983. 66 pages. 177 x 110mm.

Order As WK63T (Book BP121)  
Price £1.95 NV

# FIRST BASE



by Mike Wharton

## A Beginner's Guide to Logic Design Part 3

### Solution to Problem

If you recall, there was a little problem left for you to sort out in the last section. This was to deduce the Truth Table of an array made up of two-input NAND gates, and the result which you should have arrived at is given in Fig. 1. Comparison of this table with published ones will show it to be that of the Exclusive-OR gate, (EX-OR). The common symbol for this gate, also known as the Difference gate, is shown in Fig. 2a. It is called the Difference gate since a look at its Truth Table will reveal that the output is high only when the inputs are different; the complement of this gate is the Exclusive-NOR gate, (EX-NOR), whose symbol is shown in Fig. 2b. This gate is also known as an Equivalence gate, since its output is high when the inputs are the same, and the Truth Table for this gate is shown in Fig. 3.

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

Figure 1. Derived truth table for 2 input Exclusive OR gate.

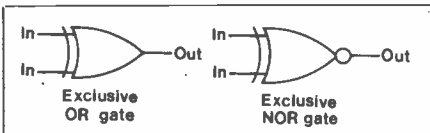


Figure 2. Symbols

A	B	C
0	0	1
0	1	0
1	0	0
1	1	1

Figure 3. Truth table for Exclusive NOR gate

It would be possible to produce an EX-NOR gate by adding an inverter to the output of the previous EX-OR gate made up from NAND gates, thus using a total of five 2-input NAND gates. This would be quite wasteful of gates, and not surprisingly it is possible to obtain both of these devices in a single package. Thus Fig. 4a. shows the pinout of the 7486, a quad 2-input EX-OR gate package, and Fig. 4b. gives the pinout of the 74266, the EX-NOR gate package.

This now completes the list of main logic gates, although there are a few others which

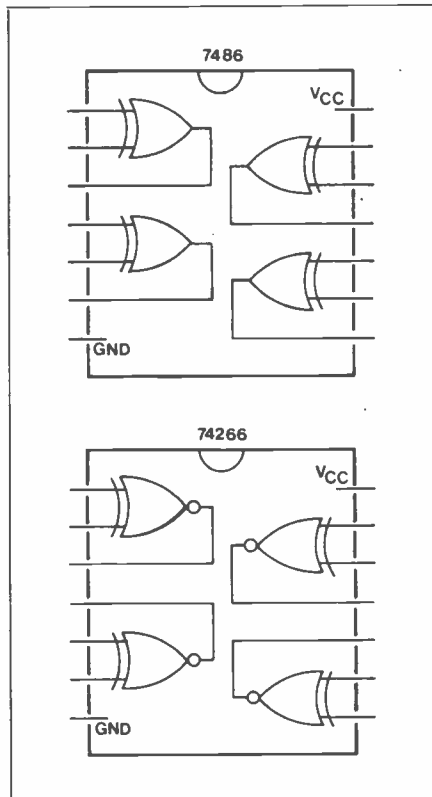


Figure 4. Pinouts

can be obtained, but these really combinations of the above types in order to obtain 'programmable' gates in the one package. An example of this is the 7451 AND-OR-INVERT gate, shown in Fig. 5; here it may be seen that the package contains two AND gates connected to the input of the NOR gate. It is left as an exercise for the reader to derive the Truth Table for this arrangement of gates.

### Multi-input gates

So far we have really only concerned ourselves with gates having one or two inputs. Many of the devices available have more than this, as a glance at the relevant pages of the Maplin Catalogue will reveal. For example, the 7430 is an 8-input NAND gate, shown for reference in Fig. 6 along with its Truth Table. Fortunately, this does not make the understanding of these gates that much more difficult. If you look back at the previous Truth Tables, as well as the one for the 8-input NAND gate, you will see that they all have a unique output state. An exception to this rule are the Truth Tables for the EX-

OR and EX-NOR gates, which are special cases. The other gates have just one value of logic output for a particular set of inputs; for example, in a 2-input AND gate the output is always low except when both inputs are high. In a 2-input NAND gate, the output is always high, except when both inputs are high, and this follows on for the 8-input NAND gate, where the output is always high except when all the inputs are high.

That this is so can be tested by connecting up a 7430 on a bread-board with a


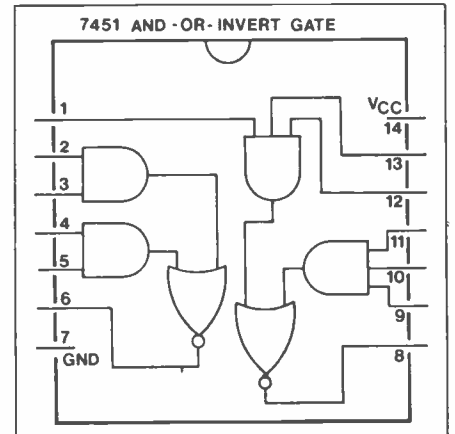


Figure 5. Pinout

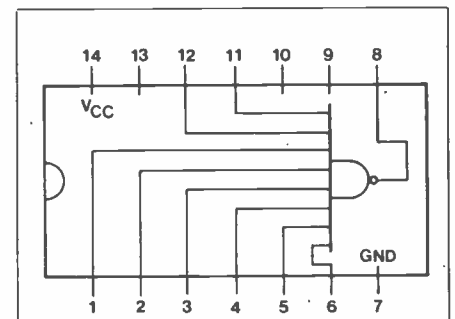

7430 8 INPUT NAND GATE

A	B	C	D	E	F	G	H	O
0	0	0	0	0	0	0	0	1
1	0	0	0	0	0	0	0	1
0	1	0	0	0	0	0	0	1
etc								
0	0	0	0	0	0	0	1	1
1	1	1	1	1	1	1	1	0

Figure 6. Pinout and truth table



LED wired to the output, as shown in the last issue. If each of the inputs is connected to logic 1 then the output will be found to be at logic 0, with the LED extinguished. If one of the inputs is now taken to logic 0, then the LED will light up, and will remain alight while any number of inputs are held at logic 0.

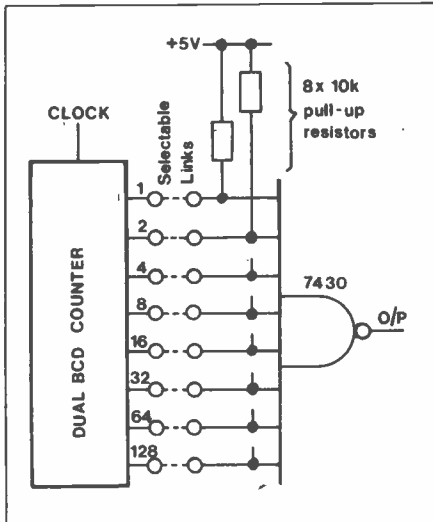


Figure 7. Part of counter/decoder circuit

The use of such a device may be demonstrated by referring to the part of a circuit shown in Fig. 7. The problem here was to produce a signal from the output of the 8-input NAND gate after the counter had counted a selectable number of clock pulses. To achieve this action, each of the inputs is connected to logic 1 by a 'pull-up' resistor, thereby ensuring that the output will be logic 0. The numbers shown by the outputs from the BCD counter are the number of clock pulses which need to be counted before that particular output goes high, assuming a start from zero. Without going into any further detail of how the outputs from the counter would appear, by connecting the appropriate links it is possible to set the circuit to count any value of pulses from 1 to 255. For example, if it were required to count up to 23 clock pulses before a logic 0 appeared at the output of the NAND gate, then the links for 1, 2, 4 and 16 would be made, since  $1+2+4+16=23$ .

The individual pull-up resistors are needed on the inputs in order to ensure that any unconnected inputs are held at logic 1; the value of these resistors is not all that critical, but it must be remembered that the output of the counter will be required to sink the current through them when it goes low. The BCD counter is a rather different type of animal from the ones we have encountered so far, belonging to the breed of sequential logic devices. This is a whole range of beasts which will be dealt with in a lot more detail in a subsequent article.

## Arithmetic Logic Units

Any reader who has perused books or articles on the subject of micro-processors or micro-computers, and these days it's hard to avoid them, may well have come across the term Arithmetic Logic Unit, or ALU. This is the part of the micro-processor which is concerned with 'doing sums' and other logical operations. Needless to say, in a real life processor, this section contains a multitude of functional devices, but it is possible to emulate one of its basic building blocks, the Adder. Side-stepping the old jokes about venomous snakes, the digital adder comes in two types, the half-adder and the full-adder. However, before we delve into the workings of these circuits, it may well be a good idea to brush up on some binary arithmetic.

I am sure everyone reading this is fully conversant with denary arithmetic, that is

working in powers of ten. In binary arithmetic the same rules apply, but in this case we are using the number base of two, with the digits 0 and 1. When two denary (or decimal) digits are added together there are two possible situations:

a) a third digit, larger than the other two results, but smaller than the base of the number system, eg,

$$\begin{array}{r} 5 \\ +3 \\ \hline 8 \end{array} \quad \begin{array}{r} 1 \\ +4 \\ \hline 5 \end{array}$$

The new digit, 8 or 5 in these examples, is called the SUM.

b) the third digit is equal to or larger than the base of the number system,

$$\begin{array}{r} 5 \\ +6 \\ \hline 1 \quad 1 \end{array} \quad \begin{array}{r} 8 \\ +7 \\ \hline 1 \quad 5 \end{array}$$

CARRY SUM CARRY SUM In this case the position of the digits comes into play and the answer consists of two parts, the SUM and the CARRY. The generation of Sum and Carry occurs whatever number base is in use. In binary addition the generation of Carry bits occurs much more often, as there are only two digits.

$$\begin{array}{r} 0 \\ +0 \\ \hline 0 \end{array} \quad \begin{array}{r} 0 \\ +1 \\ \hline 1 \end{array} \quad \begin{array}{r} 1 \\ +1 \\ \hline 1 \quad 0 \end{array}$$

These examples cover nearly all the possible combinations of binary addition, the only other one being where the 0 and 1 are reversed in the middle example!

Where binary numbers containing more than one digit are to be added, then the process can be broken down into a series of repeated two-digit additions, until the process is complete. For example:-

$$\begin{array}{r} 10 \\ +01 \\ \hline CARRY 11 \quad SUM 1001 \end{array} \quad \begin{array}{r} 111 \\ +010 \\ \hline CARRY 1001 \quad SUM 1001 \end{array}$$

In the second example, the addition of the first (right-hand) digits of 0 and 1 gives a Sum of 1, and no Carry; adding the next two digits, 1 and 1, produces a Sum of 0 and a Carry of 1. The next stage is to add together 0, 1 and the Carry; as before 0 and 1 give a Partial Sum of 1, and adding the 1 carried over gives a Sum of 0 and a Carry into the next column. The simple rules of binary addition may be summarised in a Truth Table, shown in Figure 8.

A	B	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Figure 8. Binary addition truth table

Looking at this Table it is possible to see that a Sum OR a Carry is the result of a binary addition, never a Sum AND a Carry. To perform this operation with logic gates, it is only necessary to find ones which have the same Truth Table as that for binary addition. The circuit would require two inputs, A and B and two outputs to correspond to the Sum and Carry. This can, in fact, be achieved in several different ways; if you look back at the Truth Table for the EX-OR gate and the AND gate it is apparent that the Sum part is the same as the EX-OR truth table and the Carry part is the same as the AND gate. Actually, this is not quite a full solution, since no account has been taken of the fact that a Carry bit may have been produced by an earlier stage, and hence this is known as the half-adder.

## Half-Adder Circuit

A digital half-adder circuit may be made up, on a bread-board, following the diagram given in Figure 9. Here it can be seen that the two gates which are required are the EX-OR

and the AND gates. Possibly the most convenient method of making up this circuit is to use single gates from a 7486 and a 7408, and connect them up as shown. In this case the two bits to be added are applied to inputs A and B to give the Sum and Carry appear at the corresponding outputs. It is also possible, remember, to make up such gates as these from the common NAND gate. We have already seen how the EX-OR gate may be made up from four 2-input NAND gates, and so to complete the picture figure 10 shows how the AND gate may be fashioned. It is left as a further exercise for the reader to make up the half-adder circuit from NAND gates and confirm that it is logically identical to the first design.

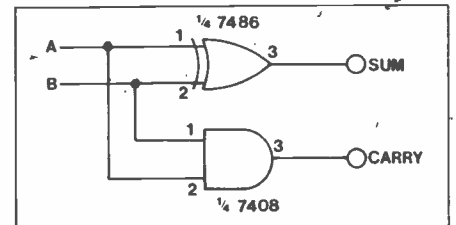


Figure 9. Circuit for half-adder

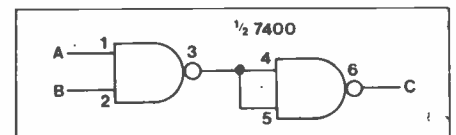


Figure 10. AND gate using NAND gates

## Full-Adder Design

The half-adder is incomplete in that no provision is made for a 'carry-in' from a previous stage. In the case of the full-adder, not only is account taken of this, but also a provision is made for the possible generation of a 'carry-out' to subsequent stages. Again, the requirements of the full-adder may best be summarised in the form of a Truth Table; this will need to have three inputs, A, B and Carry In, with two outputs, Sum and Carry Out, as shown in Figure 11.

A	B	CARRY IN	SUM	CARRY OUT
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Figure 11. Truth table for binary full adder

The full-adder is, in essence, two half-adders connected together to take account of the extra bit carried in. The circuit for the full-adder is given in Figure 12. Again, although this is shown made up from discrete gates, it can also be done with NAND gates in the same manner as the half-adder.

If more than two bits are to be summed then the block can be repeated, with the carry out from one stage being connected to the carry in of the next stage. Finally, Figure 13 shows a couple of full-adders being used to add binary 11 and 11, giving 110; ie decimal  $3+3=6$ .

## Address Decoding

Still on the micro-processor scene, another important use of TTL combinational logic designs is in the area of address decoding. The essential problem here is to produce a signal in response to a unique pattern of bits on the micro-processor address bus. This pattern of bits is, of course, the address of the device which is being sought in order to send or receive data along the data bus of the system. Typically,

Continued on page 64

# Logic Probe

by Graeme Durant

- ★ Detects pulses from around 1Hz
- ★ Instantly recognisable logic states
- ★ Low current consumption
- ★ Over volts protection

Over the years, countless designs have appeared in the electronics press for logic probes; ranging from very simple High/Low indicators, to complex pulse stretching probes. The logic probe described here, has a number of features found only on the more complex probes, and as such, lies somewhere between these two extremes. Thus it is perfectly suited to day to day fault diagnosis.

As well as detecting High and Low logic states, open circuit (floating input) and pulsing inputs are displayed. Pulse trains from around 1Hz are detected as a pulsing input, the upper limit is above that attainable in most common C-MOS logic.

The main difference between this logic probe and all others is that the output is shown on a seven segment LED display, as a letter of the alphabet; Hi for High; L for Low; F for Floating; P for Pulsing. In this way, the logic state is instantly recognisable and totally unambiguous, unlike some commercial

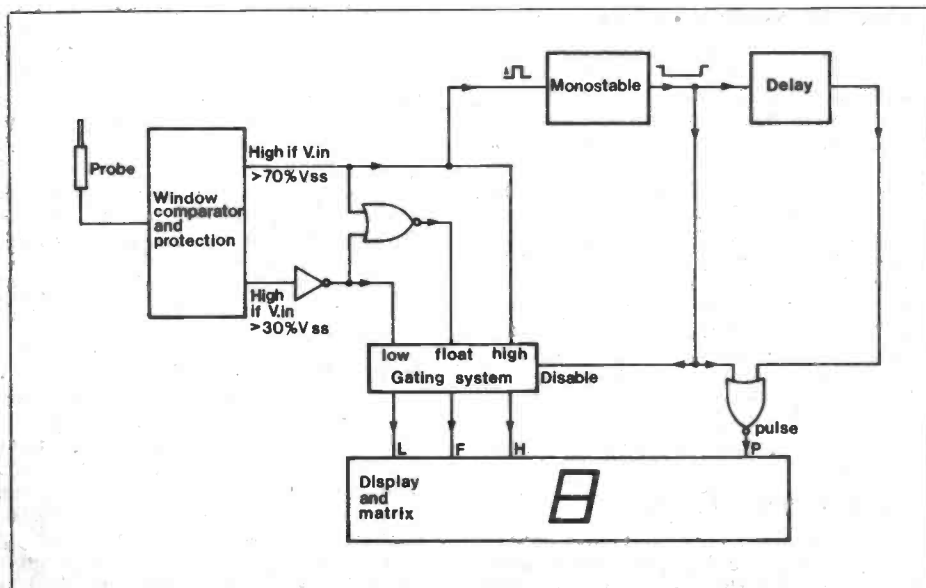
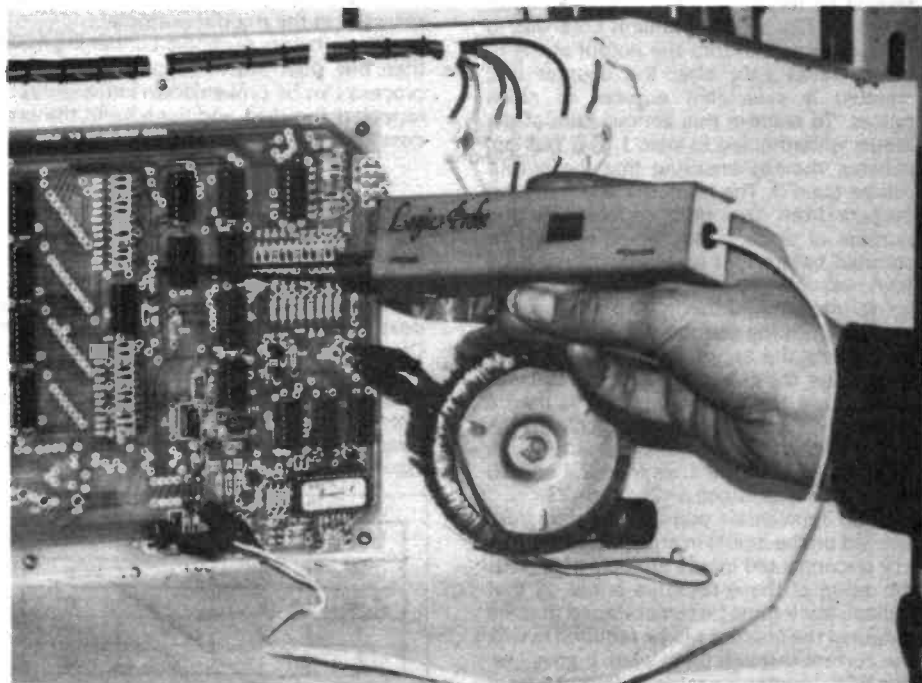


Figure 1. Block diagram.

logic displays. The use of a special high efficiency display means that the total current consumption at a supply voltage of 15v is only 15mA - quite suited to battery operated circuits. In addition, the probe is protected against over-voltage inputs, and reversed supply.

## Block Diagram

The input from the probe goes via a protection network to a window comparator, with switching levels of 70%  $V_{ss}$  and 30%  $V_{ss}$ ; these are the standard CMOS limits. If the upper limit is exceeded, then the probe input is CMOS logic high. Thus, the upper output goes on to the display circuitry for HIGH indication.

If the probe input does not exceed the lower limit, then it is at CMOS logic low. The output of the lower comparator is inverted to give a high level at the display circuitry for LOW indication. If the probe input is between logic levels,


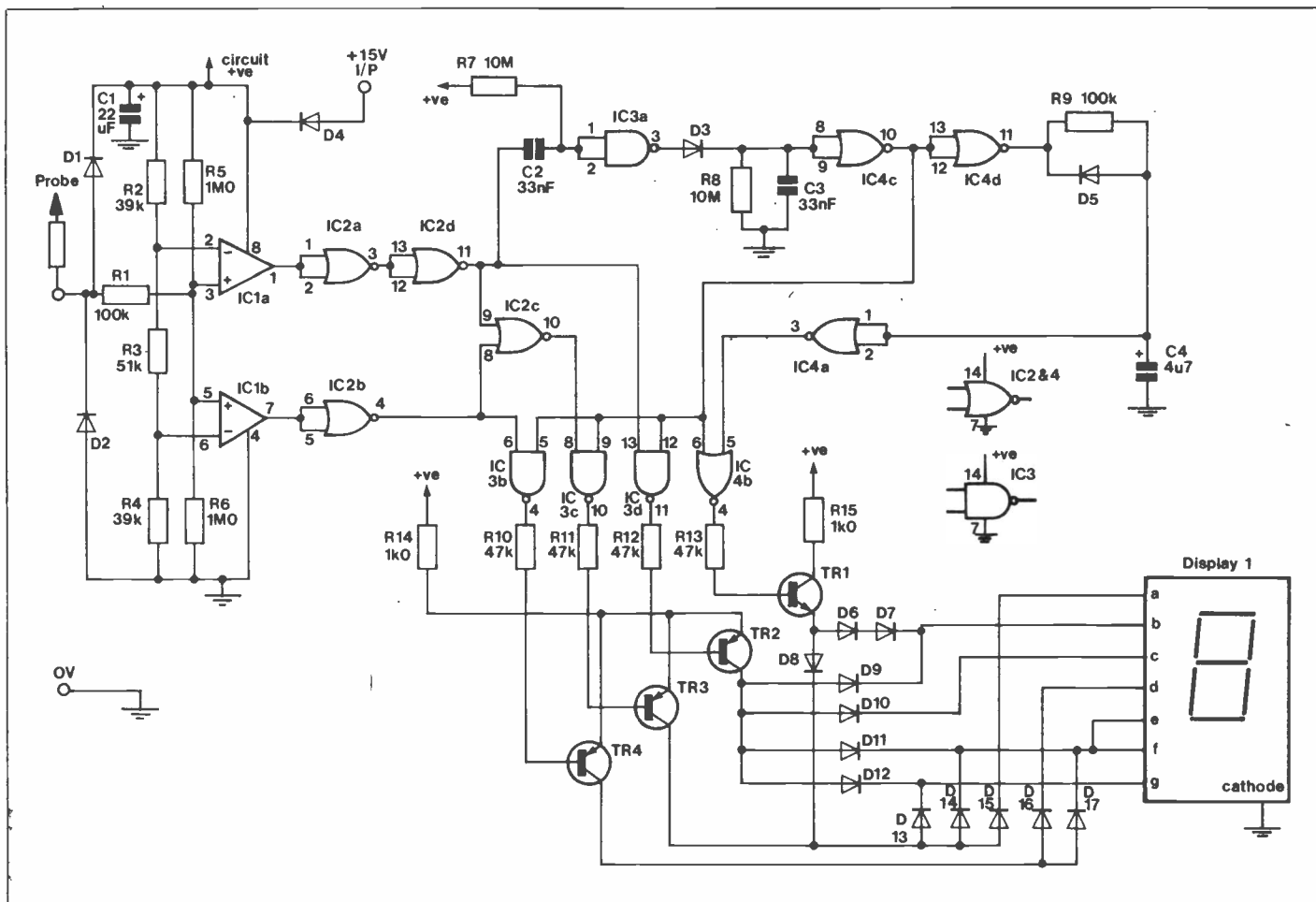


Figure 2: Circuit diagram.

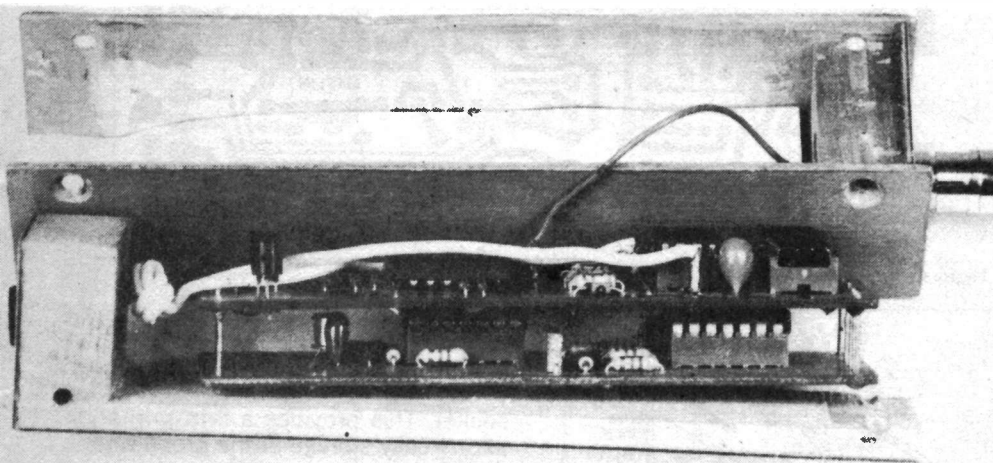

then the upper comparator will be low and the lower comparator high. These two outputs are fed to a .NOR gate, which gives a high level to the display circuitry on FLOAT.

The HIGH indication also drives a retriggerable monostable. will produce a continuous low output. If this monostable goes low, the display is disabled via a simple gating system. This is to prevent misleading displays, whilst the circuit decides whether the input is indeed pulsing, or whether a low to high transition has taken place (e.g. the probe has just touched a point at logic high). As soon as a low pulse appears at the monostable output, a delay, slightly

## PARTS LIST FOR LOGIC PROBE

Resistors: All 0.4W 1% metal film unless specified

R1,9	100k	2 off	(M100K)
R2,4	39k	2 off	(M39K)
R3	51k		(M51K)
R5,6	1M0	2 off	(M1M0)
R7,8	10M	2 off	(B10M)
R10-13	47k	4 off	(M47K)
R14, 15	1k0	2 off	(M1K0)

### Capacitors

C1	22uF 25V Tantalum		(WW73Q)
C2, 3	33nF polycarbonate	2 off	(WW35Q)
C4	4u7F 35V Tantalum		(WW65V)

### Semiconductors

IC1	CA3240E		(WQ21X)
IC2, 4	4001BE	2 off	(QX01B)
IC3	4011BE		(QX05F)
TR1	BC107B		(QB31J)

TR2, 3,4	BC557	3 off	(QQ16S)
D1, 2	BAR28	2 off	(QQ13P)
D4	1N4001		(QL73Q)
D3, 5-17	1N 4148	14 off	(QL80B)
Disp.1	Low current disp.		(QY54J)

### Miscellaneous

	Printed circuit board (top)	(GB30H)
	Printed circuit board (bottom)	(GB31J)

### Additional parts if required

	8pin DIL sct		(BL17T)
	14pin DIL sct	3 off	(BL18U)
	Screened phono plug		(HH01B)
	Threaded phono sct		(YW06G)
	Croc. clips		(HF25C)
	Zip wire	1 metre	(XR39N)
	Filter red		(FR34M)
	Veropin 2141	1 pkt	(FL21X)

A complete kit of all parts is available.  
Order As LK13P (Logic Probe Kit). Price £9.95.

longer than the monostable period is initiated. At the end of this time period, if the output of the monostable is still low, i.e. the input is pulsing, the display shows PULSE. Otherwise, the HIGH/FLOAT/LOW display is enabled again.

The display consists of driver transistors, a diode matrix to produce the desired alphabetic displays, and a seven segment LED display.

## Circuit Description

The probe input goes via R1 to a simple window comparator formed around IC1. R2, R3 and R4 determine the changeover voltage levels. The circuit input is protected from over-voltage by D1, D2 and R1; the input is biased at half supply by R5 and R6 so that if the input is open circuit, the display shows FLOAT. The upper window comparator output is buffered by IC2a and IC2d, and goes to the display switching transistor for HIGH indication, via IC3d, which allows the HIGH display to be disabled.

The low and float displays are similarly connected, using IC2b and IC3b for LOW, and IC2c and IC3c for FLOAT.

A simple CMOS monostable wired around IC3a and IC4c, and having a period of around 0.5 seconds senses a pulsing input. Its output, which is normally high, disables the HIGH/FLOAT/LOW display, and starts a delay, formed around C4 and R9, which is a little over the monostable period. The output of the RC delay is inverted and fed to IC4b, which senses whether the input is still pulsing. If it is, Q1 is switched on, and PULSE is displayed. Otherwise Q2 to 4 are enabled, a diode matrix and seven segment common cathode display decode the signals, so as to give H, F, L and P displays.

## 'Construction'

Before soldering in any components, solder in wire links on both PCBs, there are eight in all. Fit in all the resistors and capacitors, taking care with polarity on C1 and C4. If you are using IC sockets these may be fitted along with the diodes — again be careful about polarity. Note also, that D4 is fitted vertically on the PCB. Fit the transistors, and finally, the ICs. It is a good idea to use veropins for all the cable to PCB connections, but it is not vital. This only leaves the display, which requires setting at the correct height to fit inside a suitable case.

The PCBs are mounted one on top of the other in the case, with connections between made by solid wire links — cropped component leads are ideal. Solder eleven lengths of wire, about 20mm long, to the underside end connections of the top board, passing the wire through the holes until level with the topside of the PCB. See Figure 5.

Slide on the lower board, until there is a gap of a millimetre or so between the top board and the tallest components.

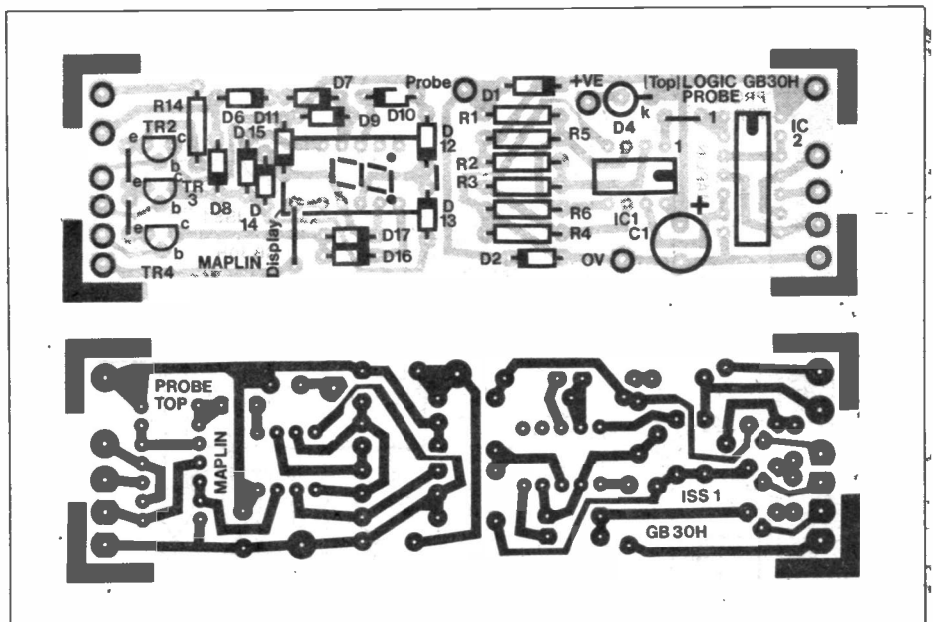


Figure 3. PCB layout.

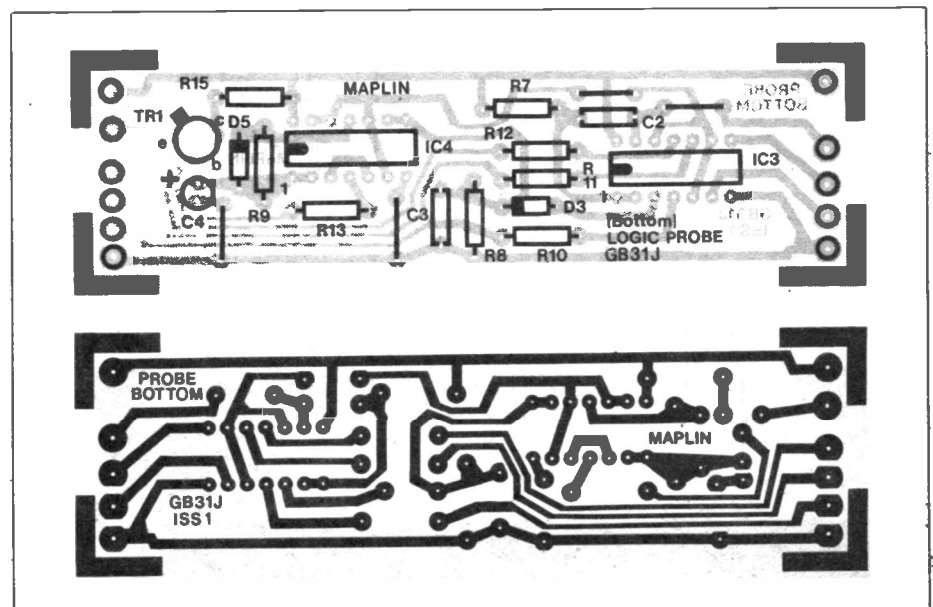


Figure 4. PCB layout.

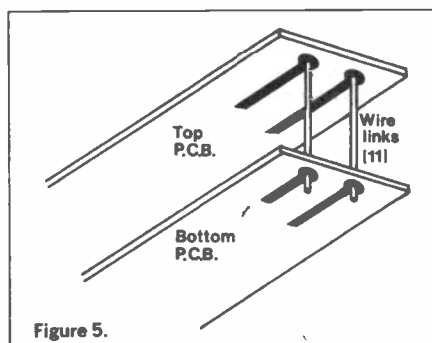


Figure 5.

on the bottom PCB. Solder the wires to the bottom board and crop as normal.

The circuit now may be fitted into the case, insulated from the case bottom by masking tape and held firmly in position by sticking a strip of thin foam rubber in the lid, with a cutout for the display. A small square of red display filter film may be stuck behind the cutout for the display for easier viewing.



The power cable, a piece of Zip wire terminated in crocodile clips must pass through the case via grommet. The

probe, made from a sharpened steel rod or knitting needle, is soldered into a Phono plug, and connected to the circuit by a case mounted Phono socket. This provides a firm grip and allows easy storage of the probe when not in use.
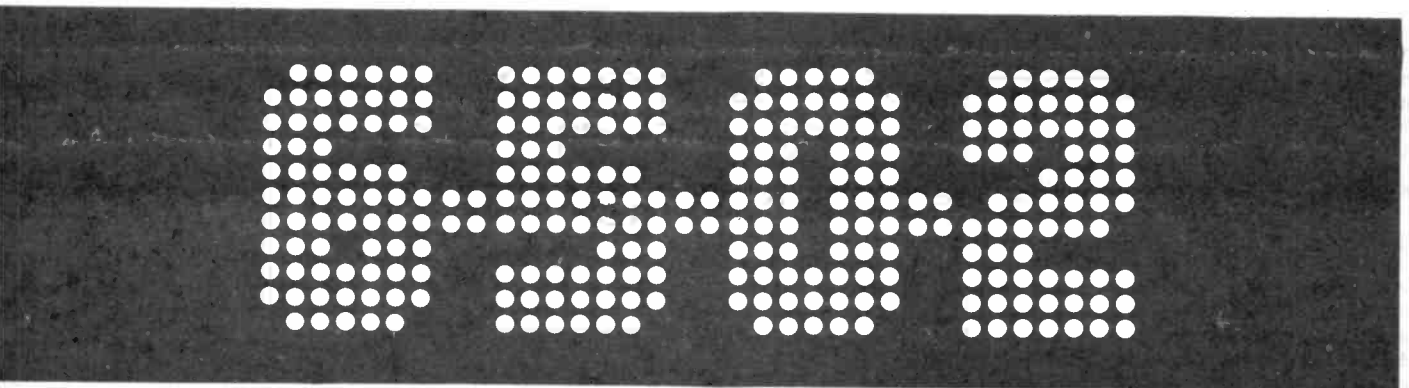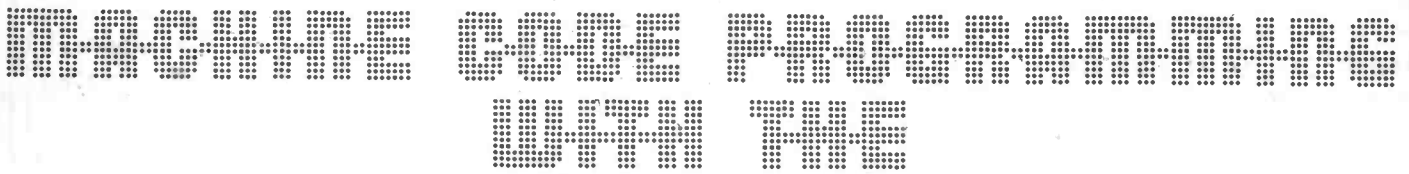
## Testing and Use

Power the circuit up with a typical CMOS supply voltage. After around half a second, the display should show a letter F. If not, disconnect quickly, and recheck the circuit. If all is well, touch the probe to positive — a letter H should be light after a brief delay. Tap the probe on and off positive a few times a second — a letter P should be displayed after a delay. Then, touch the probe to Ov — a letter L should light immediately. If all this happens, the probe is working perfectly.

The probe is designed for use with CMOS logic circuitry, and may be used to trace faults on any such logic. All that remains now is to find a suitable circuit to test!



## Part Two

Graham Dixey C.Eng., M.I.E.R.E.

### Memory Addressing

Little progress can be made in writing machine-code programs without a reasonable degree of understanding of the addressing modes available. The better the understanding, the better the programs. In a program written by the user, all of the instructions and data will be entered into the RAM area of memory, and running the program will access these instructions and data sequentially. Questions then naturally arise. Whereabouts in the RAM should the program be located? What are the criteria that determine the choice of locations? Given that there are a variety of ways of loading and storing data, how does one decide which method to use? It is the intention of this article, the second of this series, to answer these questions by showing how some of the 6502 addressing modes work. So that it is possible to 'see the wood in spite of the trees', no attempt will be made at this stage to write anything very ambitious in the way of programs. That can come later. But the first 6502 mnemonics and their corresponding op-codes will be met so that addressing can be seen to be used in a meaningful sense.

### The Paging Concept

Memory is organised in 'pages', each 256 bytes long. These are known as 'Page 0', 'Page 1', 'Page 2' ... 'Page E', etc. The page number is obtained by writing the memory addresses in numbers of four HEX digits length and examining the two most significant digits.

Thus, Page 0 runs from 0000 to 00FF  
 Page 1 runs from 0100 to 01FF  
 Page 2 runs from 0200 to 02FF

Page E runs from 0E00 to 0EFF  
 etc.

This idea of pages is more important than might be thought. For one thing, it is possible to write a shorter (and hence faster) program on Page 0 than on others - because of a unique addressing mode that will be explained shortly. Secondly, crossing a page 'boundary' in certain operations incurs a loss of speed.

A pictorial method of illustrating memory is the 'memory map', an example of which is shown in Figure 1. This shows both

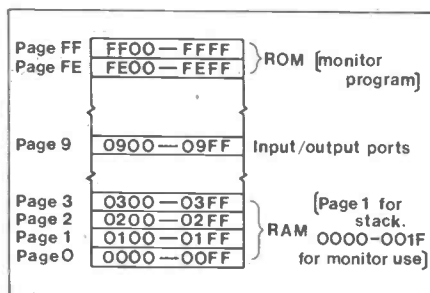


Figure 1. Memory map of a typical small microcomputer.

the pages referred to and also the way in which they are allocated. This memory map may be taken to represent a typical small development microcomputer with just 1K of RAM and 512 bytes of ROM. Whatever computer is concerned, it will be necessary to determine its memory map so as to know (a) which areas of RAM are available for user programs and (b) where the input/output ports are located. The 'stack' is standard on all 6502-based machines, being located on Page 1 - thus this page is not to be used for user programs, except in stack operations. One word of warning - the monitor program, which is stored in ROM and controls the computer operation, may well have a small part of one of the RAM pages (e.g. Page 0) reserved for its own use for what is known as a 'scratch-pad'. User programs should not be written here as strange things will happen!

### Assembly Code and Machine Code - the first mnemonics

Assembly and machine codes are both termed 'low-level languages'. Assembly code consists of easily recognisable mnemonics and is the form in which the program is first written. When there is a good chance that the program will work, then it can be put into machine code; this consists of op-codes and data, whose meanings at a glance are much less obvious. It is as well to be disciplined in approaching program writing right from the start, since a well laid out program is easier to de-bug than one in which the logical approach is missing. When writing the Assembly Code program space

should be left alongside for the related machine-code program; then a direct correspondence between the two can always be seen.

Now for a few instructions and their Assembly Code mnemonics:

SED - Set the Decimal mode (for arithmetic operations)

LDA - Load the Accumulator (with the byte of data specified in some way by what follows next)

The bracketted words actually refer to the addressing mode to be used.

CLC - Clear the Carry (flag): sets the carry flag to zero

ADC - Add with Carry (adds the contents of the accumulator - plus the carry flag - to the data specified by what follows next)

This operation was illustrated diagrammatically in Part One of this series.

STA - Store the accumulator contents (at a location determined by what follows next)

These mnemonics, as listed, actually form a short program that adds together two numbers and stores the result. The only problem that needs them to be solved is how to address the memory, both to fetch the data, i.e. the numbers to be added, and to

MNEMONIC	OP CODE	OPERATION
BRK	00	Break
CLC	18	0 → C
CLD	D8	0 → D
CLI	58	0 → I
CLV	B8	0 → V
DEX	CA	X-1 → X
DEY	8A	Y-1 → Y
INX	E8	X+1 → X
INY	C8	Y+1 → Y
NOP	EA	No operation
PHA	48	A → Stack
PHP	08	P → Stack
PLA	68	Stack → A
PLP	28	Stack → P
RTI	40	Return from interrupt
RTS	60	Return from sub-routine
SEC	38	1 → C
SED	F8	1 → D
SEI	78	1 → I
TAX	AA	A → X
TAY	A8	A → Y
TSX	BA	S → X
TXA	8A	X → A
TXS	9A	X → S
TYA	98	Y → A

Table 1. 6502 instructions using inherent addressing.

## MACHINE CODE PROGRAMMING WITH THE 6502

store the result of the addition. So now to some 6502 addressing modes.

### Inherent Addressing (Implied)

There are two instructions in the above program that use this mode. They are SED and CLC. This is the simplest form of addressing since it is complete as it stands; there is no following data byte/s. This is a 'single-byte' instruction which is performing an operation which is totally self-contained within the MPU chip. The complete list of 6502 instructions that use this mode are given in Table 1.

### Zero Page Addressing

This mode provides access to all memory locations on Page 0 i.e. the addresses in the range 000 - 00FF. These are 'two-byte' instructions; the first byte is the instruction itself e.g. LDA; the second byte is the Page 0 address where the data is located. Suppose as an example this address is 0030; using zero page addressing this is specified simply by the HEX number 30. It is a utility of 6502 programming that all Page 0 addresses can be identified by using the low byte of the address only; for all other pages of memory both bytes must in some way be specified. It is for this reason, as mentioned earlier, that programs on Page 0 run faster than those on other pages.

The op-code for LDA on Page 0 is A5 so that the program line in machine code for this operation is:

A5 30

It should now be appreciated that this represents an instruction to the MPU to load its accumulator with whatever number it finds at memory location 0030 - in a language which it can understand i.e. HEX machine code. Actually that is a half-truth since there also has to be a further translation from HEX into binary, but this is not a worry of the programmer; the machine sorts this out itself.

### Immediate Addressing

This is also a 'two-byte' addressing mode but with the following important difference. The second byte is not an actual address for the data but is the 'data itself'. To distinguish it from zero page addressing the # (hash) is used in Assembly Code and, of course, the op-code for machine-code is different. This is illustrated by the following example:

Assembly Code	Machine Code	Comments
LDA MEM1	A5 30	Zero page mode (meaning Load Accumulator with data at address 0030)
LDA #30	A9 30	Immediate mode (meaning Load Accumulator with the number given i.e. 30)

Notice one point of protocol - in the Assembly Code for zero page the memory location is simply referred to as MEM1, whereas in the corresponding machine code the actual address is specified i.e. 30=0030. MEM1 is called a 'label' and is generally used in writing Assembly Code programs so as to preserve a general approach to program writing. It is later, when the program is encoded into machine code, that the actual memory location to be used can be assigned.

Naturally it often happens that access is required to memory locations that are on another page other than Page 0. One way of achieving this is to use the 'three-byte' mode known as absolute addressing. The first byte

ASSEMBLY CODE					MACHINE CODE		
LABEL	MNEMONIC	DATA	COMMENTS	PC	OP CODE	DATA/ADDRESS	
					BYTE 1	BYTE 2	BYTE 3

Figure 2. Scheme for headed programming sheet.

ASSEMBLY CODE					MACHINE CODE		
LABEL	MNEMONIC	DATA	COMMENTS	PC	OP CODE	DATA/ADDRESS	
					BYTE 1	BYTE 2	BYTE 3
	SED		Sets dec. mode	0020	F 8		
	LDA	MEM1	MEM1 → A	21	A 5	30	
	CLC		0 → C	23	18		
	ADC	MEM2	MEM1+MEM2 → A	24	65	31	
	STA	MEM3	A → MEM3	26	85	32	
			MEM1=0030; MEM2=0031; MEM3=0032				
(b)	CLD		Clears dec. mode	0050	D 8		
	LDA	MEM4	MEM4 → A	51	A 5	60	
	SEC		1 → C	53	3 8		
	SBC	# 10	MEM4 - 10 → A	54	E 9	0A	
	STA	MEM5	A → MEM5	56	8 D	1 F	03
			MEM4=0060; MEM5=031F				

N.B. → means "goes into"

Figure 3. Two simple programs: (a) single-byte addition (b) subtraction.

MNEMONIC	OP CODE			OPERATION
	IMM.	ABS.	0 Page	
ADC	69	6D	65	A + M + C → A
AND	29	2D	25	A ∧ M → A
ASL		0E	06	C ← (A >> 1)
BIT		2C	24	A ∧ M
CMP	C9	CD	C5	A - M
CPX	E0	EC	E4	X - M
CPY	C0	CC	C4	Y - M
DEC		CE	C6	M - 1 → M
EOR	49	4D	45	A ⊕ M → A
INC		EE	E6	M + 1 → M
JMP		4C		Jump to:
JSR		20		Jump sub
LDA	A9	AD	A5	M → A
LDX	A2	AE	A6	M → X
LDY	A0	AC	A4	M → Y
LSR		4E	46	(A >> 1) ← C
ORA	09	0D	05	A ∨ M → A
ROL		2E	26	(A << 1) ← C
ROR		6E	66	C ← (A << 1)
SBC	E9	ED	E5	A - M - C → A
STA		8D	85	A → M
STX		8E	86	X → M
STY		8C	84	Y → M

Table 2. 6502 instructions using immediate, zero page or absolute addressing.

is the appropriate op-code followed by the full two bytes of the address. Straightforward enough evidently but note that in machine-code the 'low' byte of the address comes 'first', thus; the op-code for LDA in this mode is AD so that, to load the accumulator from the Page 3 memory location 031A, the program line in machine-code would be - AD 1A 03. Obviously a point to remember.

The instructions that can use the Immediate, Zero Page or Absolute addressing modes are listed in Table 2. together with their op-codes.

### Two Simple Machine Code Programs

The list of instructions for a simple 'single-byte' addition program has already

MNEMONIC	OP CODE	OPERATION
BCC	90	Branch on C = 0
BCS	B0	.. .. C = 1
BEQ	FO	.. .. Z = 1
BMI	30	.. .. N = 1
BNE	DO	.. .. Z = 0
BPL	10	.. .. N = 0
BVC	50	.. .. V = 0
BVS	70	.. .. V = 1

Table 3. 6502 instructions using relative addressing.

been given. This program can now be encoded into machine-code in order to illustrate the way in which a written program may be laid out and to clarify, if needed, some of the instructions.

It will be necessary when writing the machine-code program to assign actual memory locations. As already explained, those addresses available will vary from one machine to another. However, rather than get round the problem by putting in a series of Xs whenever an address is needed, as it is sometimes done, the memory map of Figure 1. will be used. This approach is much more meaningful in terms of learning how to write programs, and it is only necessary for the individual programmer to remember that he may well have to assign different addresses for his own machine.

A headed programming sheet might look something like that shown in Figure 2. The column headed LABEL is only needed for programs containing 'branches' or 'jumps' but, for a general purpose programming sheet it should be included. PC stands for Program Counter, of course, and it is this register that holds all of the program memory locations, in turn, as the program runs.

Figure 3. shows two of the simplest programs possible - single-byte addition, and subtraction. These are included to illustrate the use of the programming sheet as well as the addressing modes that have been discussed so far.

The addition program starts by selecting the 'decimal' mode i.e. all data is handled as Binary Coded Decimal (BCD); the alternative mode is HEX. The accumulator is then loaded with the contents of the location labelled MEM1 (actual address 0030) and the carry flag is cleared prior to the addition. This step is necessary since the state of the carry flag is quite arbitrary at this instant and the 6502 instruction set has only the one addition instruction, which always includes the carry bit. Next the accumulator contents and the data at MEM2 (0031) are added together, the result being retained in the accumulator. This sum is then stored at MEM3 (0032). The whole program has been carried out on Page 0.

The subtraction program could have been written on very similar lines but has been used, instead, as an illustration of the Immediate and Absolute addressing modes.

The program starts by clearing the decimal mode i.e. HEX arithmetic is selected (a choice entirely at the user's whim). The accumulator is loaded with the contents of MEM4 (0060) and the carry flag is 'set'. This must always be done before a subtraction so that 'borrows' can be made as required. The number subtracted from the accumulator contents is the decimal number 10 (immediate mode), which has to be written in HEX for the machine-code program and then becomes 0A. The result of this subtraction is retained in the accumulator, which is then stored on Page 3 (at 031F), which requires absolute addressing.

Unless the above is absolutely crystal clear it would be as well to study these two programs carefully alongside Tables 1 and 2 so that the op-codes used in them can be related to the addressing modes used. A look at the PC column shows that only the address for the first byte on a program line is given; however, the other addresses have been allowed for, as study of the PC column should make clear. For example, in the addition program there are eight bytes corresponding to the eight memory locations 0020 - 0027 respectively. Notice also that the subtracting program is longer at nine bytes because of the absolute mode used for the store operation.

Perhaps it might be as well to make it clear now that these two apparently trivial programs are included principally to illustrate the points made so far and to establish a structured approach towards programming. Obviously one does not need a computer just to add or subtract two numbers, but one might do so as part of a much larger and, hence, more complex program. In fact, such operations may need to be repeated many times during the course of a program run. They would then be called as 'sub-routines' each time required. It is intended to familiarise the reader with the whole of the 6502 instruction set and to show how to write programs to perform useful, mainly control-centred functions.

### Relative Addressing

This mode is used only with 'branch' instructions, i.e. where a departure is made from the current address to another part of memory, as the result of a decision. This offers alternative courses of action based on the current state of affairs. For example, taking inputs to the computer from transducers and testing their values may decide the value of the output to some control element, perhaps a relay, lamp, motor, heater, etc. Flowcharts show clearly the action of branches. For example, Figure 4(a) shows the idea of testing an input and taking the appropriate action for a computer-controlled furnace, while Figure 4(b) shows the computer making this same type of decision based on the accumulator status. Table 3 lists all of the 6502 instructions that use relative addressing.

Obviously a change in program direction can be either forward or backward, i.e. a branch can be 'positive' or 'negative'. In relative addressing the 'length' of the branch is added to or subtracted from the current contents of the program counter, thus causing the program to branch suddenly from one area of memory to another. The length of the branch is simply the number of steps that must be made through memory to the required new location.


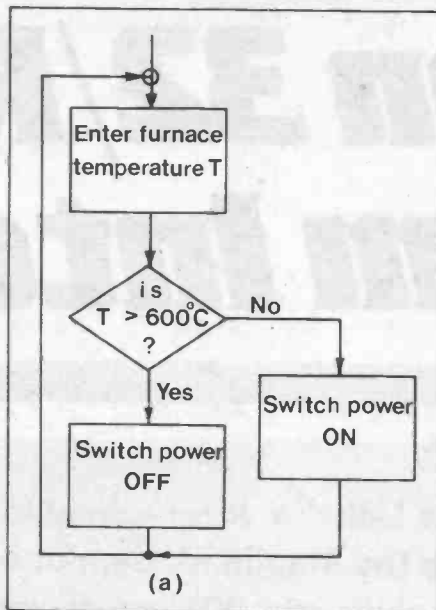


Figure 4. Flowcharts (a) computer-controlled furnace.

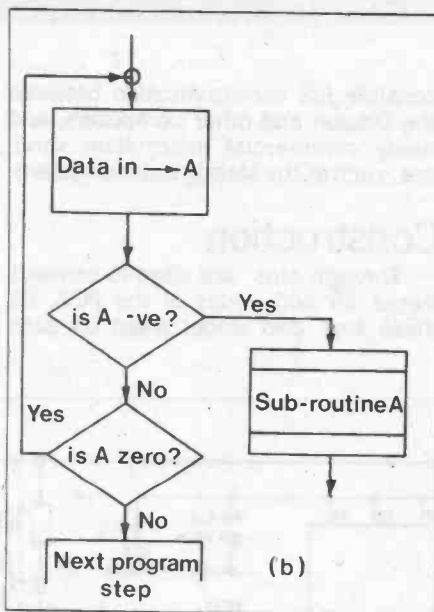

(b) decision making based on accumulator status.

Suppose that a positive branch must be made when the accumulator contents are negative and a negative branch is to be made elsewhere if these contents are instead zero, perhaps as the result of a subtraction that has just been performed. Otherwise, if the accumulator contents are positive the program doesn't branch at all but just proceeds to the next step in the program. The program segment might look like this:

```

LOAD LDA MEM1 0020 A5 E2
SEC      22 38
SBC #20 23 E9 14
BNE OUT 25 D0 0A
BEQ LOAD 27 FO F7
  
```

```
OUT STA PORT B 003B 8D 00 09
```

The data for the BNE and BEQ instructions are the branch lengths, which are 0A and F7 respectively, computed as follows.

(i) Positive branch: BNE to OUT; the memory location for the latter is seen to be 003B. When the program branches to this location it then finds the instruction to store the accumulator contents at the output port

B. In this way the decision and action is taken to output data from the computer to some peripheral device. The question now is 'from where does the branch start?' The answer is that a branch always starts from the address immediately following the one at which the branch length is to be found - in this case 0027 (the branch length being at 0026). The reason for this is quite simple. The program counter is stepping sequentially through the program instruction and data bytes, each byte being sent in turn to the 6502's instruction register where it is decoded. While this decoding is taking place, the program counter automatically increments to the next address in the sequence, so it is one step ahead when the branch length is in the instruction register. This instruction register, which has not been mentioned before, is for the decoding mentioned only and is not accessible to the programmer.

The branch length is therefore the number of steps between 0027 and 003B which is 10 in decimal or 0A in HEX. Count them!

(ii) Negative branch: BEQ to LOAD; this time it is necessary to go backwards to 0020. The branch starts at 0029 so, therefore, the branch length is -9 (the - sign indicates a negative branch) and this has to be written as a 'signed HEX number' - not as bad as it sounds.

#### Method 1.

- (i) Write 9 in binary (8 bits) = 00001001
- (ii) Complement it = 11110110
- (iii) Add '1' to it = 11110111
- (iv) Write this as two HEX digits = F7

#### Method 2.

Note the following sequence of HEX numbers:

F7	=	-9	
FD	=	-3	Negative numbers
FE	=	-2	
FF	=	-1	
00	=	zero	
01	=	+1	
02	=	+2	Positive numbers
03	=	+3	

Imagine this as a continuous sequence around the surface of a cylinder. Where will the join be between positive and negative numbers? The answer is:

80 = -128 (highest negative number)  
7F = +127 (highest positive number)

This is easy enough to grasp especially if the analogy is taken of a mechanical counter, such as the odometer in a car. If it was set at all zeros i.e. 0000, what would it read if it was turned back one notch, then two, etc? Easy enough of course - 9999,9998 and so on. So it is with HEX that going backwards (i.e. negatively) from zero gives the highest HEX digits first, then reducing by one at each step - FF, FE, etc.

A final point worth making now. Using relative addressing, the maximum distance that one can branch out through memory is 127 steps forward or 128 steps backward - or is it? There must be a way of branching as far as one likes, and this, plus more complex addressing modes will be dealt with in the next article. Also, since quite a bit of useful theory has now been covered in the first two articles, the time has come to start developing more useful and ambitious programs.

# Dragon 32/RS232 Modem Interface

- ★ RS232 Data Link   ★ Programmable word format
- ★ Will connect Dragon to the Maplin Modem or other compatible system
- ★ Module plugs into ROM expansion socket

by Dave Goodman

The first in a series of projects for the Dragon 32 computer is our Serial Communications Interface Adaptor, or SCIA. Although primarily designed for use with the Maplin Modem, the SCIA could connect to any serial RS232 compatible system where data exchange is required. It makes

possible full communication between the Dragon and other computers, and many commercial information services, such as the Maplin Cashtel system.

## Construction

Through pins are used to connect tracks on both sides of the PCB. Fit these first, and solder them on both

sides of the board. Resistors and diodes are fitted next, bending each lead before insertion. On the legend a white bar shows the position for aligning the cathode of each diode, which in turn is recognised by a black band printed on the body. Fit RV1, and all the capacitors. C4, 5, and 6 are polarised, with the negative end marked on the body, while C7 is marked with a positive sign. Make


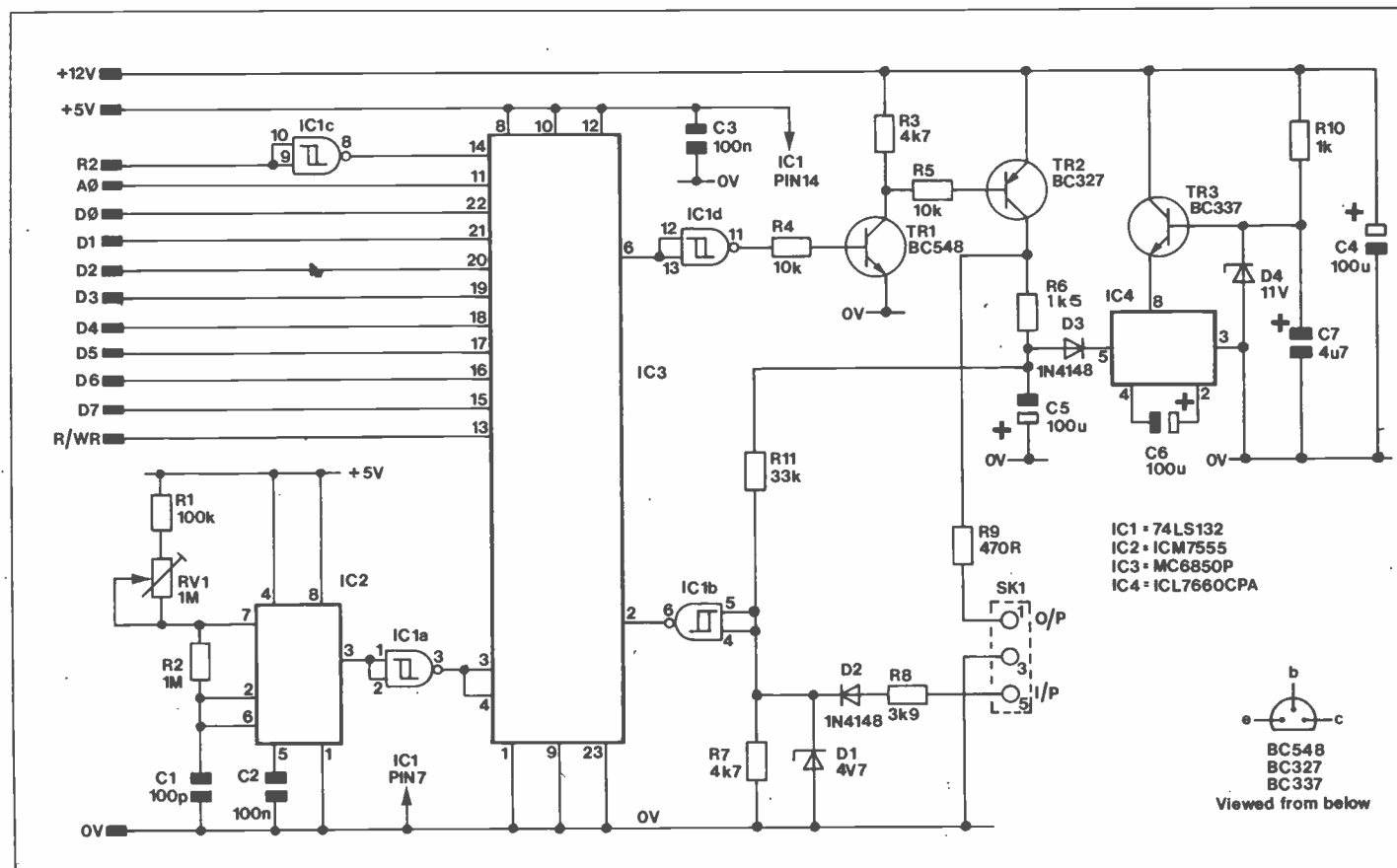


Figure 1. Circuit Diagram

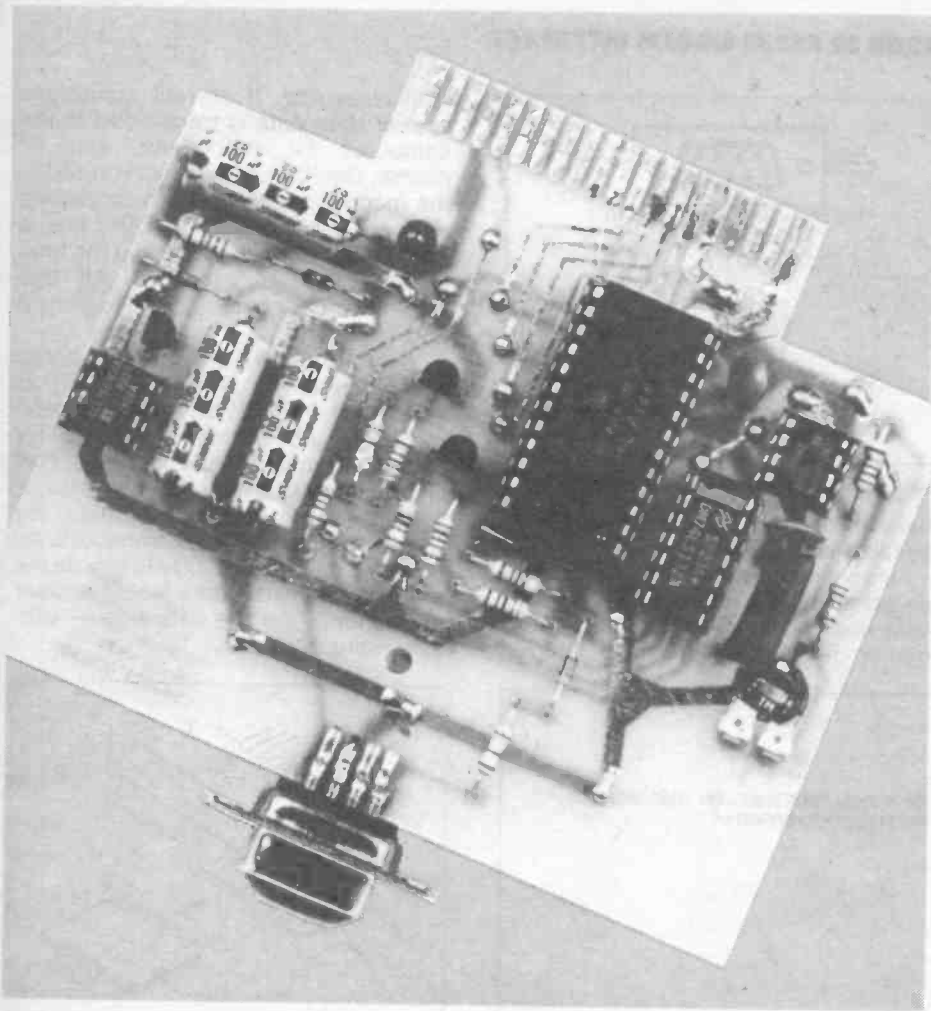



sure they are fitted the correct way round!

Transistors TR1 to TR3 and all four IC sockets should be mounted as shown on the legend. Carefully solder each component in place, remove excess leads, and clean the track. Finally fit and solder SKT1 in place, then insert IC4 only. You should inspect your work before testing, rechecking all components and solder joints for errors.

## Circuitry and Testing

Characters are transmitted or received at a particular speed, or Baud rate. The standard telecommunication speed of 300 Baud is used for the SCIA, and, although not critical, RV1 should be set with the centre of its wiper pointing to the arrow on the PCB legend. Insert the module (component side upwards) into the ROM expansion socket on the right hand side of the computer. Switch on the Dragon and wait for the usual display to appear. If vertical lining appears, or nothing at all happens, then switch off immediately and remove the module for inspection.

Using the positive end of C5 as the 0V reference point, place a voltmeter between 0V and IC4 pin 8, and check

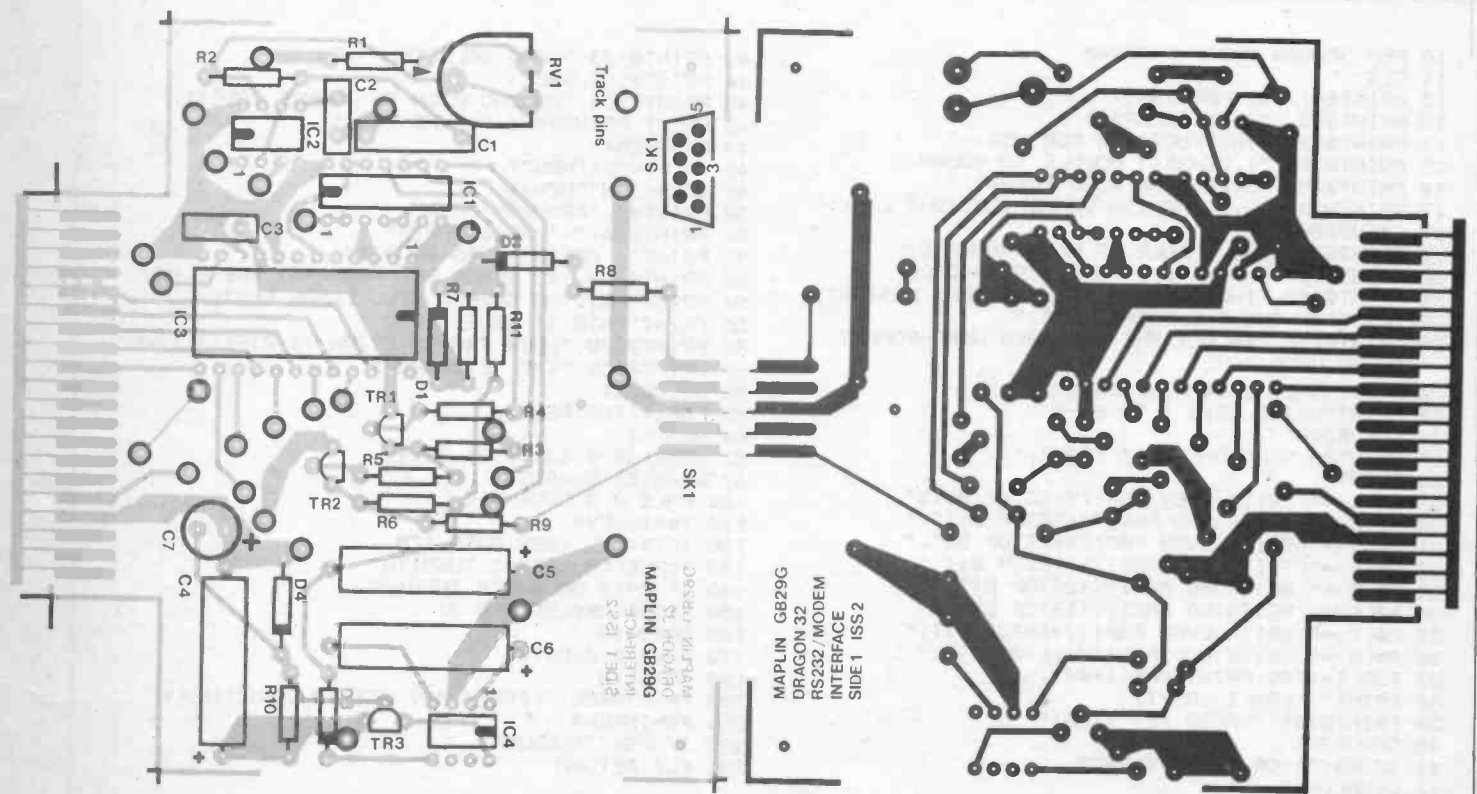


Figure 2. PCB legend and artwork

## DRAGON 32 RS232 MODEM INTERFACE

for approx. +10.3V. Now check for approx. -9.8V between 0V and pin 5 of SKT1. Remove the module, insert the remaining ICs, and re-fit the module into the Dragon.

IC2 is a CMOS 555 timer, and is used for the clock oscillator. IC3 divides the clock signal to determine the Baud speed for character transfer. With a 4.8kHz clock and a programmed divide by 16 code, the Baud rate is 300. Three divide ratios of 1, 16 and 64 are available.

IC4 is a voltage inverter, producing -10V across C5 for a +10V input from TR3. This negative voltage is necessary to produce RS232 compatible levels for signal transmission. Serially coded signals are converted from pin 6 of IC3, IC1, TR1 and TR2 to RS232 +12V, -10V levels at SKT1, pin 5. Input signals on SKT1, pin 1 are chopped and poten-

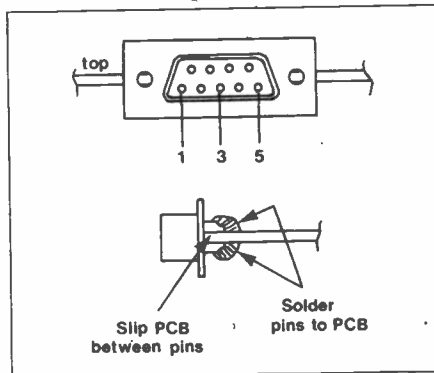


Figure 3. Plug and socket external connections

tially divided by R8, D2 and R7 to a level suitable for TTL use.

Incoming serially coded signals are decoded by IC3 into eight bit parallel data bus codes. By reading IC3, information is obtained from an internal

status register. If correct conditions appear then data is transferred to the computer for processing, etc. Of course, the IC must be synchronised to the incoming data for such conditions as the number of STOP/START bits, a PARITY bit, ODD or EVEN, and the total number of bits expected. All this information is contained in Program 2 and Table 1.

Two addresses are used as ports: PORT A address is 49152, PORT B address is 49153. Port A may be read for status checks, or written to for setting internal control conditions. Port B is read for received character data, or written to for transmitting data. By using PEEK and POKE commands, an R2 pulse on pin 14 of IC3 will enable the system, otherwise data would appear permanently on the data bus — with interesting results!

```

10 CLS
12 PRINT@40,"' TEST PROGRAM'
14 PRINT@96,"CONNECT BOTH RS.232 (IP/OP)PINS TOGETHER,ON THE MODULE."
16 PRINT"THEN TYPE CHARACTERS DIRECT FROMTHE KEYBOARD!"
18 PRINT@234,"*****"
20 A=49152:B=49153
22 POKEA,3:POKEA,21
24 T#=INKEY#:IFT#=""THEN24
26 POKEB,ASC(T#)
28 IFPEEK(A)<3THEN28
30 PRINTCHR$(PEEK(B));
32 GOTO24

```

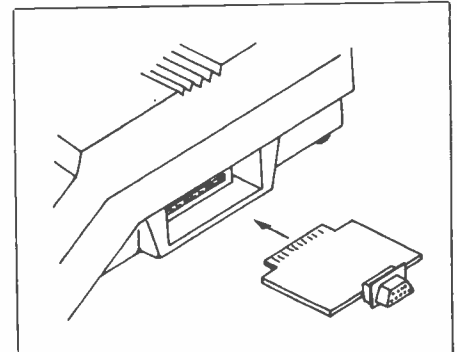


Figure 4. ROM Port

```

10 REM DRAGON MODEM PROGRAM
11 CLS
12 PRINT@41,"***MAPLIN***"
13 PRINT@73,"MODEM PROGRAM"
14 PRINT@128,"INSTRUCTIONS FOR USE:-"
15 PRINT@192,"1.CONNECT MODULE TO MODEM."
16 PRINT@256,"2.PROGRAM WORD FORMAT."
17 PRINT@320,"3.ESTABLISH COMMUNICATIONS LINK."
18 GOSUB200
19 PRINT@34,"THE MODULE IS PROGRAMMED BY"
20 PRINT@66,"ENTERING A'WORD-FORMAT'CODE"
21 PRINT@160,"THERE ARE 8 CODE OPTIONS LISTED"
22 PRINT"ON THE FOLLOWING PAGE."
23 PRINT@256,"SELECT THE REQUIRED WORD-FORMAT
    TO BE USED."
24 PRINT"THEN ENTER THE CODE"
25 PRINT"USING KEYS 1 TO 8:-"
26 GOSUB200
27 PRINT@6,"'WORD-FORMAT'TABLE."
28 PRINT
29 A$(1)="(7BITS)EVEN PARITY+2STOP BITS"
30 A$(2)="(7BITS)ODD PARITY+2STOP BITS."
31 A$(3)="(7BITS)EVEN PARITY+1STOP BIT."
32 A$(4)="(7BITS)ODD PARITY+1STOP BIT."
33 A$(5)="(8BITS)NO PARITY+2STOP BITS."
34 A$(6)="(8BITS)NO PARITY+1STOP BIT."
35 A$(7)="(8BITS)EVEN PARITY+1STOP BIT."
36 A$(8)="(8BITS)ODD PARITY+1STOP BIT."
37 FOR I=1TO8:PRINTCHR$(I+48);
38 PRINT". ";A$(I):NEXTI
39 PRINT@359,"PRESS KEY 1TO8!"
40 GOSUB201
41 IF K$<"1"OR K$>"8"THEN27
42 C=VAL(K$)
43 PRINT@103,"CODE SELECTED=";C
44 PRINT@162,A$(C)
45 PRINT@354,"DO YOU WISH TO CHANGE CODES?"
46 PRINT:PRINT@426,"(TYPE Y/N)"
47 GOSUB201
48 IF K$="Y"THEN27
49 IFK$<>"N"THEN43
50 PRINT@9,"PROGRAM DATA:-"
51 PRINT@64,"-";A$(C):PRINT
52 PRINT"- SPEED @ 300 BAUDS!"
53 PRINT@192,"TO START THE PROGRAM, PRESS ANY"
54 PRINT"KEY.THE SCREEN WILL CLEAR UNTIL"
55 PRINT"DATA IS RECEIVED!"
56 PRINT@320,"DATA TRANSMISSION IS DIRECT FROM"
57 PRINT@352,"THE KEYBOARD."
58 GOSUB201
59 FORI=1TOC:READ C
60 NEXT I
61 DATA1,5,9,13,17,21,25,29
62 A=49152:B=49153
100 POKE A,3:POKE A,C
110 T#=INKEY#
120 IFT#<>" " THEN GOTO 170
130 X=PEEK(A):IFX=2 THEN110
140 IF X=19 OR X=126 THEN100
150 PRINTCHR$(PEEK(B));
160 GOTO110
170 POKE B,ASC(T#)
180 GOTO110
200 PRINT@450,"(PRESS ANY KEY TO CONTINUE!)"
201 K#=INKEY#
202 IF K#=""THEN201
203 CLS:RETURN

```

## DRAGON 32/RS232 MODEM INTERFACE

Type in Program 1 and connect pins 1 and 5 on SKT1 together on the module. The idea is to transmit a character into the receive register and print it on the TV display, thus testing the module.

Line 22 first resets the status register and initialises both the receiver and transmitter using data code three (D0 and D1 = Logic 1), and second, a clock divide ratio of 16 is selected with code 1 (D0 = Logic 1) added to a word format code of 20 (D2 and D4 = Logic 1) or 21.

The keyboard is scanned to see if a key is being pressed, and, if so, an ASCII code value for the key is POKEd into Port B and transmitted, along with all bit information. Port A is scanned to see if correct data has been received, by looking for D0 = Logic 1. D1 will normally be at Logic 1 when the transmit data register is empty, so data code three (D0 and D1 = 1) is required to step the program forward, whereupon Port B is read and data printed on the display.

Run the program and press any key. The character will be printed, showing all is well.

Initial program requirements are for the setting of code 3 (POKE A,3) followed by divide code plus word format code (POKE A + total) 0 to 34.

Generally, code 21 can be used, which breaks down as divide clock by 16 and select word format of 8 bits (no parity) and 1 stop bit. This should suit most user requirements.

The MC6850 has many other control and status conditions associated with it, and a complete article could be written on this IC alone. However, informative data sheets are available from Maplin for those wishing to pursue the subject further. Program 2 gives information for those using the SCIA

module and sets up the programming data to your requirements. ASCII coded data may be transmitted or received over a suitable link and printed to the display. If there is no 'echo-back' facility on the equipment connected to the module, then the characters transmit-

ted from the Dragon will not be returned and printed. This facility exists for data clarification, so that you know exactly what you are sending out. Save all programs on tape for future use, and don't forget to dial 'CASHTel' when ready to use the working module.

Table 1a Register Contents (Ports A and B)

Data Bus	Port B (Rx)	Port B(Tx)	Port A (write)	Port A (read)
D0			Clock divide	Rx register full
D1	Receive	Transmit	Clock divide	Tx register empty
D2	Codes 0-127	Codes 0-127	Word Format	(Carrier Detect)
D3	ASCII	ASCII	Word Format	(Clear to Send)
D4	ASCII	ASCII	Word Format	Framing Error
D5	ASCII	ASCII	(Tx Control)	Rx Overrun
D6	ASCII	ASCII	(Tx Control)	Parity Error
D7	ASCII	ASCII	(Rx Int Enable)	(Int Request)

Table 1b (Control Register — Port A) Reset/Divide

Function	Data Bus								Code	
	D0	D1	D2	D3	D4	D5	D6	D7		
Reset	1	1	0	0	0	0	0	0	0	3
Divide by 64	0	1	0	0	0	0	0	0	0	2
Divide by 16	1	0	0	0	0	0	0	0	0	1
Divide by 1	0	0	0	0	0	0	0	0	0	0

Table 1c. (Control Register — Port A) Word Format

Word Format	D2	D3	D4	D5	D6	D7	Code
7 bits. Even par. + 2 stop bits	0	0	0	0	0	0	0
7 bits. Odd par. + 2 stop bits	1	0	0	0	0	0	4
7 bits. Even par. + 1 stop bit	0	1	0	0	0	0	8
7 bits. Odd par. + 1 stop bit	1	1	0	0	0	0	12
8 bits + 2 stop bits	0	0	1	0	0	0	16
8 bits + 1 stop bit	1	0	1	0	0	0	20
8 bits. Even par. + 1 stop bit	0	1	1	0	0	0	24
8 bits. Odd par. + 1 stop bit	1	1	1	0	0	0	28

D0 and D1 — see table 1b.

### PARTS LIST FOR DRAGON 32 RS232/MODEM INTERFACE

Resistors — All 0.4W 1% Metal Film

R1	100k	
R2	1M	
R3,7	4k7	
R4,5	10k	2 off
R6	1k5	2 off
R8	3k9	
R9	470R	
R10	1k	
R11	33k	
RV1	1M Hor sub-min Preset	

Capacitors

C1	100pF Silver Mica	
C2,3	100nF Minidisc	2 off
C4,5,6	100uF 25V Axial Electrolytic	3 off
C7	4u7F 35V Tantalum	

M100k
M1M
M4K7
M10K
M1K5
M3K9
M470R
M1K
M33K
WR64U

Semiconductors

D1	BZY88C4V7		
D2,3	1N4148	2 off	QH06G
D4	BZY88C11V		QL80B
TR1	BC548		QH15R
TR2	BC327		QB73Q
TR3	BC337		QB66W
IC1	74LS132		QB68Y
IC2	ICM7555		YF51F
IC3	MC6850P		YH63T
IC4	ICL7660CPA		WQ48C
Miscellaneous			YY75S
SK1	D-Range 9-Way Skt		RK61R
	8 Pin DIL Skt	2 off	BL17T
	14 Pin DIL Skt		BL18U
	24 Pin DIL Skt		BL20W
	P.C.B.		GB29G
	Track Pin	1 Pkt	FL82D

A complete kit of all parts is available for this project.  
Order As LK12N (Dragon/RS232 Interface kit). Price £13.75

# USING THE COMMODORE 64

by Nigel Fawcett

During the course of this and subsequent issues of Electronics I shall be including articles which should be of considerable use to the CBM 64 owner. These articles will cover many of the subjects which are not fully explained, or are merely hinted at in the manual which accompanies the 64. In many instances the 'Programmers Reference Guide' is mentioned and this publication is now available from Maplin, order code WK62S, price £13.25.

In this issue I shall demonstrate the use of the moveable object blocks or sprites as they have become known.



At the heart of the 64's graphics system lies the video interface chip (6567). This IC is responsible for managing the 40 column by 25 line text display, the 320 by 200 dot high resolution graphics display and the sprites (MOBS). In addition to these functions the 6567 also handles the character sets, split screen, colour modes, scrolling and a host of other graphics related jobs.

When the 64 user wants to write his own games, or even master the theory behind the commercially available arcade type games, it is natural that an understanding of mobs should be attained. The basic concept is that one should be able to define a shape,

reasonably recognisable and proportioned for the application, and then be able to place it anywhere on the screen (this also includes those parts of the screen which lie above, below, left or right of the screen edges and which are therefore technically out of

sight). In addition they should be able to move smoothly in any direction desired. With the 6567 all this is possible. First, graph paper should be used to design the bit pattern for the sprite. Each sprite is mapped on a grid which is 24 bits wide by 21 bits deep. Every bit which is 'on' will be displayed on the screen in the colour chosen for that sprite. In memory the data for the sprite patterns is arranged in 63 consecutive bytes

Continued on page 59

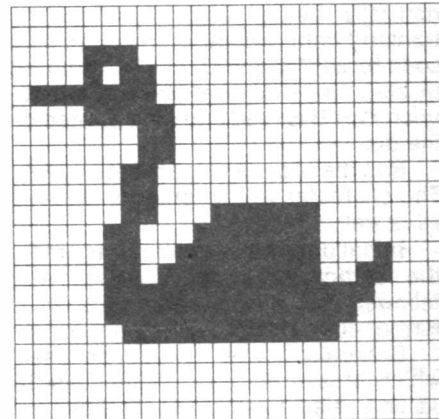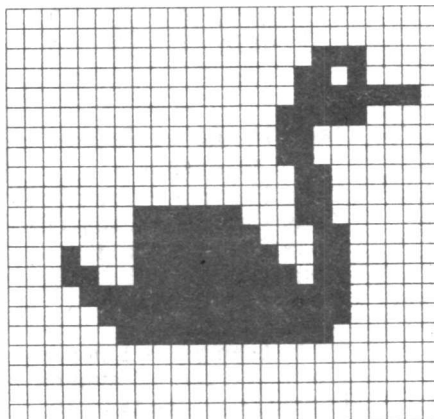

```

100 PRINT CHR$(147)
1000 FOR I=14336 TO 14463
1010 READ A : POKE I,A : NEXT I
1020 VC=53248
1030 POKE 2046,224
1040 POKE VC+21,64
1050 POKE VC+39,64
1060 VC+12,0 : POKE VC+13,100
1070 POKE VC+16,64
1080 FOR I=15360 TO 15400
1090 READ MC : POKE I,MC : NEXT I
1100 SYS 15360 : FOR I=0 TO 31
1110 NEXT I : GOTO 1100
3000 DATA 0,0,0,0,0,0,0,0,112,0,0,208
3010 DATA 0,0,254,0,1,240,0,1,128,0,1
3020 DATA 128,0,0,192,0,0,192,1,248,192
3030 DATA 1,252,96,17,254,96,25,255,96
3040 DATA 15,255,224,7,255,224,3,255
3050 DATA 192,0,0,0,0,0,0,0,0,0,0,0,0
3060 DATA 0,0,0,0,0,0,14,0,0,11,0,0,127
3070 DATA 0,0,15,128,0,1,128,0,1,128,0
3080 DATA 3,0,0,3,0,0,3,31,128,6,63,128
3090 DATA 6,127,136,6,255,152,7,255,240
3100 DATA 7,255,224,3,255,192,0,0,0,0,0
3110 DATA 0,0,0,0,0,0,0,0
3500 DATA 173,254,7,201,224,208,11,173
3510 DATA 12,208,201,36,240,15,238,12
3520 DATA 208,96,173,12,208,201,0,240
3530 DATA 10,206,12,208,96,169,225,141
3540 DATA 254,7,96,169,224,141,254,7,96
    
```

## USER VIEWS

The Maplin Modem, and the CASHtel and Maptel services have been much more successful than anyone anticipated. Especially useful to us have been the user comments, a selection of which have been printed below. We are always interested in user comments and suggestions on what you would like to see on the system, e.g. User Group pages, bulletin board services. User groups (any machine) are welcome to get in touch with us, with the information they would like displayed, and we will see what we can do.

1. Terminating the isolating transformer with 600 ohms (across D1) enables correct setting of RV3. System now seems to have high immunity from noise. Stewart Hoare.  
*We agree that 600 ohms should give correct results, but, under practical conditions, the line rarely exhibits a 600 ohm impedance, and therefore the best way of setting up is to make a call to a friend and get them to leave their phone off the hook whilst you adjust RV3 for minimum crosstalk.*

2. I have found it very difficult to get onto your system A. Perhaps it would be worth adding a few more ports? Roger Lee.

*It is not extra ports that we need, but extra lines. More will be added in the future, according to demand.*

3. If you sent Control N at the start of logon, please don't - it means reverse video to me. Andy Michaei.

*We don't.*

4. How do I get rid of the double echo? Ian Atkins.

*Either you are running in half duplex instead of full duplex, or there is something in your program which is giving a double echo.*

5. It would be nice to have column width selectable. S.R.Vann.

*It would, we agree, but there are just too many options, and this makes it impracticable at present.*

6. Why don't you use both upper and lower case? Roderick McLeod.

*We do receive both upper and lower case, but we cannot transmit using lower case because of the problems this causes for some micros (notably the Dragon), which will not accept it.*

7. A problem occurs with your system not always echoing back my characters. This is only confined to your system and not the others I use. Anon.

*Our system should always echo back, and we have not had any other complaints. Any comments from anyone else?*

# MODEM NEWS

8. When will bulletins become available? J.P. Cowell.

*During August.*

9. I would like to see a good modem program for the BBC that loads to cassette. R.H. Gregory.

*There is one published in this issue.*

10. I am using a Transdata 300 printer terminal and I find that there are two characters missing at the beginning of each line, due (I think) to the slow return of the carriage in between lines. Is there any way of delaying the output from your computer? Michael King-Beer.

*Please transmit 3-5 DEL characters after 'CR' 'LF' to allow elderly mechanical terminals time. Anon.*

*There is nothing we can do at present, but we are looking into this one. Please bear with us.*

11. At 300 Baud Maptel is fairly slow. Are there any plans for other speeds, e.g. 1200/75 and 600? Mike Harvey.

*We are looking into the possibility at the moment, and hope to have something fairly soon.*

12. Please let us have a CBM 64 group page. P.A.Friend.

*Would you consider making a page available for Maplin Modem users? Dr N. Robinson.*

*Your wish is our command.*

13. Why is there no delete feature on input of messages? Mike Hobbs.

*Delete vary too much between different computers. However, we are rethinking this one.*

14. I would appreciate it if you would enrol me as a user of your system. I have a Barclaycard number, please advise me of the procedure. Also, I would like to know if the system will eventually be available after 17.30 hours, and if so until what time? P.A.Friend.

*You do not need to be 'enrolled' into our system. The only requirement is that you have a customer number, which you can obtain by writing to us, enclosing your name and address, and details will be mailed to you. Alternatively, if you have already placed an order with us, you will have a customer number, and can use that.*

*The Maptel/Cashtel system is in the process of continuous expansion (as some of you*



## MODEM BOX

At last! The Maplin Modem has a box available. Custom built for us, the front panel is silk screened with a legend in white on black, and the rest of the box an attractive dark blue. The whole case comes in just two pieces, and will make your modem look completely professional.

**All this for the incredibly low price of only £9.95. Order As.YK62S (Modem Box).**

```

5 REM BBC VDU PROGRAM R.J.B.K. 83
10 CLS
20 * FX 7,3
30 * FX 8,3
40 * FX 2,2
50 A = INKEY(1); IF A = -1 THEN 100
60 * FX 3,7
70 VDU A
80 * FX 3,0
90 GOTO 40
100 * FX 2,1
110 * FX 3,0
120 A = INKEY(1)
130 IF A > 31 THEN VDU A AND 127
140 IF A = 41 THEN GOSUB 200
150 IF A = 13 OR A = 10 THEN VDU A
160 GOTO 40
200 A = 10 : VDU A
210 A = 13 : VDU A
220 RETURN
    
```

*may have noticed!), and we are experimenting with a non-interactive order system outside normal working hours at present. We hope this will provide a viable alternative, but we will consider making the full service available should the demand prove sufficient to justify it.*

## USING THE COMMODORE 64 *Continued from page 58*

(21 rows of 3 bytes [3 bytes = 24 bits]). The basic manual gives this information in greater detail, so refer to the relevant chapter for a fuller description.

Enough waffle — let's have a demonstration!

The following program sets up a sprite from basic, and then uses a machine code routine to handle the movement. The routine is continually recalled from basic, allowing you to add to the program which could form the basis for a game. A swan is set up using a sprite and swims backwards and forwards across the right hand side of the screen. This frees the rest of the screen for more action.

You will notice that two images are set up in memory for the swan, one facing right and one facing left. If I had not done this the poor swan would have had to swim backwards!

The assembly language routine is only shown for reference, the actual data for the machine code is included within the basic program.

September 1983 Maplin Magazine

SWAN	LDA	2046	CMP	0
	CMP	229	BEQ	RSPAT2
	BNE	RVSWAN	DEC	53260
	LDA	53260	RTS	
	CMP	46	RSPAT1	LDA 230
	BEQ	RSPAT1	STA	2046
	INC	53260	RTS	
	RTS		RSPAT2	LDA 229
RVSWAN	LDA	53260	STA	2046
			RTS	

# ZX SPECTRUM RS232/MODEM INTERFACE

Our series of computer/modem interfaces continues with one for the Spectrum, which can be operated directly from BASIC, without typing or LOADING lengthy program listings. Access to (or exit from) the module may be initiated as required, either directly from switch-on or during a normal program run, without changing any previous contents of memory except the display file, and does not require RAM space to operate.

## Interface


For computers to communicate with external sources suitable interfaces must be used. These must have the necessary facilities to enable compatibility with both devices and be under software control.

Transmitted or Received data is formatted as a character containing so many 'bits', and serialised for data transfer in a continuous stream. The speed of transfer is variable, but is usually standardised at 300 Bauds for modem/telephone links; higher Baud rates being required for higher transmission speeds.

Three wire links are used, one for transmitting data, one for receiving data, and a common 0V. Signal levels are to the RS232 standard of +12V amplitude at up to 20mA loads.
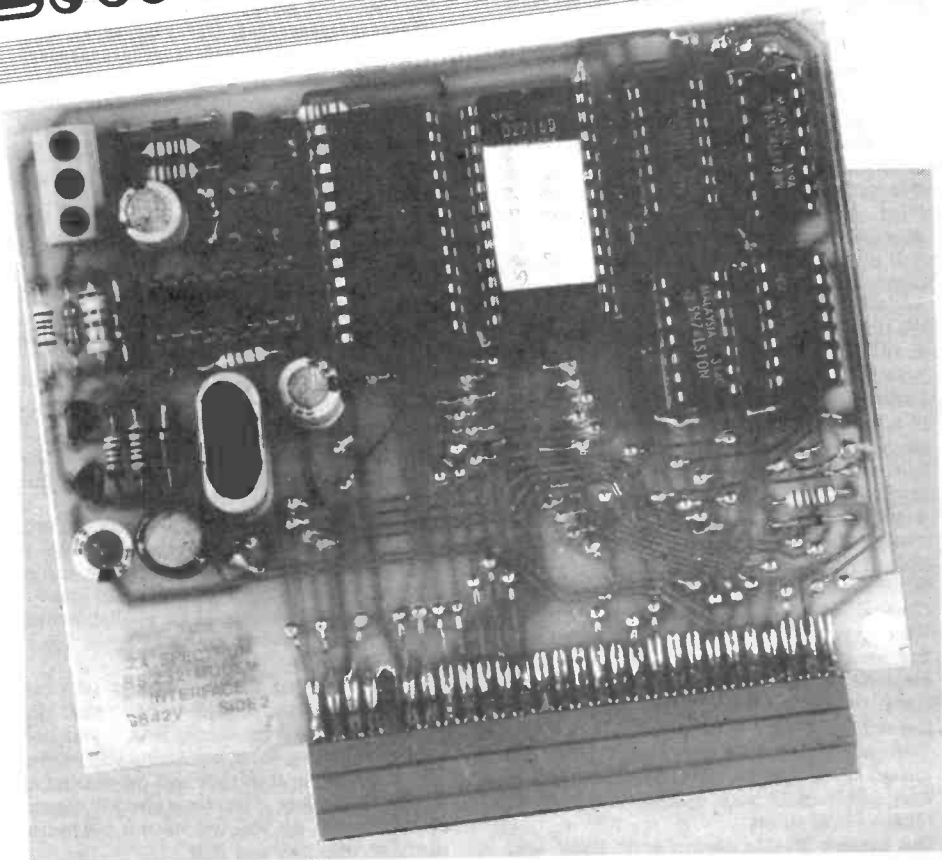
## Circuit Description

Within the Spectrum ROM, before the character set, lies an unused area of memory between addresses 14446 and 15615. By disabling the ROM at the correct time this area is freed for use by the EPROM IC7 and ASCIA IC6 (A Synchronous Communications Interface Adaptor). ICs 1 to 4 perform the decoding necessary for memory mapping two areas. Addresses 14592 to 15584 are used for printing and operating sub-routines, and addresses 15585 to 15615 are reserved for I/O scanning, word formatting, and data transfer. R1 and D1 supply the ROM CS disable pulse from IC3, also enabling IC7 during the correct read only address



block. IC6 can be read or written to by the system within the address block determined by A5,6,7 and IC4 pin 11, but only four addresses are used, and these are detailed further on in the article.

IC5 is a fourteen stage ripple counter and clock oscillator running at 2.4576MHz, with C1, R10 and X1 determining the fundamental frequency, and this produces four divider outputs, shown in table 1.

Pin	Frequency	Baud	Link
6	19.2kHz	300	A
4	38.4kHz	600	B
5	76.8kHz	1200	C
7	153.6kHz	2400	D

Table 1.

Serial data output is from IC6 pin 6 and inverter IC2, whose normally low output holds TR2 in the 'off' state. TR1 does not conduct, due to lack of base drive current, and its collector sits at -10V potential, which appears at the RS232 output socket.

Pin 23 of the edge connector is notated -12V (page 160 of the user manual), when in fact it is derived from an internal oscillator, used for generating +12V and -5V supplies for the memory ICs, and takes the form of a 20kHz pulse waveform at approximately 12V. By connecting this signal via DC blocking capacitor C4 and referencing to ground via D4, a level shifted -12V signal is developed. This is rectified and smoothed by D3 and C5 to give approximately -10V DC at R5. TR1 switches between +12V and -10V during data transmission, producing the required RS232 levels to line. Incoming data is kept to a positive potential by D2, for switching TR3 and as a TTL input to pin 2 of IC6.

## Module Operation

The EPROM IC6 holds 746 data bytes, most of which are used to display the MENU and WORD FORMAT options necessary for programming ASCIA IC6. Eight options are available for different

- by Dave Goodman
- ★ Connects the Spectrum to modems or other computers
  - ★ RS232 compatible — 300/2400 Baud rates
  - ★ Completely self-contained operating system — no programming, LOADING or SAVEing required!
  - ★ Plugs into expansion socket or motherboard


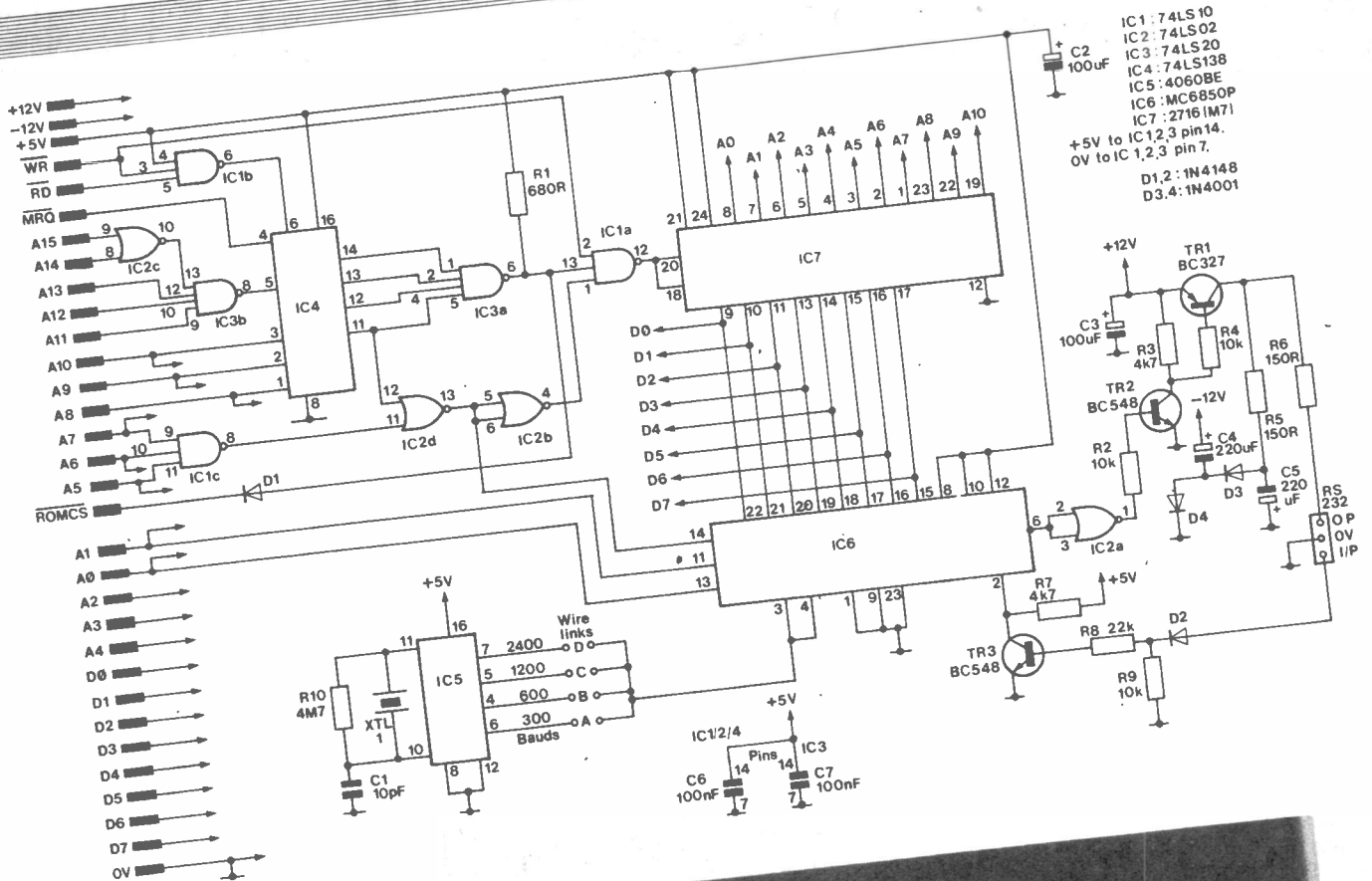


Figure 1. Circuit diagram.

word formats, setting total bits per character, odd, even, or no parity, and 1 or 2 stop bits. Master reset and clock divide ratios are also selected with these codes using data bits D0 to D4.

Within IC6 there are four registers accessible for use. Each register has a specific address and is either read or write in operation. See table 2 for definitions.

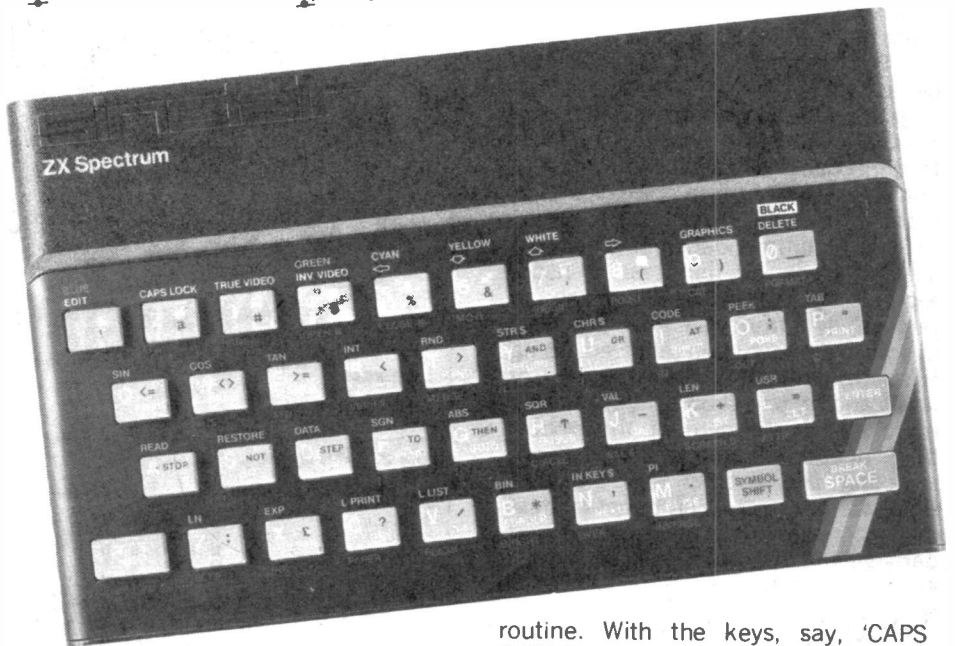After control register has been set, the status register is examined to see if any data has arrived. If not, then the Spectrum keyboard is scanned for a key down. Various routines look for shifted or normal key operations, and also too many keys down before returning to the input status scanning



Address	Register	Use
15612	Control (WR)	Reset, clock, and word format
15613	status (RD)	inspect incoming data
15614	Tx data (WR)	send 'Spectrum' codes to line
15615	Rx data (RD)	incoming data for printing

routine. With the keys, say, 'CAPS SHIFT' and 'A', depressed, the formatted ASCII code '65' is transmitted once only, but if the key is held down for more than two seconds the character code will be repeatedly transmitted until released.

During repeat time the STATUS register is being scanned so that re-

ceived data has priority over transmitted data. This ensures that characters are not lost when 'echo' is utilised. The STATUS register indicates parity error, overrun, frame error, whether the transmit register is empty, or if receive register is full. Control is directed according to these conditions so that when a character is correctly decoded it will be sent to the receive data register and read by the Spectrum CPU for printing, etc.

Specifications for the MC6850 ASCIAs are available from us if further information is required.

## Construction

A double-sided PCB is used which requires 86 track through pins to be fitted. Insert these from side 2 into all holes marked with a circle, and carefully solder each pin to both sides of the board. Close track proximity requires very careful use of the soldering iron, otherwise bridging or shorting will occur, which can be difficult to trace and could result in damage being done to the Spectrum, so keep all soldering to a high standard.

This done, refer to the parts list and fit all ten resistors by bending each lead at right angles to the body and inserting in the correct position, flat to the board. Diodes D1 and 2 are fitted in the same way, except that each black band, or cathode, must align with the white band on the legend. Repeat for diodes D3 and D4. These should have a silver band.

Now solder the component leads onto the PCB and cut off the excess wire, before mounting capacitors C1 to 7. Note that C2 to 5 are electrolytic, and must be orientated for correct polarity; the PCB legend has a positive sign, denoting the lead NOT marked with a negative sign on the component body. Finally, insert Xtal 1 and the three way PC terminal, with the terminals facing outwards. Solder these components in place.

It is recommended that a suitable solvent, such as thinners, is used, together with a stiff paint brush, to remove flux from the PCB after the excess spills have been removed. Doing this will facilitate close inspection of joints and help to show up track shorts more clearly. Remember the importance of good workmanship whilst constructing this project, as, although there are only a few components, mistakes can easily be made which can damage the Spectrum, so check your work thoroughly.

## Testing

Connect the module either directly into a motherboard if you have one, or solder a 2x28 way 0.1in socket to the edge connector (see parts list) and plug into the rear expansion port. For the moment, fit IC3 only. A voltmeter or oscilloscope will be required for making a few checks around the circuit, and the

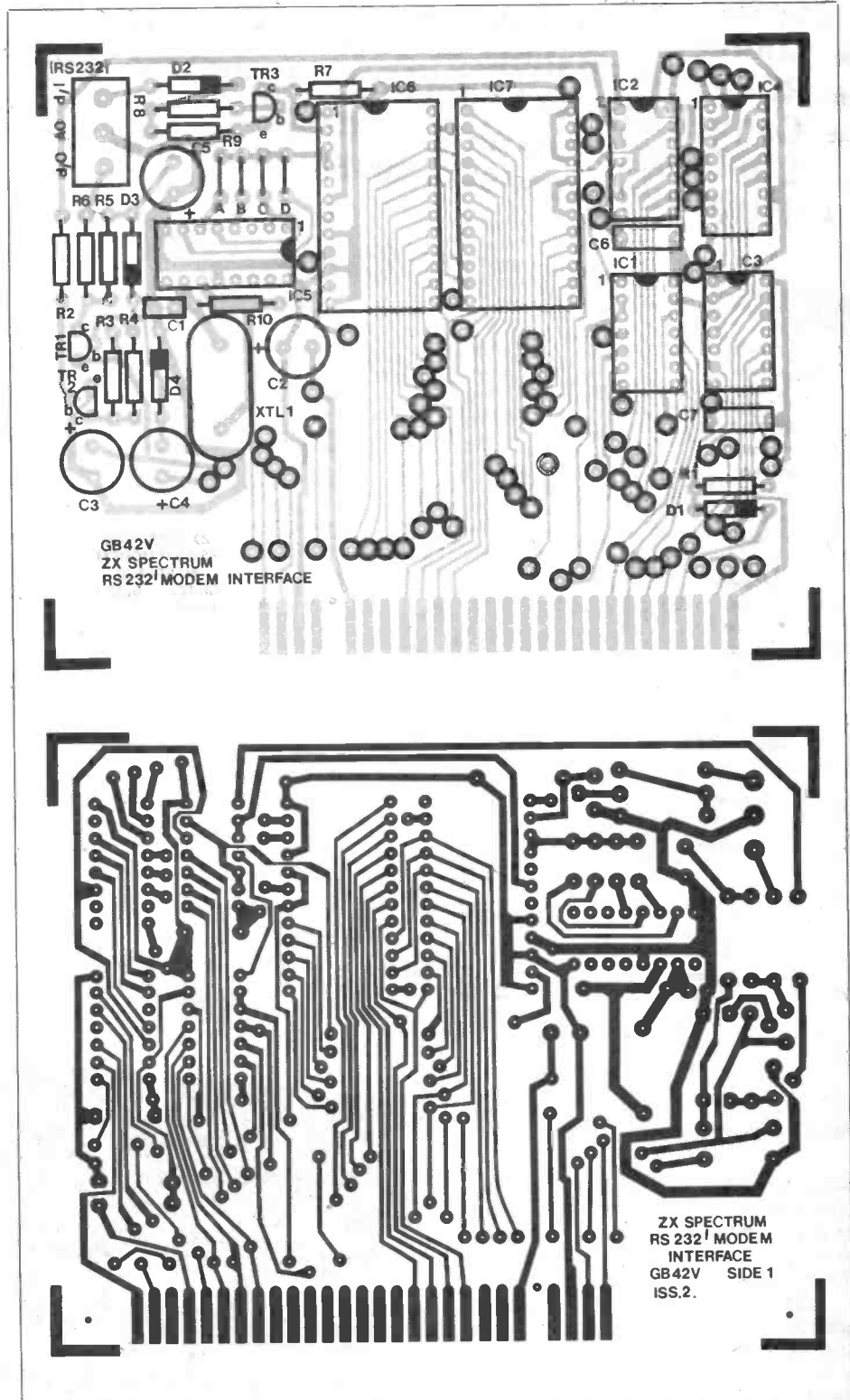


Figure 2. PCB layout.

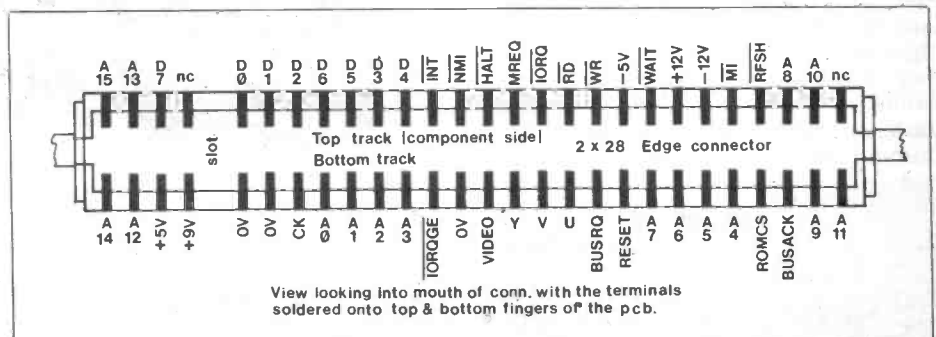


Figure 3. Pin functions.



ZX Spectrum



centre terminal of the RS232 connector socket can be used as an 0V reference point.

With TV and PSU connected, switch on and check for usual display and keyboard operation. Any problem here will appear either as vertical lining or a permanent black display, in which case you should switch off immediately and remove the module. If all is well, you should check for:

1. +4.5V between 0V and IC4 pin 16
2. +0.2V between 0V and the junction of D1 and R1
3. +11 to +12V between 0V and R3/TR1 emitter
4. -11 to -12V between 0V and the RS232 output socket

Switch off, remove the module, and fit link A. The remaining six ICs can now be fitted and the module reinserted. Switch on again, and type:

```
10 POKE 15612,3:POKE 15612,1
20 POKE 15614,85:GOTO 20
```

Recheck the RS232 output for -11V and run the program. Line 20 continually transmits ASCII code 85, or 'U' which has an even mark to space ratio. The average output reading will therefore be halfway between -11V and +11V, i.e. approximately 0V. Break the program and check that the reading returns to -11V again. This test proves that address decoding logic, ASCIA, and output converter stages are functioning correctly.

Remove the voltmeter, connect the RS232 output and input terminals together with a short length of wire and type RAND USR 14592, then ENTER, to access the module. A MENU will be displayed listing word format codes a to h and instructions showing how to return either to BASIC or MENU. All entries are direct from the key concerned, without using ENTER, and, for letters only, normal lower case is transmitted. CAPS SHIFT is used for changing from lower to upper case, but will not function with numbers 1 to 0, so that CAPS LOCK, CURSOR, and DELETE are not available. All red shift symbols can be used with the SYMBOL SHIFT

key, as can the ENTER key, remembering that shifted A (stop) will display the MENU. Pressing both CAPS and SYMBOL SHIFT keys allows a return to BASIC, upon which the module is no longer effective until called by the USR instruction.

Press both SHIFT keys to prove that this is so, and the O.K. prompt will appear. Type RAND USR 14592 again for the MENU and select WORD FORMAT code f. You will see that all single keys above H are inoperative and only A to H are recognised. The 'DATA?' prompt is waiting for incoming information for printing, so press the A key. Lower case a will appear at the start of a new line (automatic carriage return), now press CAPS SHIFT and A. Upper case A will be printed adjacent to the last character. Hold the A key down and printing will repeat, filling the line with 32 characters before auto-scrolling. Clear the screen by holding the ENTER (carriage return) key down, then select STOP to return to MENU.

systems could require different format codes. If data is being received before the module is selected the characters may be unsynchronised, and garbage will be printed, so have the module functioning before data arrives, to avoid this occurring. Baud speeds up to 2.4KB are selected by fitting a link in the appropriate position.

Connected for 300 Bauds, which is the CCITT standard for use over telephone lines, it will match Maptel and also our Modem.

In normal use, transmitted data will not be displayed unless peripheral equipment connected to the interface has an 'echo' facility, which sends data back on receipt of incoming data. Shorting both transmit and receive lines to simulate echo may cause problems when using modem systems, and is recommended for test purposes only. Finally, the EPROM IC7 has 256 spare bytes available at the end of the instruction set which have been left high or FF. Additional instructions can be placed here and called as a machine code routine, providing you have the necessary equipment for doing this.

## The Module In Use

The most common word format used is f, or 8 bits per character with one stop bit. The format is applicable to our Maptel A and B systems, but other

The first spare address is:  
Spectrum — 15338  
EPROM — 1002

## ZX SPECTRUM RS232/MODEM INTERFACE PARTS LIST

Resistors — All 0.4W 1% metal film unless specified.

R1	680R		(M680R)
R2,4,9	10k	3 off	(M10K)
R3,7	4k7	2 off	(M4K7)
R5	150R (½W carbon)		(S150R)
R6	150R		(M150R)
R8	22k		(M22K)
R10	4M7 carbon film ½W 5%		(B4M7)

### Capacitors

C1	10pF ceramic		(WX44X)
C2,3	100uF 25V P.C. electrolytic	2 off	(FF11M)
C4,5	220uF 16V P.C. electrolytic	2 off	(FF13P)
C6,7	100nF disc	2 off	(BX03D)

### Semiconductors

D1,2	IN4148	2 off	(QL80B)
D3,4	IN4001	2 off	(QL73Q)
TR1	BC327		(QB66W)

TR2,3	BC548	2 off	(QB73Q)
IC1	74LS10		(YF08J)
IC2	74LS02		(YF02C)
IC3	74LS20		(YF14Q)
IC4	74LS138		(YF53H)
IC5	4060BE		(QW40T)
IC6	MC6850P		(WQ48C)
IC7	2716/M7		(QY57M)

### Miscellaneous

XTL1	MP crystal 2.4576 MHz		(FY81C)
	P.C. Board		(GB42V)
	3 way P.C. terminal		(RK72P)
	Trackpins	2 pkts	(FL82D)
	D.I.L. socket 24 pin	2 off	(BL20W)
	D.I.L. socket 16 pin	2 off	(BL19V)
	D.I.L. socket 14 pin	3 off	(BL18U)

### Optional part

0.1 in 2 x 28 PC Edgecon	(FG23A)
--------------------------	---------

A complete kit of all parts, excluding FG23A, is available.  
Order As LK21X (Spectrum RS232 Kit) Price £17.95

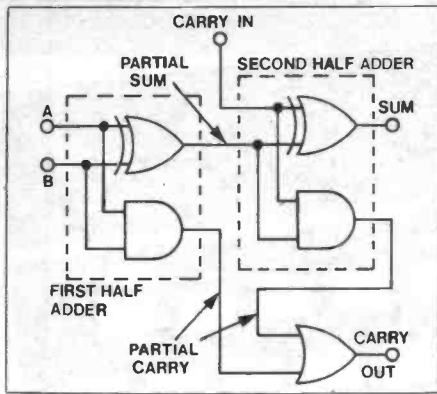


Figure 12. Full adder design

there may be 16 address lines, each of which is set to either 1 or 0 according to the specific address which the micro-processor wishes to access. The address is set in response to the requirements of the controlling program or software, and the logic must ensure that only one device is enabled if data bus contention is not to arise. With 16 address lines there are 65,536 possible unique addresses, corresponding to the locations in the memory map of the system. There are a number of logic devices which have been specially devised for address decoding, but we will consider a smaller problem using devices already described.

In some systems, the lower eight address lines are used by the micro-processor for a special purpose, that of addressing input or output devices which allow information to be fed between the processor and the 'outside world'. With only eight lines the number of possible addresses is reduced to 256, which helps to bring the problem down to more manageable proportions. What is needed, then, is a logical 'black box' into which may be sent the eight address lines along with

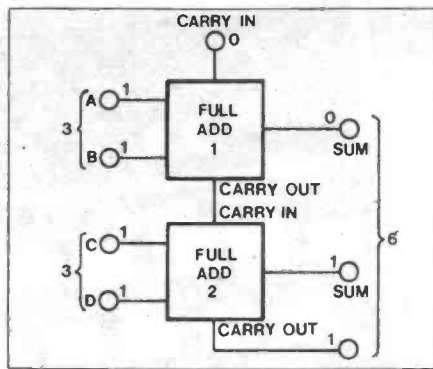


Figure 13. Full-Adders cascaded.

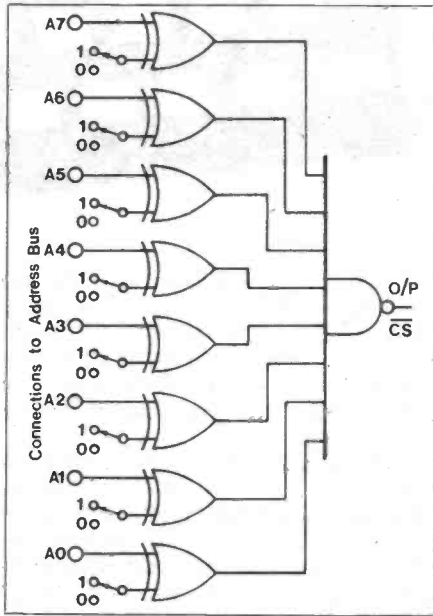


Figure 14.

signals to set a certain address, and from which emerges one line carrying the logic signal to select the particular device being addressed.

One solution to this problem is given in Figure 14 and again this may be bread-boarded to see how it works. One input of the EX-NOR gates is connected to the address bus, and the other used to select the address of the device. The output of each EX-NOR gate is then NANDed, so that the final output goes low when the appropriate address appears on the address bus. This low signal could be connected to the 'chip select', (CS) pin of the chosen device or combined with other control bus signals for further decoding. Suppose the address of the input/output device corresponds to the following bit pattern:-

Most Significant Bit Least Significant Bit (MSB) 1 1 0 1 0 0 1 1 (LSB)

If this pattern is set on the inputs to the EX-NOR gates then all the outputs from them will go high when the two bit patterns coincide. This in turn will set the inputs to the 8-input NAND gate all high, which is the only condition for the output to go low.

The required address may be fixed in a practical application by 'hard-wiring' the selecting inputs to the desired pattern; alternatively, the inputs may be connected via DIP switches, so that the address may be changed by altering the position of the switches.

A more convenient way of describing a bit pattern, such as the one in the above example, is to use the hexadecimal system. We shall be looking at this in more detail next time for any readers who are not familiar with the system. It will also be useful when dealing with the other main group of TTL devices, viz. those concerned with Sequential logic, which we shall also start to have a look at in the next article in the series.

# SUBSCRIBE NOW!

For just £2.80 a year we'll deliver every issue of the Maplin Magazine to your door.

We've got dozens of exciting projects and features coming in the next four issues. Plus lots of amazing special offers and a complete update to our catalogue each quarter.

**ALL THIS FOR JUST £2.80 A YEAR!**  
 (Overseas: surface mail £3.24, airmail £6.84)  
**Don't delay - send your cheque or postal order now!!**  
 P.S. Don't forget to renew your subscription, either!  
**ISSUE NINE ON SALE 11th NOVEMBER 1983**

Send this coupon with your cheque/PO to:  
**Maplin Magazine Subscriptions Dept.,**  
**Maplin Electronic Supplies Ltd.,**  
**P.O. Box 3, Rayleigh, Essex SS6 8LR**  
 I enclose £2.80 (plus post overseas) for 1 year's subscription to the Maplin Magazine.

Please start from Issue No. ....

Customer No. (if known) .....

Name .....

Address .....

.....Post Code .....

## NEW 1984 MAPLIN CATALOGUE

Now with prices on the page!

The new Maplin Catalogue for 1984 is 20% bigger — a massive 480 pages packed with data, circuits and pictures. Take a look at the completely revised Semiconductor section, the new Heathkit section with lots of brand new and original kits, the Computer section with lots more software for Atari, BBC, Commodore 64, Dragon, Sord, Spectrum and VIC20, and the hundreds of fascinating new products spread through the catalogue.



As always, the Maplin Catalogue is tremendous value for money and now has prices on the page!

Pick up a copy at any branch of W.H. Smith or in one of our shops for just £1.35 or send £1.65 incl. postage to our Rayleigh address. On sale from 1st November 1983. Better still — pick up a copy at the Electronic Hobbies Fair for just £1 — see back cover for details.

### Overseas Prices

Europe surface mail	£2.20
Europe air mail	£3.40
Outside Europe surface mail	£2.20
Outside Europe air mail	
(depending on distance)	£4.75/£6.25/£7.25

For surface mail anywhere in the world you may send 11 International Reply Coupons.

# DID YOU MISS THESE ISSUES?

Copies of issue 5 are still available for just 60p, and include the following projects:

**Modem.** With this low-cost, high quality modem, transmission speeds of 300 baud are obtainable over ordinary telephone lines. Send data to your friends anywhere in Europe, or talk to our computer.

**Inverter.** Ideal for camping or caravanning, this inverter uses MOFSET transistors for the ultimate in reliability. During emergency power cuts, use the inverter to keep your central heating going.

**ZX81 Sound Generator.** Here's a really noisy project for micro-computer enthusiasts. It plugs straight in to our ZX81 extension board and is really easy to make. Your ZX81 will have full BASIC control over three tone generators, with single address access.

**Central Heating Controller.** Four our more experienced constructors, this project will give your central heating system optimum performance and could save you a lot of money this winter.

**Panic Button.** A useful add-on for our Home Security System that will give many of our older citizens peace of mind. Issue five also included features on the Compact Digital Disc, Interfacing Microprocessors, and choosing the right wires for projects, and the last part of the Starting Point series, along with Basically Basic, Say it with Satellites, and Working with Op-Amps.

**All this for just 60p. Order As XA05F (Maplin Magazine Volume 2 Issue 5). Price 60p NV**



Copies of issue 6 are still available for just 70p, and include the following projects:

**Bridging Module.** This will turn two of our 75W amps into one 400W amp, and also gives you loudspeaker protection.

**Four Simple Circuits.** These easy-to-build circuits are a portable stereo amplifier, a sinewave generator, a headphone enhancer, and a stylus organ.

**Moisture Meter.** This low cost project allows you to check walls and floors for damp. It could save you thousands in costly house repairs.

**Scratch Filter.** Something to make all those scratched old records playable again.

**VIC 20 and ZX81 Talkbacks.** Allow your microcomputer the freedom of speech, and make games much more realistic. This could be just what your micro has always wanted.

**ZX81 TV Sound and Normal/Inverse Video.** Your ZX81 can now give you sound directly on to your TV set, and gives an optional video reversing switch, too!

Issue six also included features on the Sord M5 computer, Allophone Speech Synthesis, getting the best out of your oscilloscope, and the first part of a new beginners' series, First Base. Working With Op-Amps, Say it With Satellites, and the final part of the Basically Basic series were also in this issue.

**All this for just 70p. Order As XA06G (Maplin Magazine Volume 2 No. 6). Price 70p NV**



Copies of issue 7 are still available for just 70p, and include the following projects:

**CMOS Crystal Calibrator.** A radio amateur project to allow calibration of receivers and checking of the position of the edges of amateur band allocations.


**DXers Audio Processor.** Will improve the performance of many communications receivers without the need for modifications. **Enlarger Timer/Controller.** An accurate timer with a display that enables it to be used in colour printing, it will also control the switching on and off of the enlarger.

**Sweep Oscillator.** A useful, easy-to-build, piece of equipment to complement your fault-finding test gear.

**VIC20/RS232 and ZX81 Interfaces** will allow you to connect to modems, printers, VDUs, or any other RS232 compatible device. It will even let you use Maptel and Cashtel!

Issue 7 also included features on Heathkit, programming the Commodore 64, and the start of a new series on machine code programming with the 6502. First Base, Working with Op-Amps, Say it with Satellites, and all our usual news and reviews were also in this issue.

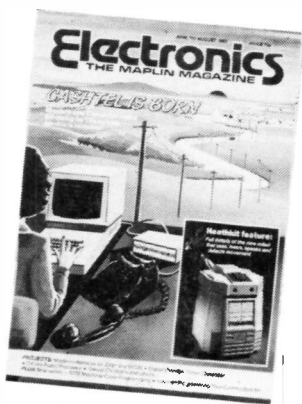**All this for just 70p. Order As XA07H (Maplin Magazine Volume 2 Issue 7). Price 70p NV**



## YOUR FULL COLOUR GUIDE TO HOME COMPUTER HARDWARE & SOFTWARE



This superb new edition of the Mapsoft catalogue is now available from all good computer retailers price 85p.

Full details are given in the catalogue of all the best and newest software for the Atari, Commodore 64, Dragon 32, Sinclair Spectrum and VIC20 and includes descriptions and colour pictures of lots of hardware as well.

Don't delay — get a copy now. It's fun to read and is an invaluable guide to what's available.

In case of difficulty send £1 to the address below and we will include the address of your nearest retailer with your copy of the catalogue. All products shown in the catalogue are available from your local dealer.

**FULL DESCRIPTIONS OF OVER 600 DIFFERENT TITLES OF SOFTWARE**

# Worth more than just a look in '83

1982 saw the first Electronic Hobbies Fair and immediately established itself as the foremost consumer electronics exhibition – the biggest attendance and the largest number of exhibitors.

The 1983 Fair will be bigger and even more exciting – offering visitors everything from resistors, ic's to home computers, transmitting and receiving units, and peripheral equipment, video games, musical instruments, radio control models. . . . In fact, whatever your particular electronic hobby you'll find this show will have something to excite you.

There will be plenty of other attractions too including radio and TV transmission, robotics,

radio controlled models and demonstrations by local and national organisations. Again British Rail will be offering cheap-rate rail fares from all major stations in the country direct to the Alexandra Palace – a special bus will be waiting to ferry you direct to the show. Your ticket also includes admission to the Exhibition.

Alternatively, for those wishing to travel independently ticket prices at the door are £2.00 for Adults, £1.00 for children. Party rates are available on request (minimum 20 people).

For more information contact the Exhibition Manager, Electronic Hobbies Fair, Reed Exhibitions, Surrey House, 1 Throwley Way, Sutton, Surrey SM1 4QQ.  
Tel: 01-643 8040.



## ELECTRONIC HOBBIES FAIR

Alexandra Palace, London – October 27-30, 1983

### Opening Times

Thursday 27 Oct – 10.00-18.00  
Friday 28 Oct – 10.00-18.00  
Saturday 29 Oct – 10.00-18.00  
Sunday 30 Oct – 10.00-17.00

Sponsored by Practical Electronics, Everyday Electronics and Practical Wireless