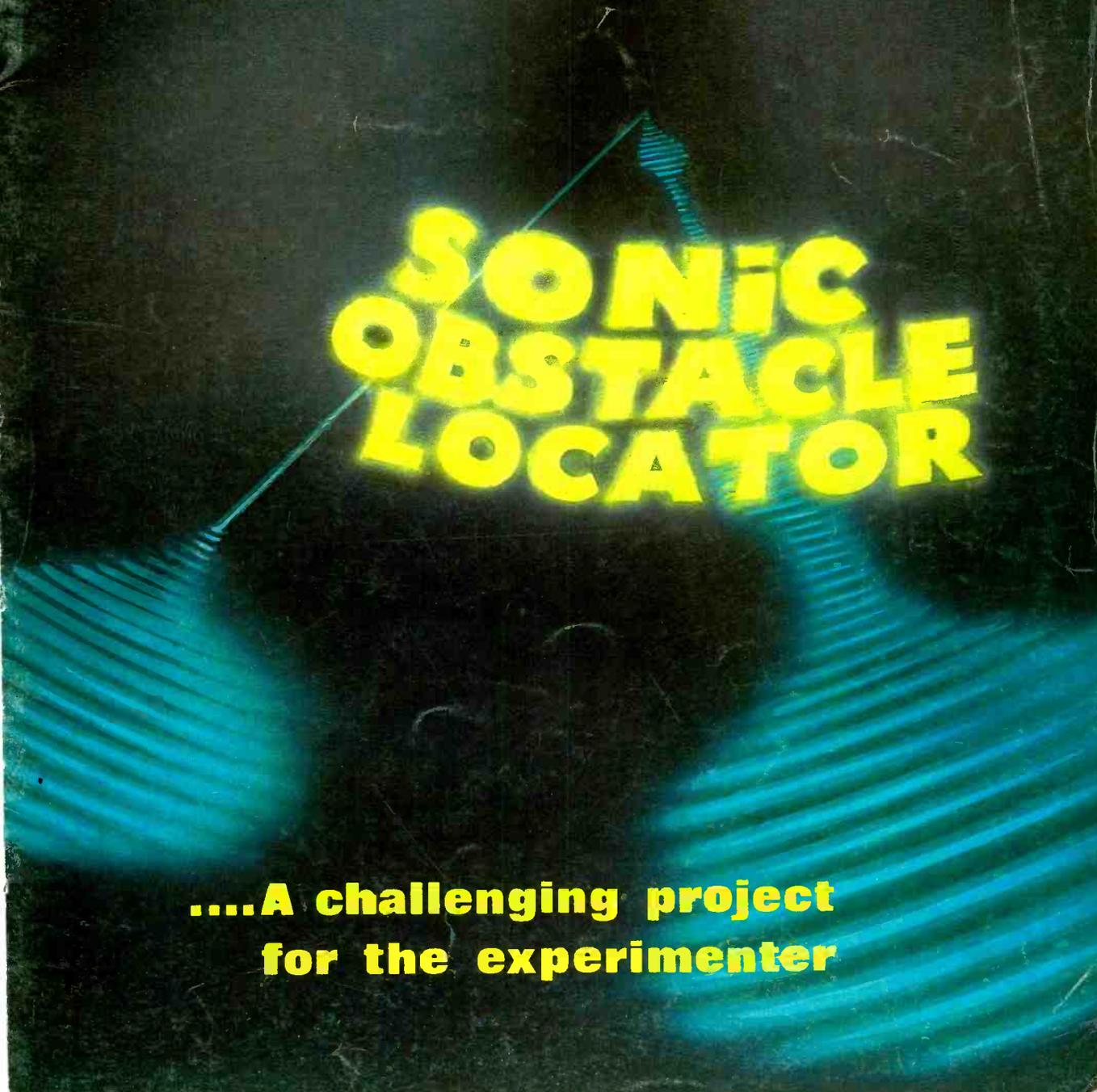


PRACTICAL

ELECTRONICS

JANUARY 1971

3/6 (17½ NEW PENCE)



SONIC OBSTACLE LOCATOR

....A challenging project
for the experimenter

ADCOLA Soldering Instruments add to your efficiency

ADCOLA 64 for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit*.
Standard temp. 360°C at 23 watts.
Special temps. from 250°C—410°C.

*Additional Stock Bits (illustrated) available

COPPER

B 38 $\frac{1}{8}$ " — 3.2 mm CHISEL FACE

B 14 $\frac{3}{32}$ " — 2.4 mm CHISEL FACE

B 24 $\frac{1}{16}$ " — 4.75 mm SCREWDRIIVER FACE

B 12 $\frac{3}{16}$ " — 4.75 mm EYELET BIT

B 58 $\frac{1}{4}$ " — 6.34 mm CHISEL FACE


LONG LIFE

B 42 LL $\frac{1}{8}$ " — 4.75 mm CHISEL FACE

B 38 LL $\frac{1}{8}$ " — 3.2 mm CHISEL FACE

B 14 LL $\frac{3}{32}$ " — 2.4 mm CHISEL FACE

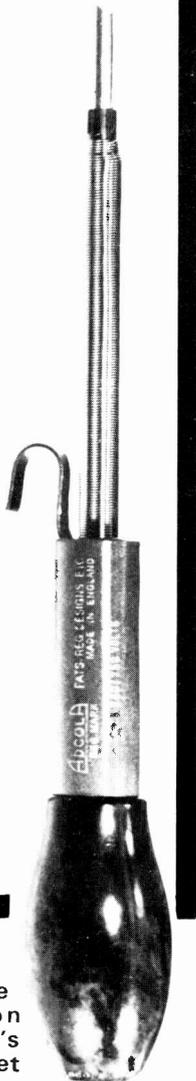B 44 LL $\frac{1}{16}$ " — 4.75 mm SCREWDRIIVER FACE



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.

* Write for price list and catalogue



ADCOLA PRODUCTS LTD.,
(Dept. L), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.
Telephone: 01-622 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851

EX RENTAL TV's

17" SLIMLINE
405 ONLY
£11.19.0

2 YEARS' GUARANTEE
FREE ILLUSTRATED
LIST OF TELEVISIONS
17"—19"—21"—23"

19" SLIMLINE
405/625
BBC 2
£29.19.0



WIDE RANGE OF MODELS
DEMONSTRATIONS DAILY



CARR. INS.
30/-

STEREO RECORD
PLAYER CABINET &
MATCHING EXTERNAL
SPEAKER CABINET £5.19.6



Cloth covered. Two tone Blue Black.
Size 14½" 24" 8½". P. & P. 10.6.

TV TUBES REBUILT
GUARANTEED 2 YEARS



14—79.6, 17 & 19"—119.-, 21 & 23"—129.-.
Exchanged Bowls. Carr. 10.6.

SPEAKERS GALORE. BRAND NEW 10.0. P. & P. 1.-. 2½" 8Ω.
4" 10Ω, 3" 5" 8Ω, 7" 4" and 8" 3" 3Ω.

TRANSISTOR CASES. 5/- each. Cloth covered & plastic. P. & P. 3.-.


PRESS BUTTON SWITCHING UNITS. 4 Banks 3'6. 6 Banks 5'6.
P. & P. 1.-.

TRANSISTORS 2 6 EACH. OC44, OC45, OC71, OC81, OC81D, AF114,
AF117, AC128.

DUKE & CO. (LONDON) LTD.
621/3 Romford Road, Manor Park, E.12
Phone 01-478 6001-2-3 Stamp for Free List

PHOTOELECTRIC KIT

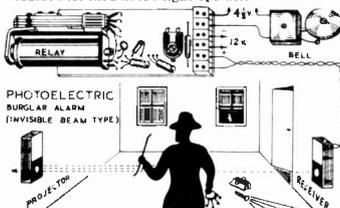CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, Condensers, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



PHOTOELECTRIC KIT
39/6

Postage and Pack. 2/6 (UK)
Commonwealth:
SURFACE MAIL 3/6
AIR MAIL £1.0.0
Australia, New Zealand
S. Africa, Canada and U.S.A.
Also Essential Data Circuits
and Plans for Building
10 Advanced Designs

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 Lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, performance data, etc. Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 8/-.

LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price 29/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/6. Air Mail 10/-.

JUNIOR PHOTOELECTRIC KIT

Versatile Invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc., for the Experimenter.

CONTENTS: Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs". Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth 2/-; Air Mail 4/-.

JUNIOR OPTICAL KIT

CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photocell receiver for use with Junior Photoelectric Kit.

Price 10/6. Post and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 4/-.

YORK ELECTRICS

335 BATTERSEA PARK ROAD, LONDON, S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.

knight-kits

FANTASTIC LOW PRICES!

Due to huge purchase these superb U.S.A. construction kits can be offered at 25%—50% off recommended list prices. Absolutely complete with most detailed construction and operating books. Available from all branches or by mail order for 7/6 CARRIAGE AND PACKING on each kit. Two kits or more carr. free.

KG-865 50 Watt Stereo Amplifier Kit

DELUXE FEATURES

All Silicon Transistors for Stability, Cleaner Sound • Extremely Wide Power Bandwidth and Frequency Response • 50W I.H.F. Power Output • Specially Selected Low-Noise Preamp Transistors • Two Printed Circuit Boards for Fast Easy Assembly • Convenient Front-Panel Stereo Headphone Jack • Teak-finished Extruded Aluminium Front Panel • Two a.c. Convenience Outlets.



Output: 50W I.H.F. (25W per channel); 31W continuous sine wave • Response: $\pm 1dB$, 1s to 30,000Hz • Output Impedance: 4 through 16 ohms, plus stereo headphones • I.M. Distortion: under 1% at 50Hz and 1,000Hz mixed 1:1 at rated power • Input Sensitivity: Magnetic Phono, 5mV; Tuner and Auxiliary, 500mV • Power Requirement: 230-250V, 50Hz a.c. Recommended List Price £34.19.6; 24 GNS. Assembled £29 GNS. Teak Case £5 Extra

ALL SILICON TRANSISTORS

The NEW KG-980 Stereo FM Receiver Kit


Designed to Satisfy the Most Critical Listener



R.F. and I.F. Panels Assembled and Aligned • Front Panel Stereo Headphone Jack and Speaker Muting Switch • Full Controls including Tape Monitor • 50W I.H.F. Output • Usable I.H.F. Sensitivity: 3 μ V • Frequency Response: $\pm 1dB$, 30 to 15,000Hz • Harmonic Distortion: less than 1% • A.M. Suppression: more than 30dB • Channel Separation: 30dB • Complementary Transformerless • Power Output: 50W I.H.F. (25W per channel); 31W continuous sine wave • Frequency Response: $\pm 1dB$, 1s to 30,000Hz • Power Bandwidth: 20-20,000Hz at 1% harmonic distortion • Two R.F. Stages • Stereo indicator light. Recommended List Price £62.19.6; 39 GNS. Assembled 49 GNS. Teak Case 5 GNS. Extra

KG-625 Deluxe 6in Vacuum Tube Voltmeter Kit

Huge 6in Meter Scale • Ranges: d.c. 0-0.5-1.5-5-15-50-150-500-1,500V full scale • Accuracy: $\pm 3\%$ of full scale reading • Input Resistance: 11M Ω to 1,500V • Ranges: a.c. 0-1.5-5-15-50-150-500-1,500V full scale, 0-4-2-1-0.5-10-120-1,100-1,200V full scale • Accuracy: $\pm 5\%$ • Frequency Response: $\pm 1dB$, 30Hz to 3MHz; $\pm 3dB$, 30Hz to 5MHz • Ohmmeter Ranges: 0-1,000-10,000 ohms; 0-1-10-100-1,000M Ω • Battery: 1.5V E2. Recommended List Price £24.19.6; 12 GNS. KG 625 as KG 625 (Same Ranges) but 4 1/2in Scale; 9; GNS.

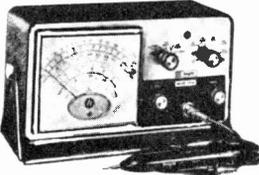

STAR ROAMER 5-Band Shortwave Receiver Kit

Bandspread: electrical, calibrated 0-100 • Sensitivity: 10 μ V for 10dB signal-to-noise ratio • I.F. Bandwidth: 5kHz at 6dB down • Beat Frequency: variable, 0-5kHz • Speaker: tin permanent magnet type • Power Supply: 100V, transformer operated • Headphone Output: low impedance • Valve Complements: 1-6BE6, 1-6J16, 1-12AX7, 1-6AK6 or 1-6AR5 • Power Requirements: 230-250V, 50Hz a.c.; 15W • Covers 200 to 400kHz and 550kHz to 30MHz in 5 Band-switched Ranges • Superheterodyne Circuit includes controlled regenerative I.F. stage • A.V.C. effectively peaks incoming signals for best reception • Illuminated "S" Meter; Large, Easy-to-Read 7 1/2in Slide Rule Dial. Recommended List Price £21.19.0; 14 GNS. Assembled Price 19 GNS.



KG-375A Deluxe Solid-State Auto Analyzer Kit

Tune-up and trouble-shoot any car, perform actual road tests

It's several testers in one... do all this


Set Engine Idle and Automatic Transmission Shift Points • Detect Condition of Point Surfaces • Detect Distributor Wear • Check Voltage and Current Regulators • Check Generators for both Current and Voltage Output • Find For or Open Earth Circuits • Detect Variation in Drive Angle. Recommended List Price £23.17.6; 16 GNS. Assembled Price £1 GNS.



100-in-1 Electronic Science Lab

LOOK AT THE PROJECTS YOU CAN BUILD

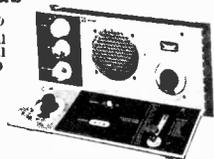• Electronic Scale • Electronic Timer • Signal Generator • Hybrid Light Meter • Signal Injector • Morse Code Buzzer • Electronic Cat • Ohmmeter • Beat Horn • CW Monitor • Hybrid Voice Relay • Air-powered Radio • Polarity Checker • Valve Checker. Includes: • Dual Headset • Photocell • Speaker • Meter • Aerial • Transistors. Recommended List Price £16.8.0; 9; GNS.



KG-371 Deluxe Solid-State Timing Light

Performance surpasses assembled units coating nichrome


Helps Set Ignition Timing • Checks Synchronisation of Double Breaker Arms • Checks for Sticking Automatic Spark-Advance Mechanism • Checks Distributor Cam Wear • Built-in d.c. Power Supply • Reliable Solid-State Circuit • Your car gives More miles per gallon; Improved performance; Greater reliability. Recommended List Price £12.10.0; 9 GNS. Available Assembled Only.



KG-640 20,000 ohms/Volt VOM Kit

BIG PROFESSIONAL SIZE 62 RANGE MULTIMETER

• A.C. Volts (12 Ranges): 0-2-4-8-16-40-50-200-400-500-1,000-2,000-4,000V • D.C. Volts (12 Ranges): 0-0.5-1-5-15-16-40-80-200-400-500-1,000V • Output Volts (8 Ranges): 0-2-4-8-16-40-80-200-400V • Resistance (8 Ranges): 0-1,000-10,000 ohms-10 meg. Centre scales at 12, 1,200 and 120K Ω • D.C. Current (10 Ranges): 0-50-160-400-800 μ A, 5-16-200-400mA, 5-16A • Decibels (12 Ranges): -12 to +7.5 • D.C. Sensitivity: 20,000 ohms per volt or 10,000 ohms per volt (function of scale multiplier switch) • Frequency Response: 20Hz to beyond 20kHz • Accuracy: d.c. 3%, a.c. 5% • Test Leads: one red, one black, each 45in long • Multiplier Resistors: All 1% carbon film. Recommended List Price £16.19.6; 9; GNS. Assembled Price 12 GNS.

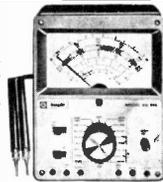

JASON TAPE

We offer you fully tensilised polyester/mylar and P.V.C. tapes of identical quality hi-fi, wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more pence than acetate, sub-standard, jointed or cheap imports. TRY ONE AND PROVE IT YOURSELF.

	Standard	Long	Double	Triple
3in. 150ft.	2/3	3in. 225ft.	2/9	3in. 300ft.
4in. 300ft.	4/8	4in. 450ft.	5/8	4in. 600ft.
5in. 600ft.	7/8	5in. 900ft.	10/8	5in. 1,200ft.
6in. 900ft.	10/8	6in. 1,200ft.	13/-	6in. 1,800ft.
7in. 1,200ft.	12/8	7in. 1,800ft.	18/8	7in. 2,400ft.
				8in. 3,000ft.
				9in. 3,600ft.
				10in. 4,200ft.
				11in. 4,800ft.
				12in. 5,400ft.
				13in. 6,000ft.
				14in. 6,600ft.
				15in. 7,200ft.
				16in. 7,800ft.
				17in. 8,400ft.
				18in. 9,000ft.
				19in. 9,600ft.
				20in. 10,200ft.
				21in. 10,800ft.
				22in. 11,400ft.
				23in. 12,000ft.
				24in. 12,600ft.
				25in. 13,200ft.
				26in. 13,800ft.
				27in. 14,400ft.
				28in. 15,000ft.
				29in. 15,600ft.
				30in. 16,200ft.
				31in. 16,800ft.
				32in. 17,400ft.
				33in. 18,000ft.
				34in. 18,600ft.
				35in. 19,200ft.
				36in. 19,800ft.
				37in. 20,400ft.
				38in. 21,000ft.
				39in. 21,600ft.
				40in. 22,200ft.
				41in. 22,800ft.
				42in. 23,400ft.
				43in. 24,000ft.
				44in. 24,600ft.
				45in. 25,200ft.
				46in. 25,800ft.
				47in. 26,400ft.
				48in. 27,000ft.
				49in. 27,600ft.
				50in. 28,200ft.
				51in. 28,800ft.
				52in. 29,400ft.
				53in. 30,000ft.
				54in. 30,600ft.
				55in. 31,200ft.
				56in. 31,800ft.
				57in. 32,400ft.
				58in. 33,000ft.
				59in. 33,600ft.
				60in. 34,200ft.
				61in. 34,800ft.
				62in. 35,400ft.
				63in. 36,000ft.
				64in. 36,600ft.
				65in. 37,200ft.
				66in. 37,800ft.
				67in. 38,400ft.
				68in. 39,000ft.
				69in. 39,600ft.
				70in. 40,200ft.
				71in. 40,800ft.
				72in. 41,400ft.
				73in. 42,000ft.
				74in. 42,600ft.
				75in. 43,200ft.
				76in. 43,800ft.
				77in. 44,400ft.
				78in. 45,000ft.
				79in. 45,600ft.
				80in. 46,200ft.
				81in. 46,800ft.
				82in. 47,400ft.
				83in. 48,000ft.
				84in. 48,600ft.
				85in. 49,200ft.
				86in. 49,800ft.
				87in. 50,400ft.
				88in. 51,000ft.
				89in. 51,600ft.
				90in. 52,200ft.
				91in. 52,800ft.
				92in. 53,400ft.
				93in. 54,000ft.
				94in. 54,600ft.
				95in. 55,200ft.
				96in. 55,800ft.
				97in. 56,400ft.
				98in. 57,000ft.
				99in. 57,600ft.
				100in. 58,200ft.

Postage 1/- reel. Post free less 5% on three reels. Quality and Trade enquiries invited. NOTE. Large tape stocks at all branches.

Stockists of Leak, Quad, Chapman, Goodman, Armstrong, Tripletone, Linear, Rodgers, Truvox, Ferrograph, Wharfedale, etc., etc.

TECHNICAL TRADING

All Mail Orders:—

- ★ ARUNDEL 15-17 Queen Street Tel. 3280
- ★ BRIGHTON 6 Queen's Road Tel. 23975
- ★ SOUTHSEA 2 Clarendon Road
- ★ PORTSMOUTH 350-352 Fratton Road, Tel. 22034
- ★ SOUTHAMPTON 72 East Street Tel. 23531

PERSONAL CALLERS Welcomed at all Branches where there are large Hi-Fi and Component stocks at the keenest prices including:

GARRARD 1025 Autochangers complete with GARRARD STEREO CARTRIDGE 7 1/2 GNS.

MAGNETIC CARTRIDGES Goldring 800M 7 1/2 GNS.

Shriro AT33 £7.10.0 (Both Listed over £10)

Laskys

TMK METER KITS

These two meter kits by TMK offer the unique opportunity of building a really first-class precision multimeter at a worthwhile saving in cost. The cabinets are supplied with the meter scale and movement mounted in position. The highest quality components and 1% tolerance resistors are used throughout. Supplied complete with full constructional, circuit and operating instructions.

MODEL 200 20,000 O.P.V. Multimeter. Features 24 measurement ranges with mirror scale. Large 3" x 2in meter. Full scale accuracy: DCV and current: $\pm 2\%$, ACV: $\pm 3\%$, resistance $\pm 3\%$. Special 0.6V DC range for transistor circuit measurements.

SPECIFICATION
 ● DCV: 0-0.6-6-30-120-600-1,200V at 20K/OPV. ● ACV: 0-0.6-30-120-600-1,200V at 10K/OPV. ● DC Current: 0-0.6-6-600mA. ● Resistance: 0-10K 100K-1M-10M/ohms (58-580-5.8K-58K at mid-scale). ● Capacitance: 0.002-0.2 μ F (AC 6V range). ● Decibels -20 to +63dB. ● Output: 0.05 μ F blocking capacitor. Uses two 1.5V (U7 type) batteries. Black bakelite cabinet—Size 5 $\frac{1}{2}$ x 3 $\frac{1}{4}$ x 1 $\frac{1}{4}$ in. Complete with test leads.



KIT PRICE ONLY 92/- Post 3/6

MODEL 5025 50,000 O.P.V. FEATURING 57 MEASUREMENT RANGES

Uses an entirely new range selection mechanism which permits the use of a really large meter in a more compact cabinet. The range selected is indicated on the meter face. High speed rotary range selection knob; polarity reversal switch, shielded meter movement with overload protection circuit; Special μ A and mA measurement ranges.

SPECIFICATION DCV: 0-0.25-2.5-10-50-250-1,000V at 25K/OPV. 0-0.125-1.25-5-25-125-500V at 50K/OPV. ACV: 0-3-10-50-250-1,000V at 2.5K/OPV. 0-1.5-5-25-125-500V at 5K/OPV. DC μ A: 0-25 μ A at 125mA; 0-50 μ A at 250mA. DCmA: 0-2.5-25-250mA at 125mV; 0-5-50-500mA at 250mV. DC Amps: 0-5A at 125mV; 0-10A at 250mV. Resistance: 0-10M/ohms. Output: Capacitor (0.1 μ F, 400V) in series with ACV ranges. Decibels: -20 to +81.5dB. Operates on two 1.5V cells. Black bakelite cabinet, size 5 $\frac{1}{2}$ x 6 $\frac{1}{2}$ x 2 $\frac{1}{4}$ in. Complete with test leads.



KIT £10.10.0 Post 5/

MODEL 5025 ALSO AVAILABLE READY BUILT AND TESTED £12.10.0 POST 5/-

TMK 100,000 OPV

"LAB MODEL"

A highly accurate yet rugged Multitester using a 10 μ A meter hand calibrated to a D.C. accuracy of $\pm 3\%$ of full scale. Special features—ultra large meter scale 6 $\frac{1}{2}$ x 3 $\frac{1}{4}$ in. Incorporating an entirely new type of range selection panel which gives instant range identification without taking your eyes from the meter. An audible buzzer is provided for easy short testing. SPEC: D.C./V ranges: 0.5, 2.5, 10, 50, 250, 500, 1,000V at 100K/O.P.V. A.C./V. ranges: 3, 10, 50, 250, 500, 1,000V at 5K/O.P.V. D.C. current: 0-10, 100 μ A, 0-10, 100mA, 0-2.5, 10A. Resistance: 0-1K, 10K, 100K-10M, 100M/ohms. Decibels: -10 to 45.4dB. Continuity test: Audible buzzer. Operates on x11.5V U2 and 1 x 1.5V B. 154 type batteries. Cabinet size 7 $\frac{1}{4}$ x 6 $\frac{1}{2}$ x 3 $\frac{1}{4}$ in. Weight 4lb.



LASKY'S PRICE £17.15.0 Post 5/-

SONICS AS-57

ELEGANT BUDGET PRICED BOOKSHELF SPEAKER SYSTEMS

The AS-57 is a real space saver. This fine miniature high-fidelity speaker system will provide good quality sound anywhere in your home at remarkably low cost. Designed for use where space is at a premium, the AS-57 system is ideal for the small apartment or isolated listening area. The special high efficiency 5 x 7in full range speaker has a frequency range of 70-18,000Hz with a peak handling capacity of 10 watts. Imp. 8 ohms. Finish: oiled walnut. Size 5 $\frac{1}{4}$ x 15 $\frac{1}{2}$ x 8 $\frac{1}{4}$ in.

LASKY'S PRICE £15 per PAIR POST 10/-

EXCLUSIVE

TM-5

5 K ohms/V POCKET MULTIMETER

Another new look pocket multi-meter from Lasky's providing top quality and value. The "slimline" impact resistant case—size 4 $\frac{1}{2}$ in x 2 $\frac{1}{2}$ in x 1 $\frac{1}{4}$ in, fitted with extra large 2 $\frac{1}{2}$ in square meter. Readability is superior on all low ranges; making this an excellent instrument for servicing transistorised equipment. Recessed click stop selection switch. Ohms zero adjustment. Buff finish with crystal clear meter cover.



- DC/V: 3-15-150-300-1,200 at 5K/OPV
- AC/V: 6-30-300-600 at 2.5K/OPV.
- DC Current 0-300 μ A, 0-300mA.
- Resistance: 0-10k Ω , 0-1M Ω .
- Decibels: -10dB to +16dB.
- Complete with test leads, battery and instructions.

LASKY'S PRICE 59/- Post 2/6

TM-1 MINI-TESTER

1 K ohms/volt

The first of Lasky's new-look top value meters, the TM-1 is a really tiny pocket multimeter providing "big" meter accuracy and performance. Precision movement calibrated to $\pm 3\%$ of full scale. Click stop range selection switch. Beautifully designed and made impact resistant black case—with white and metallic red/green figuring. Ohms zero adjustment.

Size Only 3 $\frac{1}{2}$ in. x 2 $\frac{1}{2}$ in. x 1 $\frac{1}{4}$ in

- DC/V: 0-10-50-250-1,000 at 1K/OPV.
- AC/V: 0-10-50-250-1,000 at 1K/OPV.
- DC CURRENT: 0-1mA, 100mA.
- Resistance: 0-150k Ω .
- Decibels: -10dB to +22dB.
- Complete with test leads, battery and instructions.




LASKY'S PRICE 39/- Post 2/6

AUDIO DEVELOPMENT

AD-309K

PRECISION PICK-UP ARM COMPLETE WITH AD-76K MAGNETIC CARTRIDGE

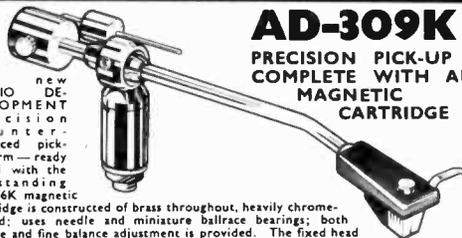The new AUDIO DEVELOPMENT precision counter-balanced pick-up arm—ready fitted with the outstanding AD-76K magnetic



cartridge is constructed of brass throughout, heavily chrome-plated; uses needle and miniature ballrace bearings; both coarse and fine balance adjustment is provided. The fixed head has standard tin, mounting centres and is finished in black enamel with chrome lifting spur. Completely wired, with all fixing nuts and washers. Arm rest also supplied. Tech. details: Overall length 285mm; needle to pivot length 223mm; offset angle 24°; overhang 10mm. Requires single 7/16in. dia. mounting hole.

LASKY'S PRICE £8.10.0 Post Free

AUDIO DEVELOPMENT AD-76K

Stereo Magnetic Cartridge. Frequency response: 20-20,000Hz. Output: 5mV. Stylus: Diamond LP. **90/-** Post Free
 Tracking force: 2 gms ± 0.5 gm.
 Replacement stylus type JS.P1 41/- post free.

AUDIO DEVELOPMENT AD-96K

Stereo Magnetic Cartridge. Frequency response: 20-20,000Hz. Output: 5mV. Stylus: Diamond LP. **£5.18.0** Post Free
 Tracking force: 2 gms.
 Replacement stylus type Y.960S.51/6, post free.

Audio Tronics 71

NOW AVAILABLE

The 1971 edition of Lasky's Audio-Tronics Catalogue is now available on request

44 tabloid pages packed with 1,000's of items from the largest stocks in Great Britain, everything for the Radio and Hi-Fi enthusiast, electronics hobbyist, serviceman and communications ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo systems and a fabulous new range of Package Deals), Tape recording and Audio accessories plus

LASKY'S AMAZING MONEY SAVING VOUCHERS, THIS YEAR WORTH OVER £32

This year Lasky's introduce an amazing new Credit card scheme giving holders £50 interest free credit per month.

All the goods shown in the 1971 Audio-Tronics Catalogue are available now from any of our branches or by Mail Order to any address in the U.K. or Overseas—bringing the benefits of shopping at Lasky's to you in the comfort of your home.

DON'T DELAY

send today your name and address plus 15p for post and inclusion in our regular mailing list only.

THE AMAZING

Astrad ORION

THE WORLD'S SMALLEST 6 TRANSISTOR

TWO WAVEBAND RADIO
THOUSANDS SOLD



Made to the highest space-age standards—this remarkable micro-size set measures only 1 1/2" x 1 1/2" x 3/4" yet it contains 6 transistors and other components combined in a photo etched circuit, only 2" x 3/4" tuning capacitor, ferrite rod aerial, battery, wave band selection switch, etc. Output to a high impedance crystal earpiece, giving ample volume (automatically adjusted) and clear tone. Brief tech. spec.: Waveband coverage—Medium wave 525 to 160kHz, Long wave 150kHz to 480kHz. Sensitivity: 35mV max. Selectivity—10dB (at 30kHz de-tuning). Power source: 1 x 1.4V Mercury battery.

Never miss your favourite music, sport, news—the Orion is an ideal gift for all, providing a constant source of enjoyment without disturbing others.

The Orion is supplied complete with battery and attractive black and ivory plastic presentation/carrying case (matching the Orion).

LASKY'S PRICE ONLY **29/6** COMPLETE

BARGAIN PACKAGE DEAL

Comprising—ORION RADIO, rechargeable battery and battery charger. **£2** Post 4/-

BATTERY CHARGER AVAILABLE SEPARATELY 17/- post 2/6

McDONALD

McDONALD MP.60

PROFESSIONAL SERIES
FOUR SPEED SINGLE
PLAY UNIT

High-precision low-mass fully counter-balanced pick-up arm, heavy balanced turntable, simply operated controls, slide in cartridge carrier, four pole motor.



LASKY'S PRICE **£11.50**

POST 35p.

complete with plinth and cover **£15.00** POST 40p.

610 AUTOMATIC TURNTABLE

Same specifications as the MP60 but with synchronous four pole motor and full automatic change facilities.

LASKY'S PRICE **£15.45** POST 35p.
WITH PLINTH AND COVER **£18.45** POST 40p.

510 AUTOMATIC TURNTABLE

Counter balanced pick-up arm, pressed steel turntable, bias compensator, viscous cueing and synchronous four pole motor.

LASKY'S PRICE **£13.45** POST 35p.
WITH PLINTH AND COVER **£16.95** POST 40p.

310 AUTOMATIC TURNTABLE

Low mass square section pick-up arm, cue and pause lever, visual stylus pressure indicator, slide in cartridge carrier, four pole motor.

LASKY'S PRICE **£9.95** POST 35p.
WITH PLINTH AND COVER **£13.45** POST 40p.

BSR McDONALD PACKAGES

PACKAGE No. 1

BSR McDONALD 510 4 Speed Autochanger	£16.03
AUDIO DEVELOPMENT AD76K Magnetic Cartridge	£ 4.50
BSR Afromosia Plinth with black mounting board	£ 4.44
BSR Smoked Perspex Dust Cover	£ 3.17
Recommended retail price	£28.14

LASKY'S PRICE **£24.95**

ADD £5.50 if MZ100/E is preferred
ADD £6.50 if Shure M44/5 is preferred

PACKAGE No. 2

BSR McDONALD 310 4 Speed Autochanger	£12.95
TTC2103 Stereo Ceramic Cartridge	£ 1.95
BSR Afromosia Plinth with black mounting board	£ 4.44
BSR Smoked Perspex Dust Cover	£ 3.17
Recommended retail price	£22.51

LASKY'S PRICE **£18.95**

ADD 50p if BSR Ceramic Cartridge is preferred

JUST ARRIVED

New Lasky's
C60, C90, C120. Exclusively
made for us in U.S.A.
Great Savings!

	EACH	FIVE FOR	TEN FOR
C60—	7/6	33/-	62/-
C90—	12/6	56/-	100/-
C120—	17/6	75/-	139/-

U.S.A. Cassette head cleaner 10/6. Post 1/-.
Post 1/- each, five for 2/-, ten for 3/-.



Lasky's Radio Limited

207 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 3271

33 TOTTENHAM CT. RD, LONDON, W1P 9RB. Tel: 01-636 2605

Open all day, 9 a.m. - 6 p.m. Monday to Saturday

109 FLEET STREET, LONDON, E.C.4. Tel: 01-353 5812

152/3 FLEET STREET, LONDON, E.C.4. Tel: 01-353 2833

Open all day Thursday, early closing 1 p.m. Saturday

HIGH FIDELITY AUDIO CENTRES

42-45 TOTTENHAM CT. RD, LONDON, W1P 9RD. Tel: 01-580 2573

Open all day, 9 a.m. - 6 p.m. Monday to Saturday

118 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 9789

Open all day Saturday early closing 1 p.m. Thursday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E1 2BN Tel: 01-790 4821

BRAND NEW FULLY GUARANTEED TRANSISTORS

SEND FOR

NEW LIST • NEW PRICES

1N4001	1/6	AAZ12	4/-	BPY10	19/8
1N4002	1/6	AAZ13	2/6	BSX20	3/6
1N4003	2/-	AAZ17	2/-	BSX21	4/-
1N4004	2/6	AC126	5/-	BSX76	3/4
1N4005	2/6	AC127	5/-	BSY27	4/-
1N4006	3/-	AC127Z	10/-	BBY28	5/-
1N4007	4/-	AC128	5/-	BSY29	5/-
1N4009	1/6	AC129	4/-	BSY60	5/-
1N4148	1/9	AC154	3/-	BSY63	5/-
2G210	12/6	AC169	3/-	BSY66	5/-
2G240	49/6	AC176	5/-	BSY67	5/-
2G301	4/-	AC187	6/-	BSY96A	4/8
2G302	4/6	AC188	6/-	BSY96	3/8
2G303	5/-	AC17	6/-	BY100	3/8
2G306	6/-	AC178	4/-	BY103	4/8
2G308	6/-	AC179	5/-	BY126	3/-
2G309	6/-	AC190	4/-	BY127	4/-
2G371	4/6	AC191	4/6	BYZ10	8/-
2G374	5/6	AC192	3/6	BYZ11	7/-
2G381	5/-	AC198	3/6	BYZ12	6/-
2G382	6/-	AC194	4/6	BYZ13	4/-
2G383	5/-	AC196	5/-	BYZ15	20/6
2N404	4/6	AC199	11/-	BYZ16	12/6
2N696	3/6	AC140	3/-	GET102	6/-
2N697	3/6	AD140	10/-	GET103	4/6
2N698	8/6	AD149	10/-	MPP102	8/6
2N708	2/-	AD161	7/6	MPF103	7/6
2N708A	2/6	AD162	7/6	MPF104	7/6
2N707	9/6	AD102	10/-	MPP105	8/6
2N708	3/-	AF114	6/6	OA5	3/-
2N914	4/6	AF115	6/6	OA7	4/-
2N916	4/6	AF116	6/6	OA9	2/-
2N918	7/6	AF117	5/-	OA10	5/-
2N919	4/6	AF118	12/6	OA47	2/-
2N920	5/6	AF124	4/-	OA2	2/-
2N922	8/6	AF125	5/-	OA11	2/-
2N930	5/-	AF126	4/-	OA73	2/-
2N1131	6/-	AF127	4/-	OA74	2/-
2N1132	6/-	AF139	6/-	OA79	2/-
2N1303	4/6	AF178	9/6	OA81	2/-
2N1304	5/-	AF181	8/6	OA85	2/6
2N1305	5/-	AF188	4/-	OA86	4/-
2N1306	5/-	AF239	8/-	OA90	2/-
2N1307	5/-	AFY19	22/6	OA91	1/6
2N1308	6/-	AFZ11	12/6	OA95	1/6
2N1309	5/-	AFZ12	15/-	OA200	1/6
2N1613	4/6	ASY26	5/-	OA202	2/-
2N1247	15/-	ASY27	7/6	OA210	5/-
2N2160	13/6	ASY28	7/6	OA211	7/6
2N2287	25/-	ASY29	6/-	OA225	7/6
2N2646	10/6	ASY67	8/6	OA228	7/6
2N2904	6/-	ABZ21	8/6	OA229	9/6
2N2905	7/6	AUY10	19/6	OA231	9/6
2N2925	4/6	B3M	19/6	OA234	7/6
2N2926	2/6	BA110	5/-	OA238	8/6
2N3011	5/-	BAY31	2/6	OC16	8/6
2N3053	5/-	BC107	2/6	OC19	7/6
2N3054	10/-	BC108	2/6	OC20	19/6
2N3055	16/-	BC109	2/6	OC22	9/6
2N3702	2/6	BC113	6/-	OC23	10/-
2N3703	2/6	BC116	8/6	OC24	10/-
2N3704	3/6	BC118	7/6	OC25	7/6
2N3705	3/6	BC134	7/6	OC26	5/-
2N3707	3/6	BC135	6/-	OC28	12/6
2N3709	2/6	BC136	7/6	OC29	12/6
2N3710	2/6	BC137	8/6	OC35	10/-
2N3711	2/6	BC138	8/6	OC36	12/6
2N3730	10/-	BCY30	5/6	OC41	5/-
2N3731	12/6	BCY31	6/-	OC42	6/-
2N3794	2/6	BCY32	10/-	OC43	8/-
2N3819	7/6	RCY33	4/-	OC44	4/-
2N3820	17/6	BCY34	5/-	OC45	3/6
2N3823	17/6	BCY38	6/-	OC46	3/6
2N4058	3/6	BCY39	9/6	OC70	2/6
2N4061	3/6	BCY40	4/6	OC71	3/6
2N4286	3/6	BCY42	5/-	OC72	5/-
2N4288	3/6	BCY43	5/-	OC73	6/-
2N4289	3/6	BCY70	4/6	OC74	6/-
2N4290	3/6	BCZ11	7/6	OC75	5/-
2N4291	3/6	BC147	3/6	OC76	5/-
2N4292	3/6	BC148	2/6	OC77	8/6
40362	11/-	BF149	4/6	OC78	8/6
40362	12/-	BF152	6/-	OC81	5/-
25001	10/-	BF194	3/6	OC81D	4/-
25002	10/6	BF195	3/6	CC82	5/-
25003	9/6	BD124	12/6	OC83	5/-
25004	9/6	BFN3000	5/-	OC84	5/-
25006	14/-	BF115	5/-	OC122	10/-
25012	25/-	BF154	8/6	OC123	10/-
25013	20/-	BF158	6/-	OC139	5/-
25017	15/-	BF159	12/6	OC140	7/6
25034	12/6	BF163	8/6	OC141	15/6
25036	25/-	BF167	5/-	OC169	4/-
25320	9/6	BF173	6/-	OC170	5/-
25321	6/6	BF180	7/6	OC171	6/-
25322	7/6	BF181	7/6	OC200	9/6
25323	10/-	BFX30	6/-	OC201	9/6
25324	12/6	BFX88	5/-	OC202	12/6
25512	9/6	BFY20	12/6	OC203	7/6
25701	8/6	BFY50	4/6	OC204	8/6
25702	11/-	BFY51	4/6	OC206	12/6
25721	8/6	BFY52	4/6	OC208	15/6
25732	8/6	BFY53	3/6	OC207	15/-
25733	9/6	BFY64	8/6	OCPT1	19/6
AA178	8/6	BLY10	20/-	ORP12	11/-
AA178	5/6	BLY11	22/6	ORP60	8/-

INTEGRATED CIRCUITS

Type	1	12+	25+	100+	500+
UL914	9/9	9/-	8/-	7/3	6/6
UL923	12/6	11/9	11/-	10/-	9/3
SL403A	42/6	41/-	40/-	37/6	35/-
MC1303	52/6	48/-	45/-	40/-	35/-
MC1304	55/-	50/-	47/6	42/6	37/6
PA246	52/6	48/-	45/-	40/-	35/-

2N3055	15/-	2N3819	7/-
Mullard 115 watt Silicon Power	25 + 6/-	Texas F.E.T.	25 + 6/-
100 + 13/-		100 + 5/3	
100 + 11/-		500 + 4/9	

2N2926	2/6	2N2646	10/6
NPN Planar All Colours	25 + 1/8	Motorola Unijunction	25 + 8/9
100 + 1/6		100 + 7/6	
		500 + 6/9	

AF139	6/-	AF186	8/-
Siemens V.H.F.	25 + 5/3	Mullard V.H.F.	25 + 7/-
100 + 4/6		100 + 6/-	
500 + 3/9		500 + 5/-	

OB170	5/-	BY126	3/-
25 + 4/3		Mullard 800v 1 amp Plastic	25 + 2/6
100 + 3/6		100 + 2/3	

OC171	6/-	BYZ13	4/-
25 + 5/3		Mullard 6a 200v	25 + 3/6
100 + 4/6		100 + 3/2	
		500 + 2/10	

BY127	4/-	BC107/8/9	2/6 ea.
Mullard 1000v 1 amp Plastic	25 + 3/3	I.T.T. Planars	25 + 2/3
100 + 3/-		100 + 2/-	
		500 + 1/9	

BT102/500R	15/-	OCPT1	19/6
Mullard Thyristor 500 p.i.v. 6.5a	25 + 12/6	Mullard Photo	25 + 17/3
100 + 11/-		100 + 14/9	
		500 + 13/6	

OA200/OA202	1/9	OC28	12/6
SILICON DIODES	25 + 1/6	Mullard Power	25 + 11/-
100 + 1/3		100 + 10/-	
500 + 1/1		500 + 8/6	

OC42	6/-	OC71	3/-
Mullard	25 + 5/3	Mullard	25 + 2/3
100 + 4/9		100 + 2/-	
500 + 4/3		500 + 1/9	

OC45	3/6	BCY34	5/-
Mullard	25 + 3/6	Mullard	25 + 4/3
100 + 2/6		100 + 3/9	
500 + 2/-		500 + 3/6	

OC75	5/-	1N4001/2/3	1/6
Mullard	25 + 4/3	1 amp 100-300v	25 + 1/4
100 + 3/6		100 + 1/2	
500 + 3/-		500 + 1/-	

OC20	19/6	ZENER DIODES	
Mullard 100v	25 + 15/9	400 MW 5%	
100 + 14/6		BZY88 Range	
500 + 13/3		All Voltages	

1N4004/5	2/6	TYPE STN18	
400-600V 1 amp	25 + 2/-	Silicon Planar Transistors npn TO-18 Metal Can. Types similar to: 2N706, 2N2220, BSY27-95A, BSX44-76-77.	
100 + 1/9		Price: 500 £9, 1,000 £15	
500 + 1/6			

1N4006/7	3/-	TYPE STP18	
800-1000V 1 amp	25 + 2/10	Silicon Planar Transistors pnp TO-18 Metal Can. Types similar to: BCY70-72, 2N2906-7, 2N2411 and BC186-7. Also used as complementary to the above npn type device type STN18.	
100 + 2/6		Price: 500 £9, 1,000 £15	
500 + 2/3			

OC139	5/-	OC140	7/6
Mullard	25 + 4/-	Mullard	25 + 6/-
100 + 3/3		100 + 5/-	
500 + 3/-		500 + 4/-	

Take your Wellerchoice* in Soldering




Low Initial Cost *

Low initial cost Marksman irons, to cover most soldering needs. Screw-in tips on 15W and 25W make it easier to change the tips, which are nickel-plated and factory pre-tinned for longer life. The shanks are stainless steel to concentrate heat at the tips.

Instant Heat for Rapid Soldering *

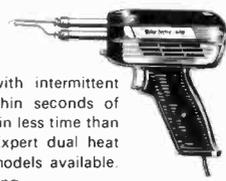Instant heat soldering guns to deal with intermittent soldering. Working heat is reached within seconds of pressing the trigger, so the job is finished in less time than it takes for a normal iron to heat up. Expert dual heat (100/140W) and Heavy Duty (275W) models available. Alternative tips available for plastics working.



Weller Electric Limited

Redkiln Way, Horsham, Sussex Tel: 0403 61747

1 MILLION SILICON PLANAR TRANSISTORS

NPN-PNP PLASTIC AND METAL CAN TYPES

Clearance of manufacturers' seconds, selected in types and guaranteed no open or short circuit units. Ideal cheap transistors for radio enthusiasts, manufacturers, schools and colleges.

TYPE STN18
Silicon Planar Transistors npn TO-18 Metal Can. Types similar to: 2N706, 2N2220, BSY27-95A, BSX44-76-77.
Price: 500 £9, 1,000 £15

TYPE STP18
Silicon Planar Transistors pnp TO-18 Metal Can. Types similar to: BCY70-72, 2N2906-7, 2N2411 and BC186-7. Also used as complementary to the above npn type device type STN18.
Price: 500 £9, 1,000 £15

TYPE STNL
Silicon Plastic Epitaxial Planar Transistors TO-92 case. I.C. 200mA, 300mW medium to high gain, available in npn or pnp and types similar to:
NPN 2N2926 — 2N2711 — 2N3391 — 2N3707 — 2N3711 — BC167-8-9
Price: 500 £7.10.0; 1,000 £13

TYPE STPL
As above but in pnp and similar to types 2N5354-56, 2N4058 2N4061 and 2N3702-3. Also used as complementary to the above npn devices type STNL.
Price: 500 £7.10.0; 1,000 £13

TYPE STNK
Silicon Planar Plastic Transistor npn with TO-18 pin circular lead configuration, I.C. 200mA, 300mW and similar to BC107-8-9, BC170, BC173, BC182-184, BC237-8-9 and BC337-8.
Price: 500 £9.10.0; 1,000 £16

When ordering, please state type required, i.e., STNK or STN18, etc.
All goods Ex-stock sent by return. Cash with order please to:

DIOTRAN SALES

P.O. Box 5, WARE, Herts.

S.A.E. For full list of surplus semiconductors

PLEASE NOTE MINIMUM ORDER SHOULD BE 10/-
Quantity prices 100+ Phone (01) 723 0401 Ex. 4. All listed devices are from stock at time of going to press. Please add 1/6 post packing to your order.

NEW AUTUMN LIST, NEW DEVICES, NEW PRICES. ASK FOR LIST 36, SEND FOR FREE COPY TODAY. Discounts 10% on 12+ any one type. 15% on 25+ any one type.



303 EDGWARE ROAD
LONDON, W.2
(01) 723 1008/9
OPEN MON-SAT 9am-6pm THURS 9am-1pm

TYPE 13A DOUBLE BEAM OSCILLOSCOPES




An excellent general purpose D/B oscilloscope. 7.5: 2 1/2-750KHz. Bandwidth 0.5 MHz. Sensitivity 33mV/CM. Operating voltage 0/110/200/250V a.c. Supplied in excellent working condition. **\$22.10.0.** Carriage 30/-.

AVO CT471A MULTIMETER

Battery operated, fully transistorised. Sensitivity 100mΩ/v. Measures AC/DC Voltages 12mV to 1,200V. AC/DC Current 12A to 1.2 Amp. Resistance 12 ohm to 120 MΩ HF, VHF, UHF. Voltage with multiplier 4v to 400v up to 50 Mc/s. 40mV to 4V up to 1,000 Mc/s. Offered in perfect condition. **\$55 each.** Carr. 10/-.

CRYSTAL CALIBRATORS No. 10

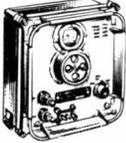

Small portable crystal controlled wavemeter. Size 7" 7 1/2" 4". Frequency range 500 Kc/s, 10 Mc/s (up to 30 Mc/s on harmonics). Calibrated dial. Power requirements 300 V.D.C. 15mA and 12 V.D.C. 0.5A. Excellent condition. **\$80/6.** Carr. 7/6.

TAPE CASSETTES

Top quality in plastic library boxes. C60 60 min 2 for **\$4/6** C90 90 min 12/3 for **\$6/6** C120 120 min 15/- 3 for **\$3/6** Cassette Head Cleaner 11/3. All Post Extra.

CLASS D WAVEMETERS



A crystal controlled heterodyne frequency meter covering 1.7-5 Mc/s. Operation on 4V d.c. Ideal for amateur use. Available in good used condition. **\$15.10.6.** Carr. 7/6, or brand new. **\$27.10.6.** Carr. 7/6.

B.C. 221 FREQUENCY METERS

latest release 125kHz to 20MHz. Excellent condition. Fully tested and checked out complete with calibrator charts. **\$27.10.0.** each, Carr. 10/-.

AM/FM SIGNAL GENERATORS



Oscillator Test No. 2. A high quality precision instrument made for the ministry by Airvac. Frequency coverage 20-80Mc/s. AM C.W./F.M. Incorporates precision dial, level meter, precision attenuator 1μV-100mV. Operation from 12V d.c. or 0/110/200/250V a.c. Size 12" 8 1/2" 8 1/2". Supplied in brand new condition complete with all connectors fully tested. **\$45.** Carr. 20/-.

AVO CT.38 ELECTRONIC MULTIMETERS

High quality 97 range instrument which measures a.c. and d.c. Voltage, Current, Resistance and Power Output Ranges d.c. volts 250mV-10,000V (10 megΩ-110 megΩ input). D.C. current 10μA-25A. Ohms 10-0.100 megΩ. a.c. volt 100mV-250V (with R.F. measuring head up to 250MHz) a.c. current 10A-25A. Power output 50 micro-watts-5 watts. Operation 0/110/200/250V a.c. Supplied in perfect condition complete with circuit lead and R.F. probe. **\$25.** Carr. 15/-.

ADMIRALTY 62B RECEIVERS



High quality 10 valve receiver manufactured by Murphy. Coverage in 3 bands 150-300 Kc/s-0.5 Mc/s-1.5 Mc/s; 3-9-30.5 Kc/s. I.F. 500KHz. Incorporates 2 R.F. and 3 I.F. stages, bandpass filter, noise limiter, crystal controlled P.F.O. calibrator for phones. Operation 150/230V a.c. Size 19 1/2" 13 1/2" 16in. Weight 114lb. Offered in good working condition. **\$22.10.0.** Carr. 30/-.

TO-2 PORTABLE OSCILLOSCOPE

A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2 CFS-1 MHz. Input Imp. 2 megΩ. 25 P.F. Illuminated scale. 2in. tube. 115 1/2" 180 230mm. Weight 8lb. 220/240 V a.c. Supplied brand new with handbook. **\$22.10.0.** Carr. 10/-.



SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC. ● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

NEW "SEW" DESIGNS!

CLEAR PLASTIC METERS BAKELITE PANEL METERS

TYPE SW. 100 100 x 80 mm		TYPE S-80 80 mm square fronts	
1mA	59/6	50μA	62/6
20V d.c.	59/6	100μA	59/6
50V d.c.	59/6	500μA	52/6
1A d.c.	59/6	1A d.c.	49/6
5A d.c.	59/6	20V d.c.	49/6
300V a.c.	59/6	50V d.c.	49/6
500μA	62/6	1A d.c.	49/6
		5A d.c.	49/6
		300V a.c.	67/6
		VU Meter	67/6

"SEW" CLEAR PLASTIC METERS

Type MR.85P. 4 1/2in 4 1/2in fronts.		Type MR.88P. 1 21/32in square fronts.	
10mA	52/-	150mA	27/6
50mA	52/-	200mA	27/6
100mA	52/-	300mA	27/6
300mA	52/-	500mA	27/6
1A	52/-	750mA	27/6
5A	52/-	1A	27/6
15A	52/-	2A	27/6
30V d.c.	52/-	5A	27/6
20V d.c.	52/-	10A	27/6
50V d.c.	52/-	3V d.c.	27/6
150V d.c.	52/-	10V d.c.	27/6
300V d.c.	52/-	15V d.c.	27/6
15V a.c.	52/-	20V d.c.	27/6
30V a.c.	52/-	100V d.c.	27/6
50V a.c.	52/-	100μA-100μA	35/-
8 Meter 1mA	57/6	200μA	35/-
VU meter	72/-	500μA	30/-
1A a.c.*	52/-	500-500μA	27/6
5A a.c.*	52/-	1mA	27/6
10A a.c.*	52/-	1-0-1mA	27/6
20A a.c.*	52/-	2mA	27/6
30A a.c.*	52/-	5mA	27/6
		10mA	27/6
		20mA	27/6
		50mA	27/6
		100mA	27/6
		VU meter	42/-

Type MR.85P. 2 1/2in square fronts.		Type MR.45P. 2in square fronts.	
50μA	42/-	50μA	45/-
50-0-50μA	42/-	50-0-50μA	42/-
100μA	42/-	100μA	42/-
100-0-100μA	47/6	100-0-100μA	37/6
500μA	45/-	200μA	37/6
1mA	40/-	500μA	32/-
5mA	40/-	500-0-500μA	30/-
10mA	40/-	1mA	30/-
50mA	40/-	5mA	30/-
100mA	40/-	10mA	30/-
500mA	40/-	50mA	30/-
1A	40/-	100mA	30/-
5A	40/-	1A	30/-
		5A	30/-
		10A	30/-
		20A a.c.*	30/-
		30A a.c.*	30/-

* MOVING IRON - ALL OTHERS MOVING COIL	
50μA	67/8
50-0-50μA	55/-
100μA	55/-
100-0-100μA	52/-
500μA	47/6
500-0-500μA	42/-
1mA	42/-
5mA	42/-
10mA	42/-
50mA	42/-
100mA	42/-
500mA	42/-
1A	42/-
5A	42/-
10V d.c.	42/-

"SEW" BAKELITE PANEL METERS	
25μA	70/-
50μA	47/6
50-0-50μA	45/-
100μA	45/-
100-0-100μA	45/-
500μA	42/-
1mA	35/-
1-0-1mA	35/-
5mA	35/-
10mA	35/-
50mA	35/-
100mA	35/-

EDGWISE METERS	
500μA	60/-
50-0-50μA	57/6
100μA	57/6
100-0-100μA	55/-
200μA	55/-
500μA	52/-
1mA	47/6
300V a.c.	47/6
VU meter	65/-

Send for illustrated brochure — Discounts for Quantities

POWER RHEOSTATS


High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range cross-stock. Single hole fixing. 1in dia. shafts. Bulk quantities available.

25 WATT. 10/25/50/100/250/500/1,000/1,500/2,500 or 5,000 ohms, 14/6. P. & P. 1/6.

50 WATT. 10/25/50/100/250/500/1,000/2,500 or 5,000 ohms, 21/- P. & P. 1/6.

100 WATT. 15/10/25/50/100/250/500/1,000 or 2,500 ohms, 27/6. P. & P. 1/6.


FTC-401 TRANSISTOR TESTER

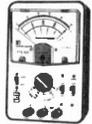

Full capabilities for measuring A, B and ICO, *npn* or *ppn*. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. **\$6.10.6.** P. & P. 3/-.

MARCONI TF148E DISTORTION FACTOR METERS. Excellent condition. Fully tested. \$20. Carr. 15/-.

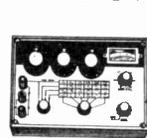TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE



A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-11.1 megΩ. G. Ranges ±1%. L. 1μH - 11.1 HENRYs. G. Ranges ±2%. C. 10pF - 11.1 μF. M.F.D. 100-1:1100. G. Ranges ±1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter Indication. Attractive 2 tone metal case. Size 7 1/2" 5 1/2" 2in. **\$20.** P. & P. 5/-.

COSSOR 1049 DOUBLE BEAM OSCILLOSCOPES. D.c. coupled. Band width 1kc/s. Perfect order. \$25. Carr. 30/-.

TE-20D RF SIGNAL GENERATOR



Accurate wide range signal generator covering 120Kc/s to 500Mc/s on 6 bands. Directly calibrated. Variable RF attenuator, audio output. Xtal socket for calibration. 220/240V a.c. Size 140 x 210 x 170mm. Brand new with instructions. **\$15.** Carr. 7/6.

LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS

Frequency 0-20 Kc/s on 2 ranges. Output 500Ω or 5kΩ. Operation 200/250V. A.C. Supplied in perfect order. **\$12.10.0.** Carr. 10/-.


TY75 AUDIO SIGNAL GENERATOR



Sine Wave 20c/s to 200Kc/s. Square Wave 20c/s to 30Kc/s. High and low impedance output. Output variable up to 6 volts. 220/240 volts a.c. Size 210 x 150 x 120mm. Brand new with instructions. **\$18.** Carr. 7/6.

MARCONI TF885 VIDEO OSCILLATORS. 0-5MHz. Sine Square Wave. \$45. Carr. 20/-.

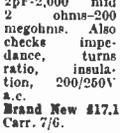LAFAYETTE TE46 RESISTANCE CAPACITY ANALYSER



2pF-2,000 mid 2 ohms-200 megohms. Also checks impedance, turns ratio, insulation, 200/250V a.c. Brand New **\$17.10.0.** Carr. 7/6.

270 500 MICROAMP METER. Incorporated in Radio Altitude Indicator 1D-14APN. Ideal for rev. counter, etc. 15/6. P. & P. 3/-.

ADVANCE TEST EQUIPMENT

Brand new and boxed in original sealed cartons. **J1B. AUDIO SIGNAL GENERATOR.** 15 c/s to 60 Kc/s. Sine wave. Output 600 ohms or 5 ohms **\$30.0.0.**

VM79. UHF MILLIVOLT METER. 100 Kc/s to 1,000 Mc/s. a.c. 10 mV to 3V. D.c. 10 mV to 3V. Current 0.01 mA to 0.3 mA. Resistance 1 ohm to 10 megohm. **\$125.0.0.**

TT15. TRANSISTOR TESTER. Full range of facilities for testing PNP and NPN transistors in or out of circuit. **\$37.10.0.** Carriage 10/- per item.

MARCONI TF158M BEAT FREQUENCY OSCILLATORS. 0-40KHz. **\$20.** Carr. 30/-.

G. W. SMITH & CO (RADIO) LTD.

Also see next two pages

SEMICONDUCTORS/VALVES

BRAND NEW & FULLY GUARANTEED

TRANSISTORS

1N914	1/6	AC128	5/-	BNY38	4/-	1L4	2/6	25L6	7/6	EL91	5/-
1N4001	1/6	AC154	3/-	BNY39	4/6	1R5	7/-	25Z4	8/6	EL95	7/-
1N4002	1/6	AC176	5/-	BNY51	6/6	8M5	5/-	25Z5	8/6	EM50	8/6
1N4003	2/-	AC187	6/6	MPI65	15/-	IT4	4/6	25Z6	15/-	EM81	8/6
1N4004	2/-	AC188	6/6	BNY45.A	3/1U	1T4	4/6	30C15	15/-	EM84	7/6
1N4005	2/6	AC177	6/6	BY106	3/6	1U5	9/6	30C17	16/-	EM85	11/-
1N4006	3/-	AC118	5/-	BY124	3/6	OA2	6/6	30C18	15/-	EM87	11/-
1N4007	4/-	AC119	5/-	BY126	3/6	OB2	6/6	30F5	17/-	EY51	8/-
1N4148	1/6	AC120	4/6	BY127	4/6	OZ4	6/6	30FL1	15/-	EY86	8/6
1N9054	4/6	AC121	4/6	BYZ10	8/6	OL4	2/6	30FL12	16/6	EY87	8/6
2G301	4/6	AC122	3/6	BYZ11	7/6	OM6	6/6	30FL14	15/6	EZ40	7/6
2G302	4/6	AC123	3/6	BYZ12	6/6	QA4	6/6	30L15	17/-	EZ41	9/-
2G303	4/6	AC124	3/6	BYZ13	5/6	384	7/6	30L17	17/-	EZ80	5/6
2G304	7/6	AD140	10/6	MJ480	10/6	3V4	8/6	30P12	16/-	EZ81	5/6
2G308	6/6	AD149	10/6	MJ481	25/6	3R4	11/6	30P19	15/6	GZ32	9/6
2G309	6/6	AD161	7/6	MPP102	8/6	5T4	8/6	30P11	16/6	GZ34	11/-
2G371	4/6	AD162	7/6	MPP103	7/6	5V4	8/6	30P13	18/6	K196	27/6
2G374	5/6	AD174	6/6	MPP104	7/6	6V4	9/6	30PL14	17/6	KT88	33/6
2G381	5/6	AF110	6/6	NK213	5/6	EZ46	7/6	35L4	9/6	MU14	8/6
2N694	8/6	AF115	6/6	NK214	3/6	G3012	15/-	35W4	5/-	PABC80	8/6
2N697	8/6	AF117	5/6	NK215	4/6	GA7	4/6	35Z4	5/6	PACB	11/6
2N698	8/6	AF118	12/6	NK216	7/6	GAG7	7/6	35Z5	7/6	PC88	13/-
2N706	2/6	AF119	8/6	NK217	8/6	GAK5	7/6	50B5	7/6	PC97	8/6
2N708A	2/6	AF124	5/6	NK224	4/6	GAK5	11/6	50C6	7/6	PC90	9/6
2N764	3/6	AF126	3/6	NK241	5/6	GA5	3/6	58A2	7/6	PC85	8/6
2N914	4/6	AF127	3/6	NK261	4/6	GAQ5	6/6	807	9/6	PC88	12/6
2N916	4/6	AF139	5/6	NK271	5/6	GAN6	6/6	1625	6/6	PC89	10/6
2N918	7/6	AF178	9/6	NK274	4/6	GAT6	5/6	5763	13/6	PCC180	11/-
2N920	4/6	AF180	10/6	NK275	5/6	GAU6	5/6	6146	30/6	PCF80	6/6
2N930	5/6	AF181	8/6	NK275	5/6	GAU6	6/6	AZ31	10/6	PCF82	6/6
2N1131	6/6	AF186	6/6	NK278	5/6	GAU6	6/6	AY21	10/6	PCF84	9/6
2N1132	6/6	AP239	8/6	NK281	5/6	GAU6	6/6	DAF91	5/6	DAP91	7/6
2N1302	4/6	AN526	5/6	NK403	15/6	BBH6	6/6	DAF91	7/6	PCF8000	15/-
2N1303	4/6	AN527	6/6	NK404	12/6	BBJ6	8/6	DAF91	4/6	PCF801	10/6
2N1304	5/6	AN528	5/6	NK405	15/6	BGQA	7/6	D96	7/6	PCF802	10/6
2N1305	5/6	AN529	5/6	NK406	15/6	BGR7	17/6	DK91	7/6	PCF805	15/-
2N1306	5/6	AN530	5/6	NK407	15/6	BRM	13/6	DK92	8/6	PCF806	15/-
2N1307	5/6	BA131	18/6	NK10439	5/6	BRW6	16/6	DK96	8/6	PCF808	13/6
2N1308	5/6	BC107	1/8	OA10	3/6	BRW6	13/6	DL92	7/6	PCL82	7/6
2N1309	5/6	BC108	2/6	OA47	2/6	BZ6	6/6	DL94	8/6	PCL83	13/6
2N1613	4/6	BC109	2/6	OA70	2/6	6C4	6/6	DL96	7/6	PCL84	8/6
2N1711	5/6	BC113	5/6	OA79	2/6	6CD6	25/6	DM70	6/6	PCL85	9/6
2N1889	6/6	BC116	8/6	OA81	2/6	6CL6	10/6	DY86	6/6	PCL86	9/6
2N1893	6/6	BC116	8/6	OA85	2/6	6CW4	12/6	EY87	7/6	PLF200	11/-
2N2147	15/6	BC125	11/6	OA90	2/6	6F1	12/6	EY87	12/6	PLF36	11/-
2N2160	12/6	BC127	11/6	OA91	1/6	6F1	12/6	EY87	12/6	PLF36	11/-
2N2193	9/6	BC148	2/6	OA95	1/6	6F13	7/6	EABCO	6/6	PL81	9/6
2N2217	5/6	BC149	4/6	OA90	1/6	6F14	12/6	EAF42	10/6	PL83	8/6
2N2218	5/6	BC167	3/6	OA202	3/6	6F15	11/6	EBC1	3/6	PL84	7/6
2N2219	6/6	BC172	3/6	OA210	3/6	6F18	8/6	EBC4	10/6	PL600	15/-
2N2369	4/6	BC177	7/6	OC20	19/6	6F23	15/6	EBC8	8/6	PL504	16/6
2N2369A	4/6	BC186	7/6	OC22	9/6	6H6	3/6	EBC8	8/6	PL602	10/6
2N2484	4/6	BC184L	4/6	OC23	10/6	6J5	4/6	EBC8	8/6	PL602	10/6
2N2613	7/6	BC212L	4/6	OC24	10/6	6J5GT	6/6	EBC21	12/6	PY81	8/6
2N2644	10/6	BCY30	5/6	OC25	7/6	6J6	3/6	EBC8	12/6	PY82	6/6
2N2905	8/6	BCY31	6/6	OC26	12/6	6J7	8/6	EBC8	12/6	PY83	7/6
2N2923	8/6	BCY32	10/6	OC29	12/6	6K8G	9/6	ECC40	11/6	PY88	8/6
2N2925	8/6	BCY33	5/6	OC35	10/6	6LGT	9/6	ECC84	6/6	PY800	10/6
2N2926	8/6	BCY34	5/6	OC36	12/6	6LGT	9/6	ECC84	6/6	PY800	10/6
2N2926A	8/6	BCY38	8/6	OC31	5/6	6A7	7/6	ECC88	8/6	PY81	10/6
2N2926B	8/6	BCY42	8/6	OC41	5/6	68A7	7/6	ECC88	8/6	PY81	10/6
2N2926C	8/6	BCY43	8/6	OC42	6/6	68G7	7/6	ECC88	8/6	PY81	10/6
2N3033	5/6	BCY71	6/6	OC44	3/6	68J7	7/6	ECC88	8/6	PY81	10/6
2N3054	10/6	BCY72	3/6	OC45	3/6	68K7	6/6	ECC21	11/6	U191	14/6
2N3085	15/6	BCZ11	7/6	OC46	5/6	68L7	6/6	ECC35	12/6	U281	8/6
2N331A	7/6	BD121	13/6	OC70	2/6	68N7	5/6	ECC41	15/6	U282	8/6
2N3416	7/6	BD123	12/6	OC71	3/6	68Q7	5/6	ECC81	8/6	U301	11/6
2N3702	17/6	BP115	5/6	OC73	6/6	6V4	6/6	ECL80	9/6	U801	30/6
2N3703	17/6	BP117	9/6	OC74	6/6	6V6GT	6/6	ECL82	6/6	UACB80	10/6
2N3704	3/6	BP167	5/6	OC75	5/6	6X4	5/6	ECL83	12/6	UBC41	9/6
2N3705	3/6	BP173	5/6	OC76	5/6	6X5GT	5/6	ECL86	8/6	UBC81	8/6
2N3706	4/6	BP180	7/6	OC77	8/6	6X5GT	5/6	EFC3A	8/6	UBF80	7/6
2N3707	4/6	BP181	7/6	OC78	8/6	6X5GT	5/6	EFC3A	8/6	UBF80	7/6
2N3708	3/6	BP182	6/6	OC81	5/6	10F1	18/6	EF40	10/6	UBF89	7/6
2N3709	2/6	BP185	5/6	OC83	5/6	10P13	11/6	EF41	12/6	UCC84	9/6
2N3711	2/6	BP194	3/6	OC84	5/6	10P14	20/6	EF42	14/6	UCC85	8/6
2N3819	7/6	BP195	3/6	OC139	5/6	12AT7	4/6	EF80	5/6	UCC89	10/6
2N3903	7/6	BP200	7/6	OC140	7/6	12A7	5/6	EF80	6/6	UCC89	10/6
2N3904	7/6	BP224	6/6	OC146	7/6	12AX7	6/6	EF80	6/6	UCH21	12/6
2N3905	7/6	BP225	6/6	OC170	5/6	12AV6	6/6	EF91	4/6	UCL81	6/6
2N3906	7/6	BP244	6/6	OC171	6/6	12BA6	6/6	EF92	7/6	UCL83	12/6
2N4058	3/6	BFX12	4/6	OC200	7/6	12BE6	6/6	EF183	6/6	UF41	10/6
2N4069	5/6	BFX13	4/6	OC201	9/6	12BH7	6/6	EF184	7/6	UF80	7/6
2N4061	3/6	BFX29	6/6	OC202	12/6	18AQ5	8/6	EH90	8/6	UF85	8/6
2N4062	4/6	BFX30	6/6	OC203	7/6	20D1	9/6	EL34	10/6	UF89	7/6
2N4286	3/6	BFX44	7/6	OC204	8/6	20L1	15/6	EL33	17/6	UL41	12/6
2N4287	3/6	BFX45	8/6	OC205	12/6	20P1	10/6	EL41	11/6	UL44	6/6
2N4288	3/6	BFX46	8/6	OC206	12/6	20P1	10/6	EL42	11/6	UY41	8/6
2N4289	3/6	BFX86	6/6	OC207	10/6	20P2	12/6	EL81	10/6	UY85	6/6
2N4290	3/6	BFX87	6/6	ORP12	10/6	20P4	20/6	EL84	5/6	VR105/30	5/6
2N4291	3/6	BFY18	8/6	ORP60	8/6	20P5	20/6	EL85	5/6	VR105/30	5/6
2N4292	3/6	BFY20	12/6	P345A	5/6						
2N5354	5/6	BFY50	4/6	PL4001	2/9						
2N5355	5/6	BFY51	4/6	PL4002	3/9						
2N5102	5/6	BFY52	4/6	PL4003	3/9						
2N5103	5/6	BFY90	18/6	PL4004	3/9						
2N5104	7/6	BFY10	8/6	PL4005	3/9						
28150	10/6	BRX20	3/6	PL4006	4/9						
40361	11/6	BRX21	7/6	PL4007	4/9						
40362	12/6	BRX76	3/6	TI843	8/9						
AC107	7/6	BY826	3/6	TI844	2/6						
AC126	5/6	BY827	4/6	TI845	3/6						
AC127	5/6	BY828	3/6	TI846	3/6						

VALVES

6X4	5/6	6X5GT	5/6	6X6	5/6	6X8	5/6	6X8GT	5/6	6X9	5/6	6X9GT	5/6	6X9GT	5/6
6Y4	5/6	6Y5	5/6	6Y6	5/6	6Y7	5/6	6Y8	5/6	6Y9	5/6	6Y9GT	5/6	6Y9GT	5/6
6Z4	5/6	6Z5	5/6	6Z6	5/6	6Z7	5/6	6Z8	5/6	6Z9	5/6	6Z9GT	5/6	6Z9GT	5/6
6Z4	5/6	6Z5	5/6	6Z6	5/6	6Z7	5/6	6Z8	5/6	6Z9	5/6	6Z9GT	5/6	6Z9GT	5/6
6Z4	5/6	6Z5	5/6	6Z6	5/6	6Z7	5/6	6Z8	5/6	6Z9	5/6	6Z9GT	5/6	6Z9GT	5/6

THYRISTORS

PIV	50	100	200	300	350	400
1A	5/6	7/6	8/6	9/6	10/6	11/6
3A	6/6	7/6	8/6	9/6	10/6	11/6
7A	11/6	13/6	14/6	15/6	16/6	17/6
10A	11/6	13/6	14/6	15/6	16/6	17/6
100A	—	—	—	50/6	55/6	—

ZENER DIODES

400mw. (3.3 to 33V)	3/6	1.5 watt (2.4 to 30V)	4/6
10 watt (3.3 to 100V)	5/6		

INTEGRATED CIRCUITS

RUSSIAN C1-16 DOUBLE BEAM OSCILLOSCOPES

5MHz Pass Band. Separate Y1, Y2 amplifiers. Calibrated triggered sweep from 0.2µsec to 100msec/cm. Supplied complete with all accessories and instructions. £27. Carr. paid.



MARCONI CT44/TF956 AF ABSORPTION WATTMETER

1 µwatt to 6 watts. £20. Carr. 20/-.

TELLI DECADE RESISTANCE ATTENUATOR

Variable range 0-11dB. Connections 1/2 balanced T and Bridge T. Impedance 600 Ω range (0-1dB : 10) + (1dB : 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200kHz (—3dB). Accuracy: 0-05dB; +indication dB ±0.01. Maximum input less than 4W (50V). Built in 600 Ω load resistance with internal external switch. Brand new £27.10. P. & P. 5/-.



BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

Sine 18-200,000Hz; Square 18-50,000Hz. Output max +10dB (10k Ω). Operation internal batteries. Attractive two-tone case 7 1/2in x 5in x 2 1/2in. Price £17.10. Carr. 3/6.




TE-16A Transistorized Signal Generator. 5 ranges 400 kHz-30 MHz. An inexpensive instrument for the handyman. Operates on 9V battery. Wide, easy to read scale. 800 kHz modulation. 5V : 0.5 : 31. Complete with instructions and leads. £7.18.6. P. & P. 4/-.



BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR

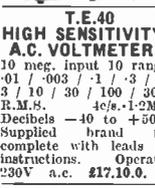New high quality portable instrument. Sine 1Hz to 100kHz. Square 20Hz to 20kHz. Output max. +10dB (10k Ω). Operation 220/240V a.c. Size 215mm x 150mm x 120mm. Price £27.10.0. Carr. 5/-.



T.E.40 HIGH SENSITIVITY A.C. VOLTMETER
10 meg. input 10 ranges: 0.1 / 0.03 / 1 / 3 / 10 / 30 / 100 / 300V. R.M.S. 4c/s. 1.2Mc/s. Decibels —10 to +50dB. Supplied brand complete with leads and instructions. Operation 230V a.c. £17.10.0. Carr. 5/-.



TE-65 VALVE VOLTMETER
High quality instrument with 28 ranges. D.c. volts 1.5-1,500V. A.c. volts 1.5-1,500V. Resistance up to 1,000 megohms, 220/240V a.c. operation. Complete with probe and instructions. £17.10.0. P. & P. 6/- Additional Probes available: R.F. 42/6. H.V. 50/-.



AUTO TRANSFORMERS
0.115/230V. Step up or step down. Fully shrouded.
150 W. £2.7.6. P. & P. 3/6
300 W. £3.5.0. P. & P. 4/6
500 W. £4.19.6. P. & P. 6/6
1,000 W. £7.5.0. P. & P. 7/6
1,500 W. £8.19.6. P. & P. 8/6
7,500 W. £15.10.0. P. & P. 25/-

SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS

Compact and panel mounting. Ideal for control of lamps, drills, electrical appliances, etc. Input 230/240V a.c. Output continuously variable from 20V to 230V. Model MR2305 5A 68 x 46 x 43mm, £27.6. Model MR210 10A 90 x 68 x 60mm, £11.19.6. Postage 2/6.



MULTIMETERS for EVERY purpose!



TECH PT-34. 1,000 Ohm P.T. Voltmeter. 0/10/50/250/500/1,000V a.c. 0/10/100/500mA. d.c. 0/1/100K. 39/6. P. & P. 2/6.



MODEL TE-200. 20,000 O.P.V. Mirror scale, overload protection. 0/3/25/125/1,000V d.c. 0/10/50/250/1,000V a.c. 0/60µA/250mA. 0/60K/4 meg. —20 to 62dB. 75/- P. & P. 3/-.



MODEL 500. 30,000 O.P.V. with overload protection, mirror scale 0/1.5/2.5/10/25/100/250/500/1,000V a.c. 0/2.5/10/25/100/250/500/1,000V a.c. 0/50µA/5/50/500 mA. 2 amp. d.c. 0/60K/6 Meg./60 Meg. Ω. £3.17.6. Post paid.



MODEL TE-70. 30,000 O.P.V. 0/315/60/300/600/1,200V d.c. 0/6/30/120/600/1,200V a.c. 0/30µA/3/300mA. 0/16K/160K/1.6M/16 meg. £5.10.0. P. & P. 3/-.



TMK MODEL TW-50K. 46 ranges, mirror scale. 50K/Volt d.c. 5K/Volt a.c. D.c. volts: 0.125, 0.25, 1.25, 2.5, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.c. volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.c. current: 25, 50µA, 2.5, 5, 25, 50, 250, 500mA, 5, 10A. Resistance: 10K, 100K, 1 meg., 10 meg. Decibels: —20 to +81.5dB. £3.17.6. P. & P. 3/6.




TE-900 20,000 Ohm/VOLT G.I.A.T. MULTIMETER. Mirror scale and overload protection. 6in full view meter. 2 colour scale. 0/2.5/10/250/1,000/5,000V a.c. 0/25/125/10/50/250/1,000/5,000V a.c. 0/50µA/110/600mA/10A. d.c. 0.2K/200K/20 meg. ohm. £15.0.0. P. & P. 5/-.



MODEL 5025. 57 ranges, giant 5 1/2 in meter, polarly reverse switch. Sensitivity: 50K/Volt d.c. 5K/Volt a.c. D.c. Volts: 0.125, 0.25, 1.25, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.c. Volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.c. current: 25, 50µA, 2.5, 5, 25, 50, 250, 500mA, 5, 10A. Resistance: 2K, 10K, 100K, 1 meg, 10 meg. Decibels: —20 to +85dB. £12.10.0. P. & P. 3/6.

AVOMETER MOVEMENTS

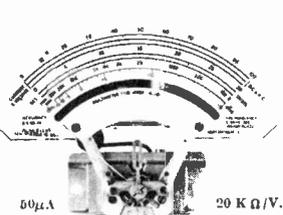

Spare movements for Model 8 or 9. (Fitted with Model 9 scale) or basis for any multimeter. Brand New Boxed 69/6. P. & P. 3/6.



"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS
Excellent quality • Low price • Immediate delivery
MODEL S-260 General Purpose Bench Mounting
1A £5.10.0
2.5A £6.15.0
5A £9.15.0
8A £14.10.0
10A £18.10.0
12A £21.0.0
20A £27.0.0
MODEL S-260 B Panel Mounting
1A £5.10.0
2.5A £6.15.0
Please add postage
ALL MODELS INPUT 230 VOLTS, 50/60 CYCLES, OUTPUT VARIABLE 0-260 VOLTS
Special discounts for quantity

HONOR TE.10A. 20k Ω / Volt. 5/25/50/250/500/2,500V d.c. 10/50/100/500/1,000V a.c. 0/50µA/2.5mA 250mA d.c. 0/6K/6 meg. ohm. —20 to +22dB. 0-10, 100 mfd. 0-100-0-1 mfd. 69/6. P. & P. 3/-.



MODEL TE-300. 30,000 O.P.V. Mirror scale, overload protection 0/0.6/3/15/60/300/1,200V d.c. 0/6/30/120/600/1,200V a.c. 0/20µA/1.6mA/160mA/300mA/600mA. 0/8K/80K/800K/8 meg. —20 to +63dB. £5.19.6. P. & P. 3/-.



MODEL TE 80. 20,000 O.P.V. 0/10/50/100/500/1,000V a.c. 0/5/25/50/250/500/1,000V d.c. 0.5µA. 5/50/500mA. 0/6K/60K/600K/6 Meg. £4.17.6. P. & P. 3/-.



MODEL TE-90. 50,000 O.P.V. Mirror scale, overload protection. 003/13/60/300/600/1,200V d.c. 0/6/30/120/300/1,200V a.c. 0/6/30/60/600mA. 0/18K/180K/1.8M/18 meg. —20 to +63dB. £7.10.0. P. & P. 3/-.



TMK MODEL TW-200B. Features Resettable Overload Button. Sensitivity: 20K Ω/Volt d.c. 5K Ω/Volt a.c. D.c. volts: 0-0.5, 0.5, 5, 50, 500mA, 10A. Resistance: 0-0.5K, 500, 0-500K, 5 meg. Decibels: —20 to +52dB. £11.10.0. P. & P. 3/6.



MODEL AS-100D 100K Ω/Volt. 5in, mirror scale. Built-in meter protection 0/3/12/60/120/300/600/1,200V d.c. 0/6/30/120/300/600V a.c. 0/10µA/6/60/300mA/12A. 0/2K/200K/2M/200M. —20 to +17dB. £12.10.0. P. & P. 3/6.



TMK LAB TESTER. 100,000 O.P.V. 6 1/2 in scale buzzer short circuit check. Sensitivity: 100,000 O.P.V. d.c. 5V/Volt a.c. D.c. volts: 0.5, 2.5, 10, 50, 250, 1,000V. A.c. volts: 3, 10, 50, 250, 500, 1,000V. D.c. current: 10, 100µA, 10, 100, 600mA, 2.5, 10A. Resistance: 1K, 10K, 100K, 10 meg, 100 meg. Decibels: —10 to +49dB. Plastic case with carrying handle, size 7 1/2in x 6 1/2in x 3 1/2in. £18.18.0. P. & P. 5/-.



SKYWOOD SW-500

50 K Ω/Volt. Mirror scale. DC Volts 0.8/3/12/30/300/600. AC Volts 3/30/300/600. DC Current 20µA/6/60/600mA. Resistance 10K/100 K/1Meg/10 Meg. Decibels —20 to +57dB £7.10.0. P. & P. 3/-.

270° WIDE ANGLE

1mA METERS
MW1-6 60mm square £3.19.6. MW1-8 80mm square £4.19.6. P. & P. extra.



UNR-30 RECEIVER
4 Bands covering 500KHz-30MHz. B.F.O. Built in Speaker 220/240V a.c. Brand new with instructions. £15.15.0. Carr. 7/6.

WS82 TRANSCEIVERS
Large quantity available for EXPORT! Excellent condition. Enquiries invited.

UR-IA SOLID STATE COMMUNICATION RECEIVER
4 Bands covering 50KHz-30MHz. FET, 8 Meter, Variable BFO for 88B. Built in Speaker, Telescopic Aerial, Bandspread, Sensitivity Control. 220/240V a.c. or 12V d.c. 12 1/2in x 4 1/2in x 7in. Brand new with instructions. £25. Carr. 7/6.

LAFAYETTE HA-600 RECEIVER
General coverage 150-400KHz, 500KHz-30MHz. FET front end, 2 mech. filters, product detector, variable B.F.O., noise limiter, 8 Meter, Bandspread, RF Gain. 13 1/2in x 9 1/2in x 8 1/2in. 18dB. Brand new with instructions. £45. Carr. 10/-.

LAFAYETTE HA-500 SOLID STATE AMATEUR COMMUNICATION RECEIVER
3.5-4, 7-7.3, 14-14.35, 21-21.45, 28-29.7, 50-54MHz. Dual conversion, 2 mech. filters, product detector, variable BFO, 8 Meter, 100KHz calibrator. 220/240V a.c. or 12V d.c. 15 1/2in x 8 1/2in. 18dB. Brand new with instructions. £27.10.0. Carr. paid (100KHz Crystal 39/6 extra).

LAFAYETTE F80 VHF FM RECEIVER
Solid State. 152-174MHz. Fully tuneable or crystal controlled (not supplied). Built in Speaker, Squelch and Volume Control. 220/240V a.c. or 12V d.c. Brand new with instructions. £27.10.0. Carr. 10/-.

FULL RANGE OF TRIO EQUIPMENT
VOLTAGE STABILISER TRANSFORMERS
150-200V input. Output 230V. Available 150W or 225W. £12.10.0. Carr. 5/-.

EDDYSTONE VHF RECEIVERS MODEL 770R. 19-105 Mc/s. Excellent condition. £150.

INTERCOM/BABY SITTER
Transistorized Incoms, ideal for home / office / workshop, etc. 2-way buzzer call system. For desk or wall mounting. Supplied complete with connecting wire, batteries, instructions, 2 station 59/6. P. & P. 2/6. 4 station £6.12.6. P. & P. 5/-.

STOP PRESS!
NEW BRANCH AT
27 TOTTENHAM COURT ROAD
Opening during December

All Mail Orders to—
147, Church Street,
London, W.2
Tel: 01-262 6562
(Trade supplied)

G.W.SMITH & CO. (RADIO) LTD

27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715
3 Lisle Street, London, W.C.2 Tel: 01-437 8204
34 Lisle Street, London, W.C.2 Tel: 01-437 9155
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387
OPEN 9-6 MONDAY TO SATURDAY (EDGWARE ROAD 1/2 DAY THURSDAY)



VARI-STAT THERMOSTATIC SOLDERING IRON

HIGH PRODUCTION MINIATURE MODEL D. 50 WATT

Weight .. 2 oz.
Heating time 50 seconds
Bit Sizes .. 1/16", 3/32", 1/8", 3/16", 1/4"
Nickel or Iron Plated
Voltage .. 250 to 12 volts
Price .. 66/-

HIGH PRODUCTION INSTRUMENT MODEL H. 150 WATT

Weight .. 6 oz.
Heating time 1 min. 45 sec.
Bit Sizes .. 3/16", 1/4", 3/8", 7/16"
Nickel or Iron Plated
Voltage .. 250 to 24 volts
Price .. 95/-

OTHER VARI-STAT IRONS:

Miniature Model M 50 watt Push-in Bits 1/32"
1/16", 3/32"
Instrument Model B 70 watt Bit Size 1/16"
Industrial Model I 500 watt Bit Size 5/8"

CARDROSS ENGINEERING CO. LTD.
Woodyard Road, Dumbarton
Phone: Dumbarton 2655

AMPLIFIER & PREAMP. PRINTED CIRCUIT BOARDS FOR MULLARD CIRCUITS

High quality Printed Circuit Boards for the following circuits shown in the Mullard publication **Transistor Audio and Radio Circuits**.

10 W high quality audio amplifier (p.102) 13/2d
25 W high quality audio amplifier (p.106) 14/0d
10/25 W high quality audio preamplifier (p.108) 14/7d
Price each including postage and packing. Cash with order.

All boards are tinned to prevent oxidization and to aid soldering and have the component identification printed on the reverse.

BRIBOND PRINTED CIRCUITS LTD
Terminus Road, Chichester, Sussex



PHASE LOCKED STEREO DECODER

*Revolutionary inductorless design no coils to adjust!
Set up with D.C. voltmeter only.*

Typical separation 45dB at 1kHz, 40dB at 10kHz. Complete kit (As in Wireless World Sept. 70) containing Fibreglass PCB (Approx. 4" x 5"), 62 low noise resistors, 3 Fairchild IC's, 15 Ferranti transistors, 8 diodes, 23 capacitors and 4 preset pots. Full instructions plus details of single and dual supply operation. £8.19.6 pp 2/6

Decoder PCB only £1.5.0 U6A747459X £1.7.6
U6E7709393 £1.0.0


STABILISED POWER SUPPLY

Complete kit for ± 6V at 50mA suitable for above £2.19.0 pp 3/6
Transistors: ZTX500 4/- ZTX108 equiv. 2/-

INTEGREX LIMITED PO BOX 45 DERBY DE1 1TW

NEW! HANDY! TIDY! multi-drawer I-N-T-E-R-L-O-C-K-I-N-G storage units

A PLACE
FOR
EVERYTHING
IN ITS
PLACE!

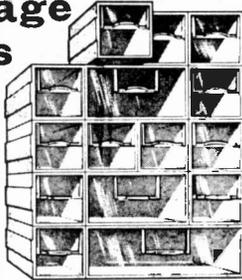

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/removable space dividers. Build up any size cabinet for wall, bench or table top.

BUY AT TRADE PRICES!

SINGLE UNITS (5ins 2 1/2ins 2 1/2ins)
Usually 2/11 each, **OUR PRICE: 27/- DOZEN**
DOUBLE UNITS (5ins 4 1/2ins 2 1/2ins)
Usually 4/11 each, **OUR PRICE: 45/- DOZEN**

PLUS QUANTITY DISCOUNTS!
Order £5 and over DEDUCT 1/- in the £
Orders £10 and over DEDUCT 1/6 in the £
Orders £20 and over DEDUCT 2/- in the £

PACKING, POSTAGE, CARRIAGE: Add 6/- to all orders under £5. Orders £5 and over, packing/postage/carrriage free.

QUOTATIONS FOR LARGER QUANTITIES ALL PRICES TAX PAID

IVORYET LIMITED (Dept. PE1) 31 ALBERT RD.
HENDON, LONDON, NW4

THE NEW JULIETTE MPR 3065

is a high quality COMMUNICATIONS RECEIVER

(replaces NA 5018A)
Recommended Price
£42 0.0

Our Price **36 Gns.**




(Cash only) plus 9/- p. & p. Complete with standard batteries and earpiece. BFO (optional extra) add 35/-.

IT NOT ONLY RECEIVES Aircraft, Shipping (VHF & SW), Taxis, Ambulances, Fire Service, T.V. Sound, Hams, Gas and Electric Boards, Public Services and many other radio telephone mobiles—BUT ALSO Classical Music, Pop and all that Jazz.

TURN ON AND TUNE IN!!! The MPR 3065 is a communications receiver and entertainment source in one neat, transistorised, portable package. It keeps aircraft, shipping, RT mobiles, FM and AM broadcasts at your fingertips. Features a colour coded illuminated tuning dial and band selector, AFC, squelch, BFO (optional extra), large speaker. Ext. Aerial Socket. Works off mains or batteries. Size: 10 1/2 x 7 1/4 inches. 22 Transistors/Diodes. **FREQUENCIES:** Medium Wave, 540-1600 Kcs.; Marine, 1.6-4.6 Mcs.; FM/VHF, 88-108 Mcs.; Aircraft, 108-136 Mcs. (Military, Civil and Ground control); High VHF/PB, 146-176 Mcs. (Commercial and Industrial RT mobiles). Availability of mobile transmissions depend on operators in each area.

Enclose 5d. stamp for reply. Trade supplied
STOCKTON PARTNERS (Dept. P.E.)
Importers and Distributors
Brighowgate, Grimsby, Lincs.
Tel. 0472 64196/58815

DIMMASWITCH

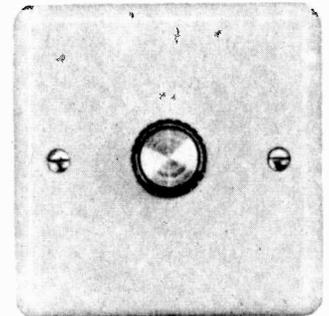

This is an attractive dimmer unit which fits in place of the normal modern light switch. The ivory mounting plate matches modern fittings and the control knob is in bright chrome. An ON/OFF switch is incorporated to control 40-600 watts of all lights except fluorescents at mains voltages from 200-250V, 50 Hz. Competitive products sell at £4 19s 6d—our price is £3 4s. We also offer at £2 14s a complete kit of parts with instructions enabling you to build this dimmer yourself.

The circuit uses a miniature RCA triac and a diac triggering device to give complete reliability. Radio interference suppression is included.

Post and Packing 1/6d extra.
Please send Cash with Order to:


DEXTER & COMPANY
ULVER HOUSE, 19 KING STREET
CHESTER CHI 2AH
Tel.: Chester 25883

As supplied to H.M. Govt. Departments, Hospitals, Local Authorities, etc.


Many New Models! in the FREE HEATHKIT 1971 Catalogue . . .



CONSUMER

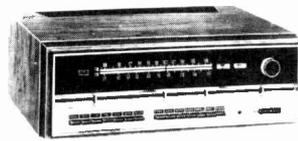

HI-FI & AUDIO

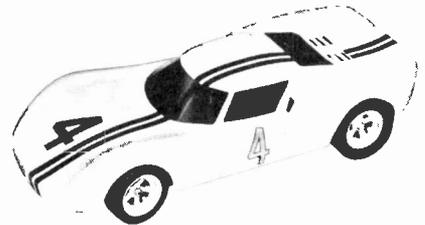

MODEL R/C CARS

Here's the bumper Heathkit catalogue for you. Read about the wonder and fascination of kit building . . . see in full colour the world's best values in Hi-Fi Radio, and even model radio control. Get up to date with what's new in scientific instrumentation . . . instruments for test and service . . . in fact there is a Heathkit for almost every purpose, in every walk of life. A wealth of information is all yours for the price of a postage stamp, in the Free Heathkit Catalogue.

- ★ No previous knowledge of electronics required.
- ★ The constructional manual supplied with every kit shows you how.
- ★ Building Heathkit models is so economic.
- ★ Save up to 50% over factory built equipment.
- ★ Money saving direct from factory prices.
- ★ They make excellent gifts.



MARINE



'TRENT' SPEAKER



A Schlumberger Company

HEATH (Gloucester) LTD., GLOUCESTER GL2 6EE

Many other models in wide range

(BLOCK CAPITALS PLEASE)

**FILL IN THE COUPON FOR YOUR
FREE CATALOGUE TODAY**

Name

Address


Post Code

R+TV

RADIO & TV COMPONENTS (Acton) Ltd.
 21d High Street, Acton, London W3 6NG
 Also at 323 Edgware Road, London, W.2
ALL ORDERS BY POST TO OUR ACTON BRANCH
 Terms C.W.O. All enquiries S.A.E.

Complete Stereo System £41

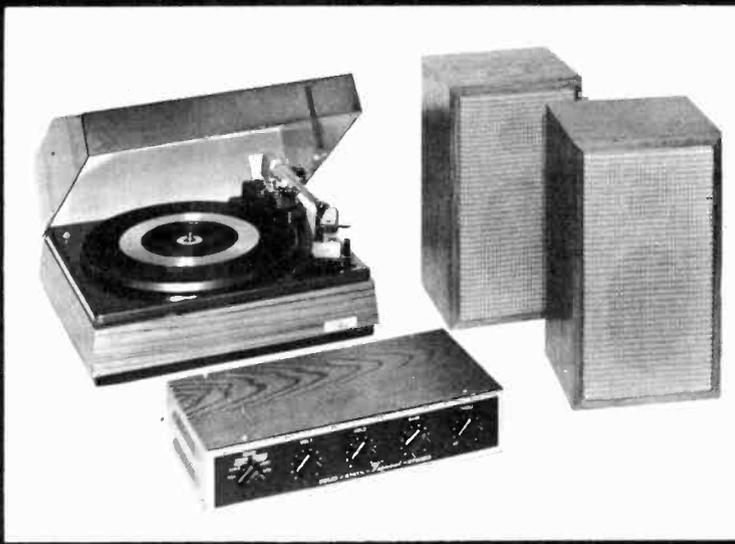WITH VISCOUNT F.E.T. FIELD EFFECT TRANSISTORS AMPLIFIER



This superb stereo system is a real price breakthrough. It comprises the VISCOUNT F.E.T. Mk. I amplifier on which full details are given below, the famous Garrard SP25 (including teak veneer base and transparent cover) with diamond cartridge or 2025 TC and the very successful DUO type 2 speakers.

Measuring 17½in x 10½in x 6½in, the Duo type 2 speakers are beautifully finished in teak veneer. They incorporate a 10½in x 6½in drive unit and high frequency speaker, both of which are of 3 ohms impedance. The Duo speaker system is also available separately at

£66.0 each plus 15/- P. & P.

Complete stereo system **£41** plus £2.10.0 P. & P.

With Mk. II Amplifier and Magnetic Cartridge **£45** plus £2.10.0 P. & P.



The Classic

Simulated teak case

£9.10

Plus P. & P. 10/-

SPECIFICATION: Sensitivities for 10 watt output at 1KHz into 3 ohms. Tape Head: 3mV (at 32 i.p.s.) Mag. P.U.: 2 mV. Cer.P.U.: 80mV. Tuner: 100mV. Aux. 100mV. Tape/Rec. Output. Equalisation for each input is correct to within +2dB (R.I.A.A.) from 20Hz to 20KHz. Tone Control Range: Bass: 12dB at 60Hz. Treble: ±14dB at 15KHz. Total Distortion: (for 10 watt output) < 1.5%. Signal Noise: < -60dB. A.C. Mains 200-250V. Size 12½in long, 4½in deep, 2½in high. Built and tested.

THE RELIANT Mk. II

SOLID STATE GENERAL PURPOSE AMPLIFIER

£75.0 Plus P. & P. 7/6

Simulated teak case



SPECIFICATION: Output: 10 watts into a 3 ohms speaker. Inputs: (1) for mike (10mV). Input (2) for gram. radio (250mV) individual bass and treble control.

Transistors: 4 silicon and three germanium. Mains input: 220/250 volts. Size: 10½ x 4½ x 2½in.

ELEGANT SEVEN Mk. III (350mW Output)

7-transistor fully tunable M.W.-L.W. Superhet portable. Set of parts. Complete with all components including ready etched and drilled printed circuit board—back printed for foolproof construction. **MAINS POWER PACK KIT: 9/6 extra.**

£5.5.0 Plus P. & P. 7/6. Circuit 2/6. Free with parts.



THE DORSET (600mW Output)

7-transistor fully tunable M.W.-L.W. Superhet portable with baby alarm facility. Set of parts. The latest modulated and pre-alignment techniques makes this simple to build. Sizes: 12 x 8 x 3in. **MAINS POWER PACK KIT: 9/6 extra.**

£5.5.0 Plus P. & P. 7/6. Circuit 2/6. Free with parts.



The Viscount F.E.T. Mk. I £14.5.0

Plus 10/- P. & P.

High fidelity transistor stereo amplifier employing field effect transistors. With this feature and accompanying guaranteed specifications below, the Viscount F.E.T. vastly surpasses amplifiers costing far more.

SPECIFICATION

Output per channel—10W rms. Frequency bandwidth 20Hz to 20kHz ±1dB @ 1W.

Total distortion @ 1kHz @ 9W 0.5%. Input sensitivities—CER. P.U. 100mV into 3 MΩ; Tuner 100mV into 100KΩ; Tape 100mV into 100kΩ.

Overload Factor—Better than 26dB. Signal to noise ratio—70dB on all inputs (with vol. max).

Mk. II (MAG. P.U.) £15.15.0

Specification same as Mk. I, but with the following inputs: Mag. P.U. CER. P.U. Tuner.

Controls—6 position selector switch (3 pos. stereo and 3 pos. mono), separate vol. controls for left and right channels. Bass ±14dB @ 60Hz; Treble (with D.P.S. on/off) ±12dB @ 10kHz.

Tape recording output sockets on each channel. Size 12½in x 6in x 2½in in simulated teak case. Built and tested.

Post & packing 10/- extra.

Spec. on Mag. P.U. 3mV @ 1kHz input impedance 47kΩ. Fully equalised to within ±1dB RIAA. Signal to noise ratio—65dB (vol. max.).


LIQUIDATED STOCK

DANSETTE

TOURISTE MK3

CAR RADIO

ALL TRANSISTOR

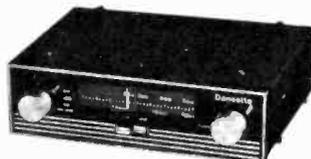

Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1 MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7" x 2" x 4½" deep.

Originally sold completely built for £15.4.6

Circuit diagram 2/6, free with parts

Speaker, baffle and fixing kit

25/- extra plus 4/- P. & P.

Speaker postage free when ordered with parts

SET OF PARTS

£6.6.0

plus 7/6 P. & P.

SOUND 50


SOUND 50 AMPLIFIER AND SPEAKER SYSTEM

The Sound Fifty valve amplifier and speakers are sturdily constructed with smart housings and thoroughly tested electronics. They are designed to last—to withstand the knocks and bumps of life on the road. Built for the small and medium sized gig, they are easy to handle and quick to set up and can be relied upon to come over with all the quality and power you need.

Output Power 45 watts R.M.S. (Sine wave drive). **Frequency response**—3db points 30 Hz at 18 KHz. **Total distortion** less than 2% at rated output. **Signal to noise ratio**: better than 60db. **Speaker Impedance** 3, 8 or 15 ohms. **Bass Control Range**—13db at 60 Hz. **Treble Control Range**—12db at 10 KHz. **Inputs** 4 inputs at 5 mV into 470 K. Each pair of inputs controlled by separate volume control. 2 inputs at 200 mV into 470 K.

To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power.

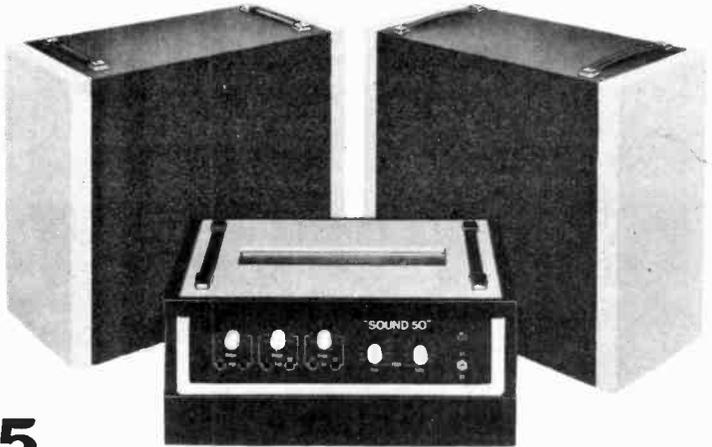SPEAKERS! Size 20" 20" 10" incorporating Baker's 12" heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two tone colour scheme—Black and grey.



COMPLETE SYSTEM £45

plus 80/- P. & P.

Amplifier £28.10.0 plus 20/- P. & P. Speakers each £12.10.0 plus 30/- P. & P.

RADIO & TV COMPONENTS (ACTON) LTD.

Post orders to:—21d High Street, Acton, London W3 6NG

Also at 323 Edgware Road, London, W.2

Goods not despatched outside U.K.

Terms C.W.O.

All Enquiries S.A.E.



YOURS FREE FOR 7 DAYS

The 'New Picture-Book' way of learning **BASIC ELECTRICITY (5 VOLS.)** **BASIC ELECTRONICS (6 VOLS.)**



You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

... carefully written ...

... I am very satisfied with these carefully written and well expressed manuals ... *A.W., Shanklin.*

... valuable assistance ...

... Your valuable assistance has enabled me to find a good position as a Radio and TV Engineer ... *D.S., Bristol.*

... they are invaluable ...

... I find that as a base for a course in Electronics they are invaluable and I have yet to find anything even to approach the same standard ... *H.N., Rotherham.*

A TECH-PRESS PUBLICATION

POST NOW FOR THIS OFFER!!

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. **BASIC ELECTRICITY 75/-**. Cash Price or Down Payment of 20/- followed by 3 fortnightly payments of 20/- each. **BASIC ELECTRONICS 90/-**. Cash Price or Down Payment of 20/- followed by 4 fortnightly payments of 20/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY

BASIC ELECTRONICS

Prices include Postage and Packing.

Signature

(If under 18 signature required of parent or guardian)

NAME
BLOCK LETTERS

FULL POSTAL
ADDRESS

PRACTICAL ELECTRONICS

Specify

CONTIL
MOD-2

CASES



PRACTICAL ELECTRONICS specify **CONTIL MOD. 2 CASES** for housing the **P.E. GEMINI AMPLIFIER** and the **P.E. AURORA LIGHT DISPLAY SYSTEM**, both of which were recently exhibited at the "International Audio & Music Fair 1970". In addition cases from this range are specified for housing the **P.E. DIGITAL CLOCK** also the **SINCLAIR PROJECT 60 SYSTEM** and **ACTIVE FILTER UNIT**.


IDEAL FOR DEVELOPMENT—CHEAPER FOR PRODUCTION

PVC COATED MATERIALS. No outside paint to be scratched. PVC easy to clean, surface is scuff resistant. PVC/ALUMINIUM FOR FRONT & BACK PANELS gives easy cutting with rigidity PVC/STEEL FOR SIDES, TOP & BOTTOM gives rigidity, low cost, ease of assembly, 3 HEIGHTS OF CASE, 4 WIDTHS, 2 DEPTHS, make 24 cases with screws on top and 24 cases with screws on side, that's 48 different cases. **LOW COST.** Prices include chassis. **MODERN DESIGN.** Metal work on front and back and chassis is made easier by aluminium with PVC cladding. PVC/steel on sides and bottom for strength. **GOOD DELIVERY.** Off the shelf range of all PVC coated cases.

The **Mod-2 type G** is also available with a very good simulated wood grain, which we think looks like teak, and it also has the PVC aluminium: grey front and back panels.

The **type G** case in either wood grain and grey or blue and grey is available either punched or unpunched, and is approved for the **SINCLAIR PROJECT 60**, with or without the active filter.

NOTE THE LOW COST

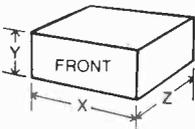

We also have available for Sinclair sets of DIN sockets, fuses, etc., to fit these particular specified parts.

★ SEE OUR STANDARD PRICE LIST FOR QUANTITY PRICES AND ALL OUR OTHER PRODUCTS

	X	Y	Z	I off	P. & P
A	4.5	3	6.5	34/-	3/-
B	4.5	7	6.5	40/-	4/6
C	4.5	10	6.5	50/-	4/6
D	9	3	6.5	50/-	4/6
E	9	7	6.5	55/-	4/6
F	9	10	6.5	65/-	4/6
G	13	3	6.5	55/-	4/6
H	13	7	6.5	65/-	4/6
I	13	10	6.5	73/-	6/-
J	18	3	6.5	65/-	4/6
K	18	7	6.5	89/-	6/-
L	18	10	6.5	107/-	6/-
M	4.5	3	13	40/-	4/6
N	4.5	7	13	55/-	4/6
O	4.5	10	13	73/-	6/-
P	9	3	13	55/-	4/6
Q	9	7	13	73/-	6/-
R	9	10	13	89/-	6/-
S	13	3	13	73/-	6/-
T	13	7	13	89/-	6/-
U	13	10	13	109/-	7/6
V	18	3	13	89/-	6/-
W	18	7	13	107/-	7/6
X	18	10	13	138/-	7/6
G			Woodgrain Sizes in inches	68/-	4/6

WH WEST HYDE

WEST HYDE DEVELOPMENTS LIMITED

Ryefield Crescent, Northwood Hills, Northwood Middlesex, HA6 1NN
Telephone: Northwood 24941/26732

YATES ELECTRONICS

(FLITWICK) LTD.

RESISTORS

High stability carbon film. Very low noise. 0.5W 5%, 4.7Ω to 2.2MΩ 2.5d each, 100+ 2d each, 0.5W 10%, 4.7Ω to 10MΩ 2d each, 100+ 1.75d each. Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% resistors 5 off each value 4.7Ω to 1MΩ
325 resistors E12 series 50/-
650 resistors E24 series 100/-

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 6d.
0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 7d. 0.047μF, 9d.
0.068μF, 0.1μF, 10d.
160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 7d.
0.1μF, 9d. 0.15μF, 0.22μF, 10d. 0.33μF, 1/3. 0.47μF, 1/6.
0.68μF, 2/3. 1.0μF, 2/6.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V: P.C. mounting miniature 20%: 0.01μF, 0.015μF, 0.022μF, 7d. 0.033μF, 0.047μF, 0.068μF, 8d. 0.1μF, 9d. 0.15μF, 0.22μF, 1/- 0.33μF, 1/4.

MYLAR FILM CAPACITORS

100V: 0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF, 6d. 0.05μF, 0.1μF, 8d.

CAPACITOR DEVELOPMENT PACK

Selection of ceramic and polyester capacitors 100pF to 1.0μF. Total 100 capacitors, £2.18.0.

MINIATURE ELECTROLYTIC CAPACITORS

50μF	6V	16μF	10V	10μF	12V	40μF	16V	16μF	40V
100μF	6V	64μF	10V	16μF	12V	6.4μF	25V	50μF	40V
200μF	6V	125μF	10V	50μF	12V	25μF	25V	2.5μF	64V
320μF	6V	200μF	10V	100μF	12V	8μF	40V	10μF	64V

1/- each

250μF 12V, 100μF 40V 1/6. 1000μF 25 volt 6/- 2500μF 25V 9/- 500μF 50 volts 5/- 1000μF 50 volt 8/-

CERAMIC DISC CAPACITORS

100pF, 150pF, 220pF, 270pF, 330pF, 470pF, 560pF, 680pF, 1000pF, 2000pF, 5000pF, 10,000pF, 5d each.

POTENTIOMETERS

5kΩ to 1MΩ log or linear, 2/6.

GANGED STEREO POTENTIOMETERS

½ watt carbon track 5kΩ + 5kΩ to 1MΩ + 1MΩ log or linear 8/- each.

SKELETON PRE-SET POTENTIOMETERS

Linear: 100, 250, 500 ohms and decades to 5M ohm ± 20% ≤ 250kΩ, ± 30%, - 250kΩ. Horizontal or vertical P.C. mounting (0-1 matrix). Sub-miniature 0.1 watt 10d each. Miniature 0.3 watt 1/- each.

TRANSISTORS

AC126 3/-	BC108 2/-	2N2926 2/3	2N3707 3/8
AC127 3/-	BC109 2/9	2N3055 14/6	2N3708 2/-
AC128 3/-	BFY50 4/6	2N3702 3/-	2N3709 2/3
AD140 8/-	BFY51 3/9	2N3703 2/10	2N3710 2/5
AF115 3/6	BFY52 4/6	2N3704 3/6	2N3711 2/10
AF117 3/6	BSY56 6/-	2N3705 3/-	ORP12 9/6
BC107 2/9	BSX21 5/-	2N3706 2/5	ZTX302 4/6

DIODES—OA85, OA91, OA202, 1/6 each

ZENER DIODE

400mW 5% 3.3V to 30V 3/6

SILICON RECTIFIERS

IN4001 50V IA 1/6	IN4006 800V IA 3/-
IN4002 100V IA 2/-	IN4007 1000V IA 3/3
IN4003 200V IA 2/3	BY124 100V ½A 1/6
IN4004 400V IA 2/6	BYZ10 800V 6A 7/-
IN4005 600V IA 2/9	BZ13 200V 6A 4/-

VEROBOARD

0.15	0.1	0.15	0.1
2½ × 3½	3/3	17 × 3½ (plain)	10/6
2½ × 5	4/9	17 × 2½ (plain)	7/6
3½ × 3½	4/9	2½ × 5 (plain)	3/6
3½ × 5	5/6	2½ × 3½ (plain)	3/-
17 × 3½	15/-	Pin insertion tool	9/6 9/6
17 × 2½	11/6	Spot face cutter	7/6 7/6
17 × 5 (plain)	15/-	Pkt. 36 pins	3/- 3/-

ROTARY SWITCHES

1P12W, 2P6W, 3P4W, 4P3W, 4/6.

JACK PLUGS AND SOCKETS

Standard Screened 3/6	2.5mm Insulated 1/6
Standard Insulated 2/9	3.5mm Insulated 1/6
Stereo Screened 7/-	3.5mm Screened 2/6
Standard Sockets 3/-	2.5mm Socket 1/6
Stereo Sockets 3/6	3.5mm Socket 1/6

BRUSHED ALUMINIUM PANELS

Self adhesive backing approx. 13 × 2½ 2/-

C.W.O. please. 1/6 post and packing on orders under £1.

Export Enquiries welcome

8E39 ELSTOW STORAGE DEPOT, KEMPSTON HARDWICK, BEDFORD



LIND-AIR AUDIO



E.M.I. LOUDSPEAKERS

MODEL 450. 13 1/2 in. 8 in. elliptical with twin tweeters. 8 ohm impedance. 10W. Brand new, guaranteed. Lind-Air Price 79/6. P. & P. 4/6.

MODEL 150. 13 1/2 in. 8 in. elliptical. 3 and 15 ohm impedance. 10W. Lind-Air Price 59/6. P. & P. 4/6.

TEAK FINISH SPEAKER CABINETS.
Size 16in x 16in x 9in. Ideal for above units. 49/6.

HI-TONE RECORDING TAPE

BRITISH MADE TOP QUALITY

J1001	3in	L.P.	PVC	235ft	5/6 P. & P. 1/2
J1002	3in	T.P.	Poly	600ft	10/6 P. & P. 1/2
J1003	5in	L.P.	PVC	900ft	10/- P. & P. 1/8
J1004	5in	D.P.	Poly	1,200ft	15/- P. & P. 1/8
J1005	5 1/2 in	L.P.	PVC	1,200ft	12/6 P. & P. 2/-
J1006	5 1/2 in	D.P.	Poly	1,800ft	22/6 P. & P. 2/-
J1007	7in	S.P.	PVC	1,200ft	12/6 P. & P. 2/6
J1008	7in	L.P.	PVC	1,800ft	17/6 P. & P. 2/6
J1009	7in	D.P.	Poly	2,400ft	25/- P. & P. 2/6
J1010	7in	T.P.	Poly	3,600ft	50/- P. & P. 2/6
C80	Cassette	(Library cased)			8/6 P. & P. 1/-
C90	Cassette	(Library cased)			13/- P. & P. 1/-
CT20	Cassette	(Library cased)			18/- P. & P. 1/-



DE-LUXE STEREO HEADPHONES

With soft rubber earpieces. Impedance 8-16ohms. Frequency response 23-13,000Hz. With lead and stereo plug. Only 59/6. P. & P. 3/6.

SOLDERING GUN



Comfortable Grip with trigger control. "U" shaped 3 1/2 in. bit to minimise wear. Light beam is automatically directed on end of bit when ON/OFF trigger is in use. 230-250 volts. 85 watt element. 49/6. P. & P. 3/6.

C1001 MULTI-TESTER



Overload protection 20,000 ohms per volt; a.c. volts 10, 50, 250, 1,000V; d.c. volts 5-25, 125, 500, 2,500V; d.c. current 0-50uA, 0-250mA; Resistance 0-60kΩ 0-6MΩ; decibels -20 to +22dB. Size of meter 4 1/2 in x 3 1/2 in x 1 in. Complete with leather case. 85/-, P. & P. 3/6.


FIRST TIME EVER! SOLID STATE RADIO HEADPHONES



* STEREO EFFECT RADIO
* POWERFUL TRANSISTOR RADIO BUILT INTO HEADPHONE WITH TUNING AND VOLUME CONTROLS
* TWIN TELESCOPIC AERIAL RODS
* TWIN MAGNETIC SPEAKERS—ONE IN EACH EARPIECE

Listen to all your favourite radio programmes anywhere and anytime. Lightweight and comfortable to wear. Covers full medium waveband, super-sensitive tuning control and variable volume control. Ideal for out and in/out. Only £10.18.6. P. & P. 4/6.

S-DEC BREADBOARD

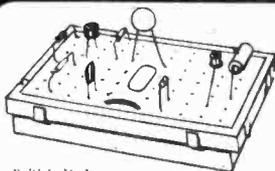

British Made
Solderless breadboard panels, for fast reliable component connections. Single DeCs. One 8-DeC with Control Panel, Jig and Accessories for solderless connections to controls, etc., with booklet "Projects on S-Dec" giving construction details for a variety of circuits. 29/6. P. & P. 2/6.
4-DeC KIT. Four S-DeCs with two Control Panels, Jigs and Accessories and the booklet "Projects on S-Dec" all contained in a strong attractive plastic case. Ideal for the professional user. £5.17.6. P. & P. 3/6.
T-DeC KIT £2.10.0. P. & P. 3/6.

62D MULTI-TESTER

20,000 ohms per volt; d.c. voltage 5, 25, 50, 250, 500V, 2.5kV (20,000 ohms per volt), a.c. voltage 10, 50, 100, 500, 1,000V (10,000 ohms per volt); d.c. current 0-50uA, 0-2.5mA, 0-250mA; resistance 0-6kΩ, 0-6MΩ (300 ohms and 30kΩ at centre scale); capacitance 10F to 0.001mF, 0.001uF to 0.1uF; decibels -20 to +22dB. Size 4 1/2 in x 3 1/2 in x 1 in. 71/-, P. & P. 3/6.



600 WATT LIGHT DIMMER SWITCH

Same size as standard wall switch and will dim incandescent lighting from full on to off. Heavy plastic box with knob. Lind-Air Price £4.10.0. P. & P. 3/6.



UNILEX Audio Modules

A good quality stereo amplifier can be built with no electrical knowledge.
All solid state—Baxendall tone control circuit—no soldering—terminal block connections throughout.
Everything you need to know about UNILEX SYSTEMS is in the Mullard book "Do it yourself stereo". Superb designs, detailed plans, simple instructions in non-technical language covering 4 systems in 4 price ranges.
Send for your copy now 5/- Post Free.

UNILEX Audio Modules

- Amplifier Module EP9000 £2.18.0 each
- Pre Amplifier Module EP9001 £3.2.0 ..
- Power Supply Module EP9002 £4.12.0 ..
- Control Panel Assembly and Escutcheon Plate £3.5.0

BUILD A STEREO AMPLIFIER FOR ONLY £16.15.0 P. & P. 7/6

UNILEX PACKAGE DEALS


Unilex Modules	£16.15.0	Unilex Modules	£16.15.0
Garrard 2025	£11.14.1	Garrard SP25 Mk II	£15.11.4
Celestion Speakers	£5.17.0	B.S.R. CI Cartridge	£3.17.3
	£34.6.1	Celestion Speakers	£5.17.0

LIND-AIR 28 GNS. PRICE P. & P. 20/-

LIND-AIR 35 1/2 GNS. PRICE P. & P. 20/-

NOW OPEN AT:
94-96 UPPER PARLIAMENT STREET
NOTTINGHAM Tel. 40403 (STD 0602)

SINCLAIR PROJECT 60

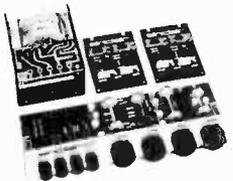

An attractive alternative for the enthusiast prepared to assemble these excellent modules to make a stereo assembly. Z.30 24W Power Amplifier 89/6 (2 required). Stereo Sixty Control/Pre-amplifier £29.19.6. PZ.5 Power Supply Unit £4.19.8. SINCLAIR PROJECT 60 Package deal price 19 Gns. P. & P. 12/6.
Project 60 is supplied complete with instruction manual and templates for plinth mounting.

SINCLAIR IC-10 INTEGRATED CIRCUIT 10W Amplifier. Size only 1in x 0.4in x 0.2in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. Guaranteed 5 years.
ONLY 59/6. P. & P. 1/6.
SPECIAL TRANSFORMER FOR OPERATING SINCLAIR IC-10 from a.c. mains 230/250V. Output 13V at 0.5A. 18/6. P. & P. 2/6.

Garrard HI-FI TURNTABLES



2025 T/C with stereo cartridge ..	£8.19.6
3000 with Sonotone 9TAHCD stereo cartridge	£10.19.6
SP25 Mk. II	£10.19.6
SL65B	£15.19.6
Base and cover for above	£5.19.6
AP75	£18.10.0
SL72P	£24.19.6
SL73B	£28.7.0
SL93B	£39.9.0
401	£28.10.0
Base and cover for above	£28.19.6
P. & P. Decks, 12/6; Base and Cover, 10/-; Deck/Base/Cover, 17/6.	

SPECIAL OFFERS!
SP25 Mk. II with base £14.10.0 || P. & P. 15/- | |
SP25 Mk. II with Sonotone 9TAHCD cartridge and base	£15.15.0
..... P. & P. 15/-	
Sonotone 9TAHCD cartridge	£2.15.0
..... P. & P. 1/6	



18/19,25 & 53 TOTTENHAM CT. ROAD, LONDON W.1

Telephone: 01-580 2255/4532/7679

Open 9-6 pm. Monday to Saturday. Thursday until 7 pm.

All Mail Orders and correspondence to Dept. L4/13, Kirkman House, 54a Tottenham Court Road, London, W.1. Tel: 01-580 7041/2.

Project 60

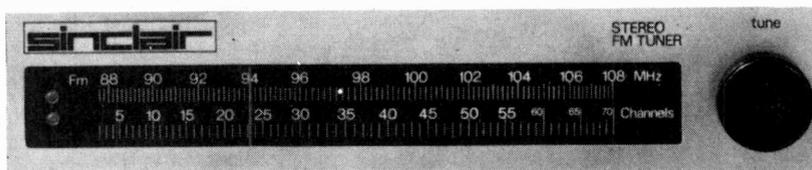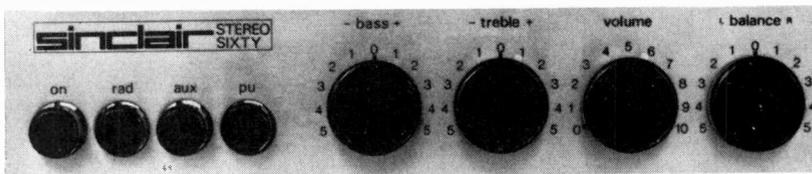

the world's most advanced high fidelity modules

With the introduction of an entirely new and original high fidelity stereo F.M. tuner, the Project 60 range can be said at this stage to be complete. It offers the constructor a most attractive choice of modular arrangements whereby a high fidelity system can be selected to suit the user's personal requirements. Equally, it is possible to use any Project 60 modules separately or partially grouped and so benefit greatly from the flexibility in use these modules afford. The chart below shows some of the most popular applications for constructors to assemble. The Project 60 manual (free with the modules) suggests others as well and its 48 pages are packed with valuable information. The new tuner, for example can be used with any good high fidelity system as well as Project 60.

Project 60 now falls into four interdependent groups: - 1. The Z.30 and Z.50 amplifiers which have only 0.02% distortion at all output levels and are useful in a wide variety of other applications. 2. The control units comprising the Stereo 60 preamp and control unit and the Active Filter Unit (A.F.U.) with which both high pass and low pass filtering can be introduced between control unit and power amplifiers. 3. The Stereo F.M. tuner as described opposite; and 4. The power supply units PZ.5,

PZ.6 and PZ.8. For most requirements when using Z.30 power amplifiers, the PZ.5 will be perfectly adequate; if low efficiency (high quality) loud speakers are used, the PZ.6 stabilised power supply unit will be used. The PZ.8 will be needed with Z.50s which can be used for any Project 60 system.

Project 60 modules incorporate some of the most advanced circuitry in the world to achieve unsurpassed standards of high fidelity and modern manufacturing techniques enable these modules to be sold at exceptionally attractive prices. Assembling the modules requires no skill or previous experience since the manual supplied with the modules explains clearly how everything can be done with nothing more than the simplest of domestic tools.

Project 60 manuals

How to assemble and use Project 60 modules to best advantage in the above and other applications will be found in the fully descriptive Project 60 manual included with Project 60 systems. This 48 page manual is available separately, price 2/6d including postage.

System	The Units to use	In conjunction with	Cost of Units	+ Project 60 tuner
A Car Radio	Z.30	Existing car radio, Sinclair Micromatic	89/6	
B Simple battery powered record player	Z.30	Crystal pick-up, 12V or more battery supply and volume control	89/6	
C Mains powered record player	Z.30 and PZ.5	Crystal or ceramic P.U. Volume control etc.	£9.9.0	£34.9.0
D 20+20 watts R.M.S. stereo amplifier for most needs	Two Z.30s, Stereo 60 and PZ.5	Crystal, ceramic or magnetic P.U., most dynamic speakers, F.M. tuner etc.	£23.18.0	£48.18.0
E 20+20 watts R.M.S. stereo amplifier for use with low efficiency (high performance) speakers	Two Z.30s, Stereo 60 and PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc All dynamic speakers	£26.18.0	£51.18.9
F 40+40 watts R.M.S. de-luxe stereo amplifier	Two Z.50s, Stereo 60 PZ.8 and mains transformer	As for E	£32.17.6	£57.17.6
G Outdoor public address system	Z.50	Microphone, up to 4 P.A. speakers, 12V car battery with converter, or 45V d.c., controls	£5.9.6	
H Indoor P.A.	One Z.50, PZ.8 and mains transformer	Microphone, guitar, heavy duty speakers etc., controls	£17.8.6.	
J High pass and low pass filters	A.F.U.	D, E or F as above	£5.19.6	

sinclair

Sinclair Radionics Limited, 22 Newmarket Road, Cambridge

Telephone (0223) 52731

Z.30 & Z.50 power amplifiers

The Z.30 together with the Z.50 are both of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use the Z.30 or Z.50 power amplifiers in your Project 60 system will depend on personal preference, but they are the same physical size and may be used with other units in the Project 60 range equally well. For operating from mains, for the Z.30 use PZ.5 for most domestic requirements, or PZ.6 if you have very low efficiency loudspeakers. For Z.50, use the PZ 8 described below.

SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).

Power Outputs

Z.30 15 watts R.M.S. into 8 ohms, using 35V; 20 watts R.M.S. into 3 ohms using 30 volts.

Z.50 40 watts R.M.S. into 3 ohms from 40 volts; 30 watts R.M.S. into 8 ohms, using 50 volts.

Frequency response 30 to 300,000 Hz \pm 1dB

Distortion 0.02% into 8 ohms

Signal to noise ratio better than 70dB unweighted

Input sensitivity 250mV into 100 Kohms.

For speakers from 3 to 15 ohms impedance.

Size 3½ x 2½ x ½ ins.



Z.30
Built, tested and guaranteed with circuits and instructions manual
89/6

Z.50
Built, tested and guaranteed with circuits and instructions manual
109/6

Stereo 60 pre amp/control unit

Designed for the Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.

SPECIFICATIONS


● Input sensitivities - Radio - up to 3mV. Mag. p.u. - 3mV; correct to R.I.A.A. curve \pm 1dB; 20 to 25,000Hz. Ceramic p.u. - up to 3mV; Aux. - up to 3mV.

● Output - 250mV.

● Signal-to-noise ratio - better than 70dB.

● Channel matching - within 1dB.

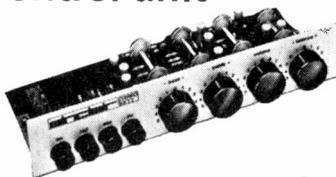● Tone controls - TREBLE +15 to -15dB at 10kHz; BASS +15 to -15dB at 100Hz.




● Front panel - brushed aluminium with black knobs and controls.
● Size 8½ x 1½ x 4 ins.

Built, tested and guaranteed **£9.19.6**

Active Filter Unit

For use between Stereo 60 unit and two Z.30s or Z.50s, the Active Filter Unit matches the Stereo 60 in styling and is as easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The Sinclair A.F.U. is suitable also for use with any other amplifier system.

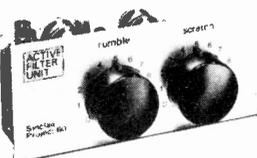Two stages of filtering are incorporated - rumble (high pass) and scratch (low pass). Supply voltage - 15 to 35V. Current - 3mA. H.F. cut-off (-3dB)



variable from 28kHz to 5kHz. L.F. cut-off (-3dB) variable from 25Hz to 100Hz. Filter slope, both sections 12dB per octave. Distortion at 1kHz (35V supply) 0.02% at rated output.

Built, tested and guaranteed **£5.19.6**

Power Supply Units

The units below are designed specially for use with the Project 60 system of your choice.

Illustration shows PZ.5 power supply unit to left and PZ.8 (for use with Z.50s) to the right. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.


PZ-5 30 volts unstabilised £4.19.6

PZ-6 35 volts stabilised £7.19.6

PZ-8 45 volts stabilised

(less mains transformers) £5.19.6

PZ-8 mains transformer £5.19.6

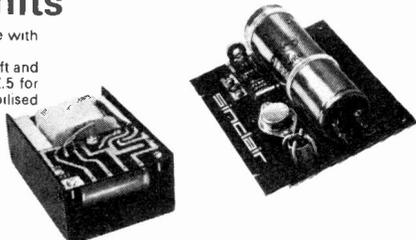

Stereo FM tuner



first in the world to use the phase lock loop principle

Before production of this tuner, the phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio over other systems. Now, for the first time the principle has been applied to an FM tuner with fantastically good results. By the inclusion of other original features such as varicap diode tuning, printed circuit coils and an I.C. in the specially designed stereo decoder, the tuner has an unsurpassed specification, which also incorporates a squelch circuit for silent tuning between stations, A.F.C. and A.G.C. Sensitivity is such that good reception becomes possible in difficult areas, foreign stations can be tuned in suitable conditions and often a few inches of wire are enough for an aerial. In terms of high fidelity, this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. Although the tuner is intended primarily for use with a Project 60 system, it can be used to advantage with any other high fidelity system. It is easily mounted into any cabinet as shown in the manual supplied with it.

Specifications

Number of transistors 16 plus 20 in I.C.

Tuning range 87.5 to 108 MHz

Capture ratio 1.5dB

Sensitivity 2µV for 30dB quieting
7µV for full limiting

Squelch level 20µV

A.F.C. range \pm 200 KHz

Signal to noise ratio > 65dB

Audio frequency response 10Hz-15kHz (\pm 1dB)

Total harmonic distortion 0.15% for 30% modulation

Stereo decoder operating level 2µV

Pilot tone suppression 30dB

Cross talk 40dB

I.F. frequency 10.7 MHz


Output voltage 2 x 150mV R.M.S.

Aerial Impedance 75 Ohms

Indicators Mains on; Stereo on; tuning indicator

Operating voltage 25-30VDC

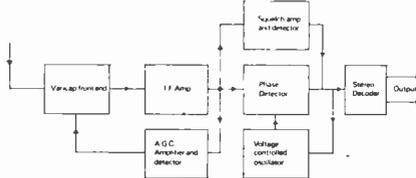Size 3.6 x 1.6 x 8.15 inches : 91.5 x 40 x 207 mm



Price: **£25** built and tested. Post free.

GUARANTEE If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail, Air-mail charged at cost.

sinclair

To: Sinclair Radionics Ltd., 22 Newmarket Road, Cambridge

Please send



.....

 for which I enclose cash/cheque money order

NAME
 ADDRESS

 PE/171.A

Sinclair IC-10

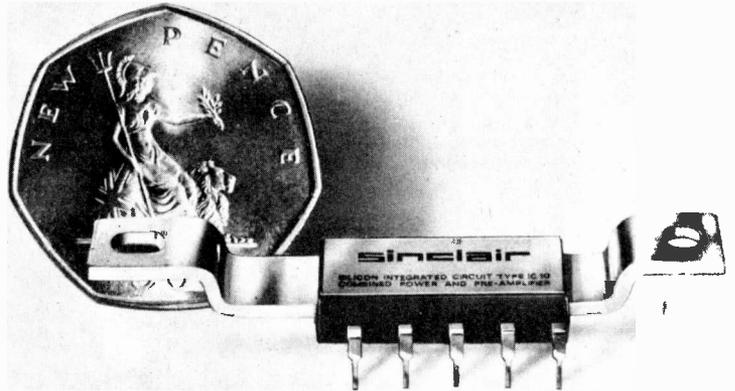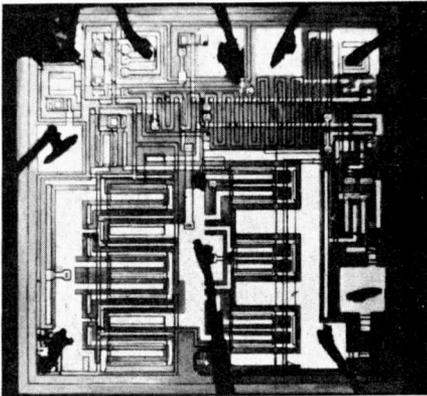

the world's most advanced high fidelity amplifier

Specifications

Output: 10 Watts peak, 5 Watts R.M.S. continuous
 Frequency response: 5 Hz to 100 KHz ± 1 dB
 Total harmonic distortion: Less than 1% at full output.
 Load impedance: 3 to 15 ohms.
 Power gain: 110dB (100,000,000,000 times) total.
 Supply voltage: 8 to 18 volts.
 Size: 1 x 0.4 x 0.2 inches.
 Sensitivity: 5mV.
 Input impedance: Adjustable externally up to 2.5 M ohms.

Circuit Description

The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. Class AB output is used with closely controlled quiescent current which is independent of temperature. Generous negative feedback is used round both sections and the amplifier is completely free from crossover distortion at all supply voltages, making battery operation eminently satisfactory.

Applications

Each IC-10 is sold with a very comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include stabilised power supplies, oscillators, etc. The pre-amp section can be used as an R.F. or I.F. amplifier without any additional transistors.

The Sinclair IC-10 is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself, a chip of silicon only a twentieth of an inch square by one hundredth of an inch thick, has 5 watts R.M.S. output (10w. peak). It contains 13 transistors (including two power types), 2 diodes, 1 zener diode and 18 resistors, formed simultaneously in the silicon by a series of diffusions. The chip is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins. This exciting device is not only more rugged and reliable than any previous amplifier, it also has considerable performance advantages. The most important are complete freedom from thermal runaway due to the close thermal coupling between the output transistors and the bias diodes and very low level of distortion.

The IC-10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of such components as tone and volume controls and a battery or mains power supply. However, it is so designed that it may be used simply in many other applications including car radios, electronic organs, servo amplifiers (it is d.c. coupled throughout), etc. Once proven, the circuits can be produced with complete uniformity which enables us to give a full guarantee on every IC-10, knowing that every unit will work as perfectly as the original and do so for a lifetime.

SINCLAIR

IC-10 with IC-10 manual 59/6
 Post free.

To: Sinclair Radionics Ltd., 22 Newmarket Road, Cambridge

Please send

NAME

ADDRESS

for which I enclose cash/cheque money order

PE/171.B

sinclair


Q.16 High fidelity loudspeaker

Developed out of the revolutionary and much praised design of the original Sinclair Q.14 comes this more advanced version to meet the requirements of even greater numbers of high fidelity enthusiasts. The Q.16 employs the same well proven acoustic principles in which a special driver assembly is meticulously matched to the physical characteristics of the uniquely designed housing. In reviewing this exclusive Sinclair design, technical journals have been loud in their praise for it and it comfortably stands comparison with very much more expensive loudspeakers. The shape of the Q.16 enables it to be positioned and matched to its environment to much better effect than is the case with conventionally styled enclosures, and with its improved styling, the Q.16 presents an entirely new and attractive appearance. A solid teak surround is used with a special all-over cellular black foam front chosen as much for its appearance as for its ability to pass all audio frequencies unimpaired.

The Q.16 is compact and slim and is the ideal shelf-mounted speaker, and brings genuine high fidelity within reach of every music lover.

Specifications

Construction:	A sealed seamless sound or pressure chamber is used with internal baffle, all of materials carefully chosen to ensure freedom from spurious tone coloration.
Loading:	Up to 14 watts R.M.S.
Input impedance:	8 ohms.
Frequency response:	From 60 to 16,000Hz, as confirmed by independently plotted B & K curve.
Driver unit:	Specially designed high compliance unit having massive ceramic magnet of 11,000 gauss, aluminium speech coil and special cone suspension. Excellent transient response is achieved.
Size and styling:	9 $\frac{3}{4}$ " square on face \times 4 $\frac{3}{4}$ " deep with neat pedestal base. Black all-over cellular foam front with natural solid teak surround.
Price:	£8 19 6.

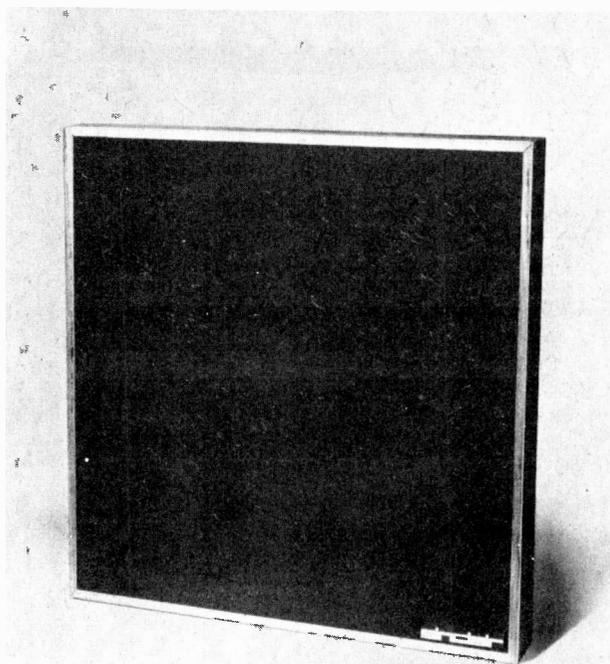

Micromatic Britain's smallest radio

Considerably smaller than an ordinary box of matches, this is a multi-stage A.M. receiver meticulously designed to provide remarkable standards of selectivity, power and quality. Powerful A.G.C. is incorporated to counteract fading from distant stations; bandspread at higher frequencies makes reception of Radio 1 easy at all times. Vernier type tuning plus the directional properties of the self-contained special ferrite rod aerial makes station separation very much easier than with many larger sets. The plug-in high fidelity type magnetic earpiece which matches exactly with the output of the Micromatic provides wonderful standards of reproduction both for speech and for music. Everything including the batteries is contained within the attractively designed case. Whether you build your Micromatic or buy it ready built and tested, you will find it as easy to take with you as your wristwatch, and dependable under the severest listening conditions.

Specifications

Size:	1 $\frac{1}{2}$ " \times 1 $\frac{7}{8}$ " \times $\frac{1}{2}$ " (46 \times 33 \times 13mm).
Weight including batteries:	1 oz. (28.35gm) approx.
Tuning:	Medium wave band with bandspread at higher frequency end.
Earpiece:	High-fidelity magnetic type.
Battery requirements:	Two Mallory Mercury Cells, type R.M. 675, for long working-life.
Case:	Black plastic with anodised aluminium front panel, spun aluminium dial.
Controls:	Tuning dial, and on/off switching by means of earpiece plug.
Price:	Available in kit form complete with earpiece, case, instructions and supply of solder in fitted pack. 49/6. Ready built, tested and guaranteed. 59/6.



Adamini

MICRO SOLDERING INSTRUMENTS

A range of micro soldering instruments combining high performance with really small dimensions and providing exceptional versatility.

Weighing about $\frac{1}{2}$ oz. (less flex) these miniature tools ensure the utmost accuracy and safety in use, resulting in consistently high standards of soldering with minimum operator fatigue.

Ultra-slim unbreakable nylon handles give a cool, comfortable grip for sustained delicacy of operation.

Slip-on bits are fitted over the element shaft, so absorbing all the heat produced and giving high performance with rapid heating and recovery. A wide range of interchangeable tip sizes is available to suit different types of work.

There are ADAMINI models from, 8 to 24 watts, in voltages from 6v. to 240v.

Please ask for NEW LEAFLETS
37/1005/7

LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon, CR9 2LL
Telephone 01-688 8589 and 4559



Selections from FELSTEAD ELECTRONIC'S

Winter List (Sent free for stamped addressed envelope to address below:—
Transformers: 2/6. AF15 3/6. AF17 4/6. OA5 1/6. OA8 1/6. OA85 1/6. OC23 6/8. OC25 6/8. OC26 7/6. OC28 8/6. OC35 8/6. OC44 2/9. OC45 2/6. OC71 2/6. OC72 2/6. OC75 2/6. OC81 2/6. OC81D 2/6. OC82D 2/6. OC170 4/6. OC171 2/6. Many more in list. S.D.E. BY100 800piv 2/10. 6 Amp series: BYZ13 300 piv 4/6. BYZ12 600piv 5/6. BYZ11 900piv 6/6. BYZ10 1200piv 7/6. (Charges 1/- upto 1/-, paid for 12 and over). Sub-Min Transformers: OUTPUT (3Ω for OC72, & c) 2/9 DRIVER 3/6. (Up to 6 either 1/-). MULTIMETER. Our famous 20000 Ω per V 24.12.6 (2/6). Details and other in list.

SOLDERING IRON. Slim, modern, British high-speed 81", all parts replaceable, highest quality, full guarantee: 21/- (1/6). **DIAMOND STYLII** Replacements for BSR TC8/LP, TC8/8, TC8LP/STEREO; COLLARO 'O': RONETTE BP40LP; GARRARD GC2/LP and GC8/LP; ACOS GP65/67, all at 7/6. (1/-) ACOS GP73, GP91; BSR 874 (8T3, 8T5), 878 (8T9); SONOTONE 8TA, 9TA, 9TAHC; PHILIPS AG3306, 3060 (3063, 3085, 3301, 3302, 3304) all at 16/- (1/-). All are of the very highest quality. Double Diamond: 8T4 (8T3, 8T5); 8T10 (8T9, 8T5); 9TA, 9TAHC, 3306, GP91 (For GP92, GP93, GP94 cartridges); GP91SC for all GP91-90 cartridges; All at 30/- each (1/-). **PICK-UP CARTRIDGES** All standard fittings and stylus. MONO GP67/2 15/- STEREO-COMPATIBLE (MONO) GP91/9C (21/-) STEREO GP93 25/6. STEREO CERAMIC GP94 38/6. SONOTONE STEREO 9TAHC (DIA.) 47/6. **GOLDRING** G850 97/8, G800 28.10.0, G800E 21.10.0 G800 SUPER E 21.10.0 (1/- all types), Reg. Post 4/-) **STYLII FOR ALL ABOVE TYPES**, including GOLDRING available. **RECORDING TAPE**, Still the finest quality British Mylar available: Standard 5" 600 ft. 7/8 51" 900 ft. 10/- 7" 1200ft. 11/8. **LONG PLAY** 5" 900 ft. 10/- 51" 1200ft. 11/8 1800ft. 13/- 1 1/2 on 5" and 51" 1200ft. on 7". **MICROPHONES** Crystal Mic 91, hand/desk 14/8. MIC45 Curvet metal handgrip 20/6. CM21 Grey hand/desk 10/8. Stick '60' 20/8 CM70 'Plane' machined metal tapered stick type with neck cord, adaptor to fit floor stands 29/8 (All 1/6) LAPEL (or hand) with clip 6/6 (1/-). All are fitted with leads. **DYNAMIC**, Cream hand/table MINY 15/8 (1/6) M810, 50K Ω for desk, tapered, with base and slide-out adaptor 39/8 M811, similar, but fixed on swivel swan neck to switch-fitted base 42/8. (Either 2/6). Type 209 Cardioid ball, 50K/600 Ω, omnidirectional, built-in vol. control, on/off switch, special lead, handle (as good as money can buy) 26/6. DM160, Non-Dir. Ball, 50K Ω, switch, cable, adaptor 77/8 (5/- either). **MICROPHONE INSERTS**, Dia., 1.75" OR 0.9" either size 5/6 (1/-). **EARPIECES** with lead & min. Jack plug (2.5 or 3.5mm, state which) Magnetic 1/9 Crystal (3.5 only) 4/9. (Up to 3 for 1/- on any). **HEADPHONES** De luxe STEREO 8-16 ohms, 47/8d. Same, fitted vol. control each earpiece, 67/8. Both have lead and stereo Jack plug. (3/-). High Res. 2000 ohm. Adjustable 18/6 (2/-) **SPEAKERS**, 12" ROUND, fitted tweeter, 3 or 15 Ω (state which) 37/6 (5/6) or for Stereo 80/- pair, cart. paid. 21" 3 Ω R Ω (state which) 7/8 (1/-) 12" powerful transistor replacement, high ohm 6/- (1/-). **EMI 13" x 8"**, 3, 8 or 15 Ω (state which) 42/6 (4/6); with single flared para. tweeter cone 8 or 15 Ω (state which) 45/6 (4/6); with two tweeters and cross-over network 75/- (5/-). **VIBRATORS**, Genuine Plessey 12v. 4 pin non-synch. 121HD4, 21" ex. pins 5/6-. Am. 12v. 4-pin, non-synch. 7/16ths, longer, 4/6 12v. 7-pin Synch. (128R7) 12/6. 6v. 7-pin. Synch. (68R7) 12/6. (All types 1/- per vibrator). **CONNECTING WIRE**, Packs of 5 coils asteel, vols. ex. coil ends. Solid core 2/9 (1/-). Flexible 3/9 (1/3). Super thin for transistor wiring 3/8 (1/2). **PICK-UP WIRE**, Super thin twin flex, screened and sheathed 1/8 yd. (1/-) upto 6yds.—over, free). **RETRACTABLE Flex Leads**, (Curlies) 6ft. phono plug ea. end 4/6. 12ft. 7/8. 6ft. phono plug/phono socket other end 5/- 12ft. 8/6 (1/- per lead, all types). **BEND SAE** for full free lists—Teleton and small 3w and 7½w trans. amplifiers, Electrolytics, Vol. Controls, all types of radio switches, car and portable expanding aerials, Meters, Test prods, all types of Brit. & cont. standard and min. plugs and sockets, SDR's, Thyristors, croc. clips (various), terminals, etc. etc. and many 'Special Offer' lines at lowest possible prices.

FELSTEAD ELECTRONICS (PE38)

LONGLEY LANE, GATLEY, CHEADLE, CHES. SK8 4EE
Cash with order only. No COD or Caller Service. Charges (Min. 1/-) in brackets after all items. Regret Orders under 5/- unacceptable. SAE please for enquiries Overseas orders welcomed—lists free.


BUILD YOUR CIRCUITS ON VEROBOARD

—the Universal Wiring Board—
obtainable from your local Retailer

Trade enquiries to:
NORMAN ROSE (ELECTRICAL) LTD.
8 St. Chad's Place, Gray's Inn Road, London, W.C.1

Technical enquiries to:
VERO ELECTRONICS LTD.
Industrial Estate, Chandler's Ford, Hants

LEARN HOW COMPUTERS WORK WITH KOMPUKIT

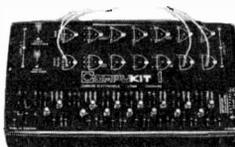

Kompukit I is a practical do-it-yourself teaching aid designed to remove the mystery from digital computers, logic and Boolean algebra. "Cheap, Quick and Clean . . . and, clear winner on all counts" says the Times Educational Supplement. Accompanied by easy-to-follow instruction book.

Ideal as a gift to amateurs, intelligent teenagers, teachers, etc.
Unassembled kit, complete, Type CK1/U £10.10.0 (P. & P. 6/-).
Assembled, fully tested, ready to use, Type CK1/A £13.5.0 (P. & P. 6/-).
Also available Kompukit I Deluxe Model and Kompukit 2 I.C. Patchboard.

Cash with order, or further information, from
LIMROSE ELECTRONICS (PE), Lymm, Cheshire

LST

ELECTRONIC COMPONENTS LTD

= BETTER QUALITY, SERVICE, PRICES & LARGEST STOCKS

AC107 7/7	BA111 6/-	BFY51 3/9	NKT127 10/6	NKT263 4/8	NKT12429 10/6	OC205 9/-	40316 9/3	2N709 8/6	2N3707 2/10	3N142 10/9
AC126 5/-	BA114 3/6	BFY52 4/6	NKT128 10/-	NKT264 4/3	OC206 15/-	40317 15/10	2N711 7/3	2N711A 7/6	2N3708 1/10	3N143 13/3
AC127 5/-	BA113 1/3	BFY53 2/2	NKT129 8/6	NKT265 5/6	NKT13329 10/6	OC207 15/-	40319 10/9	2N711A 7/6	2N3709 2/10	3N152 17/3
AC127Z 9/6	BC113 5/-	BFY90 13/6	NKT135 6/1	NKT270 6/-	OC207 15/-	OC207 15/-	40320 7/3	2N743 4/6	2N3710 2/3	AA119 2/-
AC128 4/6	BC118 7/6	BSY19 6/6	NKT137 6/1	NKT271 2/10	NKT13429 3/11	OC208 10/-	40323 10/6	2N744 6/-	2N3711 2/6	AA119 2/2
AC176 5/-	BC125 11/-	BSX20 6/6	NKT141 10/6	NKT272 2/10	OC209 3/11	OC209 3/11	40326 9/3	2N911 10/-	2N3819 7/-	AA120 1/7
AC187 6/-	BC126 11/-	BSX21 7/6	NKT142 10/-	NKT273 3/8	NKT16229 8/5	OC210 9/9	40326 7/3	2N914 3/11	2N3820 18/9	AA121 6/2
AC188 6/-	BC126 11/-	BSX22 7/6	NKT143 9/6	NKT274 2/10	OC211 8/5	OC211 8/5	40329 9/9	2N918 8/5	2N3826 6/2	AA123 3/2
AC188 6/-	BC126 11/-	BSX22 7/6	NKT144 4/6	NKT275 3/4	NKT20329 6/8	OC212 15/-	40344 3/9	5N2929 5/3	2N3866 25/-	BA110 6/-
AC197 5/9	BC143 15/-	BSY27 4/6	NKT151 8/-	NKT276 3/6	NKT20339 6/8	OC213 15/-	40347 7/6	2N930 6/2	2N4037 15/-	BA111 6/6
AC198 4/4	BC144 2/9	BSY29 3/2	NKT153 6/1	NKT279A 2/6	NKT20339 6/8	OC214 15/-	40348 10/3	2N1131 6/-	2N4058 3/4	BA112 18/-
AC199 3/10	BC148 3/9	BSY54 2/11	NKT154 6/1	NKT281 5/6	NKT35219 6/4	SIM 19/-	40360 8/6	2N1132 6/2	2N4059 5/6	BA115 1/6
AC21 3/10	BC149 3/9	BYZ14 3/3	NKT157 6/1	NKT302 12/5	SIM 33/6	SIM 33/6	40361 11/6	2N1302 3/7	2N4060 5/6	BA130 3/6
AC21 3/9	BC169 2/1	BYZ15 18	NKT162 6/1	NKT303 17/6	STZ 15/9	STZ 15/9	40362 11/6	2N1303 4/6	2N4061 4/6	BY125 3/2
AC227 3/6	BC171 2/3	C111 12	NKT166 6/8	NKT304 9/10	OC19 5/1	OC19 5/1	40370 6/2	2N1304 4/11	2N4062 4/6	BY128 3/2
AC228 3/8	BC182L 2/3	C112 12	NKT166 6/8	NKT304 9/10	OC20 19/6	OC20 19/6	40406 11/3	2N1305 4/11	2N4284 3/1	BY100 4/4
AC229 7/6	BC183L 1/10	C426 8/3	NKT165 6/1	NKT351 10/10	OC22 8/1	OC22 8/1	40408 10/3	2N1306 6/2	2N4287 3/1	BY127 4/4
AD10 11/6	BC184L 3/4	CR1-051C 8	NKT201 6/1	NKT352 17/6	OC23 10/1	OC23 10/1	40432 2/3	2N1307 6/2	2N4288 3/1	BYX10 1/5
AD149 11/6	BC121L 10/1	CR1-051C 8	NKT201 6/1	NKT361 20/-	OC24 10/1	OC24 10/1	40462 11/3	2N1308 6/2	2N4289 3/1	BYX36/300
AD161 7/6	BCY10 12/-	CR1-051C 8	NKT205 6/1	NKT401 15/6	OC25 7/6	OC25 7/6	40468A 12/10	2N1613 4/6	2N4290 3/1	BYX36/300
AD162 7/6	BCY30 5/1	GET102 6	NKT206 6/1	NKT402 15/6	OC26 12/1	OC26 12/1	40600 11/6	2N1711 5/6	2N4292 3/1	BYX36/600
AD140 12/6	BCY31 5/6	GET103 5	NKT208 6/1	NKT403 14/9	OC29 15/1	OC29 15/1	40602 8/1	2N2147 16/3	2N4292 3/1	BYX36/600
AD17 32/1	BCY32 10/-	GET111 5	NKT210 4/2	NKT404 11/-	OC35 12/6	OC35 12/6	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AD212 39/1	BCY33 4/1	GET111 5	NKT210 4/2	NKT405 11/-	OC36 12/6	OC36 12/6	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AF102 12/6	BCY33 4/1	GET111 5	NKT210 4/2	NKT405 11/-	OC36 12/6	OC36 12/6	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AF106 7/6	BCY38 5/1	M1480 20/6	NKT212 3/9	NKT406 9/11	OC41 5/1	OC41 5/1	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AF114 5/-	BCY39 9/6	M490 22/6	NKT214 3/7	NKT408 11/1	OC42 4/6	OC42 4/6	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AF115 5/-	BCY70 3/10	M1491 29/6	NKT215 3/7	NKT452 9/6	OC43 4/6	OC43 4/6	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AF116 5/-	BCY71 7/8	MPF102 8/6	NKT216 7/6	NKT453 6/6	OC45 3/1	OC45 3/1	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AF117 5/-	BCY72 3/2	MPF103 7/6	NKT217 9/1	NKT603F 4/8	OC70 2/6	OC70 2/6	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AF118 8/10	BCZ11 7/6	MPF104 7/6	NKT218 6/1	NKT613F 5/2	OC71 3/1	OC71 3/1	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AF121 6/-	BD121 22/1	MPF105 9/6	NKT219 4/7	NKT654F 4/2	OC72 4/6	OC72 4/6	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AF124 5/-	BD123 22/1	NK171 7/6	NKT221 7/1	NKT675 4/1	OC82 5/1	OC82 5/1	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AF125 4/2	BD124 20/8	NKT12 5/5	NKT222 6/1	NKT676 5/1	OC75 4/6	OC75 4/6	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AF126 3/6	BDY20 20/8	NKT32 6/1	NKT223 5/1	NKT677F 3/10	OC76 5/1	OC76 5/1	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AF127 3/6	BF163 5/1	NKT42 6/1	NKT224 3/6	NKT703 8/1	OC77 4/6	OC77 4/6	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AF139 15/-	BF167 9/1	NKT43 6/1	NKT225 3/6	NKT703 8/1	OC81 4/6	OC81 4/6	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AF178 9/6	BF173 6/1	NKT44 3/9	NKT226 11/-	NKT713 3/10	OC82 4/6	OC82 4/6	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AF179 11/6	BF178 10/6	NKT45 3/9	NKT227 9/6	NKT717 5/10	OC82 4/6	OC82 4/6	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AF180 12/6	BF179 12/6	NKT101 6/1	NKT228 6/1	NKT724 4/11	OC82 5/1	OC82 5/1	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AF186W 8/-	BF180 7/6	NKT102 6/1	NKT229 3/11	NKT736 6/2	OC82 4/6	OC82 4/6	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AF186W 8/-	BF181 7/6	NKT103 6/1	NKT231 6/1	NKT773 3/7	OC83 4/6	OC83 4/6	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AF239 7/6	BF184 5/1	NKT104 6/1	NKT232 6/1	NKT774 6/1	OC84 5/1	OC84 5/1	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AFZ11 8/-	BF185 5/1	NKT105 6/1	NKT233 5/9	NKT0013 6/6	OC123 7/1	OC123 7/1	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AS27 4/5	BF194 3/6	NKT106 6/1	NKT238 4/1	NKT10419 3/10	OC139 5/1	OC139 5/1	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AS27 4/5	BF195 3/6	NKT107 6/1	NKT239 4/1	NKT10519 3/10	OC140 7/1	OC140 7/1	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AS27 4/5	BF200 7/6	NKT108 6/1	NKT240 3/10	NKT10519 3/10	OC141 12/6	OC141 12/6	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AS27 4/5	BFX13 5/1	NKT109 6/1	NKT241 2/11	NKT10339 4/5	OC170 5/1	OC170 5/1	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AS27 4/5	BFX29 6/1	NKT121 10/6	NKT242 3/9	NKT10339 4/5	OC171 6/1	OC171 6/1	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
AUY10 10/6	BFX44 5/2	NKT122 10/10	NKT243 12/1	NKT10439 4/7	OC200 7/6	OC200 7/6	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
B2M 12/6	BFX85 6/9	NKT124 9/6	NKT244 3/1	NKT10439 4/7	OC201 9/6	OC201 9/6	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
B3M 15/-	BFX88 5/3	NKT125 6/5	NKT245 3/1	NKT12329 5/5	OC202 12/6	OC202 12/6	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600
BA102 9/-	BFY50 4/6	NKT126 4/4	NKT262 4/3	NKT12329 5/5	OC203 7/6	OC203 7/6	40602 8/1	2N2148 12/6	2N4292 3/1	BYX36/600

BC107/8/9 2/9
NPN Planar transistors
BC107 8/9 25 + 2/5 100 + 2.1
BC108 25 + 2/3 100 + 2

2N3819 7/-
Texas FET
25 6/- 100 + 5.3

SILICON RECTIFIERS

1 Amp Miniature Moulded Junction Rectifiers.

P.I.V. 1-24 25 + 100 + 500 +

IN4001	50	1/6	1/4	1/2	1/-
IN4002	100	1/6	1/4	1/2	1/-
IN4003	200	2/1	1/9	1/6	1/3
IN4004	400	2/1	1/9	1/6	1/3
IN4005	600	2/6	2/1	1/9	1/6
IN4006	800	3/1	2/10	2/6	2/3
IN4007	1000	4/1	3/3	2/9	2/6

2N4871 6/9
Motorola unijunction
25 + 5/9 100 + 4/9

MGA 100 35/-
31F2 28/6
Infra-red devices

In the event of any IN4000 series going temporarily out of stock we reserve the right to send higher voltage types at no extra charge. 1000+ and over prices on application.

2N3055 15/-
115 watt silicon power transistor
25 + 13/- 100 + 11/-

BF195 2/6
Mullard Lock-fit
25 + 2/- 100 1/9

ZENER DIODES

400mW 10% GLASS CASE. TEXAS Mfr.

IS2036	3.6 volt	IS2082	8.2 volt
IS2039	3.9 volt	IS2100	10 volt
IS2043	4.3 volt	IS2110	11 volt
IS2047	4.7 volt	IS2120	12 volt
IS2056	5.6 volt	IS2160	16 volt
IS2062	6.2 volt	IS2180	18 volt
IS2068	6.8 volt	IS2270	27 volt
IS2075	7.5 volt	IS2300	30 volt

PRICES: 1-24 3/6, 25-99 2/9, 100 + 2/3

IRC 20 7/-
Int. Rectifier thyristor
200 piv 1.2 amp (similar C106B1)
25 + 6/- 100 + 5/-

CHEAP LOGIC!!
(Fairchild-USA)
1-11 12-24 25-99 100 + uL 900 Buffer
8/- 7/- 6/6 5/6
uL914 Dual Input Gate
8/- 7/- 6/6 5/6
uL 923 DK Flip Flop
10/6 10/9 9/6 9/-
Data and circuits article, 5-pages, at 2/6. Article "30 Suggested Circuits for Micro-logic", at 3/-. TOS to D/C conversion spreaders adaptors at 1/6 each.

2N2926 2/-
NPN Planar transistors
25 + 1/8 100 + 1/6

OA91 SPECIAL OFFER
Mullard Diode
25 + 9d. 100 + 7d.

ULTRASONIC TRANSDUCERS

Operate at 40kc/s. Can be used for remote control systems without cables or electronic links. Type 1404 transducers can transmit and receive.

FREE: With each pair our complete transmitter and receiver circuit. PRICE £5.10 Pair (Sold only in pairs)



INTEGRATED CIRCUITS
Some R.C.A. Linear Types

CA3005 23/6	CA3020 25/3	CA3028B 21/-	CA3043 27/6
CA3011 14/9	CA3021 31/3	CA3035 24/6	CA3044 24/6
CA3012 17/9	CA3022 26/-	CA3036 14/6	CA3045 24/6
CA3013 21/-	CA3023 25/3	CA3039 16/9	CA3046 15/2
CA3014 24/9	CA3026 20/-	CA3041 21/9	CA3048 40/9
CA3018 16/9	CA3028A 14/9	CA3042 21/9	CA3051 26/9

Application Notes for each individual 2/6d. per copy.

PA234	GE IC 1 Watt Amplifier	17/6
PA237	GE IC 2 Watt Amplifier	37/6
PA246	GE IC 5 Watt Amplifier	52/6
PA424	GE IC Zero Voltage Switch	49/6
SL403A	Plessey 3 Watt Amplifier	42/6
SL702C	Plessey Linear	29/6
TAA263	Mullard Linear	15/-
TAA293	Mullard General Purpose Amplifier	30/-
TAA310	Record Playback Amplifier	30/-
TAA320	MOS LF Amplifier	13/-
TAD100	Mullard IC Receiver	39/



It's the Cat's Whiskers!

You must admit, the lad's keen—he's fallen asleep still tuned in to dad's vintage receiver. His cat's whiskers set lies abandoned by his other "receiver", and now he's dreaming of the super sets and gadgets he's going to build once he's got the Home Radio Components Catalogue that Father Christmas has been ordered to bring. In the morning when the lad sits up in bed and flips through its 300 pages he'll certainly come out with some such phrase as "It's the cat's whiskers!"

If you can't rely on Father Christmas to bring you a Home Radio Catalogue, play safe—give yourself one! It will cost you only 8/6, plus 4/- post and packing, and once you've got it you'll wonder how you ever managed without it. It's packed with over 8,000 items, no less than 1,500 of them illustrated; and every copy contains 6 vouchers each worth a bob when used as directed. Fill in the coupon right away and post it with your cheque or P.O. for 12/6.

The price of 12/6 applies only to catalogues purchased by customers residing in the U.K.



**A Happy
Christmas
to all our
readers.**

Please write your Name and Address in block capitals

Name _____

Address _____



Home Radio (Components) Ltd.
Dept. PE, 234-240 London Road, Mitcham, CR4 3HD.

Editor F. E. BENNETT Assistant Editor M. A. COLWELL Editorial Assistants D. BARRINGTON G. GODBOLD M. KENWARD
Art Editor J. D. POUNTNEY Technical Illustrators J. A. HADLEY P. A. LOATES
Advertisement Manager D. W. B. TILLEARD

SEEING WITH SOUND

ALMOST two whole years have passed since fog was last discussed on this page. More specifically, we then aired our hopes for an electronic system that would, to some degree, restore visibility to drivers of motor vehicles in bad weather conditions.

Two years is a long time in electronics, and one could quite reasonably expect important steps to have been taken by now toward the solution of this serious problem. But nothing concrete has emerged so far from industry or from government research establishments.

We do know that much effort has been put into the development of a radar system for vehicles operating inside airports. There is a vital need for emergency service vehicles to be able to move at speed to the scene of an aircraft mishap, no matter what state of visibility obtains. This particular radar system has not yet been put into production, presumably because the airport authorities have not yet been decided to buy.

By normal standards, a radar system is necessarily expensive and involves much sophisticated engineering. It is true that solid state devices such as Gunn-effect diodes are available for microwave operation, and these help to simplify the receiver and transmitter design and so reduce the overall bulk of the installation. But there still remains a major problem in the form of the display device. Until the c.r.t. is superseded by a solid state electro-luminescent panel, there is little likelihood that radar, even in an elementary form, can be seriously considered as a feasible proposition for installation on all types of road vehicles.

While waiting for further advances in technology to solve these engineering (and cost) problems, there is no reason why private individuals should not on their own account investigate other methods to combat the common enemy, fog.

Leaving aside electro-magnetic waves, why not explore the possibility of sound waves? The equipment needed for an acoustical system is not highly complicated, and the basic principles involved are familiar enough to most electronics enthusiasts. The Sonic Obstacle Locator described in this issue has proved itself to a marked degree. Admittedly, as a driving aid it is not infallible, and lacks, as yet, the ability to discriminate between tree, lamp post, or car. Serious limitations, in fact, for a car-borne device. But it is not offered as an instant solution to a formidable problem. It is offered as an idea worthy of further development by the experimentally inclined. And other uses may well become apparent.

We hope many will rise to the challenge. Amateurs have blazed the trail before. Most significantly, in proving the usefulness of the then neglected high frequency radio waves. Maybe private experimenters can achieve some noteworthy success in electro-acoustics. F.E.B.

THIS MONTH

CONSTRUCTIONAL PROJECTS

SONIC OBSTACLE LOCATOR	22
WASH-WIPE CONTROL	40
"P.E. GEMINI" DUAL PURPOSE STEREO AMPLIFIER	48
P.E. DIGITAL CLOCK	58

SPECIAL SERIES

MAKING THE MOST OF LOGIC IC's—7	35
---------------------------------	----

GENERAL FEATURES

BIAS IN TAPE RECORDING	44
------------------------	----

BEGINNERS

SIREN	30
-------	----

NEWS AND COMMENT

EDITORIAL	21
NEWS BRIEFS	31, 47
SPACEWATCH	32
AUDIO TRENDS	52
ON THE FRINGE	73
READOUT	74

Our February issue will be published on Friday, January 15

© IPC Magazines Limited 1971. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Subscription Rates including postage for one year, to any part of the world, £2 5s. 0d. (£2.25)
Practical Electronics, Fleetway House, Farringdon St., London, E.C.4. Phone: Editorial 01-634 4452; Advertisements 01-634 4202



SONIC OBSTACLE

ATMOSPHERIC pollution and weather conditions often combine to produce thick fogs which reduce visibility to as little as 10-20 feet. Much the same applies where there is smoke or driving snow. In such conditions man's senses are virtually useless and there is a real need for technical aids to penetrate the murk.

Short range radar would seem to provide an answer to the problem, but the equipment is expensive and involves radio licensing complications. Fog is transparent to certain bands of infra-red, but infra-red emitters and sensors for use at such wavelengths are not, as yet, sufficiently developed. Another approach would be ultrasonics, but high frequency sound waves tend to be scattered by fog droplets, and have a short range.

AUDIBLE SOUND

The Oil-bird of South America points the way to a possible solution to the problem; it finds its way around dark caves by emitting audible clicking noises, like the sound of castanets. Audible sound is, of course, only slightly attenuated by fog and other atmospheric particles, hence the use of the fog horn, and the explosive cap on railways.


Sonar has long been employed for navigation and ranging purposes underwater, and there seems to be no reason why audible sound pulses in air should not be similarly used if the equipment can be made to operate against a background of day-to-day ambient noise.

The Sonic Obstacle Locator is the result of experiments to test the practicability of using audible sound to detect the presence of unseen objects in fog. With a range of 100 feet, the equipment could be used on board small boats for docking in conditions of poor visibility, or as an outdoor, all weather intruder alarm. There are many other possible applications, such as counting passing cars on a roadway, and educational demonstrations involving the speed, refraction, and reflection of sound waves.

SENSITIVITY

Although not recommended for use on cars in fog, the Sonic Obstacle Locator will work at low speeds, and was tested on a vehicle as this provided the most adverse conditions of high ambient noise.

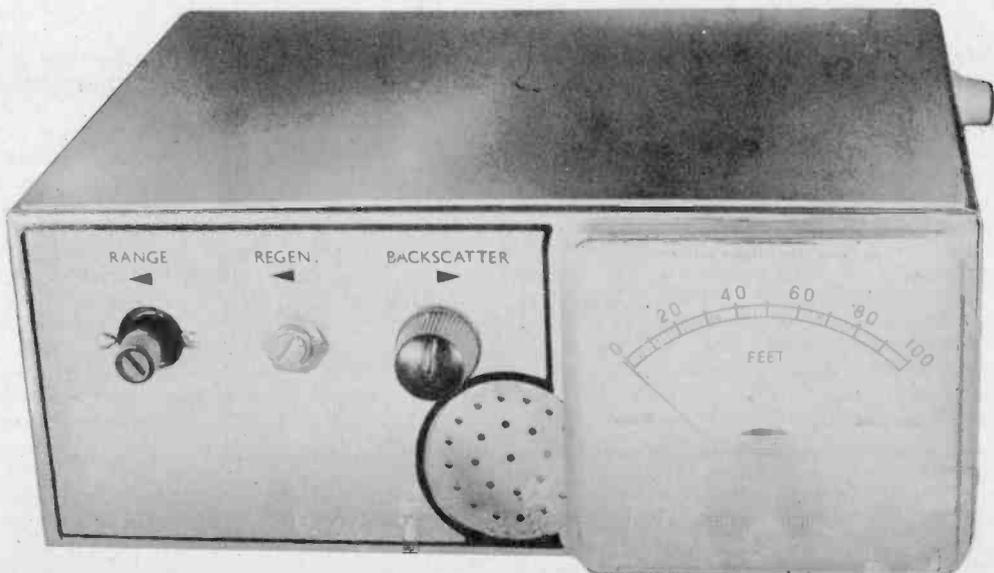To give an idea of sensitivity, a response is obtained from an adult pedestrian at up to 22 feet, a small parked car at 50 feet, or a stone wall perpendicular to



LOCATOR

By D. Bollen

the sound source axis at 100 feet. When an obstacle in the road ahead is detected, the unit inside the car emits a bleep warning note, of duration directly proportional to distance.

The note varies from a short click at 95 feet range, to an almost continuous tone at the minimum range of 5 feet. A meter linearly calibrated 0-100 feet is incorporated to show the actual distance of the obstacle.

Because of sonic interference from the exhaust noise of other vehicles, particularly diesel lorries, the equipment will only operate reliably at traffic speeds below 30 m.p.h., under typical fog driving conditions.

MEASURING DISTANCE THROUGH AIR WITH SOUND

High frequency sound is readily reflected from solid surfaces, and sound waves conform to the same general laws of reflection as light.

The time taken for a sound to travel to a reflecting surface and back again can be used as a measure of the intervening distance, with an accuracy dependent on slight changes in the speed of sound resulting mainly from variations of temperature and humidity.

Sound velocity is not significantly influenced by droplets or particles in the atmosphere, and is largely independent of air pressure and altitude when corrections are made for temperature.

The velocity of sound in dry air at 0 degrees centigrade is 1,087 feet per second; about $4\frac{1}{2}$ times slower than sound in water. If the air temperature is raised to 20 degrees centigrade a velocity increase of about 3.7 per cent will be noted.

When the air is fully saturated with water vapour, this causes a velocity increase of about 0.5 per cent, because water vapour decreases the density of air.

From the above it can be estimated that, over a temperature range ± 10 degrees centigrade, and in varying humidity, a sonic yardstick should offer a potential accuracy of about ± 2.5 per cent.

OPERATING FREQUENCY AND TRANSDUCERS

The frequency of the transmitted sound should be high, to combat interference from man-made noise, the bulk of which lies in the lower part of the audio spectrum. However, sonic transducers operating above 15kHz are usually not sensitive enough for low power sound-through-air applications, although they may be suitable for service underwater where sound conduction

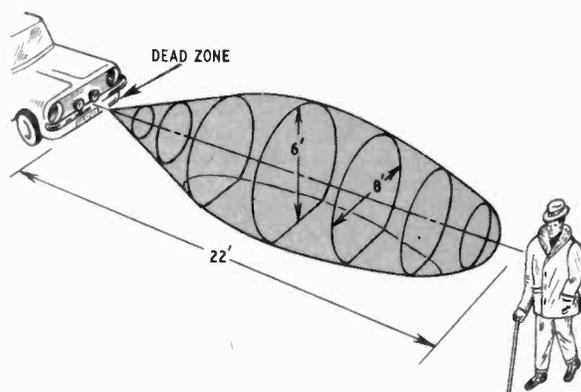


Fig. 1. Area of response of the Sonic Obstacle Locator when used for pedestrian detection

is good. In the interests of economy, it was decided that special transducers should be avoided.

Tests were made with several types of loudspeaker and microphone, to establish a suitable compromise between cost and noise rejection when choosing the operating frequency. Firstly, the upper limit was set by microphones offering a useful output above 15kHz, as they were too expensive to qualify.

It was discovered that good quality tweeters operating at 10-15kHz gave markedly inferior results when compared with small, cheap loudspeakers handling 10kHz. This somewhat surprising result was eventually attributed to sound reinforcement arising from resonances in the cheap loudspeakers, and further improvements at 10kHz were effected by cutting down the size of the loudspeaker cone, and stiffening it with cellulose dope. Obviously, if the sonic transmitter can be encouraged to provide a large acoustic output, this will tend to minimise noise, and compensate for the lower frequency.

When a loudspeaker is handling frequencies above a few kilohertz there will be only a small excursion of the voice coil and cone, and the limit to the amount of power the loudspeaker can handle is determined by voice coil overheating. If the high frequency input is pulsed on and off, with a relatively long pause between pulses, the loudspeaker can sustain very high levels of input without damage, and at the same time yield an output of high intensity.

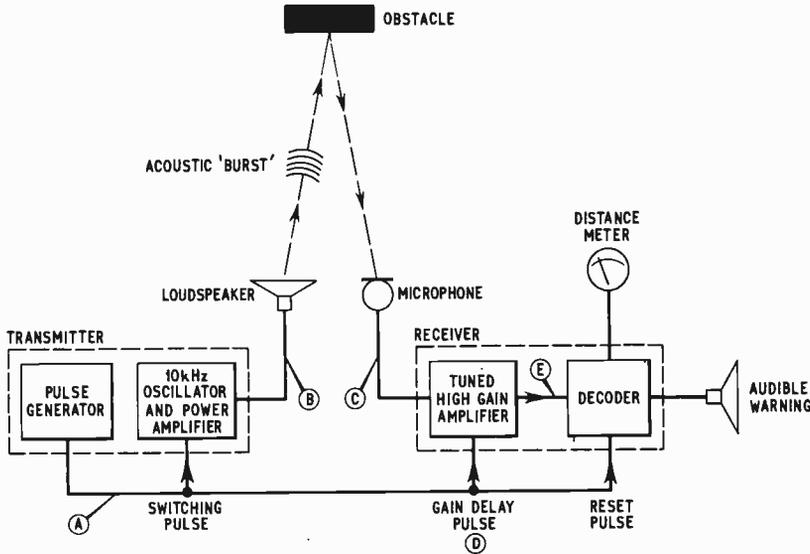


Fig. 2. Block diagram of the Sonic Obstacle Locator. 10kHz bursts of radiated acoustic energy are made to bounce off the obstacle. These are then amplified and the distance of the obstacle computed by the decoder for display by a meter. An audio bleep warning is also triggered at this final stage

DIRECTIONAL CHARACTERISTIC

In using a locator, echoes should only be obtained from obstacles in the road ahead, and not from objects which do not lie in the path of the vehicle.

A loudspeaker offers a polar response, at high frequencies, which is directional, but is not sufficiently narrow in shape for the present application; the requirement taking the form of a broad sphere slightly flattened along the sound source axis. However, a microphone can be made to see only a narrow angle by placing it at the focus of a parabolic reflector which looks along the source axis.

When loudspeaker and microphone polar responses are combined, the result is a thin, almost ideal cigar shape extending in front of the vehicle, as depicted in Fig. 1.

The plot upon which Fig. 1 is based was obtained from a 5 gallon oil drum which simulates a pedestrian wearing normal, soft clothing.

It can be seen that the area of response is roughly the width of the car and extends forwards to a distance of 22 feet. For larger obstacles, the area of detection will be wider and longer, though still of the same cigar shape.

SONIC TRANSMITTER

The basic features of the Sonic Obstacle Locator are outlined by the block diagram of Fig. 2, with associated waveforms in Fig. 3.

Dealing first with the transmitter, this consists of a pulse generator, a 10kHz square wave oscillator, and a tuned power amplifier. The pulse generator provides a master pulse of 2ms duration (Fig. 3A) at intervals of 178ms, the time taken for sound to travel to the obstacle and back at the maximum range of 100 feet.

On receipt of the pulse, the 10kHz oscillator provides an output of 2ms duration, consisting of 20 cycles of a 10kHz square wave, which is then passed to the power amplifier. Being tuned, the power amplifier converts the square wave into a sine wave, and the input to the loudspeaker is an envelope containing 20 cycles of a 10kHz sine wave as seen in Fig. 3B.

To detect echoes from obstacles very close to the transmitter, the radiated sound must be of short duration, so that it dies away completely before the

echo arrives. A time of 2ms for the acoustic burst from the transmitter is well inside the period fixed by the minimum range of 5 feet, to allow for various circuit delays and loudspeaker lag.

In passing, it is of interest to note that the short burst of 10kHz sound from the transmitter is registered by the human ear merely as a loud click, with virtually no tone content.

RECEIVER

If an untuned amplifier was used with a microphone to pick up the minute reflected signals from the transmitter, the echo pulses would be completely swamped by

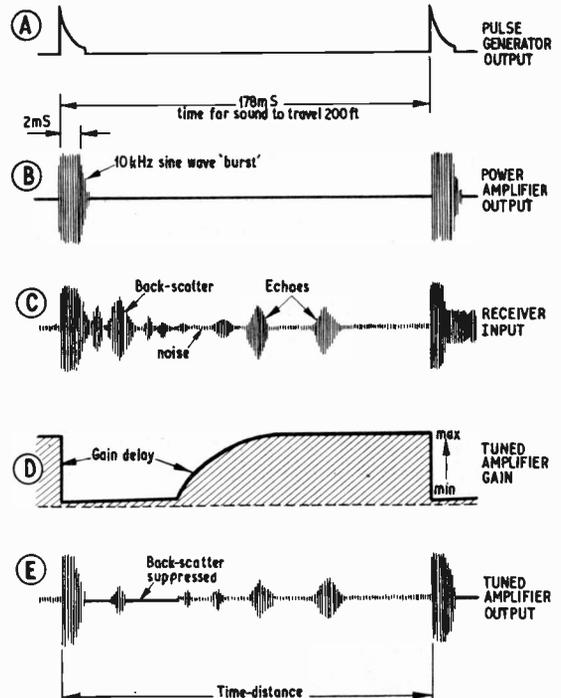


Fig. 3. Waveforms associated with Fig. 2 and identifiable by the letter. Fig. 3D is the tuned amplifier gain characteristic

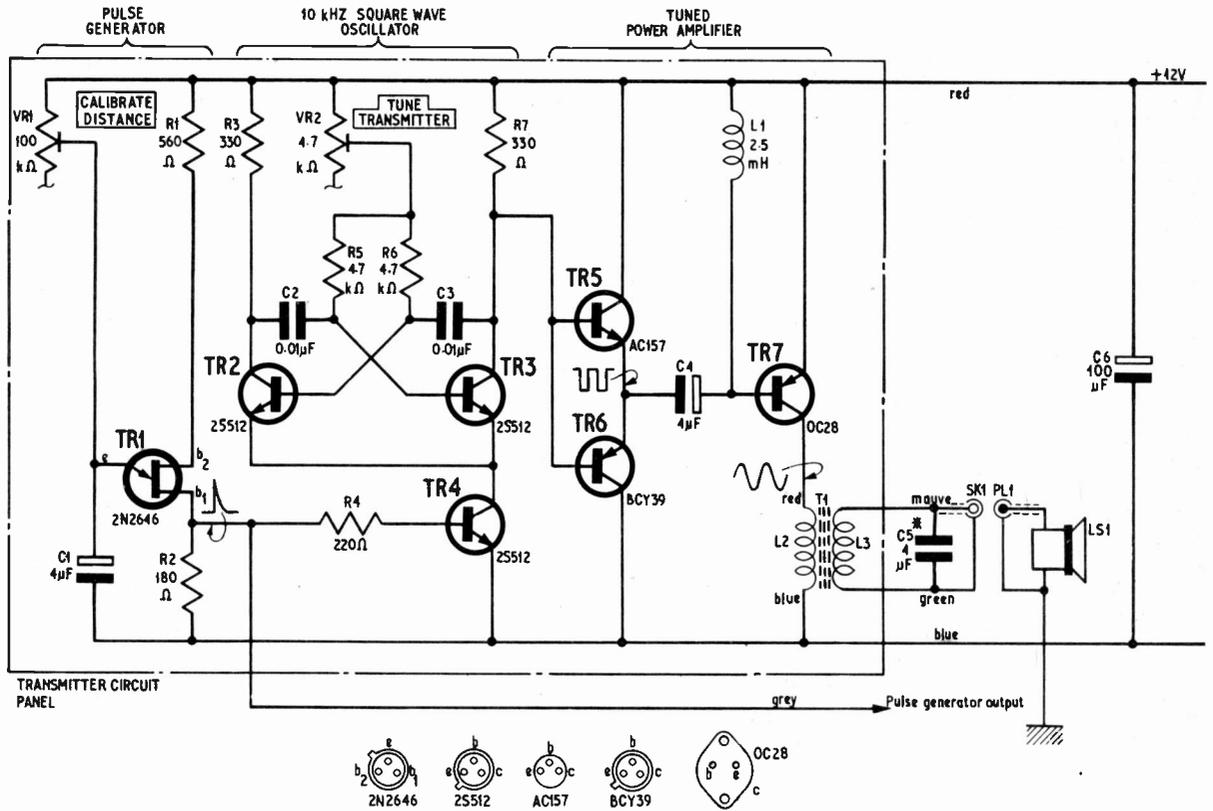


Fig. 4. Circuit diagram of the transmitter consisting of pulse generator, square wave oscillator and tuned power amplifier

broadband ambient noise, except in a very quiet environment. Therefore, the sonic receiver is tuned to the transmitter frequency. In the block diagram the receiver is seen to consist of a microphone, a tuned high gain amplifier, and an echo pulse decoder circuit.

A typical microphone response to the burst of sound from the transmitter is shown by waveform Fig. 3C. Note the presence of back-scatter, noise, and the echo pulses.

Because echoes from near objects are of greater amplitude than echoes from distant objects, rough surfaces and very small objects close to the loudspeaker and microphone tend to cause unwanted back-scattering of sound, and there is also direct pick-up of the unreflected burst from the loudspeaker.

Ideally, the receiver response should be proportional to distance; low for near objects and high for distant objects, so that an echo of the same amplitude is obtained from a given object at any distance with the range of the equipment. In practice, however, it is sufficient to ensure that the receiver is pulsed off while the acoustic burst is travelling over the first few feet of its journey, and then gain can be allowed to rise quickly to maximum for the reception of echoes.

ELIMINATING BACK-SCATTER

Controlled by the gain delay pulse derived from the pulse generator, the tuned amplifier gain characteristic takes the form shown, on an exaggerated time-distance scale, in Fig. 3D. Gain is almost zero at the time of the acoustic burst, and remains low over the region of back-scatter, then rises quickly to a stable level for the remainder of the period.

The effect of gain delay is demonstrated by comparing the resulting tuned amplifier output Fig. 3E with the amplifier input Fig. 3C. Back-scatter has been virtually eliminated from the waveform, without influencing the echo pulses. Although the tuned amplifier is switched off during the transmitter burst, it is almost impossible to remove evidence of the burst from the amplifier output (Fig. 3E) because of electrical interaction between transmitter and receiver circuits, despite careful screening. However, the decoder circuit takes this into account.

The function of the decoder, which will be examined in greater detail later, is to measure the time interval between the start of the control pulse and reception of the first significant echo, while ignoring as far as possible noise, and secondary echoes.

Distance is computed by the decoder for display by a meter, and an audio bleep warning oscillator is also triggered to give an output from a crystal insert loudspeaker.

TRANSMITTER CIRCUIT

The transmitter circuit of Fig. 4 was designed to feed a peak pulsed power of more than 20 watts, at 10kHz, into a 3 ohms nominal impedance loudspeaker (12 ohms at 10kHz), using as few components as possible.

Looking first at the pulse generator of Fig. 4, C1 is positively charged through VR1, the unijunction transistor TR1 triggers into conduction, whereupon C1 discharges rapidly through R2 to produce a steep-sided positive pulse. The interval between pulses is set by adjustment of VR1, and the duration of the pulse is determined by the fixed values of C1 and R2.

COMPONENTS . . .

SONIC TRANSMITTER

Resistors

R1	560 Ω	R5	4.7k Ω
R2	180 Ω	R6	4.7k Ω
R3	330 Ω	R7	330 Ω
R4	220 Ω		

All 10%, $\frac{1}{2}$ watt carbon

Capacitors

C1	4 μ F electrolytic 50V
C2	0.01 μ F miniature polyester 250V
C3	0.01 μ F miniature polyester 250V
C4	4 μ F electrolytic 50V
C5*	4 μ F metallised 150V (see text)
C6	1,000 μ F electrolytic 50V

Transistors

TR1	2N2646
TR2, TR3, TR4	2S512 or BSY27 (3 off)
TR5	AC157 or AC127
TR6	BCY39 or 2N2904
TR7	OC28

Potentiometers

VR1	100k Ω horizontal preset
VR2	4.7k Ω horizontal preset

Inductor

L1	2.5mH RF choke
----	----------------

Transformer

T1	LA5 pot core (see text)
----	-------------------------

Loudspeaker

LS1	3 ohm 5in dia. (see text)
-----	---------------------------

Socket

SK1	Coaxial socket
-----	----------------

Plug

PL1	Coaxial plug
-----	--------------

Miscellaneous

0.1in matrix Veroboard	4.1in \times 1.7in
3in \times 1.8in	16 s.w.g. sheet aluminium
TO3 transistor mica washer	and spacers
20 s.w.g. enamelled copper wire	

Timing components R5, R6, C2 and C3, in Fig. 4, will cause the multivibrator circuit TR2 and TR3 to oscillate close to 10kHz, but a fine frequency adjustment is provided by VR2 (tune transmitter).

The multivibrator will only oscillate when the emitters of TR2 and TR3 are connected to the negative rail by transistor switch TR4. In turn, TR4 is only switched on for a period of 2ms when it receives the pulse from TR1, via R4.

Driven by the multivibrator output, the complementary pair TR5 and TR6 alternately clamp C4 to positive and negative supply rails, and owing to the presence of tuned circuits L1, C4, and L3, C5, the switching waveform is converted into a sine wave by output transistor TR7.

Approximately 15V r.m.s. is developed across the 12 ohm speaker load during the 2ms pulse period.

Transformer T1 is hand wound on a Vinkor assembly, and one end of the secondary winding L3 is taken to a separate earth connection to accommodate positive or negative earth battery supplies.

REGENERATIVE RECEIVER

Receiver tuned amplifier and decoder circuits will be considered separately. Fig. 5 shows the tuned amplifier circuit.

Looking first at the very important stage TR9 in Fig. 5, it can be seen that this closely resembles a regenerative tuned stage in a t.r.f. radio receiver. Regeneration does away with the need for multiple tuned stages and simplifies tuning adjustments, while still giving reasonable selectivity.

Winding L6 is phased with L7 to give positive feedback between collector and base of TR9, and thus multiplies the Q value of tuned circuit L7, C12, and TC1. Regeneration is smoothly controlled by the VR5 setting.

TR9 is operated at a low collector current, near the point where gain falls off as collector current is decreased. VR4 sets the working point by establishing the amount of positive bias on the base of TR9.

A positive going pulse from the pulse generator is converted by C9, D1, and D2 into a negative pulse which counteracts the bias on the base of TR9, thus reducing gain. Owing to the slow discharge of C9 through VR4, R11, and R12 at the termination of the pulse, TR9 remains off for a period much longer than the time of the control pulse. The gain delay period is adjustable by VR4, and back-scatter control VR3.

Transformer T3 is hand-wound on an LA2107 pot core assembly.

EMITTER FOLLOWER

The signal from the microphone could be fed straight to the base of TR9, but this would demand a microphone transformer of non-standard impedance. Also, a long run of microphone cable could cause detuning. Therefore, emitter follower TR8 is included to serve as an impedance converter and buffer stage. Transformer T2 is of the type found in hand-held, moving coil stick microphones, and has an output impedance of 50 kilohms.

As the collector load of TR9 is a high Q tuned circuit; it will present a high impedance, with large voltage amplification, to a signal of 10kHz, but side frequencies will see a low impedance and are hardly amplified at all. Overall rejection of the Fig. 5 circuit is better than 30dB for signals 1kHz above and below the centre frequency.

TUNED AMPLIFIER

Triple stage amplifier TR10, TR11, and TR12, is designed to offer some selectivity, but not enough to cause problems with instability. Emitter and coupling capacitors cause some attenuation of frequencies below 10kHz, and the response is sharpened still further by tuned collector load C16, and L8.

When viewed on an oscilloscope, the tuned amplifier output will appear similar to Fig. 3E when echo signals are present. If the oscilloscope is d.c. coupled, and can offer linear timebase sweeps at around 0.2s, then distance can be read off the X axis to give the precise location of all echoes.

DECODER

Having obtained satisfactory echo signals from the receiver tuned amplifier, these must be converted into regular shaped pulses for timing purposes.

In the decoder circuit of Fig. 6, the monostable (TR13 and TR14), responds only to signals above a certain amplitude, determined by the VR7 setting, and thus rejects noise and small, spurious echoes.

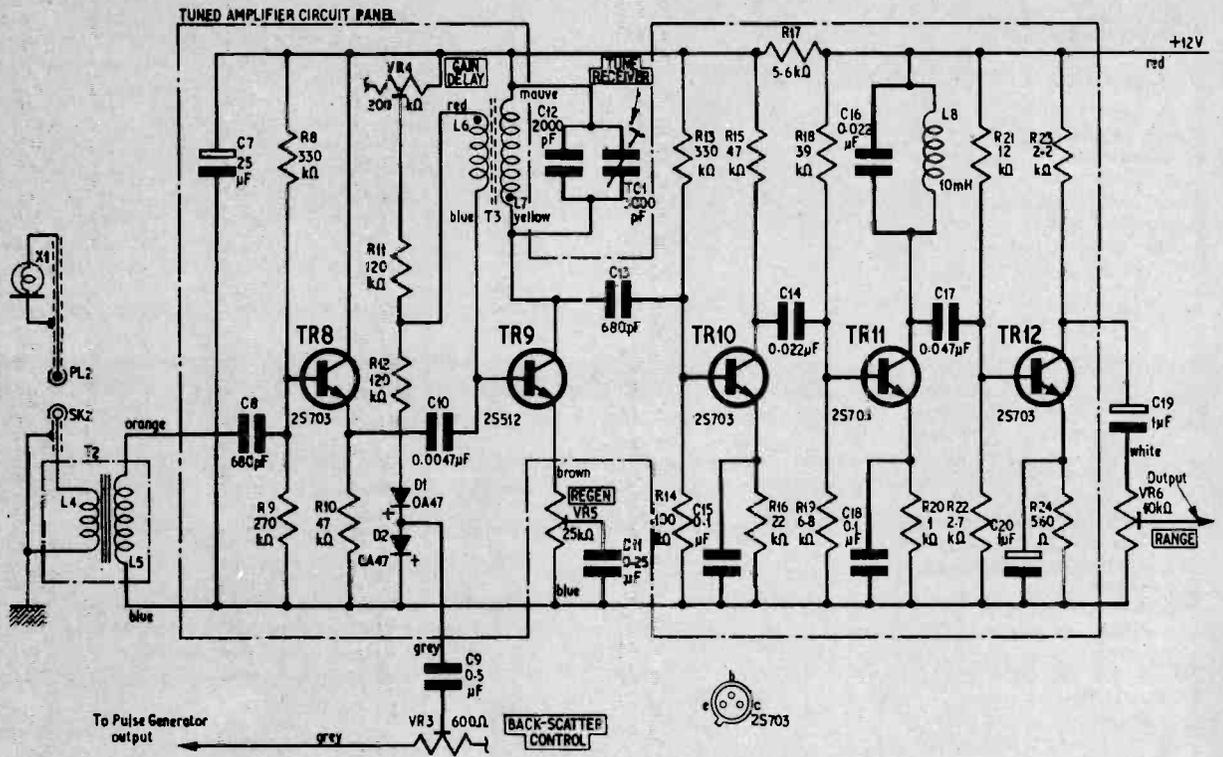


Fig. 5. Circuit diagram of the receiver tuned amplifier

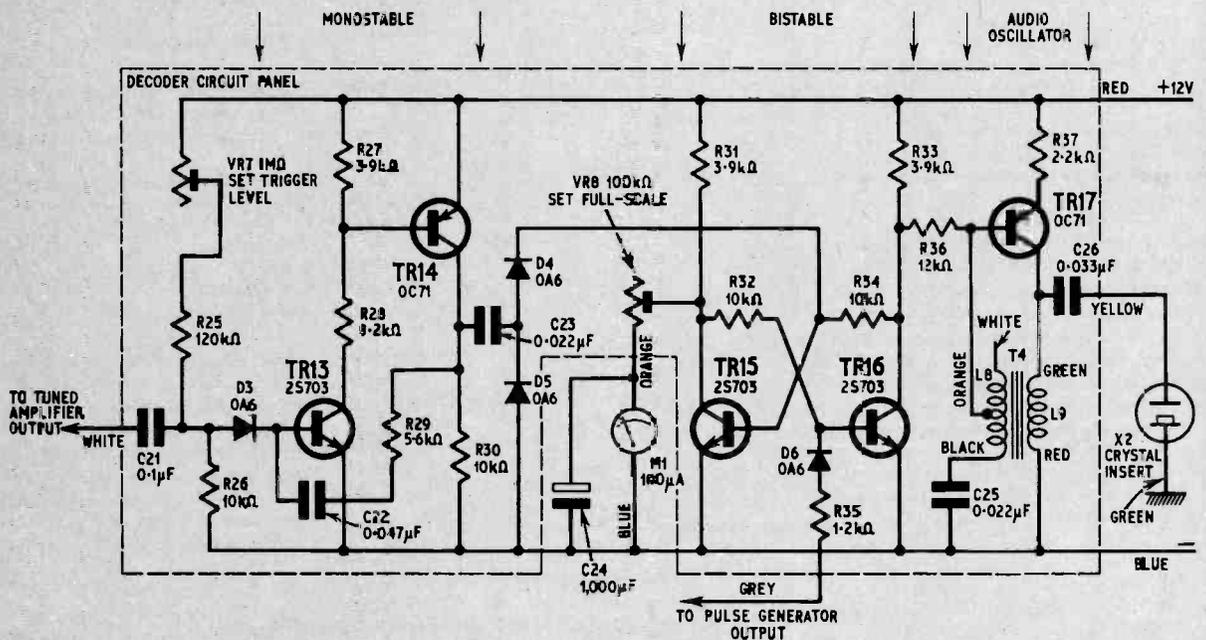


Fig. 6. Circuit diagram of decoder which converts the output from the tuned amplifier into regular shaped pulses for timing purposes

COMPONENTS...

RECEIVER DECODER

Resistors

F.25	120k Ω	R32	10k Ω
F.26	10k Ω	R33	3.9k Ω
F.27	3.9k Ω	R34	10k Ω
F.28	8.2k Ω	R35	1.2k Ω
F.29	5.6k Ω	R36	12k Ω
F.30	10k Ω	R37	2.2k Ω
F.31	3.9k Ω		

All 10%, $\frac{1}{2}$ watt carbon

Capacitors

C21	0.1 μ F moulded polyester 250V
C22	0.047 μ F moulded polyester 250V
C23	0.022 μ F miniature polyester 250V
C24	1,000 μ F electrolytic 12V
C25	0.022 μ F miniature polyester 250V
C26	0.033 μ F miniature polyester 250V

Transformer

T4 LT44 transistor driver transformer (Henry's Radio)

Meter

M1 0-100 μ A MR-65P

Loudspeaker

X2 1in-1 $\frac{1}{2}$ in diameter crystal microphone insert

Transistors

TR13, TR15, TR16 2S703 or 2N929
TR14, TR17 OC71

Diodes

D3, D4, D5, D6 OA6

Miscellaneous

0.1in matrix Veroboard 3.9in \times 1.7in

COMPONENTS...

RECEIVER TUNED AMPLIFIER

Resistors

RB	330k Ω	R17	5.6k Ω
R9	270k Ω	R18	39k Ω
R10	47k Ω	R19	6.8k Ω
R11	120k Ω	R20	1k Ω
R12	120k Ω	R21	12k Ω
R13	330k Ω	R22	2.7k Ω
R14	100k Ω	R23	2.2k Ω
R15	47k Ω	R24	560 Ω
R16	22k Ω		

All 10%, $\frac{1}{2}$ watt carbon

Potentiometers

VR3	600 Ω panel mounting
VR4	200k Ω sub-min horizontal mounting
VR5	25k Ω panel mounting
VR6	10k Ω panel mounting

All presets

Capacitors

C7	25 μ F electrolytic 50V
C3	680pF polystyrene 125V
C9	0.5 μ F metallised 250V
C10	0.0047 μ F miniature polyester 500V
C11	0.25 μ F metallised 250V
C12	2,000pF polystyrene 125V
C13	680pF polystyrene 125V
C14	0.022 μ F miniature polyester 250V
C15	0.1 μ F moulded polyester 250V
C16	0.022 μ F miniature polyester 250V
C17	0.047 μ F miniature polyester 250V
C18	0.1 μ F moulded polyester 250V
C19	1 μ F miniature electrolytic 15V
C20	1 μ F miniature electrolytic 15V

Trimmer Capacitor

TC1 3,000pF Bulgin C.P.7

Inductor

L8 10mH RF choke

Transformers

T2 50k Ω moving coil microphone, matching transformer
T3 LA5 pot core (see text)

Transistors

TR8, TR10, TR11, TR12 2S703 or 2N929
TR9 2S512 or BSY27

Diodes

D1, D2 OA47

Plug

PL1 Coaxial plug

Socket

SK2 Coaxial socket

Microphone

X1 DMI07 or similar

Miscellaneous

0.1in matrix Veroboard 6.9in \times 1.6in
40 s.w.g. enamelled copper wire

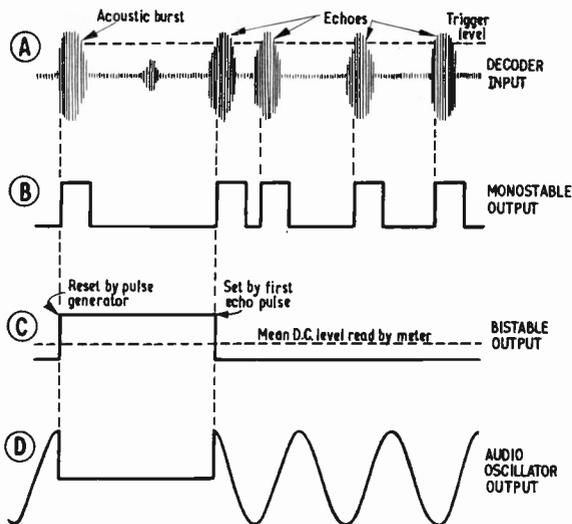


Fig. 7. Waveform sequence appearing at decoder. (A) Typical input signal. (B) Response of monostable. (C) Output of bistable. (D) Audio oscillator output

Demodulated by D3, the leading edge of a signal envelope triggers TR13 on, which in turn switches TR14 on. With the collector of TR14 now close to the positive rail, TR13 remains biased on by the slow charge of C22 through R29, giving a rectangular pulse output from the collector of TR14, of length dependent on C22 and R29 values.

Owing to the positive voltage present on the base of TR13, D3 is reversed biased, and blocks further signals until the monostable switches back into its stable state. The duration of the monostable output pulse determines the minimum distance which can be measured. If C22 is made smaller in value, a point will be reached where the monostable begins to deliver two pulses from each input signal.

BISTABLE

Looking next at the bistable in Fig. 6; a pulse via R35 and D6 from the pulse generator, at the commencement of each acoustic burst, will switch TR15 off and TR16 on. With the collector of TR15 almost at positive rail voltage, C24 will begin to charge via R31 and VR8. If no echo signals are present, C24 is allowed to become fully charged and the meter M1 will read full scale.

In the event of an echo being repeatedly received some time after each transmitter burst, however, the leading edge of a pulse from the monostable will switch TR15 on and TR16 off, thus interrupting the slow charge of C24, and giving a meter reading which is directly proportional to the distance of the nearest echo producing obstacle.

DECODER WAVEFORMS

The decoder waveforms of Fig. 7 show clearly the sequence of events. Fig. 7A is a typical input signal to the decoder, consisting of an acoustic burst waveform followed by four sizeable echo waveforms spaced in time. Fig. 7B gives the response of the monostable to the Fig. 7A signals, with a pulse for each signal envelope.

As the acoustic burst from the monostable, and the reset pulse from the pulse generator occur simultaneously, the bistable ignores the former, but will be

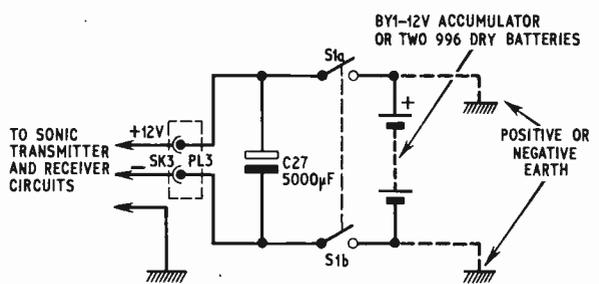


Fig. 8. Power supply circuit suitable for car battery or dry battery working. Battery impedance is minimised by large electrolytic

COMPONENTS . . .

POWER SUPPLY AND BOX

Capacitor

C27 5,000µF 15V

Battery

BY1 12V accumulator or two 996 dry batteries

Plug

PL3 Non-reversible 2 way

Switch

S1 Toggle d.p.s.t.

Socket

SK3 Non-reversible 2 way

Miscellaneous

Universal chassis 6in × 8in × 3in with extra 6in × 8in top plate and 8in × 3in side (Home Radio)

set by the leading edge of the first echo pulse to be received, see Fig. 7C. The bistable can only respond again after it has been reset, and gives an output of duration exactly corresponding to the time taken for the sound to complete its journey.

The inverse occurs with the audio oscillator waveform Fig. 7C; in the event of no echo there is no output from TR17 but an echo from a close obstacle gives an audio oscillator output of long duration.

POWER SUPPLY

There are two possible snags when the Obstacle Locator is powered from a car battery; interference and voltage fluctuations.

Charging circuit contacts, dynamo brushes, and ignition spark gaps generate quite a lot of interference, which could increase the sonic receiver noise input to the point where maximum range suffers.


Although the situation could be improved by incorporating filters and some form of voltage stabilisation, the easiest and cheapest solution is to run the equipment from suitable dry batteries.

Average current consumption of the Obstacle Locator is in the region of 50mA, so two 996 batteries coupled in series will give 100 hours operation.

A power supply circuit suitable for car battery or dry battery working is shown in Fig. 8. The large electrolytic C27 helps to minimise battery impedance.

Part two next month will cover the construction, testing, and calibration of the Sonic Obstacle Locator.

SIREN

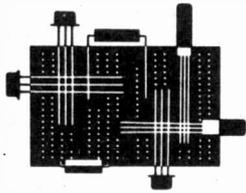

A SPECIAL PROJECT FOR BEGINNERS

MOST readers are probably familiar with the banshee wail of a siren. Rising from a low frequency beginning, the sound rises up in a smooth glissando through baritone to soprano, hovers, then falls, this being maintained through a series of undulating peaks.

For novelty appeal, this particular offering is pitched approximately to those sounds made by American police cars, albeit very much attenuated in decibels. For this reason alone it should prove an attractive project for youngsters.

PULSE GENERATOR

The active ingredients in this design are an *npn* and *pnp* complementary transistor pair arranged to form an astable multivibrator, which would be free running if R2 was connected directly to the positive rail of Fig. 1.

With such a connection the frequency would stabilise around 4kHz, this rate being determined by the time constant, or CR product, of R2 and C2. Mathematically, the pulse frequency is said to vary inversely as this product, which simply means that an increase in value of either R2 or C2 means a decrease in frequency, or alternatively with the values decreased the frequency rises.

The conduction cycle commences with the charging of C2 via R2. As discussed last month, the charging process takes the form of an exponential growth curve of voltage. No conduction takes place in the transistor pair until C2 reaches about 0.7V.

CUMULATIVE ACTION

At this voltage TR1 moves into action, passing current to its load TR2. Up to this point the collector of this transistor is at -9V relative to the emitter and with conduction this goes positive. This is immediately reflected to the base of TR1 which accelerates the overall switching of the transistor pair.

This self-regenerative feedback process, or cumulative action, results in a very sharp pulse at the speaker.

RISE AND FALL

In describing the action of the constant frequency generator it was arranged that R2 was fed from the positive line.

To produce the frequency variations necessary for the siren sound, R2 is in fact connected to the mid-point of a timing circuit C1, R1. S1 is introduced into this net so that rise and fall periods are arbitrary.

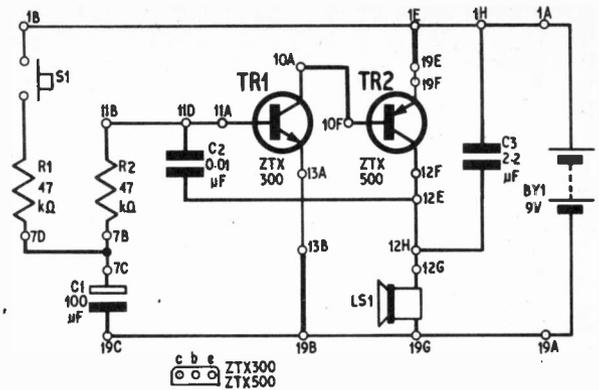


Fig. 1. Circuit diagram of the Siren; link wires are shown as thick lines. Note that an electrolytic capacitor should not be substituted for C3

COMPONENTS . . .

Resistors

R1 47kΩ
R2 47kΩ
½ watt, 10% carbon

Capacitors

C1 100µF elect 15V
C2 0.01µF
C3 2.2µF polyester

Transistors

TR1 ZTX 300
TR2 ZTX 500

Switch

S1 On/off press switch

Loudspeaker

LS1 3Ω 5 inch

Miscellaneous

T-Dec, connecting wire

With S1 closed, C1 charges on a relatively long time constant to a maximum of 4V. A rising voltage across R2 and C2 means, in effect, a diminishing time constant, so the overall frequency starts to rise.

Just as the charge transition is smooth on C2, so is the frequency change which starts at zero and glides up to about 2kHz. The output at LS1 remains constant at 4V during this period, the waveshape produced being shown in Fig. 2.


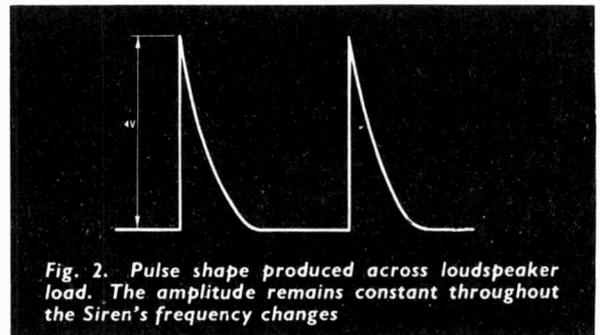


Fig. 2. Pulse shape produced across loudspeaker load. The amplitude remains constant throughout the Siren's frequency changes

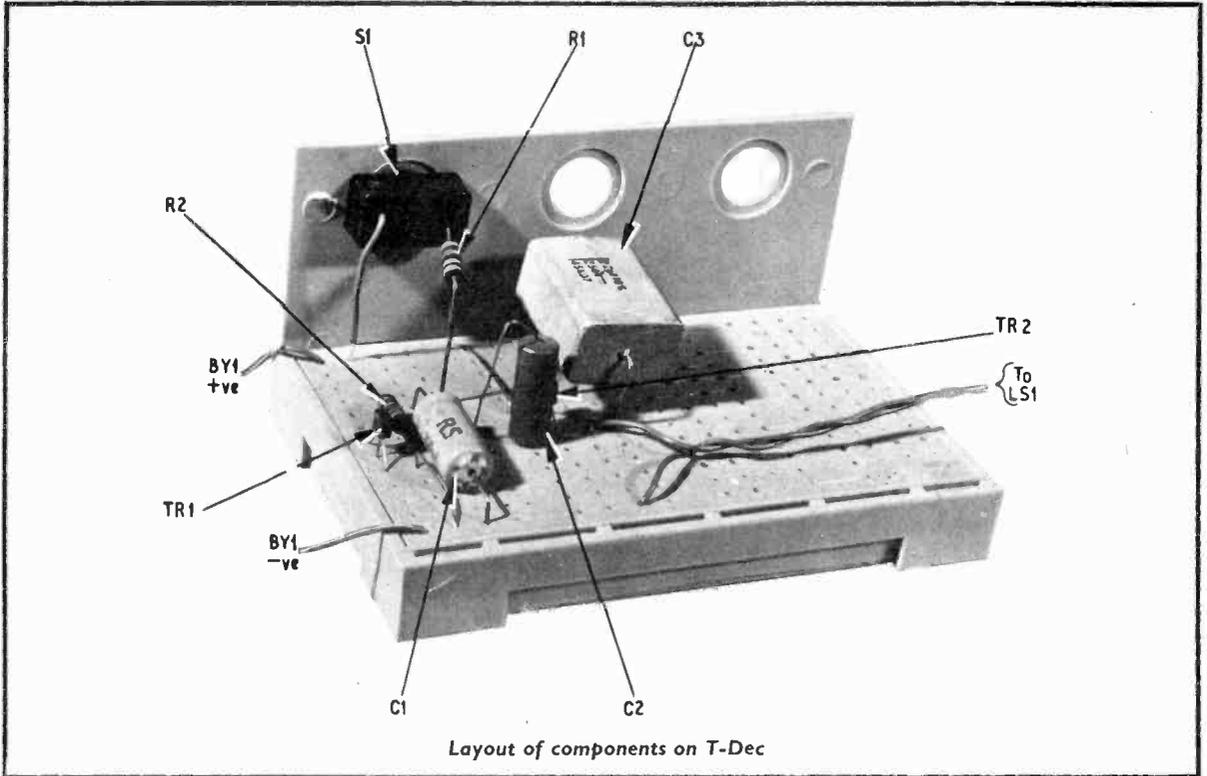

The release of S1 causes the frequency to fall. Since C1 is charged to about half the rail volts, the discharge period is reduced by this factor.

INCREASING THE OUTPUT

Without the inclusion of C3 the power available at the output would be negligible. This capacitor has the effect of increasing the pulse width and so raising the mean d.c. level.

It is most important that a capacitor with a low

power factor be used here; an electrolytic type just will not do.

To alter the frequency of the siren C2 should be changed. An increase in capacitance will mean a reduction in peak frequency and a decrease will raise it.

ALTERNATIVE CONSTRUCTION

A permanent assembly of this unit can be made on Veroboard. Component mounting can be identical to that given for the T-Dec as the hole matrix for the board is identical.

NEWS BRIEFS

Scouts Communications

THE CENTRE of the 3rd Bracknell Scouts was turned into a complete communications centre for a weekend in October by equipment loans from the nearby Racal Electronics Group. The Racal Amateur Radio Club GB3RAC, also loaned the Scouts equipment and the members assisted operations for day and night watches.

The centre had four complete transmitting/receiving stations, five separate monitoring stations manned by Scouts, a news and weather bureau with all necessary sound and TV monitoring receivers, teleprinter, and Mufax picture receiver.

Pictures of weather charts included one from Khabarovsk in Eastern Siberia. Other weather information was intercepted from weather ships in the Atlantic.

Jamboree contacts were made with numerous Scout Groups throughout the world, including Australia, S. Africa, U.S.A., Middle East and Europe.

Over 200 Scout Leaders and Scouts shared watch duties throughout the weekend and there were over 200 spectators. The photograph left shows part of the communications centre operating.



SPACEWATCH

By Frank W. Hyde

A DECADE AHEAD

As 1971 opens it is perhaps worthwhile to look at the next decade as planned at this moment. Certain programmes have already been put in hand and these have been covered by previous *Spacewatch* articles. However, in order to take an overall look at the next decade some of the programmes will of necessity be noted again.

One of the most important items in the programme is to find ways of reducing the cost of space operations. For this reason the development of the space shuttle will be a priority venture. The prospect of a re-usable shuttle vehicle which can travel between the Earth and space stations in Earth orbit offers a system that is within the range of present technology. Already the design stage has reached a definitive study. The vehicle in its present form will be launched by a booster from a rocket pad and return to Earth to land like an aircraft.

SPACE TUGS

To this must be added the rather newer proposal for a space tug which would serve for goods and personnel transport from space station to space station. Other operations to be undertaken would be the raising of satellites from lower orbits to higher and synchronous orbits and the firing of automated probes from Earth orbit into orbits that will enable a further investigation of the planets. The tug would ride in the shuttle cargo compartment. Already these programmes envisage international participation in a greatly extended manner.

In the past decade there has been considerable co-operation so far as contractors were concerned, but the new thinking is more in the terms of a cost sharing as well as contracting between the U.S.A., the United Kingdom, Federal Republic of Germany, France, Belgium and Italy. This could mean that the European Nations will provide half of the cost of the space tug (about 1,000 million dollars). The cost of the space programme for the shuttle is estimated at about 4,500 million dollars, and for the 12 man space station

upwards of 4,000 million dollars. There is to be a standardisation of technique, and both vehicles should be operative by 1978.

SKYLAB

This will be a large orbiting workshop which will examine the capability of men to live and work in space over long periods. It will use systems already developed for the *Apollo* missions. Later, there will be even more sophisticated vehicles with the exchange of personnel on varying tours of duty.

EARTH RESOURCES SATELLITES

One of the major projects already well under way is that of surveying the earth to assess its potential for the future. This programme will have an unprecedented facility for the study of crops, the location of new sources of water and the prospecting for mineral deposits. There will be the more extended use of space vehicles in the fields of weather forecasting, communications, air traffic control, geodetic map making and navigation. There will also be concentration on the use of television for education particularly directed toward the under-developed countries.

The *Apollo* programme, although curtailed somewhat from the original one, will nevertheless offer an exciting new extension of moon exploration. *Apollo 14* site will be the same as that which was originally scheduled for *Apollo 13*, that is the Fra Mauro rugged region. The site for *Apollo 15* has now been decided; it will land in the lunar plain much further North than any previous mission. There is an area known as the Hadley-Apennine region which has the 8,000 ft. Apennine range on one side and the 60 mile long meandering canyon, 600 ft. deep, known as the Hadley Rille, on the other. It is an important region and will yield a great deal of valuable scientific data.

The astronauts will be able to gather material from the base of the mountains, some of which may date from the old lunar crust, which existed more than 4,000 million years ago. It is thought this may be older

than the Mare Imbrium basin which was probably formed by meteoritic impact. There may also be materials, thrown out by this cataclysmic impact, which originated deep within the moon.

On this mission the Lunar Rover vehicle, electrically powered, will be in operation for the first time. The crew will be able to go some miles from the base of operations in order to carry out experiments, and set up scientific instruments. The crew will be David Scott, Alfred Warden and James Irwin. Launch date is likely to be July 1971. The following two *Apollo* missions (16 and 17) are scheduled for January 1972 and June 1972; no sites or crews have been decided at the moment.

MARS PROBES

These have already been noted in some detail in *Spacewatch* for June 1970 and this programme gets under way with the first launches in 1971.

GRAND TOURS

These will take advantage of the position of the planets in the solar system during the next few years. In the case of the first mission the next possible time for this to be done will not come again for 200 years and the second planned mission could not be undertaken for another 100 years. Therefore, these programmes are of great importance, for to achieve the objectives of these missions with our present technology, the gravitational effects of the planets will be needed for an effective gain in momentum for the vehicles as they move from one area to another. These will of course be unmanned. The manned tours will need nuclear or some other source of power for this to be successful. The testing of nuclear powered rockets will be made in 1978 with unmanned craft.

The *Mariner* Venus-Mercury tour will begin the series and for the first time man may be able to see a close-up of the surface of Mercury. The next will begin in 1977 with one or perhaps two unmanned craft launched toward Jupiter.

When the spacecraft arrives in the vicinity of Jupiter it will swing round the planet under the influence of the local gravitational field; four years later it will reach the planet Uranus where again gravity will influence the path to project it toward the end of its journey five years later at the planet Neptune in 1988 after a 3,000 million mile trip.

A further launch will be in 1979. The route will on this mission be more direct to Jupiter and by 1980 will swing round Saturn and will head for Pluto which it should reach five years later. Pluto itself is the most distant planet from the Earth and will at that time be some 3,700 million miles distant.



Sign here..!

**for your
miniature
soldering
iron.**

CN 15 Watts. Ideal for miniature and micro miniature soldering. 18 interchangeable spare bits available from .040" (1mm) up to 3/16" For 240, 220, 110, 50 or 24 volts. **from 34!-**



G18 watts. Fitted 3/32" bit for miniature work on production lines. Interchangeable spare bits, 1/8", 3/16" and 1/4" available. For 240, 220 or 110 volts. 36/-



E20 watts. Fitted with 1/4" bit. Interchangeable spare bits 3/32", 1/8", 3/16" available. For 240, 220, 110 volts. 36/-




ES25 watts. Fitted with 1/8" bit. Interchangeable bits 3/32", 3/16" and 1/4" available. Ideal for high speed production lines. For 240, 220, 110, 24 or 12 volts. 36/-



F40 watts. Fitted 5/16" bit. Interchangeable bits 1/4", 3/16", 1/8", 3/32" available. Very high temperature iron. For 240, 220, 110, 24 or 20 volts. 47/0. Spare bits and elements for all models and voltages immediately available from stock.

Complete precision soldering kit

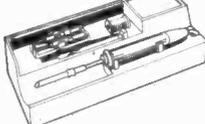

PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional.

This kit—in a rigid plastic "tool-box" — contains

- Model CN 15 watts miniature iron, fitted 3/32" bit. Interchangeable spare bits 3/32", 1/8", 3/16"
- Reel of resin-cored solder
- Felt cleaning pad
- Stand for soldering iron

From Electrical and Radio Shops or send cash to Antex. **55!-**



Model CN 240/2
15 watts - 240 volts
Fitted with nickel plated bit (3/32") and in handy transparent pack. From Electrical and Radio Shops or send cash to Antex. **34!-**



PRECISION MINIATURE SOLDERING IRONS

Antex, Mayflower House, Plymouth, Devon. Telephone: Plymouth 67377/8. Telex: 45296. Giro No. 2581000.

- Please send me the Antex colour catalogue
- Please send me the following irons

Quantity Model Bit Size Volts Price

.....
.....
.....

I enclose cheque/P.O./cash value

NAME

ADDRESS

PE 1

VARIABLE VOLTAGE TRANSFORMERS

LIGHT SENSITIVE SWITCH

Kit of parts, including ORP12 Cadmium Sulphide Photocell, Relay, Transistor and Circuit, etc., 6-12 volt d.c. op. price 25/- plus 2/6 P. & P. ORP12 including circuit. 12/6 each. Post Paid.

A.C. MAINS MODEL. Incorporates Mains Transformer, Rectifier and special relay with 2x5 amp. mains c/o contacts. Price inc. circuit, 47/6 plus 2/6 P. & P.

LIGHT SOURCE AND PHOTO CELL MOUNTING

Precision engineered light source with adjustable lens assembly and ventilated lamp housing, to take MBC bulb. Separate photo cell mounting assembly for ORP12 or similar cell. Both units are single hole fixing. Price per pair £2.15.0. P. & P. 3/6.

SANWA MULTI RANGE METERS

New Model U-50DN Multi tester, 20,000 OPV, mirror scaled with overload protection. Ranges—d.c. volts: 100mV, 0.5V, 5V, 250V, 1,000V; a.c. volts: 2.5V, 10V, 50V, 250V, 1,000V; d.c. current: 5µA, 0.5mA, 5mA, 50mA, 250mA. Complete with battery and test probe. £8.00 post paid. Ten other models. Leaflet on request.

'AVO' MODEL 48A

Ex-Admiralty in good condition with instructions, leads, plus d.c. Shunts for 120 amp and 480 amp. c. Transformer for 60 amp and 240 amp. Multiplier for 3,600V. Complete outfit in fitted case. £15.0.0. P. & P. 10/-.

ELECTRONIC ORGAN KIT

Easy to build, Solid State. Two full octaves (tess sharps and flats). Fitted hardwood case. Powered by two penlite 1½V batteries. Complete set of parts including speaker, etc., together with full instructions and 10 tunes. Have all the pleasure of building this instrument and finish with a functional and instructive gift for any boy or girl. Price £3.0.0. P. & P. 4/6.

50 in 1 ELECTRONIC PROJECT KIT

50 easy to build Projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. etc. Price £7.15.0. P. & P. 6/-.

RECHARGEABLE BUTTON CELLS

2x1.2V, 250 MA HR Nickel Cad. Cells, connected to give 2.4V @ 25 milliamperes 10 hour rate, complete with 200/250V a.c. charger. Fully tested and unused. Price 9/6 each, plus 1/6 P. & P. or 2 units for £1 post paid.

UNISELECTOR SWITCHES

NEW 4 Bank 25 Way 24V d.c. operation. £5.17.6, P. & P. 2/6. 6 Bank 25 Way 24V d.c. £6.10.0, P. & P. 2/6. 8 Bank 25 Way 24V d.c. operation. £7.12.6 plus 4/6 P. & P.

VENNER Electric Time Switch

200/250V Ex. GPO tested. Manually set 2 on, 2 off every 24h. Override switch: 10A £2.15.0, 15A £3.5.0, 20A £3.15.0. P. & P. 3/6. Also available with solar dial ON dusk, OFF dawn. Price as above.

INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V

BRAND NEW

Keenest prices in the country. All Types (and Spares) from 1/2 to 50 amp from stock.

SHROUDED TYPE

1 amp, £5.10.0. 2.5 amp, £6.15.0. 5 amp, £9.15.0. 8 amp, £14.10.0. 10 amp, £18.10.0. 12 amp, £21.0.0. 15 amp, £25.0.0. 20 amp, £37.0.0. 37.5 amp, £72.0.0. 50 amp, £92.0.0.

OPEN TYPE (Panel Mounting) 1/2 amp, £3.18.6.

1 amp, £5.10.0. 2 1/2 amp, £6.12.6. Carr. extra on open types.



STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT
Speed adjustable 1 to 36 Flash per sec. All electronic components including Veroboard S.C.R. Unijunction Xenon Tube and instructions £5.5.0 plus 5/- P. & P.

NEW INDUSTRIAL KIT

Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. Price 9 gns. 7/6 P. & P.

HY-LYGT STROBE

This strobe has been designed and produced for use in large rooms, halls and the photographic field, and utilizes a silica plug-in tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. Price £10.17.6. P. & P. 7/6.

7-inch POLISHED REFLECTOR

Ideally suited for above Strobe kits. Price 10/6. P. & P. 2/6 or post paid with kits.

Superior Quality Precision Made NEW POWER RHEOSTATS

100 WATT. 1 ohm, 10A; 5 ohm, 4.7A; 10 ohm, 3A; 25 ohm, 2A; 50 ohm, 1.4A; 100 ohm, 1A; 250 ohm, 0.7A; 500 ohm, 0.45A; 1 kΩ, 280 mA; 1.5 kΩ, 230 mA; 2.5 kΩ, 2A; 5kΩ, 140 mA. Diameter 3 1/2 in. Shaft length 3 in. dia. 1 1/2 in. All at 30/- each. P. & P. 1/6.
50 WATT. 1/5/10/25/50/100/250/500/1/1.5/2.5/5kΩ. All at 22/- each. P. & P. 1/6.
25 WATT. 10/25/50/100/250/500/1/1.5/2.5/5kΩ. All at 15/6 each. P. & P. 1/6.



RELAYS NEW SIEMENS, PLESSEY, Etc. MINIATURE RELAYS - COMPETITIVE PRICES

	2	3	4	1	2	3	4
52	6-9	6M	12/6*	700	12-24	2 c/o	12/6*
160	6-12	2 c/o E/E	8/6*	700	16-24	6M	12/6*
185	6-12	4 c/o E/E	10/6*	1250	24-36	4 c/o	12/6*
230	6-12	2 c/o	12/6*	1250	36-45	6M	12/6*
280	6-12	2 c/o	14/6*	2500	36-45	6M	12/6*
700	16-25	4M 2B	12/6*	5800	80-85	4 c/o	12/6*
700	16-24	4 c/o	15/6*	9000	40-70	2 c/o	10/-*
				15K	85-110	6M	10/-*

(1) Coil; (2) Working d.c. volts; (3) Contacts; (4) Price E-E Ex. Equipment. All Post Paid.

MAINS RELAY

230V a.c. coil 3 c/o. 10 amp a.c. contacts, 14/6 plus 1/6 P. & P.

HOSIDEN DH-02-S Stereo Headphones

8 ohm impedance 20-12,000Hz. Adjustable head band. Price only 47/6. P. & P. 2/6. Complete with lead and stereo jack plug.

MOTOROLA MAC II/16 PLASTIC TRIAC 400 PIV. 8 AMP

Now available EX STOCK. Supplied with full data and applications sheet. Price 21/- plus 1/6 P. & P.

PARVALUX TYPE SD19 230/250 VOLTS A.C.

REVERSIBLE GEARED MOTOR

30 r.p.m. 40lb in. Position of drive spindle adjustable to 3 different angles. Mounted on substantial cast aluminium base. Ex-equipment. Tested and in first class running order. A really powerful motor offered at a fraction of makers' price. 6 GNS. P. & P. 10/-.



NEW 9TH EDITION RADIO VALVE AND TRANSISTOR DATA

Characteristics of 3,000 Valves and Cathode Ray Tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits

Compiled by A. M. Ball

15/- Postage 2/-

MAKING AND REPAIRING TRANSISTOR RADIOS

by W. Oliver. 20/- Postage 1/-.

RSGB AMATEUR RADIO TECHNIQUES

by Pat Hawker. 20/- Postage 1/6.

ELECTRONICS FOR TECHNICIAN ENGINEERS

by W. W. Smith. 55/- Postage 3/6.

SECURITY ELECTRONICS

by John E. Cunningham. 34/- Postage 1/-.

RADIO AND AUDIO SERVICING HANDBOOK

by Gordon J. King. 60/- Postage 2/6.

TELECOMMUNICATIONS POCKET BOOK

by T. L. Squires. 24/- Postage 1/-.

110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR

by R. M. Marston. 18/- Postage 1/-.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON, W.2

Phone: PADDINGTON 4185 Closed Saturday 1 p.m.

OSMABET LTD.

We make transformers amongst other things

MAINS TRANSFORMERS

Prim 200/240V a.c. TX1 425-0-425V 250 mA, 6.3V 4A CT, 6.3V 4A CT, 0-5-6.3V 3A, 135/-; TX2 250-0-250V 150 mA, 6.3V 4A, CT, 0-5-6.3V 3A, 78/6; TX3 300-0-300V 120 mA, 6.3V 2A, CT, 6.3V 2A, 6.3V 1A, 78/6; TX8 250-0-250V 65 mA, 6.3V 1.5A, 42/-; MT1 200V 30 mA, 6.3V 1A, 24/-; MT2 230V 45 mA, 6.3V 1.5A, 29/6; MT3 250V 60 mA, 6.3V 2A, 37/6; MT5 Prim 110/240V Sec 250V 100 mA, 6.3V 2A, 45/-.

MULTIVOLT TRANSFORMERS

Prim 200/240V a.c. OMT4/1 one tapped sec. 5-20-30-40-60V giving 5-10-15-20-25-30-35-40-50-60, 10-10 2A 0-20-30, 30-0-30V a.c. 1A, 45/-; ditto transformer 2A OMT5/2, 67/6; OMT6/1 one tapped sec. 40-50-60-80-90-100-110V, giving 10-20-30-40-50-60-70-80-90-100-110V, 10-0-10, 20-0-20, 30-0-30, 40-0-40, 50-0-50V a.c. 1A, 67/6.

LOW VOLTAGE TRANSFORMERS

Prim 200/240V a.c.: 6.3V 1.5A, 16/9; 3A, 20/-; 6A CT, 34/-; 12V 1.5A, 21/-; 3A CT, 34/-; 6A CT, 45/-; 18V 1.5A CT, 26/6; 24V 1.5A CT, 34/-; 3A CT, 56/6; 6A, 75/-; 8A, 112/6; 12A, 185/6.

MIDGET RECTIFIER TRANSFORMERS

For FW rectification, size 11/2 x 1 1/2 in. Prim 200/240V a.c., output PPT1 0-0-9V 0.3A, PPT2 12-0-12V 0.25A, PPT3 20-0-20V 0.15A, 22/6 each.

OUTPUT TRANSFORMERS

Mullard 5/10 UL, 67/6; 7W stereo U.L., 60/-; 3W PPS, 30/-; P.P.11K/3-8-10ohm, 21/-; Multi ratio 7/10W, 35/-; 30W (KT66, etc.), 3-10ohms, 78/6; 50W (EL34 KT88, etc.), 135/-; 100W (E134 KT88, etc.), 225/-; Standard 3-W 0/1P 5K/30hm or 10K/30hm, 14/6; auto matching transformer 10W, 3-8-16 ohm up or own, 15/-; 100V line trans. to order.

LOUDSPEAKERS

New, boxed, famous makes, 25W, 110/-; 35W, 130/-; 50W, 180/-; 60W, 215/-; 100W, 350/-; E.M.I. 13 x 8in, 10W, 3, 8 and 16ohms at 45/- each; Hi-Fi 13 x 8in, 10W speakers, fitted two tweeters and crossover network 3, 8 and 16ohms, 80/- each.

BULK TAPE ERASERS

Instant erasure of magnetic tape, demagnetizing of tape heads. 200/240V ac, 47/6 post 2/6, leaflet S.A.E.

LT FLUORESCENT LIGHTING

6, 12, 24V DC 12v fittings with tube, 8 watt 75/-, 13 watt 125/-; etc., inverters from 8 to 50 watt, single or twin tubes, from 135/-, extensive range. Lists, S.A.E.

Carriage extra all orders

S.A.E. ALL ENQUIRIES PLEASE, MAIL ORDER ONLY
46 Kenilworth Road, Edgware, Middx. HA8 9YG
Tel. 958 9314

SERVICE TRADING CO

All Mail Orders—Also Callers—Ample Parking Space
Dept. P.E. 57 BRIDGMAN ROAD, LONDON W4 5BB
Phone 01-995 1560 SHOWROOM NOW OPEN CLOSED SATURDAY

Personal callers only
9 LITTLE NEWPORT ST.
LONDON, W.C.2. Tel. 01-437 0576

MAKING THE MOST OF LOGIC IC's

PART SEVEN—By R. W. COLES

TTL FLIP-FLOPS

THE range of bistables, or flip-flops as they are usually termed in i.c. parlance, is more varied in the TTL family than in either DTL or RTL. There is, in fact, a flip-flop to suit every occasion, or for those who dislike using a different component for each specialised application, there is one flip-flop which may be used for any of the normal storage circuits.

Flip-flops are one of the most important elements in a logic system, all types having one feature in common. They provide storage of one binary digit for any length of time which may be necessary, as long as the power is applied.

The differences between the various types occur only in the way that the data to be stored is "written" into them, their outputs always consist of a true and an untrue indication of the digit they contain. By connecting them together in the appropriate fashion, it is possible to build many types of counters or dividers, shift registers, and memories, which may contain a complete binary word.

DATA ENTRY

Data may be entered into a flip-flop either asynchronously, i.e. at any time, regardless of the original contents or the state of the clock pulse, or synchronously, i.e. the data is entered only when a clock pulse "enables" the data inputs.

The flip-flops in the TTL family usually have both synchronous and asynchronous inputs, which makes them most versatile in use. In fact, so many useful features have been packed into such a small package, that the discrete, specialised designs of ten years ago seem primitive in comparison.

Apart from the usual types of data entry mentioned above, TTL synchronous inputs can be further subdivided into either those which employ the positive edge of the clock pulse for gating (edge-triggered), or those which employ both edges of the clock pulse (master/slave).

EDGE TRIGGERED TYPE

With the edge-triggered type, assuming that the data to be entered is waiting at the inputs, as the clock pulse starts to rise this data is entered into the storage latch, and is thus immediately present at the outputs. As soon as the clock pulse has passed the threshold of the input gates, the input data is locked out, and can have no effect on the stored information until the clock rises again.

MASTER/SLAVE

The master/slave type is a little more complex in operation, as the individual flip-flops of this type really consist of two interconnected bistable sections, termed the master section and the slave section. Information enters the master section as the clock pulse rises, but this information does not appear at the outputs immediately because of the interposition of the slave section.

The slave bistable is also clocked, but through an inverter. The slave sees a positive clock pulse when the main clock pulse is actually falling, and enters the data present at the output of the master latch, and transfers it immediately to its outputs, which are also the outputs of the flip-flop as a whole.

Ignoring what goes on inside such a flip-flop and looking at it just as a "black box", information enters on the positive excursion of the clock, and appears at the outputs on the negative excursion. A simplified logic diagram of this type is shown in Fig. 7.1, together with a diagram of clock action.

Master/slave JK flip-flops form the backbone of TTL counting circuits, giving maximum versatility at the expense of a slightly higher power dissipation and slightly lower maximum toggle frequency than the edge-triggered type.

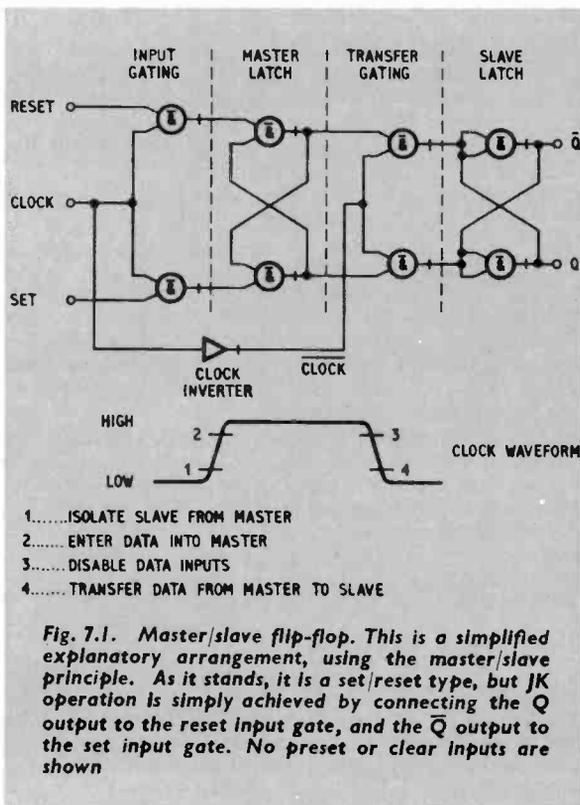


Fig. 7.1. Master/slave flip-flop. This is a simplified explanatory arrangement, using the master/slave principle. As it stands, it is a set/reset type, but JK operation is simply achieved by connecting the Q output to the reset input gate, and the Q-bar output to the set input gate. No preset or clear inputs are shown

A few examples of the many flip-flops available of both edge-triggered and master/slave type are given with their package outlines in Fig. 7.2. Note that some JK types have several J and K inputs, so that gated inputs for synchronous counters will not require separate gate packages.

Some of the flip-flops have no preset input—only clear. These are useful for counter circuits, where the asynchronous inputs are not needed other than to set up the all zeros condition before a count sequence.

TYPE-D FLIP-FLOP

There is one "odd-ball" which is a little different from the rest—the 7474 type "D" flip-flop. This one is intended specifically for shift-register applications, and belongs to the edge-triggered group.

It embodies full asynchronous input capability, but has only one data input D. The other data input is obtained internally by inverting the information on the D input. This means that only one connection is necessary to transfer data from one stage of a shift register to the next.

Perhaps this is not so obvious an advantage until you consider that many shift registers require inputs from several sources, in which case the external gating is cut by half when using the type D.

Although it is intended only for register use, it may be used in ripple counters by connecting the \bar{Q} output back to the D input, but this is by no means the best choice of flip-flop for such use.

TTL COUNTERS

Having discussed what types of flip-flop are available, it is possible to have a look at some applications. To start, let us examine counting circuits. Simple ripple counters were described in the sections on RTL and DTL, and should help here to understand the principles involved in TTL.

RIPPLE COUNTER

Ripple counters are the simplest type of design using TTL i.c.s; all that is necessary is to connect the Q output of the first flip-flop to the clock input of the second, and so on, the input being connected to the clock of the first flip-flop in the chain.

The maximum number of separate states is given by 2^n , where n is the number of flip-flops so connected. Thus a four-stage counter has sixteen states, and a five-stage counter has thirty-two states.

If a count which is not a binary multiple is required, it is necessary to force the counter to skip some of its usual states. There are several ways to achieve this, the simplest method being to detect the desired final count + 1 with a NAND gate, and use its output to reset all the flip-flops in the counter to zero.

This method may, however, result in a "race" condition if one of the counter stages resets more readily than the others, causing the NAND gate output to disappear before all stages are reset. For this reason it is not commonly used, although it is possible to include some sort of delay, such as a monostable, in the reset path to ensure that the reset pulse will last long enough to do its job properly.

IMPROVED DIVIDER

A much better method of dividing by a number which is not a binary multiple is to feed the flip-flop outputs which are in the 1 state at the desired final count, along with the counter input, or clock, to a NAND gate, and use the resultant output to set all the counter stages to 1.

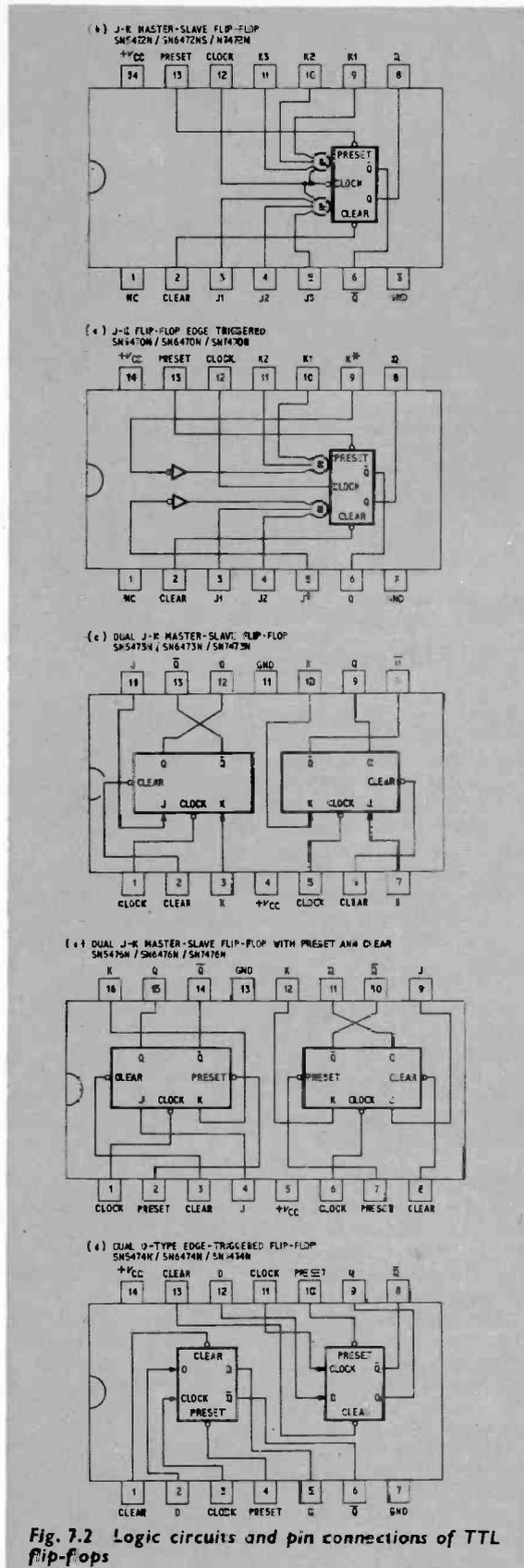


Fig. 7.2 Logic circuits and pin connections of TTL flip-flops

COMPLETE STEREO SYSTEM

FOR ONLY

39 GNS

CARRIAGE 35/-



PREMIER STEREO SYSTEM "ONE" Consists of an all transistor stereo amplifier. Garrard 2025 T/C auto/manual record player unit fitted stereo/mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor amplifier has an output of 5 watts per channel with inputs for pick-up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector. Power on/off, stereo/mono switch. Brushed aluminium front panel. Black metal case with teakwood ends: Size 12 x 5 1/2 x 3 1/2 in. high (Amplifier available separately if required £14.19.6. Carr. 7/6). **Now Available MATCHING F.M. TUNER 21gns.**

PREMIER STEREO SYSTEM "TWO"

As system "ONE" above but with Garrard SP25.


PREMIER PRICE 45 Gns. Carr. 35/-

MIDLAND AM/FM STEREO TUNER AMPLIFIERS

Two new all solid state receivers from Midland at economical prices. Beautifully styled in slimline cabinets.



MODEL 19-520

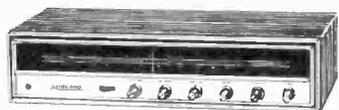

MODEL 19-542

Specifications	Model 19-520	Model 19-542
Semi-conductors	19 transistors, 12 diodes, 2 varistors	22 transistors, 12 diodes
Tuning range	FM 88-108 MHz FM Stereo Multiplex AM 535-1635 kHz	FM 88-108 MHz FM Stereo Multiplex AM 535-1605 kHz
Aerial	Internal AM and external FM	Internal AM and external FM
Frequency Response	30-17,000 Hz	30-20,000 Hz
Power Output	2 1/2 watts rms per channel (8 watts music power)	4 watts rms per channel (18 watts music power)
Inputs	Ceramic phono	Magnetic/Ceramic phono and aux.
Speaker impedance	4-8 ohm	8 ohm
Controls	Power on/off, Volume, tone, balance, tuning, AFC, Stereo indicator	On/off, Volume, bass, treble, balance, tuning, AFC, Stereo indicator
Function	AM, FM, FM Stereo, Phono (Stereo indicator light)	AM, FM, FM Stereo, Ceramic, Magnetic, Aux.
Size	15" x 8 1/2" x 3 1/2"	16 1/2" x 9 1/2" x 3 1/2"
PRICE	37 GNS. Carr. & Ins. 10/-	42 GNS. Carr. & Ins. 10/-

TELETON SAQ203E STEREO AMPLIFIER



A small but powerful amplifier designed for stereo hi-fi reproduction. 10 watts per channel music power. Inputs for Gram (Magnetic and Crystal), Tuner and Auxiliary. Tape Record output. Controls: Volume, Balance, Bass, Treble, Stereo/Mono slide switch. Stereo headphone socket. Attractive oiled walnut cabinet with brushed aluminium front panel. List Price £28.7.0.
PREMIER PRICE 22 Gns. P. & P. 10/-

PREMIER STEREO SYSTEM "FOUR"

Teleton SAQ203E Amplifier (as above)	£23.2.0
Garrard SP25	£11.9.8
Shure M3D	£6.18.8
Teak base and cover	£5.10.0
Pair of Hi-Fi Enclosures fitted E.M.I. Speakers	£26.5.0
Total cost if purchased separately	£78.16.0

PREMIER PRICE 65 GNS. Carr. 35/-

E.M.I. 13x8in. HI-FI SPEAKERS

Fitted two 2 1/2in tweeters and crossover network. Available with 8 or 15 ohm impedance. Handling capacity 10W. Brand new.



79/6 P. & P. 7/6

HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 3 1/2in. speaker units with soft padded ear muffs. Adjustable headband. 8 ohm impedance. Complete with 6ft. lead and stereo jack plug.



49/6 P. & P. 5/-

MONO HEADPHONES 2000 ohm 14/6 P. & P. 2/6.
STEREO STETHOSCOPE SET Low imp. 25/- P. & P. 2/-
MONO STETHOSCOPE SET Low imp. 10/6 P. & P. 2/-

MIDLAND CASSETTE TAPE RECORDER 12-115

Solid state incorporation of a tuning piano key controls for trouble-free 2-track recording. Inputs for mike and aux. Earphone socket. Complete with batteries and earpiece. Size 10 1/2in x 5 1/2in x 2 1/2in.
PREMIER EXCLUSIVE: £16.10.0 P. & P. 7/6



POCKET SIZE MULTI-TESTER With wide angle, jewelled meter movement, ceramic long-life, low-loss switching, tough impact resisting case. Sensitivity 20,000 ohms/volt D.C. 10,000 ohms/volt A.C.
19 Ranges: 0-5-25-50-250-500-2500 volts D.C. 0-10-50-100-500-1000 volts A.C. 0-50µA-25mA-250mA D.C. 0-6000 ohms-6 megohms, 10µA µF-0.001 mfd-1 mfd. -20 to +224B. Complete battery, test lead and instructions.
£4.19.6 P. & P. 3/6



"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

LP3 3" 250' P.V.C.	5/6	LP6 5 1/2" 1200' P.V.C.	12/6
TT3 3" 450' POLYESTER	7/6	DT6 5 1/2" 1800' POLYESTER	22/6
DT3 3 1/2" 600' POLYESTER	11/6	TT6 3 1/2" 2400' POLYESTER	37/6
SP6 5" 800' P.V.C.	8/6	SP7 7" 1200' P.V.C.	12/6
LP5 5" 900' P.V.C.	10/-	TT7 7" 1800' P.V.C.	15/-
DT5 5" 1200' POLYESTER	15/-	DT7 7" 2400' POLYESTER	25/-
		TT7 7" 3600' POLYESTER	50/-

TAPE SPOOLS 3" 1/-, 5", 5 1/2", 7" 1/0.
Post and Packing 3" 1/-, 5", 5 1/2" 1/6, 7" 2/- (3 reels and over Post Free.)



SPECIAL OFFER!



Garrard SP25 Mk. II Single Record Player, Fitted Goldring 850 Magnetic Stereo Cartridge. Complete in Teak Plinth with Rigid Perspex Cover. Total list Price over £24.
PREMIER PRICE 18 Gns. P. & P. 10/-



TAPE CASSETTES

C60 (60 min.)	7/6 3 for 21/-
C90 (90 min.)	12/6 3 for 36/-
C120 (120 min.)	17/6 3 for 51/-

P. & P. 1/-

All cassettes can be supplied with library cases at 6d extra each.

PREMIER RADIO

23 TOTTENHAM COURT ROAD, LONDON, W.1 Tel: 01-636 3451



ELECTRIC CLOCK WITH 25 AMP SWITCH

Made by Smith's, these units are as fitted to many top quality cookers to control the oven. The clock is manually driven and frequency controlled. It is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only **59/6**, less than the value of the clock alone post and insurance 2/9.



20 AMP ELECTRICAL PROGRAMMER

Learn in your sleep: Have Radio playing and kettle boiling as you awake—switch-on lights to ward off intruders—have warm house to come home to. All these and many other things you can do if you invest in an Electrical Programmer. Made by the famous Smith's Instrument Company. This is essentially a 230V volt mains operated clock and a 20 amp switch. The switch-off time which can be delayed up to 12 hours (continuous, variable not stepped). Similarly the switch-on time can be delayed. This is a beautiful unit, size 5 1/2 x 3 1/2 in. deep. Metal encased, glass fronted with chrome surround. Offered at **47/6** plus postage and insurance.



MAINS CONNECTOR

A quick way to connect equipment to the mains safely and firmly; disconnection by plugs prevents accidental switching on; has sockets which allow insertion of meter without disconnection; cable inlets firmly hold one hair wire on up to four 7,029 cables. **12/6** each.



DRILL CONTROLLER

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. **19/6**, plus 2/6 post and insurance.




CONTROL DRILL SPEEDS


BALANCED ARMATURE UNIT 500 ohm, operates speaker or microphone, so useful in intercom or similar circuits, **8/6** each, **55.10.6** doz.

BATTERY OPERATED TAPE DECK

With Capstan control. This unit is extremely well made and measures approx. 8 x 5 x 2 1/2 in deep. Has three piano key type controls for Record, Playback and Rewind. Motor is a special heavy duty type intended for operation off 4.5V. Supplied complete with 2 spools ready to install. Record, Playback is the sensitive M4 type intended for use with transistor amplifier. Un-used, ex-equipment. Price **79/6**. Post and insurance 4/6.

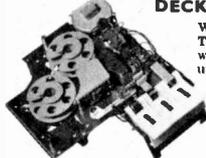


THERMOSTAT WITH PROBE

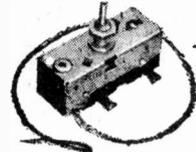

This has a sensor attached to a 15A switch by a 14in length of flexible capillary tubing—control range is 20°F to 150°F so it is suitable to control soil heating and liquid heating especially when in buckets or portable vessels as the sensor can be raised out and lowered into the vessel. This thermostat could also be used to sound a bell or other alarm when critical temp. is reached in stack or heap subject to spontaneous combustion or if liquid is being heated by gas or other means not controllable by the switch. Made by the famous Teddington Co., we offer these at **12/6** each. Postage and insurance 2/9.

MAINS MOTOR

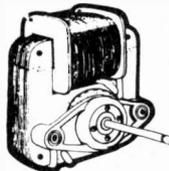Precision made — as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at **9/6**. Postage 3/- for first one then 1/- for each one ordered. 12 and over post free.



NEED A SPECIAL SWITCH? Double Leaf Contact



Very slight pressure closes both contacts, 1/8 each, 12/- doz. Plastic push-rod suitable for operating, 1/- each, 9/- doz.

MINIATURE WAFER SWITCHES

3 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at **3/6** each. 36/- dozen, your assortment.



WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 10/- post free.

MICRO SWITCH

5 amp, changeover contacts, 1/9 each, 18/- doz. 15 amp Model 2/- each or 21/- doz.



FLUORESCENT CONTROL KITS

Each kit comprises seven items—Choke, 2 tube clips, starter, starter holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Crolux" tubes for fish tanks and indoor plants. Chokes are super-silent, mostly resin filled. Kit A—15-20 w. 19/6. Kit B—30-40 w. 19/6. Kit C—80 w. 23/6. Kit E—65 w. 23/6. Kit F for 8ft. 125 w. tube 35/-. Kit MP1 is for 6 in., 9in. and 12in. miniature tubes, 19/6. Kit MP2 for 21in. 15 w. miniature tube, 20/-. Postage on Kit A and B 4/6 for one or two kits then 4/6 for each two kits ordered. Kits C, D and E 4/6 on first kit then 3/6 for each kit ordered. Kit F 6/6 then 4/6 for each kit ordered. Kit MP1 3/6 on first kit then 3/6 on each two kits ordered.

BLANKET SWITCH

Double pole with neon lamp into side so luminous in dark, ideal for dark room light or for use with waterproof element—new plastic case. 5/6 each. 3 heat model 7/6.



BLANKET SIMMERSTAT

Although looking like, and fitted as an ordinary blanket switch, this is in fact a device for switching on for varying time periods, thus giving a complete control from off to full heat. Although suitable for controlling the temperature of any other appliances using up to 1A. Listed at **27/6** each we offer these while our stocks last at only **12/6** each.

REED SWITCHES

Glass encased, switches operated by external magnet—no cold welded contacts. We can now offer 3 types: **Miniature**, 1in long x approximately 1/4 in diameter. Will make and break up to 1A up to 300 volts. Price **2/6** each, 24/- dozen. **Standard**, 2in long x 1/4 in diameter. This will break currents of up to 1A, voltages up to 250 volts. Price **2/-** each, 18/- per dozen. **Flat**, Flat type, 2in long, just over 1/4 in thick, flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp 200 volts. Price **6/-** each, 23 per dozen. Small ceramic magnets to operate these reed switches 1/9 each, 18/- dozen.

HIGH CAPACITY ELECTROLYTICS

Brand new, not ex-equipment. 100 mfd. 25V, 1/3 each 12/- doz. 200 mfd. 25V, 1/8 each 15/- doz. 250 mfd. 50V, 3/4 each 46/- doz. 400 mfd. 40V, 7/4 each 46/- doz. 500 mfd. 12V, 2/- each 11.10 doz. 500 mfd. 25V, 3/6 each 36/- doz. 500 mfd. 50V, 4/6 each 48/- doz. 500 mfd. 350V, 8/6 each 21.10.0 doz. 1000 mfd. 12V, 3/- each 18.0.0 doz. 1000 mfd. 18V, 3/4 each 34/- doz. 1000 mfd. 54V, 7/4 each 50/- doz. 2000 mfd. 25V, 6/8 each 79/- doz. 5000 mfd. 12V, 4/8 each 22.6.0 doz. 10,000 mfd. 6V, 5/9 each 23.0.0 doz. 10,000 mfd. 15V, 3/6 each 24.10.0 doz. 15,000 mfd. 10V, 10/6 each 25.0.0 doz. 60,000 mfd. 8V, 22/- each 110.0.0 doz. 70,000 mfd. 13V, 40/- each 230.0.0 doz.

3 AMP 12V BATTERY CHARGER KIT—comprising 230/40 mains transformer with 3 amp secondary and 3 amp rectifier 22/9 + 4/6 post. **12V 1A AMP POWER PACK**. This comprises double-wound 230/240V. mains transformer with full wave rectifier and 2,000 m.f.d. smoothing. Price **27/6**.

SONOTONE STEREO CARTRIDGE. Turnover type, ref. No. 19 71. This fits most British pickups and is a really excellent reproducer. Limited quantity, 10/6.

5 AMP 3 PIN SOCKETS. These are always good stock, you never know when you will need some. Famous make, brown bakelite, standard size. 12 for 13/- plus 4/6 post.

DITTO WITH SWITCH. 12 for 21 plus 4/6 post. **18 AMP SOCKETS, FLUSH MOUNTING**. Bakelite, cream, less switch, 6 for 21.

2 AMP 3 PIN SWITCHED SOCKETS for surface mounting, brown bakelite. Made by famous maker, 2/6 each or 24/- dozen.

100 ASSORTED SILICON RECTIFIERS G.P. AND SWITCHING DIODES. Small and very small sizes. A real snip for experimenters, 18/6 per 100. **MAINS SUPPRESSION ADAPTOR** for preventing mains interference caused by vacuum cleaners, razors, sewing machines, etc., rated at 4 amp—simple plug this into your 5 amp 3 pin socket, 6/- each.

40 WATT 12in. HI-FI SPEAKER

Is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for HI-FI and public address. Handling 40 watts R.M.S.—Cone moulded fibre—Freq. response 30-10,000 c.p.s.—specify 3 or 16 ohms. Chassis diam. 12in.—12 1/2in. over mounting lugs. Overall height 5 1/2 in. A £10 speaker offered this month for **25.19.6** plus post and ins.



INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A one-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade devices, definitely not sub-standard or seconds. 4 of the ICs are single silicon chip (P) amplifiers. The 5th is a monolithic NPN matched pair. Regular price of parcel well over £5. Full circuit details of the ICs are included and in addition you will receive a list of many different ICs available at bargain prices 5/- upwards with circuits and technical data of each. Complete parcel only **11** post paid. **DON'T MISS THIS TERRIFIC BARGAIN.**

THIS MONTH'S SNIP

4 AMP VARIAC CONTROLLERS

With this you can vary the voltage applied to your circuit from zero to 270 volts without generating undue heat. One obvious application therefore is to dim lighting. Ex equipment but little used—as good as new offered at approx. half price—**25** plus 12/6 post and ins.



DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work, **39/6** less plug; **45/6** with fitted 13 amp plug; **47/6** with fitted 15 amp plug, plus 4/6 P. & I.


BARGAIN OF THE YEAR MICROSONIC KEYPCHAIN RADIO

7 transistor Key chain Radio in very pretty case, size 2 1/2 x 1 1/2 in. complete with soft leather zip bag. Specification: Circuit: 7 transistor superheterodyne. Frequency range: 530 to 1,600 Kc/s. Sensitivity: 5 mv/m. Intermediate frequency: 465 Kc/s or 455 Kc/s. Power output: 40mW. Antenna: ferrite rod. Loudspeaker: Permanent magnet type. In transit from the East these sets suffered slight corrosion as the batteries were left in them but when this corrosion is cleared away they should work perfectly—offered without guarantee except that they are new. Price only **24/6** plus 2/6 post and insurance, less batteries. 6 for **27** post free. Rechargeable batteries 8/6 pair. Charger 8/6.



TANGENTIAL HEATER UNITS

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, and two elements allowing 3 heat switching and with thermal safety cut out. Can be fitted into any metal line case or cabinet. Only need control switch. 2 1/2 k.w. model **59/6**; 2 k.w. model **39/6**. Postage and insurance 6/6. Control switch 5/6.

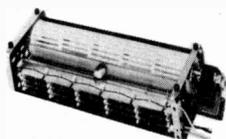

RE-CHARGEABLE TORCH

Neat flat torch, fits unobtrusively in your pocket, contains 2 Nicad cells and built-in charger. Plugs into shaver adaptor and charges from our standard 200/240 volt mains. American made, sold originally at over 4 dollars. Our price only **19/6** each.



MOTORIZED SWITCH For Animated Signs, etc.

This is a motorised programmer switch, mains operated, with six 15 amp changeover contacts operated by triggers on a rotating drum. Six triggers will put switches up and another six triggers will put switches down. This simple on/off operation or changeovers are possible. The triggers can be exactly set to any position around the drum which is rotated by a one rev. per hour motor. (Motors with other speeds available.) A beautifully made precision switch which probably cost in excess of £20. Limited quantity only **27.15** each + 4/6 post and ins. Similar programmer by Honeywell but 15 x 10 amps switches operated by 5 rpm motor: **25.15** plus 4/6 post and ins.



Where postage is not stated then orders over £5 are post free. Below £5 add 2/9. Semiconductors add 1/- post. Over £1 post free. S.A.E. with enquiries please.

ELECTRONICS (CROYDON) LTD

Dept. PE, 266 London Road, Croydon CR0 2TH

Also 102/3 Tamworth Road, Croydon

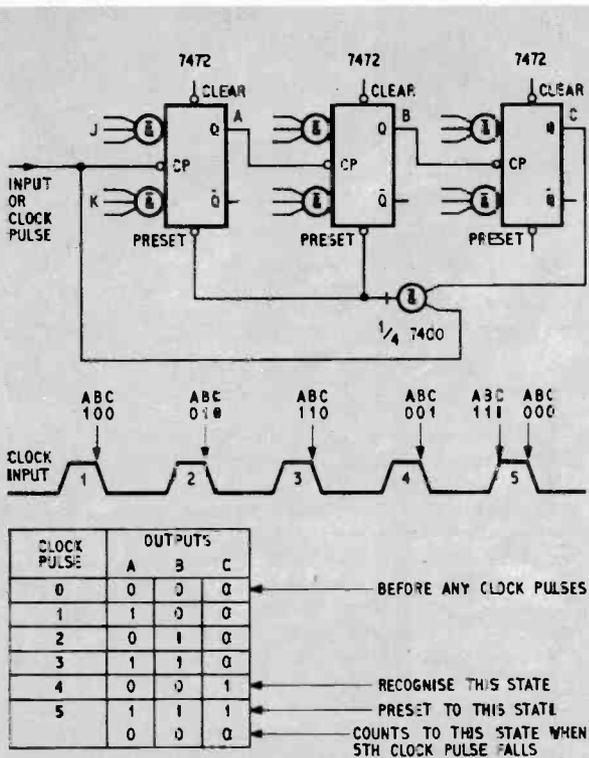


Fig. 7.3. Improved divider with truth table

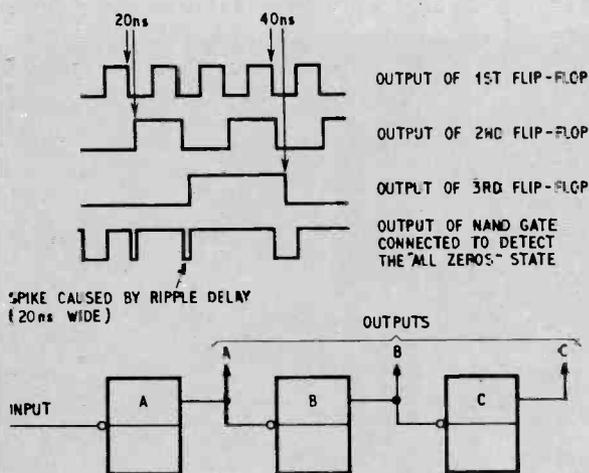


Fig. 7.4 Effect of compounded propagation delay

When the final clock pulse falls (assuming JK master/slave flip-flops), the counter will count to the all zeros state, ready to begin another cycle. The appearance of the all 1 state during the final clock pulse is unlikely to cause a problem, although this depends on the application.

To see this system operating, take as an example a divide-by-five counter using type 7472 JK flip-flops. The nearest power of 2 which is higher than 5 is 2^3 , so a three stage counter will be necessary as a basis of the design.

The final counter state will be binary four, 100, because the first state of the counter will be zero, i.e. 000. The only flip-flop which has an output of 1 at this stage is the third one, so we must feed this output together with the clock into a 2-input NAND gate, and connect the output of this gate to the preset inputs of the first two flip-flops.

The final circuit is shown in Fig. 7.3, together with a truth table and the clock pulse action. Note that the J and K inputs are not used in this application, and are therefore left disconnected, simulating a 1 input. They can, in practice, be connected to $+V_{cc}$ to ensure this state.

PROPAGATION DELAY

The counters we have considered so far have all been ripple types, and, as such, they all suffer from a drawback which can be serious in some applications.

If we look closely at such a counter which is in the all 1 state, it will be required to count to the all zeros state on the arrival of the next clock pulse. The final flip-flop in the chain will not be able to do this until all the stages preceding it have already done so; after all, it gets its own clock edge from the flip-flop immediately before it, which in turn gets its clock edge from the stage before it, and so on.

This all sounds quite straightforward, until we consider the propagation delay incurred from each stage, which in the case of the 7472, is 20ns. This seemingly insignificant delay is multiplied by the number of flip-flops there are in the counter, and may reach alarming proportions in a counter working at high speed and with a long cycle length.

Even so, it need not be a problem unless several of the counter outputs are gated together. Spikes appearing at the gate output at the wrong time may cause other circuits connected to the gate output to mistrigger. To illustrate the effect of this ripple delay, Fig. 7.4 shows the output waveforms obtained from a three stage counter, with the error due to the delay magnified.

To overcome this ripple delay error, a different kind of counter called a synchronous counter is used. With this type, the clock input is fed to every stage, not just the first. Input gating is used to determine the conditions when a flip-flop is required to "toggle", or change state.

Next month's article will continue with synchronous counters, shift registers, and ring counters using TTL flip-flops.

BE SURE OF YOUR COPY

We have many requests for back issues and cannot always guarantee supplies; to make sure of your copies why not take out a yearly subscription.

Subscription including postage for one year to any part of the world £2 5s. 0d. (£2.25).

Subscriptions dept., IPC Magazines Ltd., Carlton House, 68 Great Queen St., London WC2B 5DD.

WASH-WIPE

An electronic device for intermittent wiping and automatic wiper operation with washers, on cars with 12 volt field coil wiper motors.

A FACILITY not provided as standard on older cars but which proves to be very useful in the British climate is that of intermittent operation of windscreen wipers. Another useful facility is windscreen wiping initiated by operation of the windscreen washer control and continuing for a limited period after its release. Both facilities are provided by the circuit to be described which can be added to the existing circuits in the car without impairing the normal operation of the standard controls.

The circuit takes advantage of the windscreen self-parking mechanism fitted to most cars; reference to back numbers of practical motoring magazines will show that this mechanism can be fitted to almost any vehicle very easily at little cost. The circuit is also basically designed for negative earth connection but a modified version to suit positive earth connection is given. The unit cannot be operated with the latest permanent magnet wiper motors, or in conjunction with 6 volt systems.

CIRCUIT DESCRIPTION

The circuit diagram for negative earth connection is given in Fig. 1 and the mode of operation is as follows.

The thyristor SCR1 is connected in parallel with the manual switch controlling the windscreen wipers (S4) and when triggered will initiate wiper action. A small amount of wiper action closes the self parking switch S3, short-circuiting SCR1 and turning it off; the wipers continue under the control of the self parking switch to the end of a single sweep. If SCR1 is not in a triggered state at this time, no further wiping action will take place until SCR1 is again triggered or the wiper switch (S4) is closed.

The function of diode D2 is to bypass the inductive surge current generated when the motor is switched off. The necessary trigger pulses for SCR1 are provided by the unijunction oscillator TR2 at intervals determined by the time constant $(VR1 + VR2 + R5)C2$. The function of R5 will be described later. VR2 is a preset potentiometer which determines the fastest intermittent rate and VR1 is the rate control which can be omitted if fixed rate operation only is required, in which case VR2 determines the rate. Switch S2 is the on-off control and is incorporated in VR1.

With the component values given, the sweep rate can be adjusted to cover a range from one sweep every 1.5 seconds to one sweep every 15 seconds. Resistor

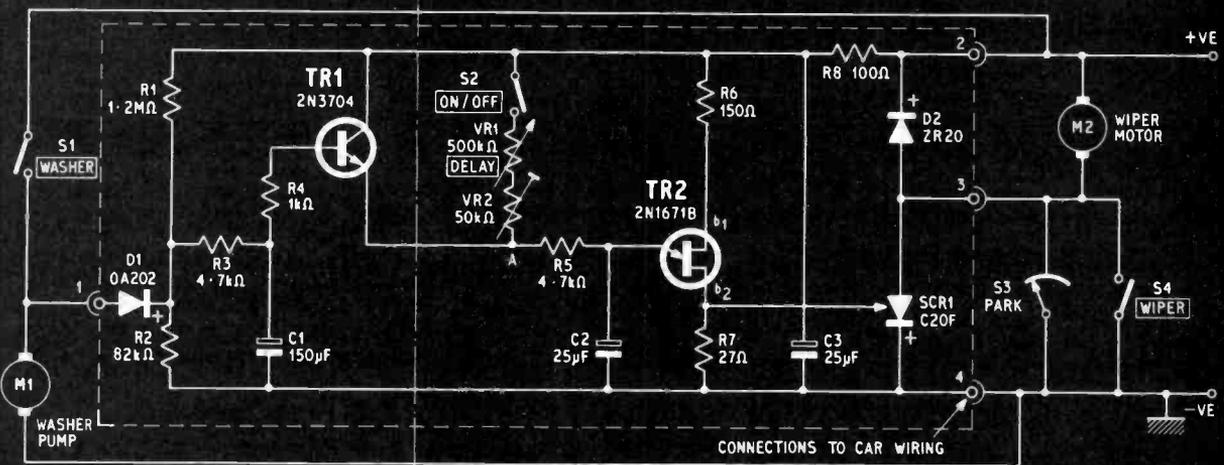


Fig. 1. Circuit diagram of the negative earth wash-and-wipe control

CONTROL

By D. E. VAUGHAN

R8 and capacitor C3 form a filter which prevents voltage disturbances on the battery line from producing false trigger pulses. If R5 is omitted together with that part of the circuit to the left of the chain dotted line (the components on tagboard A), the circuit as described will provide the intermittent sweep facility alone.

LIMITED CONTINUOUS OPERATION

The limited continuous wiper operation is obtained in the following way. In the quiescent state, with S1 open, point A (Fig. 1) is approximately at the same potential as the junction of R1 and R2 and, since this is less than ηV_b , the unijunction oscillator will not function. When S1 is closed C1 is charged rapidly through D1 and R3 and by emitter follower action in TR1 point A is raised above ηV_b , allowing the unijunction oscillator to function at a rate determined by the time constant $R_5 C_2$. (Where ηV_b is the intrinsic stand-off ratio.)

If the resistor R5 has the minimum value consistent with reliable operation, a high repetition rate is obtained so that there is minimal delay at the end of each wiping stroke before SCR1 is re-triggered. When S1 is opened C1 discharges slowly through R3 in series with the parallel combination of R1 and R2 towards a potential $R_2 V_{10} / (R_1 + R_2)$ and the potential of point A follows. When this falls below V_b the unijunction oscillator again ceases to function.

The effective time constant of the component values suggested allows three or four sweeps after the opening of S1, depending upon the speed of the windscreen wiper motor. The elaborate charge-discharge circuit

is incorporated to prevent an unwanted sweep occurring when power is first applied. It will be noted that the limited continuous wiping facility is obtained irrespective of the state of S2. If the latter is closed, intermittent operation automatically follows the end of the continuous wiping period.

COMPONENTS

The modified circuit for use in vehicles with positive earth connection is shown in Fig. 2. Two additional components are required to provide the necessary improvement in false trigger pulse suppression.

The choice of *npn* transistor TR1 and unijunction transistor TR2 are in no way critical, the particular types listed being those which were at hand. The thyristor SCR1 should have current rating at least equal to the running current of the windscreen wiper motor, typically 3 to 4 amps, although in the interests of reliability the thyristor should be of sufficiently high rating to handle the hot stall current, typically 7 to 8 amps.

Diode D2 should have a forward current rating equal to at least half of the normal running current. Other component values are selected to suit the particular devices used and to provide the desired timing intervals.

CONSTRUCTIONAL DETAILS

The simplicity of the circuit means that any form of construction which is convenient may be used without difficulty. However, details of the form of construction used in the prototype are given here as a guide.

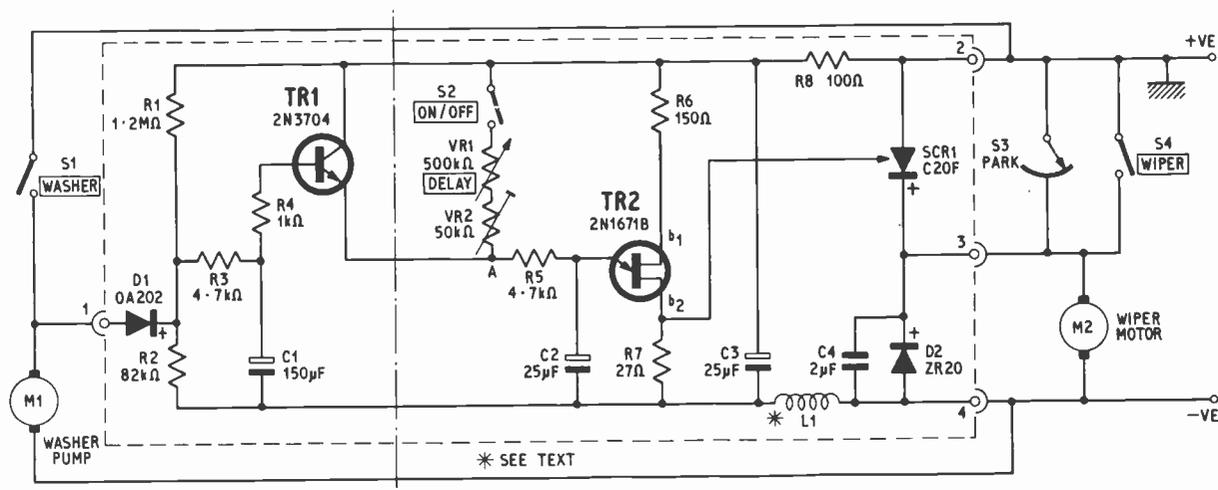


Fig. 2. Circuit diagram of the positive earth wash-and-wipe control

COMPONENTS . . .

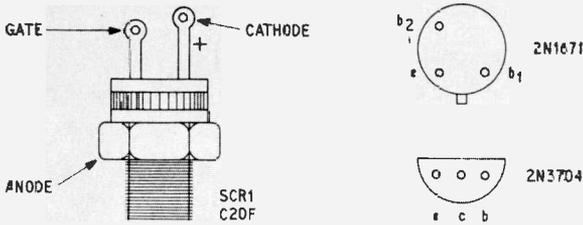


Fig. 3. Semiconductor connections for the components listed

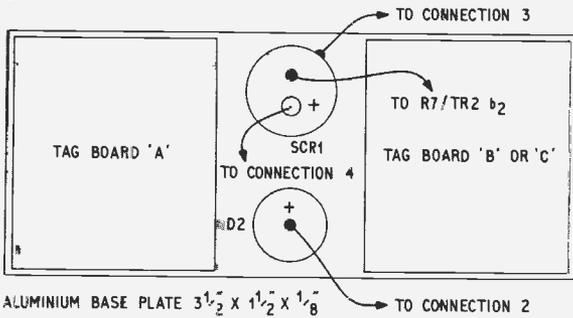


Fig. 4. General layout of the tag boards

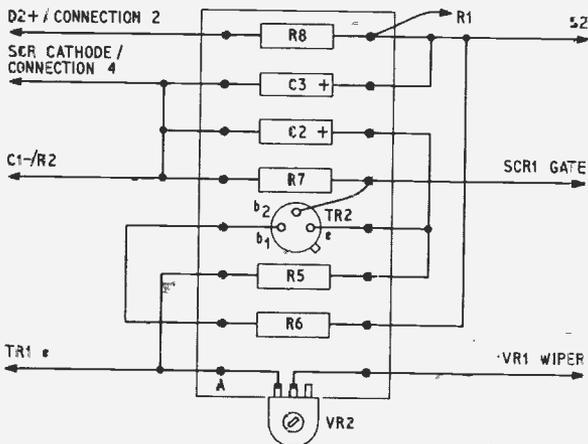


Fig. 5. Tag board B, for negative earth version

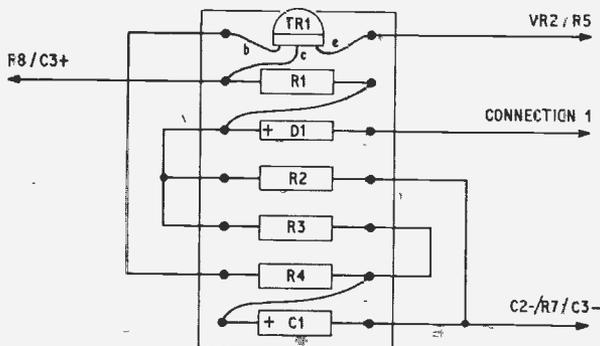


Fig. 6. Tag board A, for both versions

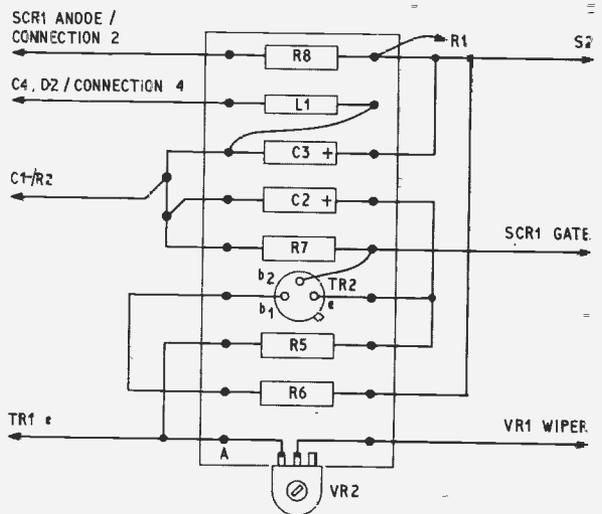


Fig. 7. Tag board C, replaces tag board B for positive earth version

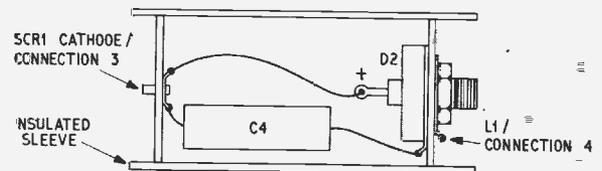


Fig. 8. Sub-assembly for positive earth version

Resistors

- R1 1.2M Ω
- R2 82k Ω
- R3 4.7k Ω
- R4 1k Ω
- R5 4.7k Ω
- R6 150 Ω
- R7 27 Ω
- R8 100 Ω

All $\frac{1}{4}$ W, $\pm 10\%$ carbon

Potentiometers

- VR1 500k Ω with single pole on-off switch (S2)
- VR2 50k Ω skeleton preset

Capacitors

- C1 150 μ F elect. 15V
- C2 25 μ F elect. 15V
- C3 25 μ F elect. 15V
- C4 2 μ F paper (for positive earth version only)

Semiconductors

- D1 OA202
- D2 ZR20
- SCR1 C20F thyristor
- TR1 2N3704
- TR2 2N1671 B unijunction

Miscellaneous

- L1 1A T.V. suppressor choke
- Control knob
- Tag boards and aluminium for heat sink
- 6B.A. fixings

For the benefit of readers who are not familiar with the unijunction transistor and the thyristor, details of the electrical connections are shown in Fig. 3. Although these are typical, should other types be used the relevant manufacturer's information must be followed.

NEGATIVE EARTH VERSION

The general layout for a negative earth system is shown in Fig. 4, SCR1 and D2 being fixed directly to the base plate which acts as a heat sink. Two tag boards are also attached to the base plate. Since the base plate is live to the circuit, it is enclosed in a small plastics box using nylon screws as mounting studs; this box can be fixed at a convenient point behind the car fascia panel (the base plate must not be earthed to the car).

Detailed component layouts on the two tag boards are shown in Figs. 5 and 6. Although VR2 is shown on the circuit diagrams as a preset component, once its value has been found it can be replaced by a fixed resistor.

Two groups of leads are taken from the box, one group going to S1, S2 and VR1 mounted on the fascia panel and the second passing through the bulkhead to the washer pump, the wiper motor and to the positive and negative battery connections.

POSITIVE EARTH VERSION

Because the stud connections to SCR1 and D2 are not common when a positive earth system is required, a slightly different form of construction has to be adopted. The general layout of the base plate differs from that shown in Fig. 4 in that D2 is omitted and one of the tag boards carries an additional component (L1) —Fig. 7 replacing Fig. 5.

Diode D2, together with the additional capacitor C4, is mounted as a separate assembly in a small insulated tube (see Fig. 8) fixed near the wiper motor. In all other respects the details of construction are similar.

CONNECTION TO WIPER MOTOR


Examination of the electrical connections to a wiper motor already fitted with a self-parking switch will show two live leads and an earth return. Reference to the workshop manual, or a few minutes work with a voltmeter, will establish which of the live leads is connected to the battery and which is the switch lead. The lead from the base plate (i.e. the common connection of the thyristor and diode anodes) is connected to the switch lead terminal. It is stressed that no modification to the wiper motor is required unless the motor does not have the self-parking facility.

In the case of wiper motors not fitted with a self-parking switch, the first step is to make the necessary modifications. When the modifications have been completed the connection can be made as previously described.

WASHER PUMP SWITCH

An electric washer pump switch is sometimes fitted in cars but is normally connected between the pump and earth. If this is so it is a simple matter to reconnect as shown in the circuit diagram (Fig. 1).

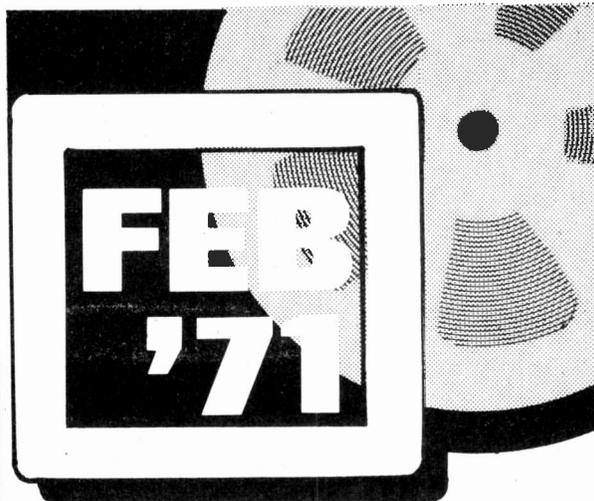Although the control for manual and vacuum washer pumps is not electrical, it should be possible to fit a microswitch, actuated by the normal control, in place of the washer switch. Other methods of switching may well be possible and no doubt some readers will add this facility to non-electric washers. ★



TAPE SLIDE CONTROLLER

This electronic control system can be added to any tape recorder to control an automatic slide projector in sequence with a recorded sound track. It has been designed so that no modifications are necessary to the tape recorder or the

SUBMARINE CHASER

A follow-up "war" game to *Operation Seasearch* (December 70). This game uses the same chassis and much of the wiring of *Operation Seasearch* but introduces depth. In *Submarine Chaser*, "Asdic" is used to narrow the search and the destroyer must adjust his depth charges correctly to destroy the submarine.

PRACTICAL
ELECTRONICS

FEBRUARY ISSUE

—ON SALE JANUARY 15—

Order yours NOW!

BIAS

IN

TAPE RECORDING

By C.W. Smedley C.Eng., M.I.E.E.

Southall College of Technology

TAPE recording has been covered by many text books, and the general principles are well known. The explanations given of bias, however, tend to be vague, and those who would like to pursue the matter are often deterred by the B/H loop, with its associated mathematics, implied if not stated. This article is intended to be a reasonably valid description avoiding the use of complicated analysis.

The object is to record signals, which can be audio, video, digital, etc. on a tape which is either coated or impregnated with magnetic material, and the system described here will be longitudinal.

THE MAGNETIC CIRCUIT

The recording/playback head consists of a winding on a ferromagnetic core, and current fed to the head will produce a magnetic flux. Fig. 1 shows the relationship between flux, B , and the magnetising force H , which is proportional to ampere-turns. If the current is increased slowly from zero, the value of flux can be plotted against the value of H , and the line OA will be traced.

At some point, A on our diagram, the value of flux will remain constant for any further increase in H , and the core is said to be saturated. P represents this maximum value of flux and S shows the corresponding value of H . If the current, i.e. H , is now reduced to

zero, the flux decays along the curve AR , and R is the remanent value of the flux.

The ratio of OR to OP is called the retentivity of the core material. Some ferrites produce a curve in which OR and OP are practically equal; these are called square loop materials and are used in computer stores.

HYSTERESIS LOOP

If the current is now increased in the reverse direction, at some point the flux will have fallen to zero, shown as point C . Further increase will bring the flux to point D , which is reverse saturation, identical in value with point A , but opposite in polarity. Reduction of current, towards zero, will reduce the flux, and the curve DQ will be traced out.

Note that this curve does not pass through point O , but rises, as current is increased in the original direction, through E to A . It can be seen that, for any value of H , there are two possible values of B , and the perpendicular drawn at the point where H equals X cuts the B/H loop at points Y and Z . When H is rising, the value of flux corresponding to Y is less than on the original trace, OA , whereas, when H is falling, the value of flux corresponding to Z is higher. This lagging effect is called hysteresis, and the curve $ACDEA$ is called the hysteresis loop.

THE AIRGAP

If the magnetic core formed a complete ring there would be no flux outside the ring, and a tape drawn across it would be unaffected. To produce flux outside the ring it is necessary to break the magnetic circuit, i.e. to have an airgap, and it will be at this point that the moving tape will be brought into contact with it.

The airgap will increase the reluctance of the magnetic circuit, and the flux for any given value of head current will be less than the value without an airgap. Another effect, however, offsets this apparent loss, and Fig. 2 has been drawn to illustrate it.

If we assume that the B/H loop is very narrow, then let OA represent the loop with no airgap. OA' shows the loop when a small gap is introduced, OA'' the loop for a bigger gap. The first trace, OA , shows extreme curvature near the ends, and would not, in fact, be linear at any point. OA' is much more linear, although the slope is less, and OA'' is better still, although the value of H necessary is increasing with the size of the airgap. This is not too important, since the amplifier gain can be increased to compensate. For the sake of linearity, therefore, the gap should be as big as possible.

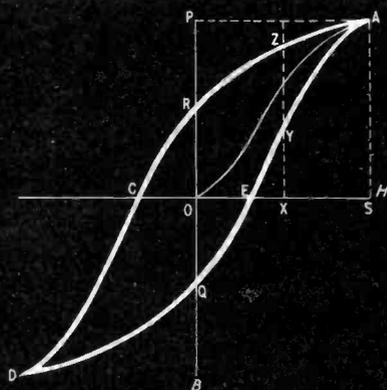


Fig. 1. BH curve or hysteresis loop

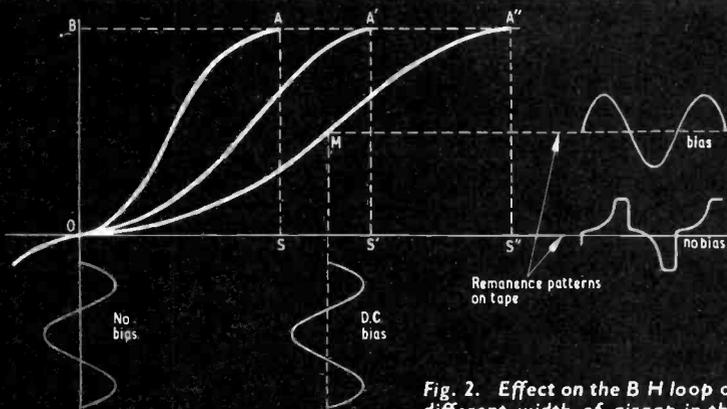


Fig. 2. Effect on the BH loop of different width of airgap in the magnetic core. The larger the gap, the better the linearity

But it can be shown that, for any given tape speed, the bigger the gap the poorer is the high frequency response of the system, and the two fundamental requirements appear to be in conflict. The practical solution is to make the actual recording/playback gap as small as possible, then to insert a second gap diametrically opposite to it.

DIAMAGNETIC GAP

Although the term airgap remains in use, the actual gap must be filled, for two reasons. One, if left open it would collect magnetic material from the tape, to re-form a closed magnetic circuit. Two, the external flux would be low in value. The gap is closed by a material which is both hard, to resist wear, and diamagnetic. Brass is a good example, and is commonly used. The flux now "fringes" out across the gap to make recording more effective.

The actual distribution, however, is not at all like the pattern across the open end of a horseshoe magnet. The brass insert acts as an obstruction to the flux and the tape itself closes the magnetic circuit. The flux can be said to enter and leave the tape at right angles to the surface of it, but all of the flux does not leave the core at the edge of the gap. It is spread each side of the gap to form a fringe which tails off within a short distance, and the electrical gap is therefore greater than the physical gap in the head. It is important to remember this when considering erasure.

THE NEED FOR BIAS

The effect of recording a signal has been shown by superimposing it on the vertical axis of Fig. 2. The recorded pattern on the tape will show the curvature near to point O, and harmonic distortion has been introduced. To prevent this effect the working area should not include the extreme curvatures near zero and saturation.

Direct current bias can be used, for example sufficient current can be passed through the record head so that every tape element is, in the absence of a signal, magnetised in the same direction, to the same degree. Such a current would correspond to a value of H somewhere between S and S' , so that the effective working point is M on the curve OA . The signal to be recorded is now shifted bodily to the right, so that it becomes symmetrical about the vertical drawn through M .

This bias system closely resembles that used for valves and transistors, where the transfer, or mutual, characteristics exhibit similar curvature at cutoff and bottoming.

Although this d.c. system is used on cheap tape recorders, there are two major limitations. One, the peak to peak signal amplitude must be only half the value of that when no bias is used. This can be partially overcome by shifting the d.c. bias point, but the benefits are marginal and still include some distortion. Second, every particle on the tape is magnetised and, on playback, will make a contribution to the output voltage in the form of noise, mainly high frequency (hiss). For these reasons supersonic (a.c.) bias is now almost universal.

HIGH FREQUENCY BIAS

The frequency chosen must meet two requirements: it must be high enough to be filtered out on playback without attenuating the wanted signal and, in general, should not be less than three times, preferably five times, the highest frequency to be recorded. At the same time, it must not be too high because the record head is highly inductive. The practical value lies between 50 and 75kHz and a sinewave form is essential to prevent head magnetisation by second harmonic. LC oscillators of the Hartley or Colpitt type are popular, and the stage often "doubles" as audio output on playback.

To understand the full effect of a.c. bias, two points should be kept in mind. One, the gap includes the fringe each side of it, and the actual flux entering the tape from the head is almost perpendicular to the surface. Two, the flux is alternating at bias frequency, and the actual value affecting each tape element will be the instantaneous value as that element leaves the fringe. Each tape element, or particle, is therefore exposed to a flux which can have any value from zero to maximum, of either polarity, but the resultant magnetic pattern on the tape is not sinusoidal.

Fig. 3a will show this more clearly, and the applied flux, H , is shown to have sine wave form. Point A on the sine wave corresponds to saturation, i.e. point A on the B/H curve, and any tape element exposed to this value of flux will have a remanent magnetisation equal to point R when it leaves the fringe. Following elements will be exposed to a flux decaying towards point R but all will have the same remanent value as point A.

REMANENT FLUX

Fig. 3b shows the remanent flux plotted against the sine wave producing it, and it can be seen that the waveform written on to the tape has a flat top from point A to point R. From R to B the applied flux is increasing in the reverse direction, but the remanent flux does not fall to zero until the applied flux has reached a point between T and B. At point B reverse saturation is reached and from B to Q the remanent flux again shows a flat top. In the absence of any other signal the bias continues to write this pattern.

If the tape is now played back at the same speed the pattern will induce small voltage pulses in the head at bias frequency, but since the pulses are symmetrical about zero, simple integration (to be discussed later) will virtually eliminate them. One thing the bias has established is the maximum wavelength of each pattern on the tape. Larger groupings, which would give rise to low frequency noise if exposed to direct current bias, have been restricted to this wavelength.

It should be noted at this stage that, although the terms amplitude and frequency are used for signal and bias currents, they should not be used when referring to the recorded tape. The pattern on the tape has intensity and wavelength.

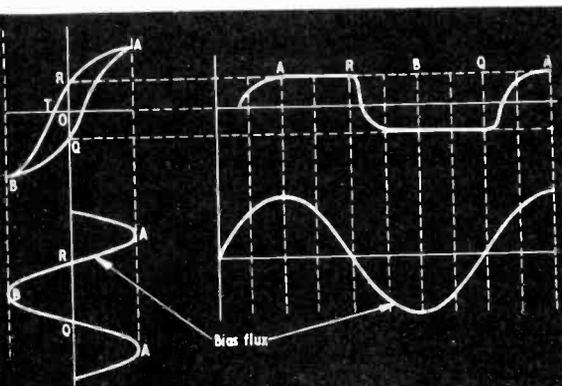


Fig. 3a (left). Applied flux on the H axis of the magnetic loop is transferred to the tape in distorted manner due to remanent magnetism, which is plotted in Fig. 3b (right) and shown against the sine wave producing it

SATURATION BIAS

If a low frequency signal, for example audio, is now fed to the head at the same time as bias the pattern on the tape will be modified. Fig. 4 shows the effect, in terms of H and B . The l.f. signal shifts the bias waveform progressively, in this case, to the right. The bias current remains the same in amplitude but now "rides" on the signal. The value of " H ", in the right hand direction, increases to well beyond saturation, but the remanence pattern cannot increase with it, as it already corresponds to the saturation value.

However, due to the shift, much more than a half period, in terms of bias, is spent at and beyond saturation, and the pattern on the tape covers a greater distance. On the left hand side, not only is " H " reduced in value, but less than half a period is spent in this region. The pattern on the tape therefore shows a reduction in intensity and in length. The overall bias wavelength has not changed, but the pattern distribution has, and any pulses produced by playback will not be equal and opposite. Integration will show a progressive change in one direction, the value depending upon signal amplitude and the direction upon signal phase.

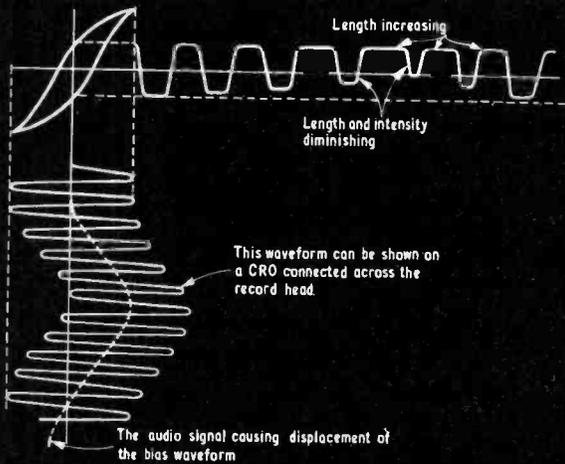


Fig. 4. The effect of applying an audio signal at the same time as the bias signal, producing a saturated magnetisation of tape particles

DISADVANTAGES

This system uses saturation bias and has disadvantages. One, the high value of bias tends to demagnetise the pattern recorded, leading to a loss of high frequency response; two, the limiting action described still gives distortion. The optimum value of bias is about half the saturation value, and the remanence pattern on the tape will be lower in intensity. The flat tops will still be present exactly as before, but, when a signal appears, both polarities will be affected, i.e. one half will be increased, the other decreased.

Integration will produce an output whenever the remanence pattern is unbalanced by a signal, but, for any given value of signal, the output will be greater than when using saturation bias because both polarities change in length and intensity.

SCOPE FOR IMPROVEMENT

The system so far described is the typical domestic sound recording, and a few practical details will help to

show the scope for improvement. Assuming a bias frequency of 70kHz and a tape speed of 7in/sec the recorded wavelength will be one tenth of a thou (0.0001in) the pattern representing each flat topped pulse will therefore be one tenth of that. Since the process produces a series of "bar magnets" along the length of the tape, the smallest unit will be the dust particle of the coating, and this will be in the region of one micron, which is about one twenty-fifth of a thou.

The flat top cannot be considered as any more than one particle, and it remains flat with or without a signal. If the dust particles were made smaller, and/or the tape speed increased the recorded length of the flat top could cover many particles and any change of signal level during that passage would modify the top. The slope of the signal would then appear superimposed on the flat top.

PLAYBACK

The surface induction (remanence pattern) on the tape has been shown to be a distorted version of the bias waveform. At very short wavelengths there is a

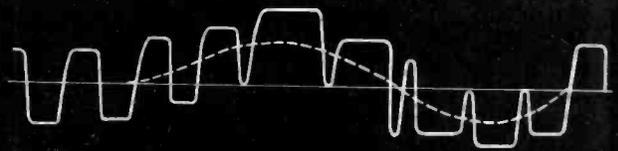


Fig. 5. Correct application of bias magnetises the tape by a series of pulses which are proportional to the applied audio signal

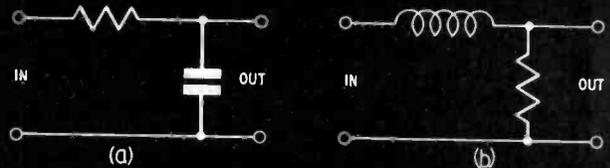


Fig. 6. Filter networks used on playback to eliminate the high frequency bias pulses. A simple CR network is shown in (a) and an LR network using the tape head inductance in (b)

strong demagnetising effect, and the actual value measurable would be less than expected. The presence of the bias has, however, made the signal effective over the linear part of the characteristic and this is its true function. Fig. 5 shows the effect of a signal on the pattern, the applied signal represented by the dotted line. Each half cycle of signal now appears as a group of pulses.

When the tape is passed over the gap this pattern will produce voltage pulses in the head circuit and the next process can be considered as filtering. Fig. 6a shows a CR network which will act as a low pass filter, suppressing the high frequency pulses, but producing an output proportional to their amplitude/duration. This action is integration, the pulses producing the charging current for the capacitor, the output signal being the voltage developed across it.

Fig. 6b, although less well known, is also an integrating circuit, having the same effect, but the inductance is that of the playback head, usually 0.5 to 1.0 henries.

ERASURE

The advantage of tape is that it can be used many times, and, to achieve this, some means must be used to remove the recorded signal.

The most common method is to mount an additional head—the erase head—fairly close to, and just ahead of, the record head. A much larger gap is used and the same bias waveform of greater amplitude, is fed to the winding. The current should be sufficient to take each tape element beyond saturation.

This head is usually tuned to bias frequency since it does not handle signal. Although the gap is large, and the erase current high, it is found that the original pattern on the tape, especially that of strong signals, often recovers after erasure. To avoid this effect a double gap is used, the gaps, in this case, being adjacent to each other.

Because the gap is larger, and bias current higher, the flux extends well beyond the physical gap, i.e. the fringe is longer. Each tape element spends much more time in the fringe than it would in that of the recording head, and many loops are traversed in that time. The loops fall off in amplitude as each element moves out of

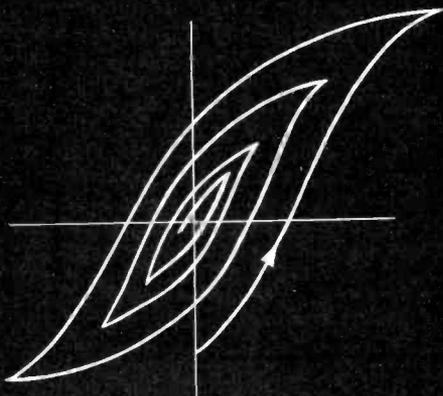


Fig. 7. The series of BH loops through which each tape particle passes, due to large air gap and increase h.f. current for erasure by saturation

the fringe so that the remanent flux is negligible. Fig. 7 shows the series of loops to which each element is exposed as it leaves the erase gap, the actual number of loops being much greater than a clear sketch could show.

CONSTANT CURRENT RECORDING

When a signal is recorded on tape the pattern must represent the amplitude as well as the frequency. The flux and therefore the head current should be independent of frequency. The recording head is highly inductive and its reactance would reduce the current as the frequency became higher, assuming a constant voltage drive.

A resistor is usually connected between the output of the signal amplifier and the head to reduce this effect, which could lead to a fall-off of 6dB per octave. If the resistor value is high, it will swamp the reactance of the head, so that the head current will be the same for all frequencies of the same original amplitude. This is called a constant current system. ★

NEWS BRIEFS

B.A.E.C.

THE British Amateur Electronics Club recently held its annual exhibition at Penarth, Glamorgan, and as a result of this, some of the exhibits were used in a BBC television programme on BBC Wales; the programme—"Heddiw"—was televised in Welsh but the B.A.E.C. were provided with an English translation of the text that they published in their October Newsletter. The games illustrated on television were all constructed by members of the B.A.E.C.

Vidicon Storage Tube


DEVELOPMENT of the first television camera tube to feature built-in stop-action capabilities was reported recently by RCA.

The unit is a small, vidicon-type device that can take—and store for later play-back—single electronic "snapshots" or "stills" of continuous programmes being transmitted by the tube.

The still picture is electronically stored inside the tube itself thus eliminating the need for an external storage medium such as film or videotape. It can be relayed to a TV monitor immediately, or kept intact within the tube for several days.

The new tube is technically referred to as a silicon storage vidicon and could be used, for example, in a space, satellite to eliminate the bulk and weight of the present video storage devices which relay individual TV pictures to earth by relatively slow communications systems.

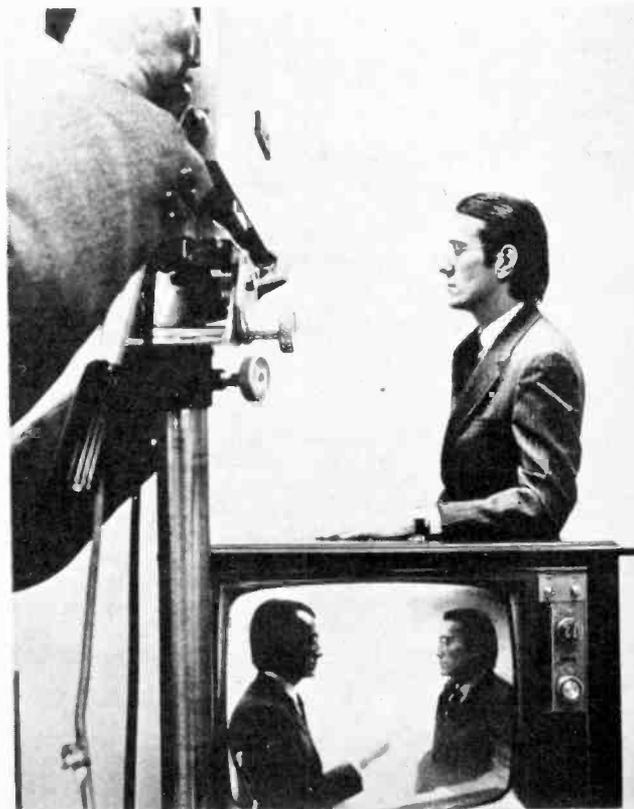The picture below shows the new tube in use. The image on the left of the screen was recorded by the tube a few minutes before, and the one on the right is being transmitted "live", giving the impression that the subject is talking to himself.





DUAL PURPOSE STEREO AMPLIFIER PART THREE

By D. S. GIBBS and I. M. SHAW (FERRANTI LTD)

A HIGH quality pre-amplifier must perform several important functions, it must have an input impedance sufficiently high not to load the signal sources, it must provide frequency equalisation where necessary, it must have filters to remove spurious noise or harsh treble from poor recordings and it must have tone controls to accommodate the preferences of the listener, the deficiencies of the loudspeakers and the acoustics of the listening room. Furthermore it should do all this without any significant increase in either distortion or background noise level over a wide range of input signal levels.

The design evolved meets all these requirements, as the specification published previously shows, and it has several other valuable facilities. A microphone channel is included which can be mixed independently with any other input. This facility is useful to tape recording enthusiasts or can be used as a "home discotheque" for parties etc. Another feature valuable to the tape recorder enthusiast is the recorder output which is taken after the equalisation and filter stages but is unaffected by volume or tone controls. The circuit diagram of the right hand channel of the pre-amplifier is shown in Fig. 24, the left hand channel is identical.

DISC INPUT

The disc input stage comprising T14, T15, T114 and T115, provides frequency equalisation to the RIAA L.P. characteristic with an accuracy of approximately $\pm 0.5\text{dB}$ between 30Hz and 15kHz as shown in Fig. 25. The circuit has been designed so that the frequency response curve falls below 20Hz. This attenuates low frequency components in the output of the pickup and makes a separate rumble filter unnecessary. The sensitivity is 3mV in the "Lo" position and about 60mV in the "Hi" position so that either magnetic or ceramic pickup cartridges may be used.

The circuit used is a complementary two stage feedback amplifier, a more detailed circuit of which is shown in Fig. 26. This was chosen in preference to the more popular circuit shown in Fig. 27, because of the greatly improved bias stability and its freedom from the subsonic ringing which the circuit of Fig. 27 tends to produce. This arises through the feedback provided by R1 becoming positive at certain frequencies due to the phase shifts produced by C1 and C2 (Fig. 27).

The shape of the frequency response curve is defined by the negative feedback provided by R39, R40 and C19 to 21; the overall gain is defined by R38. The circuit gives an output of 100 mV for an input of

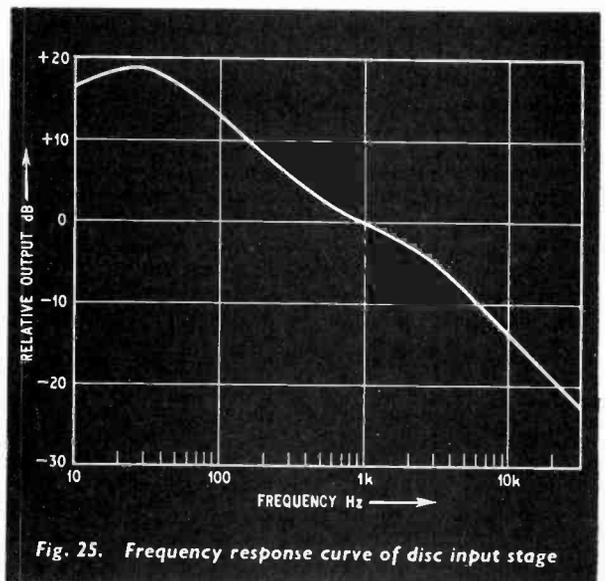


Fig. 25. Frequency response curve of disc input stage

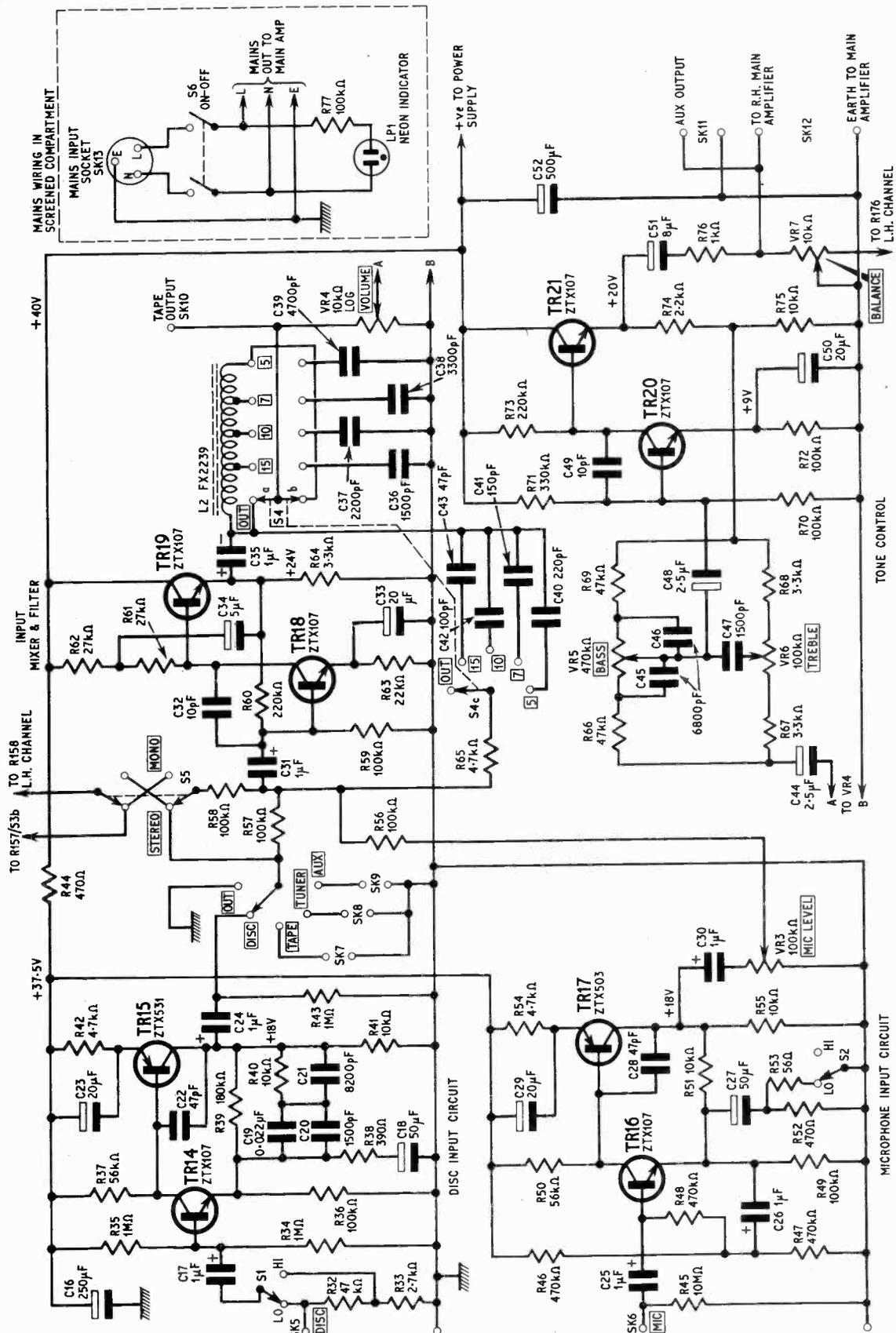


Fig. 24. Circuit diagram of the right-hand channel of the P.E. Gemini. The left-hand channel is identical — component numbers being right-hand channel plus 100, except for the switches and sockets which serve both channels by being double pole types

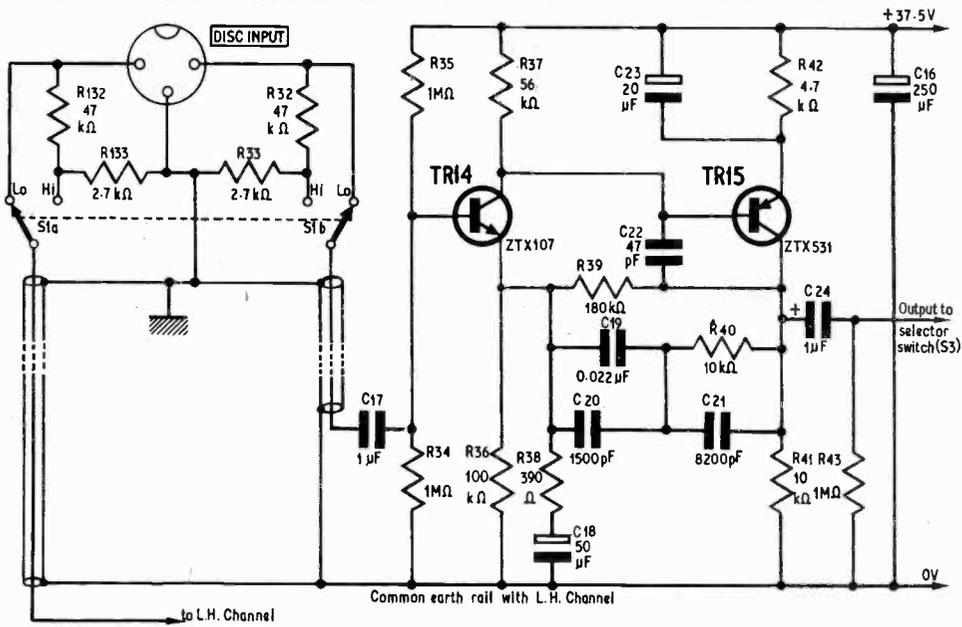


Fig. 26. Disc input circuit—right-hand channel only


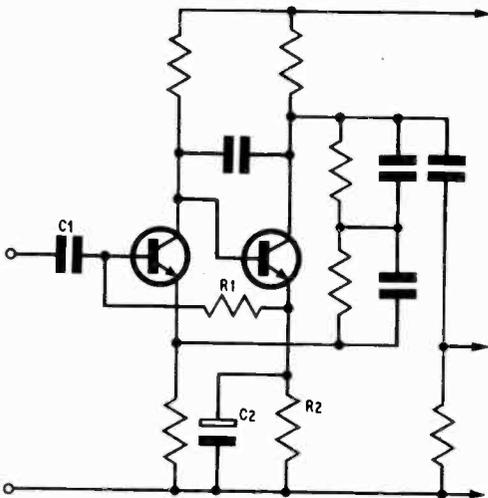


Fig. 27. A popular two transistor disc input circuit. This circuit was rejected in favour of the circuit shown in Fig. 26 because of its inferior bias stability and its tendency to subsonic ringing

Fig. 28. Microphone input circuit—right-hand channel only

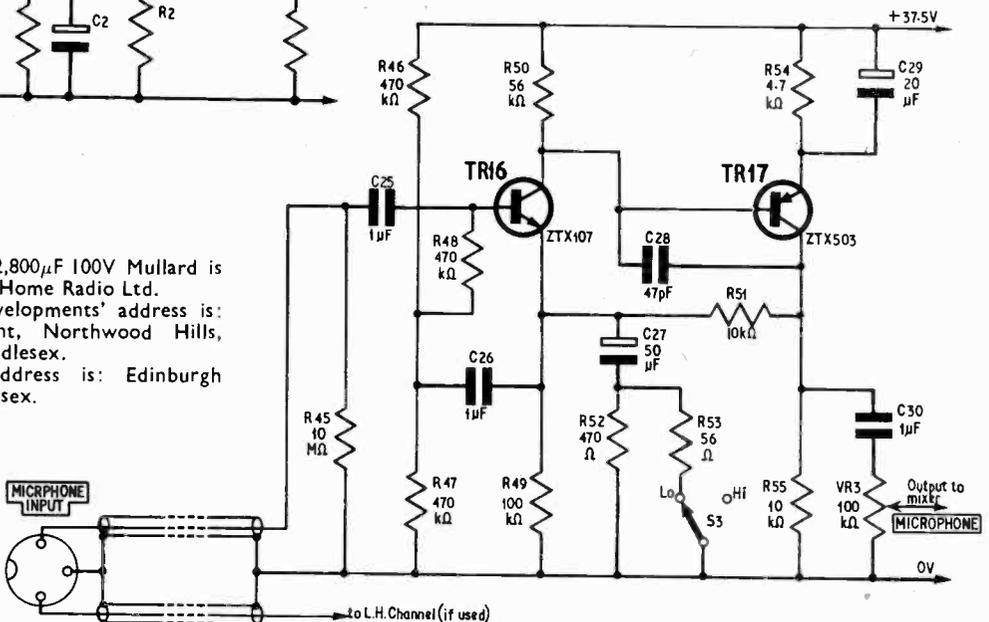

NOTE :

Capacitor C3—2,800 μ F 100V Mullard is obtainable from Home Radio Ltd. West Hyde Developments' address is: Ryfield Crescent, Northwood Hills, Northwood, Middlesex. Electronics address is: Edinburgh Way, Harlow, Essex.

3mV at 1kHz. Distortion generated by the input stage is below 0.005 per cent with 3mV input at 1kHz and below 0.05 per cent at 20dB overload. Between 100Hz and 10kHz the distortion does not exceed 0.1 per cent at any level up to 30dB overload.

MICROPHONE INPUT

The circuit of the microphone input stage (Fig. 28) is virtually the same as the disc input except that the feed-back network is replaced by a single resistor to give a flat frequency response and the bias resistors at the input are bootstrapped to increase the input impedance. Two input sensitivities have been provided. In the "Lo" position of S2 the input sensitivity is 1mV with an input impedance of 1 megohm which is suitable for most low and medium impedance dynamic and ribbon microphones. With the switch in the "Hi" position the sensitivity is reduced to 10mV and the input impedance rises to 2 megohms. This sensitivity is suitable for high impedance dynamic or crystal microphones.

Constructors not requiring the microphone input can simply omit all the components associated with this stage, or if only mono microphone operation is required only one microphone input stage need be built and the output can be fed to both mixers via separate 100 kilohm resistors (R56, R156). Potentiometer VR3 in this case need only be single gang.


The table below summarises the performance of the microphone input stage:

INPUT MIXER

The input mixer works on the virtual earth principle which is explained in Fig. 29. Because the input impedance at the base of the TR18 is low—only about 100 ohms—it can for all practical purposes be considered as a short circuit to earth, hence the name virtual earth amplifier. The total input current when

Table 1

	"Lo"	"Hi"
Input Sensitivity	1mV	10mV
Input impedance	1MΩ	2MΩ
Distortion	less than 0.005% at 1mV input and less than 0.05% at 20dB overload	less than 0.005% at 10mV and less than 0.02% at 20dB overload
Frequency response	65Hz to 70kHz at -3dB	10Hz to 200kHz at -3dB. With 500pF source (crystal microphone) frequency response is -3dB at 60Hz
Signal to noise ratio at rated sensitivity	-60dB with 100Ω source, -56dB with 1KΩ source, unweighted, 20Hz to 20kHz	-70dB with 1kΩ source, -56dB with 50KΩ source, unweighted, 20Hz to 20kHz

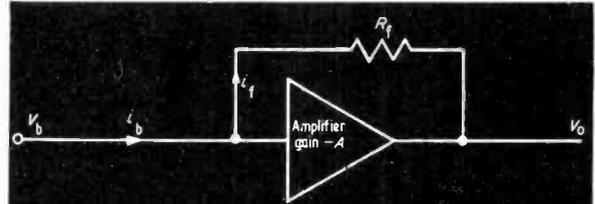

If input voltage = V_b

Then output voltage $V_o = -AV_b$


Input impedance = $\frac{V_b}{i_b} = \frac{V_b}{i_f}$ if the input current of the amplifier itself is neglected

But $i_f = \frac{V_b - V_o}{R_f} = \frac{V_b + AV_b}{R_f}$

Therefore input impedance = $\frac{R_f}{1 + A}$

In the actual circuit $R_f = 220k\Omega$ and A is approximately 2000 giving an input impedance of about 100Ω.

Fig. 29a. Virtual earth amplifier—functional diagram

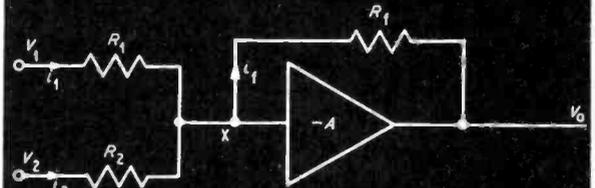

Because point X is "virtually" at earth potential the total input current when used as a mixture is

$$i_1 + i_2 = \frac{V_1}{R_1} + \frac{V_2}{R_2} = i_b$$

The output voltage $V_o = i_b R_f = \frac{V_1 R_f}{R_1} + \frac{V_2 R_f}{R_2}$

i.e. the gain from each input is given by the ratio of R_f to the appropriate input resistor and the output is proportional to the sum of the individual input currents

Fig. 29b. Virtual earth amplifier as a mixer

used as a mixer is then just simply the sum of the input currents from each signal source, which enables the microphone input to be mixed with any of the other inputs without interaction.

The input sensitivity at the tape, tuner and aux, inputs is 100mV with an input impedance of 50 kilohms, and the output at the emitter of TR19 is 400mV. Capacitor C34 is a bootstrap capacitor which increases both the gain and the available output voltage swing to give minimum distortion. At 1kHz the distortion produced is below 0.005 per cent at rated sensitivity and below 0.02 per cent at 20dB overload, at 10kHz these figures become 0.01 per cent and 0.1 per cent respectively. The circuit will give an output of 10 volts r.m.s. (28dB overload) before clipping occurs. Signal to noise ratio at rated sensitivity is -80dB (unweighted 20Hz to 20kHz).

To be continued

AUDIO TRENDS

By F. C. JUDD


WHEN stereophonic sound reproduction made its debut, only a few years ago, the various manufacturers who exhibited at the annual Audio Fair were quick to take advantage of the "moving sound" illusions that could be created with stereo. These consisted mainly of the sounds of express trains and racing cars, etc. which hurtled across the demonstration rooms at breakneck speed, and of phantom ping-pong games in which you followed the movement of the ball without seeing it. After being subjected to this and other subtle forms of audio brain-washing, you went home either cross-eyed or cross-eared but nevertheless convinced that stereo had something even if it was only two of everything.

Now it seems that stereo is out—two channel stereo that is. The "in thing" is four channel stereo alias quadrasonic, alias CD-4 alias surround sound, call it what you like. At least that's one impression gained at the 1970, 16th International Audio and Music Fair held in October at Olympia. This time, no trains and no ping-pong game. This time they sat you down in the middle with the sound all around and intensified the audio brain-washing with real solid state power.

PRACTICAL ELECTRONICS went one better. With their demonstration of the "P.E. Gemini" stereo amplifier, visitors were also treated visually with the "P.E. Aurora", an audio controlled light display, which can be adapted by the constructor for domestic settings. (Details of "Aurora" will be published very soon as a constructional project—Ed.)

FOUR CHANNEL—ON DISC

JVC-Nivico (Victor Company of Japan) recently announced their new four channel disc stereo system and its reproducing equipment known as CD-4. This was demonstrated at Olympia and is claimed to be high fidelity and also compatible with existing two channel reproducing equipment, i.e. the CD-4 four channel discs can be played on conventional two channel equipment and two channel discs can be played on CD-4 equipment.

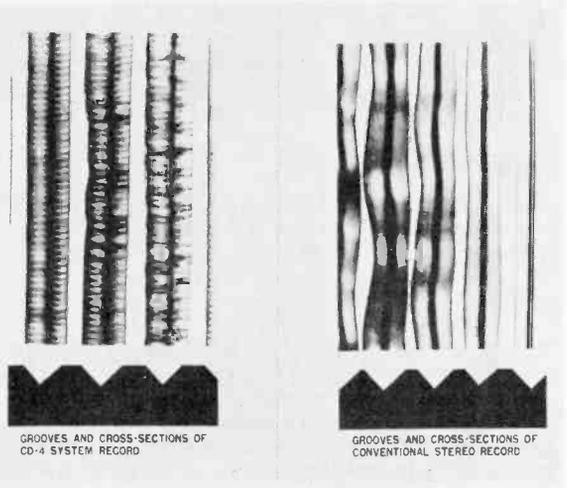

Comparison of CD-4 disc and conventional stereo record

The four channels are cut in one groove and according to the very limited technical information at present available, the system features both frequency and phase modulation which are combined to carry the signals for the extra channels. Reproduction requires four separate amplifier channels and four loudspeakers. Two loudspeakers are positioned in front of the listener and two at the rear. The photographs show the difference between recording on a two channel stereo disc and the new CD-4 disc. The U.K. distributors are Denham and Morley Limited, Denmore House, 453 Caledonian Road, London, N.7.

FOUR CHANNEL—ON TAPE


The Audiosonic system, which is four channel stereo on tape, was also demonstrated at Olympia by JVC-Nivico. The system employs four separate tape heads and offers various ambionic arrangements for the listener, i.e. two speakers in front and two at the rear or three in front and one at the rear or all four at the front. The makers claim that the system presents truly "solid music" with complete freedom of movement for the listener. As the two recommended twin channel Nivico amplifiers for this system are each rated for 140W music power (total 280W) the system could present some pretty solid sound as well.

Nivico four channel disc player



ROC ELECTRONICS

50 PROJECT ELECTRONIC KIT Model R.130

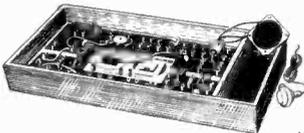

King of the Roc Electronic Kits is the Giant R.130 which makes up into no less than 50 separate projects including Radio Receivers, Transmitters, Tachometer, Rain Alarm, Testers, Electronic Switches, Amplifiers and even an Electronic Target Game. As well as a carphone, speaker, meter, relay, transformer, solar cell, buzzer, etc., etc., the R.130 is supplied complete with a fitted hardwood case and clear detailed instructions for all 50 projects.

PRICE £7.19.0

20 PROJECT SOLAR ELECTRONIC KIT Mod. R.128

This ultra modern Project Kit is shaped for the space age. Carried inside a transparent domed 4 1/2 inch capsule the R.128 comes complete with a self-contained solar cell to power any one of 20 projects ranging from a one transistor radio to a Morse set complete with key and Morse training code. Supplied complete with easy to follow instructions and even the cement to assemble this unique electronic space capsule.

PRICE £4.10.0

2 OCTAVE ELECTRONIC ORGAN KIT Mod. R.129

Complete with a music book containing 10 easy to play songs the R.129 solid state organ kit covers 2 full octaves. Slotting into a fitted hardwood case the top panel carries the key assemblies and all the components including the loudspeaker. Like all Roc Electronic Kits every item is included down to the last nut and bolt so that the constructor can start assembly within minutes of opening the package.

PRICE £4.10.0

10 PROJECT INTEGRATED CIRCUIT KIT Model R.127

Using a robust Solid State Integrated circuit the R.127 kits will build any one of these projects: (1) Germanium Radio, (2) Test Oscillator, (3) Morse Telegraph Training Set, (4) I.C.T. Transistor Radio, (5) Germanium J Transistor Radio, (6) Reel Player Amp, (7) Continuity Tester, (8) AF Signal Tracer, (9) Radio Transmitter, (10) Water Purity Tester.

PRICE £3.10.0

2 TRANSISTOR SOLAR RADIO KIT Model R.126

Like all Roc Electronic Kits the R.126 uses reliable no-solder connections to produce a complete 2 transistor radio in under 2 hours. As well as battery operation the kit is supplied complete with a solar cell to provide power from the Sun or any strong light source.

PRICE £2.10.0

CRYSTAL RADIO KIT Model R.125

This easy to build Radio is based on the same circuit developed by Marconi for the very first radio transmission but uses a modern ferrite aerial for maximum efficiency. A perfect introduction to Radio Theory.


PRICE £1.10.0

5 WATT STEREO INTEGRATED AMPLIFIER CHASSIS Model R.123

Mounted on a heavy gauge chassis the fully transistorised R.123 stereo amplifier is completely self-contained even down to ganged volume and separate tone controls. For a simple stereo amplifier of excellent quality all you have to provide is the cabinet and control knobs.

SPECIFICATION:
Output: 5W total, 2.5W per channel.
Input sensitivity: 600mV at 2:2Mohms.
AC 240V operation.

PRICE £4.19.0

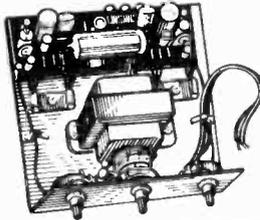

5 WATT 8 TRACK CARTRIDGE STEREO AMPLIFIER Model R.133

Just slot in one of the many 8 track cartridge tapes available for a continuous programme of your favourite music. A manual programme override switch enables you to switch from one track to the next at the push of a button at the same time a numbered indicator lights up to show which track is playing. Beautifully finished in an oiled walnut cabinet the R.133 is mechanically engineered to provide long and reliable service. **SPECIFICATION:**—Tape speed: 9.5 cm/sec (3 1/2 i.p.s.). Wow & flutter: better than 0.3%. Frequency range: 40-12,000Hz. Cross talk: better than 45dB at 1,000Hz. Output: 5W total, 2.5W per channel. Amplifier outputs: 200mV.

PRICE £36.0.0



STEREO HEADPHONES Model R.328

Built up to a standard not down to a price, the R.328 stereo headphones represent a breakthrough in value for money.

A valuable addition to any stereo installation they will provide many hours of listening pleasure. **SPECIFICATION:**
Matching impedance: 8-16 ohms.
Frequency range: 30-15,000Hz.

PRICE £2.8.0



FOUR BAND SHORT WAVE RECEIVER KIT Model R.140



This excellent transistorised battery operated kit will not only provide hours of entertainment when made up but also in its construction. It receives the normal broadcast band 550kHz to 1.6MHz and on short wave 1.5-30MHz in three bands. The 32-page manual not only shows step by step instructions on how to assemble the kit but also includes a guide on broadcasting stations throughout the world.

PRICE £9.8.0



PROFESSIONAL SOLID STATE FOUR BAND COMMUNICATION RECEIVER Model R.135

This is the communication receiver that you have long been waiting for. Fully transistorised and continuous coverage from 550kHz to 30MHz in four bands including illuminated electronic bandspread for 150-10 metres. Also incorporated is an internal speaker, automatic noise limiter, 88B/AM/CW Switch, AVC Switch, S Meter, Receive and Standby Switch, external socket for headphone or speaker, bandspread control, BFO control, on/off/AF gain, band selector, antenna trimmer and RF gain. The R.135 will run off of 240V a.c. dry batteries or any 12V d.c. negative ground source.

PRICE £45.0.0



10 WATT BUDGET STEREO ALL TRANSISTOR AMPLIFIER Model R.136



Ideal as a second stereo system or for the newcomer to Hi-Fi who wishes to upgrade existing equipment the R.136 sounds every bit as good as it looks. As well as inputs for crystal or ceramic cartridge the R.136 has a Stereo Tuner input which accepts the matching R.134 Stereo AM/FM Tuner.

The Satin Finish front panel carries a stereo headphone socket as well as volume, balance, tone, (all ganged) speaker, mode and selector controls. Supplied complete with oiled walnut enclosure.

SPECIFICATION: Output: 10 watts total, 5 watts per channel. Frequency Range: 35-18,000Hz. Inputs: Phono and Tuner.

PRICE £13.0.0



AM/FM/MPX STEREO TUNER Model R.134



Perfect Matching Unit to the R.136 Amplifier. The R.134 Stereo Tuner is designed to give years of reliable performance. The Tuning Band covers AM & FM with a separate stereo beacon to indicate when stereo broadcasts are being received.

SPECIFICATION:
FM: frequency range: 88-108MHz.
Usable sensitivity: 18µV. Stereo separation: 26dB at 1kHz. Image rejection: 53dB. AM: frequency range: 535-1,805kHz. Usable sensitivity: 290µV.

PRICE £21.0.0



4 WATT STEREO FM/AM/MPX TUNER AMPLIFIER Model R.124

Another Roc Exclusive offering top value for money performance the R.124 is a Stereo Tuner/Amp with facilities only usually found in much more expensive units. Features like separate bass and treble controls, automatic frequency control switch and stereo headphone socket give the R.124 a price to specification ratio second to none.

Housed in a handsome walnut cabinet the classical low line styling of the R.124 will grace any home. **SPECIFICATION:** FM: Frequency Range: 88-108MHz. Usable sensitivity: 20µV. Stereo Separation: 26dB at 1kHz, 20dB minimum. Image Rejection: 53dB. AM: Frequency Range: 535-1600kHz. Usable Sensitivity: 300µV. Audio Section: Total Output Power: 4W. Phono Input: 200mV at 1MΩ. Tape Input: 100mV at 100KΩ.

PRICE £29.19.0



H.P. Terms available for personal callers on purchases over £30.
RETURN OF POST MAIL ORDER SERVICE Dept. PE

Orders under £10 please add 5/- post and packing. Orders over £10 sent post free.

ROC ELECTRONICS LIMITED
193 EDGWARE ROAD LONDON W2 1ET

TELEPHONE: 01-723 6211

Shop open 9-6 Monday-Saturday (Thurs. 1 p.m.)

SURROUND STEREO

A cheaper and perhaps equally effective "ambionic" system known as "surround stereo" can be devised using any conventional two channel stereo equipment plus one extra loudspeaker. This system is introduced in a leaflet included with the new EXP-70 LP disc called "This is Stereo".

This record, one of the EXP Technical Series, will by now be available from all record dealers price 39s. It is a combined stereo demonstration and test record containing various recordings that illustrate not only the dynamic and spatial possibilities that stereo offers, but also includes test tracks for adjustment of experimental "surround stereo" systems described in the leaflet and for balance and phasing, etc. of two channel stereo.

SOME NEW AUDIO PRODUCTS

Although over 80 manufacturers were exhibiting at the 1970 Audio and Music Fair, few completely new products were to be seen. Most manufacturers were showing their current ranges of equipment, a good deal of which has already been publicised in the technical press.


The new Wharfedale Aston wall mounting loudspeaker was one new product and this breaks away from the old hi-fi tradition of dark veneer and rather uninspiring front covering. These speakers are available in glossy white enamelled cabinets and the front is finished with what Wharfedale call their "silver fox" fabric which looks like shiny metal. The Aston speaker system comprises an 8 inch bass unit and 3 inch treble unit and the cabinet measures $19 \times 11\frac{1}{2} \times 4\frac{1}{2}$ inches. Power handling capacity is 18 watts r.m.s. and the input impedance 4 to 8 ohms. These and the new Wharfedale Triton speakers, also released at the same time, are available in matched stereo pairs complete with 15 feet of connecting cables and DIN plugs.

LOUDSPEAKERS FOR THE FUTURE

The loudspeaker has always been the most inefficient link in an audio reproducing system requiring as it does a comparatively large amount of audio power to produce a useful sound output. J. B. Lansing Sound Inc. of America have not only found a way of increasing efficiency but also of producing better sound distribution. Most of their loudspeakers are intended for professional studio use but one known as Aquarius 4 has been designed for domestic use and was introduced at the Audio and Music Fair.

Mounted inside the enclosure is an 8 inch wide range transducer directed upward into a radial horn. This spreads the sound through a 360 degrees horizontal radial defraction slot. The higher frequencies emerge in a 360 degree vertical plane from a 2 inch driver separately loaded by a radial horn mounted at the rear of the enclosure. The result is a much wider distribution of sound than would be obtained with a conventional system.

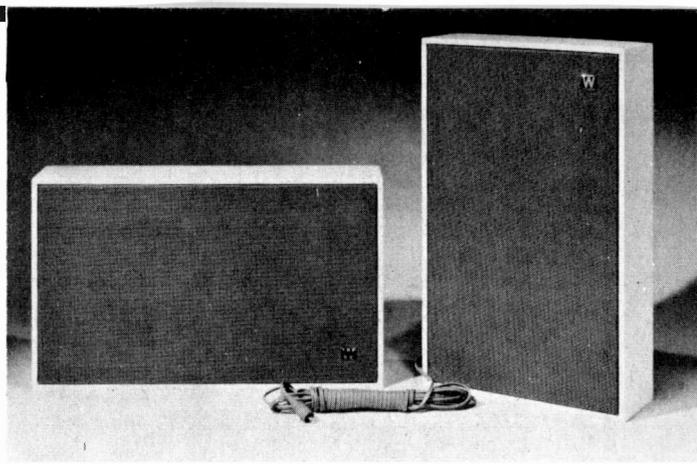The Aquarius 4 will handle power up to 30 watts r.m.s. but nothing like this power is necessary for life size sound because of the high efficiency. The same company also manufacture a very compact studio monitor speaker for power capacity up to 75 watts. The U.K. distributors are Feldon Recording Limited, 126 Great Portland Street, London, W.1.




Wharfedale Aston, wall mounting loudspeaker

LESS NOISE PLEASE

The Dolby noise reduction system has, until recently, been available only for studio use. Kellar Electronics Limited have now introduced two Dolby type B noise reduction units for use with any domestic tape recorder having radio or line inputs and line or external amplifier outputs. The KDB1 unit is switchable from record to replay and is for use with recorders having a combined record/replay head. This retails at £45. The second unit, known as the KDB2, has two separate record and replay channels for use with machines having separate record and replay heads and retails at £75. Both units are supplied complete with stabilised power supplies and VU meters and are for two channel (stereo) operation.

Kellar Electronics have also released a combined cassette recorder/amplifier known as type DTA50, with a built-in Dolby noise reduction system the retail price of which will be £148 4s 8d. It seems likely that a noise reducing system will become an integrated part of all domestic as well as professional tape recorders. Cassette tape recorders are a very obvious choice to begin with as few have a noise performance of better than -40dB.

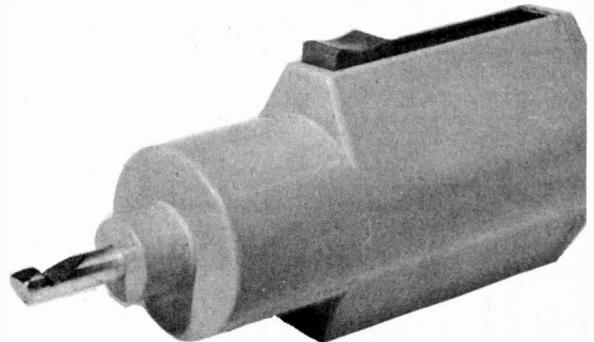Tape head magnetisation is one of the most common causes of high noise level on tape recordings. Tape heads should therefore be frequently demagnetised with a defluxing tool. Together with many other new audio accessories that Ferrograph have just released is a new tape head demagnetiser, their Defluxer type D/2 which retails at £4. The outlay is a very worthwhile



Ferrograph tape head demagnetiser

LOOK!

PRACTICAL!

VISUAL!


EXCITING!



a new 4-way method of mastering
ELECTRONICS
by doing — and — seeing . . .


1 ▶ **OWN and HANDLE** a

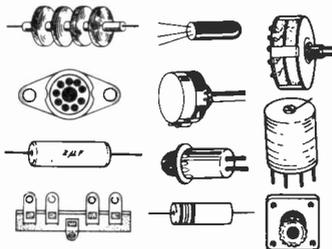complete range of present-day **ELECTRONIC PARTS and COMPONENTS**




2 ▶ **BUILD and USE**

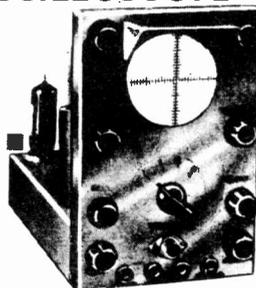a modern and professional **CATHODE RAY OSCILLOSCOPE**



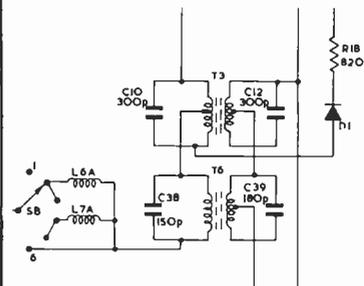3 ▶ **READ and DRAW and UNDERSTAND** **CIRCUIT DIAGRAMS**



4 ▶ **CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .**

- | | | |
|--------------------------|--------------------------|------------------------|
| ● VALVE EXPERIMENTS | ● PHOTO ELECTRIC CIRCUIT | ● A.C. EXPERIMENTS |
| ● TRANSISTOR EXPERIMENTS | ● COMPUTER CIRCUIT | ● D.C. EXPERIMENTS |
| ● AMPLIFIERS | ● BASIC RADIO RECEIVER | ● SIMPLE COUNTER |
| ● OSCILLATORS | ● ELECTRONIC SWITCH | ● TIME DELAY CIRCUIT |
| ● SIGNAL TRACER | ● SIMPLE TRANSMITTER | ● SERVICING PROCEDURES |

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: we do not employ representatives

NAME..... BLOCK CAPS

ADDRESS..... PLEASE P.E. 1

STEPHENS

ELECTRONICS
P.O. BOX 26
AYLESBURY
BUCKS.

SEND S.A.E. FOR LISTS
GUARANTEE
Satisfaction or money
refunded

The Diamond Tip is .007in radius, thus making it compatible to play stereo records on mono equipment without damage to the record; and of course full stereo.

BRITISH MADE
EXPORT ENQUIRIES WELCOMED

CARTRIDGES

ACOS	Inc. P.T.		Inc. P.T.
	each		each
GP9	12/6	SX3M	S/8
GP91-18C	21/6	SX6H	S/8
2-11	17/9	SX5M	D/8
12-49	15/6	SX5H	D/8
50-500	13/6	X4N	D/8
GP91-28C		GOLDRING	
GP91-38C		860	55.50
Suitable to replace TC8,		G800	27.70
etc.		1800E	215.00
GP92	26/5	G800 Super E.	218.10
GP93-1	24/9		
GP94-1	31/-	ROWETTE	
GP94-5	36/-	106	S/8
GP95	24/9	106	S/8
GP96	31/10	DC400	S/8
Acos 104	1-10	DC400S	S/8
11-25	39/9	105	D/8
25-50	38/3	106	D/8
51-499	35/5	DC400	D/8
		DC400SC	D/8
		SOMOTONE	
		8TA	D/8
		9TA	D/8
		9TAHC	D/8

STYLII

ACOS	Sapphire	Diamond	ELAC KST9 (PE1B)	Sapphire	Diamond
GP99	2/6	7/6	ER5MB	6/6	9/6
GP65	2/6	7/6	ER5MX	6/6	9/6
GP91-3	2/6	7/6	ER5 SB	6/6	9/6
GP73-1	2/6	7/6	ER60 Stereo	6/6	9/6
GP73-2	2/6	7/6	DECCA		
GP79	2/6	7/6	Deram., diamond only		27/9
GP81-1	2/6	7/6	GARRARD		
GP91-1	2/6	7/6	EY26 Stereo	2/6	7/6
GP91-2	2/6	7/6	GC2	2/6	7/6
GP91-3	2/6	7/6	GC8	2/6	7/6
GP91-18C	2/6	7/6	GC812	2/6	7/6
GP91-38C	2/6	7/6	GC810/1	2/6	7/6
GP93-1	2/6	7/6	GC810/2	2/6	7/6
GP94-1	2/6	7/6	S 1-2-3	2/6	7/6
GP95-1	2/6	7/6	TS1	2/6	7/6
GP96	2/6	7/6	TS2	2/6	7/6
GP97	2/6	7/6	TS3	2/6	7/6
104	2/6	7/6	GOLDRING		
B.S.R.			CM50	2/6	7/6
BSR CI (ST3)	6/6	9/6	CM50	2/6	7/6
BSR TC5H	2/6	7/6	MX1	2/6	7/6
BSR TC8M	2/6	7/6	MX2	2/6	7/6
BSR ST8	6/6	9/6	Stereo C890	2/6	7/6
BSR ST9	6/6	9/6	PERPETUUM ERNER		
BSR ST10	9/-	12/6	PE188	6/6	9/6
BSR X1M	6/6	9/6	PHILIPS		
BSR X1H	6/6	9/6	AG3016	2/6	7/6
BSR X3M	6/6	9/6	AG3063	2/6	7/6
BSR X3H	6/6	9/6	AG3306	2/6	7/6
BSR X4H	6/6	9/6	AG3100/3306	2/6	7/6
BSR X5H	6/6	9/6	AG3400	2/6	7/6
COLLARO			RONETTE BINFLOID		
Collaro Studio "O"	2/6	7/6	BF40	2/6	7/6
Collaro-Ronett TX88	2/6	7/6	DC284	2/6	7/6
Collid 8K1	2/6	7/6	SOMOTONE		
Dual CDS2/CDS3	6/6	9/6	3T	6/6	9/6
Dual CDS/329	6/6	9/6	8TA	6/6	9/6
(DN3)	6/6	9/6	9TA	6/6	9/6
ELAC KST9 (PE10)	6/6	9/6	9TA/HC	6/6	9/6
			19T	6/6	9/6
			20T	2/6	7/6

DE BANKS MAGNETIC RECORDING TAPES

POLYESTER			POLYESTER		
Length	Spool Size in.	Price	Length	Spool Size in.	Price
Standard Play			900 ft.	5	14/-
600 ft.	5	10/-	1200 ft.	5 1/2	17/-
850 ft.	5 1/2	12/6	1800 ft.	7	20/-
1200 ft.	7	14/-	Double Play		
Long Play			1800 ft.	5	17/6
210 ft.	3	5/8	1200 ft.	5 1/2	22/-
400 ft.	4	3/6	2400 ft.	7	26/-

EMPTY TAPE REELS

3 in.	1/6
4 in.	1/10
5 in.	2/3
5 1/2 in.	2/6
7 in.	2/7

CASSETTES

Boxed in Plastic Library Packs	
C60	10/6
C90	12/6
C120	17/6

P. & P. 1/6 on all orders.

SEMICONDUCTORS BRAND NEW MANUFACTURERS' MARKINGS NO REMARKED DEVICES

2N388A	12/6	2N2613	7/-	2N3708	3/6	2N5267	52/6	AC128	4/-	BC115	6/6	BD132	18/6	BFY30	10/-	D1614	8/-	NKT238	5/-	OC22	10/-
2N404	4/6	2N2614	6/-	2N3709	3/6	2N5305	7/6	AC164	4/6	BC116	12/6	BDY10	27/6	BFY41	10/-	GET102	6/-	NKT240	5/6	OC23	10/-
2N696	4/6	2N2646	11/6	2N3710	4/6	2N5306	8/6	AC176	5/6	BC116A	6/6	BDY11	37/6	BFY43	12/6	GET113	4/6	NKT241	5/6	OC24	11/6
2N697	4/6	2N2696	6/6	2N3711	4/6	2N5307	7/6	AC187	12/6	BC117	7/6	BDY17	37/6	BFY50	4/6	GET114	4/6	NKT242	4/6	OC25	10/-
2N698	5/6	2N2711	6/6	2N3713	3/6	2N5308	7/6	AC188	7/6	BC118	6/6	BDY18	49/6	BFY51	4/6	GET118	4/6	NKT243	12/6	OC26	10/-
2N699	12/6	2N2714	6/6	2N3714	35/-	2N5309	12/6	AC171	5/6	BC121	4/6	BDY19	62/6	BFY52	4/6	GET119	4/6	NKT244	3/6	OC28	12/6
2N706	2/6	2N2713	5/6	2N3819	7/6	2N5310	5/6	ACY18	5/6	BC122	4/6	BDY30	30/6	BFY53	4/6	GET120	10/6	NKT245	12/6	OC29	15/-
2N706A	2/6	2N2714	6/6	2N3823	22/6	2N5354	5/6	ACY19	5/6	BC125	11/-	BDY38	18/6	BFY56	11/6	GET873	2/6	NKT261	4/6	OC35	8/-
2N708	3/6	2N2865	12/6	2N3826	6/6	2N5355	5/6	ACY20	5/6	BC126	11/-	BDY60	36/6	BFY75	6/6	GET880	6/6	NKT264	6/6	OC36	12/6
2N709	12/6	2N2904	7/6	2N3854	5/6	2N5356	5/6	ACT21	5/6	BC134	11/6	BDY61	36/6	BFY76	6/6	GET887	4/6	NKT271	4/6	OC41	4/6
2N718	5/6	2N2904A	8/6	2N384A	5/6	2N5366	9/6	ACY22	4/6	BC140	7/6	BDY62	27/6	BFY77	11/6	GET889	4/6	NKT272	4/6	OC42	5/6
2N718A	8/6	2N2925	8/6	2N3855	5/6	2N5366	9/6	ACY28	4/6	BC147	3/6	BFY115	5/6	BFY90	13/6	GET890	4/6	NKT274	4/6	OC44	4/6
2N726	6/6	2N2906	6/6	2N3856A	6/6	2N5367	11/6	ACY40	4/6	BC148	3/6	BFY117	9/6	BFW68	5/6	GET896	4/6	NKT275	4/6	OC45	2/6
2N727	6/6	2N2906	6/6	2N3856	6/6	2N5457	7/6	ACY41	5/6	BC149	3/6	BFY163	7/6	BFW69	5/6	GET897	4/6	NKT281	4/6	OC46	3/6
2N914	3/6	2N2906A	6/6	2N3856A	6/6	2N5457	7/6	ACY44	8/6	BC182	3/6	BFY167	5/6	BFW68	5/6	GET898	4/6	NKT401	17/6	OC70	3/6
2N916	3/6	2N2907	8/6	2N3858	5/6	2N5020	37/6	AD140	8/6	BC157	4/6	BFY173	6/6	BPX25	37/6	MAT100	6/6	NKT402	18/6	OC71	2/6
2N918	6/6	2N29023	3/6	2N3858A	6/6	2N5102	6/6	AD149	11/6	BC158	3/6	BFY177	6/6	BPX29	36/6	MAT101	6/6	NKT403	15/6	OC72	2/6
2N929	4/6	2N2924	3/6	2N3859	5/6	2N5103	6/6	AD150	12/6	BC159	4/6	BFY178	7/6	BPY10	29/6	MAT120	6/6	NKT404	12/6	OC74	6/6
2N930	8/6	2N2925	3/6	2N3859A	6/6	2N5104	6/6	AD161	7/6	BC160	12/6	BFY179	14/6	BSX19	3/6	MAT121	6/6	NKT405	15/6	OC75	4/6
2N937	10/6	2N2926	6/6	2N3859A	6/6	2N5105	5/6	AD162	7/6	BC167	3/6	BFY180	7/6	BSX20	3/6	MJ400	2/6	NKT406	12/6	OC76	4/6
2N1131	5/6	Green	2/6	2N3860	6/6	2N5602	5/6	ACY18	6/6	BC168	5/6	BFY183	7/6	BSX21	7/6	MJ420	4/6	NKT451	12/6	OC77	5/6
2N1132	6/6	Yellow	2/6	2N3877	8/6	2N5053	15/6	ACY44	8/6	BC168C	3/6	BFY184	5/6	BSX26	9/6	MJ421	22/6	NKT452	12/6	OC78	5/6
2N1302	3/6	Orange	2/6	2N3877A	8/6	2N5053	15/6	AD140	8/6	BC169B	2/6	BFY185	8/6	BSX27	9/6	MJ430	20/6	NKT453	9/6	OC81	5/6
2N1303	3/6	2N3011	6/6	2N3900	7/6	2N5128	18/6	AF116	5/6	BC189C	3/6	BFY194	4/6	BSX28	6/6	MJ440	19/6	NKT463	6/6	OC81D	4/6
2N1304	4/6	2N3014	6/6	2N3900A	8/6	2N5140	19/6	AF117	5/6	BC170	3/6	BFY195	5/6	BSX60	16/6	MJ480	19/6	NKT613F	6/6	OC83	5/6
2N1305	4/6	2N3053	5/6	2N3901	19/6	2N5141	19/6	AF118	12/6	BC171	3/6	BFY196	6/6	BSX61	12/6	MJ481	25/6	NKT674F	6/6	OC84	5/6
2N1306	5/6	2N3054	11/6	2N3902	7/6	2N5142	17/6	AF119	4/6	BC172	3/6	BFY197	6/6	BSX76	4/6	MJ490	20/6	NKT677F	6/6	OC139	6/6
2N1307	5/6	2N3055	15/6	2N3904	7/6	2N5143	17/6	AF124	4/6	BC176	5/6	BFY198	8/6	BSX77	5/6	MJ491	22/6	NKT682	5/6	OC140	6/6
2N1308	6/6	2N3133	6/6	2N3905	7/6	2N5152	22/6	AF125	4/6	BC182	4/6	BFY200	7/4	BSX78	5/6	MJ1800	43/6	NKT683	5/6	OC149	6/6
2N1309	6/6	2N3134	6/6	2N3906	7/6	R.C.A.	7/6	AF126	4/6	BC183	4/6	BFY224	6/6	BSY10	5/6	ME340	12/6	NKT734	5/6	OC189	4/6
2N1367	5/6	2N3135	5/6	2N4058	5/6	400650	13/6	AF127	3/6	BC184	4/6	BFY226	6/6	BSY11	5/6	ME520	17/6	NKT736	7/6	OC191	6/6
2N1368	7/6	2N3136	5/6	2N405																	

safeguard against the high noise level that can be imparted even to pre-recorded tapes if a tape head has become magnetised.

Another new and useful device suitable for all current Ferrograph tape recorders is a signal operated switching unit which starts the recorder on arrival of wanted signals and stops it again automatically when the signals cease. The device operates from a lowest signal level of 400mV and has an adjustable over-run time of 5 to 25 seconds; retail price £30.

MUSIC AT THE FAIR

A few large musical instrument distributors were showing currently available instruments, such as electronic organs, guitars and amplifiers, but nothing that could be described as new could be found.

One of the highlights in the music field, however, was the Moog Synthesiser which is an electronic music composition and performance system. The system is partly keyboard operated but consists mainly of a large number of voltage controlled oscillators and filters



The Moog Synthesiser — this version would cost between £2,250 and £3,000

which can be interconnected to produce the pitch, waveform and envelope for an infinite range of musical sounds and even of "pseudo" human voices. One of the larger versions of the Moog Synthesiser is shown on this page but such devices are hardly for domestic use since the price range is £2,250 to over £3,000. However, a small synthesiser suitable for schools and small studio use will shortly become available at less than £600. The present U.K. distributors for Moog Synthesisers are Feldon Recording Limited, 126 Great Portland Street, London, W.1.

The designer of the Synthesiser, Dr R. A. Moog, who gave a lecture on and a demonstration of the instrument at Olympia, spoke of the possibility of combining the music synthesiser with a conventional electronic organ resulting in a musical instrument with variable voicing and effects that could be chosen at will by the player. There is already some indication of this idea in modern electronic organs.

AUDIO PRESENTATION PROGRAMME

Visitors to the Fair were also able to hear a series of lectures (many with demonstrations) by well-known

experts in sound reproduction and music. Among these were Dr R. A. Moog mentioned above, P. J. Baxandall, inventor of the almost universally used Baxandall tone control network, Desmond Briscoe from the BBC Radiophonics Workshop and Sir Arthur Bliss (Master of the Queen's Music). Many well-known audio journalists and designers also gave talks on high fidelity sound reproduction. Other special features included a recording studio where visitors could make a record, a search for a singer contest, a music tuition bookshop and a comprehensive display of musical instruments of all kinds.

A number of films of interest to audio enthusiasts such as "The Timeless Track" and "The Magic Tape" by B.A.S.F. and "Sound on Tape" by Philips Limited, were also shown during the week of the fair. All this, together with the displays and demonstrations of products by over 100 exhibitors made the 1970 Audio and Music Fair a successful and interesting venture for both the exhibitors and the visitors. However, the exhibiting manufacturers of audio equipment still had the problem of accommodating a worthwhile number of people during demonstrations; the demonstration cubicles were just not large enough.

NEW RELEASES

Rola Celestion Limited—a new loudspeaker—the Ditton 120. The 120 was displayed at the Audio Fair; it consists of three units, an HF1300 treble speaker, a long throw mid range and bass speaker and an audio bass resonator (A.B.R.) all housed in a case measuring $17 \times 7\frac{1}{2} \times 8\frac{1}{2}$ inches. Frequency response is 30Hz to 15,000Hz, power handling is 20W DIN, impedance is 4 to 8Ω; the speakers are available in matched pairs and cost £48 per pair.

K.E.F. Electronics Limited—a new range of loudspeakers known as the Cresta, Chorale, Cadenza and Concerto and each has a three speaker system. The Cadenza was released at the Audio and Music Fair and is a completely new system with a passive bass radiator. Frequency range 30 to 30,000Hz. Power handling capacity 25 watts at 8 ohms.

Uher-Bosch Limited—a new tape recorder, the Uher 724, which is a quarter-track stereo machine for $7\frac{1}{2}$ and $3\frac{1}{2}$ i.p.s. Specification is to DIN standards with an output power of 2 watts per channel. The recorder operates in the vertical or horizontal position. Retail price is £103 10s 0d plus £25 11s 5d p.t. Uher have also introduced a new portable cassette recorder for C60, C90 or C120 tapes and which features a reversible drive system to obviate having to turn the tape cassette over. Price not available at time of writing.

B.A.T.R. CONTEST

Prizes were presented at the Audio and Music Fair to winners of the 1970 British Amateur Tape Recording contest. The "Tape of the Year" winner was Mr K. McKenzie for his documentary tape called "Sunderland Hospital Broadcasts". For this he was awarded the Emitape Challenge Cup and also the Philips Shield for the best recording in the documentary class.

The 1971 and 14th British Amateur Tape Recording Contest has already been announced with a closing date of 30th June, 1971. Entry forms are available from the Secretary, B.A.T.R. Contest, 37 Fairlawnes, Maldon Road, Wallington, Surrey. As before there are six categories to choose from including one for schools.

DIGI-CLOCK

By R. W. Coles

Part 2

THE alarm board "B" carries the logic and oscillator circuitry required by the alarm system, and the 5 volt regulator, which provides the highly stable supply required by all the i.c.s used in the clock. The board is physically smaller than the main clock board "A", being a "Dualine" DL109/22, which has positions for nine 14/16 pin DIL packages, and is equipped with a single-sided 22-way edge connector.

Six i.c.s are used in all, but two of these are CA3046 transistor arrays which are 14-pin packages containing five individual transistors. These are not members of the TTL family used to perform all the clock and alarm logic.

ALARM OPERATION

The time at which the alarm is required to sound is entered by means of a bank of thumbwheel switches S2a and S2b mounted adjacent to the display on the front of the clock.

These switches are so constructed that they give a four-bit binary coded decimal output pattern for each number selected. This b.c.d. word is continuously compared with the b.c.d. output from the clock counters in a digital comparator (see Fig. 7). When the switch setting and the display are the same, the output of the comparator falls to a low level and is used to set a simple "latch" bistable in IC18.

The output of the latch enables a gate G5c which allows the alarm tone through to a 40 ohm moving-coil speaker, and thus the alarm is sounded. The alarm will

continue indefinitely unless reset by means of the miniature toggle switch S3, also mounted on the front of the clock.

The alarm setting accuracy could be extended to any degree by simply adding more switches and increasing the comparator size. A setting to within 0.1 second is quite possible if required, but with the prototype the system was intended for domestic use, and time setting in ten minute increments was considered adequate.


It was also considered unnecessary to include the hours 10.0 to 12.50 in the comparison, thus saving an expensive switch bank which would have been necessary in the "tens-of-hours" position. If this expense is unimportant, or if the aesthetic consequences of using a toggle switch in this role (for this is all that is required in this position) can be tolerated, these times are easily added because the comparator as described has allowance for this extra switch.

There is therefore a considerable amount of flexibility in the alarm circuitry which allows individual constructors to tailor the system to their own requirements.

ALARM CIRCUIT

The circuit of the alarm system is given in Fig. 7, and it can be seen that it is not very complicated at all. Of course, the alarm circuit can be omitted altogether without affecting the remainder of the clock circuit.

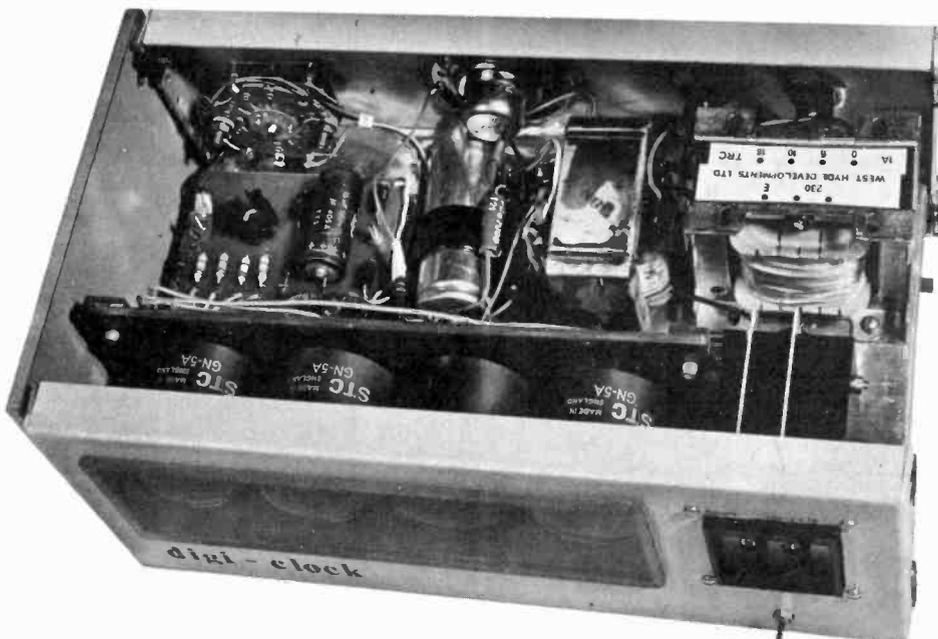The digital comparator is formed from two SN7483 MSI packages, each containing four complete full-adders, with internally connected ripple through carry.



LOW COST ELECTRONIC & SCIENTIFIC EQUIPMENT & COMPONENTS

MOTORS

SHADED POLE MOTORS 120V 50Hz
Precision made as used in record decks and tape recorders. Suitable mainly for other applications. 10/- each. P. & P. 3/-.

HYSTERESIS REVERSIBLE MOTOR

Incorporating two coils. Each coil when energied will produce opposite rotation of output shaft. 120V 60Hz. 1/10 r.p.m. 30/- each. P. & P. 5/-.

LOW TORQUE HYSTERESIS MOTOR MAZ3

Ideal for instrument chart drives. Extremely quiet, useful in areas where ambient noise levels are low. High starting torque enables relative high inertia loads to be driven up to 60z/in. Available in the following speeds and ranges: 240V 50Hz, 1 1/2 r.p.m., 1/2 r.p.m., 1/3 r.p.m., 1/4 r.p.m., 1/10 r.p.m., 1/12 r.p.m., 1/20 r.p.m., 1/40 r.p.m., 1/60 r.p.m., 1/360 r.p.m., 25/- each. P. & P. 5/-.



HYSTERESIS CLUTCH MOTOR

With integral clutch allowing the motor to drop out of engagement with the gear train, thereby facilitating easy re-actuating when used in timers or in conjunction with a light spring. 6 oz torque at 240V 50Hz, 1/12 r.p.m., 1/2 r.p.m., 1/3 r.p.m., 1/4 r.p.m., 1/10 r.p.m., 1/12 r.p.m., 1/15 r.p.m., 1/20 r.p.m., 1/30 r.p.m., 1/40 r.p.m., 1/60 r.p.m., 1/120 r.p.m., 1 r.p.m., 1 r.p.m., 24V 60Hz, 1/20 r.p.m., 4 r.p.m. 25/- each. P. & P. 5/-.

D.C. MOTORS

Similar to above type MD 83. 28V 1/20 r.p.m., 1/60 r.p.m., 1 r.p.m., 12V 1/20 r.p.m., 24V 1/15 r.p.m., 30V 1/12 r.p.m. 30/- P. & P. 5/-.

SYNCHRONOUS MOTORS

200/260V 50Hz. New condition, ex-equipment. 8.7 r.p.m. and 1 r.p.m. Self starting, complete with gearing, shaft 1/4 in dia., 1/4 in long. 30/- P. & P. 5/-.

ELECTRIC CLOCK MOTOR

NEW 200-260V, 50Hz, 2W. Synchronous induction motor. 2 revs. per hour. O/P shaft. 1/4 in dia. x 1/4 in long. Clockwise rotation. Three-holed mounting at 120° on 2in PCD. Price 15/- P. & P. 5/-.

WIDE RANGE OF PRECISION MULTI-TURN POTENTIOMETERS IN STOCK

MINIATURE UNISELECTORS

3 bank, 12 way, 250 ohm, 24V. Type 2200A. Supplied complete with plug-in base. Size 3in x 1in x 2in. A very neat precision component. Price £5.50. P. & P. 5/-.



UNISELECTORS

New 6 Bank 25 way 50V 75 Ohms Make before break. Half circle type. 2 sets of wider arms at 180°. PRICE £2/6. Miniature Uniselector 3 Banks 12 Way 12V 35 Ohms. PRICE £5.50. Packing and postage free.

PORTABLE WHEATSTONE BRIDGE

Specification. Type: Moving Coil Galvanometer. Ranges: 1. 0.05 to 5 ohms. 2. 0.5 to 50 ohms. 3. 5 to 500 ohms. 4. 50 to 5,000 ohms. 5. 500 to 50,000 ohms. Scales: Switched. Slidewire: 0.5 to 50. Galvanometer Scale: 10.0-10. Case: Moulded plastic. Internal Source: 4V Dry battery. Dimensions: 200 x 110 x 65mm. Weight: 0.9kg. List price £25. Our price £9.19.6.

AVOMETERS

These well-known portable test instruments have been overhauled and are offered complete with leads, crocodile clips and probes.



Model 98X	£33.00
Model 8	£28.00
Model 7	£17.00
Model 7 Mk. II	£15.00
Model 7X	£19.10.0
Model 48A	£16.00
Model 47A	£16.00
Model 40	£16.00

Model 48A complete with voltage multiplier for 480V and 3600V. Current shunts for 120A and 480A. A.C. Current transformer for 20A and 60A. In special wooden box. £15.10.0. P. & P. 15/-.

RESET TIMERS — ACRO TIMER BY HAYDON

Synchronous motor driven timer providing manual adjusted delay. Delay time is set on graduated dial. Press button closes contact and drives motor which drives an arm until it actuates the load switch. The cam then returns to initial position for repeat action. Various ranges available: 230V 50Hz Load contacts 15A 230V. £5.0.0.

POWER SUPPLIES. V.G. CONDITION ALL TESTED

Output Volts	Output Current	Input Volts	Stabil'd. or reg'd.	Make	Price
4-16	7A Max	240	Stabilised	Contant	£30
3-15V	6A Max	240	£25
26-37V	7A Max	240	£30
15V	5A	240	..	Advance	£20
Adjustable	1A	240	..	Farnell	£15
12V	100mA	240	..	Roband	£12-10-0
+200V	300mA	240	..	R.P.L.	£14-0-0
-20V	300mA	240
12V	4A	110	..	IBM	£18-0-0
12V	20A	110	£25-0-0
12V	12A	£12-10-0
6V	8A	£23-0-0
6V	16A	£18-0-0
20V	6A	£18-0-0
48V	6A	£18-10-0
6V	2A	240	Stabilised	Ex	£45
6V	10A	..	Adjustable	computer	£45
0-9V	..	240	£16-10-0
190-350	250mA	240	Stabilised	Airmec	705
6-3V-0-6-3V	AC	240	Unregulated	Advance	£18-10
24V	5A	240	..	DC22	£15
48V	2A	240	..	DC122	£18-10
48V	4A	240	..	Advance	DC8
350V or 250V	500mA	210	Stabilised	Solartron	£49-10
				755-2	
				6-3V CT at 5A	
				6-3V CT at 10A	

SOLARTRON 9R8152 TWIN Regulated DC Supply. High Stability 0.2% for 10% I/P change. LOW SOURCE IMPEDANCE. LOW RIPPLE 10mV. OUTPUT 0-500V Variable in 3 ranges 0-170, 160-340, 330-500V at 0-150mA. When units are used in series 0-1000V +ve or -ve or in parallel 0-500V at 300mA. AC O/P. 6-3V at 5amps. Our price £65 overhauled in VG condition.

COUNTERS

HIGH SPEED IMPULSE COUNTER

DAVIS WYNN ANDREWS 4 in dial with pointer registering up to 100 plus a 4 digit counter mounted in dial. Uses an inverse air escapement. Coil resistance 100 Ohms. 50V operation. £6.0.0. P. & P. 7/5.



BRAND NEW 4 Digit with electrical reset

High quality counter operating from 12V D.C. 1.20 mA at 10 impulses/sec W 1 1/2" H 2 1/2" L 4" PRICE £5.5.0. P. & P. FREE

4 DIGIT NON-RESETTABLE COUNTER

Totalising 10 impulses per second. Length 3 1/2 in 1 1/2 in. 24V d.c., 300 ohms. Price 5 for 25/-, P. & P. 5/-.



6 DIGIT ELECTRICAL IMPULSE COUNTER

New Type EM 101 24V Resettable £5.0.0 New P.O. Type 5 digit 330 Ohms £3.10.0 110V D.C. 4400 Ohms coil £2.10.6 Packing and postage free

VEEDER ROOT 6 DIGIT COUNTER

Suitable for counting all kinds of production runs, business machine operation. Mechanically driven. Reset type KA 1337, manual knob. Ex-equipment, but new condition. Special price 25/- plus 5/- P. & P.

3 DIGIT RESETTABLE COUNTER

Totalising 48V d.c. at 48mA; 10 impulses/sec. Length 4in x 1 1/2 in. Price £3.15.0. P. & P. 5/-.

6 DIGIT RESETTABLE COUNTER

Totalising 240V 50Hz. Viewing window 2in x 1in. Ex-equipment. Price 55/-, P. & P. 5/-.

6 DIGIT TOTALISING NON-RESETTABLE COUNTER

Mechanical operation. Chromium finish. Length 1 1/2 in x 2 1/2 in with viewing window 1 1/2 in x 1 1/2 in. Ex-equipment. Price 9/6. P. & P. 2/6.

BERKELEY DECIMAL COUNTING UNIT 0-9

Direct reading octal base plug in unit electronic counter. The number counts received is indicated by one of ten neon lamps behind acetate panel. The unit counts from 0-9 the tenth pulse resetting to zero and simultaneously generating an o/p signal. Circuits can be connected in cascade. Power supply 6-3V d.c. Cut on/Cut off 15V Price 70/- p. & p. free.



MINIATURE DIGITAL DISPLAY

Operates on a rear projection 6.3V pilot lamp. Character size 1" high, 0-9 digits with degree symbol, i.e. (45). Dimensions 1" wide, 3 1/2" deep, 1 1/2" high. List price 6 gns. P. & P. 5/-.



1" characters 55/-
4" characters 48.10.0

EAC DIGIVISOR Mk. II DIGITAL READ-OUT DISPLAY

Uses a sensitive moving coil movement to project digits 0-9 on to a viewing screen via an optical lens system. Image height 1" Lamp 6.3V. Sensitivity 250 micro-amp. Dimensions L 4 1/2" W 2 1/2" H 1 1/2" Price £3.10.0. P. & P. 5/-.



SOLENOIDS

High quality solidly constructed solenoids. Actuated by 42V 45 coil. Overall length 3" x 1" square with a 1/4" travel of the 1" dia. shaft. 8/6. P. & P. 3/6.
24V. 70 ohm. Armature 1" movement. Lug type fitting. L 1 1/2" x 1 1/2" x 1 1/2". Price 4/6. P. & P. 2/6.

LAMPS

260V, 15W, MBC. Panel lamps. Ideal making up displays, etc. Length 2 1/2 in x 1 1/2 in dia. Special offer, 10 for £1. P. & P. 5/-.

SLIDER SWITCHES

250V 1A D.P.S.T. Flush mounting Size L 1 1/2" W 3/4" 15 for £1.5.0. p. & p. free.

MINIATURE MOVING COIL RELAY S115

By Sangano Weston, suitable for D.C. circuit. A high sensitivity relay more sensitive than the electromagnetic type. Single Coil Resistance 310 micro amps. 315 Ohm. List price £4.10. Our price 20/-, P. & P. 3/-.




NUMICATORS

Fig. size 16mm. Cold cathode gas filled in line 0-9 digital display tubes. Long life expectancy. Minimum striking voltage 180V. Size reading Type XX 7, XX 23 and XX 3 amber. Price 10/6 each. P. & P. 2/6.

MEMORY CORE STORES

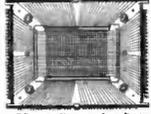42 x 32 2K bit ferrite core store complete with 84 OA 10 load diodes. Ideal for building computer store or holding information in binary form. Price 55/-, P. & P. 7/6. Handbook available on how to use core stores. 7/6.



MEMORY PLANES

Ferrite core memory planes with wired ferrite cores. Useful for building your own computer or as an interesting exhibit in the demonstration of a computer. Mounted on plastic material, frame 5 8 in. Consisting of matrices 40 x 25 x 4 cores each one individually addressable and divided into 2 halves with independent sense and inhibit wires. £8/10.0. P. & P. 3/-.


LINEAR THYRISTOR CONTROLLED LIGHT DIMMER—BRAND NEW

High grade full wave bridge circuit gives linear control of light brightness. Ideal for controlling room lighting and a.c. d.c. commutator motors fitted to portable electric hand drills. Fits standard 2in conduit box. 240V, 50Hz, 600W. Price 59/6. P. & P. 2/6.



RAPID HEAT SOURCE . . .

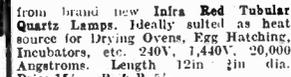from brand new Infra Red Tubular Quartz Lamps. Ideally suited as heat source for Drying Ovens, Egg Hatching, Incubators, etc. 240V, 1440V, 20,000 Angstroms. Length 12in 1/2 in dia. Price 15/-, P. & P. 5/-.



STOCK CLEARANCE


All items are offered in "As is condition"
Oscilloscope Solartron D.300 .. £10.00
.. Furzehill 0/100 .. £9.10.0
.. Furzehill 0/110 .. £11.0.0
.. Airmec 249 .. £10.0.0
.. Airmec 723 .. £10.0.0
L.C.R. Bridge Wayn Kerr B121 .. £12.10.0
L.C.R. Bridge B.P.L. VB202 .. £12.10.0
Crystal Calibrator Marconi TF 723A .. £15.0.0
Multimeter AC/DC Sangano Weston E723 .. £8.10.0
Safety Ohmmeter Evershed and Vignoles .. £5.0.0
Bridge Oscillator Airmec 703 .. £5.0.0
L.F. Oscillator Daves G 420 .. £7.10.0
P. & P. 5/- on single item.

ELECTRONIC BROKERS LTD.

(Dept. PE), 49-53 PANCRAS RD · LONDON NW1
01-837 7781 TELEX 267307

Open Mon.—Fri. 9—6 p.m.

DISCOSOUND

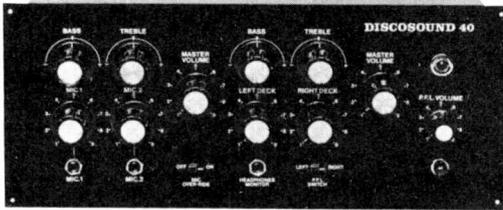

DISCOSOUND 40 PRE-AMP

The Discosound 40 offers the same specification as the D.J. Disco Amp without the power output stage. Size 16in x 7in x 7in. Self powered and ideal for use with the Discosound 100 Power Amplifier below and one of the outstanding features is that it is capable of running ten of these Power Amplifiers (Total 1,000W).

PRICE £40.10.0 inc. P. & P.


DISCOSOUND 100 POWER AMPLIFIER



A 100W RMS (8 Ohms) High Fidelity power Amplifier which utilises all silicon transistors of modular construction and features full automatic overload protection against short or open circuits. Frequency response: 20-20,000Hz \pm 2dB. The High output is ideally suited for discotheques, groups, clubs, etc., or anywhere where reliability and quality are required. This unit is the companion model for use with our control pre-amp Discosound 40, or can be used with any other high quality pre-amp control unit. Completely built and tested on steel Chassis.

PRICE £49.10.0 inc. P. & P.

DJ70S INTEGRATED MIXER-AMPLIFIER

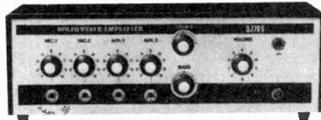

One of the finest units available on the market today, regardless of price. The front end of the unit consists of a four channel mixer with separate inputs and volume controls, plus a separate bass, treble and master volume control. One of the main features of this remarkable amplifier is its elaborate protection against short and open circuit and we can guarantee that it is virtually indestructible. Allied to this is its very high power output (70W R.M.S.) a frequency response (30-20,000Hz \pm 3dB) that is superb, and distortion that is well below 1% even at full output. The unit is suitable for use with discotheques, groups, P.A., clubs, etc., or anywhere that high quality high output is required. Size: 15½in x 5in x 6in.

PRICE £63.0.0 inc. P. & P.

Also available DJ105S 30W P.A. Amplifier. Similar specification to above.

PRICE £41.0.0 inc. P. & P.

For full details of these and all Discosound Products write direct to:

DISCOSOUND

122 BALLS POND ROAD, LONDON, N.1. Tel. 01-254 5779

Full money back guarantee if returned within 10 days

All Discosound Products are guaranteed for 12 months

Demonstrations given at any time

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
 - C. & G. Electronic Servicing
 - R.T.E.B. Radio/T.V. Servicing Certificate
 - Radio Amateurs' Examination
 - Radio Operators' Certs.
 - General Certificate of Education, etc.
- Now available, Colour T.V. Servicing

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics



INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 151, Intertext House, Stewarts Rd., London, S.W.8

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam).....

NAME AGE

(Block Capitals Please)

ADDRESS

1/71

INTERNATIONAL CORRESPONDENCE SCHOOLS

Each package has four A inputs, four B inputs, four "sum" outputs and a "carry-in" to the first adder and "carry-out" of the last.

These circuits are mainly intended for high-speed multiple bit parallel addition in computer arithmetic units, but binary adders are versatile devices, capable of performing several logic operations. The availability of four such devices in one package opens all manner of possibilities to the logic designer.

To understand exactly how these circuits can be used as comparators, consider Fig. 8. Fig. 8a shows the truth table of an "exclusive-OR" gate, which is some-

should be equal to the switch outputs before the completed comparator registers an equality. To achieve this, the eight sum outputs from the adders (each of which registers equality of one digit) are fed to an SN7430 8-input NAND gate G4 in IC17, the output of which will only fall to a logic 0 when all the individual comparisons are valid.

The output of this gate will remain low for ten minutes, until a further increment in the "tens-of-minutes" count invalidates the comparison. A period of this length would probably be sufficient for alerting the sleeper, but to make absolutely sure that the alarm

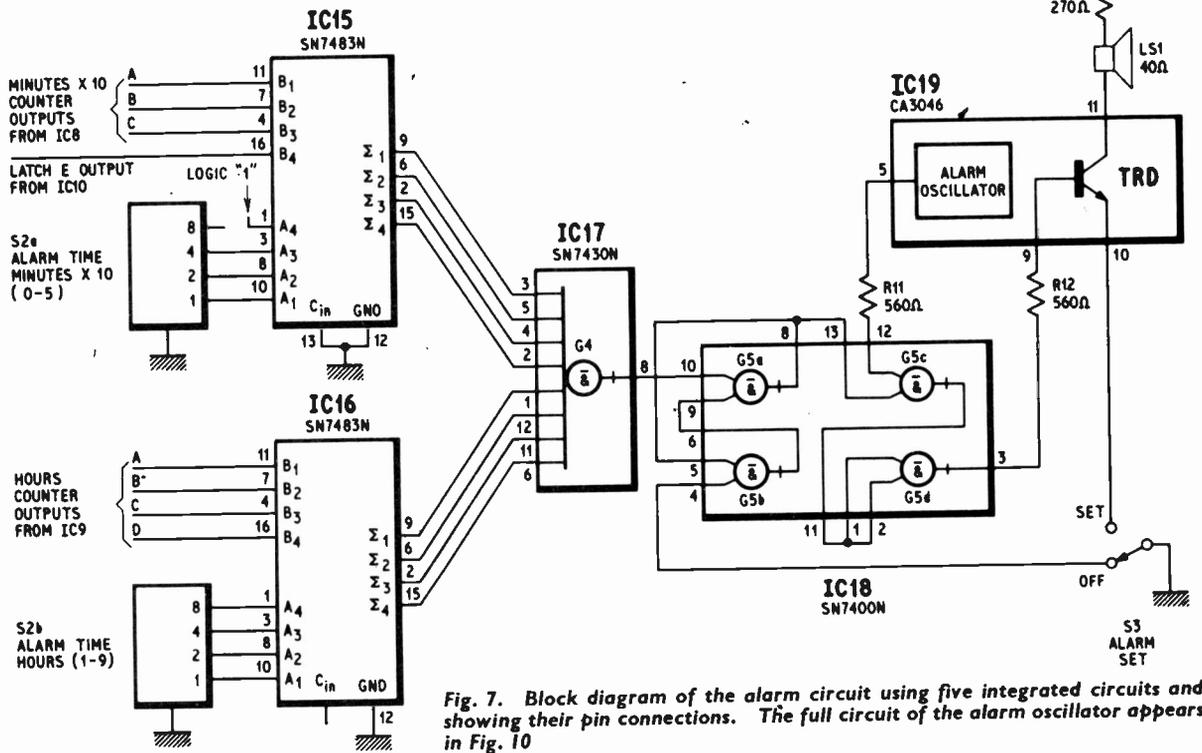


Fig. 7. Block diagram of the alarm circuit using five integrated circuits and showing their pin connections. The full circuit of the alarm oscillator appears in Fig. 10

times called a "non-equivalence" gate because its output is a logic 1 only when its inputs are exactly opposite.

To use such a gate as an equivalence circuit which gives a logic 1 output when its inputs are identical, it is only necessary to invert one of those inputs by means of an inverter gate, or if complementary inputs are available anyway, to compare the true form of one input with the negated form of the other. It follows then that this type of gate could be used to build the complete alarm comparator we require.

As Fig. 8b shows, the truth table of a full-adder is identical to that of the "exclusive-OR" gate, if we ignore the carry output and keep the carry input at 0. In fact, using the SN7483 as four "exclusive-OR" gates suits our comparator design admirably. The inverted form of one of the words to be compared is already available, because the thumbwheel switches give outputs in this form. The fact that we do have a carry input available can be put to good use in correcting the lagging output of the hours counter.

EIGHT DIGIT EQUALITY

So far this article has only considered the comparison of single digits, but all eight digits from the counters

cannot be ignored, the output of IC17 sets a latch formed from two cross-coupled 2-input NAND gates G5a and G5b in IC18, which ensures that the alarm tone will continue until reset, even if this process takes longer than ten minutes.

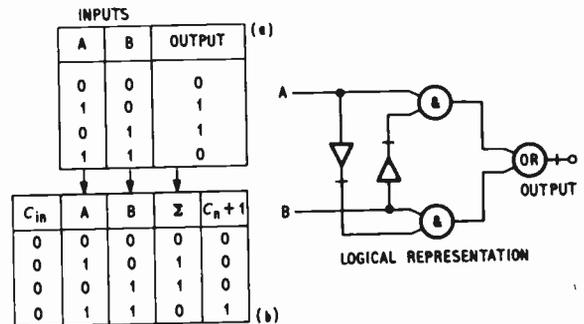


Fig. 8a. Truth table for "exclusive-OR" function

Fig. 8b. Truth table for full adder when $C_{in} = 0$

ALARM TIME SWITCHES

The switches used to set the alarm time were chosen from the Birch-Stolec "standard" range, and both banks are coded S.B.10.N1248. These switches are well suited to this application because they give an output on four lines which conforms to the binary code, a separate pattern being produced for each of the ten positions of the numbered wheel.

Any number of switch banks can be mounted together if the constructor wishes to expand the alarm system, the final assembly being finished off by means of a pair of end cheeks which give a neat appearance and provide the mounting holes.

The principle on which these switches are based is that of a four-track printed, gold plated stator, traversed by four phosphor bronze rotor contacts. The life of this assembly is at least 100,000 operational cycles when switching 24 watts, so in this application the life will be much extended due to the very small current being carried.

To fabricate a similar system using wafer switches, a four pole ten-way switch would be required in each position, with a considerable amount of wiring necessary to programme the required code.

The wafer switch system does provide a useful way of explaining the action however, and a diagram with output logic table conforming to the thumbwheel switch coding is given in Fig. 9. Note that the output is in the complement form (assuming positive logic). A logic 0 is represented by a ground connection, and a logic 1 by an open circuit.

DIGITAL COMPARISON

As discussed earlier, this inverted code is just what is required for connection to the comparator. Of course, numbers one to nine only are required as inputs to the hours comparator, and numbers zero to five for the tens-of-minutes circuit. Stops could be fitted to the switches if desired, although this is not really necessary; blanking the undesired numbers with paint would be a simple alternative.

Only six positions are required for the tens-of-minutes switch. It follows, therefore, that the full output of four digits is not needed. In fact, the "8" output from this switch can be ignored in the comparison, leaving a spare comparator section in IC15, which is put to good use as an "inhibit" while the "tens-of-hours latch" E output is high. Remember that the alarm system is not operative during this three-hour period as it stands.

This inhibiting logic is simply achieved by comparing the E line with a permanent "1", thus only permitting a 1 output from this section when the E line is at 0.

As an alternative, it would be possible to ignore this spare comparator section, and feed the \bar{E} output from IC10 (Fig. 2) to the 8-input gate in IC17 which, when using this method, would have an input available. This system was not used in the prototype simply to retain the design simplification of feeding only true outputs from the main clock board.

HOURS COUNT CORRECTION

So far so good, but up to now we have ignored the point made last month that the hours counter outputs do not conform directly to the binary code, 0000 representing decimal 1 instead of 0, and so on up to 1000 representing 9 instead of 8.

The thumbwheel switches, being "off-the-shelf" items, do not allow for this idiosyncrasy. The comparison as previously described would reveal that, when

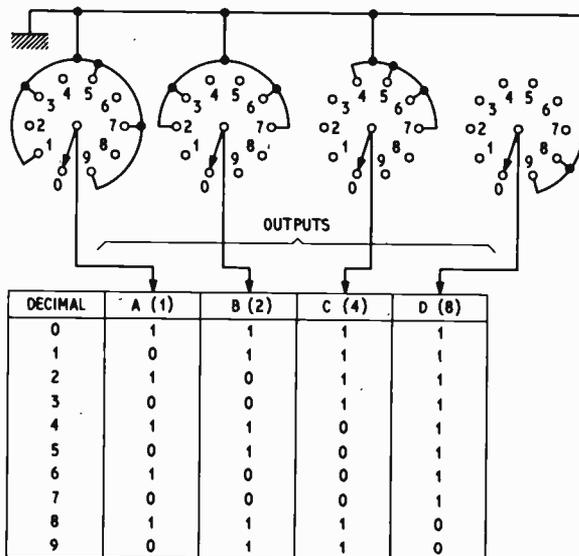


Fig. 9. Wiring of a 4-pole 10-way switch to give a four-bit binary coded decimal output in complement form. The truth table shows positive logic

the switch was set to, say, four o'clock, the alarm would sound at five o'clock, and so on, a most unhappy state of affairs.

It is evident, however, that the code output from the hours counter could be corrected by simply adding binary 0001 to it, increasing its binary value by one. This simple conversion could be carried out using a four-bit parallel adder such as the SN7483N. (A four-bit adder is necessary because carries must be allowed for over all four bits.)

A separate SN7483N could be employed to carry out this correction, but as these circuits are used as comparators anyway, this is not necessary. A 1 can be added in by feeding a carry in on the "carry" input to the least significant adder. Admittedly this is all a little difficult to grasp, but it does work, and the best way of proving it is to set an example down as a sum, thus:

$$\begin{array}{r}
 \text{Hours display: 7, Switch setting: 7.} \\
 \text{Binary 7: 0111} \\
 \text{Therefore switch output (inverted): 1000} \\
 \text{Hours counter output: 0110} \quad \text{add} \\
 \hline
 = 1110 \\
 \text{1 (plus 1 carry)} \\
 \hline
 = 1111 \text{ equal (alarm sounds)}
 \end{array}$$

RISK OF TRANSIENT OPERATION

During the "paper" design of this part of the clock it occurred to the author that, due to the relatively lengthy propagation delay of the SN7483N, and the non-synchronous inputs from the MSI ripple counters, it might be possible for all the adder outputs to be at 1 when the comparison should not show equal, thus giving a transient output from IC17.

As any such transient "low" output longer than a few nanoseconds is likely to set the latch and sound the alarm (at the wrong time), this state of affairs must obviously be avoided. A good deal of thought was


TRANSISTOR RADIOS TO BUILD YOURSELF

Backed by after sales service

NEW! roamer eight mk 1 WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, S.W.1, S.W.2, S.W.3, and Trawler Band. Built-in ferrite rod aerial for Medium and Long Waves. 4 section 24in. retractable chrome plated telescopic aerial for Short Waves for maximum performance. Push-pull output using 600Mw type transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. 8 transistors plus 3 diodes. Famous make 7 x 4in speaker. Air spaced gauged tuning condenser. On/off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build. Parts price list and easy build plans 5/- (FREE with parts).

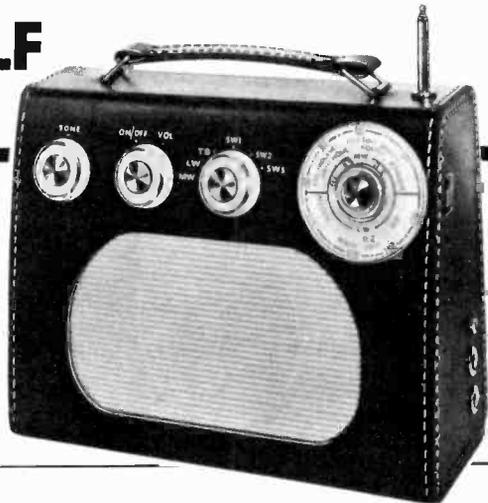Total building costs **£6.19.6** P. & P. 7/6 Overseas P. & P. 17/-



roamer seven mk IV

7 FULLY TUNABLE WAVEBANDS—M.W.1, M.W.2, L.W., S.W.1, S.W.2, S.W.3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built-in ferrite rod aerial for Medium and Long Waves. Retractable 4 section 24in chrome plated telescopic aerial for peak Short Wave listening. Socket for Car Aerial. Powerful push-pull output. 7 transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in P.M. speaker. Air spaced gauged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 3/- (FREE with parts).

Total building costs **£5.19.6** P. & P. 7/6 Personal Earpiece with switched socket for private listening, 5/- extra. Overseas P. & P. 17/-




NEW!

transeight SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case in black with red grille and black knobs and dial with spun brass inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Tunable on Medium and Long Waves, 3 Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 8 improved type transistors plus 3 diodes. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 5/- (FREE with parts).

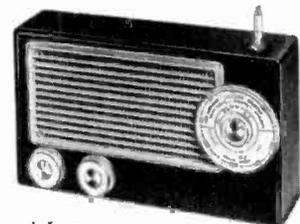Total building costs **89/6** P. & P. 5/6 Earpiece with switched socket for private listening 5/- extra. Overseas P. & P. 13/-



pocket five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER

Attractive black and gold case. Size 5 1/2 x 1 1/2 x 3 1/2 in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs **44/6** P. & P. 3/6 Overseas P. & P. 10/-

transona five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER

Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2 in. 7 stages—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Easy build plans and parts price list 1/6 (FREE with parts).




Total building costs **47/6** P. & P. 3/9 Overseas P. & P. 10/-

IMPROVED MODEL! roamer six

SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive black case with red grille and black knobs and dial with spun brass inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Tunable on Medium and Long Waves, two Short Waves, Trawler Band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and latest telescopic aerial for Short Waves. Improved circuit. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. Easy build plans and parts price list 2/- (FREE with parts).

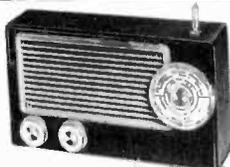

Total building costs **79/6** P. & P. 4/6 Overseas P. & P. 13/-

RADIO EXCHANGE LTD

61a, HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER EIGHT	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
TRANSEIGHT	<input type="checkbox"/>	POCKET FIVE	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>

Parts price list and plans for.....

Name.....

Address.....

* Callers side entrance Stylo Shoe Shop
* Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

PE 25

BI-PRE-PAK LIMITED

FULLY TESTED AND MARKED

AC107	3/-	OC170	4/6
AC126	2/6	OC171	4/6
AC127	3/6	OC200	5/-
AC128	2/6	OC201	5/-
AC176	5/-	2G301	2/6
ACV17	3/-	2G303	2/6
AF239	7/6	2N711	10/-
AF186	10/-	2N1302-3	4/-
AF139	7/6	2N1304-5	5/-
BC154	5/-	2N1306-7	6/-
BC171 = BC107	2/6	2N1308-9	7/-
BC172 = BC108	2/6	2N3819FET	9/-
BF194	3/-		
BF274	3/-	Power Transistors	
BFY50	4/-	OC20	10/-
BSY25	7/6	OC23	6/-
BSY26	2/6	OC25	5/-
BSY27	2/6	OC26	5/-
BSY28	2/6	OC28	6/-
BSY29	2/6	OC35	5/-
BSY95A	3/-	OC36	7/6
OC41	2/6	AD149	6/-
OC44	2/6	AUY10	25/-
OC45	2/6	2S034	5/-
OC71	2/6	2N3055	12/6
OC72	2/6	Diodes	
OC73	3/6	AA Y42	2/-
OC81	2/6	OA95	2/-
OC81D	2/6	OA79	1/9
OC83	4/-	OAB1	1/9
OC139	2/6	IN914	1/6
OC140	3/6		

FREE!
PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 10/- WITH ORDERS OVER £4

OUR VERY POPULAR 6d. TRANSISTORS

FULLY TESTED & GUARANTEED

- TYPE "A" PNP Silicon alloy, metal TO-5 can. 25300 type, direct replacement for the OC200/203 range.
- TYPE "B" PNP Silicon, plastic encapsulation, low voltage but good gain, these are of the 2N3702/3 and 2N4059/62 range.
- TYPE "D" NPN Silicon planar, plastic TO-18 case. Audio preamplifier or 500 mW output stage, of the BC113/4/5 range.
- TYPE "E" PNP Germanium AF or RF - please state on order. Fully marked and tested.

CLEARANCE LINES

DON'T MISS THIS LAST CHANCE

ONLY A FEW LEFT

UHF/VHF T.V. TUNER UNITS

TU.2 CONTAINING 2 AF186's & 2 AF178's

PRICE 10/-

TU.3 CONTAINING 2 AF186's & 2 AF178's

PLUS WAVEBAND SLIDER SWITCH

PRICE 12/6 P. & P. 2/6 EACH UNIT

All the units have many other components, e.g. Capacitors, Resistors, Coils and tuning condensers, etc. Although these are manufacturers rejects they are not beyond repair as has been proven by many of our customers.

ALL TUNER UNITS ARE SUPPLIED WITH CONNECTION DATA

COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25 kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

ONLY £1 each post and packing 4/6

SPECIAL LINE

1 AMP Bridge rectifiers, 1" Square 100 PIV. = 5/- 400 PIV. = 6/6 800 PIV. = 8/-

1970 MULLARD DATA BOOKS

Data and equivalents on semiconductors, valves and tubes PRICE 4/- P. & P. 6d.

I.C. PANELS - FEW ONLY - 50/- EACH

Each panel contains: 16-Dual 2 I/P NOR gates MC714G. 1-Dual 3 I/P NOR gate MC715G. 1-J.K. flip flop MC723G. 29-BSY95A or 2595A and 1 V405A transistors.

NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0.3 to 0.5V, 0.5 to 2mA.	10/-
B77	2	AD161-AD162 NPN/PNP Trans. Comp. Output. Pair	10/-
B81	10	Reed Switches, mixed types large and small	10/-
B89	2	5SP5 Light Sensitive Cells. Light Res. 400Ω Dark 1MΩ	10/-
B91	8	NKT163/164 PNP Germ. TO-5 equivalent to OC44, OC45	10/-
B92	4	NPN. Sil. Trans. AO6 = BSX20, 2N2369 500 MHz, 360mW	10/-
B93	5	GET113 Trans. equiv. to ACY17-21 PNP Germ.	10/-
B99	200	Mixed Capacitors. Postage 2/6. Approx. quantity, counted by weight	10/-
B98	10	XB112 and XB102 equiv. to AC126, AC156, OC81/2, OC71/2, NKT271, etc.	10/-
H4	250	Mixed Resistors. Postage 2/- Approx. quantity, counted by weight	10/-
H7	40	Wirewound Resistors. Mixed types and values. Postage 1/6	10/-
H8	4	BY127 Sil. Recs 1000 PIV. 1 amp. plastic	10/-
H9	2	OCPT1 Light Sensitive Photo Transistor	10/-

RETURN OF THE UNBEATABLE P.I PAK.

NOW GREATER VALUE THAN EVER

FULL OF SHORT LEAD SEMICONDUCTORS AND ELECTRONIC COMPONENTS, APPROX. 170. WE GUARANTEE AT LEAST 30 REALLY HIGH QUALITY FACTORY MARKED TRANSISTORS PNP AND NPN, AND A HOST OF DIODES AND RECTIFIERS MOUNTED ON PRINTED CIRCUIT PANELS. IDENTIFICATION CHART SUPPLIED TO GIVE SOME INFORMATION ON THE TRANSISTORS.

PLEASE ASK FOR PAK P.I ONLY 10/- 2/- P. & P. on this Pak.

Make a Rev. Counter for your Car. The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car. **20/- each**

FREE CATALOGUE AND LISTS for -

ZENER DIODES
TRANSISTORS, RECTIFIERS
FULL PRE-PAK LISTS
& SUBSTITUTION CHART

MINIMUM ORDER 10/- CASH WITH ORDER PLEASE. Add 1/- post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

P.O. RELAYS **8 FOR 20/-**
Various Contacts and Coil Resistances. No individual selection. Post & Packing 5/-

SPECIAL OFFER
GERMANIUM BRIDGE RECTIFIERS
GEX 541 FINNED

SINGLE PHASE 12 Amp. 48 Volts
THREE PHASE 18 Amp. 74 Volts

Ideal for Battery Chargers on Power Units

Offered at fraction of makers' cost Only **12/6** Each

Post & Packing 2/6

NEW UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	10/-
B83	200	Trans. manufacturer's rejects all types NPN, PNP, Sil. and Germ.	10/-
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	10/-
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	10/-
B88	50	Sil. Trans. NPN, PNP, equiv. to OC200/1, 2N706A, BSY95A, etc.	10/-
B60	10	7 Watt Zener Diodes Mixed Voltages	10/-
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	10/-
H10	25	Mixed volts, 1½ watt Zeners. Top hat type	10/-
H11	30	MAT Series "alloy" pnp Transistors	10/-
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	10/-
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied.	10/-
H20	20	BY126/7 Type Silicon Rectifiers, 1 amp plastic. Mixed volts	10/-

FREE! A WRITTEN GUARANTEE WITH ALL OUR TESTED SEMICONDUCTORS

BI-PRE-PAK LTD DEPT. A, 222-224 WEST ROAD, WESTCLIFF-DN-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

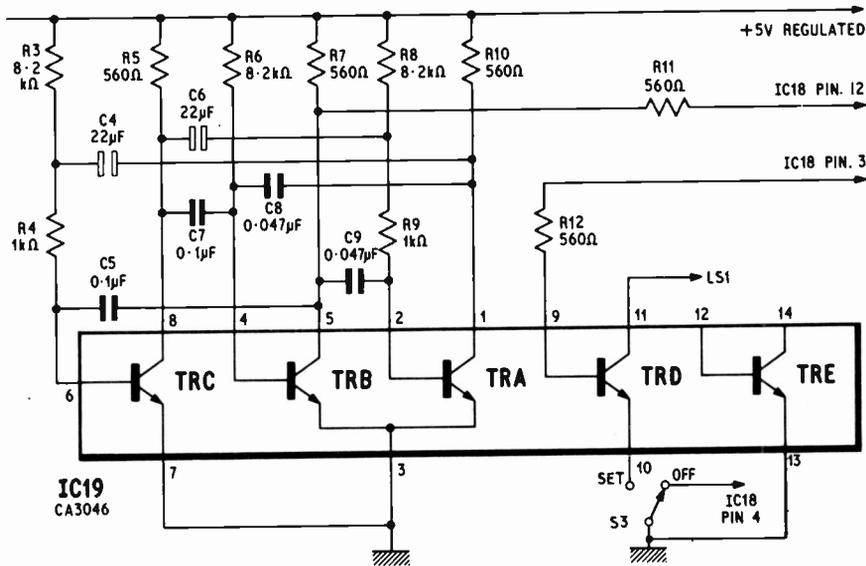


Fig. 10. Alarm oscillator circuit using an integrated package of five transistors. TRE is unused

put in to discover whether this could in fact occur. It was decided that the only way to find out was to "try it and see"!

In the event, it was found impossible to generate this condition in the completed clock, and so all was well, but the point has been made because, with the wrong combination of adders and counters, it was thought to be a possible occurrence.

If any reader should be unlucky enough to experience this phenomenon, the solution is simply to gate the comparison with a clock waveform from one of the divider stages not used in the comparison. In this way the output from IC17 could be strobed only after the hours and tens-of-minutes counters have changed and the SN7483N "carries" have propagated. Obviously some circuit modifications would be necessary to achieve this.

ALARM OSCILLATOR

The alarm oscillator circuit is shown in Fig. 10, which may attract the interest of those who are not otherwise concerned with the clock, because, of its obvious applications in many other designs.

The circuit was described by A. B. Blackwell-Jones in a letter to *Wireless World* (August 1967). He called it a "Trivibrator" or "Donkey Simulator", a very apt pair of names indeed. The circuit is based on the usual two transistor astable multivibrator arrangement, to which an extra transistor has been added, so that three separate cross-coupled timing networks result instead of the usual one, as shown in Fig. 11.

Each of the timing networks has a different natural frequency, two being audio tones of about one and two kilohertz respectively, and the other being a low frequency timing circuit giving a 5Hz gating effect. The output is taken from the centre transistor of the two a.f. arms, and consists of alternate bursts of the two tones, each lasting for about 0.2 second, controlled by the l.f. arm. When fed to the speaker this tone gives a very pleasing "space age" warble effect.

If the reader is familiar with the basic multivibrator circuit action, there should be no problem at all in

understanding this extension of the idea. It will help to refer to Fig. 11.

CIRCUIT OPERATION

Either transistor TRA or TRC will be saturated at any time. This saturation will last for about 0.1 second, as controlled by the 5Hz timing network coupling them. The saturated transistor is unable to react via its a.f. timing network with TRB during this time, so this tone is not produced. Meanwhile, however, the other transistor (of the pair TRA or TRC) is not saturated by the l.f. arm and is free to interact via its a.f. timing network with TRB, giving an a.f. output of the appropriate frequency. When the 0.1 second period has expired the l.f. arm changes over, saturating the other (TRA or TRC) transistor, and allowing the other a.f. tone to be produced, and so on.

The only unfamiliar parts of the circuitry are the two resistors, R4 and R9, which are necessary in the trivibrator to prevent the very low impedance of the l.f. coupling capacitors shunting the a.f. arms. In effect, the capacitors C4 and C6 coupling this section are taken to taps on the CR timing resistance chain.

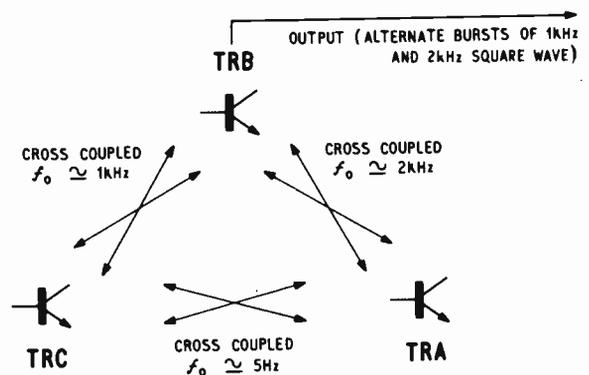


Fig. 11. Principle of operation of the alarm oscillator

The output of the oscillator is taken from TRB via a resistor R11 to gate G5c (Fig. 7), where it is held until allowed through by a logic 1 input from the alarm latch G5a. Note that the alarm oscillator runs continuously, whether the latch is set or not.

When G5c is not enabled, its output will be at a permanent 1, or positive, level. If this output is fed to the simple saturating switch used to drive the speaker directly, although the alarm would not sound, this transistor would be hard on, giving a high power drain and possibly damaging the speaker. To avoid this, G5d is interposed between G5c and the switch TRD to act as an inverter, ensuring that when the alarm circuit is inactive, the output transistor will be off, and no current will flow through the speaker.

The three transistors forming the oscillator, and the transistor used to drive the speaker, are all contained in an integrated package IC19. The other transistor in this array is not used, but it is vital that its emitter (pin 13) should be grounded, as it is connected to the substrate of the device. An open circuit on this pin would jeopardise the isolation between the separate transistors.

The positive supply for the a.f. output stage is taken from the unregulated 10V line, not to gain any power advantage, but to isolate the 5V line powering the logic circuitry from any ripple produced.

The emitter of the output stage is grounded through the combined "alarm-off/reset" switch S3. When this switch is in the "off" position the alarm cannot sound under any conditions, and a 0 is fed to G5b to reset the latch ready for the next alarm setting.

Note that during the ten-minute period that the alarm output from IC17 is active, it is not possible to reset the latch by simply flicking the switch up and down.

This concludes the description of the alarm circuitry; the 5V regulator, which is wired up on the same board, follows next. It is recommended that the 5V regulator be wired up before the alarm circuit as will be realised later in this article.

FIVE VOLT REGULATOR

The 5V regulator uses a total of seven transistors, five being contained in another CA3046 (IC20), one being a discrete 2N706, and the last being a plastic encapsulated power transistor, type MJE521, which is mounted off the board using the chassis as a heat sink.

The regulator features fold-back current limiting, excellent temperature stability, and an output impedance of less than 0.1ohm from d.c. to 100kHz together with line regulation of better than 10mV per volt.

Inputs to the circuit are 10V d.c. (nominal) and 200V d.c. (nominal), provided by conventional power supplies which are described next month. The regulator circuit is shown in Fig. 12.

The 200V line is reduced to provide a 12V biasing supply set by a discrete Zener diode D3, which is bypassed by C1 to suppress any high voltage transient surge when switching on. The 12V is used to power the temperature compensated 7.5V reference supply and the differential amplifier. Using a separate bias supply rather than the unregulated 10V to power these sections gives a great improvement in line and load regulation, and increases ripple rejection.

In the alarm oscillator circuit the advantages conferred by employing a transistor array were those of compactness and convenience, but in this circuit the benefits of the monolithic construction provide a specification which could not be equalled simply by replacing the array with discrete devices. Because

each transistor is mounted in close thermal contact with its neighbours, tight temperature tracking is assured, enabling the construction of an accurately compensated reference and a differential amplifier with a negligible input offset voltage temperature coefficient.

As each transistor was made at the same time and experienced the same diffusion process, parameter matching is also assured. The transistors' V_{be} are guaranteed to be within 5mV of each other; all these factors can be put to good use in this type of circuit.

REFERENCE SUPPLY

The reference supply is provided by TRD and TRE, which are not used as transistors in this application, but as a Zener diode and forward diode respectively. The use of a base emitter junction as a Zener is not new, and the transistors in the CA3046 provide a breakdown voltage of about seven volts when used in this way, with a temperature coefficient of plus 2mV/degree C.

A temperature induced variation of this order is not serious in itself, but if it occurs at the same time as other variations, it could take the 5V supply outside the necessary design limits of plus or minus 250mV.

To eliminate this drift, a forward biased diode, formed from another base emitter junction (TRE), is connected in series with TRD. A junction biased in this way exhibits a forward voltage of around 600mV, but it has a negative temperature coefficient of 2mV/degree C, which cancels the plus 2mV/degree C of the TRD "Zener" junction.

A variable potential divider is used to tap off an accurate 5V from the reference line, and is used as an input to the non-inverting input of the differential amplifier (TRA and TRB). A capacitor C11 is used to bypass any noise which may be present on this supply.

Because a 5V reference is used, the differential amplifier can be used in the voltage-follower mode, with the final 5V output being fed back directly to the inverting input without the usual potential divider chain being interposed. This connection gives a maximum value of loop gain for good regulation, and also increases the frequency response of the amplifier, giving good transient response.

DIFFERENTIAL AMPLIFIER

A differential amplifier was used because of its high voltage gain and absence of temperature problems which affect single-ended designs.

The output of the "error" amplifier is taken from the collector of TRA and used to drive the base of TR1 which, with the series pass power transistor TR2, forms a compound emitter follower with a very high current gain, and consequently low output impedance. TR2 has to pass all the current required by the load, which could be as high as 1A, and is therefore a power device bolted to a heat-sink.

FOLDBACK CURRENT LIMITING

The foldback current limiting circuit is provided by TRC with R21, R22, and R23. The following paragraphs describe its operation using Fig. 12.

As many constructors are aware, a short-circuit on the output of a semiconductor regulator can wreak havoc with the regulator devices in a matter of microseconds, and with a project of this complexity a short-circuit is very likely to occur, especially in the early stages of testing. Protection against this sort of disaster

Metrosound Audio Products



ST.20 Stereo Amplifier

Good looks apart the ST.20 offers outstanding performance equal to amplifiers selling at two or three times the price which makes it one of the best buys on the High Fidelity market. All silicon solid state circuitry using 20 transistors and 2 diodes provides a full 20 watts r.m.s. output (10 watts r.m.s. per channel). Conservatively rated components are used throughout to ensure long term reliability and stability. Press button selector switches are a feature of the ST.20 for magnetic phono, crystal phono, radio tuner, tape, mono/stereo and on/off facilities. The slimline cabinet in teak veneers and the front panel fascia of

brushed anodised aluminium finish with gleaming silver trims combine to give a look of expensive and stylish elegance. Size 15½" x 3½" x 10". Price £36.0.0.

"Its performance is not just on the fringe of the specification - as happens with many low-priced amplifiers - it is well within it and well within the requirements for hi-fi"

F. C. Judd "Hi-Fi Sound" August 1970




ACCEPTED BY THE COUNCIL OF INDUSTRIAL DESIGN FOR INCLUSION IN DESIGN INDEX



Stereo 10-10 Compact System

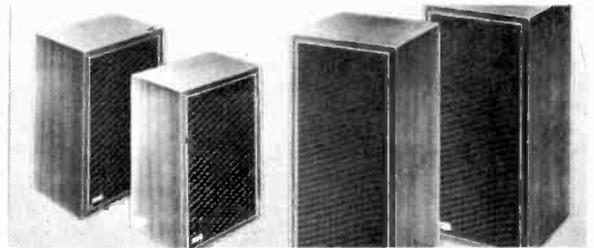Expertly designed and providing outstanding quality reproduction. Not just another compact system but a true "sound centre" incorporating an all silicon transistor amplifier, Garrard 3000 autochanger and two Metrosound HFS.10 speaker systems. Output 20 watts rms. (10 watts rms. per channel) Bass, Treble, Volume and Balance controls. Input for tuner. Tape record outlet. Price £77.6.4.



Metrosound Speaker Systems

MODEL HFS.10 10 watts handling capacity. 8 ohm impedance. Teak finish. Size 14" x 9" x 7". As used in the Stereo 10-10 Compact System and available in matched pairs at £26.3.8.

MODEL HFS.20 20 watts handling capacity. 8 ohm impedance. Teak finish. Size 23" x 11½" x 10½". Price £18.10.0. each.

Please send full details of

ST.20 Amplifier 10-10 Compact Speakers

NAME.....

ADDRESS.....

Available from all leading high fidelity dealers
Designed and Manufactured in England by

metrosound

Metrosound Manufacturing Co. Ltd., Audio Works,
Cartersfield Road, Waltham Abbey, Essex.
Telephone: Waltham Cross 31933



who wants a **£2,000+p.a.** opportunity in the dynamic new computer industry?

NOT as a **PROGRAMMER** but an **OPERATOR** — No maths and no special education.

Now for the first time anybody can train **outside** the computer industry for a lucrative career as a computer operator, **with actual experience on an Eduputer.**

Who created Eduputer? The internationally famous company Programming Science International. They developed it to the specific requirements of the massive New York city training board and its practical results have been one amazing success story.

We are proud to have been selected as the only commercial training organisation permitted to use the Eduputer in the U.K. **Thanks to Eduputer, nine out of every ten can learn to operate the most advanced computers in only four weeks. Unlike Computer Programming, no special educational qualifications and no maths required. Just you and the incredible Eduputer!**

Jobs galore! The moment you qualify, our exclusive computer appointments bureau introduces you to computer users every-where with good jobs to offer (up to £40 a week full-time, £50 a week as a temporary). More than enough to go round, too—because 144,000 new operators will be needed over the next five years alone.

This is your big opportunity to get out of a rut and into the world's fastest-growing industry. And remember—LCOT is the only commercial computer school to have Eduputer. It means a lot to employers.

Telephone: (01) 437 9906 NOW!

Or post the coupon today for full details FREE and without obligation.



London Computer Operators Training Centre,
B30, Oxford House, 9/15 Oxford Street, London W.1.
Telephone: (01) 437 9906.
127/131 The Piazza, Dept. B30, Piccadilly Plaza, Manchester 1.
Telephone: (061) 236 2935.

Please send me your free illustrated brochure on exclusive Eduputer "hands on" training for computer operating.

Name _____

Address _____

Tel.: _____



RST VALVE MAIL ORDER CO.

BLACKWOOD HALL,
WELLFIELD RD., S.W.16
SPECIAL EXPRESS MAIL ORDER SERVICE

All orders post free!

1N21	3/6	AC127	5/-	BF173	6/-	GJ4M	7/6	OC43	8/-
1N23	4/0	AC128	5/-	BF181	7/6	GJ5M	5/-	OC44	3/6
1N85	17/6	AC187	6/-	BF184	5/-	GJ7M	7/6	OC44M	3/6
1N253	10/0	AC188	6/-	BF185	5/-	HG1005	10/-	OC45	3/-
1N256	10/0	ACY17	5/-	BF194	3/6	K8100A	4/-	OC45M	3/6
1N645	5/0	ACY18	5/-	BF195	3/-	MAT100	6/-	OC46	3/6
1N725A	4/-	ACY19	5/-	BF196	3/6	MAT101	6/-	OC47	12/-
1N914	1/6	ACY20	4/6	BF197	5/6	MAT120	5/-	OC58	12/-
1N4007	4/6	ACY21	4/6	BF861	5/6	MAT121	6/-	OC59	13/-
18021	4/-	ACY22	3/6	BF898	5/6	MJE520	17/6	OC66	10/-
18113	3/-	ACY27	5/6	BFX12	5/6	MJE2955	35/-	OC70	2/6
18130	2/6	ACY28	3/6	BFX13	4/6	MJE3055	18/6	OC71	3/-
18131	2/6	ACY29	11/-	BFX29	6/-	NKT128	6/-	OC72	5/-
18902	4/6	ACY40	3/-	BFX30	8/6	NKT129	6/-	OC73	6/-
2G240	39/6	ACY41	5/-	BFX35	15/6	NKT211	5/-	OC74	6/-
2G301	3/6	ACY44	7/6	BFX63	10/-	NKT213	5/-	OC75	5/-
2G302	4/6	AD140	10/-	BFX84	6/-	NKT214	3/-	OC76	5/-
2G306	6/-	AD149	10/-	BFX85	8/-	NKT216	7/6	OC77	8/-
2G371	4/6	AD161	7/6	BFX86	6/6	NKT217	8/-	OC78	4/-
2G381	5/-	AD162	7/6	BFX87	6/6	NKT218	22/6	OC78D	2/6
2G414	6/-	AF106	6/-	BFX88	5/-	NKT219	6/6	OC79	4/6
2G417	4/6	AF114	6/6	BFY10	20/-	NKT222	4/6	OC81	5/6
2N214	8/6	AF115	6/-	BFY11	25/-	NAT1	4/6	OC81D	4/6
2N250	5/0	AF116	6/6	BFY17	4/6	NKT251	4/9	OC206	4/-
2N250	10/-	AF117	5/-	BFY18	5/-	NKT271	5/-	OC81DM	3/6
2N404	4/6	AF118	12/6	BFY19	5/-	NKT272	5/-	OC81Z	11/-
2N697	3/6	AF119	4/6	BFY24	9/-	NKT273	4/9	OC82	5/-
2N698	8/6	AF124	5/-	BFY44	20/-	NKT274	4/9	OC82D	3/6
2N706	2/-	AF125	4/-	BFY50	4/6	NKT275	5/-	OC83	5/-
2N706A	2/6	AF126	3/6	BFY51	4/-	NKT277	4/9	OC84	5/6
2G240	39/6	AF127	3/6	BFY52	4/6	NKT278	5/6	OC114	7/6
2N709	12/6	AF159	6/-	BFY53	4/6	NKT801	6/-	OC122	6/6
2N711	7/6	AF178	9/6	BFY64	8/6	NKT804	7/-	OC123	10/-
2N987	10/6	AF179	9/6	BFY90	13/6	NKT403	15/-	OC139	5/-
2N1090	6/-	AF180	10/6	B8X27	10/-	NKT404	12/6	OC140	7/6
2N1091	6/6	AF181	8/6	B8X60	18/6	NKT678	6/6	OC141	12/6
2N1131	6/6	AF186	8/-	B8X76	3/-	NKT713	5/-	OC189	4/-
2N1132	6/6	AF127	3/6	B8Y26	3/6	NKT715	5/6	OC170	5/-
2N1302	4/-	AFZ11	12/6	B8Y27	4/-	NKT777	7/6	OC171	6/6
2N1303	4/6	AFZ12	15/-	B8Y51	10/-	O78B	7/6	OC200	7/6
2N1304	5/-	ASV26	5/-	B8Y95A	3/-	OA5	3/6	OC201	9/6
2N1305	5/-	ASV27	6/6	B8Y95	3/-	OA6	2/6	OC202	12/6
2N1306	5/-	ASV28	5/-	BT102/	2/6	OA47	2/6	OC203	7/6
2N1307	5/-	ASV29	5/-	50R	15/-	OA70	2/6	OC204	9/6
2N1308	6/6	ASV36	6/-	BTY42	18/6	OA71	2/6	OC205	12/6
2N1309	6/6	ASV37	6/6	BTY79/	5/-	OA73	2/6	OC206	15/-
2N1420	18/6	ASV50	3/6	100R	15/-	OA74	2/6	OC207	15/-
2N1507	5/6	ASV53	4/-	BTY79/	5/-	OA79	2/6	OC460	4/6
2N1526	7/6	ASV55	4/-	400R	35/-	OA81	2/6	OC470	6/6
2N1909	45/-	ASV62	5/-	BY100	3/6	OA85	2/6	OCPT1	19/6
2N2147	15/-	ASV86	6/6	BY126	3/6	OA86	3/6	ORP12	10/-
2N2148	12/-	ASZ21	8/6	BY127	4/-	OA90	2/6	ORP60	8/6
2N2160	12/6	ASZ23	15/-	BY182	15/-	OA91	1/6	ORP61	8/6
2N2160	12/6	AUY10	19/6	BY213	5/-	OA95	1/6	8197	6/-
2N2218	6/6	AU101	30/-	BY210	5/-	OA200	1/6	AC40	10/-
2N2287	20/6	BC107	2/6	BZ211	7/-	OA202	2/6	SFT308	7/6
2N2297	6/6	BC108	2/6	BZ212	6/-	OA210	5/-	SFT72	7/6
2N2369A	4/-	BC109	2/6	BZ213	5/-	OA211	7/6	SFT7231	12/6
2N2613	5/6	BC113	5/6	BZ215	20/-	OA2200	11/-	8X68	4/-
2N2646	10/6	BC115	6/6	BZ216	12/6	OA2201	10/-	8X631	4/-
2N2712	5/-	BC116	8/6	BZ288C3V3	3/6	OA2202	8/6	8X635	6/-
2N2784	10/-	BC118A	8/6	C111	3/6	OA2203	8/6	8X640	5/-
2N2848	8/6	BC118	7/6	CR81/05	5/-	OA2205	8/6	8X641	5/6
2N2904	6/-	BC121	4/-	CR81/40	9/6	OA2206	8/6	8X644	6/6
2N2904A	6/6	BC125	13/6	C84B	50/-	OA2207	9/6	8X645	11/-
2N2906	6/-	BC126	13/-	C810B	62/6	OA2208	6/6	V15/30P	10/-
2N2907	7/6	BC140	11/-	DD000	3/-	OA2209	6/6	V30/201P	7/6
2N2924	4/6	BC147	3/6	DD003	3/-	OA2210	6/6	V90/201P	7/6
2N2925	3/6	BC148	2/6	DD006	3/6	OA2211	6/6	V90/201P	7/6
2N2926	2/6	BC149	4/-	DD007	8/-	OA2212	8/-	XA101	2/-
2N3054	10/-	BC157	4/-	DD008	7/6	OA2223	8/-	XA102	3/6
2N3055	15/-	BC158	4/-	GD3	6/6	OA2224	7/6	XA151	3/6
2N3702	2/6	BC160	12/6	GD4	1/-	OA2241	4/6	XA152	3/-
2N3705	3/-	BC169	2/6	GD5	6/6	OA2242	4/6	XA161	5/6
2N3706	4/6	BCY31	6/6	GD8	5/-	OA2244	4/6	XA162	5/6
2N3707	3/-	BCY32	10/-	GD12	1/-	OA2246	4/6	XB101	8/6
2N3709	2/6	BCY33	4/-	GET102	6/-	OA2290	7/6	XB102	2/-
2N3710	2/6	BCY34	5/-	GET103	4/6	OA2291	8/6	XB103	5/-
2N3711	2/6	BCY38	6/6	GET113	4/6	OC18T	7/6	XB113	2/6
2N3819	7/-	BCY39	9/6	GET114	3/-	OC19	7/6	XB121	8/6
2N3820	17/6	BCY40	8/6	GET115	9/-	OC20	19/6	ZR24	12/6
2N3823	15/-	BCY42	3/-	GET116	10/-	OC22	9/6	ZB170	2/6
2N5027	10/6	BYC70	4/-	GET120	5/-	OC23	10/-	ZB271	3/6
2N5088	6/6	BCY71	6/-	GET872	6/-	OC24	10/-	ZT21	5/-
29005	15/-	BCZ10	6/-	GET875	5/-	OC25	7/6	ZT43	5/6
28301	8/6	BCZ11	7/6	GET880	7/6	OC26	5/-	ZTX107	3/6
28304	12/6	BD121	11/6	GET881	5/-	OC28	5/-	ZTX108	3/6
28501	7/6	BD122	16/6	GET882	5/-	OC29	12/6	ZTX300	2/6
28703	12/6	BD124	12/6	GET885	4/-	OC30	8/-	ZTX304	5/6
AA129	4/-	BDY11	32/6	GEX44	1/6	OC35	10/-	ZTX500	3/6
AA212	6/-	BF115	5/-	GEX45/1	1/6	OC36	12/6	ZTX503	4/6
AAZ13	2/6	BF117	10/-	GEX941	3/-	OC41	5/-	ZTX531	6/-
AC107	7/6	BF167	5/-	GJ3M	5/-	OC42	6/6		

SEMI-CONDUCTOR SET FOR P. E. GEMINI AMPLIFIER £12-19-0

SEND S.A.E. FOR LIST OF 3,000 TYPES VALVES, TUBES AND TRANSISTORS

Open daily to callers: Mon-Sat 9 a.m.-5.30 p.m.

Closed Sat. 1.30 p.m. - 2.30 p.m.

Terms C.W.O. only | Tel. 01-769 0199/1649

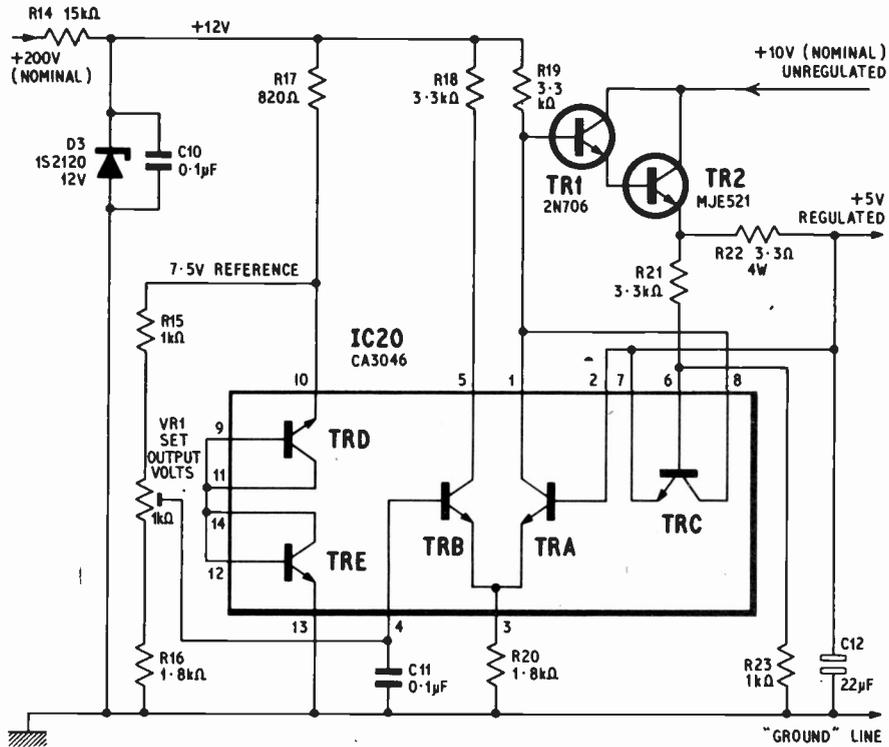


Fig. 12a. Circuit diagram of the 5V regulator circuit including foldback current limiting


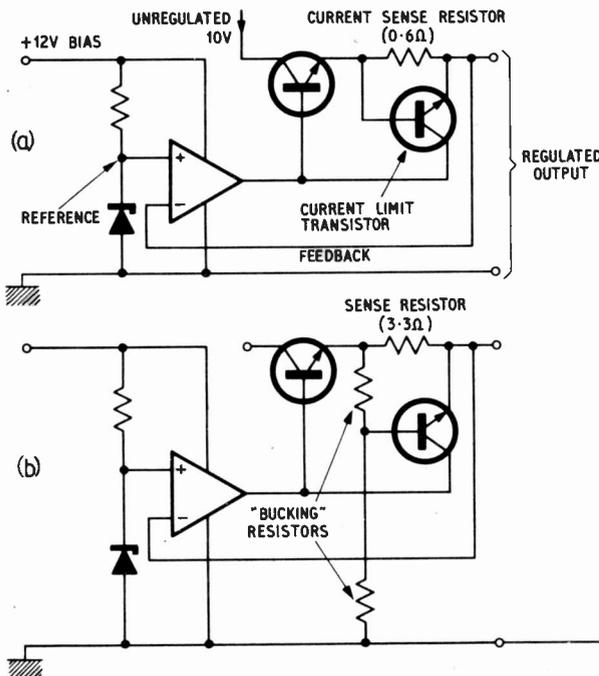


Fig. 12b. Skeleton circuit of a 5V regulator with constant current and foldback current limiting

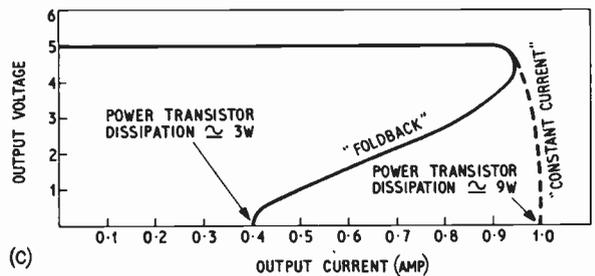

is easily provided by adding a current limiting circuit, of which there are numerous designs available, the simplest being the one transistor "constant current" arrangement.

A skeleton circuit of the regulator with this kind of limiting is shown in Fig. 12b, along with its limiting characteristic. The operation is quite straightforward; a current sense resistor in series with the 5V supply is used to develop a voltage proportional to the current drawn.

When this voltage approaches the V_{be} of the current limit transistor, it turns it on, diverting some of the base drive to the series pass transistor, and causing the output voltage to fall to maintain the preset current. If the load on the supply is reduced to zero ohms (i.e. a short circuit) the output voltage falls almost to zero allowing only a current preset by the sense resistor value to flow.


The short-circuit current must be set to greater than the permissible load current. For this particular regulator this would be up to 1A, giving a very high dissipation in the power transistor under short circuit conditions, because most of the unregulated voltage appears across this device.

HANDLING THE HEAVY LOAD

This problem could be overcome by using a heat sink large enough to handle the extra dissipation under fault conditions, but there is a much simpler method that is used in this regulator and requires only the addition of two resistors.

In Fig. 12b these extra resistors have been added, and are used as a potential divider to "buck-out" the voltage developed across the sense resistor, preventing it from turning on the transistor at the previous current level.

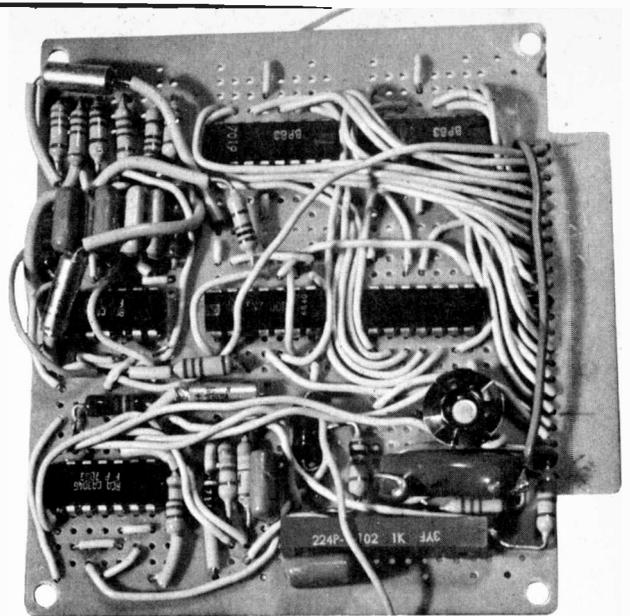With the resistor values used in this regulator, the limit transistor will not be able to turn on until the



COMPONENTS . . .

ALARM & 5V REGULATOR BOARD

(a) Alarm Oscillator

(b) 5V Regulator

Resistors

R3 8.2k Ω	R10 560 Ω	R14 15k Ω	R21 3.3k Ω
R4 1k Ω	R11 560 Ω	R15 1k Ω	R22 3.3 Ω 4W
R5 560 Ω	R12 560 Ω	R16 1.8k Ω	R23 1k Ω
R6 8.2k Ω	R13 270 Ω	R17 820 Ω	
R7 560 Ω		R18 3.3k Ω	
R8 8.2k Ω		R19 3.3k Ω	
R9 1k Ω		R20 1.8k Ω	

Potentiometer

VR1 1k Ω linear helical
(Painton Bourns type
224P-1-102)

Capacitors

C4 22 μ F tantalum 15V	C10 0.1 μ F met. foil 250V
C5 0.1 μ F met. foil 250V	C11 0.1 μ F met. foil 250V
C6 22 μ F tantalum 15V	C12 22 μ F tantalum 15V
C7 0.1 μ F	met. foil 250V (Mullard C281)
C8 0.047 μ F	
C9 0.047 μ F	

Diode

D3 1S2120,
12V 400mW Zener

Transistors

TR1 2N706
TRS MJ521 (with mica
washer)

Integrated Circuits

IC15 SN7483N (BP83)	IC20 CA3046 (R.C.A.)
IC16 SN7483N (BP83)	
IC17 SN7430N (BP30)	
IC18 SN7400N (BP00)	
IC19 CA3046 (R.C.A.)	

Further notes on purchasing i.c.s given in the article
"Making the Most of Logic ICs" last month

Miscellaneous

- S2 2-bank printed thumbwheel switch 10-way (see text) (Birch-Stolec or Radiospares)
- S3 Miniature toggle switch, single-pole, changeover LSI 40 Ω or higher miniature
- "Dualine" type DL109/22 printed circuit card (Shirehall Electronics Ltd., Station Yard, Borough Green, Sevenoaks, Kent)

current drawn approaches 1A, instead of the 250mA level set with constant current limiting and the same sense resistor.

When the transistor does turn on, however, the output voltage will drop, removing the effect of the "bucking" voltage and reducing the output current. When the output load becomes a short on the output, the final voltage will have dropped almost to zero, and the output current fallen to less than half the value at which limiting began.

This effect is termed "fold-back" limiting, for obvious reasons, and cuts the dissipation in the power transistor, under short circuit conditions, to about a third of that obtained with "constant current" limiting, operating at the same maximum current—a very worthwhile return for a couple of resistors.

In the prototype the limiter began to operate at about 1A, and with a shorted output the current dropped to 400mA, although resistor tolerances will affect these figures with later versions. The current limiting transistor TRC, is contained within the CA3046, which gives the added advantage that the operating and short-circuit current will decrease as the chip warms up, due to the negative temperature coefficient of the device's V_{be} , giving a degree of thermal feedback.

OUTPUT VOLTAGE CONTROL

The output voltage of the regulator is not affected by the limiting circuitry under normal conditions, because the feedback to the error sensing amplifier is taken from after the current sense resistor R22, the voltage drop across this resistor being automatically allowed for by the amplifier.

The capacitor C12, which should either be a 22 μ F tantalum type or an aluminium electrolytic in parallel with a 0.1 μ F paper capacitor, reduces transient spikes on the output and also ensures that the regulator remains stable at all times.

Using a miniature helical preset potentiometer for VR1 allows accurate setting of the output voltage. This type of component also features excellent temperature and long term stability. There is, however, no overriding reason why a single turn rotary control should not be substituted as an economy if a sacrifice of these qualities can be tolerated.

The construction of the regulator should precede that of the alarm circuitry; details of these will be given next month before describing the main power supply.

BSR 4-SPEED SUPERSLIM AUTO RECORD CHANGER

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. Size 13; 11in. Above motor board 3 1/2in. below 2 1/2in. AC 200/250v.



with STEREO/MONO XTAL £7 Post 5/-
 BSR UA70 Stereo/Mono Transcription Auto Changer. Calibrated Stylus Pressure. £14
 BSR Minichanger UA50 Stereo/Mono. £8
 Plays 12", 10" or 7" records. Size 12 x 8 1/2in. AC 200/250v. Post 5/-.

GARRARD PLAYERS with Sonotone 9TA Cartridges. Stereo Diamond/Mono Sapphire. SP25 Mk 11 215.
 AT60 Mk II Stereo 215. Model 5000 Stereo 213. Post 5/-.
 RECORD PLAYER PORTABLE CABINET. Space for amplifier and autochanger. Post 5/- 75/-
 BSR DE-LUXE 3 WATT AMPLIFIER. Ready made tested. 2-stage with triode pentode valve, 3 watts output. Tone and volume controls. Isolated mains transformer. Knobs. Loudspeaker, valves ECL82, E200. Response 50-12000 cps. Sensitivity 200mV. Post 5/- £4
 RGS 2 WATT AMPLIFIER with loudspeaker and valves UCL82 and UY85. Post 5/- £3

R.C.S. TEAKWOOD BASE Ready cut out for mounting (state player make and model). 65/-
 R.C.S. PLASTIC COVERS FOR ABOVE BASE. Durable tinted plastic, attractive appearance. 65/-
 EMI PICK-UP ARM. With mono xtal and stylus 25/-.
 EMI JUNIOR 4 SPEED RECORD PLAYER. Mains operated motor, turntable and pick up. Post 5/- £3
 HI-FI PICK UP CARTRIDGES
 GP4 55/-; GP93 45/-; GP91 30/-; GP67 19/-; ACOS LP. only 10/-.
 All standard fixing complete with stylus.

CRYSTAL MIKE INSERTS

1 1/2" dia. 6/-; ACOS 1 1/2" dia. 12/-; BM3, 1" dia. 8/-

PORTABLE AMPLIFIER

Portable mini p.a. system. Many uses - ideal for Parties, or as a Baby Alarm, Intercom, Telephone or Record Player Amplifier, etc. Attractive resin coated cabinet, size 12 x 9 x 4in., with powerful 7 x 4in. speaker and four transistor one watt power amplifier. Uses FP4 battery. Brand new with famous makers' guarantee. Post 5/- 75/-



WEYRAD P50 - TRANSISTOR COILS

RA2W Ferrite Aerial 13/- Spare Cores 7d.
 Osc. P50/1A/C 6/- Driver Trans. LFDT4 10/-
 LF P50/2C 470 kc/s 6/7 Printed Circuit, PCA1 10/-
 3rd LF P50/3C 6/7 T.B. Tuning Gang 11/-
 P51/1 or P51 2 6/7 Weyrad Booklet 2/-
 P50/3V 6/7 OPT1 11/-
 Mullard Ferrite Rod 8 in. 4/- 6 x 4in. 5/-

VOLUME CONTROLS

Long spindle, Midget Size 5 K. ohms to 2 Meg. LOG or LIN. L/S 3/-, D.P. 5/-
 STEREO L/S 11/-, D.P. 15/-
 Wire 5K. S.P. Transistor, 5/-
 WIRE-WOUND 3-WATT POTS. 5/-
 Small type with small knob. Values 10Ω to 30 K. Carbon 30 K to 2 meg. 8/-

80ohm Coax 9d. yd.

BRITISH AERIALITE
 AERAXIAL-AIR SPACED
 40 yd. 28/-; 60 yd. 40/-
 FRINGE LOSS 2-WATT
 IDEAL 625 lines

VEROBOARD 0-15 MATRIX
 2; 5in. 3/9; 2 1/2; 3 1/2in. 3/2; 3 1/2in. 3/9; 3; 5in. 5/2.
 EDGE CONNECTORS 18 way 5/-; 24 way 7/7.
 PINS 36 per packet 3/5, FACE CUTTERS 7/7.


S.R.B.F. Board 0-15 MATRIX 2 1/2in. wide 7d. per lin., 3 1/2in. wide 9d. per lin., 5in. wide 1 1/4/- per lin. (up to 17in.). S.R.B.F. un drilled 1/4in. Board 10/- 8in. 3/-.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2in. sides, 7 x 4in., 6/-; 11 x 3in., 8/-; 11 x 7in., 10/-; 13 x 9in., 12/-; 15 x 14in., 15/-; 9 x 7in., 8/-; 14 x 11in., 14/-.
 ALUMINIUM PANELS 18 s.w.g. 12 x 12in. 7/-; 14 x 9in., 6/-; 12 x 8in., 5/-; 10 x 7in., 4/-; 8 x 6in., 3/-; 6 x 4in., 2/-.

1 1/2inch DIAMETER WAVE-CHANGE SWITCHES. 2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way 5/- each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way 5/- each. 1 inch DIAMETER WAVECHANGE "MAKTS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way 3/- 3-way, 6 p. 2-way, 1 w. 12, 2 w. 18, 3 w. 24, 4 w. 30, 5 w. 36, 6 w. 42.
 TOGGLE SWITCHES, sp. 2/9; sp. dt. 3/7; dp. 3/7; dp. dt. 4/7

ALL PURPOSE HEADPHONES
 H.R. HEADPHONES 2000 ohms Super Sensitive 35/-
 160 RESISTANCE HEADPHONES 3-5 ohms 40/-
 DE LUXE STEREO HEADPHONES 8 ohms 65/-

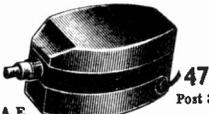"THE INSTANT"
 BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER 47/-
 Post 3/-
 200/250 v. A.C. Leallet S.A.E.
 Minimum Post and Packing 2/-.



RADIO COMPONENT SPECIALISTS

List 1/-. Written guarantee with every purchase. (Export: Remit cash and extra postage.) Buses 133, 68 pass door. S.R. Stn. Selhurst. Tel. 01-684-1666

GENERAL PURPOSE TRANSISTOR PRE AMPLIFIER BRITISH MADE

for Mike, Tape, P.U., Guitar.
 Battery 9-12v. or H.T. line 200-300V. D.C. operation. Size 1 1/2" x 1 1/2" x 3". Response 25 c.p.s. to 25 Kc/s. 28 db gain. For use with valve or transistor equipment. Full instructions supplied. Brand new. 18/- Post Guaranteed. Details S.A.E.

NEW TUBULAR ELECTROLYTICS CAN TYPES
 2/350V - 2/9 100/25V 2/- 18 + 16/500V 11/-
 4/350V - 2/9 250/25V 2/9 50 + 50/350V 7/-
 8/450V - 2/9 500/25V 4/- 80 + 100/350V 11/7
 16/450V 3/- 8 + 8/450V 3/7 32 + 32/250V 3/7
 32/450V 4/- 8 + 16/450V 4/- 32 + 32/450V 6/7
 25/25V 2/- 16 + 16/450V 5/- 32 - 32 - 32/350V 8/7
 50/50V 2/- 32 + 32/350V 5/- 100 + 50 + 50/350V 9/7
 SUB-MIN. ELECTROLYTICS 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 2/-; 500, 1000mF 12V 3/7; 2000mF 25V 7/-.
 CERAMIC. 1pF to 0.01mF, 9d. Silver Mica 2 to 5000pF, 9d. PAPER 350V-0.1 9d. 0.5 2/6; 1mF 3/-; 2mF 150V 3/-.
 500V-0.001 to 0.05 9d; 0.1 1/-; 0.25 1/6; 0.47 5/-.
 1.000V-0.001, 0.002, 0.0047, 0.01, 0.02, 1/8; 0.047, 0.1, 2/9.
 SILVER MICA. Close tolerance 1500, 2-2500pF, 1/7; 560-2000pF 2/-; 2700-5600pF 2/-; 6800pF-0.01, mid 6/- each.
 TWIN GANG. "0-0" 20pF + 176pF, 11/-; Slow motion drive 365pF + 365pF with 25pF + 25pF, 11/-; 500pF slow motion, standard 9/-; small 3-gang 600pF 22/-.
 SHORT WAVE SINGLE, 25V, 50pF, 11/-.
 CHROME TELESCOPIC AERIALS 23in. Swivel base 4/-.
 TUNING. Solid dielectric. 100pF, 500pF, 7/- each.
 TRIMMER. Compression 30, 30, 70pF, 1/-.
 100pF 150pF, 1/7; 250pF, 1/7; 600pF, 750pF, 2/-; 1000pF, 2/-.
 RECTIFIERS CONTACT COOLED half wave 60mA 7/7; 85mA 9/7. SILICON BY213 6/-; BY100 10/-.
 Full wave Bridge Rectifiers 75mA 10/-; 150mA 19/7.
 EX-GOVT. RECTIFIERS 250V, 200mA 6/-.
 NEON PANEL INDICATORS 250V, AC/DC Red or Amber 4 - RESISTORS. Preferred values 10 ohms to 10 meg.
 1 w. 1 w. 1 w. 20% 30% 2 w. 1 w. 1 w.
 HIGH STABILITY. 1 w. 2%, 10 ohms to 10 meg. 2/- Ditto 5/-. Preferred values 10 ohms to 22 meg. 9/-.
 WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K. 2/- each; 2 watt, 1 ohm to 82 ohms. 2/-

Q MAX CHASSIS CUTTER

Complete: a die, a punch, an Allen screw and key
 1in. 16/7 1in. 17/7 1in. 19/7 1in. 24/- 2 1/2in. 44/3
 1in. 16/7 1in. 19/7 1in. 20/7 1in. 20/9 2 1/2in. 57/3
 1in. 16/9 1 1/4in. 19/7 1 1/2in. 21/7 2in. 39/9 1in. sq. 36/7

AM - FM/VHF TUNING GANG

Super quality small size 1 1/4 x 1 1/2in. plus spindle 1 1/2in. 365 + 365 pF with 25 + 25 pF. British made. Geared slow motion drive 8:1. Plastic dust cover. EBA tapped front fixing. 10/- POST FREE

TRANSFORMERS

250-0-250 50 mA. 6.3 v. 2 amps, centre tapped 22/-
 250-0-250 80 mA. 6.3 v. 4 amp. 28/-
 250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. 38/-
 350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. 38/-
 300-0-300 v. 120 mA. 6.3 v. 4 a. C.T.; 6.3 v. 2 a. 50/-
 MINIATURE 200 v. 20 mA. 6.3 v. 1 a. 2 1/2in. 15/-
 MIDGET 220 v. 45 mA., 6.3 v. 2 a. 2 1/2in. 18/-
 HEATER TRANS. 6.3 v. 1 1/2amp. 11/-
 D.I.O tapped sec. 1.4 2.4 3.8 5.0 7.5 11.0 15.0
 GENERAL PURPOSE LOW VOLTAGE. Outputs 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. at 2 a. 38/-
 1 amp., 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60, 38/-
 AUTO TRANSFORMERS 0-115-230 v. Input/Output, 80w. 24/-; 150w. 38/-; 500w. 25; 1000w. £12.
 CHARGER TRANSFORMERS. Input 200/250V for 6 or 12v. 1/1 amp. 24/-; 2 amp. 11/-; 4 amp. 17/-.
 FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. outputs. 1 amp. 8/-; 2 amp. 11/-; 4 amp. 17/-.

E.M.I. 13 1/2 x 8in. LOUSPEAKERS

With flared tweeter cone and ceramic magnet. 10 watts. Bass res. 45-60 cps. Flux 10,000 gauss. 45/-
 State 3 or 8 or 15 ohm. Post 3/- each
 Also with twin tweeters. £4
 With crossover. 10 watt. £4
 State 3 or 8 or 15 ohm. Post 3/- each
 Recommended Teak Cabinet Size 16 1/2 x 9in. Post 5/- £5

MINI-MODULE LOUSPEAKER KIT

10 WATT 65/- CARRIAGES -

Triple speaker system combining on ready cut baffle. 1in. chipboard 15 in. 8 1/2in. Separate Bass, Middle and Treble loudspeakers and crossover components. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The Mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 8 ohm.
 TEAK VENEERED BOOKSHELF ENCLOSURE. 16 x 10 x 9 in. Modern Scandinavian fluted front design for Mini-Module. £5 Post 5/-

ALL MODELS "BAKER SPEAKERS" IN STOCK

BAKER 12in MAJOR £9



30-14,500 c.p.s., 12in double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell. Bass resonance 40 c.p.s. Rated 20 watts. State 3 or 8 or 15 ohm. Post Free.

Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £11.10

BAKER "GROUP SOUND" SPEAKERS - 8 or 15 ohm.
 "Group 25" "Group 35" "Group 50"
 12 inch £7 12 inch £9 15 inch £19
 25 watt 35 watt 50 watt

TEAK HI-FI SPEAKER CABINETS. Fluted wood front. For 10 or 12in round Loudspeaker £9 Post 5/-
 For 13" 8in or 8in round Loudspeaker £5 Post 5/-
 For 10 6in or 6in round Loudspeaker £4 Post 5/-
 LOUSPEAKER CABINET WADDING 18in wide, 8/- 1/4


TWO-WAY CROSSOVER NETWORK 3,000 c/s

With variable tweeter attenuator giving accurate high/low frequency balance. Mounted on panel 5 1/2in. x 4in. with control knob, tweeter and woofer leads and input 38/- terminals. Suitable for 3 to 8 ohm impedance. Post 2/-

Horn Tweeters 2-16kc/s, 10W 8 ohm or 15 ohm 30/-
 De Luxe Horn Tweeters 2-16 kc/s, 1W 8 ohm 15/-
 ELAC Moving Coil De Luxe Cone Tweeters 3 or 15 ohm 35/-
 TWO-WAY 3000 c.p.s. CROSSOVERS 3 or 8 or 15 ohm 19/-
 SPECIAL OFFER! 80 ohm. 2 1/2in. 2 1/2in. dia., 35 ohm. 3 in. 25 ohm. 3in. dia.; 6 x 4in.; 8 x 5in. 18/- EACH 15 ohm. 3 1/2in. dia.; 7 x 4in.; 8 x 5in.
 8 ohm 6 x 4in.; 3 ohm. 2 1/2in. 3in. 5in. 3in. 7 1/4in.
 LOUSPEAKERS P.M. 3 OHM. 6 1/2in. 22/-; 8 5in. 25/-; 8 1/2in. 18/-; 8in. 35/-; 10 x 6in. 38/-
 5in. WOOFER. 8 watt max. 20-10,000 cps. or 15 ohm. 36/-
 ELAC 8 in. De Luxe Ceramic 3 ohm or 15 ohm 50/-
 RICHARD ALLAN TWIN CONE LOUSPEAKERS 8in or 10in or 12in. 3 or 15 ohm 39/-
 OUTPUT TRANS. EL84 etc. 5/-
 SPEAKER COVERING MATERIALS. Samples Large S.A.E.
 GOODMAN OUTPUT TRANSFORMER 4 watt push pull for valves EL84, etc., 8, 8 and 15 ohms 17/- Post 4/-

VHF-FM TUNER FRONT END

88-108 Mc/s

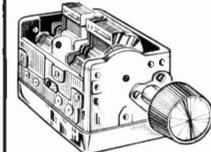

Transistor FM tuner oscillator and frequency changer printed circuit. Slow motion tuning gang condenser. Ready wired and tested including two transistors AF124 and AF125. A total of 28 components. Size 2 1/2 x 2 1/2in. Requires I.F. and Detector stages 10.7 Mc/s. 9 Volt. Connection details supplied but we have no further information available.

45/- Post Free

ALL EAGLE PRODUCTS

SUPPLIED AT LOWEST PRICES. ILLUSTRATED EAGLE CATALOGUE 5/- Post free

BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4

BARGAIN 4 CHANNEL TRANSISTOR MIXER. Add mnscial highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. £3

BARGAIN FM TUNER 88-108 Mc/s Six Transistor. 9 volt. Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 1/2in. £10

BARGAIN FM TUNER as above. Chassis only, less cabinet. £7.10

FM STEREO MULTIFLEX ADAPTOR for above or general use. Ready made with 4 transistors, 6 diodes £5

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. £3.10

COAXIAL PLUG 1/3. PANEL SOCKETS 1/3. LINE 3/7. OUTLET BOXES. SURFACE OR FLUSH 5/-.

BALANCED TWIN FEEDERS 1/- yd. 80 ohms or 300 ohms. JACK SOCKET Std. open-circuit 2/9, closed circuit 4/7; Chrome Lead Socket 7/7. Phono Plugs 1/7. Phono Socket 1/7.

JACK PLUGS Std. Chrome 3/-; 3 5mm Chrome 2/9. DIN SOCKETS Chassis 3-pin 1/7; 5-pin 2/7. DIN SOCKETS Lead 3-pin 3/7; 5-pin 5/-; DIN Flugs 3-pin 3/7; 5-pin 5/-.

VALVE HOLDERS. 1/-; CERAMIC 1/7; CANS 1/-.

E.M.I. TAPE MOTORS. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 135mA. Spindle 0-187; 0-75in. Size 3 1/2 x 2 1/2 x 2 1/2in. (Illustrated). Post 3/- 25/-

BALFOUR GRAM. MOTORS. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 50mA. Spindle 1/2 x 3/20. Size 2 1/2 x 2 1/2 x 1 1/2in. Post 3/- 17/-

RETURN OF POST DESPATCH. HI-FI STOCKISTS. CUSTOMERS FREE CAR PARK. CALLERS WELCOME.

337 WHITEHORN ROAD, CROYDON

Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-3 p.m.) Buses 133, 68 pass door. S.R. Stn. Selhurst. Tel. 01-684-1666

ELECTROVALUE

EVERYTHING BRAND NEW & TO SPEC. ● LARGE STOCKS ● NO SURPLUS

BARGAINS IN NEW SEMICONDUCTORS

Many items at new reduced prices. All power types supplied with free insulating sets

1N914	1/3	2N3706	2/6	40512	39/-	BC147	3/-	BFY61	4/-
1N3764	4/-	2N3707	4/6	40602	9/6	BC148	3/6	BXS20	3/9
1N4148	1/9	2N3708	2/6	AC107	14/6	BC149	3/6	BY164	10/-
1N5004	4/-	2N3709	2/6	AC126	4/-	BC153	7/-	BY238	3/6
1S940	1/6	2N3710	2/6	AC127	4/-	BC154	7/6	C106B1	14/8
2N696	3/6	2N3711	2/6	AC128	4/-	BC157	3/9	MC140	5/-
2N697	3/6	2N3731	24/-	AC176	6/-	BC158	3/6	MJ481	27/-
2N706	2/9	2N3794	3/-	ACY22	4/6	BC159	3/9	MJ491	30/-
2N1131	6/3	2N3819	7/-	ACY40	4/6	BC167	2/9	MFF102	7/8
2N1132	6/8	2N3820	12/-	ACY41	5/-	BC168	2/3	NKT403	15/6
2N1302	4/-	2N3904	7/8	AD142	14/3	BC169	2/3	NKT406	15/-
2N1303	4/-	2N3906	7/8	AD149	12/-	BC177	7/8	OA47	1/9
2N1304	4/6	2N4058	4/-	AD161/AD162	14/-	BC178	5/8	OA90	1/3
2N1305	4/6	2N4059	4/-	(matched)	14/-	BC179	6/-	OA91	1/3
2N1613	6/-	2N4060	4/-	AF114	7/-	BC182L	2/6	OA99	3/-
2N1711	7/-	2N4061	4/-	AF115	7/-	BC183L	2/6	OA200	1/11
2N2147	19/-	2N4062	4/-	AF116	6/6	BC184L	2/6	OA202	2/-
2N2218	9/3	2N4284	3/-	AF117	6/6	BC186	6/6	OC71	7/8
2N2218A	14/3	2N4286	3/-	AF124	7/6	BC212L	5/6	TIP31A	16/6
2N2483	6/8	2N4289	3/-	AF127	7/-	BC213L	5/-	TIP32A	20/-
2N2484	6/8	2N4291	3/-	AF139	9/8	BC214L	5/3	TIP93A	10/6
2N2646	10/9	2N4292	3/-	AF180	18/6	BCY70	21/-	T1843	3/6
2N2904	11/-	2N4410	4/9	AF239	9/9	BD121	21/-	ZTX300	3/6
2N2924	4/6	2N4284	12/3	ASY26	6/6	BD123	2/6	ZTX301	3/6
2N2926	4/6	2N5163	5/-	ASY27	8/3	BD124	20/-	ZTX302	4/6
2N2926	4/6	2N5192	25/-	ASY28	6/6	BF167	8/6	ZTX303	4/6
2N2926	2/3	2N5195	28/3	B5041	15/-	BF178	10/6	ZTX304	6/9
2N3053	5/8	2N5457	9/9	BA102	12/-	BF180	12/-	ZTX500	5/-
2N3054	14/8	2N5458	9/9	BA156	4/-	BF194	7/6	ZTX501	6/9
2N3055	15/-	2N5459	9/9	BA130	4/6	BF195	7/6	ZTX502	5/-
2N3225	10/9	40250	14/3	BA145	5/6	BFX29	6/3	ZTX503	12/-
2N3663	11/6	40361	12/6	BC107	2/9	BFX84	5/9	ZTX504	5/6
2N3702	2/6	40362	16/-	BC108	2/6	BFX85	7/6	ZTX630	5/6
2N3703	2/6	40406	16/3	BC109	2/9	BFX87	5/3	ZTX631	6/9
2N3704	2/6	40408	14/6	BC125	11/-	BFY88	8/9		
2N3705	2/6	40430	37/-	BC126	11/-	BFY60	4/6		

PEAK SOUND PRODUCTS ENGLEFIELD AMPLIFIER



12 + 12
watts RMS
per channel

Stereo amplifier in modular kit form (including cabinet) 12 watts per channel £38.9.0. Cabinet kit only £6. These prices net.

BAXANDALL SPEAKER SYSTEM



Designed by Peter Baxandall. Superb reproduction for its size. Handles 10 watts with ease. Uses ELAC 15Ω 50RM109 speaker unit. Kit £13.12.0 net.; built £19.8.6 net.

MAINLINE AMPLIFIER KITS

RCA/SGS designed main amplifier kits. Input sensitivity 500-700mV for full output into 8Ω.

Power	Kit price	Suitable unreg. power supply kit
12W	158/- net	92/-
25W	190/- net	N/A
40W	210/- net	116/10
70W	252/- net	138/10

30 WATT BAILEY AMPLIFIER KIT

Sensitivity 1.2V for full output into 8Ω. Transistors and PCB for one channel £7.5.8. Transistors and PCBs for two channels £14.11.0. Capacitors and resistors (metal oxide) 40/- per channel. Complete unregulated power supply kit £4.15.0.

ZENER DIODES

5% full range E24 values: 400mW: 2.7V to 30V 3/9 ea. 1W: 6.8V to 82V 9/- ea. 1.5W: 4.7V to 75V 12/- ea. Clip to increase 1.5W rating to 3 watts (type 266F) 9d.

CARBON TRACK POTENTIOMETERS, long spindles.

Double wiper ensures minimum noise level.
Single gang linear 220Ω to 2.2MΩ 2/6
Single gang log 4.7KΩ to 2.2MΩ 2/6
Dual gang linear 4.7KΩ to 2.2MΩ 8/5
Dual gang log 4.7KΩ to 2.2MΩ 8/5
Log/antilog 10K, 47K, 1MΩ only 8/5
Dual antilog 10K only 8/5
Any type with 1A D.P. mains switch, extra 2/5. Please note: only decades of 10, 22 and 47 are available within ranges quoted.

CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only 100Ω, 220Ω, 470Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10MΩ. Vertical or horizontal mounting 1/- each.

COMPONENT DISCOUNTS

10% on orders for components for £5 or more. 15% on orders for components for £15 or more (No discount on nett items).

POSTAGE AND PACKING

Free on orders over £2. Please add 1/6 if under. Overseas orders welcome: carriage charged at cost.

HAVE YOU HAD YOUR ELECTROVALUE CATALOGUE?

48 pages—thousands of items—packed with information, generously illustrated with product pictures and technical diagrams—2/- post free. Add 4/- if sent overseas by air mail.

RESISTORS

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	82Ω-220kΩ	E12	18d	18d	15d
C	1W	5%	4.7Ω-330kΩ	E24	2.5d	2d	1.75d
C	3W	10%	4.7Ω-10MΩ	E12	2.5d	2d	1.75d
C	1W	10%	4.7Ω-10MΩ	E24	3d	2.5d	2.25d
MO	1W	2%	10Ω-1MΩ	E24	9d	8d	7d
WW	1W	10% ± 1/20Ω	0.22Ω-3.9Ω	E12	1/8d all quantities		
WW	3W	5%	12Ω-10kΩ	E12	1/8d all quantities		
WW	7W	5%	12Ω-10kΩ	E12	1/8d all quantities		

CODES: C—carbon film high stability low noise. MO—metal oxide ElectroSil TR5 ultra low noise. WW—wire wound Pleassey.

VALUES: E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Prices are in pence each for same ohmic value and power rating. NOZ mixed values. (Ignore fractions of 1d on total resistor order.)

INTEGRATED CIRCUIT AMPLIFIERS

SINGLAIR IC10 complete with instruction book giving amplifier circuit details and range of applications. 59p nett. Components pack for stereo inc. mains transformer, controls, etc., £4.15.0 nett.

PLESSEY SL403A. Only 42/6 each nett. 3W into 7.5Ω for 15V supply. Application data 2/- free with two or more.

WAYCHANGE SWITCHES LONG SPINOLES

1P 12W; 2P 6W; 3P 4W; 4P 3W ... 4/9 each

SLIDER SWITCHES D.P.D.T.

... 3/- each

NEON INDICATOR LAMPS all 200/250V

Square bezel, red only ... 3/9
Round chrome bezel red, amber, clear ... 4/9 each
Toggle switches, 250V a.c. 1.5A. Chrome dolly and chrome milled nut S.P.S.T. 3/8; S.P.D.T. 4/8; D.P.D.T. 5/9; S.P.D.T. centre off 5/-.

S-DeC put an end to "birdnesting".

Components just plug in. Saves valuable time. Use components again and again. S-DeC (70 points) only 20/- Compact T-DeC, increased capacity, may be temperature-cycled. T-DeC (208 points) only 50/- Full range stocked.

MULLARD POLYESTER C280 series

250V 20%: 0.01, 0.022, 0.033, 0.047, 8d ea.; 0.068, 0.1, 9d ea.; 0.15, 11d; 0.22, 1/-; 10%: 0.33, 1/5; 0.47, 1/8; 0.68, 2/3; 1μF, 2/9; 1.5μF, 4/2; 2.2μF, 4/9.

MULLARD SUB-MIN ELECTROLYTIC

C426 range axial lead 1/3 each
Values (μF/V): 0.64/64, 1/40, 1.6/25, 2.5/16, 2.5/64, 4/10, 4/40, 5/64, 6.4/6.4, 6.4/25, 8/4, 8/40, 10/2.5, 10/16, 10/64, 12.6/25, 16/40, 20/16, 20/64, 25/6.4, 25/25, 32/4, 32/10, 32/40, 32/64, 40/16, 40/2.5, 50/6.4, 50/25, 50/40, 64/4, 64/10, 80/2.5, 80/16, 80/25, 100/6.4, 126/4, 126/10, 126/16, 160/2.5, 200/6.4, 200/10, 250/4, 320/2.5, 320/6.4, 400/4, 500/2.5.

LARGE CAPACITORS

High ripple current types: 1000/25 5/6; 1000/50 8/2; 1000/100 18/3; 2000/25 7/4; 2000/50 11/4; 2000/100 28/9; 2500/64 15/5; 2500/70 19/8; 5000/25 12/4; 5000/50 21/11; 5000/100 58/3; 10000/15 17/-; 10000/25 24/6; 10000/50 44/-; 10000/70 61/-.

MEDIUM RANGE ELECTROLYTICS

Axial leads: 50/50 1/9; 100/25 1/9; 100/50 2/8; 250/25 2/8; 330/25 2/8; 250/50 3/9; 500/25 3/9; 500/50 4/8; 1000/25 4/-; 1000/50 6/-; 2000/25 6/-.

SMALL ELECTROLYTICS

Axial leads: 4.7/10, 4.7/25, 5/50, 1/- ea. 10/10, 10/25, 10/50, 33/10, 50/10, 1/- ea. 25/25, 25/50, 47/25, 100/10, 220/10, 1/3 ea.

ENAMELLED COPPER WIRE even No. 8 SWG.

only: 2 oz. reels: 16-22 SWG 4/3; 24-30 SWG 5/-; 32, 34 SWG, 5/6; 36, 38 SWG, 6/3. 4 oz. reels: 16-22 SWG only 7/6.

ELECTROVALUE

Dept. PE711, 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY
Hours: 9-5.30; Sat. 1 p.m. Tel.: Egham 5533 (STD 0784-3). Telex 264475

Gerry Brown . . . ON THE FRINGE



BATH GOSSIP

"Daddy", chorused my two girls the other day, "Mummy says you're trying to talk through your bath-water. Is that true?" Well how can you best answer this sort of question when you have the bath half-full of tepid water and a whole maze of electronics and tangled wires connected to electrodes dipping over the side!

"You look as if you're going to 'lectracoot yourself'", they continued, quite unconcerned about the unanswered question, "Can we help?" Since I had no immediate desire to meet an early demise, I thought it prudent to explain just what was going on.

Actually, I had for a long while been toying with the possibility of using one of Marconi's earlier ideas for transmitting through water. His technique, which he later abandoned, was to utilise a pair of conductors on one side of a river connected to a carbon microphone and battery, and another couple of electrodes on the opposite bank hooked up to a pair of headphones. This arrangement essentially amounts to a bridge circuit, which, provided the impedances between the various electrodes are maintained as in Fig. 1, some fair results can be obtained, but only fair. Put a little two stage amplifier in at the transmitter and another in at the receiver

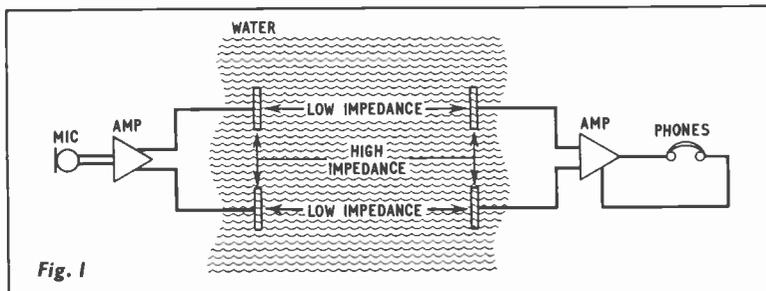


Fig. 1

and you have something that will "go-out" quite a way. Try it and see.

Two hours and four ounces of liquorice comfits later, and my bathtub project, still not off-the-ground, saw me leaving this silent epitaph of despair for the more successful reaches of the Basingstoke Canal.

WALKING MACHINES

Who, you might well ask, wants a machine that walks! Particularly since there are already such perfectly satisfactory devices as the wheel, and even caterpillar tracks for more difficult terrain. Well, it seems that at least two groups of people are extremely interested in having a viable mechanised walker at the earliest opportunity. One, the Army Tank Automotive Command in Michigan, have already got an experimental "clomper" to play with, and I understand that such a machine is likely to be brought into use where wheels or tracks leave off. This pretty sizeable piece of "iron-mongery" is apparently capable of climbing over objects in its path and walking through swamps.


The Army machine weighs 1,400 odd kilogrammes and each of the powerful legs is operated by a hydraulic "muscle" driven by high-pressure oil. Incorporated within the legs are tactile sensors which permit a degree of force-feedback control, so enabling any forces encountered by the machine to be sensed and dealt with accordingly!

Likely to have a more valid interest in walking devices are the gentlemen of the medical profession, who for years have sought the perfect walking prosthesis with precious little success. However, there seems no reason why hope should be completely abandoned because Prof. A. A. Frank of the University of Wisconsin (who has already completed a very successful four-legged creation) is currently engaged in work on a machine having two legs. This set-up, he forecasts, is anticipated to take the place of the conventional wheelchair and, in time, would give

amputees more freedom than they currently enjoy.

Coordination of the legs in Frank's device is envisaged to be under the direction of a miniaturised digital computer. This, basically, will consist of a random access core memory which can be addressed by associated read/write registers. Initially, the handicapped person would need to make the rather tedious walking movements via the artificial legs himself, but once a satisfactory gait had been established the data could be written into the memory for subsequent use. From then on, whenever walking was required, the memory would be read in a continuous fashion, rather like a tape-recorder using a loop of tape, so producing cyclic leg action; left, right, left, right, and so on until they were required to stop or maybe perform some other function.

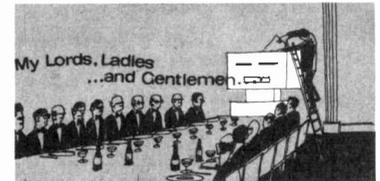A working prosthesis is expected to be in existence round about 1972; it would be nice to think that such worthwhile devices will be capable of being mass-produced fairly soon. Without a doubt the demand will be high.



CHATTY COMPUTER

For 'umpteens years now, workers in the field of speech research have hankered for a computer that could produce good synthetic speech without the prior need for human translation of input data into "machine-language" before it could "understand". They need hanker no more, for scientists at the Bell Laboratories in New Jersey have recently taught a computer to convert printed English directly into synthetic speech.

During the experiments the computer was programmed with a basic vocabulary of words, together with their categories and definitions plus such related data as the pitch, stress, and timing as used in average normal conversation. In order to achieve the most natural sound, the computer was additionally given mathematical approximations to the changes in shape which occur in the human vocal tract when making speech sounds.

In use, information for conversion to synthetic speech is fed to the computer via a conventional teletype machine. Since the programme incorporates stress data, one must trust that its digestion is not upset too greatly by such word-group similarities as "a noisy noise", and "a noise annoys", or, dare I say it, "a noisy noise annoys". "Burp!"

Readout —

A SELECTION FROM OUR POSTBAG

Correspondents wishing to have a reply must enclose a stamped addressed envelope. We regret we are unable to guarantee a reply on matters not relating to articles published in the magazine. Technical queries cannot be dealt with on the telephone.

"P.E. Gemini"

Sir—I unfortunately do not know whether Mr D. S. Gibbs or Mr I. M. Shaw was responsible for writing the introductory article for "P.E. Gemini" Stereo Amplifier, but this preamble was one of the most interesting articles which I have read for quite some time. It could easily serve as a general guide to basic amplifier design and pointing out some of the pitfalls of design and, of course, teaching one how to gain more useful information from the various technical data leaflets published by the manufacturers of stereo equipment.

I particularly liked the point about distortion at low levels. I had, up till now, thought only that distortion at the high power levels to be of importance, and how it could be "swept-under-the-carpet" by plotting the graph with a linear scale instead of a logarithmic one.

Of course, my impression of this preamble is purely subjective, not being connected in any way professionally with electronics, only in an amateur capacity, but still nevertheless, possessing a fairly good knowledge of basic valve and transistor theory through spare time reading of your own journal and various other publications. I only hope that next month's article can achieve the same level of interest; and I suspect that with the same author it will probably surpass it. As always, looking forward to next month's issue.

D. J. Whitaker,
Bromley,
Kent.

"GEMINI"

When the name *P.E. Gemini* was adopted for the Practical Electronics Stereo Amplifier, we overlooked the fact that *Gemini* was already associated with products of the Tripletone Manufacturing Co. This company has in fact used the name *Gemini* for a range of low cost amplifiers since 1959. The current version *Tripletone Gemini Mk II* is an all solid state design, previous models being valve designs. The output is 5W per channel and the retail price is £23 10s.

We hope there has been no confusion. In fact the *P.E. Gemini* and the *Tripletone Gemini Mk II* are quite dissimilar, both in specification and physical appearance.—Ed.

Beginning

Sir—I was interested to read Mr Bennett's letter (November 1970) and I appreciate the difficulty he and other beginners experience trying to find suitable books to guide them. Perhaps my own experience will be of interest to anyone finding it difficult to get started.

My interest in electronics began about 11 years ago at the age of 13. At that time transistors were relatively expensive, but I found that old televisions and radios could be acquired for next to nothing, so naturally I began by building valve circuits. I visited my local public library, renounced the children's section forever, and looked instead at the mysterious books on electronics. Nearly all of these books explained how the various electronic components functioned but hardly any of them gave practical advice on making a circuit work.

It was around this time that I discovered that magazines were available describing practical circuits and they proved to be very useful. There was nearly always some simple project that I could build and the more complex designs could be left until later. I quickly found that the practical experience helped to make the theory more meaningful.

After a year or two I was building circuits to my own designs and some of the circuits behaved in the most extraordinary way. There were audio amplifiers which oscillated and audio oscillators which didn't. This was very frustrating at the time, but clearing the faults was a challenge and further knowledge was gained in this way. Progressing from one mistake to another may not sound exciting, but its amazing how much you learn. Touching the tags of a capacitor charged to 300 volts d.c. is a mistake that you learn not to repeat too often!

Transistors and small components bring electronics within the reach of anyone having a table and a few hours to spare. A 9 volt battery makes an excellent (and inexpensive) power supply and a surprising number of projects can be built around just two transistors.

My advice to anyone thinking of taking up electronics is quite simple—

have a go! Read as many books and magazines as possible and spend as much time as you can trying out the circuits that are published.

A. M. Rudkin B.Sc.(Eng.),
St. Albans,
Herts.

Second string boost

Sir—Your reader Mr A. D. Jones (Readout, November 1970) refers to my article on guitar pick-up construction (September 1970) and points out that an important point was omitted. He is, of course, quite correct in his comment that the magnets should be mounted with like poles at the same end and I regret that this point was not included in the article.

The phenomenon known as "second string boost" amongst guitar players, has for a long time been believed to be due to the particular character of the material, tension, etc. of the second string and it is supposed that this string vibrates with a slightly wider arc than the rest of the set, so producing a stronger signal than its neighbours.

Mounting magnets with opposite poles adjacent will cause interaction between strings and certainly aggravate any tendency the second string may have to vibrate over a wider arc. Fortunately, modern technology has done much to eliminate this irritating feature and good makes of guitar strings do not usually produce this bugbear.

I have made quite a number of pick-ups in the manner described in the article, assuring that all magnets are the same way up, and all have produced an even response on all strings.

L. F. Dickson,
Salisbury,
Wilts.

MEETINGS . . .

INSTITUTION OF ELECTRICAL ENGINEERS LONDON

January 11, 5.30 p.m.
Amorphous Semiconductors, R. W. Brander, at Savoy Place, London, WC2R 0BL.

INSTITUTION OF ELECTRONIC AND RADIO ENGINEERS LONDON

January 13, 6.0 p.m.
Integrated Circuits for Colour Television, J. C. MacKellar, at 9 Bedford Square, London, WC1B 3RG.

HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD FOR EASY CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 14W r.m.s. per channel into 8 ohms. Frequency response $\pm 3dB$ 15-30,000Hz. Sensitivity better than 80mV into 1M Ω . Full power bandwidth $\pm 3dB$ 20-14,000Hz. Bass boost approx. to $\pm 12dB$. Treble cut approx. to $-16dB$. Negative feedback 18dB over main amp. Power requirements 33V at 1.0 amp. Overall size—12" wide, 8" deep, 2 1/2" high. Fully detailed 7-page construction manual and parts list free with kit or send 3/6 plus large S.A.E.

PRICES
AMPLIFIER KIT. £10.10. P. & P. 3/-.
POWER PACK KIT. £3. 0.0. P. & P. 6/-.
CABINET. £3. 0.0. P. & P. 5/-.
(Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested, £20.10. Post Free.

Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, turn record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discographic use, etc.

FANTASTIC 'POLY PLANAR' WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER
Size only 11" x 14" x 1 1/2" deep. Weight only 19 ozs. Can replace cone speaker in any application and is particularly useful for those with limited space. Extremely rugged and shockproof. Operating temperature $-20^{\circ}F$ to $+175^{\circ}F$. Power handling 10 watts rms (20 watts peak). Impedance 8 ohm only. Response 40 Hz-20 KHz. Can be mounted on ceilings, walls, doors, under tables, etc. and used with or without baffle. Send S.A.E. for full details. Only £5.10 each. P. & P. 5/-.
MAGNA VOX DESK TYPE MOVING COIL MICROPHONE. Medium impedance. Brand New—Special Price £2.10. P. & P. 2/-.
SINGLE HEADPHONE. With aluminium headband. Output 200 ohm. 5/-. P. & P. 1/6.
CRYSTAL MIKES. High imp. for desk or hand use. High sensitivity, 18/6. P. & P. 1/6.
HIGH IMPEDANCE CRYSTAL STICK MIKES. O.T.P. PRICE 2/-. P. & P. 1/6.
HIGH IMPEDANCE DYNAMIC STICK MIKES. High sensitivity. 39/6. P. & P. 2/6.

SPECIAL OFFER! PLESSEY TYPE 29 TWIN TUNING GANG. 400pF. $\pm 146pF$. Fitted with trimmers and 5:1 integral slow motion. Suitable for nominal 470 kc/s I.F. Size approx. 2 1/2" x 1 1/2" in. Only 8/6. P. & P. 2/6.
HONEYWELL MICROSWITCHES S/P. C/O. Push-button action. Rating 550V. AC at 15 amps. Size approx. 1 1/2" x 1 1/2" x 5/8" each. P. & P. 1/-. (6 or more post free).
TELESCOPIC AERIALS WITH SWIVEL JOINT. Can be angled and rotated in any direction. 6 section lacquered Brass. Extends from 6" to approx. 22 1/2". Maximum diameter 1 1/2". 5/-. P. & P. 1/-.
BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations: 0-5-10-15-20-25-30-35-40-60V half wave at 1 amp or 10-10-20, 20-20-30, 30-30-30V. at 2 amps full wave. Size 3 1/2" x 3 1/2" x 3 1/2" in. Price 35/-. P. & P. 6/-.
MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240V. Sec. 0-10-0 at 500mA. 14/-. P. & P. 2/6. Pri. 200/240V. Sec. 12-0-12 at 1 amp. 17/6. P. & P. 2/6. Pri. 200/240V. Sec. 0-10-10 at 2 amp. 27/6. P. & P. 3/6. Tapped Primary 200-220-240V. Sec. 21-5V at 500mA. 12/6. P. & P. 2/6.
BATTERY CHARGE TRANSFORMERS. 200/240V. input. Nominal output for 6 or 12V. batteries 3 amps. Size approx. 3" x 2 1/2" x 2 1/2" in. Brand New. Price 21/-. P. & P. 5/-.
HIGH GRADE COPPER LAMINATE BOARDS 8" x 6" x 1/8" in. FIVE for 10/-. P. & P. 2/-.
Open 9-5.30 Monday to Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station

SPECIAL OFFER!! HI-FI LOUDSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16 1/2" high x 10 1/2" wide x 6 1/2" deep. Fitted with E.M.I. Ceramic Magnet 13in x 8in bass unit, two H.F. tweeter units and crossover. Power handling 10W. Available 3, 8 or 15 ohm impedance.


Our Price £8.8.0 Carr. 10/-.
Also available in 8 ohm with EMI 13in x 8in bass speaker with parasitic tweeter, £6.10.0. Carr. 10/-.
LOUDSPEAKER BARGAINS
3in 4 ohm 10/-. P. & P. 1/6. 5in 3 ohm 16/-. P. & P. 3/-. 7 x 4in 3 ohm 21/-. P. & P. 4/-. 10 x 6in 3 or 15 ohm 25/-. P. & P. 6/-. E.M.I. 8 x 6in 3 ohm with high flux magnet 26/-. P. & P. 4/-. E.M.I. 13 1/2 x 8in 3 ohm with high flux ceramic magnet 42/-. (15 ohm 45/-.) P. & P. 6/-. E.M.I. 13 x 8in, 3 or 15 ohm with two built-in tweeters and crossover network 4 1/2. P. & P. 6/-.
BRAND NEW. 12in 15W H/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with HiDux ceramic ferrobar magnet assembly £5.10.0. P. & P. 7/6. Guitar models: 25w £6.10.0. 35w £8.10.0.
E.M.I. 4in HEAVY DUTY TWEETERS. Powerful ceramic magnet. Available in 3, 8 or 15 ohm 18/6 each. P. & P. 2/6.
13in "RA" TWIN CONE LOUDSPEAKER
10 watts peak handling. 3 or 15 ohm, 27/6. P. & P. 6/-.
35 OHM SPEAKERS. 3in 14/-. P. & P. 2/6.

HI-FI STEREO HEADPHONES


Adjustable headband with comfortable flexifoam earmuffs. Wired and fitted with standard stereo 3 1/2 in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. PRICE 59/-. P. & P. 3/-.
GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER. For P.U. Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9-18V. Battery or from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 20dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1 1/2". Brand new—complete with instructions. Price 17/6. P. & P. 2/6.
BRAND NEW E.M.I. LIGHTWEIGHT PICK-UP ARM WITH ARM REST (as above). Fitted mono (t/o) stylus and cartridge for LP/78. ONLY 20/-. P. & P. 1/6.
QUALITY RECORD PLAYER AMPLIFIER MK II
A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. x 8 1/2" d. x 6h. Ready built and tested. PRICE 75/-. P. & P. 6/-. ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE 97/6. P. & P. 7/6.
DE LUXE QUALITY PORTABLE R/P CABINET MK II
Tuned motor board size 14 1/2" x 12in. Clearance 2in. below. 5 1/2in. above. Will take above amplifier and any B.S.R. or GARRARD changer of Single Player (except AT60 and SP25). Size 13 1/2" x 15 1/2" in. PRICE 79/6. P. & P. 9/6.

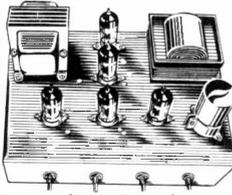10.14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Superior reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up: EL84s, ECC83, E80 and E230 rectifier, simple instruction booklet 2/6 (Free with parts). All parts sold separately, ONLY £7.19.6. P. & P. 8/6. Also available ready built and tested complete with s.t. input sockets, £9.19.6. P. & P. 8/6.
BRAND NEW TRANSISTOR BARGAINS. GET 15 (Matched Pair) 15/-. V1510/10, O71 5/-. O76 6/-. AF17 5/6. 25339 (SPN) 9/-. Set of matched 2 transistors OC44, 2-OC45, AC128D, matched pair AC128 25/- ORP12 Cadmium Sulphide Cell 10/6. All post free.
VERY POWERFUL COMPACT MOTOR
For 12v. D.C. operation. Off load consumption approx. 100mA. Totally enclosed. Quiet in operation with high starting torque. Overall size approx. 1 1/2" L x 1 1/2" dia. Free shaft 3/8" dia. x 1/8" L. Ideal for Model Makers, etc. ONLY 7/6 each P. & P. 1/-. 3 or more post free (A few Gv. versions also available).



DE LUXE STEREO AMPLIFIER

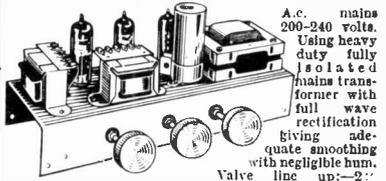

A.C. mains 200-240 volts. Using heavy duty fully rated 4 x 4 mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up—2 x ECL86 Triode Pentodes. 1 x E280 as full wave rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11in. w x 4in. x. Overall height including valve 6in. Ready built and tested to a high standard. Price £8.18.6. P. & P. 8/-.
4-SPEED RECORD PLAYER BARGAINS
Main models. All brand new in maker's packing. LATEST B.S.R. C109/A21 4-SPEED AUTOCHANGER. With latest mono compatible cartridge £6.19.6. Carr. 6/6. P. & P. 1/6. SUTABLE PLINITH UNIT FOR ABOVE with rigid plastic cover. £5.15.0 complete. P. & P. 8/6. LATEST GARRARD MODELS. All types available 1025, 2025, SP25, 3000, AT60. etc. S.A.E. for Latest Prices! PLINITH Units cut out for Garrard Models 1025, 2025, 3000, 3500, etc. With rigid transparent plastic cover. Highest design enable above models to be used with cover in position. Also suitable for housing AT60 and SP25. OUR PRICE £5.15.0 complete. P. & P. 8/6.
LATEST ACOG GP91/15C Mono Compatible Cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. 30/-. P. & P. 1/6.
ACOG HI-G Single sided mono cartridge for LP & EP. ONLY 10/-. Post Free.
SONOTONE STANC COMPATIBLE STEREO CARTRIDGE T/O stylus. Diamond Stereo LP and Sapphire 78. ONLY £2.10.0. P. & P. 2/-.
Also available fitted with twin Diamond T/O stylus for Stereo LP. ONLY £3. P. & P. 2/-.
LATEST RONETTE T/O Stereo Compatible Cartridge for EP/LP/Stereo/78. 32/6. P. & P. 2/-.
LATEST RONETTE T/O Mono Compatible Cartridge for EP/LP/78 mono or stereo records on mono equipment. 30/-. P. & P. 2/-.
HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT
Type TAI
Peak output in excess of 11 watts. All standard British components. Built on printed circuit panel size 6" x 3in. Generous size Driver and Output Transformers. Output transformer tapped for 3 ohm and 15 ohm speakers. Transistors (GET114 or S1 Mullard AC 128D and matched pair of AC128 o/p), 9 volt operation. Everything supplied, wire, battery clips, solder, etc. Comprehensive easy to follow instructions and circuit diagram 2/6 (Free with Kit). All parts sold separately. SPECIAL PRICE 49/6. P. & P. 3/-. Also ready built and tested, 65/-. P. & P. 3/-.
3-VALVE AUDIO AMPLIFIER HA34 MK II
Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4in. d. x 4 1/2in. h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4.15.0. P. & P. 6/-.
HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. 79/6. P. & P. 5/-.
HARVERSON'S SUPER MONO AMPLIFIER
A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New, completely wired and tested with good quality output transformer. FEW ONLY.
OUR ROCK BOTTOM BARGAIN PRICE 55/-. P. & P. 6/-.
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

Open 9-5.30 Monday to Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19 Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

BI-PAK WAREHOUSE CLEARANCE

Over 1 Million Semiconductors must be sold.
Order any or all of these. Bargain "SALE" PAKS
Listed Below "NOW"

UNSORTED/UNTESTED/UNCODED/UNBEATABLE
VALUE

PAK Order No.	Qty.	Description	Price per PAK
SA1	150	Germ. Trans PNP Mixed lots	10/-
SA2	200	Germ. & Sil. Alloy Trans. PNP	10/-
SA3	100	Germ. A.P. Trans. 300mW PNP	10/-
SA4	200	Sil. Alloy Low gain switching Trans. PNP	10/-
SA5	100	Sil. planar plastic trans. PNP	10/-
SA6	100	Sil. plastic planar trans. NPN	10/-
SA7	100	Sil. planar Trans. TO8 plastic PNP 800mW	20/-
SA8	100	Sil. planar trans. TO18 plastic NPN 500mW	20/-
SA9	100	Sil. planar trans. plastic NPN med. & high gain	20/-
DIODES			
SB1	200	GERM Diodes Gen.P.	10/-
SB2	200	GERM Gold Bonded	10/-
SB3	200	Sil. Switching Diodes 50mA	10/-
SB4	200	Sil. Gen.T. Diodes 200mA	10/-
SB5	300	Sil. & Germ. Mixed Diodes	10/-

The following are all new and Fully Tested Transistor Packs.

Order No.	Qty.	Description	Price per PAK
ST1	50	PNP Trans Mixed all coded Germ.	20/-
ST2	40	NPN Germ. To-5 2G339 Evtl. 2N1302 AC127	20/-
ST3	40	PNP Germ. AF 2G371B OC71-75 type	20/-
ST4	30	PNP Germ. VHF-2G407L= AF117= OC170 uncoded	20/-
ST5	30	PNP Metal Alloy VHF 800mW's Trans.	20/-
ST6	40	NPN/NPN Switching Trans all coded	20/-
ST7	40	D1374 PNP Trans Evtl. ASY22 OC44/49	20/-
ST8	40	2N706 NPN Assorted Sil. Trans.	20/-
ST9	30	2N708 NPN Sil. Trans.	20/-
ST10	30	BSY28 NPN Sil. Trans.	20/-
ST11	25	2N3703 PNP Sil. Trans	20/-
ST12	25	T1848= 2N2368 NPN 400m/cs	20/-
ST13	25	2E292846 NPN TO-18 plastic 330m/cs	20/-
ST14	40	283010 Sil. Alloy Trans PNP TO3	20/-

WHEN ORDERING PLEASE MENTION PAK, ORDER NO. IN ALL CASES. CLUBS, SCHOOLS & OTHER ORGANISATIONS REQUIRING LARGER QUANTITIES (1,000 MIN. SA & SB) (100 MIN. ST) MAY SUBMIT THEIR OFFERS NOT LATER THAN 1st FEB. 1971.

★ NEW STOCK ITEMS ★

1 AMP SILICON RECTIFIERS (MINIATURE PLASTIC CASE)

Type	Price each and Quantity Price
PIV	
1N4001	50 1.49 100 1.49 200 1.49 400 1.49 800 1.49 1000 1.49
1N4002	50 1.49 100 1.49 200 1.49 400 1.49 800 1.49 1000 1.49
1N4003	50 1.49 100 1.49 200 1.49 400 1.49 800 1.49 1000 1.49
1N4004	50 1.49 100 1.49 200 1.49 400 1.49 800 1.49 1000 1.49
1N4005	50 1.49 100 1.49 200 1.49 400 1.49 800 1.49 1000 1.49
1N4006	50 1.49 100 1.49 200 1.49 400 1.49 800 1.49 1000 1.49
1N4007	50 1.49 100 1.49 200 1.49 400 1.49 800 1.49 1000 1.49

300mW GLASS SILICON RECTIFIERS Do-7 Case

VOLTAGE RANGE 50-1000PIV and PRICE AS FOLLOWS:

Voltage	9d. each	50-99	100p.
50V	1.49	9d. each	7d. each
100V	1.49	9d. each	7d. each
200V	1.49	9d. each	7d. each
400V	1.49	9d. each	7d. each
600V	1.49	9d. each	7d. each
800V	1.49	9d. each	7d. each
1000V	1.49	9d. each	7d. each

GENERAL PURPOSE GERM. PNP POWER TRANSISTORS

Coded GF100. BRAND NEW To-3 CASE. POSS. REPLACEMENTS FOR: OC23-28-29-30-35-36, NKT401-403-404-405-406-450-451-452-453, TI3027-3028, 2N220A, 2N458A-457A-458A, 2N511-511A & B, 2E220-222, ETC.

Specification	1-24	25-99	100up.
VCBO 80V VCEO 50V IC 10A PT 30 WATTS HFE 30-170	1.24	25-99	100up.
PRICE	8/8 each	8/- each	7/8 each.

GENERAL PURPOSE SILICON NPN POWER TRANSISTORS

Coded GF300. BRAND NEW To-3 CASE. POSSIBLE REPLACEMENT FOR: 2N3055, BDY20, BDY11.

Specification	1-24	25-99	100 +
VCBO 100V. VCEO 60V. IC 15AMP'S. PT. 115 WATTS. Hfe 20-100. FTI MHZ.	1.24	25-99	100 +
PRICE	11/- each	10/- each.	9/8 each.

SEMICONDUCTOR HAND BOOK

240 PAGES OF SUGGESTED CIRCUITS—TRANSISTOR OUTLINES AND SEMI-CONDUCTOR SPECIFICATIONS. INTRODUCTION AND EXPLANATION IN 11 LANGUAGES: ENGLISH, DUTCH, FRENCH, GERMAN, INDOONESIAN, SWEDISH, SPANISH, PORTUGUESE, ITALIAN, ARABIAN, SERBO-CROATHIAN. A HANDBOOK FOR ALL SEMI-CONDUCTOR USERS. (DUTCH PUBLICATION). PRICE 28/8 incl. P. & P.

SEND ALL ORDERS FOR BY-RETURN SERVICE



BI-PAK = LOW COST I.C.'s

BI-PAK Semiconductors now offer you the largest and most popular range of I.C.'s available at these EXCLUSIVE LOW PRICES. TTL Digital 74 Series fully coded, brand new. Dual in-line plastic 14 and 16 pin packages.



BI-PAK Order No.	Similar Types to:- Description	Price and qty. prices
BP00 7400N	Quad 2-Input NAND GATE	1-24 26-99 100 up
BP01 7401N	Quad 2-Input NAND Gate—OPEN COLLECTOR	6/8 5/8 4/8
BP04 7404N	HEX INVERTER	6/8 5/8 4/8
BP10 7410N	Triple 3-Input NAND GATE	6/8 5/8 4/8
BP20 7420N	Dual 4-Input NAND GATE	6/8 5/8 4/8
BP30 7430N	Single 5-Input NAND GATE	6/8 5/8 4/8
BP40 7440N	Dual 4-Input BUFFER GATE	6/8 5/8 4/8
BP41 7441N	BCD to decimal decoder and NIT Driver	22/8 20/- 17/8
BP42 7442N	BCD to decimal decode (TTL O/P)	22/8 20/- 17/8
BP50 7450N	Dual 2-Input AND/OR/NOT GATE—expandable	6/8 5/8 4/8
BP63 7463N	Single 8-Input AND/OR/NOT GATE—expandable	6/8 5/8 4/8
BP60 7460N	Dual 4-Input—expandable	6/8 5/8 4/8
BP70 7470N	Single JK Flip-Flop—edge triggered	9/- 8/- 7/-
BP72 7472N	Single Master Slave JK Flip-flop	9/- 8/- 7/-
BP73 7473N	Dual Master Slave JK Flip-flop	10/- 9/- 8/8
BP74 7474N	Dual D Flip-flop	10/- 9/- 8/8
BP75 7475N	Quad Bistable Latch	11/- 10/- 9/8
BP76 7476N	Dual Master Slave Flip-flop with preset and clear	11/- 10/- 9/8
BP83 7483N	Four Bit Binary Adder	26/- 22/8 20/-
BP90 7490N	BCD Decade Counter	22/8 20/- 17/8
BP92 7492N	Divide by 12 4 Bit binary counter	22/8 20/- 17/8
BP93 7493N	Divide by 16 4 Bit binary counter	22/8 20/- 17/8
BP94 7494N	Dual Entry 4 Bit Shift Register	22/8 20/- 17/8
BP95 7495N	4 Bit Up-Down Shift Register	22/8 20/- 17/8
BP96 7496N	5 Bit shift register	24/- 21/- 18/8

Data is available for the above Series of Integrated circuits in booklet form, price 2/6.

BRAND NEW FULL TO MANUFACTURERS' SPECIFICATION

BP709 Operational Amplifier, dual-in-line 14 pin package — BN72709 and similar to MC709 and ZLD709C. 10/8 9/- 8/- This is a high performance operational amplifier with high impedance differential inputs and low impedance output.

TTL INTEGRATED CIRCUITS

Manufacturers "Fall outs"—out of spec. devices including functional units and part functional but classed as out of spec. from the manufacturers very rigid specifications. Ideal for learning about I.C.'s and experimental work, on testing, some will be found perfect.

PAK No.	PAK No.
UIC00 = 5 x 7400N	UIC73 = 5 x 7473N
UIC01 = 5 x 7401N	UIC74 = 5 x 7474N
UIC02 = 5 x 7402N	UIC75 = 5 x 7475N
UIC03 = 5 x 7403N	UIC76 = 5 x 7476N
UIC04 = 5 x 7404N	UIC80 = 5 x 7480N
UIC05 = 5 x 7405N	UIC82 = 5 x 7482N
UIC10 = 5 x 7410N	UIC83 = 5 x 7483N
UIC20 = 5 x 7420N	UIC86 = 5 x 7486N
UIC40 = 5 x 7440N	UIC90 = 5 x 7490N
UIC41 = 5 x 7441AN	UIC92 = 5 x 7492N
UIC42 = 5 x 7442N	UIC93 = 5 x 7493N
UIC50 = 5 x 7450N	UIC94 = 5 x 7494N
UIC61 = 5 x 7461N	UIC95 = 5 x 7495N
UIC60 = 5 x 7460N	UIC96 = 5 x 7496N
UIC70 = 5 x 7470N	UIC91 = 20 x AB87'D 74's
UIC72 = 5 x 7472N	

Packs cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1. Every PAK carries our BI-PAK Satisfaction or money back GUARANTEE.

DUAL-IN-LINE LOW PROFILE SOCKETS

14 and 16 lead sockets for use with Dual-In-Line Integrated Circuits.

Order No.	Price each
TS014 14 pin type	1-24 25-99 100 up
TS016 16 pin type	7/8 8/- 5/3
	10/- 8/8 7/9

RTL FAIRCHILD (U.S.A.) I.C.'s

RTL Micrologic Circuits	Qty. prices each
Epoxy case To-6 temp. range 15°C to 55°C	1-11 12-24 25-99 100 +
μL 900 Buffer	8/- 7/- 6/8 5/8
μL 914 Dual two-input GATE	8/- 7/- 6/8 5/8
μL 923 J-K Flip-flop	10/8 10/- 9/8 9/-
Full data and circuits for IC's in Booklet form price 1/8 each.	
μA703E Linear RF-IF AMPLIFIER	11/- 10/- 9/- 8/8
PLASTIC CASE To-6 lead up to 100 in/cs.	

DTL DIGITAL I.C.'s

DTL dual in-line package.	Price
Type MC844P expandable dual 4-input NAND Power Gate	10/- each
Type MC845P Clocked Flip-flop	15/- each
Type 882 Triple 3 Input NAND/NOR Gate	10/- each

FULL DATA SUPPLIED WITH UNITS

Please send all orders direct to our warehouse and despatch department.

BI-PAK SEMICONDUCTORS
P.O. BOX 6, WARE, HERTS.

Postage and packing add 1/- Overseas add extra for Airmail. Minimum order 10/- Cash with order please.

VALUE ALL THE WAY

LINEAR INTEGRATED CIRCUITS

BI-PAK MONOLITHIC AMPLIFIERS (TO-5 8 lead)

BF709C, Operational amplifier, 15/- each.
 BF701C, Operational amplifier with Zener output, 12/6 each.
 BF702C, Operational amplifier with direct output, 12/6 each.
 HF501, Wide band amplifier, 18/- each.
 HF521, Logarithmic wide band amp., 14/- each.
 BF703C, General purpose amplifier (TO-5 8 lead), (voltage or current amp.), 12/6 each.
 I.C. Operational Amplifier with Zener output.
Type 701C. Ideal for P.E. Projects. 8 lead TO-5 case. Full data.

Our price **12/6** each
 5 off 11/- each. Large Qty. Prices quoted for.

SIL. G.P. DIODES

300mW 30 10/-
 40PIV (Min.) 100 30/-
 Sub-Min. 500 25
 Full Tested 1,000 29
 Ideal for Organ Builders.

OA200/OA202

Each 1/8
 SILICON Diodes
 35 + 1/8
 100 + 1/3
 500 + 1/1

★ **TRADE** ★
SEND FOR YOUR FREE CATALOGUE

MULLARD I.C. AMPLIFIERS

TA243, Operational amplifier, 70/- each.
 TA263, Linear AF amplifier, 15/- each.
 TA293, General purpose amplifier, 18/6 each.

CA3020 RCA (U.S.A.) LINEAR INTEGRATED CIRCUITS

Audio Power Amplifier, 30/- each.

OTHER MONOLITHIC DEVICES

D13D1 Silicon Unilateral switch 10/- each.
 A Silicon Planar, monolithic integrated circuit having thyristor electrical characteristics, but with an anode gate and a built-in "Zener" diode between gate and cathode. Full data and application circuits available on request.

Silicon Microwave Diodes—Sylvania (U.S.A.)

IN218 and IN218R matched pair 8. Band mixer. Max. overall noise function 13.7dB at 3,000Mc/s Brand new and boxed. Clearance Price 6/- pair.

EX-EQUIPMENT MULLARD

AF117 transistors. Large can 4 lead type. Leads cut short but still usable, real value at 15 for 10/-.

ADI61 PNP

ADI62 PNP

MATCHED COMPLEMENTARY PAIRS OF GERM. POWER TRANSISTORS.

For mains driven output stages of Amplifiers and Radio receivers.
OUR LOWEST PRICE OF 12/6 PER PAIR

HIGH POWER SILICON PLANAR TRANSISTORS: TO-3

FERRANTI ZT1487 PNP

VCB60 Ic 6A I_T 1M/1ms
 VCE40 Ptot. 75W
 VEB8 hFE15-45
PRICE 6/- EACH

2N3055 115 WATT SIL. POWER NPN

OUR PRICE 12/6 EACH

FULL RANGE OF ZENER DIODES

VOLTAGE RANGE
 2-33V. 400mW (DO-7 Case) 2/6 ea. 14W (Top-Hat) 3/6 ea. 10W (SO-10 Stud) 5/- ea. All fully tested 5% tol. and marked. State voltage required.

BRAND NEW TEXAS GERM. TRANSISTORS Coded and Guaranteed

Pak No. EQVT
 T1 8 26371A OC71
 T2 8 26374 OC75
 T3 8 26374A OC81D
 T4 8 26381A OC81
 T5 8 26382T OC82
 T6 8 26344A OC44
 T7 8 26345A OC45
 T8 8 26378 OC78
 T9 8 26399A 2N1302
 T10 8 26417 AF117
 All 10/- each pack

2N2080 NPN SIL. DUAL TRANS. CODE D1699

TEXAS. Our price 5/- each.

120 VCB NIXIE DRIVER TRANSISTOR.

8im. BSN21 & C407, 2N1893 FULLY TESTED AND CODED NDI20, 1-24 3/6 each. TO-5 N.P.N. 25 up 3/- each.

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqt. ZTX300 1/- each. Any Qty.

FREE

One 10/- Pack of your own choice free with orders valued 44 or over.

AF239 PNP GERM. SIEMENS VHF TRANSISTORS. RF MIXER & OSC. UP TO 300 MHz. USE AS REPLACEMENT FOR AF139-AF186 % 100% OF OTHER USES IN VHF. OUR SPECIAL LOW PRICE.—1-24 7/6 each. —25-99 8/6 each 100 + 6/- each.

FET'S

2N 3819 7/-
 2N 3820 18/6
 MPF105 8/-

LOW COST F.E.T.'S

Fully Tested, Guaranteed Parameters equit. to 2N3819, MPF102, 2N-5459. 1-24 7/6 each; 25-99 8/3 each; 100 up 5/6 each. Coded FE19. Full data sent. TO-72 case.

CADMIUM CELLS

ORP12 8/6
 ORP60, ORP61 8/- each

PHOTO TRANS.

OCF71 Type. 8/6

KING OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back. Pak No.

- U1 120 Glass Sub-min. General Purpose Germanium Diodes 10/-
- U2 60 Mixed Germanium Transistors AF/RF 10/-
- U3 75 Germanium Gold Bonded Diodes sim. OA5, OA47 10/-
- U4 40 Germanium Transistors like OC81, AC128 10/-
- U5 60 200mA Sub-min. Sil. Diodes 10/-
- U6 30 Silicon Planar Transistors NPN sim. BSY95A, 2N708 10/-
- U7 16 Silicon Rectifiers Top-Hat 750mA up to 1,000V 10/-
- U8 50 Sil. Planar Diodes 250mA OA/200/202 10/-
- U9 20 Mixed Volts 1 watt Zener Diodes 10/-
- U11 30 PNP Silicon Planar Transistors TO-5 sim. 2N1132 10/-
- U13 30 PNP-NPN Sil. Transistors OC200 & 2N104 10/-
- U14 150 Mixed Silicon and Germanium Diodes 10/-
- U15 25 NPN Silicon Planar Transistors TO-5 sim. 2N697 10/-
- U16 10 3-Amp Silicon Rectifiers Stud Type up to 1000 PIV 10/-
- U17 30 Germanium PNP AF Transistors TO-5 like ACY 17-22 10/-
- U18 8 6-Amp Silicon Rectifiers BYZ13 Type up to 600 PIV 10/-
- U19 25 Silicon NPN Transistors like BC108 10/-
- U20 12 1.5-amp Silicon Rectifiers Top-Hat up to 1,000 PIV 10/-
- U21 30 A.F. Germanium alloy Transistors 2G300 Series & OC71 10/-
- U23 30 Madt's like MAT Series PNP Transistors 10/-
- U24 20 Germanium 1-amp Rectifiers GJM up to 300 PIV 10/-
- U25 25 300Mc/s NPN Silicon Transistors 2N708, BSY27 10/-
- U26 30 Fast Switching Silicon Diodes like IN914 Micro-min 10/-
- U28 Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc., 8 Assorted Pieces 20/-
- U29 10 1 amp SCR's TO-5 can up to 600 PIV CR51/25-600 20/-
- U31 20 Sil. Planar NPN trans. low noise Amp 2N3707 10/-
- U32 25 Zener diodes 400mW D07 case mixed Volts, 3-18 10/-
- U33 15 Plastic case 1 amp Silicon rectifiers IN4000 series 10/-
- U34 30 Sil. PNP alloy trans. TO-5 BCY26, 2N302/4 10/-
- U36 25 Sil. Planar trans. PNP TO-18 2N2906 10/-
- U36 25 Sil. Planar NPN trans. TO-5 BFY50/51/52 10/-
- U37 30 Sil. alloy trans. SO-2 PNP, OC200 2N322 10/-
- U38 20 Fast Switching Sil. trans. NPN, 400Mc/s 2N3011 10/-
- U39 30 RF Germ. PNP trans. 2N1303/3 TO-5 10/-
- U40 10 Dual trans. 6 lead TO-5 2N2060 10/-
- U41 25 RF Germ. trans. TO-1 OC45 NKT72 10/-
- U42 10 VHF Germ. PNP trans. TO-1 NKT667 AF117 10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked

NEW LOW PRICE TESTED S.C.R.'S

1A	3A	7A	16A	30A
(TO-5) (TO-66) (TO-48) (TO-48) (TO-48)				
PIV	each	each	each	PIV each
50	4/8	5/-	9/6 10/8	25 20/
100	5/-	6/6	10/6 12/6	50 22/-
200	7/-	7/8	11/6 15/6	100 28/-
400	8/6	9/6	13/6 18/6	200 32/-
600	10/6	11/6	15/6 25/6	400 35/-
800	12/6	14/-	18/-	300 40/80/-

2A POTTED BRIDGE RECTIFIERS.

200V 10/-.

DIACS

FOR USE WITH TRIACS

BR100 7/6 each

PRINTED CIRCUITS EX-COMPUTER

Packed with semiconductors and components, 10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards 10/-. Plus 2/- P. & P.

PLEASE NOTE.

To avoid any further Increased Postal Charges to our Customers and enable us to keep our "By Return Postal service" which is second to none, we have re-organized and streamlined our Despatch Order Department and we now request you to send all your orders together with your remittance, direct to our Warehouse and Despatch Department, postal address: BI-PAK SEMICONDUCTORS, Despatch Dept., P.O. Box 6, WARE, HERTS. Postage and packing still 1/- per order. Minimum order 10/-.

QUALITY-TESTED PAKS

- 6 Matched Trans. OC44/45/81/81D 10/-
- 20 Red Spot AF Trans. PNP 10/-
- 10 White Spot RF Trans. PNP 10/-
- 6 Silicon Rects. 3 A 100-400 PIV 10/-
- 2 10 A Silicon Rects. 100 PIV 10/-
- 2 OC1 140 Trans. NPN Switching 10/-
- 1 12 A SCR 100 PIV 10/-
- 3 Sil. Trans. 2N303 PNP 10/-
- 3 200 Mc/s Sil. Trans. NPN BS2Y26/27 10/-
- 3 Zener Diodes 1W 33V 5% Tol. 10/-
- 4 High Current Trans. OC42 Eqt. 10/-
- 2 Power Transistors 1 OC26 1 OC35 10/-
- 6 Silicon Rects. 400 PIV 250mA 10/-
- 4 OC75 Transistors 10/-
- 1 Power Trans. OC20 100V 10/-
- 10 OA202 Sil. Diodes Sub-min. 10/-
- 2 Low Noise Trans. NPN 2N929/30 10/-
- 1 Sil. Trans. NPN VCB 100 ZT86 10/-
- 8 OA81 Diodes 10/-
- 4 OC72 Transistors 10/-
- 4 OC77 Transistors 10/-
- 4 Sil. Rects. 400 PIV 500mA 10/-
- 6 GET884 Trans. Eqt. OC44 10/-
- 6 GET883 Trans. Eqt. OC45 10/-
- 2 2N708 Sil. Trans. 300Mc/s NPN 10/-
- 3 GT31 LF Low Noise Germ. Trans. 10/-
- 6 IN914 Sil. Diodes 75 PIV 75mA 10/-
- 8 OA95 Germ. Diodes Sub-min. IN69 10/-
- 3 NPN Germ. Trans. NKT773 Eqt. 10/-
- 2 OC22 Power Trans. Germ. 10/-
- 2 OC25 Power Trans. Germ. 10/-
- 4 AC128 Trans. PNP High Gain 10/-
- 4 AC127/128 Coup. pair PNP/NPN 10/-
- 3 2N307 PNP Switching Trans. 10/-
- 7 CG62H Germ. Diodes Eqt. OA71 10/-
- 1 AF116 Type Trans. 10/-
- 12 Assorted Germ. Diodes Marked 10/-
- 4 AC126 Germ. PNP Trans. 10/-
- 4 Silicon Rects. 100 PIV 750mA 10/-
- 3 AF117 Trans. 10/-
- 7 OC81 Type Trans. 10/-
- 3 OC171 Trans. 10/-
- 6 2N2926 Sil. Epoxy Trans. 10/-
- 7 OC71 Type Trans. 10/-
- 2 2S701 Sil. Trans. Texas 10/-
- 2 10 A 600 PIV Sil. Rects. 1845E 10/-
- 3 BC108 Sil. NPN High Gain Trans. 10/-
- 1 2N910 NPN Sil. Trans. VCB 100 10/-
- 2 1000 PIV Sil. Rect. 1.5 A R63310 AF 10/-
- 3 BSY95A Sil. Trans. NPN 200Mc/s 10/-
- 3 OC200 Sil. Trans. 10/-
- 2 GT880 Low Noise Germ. Trans. 10/-
- 1 AF139 PNP High Freq. Trans. 10/-
- 3 NPN Trans. 1 8T141 & 2 8T140 10/-
- 4 Madt's 2 MAT100 & 2 MAT120 10/-
- 4 OC44 Germ. Trans. AF 10/-
- 3 AC127 NPN Germ. Trans. 10/-
- 1 2N3906 Sil. PNP Trans. Motorola 10/-
- 2 Sil. Power Rects. BYZ13 15/-
- 1 Sil. Power Trans. NPN 100Mc/s 15/-
- 1 TK201A 15/-
- 2 2N132 PNP Epitaxial Planar Sil. 15/-
- 3 2N697 Epitaxial Planar Trans. Sil. 15/-
- 4 Germ. Power Trans. Eqt. OC16 15/-
- 1 Unijunction Trans. 2N2649 15/-
- 2 Sil. Trans. 200Mc/s 60Veb ZT83/84 15/-
- 20 NKT Trans. AF. RF. VHF. Coded + Eqt. List 10/-
- 2 2N2712 Sil. Epoxy Planar HFE225 15/-
- 8 BY100 Type Sil. Rects. 20/-
- 25 Sil. and Germ. Trans. Mixed, all marked, New 30/-

SEMICONDUCTORS FOR "P.E." 50 + 50AMP.

TYPE	EACH	TYPE	EACH
2N1613	4/6	IN914	1/-
2N3055	12/6	OA200	1/-
2N3703	3/-	BFY51	3/6
2N3704	3/6	BYZ13	4/6
2N3707	3/6	40322	14/-
2N3819	8/-	2N131W Zener	3/6

GIRO No. 388-7006

BI-PAK



KING OF THE PAKS BI-PAK GUARANTEE SATISFACTION OR MONEY BACK

BATTERY ELIMINATOR



Plug your Transistor Radio, Amplifier, Cassette, etc., into the a.c. mains through this compact eliminator. 230v 2in approx. 6V 29/8. 9V 29/8, 7.5V complete with cable and plug for Philips Cassette. **39/6** Plus 2/- P. & P. each.

CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER DEPT. No. 11
Mayes Rd.
LONDON N22 6TL



TELETON TYPE NM.33 MAGNETIC CARTRIDGE
Stereo with diamond styli. This ever popular cartridge now at economy price: Diamond Stylus, 7 mil. Frequency: 20-20kHz; Separation: 20db at 10kHz. **79/6** Plus 1/6 P. & P.


WE HOLD THE LARGEST STOCK OF RETAIL COMPONENTS IN LONDON — SEND LARGE S.A.E. FOR FREE LISTS



I.C. MODULE TYPE BP1010
3W r.m.s. power amplifier and pre-amp. Complete with data sheet. Fully guaranteed. **25/-** P. & P. 1/6 each. All Sinclair products are in stock. Please include postage with orders.

BRITISH RECORDING TAPE

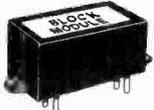of the finest quality (all guaranteed). 5in 600ft, 8/8 each, 3 for 24/-; 3in 900ft, 10/- each, 3 for 28/8. 7in 1,200ft, 11/8 each, 3 for 33/-; Please include 1/6 on each order for P. & P.



SOLID STATE BLOCK MODULES

Phono pre-amp E1311: input, 100K; gain, 28db; max. out. 3V; max. in. 50M/A; power, 9W. Tape pre-amp E1312, as above. Mic. pre-amp E1313, as above. Power amplifier E1314: input, 1,000 ohms; gain, 20db, 300M/W; power, 9V d.c. Electronic organ, tone osc. E1315: tone freq. Dual flasher E1318; flasher time, 1/4 sec; power, 6V; current, 150M/A; lamp, 6V 150M/A. We also stock the mouse code practice modules in this range. **ALL AT 25/-** Plus 2/- P. & P.



EMI SET 850

A complete speaker system **IN KIT FORM**. We supply a modern styled teak finish cabinet with black front. Overall dimensions: 14in x 9in x 9in. Made to a very high standard. A 6in EMI woofer. A 3in tweeter. A crossover network. Acoustic wadding. Output terminals, wire and fixing hardware. Specification: Max. power, 10W; frequency, 65-20kHz; imp 8-15 ohms. Kit price **9 Gns.** Plus 7/6 p. & P.

MAINS TRANSFORMER

Fused Primary 240V. Secondary 220V @ 50M/A. 6-3V @ 1A. This transformer is made to a very high standard and is a small size: 2in x 2in x 2in. **12/6** Plus 3/- P. & P.

PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel: Bass—Middle—Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 500W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) **£18.10.0.** Plus 7/6 P. & P. If you require more information please send S.A.E.

IMPORTED PANEL METERS

KA-38C 1 1/2in x 1 1/2in. 50mA, 100mA, 500mA, 1/MA, 5M/A. 8 meter 1M/A, 300V. All at **29/6** Plus 1/- P. & P.



KA-65C 3 1/2in x 3 1/2in. 300V, 8 meter 500mA, 1M/A. All at **39/6** Plus 1/6 P. & P.

EMI LOUDSPEAKER 450

10W 13in x 8in x 2in. Two 2 1/2in tweeters and crossover. All wired and ready for use. This ever-popular 450. In 3-8-15 ohm imp. **65/-** Plus 7/6 P. & P.

LOW VOLTAGE AMPLIFIER

3 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output. With high IMP input this amplifier will work as a record player, baby alarm, etc., amplifier. Few only at **35/-** plus 2/6 P. & P.



STEREO HEADSET

8 ohm impedance, complete with plug and 5ft lead. A very comfortable phone set. Listen to stereo without noise interrupting the pleasure. Wonderful value **4 9/6** Plus 3/- P. & P.



STEREO JUNCTION BOX

For stereo amplifiers without stereo jack socket. **2 5/-** Plus 1/6 P. & P.

CRESCENT CASSETTES

Top quality cassettes at unbeatable prices (complete with standard storage case): C90 7/6. C90 12/6. C120 17/6. Plus 1/- P. & P.

HIGH QUALITY IMPORTED HEADPHONES

1,000Ω per phone . . . 15/11
2,000Ω per phone . . . 17/6
Plus 2/- P. & P. per pair.

TTC
G1105



SAVE MONEY NOW!


On the famous S.D.C. DeC range of solderless breadboards

We are pleased to announce that greatly increased demand has enabled us to slash the prices of our S-DeC range. In addition we offer Practical Electronics readers a special reduction in the price of T-DeC for one month only.

S-DeC Available as single packs with accessories and control panel **NOW AT 20/-** or the DeCSTOR double pack containing 2 S-DeCs, accessories, control panel, all in a plastic storage container. **NOW ONLY 50/-**. A 4 DeC pack is available, **NOW ONLY 78/-**.

T-DeC Now available to the amateur. 208 connection points. 38 independent junctions. Accommodates I.C.s using standard carriers. Three times the capability for only twice the price! Unit pack with control panel 50/-.

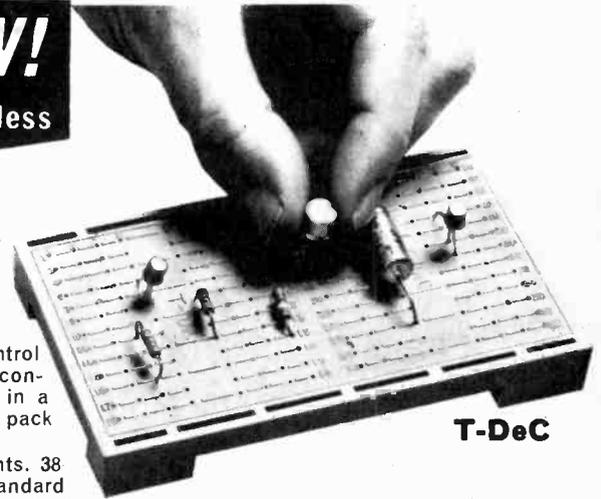μ-DeC Primarily for use with integrated circuits; further details on request.



T-DeC

SPECIAL OFFER — 7/6 OFF T-DeC
Normal recommended retail price of 50/-

Take this coupon to your local stockist who will supply one T-DeC for . . . **42/6d**


Offer closes 31st December 1970

In case of difficulty post coupon direct to:

S.D.C. ELECTRONICS (SALES) LTD.

34 Arkwright, Astmoor Industrial Estate, Runcorn, Cheshire.

Tel.: Runcorn 65041

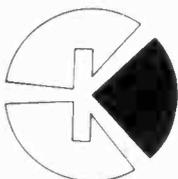

Mail Orders: DRAYTON BASSETT, TAMWORTH, STAFFS
ELECTRONIC COMPONENTS

G. F. MILWARD

Wholesale/Retail : 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

WIRE-ENDED TYPES		NOTE: IT IS ESSENTIAL THAT REFERENCE NUMBER IS QUOTED WHEN ORDERING THESE CAPACITORS												
REF. No.		REF. No.		REF. No.										
G1/1	20/450V	2/-	H1/11	8/6V	6d	G4/13	400/50V	2/-	H7/2	20/15V	REF. No.			
G1/13	40/50V	1/-	H2/1	32/150V	1/-	G4/14	500/4V	9d	H7/2A	20/6.4V	1/-	H7/10	60/15V	1/6
G2/5	10/25V	9d	H2/2	64/2.5V	9d	H5/1A	500/25V	2/-	H7/3	25/2V	9d	H7/11	64/25V	1/6
G2/6	8/12V (REV)	9d	H2/3A	24/275V	1/-	H5/6A	40/3V	6d	H7/4	25/25V	6d	H7/14	100/4V	1/6
G3/7	100/25V	2/-	H2/8	32/150V	1/-	H5/7	30/6V	6d	H7/4A	25/20V	1/6	H8/2	2/50V	1/-
G3/14	100/180V	2/-	H2/10A	2/150V	1/-	H5/11	400/6.4V	9d	H7/5	40/15V	1/6	H8/3	3/50V	1/-
G5/9	8/8/450V	3/-	H2/10A	16/32/350V	2/-	H5/12	320/10V	1/-	H7/6	50/3V	6d	H8/6	8/50V	1/6
G6/13A	40/450V	2/-	H2/11A	32/275V	1/6	H5/14	5/6V	6d	H7/6A	26/50V	1/6	H8/7	12/52V	1/6
H1/1	1/6V	6d	H3/7A	500/12V	1/6	H6/1	100/50V	1/6	H7/7	50/12V	1/6	H8/7A	15/15V	1/6
H1/3	4/4V	6d	H3/8	750/12V	1/6	H6/2	200/3V	6d	H7/7A	50/10V	1/6	H8/10	2/275V	1/-
H1/4	6/6V	6d	H3/10A	30/10V	6d	H6/7	200/16V	1/6	H7/8	50/15V	1/6	H8/11A	250/12V	1/6
H1/7	20/6V	6d	H3/12	16/50 (REV)	2/-	H6/13	500/3V	9d	H7/9	60/12V	1/6	H8/13	100/25V	2/-
H1/9	50/6V	6d	H4/1	20/4/275V	1/6	H7/1	10/12V							

CAN TYPES		REF. No.		REF. No.		REF. No.		REF. No.						
G1/1	4,000/100V	7/6	G4/1	300/700/320V	7/6	G5/4A	500/100V	3/-	G6/9	60/200/300V	5/-	H3/4	1,000/50V	6/-
G2/1	6,000/30V	7/6	G4/5A	60/350V	7/6	G5/5	400/275V	3/-	G6/11A	400/300V	3/-	H3/4A	3,000/25V	3/-
G2/5	125/200V (REV)	3/-	G4/6	60/200/275V	2/6	G5/7	100/400/300V	7/6	G6/12A	1,000/12V	3/-	H3/6	2,500/9V	2/6
G2/10	50/50V	1/-	G4/7	40/40/275V	1/6	G5/7A	45,000/12V	15/-	H5/4	325/25V	1/6	H3/6A	5,000/18V	4/-
G2/11	100/350V	2/-	G4/7A	40/40/450V	2/6	G6/1	12,000/15V	15/-	G6/14	400/275V	3/-	H3/9	100/275V	2/-
G3/2	200/200/350V	7/6	G4/11	2,000/25V	3/-	G6/2	2,500/40/60V	7/6	H1/5	2,000/18V	3/-	H3/13	16/16/375V	2/-
G3/2A	200/200/100/350V	6/-	G4/12	150/30V	1/6	G6/2A	2,500/50V	7/6	H1/6	125/200V	2/-	H4/3	500/12V	1/6
G3/4	650/300V	7/6	G4/13	100/200/16/275V	6/-	G6/3	2,000/50V	7/6	H1/12	200/275V	2/-	H4/5	32/32/350V	2/-
G3/9	100/200/250V	6/-	G5/1	8,000/70V	10/-	G6/3A	2,000/15V	3/-	H1/15	100/200/60/275V	5/-	H4/9	500/6V	2/6
G3/10	40/20/10/10/350V	3/-	G5/2	300/300/350V	4/-	G6/5	1,000/1,500/25V	7/6	H2/6	50/275V	2/-	H4/11	100/16/275V	7/6
G3/10A	200/350V	2/-	G5/2A	30,000/40V	15/-	G6/5A	1,600/80V	7/6	H2/9	16/14/450V	2/6	H6/10	250/25V	4/-
G3/13A	2,000/30V	3/-	G5/3	150/200V	15/-	G6/6	100/60V	6/-	H2/10	1,000/100V	7/6	H8/13	6,000/6V	4/-
			G5/4	39,000/10V	10/-	G6/8	200/250V	3/-	H3/2	2,500/100V	7/6			

TAG ENDS		REF. No.		REF. No.		REF. No.		REF. No.						
G1/4	4/150V	1/-	G2/4	40/300V	1/6	G4/9	8/8/350V	2/-	G6/7	100/275V	2/-	H4/2	250/25V	1/6
G1/5	8/275V	1/6	G2/13	100/50V	1/6	G4/10	350/25V	2/6	G6/12	1,000/12V	1/6	H4/7A	32/32/275V	2/6
G1/5A	32/350V	1/6	G4/3A	200/25V	1/6	G6/1A	3,000/15V	3/-	H1/9A	500/150V	2/-	H4/12	500/50V	2/6
G1/7	16/16/275V	2/-	G4/5	16/300V	1/6	G6/4	1,000/50V	6/-	H3/5	250/150V	2/-	H5/6	250/50V	2/-
G1/12	40/450V	2/-												

PRINTED CIRCUIT, CAN TYPE		REF. No.		REF. No.		REF. No.		REF. No.						
G1/6	16/32/450V	2/-	G3/12	100/200/16/16/300V	5/-	G5/14	8/8275V	1/6	H3/9	100/275V	2/-	H5/10	64/32/8/275V	2/-
G1/8A	16/250V	1/6	G3/13	64/275V	2/-	G6/4A	1,000/25V	2/6	H3/10	100/250V	1/6	H5/3	500/25V (REV)	2/6
G1/10	32/275V	1/-	G4/3	250/150V	2/-	G6/11	40/350V	1/-	H3/13A	16/16/275V	2/6	H5/8	32/32/275V	1/6
G1/14	16/275V	1/-	G4/4	50/50/200V	2/-	G6/12	250/25V	2/-	H4/3A	500/50V	1/6	H5/9	100/100/150V	2/-
G2/10	100/100/350V	3/-	G4/8	40/40/450V	2/-	H1/10A	10/10/350V	1/6	H4/4	400/6 (REV)	2/6	H5/13	32/32/8/300V	2/-
G2/12	100/150V	2/-	G5/6	60/100/275V	2/6	H1/12	200/275V	2/-	H4/6	64/275V	2/-	H5/9	50/50/350V	3/6
G2/14	20/10/10/450V	2/-	G5/8A	100/65/250V	2/6	H1/13	250/150V	2/-	H4/7	32/32/350V	2/6	H6/14	1,000/20V	2/-
G3/1	60/100/350V	3/-	G5/10	100/100/50/350V	3/-	H2/5	50/80/300V	2/6	H4/8	8/8/8/275V	2/6	H8/11	150/150V	1/6
G3/6	100/250V	2/-	G5/11	100/200/25V	2/-	H2/5	100/100/100/275V	2/6	H4/10	10/10/425V	2/6	H8/12	250/25V	2/-
G3/6A	50/50/350V	2/-	G5/12	100/20/10/350/20/50V	2/6	H2/6	50/275V	1/6	H4/13	400/250V	2/6	H8/13	3,000/6V	3/-
G3/8A	100/25V, 100/12V	2/-	G5/13	40/100/350V	2/6	H2/11	32/32/250V	1/6	H5/1	150/200V	2/-	H8/13A	100/25/200/25V	1/6
G3/11	100/350V	2/6	G5/13A	40/40/40/40/350V	2/6	H2/12	50/50/150V	1/6				H3/11	150/200V	2/-

PRINTED CIRCUIT TYPE, WIRE LEADS		REF. No.		REF. No.		REF. No.		REF. No.						
G1/9	16/275V	1/6	H3/15	350/12V	1/6	H6/10	300/9V	1/-	H7/12	65/15V	1/6	H8/4	5/15V	1/-
H2/7	10/25V	1/6	H5/1	150/30V	1/6	H6/11	300/15V	1/6	H7/15	100/16	1/6	H8/8	20/9	1/-
H2/12A	350/12V	1/6	H5/14A	1,000/10V	2/1	H6/14A	900/15V	1/6	H8/1	1/350V	2/-	H8/9	40/15	1/-
H2/15	12.5/40V	1/6	H6/5	150/25V	1/6									

SPECIAL 10/- PACKS. ORDER 10 PACKS AND WE WILL INCLUDE AN EXTRA ONE FREE !!!

RESISTORS , 1/2 watt assorted Wire-wound 1 to 3 watt 5 to 7 watt 10 watts	100 20 15 10 12	10/- 10/- 10/- 10/- 10/-	TRANSISTORS P.N.P. Untested but mainly O.K. N.P.N. Untested but mainly O.K. Light-sensitive Diodes (These produce up to 1ma from light) OC 44 Mullard 1st grade OC45 Mullard Boxed 2G378 Output, Marked 2G371 Driver, Marked ASY 22, Marked BY 27 Rectifiers IN4007 Rectifiers (1200V peak) STC 3/4 Rectifiers DIODES (0A B1 & 0A 91)	50 50 5 10 4 4 4 5 4 6 40	10/- 10/- 10/- 10/- 10/- 10/- 10/- 10/- 10/- 10/- 10/-	WIRE Solid Core, Insulated 100yds. Stranded ditto 50yds. SOLAR CELLS. Large Selenium Small (6 cells will power a Micromatic (radio) CO-AXIAL CABLE. Semi Air-spaced CRYSTAL TAPE RECORDER MIKES CRYSTAL EARPIECES 3.5mm Plug TRANSISTORISED Signal Injector TRANSISTORISED Signal Tracer TRANSISTORISED CAR REV. COUNTER KIT (Needs 1ma. meter as indicator)	10/- 10/- 10/- 2 3 10/- 10/- 10/- 10/- 10/- 10/- 10/- 10/- 10/- 10/-	SINCLAIR AMPLIFIERS AND SPEAKERS. Complete range in stock. All at 10 per cent discount on list. VEROBORD 2 1/2in. x 1in. x .15 1/3 5in. x 3 1/2in. x .15 5/6 3 1/2in. x 3 1/2in. x .1 4/9 3 1/2in. x 2 1/2in. x .15 3/3 1 7/8in. x 2 1/2in. x .15 1 1/2in. x 2 1/2in. x .1 4/7 3 1/2in. x 3 1/2in. x .15 3 1/1 1 7/8in. x 2 1/2in. x .15 1 4/8 5in. x 3 1/2in. x .1 5/6 5in. x 2 1/2in. x .15 3 1/1 3 1/2in. x 2 1/2in. x .1 4/2 Spot Face Cutter 7/6. Pin Insert Tool 9/6. Terminal Pins (1 or .15) 3/6 for 36. Special offer pack consisting of 5 2 1/2in. x 1in. boards and Spot Face Cutter... 10/- TRANSISTOR RADIOS Once again we have a supply of these excellent radios which offer superb quality sound and excellent sensitivity. They are packed in a colourful presentation box complete with battery, earpiece and carrying case. Each one is guaranteed. You would expect to pay at least £5—but our price due to a bulk purchase is only 37/6. Many of our customers have made a considerable profit by buying these radios and re-selling them to friends! RECORD PLAYER CARTRIDGES. Well below normal shop price! ACOS GP 67/2 15/- (Mono). ACOS GP 91/3 20/- (Compatible) ACOS GP 93/1 25/- (Stereo) ACOS GP 94/- 30/- (Stereo, Ceramic). ACOS GP 93/- DIAMOND 32/6. ACOS 94/1 DIAMOND 37/6. TRANSISTORISED FLUORESCENT LIGHTS. 12 volt. All with Reverse Polarity protection. 8 watt 59/6. 15 watt 79/6. 13 watt 99/6. Postage 3/- per fitting. These can be sent on approval against full payment. Thousands already sold. MULLARD POLYESTER CONDENSERS 1,000 pf., 1,200 pf., 1,800 pf., 2,200 pf., 400 volts, 3d, each. 25 per cent discount 100 any type. .15uf., .22uf., 27uf., 160 volts 6d, each. 25 per cent discount 100 any one type. RESISTORS 1/2 and 1 watt. Most values in stock. 10/- per 100 of any one value. 2/- dozen. 3d. singles. MAINS DROPPER TYPE. Hundreds on values from 7 ohm upwards. 1 watt to 50 watts. A large percentage of these are multi-tapped droppers for radio/television. Owing to the huge variety these can only be offered 'assorted'. 10/- per dozen. SILVER MICA/CERAMIC/POLYSTYRENE CONDENSERS Large range in stock. 15/- per 100 of any one value. 3/- per dozen. Singles 6d. each. RECORDING TAPE BARGAIN! The very best British Made low-noise, high-quality Tape! 5in. Standard, 7 1/6. Long-play 9 1/6. Long-play 12 1/6. 7in. Standard 12 1/6. Long-play 16 1/3. We are getting a fantastic number of repeat orders for this tape. Might we suggest that you order now whilst we still have a good stock available? £5 WORTH OF COMPONENTS FREE! !!! Thinking of learning another language? If so, apply to us for details of Linguaphone courses. We will GIVE you £5 worth of components of your selection when you purchase a language course" !!!
---	-----------------------------	--------------------------------------	---	---	--	---	--	--

MULLARD 'UNIFLEX' AMPLIFIERS
In our opinion these units are the best value for money ever offered. A complete stereo unit consisting of Control unit. Pre-amplifier, Two Main Amplifiers and Power Pack complete and ready for use—NO extra components to buy—yours for £15. (Normal retail price is £16.10s.)
GARRARD SP 25 UNITS also offered at a discount. Our price only £12.10s. Postage 9/-.

G. F. MILWARD, Drayton Bassett, Tamworth, Staffs. Postage (minimum) per order 2/-.

BRAND NEW! BANG UP-TO-DATE!
NOT JUST A RADIO—BUT TECHNOLOGICAL MAGIC!

RUSSIAN WORLD BEATER!
WE COULDN'T EVEN MAKE THEM FOR THIS FANTASTIC PRICE!

BATTERY/MAINS!

8 WAVEBAND 10 TRANSISTOR PLUS 2 DIODES PORTABLE RADIO

WORLD WIDE RECEPTION
 THOUSANDS OF TRANSMISSIONS AND STATIONS THE WORLD OVER!

BATTERY MODEL £13.19.6
 BOX POST ETC 8/6

(OR WITH MAINS/BATTERY ELIMINATOR 20/- extra)

This fantastic brand new Astrad Auriga Russian 8 waveband portable radio, designed for world wide reception will probably make your present radio seem like a "crystal set"! It's far better than any other 8 wave radio that even they have produced before! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only £13.19.6 a mere fraction of even today's Russian miracle price! In fact, we challenge you to compare the performance and value with that of 30/-gn. radios! ★ You just can't lose, we'll refund your money instantly if you are not astounded! Purer and sweeter tone than ever! Wider band spread for absolute "pin-point" station selection! Yes, the Russians have really surpassed themselves this time, proving once again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of space communications. YOU GET THIS AMAZING SET FROM US AT A PRICE THAT BEARS NO RELATION TO ITS TRUE VALUE! Yes, 8 separate wavebands, including Standard Long, Medium and Short Waves to cover the world! Unique side control waveband selection unit gives incredible ease of station tuning! Thousands of different transmissions and stations at your fingertips 24 hours a day, including ships at sea and messages from all over the world—truly nothing is secret! You must hear it to believe it! Superb, sweet tone—controlled from a whizzer to a roar that will fill a hall! Genuine push-pull output! Separate ON/OFF volume and Treble-Bass tone controls! Press-button dial illumination! Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240V a.c. mains supply. Internal ferrite rod aerial plus built-in telescopic aerial extending to full 31in length. It's also a fabulous CAR RADIO—any speed, requires no additional aerial. UNIQUE! Elegant Black & Chrome finish case. SIZE 11in 8in 3½in overall approx. Made to give years of perfect service. Complete, with WRITTEN GUARANTEE, manual with simple operating instructions and circuit diagram. ONLY £13.19.6 (mains/battery eliminator 20/- extra). POST, ETC. 8/6. Standard batteries 5/- extra. Can also be used through extension amplifier, tape-recorder, public address. Send today or call. But HURRY! It's the chance of a lifetime!

***COMPARE IT'S PERFORMANCE with 39½ GN'S RADIOS!**

Sensational News from Russia!
 For Every Lover of HI-FI!

SUPERB COMPLETE DE-LUXE STEREO RADIOGRAM System
 Comprising 4 magnificent UNITS!


GUARANTEED £140 PERFORMANCE!

LISTED IN U.K. Sept 65 AT £79—AND THAT WAS A RUSSIAN MIRACLE!

NOW FROM US! ONLY 49! 2 COMPLETE CAR ETC 2/6s

Comparable with specifications costing around £140, to be sold by others in U.K. at £79 as recently as Sept., '69. NOW—unbelievable but true—We are able to offer 300 only. BRAND SPANKING NEW with written 12 months guarantee, for only 49! gns., carriage, etc., 2 gns. You'll never appreciate the wonderful reproduction possible from your old stereo or mono records until you listen to them on this superb HI-FI Audio Unit. It's a breath-taking experience! But wait. With the 8 Waveband Radio you can get thousands of transmissions from all over the world including hfm radio, ships at sea, continental and international stations. Amazing clarity of tone and incredible station selection. Just read the magnificent specification of this compact fully transistorised, high quality sound reproduction equipment in matching unit form: Four-speed single Record Player deck, light-weight arm with "turnover" sapphire stylus and transparent deck cover, etc. (15½in 12in 6½in approx.). Two speaker Cabinets (each 18½in 9½in 8in approx.), each containing 8in high efficiency unit and 3in cone tweeter. Fully transistorised Tuner Amplifier (26 transistors, 11 diodes) (18½in 9½in 8in approx.) incorporating VHF/FM, Long, Medium and 3 Short wavebands. All instantaneous Press Button top panel controls! Push-pull output stage. Proudly controlled rotatable ferrite rod aerial, internal FM aerial, meter type tuning indicator, stereo balance control, separate variable bass and treble controls give superb balance and tone. Plus all usual extension sockets. 110, 127, 220, 240V a.c. All cabinets very strongly constructed—with beautiful high gloss walnut polyester finish. Long negotiations and a final purchase for cash made this incredible offer possible! Please don't ask questions—just hurry! Only 300 will be lucky! SPARES AND UK SERVICE CONSTANTLY AVAILABLE. Only 49! gns. plus carriage, crating, handling, etc., 2 gns., and test on 7 days approx. No more to pay! ★U.K. Trade distributors claim that British models comparing with this specification could cost you £140! We guarantee to refund your money if YOU don't agree!

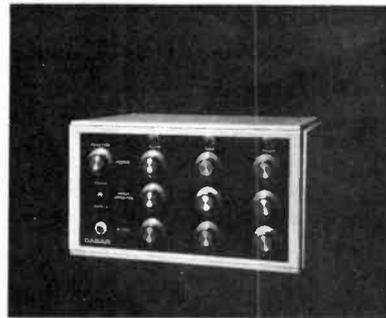SHOPUNITIES LTD. S.L. Dpt. PE/1, 164 UXBRIDGE RD., (facing Shepherd's Bush Green), London W12 8AQ. (Thurs. 1, Fri. 7). Also 37 High Holborn, London, WC1 (opp. Chancery Lane). (Wed. 1, Thurs. 7). Both stores open Mon.-Sat. from 9 a.m. until 6 p.m.



KINETIC LIGHTING EFFECTS

The DABAR range of Kinetic Lighting Effects encompass a wide range of sophisticated colour pulsing and blending units, designed for discotheques, dance halls, restaurants, shop-window displays, etc. Basically 3 facilities are available: A sound to light Psychedelic lighting unit or colour organ. This unit connects directly into an amplifier output or across loudspeakers (with negligible loading effect) and converts the audio frequency signals into a 3-colour light display; the colour depending on the frequency of the signal and the intensity of the light on the loudness of the audio source. Secondly a background control providing a variable minimum ambient lighting level if required and thirdly a colour blender providing a continuously and completely random slowly changing pattern of lights. This is fully automatic requiring no audio input and is controlled by 3 speed-control potentiometers.

Units are available providing loading of either 1kW of lighting per channel (3kW max per unit) or 3kW per channel (9kW max per unit). Latest full-wave Triac circuitry is used and radio-frequency interference filters are fitted in all units.

Case size: 13in × 7in × 9in.

Audio Activated Colour organ incorporating background controls.

1kW per channel £50

3kW per channel £88

Colour blender:


1kW per channel £40

3kW per channel £78

Audio activated colour organ with background controls and colour blender:

1kW per channel £60

3kW per channel £98

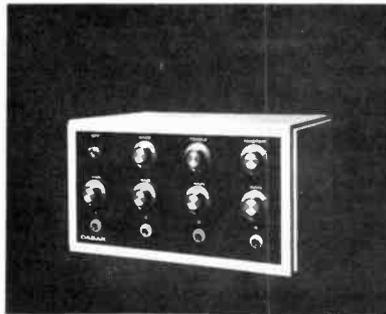

100 WATT AMPLIFIER

The latest addition to the DABAR range of equipment is a 4 channel integrated Pre-amplifier and Power amplifier, delivering a full 100W r.m.s. into a 4 ohm load. The amplifier has 4 inputs, each with their own gain control and a further master gain control, treble and bass control. A unique feature of this amplifier is in it's versatility of uses. It has been designed to accept plug-in pre-amp cards for each channel thus covering a wide range of applications. The basic unit is supplied with 4 input modules of your choice, but further modules may be purchased at moderate cost, thus enabling, with the minimum of time, effort and outlay the conversion of any one or all channels to accept an entirely different input.

Modules available include: P/U cartridges—crystal, ceramic, and magnetic (equalised R.I.A.A.); Microphones—30-60 Ω, 300-600 Ω and 50k Ω types. Guitar and two modules for high impedance outputs from tape, tuner, etc., 100mV f.e.t. and IV input.

Case size: 13in × 7in × 9in.

Price complete with 4 modules £109.0.0

Extra modules £5.0.0 each.

Please send //— in stamps for full descriptive literature.

TRADE ENQUIRIES WELCOME

Callers by appointment only. Carriage extra.

DABAR ELECTRONIC PRODUCTS

98a LICHFIELD STREET, WALSHALL, STAFFS. WS1 1UZ

Tel.: WALSHALL 34365

7,500 ITEMS

BRAND NEW

SEMICONDUCTORS & COMPONENTS

LARGEST SELECTION OF DEVICES

GUARANTEED

TRANSISTORS

Table listing various transistor models and their specifications, including part numbers like 2G301, 2G302, 2G303, etc., and their corresponding parameters.

PANEL METERS

38 Series—FACE SIZE 42 x 42mm. All prices for 1-9 pieces. 50µA, 37/6; 100µA, 35/-; 200µA, 32/6; 500µA, 27/6; 50-0-50µA, 35/-; 100-0-100µA, 32/6; 500-0-500µA, 25/-; 1mA, 25/-; 5mA, 25/-; 10mA, 25/-; 50mA, 25/-; 100mA, 25/-; 500mA, 28/-; 1A, 25/-; 5A, 25/-; 10V, 25/-; 20V, 25/-; 50V, 25/-; 300V, 25/-; 500V, 28/- ALL METERS ARE D.C.

SILICON RECTIFIERS

Table listing silicon rectifier models and their specifications, including PIV ratings and current ratings.

DIODES & RECTIFIERS

Table listing diode and rectifier models and their specifications, including part numbers like 1N461, 1N914, etc.

MAINS TRANSFORMERS

1 amp Charger, Sec. 0.3-5-9-17V ... 19/6
2 amp Charger, Sec. 0.3-5-9-17V ... 25/6
1 amp (Douglas) MT103 Sec. tappings from 6V to 50V ... 32/6
2 amp (Douglas) MT104 Sec. tappings from 6V to 50V ... 42/6

TRIACS

Table listing triac models and their specifications, including part numbers like 5C41A, 5C41B, etc.

INTEGRATED CIRCUITS
SEE OUR SEPARATE ADVERTISEMENT ON PAGE 88
SHOWING NEW I.C.'S AT NEW LOW PRICES.

SCOTCH CASSETTES C-7711. OUR PRICE 12/-
SCOTCH 3in TRIPLE PLAY 400ft.
NORMAL PRICE 24/10. OUR PRICE 18/-

PLEASE NOTE: DUE TO BULK BUYING WE CAN NOW OFFER MOST TEXAS, RCA AND NEWMARKET SEMICONDUCTORS AT INDUSTRIAL DISTRIBUTOR PRICES. NEW QUANTITY PRICE LIST NOW AVAILABLE FOR INDUSTRIAL USERS UPON REQUEST.

THYRISTORS

Table listing thyristor models and their specifications, including PIV ratings and current ratings.

CAPACITORS

A large and comprehensive range available: Electrolytic, Polystyrene, Ceramic, Polyester, Silver mica, Tantalum, Trimmers, Tuners.
Examples:
2,000µF 25V, 8/6 Most
2,500µF 50V, 13/6 Mullard
3,000µF 25V, 10/6 Electrolytics
5,000µF 50V, 19/6 in stock

VEROBOARD 0-15 0-1

Table listing Vero Board models and their specifications, including dimensions and features.

WIRE-WOUND RESISTORS

2.5 watt 5% (up to 270 ohms only), 1/6
5 watt 5% (upto 8-2kΩ only), 2/-
10 watt 5% (up to 25kΩ only), 2/6

POTENTIOMETERS

Carbon:
Log. and Lin., less switch, 3/-,
Log. and Lin., with switch, 4/6.
Type-wound pots (3WV), 5/6.
Twin Ganged Stereo Pots, Log. and Lin., 7/6.

PRESETS (CARBON)

0-1 Watt 1/-
0-2 Watt 1/3
0-3 Watt 1/6

THERMISTORS

R53 (STC) 25/6
K151 (tk) 2/6
VA3705 17/6
Mullard Thermistors also in stock. Please enquire.

HEAT SINKS

4.8 x 4 x 1in Finned or Two
TO-3 Trans., 0.6. 4.8 x 2 x 1in
Finned, for One TO-3 Trans.,
6/6. For SO-1, 6d. For TO-5,
1/- Finned. For TO-18, 1/-
Finned. For TO-18, 1/- Finned.

RESISTORS

Carbon Film
1/2 watt 5%, 3d.
1/2 watt 5%, 4d.
1/2 watt 5%, 5d.
1 watt 10%, 6d.
2 watt 10%, 1/3


Post & Packing 2/- per order. Europe 5/-, Commonwealth (Air) 13/- Minimum.
Send 6d. stamp for price list.

Send 1/- for our New Comprehensive I.C. and Semiconductor price list (24 pages)

Tel. 01-452 0161/2/3
Telex 21492
A. MARSHALL & SON
28 CRICKLEWOOD ROADWAY, LONDON, N.W.2

CALLERS WELCOME
MON-FRI 9-5.30
SAT 9-5

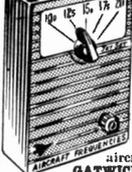LISTEN TO AIRCRAFT COMMUNICATIONS
new
V.H.F. AIRCRAFT BAND CONVERTER



ONLY 47/6

Listen in to AIRLINES, PRIVATE JET PLANES, Enavedrop on exciting cross talk between pilots, ground approach, ground control, airport tower. Hear for yourself the disciplined voices hiding tensions on talk downs. Be with them when they have to take nerve ripping decisions in emergencies—tune in to the international distress frequency. Covers aircraft frequency band including HEATHROW, GATWICK, LUTON, KINGWAY, PRESTWICK, ETC. This fantastic fully transistorised instrument can be built by anyone nine to ninety in under two hours. (Our design team built four—everyone worked first time). No soldering necessary. Fully illustrated simply worked instructions take you step-by-step. Uses standard PPS battery. Size only 4 1/2 in x 3 1/2 in. All you do is extend rod aerial, place close to any ordinary medium-wave radio (even tiny pocket radios). NO CONNECTIONS WHATSOEVER NEEDED. Use indoors or outdoors. SEND NOW. ONLY 47/6 for all parts, including case, nuts, screws, wire, etc. etc. (parts available separately).

"READ PEOPLE'S MINDS"—TEST THEIR NERVES—BEAT THEM AT CARDS—TEST THEIR MENTAL ABILITY, ETC.—ASTONISHING



57/6

ELECTRONIC BRAINBOX
Make this an exciting Christmas. If you've seen a giant computer on show at an electronics exhibition, you will have seen people of all ages queuing to put their abilities against the giant electronic brain. There is tremendous fascination that attracts ordinary people and professional engineers alike to electronic games of skill, chance and mystery. With this "Brainbox" you will be able to perform mind-boggling feats. **THE MIND READING DEVICE** will make people eager to have telepathic powers. **THE AMAZING CARD TRICK UNIT** completely mystifies and baffles from one to six people. You correctly "guess" the two cards each person has selected at random from a pack they themselves shuffled. **THE ELECTRONIC NERVES TESTER** puts your friends to a very lively test. It gives out fail and finish signals (the winner is the person with lowest number of fail signals). Can be adjusted from the weakest to strongest person. **THE ELECTRONIC MAZE** tests the mental ability of the player because it uses psychology to give an electronic twist to it. You can change the maze pathways in seconds to prevent the maze becoming too stale after lots of use. Completely safe and foolproof, uses standard battery. Size 18 in x 12 in x 6 in (Max.) You can play all these games and more besides. **WE GUARANTEE THAT ANYONE CAN EASILY ASSEMBLE THESE PROJECTS IN UNDER ONE HOUR!** No soldering, pictorial, step-by-step illustrated instructions. ONLY 57/6 plus 6/6 P. & P. for all parts including chassis, switches, stylus, signalling lights, wire, nuts, screws, etc. etc. (PARTS AVAILABLE SEPARATELY). FULL OPERATING DIRECTIONS WITH EACH OF THE PROJECTS.

P. & P. for all parts including chassis, switches, stylus, signalling lights, wire, nuts, screws, etc. etc. (PARTS AVAILABLE SEPARATELY). FULL OPERATING DIRECTIONS WITH EACH OF THE PROJECTS.

REAL WORKING ELECTRONIC ORGAN ONLY



55/-

Don't confuse with ordinary electric organs that simply blow air over mouth-organ type reeds, etc. Eight months were spent in creating and testing this superb, revolutionary electronic organ. Fully transistorised, no valves. Proper self-contained loudspeaker. Fifteen separate keys open ten full octaves—play the "Yellow Rose of Texas", "Silent Night", "Auld Lang Syne", and lots of similar tunes on this real working electronic organ. Size 13 1/2 in x 10 in x 2 1/2 in. Uses standard battery. Have the thrill and excitement of building it together with the pleasure of playing a real electronic organ. Play it anywhere. No soldering necessary. Easy as A.B.C. to make following the fully illustrated, step-by-step instructions. **BIG DEMAND ANTICIPATED FOR THIS UNIQUE INSTRUMENT** at our low price. ONLY 55/- + 4/6 P. & P. for all parts, including case, loudspeaker, transistors, condensers, resistors, knobs, transformers, volume control, wire, nuts, screws, instructions, etc. (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

FIND BURIED TREASURE!



TREASURE LOCATOR— NOW IT'S HERE AT LAST.

after experimenting for four and a half months with a multitude of different circuits and carrying out actual field tests with prototypes, our design team have come up with this real winner. This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location (no phones used). **FINDS GOLD, SILVER, LEADS, COINS, JEWELLERY, KEYS, WAE SOUVENIRS, ARCHAEOLOGICAL PIECES, METALLIC ORE, NUGGETS, ETC.** Extremely sensitive, will signal presence of certain objects buried several feet below ground! Can be built with ease in one short evening with the wonderfully clear, easy to follow, step-by-step, fully illustrated instructions. Fully transistorised—no valves. Uses standard PPS battery. No soldering necessary. Size of detector head 13 1/2 in x 10 in. Great demand expected at this remarkably low price—All parts including detector head case, nuts, screws, wire, simple instructions, etc. Send now 47/6 plus 6/6 P. & P. (Telescopic handle as illustrated 25/- extra). Parts available separately. Made up looks worth £15.

ONLY 47/6

CONCORD ELECTRONICS LTD. (P.E.14) · 8 WESTBOURNE GROVE · LONDON · W.2
(Near Bayswater Tube) Callers welcome. 9-6 including Saturdays



1.5kW FAN HEATER
Three position switching to suit changes in the weather. Switch up for full heater (2 1/2 kW), switch down for half heat (1 1/4 kW), switch central blows cold for summer cooling—adjustable thermostat acts as auto control and safety cut-out. Complete kit **£35.10.0**. Post and ins. 7/6.



HORSTMANN "TIME & SET" SWITCH
(A 30 Amp Switch). Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost on period of up to 3 hours. Equally suitable to control processing. Regular price probably around £5. Special snip price **£2.10**. Post and ins. 4/6.

SPARTAN Portable RADIO



Long and medium wave, 7 transistor, size 6 in x 4 in x 1 1/2 in. with larger than usual speaker giving very good tone. Built-in ferrite aerial and telescopic aerial for distant stations. A real bargain complete with leather case, carry sling, earplug and case. **£3.15.0**, plus 5/- post and ins.

MULTI-SPEED MOTOR

Replacement in many well known food mixers. Six speeds are available: 500, 850, and 1,100 r.p.m. from either or both of the nylon sockets (where the beaters of the food mixers normally go) and 8,000, 12,000 and 15,000 r.p.m. (ideal polishing speeds) from the main drive shaft. Very powerful and useful motor size approx. 2 in. diameter 5 in. long. Price 17/6 plus 4/6 post and ins. 12 or more post free.



MAINS OPERATED CONTACTOR

220/240V 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10A. Extremely well made by a German Electrical Company. Overall size 2 1/2 x 2 x 2 1/2 in. 19/6 each.




DOUBLE ENDED MAINS MOTOR

On feet with holes for screw-down fixing. To drive models, oven, blower heater, etc. 10/- each, plus 3/6 post and insurance, 6 or more post free.



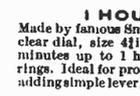0.005mFd TUNING CONDENSER

Proved design, ideal for straight or reflex circuits. 2/6 each, 24/- doz.



1 HOUR MINUTE TIMER
Made by famous Smiths company, these have a large clear dial, size 4 1/2 in. x 3 1/2 in., which can be set in minutes up to 1 hour. After preset period the bell rings. Ideal for processing, a memory jogger or, by adding simple lever, would operate micro-switch. **£2.6**.



THE FULL-FI STEREO SIX

The amplifier sensation of the year. You will be amazed at the fullness of reproduction and at the added qualities your records or tuner will reproduce. Built into metal cabinet elegantly styled and teak finished to blend with modern furnishings, this amplifier uses an integrated solid state circuit with an output power of 6 watts R.M.S. split over the two channels. The amplifier is ideal for use with normal pick-ups and tuners, it has a double wound mains transformer and ganged volume and tone controls—also switching for Mono to Stereo, tuner or pick-up. Other controls include "treble lift and cut", "balance" and separate mains on/off switch. Price is **£2.19.6** plus 7/6 post and insurance.



STANDARD WAFER SWITCHES
Standard size 1 1/2 wafers—silver-plated 5-amp contact, standard 1/2 in spindle 2 in long—with locking washer and nut. No. of Poles 2 way 3 way 4 way 5 way 6 way 8 way 9 way 10 way 12 way

1 pole	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
2 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
3 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
4 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
5 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
6 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
7 poles	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6
8 poles	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6
9 poles	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6
10 poles	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6
11 poles	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6
12 poles	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6

12 volt Car Battery Trickle Charger. Made in Japan, this is very small and neat. Regular use will keep your car battery in good trim throughout the winter. Sillily price, 25/- plus 4/6 postage and insurance.

QUICK CUPPA

Mini Immersion Heater, 350w. 200/240v. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. 24/6, post and insurance 1/6. 12v. car model also available 19/6.



PLINTH AND COVER

Suitable for most auto changers, teak base with tinted perspex cover. 85/- plus 6/6 postage.



THYRISTOR LIGHT DIMMERS

Will dim incandescent lighting up to 600 w. from full brilliance to out. Assembled and wired ready to install. 85/6.



AUTO-ELECTRIC CAR AERIAL

with dashboard control switch—fully extendable to 40 in. or fully retractable. Suitable for 12v positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. **£5.18.6** plus 5/- post and ins.



COMPUTER TAPE

2,400 ft of the best magnetic tape money can buy. Made by E.M.I., 1 in. wide almost unbreakable and on a 10 1/2 in. metal computer spool. Users have claimed successful results with video as well as sound recordings. 19/6 plus 6/6 post. Cassette to hold spool 10/- extra.



Where postage is not stated then orders over £5 are post free. Below £5 add 2/9. M.A.E. with enquiries please.

ELECTRONICS (CROYDON) LTD
Dept. PE, 266 London Road, Croydon CR0 2TH
Also 102/3 Tamworth Road, Croydon

VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94.
Set of 4 for 19/3. DAF96, DF96, DK96, DL96, 4 for 29/-

1A7GT	7/8	25U4GT11/6	DL92	5/8	EL90	5/3	PCL84	7/6	UBC41	10/6	
1H6GT	7/8	30C1	6/6	DL94	7/6	EL500	12/6	PCL85	9/-	UBF80	5/0
1N6GT	7/9	30C15	13/-	DL96	7/3	EM80	8/3	PCL86	8/3	UBF89	6/0
1R5	5/9	30C17	16/-	DY86	5/9	EM81	8/3	PCL88	14/6	UCC84	7/-
186	4/3	30C18	13/6	DY87	6/9	EM84	8/9	PCL80015/6	UCC85	7/3	
1R4	3/-	30P2	15/6	EABC80	6/6	EM87	7/6	PEN44	8/6	UCF80	7/3
384	6/9	30FL1	12/9	EAF42	10/-	EM61	7/3	PEN6C14	UCB42	12/6	
3V4	7/8	30FL212/14/6	EB91	2/3	EY86	6/6	PFL20011/9	UCH81	6/6		
5Y3GT	6/-	30FL14	14/-	EBC33	8/-	EZ40	8/9	PL36	9/9	UCL82	7/-
5Z4G	7/6	30L1	6/6	EBC41	10/6	EZ41	8/9	PL81	9/3	UCL83	11/-
6/30L2	11/9	30L15	13/-	EBC90	4/6	EZ80	4/6	PL81A	10/3	UF41	10/6
6AL5	2/3	30L17	14/9	EBF80	6/9	EZ81	4/9	PL82	6/-	UF85	6/9
6AM6	2/9	30P4	13/-	EBF89	6/3	GZ32	8/9	PL83	6/6	UF89	6/9
6AQ5	6/3	30P12	13/9	ECC81	3/9	GZ34	9/9	PL84	6/6	UL41	12/-
6AT6	4/6	30P19	13/-	ECC82	4/9	KT41	15/6	PL600	13/-	UL42	20/-
6BA6	4/6	30PL1	12/9	ECC83	7/-	KT61	9/9	PL604	13/6	UL84	7/-
6BE6	4/9	30PL13	14/6	ECC85	5/9	KT66	16/9	PL608	23/6	UM80	5/-
6BJ6	8/6	30PL14	14/-	ECC80412/-	LN329	14/6	PM84	7/6	UM84	4/6	
6C5G	4/9	35L6GT	2/9	EFC80	6/-	N78	17/6	PX25	23/6	UY41	7/6
6CD6G	22/-	35W4	4/6	EFC82	6/-	P61	10/-	PY32	11/-	UY85	5/9
6F14	9/-	35Z4GT	5/-	ECH35	6/-	PAC85	7/-	PY33	11/-	VP48	16/6
6E22	13/9	150B2	13/6	ECH42	12/9	PC86	10/3	PY81	5/3	W119	7/-
6F25	12/6	807	9/-	ECH81	5/9	PC88	10/3	PY82	5/8	Z77	4/6
6R7G	2/6	6063	12/6	ECH83	8/3	PC96	8/6	PY83	5/9	AC107	3/6
6RE6	3/6	AC/VP215/8	ECH84	7/6	PC97	8/-	PY88	6/9	AC127	2/6	
6Y6G	3/6	AZ31	9/6	ECL80	7/-	PC900	7/6	PY800	7/6	AD140	7/6
6V6GT	6/6	B349	13/6	ECL82	6/9	PCC84	6/6	PY801	7/6	AF116	4/-
6X4	4/9	BT29	12/6	ECL86	6/-	PCC85	6/-	R19	6/8	AF116	4/-
6X6GT	5/9	CCH35	13/6	ECP3A	6/6	PCC88	9/-	R20	12/-	AF117	4/-
10F18	7/-	CY31	6/9	EF41	11/9	PCC89	9/9	TH21C	17/6	AF118	9/9
10P13	12/-	DAC32	7/3	EF80	4/6	PCC80613/-	U26	12/-	AF127	3/6	
12AH8	46/-	DAF91	4/3	EF85	6/3	PCF80	6/6	U47	13/6	OC26	5/-
12AT7	3/9	DAF96	7/3	EF86	6/3	PCF82	6/6	U49	12/-	OC44	2/6
12AUG	4/9	DF91	7/9	EF89	5/3	PCF86	9/8	U78	4/9	OC45	2/6
12AU7	4/9	DF91	7/9	EF91	2/9	PCF80013/6	U191	12/6	OC71	2/6	
12AX7	4/9	DF96	7/3	EF183	5/9	PCF801	6/9	U193	8/6	OC72	2/6
12K8GT	7/3	DH77	4/6	EF184	6/6	PCF802	9/-	U251	14/6	OC75	2/6
19B6G617/6	DK32	7/8	EH190	8/6	PCF80513/6	U301	10/6	OC81	2/6		
20F2	13/6	DK91	5/9	EL33	9/9	PCF80611/3	U329	14/6	OC819	2/6	
20P3	11/8	DK92	8/6	EL34	9/6	PCF80814/-	U801	19/6	OC82	2/6	
20P4	18/6	DK96	7/3	EL41	11/-	PCL82	7/3	UABC80	6/6	OC82D	2/6
25L6GT	6/-	DL35	5/-	EL84	4/9	PCL83	12/-	UAF42	10/3	OC170	4/6

READERS RADIO (P.E.)

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.

If you can put a 'Yes' in every box, you might just make a RADIO TECHNICIAN in Air Traffic Control

An all-consuming interest in telecommunications

At least one year's practical experience in telecommunications, preferably with 'ONC' or 'C and G' technical qualifications

A highly developed sense of responsibility

Willingness to undergo a rigorous programme of training

Aged 19 or over

To the right man, the National Air Traffic Control Service offers the prospect of an interesting and steadily developing career as a Radio Technician in air traffic control.

The work involves the installation and maintenance of some of the very latest electronic equipment at civil airports, radar stations and other specialist establishments all over the country. Important today, the job will become increasingly vital as Britain's air traffic continues to grow, and prospects for promotion are excellent. Starting salary varies from £1044 (at 19) to £1373 (at 25 or over). Scale maximum £1590 (higher rates at Heathrow). The annual leave allowance is good, and there is a non-contributory pension for established staff.

If you feel you can meet the demands of this rather special job—and you have a strong determination to succeed—you are invited to complete the coupon below.

Send this coupon for full details and application form
To: A J Edwards, C Eng, MIEE, The Adelphi,
Room 705, John Adam Street, London WC2N 6BQ,
marking your envelope 'Recruitment'.

Name

Address

PET/G3

Not applicable to residents outside the United Kingdom

NATCS

National Air Traffic Control Service

You should read the Goodmans High Fidelity Manuals

Goodmans High Fidelity Manuals are of vital interest to you, and contain constructive and informative articles on all aspects of High Fidelity sound.

One manual contains specifications, descriptions and full colour illustrations of the entire current range of loudspeaker cabinets, systems, amplifiers and F.M. tuners. The construction manual contains the information needed by those enthusiasts who prefer to make their own High Fidelity or musical instrument loudspeaker systems.

These manuals are available free from

Goodmans Loudspeakers Limited

Axiom Works Lancelot Road Wembley Middx. Tel: 01-902 1200

Please send me:
Full colour manual (Tick as required)
Construction manual

Name

Address

P.E.1

Practical Electronics Classified Advertisements

RATES: 1/6 per word (minimum 12 words). Box No. 1/6 extra. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London, E.C.4

MISCELLANEOUS

We stock all those components and materials required by the home Hi-Fi constructor, including speaker grille fabrics, BAF wadding, Peerless speaker kits, Helme Cabinet Kits, cross-over networks, inductors, etc. Special offers also available. Send 5 x 5d. stamps NOW for your copy of our newly illustrated catalogue (catalogue cost refunded against purchases over 10s.). No callers please, mail-order ONLY.

AUDIOSCAN Dept. P.E.1
4, PRINCES SQUARE
HARROGATE, YORKS.

PSYCHEDELIC LUMINOPHONICS

Or is this just another way of referring to FANTASY? Either way, our Projects 24 and 1014 probably come within this category—THINK OF THE FUN YOU WOULD HAVE WITH SOMETHING LIKE THIS AT A PARTY! There are MANY OTHER UNUSUAL PROJECTS TOO—how about an ELECTRONIC STETHOSCOPE for LISTENING THROUGH WALLS, etc., or a TRANSMITTER/RECEIVER that doesn't use RF, SO LICENCE WORRIES ARE OVER! Then there's another project for a "LEARNING" MACHINE—imagine one of these in YOUR BACKROOM! YOUR FRIENDS WOULD BE AMAZED! If REALLY UNUSUAL projects interest you, then WE'VE GOT WHAT YOU WANT. In a few days from now YOU COULD BE IN THE "SCIENCE-FICTION" WORLD OF "BOFFIN"!

DON'T PUT IT OFF! SEND 3/- for your list—NOW **BOFFIN PROJECTS**
4 CUNLIFFE RD., STONELEIGH, EWELL, SURREY
Designs by GERRY BROWN and JOHN SALMON
and presented on TV

BIG BARGAIN PARCEL 13/- POST PAID

Containing multi-contact relay, transistors, resistors (some high stab), rectifiers, diodes, capacitors, pots, knobs, etc.

4 WATT GRAM AMPS.

Volume and tone controls, mains operation, 3Ω output, new and boxed **72/6 POST PAID**

SALOP ELECTRONICS Callers welcome
23 Wyle Cop
Shrewsbury, Shropshire S.A.E. for lists

GARRARD RECORD PLAYER UNITS
The Garrard 2025TC with (GCS36) Cartridge for Stereo or Mono Records, complete with Plinth and Top Cover.



only £15 plus 10 6 post and packing
Also available: Garrard SP25 Mk. IIC with GP93/1 Cartridge, £22. Garrard 3000 with GP104 Cartridge, £18. Also manufacturers of HI-FI amplifiers and car radios.

SUNDERLAND ELECTRICS LTD.
48 Princess Street, Manchester M1 6HR
Tel. 061-236 3652

CIRCUIT BOARD ETCHING KITS, full instructions, 19/6d. C.W.O. ARVIN SERVICE COMPANY, 12 Cambridge Road, St. Albans, Herts.

PARAPHYSICAL LABORATORY, Downton, Wilts. Fascinating international magazines. S.A.E. for list. Parcel 20s.

NEW LOW PRICE

Brand New and Individually Tested Transformers supplied unmarked, but packed separately for identification and guaranteed to be within their correct specification or money refunded. All at 1/9 each or

Any 16 transistors for only £1.

ACY22	BSY27	OC201	2N3702
BC108	OC45	OC202	2N3703
BC109	OC71	ZTX300	2N3705
BFY51	OC72	2NX300	2N3706
BFY52	OC200	2N2926	2N3708

ANTEX SOLDER IRON

A lightweight iron with a 15 watt nickel plated bit. Designed to enable you to weld reliable joints accurately. Model CN240 volts. Special low price. Act now. Only 29/11. **MONEY BACK GUARANTEE. P. & P. 1/-**

J. M. KING (H)

17 Buckridge, Portpool Lane, London, E.C.1

PSYCHEDELIC LIGHTING UNIT. This sound modulated lighting control unit can add a new dimension to the sort of music you prefer. It adds feeling to mood music and power to beat music. Easy to construct display units that can be built into an old TV case or hi fi console, display set-ups for mobile discotheques and many more brand new designs are described in the literature given free with each unit. Now that the festive season is coming it will be ideal for "freak-out parties" and connected to Christmas tree fairy lights will really make things swing. No connections need be made to loudspeakers or amplifiers; this unit has its own **Built-in Microphone and Amplifier** and only needs plugging into the mains. It can be loaded with up to 1,500 watts of lamps and sensitivity is fully variable. Case size is only 6in x 4in x 3in. It comes to you ready built and tested for the amazingly low price of **12/6s. P. & P. 4/-**. **Money back if not delighted. Don't delay.** Send for yours now to **REID ELECTRONICS**, 30 Second Avenue, Heaton, Newcastle-upon-Tyne, NE6 5XS.

HOLIDAY FOR BOYS. 14/16 years August 1971, specialising in engineering, electronics, photography. Tuition and practical work including karting. 11 days—**£15**. Write for free brochure: **INTER-SCHOOL CHRISTIAN FELLOWSHIP**, 47 Marylebone Lane, London, W1M 8AX.

MUSICAL MIRACLES

WAA-WAA Pedal. Complete kit of all parts, robust cabinet, mechanism and instructions. Huge sales, well proven design. Only 49/- complete. Or built and tested **£4.15s. post free.** Rhythm Box. Build your own from our pre-built electronic circuit modules, e.g. box giving waltz, foxtrot, etc., costs under £17. Organ Percussion units £14. Bass pedal and other fascinating effects, fuzz, tremolo, etc. Send s.a.e. for list: **D.E.W. LTD.** 254 Ringwood Road, Ferndown, Dorset

NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get all the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for HOUSE-TO-HOUSE USE, SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND 95/- NOW

TO: **'BOFFIN PROJECTS'**
DEPT. K210
4 CUNLIFFE ROAD
STONELEIGH, EWELL, SURREY

ENAMELLED COPPER WIRE

S.W.G.	Per 1/2 lb reel	Per 1 lb reel
18-22	11/3	16/6
23-30	11/9	17/6
31-35	12/3	18/6
36-40	15/-	24/-
41-44	17/9	29/6

Orders despatched by return of post. Please add 1/- per item P. & P. Supplied by: **BANNER TRANSFORMERS**, Brooks Street, Higher Hillgate, Stockport, Cheshire. **TRADE ENQUIRIES INVITED.**

CLEARING LABORATORY, scopes, V.T.V.M's, V.O.M's, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, M/C relays, components, etc. Lower Beeding 236.

BUILD IT in a DEWBOX quality cabinet 2in x 2 1/2in x any length. **DEW LTD.**, Ringwood Road, Ferndown, Dorset. S.A.E. for leaflet. Write now—right now.

SCRAP VALVES WANTED. Type TY5-500, TY6-800, TY6-1250A, TY7-6000A, TY8-3000, FSA1500, 16P13, BW1169, also similar types. **ELECTRONIC HEAT CO.**, 352 Lower Addiscombe Road, Croydon. Tel. 01-654 7172.



The **Nite-Lite** dimmerswitch will dim up to 400 watts of incandescent lighting from zero to full brilliance. This unit simply replaces the normal light switch, and is supplied with MK mounting frame for use where more depth is required. Price built and tested 63/- complete kit 35/-
All orders CWO + 1/6 p & p
Trade enquiries welcome
DIATHANE LTD.
111 Sheffield Road
Wyomondham, NORFOLK

PRINTED CIRCUIT PROBLEMS?

Prototype circuits produced from your artwork: 2/- per sq. in. + 2/6 p & p.
Small to medium batch production at reasonable rates!
Complete design and manufacture from circuit diagrams!
Fairchild µI 914 555 5! X STOCK 8/
Quadrac 400v 4A (as used in our lamp dimmer) 29/6
Untested SCR's 300V 1A T05 case 2/- SAE for full list

PRINTED CIRCUITS. Send circuit and board dimensions for quote. Trade inquiries welcome. **JON TECHNICAL SERVICES**, c/o Winchells, Ashford Road, Ashford, Middlesex.

FOR SALE

SEEN MY CAT? 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

MORSE MADE EASY !!

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month (normal progress to be expected). Using scientifically prepared 3-speed records you automatically learn to recognise the code BYEHEM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.
For details and course C.O.D. ring S.T.D. 01-660 2896 or send 8d. stamp for explanatory booklet to:
G3H9C (Box 19), 45 GREEN LANE, PURLEY SURREY

NEW CATALOGUE No. 18, containing credit vouchers value 10/-, now available. Manufacturers' new and surplus electronic and mechanical components, price 4/6, post free. **ARTHUR SALLIS RADIO CONTROL LTD.**, 28 Gardner Street, Brighton, Sussex.

AVO 7 METER, electronic tools, components books, and copies of P.E. for sale. **J. VERNON**, 8 Southfields Avenue, Oadby, Leicester.

EDUCATIONAL

TELEVISION



This private College provides efficient theoretical and practical training in Radio and TV Servicing. One-year day courses, commencing in Sept., January and April, are available for beginners, and shortened courses for men who have had previous training. Write for free prospectus to:—
London Electronics College, Dept. LX/3. 20 Penywern Road, Earls Court, London, S.W.5 Tel. 01-373 8721

A.M.S.E. (Elec.), City & Guilds, R.T.E.B. Cert., Radio Amateurs' Cert., etc., on "Satisfaction or Refund" terms. Wide range of courses in Elec. Engineering, Design, Installation, Repairs, Refrigeration, Electronics, Radio and TV., etc. Send for full details and illustrated book — FREE. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, Dept. 124K Aldermaston Court, Reading, RG7 4PF.

COLOUR TV SERVICING

Be ready for the coming Colour TV boom. Learn the techniques of servicing colour TV sets through new home-study courses specially prepared for the practical TV engineer technician, and approved by leading manufacturer. Full details from ICS (D.561), Intertext House, London, S.W.8, or phone 01-720 1983.

HUNDREDS OF TOP PAID JOBS in engineering await qualified men. Get a certificate through B.I.E.T. Home Study—Mech., Elec., Auto., Radio, TV, Draughts., Electronics, Computers, Building, etc. Send for helpful FREE book, B.I.E.T., Department 125K, Aldermaston Court, Reading, RG7 4PF.

GET INTO ELECTRONICS—big opportunities for trained men. Learn the practical way with low-cost Postal Training, complete with equipment. R.T.E.B., City & Guilds, Radio, TV, Telecoms, etc. For free informative Guide, write CHAMBERS COLLEGE (Dept. 856K), Aldermaston Court, Reading, RG7 4PF.

ELECTRICAL

**240 VOLT
ELECTRICITY
ANYWHERE**



BEST EVER 200/240 VOLT "MAINS" SUPPLY FROM 12 VOLT CAR BATTERY
Exclusive World Scoop Purchase. The fabulous Mk.12D American Heavy Duty Dynamotor Unit with a Massive 220 watt output and giving the most Brilliant 200/240 volt performance of all time. Marvellous for Television, Drills, Power Tools, Mains Lighting, AC Fluorescent Lighting and all 200/240 volt Universal AC/DC mains equipment. Made at tremendous cost for U.S.A. Govt. by Delco-Remy. This magnificent machine is unobtainable elsewhere. Brand New and Fully Tested. Only £4.19.6 + 10/6 postage. C.O.D. with pleasure, refund guarantee. Please send S.A.E. for illustrated details.

Dept. PE, STANFORD ELECTRONICS
Rear Derby Road, North Promenade
Blackpool, Lancashire

SERVICE SHEETS

SERVICE SHEETS. Radio, TV, etc., 8,000 models. List 2/-. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

RADIO TELEVISION, over 8,000 Models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London, W.6 (01-743 8441).

SERVICE SHEETS (1925-1970) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 1/-. Over 8,000 models available. Catalogue 2/6. Please send S.A.E. with all orders/enquiries. HAMILTON RADIO, 54 London Road, Bexhill, Sussex.

WANTED

CASH PAID for New Valves. Payment by return. WILLOW VALE ELECTRONICS, 4 The Broadway, Hanwell, London, W.7. 01-667 5400/2971.

HIGHEST CASH PRICES for good quality Tape Recorders. 9.30 to 5.00. Immediate quotations. Tel. 01-472 2185.

WE BUY NEW VALVES. Cash sent by return. A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

TOP PRICES PAID

for new valves and components

Popular T.V. and Radio types

KENSINGTON SUPPLIES

(B) 367 Kensington Street
Bradford 8, Yorks.

RECEIVERS AND COMPONENTS

PRINTED CIRCUIT BOARDS for P.E. PROJECTS
All boards drilled and roller tinned complete with layout drawing.

EXAMPLES
Marine Tachometer (May 1970) 5/- ea. Musical Stave (May 1970) 8/- ea.
Waa-Waa pedal Vol. 4 No. 7 2/9 ea. Audio Sig. Gen. (Sine and Square on one board) Vol. 5 No. 10 8/6 ea.
S.A.E. for List. Now available from:- HENRY'S RADIO LTD., Edgware Road, London, W.2
P.H. ELECTRONICS, Industrial Estate, Sandwich, Kent. Tel. 2517

DRY REED INSERTS



Overall length 1.85" (Body length 1.1"). Diameter 0.14" to switch up to 500 mA at up to 250V D.C. Gold clad contacts. 12/6d. per doz.; 75/- per 100; £27.10.0 per 1,000; £250 per 10,000. All carriage paid.

G.W.M. RADIO LTD.
40/42 Portland Road, Worthing, Sussex 0903 34897

NEW MODEL V.H.F. KIT MK2

Our latest Kit, improved design and performance plus extra Amplifier Stage, receives Aircraft, Amateurs, Mobile, Radio 2, 3, 4, etc.

This novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 Volt battery, complete with easy to follow instructions and built in Jack Socket for use with Earphones or Amplifier.

Only 68/- P. & P. Free U.K. only

Postal Orders, Cheques to:

Dept. P.E.
Galleon Trading Co., 25 Avelon Road,
Romford, Essex

MULLARD CR25 RESISTORS. 0.4W 5%
HS 2.5 x 7mm 2d. each. P. & P. 1/-.
SPRING ELECTRONICS LTD., 25 Cranley Gardens,
Muswell Hill, N.10.

SITUATIONS VACANT



Established 1891

TECHNICAL TRAINING IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

First-class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field.

ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Colour TV Servicing, also Electronics, Computers, etc.

Expert coaching for:

- C. & G. TELECOMMUNICATION TECHNICIANS' CERTIFICATES.
- C. & G. ELECTRONIC SERVICING.
- R.T.E.B. RADIO AND TV SERVICING CERTIFICATE.
- RADIO AMATEURS' EXAMINATION.
- RADIO OPERATOR CERTIFICATES.

Examination Students coached until successful.

NEW SELF-BUILD RADIO AND ELECTRONIC COURSES

Build your own 5-valve receiver, transistor portable, signal generator and multi-meter. All under expert guidance.

POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF THE ASSOCIATION OF BRITISH CORRESPONDENCE COLLEGES

INTERNATIONAL CORRESPONDENCE SCHOOLS

A WHOLE WORLD
OF KNOWLEDGE
AWAITS YOU!

International Correspondence Schools
(Dept. 152), Intertext House, Stewarts Road,
London, S.W.8

NAME.....
Block Capitals Please

ADDRESS.....

AGE..... OCCUPATION..... 1/71

R & R RADIO

51 Burnley Road, Rawtenstall
Rossendale, Lancs

Tel.: Rossendale 3152

VALVES BOXED, TESTED & GUARANTEED

EBF80	3/-	PCC84	3/-	PY81	3/6
EBF89	3/6	PCF80	3/-	PY82	3/6
ECC82	3/-	PCF82	3/6	PY800	3/-
ECL80	3/-	PCL82	4/-	PY801	3/6
EF80	1/6	PCL83	4/-	UI91	4/6
EF85	3/-	PL36	5/-	30F5	2/6
EY86	4/-	PL81	4/-	30P12	4/6
EZ40	4/6	PL83	4/-	30C15	5/6
EBC41	4/6	PY33	5/-	50CD6G	7/6

POST, ONE VALVE 9d. TWO TO SIX 6d.
OVER SIX POST PAID.

A CORNUCOPIA OF COMPONENTS! Scarce valves, selected TV components, speakers and cabinets. Computer panels—long leads, NOT printed circuits. Transistors, resistors—new and recovered. State your requirements. S.A.E. for details MAIL-MART, 6 Eastbourne Road, Pevensey Bay, Sussex.

SUB-MINIATURE RESISTORS SMALLER THAN A MATCH HEAD!

Microhm 1/4 watt. 5 per cent. Values from 51K to 100K at 10d. each. Microhm Metal Glaze Resistors for the ultimate in D.I.Y. miniaturisation. Integrated Circuits complete with Data:

SN7274N Type 741 Op. Amplifier	.. 22/-
N5709A Type 709 Op. Amplifier	.. 10/-
PA230 Audio Preamplifier	.. 18/6
PA234 1W Audio Amplifier	.. 17/6
PA237 2W Audio Amplifier	.. 21/6
SL402A 2W Audio Amplifier	.. 35/-
D40C1 4W Darlingtion Amplifier	.. 18/6
MEL 11 Photo Darlingtion Amplifier	.. 9/6
Connectors for D.I.L. i.c.'s	.. 6/-

Transistors			
2N5172	1/9	BFX86	.. 6/-
ME0412	3/6	BD124	.. 12/-
2N4039	3/6	2N3055	.. 14/-
Silicon Diode 1N914 1/-
RCA 40583 Trigger Diode 5/8
Silicon Rectifiers: 1A 1N4000 Series			
50V 1/8	200V 1/8	600V 2/4	
100V 1/8	400V 2/4	800V 2/10	
	1000V 3/4		
1.5A PL4000 Series			
	200V 2/8	400V 2/8	
Bridge Rectifiers			
1A 50V 7/6.	1A 200V 8/-.	2A 400V 12/6.	

JEF ELECTRONICS
(P.E.I.), York House, 12 York Drive
Grappenhall, Warrington, Lancs.
Mail Order Only. C.W.O. P. & P. 1/- per order.
Overseas 7/6. Money back if not satisfied.

CAPACITORS. Dubilier, 0.1μF 500V, 6/- doz., 42/- 100. Hunts, 0.04μF 500V, 3/- doz., \$1 per 100; 0.001μF and 0.005μF 350V, 3/- doz., \$1 per 100. Skeleton Presets, 2kΩ, 1/3. Co-ax Sockets on isolation panel, 1/3, 12/- doz. Jack Plugs, Standard, 1/9; 3.5mm, 1/3; 400-200-50-16μF 300V, 6/-, \$3 per doz.; Recording Tape, 5in LP, 9/-, 5 1/2in LP, 12/-. Post and packing on all orders 2/-. Send S.A.E. for list. M. DZIUBAS, 158 Bradshawgate, Bolton, Lancs.

EX COMPUTER PRINTED CIRCUIT PANELS 2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 10/- P. & P. 1/6. With a guaranteed minimum of 35 transistors. Data on transistors included.

SPECIAL BARGAIN PACK. 25 boards for \$1, P. & P. 3/6. With a guaranteed minimum of 85 transistors. Data on transistors included.

PANELS with 2 power transistors similar to OC28 on each board—components 2 boards (4 OC28) 10/-, P. & P. 1/6.

9 OA5, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long lead on panels 13in x 4in. 4 for 20/-, P. & P. 5/-.

LARGE CAPACITY ELECTROLYTICS
10,000MFD 30V } 7/6 each. P. & P. 1/6.
16,000MFD 12V }
or \$3.10.0 per doz. Carr. 10/-.

250 MIXED RESISTORS 12/6
1 1/2 & 1 watt.

150 MIXED HI STABS 12/6
1, 1/2 & 1 watt 5% & better.

EXTRACTOR/BLOWER FANS (PAPST)
100 CFM 2,800 RPM 4 1/2in x 4 1/2in x 2in. Ideal for kitchen extraction, instrument cooling, etc. etc. 50/- each. P. & P. 5/- 240V a.c. 50.

DIODES EX EGYPT. SILICON
1 Amp 1,000 PIV 4 for 10/-
20 Amp 150 PIV 4 for \$1.
P. & P. 1/-.

BARGAIN RELAY OFFER
Single pole change over silver contacts 25V to 50V. 2.5kΩ coil. 8 for 10/-, P. & P. 1/-.

KEYTRONICS mail order only
52 EARLS COURT ROAD
LONDON, W.8 01-478 8499

BRAND NEW ELECTROLYTICS 15/16V
0.5, 1, 2, 5, 10, 20, 30, 40, 50, 100mF, 9d. E12 series 5% resistors, Carbon Film 1/4W 1Ω to 1MΩ, 1.5d. Wirewound 5W 15Ω to 15KΩ, 10d. Postage 1/-. THE C.R. SUPPLY CO., 127, Chesterfield Rd., Sheffield, S8 ORN.

RAZOR-SHARP I.F. SELECTIVITY with Brush Cleveite ceramic i.f. resonators. Set of 4 TF04-442, 455kHz, with circuits, 30/-, U.K. post paid. List 6d. AMATRONIX LTD., 396 Selsdon Road, S. Croydon, Surrey CR2 0DE.

COMPUTER PANELS—5-BC108, Diodes, 4—10/-. American, Total Transistors, minimum 30. Details, types, first grade components, 3—10/6, post 1/6. Assorted Components, 7b, 20/- C.P. J.W.B. RADIO, 75 Hayfield Road, Salford 6, Lancs.

PRINTED CIRCUITS. Capacity now available. Send artwork for quote. S.A.E. Sample 1 off. Artwork, reduction, negative, 4d. per sq in. 1/2in Fibreglass, 1/6 per sq in. including tinning. Drilling extra. FREEMANTLE, 18 Pennine Road, Millbrook, Southampton.

OFFER. Copper laminated 1/2in fibreglass. Board single-sided 4d. per sq in. Double-sided 5d. per sq in. Any size cut. Minimum order 10/- P. & P. plus 10%. FREEMANTLE, 18 Pennine Road, Millbrook, Southampton.

LADDERS

VARNISHED TIMBER from manufacturer; Lowest prices anywhere: 15ft. ext., \$5.10. 17ft. ext., \$5.15; 20ft. ext., \$6.5; 21ft. ext., \$7; 24ft. ext., \$8.2; 29ft. ext., \$9.5; 31ft. ext., \$11.2.6; 36ft. triple ext., \$14.10. Carr. 13/6. Free Lists Also aluminium ext. and loft ladders. Callers welcome. Dept. PEE, HOME SALES, Baldwin, Road, Stourport, Worcs. Tel. Stourport 2574.

AUDIO EFFECTS

5 SHAW LANE, HALIFAX, YORKS.

Buy with confidence and obtain the right results. Refunds without question if any of our products fail to give 100% satisfaction.

AMATEUR BANDS ALL TRANSISTOR SUPERHET RECEIVER KIT. No fuses, no drilling. Just fit the components on our printed circuit. Slow Motion tuning. Simple IF alignment. Perspex front panel. Push pull AF amp drives your 8—15 ohm speaker. Amp can be used separately. Designed to accept a BFO signal. Uses Demco plug in coils 2T. 0.5 to 1.54 Mhz 3T. 1.67 to 6.3 Mhz 4T. 5.0 to 15 Mhz 5T. 10.5 to 31.5 Mhz Range 3T normally supplied with kit. Uses 9 Volt battery. Easy step by step instructions. Complete Kit. \$8.19.8 plus 5/6 P.P. & Ins. Extra ranges 12/- per range.

POWER CONTROLLER. Power at your finger tips. Not merely half wave control but full wave. A single variable control gives zero to full power. Uses latest 15 amp 3kV triac and special triggering device. Ideal for all types of lighting, fires, motors, drills, etc. Complete with box, power socket, cables, etc. In kit form with easy to follow instructions \$6.9.8. Ready built \$9.4.8 plus 5/6 P.P. & Ins.

REVERBERATION AMPLIFIER. Self contained transistorised, battery operated. An entirely different approach to sound reproduction. Normally, sound reproduction from a single source, has a flat one dimensional effect. With this unit, proper sound delay through reverberation, tones, are created with a truly third dimension for concert hall originality. Two controls adjust volume and reverberation. Simply plug microphone, guitar, etc. in, and the output into your amplifier. Supplied in a beautiful walnut cabinet 7 1/2in x 3in x 4 1/2in. \$10.4.0. P.P. & Ins. 6/-.

VOX SWITCH. This sound operated switch is ideal for mobile TX work, tape recorder switching, etc. You speak, it switches. High and medium imp. inputs. AF take off point. Drives your 12 volt relay. In kit form with full instructions 4/8.6. Ready built, tested and guaranteed. 6/9.6 post paid.

METRONOME UNIT. Variable beat. Listen while you play and keep in time. Easily built, pocket size with personal mini earphone. In kit form 27/6, post paid. Ready built in an attractive polythene case, 37/6 post paid.

MORE OSCILLATOR. PC board, transistors, high stab. components, battery carrier, ear piece. Adjustable tone. Just attach your key. Drives phones or speaker. In kit form 17/6 post paid. Ready built in similar case as above 27/6 post paid.


STRAIGHT FROM THE PRESS. Latest Mullard manual: Audio Amp, FM tuner, Stereo decoder. Receiver circuits, Hi Fi, Tape, etc., etc. \$2/6 post paid.

TEXAS TRANSISTORS. Complementary symmetry. Driver, NPN, PNP output. The set of three ONLY 6/6 post paid.

The most accurate
pocket size
CALCULATOR
in the world

The 66 inch OTIS KING scales give you extra accuracy. Write today for free booklet, or send 85/- for this invaluable spiral slide rule on approval with money back guarantee if not satisfied.

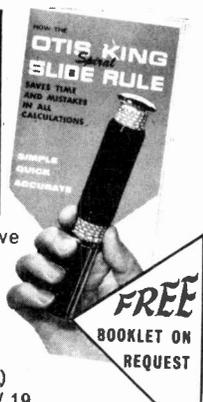CARBIC LTD. (Dept. PE32)
54 Dundonald Road, London, S.W.19




**PARKERS SHEET
METAL FOLDING
MACHINES
HEAVY VICE
MODELS**

With Bevelled Former Bars

Carr. free
No. 1. Capacity 18 gauge mild steel x 36in. wide £15.0.0
No. 2. Capacity 18 gauge mild steel x 24in. wide £10.0.0
No. 3. Capacity 16 gauge mild steel x 18in. wide £10.0.0
Also new bench models. Capacities 48in. x 18 gauge £40. 36in. x 18 gauge £30.0.0. 24in. x 16 gauge £29.0.0. Carriage free.

End folding attachments for radio chassis. Tray and Box making for 36in. model, 5/6 per ft. Other models 3/6. The two smaller models will form flanges. As supplied to Government Departments, Universities, Hospitals. One year's guarantee. Money refunded if not satisfied. Send for details.

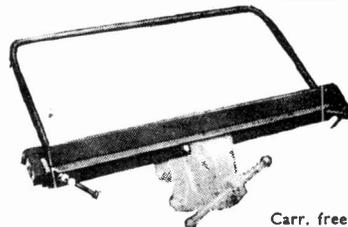A. B. PARKER, Folding Machine Works, Upper George St., Heckmondwike, Yorks. Heckmondwike 3997



People with the right connections switch to us

It's no choke. People who have zeners phase to phase and been solder relay good component can't resistors.

We're the enthusiasts ohm from ohm. Come and meters or megaphone coil now. It never hertz . . .

OPEN DAILY
9.15 a.m.-6 p.m.
(Closed all day
Thursday)

Garland Bros. Ltd.

TELEPHONE
01-692 4412

DEPTFORD BROADWAY (Corner of Brookmill Road)
LONDON, S.E.8

4-STATION INTERCOM



£6.15.0

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 7/6.

MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £12.10.0. P. & P. 9/- extra.

INTERCOM/BABY ALARM



3 Gns

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 2/6. P. & P. 4/6.

Transistor-TELEPHONE AMPLIFIER



59/6

Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Battery 2/6 extra. P. & P. 3/6. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (FE12)
169 KENSINGTON HIGH STREET, LONDON, W.8

BATTERY ELIMINATORS

The ideal way of running your TRANSISTOR RADIO, RECORD PLAYER, TAPE RECORDER, AMPLIFIER, etc. Types available: 6v, 9v, 12v, 18v (single output) 39/6 each. P. & P. 2/9. 9v + 9v; 6v + 6v; or 4.5v + 4.5v (two separate outputs) 50/- each. P. & P. 2/9. Please state completely isolated from mains by double wound transformer ensuring 100% safety.

R.C.S. PRODUCTS (RADIO) LTD.
(Dept. P.E.), 31 Oliver Road, London, E.17

Your local component stockist

East Anglia
EAGLE
Electronics
Eagle St.
IPSWICH 58075

TELERADIO ELECTRONICS

JOIN THE FASCINATING HOBBY OF RADIO CONTROL. BUILD A SINGLE CHANNEL SYSTEM FOR ABOUT £12 OR A SOPHISTICATED PROPORTIONAL SYSTEM FOR £80

Details from the specialists: TELERADIO CO. (P.E.)
325-7 FORE STREET, EDMONTON, N.9

NEW RANGE U.H.F. TV AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.

Loft Mounting Arrays, 7 element, 45.-; 11 element, 52/6; 14 element, 60.-; 18 element, 70.-; Wall Mounting with Cranked Arm, 7 element, 65.-; 11 element, 75.-; 14 element, 82/6; 18 element, 90.-; Chimney Mounting Arrays-Complete, 7 element, 80.-; 11 element, 87/6; 14 element, 95.-; 18 element, 105.-. Complete assembly instructions with every aerial. Low Loss Co-axial Cable, 18 yd. King Teleboosters—Lagbear U.H.F. Boosters from 75.-; Belling Lee "Comford" all Band V.H.F. U.H.F. mains operated pre-amp £7.10.0. State clearly channel number required on all orders. p.p. Aerials 8.-. Accessories 3.-. C.W.O. or C.O.D.

BBC . ITV . FM AERIALS



B.H.C. (Band 1). Loft, 25.-; Wall 5/D. 32/6. "H" array, 60.-; I.T.V. (Band 3). 5 element loft array, 45.-; 7 element, 55.-; Wall mounting 5 element, 65.-; Combined BBC ITV loft 1 + 5, 55.-; 1 + 7, 67/6; Wall mounting 1 + 5, 77/6; Chimney mounting 1 + 5, 90.-. Pre-amps from 75.-.

Combined BBC/ITV BBC2 Aerials. 1 + 5 + 9, 80.-; 1 + 5 + 14, 90.-; 1 + 7 + 14, 100.-. Available loft only.


F.M. Radio Loft S.D. 19.6. "H", 38/6. 3 element array, 37/6. Standard co-axial cable, 1 - yd. Coax plugs, 1/8. Outlet boxes, 6.-. Diplexer crossover boxes, 17/6. p.p. Aerials, 8.-; accessories, 3.-. C.W.O. or C.O.D. (min. C.O.D. charge 3.6.) 1.- for fully illustrated Lists.

CALLERS WELCOMED

OPEN ALL DAY SATURDAY

K.V.A. ELECTRONICS (Dept. P.E.)
40-41 Monarch Parade
London Road, Mitcham, Surrey
01-648 4884

Available now!

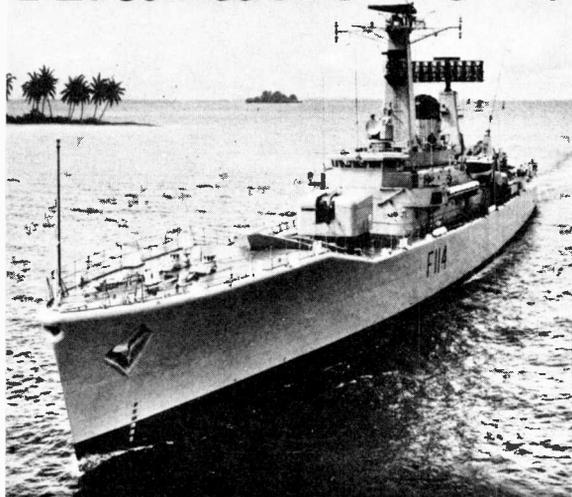

175 Naval Apprenticeships

Every six months the Navy needs 175 hand-picked men to train as its future top technicians. You could be one of the next 175. But apply early. Send now for the free booklet, all about Artificer Apprenticeships. It tells you how the Navy gives you one of the finest engineering trainings in the world.

And look what it means: You become the man in charge of advanced modern equipment in ships, submarines and helicopters—like electronic systems, computers, radar, missiles, gas and steam turbines.

The Navy gives you a full 4-year apprenticeship at its own technical schools. There are plenty of sports and hobbies too. And, during training, you get nine weeks' holiday a year.



Full union status and O.N.C. ensure you a secure, well-paid job for life—in the Navy or out.

You enjoy a life of action—exciting and adventurous, with the chance to see something of the world while you're young.

FIND OUT MORE. To enter the Navy as an Artificer Apprentice you must be 15½-17½ and pass an entry exam. (With 'O' level or C.S.E.

Grade 1 in Maths plus one Science subject or English Language, you are exempt from the written part.) If you're 17½-23 you can apply for a Mechanician Apprenticeship. Post the coupon.



In your early twenties you can be a Chief Petty Officer earning over £2,000 a year. And there are very good chances of becoming a commissioned officer.

Royal Naval Careers Service (Apprenticeships) (877GW1), Old Admiralty Building, London, S.W.1. Please send me full details without obligation.

Send for free book.

Name _____

Address _____

Date of birth _____
(Enquiries from U.K. residents only)

RN
ROYAL NAVY

Send 1/- for New Comprehensive I.C. and Semiconductor price list (24 pages)

INTEGRATED CIRCUITS

NEW LOW PRICES • FULLY GUARANTEED

RCA	MOTOROLA	1-9	10+	25+	MULLARD
CA3000	MC788P	17/6	15/-	13/6	LINEAR
3005	MC788P	19/6	17/6	16/-	TA A241
7	MC789P	17/6	15/-	13/6	242
11	MC790P	27/6	24/6	23/-	243
12	MC792P	17/6	15/-	13/6	293
13	MC799P	17/6	15/-	13/6	300
14	MC1303P	57/6	—	—	310
18	MC1304P	79/6	—	—	320
18A	MC708P	59/6	—	—	350
19	MC7490P	69/6	—	—	435
20	MC788P	19/6	—	—	521
20A	MC838P	130/-	—	115/-	622
21	MC1582G	89/6	—	79/6	530
22	MC1435P	65/-	—	59/6	811
23	MC1709CG	19/-	—	—	TAB101
26					TAB100
28A					TAD100
28B					TAD110
29					39/6
29A					
30					
35					
36					
39					
41					
42					
43					
44					
45					
46					
47					
48					
49					
50					
51					
52					
53					
54					
55					
59					
64					

Post & Packing 1/6 per order. Data sheet free if ordered with ICS.
TELEPHONE 01-452 0161 A. MARSHALL & SONS LTD. TELEX 21422
28 CRICKLEWOOD BROADWAY, LONDON, N.W.2
 CALLERS WELCOME 9-5.30 SATURDAY 9-5
SEE OUR MAIN ADVERTISEMENT ON PAGE 81 FOR SEMICONDUCTORS

WAH-WAH PEDAL KIT

SELECTIVE AMPLIFIER MODULE. The basis of the Wah-Wah pedal. Kit contains all the components to build a 2-transistor circuit module, also the sockets, control, etc., required for the constructor to assemble his own design, 35/-. Assembled and tested module 42/6.

FOOT VOLUME CONTROL PEDAL. Foot pedal unit in very strong fawn plastic. Fitted with output lead and plug for connection to guitar amplifier. May be used for volume control or converted to Wah-Wah by adding the module. Pedal unit now only £52.6.

Complete kit for Wah-Wah pedal now only £6.10.0.

All post free.

Send 2/6 for our catalogue of components, testmeters, musical electronics and more details of the above items. Callers welcome.

WILSIC ELECTRONICS LIMITED
6 COPLEY ROAD, DONCASTER, YORKSHIRE

BAKER 12in. MAJOR £9



The remarkable quality and performance of the "Major" makes possible truly brilliant and rich sound from a single loudspeaker. It recreates the entire musical spectrum from 30 to 14,500 c.p.s. The unit consists of the latest double cone, woofer and tweeter cone together with a special Baker CERAMIC magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. For Hi-Fi or P.A. Rated 20 watts. Voice coils available 3 or 8 or 15 ohms.

Major Module 30-17,000 cps with tweeter, crossover, baffle £11.10.0
 19:: 12in. and instructions.

Latest catalogue 1/- with enclosure plan.

Baker Reproducers Ltd.

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665

In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering . . .

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn on 'SATISFACTION - OR REFUND OF FEE' terms. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

WHICH SUBJECT WOULD INTEREST YOU?

Mechanical

A.M.S.E. (Mech.)
Inst. of Engineers
Mechanical Eng.
Maintenance Eng.
Welding
General Diesel Eng.
Sheet Metal Work
Eng. Inspection
Eng. Metallurgy
C. & G. Eng. Crafts
C. & G. Fabrication

Draughtsmanship

A.M.I.E.D.
Gen. Draughtsmanship
Die & Press Tools
Elec. Draughtsmanship
Jig & Tool Design
Design of Elec. Machines
Technical Drawing
Building

Electrical & Electronic

A.M.S.E. (Elec.)
C. & G. Elec. Eng.
General Elec. Eng.
Installations & Wiring
Electrical Maths.
Electrical Science
Computer Electronics
Electronic Eng.

Radio & Telecomm.

C. & G. Telecomm.
C. & G. Radio Servicing
Radio Amateurs' Exam.
Radio Operators' Cert.
Radio & TV Engineering
Radio Servicing
Practical Television
TV Servicing
Colour TV
Practical Radio & Electronics (with kit)

Auto & Aero

A.M.I.M.I.
MAA IMI Diploma
C. & G. Auto Eng.
General Auto Eng.
Motor Mechanics
A.R.B. Certs.
Gen. Aero Eng.

Management & Production

Computer Programming
Inst. of Marketing
A.C.W.A.
Works Management
Work Study
Production Eng.
Storekeeping
Estimating
Personnel Management
Quality Control
Electronic Data Processing
Numerical Control
Planning Engineering
Materials Handling
Operational Research
Metrication

Constructional

A.M.S.E. (Civ.)
C. & G. Structural
Road Engineering
Civil Engineering
Building
Air Conditioning
Heating & Ventilating
Carpentry & Joinery
Clerk of Works
Building Drawing
Surveying
Painting and Decorating.
Architecture
Builders' Quantities

General

C.E.I.
Petroleum Tech.
Practical Maths.
Refrigerator Servicing.
Rubber Technology
Sales Engineer
Timber Trade
Farm Science
Agricultural Eng.
General Plastics

General Certificate of Education

Choose from 42 'O' and 'A' Level subjects including:
English
Chemistry
General Science
Geology
Physics
Mathematics
Technical Drawing
French
German
Russian
Spanish
Biology
B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.

WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.

Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.

THEY DID IT—SO COULD YOU

"My income has almost trebled . . . my life is fuller and happier." - Case History G/321.

"In addition to having my salary doubled, my future is assured." - Case History H/493.

"A turning point in my career - you have almost doubled my standard of living." - Case History K/662.

"Completing your Course meant going from a job I detested to a job I love." - Case History B/461.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help *you*.

Free!

Why not do the thing that really interests you? Without losing a day's pay, *you* could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you . . . but it could be the best thing you ever did.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept D256, Aldermaston Court, Reading RG7 4PF.

(Write if you prefer not to cut this page)



POST THIS COUPON TODAY

To: B.I.E.T., Dept D256, Aldermaston Court, Reading RG7 4PF
Please send me book and details of your Courses in

Name Age

Address

Occupation

B.I.E.T. - IN ASSOCIATION WITH THE SCHOOL OF CAREERS - ALDERMASTON COURT, BERKSHIRE

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/asia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Kingstons Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription Rate (including postage) for one year to any part of the world £2 5s. 0d (£2 2s). Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

HENRY'S RADIO LTD FOUR ELECTRONICS CENTRES ALL WITHIN 100 YARDS

303·309·354·356 EDGWARE ROAD LONDON W.2

BUILD YOURSELF A QUALITY RADIO



Excellent printed circuit design with full power output. Fully tuneable on both MW/LW bands. 7 Mullard transistors. Fitted 5in speaker. Room filling power. Easy to build with terrific results. Two colour leathercloth cabinets with silvered front. All local and continental stations. Complete detailed instructions. Total cost £6.19.6, p.p. 6/6. All parts sold separately. Ask for Leaflet No. 1

YOU CAN SAVE 25%

on Garrard, Goldring and Mcdonald Decks.



*SP25 Mk II £10.19.6.
*SL65B £14. 9.6.
*SL72B £23. 0.0.
*MP610 £13.19.6.
GL75 £32. 0.0.

*SP25 Mk III £11.10.0.
*AP75 £16.19.6.
MP60 £10.19.6.
GL69 II £23. 0.0.
(p.p. 7/6 any type)

PLINTHS AND COVERS

* Standard 89/6 p.p. 4/6. * Deluxe £8.15.0. p.p. 6/6.
+ Deluxe £8.15.0. p.p. 6/6.

SPECIAL OFFER! The above decks supplied with 9TAH/C Diamond, add £2; 940 magnetic, add £3; G850 or AT66, add £5; G800, add £7.10.0; GP91 SC, add £1 (Also applies to MP60/FC).

SPECIAL! SP25 fitted G800 with plinth/cover wired and mounted, £20.19.6. p.p. 10/-
2025TC with 9TAH/C diamond, plinth and cover wired and mounted, £13.19.6. p.p. 10/-
GL69 II fitted G800 plinth and cover wired and mounted, £35.0.0. p.p. 12/6.

Also in Stock—2025TC/9TAHC diam. £8.17.6. 3000 LM. 9TAHC diam., £9.15.0. 3500/KS40A. £12.10.0. MP60 fitted plinth and cover (see above for cartridges), £17.12.6. p.p. 10/-
* FREE—Complete Lists Nos. 16/17 on request.

ELECTRONIC ORGANS



You can build our Mayfair Portable for

£99 p.p. 30/-

All parts available separately—several models to choose from—visit our new showrooms at 309 Edgware Road.

DISCOTHEQUE —PA CENTRE

All the latest equipment in stock. Call and see for yourself or send for latest lists.

HI-FI TO SUIT EVERY POCKET

FREE—Stock Lists Nos. 16/17 on request—BEST VALUE IN U.K.

100

STEREO SYSTEMS

and a complete range of individual units in stock—Demonstrations all day—visit our new Hi-Fi Store. LOW CASH OR CREDIT/HP TERMS (Credit terms from £30 purchase—callers only).



SPECIAL STEREO SYSTEMS

*FREE—pair of stereo headphones for private listening. C5/B Teleton 203E. 6+6W amplifier, SP25 or MP60 with deluxe plinth/cover, pair of 3-way 10W bookshelf speakers, all cables, leads, magnetic cartridge (List £79.10.0). PRICE £59. p.p. 30/-

C1/B Nova 505 Amplifier. 2025TC with 9TAH/C diamond, plinth and cover, pair of 3-way 10W bookshelf speakers, cables/leads, etc. (List £65). PRICE £49. p.p. 30/-

C9A/B Sinclair 2000 amplifier, SP25 or MP60 with G800, plinth and cover, pair of 3-way 10W bookshelf speakers, cables/leads, etc. (List £88). PRICE £69. p.p. 30/-

B11/B Teleton F2000 (or F3100) MW/FM/STEREO Tuner amplifier, SP25 or MP60 with 9TAHC diamond, pair of 3-way 10W speakers, cables/leads, etc. (List £100). PRICE £79. p.p. 30/-

(All systems add £10 for larger speakers, £14 for Dentons). SEND FOR FREE LISTS OF 100 STEREO SYSTEMS

SINCLAIR EQUIPMENT SAVE £££'s

PROJECT 60 PACKAGE DEALS

2xZ30 amplifier, stereo 60 pre-amp, PZ5 power supply, £19.0.0. Carr. 7/6. Or with PZ6 power supply, £21. Carr. 7/6. 2xZ50 amplifier, stereo 60 pre-amplifier, PZ6 power supply, £21.10.0. Carr. 7/6. Transformer for PZ6, 59/6 extra. Any of the above with Active Filter unit add 97/6 or with pair Q16 speakers add £16. All Sinclair amplifiers in stock. 2000 amplifier, £23. Carr. 7/6. Neoteric model, £46. Carr. 7/6.

BUILD THIS VHF FM TUNER



5 MULLARD TRANSISTORS 300kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately.

PARTS TOTAL COST £6.19.6. p.p. 3/6. MULTIPLEX DECODER £5.19.6 (FOR STEREO) p.p. 3/- Ask for Brochure No. 3

HENRY'S LATEST CATALOGUE

Latest edition. Now 350 pages.

* COMPONENTS, TEST GEAR * EQUIPMENT, MODULES * SPECIAL OFFERS, Etc., Etc.

Everything for the constructor. Complete with 10/- value discount voucher for use with purchase. Price 7/6, p.p. 2/-

WHY NOT SEND AWAY TODAY? FREE 8-page SEMI-CONDUCTOR LIST No. 36. New ranges and a few circuits.




TE20D RF generator. Price £15. p.p. 7/6.

TE22D Matching audio generator. Price £17. p.p. 7/6.

TE15 Grid dip meter. Price £12.10.0. p.p. 3/6.

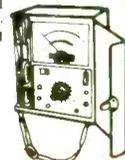TO3 Scope 3in tube. Price £37.10.0. p.p. 10/-



AF105 50kV/V multimeter (illus.). Price £8.10.0. p.p. 3/6. Leather case 28/6.

200H 20kV/V. Price £3.17.6. p.p. 3/6. Case 12/6.

500 30kV/V multimeter. Price £8.17.6. p.p. 3/6. Leather case 30/-.


THL33 2kV/V. Price £4.2.6. p.p. 3/-.

TE65 Valve voltmeter (illus.). £17.10.0. p.p. 7/6.

SE1250B Pocket pencil signal injector 35/- p.p. 1/6.

SE500 Pocket pencil signal tracer 29/6 p.p. 1/6.

NEW SELF-POWERED PREAMPLIFIERS

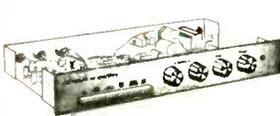


SLIM MODERN DESIGNS USING THE LATEST SILICON TRANSISTORS, FET's and IC's, DIN SOCKETS, ETC., fitted. PUSH-BUTTON SELECTION. 20dB BASS AND TREBLE BOOST AND CUT. All inputs provided plus TAPE RECORD AND REPLAY. Specifically designed for use with PA25 and PA50 Amplifiers.

GOLD AND SILVER FINISH, Mains operated. Supplied with all plugs, etc. ADJUSTABLE OUTPUT UP TO 1 VOLT.

* FET9/4. Mono with built-in mic. mixer. Accepts any ceramic or crystal cartridge. Plus tuner, tape, etc. Price £12.10.0. p.p. 4/-

* FET154 STEREO (illus.). Magnetic cart. input, tuner, tape, etc. Beautiful stereo sound. Price £16.10.0. p.p. 4/6.

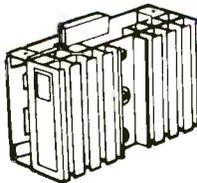* I.C. STEREO All facilities plus headphone socket without amplifiers. Uses IC's, FET's, etc. Price £24.0.0. p.p. 5/6.



25 WATT & 50 WATT SILICON AMPLIFIERS

LOOK AT THE SPECIFICATIONS!

- At full power 0.3% distortion.
- Rise time 2usec.
- At full power—1dB 11c/s to 40 kc/s.
- Short circuit proof plus limiting cct.
- Response—1dB 11 c/s to 100 kc/s.

PA25 10 transistor all silicon differential input 400mV sensitivity. 25W Rms into 8 ohms. Supplied with edge connector harness size 5in x 3in x 2in.

PA50 12 transistor version 50W Rms into 3 to 4 ohms. Size 5in x 3in x 4in.

MU442. Power supply for one or two PA25 or one PA50. PA25, £7.10.0. PA50, £9.10.0. MU442, £6.

SIMPLICITY TO MOUNT — EASY TO USE — DESIGNED FOR QUALITY, PERFORMANCE AND PRICE
All units no soldering — just edge connectors and plugs

HENRY'S RADIO LTD • MAIL ORDER AND INDUSTRIAL SALES DEPT 303, EDGWARE ROAD LONDON W.2 01 723 1008 9

● ELECTRONIC COMPONENTS AND EQUIPMENT
AUDIO AND TEST GEAR
356 EDGWARE ROAD LONDON W.2.
TEL. 01 402 4736

● ELECTRONIC ORGANS, PUBLIC ADDRESS
DISCOTHEQUE EQUIPMENT
309 EDGWARE ROAD LONDON W.2
TEL. 01 723 6963

● HIGH FIDELITY SALES
AND DEMONSTRATIONS
354, EDGWARE ROAD LONDON W.2
TEL. 01 402 5854

OPEN MONDAY TO SATURDAY 9 AM TO 6 PM. THURS 9 AM TO 1 PM. OPEN ALL DAY SATURDAY