

PRACTICAL

ELECTRONICS

JUNE 1974

25p

What are YOU getting?

... find out with our

M.P.G. Meter



TELEBELL...
REPEATS
ANYWHERE!

NEW EDU-KIT MAJOR

**COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT
BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER**

- 4 Transistor Earpiece Radio
- 7 Transistor Loudspeaker Radio MW/LW
- 2 Transistor Regenerative Radio
- Signal Tracer
- 5 Transistor Short Wave Radio
- 3 Transistor Regenerative Radio
- Transistor Tester NPN I/P
- Electronic Metronome
- Audible Continuity Tester
- 4 Transistor Push Pull Amplifier
- Electronic Noise Generator
- Sensitive Pre-Amplifier
- 5 Transistor Push Pull Amplifier
- Batteryless Crystal Radio
- One Transistor Radio

TOTAL BUILDING COSTS


£7.23 P.P. & INS. 44p
(Overseas P.P. £1.85p)
(+10% VAT 72p)

Components include:

- 24 Resistors
- 21 Capacitors
- 10 Transistors
- 31 Loudspeaker
- Earpiece
- Mica Baseboard
- 3 12-way Connectors
- 2 Volume Controls
- 2 Slider Switches
- 1 Tuning Condenser
- 3 Knobs
- Ready Wound MW/LW/SW Coils
- Ferrite Rod
- 6 1/2 yards of wire
- 1 yard of sleeving, etc.
- Parts price list and plans 50p (free with parts)

NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

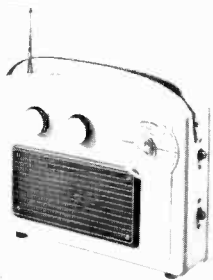


Nine Transistors, 9 Tunable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW. Retractable chrome plated telescopic aerial for VHF and SW. Push Pull output using 600 mW transistors. 9 Transistors and 3 diodes, tuning condenser with VHF section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wave change controls. Attractive all white case with red grille and carrying strap. Size 9in x 7in x 2 1/2in approx. Parts price list and plans 30p (FREE with parts).


TOTAL BUILDING COSTS **£6.95** P.P. & INS. 44p
(Overseas P. & P. £1.85)
(+10% VAT 69p)

POCKET FIVE

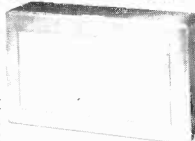3 Tunable wavebands MW/LW and Trawler Band 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, moving coil loudspeaker, attractive Black and Gold Case. Size 5 1/2in x 4 1/2in x 3 1/2in approx. Plans and parts price list 15p (FREE with parts).



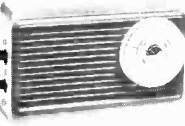Total Building Costs **£2.28**
(+10% VAT 22p)
P.P. & Ins. 26p
(Overseas P. P. £1.25)



TRANSONA FIVE


Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and parts price list 15p (FREE with parts).

Total Building Costs **£2.50** P.P. & Ins. 26p
(+10% VAT 25p)
(Overseas P. & P. £1.25)

TRANS EIGHT

8 TRANSISTORS AND 3 DIODES

6 TUNABLE WAVEBANDS, MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

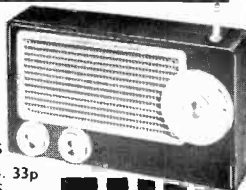

TOTAL BUILDING COSTS **£4.48** P.P. & INS. 33p
(Overseas P. & P. £1.25)
(+10% VAT 44p)

ROAMER SIX

CASE AND LOOKS AS TRANS EIGHT
6 TUNABLE WAVEBANDS; MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages

6 transistors and 2 diodes, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Plans and parts price list 25p (FREE with parts).

TOTAL BUILDING COSTS **£3.98** P.P. & IN. 31p
(Overseas P. & P. £1.85)
(+10% VAT 39p)

NEW EVERYDAY SERIES



Build this exciting New series of designs

EV5 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and loudspeaker. Attractive case with red speaker grille. Size 9in x 5 1/2in x 2 1/2in approx. Parts price list and plans 15p (FREE with parts).

TOTAL BUILDING COSTS **£2.73** P.P. & INS. 30p
(Overseas P. & P. £1.25)
(+10% VAT 27p)

EV6 Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt Battery. Ferrite rod aerial, 3 Loudspeaker, etc. MW/LW coverage. Push Pull Output. Parts price list and plans 15p (FREE with parts).

TOTAL BUILDING COSTS **£3.60** P.P. & INS. 30p
(Overseas P. & P. £1.25)
(+10% VAT 36p)

EV7 Case and looks as above. 7 transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt Battery Push Pull Output. Telescopic Aerial for Short Waves. 3 Loudspeaker. Parts price list and easy build plans 20p. (Free with parts).

TOTAL BUILDING COSTS **£4.08** P.P. & INS. 31p
(Overseas P. & P. £1.85p)
(+10% VAT 40p)

ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL



7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Retractable chrome plated telescopic aerial for short waves. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4 1/2 watt Ferrite Magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£6.98** P.P. & INS. 47p
(Overseas P. & P. £1.85)
(+10% VAT 69p)

ROAMER TEN


WITH VHF INCLUDING AIRCRAFT



10 TRANSISTORS 9 TUNABLE WAVE BANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS. ALSO AIRCRAFT BAND

Latest 4 1/2 watt Ferrite Magnet Loudspeaker. Built-in ferrite rod aerial for MW/LW. Retractable, chrome plated 7 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in x 7in x 4in. Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts).

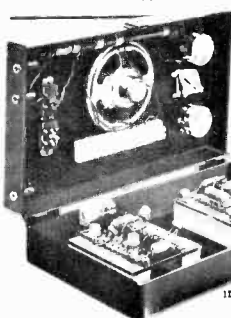TOTAL BUILDING COSTS **£8.50** P.P. & INS. 52p
(Overseas P. & P. £1.85)
(+10% VAT 85p)



EDU-KIT

Build Radios Amplifiers, etc., from easy stage, diagrams.

Five units including master unit to construct.

Components include: Tuning Condenser, 2 Volume Controls, 2 Slider switches, Fine tone 3" moving coil Speaker, Terminal Strip, Ferrite Rod Aerial, Battery Clips, 4 Tag Boards, 10 Transistors, 4 Diodes, Resistors, Capacitors, Three 1/2in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£5.50** P.P. & INS. 33p
(Overseas P. & P. £1.85)
(+10% VAT 55p)

RADIO EXCHANGE LTD

*Callers side entrance "Lavelle" shop
*Open 10-1. 2.30-4.30. Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD MK40 1SA
Tel. 0234 52387 Reg. No. 788372

I enclose £ _____ for _____
Name _____
Address _____

PRACTICAL ELECTRONICS

VOLUME 10 No. 6 JUNE 1974

CONSTRUCTIONAL PROJECTS

- R/C BRIDGE** *by D. W. Easterling* 502
A useful item of test gear
- M.P.G. METER** *by S. Jones* 507
Use's the car's electric fuel pump to give continuous reading of fuel consumption
- TELEBELL** *by J. N. Watt* 524
A remote repeater for telephone bell
- P.E. RONDO QUADRAPHONIC SOUND SYSTEM—7** *by R. A. Cole* 528
Audio section round-up and modifications
- THEATRE CUEING LIGHT** *by S. H. Davies* 532
A simple signalling system suitable for use by amateur dramatic societies

GENERAL FEATURES

- INGENUITY UNLIMITED** 511
Logic Tester—Touch Switch—Power Supply—Circuit Board—Timebase Marker—
Tunnel Diode Schmitt—Regulator—Oscillator
- FIRST STEPS IN CIRCUIT DESIGN—3** *by A. P. Stephenson* 520
Choosing components and supply voltage for correct biasing
- NEW DEVICES . . . APPLICATIONS** 535
An integrated circuit programmable counter/timer
- RANDOM TIMER** *by B. H. Baily* 54 0
A novel circuit for E.S.P. experiments

NEWS AND COMMENT

- EDITORIAL—Mind Over Matter** 501
- POINTS ARISING** 510
Anyone at Home—Auto Charger/Regulator—Boolean Algebra—
Slow Timebase Oscillator—Semiconductor Tester—Battery
Eliminator—Power Supply for I.C.'s—Rhythm Generator
- SPACEWATCH** *by Frank W. Hyde* 519
Kohoutek Results—Titan/Centaur
- NEWS BRIEFS** 531
Laser Beam Phone Calls—Medical Logging Device—Paging Down Under
- MARKET PLACE** 534
A look at a printed circuit kit, oscilloscopes and wiring boards
- ESP, etc.** *by B. H. Baily* 539
Unexplained happenings and phenomena
- INDUSTRY NOTEBOOK** *by Nexus* 542
What's happening inside industry
- PATENTS REVIEW** 545
Thought provoking ideas on file at the British Patent Office
- READOUT** 546
A selection of readers' letters


Our July issue will be published on Friday June 14, 1974.

© IPC Magazines Limited 1974. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Publisher's Subscription Rate including postage for one year, Inland £3.25, Overseas £3.50. International Giro facilities Account No. 5122007. Please state reason for payment, "message to payee".

R T V C

FOR AUDIO ON A BUDGET

PUSH BUTTON CAR RADIO KIT^(*)

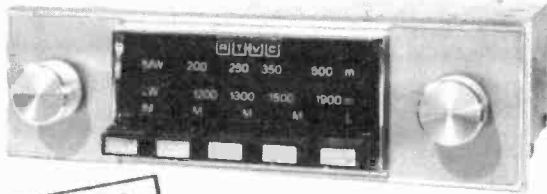

The first time Motor magazine have nominated a push button car radio for their Top Ten Accessory Awards



NOW BUILD YOUR OWN AWARD WINNING PUSH BUTTON CAR RADIO

Technical specification:

- 1.) Output 2.5 watts R.M.S. into 8 ohms. For 12 volt operation on negative or positive earth.
- 2.) Integrated circuit output stage, pre built three stage IF Module.

Controls Volume, manual tuning and five push buttons for station selection, illuminated tuning scale covering full medium and long wave bands.
Size Chassis 7 ins. wide, 2 ins. high and 4 1/8 ins. deep approx.

NOTE: The ability to solder on a printed circuitboard is necessary to complete this kit successfully. Circuit diagram and comprehensive instructions 55p. free with kit.

Car Radio Kit

£6.60 + 55p. postage & packing.

Speaker including baffle and fixing strips

£1.65 + 23p. postage & packing.

Recommended Car Aerial - fully retractable and locking.

£1.35 post paid.

STEREO 21



QUALITY SOUND^(*) FOR LESS THAN £19.00

Stereo 21 easy to assemble audio system kit, - no soldering required. Includes: -

BSR 3 speed deck, automatic, manual facilities together with ceramic cartridge.

Two speakers with cabinets.

Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

For the technically minded: -

Specifications:

Input sensitivity 600mV; Aux. input sensitivity 120mV; Power output 2.7 watts per channel; Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs. **Overall Dimensions**. Speakers approx. 15 1/2" x 8" x 4". Complete deck and cover in closed position approx. 15 1/2" x 12" x 6". Complete only **£18.95**

Extras if required.

Optional Diamond Stylus **£1.37** + £1.60 p & p.

Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance. **£3.85.**



DISCO AMPLIFIER

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Outputs 20 watts R.M.S. into 8 ohms (suitable for 15 ohms).

Inputs *5 Electrically Mixed Inputs. *3 Individual Mixing controls. *Separate bass and treble controls common to all 5 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid State Circuitry. *Attractive Styling.


INPUT SENSITIVITIES

1) Crystal Mic or Guitar 9mV. 2) Moving coil Mic or Guitar 8mV. 3), 4), 5) Medium output equipment (Gram. Tuner, Monitor, Organ, etc.) - all 250mV sensitivity.

AC Mains 240V. operation. Size approx. 12 1/2" ins x 6 ins x 3 1/2" ins

£15.00 + 60p. postage & packing

DISCO 50

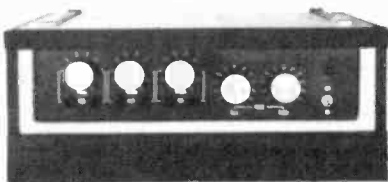

45 WATT R.M.S. MONO DISCOTHEQUE AMPLIFIER

Ideal for Disco Work. Output Power: 45 watts R.M.S. Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K. Size: 19 1/4" x 10 1/2" x 8 ins. approx. Amplifier **£27.50 + £1.50 p. & p**

Special Offer: Disco 50 plus two 15" E.M.I. speakers type 14A/780 (as illustrated on opposite page). Complete **£57.00 + £4.00 p & p.**

COMPLETE^(*) STEREO SYSTEM



£51.00

40 Watt Amplifier.
Viscount III - R102 now 20 watts per channel.
System I includes.

Viscount III amplifier - volume, bass, treble and balance controls, plus switches for mono/stereo on/off function and bass and treble filters. Plus headphone socket.

Specification

20 watts per channel into 8 ohms.
Total distortion @ 10W @ 1kHz 0.1%. *P.U.1* (for ceramic cartridges) 150mV into 3 Meg. *P.U.2* (for magnetic cartridges) 4mV @ 1kHz into 47K. Equalised within -1dB R.I.A.A. *Radio* 150mV into 220K. (Sensitivities given at full power).
Tape out facilities: headphone socket, power out 250mW per channel. *Tone controls and filter characteristics.* Bass: -12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble -12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max.) -58dB.
Crosstalk better than 35dB on all inputs.
Overload characteristics better than 26dB on all inputs. Size approx. 13 3/4" x 9" x 3 3/4".

Garrard SP25 deck, with magnetic cartridge, de luxe plinth and hinged cover.

Two Duo Type II matched speakers - Enclosure size approx. 17 1/2" x 10 3/4" x 6" in simulated teak. Drive unit 13" x 8" with parasitic tweeter

Complete System £51.00

£69.00

System II
Viscount III amplifier (As System I)
Garrard SP. 25 (As System I)

Two Duo Type IIIA matched speakers - Enclosure size approx. 31" x 13" x 11 1/2". Finished in teak veneer. Drive units approx. 13 1/2" x 8 1/2" with 3 1/2" HF speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20kHz.

Complete System £69.00

PRICES: SYSTEM 1

Viscount III R102 amplifier	£24.20	+ £1 p & p
2 Duo Type II speakers	£14.00	+ £2.20 p & p
Garrard SP25 with MAG. cartridge de luxe plinth and hinged cover	£21.00	+ £1.75 p & p.
	total	£59.20

Available complete for only **£51.00 + £3.50 p. & p.**

PRICES: SYSTEM 2

Viscount R102 amplifier	£24.20	£1.00 p. & p.
2 Duo Type IIIA speakers	£39.00	£4.00 p. & p.
Garrard SP25 with MAG cartridge de luxe plinth and hinged cover	£21.00	£1.75 p. & p.
	total	£84.20

Available complete for only **£69.00 + £4 p. & p.**

EMI SPEAKERS AT FANTASTIC REDUCTIONS

THE ULTIMATE COMPLETE SPEAKER SYSTEM
EMI LE 315. List Price £86.00



A professional standard five way speaker system with enclosure giving top quality performance.

Enclosure Dimensions
approx. (3ft. x 2ft. x 1ft.)

Drive Units

Hand built - 15" diameter bass with 3" voice coil, - two 5" diameter Mid Range units, - two 3 1/2" HF. units, plus matching crossover panel with two variable potentiometers for mid and high frequency adjustment.

Power Handling

Continuous rating 35 W rms., Peak power rating 70 W.

Frequency Response

20 Hz 20,000 Hz. Imp. 8 ohms.

Our price **£45.00 + £3.50 p. & p.**



15" 14A/780 BASS UNIT

Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz, flux density 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3" voice coil.

Recommended retail price **£40.80.**

OUR PRICE £18.70 + £1.50 p & p + £1.50 p & p Special Offer.



950 KIT

Five matched speakers and crossover unit for handling up to 45 watts, frequency response from 20 to 20,000 Hz.

Huge 19" x 14" (approx.) high efficiency Bass-Speaker with 16,500-gauss magnet built on a heavy diecast frame.

The four 10,000 gauss tweeters, each 3 1/2" dia. approx., are fed by the crossover which critically adjusts signal for maximum fidelity. Impedance at 1 kHz is 8 ohms.

Bass coil 2", others 0.5" Recommended list price £44.00.

OUR PRICE £19.50



BUILD YOUR OWN STEREO AMPLIFIER^(*)

For the man who wants to design his own stereo - here's your chance to start, with Unisound - pre-amp, power amplifier and control panel. No soldering - just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum.

£7.64 + 55p. p & p



8 TRACK CARTRIDGE PLAYER^(*)

Elegant self selector push button player for use with your stereo system. Compatible with Viscount III system, Unisound module and the Stereo 21

Technical specification Mains input, 240V. Output sensitivity 125mV

Comparable unit sold elsewhere at £24.00 approx.

Yours for only £10.95 + 90p. p & p



Just write your order giving your credit card number

DO NOT SEND YOUR CARD

● Mail orders to Acton. Terms C.W.O.
All enquires Stamped Addressed Envelope.
Goods not despatched outside U.K.

● Leaflets available for all items listed thus^(*)
Send stamped addressed envelope.



Radio and TV Components (Acton) Ltd.

21 High Street, Acton, London W3 6NG/D
323 Edgware Road, London W2

Personal — Edgware Road: 9a.m.-5.30p.m. Half day Thurs.
Shoppers — Acton: 9.30 a.m.-5 p.m. Closed all day Wed.

Connoisseur

THE B.D.2 TURNTABLE ASSEMBLY


The Famous B.D.2 belt drive turntable with press button speed change has now been developed to feature a newly designed mat and brushed aluminium trim, and the perspex cover has an easy 'hinged-on, hinged-off' movement. The B.D.2 is available as a chassis unit or spring mounted on a wood plinth.



B.D.1 TURNTABLE KIT

The B.D.1 well known for its superb performance and quality is available in kit form. Construction is simplicity itself with no soldering required. Now it's so easy to own the best.

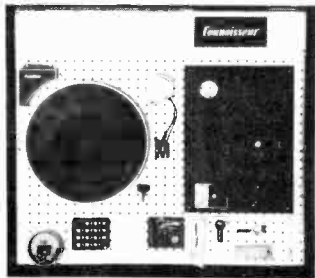Contact your dealer for information or send a stamp for brochure.



A. R. SUGDEN & CO. (ENGINEERS) LTD

Atlas Mill Road, Brighouse HD6 1ER Telephone: Brighouse (04847) 2142. Telegrams and cables: Connoisseur, Brighouse

ENGINEERS

FREE

YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost B.I.E.T. home-study course. There are no books to buy and you can pay-as-you-learn.

The B.I.E.T. guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.



CUT OUT THIS COUPON
CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

- | | | | | | | | | | | | | | |
|---|---|---------------------------------------|--|---|--|--|--|--|---|--|--|---|---|
| <input type="checkbox"/> Practical Radio and Electronics (Technatron) | <input type="checkbox"/> Radio Amateurs | <input type="checkbox"/> Practical TV | <input type="checkbox"/> Colour Television | <input type="checkbox"/> Computer Electronics | <input type="checkbox"/> C & G LI Radio TV Servicing cert. | <input type="checkbox"/> Post Master General 1st & 2nd class certs | <input type="checkbox"/> C & G Electrical Engineering Practise | <input type="checkbox"/> C & G LI Installations and Wiring | <input type="checkbox"/> General Electrical Engineering | <input type="checkbox"/> Society of Engineers (Electrical Engineering) | <input type="checkbox"/> Electrical Installations and Wiring | <input type="checkbox"/> C & G Electrical Technicians (Primary) | <input type="checkbox"/> C & G Telecommunications |
|---|---|---------------------------------------|--|---|--|--|--|--|---|--|--|---|---|

To B.I.E.T. BPE 04 Aldermaston Court, Reading RG7 4PF QK **BPE 04**


NAME (Block Capitals Please)
ADDRESS

Other subjects
Member of A B C C

Age
Accredited by

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

NEW SCORPIO Mk. 2

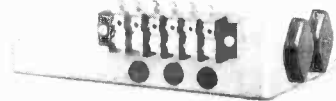

Following the phenomenally successful Scorpio Capacitor-Discharge Electronic Ignition system introduced in 1972 and proved by many thousands of satisfied motorists, we are happy to announce availability of all parts for the PE SCORPIO Mk. 2—

- * Now with added R.F.I. suppression.
- * Fully machined and painted die-cast case with AMP termination connector block.
- * Custom wound transformer.
- * NOW AVAILABLE IN 6V. and 12V.
- * Suitable for all types of Cars, Boats, Go-Karts, etc.
- * Promotes easier starting—even under sub-zero conditions.
- * Improves acceleration, gives better high speed performance and quicker engine warm up.
- * Eliminates excessive contact breaker burning and pitting.
- * PROMOTES FUEL ECONOMY.

Construction of the unit can easily be completed in an evening—installation should take about half an hour. A complete complement of components is supplied with each kit together with ready drilled, roller tinned professional quality fibreglass printed circuit board.—Uses original plugs, points, and coil.—No special parts or extras required.


- (Case size 7½in 4½in 2in)
- * All components available separately.—S.A.E. with enquiries.
- * Construction manual available separately 25p.
- Cost £12.95 incl. carr., ins. and VAT. (Carriage at cost outside U.K.—Export enquiries welcome.)

CONVERSION KIT FROM Mk. 1 to Mk. 2. FOR CONSTRUCTORS ALREADY POSSESSING Mk. 1 KITS.—Miniature P.C. assembly £1.10 incl. Carr., Ins. and VAT with full conversion instructions.

DABAR ELECTRONIC PRODUCTS
98 LICHFIELD STREET
WALSALL, Staffs WS1 1UZ

MAPLIN ELECTRONIC SUPPLIES

★ SAME DAY SERVICE

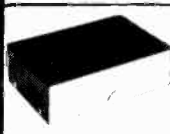

LARGE OR SMALL Centurion

PROJECTS DESERVE A PROFESSIONAL QUALITY INSTRUMENT CASE—4 MODELS

Model 120 all aluminium two part construction. Top and sides, blue hammer finish, front, rear and base: white. Others: mild steel three part construction. Top, base, sides and detachable rear panel, blue hammer. Detachable aluminium front panel finished in white. Dimensions in inches.



Model	W	H	D	Price
120	8	2½	6	£1.85
220	8	6	3½	£2.65
221	8	6	6	£2.90
320	12	8	12	£5.75

Chassis for model 320 £1.75 extra. Please send s.a.e. for free illustrated leaflet.

ORGAN BUILDERS

MES announce the very latest development in organ circuitry.

THE DMO2

13 Master Frequencies on ONE tiny circuit board. LOOK AT THESE AMAZING ADVANTAGES
 ★ 13 frequencies from C8 to C9. ★ Each frequency digitally derived from a SINGLE h.f. master oscillator.
 ★ Initial tuning for the WHOLE ORGAN—ONE SIMPLE ADJUSTMENT. ★ Relative tuning NEVER DRIFTS! ★ External control allows instant tune-up to other musicians. ★ Outputs will directly drive most types of dividers including the SAJ110. ★ And each output can also be used as a direct tone source. ★ Variable DEPTH AND RATE tremulant optional extra.
 ★ Gold-plated plug-in edge connexion. ★ Complete fibre glass board (including tremulant if required) ONLY 3.7in. x 4.5in. ★ Very low power consumption.

★ EXTREMELY ECONOMICAL! ★ 8 a.e. please for full technical details.
 PRICE: ★ Ready built, tested and fully guaranteed.
 DMO2T (with tremulant) ONLY £14.25.
 DMO2 (without tremulant) £12.25

Trade enquiries welcome.
 SAJ110 7-stage frequency divider in one 14 pin DIL package. Sine or square wave input allows operation from almost any type of master oscillator including the DMO2 (when 97 notes are available). Square wave outputs may be modified to saw-tooth by the addition of a few components. SAJ110: £2.63 each OR special price for pack of 12: £25.00. S.a.e. please for data sheet.



MAPLIN: Projected site of London's third airport.

P.E. SOUND SYNTHESISER

If this project seems expensive YOU HAVEN'T SEEN OUR PRICES! We are stocking all the parts for this exciting project, from the special I.C.'s right down to the nuts, bolts and spacers for mounting the Veroboards. Also parts for the 'Electronics Today International' Synthesiser stocked.

Send S.A.E. now for our detailed price lists

YOU SIMPLY MUST SEE OUR PRICES!

Keyboard 49 note C C	£14.35
741C 8-pin DIL	36p
MFC 6040 electronic attenuator	95p
SG 1402N for Ring Modulator	£1.69
CA 3146	69p

CAPACITORS

Sub-miniature Axial lead electrolytic

Mid V Price	Mid V Price	Mid V Price	Mid V Price
1 63 6p	68 6 30p		
1.5 63 6p	68 16 6p		
2.2 63 6p	68 63 10p		
3.3 63 6p	100 4 6p	Mid V Price	
4.7 63 6p	100 10 6p	470 6.3 6p	
6.8 40 6p	100 25 6p	470 10 10p	
6.8 63 6p	100 40 6p	470 25 12p	
10 25 6p	100 63 12p	470 40 15p	
10 63 6p	150 6.3 6p	680 6.3 10p	
15 16 6p	150 16 6p	680 16 12p	
15 40 6p	150 25 6p	680 25 18p	
15 63 6p	150 40 10p	680 40 22p	
22 10 6p	150 63 12p	1000 4 10p	
22 25 6p	220 4 6p	1000 10 12p	
22 63 6p	220 10 6p	1000 16 15p	
33 6.3 6p	220 16 6p	1000 25 22p	
33 16 6p	220 25 10p	1500 6.3 12p	
33 40 6p	220 40 12p	1500 10 18p	
47 4 6p	220 63 18p	1600 16 22p	
47 10 6p	330 4 6p	2200 6.3 18p	
47 25 6p	330 10 6p	2200 10 22p	
47 40 6p	330 16 10p	3300 6.3 22p	
47 63 6p	330 63 22p	4700 4 22p	

PLUGS AND SOCKETS

DIN PLUGS:
 2 pin (1 flat) 4p P360 3 pin 1.5A socket 62p
 3 pin 4p chassis plug with 1.5A line socket Per
 (180°) 5 pin B pair 28p
 (240°) 6 pin 10p SA 2190 3 pin 5A chassis plug 20p
 SA 1862 Line socket for above 23p

PHONO
 Plug plastic 5p
 Plug screened 12p
 Chassis socket 4p

RS8 8 way chassis socket 62p

Jack
 1/8" mono plug 13p
 Plastic 13p
 Screened 21p

STEREO
 Sid stereo plug Plastic 18p
 Screened 30p
 Open mono socket 10p
 Moulded mono socket 4" with 2 break contacts 13p
 Moulded stereo socket 4" with 1 break contacts 18p
 3.5mm plug plastic 9p
 Screened 15p
 open socket 8p

WE KNOW YOU NEED IT!

The MES 1974 CATALOGUE IS STACKED with dozens of tempting new lines. BRIMMING OVER with clear illustrations and detailed data. WE'RE WAITING TO RE-SHOW YOU A COPY. You'll be IMPRESSED with our POST FREE ordering system. EXCITED by our BIG VALUE discount vouchers. STAGGERED by our UNBEATABLE speed of service. Take the first step towards real service NOW! Send ONLY 25p for our beautifully produced catalogue and leave the rest to us!

OMNION GATHERUM

PP3 6, etc. battery clip dual min 9p.
 PP1 9, etc. battery clip separate per pair 6p.
 Pair crocodile clips 1 red, 1 black insulated sleeve 10p.
 Solder Multicore 22 x w.g. 10 metres 20p.
 Silicone grease in special dispenser 20ml 43p.
 Red neon 240V panel mounting 25p.
 Lacing Cord. Strong rayon cored PVC 25m 51p.
 Panel fuse holders 20mm 20p; 14in 35p.

Transformers
 1T700 min. output transformer Pri. 1-2kV Sec. 50 200mW 50p.
Sub-main. Mains Transformer
 6-6V 100mA 95p. 12-0-12V 50mA 95p.
 Size: Both approx. 30 x 27 x 25mm
Min. Mains Transformer
 Size: 46 x 31 x 38mm.
 0-12V 250mA 0-12V 250mA £1.36.

Mains Transformer MT3AT
 Pri. 200-220-240V. Sec. 12-15-20-24-30V 1A £3.31.
Mains Transformer MT206AT
 Pri. 200-220-240V. Sec. 0-15-20V 1A 0-15-20V 1A £3.98.

Hook-up wire, 7 strand 0.2mm. PVC covered tinned copper wire for light general connections up to 1.4A. 11 colours: black, blue, brown, green, grey, orange, pink, red, violet, white, yellow. 10 metres of any one colour 20p. Pack of 11 (1 of each colour) 10m: coils £2.05.

Single core screened 6p per metre.
 Twin individually screened 104p per metre.
 High quality single screened 501 104p per metre. Ideal for high grade audio connections 154p per metre.
 Mains 3-core sub-miniature 1A black PVC covered 19 strand 0.1mm per conductor. 71p per metre.

POTENTIOMETERS

Rotary miniature carbon track 1" spindle

Single gang Lin or Log
 5k, 10k, 25k, 50k, 100k, 200k,
 500k, 1M, 2M (and 1k Lin) 14p

Dual gang (Stereo) without switch Log or Lin 5k to 2M as above 44p

Single gang with DP switch 250V 2A Log or Lin 5k to 2M as above 20p

PRESETS
 Sub-miniature 0-1W Vert or Horiz 100, 250, 500, 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 250k, 600k, 1M 6p

LINEARS

LH0042C. TO99 (TO5). FET 1 p Op Amp	£4.25
LM101A. 8-pin DIL Op Amp	50p
MC1301L. 14-pin Stereo Preamplifier	£1.39
MC1310P. 14-pin DIL. FM Stereo Decoder (no coils needed)	£3.15
MFC4000B. 3W Audio Amp	31p
MFC8010. 8-pin case. 1W Audio Power Amp	£1.20
MFC9020. 10-lead case. 2W Audio Power Amp	£1.37
NE555V. 8-pin DIL. Precision Timer	79p
NE561B. 16-pin DIL. Phase Locked Loop	£4.48
SG1495D. 14-pin DIL. Fair Quadrant Analogue Multiplier	£2.70
µA723C. TO99 (TO5). 2 to 37V Voltage Regulator	80p
µA723C. 14-pin DIL. 2 to 37V Voltage Regulator	80p
µA741C. 8-pin DIL. Op Amp	36p
µA741C. 14-pin DIL. Op Amp	45p
µA747C. 14-pin DIL. Dual Op Amp	£1.05
µA748C. 8-pin DIL. Op Amp	39p
ZN414. TO5. TRF Radio	£1.20

More linears are listed in the 'PE SOUND SYNTHESISER' box above.
 Full data, pin connexions, etc. on nearly all types above in our catalogue. Price 25p.

SWITCHES

Rotary with adjustable stop 1 pole 2 to 12 way; 2 pole 2 to 6 way; 3 pole 2 to 4 way; 4 pole 2 or 3 way, each 32p
 Mains rotary DPDT 250V 2A 20p.

Push to make non-locking 14p

Slide Sub-miniature DPDT 9p

Sub-miniature toggle DPDT (12 x 12.5 x 14mm excl toggle) 250V 3A 70p

Toggle 250V 1.5A with ON/OFF plate 25p.

RESISTORS

Carbon Film 1W 5% 1Ω to 1M; 10% 1.2M to 10M	E12	1p
Carbon Film 1/4W 5% 1Ω to 10Ω; 10% 1.2M to 10M	E12	E12
Carbon Film 1/4W 5% 11Ω to 910k	E12 & E24	1p
Carbon Film 1W 5% 10Ω to 10M	E12	3p
Metal Oxide 1/4W 5% 10Ω to 1M	E12 & E24	4p
Wirewound 2 1/2W 10% 0.2-20ohms to 0.47ohms	E12	12p
Wirewound 2 1/2W 5% 1ohm to 270ohms	E12	12p

E12 values 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades
 E24 values 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades

VAT Please add 10% to the final total.

Post and Packing FREE in U.K. (10p handling charge on orders under 50p.)

Orders and enquiries for catalogues to MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex. Tel. Southend-on-Sea 0702 44101

THE P.E. LIQUID CRYSTAL CLOCK

- 12 or 24 hour operation
- Hours and Minutes to Minutes and Seconds at a touch
- Audible Electronic Alarm
- Liquid Crystal Display



- Visual Alarm Set
- Extra 'Snooze' Time Alarm
- Radio On/off facility
- MOS I.C. Clock Chip

A complete set of parts to build this up-to-the-minute (sorry) project at a special price. All parts available separately. Ask for Price List.

MM5316 Alarm, Clock Chip £16.50
40 pin I.C. Socket 44p
AN4132
4 digit display (inc. socket) £14.37
LM3900 quad amplifier 77p

RS Reed Relay 80p
Dil Switch 85p
Xtal Mike insert 44p
14 pin I.C. Socket 15½p

NEW
Mullard
LP1400
Stereo Decoder
Module, £4.96
P. & P. 15p. Ex Stock.
Leaflet 10p. If pur-
chased with LP1185 & 6.
normally £13.96—now £13.49.
Dual 555 Timer 2556 only £1.65

VAT INCLUSIVE PRICES



OVERSEAS CUSTOMERS DEDUCT
ONE ELEVENTH.

P & P
10p

10 WATTS PER CHANNEL RMS STEREO AMPLIFIER

at less than 0.1% distortion. Max. RMS output in excess of 15 watts per channel.

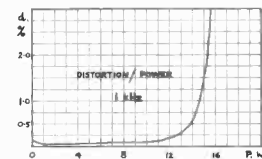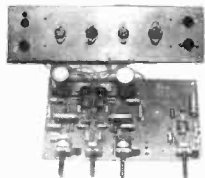- * 4-16 ohm Load
- * 15-50 kHz (—1dB)
- * 40 dB NFB
- * 150 mV input



Completely assembled PCB using top grade components (plus backplate/heatsink) including balance volume and tone controls plus mono-stereo switch. Operates from 22-24V d.c. Board also includes a single 2-stage mic. or guitar pickup preamp. (2 x BC149). Instructions are included for a simple mod. to adapt this for stereo operation giving 150mV at 1M ohm sensitivity. Full circuit supplied.

FANTASTIC AND UNREPEATABLE BARGAIN.
£9.90 plus 60p P. & P., inc. VAT. Power supply components to operate from the mains available, add £2.90 inc. VAT.

EDRICK ELECTRONICS LTD.

(DEPT. P6)

164 HIGH STREET, BARNET, HERTS.



MULTIMETER Model C-7081
GN Range Doubler 50,000 ohm/volt
High Sensitivity Meter
£14.40.

TAPE RECORDER LEVEL METER

500µA, 70p



CARDIOID DYNAMIC MICROPHONE

Model UD-130. Fre-
quency response 50-
15,000c/s. Impedance
Dual 50K and 600 ohms,
£6.40.



4½ in x 3½ in **METER.** 30µA,
50µA or 100µA, £3.65.

MULTI-METER

Model 200H
20,000 ohm/volt,
£6.60.



3 WATT STEREO AMPLIFIER
£4.30

All above prices include 10% V.A.T. Please add 10p for P. & P. on orders under £5. LARGE S.A.E. for List No. 8. Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate • Bolton • Lancs. BL2 1BA

C. T. ELECTRONICS

267 Acton Lane, London W4 5DG

Tel. 01-994 6275

MAIL ORDER DEPT./REGISTERED OFFICE/COMPONENT COUNTER

semiconductors

AC107	35p	BCY33	45p	MJE370	75p	OC77	40p	ZTX504	50p	2N2907	30p
AC125	25p	BCY34	45p	MJE371	80p	OC81	25p	ZTX531	30p	2N2906G	13p
AC126	25p	BCY38	60p	MJE520	60p	OC83	25p	ZTX550	30p	2N3053	25p
AC127	25p	BCY39	85p	MJE521	75p	OC84	25p	1N914	8p	2N3054	60p
AC128	25p	BCY55	£1.20	MJE2955	£1.95	OC139	40p	1N916	8p	2N3055	65p
AC176	25p	BCY70	22p	MJE3055	85p	OC140	25p	1N4001	7p	2N3232	70p
AC187	25p	BCY71	20p	MM1613	43p	OC170	25p	1N4002	8p	2N3440	60p
AC188	30p	BCY72	20p	MM1712	60p	OC171	25p	1N4003	8p	2N3702	14p
AD140	55p	BD121	75p	MPF102	45p	OC200	50p	1N4004	10p	2N3703	12p
AD149	65p	BD123	75p	MPF103	45p	OC201	60p	1N4005	12p	2N3704	12p
AD161	44p	BD124	75p	(2N5457)	35p	OC202	75p	1N4006	13p	2N3705	12p
AD162	44p	BD131	75p	MPF104	45p	OC205	80p	1N4007	14p	2N3706	12p
AF114	25p	BD132	75p	(2N5458)	40p	TIP29A	50p	1N4148	7p	2N3707	12p
AF115	25p	BD153	75p	MPF105	45p	TIP30A	60p	2N696	30p	2N3708	12p
AF116	25p	BD156	75p	(2N5459)	40p	TIP31A	65p	2N697	25p	2N3709	14p
AF117	25p	BDY11	£1.40	NKT135	35p	TIP32A	75p	2N698	25p	2N3771	£2.80
AF118	50p	BF152	20p	NKT222	25p	TIP33A	£1.05	2N706	12p	2N3772	£3.00
AF172	30p	BF194	14p	NKT401	75p	TIP34A	£1.55	2N706A	15p	2N3773	£3.40
BA102	30p	BF195	15p	NKT404	80p	TIP35A	£3.35	2N708	15p	2N3819	35p
BA112	60p	BF196	15p	NKT773	25p	TIP36A	£3.65	2N930	20p	2N3820	55p
BA114	18p	BFX29	30p	NKT774	25p	TIP41A	75p	2N1132	25p	2N3866	85p
BC107	14p	BFY84	30p	OA5	25p	TIP42A	95p	2N1302	25p	2N3904	22p
BC108	14p	BFX85	30p	OA10	50p	TIP29B	60p	2N1303	20p	2N3905	22p
BC109	14p	BFX86	30p	OA47	10p	TIP30B	70p	2N1304	25p	2N4058	12p
BC109c	16p	BFX87	30p	OA70	12p	TIP31B	75p	2N1305	25p	2N4059	12p
BC147	12p	BFX88	30p	OA81	10p	TIP32B	85p	2N1306	25p	2N4060	12p
BC148	12p	BFY44	50p	OA90	10p	TIP33B	£1.20	2N1307	35p	2N4061	14p
BC149	12p	BFY50	25p	OA91	10p	TIP34B	£1.75	2N1308	35p	2N4126	17p
BC157	14p	BFY51	25p	OA200	10p	TIP35C	£2.90	2N1309	30p	2N4286	15p
BC158	14p	BFY52	25p	OC202	10p	TIP36B	£3.80	2N1613	25p	2N4287	15p
BC159	14p	BFY53	25p	OA210	35p	TIP29C	75p	2N1711	25p	2N4288	15p
BC169c	15p	BFY90	60p	OA211	35p	TIP30C	85p	2N2160	65p	2N4289	15p
BC182	13p	BSW63	60p	OC16	90p	TIP31C	90p	2N2217	25p	2N4290	15p
BC183	13p	BSW68	75p	OC19	85p	TIP32C	£1.10	2N2218	30p	2N4444	£1.90
BC184	13p	BSY95a	12p	OC22	55p	TIP33C	£1.35	2N2219	35p	2N4871	35p
BC212	15p	BY127	20p	OC26	65p	TIP34C	£2.00	2N2222	25p	2N5191	96p
BC213	15p	BY164	60p	OC28	65p	TIP35C	£3.25	2N2222A	25p	2N5194	£1.10
BC214	15p	IS103	15p	OC35	60p	TIP36C	£4.25	2N2398	70p	40360	50p
BC238	14p	MJ340	50p	OC44	20p	TIS50	40p	2N2646	50p	40361	50p
BC239	14p	MJ481	95p	OC45	20p	ZTX107	15p	2N2846	£1.50	40362	50p
BCY30	40p	MJ2801	£1.20	OC71	17p	ZTX300	15p	2N2904	30p		
BCY31	55p	MJ2901	£2.00	OC75	25p	ZTX500	16p	2N2905	45p		
BCY32	95p	MJE340	£2.00	OC76	25p	ZTX501	20p	2N2906	25p		

Semiconductor QUANTITY DISCOUNTS—12 + 10%, 25 + 15%, 100 + 20% mixed types, transistors and I.C.s Larger quantity discounts Phone for details

74 SERIES I.C.'s (TTL)

SN7400	28p	SN7411	24p	SN7430	30p	SN7446	£2.00	SN7481	£1.25
SN7401	38p	SN7412	42p	SN7432	48p	SN7447	£1.75	SN7482	40p
SN7402	28p	SN7413	60p	SN7433	70p	SN7448	£2.00	SN7483	£1.00
SN7403	28p	SN7416	40p	SN7437	70p	SN7450	25p	SN7484	95p
SN7404	40p	SN7417	40p	SN7437	70p	SN7451	25p	SN7486	45p
SN7405	40p	SN7420	20p	SN7438	65p	SN7454	20p	SN7490	75p
SN7406	40p	SN7422	48p	SN7440	35p	SN7460	25p	SN7491	£1.20
SN7407	56p	SN7423	52p	SN7441	75p	SN7470	30p	SN7492	75p
SN7408	55p	SN7425	48p	SN7442	75p	SN7472	30p	SN7493	75p
SN7409	48p	SN7427	48p	SN7443	£1.05	SN7473	57p	SN7494	80p
SN7410	28p	SN7428	50p	SN7445	£2.00	SN7474	50p	SN7495	80p
				SN7446	£2.00	SN7475	96p	SN7496	£1.00
				SN7480	80p	SN7476	60p	SN7497	£6.25
						SN7478	80p	SN74100	£2.50

TRIACS

TXL228B BA 400V	95p
SC40D	£1.40
SC40E	£1.65
SC45D	£1.70
SC45E	£2.10
SC50D	£2.42
SC50E	£2.70
DIAC	25p

VEROBOARD

0 1 0 15	
2 1/2 - 3 1/2	24p 19p
2 1/2 - 5	27p 28p
3 1/2 - 3 1/2	27p 28p
3 1/2 - 5	31p 31p
17 - 2 1/2	89p 68p
17 - 3 1/2	£1.10 87p
17 - 5 (plane)	£8.90 90p
Pin insertion tool	57p 57p
Spot face cutter	46p 46p
Pk 36 Pins	80p 20p

S.C.R.'s

CRS1 05	40p
CRS1 10	56p
CRS1 20	60p
CRS1 40	65p
CRS1 60	90p
CRS1 10	62p
CRS3 20	62p
CRS3 40	90p
CRS7 400	£1.00
CRS16.100	85p
CRS16.200	90p
CRS16.600	£1.60
C106B	45p
C106D	70p
40669	90p
TIC44	35p
2N4444	£1.90

V41 Vu meter

£2.50
The V41 is calibrated -20 to -3 and 0-100% making it suitable for use as a recording level meter or as a power output indicator.
Sensitivity 30 µA Internal resistance 600 ohms Dimensions 40 x 40 x 29mm

3A 200V Rec Diode 25p

LINEAR I.C.'s	
LM309K 5V 1A voltage reg	£2.10
LM723C 2-37V 150mA voltage reg	£1.05
MFC4000 250mW audio	60p
TBA800 5W audio	£1.50
7090 OP Amp DIL TO99	45p
741C OP Amp 8 14 DIL TO99	55p
748C OP Amp DIL	75p
747C Dual OP Amp	£1.28
ZN414 Radio I.C.	£1.25
TAD100 Radio I.C. inc filter	£1.90
CA3014	£1.55
CA3018	£1.00
CA3028	£1.20
CA3036	£1.00
CA3046	95p
CA3048	£2.35
CA3075	£1.80
CA3090C	£4.85
MC1303L	£2.28

D.I.L SKTS

3 p	18p
4 p	16p
16 pin	18p

V.A.T.

Unless otherwise stated all prices are EXCLUSIVE of V.A.T. Please add 10% to all orders. Carriage orders under £5 - 20p Over £5 post free U.K.

ZENER DIODES

BZY88 series 400mW
3 3V-33V 5%
1 SW range 25p
10W range 45p

L.E.D.

TIL209	28p
HP5082	28p
MA2082R	25p
L D R	
ORP12	60p
OC71	90p

POWER SUPPLY. 12V 6.5A

Stabilised Power Supply. Contains 18 5V 8.5A sec Transformer 4 x 4000µF 25V Mullard capacitors 2 x 2N3055 on 2 Rad-point heatsinks 12A 120V Bridge rectifier stabilised p.c.b circuit diagram The parts alone are worth the asking price of £13 each inc carriage

BRIDGE RECTIFIERS

WO2 1A 200V	38p
BY164 1.4A 200V	57p
MDA952 2.6A 100V	80p

WAREHOUSE

20-24 BEAUMONT ROAD, W.4
SURPLUS COMPONENTS TEST EQUIPMENT etc etc

THOUSANDS OF BARGAINS

Test Equipment * Oscilloscopes * Signal Generators * Counters
Cabinets * Bridges * Meters * Transmitters * Receivers * Power Supplies
Laboratory Equipment * Galvanometers * Audio Equipment * Video
Equipment * Meters * Battery Chargers * Motors * Etc * Etc.

20 TONS OF ELECTRONIC EQUIPMENT

Resistors * Relays * Capacitors * Switches * Transformers * Meters
Potentiometers * Component Panels * Semiconductors * Cable * Valves
Etc * Etc.

Regret no lists available Personal callers only Cash and Carry only

AUDIO ACCESSORY SHOP

17 TURNHAM GREEN TERRACE, CHISWICK, W.4

VALVE AMPLIFIERS

5 Watt	£12.50	50 Watt	£36.25
15 Watt	£24.50	150 Watt	£75.90
30 Watt	£29.50	500 Watt	£124.50

TRANSISTOR AMPLIFIERS

FAL Phase 50W	£39.93	FAL Phase 100W	£69.95
---------------	--------	----------------	--------

DISCO CONSOLES

FAL Disco Mk 2	£82.99	FAL Power Disco (with 70W rms Amp)	£123.75
----------------	--------	------------------------------------	---------

HEAVY DUTY LOUDSPEAKERS

* SPECIAL OFFER PRICE *	3 channel sound-light	£22.50
15 in 70W E.M.I. 8 ohm	Oilwheel 6in dia	£5.25
Decca Bin. 10 watt Hi-Fi Speaker	Suitable 4rpm motor	£1.00
plus matching tweeter £7.50 complete	Strobe 4 Joule	£25.00
Suitable 2-way cross-over	Single flash box (100W Red Blue Gn Yel)	£7.50
£1.21	Triple flash box	£16.25

DISCO LIGHTING

Sound-lighting module	£7.90	150W Projector and Wheel	£25.00
-----------------------	-------	--------------------------	--------

TEAK VENEERED SPEAKER CABINETS

For 8" - 5in Speaker	Size 7 1/2in x 11 1/2in x 5 1/2in	£3.50
For 8in - Tweeter	9 1/2in x 13 1/2in x 5 1/2in	£5.00
For 13" - 8in	10 1/2in x 17in x 6in	£5.75
For 13" - 8in - Tweeter	12in x 18 1/2in x 8 1/2in	£7.50
For 12in - Tweeter	15 1/2in x 18in x 8 1/2in	£9.00

REXINE COVERED SPEAKER CABINETS

Suitable for P.A. or DISCO use takes 12in speaker unit Size approx 18in x 18in x 8in £9.00

SPEAKER CLOTH

Available in Black or Green approx width 54in £1.75/yard


HEADPHONES

Type H-200 Features Mono stereo switch Volume controls on each channel Freq response 20-20,000Hz Impedance 4-16 ohms £4.50

ALUMINIUM BOXES

AB7	2 1/2 x 5 1/2 x 1 1/2in	50p	AB14	7 x 5 x 2 1/2in	84p
AB8	4 x 4 x 1 1/2in	50p	AB15	8 x 6 x 3in	£1.08
AB9	4 x 2 1/2 x 1 1/2in	50p	AB16	10 x 7	

BIG Discounts

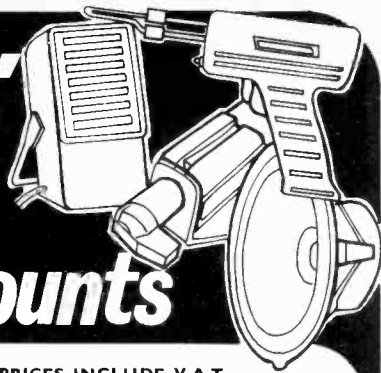

ALL PRICES INCLUDE V.A.T.


SPEAKER BARGAINS		GOODMANS	
EMI 13in x 8in 3, 8 or 15 ohm	£	6in 8 ohm Dual cone	1.80
Plain	2.05	8in Dual cone 8 ohm	2.40
With Co-Axial Tweeter	2.20	CELESTION 8in, 15 ohm	1.55
Twin Tweeter	3.55	ADASTIA 10in, 8 or 15 ohm.	3.05
Type 350, 8 or 15 ohm, 20W	7.50	BAKER GROUP 25 12in, 8 or 15 ohm, 25W	7.85
6in, 8 ohm, 10W	2.30		0.25
8in, 8 ohm, 10W	3.75		0.85
12in, 8 ohm, 20W	5.50		0.50
8in x 5in, C/Mag, 5W	1.20		0.10
8in x 5in, Dual cone 8 ohm, 10W	2.45		
ELAC 8in 8 ohm Dual cone	2.25		
ELAC 10in 8 ohm Dual cone	3.35		
TWEETER AND CROSSOVER		Dome Tweeter	
EMI 3in, 3 or 8 ohm C/Mag	1.00	8 ohm, 30W	4.85
Cone Tweeter 8 or 15 ohm, 10W	2.40	Crossovers CN23 (3 ohm), CN28 (8 ohm), CN216 (16 ohm)	1.05
Cone Tweeter 8 ohm, 3W	1.40		0.10
Horn Tweeter 8 ohm, 20W	5.85		
KIT FORM CABINETS, TEAK VENEER.		13in x 8in cutout	
8in x 5in or 6in and 3in cutout	2.45		3.50
17in x 10in x 9in with 8in or			
MICROPHONES		TW20P	
CM59 Crystal Hand	0.50	CONDENSER MIK R. 600 ohm, uni-dir	7.90
CM70 Planet stick metal, switch crystal	1.55	Cassette Stick Mike with R. Control on/off switch (2.5 and 3.5m J/Ply)	1.35
DM160 Dynamic uni-dir, ball metal	3.95		0.15
UD130 50K/600 ohm, uni-dir, ball metal	5.50		
SOLDERING IRONS		spare Bill, etc.)	
ANTEX CN240 15W	1.60	N25 25W (low leakage)	1.80
SK1 Kit (15 watt iron, 2			0.10
CARTRIDGES		BSR SC5M Stereo ceramic	
ACOR GP91/38C or GP91/38C Stereo comp	1.00	SN3H Stereo crystal	1.60
GP93/1 Stereo crystal	1.35	SN3M Stereo crystal	1.60
GP94/1 Stereo crystal	1.75	X5M Mono/stereo	1.25
GP95/1	1.35	X5M Mono/stereo	1.25
GP96/1	1.75	GOLDRING G800	3.85
GP101	0.75	G850	2.95
GP104	1.60	G800E	7.50
SONOTONE 9THAC Stereo ceramic, diam.	1.80	STYL FOR ABOVE P. & P.	0.05
9-TI Stereo crystal	0.80	Sapphire 35p D. Diamond	1.25
BATTERY ELIMINATORS		GOLDRING C800/G850	
340V input 4, 7.5 or 9.300mA	2.20	G800E	1.95
12V d.c. input (fits in car lighter socket) 6, 7.5 or 9 d.c. output at 300mA			1.95
TAPES		ONLY £2.55	
5in	Std. 45p	LP 55p	DP 70p
5in	55p	65p	95p
LOW NOISE CASSETTES		Cassette Head Cleaner	
C60	1-5 35p	8-10 33p	11-20 30p
C90	45p	43p	40p
C120	55p	52p	50p
PLASTIC LIBRARY CASES for		7in Reels	
5in Reels	0.18		0.25
5 1/2in Reels	0.22		0.10
BIB ACCESSORIES		BUDGET SPEAKER SYSTEMS	
Tape Editing Kit, Ref. 23	1.30	1. Pr. of 10watt 8ohm 2 speaker system in de luxe teak veneer cabinet 18" x 11" x 9" wired, inc. plugs. £25.00 per pair.	
Recording Tape Splicer, Ref. 20	1.15	2. Pr. of 20watt 8ohm 2 speaker system freq. response 50c.p.s. to 17,000c.p.s. Teak veneer cab. 21" x 12" x 6" with 12ft. cable and plugs. £29.95 per pair.	
Cassette Tape, Editing, Ref. 24	1.40		
Cassette Salvage Kit, Ref. 29	0.40		
12" Cassette Case, Ref. 34	1.00		
Stylus Balance, Ref. 32A	1.15		
Spirit Level, Ref. 46	0.50		
Hi-Fi Stereo Test Cassette	1.80		
Groove-Kleen Record Cleaner	1.90		
	P. & P.		0.10

Send 25p for COMPLETE CATALOGUE, refundable upon first order. ALL OUR MERCHANDISE IS FULLY GUARANTEED

Riversdale Electronics
Mail Order Department PE/6
P.O. Box 470, Manchester M60 4BU

PHOTOELECTRIC KIT

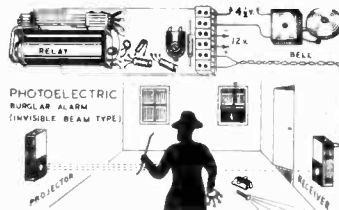CONTENTS: P.C. Chassis Board, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, Diode, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation with a few additional components.



PHOTOELECTRIC KIT £2-85

Postage and Pack. 15p (U.K.)
Commonwealth
SURFACE MAIL 25p
AIR MAIL £1-40
Australia, New Zealand,
S. Africa, Canada and U.S.A.
Also Essential Data Circuits
and Plans for Building
10 Advanced Designs

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photo-cell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.
CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, screws, nails, brackets, building plans, etc. Price £1-45. Postage and Pack. 10p (U.K.). Commonwealth: Surface Mail 20p, Air Mail 50p.

LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price £2-10. Postage 15p (U.K.). Commonwealth: Surface 20p, Air Mail £1-15.

BIOFEEDBACK AMPLIFIER KIT

Tunable, General-Purpose, Interference-Rejecting Differential Amplifier for experimental investigation of signals produced by the brain, heart and muscles. When used with an oscilloscope, or aural indicator, it enables you to monitor your brainwaves, learn to relax, meditate, etc.
CONTENTS: All Capacitors, Resistors, Pots, Semiconductors, I.C., Electrodes, Leads, Chassis, Case, Batteries, Plans and Instructions. Price £4-75 postage and pack. 25p (U.K.). Commonwealth: Surface 30p, Air Mail £1.

ALPHA-BETA-THETA BRAINWAVE MONITOR KIT

Aural Brainwave Indicator for use with a Biofeedback Amplifier. Converts subsonic brain frequencies into audible signals for easy recognition.
CONTENTS: Resistors, Pots, Capacitors, Transistors, Diodes, Leads, Chassis, Case, Earphone, Battery, Plans and Instructions. Price £3-25, postage and pack. 15p (U.K.). Commonwealth: Surface 25p, Air Mail 75p.

YORK ELECTRICS Mail Order Dept.
335 BATTERSEA PARK ROAD, LONDON, S.W.11

Send S.A.E. for full details, a brief description of all Kits and Projects



AMAZING MINI-DRILL

FOR PRECISION MODEL WORK




+ 6 TOOLS

Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4 1/2 volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) £6-35 p.p. 13p. De Luxe Professional Kit with 17 tools £9-40 p.p. 23p. Prices include V.A.T.

Money ref. g'tee. **MERLIN SUPPLY CO.**

Dept. PE6D Nailsea, Bristol BS19 2LP

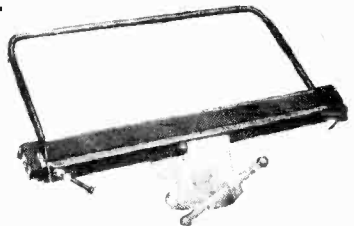PARKERS SHEET METAL FOLDING MACHINES HEAVY VICE MODELS



With Bevelled Former Bars

No. 1. Capacity 18 gauge mild steel x 36in. wide ... £21 carr. free
No. 2. Capacity 18 gauge mild steel x 24in. wide ... £15 carr. free
No. 3. Capacity 16 gauge mild steel x 18in. wide ... £15 carr. free
Also new bench models. Capacities 36in. x 18 gauge £40, 24in. x 16 gauge £38. Carriage free. Add 10% VAT to total price of machine.

End folding attachments for radio chassis. Tray and Box making. Steel Angle 36in. model, 40p per ft. Other models 30p. The two smaller models will form flanges. As supplied to Government Departments, Universities, Hospitals.

One year's guarantee. Money refunded if not satisfied. Send for details.

A. B. PARKER, Folding Machine Works, Upper George St., Heckmondwike, Yorks. Telephone 403997

VARIABLE VOLTAGE TRANSFORMERS

**INPUT 230/240V a.c. 50/60 OUTPUT
VARIABLE 0-260V**

All Types

SHROUDED TYPE

0.5 KVA (2 amp) (MAX) £10.00
1 KVA (5 amp) (MAX) £14.70
2 KVA (10 amp) (MAX) £28.10
3 KVA (15 amp) (MAX) £31.25
4 KVA (20 amp) (MAX) £72.50
37.5 amp (MAX) £102.50

CARRIAGE AND PACKING
EXTRA



L.T. TRANSFORMERS

All primaries 220-240V

Type No.	Sec. Taps	Price	Post
1	30, 32, 34, 36V at 5A	£6.90	+45p
2	30, 40, 50V at 5A	£9.15	+60p
3	10, 17, 18V at 10A	£7.20	+50p
4	6, 12V at 20A	£8.60	+60p
5	17, 18, 20V at 20A	£9.15	+60p
6	6, 12, 20V at 20A	£8.65	+60p
7	12, 20, 24V at 10A	£6.75	+50p
8	4, 6, 24, 32V at 12A	£8.60	+60p
9	6 and 12V at 10A	£4.30	+40p

VOLTAGE CHANGING TRANSFORMER

M.f.g. to highest W.D. spec. Auto wound, and tapped 0-130-160-200-250 at least 2kVA. Can also be used as 230-240V input. 115V out for U.S.A. equipment, or reverse to obtain 240V from 115V. The ideal transformer for making up solid state constant voltage unit, by use of taps the following voltages may be obtained 30-40-50-70-90V at 10 amps. Weight 40lb. length, 260mm, height 190mm, width 230mm. In original maker's wooden case, £8. Carr. £1.


PARVALUX TYPE SD19 230/250 VOLT A.C. REVERSIBLE GEARED MOTORS

30 r.p.m. 40 lb. ins. Position of drive spindle adjustable to 3 different angles. Ex-equi-pment. Tested and in first-class running order. A really powerful motor offered at a fraction of makers' price. £6.30. Post 60p.



A.C. MOTOR 'Mfg. by AEI'

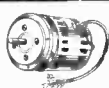Smooth running, powerful, continuously rated, reversible motor. 230/250V a.c., 50 cycle 1/50 H.P., RPM 900, 0.25A. £3.50 post 50p.



METERS NEW! 2 1/2 in. Flush

round. Available in D.C. Amps 1, 5, 10, 15, 20 or A.C. Amps 1, 5, 10, 15, 20. Voltmeter 0-300V A.C. All types £2. Post 15p.



600 WATT DIMMER SWITCH

Easily fitted. Fully guaranteed by makers. Will control up to 600W of lighting except fluorescent at mains voltage. Complete with simple instructions. £2.75. Post 25p.



2000 WATT POWER CONTROL

For Power tools, Heating, Sewing Machines, Lighting, etc. £8.00. Post 27p.

VENNER TIME SWITCH TYPE MSQP

200/250 Volt 2-ON/2-OFF every 24 hours at any manually pre-set time. 20 amp contacts. Fitted diecast case. Tested and in perfect condition £4.75. Post 25p.



FOOT SWITCH

Suitable for Motors, Drills, etc., etc. 5 amp. 250 volt. Price 75p. Post 15p.



UNISELECTOR SWITCHES

NEW 4 Bank 25 Way,

24V d.c. operation. £6.90. Post 30p.

6 Bank 25 Way, 24V d.c. £7.90. Post 30p.

8 Bank 25 Way, 24V d.c. operation. £9.50. Post 40p.



MINIATURE UNISELECTOR SWITCHES

2 Bank, 12 position, 24 volt D.C. operation, full wiper with ancillary contacts. NEW Price £2.50. Post 20p. As above but with 5 Bank, 12 position. Price £3.50. Post 20p.



STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT
Speed adjustable 1 to 30 flash per sec. All electronic components including Xenon Tube and instructions £6.30. Post 30p.

INDUSTRIAL KIT

Ideally suitable for schools, laboratories, etc. Speed adjustable 1-80 f.p.s. Approx. 1/2 output of Hy-Light. Price £12.00. Post 50p.

HY-LIGHT STROBE MK III

For use in large rooms, halls and utilises a silica tube, printed circuit. Speed adjustable 0-20 f.p.s. Light output greater than many (so called 4 Joule) strobes. £12. Post 50p.

THE 'SUPER' HY-LIGHT KIT

Approx. four times the light output of our well proven Hy-Light strobe.

- Variable speed from 1-13 flash per sec.
- Reactor control circuit producing an intense white light. ONLY £20. Post 75p.

ROBUST, FULLY VENTILATED METAL CASE. For Hy-Light Kit including reflector £5.75. Post 25p.

Super Hy-Light case including reflector £8. Post 60p.

7-inch POLISHED REFLECTOR

Ideally suited for above Strobe kits. Price 55p. Post 15p.

COLOUR WHEEL PROJECTOR

Complete with oil-filled colour wheel. 100 watt lamp. 200/240V A.C. Features extremely efficient optical system. £18.50. Post 50p.

6 INCH COLOUR WHEEL

As used for Disco lighting effects, etc. Price £4.50. Post 30p.



BIG BLACK LIGHT

400Watt. Mercury vapour ultra violet lamp. Powerful source of u.v. Innumerable industrial applications also ideal for stage, display, discos, etc. P.F. ballast is essential with these bulbs. Price of matched ballast and bulb £16. Post £1. Spare bulb £4. Post 40p.



BLACK LIGHT FLUORESCENT U.V. TUBES

4ft-40 watt. Price £5.50. Post 30p. 2ft 20 watt, £4.25. Post 25p. (For use in standard bi-pin fittings.)

MINI. 12in 8 watt, £1.60. Post 15p. 9in 6 watt, £1.30. Post 15p. Complete ballast unit and holders for 9in and 12in tube. £1.70. Post 25p. (9in and 12in measures approx.)

AUTO FADE

COLOUR BLEND MODULE

Will control up to 750W of lighting. Automatic fade-up, fade-down at a manually pre-selected timing, which may be varied between 1 second to 1 minute. Based on 10 amp triac for maximum reliability. Ready built with switch and Time Control, on 4 1/2 x 5 1/2 inch P.C. board. Three modules or more can be sequenced to obtain fantastic colour blending effects. Price £12.50. Post 30p per module.

PROGRAMME TIMERS

230/240V a.c. 15 r.p.m. Motors. Each cam operates a c/o micro switch. Ideal for lighting effects, animated displays, etc. Ex equipment tested.

4 cam model. £2.50 post 30p.
6 cam model. £3.25 post 30p.
12 cam model. £4.00 post 35p.



TRIACS

GENERAL ELECTRIC POWER-GLAS TRIACS

10 amp. Glass passivated plastic triac. Latest device from U.S.A. Long term reliability. Type SC146D 10 amp, 400 PIV. £1. Post 5p. Type SC146E 10 amp, 500 PIV. £1.30. Post 5p. (Inclusive of data and application sheet.) Suitable Diac 18p.

All prices are subject to

10% VAT. (10p in the £)

To all orders add 10% VAT to total value of goods including carriage/packaging.

Superior Quality Precision Made NEW POWER RHEOSTATS



New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.

25 WATT 10/25/50/100/250/300/500/1k/ohm

£1.15. Post 10p.

50 WATT 1/5/10/25/50/100/250/500/1k/1.5k/ohm

£1.60. Post 10p.

100 WATT 1/5/10/25/50/100/250/500/1k/1.5k/2.5k/3k/5k/ohm

£2.35. Post 15p.

Black Silver, Skirted knob calibrated in Nos. 1-9. 1 1/2 in. dia. brass bush. Ideal for above Rheostats.

22p each.

RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

Col. (1) Coil ohms	1	2	3	4
Col. (2) Working d.c. volts	52	4-6	6M	60p*
Col. 3	58	5-9	6 c/o	80p
Contracts	150	4-9	2 c/o	70p*
Col. (4) Price	185	8-12	6M	60p*
Col. (5)	308	9-14	4 c/o	75p*
Col. (6)	700	16-24	4M 2B	60p*
Col. (7)	700	16-24	4 c/o	80p*
Col. (8)	700	6-12	1 c/o HD	70p*
Col. (9)	700	20-30	6 c/o	50p*
HD=	2,500	31-43	2 c/o HD	60p*
Heavy duty	2,500	36-45	6M	60p*
Incl. Base	2,400	30-48	4 c/o	60p
All prices incl. P. & P.	5,800	24-26	2 c/o	60p*
	9,000	40-70	2 c/o	60p*
	15k	85-110	6M	60p*

6 VOLT D.C. 1 make contacts 35p. Post 5p.

6 VOLT D.C. 2 make contacts 75p. Post 5p.

9 VOLT D.C. RELAY

3 c/o 5 amp contacts. 70 ohm coil. 75p. Post 5p.

12 VOLT D.C. RELAY

3 c/o 5 amp contacts. 120 ohm coil. 75p. Post 5p.

24 VOLT D.C. 3 c/o 75p. Post 5p.

ITT LOW PROFILE RELAY

500 ohm coil, 12-24 volts D.C., 4 c/o. Price 85p. Post 5p each.



CLARE-ELLIOTT TYPE RP7641 G8

Miniature relay. 675 ohm coil. 24 Volt D.C. 2 c/o. 70p post paid.

100 VOLT A.C. 2 c/o sealed type, octal base £1. Post 10p.

24 VOLT A.C. Mfg. by ITT 2 h.d. c/o contacts. 55p. Post 5p.

240 VOLT A.C. RELAY. Mfg. by ITT. 240V A.C. 10 amp h.d. c/o contacts. Octal plug in base. (Similar to illustration below). Price 75p. Post 5p.

HEAVY DUTY A.C. SEALED RELAYS

230/240 V 2 c/o. 20 amp contacts. 110 Volt. 2 c/o 20 amp contacts. Either type £1.25. Post 10p.



DRY REED RELAYS

Mfg. by ERG. 12 volt d.c. encapsulated. Single c/o 65p, post paid. 2 c/o 85p, post paid. STC 280 ohm coil/6/12V d.c. 3 make metal shrouded. 60p post paid.

Other types available, state your requirement.

"HONEYWELL" PUSH BUTTON, PANEL MOUNTING MICRO SWITCH ASSEMBLY

Each bank comprises a c/o rated at 10 amps 240V A.C. Black knob in fixing hole in ONE bank 30p; TWO bank 40p; THREE bank 50p. Quote for quantity.



HIGH VISIBILITY PANEL MOUNTING LED'S

0.25 inch mounting, 0.16 inch lens. Typical parameters 2V, 20M amps all type. Supplied complete with snap-in mountings and data. Red 4 for £1, Green 3 for £1, Yellow 3 for £1. Post 5p. (in order) (£1).

'HONEYWELL' LEVER OPERATED MICROSWITCH

10 amps 250 volt A.C. c/o contacts. In maker's carton. PRICE: 10 for £1.90. Post 15p.



INSULATION TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L.8in, W.4in, H.6in, weight 6lb. 1,000V, 1,000 megohms, £34. Post 60p. 500V, 500 megohms, £28. Post 60p.



24 VOLT DC SOLENOIDS

Unit containing 1 heavy duty solenoid approx. 25lb pull 1 inch travel. Two x approx. 1lb pull 1/2 inch travel. 6 approx. 4oz. pull 1/2 inch travel. One 24 volt d.c., 1 heavy duty single make relay. Price £2.50 P+p 60p. ABSOLUTE BARGAIN.

Personal callers only. Open Sat.

**9 LITTLE NEWPORT STREET
LONDON WC2H 7JJ
Phone 01-437 0576**

All Mail Orders—Callers—Ample Parking
**Dept. PE6, 57 BRIDGMAN ROAD
CHISWICK, LONDON W4 5BB
Phone 01-995 1560
Showroom open Mon-Fri.**

**SERVICE
TRADING CO**

The largest selection

EX COMPUTER BOARDS

Packed with transistors, diodes, capacitors and resistors - COMPONENT VALUE £1-50. 3 for ONLY 55p + p & p 30p.
SPECIAL. As above PLUS Power Transistors ONLY 55p each + p & p 15p.
STABILISED POWER MODULES Complete with circuit diagrams, etc. 89p each + p & p 15p.
PAXOLINE BOARDS 7 1/2 x 9" approx. 4 for 30p + p & p 20p.

FIBRE-GLASS PRINTED CIRCUIT BOARDS

16 1/2 x 4" approx. 2 for 55p

DECON-DALO 33pC Marker

Each resistant printed circuit marker pen. 90p each

VEROBOARDS

Packs containing approx. 50sq. ins. various sizes, all 0.1 metric 55p

REPANCO CHOKES & COILS

RF Chokes
CH1 2.5mH 25p CH2 5.0mH 25p
CH3 7.5mH 25p CH4 10mH 25p
CH5 1.5mH 25p

COILS
DRX1 Crystal set 31p DRR2 Dual range 45p

COIL FORMERS & CORES

NORMAN 1" Cores & Formers 7p
2" Cores & Formers 8p

SWITCHES

DP/DT Toggle 25p SP/ST Toggle 18p

FUSES

1 1/2" and 20mm. 100mA, 200mA, 250mA, 500mA, 1A, 1.5A, 2A
QUICK-BLOW 4p ea. ANTI-SURGE 5p ea.

EARPHONES

Crystal 2.5mm plug 38p
Crystal 3.5mm plug 35p
8 ohms 2.5mm plug 22p
8 ohms 3.5mm plug 22p

DYNAMIC MICROPHONES

B1223 200 ohms plus on/off switch and 2.5mm and 3.5mm plugs £1-80

3-WAY STEREO HEADPHONE JUNCTION BOX

H1012 £1-87

2-WAY CROSSOVER NETWORK

K4007 80 ohms Imp. Insertion loss 3dB £1-21

SELECTED RESISTORS

R1. Our mix. 1 watt carbon. 50 for 55p

CAR STEREO SPEAKERS

(Angled) £3-85 per pair.

BI-PAK

CATALOGUE AND LISTS

Send S.A.E. and 10p.

INSTRUMENT CASES



(Black Vinyl covered)

No.	Length	Width	Height	Price
BV1	8"	4"	3"	80p
BV2	11"	6"	3"	£1-20

ALUMINIUM BOXES

BA1	5 1/2"	4"	2 1/2"	42p
BA2	4"	4"	2 1/2"	41p
BA3	4"	4"	2 1/2"	41p
BA4	5 1/2"	4"	2 1/2"	47p
BA5	4"	4"	2 1/2"	41p
BA6	3"	4"	2 1/2"	34p
BA7	7"	5"	3"	66p
BA8	8"	6"	3"	84p
BA9	8"	4"	3"	54p

VISIT OUR COMPONENT SHOP

18 BALDOCK ST., WARE, Herts. (A10)

Open Mon.-Thurs. 9.15-6 p.m. Sat. 9.15-5.30. Late Night Shopping until 7 Fri. Tel. 61693

BIB HI-FI ACCESSORIES

De Luxe Groov-Kleen

Model 42 £1-84

Chrome Finish Model 60 £1-50



Ref. 36A. Record/Stylus Cleaning Kit 82p
Ref. 43. Record Care Kit £2-35
Ref. 31. Cassette Head Cleaner 54p
Ref. 32. Tape editing Case £1-54
Model 9. Wire Stripper/Cutter 83p

Ref. P. Hi-Fi Cleaner 31p
Ref. 32A. Stylus Balance £1-36
Ref. J. Tape Head Cleaning Kit 51p
Ref. 34. Cassette Case £1-27
Ref. 56. Hi-Fi Stereo Hints & Tips 32p

ANTEX SOLDERING IRONS

X25 25 watt £1-93
CCN 240, 15 watt £2-15
Model G. 18 watt £2-15
SK2 Soldering Kit £2-86
STANDS: ST1 £1-21. ST2 77p
SOLDER: 188WG Multicore 7oz 82p
22SWG 7oz 82p. 188WG 22ft 28p
22SWG Tube 22p

ANTEX BITS and ELEMENTS

Bits No.
102 For model CN240 3/8"
102 For model CN240 1/2"
1100 For model CCN240 3/8"
1101 For model CCN240 1/2"
1102 For model CCN240 1"
1020 For model G240 3/8"
1021 For model G240 1"
1022 For model G240 1 1/2"
50 For model X25 3/8"
51 For model X25 1/2"
52 For model X25 1"

ALL 38p each

ELEMENTS

ECN 240 £1-16 ECCN 240 £1-32
EG 240 £1-16 EX 25 £1-16

ANTEX HEAT SINKS 10p

VAT included in all prices. Please add 10p P. & P. (U.K. only). Overseas orders—please add extra for postage.

NEW COMPONENT PAK BARGAINS

Pack No. Qty.	Description	Price
C1 250	Resistors mixed values approx. count by weight	0-65
C2 200	Capacitors mixed values approx. count by weight	0-55
C3 50	Precision Resistors 0-1%, 0-01% mixed values	0-55
C4 75	1/4W Resistors mixed preferred values	0-55
C5 5	Pieces assorted Ferrite Rods	0-55
C6 2	Tuning Ganges. MW/LW VHF	0-55
C7 7	Pack Wire 50 metres assorted colours	0-55
C8 10	Reed Switches	0-55
C9 3	Micro Switches	0-55
C10 15	Assorted Pots & Pre-Sets	0-55
C11 5	Jack Sockets 3 x 3.5mm Standard Switch Type	0-55
C12 40	Paper Condensers preferred types mixed values	0-55
C13 20	Electrolytics Trans. types	0-55
C14 1	Pack assorted Hardware—Nuts/Bolts, Grommets etc.	0-55
C15 4	Mains Slide Switches	0-55
C16 20	Assorted Tag Strips & Panels	0-55
C17 10	Assorted Control Knobs	0-55
C18 4	Rotary Wave Change Switches	0-55
C19 3	Relays 6—24V Operating	0-55
C20 4	Sheets Copper Laminate approx. 10" x 7"	0-55

PLUGS AND SOCKETS

SOCKETS
PS 35 DIN 2 Pin (Speaker) 0-06
PS 36 DIN 3 Pin 0-10
PS 37 DIN 5 Pin 180° 0-10
PS 38 DIN 5 Pin 240° 0-10
PS 39 Jack 2.5mm Switched 0-09
PS 40 Jack 3.5mm Switched 0-10
PS 41 Jack 1" Switched 0-17
PS 42 Jack Stereo Switched 0-28
PS 43 Phono Single 0-06
PS 44 Phono Double 0-10
PS 45 Car Aerial 0-09
PS 46 Co-Axial Surface 0-09
PS 47 Co-Axial Flush 0-14

INLINE SOCKETS

PS 21 D.I.N. 2 Pin (Speaker) 0-13
PS 22 D.I.N. 3 Pin 0-17
PS 23 D.I.N. 5 Pin 180° 0-17
PS 24 D.I.N. 5 Pin 240° 0-17
PS 25 Jack 2.5mm Plastic 0-10
PS 26 Jack 3.5mm Plastic 0-12
PS 27 Jack 1" Plastic 0-24
PS 28 Jack 1" Screened 0-28
PS 29 Jack Stereo Plastic 0-22
PS 30 Jack Stereo Screened 0-32
PS 31 Phono Screened 0-14
PS 32 Car Aerial 0-15
PS 33 Co-Axial 0-17

PLUGS

PS 1 D.I.N. 2 Pin (Speaker) 0-11
PS 2 D.I.N. 3 Pin 0-12
PS 3 D.I.N. 4 Pin 0-15
PS 4 D.I.N. 5 Pin 180° 0-14
PS 5 D.I.N. 5 Pin 240° 0-15
PS 6 D.I.N. 6 Pin 0-15
PS 7 D.I.N. 7 Pin 0-15
PS 8 Jack 2.5mm Screened 0-10
PS 9 Jack 3.5mm Plastic 0-09
PS 10 Jack 3.5mm Screened 0-12
PS 11 Jack 1" Plastic 0-13
PS 12 Jack 1" Screened 0-18
PS 13 Jack Stereo Screened 0-29
PS 14 Phono 0-06
PS 15 Car Aerial 0-15
PS 16 Co-Axial 0-10

CABLES

CP 1 Single Lapped Screen 0-06
CP 2 Twin Common Screen 0-08
CP 3 Stereo Screened 0-08
CP 4 Four Core Common Screen 0-23
CP 5 Four Core Individually Screened 0-30
CP 6 Microphone Fully Braided Cable 0-10
CP 7 Three Core Mains Cable 0-07
CP 8 Twin Oval Mains Cable 0-08
CP 9 Speaker Cable 0-04
CP 10 Low Loss Co-Axial 0-10

CARBON POTENTIOMETERS

Log and Lin
47K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M
VC 1 Single Less Switch 0-14
VC 2 Single D.P. Switch 0-20
VC 3 Tandem Less Switch 0-44
VC 4 1K Lin Less Switch 0-14
VC 5 100K Log anti-Log 0-44

HORIZONTAL CARBON PRESETS

0.1 watt 0-08 each
100, 220, 470, 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4.7M

WORLD SCOOP

JUMBO

SEMICONDUCTOR PACK

Transistors, Germ. and Silicon Rectifiers, Diodes, Triacs, Thyristors, I.C.s and Zeners. ALL NEW AND CODED.

APPROX. 100 PIECES

Offering the amateur a fantastic bargain Pak and an enormous saving—identification and data sheet in every Pak.

ONLY £2 P. & P. 20p.

EX-COMPUTER BOARDS—BY THE BOXFULL!

20 Boards packed with Semiconductors and other Electronic Components. Each board approx. size 8in x 7in. All known type numbers and easily recognisable.

FANTASTIC VALUE AT

£2-20 per Box. P. & P. 52p.

SPECIAL PURCHASE

2N3055. Silicon Power Transistors NPN. Famous manufacturers out-of-spec devices free from open and short defects—every one available 115V. TO3. Metal Case.

OUR SPECIAL PRICE 8 for £1

LOW COST CAPACITORS

0-01µF 400V. 3p each
500µF 50V. Elect. 10p each

RECORD STORAGE/CARRY CASES

7in EP, 18 1/2in x 7in x 8in (50 records) £2-10
12in LP, 13 1/2in x 7 1/2in x 12 1/2in (50 records) £2-95

CASSETTE CASES

Holds 12. 10in x 3 1/2in x 5in. Lock and handle, £1-30.

8-TRACK CARTRIDGE CASES

Holds 14. 13in x 5in x 6in. Lock and handle, £1-95.
Holds 24. 13 1/2in x 8in x 5 1/2in. Lock and handle, £2-70.

COLOURS: Red, black and tan, please state preference

REPANCO TRANSFORMERS

240V. Primary. Secondary voltages available from selected tappings: 4V, 7V, 8V, 10V, 14V, 15V, 17V, 19V, 21V, 25V, 31V, 33V, 40, 50 and 25V-0-25V.

Type	Amps	Price	P. & P.
MT50/1	1	£1-93	30p
MT50/1	1	£2-42	35p
MT50/2	2	£3-30	40p

CARTRIDGES

ACOS GP91-18C. 200mV at 1-2cm/sec £1-16
ACOS GP93-1. 280mV at 1cm/sec £1-85
ACOS GP96-1. 100mV at 1cm/sec £2-65
TTC J-2005. Crystal/Hi Output 85p
TTC J-20 10C Crystal/Hi Output Compatible £1-10
TTC J-200 C8 Stereo/Hi Output £1-60
TTC J-2105 Ceramic/Med. Output £1-64

CARBON FILM RESISTORS

The E12 Range of Carbon Film Resistors, 1 watt available in PAKS of 50 pieces, assorted into the following groups:—

R1	50 Mixed 100 ohms-820 ohms	40p
R2	50 Mixed 1K ohms-8.2K ohms	40p
R3	50 Mixed 10K ohms-82K ohms	40p
R4	50 Mixed 100K ohms-1 Meg. ohms	40p


BI-PAK SUPERIOR QUALITY LOW-NOISE CASSETTES

C60, 32p; C90, 41p; C120, 52p

-the lowest prices!

BI-PAK QUALITY COMES TO AUDIO!

AL10/AL20/AL30 AUDIO AMPLIFIER MODULES

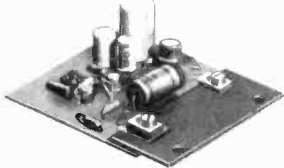

The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S.

The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

Parameter	Conditions	Performance
HARMONIC DISTORTION	Po = 3 WATTS f = 1KHz	0-25%
LOAD IMPEDANCE	—	8-16 Ω
INPUT IMPEDANCE	f = 1KHz	100 k Ω
FREQUENCY RESPONSE -3dB	Po = 2 WATTS	50 Hz-25KHz
SENSITIVITY for RATED O/P	Vs = 25V, R1 = 8 Ω f = 1KHz	75mV, RMS
DIMENSIONS	—	3" x 2 1/2" x 1"

The above table relates to the AL10, AL20 and AL30 modules. The following table outlines the differences in their working conditions.

Parameter	AL10	AL20	AL30
Maximum Supply Voltage	25	30	30
Power out for 2% T.H.D. (RL = 8 Ω f = 1KHz)	3 watts RMS Min.	5 watts RMS Min.	10 watts RMS Min.

AUDIO AMPLIFIER MODULES

AL 10. 3 watts	£2-19
AL 20. 5 watts	£2-59
AL 30. 10 watts	£3-01

POWER SUPPLIES

PS 12. (Use with AL10 & AL20)	88p
SPM 80. (Use with also AL30 & AL50)	£3-25
FRONT PANELS PA 12 with Knobs	£1-00

PRE-AMPLIFIERS

PA 12. (Use with AL10 & AL20)	£4-35
PA 100. (Use with AL30 & AL50)	£13-15

TRANSFORMERS

T461 (Use with AL10)	£1-38 P & P 15p
T538 (Use with AL20)	£1-93 P & P 15p
BMT80 (Use with AL30 & AL50)	£2-15 P & P 25p

PA12 PRE-AMPLIFIER SPECIFICATION

The PA12 pre-amplifier has been designed to match into most budget stereo systems. It is compatible with the AL 10, AL 20 and AL 30 audio power amplifiers and it can be supplied from their associated power supplies. There are two stereo inputs, one has been designed for use with "Ceramic cartridges while the auxiliary input will suit most magnetic cartridges. Full details are given in the specification table. The four controls are, from left to right: Volume and on/off switch, balance, bass and treble. Size 152mm x 84mm x 35mm.

Frequency response—
20Hz-50KHz (-3dB)
Bass control—
± 12dB at 60Hz
Treble control—
± 14dB at 14KHz
*Input 1. Impedance
1 Meg. ohm
Sensitivity 300mV
Input 2. Impedance
30 K ohms
Sensitivity 4mV


LOOK FOR OUR
SEMICONDUCTOR ADVERTISEMENTS IN
Practical Wireless and RADIO CONSTRUCTOR

ALL PRICES INCLUDE VAT

The STEREO 20

The "Stereo 20" amplifier is mounted, ready wired and tested on a one-piece chassis measuring 20 cm x 14 cm x 5.5 cm. This compact unit comes complete with on/off switch volume control, balance, bass and treble controls, Transformer, Power supply and Power amps. Attractively printed front panel and matching control knobs. The "Stereo 20" has been designed to fit into most turntable pinthos without interfering with the mechanism or, alternatively, into a separate cabinet. Output power 20w peak. Input 1 (Cer.) 300mV into 1M. Freq. res. 25Hz-25kHz. Input 2 (Aux.) 4mV into 30K. Harmonic distortion. Bass control ± 12dB at 60Hz typically 0.25% at 1 watt. Treble con. ± 14dB at 14kHz.

£14-45

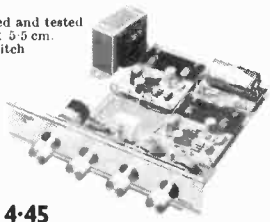

NOW WE GIVE YOU 50w PEAK (25w R.M.S.) PLUS THERMAL PROTECTION! The NEW AL60 Hi-Fi Audio Amplifier FOR ONLY £3-95




- Max Heat Sink temp 90°C.
- Frequency Response 20Hz to 100KHz
- 0-1% Distortion
- Distortion better than 1% at 1KHz
- Supply voltage 10-35 volts
- Thermal Feedback
- Latest Design Improvements
- Load — 3, 4, 8 or 16 ohms
- Signal to noise ratio 80dB
- Overall size 63mm x 105mm x 13mm

Especially designed to a strict specification. Only the finest components have been used and the latest solid state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

FULLY BUILT — TESTED and GUARANTEED

STABILISED POWER MODULE SPM80

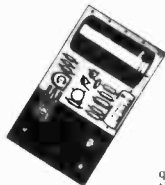

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disc Systems, Public Address, Intercom Units, etc. Handbook available 10p PRICE £3-25

TRANSFORMER BMT80 £2-15 p. & p. 28p

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

SPECIFICATION

Frequency Response 20Hz-20KHz ± 1dB
better than 0.1%
Harmonic Distortion
Inputs: 1. Tape Head 1-25 mV into 50K Ω
2. Radio, Tuner 35 mV into 50K Ω
3. Magnetic P.U. 1.5 mV into 50K Ω
All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB. from 20Hz to 20KHz.
Bass Control ± 15dB at 20KHz
Treble Control ± 15dB at 20KHz
Filters: Rumble (High Pass) 100Hz
Scratch (Low Pass) 8KHz
Signal/Noise Ratio better than -65dB
Input overload + 26dB
Supply + 35 volts at 20mA
Dimensions 292mm x 82mm x 35mm

ONLY £13-15

SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £25-30 FREE p. & p.

Giro No. 388-7006

Please send all orders direct to warehouse and despatch department


BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 11p. Overseas add extra for airmail.
Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back

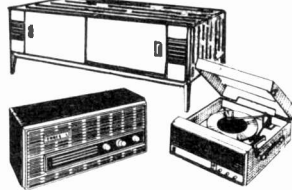The items below are from the March Supplement to our 1974 Catalogue. You can receive this catalogue and the next 12 supplements by sending 66p.



Stereo Radio Cabinet. Long, Low and Modern. Teak veneered with sliding front and tapered legs. Speaker spaces each end. Size approx. 4ft 2" x 15" x 15". Probably cost over £200 to make. Our Price £28-10 each. We can arrange delivery within 200 miles if you order 10 or more. **Bush Record Player.** Bush Ref. No. SRP 64. Separate bass and treble controls help give this unusually good sound quality. A suitable amplifier/speaker unit converts this to full stereo. Cabinet size 7" x 16" x 18" deep. Finished in charcoal grey leather cloth. Fully transistorised with 8" x 5" speaker. Controls bass, on/off, treble and volume. Socket stereo. Makers recommended price £27.73. Our Price £17-72. A saving of over £8. Post and insurance £2.

Erros Table Radio. Dutch made. Three wavebands (L.M. & S.). Nice size (16 1/2" x 8 1/2" x 5") wooden cabinet with high gloss finish. 6" x 4" speaker gives better than average tone—these radios are very well made from good quality components and should not be confused with Hong Kong makes. They recently retailed at £18 each and were well worth it. The ones we have are brand new and working but have failed final inspection because either they will work only on mains or only on batteries. It is unlikely that the fault is very much however and we are arranging for a circuit diagram. Price £28-84 plus £1 post and insurance.

Electric Welder. Big transformer in metal case with carrying handle and control switch, output through very heavy duty terminals. Output volts 1.9-4.25 volts max. 117 amps—normal mains input socket for optional foot switch. £18-00 plus £2 carriage up to 200 miles. A further £1 for each 100 miles extra.

24v 3 amp Mains Transformer. Upright mounting with fixing clamps, standard primary 240/200/195/160—£3-50 plus 30p post and service.

Mains Transformer. 0-5v-0-5.5v at 500 mA and 1V at 1 amp. Normal tapped primary. Upright mounting with fixing lugs. £1-00.

Mains Transformer. (18v-37v-39v-41v at 2 amp or this would function at 18v-0-18v). Primary tapped 110, 115, 127, 200, 220 and 240v selected by labelled plug. Primary screen and multi-tapped. Upright mounting with fixing lugs £2-95.

Midset Two Gangs. Tuning condenser as fitted to many Japanese and Hong Kong radios—probably 200pf each section with 1" spindle with terminals less trimmers. Price 38p. With trimmers 50p.

Ferrite Rods for aerials, etc. The following types are in stock: Dia. 1/8" 4" long 15p, 5" long 18p; Dia. 3/16" 5" long 20p, 6" long 25p, 8" long 30p; Dia. 3/8" 4" long 20p, 5" long 25p, 6" long 30p, 8" long 35p, 10" long 35p; Ferrite Slab 3" long x 1/2" x 1/2" 20p.

Photo Resistor. Mullard type. This drops its resistance from approx. 250Kohms in dark to only approx. 200 ohms in bright light but it is only quite small, in fact less than 1" square with leads coming out of corners on one side. Price 22p. **U.S. Cartridge** for design face for Bush mounting—moving iron, ideal for charger. 75p each.

I.F. Transformers. Tuneable around 465 Kc. Japanese manufacture as fitted to many Japanese made portable radios. Three sizes available:

Sub-miniature, approx 1 1/2" x 1" x 3" high. **Miniature,** approx 2" x 2" x 1" high. **Small,** approx. 9/16" x 9/16" x 2" and **Standard,** 9/10" x 9/10" x 2". All at 11p each.

12V Power Pack "Smooth flow" double wound mains transformer, full wave rectifier and overload protection. Completely enclosed in plastic case with output terminals and flex lead—ideal to operate models, drive motors, charge small batteries, etc., etc. Price £2-25.

Time Switch. Mains driven 24 hours clock—driving 2 pairs of on/off switches this switch sequence will repeat until re-programmed. Complete in pressed steel case with glass window in front. Continental make. Price £3-50.

Relay. Clare Elliot. Sealed and wire ended. 675 ohm coil with two pairs change over contacts. Price £1-65.


TERMS:—Add 10% V.A.T. Send postage where quoted—other items, post free if order for these items is £6-00, otherwise add 20p.

J. BULL (ELECTRICAL) LTD.

(Dept. PE), 7 Park Street
Croydon CR0 1YD Callers to:
102/103 Tamworth Road, Croydon

INTER-LOCKING PLASTIC STORAGE DRAWERS

NEAT!
HANDY!
TIDY!

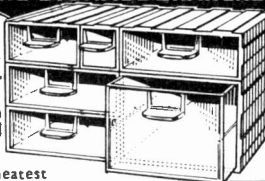

DISCOUNT PRICES

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. Build up any size cabinet for wall, bench or table top.

5 SIZES ALL INTERLOCK

BUY AT TRADE PRICES!

SINGLE UNITS (1D) (5ins x 2 1/2ins x 2 1/2ins). £1.75 DOZEN.

DOUBLE UNITS (2D) (5ins x 4 1/2ins x 2 1/2ins). £3 DOZEN.

TREBLE (3D) £2-90 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D2), £4-25 for 8, **EXTRA LARGE SIZE (6D1)** £3-90 for 8.

PLUS QUANTITY DISCOUNTS!

Orders £10 and over DEDUCT 5% in the £
Orders £20 and over DEDUCT 7 1/2% in the £
Orders £50 and over DEDUCT 10% in the £

PACKING/POSTAGE/CARRIAGE: Add 35p to all orders under £10. Orders £10 and over, packing/postage/carriage free.

QUOTATIONS FOR LARGER QUANTITIES

Please add 10% V.A.T. to total remittance

FLAIR ELECTRONICS (Dept. PE6) 124 Cricklewood Broadway, London, N.W.2, Tel. 01-450 4844

A DEXTER DIMMASWITCH

ALLOWS COMPLETE



LIGHTING CONTROL

The DEXTER DIMMASWITCH is an attractive Dimma unit which simply replaces the normal light switch. It is available as a complete "ready to install" unit or "simple to assemble" kit. Two models are available controlling up to 300W or 600W of all lights, except fluorescents, at mains 200-250V, 50Hz. All DEXTER DIMMASWITCH models have built-in radio interference suppression. 600 watt £3.52 Kit form £2.97 300 watt £2.97 Kit form £2.42

All plus 12p post and packing
Prices include VAT. Please send c.w.o. to:

DEXTER & COMPANY

1 ULVER HOUSE
19 KING STREET
CHESTER CH1 2AH
Tel: 0244-25883

AS SUPPLIED
TO H.M. GOVERNMENT
DEPARTMENTS, HOSPITALS,
LOCAL AUTHORITIES,
ETC.

SINCLAIR CALCULATORS

Cambridge Kit	£19-95 (£2-25)
Cambridge Assembled	£21-95 (£2-50)
Executive with Memory	£34-95 (£3-75)
New Sinclair Scientific	£39-95 (£4-25)

FERRANTI ZN414

IC radio chip with data £1-20 (23p) Also available kit of extra parts to complete a radio £2-39 (40p) Send S A E for free leaflet

SINCLAIR PROJECT 80

AFU	£6-95 (69p)
Z40	£5-45 (54p)
Z60	£6-95 (69p)
O16	£7-70 (77p)
PZ5	£4-98 (49p)
PZ6	£7-98 (79p)
PZ8	£7-98 (79p)



Decoder £7-45 (74p) Trans for PZ8 £2-95 (50p) Tuner £11-95 (£1-19) Stereo 80 £11-95 (£1-19) Project 805 £28-95 (£2-89)

2 x 240 Stereo 80/PZ5 £25-00 (£2-50).


2 x 240 Stereo 80/PZ6 £27-75 (£2-77)

2 x 260 Stereo 80/PZ8 Transformer £33-11 (£3-31)

Write for our most competitive quotation We specialize in exporting Project 80 and charge only token postage on large airmail orders. Send S A E for free leaflet on new quadraphonic adaptor for use with Project 80 £9-95 (£1-30)

SINCLAIR SUPER IC12

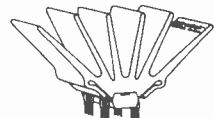6W rms power
With 44 page
booklet and
printed circuit
£2-10 (43p)



DE LUXE KIT FOR THE IC12

Includes all parts for the printed circuit and volume bass and treble controls needed to complete the mono version £1-60 (27p) Stereo model with balance control £3-60 (48p)

IC12 POWER KIT

Supplies 28V 0.5A £2-67 (50p)

LOUDSPEAKERS FOR THE IC12

5in 8 ohm £1-10 (27p) 5in x 8in 8 ohm £1-55 (37p)

PREAMP KITS FOR THE IC12

Type 1 for magnetic pickups mics and tuners Mono model £1-35 (25p) Stereo model £2-40 (36p) Type 2 for ceramic or crystal pickups Mono 65p (18p) Stereo £1-30 (25p)

SEND S A E FOR FREE LEAFLET ON KITS

BATTERY ELIMINATOR BARGAIN

The most versatile battery eliminator ever offered Switched output of 3, 4, 6, 7 1/2, 9 and 12V at 500mA £4-15 (70p)
Other eliminators stocked:
50mA-6V, £1-80 (30p), 9V, £1-80 (30p), 7 1/2V cassette type, £2-25 (30p), Double 6 - 6V, £2-50 (35p) 9 - 9V £2-50 (35p).



500mA (higher current de luxe models)—6 7/2 or 9V (state which) £2-85 (50p)

S-DECS AND T-DECS

S-DEC £1-98 (31p)


T-DEC £3-63 (47p)

U-DEC A £3-99 (51p)

U-DEC B £6-99 (81p)

IC carriers 16 dit—plain 81p (15p), with socket £1-77 (25p) 10 TOS—plain 78p (15p) with socket £1-68 (24p)

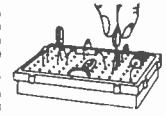Experiment guides A £1-50 (46p) B £1-77 (29p) C 90p (15p) D £2-40 (35p) E £4-20 (53p)



ZIPPY CABINETS

Attractive plastic instrument cases in 4 sizes 80 x 50 x 30mm 60p (25p) 115 x 65 x 40mm 87p (30p) 155 x 90 x 50mm £1-20 (35p) 210 x 125 x 70mm £1-80 (45p)

ECONOMICAL QUADRAPHONICS

£9-95 (£1-30)

Complete self-contained matrix quadraphonic synthesizer in attractive cabinet Just feed output of ordinary stereo hi-fi into it and hook up to 4 speakers to obtain the latest experience in sound. Send S A E for free leaflet


SWANLEY ELECTRONICS

P.O. Box 68, Swanley, Kent BR8 8TQ
Please add the sum shown in brackets after the price to cover the cost of post and VAT
Official credit orders from schools etc welcome
No VAT charged on overseas orders

SONAX ELECTRONICS FANTASTIC KIT OFFER

PE RONDO

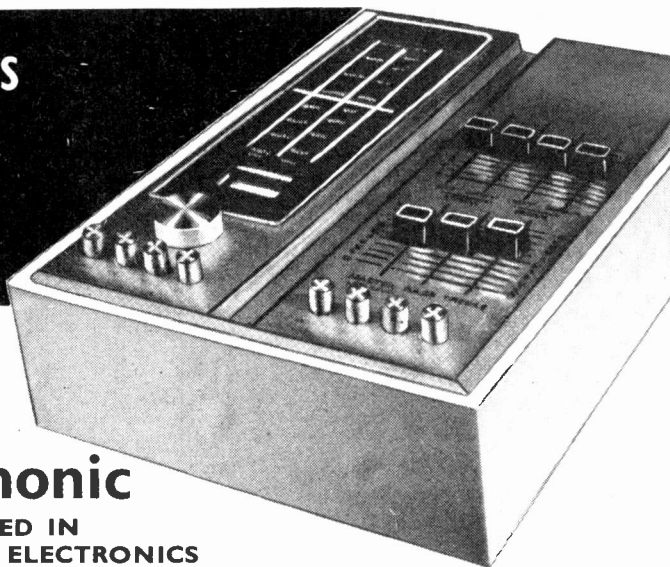complete quadraphonic Hi-Fi System AS FEATURED IN PRACTICAL ELECTRONICS



There's never been an offer like it! Construct this 80 watt RMS Quadraphonic System with 4 matched high performance speakers. All finishes including polishing of cabinets and brushing and anodising of metal work are already completed. You can achieve the finest production finish and the styling will do justice to any room setting.

PLEASE SEND ME

CBS SQ* MATRIX DECODER *TM CBS
Complete kit. Post Free. Inc. CBS Licence
Fee + VAT 80p

PREAMPLIFIER BOARD
Complete kit. Post Free. + VAT 33p

MASTER VOL./TONE/BALANCE BOARD
Complete kit. Post Free. + VAT 93p

**POWER AMP BOARD AND HEATSINK
(Stereo Pair)**
Complete kit. Per Board. Post Free. +VAT 82p

POWER SUPPLY BOARD COMPLETE
Post Free. + VAT 55p

**MAIN SMOOTHING CAPACITORS
(Two reqd.)** Post Free. + VAT 16p

MAINS TRANSFORMER
Post Free. + VAT 68p

**CHASSIS-PUNCHED AND DRILLED
WITH SCREENS** Post Free. + VAT 35p

PLEASE TICK BOX

£8-00 **RONDO CASE** Post Free. + VAT 19p **£1-92**

£3-30 **HARDWARE PACK** Post Free. + VAT 22p **£2-20**

£9-35 **CONTROL SECTION FASCIA** Post Free. + VAT 38p **£3-85**

£8-25 **STEREO DECODER KIT** Post Free. + VAT 65p **£6-54**

£5-50 **STEREO DECODER READY BUILT AND TESTED** Post Free. + VAT 76p **£7-64**

£1-65 **ALSO—Suitable record playing equipment**
Per Pair **GOLDRING G101/2 TURNTABLE** **£23-90**
Less Cartridge

£6-87 **DEUTSCHE ELAC STS 144/17 CARTRIDGE** Post Free. + VAT £2-39 **£7-90**

£3-57 **DEUTSCHE ELAC STS 144/17 CARTRIDGE** Post Free. + VAT 79p

SPEAKER KITS

All components parts for "Rondo" loudspeaker assemblies are available, including special precision machined wrapround cabinets for very easy construction and perfect professional finish—as shown in fig. 7.9 of January 1974 issue.

**COMPLETE SPEAKER KIT WITH 4 DRIVE UNITS,
CROSSOVER WADDING, ETC. INCLUDING CABINETS**
Price Per Pair **£34-50**
Post £1. + VAT £3-55

BASS DRIVE UNITS (2 per cabinet) **£4-25**
Post Free. + VAT 42p EACH

TWEETERS (2 per cabinet) **£1-20**
Post Free. + VAT 12p EACH

CROSSOVER KIT (1 per cabinet) **£2-50**
Post Free. + VAT 25p EACH

SPECIAL OFFER - SAVE £7

4 Speaker kits (as required for Rondo) **£62-00**
Post £2. + VAT £6-40

DETAILS OF ANCILLARY KITS

Comprising 16 loudspeaker drive units, FOUR 5 element crossover networks including 12 prewound coils, four fully machined and polished wrap-round cabinets, four routed front and four routed back panels, 72 feet of coded coloured wire, four recess panels containing din and 4mm sockets, 24 lengths of 2" thick special acoustic wadding and latest acoustically transparent Declon fronts to complete the finish.

We apologize to our customers for any inconvenience caused by delay in delivery. This is due to tremendous demand for our products and we are endeavouring to clear back-log with all possible speed.


MONEY ENCLOSED £..... **CHEQUE/P.O./MONEY ORDER**

NAME

ADDRESS

POST TO:

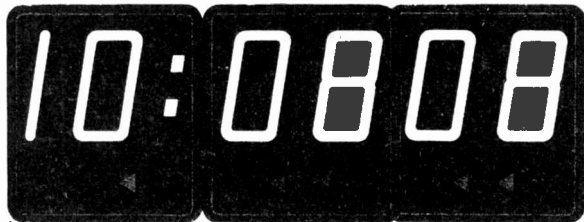SONAX ELECTRONICS, Spencer House, Brettenham Rd., Edmonton, London, N.18



SP-152	SP-352	SP-352
--------	--------	--------

BECKMAN PLANAR GAS DISCHARGE DISPLAYS
 Continuous 7 segment, attractive orange, viewing up to 40ft

SP152 1½ digits (0-55in) clock module	£4.00 + VAT = £4.40
SP352 2 digits (0-55in)	£4.00 - VAT £4.40

Other modules available, including

SP151 3½ digits (0-50in), + a.m.p.m. clock module	£7.20 - VAT - £7.92
SP332 2 digits (0-33in)	£4.00 - VAT £4.40

CT5001 4 FUNCTION CALCULATOR IC

SLA7 0-33in RED LED DIGITAL DISPLAYS

Pack of 4 4 × £1 70	£6.80 - VAT = £7.48
Pack of 6 6 × £1 70	£10.20 - VAT £11.22

MMS316N ALARM CLOCK IC £15.00 + VAT - £16.50

RCA TA8055T LIQUID CRYSTAL DISPLAY £11.60 + VAT £12.76

MMS316N - TA8055T together, ONLY £21.00 + VAT - £23.10
 Supplied with Soldercon pins to make clock chip socket

PCB for P.E. Digital Clock with RCA L-C £1.50 + VAT £1.65

NEW MOSTEK ALARM CLOCK IC MK50250N £6.00 - VAT - £6.60
 MK50250N—24hr format—Alarm—Snooze—Multiplexed 4 to 6 digit gas discharge or LED display—Display can be shared with calculator—Low cost

N.B. CONSTRUCTORS OF P.E. DIGITAL CLOCK
 With minor modifications an RCA Liquid Crystal may be substituted for the Siemens Liquid Crystal, and RCA L-Cs bought from us will include clear instructions on how this may be done

Data supplied with all devices.
 Also available separately at 10p per device
 No P. & P charge for U.K. orders Overseas P & P 50p

SINTEL, 53 ASTON STREET, OXFORD

DEKATRON UNITS
 Contain 2 CV2271 Dekatrons, 2 4-digit resettable counters, 2 sealed relays, 2 ECC81, R.s. C.s. etc. Only £1.70 (30p)

FERRIC CHLORIDE
 Anhydrous to Mill-spec in 1lb sealed packs 1lb 55p (20p); 3lb £1.32 (30p), 10lb £3.85 (60p)

VERSATILE POWER UNIT
 Contains mains transformer, 2A thermal cut-out and bridge rect. Will give 1.7-10 5V with 2 extra capacitors (provided). Ideal for Ni-Cad battery charger, 5V TTL supply, cassette or radio, etc. Brand new, complete with information, 96p (20p)

AMPLIFIER UNIT
 In fully screened case 5½ × 5 × 3½in 2 GET116 on heat sinks, 2 zeners, 3 pot cores, 4 small transformers, 1% resistors and capacitors, 40 way tagboard and fuse. With circuit, 72p (30p), 4 for £2.20 (65p), 100 for £33 plus carr

3W CASED AMPLIFIER
 Polished wooden cabinet 14 × 13 × 9in containing a sensitive 4 valve amplifier with tone and volume controls, 3 watts output to the 7 × 4in 3Ω speaker. Also included is a non-standard tape deck. Supplied in good working condition with circuit. Standard mains operation. Great for guitar practice, etc. ONLY £3.30 (£1.10 up to 200 miles, £1.35 over). Suitable cassette, £1.10 (30p). Spare head, 33p; Tape (ex-computer), 75p (20p). Amplifier chassis only, complete and tested (2x ECC83, EL84, E280) plus speaker £2.40 (40p), motors 40p (30p)

Scopes in stock for callers, ring for details
VAT INCLUDED IN ALL PRICES. Carr in brackets, small parts 5p S.A.E. list, enquiries

GREENWELD ELECTRONICS (PE3)
 24 Goodhart Way, West Wickham, Kent. SHOPS AT: 21 Deptford Broadway, S.E.8 (Tel. 01-692 2009), and 38 Lower Addiscombe Road, Croydon.

28lb FLOOR SWEEPINGS
 Clearing Deptford shop to make more room—must sell tons of components, etc. at give away price! Only £3 carr paid

7lb BARGAIN PARCELS
 Hundreds of new components—resistors, capacitors, switches, pots, plus PC boards with transistors and diodes, also crystals and loads of odds and ends. Amazing value at £1.82 (40p)

COMPONENT PACKS
 500 assorted resistors £1.10 (20p), 2,500 £4 (40p), 10,000 £13 (£1.10), 100,000 £38 plus carr. 150 poly, mica, ceramic, etc. caps 66p (10p).

COMPUTER PANELS
 3lb asstd £1.10 (30p), 7lb £2.20 (40p), 12 high quality panels with IC's, power transistors, trim pots, etc., £2.20 (30p), 100 £13 (£1)

NEW COMPONENTS
 400V 5A SCR 66p; 200V 44p; OC16 22p; OC45 9p; OC71 9p; OC91 16p; BFY18 13p; BCY72 9p; 741C 10p for photo

TRENDATA KEYBOARD
 Computer data input terminal with display. Converts to IFO code. Contains over 140 IC's. Brand new and boxed. Original cost £650, but no data available so only £88 (£2). Send 10p for photo

??????????
 80 × 80 - 20uF 350V 11p; 10 for 83p (30p)
 8uF 2,500V £2.20 (60p); 4uF 2,000V £1.10 (40p); 10uF 236V 44p (15p); 112W resistor 4p; 10Ω 2W 10 for 28p; 4 pole 8 way Yaxley 33p (10p) Min 50V ceramic plate caps 22pF-1,000pF, 2p. Heavy duty heat sink 6 × 5 × 3in with 2 power transistors, 88p (30p)



The Pictorial Method

BASIC ELECTRICITY (5 vols) ELECTRONICS (6 vols) TELEVISION (3 vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

YOUR 100% GUARANTEE

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

Amazed to see so much information and in such a self-explanatory way. *S.F., Huddersfield*

Your valuable assistance has enabled me to find a good position as a Radio and T.V. Engineer. *D.S., Bristol*

They live up to your publicity in every way. *C.L.L., London*

BEST I HAVE EVER SET EYES ON, shall definitely recommend to friends. *F.C., Fife*

WHAT A CONTRAST TO OTHER MANUALS I have grappled with. I am delighted with them. *W.A.F., Durham*

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....

BASIC ELECTRICITY 5 parts £5.30

BASIC ELECTRONICS 6 parts £6.40

BASIC TELEVISION 3 parts £3.60

Tick Set(s) required. Prices include Postage

YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME

BLOCK LETTERS

FULL POSTAL.....

ADDRESS

POST NOW FOR THIS OFFER!

Henry's

**DON'T RELY ON YOUR MEMORY
BUY NOW AT BARGAIN PRICES**
Hi Fi and Transistors - Up to date
Brochures on request

**HENRY'S
CATALOGUE**
Due to rapid price changes,
shortages of paper and raw
materials, all prices in the
existing catalogues no longer
apply. Call or phone for latest
prices. A new catalogue will
be available for Aug/Sept. 1974.



**UK's
LARGEST RANGE
OF KITS &
GADGETS**



TEST EQUIPMENT MULTIMETERS

(carr. etc. 30p)
IT1-2 20K/Volt Slimline £5-95
M210 (Case £1-25) 20K/Volt
Slimline deluxe £6-75
TLH33D 2K/Volt Robust £7-50
U437 10K/Volt Steel case. AC up to 40KHz 4-95
AF105 (Case £1-90) 50K/Volt 11-95
U4313 20K/Volt AC current. Steel case 10-50
U4341 Plus Built-in transistor tester 10-50
Model 500 (Case £1-95), 30K/Volt 9-95

OTHER EQUIPMENT

SE250B Pocket Signal Injector 2-10 carr. 15p
SE500 Pocket Signal Tracer 1-70 carr. 15p
TE15 Grid Dip meter 440KHz 280mHz 15-00 carr. 30p
TE40 AC Millivoltmeter 1-2mHz 19-75 carr. 35p
TE65 28 Range valve voltmeter 22-50 carr. 40p
TE20D 120KHz-500mHz RF Gen. 18-95 carr. 40p
TE22D 20Hz-200KHz Audio Gen. 19-95 carr. 40p
SE350A Deluxe Signal Tracer 12-50 carr. 20p
SE400 Volts/ohms/R-C sub./RF field gen. 14-75 carr. 20p

New Revolutionary Supertester 680R

680R Multi-tester £18-50
Accessories
Transistor tester 11-00
Electronic voltmeter 18-00
Amp clamp 11-95
Temperature probe 11-95
Guass meter 11-95
Signal injector 5-95
Phase Sequence 5-95
EHT Probe 5-95
Shunts 25/50/100A 4-50

A SELECTION OF INTERESTING ITEMS

C3025 Compact transistor tester 6-95 p & p 15p
Q4002 Photoelectric System £13-70
E1310 Stereo mag. carr. preamp. 4-80 p & p 25p
Easiphone D1201 telephone amp 7-50 p & p 25p
D1203 Teleamp. with PU coil 4-95 p & p 20p
LL1 Door Intercom. and chime 8-40 p & p 25p
IKW Dimmer/controller 3-00 p & p 10p
9" Twin spring unit For 3-30 p & p 15p
16" Twin spring unit Reverbs 6-85 p & p 25p
US50 Ultrasonic Switch Trans/Rec £12-75
C3041 1-250mHz £4-25
C3043 5CH 1-300mHz £5-75
VHF 105 Aircraft Band Converter 4-50 p & p 15p
B2005 4 Ch. mic. mixer 4-20 p & p 15p
B2004 2 ch. Stereo mixer 6-75 p & p 15p
PK3 Kit £1-95 p & p 20p

EXCLUSIVE: SPECIAL OFFERS

MW/LW CAR RADIO + or - Earth with speaker and fixings. £50 c/p 30p.
8 TRACK CAR STEREO (Earth) with speakers in Pods and fixings £12-50 c/p 40p. Portable Cass./Cass. Tape Player £7-25.
Car Lighter Plug and adaptor for all cassette and radio 6/7 1/9 V output (state width) £1-95 each.
Rotel Stereophones RH630 £4-50, RH700 £6-75, RH430 £3-30, Rotel RA310 15+15 watt Stereo Amplifier (List £52-00) £34-52. With W500 Battery/Mains Cassette Recorder £12-75.
AKAI GX40 Stereo cassette recorder. £59-95 c/p 50p. Pair Akai ADM microphones. £6-95 c/p 20p.
PORTABLE CASSETTE TAPE PLAYER—for car or carry around. £7-25 c/p 20p. HANIMAX BC808 POCKET CALCULATOR WITH % KEY. £28-95.
HANIMAX BC811M MEMORY VERSION £37-50
MAINS UNIT for BC808, BC11M £2-85 (state model)
HANIMAX H101 STEREO COMPACT RECORD PLAYER 2 + 7 watts. Complete with Speakers (List £54-50) Price £39-95 Plus free pair of stereo phones.

BUILD THIS RADIO

Portable MW/LW radio kit using Mullard RF/IF module. Features MW—bandspread for extra selectivity. Slow motion tuning. Fibre glass PVC cabinet. 600MW output. All parts £7-98 (battery 22p), carr. etc. 32p.

FIBRE OPTICS

0-01 diam. Mono Filament £3-00 per 50 metre reel
0-11 diam. 64 Fibres Sheathed £1-00 per metre.
SPRAYS 15mm diam. (Mare's Tail Spray £10-50, 7mm diam. £5-00).



SPECIAL PURCHASES


UHF TV TUNERS CHANNELS 21 TO 64

Brand new transistorised geared tuners for 625 Line Receiver IF output. £2-50. Post 20p.



EASY TO BUILD KITS BY AMTRON— EVERYTHING SUPPLIED

Model No.	£ p	Model No.	£ p
310 Radio control receiver	2-98	760 Acoustic switch	10-75
300 4-channel R/C transmitter	5-95	780 Metal Detector (electronics only)	9-65
345 Superhet R/C receiver	5-95	790 Capacitive Burglar alarm	6-85
455 AM signal generator	12-33	835 Guitar preamp.	4-25
65 Simple transistor tester	1-40	840 Delay car alarm	6-15
115 8 watt Amplifier	3-90	875 CAP Discharge ignition (for car engine (-V Earth))	13-15
120 12 watt amplifier	4-70	80 Scope Calibrator	2-25
125 Stereo control unit	5-70	255 Level Indicator	6-15
130 Mono control unit	3-60	525 120-160mHz VHF timer	11-30
605 Power supply for 115	4-55	715 Photo cell switch	7-70
610 Power supply for 120	4-55	795 Electronic continuity tester	4-30
615 Power supply for 2 x 120	5-73	860 Photo timer	13-25
230 AM/FM aerial amplifier	2-93	871 Slide projector auto feed control	7-15
240 Auto packing light	5-90	235 Acoustic Alarm for driver	7-60
275 Mic. preamplifier	6-08	465 Quartz XTAL checker	8-75
570 LF generator 10Hz-1mHz	15-80	220 Signal Injector	2-30
570 Sq. wave generator 20Hz-20KHz	14-60	390 VOX	15-50
590 SWR meter	12-85	432 Testkit	19-30
620 NI-CAD Charger	8-00	670 Buffer Battery Charger	6-55
630 STAB Power supply 6-12V 0-25-0-1A	8-15	885 Capacitive Contact Alarm	6-25
690 DC motor speed Gov.	2-87	850 Electronic Keyer	18-75
700 Electronic Chaffinch	7-00	820 Electronic Digital Clock	58-50
705 Windscreen wiper timer	6-80		

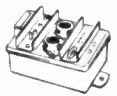

ALL KITS OFFERED SUBJECT TO STOCK AVAILABILITY
Prices correct at time of preparation.
Subject to change without notice.

BUILD THIS TUNER

MW/LW Radio Tuner to use with any amplifier. Features Mullard RF/IF module Ferrite aerial, built in battery. Excellent results. Size 7" x 2 1/2" x 3 1/2". All parts £4-85, carr. 15p.

MULTI-USE & RADIONIC KITS

10-1	10 Projects	3-60
50-1	10 Projects	8-00
150-1	150 Projects	13-20
	Telephone Communicator	7-20
	X20 20 (Elec.)	4-95
	X40 40 (radio)	9-45

(carr./packing 40p)
All transistor circuits with handbooks


TBA800 5 WATT I.C.

Suitable alternative to SL 403D. 5/30 volt operated. 8/16 ohm 5 watt output.
With circuits and data £1-50.



STROBE TUBE

ST2 (D32) DIAC 25p	£3-00
CR51/40 SCR	45p
ZFT4	£3-00
ZFT8	£3-50

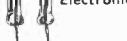

All types offered subject to availability.
Prices correct at time of press E & Q—1
10% V.A.T. TO BE ADDED TO ALL ORDERS.
UK post, etc. 15p per order unless stated.



U.K.'s LARGEST RANGE OF TRANSISTORS & DEVICES

JUST A SELECTION

*TBA800 5W IC £1-50
*Sinclair ICR 6W IC £1-80
*ZN414 IC Radio £1-20
*Ultrasonic Transducers £5-90 pr.
*3015F 5GEG Indicator £1-70
*TIL 209 LED 24p each 22p each per 10
*With circuits/data sheet.

OVER 1,500 DIFFERENT SEMI- CONDUCTOR DEVICES IN STOCK

Free stock list—latest edition (Ref. 36) on request. Includes radio valves, I.C.'s, rectifiers, triacs, SCR's, LED's, etc. More types—better prices—discounts for quantity small or large.



GARRARD BATTERY TAPE DECK

GARRARD 2 speed 9 volt tape decks. Fitted record/play and oscillator/erase heads. Wind and rewind controls. Takes up to 4" spools. Brand new complete with head circuits. £9-50 carr. 30p.

TOP QUALITY SLIDER CONTROLS

60mm stroke high quality controls complete with knobs (post, etc. 15p any quantity).

Singles Log and Lin 5K, 10K, 22K, 50K, 100K, 250K, 500K, 1 Meg. 45p each.

Ganged Log and Lin 10K, 22K, 50K, 100K, 250K, 65p each.

(Quantity discounts available)

Complete with knobs.

MARRIOT TAPE HEADS

4 TRACK MONO or 2 TRACK STEREO
" 17 " High Impedance £2-50
" 17 " Med. Impedance £2-50
" 36 " Med. Impedance £5-00
R730/E73 2 track mono Record/Eraser low imp. 75p pair.
" 18 " and " 36 " £1-00
" 63 " 2 track mono High Imp. £1-75
" 43 " Erase Head for " 63 " 75p
(Post, etc. 15p any quantity).

SINCLAIR MINIATURE AMPLIFIERS & TUNER/DECODER

A4-300, 0-3w 9 volt 1-75	SAC14, 7 + 7 watt Stereo with controls 11-75
104, 1 watt 9 volt 3-10	SAC13, 15 + 15 w Stereo with controls 14-95
102, 3 watt 9 volt 3-95	SP40-5 2Z40 Stereo 80/PZ5 25-00
555, 3 watt 12 volt 4-10	SP40-6 2Z40 Stereo 80/PZ6 27-75
E1208, 5 w 12 volt 5-10	SP60 2Z60 Stereo 80/PZ8 30-45
608, 10 w 24 volt 4-95	Transformer PZ8 3-95
410, 10 w 28 volt 4-45	
E1206, 30 w 45 volt 9-95	
E1210, 21 w 2-75	
RE500, 5 watt IC mains operated Amplifier with controls 6-30	

POWER SUPPLIES FOR EVERY PURPOSE

(All cases unless stated chassis)
470C 6/7 1/9 volt 300 MA (includes Multi-Adaptor for Tape Recorders, etc.) 2-15 post 20p
Car Lighter Voltage Adaptors 300mA (State voltage 6V, 7 1/2, 9V) 1-95 ea. post 25p
SC202 3/6 7/9 volt 400mA 3-65 carr. 30p
HC244R Stabilised version 4-90 carr. 30p
P500 9 volt 500mA 3-20 post 20p
P11 24 volt 500mA (chassis) 2-90 post 20p
P15 26/28 volt 1 amp (chassis) 2-90 post 20p
P1080 12V 1 amp (chassis) 4-50 post 20p
P1081 45V 0-9 amp (chassis) 7-50 post 20p
P12 4 1/2-12 volt 0-4-1 amp 7-15 post 30p
SE101A 3/6 7/9 12 volt 1 amp (Stab.) 12-50 post 25p
RP164 6/7 1/9 12 1 amp (Stab.) 12-95 post 30p



Henry's RADIO LIMITED
EDGWARE ROAD, LONDON W2


404-406 Electric Components and Equipment 01-402 8381
309 PA—Discs—Lighting High Power Sound 01-723 6963
303 Bargains Store (Callers only)
Home and Car Entertainment Centres London and branches now open.
120 Shaftesbury Avenue, London W1 01-437 9692
144 Burnt Oak Broadway, Burnt Oak, Edgware 01-952 7402
190-194 Station Road, Harrow, Middlesex 01-663 7788/9
354-356 Edgware Road, London W2 01-402 5854/4736

All mail to
303 Edgware Road,
London W2 1BW
All stores open 9 am to
6 pm six days a week
Hi-Fi—Tape Equipment
Discount Stock List
Free at all stores



I.L.P. (Electronics) Ltd

SECOND GENERATION 25 WATT HYBRID

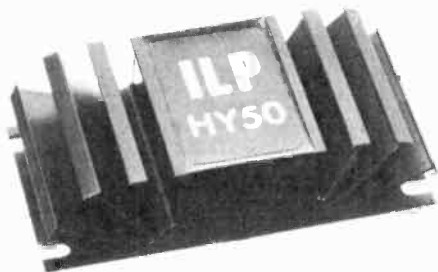

A brand new hybrid fabrication technique, recently perfected in our laboratories, has enabled us to achieve our latest range of completely integrated devices. We have now finally reduced the modular audio amplifier to a simple input/output device requiring only the addition of a basic unstabilized (split line) power supply. The HY50 takes medium power modules to their logical conclusion by incorporating with it a heatsink, which is designed in special high conductivity alloy sufficient for normal audio use without additional chassis sinking. All this without significantly increasing the size of the module comparable in size to a packet of "King-size" cigarettes. Consistent with modern thinking a triple rated output circuit with a load fuse allows for peak transient response without distortion but ensures the necessary protection.

OUTPUT POWER:
LOAD IMPEDANCE:
INPUT SENSITIVITY:
INPUT IMPEDANCE:
TOTAL HARMONIC DISTORTION:
SIGNAL/NOISE RATIO:
FREQUENCY RESPONSE:
SUPPLY VOLTAGE:
SIZE:

SPEC.

25W RMS, 50W peak music power.
4-16Ω into 8Ω
0dB (0.775V RMS).
47kΩ.
Less than 0.1% at 25W typically 0.05.
better than 75dB.
10Hz-50kHz ± 1dB.
± 25V.
105 × 50 × 25mm.

Price £5.80 mono £11.60 stereo. Price inclusive of VAT & P. & P.

NEW HY5 PREAMPLIFIER


Unchallenged for two years, the HY5, our unique multifunction preamplifier/tone hybrid, has been brought into line with the advancements in our power hybrids.

Like the HY50, the new HY5 has no external components and has been redesigned to run off a split power line with improvements in signal/noise, overload capability and reduced distortion. The output has been increased to match the power module (0dB), and share the same power supply.

Overall size is reduced by the use of a new thin film circuitry while the device still retains all the functions of the earlier device.

When combined with the HY50 and power supply only potentiometers are required to complete a simple mono amplifier with input and output facilities expected to be found on Hi-Fi amplifiers.

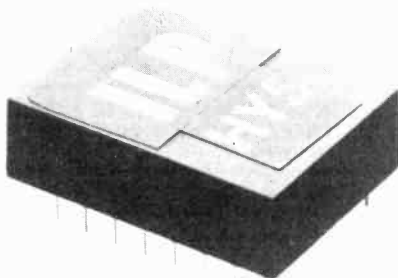The combination of two HY5's two HY50's sharing a common power supply (PSU50) are linked by a balance control to form a complete stereo system.



INPUTS

Magnetic Pick-up 3mV (within 1dB RIAA curve)
Ceramic Pick-up up to 3mV.
Microphone 10mV.
Tuner 250mV
Auxiliary 3-100mV
Input impedance 47kΩ 1 kHz

OUTPUTS

Tape 100mV.
Main output. 0dB (0.775V).

SPEC.

ACTIVE TONE CONTROLS

Treble ± 12dB at 10kHz

Bass ± 12dB at 100Hz

OVERLOAD CAPABILITY

(equalization stage) 40dB on most sensitive input.

OUTPUT NOISE LEVEL


(below 10mV magnetic input) 68dB.

DISTORTION 0.05% at 1kHz.

SUPPLY VOLTAGE ± 16-25V.

SUPPLY CURRENT 15mA.

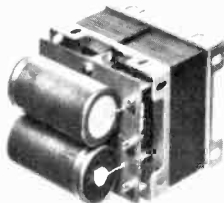Price £4.85 mono £9.70 stereo. Price inclusive of VAT and P. & P.



POWER SUPPLY PSU50

The new PSU50 has a low profile look being only 24in high and can be used for either mono or stereo systems.

SPEC.

OUTPUT VOLTAGE ± 25V.

INPUT VOLTAGE 210-240V.

SIZE: L. 70 D. 90 H. 60mm.

Price £5.23. Price inclusive of VAT & P. & P.

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

Please note we reserve the right to substitute at our discretion updated versions of advertised designs where applicable.

***STILL AT £42.50**

Solartron CD 711S.2 Double Beam Oscilloscope D.C.—9 Mc/s; 3 MV/cm; trigger delay; crystal calibrator; 4in flat faced tube. In good working condition. Carr. £1.50.

NEW WIDE RANGE WOBBLULATOR

5 MHz to 150 MHz up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10.7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6-3V A.C. and use within minutes of receiving. All this for **ONLY £5.75p.** P. & P. 25p. (Not cased, not calibrated.)

20 Hz to 200 kHz WB.

SINE and SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use, 9V supply required. £7.85 each. P. & P. 25p (Not cased, not calibrated.)

GRATICULES. 12cm x 14cm high quality plastic 15p each. P. & P. 5p. 12" Long Persistence Crt. full spec. Price £7.50 to include V.A.T. & carr. **£1 WORTH OF "UFS"**. Six brand new capacitors all between 15V and 100V. Total capacitance not less than 7,000mF. P. & P. 45p.

Large quantity of good quality components — **NO PASSING TRADE** — so we offer 3 lb of **ELECTRONIC GOODIES** for **£1.50** post paid.

ROTARY SWITCH PACK. Six brand new switches (1 ceramic; 1 off, 4 pole, 2 way, etc.). 50p. P. & P. 20p.

COMPONENT PACK consisting of 5 pots, various, brand new; 250 resistors $\frac{1}{2}$ and $\frac{1}{4}$ watt, many high stabs, etc. Fine value at 50p. P. & P. 17p.

P.C.B. PACKS & D. Quantity 2sqft — no tiny pieces. 50p plus P. & P. 20p.

FIBRE GLASS as above £1 plus P. & P. 20p. Ferric Chloride Resistance Pen FREE (whilst stock lasts) on all purchases of our £1 Fibre Glass pack.

5 CRYSTALS 70 to 90kHz. Our choice, 25p. P. & P. 15p.

SANGO 50 microamp meters. 21" diameter. Ex-new radiation equip. £1.25 each. P. & P. 17p.

CAPACITOR PACK—50 brand new components only 50p. P. & P. 17p.

POTS—10 different values. Brand new—50p. P. & P. 17p.

TRIMMER PACK. 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min. strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW. 25p the lot. P. & P. 10p.

FLAT FACED 4" Twin Beam Tube, type Cosmor 89D. Green trace. Brand new £4 each. P. & P. 37p.

LIGHT EMITTING DIODES (Red) from Hewlett-Packard. Brand New 38p each. Holder 1p each. Information 5p.

PHOTOCELL equ. OCP71, 13p each. Mullard OCP70, 10p each.

MODERN TELEPHONES type 706. Two-tone grey, £3.75 each. Two-tone green, £3.75 each. Black, £2.75 each. P. & P. 25p each.

IDEAL EXTENSION Telephones with standard GPO type dial, bell and lead coding. £1.75 each. P. & P. 25p.

DELIVERED TO YOUR DOOR 1 cwt of Electronic Scrap chassis, boards, etc. No Rubbish. **FOR ONLY £3.50.**

PLEASE ADD 10% V.A.T.

OPEN 9 a.m. to 6.30 p.m. ANY DAY

CHILTEAD LTD

7/9 ARTHUR ROAD, READING, BERKS.


(rear Tech. College)

Tel.: Reading 582605/65916

BI-PRE-PAK

STEREO DECODER

£4.95

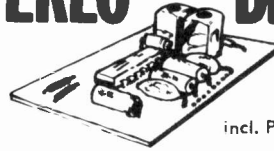


incl. P. & P. and V.A.T.

Ready built unit, ready for connection to the I.F. stages of existing FM Radio or Tuner. A tall tale light can be connected. The unit is a small printed circuit, no further alignment necessary. L.E.D. is recommended as the indicating light, suitable device available from us at 36p. Instructions included.

3 W_{R.M.S.} I.C. AMP


only **£1.65**

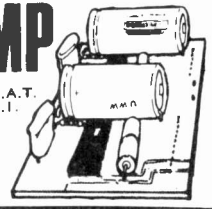incl. P. & P. and V.A.T.
Order Code I.C.A.1.



On P.C. Board with all components or 2 on one board for £2.86. Order Code I.C.A.1/5.
These amps. are supplied with a free booklet on connecting up, specifications and easy-to-build projects using the I.C.A.1

5W & 10W AMPS

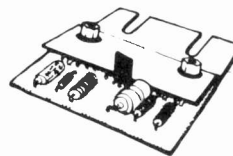

5W ONLY £1.98
10W ONLY £2.49

incl. P. & P. and V.A.T.

These matchbox size amplifiers have an exceptionally good tone and quality for the price. They are only 2 1/2in x 1 1/2in. The 5W Amp will run from a 12V car battery making it very suitable for portable voice reinforcement such as public functions. Two amplifiers are ideal for stereo. Complete connection details and treble, bass, volume and balance control circuit diagrams are supplied with each unit. Discounts are available for quantity orders. More details on request. Cheapest in the U.K. Built and tested.

Now available for 5 & 10W AMPS

Pre-assembled printed circuit boards 2in x 3in available in stereo only, will fit 0.15 edge connector.

Stereo Pre-Amp 1 (Pre 1). This unit is for use with low gain or ceramic pick-up cartridges. **£1.21**

Stereo Pre-Amp 2 (Pre 2). This unit is for use with magnetic pick-up cartridges. **£1.69**

Stereo Tone Control (STC). This unit is an active tone control board and when used with the right potentiometers will give bass and treble boost and cut. **£1.21**

Instruction leaflet supplied with all units. Post and packing and V.A.T. included in prices.

enclose £.....for
.....Decoders/.....3W Amps/.....5W Amps
.....10W Amps/.....Stereo Pre-Amps 1
.....Stereo Pre-Amps 2.....Stereo Tone Controls
(Please insert quantities and delete those not applicable).

Name
Address

BI-PRE-PAK

Co. Regn No.820919

Dept. A, 222/224 West Road,
Westcliff-on-Sea, Essex SS0 9DF.
Telephone: Southend (0702) 46344.



for fast, easy reliable soldering

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

EASY-TO-USE DISPENSERS



Size 5
Savbit alloy
18 swg, 24p
(illustrated).
Size 19A
60/40 alloy
18 swg, 25p
Size 15
60/40 alloy
22 swg, 28p

IDEAL FOR HOME CONSTRUCTORS

Size 1 cartons in 40/60, 60/40 and Savbit alloys in 7 gauges 36p




Size 12 REEL
for Service
Engineers and
Electricians.
18 swg
Savbit alloy. £1.16



BIB WIRE STRIPPER AND CUTTER

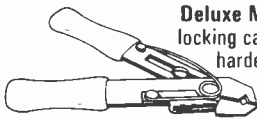Deluxe Model 9 Automatic opening spring, locking catch, plastic-covered handles. Case hardened and precision ground. Adjusts to most wire sizes. Cuts and strips flex, splits plastic twin flex. 75p



Prices shown are recommended retail, excluding V.A.T.

From Electrical and Hardware Shops. If unobtainable, send 10p p&p direct to: **Bib Hi-Fi Accessories Limited, Hemel Hempstead, Herts HP2 7EP**

New Product

CASED AUTO TRANSFORMERS


240 Volt Mains to 115 Volts, smart steel-cased units coated in tough resin, fitted with power lead, fuse and 115 Volt American type socket up to 500VA. above 500VA Cable entry.

VA (Watts)	Price	P. & P.
200 ..	£5-56	£0-38
500 ..	£9-50	£0-67
1000 ..	£15-92	£0-92
2000 ..	£29-70	£1-50


20VA version uncoated, no fuse £2-52 £0-30

MAINS KEYNECTOR

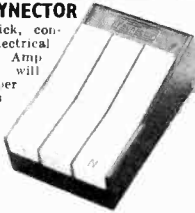The safe, quick, connector for electrical appliances. 13 Amp rating, fused, will connect a number of appliances quickly and safely to the mains. Ideal for testing, demonstrating, window displays, etc. Warning Light, interlocked to prevent connecting when live.



POWER UNIT Type P1076

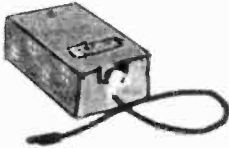

Output switched 3, 4.5, 6, 7.5, 9 and 12 Volts at 500mA D.C. Operates from 240V mains, suitable for Radios, Tape Recorders, Record Players, etc. Size 7.5 x 5.0 x 14.0cm. Price £3-85. Post 25p.

TRANSFORMERS

SAFETY ISOLATING

Prim. 120/240V. Sec. 120/240V. Centre Tap with screen.		Price		P. & P.	
VA	Ref.	Cased	Open	£	£
60	149	—	£3-74	0-38	
100	150	—	4-16	0-52	
200	151	£9-48	7-48	0-92	
250	152	12-05	9-57	0-65	
350	153	14-00	11-44	0-80	
500	154	15-80	13-20	1-00	
1000	156	30-70	27-46	1-20	
2000	158	80-85	55-44		
3000	159	79-53	72-49		

12 & 24 Volts Prim. 200-240V.

Amps	24V	Type	No.	Price	P. & P.
0.3	0.15	242	1-34	0-22	
0.5	0.25	111	1-34	0-22	
1	0.5	213	1-59	0-22	
2	1	71	2-09	0-22	
4	2	18	2-75	0-38	
6	3	70	3-56	0-42	
8	4	108	3-86	0-52	
10	5	72	4-67	0-52	
12	6	116	5-87	0-52	
16	8	17	6-64	0-52	
20	10	115	10-23	0-69	
30	15	187	13-75	0-97	
40	20	232	18-26	1-00	
60	30	226	22-52	1-10	

30 Volts

Prim. 200-240V. Sec. 12, 15, 20, 24, 30V.		Price		P. & P.	
Amps	Type	£	£	£	£
0.5	112	£1-58	£0-22		
1	79	2-20	0-38		
2	3	3-19	0-38		
3	20	3-86	0-42		
4	21	4-68	0-52		
5	51	5-80	0-52		
6	117	6-83	0-52		
8	88	9-00	0-67		
10	89	10-00	0-67		

50 Volts

Prim. 200-240V. Sec. 19, 25, 33, 40, 50V.		Price		P. & P.	
Amps	Type	£	£	£	£
0.5	102	£2-11	£0-30		
1	103	3-08	0-38		
2	104	4-29	0-42		
3	105	5-77	0-52		
4	106	7-48	0-52		
6	107	11-00	0-67		
8	118	14-19	0-97		
10	119	17-60	0-97		

60 Volts

Prim. 200-240V. Sec. 24, 30, 40, 48, 60V.		Price		P. & P.	
Amps	Type	£	£	£	£
0.5	124	£2-10	£0-38		
1	126	2-97	0-38		
2	127	5-77	0-42		
3	125	7-15	0-52		
4	123	9-35	0-67		
5	40	11-55	0-67		
6	120	13-57	0-82		
8	121	16-00	1-00		
10	122	18-40	1-00		
12	189	21-62	1-10		

MINIATURE AND EQUIPMENT

Prim. 240V with screen.		Milliamperes		Type		Price		P. & P.	
Sec. 1	Sec. 2	Sec. 1	Sec. 2	No.	£	£	£	£	£
3-0-3	—	200	—	238	1-23	0-10			
0-6	0-6	500	500	234	1-30	0-10			
0-6	0-5	1000	1000	212	1-88	0-22			
0-9-9	—	100	—	13	1-23	0-10			
0-9	0-9	330	330	235	1-43	0-10			
0-8-9	0-8-9	500	500	207	2-28	0-22			
0-8-9	0-8-9	1000	1000	208	3-03	0-30			
15-0-15	—	40	—	240	1-23	0-10			
0-15-15	0-15	200	200	236	1-30	0-10			
20-0-20	—	30	—	241	1-23	0-10			
0-20	0-20	150	150	237	1-30	0-10			
0-15-20	0-15-20	500	500	205	2-97	0-38			
0-20	0-20	300	300	214	1-76	0-22			
0-20	0-20	300	(No screen)	1116	3-00	0-40			
20-12-0-12-20	—	700 (D/C)	—	221	1-55	0-30			
0-15-20	0-15-20	1000	1000	206	3-30	0-38			
0-15-27	0-15-27	500	500	203	3-08	0-38			
0-15-27	0-15-27	1000	1000	204	3-24	0-38			

PLASTIC CASED SILICON BRIDGE RECTIFIERS


One Amp	Two Amp	Four Amp	Six Amp
50 P.I.V. 25p	50 P.I.V. 35p	100 P.I.V. 55p	50 P.I.V. 65p
100 P.I.V. 25p	100 P.I.V. 40p	200 P.I.V. 55p	100 P.I.V. 70p
200 P.I.V. 28p	200 P.I.V. 45p	400 P.I.V. 65p	200 P.I.V. 80p
600 P.I.V. 30p	400 P.I.V. 50p	600 P.I.V. 75p	400 P.I.V. 90p

PLEASE ADD 10% FOR V.A.T.

ADD 10p P. & P. PER ORDER

A.S.P. LTD.

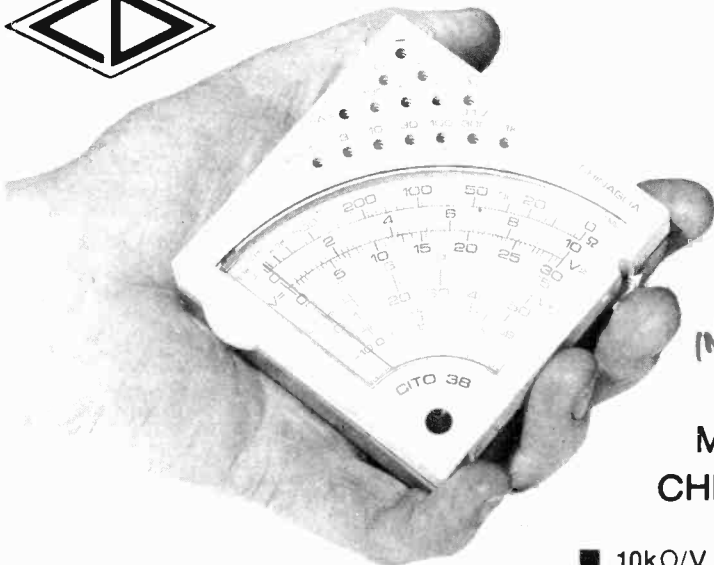BYRE HOUSE · No. 2 UNIT · SIMMONDS RD. · WINCHEAP
CANTERBURY · KENT CT1 3RW · Canterbury (0227) 52436



A CITO IN THE HAND IS

WORTH **£10.10**
A BC109 IN THE BUSH
INC. V.A.T.

THE TRULY POCKET MULTIMETER FROM CHINAGLIA OF ITALY

- 0.1V to 1kV f.s.d. d.c.; 5V to 1.5kV f.s.d. a.c.
- 100µA to 1A f.s.d. d.c.; 5mA to 0.5A f.s.d. a.c.

- 10kΩ/V d.c. sensitivity with 2.5% accuracy.
- Resistance 0-10kΩ and 0-1MΩ.
- Power -10 to +65dB in 6 ranges.

For further information on the 'CITO' or other instruments from the exciting Chinaglia range write or telephone:
CHINAGLIA (U.K.) LTD. 19 Mulberry Walk, London S.W.3 Tel. 01-352 1897
Trade enquiries welcomed

SAXON

Money saving high performance audio equipment
DIRECT FROM OUR OWN FACTORY

GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

SA35 £4.45

35W RMS 25-50V
7 transistors, 7 diodes

Carriage free

- ★ 25Hz-25kHz
- ★ 0.2% distortion
- ★ Noise—80dB
- ★ 500mV into 20K
- ★ 4-16 ohms
- ★ Simple wiring
- ★ Short and open circuit proof
- ★ Continuously rated
- ★ Top-grade components

SA50 £5.65

50W RMS 25-65V
7 transistors, 7 diodes

Carriage free

SA100 £10.90

100W RMS 45-70V
11 transistors, 6 diodes

120 watt module complete with built-in supply—extra heavy duty £19.75 Carr. 60p



THE SA100 MODULE

POWER SUPPLIES

UNSTABILISED

PU45

Suits 2 SA35 or 1 SA50

£4.90

Carriage 30p

PU70

Suits 2 SA50 or 2 SA100

£7.75

Carriage 40p

STABILISED

PS45

Suits 2 SA35 or 2 SA50

£3.50

Carriage free

MT45

Transformer for above

£3.50

Carriage 30p

PS70

Suits 2 SA100

£4.90

Carriage free

MT70

Transformer for above

N.B. PS70 is not suitable for the SA50

Mk II STEREO DISCO MIXER £19.75

Carr. 30p

This well tried unit mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, bass, treble. Left/Right fade, deck volume, bass, treble, h/phone select, vol, Mains. Size 17½in x 3in x 4in deep.



DISCO MODULE £8.00

Carr. 20p

Thousands sold of this extremely popular mono version. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: H/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12½in x 3in x 2in deep.



3-CHANNEL SOUND-LITE £22.50

Carr. 30p

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12in x 3in x 2½in deep. Professional standards at a price you can afford!



SINGLE CHANNEL VERSION £7.50

Carr. free

Recently reduced in price due to increasing sales, handles 1kW. Full wave operation

Add VAT 10% to all orders

MULTI-PURPOSE MIXERS

M4HL

£18.50 Carr. 50p

M6HL


£27.50 Carr. 50p

Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.

VA30 CHANNEL MODULE £3.50

Carr. free

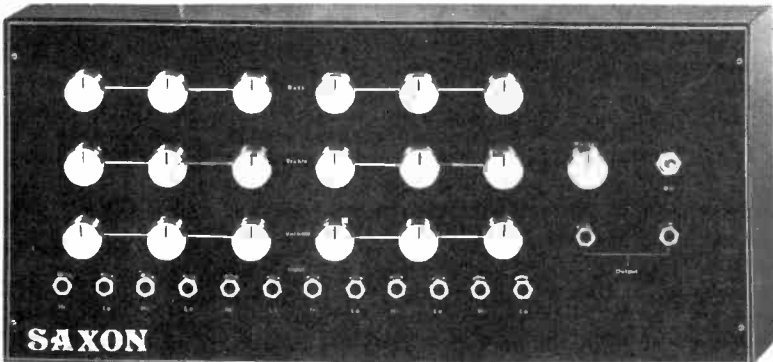This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)




SAXON CSE 100

COMPLETE AMPLIFIER

£34.90

Carr. free

100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vinyl case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.

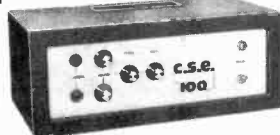

CSE 50

£29.50 Carr. free



sockets. Sturdy case, and an attractive fascia make this excellent value for money. Hundreds in use by groups, discos, clubs, etc. 50W version identical in appearance.

Four individually controlled FET input stages plus wide range bass and treble controls. 120W of speech and music output from twin loudspeaker

SAXON 100 COMPLETE AMPLIFIER

£53.00

Carr. free

SAXON 50

£37.50

Carr. free

CALLERS AND MAIL ORDER:

SAXON ENTERTAINMENTS LIMITED
327-333 WHITEHORSE ROAD · CROYDON CR0 2HS

(Please quote magazine when ordering)



SHOP HOURS: 9 a.m. - 5 p.m. — LUNCH 12.30 - 1.30 p.m. MAIL ORDER DESK: 10 a.m. - 3 p.m.
24-HOUR ANSWER SERVICE TEL. 01-684 6385

SEND 10p FOR OUR NEW 26-PAGE MANUAL which gives full details of the above products.
TERMS OF BUSINESS: C.W.O. or C.O.D. on receipt of 50p C.O.D. charge. Please include S.A.E. with all enquiries. VAT at 10% must be added to all orders including postage and carriage charges.

look! electronics really mastered

... practical
... visual
... exciting!

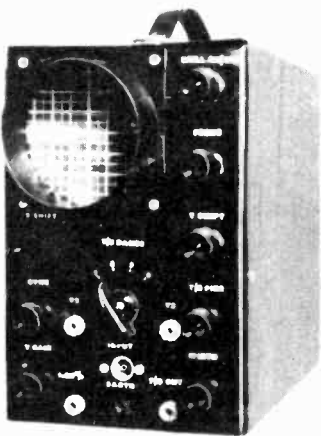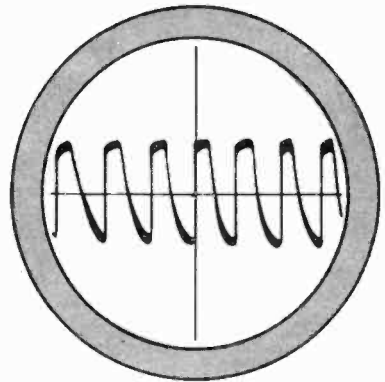no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

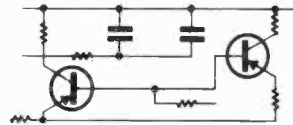2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, P.O. BOX 156, JERSEY. Please send your free brochure, without obligation, to: we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE EL64

special free gift also to all our students

MIND OVER MATTER

FOR long it has been customary to attribute all manner of so-called mystic powers to electro-magnetic forces generated within living bodies by bio-chemical processes. The intangible nature of electricity does of course make it an obvious choice when searching for an explanation of certain strange phenomena that cannot be accounted for by any mechanism within our normal range of experience and perception.

Knowledge of the electrical nature of all matter makes credible the proposition that an individual's personality radiates beyond the physical bounds of the body in some form of electro-magnetic energy. Nor does this idea have to be restricted to the animal world, but it can be applied to all biological systems including plants.

Is it therefore so very difficult and fanciful to take this line of argument yet a stage further and suggest that inanimate objects could also be endowed with some extraordinary abilities, that enable them (for example) to accept and respond to external, non-physical influences emanating from living bodies? Researches into psychical matters recognise this kind of phenomenon, and they call it psychokinesis.

If the medium for thought-transference is electro-magnetic radiation, then electronic circuits must indeed be high on the list of promising candidates for psychokinesis investigations. Especially those circuits designed to be susceptible to extremely minute signals. What an interesting thought—but what a nightmare for custodians of top security electronic installations!

This leads us to the reason why we consider such esoteric matters have a legitimate place in a magazine devoted to materialistic practicalities of electronics. The discussion is particularly timely because the writer of our *ESP, etc.* feature offers this month a circuit he has devised in order to conduct some simple "mind over matter" experiments.

Psychical investigations are, inevitably, largely influenced by the subjective responses of the individuals involved. But if electronic techniques can help in such investigations, for example in connection with psychokinesis, they ought to be tried out wherever possible—with a completely open mind. Through the sensible and carefully controlled use of electronic instruments by technically knowledgeable operators, a significant element of objectivity could be injected into the interpretation of the experiments.

Such persons are not likely to be confused or misled by such red herrings as spurious radiations and fortuitous rectification produced by random metallic contacts, or other effects "strange" to the uninitiated. Undoubtedly many reputed strange phenomena can be explained away as merely the manifestation of some well known law of physics. On the other hand variations in meter readings or in audio signals are not to be lightly dismissed as figments of the imagination. Such changes or responses have to be accounted for—malfunctioning of the equipment itself can be identified and so discounted.

All things being considered, it seems undeniable that there are certain phenomena deserving detailed and cautious investigation by the unprejudiced. To those who are intrigued by this subject there is a further challenge in developing special circuits to permit particular lines of investigation to be carried out.

F.E.B.

Editor

F. E. BENNETT

Editorial

R. D. RAILTON *Assistant Editor*
D. BARRINGTON *Production Editor*
G. GODBOLD *Technical Editor*
S. R. LEWIS B.Sc.

Art Dept.

J. D. POUNTNEY *Art Editor*
J. A. HADLEY
R. J. GOODMAN
K. A. WOODRUFF

Advertisement Manager

D. W. B. TILLEARD
Phone: 01-634 4202


P. J. MEW
Phone: 01-634 4210

C. R. BROWN, *Classified*
Phone: 01-634 4301

Editorial & Advertising Offices:

Fleetway House, Farringdon St.,
London EC4A 4AD
Phone: *Editorial* 01-634 4452
Advertisements 01-634 4202

BRIDGE

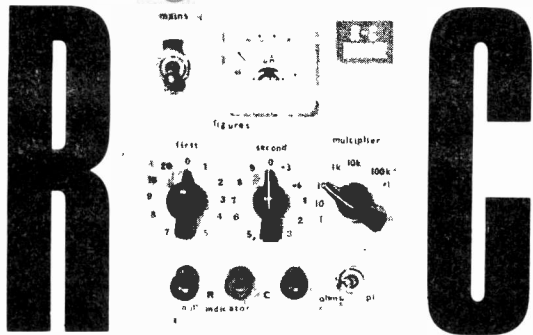

By D. W. EASTERLING

It is always useful to be able to confirm the value of a component, particularly these days when "job lot" packets of devices can be bought for low prices. Markings can be suspect and indeed in the case of capacitors can be obliterated.

Thus any instrument which is capable of measuring resistance and capacitance to a reasonable degree of accuracy is always welcome.

The R/C Bridge presented here is simple in construction and operation, and is capable of indicating resistance and capacitance over a sufficiently wide range to meet most needs. It does not set out to be either highly accurate or sophisticated, giving indication to two significant figures only and with accuracy figures of about 5 per cent on ohms and picofarads and 20 per cent on microfarads.

RANGES

The actual capacitance range covered is from 10pF to 1,090µF with indication from below 10pF and up to 2,000µF. Resistance can be measured from 0.3Ω up to 10.9MΩ, with indication up to 20MΩ. Resolution is two significant figures from 10Ω and 100pF.

The use of a switched digital readout in conjunction with a null-indicating meter avoids the calibration difficulties found with the normal analogue control system used in most bridges.

In fact, it is possible to carry out transformer ratio measurements and some inductance measurements with this instrument.

OPERATION

Operation is simple. Resistors are connected across a pair of input terminals R, as shown in Fig. 2 and capacitors across a further pair of terminals C. The centre terminal is common to both ranges. A mains switch is turned on, and the range toggle switch in line with the terminals is set to the appropriate position. Usually the approximate value of the component being tested is known, allowing the bridge to be set roughly before finally adjusting it to the

precise value. For example, suppose a 27kΩ resistor is being measured, the multiplier is set to 1k (3 noughts), the first figure switch to 2, and the second figure to 7.

Typical resistors may be a little more or a little less than the claimed value, and so the bridge is balanced by adjusting the second figure for minimum meter reading. If the meter is still tending to fall when the second figure is 0.3 or 9, the first figure should be set 1 or 3 as appropriate, and the second figure again adjusted for minimum meter reading.

Capacitors are similarly measured. A 0.47µF capacitor (470,000pF) should balance the bridge with the multiplier at 10k (4 noughts), the first figure at 4, and the second figure at 7. Slight variations can be expected according to the tolerance of the component being tested.

The actual value of a 10 per cent 27kΩ resistor would lie somewhere between 24 and 30kΩ.

If the value of the component being measured is completely unknown the bridge is balanced by moving the first figure and multiplier switches progressively through all combinations until a setting is found where the meter reading is tending to fall, and then make the final adjustment on the second figure switch as already described.

THE DESIGN

The measuring circuit is based upon the well known Wheatstone Bridge illustrated in Fig. 1. The applied voltage is common to both arms R_a , R_b and R_x , R_y , of the bridge with a null indicator connected across the centre points. The null indicator is used only to detect any potential difference between these points.

When the potential difference is zero or a minimum the bridge is said to be balanced, and in this condition $\frac{R_a}{R_b} = \frac{R_x}{R_y}$. It will be noted that it is unnecessary for both arms to have the same resistance values in order to satisfy the equation, only the ratios have to be the same.

When the bridge is used as a measuring device one branch is regarded as being the component under test; say R_x . The other branches are then made known values, then the equation can be rewritten $R_x = \frac{R_y \cdot R_a}{R_b}$.

For convenience in balancing the bridge it is normal to make one or more of the known branches adjustable. The advantages of this arrangement over an ohmmeter is that it is possible to produce a linear scale, and accuracy is then dependent on the known resistors, not the applied voltage or meter calibration.

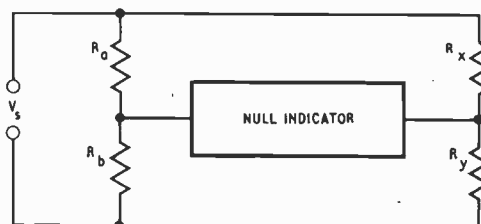


Fig. 1. The basic Wheatstone bridge circuit used in the present equipment

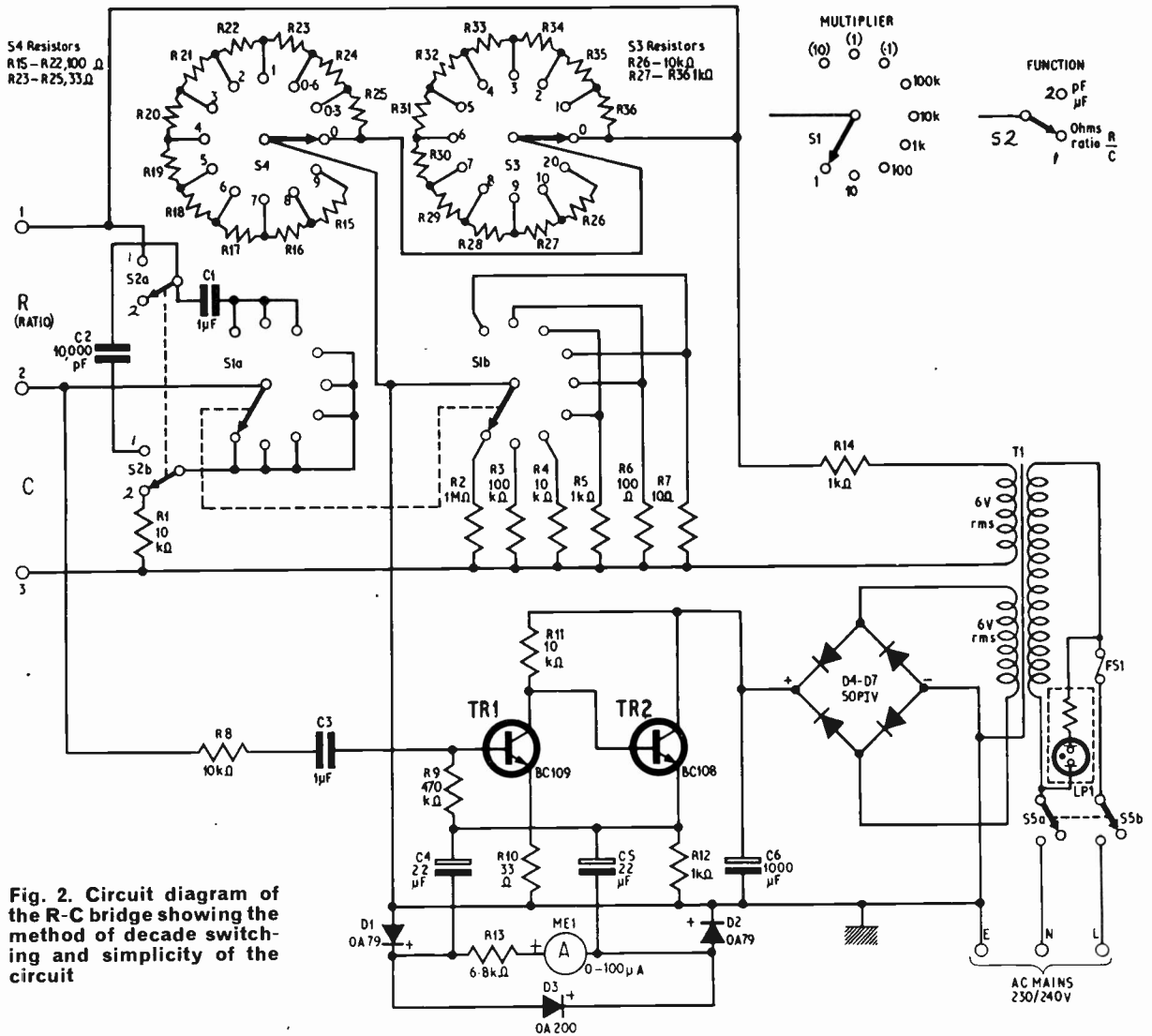


Fig. 2. Circuit diagram of the R-C bridge showing the method of decade switching and simplicity of the circuit

A further advantage is that the circuit is readily adapted to measure capacitance. In this case two capacitors, one the component under test, and the other a known standard, replace resistors R_x and R_y .

V_s must now be an alternating voltage, and the null indicator must be able to operate on a.c.

The bridge equation now becomes $\frac{R_a}{R_b} = \frac{X_{ex}}{X_{cy}} = \frac{C_y \cdot 2\pi f}{C_x \cdot 2\pi f} = \frac{C_y}{C_x}$ since the reactance of a capacitor equals $\frac{1}{C \cdot 2\pi f}$, and $2\pi f$ being the same for both capacitors cancels out.

PRACTICAL CIRCUIT


In the practical circuit illustrated in Fig. 2 the bridge includes the resistor being measured across terminals 1 and 2, the standard resistor R1, the multiplier resistor selected by switch wafer S1b, and the first and second figure variable resistors S4 and S3.

When capacitance is being measured it is placed across terminals 2 and 3, and toggle switch S2a/b is set to replace R1 by either C1 or C2 depending on whether the pF or μF ranges are selected by wafer S1a. Wafers S1a and S1b are of course mounted on the same switch assembly.

Switches S3 and S4 are detailed here and in Fig. 3 where it will be seen that they each consist of a 12-way single-pole switch arranged to select the appropriate resistance. Both assemblies start at 0 or zero resistance. The first figure S3 then increases in 1kΩ increments to 10kΩ plus a final jump of 10kΩ making a maximum value of 20kΩ.

This last step makes it easier to sense whether the multiplier should be increased, and also serves to push up the extreme range of the instrument to 20MΩ and 2,000μF.

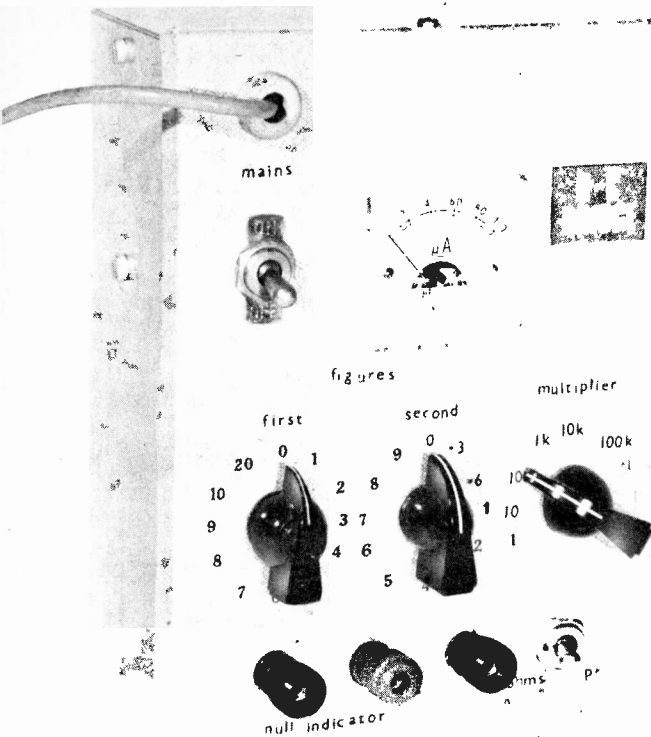The second figure S4 first increases in 33Ω steps to a nominal 100Ω, and then in 100Ω steps to 900Ω. The 33Ω steps makes it easier to sense whether the multiplier should be reduced, and also serves to push the lowest range of the instrument down to 0.33Ω.



ENERGISATION

The bridge energising voltage for both resistance and capacitance measurements is derived from a six volt winding on the mains transformer T1 via limiting resistor R14. The disadvantage of using a.c. for resistance measurements is that it limits the bridge to testing non-inductive components, although it does simplify the bridge circuitry. In practical terms the value of resistors can be measured, but not the d.c. resistance of transformers, chokes, and motors.

With no component on test the terminal voltage can rise to 6.3V r.m.s., or 10V peak. This may be thought to be an embarrassment when measuring electrolytic capacitors especially as no d.c. polarising voltage is provided. In practice this is not a problem because R14 together with the bridge impedance and the component under test effectively reduces the terminal voltage to 0.5V r.m.s. or less.

Modern electrolytic capacitors retain their dielectric characteristic long after the polarising voltage is removed, as was found when capacitors which had lain on the shelf for years still measured to their stated capacity.

This circuit differs from many published designs in that ratios as high as 2,000 : 1 are used instead of the more normal 10 : 1. This enables 2,000 μ F to be measured using a non-electrolytic 1 μ F capacitor as a standard. Electrolytic capacitors require a polarising voltage for constant use and are insufficiently accurate and stable for measurement work.

NULL INDICATION

The null indicator consists of a two transistor amplifier feeding a 100 μ A moving coil meter via diode detectors. The signal is passed from the bridge to the null detector via a limiting resistor R8 and isolating capacitor C3. Transistor TR1 is a common emitter voltage amplifier directly coupled to TR2, an emitter follower. The circuit is stabilised by the feedback loop R9 and emitter resistor R10.

The a.c. output from the null indicator is converted to d.c. by the full wave detector circuit C4/D1 and C5/D2 in order to drive the moving coil meter ME1. R13 in series with the meter produces a full scale deflection of 0.75V, but this combination is also shunted by a forward biased silicon diode D3 which starts to pass current at about 0.5V.

The result is that although the pointer can never go beyond the top end of the scale, maximum sensitivity is still available at the bottom end where the critical null point occurs. Such a non-linear response is of course ideal in this application.

POWER SUPPLY

The null indicator requires 9V d.c., and this is derived from a second 6V winding on the mains transformer via the bridge rectifier D4-7 and smoothing capacitor C6. It should be noted that this second winding on the transformer has to be completely isolated from that driving the bridge, because the earthy side of the null indicator is taken back to the junction of S4 and S1b as well as to the metal case. The mains transformer has a standard 230/240V primary which is connected to the live and neutral conductors of the mains lead via a double pole toggle switch. The earth conductor of the mains lead is taken direct to the metal case.

COMPONENTS . . .

Resistors

R1*	10k Ω	R7*	10 Ω	R13†	6.8k Ω
R2*	1M Ω	R8†	10k Ω	R14†	1k Ω
R3*	100k Ω	R9†	470k Ω	R15-22*	100 Ω (8 off)
R4*	10k Ω	R10†	33 Ω	R23-25*	33 Ω (3 off)
R5*	1k Ω	R11†	10k Ω	R26	10k Ω
R6*	100 Ω	R12†	1k Ω	R27-36	1k Ω (10 off)

* $\frac{1}{2}$ W 2% ElectroSil † $\frac{1}{2}$ W 5% Carbon

Capacitors

C1	1 μ F Tubular polyester 160V 10%
C2	10,000pF Polystyrene 160V 2%
C3	1 μ F Tubular polyester 160V 10%
C4	22 μ F Electrolytic 25V Wkg
C5	22 μ F Electrolytic 25V Wkg
C6	1,000 μ F Electrolytic 25V Wkg

Transistors

TR1	BC109	TR2	BC108
-----	-------	-----	-------

Diodes

D1	OA79	D2	OA79	D3	OA200
D4 to D7 Rectifier Bridge 50 p.i.v. $\frac{1}{2}$ A					

Switches

S1	2-Pole 9-Way
S2	2-Pole Changeover Toggle Switch
S3	1-Pole 12-Way
S4	1-Pole 12-Way
S5	2-Pole on-off Toggle Switch

Miscellaneous

Transformer T1 Eagle MT6 Primary 230/240V, Secondary 1, 6V $\frac{1}{2}$ A, Sec 2, 6V $\frac{1}{2}$ A
 Meter M1 SEW MR38P 1 $\frac{3}{4}$ inches square 100 μ A
 Aluminium box 7 x 5 x 2 $\frac{1}{2}$ inches
 Qty 3 Terminals 4mm with top socket
 Qty 3 Pointer knobs
 Qty 2 Miniature tag boards 12 tag each side
 Nuts, bolts, spacers, washers, solder tag, wire and Contact or Fablon.

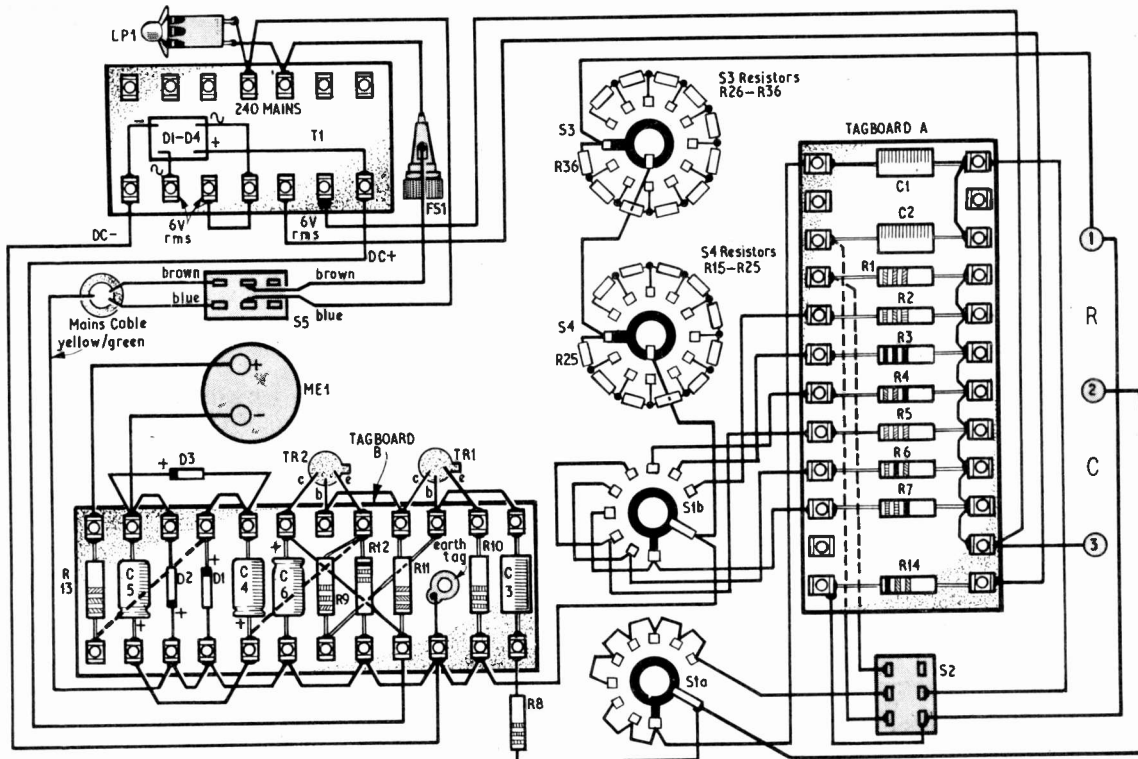


Fig. 3. Wiring diagram of the bridge illustrating the use of tag strips. Remember that S1a and S1b are mounted on the same shaft

CONSTRUCTION

The unit is housed in a standard aluminium box measuring $7 \times 5 \times 2\frac{1}{2}$ inches. All components except for the mains transformer and rectifier are mounted in the lid which becomes the front panel.

In order to provide a suitable background for the switch and terminal legends the front panel is covered with self adhesive vinyl sheet such as "Contact" or "Fablon". This material will take transfers and instant dry print lettering such as "Blick".

The lettering will rub off with a dry cloth, but is easily made permanent by applying a coat of varnish. Clear fingernail varnish is ideal. The vinyl sheet is applied after drilling the holes, but before the components are mounted. The whole panel including the holes is covered and the creases smoothed out. Finally the parts covering the holes are removed by working a half-round file along the edge of the hole. The lettering is applied after the components are mounted and the knobs fixed.

Care should be taken when fitting the terminals and switches to ensure that the securing nuts do not pucker the vinyl sheet. This can be avoided by using plain washers under the nuts, and the shakeproof washer under the front panel. The switches should be so oriented that the knob point positions conform to the layout shown.

The tagboards are mounted using 6BA bolts. Three-quarter inch spacers are used with tagboard A (see Fig. 3) so that it clears the terminals which it overlaps. The thickness of a full 4BA nut is sufficient for tagboard B to prevent the tags shorting out on the front panel. The bolt at the terminal end of this tagboard is fitted with an earthing solder tag and so provides connection to the metal case.

WIRING

The wiring diagram is shown in Fig. 3. The mains transformer is not mounted on the front panel but in the main box, and has to be connected to the front panel by flexible leads long enough to allow the box to be opened.

During the initial testing procedure it is a good idea not to wire the mains lead via S5 on the front panel, but to connect it direct to the transformer. The mains supply will then have to be controlled by the wall switch and only the low voltage supplies will come to the front panel which will receive the most handling.

Wiring the first and second figure switches S4 and S3 should present no difficulty. The main point to watch is that the component sequence starts at the correct tag. Fig. 3 shows the switch wipers at zero, the resistance value increasing as the wiper moves in a counter clockwise direction (clockwise when viewed from the front of the panel).

The high stability resistors used for these assemblies are fairly fragile, and the leads should not be bent or soldered within $\frac{1}{16}$ in of the resistor body. A heat sink such as the nose of a pliers should be used between the resistor and the joint being soldered.

To clarify the wiring diagram Fig. 3 shows wafers S1a and S1b as two separate switches. They are in fact mounted on the same switch assembly, and with the switch used by the writer they are actually two switches on the same wafer. Care should be taken to identify the tags clearly before the connections are made. The components associated with S1 are mounted on tagboard "A." The null indicator which is built as a separate assembly is on tagboard "B."

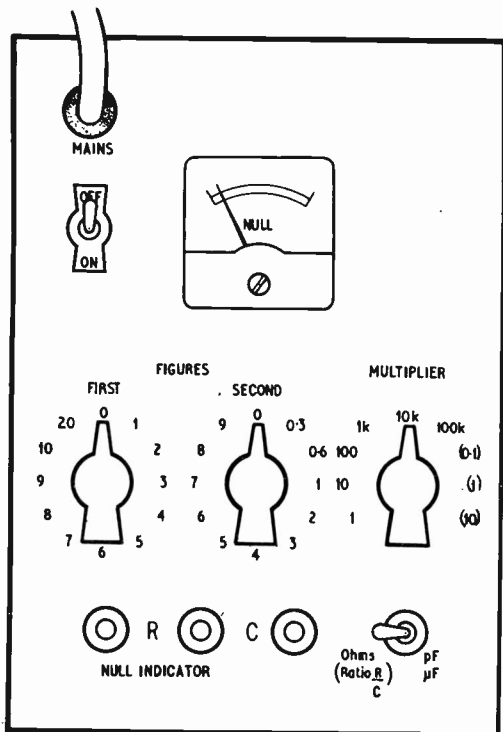


Fig. 4. The front panel showing the lettering used and general layout

Having checked the front panel wiring, the low voltage connections to the transformer may be made, and the unit assembled in its case for test. With the CR terminals unconnected and S2 switched to "ohms", the meter should read just below full scale at all positions of S1, S3 and S4, except when S1 is at (10), when the reading will be lower and drop to zero as S3/S4 are increased. Recommencing with S2 at pF and S3/S4 at maximum, the reading should again be just below maximum, falling when S1 is on 1, or as S3/S4 are decreased.


If the meter tends to go above full scale check R13, R14, and D3. If all is well try increasing R13 to 8.2kΩ. If the meter never exceeds 80μA, but otherwise appears to be working satisfactory, try decreasing R13 to 5.6kΩ. If all is now well try measuring a known component.

OPERATION

The following additional notes on operation may be of interest.

Resistance measurements can only be made with S2 on "ohms", and S1 in the first six ranges. The ranges in brackets refer to ratio measurements in this case.

Suppose the turns ratio of an output transformer is to be measured, the high impedance winding is connected across the R terminals, and the low impedance across C, the centre terminal being common to both. The bridge may then be balanced in the usual way. For example a turns ratio of 80 : 1 would be indicated with the multiplier on (1), S4 on 8, and S3 on zero. The correct ratio is that with the windings in phase. Out of phase connections give lower ratio readings.

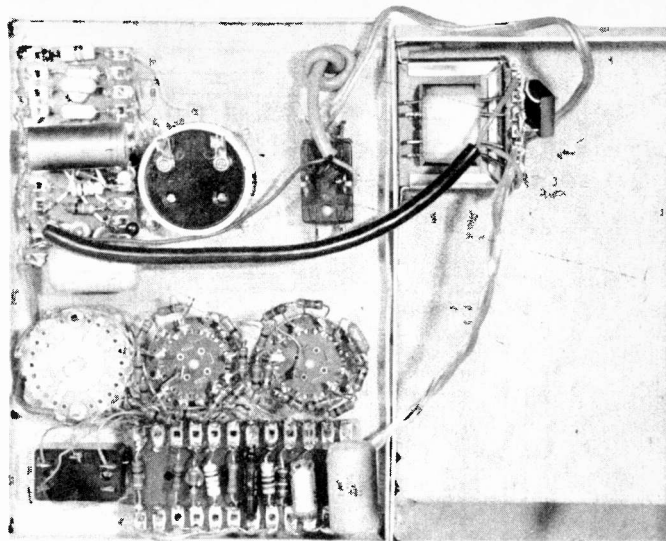

Component positioning in the prototype. The front panel is to the left and case to the right

INDUCTANCE

The ratio facility may sometimes be used to determine inductance. An unknown inductance across the C terminals can be expressed in terms of a known inductance across the R terminals. There are a number of problems associated with measuring inductance, and the particular bridge configuration used in this design is far from ideal. For instance both standard and unknown inductors may pick up hum and so invalidate the null reading.

Practical inductors have d.c. resistance which in this design is not balanced out. Stray capacitance across the windings may also have an effect. Additionally the inductance of iron cored components vary to some extent according to the d.c. current flowing through the winding, and no provision has been made for this in the equipment described.

CAPACITANCE

Capacitance measurements are made with S2 switched to "pF (μF)". This means that the first six ranges of S1 relate to picofarads and the last three ranges shown in brackets to microfarads. It will be noticed that the 100k pF range is duplicated by the 0.1 μF range. This arrangement is really due to the multiplier range being required for ratio measurements when S2 is on "ohms".


Nevertheless it is available and has the advantage that one range can be checked against the other using any external capacitor within the range 1μF to 10μF. It should be noted that the terminal voltage on the 100k pF range is less than when S1 is on (0.1) μF, and is a consideration when checking very low voltage working capacitors.

One final note is that the unit may be employed simply as a null indicator for use with some other type bridge or test equipment. For this purpose S1 is set to (10), S2 to "ohms", and S4/S3 to zero. Under these conditions the frequency response is flat from below 20Hz to above 30kHz, and the sensitivity for a mid range reading of 50μA is 12.5mV r.m.s. The input voltage should not be allowed to exceed 6V r.m.s.



Provided your car has an electric fuel pump, this meter can be fitted to give a continuous reading of fuel consumption so that speed can be adjusted for greatest economy

M.P.G

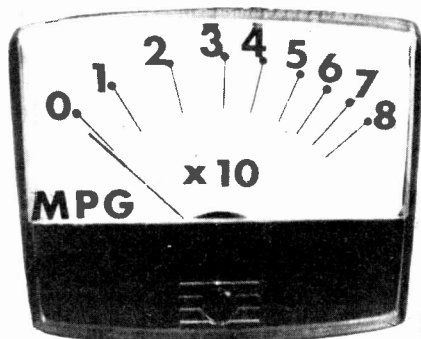

METER

By S. JONES

THE CIRCUIT to be described counts the number of rotations of the rear wheels in the time it takes the fuel pump to complete one pumping cycle. The greater the number of wheel revolutions during one pumping cycle, the higher the "miles per gallon" figure.

To count the revolutions of the rear wheel a diode pump counter is used, being operated by a reed relay and two magnets in the rear wheel.

CIRCUIT DESCRIPTION

The circuit diagram of the Miles per Gallon Meter is shown in Fig. 1. Capacitor C2 charges up via R2, D2 and C3.

When the reed relay contacts RLA1 are closed by a magnet on the rear wheel, C2 is discharged via D3 but the charge on C3 remains.

After contacts RLA1 are released by the magnet, C2 is again charged and the voltage on C3 increased by a step almost equal to its original voltage. The voltage on C3 increases in equal steps each time RLA1 is operated and continues to increase until the fuel pump operates which momentarily discharges C3 via D4 and D5.

This maximum voltage reached by C3 is a measure of the miles per gallon. It can be seen from Fig. 2 that twice the fuel consumption and twice the speed results in the same peak value on C3 and hence the same meter reading.

Transistor TR1 forms an emitter follower, the voltage across the meter being virtually equal to that across C3. Diodes D4 and D5, being silicon diodes, short C3 to their forward voltage of about 0.7V and this compensates for the base to emitter voltage drop of TR1; two diodes are used to ensure a low forward resistance.

Capacitor C4 is incorporated to ensure that readings do not fluctuate wildly as C3 is charged and discharged. However, it must be small enough to

COMPONENTS . . .

Resistors

- R1 56 Ω
- R2 47 Ω
- R3 4.7k Ω
- R4 2.2k Ω
- All $\pm 10\%$ $\frac{1}{2}$ W carbon

Potentiometer

- VR1 5k Ω skeleton preset

Capacitors

- C1 1000 μ F 12V elect.
- C2 12.5 μ F 64V elect.
- C3 470 μ F 10V elect.
- C4 1000 μ F 12V elect.

Diodes and Transistor

- D1 10V 1W Zener diode
- D2, D3 OA81 (2 off)
- D4, D5 1N4001 (2 off)
- TR1 2N2926 (-ve earth) 2N3702 (+ve earth)

Miscellaneous

- ME1 1mA f.s.d. meter
- RLA1 1in reed relay
- $\frac{1}{2}$ in dia button magnets (Eclipse) (2 off)

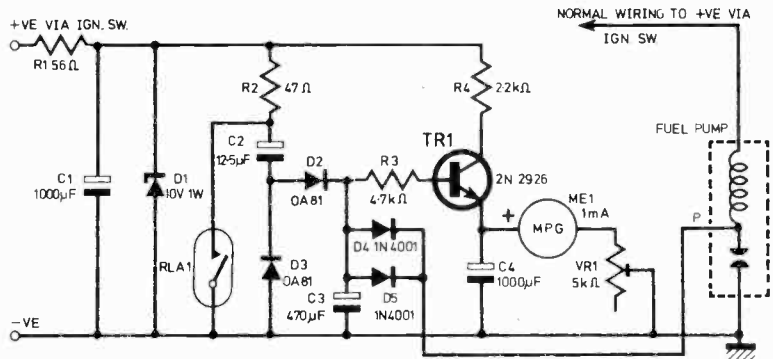


Fig. 1. Complete circuit diagram of the Miles per Gallon Meter. The circuit shown here is for the negative earth system. TR1 should be altered to a 2N3702 and all diodes and capacitors reversed for positive earth

Fig. 2. Doubling the speed and doubling the fuel consumption keeps the m.p.g. reading the same


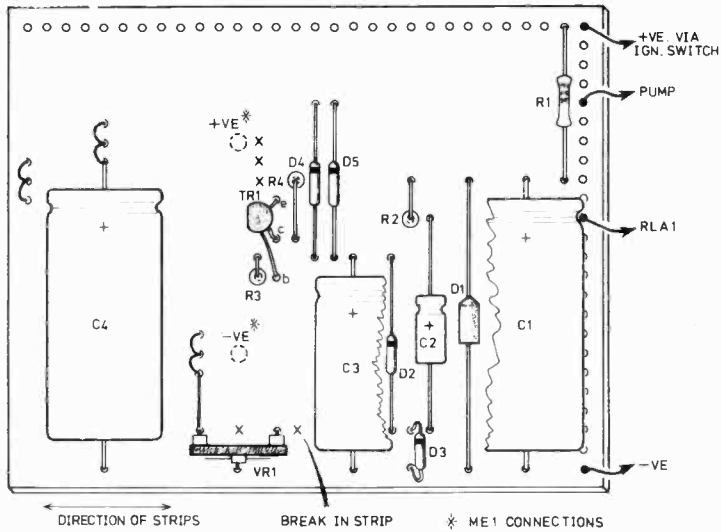
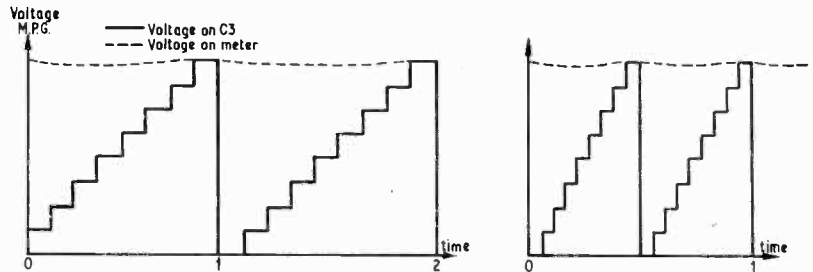


Fig. 3. Layout of the components on the Vero-board. This panel is mounted directly on the meter. Holes should be drilled to suit meter

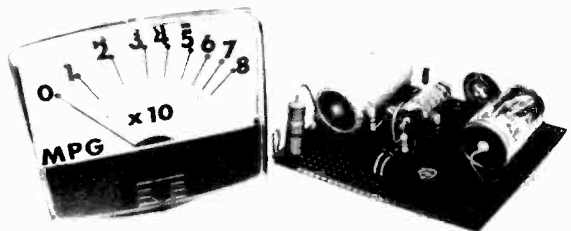Photograph of the completed Miles per Gallon Meter.



allow the meter reading to fall to a higher consumption value in a reasonable time. The values indicated proved to be the most satisfactory, readings below 30 m.p.g. being steady ± 1 m.p.g., while those above 30 m.p.g. are in themselves only temporary during gear changing, braking, etc.

A scale to 80 m.p.g. was required with a 1,600cc Capri, though under heavy braking some overloading of the meter movement occurs as the pointer attempts to reach perhaps 100 m.p.g.

CONSTRUCTION

Construction is on 0.1in matrix Veroboard, 24 holes by 31 as shown in Fig. 3. This was mounted directly onto the meter in the original, and sufficient room has been left to move the mounting holes to suite individual meters. The board may of course be mounted separately from the meter.


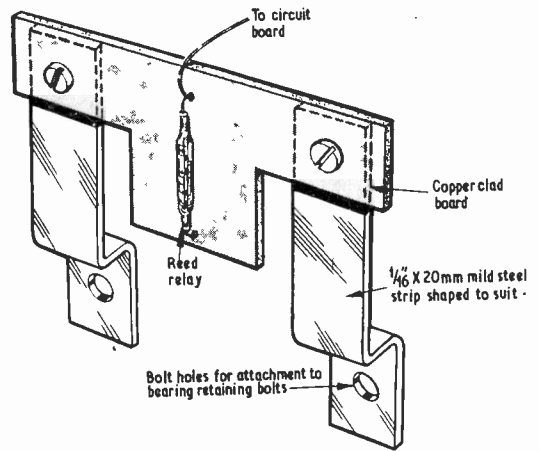


Fig. 4. Mounting details for the reed relays

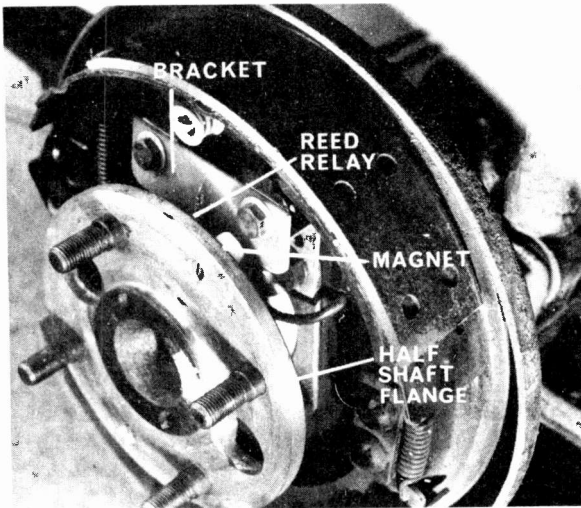

Photograph of the reed relays mounted on the half shaft flange

impede the brake action. No deterioration of the magnets has been noticed despite the temperatures inside the drum.

Four nuts retaining the wheel bearing will be noticed behind the half shaft flange—two of these can be removed through the two large holes in the half shaft flange and used to attach a strong bracket (see Fig. 4) which holds the reed vertically about 15 thousandths of an inch from the magnet.

Check the operation of the reed, ensuring that it closes twice only per revolution, and then earth one connection, and passing a wire through a small hole in the backplate, connect the other to the electronics inside the vehicle. Allow plenty of slack for rear axle movement.

FUEL PUMP

This component requires little modification. Attach a wire to the internal upper fixed contact (see photograph) and lead out the wire through a small hole

Photograph of an SU fuel pump with the cover removed showing the new connection which has to be made

POSITIVE EARTH VEHICLES


The same Veroboard can be used for positive earth vehicles, although all the capacitors and diodes (including D1) must be reversed in polarity and TRI changed for a 2N3702.

The pump and reed connections are identical, though the positive and negative supply connections to the Veroboard must be reversed.

WHEEL MAGNETS

A reed relay inside a rear brake drum is closed twice every revolution (every 0.037 sec at 60 m.p.h.), by two magnets bolted to the inside of the half shaft flange. The photograph shows how they are arranged. (The half shaft flange is the disc to which the wheel bolts are attached.)

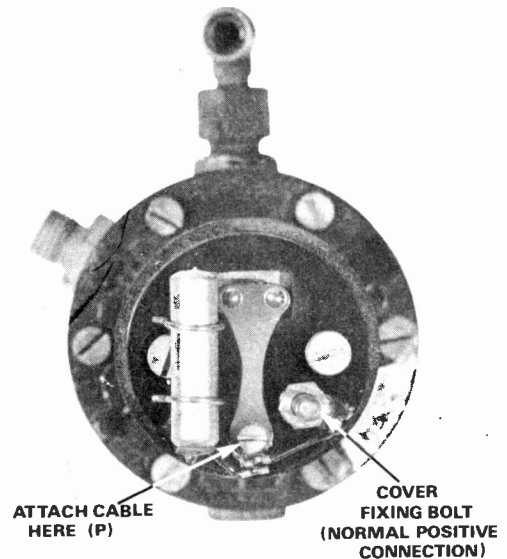Many cars will already have one hole drilled in the flange and this can be utilised—the steel is soft and can be easily drilled with a sharp 5/32in drill. Use countersunk 4BA bolts with nylock nuts to hold the magnets, as they must not shake loose to



in the case. When the pump is in normal use this wire will be connected to earth via the pump contacts each time the pump completes a pumping stroke.

Cars normally fitted with mechanical pumps will require the fitting of an electric type, but this need not be expensive if one is purchased from a breakers' yard.

The mechanical pump can be left on the car for emergency use, should the electric pump fail.

TESTING AND CALIBRATION

Before testing, fit a normally open switch between the RLAI terminal of the Veroboard and earth and the "PUMP" terminal and earth. These switches will simulate the operation of pump and reed during calibration and testing.

Connect to a suitable voltage supply and with VR1 set to its maximum, operate the "reed" test switch a few times—the meter needle should deflect and return very shortly to zero. Operate the RLAI test switch until half full scale deflection occurs, and then operate the "PUMP" test switch. The meter needle should return to zero quite quickly.

It is now necessary to calculate the number of miles per gallon indicated by each step of the diode pump counter:

$$\text{m.p.g. per step} = \frac{\text{fuel pump strokes per gallon}}{\text{revolution of wheel} \times \frac{\text{number of wheel magnets}}{\text{per mile}}}$$

The number of fuel pump strokes per gallon depends on the pump used, but will be in the range 2,500 to 3,500.

MEASURING FUEL CONSUMPTION

Connect the pump to the battery and restrict the outlet from the pump so that the strokes are slow enough to be counted. If the pump cannot be removed, disconnect at the carburettor.

Allow the pump to deliver one pint of fuel, counting the strokes, and multiply this number by eight. Paraffin is easier to handle than petrol, particularly if the pump is not yet fitted to the car.

Wheel revolutions per mile are shown below—do not try to measure the circumference of the tyre with string—a true rolling circumference is required as shown in Table 1.

Table 1: TYRE CIRCUMFERENCES

Wheel Diameter (in)	RADIAL Rev/mile	CROSSPLY Rev/mile
10	1082	1080
12	955	954
13	889	866
14	871	820
15	820	800
16	758	748

Once the calculation has been completed it is easy to adjust VR1 so that the required number of steps gives a full scale deflection of 80 m.p.g. Halve the number of steps to calibrate for 40, 20 and 10, etc.

It will be noticed that the scale is non linear; however, this is an advantage as accurate readings are of more use at low miles per gallon.

The meter can now be installed and will require no further adjustment. ★

POINTS ARISING

ANYONE AT HOME? (April 1974)

In the Veroboard diagram, Fig. 6, there should be no breaks at D29 or F21, and there should be a break at F19.

AUTO CHARGER-REGULATOR (February 1974)

In Fig. 2, the power supply pins to IC1, pins 7 and 4 should be transposed so that pin 4 goes to negative and 7 to positive.

BOOLEAN ALGEBRA—Part 2 (April 1974)

In Fig. 2.5, in the second row of integrated circuits from the left, the bottom left pin should go to the 5V line.

On the strip side two breaks are missing (a) in the ninth row from the top, between the short wire link and the capacitor body (b) in the ninth row from the bottom between the leftmost pair of diode bodies.

In Figs. 2.5 and 2.6 wires running from panel to Veroboard should be re-routed thus: wire D (panel) to ground line (Veroboard); wire R (panel) to Q (Veroboard); wire Q (panel) to D (Veroboard).

SLOW TIME BASE OSCILLATOR

(Ingenuity, March 1974)


Resistor R3 should be connected between R4 and R5, and not between R1 and R4 as shown. This error causes non-linearity in the ramp output slope at lower frequencies.

SEMICONDUCTOR TESTER (October, November 1973)

R12 in the components list may be made up from 5.1Ω, 5.1Ω, and 8.2Ω in parallel.

In the components list R17 should have been 10kΩ as in the circuit diagram.

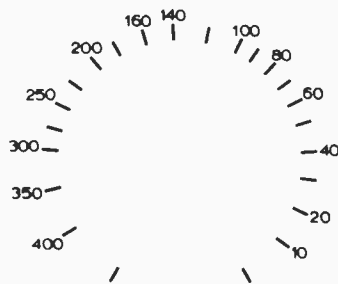We reproduce here a scale suitable for the "h" potentiometer which gives reasonable accuracy.



9V BATTERY ELIMINATOR (December 1973)

C1 in Fig. 1 should be 1,000μF as in the components list.

POWER SUPPLY FOR I.C.s (January 1974)

For use at currents greater than 40mA an MJE520 should be substituted for the BFY50 output transistor.

RHYTHM GENERATOR (March 1974)

In Fig. 3 the diagram showing the pin connections for IC1-IC3 is incorrect. GND should go to pin 11 and 4-7V to pin 4. IC4-IC5 is as shown.

In Fig. 4 the diagram of LP1 should show pin 10 connected to 4-7V not common.

INGENUITY UNLIMITED

A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. This is YOUR page and any idea published will be awarded payment according to its merits.

LOGIC CIRCUIT TESTER

WHEN experimenting with logic circuits, a source of individual pulses or series of pulses is often required. The circuit in Fig. 1 was built for low speed testing of TTL in breadboard circuits. It generates either a continual train of 10 millisecond pulses at the rate of 1 p.p.s. or 1 to 10 pulses via a telephone dial. Positive or negative going outputs are available.

The pulse generator is an SN74121 monostable multivibrator. The duration of the output pulse is governed by the timing components R3 and C2. R3 should not exceed 40 kilohms.

The pulse is generated whenever the input signal on pin 5 goes positive. With the switch in the "Dial" position, this point is held to ground via the intermittent contacts in the dial mechanism. When a number is dialled, these contacts open that number of times and generate the required number of pulses. With the switch in the "Osc" position, the input is held to ground via the output load of a unijunction oscillator. When the timing capacitor C1 discharges through the transistor, a positive pulse of about 2.5 volts appears across the load resistor and this operates the pulse generator. With the values shown, the frequency will be about 1 pulse per second.

Note that a spurious pulse is generated when the switch is operated. Each output of the device has a fan-out of 10.

A. Langton
Aberdeen.

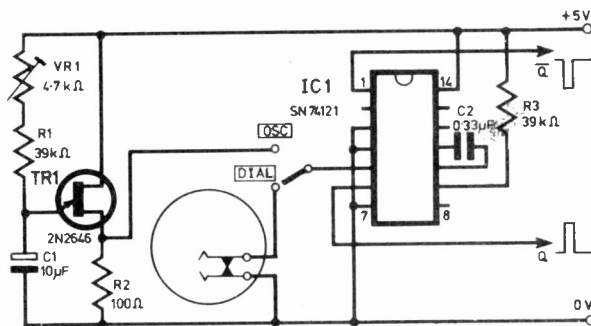


Fig. 1. Circuit diagram for the logic tester

TOUCH SWITCH WITH DELAYED SWITCH-OFF

THE circuit shown in Fig. 1 was originally designed as a "gimmick" to light a bulb when an "Aladdin's Lamp" was rubbed. It will doubtless find many other uses, the most obvious being an enlarger timer.

The circuit operates in the following way. Normally CSR2 is off and RLA de-energised, thus CSR3 is also off as contacts RLA2 are open. When the

plate is touched a small current flows through R1 and R2 triggering the silicon controlled switch CSR1. This brings on thyristor CSR2 and hence RLA. As thyristor CSR2 is supplied with smoothed d.c. from D2, D3, it latches on. Contacts RLA2 close and d.c. is applied to the timing network R6, R7, VR2 and C2. As C2 charges it eventually reaches a potential close to that set by the divider R9 and R10. In this condition CSR4 is triggered which brings on thyristor CSR3, whose anode is suddenly brought close to its cathode potential and the resulting signal is fed to the anode of CSR2 via C3 switching it off.

The cycle can be repeated by once more touching R1.

The sensitivity of the circuit is determined by VR1. Diac D1 clamps the potential at which CSR1 fires, ensuring that triggering occurs early in the mains cycle. This also reduces mains interference.

The length of the delay time is set by VR2 and longer delays can be achieved by increasing VR2 and C2. If R9 is increased extra delay time at the expense of range can be obtained.

A. J. Woollard,
Devon.

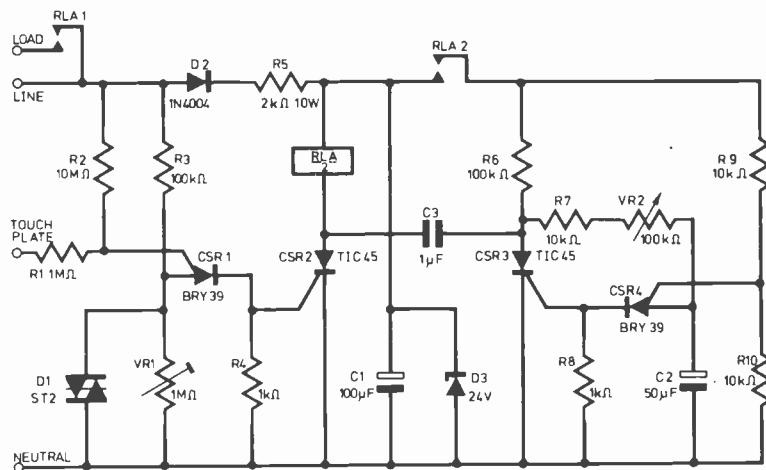


Fig. 1. Circuit of touch switch with delayed switch-off

VOLTAGE SHARING IN STABILISED POWER SUPPLIES

ONE OF the problems associated with stabilised supplies is the amount of heat dissipated in the series transistors. The usual solution to this problem is to use a parallel combination of two or more devices to share the current.

This presents a difficulty as transistors used in this manner usually need matched characteristics, with large wattage resistors in the emitters to make the current sharing as equal as possible.

The method described here does not require matched devices but is still very effective.

Instead of current sharing, voltage sharing is used. The circuit is shown in Fig. 1. Assume to begin with that TR1 is saturated so that the input voltage (V_{in}) minus the output voltage (V_{out}) will be dropped across TR2.

This voltage is fed back via a Zener diode and resistor to TR1 in such a way as to turn off TR1. This means that TR1 begins to turn off when the voltage across TR2 reaches a voltage determined by the Zener diode and the two resistors R1 and R2. The values in the diagram were chosen to give near equal sharing with 5V output, 35V input and 1A of current.

The graph of Fig. 2 shows how the power is shared between the two transistors.

To establish the voltage across TR1, use the formula

$$V_{CE(TR1)} = \frac{R_1}{R_1 + R_2} (V_{in} - V_{out} - V_z)$$

This means that only TR2 will be effective until the voltage causes the Zener diode to conduct, i.e. when $V_{in} - V_{out} \geq V_z$. R1 must be sufficiently small to supply enough base current to TR1 to saturate it at maximum current.

D. W. Lloyd,
Biggleswade.

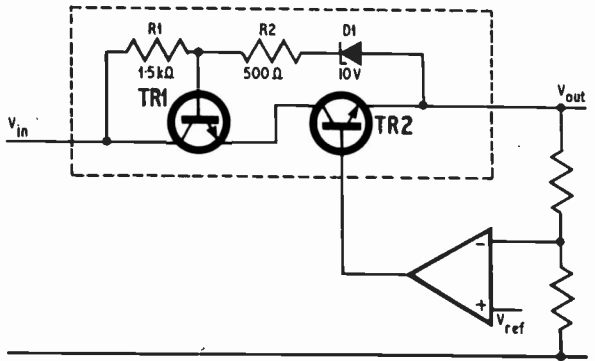


Fig. 1. Circuit diagram for a voltage sharing power supply

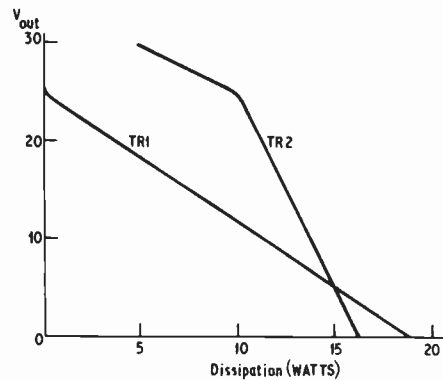


Fig. 2. Graph showing how the power is shared between TR1 and TR2

CIRCUIT BOARD PREPARATION

IT TAKES some time to prepare a printed circuit board so Veroboard is the usual answer. Veroboard is quite expensive and not always to hand. The narrow width of the strips is not always convenient.

Two simple tools which make it possible to prepare a printed circuit board in a short time will be described.

A clamp is made from two pieces of flat iron $1\frac{1}{2}$ in \times $\frac{1}{8}$ in \times 8in. Drill a hole in each end for a $\frac{3}{16}$ in screw.

The second tool is a wooden handle with a slot in it so that a piece of used hacksaw blade, 4in long and ground on each side, can be fitted.

To prepare a circuit board, put a piece of copper clad board in the clamp, tightening both screws, leaving a strip the required width protruding (Fig. 1). With a slow movement, scribe a slot in the copper, checking to see that no shorts are left at the end of the process. After this, drill holes only where you need them.

E. Koren,
Israel.


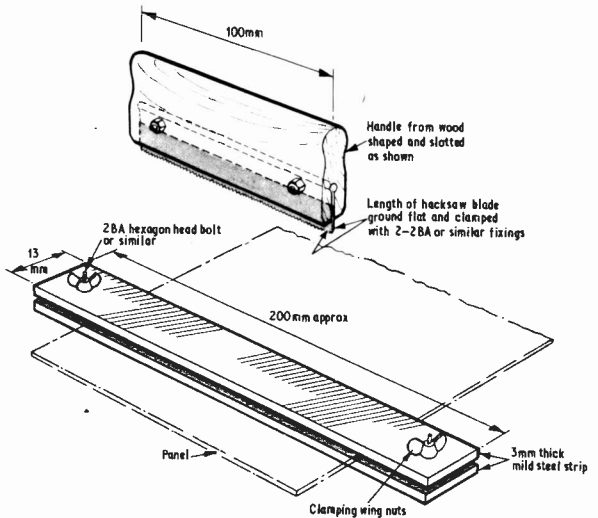


Fig. 1. Two aids for making circuit boards


GENESIS

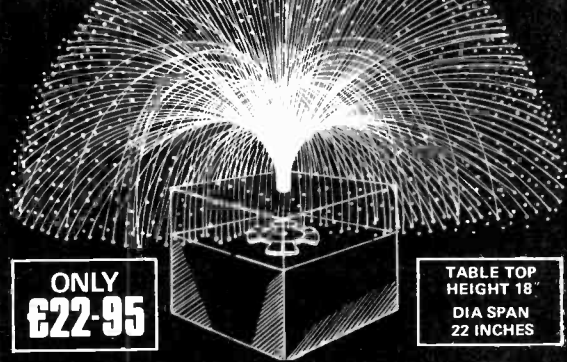

**ONLY
£22.95**


**TABLE TOP
HEIGHT 18"
DIA SPAN
22 INCHES**

At the head of our fibre optic kingdom stands the unique genesis. This fantastic model incorporates the largest mares tail you can buy. Now combined with the most sensational kinetic light base ever designed in this field. This lamp is unique in the way that the base is opaquely translucent. The tinted upper section allows one to see a slowly rotating eight coloured sculptured wheel, that seems to be floating on a blue haze, that radiates a warm mystic glow. Thousands of optical fibres energized with colour. Fibre tips flash like stars, bright with all the changing colours of the rainbow. Available in blue or green. M.M. Discount price £22.95 inc p.p. and VAT.

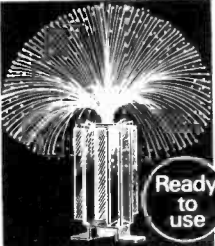

Ready to use

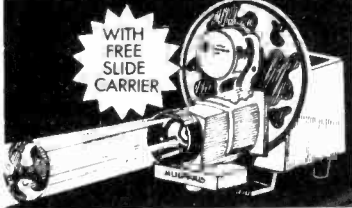CASCADE Height 18" Cascade, the fibre optic that's also a beautiful corner light. M.M. Discount price £16.65 inc p.p. and VAT.



AQUARIUS 100
A star for home parties, this budget priced 100-watt projector will transform your room into a swirling image of continuously changing liquid colour of reds, blues, yellows and greens. This machine is supplied with one six inch liquid wheel and includes lamp and lead. Complete with free 2 x 2 slide projection carrier. M & M discount price £19.95 post free.



Ready to use

LITTLE GEM
Little Gem, complete with the smaller mares tail, (8mm approx., 18" x 10" high, overall height from table approx 14"). With a single white light display, housed in a red translucent base, cowled with a special moulded three dimensional filter that throws light in array. It's amazing, we have completely shattered the style of conventional optics with the fabulous little gem.
ONLY £10 inc post and VAT.
OIL WHEEL PROJECTORS
Multi-coloured. For projecting psychedelic colours 6" or 4" diameter. Ideal for fibre optics.
6" oil wheel £5.00 + p.p. 15p.
4" (suitable for optics) £2.65 + p.p. 10p.

D.I.Y. SECTION
THE SENSATIONAL MARES TAIL
Three sizes to choose from:
18mm ferrule, 11" high x 22" dia. 7,500 fibres, £10.50 +20p p.p.
12mm ferrule, 10" high x 19" dia. 4,800 fibres £7.85 +12p p.p.
8mm ferrule, 10" high x 18" dia. 2,900 fibres £4.95 +10p p.p.
Complete instructions supplied.




Display bunching of various types of fibres at low cost. **TYPE A 1320.** Fibres contained in a tough flexible sheath. Makes delightful displays. M.M. Discount Price 40p per ft. £1.10 per yd. +5p p.p.
TYPE B. Light guides comprising of 64 fibres. Each fibre .010 inch diameter in a flexible sheath 1/8 inch. 45p per ft. £1.28 per yd +5p p.p.
TYPE C. Monofilament .040 dia, single strand flexible plastic that enables heat bending for combined use with type A or type B. 22p per ft. min order 3ft 66p +5p p.p.

SLOW SPEED MAINS MOTOR
to rotate oil wheel and static wheel 70p inc p.p.
STATIC COLOUR DISC
M.M. Discount price £1.40 inc post. Specially made for optics. Complete with metal boss. To fit motor. 4" dia, seven prominent colours contained in separate sections. Bulb and baton kit plus 6ft of flex 75p inc post and VAT.

Terms: C.W.O. cheques/po's
C.O.D. please send 50 pence when ordering

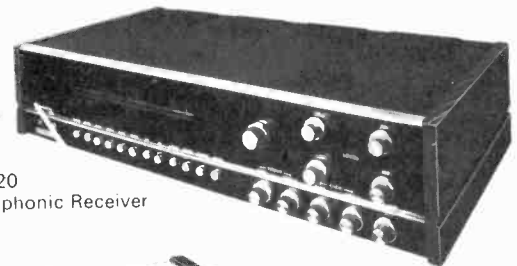BUY WITH CONFIDENCE FROM A FIRM WITH A NATIONAL REPUTATION
MIDLAND MATERIALS
OPTICS. 180 WELLINGBOROUGH ROAD, NORTHAMPTON. TEL. 33487



AR-2020 Quadraphonic Receiver




Digital Thermometer ID-1390



Pocket Calculator IC-2000



Small Engine Tune-Up Meter CM-1045

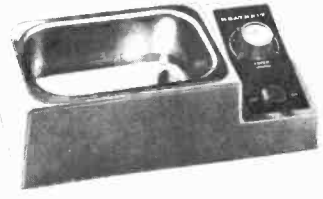


Ultrasonic Cleaner GD-1150

there's always something new from Heathkit

Handcrafted electronics with kit savings and plus values. Whatever your requirements ... Quadraphonics. Calculators. Digital home electronics, Ultrasonics, Automotive testers, etc., we offer something for every interest - every walk of life. Want to know more? Read all about the wonderful world of Heathkit electronics in the FREE Catalogue.

Free

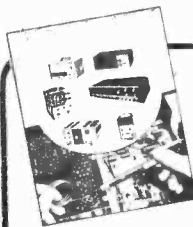

Please send me the FREE Heathkit Catalogue & details of Monthly budget plans

NAME _____

ADDRESS _____

**HEATH
Schlumberger**

HEATH (GLOS) LTD DEPT PE/6/74
Bristol Road,
Gloucester GL2 6EE

SHOWROOM LONDON. 233 Tottenham Ct. Rd.



GIRO NO. 331 7056
 C.W.O. only. P. & P. 10p on orders below £5
 Discount: £10-10%, £20-15%, (except net items)
 Export Order enquiries welcome (VAT free)
 Official Orders accepted from
 Educational & Government Departments

SPECIAL RESISTOR KITS (Prices include Post and Packing).
 10E12 1W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3-65 net
 10E12 2W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3-85 net
 25E12 1W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8-35 net
 25E12 2W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8-45 net
 20E12 1W KIT: 20 of each E12 value, 22 ohms—1M, a total of 1140 (METAL FILM 5%), £11-05 net
 15E12 1W KIT: 15 of each E12 value, 10 ohms—1M, a total of 915 (METAL FILM 5%), £13-35 net
 10E12 2W KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (METAL FILM 5%), £17-15 net

MULLARD POLYESTER CAPACITORS C280 SERIES
 250V P.C. Mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 3p, 0.068µF, 0.1µF, 4p, 0.15µF, 4p, 0.22µF, 5p, 0.33µF, 8p, 0.47µF, 9p, 0.68µF, 12p, 1µF, 15p, 1.5µF, 23p, 2.2µF, 26p.

MULLARD POLYESTER CAPACITORS C296 SERIES
 400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 2p, 0.0047µF, 3p, 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 3p, 0.047µF, 0.068µF, 0.1µF, 4p, 0.15µF, 6p, 0.22µF, 8p, 0.33µF, 12p, 0.47µF, 15p.

MINIATURE CERAMIC PLATE CAPACITORS
 50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, 10K (µF) 0.01, 0.015, 0.02, 0.033, 0.047, 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1µF.

POLYSTYRENE APACITORS 160V 5%
 (pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 4p, 10.000, 4p.

RESISTORS
 CF—High Stab Carbon Film 5%, MF—High Stab Metal Film, 5%.

W. Type	Range	1-99	100-499	500-999	1000+	Size mm
CF	22-1M	1	0.75	0.60	0.55	2.4 x 7.5
CF	22-2M2	1	0.75	0.60	0.55	3.9 x 10.5
CF	22-1M	1	0.75	0.60	0.55	5.5 x 16
MF	10-2M7	2	1.54	1.32	1.1	3 x 7
MF	10-2M2	2	1.43	1.21	0.99	4.2 x 10.8
MF	10-10M	3	1.98	1.81	1.65	6.6 x 18
MF	10-10M 4.5	3	3.52	3.08	2.75	8 x 17.5

For value mixing prices, please refer to our catalogue (price in pence each).
 VALUES AVAILABLE—E12 Series only. Net prices above 100.

PRESET SKELETON POTENTIOMETERS
 MINIATURE 0.25W Vertical or horizontal 6p each
 1K, 2K, 4K7, 10K, etc. up to 1MΩ
 SUB-MIN. 0.05W Vertical. 100Ω to 220KΩ 5p each

Wavechange Switches
 1P, 4W: 1P, 12W: 2P, 2W: 3P, 4W: 2P, 6W: 3P, 3P: 4P, 2W: 3P, 4W: 4P, 3W, 26p

B. H. COMPONENT FACTORS LTD.

(P.E.) 61 CHEDDINGTON ROAD, PITSTONE,
 NR. LEIGHTON BUZZARD, BEDS. LU9 9AQ
 Tel.: Cheddington 668446 (Std. Code 0296)
 PLEASE WRITE FOR FREE CATALOGUE

Miniature Mullard Electronics

1.0µF 63V	6p	68µF	16V	6p
1.5µF 63V	6p	68µF	63V	12p
2.2µF 63V	6p	100µF	10V	6p
3.3µF 63V	6p	100µF	25V	6p
4.0µF 40V	6p	100µF	63V	14p
4.7µF 63V	6p	150µF	16V	6p
6.8µF 63V	6p	150µF	63V	15p
8.0µF 40V	6p	220µF	6V	6p
10µF 16V	6p	220µF	10V	6p
10µF 25V	6p	220µF	16V	6p
10µF 63V	6p	220µF	63V	21p
15µF 16V	6p	330µF	16V	12p
15µF 63V	6p	330µF	63V	25p
16µF 40V	6p	470µF	6.4V	9p
22µF 25V	6p	470µF	40V	20p
22µF 63V	6p	680µF	16V	15p
32µF 10V	6p	680µF	40V	35p
33µF 16V	6p	1000µF	16V	20p
33µF 40V	6p	1000µF	25V	25p
32µF 63V	6p	1500µF	6.4V	15p
47µF 10V	6p	1500µF	16V	25p
47µF 25V	6p	2200µF	10V	25p
47µF 63V	6p	3300µF	6.4V	26p

VEROBOARD 0-1 0.15

2 1/2 x 5"	28p	28p
2 1/2 x 3 1/2"	26p	19p
3 1/2 x 5"	32p	33p
3 1/2 x 3 1/2"	28p	28p
2 1/2 x 1 1/2"	7p	7p
2 1/2 x 5" (Plain)	—	14p
2 1/2 x 3 1/2" (Plain)	—	12p
5 x 3 1/2" (Plain)	—	22p
Insertion tool	59p	59p
Track Cutter	44p	44p
Pins, Pkt. 25	10p	10p

TRANSISTORS

AC126	16p	BC212L	12p
AC128	22p	BC213L	12p
BC107	11p	BC214L	17p
BC108	12p	OC44	18p
BC109	13p	OC71	13p
BC148	12p	OC81	16p
BC149	12p	OC170	23p
BC182L	12p	TIS43	33p
BC183L	12p	2N2926	11p
BC184L	13p	2N3702	11p

POTENTIOMETERS
 Carbon Track 5KΩ to 2MΩ, log or lin. Single, 16p, Dual Gang 46p, Log Single with Switch 26p.
 Slider Pots, 10K, 100K, 500K, 30mm, 34p, 45mm, 47p, 60mm, 55p.

DIODES

IN4001 6p	12p
IN4002 7p	13p
IN4003 9p	15p
IN4004 9p	15p
IN4005 12p	18p
IN4006 14p	22p
IN914 7p	10p
IN916 7p	10p
BA100 10p	10p
OAS 42p	10p
OA47 9p	10p
OA81 11p	10p
OA200 8p	10p

PLUGS

DIN 2 Pin	12p
3 Pin	13p
5 Pin 180°	15p
Std. Jack	14p
2.5mm Jack	11p
Phono	5p

SOCKETS

DIN 2 Pin	10p
3 Pin	10p
5 Pin 180°	12p
Std. Jack	14p
2.5mm Jack	11p
Phono	5p

ELECTROLYTIC CAPACITORS. Tubular & Large Cans
 (µF/V): 1/25, 2/25, 4/25, 4.7/10, 5/25, 8/25, 10/10, 10/50, 16/25, 22/63, 25/25, 25/50, 32/25, 50/25, 100/10, 100/25, 6p, 50/50, 8p, 100/50, 200/25, 11p, 250/50, 18p, 500/10, 11p, 500/25, 15p, 500/50, 18p, 1000/10, 15p, 1000/25, 22p, 1000/50, 40p, 2000/10, 20p, 1000/100, 90p, 2000/25, 30p, 2000/100, 95p, 2500/25, 38p, 2500/50, 62p, 3000/50, 80p, 5000/25, 66p, 5000/50, £1.10, 16/450, 23p, 32/350, 33p, 50/250, 20p, 100/500, 88p.

METALLISED PAPER CAPACITORS
 250V: 0.05µF, 0.1µF, 6p, 0.25, 6p, 0.5µF, 7p, 1µF, 9p.
 500V: 0.025, 0.05, 6p, 0.1, 6p, 0.25, 7p, 0.5, 9p.
 1000V: 0.01, 11p, 0.022, 13p, 0.047, 0.1, 15p, 0.22, 23p, 0.47, 28p.

INTEGRATED CIRCUITS

µA709C	50p
µA741C	55p
µA723C	£1
µL914	35p

PE RONDO QUADRAPHONIC SYSTEM

AND OTHER DELECTABLE ITEMS
 WE SPECIALISE IN QUADRAPHONIC SOUND

RAPID ORDER FORM

Please tear off at dotted line

H-F-M 2000 TUNER AMPLIFIER
 CBS-SQ MATRIX DECODER KIT:
 CBS-SQ MATRIX DECODER BUILT AND TESTED:
 FULL STEREO PRE-AMP WITH SELECTOR:
 MASTER VOLUME/TONE/4 CH. BAL. BOARD:
 POWER AMP BOARD (FULL STEREO) TWO FOR RONDO:
 POWER SUPPLY BOARD:
 MAIN SMOOTHING CAPACITORS (per pair):
 MAINS TRANSFORMER:
 PUNCHED CHASSIS + SCREENS:
 CONTROL SECTION FASCIA AND TRIM:
 PHASE LOCKED LOOP STEREO DECODER KIT:
 STEREO DECODER BUILT AND TESTED:
 GOLDRING G101 TUNABLE, Less Cartridge:
 DEUTSCHE ELAC MAGNETIC CARTRIDGE LIST £13.90:
 RONDO LOUDSPEAKERS—FULLY BUILT (per pair):
 RONDO LOUDSPEAKERS—complete kits in pairs, with already assembled cabinets:
 BASS DRIVE UNITS (2 per cabinet): PRICE EACH
 TWEETERS: PRICE EACH
 CROSSOVER KIT:
 QUADRAPHONIC SELECTOR SWITCH:
 DECODER EDGE CONNECTORS (3 required):
 HARNESS AND WIRING PACK:
 KNOB PACK (8 KNOBS)

£59.50 post free
 £8 post free
 £11 post free
 £3.30 post free
 £9.35 post free
 £8.25 post free
 £5.50 post free
 £1.65 post free
 £6.87 post free
 £3.57 post free
 £3.85 post free
 £5.95 post free
 £6.95 post free
 £2.90 post £1
 £7.90 post free
 £4.2 post free
 £35.50 post free
 £4.25 post free
 £1.32 post free
 £2.75 post free
 £1.43 post free
 £1.10 post free
 £3.85 post free
 £1.21 post free

2000
 SQ-K
 SQ-B
 PRE
 MV
 PA
 PSU
 CAPS
 TRANS
 CHAS
 CSF
 SESDK
 SESDB
 G101
 STS144

NEW
 CAT.
 OUT
 SOON.
 ARE
 YOU
 ON
 OUR
 LIST?
 SAE
 WOULD
 BE
 APPRECIATED.

OTHER RONDO ITEMS INCLUDING FULLY BUILT AND TESTED MODULES ARE AVAILABLE—SEND SELF-ADDRESSED ENVELOPE FOR LISTS.
 QUADRAPHONIC 220 FULL 20W PER CHANNEL STEREO AMP. HIGH QUALITY, HIGH PERFORMANCE. LOW PRICE.
SUPERB BRITISH MADE ADVANCE CALCULATORS
 WE ARE NOW APPOINTED DISTRIBUTORS FOR THESE TOP-LINE MACHINES:
 ADVANCE MINI-EXECUTIVE FULL 4 FUNCTION:
 ADVANCE 80—WITH AUTO %:
 ADVANCE 88—2 MEMORY SQUARE ROOT:
 ADVANCE 16R DESK 2 MEMORY SQUARE ROOT %:
 TRADE ENQUIRIES WELCOMED ON ALL ITEMS.
 NEW ORDER SYSTEM—WE DO ACKNOWLEDGE BY RETURN!
 GARRARD TURNABLES AND PLINTHS NOW AVAILABLE.
 (All UK orders—Add 10% VAT. Overseas orders add post, send to Studio Electronics International)

£40.90 post free
 £39.95 post free
 £42.95 post free
 £99.00 post free
 £175 post free

LISTS—SAE PLEASE



Studio Electronics
 P.O. BOX 18 HARLOW
 CM 18 6SH ESSEX.
 Telephone: Harlow (std 0279) 25457

NAME _____
 ADDRESS _____

NOVEL TIMEBASE MARKER CIRCUIT

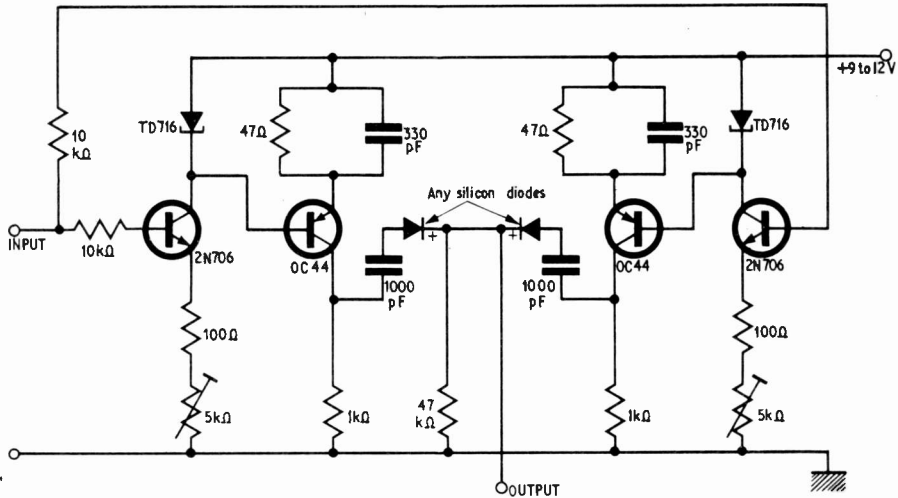


Fig. 1. Novel timebase marker circuit

A NOVEL timebase marker circuit is shown in Fig. 1. It consists of two Schmitt triggers which are set by VR1 and VR2 to fire at different input voltages. The two output pulses are fed through C2 and C3 into D1 and D2 which combines the pulses to give single output.

If the positive timebase ramp output from an oscilloscope is fed into the Schmitt triggers (marked "input" on the diagram), and the output is fed to the Y input two pips will appear on the screen.

The pip positions on the screen can be adjusted by adjustment of the input voltage controlling potentiometers VR1 and VR2 as indicated in Fig. 2. Their relative positions are not affected, however, by the timebase speed.

Therefore if your oscilloscope does not have a graticule you can still do frequency comparisons using and positioning the pips as markers.

S. H. Alsop,
Sheffield.

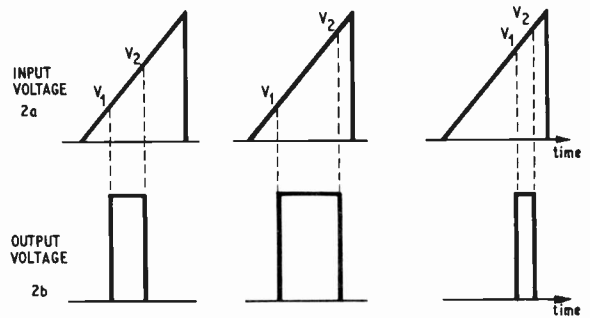


Fig. 2. (a) Input from timebase ramp showing trigger voltages of the Schmitt triggers at V_1 and V_2 . (b) Output pulse to the Y input of the oscilloscope

TUNNEL DIODE IN A SCHMITT TRIGGER

THE circuit diagram shown in Fig. 1 uses a tunnel diode as part of a Schmitt trigger.

When the input voltage is at zero volts TR1 is OFF and therefore no collector current flows. As the input voltage is increased the base current of TR1 increases. When TR1 collector current reaches 4.7mA, the voltage across the tunnel diode suddenly increases. This is amplified by TR2, a germanium transistor, which switches ON when the base-emitter potential reaches 0.2V, giving a positive pulse through C1.

The input voltage can be set by the variable resistor to give the positive pulse; with lower resistance value causing a pulse at a lower input voltage and a higher resistance raising the input voltage required for a pulse.

Typical values are zero ohms for pulsing at 1.5V input and 5kΩ for pulsing at 26V input.

S. H. Alsop,
Sheffield.

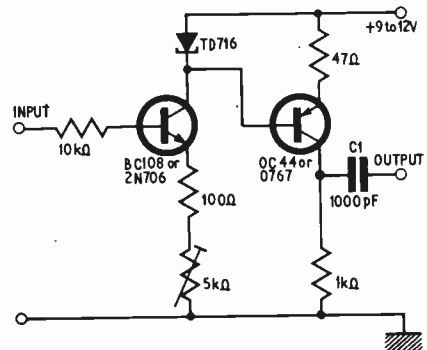


Fig. 1. Tunnel diode in a Schmitt trigger

SHUTTLE SERVICE REGULATOR

In this circuit the 555 timer is used to regulate an automatic shuttle service in which one vehicle passes back and forth along a single track line, with predetermined waiting periods at each terminus. The 555 is used in the astable mode with a relay as the load. The relay contacts control the rail current supply.

On the track itself, terminal rails X and Y are isolated at J and K respectively from main rails A and B by insulated rail-joiners, which are however by-passed for one direction of current only by diodes D2 and D3.

The cycle of operations is as follows. Suppose a vehicle to be travelling on main rails A and B towards Y; when its wheels have completely passed K it will halt because of the blocking action of D3. The model will stay at Y until the 555 timer next causes the relay to change state; direction of track current will thereby be reversed, D3 will conduct and the model will return along the track towards X, until it is stopped beyond J by D2, to await the next change of the 555 and its next trip towards Y.

Using the component values shown in the diagram, RLA is in its off state for 85 seconds, then on for

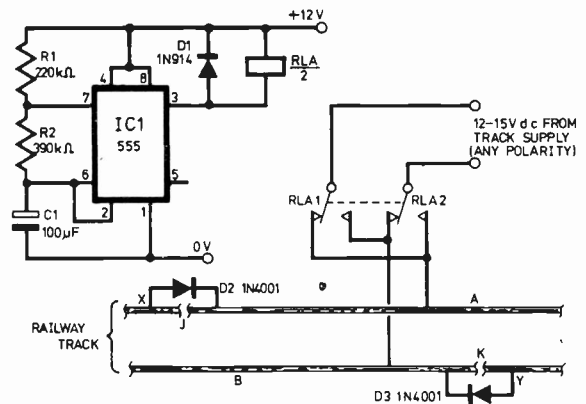


Fig. 1. Model railway track control circuit

55 seconds. These values can of course be varied, or made variable, within reasonable ranges.

Supply to the 555 should be completely independent of track supply. The orientation of diodes D2 and D3 should be verified experimentally for individual layouts.

J. Duffell,
Southam, Glos.

A SIMPLE OSCILLATOR

The circuit introduced here is one of several types of oscillator developed by the writer for specialised purposes. Where a number of audio frequencies is required from a single oscillator, and/or where a special waveform is not required, the circuit shown in Fig. 1 is offered as a more economic proposition than the standard astable multivibrator since it uses only one capacitor. The circuit produces a pulse followed by a relatively long, quiescent interval.


This oscillator is perhaps best understood by first considering S1 in the OFF position. In the resulting static conditions, TR1 conducts and its V_{ce} is such that TR2 is also turned on.

The emitter resistor R3 makes the TR2 collector voltage more positive than V_{be} of TR1 and it also serves to limit TR2 base drive. The base current of TR1 is derived via R2 from TR1 collector so that negative feedback to TR1 base stabilises the d.c. operating point and compensates for varying factors of TR1 h_{fe} .

If C1 is now switched in circuit it will begin to charge up to the voltage between TR2 collector and the base of TR1. But the initially high charging current will flow through the b/e junction of TR1 and the resulting increase of base current causes the V_{ce} of TR1 to fall to a level where TR2 turns off.

C1 therefore charges up to a voltage something less than the value fixed by the potential divider R4, R5, but when charging current ceases to flow (or nearly so) the base current of TR1 reverts back almost to its static value and TR2 again turns on.

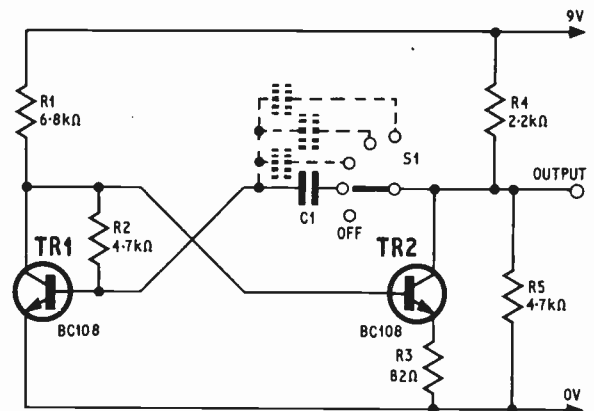Thus, the positively charged side of C1 is effectively connected to the 0V rail via TR2, R3 and the negatively charged side rapidly turns off TR1. The capacitor then discharges at a rate largely determined by the time constant C1 (R1 + R2), but after it has discharged, TR1 will again turn on and C1 will re-start the cycle by re-charging.



The static value of TR2 V_{ce} is not at all critical and the purpose of the potential divider is simply to limit the C1 charge voltage to the TR1 b/e max safe reverse value. This technique avoids certain disadvantages which would result from including a protective diode at TR1 base.

The unloaded output is sensibly constant at all frequencies and, where necessary, this characteristic can be preserved by resistive d.c. coupling to an emitter follower. An expression for determining frequency is somewhat problematical since the discharge time constant is modified by the changing drive on TR2 base during the relaxation period—thus, the h_{fe} of TR2 becomes involved. However, very roughly:

$$f \approx \frac{1}{C_1 (R_1 + R_2) + C_1 R_4}$$

But using low-leakage types of transistors, the value of R1 will not be too critical and by making part of it variable, a useful degree of tuning can be introduced.

N. Naughton,
Manchester.

ELECTROVALUE

Present

THIS MONTH'S SELECTION OF GUARANTEED-TO-SPECIFICATION COMPONENTS

EVERYTHING BRAND NEW ★ ATTRACTIVE DISCOUNTS ★ FREE POSTAGE (U.K.)

TRANSISTORS

and semi-conductors of many types from simple diodes to ICs photo-sensitive devices, threshold switches, etc., etc.

MINITRON DIGITAL INDICATORS

30154F Seven segment filament, compatible with standard logic modules. 0-9 and decimal point; 9mm characters in 16 lead DIL, £1.20. Now available in 8mA or 15mA per segment rating. Suitable BCD decoder driver 7447, £1.15. 3015G showing + or - and 1 and dec. pt, £1.20.

CAPACITORS

DALY ELECTROLYTIC

in cans, plastic sleeved
1,000mF/25V, 3p; 5,000mF/25V, 62p; 1,000mF/50V, 41p; 2,000mF/50V, 57p; 5,000mF/50V, £1.18; 5,000mF/100V, £2.91.

POLYESTER TYPE C280

Radial leads for P.C.B. mounting. Working voltage 240V d.c.
0.01, 0.015, 0.022, 0.033, 0.047, 3p each; 0.068, 0.1, 0.15, 4p each; 0.22, 5p; 0.33, 7p; 0.47, 8p; 0.68, 11p; 1.0, 14p; 1.5, 21p; 2.2, 24p.

SILVERED MICA

Working voltage 500V d.c.
Values in pF—2.2 to 820 in 32 stages, 6p each; 1,000, 1,500, 7p each; 1,800, 8p; 2,200, 10p; 2,700, 3,600, 12p each; 4,700, 5,000, 15p each; 6,800, 20p; 8,200, 10,000, 25p each.

TANTALUM BEAD

0.1, 0.22, 0.47, 1.0mF/35V, 13p each, 2.2/16V, 2.2/35V, 4.7/16V, 10/6.3V, 13p each, 4.7/35V, 10/16V, 22/6.3V, 16p each, 10/25V, 22/16V, 47/6.3V, 100/3V, 18p each.

POLYCARBONATE TYPE B32540

Working voltage 250V.
Values in mF: 0.0047, 0.0068, 0.0082, 0.01, 0.012, 0.015, 3p each, 0.018, 0.022, 0.027, 0.033, 0.039, 0.047, 0.056, 0.068, 0.082, 0.1, 4p each.

CERAMIC PLATE CAPACITORS

Working voltage 50V d.c.
In 26 values from 22pF to 6,800pF, 2p each.

POTENTIOMETERS

ROTARY, CARBON TRACK.

Double wipers for good contact and long working life.
P20 SINGLE linear 100 ohms to 4.7M Ω , 14p each.
P30 SINGLE log, 4.7k Ω to 2.2M Ω , 14p each.
JP20 DUAL GANG linear 4.7k Ω to 2.2M Ω , 48p each.
JP20 DUAL GANG log, 4.7k Ω to 2.2M Ω , 48p each.
JP20 DUAL GANG log/antilog 10K, 22K, 47K, 1M Ω only, 48p each.
JP20 DUAL GANG antilog 10k only 48p.
2A DP mains switch with any of above 14p extra.
Decades of 10, 22 and 47 only available in ranges above. SKELETON CARBON PRESETS 6p each.

SLIDER

Linear or log, 4.7k Ω to 1M Ω in all popular values, 3p each.
Escutcheon plates, black, white or light grey, 10p each.
Control knobs blk/wht/red/yel/grn/blue/dk. grey/lt grey, 7p each.

JACKS AND PLUGS

Sockets
2-circuit, unswitched, S1/SS 11p
2-circuit/2 break contacts, S1/BB 13p
3-circuit, unswitched (not GPO), S3-S5S 15p
3-circuit with 3 break contacts, S3/BBB 20p
2 circuit with chrome nut and black/white/red/green or grey unswitched, S5/SS 14p
2 circuit with chrome nut and black/white/red/green with 2 break contacts, S5/BB 17p
Miniature, 3.5mm, 2-circuit (black), 2 br. cont., S6/BB 8p

EV CATALOGUE 7 2nd Printing

112 pages, thousands of items, illustrations, diagrams, much useful technical information. The 2nd printing of this catalogue has been updated as much as possible on prices. It costs only 25p post free and includes a refund voucher for 25p for spending when ordering goods list value £5 or more.

Plugs

2-circ. screened, top entry, P.1 24p
2-circ. screened, side entry, SEP1 36p
Line socket, mono, 231 40p
Line socket, stereo, 244 40p
3-circuit, unswitched, bl/grey/wh, P.4 36p
2-circuit, unswitched, blk/wh/red/bl/grn/grey, P2 18p
3-circuit, screened, top entry, P3 53p
3-circuit, screened, side entry, SEP3 55p
Miniature, 3.5mm, 2-circ., screened, P5 13p
Miniature, 3.5mm, 2-circ., unswitched, various colours, P6 10p

INSULATED SCREW TERMINALS

In moulded polypropylene, with nickel plate on brass. With insulating set, washers, tag and nuts. 15A/250V. In blk/brown/red/yel/grn/bl/grey/wh. Type TP.1, 14p each.

RESISTORS

Code	Watts	Ohms	1 to 9	10 to 99	100 up
			(see note below)		
C	1/3	4.7-470K	1-3	1-1	0.9 nett
C	1/2	4.7-10M	1-3	1-1	0.9 nett
C	3/4	4.7-10M	1-5	1-2	0.9 nett
C	1	4.7-10M	3-2	2-5	1.9 nett
MO	1/2	10-1M	4	3-3	2.3 nett
WW	1	0.22-3.9	9	9	8
WW	3	1-10K	9	9	8
WW	7	1-10K	9	9	8

Codes:
C = carbon film, high stability, low noise.
MO = metal oxide, Electroasil TR5, ultra low noise.
WW = wire wound, Plessey.
Values: All E12 except C $\frac{1}{2}$ W, C $\frac{1}{2}$ W, and MO $\frac{1}{2}$ W. E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Tolerances:
5% except WW1 10%
 $\pm 0.05\%$ below 10 Ω and MO $\frac{1}{2}$ W 2%
Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.) Prices for 100 up in units of 100 only.

BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in "Wireless World." Simple to assemble, fantastically good results and a greater money saver. Carries 10 watts RMS, 15 ohms impedance. Size 18in x 12in x 10in. Complete kit, including pack-flat cabinet, £14.90.
The size and weight of this product obliges us to charge 70p part cost of carr. in U.K.
Equaliser Assembly: £2.30.
Loudspeaker Unit 59RM109, £2.45.
Cabinet Kit (to Baxandall design), £10.45.
Cross-over choke included in full kit above, £1.30.

ELECTROLYTICS

Axial Lead uP	3V	6.3V	10V	16V	25V	40V	63V	100V
0.47	—	—	—	—	—	11p	—	8p
1.0	—	—	—	—	—	11p	—	8p
2.2	—	—	—	—	11p	—	—	8p
4.7	—	—	—	—	—	8p	—	9p
10	—	—	—	—	—	8p	—	9p
22	—	—	—	—	—	8p	—	9p
47	8p	—	8p	8p	8p	8p	10p	13p
100	9p	8p	8p	8p	8p	8p	10p	12p
220	8p	8p	9p	10p	10p	11p	17p	28p
470	9p	10p	10p	11p	13p	17p	24p	45p
1,000	11p	13p	13p	17p	20p	25p	41p	—
2,200	15p	18p	23p	26p	37p	41p	—	—
4,700	26p	30p	39p	44p	58p	—	—	—
10,000	42p	46p	—	—	—	—	—	—

ZENER DIODES full range E24 values: 400mW: 2.7V to 36V, 14p each; 1W: 6.8V to 82V, 21p each; 1.5W: 4.7V to 75V, 48p each. Clip to increase 1.5W rating to 3 watts (type 266F) 5p.

VEROBORD

Copper clad 0.1 in. matrix—2.5 x 3.75 ins., 27p. 3.75 x 3.75 ins., 30p. 2.5 x 5 ins., 30p. 3.75 x 5 ins., 33p.
Copper clad 0.15 in. matrix—2.5 x 3.75 ins., 20p. 3.75 x 3.75 ins., 30p. 2.5 x 5 ins., 30p. 3.75 x 5 ins., 36p.
Vero spot face cutter (any matrix), 43p. 0.040 pins (for 0.1 matrix) per 100, 35p. 0.052 pins (for 0.15 matrix) per 100, 35p.

KNOBS

In a great variety of modern types, for $\frac{1}{2}$ in. shaft, from plastic to solid aluminium, from typically 63p per pack of two (Catalogue 7, page 62).

CONNECTORS

DIN from 2-way to 7-way plugs and sockets; phono types, mains connectors, etc. (Catalogue 7, page 88).

This is EV Service

DISCOUNTS

Available on all items except those shown with NETT PRICES. 10% on orders from £5 to £14.99. 15% on orders £15 and over.

PACKING AND POSTAGE FREE

in U.K. for pre-paid mail orders. For orders £2 and under, there is an additional handling charge of 10p.

GUARANTEE OF QUALITY

All goods are sold on the understanding that they conform to manufacturers' specifications and satisfaction is guaranteed as such—no rejects, "seconds" or sub-standard merchandise is offered for sale.

PRICES QUOTED DO NOT INCLUDE VAT, for which 10% must be added to total nett value of order. Every effort is made to ensure correctness of information and prices at time of going to press. Prices are subject to alteration without notice. S.A.E. with written enquiries please.

GIRO ACCOUNT No. 38/671/4002

ELECTROVALUE LTD

28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Telephone: Egham 3603 Telex 264475 Shop hours—9-5.30 daily. Saturdays 9-1 p.m.

Northern Branch: 680 BURNAGE LANE, BURNAGE, MANCHESTER M19 1NA
Telephone 061-432 4945

Shop hours—Daily 9-1 and 2-5.30 p.m. Saturdays 9-1 p.m.
U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081

YATES ELECTRONICS

(FLITWICK) LTD.

DEPT. PE, ELSTOW STORAGE DEPOT
KEMPSTON HARDWICK, BEDFORD

C.W.O. PLEASE. POST AND PACKING
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the
components listed will be sent free on request.
10p stamp appreciated.

CALLERS WELCOME Mon.-Sat. 9 a.m.-5 p.m.

PLEASE ADD 10% VAT

RESISTORS

1/2W Iskra high stability carbon film—very low noise—capless construction
1/2W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm. 1/2W 2%
ELECTROSIL TRS

Power watts	Tolerance	Range	Values available	Price 1-99	100+
1/2	5%	4.7 Ω-2.2M Ω	E24	1-3p	1-1p
1/2	10%	3.3M Ω-10M Ω	E12	1-3p	1-1p
1	2%	10 Ω-1M Ω	E24	3-5p	3-1p
1	10%	1 Ω-3.9 Ω	E12	1-1p	1-1p
2	5%	4.7 Ω-1M Ω	E12	1-3p	1-1p
4	10%	1 Ω-10 Ω	E12	1-3p	1-1p

Quantity price applies for any selection. Ign. e fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7 Ω to 1M Ω.
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5k Ω to 2M Ω. log or linear (log 1/2W, lin 1/2W).
Single, 14p. Dual gang (stereo), 49p. Single D.P. switch 28p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500 Ω and decades to 5M Ω. Horizontal or vertical P.C. mounting
(0.1 matrix).
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 7p each.

SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector. Detector GDI, £2. Kit of parts for mains operated detector including GDI but excluding case, £5.60. Suitable case, £1.50. Kit of parts for 12 or 24V battery operation, including GDI and P.C. board, £7.70. As above for PP9 battery, £6.90. Note: The battery operated kits incorporate our patented circuit to minimise battery drain—typically 90mA for 24V.

PRINTED BOARD MARKER

97p
Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to dry, the immerse the board in the etchant. On removal the circuit remains in high relief.

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 3p. 0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 3p. 0.047μF, 0.068μF, 0.1μF, 5p. 0.15μF, 6p. 0.22μF, 7p. 0.33μF, 11p. 0.47μF, 13p.
160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p. 0.1μF, 3p. 0.15μF, 4p. 0.22μF, 5p. 0.33μF, 6p. 0.47μF, 7p. 0.68μF, 11p. 1.0μF, 13p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p. 0.033μF, 0.047μF, 0.068μF, 3p. 0.1μF, 4p. 0.15μF, 0.22μF, 5p. 0.33μF, 6p. 0.47μF, 8p. 0.68μF, 11p. 1.0μF, 13p. 1.5μF, 20p. 2.2μF, 24p.

MYLAR FILM CAPACITORS 100V

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF, 0.03μF, 0.04μF, 0.05μF, 0.068μF, 0.1μF, 4p.

CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

ELECTROLYTIC CAPACITORS—MULLARD O15/6/7

(μF/V) 1/63, 1.5/63, 2.2/63, 3.3/63, 4.7/63, 6.8/40, 6.8/63, 10/25, 10/63, 15/16, 15/40, 15/63, 22/10, 22/25, 22/63, 33/63, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6.3, 68/16, 100/4, 100/10, 100/25, 150/6.3, 150/16, 220/4, 220/6.3, 220/16, 330/4, 6p. 47/63, 100/40, 150/25, 220/25, 330/10, 470/6.3, 7p. 68/63, 150/40, 220/40, 330/16, 1,000/4, 10p. 470/10, 680/6.3, 11p. 100/63, 150/63, 220/63, 1,000/10, 12p. 470/25, 680/16, 1,500/6.3, 13p. 470/40, 680/25, 1,000/16, 1,500/10, 2,200/6.3, 18p. 330/63, 680/40, 1,000/25, 1,500/16, 2,200/10, 3,300/6.3, 4,700/4, 21p.

SOLID TANTALUM BEAD CAPACITORS

Value	Voltage	Value	Voltage	Value	Voltage	12p
0.1μF	35V	2.2μF	35V	22μF	16V	
0.22μF	35V	4.7μF	35V	33μF	10V	
0.47μF	35V	6.8μF	25V	47μF	6.3V	
1.0μF	35V	10μF	25V	100μF	3V	

VEROBOARD

0.1	0.15	24p	20p
2 1/2 x 3 1/2	24p	28p	28p
3 1/2 x 5	28p	32p	28p
3 1/2 x 3 1/2	28p	32p	28p
17 x 2 1/2	85p	67p	67p
17 x 3 1/2	120p	108p	108p
17 x 3 1/2 (plain)	76p	62p	62p
17 x 2 1/2 (plain)	—	41p	—
2 1/2 x 5 (plain)	—	12p	—
2 1/2 x 3 1/2 (plain)	—	11p	—
Pin insertion tool	62p	62p	—
Spot face cutter	52p	52p	—
Pkt. 50 pins	20p	20p	—

JACK PLUGS AND SOCKETS

Standard screened	28p	2.5mm insulated	12p
Standard insulated	18p	3.5mm insulated	12p
Stereo screened	40p	3.5mm screened	18p
Standard socket	20p	2.5mm socket	10p
Stereo socket	30p	3.5mm socket	11p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin, 7 pin
Plug 12p, Socket 8p.
4 way screened cable, 25p/metre
6 way screened cable 30p/metre.

BATTERY ELIMINATOR

£1.70
9V mains power supply. Same size as PP9 battery.



become a RADIO-AMATEUR!

learn how to become a radio-amateur
in contact with the whole world. We give
skilled preparation for the G.P.O. licence

free!

Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
P.O. BOX 156, JERSEY

NAME: _____

ADDRESS: _____

EB64

BLOCK CAPS please

TRANSISTORS

POPULAR TYPES AVAILABLE EX-STOCK

AC126	12p	BC107	9p	2N2221	15p
AC127	12p	BC108	9p	2N2222	16p
AC128	12p	BC109C	10p	2N2926	8p
AC176	14p	BC147B	9p		
AC187	14p	BC148B	9p		
AC188	14p	BC149C	10p		
AC187K	18p	2N696	10p	Popular I.C.	
AC188K	18p	2N697	10p	709C	35p
AF114	14p	2N930	14p	723C	90p
AF115	14p	2N1131	16p	741C	38p
AF116	14p	2N1132	16p		
AF117	16p	2N2219	16p	TTL74 Series	
				also available	

Minimum Order £3

Please add 10% VAT on all orders

Export enquiries welcome

Special discounts available to bulk buyers

Other types available on request

Technomatic Ltd

54 Sandhurst Road, London, N.W.9

Telephone 01-204 4333

CULLED FROM KOHOUTEK

Though the observations of the comet Kohoutek were disappointing in the United Kingdom, other places had better luck. From New Mexico it was visible to the naked eye as late as January 20. On January 10 observers were recording a tail 17° long.

The *Skylab* scientists were the first to see Kohoutek emerge from perihelion.

From Tokyo came the observations of Z. Sekanina who said that there was a high state of dust activity (before perihelion) and asserted that this was the cause of the spike. He estimated that the dust activity must have begun about October. He also said that the particles gathered round the head of the comet were as large as one millimetre.

Other observers reported that there was a gas and dust trail in the direction away from the Sun and that on January 16 a wavy motion of the gas was seen extending from 10° to 15° from the head. The tail and coma showed a silicate structure and the spike had a black body spectrum. All this is consistent with a gritty or perhaps sandy structure. Measurements were made by infra-red techniques as a dusty content radiates thermally.

Spectroscopy has revealed some 200 emission lines not previously known. Optically C, C₂, CN, NH₃, CO, and Na emission have been recorded. Some of the lines not identified are probably from singly ionised water molecules. Radio astronomers have recorded Methyl Cyanide, Hydrogen Cyanide, CH and OH. Rockets carrying ultra violet equipment detected radiation from the gaseous trail extending millions of kilometres round the comet. This is similar to that which appeared with comet Bennett and could be common to certain comets.

One thing is certain, from the remarkable amount of data already processed, that the direct observation of bright comets is very desirable. This makes a rendezvous with Halley's comet a worthwhile project.

TITAN-CENTAUR

It is not often the case that failure has to be reported in *Spacewatch*, but it does happen from time to time. In dealing with the failure of the *Titan 3E/Centaur* system it has to be admitted that this has been a major disaster for NASA.

A great deal of the future projects were to be related to this system as a launch vehicle. The far reaching effects involve the Mars unmanned landings for there was much faith put in the *Titan/Centaur* vehicle for this project. One of the objects of the launch that failed was to test out a number of modifications, simulate some of the sections of the



BY FRANK W. HYDE

new missions that were to be undertaken, and the site launching facilities which had also been modified.

It was intended that the vehicle should be a sort of intermediate carrier of heavier unmanned loads into orbit and also into interplanetary trajectories until the space shuttle was ready. The fact that the guidance system failed because of vibration effects is particularly disquieting because long journeys such as the Mars landing require that extreme stability is mandatory.

The failure was in the *Centaur* section only; all systems in the *Titan* stages being quite satisfactory. It is unfortunate that the number of missions is limited and there is not much time or vehicles available if a high rate of abortive action takes place.

The modifications that were made involved two important areas of *Centaur*, the control systems, and the heat shield. The computerised control systems handling the guidance, navigation, control of fuel and telemetry, was extended to include the initiation of vehicle activity. This would have included the rocket "burns".

The time of the failure was at the moment when the rocket burn should have taken place. This did not signal an affirmative to the control centre and it had to be assumed that no "burn" had taken place, so that, following procedure, the safety officer ordered "destruct".

The heat shield modification was an important one, for the new three layer sandwich, of aluminised Mylar and Dacron, would have improved fuel losses during long term missions. Conservation of fuel combined with the ability of the vehicle to "coast" would be of great value on long missions where zero gravity was involved. Also, coasting is important in synchronous orbits.

In the case of the aborted mission the flight plan it was set to follow was a seven hour programme. This was to include an initial launch trajectory which would be the same as for the *Viking* mission, from this it was to have entered a parking orbit and coast for twelve minutes. A next burn would have transferred the vehicle to an orbit similar to the end of the *Viking* plan. The actual burn would be shorter than the *Viking* mission.

During the intermediate orbit a coasting of 80 minutes would have taken place allowing a check of fuel handling systems in conditions of zero gravity. The next transition was to be to a third burn into a transfer orbit. Ten minutes later the *Sphinx* satellite would have been ejected. The vehicle was to do a five hour coasting in the transfer orbit. The whole sequence was to test the three burn facility.

The purpose of the *Sphinx* (space plasma high voltage interaction experiment) satellite was to check the high voltage equipment. So far, space missions have used mainly low voltage solar cells for power; in the long duration missions a greater amount of power is required so that other methods are important.

The higher output solar cells would enable the heavy inboard power sources to be removed and replaced with more payload. There is a difficulty, however, and that is that as yet no one knows for sure how the high voltage cells will react. There is a possibility that there would be reaction due to particles which are charged and possible short circuits or arcing leading to loss of power. The *Sphinx* project would have been able to make a long period study.

There are some who think that a much higher orbit may be necessary for satellites equipped with high voltage cells. The effect of plasma, however, is important as also the manner in which insulation and cell layouts, which could be rolled up like blinds, would survive. With array voltages at 16kV prolonged operation may be necessary before decisions can be finally made.

WHICH CANDIDATE

The black hole problem still occupies attention and the latest candidate is now the X-1 object in Cygnus and not X-3. The reason for this is that X-1 has shown very rapid fluctuations in X-ray emissions, with periods as fast as one twentieth of a second. This is at the threshold of the instrument aboard the satellite *Uhuru* undertaking these present observations.

Larger instruments are required to extend observation and these need to have detection limits capable of measuring fluctuations of a few millionths of a second.

FIRST STEPS IN CIRCUIT DESIGN

3

By A. P. Stephenson

This series, specially written for the beginner, takes you step-by-step through transistor circuit design in a simple, non-mathematical way.

Design of a small signal amplifier will be followed by a Class B amplifier and the series will conclude with a constructional project so that your theoretical knowledge can be put into practice.

LAST MONTH we saw how the characteristics of the transistor must control our circuit design. Now that the parameters of the transistor are more fully understood we can get down to the real business of choosing the components so that the transistor behaves just the way we want it to.

An example of bad design will be given so that the impatient beginner does not fall into the more obvious traps.

As well as choosing components, there is also the supply rail voltage to be defined. This is often of major importance to successful circuits.

3.1. RELEVANT EQUATIONS TO VOLTAGE AMPLIFYING STAGE

There are four equations which must be considered as absolutely essential to the design of a simple amplifying stage. These are shown in Fig. 3.1 in a way that should immediately suggest their use.

These equations should be copied onto paper and

chanted over and over in the mind before going to sleep.

Note how the variables interact with one another. The choice of collector current will affect r_e which in turn will affect the voltage gain A and the input resistance of the stage R_{IN} .

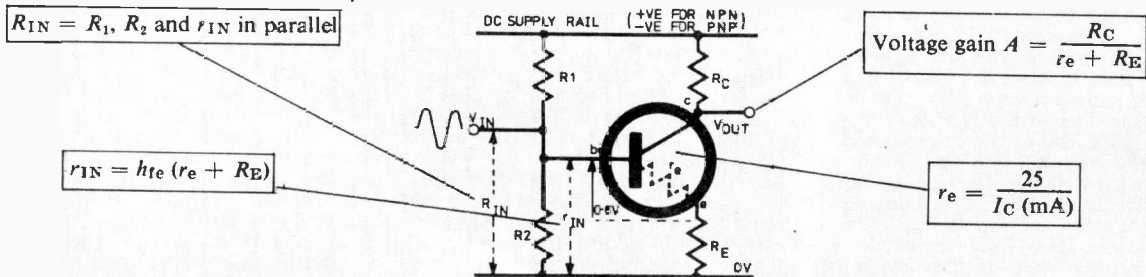


Fig. 3.1. This circuit shows how the four equations essential to amplifier design are related

3.2. CHOICE OF COLLECTOR CURRENT AND RAIL VOLTAGE

With any particular transistor there are obvious limits at both ends of the collector current scale.

The limit at the lower end is due to the reduced h_{FE} and also to the encroachment of the base current onto the leakage area. For small silicon transistors similar to the BC108, the lower limit may be taken as around ten microamps.

UPPER LIMIT

At the other end of the scale, there is the absolute limit imposed by the manufacturers known as $I_{c(max)}$, which, again quoting the BC108, is 200mA. There is a hidden danger in this figure however, unless the maximum power dissipation ($P_{(max)}$) is also examined.

The BC108 claims 300mW for $P_{(max)}$, therefore if the designer does attempt to use 200mA collector current, he had better make sure that he never allows the collector voltage to be more than one volt, or the poor thing will protest warmly.

Except for pulse circuitry, where large currents can be tolerated, the practical maximum for amplifier stages will be lower than $I_{c(max)}$. Ten milliamps is the recommended maximum for the BC108; beyond this, the h_{FE} starts to fall again.

CHOOSING COLLECTOR CURRENT

Having established the range as $10\mu A$ to 10mA, there is still the particular value to be decided upon when designing an amplifying stage.

Other things being equal, a choice of low I_c will:

- Enable the stage input resistance to be higher because R_{IN} is the parallel combination of the base bias resistors R1, R2 and the transistor input resistance r_{IN} . R1, R2 will be higher because the base current will be small. Also r_{IN} will be higher because $r_{IN} = h_{FE}(r_e + R_E)$ and both r_e and R_E can be high if I_c is low.
- The output resistance R_{out} of the stage will be high because R_c will tend to be high. This is not good.

SUPPLY RAIL VOLTAGE

The higher the supply voltage the easier the circuit is to design. There is a greater freedom of choice—more breathing space, since voltage can always be dropped but not so easily increased. The limit is, of course, $V_{CE(max)}$ which, in the case of the BC108, is around 20 volts.

3.3. DESIGN PITFALLS

The beginner to the art of design is soon faced with a frustrating problem: how to meet the conflicting demands of satisfying both the signal and the d.c. bias requirements.

To illustrate this let us assume a simple voltage amplifier is to be designed having a gain of 100. This is a harmless specification, with no mention of input resistances, supply rail voltages, etc., and the beginner might be excused for underestimating the job.

His reasoning might proceed as follows:

- Look up the equation for voltage gain
 $A = R_C / (r_e + R_E)$
- Note that R_E appears a nuisance so why not leave it out altogether?

$$A = R_C / r_e$$

(This will save a resistor and make the equation easier)

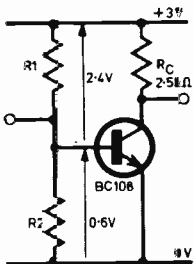


Fig. 3.2. Circuit diagram of the example in the text

- Look up the equation for r_e

$$r_e = 25 / I_c(\text{mA})$$

and note that choosing a nice figure of 1mA will make $r_e = 25$ ohms.

R_C can then be found by $R_C = 1000 \times 25 = 2.5k\Omega$.

- The circuit may now be drawn with as much data as possible included (see Fig. 3.2). The 3V rail is handy because the small family torch has a 3V battery.
- Look up h_{FE} of a BC108 which will be 300 (typically) which means that the base current will be $I_c / 300 = 1\text{mA} / 300 = 0.003\text{mA}$ (approx). Since the divider chain should carry a much larger current than the base, let this be 0.03mA. Allowing the regulation 0.6V across R2, $R2 = 0.6\text{V} / 0.03\text{mA} = 20k\Omega$.
- R1 must drop the remaining 2.4V therefore $R1 = 2.4\text{V} / 0.03\text{mA} = 80k\Omega$.

The paper work is now finished and the designer can now rig up the circuit and try it out.

What a bitter disappointment he is in for!

Voltage checks will soon reveal that:

- The 0.6V may be disturbingly out, and may drift downwards slowly.
- The transistor is almost or even completely saturated. The output terminal has no room to move since it is grovelling at almost ground voltage.

In short, it is a shocking example of bad design.

3.4. THE IMPORTANCE OF R_E

A familiar component in most small signal amplifiers is the resistor R_E connected between emitter and ground. The primary reason for its presence is to provide a simple self-adjusting mechanism for forward bias on the base.

It may be remembered that the transistor will only amplify correctly if the base voltage is held at a mean value of about 0.6V higher than its emitter (at normal temperature).

Not only is it difficult to tap off such a precise, small voltage from a divider chain, there is also the added complication of the change in this voltage when the temperature changes (remember that V_{BE} falls by about 2mV per degree C rise in temperature).

The inclusion of R_E will compensate for these effects (see Fig. 3.3).

Suppose R_1 , R_2 values were a little out, due to tolerance errors resulting in a voltage of say 1.5V instead of 1.6V. This would produce only 0.5V across base and emitter if the collector current remained the same, but of course it will not.

The collector current must fall and the 1V drop across R_E must then fall to say 0.9V.

This means that the voltage difference between base and emitter would be back again to 0.6V.

The system is thus almost completely self-regulating—if the temperature rises, more current would

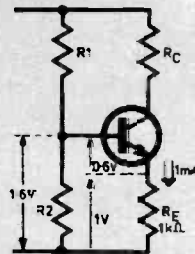


Fig. 3.3. Circuit to show the stabilising effect of R_E upon the V_{BE}

tend to flow which would increase the 1V across R_E to say 1.1V and that would reduce the forward bias in the base to 0.5V which holds the current back again.

With regard to the design equation, how big should R_E be?

Compromise as usual! The higher it is the better the stabilisation action, but the more volts are "wasted" across R_E .

A good rule of thumb is:

Make R_E at least five, but preferably ten times greater than r_e .

3.5. THE EFFECT OF R_E ON VOLTAGE GAIN AND DISTORTION

Apart from stabilising the d.c. bias conditions, R_E causes the voltage gain to fall.

This can be understood by re-examining the equation for voltage gain $A = R_C / (r_e + R_E)$.

A more convincing way of understanding the effect is to consider the effect of a signal applied between base and ground (see Fig. 3.4).

Consider first the action with the switch closed, i.e. R_E not in circuit.

If a positive-going signal of say 2mV is applied, the whole of the signal is across the base to emitter junction.

With the switch open, the 2mV signal between base and ground would cause an increase of collector current (as before) but the volts drop across R_E would cause the emitter to rise as well as the signal. Thus the effective value of the signal between base and emitter would be less than in the case above.

For example, if the base signal rises by 2mV and the emitter voltage also rises to say 1.5mV, then



Fig. 3.4. The divider to feed base bias is irrelevant to this circuit which demonstrates the effect of R_E

the effective signal between base and emitter is only 0.5mV.

From the point of view of voltage gain, it appears that R_E has in this case, reduced the effectiveness of the signal by a factor of four which means the gain is reduced by a factor of four.

This gain reduction, caused by a signal voltage, appearing across R_E is an example of negative current feedback.

ADVANTAGES OF NEGATIVE FEEDBACK

Although the gain is reduced, there are certain advantages in this kind of feedback:

1. The input resistance r_{IN} is increased, since $r_{IN} = h_{ie} (r_e + R_E)$.
2. The distortion, inevitable to some degree in all transistors, is much less. In fact the distortion is reduced by the same factor as the gain.
3. The reduced gain now tends to be less dependent on the actual transistor causing the circuit performance to be determined without worrying about tolerance variations in the h -parameters.

If a high gain is more important than these advantages R_E can be "by-passed" with a capacitor which will provide a signal short to ground.

The capacitor's reactance X_c should be smaller than R_E at the lowest frequency, a rough and ready equation being $C = 1 / (f \times R_E)$ where C is in microfarads, f in kHz and R_E in kilohms.

3.6. SETTING THE D.C. OUTPUT VOLTAGE

The output terminal of the stage should, wherever practical, rest somewhere about the middle of the available voltage swing. This will ensure that signal variations will have freedom to move in both directions without hitting the supply rail at the top, or the saturation area at the bottom.

The above remarks still apply even if the signal variations are known to be small. The percentage distortion introduced by the slight non-linearity in transistor curves is always proportional to the size of the swing.

For example, a signal swing of one volt superimposed on the output will introduce less distortion if the available limit of swing is 10 volts than if it were five.

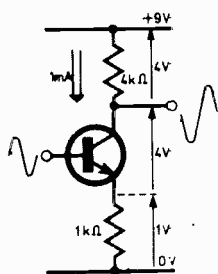


Fig. 3.5. Example A.

Gain = 4 (r_e swamped by R_E)
Maximum allowable input signal = 1V

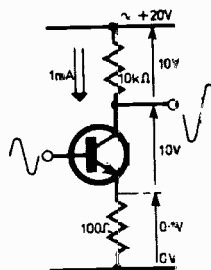


Fig. 3.6. Example B:

Gain = 100 (r_e still almost swamped by R_E)
Maximum allowable input signal = 0.1V

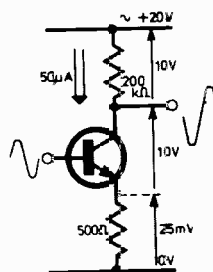


Fig. 3.7. Example C.

This gives high gain but will not obey the full equation $A = R_C (r_e + R_E)$ very accurately because (a) R_E does not swamp r_e ; in fact $R_E = r_e$ and (b) the value of R_C is not negligible in relation to the internal collector resistance. Hence don't expect the gain to be 400.

3.7. SETTING THE BIAS VOLTAGE

The setting of the output voltage should normally be tackled first. If R_{IN} is important, however, some preliminary doodling is required.

Afterwards, the required voltage drops across the divider chain, the desired base current, the divider chain current and finally the values for R_1 and R_2 (in that order) should be determined.

Suppose, for example, that we have decided on the output circuit shown in Fig. 3.8.

BASE CURRENT

Before we can calculate the bias resistors the base current must be estimated. Don't be too fussy about this; instead be pessimistic!

Assume you will be unlucky enough to pick the worse sample of a BC108, i.e. h_{FE} only about 100. This would demand a base current of $1\text{mA} \div 100 = 10\mu\text{A}$.

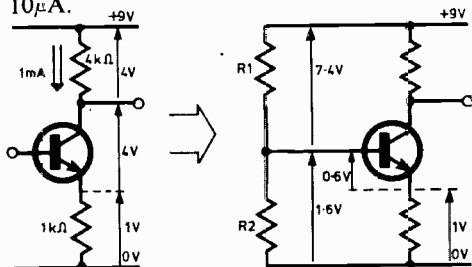


Fig. 3.8. Assuming the voltage drops and current shown in (a) the bias voltage drops must then be as in (b)

In case this reasoning appears very rough and ready, remember that the only thing of importance about the current down the divider chain is that it should be much larger than the base current.

If we use the "ten times rule" and make the current in $R_2 = 100\mu\text{A}$ when the worse transistor is used, then the current stability will always be good enough, and often better, than necessary.

$$R_2 = \frac{0.1\text{V}}{0.1\text{mA}} = 1\text{k}\Omega \quad (\text{note that changing } 100\mu\text{A}$$

to 0.1mA keeps that arithmetic easy).

R_1 should be 11 times the base current:

$$R_1 = \frac{7.4\text{V}}{0.11\text{mA}} = 67\text{k}\Omega$$

The nearest preferred values may be used because the emitter resistor R_E will always ensure that the $0.6\text{V } V_{BE}$ is maintained within reasonable limits.

STAGE INPUT RESISTANCE


It may be interesting at this point to calculate the input resistance of the stage (R_{IN}).

First R_1 and R_2 in parallel have a resistance of $13\text{k}\Omega$. The transistor itself presents an r_{IN} of $h_{fe} (r_e + R_E)$ which equals $100 (25 + 1000) = 100\text{k}\Omega$.

Since we have again assumed the worse case value of 100 for h_{fe} , it is clear that r_{IN} will probably be much higher.

It is safe to assume therefore that r_{IN} in parallel with $13\text{k}\Omega$ will have little effect on the R_{IN} of the stage which is therefore around $13\text{k}\Omega$.

Continued next month

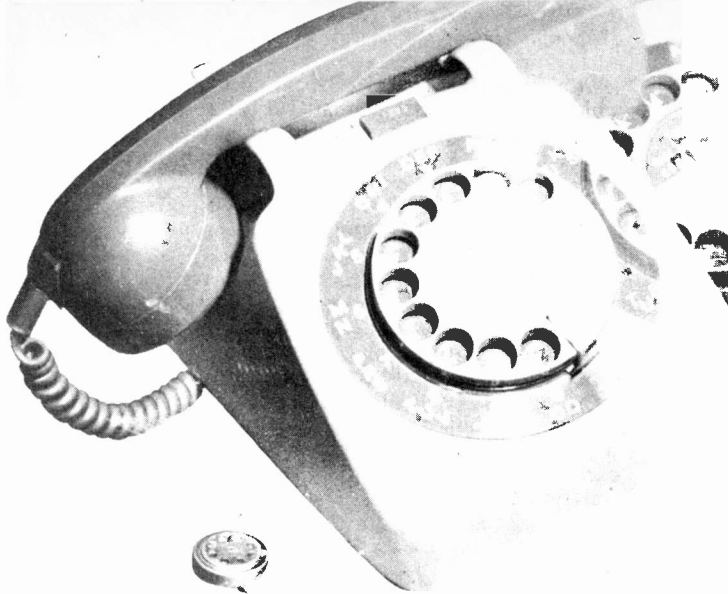

TELEBELL

... REPEATS ANYWHERE

BY J. N. WATT

THE TELEBELL is a compact phone bell repeater unit that provides remote indication that a telephone bell is ringing without having to be connected to the Post Office line. It is driven by self-contained batteries and as it has low stand-by power requirements, these have a very long life.

Useful to anyone who has ever been busy some distance from their telephone and has stopped to wonder whether it was ringing or not, the Telebell will also be extremely helpful to the hard of hearing when in another room away from the telephone.

POST OFFICE

It is of course possible to have an extension bell fitted by the Post Office, but this does have drawbacks as it costs money in the form of extra rental and is usually fitted permanently in one place, so reducing the number of places where it can be heard, compared to the unit described here, which can have its repeater bell placed anywhere at will.

Under existing Post Office regulations, no electrical connection may be made by the hirer to a telephone. How, then, can an extension bell be made to function?

The answer is to use acoustic coupling. A microphone, mounted close to the telephone, picks up the sound of the bell. The resultant electrical signal is amplified and used to trigger a thyristor, which operates the extension bell; this latter can be at almost any distance and can be placed in any particular position found convenient. The unit is battery operated and is thus completely safe, yet the current drawn in the stand-by condition is so low that batteries last for many months.

The author understands that such an arrangement does not contravene any Post Office regulations.

THE CIRCUIT

The complete circuit diagram is shown in Fig. 1. The first transistor, by means of its high value collector and emitter resistors, R2 and R3, and correspondingly high value collector-base resistor, R1,

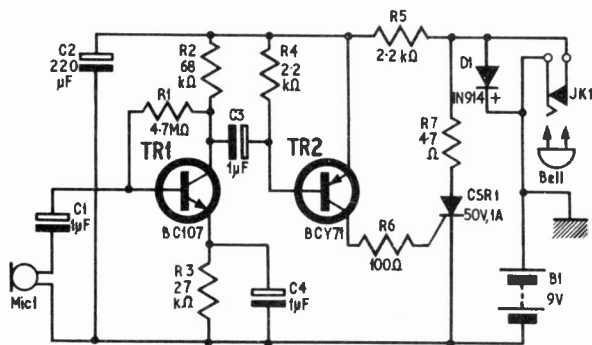


Fig. 1. Basic circuit diagram of the low-current ringing detector/bell

draws only $50\mu\text{A}$ when there is no input from the microphone.

At the same time, transistor TR2 is held non-conducting by R4, so that the thyristor CSR1 has no gate drive and passes only a very small leakage current. Thus the total current drawn is about $50\mu\text{A}$ and this, flowing through the bell coil, is far short of that required to operate it.

When the telephone bell sounds the crystal microphone MIC1 gives an output of about 100mV and this signal is amplified by TR1 to a sufficiently high level to cause TR2 to pass current; this current is fed to CSR1 gate. Thyristors have the property that if sufficient current is fed to the gate, the device conducts and will continue to do so, even without further gate current, until the current passed falls to a few mA or less.

In this instance the thyristor current is of course the bell operating current; shortly after it starts to flow it is interrupted by the action of bell circuit breaker and this interruption prevents further thyristor current passing.

However, if there is continuing microphone output the circuit operation described will continue and consequently the bell acts as a repeater of the telephone bell.

Resistor R5 and capacitor C2 isolate the amplifier stages from the transient voltages present due to the bell current changing rapidly, while R6 limits thyristor gate current to a safe value. Diode D1 eliminates reverse voltages caused by operation of the circuit breaker in the bell, which could otherwise damage the thyristor.

The battery voltage required for best operation of TR1 is 9V, while most bells call for about 4 to 5V. Thus R7 has been included to drop the voltage to ensure that no more than the correct voltage appears across the bell coil.

It will be seen that all the current drawn by the unit flows through the bell. This has been done so that disconnection of the bell also disconnects the battery from the remaining circuitry at the same time, so eliminating the need for an on-off switch.

CONSTRUCTION

Practical details are straightforward. Two 4.5V flat batteries and all else except for the bell and microphone are mounted in a small die-cast box. Connections to the bell are made by means of a 3.5mm jack, to make connection and disconnection easy.

The crystal microphone can be obtained as a "crystal microphone insert", and in the prototype is about $\frac{3}{8}$ in in diameter with leads about 2in long. These should be carefully extended (taking care to insulate the joints so made), to about 18in, so that the unit can be situated out of sight with the microphone insert placed under the telephone, where it will pick up the sound of the bell. A little experimenting may be called for to locate the best position for the microphone, but no difficulty should be experienced.

An alternative method of locating the microphone would be to fix it to a small rubber sucker with a suitable cement, such as impact adhesive, and then to attach it to the side or rear of the telephone.

The components, except for the diode D1, are mounted on a piece of 0.15in pitch Veroboard, $2\frac{1}{2}$ in \times $1\frac{1}{2}$ in; the Veroboard and component layouts used are shown in Figs. 2 and 3. Two holes are drilled in the board for fixing to the box. When drilling these, start from the copper side and use a piece of scrap wood as a backing to prevent splintering of the board as the drill breaks through.

Two 6BA screws are fixed to the base of the box in the appropriate place by means of nylon nuts, and the Veroboard dropped on top, to be secured by two steel or brass nuts. A piece of scrap cardboard, the same size as the Veroboard, is used as insulation underneath it. The protection diode, D1, can be located on the 3.5mm jack itself.

Four Veropins are located as shown on the circuit board to provide two connections for the microphone, one for battery negative and one for connection to the bell, via the jack centre contact. The

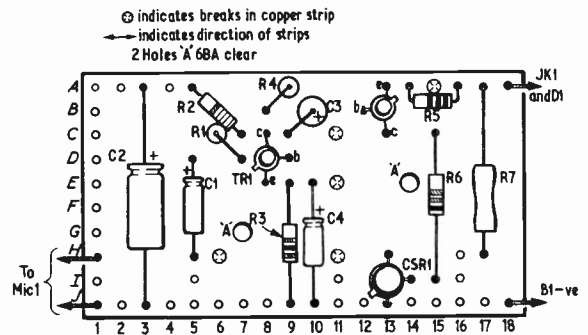


Fig. 2. Veroboard and component layout

COMPONENTS . . .

Resistors

R1	4.7MΩ
R2	68kΩ
R3	27kΩ
R4	2.2kΩ
R5	2.2kΩ
R6	100Ω
R7	4.7Ω 3W, W.W.
All $\frac{1}{4}$ W, 10% unless otherwise stated	

Capacitors


C1	1μF, 16V, elect.
C2	220μF, 16V, elect.
C3	1μF, 16V, elect.
C4	1μF, 16V, elect.

Semiconductors

TR1	BC107
TR2	BCY71
CSR1	50V 1A device
D1	1N914

Miscellaneous

Batteries, 4.5V (2 off). Diecast box $4\frac{1}{2}$ \times $3\frac{1}{2}$ \times 2in. Jack plug and socket. (3.5mm). Crystal microphone insert. Bell, 4 to 5V. Veroboard 0.15in pitch, $2\frac{1}{2}$ \times $1\frac{1}{2}$ in. Veropins. Grommet.

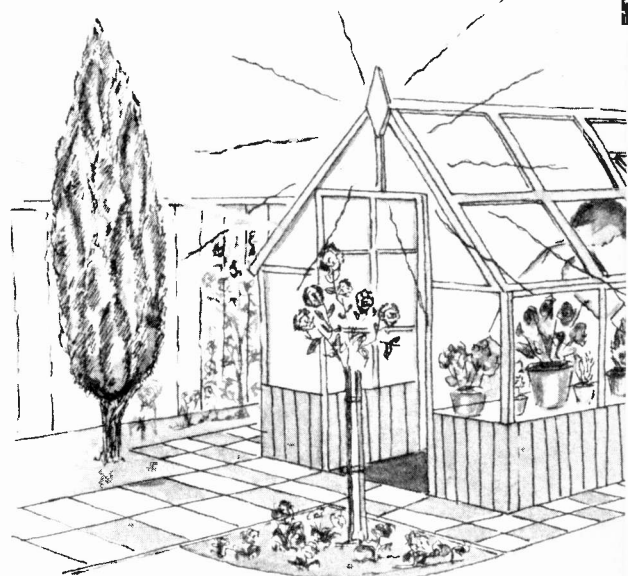

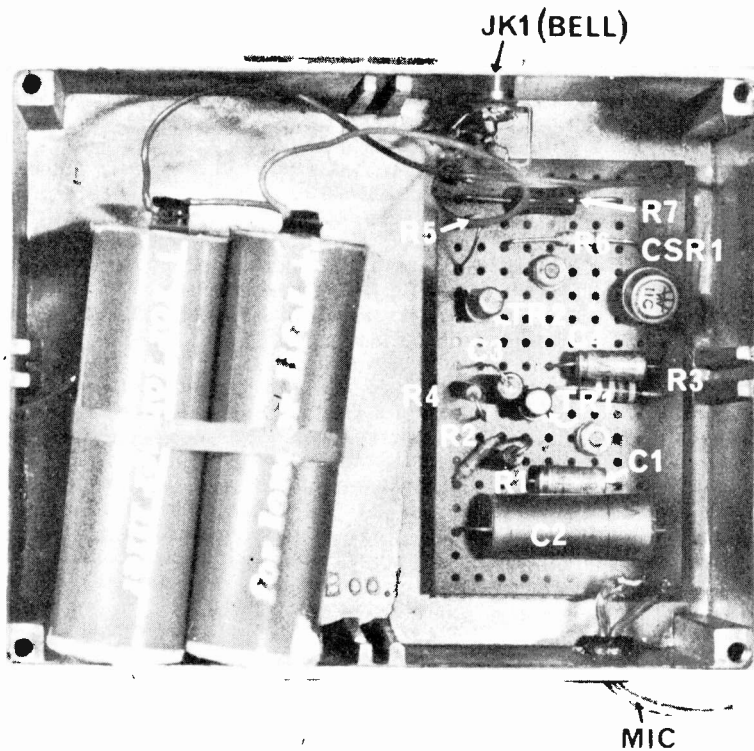


Fig. 3. Interior view of the Telebell case complete with batteries

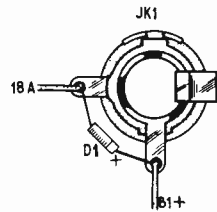


Fig. 4. Detail of the bell jack socket (JK1) showing the mounting of D1

other jack contact goes to battery positive; note that this is also joined to the box itself, so make sure that nothing else comes into contact with the case.

When inserting the Veropins, push through from the copper side and solder in place.

Leads to the batteries, from the Veroboard and jack, are best made about 5in long so that they can be made up before the batteries are dropped in. The latter are held together with a stout rubber band, and then held in place by the clamping action of the box lid, a thick piece of foam plastic being interposed to ensure that there is no movement.

The microphone leads are simply fed in through a small grommet and soldered directly to the appropriate Veropins.


When all the holes have been drilled in the box, temporarily blank them off on the inside with adhesive tape and spray the box a suitable colour, using a car touch-up or household paint aerosol. Then carry out final assembly of the unit as already described.

In use, it will be found that battery life will depend very largely on the frequency of incoming telephone calls, as the stand-by current consumption is very low. Even so, it is best to withdraw the jack plug (so eliminating all current drain) when the unit is not required, for example, when the house is unoccupied for a few hours or more.

Users may find it convenient to have a number of bells, with one located at each remote point, and to plug in which ever is required at a particular time. The use of a small jack facilitates this scheme considerably.

Some external noises can trigger the bell. For example a knock on the telephone or the like. However, the results are very brief and easily identified.

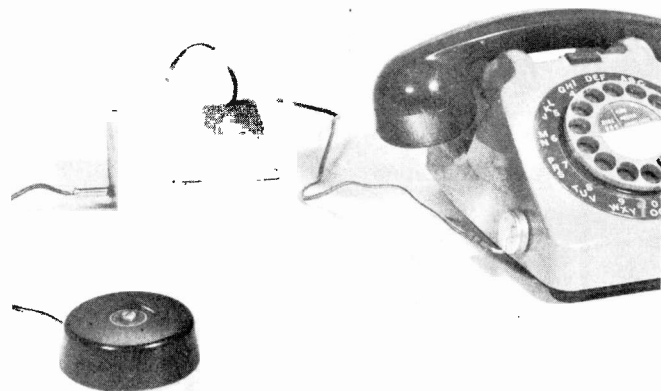If a gain control is felt to be necessary a 25k Ω variable resistor in series with 4.7 μ F electrolytic capacitor can be connected between TR1 collector and the negative rail. The lower the setting of the variable resistor the lower the gain. ★



NEXT MONTH . . .

Introducing the

PE

POWER SLAVES . . .

20

40

65

100

The first of a series describing a family of four, high quality, dual channel amplifiers providing outputs of 20, 40, 65 and 100 watts r.m.s. per channel. All versions are based on a common circuit configuration.

Low distortion figures make them ideally suited for use with high fidelity pre-amplifiers, P.A. systems, studio monitoring, electronic organs, electric guitars and servo systems.

Plus

CAR SYSTEMS MONITOR

Avoid unnecessary damage to your car with this simple electronic "black box" which gives alarm at sudden temperature or other gauge changes.

RANDOM LIGHT DISPLAY

Brighten up your life with the Random Light Display! Small enough to place on a shelf or table, yet capable of producing an endlessly varying and unpredictable pattern of colours.

*Starting
this month -*

PE **BONDO**

STEREO DECODER & F.M. TUNER

PRACTICAL

ELECTRONICS

JULY ISSUE ON SALE JUNE 14, 1974

AUDIO ROUND-UP

BY R.A. COLE

THE RONDO Quadraphonic system has proved to be of interest to many readers. As a result of work which has now been carried out by the author, various constructors and other correspondents, we are able to publish some suggestions and amendments of use to current and would-be constructors. The following includes updated information, corrections of errors which have willy-nilly crept into the various parts of this complex system and some suggestions on items such as earthing and switching.

Taking the simpler points first, in Part 1, page 757 the value of 0.7 noted in Fig. 1.10 should perhaps have been given in full as 0.707 since some readers might not have readily identified the accepted equivalent.

In the parts list on page 764 the capacitor C1 is given as 0.47 μ F when it should have been 0.047 μ F.

When setting up the amplifiers the preset VR8 should be slowly rotated clockwise until a reading of approximately 20mV is obtained. This reading corresponds to approximately 20mA.

POWER SUPPLY

The power supply board in Part 3, page 956, shows C26 as in a shaded portion of the circuit when in fact it should have been shown in the clear since it is mounted on the board as shown in Fig. 3.3. In this latter figure the components D15, C22, R34, and the components D14, C21, R33 are transposed. This does not cause circuit trouble since the circuit is symmetrical but it has proved confusing.

In the same figure the +ve and -ve 25V terminals to the right of the upper 0V terminal should be transposed + for -. The lowermost terminal to the right of this board shown as 24V a.c. should be shown as 20V a.c.

On the power board, TR6 can be replaced with an MJE3055 mounted with its metal face towards D9 to 12 and not towards C23 if one wished.

Also C23 is noted as 35V working but can be 30V working if desired. An additional hole is required for the positive end of D13 in the board.

In Fig. 3.1 the transformer winding feeding D9 to 12 should be shown as a 20V winding to agree with the earlier correction.

INPUTS

By some strange quirk of fate the input to the system from a gram. deck for stereo, SQ or QS was not shown in the original wiring or harness. In fact the input socket can be positioned to suit taste although perhaps a suitable location is at the unit "front" adjacent the tape input/output sockets.

It will, of course, be appreciated that the CD4 decode system is expected to be an add-on unit in view of the size and complexity problems involved. Hence the wired-in socket. Here it is expected that the CD4 unit will have its own tone controls and will accept 4-channel input from tape. Of course, 4-channel output is already available at the tape outputs in either coded matrix 2-channel or 4 discrete channels.

A simple modification which has been incorporated in later Rondos is the inclusion of a micro-switch as the mains switch, actuated by the slider of the master volume control. The switch is a press-to-open unit located at the low volume end of the control and actuated by the slider bar. Indication of system "on" is by means of panel illumination or perhaps an indicator lamp if needed.

In Part 4, Fig. 4.4, as in the power supply circuit, the 24V winding on the transformer should of course be 20V and again the + and -25V terminals should be transposed.

The headphone sockets in this figure were originally identified as Left and Right to conform with stereo practice but they should perhaps be annotated Rear and Front to conform to recently adopted quadraphonic practice.

POWER TRANSISTORS

There are a variety of power transistors suited to use in the Rondo power amplifier at TR4 and TR5 in Fig. 2.6. Using the p.c.b. layout given in the Fig. 2.12 TR4 may be a TIP2955 or an MJE2955K and TR5 may be a TIP3055 or an MJE3055K.

On the market there are now equivalent devices with different pin connections and to accommodate these we show in Fig. 7.1 a p.c.b. master which is electrically the equivalent of Fig. 2.12 but is capable of accepting MJE2955 for TR4 and MJE3055 for TR5.

This further board has an identical component layout and will in addition accept BC350 and BC347 from Motorola in place of BC212L and BC182L from Texas.

One or two readers have queried the power ratings in the speaker assemblies, January 1974 issue. It should be remembered that the total power output is shared between the four speaker units in each assembly, roughly in the proportions indicated in the diagram of Fig. 5.3. Thus about 50 per cent of the power appears in the lower register up to 300Hz, about 30 per cent in the zone from 300Hz to 5kHz, and the remainder in the upper register.

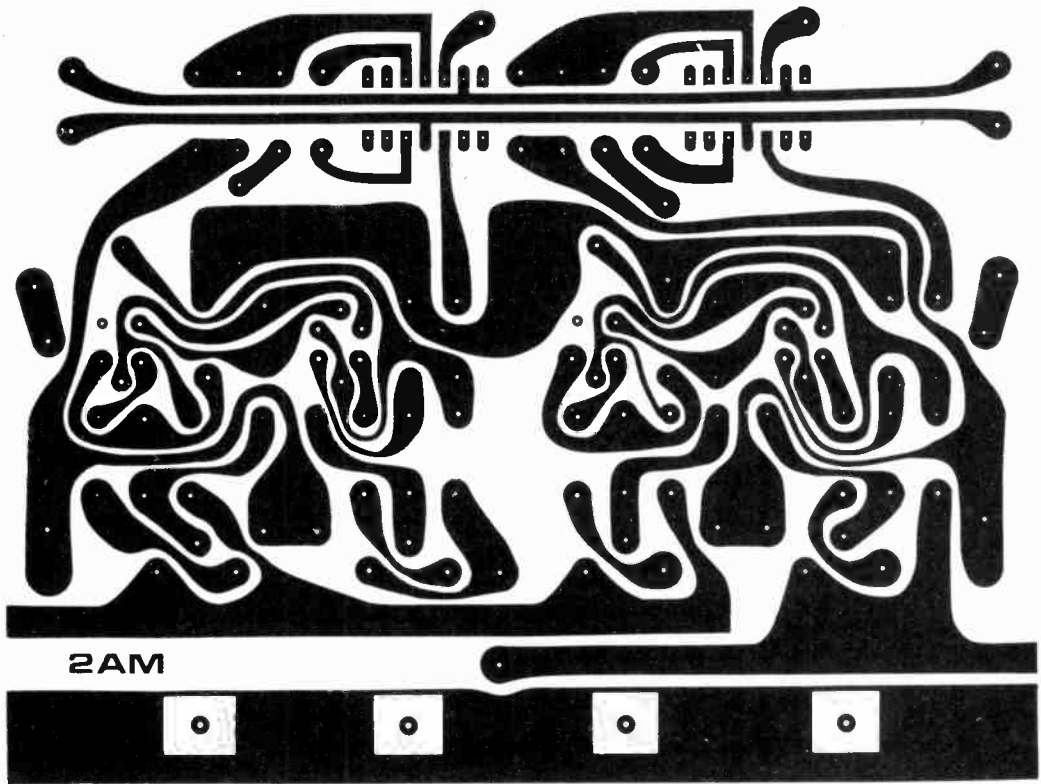


Fig. 7.1. Printed circuit master for a main amplifier stereo pair using output transistors with altered pin connections

EARTHING

It will be appreciated that in a system such as the Rondo, with four 20W channels and all the associated pre-amplifier and mixer circuitry, the avoidance of earth loops and stray pick-up is critical. Thus Fig. 7.2 shows the arrangement of earth and power links adopted for the power amplifier boards. This layout has proved useful in avoiding hum problems.


The link marked *A* in Fig. 7.2 can be made up from 16 s.w.g. wire which is passed through the board and a clearance hole cut in the heatsink so as to avoid chassis earth loops. The links from each board are joined and one is bent to go to the 0V power bus.

It should be noted that the power supply to the main amplifier boards is taken from the capacitors C19 and C20, not from the board tags, in order to reduce hum.

Other steps which can be taken include connecting the loudspeaker earths directly and individually back to the junction of C19 and C20.

If the earth connection between the pre-amplifier and tone control board is made via the screen of the signal lead, this will help. The earth from the tone to the main amplifier boards should be a separate 32/0.2mm wire of about 0.4m length which can subsequently be used to hum-buck by movement round the chassis when wired-in and in operation to a position of lowest hum value.

Fig. 7.2. Earth and power supply links used to avoid hum

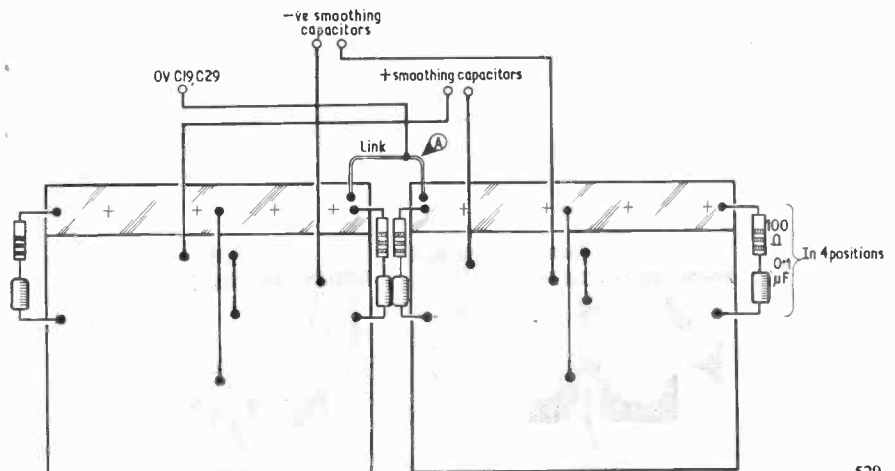

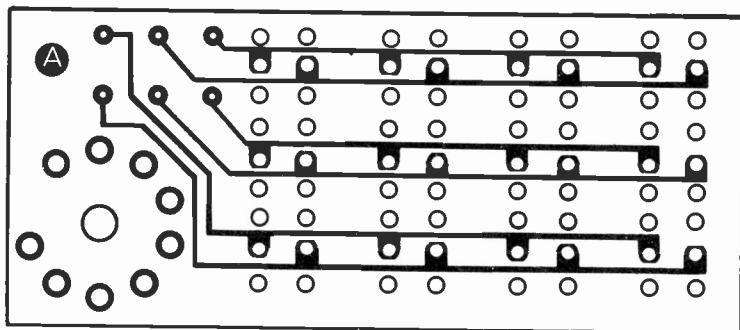
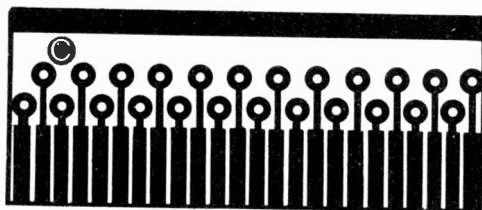
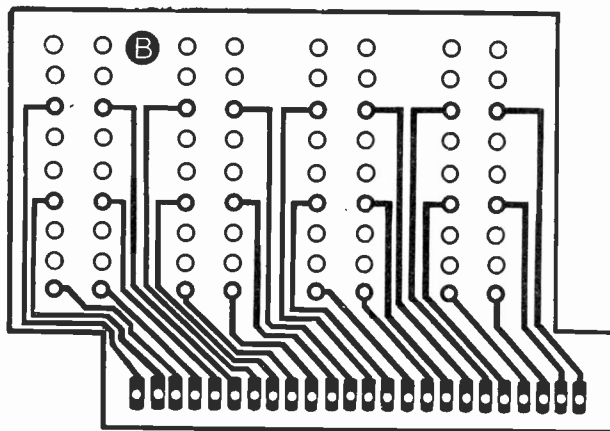
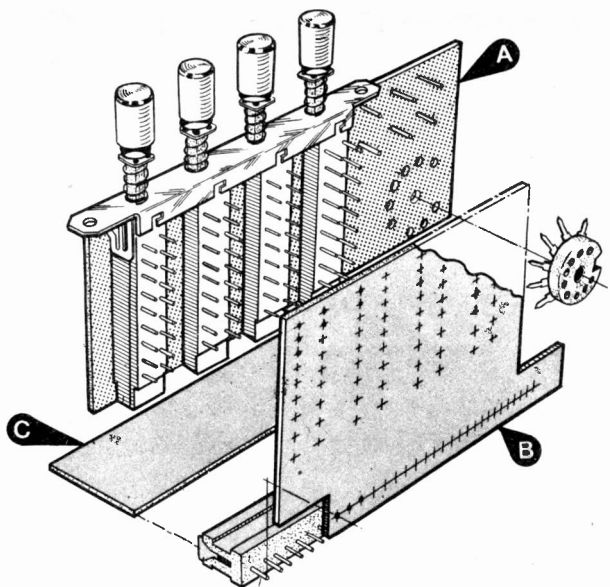


Fig. 7.3. The three items of p.c.b. and their assembly with the mode switch for simplicity of interwiring

As noted earlier, try to avoid any connection between the output transistors and the heatsinks. In fact it helps to isolate the sinks altogether if possible.

For simplicity of wiring it is possibly best not to earth all the Quad paths between the SQ socket and the selector switch. Earth only both ends of the LT and RT paths. The remainder should be earthed at the switch end only.

Apparently one or two readers have experienced difficulty in following through the circuit diagrams in relation to the inter-board wiring and input/output connections to the pre-amplifier. The following may help.

The pre-amplifier module is shown in Fig. 2.10 with the board layout at the top of the page. Output I from this board goes to the master tone/volume control board Left input and, via a $0.22\mu\text{F}$ capacitor, to the Left tape output. Output II in symmetry goes to the Right input of the one board and, via a further $0.22\mu\text{F}$ capacitor, to the Right tape output.

The inputs to the board may be connected to the pins projecting from the various parts of S1 either

from above or below the board. Thus looking at the component layout of Fig. 2.10 and identifying the switch sections as A, B, C and D from left to right, and the pins from 1 to 3 in the first column of section A and 4 to 6 in the second, from top to bottom (with corresponding numbering of the remainder) we have the tape Left input to pin A2 and Right to pin A5. Mono goes to pins 2 and 5 of B. Gram. Right goes to pin D2 whilst Left goes to D8.

In the circuit some of these switch contacts are inter-connected and the links are as follows. A3, C3 and D9 are connected together. Finally A6, B3 and C6 are connected together.

SWITCH INTERWIRING

For those who perhaps found the system interwiring diagram of Fig. 4.4 in the December issue a little overbearing, the author has developed two "back-wiring" p.c.b. panels and a "fanning strip" which can be used with the mode switches to simplify interwiring and any subsequent disassembly/assembly of a completed system.

NEWS BRIEFS

The back-wiring p.c.b. and the assembly of them with the switch units is as in Fig. 7.3. The switch button to the left in Fig. 7.3 corresponds to the lowermost button in Fig 4.4.

The p.c.b. A accepts a B9G valvebase which can be used as a socket for interwiring to the master tone control board, stereo decoder, and other fascia-mounted items, the connections to these being taken from the rear of the p.c.b. The switch interwiring is brought out to 6 Harwin pins which are similarly interwired. That deals with the interwiring "across" the switches.

The wiring "down" the switches is catered for with p.c.b. B which acts in co-operation with the fanning strip C. The p.c.b. carries a 24-way edge-connector into which the fanning strip plugs with the copper side underneath when the whole is assembled to a fascia.

Loom interconnections to the fanning strip are made as in Fig. 7.4 which also shows the strip zones for the systems not yet discussed.

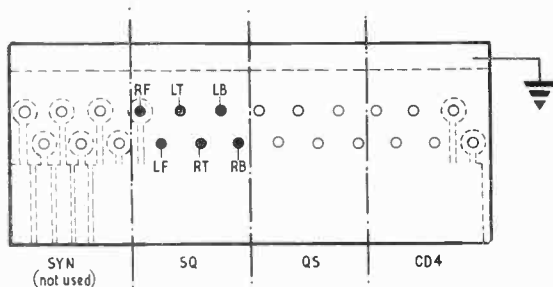


Fig. 7.4. Loom interconnections to the fanning strip C of Fig. 7.3

INPUT SENSITIVITY

The basic sensitivity of the Rondo with RIAA correction is 3mV with S1 in the "Gram" position. In the linear positions it is 45mV with the circuit as shown. This should, of course, cover most requirements for external equipment which will be met.

However, requirements can in fact extend from 3mV up to 2V when dealing with magnetic pick-ups and microphones at one end and external tape equipment at the other.

To accommodate such a range it is necessary to adjust the feedback resistor R8 (Fig. 2.3, October issue) if an increased sensitivity is required and to select suitable values of R1, 2 or 3 for lower sensitivities. As a guide, a value of R8 of 22k Ω gives a sensitivity of around 4-5mV.

If R1, 2 or 3 is 22k Ω with an R8 of 1.2k Ω a sensitivity of 100mV is obtained. For much lower sensitivities a simple attenuator including a series resistor as well as R1, 2 or 3 can be used. The values of the series R and R1, 2 or 3 can be selected to give the correct matching impedance to the feeding source and the correct ratio of voltage reduction to the Rondo equipment.

Finally, one or two components are not shown mounted on p.c.b., for example C5 and C105, the tape output decoupling capacitors. These are mounted at suitable locations in the assembly wiring. Thus C5 and C105 can be mounted at the DIN sockets.

Next month: In the July issue we will commence the Stereo decoder and f.m. tuner description.

Light Modulator enables Laser Beam to carry 25,000 Phone Calls

IT HAS long been realised that laser beams have the capability of carrying a vast amount of information, but, so far, the modulators (i.e. the devices for getting the information onto the beam) have been large, costly and consumed many hundreds of watts.

Now, scientists at RCA have made what they regard as a major electronics advance in the form of the first electro-optic modulator truly compatible with integrated circuits.

The new modulator has an active volume of only 0.12 x 0.02 x 0.02ins. It uses a thin film of lithium niobate tantalate sandwiched between minute interleaving metal fingers. The materials used have the property of changing the speed of the photons through them when a voltage is applied.

The new device is capable of 80 per cent modulation of red light with only six volts. The power needed to drive it at even the highest frequencies is only a few watts.

Though still in the research stage RCA claim that this device will give laser beams the capability of carrying 25,000 telephone calls or 20 TV channels simultaneously.

Micromotors Miniaturise Medical Logging Device

THE development of reliable micromotors by Portescap has made possible portable data logging systems small enough to fit in the pocket.

The Oxford Instruments' "Medilog" is capable of 24-hour continuous monitoring of four separate data channels, though it uses only a standard low-cost magnetic tape cassette and measures only 112 x 86 x 36mm overall.

Because the unit is so small it can be easily and unobtrusively carried by a patient whose condition is to be monitored. The batteries last up to 30 hours, so for continuous monitoring all that needs to be done is to change the batteries and the cassette.

One of the main problems in relatively slow speed recorders is the maintenance of constant speed. This was achieved by electronically controlling the speed of the motors and accurately aligning the gearbox with the capstan spindle.


Non-medical applications include use in oceanography, vehicle vibration and noise level monitoring.

Paging Down Under

THE NEW Sydney Opera House has been equipped with a radio pocket paging system designed by the London based firm of Multitone Electric Co. Ltd.

Because of the unique structure of the building, specially designed aerials had to be positioned to obtain complete coverage throughout all areas of the Opera House complex. Positioning of the transmitters was another problem, some being hidden in the ceiling of the concert hall and one even in the ceiling of the "gentlemen of the chorus" dressing room.

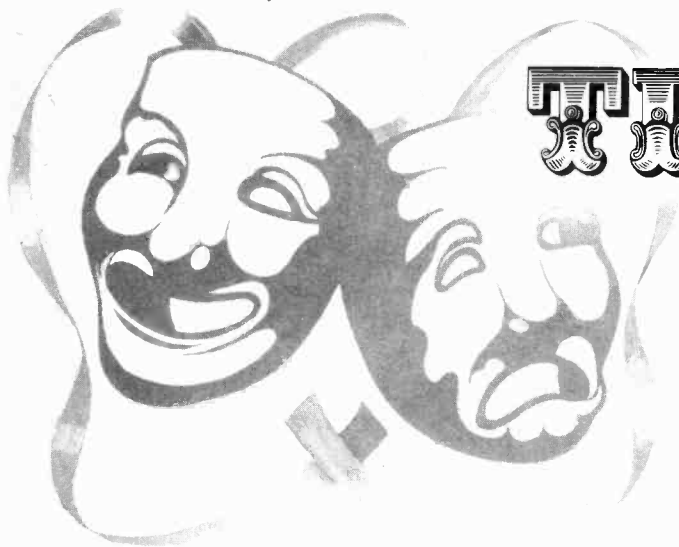A total of 40 lightweight receivers are used by the staff. There is a special alarm facility in the system which enables group calling to be used to alert such groups as fire fighters instantaneously.



THEATRE

CUEING LIGHTS

By S.H. DAVIES

Make sure the curtain goes up on time with this versatile signalling unit

THIS system was constructed to fulfil the need for a unit which could communicate with up to four remote stations using the following light signals:


1. A red and a green light on both master and remote units to signal "standby" and "go", the lights to remain illuminated until cancelled either by the master unit or by the remote unit acknowledging the signal.

2. An amber light on the master unit only, for the remote station to attract the attention of the master unit. This would also light when the remote station acknowledged the signal from the master.

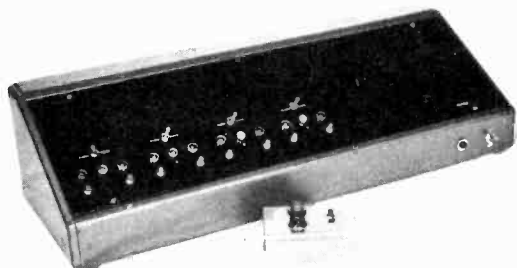3. A flash facility on red and green lights for pre-arranged emergency signals. (In one show a flashing red light to the pianist meant "keep on playing"!)

The final unit was designed to be strong, have room for additional facilities and to look reasonably presentable. It has the added advantage that if a cable breaks or becomes open circuit the appropriate lamps on the master unit will not light, giving warning of the fault.

The unit requires only three wires per channel between the master and remote terminals, enabling ordinary three-core mains cable to be used.



We would like to thank the Petts Wood and District Operatic Society for the loan of the unit

COMPONENTS . . .

FOR ONE CHANNEL

Resistors

R1, R7 4.7k Ω (2 off) R3, R8 470 Ω (2 off)
R2, R6 1k Ω (2 off) R4, R5 1k Ω (2 off)
All $\pm 10\%$ $\frac{1}{4}$ W carbon

Capacitors

C1, C2 25 μ F 25V elect. (2 off)

Diodes

D1-D4 1N4001 (4 off)

Thyristors

CSR1-CSR4 C6U (Jermyn Industries, 120 Vestry Estate, Sevenoaks, Kent) (4 off)

Lamps

LP2-LP6 6.3V 0.3A m.e.s. with holders (5 off)

Switches

S2 D.P.D.T. miniature toggle
S3, S4 Push-to-make, release-to-break push-button (2 off)
S5 Push-to-changeover pushbutton

Plugs and Sockets

PL1, SK1 3-pin mains plug and socket (Bulgin)

Miscellaneous

3in \times 2in \times 1 $\frac{1}{2}$ in aluminium case

FOR COMPLETE UNIT

Transformer

T1 Mains primary, 0-6.3V, 0-6.3V secondary (see text)

Miscellaneous

S1 D.P.D.T. mains switch
FS1 1A fuse and holder
LP1 Mains neon and holder

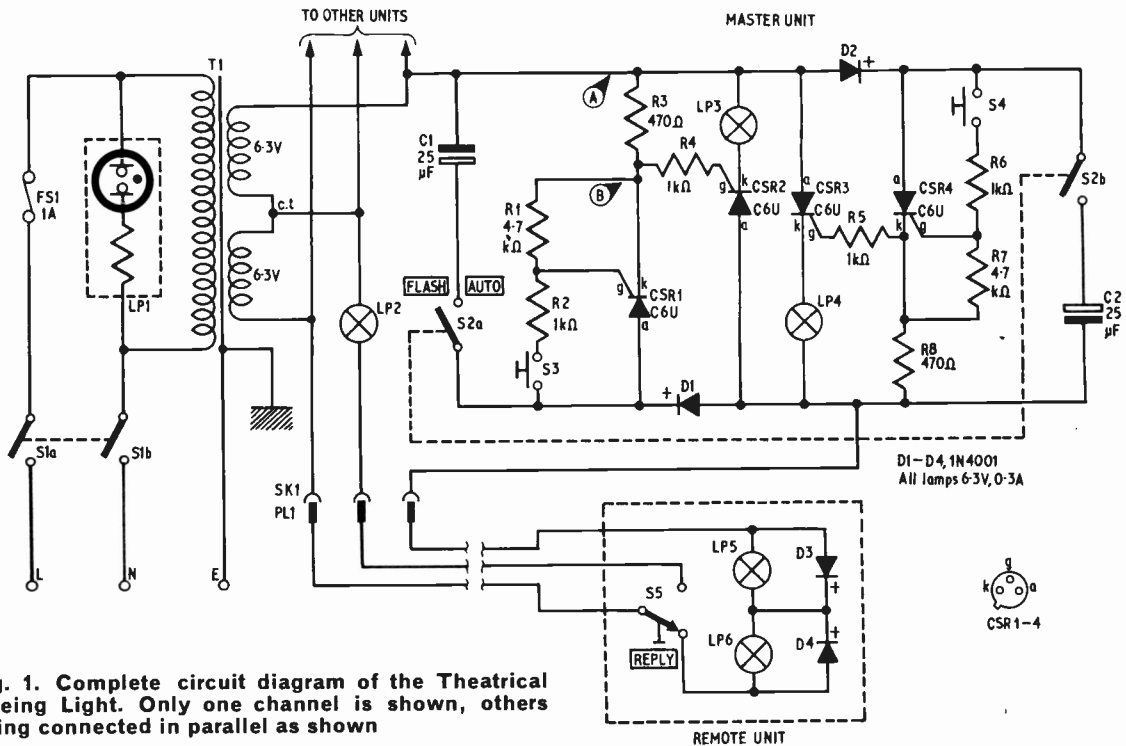


Fig. 1. Complete circuit diagram of the Theatrical Cueing Light. Only one channel is shown, others being connected in parallel as shown

CIRCUIT PRINCIPLES

The circuit of the Cueing Light is shown in Fig. 1. Considerable use is made of the fact that a thyristor will stay conducting once switched on, and will only cease conducting when the current through it falls below a certain value, called the holding current.

In the circuit the positive and negative going portions of the a.c. supply are used to power different bulbs (the thyristors also act as diodes when switched on).

First, consider what happens when S2 is open, i.e. in the "flash" position. Pressing S3 supplies gate current to CSR1 switching it on until S3 is released. Switching on CSR1 causes the voltage at B to become sufficiently positive with respect to A to switch on CSR2, lighting LP3 in the master, and LP5 in the remote units. Once S3 is released both lights will extinguish. Hence the "flash" facility.

With S2 closed (in the "auto" position), diode D1 rectifies the a.c. and C1 smooths it, giving smooth d.c. across CSR1. Providing R3 is small enough to pass the holding current, CSR1 will stay on after S3 is released and therefore CSR2 will also stay on.

Lamps LP3 and LP5 will stay on after S3 is pressed and can be switched off either by pressing S5 in the remote unit (which illuminates LP2 in the master), or by S2 which removes the smoothing capacitor causing the voltage to fall below the holding level fifty times a second.

The other half of the circuit (CSR3 and CSR4) works in exactly the same way except that it operates on the opposite half cycles of the a.c.

CONSTRUCTION

The components in the master unit were mounted directly on the panel, no board being felt necessary (see Fig. 2). Ensure that all leads are sleeved to

prevent accidental short circuits, and cover the thyristor cans with insulating tape.

The case will obviously depend on individual needs so no overall dimensions are given. The transformer should be of sufficient current rating to drive the number of units required, each taking about 300mA.

A fuse and neon indicator should be fitted, as many theatres still use unfused plugs.

The master and remote units are connected by the three-core cable fitted with a three-pin plug which fits into a socket in the back of the master.

Constructional details for only one channel are shown, others being connected in parallel with the power supply as indicated in Fig. 1.

Continued on page 541

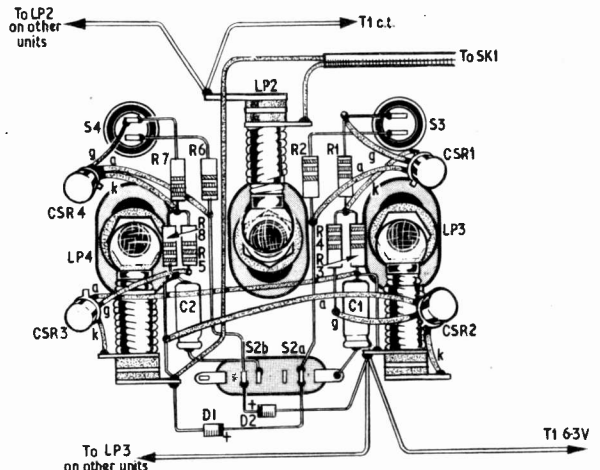


Fig. 2. Layout of the components on the master unit front panel

OSCILLOSCOPE KIT


A new oscilloscope kit specially designed for use on 2-channel and 4-channel stereo systems has been announced by **Heath (Gloucester) Ltd.** Designated type AD-1013 Audio Scope, the instrument is ideal for visual checking and monitoring of such parameters as channel separation, phasing, relative signal strengths, multipath reception and centre-tuning of receivers and tuners.

A built-in four channel decoder gives independent or simultaneous visual indication of all four channels. It is claimed that by using a triggered sweep circuit a stable, jitter free signal trace is obtained.


Inputs are provided on the rear panel for Left-Front, Left-Back, Right-Front, Right-Back and Multipath. Any of these inputs can be switched and observed on the screen, independently or in combination. Illuminated function indicators on the front panel show what function is being displayed.

An input, on the front panel, is provided for observing any external signal, permitting the equipment to be used as a conventional oscilloscope for checking out equipment malfunctions. A built-in independent 20Hz to 20kHz low distortion audio oscillator provides a convenient means of adjusting and checking any stereo system. Front panel controls are provided for frequency selection of the audio oscillator as well as controlling the amplitude of the generated signal.

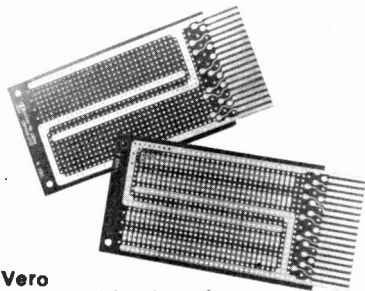Most of the components are mounted on a single circuit board and point-to-point wiring is kept to a minimum to aid construction. The price of the Heathkit AD-1013 Audio Scope is £99.55 mail order, carriage extra. More information is obtainable from Heath (Gloucester) Ltd., Bristol Road, Gloucester.



Vero printed wiring boards

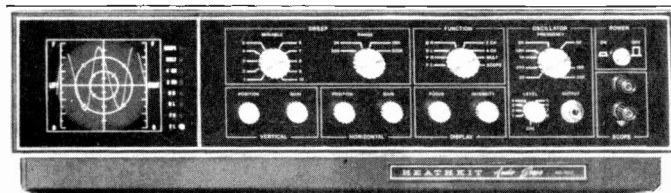

Four channel audio oscilloscope from Heath

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned.

NEW OSCILLOSCOPES

Two new low cost, high performance oscilloscopes have been introduced on the market by **Advance Electronics**. Intended for industrial or educational use, the OS140 and OS240 have a 10MHz bandwidth, input sensitivity of 5mV/0.8cm (the smaller tube face size of 10cm dictated a graticule division of 0.8cm) and a triggered time base.

The OS240 has a double beam facility implemented by i.c. switching.

A design philosophy aimed at economy in price and construction without degrading a high performance specification has resulted in relatively few piece parts and, very noticeable, a complete absence of cable looms.

Most of the circuitry is contained on three plug-in printed boards. Plug-in mounting of these boards means easy availability for servicing.

Both instruments measure 132 x 270 x 317mm and weigh approximately 5kg. Prices of the OS140 and OS240 are £107 and £125 respectively. Full technical specification for the oscilloscopes can be obtained from Advance Electronics Ltd., Roebuck Road, Hainault, Essex.

PRINTED CIRCUIT KIT

With the increasing complexity of many of the published circuits it seems that the popularity of making printed circuits to aid the ease of construction is on the increase. Readers may be interested in the new printed circuit kit from

Dattur Ltd., which provides all the requirements for etching circuit boards.

A feature of the kit is a plastics hole template which allows for transistor and i.c. configurations to be easily scribed onto the copper laminate.

Also contained in the kit are three boards, resist pen, scribe, plastics tongs and funnel, and large bottles of resist remover and etchant. The large plastics case also doubles as an etching bath.


The kit retails at £7.95 and is available from Dattur Ltd., Market Road, Richmond, Surrey.

D.I.P. BOARD


Two special d.i.p. boards have recently been introduced by **Vero Electronics**. These have a 0.1in pitch hole matrix and are designed to mate with standard D.E.C. connectors.

Initially available in two sizes, both five inches long, one being of single height and the other of double height. Readers who are commencing building the "Rhythm Generator", recently published in P.E., should find that the board is suitable for mounting the logic circuitry.

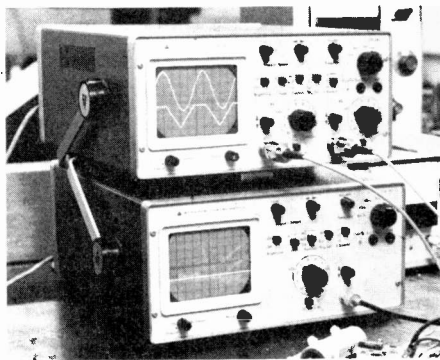Full details of the boards can be obtained from Vero Electronics Ltd., Industrial Estate, Chandlers Ford, Eastleigh, Hants.



New Advance oscilloscopes

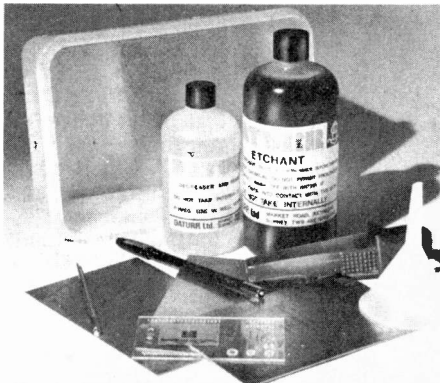

Printed circuit kit by Dattur

NEW DEVICES ... APPLICATIONS

PROGRAMMABLE TIMER/COUNTER

AN INTEGRATED circuit capable of producing programmable time delays ranging from microseconds up to five days has been produced by Exar Integrated Systems.

Accuracy is such that the device is a viable replacement for mechanical or electromechanical timers. With two devices in cascade the timing period can be increased up to five years!

CIRCUIT DESCRIPTION

A simplified circuit diagram of the device, designated XR-2240 or, in a less accurate version, XR-2340, is shown in Fig. 1. It can be seen to consist of three main sections: a time base; an eight stage binary counter; and a control bistable.

The time base circuit needs two external timing components (R and C) to produce an accurate clock oscillator.

The timing cycle is initiated by applying a positive-going trigger pulse to the TRIGGER input of the control bistable. This trigger pulse starts the time base oscillator, clears the counter stages back to zero and makes the counter ready to accept an input.

The time base oscillator produces timing pulses with a period T equal to the product of the timing components $T = CR$. The pulses from the time base are counted by

the eight bistables forming the binary counter, the output from each being available.

The timing period is ended when a reset pulse is applied to pin 10.

GENERAL PURPOSE TIMING

In most timing applications one or more of the counter outputs are connected back to the reset terminal as shown in Fig. 2, with S1 closed. This causes the timing period to start with the trigger pulse and to end when a pre-programmed count is reached.

The counter outputs are open collector types and the timing period is determined by which particular outputs are connected to the load resistor R_L and the reset input.

For instance, if a timing period of 100T was desired then pins 3 (4T), 6 (32T) and 7 (64T) would be connected to R_L (since $4T + 32T + 64T = 100T$).

LONG DELAYS

For extremely long delays with low power consumption, two XR-2240 i.c.s may be cascaded as in Fig. 3. Referring back to Fig. 1 it will be seen that a regulated voltage is available at pin 15 and it is this voltage which is fed to the second i.c.

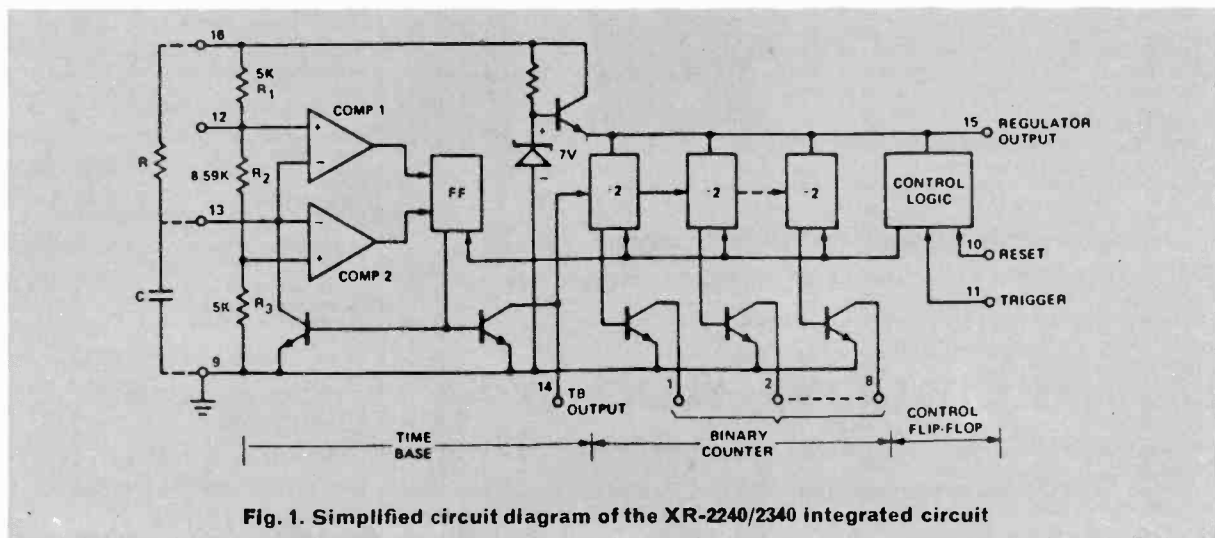


Fig. 1. Simplified circuit diagram of the XR-2240/2340 integrated circuit

WILMSLOW AUDIO

THE Firm for Speakers!

SPEAKERS

Baker Group 25, 3, 8 or 15 ohm	£7-75
Baker Group 35, 3, 8 or 15 ohm	£8-50
Baker Group 50/12, 8 or 15 ohm	£12-50
Baker Deluxe	£10-75
Baker Major	£8-50
Baker Superb	£14-50
Baker Regent	£7-75
Celestion PST8 (for Unilex)	£2-55
Celestion MF1000, 8 or 15 ohm	£10-45
Celestion HF1300 Mk. II	£6-16
Celestion G12M, 8 or 15 ohm	£12-00
Celestion G12H, 8 or 15 ohm	£15-00
Celestion G15C, 8 or 15 ohm	£24-00
Celestion G18C, 8 or 15 ohm	£33-00
EMI 13 x 8in, 3, 8 or 15 ohm	£2-15
EMI 13 x 8in d/c, 3, 8 or 15 ohm	£2-35
EMI 13 x 8in t/w, 3, 8 or 15 ohm	£3-60
EMI 13 x 8in type 350, 8 ohm	£8-25
EMI 8 x 5in cer. mag., 8 or 15 ohm	£1-65
EMI 8 x 5in, 10 watt, d/c roll, surr., 8 ohm	£2-80
EMI 6in, 93850, 4 or 8 ohm	£2-80
EMI 5in, 98132CP, 8 ohm	£2-30
Elac 9 x 5in, 59RM109 15 ohm, 59RM114 8 ohm	£2-65
Elac 6in d/c roll surr., 8 ohm	£3-35
Elac 6in d/cons, 8 ohm	£2-65
Elac Tweeter TW4 4in	£1-21
Elac 10in, 8 ohm	£2-65
Fane Pop 100 watt, 18 in	£22-50
Fane Pop 60 watt, 15in	£13-00
Fane Pop 50 watt, 12in	£11-00
Fane Pop 25.2, 12in	£6-40
Fane Pop 15 watt, 12in	£4-40
Fane Crescendo 12A or 12B	£29-00
Fane Crescendo 15	£36-00
Fane Crescendo 18	£47-50
Fane 807T 8 in d/c roll surr., 8 or 15 ohm	£3-85
Fane 808T 8in d/c, 8 or 15 ohm	£2-75
Goodmans 8P, 8 or 15 ohm	£4-49
Goodmans 10P, 8 or 15 ohm	£4-70
Goodmans 12P, 8 or 15 ohm	£11-65
Goodmans 15P, 8 or 15 ohm	£18-00
Goodmans 18P, 8 or 15 ohm	£31-00
Goodmans 12P-D, 8 or 15 ohm	£15-25
Goodmans 12P-G, 8 or 15 ohm	£14-50
Goodmans 12AX Audiomax, 8 or 15 ohm	£39-65
Goodmans Audiom 100	£9-50
Goodmans Axent 100	£6-60
Goodmans Axiom 401	£15-10
Goodmans Twinaxiom 3, 8 or 15 ohm	£6-79
Goodmans Twinaxiom 10, 8 or 15 ohm	£7-61
Kef T27	£4-75
Kef T15	£5-75
Kef B110	£6-75
Kef B200	£7-50
Kef B139	£11-75
Kef DN8	£1-92
Kef DN12	£4-12
Kef DN13	£2-75
Richard Allan 12in d/c, 3 or 15 ohm	£2-50
Richard Allan CG8T 8in d/c, 8 ohm	£6-35
WMT1 speaker match. trans., 3-15 ohm	£1-10

Wharfedale Super 10 RS/DD	£9-80
2 1/2in 64 ohm, 70mm 8 ohm, 70mm 80 ohm	65p
7 x 4in, 3, 8 or 15 ohm	£1-38
8 x 5in, 3, 8 or 15 ohm	£1-38
10 x 6in, 3, 8 or 15 ohm	£1-92
S.T.C. 4001G Super Tweeter	£6-19

Speaker Kits

Wharfedale Linton 2 (pair)	£19-25
Wharfedale Glendale 3 (pair)	£34-50
Wharfedale Dovedale 3 (pair)	£52-00
Richard Allan Tinkit (each)	£8-25
Richard Allan Triple 8 (each)	£13-00
Richard Allan Triple (each)	£18-00
Richard Allan Super Triple (each)	£21-50
Goodmans DIN 20 (each)	£8-75
Fane Mode 1 (each)	£9-90
Peerless 20-2 (each)	£10-41
Kefkit 2 (each)	£23-50
Kefkit 3 (each)	£34-00
Helme XLK25 (pair)	£18-17
Helme XLK50 (pair)	£37-18
Baker Major Module	£10-75
P.A. and Hi-Fi speaker cabinets. Send for booklet "Choosing a Speaker". Carr. and Insurance 75p per kit (£1-50 pair).	

PA/Disco Amplifiers

(Carriage and Insurance £1)	
Baker Major 100 watt	£46-00
Linear 30/40	£25-00
Linear 40/60	£30-00
Linear 80/100	£55-00

Radios/Cassettes

Grundig Solo Boy	£16-00
Grundig Top Boy	£17-75
Grundig Party Boy 500	£22-75
Grundig Melody Boy 500	£26-75
Grundig Elite Boy 500	£26-75
Grundig Signal 500	£26-50
Grundig Yacht Boy 210	£34-00
Grundig Melody Boy 1000	£38-75
Grundig Satellite 2000	£121-00
Grundig C410 Cassette	£28-50
Grundig RF430 mains radio	£26-75
Grundig RF310 mains radio	£22-00
Tanberg TP41	£43-00
ITT Weekend Auto	£18-00
ITT Golf Preset	£24-50
ITT Colt	£11-50
ITT Europa	£20-50
ITT SL53 cassette	£25-75
ITT Studio 60M cassette	£32-75
ITT Studio 73 cassette	£48-00
Bush VTR178, 5 band (inc. air)	£29-00
Koyo KTR1770 11 band	£58-95
Koyo KTR1663 or 1664, 8 band	£42-00
Koyo KTR1883, 5 band	£22-00
Murphy BA209 radio/cassette	£32-75
Carriage and Insurance 75p. FREE with each radio—World radio stations book.	

Free with speaker orders over £7—

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch. Carriage 35p per speaker (tweeters and crossovers 20p).

ALL PRICES QUOTED INCLUDE VAT

WILMSLOW AUDIO

Dept. PE

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire, SK9 1HF.

Radios, etc.: 10 Swan Street, Wilmslow, Cheshire. Telephone: Wilmslow 29599

PARTRIDGE MAINS ISOLATION TRANSFORMER, Pri: 150-250V, 5V steps, Sec: 240V, 13 amp, £15, carr. pack, £2-25.

GARDNER'S POTTED TRANSFORMER, Pri: 200-250V, Sec: 18V 500mA, 50V 150mA, 6V 250mA output, £1, p.p. 28p.

RIPLEY MAINS TRANSFORMER, Pri: 110V-240V, Sec: 12-5V, 0.12-5V 750mA 7V:0.7V 1A, £1, p.p. 25p.

MAINS TRANSFORMER, Pri: 100-250V, Sec: 22-0-22 200mA, 22-0-22 100mA 0.2-2V 200mA, 80p, p.p. 25p.

MAINS TRANSFORMER, Pri: 100-240V a.c. 36-5-0-36-5V, 27mA, 0-21-0, 260 mA, 80p, p.p. 25p. **TRANSISTOR OUTPUT TRANSFORMER**, Ratio 8:1-120mH, Centre tap 2 watts, output, 20p, p.p. 8p.

WODEN MAINS TRANSFORMER, Auto wound, Pri: 200-250V, Sec: 105-135V, 3kVA, £15, Carr. £1-50.

HADDON MAINS TRANSFORMER, Pri: 230V, Sec: 20V 1 amp, £1-60, p.p. 27p.

MIN. MAINS TRANSFORMERS, Type 608/1, Sec: 6V-0-6V, 100mA, 75p. Type 909/1, Sec: 9V-0-9V, 100mA, 81p. Type 1201/1, Sec: 12V-0-12V, 100mA, 80p, p.p. 5p each.

SMOOTHING CHOKE, 11MH, 1 1/2in x 1 1/2in x 1 1/2in, 20p, p.p. 8p.

PINNED ALUMINIUM HEATSINK, 4 1/2in x 6in x 1in, 2 x 2N3055, £1, p.p. 13p.

GOODMANS 8in SPEAKERS 3 Ω £1-50, p.p. 28p. **LOUDSPEAKER 2in Dia., 40 Ω, 300m/watts, 50p**, p.p. 8p.

PINNED ALUMINIUM HEATSINK, 3in x 8in x 1 1/2in, in C: 4 x 2N3055, £2, p.p. 29p.

GARRARD MAG. TAPE DECKS: 131.p.s., 50V, solenoid operated brakes, etc. Mains voltage motors £7-60 each, p.p. 60p.

10 REED SWITCHES operated by push buttons and magnets, 50p, p.p. 25p.

COMPONENT PANEL, 6 ser's (300V, 1-6A) 6 cond., 12 resistors, 6 diodes, 45p, p.p. 8p.

COMPONENT PANEL, 6 ser's (200V 4 amps), 6 condensers, 12 resistors, 30p, p.p. 8p.

COMPONENT PANEL, 1 ser: 100V, 15 amp, 1 diode, 1 cap., 500mfd 50V, 50p, p.p. 7p.

VEEDER ROOT ELECTRICAL IMPULSE COUNTER NON-RESETTING, A.C. 200-250V, £1-10, p.p. 13p.

GEC MAINS CIRCUIT BREAKERS, 2 amp or 5 amp, £1 each, p.p. 14p.

LEVER ACTION P.O. 1000 TYPE SWITCHES

Lock 4-pole changeover, 15p, p.p. 4p. Ex equip. Lock 2-pole changeover, 10p, p.p. 4p. Ex equip.

MULLARD & MALLORY SCREW TERMINAL CAPACITORS 4,500pF 64V, 7,100pF 40V, 50p each, 20,000 30V, 25,000 25V, 35,000 15V, 30p each, p.p. 21p.

MULLARD FULL WAVE RECTIFIERS 6-48V, 15 amp, 75p, p.p. 10p.

BELLING LEE 1-5 amp in-line rubber covered interference suppressor, 25p, p.p. 8p.

RUBBER 3 PIN 5 AMP NON-REVERSIBLE CABLE CONNECTORS, 20p, p.p. 5p.

SOLENOIDS 12 VOLT PULL ACTION 2in x 1in x 1in, 40p, p.p. 8p.

SOLENOIDS 12-24V d.c. pull action 1 1/2in x 1 1/2in x 1 1/2in, 40p, p.p. 8p.

SOLENOIDS 240V a.c. pull action 2 1/2in x 1 1/2in x 1 1/2in, 60p, p.p. 9p.

SOLENOIDS, Manf. by Bensons, 240V a.c. Pull action 2 1/2in x 1 1/2in x 1in, 75p, p.p. 9p.

OMRON MK2 MIDOET POWER RELAY, 12V d.c. Double pole changeover. New, 70p, p.p. 5p.

STC VABLEY, miniature relays 700 Ω, 17-5-37V, perspex cover, 4 pole changeover, 40p, p.p. 5p.

POTTER BRUMFIELD 12V d.c. coil 3 pole c/o contacts rated 7 amp, £1, p.p. 10p.

I.T.T. LOW PROFILE RELAYS, 4 pole c/o overs. 500 Ω 12-18V, 75p, p.p. 5p.

MAINS RELAYS, 200-250V a.c. 2 makes. Heavy duty contacts, 50p, p.p. 7p.

KEYSWITCH RELAY, 12V d.c. Coil 3 S.P.C.O. 90p, p.p. 8p.

TELESCOPIC AERIALS

Chromed 7in closed, 28in extended, 6 section ball jointed base, 23p, p.p. 5p new.

PRINTED CIRCUIT BOARD/19 ACY 19's 10 ΩA200

Diodes: 1 reed relay: 1 AZ 229 zener ass. capacitor/resistors. Power supply 22V, 250 mA d.c. 240V a.c., £1, p.p. 25p. Ex. equip.

TAPE POSITION INDICATOR

Resettable 3 digits, 30p, p.p. 5p.

All orders add 10% V.A.T.

FIELD ELECTRIC LIMITED

3 Shenley Road

Borehamwood, Herts.

Tel. 01-953 6009

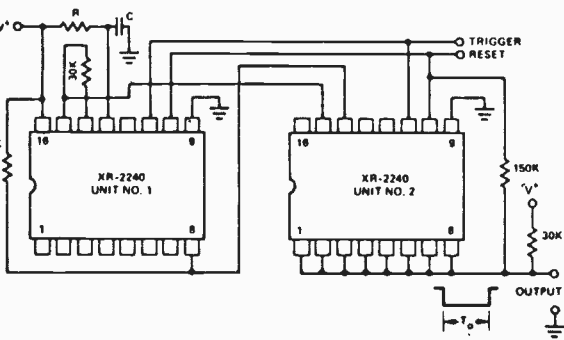
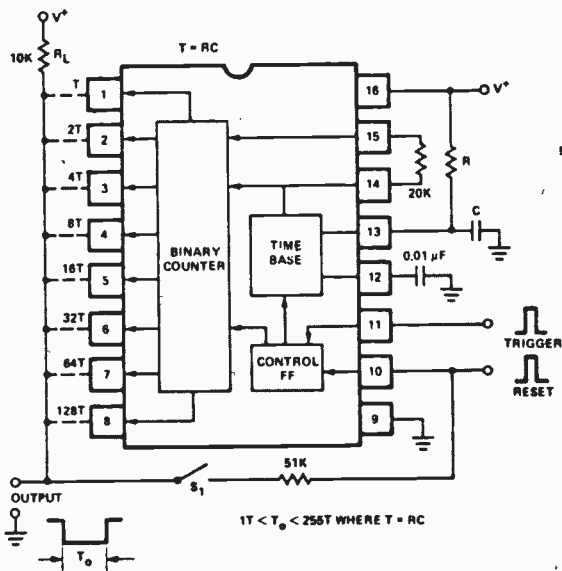


Fig. 2. Generalised circuit connection for timing applications. With S1 open the circuit operates in astable mode; with it closed, in monostable mode (left)

Fig. 3. Two devices connected in cascade for low-power, long time delay operation (above)

FREQUENCY SYNTHESIS

The programmable counter section of the XR-2240 can be used to generate 255 discrete frequencies from a given time base setting using the circuit shown in Fig. 4. The output of the circuit is a positive pulse train, the pulses being T seconds wide, and occurring at a period of $(N + 1)T$ seconds, where N is the programmed count in the counter.

Thus by changing the value of N (by shorting different outputs together) 255 frequencies are generated.

ANALOGUE-TO-DIGITAL CONVERTER

Fig. 5 shows a simple eight-bit analogue-to-digital converter using the XR-2240.

When a strobe pulse is applied, the counter is reset to zero. The time base oscillator is started and the counter begins counting. The eight resistors are connected to the counter outputs and are of values which produce a staircase waveform at the output of the operational amplifier (op amp).

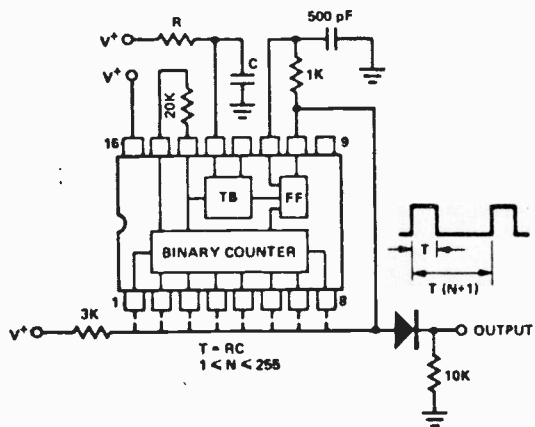


Fig. 4. Frequency synthesis using the internal time base. The frequency is altered by changing the programmed count in the counter

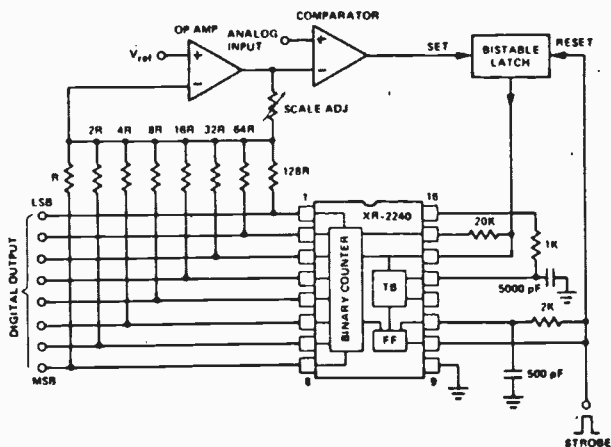


Fig. 5. An eight-bit analogue-to-digital converter using the XR-2240

This ascending staircase is compared with the input voltage by the comparator, and, as soon as the input is exceeded, the bistable latch is set, the count stopped, and the digital equivalent of the input is available at the counter outputs.

OTHER FEATURES


The supply voltage can lie anywhere between 4V and 15V, power dissipation being less than 750mW. All outputs are TTL and DTL compatible.

The device comes in a standard 16-pin dual-in-line package.

The price of the cheapest version of this programmable timer/counter (the XR-2340CP) is £3.90 subject to availability though the XR-2240N which is the same device with a smaller timing error (2% as compared with 5%) is £8.55 (add 14p postage and VAT).

These devices or further data are available from Rastra Electronics, 275-281 King Street, Hammersmith, London W6 9NF.

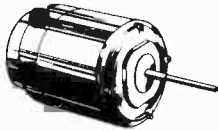"SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR



Type SS15. These fine motors are easily reversed starting and stopping in less than 5° without electrical or mechanical braking. Simple relay circuit.

can be applied to give DC to winding for a maximum holding torque of 300oz in with 35v at 0.35 amps through winding. For AC (synchronous) operation at 120r 50Hz Speed 60 rpm at 60Hz 72 rpm STEPPING Holding torque at 50 steps per second—100 oz in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0.1° per step. Non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions dia 4 body length 4 1/2 spindle length 2 1/2 dia Weight 6 1/2 lbs. BRAND NEW in maker's packing. Offered at less than 1/2 maker's price. OUR PRICE ONLY £15

NORPLEX

Fibre-glass copper-clad laminate. Finest quality epoxy resin base. Heat resistant. Ideal for P.C.B.s. Size 12" x 12" 24" x 12" 24" x 24" FULL SHEET 43" x 37" (11 sq ft.) Single-sided Copper with thickness of 3/64". Also double-sided 3/64" £1 per sq. ft. Cut sizes (1-10 sq ft.) 25p P & P Full Sheet £8 each Carr £1 for 1st sheet plus 25p each additional sheet.

SMITHS RINGER-TIMER



Reliable 15 minute times. Spring wound (concurrent with time setting) 15 x 1min divisions approximately 1/2 between divisions. Panel mounting with chrome bezel 3 1/2" dia. £1.40. 15p P & P.

KNOWLE (U.S.A.) MINIATURE MICROPHONE CAPSULES

Impedance approx. 200Ω output 60 or 80 DB at 1 Kc. As used in deaf aids, bugging device, etc. Size (60 DB) 3/8" x 3/8" x 1/2" (80 DB) 1/2" x 3/8" x 1/2" Ex-equipment, all tested £1.20 each P & P FREE

Ultra PRECISION CENTRIFUGAL BLOWER by Air Control Ltd.



30 segments individually balanced in heavy cast alloy case. 2,300 r.p.m. 240 V a.c. Very powerful and silent running. 5 1/2" dia 3" inlet/dia Outlet/flange 3" x 2 1/2". Limited number only £8.95. P & P 40p.


MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinged elbow. Bracket incorporates 2 fixing screws. Length of arm 2 1/2". 240V AC. Pull at coil is approximately 1lb. £1. FREE P & P. Special quotes for quantities.



SOLENOIDS by WESTOOL

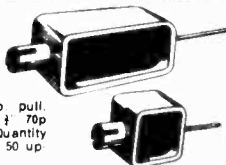240AC type MM6 3lb pull. 2 1/2" x 1 1/2" x 1 1/2" Travel 1" 90p each P & P 10p. 240AC type MM4, 2lb pull. 1 1/2" x 1 1/2" x 1 1/2" Travel 1/2" 70p each P & P 10p. Quantity discounts: 10-50 10% 50 up wards 25%.



OPEN FRAME shaded pole GEARED MOTORS

(Dural gear case) 240 AC, 28rpm NEW HIGH TORQUE, approx. overall size 3 1/2" x 3 1/2" x 2 1/2" spindle 1/2" dia as illustrated. £2.70. P & P 30p. Similar to above 19rpm £2.70. P & P 30p. 110rpm with pressed steel gear case (similar to above but SLIGHTLY SMALLER) £2.70. P & P 30p.




SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!



A magnetically activated switch. vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 5amps at 120v. 1/2amp at 240v. Size (approx.) 1 1/2" long x 1/2" dia. Ideal for burglar alarms, security systems etc. and wherever non-mechanical switching is required. 10 for £2.10; P & P 15p. 50 for £8.100 for £15.50. FREE P & P over 10.

AMPEX 7-5V. D.C. MOTOR

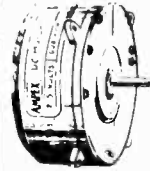

An ultra precision tape motor designed for use in the AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 60ma on run 600rpm = speed adjustment internal AF/RF suppression 1/2" dia x 1 1/2" spindle motor 3/8" dia x 1 1/2". Original cost £16.50. OUR PRICE £3.30. P & P 25p. Quantities available. Mu-metal enclosure available 75p each. FREE P & P.

ALL PRICES INCLUDE V.A.T. Whilst we welcome official orders from established companies and Educational Departments, it is no longer practical to invoice goods under £5. Therefore, please remit cash with orders below this amount.

ELECTRO-TECH COMPONENTS LTD.

315/317, EDGWARE ROAD, LONDON, W2.
Tel: 01-723 5667 01-402 5580

YES, SIR!



... there are over 8,000 electronic components WITHIN A FEW FEET OF YOU!

That is, assuming you are on the telephone.

If you're not, the distance is between you and your nearest post box.

The first thing you need, to enable you to get your components quickly, easily, economically, is a copy of the 240 page Home Radio Components Catalogue. Apart from listing the vast range of lines we stock, it contains details of our popular Credit Account Service and many other items of useful information. For example, as there are several ways of ordering, several ways of paying and several ways of delivery, the pros and cons of all methods are clearly set out in the catalogue. We have the reputation of providing the best-organised

service ever offered to buyers of electronic components. Of course, to make good use of this service you need the catalogue. It costs 55 pence, plus 22p post and packing, and when you receive your copy you'll agree it's the best investment you've made for a long time. Moreover with the catalogue we give you 10 Vouchers each worth 5 pence against orders, an up-to-date price list and a Bookmark with a useful list of technical abbreviations.

Send off the coupon today with cheque or Postal Order for 77p. Your catalogue will come by return post.

Please write your Name and Address in block capitals

Name _____

Address _____

Home Radio (Components) Ltd. Regd No. 812066 London
Dept. PE, 234-240 London Road, Mitcham, CR4 3HD.

The price of 77p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses

Time Gentlemen, Please . . .

As mentioned earlier in this series, the realm of ESP and other difficult-to-explain phenomena is wide and varied. The thinking mind fairly boggles as it tries to find some underlying common factor, to which some, if not all such happenings can be attributed. Alas, there seems little one can find to fill the bill, apart from such descriptions "very odd", "coincidental", or "let's get out out here!"

Let's have a brief look at one or two types of ESP-ery and see what develops. Take the classical example of the dream that comes true, a most eerie experience, if ever you find it happening to you. Often, the content of such dreams is most trivial, though, in the best examples, concerns incidents which the dreamer would not normally have "dreamed of happening".

At this point, whilst our sceptic friends are still with us, I had better assure them that I am fully in support of their views on such subjects as dreams, and that I, too, am highly sceptical of anyone else's experiences, and even my own sometimes. But the strange "coincidences" of dreams is one of the earlier experiences I had which opened my scientifically-motivated mind. So please stay with us, and continue to disbelieve: that is your prerogative . . . until it happens to you . . . more than three times.

If, then, we take the happening of an unlikely event identical in detail to the dreamed event, and we are forced to suppose that the dreamer *did* foresee it in sleep, then there are two possibilities to my way of thinking. Either the dreamer somehow "leaped forward" in time, returning to the "present" a little later, or part of his mind (maybe not his brain?) managed to compress part of his appreciation of time so that he was able to "see" more than he would normally.

Anyone who has used a good oscilloscope will have noticed the effect of using the Expand Trace control. If the trace is compressed, it is possible to see parts of a waveform normally occurring too early in time to be seen on the screen, i.e. normally too far to the left.

Psychometrists

So much for dreams. Time is again the only variable when we consider prediction in waking life. There are some who are good at this, despite the charlatans. Then there are the "psychometrists", people who can handle an inanimate

object and then tell you all about the events in the lives of people who may have owned it over the years. (I have scientifically tested two such people more than once and I am convinced of the validity of their claims; one subject even related the basic content of a lecture recorded on a spool of magnetic tape, without even unwinding it!) Again, then, in psychometry, there seems to be some sort of "time recording". If not, what else?

Some years ago (about 8 years) Benson Herbert, M.Sc., of the Paraphysical Laboratory, Downton, Wilts, used a randomly-flashing electric lamp as a detector to establish whether it was possible to predict correctly how long the interval would be between consecutive flashes. Careful precautions were taken to prevent temperature changes affecting timing, and elaborate measures taken to establish exact timing accuracy, using a multi-channel pen recorder. I saw the resulting traces and success in predicting flash intervals proved to be phenomenally high, and very much higher than chance.



Years Later

Some years later, I watched the same subject (a young lady) sit by the same flashing light to "tell" it (reading instructions of fast or slow from a table composed from a book of random numbers, where odd ones were interpreted as, say, long, and even numbers as short). The lamp, in most instances, obeyed her wish. I watched, fascinated. All wiring was exposed, and there were no tricks: even though those present were genuinely interested

scientifically, we have to ensure there is no room for error, deliberate or otherwise.

It would appear that the subject was able, by thought process, to interfere with normal randomness of the flashing lamp. This phenomenon is called "psycho-kinesis", or PK. My own feelings are that if anything can be changed by thought, then by far the easiest task must surely be interference with the rate of random sequences, since the resulting "bunching" is readily recognised when present, and in the case of the flashing lamp, the influence of moving one flash forward results in the interval following it to be made longer, so increasing the effect twofold.

Incidentally, experiments using the flashing of a geiger counter proved that the cosmically generated events were *not* influenced by any tested subject.

Random Timer

I am embarking on a series of experiments using a specially-designed random event timer, one version of which is described in the article on page 540 in this issue. At the time of writing results are not to hand, but I am already very hopeful, as during development tests the circuit showed surprising tendencies to display "bunching" effect, despite the special precautions. I had taken to ensure no synchronisation between the two timer elements. Careful analysis of figures over hundreds of operations, and of voltages in the circuit, showed no clue to the odd behaviour.

Readers may care to construct a circuit along the lines of the example and see if they get unexpected results (say a run of 7 second intervals) when certain people are asked to concentrate on the flashing lamp or speaker "click".

One way of looking for paranormal effects is to let the timer cycle on for a while unobserved. Then grab a stopwatch and start timing, resetting the watch and logging figures while you concentrate on obtaining high readings. After some ten results, change your concentration to obtaining low reading, for the next ten times. Then add up the seconds for each group and compare the total! The result will surprise or even shock you, if my findings are anything to go by.

Next month . . . preliminary findings on Random PK Timer plus news from other countries

RANDOM TIMER

By Brian Baily

A circuit developed for the phenomena

investigation of psycho-kinesis

THE reason for the development of this circuit is described in the *ESP etc.* feature elsewhere in this issue.

The production of randomly-timed events is not an easy task, and for true randomness to be achieved very much more circuitry than that shown would be required. However, the circuit illustrated serves its purpose to produce fairly random timing when set to run from 2 to 20 seconds. Free-running oscillators were rejected from the selection because of the danger of accidental synchronisation effects, which may upset randomness and could at best result in discrete units of time being introduced, created by the repetition rate of such an oscillator.

CIRCUIT

The block schematic Fig. 1 shows the main blocks of the circuit. A metronome-like circuit drives a speaker to produce a series of clicks. Its timing is determined by a randomising circuit, which is triggered and made to change timing information every time the metronome fires. TR4 is a unijunction transistor which uses the charging of capacitor C3 to produce the intervals between clicks. When C3 charge reaches a certain positive value, TR4 emitter becomes conductive and the capacitor is discharged through the lower base connection of TR4 producing a click in the speaker (Fig. 2).

However, TR1 circuit is not free-running, and C1 may not reach a charge voltage sufficient to fire TR1 in the time that TR2 conducts. But whatever voltage is attained on C1, remains, as there is no leak path for it to drain away, because the f.e.t. (TR3) gate draws virtually no current. However, a certain voltage, proportional to that on C1, but not equal to it, is produced across R3. By this time C3 charge would have fallen almost to zero, but because of the voltage across R3, and because D1 polarity is the way that it is, C3 is allowed to fall only to the level across R3 (less about 0.5V which polarises the diode).

Hence, when C3 charges next time, it has a head start, since it already has R3 voltage across it. So, C3 reaches TR4 firing voltage earlier than before. Next time TR4 fires, the same events occur, and more voltage is applied to C1, which may, this time, reach the firing voltage of TR1 emitter. If this occurs, C1 will discharge completely to 0 volts, but, if TR2 is still conducting when this happens, C1 will begin to charge again until the short conduction of TR2 ceases. Hence, it is most likely, in all

The charging of a capacitor through a resistance is not linear, but is exponential, i.e. for the first part of the charging the voltage across the capacitor increases quite quickly, but as it gets closer to the aiming potential the rate of ascent decreases, and so the voltage stays at nearly the same level for a relatively long time. If we try to alter the timing of TR4/C3 circuit when this exponential law is in operation, most of the effect we shall have will be in the first few seconds and this leaves about half of the time available unchanged, i.e. the part of the charge curve that is nearly horizontal. So it was necessary to change the curve of the C3 charge line by charging C3—instead of through a resistor—through a transistor, TR5, which would supply a constant charging current to C3, so that the voltage on C3 climbs at uniform rate with time. The rate of charge being set by VR1.

When C3 charge reaches the critical voltage for TR4 to conduct, the lower base conducts the charge through the speaker. At the same time, the emitter voltage falls rapidly towards zero volts. This fall discharges C2 with it, via limiting resistor R5, causing the *npn* transistor TR2 to conduct. The conduction is only momentary, as C2 charges quickly due to the base current taken by TR2.

Transistor TR2 forms a variable current source in a charge circuit for C1, which is in a very similar circuit in appearance to the metronome circuit TR4.

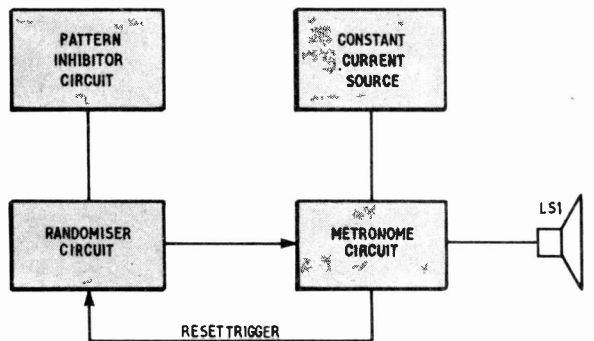


Fig. 1. Block diagram for a random timer

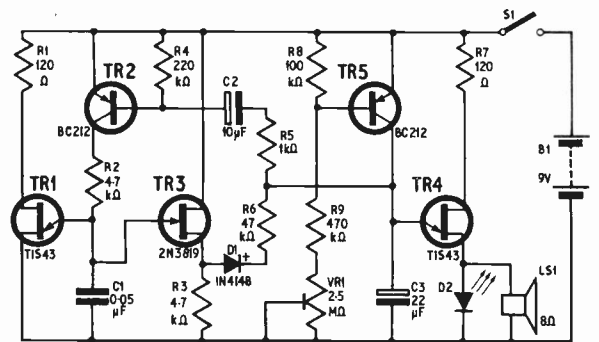


Fig. 2. Suggested circuit for the random timer

events, that C1 will reach a different charge voltage each time TR4 produces a click in the speaker.

PATTERN INHIBITOR

Originally, a diode was used to discharge C2 between pulses, but it was found that when the timer results were examined over a period of many events, a recognisable pattern was discernable. The pattern was often several cycles long or more. So it was decided to introduce a non-linear function into the circuit. This was done by using R4 as the discharge path for C2.

As explained earlier, when TR4 emitter fires and C1 charge falls rapidly, C2 charges by drawing current through TR2 base. But when C3 voltage rises again, during charge, C2 discharges much more slowly through the relatively high resistance of R4. Now, if C3 charges slowly, the discharge of C2 would be completed in the time, but when C3 charges quickly, R4 is too high to allow C2 to completely discharge.

The amount by which C2 has discharged, when next TR4 fires, has a large effect on the duration of TR2's conduction, and therefore on the amount of charge applied to C1. The time-constant of C2 and R4 ensures that, at higher repetition rates a much smaller amount of charge is allowed to be fed to C1 than at lower rates, so introducing a very non-linear function into the system. As you will remember, a capacitor and resistor produce an exponential voltage function. As soon as this small alteration was made to the circuit, the timer showed no further evidence of repetitive pattern "runs", but behaved extremely randomly. For instance, instead of a five-second interval always being followed by (say) a 15-second interval, there was no correlation on any timing.

Current consumption of the circuit was 2mA, making a PP3 battery quite adequate.

SETTING UP

The values in the circuit were those arrived at in the author's particular circuit. Unfortunately, the manufacturers' grading of unijunctions allows a wide spread of characteristics, and there can be no guarantee that these values will apply in other cases, but the circuit itself can be modified here and there to obtain a working result.


Test the circuit by first short-circuiting C1. Then set VR1 carefully until speaker clicks once every 15 or 20 seconds. Next, remove short from C1 and place a voltmeter (10V range) across R3. Note the reading each time speaker clicks, and see that reading varies each time, and does not remain the same for more than two clicks, and if at all, only occasionally. Adjustment of this is effected by value of R4, C2 and R2.

Note, tantalum capacitors were used in the prototype, and these have low leakage levels, so considerable differences would be expected using ordinary electrolytics.

The inclusion of a light-emitting diode, D2, and substitution of an earphone for the speaker make the author's version particularly suitable where it was required to limit the observations to one person. This is because in some experiments it is best for a subject not to know of failures they may have during a prolonged experiment, because of the discouragement factor. ★

THEATRE CUEING LIGHTS

Continued from page 533

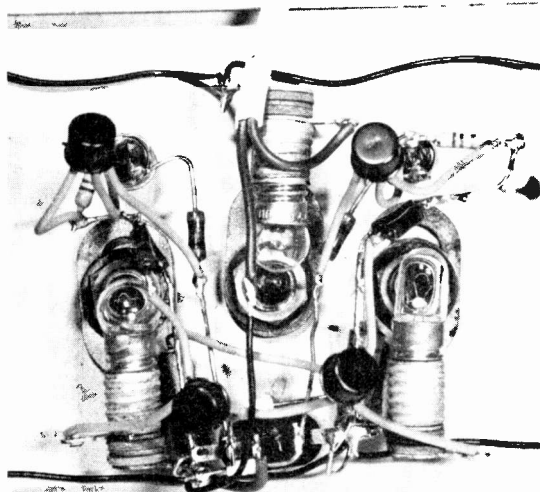

The remote units were built in small aluminium boxes as shown in the photograph. Large lamp-holders were used to make the lights more noticeable.


COMPONENTS

None of the components are particularly critical. The thyristors specified are readily available but 1A 50V types will do. Wire ended types are most convenient.

If different thyristors are used they may need more gate current. This can be produced by reducing R2 (down to 150Ω if necessary). If the thyristors light but fail to stay on increase the value of the smoothing capacitors and decrease R3 (not below 100Ω).

The toggle switches should preferably be miniature types as the normal size make rather a noise when flipped over on metal panels. ★

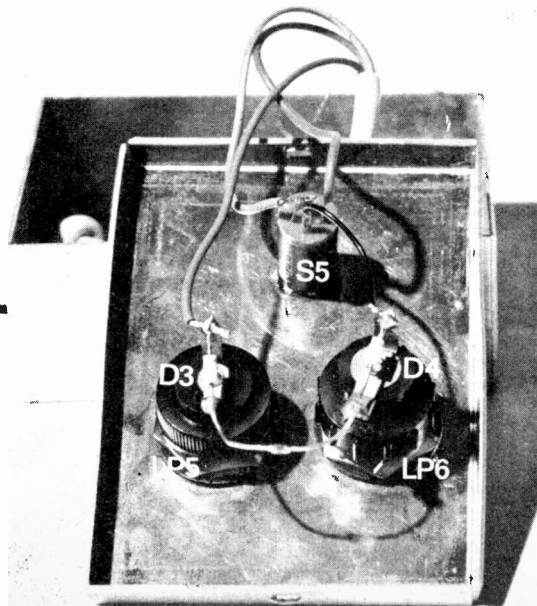Photograph showing the construction of the remote unit. The two diodes are mounted on the lampholders as shown



C'EST SI BON!

The Paris Components Show staged at the beginning of April is one of the dwindling number of giant events which still, apparently, has universal appeal. Britain's IEA (Instruments, Electronics, Automation) show, to be held in late May at Olympia, is a shadow of its former self, suffering from a bout of last-minute cancellations (accompanied by suitably heavy penalty clauses) by a number of leading companies.

Not so at Paris, despite it being just about the most expensive place in the world to exhibit. This year there were the usual 1,000 exhibitors from 25 countries with some 80 UK companies exhibiting.

And the French, themselves, have never had it so good. Well may they be cheeky to Dr. Kissinger, go their own way in oil deals with the Arabs, run their own defence arrangements outside NATO, and lay down the law on the Common Agricultural Policy.


For the French, 1973 was a fine year with 6.5 per cent overall growth which, with only a fairly modest level of inflation, gave everyone a real gain in standard of living. And the biggest success story of all at the Paris Show was the performance of the French electronic components industry.

For the past ten years it has averaged 13.2 per cent growth a year and exports have grown even more steeply so that this year total output will be worth a billion US dollars with 40 per cent of production going for export. An astonishing performance. And the pace shows no sign of slackening. What is stoking the French fire of ambition is the race to beat the Germans into top spot in Europe as an industrial and technological power. Britain was well ahead of France ten years ago. Now the French are abreast.

THE POOR BRITISH

One solid reason why the Germans and French are doing so well is because the incentives are good. In a 1973 salary survey it was revealed that a British company director with a nominal salary of £12,500 would, in fact, receive only £7,000 after tax. His French opposite number would get £14,350 in salary and keep £11,075 net, and his German equivalent would get £20,200 and keep a thumping £13,400, nearly twice that of the British director.

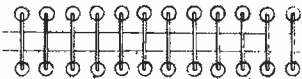In recent months three British managing directors have confessed to me that in setting up sales and service operations on the European mainland they have had to start their European managers on a salary greater than their own, even though the European manager has



INDUSTRY NOTEBOOK

By Nexxa



only a fraction of the staff of the parent company.

AFTERMATH

The three-day week did little damage to the electronics industry. After the return to normal my own personal survey revealed no company admitting to less than 80 per cent of normal production and one company actually achieved 110 per cent—a production gain.

The smaller companies with their greater flexibility did best of all. Dear old Mavis, Flo, Alice and Betty and hundreds more like them stuffed their shopping bags with PCBs and components and carried on assembly work at home. The old concept of a cottage industry was revived. One aspect was enormous loyalty. One manager told me that timekeeping improved at his plant and absenteeism was lower. The "temporary difficulty" made people think more about the value of their jobs. It can hardly be said that the enforced three-day week was good but some good did come out of it.

Best of all was that order intake was not impaired. The fear that overseas customers would start cancelling unfulfilled export orders or cease to place new orders was not realised.

IN THE BALANCE

Hardly a day passes without some new application of electronics. When Ludwig Oertling started manufacturing analytical balances in Britain 127 years ago the steam engine was the big technological achievement of the day and the discovery of Hertzian waves was still 40 years ahead in the future. Oertling is still making fine balances (see the Guinness Book of Records for the world's most accurate balance which measures one tenth of one millionth of a gram) and is making them all the

finer with the addition of electronics.

Latest top-pan Oertling balances have digital outputs for direct electronic read-out from an LED display, recording of weights on a printer, or coded on paper tape for computer analysis. These are not the fragile balances we remember from our days in the school lab but rugged yet sensitive machines for industry and commerce.

The electronic models use a moire fringe optical counting system with a 10-element self-scanning photo-diode array. The subsequent electronics employ over 70 TTL integrated circuits. Heading up Oertling's electronics design team is Rodric Dalitz, a physics graduate from Oxford University.

Oertling's sales director tells me that by the end of this decade he expects sales of electronic read-out balances to be one third of total output. But the fundamental measuring system in Oertling instruments will still be the lever system with built-in weights, a principle dating back 5,000 years which certainly may be said to have stood the test of time.

STRATEGY

Big companies need to plan for the '80s now. That's why Plessey has teamed up with French CIT-Alcatel on development of a new electronic telecommunications system to meet the £500 million market which will start in the late '70s.

The plan is to marry Plessey's System 250 stored program central processor (already developed for the British Ptarmigan military telephone switching network) with CIT's E10 digital switch, now in use on a small scale in France. The combination is a powerful new system which, when refined further, will be an attractive option for not only the British and French Post Offices but for many other countries.

In the UK the Post Office is looking to TXE4 as an interim measure before moving to a fully electronic system for which GEC's Mark 2BL processor is the front runner although still only in the development phase.

Last June GEC and STC agreed to co-operate on the TXE4 and later systems, apparently leaving Plessey out in the cold. What we didn't know then was that Plessey had been talking to CIT long before then and may well have taken the wiser course in refusing the invitation to join STC in a co-operative project. As Sir John Clark, Plessey's Chairman, commented, "We never saw that an association with an American-dominated company (STC is owned by the U.S. ITT) would be a satisfactory solution for the vast majority of European countries".

Is Sir John being a good European or just a good businessman? I suspect he's both.

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD



Telephone Corner

COMPLETE TELEPHONES
NORMAL HOUSEHOLD
TYPE

EX G.P.O. Only **£1-05p** P. & P. 45p each

TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

Only **27 1/2p** POST & PACKING 16p

Tested and Guaranteed Paks



B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV 1 amp. plastic	55p
B81	10	Reed Switches, 1" long 1" dia. Highspeed P.O. type	55p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked	55p
H38	30	Short lead Transistors, NPN Silicon Planar types	55p
H39	6	Integrating circuits 4 gates BMC 962, 2 flip flops BMC 945	55p
H41	2	BD131/BD132 Complementary Plastic Transistors	55p
H45	4	40361 Type NPN Sil. transistors TO-5 can comp. to H66	55p
H66	4	40362. Type PNP Sil. transistors TO-5 can comp. to H65	55p



Unmarked Untested Paks

B1	50	Germanium Transistors PNP, AF and RF	55p
B66	150	Germanium Diodes Min. glass type	55p
B64	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	55p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	55p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	55p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts	55p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can	55p
H67	10	3819N Channel FET's plastic case type.	55p

Make a rev counter for your car

The "TACHO BLOCK". This encapsulated block will turn any 0.1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1-10p each

Ex GPO Push Button Intercom Telephones

Exactly as internal telephone systems still in everyday use where automatic internal exchanges have not yet taken over. Available in 5, 10 or 15 ways. Complete with circuits and instructions. Necessary 24 pair cable 22p per yard. Price of each instrument is independent of the number of ways.

£2.75 p.p. **38 1/2p**

Cable can be sent by Parcel Post. Post and Packing per 50 yds.: 73p. Extension Telephones 71p each, p.p. 27p. £1-37 1/2 for 2, p.p. 55p. These phones are extensions and do not contain bells.

Electronic Transistor Ignition £6-60

Complete Kit incl. V.A.T. P. & P. 11p. Ready built and tested unit £9-90 incl. V.A.T. Now in kit form, we offer this "up-to-the-minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features. Transistor and conventional switchability, burglar proof lock-up and automatic alarm, negative and positive compatibility.

New X Hatch

Our new vastly improved Mark Two Cross Hatch Generator is now available.

Featuring plug-in ICs and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's tool box—and only measures 3in X 5 1/2in X 3in. We have already received a large order from a major TV Rental company.

Ready built **£10-92** Complete **£8-72**
Kit
(includes V.A.T. & P. & P. but no batteries)

Over 1,000,000 Transistors in stock

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very keen prices. Please send for free catalogue.

Our very popular 4p Transistors

TYPE "A" PNP Silicon Alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.
TYPE "G" NPN Silicon, similar ZTX300 range.
TYPE "H" PNP Silicon, similar ZTX500 range.

8 RELAYS FOR £1-10p PNP 271p.

High Speed Magnetic Counter

4 digit (non-reset)
24V or 48V (state which)
4x1x1 in. 33p, p.p. 5p.



Plastic Power Transistors NOW IN TWO RANGES



These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shockingly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1	VCE Min.	15	HFE Min.	15
40 watt	22p	20p	18p	18p
90 watt	261p	241p	22p	22p
Range 2	VCE Min.	40	HFE Min.	40
40 watt	1-12	13-25	26-50	26-50
90 watt	33p	31p	29p	29p
	381p	361p	33p	33p

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

LM380 AUDIO I.C. as featured in Practical Wireless December issue. Complete with application data, £1-10.

INTEGRATED CIRCUITS. We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available. This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights, etc. Pocket Size, 15p, Wall Chart, 18p.

LOW COST DUAL IN LINE I.C. SOCKETS
14 pin type at 16p each } Now new low
16 pin type at 18p each } profile type

BOOKS

We have a large selection of Reference and Technical Books in stock, details are in our latest catalogue, send for it TODAY using the coupon below.

N.B.—Books are void of V.A.T.

Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors and Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of Diodes and Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

11p P. & P. on this Pak.
Please ask for Pak P.1. only **55p**

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME.....
ADDRESS.....

ALL PRICES INCLUDE 10% V.A.T.
MINIMUM ORDER 55p. CASH WITH ORDER PLEASE. Add 11p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE.


BUY THESE GOODS WITH ACCESS

BI-PRE-PAK LTD

Co Reg. No 820919


Dept. A. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.
TELEPHONE: SOUTHEND (0702) 46344.

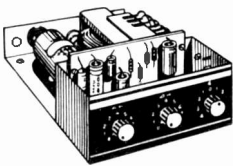PRICES INCLUDE VAT SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier, brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13W r.m.s. into 8 ohm. Frequency response 12Hz-30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3in high x 6in wide x 7 1/2in deep. A.C. 200/250V. P. & P. £12.00. P. & P. 50p.

DE LUXE STEREO AMPLIFIER

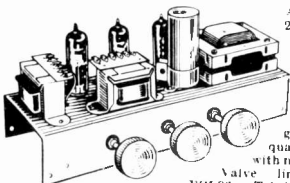

A.C. mains 200-240 volts. Using heavy duty fully wave rectifier with mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up:—2 ECL86 Triode Pentodes. 1-EZ80 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11in. w x 4in. d. Overall height including valves 5in. Ready built and tested to a high standard. P. & P. £50p.

NEW! POWER SUPPLY UNIT

200/240V A.C. input. Four switched fully smoothed D.C. outputs giving 6V and 7 1/2V and 9V and 12V at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case, overall size 6" x 3 1/2" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers, etc., etc. Ready built and tested. P. & P. £5.35p.

HI-GRADE COPPER LAMINATE BOARDS. 8" x 6". Five for 60p plus 30p P. & P.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 12 alternatives. Primary: 0-210-240V. Secondary combinations: 0-5-10-15-20-25-30-35-40-60V. Full wave at 1 amp or 10-10-10, 20-2-20, 30-3-30. At 2 amp full wave. Size 3in. x 3 1/2in. w x 3in. d. Price £2.10. P. & P. 40p

MAINS TRANSFORMER. For transistor power supplies. Fr. 200/240V Sec. 9-9-9 at 500mA. £1.10 P. & P. 25p. Pri. 200/240V Sec. 12-0-12 at 1 amp. £1.21 P. & P. 25p. Pri. 200/240V Sec. 10-0-10 at 2 amp. £1.82 P. & P. 35p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER. For P.U. Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9-18V. Battery or from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/4" x 1 1/4". Brand new — complete with instructions. Price £1. P. & P. 15p.

3 REFERENCE ENCYCLOPEDIAS FOR ELECTRONIC ENGINEERS AND DESIGNERS, covering between them, transistor characteristics, diode and transistor equivalents. Many thousands of up-to-date European types listed. Diode Equivalents 90p. Transistor Equivalents 90p. Transistor Characteristics £1.20. All three together £2.60. POST FREE

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A., European and Japanese transistors. ONLY 40p. Post 5p.

NEW 1981E—Thyristor, Triac, Diac, etc. encyclopedias 95p Post Free.

8 pole 3 way 2 bank low loss Walex type switches 1 1/2" sections. Standard spindle. 2 switches 60p + 10p P. & P.

Open 9.30-5.30 Mon. to Fri.
9.30-5 Sat. Closed Wed.

A few minutes from South Wimbledon Tube Station.

FOR PERSONAL CALLERS ONLY! Limited number of Stereo Radiogram chassis covering LW/MW/PM bands. Mono radio and stereo gram. Overall size approx. 16 1/2" W, 6 1/2" H, 8 1/4" D. 4 Watts per channel output. ONLY £16-50.

SPECIAL BARGAIN OFFER!

Limited number of BSR C123 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge. Brand new. ONLY £28.00 plus P. & P. 60p.

PRECISION ENGINEERED PLINTHS

Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 5100, SP25 II and III, SL65B, AT60, etc., or H.S.R. C123, C109, C129, A21, etc. Black leatherette finish. Size 12 1/2in x 14 1/2in x 3 1/2in high (approx. 7 1/2in high, including rigid smoked acrylic cover). P. & P. 70p. Now only £4-95

FEW ONLY. High grade mains transformers with grain orientated lamination. Primary 200/240 secondary 18.5 volts at 0.6 amps and 4.6 volts at 0.3 amps. Size 2 1/2" x 2 1/2" W. x 2" D overall. £1.25 plus 25p P. & P.

LATEST ACOS GP91/LSC Mono Compatible Cartridge with 1/6 stylus for LP/EP/78. Universal mounting bracket. £1.50. P. & P. 15p.

SONOTONE 9TABC COMPATIBLE STEREO CARTRIDGE T/O stylus. Diamond Stereo LP and Sapphire 78. ONLY £2-30. P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2-90. P. & P. 15p.

LATEST RONETTE T/O Stereo Compatible Cartridge for EP/LP/Stereo/78. £1-65. P. & P. 15p.

LATEST RONETTE T/O Mono Compatible Cartridge for EP/LP/78 mono/stereo records on mono equipment £1-50. P. & P. 10p.

QUALITY RECORD PLAYER AMPLIFIER MK II A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84 and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7 1/2in. w x 3 1/2in. d. h. Ready built and tested. PRICE £5-00. P. & P. 50p. ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £6-30. P. & P. 60p.

SPECIAL OFFER!! HI-FI LOUSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tegan vinyl front. Size 16in high x 10 1/2in wide x 9in deep. Fitted with E.M.I. Ceramic Magnet 13in x 8in bass unit, two H.F. tweeter units and crossover. Max. power handling 10W. Available 3, 8 or 15 ohm impedance.

Our Price £9-25

CARR. 75p. CABINET AVAIL. SEPARATELY £4-95. Carr. 65p. Also available in 8 ohm with EMI 13in x 8in. bass speaker with parasitic tweeter. £7-15. Carr. 75p.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7 1/2in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New, completely wired and tested with good quality output transformer.

OUR ROCK BOTTOM BARGAIN PRICE £3-85 P. & P. 40p

LOUDSPEAKER BARGAINS

3in 3 ohm £1-25. P. & P. 15p. 7 x 4in 3 ohm £1-40. P. & P. 20p. 10 x 6in 3 or 15 ohm £2-10. P. & P. 30p. E.M.I. 8 x 5in 3 ohm with high flux magnet £1-70. P. & P. 20p. E.M.I. 13 x 8in with high flux ceramic magnet with parasitic tweeter 3, 8, or 15 ohm £2-50. P. & P. 30p. E.M.I. 13 x 8in. 3, 8 or 15 ohm. Two built tweeters and crossover network £4-65. P. & P. 30p.

EMI CERAMIC MAGNET HEAVY DUTY TWEETER. approx. 3 1/2in. Av. 3 or 8 or 15 ohms. £1-25 plus 20p P. & P. BRAND NEW. 12in 15W H/D Speakers, 3, 8 or 15 ohm. (state which). Current production by well-known British maker. Now with Hilux ceramic ferrobar magnet assembly £9-90. Guitar models: 25w £9-90. 35w £11-00. P. & P. 45p each.



SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUSPEAKERS. With large ceramic magnet and plasticised cone surround. 8 ohm impedance. £3-70. P. & P. 35p.

Also available specification as above but size 10" x 6" £2-70 P. & P. 35p.

12in "RA" TWIN CONE LOUSPEAKER 10 watts peak handling, 3 or 8 or 15 ohm (state which). £2-95. P. & P. 36p.


"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2in x 14 1/2in x 1 1/2in deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £6-55 each. P. & P. 34p.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexiform ear-muffs. Wired and fitted with standard stereo jn jack plug. Frequency response 30-16,000Hz. Matching impedance 8-16 ohms. Easily converted for mono. PRICE £3-30. P. & P. 25p.

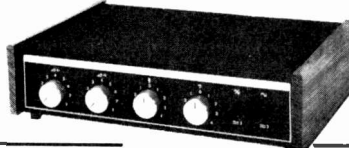HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND IMPROVED HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EASIER CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel venting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. (Very simple to modify to suit magnetic cartridge—instructions included). Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including chassis. High quality ready drilled metal work, high quality ready drilled printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 14W r.m.s. per channel into 8 ohms. Frequency response \pm 3dB 12-30,000Hz. Sensitivity better than 80mV into 1M Ω . Full power bandwidth \pm 3dB 12-15,000Hz. Bass boost approx. to +12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35V at 1.0 amp. Overall size—12" wide x 8" deep x 2 1/2" high.

Fully detailed 7-page construction manual and parts list free with kit or send 18p plus large S.A.E.

PRICES AMPLIFIER KIT. £11-55 P. & P. 25p. (Magnetic input components 33p extra) POWER PACK KIT. £3-50 P. & P. 35p. CABINET. £3-50 P. & P. 35p. (Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested, £25-10. Post Free.

Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.

3-VALVE AUDIO AMP. HA34 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2in. w x 4in. d. x 4 1/2in. h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 44 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £20-00. P. & P. 45p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £5-00. P. & P. 45p.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line up 2 EL24s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 15p plus S.A.E. (Free with parts). All parts sold separately. ONLY £9-00. P. & P. 60p. Also available ready built and tested £13-00. P. & P. 70p.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Our price £1-10 yd. length. P. & P. 16p per yd. (min. 1 yd.). S.A.E. for samples.

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

HARVERSON SURPLUS CO. LTD.

Dept. PE, 170 High St., Merton, London, S.W. 19 Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

PATENTS REVIEW...□ □ □

NOISE MAKING CIRCUIT

Audible alarms for battery operated clocks and film cameras must provide loud sounds at low voltages (often in the order of 1 or 1½V). Feedback circuits using silicon devices have been tried, but there is a crippling loss of drive voltage for the transducer.

In BP 1 333 644 P. R. Mallory & Co Inc of Indianapolis, USA, describes a sound producing piezo-electric transducer of novel construction incorporated in a feedback circuit.

Fig. 1 shows a part of the transducer in section. The piezo-electric crystal is bonded to the substrate and the electrodes T1 and T3 are isolated from the crystal; electrode T2 is mounted on the substrate. The crystal can be a lead, zirconium or titanium composite.

Electrodes T1 and T2 provide the drive for the transducer and T3 provides feedback.

In the circuit of Fig. 2 the amplifying transistors TR1 and TR2 are biased by resistors R1, R2 and R3. Transistor TR2 is connected to electrodes T1 and T2 with the collector of TR1 connected to the

base of TR2. The emitter of TR1 is connected to the emitter of TR2 to provide a common emitter amplifier.

The feedback electrode T3 is connected to the base of TR1 and by selecting the correct polarity at T1 and T2 (which depends on the initial polarisation direction of the crystal) for connection to the collector and emitter of TR2 the feedback voltage at T3 can be put in phase and oscillations created. These will be maintained at the resonant frequency of the transducer.

It is claimed that under such circumstances substantial noise is produced with low supply voltage.

recording the distance travelled by a moving object along a predetermined path. This may be on a large scale, as for instance a train moving along a track, or on a small scale; a scientific instrument moving along a programmed route. Whatever the scale of the operation, spurious revolutions, e.g. due to slippage, make it impossible to achieve this accurately simply by counting the revolutions on a wheel.

What the Japanese propose is that a coaxial cable be modified

DISTANCE MEASURING

The Japanese National Railways and Sumitomo Electric Industries Ltd., jointly describe in BP 1 337 088 an extremely clever new use for coaxial cable.

The object of the exercise is to produce a means for accurately

BP 1 337 088


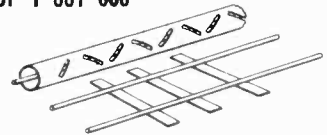


Fig. 1

to deliberately produce field leaks along its length, see Fig. 1. This they do by cutting slots through the outer coaxial conductor at regular intervals along its length. The slots are so angled, one with respect to the next, as to produce alternately reverse polarised magnetic fields from a current flowing along the cable central conductor.

A leaky coaxial cable of this type is laid along the route to be followed and the central conductor fed with a current having a wavelength longer than the interval between adjacent slits. The moving object is provided with an on-board aerial which couples with the alternating magnetic fields which occur at the discrete points of the leaks and digital counters are used to tot up the number of successive field occurrences encountered during travel.

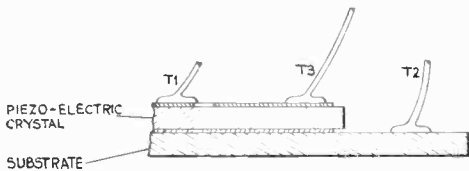The distance travelled is detected by counting the occurrences of the field and the speed of the moving object by measuring the ratio between the travelling distance and time.



BP 1 333 644

Fig. 1

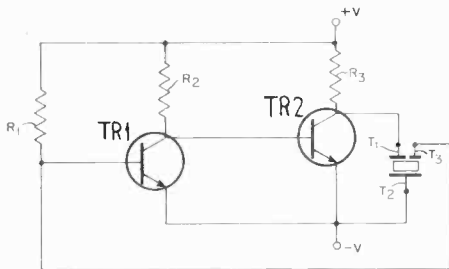


Fig. 2

Readout —

A SELECTION FROM OUR POSTBAG

Scorpio Transformer

Sir,—Recently I experienced some difficulty in obtaining the recommended ferrite cups for the transformer core. Rather than wait delivery I wound the transformer on a line output transformer core from a scrapped T.V. set. This works perfectly well and the only disadvantage I found was that the finished transformer is larger than the recommended one.

First I cut away the old windings, then dismantled the clamping assembly until I was left with the bare core which was in two pieces, C-shaped and I-shaped.

Using stiff card to protect the wire from the sharp square edges, I wound the h.t. secondary (400 turns) directly onto the C-core. The primary windings (12T + 12T) were wound onto the I-core and the feedback windings over these p.v.c. insulating tapes was used as insulation between layers of windings.

With the transformer that I used the original core-clamps were impractical but it was a simple job to fabricate alternatives.

D. Gennard,
Rotherham,
York.

P.E. Synthesiser

Sir,—Having added this above project to my other synthesiser, and having spent some time building your circuit, I feel I must point out

some difficulties encountered which may be of some use to other readers:

1. Excessive noise on output of ring modulator.
2. C3 on sample-hold/noise generator board too low to trigger IC2; I used 0.01 μ F suffix.
3. TR1 on sample-hold/noise board shown as *pnp*, this should be *pnp*.
4. Tone-control — the following modifications had to be made, due to non-operation of circuit as shown. R1 made 120k Ω . Junction of R2/R4 taken to 0V instead of -15V line as shown.
5. D5 on keyboard envelope shaper has not been valued. This should be 11V.
6. Keyboard hold, mod amps and mixer circuit—IC3 is shown with R68 to pin 3. The non invert input of IC3 and C1 to pin 2, these leads should be reversed for sample/hold function, otherwise circuit will oscillate.
7. Keyboard hold—although when setting up VR4/VR5 out of circuit, the hold time is fair, when actually connected to keyboard contacts the leakage which can be experienced from contacts to keyboard frame is enough to upset the hold circuit. I suggest a gate be interposed between C1 and R66-62, this is normally open but closes when gated from keyboard -ve busbar.



Mr. Campbell's synthesiser

My two main criticisms are the difficulty experienced in setting up the sine-shaper of the log oscillators and the lack of a good voltage controlled low pass filter. Otherwise a brilliant piece of design work especially on keyboard and log v.c.o.s.

N. Campbell,
Liverpool.

ELECTRONICS FOR SCHOOL TEACHERS

The University of Essex are holding their third Electronics Summer School for teachers on July 8-12.

Further details may be obtained from Mr. R. J. Mack, Department of Electrical Engineering Science, University of Essex, Wivenhoe Park, Colchester CO4 3SQ, phone Colchester 44144, Ext. 2408 (or 2299).

BACK NUMBERS WANTED

Anyone who can supply the undermentioned are asked to communicate directly with the reader.

January 1968

Mr. J. Rendall, 59 Hood Avenue, Southgate, London, N14 4QJ.

September, October 1973

Mr. J. Pearson, Saxelby Farm, Hebden, Nr. Skipton, Yorks.

October, November 1973

Mr. D. A. Brown, 114 Telford Way, High Wycombe, Bucks.

January, February 1973

Mr. B. Saunders, 18 Fitzroy Avenue, Ebbw Vale, Monmouthshire, NP3 5LN.

June to September 1973

Mr. C. R. Bygrave, Dept. of Communication, University of Keele, Staffordshire.

August 1973

Mr. C. Terrier, Lydford P.O., St. Ann, Jamaica, W.I.

February 1972

Mr. A. Holt, "Fairlands", Hutton Village, Guisborough, Yorkshire.

March 1973

Mr. A. B. Allen, 139 Serpentine Road, Newtown-abbey, Co. Antrim, N.I.

March and July 1973

Mr. J. Huntley, 77 Emolweni Road, Kloof, Natal, South Africa.

March 1973

Mr. A. A. Birch, 2 The Cottages, Yanwath, Penrith, Cumberland.

May, June 1971

Dr. C. Clews, 93 Oakfield Road, Cannon Hill, Birmingham, B12 9PY.

January, February 1973

Mr. H. N. Firth, 72 Victoria Street, Stromness, Orkney.

We regret that back numbers of Practical Electronics can no longer be supplied. We will try to publish announcements of readers' requirements (without a guaranteed date) free of charge.

February to December 1973

Mr. P. Rex, 277 Bennett Street, Long Eaton, NG10 4HZ.

February and November 1969, August 1971 and November 1973

Mr. R. W. Blunn, 16 Shenstone Avenue, Halesowen, Worcs. B62 8QA.

September to November 1971

Mr. M. Edwards, 6 Park Street, Bare, Morecambe, Lancs.

June to December 1968

Mr. A. G. Smith, 70 Heaton Road, Lostock, Bolton, BL6 4EF.

April 1973

Mr. I. McLintock, 93 Campsie Gardens, Clarkston, Glasgow.

March, April 1973

Mr. M. A. G. Bartlett, 55 Marston Close, Damory Down Estate, Blandford, Dorset.

ARRAW'S FASTEST SERVICE!



A SELECTION FROM OUR COMPREHENSIVE CATALOGUE

ALL ITEMS ARE BRAND NEW AND FULLY GUARANTEED

AA119	4p	BFX25	32p	JRC20	44p	TBA810S	£1 58	2N4058	15p
AC107	50p	BFX84	25p	IRT84	£2-24p	TIL112	£2 00	2N4060	13p
AC126	20p	BFX85	34p	JA424	£2-08	TIL209	30p	2N4081	13p
AC127	25p	BFX86	25p	MC1303L	£1-75	TIP31A	60p	2N4082	13p
AC128	24p	BFX87	30p	MC1305P	£2-80	TIP32A	70p	2N4441	70p
AC128 AC176	44p	BFX88	24p	MC1307P	£1-85	TIP41A	85p	2N4444	£2 20
AC151	20p	BFY50	22p	MC1310P	£2-80	TIP42A	£1 00	2N4871	44p
AC152	25p	BFY51	18p	MC1322P	80p	TR43	30p	2N4900	66p
AC153	28p	BFY52	20p	MC1352P	£2-00	TR1	20p	2N4991	46p
AC176	20p	BFY53	17p	MC1466L	£4 20	VA1033P	15p	2N5247	45p
AC183 176K	53p	BFY90	£1 20	MC1468L	£2 48	VA1040	15p	2N5457 (MPF103)	47p
AC187K	17p	BPX66	£1 30	MC4024P	£2 20	VA1066A	15p	2N5458 (MPF104)	49p
AC188K	23p	BR100	20p	MC4044P	£2 20	VA1077	15p	2N5459 (MPF105)	49p
AC187188K	46p	BRX38	45p	MFC-0008	65p	W055	25p	2N5756	24p
ACY17	27p	BSX19	20p	MFC6330	£1 43	W07	28p	2N5777	45p
ACY18	20p	BSX20	19p	MFC6040	£1 15	W07	28p	2N5827 (D1371)	45p
ACY19	20p	BSX21	20p	MFC62010	£1 38	W04	27p	3M84	£1 30
ACY20	20p	BSY27	20p	MFC8040	£1 24	W06	32p	3N129	73p
ACY21	19p	BSY29	25p	MFC9020	£2-12	W08	47p	3N140	82p
ACY22	10p	BSY95A	15p	MJE3371	£1 80	TX107	25p	3N152	82p
AD140	80p	BY779-400R	£1 20	MJE520	85p	TX108	11p	741 T05	45p
AD149	80p	BT106	£1 20	MJE521	62p	TX300	13p	741 801L	34p
AD181	44p	BY100	£1 30p	MJE2985	£1 88	TX302	18p	723 T05	£1 02
AD182	44p	BY127	22p	MJE3055	68p	TX303	15p	723 14DIL	£1 02
AD181 162	84p	BZ788C3V3	10p	MJ480	97p	TX304	23p	747 14DIL	£1 40
AF106	44p	BZ788C3V81	10p	MJ481	£1 25	TX314	11p	747 40DIL	38p
AF114	27p	BZ788C3V9	10p	MJ491	£1 35	TX320	30p	3015F	£1 40
AF115	27p	BZ788C4V3	10p	MJ802	£4-12	TX330	18p	3015G	£2 00
AF116	25p	BZ788C4V1	10p	MJ802 MJ4502	£1 50	TX340	15p	7474	24p
AF117	25p	BZ788C5V1	10p	MJ801	£1 80	TX501	18p	7474	24p
AF118	44p	BZ788C5V6	10p	MJ1000	£1 50	TX502	18p	7474	24p
AF124	25p	BZ788C6V2	10p	MJ1000	£1 44	TX503	18p	7474	24p
AF125	25p	BZ788C6V8	10p	MLM309K	£1 90	TX504	45p	7474	24p
AF126	24p	BZ788C7V5	10p	MPF 102	37p	N914	4p	7405	30p
AF139	46p	BZ788C8V2	10p	MPF 103 (2N5457)	48p	1N3754	20p	7408	30p
AF186	46p	BZ788C9V1	10p	MPF 104 (2N5458)	48p	N4001	4p	7409	30p
AF239	52p	BZ788C10V	10p	MPF 105 (2N5459)	48p	N4002	4p	7410	24p
AF279	52p	BZ788C11V	10p	NE555	78p	N4003	3p	7413	38p
ASV26	25p	BZ788C12V	10p	NKT1033	£1 04	N4004	7p	7422	24p
ASV27	30p	BZ788C13V	10p	NKT211	25p	N4005	7p	7425	38p
ASV28	23p	BZ788C15V	10p	NKT212	25p	N4006	8p	7430	24p
ASV29	30p	BZ788C16V	10p	NKT213	10p	N4007	8p	7440	25p
BA138	15p	BZ788C18V	10p	NKT216	48p	N4148	4p	7442	£1 39
BB103	30p	BZ788C20V	10p	NKT217	50p	N5400	14p	7443	£1 74
BB104	34p	BZ788C22V	10p	NKT218	25p	N5404	25p	7444	£2 47
BB105	28p	BZ788C24V	10p	NKT223	27p	N5408	25p	7445	£1 74
BC107	18p	BZ788C27V	10p	NKT271	16p	S44	16p	7447	£1 50
BC107 BC177	18p	BZ788C30V	10p	NKT274	18p	S900	8p	7450	24p
BC108	18p	BZ788C32V	28p	NKT275	20p	S940	8p	7451	24p
BC108 BC178	32p	BZ788C35V	28p	NKT279A	12p	N4004	23p	7452	24p
BC109	18p	BZ788C37V	28p	NKT281	18p	N696	5p	7453	24p
BC109 BC179	38p	BZ788C40V	28p	NKT351	75p	N697	17p	7454	24p
BC190	18p	BZ788C42V	28p	NKT401	78p	N698	30p	7460	24p
BC117	18p	BZ788C44V	28p	NKT402	80p	N705	12p	7462	38p
BC140	30p	BZ788C46V	28p	NKT403	71p	N706A	12p	7472	38p
BC147	12p	BZ788C48V	28p	NKT404	60p	N7078	18p	7473	54p
BC148	12p	BZ788C50V	28p	NKT405	67p	N9111	67p	7474	54p
BC149	12p	BZ788C52V	28p	NKT406	69p	N9114	40p	7475	54p
BC157	13p	BZ788C54V	28p	NMC409	£1 00	N9118	22p	7476	54p
BC158	12p	BZ788C56V	28p	NMC459	£1 00	N929	48p	7480	54p
BC159	13p	BZ788C58V	28p	NMC505	£3 00	N930	28p	7482	£1 04
BC147-157	25p	BZ788C62V	28p	NTGD10	40p	N1131	20p	7483	£1 58
BC148-158	25p	BZ788C64V	28p	NTGD10	40p	N1132	20p	7486	80p
BC149-159	25p	BZ788C66V	28p	OA7	8p	N1302	17p	7490	84p
BC167	11p	BZ788C68V	28p	OA79	8p	N1303	17p	7491A	£1 54
BC168	11p	BZ788C70V	28p	OA79	8p	N1304	17p	7492	£1 92
BC169	11p	BZ788C72V	28p	OA91	5p	N1305	24p	7493	90p
BC169C	12p	CA3004	£2-03	OA95	5p	N1306	30p	7494	£1 38
BC177	20p	CA3005	£2 35	OA200	80p	N1307	30p	7495	90p
BC178	18p	CA3011	£1 47	OC22	7p	N1308	34p	7496	£1 78
BC179	20p	CA3013	£1 17	OC25	45p	N1309	34p	74100	£1 97
BC182	14p	CA3014	£1 37	OC28	78p	N1310	17p	74107	£1 82
BC182L	14p	CA3018	72p	OC29	79p	N1613	15p	74121	51p
BC183	13p	CA3018A	83p	OC35	88p	N1711	15p	74141	£1 20
BC183L	14p	CA3020	£1 38	OC36	68p	N1893	43p	74150	£4 02
BC184	17p	CA3028A	79p	OC41	40p	N2218	33p	74151	£1 32
BC184L	18p	CA3035	£1 37	OC42	40p	N2218A	44p	74153	£1 82
BC212	18p	CA3043	£1 37	OC44	20p	N2219	30p	74154	£2 40
BC212L	18p	CA3044	£1 28	OC45	20p	N2219A	53p	74155	£1 88
BC238	10p	CA3046	70p	OC71	20p	N2238	17p	74156	£1 88
BC238 308	20p	CA3048	£2 11	OC72	20p	N2638	17p	74180	£2 18
BC257	11p	CA3052	£1 82	OC75	25p	N2369A	17p	74191	£2 18
BC258	10p	CA3053	47p	OC76	25p	N2484	43p	74192	£2 09
BC259	15p	CA3065	£1 28	OC77	40p	N2646	65p	74193	£2 08
BC307	12p	CA3088E	£1 24	OC81	20p	N2904	44p	74196	£1 80
BC308	10p	CA3089E	£1 94	OC82D	20p	N2904A	44p	74197	£1 80
BC309	10p	CA3090Q	£4 23	OC83	23p	N2905	65p	40265	86p
BC31	46p	CA3123E	£1 80	OC84	25p	N2905A	75p	40309	80p
BC32	58p	CD4000AE	55p	OC139	25p	N2924	18p	40310	80p
BC33	20p	CD4001AE	55p	OC170	25p	N2925	20p	40311	82p
BC34	25p	CD4007AE	55p	OC171	30p	N2926	10p	40312	82p
BC35	30p	CD4009AE	55p	OC171M	42p	N3053	24p	40320	82p
BC36	15p	CD4011AE	55p	ORP12	58p	N3054	85p	40360	58p
BC370	15p	CD4012AE	55p	ORP60	58p	N3055	85p	40361	45p
BC371	28p	CD4013AE	£1 11	ORP61	50p	N3228	£1 10	40362	45p
BC372	14p	CD4015AE	£1 82	ORP69	56p	N3391A	28p	40406	52p
BD124	40p	CD4017AE	£1 82	PM7A2	£1 85	N3525	£1 04	40407	40p
BD131	40p	CD4018AE	£2 82	PM7A6	£2 30	N3702	14p	40408	84p
BD132	40p	CD4020AE	£3 15	PN17	£3 15	N3703	12p	40409	84p
BD131 132	40p	CD4024AE	£1 09	PN71	10p	N3704	12p	40410	82p
BD20	91p	CD4027AE	£2 73	PN107	10p	N3705	12p	40410	82p
BF115	35p	CD4029AE	£3 15	PN108	10p	N3706	12p	40410	82p
BF163	35p	CD4049AE	£3 15	PN109	8p	N3707	12p	40511	£1 92
BF167	25p	CR1 051C	54p	PN3819 (2N3819)	20p	N3708	12p	40575	£1 54
BF173	25p	CR1 401C	71p	SL43A	58p	N3709	15p	40576	£1 48
BF177	25p	CR3 05AF	£1 09	SL403A (Rectifier)	60p	N3711	12p	40600	70p
BF178	25p	CR3 05AF	£1 33	SL803A	80p	N3711	12p	40601	70p
BF180	15p	DI0	£1 33	TAD100	£2 17p	TX712	£2 17p	40602	70p
BF194	15p	DI0 (NTGD10)	40p	TAA263	£1 12	N3819	28p	40603	70p
BF195	15p	HP5082	29p	TAA293	97p	N3820	80p	40659	£1 00
BF196	15p	HT841 33	£3 15	TAA320	£1 12	N3821E	52p	40673	£1 50
BF200	35p	HT841 33	£2 24	TAA320	75p	N3826	28p	40739	£1 50
BF254	14p	HT861 33	£2 24	TAA861	45p	N3866	£1 10		
BF255	14p	HT861 33	£1 17	TAD100	£1 17	N3904	28p		
BFX13	25p	RT210	85p	TAD110	£1 87	N3906	28p		

CAPACITORS—ELECTROLYTIC AXIAL LEADS

Mfd	Working Voltage	Price	Mfd	Working Voltage	Price
1 0	40V	11p	100	16V	10p
1 0	100V	9p	100	25V	10p
2 2	25V	11p	100	40V	11p
2 2	63V	9p	100	63V	14p
4 7	40V	9p	220	25V	12p
10	25V	9p	220	40V	13p
10	63V	9p	470	25V	15p
20	25V	10p	1000	25V	23p
46	20V	10p	2200	25V	43p
47	25V	10p	4700	16V	59p
47	40V	10p			

CAPACITORS—METALLISED POLYESTER

Stock values MFD	Price each
0 01 0 015 0 022 0 033	4p
0 047 0 068 0 10	5p
0 150 0 220	6p
0 33	8p
0 47	9p
0 68	12p

SCORPIO Mk2 ignition system kit new from ELECTRO SPARES

- * 6 OR 12 VOLT
- * + VE AND - VE GROUND

Here's the new, improved version of the original Scorpio Electronic Ignition System – with a big plus over all the other kits – the Electro Spares Kit is designed for *both* positive and negative ground automotive electrical systems. Not just +ve ground. Nor just –ve ground. But both! So if you change cars, you can be almost certain that you can change over your Scorpio Mk. 2 as well.

Containing all the components you need, this Electro Spares Scorpio Mk. 2 Kit is simply built, using our easy-to-follow instructions. Each component is a branded unit by a reputable manufacturer and carries the manufacturer's guarantee. Ready drilled for fast assembly. Quickly fitted to any car or motor cycle.

When your Scorpio Mk. 2 is installed, you instantly benefit from all these Scorpio Mk. 2 advantages:

- ★ Easier starting from cold
- ★ Firing even with wet or oiled-up plugs
- ★ Smoother running at high speed
- ★ Fuel saving
- ★ More power from your engine
- ★ Longer spark plug life
- ★ No more contact-breaker burn.

Electro Spares prices:

De luxe Kit only £11.50 inc. VAT and p & p.
Ready Made Unit £14.75 inc. VAT and p & p.
State 6V or 12V system.

Send SAE now for details and free list.

FM VARICAP STEREO TUNER

As featured in the May 1973 issue of 'Practical Electronics'. Superb Hi-Fi tuner Kit now available from Electro Spares. Including cabinet and all components – pre-set Mullard modules for R.F. and I.F. circuits. Motorola i.C. Phase Lock Loop Decoder for perfect stereo reception. No alignment needed. Guaranteed first time results – or send it back, and we'll return it in perfect order (for a nominal handling charge). Electro Spares price only £28.50 inc. VAT and p & p.

'GEMINI' STEREO AMPLIFIER

A superb unit with a guaranteed output of 30 watts RMS per channel into 8 ohms. Full power THD is a mere 0.02%, and frequency response is –3 dB from 20 Hz to 100 kHz into 8 or 15 ohms. Electro Spares have already sold 100s and 100s of these Kits. Get yours now! Depending on your choice of certain components, the price can vary from £50 to £60 inc. VAT and p & p.

- ★ All components as specified by original authors, and sold separately if you wish.
- ★ Full constructional data book with specification graphs, fault finding guides, etc. 55p plus 4p postage.
- ★ Price List only. Please send S.A.E. (preferably 9 x 4 minimum) for full details.

ELECTRO SPARES



The Component Centre of the North
288 ECCLESALL RD., SHEFFIELD S11 8PE (D)
Tel: Sheffield (0742) 668888

FOR
QUALITY
COMPONENTS

MOTOROLA

F. M. Multiplex Stereo Decoder	MC1310P	2.93
Four Channel SQ Decoder	MC1312P	1.75
O/P Power Transistor	2N3055	0.65

SIGNETICS

I/C Timer	NE555V	0.80
Dual I/C Timer	NE556A	1.40
High Phased Locked Loop	NE560B	4.20
High Phased Locked Loop with AM Demod	NE561B	4.20
High Phased Locked Loop with Open VCO	NE562B	4.20
Precision Phased Locked Loop	NE565A	2.90
Function Generator	NE566V	1.55
Tone Decoder	NE567V	2.90

G.I.

Eight Digit Calculator Chip	C500	11.00
Eight Digit Calculator Chip	C550	9.50
3½ Decade DVM Chip	AY-5-3510	6.40

MONSANTO

(MAN3M) 0.115" LED Seven Segment Display	Q2501	1.10
--	-------	------

FERRANTI

Radio Receiver	ZN414	1.20
----------------	-------	------

Data information supplied with each device.

Write for free catalogue of our large stocks of Ferranti, Motorola, G.I., Monsanto, Mullard, Signetics and R.C.A. components.
Add 20p Postage and Packing + 10% V.A.T. on total of order

S.C.S.
P.O. Box No 26,
(Dept PE)
Wembley,
Middlesex HA0 1SD,
England



AUDIOTRONIC Model ATM1

Top value 1,000 opv pocket multi-meter. Ranges: 0/10/50/250/1,000 volt AC and DC. DC current 0.1mA/100mA. Resistance: 0/150k ohms. Decibals: -10 to +32dB. Size 90 x 60 x 28mm. Complete with test leads.



OUR PRICE £2.95 P&P 15p

AUDIOTRONIC Model ATM5

Jewel movement, attractively moulded case with edgewise ohms adjustment. Ranges: 0.3/1.5/15/300/1200V AC. (2500 opv). 0.6/3/30/600V DC. (5000 opv). 0.300 uA/0.300mA DC. Resistance: x 10 & x 100. -10 to +16dB. Supplied with battery test leads and data booklet. Size: 121 x 73 x 29mm.



OUR PRICE £3.50 P&P 15p

MODEL C1929 MULTIMETER

Features 5,000 opv jewel movement and a good section of range functions. Edgewise ohms adjustment. Ranges: 0.3/1.5/15/300/1,200V AC. (2,500 opv). 0.6/3/30/600V DC. (5,000 opv). DC current: 0.300mA/300mA. Resistance: R x 10, R x 1,000. -10 to +16dB. Complete with battery, test leads and data booklet. Size: 120 x 73 x 28mm.



OUR PRICE £3.75 P&P 35p

MODEL TH12

20,000 opv. Overload protection. Slide switch selector. 0/0.25/2.5/10/50/150/1000V DC. 0/10/50/250/1000V AC. 0/50uA/25/250mA DC. 0/3k/30k/300k/3 Megohms. -20 to +50dB.



OUR PRICE £5.95 P&P 15p

HIKOKI Model 720X VOM

A versatile, accurate measuring instrument. 20,000 opv. 0/5/25/100/500/1000V DC. 0/10/50/250/1000V AC. 0.50uA/50uA/0.5mA/5mA/50mA/500mA. 0.20k/2k/20k/200k/2M/20 Megohms. -20 to +81.5dB.



OUR PRICE £5.97 P&P 20p

MODEL PL436


20,000 opv DC. 8000 opv AC. Mirror scale. 6/3/12/30/120/600V DC. 0/30/120/600V AC. 60/600uA/80/600mA. 10/100k/1 Meg/10 Meg Ohm. -20 to 46dB.



OUR PRICE £6.97 P&P 15p

U4323 MULTIMETER

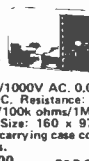20,000 opv. Simple unit with audio AF oscillator. Suitable for general receiver tuning. Ranges: 0.5/2.5/10/50/250/500/1000V DC. 0.05/0.5/5/50/500mA DC. Resistance: 5/50/500 ohms/10/100k ohms/1 Meg. Battery operated. Size: 160 x 97 x 40mm. Supplied in carrying case complete with test leads.



OUR PRICE £7.00 P&P 20p

MODEL HIKOKI 730X


30,000 opv. Overload protection. Ranges: 6.3/30/300/600/1200V DC. 12/60/1200V AC. 60 uA/30mA/300mA. 2K/200k/2 Meg Ohms. -10 to 63dB.



OUR PRICE £7.50 P&P 15p

MODEL TE300

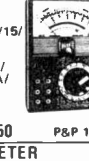30,000 opv. Mirror scale. Overload protection. 0/0.6/3/15/60/300/1200V DC. 0/6/30/120/600/1200V AC. 0/30uA/6mA/60mA/300mA/600mA. 0/8k/80k/800k/8 Meg ohms. -2 Meg Ohms.



OUR PRICE £7.50 P&P 15p

U4324 MULTIMETER

High sensitivity, overload protected. 20,000 opv. Ranges: 0.6/1.2/3/12/30/60/120/600/900V AC. Current: 0.06/0.6/5/50/500mA/3A DC. Resistance: 0.3/30/300mA/3A AC. Resistance: 25/250 ohms/0.5/5/50/500k ohms/5 Megohms. Decibals: -10 to +12dB. Size 167 x 98 x 63mm. Supplied complete with test leads, spare diode and instructions.



OUR PRICE £8.00 P&P 20p

TAK Model TW50K

46 ranges, mirror scale. 50kV DC. DC Volt: 0.125/0.25/1.25/2.5/5/10/25/50/100/500/1000 AC Volts. 1.5/15/100/250/125/250/500/1000 DC current. 0.06/0.6/5/50/500mA/3A DC. Resistance: 25/250/500/1000. DC current: 25/50uA/2.5/25/50/250/500mA/15/10A. Resistance: 10k/100k/1 Meg/10 Meg ohms. -20 to +81.5dB.



OUR PRICE £8.50 P&P 17p

U435 MULTIMETER

20,000 opv. Overload protected. Ranges: 75mV/2.5/10/25/100/250/500/1000V DC. 2.5/10/25/100/250/500/1000V AC. Current: 50uA/15/25/100mA/0.5/2.5A DC. 5/25/5A AC. Resistance: 0.3/30/300k ohms. Size: 205 x 110 x 84mm. Supplied complete with leads, crocodile clips and steel carrying case.



OUR PRICE £8.75 P&P 20p

U91 Clamp VOLT AMMETER

For measuring AC voltage and current without breaking circuit. Ranges: 300/600V AC. Current: 10/25/100/250/500mA. Accuracy: 1%. Size 285 x 94 x 36mm. Complete with carrying case, leads and fuses.



OUR PRICE £10.50 P&P 20p

U4312 MULTIMETER

extremely sturdy instrument for general electrical use. 667 opv. 0/0.3/1.5/7.5/30/60/150/300/600/900V DC & 75mV. 0/0.3/1.5/7.5/30/60/150/300/600/900V AC. 0/300uA/1.5/15/150/60/1200V DC. 0/1.5/6/15/60/150/600mA. 1.5/6A AC. 0/200/3k/30k ohms. DC accuracy: 1%. 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions.



OUR PRICE £9.75 P&P 25p

MODEL 500

30,000 opv with overload protection. Mirror scale. 0/0.5/2.5/10/25/100/250/500/1000V DC. 0/2.5/10/25/100/250/500/1000V AC. 0/50uA/15/50/500mA/12A DC. 0/60k/6 Meg/60 megohms.



OUR PRICE £13.95 Carr. paid

HIKOKI 750X VOLT-OHM-MILLIAMMETER

43 ranges: 0-0.3/0.6/1.5/3/6/12/30/60/150/300/600/1200V DC. 0-3/6/15/30/60/120/300/600/1200V AC. Current: 0-30/60uA/15/30/60mA/1.5/3/6mA/12A. Resistance: 0-3/300k/30M ohms. Decibals: -10 to +17dB. Output: 0.2/0.5/1/30/60/120/300V. Accuracy: +/- 3% DC, +/- 4% AC. Sensitivity: 50,000 opv DC, 5,000 opv AC. 4 inch meter. Built in protection. Size: 57 x 102 x 153mm.



OUR PRICE £11.95 P&P 40p

HIKOKI Model 700X


100,000 opv. Overload protection. Mirror scale. 0/3/6/1.2/1.5/3/6/15/30/60/120/300/600/1200V DC. 1.5/3/6/12/30/60/150/300/600/1200V AC. 15/30uA/3/6/30/60/150/300mA/1.5/3/6/12/20k/2M/20M Ohms. -20 to +63dB.



OUR PRICE £14.95 P&P 20p

Model HT100B4 MULTIMETER

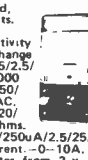Overload protected, shock proof circuit. 9.5uA Meter with mirror scale. Sensitivity 100kV. Polarity change switch. Ranges: 0.5/2.5/1.5/50/250/500/1,000 Volts DC. 2.5/10/50/250/1,000 Volts AC. DC resistance: 0-20/200k/120 Meg. ohms. DC current: -10/250uA/2.5/25/250 mA/10A. AC current: 0-10A. -20 to +62dB. Operates from 2 x 1.5V batteries. Size: 180 x 134 x 79mm.



OUR PRICE £15.00 P&P 40p

MODEL AS.100D VOM


100,000 opv. Mirror scale. Built-in motor. Protection: 0/3/12/60/120/300/600/1200V DC. 0/6/30/120/300/600V AC. 0/10uA/6/60/300mA. 12 Amp. 0/2k 200k/2M/200 Meg Ohm. 20 to 17dB.



OUR PRICE £17.50 P&P 20p

KAMODEN HM720B FET VOM

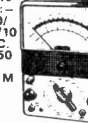Input impedance 10 Megohms. Ranges: 0.25/1.25/10/50/100V DC. 0/2.5/10/50/250/1000V AC. 0/25uA/2.5/25/250 mA DC. 0/5k/50k/500k/5 M 500 Megohms.



OUR PRICE £21.00 P&P 30p

KAMODEN 72.200 Multitester


High sensitivity tester. 200,000 opv. Overload protected. Mirror scale. Ranges: 0/0.6/3/3/30/120/600/1200V DC. 0/3/12/60/300/1200V AC. 0/30uA/600mA/12A DC. 0/12A AC. -20 to +63dB. 0/2k/200k/2 Meg/200 Megohms.



OUR PRICE £22.50 P&P 30p

U4317 MULTIMETER

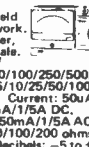High sensitivity instrument for field and laboratory work. Knife edge pointer. 86mm. mirror scale. Ranges: 100mV/0.5/2.5/10/50/100/250/500/1000V DC. 0.5/2.5/10/25/50/100/250/500/1000V AC. Current: 50uA/0.5/1.5/10/50/250mA/1.5A DC. 0.25/0.5/1.5/10/100/200 ohms/1/3/30/300k ohms. Decibals: -5 to +10dB. Battery operated. Size: 210 x 115 x 90mm. Supplied in carrying case complete with leads.



OUR PRICE £15.00 P&P 20p

MODEL U4311 Sub-standard Multi-range Volt-Ammeter

Sensitivity 330 Ohms/Volt AC and DC. Accuracy 0.5% DC. 1% AC. Scale length: 165mm. Ranges: 0/300/750uA/1.5/3/7.5/15/30/75/150/300/750mA/1.5/3/7.5/15/30/75/150/300/750V AC. Automatic cut out device. Supplied complete with test leads, manual and test certificates.



OUR PRICE £49.00 P&P 50p

TE40 HIGH SENSITIVITY AC VOLT METER

10 Meg input. 10 ranges: 0.001/0.03/0.1/0.3/1/3/10/30/100/300V RMS. 5cps-1.2MHz. -40 to +50dB. supplied complete with leads and instructions.



OUR PRICE £17.50 P&P 25p

TE65 VALVE VOLT METER

28 ranges. DC volts 1.5-1500V. AC volts 1.5-1500V. Resistance up to 1000 Megohms. 200/240V AC operation. Complete with probe and instructions.



OUR PRICE £17.50 P&P 30p

LB3 TRANSISTOR TESTER

Tests ICQ and B. PNP/NPN. Operates from 9V battery. Instructions supplied.



OUR PRICE £3.95 P&P 20p

MODEL AF.105 VOM


50,000 opv. Mirror scale. Meter protection. 0/3/12/60/120/300/600/1200V DC. 0/30uA/6/60/300mA/6/60/300mA/12 Amp. 0/10k 1m/10m/100 Meg Ohms. 20 to 17dB.



OUR PRICE £12.50 P&P 20p

LB4 TRANSISTOR TESTER

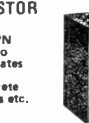Tests PNP or NPN transistors. Audio indication. Operates on two 1.5V batteries. Complete with instructions etc.



OUR PRICE £4.50 P&P 20p

U4341 Multimeter & Transistor Tester

27 ranges. 16,700 opv. Overload protected. Ranges: 0.3/1.5/6/30/60/100/300/600V DC. 1.5/7.5/30/150/300/750V AC. Current: 0.05/0.5/8/60/600mA DC. 0.3/3/30/300mA AC. Resistance: 0.05/0.5/5/50/500k ohms/2 Megohms. Battery operated. Supplied complete with probes, leads and steel carrying case. Size: 115 x 215 x 90mm.

OUR PRICE £10.50 P&P 20p

KAMODEN HMG500 insulation resistance tester

Range 0-1,000 Megohms, 500V. Battery operated. Wide range clear meter 4" x 4". Complete with deluxe carrying case, batteries and instructions.



OUR PRICE £19.95 P&P 30p

S100TR MULTIMETER TRANSISTOR TESTER

100,000 opv. Mirror scale. Overload protection. 0/0.12/0.6/3/12/30/120/600/1200V AC. 0/12/60uA/12/300mA/6/12A DC. 0/10k/1 Meg 100 Meg. -0.1 to +50dB. 0.01-0.2 MF D. Transistor tester measures Alpha, Beta and ICQ. Complete with instructions, batteries and leads.



OUR PRICE £15.95 P&P 25p

C15 PULSE OSCILLOSCOPE

For display of pulsed and periodic waveforms in electronic circuits. VERT. 100V. Bandwidth: 10MHz. Sensitivity at 100kHz VRMS/100mV. 0.1-25; HOR. 10V. Bandwidth: 500kHz. Sensitivity at 100kHz VRMS/1mm. 0.3-25. Preset triggered sweep 1-3000uSec. Free running 20-200 kHz in nine ranges. Calibrator pipe. 350 x 430mm. 115-230V AC.



OUR PRICE £39.00 Carr. paid

RUSSIAN C116 Double Beam OSCILLOSCOPE

5 MHz pass band. Scales x 1 and x 2 amplifiers. Rectangular 5" x 4" CRT. Calibrated triggered sweep from 0.2 to 100 milli-sec/cm. Free running time base, 50Hz-1MHz. Built-in time base. Calibrator and amplitude Calibrator. Supplied complete with all accessories and instruction manual.



OUR PRICE £87.00 Carr. paid

MODEL TE15 GRID DIP METER

Transistorized. Operates as Grid Dip Oscillator. Absorption Wave Meter and Oscillating Detector. Frequency range 40kHz-280MHz in six coils. 500uA meter. 9V battery operation. Size: 180 x 80 x 40mm.



OUR PRICE £19.95 P&P 20p

SWR METER Model SWR3

Handy SWR meter for transmitter antenna alignment, with built-in field strength meter. Accuracy 5%. Impedance 50 Ohm. Indicator 100uA DC. Full scale 5 section collapsible antenna. Size 145 x 60 x 60mm.



OUR PRICE £4.25 P&P 25p

AT201 Decade ATTENUATOR

Frequency range 0-200kHz. Attenuator 0-111dB. 0.1dB strength meter. 600 ohms. Input power maximum 300mW. Size: 180 x 90 x 56mm.



OUR PRICE £12.50 P&P 37p

Also see following pages

ALL PRICES EXCLUDE VAT

LIST

Also see previous page

TRANSISTORISED L.C.R. A.C. BR/8 MEASURING BRIDGE

A new portable bridge offering excellent range and accuracy at low cost. Resistance 6 ranges. 0.1 ohm-11.1 megohm. ± 1% Inductance. 6 ranges: 1 microhenry-111 henries ± 2%. Capacity: 6 ranges: 10pF-1110 mfd ± 2%. Turns Ratio: 6 ranges: 1:1/1000-1/11000 ± 1%. Bridge Voltage at 1.000cps. Operated from 9-volt battery. 100 microamp meter indication. Size 7 1/4" x 5" x 2".

OUR PRICE £25.00 P&P 25p

TE16A TRANSISTORISED SIGNAL GENERATOR

5 ranges, 400kHz to 30 MHz. An inexpensive instrument for the handy-man. Operates on 9V battery. Wide easy to read scale. 800kHz modulation. Accuracy ± 2%. Audio output to 8V. Power requirements: 105-125V, 220-240V AC. Size: 193 x 265 x 150mm. Complete with instructions and leads.

OUR PRICE £8.97 P&P 25p

MODEL TE20 RF SIGNAL GENERATOR

Six bands, 120kHz-80MHz. Dual output RF terminals. Separate variable audio output. Output to 8V. Power requirements: 105-125V, 220-240V AC. Size: 193 x 265 x 150mm. Complete with test leads etc.

OUR PRICE £17.50 P&P 40p

TE-200 RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kHz-500 kHz on 6 bands. Directly calibrated. Variable R.F. attenuator audio output. Xtal socket for calibration 220/240V a.c. Brand new with instructions. Size 140mm x 215mm x 170mm.

OUR PRICE £17.50 P&P 30p

ARF 300 AF/RF SIGNAL GENERATOR

All transistorised compact fully portable. AF sine wave 18Hz to 220 kHz. AF square wave 18Hz to 100kHz. Output Squares/ Sine wave 10V P-P RF 100kHz. Output 1V maximum. 220/240V AC operation. Complete with instructions and leads.

OUR PRICE £29.95 P&P 50p

MODEL MG100 SINE SQUARE WAVE AUDIO GENERATOR

Range 19-220,000Hz. Sine Wave 19-100,000Hz. Square Wave Output. Sine or Square wave 10V p.p. Size 180 x 90 x 90mm. Operation 220/240V. A.C.

OUR PRICE £19.95 P&P 37p

MCA220 Automatic Voltage Stabiliser

Input 180-125V AC or 175-250V AC. Output 120V AC or 240V AC. 200V/A rating. P&P 50p.

OUR PRICE £11.97

PS100B Regulated POWER SUPPLY UNIT

Solid state. Output 6, 9 or 12V DC up to 3 Amp. Meter to monitor current. Input 220/240V AC. Size: 100 x 82 x 159mm.

OUR PRICE £11.97 P&P 25p

PS200 Regulated POWER SUPPLY UNIT

Solid state. Variable output 5-20V DC up to 2 Amp. Independent meters to monitor voltage and current. Output 220/240V AC. Size: 190 x 136 x 98mm.

OUR PRICE £19.95 P&P 25p

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole for 1/8" diameter shafts. Bulk quantities available.

25 WATT 10/25/50/100/250/500/1000/2500 Ohms £1.15 P&P 10p

50 WATT 10/25/50/100/250/500/1000/2500/5000 Ohms. £1.62 P&P 10p

100 WATT 1/5/10/25/50/100/250/500/1000/2500 Ohms. £2.34 P&P 15p

AUTO TRANSFORMERS

0/1/15/250V. Step up or step down. Fully shrouded.

80 WATTS £2.75 P&P 18p

150 WATTS £3.50 P&P 18p

300 WATTS £4.50 P&P 23p

500 WATTS £6.95 P&P 33p

1000 WATTS £9.50 P&P 38p

1500 WATTS £12.50 P&P 43p

2250 WATTS £20.95 P&P 50p

5000 WATTS £44.95 P&P £1

CP110 CHASSIS PUNCH SET

Carefully machined top grade steel. Contains 1/2", 5/8", 3/4", 1" and 1 1/8" punches complete with gripper and accessories.

OUR PRICE £3.00 P&P 40p

YAMABISHI VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. Input. 220V 50/60Hz. Output 0-250V. MODEL S260 BENCH MOUNTING P&P

1A £10.50 30p

2.5A £12.00 35p

5A £17.50 37p

8A £30.35 50p

10A £33.75 75p

12A £29.50 75p

20A £85.00 125p

25A £95.00 130p

40A £120.00 150p

MODEL S260B PANEL MOUNTING P&P

1A £10.00 30p

2.5A £12.00 35p

240° Wide Angle 1mA METERS

MW 1-6 60x60mm

£6.50 P&P 15p

MW 1-8 80x80mm

£6.90 P&P 15p

BV05 Vernier TUNING DIAL

App. 7:1 ratio planetary drive vernier dial. Log scale 0-180 degrees. Blank scales 1-5. Dial size 128 x 76mm. Overall size 190 x 117 x 41mm. Deep including knob and coupling. 1/8" diam. shaft

OUR PRICE £1.62 P&P 15p

WALKIE TALKIES

SKYFON 100mW
OUR PRICE £24.95 per pair
P302 Two Channel 300mW
OUR PRICE £52.50 per pair
P1003 Three Channel 1 Watt
OUR PRICE £71.25 per pair
P&P 50p per pair
NB. Licence required for use in UK

RUH6 Reflex Horn Speaker

Built in driver unit. Impedance 16 ohms. Power rating 10W. Response 380-7000Hz. Size approx 6" x 6". Weather and shock protected.

OUR PRICE £4.97 P&P 30p

TRIO 9R590S RECEIVER

Four bands covering 550kHz to 30 MHz continuous and electrical bandspread on 10, 15, 20, 40, and 80 mtrs. 8 valve plus 7 diode circuit. 4 to 8 ohm output and phone jack. SSB-CW, ANL, variable BFO, S Meter and separate band spread dial. IF frequency 445kHz. audio output 1Watt. Variable RF and AF gain controls. 115/250V AC, with instructions.

OUR PRICE £42.50 CARR. FAID

BELTEK W5400 CAR TRANSCEIVER

Solid state mobile transceiver for 12 volt DC neg. Transmits and receives on any 12 of 28 channels between 144 and 146MHz. Power output 10W and 1W switchable. Controls: On/off volume, squelch and channel select or. Internal 3" speaker. Complete with dynamic mic. PTT switch, three sets of crystals for 144.48, 144.6 and 145MHz, mounting bracket and instructions. Size: 150 x 70 x 220mm.

OUR PRICE £75.00 P&P 50p

HITACHI FLUORESCENT LANTERN L191

A portable battery operated lantern ideal for home, motoring, camping etc. Approx 10" tall. Provides brilliant light from 9 1 1/2 batteries (not supplied).

OUR PRICE £7.90 P&P 25p

DT55G DIGITAL CLOCK MECHANISM

24 hour alarm setting, on/off and auto alarm 'sleep' switch. Illuminated rotary dial with hours, minutes and seconds. Automatically turns off radio, TV, light etc. and with auto-switching will turn on again when required. 240V AC operation. Switch rating 250V-3 Amp.

OUR PRICE £5.95 P&P 30p

KE630 3 Station INTERCOM

Master and two substations. Can be used on desk or wall mounted. Complete with cable and batteries

OUR PRICE £5.25 P&P 50p

LH02S STEREO HEADPHONES

Light weight head, phones with padded ear pieces, 4/16 ohms 20-20,000Hz. Complete with 6' lead and plug.

OUR PRICE £1.97 P&P 30p

TE1018 Deluxe Mono High Impedance Headset.

Sensitive magnetic headset with soft ear pads. Impedance 2,600 ohms (600 ohms DC). Frequency response: 200-4,000Hz.

OUR PRICE £2.25 P&P 30p

OH02S STEREO HEADPHONES

Wonderful value and excellent performance combined. Adjustable head band. Impedance 8 ohms. 20-12,000Hz. Complete with lead and plug.

OUR PRICE £2.50 P&P 30p

TE1035 Stereo HEADPHONES

Low cost with excellent response. Foam rubber earcups. Adjustable headband. 8 ohms impedance. Frequency response 25Hz-18kHz. Complete with cable and stereo jack plug.

OUR PRICE £2.60 P&P 30p

SH8DV MONO/STEREO HEADPHONES

Volume control for each channel, 4/16 ohms impedance. Frequency response 20Hz-18kHz. Complete with 10ft. coiled lead and jack plug.

OUR PRICE £4.97 P&P 30p

BH001 HEADSET and Boom Microphone

Moving coil. Ideal for language teaching, communi-cations etc. Headphone impedance 16 ohms. Microphone impedance 250 ohms.

OUR PRICE £5.95 P&P 30p

EMI LOUOSPEAKERS

Model 350 13 x 8" with single tweeter/crossover. 20-20,000Hz. 15 watts RMS. Available 8 or 15 ohms.

OUR PRICE £7.50 each P&P 37p

Model 450 13 x 8" with twin tweeter/crossover. 55-13,000Hz. 8 watts RMS. Available 8 or 15 ohms

OUR PRICE £3.62 each P&P 25p

SPECIAL PURCHASE LIMITED QUANTITY! Tannoy 12" DR/8 Bass Speakers

8 ohms 30 watt Heavy duty ideal for Hi Fi P A Group
OUR PRICE £12.50 P&P 50p

HIGH QUALITY CONSTRUCTION KITS

WE ARE APPOINTED STOCKISTS AT ALL BRANCHES

All kits are complete with comprehensive easy to follow instructions and covered by full guarantee.

Post and Packing 15p per kit.

AF20 Mono amplifier.....	£4.80
AF25 Mixer.....	£3.60
AF30 Mono pre-amplifier.....	£2.61
AF35 Emitter amplifier.....	£2.27
AF80 0.5W mc. amplifier.....	£4.22
AF305 Intercom.....	£9.52
AF310 Mono amplifier.....	£5.91
AT5 Automatic light control.....	£2.58
AT25 Window wiper robot.....	£5.82
AT30 Photo cell switch unit.....	£5.0
AT50 400W triac light dimmer/speed control.....	£4.80
AT56 2,200W triac light dimmer/speed control.....	£6.90
AT60 1 channel light control.....	£7.80
AT65 3 channel light control.....	£14.55
GP304 Circuit board.....	£4.94
GP310 Stereo pre-amplifier for use with 2 x AF310.....	£21.27
GP312 Circuit board.....	£11.45
GU330 Tremolo unit.....	£7.50
HF61 Diode detector.....	£3.32
HF65 FM transmitter.....	£2.70
HF68 FM tuner.....	£2.87
HF310 FM tuner.....	£15.81
HF325 Deluxe FM tuner.....	£24.12
HF330 Decoder (HF310/325).....	£9.96
HF380 (w/with) aerial amplifier.....	£4.94
HF395 broadband aerial amp.....	£1.77
LF380 Quadrasonic device.....	£11.36
M160 Multi-Vibrator.....	£1.71
M191 V Filter.....	£4.55
M192 Stereo balance meter.....	£4.97
M130 Transistor tester.....	£8.45
NT10 Stabilised power supply 100mA 5V.....	£6.15
NT300 Stabilised p. supply.....	£12.51
NT305 Voltage converter.....	£4.50
NT315 Power supply 240V AC to 4.5/15V DC, 500mA.....	£9.57

Amateur Electronics by Josty-Kit, the professional book for the amateur

covers the subject from basic principles to advanced electronic techniques. Complete with circuit board for AE1 to AE10.

OUR PRICE £3.30 (No VAT) P&P 25p plus VAT.

AE1 100mW output stage.....	£1.50
AE2 Pre-amplifier.....	£1.15
AE3 Diode receiver.....	£1.82
AE4 Filter.....	99p
AE5 Astable multi-vibrator.....	96p
AE6 Monostable multi-vibrator.....	93p
AE7 RC generator.....	97p
AE8 Pulse Filter.....	90p
AE9 Treble filter.....	90p
AE10 CCIR filter.....	90p

SPECIAL BARGAIN!! STEREOSOUND SPEAKERS!

Matched pair of stereo bookshelf speakers. Deluxe vinyl veneered finish. Size: 368 x 229 x 190mm. 8 ohms. 8 watts RMS. 16 watts peak. Complete with Din lead.

OUR PRICE £12.95 P&P 50p

SPECIAL BARGAIN! FERGUSON 3406 HI-FI SPEAKERS

High quality 2 way speaker systems. 25 Watts. 4-8 ohms. 40Hz-18kHz. Size: 560 x 340 x 255mm. approx. Wood grain finish with black fronts.

OUR PRICE £26.95 plus P&P, £1

FM TUNER CHASSIS

6 transistor high quality tuner. Size only 153 x 103 x 63mm. 3 IF stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Covers 88-108MHz. Ready built, ready for use. Fantastic value for money.

OUR PRICE £5.95 P&P 20p

Model A1018 FM TUNER

6 transistor high quality unit. 3 IF stages and double tuned discriminator. For use with most amplifiers. Covers 88-108MHz. Powered by 9V battery.

OUR PRICE £13.50 P&P 30p

Stereo multiplex adapter £5.95 extra.

ALL PRICES EXCLUDE VAT

SEW CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES ETC.

Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

CLEAR PLASTIC MODEL SD640

Size: 85 x 64mm

50uA	£3.80
100uA	£3.75
200uA	£3.70
500uA	£3.65
50.0-500uA	£3.75
100.0-1000uA	£3.70
1mA	£3.65
5mA	£3.65
10mA	£3.65
50mA	£3.65
100mA	£3.65
500mA	£3.65
1A DC	£3.65
5A DC	£3.65
10A DC	£3.65
5V DC	£3.65




10V DC	£3.65
20V DC	£3.65
50V DC	£3.65
300V DC	£3.65
15V AC	£3.75
30V AC	£3.75
VU Meter	£3.90

CLEAR PLASTIC MODEL SV100

Size: 100 x 80mm

50uA	£4.60
100uA	£4.50
500uA	£4.30
50.0-500uA	£4.50
100.0-1000uA	£4.45
1mA	£4.30
5mA	£4.30
10mA	£4.30
5A DC	£4.30
20V DC	£4.30
50V DC	£4.30
300V DC	£4.30

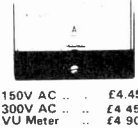

150V AC	£4.45
300V AC	£4.45
VU Meter	£4.90

EDGWISE MODEL PE70

Size: 90 x 34mm

50uA	£4.15
100uA	£4.10
200uA	£4.05
500uA	£3.90
50.0-500uA	£4.10
100.0-1000uA	£4.05
1mA	£3.85
300V AC	£3.95
VU Meter	£4.30



MODEL ED107 EDUCATIONAL METER

Size: 100 x 90 x 150mm including terminals

A range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working.



50uA	£8.50
100uA	£7.90
50.0-500uA	£7.90
1mA	£7.60
1.0-1mA	£7.60
1A DC	£7.60
5A DC	£7.60
5V DC	£7.60
10V DC	£7.60
15V DC	£7.60

20V DC	£7.60
50V DC	£7.60
50.0/5A DC	£7.60
5V/50V DC	£7.60
5V/15V DC	£7.60
1/5A DC	£7.60
1A/15A DC	£7.60

CLEAR PLASTIC MODEL MR 85P

Size: 120 x 110mm

50uA	£5.45
100uA	£5.40
200uA	£5.35
500uA	£5.25
50.0-500uA	£5.40
100.0-1000uA	£5.35
500.0-5000uA	£5.20
1mA	£5.20
1.0-1mA	£5.20
5mA	£5.20
10mA	£5.20
50mA	£5.20
100mA	£5.20
500mA	£5.20
1A DC	£5.20
5A DC	£5.20
15A DC	£5.20
30A DC	£5.20
10V DC	£5.20
20V DC	£5.20
50V DC	£5.20
150V DC	£5.20



300V DC	£5.20
15V AC	£5.30
300V AC	£5.30
S Meter 1mA	£5.20
VU Meter	£5.55
1A AC	£5.20
5A AC	£5.20
10A AC	£5.20
5A AC	£5.20
10A AC	£5.20
20A AC	£5.20
30A AC	£5.20

*Items with asterisk are Moving Iron type, all others are Moving Coil

CLEAR PLASTIC MODEL SD830

Size: 110 x 83mm

50uA	£4.30
100uA	£4.25
200uA	£4.20
500uA	£4.15
50.0-500uA	£4.25
100.0-1000uA	£4.20
1mA	£4.10
5mA	£4.10
10mA	£4.10
50mA	£4.10
100mA	£4.10
500mA	£4.10
1A DC	£4.10
5A DC	£4.10
10A DC	£4.10
5V DC	£4.10



10V DC	£4.10
20V DC	£4.10
50V DC	£4.10
300V DC	£4.10
15V AC	£4.20
30V AC	£4.20
VU Meter	£4.40

CLEAR PLASTIC MODEL MR 45P

Size: 50 x 50mm

50uA	£3.20
100uA	£3.15
200uA	£3.10
500uA	£3.00
50.0-500uA	£3.15
100.0-1000uA	£3.10
500.0-5000uA	£2.95
1mA	£2.95
5mA	£2.95
10mA	£2.95
50mA	£2.95
100mA	£2.95
500mA	£2.95
1A DC	£2.95
5A DC	£2.95
10V DC	£2.95
20V DC	£2.95
50V DC	£2.95
300V DC	£2.95
15V AC	£3.05



300V AC	£3.05
VU Meter	£3.40
1A AC	£2.95
5A AC	£2.95
20V AC	£2.95
50V AC	£2.95
20A AC	£2.95
30A AC	£2.95

CLEAR PLASTIC MODEL MR 38P

Size: 42 x 42mm

50uA	£3.10
100uA	£3.05
200uA	£3.00
500uA	£2.85
50.0-500uA	£3.05
100.0-1000uA	£3.00
500.0-5000uA	£2.80
1mA	£2.80
1.0-1mA	£2.80
2mA	£2.80
5mA	£2.80
10mA	£2.80
20mA	£2.80
50mA	£2.80
100mA	£2.80
150mA	£2.80
200mA	£2.80
300mA	£2.80
500mA	£2.80
750mA	£2.80
1A DC	£2.80
2A DC	£2.80
5A DC	£2.80
10A DC	£2.80
3V DC	£2.80
10V DC	£2.80
15V DC	£2.80



20V DC	£2.80
50V DC	£2.80
100V DC	£2.80
150V DC	£2.80
200V DC	£2.80
300V DC	£2.80
500V DC	£2.80
750V DC	£2.80
15V AC	£2.90
50V AC	£2.90
150V AC	£2.90
300V AC	£2.90
500V AC	£2.90
S Meter 1mA	£2.80
VU Meter	£3.20

CLEAR PLASTIC MODEL SD460

Size: 59 x 46mm

50uA	£3.50
100uA	£3.45
200uA	£3.40
500uA	£3.35
50.0-500uA	£3.45
100.0-1000uA	£3.40
500.0-5000uA	£3.20
1mA	£3.20
5mA	£3.20
10mA	£3.20
50mA	£3.20
100mA	£3.20
500mA	£3.20
1A DC	£3.20
5A DC	£3.20
10A DC	£3.20
5V DC	£3.20



10V DC	£3.30
20V DC	£3.30
50V DC	£3.30
300V DC	£3.30
15V AC	£3.45
30V AC	£3.45
VU Meter	£3.65

POSTAGE & PACKING 15p

CLEAR PLASTIC MODEL MR 65P

Size: 86 x 78mm

50uA	£3.95
100uA	£3.85
200uA	£3.80
500uA	£3.75
50.0-500uA	£3.85
100.0-1000uA	£3.80
500.0-5000uA	£3.70
1mA	£3.70
1.0-1mA	£3.70
5mA	£3.70
10mA	£3.70
50mA	£3.70
100mA	£3.70
500mA	£3.70
1A DC	£3.70
5A DC	£3.70
10A DC	£3.70
15A DC	£3.70
20A DC	£3.70
30A DC	£3.70
50V DC	£3.70
10V DC	£3.70
15V DC	£3.70
20V DC	£3.70
50V DC	£3.70
150V DC	£3.70



300V DC	£3.70
15V AC	£3.80
50V AC	£3.80
150V AC	£3.80
300V AC	£3.80
500V AC	£3.80
S Meter 1mA	£4.10
VU Meter	£3.70
1A AC	£3.70
5A AC	£3.70
10A AC	£3.70
20A AC	£3.70
30A AC	£3.70
50A AC	£3.70
100A AC	£3.70
200A AC	£3.70
500A AC	£3.70

BAKELITE MODEL S80 Enlarged Window

Size: 80 x 80mm

50uA	£4.50
100uA	£4.45
500uA	£4.20
50.0-500uA	£4.45
100.0-1000uA	£4.40
1mA	£4.20
5mA	£4.20
10mA	£4.20
50mA	£4.20
100mA	£4.20
500mA	£4.20
1A DC	£4.20
5A DC	£4.20
10V DC	£4.20
20V DC	£4.20
50V DC	£4.20
300V DC	£4.20
VU Meter	£4.70



S Meter 1mA	£3.30
VU Meter	£3.80
1A AC	£3.30
5A AC	£3.30
10A AC	£3.30
20A AC	£3.30
30A AC	£3.30

CLEAR PLASTIC MODEL MR 52P

Size: 60 x 60mm

50uA	£3.70
100uA	£3.50
500uA	£3.35
50.0-500uA	£3.50
100.0-1000uA	£3.45
1mA	£3.30
5mA	£3.30
10mA	£3.30
50mA	£3.30
100mA	£3.30
500mA	£3.30
1A DC	£3.30
5A DC	£3.30
10V DC	£3.30
20V DC	£3.30
50V DC	£3.30
300V DC	£3.30



S Meter 1mA	£3.30
VU Meter	£3.80
1A AC	£3.30
5A AC	£3.30
10A AC	£3.30
20A AC	£3.30
30A AC	£3.30

BAKELITE MODEL MR 65

Size: 80 x 80mm

25uA	£5.25
50uA	£4.90
100uA	£3.95
500uA	£3.65
50.0-500uA	£3.95
100.0-1000uA	£3.90
500.0-5000uA	£3.60
1mA	£3.60
1.0-1mA	£3.60
5mA	£3.60
10mA	£3.60
50mA	£3.60
100mA	£3.60
500mA	£3.60
1A DC	£3.60
2A DC	£3.60
5A DC	£3.60
10A DC	£3.60
15A DC	£3.60
50V DC	£3.60
10V DC	£3.60
15V DC	£3.60
20V DC	£3.60
50V DC	£3.60
150V DC	£3.60



300V DC	£3.60
15V AC	£3.60
50V AC	£3.60
150V AC	£3.60
300V AC	£3.60
500V AC	£3.60
VU Meter	£4.10
1A AC	£3.60
5A AC	£3.60
10A AC	£3.60
20A AC	£3.60
30A AC	£3.60
50A AC	£3.60
100A AC	£3.60
500A AC	£3.60
50V DC	£3.60
100V DC	£3.75
150V DC	£3.75

SINCLAIR Project 80 Modules

Z40 Power Amplifier	£5.45
Z40 Power Amplifier	£6.95
Stereo 80 Pre-Amplifier	£11.95
Active Filter Unit	£6.95
P23 Power Supply	£26.95
P23 Power Supply	£4.98
P26 Power Supply	£7.98
P28 Power Supply	£7.98
Transformer for P28	£4.05

SINCLAIR Project 80 Packages

2 x Z40/Stereo 80/P25	£27.75
2 x Z40/Stereo 80/P26	£27.75
2 x Z60/Stereo 80/P28	£30.45

POST & PACKING 35p each.

MP7 MIXER-PREAMPLIFIER

5 Microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. Size: 235 x 127 x 76mm. Input: 3 x 3mV 50k; 2 x 3mV 600 ohms. Phono. Mag. 40mV 50k; Phono Ceramic 100mV 1 ohm. Output 250mV 100k.

OUR PRICE £8.97 P&P 20p

1021 Stereo Listening Station

For balancing and gain selection of loudspeakers with additional facility for stereo switching. Two gain controls, speakers on-off side switch, stereo headphone socket.

OUR PRICE £2.

Marshall's

A. Marshall & Son (London) Limited
 42 Cricklewood Broadway London NW2 3HD, Telephone 01-452 0161
 & 65 Bath Street Glasgow G2 2BX, Telephone 041-332 4133

EVERYTHING YOU NEED IN OUR
NEW CATALOGUE
 PRICE 20p
 AVAILABLE
NOW!

Transistors

2G301	0-15	2N3392	0-18	3N187	1-55	8SY29	0-38	8CY72	0-13	8FY11	0-45
2G302	0-15	2N3393	0-18	3N200	2-49	8SY26	0-30	8CY87	0-34	8FY17	0-90
2G303	0-25	2N3394	0-18	3N201	4-12	8AY50	0-15	8CY88	2-42	8FY18	0-35
2G304	0-30	2N3402	0-18	40050	0-78	8C107	0-16	8CY89	0-97	8FY19	0-85
2G309	0-30	2N3403	0-19	40251	0-81	8C108	0-15	8CZ10	0-35	8FY20	0-50
2G341A	0-25	2N3404	0-24	40309	0-30	8C109	0-19	8CZ11	0-50	8FY29	0-40
2G371	0-15	2N3405	0-27	40310	0-50	8C113	0-13	8D115	0-70	8FY37	0-20
2G374	0-15	2N3414	0-11	40313	0-92	8C114	0-12	8D116	0-75	8FY41	0-43
2N174	1-40	2N3415	0-10	40316	0-50	8C115	0-15	8D121	0-70	8FY43	0-15
2N404	0-44	2N3416	0-15	40318	0-92	8C116	0-15	8D123	0-82	8FY60	0-221
2N456	0-75	2N3417	0-21	40360	0-40	8C118A	0-18	8D124	0-67	8FY51	0-181
2N456A	0-75	2N3570	1-25	40361	0-48	8C117	0-21	8D131	0-40	8FY52	0-201
2N457A	0-80	2N3571	1-12	40362	0-50	8C118	0-11	8D132	0-50	8FY53	0-16
2N491	2-58	2N3372	0-97	40363	0-61	8C119	0-29	8D135	0-43	8FY56	0-84
2N696	0-15	2N3702	0-11	40383	0-41	8C121	0-23	8D136	0-49	8FY6A	0-41
2N697	0-15	2N3703	0-12	40393	0-56	8C122	0-36	8D137	0-56	8FY75	0-20
2N698	0-25	2N3704	0-14	40395	0-65	8C126	0-20	8D138	0-63	8FY76	0-22
2N699	0-29	2N3705	0-12	40406	0-44	8C132	0-40	8D139	0-71	8FY77	0-24
2N706	0-16	2N3706	0-09	40407	0-33	8C134	0-11	8D140	0-87	8FY78	0-36
2N706A	0-18	2N3707	0-13	40408	0-50	8C135	0-11	8D141	1-20	8FY90	0-80
2N708	0-14	2N3708	0-70	40409	0-52	8C136	0-15	8D142	1-15	8FY99	0-28
2N709	0-30	2N3710	0-11	40410	0-52	8C137	0-15	8D143	1-50	8BX19	0-13
2N711	0-30	2N3710	0-12	40411	0-25	8C138	0-24	8D148	1-75	8BX20	0-201
2N718	0-21	2N3711	0-11	40414	0-35	8C140	0-34	8D149	1-97	8BX21	0-201
2N718A	0-49	2N3712	0-06	40467	0-69	8C141	0-29	8D150	1-05	8BX26	0-40
2N720	0-50	2N3713	1-20	40468A	0-44	8C142	0-23	8D153	0-65	8BX27	0-34
2N721	0-55	2N3714	1-38	40470	0-69	8C143	0-21	8D159	0-85	8BX28	0-25
2N724	0-22	2N3715	1-54	40481	0-27	8C144	0-25	8D161	1-25	8BX29	0-47
2N916	0-41	2N3716	1-80	40602	0-46	8C145	0-21	8D162	1-00	8BX60	0-54
2N918	0-47	2N3773	2-65	40603	0-58	8C147	0-12	8D165	0-25	8BX61	0-42
2N920	0-30	2N3779	3-15	40604	0-56	8C148	0-13	8D166	0-23	8BX76	0-15
2N929	0-48	2N3790	2-40	40636	1-10	8C149	0-12	8D167	0-43	8BX77	0-20
2N1090	0-30	2N3791	2-35	40673	0-70	8C153	0-18	8D169	0-58	8BX78	0-25
2N1091	0-32	2N3792	2-69	40707	0-85	8C154	0-12	8D171	0-25	8BX79	0-28
2N1132	0-54	2N3794	0-10	40113	0-16	8C157	0-14	8D173	0-27	8BX79	0-28
2N1302	0-181	2N3819	0-27	40117	0-20	8C158	0-13	8D175	0-25	8BY25	0-20
2N1303	0-181	2N3820	0-38	40121	0-13	8C159	0-14	8D176	0-20	8BY26	0-20
2N1304	0-24	2N3823	1-42	40126	0-25	8C160	0-37	8D173	0-21	8BY27	0-15
2N1305	0-24	2N3824	1-33	40127	0-25	8C167 B	0-13	8D174	0-18	8BY28	0-16
2N1306	0-31	2N3826	0-23	40128	0-25	8C168 B	0-13	8D175	0-23	8BY38	0-181
2N1307	0-22	2N3854	0-18	40141 K	0-30	8C169	0-17	8D176	0-27	8BY39	0-181
2N1308	0-25	2N3854A	0-16	40142 K	0-25	8C169 B	0-13	8D170	0-23	8BY51	0-25
2N1309	0-351	2N3855	0-19	40151A	0-14	8C169 C	0-13	8D161	0-41	8BY52	0-25
2N1483	0-90	2N3855A	0-20	40132V	0-17	8C170	0-11	8D163	0-31	8BY53	0-25
2N1507	0-30	2N3856	0-19	40153	0-25	8C171	0-13	8D166	0-31	8BY54	0-30
2N1613	0-33	2N3856A	0-20	40153 K	0-25	8C172	0-11	8D167	0-21	8BY56	0-79
2N1631	0-38	2N3858	0-16	40154	0-30	8C182	0-12	8D173	0-24	8BY63	0-15
2N1638	0-36	2N3858A	0-19	40176	0-18	8C182L	0-12	8D177	0-29	8BY78	0-40
2N1637	0-32	2N3859	0-14	40176 K	0-25	8C183	0-09	8D178	0-35	8BY79	0-40
2N1701	1-19	2N3859A	0-19	40187 K	0-28	8C183L	0-09	8D179	0-43	8BY790	0-45
2N1702	2-15	2N3860	0-10	40188 K	0-34	8C184	0-11	8D180	0-35	8BY95A	0-101
2N1711	0-45	2N3866	1-09	40177	0-351	8C184L	0-11	8D181	0-34	8U104	1-42
2N1893	0-81	2N3877	0-25	40184	0-25	8C185	0-05	8D182	0-40	8U105	2-25
2N2102	0-30	2N3877A	0-36	40184	0-57	8C187	0-07	8D183	0-40	8U111	1-52
2N2147	0-70	2N3900	0-21	40220	0-22	8C207	0-12	8D184	0-30	8D403	0-55
2N2148	0-94	2N3900A	0-21	40221	0-28	8C208	0-11	8D185	0-17	8E111	0-45
2N2192	0-40	2N3901	0-32	40222	0-17	8C212 K	0-10	8D194	0-16	8E113	0-25
2N2192A	0-40	2N3903	0-24	40223	0-20	8C212L	0-16	8D195	0-17	8E114	0-20
2N2913	0-40	2N3904	0-27	40230	0-42	8C214 L	0-21	8D196	0-15	8E115	0-50
2N2193A	0-41	2N3905	0-27	40231	0-51	8C217	0-05	8D197	0-15	8E116	0-50
2N2194	0-73	2N3906	0-27	40234	0-17	8C228	0-09	8D198	0-18	8E120	0-40
2N2194A	0-30	2N4036	0-621	40241	0-17	8C239	0-09	8D199	0-18	8E135	0-20
2N2218A	0-88	2N4037	0-42	40244	0-31	8C251	0-20	8D200	0-40	8E136	0-20
2N2219	0-67	2N4058	0-16	40136V	0-96	8C252	0-16	8D224J	0-14	8E138	0-20
2N2219A	0-88	2N4059	0-09	AD142	0-50	8C253	0-23	8D225J	0-19	8E173	0-12
2N2220	0-45	2N4060	0-11	AD143	0-45	8C257	0-09	8E237	0-22	8E175	0-15
2N2221	0-41	2N4061	0-11	AD149V	0-68	8C258	0-09	8E238	0-22	8E180	0-35
2N2221A	0-83	2N4062	0-11	AD150	0-63	8C259	0-13	8E244	0-16	8E183	0-20
2N2222	0-60	2N4302	0-25	AD161	0-45	8C261	0-20	8E245	0-33	8E187	0-20
2N2222A	0-91	2N4303	0-47	AD162	0-45	8C262	0-18	8E246	0-43	8E189	0-25
2N2368	0-81	2N4916	0-11	AD161	1-1	8C263	0-23	8E247	0-49	8E189	0-25
2N2369	0-87	2N4917	0-17	AD162	1-05	8C300	2-12	8E254	0-16	8E193A	0-49
2N2369A	0-41	2N4918	0-73	AF109B	0-40	8C301	0-34	8E255	0-17	8E193A	0-59
2N2646	0-77	2N4919	0-84	AF114	0-25	8C302	0-49	8E257	0-47	8E193A	0-72
2N2647	1-12	2N4920	0-99	AF115	0-24	8C303	0-54	8E258	0-69	8E193A	0-84
2N2711	0-13	2N4921	0-73	AF116	0-25	8C307	0-10	8E259	0-55	8E193A	1-01
2N2712	0-12	2N4922	0-84	AF117	0-20	8C307A	0-10	8E270	0-21	8E194A	1-51
2N2713	0-17	2N4923	0-83	AF118	0-50	8C308	0-09	8E272	0-53	8E195A	2-90
2N2714	0-18	2N5172	0-12	AF119	0-22	8C308A	0-12	8E273	0-15	8E196A	3-70
2N2904	0-45	2N5174	0-22	AF124	0-24	8C308 B	0-09	8E274	0-17	8E197A	0-79
2N2904A	0-70	2N5175	0-26	AF125	0-20	8C309	0-10	8E457	0-53	8E198A	0-90
2N2905	0-71	2N5176	0-32	AF126	0-19	8C309A	0-10	8E458	0-65	8E199	0-90
2N2905A	0-88	2N5190	0-92	AF127	0-20	8C309B	0-10	8E821A	2-30	8E200	0-18
2N2906	0-65	2N5191	0-95	AF139	0-38	8C327	0-21	8E828	0-22	8E0401	0-10
2N2906A	0-70	2N5192	1-84	AF170	0-25	8C328	0-19	8E861	0-27	8E0402	0-10
2N2907	0-58	2N5193	1-48	AF172	0-25	8C337	0-20	8E866	0-25	8E0403	0-11
2N2907A	0-41	2N5143	0-43	AF178	0-45	8C338	0-22	8E867	0-25	8E0404	0-12
2N2923	0-12	2N5457	0-49	AF179	0-65	8C339	0-43	8E868	0-23	8E0412	0-18
2N2924	0-14	2N5458	0-45	AF180	0-50	8C339A	0-51	8E829	0-30	8E0413	0-14
2N2925	0-17	2N5459	0-49	AF186	0-40	8C332	1-15	8E830	0-25	8E1120	0-25
2N2926		3N128	0-78	AF200	0-35	8C333	0-34	8E837	0-33	8E4001	0-09
Green	0-12	3N138	1-65	AF239	0-51	8C334	0-361	8E844	0-33	8E4002	0-11
Yellow	0-11	3N139	1-42	AF240	0-79	8C335	0-22	8E845	0-25	8E4003	0-11
Orange	0-11	3N140	0-92	AF279	0-54	8C339	1-05	8E868	0-30	8E6101	0-10
0-11	3N141	0-81	AF280	0-54	8C340	0-87	8E884	0-24	8E4102	0-11	
2N3053	0-32	3N142	0-58	AF142	0-74	8C342	0-15	8E885	0-30	8E4103	0-10
2N3054	0-88	3N143	0-75	AL102	0-75	8C343	0-15	8E886	0-25	8E4104	0-11
2N3055	0-75	3N142	0-92	AL103	0-70	8C338	0-21	8E887	0-28	8E4101	0-14
2N3390	0-28	3N153	0-81	8SY36	0-52	8C338	0-22	8E888	0-25	8E4102	0-16
2N3391	0-28	3N154	0-81	8SY37	0-38	8C37					

TRANSFORMERS

SAFETY MAINS ISOLATING TRANSFORMERS
Prim. 120/240V. Sec 120/240V Centre Tapped and Screened

ALSO AVAILABLE WITH 115/120V SEC. WINDING

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P £ p
07	20	1 8	7.0 x 6.0 x 6.0	2.32 30
149	60	3 12	9.9 x 7.7 x 8.6	3.45 36
150	100	5 8	9.9 x 8.9 x 8.6	3.79 52
151	200	8 0	12.1 x 9.3 x 10.2	6.45 52
152	250	13 12	12.1 x 11.8 x 10.2	8.41 67
153	350	15 0	14.0 x 10.8 x 11.8	11.20 82
154	500	19 8	14.0 x 13.4 x 11.8	16.25 *
155	750	29 0	17.2 x 14.0 x 14.0	22.10 *
156	1000	38 0	17.2 x 16.6 x 14.0	29.87 *
158	2000	60 0	21.6 x 15.3 x 18.1	49.25 *

AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P £ p
113	20	1 0	5.8 x 5.1 x 4.5	0-115-210-240	1.22 22
64	75	2 4	7.0 x 6.7 x 6.1	0-115-210-240	2.40 30
4	150	3 4	8.9 x 7.7 x 7.7	0-115-200-220-240	2.89 36
66	300	6 4	9.9 x 9.6 x 8.6	..	5.63 52
67	500	12 8	12.1 x 11.2 x 10.2	..	8.36 67
84	1000	19 8	14.0 x 13.4 x 14.3	..	15.19 82 *
93	1500	30 4	14.0 x 15.9 x 14.3	..	21.99 *
95	2000	32 0	17.2 x 16.6 x 14.0	..	28.70 *
73	3000	40 0	21.6 x 13.4 x 18.1	..	39.17 *

CASED AUTO TRANSFORMERS

115 500W enclosed transformer, with mains lead and two 115V outlet sockets, £9.49, P & P 67p. 20W version, £2.02, P & P 22p.

LOW VOLTAGE SERIES (ISOLATED)

PRIMARY 200-250 VOLTS 12 AND/OR 24 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Windings	P & P £ p
111	0.5	0.25	4.8	0-12V at 0.25A x 2	1.22 22
213	1.0	0.5	6.1	0-12V at 0.5A x 2	1.44 22
71	2	1 12	7.0	0-12V at 1A x 2	1.90 22
18	4	2 2	8.3	0-12V at 2A x 2	2.68 36
70	6	3 3	8.9	0-12V at 3A x 2	3.20 42
108	8	4 5	9.9	0-12V at 4A x 2	3.60 52
72	10	5 6	9.9	0-12V at 5A x 2	4.25 52
116	12	6 12	9.9	0-12V at 5A x 2	5.10 52
17	16	8 8	12.1	0-12V at 8A x 2	6.56 52
115	20	10 11	14.0	0-12V at 10A x 2	8.36 67
187	30	15 15	14.0	0-12V at 15A x 2	15.40 82 *
226	60	30 32	17.2	0-12V at 30A x 2	28.44 *

30 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
112	0.5	1 4	6.1	0-12-15-20-24-30V	1.42 22
79	1.0	2 4	7.0	..	1.92 36
3	2.0	3 4	8.9	..	2.90 36
20	3.0	4 8	9.9	..	3.58 42
21	4.0	6 4	9.9	..	4.25 52
51	5.0	6 12	12.1	..	5.30 52
117	6.0	8 0	12.1	..	6.31 52
88	8.0	12 0	12.1	..	8.18 67
89	10.0	13 12	14.0	..	10.33 67

50 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
102	0.5	1 12	7.0	0-19-25-33-40-50V	1.90 30
103	1.0	2 12	8.3	..	2.80 36
104	2.0	5 8	7.9	..	3.87 42
105	3.0	6 12	9.9	..	5.26 52
106	4.0	10 0	12.1	..	6.99 52
107	6.0	12 0	14.0	..	10.35 67
118	8.0	12 0	14.0	..	13.51 97
119	10.0	25 0	17.2	..	16.95 **

60 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
124	0.5	2 4	7.0	0-24-30-40-48-60V	1.93 36
126	1.0	3 4	7.7	..	2.70 36
127	2.0	6 4	9.9	..	4.25 42
125	3.0	8 12	12.1	..	6.46 52
123	4.0	13 12	12.1	..	8.36 67
40	5.0	12 00	14.0	..	9.85 67
120	6.0	15 8	14.0	..	12.14 82 *
121	8.0	25 00	14.0	..	13.65 *
122	10.0	25 0	17.2	..	20.09 *
189	12.0	29 00	17.2	..	22.49 *

MINIATURE TRANSFORMERS WITH SCREENS

Ref. No.	mA	Weight lb oz	Size cm.	Volts	P & P £ p
238	200	1 2	2.8 x 2.6 x 2.0	3-0-3	1.31 10
212	1A, 1A	1 4	6.1 x 5.8 x 4.8	0-6, 0-6	1.52 22
13	100	1 4	3.9 x 2.6 x 2.9	9-0-9	1.12 10
235	300, 330	4	4.8 x 2.9 x 3.5	0-9, 0-9	1.52 10
207	500, 500	1 00	6.1 x 5.4 x 4.8	0-8-9, 0-8-9	2.03 22
208	1A, 1A	1 12	7.0 x 6.4 x 6.1	0-8-9, 0-8-9	2.73 30
236	200, 200	4	4.8 x 2.9 x 3.5	0-15, 0-15	1.52 10
214	300, 300	1 4	6.1 x 5.8 x 4.8	0-20, 0-20	1.60 22
221	700 (d.c.)	1 8	7.0 x 6.1 x 6.1	20-12.0-12-20	1.41 30
206	1A, 1A	2 12	8.3 x 7.7 x 7.0	0-15-20, 0-15-20	3.08 38
203	500, 500	2 4	8.3 x 7.0 x 7.0	0-15-27, 0-15-27	2.82 38
204	1A, 1A	3 4	8.9 x 7.7 x 7.7	0-15-27, 0-15-27	2.86 38

*Carriage via B.R.S.

PLEASE ADD 10% FOR V.A.T. INCLUDING P. & P.

BARRIE electronics

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS ALDGATE & ALDGATE EAST

TO SPARK YOUR IMAGINATION!

Kit comprises **EVERYTHING:**

Case, cables, coil connectors, Silicon grease, 8-page instruction leaflet.



NEW

the SPARKRITE Mk II

Electronic Ignition Kit only £11.62

Fascinating to build. Fantastic improvement to your car's performance. Complete Capacitive Discharge ignition system, fully proven, components fully guaranteed. Printed circuit design. All metalwork drilled ready. Fitted to car in 15 minutes when built.

- Sustained peak performance.
- Up to 20% fuel saving.
- Instant all-weather starting. Faster acceleration, higher top speed.
- Suitable for all engines up to 8 cyls.
- Longer spark plug life.
- Longer battery life.
- Contact breaker burn eliminated.
- Purer exhaust gas emission.

A new development from the manufacturers of Gunton ignition. Price: £11.62 inc. V.A.T. and postage. (12 volt only, State Pos. or Neg. earth). Ready built unit also available £14.85 inc. V.A.T. and postage. GUARANTEED 5 YEARS.

ORDER NOW To: ELECTRONICS DESIGN ASSOCIATES, 82 Bath Street, Walsall WS1 3DE. Phone: 33652

Please send me one SPARKRITE Kit complete. I enclose P.O./Cheque for £11.62. Or for ready built unit £14.85.

NAME

ADDRESS

(Live near Walsall? Call in for an actual workshop demo. It really is convincing).

PE6

RST

VALVE MAIL ORDER CO.
 16a WELLFIELD ROAD, LONDON SW16 2BS
SPECIAL EXPRESS MAIL ORDER SERVICE
 Express postage 1p per transistor, over ten post free
 INTEGRATED CIRCUITS 5p + 1p each added

Sp	Part	Sp	Part	Sp	Part	Sp	Part
IN21	0-17	AFZ41	1-18	BY213	0-25	OAZ205	0-46
IN23	0-85	AFZ42	0-47	BY210	0-40	OAZ206	0-46
IN85	0-88	AS120	0-20	BY211	0-40	OAZ207	0-46
IN263	0-50	AS127	0-30	BY212	0-40	OAZ208	0-40
IN265	0-50	AS128	0-20	BY213	0-85	OAZ209	0-40
IN645	0-18	AS129	0-20	BY215	1-25	OAZ210	0-40
IN726A	0-80	AS130	0-20	BY216	0-60	OAZ211	0-40
IN914	0-08	AS150	0-20	BY288CV3	0-10	OAZ222	0-46
IN4007	0-10	AS151	0-20	BY288CV3	0-10	OAZ223	0-46
18113	0-25	AS153	0-20	BZY88CV3	0-10	OAZ224	0-46
18131	0-13	AS155	0-20	C111	0-55	OAZ241	0-25
18202	0-23	AS162	0-25	CR81/05	0-60	OAZ242	0-15
20371	0-40	AS168	0-23	CR81/05	0-60	OAZ244	0-25
20381	0-22	ASZ21	1-00	CR81/40	0-45	OAZ246	0-15
20414	0-20	ASZ23	0-75	CS41	1-50	OAZ290	0-88
20417	0-25	AT101	1-50	CS10B	1-50	OC116	1-00
2N404	0-25	AT110	1-00	DD000	0-15	OC18T	1-00
2N697	0-15	BC107	0-12	DD003	0-15	OC19	0-60
2N698	0-30	BC108	0-12	DD006	0-25	OC20	2-00
2N705	0-10	BC109	0-12	DD007	0-40	OC22	1-00
2N708A	0-12	BC113	0-10	DD008	0-25	OC23	1-25
2N708	0-15	BC115	0-20	GD1	0-55	OC24	1-10
2N709	0-09	BC118	0-20	GD4	0-10	OC25	0-40
2N1091	0-55	BC116A	0-25	GD5	0-25	OC26	0-40
2N1131	0-25	BC118	0-20	GD8	0-25	OC28	0-70
2N1132	0-25	BC121	0-20	GD12	0-10	OC29	0-65
2N1302	0-18	BC122	0-20	GET102	0-50	OC30	0-40
2N1303	0-18	BC125	0-08	GET103	0-40	OC35	0-65
2N1304	0-22	BC126	0-08	GET113	0-35	OC36	0-65
2N1305	0-25	BC129	0-25	GET114	0-30	OC41	0-65
2N1306	0-25	BC147	0-12	GET115	0-75	OC42	0-40
2N1307	0-22	BC148	0-10	GET116	0-65	OC43	0-70
2N1308	0-22	BC149	0-12	GET120	0-50	OC44	0-18
2N2147	0-75	BC157	0-14	GET872	0-30	OC44M	0-17
2N2148	0-80	BC158	0-12	GET875	0-50	OC45	0-18
2N2160	1-00	BC160	0-55	GET876	0-65	OC45M	0-18
2N2219	0-25	BC169	0-14	GET881	0-25	OC48	0-27
2N2219	0-25	BCY31	0-45	GET882	0-25	OC57	0-80
2N2369A	0-16	BCY32	1-20	GET886	0-40	OC58	0-60
2N2444	1-99	BCY33	0-25	QEX44	0-08	OC59	0-60
2N2613	0-25	BCY34	0-45	QEX46/1	0-05	OC66	0-80
2N2646	0-50	BCY35	0-55	QEX941	0-45	OC70	0-18
2N2904	0-20	BCY36	1-50	QJ4M	0-50	OC71	0-18
2N2904A	0-25	BCY40	0-80	QJ4M	0-50	OC72	0-25
2N2906	0-20	BCY42	0-80	OJ6M	0-25	OC73	0-50
2N2907	0-22	BCY70	0-15	OJ7M	0-50	OC74	0-80
2N2924	0-18	BCY71	0-20	HO1006	0-50	OC75	0-80
2N2925	0-15	BCZ10	0-60	H8100A	0-20	OC76	0-80
2N2926	0-10	BCZ11	0-65	MAT100	0-20	OC77	0-65
2N3024	0-50	BD121	1-00	MAT101	0-25	OC78	0-25
2N3055	0-60	BD123	1-00	MAT120	0-20	OC79	0-20
2N3702	0-11	BD124	0-80	MAT121	0-25	OC81	0-25
2N3705	0-15	BDY11	1-45	MJE520	0-65	OC81D	0-25
2N3706	0-11	BF115	0-22	MJE2955	1-10	OC81M	0-20
2N3707	0-18	BF117	0-60	MJE3055	0-75	OC81DM	0-18
2N3709	0-20	BF167	0-25	MFF101	0-40	OC81Z	0-45
2N3710	0-11	BF173	0-25	MFF103	0-80	OC82	0-80
2N3711	0-11	BF181	0-85	MFF104	0-85	OC82D	0-25
2N3819	0-85	BF184	0-22	MFF105	0-45	OC83	0-25
2N4289	0-20	BF185	0-25	NKT128	0-45	OC84	0-80
2N5027	0-43	BF194	0-18	NKT129	0-20	OC114	0-88
2N5088	0-25	BF195	0-18	NKT211	0-25	OC122	1-00
28301	0-59	BF196	0-15	NKT212	0-25	OC123	1-10
28304	1-15	BF197	0-15	NKT214	0-25	OC129	0-40
28501	0-75	BF861	0-25	NKT216	0-40	OC140	0-65
28703	1-00	BF898	0-25	NKT217	0-45	OC141	0-80
AA129	0-20	BFX12	0-20	NKT218	1-13	OC169	0-20
AA212	0-75	BFX13	0-25	NKT219	0-85	OC170	0-25
AAZ13	0-10	BFX29	0-85	NKT222	0-80	OC171	0-80
AC107	0-25	BFX30	0-22	NKT224	0-80	OC200	0-55
AC126	0-25	BFX35	0-98	NKT251	0-24	OC201	0-55
AC127	0-25	BFX63	0-50	NKT271	0-20	OC202	0-90
AC128	0-20	BFX84	0-25	NKT272	0-20	OC203	0-55
AC187	0-20	BFX85	0-25	NKT273	0-20	OC204	0-65
AC188	0-20	BFX86	0-25	NKT274	0-20	OC205	1-00
AC171	0-75	BFX87	0-25	NKT275	0-25	OC206	1-10
AC178	0-27	BFY10	0-20	NKT277	0-20	OC207	1-00
AC179	0-27	BFY10	1-00	NKT278	0-25	OC460	0-20
AC190	0-22	BFY11	0-20	NKT291	0-85	OC470	0-80
AC191	0-22	BFY11	0-40	NKT304	0-75	OC7P1	1-00
AC192	0-16	BFY18	0-45	NKT403	0-70	ORP12	0-85
AC193	0-25	BFY19	0-55	NKT404	0-60	ORP60	0-45
AC194	0-25	BFY24	0-45	NKT676	0-20	ORP61	0-48
AC195	0-25	BFY44	1-00	NKT713	0-20	P1044	0-29
AC196	0-22	BFY50	0-20	NKT773	0-25	8X68	0-80
AC197	0-22	BFY51	0-20	NKT777	0-25	8X69	0-45
AC198	0-22	BFY52	0-20	O78B	0-38	8X65	0-55
AD140	0-50	BFY53	0-17	OA6	0-12	8X64	0-75
AD149	0-50	BFY54	0-45	OA7	0-05	8X41	0-75
AD151	0-30	BFY90	0-45	OA70	0-10	8X47	0-65
AD162	0-30	B8X27	0-50	OA71	0-20	8X64	0-85
AF106	0-20	B8X60	0-98	OA73	0-15	8X64	0-85
AF114	0-25	B8X76	0-12	OA74	0-15	T1843	0-26
AF115	0-25	B8Y26	0-17	OA79	0-10	V16/30P	0-75
AF116	0-25	B8Y27	0-20	OA81	0-10	V30/201P	0-75
AF117	0-25	B8Y28	0-20	OA85	0-15	V80/201	0-50
AF118	0-20	B8Y95A	0-18	OA86	0-15	V90/201P	0-70
AF119	0-20	B8Y95	0-12	OA90	0-07	XA101	0-10
AF124	0-20	BT102/500R	0-95	OA91	0-07	XA102	0-15
AF125	0-20	BT102	0-75	OA95	0-07	XA151	0-15
AF126	0-20	BTY42	0-92	OAZ200	0-08	XA152	0-15
AF127	0-20	BTY79/100R	0-92	OAZ201	0-10	XA161	0-25
AF128	0-20	BTY81	0-75	OAZ210	0-20	XA162	0-25
AF178	0-65	BTY79/400R	0-92	OAZ211	0-25	XB101	0-45
AF179	0-65	BY100	1-10	OAZ220	0-50	XB102	0-25
AF180	0-65	BY106	0-15	OAZ221	0-45	XB103	0-25
AF181	0-60	BY126	0-14	OAZ222	0-45	XB113	0-80
AF186	0-60	BY127	0-15	OAZ223	0-45	XB121	0-40
AF189	1-18	BY182	0-85	OAZ224	0-45		

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.
 Valves, Tubes and Transistors - Closed Sat. 1 p.m.-3 p.m.
 Terms C.W.O. only - Tel. 01-677 2424-7
 All orders subject to V.A.T. at 10% rate. This must be added to the total order including postage.

Prices correct when going to press.

Liquid-Crystal Clocks

- MM5316 DIGITAL ALARM CLOCK CHIP—**
- 1 As in P.E. April '74 issue
- MM5316 Chip + data £15.00
 - 40-pin D.I.L. socket for MM5316 £1.35
 - LM3900 £0.69
 - 3M Display Film 3in x 1½in £0.50
- KIT PRICE £17.00 + VAT**
- DIL2-4 switch £0.80
- 2 Bywood 5316-LC Kit**
- MM5316 Chip + data £15.00
 - 40-pin socket £1.35
 - RCA Liquid Crystal Display £13.00
 - PCB £2.50
 - 3M Display Film 3in x 1½in £0.50
- KIT PRICE £30.00 + VAT**

Please note that Siemens and RCA L-Cs are not pin compatible. Other kits, chips, displays available.

BYWOOD HAS TIME FOR YOU!

CLOCK DATA SHEETS—S.A.E. ADVICE—PHONE 0422-62757
 POST & PACKING—10p OVERSEAS (AIRMAIL) 50p VAT—ALL PRICES EXCLUDE VAT
 PAYMENT C.W.O. or ACCOUNT ACCESS ORDERS & PAYMENTS BY PHONE ACCEPTED
 QUANTITY DISCOUNTS ON MOST ITEMS—STATE REQUIREMENTS FOR QUOTATION

BYWOOD ELECTRONICS
 181 EBBERS ROAD
 HEMEL HEMPSTEAD
 HP3 9DS TEL 0442-62757
 24 HOUR ANSWERPHONE ON-LINE

F.M.O. VARICAP TUNER

- LP1185/86 £10.25/pair
- MC1310P £3.15 each
- MFC4060 78p
- P.C. BOARDS £1.87
- READY BUILT BOARDS £23.00
- COMPLETE TUNERS IN CABINETS £33.00

NEW! LP1400 DECODER MODULES
 —LIMITED STOCKS £4.96
 Prices include V.A.T. P. & P. 25p.

B. & B. ELECTRONICS


64 MANNERS ROAD, BALDERTON, NEWARK, NOTTS.
 Telephone: NEWARK 6895

CARBON SLIDE POTENTIOMETERS


- 60 mm Twin Track, including black knob 60p (inc. V.A.T.)
- 60 mm Single Track, including black knob 50p (inc. V.A.T.)
- 1K, 10K, 22K, 47K, 100K, 500K Ohms Log, Lin, Antilog.
- Metal Case
- 3-2 dB matched track
- 15 mV nominal noise (BS2122)
- Life exceeds 20,000 cycles
- Fixing holes 2 x M3 on 80 mm centres

Designed, Manufactured and Supplied by:
RIVLIN INSTRUMENTS LTD.
 DOMAN ROAD
 CAMBERLEY, SURREY GU15 3DJ

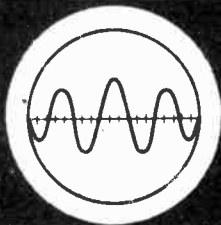
Send cash with order to above address. Postage and packing 15p per order. Trade enquiries invited.



TUAC

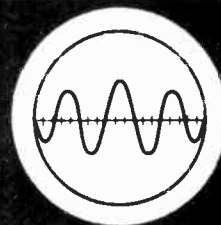

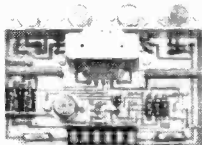NEW TUAC POWER MODULES. Now in their second successful year offering more power and quality than ever before.



TP100 ★ 125 Watts RMS continuous sine wave output
 Illustrated ★ 4 RCA 150 Watt 15 Amp output transistors
£17.25 ★ Special layer wound driver transformer
 ★ Short, open, and thermal overload protection
 ★ Compact size: 7 x 6½ x 3 in.



TL100 ★ 100 Watts RMS sine wave
 Illustrated ★ 2 RCA 15 Amp output transistors
£13.00 ★ Rugged transformer driver
 ★ Full thermal overload protection
 ★ Compact size: 5 x 5 x 3 in.

TL60 ★ 60 Watts RMS sine wave
£12.00 ★ RCA 115 Watt output transistors
 ★ Only six connections to make
 ★ Same size as TL100

TL30 ★ 30 Watts RMS sine wave
£9.50 ★ Full thermal overload protection
 ★ Short and open circuit proof
 ★ Rugged transformer driver

Specification on all four power modules

All output power ratings ± 1dB Output impedance 8-15 Ohms THD at full power 1% typically 0.5%
Input sensitivity 60mV into 10kΩ Frequency response 10Hz-25kHz ± 2dB Hum and noise better than -75dB

Power supplies vacuum impregnated Transformers with supply board incorporating pre-amp supply:

PS 125 ± 50 volts for one TP100	£11.75
PS 100 ± 45 volts for one TL100	£10.75
PS 60 ± 40 volts for one TL60	£9.50
PS 30 ± 50 volts for one TL30	£7.00
PSU 2 for supplying Disco Mixer	£4.75



TUAC DISCO THEQUE MIXER WITH AUTO FADE

Designed for the discerning D.J. of professional standard
Offering a vast variety of functions

Controls: Mic Vol. Tone. Over-ride depth. Auto Manual Sw. Tape Vol. L & R Deck Faders. Deck Volume. Treb. and Bass. H. Phon Vol. Selector. Master Vol. on/off sw. Max. output 1V RMS Specification as VA06

£27.00

PANEL SIZE 18" x 4½" DEPTH 3"

ALL PRICES INCLUDE V.A.T. AND POSTAGE AND PACKING
ACCESS & BARCLAY CARDS ACCEPTED, JUST SEND US YOUR NUMBER. H.P. ARRANGED THROUGH PAYBONDS.

PREAMPLIFIERS

All Tuac audio modules are constructed on glass fibre P.C. board, are ready assembled and fully tested. Low noise silicon and FET transistors together with H.S. carbon film resistors are used throughout. Extensive research has gone into the various wide range tone control circuits producing superb sound quality from any signal.

VA08 Vol. Treb. Mid and Bass Controls. HI IMP. FET I/P. Suitable Mic. Guitar, Radio, Crystal/Ceramic P U
Sensitivity 4mV Treb +35dB at 16kHz. Mid -20-15dB at 1kHz. Bass -20-10dB at 40Hz **£5.00**

VA06 Vol. Treb and Bass Controls. 8mV sensitivity Treb -28-15dB at 12kHz. Bass ±18dB at 40Hz **£4.25**


AMF01 Tuac Auto Fade Unit fades music when you speak.
Auto Mic Over-ride for Disco use. Feed Deck and Mic Pre-amps in. Auto fade O/P to main Amp. 38mV operating level. Depth and Vol. Controls **£5.00**

VA08 ILLUSTRATED




SIZE 6½" x 2" x 1"

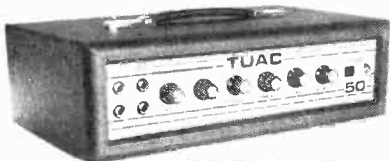TUAC HIGH POWER AMPLIFICATION—built to high standards, and built to last



50 WATT RMS SINE WAVE ALL PURPOSE AMPLIFIER

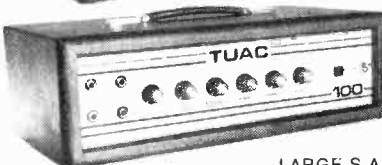Suitable for Disco, PA, Guitar, 4 inputs. 2 volume controls Master volume, treble, middle and bass controls. Rugged circuit rugged leathercloth covered case, short and open circuit protection. Tone control specification as VA08 pre-amp. FULLY FUSED



50 WATT £44.00


100 WATT £66.00

LARGE S.A.E. WITH ALL ENQUIRIES PLEASE

TUAC MAIN DEALERS

BRISTOL DISCO CENTRE, 86 Stokes Croft, Bristol 1. Tel. Bristol 41666.
CALBARRIE AUDIO, 38 Cromwell Road, Luton, Beds. Tel. Luton 411733.
SOCODI, 9 The Friars, Canterbury, Kent. Tel. Canterbury 60948.

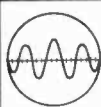MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT
OPEN 6 DAYS A WEEK. 9.30 a.m. - 6.00 p.m.




TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION COMPANY LTD. (DEPT. E)
163 MITCHAM ROAD LONDON SW17 9PG
01-672 3137/9080

ALL OUR PRICES INCLUDE V.A.T.

BSR HI-FI AUTOCHANGER STEREO AND MONO

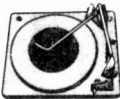Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. A.C. 200/250V Size 13" x 11 1/2". Above motor board 3 1/2". Below motor board 2 7/8". with STEREO and MONO XTAL £6.75 Post 25p.



PORTABLE PLAYER CABINET

Modern design. Black rexine covered Silver front grille. Chrome fittings. Motor board cut for above BSR deck £4.50 Post 45p.

COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 1 1/2" x 10" x 3 1/2". Player unit clips to loudspeakers making it extremely compact. Overall size only 13 1/2" x 10" x 8 1/2". 3 watts per channel. Plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls 240V a.c. mains.



Attractive Teak finish Weight 13 lb. Bargain Price £25 85p carriage

SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH

0-80 MINUTES Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Makers' last price £4.50. Brand new and fully guaranteed. Fully insulated. OUR PRICE £1.65. Post 25p



WEYRAD P50 - TRANSISTOR COILS

RA2W Ferrite Aerial 85p
Osc. P50/1AC 40p
I.F. P50/2CC 470 kc/s 40p
3rd I.F. P50/3CC 40p
Speaker Cores 30p
Mullard Ferrite Rod 8 x 3/16", 20p. 6 x 1/8", 20p. 3 x 1/4", 10p.

VOLUME CONTROLS

5 K. ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p. STEREO L/S 55p. D.P. 75p. Edge 5K.S.P. Transistor 25p.

80 Ohm Coax 5p yd.

BRITISH AERIALITE AERAXIAL-AIR SPACED 40p. £1.75: 60 yd. £2.60 FRINGE LOW LOSS Ideal 625 and colour 10p yd


8in. or 10in. ELAC HI-FI SPEAKER

Dual cone plasticated roll around. Large ceramic magnet. 50-16,000 c/s. Bass resonance 55 c/s. 8 ohm impedance. 8in 10 watts, 10in 12 watts music power. £3.75 Post 25p



E.M.I. 13 1/2 x 8in. SPEAKER SALE!

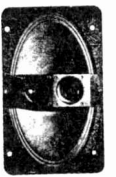With twin tweeters. And crossover. 16 x 8in 90p. 12 x 3in 50p. 16 x 10in £1.10. State 3 or 8 or 15 ohm. As illustrated. Post 25p £4.50



With Harced tweeter cone and ceramic magnet. 10 watt. Bass resp. 45-80 c/s. Flux 10,000 gauss. £2.75

State 3 or 8 or 15 ohm. Post 25p. Bookshelf Cabinet 16 x 10 x 9in. £6.60 Teak finish Post 45p

SET OF 3 MOTORS FOR COLLARO STUDIO 115 VOLT TAPE DECK £2.50 Post 50p

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 in sides 8 x 4 in 45p; 8 x 6 in 53p; 10 x 7 in 65p; 12 x 8 in 85p; 14 x 8 in 90p; 12 x 3 in 50p; 16 x 10 in £1. ALUMINIUM BOXES. 3 x 3 x 3 in 60p; 4 x 4 x 4 in 70p; 6 x 4 x 4 in 80p; 8 x 4 x 4 in £1; 12 x 4 x 4 in £1.30. ALUMINIUM PANELS 18 s.w.g. 6 x 4 in 12p; 8 x 6 in 19p; 14 x 3 in 20p; 10 x 7 in 24p; 12 x 5 in 25p; 12 x 8 in 34p; 16 x 8 in 34p; 14 x 8 in 40p; 12 x 12 in 47p; 16 x 10 in 60p. PAXOLIN PANEL 10 x 8 in 20p.

ANOTHER R.C.S. BARGAIN!

ELAC 9 x 5in HI-FI SPEAKER TYPE 59RN

This famous unit now available. 10 watts. 8 ohm.

Price £3.30 Post 25p

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer Input 200/240V a.c. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. £2.20 Post Details S.A.E. Size 3 1/2 x 1 1/2 x 1 1/2 in.

RCS POWER PACK KIT

12 VOLT, 750mA. Complete with printed circuit board and assembly instructions. £2.95 Post 25p

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12V or H.T. line 200-300V d.c. operation. Size: 1 1/2 x 1 1/2 x 1 1/2 in. Resonance 25 c/s to 25 kc/s. 26 dB gain. For use with valve or transistor equipment. £99p Post Full instructions supplied. Details S.A.E.

ELECTRO MAGNETIC PENDULUM MECHANISM

1.5V d.c. operation over 300 hours continuous on SP2 battery, fully adjustable swing and speed. Ideal displays. Teaching electro magnetism or for metronome, strobe, etc. 95p Post 20p

BRITISH FM/VHF TUNING HEART

88 to 108 M/Cs British made. 2 Transistors ready aligned requires 10.7 M/Cs I.F. Complete with tuning gang. Connections supplied but some technical experience essential. Our price £3.95 Post 20p

MAINS TRANSFORMERS

Eagle MT12 12-0-12V 50 mA 90p
250-0-250 80 mA, 6-3V 3-5A 6-3V 1A or 5V 2A £2.50
350-0-350 80 mA, 6-3V 3-5A, 6-3V 1A or 5V 2A £3.00
300-0-300V 120 mA, 6-3V 4A C.T., 6-3V 2A £3.95
MINIATURE 200V 20 mA, 6-3V 1A 2 1/2 x 2 1/2 in 75p
MIDGET 220V 45 mA, 6-3V 2A 2 1/2 x 2 1/2 in 90p
HEATER TRANS. 3V 1.5A 75p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V £3.00
1 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £3.00
2 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £4.00
5 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £9.75
5, 6 and 12V 5 amp. £1.20
3 amp. 3, 5, 8, 10, 12 and 5-0-5V £1.30, Dillo 5 amp. £1.50; 6-0-6V 500mA 90p 5V 1amp. 95p, 12V 300mA 75p, 12V 500mA 85p, 12V 750mA 95p, 40V 1 amp. £1.75.
AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 150W £3.00; 500W £6.25; 750W £10; 1000W £15
CHARGER TRANSFORMERS. Input 200/250V for 6 or 12V, 1 1/2 amp £1.50; 2 amp £1.80; 4 amp £2.50
BATTERY CHARGERS. Ready built with leads and clips 1 1/2 amp £2; 4 amp £4; 5 amp £4.50.
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs, 1 1/2 amp 40p; 2 amp 55p; 4 amp 85p.

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V. 3A. 720W. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. OUR PRICE £10 Carr. 50p
Can be used as 800W auto transformers 240-110V. IDEAL FOR COLOUR T.V. OR GARDEN TOOLS.

NEW ELECTROLYTIC CONDENSERS			
2/350V 14p	250/25V 14p
4/350V 14p	500/25V 20p
8/450V 18p	1000/25V 35p
16/450V 22p	1000/50V 47p
32/500V 50p	8-8/450V 22p
25/25V 10p	8-16/450V 25p
50/50V 10p	16-16/450V 40p
100/25V 10p	32-32/500V 40p

LOW VOLTAGE ELECTROLYTICS.
1, 2, 4, 5, 8, 10, 25, 30, 50, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 20p; 50V 30p.
1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p.
2000mF 8V 25p; 25V 42p; 50V 57p.
2500mF 50V 82p; 3000mF 25V 47p; 50V 85p.
5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p.

CERAMIC. 1pF to 0.01mF. 4p; Silver Mica 2 to 5000pF. 4p. PAPER 350V-0.1 4p. 0.5 13p; 1MF 150V 15p; 2MF 150V 15p. 500V-0.001 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p. SILVER MICA. Close tolerance 1%. 2-2-500pF 8p; 560-2,200pF 10p; 2,700-5,000 pF 20p; 8,000pF-0.1, mfd 30p each. TWIN GANG. "0-0" 200pF + 170pF. 65p; 500pF standard 45p. 365pF + 365pF with 25pF + 25pF. Slow motion drive 50p. SHORT WAVE SINGLE. 10pF, 30p, 25pF, 55p, 50pF, 55p. NEON PANEL INDICATORS 250V AC/DC. Amber 20p. RESISTORS. 1W, 1/2W, 20%, 1p; 2W, 5p, 10p to 10M. HIGH STABILITY. 1W 2% 10 ohms to 6 meg., 10p. DITO 5%. Preferred values 10 ohms to 10 meg., 4p. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 10p each; 0.5 ohm to 8.2 ohms 10p. TAPE OSCILLATOR COIL Valve type 35p.

NEW MODEL "BAKER LOUDSPEAKER" 12IN 50 WATT. GROUP 50/12. 8 OR 15 OHM HIGH POWER. FULL RANGE PROFESSIONAL QUALITY. £17.60

BAKER MAJOR 12" £9.90

30-14,500 c/s, 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 20W. NOTE: 3 or 8 or 15 ohms must be stated.
Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. £12.50
Please state 3 or 8 or 15 ohms. Post free

BAKER "BIG-SOUND" SPEAKERS Post free

'Group 25' 12in. £8.80 25W 3 or 8 or 15 ohm
'Group 35' 12in. £9.90 35W 3 or 8 or 15 ohm
'Group 50' 15in. £22 50W 8 or 15 ohm

TEAK VENEERED HI-FI SPEAKER & CABINETS

For 12in or 10in dia. speaker 20 x 13 x 9in. £10.00. Post 50p
For 13 x 8in or 8 in speaker 16 x 10 x 9in. £6.60. Post 35p
For 8 x 5in speaker 16 x 8 in. £5.00. Post 25p
For 8in and Tweeter 16 x 10 x 9in. £4.00. Post 25p
Loudspeaker Cabinet Wadding 18in wide. 15p ft.

GOODMANS 6 1/2in. HI-FI WOOFER

8 ohm. 10W. Large ceramic magnet. Special Cambric cone surround. Frequency response. 30-12,000 c/s. £4
Ideal P.A. Columns. Hi-Fi enclosure 50mas, etc. Suitable Cabinet 12 x 8 x 6 1/4 Suitable Tweeter £2

ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth exponential fall of total response from 1,000 c/s to 18,000 c/s. Size 3 1/2 x 3 1/2 in deep. Rating 10W. 3 ohm. Crossover £1.25 £1.90 Post 20p.

SPEAKER COVERING MATERIALS. Samples Large S.A.E.

Horn Tweeters 2-16kc/s. 10W 8 ohm or 15 ohm £2.25. De Luxe Horn Tweeters 2-16kc/s. 15W. £3.50. CROSSOVERS. TWO-WAY 3,000 c/s 3 or 8 or 15 ohm £1.25. LOUDSPEAKERS P.M. 3 OHMS. 7 x 4in., £1.25; 6 1/2in., £1.50; 8 x 5in., £1.60; 10in., £2.00; 8in., £1.75; 10 x 6in., £1.90. SPECIAL OFFER! 80 ohm, 2 1/2in, 2 1/2in; 35 ohm, 2in, 3in, 25 ohm, 2 1/2in dia., 3in dia., 5in dia., 15 ohm, 3 1/2in dia., 6 x 4in, 7 x 4in, 8 x 5in, 3 ohm, 2 1/2in, 2 1/2in, 3in dia. (6 x 4in 8 ohms £1.50.) RICHARD ALLAN TWIN CONE LOUDSPEAKERS: 8in diameter 4W £2.50, 10in diameter 5W £2.50, 12in diameter 6W £2.95/15 ohms, please state. VALVE OUTPUT TRANS. 40p; MIKE TRANS. 50.1 40p. Mike trans. mu metal 100.1 £1.25.

MAJOR 100 WATT ALL PURPOSE GROUP AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm c/s. Mains. Separate treble and bass controls. Guaranteed. Details S.A.E. £49 Carr. £1.00
PROFESSIONAL VALVE MODEL, 100W, callers only, £69.



BARGAIN AM TUNER. Medium Wave. £4.95

Transistor Superhet, Ferrite aerial. 9 volt.

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. £4.50

Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9V. TWO CHANNEL STEREO VERSION £5.95

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume. Treble and bass controls. 18 volt d.c. £4.50

COAXIAL PLUG 10p. PANEL SOCKETS 10p. Line 18p. OUTLET BOXES, SURFACE 25p. FLUSH 60p. TWIN 85p. BALANCED TWIN RIBBON FEEDER 30 ohms. 5p yd. JACK SOCKET Std. open-circuit 14p. closed circuit 23p. Chrome Lead Socket 45p. Phone 1 1/2 x 3/4. Phone Socket 5p. JACK PLUGS Std. Chrome 20p; 3-5mm Chrome 12p. DIN SOCKETS Chassis 3-pin 10p. 5-pin 10p. DIN SOCKETS lead 3-pin 18p; 5-pin 15p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS. S.A.E. CERAMICS 10p; CANS 5p.

REVERSIBLE 4 POLE MOTOR £2.20

1,400 r.p.m. Reversible 42 Watt. 1 1/2 x 1 1/2 x 1 1/2 in. size 3 1/2 x 3 1/2. As illustrated. With Cooling Fan. a.c. 240V. Post 25p

E.M.I. GRAM. MOTOR. £1

120V or 240V a.c. 2,400 r.p.m. 2 pole 70mA. Size 2 1/2 x 2 1/2 in. Post 25p.

SPECIAL OFFER

100 ohm 20W Rheostat 2 1/2in diam. Ceramic Former, screw terminals, 3in diam. spindle. 95p, post 25p.


337 WHITEHORSE ROAD, CROYDON

Open 9-6, Wed. 9-1, Sat. 9-5 (Closed for lunch 1.15-2.30)

Buses 50, 68, 159. Rail Selhurst. Tel. 01-684 1665

RADIO COMPONENT SPECIALISTS

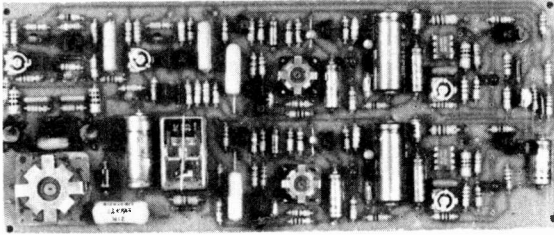Radio Books and Component Lists 10p. (Minimum posting charge 20p.)



HI-FI TAPE LINK

(PE Mar./Apr. 73) S/c's, i.c.'s, Rs, Cs, Relay and pc-base. Pot Cores and pc-bases Sw s. Pots. Panel Lamp—Mono. £12.78; Stereo. £20.41. PSU. £3.58. Main Circuit PCB (3 1/2in x 9in) Stereo (also holds relay and cores). £2-10. Sub-assembly PCB (2 1/2in x 6 1/2in). Stereo 80p.

BIOLOGICAL AMPLIFIER

(PE Jan./Feb. 73) P/A Set—S/c's, i.c.'s, Rs, Cs, Pots. PCB. £3.46. Output Stages—S/c's, Rs, Cs, Pots. Rotary Sw's and PCBs for Alphaphone, Cardio, Freq-Meter, Vis-Feed, £4.96. Audio Amps PC7. £5.20; EA1000. £3.30.

ENLARGER EXPOSURE METER AND THERMOMETER

(PE Sept. 73) S/c's, Thermistor, LDR. Rs. Pots. PCB. £3.90.

ELECTRONIC PIANO

(PE Sept. 72/Jan. 73) Details in lists.

GEMINI STEREO AMPLIFIER

(PE Nov. 70/Mar. 71) Stereo Sets and PCBs. Pre-amp—Rs, Cs, Pots, Sw s—with iW MO Rs. £14.18—with iW CF Rs. £10.40. PCB as published. £2.20. Main Amp—Rs, Cs, Pots. £5.88. PCB (3 1/2in x 5in). £1.28. Power supply—Rs, Cs, Pot. £4.56. PCB (2in x 4in). 65p.

AUDIO MILLIVOLTMETER

(PE Feb. 74) S/c's, Rs, Cs, Pots, Sw s. PCBs. £4.95.

MICROPHONE MIXER

(PE Apr. 69) S/c's, Rs, Cs, Pots, PCB (also holds pots). £4-12. While Stocks Last

8 WATT AMPLIFIER

(PW Nov./Dec. 72) Pre-amp—S/c's, Rs, Cs, Pots, Sw—Mono. £2.90; Stereo. £6.03. PCB (3 1/2in x 7 1/2in) (Stereo) also holds rotary or slider pots, and Sw. £1.66. Main Amp—S/c's, Rs, Cs, Pot—Mono. £4.18; Stereo. £8.36. PCB (2 1/2in x 3in) (Mono). 60p. PSU. £3.90.

SOUND SYNTHESISER

(PE Feb. 73/Febr. 74)

RHYTHM GENERATOR

(PE Mar./June 74)

SOUND BENDER

(PE May 74)

Details of all these in List

REVERBERATION UNIT

(PW Nov./Dec. 72) S/c's, Rs, Cs, T/frmtr —with Rotary Pots. £6.44—with Slider Pots. £7.28. PCB (2in x 1 1/2in) also holds sliders. £1-20. 9in Spring Unit. £4.50.

LOUDHAILER AND SIREN

(PW Dec. 72) Pre-amp and Siren Generator —S/c's, Rs, Cs, Pot. PCB (2 1/2in x 2 1/2in). £2-20. While Stocks Last. Main Amp Module P.C.S. £6.25.

MISCELLANEOUS PCBs (While Stocks Last)

LOGICAL RADIO CONTROL (PE Dec. 71/Jan. 72) PCBs—2A, 2B—Decoder 50p each
MODEL SERVO CONTROL (PE Feb./Mar. 72) PCBs—B—Fail-safe, 33p each
DIGITAL PSU PCB (PE Aug. 72), 50p. OSCILLOSCOPE P/A PCB (PE Aug. 72), 33p.
GEMINI STEREO TUNER PCB (PE Apr. 72), £1-50. TRAFFIC PCB (PE Feb. 73), 60p.
(The above PCBs are as published)
DIGITRONIC (PW Mar. 73) Read-out PCB (1 1/2in x 3 1/2in), 50p. CALLERCOD (PE Jul. 72) Main Control PCB (4in x 7 1/2in)

PHONOSONICS PCB'S AND KITS

PHOTOPRINT PROCESS CONTROL

(PE Jan./Feb. 72) For Colour and B & W—finds exposure, controls timing, stabilises mains voltage. S/c's, SCR, LDR, Rs, Cs, Pots, Relay, Keypad, T/frm, £7-98. PCB (3 1/2in x 5 1/2in) also holds pots, Sw, relay. £1-60.

PROJECT Q4


(PW Oct. 73/Jan. 74) Multisystem Quadraphonic Decoder S/c's, i.c.s, Rs, Cs, Pots, Makeswitches. £12.48. PSU. £3-17. Set of PCBs. £2-60.

RONDO

(PE Sept. 73/Febr. 74) Details in List

PHASING UNIT

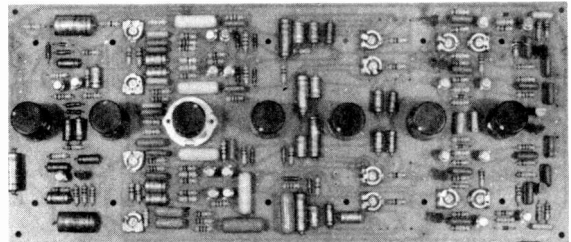(PE Sept. 73) S/c's, Rs, Cs, Pots. PCB (1 1/2in x 2 1/2in). £2-20.



AURORA

(PE Apr./Aug. 71) Multichannel Sound Controlled Light S/c's (Excl. SCRs), Rs, Cs, Pots, Cores—Pre-amp, Sync Generator and 4 Chans. £10-97; 4 extra chans. £8-35. Reg. PSU. £3-95. PCB (4 1/2in x 10 1/2in) for Pre-amp and 4 Chans (also holds pots). £2-50. PCB (4 1/2in x 5in) for Sync Gen. PSU, 8 cores, 8 SCRs. £1-30.

AURORA AUXILIARY CONTROL UNIT

2 Variable Frequency Strobe Generators and 4 Variable Amplitude Frequency Generators S/c's, Rs, Cs, Pots. PCB (3 1/2in x 5 1/2in). £4-87.

SEMICONDUCTOR TESTER

(PE Oct. 73) S/c's, Rs, Cs, Pots, Makeswitches. Sub-assembly PCB. £5-30.

TAPE NOISE LIMITER

(PE Feb. 72) S/c's, Rs, Cs, Pot, Sw. PCB (1 1/2in x 3in). £2-30. Reg. PSU and PCB (1 1/2in x 2 1/2in). £3-40.

ULTRASONIC TRANSMITTER-RECEIVER

(PE May 72) S/c's, Rs, Cs, Pot, Relay, Dual PCB (2in x 5 1/2in). £4-40. Transducers excluded

VERSATILE LIGHT EFFECTS UNIT

Single Channel Sound Controlled Light with built-in variable strobe (PE Jun. 72). S/c's, Rs, Cs, Pots, T/frmrs, Keypad, £11-28. PCB (3 1/2in x 7 1/2in) also holds pots and switch. £1-70. SCRs excluded

VIBRASONIC GUITAR PRE-AMP

(PW Sept. 70) Incl. Mic P/A, 2-Guitar P.A. Trem and Tone Controls, Master Volume S/c's, Rs, Cs, LDR, Rotary Pots, Lamps, Coupling T/frm. £7-64. PCB (3 1/2in x 10 1/2in) also holds pots. £1-92. Power Supply. £3-90.

VOICE OPERATED FADER

(PE Dec. 73) S/c's, Rs, Cs, Pot. PCB (1 1/2in x 3 1/2in). £2-95.

WIND AND RAIN EFFECTS

(PE Oct. 73) S/c's (incl. special noise diode), Rs, Cs, Pots. £1-95.

RESISTORS

±W and ±W
CARBON FILM
MANUFACTURED BY
AEI TO DEF 6112A
E24 SERIES
±W 5% 4E7 to 1M
to 2M2 then 10% to
10M
COMPREHENSIVE
STOCKS
FACILITATE RAPID
PROCESSING
AS APPOINTED
DISTRIBUTORS
WE WELCOME
TRADE AND EXPORT
ENQUIRIES
Write or Phone
Trade Dept.
ERITH 30737

SEMICONDUCTORS

AC138 25p
AC176 28p
AD161 40p
BC107 13p
BC108 13p
BC109 13p
BC147 12p
BC148 12p
BC149 12p
BC157 12p
BC158 12p
BC159 12p
BC182L 12p
BC204 12p
BC209C 14p
BC212L 15p
BCY11 22p
BFY50 22p
BFY52 23p
BSY55A 12p
MJE2955 118p
MJE3055 75p
NKT3033 112p
OC28 65p
OC71 14p
OC84 25p
ORP12 55p
T1543 36p
2N706 13p
2N914 22p
2N1304 22p
2N2219 27p

2N2905 27p
2N2907 22p
2N3702 12p
2N3703 12p
2N3704 12p
2N3815 35p
2N3822E 39p
2N4871 36p
10 63
2 2 65
4 7 35
1 7 63
6 8 40
10 25
10 63
15 40
33 18
22 25
33 6 3
7p
8p
33 50
33 50
47 25
47 40
50 6 4
50 6 4

DIODES

1N916 4p
1N4001 7p
1N4002 7p
1N4004 8p
1N4005 8p
BA145 23p
OA91 7p
OA200 8p
1GP7 12p
1S-150 11p

INTEGRATED CIRCUITS

709 T05 48p
723 T05 95p
741 8P DIL 80p
747 14P DIL 115p
748 T05 63p
7400 20p
7402 20p
7420 20p

ELECTROLYTIC (µF/V)

0 47 63 8p
1 0 63 8p
2 2 65 8p
4 7 35 12p
1 7 63 12p
6 8 40 12p
10 25 12p
10 63 12p
15 40 12p
33 18 12p
22 25 12p
33 6 3 12p
7p
8p
33 50 12p
33 50 12p
47 25 12p
47 40 12p
50 6 4 7p
50 6 4 7p
680 25 28p
1000 10 14p
2200 25 45p
1000 25 25p
1000 40 80p
2200 25 45p
2200 40 80p
2800 100 350p
3300 83 133p
3300 100 350p
4700 18 16p
4700 25 3 16p
8000 40 93p

POLYESTER (µF)

0 01 3p
0 015 3p
0 022 3p
0 033 3p
0 047 3p
0 068 3p
0 1 4p
0 15 5p
0 22 5p
0 33 7p
0 47 9p
0 68 11p
1 0 14p
0 1 35 12p
0 2 35 12p
0 47 35 12p
1 0 35 12p
1 5 35 12p
1 5 35 12p
2 2 35 12p
4 7 35 12p
10 18 12p
10 25 16p
15 3 16p
15 6 16p
22 18 16p
47 25 3 16p
80 40 93p

TANTALUM BEAD (µF/V)

0 1 35 12p
0 2 35 12p
0 47 35 12p
1 0 35 12p
1 5 35 12p
2 2 35 12p
4 7 35 12p
10 18 12p
10 25 16p
15 3 16p
15 6 16p
22 18 16p
47 25 3 16p
80 40 93p

ADD 15p P. & P.
ADD 10% VAT to total cost (including P & P)
SEND S A E (Stamped Addressed Envelope) for Free Itemised List (and with all enquiries please)
OVERSEAS COSTS P & P will be charged at cost (most kit weights and postal rates are shown in list) Send International Reply Coupon for Free List & with all enquiries VAT does not apply to exports. EXPORT ORDERS ARE ALWAYS WELCOME
MAILING LIST SERVICE—details with list
COLOUR CODE identification supplied with most kits and as part of list
PCBs are Fibreglass. Drilled, Tinned, and designed by Phonosonics unless stated as published
PCB Layout and Circuit Diagram supplied free with Phonosonics-designed PCBs
POTS are rotary unless stated as slider.
PRICES correct at time of press E & OE DELIVERIES subject to availability

**PHONOSONICS, DEPT. PE26, 25 KENTISH ROAD, BELVEDERE, KENT DA17 5BW
MAIL ORDER ONLY**

CRESCENT RADIO LTD.

11-15 & 17 MAYES ROAD, LONDON N22 6TL
(also) 13 SOUTH MALL, EDMONTON, N.9

MAIL ORDER DEPT.
11 MAYES ROAD, LONDON N22 6TL
Phone 888 3206 & (EDM.) 803 1685

ADD LUXURY TO YOUR CAR

WITH A MOTOR DRIVEN CAR AERIAL
Spec.: 5 Section

Extended Length 100cm
Length under Feeder 40cm
Cable Length 120cm
Supplied complete with Fixing Bracket and £6.75 P. & P.
Control Switch



"CRESCENT BEAT-BRITE" SINGLE CHANNEL SOUND TO LIGHT UNIT
This fantastic little box approx. 4" x 3" x 2" when connected to the output of a sound source from 1 to 100 watts produces a psychedelic light display of up to 1000 watts. Complete with a sensitive level control the unit is fused and cannot harm your amplifier. A Bargain at £7.50 plus 10p.

"CRESCENT" BUBBLE LIGHT SHOW

A new and exciting feature for the professional disc jockey or to give the private party an electric atmosphere, a projected kaleidoscope of colour. Specification: Projector, 100W, convection cooled, at 30ft the projected image is 16ft. Motor: 1 rev per 2 min. Liquid Wheel: 6in diameter multicolour. The Motor is fitted to the Projector and can only be purchased as a single unit. The Liquid Wheel, however, is our very popular standard model & may be purchased separately. A bargain—Projector with Motor ready for instant use, £15; 6in Liquid Wheel, £5—£20 + 75p carr.

TRI-VOLT BATTERY ELIMINATOR

Enables you to work your Transistor Radio, Amplifier or Cassette, etc., from the a.c. mains through this compact Eliminator. Just by moving a plug you can select the voltage you require, 6, 7½ or 9 volt. This means all your transistor power pack applications can be handled by this one unit. Approx. size 2½in x 2½in x 3½in. Our Price £2.75 plus 10p P. & P. Same model suitably wired for the Philips Cassette £3 plus 10p P. & P.

7in x 4in LOUDSPEAKER

A top quality speaker ideal where small size is important. Manufactured by E.M.I. for a well-known hi-fi set maker. Size: 7in x 4in. Impedance: 8 ohms. Flux: 38,000. Max. Free range: 90Hz to 12kHz. Power handling: 5W. Unbeatable. Price: £1.60. Free postage on this item.

CRESCENT CATALOGUE

If you construct you should own one. Read 20p inc. carriage.

AMTROP KITS

UK65	Transistor Tester	£1.66
UK92	Telephone Amp	£8.26
UK115	Hi-Fi Amp—8W	£4.50
UK130	Mono Control Unit	£4.15
UK145	Amp—15W	£3.81
UK165	RIAA Equalised Stereo Amp	£5.30
UK195	Mini-Amp—2W	£3.66
UK220	Signal Injector	£2.65
UK230	AM-FM Aer. Amp	£3.20
UK275	Mike Pre-Amp	£6.98
UK300	4 Channel Radio Control T.X.	£6.61
UK310	Radio Control Receiver	£3.29
UK415	MW Radio Receiver	£7.92
UK520	AM Tuner	£4.60
UK710	4 Channel A.F. Mixer	£19.58
UK715	Photoelectric Cell Switch	£3.87
UK835	Guitar Pre-Amp	£4.98
UK875	Cap. Discharge Ignition	£13.19
UK915	R.F. Amp 12-170MHz	£2.66
UK935	Wide Band Amp 20Hz to 150MHz	£2.86

TRI-VOLT CAR SUPPLY
Enables you to work your Transistor Radio, Amplifier or Cassette, etc. from the 12 volt car supply. Positive or negative earth. Approx. size is 2in x 3½in x 1½in. This converter supplies 6, 7½ or 9 volts and is transistor regulated. A real money saving device for £2.50. 10p P. & P.

"C.300" DISCO CONTROL PACK

A control Unit which when connected to twin decks makes a disco of professional quality. We supply a smart front panel which incorporates controls, switches and input sockets. The control module, I.C. construction incorporating mixing, pre-amp and headphone listening amplifier. The power pack enables this unit to work from the standard mains. * Inputs include Mic., Tape/Cassette and Twin Decks. * Controls include Mic., Tape, Each Deck, Mono, £14. Stereo, £17 plus 20p carr.

3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT



Three Channel: Bass—Middle—Trebble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 1000V lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) £18.50 plus 38p P. & P.

LOW VOLTAGE AMPLIFIER

5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.e. supplies. Will give about 1W at 8 ohm output. With high IMP input this amplifier will work as a record player, baby alarm, etc., amplifier. £1.75 plus 13p P. & P.

200/250V MAINS RELAY

Heavy duty contacts. 2,500V coil. All new and unused D.P.D.T. mains relays \$0p + V.A.T. Carr. Free. Special quantity price: £40 per 100 relays.

MINI LOUDSPEAKERS

2½in 80 ohm, 50p; 2½in 40 ohm, 50p. Please include 3p P. & P. on each L.S.

VAT

★ Please include 10% VAT on goods plus carriage.

The new Oryx 50 is temperature controlled, light, small, easy to handle, rapid heating and high performance. It has a temperature control within ± 2°C and adjusted in seconds whilst running to any value between 200°C and 400°C. Long life iron coated tip as standard (11 sizes available).

Oryx De-Soldering Irons—small model SR3A instantly removes solder from printed circuits etc. accurate, reliable, simple. PTFE nozzle. Larger instrument SR2 gives more suck, less recoil as only piston moves.



De-Soldering Tools
SR3A £5.06
SR2 £6.65
Oryx 50 Iron
1 at £6.60



ORYX 50
TEMPERATURE CONTROLLED IRON
ORYX SR3A
DESOLDERING TOOL

Lower prices for quantities


Safety Stand £2.44

Prices correct May 1974
Prices include P. & P. and 10% VAT

WH-MK spacemiser storage system

Cabinets have stove enamelled steel frames in three heights all of equal width and depth. The frames are strong and rigid, fitted with top and bottom locating pegs and rear slots making stacking, wall or frame mounting positive and simple.

121, 122, 123, 124	1 off	£4.07	4 off	£3.70
251, 252, 253		£6.16		£5.50
501, 502, 503		£10.67		£9.68
254, 257, 258		£5.83		£5.30
504, 507, 508		£10.01		£9.08

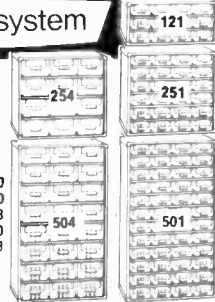

Less for quantities

All prices include P. & P. and 10% VAT. Prices correct May 1974.



CONTIL MOD-3

Contil Mod-3 cases are in six sizes and offer the manufacturer of small instruments an attractive low cost case available ex stock. Made in blue PVC coated steel and complete with front and rear panels and chassis. They are light, strong and rigid. PCE and PSU mounting systems available.

Mod	£3	£4	£5	Width	Height	Depth
Mod-301	£3	£4	£5	7	3	5
Mod-302	£3	£4	£5	7	4	5
Mod-303	£4	£5	£6	7	6	5
Mod-304	£4	£5	£6	11	3	5
Mod-305	£5	£6	£7	11	4	5
Mod-306	£5	£6	£7	11	6	5

Less for quantities. Prices correct May 31. Prices include P. & P. 10% VAT feet and screws.



BRADRAD DRILLING AND DEBURRING TOOL

BRADRAD DRILLING AND DEBURRING TOOL equals eleven drills. One cut drills and deburs the normal run of steels, aluminium, brass, copper and all types of plastics, perspex, fibre glass etc. and hardboard should the need arise it is designed to overcome all the problems associated with drilling thin materials. It drills interlocking holes for instance.

Q-MAX METAL PUNCH

Q-MAX PUNCHES

1½-2½ in	1/2 steps or 6-36mm in 3mm steps. Both with 3 shanks. £10.75. Also 1½-2½ and 36-60 mm. £27.88.
1½-2½ in	1/2 steps or 6-36mm in 3mm steps. Both with 3 shanks. £10.75. Also 1½-2½ and 36-60 mm. £27.88.

All prices include P. & P. and 10% VAT. Prices correct May 31.

ADEL NIBBLING TOOL
ADEL The Adel cuts holes of virtually any shape and size starting from a hole cutting cleanly like a punch and die. Ideal for notching clearances on flanges of cabinets or chassis. £4.81.



CONTIL TEXTURED CASES

Width	Depth	Height	No.	Case	Extra for cost alu panel
7	5	5	755	£5.59	23p
8	6	7	867	£6.12	19p
9	7	5	975	£6.12	19p
12	7	7	1277	£6.73	18p
12	7	7	1277	£5.56	—
18	12	7	18127	£9.55	50p
19	10	10	191010	£13.17	—


Less for quantities. Prices include steel panel with feet and screws. P. & P. and 10% VAT. Prices correct May 31.

WEST HYDE


WEST HYDE DEVELOPMENTS LTD. Ryefield Cres., Northwood Hills, Northwood, Middx HA6 1NN. Tel. Northwood 24941/26732. Telex: 923231
Write or phone for new free catalogue. Prices correct May 31.

Sinclair Project 80

exciting

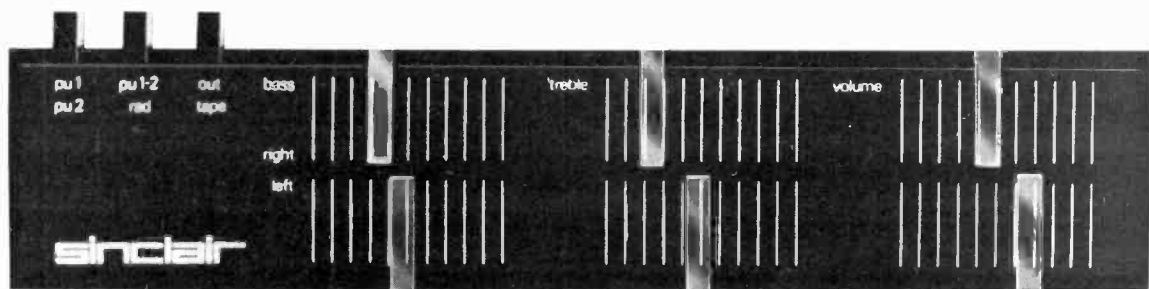

Stereo 80 pre-amplifier/control unit

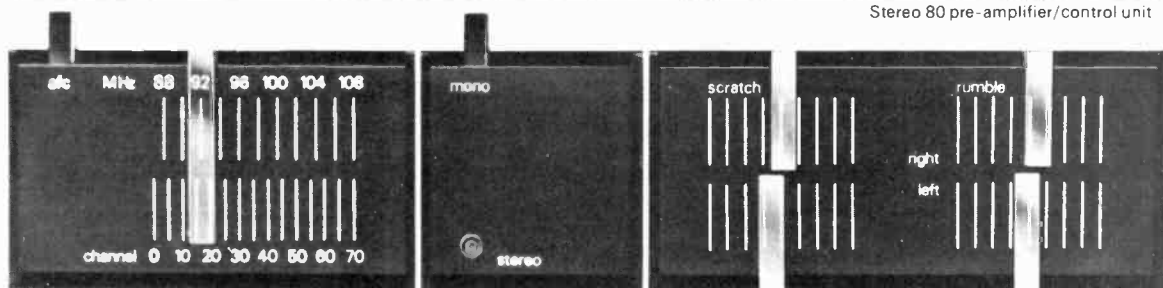

Project 80 tuner

Stereo decoder

Project 80 Active Filter Unit (AFU)

only $\frac{3}{4}$ " deep x 2" high


Living with hi-fi takes on new meaning with Sinclair Project 80. The electronics of these revolutionary new modules are all contained within elegantly designed matching cases no more than three-quarters of an inch deep. They are designed for mounting on any appropriate flat surface by means of 6BA bolts extending from the rear of each module and which pass through suitably drilled holes. Connections are taken away out of sight in a similar manner. The possibilities opened up by Project 80 are endless – superb hi-fi systems can be installed in ways hitherto only dreamed about and never before made practical. No more cutting out and shaping to put modules in position. A few holes drilled with the aid of templates supplied and the job is done. Now you need never again be faced with problems of keeping the hi-fi from clashing with carefully thought-out furnishing schemes. (That will surely please wives!) Slider controls have been introduced in place of knobs and all modules in the range incorporate new up-dated circuitry with emphasis on performance standards and built-in protection against overload and shorting. The aim was to re-think modular construction completely – to make it infinitely more versatile, even simpler and more reliable – the result – Project 80 – another triumph for Sinclair, and the most exciting construction modules ever.

the slimmest, most elegant hi-fi modules ever made

Typical Project 80 applications

System	The Units to use	Units cost
Simple battery record player	Z.40	£5 45 +54p V.A.T.
Mains powered record player	Z.40, P.Z.5	£10 43 +£1.04 V.A.T.
30W. RMS continuous sine wave stereo amp.	2 x Z.40s, Stereo 80; P.Z.6	£30 83 +£3.08 V.A.T.
50W (8 Ω) RMS continuous sine wave de luxe stereo amp.	2 x Z.60s, Stereo 80; P.Z.8	£33 83 +£3.38 V.A.T.
Indoor P.A.	Z.60, P.Z.8	£14 93 +£1.49 V.A.T.

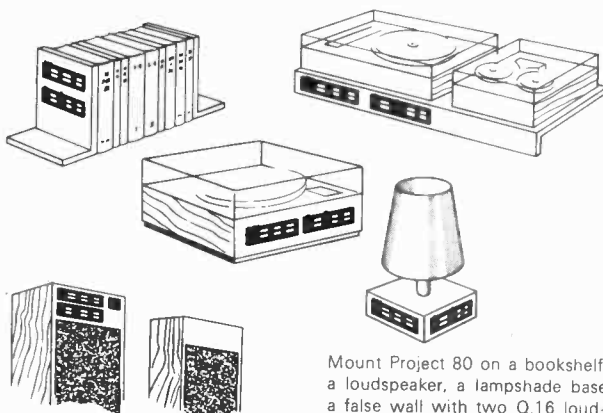
Project 80 FM tuner, decoder, and A.F.U. may be added as required



Mount Project 80 on a bookshelf, a loudspeaker, a lampshade base a false wall with two Q.16 loudspeakers... almost anywhere.

new thinking in modular hi-fi

Stereo 80 pre-amplifier and control unit

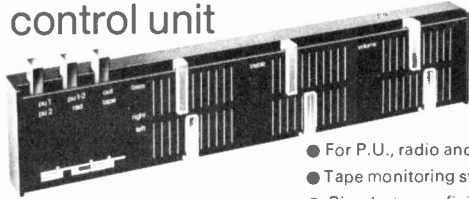

- For P.U., radio and tape
- Tape monitoring switch
- Simplest ever fixing



Each channel has its own separate tone and volume controls operated by sliders, enabling ideal environmental matching to be obtained. A virtual earth input stage forms part of the up-dated circuitry that ensures the finest possible quality from all signal sources. Generous overload margins are allowed on all inputs. Clear instructions with template are supplied.

TECHNICAL SPECIFICATIONS

Size - 260 x 50 x 20mm (10 1/4 x 2 x 3/4 ins)
 Finish - Black with white indicators and transparent sliders
 Inputs - Magnetic pick-up 3mV RIAA corrected, Ceramic pick-up 300mV
 Radio 300mV; Tape 30mV
 Signal/noise ratio - 60dB
 Frequency range - 20Hz to 15KHz : 1dB, 10Hz to 25KHz : 3dB
 Power requirements - 20 to 35 volts
 Outputs - 100mV + AB monitoring for tape
 Controls - Press button for tape, radio and P.U. Sliders for volume, bass (-12dB to -14dB at 100Hz) treble (+11dB to -12dB at 10KHz)

R.R.P. **£11.95** +£1.19 V.A.T.

Project 80 FM tuner and stereo decoder

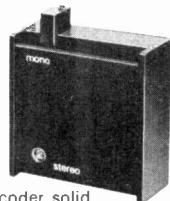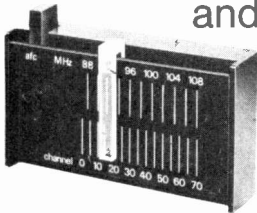

- Twin dual varicap tuning: 4 pole ceramic filter; switchable A.F.C.
- On the decoder, solid state stereo indicating beacon.

Making the Project 80 F.M. tuner and decoder available separately gives a wider choice of systems and saves money where stereo reception may not be required. The tuner is a triumph of electronic design and assures excellent performance. The decoder gives a 40dB channel separation with 150mV output per channel. Both units may be used with other than Project 80 systems.

TECHNICAL SPECIFICATIONS OF TUNER

Size - 85 x 50 x 20mm (3 1/2 x 2 x 3/4 ins)
 Tuning range - 87.5 to 108 MHz
 Detector - I.C. balanced coincidence for good A.M. rejection
 One I.C. equal to 26 transistors
 Distortion - 0.2% at 1KHz for 30% modulation
 4 pole ceramic filter in I.F. section
 Aerial impedance - 75 Ω or 240-300 Ω
 Sensitivity - 4 microvolts for 30dB quieting
 Output - 300 mV for 30% modulation
 Power requirements - 23 to 33 volts

DECODER

Size - 47 x 50 x 20mm (1 7/8 x 2 x 3/4 ins)
 One 19 transistor I.C.


R.R.P. **£11.95** +£1.19 V.A.T.

R.R.P. **£7.45** +0.74 V.A.T.


Guarantee

If, within 3 months of purchasing any product direct from us, you are dissatisfied with it, your money will be refunded on production of receipt of payment. Many Sinclair appointed stockists also offer this guarantee. Should any defect arise in normal use, we will service it without charge.

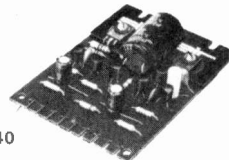Z.40 & Z.60 power amplifiers totally short-circuit proof



Z.40

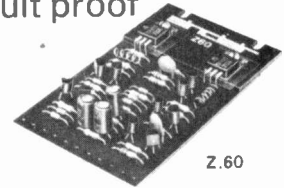

Z.60

Intended for use in Project 80 installations, these modules readily adapt to an even wider range of applications. Both incorporate built-in protection against short circuiting and risk of damage from mis-use is greatly reduced.

Z.40 TECHNICAL SPECIFICATIONS

Size - 55 x 80 x 20mm (2 1/4 x 3 1/4 x 3/4 ins) 9 transistors
 Input sensitivity - 100mV
 Output - 15 watts RMS continuous into 8 Ω (35V)
 Frequency response - 10Hz - 100KHz ± 1dB
 Signal/noise ratio - 64dB
 Distortion - at 10 watts into 8 Ω less than 0.1%
 Power requirements - 12 to 35 volts


Z.60 TECHNICAL SPECIFICATIONS

Size - 55 x 98 x 15mm (2 1/4 x 3 7/8 x 3/4 ins) 12 transistors
 Input sensitivity - 100-250mV
 Output - 25 watts RMS continuous into 8 Ω (45V).
 Distortion - typically 0.03%
 Frequency response - 10Hz to more than 200KHz : 1dB
 Signal/noise ratio - better than 70dB
 Built-in protection against transient overload and short circuiting
 Load impedance - 4 Ω min, max. safe on open circuit

Z.40 R.R.P. **£5.45** + 0.54 V.A.T. Z.60 R.R.P. **£6.95** - 0.69p V.A.T.

Project 80 active filter unit

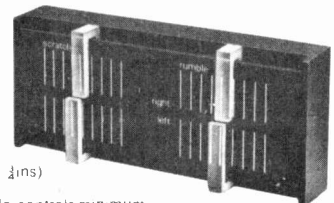Makes a highly desirable part of any worthwhile system where inputs may be from record, radio or tape. As with Stereo 80, separate controls applied to each channel make it easier to obtain ideal stereo balance.



TECHNICAL SPECIFICATIONS

Size - 108 x 50 x 20mm (4 1/4 x 2 x 3/4 ins)
 Voltage gain - minus 0.2dB
 Frequency response - 36Hz to 22KHz controls minimum
 Distortion - at 1KHz - 0.03% using 30V supply
 HF cut off (scratch) - 22KHz to 5.5KHz, 12dB/oct slope
 L.F. cut off (rumble) - 28dB at 20Hz, 9dB/oct slope


- For scratch and rumble control
- Transistorised active circuitry

R.R.P. **£6.95** +0.69 V.A.T.

Power supply units

PZ.8

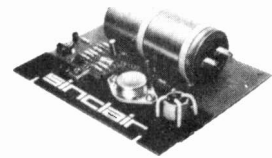Stabilised. Re-entrant current limiting makes damage from overload or even direct shorting impossible. Normal working voltage (adjustable) 45V.



R.R.P. **£7.98** + 0.79p V.A.T.
 Without mains transformer

PZ.5 30V un stabilised
 R.R.P. **£4.98** + 0.49p V.A.T.

PZ.6 35V stabilised
 R.R.P. **£7.98** + 0.79p V.A.T.

To **SINCLAIR RADIONICS LTD. ST. IVES, HUNTINGDON PE17 4HJ**

Please send post paid _____

for which I enclose Cash/Cheque for £ _____ including V.A.T.

Name _____

Address _____

PE6

sinclair

Sinclair Radionics Ltd. London Road, St. Ives, Huntingdon PE17 4HJ
 Telephone St. Ives (0480) 64646

SPECIAL OFFER !!!

SMALL ELECTROLYTICS

Ref No	Capacity	Voltage	Price	Ref No	Capacity	Voltage	Price
H8 1	1µF	150V	4p	H7 4	64µF	15V	4p
H8 2	2 2µF	25V	4p	H7 4A	64µF	35V	5p
H8 2A	3 3µF	25V	4p	H7 5	80µF	16V	4p
H8 3	3µF	50V	4p	H7 8	125µF	16V	5p
H8 3A	4µF	50V	4p	H7 8A	100µF	35V	6p
H8 4	4 7µF	25V	4p	H7 9	100µF	63V	6p
H8 5	5µF	10V	4p	H7 9A	125µF	4V	4p
H8 6A	10µF	10V	4p	H7 10	125µF	25V	6p
H8 8A	16µF	16V	4p	H7 10A	160µF	2 5V	3p
H8 9	20µF	6V	2p	H7 11	160µF	25V	6p
H8 9A	20µF	70V	4p	H7 11A	150µF	16V	5p
H8 10	22µF	50V	4p	H7 13A	200µF	25V	8p
H8 10A	22µF	100V	4p	H7 14	220µF	50V	10p
H8 11	25µF	12V	4p	H7 14A	220µF	16V	6p
H8 11A	24µF	275V	4p	H7 15	220µF	25V	5p
H8 12	32µF	15V	4p	H7 15A	220µF	35V	10p
H8 12A	30µF	10V	4p	H8 11A	250µF	4V	3p
H8 13A	32µF	50V	4p	H6 2	250µF	25V	3p
H8 14	40µF	16V	4p	H6 3A	320µF	2 5V	3p
H8 14A	40µF	16V	4p	H6 4	320µF	10V	4p
H8 15	47µF	50V	4p	H6 4A	330µF	16V	5p
H8 15A	40µF	35V	4p	H6 5	330µF	25V	10p
H7 1	50µF	6V	3p	H6 5A	330µF	35V	15p
H7 1A	50µF	10V	4p	H6 8	470µF	25V	10p
H7 2A	64µF	2 5V	2p	H6 8A	470µF	35V	20p
H7 3A	64µF	25V	4p	H6 9A	400µF	40V	20p

POSTAGE: 15p PER ORDER

ALL GOODS PLUS 10% V.A.T.

MULLARD ELECTROLYTIC CAPACITORS

071 and 072 Series		Working Voltage Vdc	Capacitance µF	Max Ripple Current at 50° C	Weight	Price
Type No.	15332	16	3300	2-4 amps	1oz	15p
071	15472	16	4700	3-9 amps	1oz	17p
071	15682	16	6800	5-8 amps	1½oz	22p
072	15752	16	7500 + 7500	10-5 amps	3oz	37p
072	15113	16	11000 + 11000	13-8 amps	4½oz	49p
072	16502	25	5000 + 5000	9-6 amps	3½oz	37p
072	16752	25	7500 + 7500	12-6 amps	4½oz	49p
071	16861	63	680	2-1 amps	1oz	15p

106 and 107 Series		Working Voltage Vdc	Capacitance µF	Max Ripple Current at 50° C	Weight	Price
106	16223	25	22000	17 amps	10oz	£1.12
106	17103	40	10000	12 amps	7½oz	94p
107	10222	100	2200	10 amps	5½oz	74p

Type No	Voltage	Capacitance	Weight	Price	
102	15163	16	16000	8oz	20p
104	90003	20	39000	16oz	30p
102	16802	25	8000	7oz	25p
104	90001	45	20000	16oz	50p

A further 10% discount on lots of 100 of any one type
Please calculate the weight of your order and include appropriate postage.

Not over	Ordinary Parcels	Not over	Ordinary Parcels
1½lb	20p	10lb	42p
2lb	22p	14lb	52p
4lb	27p	18lb	62p
6lb	32p	22lb	72p
8lb	37p		

UNIJUNCTION TRANSISTORS similar to 2N2646 **25p**

£1 100 ± WATT RESISTORS
100 CERAMIC CAPACITORS
100 DIODES

POSTAGE 15p

PACK No. 1

£1 1 VERO-BOARD CUTTER
5 2½in x 1½in x 0.15 BOARDS
50 BQ. IN "ODD PIECES"
VERO

POSTAGE 15p

PACK No. 3

£1 20 ASSORTED UNUSED MARKED, TESTED TRANSISTORS BC108, ETC.

POSTAGE 20p

PACK No. 5

£1 6 COMPUTER PANELS CONTAINING MASSES OF DIODES, TRANSISTORS, INDUCTORS, RESISTORS AND CAPACITORS

POSTAGE 27p

PACK No. 7

£1 100 RESISTORS
100 CERAMIC CAPACITORS
100 POLYSTYRENE CAPACITORS

POSTAGE 15p

PACK No. 2

£1 100 RESISTORS
100 CERAMIC CAPACITORS
50 MULLARD POLYESTER CAPACITORS

POSTAGE 15p

PACK No. 4

£1 1 TRANSISTORISED SIGNAL TRACER KIT
1 TRANSISTORISED SIGNAL INJECTOR KIT

POSTAGE 20p

PACK No. 6

£1 100 RESISTORS
100 CAPACITORS (ASSORTED TYPES)

POSTAGE 20p

PACK No. 8

TRAMPUS

MONEY BACK IF NOT SATISFIED

all brand new, full spec. Top grade.

Free fabulous NEW catalogue. Send S.A.E.

red+ data source **LED's 17p!** Til209 & clip 22p
BIG 4 panel clip & RED LED 28p. GREEN & clip 59p
INFRA RED LED £1. IC photo amp 44p. & amp switch 85p

Digital Display LED 1/3 0-9 DP. DIL £1-69

Minitron type 0-9 DP. DIL £1-19. SOCKETS 13p.

IC DIGITAL CLOCK CHIPS.

Texas etc with 4 displays £12. 6 displays & chip £14. pcb £1-49

Mostek date & alarm chips with 6 displays £19.

hit: All parts & case. National chip. 4 digit £20. 6x £23.

integrated circuits

741: 8pin 29p, to 99 & 14pin 27p. 748 33p 709 21p

710 35p 723 59p. 555 timer 79p. ZN414 rx. £1-10

703 rf if 28p mc1310 & led £2-76 mc1339 £1-20 TAD100 & if £2

1AMP + REGULATOR 7805, 5.1 & 7-20V. also 12 & 15V £1-49

AUDIO AMPS: mfc40 0.0 50p; l & 2W £1-19; 3W £1-29; 6W...

gates 7400 etc 16p 7413 32p. 7447 £1-25

7470/72 32p 7474/76 39p 7490 63p

7492 69p 74121 49p. & all others in cat. low prices.

NEW 16pin counter/driver 90/47 £2-25 DALO pcb. PEN 69p.

DIL SOCKETS: Professional / gold P.Pins hi or lo Profile 8, 14, 16 Pin 13p

2N3055 33p. four £1. BC107, BC108, BC109 all 7p ea

IN914 3p ZENERS BZY88 8p. 1A RECTS 50v 3½p 400v 5p. BRIDGE 20p

FETS: 2N3819 19p 2N3823E 20p 441GE 25p BC182/3/4 10p

BC212/3/4 11p BCY70 13p BD131/2 35p ea. BFY5V23 15p TIS43 25p

2N2926 0y 7p 2N3053 15p 2N3702/3/4/5/6/7/8/9/10/11 all 9p ea

2N3904/6 14p HEATSINKS 5T/10S 18c/1018 5p. T03: 4YL 29p TV3 14p

CAPACITORS 25V10, 50V100µF 5p. DISCS 4p. PRESETS 5p. CARBON -

POTS 11P. Switch 11P. Dual 5 SP. ULTRASONIC TRANSDUCERS £2-50

FLUORESCENT LIGHTS, 8W, 13V 20V £2-59

Trampus ADD 10% VAT TO PRICES. P&P 10P C.W.O.

electronics P.O. BOX 29, BRACKNELL, BERKS.

GLUM?

SICK OF WAITING FOR COMPONENTS

Try our express service (normally return of post)

Prices very competitive — for example:—

½W 5% carbon film resistors — 1p.

¼W 2% metal oxide — 3½p.

BC 107/8/9	— 10p.	2N 3704	— 13p.
BC 177	— 17p.	2N 3707	— 13p.
2N 1302/3	— 16p.	1N 4001/2	— 6p.
2N 3055	— 53p.	1N 4003/4	— 7p.
2N 3702	— 13p.	1N 4148	— 5p.
2N 3703	— 14p.	1N 5401	— 16p.

SINCLAIR CAMBRIDGE CALCULATOR

Ready to use—only £26-50

PRICES EXCLUDE VAT. 10P P. & P.


Forward 15p. for our illustrated catalogue to:—
DART ELECTRO SERVICES, 24 South Town,
Dartmouth, Devon. Competitive prices and descrip-
tions of hundreds of components, accessories etc.

Name:

Address:

Dimmit

range of light dimmers

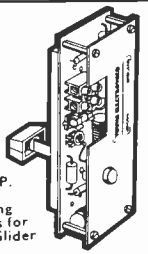


Illustrated is the popular PMSD1000 module. A 1000W professional quality dimmer, linear operation, interference suppression, 60mm slider range; size 12x5x4 cm. Ideal for low cost stage and disco lighting. Used by schools, theatres, studios, etc. Complete with scale plate, fixing screws and full instructions. £6.50 inc. VAT, add 10p P. & P. Also available in 2kV, with separate heatsink.

The Dimmit range includes standard wall mounting models for home and office, etc. Professional modules for use on lamps, heaters, motors, etc. Rotary and Slider control versions. Ratings: 1,000W, 2,000W.

NEW addition to Dimmit range—Model SL800 sound to light converter. Modulates the light in time with sound. Built-in microphone. Just place unit near any sound source—radio, hi-fi, tv, human voice, etc. No connections to speaker required, simple wiring—similar to dimmer. Rating 800 watt. Full instructions. £7.60 inc. VAT, add 10p P. & P. Send 10p for complete illustrated catalogue and price list.

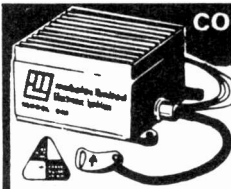YOUNG ELECTRONICS Mail Order Dept.
54 Lawford Road, London NW5 2LN. Telephone 01-267 0201



CONTACTLESS ELECTRONIC IGNITION BY MOBELEC

We break the price barrier with this trouble-free inductive discharge contactless ignition which replaces contact points by a solid-state trigger-head giving high energy spark for excellent cold-weather starting and super-smooth tick-over. Designed for 4 or 6 cylinder neg. earth cars at a price you can afford. Easy to fit, clear illustrated instructions, free fitting kit. State model, make and year. Other Mobelec capacitive discharge E series models available. Mobelec E series for high performance engines. 4 and 6 cylinder NEG. AND POS. EARTH, £22.82. 8 cyl., £24.75. Post free.

FROM ONLY **£13.95** p&p 25p

SILHILL PRODUCTS Dept. PE/6, 226 Mary Street, Birmingham B12 9RJ. Tel. 021-440 3600

would you pay twice the money for only half the performance?

FREE!

32 page booklet Collectors' Guide to 100 Great Records

Which is the best version of Brahms' 3rd Symphony ... or the Rolling Stones at their greatest? It may not be the £2.45 version ... it could be 99p! This outstanding guide, lists Audio's 100 great records—and the reason why ... classic ... rock ... jazz ... pop ...

CARL PALMER of ELP

First—and only—man with a synthesized drum kit.

Build your own HI-FI cabinet

Specially designed equipment storage unit.

MANY OTHER FEATURES—MAY ISSUE

Audio

OUT NOW 25p
THE HI-FI MAGAZINE
FOR LEISURE LISTENING



Practical Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 20p extra. Semi-Display £7 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4H 4AD

SITUATIONS VACANT

TECHNICIANS AND ENGINEERS FOR ST. ALBANS AND LUTON

QUALIFIED OR NOT!

OPPORTUNITIES for challenging work on testing and calibrating valve and solid-state electronic measuring equipments embracing all frequencies up to u.h.f. in Production, Service and Calibration departments.

APPLICATIONS are invited from people of all ages with experience or formal training in electronics and from Ex-Services technicians.

HIGHLY COMPETITIVE SALARIES, negotiable and backed by valuable fringe benefits. Overtime normally available.

GENEROUS RE-LOCATION EXPENSES available in most instances.

CONDITIONS excellent; free life assurance, pension schemes, canteen, social club.

37½ hour, 5-day, working week.

WRITE or phone for application forms quoting reference PE746.



MARCONI INSTRUMENTS LTD,
Longacres, St. Albans, Herts
Tel: St. Albans 59292
Luton Airport, Luton, Beds
Tel: Luton 33866

A GEC-Marconi Electronics Company



COME DOWN UNDER

Here's a once in a lifetime opportunity to work for Australia's leading electronics company specialising in the supply of components to hobbyists and industry. The Dick Smith Electronics Centre, situated in Sydney, is expanding its activities very rapidly and we desperately need staff, both for counter sales and mail orders. Interested?

We want people with experience in this field who will come out for at least two years. In return we will guarantee your return flight (but we know with all the opportunities out here you will never go back).

Pay naturally depends on experience but would be in the vicinity of £3000 p.a. for counter and mail order staff rising to £5000 for those with management experience.

The weather is great, our winter is like your summer. The beaches fabulous. The future unlimited. So please write to Dick himself (airmail of course) giving a brief life story and enclosing a photo if possible. All replies will be treated in strict confidence. Write now to:

**Dick Smith, Managing Director, Dick Smith Electronics Centre,
162 Pacific Highway, Gore Hill, N.S.W. 2065, Australia**

P.S. This advertisement was written by someone who grabbed a similar opportunity three years ago and hasn't looked back since!

SERVICE SHEETS

SERVICE SHEETS, Radio, TV, etc. 8,000 models. Catalogue 15p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS for televisions, radios, transistors, record players, tape recorders, etc., from 5p with free fault-finding guide. Over 10,000 models available. S.A.E. enquiries. Catalogue 20p and S.A.E. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 429066.

MEN!
£70 p.w.
can be yours

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £3,500 + p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or 'phone TODAY, without obligation.

**London Computer Operators
Training Centre**
T58, Oxford House
9-15 Oxford Street, W.1
Telephone 01-734 2874

AUDIO TESTERS

EXPERIENCED

FOR LEADING ELECTRO-
MUSICAL COMPANY

Interesting work with Mixers—
Echo Units—Amplifiers (Valve
and Transistor), etc.

High rates for right man

wem 66 OFFLEY ROAD
LONDON, S.W.9
Phone 01-735 6568

TEST ENGINEERS

Vacancies for young engineers eager
to work in an expanding company
specialising in portable electronic
instruments.

**Levell Electronics Ltd., Moxon St.,
Barnet, Herts. Telephone 01-440 8686**

WANTED

**TOP PRICES PAID
NEW VALVES AND TRANSISTORS**
Popular T.V. and Radio types
KENSINGTON SUPPLIES (B)
367 Kensington Street
Bradford 8, Yorks.

LADDERS

LADDERS. "Special Offer" unvarnished
triples. 9ft 7in closed—23ft 1in extended.
£18-90 delivered. HOME SALES LADDER
CENTRE (PEE2), Haldane (North), Hales-
field (1), Telford, Shropshire. Tel. 0952
586644.

EDUCATIONAL

CITY AND GUILDS EXAMINATIONS

Make sure you succeed with an ICS home study course for C & G Electrical Installations, Telecommunications Technicians and Radio Amateurs. Free details from: International Correspondence Schools, Dept. 730G, Intertext House, London, SW8 4UJ.

COLOUR TV SERVICING

Make the most of the current boom. Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers. Also radio and audio courses. Free details from: International Correspondence Schools, Dept. 730G2, Intertext House, London, SW8 4UJ.

TECHNICAL TRAINING

Get the qualifications you need to succeed. Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self build radio kits. Free details: International Correspondence Schools, Dept. 730G3, Intertext House, London, W8 4UJ.

FOR SALE

TV LINE OUT-PUT TRANSFORMERS
Tidman Mail Order Ltd., 236 Sandycroft
Road, Richmond, Surrey TW9 2EQ
01-948 3702

SEEN MY CAT? 5,000 items, Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

CATALOGUE NO. 18, Electronic and Mechanical Components and manufacturers' surplus. (Credit vouchers value 50p. Price 23p, including post. **ARTHUR SALLIS RADIO CONTROL LTD.**, 28 Gardner Street, Brighton, Sussex.

LIGHTSHOW PROJECTORS from only £17. effect wheels from only £4. Many lightshow bargains at **ROGER SQUIRE'S** (Disco Centre), 176 Junction Road, London, N.19. Tel. 01-272 7474.

SAVE PETROL—Know instantly your m.p.g. with a **BARON M.P.G. Meter**. Model 1b now available, suitable for 12V neg. or pos. earth cars with S.U. electric fuel pump, not P.I. models. Kit complete with all components, P.C. board and 8 I.C.s; requires 1mA meter (not supplied), £10-50 plus 20p P. and P. Please state make, model and year. **BARON ELECTRONICS** (Dept. PE/6), 176 Brookhurst Avenue, Bromborough, Wirral, L63 0PP.

SPECIAL OFFER—Indicators 3015F and G, CD43, CD66, only 95p. Chips 7447 (BCD-7 SEG), £1; IC12 6W amp. £1-50; 743P8U, 55p; BC182, 183, 108, 141, 8p each; MJ3001, £1. 150W *npn*, *npn* photo transistors, 25p. 1N4001 41N4148, 5p. 10A, 150V bridge, £1. Interested? Then get our cat. (10p P.O.) now! **ALPHA ELECTRONICS**, 73 Moorgate, London, EC2. (Mail order only. Prices exclude VAT.)

SINCLAIR STEREO-60 with P.Z.B., etc. Almost completed, requires resistors. Modules guaranteed July '75, £22 o.n.o. Box No. 55.

VALVES, VALVES AND MORE VALVES. Large stocks, many types, 1930 to 1974. S.A.E. for quotation. List 10p. **COX RADIO**, The Parade, East Wittering, Sussex.

£30. Cossor D.B. Oscilloscope 1052. Handbook and spare tube. Phone Bordon Hants 2405.

EXCESS STOCK SALE. TTL, I.C.s and other components. Send s.a.e. for list to M/S A. LENNOX-MARTIN, E.M.S. LTD., 46b Cricklewood Lane, N.W.2.

SUBMINIATURE RELAYS. Coil 100 ohms 4.5-9V d.c. Contacts N.P.C.O. 1A. 24V a.c./d.c. Dimensions 25 x 18 x 10mm. Mounted on P.C. strip, 50p, inc. P. & P., etc. P. D. SMITH, 38 Leasway, Wickford, Essex, SS12 0HE.

SUPERB INSTRUMENT CASES by Bazelli, manufactured from heavy duty PVC faced steel, choice of 30 types, send for free list. **BAZELLI INSTRUMENT CASES**, Dept. 23, St. Wilfrids, Foundry Lane, Halton, LA2 6LT, Nr. Lancaster.

BOOKS AND PUBLICATIONS

Technical Books - Radio & Electronics

Handbook of Tested Transistor Circuits.....	£0-40
Radio Servicing for Amateurs.....	£0-20
Practical Radio Inside Out.....	£0-40
Coil Design and Construction Manual.....	£0-30
Boys Bk of Crystal Sets and Simple Circuits.....	£0-18
Transistor Circuits Manual No. 1.....	£0-15
Transistor Circuits Manual No. 2.....	£0-15
Transistor Circuits Manual No. 4.....	£0-15
Transis Circuits for Radio Controlled Models.....	£0-40
Rad & Electr Colour Codes and Data Chart.....	£0-15
Handbk of Transistor Equiv and Substitutes.....	£0-40
Hi Fi, PA & Disco Amplifier Design Hndbk.....	£0-75
Radio Servicing Problems.....	£0-45
Electronic Circuits for the Amat Photographer.....	£0-60
Handbook of Simple Transistor Circuits.....	£0-35
Modern Transistor Circuits for Beginners.....	£0-40
Sound and Loudspeaker Manual.....	£0-50
Practical Car Radio Handbook.....	£0-30
Radio TV and Industrial Tube & Valve Equiv.....	£0-40
Know Your Oscilloscope.....	£1-70
Television Servicing Vol. No. 1.....	£0-85
Television Servicing Vol. No. 3.....	£0-60
Television Servicing Vol. No. 4.....	£0-85
Using an Oscilloscope.....	£0-70
Servicing Transistor Radio Receivers.....	£0-75
Television Timebase Circuits.....	£1-00

NEW TITLES NOW AVAILABLE

2nd Book of Hi Fi Loudspeaker Enclosures.....	£0-60
Manual of Electronic Circuits for the Home.....	£0-50
Modern Crystal Set Circuits for Beginners.....	£0-35
Electronic Novelities for the Motorist.....	£0-50
2nd Book of Transistor Equiv & Substitutes.....	£0-95
Handbook of Electronic Musical Novelities.....	£0-50
Transistorised Novelities for Hi Fi Enthusiast.....	£0-35
Fault Location Exercises in Rad. & TV Vol.1.....	£0-80
Fault Location Exercises in Rad. & TV Vol.2.....	£1-35
Colour TV Picture Faults.....	£2-50
Practical Transistor Novelty Circuits.....	£0-40
Semi-conductors from A-Z.....	£1-50
Radio Receiver Construction using ICs & Transis.....	£0-60
104 Ham Rad. Proj. for Novice & Technician.....	£1-25
ICs & Transistor Gadgets Construction Handb'k.....	£0-60
Integrated Circuits Equiv. & Substitutes Hbk.....	£0-75

PLEASE ADD 10% FOR POSTAGE & PACKING

FREE lists of other titles avail on request. Send to:

RADIO BOOK SERVICE
Dept A 40 Elwill Way, Beckenham BR3 2RZ

RECEIVERS AND COMPONENTS

STEREO FADERS

78 mm fixing centres. 64 mm travel.

1,000 long Egen moulded slide faders, 10K log stereo, only 39p each including post and V.A.T.

Cash with order to:

CHYMES

P.O. Box 87, Reading, Berks.

UNIT IN SMART ALI CASE, 11 x 11 x 4in., contains 8 silicon diodes, 600V, 20A, 8 SCR's 3 OR 400V 16A, Vinkors, 4 small, 2 large, together with other components, £6 (45p). **M.C. METERS,** 3 assorted 2-3in. £1-15 (27p). **5 FIGURE RESETTABLE COUNTER,** 18/22V, works on 12V, £2-20 (20p). **7400 SERIES ICs,** 10 on panel(9), £1 c.p. **2N8055 MOTOROLA,** 54p post paid. **COPPER CLAD FAX PANELS,** 5 1/2 x 5 1/2in, 6 for 45p c.p., 7 1/2 x 9in, 6 for £1-95 c.p. **FIBREGLASS,** 15 x 3in. 30p c.p. **SMALL UNIT WITH 4 SILICON DIODES,** 650V, 11A, 4 BFY51 with heat sinks plus resistors, 55p c.p. **TAGBOARD** with 2 BCY39, *ppp* 250mA (these are over £1 each new), 4 silicon diodes, resistors, 55p c.p. **VALUPAKS,** P9, 100 assorted s/nica caps, 55p; P11, 100 assorted polystyrene caps, 75p; P13, 10 wire ended neons, 50p, post 10p any number of Paks. Send 10p stamp for list of Valupaks together with computer panels, etc. Refund on purchase.

7LB ASSORTED COMPONENTS, £1-65 c.p.
8LB FIRSTS COMPUTER PANELS, £1-65 c.p.
8LB SECONDS COMPUTER PANELS, £1-40 c.p.

J.W.B. RADIO

2 BARNFIELD CRESCENT, SALE, CHESHIRE M33 1NL
Postage in brackets. Mail order only.

R.T. SERVICES

(MAIL ORDER ONLY)

77 Hayfield Rd., Salford 6, Lancs.

Veroboard 6 x 5 0-1 Matrix, 2 for £1. 4 x 4 1/2 0-1 Matrix, 4 for £1. 12 x 3 1/2 0-15 Matrix, 75p each.

Mullard A.M. Module. I.F. Strip, LP1166, £1-10 inc. P.P.

FM Tuner with R.F. Stage and A.G.C., 3 transistors, neg. earth, 2 1/2 x 2 x 1 1/2 in with circuit, £1-37 1/2 inc. P.P.

Crouzet Geared Motors, 30 or 60 r.p.m. **Now,** £1-54 inc. P.P.

UHF TV Tuners. Transistorised, £1-65 inc. P.P.

250N Miniature Uni-selectors with base, £3 inc. P.P.

Transformers. 7.5V + 7.5V 1/4A, 88p inc. P.P. 12-0-12V, 100mA, 90p inc. P.P. 9-0-9V, 100mA, 90p inc. P.P. 29V 50mA, 70p inc. P.P.

Brand new Boxed Rola Celestion Reentrant Speakers SD 25 with 100V line transformer fitted 15Ω without transformer £14 inc. P.P.

Transformer. 45-0-45V, approx. 2 amp, £2-50 inc. P.P.

P.C. Board. S/S, 5 1/2 x 5 1/2in, 10 for 70p inc. P.P. Panel with 2 SN7490, 2 SN7441 counting circuit with end connector, £2-20 inc. P.P.

Transistorised Timer. Variable delay. 110 or 250V A.C. input. With instructions. Brand new, £2 inc. P.P. Size 3" x 2" x 2".

Woods 5" fans. Very good quality. £3-30 inc. P.P.

Electrolytic Capacitors, 4,000 MF, 50 VV, 4 1/2" x 1 1/2" 75p. inc. PP.

DRY REED INSERTS

Overall length 1.85" (Body length 1.1"). Diameter 0.14". Max. ratings 250V D.C. and 500 mA. Gold clad normally open contacts. 69p per dozen; £4-12 per 100; £20-25 per 1,000; £275 per 10,000. VAT and post paid.

G.W.M. RADIO LTD.

40/42 Portland Road, Worthing, Sussex 0903 34897

MICROCIRCUIT ELECTRONICS

SYSTEM 30 HI-FI AUDIO MODULES

MEA30-2: 30W r.m.s. per channel stereo amplifier (s/c protection) .. £10-00

PS22-2: Twin stabilised heavy-duty (3-5A) power supply .. £6-80

Suitable Transformer .. £3-00

Simple power supply kit .. £4-00

MEP-32: Stereo pre-amp with rumble and variable scratch filters, full range tone controls, and 4 inputs (including magnetic) .. £13-00

DATA: 25p (not stamps, price refundable on purchase of any module)

All prices include post and VAT.

Mail Order Service Only, Orders to:

MICROCIRCUIT ELECTRONICS (EI)

23 Pages Lane, LONDON N10 1PU

PRECISION POLYCARBONATE CAPACITORS

ALL HIGH STABILITY—
EXTREMELY LOW LEAKAGE

440V AC (±10%)	63V Range	±1%	±2%	±5%
0.1μF (11' × 1')	50p	0.47μF	50p	46p 38p
0.22μF (11' × 1')	50p	1.0μF	60p	56p 46p
0.33μF (11' × 1')	82p	2.2μF	80p	65p 55p
0.47μF (11' × 1')	71p	4.7μF	£1.80	£1.05 85p
0.5μF (11' × 1')	75p	6.8μF	£1.64	£1.29 £1.09
0.68μF (2' × 1')	80p	10.0μF	£2.00	£1.40 £1.40
1.0μF (2' × 1')	91p	15.0μF	£2.75	£2.15 £1.90
2.0μF (2' × 1')	£1.22			

TANTALUM LEAD CAPACITORS—Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8μF at 15V/25V or 35V; 10.0μF at 16V/20V or 25V; 22.0μF at 6V/10V or 16V; 33.0μF at 6V or 10V; 47.0μF at 3V or 6V; 100.0μF at 3V. ALL at 10p each, 10 for 95p, 50 for 24.

TRANSISTORS—All brand new and marked, full spec. devices:

BC107	9p	BC182/182L	11p	BFY50	20p
BC108	9p	BC183/183L	11p	BFY51/52	20p
BC109	9p	BC184/184L	12p	OC71	12p
AF178	80p	BC212/212L	14p	2N3055	50p

POPULAR DIODES—All brand new and marked: 1N914 8p, 8 for 45p, 18 for 20p; 1N914 8p, 6 for 45p, 14 for 90p; 1S44 5p, 11 for 50p, 24 for £1; 1N4148 5p, 6 for 27p, 12 for 48p.

LOW PRICE ZENER DIODES—400mW, Tol. ± 5% at 5mA. Values available: 4.7V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13.5V, 15V, 16V, 27V, 30V. ALL at 7p each, 6 for 39p. SPECIAL OFFER: 6 off each voltage (90 Zeners) £4.95.

RESISTORS—High stability, low noise carbon film 5%, ¼W at 40°C, ¼W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (230 resistors) £5.

SILICON PLASTIC RECTIFIERS—1.5 amp, brand new wire ended DO27: 100 P.I.V. 7p (4 for 26p); 400 P.I.V. 8p (4 for 30p); 800 P.I.V. 11p (4 for 42p).

BRIDGE RECTIFIERS—2½ amp: 200V 40p; 350V 45p; 600V 55p.

SUBMINIATURE VERTICAL PRESETS—0.1W only: ALL at 3p each: 100Ω, 220Ω, 470Ω, 680Ω, 1kΩ, 2.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 22kΩ, 47kΩ, 100kΩ, 1MΩ.

PLEASE ADD 10p POST AND PACKING ON ALL ORDERS BELOW £5. ALL EXPORT ORDERS ADD COST OF SEA/AIRMAIL.

PLEASE ADD 10% V.A.T. TO ORDERS Send S.A.E. for lists of additional stock items. Wholesale price lists available to bona fide companies.

MARCO TRADING

Dept. E.8, The Maltings, Station Road,
Wem, Shropshire
Tel.: Nantwich (Cheshire) 63291 (STD 0270)
(Proprs.: Minicost Trading Ltd.)

BRAND NEW COMPONENTS by return Electrolytics 16V, 25V, 50V—0.47, 1, 2.2, 4.7, 10MF, 4p, 22, 47, 4½p (50V), 5p; 100, 5½p (50V, 7p); 220, 6p (50V, 9p). Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V, 22/16V, 47/6V, 100/3V, 8p. Mylar Film 100V, 0.001, 0.002, 0.005, 0.01, 0.02, 2½p; 0.04, 0.05, 3p. Polystyrene 63V E12 series 10pF—1000pF, 2p; 1.200pF—10,000pF, 3p. Miniature High-stab. resistors 5%, E12 series carbon film ¼W, 1Ω—10MΩ, (10% over 1MΩ). Metal film ¼W, 10Ω—2.2MΩ, and 1W, 27Ω—10MΩ all 1p each. Postage 8p. The C.R. SUPPLY CO., 127 Chesterfield Rd., Sheffield, S8 0RN.

5 N-CANAL FETS. Type 3819E (2N3819) for £1 (inc. VAT). Full spec. transistors complete with circuit details for building voltmeter, timer, ohmmeter, etc. For complete list of FETs and other transistors available send 10p P.O. REDHAWK SALES LTD., 45 Station Road, Gerrards Cross, Bucks. Mail Order Only.

COMPONENTS GALORE. Pack of 500 mixed components. Manufacturers' surplus plus once used. Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers, etc. Send £1 + 10p P. & P. C.W.O. to: CALEDONIAN COMPONENTS, Strathore Road, Thornton, Fife.

RADIO & TELEVISION AERIAL BOOSTERS £2-95, five television valves 45p. 50p bargain transistor packs, bargain £1 resistor and capacitor packs, UHF-VHF televisions £7-50. Carr. £1-50. S.A.E. for 3 leaflets. VELCO ELECTRONICS, Bridge St., Ransbottom, Bury, Lancs.

TUNBRIDGE WELLS. Components from TELESERVICE, 108 Camden Road, Tunbridge Wells, Kent. Telephone 31803.

SILICON TRANSISTORS. Unmarked, untested, 25 for 35p. Silicon diodes, tested, unmarked, 50V P.I.V., 150mA, 30 for 35p. I.C.s 74 series untested, unmarked 25 for 35p. Why not try a pack? One pack of each for 95p. SELECTED SEMICONDUCTORS, 17 Coniston Way, Elm Park, Hornchurch, Essex.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO., P.O. Box 5, Frome, Somerset. Immediate cash settlement.

MISCELLANEOUS

DON'T LOOK

unless you can resist the temptation to get these super 'attention-getters':

★ **POCKET-SIZED MAXI-VOLT** Big ¼ inch Spark Generator (instant 15,000 volts!) Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz (85g). Send £1.35 for your Maxi-volt now!

★ **UNIQUE TRANSMITTER/RECEIVER KIT.** No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send £5-90 for yours now!

★ **PSYCHEDELIC MINI-STROBE KIT.** Take a pocket-sized lightning storm to Disco's and Parties. "BRAIN-FREEZE" EM with vari-speed stop-motion flashes. Includes super case, too. Send £2-20 now! (All prices include VAT, packing & postage)

Send remittance to:
BOFFIN PROJECTS
4 Cunliffe Road, Stoneleigh
Ewell, Surrey
(Mail order U.K. only)
Or for more details, send 20p for lists, plus free design project sheet

BUILD THE TREASURE TRACER MK III Metal Locator



- Varicap tuning
- Britain's best selling metal locator kit
- Weights only 22oz
- Speaker and earphone operation
- Knocks down to only 17in
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- As seen on BBC-1 & BBC-2 TV

Send e.s.a. for leaflet

Complete Kit Post: 35p **£9-80** Built, tested and guaranteed Post: 35p **£13-75**

MINIKITS ELECTRONICS, 35g LANGLEY DRIVE, WANSTEAD, LONDON E11 2LN (Mail Order only)

ENAMELLED COPPER WIRE


S.W.G.	1lb Reel	½lb Reel
10-14	£1-40	80p
15-19	£1-40	80p
20-24	£1-43	83p
25-29	£1-52	91p
30-34	£1-57	97p
35-40	£1-69	£1-04

Please add 10% to all above prices to cover VAT. The above prices cover P. & P. in U.K. Supplied by **INDUSTRIAL SUPPLIES** 102 Parrswood Rd., Withington, Manchester 20 Telephone No. 061-224 3553

PRINTED CIRCUIT MANUFACTURERS offer any P.E. Project Print ready drilled, One Price 65p. C.W.O. Any P.C. work undertaken. For estimate by return post, send basic circuit, print design or print master. State quantity required. Print design, art work, photography undertaken. Orders, estimates, write or phone: W.K.F. ELECTRONICS, Dept. P.C., Welbeck Street, Whitwell, Nr. Workop, Notts., S80 4TW. Tel. Whitwell (Derbys.) 695.


MORE RANGES FOR LESS MONEY!

AC/DC Multimeter type U4324




A-DC 0.06-3A-6 Ranges
A-AC 0.3-3A-5 Ranges
V-DC 0.5-1200V-9 Ranges
V-AC 3-300V-8 Ranges
Frequency in the range of 45 to 20kHz. Resistance 500 ohm to 5 Mohm—5 ranges. Decibel: -10 to +12dB. Accuracy ±2.5% D.C. ±% a.c. Dimensions: 167 × 98 × 63mm
Only **£8-00**

SUPERTESTER 680 RICE

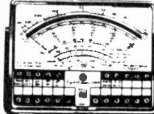

10 Fields—80 Ranges! Plus a lot of accessories for measurements of 500A-AC 100 A/DC Temperature—50C to -200C Magnetic fields up to 15 KGauss-Phase indicator EHT 25KV Electronic Volt/Ohm-meter Transistor Diode Tester, etc.
Dimensions 128 × 95 × 32 mm
300 grams 20KOhm V Accuracy 1% DC Ask for free catalogue
£18-50 Accessories Extra

ALPHANUMERIC NIXIE TUBES B791

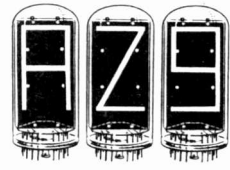

The Alphanumeric NIXIE tube has the ability to display all the letters of the alphabet, numerals 0 thru 9 and special characters in a single tube. From the stand point of both readability and electrical characteristics the Alpha numeric NIXIE tube provides many unique benefits including: * All d.c. operation * Uniform continuous line characters of equal height * Memory with simple solid state drive circuits * Readability in high ambient light * 200 footcandle brightness * Long life with no loss of brightness * Character height 2½in.
Price only 99p each plus 16p P.P.

Add 10% VAT to all items - 35p P&P
ELECTRONIC BROTHERS LTD.
49-53 Pancras Road London NW1 2QB Tel 837 7781

NEW LENSES OPTIKIT L5 5 convex lenses for photoelectric devices, detector beams, tachometers, sensors. 1 off each diameter/focal length 7/7, 14/12, 21/18, 26/23, 45/50mm, £2-20.

LIGHT SOURCES, DETECTORS: MV54 miniature (2mm) red LED: MLED500-TO-92 PC mounting red LED: MLED92 TO-92 infrared emitter; 2N5777 high sensitivity silicon photo-darlington amplifier. Response Time 200 sec, 25V max. Superior to CdS cell, OC71. MRD150 miniature (2mm) silicon phototransistor. Fast response 2 sec, 40V max.

MV54	22p	44p	£1-10	£2-09	£3-52
MLED500	22p	44p	£1-10	£2-20	£3-74
MLED92	33p	66p	£1-54	£2-86	£6-60
2N5777	55p	£1-10	£2-53	£4-62	£9-90
MRD150	60p	£1-32	£3-19	£6-16	£14-85

ULTRASONIC TRANSDUCERS for remote control 40kHz Tx/Rx pair £3-85.
CIRCULAR POLARISERS for glare reduction—enhance contrast ratio from LED display, nixies, scope. HRC7P red, HAC24 amber, HGCP24 green, HNC37 neutral. 50mm × 50mm 66p; 75mm × 75mm £1-21; 150mm × 150mm £4-40.

CROFON 1610 64 strand plastic light conduit, bundle dia. 1.8mm, O.D. 3.3mm. 1m £1-32; 5m £5-50; 10m £10-45; 25m £22.

PLASTIC OPTICAL MONOFIBRE for easy light circuitry, displays, effects. Diameter 0.5mm—FP20; 1.0mm—FP40; 1.5mm—FP60. 83p
200m 5 10 25 50 100 200
FP20 £1-32 £2-20 £3-85 £6-60
FP40 £1-10 £1-98 £3-85 £6-60 £12-10 £22-00
FP60 £1-98 £3-85 £7-70 £13-20 £24-20 £44-00

OPTIKIT 103: Experimenter pack, 2 metres Crofon 1610 + 5m each FP20, FP40, FP60—£4-84.

FIBROFLEX SIZE 1: Glass light conduit, 440 Strand, bundle dia. 1.14mm, O.D. 3.3mm (p.v.c. jacket). 5m £2-97; 10m £3-85; 25m £6-60; 50m £11-00; 100m £17-05, all inc. 10 ferrules + epoxy resin for terminations.

MARE'S TAILS: Decorative effects. 7,000 fibres in 18mm O.D. ferrule. Professionally finished. 22in diameter in use. Add lamp, stand, cover to make Fibre Optic Lamp. Eye catching in boardroom, hall or foyer.

NEW LOW PRICE £10-45 each.
All prices include p. & p. VAT and delivery. Send 9in × 6in S.A.E. for details.

FIBRE OPTIC SUPPLIERS (Dept. PE), P.O. Box 702, London W10 6SL

Build your next project in a BEC (Book end chassis)



New improved with alloy trim on bottom of all cabinets. Now in easy to assemble kits.

GB3 (illustrated) 14 x 9 x 4 £5.44 incl VAT and postage. Other sizes SAE with enquiries. Callers welcome after 10 a.m.

P.C. BOARDS & PANELS

We specialise in small runs of P.C. Boards and screen printed or anodised aluminium panels. From 1 to 500 send sketch or negative and we will send you our quotation.

H.M. ELECTRONICS, 275a Fulwood Rd., Sheffield S10 3BD (Behind Bloomhill P.O.)



MICROJET WELDER
A TINY FLAME UP TO 5000°F!
WELDS BRAZES SOLDERS

A precision tool using a combination of butane and compressed oxygen or micro-nox. Gives a flame of pencil lead thickness. Adjustable temperatures up to 5,000°F. Lights instantly, no priming. Cuts metals, welds, brazes and solders, etc., gold and silver. Ideal for electrical work, jewelers, clockmakers, silversmiths. Up to 40 minutes' operation using fuel supplied. Replacement set of 2 micronox and 1 butane cylinders £1.50 extra inc. post. Complete with instructions.

Our price £13.25 + 35p p. & p. Send £13.60.
JOHN DUDLEY & CO. LTD., Dept. FE9
301 Criclewood Lane, Child's Hill, London, N.W.2
Tel. 01-458 3917. Callers welcome.

LOUDSPEAKER KITS for hi-fi stereo by Helme, the speaker kit people, all complete with full instructions. Prices from as little as £14.95 per pair including VAT! Send now for free illustrated brochure and stockist list to: HELME AUDIO PRODUCTS LTD., Dept. PEB-74, Summerbridge, Harrogate, Yorkshire. Tel: Darley 279.

HARDWARE SUPPLIES—Sheet aluminium individual sizes or standard packs, drilled to spec. Screws, nuts, washers, etc., Fascia panels in aluminium individual requirements. Printed circuit boards, one-off or small runs. Printed circuit drafting tapes, etc., 7p for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwks., CV37 9JP.

CLEARING LABORATORY, scopes, V.T.V.M.'s, V.O.M.'s, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, MC relays, components, etc. Lower Beeding 236.

AUDIOSCAN, the "do-it-yourself" speaker mail-order specialists. High fidelity speaker kits, chassis units, sound absorbent, grille fabric and much more. Send s.a.o. for bargain list to: AUDIOSCAN, Dept. PE2, 4 Princes Square, Harrogate, Yorkshire.

METER REPAIRS. Ammeters, voltmeters, multi-range meters, etc. Send to: METER REPAIRS, 39 Chesholm Road, London, N16 0DS.

SLOW SPEED MOTORS required (about 1 r.p.m.) any quantity considered. Phone Mr. SMITH, 061-633 3527.

SYNTHESISER BUILDING? Using Dewtron modules? VCO2, SHE1, OFT, PPA, modules on boards, one year old. Hardly used. £30 o.n.o. Also 3 octave keyboard. Box No. 54.


Build the Mullard C.C.T.V. Camera

Kits are now available with comprehensive construction manual (also available separately at 76p)

SEND 5" x 7" S.A.E. FOR DETAILS TO:
CROFTON ELECTRONICS
15/17 Cambridge Road, Kingston-on-Thames, Surrey KT1 3NG

Digital Clock Kits

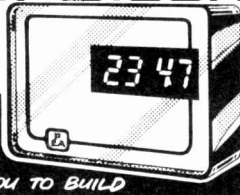SPACE RESEARCH BRINGS YOU A DIGITAL CLOCK - WITH NO MOVING PARTS - FOR YOU TO BUILD



KIT 0 All components, including P.C.B. designed for easy home assembly. Bright and clear digits. Tough A.B.S. plastic case with contrasting front panel.

PRICE: £23.00 plus £2.30 VAT/Total £25.30 inc. post./pkg
Only our advanced design techniques make this low price possible. Kits are tested before they leave us and are covered by the P.E.A. money back guarantee.



Please send me details of your clock kits

NAME _____

ADDRESS _____

P.E.A. Ltd.
35 High St. WELWYN, Herts. AL6 9EE

OSMABET LTD.

We make transformers amongst other things.

AUTO TRANSFORMERS, 110/200/220/240V. 30W, £1.70; 50W, £2.40; 75W, £2.85; 100W, £3.80; 500W, £10.80; 750W, £14.25; 1000W, £18.00, etc.

LOW VOLTAGE TRANSFORMERS
Prim. 200/240V a.c. 6.3V 1.5A, £1.80; 3A, £1.60; 6A, £2.55; 12V 1.5A, £1.50; 3A, £2.55; 6A CT, £3.40; 12V 1.5A CT, £2.55; 24V 1.5A CT, £2.65; 3A CT, £2.45; 6A, £4.80; 8A, £7.35; 12A, £10.85; 40V 3A CT, £4.60; 50V 6A CT, £18.50; 25V 2A-25V 2A, £4.90; 12V 4A + 12V 4A, £4.90.

LT TRANSFORMERS TAPPED SEC. Prim. 200/240V 0-10-12-14-16-18V 2A, £2.60; 4A, £3.75; 0-12-15-20-24-30V 2A, £3.40; 4A, £4.60; 0-5-20-30-40-60V 2A, £2.40; 2A, £4.60; 0-40-60-80-80-100-110V 1A, £4.90.

MIDGET RECTIFIER TRANSFORMERS.
For FW rect. 200/240V a.c. 0-0-9V 0.3A; 12-0-12V 0.25A; 20-0-20V 0.15A, 6V 0-5A + 6V 0-5A, 9V 0-3A + 9V 0.35A; 12V 0-25A + 12V 0-25A or 20V 0.15A + 12V 0.15A at £1.65 each; 9-0-9V 1A, £1.35; 12-0-12V 1A or 20-0-20V 0.75A £1.50 each.

MAINS TRANSFORMERS
Prim. 200/240V a.c. TX6 sec. 425-0-425 500 Ma, 6.3V CT 6A, 6.3V CT 6A, 0-5-6-3V 3A, £18.50; TX1 425-0-425V 250 Ma, 6.3V CT 4A, 6.3V CT 4A, 0-6-6-3V 3A, £9.75; MT3 Prim. 0-110-240V sec. 250V 100 Ma, 6.3V 2A, £18.70.

O/P TRANSFORMERS FOR POWER AMPLIFIERS
P.P. sec. tapped 3-8-15ohms, A-A 6-6K 0 30W, £6.70; A-A 3K 0 50W, £9.00; 100W (EL34 KT88, etc.), £15.75; tapped Multi o/p 10W £3.

G.E.C. MANUAL OF POWER AMPLIFIERS
Covering valve amplifiers of 30W to 400W 85p.

LOUDSPEAKERS FOR AMPLIFIERS
BAKER 25W, £7.60; 35W, £9.40; HI-PI Major Module 20W w/tweeter Xover, £11.80; Baker speaker lets: FANE 50W, £10.50; 60W, £13.50; HI-PI speakers, EM1 bass 12 x 8in 3 or 15 Q, £2.00; 3in 8 Q, £1.15; 7 x 4in 15 Q, £1.60; 8 x 5in 3, 4, 15, 25 or 80 Q, £1.75 each.

LOUDSPEAKERS
2 1/2in 8, 16 or 75 Q, 2 1/2in 8 or 25 Q, 3in 3, 8, 25 or 35 Q, 3 1/2in 8, 15 or 50 Q 90p each; 3in 3, 8 or 25 Q, 5 x 3in 3 or 8 Q, £1.05; 7 x 4in 3 or 15 Q, 6 1/2in 3 Q, £1.25; 10 x 6in 3 Q, £1.50.

SPEAKER MATCHING TRANSFORMERS
12W 3 to 8 or 15 Q up or down, £1.20

"INSTANT" BULK TAPE/CASSETTE ERASER
Instant erasure, any diameter tape spools, cassettes, demagnetises tape heads. 200/240V a.c. £3.25.

CONDENSERS
Paper block 4mf 800V, 75p; Electrolytic 1000mf 350V, 50p; 200 + 100 + 100mf 350V, 50p.

Carriage and VAT on all orders.

S.A.E. ENQUIRIES-LISTS, MAIL ORDER ONLY
46 Kenilworth Road, Edgware, Middx. HA8 9YG
Tel. 01-958 9314

RHYTHM GENERATOR

COMPONENT KITS FOR THESE EXCITING PROJECTS
4p STAMP BRINGS DETAILS

SYNTHESISER

SEMICONDUCTOR DEVICES

AC176	24p	HIGH VOLTAGE TYPES	3p
BC182	9p	MPSL01 120V/300mW	3p
BC184	11p	MPSL51 100V/300mW	4p
BC204	11p	Complementary Pair	3p
BC209C	11p	MPSU7 100V/1W	69p
BC213	9p	MPSU7 100V/1W	85p
BC213L	15p	Complementary Pair (3 wats with H/S)	£1.50
2N2905	27p	SDT9203 100V/100W	£1.50
2N2219	22p		
2N3819	46p		
MPF111	26p		

SIGNAL DIODES

IN914	5p
1N510	12p
1N570	12p
1N67	12p

NOISE DIODES

Z11	53p
Z1M(w/b)	£1.20

RECTIFIERS

1N5401	21p
REC41A21	20p
REC70	45p

V. REGULA-TORS

uA723	£1.80
uA7815	£2.04
MV15	£2.20

DIGITAL I.C.'s

74001	39p	7473N	48p
7402N	38p	7475	63p
7404N	27p	7476N	49p
7410PC	24p	7489j	£6.60
7420N	24p	7493PC	85p
7430PC	23p	74121j	85p
7447PC	89p	74150N	£2.10

HIGH VOLTAGE TYPES

MPSL01	120V/300mW	3p
MPSL51	100V/300mW	4p
Complementary Pair		3p
MPSU7	100V/1W	69p
MPSU7	100V/1W	85p
Complementary Pair (3 wats with H/S)		£1.50
SDT9203	100V/100W	£1.50

LINEAR I.C.'s

741CS	37p
748CS	48p
ML3046P	75p
SG3402N	£1.74
SG3402T	£1.74
SG1495D	£2.90
MFC6040	

ZENERS BZY88

3.3	3.6	3.9	5.1	6.2
7.5	11.0	12.0	all 22p	
BZX61 SERIES				
11.0	12.0	all 27p		

ALL ITEMS LISTED ARE EX-STOCK AT TIME OF GOING TO PRESS

1K Q	25k Q	10k Q	50k Q	42p each
CARBON: 470	10k Q	470k Q	100 Q	11p each
CERMET	100; 500; 1K Q	25k Q	10k Q	50k Q
TRIMMER 15T	10k Q	10k Q	£1.20 each	
SEMI-PRECISION W/W POT.	52p			

POTENTIOMETERS

MIDG. MOULDED CARBON	24mm dia.	10k Q	25k Q	50k Q	100k Q	1M
LOG.	10k Q	25k Q	50k Q			

GANGED

10k Q	10k Q	10k Q	10k Q
5k Q	10k Q	10k Q	10k Q

MIDG./W.C. SWITCHES

28mm dia.	1P 12W	2P 6W	3P 4W	4P 3W	43p each
-----------	--------	-------	-------	-------	----------

WAKA TYPE

E12, E24 series from 10R to 1M Q	10R to 1M Q	10R to 1M Q	10R to 1M Q
E12, E24 series from 10R to 1M Q	10R to 1M Q	10R to 1M Q	10R to 1M Q

MINIATURE PRESETS

CERMET: 100; 500; 1K Q	25k Q	10k Q	50k Q	42p each
CARBON: 470	10k Q	470k Q	100 Q	11p each

CARBON: 470

10k Q	470k Q	100 Q	11p each	
CERMET	100; 500; 1K Q	25k Q	10k Q	50k Q
TRIMMER 15T	10k Q	10k Q	£1.20 each	
SEMI-PRECISION W/W POT.	52p			

CAPACITORS

Tubular Electro.	25V, 25uF, 47uF, 100uF, 16p, 470uF, 29p
1000uF, 46p	5000uF, 46p
1000uF, 57p	63V, 10uF, 22p
100uF, 24p	

PRINTED CIRCUIT ELECTROLYTIC

4.7/40V	10/63V	22/40V	47/40V
13p each	470/16V	23p each	

HIGH RIPPLE TYPE

3300uF, 63V	£2.20
-------------	-------

C280E SERIES

0.01; 0.015	4p
0.022; 0.033; 0.047	5p
0.068	5p
0.1; 0.15; 0.22	6p
0.33	9p
0.47	10p
0.68	14p

BEAD TANTALUMS.

0.1; 0.22; 0.47; 1.0	2.2; 4.7 all at 35V
10/6.3; 10/16; 10/25	22/16; 47/16.3; 100/3
	18p each


POLYSTYRENE

10; 47; 470	6p
680; 1.000; 1.500;	3.300
10,000	7p


EATON AUDIO

P.O. BOX 3, ST. NEOTS HUNTINGDON PE19 3JB

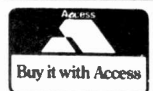TERMS: MAIL ORDER ONLY. C.W.O., Cheques or P.O.'s payable to Eaton Audio. Orders over £5 free of P.&P. Otherwise please add 10p in the £1.



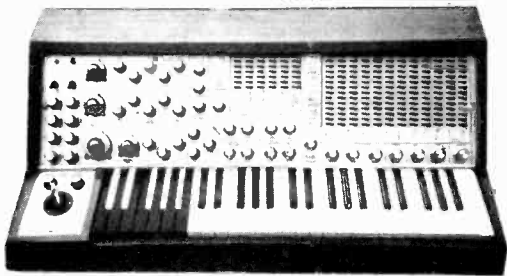BUILD A CHORDING PROFESSIONAL SYNTHESISER



The Synthesiser shown above is the Dewtron "Apollo" A.1. which we sell ready-built to professionals. Believe it or not, it uses the SAME precision modules as we sell to you, the Constructor, to build any kind you like. The revolutionary Modumatrix system of routing makes old-fashioned patching a thing of the past. VCO-2 voltage-controlled oscillator module has accurate built-in log-law for chording and other professional effects. 3 and 4 octave keyboards and contacts. **VCO-2 STABLE, PRECISION V/C OSCILLATOR** gives SINE, TRIANGULAR AND SQUAREWAVE outputs, 1 volt/octave voltage control. £24 each or £27 each 2 or more matched. **SHE-1 SAMPLE, HOLD AND ENVELOPE MODULE** gives variable attack, sustain, touch sensitive playing when used with VCO-2 signals. £17. OFT-1 chording module £9. Modules (except VCO-1) guaranteed two years.

With over 7 years' unblemished reputation in these pages, Dewtron continues to lead in new technical developments in electronic sound effects! Ask any of our customers. See our products in the music stores, too. Suppliers of special equipment to leading groups. Our modules are used in professional equipment by other manufacturers and in our own built synthesisers, e.g. "Gipsy" G.I. Send 15p for full catalogue of our famous musical effects.

D.E.W. LTD.

254 Ringwood Road, FERNDOWN, Dorset BH22 9AR

using **Dewtron** (Regd. Trademark)
PROFESSIONAL MODULES

LATEST ADDITIONS INCLUDE PITCH-TO-VOLTAGE AND SEQUENCER MODULES! AND MANY OTHERS.

CASH SAVINGS

by buying modules and parts in bulk!

All modules are available separately:

Ring Modulator RM2, £8. Voltage-controlled Oscillator VCO1, £10-50, giving sawtooth and square-wave outputs. Envelope shapers, ES1, self-triggered or ES2 keyboard-triggered, either type £13. White noise type WN1, £7. Voltage-controlled amplifier VCA1, £10. Voltage-controlled selective amplifier (filter for waa-waa, etc.) SA1, £13. Voltage-controlled Phase PH1, £17. Automatic Announcement Fader module for fading of music by microphone announcement, AF1, £10. etc., etc. **ALL MODULES ARE BUILT, TESTED AND SEALED FOR LONG LIFE.** Simply connect coloured wire connections as per easy instructions, build cabinet and wire in controls and patchboard connections! Joystick controls £5-50. REVERB Module and spring unit £15. V.A.T. 10% extra. V.A.T. paid orders over £75.



BAKER 12" MAJOR £11-55

30-14,500 cps. Double cone woofer and tweeter loudspeaker. Baker ceramic magnet assembly, flux density 145,000 gauss. BASS RESONANCE 40 cps 20 watt RMS.

MAJOR MODULE KIT £14-85

30-17,000 cps. woofer, tweeter, crossover and baffle as illustrated. Size 19in x 12 1/2in.

NOTE—When ordering state 3 or 8 or 15 ohms.

BAKER LOUDSPEAKERS 100% BRITISH MADE

Regent 12 in. 15W £10-45	Superb 12 in. 20W £18-70	New Group 60/12
Major 12 in. 20W £11-55	Group 25 12 in. 25W £10-45	12 in. 50W
Deluxe 12 in. 15W £13-20	Group 35 12 in. 35W £11-55	30-16000 cps. £17-60

BAKER LOUDSPEAKER CO., BENSHAM MANOR PASSAGE

THORNTON HEATH, SURREY Tel. 01-684-1665

PRICES INCLUDE VAT. HI-FI ENCLOSURE PLANS 42p



W.H.M. 20W AUDIO POWER AMPLIFIER

involves radical departures in conception.

- ★ Class A performance with Class B economy.
 - ★ T.H.D. < 0.05% at all frequencies and power levels.
 - ★ No crossover distortion.
 - ★ Unsurpassed stability into reactive loads.
- £7-28 + VAT. £15 per stereo pair inc.
Full spec. on written request.

Sydney House, 35 Villiers Road, Watford

WORLD RADIO & T.V. HANDBOOK 1974

A COMPLETE DIRECTORY OF
INTERNATIONAL RADIO & T.V.

Price £3-20

SIMPLE SINGLE CHANNEL RADIO CONTROL by R. H. Warring. Price £1-60.

SERVICING WITH THE OSCILLOSCOPE by G. J. King. Price £1-90.

TRANSISTOR AUDIO AND RADIO CIRCUITS by Mullard. Price £1-90.

VIDEO RECORDING RECORD AND REPLAY SYSTEMS by G. White. Price £3-45.

IMPROVING YOUR HI-FI by J. Earl. Price £3-20.

ELECTRONIC HOBBYIST'S I.C. PROJECTS HANDBOOK by B. Brown. Price £1-50.

THE PYE BOOK OF AUDIO by Pye Ltd. Price £1-10.

HOW TO FIX TRANSISTOR RADIOS AND PRINTED CIRCUITS by L. C. Lane. Price £1-70.

RADIO TECHNICIAN'S BENCH MANUAL by H. W. Hellyer. Price £3-20.

THE MAZDA BOOK OF PAL RECEIVER SERVICING by D. J. Seal. Price £4.

ELECTRONIC SYSTEMS FOR RADIO, T.V. AND ELECTRONICS MECHANICS by R. Lewis. Price £2-50.

* ALL PRICES INCLUDE POSTAGE *

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books


19-21 PRAED STREET
LONDON W2 1NP

Phone 01-723 4185

Closed Saturday 1 p.m.

FREE!

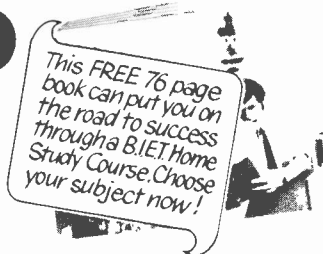Over 150 ways to engineer a better future



This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!

HIGHER PAY **A BETTER JOB**
SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained... a view echoed by two colleagues who recently commenced the course". - Student D.L.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects". - Student J.A.O., Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased tenfold!". - Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to **B.I.E.T. Dept. BPE01, Aldermaston Court, Reading RG7 4PF.**

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.

CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

<input type="checkbox"/> MECHANICAL Society of Engineers— A.M.S.E. (Mech.) Institute of Engineers & Technicians (A.M.I.E.) CITY & GUILDS Gen. Mech. Eng. Maintenance Eng. Welding Gen. Diesel Eng. Sheet Metal Work Eng. Inspection Eng. Metallurgy	<input type="checkbox"/> DRAUGHTSMANSHIP Institute of Engineering Designers (A.M.I.E.D.) General Draughtsmanship Elec. Draughtsmanship Architectural Technical Drawing	<input type="checkbox"/> A.B.T. Clerk of Works Construction Surveyors Institute L.C.S.I. CITY & GUILDS General Building (all branches) Heating & Vent. Inst. Clerk of Works Site Surveying Health Engineering Road Construction Quantities Estimates Hydraulics Structural Eng.
<input type="checkbox"/> ELECTRICAL & ELECTRONIC Society of Engineers— A.M.S.E. (Elec.) CITY & GUILDS Gen. Electrical Engineering Electrical Installations Electrical Maths Computer Electronics Electronic Eng. Practical Radio & Electronics (with kit)	<input type="checkbox"/> RADIO & TELECOMMUNICATIONS CITY & GUILDS Radio, TV Electronics CITY & GUILDS Telecom. Gen. Radio & TV Eng. Radio Amateurs Exam Radio Servicing TV Servicing Colour TV	<input type="checkbox"/> GENERAL Agricultural Eng. Court. of Eng. Institutions Farm Science Plastics
<input type="checkbox"/> MANAGEMENT & PRODUCTION Institute of Cost & Management Accnts. Computer Programming Works M'nt. Work Study Gen. Production Eng. Estimating & Planning Storekeeping Management Skills Quality Control	<input type="checkbox"/> AUTOMOBILE & AERONAUTICAL Institute of the Motor Industry A.M.I.I. M.A. IMI CITY & GUILDS Auto Eng. Gen. Auto Eng. Motor Mechanics Auto Diesel Eng. Garage M'nt. ARB Aero Engineering Certs. Gen. Aero Eng.	<input type="checkbox"/> Supplementary courses for Nat. Certificates.
<input type="checkbox"/> CONSTRUCTIONAL Society of Engineers— A.M.S.E. (Civ.) Institute of Building—L.I.O.B.	<input type="checkbox"/> G.C.E. — choose from 58 'O' & 'A' level subjects.	<input type="checkbox"/> Coaching for many exams, including C & G

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPE01, Aldermaston Court, Reading RG7 4PF

QN BPE01

NAME
Block Capitals Please
ADDRESS

OTHER SUBJECTS

AGE

Accredited by C.A.C.C.

Member of A.B.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Henry's

DON'T RELY ON YOUR MEMORY
BUY NOW AT BARGAIN PRICES
Hi Fi and Transistors - Up to date
Brochures on request

HENRY'S CATALOGUE
Due to rapid price changes
shortages of paper and raw
materials, all prices in the
existing catalogues no longer
apply. Call or phone for latest
prices. A new catalogue will
be available for Aug/Sept 1974

130 LOVE

You pay less
VAT with Henry's
Low Prices



Now built and
used by thousands
of satisfied cus-
tomers.

FEATURES: slim
design, overall size in
cabinet 15in x 22in x 6in
6-IC's, 10 transistors, stabilisers,
Gardners low field transformer, Fibre
Glass PC Panel, complete chassis work.
Now available built and tested as well
as in kit form.


**HIGH QUALITY & STABILITY ARE
DOMINANT FEATURES—DEVELOPED
BY TEXAS ENGINEERS FOR PERFORMANCE, BY
RELIABILITY AND EASE OF CONSTRUCTION,
FACILITIES.** On/off switch indicator, headphones
socket, separate treble, bass, volume and balance controls,
scratch and rumble filters, mono/stereo switch, input selector;
Mag. P. U. Radio Tuner, Aux. Can be altered for Mic, Tape, Tape-head, etc.
Constructional details Ref. No. 21, 30p.
Distributed by Henry's throughout UK.

FREE Teak cabinet with complete kit.

KIT (+ VAT + 50p
PRICE £28.50 carr/packing) or
built and (+ VAT + 50p
tested £35.00 carr/packing)
as illustrated

BUILD THE TEXAN 20 + 20 WATT IC STEREO AMPLIFIER

As featured by
Practical Wireless 1972

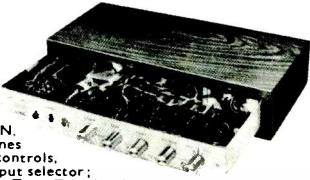


BUILD THE NEW HENELEC STEREO FM TUNER

A completely new high stability stereo FM tuner.
Features variable capacity diode tuning, stabiliser power supply, IC
Decoder, high gain low noise, IF stages, LED
indicators, Tuning meter, AFC,
Easy to construct and use.
Mains operated. Slim
modern design with fibre
glass PC, teak cabinet,
etc. Available as a kit to
build or ready built.
Overall size: 8in x 22in
x 6in. Produced to give
high performance with a
realistic price. (Parts list
and constructional details
Ref. No. 5, 30p.) Henry's
are sole distributors UK and Europe.




Kit Price £21.00 (+ VAT)
or built and tested £24.95 (+ VAT)

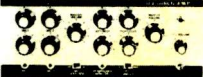EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT



DISCO MINI: A complete portable disco,
fitted mixer/preamp, 2 decks all facilities... £98.50
As above but with Slider Controls... £118.50
100 watt amplifier for above... £49.50
SDLS100: 100 watt mixer/amplifier with
slider controls... £69.00
R50: 50 watt mixer/amplifier... £49.50
R100: 100 watt mixer/amplifier... £57.50
DISCO AMP: 100 watt mixer/amplifier
Northcourt... £73.00
400 40 watt mixer amp... £37.50
800 80 watt mixer rmp... £45.00
DISCO MIXER/PREAMPLIFIERS (O/P
for up to 6-100 watt amplifiers):
SDLI (rotary controls)... £49.50
SDLI (slider controls)... £58.50
DISCO VOX (slider controls): The complete
disco preamp... £72.00
DJ100: 100 watt power amplifier for above... £49.50
DJ30L Mk II 3 channel 3kW sound to light... £41.25
DJ30L Mk III. Slider Controls... £45.50
DJ DISCLITE. As 30L/II + Variable speed
flashes... £54.00
Carlsbro Reverberation Unit... £44.00
Disco anti-feedback microphone... £11.95
Colt 150 watt liquid wheel projector... £23.50
150 watt Q1 liquid wheel projector... £50.00
150 watt Q1 cassette wheel projector... £50.00
Spare Effects and Liquid cassettes, large
range of patterns... £6.00
6in liquid wheels... £5.00
Various Cassettes... £6.00
Mini spot bank fitted 3 lamps... £12.95
Auto Trilite (mini with flashes)... £17.00
Bubblemaker with 1 gal. liquid... £22.50
MIXERS/MICS/SPEAKERS/LIGHTING
U.K.'s largest range of Disco lighting
FREE STOCK LIST Ref. No. 18 ON REQUEST
AKG/RESLO/DJ/CARLSBRO/EAGLE
CHASSIS AND COMPLETE SPEAKER
SYSTEMS, MEGAPHONES, TURNTABLES,
PUBLIC ADDRESS COMPONENTS, MICS.,
STANDS, MIXERS, CABINETS

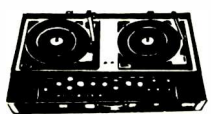

All prices carr. paid (UK) (VAT EXTRA).
Barclaycard/Access call, write or phone your order
01-723 6963—easy terms for callers.

EXCLUSIVE DECCA KELLY SPEAKERS



12 watt speaker Tweeter
systems. 8in Bass/Midrange
and Melinex Domed HF radiator plus
crossover £12.50 per pair of systems
(carr/pack. 40p) or built into vene-
ered cabinets, size 18 x 12 x 6in.
£19.50 pair (carr. £1).

HI-FI TAPE EQUIPMENT



U.K.'s largest range
with discounts and
demonstrations for
callers. Latest stock lists on request
(Ref. No. 17).
Phone 01-402 4736 for Barclay/Access
Card, Direct orders and latest prices.

TRANSISTORS SEMICONDUCTORS

U.K.'s largest range for every applica-
tion. Small quantity discounts.
Also Trade, Export and Industrial
enquiries invited. Latest stock list
(Ref. No. 36). Including valves on
request.

ELECTRONICS SUPPLIES

Specialists in electronics for more
than 30 years. Trade and industry
supplies—every type of component
and equipment.

SINCLAIR PROJECT 80

Stereo Preamplifier... £11.95
Audio Filter Unit... £6.95
Z40 15 watt Amplifier... £5.45
Z60 25 watt Amplifier... £6.95
PZ5 Mod. for 1 or 2 Z40... £4.98
PZ6 Mod. (S Tab) 1 or 2
Z40... £7.98
PZ8 Mod. (S Tab) 1 or 2
Z60... £7.98
TRANSFORMER FOR
PZ8... £3.95
NEW FM TUNER... £11.95
STEREO DECODER... £7.45
All items post paid.

LIVING SOUND LOW NOISE TOP QUALITY CASSETTES MADE BY EMI TAPES LTD. TO INTERNATIONAL STANDARDS ESPECIALLY FOR HENRY'S. ALL POST PAID LESS THAN REC. PRICES. COMPLETE WITH LIBRARY CASES.

	3 for	6 for	10 for	25 for
C60	£1.10	£1.98	£3.00	£7.40
C90	£1.46	£2.80	£4.60	£11.25
C120	£1.80	£3.45	£5.50	£13.45



Quantity and trade enquiries invited.
LEARN A LANGUAGE—complete with phrase book. German,
French, Spanish, Italian. £1.36 per course. £5 for any 4.

LOW COST HI-FI SPEAKERS SPECIAL OFFERS

EMI 13in x 8in—full range speakers (post 20p each or 30p pair);
*150TC—8 ohms Twin Cone 10 watt, £2.20 each or £4 pair; *450 10
watt c/o Twin Tweeters 3, 8 or 15 ohms, £3.85 each; EW 15 watt 8
ohms c/o Tweeter, £5.25 each; 350 20 watt c/o Tweeters 8 or 15
ohms, £7.80 each.
* Polished wood cabinet. £4.80, post 35p.



8 ohms full range (post 20p)
FR4 4in 5 watt, £4.75; FR65 6in 10 watt, £6.30;
FR8 8in 15 watt, £8.50; FR23 9 x 6in 15 watt,
£8.40.

BASS AND MID RANGE—8 ohms (post 20p)
AA12 5in 15 watt, £3.75; B110 5 1/2in 15 watt,
£7.20; B200 8in 15 watt, £8.50; B139/2 13in x 8in
30 watt LF, £13.75.

TWEETERS AND CROSSOVERS (post 20p)
K2006 10 watt 8 or 15 ohms, £2.10; FHT6 15 watt 8 ohms, £3.35; K2011
30 watt 8 ohms, £4.80; T27 KEF, £5.50; Axent 100 30 watt 8 ohms
£5.50; K4009 1kHz/5kHz c/o, £2.70; SN75 3kHz var. c/o, £3.10.

SPEAKER KITS (carr. etc. 35p)
20-2 8in x 8in, £4.80; 20-3 8in 40 watt, £35.95 pair; LINTON 2
20 watt, £18.30 pair; GLENDALE 3 30 watt, £32.95 pair; DOVEDALE 3
50 watt, £51.50 pair; KEF KK2, £55.00 pair; KEF KK3, £78.00 pair.

BUILD YOURSELF A POCKET CALCULATOR

A complete kit, packaged in a polystyrene con-
tainer and taking about 3 hours to assemble—
that's the Sinclair Cambridge pocket calculator
from Henry's. Some of the many features include
interface chip, thick-film resistor pack, printed
circuit board, electronic components pack.
Size: 4 1/2in long x 2in wide x 1 1/2in deep.
Free of charge with the kit for the more advanced
technologist is a 32-page booklet explaining how
to calculate Logs, Tangents, Sines, etc.



Price £19.95 (+ VAT)
Also assembled £22.50 (+ VAT)
ready to use

10% VAT TO BE ADDED TO ALL ORDERS. EXPORT SUPPLIED. Prices and descriptions correct at time of proof. Subject to change without notice
E & O. See page 495 of this magazine.
Like a permanent job at Henry's? Experienced and trainee salesmen required. Tel. 01-402 8791.

Henry's RADIO LIMITED

EDGWARE ROAD, LONDON W2

404-406 Electronic Components and Equipment 01-402 8381
309 P.A.—Disco—Lighting High Power Sound 01-723 6963
303 Bargains Store (Callers only)
Home and Car Entertainment Centres London and branches now open.
120 Shaftesbury Avenue, London W1 01-437 9692
144 Burnt Oak Broadway, Burnt Oak, Edgware 01-952 7402
190-194 Station Road, Harrow, Middlesex 01-663 7788/9
354-356 Edgware Road, London W2 01-402 5854/4736

All mail to
303 Edgware Road,
London W2 1BW
All stores open 9 am to
6 pm six days a week
Hi-Fi—Tape Equipment
Discount Stock List
Free at all stores