


PRACTICAL

ELECTRONICS

JULY 1975

30p

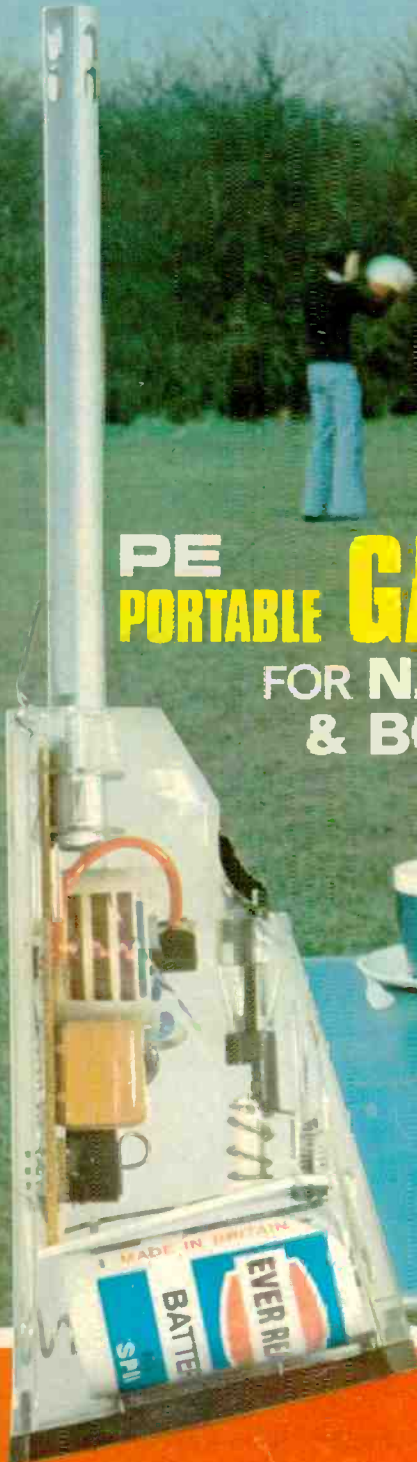PE
PORTABLE GAS IGNITOR
FOR NATURAL, TOWN
& BOTTLED GAS



Also... **Guitar Effects Pedal**
SINE/SQUARE WAVE SIGNAL GENERATOR

NEW EDU-KIT MAJOR

**COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT
BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER**

- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester NPN -PNP
- 4 Transistor Push Pull Amplifier
- 5 Transistor Push Pull Amplifier
- 7 Transistor Loudspeaker Radio MW/LW.
- 5 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- Batteryless Crystal Radio
- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier

Components include:

- 24 Resistors ● 21 Capacitors ● 10 Transistors ● 31" Loudspeaker ● Earpiece ● Mica Baseboard
- 3 12-way Connectors ● 2 Volume Controls ● 2 Slider Switches ● 1 Tuning Condenser ● 3 Knobs
- Ready Wound MW/LW/SW Coils ● Ferrite Rod ● 6½ yards of wire ● 1 yard of sleeving, etc.
- Parts price list and plans 65p (free with parts)


TOTAL BUILDING COSTS

£7-23 P.P. & Ins. 58p
(Overseas Seamail P. & P. £3.40)
(+25% VAT £1-80)

ROAMER TEN

Mk. II

WITH VHF INCLUDING AIRCRAFT

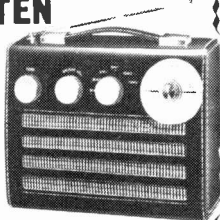

Now with free earpiece and switched socket.


10 TRANSISTORS. 9 TUNABLE WAVE BANDS. MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS. ALSO AIRCRAFT BAND

Latest 4" 2 watt Ferrite Magnet Loudspeaker. Built-in ferrite rod aerial for MW/LW. Chrome plated 6 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in x 7in x 4in. Easy to follow instructions and diagrams. Parts price list and plans 50p (FREE with parts).

TOTAL BUILDING COSTS **£9-50** P.P. & Ins. 65p
(Overseas Seamail P. & P. £3-50)
(+25% VAT £2-37)

POCKET FIVE

NOW WITH 3" LOUDSPEAKER

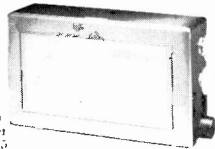

3 Tunable wavebands MW/LW and Trawler Band. 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive Black and Gold Case. Size 5½in x 1½in x 3¼in approx. Plans and parts price list free with parts.

Total Building Costs **£2-95**
(+25% VAT 75p)
P.P. & Ins. 38p
(Overseas Seamail P. & P. £2-30)

ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL



7 TUNABLE WAVEBANDS:


MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Chrome plated telescopic aerial can be angled and rotated for peak short-wave listening. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt Ferrite Magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£6-98** P.P. & Ins. 65p
(Overseas Seamail P. & P. £3-50)
(+25% VAT £1-75)

NEW JIFFY TESTER

Easy to build and operate, fits in the pocket. A quick checker for continuity of resistors, chokes, diodes, transistors, circuit wiring (not mains) and loudspeakers. Also for checking short circuits of capacitors, tuning capacitors and many other uses not listed here. See instruction sheet free with kit.

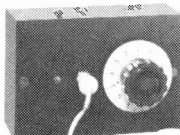Complete with earpiece, jack plug and socket, resistors, capacitors, components, etc. Parts Price List and Easy Build Plans free with Parts



Total Building Costs **£2-25**
(+25% VAT 56p)
P.P. & Ins. 22p (Overseas Seamail P. & P. £1-70)

NEW EVERYDAY SERIES




EV6

Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5½ x 2½in, approx. 6 Transistors and 3 diodes. Powered by 9 volt Battery. Ferrite rod aerial, 3" loudspeaker, etc. MW/LW coverage. Push Pull Output. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£3-98** P.P. & Ins. 50p
(Overseas Seamail P. & P. £2-30)
(+25% VAT £1-00)

TRANS EIGHT

8 TRANSISTORS AND 3 DIODES

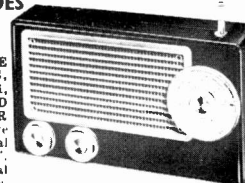

6 TUNABLE WAVE BANDS. MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves.

3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in x 5½in x 2½in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£4-78** P.P. & Ins. 50p
(Overseas Seamail P. & P. £2-50)
(+25% VAT £1-20)

"Edu-Kit"

Build Radios, Amplifiers, etc., from easy stage diagrams. Five units including master unit to construct.

Components include: Tuning Condenser; 2 Volume Controls; 2 Slider Switches; Fine tone 3" moving coil Speaker; Terminal Strip; Ferrite Rod Aerial; Battery Clips; 4 Tag Boards; 10 Transistors; 4 Diodes; Resistors; Capacitors; Three ½in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£5-50** P.P. & Ins. 50p
(Overseas Seamail P. & P. £3-40)
(+25% VAT £1-37)



RADIO EXCHANGE LTD

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD MK40 1SA
Tel. 0234 52367 Reg. No. 788372

I enclose £..... for.....

- | | | | |
|--------------|--------------------------|---------------|--------------------------|
| ROAMER TEN | <input type="checkbox"/> | EV6 | <input type="checkbox"/> |
| ROAMER EIGHT | <input type="checkbox"/> | TRANS EIGHT | <input type="checkbox"/> |
| JIFFY TESTER | <input type="checkbox"/> | MAJOR EDU-KIT | <input type="checkbox"/> |
| POCKET FIVE | <input type="checkbox"/> | EDU-KIT | <input type="checkbox"/> |

Name.....

Address.....

- ★ Callers side entrance "Lavells" shop
- ★ Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

PRACTICAL ELECTRONICS

VOLUME 11 No. 7 JULY 1975

CONSTRUCTIONAL PROJECTS

- P.E. PORTABLE GAS IGNITOR** *by R. Bullen*
Ignite town, bottle and natural gas with this simple project 552
- GUITAR EFFECTS PEDAL** *by R. Gwinn*
Eight variable sound treatments in one unit 559
- P.E. JOANNA—3** *by A. J. Boothman*
Envelope generation systems 572
- SINE/SQUARE WAVE SIGNAL GENERATOR** *by J. Smith*
General purpose a.f. test instrument 582

GENERAL FEATURES

- TRANSDUCERS—4** *by P. R. Allcock*
Concluding section on the inductive transformer 562
- INGENUITY UNLIMITED**
Tunnel Diode B.F.O./I.F. Marker—Adding Circuit—Random Number Generator—Desoldering Components 567
- SYMBIOSIS—2** *by M. Pointon*
Concluding article on composing with the P.E. Minisonic 578
- NEW DEVICES . . . APPLICATIONS**
Solid-state power control 580

NEWS AND COMMENT

- EDITORIAL—An Indiscriminate Tax** 551
- NEWS BRIEFS**
Electronics For School Teachers—Queen's Award 557
- SPACEWATCH** *by Frank W. Hyde*
A new X-ray source 558
- MARKET PLACE**
Interesting new products and a V.A.T. announcement 571
- POINTS ARISING**
Ultrasonic Intruder Alarm—Light Pipe—Thermometer/Controller 576
- INDUSTRY NOTEBOOK**
A look at the American scene 589
- PATENTS REVIEW**
Thought provoking ideas on file at the British Patent Office 590
- READOUT**
A selection of readers' letters 593

Our August issue will be published on Friday, July 11, 1975


© IPC Magazines Limited 1975. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Publisher's Subscription Rate including postage for one year, Inland £4.80, Overseas £5.00. USA and Canada \$13.50. International Giro facilities Account No. 5122007. State reason for payment, "message to payee".

Sound to Light Master Unit



600 watts per channel

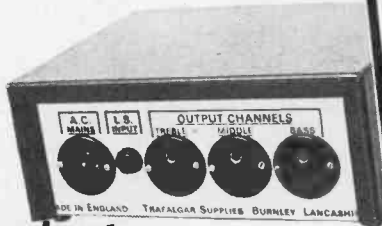Connects to your loudspeaker or loud-speaker socket. The unit can be connected to your existing spotlight fittings or to our type A or B fittings.



Special Introductory Price

Including channel output plugs and mains input socket.

Only **£29.95** incl VAT plus p&p £1.00

Type B 3 BANK UNIT



B.C. fitting (less lamp)

£6.50 incl VAT plus p&p 40p each

Type A

(less lamp) **£1.60** incl VAT plus p&p 25p each.



B.C. fitting

100 WATT Red, pink, yellow, green, blue, clear.
SPOT LAMPS Only £1.00 each
Minimum 3 lamps £3.00 plus p&p 25p.
B.C. fitting

TRAFALGAR SUPPLIES
Dept. H.T., STANDISH STREET,
BURNLEY, LANCs.

ENGINEERS

FREE

YOURSELF FOR A BETTER JOB

WITH MORE PAY!



This 76 page FREE book shows how!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

CUT OUT THIS COUPON

CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.


- | | | |
|---|---|--|
| Practical Radio and Electronics (Technatron) <input type="checkbox"/> | C. & G. Radio, TV Electronics, Mechanics <input type="checkbox"/> | C. & G. LI Installations and Wiring <input type="checkbox"/> |
| Electronic Engineering <input type="checkbox"/> | Radio Amateurs <input type="checkbox"/> | General Electrical Engineering <input type="checkbox"/> |
| Television Maintenance and Servicing <input type="checkbox"/> | Practical TV <input type="checkbox"/> | Society of Engineers (Electrical Engineering) <input type="checkbox"/> |
| General Radio and TV Engineering <input type="checkbox"/> | Colour Television <input type="checkbox"/> | Electrical Installations and Wiring <input type="checkbox"/> |
| Radio Servicing, Maintenance and Repairs <input type="checkbox"/> | Computer Electronics <input type="checkbox"/> | C. & G. Electrical Technicians (Primary) <input type="checkbox"/> |
| | C. & G. LI Radio TV Servicing cert. <input type="checkbox"/> | C. & G. Telecommunications <input type="checkbox"/> |
| | Post Master General 1st & 2nd class certs. <input type="checkbox"/> | |
| | C. & G. Electrical Engineering Practise <input type="checkbox"/> | |

To **ALDERMASTON COLLEGE** Dept. EPE07 Reading RG7 4PF
Also at our London Advisory Office, 4 Fore St. Avenue, Moorgate, London EC2Y 5EJ. Tel: 01-628 2721.

NAME (Block Capitals Please) _____
ADDRESS _____
POST CODE _____
Other subjects _____ Age _____
Accredited by C.A.C.C. Member of A.B.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

COLBERT WORK POSITIONERS - 300 SERIES

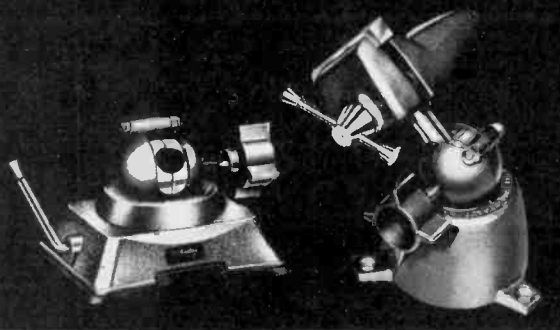

Colbert Pana-Vise WORK POSITIONERS are specially designed to quickly and easily achieve the most CONVENIENT, COMFORTABLE and TIME-SAVING work position.

Available with vacuum clamp or screw-on base. They can be ROTATED, TIPPED, TILTED, ANGLED, ELEVATED, LOWERED.

The required work position is firmly secured with a patented ONE KNOB CONTROL, a unique feature of COLBERT POSITIONERS.

A series of special holders is available for various types of work.

Full details available on request

Distributors:

SPECIAL PRODUCTS DISTRIBUTORS LTD.
81 PICCADILLY, LONDON, W1V 0HL Tel. 01-629 9556
Cables: SPECIPROD LONDON (made in U.S.A.)

CHROMASONIC electronics

Dept. 2, 56, Fortis Green Road,
Muswell Hill, London. N10 3HN.
telephone: 01-883 3705

C-MOS

74 TTL

LINEAR I.C.'s

C-MOS			74 TTL			LINEAR I.C.'s									
1-24	25-99	100up	1-24	25-99	100+										
CD4000AE	23p	19p	15p	7400	14p	12p	10p	555 (8 pin dip) V	55p	BHA0002	£3.01	MC1358 (CA3065)	£1.16	SN76544N	£1.81
CD4001AE	23p	19p	15p	7401	14p	12p	10p	555 (TO-99) T	81p	CA2111	£1.19	MC1375	£1.48	SN76550-2 (TAA550)	85p
CD4002AE	23p	19p	15p	7402	14p	12p	10p	556 (14 pin dip)	£1.29	CA3045	£1.89	MC1455 (555T)	62p	SN76660N (TBA120)	79p
CD4006AE	£1.59	£1.33	£1.06	7403	15p	12p	10p	703 (RF/IF Amp)	59p	CA3046	88p	MC1456CPI	£1.68	SN76666N (CA3065)	£1.12
CD4007AE	23p	19p	15p	7404	16p	13p	11p	709 (8 pin dip)	38p	CA3053	59p	MC1458CPI	84p	TAA263	£1.50
CD4008AE	£1.75	£1.46	£1.17	7405	16p	13p	11p	709 (TO-99)	45p	CA3065	£1.60	MC1468G	£2.18	TAA300	£2.16
CD4009AE	Use	CD4049		7408	16p	13p	11p	710 (8 pin dip)	39p	CA3078	£1.26	MC1495L	£4.24	TAA310A	£1.87
CD4010AE	Use	CD4050		7409	16p	13p	11p	710 (TO-99)	45p	CA3080	59p	MC1496G	96p	TAA320	£1.44
CD4011AE	23p	19p	15p	7413	20p	24p	20p	711 (14 pin dip)	44p	CA3081	£1.86	MC3302P	£1.50	TAA350	£2.43
CD4012AE	23p	19p	15p	7417	20p	22p	20p	711 (TO-99)	51p	CA3082	£1.86	MC3401P	74p	TAA370	£3.45
CD4013AE	69p	58p	46p	7420	16p	13p	11p	711 (14 pin dip)	44p	CA3089E (TDA1200)E.2.43				TAA550	75p
CD4014AE	£1.75	£1.46	£1.17	7427	27p	22p	18p	720 (A.M. Radio)	£1.76	CA3097E	£1.67	MFC4000B	87p	TAA570	£2.74
CD4015AE	£1.75	£1.46	£1.17	7430	16p	13p	11p	723 (TO-99)	£1.09	CA3123E	£1.76	MFC4060A	79p	TAA700	£5.03
CD4016AE	69p	58p	46p	7432	27p	22p	18p	723 (14 pin dip)	74p	CA3401E (LM3900)	68p	MFC6030A	96p	TAA820	£1.44
CD4017AE	£1.75	£1.46	£1.17	7437	27p	22p	18p	741 (8 pin dip)	36p	CA3600E	£1.44	MFC6070	£1.66	TBA120S	£1.25
CD4018AE	£2.51	£2.09	£1.67	7441	75p	62p	50p	741 (TO-99)	43p	CT7001	£5.34			TBA231	£1.02
CD4019AE	80p	66p	53p	7442	65p	55p	43p	741 (14 pin dip)	£1.64					TBA281 (723)	£2.59
CD4020AE	£1.97	£1.64	£1.31	7445	85p	71p	57p	747 (14 pin dip)	36p			MM5314	£4.80	TBA500Q	£3.16
CD4021AE	£1.75	£1.46	£1.17	7447	95p	83p	67p	748 (8 pin dip)	42p			MM5316	£9.99	TBA520Q	£3.85
CD4022AE	£1.83	£1.53	£1.22	7447A	95p	83p	67p	748 (TO-99)	51p					TBA530Q	£3.27
CD4023AE	23p	19p	15p	7448	85p	71p	57p	748 (14 pin dip)	49p					TBA540Q	£3.72
CD4024AE	£1.26	£1.05	£0.84	7470	30p	25p	20p	753 (F.M. Tr. I.F.)	£1.08					TBA550Q	£5.29
CD4025AE	23p	19p	15p	7472	25p	21p	17p							TBA560CQ	£5.29
CD4026AE	£2.79	£2.33	£1.86	7473	30p	25p	20p								
CD4027AE	98p	82p	65p	7474	32p	26p	21p								
CD4028AE	£1.53	£1.28	£1.02	7475	47p	39p	31p								
CD4029AE	£1.12	£1.76	£1.41	7476	32p	26p	21p								
CD4030AE	71p	59p	47p	7482	75p	62p	50p								
CD4035AE	£1.75	£1.46	£1.17	7485	£1.30	£1.09	87p								
CD4040AE	£2.01	£1.68	£1.34	7486	32p	26p	21p								
CD4042AE	£1.49	£1.24	£0.99	7489	£3.56	£2.80	£2.10								
CD4049AE	69p	58p	46p	7490	49p	40p	32p								
CD4050AE	69p	58p	46p	7491	65p	55p	45p								
CD4051AE	£2.78	£2.32	£1.85	7492	57p	46p	36p								
CD4052AE	£2.78	£2.32	£1.85	7493	49p	40p	32p								
CD4053AE	£2.12	£1.76	£1.41	7495	£1.30	£1.09	87p								
CD4054AE	£2.51	£2.09	£1.67	74100	£1.30	£1.09	87p								
CD4064AE	£1.13	94p	75p	74107	35p	28p	22p								
CD4068AE	28p	24p	19p	74121	34p	28p	23p								
CD4069AE	28p	24p	19p	74122	47p	39p	31p								
CD4070AE	28p	24p	19p	74141	78p	63p	53p								
CD4071AE	28p	24p	19p	74145	68p	58p	48p								
CD4077AE	71p	59p	47p	74154	£1.75	£1.48	86p								
CD4081AE	28p	24p	19p	74174	£1.00	83p	67p								
CD4082AE	28p	24p	19p	74180	£1.06	88p	71p								
CD4085AE	£1.28	£1.06	85p	74181	£3.20	£2.50	£1.90								
CD4086AE	£1.28	£1.06	85p	74192	£1.35	£1.14	90p								
CD4092AE	£1.56	£1.20	£1.04	74193	£1.35	£1.14	90p								
CD4099AE	£2.95	£2.46	£1.96	74196	£1.64	£1.34	99p								

SIEMENS LCD's

LINE-O-LIGHT

LIQUID CRYSTAL DISPLAY complete with socket and removable reflective backing. Ref AN4132R 13mm character height. Can be directly driven by National Semiconductors Alarm Clock chip MM5316. £13.99



NEW LED Linear Cursors each device contains 10 light emitting diodes in a 20pin dual-in-line package. Ideal for solid state analogue meters or dials. Type 101 RD £2.26



PHOTO-DARLINGTON

SPECIAL PURCHASE

SEVEN SEGMENT DISPLAYS

2N5777
V_{ceo}, V_{ceo} 25v; V_{ebo} 8v
V_{ceo}, V_{ceo} 25v; V_{ebo} 8v
I_{fe} 2500; I_c 250 mA **35p.**

enables
LIT707 90p; LIT747 £1.99

litronix
Monanto

	COMMON ANODE R/H Dec. Pr.	COMMON ANODE L/H Dec. Pr.	COMMON ANODE I Dec. Pr.	COMMON CATHODE R/H Dec. Pr.	Our Price
RED	DL707R	DL707	DL701	DL704	£1.82
GREEN	MAN51	MAN52	MAN53	MAN54	£1.82
RED	MAN71	MAN72	MAN73	MAN74	£1.82
YELLOW	MAN81	MAN82	MAN83	MAN84	£1.82
ORANGE	MAN3610	MAN3620	MAN3630	MAN3640	£1.82
GREEN	XAN51	XAN52	-	XAN54	£1.49
RED	XAN71	XAN72	-	XAN74	£1.49
YELLOW	XAN81	XAN82	-	XAN84	£1.49
GREEN	MAN4510	MAN4520	MAN4530	MAN4540	£2.32
RED	MAN4710	MAN4720	MAN4730	MAN4740	£2.32
YELLOW	MAN4810	MAN4820	MAN4830	MAN4840	£2.32
ORANGE	MAN4610	MAN4620	MAN4630	MAN4640	£2.32
	C.A. L/H Dec. Pr.	C.A. L/H Dec. Pr.	C.C. L/H Dec. Pr.	C.C. L/H Dec. Pr.	
0.3"	DL747	DL746	DL750	DL749	£2.42

I.C. SOCKETS
Dual-in-line TOS
Pins 9 14 16 24 28 36 40 8 10
Price 13p 15p 26p 30p 39p 44p 31p 35p

NEW
Litronix Double Digit Displays
0.5" Common Anode 2 R/H
D.P.'s
DL721 gives 1.9
DL722 gives 0.0 to 9.9
Suitable for Clocks; Instruments; T.V. Channel Indicator
Our Price £4.75 each.

L.E.D.'s
Free snap-on plastic retainer

0.125" dia. lens (TIL209)	0.16" dia. lens	0.2" dia. lens (MLED 650)
1p 10p 100p	1p 10p 100p	1p 10p 100p
Red 15p 15p 22p	27p 24p 22p	18p 16p 14p
Green 27p 24p 22p	33p 30p 27p	30p 27p 25p
Orange 27p 24p 22p	33p 30p 27p	30p 27p 25p
Yellow 34p 31p 29p	35p 32p 29p	35p 33p 30p

NOTICE
Postage & Packing Charges
With the recent increase in postal charges and a continuing increase in packaging cost we have been forced to review our policy.
Henceforward:
1. Orders valued at £5 or more will be post free.
2. All U.K. 'small package' orders will go first class mail.
3. Minimum postage & packing charge will increase to 20p.

Low Cost Red Gax's
Motorola MLED 500 in a T092 package. 15p

NEW Opto-isolators
ILL14N25 or TIL116
& pin industry standard package
2.5KV isolation £1.00

Items marked with a • Include 8% VAT
Items unmarked include VAT at 25%

CALIERS WELCOME

ADVERT. No.1 of Series B.

CRESCENT RADIO LTD.

11-15 & 17 MAYES ROAD, LONDON N22 6TL

(also) 13 SOUTH MALL, EDMONTON, N.9

MAIL ORDER DEPT.

11 MAYES ROAD, LONDON N22 6TL
Phone 888 3206 & (EDM.) 803 1685

ADD LUXURY TO YOUR CAR WITH A MOTOR DRIVEN CAR AERIAL
Spec.: 5 Section
Extended Length 100cm
Length under Fender 40cm
Cable Length 120cm

Supplied complete with Fixing Bracket and Control Switch. **£7-50** plus 20p P. & P. + 25%.



"CRESCENT BEAT BRITE" SINGLE CHANNEL SOUND TO LIGHT UNIT

This fantastic little box approx. 4" x 3" x 2 1/2" when connected to the output of a sound source from 1 to 100 watts produces a psychedelic light display up to 1000 watts. Complete with a sensitive level control the unit is fused and cannot harm your amplifier. A bargain at **£7-50** plus 10p P. & P. + 8%.



MINIATURE RELAYS

Brand new range of British made relays, size: 1 1/2in x 1in x 1/2in. All two changeovers with 250V 1-5A contacts and suitable for fitting on 0.1m veroboard.
Type Volts Current Ohms
2 1/2A 12V 17mA 700 All
2 1/2A 12V 28mA 430 21-30
1 1/2A 6V 33mA 185 each
200/250V Mains Relay + 8%
Heavy duty contacts 2,500 ohm coll. All new and unused D.P.D.T. mains relays 50p, Carr. free. Special quantity £40 per 100 off. + 8%.

MIDGET MAINS TRANSFORMER

Varnish Impregnated
Size 40mm x 36mm x 31mm
PRI 240V
Sec 3-0-3 100mA
Sec 6-0-6 100mA
Sec 9-0-9 100mA
Sec 12-0-12 100mA
Sec 20-0-20 100mA
£1-23 10p P. & P. + 8%.

CRESCENT BUBBLE LIGHT SHOW

This budget system compares very favourably with more sophisticated and higher priced models.
Specification:
Projector—150W convection cooled. At 30ft the projected image is 18ft.
Motor—1 rev. per 2 min.
Liquid Wheel—6in diameter multi colour.
The motor is fitted to the projector and can only be purchased as a single unit.
The liquid wheel is our standard model and may be purchased separately.
A bargain at: Projector, **£16**; Wheel, **£6**; Total **£20**. Plus 75p carr. + 8%.

CABLE LESS SOLDERING IRON WAHL "ISO-TIP"

★ Completely portable
★ Solders up to 150 joints per charge.
★ Recharges in its own stand.
★ Fine tip for all types of soldering.
★ Only 4in long and weighs just 6 ozs.
OUR PRICE **£9-75** + 8%.
(Spare bits are available)

"CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U. BUILD. IT

We supply the three modules for you to build this Disco-Group-P.A. amplifier into the cabinet of your choice.

★ **THE POWER AMP MODULE**
170W r.m.s. sq. wave 300W instantaneous peak into 8 ohm (60W into 16 ohm).

★ **THE PRE-AMP MODULE**
Four control pre-amp, Vol, Bass, Treble. Middle controls. Designed to drive most amplifiers using F.E.T. first stage.

★ **THE POWER SUPPLY**
Is supplied complete with the mains transformer. Complete fixing instructions are supplied and no technical knowledge is required to connect the three ready wired modules. A fantastic bargain. **£25**, carr. 75p. Send S.A.E. for further details on this or our ready built amplifiers. + 25%.

12-0-12V 500M/A
240V primary transformer bargain. Approx. size: 60mm x 40mm x 50mm; fixing centres: 75mm. Our price **£1-20**.

18V 500M/A + 8%
240V primary. Approx. size: 60mm x 40mm x 50mm; fixing centres: 75mm. Our Price **£1** each

LOW NOISE, LOW PRICE CASSETTES

Good quality tape in well made screw type cassettes. Presented in single plastic cases.
C80 31p C90 42p C120 53p
10% discount on ten or more cassettes of one type. + 8%.

ABS PLASTIC BOXES

Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels. 1005, 105mm x 73mm x 45mm 51p; 1066, 150mm x 75mm x 47mm 66p; 1007, 184mm x 134mm x 60mm 96p; 1021, 106mm x 74mm x 45mm (sloping front) 50p. + 8%.

BARGAIN BOARDS

Components galore for the experimenter. Ex-Computer boards with resistors, capacitors and useful transistors—at least 4 transistors per board. Five boards **£1**. + 8%.

2in. PANEL METERS

Size 59mm x 46mm
0-50µA—ME6 0-100mA—ME13
0-500µA—ME7 0-500mA—ME14
0-100µA—ME8 0-1A—ME15
0-1mA—ME9 0-50V—ME16
0-5mA—ME10 0-300V a.c.—ME17
0-10mA—ME11 8 meter—ME18
0-50mA—ME12 V.U. meter—ME19
£3 each, 10p P. & P. + 8%.

POWER PACKS


PP1 Switched 3-41-6-71-9 and 12V at 500M/A with on/off switch and pilot light. Size 130M/J x 53M/J x 75M/J, only **£4**.
PP2 Switched 6-71-9V Battery Eliminator. Approx. size 2 1/2in x 2 1/2in x 3 1/2in. Ideal for cassette recorders, **£3-25**.
PP3 Car converter. From 12V Pos. or Neg. to ± 6-71-9V. Easy to fit and transistor regulated, **£3-90**. + 8%.

3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel: Bass, Middle, Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed.)
£18-50 plus 38p P. & P. + 8%.

MINI LOUSPEAKERS

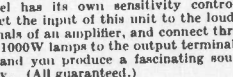2 1/2in 80 ohm, 50p; 2 1/2in 40 ohm, 50p. Please include 5p P. & P. on each L.S. + 25%.





FAST VALVE MAIL ORDER CO.

16a WELLFIELD ROAD, LONDON SW16 2BS
SPECIAL EXPRESS MAIL ORDER SERVICE
Express postage 10p per order in U.K.

1N21	0-17	AFZ11	1-15	BY213	0-25	OAZ205	0-45	Z8170	0-10
1N23	0-35	AFZ12	2-00	BY210	0-45	OAZ206	0-45	Z8271	0-25
1N55	0-88	AY26	0-25	BY211	0-40	OAZ207	0-45	ZT31	0-25
1N253	0-50	AY27	0-33	BY212	0-40	OAZ208	0-40	ZTX107	0-12
1N256	0-50	AY28	0-25	BY213	0-42	OAZ209	0-40	ZTX108	0-08
1N645	0-16	AY29	0-30	BY215	1-25	OAZ210	0-40	ZTX300	0-13
1N725A	0-20	AY36	0-25	BY216	0-60	OAZ211	0-40	ZTX304	0-24
1N914	0-06	AY50	0-20	BZY98	0-10	OAZ222	0-45	ZTX500	0-13
1N4007	0-12	AY51	0-40	C111	0-55	OAZ223	0-35	ZTX503	0-16
18113	0-25	AY55	0-20	C181/105	0-35	OAZ224	0-45	ZTX531	0-25
18202	0-23	AY62	0-25	C84B	1-90	OAZ242	0-15		
2G371	0-40	AY66	0-33	C810B	3-50	OAZ244	0-25	INTEGRATED CIRCUITS	
2G381	0-22	AZ21	1-00	D800	0-15	OAZ246	0-15	7400	0-16
2G414	0-30	AZ23	0-75	D803	0-15	OAZ290	0-38	7401	0-16
2G417	0-25	AU104	1-00	D806	0-25	OC16	1-00	7402	0-16
2N404	0-23	BU107	0-14	D808	0-38	OC18	1-00	7403	0-16
2N697	0-16	BC108	0-13	G13	0-33	OC19	0-50	7404	0-28
2N698	0-30	BC109	0-14	G14	0-32	OC22	1-00	7405	0-22
2N706	0-12	BC113	0-15	GD5	0-23	OC23	1-25	7406	0-42
2N706A	0-12	BC115	0-15	GD8	0-23	OC24	1-10	7407	0-42
2N708	0-15	BC116	0-20	GD8	0-25	OC25	0-40	7408	0-28
2N709	0-40	BC116A	0-23	GD12	0-10	OC26	0-40	7409	0-28
2N1091	0-55	BC118	0-20	GET103	0-40	OC28	0-66	7410	0-28
2N1131	0-25	BC121	0-20	GET113	0-35	OC29	0-50	7411	0-25
2N1132	0-24	BC122	0-20	GET114	0-30	OC30	0-40	7412	0-30
2N1302	0-18	BC125	0-68	GET115	0-90	OC36	0-60	7416	0-36
2N1308	0-18	BC126	0-85	GET116	0-85	OC41	0-35	7417	0-36
2N1305	0-23	BC140	0-65	GET120	0-50	OC42	0-40	7420	0-16
2N1306	0-28	BC147	0-10	GET122	0-40	OC43	0-70	7423	0-16
2N1307	0-28	BC148	0-08	GET875	0-40	OC44	0-40	7423	0-37
2N1308	0-28	BC149	0-10	GET880	0-60	OC44M	0-17	7425	0-37
2N2147	0-78	BC167	0-14	GET881	0-25	OC45	0-80	7427	0-37
2N2148	0-60	BC168	0-12	GET882	0-35	OC45M	0-18	7428	0-40
2N2160	0-78	BC180	0-62	GET885	0-40	OC46	0-27	7430	0-16
2N2218	0-28	BC189	0-16	GEX44	0-08	OC57	0-60	7432	0-37
2N2219	0-25	BCY31	0-45	GEX45	0-10	OC58	0-60	7433	0-37
2N2369A	0-16	BCY32	0-85	GEX941	0-45	OC59	0-60	7437	0-37
2N2444	1-99	BCY33	0-88	GJ3M	0-50	OC66	0-50	7438	0-37
2N2613	0-28	BCY34	0-45	GJ4M	0-50	OC70	0-18	7440	0-22
2N2646	0-50	BCY38	0-55	GJ5M	0-25	OC71	0-18	7441AN	0-92
2N2904	0-20	BCY39	1-50	G37M	0-50	OC72	0-28	7442	0-79
2N2904A	0-25	BCY40	0-80	HG1005	0-50	OC73	0-50	7450	0-16
2N2906	0-20	BCY42	0-30	H8100A	0-20	OC74	0-80	7451	0-18
2N2907	0-23	BCY71	0-22	MAT100	0-20	OC75	0-80	7453	0-16
2N2924	0-12	BCZ10	0-60	MAT120	0-20	OC76	0-70	7454	0-16
2N2926	0-12	BCZ11	0-65	MAT121	0-25	OC78	0-25	7470	0-38
2N3054	0-48	BD123	1-00	MJE2340	0-47	OC79	0-80	7472	0-58
2N3055	0-45	BD124	0-65	MJE2390	0-63	OC81	0-29	7473	0-11
2N3702	0-11	BDY11	1-45	MJE2955	1-27	OC81D	0-20	7474	0-42
2N3705	0-15	BF115	0-20	MPP102	0-40	OC81D	0-18	7476	0-45
2N3706	0-11	BF167	0-25	MPP103	0-38	OC81Z	0-45	7480	0-80
2N3709	0-10	BF173	0-22	MPP104	0-35	OC82	0-25	7482	0-87
2N3710	0-11	BF181	0-25	MPP105	0-38	OC82D	0-28	7483	1-10
2N3711	0-11	BF185	0-22	NKT128	0-45	OC83	0-27	7484	1-10
2N3819	0-88	BF194	0-10	NKT129	0-30	OC84	0-80	7486	0-47
2N4289	0-30	BF196	0-18	NKT211	0-25	OC114	0-38	7490	0-65
2N5027	0-53	BF196	0-15	NKT212	0-25	OC122	1-10	7491AN	1-00
2N5088	0-33	BF197	0-15	NKT214	0-24	OC123	1-10	7492	0-70
2S301	0-59	BF197	0-15	NKT216	0-40	OC139	0-40	7493	0-70
28304	1-15	BF681	1-05	NKT217	0-45	OC140	1-14	7494	0-40
28501	0-75	BF898	0-25	NKT218	0-45	OC141	0-60	7495	0-80
28703	1-00	BFX12	0-20	NKT219	0-33	OC169	0-20	7496	0-95
AA129	0-20	BFX13	0-28	NKT222	0-30	OC170	0-30	7497	3-87
AAZ12	0-75	BFX29	0-28	NKT224	0-25	OC171	0-30	74100	1-89
AAZ13	0-12	BFX30	0-28	NKT251	0-24	OC200	0-54	74107	0-45
AC107	0-51	BFX63	0-50	NKT271	0-20	OC201	1-00	74110	0-58
AC126	0-25	BFX84	0-25	NKT272	0-20	OC202	0-80	74111	0-88
AC127	0-25	BFX85	0-25	NKT273	0-20	OC203	0-65	74118	0-90
AC128	0-15	BFX86	0-25	NKT274	0-20	OC204	0-65	74119	1-68
AC187	0-21	BFX86	0-25	NKT275	0-25	OC205	1-00	74121	0-50
AC188	0-20	BFX87	0-25	NKT277	0-20	OC206	1-10	74122	0-70
ACY17	0-40	BFX88	0-24	NKT278	0-25	OC207	1-00	74123	1-00
ACY18	0-27	BFY11	0-50	NKT301	0-85	OC460	0-20	74141	0-90
ACY19	0-27	BFY17	0-40	NKT304	0-75	OC470	0-30	74145	1-26
ACY20	0-22	BFY18	0-45	NKT403	0-70	OCPT1	1-20	74150	1-75
ACY21	0-22	BFY19	0-55	NKT404	0-66	ORP12	0-60	74151	1-00
ACY22	0-18	BFY24	0-45	NKT678	0-30	ORP60	0-55	74154	2-00
ACY27	0-25	BFY24	0-45	NKT713	0-30	ORP61	0-48	74155	1-00
ACY28	0-25	BFY44	1-00	NKT773	0-25	SX88	0-20	74156	1-00
ACY29	0-78	BFY50	0-21	NKT777	0-38	SX89	0-28	74157	

Kit inspection

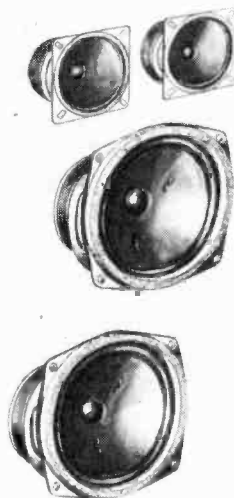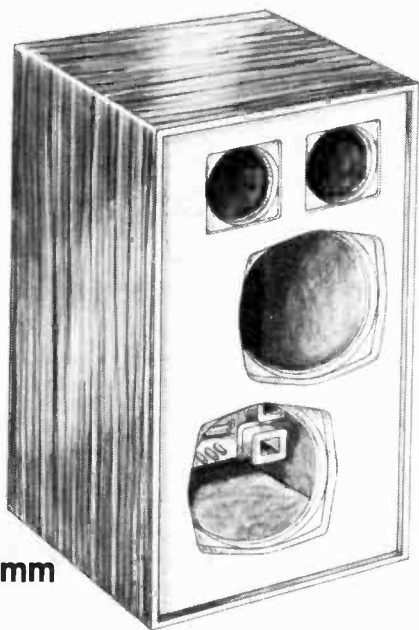

Dimensions
410 × 260 × 190mm

STUDIO ELECTRONICS EASIKIT

We invite your closest inspection of our loudspeaker kits. Here at last is a kit which doesn't require you to be either an electronic genius or a master carpenter. The assembly is simplicity itself, taking barely 15 minutes and requiring only a soldering iron, screwdriver and our easy to follow instructions, the cabinet being already built. 4 drive units provide excellent reproduction free from colouration, cabinet resonance and listening fatigue. In teak or white. Based on an original design as also selected for the outstanding Practical Electronics Rondo Quadraphonic system.

SPECIFICATIONS

Impedance 4-8 ohms.
Power Handling 20W r.m.s.
Crossover Frequencies 250Hz, 5kHz.
Frequency response 30Hz to 20kHz ± 5dB.
4 Drive units, Bass (13cm dia.), Bass/Mid-range (13cm dia.), 2 Tweeters (6.5cm dia.).

£42.50 per pair. Post free. Plus VAT.

ready assembled £49.50 per pair. Post free. Plus VAT.

Trade enquiries welcomed.

Demonstrations by telephone appointment.

SOUND SPHERES

The little speaker with the big sound! Only 4 1/2in diameter and weighing 700 grams, it is capable of handling 10W. A very versatile little performer, ideally suited to rear channel systems, in the car, extension speakers, etc. The magnetic base enables them to be mounted virtually anywhere. Superbly finished in black, white or orange.




SPECIFICATIONS

Impedance 4-5 ohms.
Power Handling 10W.
Response 100Hz to 16kHz.

£19.95 per pair. Post free.

Plus VAT.

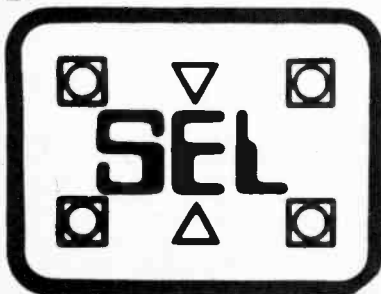

NAME PE7

ADDRESS

Please forward by return

I enclose cheque/PO/Cash

Barclaycard or Access cards welcome.

Reg. VAT No. 1182 359

Studio Electronics Ltd
LEVEL 16, TERMINUS HOUSE, HARLOW, ESSEX, CM18 6SH
Tel. Harlow 416771



CHINAGLIA



THE PROFESSIONAL QUALITY
MINOR TEST EQUIPMENT

WITH

33 RANGES
20kΩ/V d.c.
4kΩ/V a.c.

- ROBUST CLASS 1.5 PRECISION MOVEMENT
- ACCURACY 2.5% D.C. AND 3.5% A.C.
- 12 MONTH GUARANTEE
- SELF-POWERED AND POCKET-SIZED
- OPTIONAL 30kV D.C. PROBE

PRICE £16.30 inc. VAT (P. & P. 80p)
PROBE £8.80

For details of this and the many other exciting instruments in the Chinaglia range, including multimeters, component measuring, automotive and electronic instruments please write or telephone:

CHINAGLIA
(U.K.) LTD. 19 Mulberry Walk, London
SW3 6DZ Tel: 01-352 1897

TRADE ENQUIRIES WELCOMED

THE RADIO SHOP

16 Cherry Lane, Bristol BS1 3NG
Tel.: Bristol 421196. STD Code 0272

Your West Country shop for electronic components and solid state devices

PIV	THYRISTORS					
	1-6A	4A	6A	8A	10A	15A
50	0-25	0-28	0-37	0-41	0-45	0-50
100	0-28	0-30	0-42	0-47	0-50	0-58
200	0-31	0-36	0-50	0-50	0-65	0-73
400	0-40	0-57	0-77	0-85	0-97	1-15

PIV	TRIACS					
	1-6A	3-5A	6A	8A	10A	15A
100	0-28	0-52	0-61	0-68	0-72	0-80
200	0-29	0-58	0-65	0-76	0-76	1-02
400	0-38	0-67	0-70	0-85	0-88	1-51
600	0-45...	0-68	0-78	1-06	1-24	1-84


PIV	TRIACS WITH INTERNAL TRIGGERS					
	1-6A	3-5A	6A	8A	10A	15A
100	0-28	0-52	0-65	0-68	0-72	0-88
200	0-30	0-67	0-66	0-76	0-76	1-02
400	0-39	0-68	0-72	0-88	1-04	1-52
600	0-50	0-84	0-88	1-10	1-31	1-89

Quantity prices on application S.A.E.
Diacs for use with triacs 23p.

- 704 7 seg. LED display 0.3in high. £1.10.
- 707 7 seg. LED display 0.3 high, common anode. 90p.
- 747 7 seg. LED display 0.6in high, common anode. £1.75.
- NE555 Timer i.c. 8-pin DIL with data. 55p.
- 741 Op. amp. i.c. 8-pin DIL with data. 40p.
- ZN414 This is a 10 transistor TRF circuit in TO18 can with data and circuit. 75p.
- TBA800 Linear integrated circuit audio power amplifier, 2W with data. 80p.
- LATEST Decon-Dalo PC33, Quick Dri, etch-resist pen. 80p.
- 1000MFD 35V wire ended 1/2in x 1 1/2in. Only 20p.
- 2200MFD 16V wire ended 1/2in x 1 1/2in. Only 12p.

Catalogue 15p post paid.
Please add 25% VAT to all listed prices.
Postage and packing 15p per order.
Callers welcome.

INTER-LOCKING PLASTIC STORAGE DRAWERS

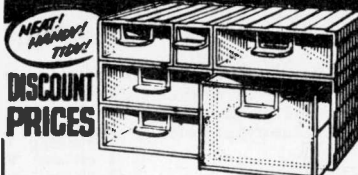

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

BUY AT DISCOUNT PRICES!

SINGLE UNITS (1D) (5ins x 2 1/2ins x 2 1/2ins). £2 DOZEN.

DOUBLE UNITS (2D) (5ins x 4 1/2ins x 2 1/2ins). £3-50 DOZEN.

TREBLE (3D) £3-50 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D2), £4-90 for 8.

EXTRA LARGE SIZE (6D1) £4-50 for 8.

PLUS QUANTITY DISCOUNTS!

Orders over £20, less 5%.
Orders over £60, less 7 1/2%.

PACKING/POSTAGE/CARRIAGE: Add 50p to all orders under £10. Orders £10 and over, please add 10% carriage.

QUOTATIONS FOR LARGER QUANTITIES
Please add 8% V.A.T. to total remittance

FLANNERY (Dept. PE7), 124 Cricklewood Broadway, London, N.W.2
Tel. 01-450 4644

GETTING THE MOST OUT OF YOUR ELECTRONIC CALCULATOR

by W. L. Hunter Price £2.10

IC OP-AMP COOKBOOK by W. G. Jung. Price £6.95.

THE AUDIO HANDBOOK by G. J. King. Price £3.25.

COLOUR T.V. SERVICING by G. J. King. Price £4.75.

THE RADIO AMATEUR'S HANDBOOK 1975 by A.R.R.L. Price £3.60.

DIGITAL ELECTRONICS CIRCUITS AND SYSTEMS by N. Morris. Price £2.50.

ELECTRONICS SELF-TAUGHT WITH EXPERIMENTS AND PROJECTS by J. Ashe. Price £2.10.

BASIC ELECTRONICS PROBLEMS SOLVED by D. A. Smith. Price £1.85.

WORKING WITH THE OSCILLOSCOPE by A. C. W. Saunders. Price £1.75.

TOWERS' INTERNATIONAL TRANSISTOR SELECTOR by T. D. Towers. Price £3.40.

★ PRICE INCLUDES POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON W2 1NP

Phone 01-723 4185
Closed Saturday 1 p.m.

BI-PRE-PAK

Bargains in Semi-Conductors, components, modules & equipment.

BARGAINS FROM OUR FREE CATALOGUE

6th edition. 20 large pages filled with real bargains in transistors, I.C.s, components, equipment, etc. Send large S.A.E. with 7p stamp for your FREE copy by return. Meanwhile, for prompt delivery order from our ad. this month NOW.

X-HATCH GENERATOR MK.2



Rotary selector switch provides choice of four patterns—essential for colour TV alignment. Featuring plug in IC's and a more sensitive sync-pick-up circuit. The reinforced fibre-glass case is virtually unbreakable—ideal for the engineer's toolbox—only measures 3in x 5 1/2in x 3in. Operates from three U-2-type batteries (extra).

Ready built unit only **£9.93**
P. & P., add 30p

Complete kit **£7.93**

PLASTIC POWER TRANSISTORS

40 WATT SILICON				90 WATT SILICON			
Type No.	Gain	VCE	Polarity Price	Type No.	Gain	VCE	Polarity Price
40N1	15	15	NPN 20p	90N1	15	15	NPN 25p
40N2	40	40	NPN 30p	90N2	40	40	NPN 35p
40P1	15	15	PNP 20p	90P1	15	15	PNP 25p
40P2	40	40	PNP 30p	90P2	40	40	PNP 35p

TRANSISTOR PACKS—ALL AT 50p EACH TESTED AND GUARANTEED

B79	4	IN4007 Sil. Rec. diodes 1,000 PIV 1 amp plastic	H39	6	Integrated circuits 4 gates BMC 362, 2 flip flops BMC 945
B81	10	Reed Switches, 1in long 1/4in dia. Highspeed P.O. type	H41	2	BD131/BD132 Complementary Plastic Transistors
H35	100	Mixed Diodes, Germ Gold bonded, etc. Marked and Unmarked	H65	4	40361 Type NPN Sil. transistors TO-5 can comp. to H66
H38	30	Short lead Transistors NPN Silicon Planar types Ex-equipment	H66	4	40362 Type PNP Sil. transistors TO-5 can comp. to H65

UNMARKED AND UNTESTED

B1	50	Germanium Transistors PNP, AF and RF	H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can
B66	150	Germanium Diodes Min. glass type	H67	10	3819N Channel FET's plastic case type
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	OVER A MILLION TRANSISTORS IN STOCK—All most-needed types MARKED — TESTED — GUARANTEED—SEE CATALOGUE		
B86	100	Sil. Diodes min. 1N914 glass equivalent to 1N4148			

TO CLEAR

Hundreds of various portable transistor radio chassis FM and AM. Ideal for experimenters. Components electronically sound, chassis not all perfect. No instructions, or tuning drives. A cheap way to make a radio set. **£1** Each

MAINS TRANSFORMERS

P. & P., add 35p per unit
Type A—18V/1A (suit SS. 103) £1.50.
Type B—25V/2A (suit SS. 110) £2.00.
Type C—30V/2A (suit SS. 140) £3.25.

Bridge Rectifiers: Type A 27p; Types B & C 36p.

CAPACITOR DISCHARGE IGNITION KIT

Easy to assemble and fit to your car. 12V. With instructions. (P. & P. add 30p) **£7.50**

TERMS OF BUSINESS

V.A.T. Prices shown do NOT include V.A.T. Please add 25% to total value of your order including postage for V.A.T. except for items marked ● or (8%) for which the V.A.T. rate is 8%. No V.A.T. on overseas orders. Overseas—add £1, any difference being charged or refunded. PAYMENT Cash with order. Cheque or money order. Minimum value—£1. You can also pay by ACCESS. IMPORTANT—Every effort is made to ensure accuracy of prices and description at time of preparing this advertisement and going to press. Prices are subject to alteration without notice.

BI-PRE-PAK LTD

Co Reg No B20019

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.

TELEPHONE: SOUTHEND (0702) 46344.


WRITE ORDER SEPARATELY AND ATTACH COUPON IF NECESSARY

CHALLENGING VALUES!



Stirling Sound

STIRLING SOUND AUDIO MODULES come to you as basic units assembled on P.C.B.s enabling you to add required components in layouts of your own choice. Modules are tested and boxed before despatch and include well printed instructions.

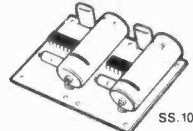


SS.103-3

AMPLIFIER MODULES

Pre-amplifiers; tone control


- SS.100 Active tone control unit to provide bass, treble, balance and volume controls **£1.60**
- SS.101 Pre-amp for ceramic cartridge, tape and radio **£1.60**
- SS.102 Pre-amp for low output magnetic cartridge tape and radio. With R.I.A.A. correction $\pm 1\text{dB}$ at 1kHz **£2.25**

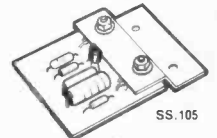


SS.105

POWER AMPLIFIERS

- SS.103 Compact I.C. amp. with 3 watts R.M.S. output. Operating voltage 10-20. Size 3 1/2in x 2in. **£1.75**
- SS.103-3 Stereo version of above using one I.C. on each channel **£3.25**
- SS.105 A compact and useful all-purpose amplifier which will run excellently on a 12V supply. With 5 watt output, two make a good stereo amp. Size 3 1/2in x 2in. New Mk. 2 version. **£2.25**
- SS.110 Similar in size to SS.105 but with a 10 watt output. Ideal for many domestic and small-size P.A. applications. Operates from 26-32V. **£2.70**
- SS.140 Excellently designed 40 watt R.M.S. (into 4 ohms) hi-fi amplifier. S/N ratio better than 75dB. T.H.D. better than 0.2%. Power requirements—45V d.c. With 0.15in centre edge connections. Two can be bridged to give 80 watts R.M.S. into 8 ohms. **£3.60**

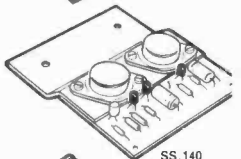


SS.140

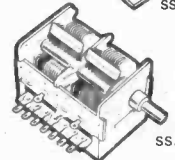

SS.201

BUILD A STEREO F.M. TUNER!


- SS.201 Front end with ganged tuning and geared slow-motion drive in rugged housing. Excellent sensitivity. Tunes 88-108MHz. With A.F.C. facility. Operates from 6-16V. **£6.25**
- SS.202 I.F. stage (with I.C.). Pre-tuned. A.F.C. connection. Operates from 4.5-14V. **£5.25**
- SS.203 Stereo Decoder. Designed essentially for use with SS.201 and SS.202, this module can also be used on most mono F.M. tuners. A L.E.D. may be attached. Operating voltage 9-16V d.c. **£5.62**

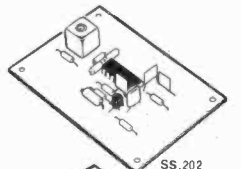

SS.202

SPECIAL MONEY SAVING OFFER!

Save £5—buy all 3 units (SS.201, SS.202 and SS.203) together for **£12.12**

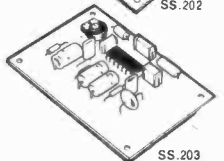

SS.203

POWER SUPPLY STABILISER

SS.300 Add this to an unregulated supply (say typically 45V output) to obtain a steady powerful working output adjustable from 12 to 60V. Essential for your audio and special systems. Money saving, very reliable and ideal for the workbench. **£3.25**

STIRLING SOUND DISCO MINOR

Twin turntable console with cross-fade mic (with over-ride) and headphone monitor jacks, etc. plus unique 'AMPOWER 40' speaker with built in 40 watt R.M.S. power amp. You can add up to ten to give 400 watts! Portable console and one AMPOWER £100 plus £3.50 carr. U.K., plus VAT.

Have you had your FREE CATALOGUE?

To BI-PRE-PAK, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX

Please send

for which I enclose inc. V.A.T.

NAME

ADDRESS PE7

RTVC*

NEW!

VISCOUNT IV STEREO SYSTEM

System 1a. £69.00

The new 20+20 watt Stereo Amplifier incorporating the latest silicon transistor solid state circuitry, the RT-VC VISCOUNT IV gives you a powerful 20 watts RMS per channel into 8 ohms. Superb teak-finished cabinet, with anodised fascia to harmonise with any decor. Polished trim and knobs.

The VISCOUNT IV has a comprehensive range of controls — volume, bass, treble, balance, mono/stereo, mode selector, and scratch filter.

Front panel socket for stereo headphones. And a host of sockets at the rear — for left and right speakers, tape recorder, auxiliary, tuner, disc and microphone.

SPECIFICATION: 20 watts RMS per channel 40 watts peak. Suitable 8-15 ohms speakers. Total distortion @ 10 watts better than 0.2%. Six switched inputs: 1. Magnetic P.U. — 3 millivolts @ 47 K ohms (R.I.A.A.); 2. Crystal/ceramic P.U. — 50 millivolts @ 50 K ohms (R.I.A.A.); 3. 4, 6, 8 Tape Tuner/Aux. — 140 millivolts @ 50 K ohms (flat frequency response); 5. Microphone — 3 millivolts @ 50 K ohms (flat frequency response).

CONTROLS: Push button ON/OFF, stereo/mono, scratch filter, 6 position rotary selector. Individual rotary controls for treble, bass, balance and volume. Headphone socket, tape out socket. Aux. mains output. Frequency response: 25 Hz to 25 KHz @ full rated output. Signal to noise ratio: better than —50 dB on all inputs. Tone control range: Bass ±15 dB @ 50 Hz; Treble ±12 dB @ 10 KHz. Power requirements: 200-250V A.C. mains @ 60 watts. Approx. size: 15½" x 3" x 10". Garrard SP 25 deck with magnetic cartridge, de luxe plinth and cover.

Two Duo Type IIa matched speakers — Enclosure size approx. 19½" x 10½" x 7½" in simulated teak. Drive unit 13" x 8" with 3" tweeter. 15 watts handling 30 watts peak. Complete System with these speakers £69.00+£6.50 p & p.

System 2. £85.00

Viscount IV amplifier (As System 1a)
Garrard SP 25 deck (As System 1a)
Two Duo Type III matched speakers — Enclosure size approx. 27" x 13" x 11½". Finished in teak simulate. Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters 20 watts RMS, 8 ohms frequency range — 20 Hz to 18,000 Hz. Complete System with these speakers £85.00+£7.60 p & p.

PRICES: SYSTEM 1a

Viscount IV RT03 amplifier £25.00+£1.90 p & p.
2 Duo Type IIa speakers £30.00+£6.50 p & p.
Garrard SP 25 with Mag. cartridge de luxe plinth and cover £24.50+£3.30 p & p.
Total if purchased separately: £79.50
Available complete for only: £69.00+£6.50 p & p.

PRICES: SYSTEM 2


Viscount IV RT03 amplifier £25.00+£1.90 p & p.
2 Duo Type III speakers £46.00+£7.50 p & p.
Garrard SP 25 with Mag. cartridge de luxe plinth and cover £24.50+£3.30 p & p.
Total if purchased separately: £95.50
Available complete for only: £85.00+£7.60 p & p.



20x20 SYSTEM

Scotland P & P Surcharge
System 1a £1.75 System 2 £3.50

EMI SPEAKERS AT FANTASTIC REDUCTIONS

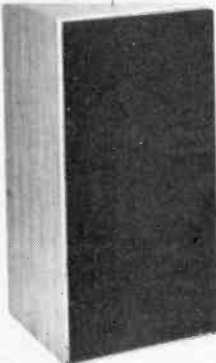

LE-4 SPEAKERS

Superb performance and beautifully finished in selected teak veneers. A professional standard four-way speaker system giving 25 watts RMS power handling. Bass unit is 14" x 9" with 8" x 5" unit for mid-range and twin 3" high frequency units to give monitor type quality and performance.

Specification — Size 33" x 14" x 16" approx. Impedance 8 ohms. Power handling 25W RMS. (Peak 50 watts.) Frequency range 35 Hz—20 KHz.


Our Price £34.00
(normally £66.00)+£5.80 p & p.

EMI 350 KIT

System consists of a 13" x 8" approx. woofer with a 3" tweeter, crossover components and circuit diagram. Frequency response: 20 Hz to 20 KHz. Power handling 15 watts RMS into 8 ohms. (Peak 30 watts.)

Complete with crossover Components and circuit diagram **£6.50+£1.20 p & p.**

20 WATT SPEAKER SYSTEM*

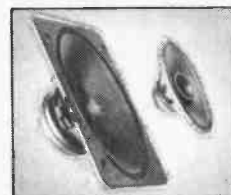

System consists of a 13" x 8" (approx.) elliptical woofer unit with a 8" x 5" (approx.) mid-range unit incorporating parasitic tweeter and crossover components and circuit diagram

Technical Specification: Bass Unit: Flux density — 100 K, speech coil — 1½". Cone. Triple laminated paper with P.V.C. surround. Mid-Range Unit: Flux density — 33 K, speech coil — 1" with parasitic tweeter. Power handling: 20 watts RMS, impedance — 8 ohms, frequency response —

Our Price £8.70
Complete+£1.60 p & p.

EASY TO BUILD SPEAKER KITS

These superb simulated teak-finished speaker kits have been specially designed by RT-VC for the cost-conscious hi-fi enthusiast who wants top quality speakers but doesn't want to spend the earth. Built to EMI's exacting specification, these new RT-VC speaker kits (350 type kit) incorporate 13" x 8" woofer, 3½" tweeter and matching crossover.

Easily put together with just a few basic tools. **Specification (each speaker):** Impedance 8 ohms. Power handling 15 watts RMS (30 watts peak). Response 20—20,000Hz. Size 20" x 11" x 9½" approx. Comparable built units (EMI LE3) sold elsewhere for over £45 pair.


£22.00 pair complete
+£5.20 p & p. Complete with crossover Components and circuit diagram



DECCA STEREO AMPLIFIER CHASSIS

Specification: 4+4 watts into 8 ohms. Input Sensitivity 4mV into 47K (for magnetic cartridges). AC Mains only 240V. Controls — volume, bass, treble, on/off, mono/stereo switch. Chassis size 11" x 5½" x 3¼" approx.

£6.90+£1.20 p & p.

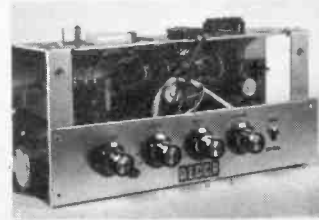

PUSH BUTTON CAR RADIO KIT— THE TOURIST TT*



NO SOLDERING REQUIRED

NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO

Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly.

Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.


TECHNICAL SPECIFICATION: (1) Output 4 watts RMS output. For 12 volt operation on negative or positive earth. (2) Integrated circuit output stage, pre-built three stage IF Module.

Controls volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands.

Size chassis 7" wide 2" high and 4½" deep approx. **£9.50** +£1.05 p & p. Speaker including baffle and fixing strip **£2.00** +45p p & p. Car Aerial Recommended — fully retractable **£1.60** +40p p & p.

The Tourist I Kit for the experienced constructor. If you can solder on a printed circuit board you can build this model. Same technical specification as Tourist TT. **Price £8.20** +£1.05 p & p.

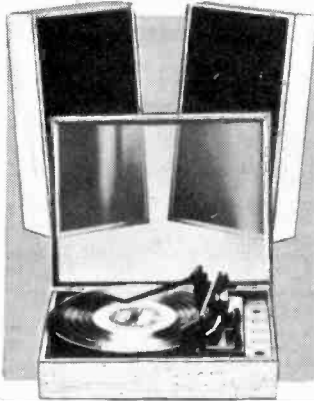*STEREO 21 QUALITY SOUND FOR LESS THAN £24.00



Stereo 21, easy to assemble audio system kit. No soldering required.

The unit is finished in white P.V.C. and the acrylic top presents an unusually interesting variation on the modern deck plinth.

Includes — BSR 3 speed deck, automatic, manual facilities together with stereo cartridge.

Two speakers with cabinets.

Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

Specifications — For the technically minded:

Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel. Output impedance 8–15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs — radio, tape, etc. and outputs for taping discs.


Overall Dimensions. Speakers approx 15½" x 8" x 4". Complete deck and cover in closed position approx. 15½" x 12" x 6".

Complete only £23.20 +£3.00 p & p.

Extras if required. Optional Diamond Stylus **£1.60**.

Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance **£5.80**.

*DISCO AMPLIFIER

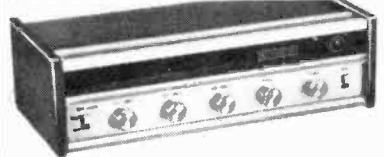

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Output 20 watts RMS into 8 ohms (suitable for 15 ohms).

Inputs * 4 electrically mixed inputs. * 3 individual mixing controls. * Separate bass and treble controls common to all 4 inputs. * Mixer employing F.E.T. (Field Effect Transistors). * Solid State circuitry. * Attractive styling.

INPUT SENSITIVITIES — Input — 1). Crystal mic. guitar or moving coil mic, 2 and 10mV. (Selector switch for desired sensitivity.) — Inputs — 2), 3), 4). Medium output equipment — ceramic cartridge, tuner, tape recorder, organs, etc. — all 250mV sensitivity. AC Mains, 240V operation. Size approx. 12½" x 6" x 3½".


£20.00 +£1.35 p & p.

*8 TRACK HOME CARTRIDGE PLAYER



Elegant self selector push button player for use with your stereo system. Compatible with Viscount IV system, Unisound module and the Stereo 21. Technical specification Mains input. 240V. Output sensitivity 125mV. Comparable unit sold elsewhere at **£24.00** approx. Yours for only

£16.20 +£1.70 p & p.

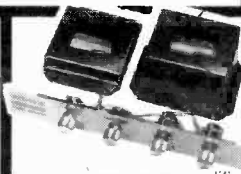


BUILD YOUR OWN *STEREO AMPLIFIER

For the man who wants to design his own stereo — here's your chance to start, with Unisound — pre-amp, power amplifier and control panel. No soldering — just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

Also available with 2 speakers (7" x 4") **£10** +£1.75 p & p. **£8.95** +£1.05 p & p.

PORTABLE DISCO CONSOLE*

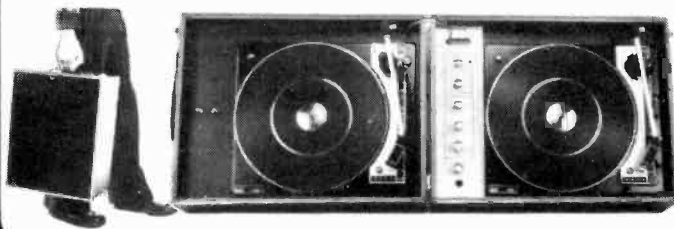

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables. Two B.S.R. MP60 type single play professional series decks, fitted with crystal cartridges.

TECHNICAL SPECIFICATION:

Pre-amp — Output — 200mV. Auxiliary inputs — 200mV and 750mV into 1 meg. Mic input — 6mV into 100K. 240 volt operation. Turntables capacity — 7", 10" or 12" records. Rumble, wow and flutter Rumble Better than —35dB. Wow Better than 0.2%. Flutter Better than 0.06% (GauMont kalee meter).

Finish — Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

Console size —

Unit Closed — 17½" x 13½" x 8½" (app.)
Unit Open — 35½" x 13½" x 4½" (app.)
This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.

The unit is finished in black PVC with contrasting simulated teak edging, diamond spun control knobs with matching control panel.

Yours for only

£57.00 +£6.50 p & p.



DO NOT SEND CARD

Just write your order giving your credit card number

Mail orders to action. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K.

Leaflets available for all items listed thus* Send stamped addressed envelope. All items subject to availability. Prices correct at 1st May 1975 and subject to change without notice.

All prices include V.A.T. at 25% rate



21D HIGH STREET, ACTON, LONDON W3 6NG
323 EDGWARE ROAD, LONDON W2

Personnal Shoppers EDGWARE RD: 9 a.m.—5.30p.m. Half day Thurs.
ACTON: 9.30a.m.—5p.m. Closed all day Wed.



GIRO NO. 331 7056. Access accepted.
C. W. O. only. P. & P. 15p on orders below £5.
Discount: £10-10% (except net items)
Export Order enquiries welcome (VAT free)

Official Orders accepted from
Educational & Government Departments
ALL PRICES INCLUDE VAT AT 8%

SPECIAL RESISTOR KITS (Prices include post & packing)

10E12 ½W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.85 net
10E12 ¼W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.95 net
25E12 ½W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £9.00 net
25E12 ¼W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £9.00 net
5E12 ½W KIT: 5 of each E12 value, 10 ohms—1M, a total of 305 (METAL FILM 5%), £3.45 net
Due to current world shortages, resistor kits may contain some wattage and value substitutions.

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. Mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 31p. 0.068µF, 0.1µF, 44p. 0.15µF, 5p. 0.22µF, 6p. 0.33µF, 8p. 0.47µF, 10p. 0.68µF, 13p. 1.1µF, 16p. 1.5µF, 24p. 2.2µF, 27p.

MULLARD POLYESTER CAPACITORS C296 SERIES
400V, 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 3p. 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 31p. 0.047µF, 0.068µF, 0.1µF, 44p. 0.15µF, 7p. 0.22µF, 9p. 0.33µF, 13p. 0.47µF, 15p.
160V: 0.01µF, 0.15µF, 0.022µF, 3p. 0.047µF, 0.068µF, 31p. 0.1µF, 44p. 0.15µF, 5p. 0.22µF, 6p. 0.33µF, 7p. 0.47µF, 9p. 0.68µF, 13p. 1.1µF, 15p.

MINIATURE CERAMIC PLATE CAPACITORS
50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0.01, 0.015, 0.022, 0.033, 0.047, 24p. each. 0.1, 30V, 5p.

POLYSTYRENE CAPACITORS 160V 5%
(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10,000, 41p.

RESISTORS

CF—High Stab Carbon Film, 5%	MF—High Stab Metal Film, 5%	Size mm			
W. Type Range 1-99	100-499	500-999	1000+		
½ CF 12-1M	1	0.80	0.65	0.60	2.4x7.5
½ CF 22-2M2	1	0.80	0.65	0.60	3.9x10.5
½ CF 22-1M	1	0.80	0.65	0.60	5.5x16
½ MF 10-2M7	2	1.7	1.4	1.2	3x7
1 MF 10-2M2	2	1.6	1.3	1.1	4.2x10.8
1 MF 10-10M	3	1.98	1.81	1.65	6.6x13
2 MF 10-10M	4.5	3.52	3.08	2.75	8x17.5

For value mixing prices, please refer to our catalogue. (Price in pence each). VALUES AVAILABLE—E12 Series only. (Net prices above 100.)

PRESET SKELETON POTENTIOMETERS

MINIATURE 0-25W Vertical or horizontal 7p each I, K, 2K, 4K, 7K, 10K, etc. up to 1M Ω
SUB-MIN 0-05W Vertical, 100 Ω to 220K Ω 7p each.



B. H. COMPONENT FACTORS LTD.

(P.E.), LEIGHTON ELECTRONICS CENTRE,
59 NORTH STREET, LEIGHTON BUZZARD,
LU7 7EG. Tel.: Leighton Buzzard 2316 (Std. Code 05253). CATALOGUE No. 4, 20p.

Miniature Mullard Electrolytics

1.0µF 63V	7p	68µF 16V	7p
1.5µF 63V	7p	68µF 63V	14p
2.2µF 63V	7p	100µF 10V	7p
3.3µF 63V	7p	100µF 25V	7p
4.0µF 40V	7p	100µF 63V	17p
4.7µF 63V	7p	150µF 16V	7p
6.8µF 63V	7p	150µF 63V	17p
8.0µF 40V	7p	220µF 6.4V	7p
10.1µF 16V	7p	220µF 10V	7p
10.1µF 25V	7p	220µF 16V	8p
10.1µF 63V	7p	220µF 63V	21p
15µF 16V	7p	330µF 16V	8p
15µF 63V	7p	330µF 63V	25p
16µF 40V	7p	470µF 6.4V	14p
22µF 25V	7p	470µF 40V	26p
22µF 63V	7p	680µF 16V	8p
32µF 10V	7p	680µF 40V	25p
33µF 16V	7p	1000µF 16V	17p
33µF 40V	7p	1000µF 25V	28p
32µF 63V	7p	1500µF 6.4V/25p	
47µF 10V	7p	1500µF 16V	28p
47µF 25V	7p	2200µF 10V	17p
47µF 63V	8p	3300µF 6V	28p

VEROBOARD 0.1 0.15

2½ x 5"	36p 36p
2½ x 3½"	33p 25p
3½ x 5"	43p 46p
3½ x 3½"	36p 36p
2½ x 1"	10p 9p
2½ x 5" (Plain)	— 19p
2½ x 3½" (Plain)	— 16p
5 x 3½" (Plain)	— 29p
Insertion tool	73p 73p
Track Cutter	56p 56p
Pins, Pkt. 25	23p 22p

POTENTIOMETERS

CarbonTrack 5K Ω to 2M Ω, log or lin (and 1K lin). Single, 17½p Dual Gang 48p. Log single with switch 28p. Slider Pots. 10K, 100K, 500K, semi log 30mm, 34p. 45mm, 47p. 60mm, 55p.

DIODES

IN4001 7½p	Din 2 Pin	12p
IN4002 7½p	3 Pin	13p
IN4003 42p	5 Pin 180°	16p
IN4004 9p	Std. Jack	20p
IN4005 12p	2.5mm jack	13p
IN4006 14p	Phono	7p
IN914 1p	Din 2 Pin	10p
IN916 7p	3 Pin	13p
BA109 10p	5 Pin 180°	12p
OAS 42p	Std. Jack	18p
OA47 11p	2.5mm Jack	13p
OA200 8p	Phono	7p

PLUGS

IN4001 7½p	Din 2 Pin	12p
IN4002 7½p	3 Pin	13p
IN4003 42p	5 Pin 180°	16p
IN4004 9p	Std. Jack	20p
IN4005 12p	2.5mm jack	13p
IN4006 14p	Phono	7p

ELECTROLYTIC CAPACITORS. Tubular & Large Cans

(µF/V): 1/25, 2/25, 4/25, 4.7/10, 5/25, 8/25, 10/10, 10/50, 16/25, 22/63, 25/25, 25/50, 32/25, 50/25, 100/10, 100/25, 7p, 50/50, 8p, 100/50, 200/25, 10p, 250/50, 18p, 500/10, 8p, 500/25, 17p, 500/50, 25p, 1000/10, 17p, 1000/25, 25p, 1000/50, 40p, 2000/10, 20p, 1000/100, £1.10, 2000/25, 35p, 2000/100, £1.20, 2500/25, 38p, 2500/50, 68p, 5000/25, 68p, 5000/50, £1.20.


HI-VOLT: 4/350, 20p, 8/350, 23p, 100/100, 27p, 16/350, 35p, 16/450, 38p, 32/350, 38p, 50/250, 40p, 100/250, 40p.

METALLISED PAPER CAPACITORS

250V: 0.05µF, 0.1µF, 6p, 0.25, 6p, 0.5µF, 7½p, 1µF, 9p, 500V: 0.025, 0.05, 6p, 0.1, 6p, 0.25, 7½p, 0.5, 9p, 1000V: 0.01, 11p, 0.022, 13p, 0.047, 0.1, 19p, 0.22, 28p, 0.47, 36p.

MULTIMETER U4323

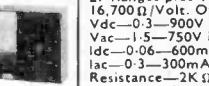
22 Ranges plus AF/IF Oscillator, 20,000Ω/Volt.
Vdc—0.5—1000V in 7 ranges
Vac—2.5—1000V in 6 ranges
Idc—0.05—500mA in 5 ranges
Resistance—5Ω—1M Ω in 4 ranges
Accuracy—5% of F.S.D.
OSCILLATOR—1 KHz and 465KHz (A.M.) at approx. 1 Volt.
Size—160 x 97 x 40mm.
Supplied complete with carrying case, test leads and battery.
PRICE £8.64 net P. & P. 50p.



U4323

MULTIMETER U4341

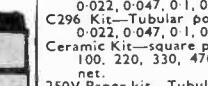
27 Ranges plus Transistor Tester, 16,700Ω/Volt. Overload protected.
Vdc—0.3—900V in 8 ranges.
Vac—1.5—750V in 6 ranges.
Idc—0.06—600mA in 5 ranges.
Iac—0.3—300mA in 4 ranges.
Resistance—2K Ω—2M Ω in 4 ranges. Accuracy—dc—2½%, ac—4% of F.S.D.
Ife—10—350 in 2 ranges.
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £11.88 net P. & P. 50p.



U4341

MULTIMETER U4324

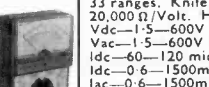
34 Ranges. High sensitivity, 20,000Ω/Volt. Overload protected.
Vdc—0.6—1200V in 9 ranges.
Vac—3—900V in 8 ranges.
Idc—0.06—3A in 6 ranges.
Iac—0.3—3A in 5 ranges.
Resistance—25 Ω—5M Ω in 5 ranges.
Accuracy—dc and R—2½% of F.S.D. ac and db—4% of F.S.D.
Size—167 x 98 x 63mm.
Supplied complete with storage case, test leads, spare diode, and battery.
PRICE £10.64 net P. & P. 50p.



U4324

MULTIMETER U4313

33 Ranges. Knife edge with mirror scale, 20,000Ω/Volt. High accuracy, mVdc—75mV.
Vdc—1.5—600V in 9 ranges.
Vac—1.5—600V in 9 ranges.
Idc—60—120 microamps in 2
Idc—0.6—1500mA in 6 ranges.
Iac—0.6—1500mA in 6 ranges.
Resistance—1K Ω—1M Ω in 4 ranges.
db scale—10 to +12db.
Accuracy—dc—1%, ac—2½%.
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £14.90 net P. & P. 50p.

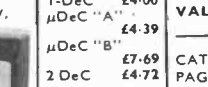

U4313

INVERTORS

240V—50Hz from your 12V car battery.	150W—£18.30 + 80p p & p.
25W—£3.90 + 30p p & p.	30W (12V)—£28.80 + £1.05 p & p.
40W—£6.80 + 55p p & p.	300W (24V)—£22.70 + £1.05 p & p.
75W—£9.96 + 75p p & p.	

All above invertors are in kit form but may be purchased built up and ready for use. Price list sent on receipt of stamped addressed envelope.

P.W. AUTOMATIC EMERGENCY SUPPLY

250V—50Hz—150W inverter with built in battery charger, in event of power failure switches over automatically from battery charging to inverter operation. Cct as appeared in Dec. 73 P.W. Complete kit of parts (excluding meter) £22.50 + £1.10 p & p.

COMPLETE FLUORESCENT LIGHT INVERTOR KIT

8W—12V—Fluorescent light, suitable for tents, caravans, houses, boats and secondary lighting for factories, hotels etc. 12in—8W £2.90 + 25p p & p. 21in—15W £3.30 + 30p p & p.

TRANSFORMERS AND COILS

Both high volume and small order capacity available for Mains, R.F., and I.F. Transformers. Before you buy elsewhere let us quote you and see what you save. V.A.T. at 8% included

TRADE AND EXPORT ENQUIRIES WELCOMED

ASTRO ELECTRONICS, 10A SPRINGBANK ROAD, CHESTERFIELD, DERBS.

NEW! SOUP UP YOUR TUNER!

New De-Luxe I.F. Strip

- SHARP SKIRT SELECTIVITY
- CONTROLLABLE SQUELCH
- CENTRE ZERO TUNING METER + SIGNAL STRENGTH METER OUTPUT

This I.F. Amp. has a low noise pre-amplifier stage. Matching two 10-7MHz filters into an I.C./I.F. amp. Full application notes available, send S.A.E. + 8p.

SEND **£8.60** (includes VAT and P. & P.)

Sole U.K. Agents: **REEDHAMPTON LTD**
182-184 Addington Road, Selsdon, Surrey CR2 8LB

SUPERSOUND 13 HI-FI MONO AMPLIFIER

A superb solid state audio amplifier. Brand new components throughout. 3 Silicon transistors plus 2 power out-put transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE £15.00. P. & P. 65p.

DE LUXE STEREO AMPLIFIER

A.C. mains 200-240 v. Single heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line-up: 2 x ECL86 Triode Pentodes, 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" x 4 1/2". Overall height including valves 5". Ready built and tested to a high standard. £12.50. P. & P. 65p.

ALL PURPOSE POWER SUPPLY UNIT 200/240V. A.C. input. Four switched fully smoothed D.C. outputs giving 6v, and 7 1/2v, and 9v, and 12v, at 1 amp on lead wire. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/4" x 2 1/2". Ready built and tested. PRICE £6.35. P. & P. 55p.

VYNAIR & REKINE SPEAKERS & CABINET FABRICS per yd. in. (incl. 1 yd.). S.A.E. for samples.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 8 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New completely wired and tested with good quality output transformer. P. & P. 60p. BARGAIN PRICE £5.00

FEW ONLY. High grade mains transformer with grain orientated lamination. Primary 200/240. Secondary 15.5 volts at 0.6 amps and 4.6 volts at 0.3 amps. Size 2in. long x 2 1/2in. wide x 2in. deep overall. £1.40 plus 35p P. & P.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations 0-5-10-15-20-25-30-35-40-50-60v. half wave at 1 amp, or 10-0-10, 20-0-20, 30-0-30v, at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £2.75. P. & P. 65p.

MAINS TRANSFORMER For power supplies. Pro. 200/240V. Sec. 9-0-9 at 500 mA. £1.35. P. & P. 30p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. £1.50. P. & P. 30p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. £2.20. P. & P. 40p.

3 VOLT RELAY. 100 m/a single pole normally closed. 2 for 60p. P. & P. 15p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/4" x 1 1/4". Brand new complete with instructions. Price £1.36. P. & P. 15p.

HANDBOOK OF TRANSISTOR EQUIVS. AND SUBS. A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 7p.

3 Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristic, diode and transistor equivalents. Many thousands of up to date European types listed. Diode Equivalents £1. Transistor Equivalents £1.20. Transistor Characteristics £1.40. POST FREE All three together £3.20.

NEW ISSUE

Thyristor, Triac, Diac etc. encyclopedias £1.70. Post Free. 8 pole 3 way 2 bank low loss Yaxley type switches 1 1/2" standard spindle. 2 switches 75p + 15p P. & P.


Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday. Closed Wednesday. Prices and specifications correct at time of press. Subject to alteration without notice

HARVERSON SURPLUS CO. LTD.

(Dept. P.E.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station
SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

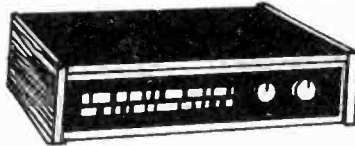HARVERSON MAINS OPERATED SOLID STATE STEREO FM TUNER



Enjoy Fabulous Stereo Radio at this Low Introductory Price!

Designed and styled to match our 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high-gain, low noise IF stages. Automatic frequency control to "lock on" station and prevent drift. IC stereo decoder for maximum stereo separation. L.E.D. for stereo beacon indicator. Nominal output of tuner 100mV. Approximate size 12in wide x 8in deep by 2 1/2in high. Supplied ready built, fully tested and fully guaranteed (not available in kit form). PRICE £27.50. Post and Packing £1.00.

STEREO-DECODER SIZE 2" x 3" x 1 1/2"

Ready built. Pre-aligned and tested. Sens. 20-560mV for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £6.25 plus 15p P. & P. Stereo beacon light if required 45p extra.

LATEST HI SENSITIVITY UNI-DIRECTIONAL SLIM-LINE CONDENSER MICROPHONE as used by many professionals. Very low acoustic feedback. Available Hi impedance or low impedance. State which required. £18.25. P. & P. 25p.

LATEST ACOS GP29/150 mono compatible cartridge with 1/2" stylus for LP/EP/78. Universal mounting bracket. £1.75. P. & P. 15p.

CERAMIC STEREO CARTRIDGE. Universal mounting brackets and turnover stylus. 70mV per channel output. ONLY £2.06. P. & P. 15p.

SONOTONE STABCOMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2.62. P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3.18. P. & P. 15p.

LATEST RONETTE T/O STEREO COMPATIBLE CARTRIDGE GP/PL/Stereo 78 £1.88. P. & P. 15p. **LATEST T/O MONO COMPATIBLE CARTRIDGE** for playing EP/EP/78 mono or stereo records on mono equipment. Only £1.75. P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK. II A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 8 ohm speaker. Size 7in wide x 3in deep x 6in high. Ready built and tested. PRICE £8.50. P. & P. 75p. ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £7.75. P. & P. 75p.

HI-FI LOUDSPEAKER SYSTEM Mk II

Beautifully made simulated teak finish enclosure now with most attractive slatted front. Size 16 1/2" high x 10 1/2" wide x 8" deep (approx.). Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, H.F. tweeter unit and crossover. AVAILABLE IN NOMINAL 4 ohm, 8 ohm or 15 ohm impedance (static whch). OUR PRICE £11.25 each. Carr. £1.25

Cabinet Available Separately £6.25. Carr. £1.10. Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £10.00. Carr. £1.25.

LOUDSPEAKER BARGAINS

5in. 3 ohm £1.45. P. & P. 15p. 7 x 4in. 3 ohm £1.60. P. & P. 25p. 10 x 6in. 3 or 15 ohm £2.50. P. & P. 35p. E.M.I. 8 x 5in. 3 ohm with high flux magnet £2.06. P. & P. 25p. E.M.I. 13 1/2 x 8in. with high flux ceramic magnet with crossover network £3. 8 or 15 ohm £4.12. P. & P. 35p. E.M.I. 13 x 8in. 3 or 15 ohm with inbuilt tweeter and crossover network £5.50. P. & P. 35p. E.M.I. tweeter. Approx. 3 1/2". Available 3 or 8 or 15 ohms, £2.00 + 25p. P. & P.

BRAND NEW. Bakers Loudspeakers at substantial discounts. 12in. 15w. 1 1/2" D Speakers, 3, 8 or 15 ohms. State which. Current production by well-known British maker. Now with Hifux ceramic ferrobar magnet assembly £9.50. Guitar models: 25w. £9.50. 35w. £11.50. P. & P. 75p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for details. Only £7.68 each. P. & P. 60p. NOW ALSO AVAILABLE 8in. 10W rms 20W peak 40Hz-20,000Hz. Overall depth 1in. Ideal for Hi-Fi or for use in cars. £5.18. P. & P. 40p.

SPECIAL BARGAIN OFFER! Limited number of BSR C123 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge. Brand new. ONLY £9.50 + p. & p. 60p.

HARVERSON SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specifications: Power output: 14 watts r.m.s. per channel into 8 ohms. Frequency response \pm 3dB 12-30,000 Hz. Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass, boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h.

Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E. **AMPLIFIER KIT** £15.00. P. & P. 50p (Magnetic input components 33p extra) **POWER PACK KIT** £5.35 P. & P. 65p **CABINET** £5.35 P. & P. 15p (Post Free if all units purchased at same time) Full after sales service.

Also available ready built and tested £22.50. Post Free. Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.

3-VALVE AUDIO AMPLIFIER HA34 MK II. Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4 1/2" x 4 1/2" h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 8 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £7.75. P. & P. 70p.

HE "POWER" AMPLIFIER KIT. Similar in appearance to HA34 but employs entirely different and advanced circuitry. Complete set of parts, etc. £6.50. P. & P. 70p.

10/14 WATT HI-FI AMPLIFIER KIT A stylish finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate base and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 25p x S.A.E. (Free with parts). All parts sold separately. ONLY £12.00. P. & P. £1.00. Also available ready built and tested £16.50. P. & P. £1.00.

HI-FI STEREO HEADPHONES Adjustable headband with comfortable flexiform ear-muffs. Wired and fitted with standard stereo 1/4" jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £4.05. P. & P. 25p.

PRICES INCLUDE VAT

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

P.E. Portable gas ignitor kit for only £3.00

(including VAT & postage — sent anywhere in the world)


The Kit contains everything you need to make this electronic gas ignitor and includes an elegant transparent case moulded in high impact polycarbonate, ready wound coils and full assembly instruction



- Uses a 1½ volt battery
- Provides a continuous stream of high voltage sparks
- Gives years of normal use

See through case shows your skill in action.

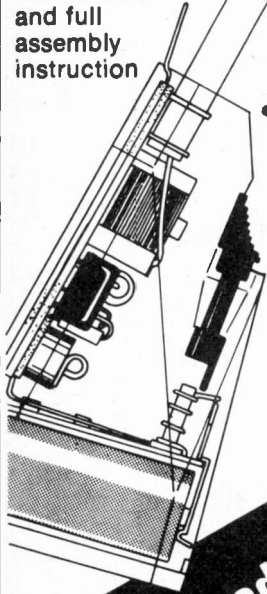Please send S.A.E. for price list of individual components.



As featured in this issue

Lights Natural, Town and bottled fuel gases quickly and easily — ideal for the kitchen, camping, boating and workshop

Please send me _____ gas ignitor kit(s) for £_____ payable
I enclose a cheque/P.O. No. _____
Name _____ Address _____
TO: Greenweld Electronics
Dept CK1, 51 Shirley
Park Rd., Southampton
SO1 4FX

- ★ ELECTRONIC PIANO KIT
- ★ SYNTHESISER KIT
- ★ ELECTRONIC ORGAN KITS



There are five superb Electronic Organ kits specially designed for the D-I-Y enthusiast. With the extreme flexibility allowed in design, you can build an organ to your requirements, which will compare with an organ commercially built costing double the price.

★ Portable organ with 4 octave keyboard, £145.29. ★ Console organ with 5 octave keyboard, £250.93. ★ Console organ with 2 x 4 octave keyboards and 13 note pedal board, £470.65. ★ Console organ with 2 x 5 octave keyboards and 32 note pedal board, £680. ★ Console organ with 3 x 5 octave keyboards and 32 note pedal board, £960. ★ W/W Sound Synthesiser Kit, £149. ★ W/W Touch Sensitive Electronic Piano, £110.

All components can be purchased separately, i.e., semiconductor devices, M.O.S. master oscillators, coils, keyboards, pedal boards, stop tabs, draw bars, key-contacts, etc. Lesley type speaker units from £50. Send 50p for catalogue which includes 5 x 10p vouchers or send your own parts list, enclosing S.A.E. for quotation.

Elvins Electronic Musical Instruments

12 Brett Road, Hackney, London E8 1JP (Tel. 01-986 8455);
8 Putney Bridge Road, London SW18 1HU (Tel. 01-870 4949);
40a/42a Dalston Lane, Dalston Junction, London E8 (Tel 01-249 5624).

Business hours: Open 10 a.m. to 7 p.m. Monday to Saturday. Closed all day Thursday. Open 10 a.m. to 1 p.m. Sunday.

Vacancy for shop assistant with electronic knowledge



4¼in x 3¼in METER. 30µA, 50µA or 100µA, £3.85. 13p P. & P.

TAPE RECORDER LEVEL METER



500µA, 70p. 10p P. & P.



CARDIOID DYNAMIC MICROPHONE

Model UD-130. Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms, £6.55. 13p P. & P.



42 x 42mm meters 100µA, 500µA, 1mA, 500mA, £2.76. 11p P. & P.

60 x 45mm meters 50µA, 100µA, 500µA and 1mA VU meter, £2.92. 11p P. & P.

Edgewise meters 90mm x 34mm 1mA, £3.40. 13p P. & P.

MULTI-METER

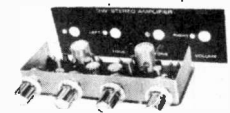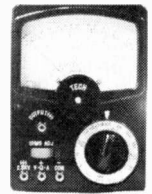Model ITI-2
20,000 ohm/volt, £6.90.
16½p P. & P.



3 WATT STEREO (1½ + 1½) PER CHANNEL AMPLIFIER
£4.30. 12½p P. & P.

All above prices include 8% V.A.T. LARGE S.A.E. for List No. 11. Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate • Bolton • Lancs. BL2 1BA

ORDER DIRECT FROM THE U.S. AND SAVE


SHIPMENT MADE WITHIN 3 DAYS FROM RECEIPT OF ORDER VIA AIR MAIL - POSTAGE PAID

10% Off on orders over £10
15% Off on orders over £50
20% Off on orders over £100

SPECIAL PURCHASE
LED DISPLAY MAN 3M
 12 p ea. 4/40p 12/£1-13p

JULY SPECIALS

POCKET CALCULATOR KIT

5 function plus constant - addressable memory with individual recall - 8 digit display plus overflow - battery saver - uses standard or rechargeable batteries - all necessary parts in ready to assemble form - instructions included 1 x 5" 

£12

ASSEMBLED £13-50

WITH ALKALINE BATTERIES £15

5262 MEMORY
 2048 bit RAM £2-90

8038 FUNCTION GENERATOR
 Voltage Controlled Oscillator Sine, Square, Triangular Output 16 Pin Dip £2-15

CT7001 CLOCK CHIP
 4 or 6 digit - 12, 24 hr - alarm - timer & date circuits £3 ea.

NINE DIGIT LED ARRAY
FAIRCHILD 37.17" DIGITS
 with clear magnifying lens

£2-90

NINE DIGIT SPERRY GAS DISCHARGE DISPLAY
 SP-425-09 1.25" x 3" overall - 25" digits - connects to 18 lead edge connector - hi voltage - prime quality £8p

4 DIGIT DISPLAY
 HP 50827414 Comm. Cathode £1-35p

5 DIGIT DISPLAY
 HP 50827405 £1-45p

DIGITAL CIRCUITS (DIP)

7447 BCD to 7 seg dec/drvr 69p
 7490 Decade Counter 35p
 74145 BCD to dec dec/drvr 65p
 74150 16 line multiplier 65p
 74175 Quad D flip flop w/clr 79p
 74192 Decade up/down counter

LINEAR CIRCUITS

555 Timer mDIP 27p
 567 Tone Deboder mDIP 95p
 747 Op-Amp Dual 741 DIP 35p

CT5002 CALCULATOR CHIP
 12 digit - 4 function - chain operation - battery operation - 28 pin £1-50p

TTL



7400 £0-11p	7448 £0-80p	74150 £0-75p
7401 11	7450 12	74151 80
7402 11	7451 13	74153 71
7403 11	7453 13	74154 1-05
7404 13	7454 14	74155 95
7405 13	7460 11	74156 71
7406 22	7464 21	74157 91
7407 22	7465 21	74161 96
7408 14	7472 22	74163 1-05
7409 14	7473 26	74164 1-25
7410 11	7474 26	74165 1-25
7411 16	7475 41	74166 1-15
7413 35	7476 26	74173 95
7415 22	7483 70	74175 95
7416 22	7485 80	74176 95
7417 22	7486 24	74177 85
7420 11	7489 1-50	74180 80
7422 22	7490 45	74181 2-50
7423 22	7491 71	74182 80
7425 22	7492 44	74184 1-55
7426 23	7493 44	74185 1-45
7427 22	7494 49	74190 95
7430 12	7495 49	74191 95
7432 22	7496 55	74192 90
7437 25	74100 1-25	74193 95
7438 21	74105 60	74194 95
7440 11	74107 27	74195 80
7441 60	74121 32	74196 1-00
7422 55	74122 50	74197 75
7443 55	74123 55	74198 1-70
7444 60	74125 50	74199 1-70
7445 75	74126 50	74200 3-90
7446 85	74141 68	
7447 80	74145 75	

LOW POWER

74L00 £0-16p	74L51 £0-16p	74L90 £0-93p
74L02 16	74L55 18	74L91 80
74L03 16	74L71 18	74L93 89
74L04 18	74L72 27	74L95 89
74L06 18	74L73 38	74L98 1-53
74L10 16	74L74 38	74L164 1-53
74L20 16	74L78 44	74L165 1-53
74L30 16	74L85 85	
74L42 89	74L86 38	

HIGH SPEED

74H00 £0-16p	74H21 £0-16p	74H55 £0-20p
74H01 16	74H22 18	74H60 21
74H04 16	74H30 18	74H61 21
74H08 16	74H40 16	74H62 20
74H10 16	74H50 16	74H74 32
74H11 16	74H52 18	
74H20 16	74H53 20	

8000 SERIES

8091 £0-33p	8214 £0-93p	8811 £0-38p
8092 33	8220 93	8812 60
8095 76	8230 1-42	8822 1-42
8121 49	8520 71	8830 1-42
8123 88	8551 91	8831 1-42
8130 1-20	8552 1-37	8836 27
8200 1-42	8554 1-37	8880 73
8210 1-92	8810 44	

9000 SERIES

9002 £0-21p	9309 £0-49p	9601 £0-54p
9301 63	9312 49	9602 49

Data sheets supplied only on request. Add 25p ea. for data supplied on items less than 50p ea.

MEMORIES w/data

1101	256 bit RAM MOS	£0-96p
1103	1024 bit RAM MOS	2-72
5203	2048 bit erasable PROM	13-68
5260	1024 bit RAM Low Power	2-16
7489	64 bit RAM TTL	1-50
8223	Programmable ROM	2-72

CALCULATOR & CLOCK CHIPS w/data

5001	12 DIG 4 funct fix dec	£1-46p
5002	Same as 5001 exc btry pwr	1-95
5005	12 DIG 4 funct w/mem	2-42
MM5725	8 DIG 4 funct chain & dec	1-10
MM5736	18 pin 6 DIG 4 funct	2-42
MM5738	8 DIG 5 funct K & Mem	2-42
MM5739	9 DIG 4 funct (btry sur)	2-42
MM5311	28 pin BCD 6 dig mux	2-42
MM5312	24 pin 1 pps BCD 4 dig mux	1-94
MM5313	28 pin 1 pps BCD 6 dig mux	2-42
MM5314	24 pin 6 dig mux	2-42
MM5316	40 pin alarm 4 dig	2-42

LED & OPTO ISOLATOR

MV108	Red TO 18	£0-14p
MV50	Axial leads	8
MV5020	Jumbo Vis. Red (Red Dome)	18
	Jumbo Vis. Red (Clear Dome)	18
ME4	Infra red diff. dome	1-18
MAN 1	Red 7 seg. 270"	2-72
MAN 2	Red alpha num. 32"	2-72
MAN 4	Red 7 seg. 190"	1-18
MAN 5	Green 7 seg. 270"	1-62
MAN 6	6" high solid seg.	3-81
MAN 7	Red 7 seg. 270"	2-74
MAN 8	Yellow 7 seg. 270"	2-17
MAN 64	4" high solid seg.	2-45
MAN 66	6" high spaced seg.	2-55
DL 707	Red 7 seg. 3"	1-18
MCT2	Opto-iso transistor	38

DTL

930	10p	937	10p	949	10p
932	10	944	10	962	10
936	10	946	10	963	10

4000 SERIES RCA EQUIVALENT

CD4001 £0-31p	CD4013 £0-66p	CD4023 £0-31p
CD4009 47	CD4016 69	CD4025 31
CD4010 47	CD4017 1-62	CD4027 74
CD4011 31	CD4019 74	CD4030 52
CD4012 31	CD4022 1-50	CD4035 1-56

Data sheets supplied only on request. Add 25p ea. for data supplied on items less than 50p ea.

CMOS

74C00 £0-21p	74C74 £0-63p	74C162 £1-78p
74C02 30	74C76 93	74C163 1-78
74C04 41	74C107 82	74C164 1-92
74C08 41	74C151 1-59	74C173 1-59
74C10 36	74C154 1-92	74C195 1-65
74C20 36	74C157 1-20	80C95 82
74C42 118	74C160 1-78	80C97 82
74C73 85	74C161 1-78	

The prices as listed are in British pounds and pence. Send bank cheque or personal cheque with order. If international postal money order is used, send receipt with order. Minimum order £2-50p.

INTERNATIONAL ELECTRONICS UNLIMITED
 P.O. BOX 1708 MONTEREY, CA. 93940 USA

PHONE (408) 659-3171

The above prices do not include any taxes leviable by a purchaser's country of residence.



The Shop Window for the Very Best...

IPC



**COMBINED
PRECISION
COMPONENTS
(PRESTON) LTD**

Department PE
194-200 North Rd,
Preston PR1 1YP
Tel: 55034
Telex: 677122.

TOSHIBA VALVES

Type	Price	Type	Price
	Each (p)		Each (p)
DY87	30.0	AD149	40
DY802	30.0	AD161	38
ECC82	28.0	AD162	38
EF80	28.5	AF114	24
EF183	34.5	AF115	21
EF184	34.5	AF116	22
EH90	35.5	AF117	19
PC900	24.5	AF118	50
PCC89	40.0	AF139	35
PCC189	41.0	AF178	45
PCF80	31.5	AF180	45
PCF86	39.0	AF181	45
PCF801	42.0	AF239	40
PCF802	40.0	AF240	60
PCL82	39.0	BC107	11
PCL84	39.0	BC108	10
PCL85	44.5	BC109	14
PCLB6	41.0	BC109C	14
PFL200	59.5	BC113	13
PL36	56.5	BC116A	18
PL84	25.0	BC117	14
PL504	64.5	BC125B	15
PL508	67.0	BC132	25
PL519	£1.80	BC135	15
PV88	35.5	BC137	19
PV800	33.0	BC138	26
PV500A	85.0	BC142	23
		BC143	25

SEMI CONDUCTORS

Type	Price	Type	Price
	Each (p)		Each (p)
AC127	17	9C147A	11
AC128	13	9C148	10
AC141K	25	9C149	10
AC142K	25	9C153	15
AC151	20	9C154	15
AC154	18	9C157	14
AC155	18	9C158	10
AC156	20	9C159	11
AC176	22	9C173	18
AC187	19	9C178B	20
AC187K	24	9C182L	12
AC188	17	9C183L	12
AC188K	26	9C187	25
AD142	45	9C214L	15
		9C328	28
		9C337	19

DIODES

Type	Price	Type	Price
	Each (p)		Each (p)
BD124	75	BF194	9
BD131	45	BF195	8
BD132	39	BF196	10
BD160	£1.39	BF197	12
BD235	49	BF198	23
BD237	52	BF200	25
BDX32	£2.40	BF218	30
BF115	20	BF224	23
BF160	15	BF258	34
BF167	20	BF336	28
BF173	20	BF337	35
BF178	35	BF355	54
BF179	40	BFX86	28
BF180	31	BFY50	19
BF181	11	BFY52	20
BF184	25	BSV52	35
BF185	25	BT106	£1.20
BF194	9	BU105/02	£1.95
BF195	8	BU108	£2.10
BF196	10	BU208	£2.95
BF197	12	E1222	30
BF198	23	MJE340	45
BF200	25	OC71	15
BF218	30	OC72	16
BF224	23	R2008B	£2.00
BF258	34	R2010B	£2.00
BF336	28	RCA18334	80
BF337	35	RCA16335	80
BF355	54		

DIODES

Type	Price
	Each (p)
BA-15	7
BA-45	14
BA-48	19
BA-54 201	11
BY126	11
BY127	12
BY199	27
BY206	21
BY238	25
OA50	6
OA202	7.5
IN60/OA91	5

NEW TOSHIBA TUBES

Type	Price
	Each (p)
19" A49/191X	£48.96
20" 510DJB22	£50.75
22" A56/120X	£54.25

EHT MULTIPLIERS MONOCHROME (BRC)

Type	Price
	Each (p)
2HD 950Mk1	960
2TQ 950Mk2	1400
2DAK 1500 (17" & 19")	
2TAK 1500 (23" & 24")	

EHT MULTIPLIERS - COLOUR


Type	Price
	Each (p)
11TAQ IIT CVCI, 2 & 3	£4.50
ITN GEC/Sobell	£4.50
11TAZ GEC 2110	£4.85
11TAM Philips G8	£4.50
11T3D Philips 550	£5.00
3TCW Pye 691/693	£3.50
1TH Decca 30 Series	£4.50
11TAQ Decca Bradford	£4.50
3TCU Thorn 3000/3500	£5.00
11HAA Thorn 8000	£1.90
11HAB Thorn 8500	£4.25

PRICES SUBJECT TO 25% V.A.T.
All goods subject to settlement
discount of 5% 7 days and 2%
monthly.
No postage charges or minimum
order values.
Write or phone for full details now.

...In Prices, Quality and Service.

IMPROVE PETROL CONSUMPTION

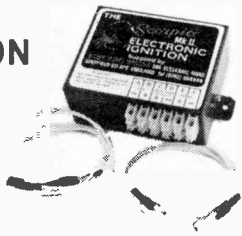Fit the
Brilliant New
P.E. Scorpio Mk. II
"Dual Polarity"
Capacitive Discharge
Electronic Ignition system



- * Genuine improvement in overall petrol consumption (independent report claims at least 8%-10%)
 - * Much easier cold weather starting, less strain on your battery
 - * Less use of choke—increases engine life
 - * Smoother running at lower revs—makes your four cylinder car feel like a six cylinder
- Together with the following "Scorpio Mk. II" plus features not previously available with other makes:
- * Only one model used for both positive (+) and negative (-) earth vehicles—if you change your car, you can certainly transfer your "Scorpio".
 - * Retains your original contact breaker points, which last their mechanical life—no points burn
 - * Will drive electronic tachometers.

Send a stamped addressed envelope for our free interesting brochure, "Electronic Ignition—How it Works", containing circuit and itemised price list.

Price for complete kit of parts, with easy to follow, comprehensive instructions, connecting wire, etc. ONLY £10.85, including VAT and postage and packing.
Ready made unit, fully tested, for immediate installation with easy to follow instructions, all leads, etc.. ONLY £13.65, including VAT and postage and packing.

THOUSANDS ALREADY IN USE—FULLY GUARANTEED.

P.E. "VARICAP" STEREO PUSH BUTTON F.M. TUNER



The P.E. "Varicap" Stereo Tuner uses the latest Mullard modules for R.F. and I.F. circuits—highly sensitive and pre-aligned for ease of construction.

This superb kit has everything to enable you to construct this highly sensitive F.M. Stereo Tuner, with instant push button station selection, self contained regulated power supply, stereo decoder, etc., etc. Easy to construct, highest quality reproduction.

Price only £34.50, including VAT and postage and packing. Please send stamped addressed envelope for our free brochure on the Varicap, which gives performance figures, detailed description, etc., etc.

P.E. "GEMINI" STEREO AMPLIFIER

Output genuine 30W R.M.S. per channel!
Distortion 0.01% (maximum)!
Frequency response—3dB, 20Hz to 100kHz into 8 ohms!
Fully comprehensive inputs, disc, tape, MIC, etc.!

Yes, we are still supplying all components for this superb Stereo Amplifier, since we have not yet found a better one!

Fully comprehensive constructional booklet available, containing full specification, performance graphs, step-by-step assembly instructions, photographs, fault finding guide, etc. etc. Price 55p plus 9p postage and packing.

For itemised price list only please forward stamped addressed envelope.

ELECTRO SPARES, 288 ECCLESALL ROAD, SHEFFIELD S11 8PE


Please allow 14 days minimum for delivery, for postal delays, cheque clearance, etc.

SAXON

Money saving high performance audio equipment
DIRECT FROM OUR OWN FACTORIES

GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

SA35 £6.60	Carriage free	★ 25Hz–25kHz
35W RMS 25–50V		★ 0.2% distortion
7 transistors, 7 diodes		★ Noise—80dB
SA50 £8.50	Carriage free	★ 500mV into 20K
50W RMS 25–65V		★ 4–16 ohms
7 transistors, 7 diodes		★ Simple wiring
SA100 £12.50	Carriage free	★ Short and open circuit proof
100W RMS 45–70V		★ Continuously rated
10 transistors, 7 diodes		★ Top-grade components
120 watt module complete with built-in supply—extra heavy duty £24.75 Carr. 60p		

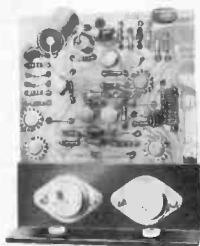

THE SA100 MODULE

POWER SUPPLIES

UNSTABILISED — READY WIRED AND FUSED			
PU45	Suits 2 SA35 or 1 SA50 (4 ohm)	£6.50	Carriage 50p
PU70	Suits 2 SA50 or 2 SA100 (8 ohm)	£9.50	Carriage 60p
STABILISED			
PS45	Suits 2 SA35 or 2 SA50 (4 ohm)	£5.50	Carriage free
MT45	Transformer for above	£3.90	Carriage 50p
PS70	Suits 2 SA100	£6.50	Carriage free
MT70	Transformer for above	£5.50	Carriage 60p

N.B. PS70 is not suitable for the SA50

Mk II STEREO DISCO MIXER £29.50 Carr. 50p

This well tried Pre-Amp mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, bass, treble. Left/Right fade, deck volume, bass, treble, h/phone select, vol, Mains. Size 17½in x 3in x 4in deep.



DISCO MODULE £12.50 Carr. 50p

Thousands sold of this extremely popular mono Pre-Amp. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: H/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12½in x 3in x 2in deep.



3-CHANNEL SOUND-LITE £24.75 Carr. 50p

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12in x 3in x 2½in deep. Professional standards at a price you can afford!



SINGLE CHANNEL VERSION £7.90 Carr. free

High sensitivity, compact, handles 1kW. Full wave operation

Add 8% VAT to all orders

MULTI-PURPOSE MIXERS


M4HL £25.00 Carr. 60p

M6HL £35.00 Carr. 60p

Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.

VA30 CHANNEL MODULE £3.90 Carr. free

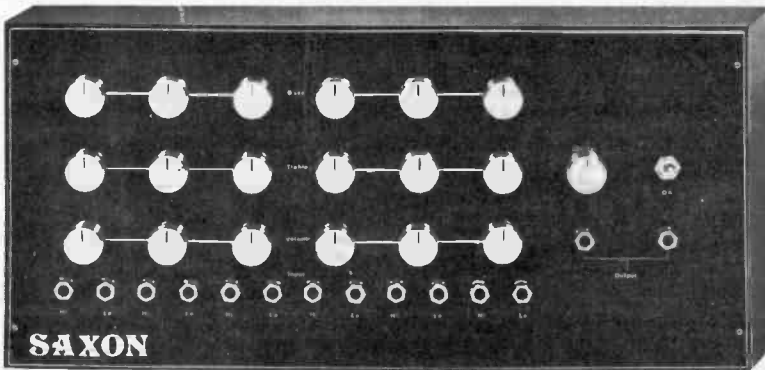This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9–100V)




SAXON CSE 100

COMPLETE AMPLIFIER

£39.90 Carr. 60p

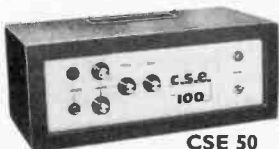100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vinyl case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.



CSE 100 £33.00 Carr. 60p

NEW!!

SAXON MULTIMIX 100 £57 CARR. £1.00

100W RMS SLIDER controls PLUS master slider. Wide range bass and treble controls—fantastic value. Ideal for complete Disco's, Groups, Clubs, etc.

SAXON MULTIMIX 50 EXACTLY AS ABOVE £45 BUT 50W RMS

CALLERS AND MAIL ORDER:
SAXON ENTERTAINMENTS LIMITED
329-333 WHITEHORSE ROAD • CROYDON CR0 2HS

(Please quote magazine when ordering)

SHOP HOURS: 9 a.m. 5 p.m. — LUNCH 12.30 1.30 p.m. MAIL ORDER DESK: 10 a.m.—3 p.m.
24-HOUR ANSWER SERVICE TEL. 01-684 6385. TECHNICAL ENQUIRIES 01-684 0098

SEND 15p FOR OUR NEW 26-PAGE MANUAL—full circuits and details.
TERMS OF BUSINESS: C.W.O., C.O.D. or ACCESS (just send in card number). Send £1 for C.O.D.
Please include S.A.E. with all enquiries.
VAT at 8% must be added to all orders including carriage charges.

The largest selection

EX-COMPUTER STABILISED POWER MODULES

(Complete with circuit diagrams, etc.)

99p each plus 22p P. & P.

LOW COST CAPACITORS

0.01µF 400V. 3p each
500µF 50V. Elect. 10p each

DECON-DALO 33PC Marker

Etch resistant printed circuit marker pen
99p each

VEROBOARDS

Packs containing approx. 50sq. in. various sizes, all 0.1 metric 55p

REPAKCO CHOKES & COILS

RF Chokes
CH1 2.5mH 20p CH2 5.0mH 30p
CH3 7.5mH 31p CH4 10mH 33p
CH5 15mH 28p

COILS

DRX1 Crystal set 31p DRR2 Dual range 45p

COIL FORMERS & CORES

NORMAN 1" Core & Formers 8p
1" Cores & Formers 10p

SWITCHES

DP/DT Toggle 36p SP/ST Toggle 30p

FUSES

1" and 20mm. 100mA, 200mA, 250mA,
500mA, 1A, 1.5A, 2A
QUICK-BLOW 5p each.

EARPHONES

Crystal 2.5mm plug 42p
Crystal 3.5mm plug 42p
8 ohms 2.5mm plug 22p
8 ohms 3.5mm plug 22p

DYNAMIC MICROPHONES

B1223, 200 ohms plus on/off switch and
2.5mm and 3.5mm plugs £1.85

3-WAY STEREO HEADPHONE JUNCTION BOX

H1012 £1.87

2-WAY CROSSOVER NETWORK

K4007, 80 ohms Imp. Insertion loss 3db £1.21

CAR STEREO SPEAKERS

(Angled) £3.85 per pair.

BI-PAK

CATALOGUE AND LISTS

Send S.A.E. and 10p.

INSTRUMENT CASES



(Black Vinyl covered)

No.	Length	Width	Height	Price
BV1	8"	5 1/2"	2"	£1.35
BV2	11"	6"	3"	£1.75

ALUMINIUM BOXES

BA1	5 1/2"	4"	1 1/2"	49p
BA2	4"	4"	1 1/2"	49p
BA3	4"	2 1/2"	1 1/2"	49p
BA4	3 1/2"	4"	1 1/2"	58p
BA5	4"	2 1/2"	2"	49p
BA6	3"	2"	1"	42p
BA7	7"	5"	2 1/2"	85p
BA8	8"	6"	3"	£1.10
BA9	6"	4"	2"	70p

P. & P. 10p on each box

VISIT OUR COMPONENT SHOP

18 BALDOCK ST., WARE, Herts. (A10)

Open Mon.-Sat. 9-5.30 p.m. Tel. 61593

BIB HI-FI ACCESSORIES

De Luxe Groov-Kleen

Model 42 £1.95

Chrome Finish

Model 60 £1.50



Ref. 36A. Record/Stylus Cleaning Kit 33p
Ref. 43. Record Care Kit £2.42
Ref. 31. Cassette Head Cleaner 58p
Ref. 32. Tape editing Kit £1.68
Model 9. Wire Stripper/Cutter 83p
Ref. 46. Spirit Level 82p

Ref. B. Stylus and Turntable Cleaning Kit
Ref. P. Hi-Fi Cleaner 31p
Ref. 32A. Stylus Balance £1.37
Ref. J. Tape Head Cleaning Kit 62p
Ref. 56. Hi-Fi Stereo Hints and Tips 42p
Ref. 45. Auto Changer Groove Cleaner £1.08

ANTEX SOLDERING IRONS

X25, 25 watt £2.05

CCN 240, 15 watt £2.48

Model G, 18 watt £2.26

SK2, Soldering Kit £3.25

STANDS: ST3, suitable for all models £1

SOLDER: 18SWG Multicore 7oz £1.61

28SWG 7oz £1.61. 18SWG 22ft 51p

28SWG Tube 33p

ANTEX BITS AND ELEMENTS

Bits No.

102 For model CCN240 3/4" 42p

104 For model CCN240 1/2" 42p

1100 For model CCN240 3/8" 42p

1101 For model CCN240 3/4" 42p

1102 For model CCN240 1" 42p

1020 For model G240 3/8" 42p

1021 For model G240 1" 42p

1022 For model G240 1/4" 42p

50 For model X25 3/8" 48p

51 For model X25 1" 48p

52 For model X25 1/2" 48p

ELEMENTS

ECN 240 £1.30

ECCN 240 £1.32

EG 240 £1.07

EX 25 £1.16

ANTEX HEAT SINKS 10p

VAT included in all prices. Please add
10p P. & P. (U.K. only). Overseas orders—
please add extra for postage.

NEW COMPONENT PAK BARGAINS

Pack	No. Qty.	Description	Price
C1	200	Resistors mixed values approx. count by weight	0.54
C2	150	Capacitors mixed values approx. count by weight	0.54
C3	50	Precision Resistors mixed values	0.54
C4	75	1/4 W Resistors mixed preferred values	0.54
C5	5	Pieces assorted Ferrite Rods	0.54
C6	2	Tuning Gangs, MW/LW VHF	0.54
C7	1	Pack Wire 50 metres assorted colours	0.54
C8	10	Reed Switches	0.54
C9	3	Micro Switches	0.54
C10	15	Assorted Pots & Pre-Sets	0.54
C11	5	Jack Sockets 3 x 3.5m 2 x Standard Switch Type	0.54
C12	30	Paper Condensers preferred types mixed values	0.54
C13	20	Electrolytics Trans. types	0.54
C14	1	Pack assorted Hardware—Nuts/Bolts, Grommets, etc.	0.54
C15	5	Mains Slide Switches	0.54
C16	20	Assorted Tag Strips & Panels	0.54
C17	10	Assorted Control Knobs	0.54
C18	4	Rotary Wave Change Switches	0.54
C19	2	Relays 6—24V Operating	0.54
C20	1	Pack Sheets of Copper Laminate approx. 20 sq. ins.	0.54

PLUGS AND SOCKETS

PLUGS

PS 1 D.I.N. 2 Pin (Speaker) 0-11

PS 2 D.I.N. 3 Pin 0-12

PS 3 D.I.N. 4 Pin 0-15

PS 4 D.I.N. 5 Pin 180° 0-16

PS 5 D.I.N. 5 Pin 240° 0-16

PS 6 D.I.N. 6 Pin 0-17

PS 7 D.I.N. 7 Pin 0-18

PS 8 Jack 2.5mm Screened 0-18

PS 9 Jack 3.5mm Plastic 0-12

PS 10 Jack 3.5mm Screened 0-18

PS 11 Jack 1" Plastic 0-15

PS 12 Jack 1" Screened 0-22

PS 13 Jack Stereo Screened 0-36

PS 14 Phono 0-10

PS 15 Car Aerial 0-22

PS 16 Co-Axial 0-15

INLINE SOCKETS

PS 21 D.I.N. 2 Pin (Speaker) 0-14

PS 22 D.I.N. 3 Pin 0-20

PS 23 D.I.N. 5 Pin 180° 0-20

PS 24 D.I.N. 5 Pin 240° 0-20

PS 25 Jack 2.5mm Plastic 0-16

PS 26 Jack 3.5mm Plastic 0-16

PS 27 Jack 1" Plastic 0-30

PS 28 Jack 1" Screened 0-35

PS 29 Jack Stereo Plastic 0-30

PS 30 Jack Stereo Screened 0-38

PS 31 Phono Screened 0-18

PS 32 Car Aerial 0-22

PS 33 Co-Axial 0-22

SOCKETS

PS 35 D.I.N. 2 Pin (Speaker) 0-08

PS 36 D.I.N. 3 Pin 0-11

PS 37 D.I.N. 5 Pin 180° 0-11

PS 38 D.I.N. 5 Pin 240° 0-11

PS 39 Jack 2.5mm Switched 0-12

PS 40 Jack 3.5mm Switched 0-12

PS 41 Jack 1" Switched 0-20

PS 42 Jack Stereo Switched 0-30

PS 43 Phono Single 0-08

PS 44 Phono Double 0-10

PS 46 Co-Axial Surface 0-10

PS 47 Co-Axial Flush 0-20

LEADS

LS 1 Speaker Lead 2 pin D.I.N. plug to open ends approx 3 metres long (coded) 0-20

CABLES

CP 1 Single Lapped Screen 0-07

CP 2 Twin Common Screen 0-11

CP 3 Stereo Screened 0-12

CP 4 Four Core Common Screen 0-23

CP 5 Four Core Individually Screened 0-30

CP 6 Microphone Fully Braided Cable 0-10

CP 7 Three Core Mains Cable 0-09

CP 8 Twin Oval Mains Cable 0-07

CP 9 Speaker Cable 0-05

CP 10 Low Loss Co-Axial 0-18

CARBON POTENTIOMETERS

Log and Lin

4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M

VC 1 Single Less Switch 0-15

VC 2 Single D.P. Switch 0-28

VC 3 Tandem Less Switch 0-46

VC 4 1K Lin Less Switch 0-15

VC 5 100 K anti-Log 0-46

HORIZONTAL CARBON PRESETS

0-1 watt 0-06 each

100, 220, 470, 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4.7M

SOLVE THOSE STICKY PROBLEMS!

with



CYANOACRYLATE G2 ADHESIVE

The wonder bond which works in seconds—bond plastic, rubber, metals, transistors, components, permanently, immediately.

OUR PRICE ONLY 54p for 2 gm. phial

BATTERY HOLDER

Takes 6, HP7's complete with terminal, clip and lead. 34p.

WORLD SCOOP JUMBO SEMICONDUCTOR PACK

Transistors, Germ. and Silicon Rectifiers, Diodes, Triacs, Thyristors, I.C.s and Zeners. ALL NEW AND CODED.

APPROX. 100 PIECES

Offering the amateur a fantastic bargain Pack and an enormous saving—identification and data sheet in every Pak.

Only £2 p. & p. 20p

RECORD STORAGE / CARRY CASES

7in EP. 18 1/2in x 7in x 8in (50 records) £2.10
12in LP. 13 1/2in x 7 1/2in x 12 1/2in (50 records) £2.95

CASSETTE CASES £1.30

Holds 12, 10in x 3 1/2in x 5in. Lock and handle

8-TRACK CART. CASES

Holds 14, 13in x 5in x 6in £1.95
Holds 24, 13 1/2in x 8in x 5 1/2in £2.70
Both with lock and handle.

SPECIAL PURCHASE

2N3055, Silicon Power Transistors NPN. Famous manufacturers out-of-spec devices free from open and short defects—every one abiel 115W. TO3. Metal Case.

OUR SPECIAL PRICE 8 for £1

REPAKCO TRANSFORMERS

240V. Primary. Secondary voltages available from selected tappings 4V, 7V, 8V, 10V, 14V, 15V, 17V, 19V, 21V, 25V, 31V, 33V, 40, 50 and 25V-0-25V.

Type	Amps	Price	P. & P.
MT50/1	1	£2.42	48p
MT50/2	2	£3.30	60p

CARTRIDGES

ACOS

GP91-18C 200mV at 1.2cm/sec	£1.35
CP92-1 280mV at 1cm/sec	£1.85
GP96-1 100mV at 1cm/sec	£2.80
J-2005 Crystal/Hi Output	£1.05
J-2010C Crystal/Hi Output Compatible	£1.20
J-2006S Stereo/Hi Output	£1.75
J-2105 Ceramic/Med Output	£1.95
J-2203 Magnetic 5mV/5cm/sec, including stylus	£4.95
J-2205 Replacement stylus for above £3.00	
AT-55 Audio-technica magnetic cartridge 4mV/5cm/sec	£3.80

CARBON FILM RESISTORS

The E12 Range of Carbon Film Resistors, 4 watt available in PAKS of 50 pieces, assorted into the following groups:

R1 50 Mixed 100 ohms-820 ohms	50p
R2 50 Mixed 1k Ω-8.2k Ω	50p
R3 50 Mixed 10k Ω-82k Ω	50p
R4 50 Mixed 100k Ω-1M Ω	50p

THESE ARE UNBEATABLE PRICES—JUST 1p EACH INCL. V.A.T.


BI-PAK SUPERIOR QUALITY LOW - NOISE CASSETTES

C60, 36p; C90, 48p; C120, 60p.

-the lowest prices!

BI-PAK QUALITY COMES TO AUDIO!

AL10/AL20/AL30 AUDIO AMPLIFIER MODULES

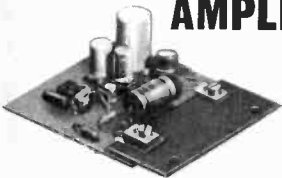

The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S. The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

Parameter	Conditions	Performance
HARMONIC DISTORTION	Po = 3 WATTS f = 1KHz	0.25%
LOAD IMPEDANCE	—	8-16 Ω
INPUT IMPEDANCE	f = 1KHz	100 k Ω
FREQUENCY RESPONSE --3dB	Po = 2 WATTS	50 Hz-25KHz
SENSITIVITY for RATED O/P	Vs=25V, R1=8Ω f=1KHz	75mV, RMS
DIMENSIONS	—	3" x 2 1/2" = 1"

The above table relates to the AL10, AL20 and AL30 modules. The following table outlines the differences in their working conditions.

Parameter	AL10	AL20	AL30
Maximum Supply Voltage	25	30	30
Power out for 2% T.H.D. (RL = 8Ω f = 1KHz)	3 watts RMS Min.	5 watts RMS Min.	10 watts RMS Min.

AUDIO AMPLIFIER MODULES

AL 10. 3 watts	£2.50
AL 20. 5 watts	£2.85
AL 30. 10 watts	£3.20

POWER SUPPLIES

PS 12. (Use with AL10, AL20, AL30) 85p
SPM 80. (Use with AL60) £3.25
FRONT PANELS FP 12 with Knobs £1.00

PRE-AMPLIFIERS

PA 12. (Use with AL10, AL20 and AL30)	£4.85
PA 100. (Use with AL60)	£13.15

TRANSFORMERS

T461 (Use with AL10)	£1.60 P & P	22p
T538 (Use with AL20, AL30)	£2.30 P & P	22p
BMT80 (Use with AL60)	£2.75	22p

P & P 37p

PA12 PRE-AMPLIFIER SPECIFICATION

The PA12 pre-amplifier has been designed to match into most budget stereo systems. It is compatible with the AL 10, AL 20 and AL 30 audio power amplifiers and it can be supplied from their associated power supplies. There are two stereo inputs, one has been designed for use with ceramic cartridges while the auxiliary input will suit most magnetic cartridges. Full details are given in the specification table. The four controls are, from left to right: Volume and on/off switch, balance, bass and treble. Size 152mm x 84mm x 35mm.

Frequency response—
20Hz-50KHz (-3dB)
Bass control—
± 12dB at 60Hz
Treble control—
± 14dB at 14KHz
*Input 1. Impedance
1 Meg. ohm
Sensitivity 300mV
†Input 2. Impedance
30 K ohms
Sensitivity 4mV


Look for our

SEMICONDUCTOR ADVERTISEMENTS in
Practical Wireless Wireless World Radio Constructor

ALL PRICES INCLUDE V.A.T.

The STEREO 20

The "Stereo 20" amplifier is mounted, ready wired and tested on a one-piece chassis measuring 20 cm x 14 cm x 5.5 cm. This compact unit comes complete with on/off switch volume control, balance, bass and treble controls, Transformer, Power supply and Power amps. Attractively printed front panel and matching control knobs. The "Stereo 20" has been designed to fit into most turntable plinths without interfering with the mechanism or, alternatively, into a separate cabinet. Output power 20w peak. Input 1 (Cer.) 300mV into 1M. Freq. res. 25Hz-25kHz. Input 2 (Aux.) 4mV into 30K. Harmonic distortion. Bass control ± 12dB at 60Hz typically 0.25% at 1 watt. Treble con. ± 14dB at 14kHz.

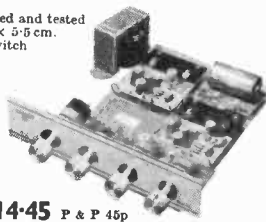

£14.45 P & P 45p

TC20 TEAK VENEERED CABINET

For Stereo 20 (front board undrilled) Size 10 1/2" x 8 1/2" x 3", £3.95 plus 45p postage.

SHP80 STEREO HEADPHONES

4-16 ohms impedance. Frequency response 20 to 20,000Hz. Stereo/mono switch and volume controls, £4.95


NOW WE GIVE YOU
50w PEAK (25w R.M.S.)
PLUS THERMAL PROTECTION!
The NEW AL60 Hi-Fi
Audio Amplifier FOR ONLY £4.25



- Max Heat Sink temp 90°C.
- Frequency Response 20Hz to 100KHz
- Distortion better than 0.1% at 1KHz
- Supply voltage 15-50 volts
- Thermal Feedback
- Latest Design Improvements
- Load — 3, 4, 8 or 16 ohms
- Signal to noise ratio 80dB
- Overall size 63mm x 105mm x 13mm

Especially designed to a strict specification. Only the finest components have been used and the latest solid state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiasts.

STABILISED POWER MODULE SPM80

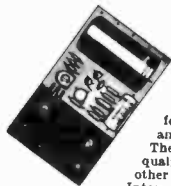

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disco Systems, Public Address, Intercom Units, etc. Handbook available 10p

PRICE £3.25
TRANSFORMER BMT80 £2.75 p. & p. 40p

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL60 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.



SPECIFICATION

Frequency Response 20Hz-20KHz ± 1dB
Harmonic Distortion better than 0.1%
Inputs: 1. Tape Head 2.25 mV into 50K Ω
2. Radio, Tuner 75 mV into 60K Ω
3. Magnetic P.U. 3 mV into 50K Ω
All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB, from 20Hz to 20KHz.
Bass Control ± 16dB at 20Hz
Treble Control ± 15dB at 20KHz
Filters: Rumble (High Pass) 100Hz
Scratch (Low Pass) 8KHz
Signal/Noise Ratio better than -65dB
Input overload + 26dB
Supply + 35 volts at 20mA
Dimensions 292mm x 82mm x 35mm

ONLY £14.25

MK 60 AUDIO KIT

Comprising: 2 x AL60, 1 x SPM80, 1 x BMT80, 1 x PA 100, 1 front panel, 1 kit of parts to include on-off switch, neon indicator, stereo headphone sockets plus instruction booklets. Complete Price: £29.75 plus 45p postage.

TEAK 60 AUDIO KIT

Comprising: Teak veneered cabinet size 16 1/2" x 11 1/2" x 3 1/2", other parts include aluminium chassis, heat sink and front panel bracket, plus back panel and appropriate sockets, etc. Kit price: £29.95 plus 45p postage.

giro No. 388-7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE, HERTS

Postage and packing add 20p Overseas add extra for airmail.
Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back

ALL MAIL ORDER BY RETURN. C.O.D. SERVICE WELCOME

C. T. ELECTRONICS

VAT Unless otherwise stated all prices are EXCLUSIVE of VAT. Please add 25% to all orders. Carriage: orders under £10 plus 35p. Over £10 post free.

All mail order and enquiries to 270 Acton Lane, Chiswick W4 5DG. Tel. 01-994 6275

SEMICONDUCTORS

AC107	35p	BCY38	£5.00	MPP104	
AC125	25p	BCY39	£1.50	(2N5458)	35p
AC127	21p	BCY55	£1.50	MPP105	
AC128	25p	BCY70	22p	(2N5459)	40p
AC176	25p	BD121	75p	OA47	10p
AC188	30p	BD123	75p	OA79	10p
ACY17	25p	BD124	65p	OA80	10p
ACY18	30p	BD131	40p	OA81	10p
ACY19	30p	BD132	50p	OA200	10p
ACY20	25p	BF153	75p	OA202	10p
ACY21	30p	BD158	75p	OA210	35p
AD140	60p	BDY11	£1.40	OA211	35p
AD142	50p	BDY17	£1.00	OC16	90p
AD149	80p	BDY19	£1.95	OC19	85p
AD181	44p	BDY20	£1.40	OC22	55p
AD182	44p	BF142	21p	OC26	65p
AF114	25p	BF194	14p	OC28	80p
AF115	25p	BF195	15p	OC35	80p
AF116	25p	BF196	15p	OC38	85p
AF117	25p	BF197	20p	OC42	40p
AF118	60p	BF200	30p	OC44	20p
AS221	60p	BF243	30p	OC45	25p
ASV28	30p	BF429	30p	OC70	15p
BA102	33p	BFX34	30p	OC71	12p
BA112	50p	BFX85	30p	OC72	20p
BA114	16p	BFX86	30p	OC75	25p
BA156	15p	BFX88	30p	OC76	25p
BC107	12p	BFY10	35p	OC77	40p
BC108	12p	BFY44	50p	OC81	25p
BC109	14p	BFY50	25p	OC83	25p
BC113	15p	BFY51	25p	OC84	40p
BC115	15p	BFY52	25p	OC139	30p
BC116	16p	BFY53	25p	OC170	25p
BC147	20p	BFY90	65p	OC171	30p
BC118	12p	BFY44B	60p	OC200	60p
BC147	11p	BSW84	40p	OC201	60p
BC148	11p	BSW83	85p	OC202	75p
BC149	12p	BSW68	80p	TIP29A	45p
BC153	14p	BY127	20p	TIP30	55p
BC157	15p	BY134	85p	TIP31A	57p
BC158	15p	IS100	15p	TIP32A	60p
BC189	15p	IS100	15p	TIP33A	£1.00
BC182	12p	MJ340	50p	TIP34A	£1.40
BC183	12p	MJ481	85p	TIP35A	£3.20
BC184	14p	MJ2801	£1.25	TIP36A	£3.50
BC196	25p	MJE2901	£1.95	TIP41A	70p
BC212	14p	MJE340	50p	TIP42A	85p
BC212L	16p	MJE370	75p		
BC213	14p	MJE371	80p	TIP29B	54p
BC214	14p	MJE520	65p	TIP30B	60p
BC301	25p	MJE2955	£1.20	TIP31B	85p
BC302	25p	MJE3055	75p	TIP32B	77p
BC303	40p	MN1813	45p	TIP33B	£1.00
BCY30	40p	MN1813	45p	MN1813	45p
BCY31	50p	MPP102	45p	TIP35B	£2.71
BCY32	85p	MPP103	45p	TIP36B	£3.50
BCY34	80p	(2N5457)	35p	TIP41B	78p

QTY. DISCOUNTS 12 + 10%; 25 + 15%; 100 + 20%

DIGITAL INTEGRATED CIRCUITS

SN7400	18p	SN7428	50p	SN7473	40p	SN74107	55p	SN74110	80p
SN7401	18p	SN7430	20p	SN7474	40p	SN74111	£1.00	SN74111B	£1.00
SN7402	20p	SN7432	42p	SN7475	55p	SN74121	65p	SN74170	£4.10
SN7403	20p	SN7433	70p	SN7476	45p	SN74122	£1.35	SN74174	£2.00
SN7404	20p	SN7437	50p	SN7480	80p	SN74123	£2.00	SN74175	£1.25
SN7405	20p	SN7438	50p	SN7481	£1.25	SN74141	£1.00	SN74176	£1.00
SN7406	30p	SN7440	20p	SN7482	17p	SN74142	£1.00	SN74177	£1.00
SN7407	30p	SN7441A	75p	SN7483	£1.00	SN74150	£1.35	SN74178	£1.00
SN7408	20p	SN7442	75p	SN7484	90p	SN74151	£1.35	SN74179	£1.00
SN7409	40p	SN7443	£1.00	SN7486	45p	SN74153	£1.35	SN74180	£1.00
SN7410	18p	SN7445	£1.70	SN7490	75p	SN74154	£1.35	SN74181	£0.00
SN7411	23p	SN7446	£2.00	SN7491A	£1.00	SN74155	£1.35	SN74182	£1.00
SN7412	23p	SN7447	£1.50	SN7492	75p	SN74156	£1.35	SN74183	£2.00
SN7413	40p	SN7448	£1.75	SN7493	75p	SN74157	£1.00	SN74184	£2.00
SN7416	30p	SN7450	20p	SN7494	80p	SN74160	£1.00	SN74185	£2.00
SN7417	30p	SN7451	20p	SN7495	80p	SN74161	£1.00	SN74195	£1.85
SN7420	20p	SN7453	20p	SN7496	£1.00	SN74162	£1.00	SN74199	£2.00
SN7422	30p	SN7454	20p	SN7497	£2.25	SN74163	£3.40		
SN7423	38p	SN7470	30p	SN7498	£2.00	SN74164	£2.75		
SN7425	38p	SN7480	30p	SN7499	£1.45	SN74165	£2.00		
SN7427	42p	SN7482	30p	SN7405	£1.45	SN74166	£2.75		

TRIACS

CRS1/05	40p	TXL228B	8A 400V	85p
CRS1/10	50p	SC40D		£1.40
CRS1/20	60p	SC40E		£1.40
CRS1/40	85p	SC45D		£1.70
CRS1/60	90p	SC45E		£2.10
CRS3/10	62p	SC50D		£2.42
CRS3/20	62p	SC50E		£2.74
CRS3/40	90p	DIAC		25p
CRS7/400	£1.00			
CRS16/100	85p			
CRS16/200	90p			
CRS16/600	£1.80			
C106B	45p			
C106D	70p			
40689	90p			
TIC44	35p			
2N4444	£1.90			
BT10/500A	90p			

BRIDGE RECTIFIERS

W02 1A 200V	30p
BY164 1-4A	11p
200V	57p
MDA952/2 6A	100V
100V	80p

ZENER DIODES

BZV88 Series 400mW	
3.3V-33V, 5%	11p
1.5W range	25p
10W range	45p

L.E.D.

TIL209	38p
HP5082	28p
MA2082R	20p

L.D.R.

ORP12	60p
NE555 Timer	70p

TO3 VOLTAGE REGULATORS

L005 5V 650mA	
L036 12V 500mA	
L037 15V 450mA	£1.60 each

PERSONAL CALLERS ALWAYS WELCOME

VEROBOARD

2 1/2 x 3 1/2	32p	0-15	23p
2 1/2 x 5	35p		35p
3 x 3 1/2	35p		35p
3 x 5	40p		41p
17 x 2 1/2	£1.18		90p
17 x 3 1/2	£1.85		£1.24
17 x 5	£2.65		72p
PIN INS. TOOL	75p		72p
SP. F. CUTTER	52p		52p
100 PINS SS	30p		30p
500 PINS SS	£1.20		£1.20
500 PINS DS	£1.20		£1.20

ALSO STOCKED

Electrolytic Capacitors Mullard, Sprague, Lorin etc. Polyester, Polystyrene, Silver Mica Capacitors, etc. Resistors 1W-10Watt. Potentiometers: carbon, wirewound. Preset. Rectilinear multiturn. Antex Soldering Irons, switches, rotary, slide, toggle, etc. Cable, veroboard.

Potentiometers

Linear or Log	Single	Double
Rotary Pots	17p	45p
Rotary Switched	17p	—

★ SPECIAL OFFERS ★

MINIATURE MAINS TRANSFORMER. PRI 240V SEC. 12V 100MA Manuf.: Hinchley. Size: 36 x 45 x 40mm F.C. 53mm. Price 1—85p. 100—80p ea. 1,000—50p ea. 10,000—40p ea.

3 CORE PVC INSULATED MAINS CABLE, GREY ML6850. 3 x 7/0.2mm. Price 100m—£4.50. 1,000m—£35. 10,000m—£330.

MINIATURE MAINS TRANSFORMER, PRI 110, 240V, SEC. 18V at 250mA. Price 80p each.

240V A.C. SOLENOID. Reversible operation; twin coil. Size approx. 2 1/2in x 1 1/2in x 1 1/2in.

30 unmarked OC71 transistors £1.00

25 Unmarked 250mW Zenerdiode, 4-7V, 5-1V, 6-2V, 7-5V, 9-1V, 10V. Measured and tested £1.00

Please state voltage required

50 GE Diode OA4 equivalent £1.00

TRANSFORMER: DOUGLAS PRI. 0, 115, 200, 220, 240 SEC. 25-0-25-0-6V, 2JA, £4.50 + 50p p.p.

FERRITE CORE, Mullard type FX2241. Price 50p each.

MULLARD TUBULAR CERAMIC UHF TRIMMERS (PROFESSIONAL)

Type 092 0-0.2-2pF

801 0-0.2-2pF Price 10p ea.

991 0-5-1-3pF

QUANTITY DISCOUNTS PLEASE TELEPHONE 1,000P/F Feedthrough capacitor 5p ea.

Miniature tubular P.C. trimmers

3-5-13pF

6-30pF 10p ea.

4p c/o Varley 700n relay 50p ea.

METAL BOXES

ALUMINIUM BOXES IDEAL FOR VEROB-BOARD WITH BASE AND P.K. screws

Length	Width	Height	55p
AB7 2 1/2in	5 1/2in	1 1/2in	55p
AB8 4in	4in	1 1/2in	55p
AB9 4in	2 1/2in	1 1/2in	55p
AB10 4in	5 1/2in	1 1/2in	55p
AB11 4in	2 1/2in	2in	85p
AB12 3in	2in	1in	50p
AB13 6in	4in	2 1/2in	77p
AB14 7in	5in	2 1/2in	90p
AB15 8in	6in	3in	£1.18
AB16 10in	7in	3in	£1.12
AB17 10in	4 1/2in	3in	£1.32
AB18 12in	5in	3in	£1.32
AB19 12in	8in	3in	£1.80

ALUMINIUM BOXES WITH SLOPING TOP PANEL—IDEAL FOR PRE-AMPS, ETC., USING SLIDER CONTROLS

AB20 8in Long 9in Wide 3 1/2in High at back £2.20

With P.K. Screws

AB21 As above but 10in long £2.40

AB22 As above but 12in long £2.60

20 CORE CABLE + SCREEN, SIZE 14/0076 60p + VAT per yard. Phone for postage rate.

LARGE SELECTION OF MOVING IRON METERS IN STOCK. From 5A-300A. Send for list.

TEAK VENEERED SPEAKER CABINET Suitable for 8in + Tweeter. Approx. size 8in x 12in x 6in. Price £3.50 + 70p P. & P. each.

TEAK VENEERED SPEAKER CABINET Suitable for 12in + Tweeter. Approx. size 15in x 18in x 9in. Price £8 + £1 P. & P. each.

Any queries regarding VAT, phone for details as there will be a two-tier system for VAT.

★ ★ SPECIAL OFFERS ★ ★

MULTICORE CABLE. 25-way, individually screened, 14/0076. £1.00 per yard + VAT. Postage by weight.

IMHOFF 19in RACKING CABINETS. 13 1/2in high, 22in wide, 13in deep. Brand new. £18.00 each + VAT. Carriage £1.00.

PLASTIC SLEEVING, 1,000 PIECES OF 1/2in x 2mm at £1 + VAT of 8%.

METAL OXIDE RESISTORS TR4/5/8 in stock. All Values. 1-off price 3p each. Discount on quantity.

10 TURN TRIMPOTS by Bourns, Mec, Palnton, etc. All values in stock. 50p each. Discount on quantity.

W. WOUND POTS, 1Ω-100kΩ at 30p each. Colvern or Reliance types.

B.N.C. PLUGS, brand new in manufacturer's packing at 35p each + VAT 8%.

THE NEW 1975 DIGITAL DATA BOOK, now in stock. Over 500 pages of very useful information, £4 each. No VAT. Postage 33p each.

We are open from 9.30 a.m.—6.00 p.m. Monday—Saturday

We have the largest retail selection of components available. Phone or write if you are in difficulties obtaining a particular component.

C.O.D. service welcome. All mail order by return. Official orders welcome by Government establishments, Education authorities, etc. Tel. 01-994 6275

AN INDISCRIMINATE TAX

THE electronics constructor has suffered a substantial blow from the April Budget, since the new V.A.T. rate of 25 per cent applies to all electronic parts and accessories which can be used in or with radio, television, or audio equipment, electronic musical instruments, and a wide range of electrically operated domestic appliances. Very few circuit devices will escape this definition; though just how in practice the authorities will determine the finer points of distinction is currently a subject of much interest and speculation.

In fact, the whole scheme for a higher rate of V.A.T. effecting electronic components has been greeted with dismay by the manufacturers, distributors, and retailers alike. Confusion runs rife; already conflicting interpretations are reported from different tax offices up and down the country, and the Chancellor is under pressure from industrial and trade organisations to modify this unworkable and illogical scheme.

As it stands, in the original form, we must assume that very few components will be allowed to slip through at the lower rate of 8 per cent.

Hearing aids and electronic calculators are excluded from the higher rate. But what does the retailer charge for a resistor or semiconductor required to repair one of these instruments? Does he demand an affidavit that this component will not be used to build or service a radio set or amplifier?

Impending or future developments could very well embrace certain components which at this particular moment may not have any plausible connection with the classes of goods that are subject to the higher rate. In terms of technical feasibility there is scarcely anywhere where it is prudent to draw the line. Thus practically all active and passive components designed for use in the field of electronic engineering could conceivably be applied sensibly in electronic equipment suitable for domestic or recreational use, or in certain domestic appliances, (if not today, quite probably tomorrow).

This is not to argue a case on behalf of Customs and Excise for a blanket imposition of the higher rate of V.A.T. upon all electronic components. It is to illustrate the ludicrous situation brought about by those responsible for drafting the new Budget proposals. The authors seem to be oblivious of the fact that electronics is the common base of a multitude of products which may differ widely in all other respects. Complete equipments, sets, and machines can indeed be divided arbitrarily into classes as "luxury items" or otherwise, if so desired. But their component parts and related accessories cannot, for the greater part, be segregated in this same neat and tidy way.

We support all those who claim that the new system is unfair and largely unworkable. In particular we are concerned at the indiscriminate way in which this higher rate of tax, supposedly created in order to curb public spending on luxury goods, penalises the home constructor no matter what kind of project he happens to be building. Many home assembled units and equipments are clearly in the non-luxury class; others, due to some strange quirk of our legislators, have to be considered luxury items and they include the like of d.c. to a.c. converters, electronic power controllers, and control systems for central heating systems, for example. The very kind of equipments that should be welcomed and encouraged by the Government as valuable weapons in the battle against the waste of energy!

And just why *have* components been brought into this higher rate? It must be because, we presume, a few individuals will be tempted to build the so-called luxury goods themselves and thus cheat the Exchequer of a few paltry pounds.

All the indications are that the far reaching repercussions of this extra tax imposition upon (in effect) all electronic components were never foreseen by those responsible for compiling this part of the Budget proposals. This is a charitable interpretation, but it cannot give the taxpayer cause for confidence in those who originate new tax schemes.

(See *Market Place* for some further information on the new V.A.T. situation.)

F.E.B.

Editor

F. E. BENNETT

Editorial

R. D. RAILTON *Assistant Editor*
D. BARRINGTON *Production Editor*
G. GODBOLD *Technical Editor*

Art Dept.

J. D. POUNTNEY *Art Editor*
D. J. GOODING
R. J. GOODMAN
K. A. WOODRUFF

Advertisement Manager

D. W. B. TILLEARD
Phone: 01-634 4202

P. J. MEW
Phone: 01-634 4210

C. R. BROWN, *Classified*
Phone: 01-634 4301

Editorial & Advertising Offices:
Fleetway House, Farringdon St.
London EC4A 4AD
Phone: *Editorial* 01-634 4452
Advertisements 01-634 4202

- The first electronic spark gas ignitor powered by a 1.5V cell for the home constructor
- Simple circuitry provides a constant stream of sparks capable of lighting natural, town and bottled gas easily and swiftly
- Suited to use in the home, caravan, boat or anywhere gas ignition is required

PE PORTABLE GAS

IGNITOR

By R. BULLEN

FOR THOUSANDS of years a spark has been the conventional means of obtaining ignition, and the conventional means of generating the spark has been a flint. However, attempting to ignite natural gas using a flint would have posed our ancestors with a rather tedious problem. Compared to even ordinary town gas the energy required to ignite natural gas is considerably higher and the combustion limits of the gas/air mixture are considerably narrower, see Fig. 1.

Fortunately there is an effective electronic solution—the following design will provide a portable gas ignitor, which will light easily and effectively both natural, town and bottled gases.

The application of a high voltage across a pair of electrodes produces a field in the gas between them, this can lead to ionisation and breakdown of the gas and produce a spark across the gap. The ignitor featured here relies on this principle to produce a continuous stream of high voltage sparks from a 1.5V dry cell battery.

CIRCUIT CONSIDERATIONS

The method of achieving the spark from a low voltage source is outlined in Fig. 2. The power source feeds a d.c. to d.c. converter. When the switch shown in the central block is actuated the stored energy is released into the primary winding of a step-up transformer

and sufficient voltage is generated at the electrodes to cause air breakdown. The oscillation caused by the discharge of an associated capacitor is sufficient to maintain the breakdown for several tens of microseconds.

POWER AND D.C./D.C. CONVERSION

Power is supplied from 1.5V dry cell battery noted as B1 in Fig. 3 which shows the complete circuit of the ignitor. The oscillator circuit is a ringing choke type which utilises feedback between base (AB) and collector (CD) windings for its operation.

When the circuit is switched on by S1, most of the rail voltage will appear across CD as the collector current increases exponentially. The base winding AB is wound in the opposite direction to the collector winding and so the inductive coupling from the collector winding tends to drive the base positive thus driving the transistor TR1 into saturation.

When the collector current reaches saturation the induced voltage in the base falls to zero causing a reduction in base current. This tends to reduce the collector current and induce a reverse voltage in the collector winding. The overall effect is to bring the transistor out of saturation.

The regenerative effect continues until the transistor enters the cut-off region. The discharge of winding capacitance is sufficient to generate a voltage across

the collector winding which causes the cycle to be repeated. Hence whilst the switch remains closed a series of pulses are generated at the collector. Figs. 4a and b show the collector current and voltage waveforms.

A tertiary winding EF, wound in phase with the collector winding, steps up the voltage appearing across CD to a level of approximately 600V. The resulting pulses are used to charge C1.

The transistor used should have a low $V_{ce(sat)}$ to minimise the energy loss and also have a good collector-to-base breakdown voltage.

WINDINGS

The design of windings is related to the transistor used. The base and collector windings should be optimised to achieve maximum output without drawing too large a collector current. For this design, using a Microelectronics type ME 8001 transistor or its equivalent (BFY 50, 2N2297), a base winding of 12 turns of 37 s.w.g. and a collector winding of 18 turns of 33 s.w.g. will be found suitable.

The collector voltage should be approximately 28V, choice of 600 turns of 44 s.w.g. for the secondary provides the requisite intermediate voltage.

The oscillator windings are housed in a 14mm pot core. The main requirement for the ferrite material is that the saturation level is not too low.

SWITCHING AND DISCHARGE CIRCUIT

Charging the capacitor is achieved through a rectifying diode D1 which should be an 800V type. The diode should also have a fast switch-off time to minimise leakage from the capacitor. A BA157 is chosen as a suitable component.

The main discharge capacitor is a 250V type the capacitance of which is governed by the energy requirements of the spark. Generally a 0.47 μ F is suitable for the application. The I.T.T. range of PMT capacitors is recommended as they appear to withstand the high current discharges which occur during the oscillation.

THE SWITCH

The switch used is a device known as a surge voltage protector. This component originated as a protection for equipment which was liable to high voltage spikes. The device is similar to a neon in that a pair of electrodes are contained in a glass envelope which is filled with an inert gas.

When sufficient electrical stress appears across the electrodes breakdown will occur and current of up to several tens of amps will be allowed to pass under pulse conditions. Subsequent to breakdown a voltage of about 25V exists across the device. The type used in this case has a breakdown of about 220V, thus the capacitor charges to 220V, the protector flashes over and the resulting oscillation generates the high voltage for the spark.

TRANSFORMER DESIGN

The number of primary turns required may be estimated on the basis of impedance matching and energy input to the transformer. From this the secondary turns may be estimated from simple transformer theory. For the size of electrode gap used here an output of 8kV will be required.

A primary of 40 turns of 30 s.w.g. and a secondary of 3000 turns of 40 s.w.g. will be found suitable. The

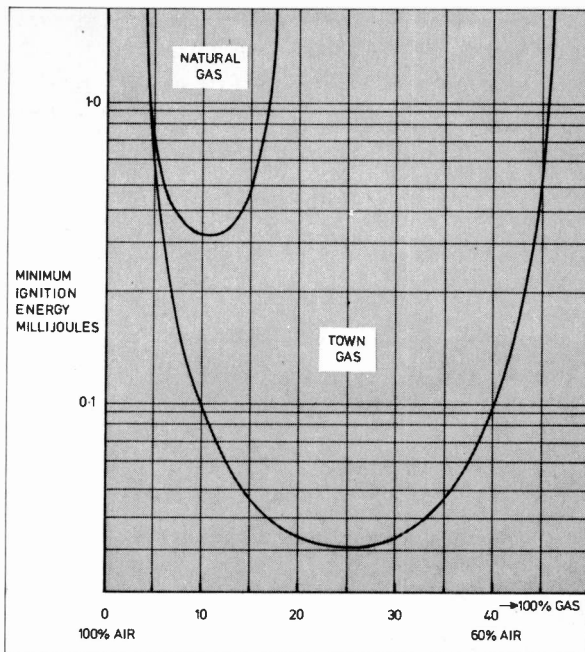


Fig. 1. The energy required to ignite natural gas/air mixtures compared with that required to ignite a town gas/air mixture

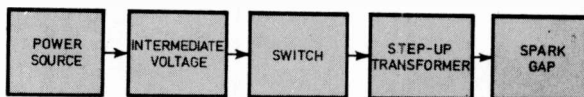


Fig. 2. System diagram of the high voltage production concept using a low voltage source

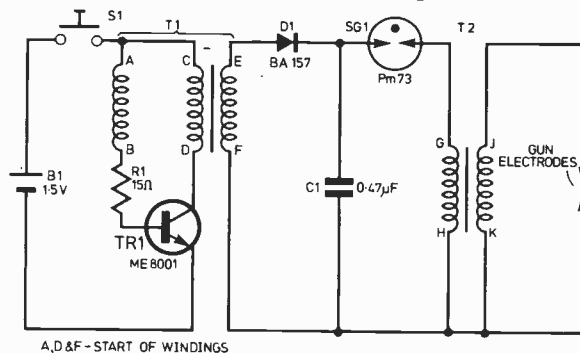


Fig. 3. Circuit diagram of the gas ignitor

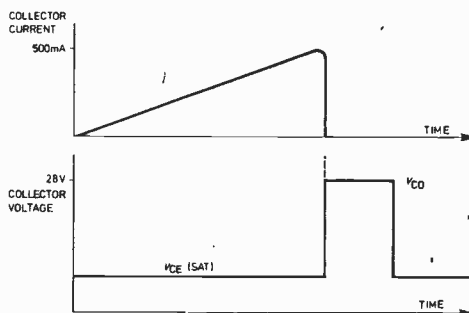


Fig. 4. Collector current (above) and voltage (below) waveforms for TR1 in Fig. 3.

MATRIX BOARD VERSION

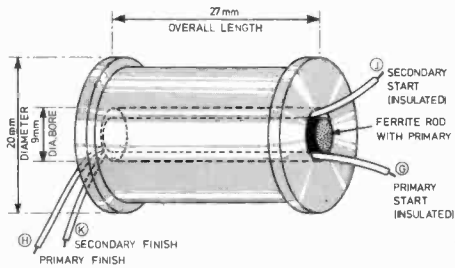


Fig. 5. Constructional details of the output transformer T2

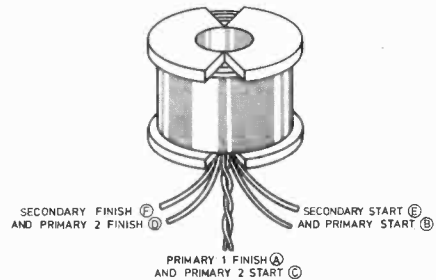


Fig. 6. Details of the oscillator transformer T1

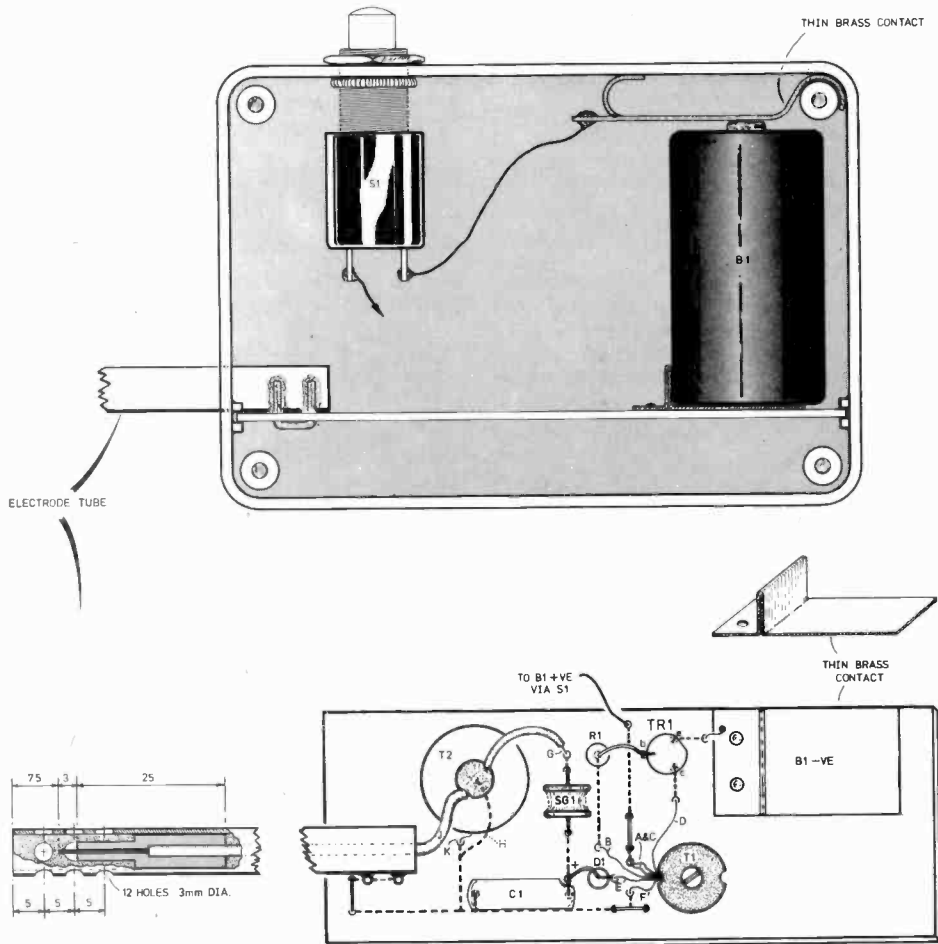


Fig. 7. Construction and component layout for the matrix board and case, together with details of the electrode tube

COMPONENTS...

Resistor

R1 15Ω, ¼W carbon

Capacitor

C1 0.47μF, 750VW, d.c.

Transistor

TR1 ME8001

Diode

D1 BA157

Coils

Oscillator coil: Single section 14mm bobbin, 14mm ferrite core, FX 3594, 1g of 44 s.w.g. enamelled copper wire, 0.1g of 37 s.w.g. and 0.3g of 33 s.w.g., tape to suit.


Output transformer: Ferrite rod, 27mm by 8mm; bobbin, see text; 1g 30 s.w.g. enamelled copper wire, 1g 44 s.w.g.; tape to suit.

Electrode tube: Brass or copper tube, 9mm o.d., 0.5 to 1mm wall thickness, 150mm; 20 s.w.g. tinned copper wire insulated with 1mm wall-thickness silicone rubber tube or equiv.; epoxy putty, fire clay etc. as needed.

Miscellaneous

Matrix board, 0.1 or 0.15in. hole spacing; S1, push-to-make switch; Voltage protector, Siemens KASO2; plastic box ref. 1005; solder, wire etc. as required.

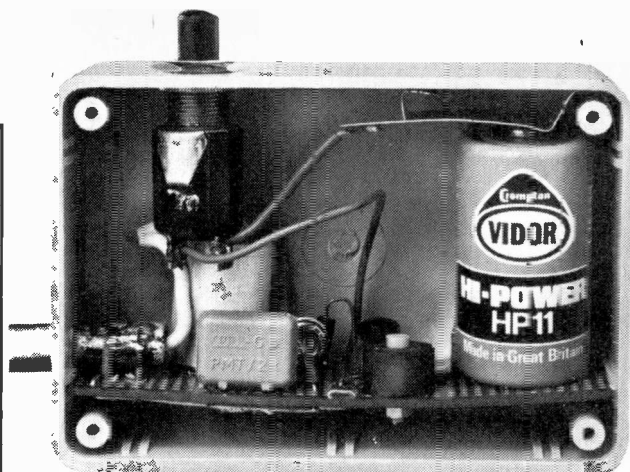For the fully described version the plastic case can be obtained from Crescent Radio Ltd., 11 Mayes Road, London, N.22. The case and a complete kit for the second proprietary version can be obtained from Greenweld, 51 Shirley Park Road, Southampton, SO1 4FX, Tel. 772501. The Siemens voltage protector can be obtained from Jermyn Distribution, Vestry Way, Sevenoaks, Kent.



the winding with adhesive tape. To reduce the possibility of breakdown due to the voltage gradient across the coil, tape layers should be introduced at approximate intervals of 750 turns.

Finally the primary coil should be fitted into the bore of the secondary bobbin with a good fit.

OSCILLATOR COIL

This coil is wound on a proprietary bobbin in the form of three separate windings although when connected, the two primaries become a single winding with a tap. The windings should be as even as possible, reasonably tight and in the order shown in Fig. 6.



Insulation between windings is not necessary but a layer of tape may be usefully used. A final wrap of tape is recommended to secure the windings. All windings should be in the same direction to ensure correct phasing, with the ends left sufficiently long to allow connection. Turns details are given under windings.

magnetic core for the transformer should be a ferrite rod which will fit inside the former on which the secondary is wound.

The primary winding can be wound directly on to the ferrite rod which can then be inserted inside the secondary winding, see Fig. 5.

This coil is constructed in two separate parts to ensure adequate insulation between primary and secondary. Again both windings are in the same direction. The primary is wound using 30 s.w.g. enamelled copper wire directly onto the ferrite rod and consists of 40 turns close wound in a single layer wire so as to ensure a firm fit into the bore of the secondary bobbin.

The secondary requires a suitable plastic bobbin which approximates to the dimensions shown in Fig. 5, onto which are wound 3,000 turns of 40 s.w.g. enamelled copper wire. The start wire is brought out through a hole in the cheek and due to the thinness of the wire, re-inforcement of the lead is recommended, either by skeining or by soldering a more substantial insulated lead onto the wire prior to winding. In the latter case, the joint should be well insulated and secured inside

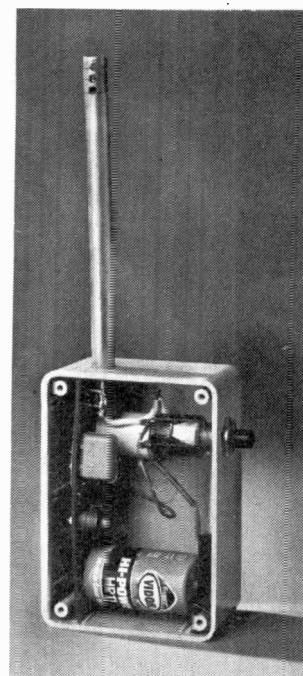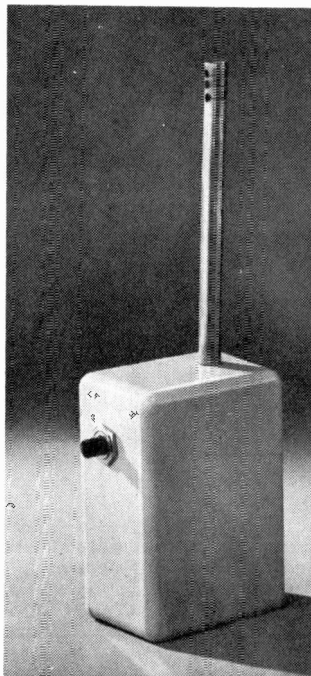

P.C.B. VERSION

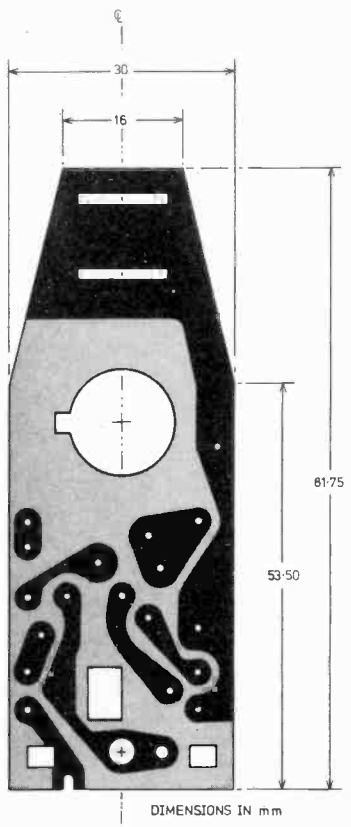
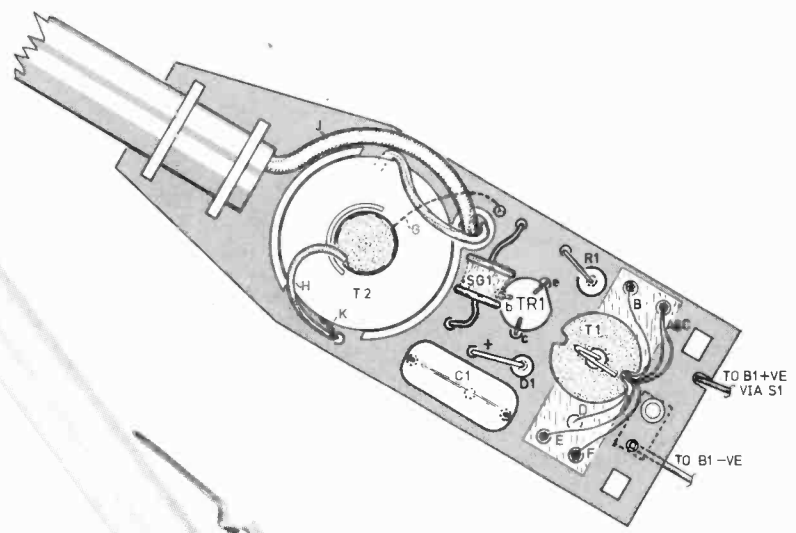


Fig. 8. General layout, component details and p.c.b. master for the printed circuit version

ELECTRODE TUBE ASSEMBLY

Since it is the function of this unit to ignite gas virtually instantly, this part should be constructed in such a way that the best possible spark gap is produced and that gas is able to surround the electrode easily. Materials should be heat resistant, the tube being conductive and preferably solderable. For this purpose brass or copper are recommended.

Basically the assembly consists of a well insulated wire, the end of which is bared to discharge the spark across an air gap of 3 to 4mm to the outer tube. An essential part of the structure is a heat resistant inner insulating tube which positions longitudinally and centralises the electrode wire.

For the model this part was constructed from a 2-part epoxy putty which cures hard, resists heat and adheres to the inside of the tube. This part could equally well be produced from clay or fabricated from fire brick, etc. and secured in position with an epoxy adhesive or the like.

Fig. 7 shows the electrode tube assembly.

ASSEMBLY AND MOUNTING

The first stage is to cut a 100 × 37mm section of matrix board to size, drill additional holes and fit the spring battery connection (28 s.w.g. brass or similar) as shown in Fig. 7. The components are mounted as shown, securing the oscillator ferrite core halves together and to the board with a 6 B.A. brass screw. The output transformer was fixed in position with two layers of double-sided adhesive tape although a suitable adhesive would have been quite adequate.

Next the board assembly is slid into a plastic box in which two holes have been drilled as shown and the electrode tube positioned through one hole before soldering it to the double bar of 16 s.w.g. tinned copper wire for retention and connection. The output wire is soldered to the electrode from J on the output winding and the joint well insulated. The switch is fitted and connections made to the board and the second battery spring which is bent to engage a pillar in the box chosen.

The battery is located between the two springs as shown in the accompanying photographs noting the polarity.

APPLICATION

Ignition is normally best obtained by touching the tip of the electrode tube against the gas burner and allowing 1 or 2 seconds after opening the burner before operating the igniter.

It has been suggested that in the absence of ignition after a few sparks, turn the gas off and blow away the surplus before trying again. Some experiment may be required before the best spark-to-burner distance is accurately achieved.

You will find this igniter ideal for camping, boating, caravanning as well as for use in the kitchen. It will provide you with many years of normal use.

PRINTED CIRCUIT VERSION

For those who wish, a second version of the igniter is proposed here using a printed circuit board, a diagram of which appears in Fig. 8.

This version makes use of a proprietary clear plastic case with self-contained "trigger" switch, battery

retaining members, ignitor tube and even a spring clip with which the ignitor can be hung up on a hook.

Of course, there is nothing to stop anyone from using p.c.b. techniques in the manufacture of the first version or, for that matter, Veroboard techniques.

The clear plastic case version makes use of a complex moulding which holds the trigger tube in place with snap-action clips. The tube holds the p.c.b. in place using two metal clips which engage through the board, and the whole is held in place finally with a moulded plastic element which acts as an end plate against which the battery is pressed by a cover.

The moulding includes an access through which a trigger passes to engage with a spring and suitable contacts on the end plate. The mouldings and various parts are available from Greenweld. ★

NEWS BRIEFS

Electronics For School Teachers

THE University of Essex is holding its fourth Electronics Summer School for teachers from July 7-11. This will take the form of two courses which will be run simultaneously.

The first course, ESS 8—Linear Circuit Design—is concerned with the use of transistors and operational amplifiers in linear applications such as amplifiers, filters and power supplies. The second course, ESS 9—Digital Circuit Design—concentrates on the use of the transistor as a switch and develops design using integrated logic circuits.

A full laboratory programme backs up the topics covered in the lectures, and tutorials are held to discuss the design for the practical sessions.

Further details can be obtained by writing to Bob Mack at The Department of Electrical Engineering Science, University of Essex, Wivenhoe Park, Colchester, Essex, CO4 3SQ.

Queen's Award

THE Queen's Award to Industry, 1975 in recognition of its export achievement and for technological innovation in scientific electronic calculators has been awarded to Sinclair Radionics for their "Sinclair Scientific".

During a three year period ending in April 1974 the company, which is claimed to be Europe's largest manufacturer of electronic calculators, increased its exports tenfold to £2,232,040 p.a. or 56 per cent of turnover.

Sinclair is one of only two companies that have won the award in both categories this year. In the previous three years only three companies have been successful in both categories.

JUST THE IDEA!

VALUABLE PRIZES TO BE WON

A competition for the most novel ideas for practical applications of a particular circuit in this issue.

Details Next Month.

CHRISTMAS PRESENT

The name of Jocelyn Bell became recognised by the scientific world when her observations of the first pulsar were announced. Since then she has changed both her location and her name. Her new location is the Mullard Space Science Laboratory at Dorking and her new name Jocelyn Bell Burnell.

With the team at Dorking, John Ives, Peter Sanford, Jocelyn Bell Burnell is engaged on carrying out the task of reducing data from *Ariel 5*, the United Kingdom's first X-ray Satellite. The whole of the programme of this satellite is devoted to observations of existing X-ray sources and the search for new ones.

One new star which flared up at Christmas was named, by Jocelyn Bell Burnell, Cen-Xmas. It was observed from December 19 to January 27. This star may well supply the clue to a class of X-ray sources not previously known.

Cen-Xmas was discovered in the constellation of Centaurus near to an already known source Cen X-3. Cen-Xmas flared up on Christmas day and showed a light curve much like that which appears at optical wavelengths by fast moving Novae.

The team observed that there was a regular rising and falling of intensity every 6.755 minutes. This was a point of great interest since the usual periods of variation for X-ray binary systems is hours or even days and the periods for pulsars a few seconds or less. It does not seem likely that it was a slowly rotating neutron star.

OPINION

The team are of the opinion that the source may be a binary system of two collapsed objects. These could be perhaps a white dwarf and a neutron star. Another possibility has been put forward and that is the objects could be a white dwarf and a black hole. Clearly the object is unusual in the present catalogue. The official catalogue number is *Ariel 1118-61*.

A search is now being made in the data of the *Copernicus* satellite to see whether there have been earlier bursts. A request has been made that *Copernicus*, which has better pointing facilities than *Ariel*, should specially observe this area of the sky.

Satellite *Ariel 5* has more than justified its launch in this valuable study of X-ray sources.

ANOTHER DISCOVERY

A second bonus is the discovery of a very bright source near the galactic centre. This, according to Professor



BY FRANK W. HYDE

K. A. Pounds of Leicester, a pioneer in these observations, was not visible in November when that area was studied. The new source is second only in brightness to a source called Sco X-1.

This new source as yet un-named is at such a vast distance that its intensity must be at the upper limit for normal galactic X-ray sources. Both Cambridge and the Jodrell Bank teams have been asked to watch the area in case the X-ray flare up should be followed by radio bursts.

FURTHER EXPERIMENT

Another experiment aboard the satellite also controlled by Leicester, with the team led by Professor Pounds has indicated that an excess of heavy elements such as iron have been found in the super nova remnants of Tycho and Cassiopeia A. As this is the first report of the X-ray detection of spectral lines from a cosmic source it adds weight to the growing feeling that the heavy elements in the universe may be produced at the time of the explosions associated with supernovae.

It would seem that the fluctuating nature of X-ray sources is a common factor. Professor Pounds thinks that they may account for 30 per cent of the known sources. There are now more than two hundred recorded.

FADE-OUT!

A notable feature, derived from data received from *Ariel*, is the number of sources that do not last all the time. During the present period of observation some 16 sources have disappeared from the

areas. This may be because they are now out of the limits of detection or that there has been a change of such a nature that there are no longer X-ray types of emission. The sixteen sources that have disappeared were originally detected by the *Uhuru* satellite.

It is expected that *Ariel 5* will be able to continue operations for a year with the gas available on board. Thereafter it will be a waiting period till the next British X-ray satellite is launched in 1977.

SATELLITE DETAILS

The data handling system of the *Ariel 5* satellite is effectively a fixed programme computer with two core stores. This enables the integration of experimental data so that the best may be made of the low data rate of transmission from the spacecraft. Only by keeping the data rate low is it possible to utilise long ground data-links.

The details of the satellite are:

<i>Dimensions</i>	Diameter 38 in, length 34 in, weight 298 lbs
<i>Stabilisation</i>	Spin 10 ± 2 r.p.m.
<i>Attitude control</i>	Propane gas jets
<i>Power supply</i>	Solar array 35W
<i>Telemetry</i>	PCM
Frequency	137.68MHz
Real time power	85mW
Real time rate	2048 bits/second
Playback power	80W
Playback rate	2048 bits/second
Stations	Quito and Ascension (Nasa stations)
<i>Telecommand</i>	Digital tone
Frequency	148.25MHz

NEWS FROM RUSSIA

India's first satellite is being prepared for launching from a Soviet site. Academician Boris Petrov, chairman of the Intergovernmental Council, said that the joint work of the Soviet scientists and experts had produced an elaborate spacecraft for experiments connected with research in the short wave radiation of celestial bodies, together with studies of the ionosphere.

Launched on March 27, *Intergovernmental 13* is a joint socialist countries enterprise. The main aim is to study dynamic processes in the magnetosphere and the polar ionosphere. Research is also directed to low frequency electromagnetic waves.

The satellite carries instrumentation from the Soviet Union and Czechoslovakia. The participating observation points are in Bulgaria, the German Democratic Republic, the Soviet Union and Czechoslovakia.

THERE are numerous guitar effects pedals available today, but there are still many areas of sound treatment in which it is possible for the amateur to produce something which is not just a copy of a commercial effect.

The pedal to be described makes use of voltage control techniques. There are two treatments, a voltage controlled amplifier and a voltage controlled filter; either of which can be selected by a switch. These are controlled by an oscillator which produces triangle, square and rising and falling ramps at controllable frequency and amplitude. The combination of four waveforms and two treatments gives eight basic effects, all of which can be considerably modified by adjustment of the controls.

WAVEFORM GENERATOR

The basic rising ramp wave is generated by IC1 and 2 (see Fig. 1). Integrator IC1 ramps upwards at a rate set by the speed control until it exceeds a limit set by comparator IC2. Then, a large reset current flows through D1 and R2 until the integrator is back to its starting point.

When the waveform switch is in the falling ramp position, IC3 acts as a unity gain inverter to give the required waveform.

In the square position, IC3 acts as a comparator. This gives a square wave of $\pm 8V$ at the i.c. output, which is reduced by R14 to the same level as the other waveforms.

The triangle wave is shaped from the ramp wave by TR1. When out of saturation, this has a gain of -1 . It is biased by VR2 so that for half the cycle it is saturated, when it has a gain of $+1$. The triangular wave at the collector of TR1 is amplified by IC3. VR3 is adjusted to offset the d.c. introduced by TR1 and its associated components.

VOLTAGE CONTROLLED FILTER

When S2 is in the filter position, IC5 has multipath feedback with a minimum at a single frequency. The overall response is then bandpass peaking at that frequency, which can be changed by changing the voltage on the gate of the f.e.t.

VOLTAGE CONTROLLED AMPLIFIER

R22 and TR2 form an attenuator, and since the effective resistance of the f.e.t. can be varied by changing the gate voltage, the degree of attenuation can be changed. IC5 becomes an amplifier with a gain of 10 with S2 in the envelope position; this amplifies the previously attenuated signal.

In both the v.c.a. and the v.c.f. the f.e.t. is being used as a voltage controlled resistor. The effective resistance between the drain and source depends on the amount of negative bias on the gate. As the amount required varies from transistor to transistor, preset VR5 is included.

The control voltage from VR4 is also fed to the gate via a low-pass filter R15, R16, C5 and C6. This removes the sharp edges from the signal and so reduces the breakthrough of the control into the output.

BATTERY SWITCHING

There are two batteries to be switched on by the insertion of a jack plug to SK1. It is possible to get sockets which have a single make connection, which is used to turn on the positive supply. This turns on TR3, which then turns on the negative rail. The leakage through TR3 when it is off is negligible.

GUITAR EFFECTS PEDAL

By R. GWINN



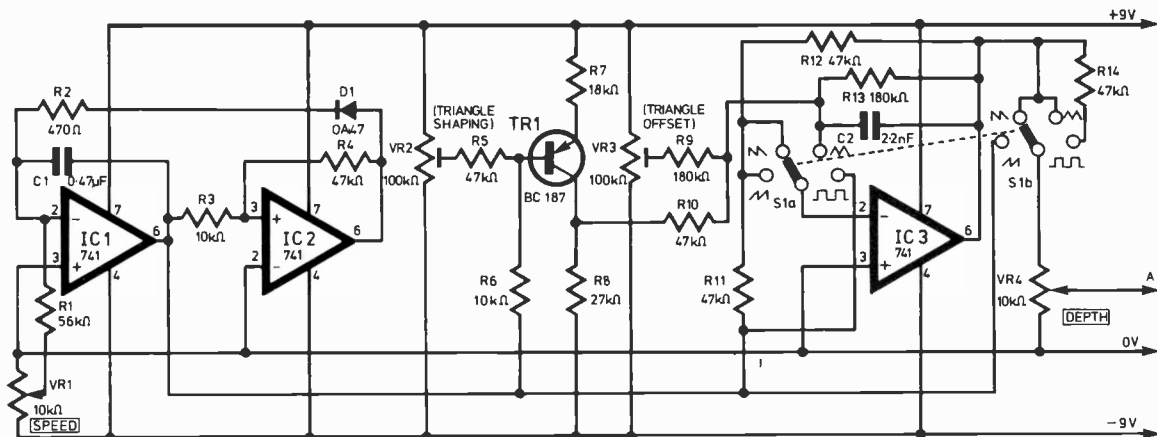


Fig. 1. Circuit of the Effects Pedal

CONSTRUCTION

Most of the components are mounted on a piece of Veroboard 67mm × 112mm (Fig. 2). These are rather tightly packed as there is a lot to be fitted on. The board is screwed into a plastic bracket to hold it in place.

The unit can be housed in any convenient case, which should be earthed to prevent hum. This could be done by soldering onto the back of a pot.

The batteries are prevented from moving with a sheet of foam rubber.

SETTING UP

Turn all presets to mid-positions. While monitoring the waveform at the output of IC3, with the waveform switch set to "triangle", adjust VR2 for the best triangle wave shape. A scope is useful for this. Now set VR3 for 0V d.c. at IC3 output.

Set S2 to "filter". With the depth control at maximum, adjust VR5 for the best sound—a smooth change in filter frequency without it breaking into oscillation.

Finally set VR6 so that the volume of the treated signal is the same as in the straight through position.

PLAYING TECHNIQUE

All the effects are repetitive, so it is best used on sustained chords or single notes. Apart from that, there are no set rules to stick to.

It will be noticed that rising and falling ramps have opposite effects on the two treatments; this is so that subjectively more interesting changes can be made simply by switching effects with one's feet. Thus a rising ramp selected on the switch will produce a decaying sound on the v.c.a.

A fast decaying ramp on the v.c.a. produces a sound like a mandolin; the same control into the filter gives a bubbling, which slows down into a repeated "Waa-Waa". A very slow triangle into the filter can be applied to any playing including fast runs.

The unit can of course be used to treat any instrument, with due attention to the matching of signal levels. ★


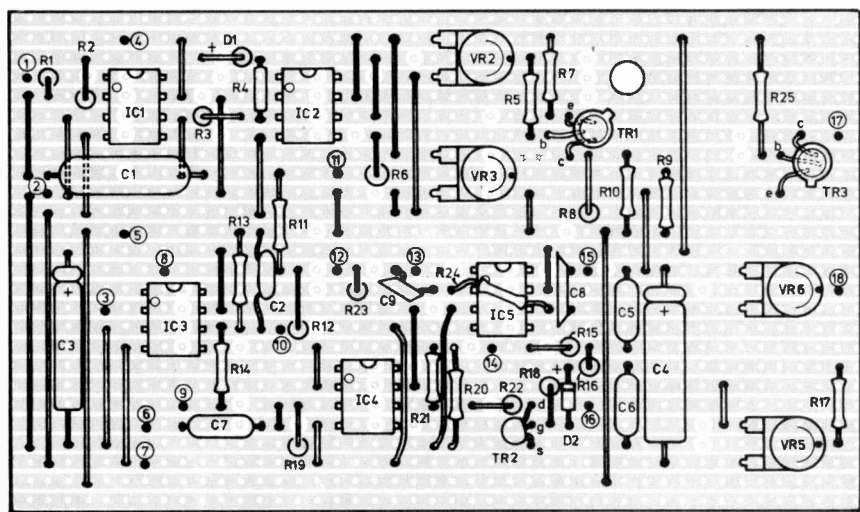


Fig. 2. Component layout and track cuts

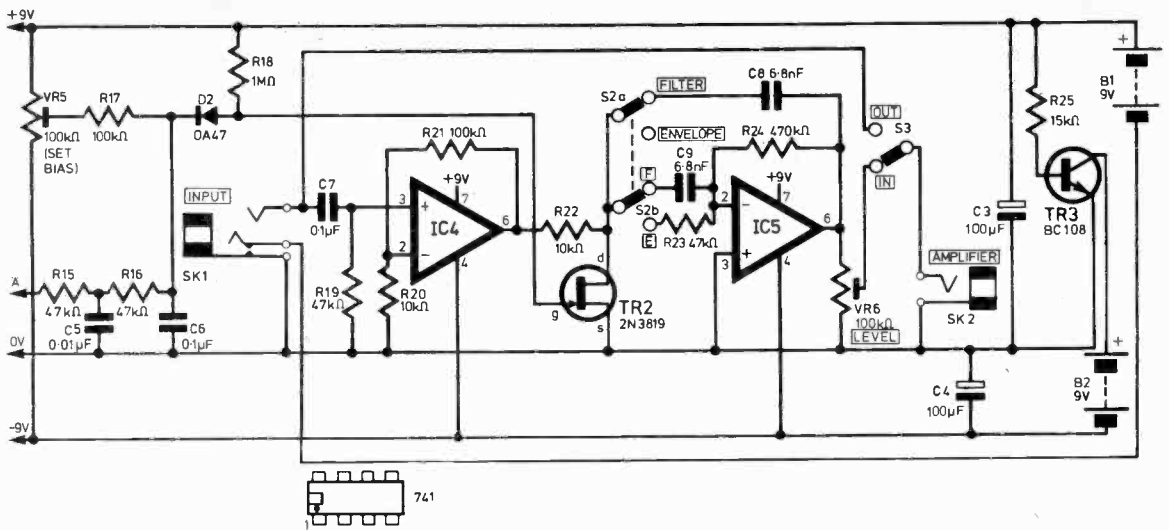

COMPONENTS . . .

Resistors

R1	56k Ω	R14	47k Ω
R2	470 Ω	R15	47k Ω
R3	10k Ω	R16	47k Ω
R4	47k Ω	R17	100k Ω
R5	47k Ω	R18	1M Ω
R6	10k Ω	R19	47k Ω
R7	18k Ω	R20	10k Ω
R8	27k Ω	R21	100k Ω
R9	180k Ω	R22	10k Ω
R10	47k Ω	R23	47k Ω
R11	47k Ω	R24	470k Ω
R12	47k Ω	R25	15k Ω
R13	180k Ω		

All $\frac{1}{2}$ watt 10% carbon

Potentiometers

VR1	10k Ω log
VR2	100k Ω linear
VR3	100k Ω linear
VR4	10k Ω linear
VR5	100k Ω linear
VR6	100k Ω linear

Capacitors

C1	0.47 μ F
C2	2.2nF
C3-C4	100 μ F elect. 25V (2 off)
C5	0.01 μ F
C6	0.1 μ F
C7	0.1 μ F
C8-C9	6.8nF (2 off)

Semiconductors

IC1-IC5	741 (5 off)
TR1	BC187
TR2	2N3819
TR3	BC108
D1-D2	OA47 (2 off)

Miscellaneous

B1-B2 9V PP3 (2 off), S1-2 pole, 4 way switch, S2-2 pole, 2 way switch, S3-single pole change-over, SK1-jacket socket with make contacts, SK2-standard jack socket.

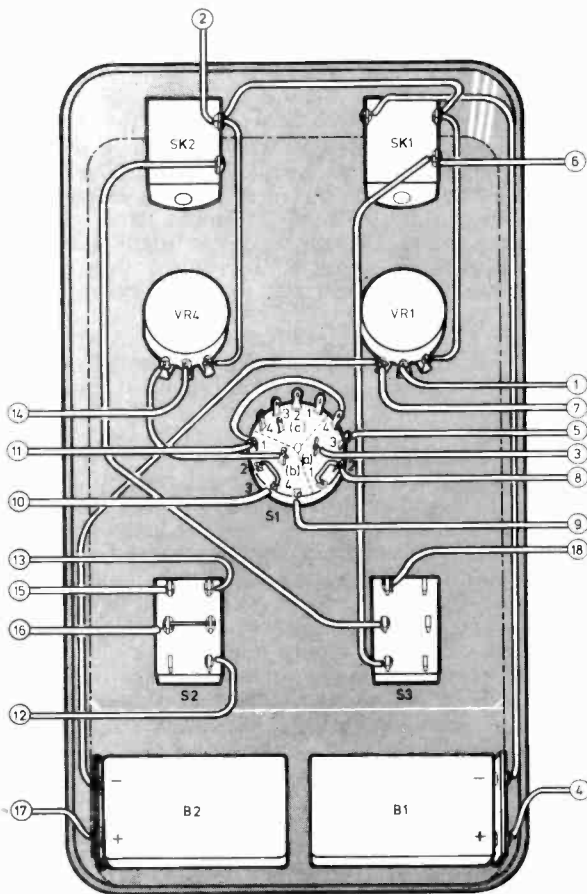


Fig. 3. Control panel wiring details

Distance Heat Light Temperature Speed Force Frequency Distance Heat Light Temperature PART 4 Inductive Devices Heat Light & Physical Parameters Frequency Distance Force Load Sound Frequency Distance Heat

PART 4 Inductive Devices & Physical Parameters

By P.R. ALLCOCK

THE second section on inductive devices is concerned mainly with synchronous and stepping transducers.

SYNCHRO TRANSFORMERS

This group includes a wide variety of devices such as torque-producing synchros, control synchros, resolvers and related devices. These devices are widely used in systems involving angular displacement and angular position control and are similar in construction to small three phase alternators of fractional horse power rating.

They are often classified according to their intended application, construction or manufacturers' trade names.

The form of the rotor and the arrangement of the rotor winding identify the type of synchro and its

function. Generally the synchro stator is a cylindrical slotted structure made up of laminations and having three separate windings arranged in slots which are displaced, spatially, by 120° from each other.

The slots are often skewed one slot pitch to avoid any tendency for slot locking and the resulting angular displacement error. Sometimes the stator slots are parallel to the rotor axis in which case the rotor laminations are normally skewed for the above reasons. Unlike the usual three phase system the voltages associated with the three stator windings are all in step or phase with each other as far as their voltage-time variation is concerned.

The rotor of a control or torque synchro usually carries a single winding and often has a salient-pole form, the coil connections being made available via slip rings. Resolvers on the other hand usually have two rotor and stator coils.

PRINCIPLE

The synchro principle is illustrated in Fig. 4.1. The magnitude of the voltages induced into the three stator coils depends on the rotor position and varies sinusoidally with shaft displacement from some reference position. The system is essentially a transformer with three output coils in which the degree of coupling to the primary rotor coil varies with rotor position.

There is always an output from the system whether the rotor is in motion or not—consequently slowly varying or static angular displacement can be determined.

The resolver usually operates as a two phase system as illustrated at Fig. 4.1b. The rotor coils provide output voltages which vary as the cosine and sine of the angular displacement, by virtue of the variation of coupling and the relative coil displacements. When output from coil O1 is maximum, that from coil O2 will be zero. A rotation of 90° will cause the output of coil O1 to be zero whilst that of coil O2 reaches its maximum.

In some applications only one coil may be used in which case the unused coil is normally short circuited. With two primary and two secondary coils four vector combinations are possible for both coil sets according to the sense of the coils.

Synchros and resolvers are usually designed to operate at 50, 60 or 400Hz, often at specified voltage levels and in all cases it is essential to follow the manufacturers' advice and ratings if the best accuracy is to be achieved. For further details the reader should consult the references listed, together with manufacturers' data/application sheets.

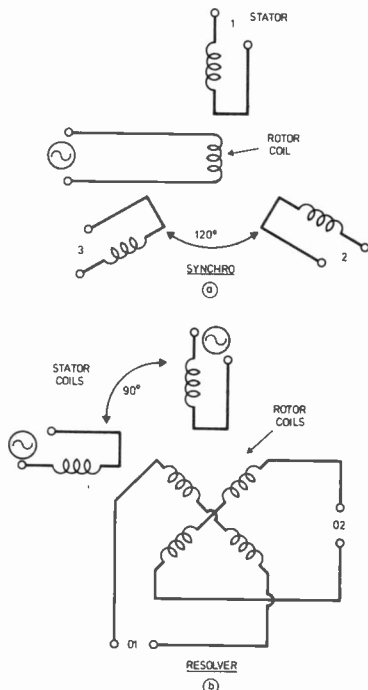


Fig. 4.1. The principle of the synchro/resolver system for transmitting rotary position information

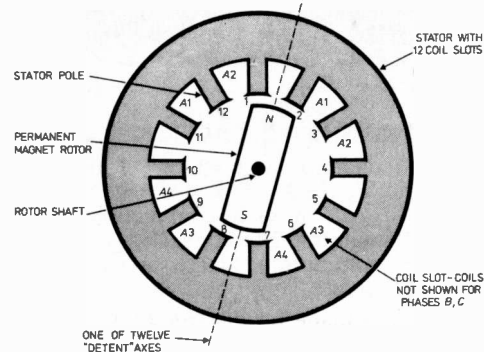


Fig. 4.2. The stepper motor concept in diagrammatic form

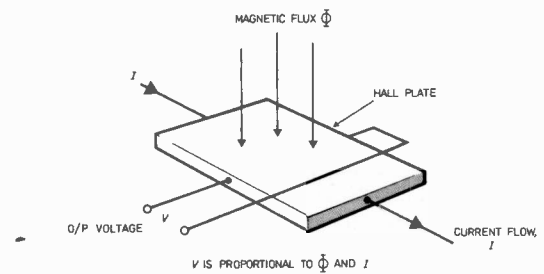


Fig. 4.5. Principle of operation of a Hall Effect probe

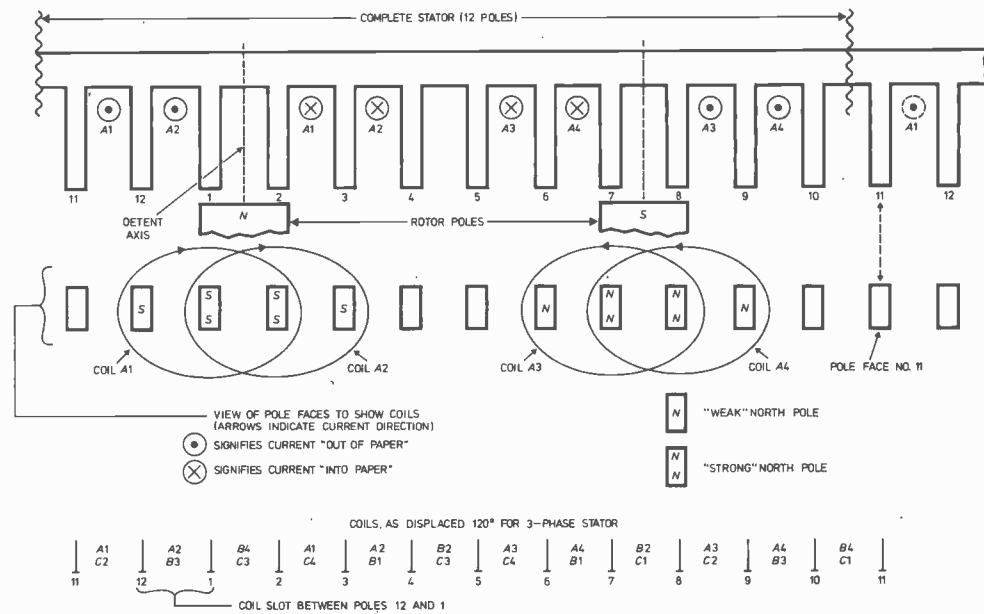


Fig. 4.3. The motor of Fig. 4.2 opened out to show the coil and pole orientation

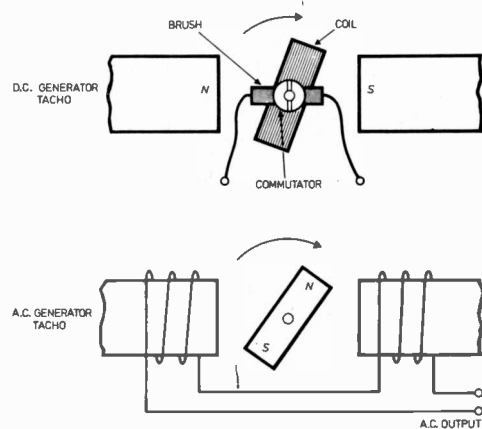


Fig. 4.4. Three versions of the electromagnetic tachometer principle, the d.c. generator, a.c. generator and toothed rotor

STEPPER MOTORS

Several devices have been invented for imparting a given amount of angular movement to a shaft, in response to an electrical input. Two common examples are the stepping uniselector mechanism and the Ledex solenoid system, both of which involve a form of ratchet action. The stepper motor, however, does not use a mechanical ratchet but achieves its position latching feature by virtue of its special magnetic system.

Two main types exist, those using permanent magnet rotors and those using variable reluctance techniques. The variable reluctance group can be further subdivided into vernier and non vernier types. (vernier motors achieve more steps per revolution than might be indicated by the number of teeth on the rotor or stator.)

Stepper motors do not have brushes or slip rings and are consequently robust and reliable with a low maintenance requirement. The electrical excitation is provided by a two, three or four phase coil system on the stator portion of the motor.

Fig. 4.2 illustrates the operation of a permanent magnet rotor, three phase stator, type of construction. The rotor only has two poles and with the stator un-energised, the motor has 12 magnetic "detent" positions as illustrated where the rotor is aligned on an axis midway between adjacent pairs of stator poles.

If the shaft of such a motor is rotated by hand these detent positions can easily be felt since the rotor tends to pull into the nearest available detent position as the shaft turns.

To illustrate the stepping action under drive conditions the motor stator is shown opened out into a straight line in Fig. 4.3. Each of the three separate stator coil sets is made up of four coils in series such as *A1, A2, A3, A4* for the "A" phase. The sense of the currents that flow in these four coils is shown by arrows and it can be seen that coils *A1, A2* produce four south poles whilst coils *A3, A4* produce four north poles.

The flux of the innermost two poles in each group of four is greater than that of the outermost poles since two aiding coils encircle the inner poles but only one coil encircles each of the outermost poles. The rotor thus aligns itself as illustrated in Fig. 4.3 if only the *A* phase is energised.

The *B* and *C* phases also employ four coils each, in exactly the same pattern as for phase *A*. However, the slots used are displaced by 120° in each case. Thus coil *A1* is displaced 120° from *B1* which in turn is displaced 120° from *C1*. Likewise coils *A2, B2, C2* are displaced 120° apart and so on. The effect of this is that each of the 12 coil slots in the stator carries two coils from different phase coil-groups.

STEPPING ACTION

The stepping action is determined, for a given construction and coil system, by the manner in which the various phases are energised. If the phases are energised singly in the sequence *A, B, C* the rotor will take three steps to complete one complete revolution of 360° . Energising the *A* phase brings the rotor north pole to midway between poles 1 and 2. Subsequent energisation of the *B* phase pulls the rotor north pole to an equivalent position with regard to coils *B1, B2* which gives an axis midway between poles 5 and 6, a rotation of four poles or 120° .

Subsequent energisation of the *C* phase gives a rotor axis midway between poles 9 and 10.

Smaller angular steps can be achieved by controlling the phases in the sequence *A* only; *A* and *B*, *B* only, *B* and *C*, *C* only, *C* and *A*, etc. This gives six steps of 60° each.

ELECTROMAGNETIC TACHOMETERS

The most common tachometer arrangements are illustrated in Fig. 4.4. The d.c. tachometer uses a permanent magnet stator in conjunction with a rotor coil and commutator. The connections to the coil are made via the commutator and associated brushes and the output voltage is proportional to the angular velocity. Reversing the direction of rotation reverses the output voltage polarity and this is a useful characteristic in some applications. The brush/commutator arrangement requires periodic maintenance if reliable operation is to be obtained.

The a.c. tachometer uses a rotating magnet and fixed stator coil thus avoiding the need for brushes and commutator. Both the amplitude and frequency of the output depend on angular velocity and in modern systems an electronic frequency meter is usually employed to give the shaft speed directly, in, say, rev/min, as this avoids the inaccuracies associated with measurement of voltage.

Variable-reluctance pulse generating systems are also widely used due to their simplicity and reliability, the number of output pulses per revolution in this case depends on the number of teeth on the rotor wheel or disc.

INTERFERENCE


All magnetic devices can be influenced to some extent by external magnetic fields due to solenoids operating, mains wiring and stray fields of transformers and motors. In some instances the interfering field cannot be removed and the only course of action is to employ magnetic screening and select the best orientation of the transducer to minimise the unwanted coupling. In some situations hum-cancellation coils can be fitted to introduce an opposing interfering voltage into the output circuit. Connecting leads from low-output devices should be tightly twisted and screened to minimise the effective loop area available for flux linkage with the stray field.

HALL EFFECT DEVICES

When a conductor carries a current at right angles to a magnetic field a charge difference is set up on the surface of the conductor in a direction which is mutually perpendicular to both the magnetic field and the current. Modern high mobility semiconducting materials such as Indium Arsenide and Indium Antimonide have made the Hall Effect a useful practical phenomenon due to the magnitude of the voltage available with reasonable levels of magnetic flux density and current. Fig. 4.5 illustrates the basic principles which can be incorporated into a transducer in various ways.

Either the current or magnetic field can be varied to give a change in the output voltage and Hall Effect plates, together with varying magnetic fields, have been used in flowmeters, tachometers, wattmeters, accelerometers and displacement transducers.

Next month: Piezoelectric devices.

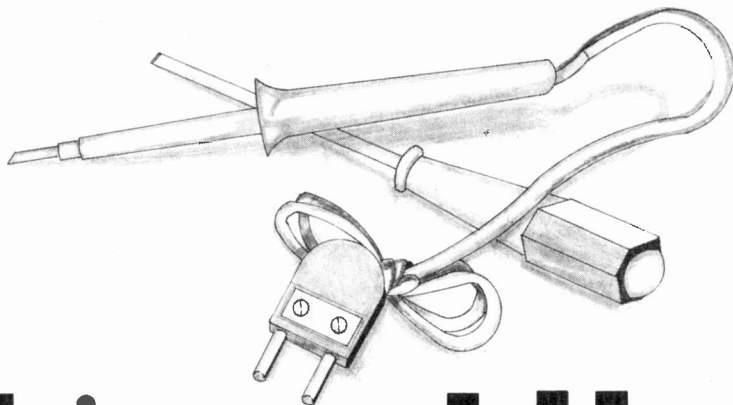

This could lead to something big.

A soldering iron and a screw driver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.


You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you

how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

This course is accepted by and used in a large number of schools and colleges and forms an invaluable grounding for professional training in the subject. All the training is planned to be carried out in the comfort of your own home and work in your own time. You send them in when you are ready and not before. These culminate in a final test and a certificate of success.


1

Build an oscilloscope.

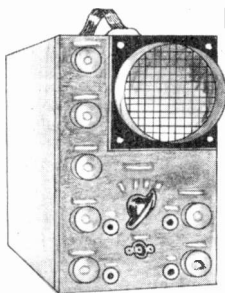

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a professional test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.


2

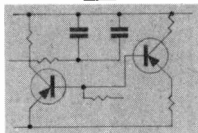

Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.


3

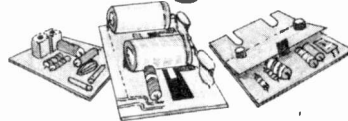

Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

PLUS

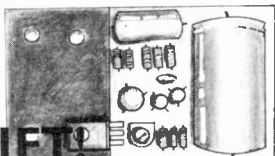

FREE GIFT!

ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

WAA

Brochure without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept EL75
P.O. Box 156, Jersey, Channel Islands.

NAME

ADDRESS

(Block caps please)

Marshall's

Everything you need is in our
New 1975 Catalogue
available now price 25p
(100 pages of prices and data)

A. Marshall (London) Ltd. Dept. PE
42 Cricklewood Broadway London NW2 3DH Telephone 01-452 0161/2 Telex 21492
& 85 West Regent Street Glasgow G2 2QD Telephone 041-332 4133

Call In and see us 9-5.30 Mon-Fri
9-5.00 Sat


Trade and export enquiries welcome

Top 500 Semiconductors From the Largest Range in the U.K.

2N456	0-80	Orange	0-12	2N5192	1-24	AF106	0-40	BC184	0-13	BF153	0-25	LM308	2-50	OC35	0-80
2N456A	0-50	2N3053	0-25	2N5195	1-46	AF109R	0-40	BC184L	0-13	BF154	0-20	LM309K	1-88	OC42	0-50
2N457A	1-20	2N3054	0-60	2N5245	0-47	AF114	0-35	BC186	0-25	BF159	0-27	LM380	1-10	OC45	0-20
2N490	4-14	2N3055	0-75	2N5294	0-48	AF115	0-35	BC187	0-27	BF160	0-23	LM381	2-20	OC71	0-20
2N491	4-38	2N3390	0-45	2N5295	0-48	AF116	0-35	BC207	0-12	BF162	0-42	LM382	2-20	OC72	0-25
2N492	5-00	2N3391	0-28	2N5296	0-48	AF117	0-35	BC208	0-11	BF166	0-40	LM382C	0-75	OC81	0-25
2N493	5-00	2N3391A	0-28	2N5298	0-50	AF118	0-35	BC212K	0-16	BF167	0-25	LM383	0-20	OC83	0-24
2N496	0-22	2N3392	0-15	2N5457	0-49	AF124	0-30	BC212L	0-16	BF173	0-27	LM384	0-48	OPR12	0-55
2N497	0-22	2N3393	0-15	2N5458	0-49	AF125	0-30	BC214L	0-18	BF177	0-29	LM385	0-48	R53	1-80
2N498	0-82	2N3394	0-15	2N5459	0-49	AF126	0-28	BC237	0-16	BF178	0-35	LM401	0-40	SL44A	1-80
2N499	0-58	2N3402	0-18	2N5492	0-58	AF127	0-28	BC238	0-15	BF179	0-43	LM402	0-40	SL610C	1-70
2N706	0-14	2N3403	0-19	2N5494	0-58	AF139	0-65	BC239	0-15	BF180	0-35	LM403	0-40	SL611C	1-70
2N706A	0-16	2N3440	0-59	2N5496	0-61	AF186	0-46	BC251	0-25	BF181	0-36	LM404	0-40	SL612C	1-70
2N708	0-17	2N3441	0-57	2N5777	0-45	AF200	0-65	BC253	0-25	BF182	0-35	LM405	0-40	SL623	4-58
2N709	0-42	2N3442	1-40	2N6027	0-45	AF239	0-65	BC257	0-16	BF183	0-55	LM406	0-40	SL640C	3-10
2N711	0-11	2N3443	0-41	40392	0-41	AF240	0-65	BC258	0-16	BF184	0-55	LM407	1-80	SL641C	3-10
2N718	0-23	2N3415	0-21	3N139	1-42	AF279	0-70	BC259	0-16	BF185	0-30	LM408	0-40	SL642C	3-10
2N718A	0-28	2N3416	0-34	3N140	1-00	AF280	0-70	BC261	0-25	BF194	0-12	LM409	0-40	SL643C	3-10
2N720	0-57	2N3417	0-24	3N141	1-00	AL120	0-79	BC262	0-25	BF195	0-12	LM410	0-40	SL644C	3-10
2N914	0-39	2N3638	0-15	3N200	2-49	AL103	1-00	BC263	0-25	BF196	0-13	LM411	0-40	SL645C	3-10
2N916	0-28	2N3638A	0-15	40361	0-14	BC107	0-14	BC300	0-38	BF197	0-15	LM412	0-40	SL646C	3-10
2N918	0-28	2N3639	0-15	40407	0-15	BC108	0-14	BC301	0-34	BF198	0-18	LM413	0-40	SL647C	3-10
2N929	0-37	2N3641	0-17	40363	0-88	BC109	0-14	BC302	0-40	BF200	0-40	LM414	0-40	SL648C	3-10
2N930	0-22	2N3702	0-12	40389	0-46	BC113	0-15	BC303	0-54	BF225J	0-23	LM415	0-40	SL649C	3-10
2N1302	0-19	2N3703	0-13	40394	0-56	BC115	0-17	BC307	0-17	BF244	0-21	LM416	0-40	SL650C	3-10
2N1303	0-19	2N3704	0-15	40395	0-65	BC116	0-17	BC308A	0-15	BF245	0-45	LM417	0-40	SL651C	3-10
2N1304	0-26	2N3705	0-15	40406	0-44	BC116A	0-18	BC309C	0-20	BF248	0-58	LM418	0-40	SL652C	3-10
2N1305	0-24	2N3706	0-15	40407	0-45	BC117	0-21	BC310	0-27	BF247	0-65	LM419	0-40	SL653C	3-10
2N1306	0-24	2N3707	0-15	40408	0-50	BC118	0-14	BC328	0-28	BF254	0-19	LM420	0-40	SL654C	3-10
2N1307	0-30	2N3708	0-14	40409	0-52	BC119	0-29	BC337	0-20	BF255	0-19	LM421	0-40	SL655C	3-10
2N1308	0-47	2N3709	0-15	40410	0-52	BC121	0-35	BC338	0-20	BF257	0-47	LM422	0-40	SL656C	3-10
2N1309	0-47	2N3710	0-15	40411	2-00	BC125	0-16	BCY30	0-80	BF258	0-53	LM423	0-40	SL657C	3-10
2N1671	1-54	2N3711	0-15	40594	0-74	BC126	0-23	BCY31	0-85	BF259	0-55	LM424	0-40	SL658C	3-10
2N1671A	1-67	2N3712	1-20	40595	0-84	BC132	0-30	BCY32	1-15	BF259	0-55	LM425	0-40	SL659C	3-10
2N1571B	1-85	2N3713	1-20	40601	0-67	BC134	0-13	BCY33	0-85	BF279	0-24	LM426	0-40	SL660C	3-10
2N1711	0-45	2N3714	1-38	40602	0-61	BC135	0-13	BCY34	0-79	BF282A	0-20	LM427	0-40	SL661C	3-10
2N1907	5-50	2N3715	1-50	40603	0-58	BC136	0-17	BCY38	1-00	BF282	0-92	LM428	0-40	SL662C	3-10
2N2102	0-64	2N3716	1-80	40604	0-56	BC137	0-17	BCY39	1-50	BF561	0-27	LM429	0-40	SL663C	3-10
2N2147	0-78	2N3721	2-20	40636	1-10	BC138	0-24	BCY40	0-47	BF598	0-25	LM430	0-40	SL664C	3-10
2N2148	0-94	2N3722	1-80	40659	1-00	BC140	0-68	BCY42	0-28	BF599	0-30	LM431	0-40	SL665C	3-10
2N2160	0-90	2N3723	2-55	40673	0-73	BC141	0-68	BCY58	0-30	BF599	0-30	LM432	0-40	SL666C	3-10
2N2218A	0-22	2N3789	2-06	AC126	0-20	BC142	0-23	BCY59	0-32	BF598A	0-24	LM433	0-40	SL667C	3-10
2N2219	0-24	2N3790	2-40	AC127	0-20	BC143	0-25	BCY70	0-17	BF598	0-30	LM434	0-40	SL668C	3-10
2N2219A	0-26	2N3791	2-35	AC128	0-20	BC145	0-21	BCY71	0-22	BF598	0-28	LM435	0-40	SL669C	3-10
2N2220	0-25	2N3792	2-60	AC151V	0-27	BC147	0-14	BCY72	0-15	BF598	0-25	LM436	0-40	SL670C	3-10
2N2221	0-18	2N3794	0-24	AC152V	0-49	BC148	0-14	BD115	0-75	BF599	0-20	LM437	0-40	SL671C	3-10
2N2221A	0-21	2N3819	0-37	AC153	0-35	BC149	0-15	BD116	0-75	BF599	0-23	LM438	0-40	SL672C	3-10
2N2222	0-20	2N3820	0-64	AC153K	0-40	BC150	0-18	BD121	1-00	BF599	0-23	LM439	0-40	SL673C	3-10
2N2222A	0-25	2N3823	0-78	AC154	0-25	BC154	0-18	BD123	0-82	BF599	0-21	LM440	0-40	SL674C	3-10
2N2268	0-25	2N3904	0-27	AC176	0-30	BC157	0-16	BD124	0-67	BF599	0-18	LM441	0-40	SL675C	3-10
2N2369	0-20	2N3906	0-27	AC176K	0-40	BC158	0-16	BD131	0-40	BFY90	0-75	LM442	0-40	SL676C	3-10
2N2369	0-20	2N4036	0-67	AC187K	0-35	BC160	0-60	BD132	0-50	BRY39	0-23	LM443	0-40	SL677C	3-10
2N2646	0-55	2N4037	0-42	AC188K	0-40	BC167B	0-15	BD135	0-43	BSX20	0-21	LM444	0-40	SL678C	3-10
2N2647	0-58	2N4038	0-18	AC189	0-24	BC168B	0-15	BD136	0-46	BSX21	0-29	LM445	0-40	SL679C	3-10
2N2904	0-22	2N4059	0-15	ACY19	0-27	BC168C	0-15	BD137	0-55	BU104	2-00	LM446	0-40	SL680C	3-10
2N2904A	0-24	2N4060	0-15	ACY20	0-22	BC169B	0-15	BD138	0-63	BU105	2-25	LM447	0-40	SL681C	3-10
2N2905	0-25	2N4061	0-15	ACY21	0-26	BC169C	0-15	BD139	0-61	CI06D	0-65	LM448	0-40	SL682C	3-10
2N2905A	0-26	2N4062	0-15	ACY28	0-20	BC170A	0-15	BD140	0-87	CA3018A	0-85	LM449	0-40	SL683C	3-10
2N2906	0-19	2N4126	0-21	ACY30	0-58	BC171	0-18	BD529	0-80	CA3020A	1-80	LM450	0-40	SL684C	3-10
2N2906A	0-19	2N4289	0-20	ACY31	0-58	BC172	0-18	BD530	0-80	CA3028A	0-85	LM451	0-40	SL685C	3-10
2N2907	0-22	2N4290	0-95	AD143	0-68	BC177	0-28	BDY20	0-12	CA3035	1-36	LM452	0-40	SL686C	3-10
2N2907A	0-24	2N4920	1-10	AD149V	1-20	BC178	0-27	BF115	0-36	CA3046	0-70	LM453	0-40	SL687C	3-10
2N2924	0-20	2N4921	1-83	AD150	1-15	BC179	0-30	BF117	0-55	CA3048	2-11	LM454	0-40	SL688C	3-10
2N2925	0-20	2N4922	1-00	AD161	0-50	BC182	0-12	BF121	0-35	CA3052	1-62	LM455	0-40	SL689C	3-10
2N2926	0-20	2N4923	1-00	AD162	0-50	BY182L	0-12	BF123	0-35	CA3089E	1-96	LM456	0-40	SL690C	3-10
Green	0-12	2N5190	0-82	AD161	PR	BC183	0-12	BF125	0-35	CA3090Q	4-23	LM457	0-40	SL691C	3-10
Yellow	0-12	2N5191	0-86	AD162	1-15	BC183L	0-12	BF152	0-20	LM301A	0-48	OC28	0-75	SL692C	3-10

LM308	2-50	OC35	0-80
LM309K	1-88	OC42	0-50
LM380	1-10	OC45	0-20
LM381	2-20	OC71	0-20
LM382	2-20	OC72	0-25
LM382C	0-75	OC81	0-25
LM383	0-20	OC83	0-24
LM384	0-48	OPR12	0-55
LM385	0-48	R53	1-80
LM401	0-40	SL44A	1-80
LM402	0-40	SL610C	1-70
LM403	0-40	SL611C	1-70
LM404	0-40	SL612C	1-70
LM405	0-40	SL620C	2-80
LM406	0-40	SL621C	2-80
LM407	0-40	SL623	4-58
LM408	0-40	SL640C	3-10
LM409	0-40	SL641C	3-10
LM410	0-40	SL642C	3-10
LM411	0-40	SL643C	3-10
LM412	0-40	SL644C	3-10
LM413	0-40	SL645C	3-10
LM414	0-40	SL646C	3-10
LM415	0-40	SL647C	3-10
LM416	0-40	SL648C	3-10
LM417	0-40	SL649C	3-10
LM418	0-40	SL650C	3-10
LM419	0-40	SL651C	3-10
LM420	0-40	SL652C	3-10
LM421	0-40	SL653C	3-10
LM422	0		

INGENUITY UNLIMITED

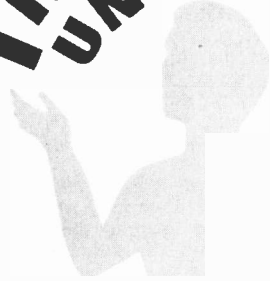

A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. Any idea published will be awarded payment according to its merits. Why not submit YOUR IDEA?

TUNNEL DIODE B.F.O. I.F. MARKER

CIRCUIT 1 shows a tunnel diode beat frequency oscillator, which was designed for reception of s.s.b. and c.w. in conjunction with a short-wave a.m. receiver. It also served as an i.f. marker by f.m. modulating the anode of the tunnel diode via a coupling capacitor.

By setting up a potential divider (R1/R2) across the main d.c. supply rail, a low impedance voltage of around 150mV can be supplied to the tunnel diode which will oscillate when the current rises to about 5mA. The frequency of oscillation is determined by the i.f. transformer which is chosen to suit the receiver i.f.

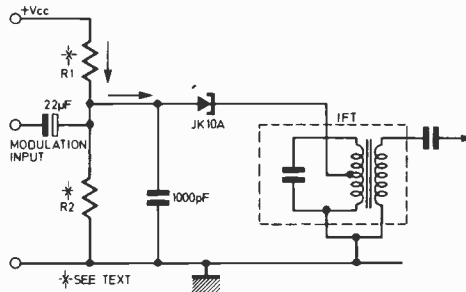


Fig. 1

A. Morter,
Norwich

ADDING CIRCUIT

THE adding circuit of Fig. 1 outputs a number of pulses equal to the binary number set up at the control inputs. If the output is connected to a conventional decimal counter with decoder and display a simple adding circuit can be constructed giving the sum of the binary numbers set up on the inputs.

The first binary number is set up on the control inputs and entered by pulsing the 7473 J-K flip-flop once with a bounce-free pulse. The next number can then be set up on the input, the 7473 pulsed and the sum will appear on the display of the associated counter.

The 7490 b.c.d. counter outputs are compared with the binary input numbers by the EXCLUSIVE OR gates G3 to G6 and the outputs of the latter are connected to a 4-input NOR gate made up from three 2-input NOR gates G7, G9 and G11 and two inverters G8 and G10.

When the 7490 outputs and the control inputs are equal the 4-input NOR gate gives a pulse which clears the 7473 and the 7490. When the 7473 output goes low the NAND gate cuts off the clock pulses to the 7490 and the output.

A 7400 can be used for the NAND gate G1 and the inverters G8, G10 and G2. A 7402 can be used for the NOR gates G7, G9 and G11 and a 7486 for the EXCLUSIVE OR gates G3 to G6.

G. W. J. van der Berg,
Pretoria, South Africa.


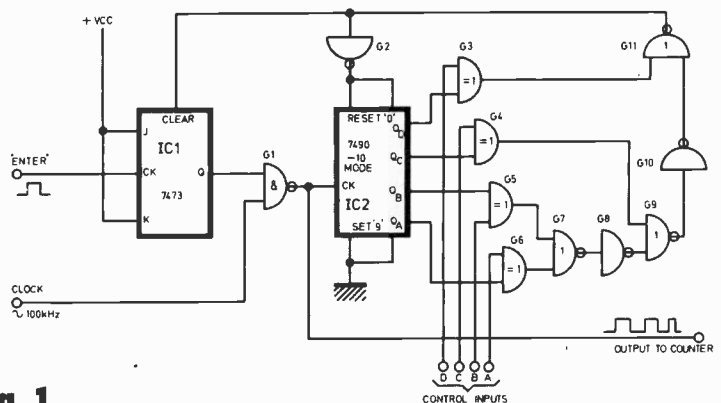


Fig. 1

Fig. 1

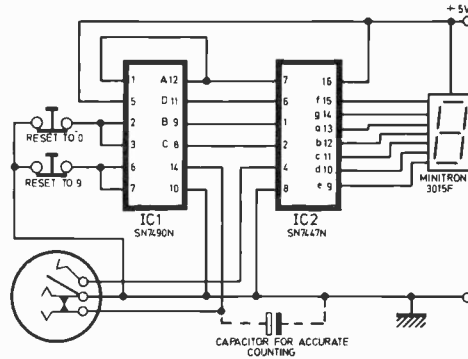

RANDOM NUMBER GENERATOR

A SIMPLE random number generator using TTL is shown in Fig. 1. This may be of interest to anyone experimenting in "psychokinesis" and associated e.s.p. phenomena.

A telephone dial is used to generate pulses which are fed to the A input of an SN7490 decade counter. This counts round from 0 to 9 and gives an output in b.c.d. which is fed to an SN7447 b.c.d.-to-seven segment decoder-driver. The latter drives a Minitron 3015F indicator.

Dial switch contact bounce ensures that the number of pulses counted by the circuit is always greater than the number dialled and completely random. Thus if a 10 is dialled something like 20 to 30 pulses are applied to the counter

which cycles and finally comes to rest on an effectively random figure.

If required, a pair of the normally open contacts in the dial can be used to blank the display whilst dialling. An "0" is applied to the blanking input of the SN7447 whilst the dial is moving. In addition, the ability to reset to "0" and "9" is useful in experimental work.

The circuit may be used as a "wide-range" dice, operated by dialling 10.

If it is required to generate a specific number of pulses then the insertion of a large capacitor, about 125µF, across the pulsing switch, should dispose of the effects of switch bounce and convert the circuit to normal counting.

N. J. C. Ray, Northampton.

DESOLDERING COMPONENTS

MANY constructors are faced with the problem of removing i.c.s from circuit boards for various reasons without doing damage to the associated printed circuit track and, of course, the component itself.

The following method has been used for some time to save the outlay on special de-soldering tools.

Strip the end from a length of scrap p.v.c. wire and dip it in Fry's Fluxite soldering paste (available in most hardware stores), apply the wire and a hot iron to the joint to be cleaned and the solder will be drawn up the wire by capillary action. With large blobs of solder it may require more than one application of clear wire and of course care should be exercised over the amount of heat applied to the joint.

After removal of the bulk of the solder the component may be lifted off without undue physical strain to the leads or thermal strain to the i.c.

Any residual flux should be removed from the component and the board to avoid corrosion problems.

J. Barvie-Smith,
Fareham, Hants.

ASTOUNDING OFFER

We are offering you the choice of two superb scientific pocket slim calculators (size 13.5cm x 6.75cm x 1.75cm) at a fantastic price.

DECIMO 2001

In addition to common functions it registers all functions appertaining to natural logs,

common logs, trigonometry in algebraic logic. A special feature is a memory exchange.

DECIMO 2001E

In addition to all the above features it has a 10 digit mantissa with 2 figure exponent, 2 figure display hyperbolics and functions on separate keys.

Functions

- 8 figure Mantissa
- Common Logs
- Natural Logs
- Trig. functions
- Memory
- Memory + -
- Memory Exchange
- Sign Change
- Reciprocals
- Square Roots
- Radians/Degrees
- Register Exchange
- π
- Algebraic Logic
- Floating point
- Positive feel
- 25hr battery time

£29.95

+ P. & P. + 8% VAT including carry case



Functions

- 10 figure Mantissa
- 2 figure Exponents
- 2 sign display
- Common Logs
- Natural Logs
- Trig. functions
- Memory
- Memory + -
- Memory Exchange
- Radians/Degrees
- Grads.
- Hyperbolics
- Register Exchange
- π
- Algebraic Logic
- Floating point
- Positive feel
- 25hr Battery time

£37.46

+ P. & P. + 8% VAT including carry case



To Dept. 10P, BARCLAY ELECTRONICS
Stanley House, 1115 Finchley Road, London, N. W. 11

Please send me (number) Mains adp. Add £3 to total
 Decimo (type) Total £ p.
 Name
 Address

2001E—£37.46 + 80p P. & P. + £3.05
 VAT
 Total £41.10 each

2001—£29.95 + 80p P. & P. + £2.44
 VAT
 Total £32.99 each

Now there's Doram, you need never wait for electronic components.

7-day service.
Buy the new Doram catalogue and you could have your components within 7 days of our receipt of your order. If you don't you'll have your money back and no questions asked.

What if you won't get it a tedious wait. Which goes on And on And on And on. You know just where you are with Doram.

Millions of components.
Doram is a brand new deal for serious amateurs. It's a complete door-to-door components service operated by mail order.

You buy the Doram yearly reference book for the price of a pint and then you order from it.

We're big enough to offer you stocks of millions of components on over 4,000 product lines.

And so confident of our service that if we can't supply the part you want within 7 days of placing your order we'll give you your money back immediately.

No-quibble guarantee.
It's just about impossible to buy a defective component from us without asking.

But even if the inevitable does happen - and you're unhappy - then we'll still make you happy quickly. Because so we offer a no-quibble replacement plan service.

And our guarantee is guaranteed by the fact that we belong to the largest electronics distribution group in Britain.

All branded goods.
All goods are genuine branded goods. Made by leading name manufacturers. Mullard, Philips, GEC, Ferranti, and many more.

Doram bring the amateur the sort of service only professionals have enjoyed before.

So don't delay. Use the coupon. Send today for your first Doram catalogue. It can make your life a whole lot easier for 25p that can't be had any other way.

I ENCLOSE 25p PLEASE SEND ME THE NEW DORAM CATALOGUE

Name _____
Address _____
Doram Electronics Limited
107 Park Road
Leeds LS12 2UF
Tel: 0532 455111

DORAM

Already we know of 22,000 people who like our ideas.

In October of last year we ran several ads announcing a brand-new service for amateur electronics enthusiasts.

The new service was called Doram.

And it promised the first-ever professional electronics service for amateurs.

We said that if you didn't get your order within seven days we'd refund your money. So you'd have no long wait.

We said that we'd only give you top quality, big-name components.

We said that we'd give you a no-quibble guarantee and replace any component which arrived faulty.

And finally we said that we'd offer you a choice of millions of components on over 4,000 product lines.

Buy the Doram catalogue for 25p, we said, and you'll get a fantastic electronic component mail

order service.

We were as good as our word.

And your letters of thanks flooded in. Thousands tried our service. Hundreds went out of their way to write congratulating us.

'Your storeman must be power assisted,' you said.

'I think you are a good firm and live up to your advertisement well,' you said.

'How nice to find a firm which actually stocks all the items in its catalogue,' you said.

And an awful lot more we'd blush to admit.

The Doram catalogue is still available, price 25p.

To encourage you to try us we'll give a £10 voucher to the first catalogue buyer out of the post bag on 30th June. And a £5 voucher to the next 19 new buyers.

Similarly, on 31st July, we'll give a £10 voucher to the first new

catalogue buyer. And a £5 voucher to the next 19 new buyers.

Use the coupon now while the offer lasts. Only these coupons are eligible, and all unsuccessful coupons from the June draw will also be entered for the July draw.

£10 VOUCHERS AND £5 VOUCHERS TO BE WON

I enclose 25p and look forward to receiving my Doram catalogue.

Doram Electronics Ltd., PO Box TR8, Wellington Road Industrial Estate, Leeds LS12 2UF.

Name _____

Address _____

PE/7/75

DORAM

TRANSFORMERS

SAFETY MAINS ISOLATING TRANSFORMERS
Prim. 120/240V. Sec 120/240V Centre Tapped and Screened

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P £
07	20	1 8	7.0 × 6.0 × 6.0	2.80 38
149	60	3 12	9.9 × 7.7 × 8.6	4.37 45
150	100	5 8	9.9 × 8.9 × 8.6	4.89 45
151	200	8 0	12.1 × 9.3 × 10.2	8.13 53
152	250	13 12	12.1 × 11.8 × 10.2	9.83 73
153	350	15 0	14.0 × 10.8 × 11.8	11.88 73
154	500	19 8	14.0 × 13.4 × 11.8	13.65 91
155	750	29 0	17.2 × 14.0 × 14.0	20.51 *
156	1000	38 0	17.2 × 16.6 × 14.0	29.15 *
157	1500	46 0	21.6 × 13.4 × 18.1	33.23 *
158	2000	60 0	21.6 × 15.3 × 18.1	37.07 *

AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P £
113	20	1 4	5.8 × 5.1 × 4.5	0-115-210-240	1.67 30
64	75	2 4	7.0 × 6.7 × 6.1	0-115-210-240	2.90 38
4	150	3 4	8.9 × 7.7 × 7.7	0-115-200-220-240	4.12 45
66	300	6 4	9.9 × 9.6 × 8.6	...	5.82 53
67	500	12 8	12.1 × 11.2 × 10.2	...	8.82 67
84	1000	19 8	14.0 × 13.4 × 14.3	...	13.68 91
93	1500	30 4	14.0 × 15.9 × 14.3	...	18.31 *
95	2000	32 0	17.2 × 16.6 × 14.0	...	24.20 *
73	3000	40 0	21.6 × 13.4 × 18.1	...	35.09 *

CASED AUTO TRANSFORMERS

240V mains lead input and U.S.A. 2-pin outlets, 20VA £3.13. P & P 38p. 500VA £10.45, P & P 80p. 1000VA £17.51, via B.R.S.

LOW VOLTAGE SERIES (ISOLATED)

Ref. No.	Amplitude	Weight lb oz	Size cm.	Secondary Windings	P & P £
111	0.5	0.25	4.8 × 2.9 × 3.5	0-12V at 0.25A × 2	1.35 23
213	1.0	0.5	6.1 × 5.8 × 4.8	0-12V at 0.5A × 2	1.74 30
71	2	1 1/2	7.0 × 6.4 × 6.1	0-12V at 1A × 2	2.29 38
18	4	2 1/2	8.3 × 7.7 × 7.0	0-12V at 2A × 2	2.86 38
70	6	3 1/2	8.9 × 8.0 × 7.7	0-12V at 3A × 2	4.12 45
108	8	4 5/8	9.9 × 8.9 × 8.6	0-12V at 4A × 2	4.56 45
72	10	5 6/8	9.9 × 9.6 × 8.6	0-12V at 5A × 2	5.14 53
116	12	6 6/12	9.9 × 10.2 × 8.6	0-12V at 6A × 2	5.52 53
17	16	8 8/12	12.1 × 9.9 × 10.2	0-12V at 8A × 2	7.26 60
115	20	10 11/8	14.0 × 9.6 × 11.8	0-12V at 10A × 2	10.39 73
187	30	15 15/8	14.0 × 12.1 × 11.8	0-12V at 15A × 2	13.59 85
226	60	30 32/0	17.2 × 15.3 × 14.0	0-12V at 30A × 2	16.83 *

30 VOLT RANGE

Ref. No.	Amplitude	Weight lb oz	Size cm.	Secondary Taps	P & P £
112	0.5	1 4	6.1 × 5.8 × 4.8	0-12-15-20-24-30V	1.81 30
79	1.0	2 4	7.0 × 6.7 × 6.1	...	2.40 38
3	2	3 4	8.3 × 7.7 × 7.0	...	3.49 38
20	3	4 8	9.9 × 8.3 × 8.6	...	4.55 45
21	4	6 4	9.9 × 9.6 × 8.6	...	5.13 53
51	5	6 12	12.1 × 8.6 × 10.2	...	6.41 53
117	6	8 0	12.1 × 9.3 × 10.2	...	7.15 60
88	8	12 0	12.1 × 11.8 × 10.2	...	9.90 67
89	10	13 12	14.0 × 10.2 × 11.8	...	9.87 73

50 VOLT RANGE

Ref. No.	Amplitude	Weight lb oz	Size cm.	Secondary Taps	P & P £
102	0.5	1 12	7.0 × 6.4 × 6.1	0-19-25-33-40-50V	2.58 30
103	1.0	2 12	8.3 × 7.4 × 7.0	...	3.38 38
104	2.0	5 8	7.9 × 8.9 × 8.6	...	4.68 45
105	3.0	6 12	9.9 × 10.2 × 8.6	...	5.81 53
106	4.0	10 0	12.1 × 10.5 × 10.2	...	7.60 67
107	6.0	12 0	14.0 × 10.2 × 11.8	...	12.10 67
118	8.0	18 0	14.0 × 12.7 × 11.8	...	12.98 85
119	10.0	25 0	17.2 × 12.7 × 14.0	...	16.99 *

60 VOLT RANGE

Ref. No.	Amplitude	Weight lb oz	Size cm.	Secondary Taps	P & P £
124	0.5	2 4	7.0 × 6.7 × 6.1	0-24-30-40-48-60V	2.33 38
126	1.0	3 4	8.9 × 7.7 × 7.7	...	3.41 38
127	2.0	6 4	9.9 × 9.6 × 8.6	...	5.08 45
125	3.0	8 12	12.1 × 9.9 × 10.2	...	7.52 60
123	4.0	13 12	12.1 × 11.8 × 10.2	...	8.75 67
40	5.0	12 0	14.0 × 10.2 × 11.8	...	9.75 73
120	6.0	15 8	14.0 × 12.1 × 11.8	...	11.30 85
121	8.0	25 0	14.0 × 14.7 × 11.8	...	15.00 *
122	10.0	25 0	17.2 × 12.7 × 14.0	...	17.52 *
189	12.0	29 0	17.2 × 14.0 × 14.0	...	19.98 *

MINIATURE TRANSFORMERS WITH SCREENS

Ref. No.	mA	Weight lb oz	Size cm.	Volts	P & P £
238	200	2	2.8 × 2.6 × 2.0	3.0-3	1.54 10
212	1A, 1A	1	6.1 × 5.8 × 4.8	0.6, 0.6	1.84 30
13	100	4	3.9 × 2.6 × 2.9	0.9-0.9	1.41 13
235	330, 330	4	4.8 × 2.9 × 3.5	0.9, 0.9	1.56 19
207	500, 500	1 00	6.1 × 5.4 × 4.8	0.8-9, 0.8-9	1.92 30
208	1A, 1A	1 12	7.0 × 6.4 × 6.1	0.8-9, 0.8-9	3.30 38
236	200, 200	4	4.8 × 2.9 × 3.5	0.15, 0.15	1.43 19
214	300, 300	1	6.1 × 5.8 × 4.8	0.20, 0.20	1.93 30
221	700 (d.c.)	1 8	7.0 × 6.1 × 6.1	20-12-0-12-20	2.17 38
206	1A, 1A	2	8.3 × 7.7 × 7.0	0-15-20, 0-15-20	3.46 38
203	500, 500	2	4.8 × 3.7 × 7.0	0-15-27, 0-15-27	3.00 38
204	1A, 1A	4	8.9 × 7.7 × 7.7	0-15-27, 0-15-27	3.85 38

*Carriage via B.R.S.

PLEASE ADD 25% FOR V.A.T. INCLUDING P. & P.

Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.

P.E. ORION

Complete Kit of semiconductors £10.95
High quality printed circuit £3.40

THIS GLASS FIBRE P.C.B. IS ROLLER TINNED AND SCREEN PRINTED WITH COMPONENT LOCATIONS.

FERRANTI semiconductors

BFS59	17p	ZTX304	24p	ZTX503	21p	ZS170	14p
BFS80	18p	ZTX310	14p	ZTX504	25p	ZS171	16p
BFS81	19p	ZTX311	15p	ZTX530	22p	ZS172	22p
BFS96	18p	ZTX312	17p	ZTX531	23p	ZS174	26p
BFS97	19p	ZTX313	20p	ZTX550	20p	ZS176	33p
BFS98	20p	ZTX314	25p	ZTX551	21p	ZS178	58p
ZTX107	14p	ZTX320	20p	2N3055	88p	ZS270	15p
ZTX108	12p	ZTX330	21p			ZS271	22p
ZTX109	14p	ZTX331	23p			ZS272	25p
ZTX212	19p	ZTX382	20p	* DIODES *		ZS274	29p
ZTX213	18p	ZTX383	19p	ZS120	17p	ZS275	38p
ZTX214	22p	ZTX384	21p	ZS122	22p	ZS278	61p
ZTX239	13p	ZTX450	20p	ZS123	29p		
ZTX300	15p	ZTX451	20p	ZS124	33p	* ZENERS *	
ZTX301	16p	ZTX500	16p	ZS140	30p	KS030A to	
ZTX302	19p	ZTX501	17p	ZS141	46p	KS180A	28p
ZTX303	21p	ZTX502	20p	ZS142	45p	BZV19 series	18p

MOTOROLA BD699 £1.27, BD700 £1.41, MJE2955 £1.50, MJE3055 87p.

SIGNETICS UA748CV operational amplifier 84p each.

FERRANTI ZN414, only £1.50 with circuits and data.

PE SCORPIO IGNITION SYSTEM. Complete kit of semiconductors £8.25.

PE JOANNA 77 ZTX108 £6.25, 183 ZS170 £18.30, ZN7404 40p, ZN7472 50p, ZN7473 72p each.


POSTAGE AND PACKING 10p per order. Orders over £3 post free.

All devices top grade, brand new, and to full manufacturers spec. We do not sell seconds or rejects. Send S.A.E. for our data sheet and price list. We can supply any Ferranti device to order. S.A.E. for quotation.

ALL PRICES INCLUDE 25% V.A.T.

DAVIAN ELECTRONICS

PO BOX 38, OLDHAM, LANCs, OL2 6XJ

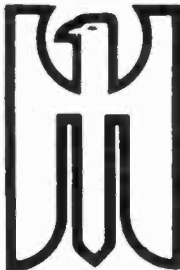

Phoenix Electronics (Solent) Ltd.

139-141 Havant Road
Drayton, Portsmouth, Hants
PO6 2AA

You already know us—get to know us better! Our catalogue is now only 20p—returnable on your first order.

Our prices on a wide range of semiconductors, i.c.'s and passive components include VAT, and, despite rising postal costs, carriage is only 20p, too!

THIS MONTH'S BARGAIN OFFER!

74TTL Digital logic kit—6 gates, 2 flip-flops, decoder, decade counter, 8-bit shift register + 5 D.I.L. sockets. Catalogue value £6.76. Bargain pack PEP/3A—£4.90.

Please send your catalogue — now!

Name _____

Address _____

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

ELECTRONIC IGNITION

Well-known for their "Sparkrite" capacitive discharge ignition systems, Electronics Design Associates, of Walsall, have extended the range recently by the addition of two new models, the Sparkrite G.T. (12V -ve and +ve earth) and the Sparkrite G.T.3 (12V -ve earth only).

Both these new models, which are a development of the Sparkrite Mk 2, incorporate a high voltage a.c. accessory outlet socket into which can be plugged the Sparkrite G.T. Fluorescent Inspection Light (extremely useful for emergency repairs at night) and the Sparkrite G.T. Xenon Dynamic Timing Light for those who wish to accurately "time" the engine to help obtain the best fuel consumption and performance. Also, both models can be used with all types of tachometer.

The G.T.3 version has two indicator lamps, one to tell you the system is wired in correctly and the other a static timing light which only lights if the unit is wired in correctly with the points open. Full details of the use of the latter are included with the comprehensive instructions accompanying each unit.

One other feature on the G.T.3 version is the inclusion of an automatic contact breaker cleaning circuit which burns oil and dirt from the surfaces of the points. Thus the life of the points is increased, pitting and burning being virtually eliminated.

The G.T.3, which is suitable for all vehicles with conventional coil/contact breaker ignition up to eight cylinders, was fitted to an Audi 100LS in need of an engine tune. Also the car battery was in a poor condition and there was a bad connection to one of the sparking plugs. Before fitting the unit, starting—especially in the early morning—was, needless to say, difficult, and occasionally needed a bump start. After starting, it was not unusual for the spark plug with the faulty lead to foul up for a while.

After fitting the unit, which took about half an hour, the difference was incredible. The car did not start first time, but when it did, at the third attempt, it was running smooth

and quiet and purred like a tiger. Response to the accelerator was instant. The car was immediately taken for a trial run and found to have a lively response to accelerator demands with greatly increased acceleration. If it can transform a neglected engine to a lively powerful vehicle, just think what it can do for a tuned engine!

The device has been fitted to the car for about 1,000 miles. No precise quantitative measurements have been recorded during this period as far as fuel consumption is concerned, but it has been noticed that the number of visits to the garage for petrol has decreased. Since fitting the G.T.3 no plug foul up has occurred and the car has always started at the first or second attempt.

For further details and price of the Sparkrite range of ignition systems and accessories, contact Electronics Design Associates, 82 Bath Street, Walsall, WS1 3DE.



G.T.3 Ignition from Electronics Design Associates

MODEL RAILWAY CONTROLLER

For those of our readers who are keen model railway enthusiasts, Routier (Electronic Engineers) Ltd., are producing a new power unit and controllers for gauge 00 and gauge N tracks.

Called the Brakeman Power-Pak and Brakeman Controllers, the units are of modular design, the controllers plugging in to the sides of the power units. A power unit can be used alone, with one or two controllers for gauge 00 or with up to six controllers for N gauge tracks.

Each controller has a forward, reverse and central off slide-lever control which governs the motion of one locomotive.

The Power-Pak is fitted with a double insulated transformer (no earth lead required) and an automatic resetting cut-out gives overload protection for all outputs. Two independent isolated output windings of 12V d.c. provide 1A on either side in addition to which a 16V a.c. output with two wander plugs is located at the front panel to provide power for points, motors, signals, etc.

Further information and prices for the Power-Pak and Controller can be obtained from Routier (Electronic Engineers) Ltd., Ion House, Sheep Lane, London, E8 4QS.

LOUDSPEAKER KIT

You don't have to be a good carpenter to build the Easikit loud-speaker kits from Studio Electronics.

The teak veneer or white cabinets are ready built and the kit consists of 4 drive units, 4 tweeters, 2 Declon foam fronts, cabinet wadding and sealant, and a p.c.b. crossover pack.

Capable of handling up to 20W, the frequency response of the enclosure is 30Hz to 20kHz ± 5 dB.

Full details and price list of the Easikit enclosures can be obtained from Studio Electronics Ltd., P.O. Box 18, Harlow, Essex, CM18 6SH.

COMPONENTS AND V.A.T.


How, precisely, the new V.A.T. rules will be interpreted is far from clear at the time of writing. But one thing is sure. Suppliers of components are in the front line and they have our sympathy. They face the wrath or indignation of their customers when they apply the higher rate of V.A.T. to all components (with perhaps those few unarguable exceptions). The suppliers are, of course, accountable to the tax authorities, so they cannot take chances. In short, when in doubt, the higher rate of 25 per cent is bound to be applied.

The individual customer has no option but to accept the increased price, though if he does feel there is a particular case for exemption from the higher rate he can take the matter up with his local V.A.T. office. This is the only advice we can offer our readers at this time. Some clarification of the situation must emerge before long, though it is doubtful whether much or any relief will be forthcoming.

Soldering irons (and other tools) remain at 8 per cent; so do electronic calculators and hearing aids. Multimeters should by our reckoning also remain as before, but any meter movement capable of being incorporated in radio or audio equipment is subject to the higher rate.

There are many other questionable items . . .

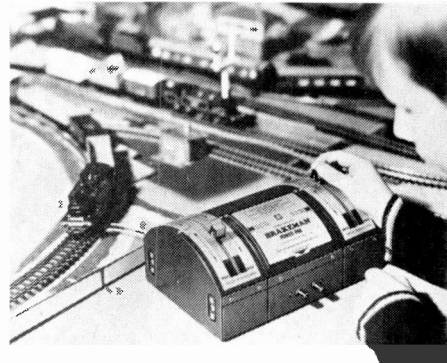Brakeman model railway power supply and controllers from Routier



In order to achieve independent operation for each note in the Piano it is necessary to provide a complete envelope generation system linked to each key on the keyboard. Each envelope shaper consists of a Touch Sensitive circuit followed by a Decay circuit. The latter is also designed to mix in the required pitch and to simulate the sustain pedal and damper action of a conventional piano.

TOUCH SENSITIVITY

The touch characteristics are shown in Fig. 3.1, together with the circuitry used to achieve the effect. The keyswitch is normally at ground potential until a note is played, such that the voltage across capacitor C_T is zero. On depression of a key, the switch leaves the ground busbar and starts to travel towards the rail (19 volts) busbar. This allows capacitor C_T to charge through the resistor R_T , such that the voltage on

A closer investigation of the attack pulse shows that two pulses do in fact occur. The first pulse is very small, and occurs at the moment when the keyswitch leaves the ground busbar, and is kept to a minimum by the choice of a high ratio for $R_T : R_I$. Later components in the Decay circuit ensure that this pulse does not get through to the preamplifiers. The values established for R_T are critical in obtaining maximum touch feel, and since they obviously take a fairly high current drain in the rest position, consumption has been minimised by the use of slightly higher values than optimum at the extreme ends of the keyboard. The attack trigger decays very quickly ($C_T R_I$) due to the necessarily low value of R_I . The attack level is proportional to the average speed of depression of the key over the full travel, which is a very similar situation to the final key velocity characteristic of a conventional piano since the latter is normally achieved by an even application of energy.

PE JOANNA PART 3

By A.J. BOOTHMAN B.Sc.

the positive plate of C_T follows curve A, according to the time constant $R_T C_T$ to the final touch level voltage on R_T of approximately 17 volts.

When the key completes its travel a 19 volt pulse is applied to C_T , which for a very short time raises the voltage at the junction of C_T and R_T by an amount equal to 19 volts minus the voltage across C_T at that time. This results in an output which follows curve B, over the range of normal key-travel times of between 40ms and 2ms, offering a variable attack voltage which is passed on to the Decay circuitry.


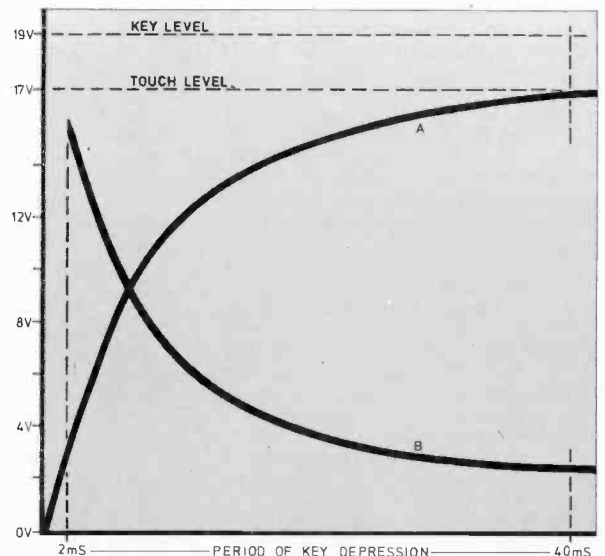
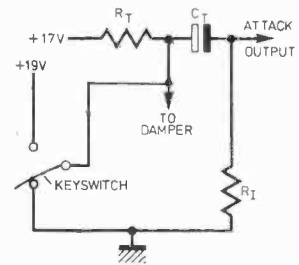


Fig. 3.1. Basic Touch circuitry and explanatory curves

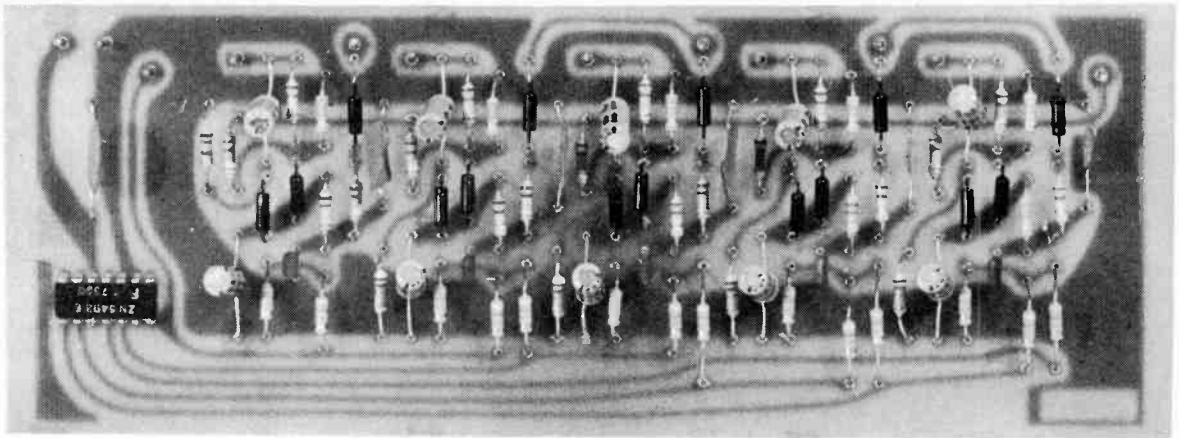

Complete Envelope Board assembly

DECAY CHARACTERISTIC

The Decay circuitry is shown in Fig. 3.2 together with the resulting characteristics in the various modes of operation. The circuit consists of a capacitor C_S , which stores the energy passed to it from the attack pulse, a Damper and Early Decay circuit, and a chopper circuit via which the envelope is modulated to introduce the pitch.

At the moment when the keyswitch reaches the rail busbar, as described in the previous section, the rail voltage is applied to the Damper circuit and the attack pulse appears at the isolating diode D_I in Fig. 3.2. Damper diode D_D normally holds the voltage across capacitor C_S to nearly zero via the damper resistor R_D , but the application of the rail voltage lifts the voltage on the cathode of D_D to approximately three volts. Thus as the attack pulse is applied to C_S through diode D_I the capacitor is allowed to charge to a voltage determined by the ratio of C_S to C_T , followed by a quick decay to a level of three volts plus the forward volt drop of diode D_D . This action is termed the "early decay", and whilst it is fast compared with the final decay action, it is long compared with the collapse of the attack pulse ($C_T R_I$), such that it is not influenced by the touch portion of the circuit which is isolated by diode D_I immediately after the attack voltage has appeared. The early decay characteristic emphasises the percussive nature of the instrument.

Assuming the key remains depressed the voltage across C_S will continue to decay, but at the much slower rate defined by resistors R_A and R_B . It will be shown later that the chopper transistor works on a 1 : 3 mark space ratio, such that for three quarters of the period the decay time is determined by R_A , and for the remaining quarter of the period it is defined by the sum of R_A and R_B . Different values of R_A and R_B are used for each octave to give a variation in decay time of from approximately 6 seconds to 3 seconds across the compass.

If the key is released before the voltage has fully decayed, the damper resistor R_D will determine the rate of final decay. This action will however be overridden if the sustain pedal is used since the voltage on the cathode of D_D is pulled up by the sustain voltage in a similar manner to the damper release action described above. Release of the sustain pedal brings back the $C_S R_D$ decay as before.

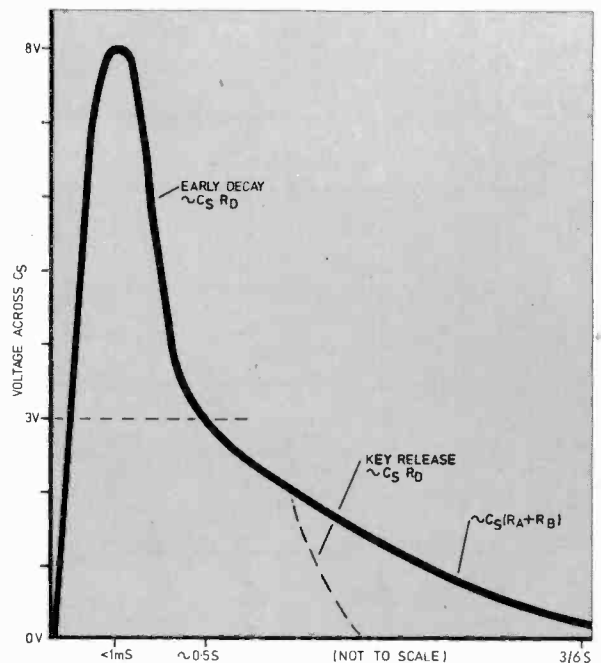
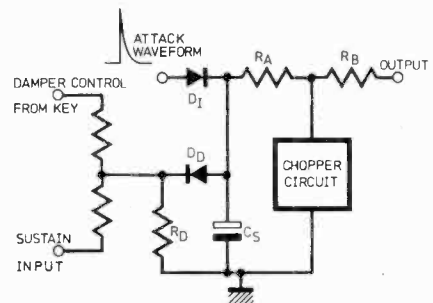


Fig. 3.2. Basic Decay circuit and curve

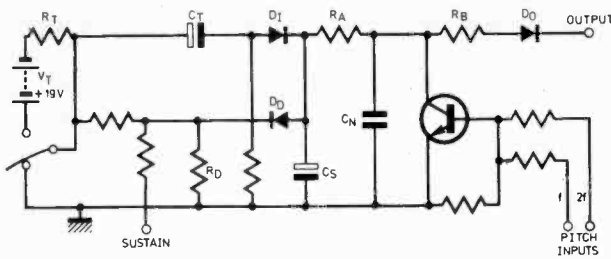


Fig. 3.3. Complete Envelope circuit

Fig. 3.4. Harmonic spectrum of basic waveform is shown on right

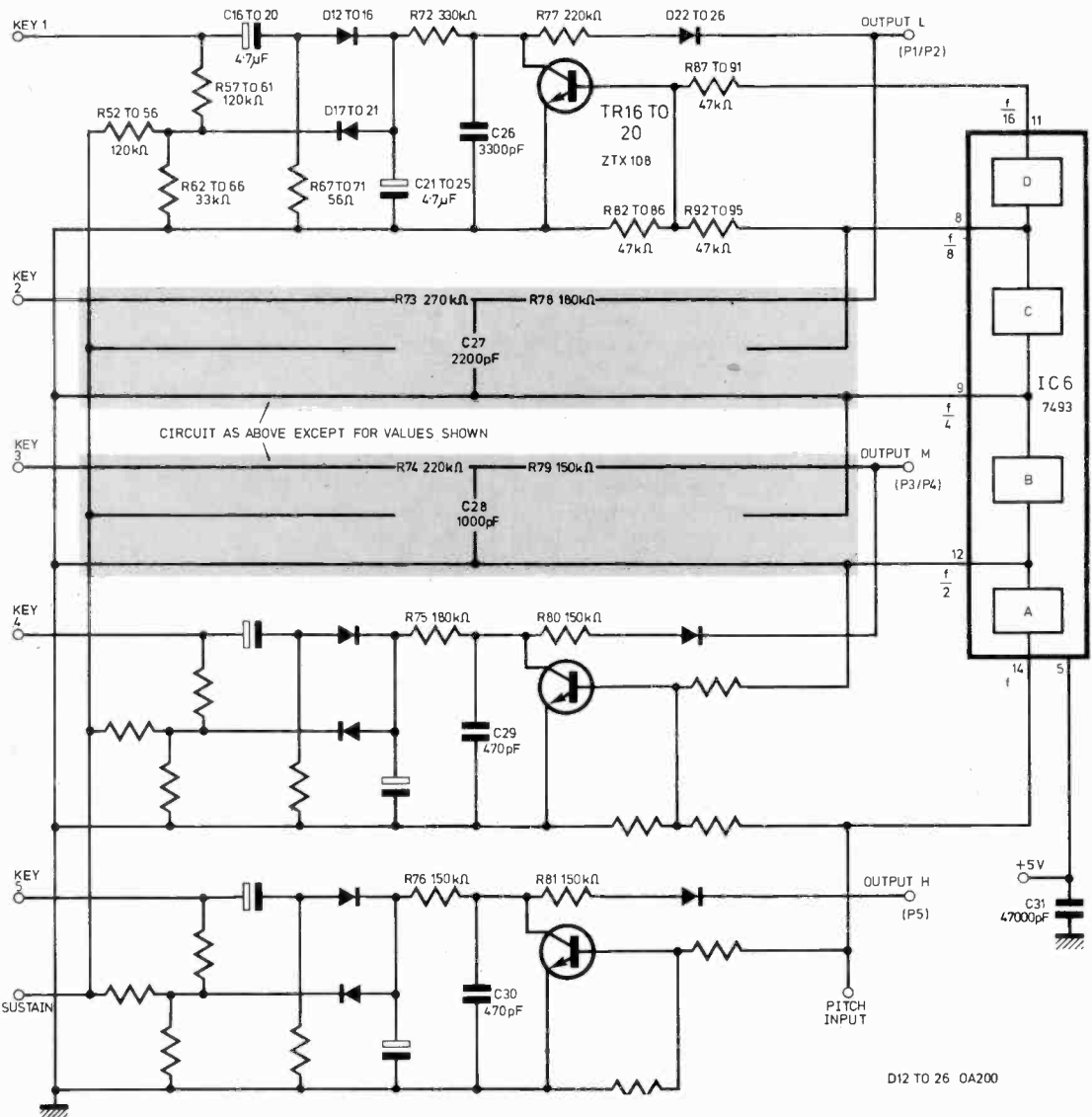
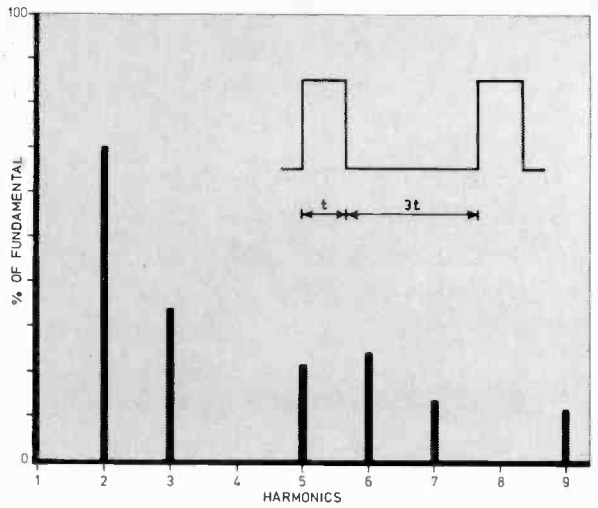


Fig. 3.5. Circuit of an Envelope Board

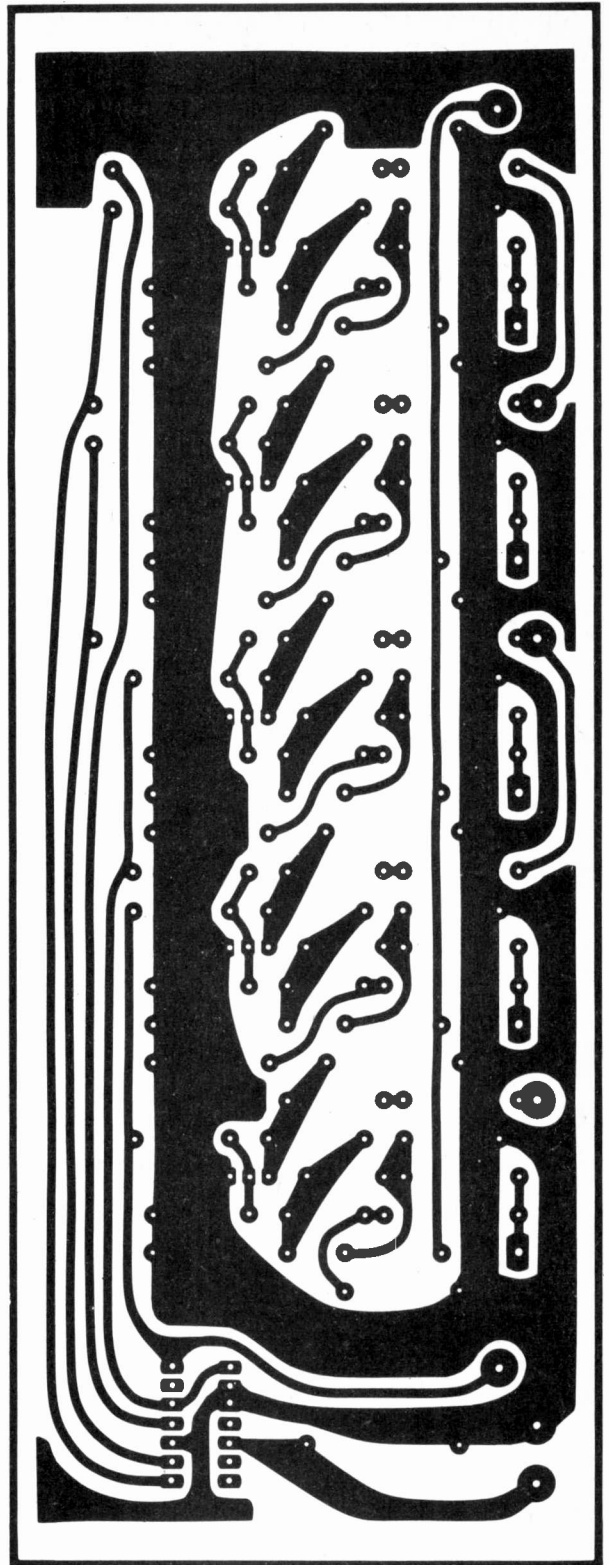
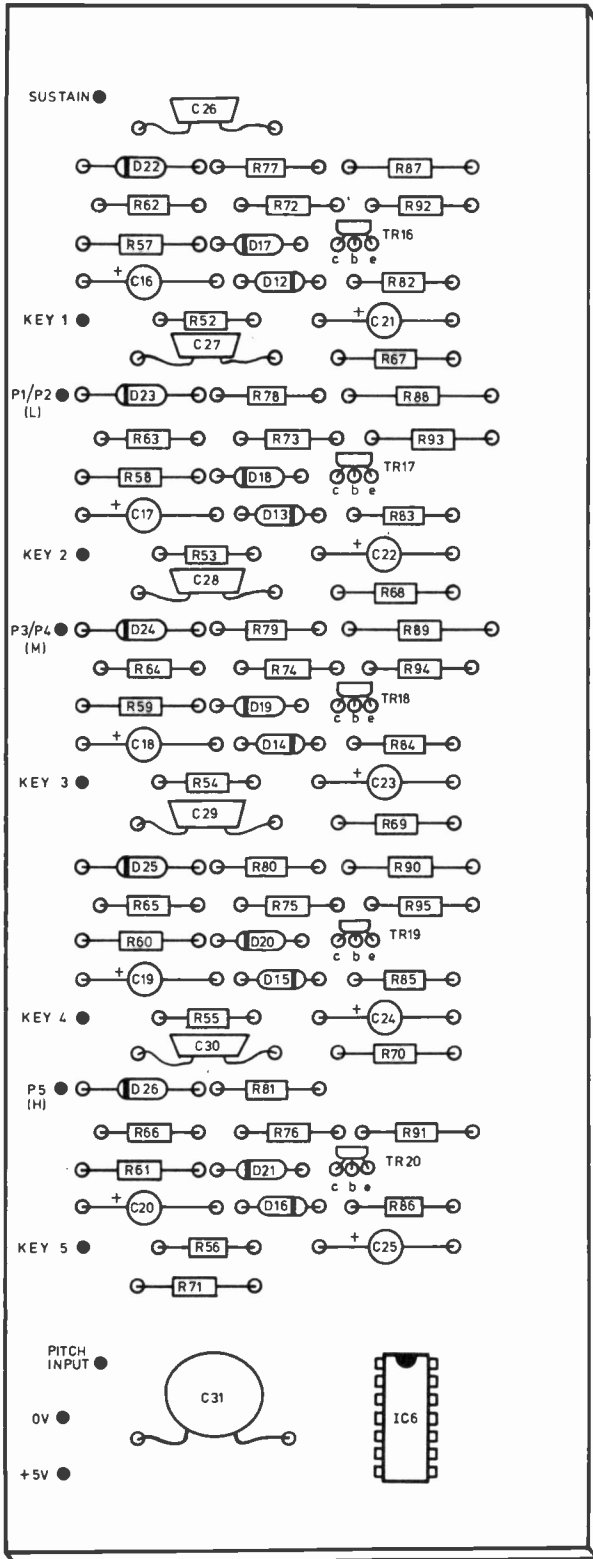


Fig. 3.6. Component layout and etching details for one Envelope Board

COMPONENTS . . .

ENVELOPE BOARD (12 REQUIRED)

Resistors

R52-61	120k Ω	R75	180k Ω
R62-66	33k Ω	R76	150k Ω
R67-71	56 Ω	R77	220k Ω
R72	330k Ω	R78	180k Ω
R73	270k Ω	R79-81	150k Ω
R74	220k Ω	R82-95	47k Ω

All $\frac{1}{2}$ watt 5% carbon

Capacitors

C16-20	4.7 μ F 25V	C28	1nF
C21-25	4.7 μ F 16V	C29-30	470pF
C26	3.3nF	C31	47nF
C27	2.2nF		

Diodes

D12-26 Cheap Silicon Diodes (e.g. 1S44, OA200 types)

Transistors

TR16-20 ZTX108

Integrated Circuit

IC6 7493

Miscellaneous

Terminal Pins—12 off.

Glass fibre printed circuit boards, and complete component kits, are available for this project from Clef Products, 31 Mountfield Road, Bramhall, Stockport, Cheshire SK7 1LY.

CHOPPER ACTION

The complete Envelope circuit is shown in Fig. 3.3, which also gives the chopper circuitry. The transistor is driven by two waveforms taken from the quad divider. The two basic frequencies are the fundamental and the second harmonic, both in the form of square waves. The resulting waveform on the collector of the transistor is shown in Fig. 3.4, together with its harmonic spectrum. This is a relatively easy waveform to handle in circuits which are inherently non-linear a more usual staircase type of waveform is completely unsuitable, producing a harmonic change over the period of the decay which is the inverse of the conventional piano tone. The fast edges of this waveform can be dangerous in their tendency to produce "beehive" breakthrough—i.e. a continuous background of every note in the instrument. Capacitor C_N slows the leading edge of the waveform to reduce this effect, and the output diode D_O also acts as a noise reducing element. Further beehive reduction is incorporated in the Voice circuits.

FREQUENCY DIVIDERS

The square waves to drive the chopper transistors are produced by a divide-by-sixteen counter, which has four outputs at half (A), one quarter (B), one eighth (C), and one sixteenth (D) of the input frequency. The divider input is obtained from the gate outputs on the Tone Generator Board, described earlier, and is fed into the circuit shown in Fig. 3.5. The input frequency is also used to produce the top octave pitch waveforms which are simple 1:1 square waves.

PRACTICAL ENVELOPE CIRCUIT

The Envelope circuits are grouped as five per board, together with one quad-divider. Each of these combinations copes with all octaves of one semitone across the keyboard, leading to 12 identical

Envelope Boards being required. The full circuitry for one board is shown in Fig. 3.5. The board contains five key inputs, one sustain input, and one pitch input. The outputs are grouped to cover the bottom two octaves, the middle two octaves, and the top octave, at separate output terminals. The board requires only one 5 volt supply, to power the divider.

ENVELOPE BOARD CONSTRUCTION

Each group of Envelope circuits is constructed on a printed circuit board 203 \times 76mm, the etching and drilling details for which are given in Fig. 3.6 together with component details.

To assemble the board the terminal pins should be fitted, followed by resistors, capacitors, diodes, transistors and integrated circuit. It is important that both the transistors and the integrated circuit should be inserted with the correct orientation.

DIODES

The author has used diodes in the prototype which can be described loosely as manufacturer's rejects, of silicon planar type in DO-7 encapsulation. To test the diodes a multimeter was used with 20k Ω /volt sensitivity (1k Ω range). Diodes were rejected where a movement of the needle was observed in the reverse polarity position, whilst the forward resistance was generally of the order of 12k Ω , although no specification was applied to this parameter. Occasionally a diode selected in this way gave some trouble if used in the output position (breakthrough) but the success rate was very high, after the diodes had passed the test. The forward resistance is measured when the negative lead of the multimeter is connected to the anode, and the positive lead to the cathode of the diode.

TESTING THE ENVELOPE BOARDS

The Envelope Boards can be tested one at a time using the jig described in earlier articles. Since the power supplies are unregulated (apart from the 5 volt logic supply) the warning is repeated to keep a check on the supply levels, particularly to the Tone Generator Board, whilst performing any partial check-out experiments.

NOTE: in Fig. 2.3 the 9V and 17V legends should be reversed.

Next month: Voice Filters and final circuitry

POINTS ARISING

ULTRASONIC DOPPLER SHIFT INTRUDER ALARM (March 1975)

The battery and S1 connections as shown in Fig. 5, page 208, should be reversed to agree with the circuit diagram of Fig. 2.


LIGHT PIPE (January 1975)

Parts list, page 31, Veroboard dimensions should be 24 strips by 37 holes.

THERMOMETER/CONTROLLER (December 1974)

In the component layout of Fig. 2 the circuit points 1 and 8 should be reversed together with their polarities. In the Veroboard cutting details there is no need for a cut at B5, Fig. 2. In Fig. 3, the switch positions 3 and 4 should be identified 0 to -100°C and 0 to $+100^{\circ}\text{C}$ respectively.

IN NEXT MONTH'S ISSUE...

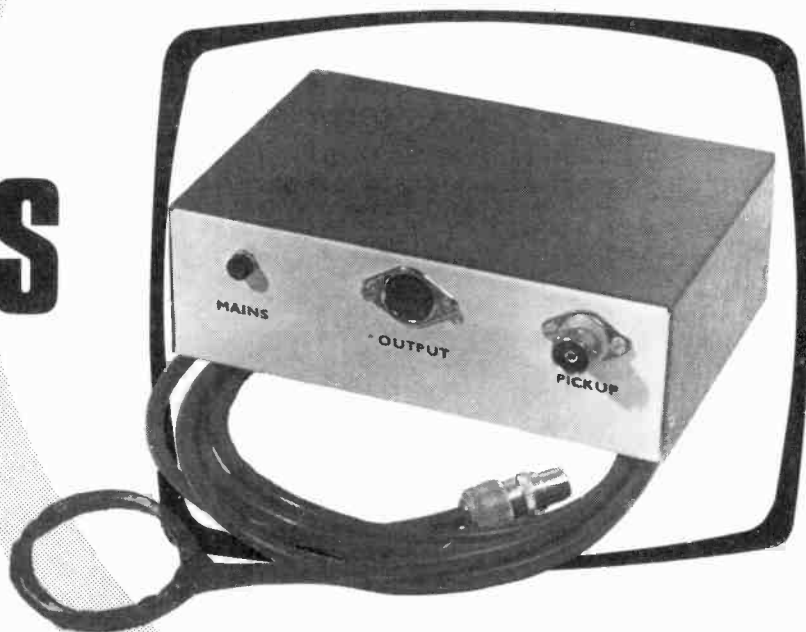

T.V. SOUND UNIT

A sound unit designed to detect the 6MHz radiation from a t.v. set i.f. strip and convert this into quality sound output suited to processing in the normal domestic hi-fi equipment, thus avoiding the hum and narrow bandwidth problems normally associated with t.v. sets

8-Channel Logic Trace Multiplier

Converts normal single-beam oscilloscope into an 8-channel unit for logic waveform examination; or a double-beam unit into a 9-beam instrument capable of displaying one channel of analogue data and eight of logic



DIGITAL CLOCK

An electronic clock using proprietary components to achieve a simple and sensible design suited to use on 50 or 60Hz mains as either a 12 or a 24-hour unit with equal facility

PRACTICAL
ELECTRONICS

AUGUST ISSUE ON SALE JULY 17, 1975 — PRICE 30p

PLACE A FIRM ORDER WITH YOUR NEWSAGENT TO AVOID DISAPPOINTMENT

SYMBIOSIS...

A composition for the

PE

MINISONIC

By M. POINTON

B. Mus.



This is the second and final part for setting up the Minisonic for performing the specially prepared composition "Symbiosis".

SEQUENCE I TO O

This is the central section of the piece and the one requiring the most careful setting up. The pitches (which appear on the score as thick horizontal lines tapered at the end) are crucial to the effect produced.

Firstly the keyboard must have its Span set to give an equal-tempered scale (i.e. 12 equal divisions of pitch from one note to its counterpart an octave higher). Set KBD CON Span to 5, adjust KBD CON Tune to a comfortable mid-range level (about 6 with VCO2 Freq at 6.2). Set the note a at Concert A pitch (440Hz) using some external musical instrument. When you have this, insert a spare 3.5mm jack into the keyboard over-ride plug of VCO1. Now tune VCO1 to an octave below the note on VCO2. This is now your standard reference frequency. By gradually adjusting KBD CON Tune and Span you will eventually reach a perfect octave span. This will take quite a long time to achieve, so do not be dismayed if things do not go well right away. Once the Span is fixed the niggling problems are over. Make quite sure that you do not accidentally move KBD CON Span whilst working on this sequence or all the blood, sweat and tears will have to be re-lived.

Remove the jack plug from VCO1 keyboard over-ride and re-tune the oscillator to an octave below VCO2. The two v.c.o.s will track each other quite faithfully over a large part of the keyboard's range. The rest of the settings can now be made quite quickly. For controls:

VCA1 and 2	Level 11
ES1	Attack 2
	Decay 3.8
ES2	Attack 1
	Decay 4
VCF	Level 11
	Q 9
	Freq 7.5
CE	Fully clockwise
VCOs, KBD CON	as above

For patch-cords:

3D to 5C; 3C to 3F

As you will see from the score there are 15 repetitions, lasting eight seconds each, of a simple

two-note figure along the bottom line. The first (A) lasts for two seconds, the second (A#) lasts for six seconds. As you play these two notes, touch the keyboard for only about half a second to allow the resultant harmonics to sing through. With the control settings given the A# will last about nine seconds, so the continuity of line is built in.

ADDING REVERBERATION

The last refinement concerns the tape machine. Arrange your input and output levels on both the mixer and the stereo machine (track one) so that a small touch of tape reverberation is added to the sound. Too much will muddy the signal, too little will take away its resonance. Make two separate recordings of this sequence of events; the second one will be used again towards the end of the piece.

At letter L you are free to choose which notes you play provided: (a) they begin at about one per second and accelerate to no more than three per second, and (b) they do not wander very far in pitch from the four or five notes immediately above A#. At letter M you increase the amount of tape feedback until the sounds you are making distort into a general mess of reverberant tape noise; this reaches its peak after four seconds, and over the next ten seconds ease the feedback down to a level where the sound dies away of its own accord.

Having laid down one line on track one, change over to record on track two and set up the synthesiser for the line of thick horizontal strokes and the wedge-shapes above them. This musical line is dealt with in a similar way to the material just completed, although the control settings and patches are different—except, of course, for KBD CON Span and VCO2. For controls:

VCA1	Level 11
VCA2	Level 1
ES1	Attack 1; Decay 3.2
ES2	Attack 1; Decay 1
VCO1	Level 1
VCF	Level 11
	Q 11
	Freq 6.8
CE	Fully Clockwise
N	Level 3

For patch-cords:

3C to 3F; 3A to 3E; 3D to 1A

Set the previously recorded channel running. As soon as you have heard the first two notes of the

recorded sequence, add the next two notes (c' and c#') in equal time—i.e. two seconds after the prerecorded second note and lasting two and six seconds respectively meanwhile increasing the level on the mixer from silence to a comfortable maximum over 24 seconds. When you arrive at letter L try to follow the speed of the notes in the recorded channel without wandering too far in pitch from c#' and again, at M increase the reverberation as before until it overwhelms the system and then is allowed to die away.

The final overlay does not require tape reverberation, so feed both the recorded channels through the mixer into the second tape machine.

IMPROVISATION

The score at this point allows for some freedom of melodic line; for 40 seconds you improvise on the notes f, a, a#, c#, and d#, and for 48 further seconds the notes f#, g#, a#, c#, d#. At letter L you stop playing until letter N where two slow notes appear amidst the aftermath of the tape reverberation—g# followed by g. The settings for this line of music are:

VCO1 and 2	As previous setting
KBD CON	Ditto
ES1	Attack 2.5; Delay 4.5
CE	Fully clockwise
VCF	Level 11; Q 11; Freq 3.5

For patch-cords: 3D to 1A; 3C to 3F; 5D to 3E.
At letter O the tape is cut.

The final triangular block in this sequence is a cataclysmic slam of white noise which is tape reverberated and allowed to die at its own rate, recorded separately and spliced on to the previous recording. The control setting is:

VCA1	Level 11
VCO1	Level 1
ES1	Attack 1; Decay 4
N	Level 10

For patch-cord: 3A to 1A.

FINAL SEQUENCE: P TO END

Between P and R three separate kinds of sounds are heard in counterpoint. The first to appear (small black arrowheads in the score) is a sequence of band-pass filtered white noise; the second (shown as a wavy line) is a modulated and filtered VCO signal; the third (small egg shapes) is a short-lived "Wah-Wah" sound.

The recording procedure is identical to that used in Sequence D to I but, of course, this time you need to make three separate control settings and patches. If you are to save time in producing this Sequence then pretty precise timing will be required between P and S; the arrowhead sign appears consistently between P and Q, once only between Q and R, and very exposed between R and S—and all this over almost two minutes' duration. Similarly the occurrence of the other two symbols which appear at various times after Q.

The KBD CON Span is not critical in this Sequence since the randomness works much in the same way as the counterpoint beginning at D. However, the egg-shaped symbols must be kept around mid-range and the overall speed of events is slower than before.

Begin by recording, with the aid of a watch with a seconds hand, the arrowheads at a fairly high dynamic level throughout; the lowering of dynamic at Q et seq. can be effected on the final dub using a mixer control. The single arrowhead between Q and R will appear at approximately 71 seconds from the beginning. Record

the whole of this line of music on your *second* tape machine. "Arrowhead" control settings are:

VCA1	Level 11
ES1	Attack 1; Decay 2.5
VCO1 and 2	Level 1
N	Level 9
VCF	Level 11
	Q 11
	Freq 7
KBD CON	Tune 10; Span 11

For patch-cords:

3D to 1A; 3A to 3E; 2E to 3F

Next play back the recording from the second tape machine through the mixer on to track one of the stereo tape machine along with the egg-shaped symbols. Again you will need to "watch the clock". Do not forget to let the tape run well over the 113 seconds required before switching off otherwise unwanted clicks will occur in the finished sequence.

"Egg-shaped" control settings:

VCA1 and 2	Level 1
ES1	Attack 2; Decay 2.5
VCO1	Level 10; Freq 7
VCO2	Level 10; Freq 6.5
VCF	Level 11
	Q 11
	Freq 4
CE	Fully clockwise
KBD CON	Tune 4; Span 5

For patch-cords:

3D to 1C; 1D to 3E to 5D; 3F to 3C

The next overlay will be recorded on to track two of the stereo tape machine. Your second tape machine has the tape made earlier of the eight-second note patterns in Sequence I to P. This will be fed in at R, rather quietly, just after you have finished your last bit of stylus work on the wavy line. For "Wavy Line" controls:

VCA1 and 2	Level 1
ES1	Attack 1; Decay 2.3
VCO1	Level 11; Freq 4.5
VCO2	Level 11; Freq 7
VCF	Level 11
	Q 11
	Freq 4
CE	Fully clockwise
RMOD	Level 10
KBD CON	Tune 6.5; Span 11

Patch-cords:

F1 (over-ride plug); 3E to 4D; 3C to 3F;
4E to 5D; 3D to 1C

VCO1 frequency may need slight adjustment in order to give this sound a distinctive stuttering effect.

The last three surges of white noise are dealt with manually by means of the VCF frequency control and then spliced on to the rest of the work. For white sound controls:

N	Level 9
VCF	Level 11
	Q1
	Freq as required.

All other units level 1.

Patch-cords:

3D to 1C; 3A to 3E

And that completes "Symbiosis".

NEW DEVICES ... APPLICATIONS

SOLID-STATE POWER CONTROL

THE CONTROL of power to fairly large unity power factor loads, that is loads which do not normally include inductive and capacitive items, such as electrode water heaters and radiant heating processes, has always been difficult for two basic reasons.

The already well-known phase control technique which is used for power control in resistive loads, as shown in Fig. 1, is just out of the question since it causes disturbances in the supply waveform as in Fig. 2.

Such disturbances can be avoided by using zero-crossover switching, Fig. 3, when the power is controlled by allowing more or less cycles of the supply to pass to the load. Switching of the selected cycles occurs as the voltage (or current) passes through the zero condition, thus avoiding r.f.i. problems.

However, if a wide area of control is to be achieved as from zero to 100 per cent with a three-phase supply, then a new problem appears; lamp flicker can be induced because of subharmonics met in the various combinations of switching. Equally, conduction sequences can introduce periods of d.c. in the load which, for electrode water heaters, would cause electrolysis.




Two workers at the University of Nottingham, R. M. Davis and B. R. Downing, have developed a solid state system for control of power under such circumstances which avoids the problems.

SWITCHING SEQUENCE

Taking the case of three phase resistive loads and in particular an electrode water heater as an example, their method can be described with reference to Figs. 4 and 5. With the load in a star-delta configuration and the constraint that the triacs be switched only at zero crossing, a switching sequence was developed.

With a switching sequence which repeated itself every three cycles the number of different permutations in which the three triacs could be switched can be shown to be in excess of 2×10^6 but this number includes many identical power levels and many sequences which would produce a d.c. component.

A computer selection programme was utilised to remove these problem sources altogether, together with those other sequences which might produce 16Hz or 25Hz lamp flicker, and a final set of 24 acceptable power levels were produced.

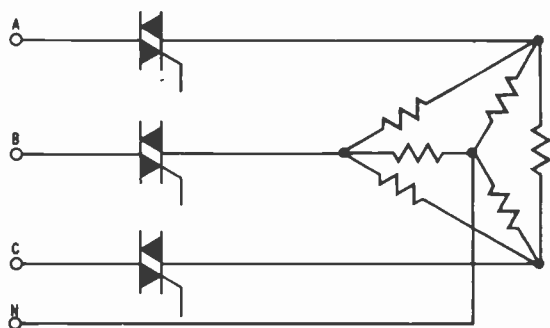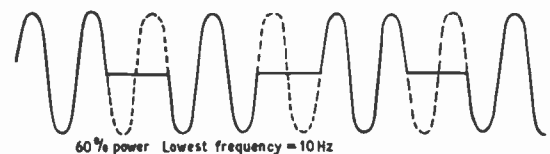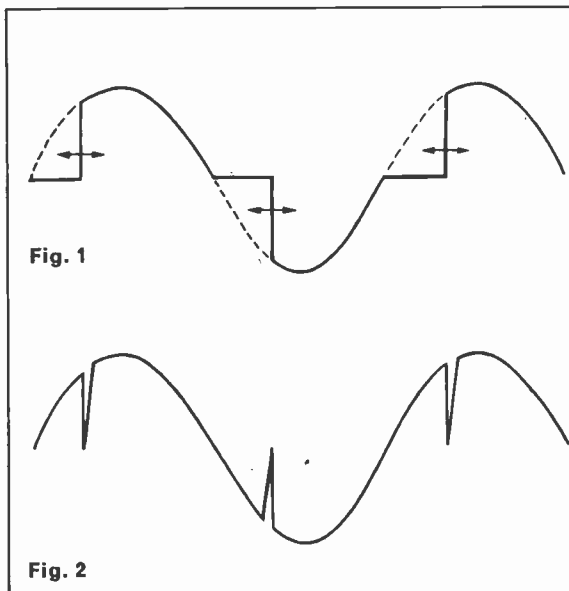

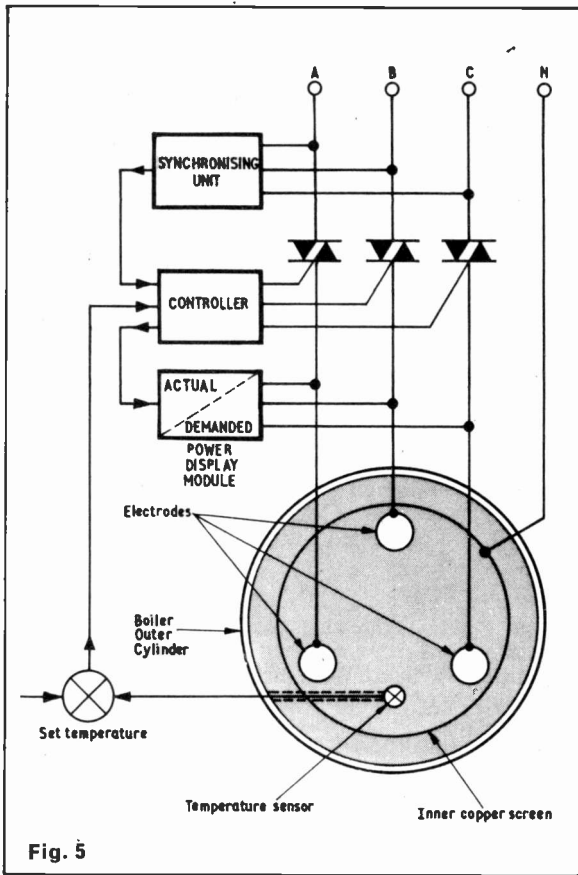


Fig. 5

From these some 19 were selected to give an even 0 to 100 per cent power control.

Currently a 75kW version of the controller is in use with an electrode water heater. The temperature of the water is continuously monitored and fed back to the controller to provide temperature maintenance to a required level. The system is cheap, simple and compact, and other areas of application will include such items as paint-drying ovens, three-phase immersion heaters, ovens and so on.

Further information can be obtained from **Electrical Engineering & Electronics Group, NRDC, Kingsgate House, 66-74 Victoria Street, London, SW1E 6SL.**

ULTRASONIC I.C.

Remote control of T.V. sets, particularly colour sets, is a subject which has gained particular interest in manufacturing circles for some time now. Various methods of linking the hand-held control unit to the set have been proposed ranging from the obvious hard-wired style through to infra-red and ultrasonic linking.

Each method has associated advantages and disadvantages but obviously any solution using hard wiring is out. Of the others, a great deal depends on the sound or light characteristics of the domestic environ.

After much deliberation and research, ITT Semiconductors have come up with an integrated circuit ultrasonic solution to the problem using two basic chips, a transmitter and a receiver. These are available in 15-channel and a 30-channel form as pairs and can be used to effect both discrete switching functions

for channel changing, and analogue (gradual) adjustments to such parameters as volume, colour and brilliance.

The new devices use discrete frequency steps in the 30kHz to 45kHz band and these are crystal-controlled at both transmitter and receiver to avoid incorrect triggering. Cost is envisaged to be in the region of £10/pair for 15 channels and £15/pair for the 30 channel. The final cost to the set user would of course be more.

Further details from **ITT Semiconductors, Footscray, Sidcup, Kent.**

SINGLE IC TV SOUND CHANNEL

The TDA 1190 is a new integrated circuit from SGS-ATES which, with the addition of a few external components, forms a complete TV sound channel taking the sound i.f. from the tuner and producing up to 4.2W into a 16 ohm load.

The input limiting voltage of the i.f. section is only 30µV and the electrical characteristics remain constant over the range 4.5 to 6MHz making the i.c. suitable for use with all television standards.

A single resistor is used to set the a.f. amplifier gain and a single capacitor sets the upper cut-off frequency. There is d.c. volume control which can be achieved by connecting a variable resistor between an i.c. pin and earth. This gives a control range of typically 90dB.

Supply voltage can be anywhere between 9 and 28V. Further details from **SGS-ATES, Planar House, Walton Street, Aylesbury, Bucks.**

QUAD 80-BIT STATIC SHIFT REGISTER

Another new i.c. from SGS-ATES is the M142, a quad, 80-bit static shift register. Most semiconductor manufacturers produce quad 80-bit MOS devices, but the M142 is unusual in that it only requires a single 5V supply line. This completely eliminates the need for interface circuits when using the device with TTL.

Each of the four 80-bit shift registers has an independent input, output and recirculate control, though the single clock line is common to all four registers.

The data can be shifted into or out of the registers at anything up to 3MHz. Total power dissipation is a mere 125mW.

PE

A VOLUME OF PRACTICAL KNOW-HOW

... can be made using these new-look self binders for PRACTICAL ELECTRONICS to become your most valuable source of reference. With the Easi-Binder current copies can be inserted as they are received, without waiting for the completion of twelve issues.

They are attractively made with the title blocked in gold on the spine with the current (or last) volume number and year. For any previous volume numbers, please advise year and volume and a separate set of gold transfer figures will be supplied.

At **£1.90** (including VAT and postage), they are obtainable from:

**Post Sales Department, IPC Magazines Ltd.
Carlton House, 66-68 Great Queen Street
London, W.C.2**

I enclose P.O./cheque value for binders at £1.90 each for **Practical Electronics Vol. No's.**

Name.....

Address.....


.....

Date.....

PE

SINE/SQUARE WAVE SIGNAL GENERATOR

By J. SMITH

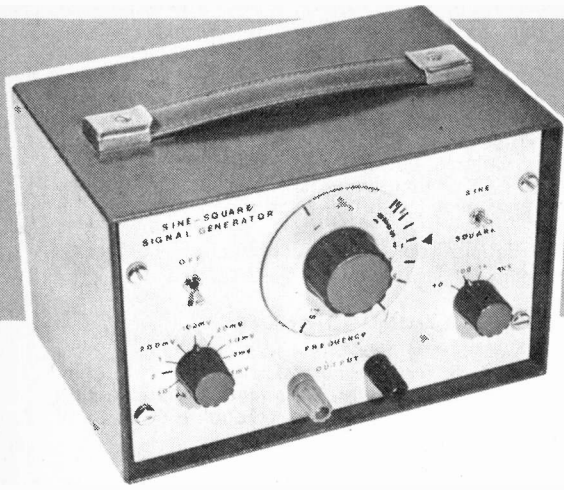

A GENERAL purpose oscillator is a useful item of test gear in any electronic workshop. The instrument described in this article is intended for audio, digital and general purpose use. The design employs simple components which are readily available from component suppliers. Output frequency is continuously variable over four decade ranges from 10Hz to 100kHz and the output signal, which is 10V peak-to-peak, can be attenuated with a switched attenuator down to 1mV.

The output will drive loads down to 600Ω on the 1 to 10mV ranges and 100kΩ on the ranges above 20mV.

The oscillator requires a positive and a negative 15V supply. Readers having suitable external power supplies can economise by using such a source. However, the full design incorporates a suitable power supply since we believe that most people will prefer a compact, self-contained instrument.

OSCILLATOR

Fig. 1 shows the sine oscillator circuit. In this circuit an SN 72709 integrated circuit IC1 is wired as a thermistor-stabilised Wein Bridge oscillator, the main requirements of which are to produce positive feedback with unity gain. In this instance the Wein Bridge supplies the positive feedback required, but in doing so attenuates by 1/3. Therefore, to sustain oscillation the resistor ratio R5 to R3 achieves the required gain of


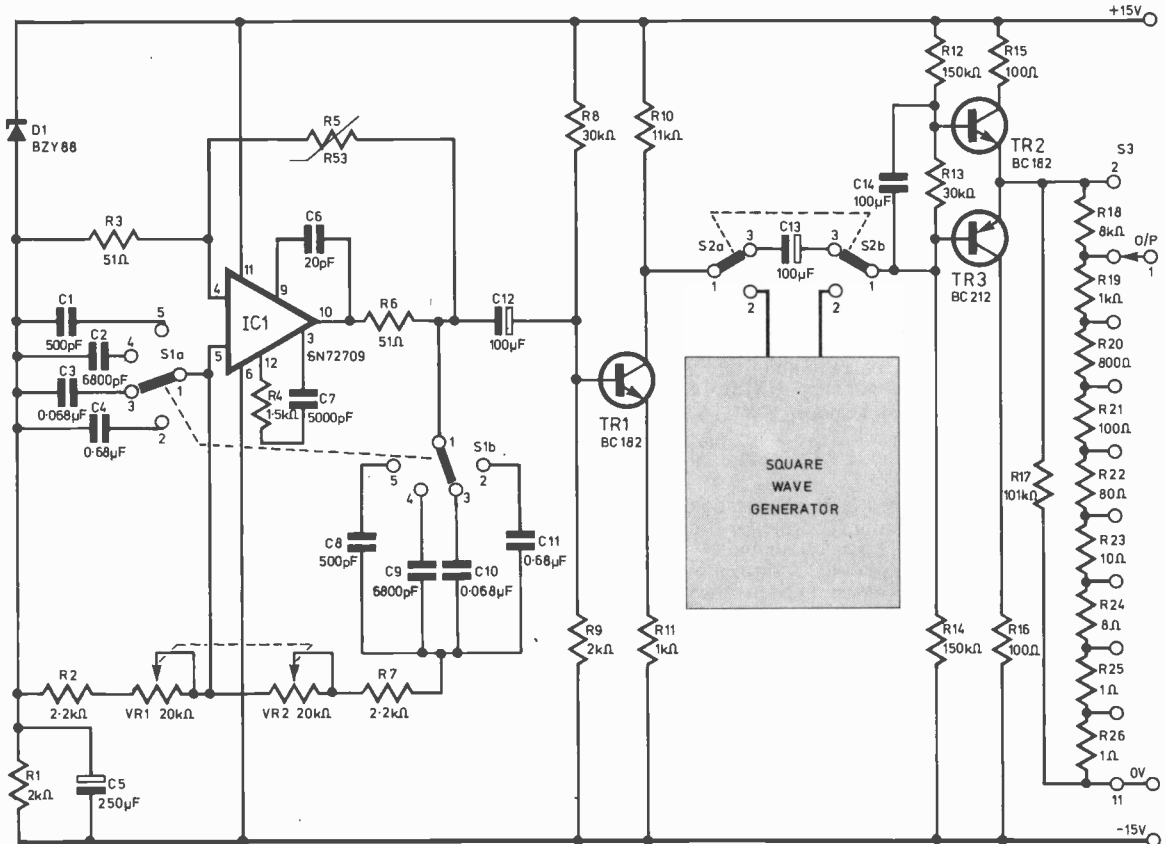


Fig. 1. Circuit diagram of the sinewave generator and output amplifier/attenuator

Fig. 2. Double-rail power supply for the complete generator

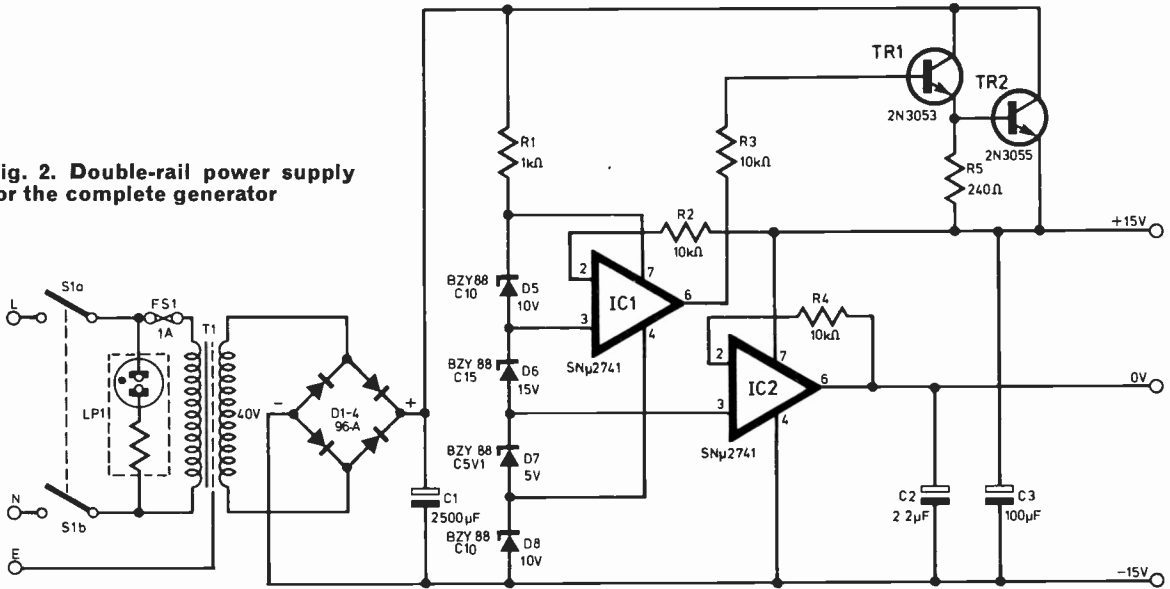

3; here R5 is a thermistor. The circuit incorporates frequency compensating components C7, C6 and R4 to form a basic stable amplifier.

The stabilisation thermistor, R5, controls the output voltage level: an increase in voltage will heat up the thermistor, so decreasing its resistance, and reducing the gain. Conversely, a fall in output voltage reduces the power dissipated in R5, so it cools down, and its resistance increases. This arrangement stabilises the output level of the oscillator. This output feeds the positive feedback loop via the frequency selective components C8 to C11 and VR2 to pin 5 of IC1.

The product of capacitance *C* and resistance *R* determines the frequency of oscillator output according to the formula:

$$\text{Frequency} = \frac{1}{2\pi CR}$$

Since in this oscillator both the series resistance R7 and the variable resistance VR2 affect the frequency, we must substitute (VR2+R7) for *R* in the formula, so that in this instance:

$$\text{Frequency} = \frac{1}{2\pi C (VR2 + R7)}$$

Because of its limited slew rate the 72709 operational amplifier IC1 will produce a distorted large signal output at high frequencies, so the output swing is limited to a few volts. The Zener chain, R1, D1, ensures that the swing is either side of earth potential.

Coupling the limited output from IC1 to a transistor amplifier TR1 through capacitor C12 produces a high signal level. The amplified oscillator signal appears across R10, the collector load of TR1. This signal passes from the amplifier via switch S2 and C13 to the output driver circuit TR2/TR3.

OUTPUT ATTENUATION

The square wave generator is an add-on circuit which one can omit readily by coupling directly through C13, so leaving out the sine/square switch S2. TR2 and TR3 feed the output signal to a simple attenuator circuit, which gives off-load peak voltages from 10V down to 1mV in a 10, 2, 1-sequence.

Loads down to 600Ω on the 1 to 10mV ranges and loads of 100kΩ or more on the 20mV to 10V ranges will have little effect on these output voltages.

Readers who have suitably stable power supplies to attach to it will find that the circuit shown in Fig. 1 makes an extremely simple and useful instrument in its own right. Anyone requiring more accurate control of the output voltage can easily fit a meter circuit measuring the 10V peak across R17. In such an arrangement varying R10 or R11 by a small amount before making each measurement will adjust the output voltage to a pre-set level. We have not included such an arrangement since the instrument is stable enough for the majority of applications.

POWER SUPPLY

As many readers who decide to construct this instrument will require a self-contained unit, a suitable stable power supply is given. Fig. 2 shows the circuit diagram for this supply.

In this circuit 40V output transformer T1 together with diode bridge D1-D4 and the smoothing capacitor C1 provide a roughly smoothed output of 55V. This voltage feeds the Zener chain D5 to D8 through resistor R1 to provide the reference voltages shown on the circuit diagram.

The roughly smoothed d.c. also passes to a series regulator TR2. Primarily this section of the instrument provides a 30V stabilised supply. IC2 samples the output voltage through R2 and compares it with a reference voltage of 30V developed at the junction of D5 and D6. The error signal passes via R3 to amplifier TR1 which drives the series regulator TR2, thus forming a conventional 30V stabilised supply. IC2 changes the 30V supply into the ±15V supply required to drive the oscillator.

Because IC3 will only function correctly with the balanced load of the oscillator, this arrangement is quite unsuitable as a general purpose power supply and on no account should be used as such.

The two circuits shown in Figs. 1 and 2 together make a very compact instrument for constructors, who do not wish to incorporate the square wave circuits.

COMPONENTS . . .

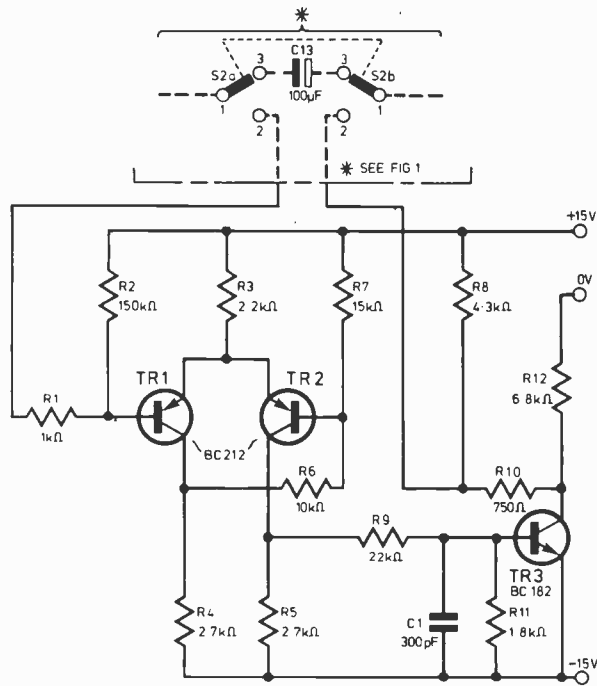


Fig. 3. The squarewave generator section circuit

SQUARE WAVE GENERATION

The sine wave oscillator is designed so that the square wave circuit is add-on, as it were. This enables users not immediately interested in square waves to use the signal generator and to add the squaring facility later. Fig. 3 shows the circuit diagram of the square wave generator with details of S2, Fig. 1, included.

When S2 is switched to square-wave, the sine wave signal passes to a Schmitt trigger circuit consisting of

SQUAREWAVE GENERATOR

Resistors

- R1 1kΩ
- R2 150kΩ
- R3 2.2kΩ
- R4 2.7Ω
- R5 2.7Ω
- R6 10kΩ
- R7 15kΩ
- R8 4.3kΩ
- R9 22kΩ
- R10 750Ω
- R11 1.8kΩ
- R12 6.8kΩ

All 5% ¼W carbon

Capacitors

- C1 300pF

Semiconductors

- TR1/TR2 BC212, 2-off
- TR3 BC182

TR1 and TR2. In this trigger circuit TR1 is normally off and TR2 is fully conducting since its base is driven from the -15V line via R4 and R6; the circuit remains in this condition as long as a positive half-cycle is applied to TR1 via R1.

When the sine wave input falls through zero to a negative potential, TR1 starts to conduct and the potential at its collector starts to fall, so reducing the current through R5. This change in current is transferred via the emitter of TR2 to the emitter of TR1 and encourages TR1 to "switch on" even faster, so the circuit "changes over" regeneratively.

A similar regenerative action occurs as the sine wave passes from negative to positive. The collectors of both TR1 and TR2 show a square wave signal and that from TR2 passes to amplifier TR3 which ensures that the output signal switches between $\pm 10V$.

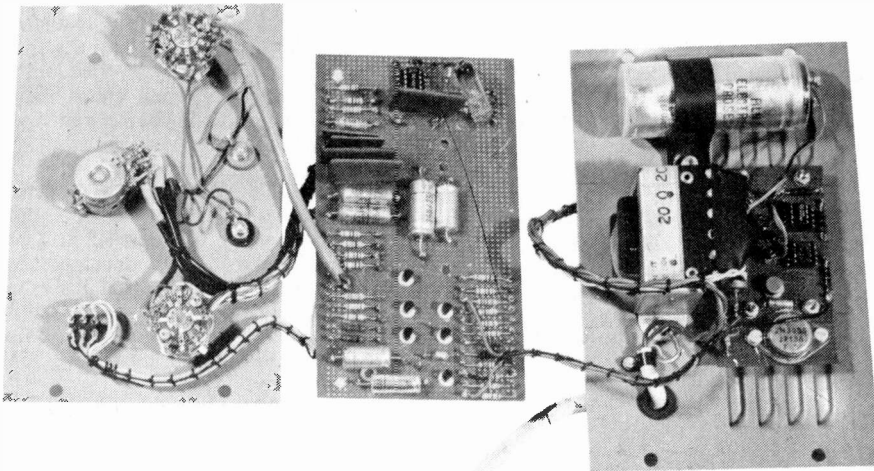


Fig. 4. General arrangement of the circuit boards and main components on the front and back panels

COMPONENTS . . .

POWER SUPPLY

Resistors

- R1 1k Ω
- R2 10k Ω
- R3 10k Ω
- R4 10k Ω
- R5 240 Ω
- All 5% $\frac{1}{4}$ W carbon

Capacitors

- C1 2,500 μ F, 64V
- C2 2.2 μ F
- C3 100 μ F, 50V

Semiconductors

- IC1/IC2 SN72741, 2-off
- TR1 ZN3053, 2N3053
- TR2 ZN3055, 2N3055
- D1, 2, 3, 4 100 V p.i.v. bridge, 40mA (96A, ITT)
- D5 BZY88 C10
- D6 BZY88 C15
- D7 BZY88 C5V1
- D8 BZY88 C10

Miscellaneous

- S1 2-pole mains on/off
- FS1 1A cartridge fuse and holder
- LP1 Neon indicator unit
- TR1 Mains (240) to 40V (20-0-20), 40mA transformer
- Matrix board, 95 \times 55mm

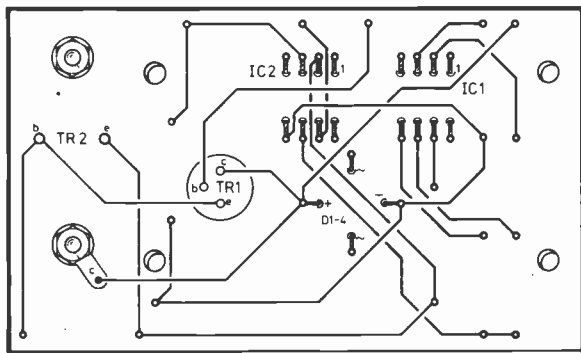
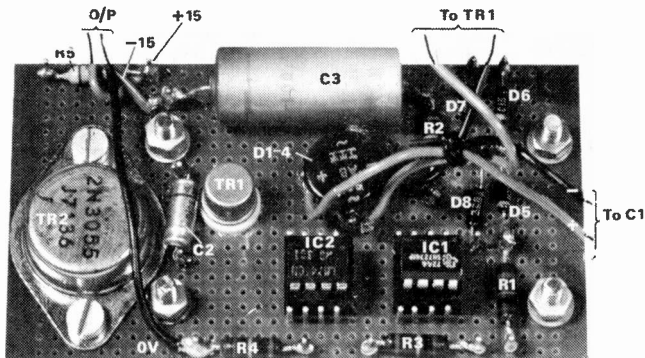


Fig. 5 (top). Component layout for the power supply board

Fig. 6 (bottom). Wiring details for the layout of Fig. 5

CONSTRUCTION

A standard instrument case measuring $8\frac{1}{2} \times 5\frac{1}{2} \times 5\frac{1}{2}$ in ($216 \times 140 \times 140$ mm), provides a suitable unit in which to house the generator. The photograph of Fig. 4 shows the general arrangement of the three main sections, front panel, main board and back panel.

First the power supply components are mounted as shown in Figs. 5 and 6, with the exception of the capacitor C1 and mains transformer, on a 55×95 mm, 0.1in matrix board. The matrix is mounted on the back panel using 4BA spacers to give the required board clearance. Next mount the transformer and capacitor directly on to the back panel using a "P" clip to fasten the capacitor as in Fig. 4. FS1 and LP1 are omitted in the prototype.

The oscillator assembly is made up on a 175×95 mm matrix board as in Figs. 7 and 8. This assembly includes the components which comprise the oscillator and square wave generator. This board is mounted on the bottom of the unit, again using 4BA spacers to provide the required board clearance.

Fig. 1 shows the oscillator as two distinct sections, oscillator and output amplifier, and the square wave generator. The recommended layout shown in Figs. 7 and 8 preserves these distinctions.

Board wiring is not critical providing one adopts a sensible approach. Mount all other components having control functions on the front panel, for example the attenuator output switch, S3, with the resistors R18 to R26 mounted on the switch itself.

Finally, attach the flexible interconnecting leads to the oscillator board, power supply and front panel.

Keep the transformer wiring separate and connect it directly to the mains switch S1 and bridge rectifier connections. Make the mains earth connection to the chassis. Run the two wires from the output terminals directly to the output switch S3 pins 1 and 11.

The remaining interconnecting wiring in the prototype was divided into three distinct looms, wire idents providing individual wire identification. The first loom consisted of three power supply wires, the second of the wiring concerned with the sine-square switch S2, and the third included the Wein bridge potentiometer wires and the output wiring to the attenuator switch S3. These wires must be screened and the screens connected to the chassis via a tag on the front panel. Keep wire lengths to a minimum, but long enough to enable back and front panels to be laid flat for wiring and test purposes.

COMPONENTS

Close tolerance capacitors in the timing circuits will yield the best results; silver mica capacitors are particularly suitable. Also the twin ganged potentiometer VR1, VR2 needs to be of good quality. Because single screened wire has an inherent capacitance, this affects the frequency output in the 100kHz range, and to compensate for the value of the capacitor, C8 is varied from that determined by the formula. Readers who do not have accurate resistance or frequency measuring test gear should obtain the best possible twin potentiometers they can afford, together with 1 or 2 per cent capacitors in the timing circuits. This helps to increase the accuracy of calibration.

SINEWAVE GENERATOR

Resistors

R1	2kΩ 5%
R2	2.2kΩ 2%
R3	51Ω 2%
R4	1.5kΩ 5%
R5	STC Thermistor, R53
R6	51Ω 5%
R7	2.2kΩ 2%
R8	30kΩ 5%
R9	2kΩ 5%
R10	11kΩ 5%
R11	1kΩ 5%
R12	150kΩ 5%
R13	30kΩ 5%

R14	150kΩ 5%
R15	100Ω 5%
R16	100Ω 5%
R17	1kΩ 1%
R18	8kΩ 1%
R19	1kΩ 1%
R20	800Ω 1%
R21	100Ω 1%
R22	80Ω 5%
R23	10Ω 5%
R24	8Ω 5%
R25	1Ω 5%
R26	1Ω 5%

Potentiometers

VR1/2 2-gang linear 20kΩ pot., ±10% tol., ±1% linearity

Capacitors

C1	500pF 1%
C2	6,800pF 1%
C3	0.068μF 5%
C4	0.68μF 5%
C5	250μF, 25V
C6	20pF
C7	5,000pF
C8	500pF 1%
C9	6,800pF 1%
C10	0.068μF 5%
C11	0.68μF 5%
C12	100μF, 50V
C13	100μF, 50V
C14	100μF 5V

Semiconductors

TR1/2	BC182, 2-off
TR3	BC212
D1	BZY88 C15
IC1	SN72709

Switches

S1	2-pole, 4-way
S2	2-pole changeover
S3	1-pole, 9-way

Miscellaneous

Matrix board, 175 × 95mm.
Suitable case, wire, solder

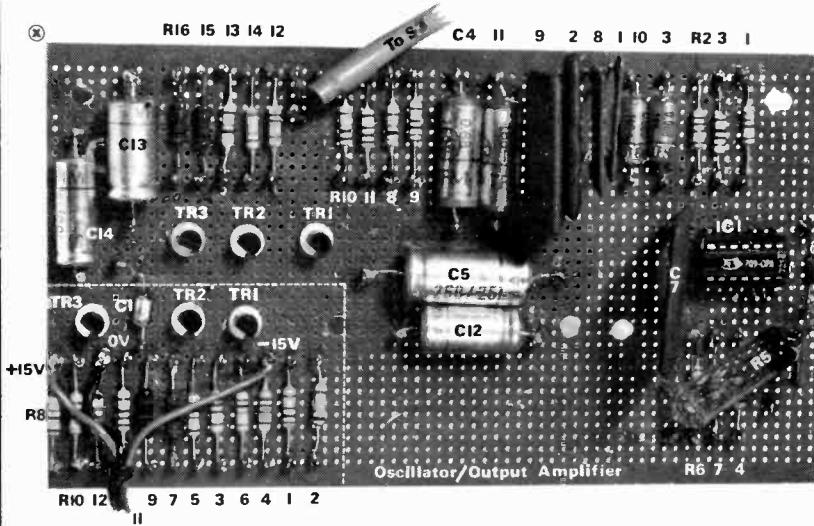


Fig. 7. Component layout for the oscillator board

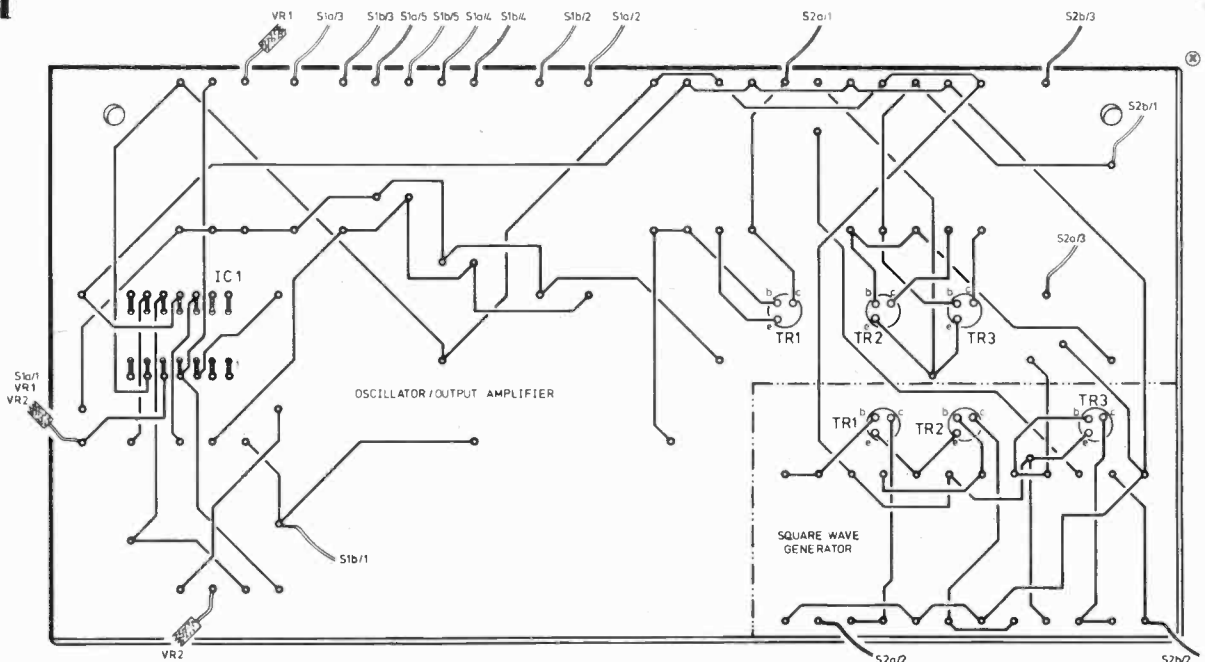


Fig. 8. Wiring details for the layout of Fig. 7

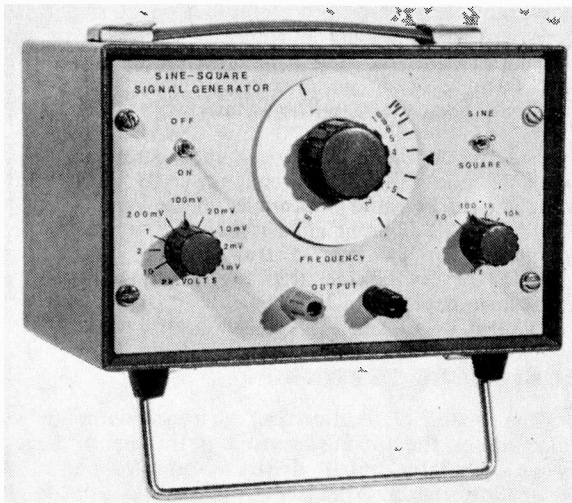


Fig. 9. Squarewave testing waveforms

CALIBRATION

The dial showing frequency settings may be a simple dial, knob and pointer, or an elaborate linear dial as used on a receiver. But whichever dial one uses, one must calibrate it. To allow for the various types of dial and potentiometer available, the calibration data is tabulated in Table 1. The best way of calibrating the instrument is to measure the frequency and to mark the dial accordingly; the next best method is to measure resistance.

However, if one does not have suitable measuring facilities one can still obtain quite good results by measuring dial positions with a protractor or ruler and using the data given in Table 1. Because the instrument has decade ranges, one needs only to plot one range of frequency.

If the instrument incorporates a linear dial, mark the two end stops to give 1.05kHz and 10.6kHz and use a rule to measure the distance between these two stops.

If it incorporates a rotary dial, mark the end stops to give 1.05kHz and 10.6kHz and use a protractor to measure the angle (in degrees) between them.

Table 1 shows corresponding values of frequency measured directly with frequency measuring equipment, resistance measured with resistance measuring equipment, and the multiplying factor for determining the dial setting.

To calculate the dial setting corresponding to the required frequency, multiply the factor given in column 3 of Table 1 by the angle or distance measured between the two end stops. The result is the angle or distance from the 10.6kHz marker which one should mark on the dial. To illustrate how multiplying the total angle by the factor gives the calibration angle required, column 4 gives the angles calculated for the prototype instrument.

Because frequency is proportional to the reciprocal of resistance, the frequency scale marked on the dial will not be linear.

SQUARE WAVE TESTING

Using a square wave source for testing digital circuits such as counters and frequency meters is a fairly obvious application for these units. In contrast many enthusiasts are not aware of the value of square wave testing of high-fidelity amplifiers.

Gain frequency plots of amplifiers tell us a little about their characteristics, but such a plot does not indicate how the amplifier responds to transient signals. Plotting may miss small changes in level at different frequencies which can contribute to a reduced performance under transient conditions.

A good-shaped square wave signal consists of the fundamental frequency plus a large number of harmonics, which are necessary to form a precise square wave signal. Therefore, when one applies a square wave to an amplifier one is, in effect, sweeping a whole band of frequencies. This means that when one views the square wave signal output with an oscilloscope, one sees the effect of the overall response of the amplifier.

One can investigate the principal characteristics of square wave testing by connecting an audio amplifier to a resistive load and applying a low frequency, low amplitude square wave to the input. This gives rise to the three basic output waveforms shown in Fig. 9b, c and d. Fig. 9a represents the input square wave and also the output waveform which one might expect from a perfectly flat response amplifier.

The curve at b represents the output to be expected from a capacitively coupled amplifier. Here the pulse droops with an amount related to the low frequency characteristics of the amplifier.

Strictly speaking it is difficult to relate droop to the 3dB point in an amplifier, because the rate at which the amplifier falls towards cut-off influences the droop. However, many people assume that a single time constant operates (6dB per octave) and estimate the 3dB point from the droop which this single time constant causes. These estimates are quite accurate enough for most applications. Droop is also caused by the bass cut control of the amplifier, so we can use a square wave source for evaluating the operation of the tone circuits as well.

Table 1: Calibration

Frequency (kHz)	Potentiometer Resistance k Ω	Multiplying Factor Angle or Distance	Typical Dial Angle 285°
1.05	20.1	1.0	285
1.5	13.40	0.652	190
2.0	9.50	0.475	135
2.5	7.16	0.358	102
3.0	5.60	0.28	78.8
3.5	4.49	0.224	64
4.0	3.65	0.182	52
4.5	3.00	0.15	43
5.0	2.48	0.124	35
5.5	2.05	0.10	28.5
6.0	1.70	0.085	24
6.5	1.40	0.07	20
7.0	1.14	0.057	16
7.5	0.92	0.046	12.8
8.0	0.72	0.036	10.2
8.5	0.55	0.028	7.9
9.0	0.40	0.02	5.7
9.5	0.26	0.013	3.7
10.0	0.14	0.007	1.9
10.6	0.01	0.00	0

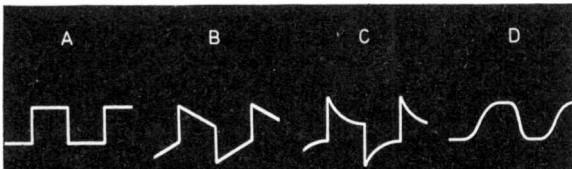


Fig. 9. Squarewave testing waveforms

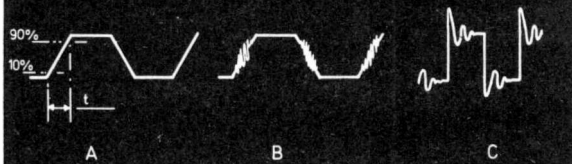


Fig. 10. High frequency waveforms

LOW FREQUENCY RESPONSE

Fig. 9c shows the characteristic effect of a rising high frequency response. The leading edge of a pulse contains the majority of the high frequencies, so when one increases the treble boost control, the pulse acquires leading-edge spikes. Adjusting the "treble cut" will remove high frequencies from the pulse as shown in Fig. 9d. These tests are normally carried out with square wave frequencies below 500Hz. The low frequency droop characteristics show up even better on lower frequencies, such as 50 to 100Hz, while the high frequency effects are more apparent at the higher frequencies.

HIGH FREQUENCY RESPONSE

At much higher frequencies square wave testing has several useful applications. Fig. 10 shows examples of high frequency waveforms. At 10a, the response of a good amplifier to a well-shaped square wave is shown. This waveform has sloping sides caused by the fall off in high frequency response of the amplifier.

Specifications often quote rise times for amplifiers, especially oscilloscope amplifiers. The rise time is the time the pulse takes to grow from 10 per cent of its final amplitude to 90 per cent of its final amplitude, hence the expression "the 10 to 90 per cent rise time t ".

As with low frequency and droop, rise time may be related to the high frequency 3dB point in the amplifier, if one assumes a single time constant cut-off. Since one may measure the 3dB point directly using the sine generator, it is not worth making either of the latter calculations.

H.F. OSCILLATIONS

Waveform 10b represents a more important aspect of square wave testing in which the pulse causes some high frequency oscillation. Oscillations of this type are caused by stray capacity giving positive feedback and instability which shows up on transient signals. The source of such oscillations must be located and stopped.

The waveform of 10c shows a typical underdamped response which one would expect from many electro-mechanical systems. A transformer coupled circuit,

for example, would often exhibit this type of characteristic. After finding a response of this type one would seek out the source of underdamped responses and in an effort to improve performance increase the damping to give a response as near as possible to Fig. 10a.

The frequency at which one should test amplifiers depends upon the high frequency 3dB point f_{3dB} . One should examine frequencies in the range $f_{3dB}/10$ to $f_{3dB}/2$ as different effects show up at various frequencies, for example a frequency of $f_{3dB}/4$ e.g. 25kHz for a 100kHz amplifier might produce the waveform depicted in Fig. 10a.

ENCLOSURE TESTING

The testing of loudspeaker enclosure damping will also interest the hi-fi enthusiast. In this test the square wave generator must drive a powerful amplifier coupled to the loudspeaker through a high impedance. An impedance some ten times that of the loudspeaker will be necessary using an amplifier which is capable of operating without the loudspeaker load. Few valve amplifiers can be used for this test. The amplifier must also be capable of amplifying at frequencies below that of the speaker resonance under test, and producing satisfactory square waves at 20Hz or less.

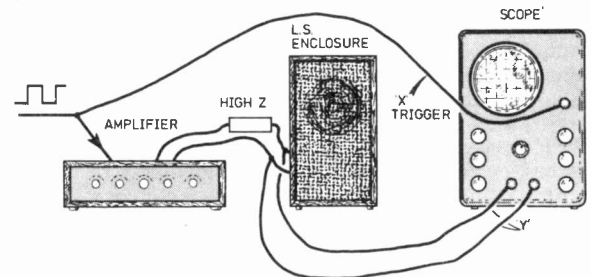


Fig. 11. Loudspeaker test rig arrangement


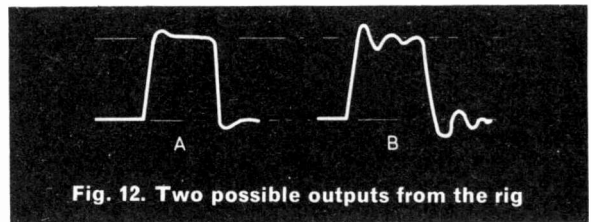


Fig. 12. Two possible outputs from the rig

Fig. 11 shows the test circuit arrangement. One needs a high gain oscilloscope to see the effects shown in Fig. 12a and b. Waveform 12a is the type of response one should try to achieve while 12b shows an underdamped system. This method provides a means of investigating the effect of various cavities and baffles using a variety of loudspeakers.

Square wave frequencies of the order 20 to 30Hz are necessary for these tests. Removing or omitting the high impedance will cause the amplifier to damp the loudspeaker system (a highly desirable characteristic in practice), but will mask out the effects of the acoustic damping system, which is being investigated.

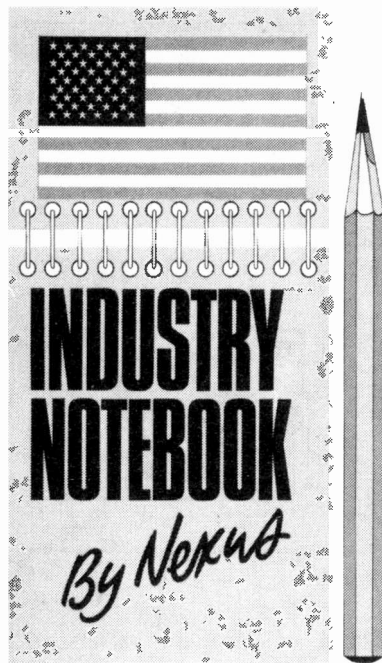In square wave testing one must be absolutely sure that the circuits are not being overdriven as this will remove any ringing or oscillatory responses one is investigating, so it is better to start off with a very small amplitude and increase it to the desired level. ★



THE US SCENE

Arriving in New York for the IEEE electronics show, one expected to find signs of recession and first impressions confirmed all expectations. Unemployment almost 9 per cent which meant 8 million workless citizens. Worse still, a survey showed that of these, over a million had given up all hope of finding a job and were not even bothering to try any more. The city itself is bankrupt—not enough income from rates and taxes to meet its bills.

In foreign affairs there was the added depression of the collapse of American policy in South East Asia and little comfort to be had from the Middle East where the Kissinger initiative had failed—at least for the time being.

Enough to give anyone the shivers and suddenly the European situation didn't look so bad after all. But strangely, when the show opened things seemed not nearly so desperate. True, Senator Barry Goldwater in the opening speech of the technical congress said the chips were down, the USA was running into bankruptcy, losing credibility in the world, but his was a political rather than a business speech.

At the New York Coliseum, where nearly 400 companies were exhibiting and attracting 22,000 visitors in three days, there was an optimistic outlook. Were these exhibitors and buyers just whistling in the dark to keep up their courage? This was not my impression. The consensus was

that the recession was about to bottom out, perhaps had already done so. Another three months, perhaps, and things would be taking off. In twelve months the outlook would really be bright. Old hands in the game remembered being caught unprepared in former trade cycles. They had cut back in times of recession and missed out on market shares when the upturn came. This time they wouldn't be caught with their pants down.

This was the busiest show I had seen in years and among the least gloomy. It demonstrated that whatever the shortcomings of Government—the Americans are still in a state of shock from Watergate and have little confidence in the present administration—the hard core of the US electronics industry is showing resilience and enterprise.

The United States, recession or not, remains more than 50 per cent of the world's total electronics market and should not be neglected. In Europe, and especially in Britain, we are so mesmerised by the new affluence in the Arab states that all eyes are looking East. Those British companies who exhibited in New York were not disappointed.

Companies already established in the US market like Marconi Instruments, Plessey and Ferranti, widened their business base this year. Newcomers like Brandenburg, Mirvalle and the still tiny Linton Laboratories found new markets, new opportunities. And did you know that American semi-conductor manufacturers send wafers to Harwell for ion implantation? Well, Harwell Industrial Research, who offer this specialised service, also did good business.

Ten British companies exhibited. There should have been a hundred. British technology is highly respected in the USA and is in demand provided, of course, the price is right. Our problem is inflation, not technology.

HOT MARKETS

The two hottest and toughest markets in the United States are calculators and watches. The British Sinclair-made model designed for Gillette was test-marketed in San Francisco and St. Louis and, according to reports, exceeded all expectations. It was planned to sell the 4-function, 8-digit model at 30 dollars (£12.50) but the week before the test marketing started Novus came out with a competitive unit at 20 dollars so Gillette dropped the price to 25 dollars.

Although the operation was a success, Gillette has now pulled out of the business, blaming unstable pricing. Gillette was reported to have ordered 100,000 calculators for the test-marketing. It was good business

for Sinclair because the British company is left with world marketing rights and those machines designed for Gillette have now appeared as the Sinclair Oxford range.

The 5-function 8-digit calculator from Texas Instruments had a retail price of 25 dollars (a little over £10) as I left for home, but even lower prices could be negotiated by individuals at the point of sale in many New York stores. One wag suggested to me that the way things are going the batteries will soon cost more than the calculators. He could be right!

Innovators are already working on getting some added value into calculators by making them part of a larger assembly. For example, by building a calculator into a notebook and daily diary. This model sells for 35 dollars and makes a nice present in a new market dubbed locally as "Gimmick Calculators".

PACESETTERS

Electronic watches are going the same way. If you are a watch manufacturer you can buy the complete i.e.d. electronics kit from Fairchild for a reported 10 dollars (just over £4) in 1,000 lots. This market is somewhat different because a lot of the value of a watch is not so much in the "movement" but in the case.

It is still not clear how many semi-conductor manufacturers will go directly into the manufacture of complete watches but a number have already done so, two of them having already reached the low retail price level of 50 dollars (£21). It's hard to find any other product not going up in price but electronics goods still fall in price.—Amazing!

Nobody's yet done it but the next step, believe it or not, is the combined wristwatch and calculator in a single case. An enterprising plastics manufacturer has already produced a prototype case which can be plated to look like metal. There are 18 tiny dimpled calculator keys which can be depressed with the tip of a pen or pencil.

Expected to be a popular new line in the States is a calculator variant which caters for the individual (actually, nearly everybody) who runs his bank balance perilously near the red. It's called the CheckMaster. You enter in your bank balance and every time you pay by check (we spell it cheque) you key in the amount and it gives you your new balance statement. You also enter any deposits. Snapping the lid shut switches the CheckMaster off but the balance remains stored in the memory and shows up again next time you use the machine.

A curvilinear lens on the i.e.d. display gives a very narrow angle of view so that Peeping Toms can't see how hard you are.

PATENTS REVIEW...

PAGING BY PHONE

Radio paging systems often use a radio frequency carrier, modulated by a sub-audio tone signal to alert the attention of someone carrying the necessary receiver. But usually the centre of paging operations is remote from the transmitter and connection must be via standard telephone lines and these attenuate all signals below 300Hz. Thus to transmit a sub-audio tone from a remote point involves the expense of hiring special phone line connections.

In BP 1 373 748, Motorola Inc. provide a simple answer which could have wider uses in the art of remote control over phone lines.

As shown in the block schematic diagram (Fig. 1) an encoder at the centre of operations incorporates a bank of oscillators which develop audio tone signals. These signals, in the range from 300-3,000Hz, can be transmitted without attenuation over the phone line to the transmitter station.

The audio tones produced are exact harmonics of the sub-audible tones which are needed to actuate a paging receiver. In the example given two sequentially received sub-audio tones are needed to actuate the paging receiver and the encoder sequentially develops two corresponding audible tones.

D.C. signals are also sent down the line for transmitter switching, and at the transmitter station the d.c. separator directs these to the transmitter and directs the audio tone signals to an amplifier and bistable clipper.

The square wave signal at the output of the amp and clipper have the same frequency as the tones sent down the phone line. A divider network separates these square wave signals by the requisite number, to produce a second spectrum of square wave signals of the required sub-audio frequencies.

For example, 1,800Hz square waves coupled to the divider will be divided by eight to develop 225Hz square wave signals. The latter are coupled to the frequency selector which routes all signals

BP 1 373 748

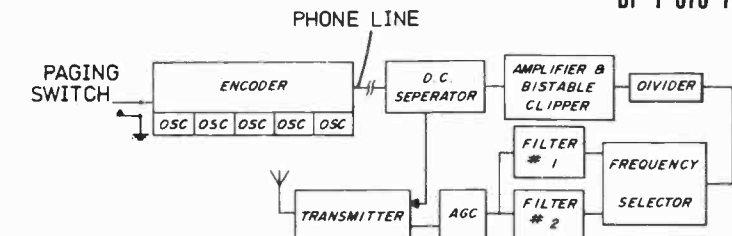


Fig. 1

with a frequency in excess of 125Hz to filter 1 and all signals below 125Hz to filter 2.

Filter 1 has low pass characteristics to remove all harmonics above 250Hz and prevent inter-modulation products. Filter 2 functions similarly on all frequencies above 125Hz.

An automatic gain control circuit (a.g.c.) compensates for filter variation, provides a constant amplitude output signal for all sub-audio tones in the range 65-225Hz and passes them to the transmitter for transmission and reception in conventional manner.

The patent contains detailed descriptions of suitable circuitry for realising the schematic.

warning of important patents by listing 12,000 per week from 24 countries. The aim is to break through the language barrier and provide a summarised and indexed world-wide surveillance for researchers.

The Foreign Patents Section of the Science Reference Library, just over the road from the British Patent Office, in Southampton Buildings, Chancery Lane, has the WPI material available for the public's use free of charge.

Part of the Derwent scheme is to identify "basic" and "equivalent" patents as such. As the terms imply, basic patents are concerned with initial protection for new inventions, and equivalents relate to further protection elsewhere.

The WPI material, at least initially, is somewhat off putting. A researcher will need time and patience to accustom himself to the terminology and symbols used. American and British patents are logically listed as US and GB, but their normal seven-digit numbers are broken up with hyphens in a manner which may confuse workers used to dealing with conventional patent numbers.

The Foreign Patents Section enquiry desk has a guide hand-book available to help readers who wish to use the index and need to familiarise themselves with the system. In fields such as electronics, where new developments are continually emerging and there is a real risk of laboratories wasting time by duplicating work already done by others, it could be of value for small or medium sized firms to form a consortium and use the WPI together.

WORLD PATENT INDEX

Patents reported here are almost exclusively British issues and represent only a few culled monthly, on a purely arbitrary basis, from the vast number (around 50,000) published every year by the British Patent Office. Even more daunting to anyone interested in keeping a close watch on patents for inventions in their own particular field, is the fact that comparable numbers of patents are continually being published in every other civilised country in the world.

The Derwent World Patents Index (WPI) is a weekly publication which seeks to give an early

PHONOSONICS

SUPPLIERS OF QUALITY PRINTED
CIRCUIT BOARDS, KITS AND
COMPONENTS TO A WORLD-WIDE MARKET

SOUND-TO-LIGHT (P.E. Apr./Aug. 71)

The ever-popular AURORA—4 or 8 channels each responding to a different sound frequency and controlling its own light. Can be used with most audio systems and lamp intensities. A MUST for any Disco, and a fascinating visual display for the home.

4 channel component set (excl. thyristors)	£11-49
8 channel component set (excl. thyristors)	£20-32
Power supply component set	£4-78
PCB for 4 frequency channels	£2-50
PCB for power supply and 8 lamp drivers	£1-25
1 Amp 400V thyristors (1 per chan. requ.) each	75p
Panel meter (1mA) (optional)	£3-50

VOICE OPERATED FADER (P.E. Dec. 73)

For automatically reducing music volume during "talk-over"—particularly useful for Disco work or for home-movie shows.

Component set incl. PCB £2-95

TAPE-NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings.

Component set (incl. PCB) £2-30
Regulated power supply (incl. PCB) £3-71

P.E. SYNTHESISER

The well-acclaimed and highly versatile large-scale mains-operated Sound Synthesiser complete with keyboard circuits, and having a wider range of functions than the P.E. Minisonic, though the two may be used in conjunction with each other to great advantage. Published in P.E. Feb. 1973 to Feb. 1974.

Full details of component sets, printed circuit boards and discount facilities are in our list. Send S.A.E.

HI-FI TAPE-LINK (P.E. Mar./Apr. 73)

Designed for use with reasonable quality tape-decks, this high performance pre-amp includes record, playback and metering circuits.

Stereo component set (excl. panel meter)	£22-95
Mono component set (excl. panel meter)	£13-31
Power supply component set	£3-72
Stereo main PCB	£2-50
Stereo sub-assembly PCB	86p

P.E. GEMINI 30W STEREO AMPLIFIER

An exceptionally high quality Stereo Amplifier system, specifications for which are shown in detail in our list, together with semiconductor requirements. While stocks last.

Main Amplifier:	
Set of resistors, capacitors and presets	£5-96
Stereo printed circuit board	£1-28
Pre-Amplifier	
Set of resistors, capacitors, potentiometers and switches	£10-57
Standard tolerance set	£18-04
Superior tolerance set	£2-20
Stereo PCB (as published)	
Regulated Power Supply:	
Set of resistors, capacitors and preset	£4-58
Printed circuit board	72p

SIGNAL GENERATOR

SEND S.A.E. FOR DETAILS

VOLTAGE CONTROLLED FILTER (P.E. Oct. 74)

An independently designed VCF that can be used with the P.E. Synthesiser.

Component set	£3-41
Printed circuit board	£1-10

RHYTHM GENERATOR

Programmable for 64,000 rhythm patterns from 8 effects circuits (high and low bongos, bass and snare drums, long and short brushes, blocks and cymbal), and with variable time signatures. Really fascinating and useful! (Published in P.E. Mar./Apr. 1974).

NOW AVAILABLE WITH ALTERNATIVE INDEPENDENTLY DESIGNED PRE-AMPS AND MIXER GIVING EVEN GREATER VERSATILITY.

Full details of component sets, PCB's and discounts are in our list—send S.A.E.

SOUND BENDER (P.E. May 74)

A multi-purpose sound controller, the functions of which include envelope shaper, tremolo, voice operated fader, automatic fader and frequency-doubler.

Component set for above functions (excl. sw's)	£5-86
Printed circuit board	£1-44

Optional extra—additional Audio Modulator, the use of which, in conjunction with the above component set, can produce "jungle-drum" rhythms.

Component set (incl. PCB) £2-10

PHASING UNIT (P.E. Sept. 73)

A simple but effective manually controlled unit for introducing the "phasing" sound into live or recorded music.

Component set (incl. PCB) £2-20

PHASING CONTROL UNIT (P.E. Oct. 74)

For use with the above Phasing Unit to automatically control the rate of phasing.

Component set (incl. PCB) £3-50

P.E. JOANNA

The new Electronic Piano published in P.E., series commencing May 1975. Send S.A.E. for our details and discounts.

WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds.

Component set incl. PCB £2-40

OTHER PCBs (all "as published") While stocks last

Bench Power Supply (P.E. Sept. 74)	80p
Digital Power Supply (P.E. Aug. 72)	50p
Electronic Piano:	
Pre-amp PCB (P.E. Oct. 72)	95p
Pitch PCB (P.E. Nov./Dec. 72)	£1-50
Power Supply PCB (P.E. Oct. 72)	85p
Gemini Stereo Tuner (P.E. June 72)	£1-50
Power Slaves (P.E. Aug. 74):	
Power Supply PCB	55p
Rondo:	
CBS SQ Decoder PCB (P.E. Sept. 73)	60p
Pre-amp PCB (P.E. Oct. 73)	60p
Tone, Balance and Vol-control PCB (Oct. 73)	£1-50
Trifid I.C. Radio (P.E. Feb. 73)	60p

BIOLOGICAL AMPLIFIER (P.E. Jan./Feb. 73)

Multi-function circuits that, with the use of other external equipment, can serve as lie detector, alphaphone, cardiophone, etc.

Pre-Amplifier Module	
Component set and PCB	£3-48
Basic Output Circuits	
Combined component set with PCBs, for alphaphone, cardiophone, frequency meter and visual feed-back lamp driver circuits	£4-96
Audio Amplifier Module	
Type PC7	£5-50

PHOTOPRINT PROCESS CONTROL

(P.E. Jan./Feb. 72)

For colour and B & W, an indispensable dark-room unit for finding exposure, controlling enlarger timing, and stabilising mains voltage.

Component set (excl. meter)	£8-85
Printed circuit board	£1-60
Panel meter (1mA)	£3-50

ENLARGER EXPOSURE METER AND THERMOMETER (P.E. Sept. 73)

Dual-purpose dark-room unit with good accuracy.

Component set with PCB but excl. meter	£4-00
Panel meter (100µA)	£3-50

P.E. MINISONIC

A portable, battery or mains operated, miniature sound synthesiser, with keyboard circuits. Although having slightly fewer facilities than the large P.E. Synthesiser, the functions offered by this design give it great scope and versatility.

Full details of component sets, printed circuit boards and discount facilities are in our list. Send S.A.E.

REVERBERATION UNIT (P.W. Nov./Dec. 72)

A high quality unit having microphone and line input pre-amps, and providing full control over reverberation level.

Component set (excl. spring unit)	£6-82
Printed circuit board	£1-40
9 inch spring unit	£4-95
Panel meter (50µA) (optional)	£3-50

ULTRASONIC TRANSMITTER-RECEIVER

(P.E. May 1972)

A highly sensitive, tight-beam, long-range, "invisible beam" detection circuit with numerous applications.

Component set with PCBs but excluding transducers £4-40

SEMICONDUCTOR TESTER (P.E. Oct. 73)

Essential test equipment for the enterprising home constructor.

Set of resistors, capacitors, semiconductors, potentiometers, maks switches and PCB	£8-56
Panel meter (500µA)	£3-50

PCB LAYOUT AND CIRCUIT DIAGRAMS

SUPPLIED WITH ALL PCBs DESIGNED BY PHONOSONICS

COLOUR CODE IDENTIFICATION

SUPPLIED WITH MOST KITS AND AS PART OF LIST

ALL PCBs ARE FIBRE-GLASS, DRILLED AND TINNED

Semiconductors	BFY50	22p	2N3703	12p	Integrated Circuits	Zeners	Electrolytic Capacitors (µF/V)	Polyester (µF)	Tantalum (µF/V)		
AC128	28p	BSY55A	22p	2N3822	48p	3 3V 400mW	12p	0 01	3p	0 1/35	12p
AC178	28p	MJE2955	11p	2N4080	12p	4 7V 1W	25p	0 022	3p	0 2/35	12p
BC107	13p	MJE3055	75p	2N4080	12p	723 TOS	15p	0 033	31p	1 0/35	12p
BC108	13p	NKT10033	112p	2N5245	81p	741 8-pin DIL	11p	0 047	31p	1 5/35	12p
BC109	13p	OC71	14p	2N5777	45p	747 14-pin DIL	65p	0 068	31p	2 2/35	12p
BC147	12p	OC72	14p	748 TOS	65p	748 8-pin DIL	83p	0 1	49	4 7/35	12p
BC148	12p	OC72	14p	748 14-pin DIL	83p	11V 1W	25p	0 15	8p	10 1/16	14p
BC149	12p	OC72	14p	748 14-pin DIL	83p	12V 400mW	15p	0 22	8p	10 2/16	14p
BC157	12p	OC72	14p	748 14-pin DIL	83p	18V 1W	20p	0 33	8p	15 6/3	16p
BC158	13p	ZTX107	12p	1N4001	4p	12V 1.3W	30p	0 47	8p	18 2/16	14p
BC159	13p	ZTX503	12p	1N4002	7p	18V 400mW	15p	0 68	8p	22 1/16	14p
BC182L	13p	ZTX531	22p	1N4004	4p	20V 400mW	15p	1 0	14p	27 1/16	14p
BC184	12p	2N708	12p	1N4005	4p	18V 1W	20p	1 5	14p	33 1/16	14p
BC204	14p	2N814	22p	1N4007	10p	20V 400mW	15p	2 2	14p	47 1/16	14p
BC290C	14p	2N1504	22p	CA31	7p	20V 1W	23p	3 3	14p	68 1/16	14p
BC212L	15p	2N2219	27p	CA30	5p	27V 400mW	15p	4 7	14p	100 1/16	14p
BC213	15p	2N2905	37p	µA7815 TO220	25p			6 8	14p	150 1/16	14p
BC478	15p	2N2907	22p	CA3048	8p			10	14p	200 1/16	14p
BCY71	22p	2N3054	66p	µF0040	65p			15	14p	300 1/16	14p
BF178	28p	2N3702	12p	1LJ50	11p			22	14p	470 1/16	14p
				2LJ (2LJ)	75p			33	14p	680 1/16	14p
								47	14p	1000 1/16	14p
								68	14p	1500 1/16	14p
								100	14p	2200 1/16	14p
								150	14p	3300 1/16	14p
								220	14p	4700 1/16	14p
								330	14p	6800 1/16	14p
								470	14p	10000 1/16	14p
								680	14p	15000 1/16	14p
								1000	14p	22000 1/16	14p
								1500	14p	33000 1/16	14p
								2200	14p	47000 1/16	14p
								3300	14p	68000 1/16	14p
								4700	14p	100000 1/16	14p
								6800	14p	150000 1/16	14p
								10000	14p	220000 1/16	14p
								15000	14p	330000 1/16	14p
								22000	14p	470000 1/16	14p
								33000	14p	680000 1/16	14p
								47000	14p	1000000 1/16	14p
								68000	14p	1500000 1/16	14p
								100000	14p	2200000 1/16	14p
								150000	14p	3300000 1/16	14p
								220000	14p	4700000 1/16	14p
								330000	14p	6800000 1/16	14p
								470000	14p	10000000 1/16	14p
								680000	14p	15000000 1/16	14p
								1000000	14p	22000000 1/16	14p
								1500000	14p	33000000 1/16	14p
								2200000	14p	47000000 1/16	14p
								3300000	14p	68000000 1/16	14p
								4700000	14p	100000000 1/16	14p
								6800000	14p	150000000 1/16	14p
								10000000	14p	220000000 1/16	14p
								15000000	14p	330000000 1/16	14p
								22000000	14p	470000000 1/16	14p
								33000000	14p	680000000 1/16	14p
								47000000	14p	1000000000 1/16	14p
								68000000	14p	1500000000 1/16	14p
								100000000	14p	2200000000 1/16	14p
								150000000	14p	3300000000 1/16	14p
								220000000	14p	4700000000 1/16	14p
								330000000	14p	6800000000 1/16	14p

Don't miss your copy of HENRY'S NEW 1975 CATALOGUE



- ★ OVER 5,000 ITEMS - largest UK range of electronic components for home constructors.
- ★ 200 PAGES - every aspect of electronics and components for amateurs and hobbyists - kits, projects, test gear.
- ★ DOZENS of new lines and new ranges.
- ★ MANY price reductions throughout the new Catalogue.
- ★ A Discount Voucher with every copy, worth 50p.

FREE TO EDUCATIONAL ESTABLISHMENTS when ordered on official notepaper.

Write now for your copy, enclosing 65p remittance.

NOW OPEN SUPERMARKET, BROWSE ROUND THE NEW SUPERMARKET AT 404 EDGWARE ROAD

Henry's

Electronic Centres
404-405 Electronic Components & Equipment 01-462 8381
309 PA-Disco Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road London W2 1BW
Prices correct at time of preparation. Subject to change without notice. £ 60 £

ELECTRONIC FOOTBALL AND TENNIS WITH THE FABULOUS

VIDEO SPORT

ON YOUR OWN TV

Play three exciting electronic ball games. FOOTBALL, TENNIS, HOLE IN THE WALL on your own TV! Just plug Video Sport into the aerial socket of your TV and away you go. Completely safe for you, your children and your TV. Mains operated.



OUR INCREDIBLE PRICE

£35

Demonstrations now in all HI-FI CENTRES!

AM/FM MODULES

LP1179 LP1171

Combined AM/FM tuner modules, together with a small number of R.C.s & Ferrite Aerials, make up a sensitive FM/MW/LW tuner. 6 Volts supply, supplied with data and circuit sheets.

LP1171 combined IF strip £4-60.
LP1179 FM front end and AM gang £4-60.

£3-82 the pair.
Suitable Ferrite aerial 87p.



UHF TV TUNERS

625 line receiver UHF transistorised tuners U.K. operation. Brand new. (Post/packing 25p each). TYPE A variable tuning slow motion drive £2-87. TYPE C variable tuning £2-87. TYPE B 4-button push button (adjustable) £4. TYPE D 6-button UHF/VHF tuner £5-20.

You can build the Texan and Stereo FM Tuner

Features glass fibre PC board, Gardners low field transformer, 51-C.s., 10-transistors plus diodes, etc. Designed by Texas instruments engineers for Henry's and P.W. 1972. Overall size 151 x 21 x 61/2in. Mains operated. Free teak sleeve with every kit.

£38.75 (carriage 50p)

(also built and tested £46-87).



HENELEC STEREO FM TUNER

Features capacity diode tuning, lead and tuning meter indicators, mains operated. High performance and sensitivity. Overall size in teak sleeve 8 x 2 1/2 x 6 1/2in. Complete kit with teak sleeve.

£26.25 (carriage 50p)

(also built and tested £31-20)

JOIN THE LARGE BAND OF CONSTRUCTORS!

FREE

Send now for our free list No. 36 for our complete range of over 10,000 semiconductor devices at new low prices.



EXTRA DISCOUNTS

Semiconductors: Any one type or mixed SN74 Series: 11-C.s. 12-extra 10%; 25-extra 15%; 100-extra 20%.

TRANSISTORS AND INTEGRATED I.C.s

TTL 7400 series I.C.s from 18p each. Cosmos 4000 series I.C.s from 28p each. Linear op-amps from 46p each. Signetics phase lock I.C.s RCA linear I.C.s. TO3 power devices in pnp and npn. BC107 and BC range from 13p each. Range of OC types 30p. Plastic power devices, rectifiers, zenar, power regulator I.C.s and many others. Diodes up to 10W.

ALL PRICES INCLUSIVE OF VAT

PC ETCHING KIT

Contains 1lb ferric chloride, 100sq.in copper clad board, DALO etch-resist pen, abrasive cleaner, etching dish and instructions £3-50.

FERRIC CHLORIDE

Anhydrous technical quality in 1lb double sealed packs. 1lb 90p; 3lb £1-80; 10lb £4-65; 100lb £35.

COMPUTER PANELS

Large quantity always available. 3lb assorted £1-60; 7lb £2-85; 50lb £15. Pack with about 500 components inc. at least 50 transistors £1. Pack with 10 200V 1A SCR's + 120 other parts £1-10. Pack with 18 2N2369, etc. 50p.

7lb BARGAIN PARCELS

Hundreds of new components—resistors, capacitors, pots, switches, + PC boards with transistors and diodes, also loads of odds and ends. Contents always changing £3.

POWER SUPPLY UNIT

G101: Mains transformer, 2A thermal cut-out, bridge rect., will give 1.7 to 10.5V output with 2 extra capacitors (provided). With data £1-30.

TRANSISTOR PACKS

Large quantity of mostly unmarked transistors just arrived—samples tested show 75% O.K. All types included—pnp, npn, plastic, metal, RF, AF, small signal and power. At least 200 for £1-50; 500 £3; 1,000 £5-50.

All prices quoted include U.K. post and VAT at 8% or 25% as appropriate. Surplus components and equipment wanted for cash. S.A.E. for list or enquiries.

GREENWELD (PE7)

51 Shirley Park Road, Southampton, SO1 4FX. Tel. (0703) 772501. Also callers at 21 Deptford Broadway, SE8. Tel. 01-692 2009, and 38 Lower Addiscombe Road, Croydon. Tel. 01-688 2950.

BARGAIN PACKS

12 BC107	£1-20	25 1N4001	£1-20
14 BC108	£1-20	22 1N4002	£1-20
12 BC109	£1-20	20 1N4003	£1-20
15 BC148	£1-20	18 1N4004	£1-20
13 BC149	£1-20	16 1N4005	£1-20
12 BC157	£1-20	14 1N4006	£1-20
12 BC158	£1-20	12 1N4007	£1-20
12 BC159	£1-20	40 1N4148	£1-20
2 2N2646	£1-20	3 2N3055	£1-20
10 BC328	£1-20	12 BC548	£1-20
12 BF194	£1-20	12 BF195	£1-20
7 BF173	£1-20	5 BF181	£1-20

All full spec. marked components.

2N3055s—FULL SPEC.

10 + 35p; 25 + 32p; 100 + 30p.

555 TIMERS

3 + 60p; 10 + 50p; 25 + 46p; 100 + 43p.

8-PIN DIL 741s

10 + 30p; 25 + 26p; 100 + 24p; 250 + 23p.

7 SEGMENT LEDS

Standard DIL package, 0.33in, 4 for £3-60; 6 for £5-20.

VEROBOARD

100sq.in. about 8 pieces assorted sizes and pitches £1-15.

TRANSFORMERS

All mains primary, 6-0-6V at 100mA 85p; 9-0-9V 90p; 12-0-12V 95p; 6-5-0-6-5 at 500mA £1-50; 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 or 30V at 1A, also 12-0-12 or 15-0-15V £2-70; 2A version £3-90.

EDGE CONNECTORS

0.1in pitch, gold plated 11 way 30p; 25 way 50p; 33 way 70p.

RESISTORS AND CAPACITORS

400 assorted carbon resistors £1-40, 250 Hi-stabs, 1, 2 and 5% £1-35; 100 wirewounds, 2-15W £2; 200 poly, mlca ceramic, etc., caps £1-10; 100 C280 polyesters, 0.01-0.47µF £1-30; 200 miniature electrolytics, but mostly unmarked, so only £1-30.

MISCELLANEOUS

9 pole 6-way Yaxley switches 50p; SPCO 5A microswitch 12p; 15 assorted pots 75p; 15 assorted trimmers £1; Plug in relay, 2500Ω 4c/o 25p; Crystal mic insert 40p; 4 x 80V 10A recls. on heat sink, ideal batt. charger £1-20; SN75660N £1. Good range of close tolerance resistors—S.A.E. list.

SCREWS

WASHERS, NUTS, ETC.

BARGAIN PACK FOR HOME CONSTRUCTOR

100 assorted steel screws, nuts and washers—various BA sizes and lengths—all plated for rust prevention £1-50 or 10 bargain packs for £13-50.

Packs of 10 individual parts:


Length	2BA	4BA	6BA
1/4in.	10p	7p	7p
1/2in.	10p	8p	8p
3/4in.	12p	10p	10p
Nuts	8p	7p	6p
S/p washers	2p	2p	2p
Washer washers	5p	5p	4p

Also available 10A terminal blocks 3-way moulded pvc 250V a.c. wkg. 10p each. Panel mounting variable transformers 0-9A output complete with knob and dial, £7-50 each. Terms: C.W.O. only, P. & P. 20p up to £5; 50p up to £10; 75p above £10. Please add 8% VAT to total. Phone: 023-063 542.

INSTRUMENT ENGINEERING

High Street, Riseley, Bedford, MK44 1DX

NEW! V.H.F. FRONT END/CONVERTOR

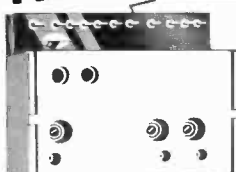

- ADVANCED DESIGN
- DUAL-GATE MOSFET FIRST STAGE

COVERS: AIRCRAFT WEATHER SATELLITES AMATEURS VARICAP TUNED INPUT 118-150 MHz I.F. OUTPUT 10.7 MHz

A high performance front-end combining high gain with low noise factor (8dB typ.). Each unit is fully tested and aligned before leaving the factory.

PRICE **£10.90** (includes VAT and P. & P.)

Sole Agents: REEDHAMPTON LTD., 182-184 Addington Road, Selsdon, Surrey, CR2 8LB

Readout —

A SELECTION FROM OUR POSTBAG

Readers requiring a reply to any letter must include a stamped addressed envelope. We regret that we cannot answer any technical queries on the telephone.

Voice control

Sir,—I recently built the "Voice Operated Fader" described in your December 1973 issue of PRACTICAL ELECTRONICS. The fader worked quite well apart from one disadvantage. This was that when the unit operated, the signal from the deck was attenuated too much causing an unacceptable interruption in the music.

What was needed was some form of control over the level to which the music was attenuated. My first attempt at providing this is shown in Fig. 1. Although this enabled the final voltage level to which C5 charged and thus the level of attenuation, to be set, the rate of attenuation was markedly reduced. This was due to the operating point being at the top of the charging curve to C5.

After some thought the circuit shown in Fig. 2 was evolved. This operates as follows: Suppose VR2 is set so that its slider is at 2V and TR4 is turned on. TR4 collector will be at 0.8V and diode D1 reversed biased. Hence, IC1 pin 2 will also be at approximately 0.8V. When TR4 turns off, capacitor C5 charges through R7. When the voltage across C5 reaches 0.6V greater than VR2 slider, D1 begins to conduct. Further increase of the voltage across C5 has little effect on VR2 slider voltage due to its relatively lower impedance than R7 and R10 and therefore IC1 pin 2 remains, substantially at 2.6V.

The circuit effectively clamps the rising voltage on IC1 pin 2 (attenuation control input) at any level 0.6V higher than that set by VR2 slider without effecting the rate of rise and hence the rate of attenuation.

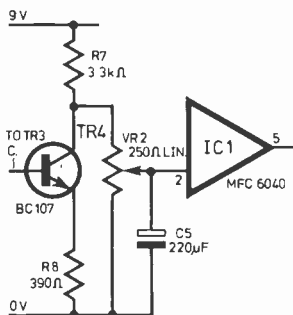


Fig. 1

Because of the increase in current due to R11 and VR2, R9 will need to be re-calculated to maintain the 9V supply rail.

J. H. Taylor,
Sunderland, Tyne & Wear.

So what!

Sir,—As a relative newcomer to P.E., I am amazed at some of the comments given with regard to electronically produced or synthesised music. I agree that some of the results are fairly hideous but I feel that some people allow their musical appreciation and technical ability to run away with common reasoning.

I speak as a fairly experienced D.J., also as a fairly experienced electrician dealing with radio/radar and so on in the aircraft industry. So what, if a machine is capable of producing over n thousand combinations of notes, etc. and only 100 of them are being used? So what, if a group chooses to use a simple application of £10,000 worth of electronic noise producing equipment? Surely, the general public have a say in the music that gets thrown at them. If they like a particular sound the record sales will reflect this; if it's not liked then it's tough luck on all concerned.

I suggest that if some of your readers are not satisfied with electronic music as it is now, they should make their own recordings, but I, as a D.J. do not relish the thought of playing "Handels Second Logical Computation" performed on an OC21! No sir, the proof of music is in its adaptation, not its rigid application.

M. D. Wells,
Hayling Island.

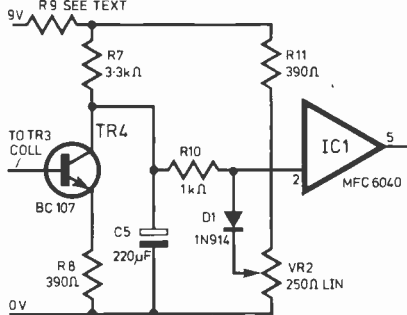


Fig. 2

"Borus-calculatii"

Sir,—With reference to the article *Mild & Bitter*—"The Pocket Calculator Bore" by A.P.S. in your May issue, may I shine a ray of hope by offering a partial solution to the problem.

Recent research in the north-west shows that there exists a mutation of Borus-calculatii-simplex known as Borus-calculatii-simplex-erroneous, a particularly virulent strain of which appears to originate from the Oxbridge area. As far as can be ascertained, the mutation arose—through no fault of the Fish Fryer's Association—from the consumption of questionable chips.

The strain can be readily discerned. On being approached the challenge "0-3.5=K8+" is given. If the reply "-2.285714" is obtained, then the menace is of the normal strain. If however, the reply is "0.6530612" then the mutant strain has been identified and isolated.

Now for the annihilation of the pest. Leaving the constant of -3.5 still set, ask the menace to perform $8.0 \div 9$ and $9.0 \div 9$ and closely observe his face. There should be some reddening accompanied by bulging of the eyes and general emission of steam. It is of the essence to move quickly at this stage before the blood pressure has a chance to subside.

The next step is to present the sequence "0-3 = K36998784" which will give "26972112" instead of "-8990704". Tension will be mounting at this point so step back two paces and ask that 10^{-12} should be added to, or subtracted from, 10^{+50} . This final operation will almost certainly cause the simultaneous bursting of several major blood vessels, which, according to my calculator, should leave the world one (or is it minus six) Borus-calculatii-simplex-erroneous fewer.

R. Lane,
Glossop, Derbyshire.

Moving speech

Sir,—In your article "Loudspeaker Breakthrough", published in the May edition, the author comments that C. W. Rice and E. W. Kellogg invented what is now known as the "moving-coil" or dynamic speaker "almost forty years ago".

It was in fact ten years earlier—nearly Half A Century ago—in the mid-twenties (not the thirties), when the R.K. was offered to the public.

The original production models were all energised from a low-voltage source (a car accumulator!), and in a 1929 wireless catalogue now in our archives, they are advertised side by side with balanced-armature cone units, and even horn-speakers!

Douglas Byrne, G3KPO,
The Wireless Museum,
Shanklin, I.o.W.

Sixth Sense, or Nonsense

Sir—Experiments with plants were reported by Mr Patrovsky (Readout, January 1975), in which he was able to speed germination and growth rate using either a magnetic field, hand movements of water acted upon by a magnetic field. He felt that the mechanism concerned was "polarisation" of water.

There have been many experiments of this nature around the world and some have yielded inexplicable results. A non-technical account of the whole subject can be found in "The Secret Life of Plants" by Peter Tomkins and Christopher Bird; a fascinating book.

One such experiment involved irradiating vermiculite using some kind of electronic apparatus. The vermiculite, which is an entirely inactive substance, was mixed with the earth in which plants were grown, and resulted in some 186 per cent increase in weight of those with irradiated vermiculite over the rest. The whole system was handed over to a commercial firm which tried it out and achieved no increased weight in their plants whatever. Later the original experimenters themselves (the De La Warrs) repeated the firm's trials at their nurseries and again showed increased growth. Finally, they supplied interested nurserymen with two lots of vermiculite. One was irradiated, and so labelled, and the other not. Again, increased growth was found in the plants grown with the irradiated vermiculite. The interesting part of this last experiment was that the De La Warrs in fact did nothing at all to either lot of vermiculite.

If Mr Patrovsky were to repeat his experiments by getting some other person to do them, and supplied him with two lots of water, one "polarised" and the other plain, and so labelled, the same increase in growth would most probably be observed even if nothing at all had been done to either supply of water.

The mechanism of this form of communication with plants is entirely unknown and it does the advancement of knowledge in this sphere a disservice by trying to tie it to magnetism, polarisation, radiation or any other well established physical process. Anyone doing so will be assumed by scientists to be either a charlatan or a fool.

That plants take heed of some as yet inexplicable message delivered to them can also be shown by a change in electrical resistance between two points, say, on a leaf, and lie detectors have been used to show it. This involves passing a current through the leaf and is

therefore suspect. Similar results have been obtained, however, using an electrocardiograph, which is a recording millivoltmeter capable of showing changes of a millivolt or two. Mr Baily reported the same kind of result in "ESP" (April 1974) using a voltage controlled oscillator as an indicator.

When life first started on this planet there must have been a time when there was a little chunk of something different from every other little chunk because it was living. It absorbed energy and nourishment from its surroundings and became larger. A time came when its bulk, and therefore the ratio between mass and surface area, became too large, so it divided into two smaller chunks, to be able to absorb essential nourishment more easily. The two may well have remained in contact. The process must have repeated itself countless times with the formation later of separate chunks of living matter. It was obviously advantageous for each chunk to maintain some kind of communication with its neighbours, and it is reasonable to assume that such communication existed, and that every chunk of life in a group communicated with every other chunk. As the number of living organisms increased and different types started to appear, such universal communication would have become impossibly complex and no longer advantageous. So presumably links between separate organisms grew less generalised. Links between parts of the same organism became highly specialised and ultimately in animals, as distinct from vegetables, formed the nervous system.

If human imagination can accept the possibility of a perhaps fortuitous grouping of atoms into molecules of some primitive form of protein from which we all have developed, it should not stretch that imagination beyond its limit to accept as possible that the remnants of this primitive form of communication exist still between humans and plants, and that it can be demonstrated by those with green fingers and possibly by all of us to some extent. If between humans and plants, then it would seem even more likely that it still exists between human and human. Telepathists and ju-ju witch doctors at least, would agree.

Mr Baily (ESP, June 1974) has described experiments where efforts have been made by thought alone to influence an electronic device producing random readings. If the communication system, whatever its mechanism, depends upon there being living tissue at both the sending and receiving ends, then such experiments are doomed to failure. This may not be so, in which case there is presumably another system or sense and the astonishing feats

of Uri Geller suggest that living tissue can have some kind of influence on inanimate material.

Any experiment to try to probe this almost entirely unexplained region should be as simple as possible. In Mr Russell's "Probability Anomaly Detector" (PE, Feb. 1975), supposing someone is found who can influence it, and that physical effects like hand capacity, static charge and so on can be eliminated, as well of course as chicanery, then one would still not be able to tell which part of it was being influenced.

A simpler system is needed. Such a system exists in the form of crystal growth, which some of us will remember from early chemistry days. A crystal of copper sulphate suspended by a strand of glass fibre in a saturated copper sulphate solution gradually grows larger as the water evaporates. It would be a simple matter to set up two equal crystals under identical conditions and try by will alone to influence the growth of one of them. Nothing could be more inanimate than copper sulphate. Perhaps something involved in animal metabolism would be more likely to be influenced. Glucose, urea or even common salt are possibilities.

This will not appeal to those who feel that electronics ought to be somehow involved. It may not perhaps be generally known that a neon lamp supplied with a voltage on the verge of its striking voltage can be triggered on by light, X-rays, cosmic rays and, who knows, Uri Geller and some of you, the readers—always assuming you have read this far. A possible device consists of a battery of about 180 volts with a 50 kilohm potentiometer across it. The voltage between the slider and one end is applied via a 0.25-0.5 megohm resistor to a 0.1 mf capacitor. The neon lamp, an Osrasm Osglim, is connected across the capacitor via a pair of headphones. The neon lamp is enclosed in a tin to avoid the effects of light and the potentiometer adjusted so that a few clicks are heard per minute in the headphones. These clicks are due to natural radiation.

A simple experiment might consist of setting the device to give an occasional click and at the start to press simultaneously a typewriter key and the start button of a stopwatch. At each click a letter would be typed and when the bell rang at the end of the line the watch would be stopped. If by willing the count rate to increase and decrease line by line alternately, a significant difference in time for alternate lines typed could be shown—then such a result would be utterly inexplicable but a basis for further experiment.

R. Parfitt,
Croydon.

NEW! SPACE AGE KITS

PRESENTING

THE WORLD'S FIRST LED DIGITAL WRIST WATCH KIT

SINGLE I.C. WATCH PROVIDES HOURS/MINUTES/SECONDS/DATE ON DEMAND—SAVES BATTERY POWER



ONLY **£36.50** Complete kit less band
+ £1.25 Airmail postage, insurance, etc.

THE LOWEST PRICE ANYWHERE

LOOK AT THESE AMAZING FEATURES!

- * Easy 3 button operation.
- * Easy to read LED display with anti-glare filter.
- * Displays hours, minutes, seconds and date on demand.
- * Crystal controlled accuracy, adjustable to 2 seconds or better per month.
- * Incorporates the latest in solid state technology.
- * Quality nickel-silver case included.
- * Detailed pictorial instructions supplied with every kit.
- * All parts included, except band.
- * Batteries included at no extra cost.
- * Batteries last up to one full year.

This kit not recommended for beginners

NOW YOU CAN BUY THE SPACE AGE WATCH OF TOMORROW—TODAY! You don't have to pay £150 for this amazing technological miracle. Order yours direct from the exporter and SAVE up to £112. NO MOVING PARTS—NOTHING TO WEAR OUT! Batteries last up to one full year and are widely available. SILENT OPERATION! BRIGHT LED DISPLAY visible in any light. Readout is on an on-demand basis. conserves battery power. SPECIAL INTRODUCTORY OFFER—ORDER YOURS NOW AND SAVE. Only £36.50 complete kit, less band. +£1.25 Airmail postage and insurance. ALL OTHER COUNTRIES U.S. \$90.00 postage and insurance paid.

The above prices do not include taxes leviable by a purchaser's country of residence

For your safety send all remittance via registered mail

Send payment with order (U.S. FUNDS only) BANK DRAFT or INTERNATIONAL MONEY ORDER (include receipt with order). Shipment made via first class airmail parcel within five days after receipt of order. Sorry no C.O.D.

DIRECT FROM THE U.S.

★ NEW ★

LOW COST DIGITAL MULTIMETER KIT

with features found only on more expensive types

NEW BRIGHT YELLOW 0.27in HIGH LED DISPLAY

EASY TO READ

BATTERY OPERATED · AUTO POLARITY · AUTO ZERO


D.C. VOLTS
1mV to 600V

A.C. VOLTS
1mV to 300V

OHMS
1Ω to 6MΩ

CURRENT
1μA to 2A d.c.
1μA to 300mA a.c. ONLY **£44.75**

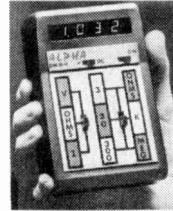Complete kit less batteries and test leads - £1.25 P & P and insurance



FEATURES

- * Automatic polarity automatic zeroing
- * Measures a.c. d.c. volts a.c. d.c. current resistance
- * Overrange indicated by blinking display
- * Easy to read 0.27in high yellow LED display
- * Anti-glare display filter
- * High-impact CYCOLAC case
- * High-Z input assures greater accuracy
- * Battery operated, Ni-Cad or regulator (4 - penlight size)
- * Small size (5 1/2in L x 3 3/8in W x 1 1/2in H) light weight
- * Complete easy to assemble kit (except batteries and test leads)
- * Detailed illustrated instructions supplied with each kit

TECHNICAL SPECIFICATIONS

D.C. VOLTS 1mV-600 volts in three ranges Accuracy better than 0.1% on 3- and 30-volt ranges 1% on 300- and 600-volt ranges Input resistance 10MΩ on all ranges
A.C. VOLTS 1mV-300 volts in three ranges 0-full scale voltage between 40 and 100Hz 0-2.4V between 100Hz and 50kHz Accuracy within these limits ±1% Input imp. 10MΩ
D.C. CURRENT 1μA to 2A in three ranges Accuracy 1% on all ranges
A.C. CURRENT 1μA to 300mA in three ranges Accuracy and frequency same as for a.c. volts
RESISTANCE 1Ω to 6MΩ in three ranges Accuracy 0.1%
ORDER YOURS NOW! SPECIAL INTRODUCTORY OFFER FOR A LIMITED TIME ONLY! Only £44.75 - £1.25 Airmail postage and insurance (batteries and test leads not included in kit)
ALL OTHER COUNTRIES U.S. \$100.50 post paid

New calculator ICs/lower prices from Thurlby

Increasing demand for the XE series high performance calculator chips has resulted in increases in scale allowing us to offer even better value for money.


Thurlby Electronics offer you the opportunity to build yourself an advanced electronic calculator at amazingly low cost using one of the XE series MOS single chip calculator I.C.'s.

Every IC is brand new, tested and guaranteed. It comes complete with full data, circuit diagrams and wiring details covering the use of different types of displays, describing how to construct both very simple and more elaborate keyboards, and explaining the operation of the calculator - both in normal calculations and in more complex operations.

Full money back refund.
Cash with order.
Postage and packing 25p per order.
Please add 8% VAT to total order value.

XE303 Calculator IC

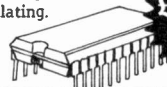
- New XE303 series with memory and %
- 5 functions, + - x ÷ with automatic constant facility on all 4 plus live % key.
 - Full performance memory, store-recall-exchange, or automatic accumulating.
 - Full 8 digits with floating decimal point and algebraic logic
 - Built-in clock generator, single power supply.
 - Direct segment drive, suppression of non-significant zeros.



£3.25 + VAT

XE202 Calculator IC

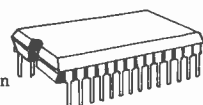
- XE202 series 4 function and constant
- Full 8 digits with floating decimal point and algebraic logic
 - Powerful keyed constant facility on all 4 functions
 - Enormous exponent range: 10⁻²⁰ to 10⁺⁷⁹
 - Single strobe line facilitates very simple keyboard construction
 - Direct segment drive, suppression of non-significant zeros



£2.25 + VAT

Display driving interface chips

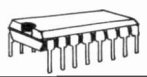- TK9 9 digit driver IC suitable for use with XE303 series. 95p + VAT
7105 8 digit driver IC suitable for use with XE202 series. 75p + VAT



Special magnified LED displays

- 9 digit suitable for use with XE303 series. **£3.75 + VAT**
8 digit suitable for use with XE202 series. **£3.25 + VAT**



To Thurlby Electronics Church Farm House Church End, Over Cambs. CB4 5NH

Please supply for which I enclose cash/cheque/PO for £ _____ including VAT & postage


Name _____

Address _____

ALL OUR PRICES INCLUDE V.A.T.

BSR HI-FI AUTOCHANGER STEREO & MONO

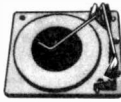Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250V. Size 13" x 11 1/2". Above motor board 3 1/2". Below motor board 2 1/2".



with STEREO and MONO XTAL £9.25 Post 45p.

PORTABLE PLAYER CABINET

Modern design. Rexine covered. Large front grille. Lift-up Lid. Chrome fittings. Approx. size 17 1/2" x 15 1/2" x 7 1/2". Few only in red and black rexine. Motor board cut for Garrard deck £5.25 Post 50p

BSR JUNIOR SINGLE PLAYER

Heavy duty 4-speed motor with separate pick-up arm fitted. L.F. 78 turnover mono. £4.95 Post 25p compatible cartridge.



R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop. Compatible cartridge. Baseplate. Size 11in x 8in. Turntable. Size 7in diameter. A/C mains. 200/250V motor has a separate winding 14 volt to power a small amplifier. Three speeds. Plays all records.

£6.95 Post 35p

SOLID MAHOGANY PLINTH

With P.V.C. Cover. Cut out for most B.S.R. or Garrard decks. Size 12" x 14" x 7 1/2".

Post 75p £7.50

COMPLETE STEREO HI-FI SYSTEM

Two full size loudspeakers 13 1/2" x 10" x 3 1/2". Player unit clips to loudspeakers making it extremely compact, overall size only 13 1/2" x 10" x 8 1/2". 3 watts per channel, plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls.



Attractive Teak finish Weight 13 lb.

Bargain Price £29 85p Carriage

SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH 0 TO 60 MINUTES



Single pole two-way Surface mounting with fixing screws. Will replace existing wall switch to give light for return home. Garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Fully insulated. Makers' last list price £4.50. Brand new and fully guaranteed.

OUR PRICE £2.50 Post 35p

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2in sides 8 x 4in 45p; 8 x 4in 53p; 10 x 7in 65p; 12 x 8in 85p; 14 x 9in 90p; 16 x 9in 90p; 12 x 3in 50p; 13 x 10in £1. ALUMINIUM PANELS 18 s.w.g. 8 x 4in 12p; 8 x 6in 19p; 14 x 3in 20p; 10 x 7in 24p; 12 x 5in 25p; 12 x 8in 34p; 16 x 6in 34p; 14 x 9in 40p; 12 x 12in 47p; 16 x 10in 60p. 1 1/2 inch DIAMETER WAVECHANGE SWITCHES. 45p ea. 2 p. 2-way, or 2 p. 2-way, or 3 p. 4-way. 1 p. 1. 2-way, or 2 p. 2-way, or 3 p. 4-way. TOGGLE SWITCHES. sp. 20p; dp. 25p; dp. dt. 30p.

BRITISH FM/YHF TUNING HEART

88 to 108 Mc/s British made. 2 Transistors ready aligned requires 10-7 Mc/s L.F. Complete with tuning gang. Connections supplied but some technical experience essential.

Our price £3.95 Post 20p

SUITABLE I.F. STRIP £4.95. DECODER £4.95

R.C.S. STEREO FM TUNER BRITISH MADE



This completely cased mains powered Hi-Fi Tuner with brushed aluminium fascia is British made using the latest circuitry. £30 Post 45p.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12V or H.T. line 200-300V d.c. operation. Size: 1 1/2 x 1 1/2 x 1 1/2 in. Response 25 c/s to 25 kc/s. 26 dB gain. For use with valve or transistor equipment. Full instructions supplied. Details S.A.E. £1.45 Post 10p

R.C.S. POWER PACK KIT

12 VOLT, 750mA. Complete with printed circuit board and assembly instructions. £3.25 Post 35p
12 VOLT 300mA KIT, 23 9 VOLT 1 AMP KIT, 23.25.

NEW TUBULAR ELECTROLYTICS		CAN TYPES	
2/350V 14p	250/25V 14p	50+50/300V 50p	
4/350V 14p	500/25V 20p	32+32/350V 35p	
6/350V 22p	100+100/275V 70p	32+32/450V 60p	
18/350V 30p	150+200/275V 70p	350+50/325V 55p	
32/500V 50p	8+8/450V 22p	16+16+16/275V 45p	
25/25V 10p	8+16/450V 22p	32+32+32/350V 65p	
50/50V 10p	16+16/450V 40p	800/350V 95p	
100/25V 10p	32+32/350V 40p	4700/63V 95p	

LOW VOLTAGE ELECTROLYTICS.
1. 2, 4, 6, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 20p; 50V 30p.
1000mF 12V 20p; 25V 35p; 50V 47p; 100V 70p.
2000mF 6V 25p; 25V 42p; 50V 57p.
2500mF 50V 62p; 3000mF 25V 47p; 50V 65p.
5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p.
CERAMIC 1pF to 0.01mF, 4p. Silver Mica 2 to 5000pF, 4p.
PAPER 350V 0.1 7p; 0.5 18p; 1 15p; 2 15V 15p.
500V 0-001 to 0-05 4p; 0-1 10p; 0-25 8p; 0-47 25p.
TWIN GANG. "0-0" 208pF + 176pF, £1.20p.
Slow motion drive 365pF + 365pF with 25pF + 25pF, 50p;
Twin 500pF 75p, Twin 410pF 50p, Twin 120pF 50p.
SHORT WAVE SINGLE. 25pF, 45p; 50pF, 55p.
NEON PANEL INDICATORS 250V AC/DG. Amber 30p.
RESISTORS. 1W, 1/4W, 1W, 20%; 1/2W, 10%; 10W, 10% to 10M.
HIGH STABILITY. 1W 2%, 10 ohms to 6 meg., 10p.
Ditto 5%. Preferred values 10 ohms to 10 meg., 4p.
WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 10p each.
TAPE OSCILLATOR COIL Valve type 35p.
FERRITE ROD 8 x 1/2in 20p; 6 x 1/2in 20p; 3 x 1/2in 10p.

MAINS TRANSFORMERS ALL POST 45p each

250-0-250 80mA. 6-3V 2 amp £2-80
350-0-350 80 mA. 6-3V 3-5A 6-3V 1A or 5V 2A £4-60
350-0-350 80 mA 6-3V 3-5A 6-3V 1A or 5V 2A £5-80
800-0-800 120mA. 6-3V 4A C.T. 6-3V 2A £7-00
MIDGET 220V 45mA. 6-3V 2A 2 1/2 x 2 1/2 in. £1.25
HEATER TRANS. 6-3V 1 amp 85p, 3 amp £1.40p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V £4-80
1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £4-60
2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £7-00
5 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £11-25
10, 30, 40V 2 amp. £2.50; 20V 3 amp. £2.30. 5, 8, 13V, 5 amp. £1.50; 6-0-6V 500mA 90p; 9V 1 amp. 95p; 12V 300mA 75p; 12V 500mA 85p; 12V 750mA 95p;
40V 3 amp. £2.75; 22-0-22V 4 amp. 23.45; 16V 1 amp. 95p;
16V 2 amp. £2.5V, 8V, 10V, 16V 1 amp. £1.90.
AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 150W £4-60; 500W £8-70; 750W £17-50; 1000W £21.
CHARGER TRANSFORMERS. 200/250V, 4 amp £4-00.
BATTERY CHARGERS. Ready built with leads and clips, 4 amp £4; 5 amp. £4-60.
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs. 1 1/2 amp 40p; 2 amp 55p; 4 amp 85p.

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V 3 amps 720 watts. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. Famous make (Value £18) OUR PRICE £13.50 Carr. 95p
Can be used as 800 watt auto transformers 240-110V.

VOLUME CONTROLS

Long spindles. Midget Size 5 K ohms to 2 Meg. LOG or LIN. L/S 20p. D.P. 35p. STEREO L/S 55p. D.P. 275p. EDGE 5K. S.P. Transistor 25p.

80 ohm Coax 5p yd.

BRITISH AERIALITE AERAXIAL-AIR SPACED 40 yd £2-00; 60 yd £3-00. FRINGE LOW LOSS 10 p yd Ideal 825 and colour.

Wire Wound controls 1 1/2in diam. 3 Watts. 10 ohms to 100K British Made with long spindle 1in dia. 35p each.
DUAL CONCENTRIC POT 500K LOG AND 500K LIN D.P. switch. Inner spindle 3 1/2in; outer spindle 2 1/2in 75p.

E.M.I. 13 1/2 x 8in. SPEAKER SALE!

With tweeter and crossover. 10 watt. Size 3 or 8 or 15 ohm. As illustrated. Post 35p



With flared tweeter cone and ceramic magnet. 10 watt. Bass res. 45-60 c/s. Flux 10,000 gauss. Size 3 or 8 or 15 ohm. Post 25p

13 1/2 x 8in Bass unit 20 watt rubber cone surround £6-60

LOUDSPEAKER FRONT GRILLES

Teakwood strips mounted on cloth backing, easily glued on to baffle to modernise cabinets. Size 18 1/2 in x 10 1/2 in. 75p Or size 10 1/2 in x 7 1/2 in. 45p

E.M.I. 6in. HI-FI WOOFER

8 ohm. 10W. Large ceramic magnet. Special Rubber cone surround. Frequency response 30-12,000 c/s. Ideal P.A. Columns. Hi-Fi Enclosure Systems, etc. £4.60



ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 18,000 c/s. Size 3 1/2 x 3 1/2 in deep. Rating 10W. 8 ohm. Crossover £1-85 £2.20 Post 30p.

GOODMANS 8in. WOOFER

8 ohm 12 watt. Deep cone. Heavy ceramic magnet. Bass frequency response 30-12,000 c/s. Frequency response 30-8,000 cps. Ideal bass unit for Hi-Fi system. £4.35



SPECIAL OFFER LOUDSPEAKERS

3 ohm, 2 1/2in; 2 1/2in; 3 1/2in; 5in; 7 x 4in; 8 x 6in. 8 ohm, 2 1/2in; 2 1/2in; 3 1/2in; 5in; 7 x 4in; 8 x 4in. 15 ohm, 3 1/2in; 5in; 6 x 4in; 5 x 3in; 7 x 4in; 8 x 5in. 25 ohm, 2 1/2in; 5 x 3in; 5in; 6 x 4in; 7 x 4in. 35 ohm, 3in; 6in. 80 ohm, 2 1/2in; 2 1/2in. 120 ohm 3in. £1.25 EACH

RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8in diameter 4W £2-50, 10 in diameter 5W £2-95; Post 25p 12in diameter, 6W, £2-50; 3 or 8 or 15 ohm models. SPEAKER COVERING MATERIALS. Samples L.A.S.E Horn Tweeters 2-16Kc/s. 8W 8 ohm or 15 ohm £2-50 De Luxe Horn Tweeters 2-16Kc/s, 15W, 15 ohm £4-50 TWO-WAY 3,000 c.p.s. CROSSOVERS 3, 8 or 15 ohm £1-85

CASSETTE MACHINE MOTOR. 6 Volt.

Will replace many types £1.25.

R.C.S. 3 WAY CROSSOVER

Complete with 12 ft. twin lead fitted with dim speaker plug. Ready assembled with leads for speakers, bass, mid and tweeter. Crossover frequencies—950 cps and 3,000 cps. £2.25

VALVE OUTPUT TRANSFORMER 50p. MIKE TRANSFORMER MU metal 100-£1.25. PUSH-PULL VALVE OUTPUT TRANSFORMERS. 50 watt £21-00 100 watt £20-00

ELECTRO MAGNETIC PENDULUM MECHANISM

1.5V d.c. operation over 200 hours continuous on 8P9 battery, fully adjustable swing and speed. Ideal display, teaching electro magnetism or for metronome. 95p Post 20p

R.C.S. RECORD PLAYER AMPLIFIER

2 Stage triode pentode valve. 3 watts output. Volume on/off and tone control. Printed circuit £4.50 Post 85p Complete with speaker.

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18 OUTLET BOXES, SURFACE MOUNTING 50p. BALANCED TWIN RIBBON FEEDER 300 ohms, 7p yd. JACK SOCKET 8in. open-circuit 20p. closed circuit 30p; Chrome Lead Socket 45p. Phono Plugs 7p. Phono Socket 7p. JACK PLUGS 8in. Chrome 30p; 3-5mm Chrome 20p. DIN SOCKETS Chassis 8-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 25p; 5-pin 25p. DIN PLUGS 3-pin 25p; 5-pin 25p. VALVE HOLDERS 5p; CERAMIC 10p; CANS 5p.

ALL PRICES INCLUDE VAT • 30p MINIMUM POST AND PACKING • CALLERS WELCOME •

RADIO COMPONENT

Illustrated Brochure, Radio Books & Component Lists 10p Written guarantee.

ALL OUR PRICES INCLUDE V.A.T.

E.M.I. WOOFER AND TWEETER KIT

£6-75 THE PAIR, Post 45p. (Available separately. Woofer 24-25; Tweeter £1-90)

Comprising a fine example of a Woofer 10 1/2 x 6 1/2 in with a massive Ceramic Magnet, 440z Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2 in square has a special lightweight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.

Impedance Standard 8 ohms
Maximum power 12 watts
Useful Response 35 to 18,000 cps
Bass Resonance 45 cps
SUITABLE ENCLOSURE 20 x 18 x 1 1/2 in.
MODERN DESIGN. TEAK WOOD FINISH.



£14
Post 75p

ANOTHER R.C.S. BARGAIN!

ELAC 9 x 5 in. HI-FI SPEAKER TYPE 59RM
This famous unit now available, 10 watts, 8 ohm.

Price **£3-45** Post 30p



8" or 10" x 6" ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-18,000 cps. Bass resonance 55 cps. 8 ohm impedance. 10 watts.

£4-35

10 in round **£5.**

TEAK VENEER HI-FI SPEAKER CABINETS

Fluted Wood Fronts
MODEL "A". 20 x 18 x 12 in
For 12 in. dia. or 10 in speaker. **£14** Post 75p

MODEL "B". 18 x 10 x 7 in
For 13 x 8 in. or 8 in. speaker **£7-60** 45p

MODEL "4C". 30 x 20 x 12 in.
Reflex cabinet will accept 1-12 in. bass unit, 1-5 in. mid range, 1-3 in. tweeter. Teak finish. Grooved front. **£21-50** 25p

LOUDSPEAKER CABINET
WADDING 18 in wide, 20p ft.




GOODMANS CONE TWEETER

3 1/2 in. diam. 18,000 C.P.S. 25 WATTS 8 ohm **£3-60**

BARGAIN 4 CHANNEL TRANSISTOR MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated. **£5-20**

STEREO VERSION OF ABOVE **£6-85.**
BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. Mains Supply **£3-45.**

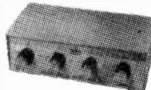THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER. Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E. **£4-35** Post 20p



WAFER HEATING ELEMENTS


OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse factory (available in manufacturing quantities) Approx size 10 1/2 x 8 1/2 x 1/2 in. Operating voltage 200/250V, a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photocopiers and print drying equipment.

Ideal for home handymen and experimenters. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryers, towel rails—ideal for airing cupboards. Ideal for anti-iron device for the garage—preventing frozen radiators or acting as oil sump heater. Use in greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY **40p EACH** (FOUR FOR **£1-50**)

ALL POST PAID—Discounts for quantity.

BAKER MAJOR 12" £11-50

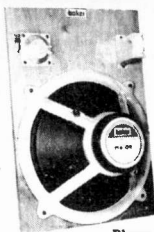

30-14,500 c/s, 12 in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s Rated 20 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£14-50**

Please state 3 or 8 or 15 ohms.

BAKER SPEAKERS "BIG SOUND"

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass Resonance 55 cps.

GROUP "25"

12 in 25 watt 3, 8 or 15 ohms.

£9-50

Post 40p

GROUP "35"

12 in 35 watt 3, 8 or 15 ohms.

£11-50

Post 40p

GROUP "50"

15 in. 50 watt 8 or 15 ohms.

£22

Post 50p

GROUP "50/12"

12 in 50 watt professional model. 8 ohms or 15 ohms

£16



MAJOR 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm a.c. Mains. Separate treble and bass controls. Guaranteed. Details S.A.E.

£59 Carr. £1-00




DE-LUXE MODEL IN WOOD CABINET. BLACK. **£69.**

NEW MODEL MAJOR 50 WATT

4 inputs, 2 way mixing, £49-95. Carr. £1. Ideal disco amp.

QUALITY LOUDSPEAKER ENCLOSURE

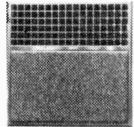Teak veneered jin thick wood cabinet. Size 18 1/2 in x 18 1/2 in x 8 1/2 in. Weight 23lb. This cabinet features a wide mesh Silver Grill covering a separate compartment for mounting Tweeters or Mid-Range Horn. The fully sealed bass compartment is cut out for 6 1/2 in Woofer. £28-50. Carr. 85p. Rosewood Version £29-50. Carr. 85p. Baffle could be cut for larger speaker.



SPECIAL OFFER 95p. Post 25p. 100 Ohm 20 watt Rheostat 2 1/2 in dia. Ceramic Former. Screw Terminals jin. dia. spindle.

R.C.S. STEREO DECODER

British made. Ready aligned and tested. Complete with instructions. Size 3 in x 2 in. **£4-95**

WEYRAD COILS

P50/2CC	40p	RA2W	85p
P50/1AC	80p	OFT1	85p
P50/3CC	40p	LFTD4	85p
PCAI	85p	Twin gang	£1-20

DELUXE 4 POLE MOTOR

1,400 r.p.m. reversible 42 Watt, spindle 1 1/2 in x 7/32 in, size 3 1/2 in x 3 in. As illustrated. 240V a.c. mains. **£2-60** Post 25p

E.M.I. GRAM MOTOR

120V or 240V a.c. 2,400 rpm. 2-pole 70mA. Size 2 1/2 x 2 1/2 in. **£1-25** Post 25p



BAKER HI-FI SPEAKERS HIGH QUALITY—BRITISH MADE REGENT

12 in. 15 watts

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to improve any Radio, Amplifier, Hi-Fi or Television receiver.

Bass Resonance 45cps
Flux Density 12,000 gauss
Useful response 45-13,000cps
3 or 8 or 15 ohm models.

£9-50 Post 40p

DE-LUXE Mk II

12 in. 15 watts

Especially designed to provide full range reproduction at an economical cost. Suitable for use with any high fidelity system. Built-in concentric tweeter cone.

Bass Resonance 30cps
Flux Density 14,000 gauss
Useful response 25-18,000cps
8 or 15 ohms models.

£12-50 Post 40p

SUPERB

12 in. 20 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.

Bass Resonance 25cps
Flux Density 18,500 gauss
Useful response 20-17,000cps
8 or 15 ohms models.

£17 Post 50p

AUDITORIUM

12 in. 25 watts

A full range reproducer for high power, Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Discotheques.

Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 25-16,000cps
8 or 15 ohms models.

£16 Post 50p

AUDITORIUM

15 in 35 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home Hi-Fi.

Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 25-14,000cps
8 or 15 ohms models.

£22 Post 50p

Hi-Fi Enclosure Manual containing plans, designs, crossover data and cubic tables. 68p.

CUSTOMERS FREE CAR PARK

OPEN 9-6 p.m. WEDNESDAYS 9-1 p.m., SATURDAYS 9-5 p.m. (Closed for Lunch 1.15-2.30)

SPECIALISTS 337 WHITEHORSE ROAD · CROYDON

(Export: Remit cash and extra postage.)

Buses 50, 68, 159. Rail Selhurst

Telephone 01-684-1665

BIG Discounts



SPEAKER BARGAINS		£		
P. & P. 40p per speaker.				
EMI 13in x 8in 3 or 8 ohm				
Plain	2-20		8in x 5in, Dual cone 8 ohm, 10W	2-55
With Co-Axial Tweeter 8 ohm only	2-30		ELAC 6 1/2in 8 ohm Dual cone	2-25
With Tweeter and Crossover 3, 8 or 15 ohm	3-95		ELAC 8in 8 ohm Dual cone	2-50
Type 350, 8 ohm, 20W	7-95		ELAC 10in 8 ohm Dual cone	3-50
6 1/2in, 8 ohm, 10W	2-80		ADASTRA 10in, 8 or 15 ohm, 10W	3-55
8in, 8 ohm, 10W	4-50		BAKER GROUP 25 12in, 8 or 15 ohm, 25W	7-95
8in x 5in, C/Mag. 5W, 3, 8 or 15 ohm	1-40		The following, P. & P. 15p per speaker	
TWEETER AND CROSSOVER				
10me Tweeter 8 ohm, 30W				
One Tweeter 8 or 15 ohm, 10W	2-80		3in, 8 ohm, C/Mag.	0-85
One Tweeter 8 ohm, 3W	1-45		2 1/2in, 8 ohm or 64 ohm	0-55
Horn Tweeter 8 ohm, 20W	6-40		7in x 4in, 3 or 8 ohm	1-00
KIT FORM CABINETS, TEAK VENEER.				
12in x 12in x 6in with 8in, 8in x 5in or 6in and 3 1/2in cutout				
17in x 10in x 9in with 8in or 13in x 8in cutout	3-50		10me Tweeter 8 ohm, 30W	5-60
MICROPHONES				
CM70 Planet stick metal, switch crystal				
DM160 Dynamic omni-dir. ball metal	4-90		Crossovers CN23 (3 ohm), CN28 (8 ohm), CN216 (16 ohm)	1-30
UD130 50K/600 ohm, uni-dir. ball metal	6-40			P. & P. 0-15
UD147	8-95			
SOLDERING IRONS				
ANTEX CN240 15W				
SK1 Kit (15 watt iron, 2 spare Bih, etc.)	2-10			3-40
CARTRIDGES AND STYLII				
ACOS GP91/28C or 38C Stereo comp.				
GP93/1 or 95/1 Stereo crystal	1-50		SONOTONE 9TAHC or 9TAHC/G diam.	2-00
GP94/1 or 96/1 Stereo ceramic	1-85		3509 Stereo ceramic diam.	2-00
GP101 Crystal comp.	0-80		GOLDRING G850	3-25
GP104 Stereo ceramic	1-95		G800	4-10
BSR X3M or 5XH Crystal comp.	1-95		G800E	7-10
8X6M or 8X6H Crystal comp.	2-00			P. & P. 0-15
SC5M Stereo ceramic	2-75		D. Diamond Stylil for above	1-25
BATTERY ELIMINATORS				
240V input 6, 7.5 or 9.300mA				
	2-95		G800E	3-95
TAPES				
5in	50p	1P	5in Reels 18p, 5 1/2in 22p, 7in 25p	4-25
7in	85p	80p		P. & P. 0-15
	80p	1-10p		
LOW NOISE CASSETTES				
C80	1-5	6-10		4-25
C90	35p	33p		P. & P. 0-05
C120	85p	43p		0-20
	75p	52p		
BIB ACCESSORIES				
Tape Editing Kit, Ref. 23				
Recording Tape Splicer, Ref. 20	1-35			0-35
Cassette Tape, Editing, Ref. 24	1-50			0-20
Cassette Salvage Kit, Ref. 29	0-45			
Stylus Balance, Ref. 32A	1-20			
Spirit Level, Ref. 46	0-65			
Hi-Fi Stereo Test Cassette	2-20			
Groove-Kleen Record Cleaner	1-90			
	P. & P. 0-15			
WHARFEDALE SPEAKER BARGAINS				
Linton 2 Kit (pr.)				
Glendale 3 Kit (pr.)	1-35			19-95 1-50
Dovedale 3 Kit (pr.)	1-20			33-50 2-00
Denton 2 Speaker (pr.)	0-65			52-00 2-00
Linton 2 Speaker (pr.)	1-20			30-00 2-50
Dovedale 3 Speaker (pr.)	1-90			39-50 2-50
Glendale 3 Speaker (pr.)	1-90			42-00 2-50
Kingdale 3 Speaker (pr.)	1-90			57-00 3-50
	P. & P. 0-15			59-95 4-00

VAT AT THE CURRENT RATE MUST BE ADDED TO ALL ORDERS
Send 25p for COMPLETE CATALOGUE, refundable upon first order.
ALL OUR MERCHANDISE IS FULLY GUARANTEED
Subject to manufacturers' increase and availability

Riversdale Electronics
Mail Order Department PE7
P.O. Box 470, Manchester M60 4BU

CJL PRICES INCLUDE P&P AND V.A.T.

BIB HI-FI ACCESSORIES

CASSETTE TAPE RECORDER CARE KIT	£1.95
CASSETTE SPLICING AND EDITING KIT	£1.50
HI-FI STEREO TEST CASSETTE	£2.10
1/4" TAPE EDITING KIT	£1.35
GROOV-KLEEN RECORD CLEANER	£1.85

COMPONENT PACKS

CAPACITORS-Electrolytic-Tubular Submin-Mixed	£0.50
CAPACITORS-P.C.B. Polyester-Mixed Preferred	£0.50
RESISTORS-Carbon Film-Mixed Preferred	£0.50
POTENTIOMETERS-Midget Carbon Track-Mixed	£0.50
EARPHONE, stethoscope style, 8 ohm dynamic	£1.00
HAND DRILL, (Leytool), compact precision drill, 5/16" chuck. Gears totally enclosed. S/L bearings	£2.99

INTEGRATED CIRCUITS

AUDIO POWER AMPLIFIER (National) LM380	£1.00
A.M. RADIO RECEIVER (RCA) CA3123E	£1.40
F.M. STEREO DECODER (Motorola) MC1210P	£2.80
TIMER (Signetics) NE555V	£0.78
VOLTAGE REGULATOR (Fairchild) UA7805	£1.70
VOLTAGE REGULATOR (Signetics) NE550A	£0.80
D.I.L. SOCKETS (Pk of 3) 8 or 14 pin	£0.50

KEYNECTOR, rapid connect to mains-single/multiple leads. Built-in piano switches, neon & 13A fuse	£3.20
LOCKFLEX RULE, (Rabone Chesterman), 3m/10ft precision pocket rule. Easy to read, 13mm/1/2" wide steel tape. Blade length lockable-power return.	
A superb rule	£0.93

MICROPHONE, lightweight dynamic, remote start stop, 200 ohms, 100-10KHz, 6mV average output	£1.80
SIGNAL INJECTOR, audio through video signals, excellent for servicing amplifiers, radio & tv	£3.92

SOLDERING IRON, 25 WATT, (Antex), X25, 240V, Very low leakage, 1/8" long life bit (Interchangeable)	£2.05
3/32" bit	£0.47
3/16" bit	£0.47
Element	£1.10

STAND, ST3, High grade base, chrome plated spring, sponges and accommodation for spare bits	£1.00
---	-------

CJL CJL LTD. P.O. BOX 34, CANTERBURY, CT1 1YT

DIGITAL CLOCK KITS SPECIAL OFFER

£2 OFF

USUAL PRICE (COMPLETE KIT)
EXCLUSIVE TO P.E. READERS

QUICK TO BUILD—NO KNOWLEDGE OF
ELECTRONICS REQUIRED

LATEST 1975 DESIGN—ONLY £14

(including P. & P., VAT. Circuit)

COMPARE OUR PRICES

	£
1 MOS Clock Chip 12-24 hr option	4.00
4 0.63" LED Displays (latest HI BRI Type)	5.00
1 Segment Driver Chip	0.30
1 Pack Resistors, Caps., Transistors, Switch, etc.	1.20
1 Double Sided Glass Fibre P.C. Board	1.00
1 Double-wound Mains Transformer	1.00
1 Circuit/Assembly Manual	0.50
1 Futuristically-styled Case (state colour)—Yellow, Orange, Red, Black, White, Mauve, Green, Blue	3.00

C.W.O. to:

Pulse Electronics Ltd



Dept. PE1, 202 Shefford Road, Clifton, Beds.
Tel. Hitchin (0462) 813453



RELAYS

SIEMENS, PLESSEY, Etc.
MINIATURE RELAYS

Col. (1) Coil ohms	1	2	3	4
Col. (2)	52	4-8	2 c/o	70p*
Working d.c. volts	58	5-9	6 c/o	80p
Col. 3	185	8-12	6M	60p*
Contacts	230	9-18	2 c/o	70p*
Col. (4)	430	15-24	4 c/o	80p*
Price	700	12-24	2 c/o	60p*
HD=	700	16-24	4M 2B	60p*
Heavy duty	1,250	18-36	2 c/o	60p*
	2,500	31-43	2 c/o	60p*
	2,500	36-45	6M	60p*
	9,000	40-70	2 c/o	60p*
	15k	85-110	6M	60p*

*Incl. Base. All prices incl. P. & P.

OPEN TYPE RELAYS

6 VOLT D.C. 1 make contacts 35p. Post 15p.

9 VOLT D.C. RELAY

3 c/o 5 amp contacts. 70 ohm coil. 75p. Post 15p.

12 VOLT D.C. RELAY

3 c/o 5 amp contacts. 120 ohm coil. 75p. Post 15p.

24 VOLT D.C. RELAY

3 c/o 5 amp contacts. Price 75p. Post 15p.

ENCLOSED TYPE RELAYS

24 VOLT D.C. 3 c/o 75p. Post 15p. Base 15p extra.

24 VOLT A.C. Mfg. by ITT. 3 h.d. c/o contacts.

55p. Post 15p. Base 15p.

55 VOLT A.C. RELAY

3 h.d. c/o contacts. Price 55p. Post 15p. Base 15p.

100 VOLT A.C. 3 c/o sealed type. 75p. Post 15p.

240 VOLT RELAY

3 h.d. c/o contacts. Price 75p. Post 15p. Octal plug in base 15p extra.

230/240 VOLT A.C. RELAY. Mfg. by Arrow 2 h.d.

15 amp c/o contacts. Amp connectors. Price £1.

CLARE-ELLIOTT TYPE RP7641 G8

Miniature relay. 675 ohm coil. 24 Volt D.C. 2 c/o.

70p post paid.

110V. 2 c/o. 20 amp contacts. £1.25. Post 10p.

Many others from stock—phone for details.

VERY SPECIAL OFFER

Honeywell Type N100

10A changeover micro switch.

10 for £2.50. Post 25p.



PUSH BUTTON

MICRO SWITCH. 5 amp. c/o

contacts. NEW. 20 for £2. Post

15p. (Min. order 20). Ditto press

to break, 20 for £1.50. Post 15p.



SUB-MINIATURE REED

RELAY 3-9V d.c. 250 ohm Coil

Single make, size 1 1/2 x 1/2 x 1/8 in.

Outstanding Value only

£1 for six, £1.50 for ten. Post 15p. (Min. order

six.)




LATCHING RELAY

Twin latching relay, "flip-flop" 2 c/o

each relay. Mains contacts. 115V

A.C. or 50V D.C. operation. 240V

A.C. with 2-5K resistor. 85p. Post 15p.

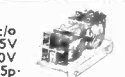

TRIAC

Raytheon Tag symmetrical Triac. Type TAG.

250/500V, 10 amp, 500 p.i.v. Glass passivated plastic

triac. Swiss precision product for long term

reliability £1.00. Post 10p. (Inclusive of Data and

application sheet.) Suitable Diac 18p.

230/250 VOLT A.C. SOLENOID

Approximately 1 1/2 lb pull. Size of feet 1 1/2" x 1 1/2".

Price £1.00. Post 15p.

24 VOLT DC SOLENOIDS

UNIT containing 1 heavy duty solenoid approx. 25lb

pull 1 inch travel. Two x approx. 1lb pull 1/2 inch

travel. 6 x approx. 4oz. pull 1/4 inch travel. One

24 volt d.c., 1 heavy duty single make relay. Price

£2.50. Post 75p. ABSOLUTE BARGAIN.

COIN MECHANISM (Ex London Transport)

Unit containing, selector mechanism for 1p, 2p and

5p coins. Micro switches, relays, solenoid operated

hopper. 24 volt D.C. Precision built to high stand-

ard. Incredible VALUE at only £2.50. Post 70p.

CENTRIFUGAL BLOWER

Mfg. Airflow Developments Ltd.

Precision continuously rated,

smooth running, 230/240V a.c.

motor 80 c.f.m. As illustration

but with round aperture. £6.50.

Post 50p.



VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT

VARIABLE 0-260V All Types

SHROUDED TYPE

200 watt (1 amp) £10.00

0-5 KVA (2 1/2 amp) (MAX) £11.50

1 KVA (5 amp) (MAX) £15.50

2 KVA (10 amp) (MAX) £30.00

3 KVA (15 amp) (MAX) £33.00

4 KVA (20 amp) (MAX) £60.00

37.5 amp (MAX) £102.50

CARRIAGE AND PACKING EXTRA

OPEN TYPE 1 amp (panel mount) £10.00



L.T. TRANSFORMERS

0, 6, 12 Volt at 10 amp. £5-60. Post 70p.

0, 10, 17, 18 Volt at 10 amp. £7-90. Post 70p.

0, 4, 6, 24, 32 Volt at 12 amp. £9-90. Post 70p.

0, 6, 12 Volt at 20 amp. £9. Post 70p.

0, 12, 24 Volt at 10 amp. £9-20. Post 70p.

0, 6, 12, 17, 18, 20 Volt at 20 amp. £10-40. Post 70p.

Other types to order at short notice—Phone your enquiries.

AUTO TRANSFORMERS

Step up step down

0-115/200/220/240 Volts. 75 watt £2-64. Post 40p.

150 watt £3-50. Post 50p. 300 watt £6-20. Post

60p. 500 watt £9-20. Post 75p. 1000 watt £12-00.

Post 90p.

REVERSIBLE MOTOR

A.E.I. 1/8 h.p. reversible motor 100/

120 volt A.C. 50/60 cycle 1400/1680

r.p.m. Flange frame. Dia. 4"

length 6 1/2", shaft 1" x 5/8". Brand

New. Price £2-50. Post 50p. Suit-

able 110/240V. 150 watt Auto Transformer £3 50.

Post 50p. (Post for both items together 75p.)



230/240 VOLT A.C. MINIATURE MOTOR.

20 R.P.M. Price £1. Post 15p.

BODINE TYPE N.C.I.

GEARED MOTOR

(Type J) 71 r.p.m. torque 10 lb. in.

Reversible 1/70th h.p. cycle 0-38

amp. (Type 2) 28 r.p.m. torque 20

lb. in Reversible 1/80th h.p. 50 cycle 0-28 amp.

The above two precision made U.S.A. motors are

offered in 'as new' condition. Input voltage of motor

115V A.C. Supplied complete with transformer for

230/240V A.C. input.

Price, either type £6-25. Post 65p or less trans-

former £3-75. Post 50p.



'FRACMO' 240 VOLT A.C.

50 CYCLE SINGLE PHASE


GEARED MOTOR

33 r.p.m. 30 lb. ins. Reversible.

Fitted with mounting feet.

Brand New. £14. Post £1.00.

(Total price incl. VAT £16-20).

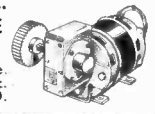

9-12 VOLT D.C. GOVERNED REVERSIBLE

MOTOR

Machine cut gear train, giving

final speed of 2 r.p.m. with cam


driving 3 sub-miniature micro-

switches (removable). Spindle

12mm long 6mm dia. Built to

PO spec., in heavy metal hinged

case. £3-75. Post 40p.

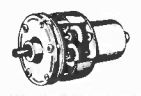

'CARTER' 230 VOLT A.C.


GEARED MOTOR

230/240V A.C., smooth, powerful,

continuously rated. Two types: 32

r.p.m. or 110 r.p.m. Either type

£4-50. Post 50p.

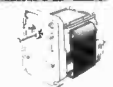

POWER RHEOSTATS !!!

Superior Quality Precision Made

NEW POWER RHEOSTATS

New ceramic construction, vitreous

enamel embedded winding, heavy

duty brush assembly, continuously

rated.

25 WATT 10/25/50/100/150/250/500/1k/1.5k/2.5k

ohm. £1-70. Post 15p.

50 WATT 15/10/25/50/100/250/500/1k ohm

£2-10. Post 20p.

100 WATT 15/10/25/50/100/250/500/1k/1.5k/2.5k/

3.5k/5k ohm £3-30. Post 25p.

Black Silver, Skirted knob calibrated in Nos. 1-9

1 1/2 in. dia. brass bush. Ideal for above 22p each.



VAT

VAT AT THE APPROPRIATE RATE

MUST BE ADDED TO ALL ORDERS

FOR THE TOTAL VALUE OF GOODS

INCLUDING POSTAGE.

SERVICE TRADING CO.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation. RANGE OF FOUR STROBE KITS FROM STOCK. PRICES FROM £6-30 to £22. S.A.E. for details.

BIG BLACK LIGHT

400 Watt. Mercury vapour ultra violet lamp.

Powerful source of u.v. P.F. ballast essential.

Price of matched ballast and bulb £21.

Post £1. Spare bulb £8. Post 40p.

BLACK LIGHT FLUORESCENT U.V. TUBES

4ft 40 watt, £5.50 (callers only).

2ft 20 watt, £4.25. Post 40p. (For use in

standard bi-pin. MINI. 12in 8 watt, £1-60.

Post 25p. 9in 6 watt, £1-30. Post 25p.

Complete ballast unit and holders for 9in and

12in tube. £1-70. Post 25p. (9in and 12in

measures approx.)

METERS NEW

90mm diameter

Type 65C5. 2A D.C. M/C; 5A D.C. M/C 10A D.C.

M/C; 20A D.C. M/C; 50A D.C. M/C;

Type 62TL. 1A A.C. M/I; 20A A.C. M/I; 300V A.C.

M/I; ALL ABOVE £2-50. Post 20p.

Type 65L5. 300V A.C. R/M/C; £2-75. Post 20p.



64mm X 56mm RECTANGULAR

Type 85C1. 5A D.C. M/C; 20A D.C. M/C;

Type 85L1. 5A A.C. R/M/C; 10A A.C. R/M/C; 300V

A.C. R/M/C; All at £3. Post 20p.

ROTARY VACUUM AIR PUMP AND COMPRESSOR

Carbon vane, oilless, 100/115V a.c.,

1/2 h.p. motor; 50/60 cycle, 2875/3450

r.p.m., 20 in vacuum, comp. 1-25

c.f.m., 10 p.s.i. (approx. figures).

New unused surplus stock. Supplied

with electrical connection data. FRACTION

OF MAKERS' PRICE £12. Post 50p. Suitable 110/240V,

150 watt auto transformer £3-50, Post 50p. (Both

items together Post 75p.)



PROGRAMME TIMERS

230/240V a.c. 15 r.p.m. Motors.

Each cam operates a c/o micro

switch. Ideal for lighting effects,

animated displays, etc. Ex equipment

tested.

2 cam model. £2-00 post 35p.

4 cam model. £2-50 post 35p.

8 cam model. £4-75 post 40p.

8 cam model, each cam fully adjustable. 6 r.p.m.

M.f.g. by Magnetic Devices. £7-50. Post 35p.

TRANSISTORS	
BC204	11p
BC209C	11p
BC182	10p
BC184	11p
BC212	14p
BC214	16p
BC213	15p
BC213L	15p
ZTX300	15p
ZTX500	17p
2N2484	24p
2N2904	30p
2N2905	27p
2N2219	22p
2N3054	100p
FETS	
2N3819	46p
2N5459	60p
DIODES	
1N5401	21p
1N914	5p
BA148	25p
1S150	12p
1GP7	10p
NOISE DIODES	
Z1J	75p
Z1M	120p
RECTIFIERS	
REC41A	120p
REC46	235p
REC70	40p
EA100 10	100p
MDA942A 1	210p

VOLTAGE REGULATORS	
µA7815	220p
723	180p
ARRAYS	
ML3046P	75p
CA3096AE	120p
OP. AMPS	
709 8 Dip	39p
710 TOS	39p
741	37p
748	48p
FETMOPA	450p
SPECIAL PURPOSE LINEARS	
SG3402N	174p
SG3402T	174p
SG1495D	290p
MFC6040	100p
MFC4000B	70p
T.T.L.	
7402N	38p
7410PC	24p
7420N	24p
7430PC	23p
7473N	48p
7475N	75p
7476N	49p
7489N	660p
7493PC	89p
74121J	85p
74122N	90p
74123N	144p
74150N	210p

P.E. POWER SLAVES
Special components available while stocks last.

High Voltage
MPSL01 39p; MPSL51 41p; MPSU07 69p; MPSU57 85p; SDT9203 150p.

Constanlan Wire
0.03 ohms cm as specified for the POWER SLAVES. 20cm lengths 10p.

LISTS
New lists are available for the:

P.E. SOUND SYNTHESIZER;
P.E. MINISONIC;
P.E. RHYTHM GENERATOR

Please include 7p stamp or 9 x 4in S.A.E. with all requests for lists or information.

P E MINI SONIC

MINISONIC P.C.B.'S

EA008a (Main Board). £3.35. Post free.

EA008b (Power supply and Temp. Stabilisation) £1.86. Post free.

CASSETTES NEW !!!

"SYMBIOSIS"

a companion tape to Malcolm Pointons latest article on using the Minisonic. "INTRODUCING THE MINISONIC".

Each tape £1.06, U.K. post free. One of each for £1.86.

MINISONIC COMPONENT KITS—PRICES ARE DOWN

V.C.O. (2 required) £3.07
V.C.F. (1 required) £4.24
ES/V.C.A. (2 required) £4.98
Voltage Ref. £0.54
Ring. Mod. (1 required) £3.62
Noise Gen. (1 required) £1.64
Kbd. Control (1 required) £3.70
HF Osc. and Det. £1.80
Power Amps £2.41

All above prices are for single kits of each type and include P. & P. Full details are included in lists.

Miscellaneous Items NEW !!!

5 way 180° DIN sockets 27p
5 way 180° DIN plugs 34p
Battery connectors 9p/pair
Hook up wire, 36 colours, ½ metre of each 70p
Min. DPDT toggle switch £1.20

SAVE BY PURCHASING A COMPLETE SET OF KITS AS DETAILED TOGETHER WITH SWITCH, BATTERY CONNECTORS, HOOK-UP WIRE AND P.C.B.

Price £38. U.K. post free.

TERMS: MAIL ORDER ONLY. C.W.O.

Cheques or P.O.'s payable to Eaton Audio. Orders over £5 free of P. & P. Otherwise please add 10p in the £1.

RESISTORS
Triple rated high stability carbon film. 7p for 5
0.5W metal oxide. 16p for 5
Stocked in E12 values from 4R7 to 3M9

VERO CARD FRAME CASE SYSTEM

As first advertised in P.E. May '75 issue. Build your modular project into this superbly styled economically priced case system. Send for illustrated leaflet and price list.

VAT AT CURRENT RATE SHOULD BE ADDED TO FINAL TOTAL OF ORDER

POTS GALORE

24mm Carbon without switch. All values log. or lin. 5kΩ to 1MΩ 25p each
Wirewound 1W semi-precision. All values 10Ω to 25kΩ 82p each
Min. horiz. carbon presets. 100Ω to 2.2MΩ 10p each
Cermet presets. horiz. mtg.. 100Ω to 1MΩ 45p each
Helical 10 turn W/W. 1kΩ. 5kΩ. 10kΩ £3.40 each

EATON AUDIO

P.O. BOX 3, ST. NEOTS
HUNTINGDON, CAMBS. PE19 3JB

BYWOOD

The company with the largest range of full spec. devices with new prices from 1st May.

DISPLAYS

DL707	£1.70
DL704	£1.70
DL701	£1.70
DL747	£2.45
DL750	£2.45
DL746	£2.45
3015F	£1.25
3017F	£2.00
RDS1	£8.00
RDM2	£24.80
DG12	£1.20

CLOCK CHIPS

5LT01	£5.80
MM5311	£5.18
MM5314	£4.44*
MM5316	£9.25
MK50250	£5.60*
HEEC2	£8.50
CT7001	£7.30*
CT7002	£7.30
CT7003	£7.30
CT6002	£15.00
TMS3952	£10.50

* Available in a MHI kit.

Other chips and displays usually available, ring for details or S.A.E. for catalogue and prices.

VAT on clocks, clock chips and displays still 8%.

We advise the use of sockets for all I.C.s. 24/28/40-pin £1.

BYWOOD ELECTRONICS
181 Ebbens Road, Hemel Hempstead, Herts., HP3 9RD.

Terms: C.W.O., Access, Barclaycard (quote card No.).
All prices on this advert exclude VAT. Tel. 0442 62757

FABULOUS—FANTASTIC

P.E. ORION

FULL KIT OF PARTS. £38.
Transformer and Screen Printed Board. £11.
Complete Semiconductor Kit. £9.50.
H.M. Bookend Case. £4.
As above but drilled, punched with Silk Screened Front Panel, £5.80.

ASTRO IGNITION SYSTEM

Complete Kit of Parts for this well proven Transistorised Ignition System. £9.50
Ready-built with only 2 connections to alter. £12.50
Thousands of these units are in use today and have been proven to give the following advantages: fuel economy, faster acceleration, excellent cold start, smoother running, no contact-breaker burning and many more.

Money back guarantee if you are not satisfied. Please state whether positive or negative earth.

Postage included in above prices but add V.A.T. at 8%.

ASTRO ELECTRONICS
Spring Bank Road, West Park, Chesterfield, Derbyshire

SPECIAL OFFER


Ferranti ZN414 Radio I.C. £1.06

NEW PRECISION TIMER I.C.
Ferranti ZN1034E £2.90

Ferranti Applications Booklet for ZN414, 25p includes circuits for earpiece radios, loudspeaker radios, crystal controlled receiver and frequency standard receiver.

RADNAGE RADIO & ELECTRONICS

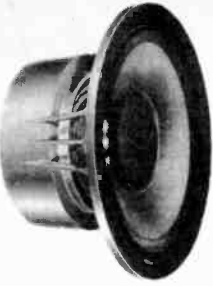2 Bottom Road, Radnage, High Wycombe, Bucks.
Prices inclusive plus 15p Post and Packing
Mail order only



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 253, 8 or 15 ohm	£8-64
Baker Group 353, 8 or 15 ohm	£10-25
Baker Group 5012, 8 or 15 ohm	£14-00
Baker Deluxe 12in d/cone	£13-75
Baker Major 12in d/cone	£11-87
Baker Regent	£10-00
Baker Superb	£18-12
Baker Auditorium 12	£16-25
Celestion MF1000, 8 or 15 ohm	£10-95
Celestion PS8 for Unilex	£3-75
Celestion G12M 8 or 15 ohm	£12-00
Celestion G12H 8 or 15 ohm	£15-00
Celestion G15C 8 or 15 ohm	£24-00
Celestion G18C 8 or 15 ohm	£33-00
EMI 13in x 8in 150 d/c 8 ohm	£2-94
EMI 13in x 8in type 350 8 or 15 ohm	£9-56
EMI 13in x 8in 20W base	£7-69
EMI 6jin 93850 4 or 8 ohm	£2-90
EMI 5in 14A/7030 mid range 8 ohm	£3-50
EMI 2jin tweeter 97492AT	£0-77
Eagle DT33 30W tweeter	£6-31
Eagle HT15 horn tweeter	£4-40
Eagle CT5 cone tweeter	£2-06
Eagle CT10 tweeter 8 or 16 ohm	£3-00
Eagle MHT10 horn tweeter	£4-44
Eagle crossover CN23, CN28, CN216	£1-75
Eagle FR4	£6-12
Eagle FR5	£9-62
Eagle FR8	£12-31
Elac 3 x 5 59RM109 15 ohm, 59RM114 8 ohm	£3-44
Elac 6jin 6RM171 d/c roll surr.	£4-06
Elac 6jin 6RM220 d/c cone	£3-12
Elac 4in tweeter TW4	£1-75
Elac 10in d/cone 10RM239 8 ohm	£3-12
Elac 8in 8CS175 3 ohm	£2-87
Fane Pop 15W 12in	£5-25
Fane Pop 25T 30W 12in	£7-50
Fane Pop 50W 12in	£12-00
Fane Pop 55 60W 12in	£12-95
Fane Pop 60W 15in	£13-75
Fane Pop 100W 18in	£25-95
Fane Crescendo 12A 100W 12in	£34-50
Fane Crescendo 12B bass	£36-50
Fane Crescendo 15in 100W	£47-50
Fane Crescendo 18in 150W	£62-95
Fane 801T 8in d/c roll surr.	£8-12
Fane 807T 8in d/c roll surr.	£4-62
Fane 808T 8in d/c	£3-44
Fane 701 twin ribbon horn	£40-50
Fane 910 horn	£14-95
Fane 920 horn	£33-95
Goodmans 8P 8in 8 or 15 ohm	£5-50
Goodmans 10P 8 or 15 ohm	£5-80
Goodmans 12P 8 or 15 ohm	£13-95

Goodmans 12P-D 8 or 15 ohm	£16-95
Goodmans 12P-G 8 or 15 ohm	£15-95
Goodmans Audiomax 12AX 100W	£36-50
Goodmans Audiomax 15AX	£40-25
Goodmans 15P 8 or 15 ohm	£21-00
Goodmans 18P 8 or 15 ohm	£36-00
Goodmans Hifex 750	£16-00
Goodmans Akent 100 tweeter	£8-44
Goodmans Auditorium 100 12in	£13-90
Goodmans Axiom 402 12in	£20-00
Goodmans Twinaxiom 8	£10-14
Goodmans Twinaxiom 10	£10-75
Kef T27	£6-06
Kef T15	£6-94
Kef B110	£8-37
Kef B200	£9-50
Kef B139	£16-50
Kef DN8	£2-31
Kef DN12	£5-75
Kef DN13	£3-87
STC 4001G Super Tweeter	£6-56
Richard Allan CG8T d/c r/surr.	£7-37
2jin 64 ohm, 70mm 80 ohm, 70mm 8 ohm	£0-77
2jin 75 ohm	£0-59
7in x 4in 3 or 8 ohm	£1-63
8in x 5in 3 or 8 ohm	£1-75
10in x 6in 3, 8 or 15 ohm	£2-69

SPEAKER KITS

Baker Major Module	each £13-44
Decca London Ribbon Horn	£30-00
Decca London Crossover	£7-50
Goodmans Mezzo twinkit	pair £47-19
Helme XLK25	pair £25-44
Helme XLK30	pair £17-19
Helme XLK50	pair £6-25
Jordan Watts Module	£17-06
Kefkit 1	pair £48-44
Kefkit 3	each £42-50
Peerless Dome Tweeter	£8-06
Radford BD25	£18-44
Radford MD9	£11-50
Radford TD3	£8-06
Radford FN12	£12-44
Richard Allan Twinkit	each £10-37
Richard Allan Triple 8	each £15-94
Richard Allan Triple 12	each £23-12
Richard Allan Super Tripe	each £27-50
Super 8 RS/DD	£10-31
Wharfedale Linton 2 kit	pair £23-12
Wharfedale Glendale 3 kit	pair £40-62
Wharfedale Dovedale 3 kit	pair £63-12

Baker, Linear and Eagle PA disco amplifiers in stock. Send stamp for list.

FREE with Speaker Orders over £7

Hi-Fi Loudspeaker Enclosures' book.

All units guaranteed new and perfect. Prompt despatch. Carriage and packing: speakers 38p each, 12in and up 50p each, speaker kits 75p each (£1.50 pair), tweeters and crossovers 25p. Send stamp for free booklet. 'Choosing a Speaker' including VAT 25% on Hi-Fi, 8% on PRO and PA.

WILMSLOW AUDIO (Dept. PE)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire, SK9 1HF.
Discount Radio, PA, Hi-Fi: 10 Swan Street, Wilmslow.



Cassettes

The best buy!

Agfa Low Noise Cassettes AT. LESS THAN HALF PRICE!

AGFA HIGH DYNAMIC SUPER

AGFA STEREO-CHROM CHROMIUM DIOXIDE

	1	5	10
C60	40p	£2-00	£3-98
C90	54p	£2-70	£5-38
C120	75p	£3-70	£7-38
	1	5	10
C60 - 6	54p	£2-70	£5-35
C90 - 6	70p	£3-50	£6-75
C120	95p	£4-95	£8-85
	1	5	10
C60	80p	£4-50	£8-75
C90	£1-10	£5-50	£10-90

SAME DAY DESPATCH. P. & P. 15p per order

WILMSLOW AUDIO

(DEPT. PE)
10 SWAN STREET, WILMSLOW,
CHESHIRE, SK9 1HF

Cut-price prerecorded cassettes—send stamp for list

P. E. JOANNA

Electronic Piano



ALL PARTS WILL BE AVAILABLE

Keyboard, Keyswitch, P.C.B.s, Hardware, Semiconductors, Resistors, Capacitors

Complete kits or easy stages
Send 5p stamp for details

Clef Products

31 Mountfield Road, Bramhall
Stockport, Cheshire SK7 1LY

4-STATION INTERCOM



£16-15

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals, Office and Home. Operates on one 9V battery. On/off switch, volume control. Complete with 3 connecting wires each 66ft and other accessories. P. & P. 65p.

MAINS INTERCOM NEW MODEL

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £25-91 per pair. P. & P. 65p.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



ONLY £11-95 + VAT 96p.

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume. Direct tape recording model at £12-95 + VAT £1-04. P. & P. 65p. 10-day price refund guarantee.


WEST LONDON DIRECT SUPPLIES (PET)
189 KENSINGTON HIGH STREET, LONDON, W.8

For all who want to know about electronic circuits

circuit designs 1

Collected Circards

PWilliams J Carruthers JHEvans JKinsler

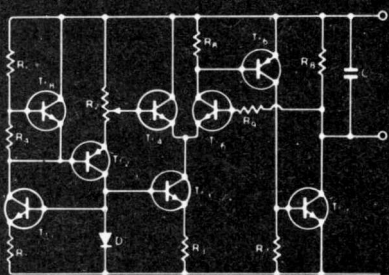

A WIRELESS WORLD PUBLICATION

Here's a book of very special appeal to all concerned with designing, using or understanding electronic circuits. It comprises information previously included in the first ten sets of Wireless World's highly successful Circards - regularly published cards giving *selected* and *tested* circuits, descriptions of circuit operation, component values and ranges, circuit limitations, modifications, performance data and graphs. Each of the ten sets - including 29 additional circuits - in this magazine size hard cover book has been updated where necessary, and is preceded by an explanatory introduction. Circuit designs (1) is the first collection of its kind. Circuits covered are:

Basic active filters
Switching circuits
Waveform generators
AC measurements
Audio circuits

Constant-current circuits
Power amplifiers
Astable circuits
Optoelectronics
Micropower circuits

A new book from Wireless World

ORDER FORM

To: General Sales Department, IPC Business Press Limited, Room 11, Dorset House, Stamford Street, London SE1 9LU.

Please send me _____ copy/copies of Circuit Designs - Number 1 at £10.40 each inclusive. I enclose remittance value £ _____ (cheques payable to IPC Business Press Ltd.)


NAME (please print) _____

ADDRESS _____

Company registered in England and a subsidiary of Reed International Limited Registered No 677128 Regd. office Dorset House, Stamford Street, London SE1 9LU.

Dimmit

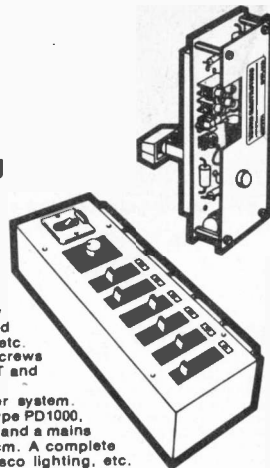range of light dimmers and lighting control systems



Illustrated is the popular PMSD1000 module. A 1kW slider control dimmer. Interference suppressed, 60mm slider range size 12 x 5 x 4cm. Ideal for low cost stage and disco lighting. Used by schools, theatres, studios, etc. Complete with scale plate, fixing screws and full instructions. £8.40 inc. VAT and P. & P.

Illustrated is the DD61 dimmer system. Contains: six 1 kW slider dimmers type PD1000, six outlet sockets, a master control and a mains on/off switch. Size 59 x 22 x 12cm. A complete system in one unit for stage or disco lighting, etc. Also available DD261 dimmer system, as above, but with 2-preset arrangement. Future systems available with 2 kW dimmers. Specials made. DD61 £110 inc. VAT and P. & P. DD261 £131.80 inc. VAT and P. & P.

The Dimmit range includes standard wall mounting models for home and office, etc. Professional modules for industrial heating applications, etc. Rotary and slider control versions. Ratings: 1000W; 2000W; 3000W; 110V and 240V.

Model SL800 sound to light converter. Modulates the light in time with sound. Built-in microphone. No connections to speaker required. Simple wiring—similar to dimmer. Rating 800W.

All products are guaranteed and are supplied with full instructions and applications. Full after-sales service. Technical advice given.

For full information on all modules and lighting control systems send 15p for our illustrated catalogue and price list. Callers welcome, visit our showroom for a demonstration of any of the modules or systems. Mon-Fri. 9.30 to 6.0 p.m. Sat. by arrangement.

YOUNG ELECTRONICS LTD.

184 Royal College Street, London NW1 9NN.

Tel. 01-267 0201

OSMABET LTD

We make transformers amongst other things

AUTO TRANSFORMERS 110-200/220/240V
30W, £2-10; 50W, £2-70; 75W, £3-48; 100W, £4; 500W, £12; 750W, £18-50; 1000W, £20-25, etc.

LOW VOLTAGE TRANSFORMERS
Prim. 200/240V a.c. 5V 1A, 80p; 8.3V 1.5A, £1-45; 3A, £1-80; 6A, £3-80; 12V 1.5A, £1-80; 3A, £3-30; 6A CT, £4-50; 18V 1.5A CT, £3-30; 24V 1.5A CT, £3-30; 3A CT, £4-50; 5A, £8-75; 6A, £8-70; 12A, £12-40; 40V 3A CT, £8; 50V 6A CT, £15-75; 25V 2A + 25V 2A, £8-40; 12V 4A + 12V 4A, £8-40.

LT TRANSFORMERS TAPPED SEC. Prim. 200/240V
0-10-12-14-16-18V 2A, £3-30; 4A, £4-50.
0-12-15-20-24-30V 2A, £4-20; 4A, £8.
0-20-30-40-60V 1A, £4-20; 2A, £8.
0-40-50-60-80-100-110V 1A, £8-40.

MIDGET RECTIFIER TRANSFORMERS
For FW rect. 200/240V a.c. 6-0-6V 1.5A or 0-0-9V 1A
£1-65 each; 12-0-12V 1A or 20-0-20V 0.75A or 0-0-9V 0.3A or 12-0-12V 0.25A or 20-0-20V 0.15A or 8V 0.5A + 8V 0.5A or 9V 0.35A + 9V 0.35A or 12V 0.25A + 12V 0.25A or 20V 0.15A + 20V 1.5A, all at £1-90 each

MAINS TRANSFORMERS
Prim. 200/240V a.c. TX6 sec., 425-0-425V 500 MA, 6.3V CT 6A, 6.3V CT 8A, 0-5-3V 3A £16-75; TX1 425-0-425V 250 MA, 6.3V CT 4A, 6.3V CT 4A, 0-5-6.3V 3A, £11-25; MT3 Prim. 0-110-240V, sec., 250V 100 MA, 6.3V 2A, £/S, £3-75.

O/P TRANSFORMERS FOR POWER AMPLIFIERS
P.P. sec., tapped 3-8-15 ohms, A-A 8.8kΩ 30W £8-75; A-A 3kΩ 30W £18-15; 100W (EL34 KT88, etc.), £17-25.

G.E.C. MANUAL OF POWER AMPLIFIERS
Covering valve amplifiers of 30W to 400W 35p.

HI FI SPEAKERS
5in 8Ω, £1-15; 7 x 4in 15Ω, £1-80; 8 x 5in 3, 8, 15 or 25Ω, £1-75 each; 8in 4Ω, £1-50; EMI 13 x 8in 8Ω, £2-20; 8 x 5in 3, 8 or 80Ω, £1-75.

LOUDSPEAKERS
2 1/2in 8 or 75Ω, 2 1/2in 8 or 25Ω, 3in 3, 8, 25 or 35Ω, 3 1/2in 8Ω, 15Ω or 80Ω, 80p each; 5in 3, 8 or 25Ω, 5 x 3in 3 or 8Ω, £1-15; 7 x 4in 3 or 15Ω, 10 x 6in 3Ω, £1-50.

SPEAKER AUTO MATCHING TRANSFORMER
12W 3 to 8 or 15Ω up or down, £1-50.

TAPE RECORDER MOTORS
New, blowers, fans, etc., 110V a.c. 60p, £1 pair.

"INSTANT" BULK TAPE/CASSETTE ERASER
Instant erasure, any diameter tape spools, cassettes, demagnetises tape heads, 200/240V a.c., £3-75.

SYNCHRONOUS GEARED MOTORS, 200/240V a.c.
Brand new, Smiths. Built-in gearbox, 2r.p.h., 75p each.
Carriage and VAT extra on all orders

S.A.E. ENQUIRIES, LISTS, MAIL ORDER ONLY


46 Kenilworth Road, Edgware, Middx. HA8 5YG

Tel. 01-858 9314





I.L.P. (Electronics) Ltd

SHEER SIMPLICITY!

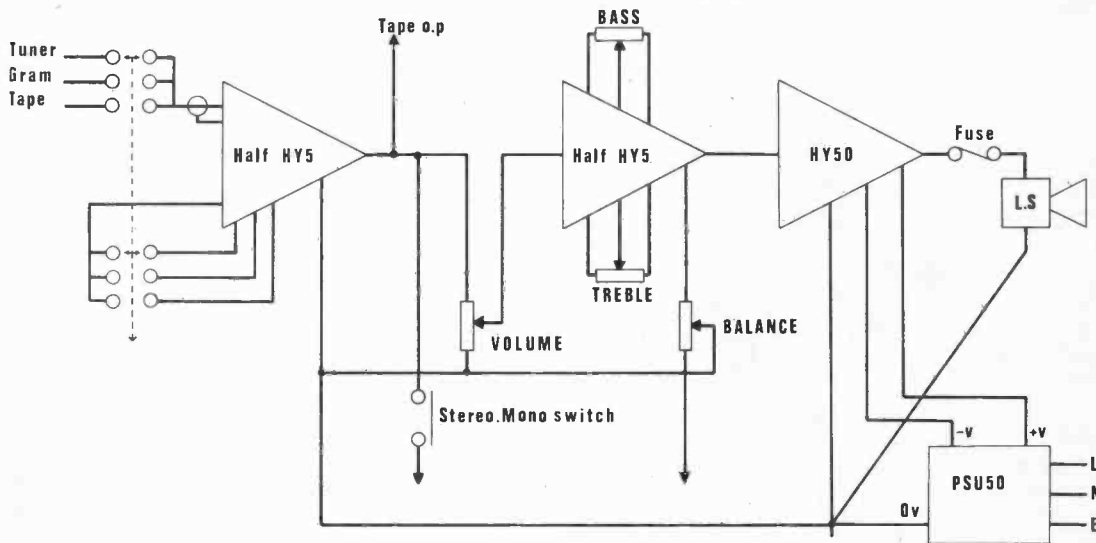

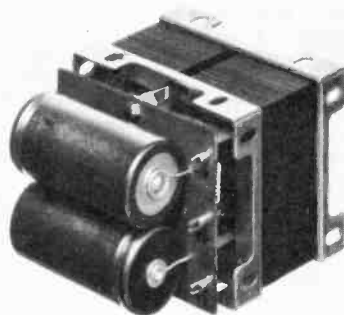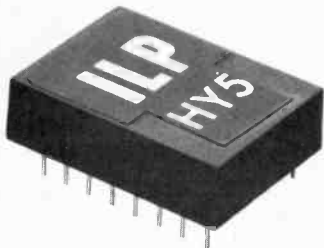MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN



The HY5 is a complete mono hybrid preamplifier, ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

TECHNICAL SPECIFICATION

Inputs: Magnetic Pick-up 3mV RIAA; Ceramic Pick-up 30mV; Microphone 10mV; Tuner 100mV; Auxiliary 3-100mV; Input Impedance 47k Ω at 1kHz. Outputs: Tape 100mV; Main output 0db (0.775V RMS). Active Tone Controls: Treble \pm 12db at 10kHz; Bass \pm 12db at 100Hz. Distortion: 0.5% at 1kHz. Signal/Noise Ratio: 68db. Overload Capability: 40db on most sensitive input. Supply Voltage: \pm 16-25V.

The HY50 is a complete solid state hybrid Hi-Fi amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided, input, output, power lines and earth.

TECHNICAL SPECIFICATION

Output Power: 25W RMS into 8 Ω . Load Impedance: 4-16 Ω . Input Sensitivity: 0db (0.775V RMS). Input Impedance: 47k Ω . Distortion: Less than 0.1% at 25W typically 0.05%. Signal/Noise Ratio: Better than 75db. Frequency Response: 10Hz-50kHz \pm 3db. Supply Voltage: \pm 25V. Size: 105 x 50 x 25mm.

The PSU50 incorporates a specially designed transformer and can be used for either mono or stereo systems.

TECHNICAL SPECIFICATIONS

Output voltage: \pm 25V. Input voltage: 210-240V. Size: L 70, D 90, H 60mm.

PRICE £4.75

+£1.19 VAT
P. & P. free

PRICE £6.20

+£1.55 VAT
P. & P. free

PRICE £6.25

+£1.56 VAT
P. & P. free

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury,
Kent CT4 7AD.
Tel. (0227) 63218

Please Supply
Total Purchase Price
I Enclose Cheque Postal Orders Money Order
Please debit my Access account Barclaycard account
Account number
Name and Address
Signature



TRAMPUS

Electronics Ltd.
WINDSOR, BERKS.
58/60 GROVE RD;
SEND C.W.O. ADD VAT TO ALL PRICES IN U.K. P&P 15p. EXPORTS 60p.

MONEY BACK IF NOT SATISFIED.
LARGE STOCKS. LOW PRICES.
ALL BRAND NEW TOP GRADE FULL SPEC SERVICES. CALLERS WELCOME.
CATALOGUE/LIST FREE SEND SAE.
BARCLAYCARD & ACCESS X POST.

Digital Displays



SLA7 RED LED 0.3" DIGIT 0-9DP 89p ea
GREEN/YELLOW £1.40
JUMBO LED 0.6" 747 DISPLAY £2.25 ea.
3015F 0-9DP £1 ea.
ZENON FLASH TUBE £4. Data 15p.

LEDS red 13P

LEDS 209 STYLE ONLY 13p ea
TIL 209 WITH CLIP RED 15p ea
TIL 211 & CLIP GREEN 29p ea
LARGE 0.2" & CLIP RED 17p ea
LARGE 0.2" CLIP GREEN 30p ea
209 STYLE OR .2"ORANGE 29p ea
INFRA RED LED £1.2N5777 33p.

PHOTO IC 81P

TEC12 PHOTO AMP/SCHITT/RELAY DRIVER or LED TTL INTERFACE 81p



FLUORESCENT LIGHTS 12W MADE IN UK 8 WAT 13" £3. 13W 22" £3.50

DIGITAL CLOCK

IC AY51224 4 DIGIT CLOCK £3.75
MMS511/4 6 DIGIT CLOCK £7

CASSETTE mechanics £13-75

NEW 8tk CARTRIDGE MECHANISM £8
STEREO CASSETTE MECHANISM £13.75
Suitable for 'PW ASCOT' recorder with heads etc. SEND 15p for DATA

INTEGRATED CIRCUITS

709 D1L14	29p	LM377 2x2WE	87
555 TIMER	54p	LM380 2W AF	89p
703 RF/IF	28p	LM381 2xPre	£2
709 T099	23p	LM3900 4xOPA	69p
709 D1L 14	28p	MC1303	£1.20
710 D1L 14	34p	MC1306	49p
723 Reg.	54p	MC1310&LED	£2.65
741 D1L 8	27p	MC1312 SQ	£2.10
741 D1L 14	29p	MC1330	69p
741 T099	29p	MC1339 2xPre	£1
747 2x741	70p	MC1350	55p
748 D1L 8	33p	NE536 fetOPA	£2
7805 5V	£1.40	NE540 Driver	1p
7812 & 15	£1.40	NE550 2vRef	79p
76013 6W AF	£1	NE555 Timer	55p
8038 SIG GEN	£3	NE556 2x" £1.20	
CA3028	£1	NE560 PLL	£3.15
CA3046	55p	NE561 PLL	£3.15
CA3048	£2	NE562 PLL	£3.19
CA3052	£1.50	NE565 PLL	£2.69
CA3054	£1	SN7209 709 28p	
LM300 2-20V	£2	SN7241 741 26p	
LM301 OPA	45p	SN7248 748 33p	
LM304 0-40V	£3	SN7660 IF1	25p
LM307 OPA	49p	SN76611 IPF1	25p
LM308 HiBo	95p	TAD110 &IF	£2
LM309K 5V	£1.48	TB810 7WAF	99p
LM372 IF	£1.80	ZN414 RX	£1.09

SPECIAL OFFERS

2N3055 FULL HIGH SPEC 115W 37p
741C 8PIN DIL 27p MFC4005 33p
NE555 TIMER 55p. ZN414 RX £1.09
BC109 9p. 2N3819e 16p. BFY51 15p

799 TTL

7400 GATES	13p	7473/7476	29p
7404 INVERT	17p	7475	45p
7401/2/10etc14p		7490	52p
7413 SCMITT	31p	7491/2/3/4	59p
7440 BUFFER	14p	74100 74175	£1
7447 DRIVER	89p	74121	32p
7470 & 7472	29p	74123	59p
		74141(&7441)	73p

TRANSISTORS & DIODES

Price each	MATCHING	16p	
AC127 & 128	16p	INS. BUSH SET10p	
AC187 & 188	19p	TIP 41	70p
AD149	43p	TIP 42	88p
AD161 & 162	33p	TIP 2955	90p
BC107 & 108	9p	TIP 3055	55p
BC109	10p	T1S43 see 2N2646	
BC147/8/9	10p	ZTX109&301	13p
BC157/8/9	12p	IN4001	4p
BC177/8/9	18p	IN4004 & 7	7p
BC182/3/4&4L10p		IN4148 & 914	4p
BC212/3/4&4L11p		2N697	14p
BCY70/1/2	17p	2N7068H	11p
BD131 & 132	39p	2N2646 UJT	32p
BFR51		2N2904 & 5	20p
BFR50/51	23p	2N2926royg	9p
BFR50/51	23p	2N3053	17p
BFR88 250V	29p	2N3055 115W	37p
BFY50/1/2	15p	2N3543 & 64	16p
BSX19/20/21	16p	2N3614	49p
MJE2955	90p	2N3702 & 3	9p
MJE3055	65p	2N3704 & 5	10p
MPU131 PUT	49p	2N3706 & 7	9p
OA91 OA81	6p	2N3708 & 9	8p
OA81 & OA91	6p	2N3710 & 11	10p
TIP 29 & 30	52p	2N3819E FET	16p
TIP 31 & 32	69p	2N3823E FET	17p
		2N3904/5/6	15p

FULL SELECTION IN OUR FREE LISTS.

NEW TRAMPUS FULL SPEC PAKS

PAK A	10 RED LEDS	our choice	£1
PAK B	4 741 OP AMP		£1
PAK C	4 2N3055	£1. D 12 BC109	£1
PAK E	10 BC182	£1. F 11 2N3704	£1
PAK G	8 BFY51	£1. H 9 2N3819e	£1
PAK J	9 2N3053	£1. K 40 1N914	£1

BZY88 400mW	1A/50V SCR	36p
ZENER DIODES	TAG1/400	55p
BRIDGE RECT	C106 & 7 SCR	D1
1A 50V	4A/400V	53p
BK100 DIAC	SC146D TRIAC	
	10A 400V	75p

vero

VERO PINS x36 28p.
COPPER CLAD VERBOARD 0.1"
21"x5" 29p 21x3" 26p. 31x3" 31p.
31"x5" 31p 31x 17" £1.50
DIL IC's BOARDS 6x41" £1.50
24 way edge connector 60p.
36 way 90P. PLAIN 31"x17" £1.
FACE CUTTER 45p. FEC ETCH PAK 50p

DALOpen69p

PRINTED CIRCUIT BOARD KIT £1.69
DECON NO MESS ETCH PAK NEW 69p
DECON DESOLDER BRAID REEL 59p
HEATSINKS
5F/T05 & 18F/T018 5p ea. TV4 15p.
TV3/T03 16p. EXTRUDED 4" 4Y1 29p.
TGS308 GAS DETECTOR £1.80 ea.
LOGIC PROBE TTL TESTER PEN £5

CAPACITORS

CERAMIC 22pf to 0.1uf 50v 5p.
ELECTROLYTIC: 10/50/100 uf in
10v 5p. 25v 6p. 50v 8p. 2uf/10v 5p.
1000 uf/25v 18p. 200/500 25v 9p.

POTENTIOMETERS (POTS) AB or EGIN

LIN or LOG ROTARY 13p. SWITCH 14p
DUAL 45p. SLIDERS 29p. STEREO 57p
KNOBS 7p. PRESETS 6P. RESISTORS 13p
SWITCHES: SPST 18p. DPDT 25p.

DIN PLUGS ALL 12P. SOCKETS 10P.
ALI CASES AB5/AB7 50p. AB13 65p.
TRANSFORMERS 1A 6v6v or 12v12v
Only £1.34. 100mA type CT 75p.

OIL sockets

TEXAS GOLD
LOW PROFILE ea
8, 1.4 & 16 PIN 13p
SOLDERCON STRIPS:
100 PINS 50p. 1K £3.


SPARKRITE MK 2

CAPACITIVE DISCHARGE ELECTRONIC IGNITION KIT

'Sparkrite MK 2' is a high performance, high quality, capacitive discharge, electronic ignition system. Sparkrite completely eliminates problems of the contact breaker. Misfire due to contact breaker bounce is electronically eliminated, contact breaker burn is eliminated, the condition of the contacts is not relevant to the performance of the ignition, and the system is no longer dependent on the dwell period for recharging.
Sparkrite will give you: Up to 20% better fuel consumption, instant all weather starting, cleaner plugs—they last up to five times longer without attention, faster acceleration, higher top speed, longer coil and battery life, efficient fuel burning and less air pollution, smoother running, continual peak performance.
The kit comprises everything needed: Ready drilled, pressed steel case coated in matt black epoxy resin, ready drilled base and heatsink (top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.
WE SAY IT IS THE BEST SYSTEM AT ANY PRICE

Voted best of 8 Ignition systems tested by a leading Motoring Magazine

Prices: D.I.Y. assembly kit £18.93 including VAT post and packing. Ready built unit £13.96 including VAT post and packing. (Both fit all vehicles with coil distributor ignition up to 8 cylinders.) Switch for instant changeover from Sparkrite ignition to conventional ignition £2.79 including VAT post and packing. R.P.M. limiting control £2.42 including VAT post and packing. (Fitted in case on ready built unit, dashboard mounting on kit.) We can supply units for any petrol-engined vehicle (boat, motorcycle, etc.) with coil/contact breaker ignition. Details on request.
CALL IN AND SEE US FOR A DEMONSTRATION

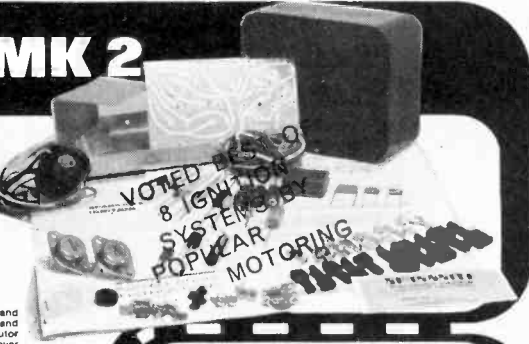

ORDER NOW

To: Electronics Design Associates Dept. PE7
82 Bath Street, Walsall, WS1 3DE. Phone 33552

From: Name
Address

Quantity Please Supply

- Sparkrite MK 2 D.I.Y. Assembly kits at £18.93
- Sparkrite MK 2 Ready Built Negative earth at £13.96
- Sparkrite MK 2 Ready Built Positive earth at £13.96
- Ignition changeover switches at £2.79
- R.P.M. Limit systems in the above units at £2.42
- Fluorescent light assembly kits at £3.44
- Fluorescent light built units at £4.10
- Diffusers for the above at 59p

I enclose cheque/P.O. for £..... Cheque No.
(Send S.A.E. if brochure only required).

ELECTRONICS DESIGN ASSOCIATES of WALSALL

ALUMINIUM BOXES

Prices include lids, screws and VAT (at 8%). 10p should be added to the total order value for postage and packing.

No. 7	5 1/2"	by 2 1/2"	by 1 1/2"	high	47p
No. 8	4"	by 4"	by 1 1/2"	high	48p
No. 9	4"	by 2 1/2"	by 1 1/2"	high	48p
No. 10	5 1/2"	by 4"	by 1 1/2"	high	48p
No. 11	4 1/2"	by 2 1/2"	by 2"	high	48p
No. 12	3"	by 2"	by 1 1/2"	high	38p
No. 13	6"	by 4"	by 2"	high	58p
No. 14	7"	by 5"	by 2"	high	75p
No. 15	8"	by 6"	by 2"	high	83p
No. 16	10"	by 7"	by 3"	high	£1.14

FLUORESCENT LIGHT KIT

You can build this reverse polarity protected 12V 8W fluorescent light. Everything needed is supplied: white enamelled drilled metalwork, ready drilled heatsink, printed circuit board, high quality components and transformer, and caps, cables, the fluorescent tube, nuts, bolts, washers and simple assembly and operating instructions. When complete the light has many uses: workshop and workbench illumination, garage lighting, emergency lighting, lighting for camping and boating, as an inspection lamp and many more.
Prices: Assembly kit £3.44 inc. VAT post and packing. Ready built £4.10 inc. VAT post and packing. Diffuser 59p inc. VAT post and packing.

ELECTROVALUE

The best of all!

CATALOGUE 7 ISSUE 3

With 25p refund voucher

Up-dated Price and Product Information

112 pages plus cover. As comprehensive and up-to-the-minute as possible. Thousands of items from vast ranges of semi-conductors including I.C.s to components, tools, accessories, technical information and diagrams are included as well as a refund voucher worth 25p for spending on orders list value £5 or more SEND NOW FOR YOUR COPY BY RETURN post. It's an investment in practical money-saving and reliability! **30p** paid

PRICES as shown in our latest catalogue (No. 7, issue 3), were due for review by April 1st. In fact these have remained unchanged since January, reviewed only at 3-monthly intervals as from July 1st next. This is instead of making day-to-day price changes.

DISCOUNTS apply on all items except the few where prices are shown NETT. 5% on orders from £5 to £14.99; 10% on orders list value £15 or more.

FREE POST AND PACKING in U.K. for pre-paid mail orders over £2 (except Baxandall cabinets). If under there is an additional handling charge of 10p.


QUALITY GUARANTEE. All goods are sold on the understanding that they conform to maker's specification. No rejects, seconds or sub-standard merchandise.

ELECTROVALUE LTD

All communications to Section 2/5, 28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB. Telephone Egham 3603, Telex 284475. Shop hours: 9-5.30 daily, 9-1 pm Sats.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA. Telephone (061) 432 4945. Shop hours: Daily 9-5.30 pm; 9-1 pm Sats.

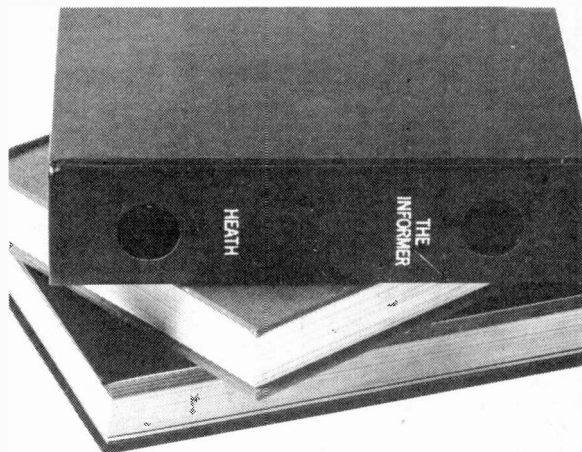Enough books are written about crime, this one stops it.



Outside it's a book. Inside it's an ingenious ultrasonic burglar alarm from Heathkit. The GD-39.


A complete kit that can be assembled in only a few enjoyable hours, with the help of a very easy to follow instruction manual.

The GD-39 works by transmitting a silent, ultrasonic signal throughout the room. And continuously monitoring it. Any movement made by an intruder in the room will then automatically produce a change in the signal. Which triggers off a lamp and, thirty seconds later, a remote buzzer, that just you hear, or a loud bell.

Enough to scare the living daylights out of a burglar.


For more details, and a bookful of other ideas, just post the coupon now for your free Heathkit catalogue. Or, if you're in London or Gloucester, call in and see us. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road.

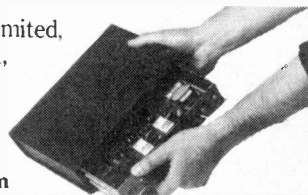Heath (Gloucester) Limited,
Dept. PE75, Bristol Road,
Gloucester GL2 6EE.
Tel: (0452) 29451.



The GD-39 Ultrasonic Burglar Alarm

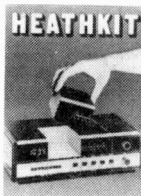To: Heath (Gloucester) Limited, Dept. PE75, Gloucester GL2 6EE. Please send me a free Heathkit catalogue.




Name

Address

Postcode

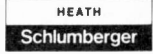Remember easy terms are available with the Heathkit Monthly Budget Plan.



12in LONG PERSISTENCE CRT. Full spec. Price £6-50 to include V A T and Carriage

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2Hz to 8MHz. Hook up to a 9 volt battery and connect to your scope and have two traces for ONLY £6-25, P & P 25p. (Not cased, not calibrated)

WIDE RANGE WOBBLATOR. 5MHz to 150MHz up to 15MHz sweep width. Only 3 controls: preset RF level, sweep width and frequency. Ideal for 10.7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6.3V a.c. and use within minutes of receiving. All this for ONLY £6-75, P & P 35p. (Not cased, not calibrated)

20Hz to 200kHz WB, SINE and SQUARE GENERATOR. Four ranges. Independent amplitude control, thermostat stabilised. Ready to use. 9V supply required. £8-85 each, P & P 35p. (Not cased, not calibrated)

GRATICULES 12cm x 14cm high quality plastic 15p each, P & P 8p

Large quantity of good quality components—NO PASSING TRADE—so we offer 3lb of **ELECTRONIC GOODIES** for £1-70. Post paid.

ROTARY SWITCH PACK—6 brand new switches (1 ceramic, 1 off 4 pole, 2 way, etc.). 50p, P & P 37p

P.C.B. PACKS. S & D. Quantity 2 sq. ft.—no tiny pieces. 50p, P & P 37p.

CAPACITOR PACK—50 brand new components, only 50p, P & P 37p.

TRIMMER PACK. 2 twin 50/200pF ceramic, 2 twin 10/60pF ceramic, 2 min strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW. 25p the lot, P & P 15p.

PHOTOCELL equ. OCP71, 13p each. MULLARD OCP70, 10p each.

DELIVERED TO YOUR DOOR, 1cwt of Electronic Scrap chassis, boards, etc. No rubbish. FOR ONLY £4.

MODERN TELEPHONES. Type 706: two-tone grey or black, £3-75 each. Type 7006: two-tone grey or green, £3-75 each. Style similar to Type 746: grey, green or black, £3 each. P & P. all types 45p each.

Ideal EXTENSION TELEPHONES with standard GPO type dial, bell and lead coding. £1-75 each, P & P 45p.

HANDSETS. Complete with 2 inserts and lead. 75p each, P & P 37p.

DIALS. ONLY 75p each, P & P 25p.

HIGH VALUE—PRINTED BOARD PACK. Hundreds of components, transistors, etc.—No 2 boards the same. No short leaded transistor computer boards. £1-75, post paid.

BEEHIVE TRIMMER 3/30 pF. Brand new. Qty 1-9 13p each, P & P 15p. 10-99 10p each, P & P 25p. 100-999 7p each, P & P free.

HE CRYSTAL DRIVE UNIT. 19in rack mount. Standard 240V input with superb crystal oven by Labgear (no crystals) £5 each. Carr. £2.

1,000pF FEED THRU CAPACITORS. Only sold in packs of 10, 30p, P & P 15p.

ALWAYS SOME CHEAP SCOPES AVAILABLE—or build your own. Send for our tube list with a S.A.E.

PLEASE ADD V.A.T. AT 8%
OPEN 9 a.m. to 6.30 p.m. ANY DAY

CHILTMEAD LTD

7/9 ARTHUR ROAD, READING, BERKS.
(rear Tech. College) Tel.: Reading 582605/65916



TRANSISTORS			
AC107	0-10	BC156	0-11
AC126	0-10	BC159	0-12
AC127	0-10	BC171	0-10
ACJ28	0-10	BC172	0-10
AC138	0-20	BC173	0-10
AC141	0-20	BC184	0-10
AC142	0-20	BC206	0-12
AC153	0-22	BC209	0-13
AC154	0-22	BC212L	0-14
AC167	0-21	BC213	0-12
AC168	0-27	BC214L	0-14
AC169	0-16	BC301	0-30
AC176	0-15	BC337	0-15
AC178	MP	CG213	0-12
AC178	0-25	BD131	0-40
AC177	0-26	BD132	0-40
AC178	0-25	BD131	MP
AC177	0-26	BD132	MP
AC178	0-25	BD131	MP
AC177	0-26	BD132	MP
AC178	0-25	BD131	MP
AC177	0-26	BD132	MP
AC178	0-25	BD131	MP
AC177	0-26	BD132	MP
AD140	0-53	BF182	0-30
AD142	0-53	BF183	0-30
AD149	0-55	BF194	0-32
AD161	0-30	BF195	0-30
AD162	MP	BF197	0-15
AD162	0-75	BF200	0-12
AF115	0-26	BF274	0-39
AF116	0-26	BU105	2-00
AF124	0-33	BFX29	0-28
AF125	0-31	BF182	0-30
AF178	0-50	BFX85	0-33
ASV51	0-20	BFY50	0-20
ASV52	0-22	BFY51	0-18
BC107	0-09	BFY52	0-20
BC108	0-09	BFY53	0-20
BC109	0-09	BSY38	0-20
BC142	0-30	BSY39	0-20
BC143	0-30	BSY40	0-20
BC147	0-10	BY141	0-31
BC148	0-10	C111	0-50
BC149	0-10	C111E	0-55
BC157	0-11	CV5441	0-20
CV7464	0-19	20106	0-21
CV7594	0-25	20306	0-44
CV7648	0-30	20345A	0-40
CV7862	0-40	20402	0-25
CV8256	0-16	20586	0-16
ME4102	0-12	2N687	0-15
MJE2021	0-85	2N715	0-35
MJE2955	0-95	2N726	0-25
MJE355	0-90	2N753	0-65
MKT169	0-25	2N1303	0-16
NKT164	0-25	2N1304	0-19
NKT212	0-20	2N1305	0-19
NKT221	0-17	2N1309	0-25
NKT274	0-30	2N1754	0-20
NKT270	0-15	2N2484	0-30
NKT278	0-15	2N2923	0-16
OC22	0-50	2N2924	0-16
OC28	0-50	2N2925	0-15
OC35	0-45	2N2926G	0-12
OC36	0-55	2N2926J	0-12
OC44	0-17	2N2926F	0-11
OC45	0-14	2N2926O	0-11
OC70	0-11	2N2926B	0-11
OC71	0-11	2N3053	0-19
OC72	0-15	2N3054	0-50
OC81	0-17	2N3055	0-50
OC82	0-17	2N3056	0-50
OC201	0-32	2N3703	0-12
OC202	0-27	2N3704	0-14
OC203	0-29	2N3705	0-13
OC204	0-29	2N3706	0-14
OC44K	0-20	2N3710	0-10
SGS2620	0-15	2N3711	0-10
SGS2642	0-14	2N3713	1-20
SGS2649	0-20	2N3714	0-23
SGS2702	0-18	2N3905	0-31
SGS2703	0-18	2N3906	0-31
SGS2704	0-18	2N3907	0-31
SGS2900	0-18	2N4103	0-31

WATCH OUR Television

NOW IT'S BIGGER & BETTER

More pages! Larger size! Extra features!


SERVICING-VIDEO-CONSTRUCTION-COLOUR-DEVELOPMENTS

Television

JULY 1975 40p

**Larger size
More pages**

Large-screen TV OSCILLOSCOPE

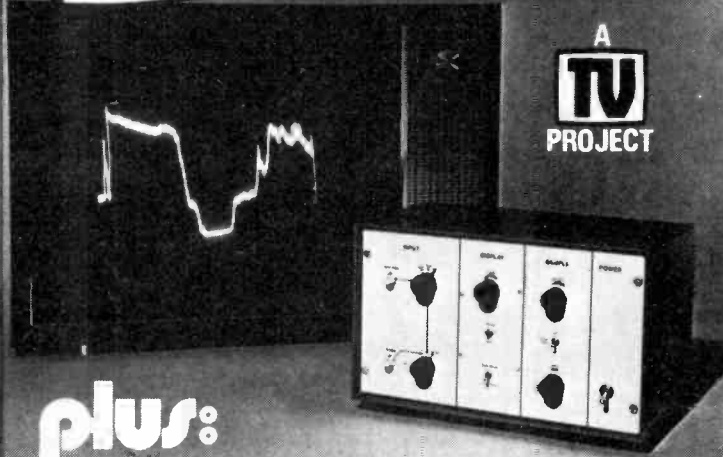

plus:

SERVICING: PHILIPS G6 COLOUR CHASSIS
VIDEO: SIGNAL EXTRACTION FOR VCRs
DEVELOPMENTS: NEW RANK COLOUR CIRCUITRY
NEW SERIES: CEEFAX/ORACLE RECEPTION TECHNIQUES

Special Features this month:

LARGE SCREEN TV OSCILLOSCOPE

How a large-screen monochrome receiver can be converted for displaying television waveforms.

CEEFAX/ORACLE RECEPTION

Start of a new series explaining the principles and the practical techniques used for teletext news displays.

LATEST COLOUR RECEIVER CIRCUITRY

An account of the many novel circuit techniques used in the latest Rank colour chassis.

VIDEO SIGNAL EXTRACTION

Many VCRs require a v.f. input. K. Cummins presents a suitable circuit for extracting the video signal from a domestic TV set.

COLOUR RECEIVER SERVICING

Les Lawry-Johns deals with faults experienced on the Philips G6 colour chassis

PLUS ALL THE REGULAR FEATURES

JULY ISSUE OUT MONDAY 16th JUNE, PRICE 40p

Practical Electronics Classified Advertisements

RATES: 11p per word (minimum 12 words). Box No. 30p extra. Semi-Display £8.50 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4H 4AD

RECEIVERS AND COMPONENTS

BETA DEVICES

MANUFACTURERS BRANDED PRODUCTS

TRANSISTORS	I.C.'s	DIODES & RECT.	
AC187/188	709C TO99 0-30	1N914 0-04	
PR.	709C D.I.L. 0-30	1N4148 0-04	
BC107/	741C TO99 0-30	0A202 0-00	
BC108	741C D.I.L. 0-30	1N4002/2 0-05	
BC109C	0-11 723C D.I.L. 0-80	1N4003/4/5 0-08	
BC147/8	0-10 747C D.I.L. 0-85	1N4006/7 0-08	
BCY70/71/72/13	748C D.I.L. 0-30	BRIDGES	
BFX86/87/88	0-20 655-8-Pin 0-50	W01 1A	0-20
	556-14-Pin 1.00	100V	
BFY50	0-18 8-Pin 0-12	W05 1A	0-80
BFY51/52	0-18 8-Pin 0-12	600V	
OC28	0-45 2N3055 0-38	ZENERS	
OC35	0-35 D.I.L. SOCKETS	BZY88 3-3-	
2N2646	0-30 8-Pin 0-12	33V 5%	0-00
2N3053	0-14 14-Pin 0-12	1 Watt 6-8-	
TIP29A	0-49 16-Pin 0-14	200V 5%	0-15
TIP31A	0-61	L.E.D.	
TIP41A	0-74	409-Red	0-17
TIP42A	0-90	include V.A.T.	L.E.D. Chip 0-02

C.W.O. PLUS P.P. 15p TO BETA DEVICES

4 High Bridge Street, Waltham Abbey, Essex

BRAND NEW COMPONENTS BY RETURN. Electrolytics 16V, 25V, 50V, 0.47, 1.0, 2.2, 4.7, 10mfd, 5p; 22, 47, 51p (50V, 6p); 100, 7p (50V, 8p); 220, 8p (50V, 10p); 500, 11p (50V, 16p); 1000/25V, 15p. Subminiature bead-type tantalums, 1000/25V, 0.1/35V, 0.22/35V, 0.47/35V, 1.0/35V, 2.2/35V, 4.7/35V, 10/20V, 22/16V, 47/8V, 100/3V, 11p. Mylar Film 100V, 0.001, 0.002, 0.005, 0.01, 0.02, 3p; 0.04, 0.05, 3.1p. Mullard tubular polyester 400V E6 series 0.001-0.022, 3.1p; 0.033-0.1, 4.1p. Mullard polyester 160V tubular or 250V miniature for vertical mounting E6 series, 0.01-0.047, 3.1p; 0.068, 0.1, 4.1p; 0.15, 0.22, 6p; 0.33, 7p; 0.47, 9p; 0.68, 11p; 1.0, 14p; 1.5/250V, 18p; 2.2/250V, 22p. Mullard miniature C333 ceramics 63V E12 series 2%, 1-8pF-47pF, 3p; 56pF-330pF, 3.1p. Plate ceramics 50V E6 series 470pF-47,000pF, 2p. Polystyrene 63V, E12 series 10pF-1,000pF, 3p; 1,200pF-10,000pF, 4p. Miniature highstab carbon film resistors 1/4W E12 series 5%, (10% over 1MΩ) 1Ω-10MΩ, 1-2p; 1N4002, 6p; 1N4006, 8p; 1N4148, 4p. Postage 10p. Prices VAT inclusive. THE C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield, S8 0RN.

BULK OFFERS

All goods full spec and marked

IN4001	£2.50	BC116A	£8.00	BF181	£20.00
IN4002	£2.80	BC147	£8.00	BF394	£8.00
IN4003	£3.20	BC148	£5.00	BF195	£8.00
IN4004	£3.60	BC149	£8.00	BSY95A	£8.00
IN4005	£4.20	BC157	£8.00	2N2646	£24.00
IN4006	£4.70	BC158	£8.00	2N3055	£28.00
IN4007	£5.00	BC159	£8.00	NE555V	£38.00
IN4148	£2.20	BC161	£10.00	709C	£18.00
BC107	£7.00	BC267	£8.00	741C	£19.00
BC108	£7.00	8128	£10.00	All prices per	
BC109	£7.00	BC548	£8.00	min. quantity 100	

Out-of-spec., mainly unmarked transistors 2500, £10. Ferric Chloride £30 per 100 lb bags (8% VAT). Miniature mains transformers, 100mA sec 6-0-6V £5/10; 9-0-9V £5-50/10; 12-0-12V £8/10; subminiature 6-0-6V 100mA £8/10. 400mW Zeners, most voltages, £5/100. Assorted small value capacitors—ceramic, mica, poly, etc., £28/10,000. Assorted C280 polyester £28/10,000. Minimum Order £5; Carr. Free. Add VAT at the appropriate rate (25%). S.A.E. enquiries.

JUNIPER ELECTRONICS (PE3)

PO Box 61, Southampton SO9 7EE

3 ASS. M.C. METERS £1.30 (40p). BANK OF 20 NEONS 74p (11p). 3-FIGURE RESETTABLE COUNTER 19/22p. works on 12, £2.50 (30p). BOX WITH 20 x LA2 POT CORES + 20 1% CAPS £1.50 (50p). COPPER CLAD FIBRE GLASS PANELS 1 1/2 x 7in 80p; 1 1/2 x 4in 75p c.p. COPPER CLAD PAX. PANELS 5 1/2 x 5 1/2in, 6 for 65p; 8 x 9 1/2in, 3 for £1.16 x 9 1/2in, 60p; 12 x 12in, 60p. A.I.P.P. 74 SERIES I.C.s ON PANELS 10 for 80p (10p). List of Valupacs, Computer panels, etc. 12p. Refund on purchase. 71b ASSORTED COMPONENTS £2.20 c.p.

J.W.B. RADIO

2 Barnfield Crescent, Sale, Cheshire M33 1NL Postage in brackets Mail order only

CLEARING DISTRIBUTOR STOCKS, transistors, diodes, components, etc. Sample pack 65p incl. postage or send stamp for list. REDHAWK SALES LTD., 10 Maple Lodge Close, Rickmansworth, Herts. Mail order only.

AXIAL PRODUCTS

DEPT. 27
23 AVERY AVENUE
HIGH WYCOMBE
BUCKS.

AERIALS
4 ELEMENT FM STEREO
£3.80 + VAT + 50p P. & P.
18 ELEMENT TV
£2.00 + VAT + 50p P. & P.
10 ELEMENT TV
£1.75 + VAT + 50p P. & P.

New design, superior quality, including mounting bracket and full instructions.

AC127	20p	BCY70	18p	1N4148	4p
AC128	20p	BFY51	15p	400mV ZENER	
BC107	8p	2N2828	12p	DIODES	
BC108	8p	2N3055	6p		
BC109	10p	1N4001	5p	3-33V	8p
BC113	10p	1N4002	5p	741 op amp	28p
BC148	18p	1N4003	6p	1N301 op amp	6p
BC149	18p	1N4004	6p	37p	

ADD 8% VAT + 10p P. & P. per £ under £5
C.W.O. MAIL ORDER ONLY

"P.E. JOANNA". Kit of all semiconductors £31 inc. VAT. Postage, etc., free. 124 x 4-7µF electrolytic capacitors (miniature) 2K7. Resistor pack containing 61 x 56R, 12 x 2K2, 61 x 33K, 170 x 47K, 122 x 120K, 50 x 150K, 24 x 180K, 26 x 220K, 12 x 270K and 12 x 330K £4.50. All other components will be available. Send S.A.E. for lists. Mail order only to: G. NEWMAN, 12 Francis Avenue, St. Albans, AL1 6BX.

PRECISION POLYCARBONATE CAPACITORS

ALL HIGH STABILITY—EXTREMELY LOW LEAKAGE

440V AC (±10%)	63V Range	±1%	±2%	±5%
0.1µF (1 1/2" x 1")	50p	0.47µF	80p	46p 38p
0.25µF (1 1/2" x 1")	80p	1.0µF	80p	58p 48p
0.47µF (1 1/2" x 1")	71p	2.2µF	80p	65p 55p
0.5µF (1 1/2" x 1")	75p	4.7µF	£1.30	£1.05 85p
0.68µF (2" x 1")	80p	6.8µF	£1.04	£1.28 £1.09
1.0µF	81p	10.0µF	£2.00	£1.60 £1.40
2.0µF (2" x 1")	£1.22	15.0µF	£2.75	£2.15 £1.90

TANTALUM BEAD CAPACITORS—Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V; 10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. ALL at 10p each, 10 for 95p, 50 for 24.

TRANSISTORS: BC183/183L 11p BFY50 20p BC107/8/9 8p BC184/184L 12p BFY51 20p BC114 12p BC212/212L 14p BFY52 20p BC147/8/9 12p BC547/568A 15p APT78 30p BC153/7/8 12p BF194 12p OC71 12p BC182/182L 11p BF197 12p 2N3055 50p

POPULAR DIODES—1N914 6p, 8 for 45p, 18 for 90p; 1N916 8p, 6 for 45p, 14 for 80p; 1844 6p, 11 for 50p, 24 for 81; 1N4148 6p, 6 for 27p, 12 for 48p; 1N4001 5p; 1N4002 6p, 1N4003 6p; 1N4004 7p; 1N4005 7p; 1N4006 8p; 1N4007 8p.

LOW PRICE ZENER DIODES—400mW. Tel. ±5% at 5mA. Values available: 3V, 3.3V, 3.6V, 4.7V, 5.1V, 6.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 18.5V, 16V, 16V, 18V, 20V, 22V, 24V, 27V, 30V, 33V. ALL at 7p each, 6 for 38p, 14 for 84p. SPECIAL OFFER: 100 Zeners for 25-50.

RESISTORS—High stability, low noise carbon film 5% 1W at 40°C, 1W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) 25.

SILICON PLASTIC RECTIFIERS—1.5 amp, brand new wire ended DO27: 100 P.I.V. 7p (4 for 28p); 400 P.I.V. 8p (4 for 30p).

BRIDGE RECTIFIERS—2 amp: 200V 40p; 350V 45p; 600V 55p.

SUBMINIATURE VERTICAL PRESETS—0.1W only: ALL at 5p each: 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1kΩ, 2.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, 2.5MΩ, 5MΩ.

PLEASE ADD 15p POST AND PACKING ON ALL ORDERS BELOW £5. ALL EXPORT ORDERS ADD COST OF SEA/AIRMAIL.

PLEASE ADD 25% V.A.T. TO ORDERS Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona fide companies

MARCO TRADING

Dept. E.7, The Old School, Edlaston, Nr. Wem, Shropshire
Tel.: Whixall 464/465 (STD 0948 72)
(Proprs.: Minicoat Trading Ltd.)

TTL AT LOW PRICES!

ALL FULL SPECIFICATION BY FAMOUS MANUFACTURERS

Type	1/24	25/99	Type	1/24	25/99
7400	0-13	0-12	7472	0-26	0-23
7401	0-13	0-12	7473	0-31	0-29
7402	0-13	0-12	7474	0-31	0-29
7403	0-13	0-12	7475	0-42	0-41
7404	0-15	0-14	7476	0-32	0-29
7405	0-15	0-14	7480	0-44	0-39
7408	0-15	0-14	7483	0-83	0-74
7410	0-13	0-12	7486	0-28	0-24
7412	0-15	0-14	7489	2-77	2-60
7413	0-30	0-29	7490	0-43	0-41
7417	0-28	0-27	7491	0-69	0-64
7420	0-13	0-12	7492	0-44	0-42
7427	0-25	0-23	7493	0-43	0-41
7430	0-13	0-12	7495	0-57	0-54
7432	0-25	0-23	7496	0-72	0-64
7437	0-27	0-24	74107	0-32	0-29
7440	0-13	0-12	74121	0-32	0-29
7442	0-64	0-59	74123	0-60	0-57
7445	0-83	0-76	74141	0-71	0-67
7447	0-83	0-73	74145	0-80	0-72
7450	0-13	0-12	74153	0-71	0-67
7451	0-13	0-12	74157	0-81	0-73
7452	0-13	0-12	74174	0-92	0-83
7454	0-13	0-12	74175	0-92	0-83
7460	0-13	0-12	74181	1-93	1-80

TTL MAY BE MIXED TO QUALIFY FOR QUANTITY PRICES

IN4001	4p	ZTX109	9p	ZTX312	11p
IN4002	4 1/2p	ZTX300	13p	ZTX313	13p
IN4003	5p	ZTX301	14p	ZTX500	13p
IN4004	5 1/2p	ZTX302	19p	ZTX501	14p
IN4148	3 1/2p	ZTX303	15p	ZTX502	19p
ZTX107	9 1/2p	ZTX310	9 1/2p	ZTX502	19p
ZTX108	7 1/2p	ZTX311	11p	ZTX503	15p

Send S.A.E. for latest catalogue (includes TTL pin layout guide). 10p P. & P. on orders under £2. PLEASE ADD VAT AT CURRENT RATES. ALL GOODS SENT BY 1st CLASS POST.

J. C. JONES

Dept. PE7, 46 BURSTALLS, ST. IVES, HUNTINGDON PE17 4XX (MAIL ORDER ONLY)

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO., P.O. Box 5, Frome, Somerset. Immediate cash settlement.

R.T. SERVICES

(MAIL ORDER ONLY)

77 Hayfield Rd., Salford 6, Lancs.

Tapped Auto Transformer, 240V-110V, 80 watts, £2 P.P. New.

Tapped Auto Transformer, 240V-115V, 200 watts, £4-50 P.P. New.

100 Watt Valve Output Transformer. KT8Bs, etc. 8 or 15Ω or 100 volt line output, £13-60 P.P.

FM Tuner with R.F. Stage and A.G.C., 3 transistors, neg. earth, 2 1/2 x 2 1/4 in with circuit, £1-54 P.P.

Crouzet Geared Motors, 30 r.p.m. New, £1-75 P.P.

UHFT Tuners. Transistorised, £2-10 P.P. Panels with I.C.'s on 8 1/2p per I.C. min. order 10 I.C.'s.

Transformers. 7.5V+7.5V 1/4, £1-12 inc. P.P. 12-0-12V, 100mA, £1-25 inc. P.P. 9-0-9V, 100mA, £1-25 inc. P.P. 29V 50mA, 95p inc. P.P. 6-0-6V, 100mA, £1-25 inc. P.P.

Transformer. 24 volt, approx. 1 amp + 6.3V CT approx. 500mA, £1-60 inc. P.P.

Transformer. 20 volt, 1 amp, £1-40 P.P.

Transformer. 45 volt, 1 amp, £3-38 P.P.

P.C. Board, 5/5, 5 1/2 x 5 1/2 in, 10 for £11-10 P.P.

Transistorised Timer. Variable delay, 110 or 250V A.C. input. With instructions. Brand new, £2-25 inc. P.P. Size 3" x 2" x 2".


Power Unit Components Transformer. 18 volt 1 amp F/W bridge rectifier, 2,1250 mfd capacitors, all new £1-60 per kit. P.P.

Electrolytic Capacitors, 4,000 MF, 50VW, 4 1/2" x 1 1/2" 90p, inc. P.P.

Mixed Pack of C280 series Mullard capacitors. 100 for £13-30 inc. P.P.

LED with Data clip 1p	S	0-125	0-2	INFRA RED 550uW Axial lead 49p 1-5mW TO46 £1-10		
	RED	15p	19p			
	GRE	27p	33p			
	YEL	27p	33p			
OPTO-ISOLATORS		SCR's	50V	100V	400V	
IL74	1-SKV, 150kHz	£1	TOS 1A	25p	27p	46p
4350	2-SKV, 5MHz	£2-25	TO66 3A	27p	35p	50p
Data free with all OPTO		TRIAC	TOS 2A	400V	60p	
AC127/8	15p	2N2926(G)	12p	VOLTAGE REGS.		
AF117	20p	2N3053	15p	7805 Plastic	5V	
BC107	11p	2N3055	41p	1-5A	£1-50	
BC108	9p	2N3702/3/4	12p	L129 Plastic	5V	
BC109C	12p	TIS43	25p	600mA	£1-40	
BC147/8/9	10p	MPP102	40p	BRIDGE RECTS.		
BC157/8/9	11p	2N3819	25p	2A 50V	30p	
BC167/8/9	11p	2N3823	30p	2A 100V	38p	
BC169C	12p			2A 200V	41p	
BC177/8/9	17p	IN914	3p	2A 400V	48p	
BC182/3/4/L	11p	IN4001	5p	ZENERS BZY88		
BC212/3/4/L	12p	IN4002	6p	2-7-33V	9p	
BCY70	15p	IN4004/5	7p	NE555V	£1-10	
BCY71	22p	IN4148	4p	2N414	60p	
BCY72	12p	0A47	6p	7400	76p	
BFY50/51	16p	0A81	7p	Dalo Pen	10p	
BFX29	30p	0A91	5p	D.I.L. SOCKETS		
BFX84	24p	0A95	5p	8-pin	12p	
BSX19	16p	0A200	6p	14-pin	13p	
BSX20	16p	0A202	7p	16-pin	14p	
OC71	10p			Mica + bushes	TO3 TO86 5p	
2N706	10p			OP. AMPS		
2N1711	20p			748 D.I.L.	36p	
2N2904/6	18p			PRICES INCLUSIVE + 15p P. & P. (1st class)		
2N2904/6A	18p			ISLAND DEVICES, P.O. Box 11, Margate, Kent		
2N2926(F)	7p					

DRY REED INSERTS

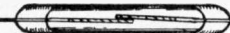

Overall length 1.85" (Body length 1.1"). Diameter 0.14". Max. ratings 250V D.C. and 500 mA. Gold clad normally open contacts. 75p per dozen; £4.12 per 100; £30.25 per 1,000; £275 per 10,000. VAT and post paid.

G.W.M. RADIO LTD.

40/42 Portland Road, Worthing, Sussex 0903 24897

VALVES. Radio, TV, transmitting, industrial 1930 to 1975. Many obsolete. 2,000 types in stock. List 20p. We wish to purchase new and boxed valves, also transistors. COX RADIO (SUSSEX) LTD., The Parade, East Wittering, Sussex. Tel. West Wittering 2023.

REVERB LINES

163" long—Twin Spring—600Ω input. Will drive from 741 I.C.

Phone for more data if required.

Price £6.50 plus £1.65 V.A.T.

P. & P. free in U.K. Cash with order only.

G.P. ELECTRONICS

Pottery Rd., Bovey Tracey, Devon 0626 832670

SITUATIONS VACANT

MEN!
£90 p.w.
can be yours

Jobs galore! Tens of thousands of new computer personnel needed over the next few years alone. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks!

It can pay around £35 p.w. as a starter and can reach over £90 p.w.

After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or 'phone TODAY, without obligation.

London Computer Operators

Training Centre Y37, Oxford Hse.

9-15 Oxford St., W.1. Tel. 01-734 2874

BOOKS AND PUBLICATIONS

THE McCOURT T.V. REPAIR MANUALS MAKE REPAIRS SIMPLE AS A.B.C.

Set out in the easiest to follow style, showing symptom, cause and cure for every common fault and virtually every possible one, for every British standard or portable set plus many foreign. Contained in 4 large manuals, only £12 set or send your model, make and £3.35 for the correct manual by return. Colour manuals £3.35 each, full details from:

T.V. TECHNIC, 76 CHURCH ST., LARKHALL, LANARKS.

EDUCATIONAL

TECHNICAL TRAINING.

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers; also self-build radio kits. Full details from: ICS SCHOOL OF ELECTRONICS, Dept. 316, Intertext House, London, SW8 4UJ. Tel. 01-622 9911 (all hours).

CITY & GUILDS EXAMS.

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from: ICS SCHOOL OF ELECTRONICS, Dept. 315, Intertext House, London, SW8 4UJ. Tel. 01-622 9911 (all hours).

TELEVISION TRAINING

16 MONTHS' full-time practical and theoretical training course in Radio and TV Servicing (Mono and Colour) for beginners.

13 WEEKS' full-time Colour TV Servicing course. Includes 100 hours practical training. Mono revision if necessary. Good electronics background essential.

NEXT SESSION commences on September 15th.

Prospectus from London Electronics College, Dept. A7, 20 Pennywern Road, London SW5 9SU. Tel. 01-373 8721.

COLOUR TV SERVICING.

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from: ICS SCHOOL OF ELECTRONICS, Dept. 317, Intertext House, London, SW8 4UJ. Tel. 01-622 9911 (all hours).

LADDERS

LADDERS, timber and aluminium. Tel. Telford 586644 for brochure.

SERVICE SHEETS

SERVICE SHEETS, radio, TV, etc. 10,000 models. Catalogue 24p plus S.A.E. with orders-enquiries. TELRAY, 154 Brook Street, Preston, PR1 7HP.

FOR SALE

PRACTICAL WIRELESS 1951 to 1972, Radio Constructor 1951 to 1972, Practical Electronics 50 issues. Offers to: JACKSON, 68 Hartforde Road, Boreham Wood, Herts. Tel. 01-953 5057.

WANTED

TOP PRICES PAID
NEW VALVES AND TRANSISTORS
Popular T.V. and Radio types
KENSINGTON SUPPLIES (B)
367 Kensington Street
Bradford 8, Yorks.

MISCELLANEOUS

PCB MANUFACTURERS OFFER: SPECIAL this month, "P.W." Easybuild organ PCBs in Epoxy/fibreglass, roller-tinned and drilled I.P.C. approved, **£5-50** (20p) the set. Also full spec., ready to assemble PCBs for: "P.W." Tricolour, **£1-25** (12p); Tele-tennis (6 PCBs), **£3-50** (15p); Telephone exchange, **£70** (12p); Derby, **70p** (8p). "P.E." ORION with printed layout on PCB, **£1-10** (12p); Power slaves (3 PCBs), **£1-35** (13p); C.C.T.V. (2 PCBs), **£1-40** (15p); Smoke detectors **70p** (12p); Digital leaf, Scorpio 2, ferret locator, all **65p** (9p). C.W.O. P. & P. in brackets. MANY OTHERS available. S.A.E. for lists. PRODUCTION SPACE FOR PCB production, electroplating, silk-screen printing, tinning plus all ART/GRAPHIC photographic and design facilities. Estimates by return or phone. W.K.F. ELECTRONICS, Welbeck Street, Whitwell, Worksop, Notts., S80 4TW. Tel. Whitwell 695 (Derbys). Callers only to 2/3 Station Road.

35 WATT/CHANNEL Stereo Amplifier Chassis

Just needs 50 volt, 2-3 amp power supply. 1 glass fibre P.C.B. board including DIN sockets, etc.

35 WATT RMS @ 4Ω ch.

25 WATT RMS @ 8Ω ch.

Disc 2mv. Aux. 1, Aux. 2, tape 200mv, £38 inc. P. & P. 50p.

P. F. STEVENS ELECTRO-ACOUSTICS
8A CLARENCE ROAD
SOUTH BENFLEET, ESSEX

IC SOCKET PINS for low cost mounting of 8 to 40 pin DILs. 50p (+ 4p VAT) for strip of 100, £1.50 (+ 12p VAT), for 3 x 100, £4 (+ 32p VAT) for 1,000. Instructions included—send S.A.E. for sample. 10p P. & P. for orders under £2. SINTEL, 53b Aston Street, Oxford. Tel. 0865 43203.

THYRISTORS gold bonded BT119 95p, P. & P. 8p. Numerical read out tubes type GN4 95p, P. & P. 7p. B7G bases 3p, P. & P. 7p. 8-pin octal bases 9p, P. & P. 7p. Gen/purpose diodes GEX54 6p, P. & P. 7p. Neons W/ ended 6p, P. & P. 7p. 1000mf 16V 10p, P. & P. 7p. Lead with two female bnc plugs 32p, P. & P. 7p. P/CB B9A ceramic bases 4p, P. & P. 7p. 24V a.c. plug in relay octal base dp/co 75p, P. & P. 27p. 6V miniature relay dp/co ex-equip new 75p, P. & P. 27p. Foot operated switch 3½ x 2½ 95p, P. & P. 35p. 10 damaged TV panels some colour delay lines, etc. and B/W fantastic value at £1-65, P. & P. 60p. 1 panel containing 7 common electrolytic capacitors ex-250mf 50V, etc. and 1 1A bridge rectifier, 8 1A diodes and 7 other devices 75p, P. & P. 35p. Giant switch cleaner in aerosol can 80p, P. & P. 35p. Orders over £10 P. & P. free. Orders for 7p P. & P. over 10 items P. & P. 27p. To: INDUSTRIAL RF SERVICES, 51 Deptford Broadway, London, SE8 4PH. Tel. 01-602 4284.

HOME SCIENTISTS

Get the key to a FANTASTIC WORLD of previously UNHEARD-OF PROJECTS. The NEW Boffin catalogue lists LOTS of HIGHLY UNUSUAL, LOW-COST BARGAINS, READY-BUILT MODULES.

Here are just a few examples, there are stacks more!

Dazzling MINI-STROBE (pocket size) £2-90
 PEOPLE DETECTOR £3-20
 Big-Ear SOUND-CATCHER £3-20
 Mini DREAM LABORATORY £3-20

Don't take our word for it though! GET A COPY AND SEE! SEND ONLY 20p and we'll RUSH you a COPY (YOU'LL GET THE 'GOODIES' JUST AS QUICKLY TOO!)

BOFFIN PROJECTS

4 Cunliffe Road, Stoneleigh
 Ewell, Surrey

(Mail Order U.K. only)

SUPERB INSTRUMENT CASE by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of Radio, Electronic, Hi-Fi enthusiasts and Industrial users are choosing the cases they require from our range. Make your VAT go further with our competitive prices which begin at a low 75p. Examples: Width, Depth, Height, 7" x 7" x 5" £2-65; 8" x 10" x 6" £3-60; 12" x 8" x 7" £4; 12" x 12" x 7" £4-40. Over 200 Models to choose from. Prompt despatch. Free literature (stamp would be appreciated). BAZELLI, Dept. No. 23, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

ULTRASONIC TRANSDUCERS

Suitable for INTRUDER DETECTOR

Practical Electronics, March 1975

Tx/Rx Pair £3-50 + 28p VAT

NEW SE05B-25T/R 25kHz Tx/Rx Pair
 £3-70 + 30p VAT

FIBRE OPTIC SUPPLIERS

2 Loudoun Road Mews, London NW8 0DN

DIFFICULT TO GET AT? Hold that screw with a Slot-Grip screwdriver. Split blade holds screw firmly. Screw can be driven home with same force as standard screwdriver. High quality product. Blade 1in wide 6in long for M3-M4 screws. £1-70 plus 10p P. & P. E. & S., Cranbrook, Laverstock Park, Salisbury, Wilts.

fibre optic suppliers

MARE'S TAILS. Build a decorative display with this professionally finished unit, 22in diameter with 7,000+ fibres. Looks immaculate. £10.00 per metre (£3 per 10m).

FIBROFLEX SIZE 1. Flexible 440 strand glass light conduit, bundle dia. 1-14mm. 40p per metre (£3 per 10m).

FIBROFLEX SIZE 4. 2-20mm bundle dia. £1-50 per metre (£12 per 10m).

CROFON 1610. 64-strand plastic light conduit, bundle dia. 1-8mm, O.D. 3-3mm. £1-20 per metre (£3 per 10m).

PLASTIC OPTICAL MONOFIBRE. For multiple illumination from one source, displays, internal illumination, effects, optical coupling, etc.

FP20 (0-5mm dia.)—80p per 10m; £4 per 100m.
 FP40 (1mm dia.)—£2-20 per 10m; £15 per 100m.
 FP60 (1-5mm dia.)—£4 per 10m; £36 per 100m.

OPTIKIT 103. Contains 2m Crofon 1610 plus 5m each FP20, FP40, FP60 plus polishing compound. A handy pack for the experimenter and laboratory. £4-90.

LENSES AND REFLECTORS. We stock a range of 6 lenses and 5 reflectors for use in proximity detectors, intruder detectors, batch counters, tachometers, short range optical communications.

OPTIKIT L6. 1 each of 6 lenses, £3.

OPTIKIT RR5. 1 each of 5 reflectors, £2-50.

CIRCULAR POLARISERS. Cut that glare. Reduce specular reflection by up to 20x—enhance contrast on CRT, LED displays, mirrors, instruments, etc. Available in red/amber/green/neutral. 50mm square 70p; 75mm £1-40; 150mm £4-50.

LIGHT SOURCES AND DETECTORS: MV54 Miniature (2mm) Red LED, 20p (10 + 17p); MLED500 T092 Red LED, 20p (10 + 17p); MLED22 Infra-Red Emitter, 30p (10 + 25p); XC20R 3mm Red LED, 20p (10 + 17p); XC20R-Y or -G Yellow/Green, 30p (10 + 25p); 2N5777 High Sensitivity Photodarlington Silicon Detector, gain x2,500, 50p (10 + 42p); MFD15 Silicon Photodiode—high speed, 4us good sensitivity, 70p (10 + 47p).

****NEW MLS203.** Latest Motorola Light Activated SCR. High sensitivity 10mW/cm²; high current 400mA (5A peak); 60V. Switch small motors or relay direct from optical control, up to 24W power. £1-20 (10 + 17p).

SE05B-40T/R ULTRASONIC TRANSDUCER PAIR. Suitable for "Ultrasonic Doppler Shift Intruder Detector", Practical Electronics, March 1975. Tx/Rx pair £3-50.

SE05B-25T/R ULTRASONIC TRANSDUCER PAIR. ** NEW ** The SE05B-40T/R has proved to be an extremely popular item in our range and we are therefore introducing the 25kHz version. Although bandwidth is less at >500Hz, sensitivity is better by 10dB. Suitable for burglar alarm systems, proximity switches, counters, level meters, anti-collision devices. 25kHz Tx/Rx pair £3-70.

Please add 8% VAT to prices above (plus 22p on orders less than £3). Send 9in x 6in S.A.E. for short form list.

FIBRE OPTIC SUPPLIERS

(Dept. PE), 2 Loudoun Road Mews

London NW8 0DN

(Please note change of address)

PRINTED CIRCUIT COPPER GLAD.

Single sided. Quality material. Flame retardant to N.E.M.A. Spec. Paper Base (FR2) ½ x 7 x 5, 3 for £1. Epoxy Glass (FR4) ½ x 7 x 5, 2 for £1. Also panels cut to your requirements, quotation by return. Prices include P. & P. Cash with Order.

P. G. OLIVER & CO.

4 Hearsall Lane, Coventry, CV5 6HH.

CLEARING LABORATORY, scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.

SINTEL

Add 10p P. & P. for orders under £2. Data and circuit where appropriate, supplied with orders or available separately (send 9in x 4in S.A.E.). ADD 8% VAT—Not 25%

DISPLAYS		CLOCK ICs—PCBs—KIT	
DL7M(Econ)	0-3in CC 10-85	MK8089N Alarm	£3-80
DL707	0-3in CA 11-70	PCBs, sht. for above	£2-45
DL737	0-9in CA 12-45	PCB for x DL704	£1-35
N9N33	3 x 0-12in CC 11-85	8 dig Alarm Cl. Kit	£16-55
MAN3M	0-12in CC 10-40	(test case, sws, trfmr, LS)	£4-25
FMD500	0-25in CC 11-15		
SOLDERCON	Pin 100 for 80p, 400-£2, 1,000-£4, 3,000-£10-50		
CMOS from RCA and MOTOROLA			
CD4001AE	£8-21	CD4023AE	£9-21
CD4011AE	£8-21	CD4042AE	£1-37
CD4012AE	£8-21	CD4049AE	£9-28
CD4013AE	£8-63	CD4050AE	£8-62
CD4018AE	£8-62	CD4082AE	£1-17
CD4019AE	£8-73	MC14501CP	£8-32
CD4022AE	£1-89	CD4089BE	£1-56
		MC14510CP	£1-77
		MC14518CP	£1-87

Other displays, ICs, RCA CMOS, Relators, etc. available send S.A.E. or phone (8.30 to 7p.m.) for further information
 SINTEL, 53B ASTON STREET, OXFORD. Tel. (0865) 43203

GLASS FIBRE P.C.B.s for all projects. Drilled and tinned. Send master print and 30p per board plus 5p per square inch. ELECTRO CIRCUITS, 4 Highcliffe Way, Wickford, Essex.

BE PROUD OF YOUR WORK AND BUILD IT IN A BEC (Book End Chassis)

PUNCHING SERVICE IF REQ'D.



GB1	14 x 6 x 2 1/2 in
GB1A	9 x 6 x 2 1/2 in
GB2	14 x 7 x 3 in
GB3	14 x 9 x 4 1/2 in
GB4	14 x 9 x 6 in

A beautifully designed modern cabinet with simulated black leatherette top (PVC bonded to metal)



The PE ORION HI-FI STEREO AMPLIFIER uses our GB1 Bec cabinet (illustrated in Jan. 1975, Practical Electronics). Can be supplied punched or unpunched.

Please send 15p for folder of leaflets (refundable).
H.M. ELECTRONICS (PE), 275a Fulwood Road, Sheffield S10 3BD (Behind Broomhill P.O.)

4 x 741 (8 DIL) £1

13 x BC108 EQUIV. IN PLASTIC CASE (BC148) £1. 30 x IN4148 G.P. DIODES £1.

FULL SPEC. DEVICES. PRICES INCLUDE 25% VAT. P. & P. 20p. ON ORDERS UNDER £3.

SCOTT ELECTRONICS (Dept. P.E.)
 P.O. Box 42, Wembley, Middx.

HARDWARE. Comprehensive range of screws, nuts, washers, etc. in small quantities, and many useful constructors' items. Sheet aluminium to individual requirements, punched, drilled, etc. Fascia panels, dials, nameplates in etched aluminium. Printed circuit boards for this magazine, and other individual requirements, one-off's and small runs. Machine engraving in metals and plastics, contour milling. Send 2 4½ stamps for catalogue. **RAMAR CONSTRUCTOR SERVICES, Masons Road, Stratford on Avon, Warwick, CV37 9NF.**

12 VOLT 21w 13 watt FLUORESCENT LIGHTING (by THORN/AEL)

with diffuser and on/off switch. Ideal, caravan, boat, emergency lighting, etc.

£5-50

inc. VAT and post. List price £7-02 inc. VAT.

SALOP ELECTRONICS Tel. 53206
 23 Wyle Cop. Shrewsbury, Shropshire

LOW COST I.C. MOUNTING. 100 I.C. pin sockets 50p. Quantity rates. S.A.E. details and sample. 7 and 8 hole plastic supports 5p/pair. (P. & P. 8p/order). LED (MLED500) 20p each post free. Quantity rates. P.K.G. ELECTRONICS, Oak Lodge, Tansley, Derbyshire, DE4 5FE.

I.C. EXPERIMENTER'S KITS

Learn about modern electronics with our new step-by-step kits. Use and understand digital logic techniques. Kits contain specially selected I.C.'s, Holders, Veroboard, L.E.D.'s, instructions and data. Kit One (Gates) and Kit Two (Flip-Flops) now available, £2-90 each. P. & P. 10p. Bargain Offer—EXPERIMENTER'S PAK £2-90 Gates, Inverters, Flip Flops, Counters P. & P. 10p S.A.E. for further details to: **AUTOMATED HOMES, 69 High St., RYTON, Coventry CV8 3FJ.** (Mail Order Only)

ENAMELLED COPPER WIRE

S.W.G.	1/8 Reel	1/2 Reel
10-14	£2-05	£1-15
15-19	£2-15	£1-20
20-24	£2-20	£1-25
25-29	£2-25	£1-30
30-34	£2-35	£1-38
35-40	£2-50	£1-45

All the above prices are inclusive in U.K.

COPPER SUPPLIES

102 PARRSWOOD RD., WICHINGTON, MANCHESTER 20
 Telephone 061-445 8753

BUILD THE TREASURE TRACER MK III Metal Locator

- Varicap tuning
- Britain's best selling metal locator kit
- Fitted with Faraday shield
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- As seen on BBC-1 and BBC-2 TV

Send stamped, addressed envelope for leaflet

Complete kit £10-90
 Post 60p - 92p VAT (8%)

Built and tested £15-25
 Post 60p - £1-27 VAT (8%)

MINIKITS ELECTRONICS, 6g CLEVELAND ROAD LONDON E18 2AN (Mail Order Only)

DIGITAL CLOCK CHIP, AY-5-1224, with data and circuit diagram, **£3.66** plus VAT. "Jumbo" LED digits (16 mm high), Economy type. DL-747, only **£2.04** each plus VAT, post free. GREENBANK ELECTRONICS, 94 New Chester Road, Wirral, Merseyside, L62 5AG.

P. HOLROYD
(Engineering)

Supplier of Alum. & Steel
BOXES CONSOLES
CASES & HOUSINGS

Standard & Made to Order
GENERAL METALWORK

Write for details:

7 Nursery Road • Salisbury
Wiltshire Tel. (0722) 23120

BUDGET MINI AUDIO MIXERS

With Professional Facilities.
Slider Faders ★ Tone Controls ★
Monitoring ★ V.U. Meter.
Mono or Stereo ★ Ready to use or
Kits.

Details Ref. PE:

PARTRIDGE ELECTRONICS
21-25 Hart Road, Benfleet, Essex.

LIGHTING CONTROL UNITS

3 x 1kW per channel sound-to-light converter using isolated control circuitry for maximum safety. The unit comes in kit or ready built form and features individual sensitivity controls, sensitivity range switch and dimming switch. (Bypass controls as an optional extra.) Kit: £13.99. Ready built: £16.99

Details of dimmers, sequencers and other lighting control units available on request.
Mail order or written enquiries only to:

SELEKTRON

21 Prior's Road, Windsor, Berks. SL4 4PD


HIGH QUALITY INSTRUMENT CASES

Size: 7½ x 4½ x 2½in

MODERN STYLE PANEL METERS

100µA

Size: 4½ x 3½in

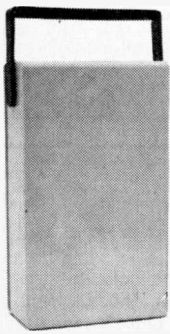

Price **£1.98**

Plus 16p VAT

Price **£4.45**

Plus 36p VAT

P. & P. 20p

GIVE YOUR INSTRUMENTS QUALITY AT LOW COST

METAC

Cross Lane, Braunston
Daventry, Northants.

FANTASTIC NEW MICROTEST 80

MEASURES ONLY


90 x 70 x 18mm
ELECTRONIC ZERO Ω



Amazing Value at £11.95
8 fields of measurement
and 40 ranges

PRINTED CIRCUIT BOARD IS REMOVABLE WITHOUT SOLDERING

Volts d.c. 6 ranges: 100mV, 2V, 10V, 50V, 200V, 1,000V (20kΩ/V), 2% precision on d.c. and a.c.
Volts a.c. 5 ranges: 1.5V, 10V, 50V, 250V, 1,000V (4kΩ/V).
Amp. d.c. 6 ranges: 50µA, 500µA, 5mA, 50mA, 500mA, 5A
Amp. a.c. 5 ranges: 250µA, 2.5mA, 25mA, 250mA, 2.5A
Ohms 4 ranges: Low Ω, Ω x 1, Ω x 10, Ω x 100 (from 1/10 Ω to 5MΩ)
V Output 5 ranges: 1.5V, 10V, 50V, 250V, 1,000V.
Decibels 5 ranges: +6dB, +22dB, +36dB, +50dB, +62dB.
Capacity 4 ranges: 25pF, 250pF, 2.500pF, 25,000pF.

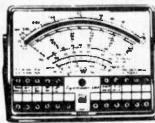

SUPERTESTER 680R ICE

20,000 Ohm per Volt sensitivity
Fully screened against external magnetic fields
Scale width and small case dimensions (128 x 95 x 32mm)
Accuracy and stability (1% in D.C., 2% in A.C.) of indicated reading
Simplicity and ease of use and readability
Full ranges of accessories

1,000 times overload
Printed circuit board is removable without de-soldering
More ranges than any other meter. Ask for free catalogue.
Accessories (extra) available to convert Microtest 80 and Supertester 680R into following: LIGHTMETER, GAUSS METER, ELECTRONIC VOLTMETER, AMPER-CLAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR, Ω x 100kΩ Multiplier, SIGNAL INJECTOR—Send for details.

£18.50
Accessories Extra

MORE RANGES FOR LESS MONEY!


AC/DC Multimeter type U4324

A-DC 0.06-3A-6 Ranges
A-AC 0.3-3A-5 Ranges
V-DC 0.6-1200 V-9 Ranges
V-AC 3-900 V-8 Ranges
Frequency in the range of 45 to 20kHz. Resistance: 500 ohm to 5 Mohm—5 ranges. Decibel: -10 to +12dB. Accuracy: ±2.5%. DC +4% AC. Dimensions: 167 x 98 x 63mm.
Only **£9.25**



ALPHANUMERIC NIXIE TUBES B7971

The Alphanumeric NIXIE tube has the ability to display all the letters of the alphabet, numerals 0 thru 9 and special characters in a single tube. From the standpoint of both readability and electrical characteristics, the Alphanumeric NIXIE tube provides many unique benefits including: * 170V-21mA * All d.c. operation * Uniform, continuous line characters of equal height * Memory with simple solid state drive circuits * Readability in high ambient light * 200 footlamberts brightness * Long life with no loss of brightness * Character height 2½in.

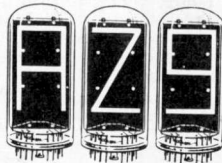

Bases for above 60p each.

Price only **99p** each plus 16p P.P.

JUST ARRIVED! !

NUMERIC INDICATOR TUBES

Ultra-long life, high quality, 0-9 and 2 independent decimal points. Supply voltage 200V d.c. Current 14mA. Pulse duration 100µs. Character height 0.51, overall size 1.4.

Brand new, guaranteed. Surplus to manufacturer's requirements. Type B5853at

1-25 **£1.00**; 25+ **90p**; 100+ **80p**;
1,000+ price on application.

Add 8% VAT to all items + 35p P. & P.
ELECTRONIC BROKERS LTD.
49-53 Pancras Road, London NW1 2QB
Tel. 01-837 7781

ARROW

ELECTRONICS LTD.
DEPT. PE13
7 COPTFOLD ROAD
BRENTWOOD, ESSEX

★ **ULTRASONICS** ★

40kHz transducers at low price as used in many magazine articles. Price includes suggested circuits, order as RL400PP per pair £4.58 VAT inclusive.

CA3035—I.C.

3 amplifier array—129DB. Ideal for use in RL400PP transducer receiver. Price £1.78, VAT inclusive. Data only 17p.

COS—MOS LOGIC

NEW LOW PRICES

CD4000AE	0-27	CD4025AE	0-27
CD4001AE	0-27	CD4026AE	2-21
CD4002AE	0-27	CD4027AE	1-03
CD4007AE	0-27	CD4028AE	1-59
CD4009AE	0-85	CD4029AE	2-21
CD4010AE	0-77	CD4030AE	0-77
CD4011AE	0-27	CD4035AE	1-85
CD4012AE	0-27	CD4040AE	2-11
CD4013AE	0-71	CD4042AE	1-56
CD4014AE	1-83	CD4043AE	2-29
CD4015AE	1-83	CD4044AE	2-29
CD4016AE	0-71	CD4046AE	2-29
CD4017AE	1-85	CD4049AE	0-27
CD4018AE	2-59	CD4050AE	0-71
CD4019AE	0-84	CD4051AE	2-92
CD4020AE	2-06	CD4056AE	1-83
CD4022AE	1-92	CD4069AE	0-27
CD4023AE	0-27		
CD4024AE	1-32	Data only 11p	

All prices include VAT

ALSO

AC128	0-22	MC1310P	2-86
AC176	0-26	NE555V	0-63
AD161	0-51	ORP12	0-56
AD162	0-51	TBA810S	1-29
BC107	0-12	TIL200	0-14
BC108	0-12	ZTX309	0-15
BC109	0-12	ZTX500	0-15
BC109C	0-21	2N2926	0-12
BC182	0-14	all colours	
BC212	0-17	2N3055	0-48
BFY51	0-26	2N3702	0-15
BZY88	0-11	741/BDIL	0-33
series		40673	0-68

IMPORTANT. All prices include VAT. No hidden extras.

ARROW SERVICE PLUS

COMPREHENSIVE LIST
NO HIDDEN EXTRAS. TOP
QUALITY PRODUCTS BY RETURN

I enclose PO/Cheque for 20p

Name

Address

Arrow Electronics Limited
Dept. PE13

7 Coptfold Road, Brentwood, Essex.

TTL 74 I.C.s				Popular Op Amps		MFC4000		Zero Voltage Switch		5314 Clock Chip 24-pin DIL 650p				
7400	13p	7441	65p	7485	120p	709	OPA with ext comp	30p	MFC6040	Zero Voltage Switch	90p	Alarm Clock Chip 40-pin		
7401	14p	7442	60p	7486	30p	710	Diff comparator	35p	MFC8070	FET Op Amp	250p	DIL (similar MMS316)	750p	
7402	14p	7447	75p	7489	270p	741	OPA with int comp (8 pin DIL)	25p	NE536	PLL with AM Demod 16-pin	325p	5001 12 Digit Calculator		
7403	18p	7448	70p	7490	40p	747	Dual 741	70p	NE555	PLL with VCO 16-pin	325p	Chip 28-pin DIL	485p	
7404	16p	7449	15p	7491	75p	748	OPA with ext comp	30p	NE560	PLL FM IF Demod 16-pin DIL	300p	(All above supplied with basic data; data separately 25p each + S.A.E.)		
7405	16p	7451	18p	7492	45p	LINEAR I.C.s		Data sheets on above I.C.s 10p each + S.A.E.		PC Keyboard (0-9, decimal, 4 function, C, K, keys), Size 2-36" x 3-76" x 0-45" 400p				
7406	18p	7453	18p	7493	40p	CA3046	Transistor Array	50p	NE561	PLL 14-pin DIL	325p			
7407	13p	7454	16p	7494	48p	CA3048	4 independent Amplifiers	230p	NE562	PLL with VCO 16-pin	325p			
7410	13p	7470	27p	7495	85p	CA3038	VCO Fun. Gen. 14-pin DIL	275p	NE563	PLL FM IF Demod 16-pin DIL	300p			
7413	35p	7472	25p	7496	78p	LM301A	Op. Amp with ext. comp.	36p	NE565	PLL 14-pin DIL	325p			
7414	60p	7473	30p	7497	30p	LM380	Audio Amplifier	90p	NE566	Function Generator 8-pin DIL	250p			
7416	33p	7473	30p	74107	30p	LM381	Stereo Pre Amp	150p	NE567	PLL Tone Decoder 8-pin DIL	250p			
7420	14p	7474	30p	74121	30p	LM3900	Quad Op Amp	70p	TBA570	AM/FM Radio receiver	160p			
7422	25p	7475	45p	74141	65p	MC1310	Colex FM Stereo Dec.	210p	TBA800	5 Watt Audio Amp.	90p			
7425	30p	7476	30p	74142	250p	MC1312	SQ Quadrasonic Dec.	220p	TBA810	7 Watt Audio Amp.	100p			
7427	37p	7480	50p	74154	150p	MC1314	SQ Quadrasonic Dec.	400p	TA820	2 Watt Audio Amp.	80p			
7430	14p	7481	95p	74164	120p	MC1315	SQ Quadrasonic Dec.	475p	ZN414	TRF Radio Receiver	110p			
7432	25p	7482	70p	74192	120p	VOLTAGE REGULATORS (PLASTIC)		SCR-THYRISTORS		TRIACS 100V 400V 500V				
7437	25p	7483	80p	74193	120p	723	1 Amp + Ve -Ve	7905 250p	1A 50V 100V 400V 600V	Other	3A 85p 95p 120p			
7440	14p	7484	95p			14-pin DIL 45p	5V 7805 140p	7912 250p	1A 40p 42p 50p 70p 2N3525	91p	6A 88p 120p 150p			
DIL Sockets by Texas				Data sheets on val reg's 10p each.		15V 7815 140p	7915 250p	16A 250p 84p	2N5060 33p	15A 145p 180p 200p	Other 40430 99p, 40486 95p, 40669 99p.			
8-pin 12p; 14-pin 13p; 16-pin 14p.						18V 7818 140p	7924 250p	Other	2N5062 45p					
Mica - 2 bushes for TO3 and TO6 5p.						24V 7824 140p		BT106 140p, C106D 45p, MCR101 25p, 2N5064 48p						
BR100—BI-DIRECTIONAL TRIGGER FOR SCRS AND TRIACS. 21p.														
Transistors			Diodes			ZENERS			C-MOS LOGIC I.C.s			OPTO-ELECTRONICS		
AC126 7	11p	BC213 10p	OC35 48p	2N2219 2	20p	50p	85p	OA202 7p	IN914 4p	3.3V to 33V	CD4000AE 19p	ORP12 50p	OCPT70 30p	
AC128 11p	BD115 55p	OC41 2	15p	2N2369 14p	UJTS	25p	BY126 12p	IN4001 5p	400mW 9p	CD4001AE 19p	ORP60 60p	OCPT1 90p		
AC176 11p	BD124 75p	OC44 5	11p	2N2484 30p	TIS43	25p	BY127 12p	IN4004 6p	1.3W 18p	CD4002AE 19p	ORP61 60p	2N5777 40p		
AC187 12p	BD131 42p	OC70 1 2	11p	2N2904 20p	2N2160	70p	OA47 7p	IN4007 7p		CD4009AE 67p	LEDS			
AC188 11p	BD132 45p	OC73 6	60p	2N2905 18p	2N2846	35p	OA70 8p	IN4148 4p	Tunnel	CD4011AE 21p	TL209 with clip 16p.			
AD149 43p	BF115 22p	OC81 2	12p	2N2926B 8p	2N4871	30p	OA79 8p	OTHER	AEY11 50p	CD4013AE 55p	Green/Yellow with clip 35p.			
AD161 36p	BF167 23p	OC83 4	28p	2N2958 8p	FETS		OA79 7p	BA145 15p	Varicap	CD4016AE 120p	SEVEN SEGMENT DISPLAYS			
AD162 36p	BF173 25p	TIP2955 70p	2N2956V 9p	BF244 36p	MPP102.3	28p	OA81 7p	BA148 13p	BB105 30p	CD4022AE 189p	3015F 0-35in DIL 120p			
AF114 5	13p	BF184 22p	TIP41A 65p	2N3053 18p	MPP104.5	28p	OA85 9p	BA148 13p		CD4023AE 19p	LIT704 0-33in DIL 130p			
AF136 7	13p	BF194 9p	TIP42A 70p	2N3054 45p	MPP104.5	28p	OA90 6p	BA148 13p		CD4024AE 120p	LIT747 0-63in DIL 225p			
AF139 30p	BF195 9p	ZTX300 12p	2N3055 50p	MPP102.3	MPP104.5	28p	OA91 6p	BA148 13p		CD4027AE 91p	MAN-3M 0-127in PCB 120p			
AF239 44p	BF196 11p	ZTX500 15p	2N3055 50p	MPP104.5	MPP104.5	28p	OA95 7p	LED		CD4028AE 140p	MAN-4 0-19in DIL 180p			
BC107 8	9p	BF197 12p	ZTX108 8p	2N3702.3 11p	2N3819 22p		OA200 6p	TIL209 15p	ZJ 75p	CD4028AE 175p	NEW VAT RATES			
BC109 C	9p	BF199 28p	2N697 13p	2N3704.5 11p	2N3820 57p		BRIDGE RECTIFIERS			CD4046AE 154p	25% on Transistors, Diodes, Bridges, Op Amps, and Radio, Audio and T.V.I.C.s			
BC117 8	7p	BF179 28p	2N698 30p	2N3706 7p	2N3823 50p		0-25A	50V 100V 400V 600V		CD4047AE 196p	8% on all others, e.g. T.L.C.s			
BC149 9p	BFX29 30	30p	2N706 12p	2N3708 9p	2N5457 28p		1A	22p 24p 27p 29p		CD4054AE 229p	C-MOS V.R.s. S.C.R.s.			
BC157 10p	BFX8 5 6	25p	2N708 18p	2N3772 161p	2N5458 28p		2A	30p 35p 45p 48p		CD4071AE 26p	Triacs, Opto and many linear I.C.s			
BC158 9p	BFY50 1 2	15p	2N730 18p	2N3773 220p	2N5459 26p		4A	55p		CD4081AE 120p				
BC159 10p	BFY50 1 2	15p	2N1131 2	18p	2N3903/4 15p		6A	55p 60p		CD4510AE 120p				
BC169C 12p	BRV39 34p	2N1302.3 17p	2N3905 6 15p	15p	2N4058 15p					CD4511AE 236p				
BC177 18p	MJE340 45p	2N1304 5 21p	2N4058 15p	15p	MOSFETS					CD4528AE 120p				
BC178 12p	MJE2955 99p	2N1306 7 28p	2N4060 13p	40603 58p										
BC179 18p	MJE3055 65p	2N1308 9 28p	2N4289 18p	40673 58p										
BC182 3	MPSU06 58p	2N1613 20p	40361 40p	3N128 75p										
BC184 11p	OC28 47p	2N1711 20p	40362 43p	3N140 85p										
BC212 11p	OC28 55p	2N1893 27p	40594 75p	3N141 75p										

Minimum order £2. P. & P. 20p. MAIL ORDER ONLY. Government, colleges, etc., orders welcome. **TECHNOMATIC LTD** 54 Sandhurst Road, London NW9. Tel. 01-204 4333

SYNTHESISER

Modules by Dewtron®



The synthesiser illustrated was built using Dewtron modules, as sold to constructors for some years now. With over 10 years' experience in mail-order, we have supplied many famous people and groups. Over 30 types of synthesis modules, some of extremely precision design, e.g. VCO-2 log-law oscillator; 3-wave o/p/s; sample/hold/envelope module; pitch-to-voltage module allowing a whole equipment to "play itself" in unison/harmony with any solo input or voice. Modules for sequencer construction, too. Famous "Modumatrix" patching system makes other patching a thing of the past! Send just 20p for full catalogue to:

D.E.W. LTD.

254 Ringwood Road, Ferndown
Dorset BH22 9AR

SCOTT ELECTRONICS

ESTCOURT HOUSE, ESTCOURT ROAD
GREAT YARMOUTH, NORFOLK
Tel. Great Yarmouth 57066

5W Chassis Stereo Amplifier (2.5W/CH). Power requirements: 12V d.c. Output: 2.5W/CH into 8 ohms. Two inputs: tape head (3mV) and 100mV min./P.U. with suitable external components. Controls: volume, balance and tone (slider controls). £4 plus 25% VAT

12V d.c. Solenoids (short duration), 2in x 1in x 1in approx.: 55p inc. VAT

12V Miniature Lamps fitted with flying leads. Pack of 10: 60p inc. VAT

8 Track Car Stereo Players, 12V negative earth: £14 plus 25% VAT

Decade Resistance Box 0-111kΩ in 0.1 ohm steps. £38 plus 8% VAT

All prices include postage and packing.
All goods supplied are new and guaranteed

TUAC

Important Announcement

Prices quoted in our June advertisement included 25% V.A.T. V.A.T. should be 8%. When ordering, the following prices apply: Disco Mix £31.50; 3 Channel Light Modulator £15.50, Single Channel version £7.25; Power Modules—TP125 £19.50, TL30 £7.90, TL60 £12.50, TL100 £15.00; Preamplifiers—VAO8 £5.75, VAO6 £5.00, SVAO1 £10.00; PS125 £12.25, PS100 £11.25, PS60 £10.00, PS30 £5.90, PSU2 £4.75.

TUAC
163 Mitcham Road, London SW17 9PG
01-672 3137/9080

FREE!

Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

Find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it today and we'll send you full details and a free book. We have successfully trained thousands of men at home—equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost home study course gets results fast—makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained, a view echoed by two colleagues who recently commenced the course."—Student D.I.B., Yorks.
 "Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects."—Student J.A.O., Dublin.
 "My training quickly changed my earning capacity and, in the next few years, my earnings increased fourfold."—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters, and there are many more on file at Aldermaston College, speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to:

ALDERMASTON COLLEGE

Dept. TPE07, Reading RG7 4PF

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.

This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!



CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

<input type="checkbox"/> ELECTRICAL ENGINEERING City & Guilds Wiring and Installations C & G Electrical Tech—Primary Gen. Electrical Eng	<input type="checkbox"/> RADIO & TV Gen. Radio and TV Eng Radio Servicing, Maintenance and Repairs <input type="checkbox"/> Practical Radio & Electronics (with self-build kit) Radio Amateurs Exam.	<input type="checkbox"/> General Draughtsmanship <input type="checkbox"/> Architectural Draughtsmanship <input type="checkbox"/> Technical Drawing
<input type="checkbox"/> AERONAUTICAL ENGINEERING Air Registration Board Certificates (Gen. Aero Engineering)	<input type="checkbox"/> ELECTRONIC ENGINEERING Gen. Electronic Eng <input type="checkbox"/> Practical Electronics (with kit)	<input type="checkbox"/> CONSTRUCTION & BUILDING Institute of Building Construction Surveyor's Inst Clerk of Works Diploma C & G Building Quantities General Building General Civil Eng Heating, Ventilation & Air Conditioning Carpentry & Joinery Painting & Decorating Plumbing C.E.I. (Part 1) Inst. Cost & Management Accountants Works Management
<input type="checkbox"/> AUTO ENGINEERING City & Guilds Auto Engineering Practice Inst. Motor Industry M.A.A.T.M.I. Management Diploma Gen. Auto Engineering Auto Diesel Maintenance Motor Mechanics Service Station and Garage Management	<input type="checkbox"/> AGRICULTURAL ENG. REFRIGERATOR SERVICING	<input type="checkbox"/> MECHANICAL ENGINEERING Society of Engineers Inst. Engineers and Technicians General Mechanical Eng Welding Maintenance Eng General Diesel Eng
<input type="checkbox"/> TELE-COMMUNICATIONS City & Guilds Telecommunications	<input type="checkbox"/> DRAUGHTSMANSHIP Institute of Engineering Draughtsmen & Designers	<input type="checkbox"/> G.C.E. —58 'O' & 'A' Level Subjects—over 10,000 Group Passes!

POST TODAY FOR A BETTER TOMORROW

To Aldermaston College, TPE07
Dept. TPE07, Reading RG7 4PF

Also at our London Advisory Office, 4 Fore St Avenue, Moorgate, London EC2Y 5EJ Tel 01-628 2721

NAME _____
Block Capitals Please
ADDRESS _____

OTHER SUBJECTS _____ POST CODE _____

AGE _____
Accredited by C.A.C.C. Member of A.B.C.C.

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, EC4A 4AD. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/sia) Ltd., South Africa—Central News Agency Ltd. Publisher's Subscription Rate including postage for one year. Inland £4.80, Overseas £5.00, U.S.A. and Canada \$13.50. International Giro facilities Account No. 5122007. Please state reason for payment. "message to payee" Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eric where the selling price is subject to V.A.T., and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

More than just a catalogue

Projects for you to build.

4-digit clock, 6-digit clock, 10W high quality power amp., High quality stereo pre-amp., Stereo Tuner, F.M. Stereo decoder, etc., etc. . . .

CIRCUITS Frequency Doublers, Oscillators, Timers, Voltmeters, Power Supplies, Amplifiers, Capacitance Multiplier, etc., etc. . . .


Full details and pictures of our wide range of components, e.g. capacitors, cases, knobs, veroboards, edge connectors, plugs and sockets, lamps and lampholders, audio leads, adaptor plugs, rotary and slide potentiometers, presets, relays, resistors (even 1% types!), switches, interlocking pushbutton switches, pot cores, transformers, cable and wire, panel meters, nuts and bolts, tools, organ components, keyboards, L.E.D.'s, 7-segment displays, heatsinks, transistors, diodes, integrated circuits, etc., etc., etc. . . .

REALLY GOOD VALUE FOR MONEY AT JUST 40p.

**MAPLIN
ELECTRONIC
SUPPLIES**

**SUPERSONIC
SAME-DAY-SERVICE
QUALITY COMPONENTS
-FAST!**

ELECTRONIC ORGAN

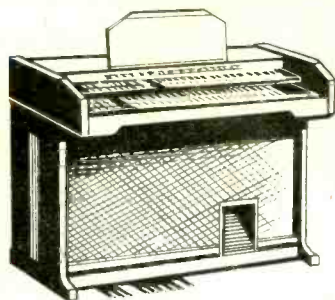

Build yourself an exciting Electronic Organ. Our leaflet MES51, price 15p, deals with the basic theory of electronic organs and describes the construction of a simple 49-note instrument with a single keyboard and a limited number of stops.

Leaflet MES52, price 15p, describes the extension of the organ to two keyboards each with five voices and the extension by an octave of the organ's range.

Solid-state switching and new footages along with a pedal board and a further extension of the organ's range are shown in leaflet MES53, also priced at 15p.

No more doubts about prices

Now our prices are GUARANTEED (changes in VAT excluded) for two month periods—and we'll tell you about price changes in advance for just 30p a year (refunded on purchases). If you already have our catalogue send us an S.A.E. and we'll send you our latest list of GUARANTEED prices. Send us 30p and we'll put you on our mailing list—you'll receive immediately our latest price list then every two months from the starting date shown on that list you'll receive details of our prices for the next GUARANTEED period before the prices are implemented!—plus details of any new lines, special offers, interesting projects—and clip-off coupons to spend on components to repay your 30p when used as directed.

NOTE: The price list is based on the Order Codes shown in our catalogue so an investment in our super catalogue is an essential first step.

Call in at our shop, 284 London Road, Westcliff-on-Sea, Essex. Please address all mail to P.O. Box 3, Rayleigh, Essex, SS6 8LR.

SYNTHESISER



A reprint of the complete article giving full construction details published by "Electronics Today International" between January-September '74 of the International Voltage Controlled Synthesiser, developed as a "state of the art", will be available shortly, price £1.50. S.A.E. please for detailed price list.

GRAPHIC EQUALISER



A really superior high quality stereo graphic equaliser as described in the January edition of "Electronics Today International". We stock all the parts (except woodwork) including the metalwork drilled and printed. 15p brings you a reprint of the article or a S.A.E. please for our detailed price list.

MAPLIN

**ELECTRONIC
SUPPLIES**

P.O. Box 3 Rayleigh Essex SS6 8LR.
Telephone: Southend-on-Sea (0702) 44101